

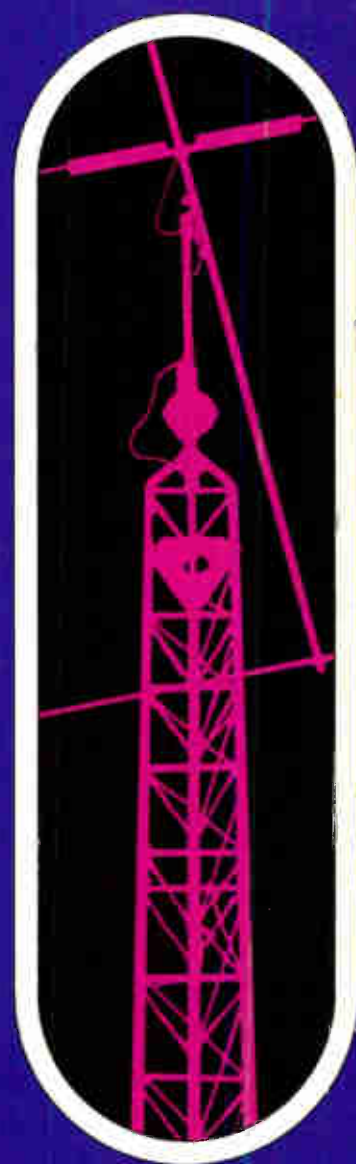
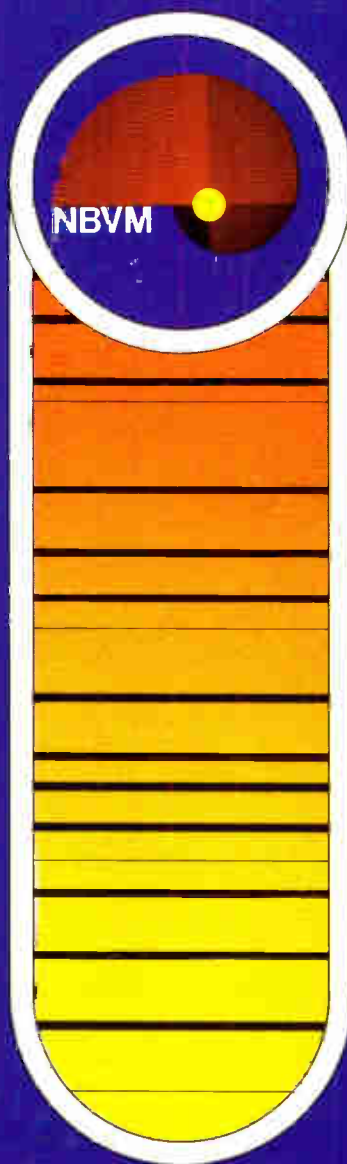


3975  
© 1978  
ARRL  
USA

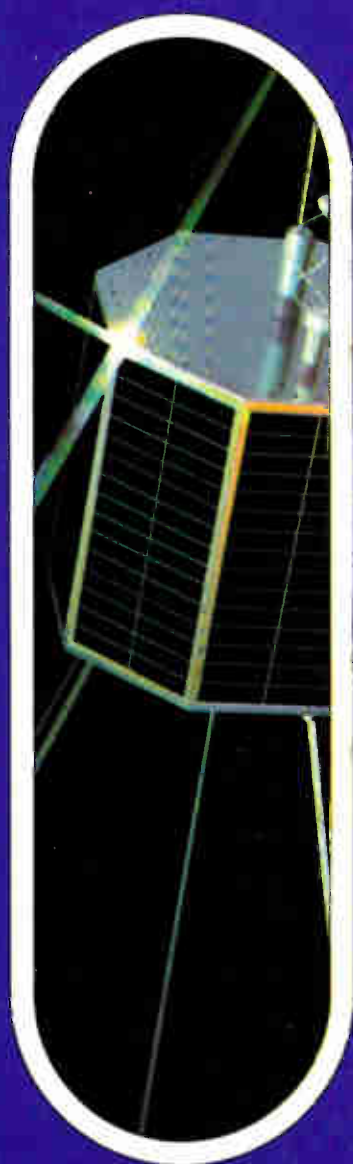

# 1979 THE RADIO AMATEUR'S HANDBOOK

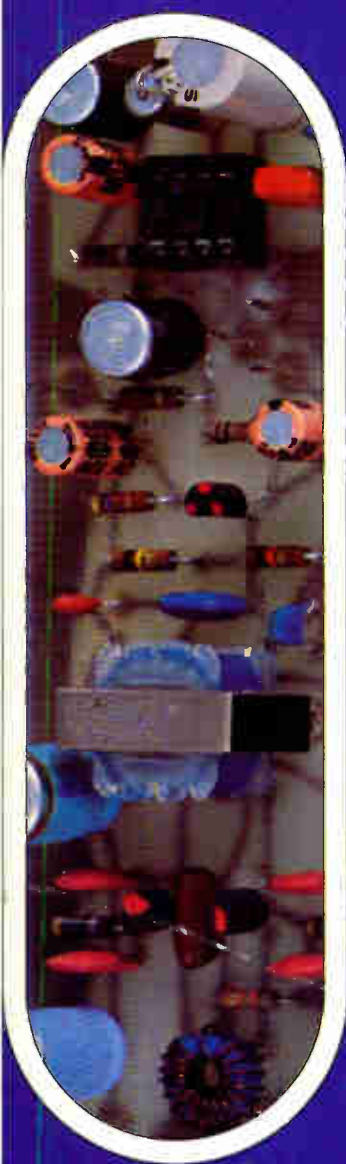

PUBLISHED BY THE AMERICAN RADIO RELAY LEAGUE



# The Radio Amateur's Handbook

By the HEADQUARTERS STAFF  
of the  
**AMERICAN RADIO RELAY LEAGUE**  
NEWINGTON, CONN., U.S.A. 06111

*Editor*

Doug DeMaw, W1FB

*Assistant Editors*

Marian S. Anderson, WB1FSB

Clarke Greene, K1JX

Jay Rusgrove, W1VD

*Contributors*

Charles Bender, W1WPR

Jean DeMaw, W1CKK

Tom Frenaye, K1KI

Bob Halprin, K1XA

George Hart, W1NJM

Stan Horzempa, WA1LOU

Bill Jennings, K1WJ

Jim Kearman, W1XZ

Joel Kleinman, WA1ZUY

Jim LaPorta, N1CC

Jim Morris, K1UJ

Don Search, W3AZD

Bob Shriner, WA0UZO

Ellen White, W1YL

Perry Williams, W1UED



## 1979

Fifty-Sixth Edition

**Copyright © 1978 by**

**The American Radio Relay League, Inc.**

**Copyright secured under the Pan-American Convention**

**International Copyright secured ©**

**This work is publication No. 6 of the Radio Amateur's Library, published by the League. All rights reserved. No part of this work may be reproduced in any form except by written permission of the publisher. All rights of translation are reserved.**

**Printed in U.S.A.**

***Quedan reservados todos los derechos***

***Library of Congress Catalog Card Number: 41-3345  
Fifty-Sixth Edition***

**\$9.75 in the U.S.A. and Possessions,  
\$10.75 in Canada, \$12.00 elsewhere.**

**Clothbound edition \$15.75 in the U.S.A and Possessions, \$18.00 in Canada and elsewhere.**



# Foreword

The new, larger format of this, the 56th edition of *The Radio Amateur's Handbook*, will make both casual perusal and serious research a pleasant experience. But we're most proud of the content of this 1979 *Handbook*. Many chapters have been extensively revised to reflect the present state of the art. One is totally new: "Narrow-Band Voice Modulation," an exciting new Amateur Radio development that promises to revolutionize voice communications. New photographs and clear, precise schematic drawings add to the book's usefulness.


As with all ARRL publications, we have structured this *Handbook* to appeal to all licensed amateurs, whatever aspects of the hobby they happen to be involved in. Even persons who have yet to experience the excitement of Amateur Radio will find it helpful. It will also be an important part of any technical library, amateur or professional, as in years past. This book is bound to become an Amateur Radio classic. Once you begin to delve inside it, that fact will become readily apparent.

Richard L. Baldwin, W1RU


*General Manager*

Newington, Conn.  
November 1978
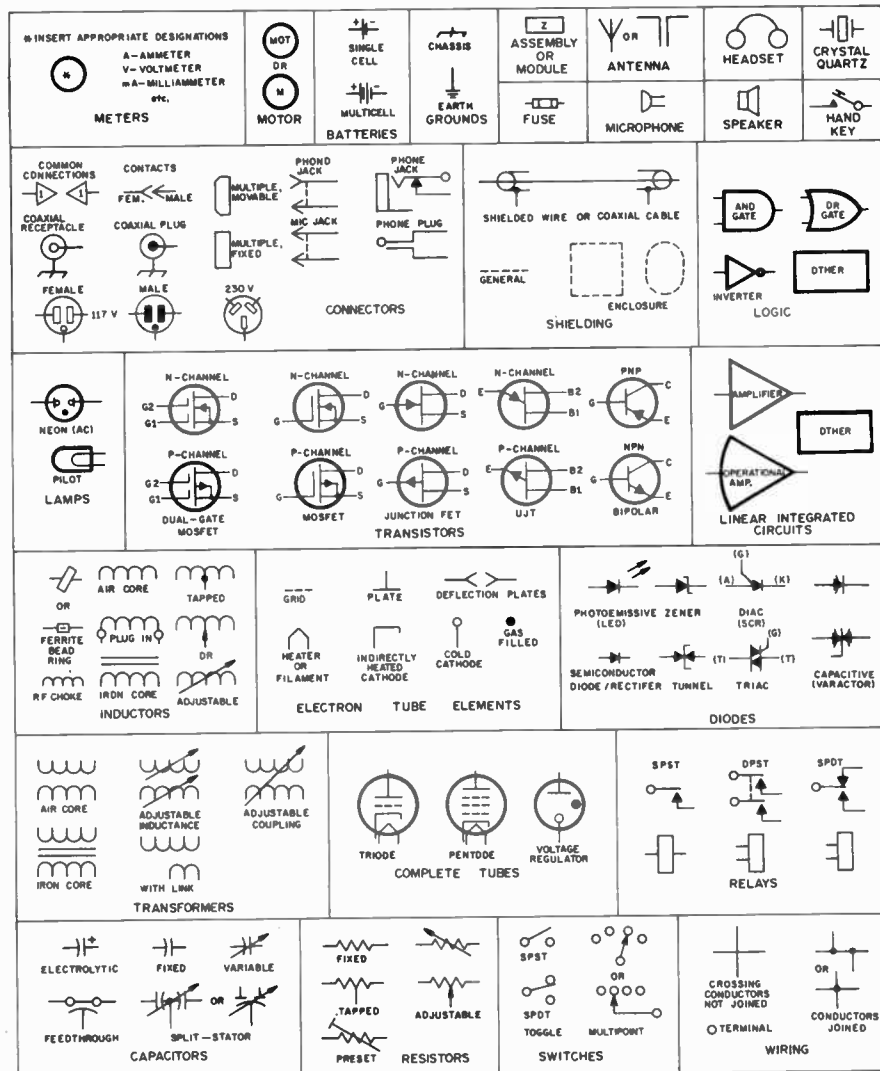
# Schematic Symbols Used in Circuit Diagrams



# Contents

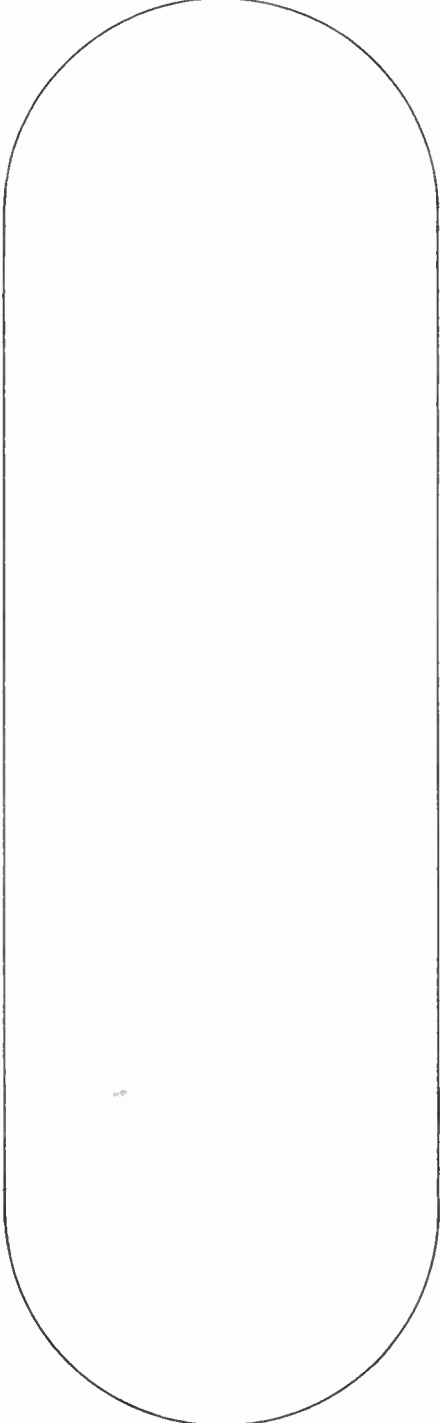- 
- 1 **Amateur Radio**
  - 2 **Electrical Laws and Circuits**
  - 3 **Radio Design Technique and Language**
  - 4 **Solid-State Fundamentals**
  - 5 **AC-Operated Power Supplies**
  - 6 **HF-Transmitting**
  - 7 **VHF and UHF Transmitting**
  - 8 **Receiving Systems**
  - 9 **VHF and UHF Receiving Techniques**
  - 10 **Mobile, Portable and Emergency  
Equipment**
  - 11 **Code Transmission**
  - 12 **Single-Sideband Transmission**
  - 13 **Frequency Modulation and Repeaters**
  - 14 **Narrow-Band Voice Modulation**
  - 15 **Interference with other Services**
  - 16 **Test Equipment and Measurements**
  - 17 **Construction Practices and Data Tables**
  - 18 **Wave Propagation**
  - 19 **Transmission Lines**
  - 20 **Antennas for High Frequency**
  - 21 **VHF and UHF Antennas**
  - 22 **Operating a Station**

# The Amateur's Code

## **ONE**

***The Amateur is Considerate*** . . . He never knowingly uses the air in such a way as to lessen the pleasure of others.

## **TWO**

***The Amateur is Loyal*** . . . He offers his loyalty, encouragement and support to his fellow radio amateurs, his local club and to the American Radio Relay League, through which Amateur Radio is represented.

## **THREE**

***The Amateur is Progressive*** . . . He keeps his station abreast of science. It is well-built and efficient. His operating practice is above reproach.

## **FOUR**

***The Amateur is Friendly*** . . . Slow and patient sending when requested, friendly advice and counsel to the beginner, kindly assistance, cooperation and consideration for the interests of others; these are marks of the amateur spirit.

## **FIVE**


***The Amateur is Balanced*** . . . Radio is his hobby. He never allows it to interfere with any of the duties he owes to his home, his job, his school, or his community.

## **SIX**

***The Amateur is Patriotic*** . . . His knowledge and his station are always ready for the service of his country and his community.

— PAUL M. SEGAL

# Amateur Radio

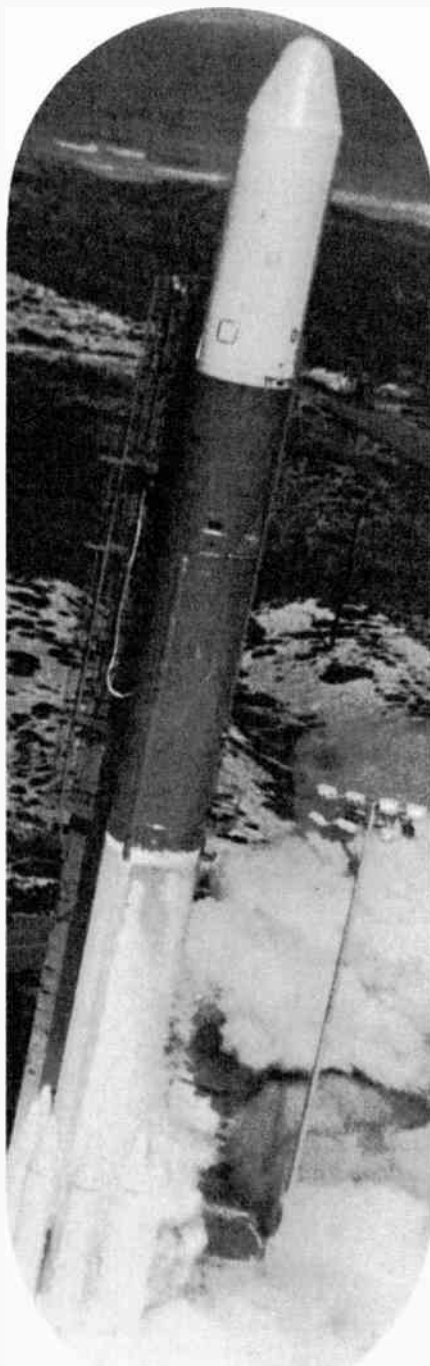

**A**mateur Radio. You've heard of it. You probably know that amateur radio operators are also called "hams." (Nobody knows quite why!) But who are these people and what do they do?

Every minute of every hour of every day, 365 days a year, radio amateurs all over the world communicate with each other. It's a way of discovering new friends while experimenting with different and exciting new ways to advance the art of their hobby. Ham radio is a global fraternity of people with common and yet widely varying interests, able to exchange ideas and learn more about each other with each new on-the-air contact. Because of this Amateur Radio has the ability to enhance international relations as does no other hobby. How else is it possible to talk to an engineer involved in a space program, a Tokyo businessman, a U.S. legislator, a Manhattan store owner, a camper in a Canadian national park, the head of state of a Mediterranean-area country, a student at a high school radio club in Wyoming, or a sailor on board a ship in the middle of the Pacific? And all without leaving your home! Only with amateur radio — that's how!

The way communication is accomplished is just as interesting as the people you get to "meet." Signals can be sent around the world using reflective layers of the earth's ionosphere or beamed from point to point from mountaintops by relay stations. Orbiting satellites that hams built are used to achieve communication. Still other hams bounce their signals off the moon! The possibilities are almost unlimited. Not only do radio amateurs use international Morse code and voice for communication, but they also use radioteletype, facsimile and various forms of television. Some hams even have computers hooked up to their equipment. As new techniques and modes

The continuous achievements of the Amateur Radio Service are symbolized by these photos, of Hiram Percy Maxim, inventor of the Maxim Silencers, pioneer radio amateur and cofounder, with Clarence Tuska in 1914, of the ARRL; and of the Thor-Delta space vehicle, launching OSCAR 8, the latest Orbiting Satellite Carrying Amateur Radio in 1978.



of communication are developed, hams continue their long tradition of being among the first to use them.

What's in the future? Digital voice-encoding techniques? Three-dimensional TV? One can only guess. But if there is ever such a thing as a Star Trek transporter unit, hams will probably have them!


Once radio amateurs make sure that their gear does work, they look for things to do with the equipment and special skills they possess. Public service is a very large and integral part of the whole Amateur Radio Service. Hams continue this tradition by becoming involved and sponsoring various activities in their community.

Field Day, just one of many public service-type activities, is an annual event occurring every June when amateurs take their equipment into the great outdoors (using electricity generated at the operation site) and test it for use in case of disaster. Not only do they test their equipment, but they make a contest out of the exercise and try to contact as many other hams operating emergency-type stations as possible (along with "ordinary" types). Often they make Field Day a club social event while they are operating.

Traffic nets (networks) meet on the airwaves on a schedule for the purpose of handling routine messages for people all over the country and in other countries where such third-party traffic is permitted. By doing so, amateurs stay in practice for handling messages should any real emergency or disaster occur which would require operating skill to move messages efficiently. Nets also meet because the members often have common interests: similar jobs, interests in different languages, different hobbies (yes, some people have hobbies other than ham radio!), and a whole barrelful of other reasons. It is often a way to improve one's knowledge and to share experiences with other amateurs for the good of all involved.

DX (distance) contests are popular and awards are actively sought by many amateurs. This armchair travel is one of the more alluring activities of amateur radio. There are awards for Worked All States (WAS), Worked All Provinces (WAVE), Worked All Continents (WAC), Worked 100 Countries (DXCC), and many others.

Mobile operation (especially on the very high frequencies) holds a special attraction to many hams. It's always fun to keep in touch with ham friends over the local repeater (devices which receive your signal and retransmit it for better coverage of the area) or finding new friends on other frequencies while driving across the country. Mobile units are often the vital link in emergency communications, too, since they are usually first on the scene of an accident or disaster.

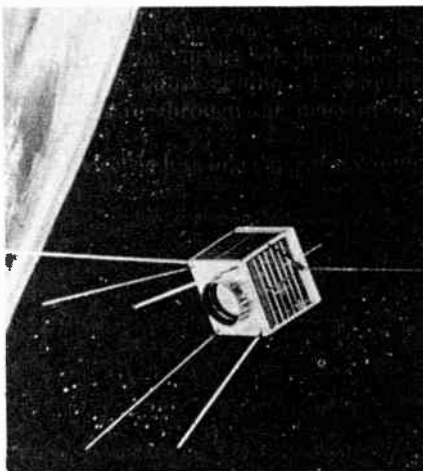

Hurting through the airless reaches of space, OSCAR 8 is a relay station for amateurs around the world. It provides reliable vhf and uhf communications, and is the focus of a wide range of experiments that advance the radio art.

The *OSCAR* (Orbiting Satellite Carrying Amateur Radio) program is a relatively new challenge for the amateur radio fraternity. Built by hams from many countries around the world, these ingenious devices hitch rides as secondary payloads on space shots for commercial and government communications or weather satellites. OSCAR satellites then receive signals from the ground on one frequency and convert those signals to another frequency to be sent back down to earth. Vhf (very high frequency) and uhf (ultra-high frequency) signals normally do not have a range much greater than the horizon, but when beamed to these satellites, a vhf/uhf signal's effective range is greatly increased to make global communication a possibility. These OSCAR satellites also send back telemetry signals either in Morse or radioteleprinter (RTTY) code, constantly giving information on the condition of equipment aboard the satellite.

Self-reliance has always been a trademark of the radio amateur. This is often best displayed by the many hams who design and build their own equipment. Many others prefer to build their equipment from kits. The main point is that hams want to know how their equipment functions, what to do with it and how to fix it if a malfunction should occur. Repair shops aren't always open during hurricanes or floods and they aren't always out in the middle of the Amazon jungle, either. Hams often come up with variations on a circuit design in common use so that they may achieve a special function, or a totally original electronic design may be brought out by a ham, all in the interest of advancing the radio art.

#### Radio Clubs

Amateur Radio clubs often provide social as well as operational and technical activities. The fun provided by amateur

radio is greatly enhanced when hams get together so they can "eyeball" (see) each other. It's a good supplement to talking to each other over the radio. The swapping of tales (and sometimes equipment), and a general feeling of high spirits add a bit of spice to club meetings along with technical matters on the agenda. Clubs offer many people their first contact with amateur radio by setting up displays in shopping centers and at such events as county fairs, Scout jamborees and parades.

Nearly half of all U.S. amateurs belong to a radio club. And nearly every amateur radio club is affiliated with the ARRL. Club affiliation is available to most organized amateur radio groups. The benefits are many: Use of films and slide shows for club classes and meetings, a quarterly club newsletter, rebate on ARRL membership dues, special publication offers, and other services. Complete information on the requirements and privileges of affiliation is available from the Club and Training Department, ARRL hq., Newington, CT 06111.

#### Getting Started in Amateur Radio?

"All of this sounds very interesting and seems to be a lot of fun, but just how do I go about getting into this hobby? Don't you almost need a degree in electronics to pass the test and get a license?"

Nothing could be further from the truth. Although you are required to have a license to operate a station, it only takes a minimal amount of study and effort on your part to pass the basic, entry-grade exam and get on the air.

"But what about the code? Don't I have to know code to get a license?" Yes, you do. International agreements require amateur radio operators to have the ability to communicate in international Morse code. But the speed at which you are required to receive it is relatively low so you should have no difficulty. Many grade-school students have passed their tests and each month hundreds of people from 8 to 80 join the ever-growing number of amateur radio operators around the world.

Concerning the written exam: To get a license you need to know some basic electrical and radio principles and regulations governing the class of license applied for. The ARRL's basic beginner package, *Tune in the World with Ham Radio*, is available for \$7 from local radio stores or by mail from ARRL.

#### Finding Help

One of the first obstacles for a person seriously interested in amateur radio is finding a local amateur to provide assistance. This volunteer amateur is called an "Elmer." A nearby ham can help a newcomer with technical advice, putting up and testing antennas, advice on buying that first radio or just some needed encouragement. Also, nearly all would-be amateurs attend an amateur radio class

for code, regulations and electronic theory instruction. Where do you find this assistance? The ARRL Club and Training Department helps the prospective amateur in every possible way. It coordinates the work of more than 5000 volunteer amateur radio instructors throughout the United States and Canada and provides a large variety of audio-visual aids and refers inquiries on amateur radio to one of the 5000 instructors. If you are looking for an amateur radio class or advice on how to get started, write the ARRL Club and Training Department for the name and address of the nearest Elmer.

### Looking Back

How did amateur radio become the almost unlimited hobby it is today? The beginnings are slightly obscure, but electrical experimenters around the turn of the century, inspired by the experiments of Marconi and others of the time, began duplicating those experiments and attempted to communicate among themselves. There were no regulatory agencies at that time and much interference was caused by these "amateur" experimenters to other stations until governments the world over stepped in and established licensing, laws and regulations to control the problems involved in this new technology. "Amateur" experimenter stations were then restricted to the "useless" wavelengths of 200 meters and below. Amateurs suddenly found that they could achieve communication over longer distances than commercial stations on the longer wavelengths. Even so, signals often had to be relayed by intermediate amateur stations to get a message to the proper destination. Because of this, the American Radio Relay League was organized to establish routes of amateur radio communication and serve the public interest through amateur radio. But the dream of eventual transcontinental and even transoceanic amateur radio contact burned hot in the minds of radio amateur experimenters.

World War I broke out and amateur radio, still in its infancy, was ordered out of existence until further notice. Many former amateur radio operators joined the armed services and served with distinction as radio operators, finding their skills to be much needed.

After the close of the "War to End All Wars," amateur radio was still banned by law; yet there were many hundreds of formerly licensed amateurs just itching to "get back on the air." The government had tasted supreme authority over the radio services and was half inclined to keep it. Hiram Percy Maxim, one of the founders of the American Radio Relay League, called the pre-war League's officers together and then contacted all the old members who could be found in an attempt to re-establish amateur radio.



Whether it's a week at a lakeside cottage or to the ends of the earth, where hams go amateur radio will often go as well. Japanese explorer Naomi Uemura, JG1QFW, used amateur radio for backup emergency communications during his solo trek to the North Pole in 1978.

Maxim traveled to Washington, DC and after considerable effort (and untold red tape) amateur radio was opened up again on October 1, 1919.

Experiments on shorter wavelengths were then begun with encouraging results. It was found that as the wavelength dropped (i.e., frequency increased) greater distances were achieved. The commercial stations were not about to miss out on this opportunity. They moved their stations to the new shorter wavelengths while the battle raged over who had the right to transmit in this new area. Usually, it turned out to be the station with the stronger signal able to blot out everyone else.

National and international conferences were called in the twenties to straighten out the tangle of wavelength allocations. Through the efforts of ARRL officials, amateurs obtained frequencies on various bands similar to what we have today: 160 through 6 meters. When the amateur operators moved to 20 meters, the dream of coast-to-coast and transoceanic communication without a relay station was finally realized. (A more detailed history of the early days of amateur radio is contained in the ARRL publication *Two Hundred Meters and Down* by Clinton B. DeSoto.)

### Public Service

Amateur radio is a grand and glorious hobby, but this fact alone would hardly merit the wholehearted support given it by nearly all the world's governments at international conferences. There are other reasons. One of these is a thorough appreciation of the value of amateurs as sources of skilled radio personnel in time of war. Another asset is best described as "public service."

The "public service" record of the amateur is a brilliant tribute to his work. These activities can be roughly divided into two classes, expeditions and emergencies. Amateur cooperation with expeditions began in 1923 when a League member, Don Mix, ITS, accompanied MacMillan to the Arctic on the schooner *Bowdoin* with an amateur station. Amateurs in Canada and the U.S. provided the home contacts. The success of this venture was so outstanding that other explorers followed suit. During subsequent years amateur radio assisted perhaps 200 voyages and expeditions, the several explorations of the Antarctic being perhaps the best known. And this kind of work is not all in the distant past, either: In 1978 Japanese explorer Naomi Uemura, JG1QFW, became the first person to trek to the North Pole alone. Amateur radio, through member stations of the National Capitol DX Association and the Polar Amateur Radio Club, VE8RCS, at Alert, NWT, Canada, provided important backup communications.

Sometimes Mother Nature goes on a rampage — with earthquakes such as those in Alaska in 1964, Peru in 1970, California in 1971, Guatemala and Italy in 1976; floods like those in Pennsylvania and New York in 1972, Big Thompson Canyon, Colorado, in 1976, Kentucky, Virginia, West Virginia, and Johnstown, Pennsylvania in 1977; the big forest fires of California, particularly in 1977; tornadoes, hurricanes and typhoons, most anywhere, any year, and the blizzards of 1978. When disaster strikes, amateurs are ready, with equipment not needing power from the electric company, to carry on communications for police, fire departments, and relief organizations. The ability of radio amateurs to help the



public in emergencies is one big reason amateur radio has survived and prospered.

### Technical Developments

Amateurs started the hobby with spark-gap transmitters, which took up great hunks of frequency space. Then they moved on to tubes when these devices came along. Much later, transistors were utilized; now integrated circuits are a part of the everyday hardware in the amateur radio shack. This is because the amateur is constantly in the forefront of technical progress. His incessant curiosity and eagerness to try anything new are two reasons. Another is that ever-growing amateur radio continually overcrowds its frequency assignments, spurring amateurs to the development and adoption of new techniques to permit the accommodation of more stations.

Amateurs have come up with ideas in their shacks while at home and then taken them to industry with surprising results. During World War II, thousands of skilled amateurs contributed their knowledge to the development of secret radio devices, both in government and private laboratories. Equally as important, the prewar technical progress by amateurs provided the keystone for the development of modern military com-

munications equipment.

In the fifties, the Air Force was faced with converting its long range communications from Morse to voice; jet bombers had no room for skilled radio operators. At the time, amateurs had been using single sideband for about a decade, and were communicating by voice at great distances with both homemade and commercially built equipment. Generals LeMay and Griswold, both radio amateurs, hatched an experiment in which ham equipment was used to keep in touch with Strategic Air Command headquarters in Omaha, Nebraska, from an airplane travelling around the world. The system worked well, the equipment needed only slight modification to meet Air Force needs, and the expense and time of normal research and development procedures was saved.

Many youngsters build an early interest in amateur radio into a career. Later, as professionals, they may run into ideas which they try out in ham radio. A good example is the OSCAR series of satellites, initially put together by amateurs who worked in the aerospace industry and launched as secondary payloads with other space shots. At this writing there have been eight satellites in the series. OSCARs 7 and 8, portions of which were built by amateurs of several different

countries, are currently in space relaying the signals of amateurs. OSCARs 7 and 8 can be heard on almost any 29-MHz receiver. Operation of OSCAR 8 is coordinated by ARRL; write us for more information. Development of "third-generation" satellites proceeds under the guidance of The Radio Amateur Satellite Corporation (AMSAT) with the assistance of Project OSCAR, Inc., the original nonprofit group, both affiliated with ARRL.

### The American Radio Relay League

Since its establishment in 1914 by Hiram Percy Maxim and Clarence Tuska, the American Radio Relay League has been and is today not only the spokesman for amateur radio in the U.S. and Canada, but the largest amateur organization in the world. It is strictly of, by and for amateurs, is noncommercial and has no stockholders. The members of the League are the owners of the ARRL and *QST*, the monthly journal of amateur radio published by the League.

The League is pledged to promote interest in two-way amateur communication and experimentation. It is interested in the relaying of messages by amateur radio. It is concerned with the advancement of the radio art. It stands for the maintenance of fraternalism and a

Table 1

#### Canadian Amateur Bands

Band (Limitations)	Frequency-MHz	Emissions
80 meters (1, 3, 4, 5)	3.500- 3.725	A1, F1
	3.725- 4.000	A1, A3, F3
40 meters (1, 3, 4, 5)	7.000- 7.150	A1, F1
	7.150- 7.300	A1, A3, F3
20 meters (1, 3, 4, 5)	14.000- 14.100	A1, F1
	14.100- 14.350	A1, A3, F3
15 meters (1, 3, 4, 5)	21.000- 21.100	A1, F1
	21.100- 21.450	A1, A3, F3
10 meters (2, 3, 4, 5)	28.000- 28.100	A1, F1
	28.100- 29.700	A1, A3, F3
6 meters (3, 4)	50.000- 50.050	A1
	50.050- 51.000	A1, A2, A3, F1, F2, F3
	51.000- 54.000	A0, A1, A2, A3, A4, F1, F2, F3, F4
2 meters (3, 4)	144.000- 144.100	A1
	144.100- 148.000	A0, A1, A2, A3, A4, F1, F2, F3, F4
1-1/4 meters (3, 4)	220.000- 225.000	A0, A1, A2, A3, A4, F1, F2, F3, F4
(4, 6)	420.000- 450.000	
	1215.000- 1300.000	
	2300.000- 2450.000	
	3300.000- 3500.000	A0, A1, A2, A3,
	5650.000- 5925.000	A4, A5, F1, F2,
	10000.000-10500.000	F3, F4
	24000.000-24250.000	

#### Limitations

1) Phone privileges are restricted to holders of Advanced Amateur Radio Operator Certificates, and of Commercial Certificates.

2) Phone privileges are restricted as in footnote 1, and to holders of Amateur Radio Operators Certificates, whose certificates have been endorsed for operation on phone in these bands.

3) Amplitude modulation (A2, A3, A4) shall not exceed  $\pm 3$  kHz (6A3).

4) Frequency modulation (F2, F3, F4) shall not produce a carrier deviation exceeding  $\pm 3$  kHz, (6F3) except that in the 52-54 MHz and 146-148 MHz bands and higher the carrier deviation shall not exceed  $\pm 15$  kHz (30F3).

5) Slow scan television (A5), permitted by special authorization, shall not exceed a bandwidth greater than that occupied by a normal single-sideband voice transmission.

6) Television (A5), permitted by special authorization, shall employ a system of standard interlace and scanning with a bandwidth of not more than 4 MHz.

Operation in frequency band 1.800-2.000 MHz shall be limited to the area as indicated in the following table and shall be limited to the indicated maximum dc power input to the anode of the final radio frequency stage of the transmitter during day and night hours respectively; for the purpose of this table "day" means the hours between sunrise and sunset, and "night" means the hours between sunset and sunrise. A1, A3 and F3 emissions are permitted.

	A	B	C	D	E	F	G	H
British Columbia	3'	3	3	1	0	0	0	0
Alberta	3'	3	3	3	1	0	0	1
Saskatchewan	3'	3	3	3	3	1	1	3
Manitoba	3'	2	2	2	2	2	2	3'
Ontario	3	1	1	1	1	0	0	2
North of 50°N.								
Ontario	3'	2	1	0	0	0	0	1
South of 50°N.								
Province of Quebec	1	0	0	1	1	0	0	2
North of 52°N.								
Province of Quebec	3	2	1	0	0	0	0	0
South of 52°N.								
New Brunswick	3	2	1	0	0	0	0	0
Nova Scotia	3	2	1	0	0	0	0	0
Prince Edward Island	3	2	1	0	0	0	0	0
Newfoundland (Island)	3	1	1	0	0	0	0	0
Newfoundland (Labrador)	2	0	0	0	0	0	0	0
Yukon Territory	3'	3	3	1	0	0	0	0
District of MacKenzie	3'	3	3	3	1	0	0	1
District of Keewatin	3	1	1	3	2	0	0	2
District of Franklin	0	0	0	0	1	0	0	1

\*The power levels 500 day — 100 night may be increased to 1000 day — 200 night when authorized by a Radio Inspector of the Department of Communications.

#### Frequency Band

A	1.800-1.825 MHz	E	1.900-1.925 MHz
B	1.825-1.850 MHz	F	1.925-1.950 MHz
C	1.850-1.875 MHz	G	1.950-1.975 MHz
D	1.875-1.900 MHz	H	1.975-2.000 MHz

#### Power Level — Watts

0	— Operation not permitted
1	— 25 night 125 day
2	— 50 night 250 day
3	— 100 night 500 day

high standard of conduct. It represents the amateur in legislative matters.

One of the League's principal purposes is to keep amateur activities so well conducted that the amateur will continue to justify his existence. Amateur radio offers its followers countless pleasures and unending satisfaction. It also calls for the shouldering of responsibilities — the maintenance of high standards, a cooperative loyalty to the traditions of amateur radio, a dedication to its ideals and principles — so that the institution of amateur radio may continue to operate "in the public interest, convenience and necessity."

In addition to publishing *QST*, the

ARRL maintains an active amateur radio station, WIAW, which conducts code practice and sends bulletins of interest to amateurs the world over. ARRL sponsors an Intruder Watch Program so that unauthorized use of the amateur radio frequencies may be detected and appropriate action taken. At the headquarters of the League in Newington, Connecticut, is a well-equipped laboratory to assist staff members in preparation of technical material for *QST* and *The Radio Amateur's Handbook*. Among its other activities, the League maintains a Communications Department concerned with the operating activities of League members. A large field organization is

headed by a section communications manager in each of the League's 74 sections. There are appointments for qualified members in various fields, as outlined in chapter 22. Special activities and contests promote operating skill. A special place is reserved each month in *QST* for amateur news from every section.

The ARRL publishes a virtual library of information on amateur radio. *Tune in the World with Ham Radio* is written for the person without previous contact with amateur radio. It is designed to assist the prospective amateur to get into the hobby in the shortest possible time. *Tune in the World* comes complete with a code instruction and practice tape. For the

**Table 2**  
**U.S. Amateur Radio Frequency Allocations**

Frequency Band	Emissions	Limitations	Frequency Band	Emissions	Limitations	Frequency Band	Emissions	Limitations
<i>kHz</i>								
1800-2000	A1, A3	1, 2	28.000-29.700	A1			A4, A5, F0, F1, F2, F3, F4, F5, P	5, 8
3500-4000	A1		28.000-28.500	F1		3300-3500	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 12
3500-3775	F1		28.500-29.700	A3, F3, A5, F5				
3775-3890	A5, F5		50.000-54.000	A1		5650-5925	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 9
3775-4000	A3, F3	4	50.100-54.000	A2, A3, A4, A5				
4383.8	A3J/A3A	13		F1, F2, F3, F5				
7000-7300	A1	3, 4	51.000-54.000	A0		<i>GHz</i>		
7000-7150	F1	3, 4	144-148	A1		10.0-10.5	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5	5
7075-7100	A3, F3	11	144.100-148.000	A0, A2, A3, A4, A5, F0, F1, F2, F3, F5		24.0-24.25	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	5, 10
7150-7225	A5, F5	3, 4			5	48-50, 71-76	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
7150-7300	A3, F3	3, 4			5, 7	165-170, 240-250		
14000-14350	A1		220-225	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5		Above 300	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5, P	
14000-14200	F1							
14200-14275	A5, F5		420-450	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5				
14200-14350	A3, F3							
<i>MHz</i>								
21.000-21.450	A1		1215-1300	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5				
21.000-21.250	F1							
21.250-21.350	A5, F5		2300-2450	A0, A1, A2, A3, A4, A5, F0, F1, F2, F3, F4, F5				
21.250-21.450	A3, F3							

**Limitations**

1) The use of frequencies in this band is on a shared basis with the Loran-A radionavigation system and is subject to cancellation or revision, in whole or in part, by order of the Commission, without hearing, whenever the Commission shall determine such action is necessary in view of the priority of Loran-A radionavigation system. The use of these frequencies by amateur stations shall not cause harmful interference to Loran-A system. If an amateur station causes such interference, operation on the frequencies involved must cease if so directed by the Commission.

2) Operation shall be limited to [the subbands and input powers in watts shown on page 6.]

3) Where, in adjacent regions or subregions, a band of frequencies is allocated to different services of the same category, the basic principle is the equality of right to operate. Accordingly, the stations of each service in one region or subregion must operate so as not to cause harmful interference to services in the other regions or subregions (No. 117, the Radio Regulations, Geneva, 1959).

4) 3900-4000 kHz and 7100-7300 kHz are not available in the following U.S. possessions: Baker, Canton, Enderbury, Guam, Howland, Jarvis, Palmyra, American Samoa and Wake Islands.

5) Amateur stations shall not cause interference to the Government radio-location service.

6) (Reserved)

7) In the following areas dc plate input power to the final transmitter stage shall not exceed 50 watts, except when authorized by the appropriate Commission engineer in charge and the appropriate

military area frequency coordinator.

i) Those portions of Texas and New Mexico bounded by latitude 33°24' N., 33°53' N., and longitude 105°40' W. and 106°40' W.

ii) The state of Florida, including the Key West area and the areas enclosed within circles of 200-mile radius centered at 28°21' N., 80°43' W. and 30°30' N., 86°30' W.

iii) The state of Arizona.

iv) Those portions of California and Nevada south of latitude 37°10' N. and the area within a 200-mile radius of 34°09' N., 119°11' W.

8) No protection in the band 2400-2450 MHz is afforded from interference due to the operation of industrial, scientific and medical devices on 2450 MHz.

9) No protection in the band 5725-5875 is afforded from interference due to the operation of industrial, scientific and medical devices on 5800 MHz.

10) No protection in the band 24.00-24.25 GHz is afforded from interference due to the operation of industrial, scientific and medical devices on 24.125 GHz.

11) The use of A3 and F3 in this band is limited to amateur radio stations located outside Region 2.

12) Amateur stations shall not cause interference to the Fixed-Satellite Service operating in the band 3400-3500 MHz

13) The frequency 4383.8 kHz, maximum power 150 watts, may be used by any station authorized under this part of communications with any other station authorized in the state of Alaska for emergency communications. No airborne operations

will be permitted on this frequency. Additionally, all stations operating on this frequency must be located in or within 50 nautical miles of the state of Alaska.

14) All amateur frequency bands above 29.5 MHz are available for repeater operation except 50.0-52.0 MHz, 144.0-144.5 MHz, 145.5-146.0 MHz, 220.0-220.5 MHz, 431.0-433.0 MHz, and 435.0-438.0 MHz. Both the input (receiving) and output (transmitting) frequencies of a station in repeater operation shall be frequencies available for repeater operation.

15) All amateur frequency bands above 220.5 MHz, except 431-433 MHz, and 435-438 MHz, are available for auxiliary operation.

**NOTE**

The types of emission referred to in the amateur rules are as follows:

- Type A0 — Steady, unmodulated pure carrier.
- Type A1 — Telegraphy on pure continuous waves.
- Type A2 — Amplitude tone-modulated telegraphy.
- Type A3 — A-m telephony including single and double sideband, with full, reduced or suppressed carrier.
- Type A4 — Facsimile.
- Type A5 — Television.
- Type F0 — Steady, unmodulated pure carrier.
- Type F1 — Carrier-shift telegraphy.
- Type F2 — Audio frequency-shift telegraphy.
- Type F3 — Frequency- or phase-modulated telephony.
- Type F4 — Fm facsimile.
- Type F5 — Fm television.
- Type P — Pulse emissions.

person seeking the General class or higher license, there are the *License Manual* and the *ARRL Code Kit*. All are available from either local radio stores or the ARRL.

Once you have studied, taken the test

and have received your license, you will find that there is no other thrill quite the same as amateur radio. You may decide to operate on the lowest amateur band, 160 meters (see map). Or you may prefer

to operate in the gigahertz bands (billions of cycles per second) where the entire future of communications may lie. Whatever your interest, you are sure to find it in amateur radio.

### U.S. 160-METER ALLOCATIONS



**Input Power (Watts)**

- 0 No operation, day or night
- 1 100 day, 25 night
- 2 200 day, 50 night
- 3 500 day, 100 night
- 4 1000 day, 200 night
- 5 125 day, 25 night
- 6 250 day, 50 night

**Segments (kHz)**

- A 1800-1825
- B 1825-1850†
- C 1850-1875
- D 1875-1900
- E 1900-1925
- F 1925-1950
- G 1950-1975
- H 1975-2000

†The range 1825-1830 kHz is used by DX stations attempting to contact North American stations. Use of this "DX Window" should be avoided by stations on this continent.

# Electrical Laws and Circuits

Some of the manifestations of electricity and magnetism are familiar to everyone. The effects of static electricity on a dry, wintry day, an attraction by the magnetic north pole to a compass needle, and the propagation and reception of radio waves are just a few examples. Less easily recognized as being electrical in nature perhaps, the radiation of light and even radiant heat from a stove are governed by the same physical laws that describe a signal from a TV station or an amateur transmitter. The ability to transmit electrical energy through space without any reliance on matter that might be in that space (such as in a vacuum) or the creation of a disturbance in space that can produce a force are topics that are classified under the study of *electromagnetic fields*. Knowledge of the properties and definitions of fields is important in understanding such devices as transmission lines, antennas, and circuit-construction practices such as shielding.

Once a field problem is solved, it is often possible to use the results over and over again for other purposes. The field solution can be used to derive numerical formulas for such entities as *resistance*, *inductance* and *capacitance* or the latter quantities can be determined experimentally. These elements, then, form the building blocks for more complex configurations called *networks* or *circuits*. Since there is no need to describe the physical appearance of the individual elements, a pictorial representation is often used and it is called a *schematic diagram*. However, each element must be assigned a numerical value, otherwise the schematic diagram is incomplete. If the numerical values associated with the sources of energy (such as batteries or generators) are also known, it is then possible to determine the power trans-

ferred from one part of the circuit to another element by finding the numerical values of entities called *voltage* and *current*.

Finally, there is the consideration of the fundamental properties of the matter that makes up the various circuit elements or devices. It is believed that all matter is made up of complex structures called *atoms* which in turn are composed of more or less unchangeable particles called *electrons*, *protons* and *neutrons*. Construction of an atom will determine the chemical and electrical properties of matter composed of like atoms. The periodic table of chemical elements is a classification of such atoms. Electrons play an important role in both the chemical and electrical properties of matter and elements where some of the electrons are relatively free to move about. These materials are called *conductors*. On the other hand, elements where all of the electrons are tightly bonded in the atomic structure are called *insulators*. Metals such as copper, aluminum, and silver are very good conductors while glass, plastics, and rubber are good insulators.

Although electrons play the principal role in the properties of both insulators and conductors, it is possible to construct matter with an apparent charge of opposite sign to that of the electron. Actually, the electron is still the charge carrier but it is the physical absence of an electron location that moves. However, it is convenient to consider that an actual charge carrier is present and it has been labeled a *hole*. Materials in which the motion of electrons and holes determine the electrical characteristics are called *semiconductors*. Transistors, integrated circuits and similar *solid-state devices* are made up from semiconductors. While

there are materials that fall in between the classifications of conductor and insulator, and might be labeled as semiconductors, the latter term is applied exclusively to materials where the motion of electrons and holes is important.

### Electrostatic Field and Potentials

All electrical quantities can be expressed in the fundamental dimensions of *time*, *mass*, *force* and *length*. In addition, the quantity or dimension of *charge* is also required. The metric system of units (SI — *Systeme International d'Unites*) is almost exclusively used now to specify such quantities, and the reader is urged to become familiar with this system. In the metric system, the basic unit of charge is the *coulomb*. The smallest known charge is that of the electron which is  $-1.6 \times 10^{-19}$  coulombs. (The proton has the same numerical charge except the sign is positive.)

The concept of electrical charge is analogous to that of mass. It is the mass of an object that determines the force of gravitational attraction between the object and another one. A similar phenomenon occurs with two charged objects. If the charges can be considered to exist at points in space, the force of attraction (or repulsion if the charges have like signs) is given by the formula

$$F = \frac{Q_1 Q_2}{4 \pi \epsilon r^2}$$

where  $Q_1$  is the numerical value of one charge,  $Q_2$  is the other charge value,  $r$  is the distance in meters,  $\epsilon$  is the *permittivity* of the medium surrounding the charges, and  $F$  is the force in newtons. In the case of free space of a vacuum,  $\epsilon$  has a value of  $8.854 \times 10^{-12}$  and is the permittivity of



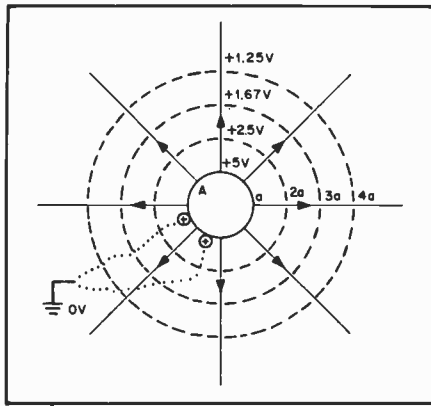


Fig. 1 — Field (solid lines) and potential (dotted lines) lines surrounding a charged sphere.

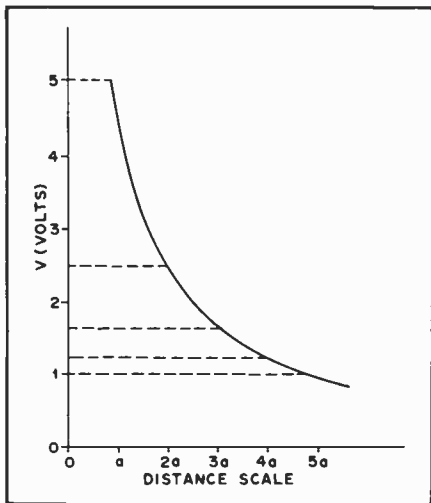


Fig. 2 — Variation of potential with distance for the charged sphere of Fig. 1.

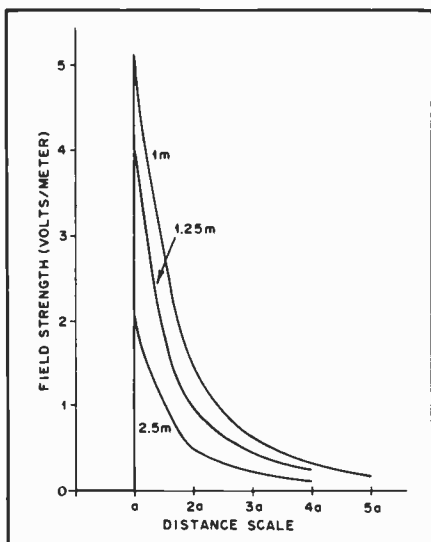


Fig. 3 — Variation of field strength with distance around a sphere charged to 5 volts for spheres of different radii.

free space. The product of relative permittivity and  $\epsilon_0$  (the permittivity of free space) gives the permittivity for a condition where matter is present. Permittivity is also called the *dielectric constant* and relative dielectric constants for plastics such as polyethylene and Teflon are 2.26 and 2.1, respectively. (The relative dielectric constant is also important in transmission-line theory. The reciprocal of the square root of the dielectric constant of the material used to separate the conductors in a transmission line gives the *velocity factor* of the line. The effect of velocity factor will be treated in later chapters.)

If instead of just two charges, a number of charged objects are present, the force on any one member is likely to be a complicated function of the positions and magnitudes of the other charges. Consequently, the concept of *electric-field strength* is a useful one to introduce. The field strength or *field intensity* is defined as the force on a given charge (concentrated at a point) divided by the numerical value of the charge. Thus, if a force of 1 newton existed on a test charge of 2 coulombs, the field intensity would be 0.5 newtons/coulomb.

Whenever a force exists on an object, it will require an expenditure of energy to move the object against that force. In some instances, the mechanical energy may be recovered (such as in a compressed spring) or it may be converted to another form of energy (such as heat produced by friction). As is the case for electric-field intensity, it is convenient to express energy  $\div$  charge as the *potential* or voltage of a charged object at a point. For instance, if it took the expenditure of 5 newton-meters (5 joules) to move a charge of 2 coulombs from a point of zero energy to a given point, the voltage or potential at that point would be 2.5 joules/coulomb. Because of the frequency of problems of this type, the dimension of joules/coulombs is given a special designation and one joule/coulomb is defined as 1 *volt*. Notice that if the voltage is divided by length (meters), the dimensions of field intensity will be obtained and a field strength of one newton/coulomb is also defined as one volt/meter. The relationship between field intensity and potential is illustrated by the following example shown in Fig. 1.

A conducting sphere receives a charge until its surface is at a potential of 5 volts. As charges are placed on the surface of a conductor, they tend to spread out into a uniform distribution. Consequently, it will require the same amount of energy to bring a given amount of charge from a point of zero reference to any point on the sphere. The outside of the sphere is then said to constitute an *equipotential* surface. Also, the amount of energy expended will be independent of the path traveled to get to the surface. For instance, it will require 5

joules of energy to bring a charge of 1 coulomb from a point of 0 voltage to any point on the sphere (as indicated by the dotted lines in Fig. 1). The *direction* of the force on a charged particle *at the surface* of the surface of the sphere must be perpendicular to the surface. This is because charges are able to flow about freely *on* the conductor but not *off* it. A force with a direction other than a right angle to the surface will have a component that is parallel to the conductor and will cause the charges to move about. Eventually, an equilibrium condition will be reached and any initial field component parallel to the surface will be zero. This motion of charge under the influence of an electric field is a very important concept in electricity. The *rate* at which charge flows past a reference point is defined as the current. A rate of 1 coulomb per second is defined as 1 *ampere*.

Because of the symmetry involved, the direction of the electric force and electric field can be represented by the solid straight lines in Fig. 1. The arrows indicate the direction of the force on a positive charge. At points away from the sphere, less energy will be required to bring up a test charge from zero reference. Consequently, a series of concentric spherical shells indicated by the dashed lines will define the equipotential surfaces around the sphere. From mathematical considerations (which will not be discussed here), it can be shown that the potential will vary as the inverse of the distance from the center of the sphere. This relationship is indicated by the numbers in Fig. 1 and by the graph in Fig. 2.

While the electric field gives the direction and magnitude of a force on a charged object, it is also equal to the negative *slope* numerical value of the curve in Fig. 2. The slope of a curve is the rate of change of some variable with distance and in this case, the variable is the potential. This is why the electric field is sometimes called the *potential gradient* (gradient being equivalent to slope). In the case of a curve that varies as the inverse of the distance, the slope at any point is proportional to the inverse of the distance squared.

An examination of Fig. 1 would indicate that the potential variation is only dependent upon the shape of the conductor and not its actual physical size. That is, once the value of the radius  $a$  of the sphere in Fig. 1 is specified, the potential at any other point a given distance from the sphere is also known. Thus, Fig. 1 can be used for any number of spheres with different radii. When it is changed by a certain percentage, all the other values would change by the same percentage too. However, the amount of charge required to produce a given voltage, or voltage change, does depend upon the size of the conductor, its shape,

and its position in relation to other conductors and insulators. For a given conductor configuration, the voltage is related to the required charge by the formula

$$V = \frac{Q}{C}$$

where the entity C is defined as the capacitance. Capacitance will be discussed in more detail in a later section.

Since the electric-field intensity is related to the change in potential with distance, like potential, the manner in which it changes will be unaffected by the absolute physical size of the conductor configuration. However, the exact numerical value at any point *does* depend on the dimensions of the configuration. This is illustrated in Fig. 3 for spheres with different radii. Note that for larger radii, the numerical value of the field strength at the surface of the sphere (distance equal to a) is less than it is for smaller radii. This effect is important in the design of transmission lines and *capacitors*. (A capacitor is a device for storing charge. In older terminology, it was sometimes called a *condenser*.) Even though the same voltage is applied across the terminals of a transmission line or capacitor, the field strength between the conductors is going to be higher for configurations of small physical size than it is for larger ones. If the field strength becomes too high, the insulating material (including air) can "break down." On the other hand, the effect can be used to advantage in spark gaps used to protect equipment connected to an antenna which is subject to atmospheric electricity. The spark-gap conductors or electrodes are filed to sharp points. Because the needlepoints appear as conductors of very small radii, the field strength is going to be higher for the same applied potential than it would be for blunt electrodes (Fig. 4). This means the separation can be greater and the effect of the spark gap on normal circuit operation will not be as pronounced. However, a blunt electrode such as a sphere is often

used on the tip of a whip antenna in order to lower the field strength under transmitting conditions.

An examination of Fig. 3 reveals that the field strength is zero for distances less than a which includes points *inside* the sphere. The implication here is that the effect of fields and charges cannot penetrate the conducting surface and disturb conditions inside the enclosure. The conducting sphere is said to form an *electrostatic shield* around the contents of the enclosure. However, the converse is not true. That is, charges inside the sphere will cause or induce a field on the outside surface. This is why it is very important that enclosures designed to confine the effects of charges be connected to a point of zero potential. Such a point is often called a *ground*.

### Fields and Currents

In the last section, the motion of charged particles in the presence of an electric field was mentioned in connection with charges placed on a conducting sphere and the concept of current was introduced. It was assumed that charges could move around unimpeded on the surface of the sphere. In the case of actual conductors, this is not true. The charges appear to bump into atoms as they move through the conductor under the influence of the electric field. This effect depends upon the kind of material used. Silver is a conductor with the least amount of opposition to the movement of charge while carbon and certain alloys of iron are rather poor conductors of charge flow. A measure of how easily charge can flow through a conductor is defined as the conductivity and is denoted by  $\sigma$ .

The *current density* J, in a conductor is the rate of charge flow or current through a given cross-sectional area. It is related to the electric field and conductivity by the formula

$$J = \sigma E$$

In general, the conductivity and electric field will not be constant over a large

cross-sectional area, but for an important theoretical case this is assumed to be true (Fig. 5).

A cylinder of a material with conductivity  $\sigma$  is inserted between two end caps of infinite conductivity. The end caps are connected to a voltage source such as a battery or generator. (A battery consists of a number of cells that convert chemical energy to electrical energy and a generator converts mechanical energy of motion to electrical energy.) The electric field is also considered to be constant along the length, l, of the cylinder and, as a consequence, the slope of the potential variation along the cylinder will also be a constant. This is indicated by the dashed lines in Fig. 5. Since the electric field is constant, the current density will also be constant. Therefore, the total current entering the end caps will just be the product of the current density and the cross-sectional area. The value of the electric field will be the quotient of the total voltage and the length of the cylinder. Combining the foregoing results and introducing two new entities gives the following set of equations:

$$J = \sigma \left( \frac{V}{l} \right) \text{ since } J = \sigma E \text{ and } E = \frac{V}{l}$$

$$I = J(A) = \frac{\sigma AV}{l}$$

$$\rho = \frac{l}{\sigma} \text{ and } V = I \left( \frac{\rho l}{A} \right)$$

$$R = \frac{\rho l}{A} \text{ and } V = IR$$

where  $\rho$  = the *resistivity* of a conducting material, R = the resistance. The final equation is a very basic one in circuit theory and is called Ohm's Law. Configurations similar to the one shown in Fig. 5 are very common ones in electrical circuits and are called *resistors*.

It will be shown in a later section that the power dissipated in a resistor is equal to the product of the resistance and the square of the current. Quite often resistance is an undesirable effect (such as in a wire carrying current from one location to another one) and must be reduced as much as possible. This can be accomplished by using a conductor with a low resistivity such as silver (or copper which is close to silver in resistivity, but is not as expensive) with a large cross-sectional area and as short a length as possible. The current-carrying capability decreases as the diameter of a conductor size gets smaller.

### Potential Drop and Electromotive Force

The application of the relations between fields, potential, and similar concepts to the physical configuration shown in Fig. 5 permitted the derivation of the formula that eliminated further consideration of the field problem. The idea of an electrical energy source was also introduced. A similar analysis involving

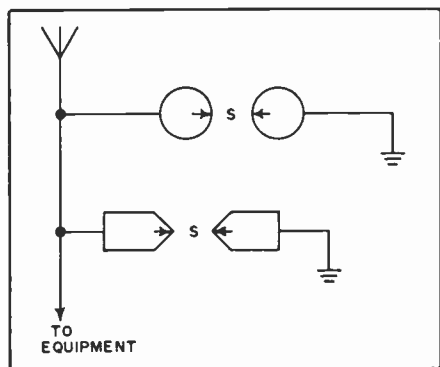


Fig. 4 — Spark gaps with sharp points break down at lower voltages than ones with blunt surfaces even though the separation is the same.

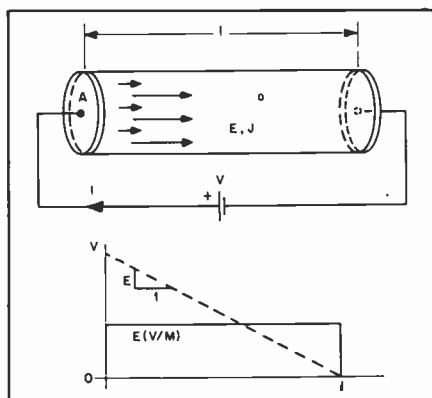


Fig. 5 — Potential and field strength along a current-carrying conductor.

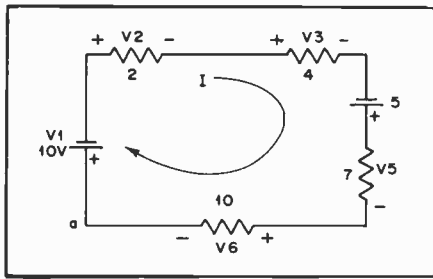


Fig. 6 — A series circuit illustrating the effects of emf and potential drop.

mechanics and field theory would be required to determine the characteristics of an electrical generator and an application of chemistry would be involved in designing a chemical cell. However, it will be assumed that this problem has been solved and that the energy source can be replaced with a symbol such as that used in Fig. 5.

The term *electromotive force* (emf) is applied to describe a source of electrical energy, and potential drop (or voltage drop) is used for a device that consumes

electrical energy. A combination of sources and resistances (or other elements) that are connected in some way is called a network or circuit. It is evident that the energy consumed in a network must be equal to the energy produced. Applying this principle to the circuit shown in Fig. 6 gives an important extension of Ohm's Law.

In Fig. 6, a number of sources and resistances are connected in tandem or in *series* to form a *circuit loop*. It is desired to determine the current  $I$ . The current can be assumed to be flowing in either a clockwise or counterclockwise direction. If the assumption is not correct, the sign of the current will be negative when the network equations are solved and the direction can be corrected accordingly. In order to solve the problem, it is necessary to find the sum of the emfs (which is proportional to the energy produced) and to equate this sum to the sum of the potential drops (which is proportional to the energy consumed). Assuming the current is flowing in a clockwise direction, the first element encountered at point  $a$  is an emf,  $V_1$ , but it appears to be connected "backward." Therefore, it receives a

minus sign. The next source is  $V_4$ , and it appears as a voltage rise so it is considered positive. Since the current flow in all the resistors is in the same direction, all the potential drops have the same sign. The potential drop is the product of the current in amperes and the resistance in *ohms*. The *sums* for the emfs and potential drops and the resulting current are given by

$$\begin{aligned} \text{Sum of emf} &= V_1 + V_4 = -10 + 5 \\ &= -5 \text{ volts} \end{aligned}$$

$$\begin{aligned} \text{Sum of pot. drops} &= V_2 + V_3 + V_5 + V_6 \\ &= 1(2 + 4 + 7 + 10) = 23 \end{aligned}$$

$$I = \frac{-5}{23} = -0.217 \text{ ampere}$$

Because the sign of the current is negative, it is actually flowing in a counterclockwise direction. The physical significance of this phenomenon is that one source is being "charged." For instance, the circuit in Fig. 6 might represent a direct current (dc) generator and a battery.

## Resistance

Given two conductors of the same size and shape, but of different materials, the amount of current that will flow when a given emf is applied will be found to vary with what is called the *resistance* of the material. The lower the resistance, the greater the current for a given value of emf.

Resistance is measured in *ohms*. A circuit has a resistance of 1 ohm when an applied emf of 1 volt causes a current of 1 ampere to flow. The *resistivity* of a material is the resistance, in ohms, of a cube of the material measuring one centimeter on each edge. One of the best conductors is copper, and it is frequently convenient, in making resistance calculations, to compare the resistance of the material under consideration with that of a copper conductor of the same size and shape. Table 1 gives the ratio of the resistivity of various conductors to that of copper.

The longer the path through which the current flows, the higher the resistance of that conductor. For direct current and low-frequency alternating currents (up to a few thousand cycles per second) the resistance is inversely proportional to the cross-sectional area of the path the current must travel; that is, given two conductors of the same material and having the same length, but differing in cross-sectional area, the one with the

larger area will have the lower resistance.

### Resistance of Wires

The problem of determining the resistance of a round wire of given diameter and length — or its opposite, finding a suitable size and length of wire to supply a desired amount of resistance — can be easily solved with the help of the copper wire table given in a later chapter. This table gives the resistance, in ohms per thousand feet, of each standard wire size.

Example: Suppose a resistance of 3.5 ohms is needed and some no. 28 wire is on hand. The wire table in chapter 17 shows

that no. 28 has a resistance of 66.17 ohms per thousand feet. Since the desired resistance is 3.5 ohms, the length of wire required will be

$$\frac{3.5}{66.17} \times 1000 = 52.89 \text{ feet.}$$

Or, suppose that the resistance of the wire in the circuit must not exceed 0.05 ohm and that the length of wire required for making the connections totals 14 feet. Then

$$\frac{14}{1000} \times R = 0.05 \text{ ohm}$$

where  $R$  is the maximum allowable resistance in ohms per thousand feet. Rearranging the formula gives

$$R = \frac{0.05 \times 1000}{14} = 3.57 \text{ ohms/1000 ft.}$$

Reference to the wire table shows that no. 15 is the smallest size having a resistance less than this value.

When the wire is not copper, the resistance values given in the wire table should be multiplied by the ratios given in Table 1 to obtain the resistance.

Example: If the wire in the first example

Table 1  
Relative Resistivity of Metals

Materials	Resistivity Compared to Copper
Aluminum (pure)	1.6
Brass	3.7-4.9
Cadmium	4.4
Chromium	1.8
Copper (hard-drawn)	1.03
Copper (annealed)	1.00
Gold	1.4
Iron (pure)	5.68
Lead	12.8
Nickel	5.1
Phosphor Bronze	2.8-5.4
Silver	0.94
Steel	7.6-12.7
Tin	6.7
Zinc	3.4



were nickel instead of copper, the length required for 3.5 ohms would be

$$\frac{3.5}{66.17 \times 5.1} \times 1000 = 10.37 \text{ feet}$$

### Temperature Effects

The resistance of a conductor changes with its temperature. Although it is seldom necessary to consider temperature in making resistance calculations for amateur work, it is well to know that the resistance of practically all metallic conductors increases with increasing temperature. Carbon, however, acts in the opposite way; its resistance *decreases* when its temperature rises. The temperature effect is important when it is necessary to maintain a constant resistance under all conditions. Special materials that have little or no change in resistance over a wide temperature range are used in that case.

### Resistors

A "package" of resistance made up into a single unit is called a *resistor*. Resistors having the same resistance value may be considerably different in size and construction (Fig. 7). The flow of current through resistance causes the conductor to become heated; the higher the resistance and the larger the current, the greater the amount of heat developed. Resistors intended for carrying large currents must be physically large so the heat can be radiated quickly to the surrounding air. If the resistor does not get rid of the heat quickly it may reach a temperature that will cause it to melt or burn.

### Skin Effect

The resistance of a conductor is not the same for alternating current as it is for direct current. When the current is alternating there are internal effects that tend to force the current to flow mostly in the outer parts of the conductor. This decreases the effective cross-sectional area of the conductor, with the result that the resistance increases.

For low audio frequencies the increase in resistance is unimportant, but at radio frequencies this skin effect is so great that practically all the current flow is confined within a few thousandths of an inch of the conductor surface. The rf resistance is consequently many times the dc resistance, and increases with increasing frequency. In the rf range a conductor of thin tubing will have just as low resistance as a solid conductor of the same diameter, because material not close to the surface carries practically no current.

### Conductance

The reciprocal of resistance (that is, 1/R) is called *conductance*. It is usually represented by the symbol G. A circuit

having large conductance has low resistance, and vice versa. In radio work the term is used chiefly in connection with vacuum-tube characteristics. The unit of conductance is the mho. A resistance of 1 ohm has a conductance of 1 mho, a resistance of 1000 ohms has a conductance of 0.001 mho, and so on. A unit frequently used in connection with vacuum tubes is the *micromho*, or one-millionth of a mho. It is the conductance of a resistance of 1 MΩ.

### Ohm's Law

The simplest form of electric circuit is a battery with a resistance connected to its terminals, as shown by the symbols in Fig. 8. A complete circuit must have an unbroken path so current can flow out of the battery, through the apparatus connected to it, and back into the battery. The circuit is broken, or open, if a connection is removed at any point. A switch is a device for making and breaking connections and thereby closing or opening the circuit, either allowing current to flow or preventing it from flowing.

The values of current, voltage and resistance in a circuit are by no means independent of each other. The relationship between them is known as *Ohm's Law*. It can be stated as follows: The current flowing in a circuit is directly proportional to the applied emf and inversely proportional to the resistance. Expressed as an equation, it is

$$I \text{ (amperes)} = \frac{E \text{ (volts)}}{R \text{ (ohms)}}$$

The equation above gives the value of current when the voltage and resistance are known. It may be transposed so that each of the three quantities may be found when the other two are known:

$$E = IR$$

(that is, the voltage acting is equal to the current in amperes multiplied by the resistance in ohms) and

$$R = \frac{E}{I}$$

(or, the resistance of the circuit is equal to the applied voltage divided by the current).

All three forms of the equation are used almost constantly in radio work. It must be remembered that the quantities are in *volts*, *ohms* and *amperes*; other units cannot be used in the equations without first being converted. For example, if the current is in milliamperes it must be changed to the equivalent fraction of an ampere before the value can be substituted in the equations.

Table 2 shows how to convert between



Fig. 7 — Examples of various resistors. In the foreground are 1/4-, 1/2- and 1-watt composition resistors. The three larger cylindrical components at the center are wirewound power resistors. The remaining two parts are variable resistors, pc-board mount at the lower left and panel mount at the upper center.

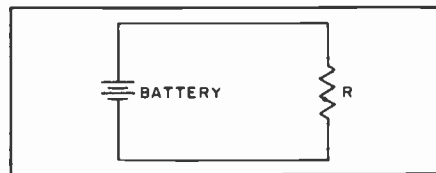


Fig. 8 — A simple circuit consisting of a battery and resistor.

Table 2  
Conversion Factors for Fractional and Multiple Units

Change From	To	Divide by	Multiply by
Units	Microunits		1,000,000
	Milliunits		1000
	Kilounits	1000	
	Megaunits	1,000,000	
Micro-units	Milliunits	1000	
	Units	1,000,000	
Milli-units	Microunits		1000
	Units	1000	
Kilo-units	Units		1000
	Megaunits	1000	
Mega-units	Units		1,000,000
	Kilounits		1000

the various units in common use. The prefixes attached to the basic-unit name indicate the nature of the unit. These prefixes are

- micro — one-millionth (abbreviated  $\mu$ )
- milli — one-thousandth (abbreviated m)
- kilo — one thousand (abbreviated k)
- mega — one million (abbreviated M)

For example, 1 microvolt is one-millionth of a volt, and 1 megohm is 1,000,000 ohms. There are therefore 1,000,000 microvolts in one volt, and 0.000001 megohm in 1 ohm.

The following examples illustrate the use of Ohm's Law:

The current flowing in a resistance of 20,000 ohms is 150 milliamperes. What is the voltage? Since the voltage is to be found, the equation to use is  $E = IR$ . The current must first be converted from milliamperes to amperes, and reference to the table shows that to do so it is necessary to divide by 1000. Therefore,

$$E = \frac{150}{1000} \times 20,000 = 3000 \text{ volts}$$

When a voltage of 150 is applied to a circuit, the current is measured at 2.5 amperes. What is the resistance of the circuit? In this case  $R$  is the unknown, so

$$R = \frac{E}{I} = \frac{150}{2.5} = 60 \text{ ohms}$$

No conversion was necessary because the voltage and current were given in volts and amperes.

How much current will flow if 250 volts is applied to a 5000-ohm resistor? Since  $I$  is unknown

$$I = \frac{E}{R} = \frac{250}{5000} = 0.05 \text{ ampere}$$

Milliampere units would be more con-

venient for the current, and  $0.05 \text{ ampere} \times 1000 = 50 \text{ milliamperes}$ .

### Series and Parallel Resistances

Very few actual electric circuits are as simple as the illustration in the preceding section. Commonly, resistances are found connected in a variety of ways. The two fundamental methods of connecting resistances are shown in Fig. 9. In the upper drawing, the current flows from the source of emf (in the direction shown by the arrow, let us say) down through the first resistance,  $R_1$ , then through the second,  $R_2$ , and then back to the source. These resistors are connected in series. The current everywhere in the circuit has the same value.

In the lower drawing, the current flows to the common connection point at the top of the two resistors and then divides, one part of it flowing through  $R_1$  and the other through  $R_2$ . At the lower connection point these two currents again combine; the total is the same as the current that flowed into the upper common connection. In this case the two resistors are connected in parallel.

#### Resistors in Series

When a circuit has a number of resistances connected in series, the total resistance of the circuit is the sum of the individual resistances. If these are numbered  $R_1, R_2, R_3$ , and so on, then  $R$  (total) =  $R_1 + R_2 + R_3 + R_4 + \dots$  where the dots indicate that as many resistors as necessary may be added.

Example: Suppose that three resistors are connected to a source of emf as shown in Fig. 10. The emf is 250 volts.  $R_1$  is 5000 ohms,  $R_2$  is 20,000 ohms, and  $R_3$  is 8000 ohms. The total resistance is then

$$\begin{aligned} R &= R_1 + R_2 + R_3 \\ &= 5000 + 20,000 + 8000 \\ &= 33,000 \text{ ohms} \end{aligned}$$

The current flowing in the circuit is then

$$\begin{aligned} I &= \frac{E}{R} = \frac{250}{33,000} = 0.00757 \text{ amp.} \\ &= 7.57 \text{ mA.} \end{aligned}$$

(We need not carry calculations beyond three significant figures, and often two will suffice because the accuracy of measurements is seldom better than a few percent.)

#### Voltage Drop

Ohm's Law applies to *any part* of a circuit as well as to the whole circuit. Although the current is the same in all three of the resistances in the example, the total voltage divides among them. The voltage appearing across each resistor (the voltage drop) can be found from Ohm's Law.

Example: If the voltage across  $R_1$  (Fig. 10) is called  $E_1$ , that across  $R_2$  is called

$E_2$ , and that across  $R_3$  is called  $E_3$ , then  $E_1 = IR_1 = 0.00757 \times 5000 = 37.9 \text{ volts}$   
 $E_2 = IR_2 = 0.00757 \times 20,000 = 151.4 \text{ volts}$   
 $E_3 = IR_3 = 0.00757 \times 8000 = 60.6 \text{ volts}$

The applied voltage must equal the sum of the individual voltage drops:

$$\begin{aligned} E &= E_1 + E_2 + E_3 \\ &= 37.9 + 151.4 + 60.6 \\ &= 249.9 \text{ volts} \end{aligned}$$

The answer would have been more nearly exact if the current had been calculated to more decimal places, but as explained above a very high order of accuracy is not necessary.

In problems such as this considerable time and trouble can be saved, when the current is small enough to be expressed in milliamperes, if the resistance is expressed in kilohms rather than ohms. When resistance in kilohms is substituted directly in Ohm's Law the current will be milliamperes if the emf is in volts.

#### Resistors in Parallel

In a circuit with resistances in parallel, the total resistance is *less* than that of the *lowest* value of resistance present. This is because the total current is always greater than the current in any individual resistor. The formula for finding the total resistance of resistances in parallel is

$$R = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} + \dots}$$

where the dots again indicate that any number of resistors can be combined by the same method. For only two resistances in parallel (a very common case), the formula becomes

$$R = \frac{R_1 \times R_2}{R_1 + R_2}$$

Example: If a 500-ohm resistor is paralleled with one of 1200 ohms, the total resistance is

$$\begin{aligned} R &= \frac{R_1 R_2}{R_1 + R_2} = \frac{500 \times 1200}{500 + 1200} \\ &= \frac{600,000}{1700} \\ &= 353 \text{ ohms} \end{aligned}$$

It is probably easier to solve practical problems by a different method than the "reciprocal of reciprocals" formula. Suppose the three resistors of the previous example are connected in parallel as shown in Fig. 11. The same emf, 250 volts, is applied to all three of the resistors. The current in each can be found from Ohm's Law as shown below,  $I_1$  being the current through  $R_1$ ,  $I_2$  the current through  $R_2$

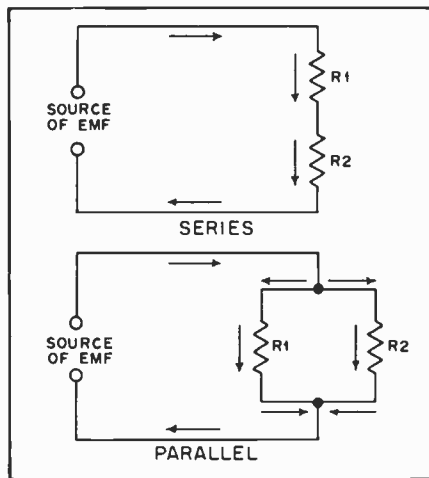


Fig. 9 — Resistors connected in series and in parallel.

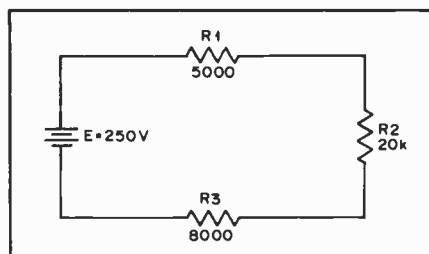


Fig. 10 — An example of resistors in series. The solution of the circuit is worked out in the text.

and I3 the current through R3.

For convenience, the resistance will be expressed in kilohms so the current will be in milliamperes.

$$I_1 = \frac{E}{R_1} = \frac{250}{5} = 50 \text{ mA}$$

$$I_2 = \frac{E}{R_2} = \frac{250}{20} = 12.5 \text{ mA}$$

$$I_3 = \frac{E}{R_3} = \frac{250}{8} = 31.25 \text{ mA}$$

The total current is

$$\begin{aligned} I &= I_1 + I_2 + I_3 \\ &= 50 + 12.5 + 31.25 \\ &= 93.75 \text{ mA} \end{aligned}$$

The total resistance of the circuit is therefore

$$\begin{aligned} R &= \frac{E}{I} = \frac{250}{93.75} = 2.66 \text{ kilohms} \\ &= 2660 \text{ ohms} \end{aligned}$$

### Resistors in Series-Parallel

An actual circuit may have resistances both in parallel and in series. To illustrate, we use the same three resistances again, but now connected as in Fig. 12. The method of solving a circuit such as Fig. 12 is as follows: Consider R2 and R3 in parallel as though they formed a single resistor. Find their equivalent resistance. Then this resistance in series with R1 forms a simple series circuit, as shown at the right in Fig. 12. An example of the arithmetic is given under the illustration.

Using the same principles, and staying within the practical limits, a value for R2 can be computed that will provide a given voltage drop across R3 or a given current through R1. Simple algebra is required.

Example: The first step is to find the equivalent resistance of R2 and R3. From the formula for two resistances in parallel,

$$\begin{aligned} R_{eq} &= \frac{R_2 \times R_3}{R_2 + R_3} = \frac{20 \times 8}{20 + 8} = \frac{160}{28} \\ &= 5.71 \text{ k}\Omega \end{aligned}$$

The total resistance in the circuit is then

$$\begin{aligned} R &= R_1 + R_{eq} = 5 \text{ k}\Omega + 5.71 \text{ k}\Omega \\ &= 10.71 \text{ k}\Omega \end{aligned}$$

The current is

$$I = \frac{E}{R} = \frac{250}{10.71} = 23.3 \text{ mA}$$

The voltage drops across R1 and Req are

$$E_1 = I \times R_1 = 23.3 \times 5 = 117 \text{ volts}$$

$$E_2 = I \times R_{eq} = 23.3 \times 5.71 = 133 \text{ volts}$$

with sufficient accuracy. These total 250 volts, thus checking the calculations so far, because the sum of the voltage drops must equal the applied voltage. Since E2 appears across both R2 and R3.

$$I_2 = \frac{E_2}{R_2} = \frac{133}{20} = 6.65 \text{ mA}$$

$$I_3 = \frac{E_2}{R_3} = \frac{133}{8} = 16.6 \text{ mA}$$

where I2 = current through R2

I3 = current through R3

The total is 23.25 mA, which checks closely enough with 23.3 mA, the current through the whole circuit.

### Power and Energy

Power — the rate of doing work — is equal to voltage multiplied by current. The unit of electrical power, called the *watt*, is equal to one volt multiplied by one ampere. The equation for power therefore is

$$P = EI$$

where

P = power in watts

E = emf in volts

I = current in amperes

Common fractional and multiple units for power are the *milliwatt* one one-thousandth of a watt, and the *kilowatt*, or 1000 watts.

Example: The plate voltage on a transmitting vacuum tube is 2000 volts and the plate current is 350 milliamperes. (The current must be changed to amperes before substitution in the formula, and so is 0.35 amp.) Then

$$P = EI = 2000 \times 0.35 = 700 \text{ watts}$$

By substituting the Ohm's Law equivalent for E and I, the following formulas are obtained for power:

$$P = \frac{E^2}{R}$$

$$P = I^2R$$

These formulas are useful in power calculations when the resistance and either the current or voltage (but not both) are known.

Example: How much power will be used up in a 4000-ohm resistor if the

voltage applied to it is 200 volts? From the equation

$$\begin{aligned} P &= \frac{E^2}{R} = \frac{(200)^2}{4000} = \frac{40,000}{4000} \\ &= 10 \text{ watts} \end{aligned}$$

Or, suppose a current of 20 milliamperes flows through a 300-ohm resistor. Then

$$\begin{aligned} P &= I^2R = (0.02)^2 \times 300 \\ &= 0.0004 \times 300 \\ &= 0.12 \text{ watt} \end{aligned}$$

Note that the current was changed from milliamperes to amperes before substitution in the formula.

Electrical power in a resistance is turned into heat. The greater the power the more rapidly the heat is generated. Resistors for radio work are made in many sizes, the smallest being rated to "dissipate" (or carry safely) about 1/8 watt. The largest resistors commonly used in amateur equipment will dissipate about 100 watts.

### Generalized Definition of Resistance

Electrical power is not always turned into heat. The power used in running a

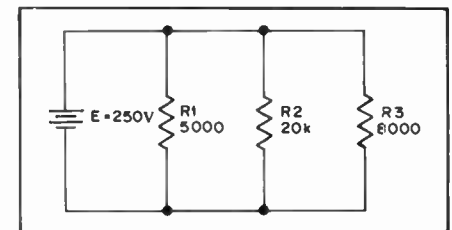


Fig. 11 — An example of resistors in parallel. The solution is worked out in the text.

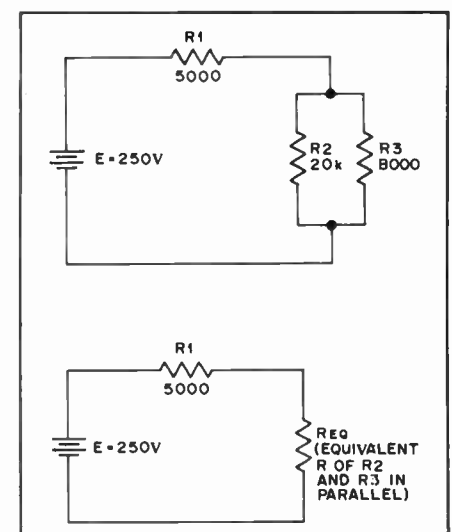


Fig. 12 — An example of resistors in series-parallel. The equivalent circuit is below. The solution is worked out in the text.

motor, for example, is converted to mechanical motion. The power supplied to a radio transmitter is largely converted into radio waves. Power applied to a loudspeaker is changed into sound waves. But in every case of this kind the power is completely "used up" — it cannot be recovered. Also, for proper operation of the device the power must be supplied at a definite ratio of voltage to current. Both these features are characteristics of resistance, so it can be said that any device that dissipates power has a definite value of "resistance." This concept of resistance as something that absorbs power at a definite voltage/current ratio is very useful, since it permits substituting a simple resistance for the *load* or power-consuming part of the device receiving power, often with considerable simplification of calculations. Of course, every electrical device has some resistance of its own in the more narrow sense, so a part of the power supplied to it is dissipated in that resistance and hence appears as heat even though the major part of the power may be converted to another form.

### Efficiency

In devices such as motors and vacuum tubes, the object is to obtain power in

some other form than heat. Therefore power used in heating is considered to be a loss, because it is not the *useful* power. The *efficiency* of a device is the useful power output (in its converted form) divided by the power input to the device. In a vacuum-tube transmitter, for example, the object is to convert power from a dc source into ac power at some radio frequency. The ratio of the rf power output to the dc input is the efficiency of the tube. That is,

$$\text{Eff.} = \frac{P_o}{P_i}$$

where Eff. = efficiency (as a decimal)  
 $P_o$  = power output (watts)  
 $P_i$  = power input (watts)

Example: If the dc input to the tube is 100 watts, and the rf power output is 60 watts, the efficiency is

$$\text{Eff.} = \frac{P_o}{P_i} = \frac{60}{100} = 0.6$$

Efficiency is usually expressed as a percentage; that is, it tells what percent of the input power will be available as useful

output. The efficiency in the above example is 60 percent.

### Energy

In residences, the power company's bill is for electrical energy, not for power. What you pay for is the *work* that electricity does for you, not the *rate* at which that work is done. Electrical work is equal to power multiplied by time; the common unit is the *watt-hour*, which means that a power of 1 watt has been used for one hour. That is,

$$W = PT$$

where W = energy in watt-hours  
 P = power in watts  
 T = time in hours

Other energy units are the *kilowatt-hour* and the *watt-second*. These units should be self-explanatory.

Energy units are seldom used in amateur practice, but it is obvious that a small amount of power used for a long time can eventually result in a "power" bill that is just as large as though a large amount of power had been used for a very short time.

## Capacitance

Suppose two flat metal plates are placed close to each other (but not touching) and are connected to a battery through a switch, as shown in Fig. 13. At the instant the switch is closed, electrons will be attracted from the upper plate to the positive terminal of the battery, and the same number will be repelled into the lower plate from the negative battery terminal. Enough electrons move into one plate and out of the other to make the emf between them the same as the emf of the battery.

If the switch is opened after the plates have been *charged* in this way, the top plate is left with a deficiency of electrons and the bottom plate with an excess. The plates remain charged despite the fact that the battery no longer is connected. However, if a wire is touched between the two plates (*short-circuiting* them) the excess electrons on the bottom plate will flow through the wire to the upper plate, thus restoring electrical neutrality. The plates have then been *discharged*.

The two plates constitute an electrical *capacitor*; a capacitor possesses the property of storing electricity. (The energy actually is stored in the electric field between the plates.) During the time the electrons are moving — that is, while the capacitor is being charged or discharged — a current is flowing in the circuit even though the circuit is "broken" by the gap between the capacitor plates. However,

the current flows only during the time of charge and discharge, and this time is usually very short. There can be no continuous flow of direct current "through" a capacitor, but an alternating current can pass through easily if the frequency is high enough.

The charge or quantity of electricity that can be placed on a capacitor is proportional to the applied voltage and to the capacitance of the capacitor. The larger the plate area and the smaller the spacing between the plate the greater the capacitance. The capacitance also depends upon the kind of insulating material between the plates; it is smallest with air insulation, but substitution of other insulating materials for air may increase the capacitance many times. The ratio of the capacitance with some material other than air between the plates, to the capacitance of the same capacitor with air

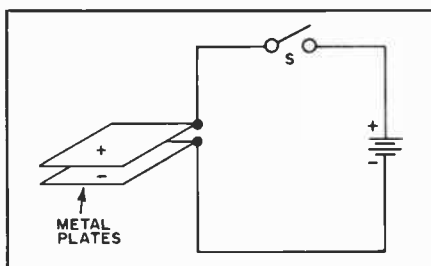


Fig. 13 — A simple capacitor.

insulation, is called the *dielectric constant* of that particular insulating material. The material itself is called a *dielectric*. The dielectric constants of a number of materials commonly used as dielectrics in capacitors are given in Table 3. If a sheet of polystyrene is substituted for air between the plates of a capacitor, for example, the capacitance will be increased 2.6 times.

### Units

The fundamental unit of capacitance is

Table 3  
 Dielectric Constants and Breakdown Voltages

Material	Dielectric Constant*	Puncture Voltage**
Air	1.0	240
Alsimag 196	5.7	240
Bakelite	4.4-5.4	300
Bakelite, mica-filled	4.7	325-375
Cellulose acetate	3.3-3.9	250-600
Fiber	5-7.5	150-180
Formica	4.6-4.9	450
Glass, window	7.6-8	200-250
Glass, Pyrex	4.8	335
Mica, ruby	5.4	3800-5600
Mycalex	7.4	250
Paper, Royalgrey	3.0	200
Plexiglas	2.8	990
Polyethylene	2.3	1200
Polystyrene	2.6	500-700
Porcelain	5.1-5.9	40-100
Quartz, fused	3.8	1000
Steatite, low-loss	5.8	150-315
Teflon	2.1	1000-2000

\* At 1 MHz \*\* In volts per mil (0.001 inch)



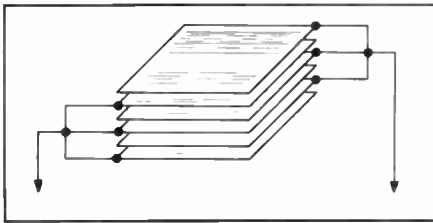


Fig. 14 — A multiple-plate capacitor. Alternate plates are connected together.

the farad, but this unit is much too large for practical work. Capacitance is usually measured in *microfarads* (abbreviated  $\mu\text{F}$ ) or *picofarads* ( $\text{pF}$ ). The microfarad is one-millionth of a farad, and the picofarad (formerly micromicrofarad) is one-millionth of a microfarad. Capacitors nearly always have more than two plates, the alternate plates being connected together to form two sets as shown in Fig. 14. This makes it possible to attain a fairly large capacitance in a small space, since several plates of smaller individual area can be stacked to form the equivalent of a single large plate of the same total area. Also, all plates, except the two on the ends, are exposed to plates of the other group on *both sides*, and so are twice as effective in increasing the capacitance.

The formula for calculating capacitance is

$$C = 0.224 \frac{KA}{d} (n - 1)$$

where  $C$  = capacitance in  $\text{pF}$

$K$  = dielectric constant of material between plates

$A$  = area of one side of one plate in square inches

$d$  = separation of plate surfaces in inches

$n$  = number of plates

If the plates in one group do not have the same area of the plates in the other, use the area of the *smaller* plates.

### Capacitors in Radio

The types of capacitors used in radio work differ considerably in physical size, construction, and capacitance. Some representative types are shown in the photograph (Fig. 15). In *variable* capacitors (almost always constructed with air for the dielectric) one set of plates is made movable with respect to the other set so that the capacitance can be varied. Fixed capacitors — that is, assemblies having a single, nonadjustable value of capacitance — also can be made with metal plates and with air as the dielectric, but usually are constructed from plates of metal foil with a thin solid or liquid dielectric sandwiched in between, so that a relatively large capacitance can be secured in a small

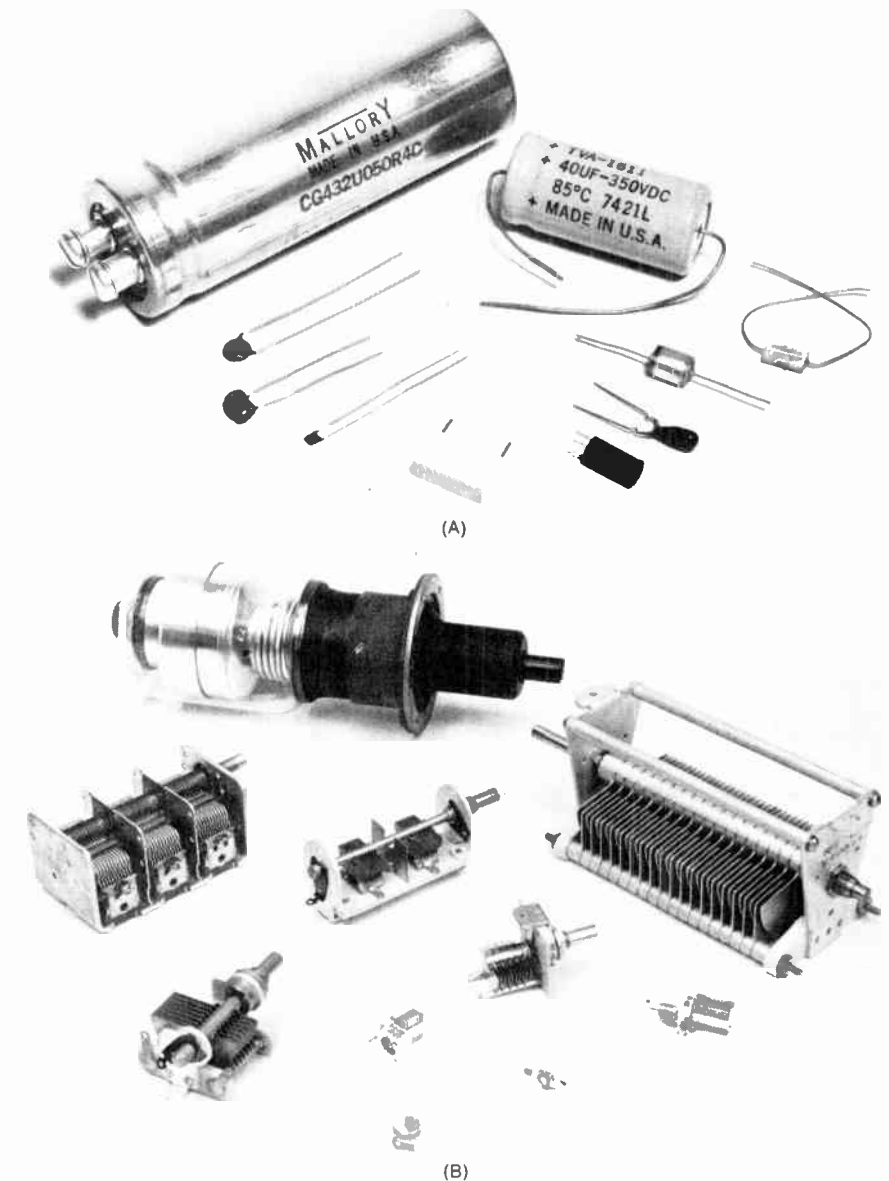


Fig. 15 — Fixed-value capacitors are seen at A. A large computer-grade unit is at the upper left. The 40- $\mu\text{F}$  unit is an electrolytic capacitor. The smaller pieces are silver-mica, disk-ceramic, tantalum, polystyrene and ceramic chip capacitors. The small black unit (cylindrical) is a pc-board-mount electrolytic. Variable capacitors are shown at B. A vacuum variable is at the upper left.

unit. The solid dielectrics commonly used are mica, paper and special ceramics. An example of a liquid dielectric is mineral oil. The *electrolytic* capacitor uses aluminum-foil plates with a semiliquid conducting chemical compound between them; the actual dielectric is a very thin film of insulating material that forms on one set of plates through electrochemical action when a dc voltage is applied to the capacitor. The capacitance obtained with a given plate area in an electrolytic capacitor is very large, compared with capacitors having other dielectrics, because the film is so thin — much less than any thickness that is practicable with a solid dielectric.

The use of electrolytic and oil-filled capacitors is confined to power-supply filtering and audio-bypass applications. Mica and ceramic capacitors are used throughout the frequency range from

audio to several hundred megacycles.

### Voltage Breakdown

When a high voltage is applied to the plates of a capacitor, a considerable force is exerted on the electrons and nuclei of the dielectric. Because the dielectric is an insulator the electrons do not become detached from atoms the way they do in conductors. However, if the force is great enough the dielectric will “break down;” usually it will puncture and may char (if it is solid) and permit current to flow. The breakdown voltage depends upon the kind and thickness of the dielectric, as shown in Table 3. It is not directly proportional to the thickness; that is, doubling the thickness does not quite double the breakdown voltage. If the dielectric is air or any other gas, breakdown is evidenced by a spark or arc between the plates, but if

the voltage is removed the arc ceases and the capacitor is ready for use again. Breakdown will occur at a lower voltage between pointed or sharp-edged surfaces than between rounded and polished surfaces; consequently, the breakdown voltage between metal plates of given spacing in air can be increased by buffing the edges of the plates.

Since the dielectric must be thick to withstand high voltages, and since the thicker the dielectric the smaller the capacitance for a given plate area, a high-voltage capacitor must have more plate area than a low-voltage one of the same capacitance. High-voltage, high-capacitance capacitors are physically large.

### Capacitors in Series and Parallel

The terms "parallel" and "series" when used with reference to capacitors have the same circuit meaning as with resistances. When a number of capacitors are connected in parallel, as in Fig. 16, the total capacitance of the group is equal to the sum of the individual capacitances, so

$$C_{\text{total}} = C_1 + C_2 + C_3 + C_4 + \dots$$

However, if two or more capacitors are connected in series, as in the second drawing, the total capacitance is less than that of the smallest capacitor in the group. The rule for finding the capacitance of a number of series-connected capacitors is the same as that for finding the resistance of a number of *parallel*-connected resistors. That is,

$$C_{\text{total}} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \frac{1}{C_4} \dots}$$

and, for only two capacitors in series,

$$C_{\text{total}} = \frac{C_1 \times C_2}{C_1 + C_2}$$

The same units must be used throughout; that is, all capacitances must be

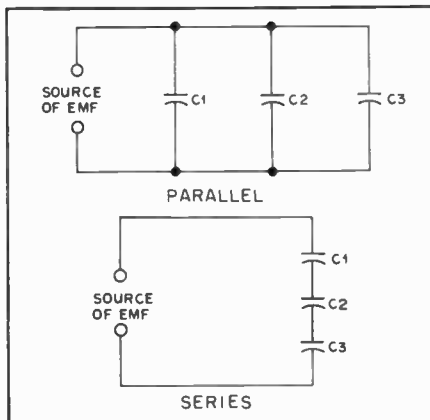


Fig. 16—Capacitors in parallel and in series.

expressed in either  $\mu\text{F}$  or  $\text{pF}$ ; both kinds of units cannot be used in the same equation.

Capacitors are connected in parallel to obtain a larger total capacitance than is available in one unit. The largest voltage that can be applied safely to a group of capacitors in parallel is the voltage that can be applied safely to the one having the *lowest* voltage rating.

When capacitors are connected in series, the applied voltage is divided up among them, the situation is much the same as when resistors are in series and there is a voltage drop across each. However, the voltage that appears across each capacitor of a group connected in series is in *inverse* proportion to its capacitance, as compared with the capacitance of the whole group.

Example: Three capacitors having capacitances of 1, 2 and 4  $\mu\text{F}$ , respectively, are connected in series as shown in Fig 17. The total capacitance is

$$C = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}} = \frac{1}{\frac{1}{1} + \frac{1}{2} + \frac{1}{4}} \\ = \frac{1}{\frac{7}{4}} = \frac{4}{7} = 0.571 \mu\text{F}$$

The voltage across each capacitor is proportional to the *total* capacitance divided by the capacitance of the capacitor in question, so the voltage across  $C_1$  is

$$E_1 = \frac{0.571}{1} \times 2000 = 1142 \text{ volts}$$

Similarly, the voltages across  $C_2$  and  $C_3$  are

$$E_2 = \frac{0.571}{2} \times 2000 = 571 \text{ volts}$$

$$E_3 = \frac{0.571}{4} \times 2000 = 286 \text{ volts}$$

totaling approximately 2000 volts, the applied voltage.

Capacitors are frequently connected in series to enable the group to withstand a larger voltage (at the expense of decreased total capacitance) than any individual capacitor is rated to stand. However, as shown by the previous example, the applied voltages does not divide equally among the capacitors (except when all the capacitances are the same) so care must be taken to see that the voltage rating of no capacitor in the group is exceeded.

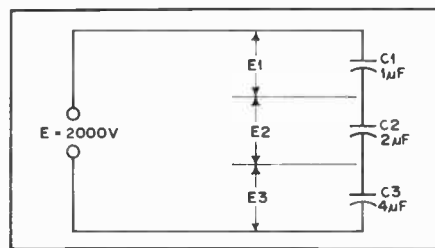


Fig. 17—An example of capacitors connected in series. The solution to this arrangement is worked out in the text.

## Inductance

It is possible to show that the flow of current through a conductor is accompanied by magnetic effects; a compass needle brought near the conductor, for example, will be deflected from its normal north-south position. The current, in other words, sets up a magnetic field.

The transfer of energy to the magnetic field represents work done by the source of emf. Power is required for doing work, and since power is equal to current multiplied by voltage, there must be a voltage drop in the circuit during the time in which energy is being stored in the field.

This voltage "drop" (which has nothing to do with the voltage drop in any resistance in the circuit) is the result of an opposing voltage "induced" in the circuit while the field is building up to its final value. When the field becomes constant the *induced emf* or *back emf* disappears, since no further energy is being stored.

Since the induced emf opposes the emf of the source, it tends to prevent the current from rising rapidly when the circuit is closed. The amplitude of the induced emf is proportional to the rate at which the current is changing and to a

constant associated with the circuit itself, called the *inductance* of the circuit.

Inductance depends on the physical characteristics of the conductor. If the conductor is formed into a coil, for example, its inductance is increased. A coil of many turns will have more inductance than one of few turns, if both coils are otherwise physically similar. Also, if a coil is placed around an iron core its inductance will be greater than it was without the magnetic core.

The polarity of an induced emf is always such as to oppose any change in

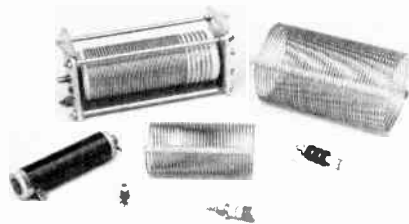


Fig. 18 — Assorted inductors. A rotary (continuously variable) coil is at the upper left. Slug-tuned inductors are visible in the lower foreground. An rf choke (three pi windings) is seen at the lower right.

the current in the circuit. This means that when the current in the circuit is increasing, work is being done against the induced emf by storing energy in the magnetic field. If the current in the circuit tends to decrease, the stored energy of the field returns to the circuit, and thus adds to the energy being supplied by the source of emf. This tends to keep the current flowing even though the applied emf may be decreasing or be removed entirely.

The unit of inductance is the *henry*. Values of inductance used in radio equipment vary over a wide range. Inductance of several henrys is required in power-supply circuits (see chapter on power supplies), and to obtain such values of inductance it is necessary to use coils of many turns wound on iron cores. In radio-frequency circuits, the inductance values used will be measured in *millihenrys* (a mH, one one-thousandth of a henry) at low frequencies, and in *microhenrys* ( $\mu\text{H}$ , one one-millionth of a henry) at medium frequencies and higher. Although coils for radio frequencies may be wound on special iron cores (ordinary iron is not suitable), most rf coils made and used by amateurs are of the "air-core" type; that is, wound on an insulating support consisting of non-magnetic material (Fig. 18).

Every conductor has inductance, even

though the conductor is not formed into a coil. The inductance of a short length of straight wire is small, but it may not be negligible because if the current through it changes its intensity rapidly enough the induced voltage may be appreciable. This will be the case in even a few inches of wire when an alternating current having a frequency of the order of 100 MHz, or higher is flowing. However, at much lower frequencies the inductance of the same wire could be ignored because the induced voltage would be negligibly small.

### Calculating Inductance

The approximate inductance of single-layer air-core coils may be calculated from the simplified formula

$$L (\mu\text{H}) = \frac{a^2 n^2}{9a + 10b}$$

where  $L$  = inductance in microhenrys  
 $a$  = coil radius in inches  
 $b$  = coil length in inches  
 $n$  = number of turns

The notation is explained in Fig. 19. This formula is a close approximation for coils having a length equal to or greater than  $0.8a$ .

Example: Assume a coil having 48 turns wound 32 turns per inch and a diameter of  $3/4$  inch. This  $a = 0.75/2 = 0.375$ ,  $b = 48/32 = 1.5$ , and  $n = 48$ . Substituting,

$$L = \frac{.375 \times .375 \times 48 \times 48}{(9 \times .375) + (10 \times 1.5)} = 17.6 \mu\text{H}$$

To calculate the number of turns of a single-layer coil for a required value of inductance,

$$n = \sqrt{\frac{L(9a + 10b)}{a^2}}$$

Example: Suppose an inductance of  $10 \mu\text{H}$  is required. The form on which the coil is to be wound has a diameter of one inch and is long enough to accommodate a coil of 1-1/4 inches. Then  $a = 0.5$ ,  $b = 1.25$ , and  $L = 10$ . Substituting,

$$n = \sqrt{\frac{10(4.5 + 12.5)}{0.5 \times 0.5}} = \sqrt{680} = 26.1 \text{ turns}$$

A 26-turn coil would be close enough in practical work. Since the coil will be 1.25 inches long, the number of turns per inch will be  $26.1/1.25 = 20.8$ . Consulting the wire table, we find that no. 17 enameled wire (or anything smaller) can be used. The proper inductance is obtained by winding the required number of turns on the form and then adjusting the spacing between the turns to make a uniformly spaced coil 1.25 inches long.

### Inductance Charts

Most inductance formulas lose accuracy when applied to small coils (such as are

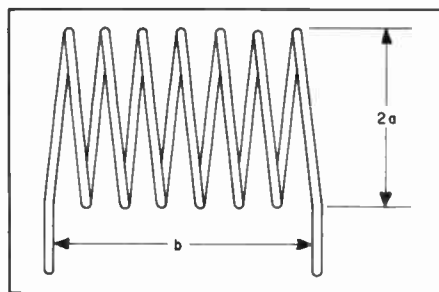


Fig. 19 — Coil dimensions used in the inductance formula. The wire diameter does not enter into the formula.

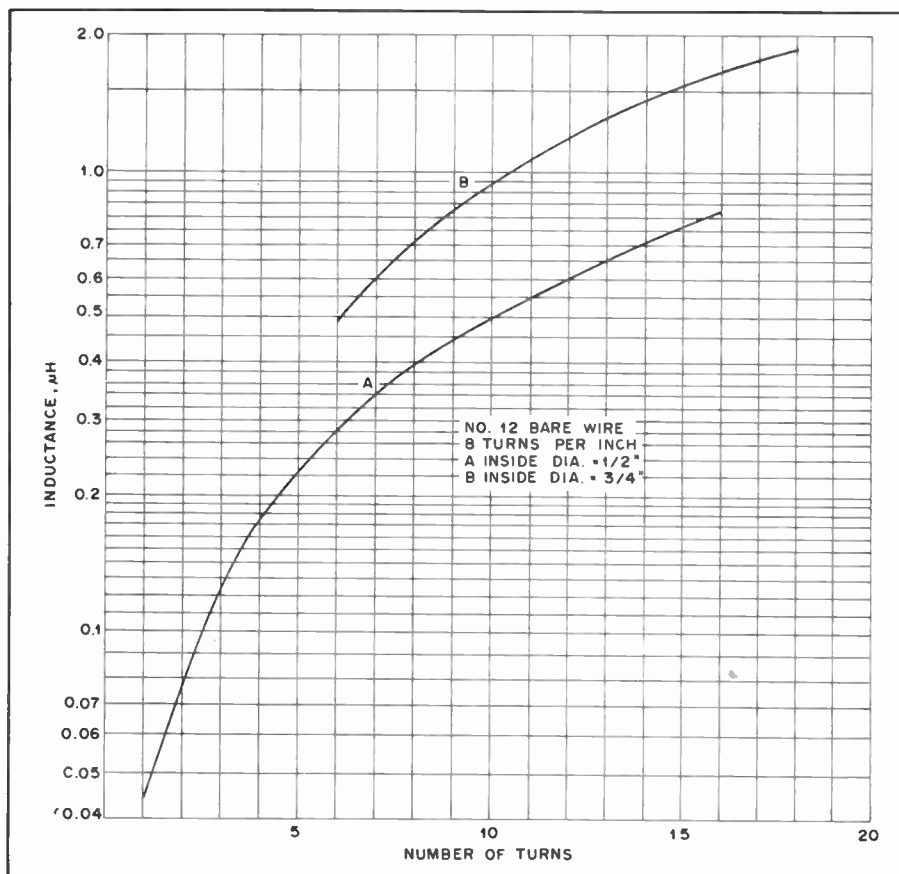


Fig. 20 — Measured inductance of coils wound with no. 12 bare wire, eight turns to the inch. The values include half-inch leads. Inches  $\times 25.4 = \text{mm}$ .



Fig. 21


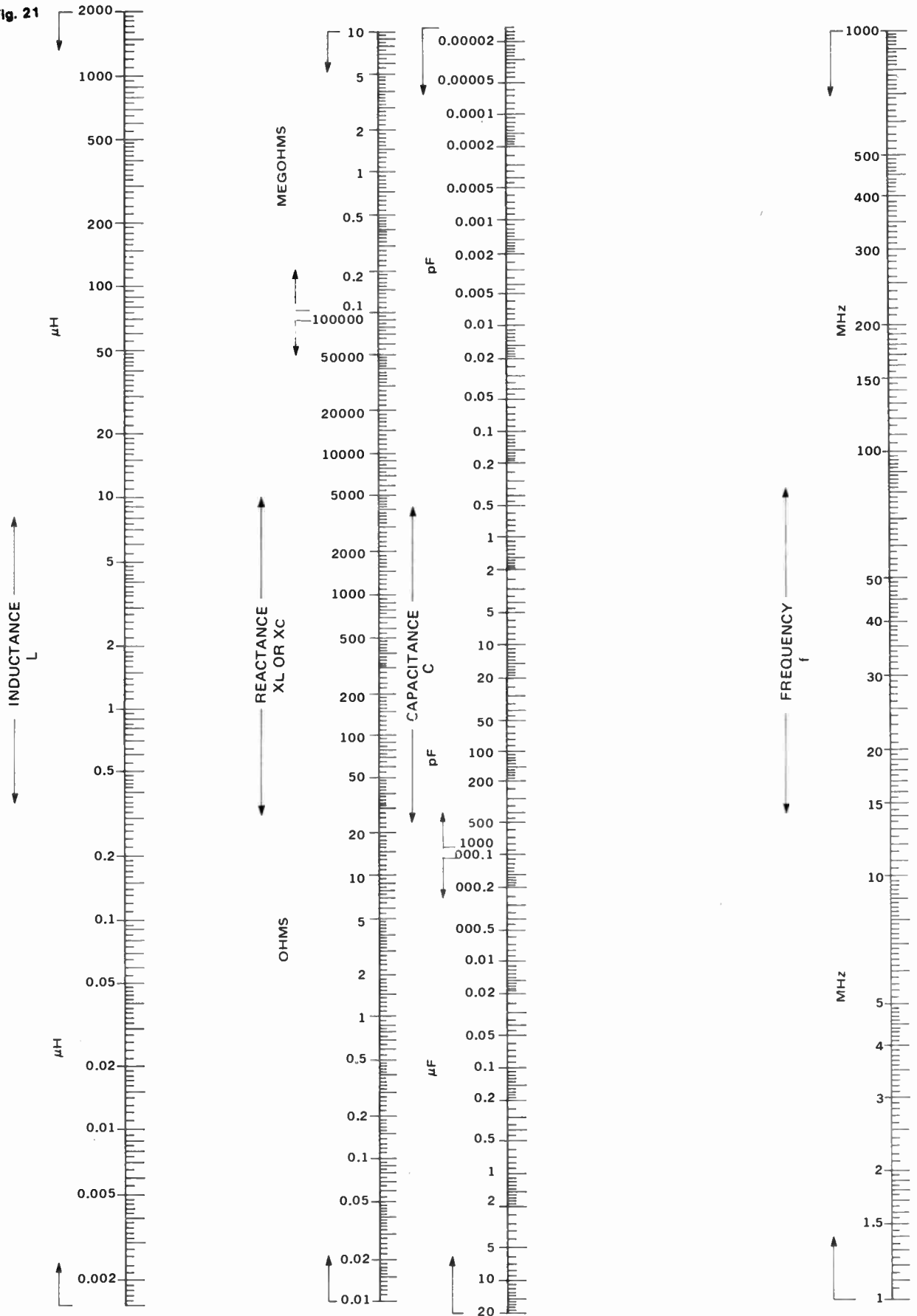


Fig. 22

SINGLE-LAYER WOUND COIL CHART

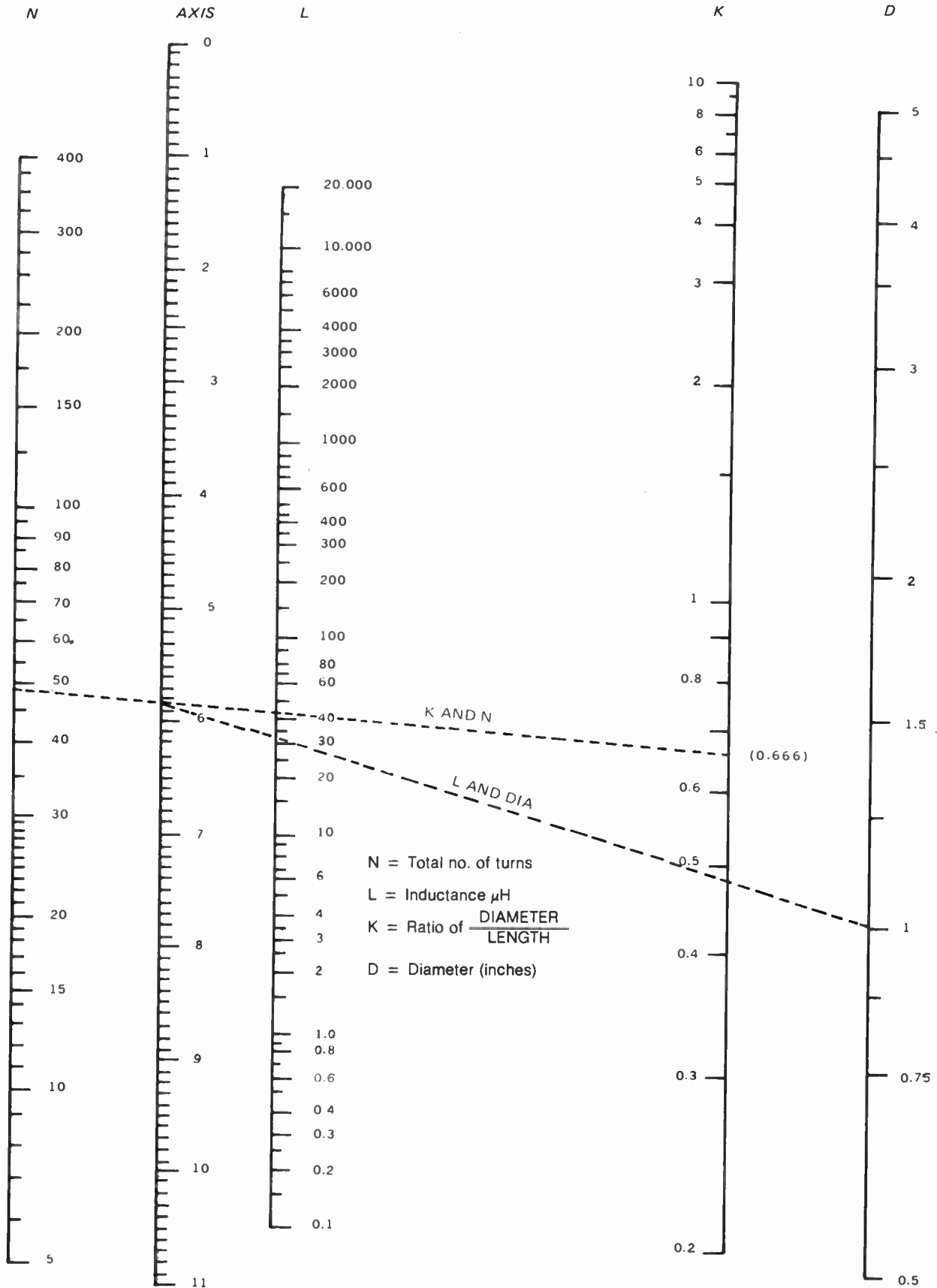

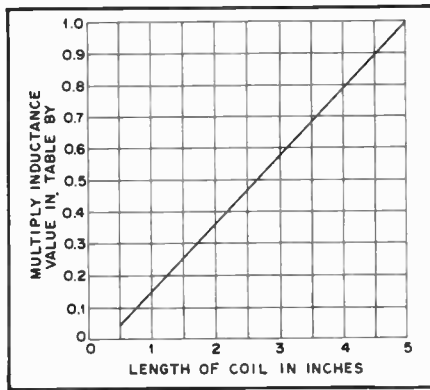


Fig. 23— Factor to be applied to the inductance of coils listed in Table 4 for coil lengths up to five inches.

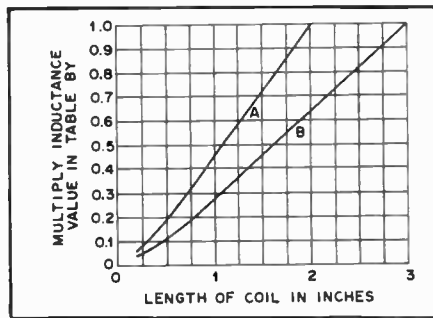


Fig. 24 — Factor to be applied to the inductance of coils listed in Table 5, as a function of coil length. Use curve A for coils marked A, and curve B for coils marked B.

Coil Dia, Inches	No. of Turns Per Inch	Inductance In $\mu\text{H}$
1-1/4	4	2.75
	6	6.3
	8	11.2
	10	17.5
1-1/2	4	3.9
	6	8.8
	8	15.6
	10	24.5
1-3/4	4	5.2
	6	11.8
	8	21
	10	33
2	4	6.6
	6	15
	8	26.5
	10	42
2-1/2	4	6.6
	6	23
	8	41
	10	64
3	4	14
	6	31.5
	8	56
	10	89

Inches  $\times$  25.4 = mm.

used in vhf work and in low-pass filters built for reducing harmonic interference to television) because the conductor thickness is no longer negligible in comparison with the size of the coil. Fig. 20 shows the measured inductance of vhf coils, and may be used as a basis for circuit design. Two curves are given: curve A is for coils wound to an inside diameter of 1/2 inch; curve B is for coils of 3/4 inch inside diameter. In both curves the wire size is no. 12, winding pitch eight turns to the inch (1/8 inch center-to-center turn spacing). The inductance values given include leads 1/2 inch long.

The nomograph of Fig. 21 can be used for fast determination of the inductance of coils, their reactances, the amount of capacitance necessary for resonance, and the capacitive reactance. The frequency range is from 1 to 1000 MHz.

If the coil diameter and winding length are known, the number of wire turns necessary for a specific inductance can be found in the nomograph of Fig. 22. It is necessary also to know how many turns of a given wire gauge will fit in one inch of space, close wound. This information is available from the wire table elsewhere in this handbook.

Machine-wound coils with the diameters and turns per inch given in Tables 4 and 5 are available in many radio stores, under the trade names of "B&W Mini-ductor" and "Polycoils." Figs. 23 and 24 are used with Tables 4 and 5.

### Iron-Core Coils: Permeability

Suppose that the coil in Fig. 25 is wound on an iron core having a cross-sectional area of 2 square inches. When a certain current is sent through the coil it is found that there are 80,000 lines of force in the core. Since the area is two square inches, the flux density is 40,000 lines per square inch. Now suppose that the iron core is removed and the same current is maintained in the coil, and that the flux density without the iron core is found to be 50 lines per square inch. The ratio of the flux density with the given core material to the flux density (with the same coil and same current) with an air core is called the *permeability* of the material. In this case the permeability of the iron is  $40,000/50 = 800$ . The inductance of the coil is increased 800 times by inserting the iron core since, other things being equal, the inductance will be proportional to the magnetic flux through the coil.

The permeability of a magnetic material varies with the flux density. At low flux densities (or with an air core) increasing the current through the coil will cause a proportionate increase in flux, but at very high flux densities, increasing the current may cause no appreciable change in the flux. When this is so, the iron is said to be saturated. Saturation causes a rapid decrease in permeability, because it

decreases the ratio of flux lines to those obtainable with the same current and an air core. Obviously, the inductance of an iron-core inductor is highly dependent upon the current flowing in the coil. In an air-core coil, the inductance is independent of current because air does not saturate.

Iron core coils such as the one sketched in Fig. 25 are used chiefly in power-supply equipment. They usually have direct current flowing through the winding, and the variation in inductance with current is usually undesirable. It may be overcome by keeping the flux density below the saturation point of the iron. This is done by opening the core so that there is a small "air gap," as indicated by the dashed lines. The magnetic "resistance" introduced by such a gap is so large — even though the gap is only a small fraction of an inch — compared with that of the iron that the gap, rather than the iron, controls the flux density. This reduces the inductance, but makes it practically constant regardless of the value of the current.

For radio-frequency work, the losses in iron cores can be reduced to a satisfactory figure by grinding the iron into a powder and then mixing it with a "binder" of insulating material in such a way that the individual iron particles are insulated from each other. By this means cores can be made that will function satisfactorily even through the vhf range — that is, at frequencies up to perhaps 100 MHz. Because a large part of the magnetic path is through a nonmagnetic material, the permeability of the iron is low compared with the values obtained at power-supply frequencies. The core is usually in the form of a "slug" or cylinder which fits inside the insulating form on which the

Table 5

Coil Dia, Inches	No. of Turns Per Inch	Inductance In $\mu\text{H}$
1/2 (A)	4	0.18
	6	0.40
	8	0.72
	10	1.12
	16	2.9
5/8 (A)	32	12
	4	0.28
	6	0.62
	8	1.1
	10	1.7
3/4 (B)	16	4.4
	32	18
	4	0.6
	6	1.35
	8	2.4
1 (B)	10	3.8
	16	9.9
	32	40
	4	1.0
	6	2.3
3/4 (B)	8	4.2
	10	6.6
	16	16.9
	32	68

Inches  $\times$  25.4 = mm.

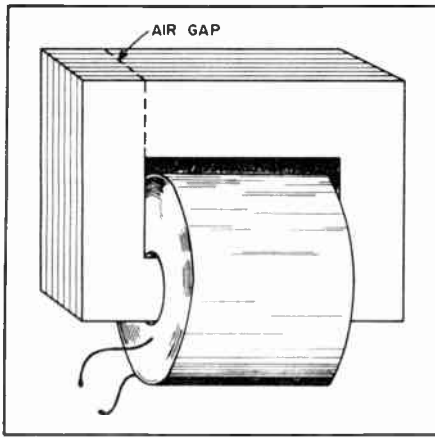


Fig. 25 — Typical construction of an iron-core inductor. The small air gap prevents magnetic saturation of the iron and thus maintains the inductance at high currents.

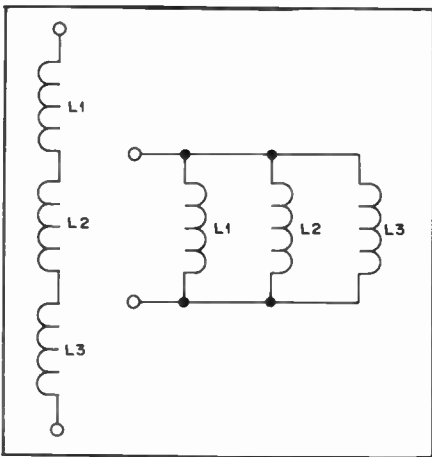


Fig. 26 — Inductances in series and parallel.

coil is wound. Despite the fact that with this construction the major portion of the magnetic path for the flux is in air, the slug is quite effective in increasing the coil inductance. By pushing the slug in and out of the coil, the inductance can be varied over a considerable range.

### Eddy Currents and Hysteresis

When alternating current flows through a coil wound on an iron core an emf will be induced, as previously explained, and since iron is a conductor a current will flow in the core. Such currents (called *eddy currents*) represent a waste of power because they flow through the resistance of the iron and thus cause heating. Eddy-current losses can be reduced by *laminating* the core; that is, by cutting it into thin strips. These strips or *laminations* must be insulated from each other by painting them with some insulating material such as varnish or shellac.

There is also another type of energy loss: The iron tends to resist any change in its magnetic state, so a rapidly-changing current such as ac is forced continually to supply energy to the iron to overcome this "inertia." Losses of this sort are called *hysteresis* losses.

Eddy-current and hysteresis losses in iron increase rapidly as the frequency of the alternating current is increased. For this reason, ordinary iron cores can be used only at power and audio frequencies — up to, say, 15,000 hertz. Even so, a very good grade of iron or steel is necessary if the core is to perform well at the higher audio frequencies. Iron cores of this type

are completely useless at radio frequencies.

### Inductances in Series and Parallel

When two or more inductors are connected in series (Fig. 26) the total inductance is equal to the sum of the individual inductances, *provided the coils are sufficiently separated so that no coil is in the magnetic field of another.*

That is,

$$L_{\text{total}} = L_1 + L_2 + L_3 + L_4 + \dots$$

If inductors are connected in parallel (Fig. 26) — and the coils are separated sufficiently, the total inductance is given by

$$L_{\text{total}} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3} + \frac{1}{L_4} + \dots}$$

and for two inductances in parallel,

$$L = \frac{L_1 \times L_2}{L_1 + L_2}$$

Thus the rules for combining inductances in series and parallel are the same for resistances, if the coils are far enough apart so that each is unaffected by another's magnetic field. When this is not so the formulas given above cannot be used.

### Mutual Inductance

If two coils are arranged with their axes on the same line, as shown in Fig. 27, a current sent through coil 1 will cause a magnetic field which "cuts" coil 2. Consequently, an emf will be induced in coil 2 whenever the field strength is changing. This induced emf is similar to the emf of self-induction, but since it appears in the *second* coil because of current flowing in the *first*, it is a "mutual" effect and results from the *mutual inductance* between the two coils.

If all the flux set up by one coil cuts all the turns of the other coil, the mutual inductance has its maximum possible value. If only a small part of the flux set up by one coil cuts, the turns of the other the mutual inductance is relatively small. Two coils having mutual inductance are said to be *coupled*.

The ratio of actual mutual inductance to the maximum possible value that could theoretically be obtained with two given coils is called the *coefficient of coupling* between the coils. It is frequently expressed as a percentage. Coils that have nearly the maximum possible (coefficient = 1 or 100 percent) mutual inductance are said to be *closely*, or *tightly*, coupled, but if the mutual inductance is relatively small the coils are said to be *loosely* coupled. The degree of coupling depends upon the physical spacing between the coils and how they are placed with respect to each

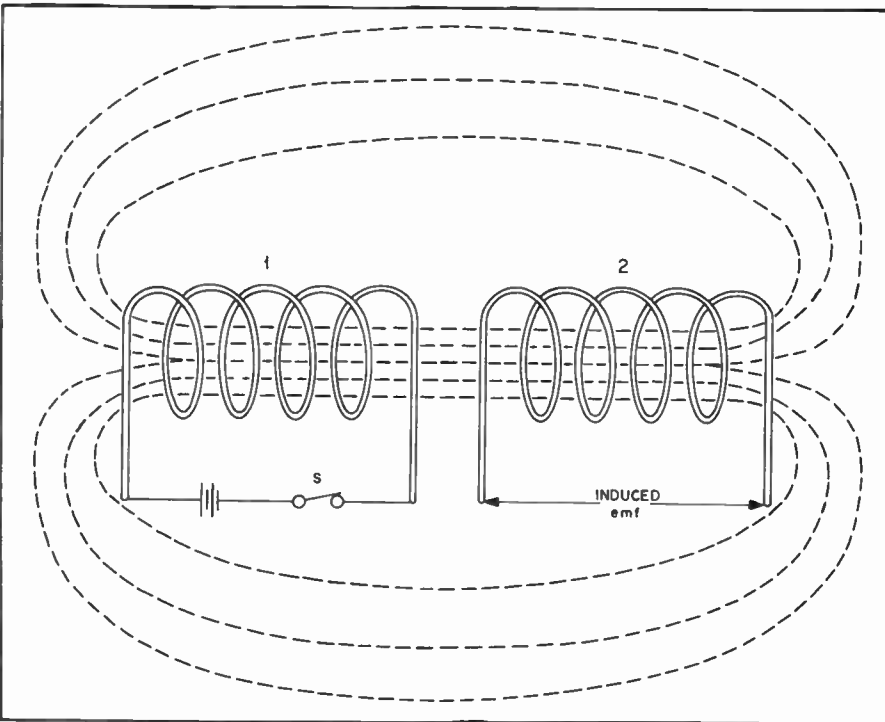


Fig. 27 — Mutual inductance. When the switch, S, is closed current flows through coil no. 1, setting up a magnetic field that induces an emf in the turns of coil no. 2.

other. Maximum coupling exists when they have a common axis and are as close together as possible (one wound over the other). The coupling is least when the coils are far apart or are placed so their axes are at right angles.

The maximum possible coefficient of coupling is closely approached only when the two coils are wound on a closed iron core. The coefficient with air-core coils may run as high as 0.6 or 0.7 if one coil is wound over the other, but will be much less if the two coils are separated.

### Time Constant: Capacitance and Resistance

Connecting a source of emf to a capacitor causes the capacitor to become charged to the full emf practically instantaneously, if there is no resistance in the circuit. However, if the circuit contains resistance, as in Fig. 28A, the resistance limits the current flow and an appreciable length of time is required for the emf between the capacitor plates to build up to the same value as the emf of the source. During this "building-up" period, the current gradually decreases from its initial value, because the increasing emf stored on the capacitor offers increasing opposition to the steady emf of the source.

Theoretically, the charging process is never really finished, but eventually the charging current drops to a value that is smaller than anything that can be measured. The *time constant* of such a circuit is the length of time, in seconds, required for the voltage across the capacitor to reach 63 percent of the applied emf (this figure is chosen for mathematical reasons). The voltage across the capacitor rises with time as shown by Fig. 29.

The formula for time constant is

$$T = RC$$

where  $T$  = time constant in seconds  
 $C$  = capacitance in farads  
 $R$  = resistance in ohms

Example: The time constant of a  $2\text{-}\mu\text{F}$  capacitor and a  $250,000\text{-ohm}$  ( $0.25\text{ M}$ ) resistor is

$$T = RC = 0.25 \times 2 = 0.5 \text{ second}$$

If the applied emf is 1000 volts, the voltage between the capacitor plates will be 630 volts at the end of  $1/2$  second.

If  $C$  is in microfarads and  $R$  in megohms, the time constant also is in seconds. These units usually are more convenient.

If a charged capacitor is *discharged* through a resistor, as indicated in Fig. 28B, the same time constant applies. If there were no resistance, the capacitor would discharge instantly when  $S$  was closed. However, since  $R$  limits the current flow the capacitor voltage cannot

instantly go to zero, but it will decrease just as rapidly as the capacitor can rid itself of its charge through  $R$ . When the capacitor is discharging through a resistance, the time constant (calculated in the same way as above) is the time, in seconds, that it takes for the capacitor to lose 63 percent of its voltage; that is, for the voltage to drop to 37 percent of its initial value.

Example: If the capacitor of the example above is charged to 1000 volts, it will discharge to 370 volts in  $1/2$  second through the  $250\ \Omega$  resistor.

### Inductance and Resistance

A comparable situation exists when resistance and inductance are in series. In Fig. 30, first consider  $L$  to have no resistance and also assume that  $R$  is zero. Then closing  $S$  would tend to send a current through the circuit. However, the instantaneous transition from no current to a finite value, however small, represents a very rapid *change* in current, and a *back emf* is developed by the self-inductance of  $L$  that is practically equal and opposite to the applied emf. The result is that the initial current is very small.

The back emf depends upon the change in current and would cease to offer opposition if the current did not continue to increase. With no resistance in the circuit (which would lead to an infinitely large current, by Ohm's Law) the current would increase forever, always growing self-fast enough to keep the emf of self-induction equal to the applied emf.

When resistance is in series, Ohm's Law sets a limit to the value that the current can reach. The back emf generated in  $L$  has only to equal the difference between  $E$  and the drop across  $R$ , because that difference is the voltage actually applied to  $L$ . This difference becomes smaller as the current approaches the final Ohm's Law value. Theoretically, the back emf never quite disappears and so the current never quite reaches the Ohm's Law value, but practically the differences become unmeasurable after a time. The time constant of an inductive circuit is the time in seconds required for the current to reach 63 percent of its final value. The formula is

$$T = \frac{L}{R}$$

where  $T$  = time constant in seconds  
 $L$  = inductance in henrys  
 $R$  = resistance in ohms.

The resistance of the wire in a coil acts as if it were in series with the inductance.

Example: A coil having an inductance of 20 henrys and a resistance of 100 ohms has a time constant of

$$T = \frac{L}{R} = \frac{20}{100} = 0.2 \text{ second}$$

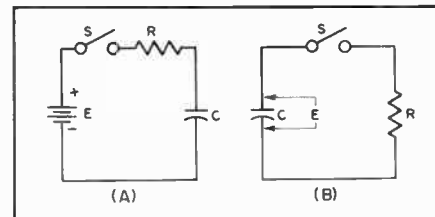


Fig. 28 — Illustrating the time constant of an RC circuit.

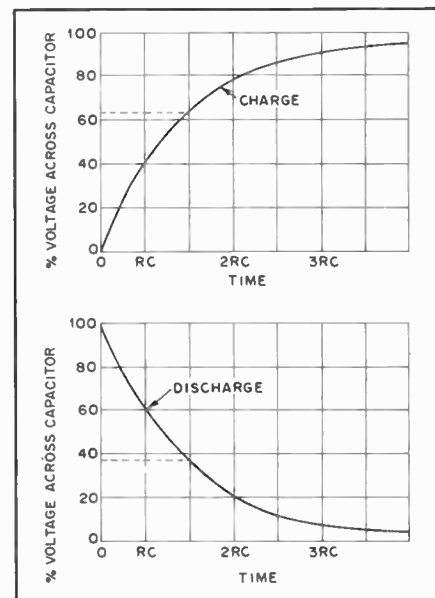


Fig. 29 — How the voltage across a capacitor rises, with time, when charged through a resistor. The lower curve shows the way in which the voltage decreases across the capacitor terminals on discharging through the same resistor.

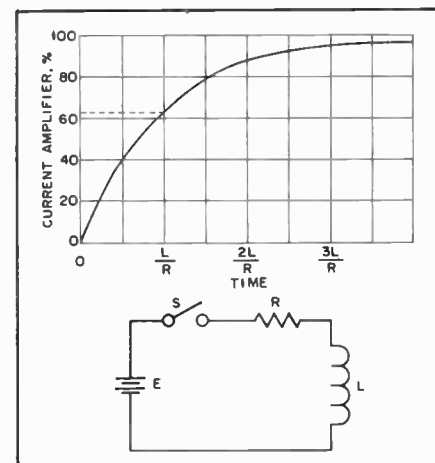


Fig. 30 — Time constant of an LR circuit.

if there is no other resistance in the circuit. If a dc emf of 10 volts is applied to such a coil, the final current, by Ohm's Law, is

$$I = \frac{E}{R} = \frac{10}{100} = 0.1 \text{ amp. or } 100 \text{ mA}$$



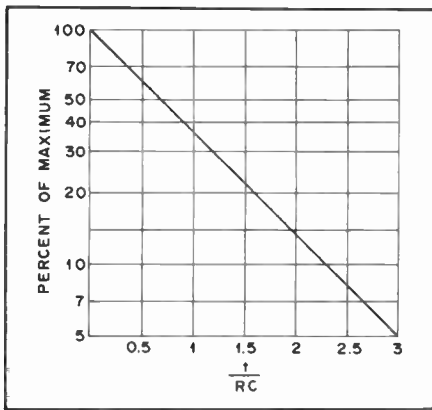


Fig. 31 — Voltage across capacitor terminals in a discharging RC circuit, in terms of the initial charged voltage. To obtain time in seconds, multiply the factor  $t/RC$  by the time constant of the circuit.

The current would rise from 0 to 63 milliamperes in 0.2 second after closing the switch.

An inductor cannot be “discharged” in the same way as a capacitor, because the

magnetic field disappears as soon as current flow ceases. Opening S does not leave the inductor “charged.” The energy stored in the magnetic field instantly returns to the circuit when S is opened. The rapid disappearance of the field causes a very large voltage to be induced in the coil — ordinarily many times larger than the voltage applied, because the induced voltage is proportional to the *speed* with which the field changes. The common result of opening the switch in a circuit such as the one shown is that a spark or arc forms at the switch contacts at the instant of opening. If the inductance is large and the current in the circuit is high, a great deal of energy is released in a very short period of time. It is not at all unusual for the switch contacts to burn or melt under such circumstances. The spark or arc at the opened switch can be reduced or suppressed by connecting a suitable capacitor and resistor in series across the contacts.

Time constants play an important part in numerous devices, such as electronic keys, timing and control circuits, and

shaping of keying characteristics by vacuum tubes. The time constants of circuits are also important in such applications as automatic gain control and noise limiters. In nearly all such applications a resistance-capacitance (RC) time constant is involved, and it is usually necessary to know the voltage across the capacitor at some time interval larger or smaller than the actual time constant of the circuit as given by the formula above. Fig. 31 can be used for the solution of such problems, since the curve gives the voltage across the capacitor, in terms of percentage of the initial charge, for percentages between 5 and 100, at any time after discharge begins.

Example: A  $0.01\text{-}\mu\text{F}$  capacitor is charged to 150 volts and then allowed to discharge through a 0.1-megohm resistor. How long will it take the voltage to fall to 10 volts? In percentage,  $10/150 = 6.7$  percent. From the chart, the factor corresponding to 6.7 percent is 2.7. The time constant of the circuit is equal to  $RC = 0.1 \times 0.01 = 0.001$ . The time is therefore  $2.7 \times 0.001 = 0.0027$  second, or 2.7 milliseconds.

## Alternating Currents

The term phase essentially means “time,” or the *time interval* between the instant when one thing occurs and the instant when a second related thing takes place. The later event is said to *lag* the earlier, while the one that occurs first is said to *lead*. In ac circuits the current amplitude changes continuously, so the concept of phase or time becomes important. Phase can be measured in the ordinary time units, such as the second, but there is a more convenient method: Since each ac cycle occupies exactly the same amount of time as every other cycle of the same frequency, we can use the cycle itself as the time unit. Using the cycle as the time unit makes the specification or measurement of phase independent of the frequency of the current, so long as only one frequency is under con-

sideration at a time. When two or more frequencies are to be considered, as in the case where harmonics are present, the phase measurements are made with respect to the lowest, or fundamental, frequency.

The time interval or “phase difference” under consideration usually will be less than one cycle. Phase difference could be measured in decimal parts of a cycle, but it is more convenient to divide the cycle into 360 parts or *degrees*. A phase degree is therefore  $1/360$  of a cycle. The reason for this choice is that with sine-wave alternating current the value of the current at any instant is proportional to the sine of the angle that corresponds to the number of degrees — that is, length of time — from the instant the cycle began. There is no actual “angle” associated with an alternating current. Fig. 32 should help make this method of measurement clear.

### Measuring Phase

The phase difference between two currents of the same frequency is the time or angle difference between corresponding parts of cycles of the two currents. This is shown in Fig. 33. The current labeled A leads the one marked B by 45 degrees, since A’s cycles begin 45 degrees earlier in time. It is equally correct to say that B lags A by 45 degrees.

Two important special cases are shown in Fig. 34. In the upper drawing B lags 90 degrees behind A; that is, its cycle begins just one-quarter cycle later than that of A.

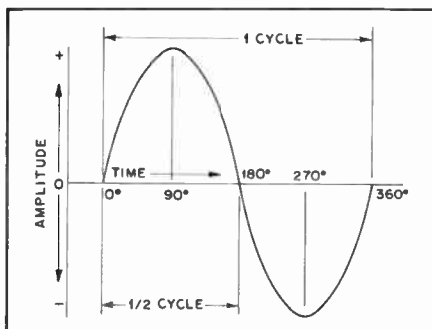


Fig. 32 — An ac cycle is divided off into 360 degrees that are used as a measure of time or phase.

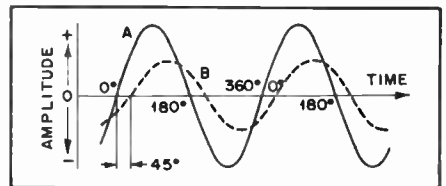


Fig. 33 — When two waves of the same frequency start their cycles at slightly different times, the time difference or phase difference is measured in degrees. In this drawing wave B starts 45 degrees (one-eighth cycle) later than wave A, and so lags 45 degrees behind A.

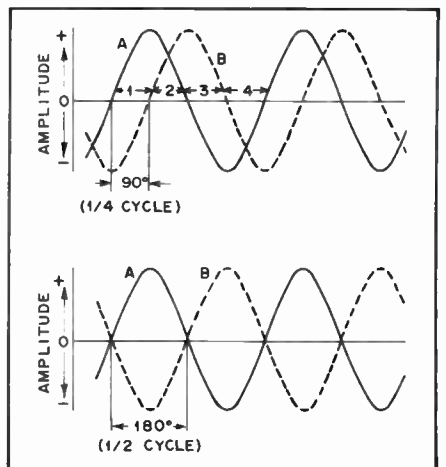


Fig. 34 — Two important special cases of phase difference. In the upper drawing, the phase difference between A and B is 90 degrees; in the lower drawing the phase difference is 180 degrees.

When one wave is passing through zero, the other is just at its maximum point.

In the lower drawing A and B are 180 degrees out of phase. In this case it does not matter which one is considered to lead or lag. B is always positive while A is negative, and vice versa. The two waves are thus *completely* out of phase.

The waves shown in Figs. 34 and 35 could represent current, voltage, or both. A and B might be two currents in separate circuits, or A might represent voltage and B current in the same circuit. If A and B represent two currents in the *same* circuit (or two voltages in the same circuit) the total or *resultant* current (or voltage) also is a sine wave, because adding any number of sine waves of the same frequency always gives a sine wave also of the same frequency.

### Phase in Resistive Circuits

When an alternating voltage is applied to a resistance, the current flows exactly in step with the voltage. In other words, the voltage and current are *in phase*. This is true at any frequency if the resistance is "pure" — that is, is free from the reactive effects discussed in the next section. Practically, it is often difficult to obtain a purely resistive circuit at radio frequencies, because the reactive effects become more pronounced as the frequency is increased.

In a purely resistive circuit, or for purely resistive parts of circuits, Ohm's Law is just as valid for ac of any frequency as it is for dc.

### Reactance: Alternating Current in Capacitance

In Fig. 35 a sine-wave ac voltage having a maximum value of 100 is applied to a capacitor. In the period OA, the applied voltage increases from 0 to 38; at the end of this period the capacitor is charged to

that voltage. In interval AB the voltage increases to 71; that is, 33 volts additional. In this interval a *smaller* quantity of charge has been added than in OA, because the voltage rise during interval AB is smaller. Consequently the average current during AB is smaller than during OA. In the third interval, BC, the voltage rises from 71 to 92, an increase of 21 volts. This is less than the voltage increase during AB, so the quantity of electricity added is less; in other words, the average current during interval BC is still smaller. In the fourth interval, CB, the voltage increases only 8 volts; the charge added is smaller than in any preceding interval and therefore the current also is smaller.

By dividing the first quarter cycle into a very large number of intervals, it could be shown that the current charging the capacitor has the shape of a sine wave, just as the applied voltage does. The current is largest at the beginning of the cycle and becomes zero at the maximum value of the voltage, so there is a phase difference of 90 degrees between the voltage and current. During the first quarter cycle the current is flowing in the normal direction through the circuit, since the capacitor is being charged. Hence the current is positive, as indicated by the dashed line in Fig. 35.

In the second quarter cycle — that is, in the time from D to H, the voltage applied to the capacitor decreases. During this time the capacitor *loses* its charge. Applying the same reasoning, it is plain that the current is small in interval DE and continues to increase during each succeeding interval. However, the current is flowing *against* the applied voltage because the capacitor is discharging into the circuit. The current flows in the *negative* direction during this quarter cycle.

The third and fourth quarter cycles repeat the events of the first and second, respectively, with this difference — the polarity of the applied voltage has reversed, and the current changes to correspond. In other words, an alternating current flows in the circuit because of the alternate charging and discharging of the capacitance. As shown by Fig. 35, the current starts its cycle 90 degrees before the voltage, so the current in a capacitor leads the applied voltage by 90 degrees.

### Capacitive Reactance

The quantity of electric charge that can be placed on a capacitor is proportional to the applied emf and the capacitance. This amount of charge moves back and forth in the circuit once each cycle, and so the *rate* of movement of charge — that is, the current — is proportional to voltage, capacitance and frequency. If the effects of capacitance and frequency are lumped together, they form a quantity that plays a part similar to that of resistance in Ohm's Law. This quantity is called *reactance*, and the unit for it is the ohm, just as in the case of resistance. The formula for it is

$$X_C = \frac{1}{2\pi fC}$$

where  $X_C$  = capacitive reactance in ohms  
 $f$  = frequency in hertz  
 $C$  = capacitance in farads  
 $\pi$  = 3.14

Although the unit of reactance is the ohm, there is no power dissipation in reactance. The energy stored in the capacitor in one quarter of the cycle is simply returned to the circuit in the next.

The fundamental units (cycles per second, farads) are too cumbersome for practical use in radio circuits. However, if the capacitance is in microfarads ( $\mu F$ ) and the frequency is in megahertz (MHz), the reactance will come out in ohms in the formula.

Example: The reactance of a capacitor of 470 pF (0.00047  $\mu F$ ) at a frequency of 7150 kHz (7.15 MHz) is

$$X = \frac{1}{2\pi fC} = \frac{1}{6.28 \times 7.15 \times 0.00047} = 47.4 \text{ ohms}$$

### Inductive Reactance

When an alternating voltage is applied to a *pure* inductance (one with no resistance — all *practical* inductors have resistance) the current is again 90 degrees out of phase with the applied voltage. However, in this case the current *lags* 90 degrees behind the voltage — the opposite of the capacitor current-voltage relationship.

The primary cause for this is the *back emf* generated in the inductance, and since the amplitude of the back emf is proportional to the rate at which the

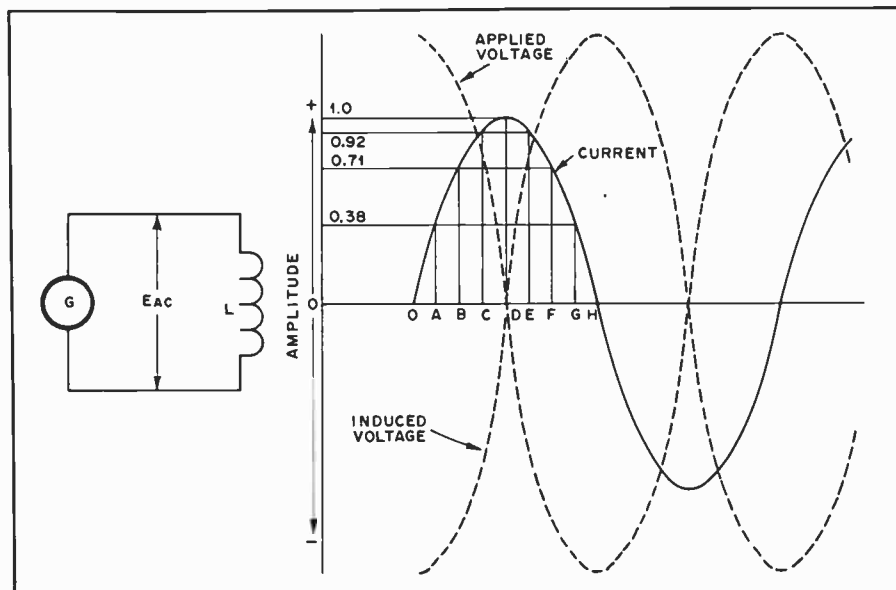


Fig. 35 — Voltage and current phase relationships when an alternating voltage is applied to a capacitor.



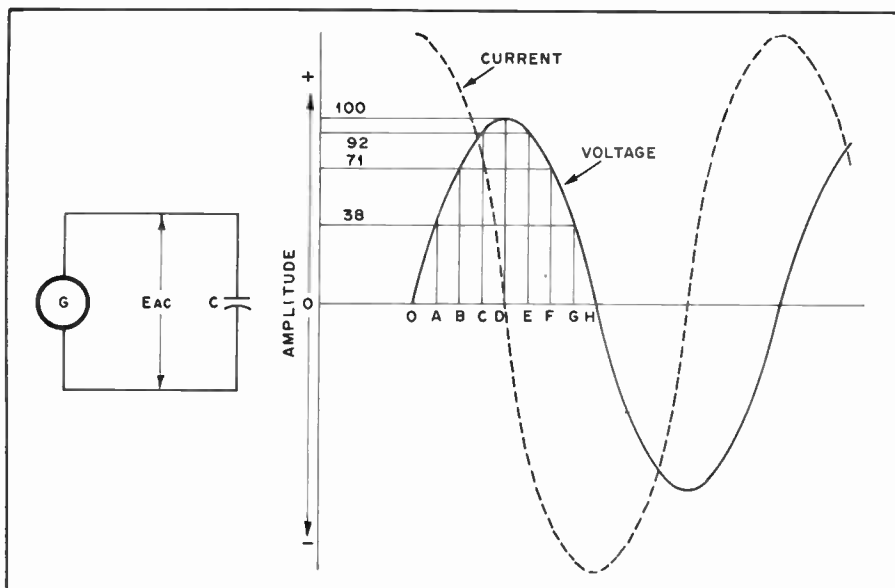


Fig. 36 — Phase relationships between voltage and current when an alternating voltage is applied to an inductance.

current changes, and this in turn is proportional to the frequency, the amplitude of the current is inversely proportional to the applied frequency. Also, since the back emf is proportional to inductance for a given rate of current change, the current flow is inversely proportional to inductance for a given applied voltage and frequency. (Another way of saying this is that just enough current flows to generate an induced emf that equals and opposes the applied voltage.)

The combined effect of inductance and frequency is called *inductive reactance*, also expressed in ohms, and the formula for it is

$$X_L = 2\pi fL$$

where  $X_L$  = inductive reactance in ohms  
 $f$  = frequency in hertz  
 $L$  = inductance in henrys  
 $\pi = 3.14$

Example: The reactance of a 15-microhenry coil at a frequency of 14 MHz is

$$X_L = 2\pi fL = 6.28 \times 14 \times 15 = 1319 \text{ ohms}$$

In radio-frequency circuits the inductance values usually are small and the frequencies are large. If the inductance is expressed in millihenrys and the frequency in kilohertz, the conversion factors for the two units cancel, and the formula for reactance may be used without first converting to fundamental units. Similarly, no conversion is necessary if the inductance is in microhenrys and the frequency is in megahertz.

Example: The reactance of a coil having an inductance of 8 henrys, at a frequency of 125 hertz, is

$$X_L = 2\pi fL = 6.28 \times 120 \times 8 = 6029 \text{ ohms}$$

The resistance of the wire of which the coil is wound has no effect on the reactance, but simply acts as though it were a separate resistor connected in series with the coil.

#### Ohm's Law for Reactance

Ohm's Law for an ac circuit containing *only* reactance is

$$I = \frac{E}{X}$$

$$E = IX$$

$$X = \frac{E}{I}$$

where  $E$  = emf in volts  
 $I$  = current in amperes  
 $X$  = reactance in ohms

The reactance in the circuit may, of course, be either inductive or capacitive.

Example: If a current of 2 amperes is flowing through the capacitor of the earlier example (reactance = 47.4 ohms) at 7150 kHz, the voltage drop across the capacitor is

$$E = IX = 2 \times 47.4 = 94.8 \text{ volts}$$

If 400 volts at 120 hertz is applied to the 8-henry inductor of the earlier example, the current through the coil will be

$$I = \frac{E}{X} = \frac{420}{6029} = 0.697 \text{ A} = 69.7 \text{ mA}$$

#### Reactance Chart

The accompanying chart, Fig. 37, shows the reactance of capacitances from 1 pF to 100  $\mu$ F, and the reactance of

inductances from 0.1  $\mu$ H to 10 henrys, for frequencies between 100 hertz and 100 megahertz. The approximate value of reactance can be read from the chart or, where more exact values are needed, the chart will serve as a check on the order of magnitude of reactances calculated from the formulas given above, and thus avoid "decimal-point errors."

#### Reactances in Series and Parallel

When reactances of the same kind are connected in series or parallel the resultant reactance is that of the resultant inductance or capacitance. This leads to the same rules that are used when determining the resultant resistance when resistors are combined. That is, for series reactances of the same kind the resultant reactance is

$$X = X_1 + X_2 + X_3 + X_4$$

and for reactances of the same kind in parallel the resultant is

$$X = \frac{1}{\frac{1}{X_1} + \frac{1}{X_2} + \frac{1}{X_3} + \frac{1}{X_4}}$$

or for two in parallel,

$$X = \frac{X_1 \times X_2}{X_1 + X_2}$$

The situation is different when reactances of opposite kinds are combined. Since the current in a capacitance leads the applied voltage by 90 degrees and the current in an inductance lags the applied voltage by 90 degrees, the voltages at the terminals of opposite types of reactance are 180 degrees out of phase in a series circuit (in which the current has to be the same through all elements), and the currents in reactances of opposite types are 180 degrees out of phase in a parallel circuit (in which the same voltage is applied to all elements). The 180-degree phase relationship means that the currents or voltages are of opposite polarity, so in the series circuit of Fig. 38A the voltage  $E_L$  across the inductive reactance  $X_L$  is of opposite polarity to the voltage  $E_C$  across the capacitive reactance  $X_C$ . Thus if we call  $X_L$  "positive" and  $X_C$  "negative" (a common convention) the applied voltage  $E_{AC}$  is  $E_L - E_C$ . In the parallel circuit at B the total current,  $I$ , is equal to  $I_L - I_C$ , since the currents are 180 degrees out of phase.

In the series case, therefore, the resultant reactance of  $X_L$  and  $X_C$  is

$$X = X_L - X_C$$

and in the parallel case (Fig. 38B),

$$X = \frac{-X_L X_C}{X_L - X_C}$$

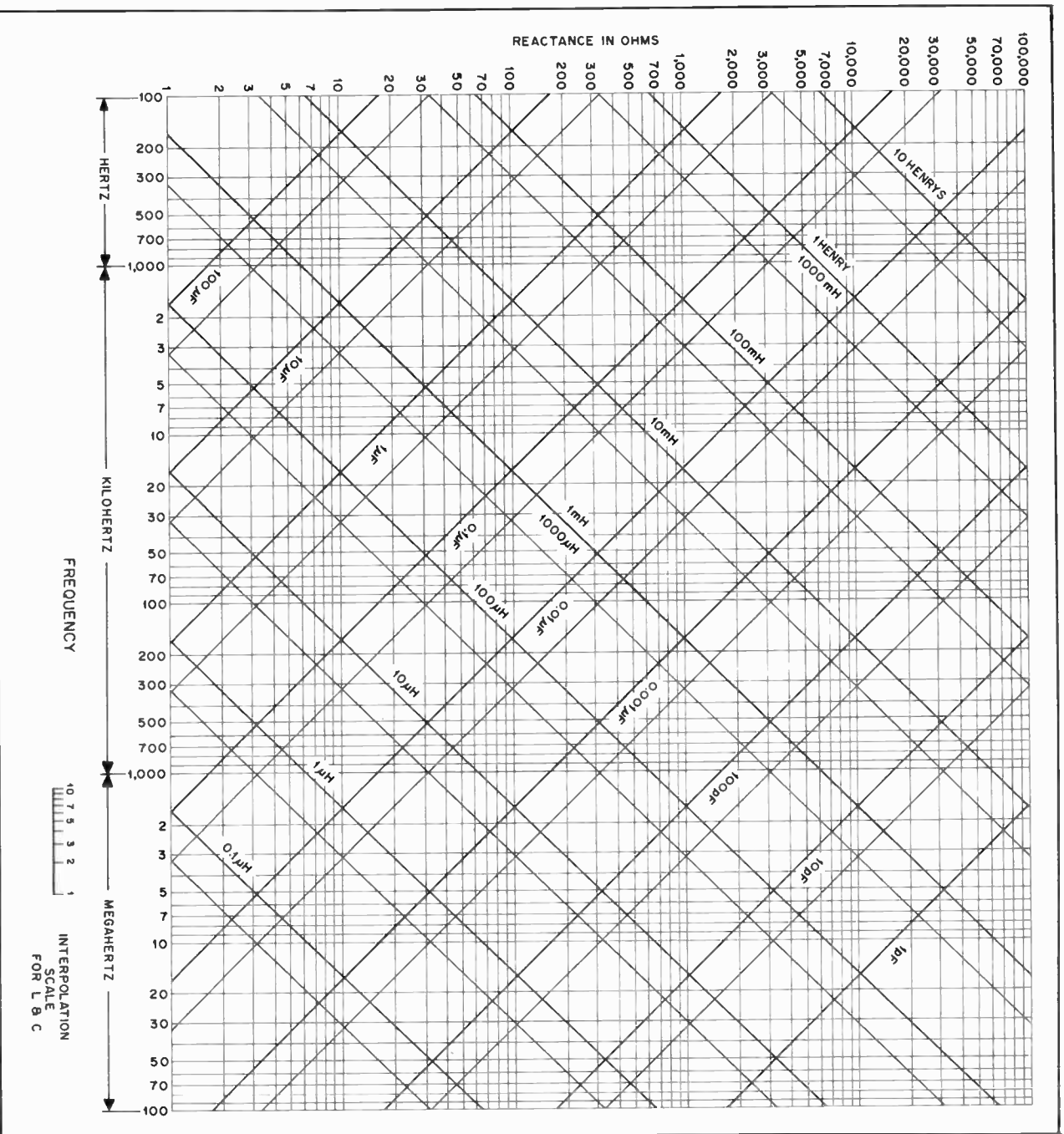


Fig. 37 — Inductive and capacitive reactance vs. frequency. Heavy lines represent multiples of 10, intermediate light lines multiples of five; e.g., the light line between 10  $\mu\text{H}$  and 100  $\mu\text{H}$  represents 50  $\mu\text{H}$ , the light line between 0.1  $\mu\text{F}$  and 1  $\mu\text{F}$  represents 0.5  $\mu\text{F}$ , etc. Intermediate values can be estimated with the help of the interpolation scale. Reactances outside the range of the chart may be found by applying appropriate factors to values within the chart range. For example, the reactance of 10 henrys at 60 Hz can be found by taking the reactance to 10 henrys at 600 Hz and dividing by 10 for the 10-times decrease in frequency.

Note that in the series circuit the total reactance is negative if  $X_C$  is larger than  $X_L$ ; this indicates that the total reactance is capacitive in such a case. The resultant reactance in a series circuit is always smaller than the larger of the two individual reactances.

In the parallel circuit, the resultant reactance is negative (i.e., capacitive) if  $X_L$  is larger than  $X_C$ , and positive (inductive) if  $X_L$  is smaller than  $X_C$ , but in every case is always larger than the smaller of the two individual reactances.

In the special case where  $X_L = X_C$ , the total reactance is zero in the series circuit

and infinitely large in the parallel circuit.

### Reactive Power

In Fig. 38A the voltage drop across the inductor is larger than the voltage applied to the circuit. This might seem to be an impossible condition, but it is not; the explanation is that while energy is being stored in the inductor's magnetic field, energy is being returned to the circuit from the capacitor's electric field, and vice versa. This stored energy is responsible for the fact that the voltages across reactances in series can be larger than the voltage applied to them.

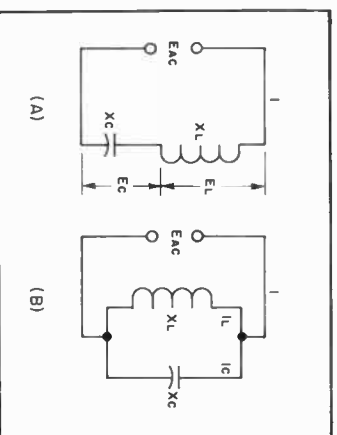


Fig. 38 — Series and parallel circuits containing opposite kinds of reactance.

In a resistance the flow of current causes heating and a power loss equal to  $I^2R$ . The power in a reactance is equal to  $I^2X$ , but is not a "loss"; it is simply power that is transferred back and forth between the field and the circuit but not used up in heating anything. To distinguish this "nondissipated" power from the power which is actually consumed, the unit of reactive power is called the *volt-ampere-reactive*, or *var*, instead of the watt. Reactive power is sometimes called "wattless" power.

### Impedance

When a circuit contains both resistance and reactance the combined effect of the two is called *impedance*, symbolized by the letter *Z*. (Impedance is thus a more general term than either resistance or reactance, and is frequently used even for circuits that have only resistance or reactance although usually with a qualification — such as "resistive impedance" to indicate that the circuit has only resistance, for example.)

The reactance and resistance comprising an impedance may be connected either in series or in parallel, as shown in Fig. 39. In these circuits the reactance is shown as a box to indicate that it may be either inductive or capacitive. In the series circuit the current is the same in both elements, with (generally) different voltages appearing across the resistance and reactance. In the parallel circuit the same voltage is applied to both elements, but different currents flow in the two branches.

Since in a resistance the current is in

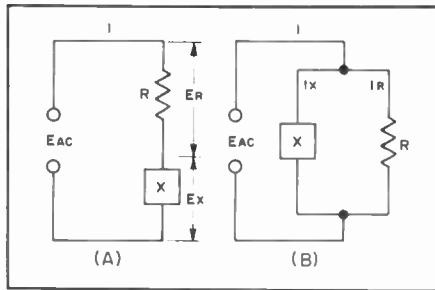


Fig. 39 — Series and parallel circuits containing resistance and reactance.

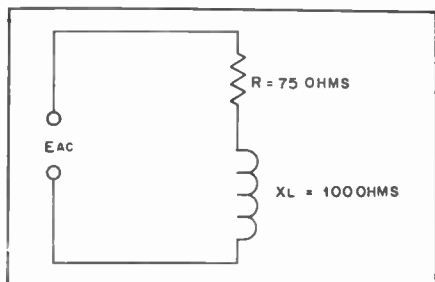


Fig. 40 — Circuit used as an example for impedance calculations.

phase with the applied voltage while in a reactance it is 90 degrees out of phase with the voltage, the phase relationship between current and voltage in the circuit as a whole may be anything between zero and 90 degrees, depending on the relative amounts of resistance and reactance.

### Series Circuits

When resistance and reactance are in series, the impedance of the circuit is

$$Z = \sqrt{R^2 + X^2}$$

where *Z* = impedance in ohms  
*R* = resistance in ohms  
*X* = reactance in ohms

The reactance may be either capacitive or inductive. If there are two or more reactances in the circuit they may be combined into a resultant by the rules previously given, before substitution into the formula above; similarly for resistances.

The "square root of the sum of the squares" rule for finding impedance in a series circuit arises from the fact that the voltage drops across the resistance and reactance are 90 degrees out of phase, and so combine by the same rule that applies in finding the hypotenuse of a right-angled triangle when the base and altitude are known.

### Parallel Circuits

With resistance and reactance in parallel, as in Fig. 39B, the impedance is

$$Z = \frac{RX}{\sqrt{R^2 + X^2}}$$

where the symbols have the same meaning as for series circuits.

Just as in the case of series circuits, a number of reactances in parallel should be combined to find the resultant reactance before substitution into the formula above; similarly for a number of resistances in parallel.

### Equivalent Series and Parallel Circuits

The two circuits shown in Fig. 39 are equivalent if the same current flows when a given voltage of the same frequency is applied, and if the phase angle between voltage and current is the same in both cases. It is in fact possible to "transform" any given series circuit into an equivalent parallel circuit, and vice versa.

Transformations of this type often lead to simplification in the solution of complicated circuits. However, from the standpoint of practical work the usefulness of such transformations lies in the fact that the impedance of a circuit may be modified by the addition of *either* series or parallel elements, depending on which happens to be most convenient in the particular case. Typical applications are

considered later in connection with tuned circuits and transmission lines.

### Ohm's Law for Impedance

Ohm's Law can be applied to circuits containing impedance just as readily as to circuits having resistance or reactance only. The formulas are

$$I = \frac{E}{Z}$$

$$E = IZ$$

$$Z = \frac{E}{I}$$

where *E* = emf in volts  
*I* = current in amperes  
*Z* = impedance in ohms

Fig. 40 shows a simple circuit consisting of a resistance of 75 ohms and a reactance of 100 ohms in series. From the formula previously given, the impedance is

$$Z = \sqrt{R^2 + X_L^2} \\ = \sqrt{(75)^2 + (100)^2} = 125$$

If the applied voltage is 250, then

$$I = \frac{E}{Z} = \frac{250}{125} = 2 \text{ amperes}$$

This current flows through both the resistance and reactance, so the voltage drops are

$$E_R = IR = 2 \times 75 = 150 \text{ volts} \\ E_X = IX_L = 2 \times 100 = 200 \text{ volts}$$

The simple arithmetical sum of these two drops, 350 volts, is greater than the applied voltage because the two voltages are 90 degrees out of phase. Their actual resultant, when phase is taken into account, is

$$\sqrt{(150)^2 + (200)^2} = 250 \text{ volts}$$

### Power Factor

In the circuit of Fig. 40 an applied emf of 250 volts results in a current of 2 amperes, giving an apparent power of  $250 \times 2 = 500$  watts. However, only the resistance actually consumes power. The power in the resistance is

$$P = I^2R = (2)^2 \times 75 = 300 \text{ watts}$$

The ratio of the power consumed to the apparent power is called the *power factor* of the circuit, and in this example the power factor would be  $300/500 = 0.6$ . Power factor is frequently expressed as a percentage; in this case, it would be 60 percent.

"Real" or dissipated power is measured in watts; apparent power, to distinguish it from real power, is measured in volt-amperes. It is simply the product of volts and amperes and has no direct relation-



ship to the power actually used up or dissipated unless the power factor of the circuit is known. The power factor of a purely resistive circuit is 100 percent or 1, while the power factor of a pure reactance is zero. In this illustration, the reactive power is

$$\begin{aligned} \text{VAR} &= I^2 X = (2)^2 \times 100 \\ &= 400 \text{ volt-amperes} \end{aligned}$$

### Reactance and Complex Waves

It was pointed out earlier in this chapter that a complex wave (a "nonsinusoidal" wave) can be resolved into a fundamental frequency and a series of harmonic frequencies. When such a complex voltage wave is applied to a circuit containing

reactance, the current through the circuit will not have the same wave shape as the applied voltage. This is because the reactance of an inductor and capacitor depend upon the applied frequency. For the second-harmonic component of a complex wave, the reactance of the inductor is twice and the reactance of the capacitor one-half their respective values at the fundamental frequency; for the third harmonic the inductor reactance is three times and the capacitor reactance one-third, and so on. Thus the circuit impedance is different for each harmonic component.

Just what happens to the current wave shape depends upon the values of resistance and reactance involved and how the circuit is arranged. In a simple circuit with resistance and inductive

reactance in series, the amplitudes of the harmonic currents will be reduced because the inductive reactance increases in proportion to frequency. When capacitance and resistance are in series, the harmonic current is likely to be accentuated because the capacitive reactance becomes lower as the frequency is raised. When both inductive and capacitive reactance are present the shape of the current wave can be altered in a variety of ways, depending upon the circuit and the "constants," or the relative values of L, C and R, selected.

This property of nonuniform behavior with respect to fundamental and harmonics is an extremely useful one. It is the basis of "filtering," or the suppression of undesired frequencies in favor of a single desired frequency or group of such frequencies.

## Transformers

Two coils having mutual inductance constitute a *transformer*. The coil connected to the source of energy is called the *primary* coil, and the other is called the *secondary* coil.

The usefulness of the transformer lies in the fact that electrical energy can be transferred from one circuit to another without direct connection, and in the process can be readily changed from one voltage level to another. Thus, if a device to be operated requires, for example, 7 volts ac and only a 440-volt source is available, a transformer can be used to change the source voltage to that required. A transformer can be used only with ac, since no voltage will be induced in the secondary if the magnetic field is not changing. If dc is applied to the primary of a transformer, a voltage will be induced in the secondary only at the instant of closing or opening the primary circuit, since it is only at these times that the field is changing.

### The Iron-Core Transformer

As shown in Fig. 41, the primary and secondary coils of a transformer may be wound on a core of magnetic material. This increases the inductance of the coils so that a relatively small number of turns may be used to induce a given value of voltage with a small current. A *closed core* (one having a continuous magnetic path) such as that shown in Fig. 41 also tends to insure that practically all of the field set up by the current in the primary coil will cut the turns of the secondary coil. However, the core introduces a power loss because of hysteresis and eddy currents, so this type of construction is normally practicable only at power and audio frequencies. The discussion in this section

is confined to transformers operating at such frequencies.

### Voltage and Turns Ratio

For a given varying magnetic field, the voltage induced in a coil in the field will be proportional to the number of turns in the coil. If the two coils of a transformer are in the same field (which is the case when both are wound on the same closed core) it follows that the induced voltages will be proportional to the number of turns in each coil. In the primary the induced voltage is practically equal to, and opposes, the applied voltage, as described earlier. Hence,

$$E_s = \left( \frac{n_s}{n_p} \right) E_p$$

where  $E_s$  = secondary voltage

$E_p$  = primary applied voltage

$n_s$  = number of turns on secondary

$n_p$  = number of turns on primary

The ratio,  $n_s/n_p$  is called the secondary-to-primary *turns ratio* of the transformer.

Example: A transformer has a primary of 400 turns and a secondary of 2800 turns, and an emf of 117 volts is applied to the primary.

$$\begin{aligned} E_s &= \left( \frac{n_s}{n_p} \right) E_p = \frac{2800}{400} \times 117 = 7 \times 117 \\ &= 819 \text{ volts} \end{aligned}$$

Also, if an emf of 819 volts is applied to the 2800-turn winding (which then becomes the primary) the output voltage from the 400-turn winding will be 117 volts.

Either winding of a transformer can be

used as the primary, providing the winding has enough turns (enough inductance) to induce a voltage equal to the applied voltage without requiring an excessive current flow.

### Effect of Secondary Current

The current that flows in the primary when no current is taken from the secondary is called the *magnetizing current* of the transformer. In any properly designed transformer the primary inductance will be so large that the magnetizing current will be quite small. The power consumed by the transformer when the secondary is "open" — that is, not delivering power — is only the amount necessary to supply the losses in the iron core and in the resistance of the wire with which the primary is wound.

When power is taken from the secondary winding, the secondary current sets

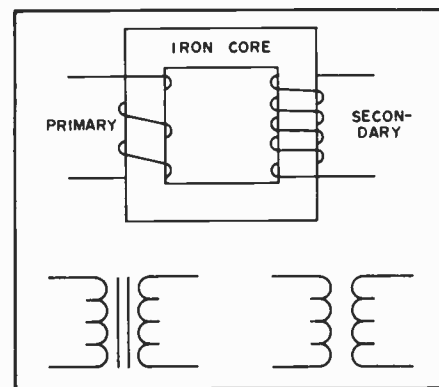


Fig. 41 — The transformer. Power is transferred from the primary coil to the secondary by means of the magnetic field. The upper symbol at right indicates an iron-core transformer, the lower one an air-core transformer.



up a magnetic field that opposes the field set up by the primary current. But if the induced voltage in the primary is to equal the applied voltage, the original field must be maintained. Consequently, the primary must draw enough additional current to set up a field exactly equal and opposite to the field set up by the secondary current.

In practical calculations on transformers it may be assumed that the entire primary current is caused by the secondary "load." This is justifiable because the magnetizing current should be very small in comparison with the primary "load" current at rated power output.

If the magnetic fields set up by the primary and secondary currents are to be equal, the primary current multiplied by the primary turns must equal the secondary current multiplied by the secondary turns. From this it follows that

$$I_p = \left( \frac{n_s}{n_p} \right) I_s$$

where  $I_p$  = primary current  
 $I_s$  = secondary current  
 $n_p$  = number of turns on primary  
 $n_s$  = number of turns on secondary

Example: Suppose that the secondary of the transformer in the previous example is delivering a current of 0.2 ampere to a load. Then the primary current will be

$$I_p = \left( \frac{n_s}{n_p} \right) I_s = \frac{2800}{400} \times 0.2 = 7 \times 0.2 = 1.4 \text{ ampere}$$

Although the secondary voltage is higher than the primary voltage, the secondary current is lower than the primary current, and by the same ratio.

#### Power Relationships; Efficiency

A transformer cannot create power; it can only transfer it and change the emf. Hence, the power taken from the secondary cannot exceed that taken by the primary from the source of applied emf. There is always some power loss in the resistance of the coils and in the iron core, so in all practical cases the power taken from the source will exceed that taken from the secondary. Thus,

$$P_o = nP_i$$

where  $P_o$  = power output from secondary  
 $P_i$  = power input to primary  
 $n$  = efficiency factor

The efficiency,  $n$ , always is less than 1. It is usually expressed as a percentage; if  $n$  is 0.65, for instances, the efficiency is 65 percent.

Example: A transformer has an efficiency of 85 percent as its full-load output of 150 watts. The power input to the primary at full secondary load will be

$$P_i = \frac{P_o}{n} = \frac{150}{0.85} = 176.5 \text{ watts}$$

A transformer is usually designed to have the highest efficiency at the power output for which it is rated. The efficiency decreases with either lower or higher outputs. On the other hand, the losses in the transformer are relatively small at low output but increase as more power is taken. The amount of power that the transformer can handle is determined by its own losses, because these heat the wire and core. There is a limit to the temperature rise that can be tolerated, because a too-high temperature either will melt the wire or cause the insulation to break down. A transformer can be operated at reduced output, even though the efficiency is low, because the actual loss will be low under such conditions.

The full-load efficiency of small power transformers such as are used in radio receivers and transmitters usually lies between about 60 and 90 percent, depending upon the size and design.

#### Leakage Reactance

In a practical transformer not all of the magnetic flux is common to both windings, although in well-designed transformers the amount of flux that "cuts" one coil and not the other is only a small percentage of the total flux. This leakage flux causes an emf of self-induction; consequently, there are small amounts of leakage inductance associated with both windings of the transformer. Leakage inductance acts in exactly the same way as an equivalent amount of ordinary inductance inserted in series with the circuit. It has, therefore, a certain reactance, depending upon the amount of leakage inductance and the frequency. This reactance is called leakage reactance.

Current flowing through the leakage reactance causes a voltage drop. This voltage drop increases with increasing current, hence it increases as more power is taken from the secondary. Thus, the greater the secondary current, the smaller the secondary terminal voltage becomes. The resistances of the transformer windings also cause voltage drops when current is flowing; although these voltage drops are not in phase with those caused

by leakage reactance, together they result in a lower secondary voltage under load than is indicated by the turns ratio of the transformer.

At power frequencies (60 Hz) the voltage at the secondary, with a reasonable well-designed transformer, should not drop more than about 10 percent from open-circuit conditions to full load. The drop in voltage may be considerably more than this in a transformer operating at audio frequencies because the leakage reactance increases directly with the frequency.

#### Impedance Ratio

In an ideal transformer — one without losses or leakage reactance — the following relationship is true:

$$Z_p = Z_s \left[ \frac{N_p}{N_s} \right]^2$$

where  $Z_p$  = impedance looking into primary terminals from source of power

$Z_s$  = impedance of load connected to secondary

$N_p/N_s$  = turns ratio, primary to secondary

That is, a load of any given impedance connected to the secondary of the transformer will be transformed to a different value "looking into" the primary from the source of power. The impedance transformation is proportional to the square of the primary-to-secondary turns ratio.

Example: A transformer has a primary-to-secondary turns ratio of 0.6 (primary has 6/10 as many turns as the secondary) and a load of 3000 ohms is connected to the secondary. The impedance looking into the primary then will be

$$Z_p = Z_s \left[ \frac{N_p}{N_s} \right]^2 = 3000 \times (0.6)^2 = 3000 \times 0.36 = 1080 \text{ ohms}$$

By choosing the proper turns ratio, the impedance of a fixed load can be transformed to any desired value, within practical limits. If transformer losses can be neglected, the transformed or "reflected" impedance has the same phase angle as

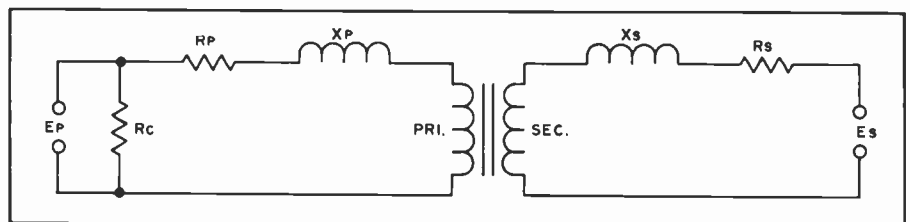


Fig. 42 — The equivalent circuit of a transformer includes the effects of leakage inductance and resistance of both primary and secondary windings. The resistance  $R_c$  is an equivalent resistance representing the core losses, which are essentially constant for any given applied voltage and frequency. Since these are comparatively small, their effect may be neglected in many approximate calculations.

the actual load impedance; thus, if the load is a pure resistance, the load presented by the primary to the source of power also will be a pure resistance.

The above relationship may be used in practical work even though it is based on an "ideal" transformer. Aside from the normal design requirements of reasonably

low internal losses and low leakage reactance, the only requirement is that the primary have enough inductance to operate with low magnetizing current at the voltage applied to the primary.

The primary impedance of a transformer — as it appears to the source of power — is determined wholly by the load connected to the secondary and by the turns ratio. If the characteristics of the transformer have an appreciable effect on the impedance presented to the power source, the transformer is either poorly designed or is not suited to the voltage and frequency at which it is being used. Most transformers will operate quite well at voltages from slightly above to well below the design figure.

### Impedance Matching

Many devices require a specific value of load resistance (or impedance) for optimum operation. The impedance of the actual load that is to dissipate the power may differ widely from this value, so a transformer is used to change the actual load into an impedance of the desired value. This is called *impedance matching*. From the preceding,

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}}$$

where

$N_p/N_s$  = required turns ratio, primary to secondary

$Z_p$  = primary impedance required

$Z_s$  = impedance of load connected to secondary

Example: A vacuum-tube af amplifier requires a load of 5000 ohms for optimum performance, and is to be connected to a loudspeaker having an impedance of 10 ohms. The turns ratio, primary to secondary, required in the coupling transformer is

$$\frac{N_p}{N_s} = \sqrt{\frac{Z_p}{Z_s}} = \sqrt{\frac{5000}{10}} = \sqrt{500} = 22.4$$

The primary therefore must have 22.4 times as many turns as the secondary.

Impedance matching means, in general, adjusting the load impedance — by means of a transformer or otherwise — to a desired value. However, there is also another meaning. It is possible to show that any source of power will deliver its maximum possible output when the impedance of the load is equal to the internal impedance of the source. The impedance of the source is said to be "matched" under this condition. The efficiency is only 50 percent in such a case; just as much power is used up in the source as is delivered to the load. Because of the poor efficiency, this type of impedance matching is limited to cases where only a small amount of power is

available and heating from power loss in the source is not important.

### Transformer Construction

Transformers usually are designed so that the magnetic path around the core is as short as possible. A short magnetic path means that the transformer will operate with fewer turns, for a given applied voltage, than if the path were long. A short path also helps to reduce flux leakage and therefore minimizes leakage reactance.

Two core shapes are in common use, as shown in Fig. 43. In the shell type both windings are placed on the inner leg, while in the core type the primary and secondary windings may be placed on separate legs, if desired. This is sometimes done when it is necessary to minimize capacitive effects between the primary and secondary, or when one of the windings must operate at very high voltage.

Core material for small transformers is usually silicon steel, called "transformer iron." The core is built up of laminations, insulated from each other (by a thin coating of shellac, for example) to prevent the flow of eddy currents. The laminations are interleaved at the ends to make the magnetic path as continuous as possible and thus reduce flux leakage.

The number of turns required in the primary for a given applied emf is determined by the size, shape and type of core material used, and the frequency. The number of turns required is inversely proportional to the cross-sectional area of the core. As a rough indication, windings of small power transformers frequently have about six to eight turns per volt on a core of 1-square-inch (645 sq. mm) cross section and have a magnetic path 10 or 12 inches (252 or 302 mm) in length. A longer path or smaller cross section requires more turns per volt, and vice versa.

In most transformers the coils are wound in layers, with a thin sheet of treated-paper insulation between each layer. Thicker insulation is used between coils and between coils and core.

### Autotransformers

The transformer principle can be utilized with only one winding instead of two, as shown in Fig. 44; the principles just discussed apply equally well. A one-winding transformer is called an *autotransformer*. The current in the common section (A) of the winding is the difference between the line (primary) and the load (secondary) currents, since these currents are out of phase. Hence, if the line and load currents are nearly equal, the common section of the winding may be wound with comparatively small wire. This will be the case only when the primary (line) and secondary (load) voltages are not very different. The autotransformer is used chiefly for boosting or reducing the power-line voltage by

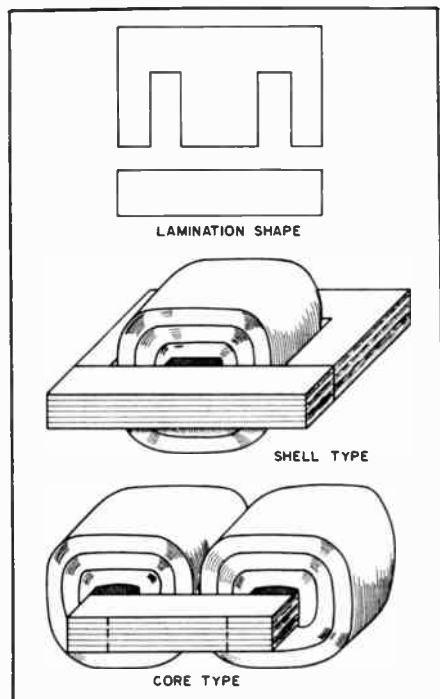


Fig. 43 — Two common types of transformer construction. Core pieces are interleaved to provide a continuous magnetic path.

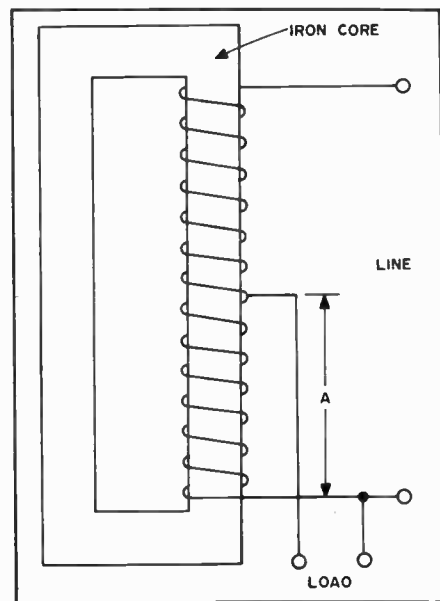


Fig. 44 — The autotransformer is based on the transformer principle, but uses only one winding. The line and load currents in the common winding (A) flow in opposite directions, so that the resultant current is the difference between them. The voltage across A is proportional to the turns ratio.

relatively small amounts. Continuously variable autotransformers are commercially available under a variety of trade names; "Variac" and "Powerstat" are typical examples.

### Ferromagnetic Transformers and Inductors

The design concepts and general theory of transformers which is presented earlier in this chapter apply also to transformers which are wound on ferromagnetic core materials (ferrite and powdered iron). As is the case with stacked cores made of laminations in the classic I and E shapes, the core material has a specific permeability factor which determines the inductance of the windings versus the number of wire turns used. Both ferrite and powdered-iron materials are manufactured with a wide range of  $\mu_i$  (initial permeability) characteristics. The value chosen by the designer will depend upon the intended operating frequency and the desired bandwidth of a given broadband transformer.

#### Core Types in Common Use

For use in radio-frequency circuits especially, a suitable core type must be chosen to provide the Q required by the designer. The wrong core material destroys the Q of an rf type of inductor.

Toroid cores are useful from a few hundred hertz well into the uhf spectrum. Tape-wound steel cores are employed in some types of power supplies — notably dc-to-dc converters. The toroid core is doughnut shaped, hence the name *toroid* (Fig. 45). The principal advantage to this type of core is the self-shielding characteristic. Another feature is the compactness of a transformer or inductor, which is possible when using a toroidal format. Therefore, toroids are excellent not only in dc-to-dc converters, but at audio and radio frequencies up to at least 1000 MHz, assuming the proper core material is selected for the range of frequencies over which the device must operate. Toroid cores are available from micro-miniature sizes well up to several inches in diameter. The latter can be used, as one example, to build a 20-kW balun for use in antenna systems.

Another form taken in ferromagnetic transformers and inductors is the "pot-core" or "cup-core" device. Unlike the toroid, which has the winding over the outer surface of the core material, the pot-core winding is inside the ferromagnetic material (Fig. 46). There are two cup-shaped halves to the assembly, both made of ferrite or powdered iron, which are connected tightly together by means of a screw which is passed through a center hole. The wire for the assembly is wound on an insulating bobbin which fits inside the two halves of the pot-core unit. The advantage to this type of construction is that the core permeability can be chosen to ensure a minimum number of wire turns for a given value of inductance. This reduces the wire resistance and increases

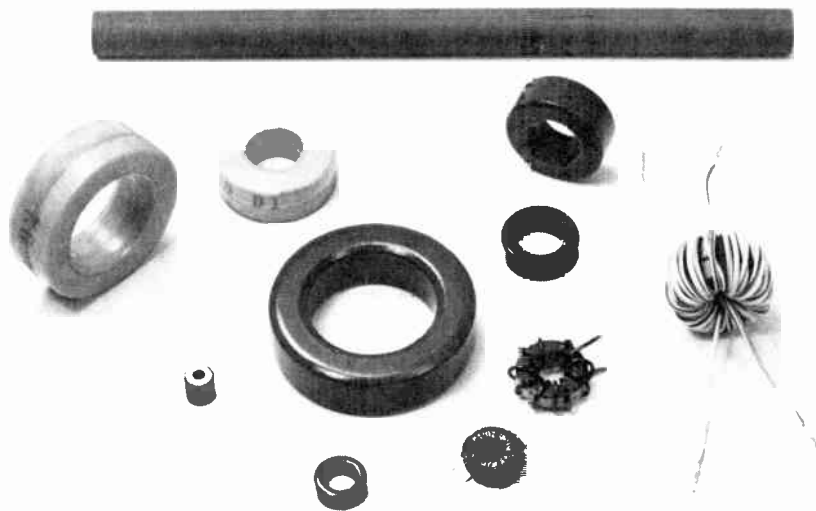


Fig. 45 — An assortment of toroid cores. A ferrite rod is placed at the top of the picture for comparison. The two light-colored, plastic-encased toroids at the upper left are tape-wound types (Hypersil steel) are suitable for audio and dc-to-dc converter transformers. The wound toroid at the right center contains two toroid cores which have been stacked atop one another to increase the power capability.

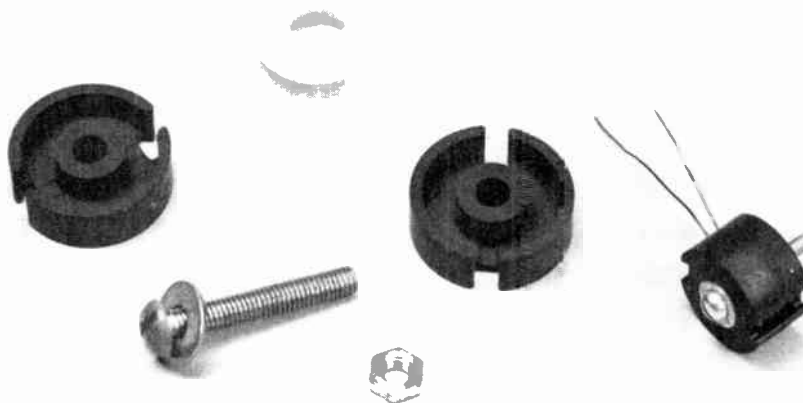


Fig. 46 — Breakaway view of a pot-core assembly (left) and an assembled pot core (right).

the Q as opposed to an equivalent inductance which is wound on a core that has relatively low permeability, or none at all. By virtue of the winding being contained inside the ferrite or powdered-iron pot core, shielding is excellent.

Still another kind of ferromagnetic-core inductor is found in today's technology — the solenoidal type (Fig. 47). Transformers and inductors fabricated in this manner consist of a cylindrical, oval or rectangular rod of material over which the wire winding is placed. This variety of device does not have a self-shielding trait. Therefore it must be treated in the same manner as any solenoidal-wound inductor

(using external shield devices). An example of a ferrite-rod inductor is the built-in loop antennas found in portable radios and direction finders.

#### Core Size

The cross-sectional area of ferromagnetic core is chosen to prevent saturation from the load seen by the transformer. This means that the proper thickness and diameter are essential parameters to consider. For a specific core the maximum ac excitation can be determined by

$$B_{\max(\text{ac})} = \frac{E_{\text{rms}} \times 10^8}{4.44 f N_p A_c} \text{ (gauss)}$$





Fig. 47 — A bc-band ferrite rod loop antenna is at the top of the picture (J.W. Miller Co.). A blank ferrite rod is seen at the center and a flat bc-band ferrite loop antenna is in the lower foreground.

where  $A_e$  = equivalent area of the magnetic path in  $\text{cm}^2$   
 $E_{\text{rms}}$  = applied voltage  
 $N_p$  = number of core turns  
 $f$  = operating frequency in Hz  
 $B_{\text{max}}$  = maximum flux density in gauss

The foregoing equation is applicable to inductors which do not have dc flowing in the winding along with ac. When both ac and dc currents flow

$$B_{\text{max (total)}} = \frac{E_{\text{rms}} \times 10^8}{4.444 f N_p A_e} + \frac{N_p I_{\text{dc}} A_L}{10 A_e}$$

where  $I_{\text{dc}}$  = the dc current through the winding  
 $A_L$  = the manufacturer's index for the core being used

The latter can be obtained for the core in use by consulting the manufacturer's data sheet.

### Types of Transformers

The most common ferromagnetic transformers used in amateur radio work are the narrow-band, broadband, conventional and transmission-line varieties. *Narrow-band* transformers are used when selectivity is desired in a tuned circuit, such as an audio peaking or notching circuit, a resonator in an rf filter, or a tuned circuit associated with an rf amplifier. *Broadband* transformers are employed in circuits which must have uniform response over a substantial spread of frequency, as in a 2- to 30-MHz broadband amplifier. In such an example the reactance of the windings should be at least four times the impedance the winding is designed to look into. Therefore, a transformer which has a 300-ohm primary and a 50-ohm secondary load should have winding reactances ( $X_L$ ) of at least 1200 ohms and 200 ohms, respectively. The windings, for all practical purposes, can be regarded as rf chokes, and the same rules apply. The permeability of the core material plays a vital role in designing a good broadband transformer. The performance of the transformer at the low-frequency end of the operating range depends on the permeability. That is, the  $\mu_i$  must be high enough in value to provide ample winding reactance at the low end of the operating range. As the operating frequency is increased, the effects of the core tend to disappear progressively until there are scarcely any core effects at the upper limit of the operating range. For this reason it is common to find a very low frequency core material utilized in a transformer that is contained in a broadband circuit which reaches well into the upper hf region, or even into the vhf spectrum. By way of simple explanation, at high frequency the low-frequency core material becomes inefficient and tends to vanish electrically. This desirable trait makes

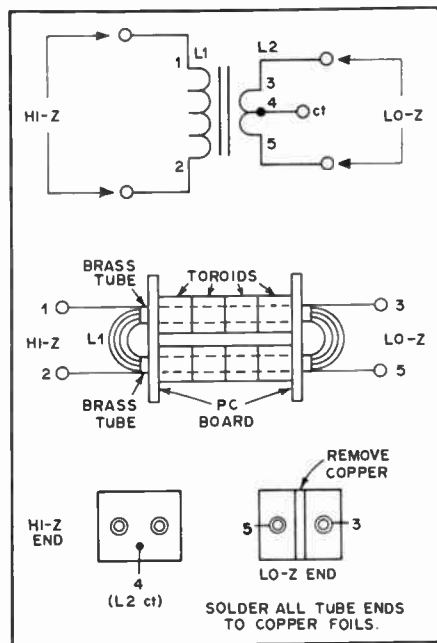


Fig. 48 — Schematic and pictorial representations of one type of "conventional" transformer. This style is used frequently at the input and output ports of rf power amplifiers which use transistors. The magnetic material consists of two rows of 950- $\mu$  toroid cores for use from 1.8 to 30 MHz. The primary and secondary windings are passed through the center holes of the toroid-stack rows as shown.

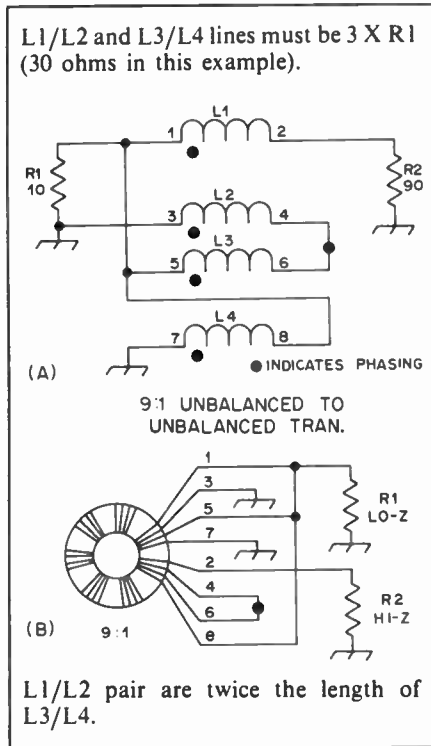


Fig. 50 — Schematic and pictorial presentations of a transmission-line transformer in which the windings need to be configured for a specific impedance.

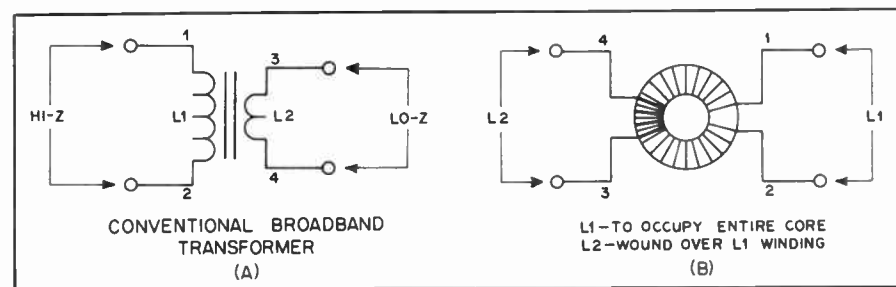


Fig. 49 — Another conventional transformer. Primary and secondary windings are wound over the outer surface of a toroid core.



**Table 6**

**Powdered-Iron Toroidal Cores dal A<sub>L</sub> VALUES (μH/100 turns)**

Core Size	41-Mix Green μ=75	3-Mix Grey μ=35 0.05-0.5 MHz	15-Mix Rd & Wh μ=25 0.1-2 MHz	1-Mix Blue μ=20 0.5-5 MHz	2-Mix Red μ=10 1-30 MHz	6-Mix Yellow μ=8 10-90 MHz	10-Mix Black μ=6 60-150 MHz	12-Mix Gn & Wh μ=3 100-200 MHz	0-Mix Tan μ=1 150-300 MHz
T-200	755	360	NA	NA	120	105	NA	NA	NA
T-184	1640	720	NA	NA	240	195	NA	NA	NA
T-157	970	420	NA	NA	140	115	NA	NA	NA
T-130	785	330	215	200	110	96	NA	NA	15.0
T-106	900	405	330	280	135	116	NA	NA	19.2
T- 94	590	248	NA	160	84	70	58	32	10.6
T- 80	450	180	170	115	55	45	34	22	8.5
T- 68	420	195	180	115	57	47	32	21	7.5
T- 50	320	175	135	100	50	40	31	18	6.4
T- 44	229	180	160	105	57	42	33	NA	6.5
T- 37	308	110	90	80	42	30	25	15	4.9
T- 30	375	110	93	85	43	36	25	16	6.0
T- 25	225	100	85	70	34	27	19	13	4.5
T- 20	175	90	65	52	27	22	16	10	3.5
T- 16	130	61	NA	44	22	19	13	8	3.0
T- 12	112	60	NA	48	24	19	12	7.5	3.0

NA — Not available in that size.

Turns = 100√L<sub>μH</sub> + A<sub>L</sub> Value (above).

All frequency figures optimum.

**Number of Turns vs. Wire Size and Core Size**

Approximate maximum of turns — single layer wound enameled wire

Wire Size	T-200	T-130	T-106	T-94	T-80	T-68	T-50	T-37	T-25	T-12
10	33	20	12	12	10	6	4	1		
12	43	25	16	16	14	9	6	3		
14	54	32	21	21	18	13	8	5	1	
16	69	41	28	28	24	17	13	7	2	
18	88	53	37	37	32	23	18	10	4	1
20	111	67	47	47	41	29	23	14	6	1
22	140	86	60	60	53	38	30	19	9	2
24	177	109	77	77	67	49	39	25	13	4
26	223	137	97	97	85	63	50	33	17	7
28	281	173	123	123	108	80	64	42	23	9
30	355	217	154	154	136	101	81	54	29	13
32	439	272	194	194	171	127	103	68	38	17
34	557	346	247	247	218	162	132	88	49	23
36	683	424	304	304	268	199	162	108	62	30
38	875	544	389	389	344	256	209	140	80	39
40	1103	687	492	492	434	324	264	178	102	51

**Physical Dimensions**

Core Size	Outer Dia. (in.)	Inner Dia. (in.)	Height (in.)	Cross Sect. Area cm <sup>2</sup>	Mean Length cm	Core Size	Outer Dia. (in.)	Inner Dia. (in.)	Height (in.)	Cross Sect. Area cm <sup>2</sup>	Mean Length cm
T-200	2.000	1.250	0.550	1.330	12.97	T- 50	0.500	0.303	0.190	0.121	3.20
T-184	1.840	0.950	0.710	2.040	11.12	T- 44	0.440	0.229	0.159	0.107	2.67
T-157	1.570	0.950	0.570	1.140	10.05	T- 37	0.375	0.205	0.128	0.070	2.32
T-130	1.300	0.780	0.437	0.930	8.29	T- 30	0.307	0.151	0.128	0.065	1.83
T-106	1.060	0.560	0.437	0.706	6.47	T- 25	0.255	0.120	0.096	0.042	1.50
T- 94	0.942	0.560	0.312	0.385	6.00	T- 20	0.200	0.088	0.067	0.034	1.15
T- 80	0.795	0.495	0.250	0.242	5.15	T- 16	0.160	0.078	0.060	0.016	0.75
T- 68	0.690	0.370	0.190	0.196	4.24	T- 12	0.125	0.062	0.050	0.010	0.74

Inches × 25.4 = mm.

Courtesy of Amidon Assoc., N. Hollywood, CA 91607

possible the use of ferromagnetics in broadband applications.

*Conventional transformers* are those that are wound in the same manner as a power transformer. That is, each winding is made from a separate length of wire, with one winding being placed over the previous one with suitable insulation in between (Figs. 48 and 49). A *transmission-line transformer* is, conversely, one that uses windings which are configured to simulate a piece of transmission line of a specific impedance. This can be achieved

by twisting the wires together a given number of times per inch, or by laying the wires on the core (adjacent to one another) at a distance apart which provides a two-wire line impedance of a particular value. In some applications these windings are called *bifilar*. A three-wire winding is known as a *trifilar* one, and so forth (Fig. 50). It can be argued that a transmission-line transformer is more efficient than a conventional one, but in practice it is difficult to observe a significant difference in the performance characteristics. An interest-

ing technical paper on the subject of toroidal broadband transformers was published by Sevick, W2FMI.<sup>1</sup> The classic reference on the subject is by Ruthroff.<sup>2</sup>

**Ferrite Beads**

Another form of toroidal inductor is the *ferrite bead*. This component is

<sup>1</sup>Sevick, "Simple Broadband Matching Networks," *QST*, January, 1976.

<sup>2</sup>Ruthroff, "Some Broadband Transformers," *Proc. IRE*, Vol. 47, Aug., 1959, p. 137.

**Table 7**

Ferrite Toroids	$A_L$ - Chart (mH per 1000 turns) Enameled Wire				
	63-Mix $\mu=40$	61-Mix $\mu=125$	43-Mix $\mu=950$	72-Mix $\mu=2000$	75-Mix $\mu=5000$
Core Size					
FT- 23	7.9	24.8	189.0	396.0	990.0
FT- 37	17.7	55.3	420.0	884.0	2210.0
FT- 50	22.0	68.0	523.0	1100.0	2750.0
FT- 82	23.4	73.3	557.0	1172.0	2930.0
FT-114	25.4	79.3	603.0	1268.0	3170.0

Number turns =  $1000\sqrt{\text{desired L (mH)} + A_L \text{ value (above)}}$

**Ferrite Magnetic Properties**

Property	Unit	63-Mix	61-Mix	43-Mix	72-Mix	75-Mix
Initial Perm. ( $\mu_i$ )		40	125	950	2000	5000
Maximum Perm.		125	450	3000	3500	8000
Saturation Flux Density @ 13 oer	Gauss	1850	2350	2750	3500	3900
Residual Flux Density	Gauss	750	1200	1200	1500	1250
Curie Temp.	°C	500	300	130	150	160
Vol. Resistivity	ohm/cm	$1 \times 10^8$	$1 \times 10^8$	$1 \times 10^5$	$1 \times 10^2$	$5 \times 10^2$
Opt. Freq. Range	MHz	15-25	.2-10	.01-1	.001-1	.001-1
Specific Gravity		4.7	4.7	4.5	4.8	4.8
Loss Factor	$\frac{1}{\omega O}$	$9.0 \times 10^{-5}$ @ 25 MHz.	$2.2 \times 10^{-5}$ @ 2.5 MHz	$2.5 \times 10^{-5}$ @ .2 MHz	$9.0 \times 10^{-6}$ @ .1 MHz	$5.0 \times 10^{-6}$ @ .1 MHz
Coercive Force	Oer.	2.40	1.60	0.30	0.18	0.18
Temp. Co-eff of initial Perm.	%/°C	0.10	0.10	0.20	0.60	

Ferrite Toroids	Physical Properties							
	Core Size	OD	ID	Height	$A_e$	$l_e$	$V_e$	$A_s$
FT- 23	0.230	0.120	0.060	0.00330	0.529	0.00174	0.1264	0.01121
FT- 37	0.375	0.187	0.125	0.01175	0.846	0.00994	0.3860	0.02750
FT- 50	0.500	0.281	0.188	0.02060	1.190	0.02450	0.7300	0.06200
FT- 82	0.825	0.520	0.250	0.03810	2.070	0.07890	1.7000	0.21200
FT-114	1.142	0.748	0.295	0.05810	2.920	0.16950	2.9200	0.43900

- OD - Outer diameter (inches)
- ID - Inner diameter (inches)
- Hgt - Height (inches)
- $A_w$  - Total window area (in)<sup>2</sup>
- $A_e$  - Effective magnetic cross-sectional area (in)<sup>2</sup>
- $l_e$  - Effective magnetic path length (inches)
- $V_e$  - Effective magnetic volume (in)<sup>3</sup>
- $A_s$  - Surface area exposed for cooling (in)<sup>2</sup>

Inches  $\times$  25.4 = mm. Courtesy of Amidon Assoc., N. Hollywood, CA 91607

available in various  $\mu_i$  values and sizes, but most beads are less than 0.25-inch (6.3-mm) diameter. Ferrite beads are used principally as vhf/uhf parasitic suppressors at the input and output terminals of amplifiers. Another practical application for them is in decoupling networks which are used to prevent unwanted migration of rf energy from one section of a circuit to another. They are used also in suppressing RFI and TVI in hi-fi and television sets. In some circuits it is necessary to only place one or more beads over a short length of wire to obtain ample inductive reactance for creating an rf choke. A few turns of small-diameter enameled wire can be looped through the larger beads to increase the effective inductance. Ferrite beads are suitable as low-Q base impedances in solid-state vhf and uhf amplifiers. The low-Q characteristics prevents self-

oscillation that might occur if a high Q solenoidal rf choke was used in place of one which was made from beads. Miniature broadband transformers are sometimes fashioned from ferrite beads. For the most part, ferrite beads can be regarded as small toroid cores.

**Number of Turns**

The number of wire turns used on a toroid core can be calculated by knowing the  $A_L$  of the core and the desired inductance. The  $A_L$  is simply the *inductance index* for the core size and permeability being used. Table 6 provides information of interest concerning a popular assortment of powdered-iron toroid cores. The complete number for a given core is composed of the core-size designator in the upper left column, plus the corresponding mix number. For example, a half-inch

diameter core with a no. 2 mix would be designated as a T-50-2 unit. The  $A_L$  would be 50 and the suggested operating frequency would be from 1 to 30 MHz. The  $\mu_i$  for that core is 10.

The required number of wire turns for a specified inductance on a given type of core can be determined by

$$\text{Turns} = 100 \sqrt{\text{desired L } (\mu\text{H}) + A_L}$$

where  $A_L$  is obtained from Table 6. The table also indicates how many turns of a particular wire gauge can be close wound to fill a specified core. For example, a T-68 core will contain 49 turns of no. 24 enameled wire, 101 turns of no. 30 enameled wire, and so on. Generally speaking, the larger the wire gauge the higher the unloaded Q of the toroidal inductor. The inductance values are based on the winding covering the entire circumference of the core. When there is space between the turns of wire, some control over the net inductance can be effected by compressing the turns or spreading them. The inductance will increase if compression is used and will decrease when the turns are spread farther apart.

Table 7 contains data for ferrite cores. The number of turns for a specified inductance in mH versus the  $A_L$  can be determined by

$$\text{Turns} = 1000 \sqrt{\text{desired L (mH)} + A_L}$$

where the  $A_L$  for a specific core can be taken from Table 7. Thus, if one required a 1-mH inductor and chose a no. FT-82-43 toroid core, the number of turns would be

$$\begin{aligned} \text{Turns} &= 1000 \sqrt{1 + 557} \\ &= 1000 \sqrt{0.001795} \\ &= 1000 \times 0.0424 = 42.4 \text{ turns} \end{aligned}$$

For an FT-82 size core no. 22 enameled wire would be suitable as indicated in Table 6 (using the T-80 core size as the nearest one to an FT-82). If the toroid core has rough edges (untumbled), it is suggested that insulating tape (3M glass epoxy tape or Mylar tape) be wrapped through the core before the wire is added. This will prevent the rough edges of the core from abrading the enameled wire.

**Checking RF Toroidal Devices**

The equations given previously will provide the number of wire turns needed for a particular inductance, plus or minus 10 percent. However, slight variations in core permeability may exist from one production run to another. Therefore, for circuits which require exact values of inductance it is necessary to check the toroid winding by means of an RCL bridge or an RX meter. If these instruments are not available, close approximations can be had by using a dip

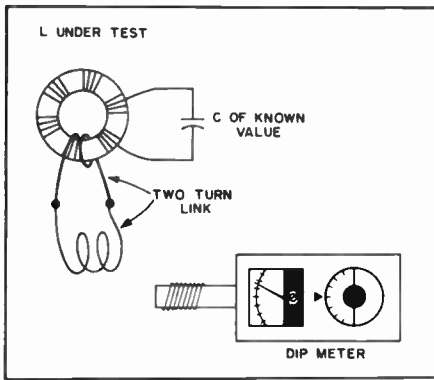


Fig. 51 — Method for checking the inductance of a toroid winding by means of a dip meter, known capacitance value and a calibrated receiver. The self-shielding properties of a toroidal inductor prevent dip-meter readings when the instrument is coupled directly to the toroid. Sampling is done by means of a coupling link, as illustrated.

meter, standard capacitor (known value, stable type, such as a silver mica) and a calibrated receiver against which to check the dipper frequency. Fig. 51 shows how to couple a dip meter to a completed toroid for testing. The coupling link in the illustration is necessary because the toroid has a self-shielding characteristic. The latter makes it difficult, and often impossible, to secure a dip in the meter reading when coupling the instrument directly to the toroidal inductor or transformer. The inductance can be determined by  $X_L$  since  $X_L = X_C$  at resonance. Therefore,

$$X_C = \frac{1}{2\pi f C}$$

$$\text{and } L_{(\mu H)} = \frac{X_L}{2\pi f}$$

where  $X_C$  is the reactance of the known capacitor value,  $f$  is in MHz and  $C$  is in  $\mu F$ . Using an example, where  $f$  is 3.5 MHz (as noted on a dip meter) and  $C$  is 100 PF,  $L$  is determined by

$$X_C = \frac{1}{6.28 \times 3.5 \times 0.0001} = 455 \text{ ohms}$$

Since  $X_L = X_C$  at resonance,

$$L_{(\mu H)} = \frac{455}{6.28 \times 3.5} = 20.7 \mu H$$

It is assumed, for the purpose of accuracy, that the dip-meter signal is checked for precise frequency by means of a calibrated receiver.

## The Decibel

In most radio communication the received signal is converted into sound. This being the case, it is useful to appraise signal strengths in terms of relative loudness as registered by the ear. A peculiarity of the ear is that an increase or decrease in loudness is responsive to the *ratio* of the amounts of power involved, and is practically independent of absolute value of the power. For example, if a person estimates that the signal is "twice as loud" when the transmitter power is increased from 10 watts to 40 watts, he will also estimate that a 400-watt signal is twice as loud as a 100-watt signal. In other words, the human ear has a *logarithmic* response.

This fact is the basis for the use of the relative-power unit called the decibel

(abbreviated dB). A change of one decibel in the power level is just detectable as a change in loudness under ideal conditions. The number of decibels corresponding to a given power ratio is given by the following formula:

$$dB = 10 \log \frac{P_2}{P_1}$$

Common logarithms (base 10) are used.

### Voltage and Current Ratios

Note that the decibel is based on *power* ratios. Voltage or current ratios can be used, but only when the impedance is the same for both values of voltage, or current. The gain of an amplifier cannot be expressed correctly in dB if it is based on the ratio of the output voltage to the input voltage unless both voltages are measured across the same value of impedance. When the impedance at both points of measurement is the same, the following formula may be used for voltage or current ratios:

$$dB = 20 \log \frac{V_2}{V_1}$$

$$\text{or } 20 \log \frac{I_2}{I_1}$$

where  $V$  = voltage  
 $I$  = current

The *S unit* and dB are used as references on receiver signal-strength meters. No particular standard has been adopted by the industry at this time, as an *S meter* is a

relative-reading instrument on most amateur receivers. However, during WW II at least one receiver manufacturer used 50  $\mu V$  for S9 and each S unit below S9 was supposed to be equivalent to 6 dB. The meter divisions above S9 were given in dB. Calibration of this kind is practical if the receiver is designed for a single amateur band, but multiband receivers exhibit different overall sensitivities for the various bands, rendering an S meter grossly inaccurate except for a single band in which calibration may have been attempted.

### Decibel Chart

The two formulas are shown graphically in Fig. 52 for ratios from 1 to 10. Gains (increases) expressed in decibels may be added arithmetically; losses (decreases) may be subtracted. A power decrease is indicated by prefixing the decibel figure with a minus sign. Thus +6 dB means that the power has been multiplied by 4, while -6 dB means that the power has been divided by 4.

The chart may be used for other ratios by adding (or subtracting, if a loss) 10 dB each time the ratio scale is multiplied by 10, for power ratios; or by adding (or subtracting) 20 dB each time the scale is multiplied by 10 for voltage or current ratios. For example, a power ratio of 2.5 is 4 dB (from the chart). A power ratio of 10 times 2.5, or 25, is 14 dB (10 + 4), and a power ratio of 100 times 2.5, or 250, is 24 dB (20 + 4). A voltage or current ratio of 4 is 12 dB, a voltage or current ratio of 40 is 32 dB (20 + 12), and one of 400 is 52 dB (40 + 12). Table 8 provides an easy reference for voltage power and current ratios versus dB.

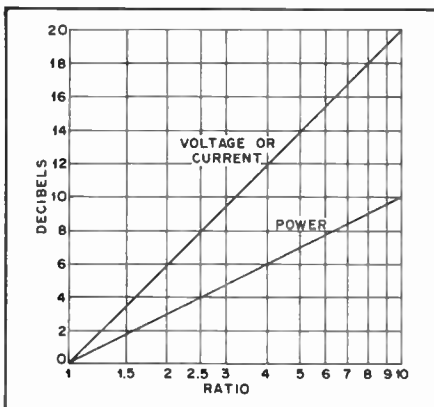


Fig. 52 — Decibel chart for power, voltage and current ratios for power ratios of 1:1 and 10:1. In determining decibels for current or voltage ratios the currents (or voltages) being compared must be referred to the same value of impedance.

**Table 8**

**Decibel equivalents E, I, and P ratios**

Voltage or Current Ratio	Power Ratio	dB	Voltage or Current Ratio	Power Ratio	Voltage or Current Ratio	Power Ratio	dB	Voltage or Current Ratio	Power Ratio
1.0000	1.0000	0	1.000	1.000	0.4898	0.2399	6.2	2.042	4.169
0.9886	0.9772	0.1	1.012	1.023	0.4842	0.2344	6.3	2.065	4.266
0.9772	0.9550	0.2	1.023	1.047	0.4786	0.2291	6.4	2.089	4.365
0.9661	0.9333	0.3	1.035	1.072	0.4732	0.2239	6.5	2.113	4.467
0.9550	0.9120	0.4	1.047	1.096	0.4677	0.2188	6.6	2.138	4.571
0.9441	0.8913	0.5	1.059	1.122	0.4624	0.2138	6.7	2.163	4.677
0.9333	0.8710	0.6	1.072	1.148	0.4571	0.2089	6.8	2.188	4.786
0.9226	0.8511	0.7	1.084	1.175	0.4519	0.2042	6.9	2.213	4.898
0.9120	0.8318	0.8	1.096	1.202	0.4467	0.1995	7.0	2.239	5.012
0.9016	0.8128	0.9	1.109	1.230	0.4416	0.1950	7.1	2.265	5.129
0.8913	0.7943	1.0	1.122	1.259	0.4365	0.1905	7.2	2.291	5.248
0.8810	0.7762	1.1	1.135	1.288	0.4315	0.1862	7.3	2.317	5.370
0.8710	0.7586	1.2	1.148	1.318	0.4266	0.1820	7.4	2.344	5.495
0.8610	0.7413	1.3	1.161	1.349	0.4217	0.1778	7.5	2.371	5.623
0.8511	0.7244	1.4	1.175	1.380	0.4169	0.1738	7.6	2.399	5.754
0.8414	0.7079	1.5	1.189	1.413	0.4121	0.1698	7.7	2.427	5.888
0.8318	0.6918	1.6	1.202	1.445	0.4074	0.1660	7.8	2.455	6.026
0.8222	0.6761	1.7	1.216	1.479	0.4027	0.1622	7.9	2.483	6.166
0.8128	0.6607	1.8	1.230	1.514	0.3981	0.1585	8.0	2.512	6.310
0.8035	0.6457	1.9	1.245	1.549	0.3936	0.1549	8.1	2.541	6.457
0.7943	0.6310	2.0	1.259	1.585	0.3890	0.1514	8.2	2.570	6.607
0.7852	0.6166	2.1	1.274	1.622	0.3846	0.1479	8.3	2.600	6.761
0.7762	0.6026	2.2	1.288	1.660	0.3802	0.1445	8.4	2.630	6.918
0.7674	0.5888	2.3	1.303	1.698	0.3758	0.1413	8.5	2.661	7.079
0.7586	0.5754	2.4	1.318	1.738	0.3715	0.1380	8.6	2.692	7.244
0.7499	0.5623	2.5	1.334	1.778	0.3673	0.1349	8.7	2.723	7.413
0.7413	0.5495	2.6	1.349	1.820	0.3631	0.1318	8.8	2.754	7.586
0.7328	0.5370	2.7	1.365	1.862	0.3589	0.1288	8.9	2.786	7.762
0.7244	0.5248	2.8	1.380	1.905	0.3548	0.1259	9.0	2.818	7.943
0.7161	0.5129	2.9	1.396	1.950	0.3508	0.1230	9.1	2.851	8.128
0.7079	0.5012	3.0	1.413	1.995	0.3467	0.1201	9.2	2.884	8.318
0.6998	0.4898	3.1	1.429	2.042	0.3428	0.1175	9.3	2.917	8.511
0.6918	0.4786	3.2	1.445	2.098	0.3388	0.1148	9.4	2.951	8.710
0.6839	0.4677	3.3	1.462	2.138	0.3350	0.1122	9.5	2.985	8.913
0.6761	0.4571	3.4	1.479	2.188	0.3311	0.1096	9.6	3.020	9.120
0.6683	0.4467	3.5	1.496	2.239	0.3273	0.1072	9.7	3.055	9.333
0.6607	0.4365	3.6	1.514	2.291	0.3236	0.1047	9.8	3.090	9.550
0.6531	0.4266	3.7	1.531	2.344	0.3199	0.1023	9.9	3.126	9.772
0.6457	0.4169	3.8	1.549	2.399	0.3162	0.1000	10.0	3.162	10.000
0.6383	0.4074	3.9	1.567	2.455	0.2985	0.08913	10.5	3.350	11.22
0.6310	0.3981	4.0	1.585	2.512	0.2818	0.07943	11.0	3.548	12.59
0.6237	0.3890	4.1	1.603	2.570	0.2661	0.07079	11.5	3.758	14.13
0.6166	0.3802	4.2	1.622	2.630	0.2512	0.06310	12.0	3.981	15.85
0.6095	0.3715	4.3	1.641	2.692	0.2371	0.05623	12.5	4.217	17.78
0.6026	0.3631	4.4	1.660	2.754	0.2239	0.05012	13.0	4.467	19.95
0.5957	0.3548	4.5	1.679	2.818	0.2113	0.04467	13.5	4.732	22.39
0.5888	0.3467	4.6	1.698	2.884	0.1995	0.03981	14.0	5.012	25.12
0.5821	0.3388	4.7	1.718	2.951	0.1884	0.03548	14.5	5.309	28.18
0.5754	0.3311	4.8	1.738	3.020	0.1778	0.03162	15.0	5.623	31.62
0.5689	0.3236	4.9	1.758	3.090	0.1585	0.02512	16.0	6.310	39.81
0.5623	0.3162	5.0	1.778	3.162	0.1413	0.01995	17.0	7.079	50.12
0.5559	0.3090	5.1	1.799	3.236	0.1259	0.01585	18.0	7.943	63.10
0.5495	0.3020	5.2	1.820	3.311	0.1122	0.01259	19.0	8.913	79.43
0.5433	0.2951	5.3	1.841	3.388	0.1000	0.01000	20.0	10.000	100.00
0.5370	0.2884	5.4	1.862	3.467	0.03162	0.00100	30.0	31.620	1,000.00
0.5309	0.2818	5.5	1.884	3.548	0.01	0.00010	40.0	100.00	10,000.00
0.5248	0.2754	5.6	1.905	3.631	0.003162	0.00001	50.0	316.20	10 <sup>5</sup>
0.5188	0.2692	5.7	1.928	3.715	0.001	10 <sup>-6</sup>	60.0	1,000.00	10 <sup>6</sup>
0.5129	0.2630	5.8	1.950	3.802	0.0003162	10 <sup>-7</sup>	70.0	3,162.00	10 <sup>7</sup>
0.5070	0.2570	5.9	1.972	3.890	0.0001	10 <sup>-8</sup>	80.0	10,000.00	10 <sup>8</sup>
0.5012	0.2512	6.0	1.995	39.31	0.00003162	10 <sup>-9</sup>	90.0	31,620.00	10 <sup>9</sup>
0.4955	0.2455	6.1	2.018	4.074	10 <sup>-5</sup>	10 <sup>-10</sup>	100.00	10 <sup>5</sup>	10 <sup>10</sup>



# Radio Frequency Circuits

The designer of amateur equipment needs to be familiar with radio-frequency circuits and the various related equations. This section provides the basic data for most amateur circuit development.

## Resonance in Series Circuits

Fig. 53 shows a resistor, capacitor and inductor connected in series with a source of alternating current, the frequency of which can be varied over a wide range. At some *low* frequency the capacitive reactance will be much larger than the resistance of R, and the inductive reactance will be small compared with either the reactance of C or the resistance of R. (R is assumed to be the same at all frequencies.) On the other hand, at some very *high* frequency the reactance of C will be very small and the reactance of L will be very large. In either case the current will be small, because the net reactance is large.

At some intermediate frequency, the reactances of C and L will be equal and the voltage drops across the coil and capacitor will be equal and 180 degrees out of phase. Therefore, they cancel each other completely and the current flow is determined wholly by the resistance, R. At that frequency the current has its largest possible value, assuming the source voltage to be constant regardless of frequency. A series circuit in which the inductive and capacitive reactances are equal is said to be *resonant*.

The principle of *resonance* finds its most extensive application in radio-frequency circuits. The reactive effects associated with even small inductances and capacitances would place drastic limitations on rf circuit operation if it were not possible to "cancel them out" by supplying the right amount of reactance of the opposite kind — in other words, "tuning the circuit to resonance."

## Resonant Frequency

The frequency at which a series circuit is resonant is that for which  $XL = XC$ . Substituting the formulas for inductive

and capacitive reactance gives

$$f = \frac{1}{2\pi \sqrt{LC}}$$

where  $f$  = frequency in hertz  
 $L$  = inductance in henrys  
 $C$  = capacitance in farads  
 $\pi = 3.14$

These units are inconveniently large for radio-frequency circuits. A formula using more appropriate units is

$$f = \frac{10^6}{2\pi \sqrt{LC}}$$

where  $f$  = frequency in kilohertz (kHz)  
 $L$  = inductance in microhenrys ( $\mu\text{H}$ )  
 $C$  = capacitance in picofarads (pF)  
 $\pi = 3.14$

Example: The resonant frequency of a series circuit containing a 5- $\mu\text{H}$  inductor and a 35-pF capacitor is

$$f = \frac{10^6}{2\pi \sqrt{LC}} = \frac{10^6}{6.28 \times \sqrt{5 \times 35}}$$

$$= \frac{10^6}{6.28 \times 13.23} = \frac{10^6}{83.08} = 12,036 \text{ kHz}$$

The formula for resonant frequency is not affected by resistance in the circuit.

## Resonance Curves

If a plot is drawn on the current flowing in the circuit of Fig. 53 as the frequency is varied (the applied voltage being constant) it would look like one of the curves in Fig. 54. The shape of the *resonance curve* at frequencies near resonance is determined by the ratio of reactance to resistance.

If the reactance of either the coil or capacitor is of the same order of magnitude as the resistance, the current decreases rather slowly as the frequency is moved in either direction away from resonance. Such a curve is said to be *broad*. On the other hand, if the reactance is considerably larger than the resistance the current decreases rapidly as the frequency moves away from resonance and the circuit is said to be *sharp*. A sharp circuit will respond a great deal more readily to the resonant frequency than to frequencies quite close to resonance; a broad circuit will respond almost equally well to a group or band of frequencies centering around the resonant frequency.

Both types of resonance curves are useful. A sharp circuit gives good *selectivity* — the ability to respond strongly (in terms of current amplitude) at one desired

frequency and discriminate against others. A broad circuit is used when the apparatus must give about the same response over a band of frequencies rather than to a single frequency alone.

## Q

Most diagrams of resonant circuits show only inductance and capacitance; no resistance is indicated. Nevertheless, resistance is always present. At frequencies up to perhaps 30 MHz this resistance is mostly in the wire of the coil. Above this frequency energy loss in the capacitor (principally in the solid dielectric which must be used to form an insulating support for the capacitor plates) also becomes a factor. This energy loss is equivalent to resistance. When maximum sharpness or selectivity is needed the object of design is to reduce the inherent resistance to the lowest possible value.

The value of the reactance of either the inductor or capacitor at the resonant frequency of a series-resonant circuit, divided by the *series* resistance in the circuit, is called the Q (quality factor) of the circuit, or

$$Q = \frac{X}{r}$$

where  $Q$  = quality factor  
 $X$  = reactance of either coil or capacitor in ohms  
 $r$  = series resistance in ohms

Example: The inductor and capacitor in a series circuit each have a reactance of

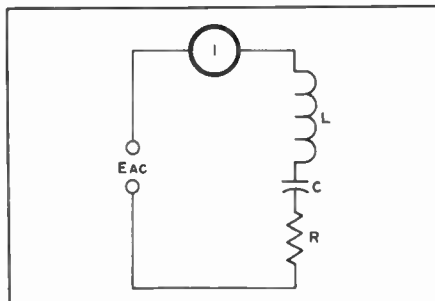


Fig. 53 — A series circuit containing L, C and R is "resonant" at the applied frequency when the reactance of C is equal to the reactance of L.

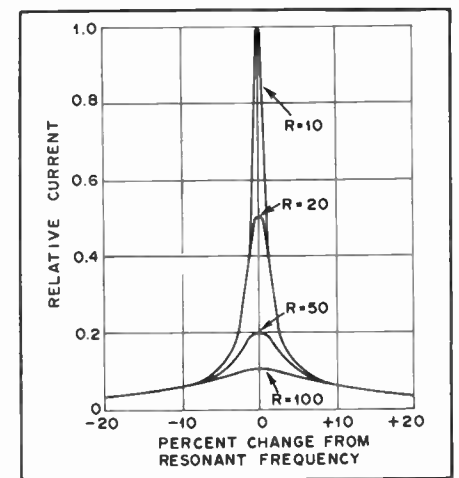


Fig. 54 — Current in a series-resonant circuit with various values of series resistance. The values are arbitrary and would not apply to all circuits, but represent a typical case. It is assumed that the reactances (at the resonant frequency) are 1000 ohms. Note that at frequencies more than plus or minus 10 percent away from the resonant frequency, the current is substantially unaffected by the resistance in the circuit.

350 ohms at the resonant frequency. The resistance is 5 ohms. Then the Q is

$$Q = \frac{X}{r} = \frac{350}{5} = 70$$

The effect of Q on the sharpness of resonance of a circuit is shown by the curves of Fig 55. In these curves the frequency change is shown in percentage above and below the resonant frequency. Qs of 10, 20, 50 and 100 are shown; these values cover much of the range commonly used in radio work. The *unloaded* Q of a

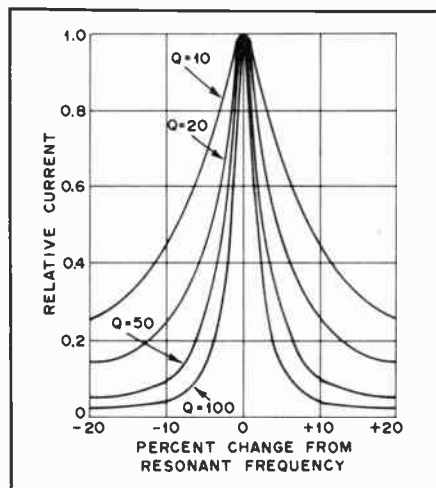


Fig. 55 — Current in series-resonant circuits having different Qs. In this graph the current at resonance is assumed to be the same in all cases. The lower the Q, the more slowly the current decreases as the applied frequency is moved away from resonance.

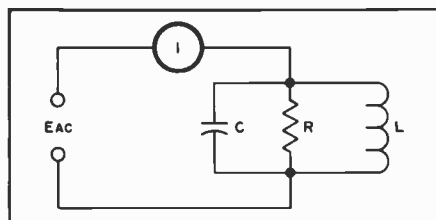


Fig. 56 — Circuit illustrating parallel resonance.

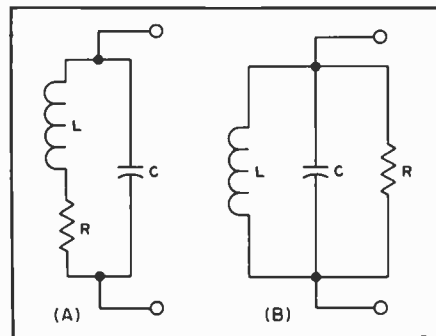


Fig. 57 — Series and parallel equivalents when the two circuits are resonant. The series resistance,  $r$ , in A is replaced in B by the equivalent parallel resistance ( $R = X^2 C/r = X^2 L/r$ ) and vice versa.

circuit is determined by the inherent resistances associated with the components.

### Voltage Rise at Resonance

When a voltage of the resonant frequency is inserted in series in a resonant circuit, the voltage that appears across either the inductor or capacitor is considerably higher than the applied voltage. The current in the circuit is limited only by the resistance and may have a relatively high value; however, the same current flows through the high reactances of the inductor and capacitor and causes large voltage drops. The ratio of the reactive voltage to the applied voltage is equal to the ratio of reactance to resistance. This ratio is also the Q of the circuit. Therefore, the voltage across either the inductor or capacitor is equal to QE where E is the voltage inserted in series. This fact accounts for the high voltages developed across the components of series-tuned antenna couplers.

### Resonance in Parallel Circuits

When a variable-frequency source of constant voltage is applied to a parallel circuit of the type shown in Fig. 56 there is a resonance effect similar to that in a series circuit. However, in this case the "line" current (measured at the point indicated) is *smallest* at the frequency for which the inductive and capacitive reactances are equal. At that frequency the current through L is exactly canceled by the out-of-phase current through C, so that only the current taken by R flows in the line. At frequencies *below* resonance the current through L is larger than that through C, because the reactance of L is smaller and that of C higher at low frequencies; there is only partial cancellation of the two reactive currents and the line current therefore is larger than the current taken by R alone. At frequencies *above* resonance the situation is reversed and more current flows through C than through L, so the line current again increases. The current at resonance, being determined wholly by R, will be small if R is large and large if R is small.

The resistance R shown in Fig 56 is not necessarily an actual resistor. In many cases it will be the series resistance of the coil "transformed" to an equivalent parallel resistance (see later). It may be antenna or other load resistance coupled into the tuned circuit. In all cases it represents the total effective resistance in the circuit.

Parallel and series resonant circuits are quite alike in some respects. For instance, the circuits given at A and B in Fig 57 will behave identically, when an external voltage is applied, if (1) L and C are the same in both cases, and (2) R multiplied by  $r$ , equals the square of the reactance (at resonance) of either L or C. When these conditions are met the two circuits will

have the same Q. (These statements are approximate, but are quite accurate if the Q is 10 or more). The circuit at A is a *series* circuit if it is viewed from the "inside" — that is, going around the loop formed by L, C and  $r$  — so its Q can be found from the ratio of X to  $r$ .

Thus, a circuit like that of Fig. 57A has an equivalent *parallel impedance* (at resonance) of

$$R = \frac{X^2}{r}$$

X is the reactance of either the inductor or the capacitor. Although R is not an actual resistor, to the source of voltage the parallel-resonant circuit "looks like" a pure resistance of that value. It is "pure" resistance because the inductive and capacitive currents are 180 degrees out of phase and are equal; thus there is no reactive current in the line. In a practical circuit with a high-Q capacitor, at the resonant frequency the parallel impedance is

$$Z_r = QX$$

where  $Z_r$  = resistive impedance at resonance

Q = quality factor of inductor  
X = reactance (in ohms) of either the inductor or capacitor

Example: The parallel impedance of a circuit with a coil Q of 50 and having inductive and capacitive reactance of 300 ohms will be

$$Z_r = QX = 50 \times 300 = 15,000 \text{ ohms}$$

At frequencies off resonance the impedance is no longer purely resistive because the inductive and capacitive currents are not equal. The off-resonant impedance therefore is complex, and is lower than the resonant impedance for the reasons previously outlined.

The higher the circuit Q, the higher the parallel impedance. Curves showing the variation of impedance (with frequency) of a parallel circuit have just the same shape as the curves showing the variation of current with frequency in a series circuit. Fig. 58 is a set of such curves. A set of curves showing the relative response as a function of the departure from the resonant frequency would be similar to Fig. 55. The -3 dB bandwidth (bandwidth at 0.707 relative response) is given by

$$\text{Bandwidth } -3 \text{ dB} = f_0/Q$$

where  $f_0$  is the resonant frequency and Q the circuit Q. It is also called the "half-power" bandwidth, for ease of recollection.

### Parallel Resonance in Low-Q Circuits

The preceding discussion is accurate for Qs of 10 or more. When the Q is below 10,

resonance in a parallel circuit having resistance in series with the coil, as in Fig. 57A, is not so easily defined. There is a set of values for L and C that will make the parallel impedance a pure resistance, but with these values the impedance does not have its maximum possible value. Another set of values for L and C will make the parallel impedance a maximum, but this maximum value is not a pure resistance. Either condition could be called "resonance," so with low-Q circuits it is necessary to distinguish between *maximum impedance* and *resistive impedance* parallel resonance. The difference between these L and C values and the equal reactances of a series-resonant circuit is appreciable when the Q is in the vicinity of 5, and becomes more marked with still lower Q values.

### Q of Loaded Circuits

In many applications of resonant circuits the only power lost is that dissipated in the resistance of the circuit itself. At frequencies below 30 MHz most of this resistance is in the coil. Within limits, increasing the number of turns in the coil increases the reactance faster than it raises the resistance, so coils for circuits in which the Q must be high are made with relatively large inductance for the frequency.

However, when the circuit delivers energy to a load (as in the case of the resonant circuits used in transmitters) the energy consumed in the circuit itself is usually negligible compared with that consumed by the load. The equivalent of such a circuit is shown in Fig. 59A, where the parallel resistor represents the load to which power is delivered. If the power dissipated in the load is at least ten times as great as the power lost in the inductor and capacitor, the parallel impedance of the resonant circuit itself will be so high compared with the resistance of the load that for all practical purposes the impedance of the combined circuit is equal to the load resistance. Under these conditions the Q of a parallel resonant circuit loaded by a resistive impedance is

$$Q = \frac{R}{X}$$

where R = parallel load resistance (ohms)  
X = reactance (ohms)

Example: A resistive load of 3000 ohms is connected across a resonant circuit in which the inductive and capacitive reactances are each 250 ohms. The circuit Q is then

$$Q = \frac{R}{X} = \frac{3000}{250} = 12$$

The "effective" Q of a circuit loaded by a parallel resistance becomes higher when the reactances are decreased. A circuit loaded with a relatively low resistance (a

few thousand ohms) must have low-reactance elements (large capacitance and small inductance) to have reasonable high Q.

### Impedance Transformation

An important application of the parallel-resonant circuit is as an impedance-matching device in the output circuit of a vacuum-tube rf power amplifier. There is an optimum value of load resistance for each type of tube or transistor and set of operating conditions. However, the resistance of the load to which the active device is to deliver power usually is considerably lower than the value required for proper device operation. To transform the actual load resistance to the desired value the load may be tapped across part of the coil, as shown in Fig. 59B. This is equivalent to connecting a higher value of load resistance across the whole circuit, and is similar in principle to impedance transformation with an iron-core transformer. In high-frequency resonant circuits the impedance ratio does not vary exactly as the square of the turns ratio, because all the magnetic flux lines do not cut every turn of the coil. A desired reflected impedance usually must be obtained by experimental adjustment.

When the load resistance has a very low value (say below 100 ohms) it may be connected in series in the resonant circuit (as in Fig. 57A, for example), in which case it is transformed to an equivalent parallel impedance as previously described. If the Q is at least 10, the equivalent parallel impedance is

$$Z_r = \frac{X^2}{r}$$

where  $Z_r$  = resistive parallel impedance at resonance

X = reactance (in ohms) of either the coil or capacitor

r = load resistance inserted in series

If the Q is lower than 10 the reactance will have to be adjusted somewhat, for the reasons given in the discussion of low-Q circuits, to obtain a resistive impedance of the desired value.

While the circuit shown in Fig. 59B will usually provide an impedance step-up as with an iron-core transformer, the network has some serious disadvantages for some applications. For instance, the common connection provides no dc isolation and the common ground is sometimes troublesome in regards to ground-loop currents. Consequently, a network in which only mutual magnetic coupling is employed is usually preferable. However, no impedance step-up will result unless the two coils are coupled tightly enough. The equivalent resistance seen at the input of the network will always be lower regardless of the turns ratio employed. However, such networks

are still useful in impedance-transformation applications if the appropriate capacitive elements are used. A more detailed treatment of matching networks and similar devices will be taken up in the next section.

Unfortunately, networks involving reactive elements are usually narrowband in nature and it would be desirable if such elements could be eliminated in order to increase the bandwidth. With the advent of ferrites, this has become possible and it is now relatively easy to construct actual impedance transformers that are both broadband and permit operation well up into the vhf portion of the spectrum. This is also accomplished in part by tightly coupling the two (or more) coils that make up the transformer either by twisting the conductors together or winding them in a parallel fashion. The latter configuration is sometimes called a *bifilar* winding, as discussed in the section on ferromagnetic transformers.

### Coupled Circuits and Filters

Two circuits are said to be coupled when a voltage or current in one network produces a voltage or current in the other one. The network where the energy originates is often called the *primary* circuit and the network that receives the energy is called the *secondary* circuit. Such

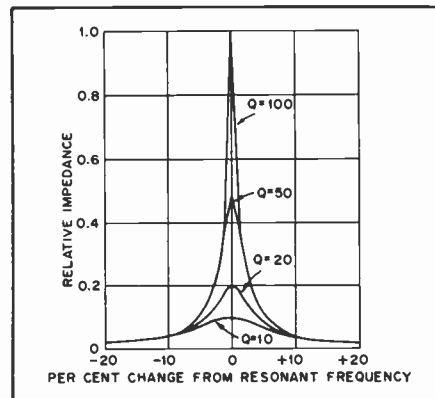


Fig. 58 — Relative impedance of parallel-resonant circuits with different Qs. These curves are similar to those in Fig. 55 for current in a series-resonant circuit. The effect of Q on impedance is most marked near the resonant frequency.

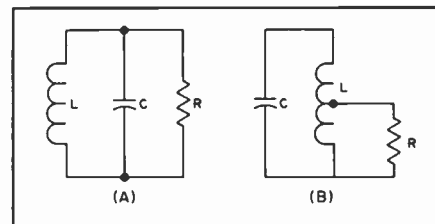


Fig. 59 — The equivalent circuit of a resonant circuit delivering power to a load. The resistor R represents the load resistance. At B the load is tapped across part of L, by which transformer action is equivalent to using a higher load resistance across the whole circuit.



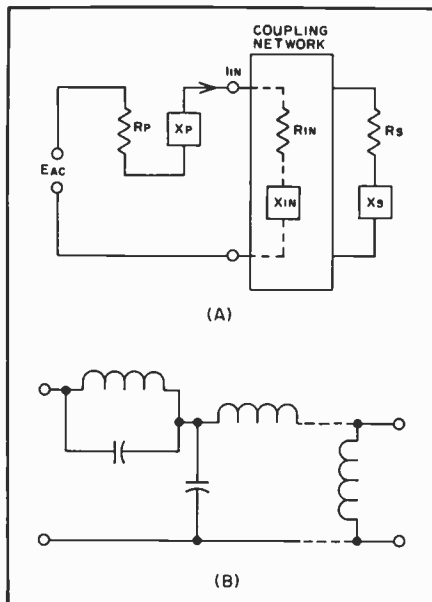


Fig. 60— A representative coupling circuit (A) and ladder network (B).

coupling is often of a desirable nature since in the process, unwanted frequency components or noise may be rejected or isolated and power transferred from a source to a load with greatest efficiency. On the other hand, two or more circuits may be coupled inadvertently and undesirable effects produced. While a great number of coupling-circuit configurations are possible, one very important class covers so many practical applications that analysis of it will be covered in detail.

### Simple Ladder Networks

Any two circuits that are coupled can be drawn schematically as shown in Fig. 60A. A voltage source represented by  $E_{ac}$  with a source resistance  $R_p$  and a source reactance  $X_p$  is connected to the input of the coupling network, thus forming the primary circuit. At the output, a load reactance  $X_s$  and a load resistance  $R_s$  are connected as shown to form the secondary circuit. The circuit in the box could consist of an infinite variety of resistors, capacitors, inductors, and even transmission lines. However, it will be assumed that the network can be reduced to a combination of series and shunt elements consisting only of inductors and capacitors as indicated by the circuit shown in Fig. 60B. For obvious reasons, the circuit is often called a *ladder network*. In addition, if there are no resistive elements present, or if such elements can be neglected, the network is said to be *dissipationless*.

If a network is dissipationless, all the power delivered to the input of the network will be dissipated in the load resistance  $R_s$ . This effect leads to important simplifications in computations involved in coupled networks. The assumption of a dissipationless network is

usually valid with transmitting circuits since even a small network loss (0.5 dB) will result in considerable heating at the higher power levels used in amateur applications. On the other hand, coupled circuits used in some receiving stages may have considerable loss. This is because the network may have some advantage and its high loss can be compensated by additional amplification in another stage. However, such devices form a relatively small minority of coupled networks commonly encountered and only the dissipationless case will be considered in this section.

### Effective Attenuation and Insertion Loss

The most important consideration in any coupled network is the amount of power delivered to the load resistance,  $R_s$ , from the source,  $E_{ac}$ , with the network present. Rather than specify the source voltage each time, a comparison is made with the maximum available power from any source with a given primary resistance,  $R_p$ . The value of  $R_p$  might be considered as the impedance level associated with a complex combination of sources, transmission lines, coupled networks, and even antennas. Typical values of  $R_p$  are 52, 75, 300 and 600 ohms. The maximum available power is given by

$$P_{max} = \frac{E_{ac}^2}{4R_p}$$

If the network is also dissipationless, the power delivered to the load resistance,  $R_s$ , is just the power "dissipated" in  $R_{in}$ . This power is related to the input current by

$$P_o = I_{in}^2 R_{in}$$

and the current in terms of the other variables is

$$I_{in} = \frac{E_{ac}}{\sqrt{(R_p + R_{in})^2 + (X_p + X_{in})^2}}$$

Combining the foregoing expressions gives a very useful formula for the ratio of power delivered to a load in terms of the maximum available power. This ratio expressed in decibels is given by

$$\text{Attn} = -10 \log \left( \frac{P_o}{P_{in}} \right) = -10 \log \left[ \frac{4R_{in}R_p}{(R_p + R_{in})^2 + (X_p + X_{in})^2} \right]$$

and is sometimes called the *effective attenuation*.

In the special case where  $X_p$  and  $X_s$  are either zero or can be combined into a coupling network, and where  $R_p$  is equal to  $R_s$ , the effective attenuation is also equal to the *insertion loss* of the network. The insertion loss is the ratio of the power delivered to the load with the coupling network in the circuit to the power delivered to the load with the network absent. Unlike the effective attenuation which is always positive when defined by

the previous formula, the insertion loss can take on negative values if  $R_p$  is not equal to  $R_s$  or if  $X_p$  and  $X_s$  are not zero. In effect, the insertion loss would represent a *power gain* under these conditions. The interpretation of this effect is that maximum available power does not occur with the coupling network out of the circuit because of the unequal source and load resistances and the non-zero reactances. With the network in the circuit, the resistances are now "matched" and the reactances are said to be "tuned out." The action of the coupling network in this instance is very similar to that of a transformer (which was discussed in a previous section) and networks consisting of "pure" inductors and capacitors are often used for this purpose. Such circuits are often referred to as matching networks. On the other hand, it is often desired to deliver the greatest amount of power to a load at some frequencies while rejecting energy at other frequencies. A device that accomplishes this action is called a *filter*. In the case of unequal source and load resistance, it is often possible to combine the processes of filtering and matching into one network.

### Solving Ladder-Network Problems

From the last section, it is evident that if the values of  $R_{in}$  and  $X_{in}$  of Fig. 60A can be determined, the effective attenuation and possibly the insertion loss are also easily found. Being able to solve this problem has wide applications in rf circuits. For instance, design formulas for filters often include a simplifying assumption that the load resistance is constant with frequency. In the case of many circuits, this assumption is not true. However, if the value of  $R_s$  and  $X_s$  at any particular frequency is known, the attenuation of the filter can be determined even though it is improperly terminated.

Unfortunately, while the solution to any ladder problem is possible from a theoretical standpoint, practical difficulties are encountered as the network complexity increases. Many computations to a high degree of accuracy may be required, making the process a tedious one. Consequently, the availability of a calculator or similar computing device is recommended. The approach used here is adapted readily to any calculating method including the use of an inexpensive pocket calculator.

### Susceptance and Admittance

The respective reactances of an inductor and a capacitor are given by

$$X_L = 2\pi fL$$

$$X_C = \frac{-1}{2\pi fC}$$

In a simple series circuit, the total resistance is just the sum of the individual



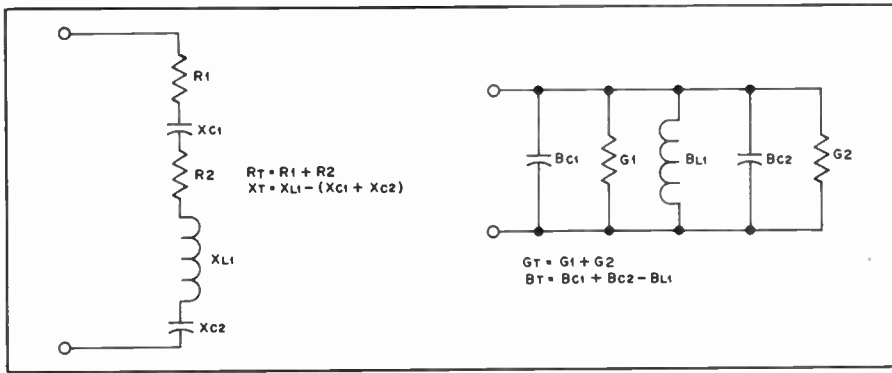


Fig. 61 — Resistances and reactances add in series circuits while conductances and susceptances add in parallel circuits. (Formulas shown are for numerical values of X and B.)

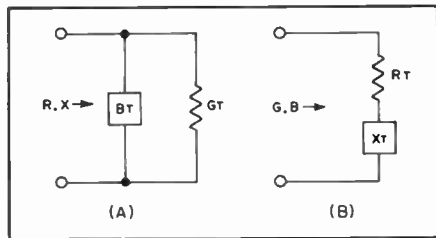


Fig. 62 — Application of conversion formulas can be used to transform a shunt conductance and susceptance to a series equivalent circuit A. The converse is illustrated at B.

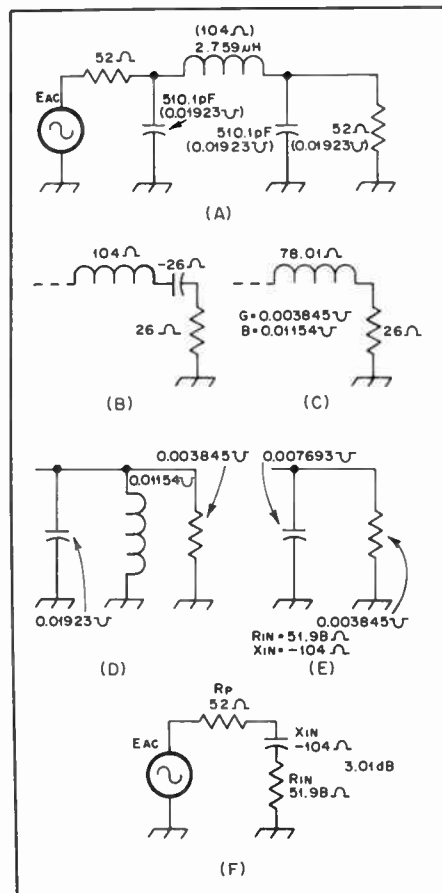


Fig. 63 — Problem illustrating network reduction to find insertion loss.

resistances in the network and the total reactance is the sum of the reactances. However, it is important to note the sign of the reactance. Since capacitive reactance is negative and inductive reactance is positive, it is possible that the sum of the reactances might be zero even though the individual reactances are not zero. In a series circuit, it will be recalled that the network is said to be resonant at the frequency where the reactances cancel.

A complementary condition exists in a parallel combination of circuit elements and it is convenient to introduce the concepts of *admittance*, *conductance* and *susceptance*. In the case of a simple resistance, the conductance is just the reciprocal. That is, the conductance of a 50-ohm resistance is  $1/50$  or  $2 \times 10^{-2}$ . The reciprocal unit of the ohm is the mho. For simple inductances and capacitances, the formulas for the respective reciprocal entities are

$$B_L = \frac{-1}{2\pi fL}$$

$$B_C = 2\pi fC$$

and are defined as susceptances. In a parallel combination of conductances and susceptances, the total conductance is the sum of the individual conductances, and the total susceptance is the sum of the individual susceptances, taking the respective signs of the latter into account. A comparison between the way resistance and reactance add and the manner in which conductance and susceptance add is shown in the example of Fig. 61. An entity called admittance can be defined in terms of the total conductance and total susceptance by the formula

$$Y = \sqrt{G_T^2 + B_T^2}$$

and is often denoted by the symbol Y. If the impedance of a circuit is known, the admittance is just the reciprocal. Likewise, if the admittance of a circuit is

known, the impedance is the reciprocal of the admittance. However, conductance, reactance, resistance and susceptance are not so simply related. If the total resistance and total reactance of a series circuit are known, the conductance and susceptance of the circuit are related to the latter by the formulas

$$G = \frac{R_T}{R_T^2 + X_T^2}$$

$$B = \frac{-X_T}{R_T^2 + X_T^2}$$

On the other hand, if the total conductance and total susceptance of a parallel combination are known, the equivalent resistance and reactance can be found from the formulas

$$R = \frac{G_T}{G_T^2 + B_T^2}$$

$$X = \frac{-B_T}{G_T^2 + B_T^2}$$

These relations are illustrated in Fig. 62A and Fig. 62B respectively. While the derivation of the mathematical expressions will not be given, *the importance of the sign change cannot be stressed too highly*. Solving network problems with a calculator is merely a matter of book-keeping, and failure to take the sign change associated with the transformed reactance and susceptance is the most common source of error.

#### A Sample Problem

The following example illustrates the manner in which the foregoing theory can be applied to a practical problem. A filter with the schematic diagram shown in Fig. 63A is *supposed* to have an insertion loss at 6 MHz of 3 dB when connected between a 52-ohm load and a source with a 52-ohm primary resistance (both  $X_p$  and  $X_s$  are zero). Since this is a case where the effective attenuation is equal to the insertion loss, the previous formula for effective attenuation applies. Therefore, it is required to find  $R_{in}$  and  $X_{in}$ .

Starting at the output, the values for the conductance and susceptance of the parallel RC circuit must be determined first. The conductance is just the reciprocal of 52 ohms and the previous formula for capacitive susceptance gives the value shown in parentheses in Fig. 63A. (The upside-down  $\Omega$  is the symbol for mho.) The next step is to apply the formulas for resistance and reactance in terms of the conductance and susceptance and the results give a 26-ohm resistance in series with a -26-ohm capacitive reactance as indicated in Fig. 63B. The reactance of the inductor can now be added to give a total reactance of 78.01 ohms. The

conductance and susceptance formulas can now be applied and the results of both of these operations is shown in Fig. 63C. Finally, adding the susceptance of the 510.1-pF capacitor (Fig. 63D) gives the circuit at Fig. 63A and applying the formulas once more gives the value of  $R_{in}$  and  $X_{in}$  (Fig. 63F). If the latter values are substituted into the effective attenuation formula, the insertion loss and effective attenuation are 3.01 dB, which is very close to the value specified. The reader might verify that the insertion loss is 0.167, 0.37 and 5.5 dB at 3.5, 4.0 and 7.0 MHz respectively. If a plot of insertion loss versus frequency was constructed it would give the frequency response of the filter.

### Frequency Sealing and Normalized Impedance

Quite often, it is desirable to be able to change a coupling network at one frequency and impedance level to another one. For example, suppose it was desired to move the 3-dB point of the filter in the preceding illustration from 6 to 7 MHz. An examination of the reactance and susceptance formulas reveals that multiplying the frequency by some constant  $k$  and dividing both the inductance and capacitance by the same value of  $k$  leaves the equations unchanged. Thus, if the capacitances and inductance in Fig. 63A are multiplied by 6/7, all the reactances and susceptances in the new circuit will now have the same value at 7 MHz that the old one had at 6 MHz.

It is common practice with many filter tables especially, to present all the circuit components for a number of designs at some convenient frequency. Translating the design to some desired frequency is simply accomplished by multiplying all the components by some constant factor. The most common frequency used is the value of  $f$  such that  $2\pi f$  is equal to 1.0. This is sometimes called a radian frequency of 1.0 and corresponds to 0.1592

Hz. To change a "one-radian" filter to a new frequency  $f_0$  (in Hz), all that is necessary is to multiply the inductances and capacitances by  $0.1592/f_0$ .

In a similar manner, if one resistance (or conductance) is multiplied by some factor  $n$ , all the other resistances (or conductances) and reactances (or susceptances) must be multiplied by the same factor in order to preserve the network characteristics. For instance, if the secondary resistance,  $R_s$  is multiplied by  $n$ , all circuit inductances must be multiplied by  $n$  and the circuit capacitances divided by  $n$  (since capacitive reactance varies as the inverse of  $C$ ). If, in addition to converting the filter of Fig. 63A to 7 MHz from 6 MHz, it was also desired to change the impedance level from 52 to 600 ohms, the inductance would have to be multiplied by  $(6/7)(600/52)$  and the capacitances by  $(6/7)(52/600)$ .

### Using Filter Tables

In a previous example, it was indicated that the frequency response of a filter could be derived by solving for the insertion loss of the ladder network for a number of frequencies. The question might be asked if the converse is possible. That is, given a desired frequency response, could a network be found that would have this response? The answer is a qualified yes and the technical nomenclature for this sort of process is network synthesis. Frequency responses can be "cataloged" and, if a suitable one can be found, the corresponding network elements can be determined from an associated table. Filters derived by network synthesis and similar methods (such as optimized computer designs) are often referred to as "modern filters" even though the theory has been in existence for years. The term is useful in distinguishing such designs from those of an older approximate method called *image-parameter* theory.

### Butterworth Filters

Filters can be grouped into four general categories as illustrated in Fig. 64A. Low-pass filters have zero insertion loss up to some critical frequency ( $f_c$ ) or cutoff frequency and then provide high rejection above this frequency. (The latter condition is indicated by the shaded lines in Fig. 64.) Band-pass filters have zero insertion loss between two cutoff frequencies with high rejection outside of the prescribed "bandwidth." (Band-stop filters reject a band of frequencies while passing all others.) And high-pass filters reject all frequencies below some cutoff frequency.

The attenuation shapes shown in Fig. 64A are ideal and can only be approached or approximated in practice. For instance, if the filter in the preceding problem was used for low-pass purposes in an 80-meter transmitter to reject harmonics on 40 meters, its performance would leave a lot to

be desired. While insertion loss at 3.5 MHz was acceptable, it would likely be too high at 4.0 MHz and rejection would probably be inadequate at 7.0 MHz.

Fortunately, design formulas exist for this type of network and form a class called *Butterworth* filters. The name is derived from the shape of the curve for insertion-loss vs. frequency and is sometimes called a *maximally flat response*. A formula for the frequency response curve is given by

$$A = 10 \log_{10} \left[ 1 + \left( \frac{f}{f_c} \right)^{2k} \right]$$

where  $f_c$  = the frequency for an insertion loss of 3.01 dB

$k$  = the number of circuit elements

The shape of a Butterworth low-pass filter is shown in the left-hand portion of Fig. 64B. (Another type that is similar in nature, only one that allows some "ripple" in the passband, is also shown in Fig. 64B. Here, a high-pass characteristic illustrates a *Chebyshev* response.)

As can be seen from the formula, increasing the number of elements will result in a filter that approaches the "ideal" low-pass shape. For instance, a 20-element filter designed for a 3.01-dB cutoff frequency of 4.3 MHz, would have an insertion loss at 4 MHz of 0.23 dB and 84.7 dB at 7 MHz. However, practical difficulties would make such a filter very hard to construct. Therefore, some compromises are always required between a theoretically perfect frequency response and ease of construction.

### Element Values

Once the number of elements,  $k$ , is determined, the next step is to find the network configuration corresponding to  $k$ . (Filter tables sometimes have sets of curves that enable the user to select the desired frequency response curve rather than use a formula. Once the curve with the fewest number of elements for the specified passband and stop-band insertion loss is found, the filter is then fabricated around the corresponding value of  $k$ .) Table 9 gives normalized element values for values of  $k$  from 1 to 10. This table is for 1-ohm source and load resistance (reactance zero) and a 3.01-dB cutoff frequency of 1 radian/second (0.1592 Hz). There are two possible circuit configurations and these are shown in Fig. 65. Here, a five-element filter is given as an example with either a shunt element next to the load (Fig. 65A) or a series element next to the load (Fig. 65B). Either filter will have the same response.

After the values for the 1-ohm, 1-radian/second "prototype" filter are found, the corresponding values for the actual frequency/impedance level can be determined (see the section on frequency and impedance scaling). The prototype in-

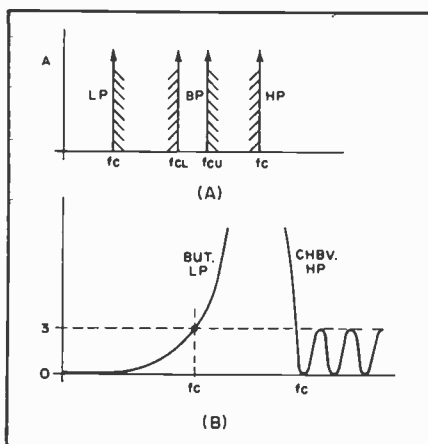


Fig. 64 — Ideal filter response curves are shown at A and characteristics of practical filters are shown at B.

ductance and capacitance values are multiplied by the ratio  $(0.1592/f_c)$  where  $f_c$  is the actual 3.01-dB cutoff frequency. Next, this number is multiplied by the load resistance in the case of an inductor and divided by the load resistance if the element is a capacitance. For instance, the filter in the preceding example is for a three-element design ( $k$  equal to 3) and the reader might verify the values for the components for an  $f_c$  of 6 MHz and load resistance of 52 ohms.

### High-Pass Butterworth Filters

The formulas for change of impedance and frequency from the 1-ohm, 1-radian/second prototype to some desired level can also be conveniently written as

$$L = \frac{R}{2\pi f_c} L_{\text{prototype}}$$

$$C = \frac{1}{2\pi f_c R} C_{\text{prototype}}$$

where  $R$  = the load resistance in ohms  
 $f_c$  = the desired 3.01-dB frequency in Hz

Then  $L$  and  $C$  give the actual circuit-element values in henrys and farads in terms of the prototype element values from Table 9.

However, the usefulness of the low-pass prototype does not end here. If the following set of equations is applied to the prototype values, circuit elements for a high-pass filter can be obtained. The filter is shown in Fig. 66A and Fig. 66B which correspond to Fig. 65A and Fig. 65B in Table 9. The equations for the actual high-pass circuit values in terms of the low-pass prototype are given by

$$C = \frac{1}{R 2\pi f_c C_{\text{prot.}}}$$

$$L = \frac{R}{2\pi f_c L_{\text{prot.}}}$$

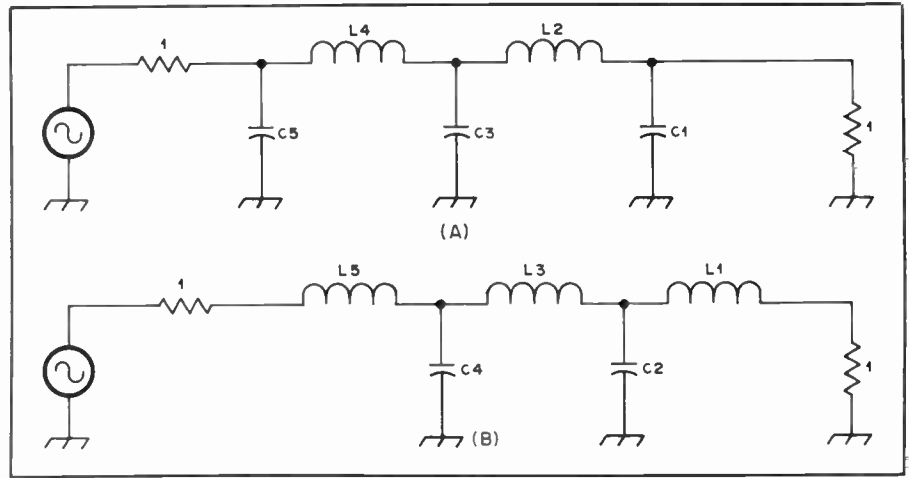


Fig. 65 — Schematic diagram of a Butterworth low-pass filter. (See Table 9 for element values.)

and the frequency response curve can be obtained from

$$A = 10 \log \left[ 1 + \left( \frac{f_c}{f} \right)^{2k} \right]$$

For instance, a high-pass filter with three elements, a 3.01-dB  $f_c$  of 6 MHz and 52 ohms, has a  $C1$  and  $C3$  of 510 pF and an  $L2$  of 0.6897  $\mu$ H. The insertion loss at 3.5 and 7 MHz would be 14.21 and 1.45 dB respectively.

### Butterworth Band-Pass Filters

Band-pass filters can also be designed through the use of Table 9. Unfortunately, the process is not as straightforward as it is for low- and high-pass filters if a practical design is to be obtained. In essence, a low-pass filter is resonated to some "center frequency" with the 3.01-dB cutoff frequency being replaced by the filter bandwidth. The ratio of the bandwidth to center frequency must be relatively large, otherwise component values tend to become unmanageable.

While there are many variations of specifying such filters, a most useful approach is to determine an upper and lower frequency for a given attenuation.

The center frequency and bandwidth are then given by

$$f_o = \sqrt{f_1 f_2}$$

$$BW = f_2 - f_1$$

If the bandwidth specified is *not* the 3.01-dB bandwidth ( $BW_c$ ), the latter can be determined from

$$BW_c = \frac{BW}{\left[ \frac{A}{10^{10}} - 1 \right]^{\frac{1}{2k}}}$$

in the case of a Butterworth response or from tables of curves.  $A$  is the required attenuation at the cutoff frequencies. The upper and lower cutoff frequencies ( $f_{cu}$  and  $f_{cl}$ ) are then given by

$$f_{cl} = \frac{-BW_c + \sqrt{(BW_c)^2 + 4f_o^2}}{2}$$

$$f_{cu} = f_{cl} + BW_c$$

A somewhat more convenient method is to pick a 3.01-dB bandwidth (the wider the better) around some center frequency

Table 9

Fig. 65A Fig. 65B	C1 L1	L2 C2	C3 L3	L4 C4	C5 L5	L6 C6	C7 L7	L8 C8	C9 L9	L10 C10
$k$										
1	2.0000									
2	1.4142	1.4142								
3	1.0000	2.0000	1.0000							
4	0.7654	1.8478	1.8478	0.7654						
5	0.6180	1.6180	2.0000	1.6180	0.6180					
6	0.5176	1.4142	1.9319	1.9319	1.4142	0.5176				
7	0.4450	1.2470	1.8019	2.0000	1.8019	1.2470	0.4450			
8	0.3902	1.1111	1.6629	1.9616	1.9616	1.6629	1.1111	0.3902		
9	0.3473	1.0000	1.5321	1.8794	2.0000	1.8794	1.5321	1.0000	0.3473	
10	0.3129	0.9080	1.4142	1.7820	1.9754	1.9754	1.7820	1.4142	0.9080	0.3129

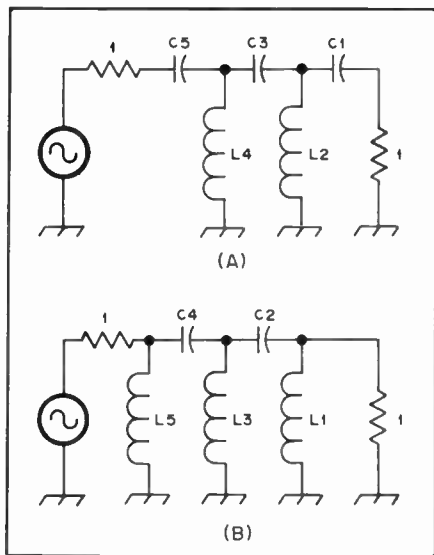


Fig. 66 — Network configuration of a Butterworth high-pass filter. The low-pass prototype can be transformed as described in the text.

and compute the attenuation at other frequencies of interest by using the transformation:

$$\frac{f}{f_c} = \left[ \left( \frac{f}{f_0} - \frac{f_0}{f} \right) \frac{f_0}{BW_c} \right]$$

which can be substituted into the insertion-loss formula or table of curves.

As an example, suppose it is desired to build a band-pass filter for the 15-meter Novice band in order to eliminate the possibility of radiation on the 14- and 28-MHz bands. For a starting choice, 16 and 25 MHz will be picked as the 3.01-dB points giving a 3-dB bandwidth of 9 MHz. For these two points,  $f_0$  will be 20 MHz. It is common practice to equate the number of branch elements or filter resonators to certain mathematical entities called "poles" and the number of poles is just the value of  $k$  for purposes of discussion here. For a three-pole filter ( $k$  of 3), the insertion loss will be 12.79 and 11.3 dB at 14 and 28 MHz, respectively.

$C1$ ,  $C3$  and  $L2$  are then calculated for a 9-MHz low-pass filter and the elements for this filter are resonated to 20 MHz as shown in Fig. 67A. The response shape is plotted in Fig. 67B and it appears to be unsymmetrical about  $f_0$ . In spite of this fact, such filters are called symmetrical band-pass filters and  $f_0$  is the "center frequency."

If the response is plotted against a logarithmic frequency scale, the symmetry will become apparent. Consequently, using a logarithmic plot is helpful in designing filters of this type.

Examination of the component values reveals that while the filter is practical, it is a bit untidy from a construction standpoint. Rather than using a single 340.1-pF capacitor, paralleling a number

of smaller valued units would be advisable. Encountering difficulty of this sort is typical of most filter designs, consequently, some tradeoffs between performance, complexity and ease of construction are usually required.

### Coupled Resonators

A problem frequently encountered in rf circuits is that of a coupled resonator. Applications include simple filters, oscillator tuned circuits, and even antennas. The circuit shown in Fig. 68A is illustrative of the basic principles involved. A series RLC circuit and the external terminals  $ab$  are "coupled" through a common capacitance,  $C_m$ . Applying the formulas for conductance and susceptance in terms of series reactance and resistance gives

$$G_{ab} = \frac{R_r}{R_r^2 + X^2}$$

$$B_{ab} = B_{cm} - \frac{X}{R_r^2 + X^2}$$

The significance of these equations can be seen with the aid of Fig. 68B. At some point, the series inductive reactance will cancel the series capacitive reactance (at a point slightly below  $f_0$  where the conductance curve reaches a peak). Depending upon the value of the coupling susceptance,  $B_{cm}$ , it is possible that another point can be found where the total input susceptance is zero. The input conductance at this frequency,  $f_0$ , is then  $G_0$ .

Since  $G_0$  is less than the conductance at the peak of the curve,  $1/G_0$  or  $R_0$  is going to be greater than  $R_r$ . This effect can be applied when it is desired to match a low-value load resistance (such as found in a mobile whip antenna) to a more practical value. Suppose  $R_r$  and  $C_r$  in Fig. 68A are 10 ohms and 21 pF, respectively, and represent the equivalent circuit of a mobile antenna. Find the value of  $L_r$  and  $C_m$  which will match this antenna to a 52-ohm feed line at a frequency of 3900 kHz. Substituting the foregoing values into the formulas for input conductance gives

$$\frac{1}{52} = \frac{10}{10^2 + X^2}$$

Solving for  $X$  (which is the total series reactance) gives a value of 20.49 ohms. The reactance of a 21-pF capacitor at 3900 kHz is 1943.3 ohms so the inductive reactance must be 1963.7 ohms. While either a positive or negative reactance will satisfy the equation for  $G_{ab}$ , a positive value is required to tune out  $B_{cm}$ . If the coupling element was a shunt inductor, the total reactance would have to be capacitive or negative in value.) Thus, the

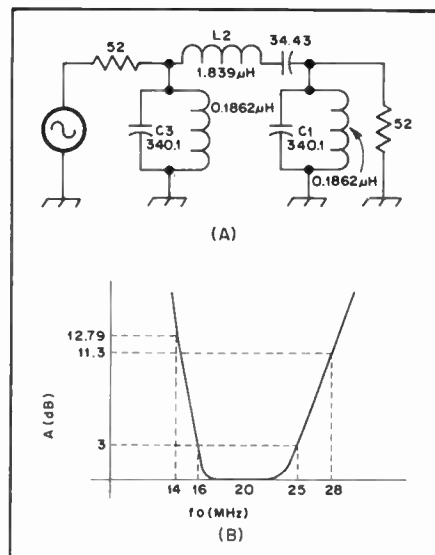


Fig. 67 — A Butterworth band-pass filter. (Capacitance values are in picofarads.)

required inductance value for  $L_r$  will be 80.1  $\mu$ H. In order to obtain a perfect match, the input susceptance must be zero and the value of  $B_{cm}$  can be found from

$$0 = B_{cm} - \frac{20.49}{10^2 + (20.49)^2}$$

giving a susceptance value of 0.04 mhos which corresponds to a capacitance of 1608 pF.

### Piezoelectric Crystals

A somewhat different form of resonator consists of a quartz crystal between two

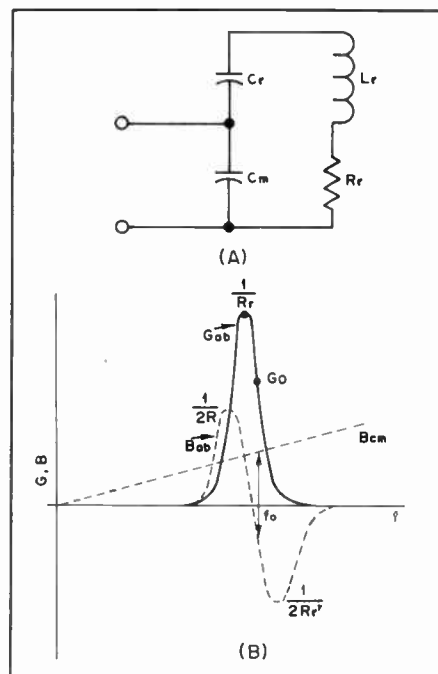


Fig. 68 — A capacitively coupled resonator is shown at A. See text for explanation of figure shown at B.



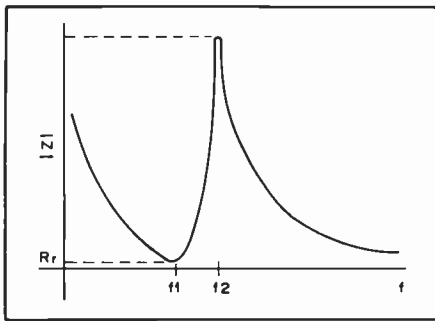


Fig. 69 — Frequency response of a quartz-crystal resonator. The minimum value is only approximate since holder capacitance is neglected.

conducting plates. If a voltage is applied to the plates, the resultant electric field causes a mechanical stress in the crystal. Depending upon the size and "cut" of the crystal, a frequency will exist at which the crystal begins to vibrate. The effect of this mechanical vibration is to simulate a series RLC circuit as in Fig. 68A. There is a capacitance associated with the crystal plates which appears across the terminals ( $C_m$  in Fig. 68A). Consequently, this circuit can also be analyzed with the aid of Fig. 68B. At some frequency ( $f_1$  in Fig. 69), the series reactance is zero and  $G_{ab}$  in the preceding formula will just be  $1/R_r$ . Typical values for  $R_r$  range from 10 k-ohm and higher. However, the equivalent inductance of the mechanical circuit is normally extremely high (over 10,000 henrys in the case of some low-frequency units) which results in a very high circuit Q (30,000). Above  $f_1$ , the reactance is "inductive" and at  $f_2$ , the susceptance of the series resonator is just equal to the susceptance of the crystal holder,  $B_{cm}$ . Here, the total susceptance is zero. Since  $B_{cm}$  is usually very small, the equivalent series susceptance is also small. This means the value for X in the susceptance formula will be very large and consequently  $G_{ab}$  will be small, which corresponds to a high input resistance. A plot of the magnitude of the impedance is shown in Fig. 70. The dip at  $f_1$  is called the series-resonant mode and the peak at  $f_2$  is referred to as the parallel-resonant or "anti-resonant" mode. When specifying crystals for oscillator applications, the type of mode must be given along with external capacitance across the holder or type oscillator circuit to be used. Otherwise, considerable difference in actual oscillator frequency will be observed. The effect can be used to advantage and the frequency of a crystal oscillator can be "pulled" with an external reactive element or even frequency modulated with a device that converts voltage or current fluctuations into changes in reactance.

### Coefficient of Coupling

If the solution to the mobile whip-antenna problem is examined, it can be

seen that for a given frequency,  $R_r$ ,  $L_r$ , and  $C_r$ , only one value of  $C_m$  results in an input load that appears as a pure resistance. While such a condition might be defined as resonance, the resistance value obtained is not necessarily the one required for maximum transfer of power.

A definition that is helpful in determining how to vary the circuit elements in order to obtain the desired input resistance is called the *coefficient of coupling*. The coefficient of coupling is defined as the ratio of the common or mutual reactance and the square root of the product of two specially defined reactances. If the mutual reactance is capacitive, one of the special reactances is the sum of the series capacitive reactances of the primary mesh (with the resonator disconnected) and the other one is the sum of the series capacitive reactances of the resonator (with the primary disconnected). Applying this definition to the circuit of Fig. 68A, the coefficient of coupling,  $k$ , is given by

$$k = \sqrt{\frac{C_r}{C_r + C_m}}$$

How meaningful the coefficient of coupling will be depends upon the particular circuit configuration under consideration and which elements are being varied. For example, suppose the value of  $L_r$  in the mobile-whip antenna problem was fixed at 100  $\mu$ H and  $C_m$  and  $C_r$  were allowed to vary. (It will be recalled that  $C_r$  is 21 pF and represents the antenna capacitance. However, the total resonator capacitance could be changed by adding a series capacitor between  $C_m$  and the antenna. Thus,  $C_r$  could be varied from 21 pF to some lower value but not a higher one.)

A calculated plot of  $k$  versus input resistance,  $R_{in}$ , is shown in Fig. 70. Note the unusually high change in  $k$  when going from resistance values near 10 ohms to slightly higher ones.

Similar networks can be designed to work with any ratio of input resistance and load resistance but it is evident small ratios are going to pose difficulties. For larger ratios, component tolerances are more relaxed. For instance,  $C_m$  might consist of switchable fixed capacitors with  $C_r$  being variable. With a given load resistance,  $C_m$  essentially sets the value of the reactance and thus the input resistance while  $C_r$  and  $L_r$  provide the required reactance for the conductance formula. However, if  $L_r$  is varied,  $k$  varies also. Generally speaking, higher values of  $L_r$  (and consequently circuit Q) require lower values of  $k$ .

At this point, the question arises as to the significance and even the merit of such definitions as coefficient of coupling and Q. If the circuit element values are known,

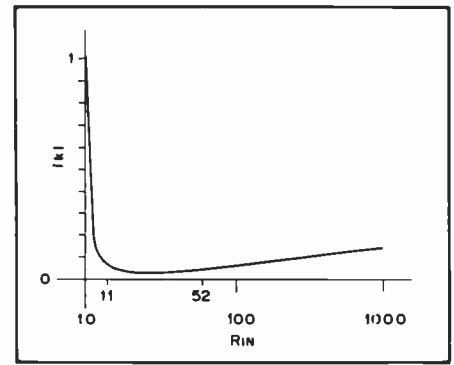


Fig. 70 — Variation of  $k$  with input resistance for circuit of Fig. 68.

and if the configuration can be resolved into a ladder network, important properties such as input impedance and attenuation can be computed directly for any frequency. On the other hand, circuit information might be obscured or even lost by attempting to attach too much importance to an arbitrary definition. For example, the plot in Fig. 70 merely indicates  $C_m$  and  $C_r$  are changing with respect to one another. But it doesn't illustrate how they are changing. Such information is important in practical applications and even a simple table of  $C_m$  and  $C_r$  vs.  $R_{in}$  for a particular  $R_r$  would be much more valuable than a plot of  $k$ .

Similar precautions have to be taken with the interpretation of circuit Q. Selectivity and Q are simply related for single resonators and circuit components, but the situation rapidly deteriorates with complex configurations. For instance, adding loss or resistance to circuit elements would seem to contradict the idea that low-loss or high-Q circuits provide the best selectivity. However, this is actually done in some filter designs to improve frequency response. In fact, the filter with the added loss has identical characteristics to one with "pure" elements. The method is called *predistortion* and is very useful in designing filters where practical considerations require the use of circuit elements with parasitic or undesired resistance.

As the frequency of operation is increased, discrete components become smaller until a point is reached where other forms of networks have to be used. Here, entities such as  $k$  and Q are sometimes the only means of describing such networks. Another definition of Q that is quite useful in this instance is that it is equal to the ratio of 2 (energy stored per rf cycle)/(energy lost per rf cycle).

### Mutually Coupled Inductors

A number of very useful rf networks involve coupled inductors. In a previous section, there was some discussion on iron-core transformers which represent a special case of the coupled-inductance problem. The formulas presented apply to

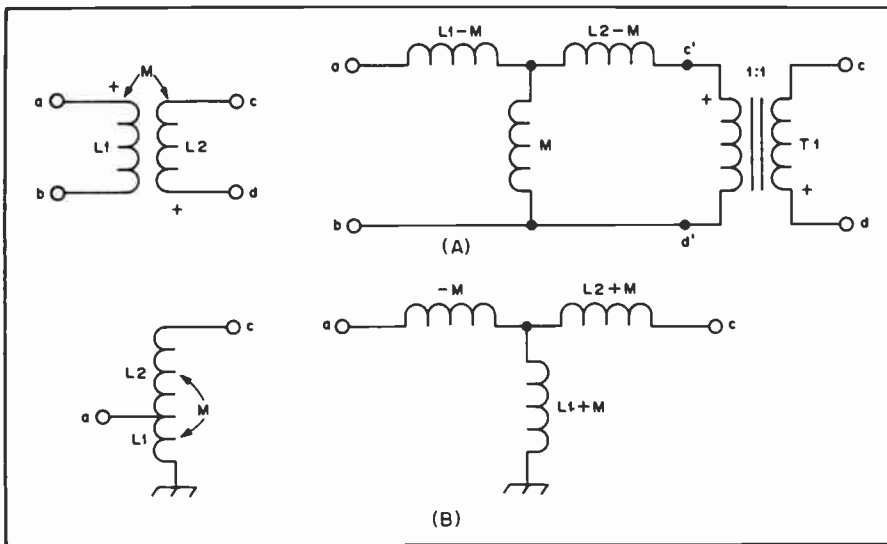


Fig. 71 — Two types of magnetically coupled circuits. At A, only mutual magnetic coupling exists while the circuit at B contains a common inductance also. Equivalents of both circuits are shown at the right which permit the application of the ladder-network analysis discussed in this section. (If the sign of voltage is unimportant, T1 can be eliminated.)

instances where the coefficient of coupling is very close to 1.0. While it is possible to approach this condition at frequencies in the rf range, many practical circuits work at values of  $k$  that are considerably less than 1.0. A general solution is rather complex but many practical applications can often be simplified and solved through use of the ladder-network method. In particular, the sign of the mutual inductance must be taken into account if there are a number of coupled circuits or if the phase of the voltage between two coupled circuits is important.

The latter consideration can be illustrated with the aid of Fig. 71A. An exact circuit for the two mutually coupled coils on the left is shown on the right. T1 is an "ideal" transformer that provides the "isolation" between terminals ab and cd. If the polarity of the voltages between these terminals can be neglected, the transformer can be eliminated and just the

circuit before terminals c'd substituted. A second circuit is shown in Fig. 71B. Here, it is assumed that the winding sense doesn't change between L1 and L2. Is so, then the circuit on the right of Fig. 71B can be substituted for the tapped coil shown at the left.

Coefficients of coupling for the circuits in Figs. 71A and 71B are given by

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$k = \frac{L_1 + M}{\sqrt{L_1(L_1 + L_2 + 2M)}}$$

If L1 and L2 do not have the same value, an interesting phenomenon takes place as the coupling is increased. A point is reached where the mutual inductance exceeds the inductance of the smaller coil. The interpretation of this effect can be illustrated with the aid of Fig. 72. While all of the flux lines (as indicated by the dashed lines) associated with L1 also encircle turns of L2, there are additional ones that encircle extra turns of L2, also. Thus, there are more flux lines for M than there are for L1. Consequently, M becomes larger than L1. Normally, this condition is difficult to obtain with air-wound coils but the addition of ferrite material greatly increases the coupling. As  $k$  increases so that M is larger than L1 (Fig. 72), the network begins to behave more like a transformer and for a  $k$  of 1, the equivalent circuit of Fig. 71A yields the transformer equations of a previous section. On the other hand, for small values of  $k$ , the network becomes merely three coils arranged in a "T" fashion. One advantage of the circuit of Fig. 12A is that

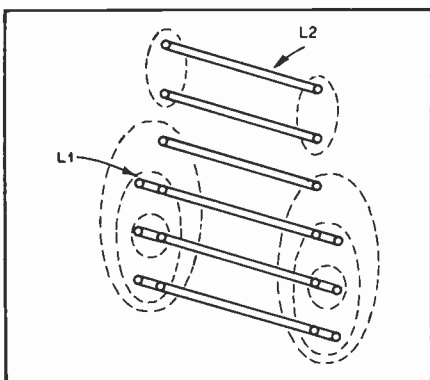


Fig. 72 — Diagram illustrating how M can be larger than one of the self inductances. This represents the transition from lightly coupled circuits to conventional transformers since an impedance step up is possible without the addition of capacitive elements.

there is no direct connection between the two coils. This property is important from an isolation standpoint and can be used to suppress unwanted currents that are often responsible for RFI difficulties.

### Matching Networks

In addition to filters, ladder networks are frequently used to match one impedance value to another one. While there are many such circuits, a few of them offer particular advantages such as simplicity of design formulas or minimum number of elements. Some of the more popular ones are shown in Fig. 73. Shown at Fig. 73A and 73B, are two variations of an "L" network. These networks are relatively simple to design.

The situation is somewhat more complicated for the circuits shown at 73C and 73D. For a given value of input and output resistance, there are many networks that satisfy the conditions for a perfect match. The difficulty can be resolved by introducing the "dummy variable" labeled N.

From a practical standpoint, N should be selected in order to optimize circuit component values. Either values of N that are too low or too high result in networks that are hard to construct.

The reason for this complication is as follows. Only two reactive elements are required to match any two resistances. Consequently, adding a third element introduces a redundancy. This means one element can be assigned a value arbitrarily and the other two components can then be found. For instance, suppose  $C_2$  in Fig. 73C is set to some particular value. The parallel combination of  $C_2$  and  $R_2$  can then be transformed to a series equivalent (see Fig. 74). Then, L could be found by breaking it down into two components,  $L'$  and  $L''$ . One component ( $L''$ ) would tune out the remaining capacitive reactance of the output series equivalent circuit. The network is then reduced to the one shown in Fig. 73A and the other component ( $L'$ ) of L along with the value for  $C_1$  could be determined from formulas (Fig. 73A). Adding the two inductive components would give the actual inductive reactance required for match in the circuit of Fig. 73C.

As mentioned before, it is evident an infinite number of networks of the form shown in Fig. 73C exist since  $C_2$  can be assigned any value. Either a set of tables or a family of curves for  $C_1$  and L in terms of  $C_2$  could then be determined from the foregoing method and as illustrated in Fig. 74. However, similar data along with other information can be obtained by approaching the problem somewhat differently. Instead of setting one of the element values arbitrarily and finding the other two, a third variable is contrived and in the case of Fig. 73C and Fig. 73D is labeled N. All three reactances are then expressed in terms of the variable N.

The manner in which the reactances

change with variation in  $N$  for two representative circuits of the type shown in Fig. 73C is shown in Fig. 75. The solid curve is for an  $R_1$  of 3000 ohms and  $R_2$  equal to 52 ohms. The dashed curve is for the same  $R_2$  (52 ohms) but with  $R_1$  equal to 75 ohms. For values of  $N$  very close to the minimum specified by the inequality (Fig 73C),  $X_{C2}$  becomes infinite which means  $C_2$  approaches zero. As might be expected, the values of  $X_L$  and  $X_{C1}$  at this point are approximately those of an L network (Fig 73A) and could be determined by means of the formulas in Fig 73A for the corresponding values of  $R_1$  and  $R_2$ .

The plots shown in Fig. 75 should give a general idea of the optimum range of component values. The region close to the left-hand portion should be avoided since there is little advantage to be gained over an L network, while an extra component is required. For very high values of  $N$ , the capacitance values become large without producing any particular advantage either. A good design choice is an  $N$  a few percent above the minimum specified by the inequality.

Quite often, one of the elements is fixed with either one or the other or both of the remaining two elements variable. In many amateur transmitters, it is the inductor that remains fixed (at least for a given band) while  $C_1$  and  $C_2$  (Fig 73C) are made variable. While this system limits the bandwidth and matching capability somewhat, it is still a very useful approach. For instance, the plot shown in Fig. 76 indicates the range of input resistance values that can be matched for an  $R_2$  of 52 ohms. The graph is for an inductive reactance of 219 ohms.  $X_{C1}$  varies from 196 to 206 ohms over the entire range of  $R_1$  (or approximately 20 percent). However,  $X_{C2}$  varies from 15 to almost 100 ohms as can be seen from the graph.

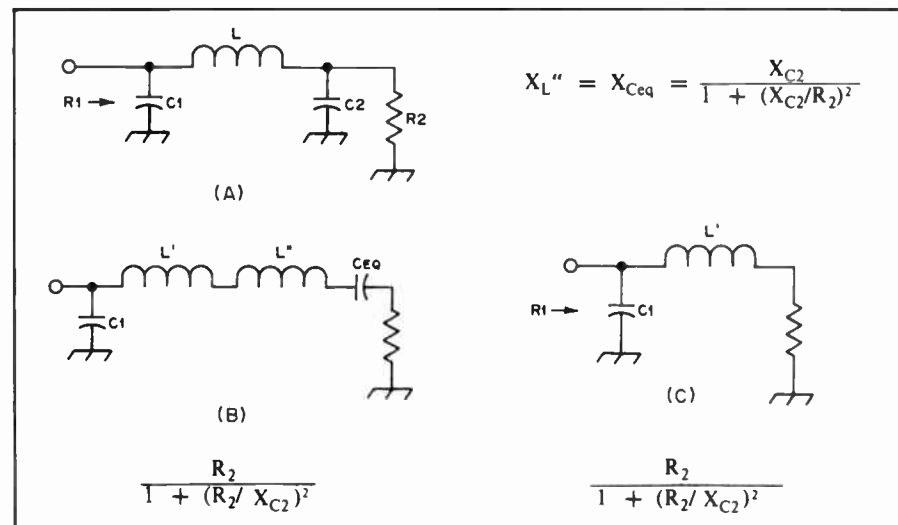


Fig. 74 — Illustration of the manner in which the network of Fig. 73C can be reduced to the one of Fig. 73A assuming  $C_2$  is assigned some arbitrary value. (The formulas shown are for numerical reactance values.)

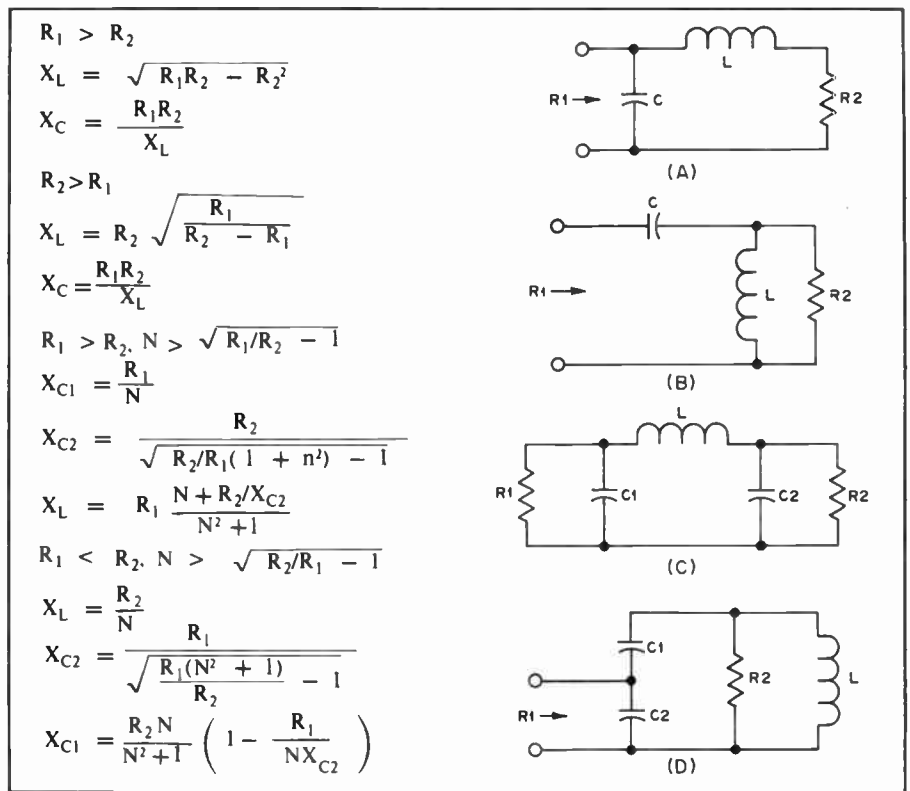


Fig. 73 — Four matching networks that can be used to couple a source and load with different resistance values. (Although networks are drawn with  $R_1$  appearing as the source resistance, all can be applied with  $R_2$  at the source end. Also, all formulas with capacitive reactance are for the numerical or absolute value.)

Since  $C_2$  more or less sets the transformed resistance, it is often referred to as the "loading" control on transmitters using the network of Fig. 73C, with  $C_1$  usually labeled "Tune." While the meaning of the latter term should be clear, the idea of loading in a matching application perhaps needs some explanation. For small values of  $X_{C2}$  (very large  $C_2$ ), the

transformed resistance is very high. Consequently, a source that was designed for a much lower resistance would deliver relatively little power. However, as the resistance is lowered, increasing amounts of current will flow resulting in more power output. Then, the resistance is said to be "loaded" more heavily.

Similar considerations such as those

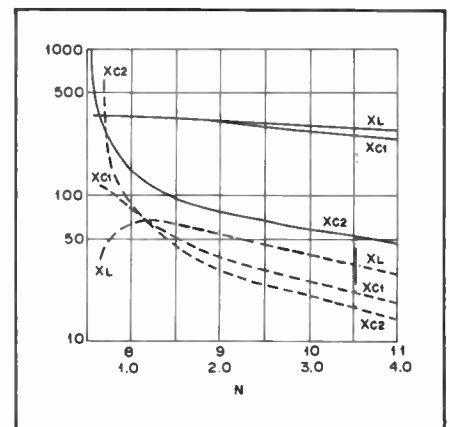


Fig. 75 — Network reactance variation as a function of dummy variable  $N$ . Solid curves and values of  $N$  from 8 to 11 are for an input resistance of 3000 ohms and an output resistance of 52 ohms. The dashed curves are for a similar network with an input and output resistance of 75 and 52 ohms, respectively. Values of  $N$  from 1 to 4 are for the latter curves.



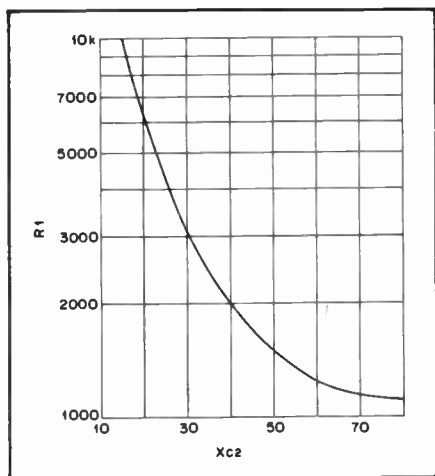


Fig. 76 — Input resistance vs. output reactance for an output resistance of 52 ohms. The curve is for a fixed inductor of 219 ohms (Fig. 73C).  $X_{C1}$  varies from 196 to 206 ohms.

discussed for the network of Fig. 73C also exist for the circuit of Fig. 73D. Only the limiting L network for the latter is the one shown in Fig. 73B. The circuit of Fig. 73C is usually called a pi network and as pointed out, it is used extensively in the output stage of transmitters. The circuit of Fig. 73D has never been given any special name, but it is quite popular in both antenna and transistor-matching applications.

The plot shown in Fig. 75 is for fixed input and output resistances with the reactances variable. Similar figures can be plotted for other combinations of fixed and variable elements. An interesting case is for  $X_L$  and  $R_1$  fixed with  $R_2$ ,  $X_{C1}$ , and  $X_{C2}$  variable. A lower limit for  $N$  also exists for this plot only instead of an L network, the limiting circuit is a network of three equal reactances. A feature of this

circuit is that the output resistance is the ratio of the square of the reactance and the input resistance. An analogous situation exists with a quarter-wavelength transmission-line transformer. The output resistance is the ratio of the square of the characteristic impedance of the line and the input resistance. Consequently, the special case where all the reactances are equal in the circuit of Fig. 73C is the lumped-constant analog of the quarter-wavelength transformer. It has identical phase shift (90 degrees) along with the same impedance-transforming properties.

### Frequency Response

In many instances, a matching network performing a dual role in transforming a resistance value while providing frequency rejection. Usually, matching versatility, component values, and number of elements are the most important considerations. But a matching network might also be able to provide sufficient selectivity for some application, thus eliminating the need for a separate circuit such as a filter.

It will be recalled that  $Q$  and selectivity are closely related for simple RLC series and parallel circuits. Bandwidth and the parameter  $N$  of Fig. 73 are approximately related in this manner. For values of  $N$  much greater than the minimum specified by the inequality  $N$  and  $Q$  can be considered to mean the same thing for all practical purposes. However, the frequency response of networks that are more complex than simple RLC types is usually more complicated also. Consequently, some care is required in the interpretation of  $N$  or  $Q$  in regard to frequency rejection. For instance, a simple circuit has a frequency response that results in increasing attenuation for increasing excursions from resonance. This is not true for the pi network as can be seen from Fig. 77. For slight frequency changes below resonance, the attenuation increases as in the case of a simple RLC network. At lower frequencies, the attenuation decreases and approaches 2.55 dB. This plot is for a resistance ratio of 5:1, and the low-frequency loss is just caused by the mismatch in source and load resistance. Thus, while increasing  $N$  improves the selectivity near resonance, it has little effect on response for frequencies much farther away.

A somewhat different situation exists for the circuit of Fig. 73D. At frequencies far from resonance, either a series capacitance provides decoupling at the lower frequencies or a shunt capacitance causes additional mismatch at the higher ones. This circuit then, has a response resembling those of simple circuits unlike the pi network. Curves a and b are for a resistance ratio of 5:1 with  $N$  equal to 2.01 for curve a. Curve b is for an  $N$  of 10. Curves c and d are for a resistance ratio of 50:1 with  $N$  equal to 7.04 and 10 respectively.

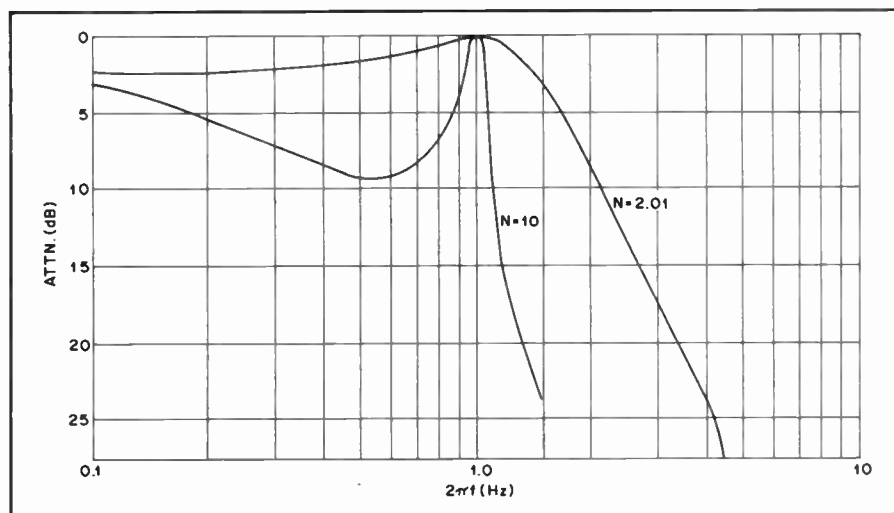


Fig. 77 — Frequency response of the network of Fig. 73C for two values of  $N$ .

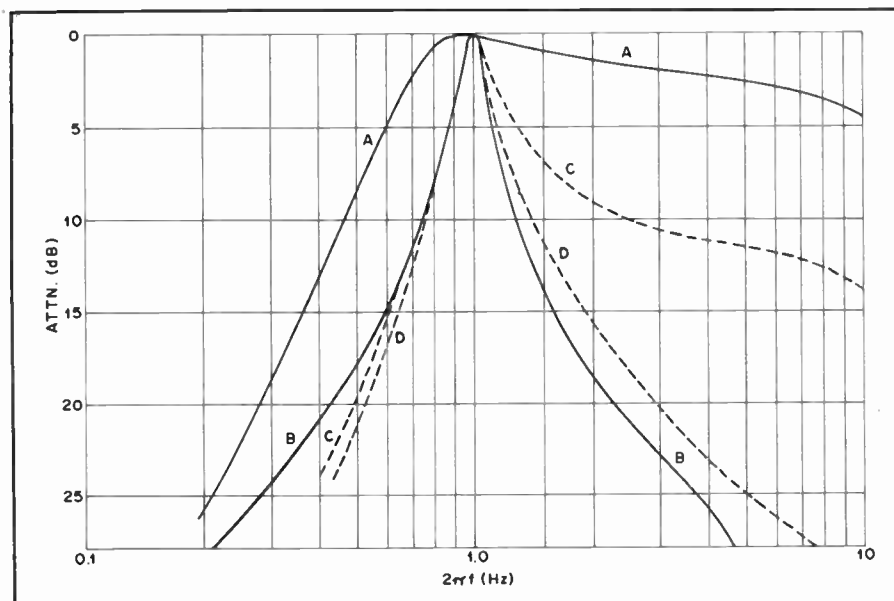


Fig. 78 — Frequency response of the circuit of Fig. 73D (see text).



# Radio Design Technique and Language

Many amateurs desire to construct their own radio equipment and some knowledge of design procedures becomes important. Even when some commercially manufactured equipment is used, these techniques may still be required in setting up peripheral equipment. Also, an applicant for an amateur radio license might be tested on material in this area.

### "Pure" vs. "Unpure" Components

In the chapter on electrical laws and circuits, it is assumed that the components in an electrical circuit consist solely of elements that can be reduced to a resistance, capacitance or inductance. However, such elements do not exist in nature. An inductor always has some resistance associated with its windings and a carbon-composition resistor becomes a complicated circuit as the frequency of operation is increased. Even conductor resistance must be taken into account if long runs of cable are required.

In many instances, the effects of these "parasitic" components can be neglected and the actual device can be approxi-

mated by a "pure" element such as a resistor, capacitor, inductor or a short circuit in the case of an interconnecting conductor. In other cases, the unwanted component must be taken into account. However, it may be possible to break the element down into a simple circuit consisting of single elements alone. Then, the actual circuit may be analyzed by means of the basic laws discussed in the previous chapter. It may be also possible to make a selection such that the effects of the residual element are negligible.

However, there are other parasitic elements that may not only be difficult to remove but will affect circuit operation adversely as well. In fact, such considerations often set a limit on how stringent a design criteria can be tolerated. For instance, it is a common practice to connect small-value capacitors in various parts of a complex circuit, such as a transmitter or receiver, for bypassing purposes. A bypass capacitor permits energy below some specified frequency to pass a given point while providing rejection to energy at higher frequencies. In essence, the capacitor is used in a crude form of filter. In more complicated filter designs, capacitors may be required for complex functions (such as matching) in addition to providing a low reactance to ground.

An equivalent circuit of a capacitor is shown in Fig. 1A. Normally, the series resistance,  $R_s$ , can be neglected. On the other hand, the upper frequency limit of the capacitor is limited by the series inductance,  $L_s$ . In fact, above the point where  $L_s$  and  $C_p$  form a resonant circuit, the capacitor actually appears as an inductor at the external terminals. As a result, it becomes useless for bypassing purposes. This is why it is common practice to use two capacitors in parallel for bypassing, as shown in Fig. 2. At first inspection, this might appear as superfluous duplication. But the "self-resonant"

frequency of a capacitor is lower for high-capacitance units than it is for smaller-value ones. Thus,  $C_1$  in Fig. 2 provides a low reactance for low frequencies such as those in the audio range while  $C_2$  acts as a bypass for frequencies above the self-resonant frequency of  $C_1$ .

### RF Leakage

Although the capacitor combination shown in Fig. 2 provides a low-impedance path to ground, it may not be very effective in preventing rf energy from reaching point 2 that travels along the conductor from point 1. At dc and low-frequency applications, a circuit must always form a closed path in order for a current to flow. Consequently, two conductors are required if power is to be delivered from a source to a load. In many instances, one of the conductors may be common to several other circuits and constitutes a local ground.

However, as the frequency of operation is increased, a second type of coupling mechanism is possible. Power may be transmitted *along a single conductor*. (Although the same effect is possible at low frequencies, unless circuit dimensions are extremely large, such transmission effects can be neglected.) The conductor acts as a waveguide in much the same manner as a large conducting surface, such as the earth, will permit propagation of a radio wave close to its boundary with the air. This latter type of propagation is often called a ground wave and is important up to and slightly above the standard a-m broadcast band. At higher frequencies, the conductivity of the earth is such to attenuate ground-wave propagation.

A mode similar to ground-wave propagation that can travel along the boundary of a single conductor is illustrated by the dashed lines in Fig. 2. As with the wave traveling close to the earth, a poor conducting boundary will cause attenuation.

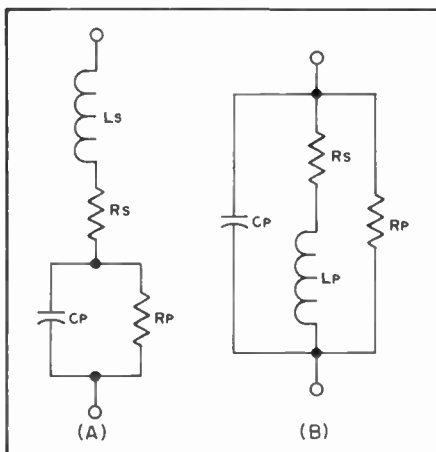


Fig. 1 — Equivalent circuit of a capacitor is shown at A, and for an inductor in B.

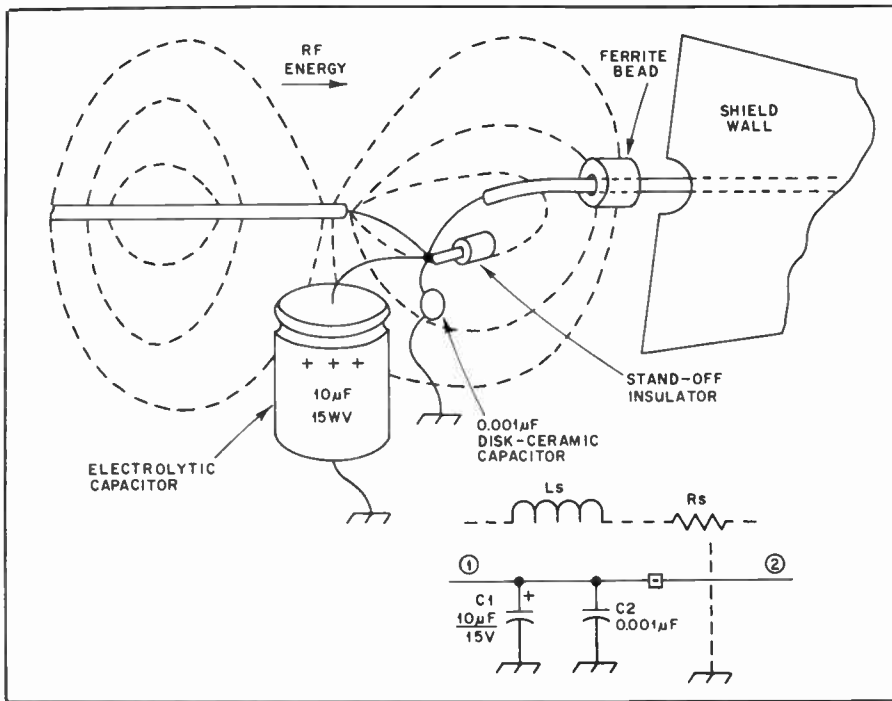


Fig. 2 — A bypassing arrangement that affords some measure of isolation (with the equivalent circuit shown in the inset). Dashed lines indicate a mode of wave travel that permits rf energy to leak past the bypass circuitry and should be taken into account when more stringent suppression requirements are necessary. ( $L_s$  and  $R_s$  in the inset represent the equivalent circuit of the ferrite bead.)

This is why a ferrite bead is often inserted over the exit point of a conductor from an area where rf energy is to be contained or excluded. In addition to loss (particularly in the vhf range), the high permeability of the ferrite introduces a series-inductive reactance as well. Finally, the shield wall provides further isolation.

While the techniques shown in Fig. 2 get around some of the deficiencies of capacitors that are used for bypass purposes, the resulting suppression is inadequate for a number of applications. Examples would be protection of a VFO to surrounding rf energy, a low-frequency receiver with a digital display, and suppression of radiated harmonic energy from a transmitter. In each of these cases, a very high degree of isolation is required. For instance, a VFO is sensitive to voltages that appear on dc power supply lines and a transmitter output with a note that sounds “fuzzy” or rough may result. Digital displays usually generate copious rf energy in the low-frequency spectrum. Consequently, a receiver designed for this range presents a situation where a strong source of emission is in close proximity to very sensitive receiving circuits. A similar case exists with transmitters operating on a frequency that is a submultiple of a fringe-area TV station. In the latter two instances, the problem is not so severe if the desired signal is strong enough to “override” the unwanted energy. Unfortunately, this is not the case normally and stringent measures are required to isolate the sensitive circuits from the strong source.

A different type of bypass-capacitor configuration is often used with associated shielding for such applications, as shown in Fig. 3. In order to reduce the series inductance of the capacitor, and to provide better isolation between points 1 and 2, either a disk-type (Fig. 3A) or a coaxial configuration (Fig. 3B) is employed. The circuit diagram for either configuration is shown in the inset. While such “feedthrough” capacitors are always connected to ground through the shield, this connection is often omitted on drawings. Only a connection to ground is shown, as in the inset in Fig. 3.

#### Dielectric Loss

Even though capacitors are usually high-Q devices, the effect of internal loss can be more severe than the case of a coil. This is because good insulators of electricity are usually good insulators of heat also. Therefore, heat generated in a capacitor must be conducted to the outside via the conducting plates to the capacitor leads. In addition, most capacitors are covered with an insulating coating that further impedes heat conduction. The problem is less severe with capacitors using air as a dielectric for two reasons. The first advantage of air over other dielectrics is that the loss in the presence of an alternating electric field is extremely small. Secondly, any heat generated by currents on the surface of the conducting plates is either conducted away by air currents or through the mass of the metal.

The dielectric loss in a capacitor can be

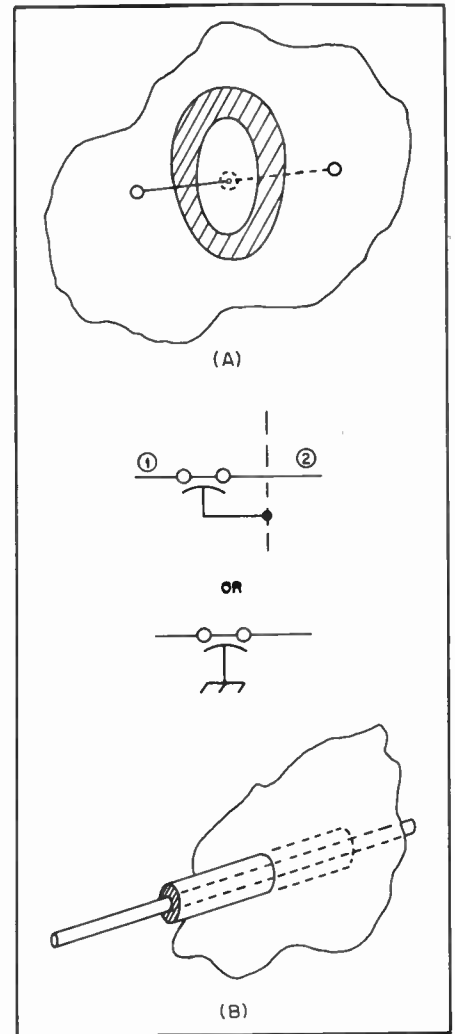


Fig. 3 — A superior type of bypassing arrangement to that shown in Fig. 2. Concentric conductors provide a low-inductance path to ground and better rejection of unwanted single-wire wave modes.

represented by  $R_p$  as shown in Fig. 1A. However, if a dc ohmmeter was placed across the terminals of the capacitor, the reading would be infinite. This is because dielectric loss is an ac effect. Whenever an alternating electric field is applied to an insulator, there is a local motion of the electrons in the individual atoms that make up the material. Even though the electrons are not displaced as they would be in a conductor, this local motion requires the expenditure of energy and results in a power loss.

Consequently, some care is required in the application of capacitors in moderate to high-power circuits. The applied voltage should be such that rf-current ratings are not exceeded for the particular frequency of operation. This is illustrated in Fig. 4. A parallel-resonant circuit consisting of  $L_p$ ,  $C_p$  and  $R_L$  is connected to a voltage source,  $V_s$ , through a coupling capacitor,  $C_c$ . It is also assumed the  $R_L$  is much greater than either the inductive or capacitive reactance taken alone. This

condition would be typical of that found in most rf-power amplifier circuits employing vacuum tubes.

Since the inductive and capacitive reactance of  $L_p$  and  $C_p$  cancel at resonance, the load presented to the source would be just  $R_L$ . This would mean the current through  $C_c$  would be much less than the current through either  $C_p$  or  $L_p$ . The effect of such "current rise" is similar to the voltage rise at resonance discussed in the previous chapter. Even though the current at the input of the parallel-resonant circuit is small, the currents that flow in the elements that make up the circuit can be quite large.

The requirements for  $C_c$  then, would be rather easy to satisfy in regards to current rating and power dissipation. On the other hand,  $C_p$  would ordinarily be restricted to air-variable types although some experiments have been successful using Teflon as a dielectric.<sup>1</sup> Generally speaking, the coupling capacitor should have a low reactance (at the lowest frequency of operation) in comparison to the load presented by the tuned circuit. The effect of the coupling-capacitor reactance could then be compensated by slightly retuning the parallel-resonant circuit.

### Inductors

Similar considerations to those discussed in the previous sections exist with inductors also, as shown in Fig. 1B. Since an inductor usually consists of a coil of wire, there will be a resistance associated with the wire material and this component is represented by  $R_s$  (Fig. 1B). In addition, there is always a capacitance associated with conductors in proximity as illustrated in Fig. 5. While such capacitance is distributed throughout the coil, it is a convenient approximation to consider an equivalent capacitance,  $C_p$ , exists between the terminals (Fig. 1B). Finally, inductors are often wound on materials that have high permeability in order to increase the inductance. Thus, it is possible to build an inductor with fewer turns and smaller in size than an equivalent coil with an "air core."

Unfortunately, high-permeability materials presently available have considerable loss in the presence of an rf field. It will be recalled a similar condition existed with the dielectric in a capacitor. Consequently, in addition to the wire resistance, a loss resistance is associated with the core and represented by  $R_p$ . (See Fig. 1B.) Since this loss is more or less independent of the current through the coil but dependent upon the applied voltage, it is represented by a parallel resistance.

### RF Transformers

Although the term transformer might be applied to any network that "trans-

<sup>1</sup>DeMaw and Dorbuck, "Transmitting Variables," QST February, 1975.

formed" a voltage or an impedance from one level to another one, the term is usually reserved for circuits incorporating mutual magnetic coupling. Examples would be i-f transformers, baluns, broadband transformers, and certain antenna matching networks (see chapter 2). Of course, many devices used at audio and power frequencies are also transformers in the sense used here and have been covered in a previous chapter.

Networks that use mutual magnetic coupling exclusively have attractive advantages over other types in many common applications. A principal advantage is that there is no direct connection between the input and output terminals. Consequently, dc and ac components of current are separated easily thus eliminating the need for coupling capacitors. Perhaps even more importantly, it is also possible to isolate rf currents because of the lack of a common conductor. Quite often, an hf receiver in an area where strong local broadcast stations are present will suffer from "broadcast harmonics" and possibly even rectified audio signals getting into sensitive af circuits. In such cases, complicated filters sometimes prove ineffective while a simple tuned rf transformer clears up the problem completely. This is because the unwanted bc components are prevented from flowing on the receiver chassis along with being rejected by the tuned-transformer filter characteristic.

A second advantage of coupled circuits using mutual magnetic coupling exclusively is that analysis is relatively simple compared to other forms of coupling although exact synthesis is somewhat complicated. That is, finding a network with some desired frequency response would be quite difficult in the general case.

However, circuits using mutual-magnetic coupling usually have very good out-of-band rejection characteristics when compared to networks incorporating other forms. (A term sometimes applied to transformer or mutual-magnetic coupling is *indirect coupling*. Circuits with a single resistive or reactive element for the common impedance are called direct-coupled networks. Two or more elements in the common impedance are said to comprise complex coupling.) For instance, relatively simple band-pass filters are possible with mutual-magnetic coupling and are highly recommended for vhf-transmitter multiplier chains. For receiving, such filters are often the main source of selectivity. Standard a-m and fm broadcast receivers would be examples where intermediate-frequency (i-f) transformers derive their band-pass characteristics from mutually coupled inductors.

A third advantage of mutually coupled networks is that practical circuits with great flexibility particularly in regard to matching capabilities are possible. For

this reason, variable-coupling matching networks or those using "link coupling" have been popular for many years. In addition to matching flexibility, these circuits are good band-pass filters and can also provide isolation between antenna circuits and those of the transmitter.

### Design Formulas

A basic two-mesh circuit with mutual magnetic coupling is shown in Fig. 6. The reactance,  $X$ , is arbitrary and could be either inductive or capacitive. However, it is convenient to combine it with the secondary reactance ( $X_L$ ) since this makes the equations somewhat more compact. Hence, the total secondary reactance is defined by

$$X_s = 2\pi fL_s + X$$

The primary reactance and mutual reactance are also defined respectively as

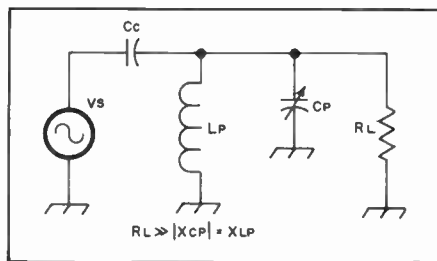


Fig. 4 — Consideration of capacitor voltage and current ratings should be kept in mind in moderate-power applications.

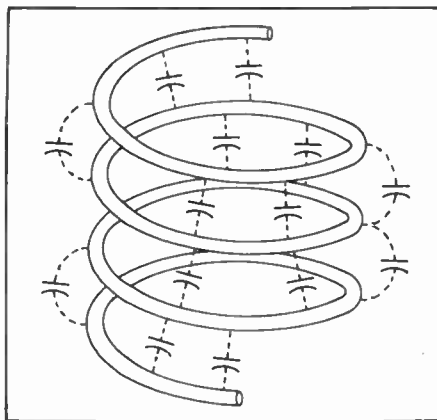


Fig. 5 — Distributed capacitance (indicated by dashed lines) affects the operation of a coil at high frequencies.

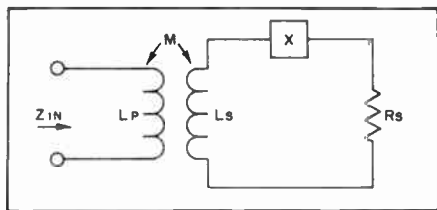


Fig. 6 — Basic magnetically coupled circuit.



$$X_p = 2\pi fL_p, X_m = 2\pi fM$$

A set of equations for the input resistance and reactance is given by

$$R_{in} = \frac{R_s X_m^2}{R_s^2 + X_s^2}$$

$$X_{in} = X_p - \frac{X_m^2 X_s}{R_s^2 + X_s^2}$$

This permits reducing the two-mesh circuit of Fig. 6 to the single-mesh circuit of Fig. 7.

### Double-Tuned Circuits

A special case occurs if the value of  $X_s$  is zero. This could be accomplished easily by tuning out the inductive reactance of the secondary with an appropriate capacitor or by varying the frequency until a fixed capacitor and the secondary inductance resonated. Under these conditions, the input resistance and reactance would be

$$R_{in} = \frac{X_m^2}{R_s}, X_{in} = X_p$$

Then, in order to make the input impedance purely resistive, a second series capacitor could be used to cancel the reactance of  $X_p$ . The completed network is shown in Fig. 8 with  $C_1$  and  $C_2$  being the primary and secondary series capacitors.

If  $X_m$  could be varied, it is evident that the secondary resistance could be transformed to almost any value of input resistance. Usually, the desired resistance, would be made equal to the generator resistance,  $R_g$ , for maximum power transfer. It might also be selected to satisfy some design goal, not necessarily related to maximum power transfer. This brings up a minor point but one that can cause considerable confusion. Normally, in transmitting circuits, the "unloaded Q" of the reactive components would be very high and the series parasitic resistances (discussed in a previous section) could be neglected. However, if it is not desired to do so, how should these resistances be taken into account? If maximum power transfer is the goal, the series resistance of the primary coil would be added to the generator resistance,  $R_g$ , and the transformed secondary resistance would be made equal to this sum.

On the other hand, a more common case requires the *total* input resistance to be equal to some desired value. For instance, an amplifier might provide optimum efficiency or harmonic suppression when terminated in a particular load resistance. Transmission lines also require a given load resistance in order to be "matched." In such cases, the series resistance of the primary coil would be

subtracted from the actual resistance desired and the transformed resistance made equal to this difference. As an example, suppose an amplifier required a load resistance of 3000 ohms, and the primary-coil resistance was 100 ohms. Then, the transformed resistance must be equal to 2900 ohms. (In either case, the secondary coil resistance is merely added to the secondary load resistance and the sum substituted for  $R_s$ .)

### Coefficient of Coupling

Although the equations for the input impedance can be solved in terms of the mutual reactance, the transforming mechanism involved becomes somewhat clearer if the coefficient of coupling is used instead. The coefficient of coupling,  $k$ , in terms of the corresponding reactances of inductances is

$$k = \frac{X_m}{\sqrt{X_p X_s}} = \frac{L_m}{\sqrt{L_p L_s}}$$

Then, the input resistance becomes

$$R_{in} = \frac{k^2 X_p X_s}{R_s}$$

The primary and secondary Qs are defined as

$$Q_p = \frac{X_p}{R_g}, Q_s = \frac{X_s}{R_s}$$

where a "loaded" Q is assumed. This would mean  $R_s$  included any secondary-coil loss. For maximum-power transfer,  $R_g$  would be the total primary resistance which consists of the generator and coil resistance.

The coefficient of coupling under these conditions reduces to a rather simple formula

$$k_c = \frac{1}{\sqrt{Q_p Q_s}}$$

However, if it is desired to make the input resistance some particular value (as in the case of the previous example), the coefficient of coupling is then

$$k_c = \sqrt{\frac{R_{in} - R_p}{X_p Q_s}}$$

If the primary "loss" resistance is zero, both formulas are identical.

At values of  $k$  less than  $k_c$ , the input resistance is lower than either the prescribed value or for conditions of maximum power transfer. Higher values of  $k$  result in a higher input resistance. For this reason,  $k_c$  is called the critical coefficient of coupling. If  $k$  is less than  $k_c$ , the circuit is said to be undercoupled and for  $k$  greater than  $k_c$ , an overcoupled condition results. A plot of attenuation vs. frequency for the three cases is shown in Fig.

9. Critical coupling gives the flattest response although greater bandwidth can be obtained by increasing  $k$  to approximately 1.5  $k_c$ . At higher values, a pronounced dip occurs at the center or resonant frequency.

In the undercoupled case, a peak occurs at the resonant frequency of the primary and secondary circuit but the transformed resistance is too low and results in a mismatch. As the coupling is decreased still further, very little power is transferred to the secondary circuit and most of it is dissipated in the primary-loss and generator-source resistances. On the other hand, an interesting phenomenon occurs with the overcoupled case. It will be recalled that the transformed resistance is too high at resonance because the coefficient of coupling is greater than the critical value. However, a special case occurs if the primary and secondary circuits are identical which also means the transformed resistance,  $R_{in}$  must equal  $R_s$ .

The behavior of the circuit under these conditions can be analyzed with the aid of Fig. 7. Assuming the Q of both circuits is high enough, the reactance,  $X_s$ , increases very rapidly on either side of resonance. If this variation is much greater than the variation of  $X_m$  with frequency, a frequency exists on each side of resonance where the ratio of  $X_m^2$  and  $R_s^2 + X_s^2$  is 1.0. Consequently,  $R_{in}$  is equal to  $R_s$  and the transformed reactance is  $-X_s$ . Since the primary and secondary resonators are identical, the reactances cancel because of the minus sign. The frequency plot for a  $k$  of 0.2 ( $k_c$  is 0.1) is shown in Fig. 9. If the primary and secondary circuits are not identical, a double-hump response still

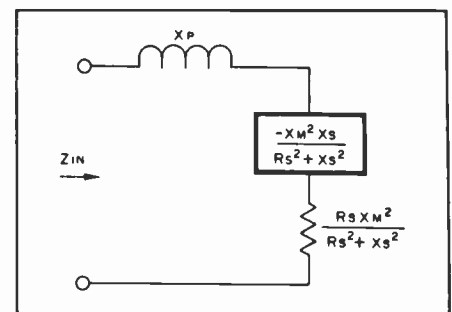


Fig. 7 — Equivalent single-mesh network of the two-mesh circuit of Fig. 6.

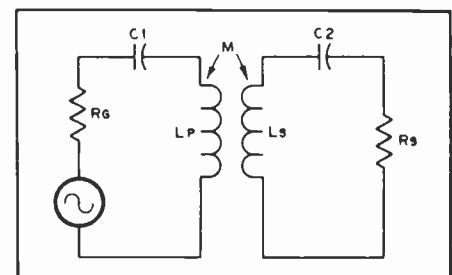


Fig. 8 — Double-tuned series circuits with magnetic coupling.



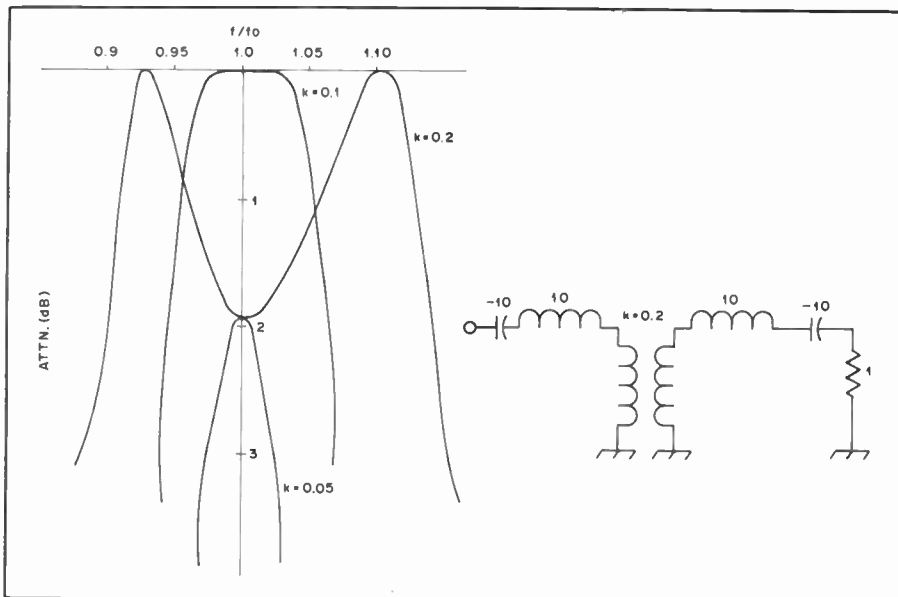


Fig. 9 — Response curves for various degrees of coupling coefficient  $k$ . The critical coefficient of coupling for the network shown in the inset is 0.1. Lower values give a single response peak (but less than maximum power transfer) while "tighter" coupling results in a double-peak response.

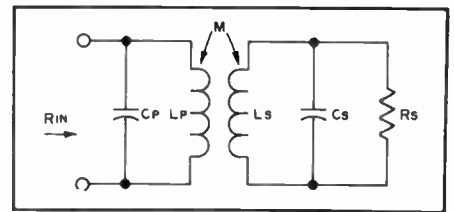


Fig. 10 — Coupled network with parallel-tuned circuits or "i-f" transformer.

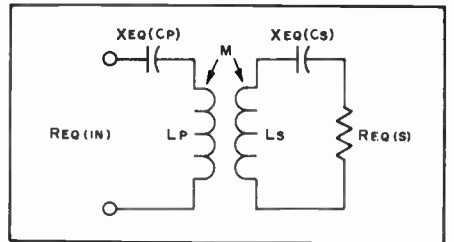


Fig. 11 — Equivalent series circuit of the parallel network shown in Fig. 10. This transformation is only valid at single frequencies and must be revalued if the frequency is changed.

occurs but the points where the transformed resistance is equal to the desired value, the reactances are not the same numerically. Consequently, there is attenuation at peaks unlike the curve of Fig. 9.

### Other Circuit Forms

While the coupled network shown in Fig. 8 is the easiest to analyze, it is not commonly encountered in actual circuits. As the resistance levels are increased, the corresponding reactances become very large also. In transmitting circuits, extremely high voltages are then developed across the coils and capacitors. For high-impedance circuits, the circuit shown in Fig. 10 is often used. Although the frequency response is somewhat different than the circuit of Fig. 8 (in fact, the out-of-band rejection is greater), a matching network can be designed based upon the previous analysis for the series circuit.

This is accomplished by changing the parallel primary and secondary circuits to series equivalents. (It should be emphasized that this transformation is good at one frequency only.) The equivalent circuit of the one shown in Fig. 10 is illustrated in Fig. 11 where the new resistance and reactance of the secondary are given by

$$R_{eq}(S) = \frac{R_s}{1 + \gamma^2}$$

$$X_{eq}(C_s) = \frac{-R_s \gamma}{1 + \gamma^2}$$

$$\gamma = R_s/X_c$$

A similar set of transformations exists for the primary circuit also. In most in-

stances, where one high-impedance load is matched to another one,  $R_s$  in Fig. 10 is much greater than the reactance of  $C_s$  and  $C_p$ . This simplifies the transformations and approximate relations are given by

$$R_{eq}(S) \cong \frac{X_c^2}{R_s}$$

$$X_{eq}(C_s) \cong X_c$$

As an example, suppose it was desired to match a 3000-ohm load to a 5000-ohm source using a coupled inductor with a 250-ohm (reactance) primary and secondary coil. Assume the coupling can be varied. Determine the circuit configuration and the critical coefficient of coupling.

Since the load and source resistance have a much higher numerical value than the reactance of the inductors, a parallel-tuned configuration must be used. In order to tune out the inductive reactance, the equivalent series capacitive reactance must be  $-250$  ohms. Since both  $R_s$  and  $R_p$  are known, the exact formulas could be solved for  $\gamma$  and  $R_{eq}$ . However, because the respective resistances are much greater than the reactance, the simplified approximate formulas can be used. This means the primary and secondary equivalent capacitive reactances are  $-250$  ohms. The equivalent secondary resistance is  $(250)^2/3000$  or 20.83 ohms resulting in a secondary  $Q$  of  $250/20.83$  or 12. (A formula could be derived directly for the  $Q$  from the approximate equations.) The equivalent primary resistance and  $Q$  are 12.5 ohms and 20, respectively. Substituting the values for  $Q$  into the formula for the critical coefficient of coupling gives  $1/\sqrt{(20)(12)}$  or 0.065.

Double-tuned coupled circuits of the

type shown in Fig. 10 are widely used in radio circuits. Perhaps the most common example is the i-f transformer found in a-m and fm bc sets. Many communications receivers have similar transformers although the trend has been toward somewhat different circuits. Instead of achieving selectivity by means of i-f transformers (which may require a number of stages), a single filter with quartz-crystal resonators is used instead. (The subject of receivers is treated in a later chapter.)

### Single-Tuned Circuits

In the case of double-tuned circuits, separate capacitors are used to tune out the inductive components of the primary and secondary windings. However, examination of the equivalent circuit of the coupled coil shown in Fig. 7 suggests an alternative. Instead of a separate capacitor, why not "detune" a resonant circuit slightly and "reflect" a reactance of the proper sign into the primary in order to tune out the primary inductance. Since the transformation function (shown in the box in Fig. 7) reverses the sign of the secondary reactance, it is evident  $X_s$  must be *inductive* in order to tune out the primary inductance.

This might seem to be a strange result but it can be explained with the following reasoning. From a mathematical point of view, the choice of the algebraic sign of the transformed reactance is perfectly arbitrary. That is, a set of solutions to the equations governing the coupled circuit is possible assuming either a positive or negative sign for the transformed reactance. However, if the positive sign is chosen, the transformed resistance *would be negative*. But from a physical point of

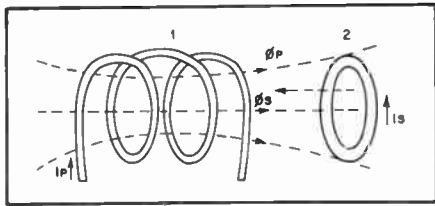


Fig. 12 — A coil coupled magnetically to a "shorted" turn provides insight to coils near solid shield walls.

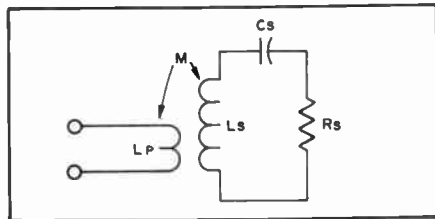


Fig. 13 — "Link" coupling can be used to analyze a number of important circuits.

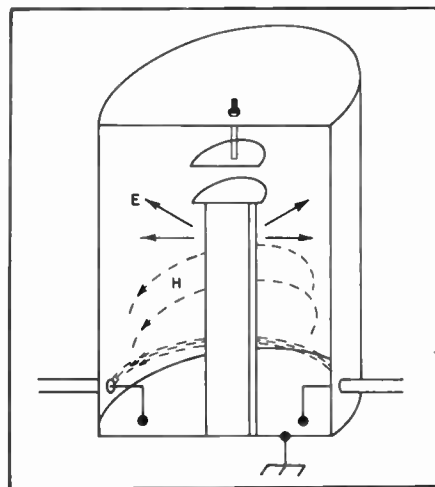


Fig. 14 — A vhf/uhf circuit which can be approximated by a link-coupled network using "conventional" components.

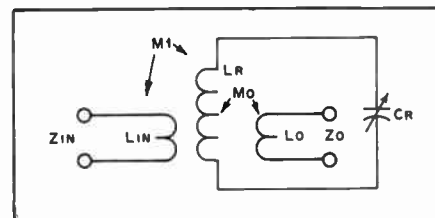


Fig. 15 — Equivalent low-frequency analog of the circuit shown in Fig. 14.

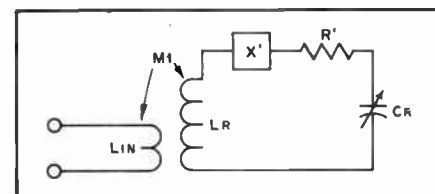


Fig. 16 — The network of Fig. 15 can be reduced with the transformation shown in Fig. 7.

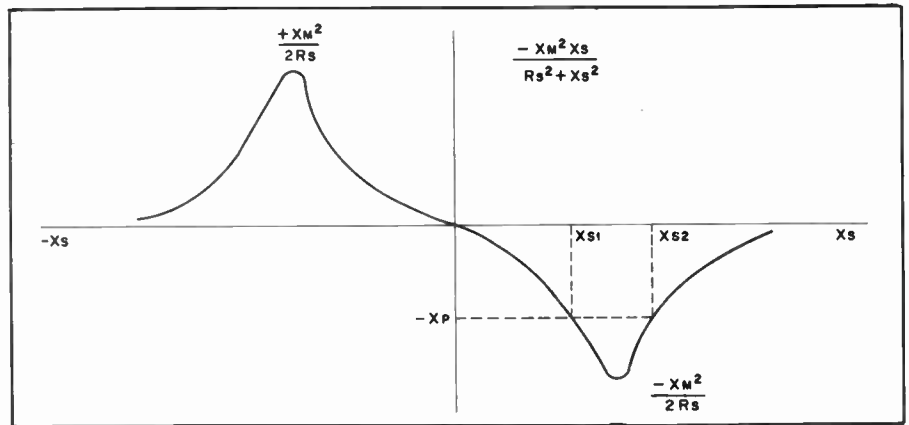


Fig. 17 — "Reflected" reactance into the primary of a single-tuned circuit places restraints on resistances that can be matched. This gives rise to a general rule that high-Q secondary circuits require a lower coefficient of coupling than low-Q ones.

view, this is a violation of the conservation of energy since it would imply the secondary resistance acts as a source of energy rather than an energy "sink." Consequently, the solution with the negative resistance does not result in a physically realizable network.

The foregoing phenomenon has implications for circuits one might not normally expect to be related to coupled networks. For instance, consider coil 1 (Fig. 12) in proximity to the one-turn "shorted" coil 2. A time-varying current in coil 1 will induce a current in coil 2. In turn, the induced current will set up a magnetic field of its own. The question is will the induced field aid or oppose the primary field. Since the energy in a magnetic field is proportional to the square of the flux, the induced field must oppose the primary field, otherwise the principle of the conservation of energy would be violated as it was with the "negative" resistance. Consequently, the induced current must always be in a direction such that the induced field opposes changes in the generating field. This result is often referred to as Lenz's Law.

If, instead of a one-turn loop, a solid shield wall was substituted, a similar phenomenon would occur. Since the total flux (for a given current) would be less with the shield present than it would be in the absence of the shield, the equivalent coil inductance is decreased. That is why it is important to use a shield around a coil that is big enough to reduce the effect of such coupling. Also, a shield made from a metal with a high conductivity such as copper or aluminum is advisable, otherwise a loss resistance will be coupled into the coil as well.

#### Link Coupling

An example of a very important class of single-tuned circuits is shown in Fig. 13. The primary inductor consists of a small coil either in close proximity or wound over one end of a larger coil. Two

resonators can be coupled in this manner although there may be considerable separation (and no mutual coupling between the larger coils) hence the term "link" coupling. While this particular method is seldom used nowadays, the term is still applied to the basic configuration shown in Fig. 13. Applications would be antenna-matching networks, output stages for amplifiers and, especially important, many circuits used at vhf that have no direct hf equivalent.

The cavity resonators used in repeater duplexers are one form of vhf circuit that uses link coupling. A cross-sectional view of a representative type is shown in Fig. 14. Instead of ordinary coils and capacitors, a section of coaxial transmission line comprises the resonant circuit. The frequency of the resonator may be varied by adjusting the tuning screw which changes the value of the capacitor. Energy is coupled into and out of the resonator by means of two small, one-turn loops. Current in the input loop causes a magnetic field (shown by dashed lines). If the frequency of the generating field is near one of the resonant "modes" of the configuration, an electric field will also be generated (shown by solid lines). Finally, energy may then be coupled out of the resonator by means of a second loop.

A low-frequency equivalent circuit of the resonator is shown in Fig. 15. However, the circuit can only be used to give an approximate idea of the actual frequency response of the cavity. At frequencies not close to the resonant frequency, the mathematical laws governing resonant circuits are different from those of "discrete" components used at hf. Over a limited frequency range, the resonator can be approximated by the series LC circuit shown in Fig. 15.

Applying the formulas for coupled networks shown in Fig. 7 to the two-link circuit of Fig. 15, the output link and load can be transformed to an equivalent series resistance and reactance as shown in Fig. 16. In most instances, the reactance,  $X_s$ , in

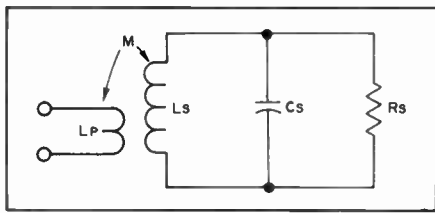


Fig. 18 — Single-tuned circuit with a parallel RC secondary.

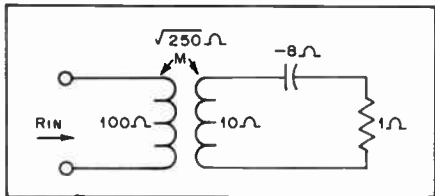


Fig. 19 — Text example of a single-tuned circuit.

the formula is just the reactance of the output link. Since the two-link network has been reduced to a single coupled circuit, the formulas can be applied again to find the input resistance and reactance.

### Analysis of Single-Tuned Circuits

Single-tuned circuits are very easy to construct and adjust experimentally. If desired, the tuned circuit consisting of  $L_s$ ,  $C_s$ , and perhaps the load,  $R_s$ , can be constructed first and tuned to the "natural" resonant frequency

$$f_0 = \frac{1}{2\pi \sqrt{L_s C_s}}$$

Then, the primary inductor, which may be a link or a larger coil, is brought into proximity of the resonant circuit. The resonant frequency will usually shift upward. For instance, a coil and capacitor combination was tuned to resonance by means of a grid-dip oscillator (see the chapter on measurements) at a frequency of 1.8 MHz. When a two-turn link was wound over the coil, and coupled to the grid-dip oscillator the resonant frequency had increased to 1.9 MHz. A three-turn link caused a change to 2 MHz.

Quite often an actual load may be an unknown quantity, such as an antenna, and some insight into the effects of the various elements is helpful in predicting single-tuned circuit operation. Usually, as in the case of most matching networks,  $R_s$  (Fig. 7) and the input resistance are specified with the reactive components being the variables. Unfortunately, the variables in the case of mutually coupled networks are not independent of each other which complicates matters somewhat.

Examination of the equivalent circuit shown in Fig. 7 would indicate the first condition is that the reactance reflected from the secondary into the primary be sufficient to tune out the primary reactance. Otherwise, even though the proper resistance transformation is obtainable, a reactive component would always be

present. A plot of the reflected reactance as a function of  $X_s$  is shown in Fig. 17. From mathematical considerations (which will not be discussed) it can be shown that the maximum and minimum of the curve have a value equal to  $X_m^2/2R_s$ . Consequently, this value must be greater than or equal to  $X_p$  in order that a value of  $X_s$  exists such that the reflected reactance will cancel  $X_p$ . In the usual case where  $X_m^2/2R_s$  is greater than  $X_p$ , it is interesting to note that two values of  $X_s$  exist where  $X_p$  and the reflected reactance cancel. This means there are two cases where the input impedance is purely resistive and  $R_s$  could be matched to either one of two source resistances if so desired. The value of  $X_s$  at these points is designated as  $X_{s1}$  and  $X_{s2}$ .

On the other hand, a high value of  $R_s$  requires  $X_m$  to be large also. This could be accomplished by increasing the coefficient of coupling or by increasing the turns on the secondary coil. Increasing the turns on the primary also will cause  $X_m$  to be higher but  $X_p$  will increase also. This is somewhat self-defeating since  $X_m^2$  is proportional to  $X_p$ .

An alternate approach is to use the parallel configuration of Fig. 18. The approximate equivalent series resistance of the parallel combination is then  $X(C_s)^2/R_s$  and the reactance is approximately  $X(C_s)$ . (See diagram and text for Fig. 11.) This approach is often used in multiband antenna systems. On some frequencies, the impedance at the input of the feed line is high so the circuit of Fig. 18 is employed. This is referred to as parallel tuning. If the impedance is very low, the circuit of Fig. 13 is used and is called series tuning.

As an example, suppose a single-tuned circuit is to be used to match a 1-ohm load to a 50-ohm source as shown in Fig. 19. It might be pointed out at this juncture that coupling networks using mutual magnetic coupling can be scaled in the same manner that filter networks are scaled (as discussed in chapter 2). For instance, the circuit of Fig. 19 could be scaled in order to match a 50-ohm load to a 2500-ohm source merely by multiplying all the reactances by a factor of 50.

The input resistance and reactance of the circuit of Fig. 19 are plotted in Figs. 20 and 21, respectively. As pointed out earlier, there are two possible points where the reactance is zero and this circuit could be used to match the 1-ohm load to either a 50-ohm or 155-ohm source. Assuming a 50-ohm source was being used, the attenuation plot as a function of frequency would be given by the solid curve in Fig. 22.

With slight modification to include the effect of the source, the transformation of Fig. 7 can be applied to the primary side of the coupled circuit shown in Fig. 19. This is illustrated in Fig. 23. The complete circuit is shown at Fig. 23A and the network with the transformed primary

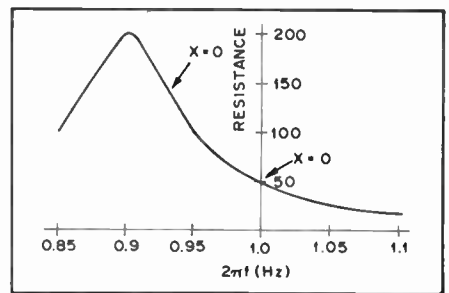


Fig. 20 — Input resistance of the Fig. 19 circuit as a function of frequency.

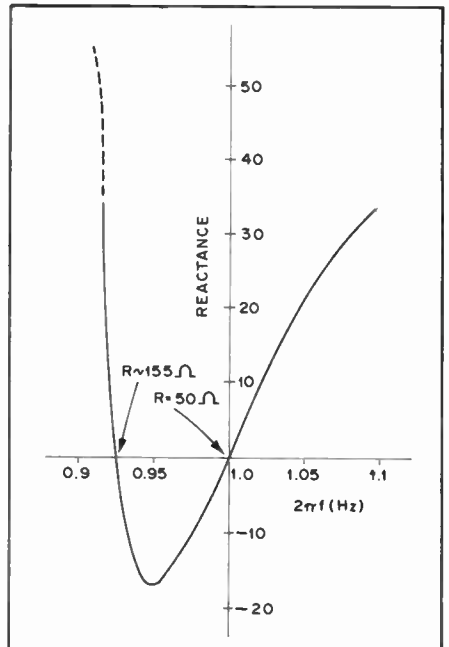


Fig. 21 — Input reactance of the Fig. 19 network. Note two "resonant" frequencies (where reactance is zero).

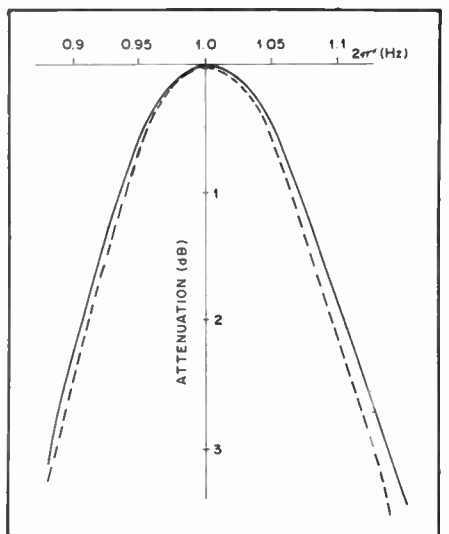


Fig. 22 — Response of the circuit shown in Fig. 19.

resistance and reactance is shown in Fig. 23B.

In a lossless transformer, the maximum available power at the secondary must be the same as that of the original source on the primary side neglecting the effects of reactance. That is, the power delivered to

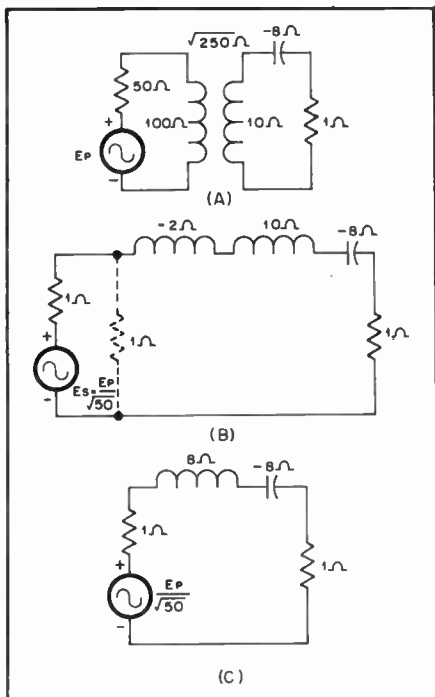


Fig. 23 — The transformation of Fig. 7 applied to the primary side of the circuit of Fig. 19.

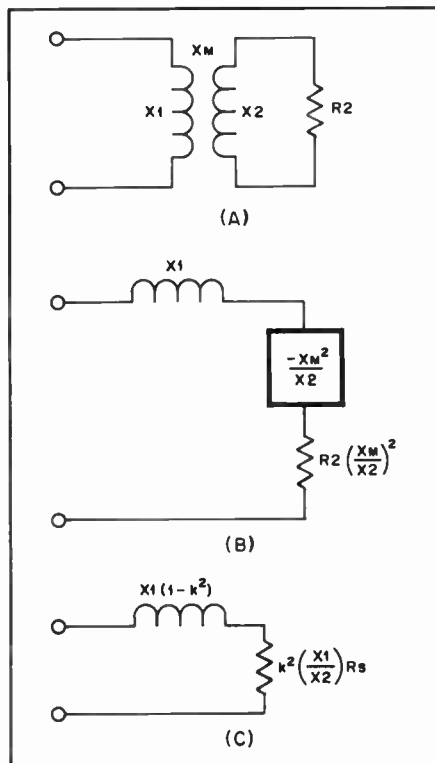


Fig. 24 — Equivalent-circuit approximation of two coupled coils.

a 1-ohm resistance (shown as a dashed line in Fig. 23B) must be the same as that delivered to a 50-ohm load in Fig. 23A. This assumes that the rest of the circuit has been disconnected in either case. In order to fulfill this requirement, the original source voltage must be multiplied by the square root of the ratio of the new and old source resistance.

The single-mesh transformed network is shown in Fig. 23C and it is interesting to compare the response of an RLC series circuit that actually possessed these element values at resonance with the circuit of Fig. 19. For comparison, the response of such a circuit is shown in Fig. 22 as a dashed curve and it can be seen that it differs only slightly from the coupled-circuit curve. The reason for the similarity is that even though the transformation of the primary resistance and reactance also changes with frequency, the effect is not that great in the present case.

### Broadband RF Transformers

The "sensitivity" of the frequency characteristic of the transformation shown in Fig. 7 depends mostly on the ratio of  $X_s$  to  $R_s$ . However, if  $X_s$  is much greater than  $R_s$ , the transformed reactance can be approximated by

$$\frac{-X_m^2 X_s}{R_s^2 + X_s^2} \approx \frac{-X_m^2}{X_s}$$

and the resistance becomes

$$\frac{R_s X_m^2}{R_s^2 + X_s^2} \approx R_s \frac{X_m^2}{X_s^2}$$

Applying this approximation to the general coupled circuit shown in Fig. 24A results in the transformed network of Fig. 24B. The coefficient of coupling for the

circuit of Fig. 24A is

$$k = \frac{X_m}{\sqrt{X_1 X_2}}$$

and the network shown in Fig. 24B in terms of the coefficient of coupling is illustrated in Fig. 24C. For  $k$  equal to 1.0, the input reactance is zero and the input resistance is given by

$$R_{in} = \left(\frac{X_1}{X_2}\right) R_2 = \left(\frac{L_1}{L_2}\right) R_2 \approx \left(\frac{N_1}{N_2}\right)^2 R_2$$

where  $N_1$  and  $N_2$  are the number of turns on coil 1 and 2, respectively. From maximum-power transfer considerations, such as those discussed for the circuit of Fig. 23, the voltage transfer ratio becomes

$$e_2 = \left(\frac{N_2}{N_1}\right) e_1$$

It will be recalled that the foregoing equations occurred in the discussion of the "ideal transformer" approximation in Chapter 2. It was assumed then that the leakage reactance and magnetizing current were negligible. The effects on circuit operation of these variables are shown in Fig. 25. The curves were computed for various load resistances ( $R_s$ ) using the exact equations shown in Fig. 7.

$X_1$  and  $X_2$  are assumed to be 100 and 10 ohms, respectively, with the solid curves for a  $k$  of 1.0 and the dashed reactance curve for  $k$  equal to 0.99 (the resistance curve for the latter value is the same as the one for  $k$  equal to 1.0). The ideal-transformer representation can be modified slightly to approximate the curve of Fig. 25 as shown in Fig. 26. The shunt reactance,  $X_{mag}$  is called the magnetizing

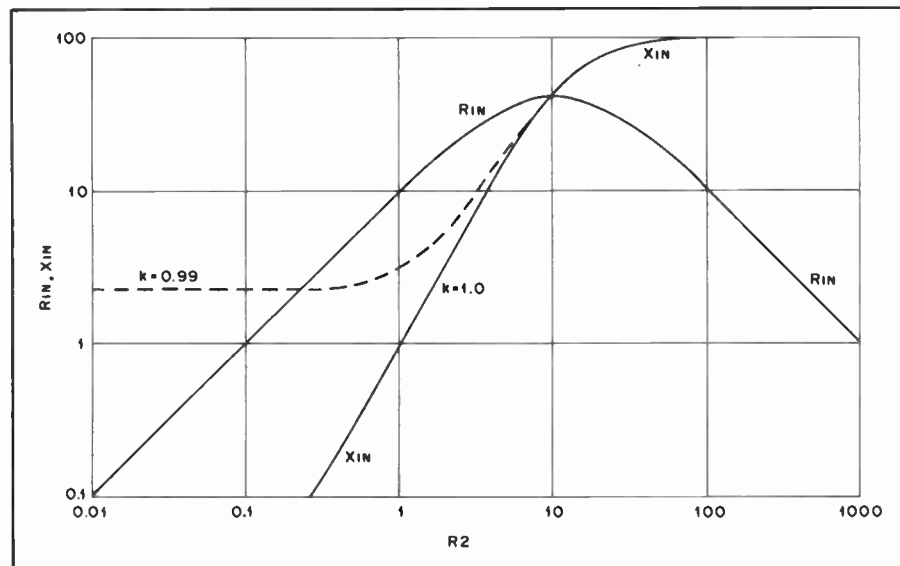


Fig. 25 — Input resistance and reactance as a function of output load resistance for  $X_1$  and  $X_2$  equal to 100 ohms and 10 ohms respectively (Fig. 24).



reactance and  $X_L$  is referred to as the leakage reactance.

Unfortunately, the two reactances are not independent of each other. That is, attempts to change one reactance so that its effect is suppressed causes difficulties in eliminating the effects of the other reactance. For instance, increasing  $X_1$ ,  $X_m$ , and  $X_2$  will increase  $X_{mag}$  which is desirable. However, examination of Fig. 24C reveals that the coefficient of coupling,  $k$ , will have to be made closer to 1.0. Otherwise, the leakage reactance increases since it is proportional to  $X_1$ .

### High-Permeability Cores

As a consequence of the interaction between the leakage reactance and the magnetizing reactance, transformers that approach ideal conditions are extremely difficult (if not impossible) to build using techniques common in air-wound or low-permeability construction. In order to build a network that will match one resistance level to another one over a wide range of frequencies, ideal-transformer conditions have to be approached quite closely. Otherwise, considerable inductive reactance will exist along with the resistive component as shown in Fig. 25.

One approach is to use a core with a higher permeability than air. Familiar examples would be power transformers and similar types common to the af range. However, when an inductor configuration contains materials of more than one permeability, the analysis relating to Fig. 24C has to be modified somewhat. The manner in which the core affects the circuit is a bit complicated although even a qualitative idea of how such transformers work is very useful.

First, consider the coupled coils shown in Fig. 27. For a given current,  $I_1$ , a number of "flux lines" are generated that link both coil 1 and coil 2. Note that in coil 1, not all of the flux lines are enclosed by all the turns. The inductance of a coil is equal to the ratio of the sum of flux linkages each turn and the generating current or

$$L_1 = \frac{\Lambda_{TOTAL}}{I_1}$$

where for the example shown in Fig. 27,  $\Lambda_{TOTAL}$  is given by

$$\Lambda_{TOTAL} = \Lambda_1 + \Lambda_2 + \Lambda_3 + \Lambda_4 + \Lambda_5$$

Counting up the number of flux linkages in coil 1 gives

$$\Lambda_{TOTAL} = 5 + 5 + 7 + 7 + 5 = 29$$

If all the flux lines linked all the turns,  $\Lambda_{TOTAL}$  would be 35 so  $L_1$  is 29/35 or 83 percent of its maximum possible value. Likewise, if all the flux (7 lines) generated in coil one linked all the turns of coil 2, the maximum number of flux linkages would be the number of turns on coil 2 times 7 or

28. Since only three lines link coil 2, the mutual inductance is  $3 \times 4/28$  or 43 percent of maximum.

Assuming both coils are "perfect," if a current  $I_1$  produced 7 flux lines in a five-turn coil, then the same current in a four-turn coil would produce (4/5)(7) flux lines, since the flux is proportional to the magnetizing current times the number of turns. Consequently, the maximum flux linkages in coil 1 from a current of the same value as  $I_1$  but in coil 2 instead would be (4/5)(7)(5) or 28. Therefore, it can be seen that the mutual inductance is independent of the choice of coil used for the primary or secondary. That is, a voltage produced in one coil by a current in the other one would be the same if the coils were merely interchanged. (This result has been used implicitly on a number of previous occasions without proof.) In addition, the maximum flux linkages in coil 2 produced by a current,  $I_1$ , would be (4/5)(7)(4). As an exercise, substitute the maximum inductance values into the formula for the coefficient of coupling and show that  $k$  is 1.0.

The next step is to consider the effect of winding coils on a form with a magnetic permeability much higher than that of air. An example is illustrated in Fig. 28 and the configuration shown is called a toroidal transformer. Since the flux is proportional to the product of the permeability and the magnetizing current, the flux in the core shown in Fig. 28 will be much greater than the coil configuration of Fig. 27. However, not all of the flux is confined to the core. As can be seen in Fig. 28, some of the flux lines never penetrate the core (see lines marked a in Fig. 28) while others enclose all the windings of coil 1 but not coil 2 (see line marked b). The significance of these effects is as follows. The total flux linkage produced by the current,  $I_1$ , is

$$\Lambda_{TOTAL} = \Lambda_{air} + \Lambda_{core}$$

and dividing both sides of the equation by  $I_1$  gives

$$L_T = L_{air} + L_{core}$$

Consequently, the circuit of Fig. 24 can be represented as shown in Fig. 29A. For  $X_2$  much greater than the load resistance, the approximate network of Fig. 29B can replace the one of Fig. 29A.

At first sight, it might seem as though little advantage has been gained by introducing the core since the formulas are much the same as those of Fig. 24C. However, the reactances associated with the core can be made very high by using a material with a high permeability. Also, even though there may be some "leakage" from the core as indicated by line b in Fig. 28, it is ordinarily low and the coefficient of coupling in the core can be considered 1.0 for all practical purposes. This is

especially true at af and power frequencies with transformers using iron cores where the permeability is extremely high. This means the magnetizing reactance can be made very high without increasing the leakage reactance accordingly as is the case with the circuit in Fig. 24C. Therefore, ideal transformer conditions are considered to exist in the core and the final circuit can be approximated by the one shown in Fig. 29C.

### Bifilar and Twisted-Pair Windings

Although the core helps alleviate some of the problems with leakage and mag-

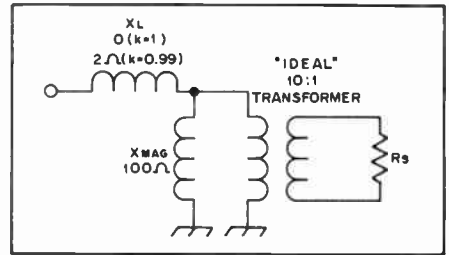


Fig. 26 — Approximate network for the curves of Fig. 25.

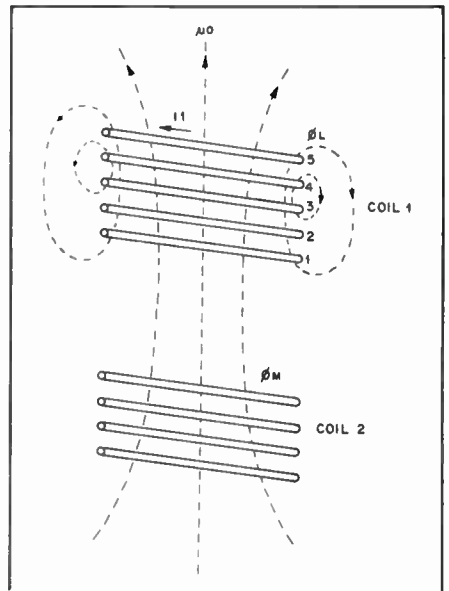


Fig. 27 — Coupled coils showing magnetic flux lines.

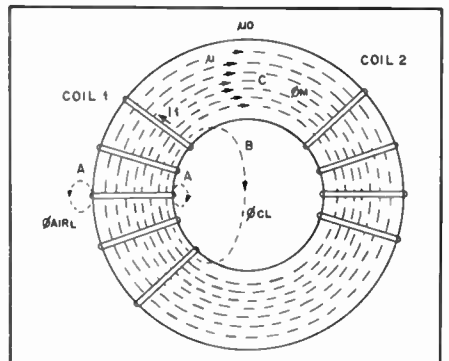


Fig. 28 — Toroidal transformer.

netizing reactance, the residual parasitic elements must still be made as low as possible. This is especially important in matching applications as the following example illustrates. A transformer has a primary and secondary leakage reactance of 1 ohm and 0.1 ohm, respectively, with a coefficient of coupling of 1.0 in the core.  $X_1$  and  $X_2$  are 1000 ohms and 100 ohms.

A plot similar to the one of Fig. 25 is shown in Fig. 30 along with a curve for

voltage-standing-wave ratio (VSWR). These results are based on the exact equations and it can be seen that the approximate relations shown in Fig. 29C are valid up to 1 ohm or so. Curve A (Fig. 30) only includes the effect of the secondary reactance and illustrates the manner in which the reactance is transformed. Curve B is the total input reactance which merely requires the addition of 1 ohm. The VSWR curve includes the effect of the latter. Useful range of the transformer is between 1 and 10 ohms with rapid deterioration in VSWR outside of these values. (The VSWR curve is for a characteristic impedance equal to 10 times the secondary resistance. For instance, the transformer would be useful in matching a 5-ohm load to a 50-ohm line.)

As mentioned previously, these difficulties are less pronounced at audio frequencies since the permeabilities normally encountered in iron-core transformers are so high, the actual inductance of the winding itself is small in comparison to the component represented by the core. That is, a small number of turns of wire wound on a core may actually be the equivalent of a very large coil. However, materials suitable for rf applications have much lower permeabilities and a narrower range of matching values is likely to be the result (such as in the example of Fig. 30). Therefore, other means are required in keeping the parasitic elements as low as possible. Either that, or less conventional transformer designs are used.

One approach is shown in Fig. 31. Instead of separating the windings on the core as shown in Fig. 28, they are wound in parallel fashion. This is called a bifilar winding although a more common approach to achieve the same purpose is to

twist the wires together. Either way, there are a number of advantages (and some disadvantages) to be gained. Referring to Fig. 27, the fact that not all the flux lines linked all of the turns of a particular coil meant the self inductance was lower than if all the turns were linked. Since the separation between turns of a particular coil is quite large in the configuration of Fig. 31, the flux linkage between turns is quite low. This means the corresponding leakage inductance is reduced accordingly. However, the coupling between both coils is increased because of the bifilar winding (flux line A) in Fig. 31 which also tends to reduce the leakage inductance of either coil.

On the other hand, the capacitance between windings is increased considerably as indicated by B in Fig. 31. As a result, the coupling between windings is both electrical and magnetic in nature. Generally speaking, analysis of the problem is quite complicated. However, a phenomenon usually associated with such coupling is that it tends to be directional. That is, energy transferred from one winding to another one propagates in a preferred direction rather than splitting equally.

### Directional Coupling

Two conductors are oriented side by side over a conducting plane as shown in Fig. 32. A current  $I$  in conductor 1 will induce a current  $I_m$  in conductor 2 because of magnetic coupling. The actual value of the current will depend upon the external circuitry attached to the conductors but it will be assumed that the two of them extend to infinity in both directions.

Since capacitive coupling exists also, a second set of current components denoted by  $I_c$  will also flow. The result is that a wave traveling toward the *right* in conductor 1 will produce a wave traveling toward the *left* in conductor 2. Such coupling is called *contradirectional coupling* since the induced wave travels in the opposite direction to the generating wave.

This is the principle behind many practical devices and ones that are quite common in amateur applications. In adjusting a load such as an antenna, it is desirable to insure that energy is not reflected back to the transmitter. Otherwise, the impedance presented to the transmitter output may not be within range of permissible values. A directional coupler is useful in determining how much power is reflected as indicated in Fig. 33. Energy originating from the transmitter and flowing to the right causes a voltage to be produced across the resistor at the left. On the other hand, a wave traveling from the right to the left produces a voltage across the right-hand resistor. If both of these voltages are sampled, some idea of the amount of power reflected can be determined. (The subject of reflected-power is taken up in more detail in the

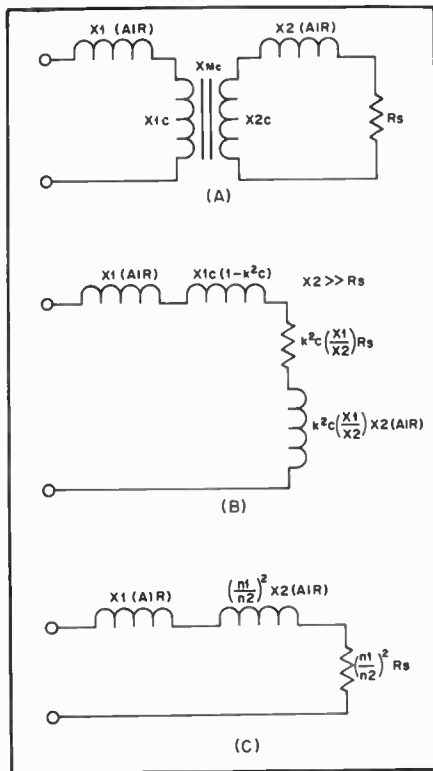


Fig. 29 — Effect of a high-permeability core on transformer equivalent circuit.

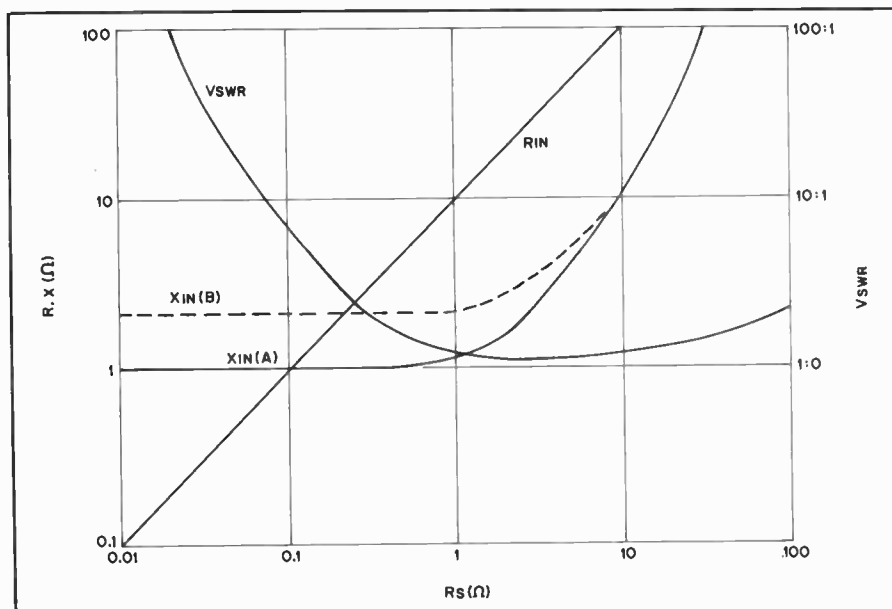


Fig. 30 — Curve for transformer problem discussed in the text.

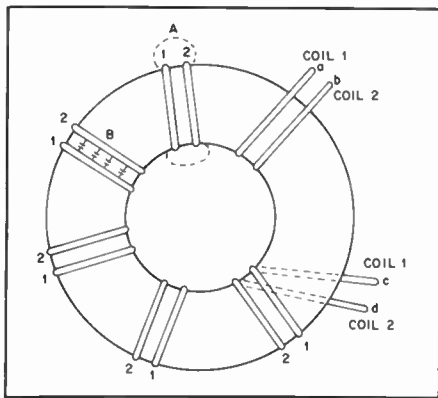


Fig. 31 — Bifilar-wound transformer on toroidal core.

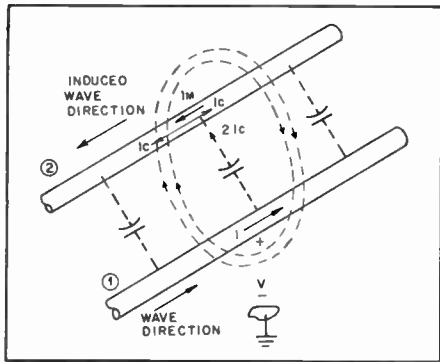


Fig. 32 — Effect of distributed capacitance on transformer action.

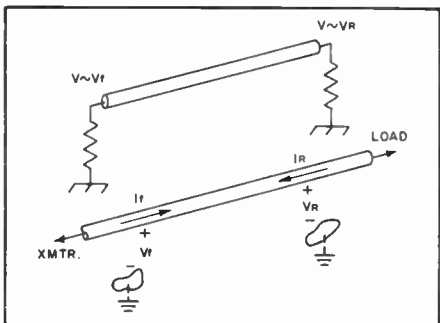


Fig. 33 — Basic configuration for a directional-coupler type VSWR detector.

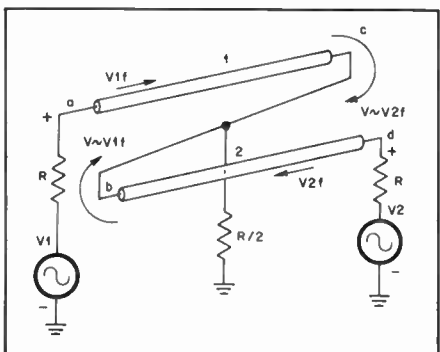


Fig. 34 — Directional-coupler hybrid combiner.

chapter on transmission lines.)

In some situations, the coupling described can be very undesirable. For instance, the lines shown in Fig. 33 might be conductors on a circuit board in a piece of equipment. As a result, the coupling between lines can cause "feedback" and because of its directional nature, it can be very difficult to suppress with conventional methods. Therefore, it is good design practice to use "double-sided" board (board with conductive foil on both sides) so that a ground plane of metal is in close proximity to the conductors. This tends to confine the fields to the region in the immediate vicinity of wires.

### Transmission-Line Transformers

In effect, sections of transmission line in close proximity act as transformers with the unique feature that the coupling is directional. For instance, if only magnetic coupling was present in the configuration of Fig. 33, power would be divided equally between the resistors at either end of the "secondary" section of transmission line. As another example of directional effects, the network shown in Fig. 34 can be used to couple two sources to a common load without "cross-coupling" of power from one source to the other. (This assumes the sources have the same frequency and phase. Otherwise, a resistance of value  $2R$  must be connected from points a to d.) Such a configuration is called a hybrid combiner and is often used to combine the outputs of two solidstate amplifiers in order to increase the powerhandling capability. This permits the use of less expensive low-power devices rather than very expensive high-power ones. Even though more devices are required, it is still simpler since the difficulties in producing a high-power transistor increase in a greater proportion as the power level is raised.

The manner in which the circuit shown in Fig. 34 operates is as follows. A wave from the generator on the left end of line 1 travels toward the right and induces a wave in line 2 that travels toward the left and on into the load. No wave is induced in line 2 that travels toward the right except for a small fraction of power.

A similar situation exists with the second generator connected at the right end of line 2. A wave is induced in line 1 that travels toward the right. Since the load is also connected to the right end of line 1, power in the induced wave will be dissipated here with little energy reaching the generator at the left end of line 1. In order to "simulate" a single load (since there are two generators involved), the value of the load resistance must be half of the generator resistance. Assuming that two separate resistors of value  $R$  were connected to the ends of the line, it would be possible to connect them together without affecting circuit operation. This is because the voltage across both resistors is

of the same phase and amplitude. Consequently, no additional current would flow if the two resistors were paralleled or combined into a single resistor of  $R/2$ .

### Extending the Low-Frequency Range

As might be expected, the coupling mechanism illustrated in Figs. 32 through 34 is highly dependent on dimensions such as conductor spacing and line length. For instance, maximum coupling of power from the primary wave to the induced wave occurs when the "secondary" line is a quarter-wavelength long<sup>2</sup> or some odd multiple of a quarter-wavelength. This would normally make such couplers impractical for frequencies in the hf range. However, by running the leads through a ferrite core as shown in Fig. 35, lower-frequency operation is possible. Although the transformer of Fig. 35A is seldom used, it illustrates the manner in which the conductors are employed electrically in the more complicated configurations of Fig. 31 and Fig. 35B. Also, the relationship between the parallel-line coupler in Fig. 34 and the "loaded" version of Fig. 35A is easier to visualize.

Recalling an earlier problem discussion (Fig. 28), a set of coupled coils wound on a high-permeability core can be broken down into combinations of two series inductances. One inductance represents the path in air while the other one includes the effects of the flux in the core. As

<sup>2</sup>Oliver, "Directional Electromagnetic Couplers," *Proceedings of the I.R.E.*, Vol. 42, p. 1686-1692; November, 1954.

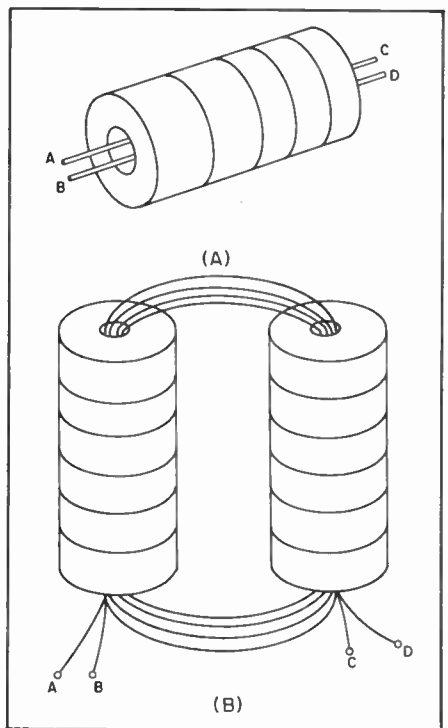


Fig. 35 — Transmission-line transformers with ferrite cores.



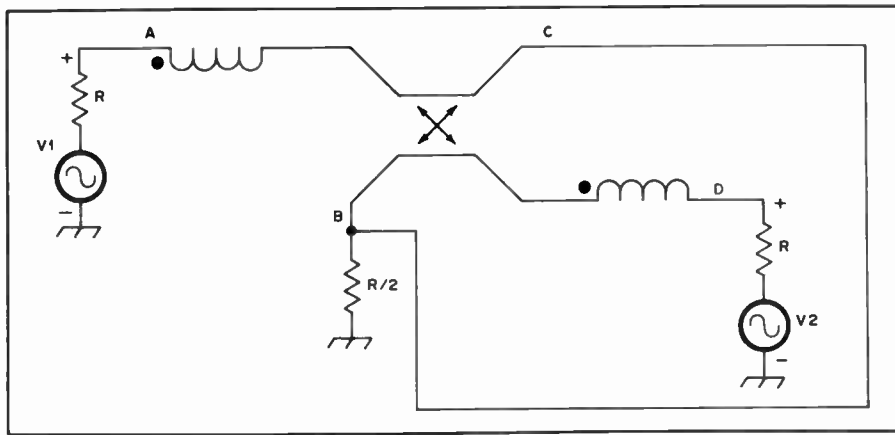


Fig. 36 — Equivalent circuit of transmission-line transformer in the presence of the core. Dots indicate winding sense of coils. A positive current into a dotted end of one coil will produce a voltage in the other coil because of mutual coupling. The polarity of this voltage will be such that dotted end of the "secondary" coil will be positive. (See text for crossed-arrow symbol in the middle of the parallel lines.)

before, it is assumed that the coefficient of coupling in the core is 1.0.

If the hybrid combiner of Fig. 34 is wound on a core (such as those of Fig. 31 or Fig. 35), the low-frequency range of the entire system is increased considerably. The equivalent circuit showing the effect of the core on the air-wound coupler is illustrated in Fig. 36. (The symbol in the middle of the parallel lines is the standard one for a directional coupler.) At the higher frequencies, most core materials decrease in permeability so the operation approaches that of the original air-wound coupler and the inductance produced by the core can be neglected. At the low end of the frequency range, the line lengths are

usually too short to provide much coupling or isolation. Therefore, the circuit can be represented by the set of coupled coils shown in Figs. 37 and 38.

For a current  $I_2$  flowing from a source 1 over to the mesh that includes source 2, the mutual-reactance components *add* to the self inductance of each coil. Consequently, a large reactance appears in series between the two sources which effectively isolates them. On the other hand, currents from both sources that flow through the load resistor  $R/2$  produce fluxes that cancel and the voltages produced by the self- and mutual-reactance terms *subtract*. If both sources have the same amplitude and

phase, currents  $I_1$  and  $I_2$  must be identical because of the symmetry involved. However, if the coefficient of coupling is 1.0, the self and mutual-reactance must be equal. Therefore, the voltage across either coil is zero since the terms subtract and a low-impedance path exists between both sources and the load.

### Other Transformer Types

The hybrid combiner is only one application of a combination transmission-line or directional-coupler transformer and conventional coupled-coil arrangement. With other variations, the low-frequency isolation is accomplished in the same manner. Mutual-reactance terms add to the self reactance to provide isolations for some purpose with cancellation of reactive components in the path for the desired coupling. Very good bandwidth is possible with a range from bc frequencies to uhf in the more esoteric designs. Models that cover all the amateur hf bands can be constructed easily.<sup>3</sup>

Unfortunately, there is also a tendency to expect too much from such devices on occasion. Misapplication or poor design often results in inferior performance. For instance, as indicated in an earlier example (Fig. 30), actual impedance levels were important along with the desired transforming ratio. Using a transformer for an impedance level that it was not intended for resulted in undesirable reactive components and improper transforming ratio. However, when applied properly, the transformers discussed in the previous sections can provide bandwidth characteristics that are obtainable in no other way.

Another transformer type is shown in Fig. 39A. The windings of the coils are such that the voltages across the inductors caused by the desired current are zero. This is because the induced voltages produced by the current in the mutual-reactance terms just cancel the voltage drop caused by the current flowing in the self reactances of either coil. (Assuming that the coefficient of coupling is 1.0.) However, an impedance connected to ground at point c would be in series with the self reactance ( $X_L$ ) of the coil connected between points a and c. But there would be no induced voltage to counter the voltage drop across this coil. Therefore, if  $X_L$  is large, very little current would flow in the impedance Z and it would effectively be isolated from the source.

In fact, terminal c could be grounded as shown in Fig. 39B. The voltage drop across the coil from a to c would then be equal to  $V_1$ . However, the induced voltage in the coil connected between points b and d would also be  $V_1$  assuming unity coupling ( $k$  equal to 1.0). Although the

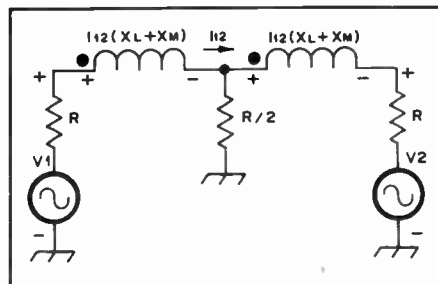


Fig. 37 — Low-frequency equivalent circuit of hybrid combiner showing isolation of sources.

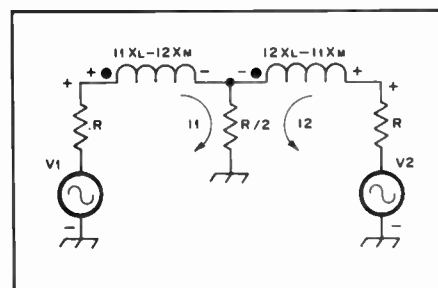


Fig. 38 — Desired coupling mode of hybrid combiner.

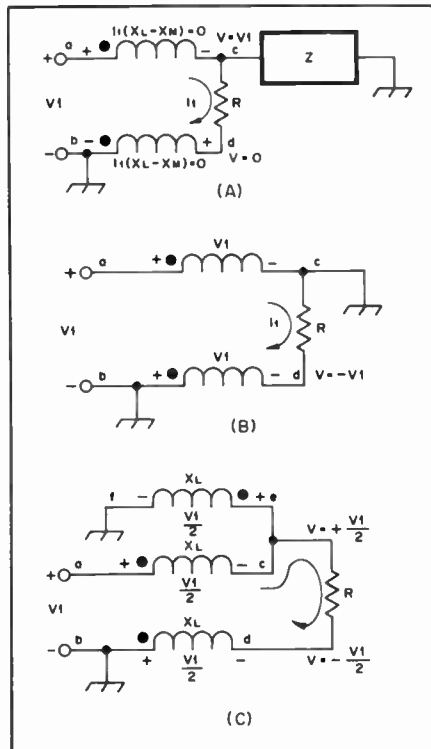


Fig. 39 — Other applications of transmission-line transformers.

<sup>3</sup>Ruthroff, "Some Broad-Band Transformers," *Proceedings of the I.R.E.*, Vol. 97, pp. 1337-1342; August, 1959.



voltage drop produced by the inductors around the mesh through which  $I_1$  flows is still zero, point d is now at potential  $-V_1$  and a phase reversal has taken place. For this reason, the configuration shown in Fig. 39B is called a phase-reversal transformer.

### Baluns

The circuit shown in Fig. 39A is useful in isolating a load from a grounded source. This is often required in many applications and the device that accomplishes this goal is called a balun (*balanced* to *unbalanced*) transformer. Baluns may also be used in impedance transforming applications along with the function of isolation and a "1:1 balun" such as the one shown in Fig. 39A means the impedance at the input terminals ab will be the same as the load connected across terminals cd. Other transforming ratios are possible such as 4:1 with the

appropriate circuit connections.

One disadvantage of the network of Fig. 39A is that although the load is isolated from the source, the voltages at the output are not balanced. This is important in some applications such as diode-ring mixers where a "push-pull" input is required and so the circuit of Fig. 39C is used. A third coil connected between points e and f is wound on the same core as the original transformer (Fig. 39A). This coil is connected so that a voltage across it produces a flux that adds to that produced by the coil between a and c. Assuming that both coils are identical, the voltage drop across either one must be the same or half the applied voltage. However, since the coil between b and d is also coupled to this combination (and is an identical coil), the induced voltage must also be  $V_1/2$ . Consequently, the end of the load connected to points c and e is at a potential of  $+V_1/2$  with respect to

ground while point d is  $-V_1/2$  with respect to ground when the input voltage has the polarity shown. Therefore, this circuit not only isolates the load from the source but provides a balanced voltage also.

Either the circuit of Fig. 39A or Fig. 39C can be used if only isolation is desired. However, the network shown in Fig. 39C is more difficult to design and construct since the reactance of the coils between points a and f must be very high throughout the frequency range of the transformer. With both transformers, the coefficient of coupling must also be very close to 1.0 in order to prevent undesirable reactance in series with the load. This problem can be offset somewhat by reducing  $X_L$  slightly (by using fewer turns) but this is counter to the requirement of large  $X_L$  in the circuit of Fig. 39C. Isolation is reduced in both cases although no detrimental effect on input impedance results in the transformer of Fig. 39A by reducing  $X_L$ .

## Nonlinear and Active Networks

Almost all the theory in previous sections has dealt with so-called passive components. Passive networks and components can be represented solely by combinations of resistors, capacitors and inductors. As a consequence, the power output at one set of terminals in a passive network cannot exceed the total power input from sources connected to other terminals in the circuit. This assumes all the sources are at one frequency. Similar considerations hold true for any network, however, it is possible for energy to be converted from one frequency (including dc) to other ones. While the total power input must still equal the total power output, it is convenient to consider certain elements as controllable sources of power. Such devices are called amplifiers and are part of a more general class of circuits called active networks. An active network generally possesses characteristics that are different than those of simple RLC circuits although the goal in many instances is to attempt to represent them in terms of passive elements and generators.

### Nonlinearity

Two other important attributes of passive RLC elements are that they are linear and bilateral. A two-terminal element such as a resistor is said to be bilateral since it doesn't matter which way it is connected in a circuit. Semiconductor and vacuum-tube devices such as triodes, diodes, transistors and integrated circuits (ICs) are all examples where the concept of bilateral element breaks down. (For readers with limited backgrounds in the basic operation of vacuum tubes, recom-

mended study would be *The Radio Amateur's License Manual* and *Understanding Amateur Radio*. Both publications contain fundamental treatments of vacuum-tube principles and are available from The American Radio Relay League.) The manner in which the device is connected in a circuit and the polarity of the voltages involved are very important.

An implication of the failure to satisfy the bilateral requirements is that such devices are nonlinear in the strictest sense. Linearity means that the amplitude of a voltage or current is related to other voltages and currents in a circuit by a single proportionality constant. For instance, if all the voltages and currents in a circuit were doubled, a single remaining voltage or current would be doubled also. That is, it couldn't change by a factor of one half or three no matter how complex the network might be. Likewise, if all the polarities of the currents and voltages in a circuit are reversed, the polarity of a remaining voltage or current must be reversed also. Finally, if all the generators or sources in a linear network are sine waves at a single frequency, any voltage or current produced by these sources must also be a sine wave at the same frequency too.

Consequently, if a device is sensitive to the polarity of the voltage applied to its terminals, it doesn't meet the requirements of a bilateral element or a linear one either. However, because of the extreme simplicity of the mathematics of linear circuits as compared to the general nonlinear case, there is tremendous motivation in being able to represent a nonlinear circuit by a linear approxima-

tion. Many devices exhibit linear properties over part of their operating range or may satisfy some but not all of the requirements of linear circuits. Such devices in these categories are sometimes termed piece-wise linear. Either that, or they are just referred to simply as linear. For instance, a linear mixer doesn't satisfy the rule that a voltage or current must be at the same frequency as the generating source(s). However, since the desired output voltage (or current) varies in direct proportion to the input voltage (or current), the term linear is applied to distinguish the mixer from types without this "quasi-linear" property.

### Harmonic-Frequency Generation

In a circuit with only linear components, the only frequencies present are those generated by the sources themselves. However, this is not true with nonlinear elements. One of the properties of nonlinear networks mentioned earlier is that energy at one frequency (including dc) may become converted to other frequencies. In effect, this is how devices such as transistors and vacuum tubes are able to amplify radio signals. Energy from the dc power supply is converted to energy at the desired signal frequency. Therefore, a greater amount of signal power is available at the output of the network of an active device than at the input.

On the other hand, such frequency generation may be undesirable. For instance, the output of a transmitter may have energy at frequencies that could cause interference to nearby receiving equipment. Filters and similar devices must be used to suppress this energy as

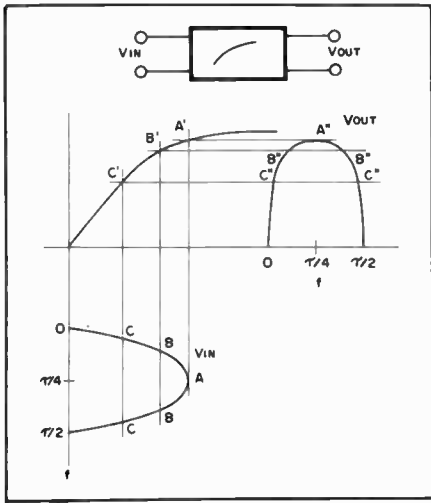


Fig. 40 — Nonlinear transfer characteristic (see text discussion).

much as possible.

The manner in which this energy is produced is shown in Fig. 40. A sine-wave at the input of a nonlinear network ( $V_{in}$ ) is "transformed" into the output voltage waveform ( $V_{out}$ ) illustrated. If the actual device characteristic is known, the waveform could be constructed graphically. It could also be tabulated if the output voltage as a function of input voltage was available in either tabular or equation form. (Only one-half of the period of a sine-wave is shown in Fig. 40 for clarity.)

Although the new waveform retains

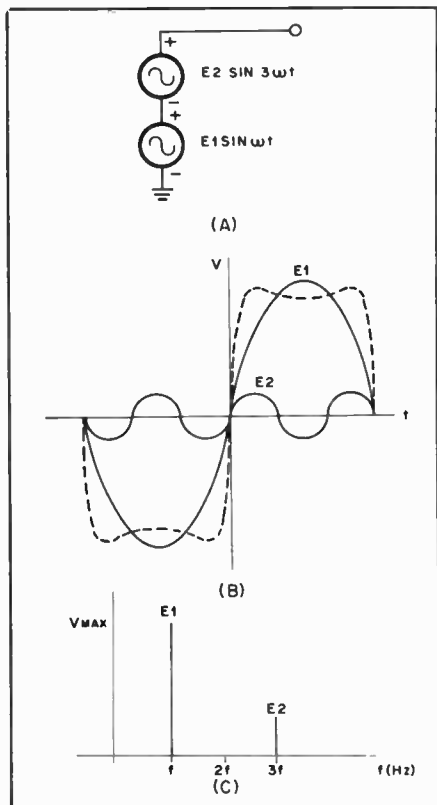


Fig. 41 — Harmonic analysis and spectrum.

many of the characteristics of the original sine-wave, some transformations have taken place. It has zero value when  $t$  is either 0 or  $T/2$  and attains a maximum at  $T/4$ . However, the fact that the curve is flattened somewhat means energy at the original sine-wave frequency has been converted to other frequencies. It will be recalled that the sum of a number of sine waves at one frequency result in another sine-wave at the same frequency. Therefore, it must be concluded that the waveform of Fig. 40 has more than one frequency component present since it is no longer a sine-wave.

One possible "model" for the new waveform is shown in Fig. 41A. Instead of one sine-wave at a single frequency, there are two generators in series with one generator at three times the "fundamental" frequency  $\omega$  where  $\omega$  is  $2\pi f$  (Hz). If the two sine waves are plotted point by point, the dashed curve of Fig. 41B results. While this curve doesn't resemble the one of Fig. 40 very closely, the general symmetry is the same. It would take an infinite number of generators to represent the desired curve exactly, but it is evident all the frequencies must be odd multiples of the fundamental. Even multiples would produce a lopsided curve which might be useful for representing other types of waveforms.

In either case, the multiples have a specific name and are called harmonics. There is no "first" harmonic (by definition) with the second, third and fourth multiples designated as the second, third and fourth harmonics. Thus the dashed curve of Fig. 41 is the sum of the fundamental and third harmonic.

Analyzing waveforms such as those of Fig. 40 is a very important subject. A plot of harmonic amplitude such as that shown in Fig. 41C is called the spectrum of the waveform and can be displayed on an instrument called a spectrum analyzer. If the mathematical equation or other data for the curve is known, the harmonics can also be determined by means of a process called Fourier Analysis.

### Linear Approximations of Nonlinear Devices

Nonlinear circuits may have to be analyzed graphically as in the previous example. There are many other instances where only a graphical method may be practical such as in power-amplifier problems. However, a wide variety of applications permit a different approach. A model is derived from the nonlinear characteristics using linear elements to approximate the more difficult nonlinear problem. This model is then used in more complicated networks instead of the nonlinear characteristics which simplifies analysis considerably.

The following example illustrates how this is accomplished and although a vacuum-tube application is considered, a

similar process is employed in solving semiconductor problems as well. However, there are some additional factors involved in semiconductor design that do not apply to vacuum tubes. Device characteristics of early transistors were less uniform than those of tubes although this is much less of a problem than it was formerly. In fact, much of the analysis required with vacuum tubes is unnecessary with modern solid-state components since many of the problems have already been "solved" before the device leaves the counter at the radio store. That is, amplifiers such as those in integrated circuits have the peripheral elements built in and there is no need to determine the gain or other parameters such as the values of bias resistors.

### The Triode Amplifier

A simple network using a triode vacuum type is shown in Fig. 42A and a typical set of characteristic curves is illustrated in Fig. 43A. The first chore in finding a suitable linear approximation for the triode is to determine an optimum operating point. Generally speaking, a point in the center of the set of curves is desirable and is indicated by point Q in Fig. 43A. (Other areas are often picked for power-amplifier operation but the goal here is to find a point where the maximum voltage swing is possible with-

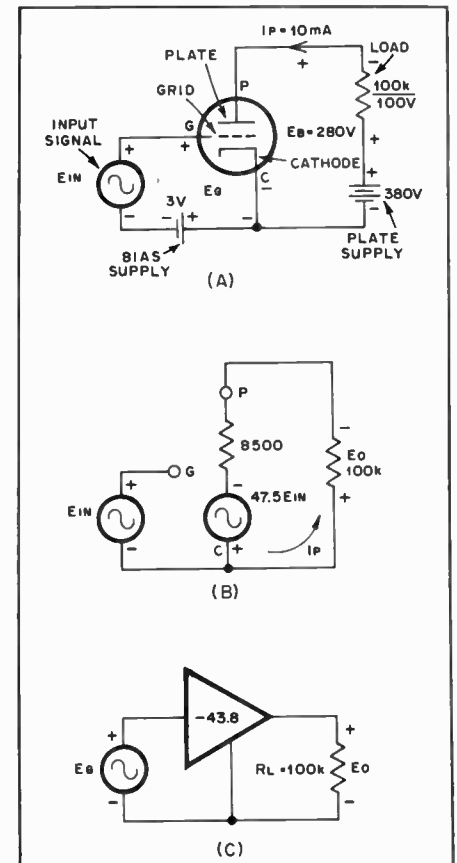


Fig. 42 — Basic triode amplifier and equivalent circuit.

out entering regions where the nonlinearities affect the linear approximation.)

In the particular operating point chosen, the cathode-to-grid voltage is  $-3$ , the cathode-to-plate voltage is  $280$ , and the plate current is  $10$  mA. It is assumed that the input-signal source in Fig. 42A is a "short circuit" at dc and a 3-V battery connected as shown results in a dc voltage of  $-3$  being applied to the grid at all times. Such a battery is called a bias battery or bias supply.

The next step is to determine how the plate voltage varies with grid voltage ( $e_g$ ) for a constant plate current. Assuming that the characteristic curves were completely linear, this would permit evaluation of an equivalent ac voltage generator as shown in Fig. 42B. For a constant plate current of  $10$  mA, the plate voltage changes from  $325$  (point b) to  $230$  (point a) when the grid voltage is changed from  $-4$  to  $-2$  (Fig. 43A).

These numbers can be used to compute the amplification factor ( $\mu$ ) of the triode which is

$$\mu = \frac{325 - 230}{(-4) - (-2)} = -47.5$$

Quite often, a set of characteristics will not be published for a triode and only the amplification factor will be given along with a typical operating point. However, note that the amplification factor is *negative*. This means that for an increase in the signal voltage ( $e_{in}$ ), the controlled generator decreases in voltage. Consequently, there is a  $180$  degree phase shift between the input voltage and the controlled source. (Note the polarity of the generator shown in Fig. 42B.)

In order to complete the equivalent generator circuit, the source "impedance" must be computed. This is accomplished by determining how the plate voltage varies with plate current at constant grid voltage as shown in Fig. 43B. The plate resistance is then

$$r_p = \frac{325 - 240}{(15 - 5) \times 10^{-3}} = 8500 \text{ ohms}$$

which must be considered to be in series with the controlled source of Fig. 42B.

It should be pointed out at this juncture that the reasoning *why* the foregoing procedure is valid has not been presented. That is, why was the amplification factor defined as the ratio of a change in plate voltage to change in grid voltage at constant current? Unfortunately, the mathematics involved although not difficult is somewhat sophisticated. Some knowledge of the subject of partial differential equations is required for the theoretical derivation of these parameters. However, an intuitive idea can be obtained from the following.

If the characteristics were completely

linear, instead of being nonlinear as shown, the equivalent generator would be unaffected by *changes* in plate current but only by changes in grid voltage. For instance, if the plate current was increased from  $10$  to  $17$  mA (Fig. 43A), the amplification factor would be the equivalent of the change in voltage represented by the line cd divided by  $-2$ . However, since the length of cd is almost the same as that of ab (the difference in plate voltage for a  $-2$ -V change at  $10$  mA), it can be concluded  $\mu$  doesn't change very much. Not at least in the center region of the characteristics.

Similar considerations hold for the plate resistance,  $r_p$ . It wouldn't matter if the curve for  $-4$  or  $-2$  V was picked (Fig. 43B), since the change in plate voltage vs. plate current would be approximately the same. Entities such as  $\mu$  and  $r_p$  are often called *incremental* or *small-signal* parameters. This means they are valid for small ac voltages or currents around some operating point but less so for large variations in signal or for regions removed from the specified operating point. Also, such parameters are not closely related to *dc* voltage characteristics. For instance, a "static" plate resistance could be defined as the ratio of plate voltage to plate current. For the  $-3$ -V operating point chosen, the static plate resistance would be  $280$  divided by  $10 \times 10^{-3}$  or  $280$  k $\Omega$ . This is considerably different from the small-signal plate resistance determined previously which was  $8500$  ohms.

#### Amplifier Gain

The ratio of the variation in voltage across the load resistance to change in input voltage is defined as the gain of the amplifier. For the equivalent circuit shown in Fig. 42B, this ratio would be

$$A = \frac{e_o}{e_{in}}$$

In order to solve for the gain, the first step is to determine the incremental plate current. This is just the source voltage divided by the total resistance of the circuit mesh or

$$i_p = \frac{47.5e_{in}}{100 + 8.5} \text{ mA}$$

The output voltage is then

$$e_o = i_p 100$$

and combining the two foregoing equations gives

$$A = \frac{e_o}{e_{in}} = \frac{(47.5)(100)}{100 + 8.5} = 43.8$$

It is somewhat inconvenient to have the input and output voltages defined with

opposite polarities as shown in Fig. 42B. Therefore, the gain becomes negative as illustrated in the triangle in Fig. 42C. A triangle is the standard way of representing an amplifier stage in "block-diagram" form. The amplifier gain depends of course on the load resistance,  $R_L$ , and a general formula for the gain of the circuit of Fig. 42B is

$$A = \frac{-\mu R_L}{r_p + R_L}$$

#### Feedback

Being able to eliminate the equivalent circuit and use only one parameter such as the gain permits analysis of more complicated networks. A very important application occurs when part of the output energy of an amplifier is returned to the input circuit and gets amplified again. Since energy is being "fed back" into the input, the general phenomenon is called feedback. The manner in which feedback problems are analyzed is illustrated in Fig. 44. The output voltage is "sampled" by a network in the box marked beta and multiplied by this term. This transformed voltage then appears in series with the input voltage,  $e_{in}$  which is applied to the input terminals of the amplifier (triangle with  $A_o$ ).  $A_o$  is defined as the open-loop gain. It is the ratio of the voltage that appears between terminals 3 and 4 when a voltage is applied to terminals 1 and 2. The circuit of Fig. 44 is an example of voltage feedback and a similar analysis holds for networks incorporating current feedback.

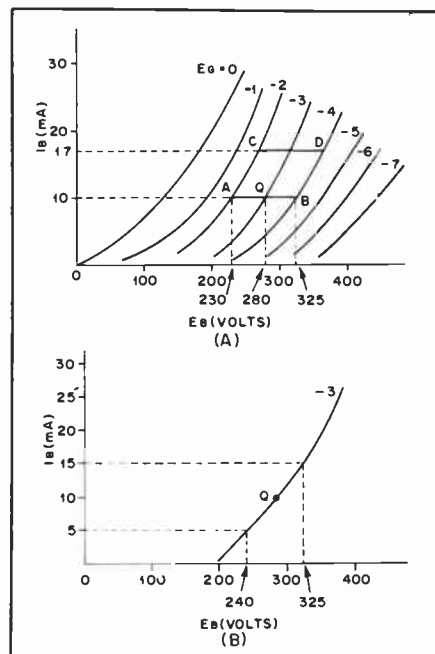


Fig. 43 — Triode characteristics and derivation of small-signal parameters.



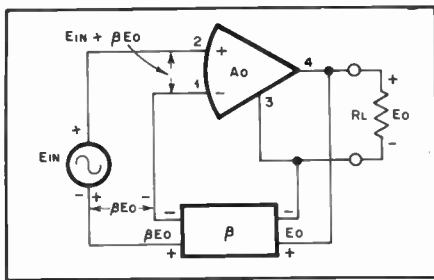


Fig. 44 — Network illustrating voltage feedback.

The closed-loop gain,  $A_c$ , can then be found by inspection of Fig. 44. From the diagram, the output voltage must be

$$e_o = A_o (e_{in} + \beta e_o)$$

rearranging terms gives

$$e_o (1 - \beta A_o) = A_o e_{in}$$

and the closed-loop gain is defined by

$$A_c = \frac{A_o}{1 - \beta A_o} = \frac{e_o}{e_{in}}$$

### Cathode Bias

As an application of the feedback concept, consider the amplifier circuit shown in Fig. 45. It will be recalled that a bias battery was required in the previous example and a method of eliminating this extra source is to insert a small-valued resistor in series with the cathode lead to ground (Fig. 45A). In terms of the amplifier block diagram, the circuit of

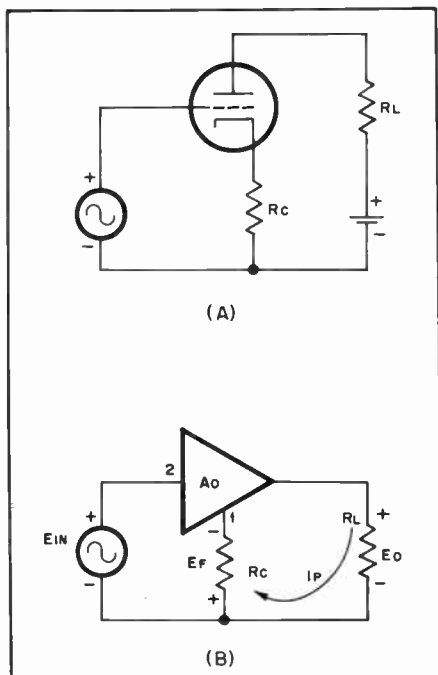


Fig. 45 — Feedback example of an amplifier with cathode bias.

Fig. 45B results. The next task is to evaluate the open-loop gain and the value of  $\beta$ .

With the exception of the cathode resistor, the circuit of Fig. 45 is the same as that of Fig. 42. Consequently, the ac plate current must be

$$i_p = \frac{-\mu e_{i2}}{r_p + R_L + R_c}$$

The open-loop gain can then be determined and is

$$\frac{e_o}{e_{i2}} = A_o = \frac{-\mu R_L}{r_p + R_L + R_c}$$

Next,  $\beta$  is determined from the expression for output voltage

$$e_o = i_p R_L$$

and the feedback voltage which is

$$e_f = i_p R_c$$

$\beta$  is then

$$\beta = \frac{e_f}{e_o} = \frac{i_p R_c}{i_p R_L} = \frac{R_c}{R_L}$$

Note that  $\beta$  is positive since if the path 1 to 2 is considered, the feedback voltage is added to the input signal. Substituting the values of  $\beta$  and  $A_o$  into the feedback equation gives

$$A_c = \frac{A_o}{1 - \frac{R_c A_o}{R_L}}$$

which after some manipulation becomes

$$A_c = \frac{-\mu R_L}{r_p + R_L + (1 + \mu) R_c}$$

Comparison of this equation with the one for the previous circuit with no cathode resistor reveals that the gain has decreased because of the term  $(1 + \mu) R_c$  in the denominator. Such an effect is called *negative* or *degenerative* feedback.

On the other hand, if the feedback was such that the gain increased, *regenerative* or *positive* feedback would result. Positive feedback can be either beneficial or detrimental in nature and the study of feedback is an important one in electronics. For instance, frequency generation is possible in a circuit called an oscillator. But on the other hand, unwanted oscillation or *instability* in an amplifier is very undesirable.

### Oscillators

A special case of feedback occurs if the term

$$1 - \beta A_o$$

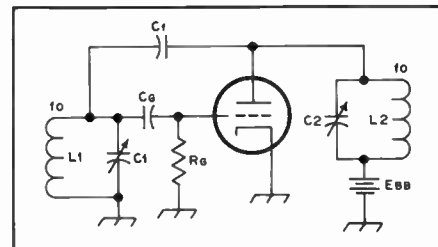


Fig. 46 — Tuned-plate tuned-grid oscillator.

becomes zero. This would mean the closed-loop gain would become infinite. An implication of this effect is that a very small input signal would be amplified and fed back and amplified again until the output voltage became infinite. Either that, or amplifier output would exist with *no* signal input. Random noise could "trigger" the input into producing output.

Of course, an infinite output voltage is a physical impossibility and circuit limitations such as the nonlinearities of the active device would alter the feedback equation. For instance, at high output voltage swings, the amplifier would either "saturate" (be unable to supply more current) or "limit" (be cutoff because the grid was too negative) and  $A_o$  would decrease.

### Tuned-Plate Tuned-Grid Oscillator

It should be stressed that it is the *product* of  $\beta A_o$  that must be 1.0 for oscillations to occur. In the general case, both  $\beta$  and  $A_o$  may be complex numbers unlike those of the cathode-bias problem just discussed. That is, there is a phase shift associated with  $A_o$  and  $\beta$  with the phase shift of the product being equal to the sum of the individual phase shifts associated with each entity.

Therefore, if the total phase shift is 180 degrees and if the amplitude of the product is 1.0, oscillations will occur. At low frequencies, these conditions normally are the result of the effects of reactive components. A typical example is shown in Fig. 46 and the configuration is called a tuned-plate tuned-grid oscillator. If the input circuit consisting of  $L_1$  and  $C_1$  is tuned to a frequency  $f_0$ , with the output circuit ( $L_2$ ,  $C_2$ ) tuned to the same frequency, a high impedance to ground will exist at the input and output of the amplifier. Consequently, a small capacitance value represented by  $C_f$  is capable of supplying sufficient voltage feedback from the plate to the grid.

At other frequencies, or if either circuit is detuned, oscillations may not occur. For instance, off-resonant conditions in the output tank will reduce the output voltage and in effect, reduce the open-loop gain to the point where oscillations will cease. On the other hand, if the input circuit is detuned far from  $f_0$ , it will present a low impedance in series with the relatively high reactance of  $C_f$ . The



voltage divider thus formed will result in a small-valued  $\beta$  and the conditions for oscillations will not be fulfilled. However, for conditions near  $f_0$ , both the amplitude and phase of the  $\beta A_0$  product will be correct for oscillations to occur.

Under some conditions, the voltage across the tank circuit may be sufficient to cause the grid to be driven positive with respect to the cathode and grid current

will flow through  $C_g$ . During the rest of the rf cycle,  $C_g$  will discharge through  $R_g$  causing a negative bias voltage to be applied to the grid. This bias voltage sets the operating point of the oscillator and prevents excessive current flow.

### Miscellaneous Oscillator Circuits

Two other common type of oscillators are shown in Fig 47. In Fig. 47A, feedback voltage is applied across a tapped inductor while in Fig 47B, the voltage is applied across a capacitor instead. Quite often, a tuned plate circuit is not employed and an rf choke coil provides a high impedance load instead.

So-called "conventional" components such as tubes, transistors, ICs, resistors, inductors and capacitors are suitable up to and including the uhf range. However, at higher frequencies and for higher power levels in the uhf range, physical restrictions on the size of such components makes them impractical. Consequently, a different approach is required. All the components necessary for a particular application may be included in the active device itself. This is true in the klystron oscillator shown in Fig. 48. Here the feedback action takes place inside of the tube and in the electron stream. Electrons emitted from the cathode are accelerated and "modulated" on the first pass through the cavity resonator (which replaces the conventional tuned circuit used at lower frequencies). The electrons are then turned around by the repeller electrode and pass through the cavity again. On entering the cavity, the phase of the ac field there is such that the stream is retarded. However, this means that energy must be given up to the cavity and on out to the external circuit. As a result, the oscillations in the cavity are sustained.

Similar effects are employed in other microwave oscillators and amplifiers. Motional energy in the electron stream is transferred to a desired ac field. In doing so, dc energy in the power supply is converted to useful ac energy at the microwave frequency.

### Solid-State Microwave Oscillators

Since transistors are capable of amplification they can function also as oscillators. As was discussed earlier in this section, it is necessary only to feed back some of the output power to the input port, in the correct phase, to obtain oscillation. At microwaves it is very difficult to determine the actual  $f_{max}$  (maximum frequency of oscillation) of a given transistor because of the parasitic elements which exist (L and C). Therefore, most microwave oscillators which employ transistors require some empirical work in order to learn their capabilities as oscillators in the upper uhf and microwave regions.

Fig. 49 shows the fundamental circuitry for a Colpitts microwave oscillator. The inductance L and the C1, C2 capacitances

represent the parasitic components of the transistor package.

An L-band transistor oscillator is illustrated in Fig. 50. An RCA 2N5108 is used as a 1.68-GHz oscillator. The collector of Q1 is connected to the ground plane of a 1/16-inch (1.6-mm) Teflon/fiberglass micro-stripline pc board. Output power is extracted from the base of Q1 through L1, a 0.75-inch (19.1-mm) length of 50-ohm micro-stripline, plus C1 and C2. Efficiency is approximately 20 percent. Power output at 1.68 GHz is in excess of 300 mW at -25 volts collector supply.

An S-band solid-state oscillator is shown in Fig. 51. It operates at 2.0 GHz in the common-base oscillator mode. The RCA 2N5470 delivers approximately 300 mW of output when a collector supply of +24 volts is used. Line section L4 and

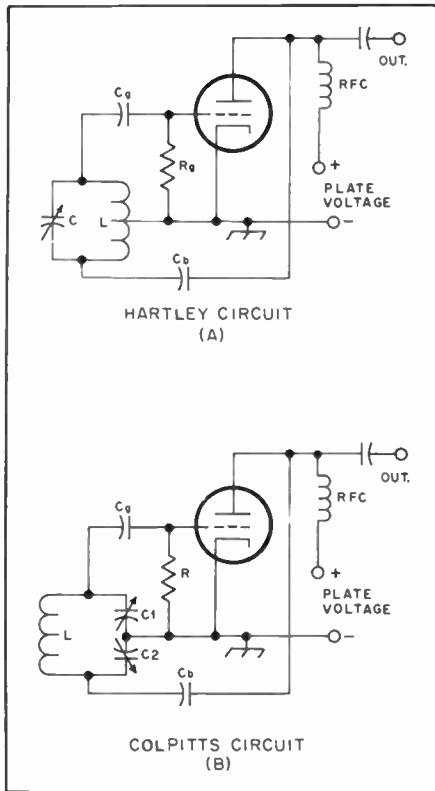


Fig. 47 — Hartley and Colpitts oscillators.

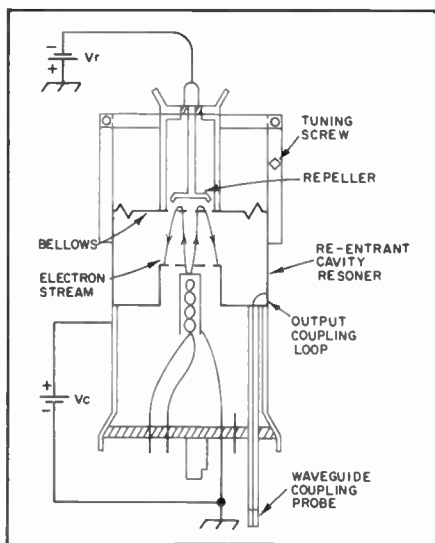


Fig. 48 — Cross-sectional view of a typical reflex klystron oscillator. Such types as the 732 may still be available on occasion in surplus sales.

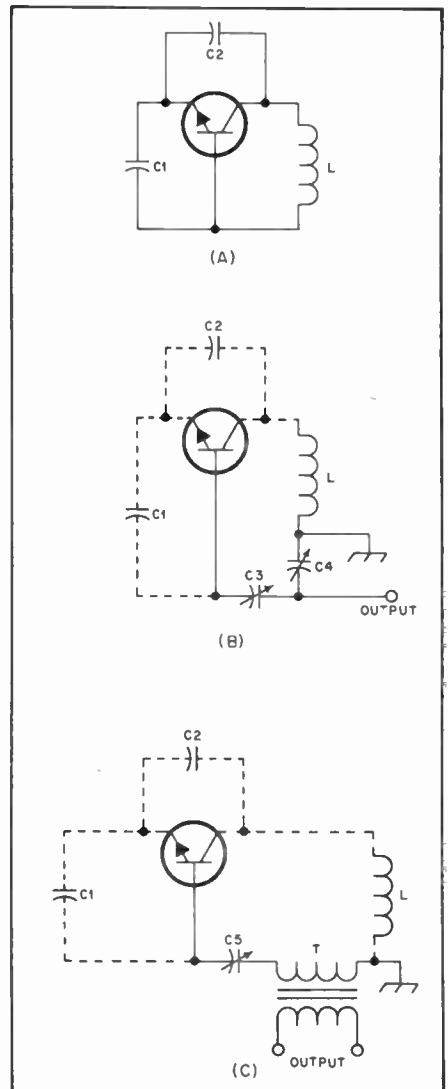


Fig. 49 — Colpitts oscillator for use at microwave frequencies: (A) basic ac circuit configuration; (B) basic circuit with the collector returned to ground through a parasitic inductance, L, and the output taken from base through capacitive voltage divider; (C) basic ac circuit with transformer-coupled output.

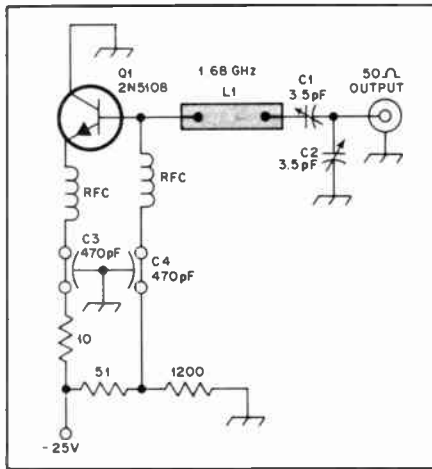


Fig. 50 — 1.68-GHz oscillator using the RCA 2N5108.

C1 form a phase-resonant loop to provide the required feedback.

### Gunn-Diode Microwave Oscillators

In the area of low-power microwave generation, klystrons have been replaced largely by solid-state devices. One device which is popular with amateurs is the Gunn diode. When the dc voltage applied across a sample of n-type gallium arsenide (GaAs) is increased, a point is reached beyond which the current flow fluctuates at a regular rate. The frequency of this variation is dependent upon the thickness of the GaAs material, becoming higher as the material is made thinner. Thinner slabs require a lower threshold voltage to initiate the "Gunn effect."

In practice, a Gunn-diode package (see Fig. 52) is mounted in a resonant cavity. Dc bias is applied through a quarter-wave-length choke. At millimeter wavelengths

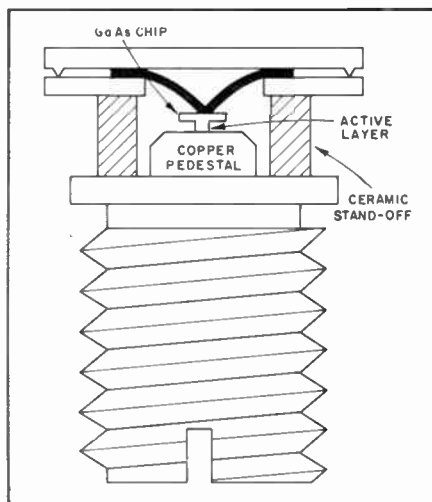


Fig. 52 — Cross-section drawing of a typical Gunn-diode package. The GaAs chip is sandwiched between the copper pedestal and the top section of the holder. Actual size of this package is about 0.2-inch (5.1-mm) long and 0.13-inch (3.3-mm) in diameter.

this choke is very short and may be part of the cavity wall. A small-value bypass capacitor may also form part of the cavity wall. A drawing of a typical Gunn-diode oscillator is given in Fig. 53. While application of Gunn diodes is mechanically and electrically simple, the devices do have several shortcomings the user should be aware of. Gunn-diode efficiency is on the order of two to five percent, meaning the input power is 20 to 50 times the output power. Compared with the power-supply requirements of the klystron however, this fact poses no great hardship.

A more serious problem with Gunn diodes is that of frequency instability with voltage and temperature fluctuation. The former is easily compensated for, but the latter is not. At 10,000 MHz (10 GHz), a Gunn oscillator will drift on the order of 350 kHz for a temperature change of 1°C. The entire cavity may be enclosed in a thermal oven similar to those used with piezoelectric crystals, or the ambient temperature of the cavity may be raised with a heating element. These cures only degrade system efficiency by wasting additional power. Automatic-frequency-control techniques may be used to stabilize the oscillator, with some increase in circuit complexity. Alternatively, the Gunn oscillator may be locked to a stable reference through a technique called injection locking. Here, a sample reference signal is injected into the oscillator cavity. If it is within the range of the Gunn oscillator, the circuit will lock to this reference. Locking may be maintained over a large range of bias and temperature changes.

Gunn-diode oscillators available to amateurs can provide power outputs up to 100 mW. At present, they are used mostly on the 10- and 24-GHz bands. Devices are available to operate on the 5.6-GHz band as well.

In addition to microwave oscillation, a Gunn diode produces significant output at lower frequencies. This oscillation will modulate the bias voltage causing undesired extreme shifts in frequency. A

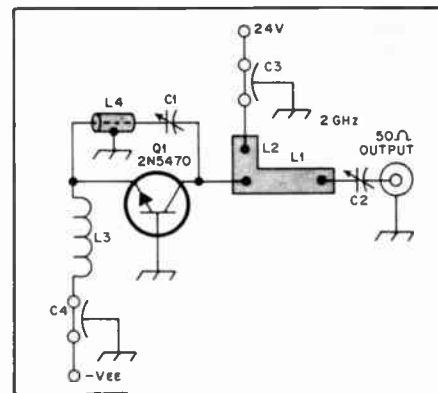


Fig. 51 — Microstripline 2-GHz oscillator circuit using the RCA 2N5470.

C1, C2 — 0.35-3.5 pF, Johanson type 4702 or equiv.

C3, C4 — 100 pF, Allen-Bradley type 5A5C or equiv.

L1 — Microstripline 0.70-inch (17.8-mm) long × 0.30-inch (7.6-mm) wide, mounted on 1/32-inch (0.8-mm) Teflon fiberglass board.

L2 — Microstripline 0.43-inch (10.9-mm) long × 0.08-inch (2.0 mm) wide mounted on 1/32-inch Teflon fiberglass board.

L3 — 5 turns no. 33 wire, 1/16-inch (1.6-mm) ID × 3/16-inch (4.8-mm) long.

L4 — 50-ohm miniature coaxial line, 1-1/2 inches long.

10 μF electrolytic capacitor connected across the bias terminal will prevent such oscillation. It is also desirable to protect the Gunn diode from possible application of overvoltage or voltage of an incorrect polarity. A Zener diode will afford this protection at low cost and should be mounted on the bias terminal as well. The schematic of a basic Gunn oscillator and power supply is given in Fig. 54.

Frequency modulation of a Gunn oscillator may be accomplished by modulation of the bias supply. Audio may also be applied to the bias terminal through a coupling capacitor. Frequency deviation will be greater if the supply voltage is directly modulated. Because oscillator frequency is affected by supply voltage, the bias regulation must be very good. Typical bias requirements for Gunn diodes are from 10 to 14 volts. This voltage may be obtained from a variable

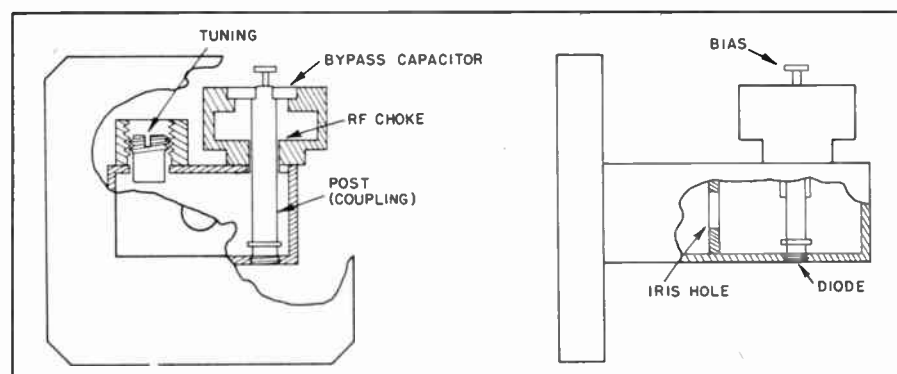


Fig. 53 — A simple Gunn-diode-oscillator cavity for direct mounting to waveguide or a waveguide horn. Coarse frequency adjustment is accomplished by means of the tuning screw. A smaller cavity which functions as an rf choke is discussed in the text.

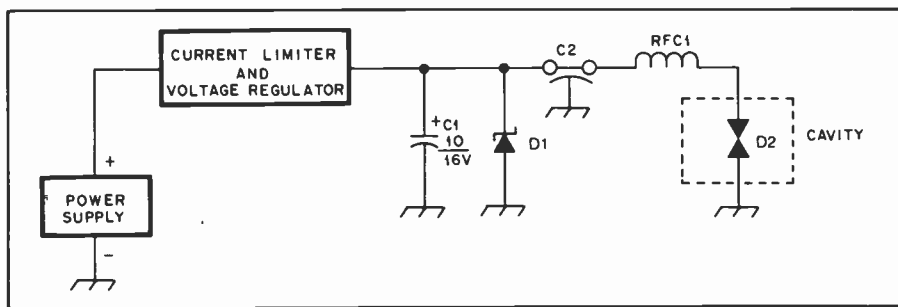


Fig. 54 — Block diagram of a basic Gunn-diode oscillator, showing the various components necessary for proper operation. Current limiting is desirable to prevent damage to the supply in the event of Gunn or Zener-diode failure.

- C1 — Electrolytic capacitor.  
 C2 — Feedthrough/bypass capacitor (part of microwave cavity).  
 D1 — Zener diode. Voltage rating selected slightly higher than maximum safe operating

- voltage of Gunn diode.  
 D2 — Gunn diode.  
 RFC1 — 1/4-wavelength cavity. May be machined into cavity wall. A similar length of transmission line may be used.

output regulator such as the 723. If additional current capacity is needed an external pass transistor may be added.

### Glossary of Radio Terms

It is not unusual for an inexperienced radio amateur to be confused by some of the terms which are taken for granted by those who have been involved with the pastime for many years. Many of the "strange" words which are found in this handbook and other amateur publications are listed here for the convenience of the layman in the radio field. Although this glossary is far from being all-inclusive, it does contain the most-used words which may cause confusion. A complete dictionary of modern electronics words and expressions is available to those wishing to complement the radio library — *IEEE Standard Dictionary of Electrical and Electronics Terms* by John Wiley & Sons, Inc., New York, NY 10016

### The Terms

**active** — As used in *active filter* or *active device*: A device or circuit which requires an operating voltage. (See *passive*.)  
**analog** — A term used in computer work, meaning a system which operates with numbers represented by directly measurable quantities (analog readout — mechanical dial system. See *digital*).  
**balun** — Balanced to unbalanced-line transformer.  
**bank wound** — Pertaining to a coil (inductor) which has two or more layers of wire, each being wound over the top of the preceding one. (See *solenoid*.)  
**bandpass** — A circuit or component characteristic which permits the passage of a single band of frequency while attenuating those frequencies which lie above and below that frequency band.  
**band-reject** — A circuit or device which rejects a specified frequency band while passing those frequencies which lie above and below the rejected band (opposite of *band-pass*). Sometimes called "band-rejection," as applied to a filter.

**bandwidth** — The frequency width of circuit or component, such as a band-pass filter or tuned circuit. Usually measured at the half-power points of the response curve (−3 dB points).

**base loading** — Applies to vertical antennas for mobile and fixed-location use; an inductance placed near the ground end of a vertical radiator to change the electrical length. With variations the inductor aids in impedance matching.

**bifilar** — Two conducting elements used in parallel; two parallel wires wound on a coil form, as one example.

**bilateral** — Having two symmetrical sides or terminals; a filter (as one example) which has a 50-ohm characteristic at each port, with either port suitable as the input or output one.

**bias** — To influence current to flow in a specified direction by means of dc voltage; forward bias on a transistor stage, or grid bias on a tube type of amplifier.

**binary** — Relating to two logical elements; a system of numbers having two as its base.

**bit** — An abbreviation of a binary digit; a unit of storage capacity. Relates primarily to computers.

**blanker** — A circuit or device which momentarily removes a pulse or signal so that it is not passed to the next part of a circuit; a noise blanker. Not to be confused with a *clipper*, which clips part of a pulse or waveform.

**bridge** — An electrical instrument used for measuring or comparing inductance, impedance, capacitance or resistance by comparing the ratio of two opposing voltages to a known ratio; to place one component in parallel with another; to join two conductors or components by electrical means.

**byte** — A sequence of adjacent binary digits operated upon as a unit — usually shorter than a word.

**cascade** — One device or circuit which directly follows another; two or more similar devices or circuits in which the output of one is fed to the input of the

succeeding one (tandem).

**cascode** — Cascaded stages which are cathode-coupled.

**chip** — Slang term for an integrated circuit, meaning a chip of semiconductor material upon which an IC is formed.

**clamp** — A circuit which maintains a predetermined characteristic of a wave at each occurrence so that the voltage or current is "clamped" or held at a specified value.

**clipper** — A device or circuit which limits the instantaneous value of a wave form or pulse to a predetermined value (see *blanker*).

**closed loop** — A signal path which includes a forward route, a feedback path, and a summing point which provides a closed circuit. In broad terms, an amplifying circuit which is providing voltage or power gain while being terminated correctly at the input and output ports, inclusive of feedback.

**cold end** — The circuit end of a component which is connected to ground or is bypassed for ac or rf voltage (the grounded end of a coil or capacitor).

**composite** — Made up of a collection of distinct components; a complete ("composite") circuit rather than a discrete part of an overall circuit.

**conversion loss/gain** — Relating to a mixer circuit from which less output energy is taken than is supplied at the input-signal port (loss); when a mixer delivers greater signal output than is supplied to the input-signal port (gain).

**damping** — A progressive reduction in the amplitude of a wave with respect to time (usually referenced to microseconds or milliseconds); a device or network added to a circuit to "damp" unwanted oscillations.

**decay time** — The period of time during which the stored energy or information "decays" to a specified value less than its initial value, such as the discharge time of a timing network.

**differential amplifier** — An amplifier that has an output signal which is proportional to the algebraic difference between two input signals (sometimes called a "difference amplifier").

**digital** — Relating to data which is rendered in the form of digits; digital readout or display (see *analog*).

**diplexer** — The simultaneous transmission or reception of two signals while using a common antenna, made possible by using a "diplexer." Used in TV broadcasting to transmit visual and aural carriers by means of a single antenna.

**discrete** — A single device or circuit (a transistor as opposed to an IC) (see *composite*).

**dish** — An antenna reflector for use at vhf and higher which has a concave shape. For example, a part of a sphere or paraboloid.



- drive** — Rf energy applied at the input of an rf amplifier (rf driving power or voltage).
- duplexer** — A device which permits simultaneous transmission and reception of related signal energy while using a common antenna (see *diplexer*).
- dynamic range** — Difference in dB or dBm between the overload level and minimum discernible signal level (MDS) in a system, such as a receiver. Parameters include desensitization point and distortion products as referenced to the receiver noise floor.
- empirical** — Not based on mathematical design procedures; experimental endeavor during design or modification of a circuit. Founded on case-history experience or intuition.
- enabling** — The preparation of a circuit for a subsequent function (enabling pulse or signal).
- encoder** — A device for enabling a circuit; to express a character or message by means of a code while using an encoder. Using a tone or tones to activate a repeater, as one example, in which case a Touch-Tone pad could be the encoder.
- excitation** — Signal energy used to drive a transmitter stage (see *drive*). Voltage applied to a component to actuate it, such as the field coil of a relay.
- feedback** — A portion of the output voltage being fed back to the input of an amplifier. Description includes ac and dc voltage which can be used separately or together, depending on the particular circuit.
- feedthrough** — Energy passing through a circuit or component, but not usually desired. A type of capacitor which can be mounted on a chassis or panel wall to permit *feeding through* a dc voltage while bypassing it to ground at ac or rf. Sometimes called a "coaxial capacitor."
- ferromagnetic** — Material which has a relative permeability greater than unity and requires a magnetizing force. (Ferrite and powdered-iron rods and toroids).
- finite** — Having a definable quantity; a finite value of resistance or other electrical measure.
- flip-flop** — An active circuit or device which can assume either of two stable states at a given time, as dictated by the nature of the input signal.
- floating** — A circuit or conductor which is above ac or dc ground for a particular reason. Example: A floating ground bus which is not common to the circuit chassis.
- gate** — A circuit or device, depending upon the nature of the input signal, which can permit the passage or blockage of a signal or dc voltage.
- GDO** — Abbreviation for a grid-dip oscillator (test instrument). Correct for only a tube-type of dip meter.
- ground loop** — A circuit-element condition (pc-board conductor, metal chassis or metal cabinet wall) which permits the unwanted flow of ac current from one circuit point to another.
- half-power point** — The two points on a response curve which are 3 dB lower in level than the peak power. Sometimes called the "3 dB bandwidth."
- high end** — Refers generally to the "hot" (rf or dc) end of a component or circuit; the end opposite the grounded or bypassed end (see *cold end*).
- high level** — The part of a circuit which is relatively high in power output and consumption as compared to the small-signal end of a circuit. Example: A transmitter PA stage is the high-level amplifier, as might be the driver also.
- high-pass** — Related mainly to filters or networks which are designed to pass energy above a specified frequency, but attenuate or block the passage of energy below that frequency.
- high-Z** — The high-impedance part of a circuit; a high-impedance microphone; a high-impedance transformer winding.
- hot end** — see *high end*.
- hybrid** — A combination of two generally unlike things; a circuit which contains transistors and tubes, for example.
- ideal** — A theoretically perfect circuit or component; a lossless transformer or device that functions without any faults.
- insertion loss** — That portion of a signal, current or voltage which is lost as it passes through a circuit or device. The loss of power through a filter or other passive network.
- interpolate** — To estimate a value between two known values.
- leakage** — The flow of signal energy beyond a point at which it should not be present. Example: Signal leakage across a filter because of poor layout (stray coupling) or inadequate shielding.
- linear amplification** — The process by which a signal is amplified without altering the characteristic of the input waveform. Class A, AB and B amplifiers are generally used for linear amplification.
- load** — A circuit or component that receives power; the power which is delivered to such a circuit or component. Example: A properly matched antenna is a load for a transmitter.
- loaded** — A circuit is said to be *loaded* when the desired power is being delivered to a load.
- logic** — Decision-making circuitry of the type found in computers.
- long wire** — A horizontal wire antenna which is one wavelength or greater in size. A long piece of wire does not (less than one wavelength) qualify as a long wire.
- low end** — See *cold end*.
- low level** — Low-power stage or stages of a circuit as referenced to the higher-power stages (see *high level*).
- low pass** — A circuit property which permits the passage of frequencies below a specified frequency, but attenuates or blocks those frequencies above that frequency (see *high pass*).
- low-Z** — Low impedance (see *high-Z*).
- mean** — A value between two specified values; an intermediate value.
- master oscillator** — The primary oscillator for controlling a transmitter or receiver frequency. Can be a VFO (variable-frequency oscillator), VXO (variable crystal oscillator), PTO (permeability-tuned oscillator), PLL (phase-locked loop), LMO (linear master oscillator) or frequency synthesizer.
- network** — A group of components connected together to form a circuit which will conduct power, and in most examples effect an impedance match. Example: An LC matching network between stages of a transistorized transmitter.
- nominal** — A theoretical or designated quantity which may not represent the actual value. Sometimes referred to as the "ball-park value."
- op amp** — Operational amplifier. A high-gain, feedback-controlled amplifier. Performance is controlled by external circuit elements. Most op amps are used as dc amplifiers.
- open loop** — A signal path which does not contain feedback (see *closed loop*).
- parameter** — The characteristic behavior of a device or circuit, such as the operating characteristics of a 2N5109 transistor.
- parametric amplifier** — Synonym for "reactance amplifier." An inverting parametric device for amplifying a signal without frequency translation from input to output.
- parasitic** — Unwanted condition or quantity, such as *parasitic oscillations* or *parasitic capacitance*; additional to the desired characteristic.
- passive** — Operating without an operating voltage. Example: An LC filter which contains no amplifiers, or a diode mixer.
- PEP** — Peak envelope power; maximum amplitude that can be achieved with any combination of signals.
- permeability** — A term used to express relationships between magnetic induction and magnetic force.
- pill** — Slang expression for a transistor or an IC.
- PL** — Private line, such as a repeater which is accessed by means of a specified tone.
- PLL** — Phase-locked loop type of oscillator.
- port** — The input or output terminal of a circuit or device.
- prototype** — A first full-scale working version of a circuit design.
- QL** — Loaded Q of a circuit.
- Qu** — Unloaded Q of a circuit.
- resonator** — A general term for a high-Q



- resonant circuit, such as an element of a filter.
- return* — That portion of a circuit which permits the completion of current flow, usually to ground — a “ground return.”
- ringing* — The generation of an audible or visual signal by means of oscillation or pulsating current; the annoying sound developed in some audio filters when the Q is extremely high.
- ripple* — Pulsating current. Also, the gain depressions which exist in the flat portion of a bandpass response curve (above the -3 dB points on the curve). Example: Passband ripple in the nose of an i-f filter response curve.
- rise time* — The time required for a pulse or waveform to reach the peak value from some smaller specified value.
- rms* — Root mean square. The square root of the mean of the square of the voltage or current during a complete cycle.
- rotor* — A moving rotary component within a rotation-control device. Not to be confused with a *rotator*, which is the total assembly.
- saturation* — A condition which exists when a further change in input produces no additional output (a saturated amplifier).
- selectivity* — A measure of circuit capability to separate the desired signal from those at other frequencies.
- shunt* — A device placed in parallel with or across part of another device. Examples: Meter shunts, shunt-fed vertical antennas and a capacitor placed (shunted) across another capacitor.
- solenoidal* — A single-layer coil of wire configured to form a long cylinder.
- spectral purity* — An emission which contains essentially the desired signal component, with all mixing products and harmonics attenuated greatly.
- strip* — General term for two or more stages of a circuit which in combination perform a particular function. Examples: A local-oscillator strip, an audio strip or an i-f strip.
- subharmonic* — A frequency that is an integral *submultiple* of a frequency to which it is referred. A misleading term which implies that subharmonic energy can be created along with harmonic energy (not true). More aptly, a 3.5-MHz VFO driving a 40-meter transmitter, with 3.5-MHz leakage at the output, qualifying as a subharmonic.
- SWR* — Standing-wave ratio. The ratio of the forward power to the power reflected from a load as a result of impedance mismatch.
- toroidal* — Doughnut-shaped physical format, such as a toroid core.
- transducer* — A device which is used to transport energy from one system (electrical, mechanical or acoustical) to another. Example: A loudspeaker or phonograph pickup.
- transceiver* — A combination transmitter and receiver which uses some parts of the circuit for both functions.
- transverter* — A converter which permits transmitting and receiving at a specified frequency apart from the capability of the transceiver to which it is connected as a basic signal source. Example: A 2-meter transverter used in combination with an hf-band transceiver.
- Transmatch* — An LC network used to effect an impedance match between a transmitter and a feed line to an antenna. Not an “antenna tuner” or “antenna coupler.”
- trap* — A device consisting of L and C components which permits the blockage of a specified frequency while allowing the passage of other frequencies. Example: A wave trap or an antenna trap.
- trifilar* — Same as *bifilar*, but with three parallel conductors.
- trigger* — To initiate action in a circuit by introducing an energy stimulus from an external source, such as a scope trigger.
- U* — Symbol for unrepairable assembly, such as an integrated circuit.
- unloaded* — The opposite condition of *loaded*.
- varactor* — A two-terminal semiconductor device (diode) which exhibits a voltage-dependent capacitance. Used primarily as a tuning device or frequency multiplier at vhf and uhf.
- VCO* — Voltage-controlled oscillator. Uses tuning diodes which have variable dc applied to change their junction capacitances.
- VSWR* — Voltage standing-wave ratio. (See *SWR*.)
- VU* — Volume Unit.
- Z* — Symbol for a device or circuit which contains two or more components. Example: A parasitic suppressor which contains a resistor and an inductor in parallel.
- Zener diode* — Named after the inventor. A diode used to regulate voltage or function as a *clamp* or *clipper*.
- Z ratio* — Impedance ratio which exists between two specific impedance values.

# Solid-State Fundamentals

The electrical characteristics of solid-state devices such as diodes and transistors are dependent upon phenomena that take place at the atomic level. While semiconductors can be employed without a complete knowledge of these effects, some understanding is helpful in various applications. Electrons, which are the principal charge carriers in both vacuum tubes and semiconductors, behave much differently in either of the two circumstances. In free space, an electron can be considered as a small charged solid particle. On the other hand, the presence of matter affects this picture greatly. For instance, an electron attached to an atom has many properties similar to those of rf energy in tuned circuits. It has a frequency and wavelength that depend upon atomic parameters just as the frequency associated with electrical energy in a tuned circuit depends upon the values of inductance and capacitance.

A relation between the energy of an electron in an atomic "orbit" and its associated frequency is given by

$$f(\text{Hz}) = \frac{E \text{ (joules)}}{6.625 \times 10^{-27}}$$

where the constant in the denominator is called Planck's constant. This equation is

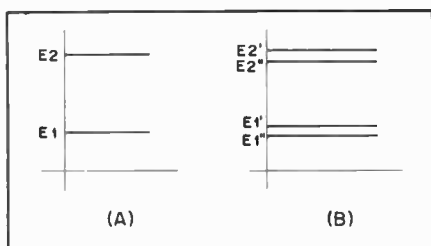


Fig. 1 — Energy-level diagram of a single atom is shown at A. At B, the levels split when two atoms are in close proximity.

quite important when an electron is either raised or falls between two different energy "states." For instance, when an electron drops from one level to a lower one, energy is emitted in the form of electromagnetic radiation. This is the effect that gives the characteristic glow to neon tubes, mercury-vapor rectifiers, and even light-emitting diodes. The frequency of the emitted radiation is given by the foregoing formula where E is the difference in energy. However, if an electron receives enough energy such that it is torn from an atom, a process called ionization is said to occur (although the term is also loosely applied to transitions between any two levels). If the energy is divided by the charge of the electron ( $-1.6 \times 10^{19}$  coulombs), the equivalent in voltage is obtained.

A common way of illustrating these energy transitions is by means of the energy-level diagram shown in Fig. 1A. It should be noted that unlike ordinary graphical data, there is no significance to the horizontal axis. In the case of a single atom, the permitted energy can only exist at discrete levels (this would be characteristic of a gas at low pressure where the atoms are far apart). However, if a single atom is brought within close proximity of another one of similar type, the single energy levels split into pairs of two that are very close together (Fig. 1B). The analogy between tuned circuits and electron energy levels can be carried even further in this case.

Consider the two identical circuits that are coupled magnetically as shown in Fig. 2A. Normally, energy initially stored in C1 would oscillate back and forth between L1 and C1 at a single frequency after the switch was closed. However, the presence of the second circuit consisting of L2 and C2 (assume L1 equals L2 and C1 equals C2) results in the waveform shown in Fig. 2B. Energy also oscillates back and forth

between the two circuits and the current then consists of components at two slightly different frequencies. The effect is similar to the splitting of electron energy levels when two atoms are close enough to interact.

## Conductors, Insulators and Semiconductors

Solids are examples of large numbers of atoms in close proximity. As might be expected, the splitting of energy levels continues until a band structure is reached. Depending upon the type of atom, and the physical arrangement of the component atoms in the solid, three basic conditions can exist. In Fig. 3A, the two discrete energy levels have split into two bands. All the states in the lower band are "occupied" by electrons while the ones in the higher energy band are only partially filled.

In order to impart motion to an electron, the expenditure of energy is required. This means an electron must then be raised from one energy state to a higher one. Since there are many permitted states in upper level of Fig. 3A that are both unoccupied and close together, electrons in this level are relatively free to move about. Consequently, the material is a conductor. In Fig. 3B, all the states in the lower level are occupied, there is a big gap between this level and the next higher one, and the upper level is empty. This means if motion is to be imparted to an electron, it must be raised from the lower level to the upper one. Since this requires considerable energy, the material is an insulator. (The energy-level representation gives an insight into the phenomena of breakdown. If the force on an electron in an insulator becomes high enough because of an applied field, it can acquire enough energy to be raised to the upper level. When this happens, the material goes into a conducting state.)

A third condition is shown in Fig. 4. In

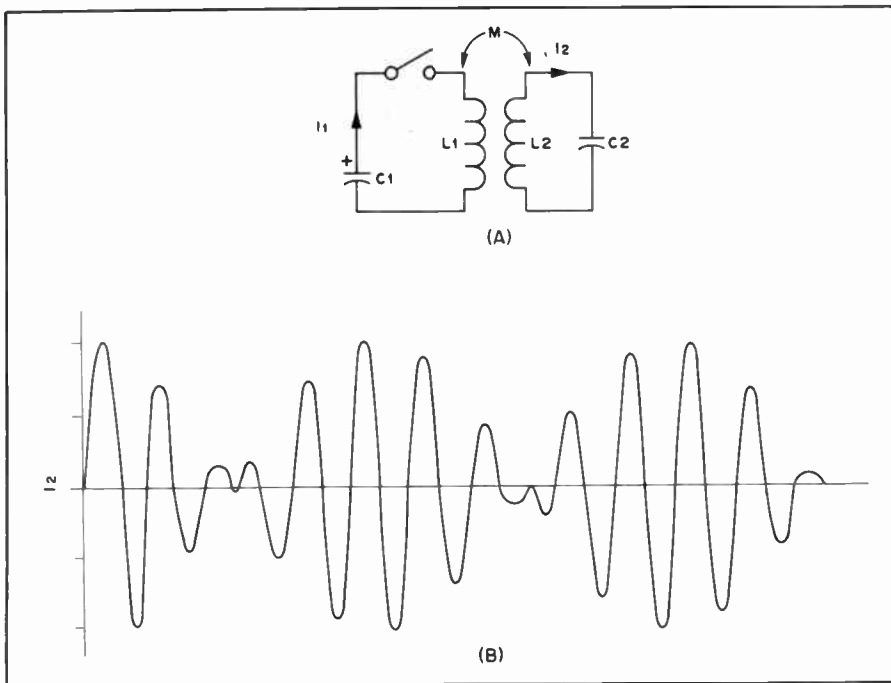


Fig. 2 — Electrical-circuit analog of coupled atoms.

the material associated with this diagram, the upper level is unoccupied but is very close to the occupied one. Hence, under conditions where the random electron motion is low (low temperature), the material acts as an insulator (Fig. 4A). However, as the random or thermal motion increases, some electrons acquire enough energy to move up to states in the upper level. Consequently, both levels are partially occupied as shown in Fig. 4B. The line marked  $W_f$  represents a statistical entity related to the "average" energy of electrons in the material and is called the Fermi Level. At absolute zero (no thermal motion),  $W_f$  is just at the top of the lower energy level. As electrons attain enough energy to move to the upper level,  $W_f$  is approximately halfway between the two levels.

### The PN Junction

The material for the diagram shown in Fig. 4 is called an intrinsic semiconductor and examples are the elements germanium and silicon. As such, the materials do not have any rectifying properties by themselves. However, if certain elements are mixed into the intrinsic semiconductor in trace amounts, a mechanism for rectification exists. This is shown in Fig. 5A. If an element with an occupied energy level such as arsenic is introduced into germanium, a transformation in conductivity takes place. Electrons in the new occupied level are very close to the upper partially filled band of the intrinsic germanium. Consequently, there are many extra charge carriers available when thermal energy is sufficient to raise some of the electrons in the new level to the partially filled one. Germanium with an

excess of mobile electrons is called an n-type semiconductor.

By introducing an element with an empty or unoccupied energy level near the lower partially filled level (such as boron), a somewhat different transformation in conductivity occurs. This is shown in Fig. 5B. Electrons from the lower level can move into the new unoccupied level if the thermal energy is sufficient. This means there is an excess of *unoccupied* states in the germanium lower energy level. Germanium treated this way is called a p-type semiconductor.

A physical picture of both effects is shown in Fig. 6. The trace elements or impurities are spread throughout the intrinsic crystal. Since the distance of separation is much greater for atoms of the trace elements than it is for ones of the intrinsic crystal, there is little interaction between the former. Because of this lack of "coupling," the distribution of energy states is a single level rather than a band. In Fig. 6A, atoms of the trace element are represented by the + signs since they have lost an electron to the higher energy level. Consequently, such elements are called donors. In Fig. 6B, the impurity atoms that have "trapped" an electron in the new state are indicated by the - signs. Atoms of this type are called acceptor impurities.

While it is easy to picture the extra free electrons by the circled "minus" charges in Fig. 6A, a conceptual difficulty exists with the freed "positive" charges shown in Fig. 6B. In either case, it is the motion of electrons that is actually taking place and the factor that is responsible for any current. However, it is convenient to consider that a positive charge carrier

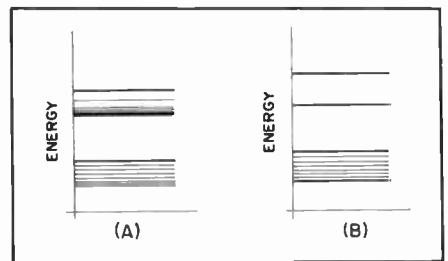


Fig. 3 — The energy level of a conductor is illustrated at A. A similar level for an insulator is depicted at B.

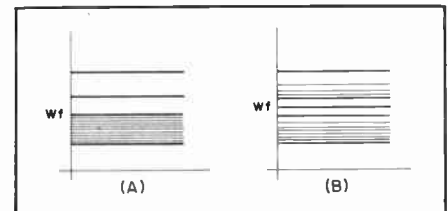


Fig. 4 — Semiconductor energy-level representation.

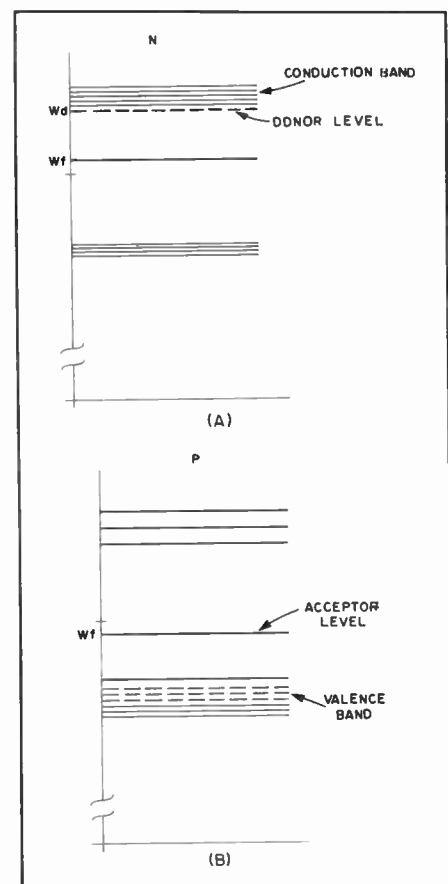


Fig. 5 — The effects on the energy level if impurity atoms are introduced.

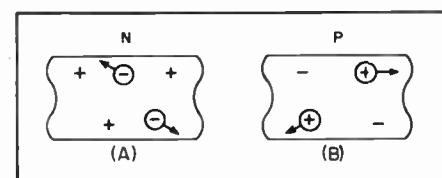


Fig. 6 — N- and p-type semiconductors.

exists called a hole. It would seem as though a dislocation in the crystal-lattice structure was moving about and contributing to the total current.

If a section of n-type material is joined to another section made from p-type, a one-way current flow results. This is shown in Fig. 7. A positive potential applied to the p-type electrode attracts any electrons that diffuse in from the n-type end. Likewise, holes migrating from the p-type end into the n-type electrode are attracted to the negative

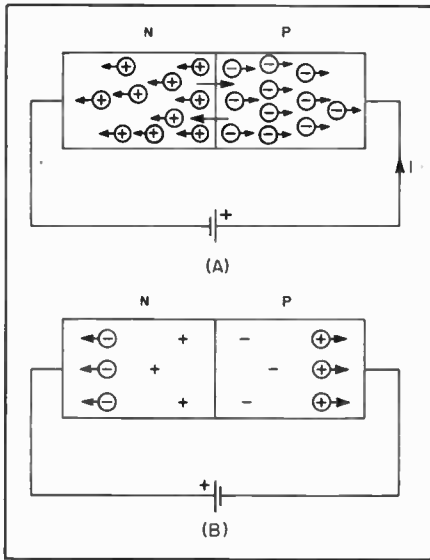


Fig. 7 — Elementary illustration of current flow in a semiconductor diode.

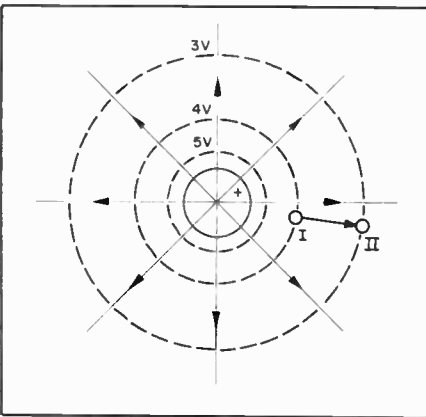


Fig. 8 — Potential diagram of an electron in atomic orbit.

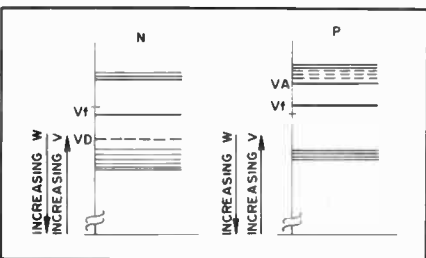


Fig. 9 — Energy-level diagram in terms of potential.

terminal. Note that the diagram indicates not all the carriers reach the terminals. This is because some carriers combine with ones of the opposite sign while enroute. In the case of a diode, this effect doesn't present much of a problem since the total current remains the same. Other carriers take the place of those originally injected from the opposite regions. However, such recombination degrades the performance of transistors considerably and will be discussed shortly.

If a voltage of the opposite polarity to that of a Fig. 7A is applied to the terminals, the condition in Fig. 7B results. The mobile charge carriers migrate to each end as shown leaving only the fixed charges in the center near the junction. Consequently, little current flows and the pn junction is "back biased." It can be seen that the pn junction constitutes a diode since current can flow readily only in one direction. While this simple picture suffices for introductory purposes, proper treatment of many important effects in semiconductors requires a more advanced analysis than the elementary model affords. Returning to Figs. 3, 4 and 5, it would be convenient if the diagrams were in terms of voltage rather than energy. As pointed out earlier, the relation between energy and voltage associated with an electron is given by

$$W = eV = (-1.6 \times 10^{-19})V$$

Because the electron has been assigned a minus charge, a somewhat upside-down world results. However, if it is kept in mind that it requires the *expenditure* of energy to move an electron from a point of *higher* potential to one at a *lower* value, this confusion can be avoided. As an illustration, suppose an electron is moved from an atomic orbit indicated by I in Fig. 8 to orbit II. This would mean the electron would have had to been moved against the force of attraction caused by the positive nucleus resulting in an *increase* in potential energy. (In other words, orbit II is at a higher energy level than orbit I.) However, note that the electrostatic potential around the nucleus decreases with distance and that orbit II is at a lower potential than orbit I.

Consequently, the energy-level diagram in terms of voltage becomes inverted as shown in Fig. 9. It is now possible to approach the problem of the pn junction diode in terms of the energy-level diagrams presented previously. If a section of n-type and p-type material is considered separately, the respective energy (or voltage) levels would be the same. However, if the two sections were joined together and connected by an external conductor as shown in Fig. 10, a current would flow initially. This is because the voltage corresponding to the statistical energy referred to previously (Fermi Level)

is not the same for p- and n-type materials at the same temperature. At the Fermi Level, the probability that a particular energy state is occupied is one half. For n-type material, the Fermi Level is shifted upward toward the "conduction band" (Fig. 5A). In a p-type material, it is shifted downward toward the "valence band." Although the theory behind the Fermi Level and definitions concerning the conduction and valence bands won't be dealt with here, it is sufficient to know that the band structure shifts so that the Fermi Levels are the same in both parts of the joined sections (Fig. 10).

The reasoning behind this effect is as follows. Consider conditions for hole flow only for the moment. Since there is an excess of holes in the p region (Fig. 10), there is a tendency for them to move over into the adjacent n region because of diffusion. The process of diffusion is demonstrated easily. If a small amount of dye is dropped into some water, it is concentrated in a small area at first. However, after a period of time has passed, it spreads out completely through the entire volume.

Once the holes diffuse into the n region, they recombine with the electrons present and produce a current in the external terminals denoted by  $I_D$  (Fig. 10). But a paradox results because of this current. If  $S_1$  is opened so that  $I_D$  flows through R, where does the energy that is transferred (irreversibly) to this resistance come from? In effect, it represents a perpetual-motion dilemma or else the semiconductor will cool down since the diffusion process is the result of a form of thermal motion. Both conclusions are against the laws of physics, so a third alternative is necessary. It is then assumed that the Fermi Levels align so that the potential across the terminals becomes zero, and no current will flow in the external circuit.

However, if the Fermi Levels are the same, the conduction and valence bands in either section will no longer align. As a consequence, a difference in potential between the two levels exists and is indicated by  $V_B$  in Fig. 10. *The formation of this junction or barrier voltage is of prime importance in the operation of pn-junction devices.* Note that holes in the p region must overcome the barrier voltage which impedes the flow of the diffusion current. It will also be recalled that both holes and electrons were generated in the intrinsic semiconductor because of thermal effects (Fig. 4B). The addition of either donor or acceptor atoms modifies this effect somewhat. If donor atoms are present (n-type material), fewer holes are generated. On the other hand, if acceptor atoms represent the impurities, fewer electrons are generated in comparison to conditions in an intrinsic semiconductor. In the case of p-type material, holes predominate and are termed the majority carriers. Since there



are fewer electrons in p-type material, they are termed the minority carriers.

Referring to Fig. 10A, there are some holes in the n region (indicated by the + signs) because of the foregoing thermal effects. Those near the junction will experience a force caused by the electric field associated with the barrier voltage. This field will produce a flow of holes into the p region and the current is denoted by  $I_T$ . Such a current is called a drift current as compared to the diffusion current  $I_D$ . Under equilibrium conditions, the two currents are equal and just cancel each other. This is consistent with the assumption that no current flows in the external circuit because of the fact that the Fermi Levels are the same and no voltage is produced.

So far, only conditions for the holes in the upper (or conduction) band have been considered, but identical effects take place with the motion of electrons in the lower energy band (valence band). Since the flow of charge carriers is in opposition, but because holes and electrons have opposite signs, the currents *add*.

### The Forward-Biased Diode

If an external emf is applied to the diode terminals as shown in Fig. 10B, the equilibrium conditions no longer exist and the Fermi Level voltage in the right-hand region is shifted upward. This means the barrier voltage is decreased and considerable numbers of carriers may now *diffuse* across the junction. Consequently,  $I_D$  becomes very large while  $I_T$  decreases in value because of the decrease in barrier voltage. The total current under "forward-bias" conditions then becomes

$$I = I_s \left( e^{\frac{eV_x}{kT}} - 1 \right)$$

At room temperature, the ratio  $kT/e$  is approximately 0.026 volts and so for an external voltage,  $V_x$ , that exceeds this value, the current increases very rapidly.

### The Reverse-Biased Diode

If the source,  $V_x$ , is reversed as shown in Fig. 10C, the barrier voltage is *increased*.

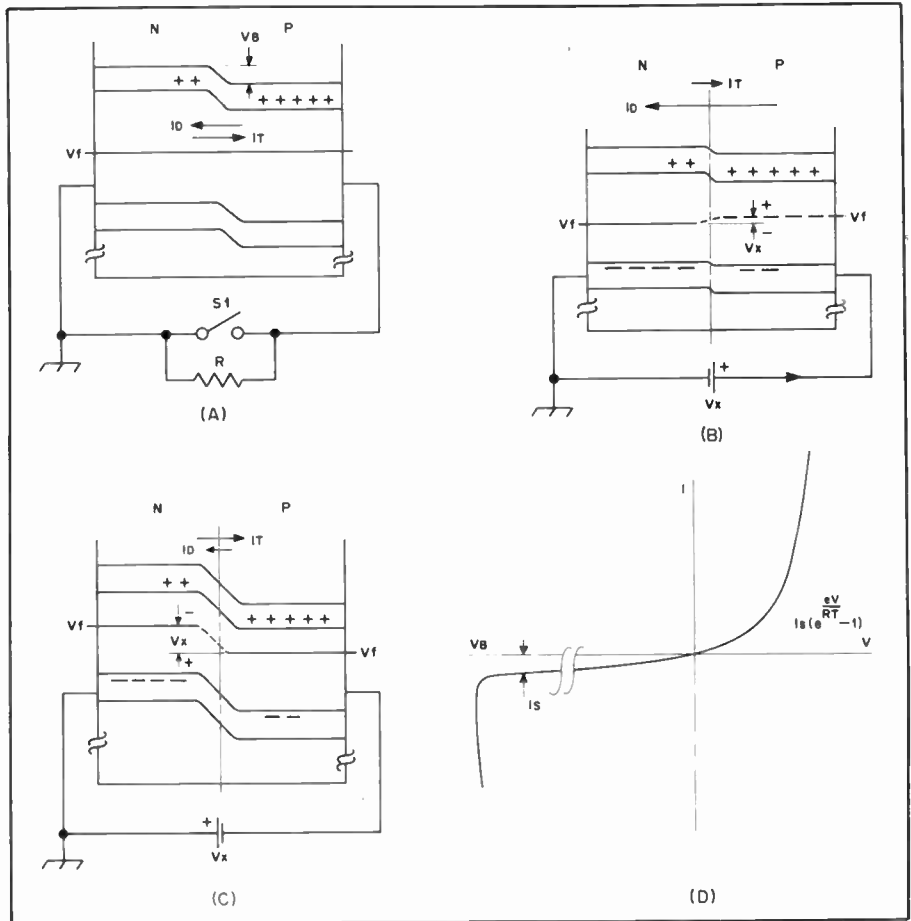


Fig. 10 — Energy-level diagrams for unbiased (A), forward-biased (B), and reversed-biased diode (C). Illustration D shows the resultant characteristics of the diode.

Consequently, charge carriers must overcome a large "potential hill" and the diffusion current becomes very small. However, the drift current caused by the thermally generated carriers returns to the value it had under equilibrium conditions. For large values of  $V_x$ , the current approaches  $I_s$ , defined as the reverse saturation current,  $I_s$  is the sum of  $I_T$  and its counterpart in the lower or "valence" band. Finally, the characteristic curves of the forward- and reversed-bias diode can be constructed and are shown in Fig. 10D.

It is obvious that  $I_s$  should be as small

as possible in a practical diode since it would only degrade rectifier action. Also, since it is the result of the generation of thermal carriers, it is quite temperature sensitive which is important when the diode is part of a transistor. If the reverse voltage is increased further, an effect called avalanche breakdown occurs as indicated by the sudden increase in current at  $V_b$ . In such an instance, the diode might be damaged by excessive current. However, the effect is also useful for regulator purposes and devices used for this purpose are called Zener diodes.

## Semiconductor Devices and Practical Circuits

The radio amateur may be more interested in the practical aspects of semiconductors than he or she might be in the theoretical considerations that are covered in the previous section. This portion of the chapter provides a practical treatment of how diodes, transistors and ICs perform in actual circuits. Greater coverage of the chemistry and in-depth theory of solid-state devices can be obtained by reading some of the texts

listed in the bibliography at the end of the chapter. *Solid State Design for the Radio Amateur* (an ARRL publication) is recommended as a primer on basic semiconductor theory. The book also contains many pages of proven construction projects which use semiconductor devices.

### Semiconductor Diodes

The vacuum-tube diode has been replaced in modern equipment designs.

Semiconductor diodes are more efficient because they do not consume filament power. They are much smaller than tube diodes. In low-level applications they operate cooler than tubes do. Solid-state diodes are superior to tube types with respect to operating frequency. The former are suitable into the microwave region: Most vacuum-tube diodes are not practical at frequencies above 50 MHz.

Semiconductor diodes fall into two

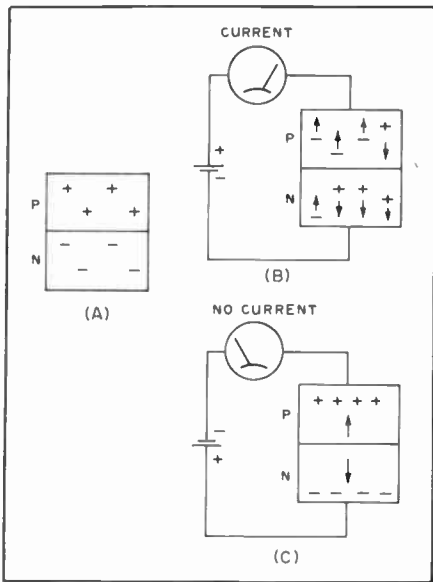


Fig. 11 — A p-n junction (A) and its behavior when conducting (B) and nonconducting (C).

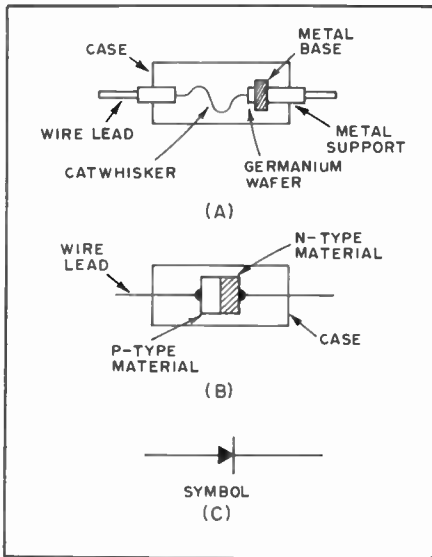


Fig. 12 — A point-contact type of diode is seen at A. A junction diode is depicted at B and the diode symbol is at C.

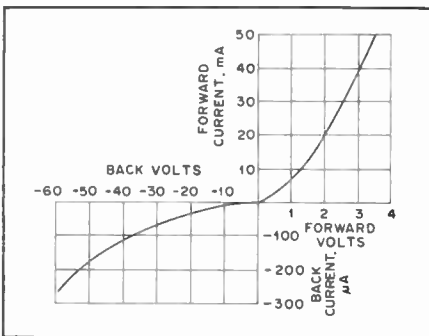


Fig. 13 — Typical point-contact diode (germanium) characteristic curve. Because the back current is much smaller than the forward current, a different scale is used for back voltage and current.

main categories, structurally. Although they can be made from silicon or germanium crystals, they are usually classified as p-n junction diodes or point-contact diodes. These formats are illustrated in Fig. 12. Junction diodes are used from dc to the microwave region, but point-contact diodes are intended primarily for rf applications. The internal capacitance of a point-contact diode is considerably less than that of a junction diode designed for the same circuit application. As the operating frequency is increased the unwanted internal and external capacitance of a diode becomes more troublesome to the designer. Where a given junction type of diode may exhibit a capacitance of several picofarads, the point-contact device will have an internal capacitance of 1 pF or less.

### Germanium Diodes

The germanium diode is characterized by a relatively large current flow when small amounts of voltage are applied in the "forward" direction (Fig. 11). Small currents will flow in the reverse (back) direction for much larger applied voltages. A representative curve is shown in Fig. 13. The dynamic resistance in either the forward or back direction is determined by the change in current that occurs, when the applied voltage is changed by a small amount. The forward resistance will vary somewhat in the region of very small applied voltages. However, the curve is

mostly straight, indicating a relatively constant dynamic resistance. For small applied voltages the resistance is on the order of 200 ohms or less. The back resistance exhibits considerable variation and is dependent upon the specific applied voltage during the test. It may vary from a few thousand ohms to well over a megohm. The back resistance of a germanium diode is considerably lower than that of a silicon diode. The latter is greater than a megohm in most instances, but the germanium diode is normally less than a megohm.

### Common Silicon Diodes

Apart from the fact that silicon p and n materials are used in the formation of a silicon junction diode, the characteristics of these devices are similar to those of germanium diodes. The voltage/current curves of Fig. 13 are representative.

The junction barrier voltage for silicon diodes is somewhat higher (approximately 0.7 volt) than that of a germanium diode. The latter is on the order of 0.3 volt. The majority of the diodes in use today fall into the silicon class. They are rugged and reliable from rf small-signal applications to dc power use.

Silicon diodes are available in ratings of 1000 volts (PRV) or greater. Many of these diodes can accommodate dc current in excess of 100 amperes. The primary rule in preventing damage to any diode is to operate the device within the maximum ratings specified by the manufacturer. The

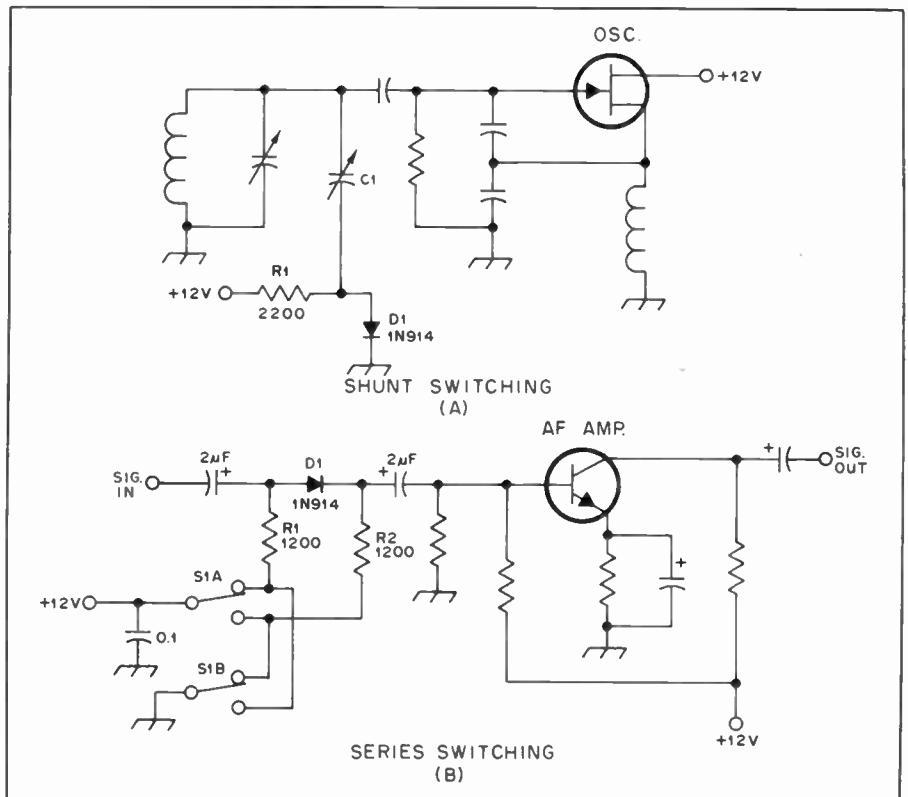


Fig. 14 — A silicon-switching diode, D1, is used at A to place C1 in the circuit. At B is seen a series switch with D1 in the signal path.

device temperature is one of the important parameters. Heat sinks are used with diodes that must handle large amounts of power, thereby holding the diode junction temperature at a safe level.

### Diodes as Switches

Solid-state switching is accomplished easily by using diodes or transistors in place of mechanical switches or relays. The technique is not a complicated one at dc and audio frequencies when large amounts of power are being turned on and off, or transferred from one circuit point to another. The present technology has not advanced far enough to permit high-power rf switching within the financial means of most radio amateurs.

Examples of shunt and series diode switching are given in Fig. 14. The illustration at A shows a 1N914 rf-switching type of diode as a shunt on-off element between C1 and ground. When +12 volts are applied to D1 through R1, the diode saturates and effectively adds C1 to the oscillator tank circuit. R1 should be no less than 2200 ohms in value to prevent excessive current flow through the diode junction.

Series diode switching is seen in Fig. 14B. In this example the diode, D1, is inserted in the audio signal path. When S1 is in the ON position the diode current path is to ground through R2, and the diode saturates to become a closed switch. When S1 is in the OFF state R1 is grounded and +12 volts are applied to the diode cathode. In this mode D1 is back biased (cut off) to prevent audio voltage from reaching the transistor amplifier. This technique is useful when several stages in a circuit are controlled by a single mechanical switch or relay. Rf circuits can also be controlled by means of series diode switching.

A significant advantage to the use of diode switching is that long signal leads are eliminated. The diode switch can be placed directly at the circuit point of interest. The dc voltage which operates it can be at some convenient remote point. The diode recovery time (switching speed) must be chosen for the frequency of operation. In other words, the higher the operating frequency the faster the switching speed required. For dc and audio applications one can use ordinary silicon power-supply rectifier diodes.

### Diodes as Gates

Diodes can be placed in series with dc leads to function as gates. Specifically, they can be used to allow current to flow in one direction only. An example of this technique is given in Fig. 15A.

A protective circuit for the solid-state transmitter is effected by the addition of D1 in the 13.6-volt dc line to the equipment. The diode allows the flow of positive voltage, but there will be a drop of approximately 0.7 volt across the

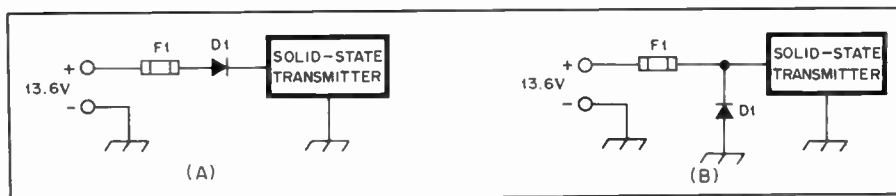


Fig. 15 — D1 at A protects the equipment if the supply leads are cross-polarized in error. At B the fuse will blow if the power supply is connected for the wrong polarity.

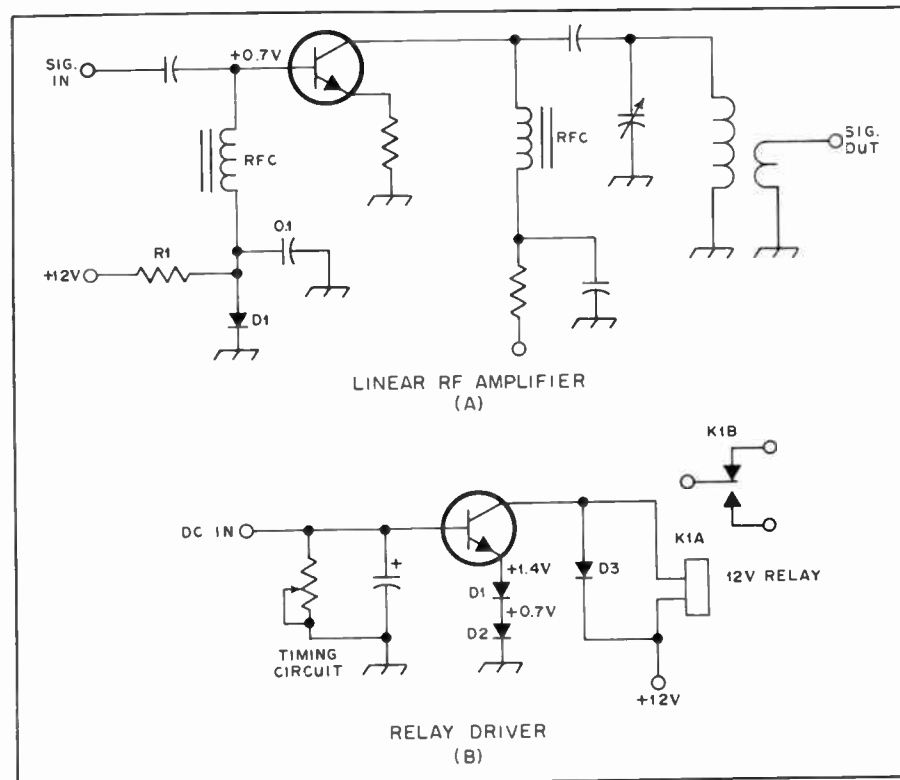


Fig. 16 — D1 establishes a 0.7-volt bias reference at A. Approximately 1.4 volts of emitter bias are established by connecting D1 and D2 in series at illustration B.

diode, requiring a supply voltage of 14.3. Should the operator mistakenly connect the supply leads in reverse, voltage will not flow through D1 to the transmitter. In this application the diode acts as a gate. D1 must be capable of passing the current taken by the transmitter, without overheating.

A power type of diode can be used in shunt with the supply line to the transmitter for protective purposes. This method is illustrated in Fig. 15B. If the supply polarity is crossed accidentally, D1 will draw high current and cause F1 to open. This is sometimes referred to as a "crowbar" protection circuit. The primary advantage of circuit B over circuit A is that there is no voltage drop between the supply and the transmitter.

### Diodes as Voltage References

Zener diodes are discussed later in this chapter. They are used as voltage references or regulators. Conventional junction diodes can be used for the same purposes by taking advantage of their barrier-

voltage characteristics. The greater the voltage needed, the higher the number of diodes used in series. Some examples of this technique are given in Fig. 16. At A the diode (D1) establishes a fixed value of forward bias (0.7 V) for the transistor, thereby functioning as a regulator. R1 is chosen to permit a safe amount of current to flow through the diode junction while it is conducting at the barrier voltage.

The circuit of Fig. 16B shows two diodes inserted in the emitter return of a relay-driver transistor. D1 and D2 set up a cutoff voltage of approximately 1.4. This reduces the static current of the transistor when forward bias is not provided at the transistor base. If too much static current flows the relay may not drop out when the forward bias decays across the timing network. The more sensitive the relay the greater the chance for such a problem. D1 and D2 prevent relay dropout problems of this variety. D3 is used as a transient suppressor. A spike will occur when the relay coil field collapses. If the amplitude of the spike is great enough, the transient,

while following the dc bus in a piece of equipment, can destroy transistors and diodes elsewhere in the circuit. In this application the diode (D3) can be regarded as a *clamp*, since it clamps the spike at approximately 0.7 volt.

### Using Diodes as Capacitors

Later in this chapter there is a discussion about VVC (voltage-variable capacitor) diodes. They are known also

as tuning diodes and Varicap diodes. It is possible, however, to use ordinary silicon diodes as voltage-variable capacitors. This is accomplished by taking advantage of the inherent changes in diode junction capacitance as the reverse bias applied to them is changed. The primary limitation in using high-speed switching diodes of the 1N914 variety is a relatively low maximum capacitance. At a sacrifice to low minimum capacitance, diodes can be used

in parallel to step up the maximum available capacitance. An example of two 1N914 silicon diodes in a diode tuning circuit is given in Fig. 17. As R1 is adjusted to change the back bias on D1 and D2, there will be a variation in the junction capacitance. That change will alter the VFO operating frequency. The junction capacitance increases as the back bias is lowered. In the circuit shown here the capacitance will vary from roughly 5 pF to 15 pF as R1 is adjusted. The diodes used in circuits of this kind should have a high Q and excellent high-frequency characteristics. Generally, tuning diodes are less stable than mechanical variable capacitors are. This is because the diode junction capacitance will change as the ambient temperature varies. This circuit is not well suited to mobile applications because of the foregoing trait.

### Diode Clippers and Clamps

The previous mention of diode clamping action (D3 in Fig. 16) suggests that advantage can be taken of the characteristic barrier voltage of diodes to clip or limit the amplitude of a sine-wave. Although there are numerous applications in this general category, diode clippers are more familiar to the amateur in noise limiter, audio limiter and audio compressor circuits. Fig. 18 illustrates some typical circuits which employ small-signal diodes as clamps and clippers. D1 in Fig. 18A functions as a bias clamp at the gate of the FET. It limits the positive sine-wave swing at approximately 0.7 V. Not only

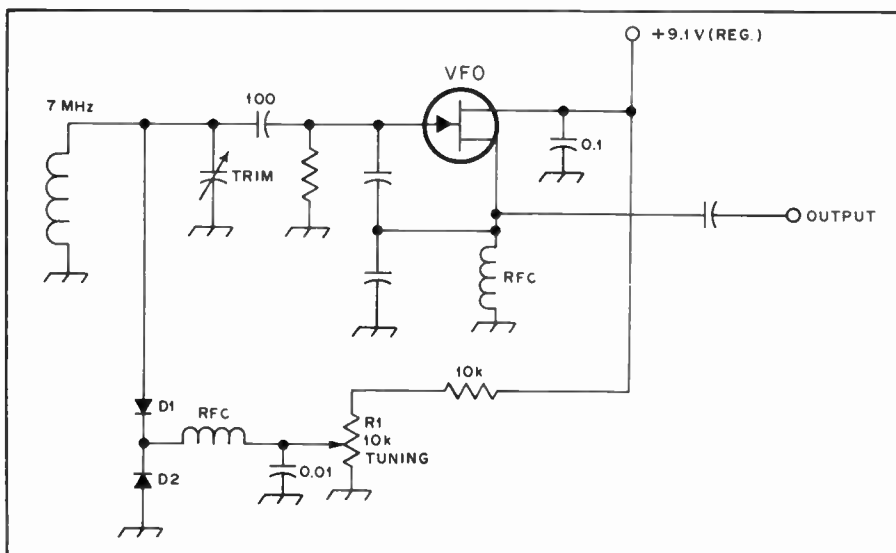


Fig. 17 — High-speed switching diodes of the 1N914 variety can be connected back to back and used as tuning diodes. As the reverse voltage is varied by means of R1, the internal capacitance of the diodes will change.

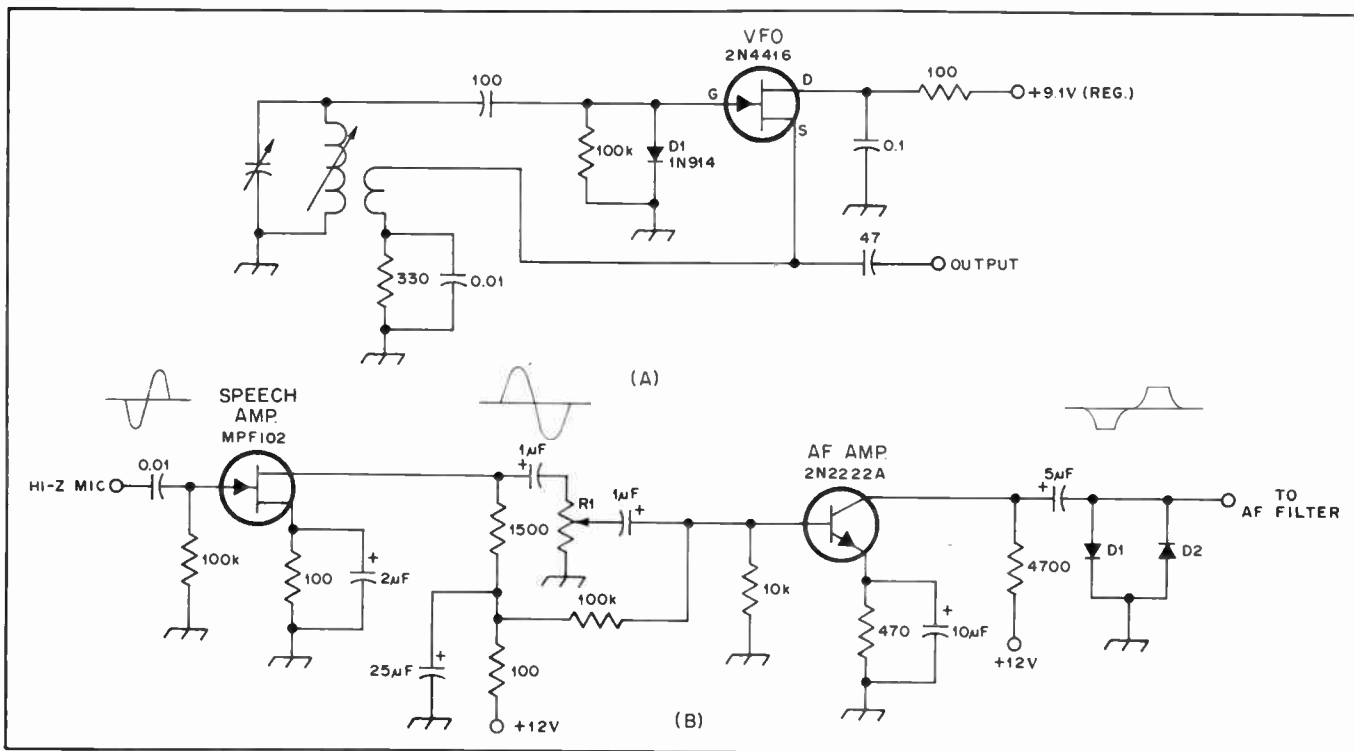


Fig. 18 — D1 serves as a bias stabilization device at A (see text). At B, D1 and D2 are employed as clippers to flatten the positive and negative af peaks. Clipping will occur at roughly 0.7 volt if silicon diodes are used. Audio filtering is required after the clipper to remove the harmonic currents caused by the diode action.



does the diode tend to regulate the bias voltage, it limits the transconductance of the FET during the positive half of the cycle. This action restricts changes in transistor junction capacitance. As a result, frequency stability of the oscillator is enhanced and the generation of harmonic currents is greatly minimized.

The circuit of Fig. 18B shows how a pair of diodes can be connected in back-to-back fashion for the purpose of clipping the negative and positive sine-wave peaks in an audio amplifier. If germanium diodes are used at D1 and D2 (1N34As or similar) the audio will limit at roughly 0.3 V. With silicon diodes (1N914 or rectifier types) the voltage will not exceed 0.7 V. R1 serves as the clipping-level control. An audio gain control is normally used after the clipper filter, along with some additional gain stages. The output of the clipper must be filtered to restore the sine-wave if distortion is to be avoided. Diode clippers generate considerable harmonic currents, thereby requiring an RC or LC type of audio filter.

### Diode Frequency Multipliers

Designers of rf circuits use small-signal diodes as frequency multipliers when they want to minimize the number of active devices (tubes or transistors) in a circuit. The primary disadvantage of diode multipliers is a loss in gain compared to that which is available from an active multiplier. Fig. 19 contains examples of diode frequency multipliers. The circuit at A is useful for obtaining odd or even multiples of the driving voltage. The efficiency of this circuit is not high, requiring that an amplifier be used after the diode multiplier in most applications. Resonator L1/C1 must be tuned to the desired output frequency.

A diode frequency doubler is seen at B in Fig. 19. It functions like a full-wave power-supply rectifier, where 60-Hz energy is transformed to 120-Hz by virtue of the diode action. This circuit will cause a loss of approximately 8 dB. Therefore, it is shown with a succeeding amplifier stage. If reasonable circuit balance is maintained, the 7-MHz energy will be down some 40 dB at the output of D1 and D2 — prior to the addition of L1 and C1. Additional suppression of the driving energy is realized by the addition of resonator L1/C1. T1 is a trifilar-wound toroidal transformer. At this frequency (7 MHz) a 0.5-inch diameter ferrite core (permeability of 125) will suffice if the trifilar winding contains approximately 10 turns. Additional information on this subject is given in *Solid State Design for the Radio Amateur*.

### Diode Detectors and Mixers

Diodes are effective as detectors and mixers when circuit simplicity and strong-signal handling capability are desired.

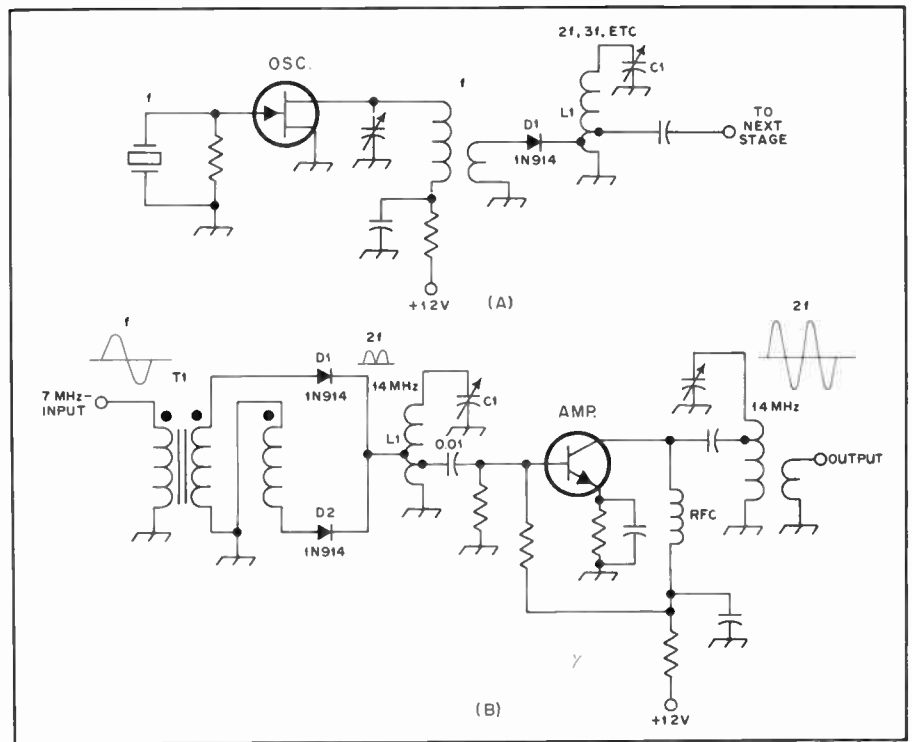


Fig. 19 — A simple diode frequency multiplier is shown at A. A balanced diode frequency doubler is seen at B. T1 is a trifilar-wound broadband toroid transformer.

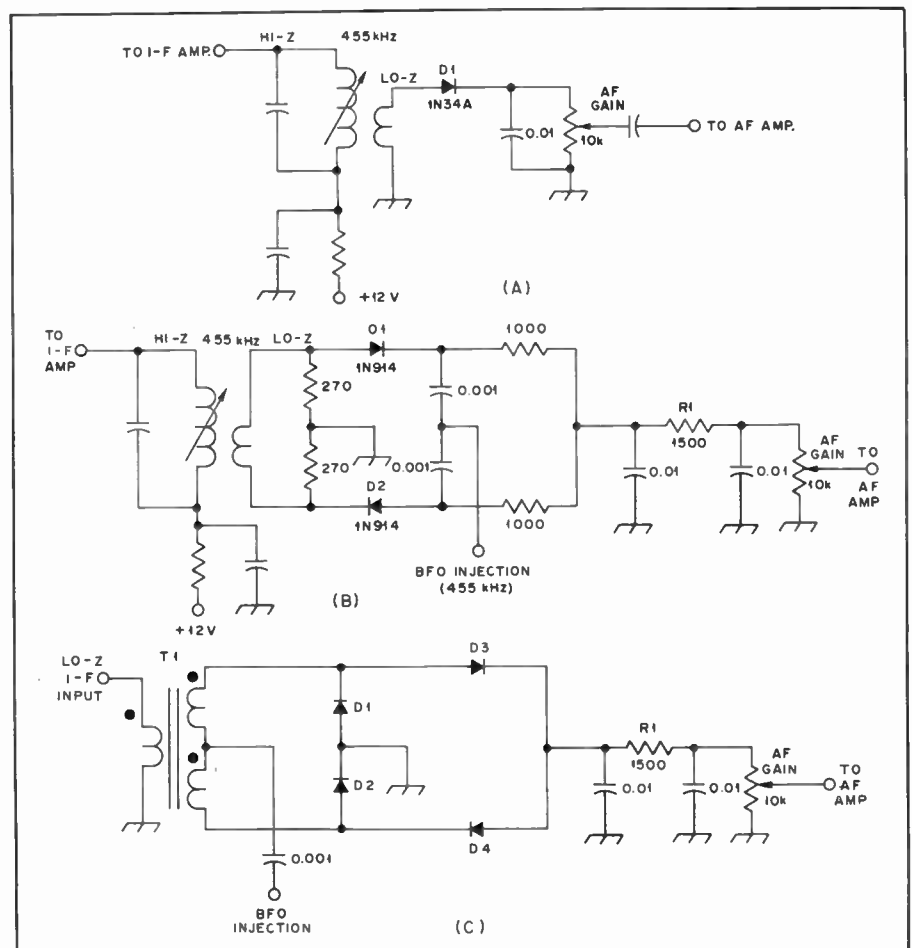


Fig. 20 — D1 at A is used as a simple a-m detector. Two versions of diode product detectors are illustrated at B and C. BFO injection for B and C should be approximately 10 volts pk-pk for best detector performance.

Impedance matching is an important design objective when diodes are used as detectors and mixers. The circuits are lossy, just as is the case with diode frequency multipliers. A diode detector or mixer will exhibit a conversion loss of 7 dB or more in a typical example. Therefore, the gain before and after the detector or mixer must be chosen to provide an acceptable noise figure for the overall circuit in which the diode stage is used. This is a particularly critical factor

when diode mixers are used at the front end of a receiver. A significant advantage in the use of diode mixers and detectors is that they are broadband in nature, and they provide a wide dynamic range. Hot-carrier diodes are preferred by some designers for these circuits, but the 1N914 class of switching diodes provide good performance if they are matched for a similar resistance before being placed in the circuit.

Fig. 20 illustrates some examples of

diode detectors. A basic a-m detector is seen at A. The circuit at B is that of a two-diode product detector. R1 and the two bypass capacitors serve as an rf filter to keep signal and BFO energy out of the following af amplifier stage. A four-diode product detector is illustrated at C. T1 is a trifilar-wound broadband transformer. The characteristic input impedance of T1 is 50 ohms. An rf filter follows this detector also. BFO injection voltage for the detectors at B and C should be between 8 and 10 volts pk-pk for best detector performance.

Circuits for typical diode mixers are given in Fig. 21. Product detectors are also mixers except for the frequencies involved. The output energy is at audio frequencies rather than at some rf intermediate frequency. The examples at A and B can be compared to those at C and D for the purpose of illustrating the similarity between balanced modulators and mixers. It is evident that product detectors, balanced modulators and mixers are of the same family. The diodes in all examples can be hot-carrier types or matched silicon switching diodes of the 1N914 class.

C1 and C2 in Fig. 21C and D are used for balancing purposes. They can be employed in the same manner with the circuits at A and B. The transformers in each illustration are trifilar-wound toroi-

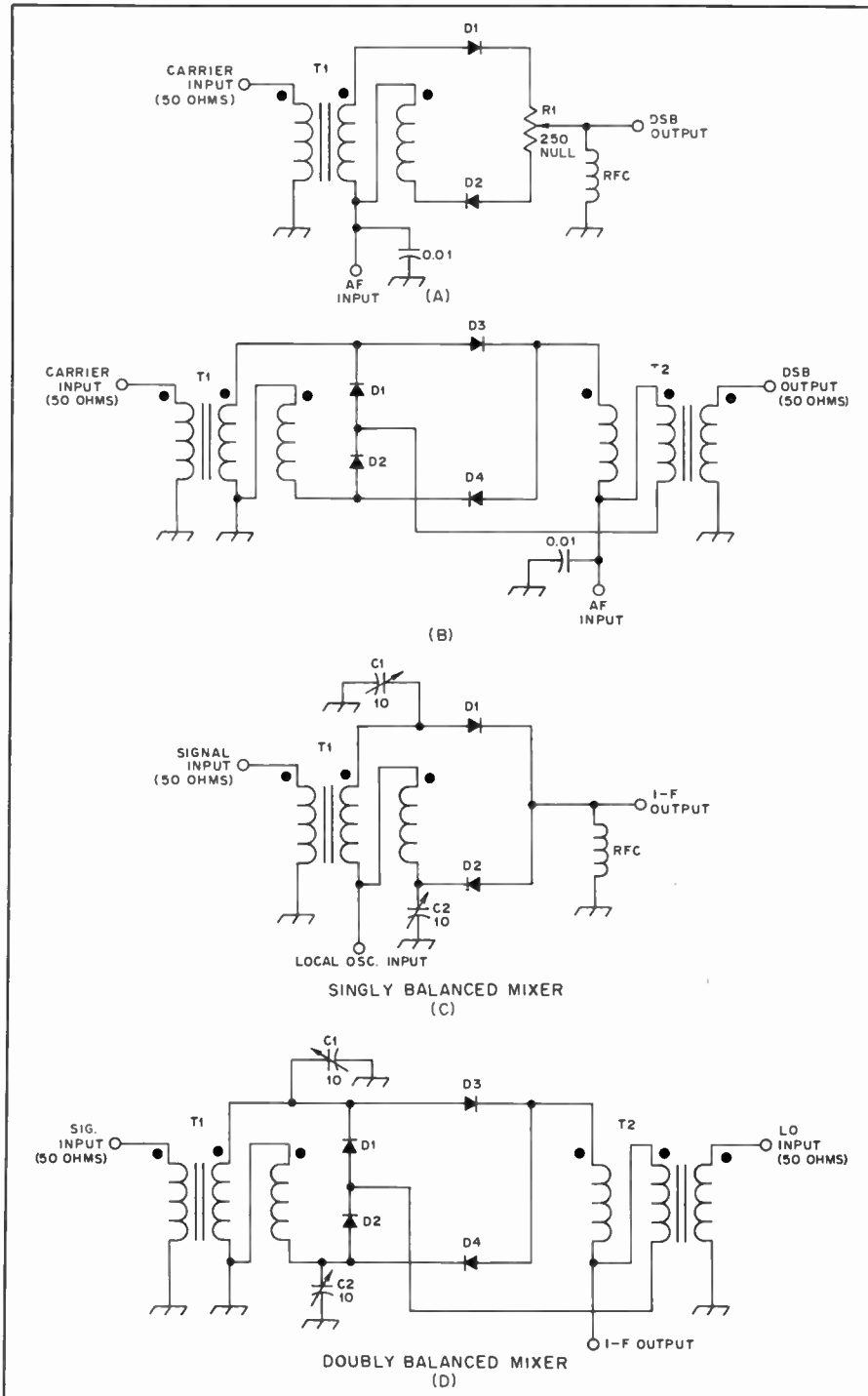


Fig. 21 — The examples at A and B are for use in balanced modulators. The similarity between these and balanced mixers is shown at C and D.

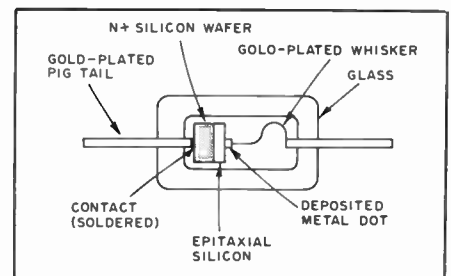


Fig. 22 — Cross-sectional representation of a hot-carrier diode (HCD).

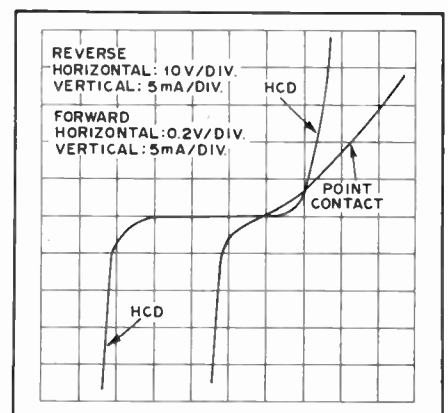


Fig 23 — Forward and reverse characteristics of a hot-carrier diode as compared to a p-n junction diode.

dal types. They provide a broadband circuit characteristic.

### Hot-Carrier Diodes

One of the more recent developments in the semiconductor field is the *hot-carrier diode*, or "HCD." It is a metal-to-semiconductor, majority-carrier conducting device with a single rectifying junction. The carriers are typically high-mobility electrons in an n type of semiconductor material. The HCD is particularly useful in mixers and detectors at vhf and higher. Notable among the good features of this type of diode are its higher operating frequency and lower conduction voltage compared to a p-n junction diode such as the 1N914.

When compared to a point-contact diode, the HCD is mechanically and electrically superior. It has lower noise, greater conversion efficiency, larger square-law capability, higher breakdown voltage, and lower reverse current. The internal capacitance of the HCD is markedly lower than that of a p-n junction diode and it is less subject to temperature variations.

Fig. 22 shows how the diode is structured internally. A typical set of curves for an HCD and a p-n junction diode are given in Fig. 23. The curves show the forward and reverse characteristics of both diode types.

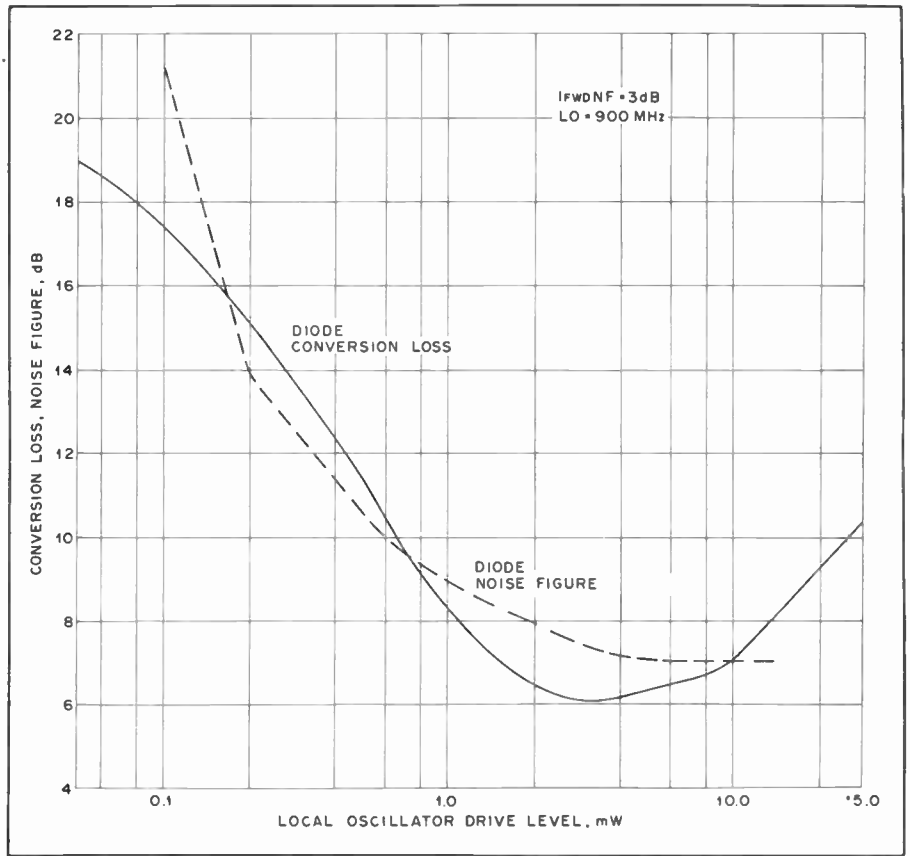


Fig. 24 — Noise figure and the conversion loss of a typical HCD that has no bias applied.

Fig. 25 — Curves for hot-carrier diode noise figure versus local-oscillator drive power. The bias currents are in mA as measured at point A in the representative test circuit.

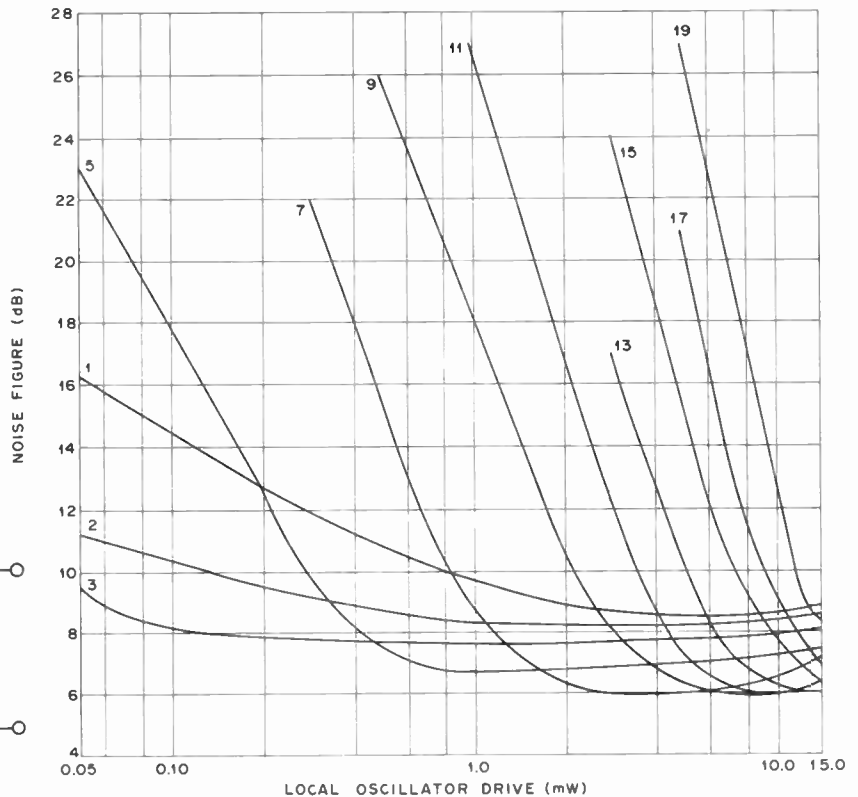
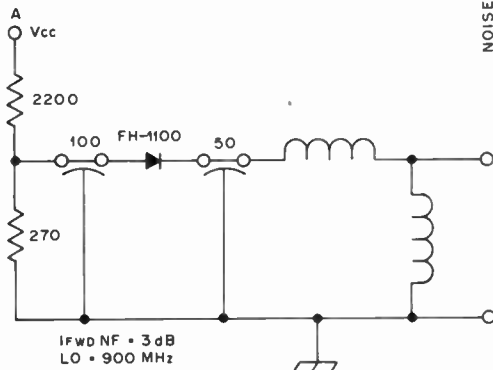


Fig. 24 illustrates the noise figure and conversion loss of an HCD with no bias is applied. When forward bias is applied to the diode, the noise figure will change from that which is seen in Fig. 24. Curves for various bias amounts are seen in Fig. 25. The numbers at the ends of the curves signify the amount of current (in mA) flowing into the test circuit at point A.

A set of curves which show conversion loss versus LO drive for an HCD mixer are given in Fig. 26. The test circuit used for the curves of Fig. 25 applies. The curve numbers indicate mA measured at point A. Further information on hot-carrier diodes can be found in the Fairchild *Application Note APP-177* and in the Hewlett Packard *Application Note 907*.

### Varactor Diodes

Mention was made earlier in this chapter of diodes being used as voltage-variable capacitors, wherein the diode junction capacitance can be changed by varying the reverse bias applied to the diode. Manufacturers have designed certain diodes for this application. They are called Varicaps (variable capacitor diodes) or varactor diodes (variable reactance diodes). These diodes depend upon the change in capacitance which occurs across their depletion layers. They are not used as rectifiers.

Varactors are designed to provide various capacitance ranges from a few picofarads to more than 100 pF. Each one has a specific minimum and maximum capacitance, and the higher the maximum amount the greater the minimum value. Therefore, the amateur finds it necessary to tailor his circuits for the midrange of the capacitance curve. Ideally, he will choose the most linear portion of the curve. Fig. 27A shows typical capacitance-voltage curves for three varactor diodes.

A representative circuit of a varactor diode is presented in Fig. 28. In this equivalent circuit the diode junction consists of  $C_j$  (junction capacitance) and  $R_j$  (junction resistance). The bulk resistance is shown as  $R_s$ . For the most part  $R_j$  can be neglected. The performance of the diode junction at a particular frequency is determined mainly by  $C_j$  and  $R_s$ . As the operating frequency is increased, the diode performance degrades, owing to the transit time established by  $C_j$  and  $R_s$ .

An important characteristic of the varactor diode is the Q, or figure of merit. The Q of a varactor diode is determined by the ratio of its capacitive reactance ( $X_j$ ) and its bulk resistance,  $R_s$ , just as is true of other circuit elements, such as coils and capacitors, where  $Q = X/R_s$  at a specified frequency. Fig. 27B characterizes the Q of three Motorola varactor diodes (versus

reverse bias) at 50 MHz.

Present-day varactor diodes operate into the microwave part of the spectrum. They are quite efficient as frequency multipliers at power levels as great as 25 watts. The efficiency of a correctly designed varactor multiplier exceeds 50 percent in most instances. Fig. 29 illustrates the basic circuit of a frequency multiplier which contains a varactor diode. D1 is a single-junction device which serves as a frequency tripler in this example. FL1 is required in order to assure reasonable purity of the output energy. It is a high-Q strip-line resonator. Without FL1 in the circuit there would be considerable output energy at 144, 288 and 864 MHz. Similar circuits are used as doublers, quadruplers and higher.

A Motorola MV104 tuning diode is used in the circuit of Fig. 30. It contains two varactor diodes in a back-to-back arrangement. The advantage in using two diodes is reduced signal distortion, as compared to a one-diode version of the same circuit. Reverse bias is applied equally to the two diodes in the three-terminal device. R1 functions as an rf isolator for the tuned circuit. The reverse bias is varied by means of R2 to shift the operating frequency. Regulated voltage is as important to the varactor as it is to the FET oscillator if reasonable frequency stability is to be assured. Varactor diodes are often used to tune two or more circuits at the same time (receiver rf amplifier, mixer and oscillator), using a single potentiometer to control the capacitance of the diodes. It is worth mentioning that some Zener diodes and selected silicon power-supply rectifier diodes will work effectively as varactors at frequencies as high as 144 MHz. If a Zener diode is used in this manner it must be operated below its reverse breakdown voltage point. The stud-mount variety of power supply diodes (with glass headers) are reported to be the best candidates as varactors, but not all diodes of this type will work effectively: Experimentation is necessary. Additional data concerning varactor diodes can be found in the Motorola booklet, *Designer's Manual for VVC Tuning Diodes*, LIB 2 R1.

### Gunn Diodes

Gunn diodes are named after the developer, J. B. Gunn, who was studying carrier behavior at IBM Corp. in 1963. During that period he discovered what is known today as the "Gunn effect."

Recently, semiconductor devices of the "bulk effect" variety have become so practical that in areas where advanced technology is practiced they are commonplace. Among these newer devices are the TDO (tunnel-diode oscillator), the ADO (avalanche-diode oscillator) and the TEO (transferred-electron oscillator). With some of the present-day techniques and solid-state devices it is possible to generate

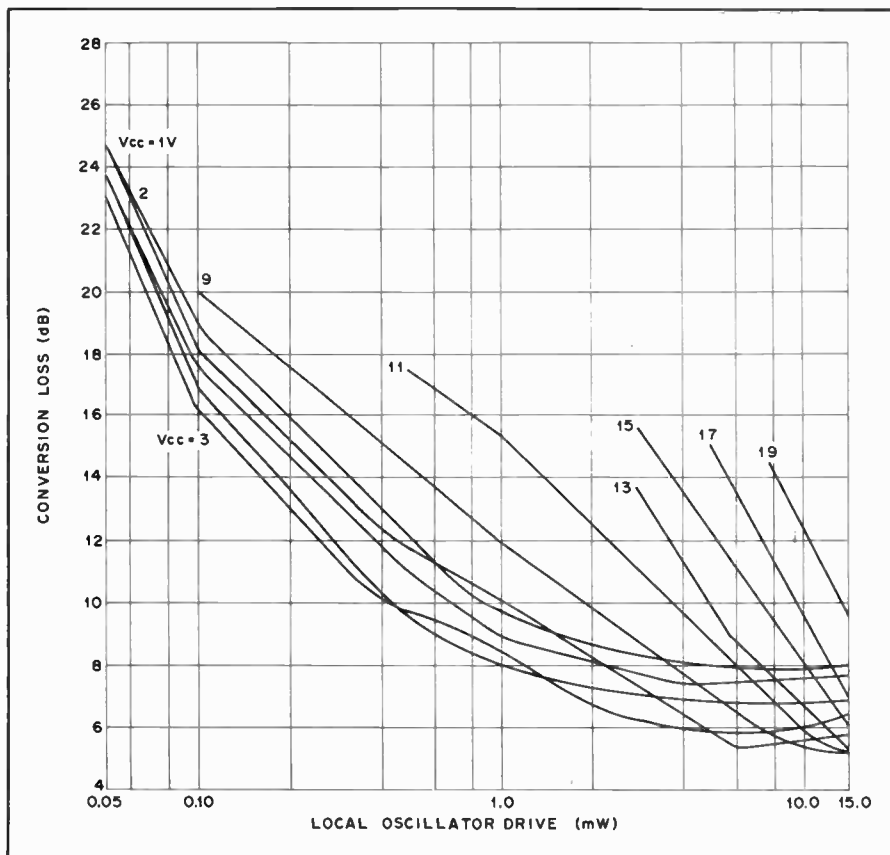


Fig. 26 — Local-oscillator drive power versus conversion loss for a specified bias amount. Bias currents are in mA as measured at point A of the circuit in Fig. 25.



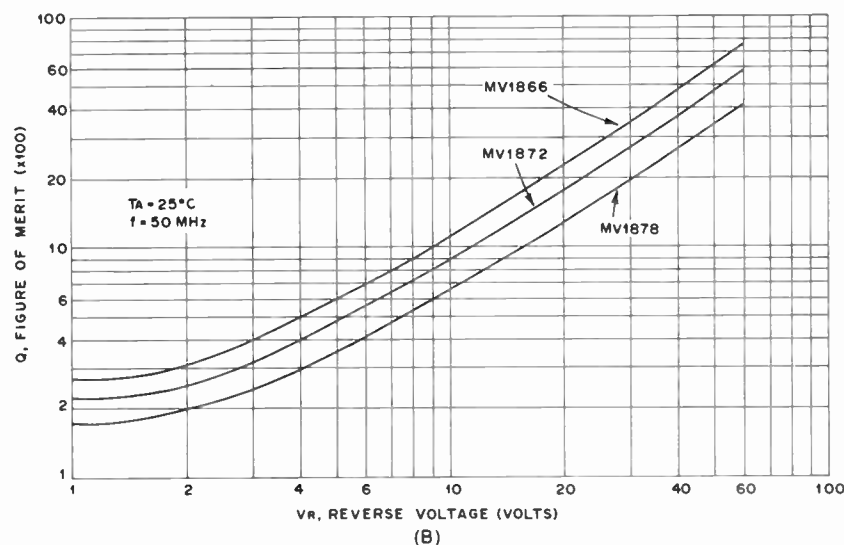
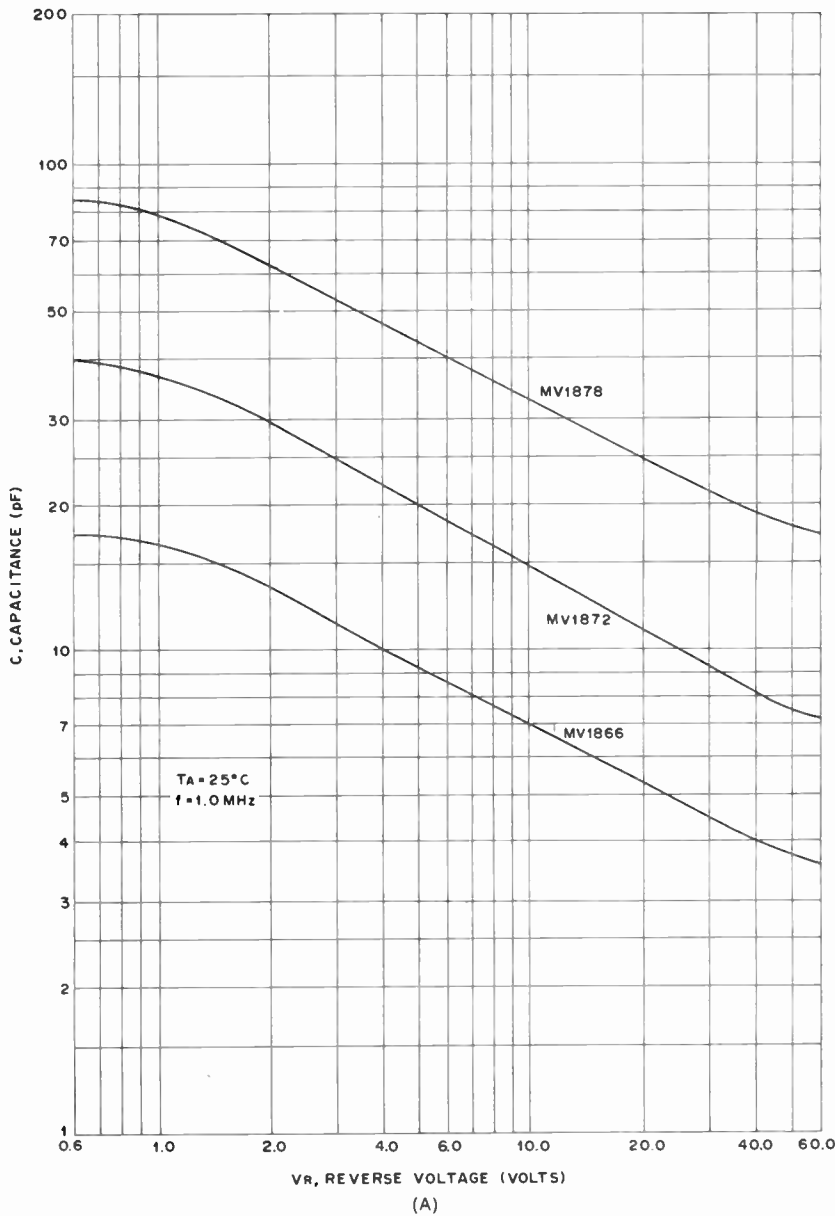


Fig. 27 — Reverse voltage respective to diode capacitance of three Motorola varactor diodes (A). Reverse voltage versus diode Q for the varactors at A are shown at B.

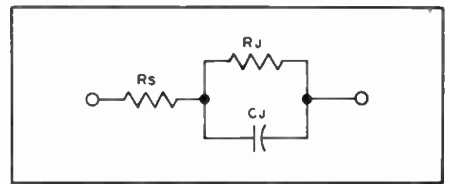


Fig. 28 — Representative circuit of a varactor diode showing case resistance, junction resistance and junction capacitance.

useful power up to 35 GHz.

Amateurs have been using Gunn diodes at 10 GHz, but it is important to realize that these diodes are available for other microwave frequencies. An in-depth treatment of the technology and chemistry of Gunn diodes is provided in the *Gunn Diode Handbook* by Microwave Associates, Incorporated.

Fig. 31 shows a cross-sectional representation of a slice of the material from which Gunn diodes are made. Layer no. 1 is the active region of the device. The thickness of this layer depends on the chosen frequency of operation. For the 10-GHz band it is approximately  $10\ \mu\text{m}$  ( $10^{-6}$  meters) thick. The threshold voltage is roughly 3.3 volts. At 16 GHz the layer would be formed to a thickness of  $8\ \mu\text{m}$ , and the threshold voltage would be about 2.6 volts.

Layer no. 2 is grown epitaxially and is doped to provide low resistivity. This layer is grown on the active region of the semiconductor, but it is not essential to the primary operation of the diode. It is used to ensure good ohmic contact and to prevent metalization from damaging the n-layer of the diode.

The composite wafer of Fig. 31 is metalized on both sides to permit bonding into the diode package. This process of metalization also ensures a low electrical and thermal resistance. The completed chip is bonded to a gold-plated copper pedestal, with layer no. 2 next to the heat sink. A metal ribbon is connected to the back side of the diode to provide for electrical contact.

The curve in Fig. 32 shows the relationship of the diode active-region thickness to the frequency of operation. The curve illustrates an approximation because the actual thickness of the active region depends on the applied bias voltage and the particular circuit used. The input power to the diode must be 20 to 50 times the desired output power. Thus the efficiency from dc to rf is on the order of two to five percent.

The resonant frequency of the diode assembly must be higher than the operating frequency to allow for parasitic C and L components which exist. Fig. 33 shows the equivalent circuit of a packaged Gunn diode. Assuming a diode natural resonant frequency of 17 GHz, the

following approximate values result:  $L_p = 0.25$  nH,  $C_a = 0.15$  pF and  $C_b = 0.15$  pF. Additional components exist within the diode chip. They are represented by  $C_d$  (capacitance) and  $-R_d$  (negative resistance). These quantities, plus the stray resonances in the diode holder and bias leads in the microwave cavity, have a direct bearing on the electrical behavior of the Gunn oscillator. A cross-sectional representation of a packaged Gunn diode is shown at Fig. 34.

Presently, Gunn diodes are useful for generating powers between 0.1 and 1 watt. As the technology advances these power limits will increase. IMPATT (impact-avalanche transit time) diodes are useful as microwave amplifiers after a Gunn diode signal source. IMPATT diodes are also capable of providing power output in the 0.1 to 1-watt class. Fig. 35 shows block diagrams of two Gunn-diode systems. In each example an IMPATT diode is used as an amplifier. Fig. 35A shows a direct fm transmitter which employs a varactor-deviated Gunn-diode oscillator as a signal source. Fm is provided by applying audio to the bias lead of the varactor diode. The latter is coupled to the Gunn-diode cavity. Fig. 35B illustrates a microwave relay system in which a Gunn diode is used as an LO

source. Essentially, the equipment is set up as a heterodyne up-converter transmitter. The upper sideband from the mixer is amplified at microwave frequency by means of an IMPATT diode.

### PIN Diodes

The pin diode is formed by combining heavily doped p+ and n+ end regions. These are separated by a lightly doped region which is generally considered *intrinsic* (the concentration of charge carriers is characteristics of the material itself rather than of the content of impurity materials which are added).

These diodes are useful as high-voltage rectifiers when the center region is made thick, say, 10 to 100  $\mu$ m. The forward voltage drop will be low at relatively high currents.

Pin diodes are used commonly as variable resistors at vhf and above. In such applications they are useful as series elements in the front ends of fm receivers for obtaining agc action. At the higher frequencies pin diodes will not rectify because of the large recovery time of the center layer of material. With zero or reverse bias this layer provides a high resistance. When forward bias is applied the storage and injection carriers lower the resistance of the center region of the

diode. By applying abrupt forward-bias changes the diodes serve well as high speed switches. The device impedance in the ON state is typically 1 ohm. At zero bias (diode shunted by a typical case capacitance of 0.15 pF) the impedance will approach 8000 ohms. A series inductance of roughly one to three nanohenries is introduced by the diode package.

Pin diodes which are built with thin center layers (less than 5  $\mu$ m) exhibit recovery times which are fast enough to make them practical as charge-storage diodes for harmonic generation. Fig. 36 shows the internal layout of a pin diode.

### Light-Emitting Diodes (LEDs)

The primary component in optoelectronics is the LED. This diode contains a p-n junction of crystal material which produces luminescence around the junction when forward bias current is applied. LED junctions are made from gallium arsenide (GaAs), gallium phosphide (GaP), or a combination of both materials (GaAsP). The latter is dependent upon the color and light intensity desired. Today, the available LED colors are red, green and yellow.

Some LEDs are housed in plastic which is affixed to the base header of a transistor package. Other LEDs are contained entirely in plastic packages which have a dome-shaped head at the light-emitting end. Two wires protrude from the opposite end (positive and negative leads) for applying forward bias to the device.

There are countless advantages to the use of LEDs. Notable among them are the low current drain, long life (sometimes 50 years, as predicted), and small size. They are useful as visual indicators in place of incandescent panel lamps. One of their greatest applications is in digital display units, where arrays of tiny LEDs are

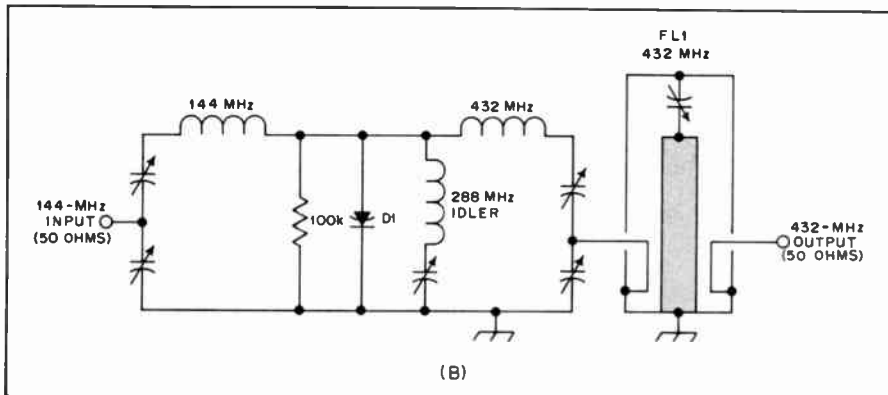


Fig. 29 — Typical circuit for a varactor-diode frequency tripler.

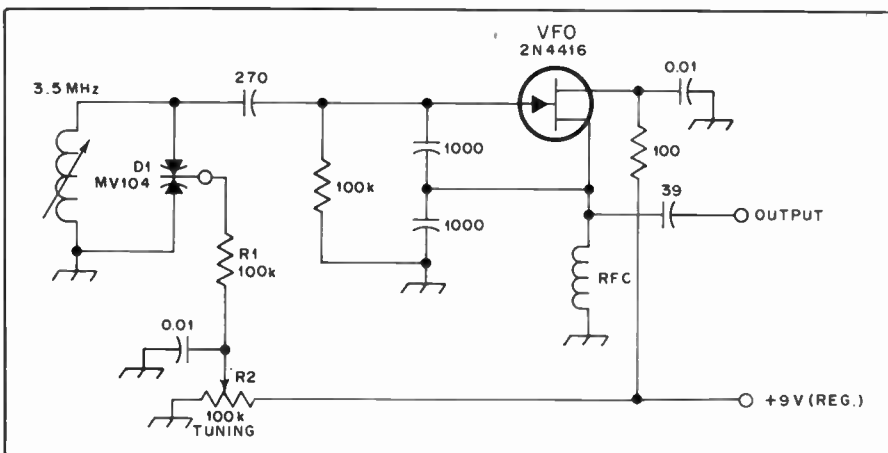


Fig. 30 — Example of a varactor-tuned VFO. D1 contains two varactors, back to back (see text).

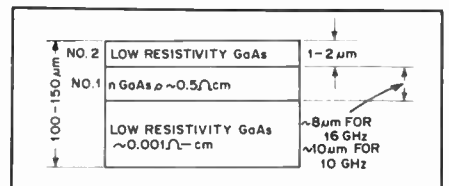


Fig. 31 — Cross-sectional illustration of Gunn diode.

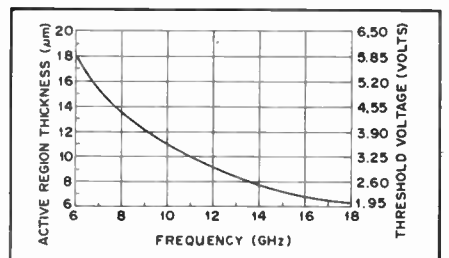


Fig. 32 — Active region thickness versus frequency of a Gunn diode.

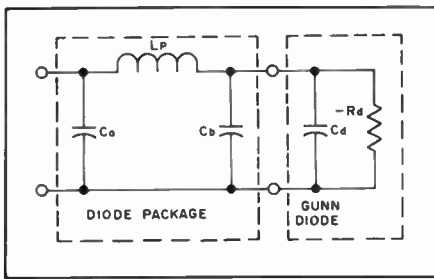


Fig. 33 — Equivalent circuit of a Gunn diode. The parasitic reactances of the diode package are included.

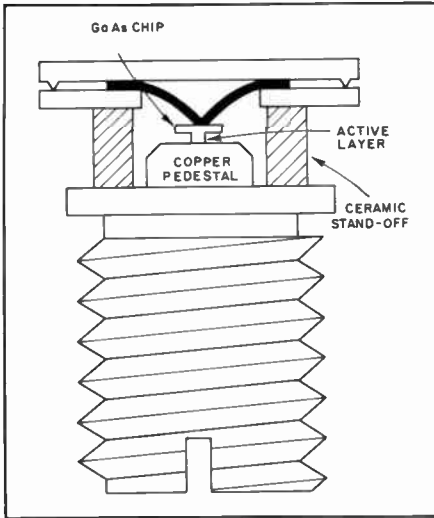


Fig. 34 — Illustration of a packaged Gunn diode as seen in literature from Microwave Associates.

arranged to provide illuminated segments in numeric-display assemblies.

The forward bias current for a typical LED ranges between 10 and 20 mA for maximum brilliance. An applied voltage of 1-1/2 to 2 is also typical. A 1000-ohm resistor in series with a 12 volt source will permit the LED to operate with a forward current of approximately 10 mA (IR drop = 10 V). A maximum current of 10 mA is suggested in the interest of longevity for the device.

LEDs are also useful as reference diodes, however unique the applications may seem. They will regulate dc at approximately 1.5 V.

Perhaps the most concise treatment given to LEDs is that which was authored by Bergh and Dean.<sup>1</sup> Also, see Blakelee.<sup>2</sup>

### Solar-Electric Diodes

Sunlight can be converted directly into electricity by a process known as *photovoltaic conversion*. For this purpose a solar cell is used. It relies on the photoelectric properties of a semiconductor. Practically, the solar cell is a large-area p-n junction diode. The greater the area of the cell, the higher the output current will be. A dc voltage output of approximately 0.5 is obtained from a single cell. Numerous cells can be connected in series to provide 6, 9, 12, 24 or whatever low voltage is required. In a like manner, cells can be connected in parallel to provide higher output current, overall.

<sup>1</sup>Bergh and Dean, "Light-Emitting Diodes," *Proc. IEEE*, Feb., 1972, p. 156.

<sup>2</sup>Blakelee, "By the Light of a Diode," *QST*, May, 1972, p. 30.

The solar diode cell is built so that light can penetrate into the region of the p-n junction, Fig. 37. Most modern solar cells use silicon material. Impurities (doping) are introduced into the silicon material to establish excess positive or negative charges which carry electric currents. Phosphorous is used to produce n-type silicon. Boron is used as the dopant to produce p-type material.

Light is absorbed into the silicon to generate excess holes and electrons (one hole/electron pair for each photon absorbed). When this occurs near the p-n junction, the electric fields in that region will separate the holes from the electrons. This causes the holes to increase in the p-type material. At the same time the electrons will build up in the n-type material. By making direct connection to the p and n regions by means of wires, these excess charges generated by light (and separated by the junction) will flow into an external load to provide power.

Approximately 0.16 A can be secured from each square inch of solar-cell material exposed to bright sunlight. A 3-1/2 inch diameter cell can provide 1.5 A of output current. The efficiency of a solar cell (maximum power delivered to a load versus total solar energy incident on the cell) is typically 11 to 12 percent.

Arrays of solar cells are manufactured for all manner of practical applications. A storage battery is used as a buffer between the solar panel and the load. A p-n junction diode should be used between the solar-array output and the storage battery to prevent the battery from discharging back into the panel during dark periods.

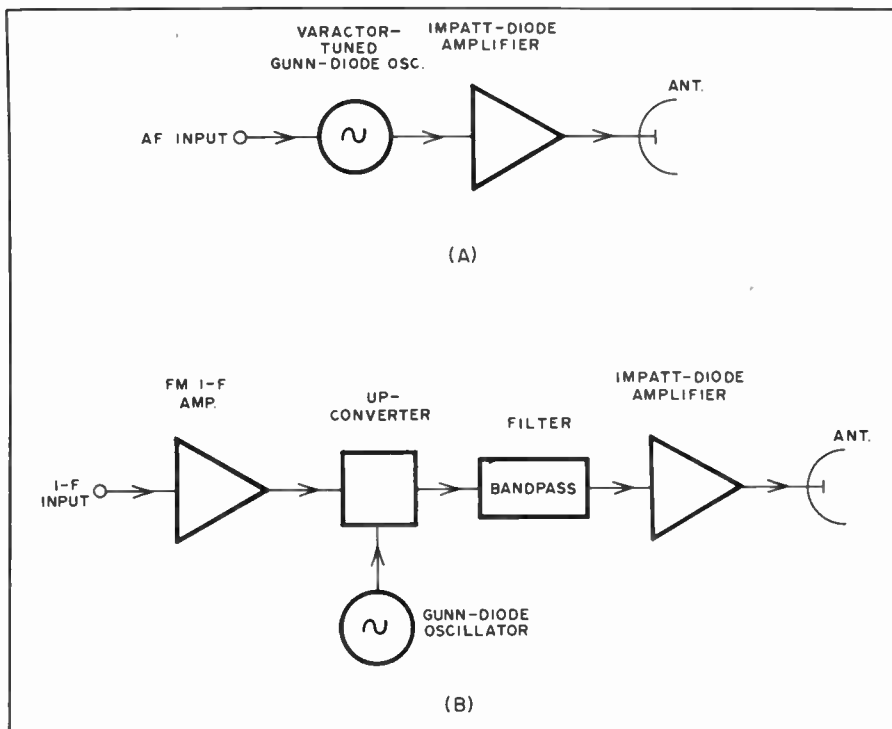


Fig. 35 — Block diagram of a simple Gunn-diode transmitter for fm (A) and an up-converter Gunn-diode transmitter (B).

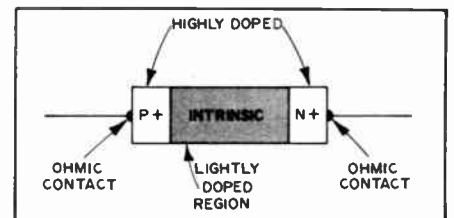


Fig. 36 — Illustration of the internal structure of a PIN diode.

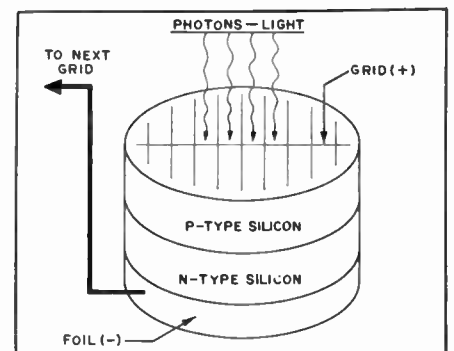


Fig. 37 — A solar-energy diode cell. Electrons flow when light strikes the upper surface. The bottom of the cell is coated with foil to collect current for the load, or for the succeeding cell in series-connected arrays of cells.

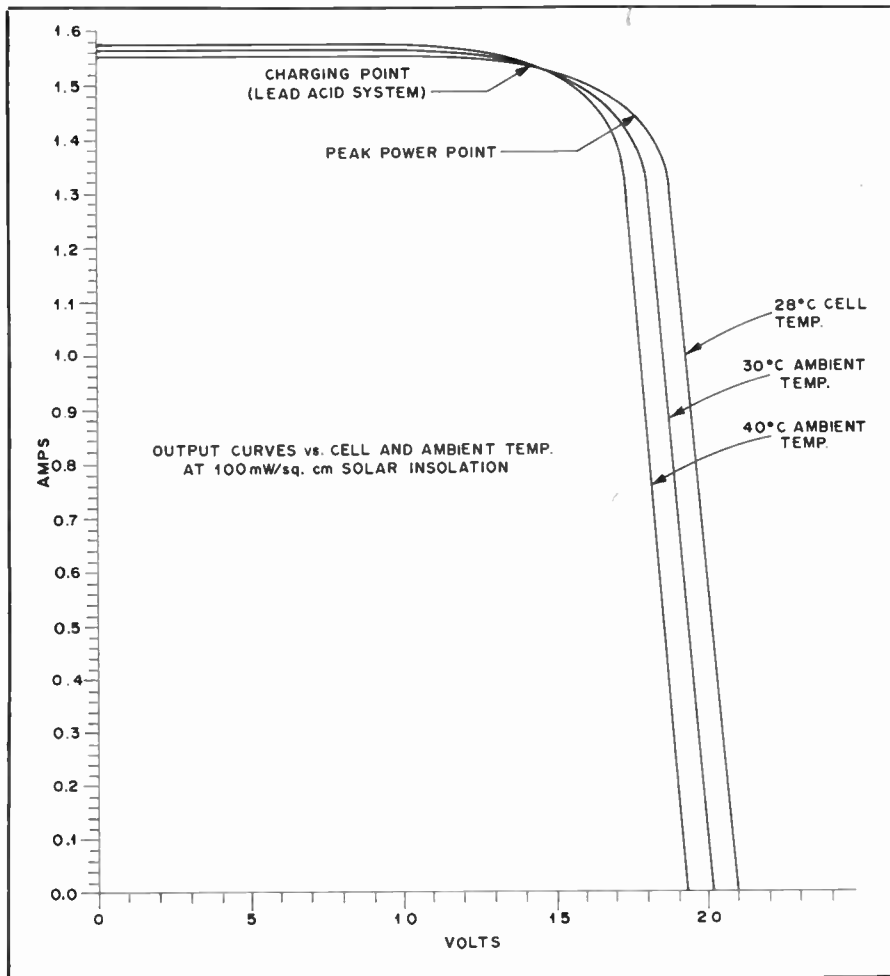


Fig. 38 — Voltage/current/temperature curve for a Solar Power Corp. array which contains 36 solar-electric cells in series. The curves are for a model E12-01369-1.5 solar panel.

An article on the subject of solar cells and their amateur applications was written by DeMaw ("Solar Power for the Radio Amateur," August 1977 *QST*) and should be of interest to those who wish to utilize solar power. *Solar Electric Generator Systems*, an application pamphlet by Solar Power Corp. of N. Billerica, MA 01862, contains valuable information on this subject.

Fig. 38 shows the voltage/current

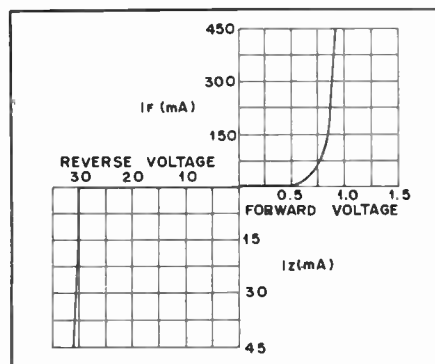


Fig. 39 — Typical characteristics of a Zener diode (30 V).

curves for a Model E12-01369-1.5 solar array manufactured by Solar Power Corp. It can be seen that temperature has an effect on the array performance.

#### Zener Diodes

Zener diodes have, for the most part, replaced the gaseous regulator tube. They have been proved more reliable than tube types of voltage regulators, are less expensive and far smaller in size.

These diodes fall into two primary classifications: Voltage regulators and voltage-reference diodes. When they are used in power supplies as regulators, they provide a nearly constant dc output voltage even though there may be large changes in load resistance or input voltage. As a reference element the Zener diode utilizes the voltage drop across its junction when a specified current passes through it in the reverse-breakdown direction (sometimes called the *Zener direction*). This "Zener voltage" is the value established as a reference. Therefore, if a 6.8-volt Zener diode was set up in the foregoing manner, the resultant reference voltage would be 6.8.

At the present time it is possible to

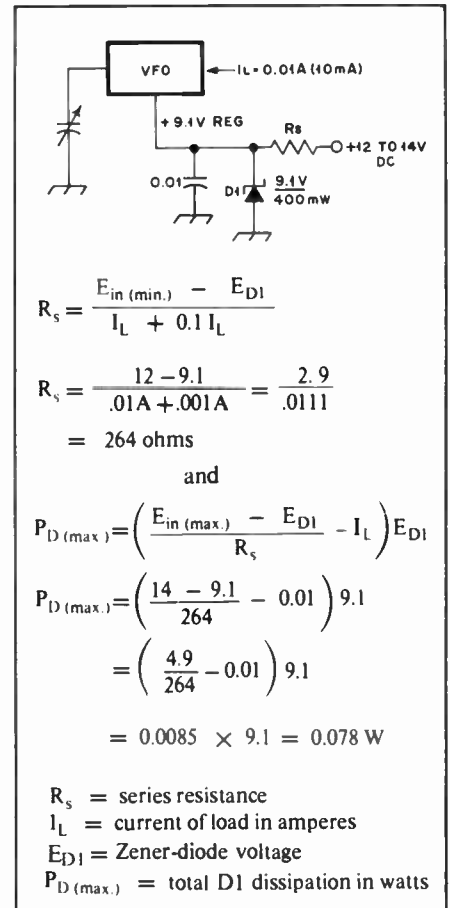


Fig. 40 — Example of how a shunt type of Zener diode regulator is used. The equations show how to calculate the value of the series resistor and the diode power dissipation. In this example a 400-mW Zener diode will suffice (D1).

purchase Zener diodes which are rated for various voltages between 2.4 and 200. The power ratings range from 1/4 to 50 watts, respectively. Fig. 39 the characteristics of a Zener diode designed for 30-volt operation.

Fig. 40 shows how to calculate the series resistance needed in a simple shunt regulator which employs a Zener diode. An equation is included for determining the wattage rating of the series resistor. Additional data on this subject is given in chapter 7 of *Solid State Design for the Radio Amateur*.

Some practical applications for Zener diodes are illustrated in Fig. 41. In addition to the shunt applications given in the diagram, Zener diodes can be used as series elements when it is desired to provide a gate which conducts at a given voltage. These diodes can be used in ac as well as dc circuits. When they are used in an ac type of application they will conduct at the peak voltage value or below, depending upon the voltage swing and the voltage rating of the Zener diode. For this reason they are useful as audio and rf clippers. In rf work the reactance of the diode may be the controlling factor above



approximately 10 MHz with respect to the performance of the rf circuit and the diode.

Most Zener diodes which are rated higher than 1 watt in dissipation are contained in stud-mount packages. They should be affixed to a suitable heat sink to prevent damage from excessive junction temperatures. The mounting techniques are the same as for power rectifiers and high-wattage transistors.

### Transistors

The word "transistor" was chosen to describe the function of a three-terminal p-n junction device which is able to amplify signal energy (current). The inherent characteristic is one of "transferring current across a resistor." The transistor was invented by Shockley, Bardeen and Brattain at Bell Labs in 1947 and has become the standard amplifying device in electronics equipment. In rf and audio applications it is practical to obtain output power in excess of 1000 watts by using several amplifier blocks and hybrid power combiners. The primary limitation at the higher power levels is essentially a practical or economic one: Low voltage, high-current power supplies are required, and the cost can exceed that of a high-voltage, moderate-current supply of the variety which would be employed with a vacuum-tube amplifier of comparable power. The primary advantages obtained through the use of solid-state power amplifiers are compactness and reliability.

In small-signal applications the transistor outweighs the vacuum-tube in performance. The former is more efficient, operates cooler, has much longer life, is considerably smaller in size, and is less expensive. A naive designer might insist that "tubes are better," but the transistor ranks no. 1 in the industry at this time.

There remains in isolated instances a belief that transistors are hard to tame, noisier than tubes and that they are subject to damage at the flick of a switch. None of this is true. A transistorized circuit which is designed and operated correctly is almost always capable of exceeding an equivalent vacuum-tube circuit in all respects. An understanding of how transistors function will help to prevent poor circuit performance. The fundamentals outlined in this chapter are provided for the amateur designer so that the common pitfalls can be avoided.

Fig. 42 shows a "sandwich" made from two layers of p-type semiconductor material with a thin layer of n-type between. There are in effect two pn junction diodes back-to-back. If a positive bias is applied to the p-type material at the left, current will flow through the left-hand junction, the holes moving to the right and the electrons from the n-type material moving to the left. Some of the holes moving into the n-type material will combine with the electrons there and be

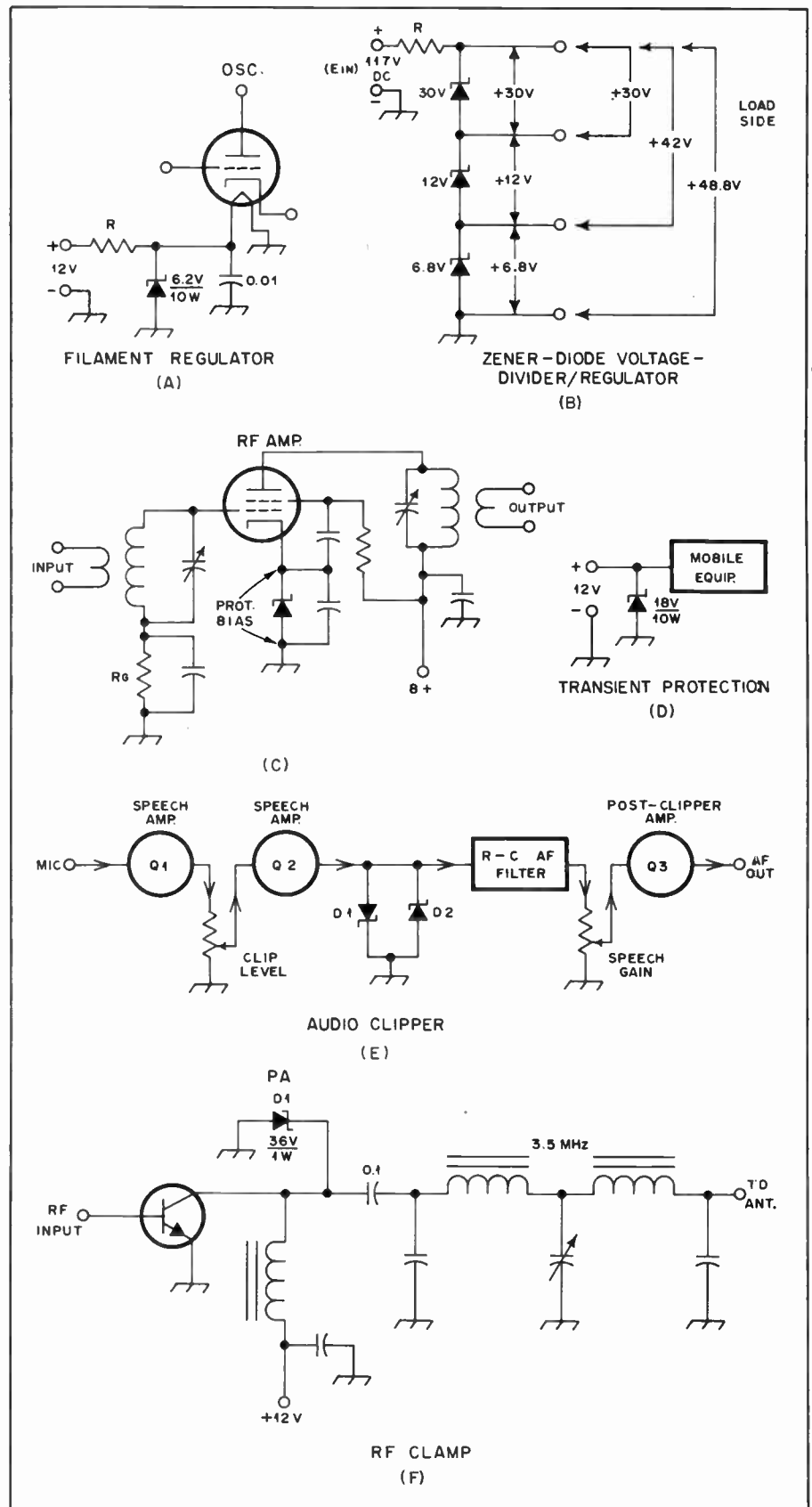


Fig. 41 — Practical examples of Zener diode applications. The circuit at A is useful for stabilizing the filament voltage of oscillators. Zener diodes can be used in series to obtain various levels of regulated voltage (B). Fixed-value bias for transmitter stages can be obtained by inserting a Zener diode in the cathode return (C). At D an 18-volt Zener diode prevents voltage spikes from harming a mobile transceiver. A Zener-diode speech clipper is shown at E and an rf clamp is seen at F. D1 in the latter circuit will clamp at 36 volts to protect the PA transistor from dc voltage spikes and extreme sine-wave excursions at rf. This circuit is useful in protecting output stages during no-load or short-circuit conditions.

neutralized, but some of them also will travel to the region of the right-hand junction.

If the pn combination at the right is biased negatively, as shown, there would normally be no current flow in this circuit. However, there are now additional holes available at the junction to travel to point B and electrons can travel toward point A, so a current can flow even though this section of the sandwich is biased to prevent conduction. Most of the current is between A and B and does not flow out through the common connection to the n-type material in the sandwich.

A semiconductor combination of this type is called a *transistor*, and the three sections are known as the *emitter*, *base* and *collector*, respectively. The amplitude of the collector current depends principally upon the amplitude of the emitter current; that is, the collector current is controlled by the emitter current.

Between each p-n junction exists an area known as the *depletion*, or *transition region*. It is similar in characteristics to a dielectric layer, and its width varies in accordance with the operating voltage. The semiconductor materials either side of the

depletion region constitute the plates of a capacitor. The capacitance from base to emitter is shown as  $C_{be}$  (Fig. 42), and the collector-base capacitance is represented as  $C_{bc}$ . Changes in signal and operating voltages cause a nonlinear change in these junction capacitances, which must be taken into account when designing some circuits. A base-emitter resistance,  $rb'$ , also exists. The junction capacitance, in combination with  $rb'$ , determines the useful upper frequency limit ( $f_T$  or  $fa$ ) of a transistor by establishing an RC time constant.

### Power Amplification

Because the collector is biased in the back direction the collector-to-base resistance is high. On the other hand, the emitter and collector currents are substantially equal, so the power in the collector circuit is larger than the power in the emitter circuit ( $P = I^2R$ , so the powers are proportional to the respective resistances, if the currents are the same). In practical transistors emitter resistance is of the order of a few hundred ohms while the collector resistance is hundreds or thousands of times higher, so power gains of 20 to 40 dB or even more are possible.

### Types

The transistor may be one of the types shown in Fig. 43. The assembly of p- and n-type materials may be reversed, so that pnp and npn transistors are both possible.

The first two letters of the npn and pnp designations indicate the respective polarities of the voltages applied to the emitter and collector in normal operation. In a pnp transistor, for example, the emitter is made positive with respect to both the collector and the base, and the collector is made negative with respect to both the emitter and the base.

Manufacturers are constantly working to improve the performance of their transistors — greater reliability, higher power and frequency ratings, and improved uniformity of characteristics for any given type number. One such development provided the *overlay transistor*, whose emitter structure is made up of several emitters which are joined together at a common case terminal. This process lowers the base-emitter resistance,  $rb'$ , and improves the transistor input time constant. The latter is determined by  $rb'$  and the junction capacitance of the device. The overlay transistor is extremely useful in vhf and uhf applications. It is capable of high-power operation well above 1000 MHz. These transistors are useful as frequency doublers and triplers, and are able to provide an actual power gain in the process.

Another multi-emitter transistor has been developed for use from hf through uhf. It should be of interest to the radio amateur. It is called a *balanced-emitter transistor* (BET), or "ballasted" transistor. The transistor chip contains several

triode semiconductors whose bases and collectors are connected in parallel. The various emitters, however, have built-in emitter resistors (typically about 1 ohm) which provide a current-limiting safety factor during overload periods, or under conditions of significant mismatch. Since the emitters are brought out to a single case terminal the resistances are effectively in parallel, thus reducing the combined emitter resistances to a fraction of an ohm. (If a significant amount of resistance were allowed to exist it would cause degeneration in the stage and would lower the gain of the circuit.)

Most modern transistors are of the junction variety. Various names have been given to the several types, some of which are junction alloy, mesa, and planar. Though their characteristics may differ slightly, they are basically of the same family and simply represent different physical properties and manufacturing techniques.

### Transistor Characteristics

An important characteristic of a transistor is its *beta* ( $\beta$ ), or *current-amplification factor*, which is sometimes expressed as  $h_{FE}$  (static forward-current transfer ratio) or  $h_{fe}$  (small-signal forward-current transfer ratio). Both symbols relate to the grounded-emitter configuration. Beta is the ratio of the collector current to the base current

$$\beta = \frac{I_c}{I_b}$$

Thus, if a base current of 1 mA causes the collector current to rise to 100 mA the beta is 100. Typical betas for junction transistors range from as low as 10 to as high as several hundred.

A transistor's *alpha* ( $\alpha$ ) is the ratio of the emitter and collector currents. Symbols  $h_{FB}$  (static forward-current transfer ratio) and  $h_{fb}$  (small-signal forward-current transfer ratio), common-base hookup, are frequently used in connection with gain. The smaller the base current, the closer the collector current comes to being equal to that of the emitter, and the closer alpha comes to being 1. Alpha for a junction transistor is usually between 0.92 and 0.98.

Transistors have frequency characteristics which are of importance to circuit designers. Symbol  $f_T$  is the *gain bandwidth product* (common-emitter) of the transistor. This is the frequency at which the gain becomes unity, or 1. The expression "alpha cutoff" is frequently used to express the useful upper-frequency limit of a transistor, and this relates to the common-base hookup. Alpha cutoff is the point at which the gain is 0.707 its value at 1000 Hz.

Another factor which limits the upper frequency capability of a transistor is its *transit time*. This is the period of time required for the current to flow from

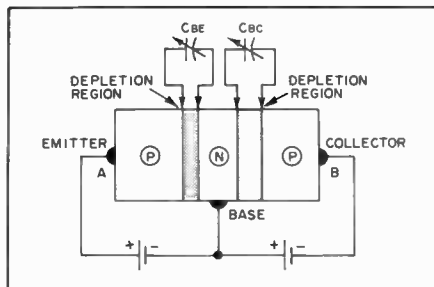


Fig. 42 — Illustration of a junction pnp transistor. Capacitances  $C_{be}$  and  $C_{bc}$  vary with changes in operating and signal voltage (see text).

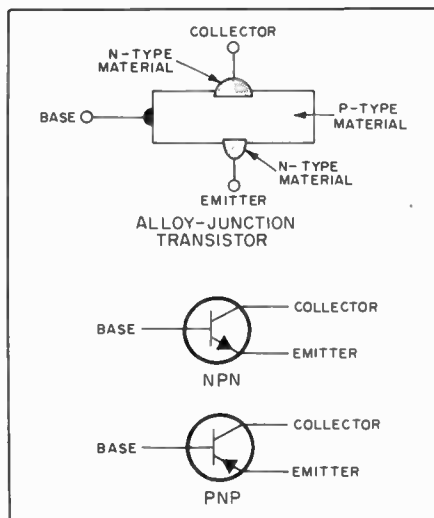


Fig. 43 — Pictorial and schematic representations of junction transistors. By way of analogy the base, collector and emitter can be compared to the grid, plate and cathode of a triode tube, respectively.

emitter to collector, through the semiconductor base material. The thicker the base material, the greater the transit time. Hence, the thicker the base material the more likelihood there will be of phase shift of the signal passing through it. At frequencies near and above  $f_T$  or alpha cutoff, partial or complete phase shift can occur. This will give rise to *positive feedback* because the internal capacitance,  $C_{be}$ , feeds part of the in-phase collector signal back to the base. The positive feedback can cause instability and oscillation, and in most cases will interlock the input

and output tuned circuits of an rf amplifier so that it is almost impossible to tune them properly. This form of feedback can be corrected by using what is termed "unilateralization." Conventional positive feedback can be nullified by using neutralization, as is done with vacuum-tube amplifiers.

### Characteristic Curves

The operating principles of transistors can be shown by a series of characteristic curves. One such set of curves is shown in Fig. 44. It shows the collector current vs. collector voltage for a number of fixed values of emitter current. Practically, the collector current depends almost entirely on the emitter current and is independent of the collector voltage. The separation between curves representing equal steps of emitter current is quite uniform, indicating that almost distortionless output can be obtained over the useful operating range of the transistor.

Another type of curve is shown in Fig. 45, together with the circuit used for obtaining it. This also shows collector current vs. collector voltage, but for a number of different values of base current. In this case the emitter element is used as the common point in the circuit. The collector current is not independent of collector voltage with this type of connection, indicating that the output resistance of the device is fairly low. The

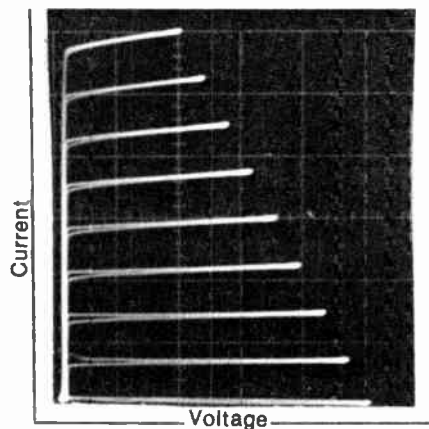


Fig. 46— Curve-tracer display of a small-signal transistor characteristics.

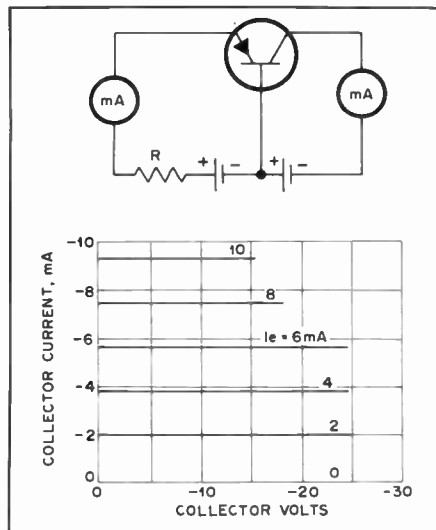


Fig. 44 — Typical collector-current versus collector-voltage characteristics of a junction transistor for various emitter-current values. Because the emitter resistance is low, a current-limiting resistor (R) is placed in series with the source current. The emitter current can be set at a desired value by adjustment of this resistance.

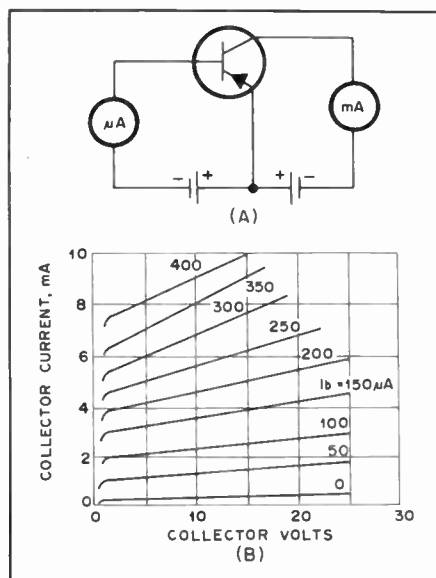


Fig. 45 — Collector current versus collector voltage for various values of base current in a junction transistor. The illustration at A shows how the measurements are made. At B is a family of curves.

base current also is quite low, which means that the resistance of the base-emitter circuit is moderately high with this method of connection. This may be contrasted with the high values of emitter current shown in Fig. 44. An actual oscillograph of a characteristic family of curves for a small-signal transistor is shown in Fig. 46. It was obtained by means of a curve tracer.

### Transistor Amplifiers

Amplifier circuits used with transistors

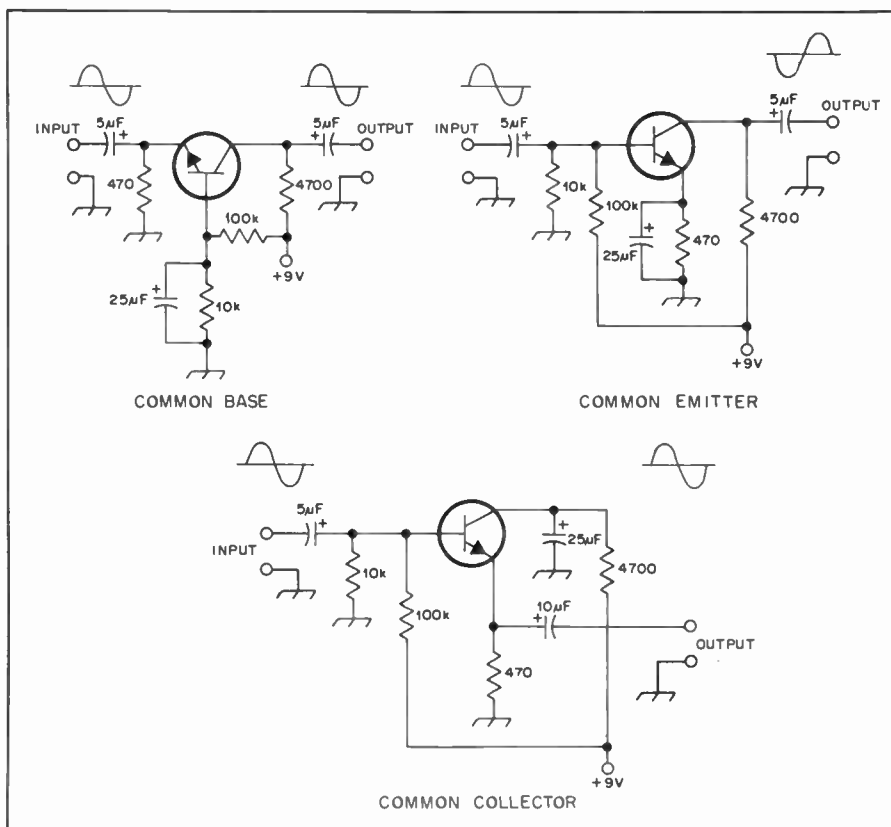


Fig. 47 — Basic transistor amplifiers. Observe the input and output phase relationships for the various configurations.



fall into one of three types, known as the *common-base*, *common-emitter*, and *common-collector* circuits. These are shown in Fig. 47 in elementary form. The three circuits correspond approximately to the grounded-grid, grounded-cathode and cathode-follower circuits, respectively, used with vacuum tubes.

The important transistor *parameters* in these circuits are the *short-circuit current transfer ratio*, the *cut-off frequency*, and the *input and output impedances*. The short-circuit current transfer ratio is the ratio of a small change in output current to the change in input current that causes it, the output circuit being short-circuited. The cutoff frequency was discussed earlier in this chapter. The input and output impedances are, respectively, the impedance which a signal source working into the transistor would see, and the internal output impedance of the transistor (corresponding to the plate resistance of a vacuum tube, for example).

### Common-Base Circuit

The input circuit of a common-base amplifier must be designed for low impedance, since the emitter-to-base resistance is of the order of  $25/I_e$  ohms, where  $I_e$  is the emitter current in milliamperes. The optimum output load impedance,  $R_L$ , may range from a few thousand ohms to 100,000, depending upon the requirements.

In this circuit the phase of the output (collector) current is the same as that of the input (emitter) current. The parts of these currents that flow through the base resistance are likewise in phase, so the circuit tends to be regenerative and will oscillate if the current amplification factor is greater than one.

### Common-Emitter Circuit

The common-emitter circuit shown in Fig. 47 corresponds to the ordinary grounded-cathode vacuum-tube amplifier. As indicated by the curves of Fig. 45, the base current is small and the input impedance is therefore fairly high — several thousand ohms in the average case. The collector resistance is some tens of thousands of ohms, depending on the signal source impedance. The common-emitter circuit has a lower cutoff frequency than does the common-base circuit, but it gives the highest power gain of the three configurations.

In this circuit the phase of the output (collector) current is opposite to that of the input (base) current so such feedback as occurs through the small emitter resistance is negative and the amplifier is stable.

### Common-Collector Circuit

Like the vacuum-tube cathode follower, the common-collector transistor amplifier has high input impedance and low output impedance. The latter is approximately

equal to the impedance of the signal input source multiplied by  $(1 - \alpha)$ . The input resistance depends on the load resistance, being approximately equal to the load resistance divided by  $(1 - \alpha)$ . The fact that input resistance is directly related to the load resistance is a disadvantage of this type of amplifier if the load is one whose resistance or impedance varies with frequency.

The current transfer ratio with this circuit is

$$\frac{1}{1 - \alpha}$$

and the cut-off frequency is the same as in the grounded-emitter circuit. The output and input currents are in phase.

### Bipolar Transistor Dissipation

Apart from the characteristics mentioned earlier, it is necessary to consider the matters of collector dissipation, collector voltage and current, and emitter current. Variations in these specifications are denoted by specific parameter symbols which appear later in the chapter. The maximum dissipation ratings of transistors, as provided on the manufacturer's data sheets, tend to confuse some amateurs. An acceptable rule of thumb is to select a transistor which has a maximum dissipation rating of approximately twice the dc input power of the circuit stage. That is, if a 5-watt dc input is contemplated, choose a transistor with a 10-watt or greater rating. When power levels in excess of a few hundred mW are necessary there is a need for heat sinking. A sink is a metal device which helps to keep the transistor cool by virtue of heat transfer from the transistor case to the sink. At power levels below 5 watts it is common practice to employ clip-on heat sinks of the crown variety. For powers greater than 5 watts it is necessary to use large-area heat sinks which are fashioned from extruded aluminum. These sinks have cooling fins on one or more of their surfaces to hasten the cooling process. Some high-power, solid-state amplifiers employ cooling fans from which the air stream is directed on the metallic heat sink. Regardless of the power level or type of heat sink used, silicone heat-transfer compound should always be used between the mating surfaces of the transistor and the heat sink. Another rule of thumb is offered: If the heat-sink-equipped transistor is too warm to touch with comfort, the heat sink is not large enough in area.

Excessive junction heat will destroy a transistor. Prior to destruction the device may go into *thermal runaway*. During this condition the transistor becomes hotter and its internal resistance lowers. This causes an increase in emitter/collector and emitter/base current. This increased current elevates the dissipation and further lowers the internal resistance.

These effects are cumulative: Eventually the transistor will be destroyed. A heat sink of proper size will prevent this type of problem. Excessive junction temperature will eventually cause the transistor to become open. Checks with an ohmmeter will indicate this condition after a failure.

Excess collector voltage will also cause immediate device failure. The indication of this type of failure, as noted by means of an ohmmeter, is a shorted junction.

### Bipolar Transistor Applications

Silicon transistors are the most common types in use today, although a few germanium varieties are built for specific applications. Collector voltages as great as 1500 can be accommodated by some of the high-power silicon transistors available now. Most small-signal transistors will safely handle collector voltages of 25 or greater. Generally speaking, transistors in the small-signal class carry dissipation ratings of 500 mW or less. Power transistors are normally classed as 500-mW and higher devices. The practical applications for all of these semiconductors range from dc to the microwave spectrum.

### Bipolar Transistor Switches

Our present-day technology includes the use of solid-state switches as practical alternatives to mechanical switches. When a bipolar transistor is used in a switching application it is either in an *on* or *off* state. In the on state a forward bias is applied to the transistor, sufficient in level to saturate the device. The common-emitter format is used for nearly all transistor switches. Switching action is characterized by large-signal nonlinear operation of the device. Fig. 48 shows typical output characteristics for an npn switching transistor in the common-emitter mode. There are three regions of operation — *cutoff*, *active* and *saturation*. In the cutoff region the emitter-base and collector-base junctions are reverse biased. At this period the collector current is quite small

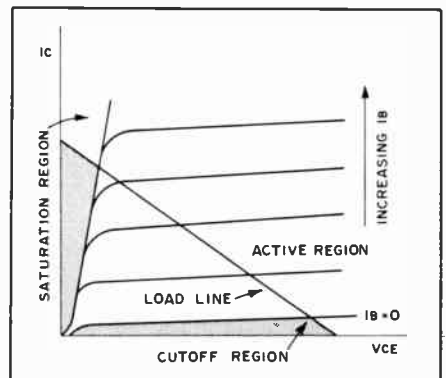


Fig. 48 — Typical characteristic for the collector of an npn transistor which shows the three primary regions involved during switching.



and is comparable to the leakage current,  $I_{c0}$ ,  $I_{ev}$  or  $I_{cb0}$ .

Fig. 49 illustrates the minority-carrier concentration relative to an npn transistor. During cutoff the concentration is zero at both junctions because they are reverse biased (curve no. 1).

The emitter-base junction is forward biased in the active region. At this time the collector-base junction is reverse biased. Fig. 48 shows a load line along which switching from the cutoff to the active region is done. The transit time (speed) through the active region is dependent upon the transistor frequency-response characteristics. Thus, the higher the frequency rating of the device, the faster the switching time. Curve no. 2 in Fig. 49 depicts the minority-carrier concentration of the active region.

In the saturation region the emitter-base and collector-base junctions are forward biased. During this period the forward voltage drop across the emitter-base junction  $V_{BE(sat)}$  is larger than it is across the collector-base junction. This results in a collector-emitter voltage termed  $V_{CE(sat)}$ . Series resistances present in the emitter and collector legs of the circuit contribute to the determination of  $V_{CE(sat)}$ . Since the collector in this state is forward biased, additional carriers are injected into the base. Some also reach the collector. Curve no. 3 of Fig. 49 shows this minority-carrier concentration. Fig. 50 contains the circuit for a basic saturated-transistor switch.

It is extremely important to make

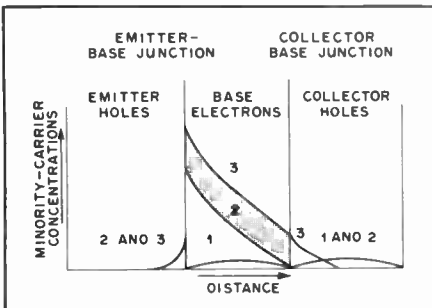


Fig. 49 — Illustration of the minority-carrier concentrations in an npn transistor. No. 1 shows the cutoff region. No. 2 is the active region at the threshold of the saturation region. No. 3 is in the saturation region.

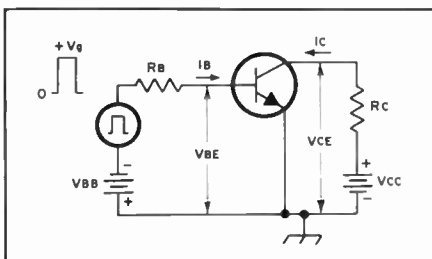


Fig. 50 — Circuit for a transistor switching circuit (saturated).

certain that none of the transistor voltage ratings are exceeded during the "off" period: The minimum emitter-base breakdown voltage,  $V_{(BR)EBO}$ , must not exceed  $V_{BE(off)}$ . Also, the minimum collector-base breakdown voltage,  $V_{(BR)CBO}$ , should be no greater than  $V_{CC} + V_{BE(off)}$ . Finally, the minimum collector-to-emitter breakdown voltage,  $V_{(BR)CERL}$ , must be greater than  $V_{CC}$ . As is true in any transistor application, the junction temperature must be maintained at a safe value by whatever means necessary.

A transistor switch can be turned on by means of a pulse (Fig. 50) or by application of a dc forward bias. Typical circuits for the latter are given in Fig. 51. The circuit at A illustrates how a pnp transistor can be used as a low-power switch to turn oscillator Q2 on and off. In the "on" state R1 is grounded. This places the bipolar switch, Q1, in a saturated mode, thereby permitting current to flow to Q2. A transistor switch of the type shown at A of Fig. 51 can be used to control more than one circuit stage simultaneously. The primary criterion is that the switching transistor be capable of passing the combined currents of the various stages under control. The method seen at A is often used in keying a transmitter.

An npn transistor switch is shown in Fig. 51B. If desired, it can be "slaved" to the circuit of Fig. 51A by attaching R1 of circuit B to the collector of Q1 in circuit A. Because an npn device is used at B, a positive forward bias must be applied to the base via R1 to make the transistor saturate. When in that state, current flows through the relay (K1A) field coil to actuate the contacts at K1B. D1 and D2 may not be necessary. This will depend on the sensitivity of the relay and the leakage current of Q1 in the off state. If there is considerable leakage, K1 may not release when forward bias is removed from Q1. D1 and D2 will elevate the emitter to approximately 1.4 volts, thereby providing sufficient reverse bias to cut off Q1 in the off state. It can be seen from the illustrations in Fig. 51 that either npn or pnp transistors can be used as electronic switches.

### Transistor Audio Amplifiers

Bipolar transistors are suitable for numerous audio-amplifier applications from low-level to high power. It is common practice to use all npn or all pnp devices, regardless of the polarity of the power supply. In other circuits a mixture of the two types may be found, especially when direct-coupled or complementary-symmetry stages are included. Fig. 52 shows how pnp or npn stages can be used with power supplies which have positive or negative grounds. The essential dif-

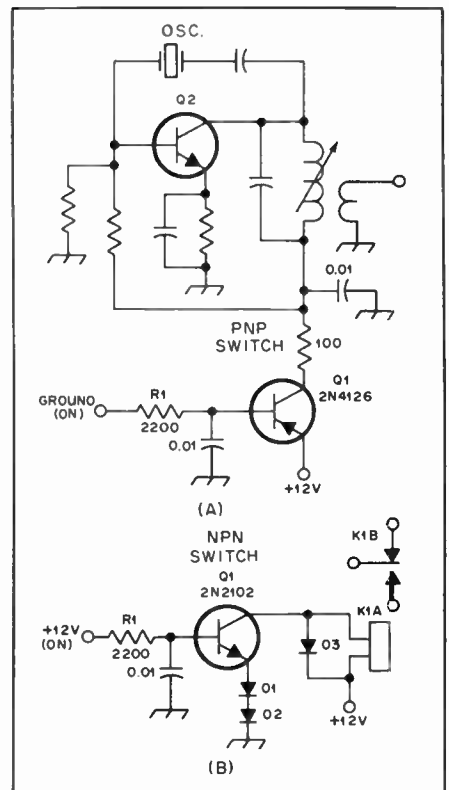


Fig. 51. — Examples of practical switching circuits. A pnp switch is used to key an oscillator at A. When R1 is grounded the switching transistor is forward biased to saturation, thereby permitting current to flow from the dc supply line to Q2. The circuit at B shows Q1 as a relay-driver npn switch. When +12 volts are applied to the base of Q1 it is forward biased to saturation, permitting current to flow through the field coil of K1A. D1 and D2 are included to reduce the static collector current of K1A, which in some instances could cause K1A to remain closed after forward bias was removed from Q1. D3 serves as a spike suppressor when the field of K1A collapses.

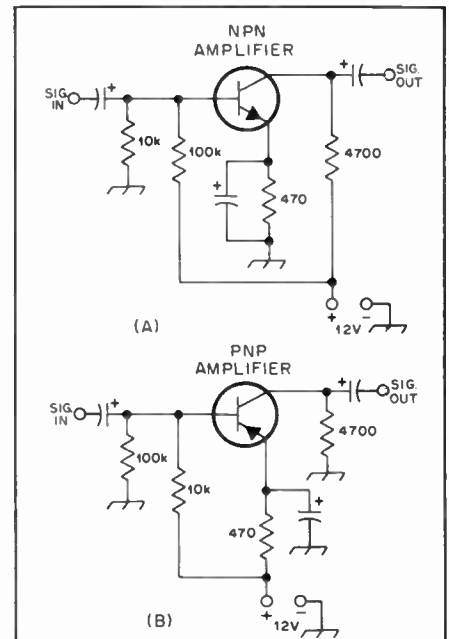


Fig. 52 — Examples of npn and pnp amplifiers operating from a power supply with a negative ground.

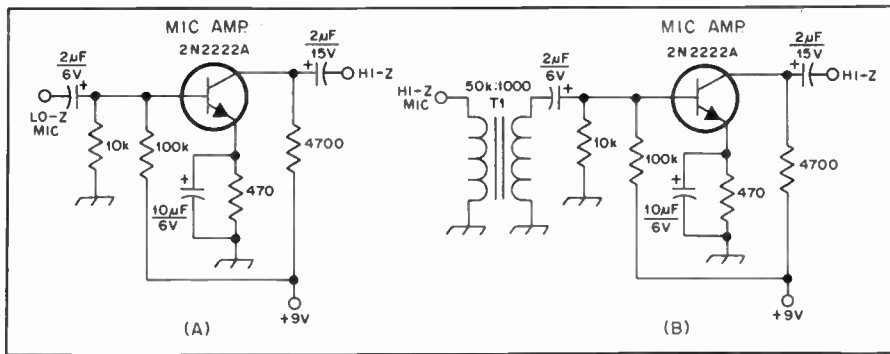


Fig. 53 — RC and transformer-coupled audio amplifiers suitable for high- and low-impedance microphones.

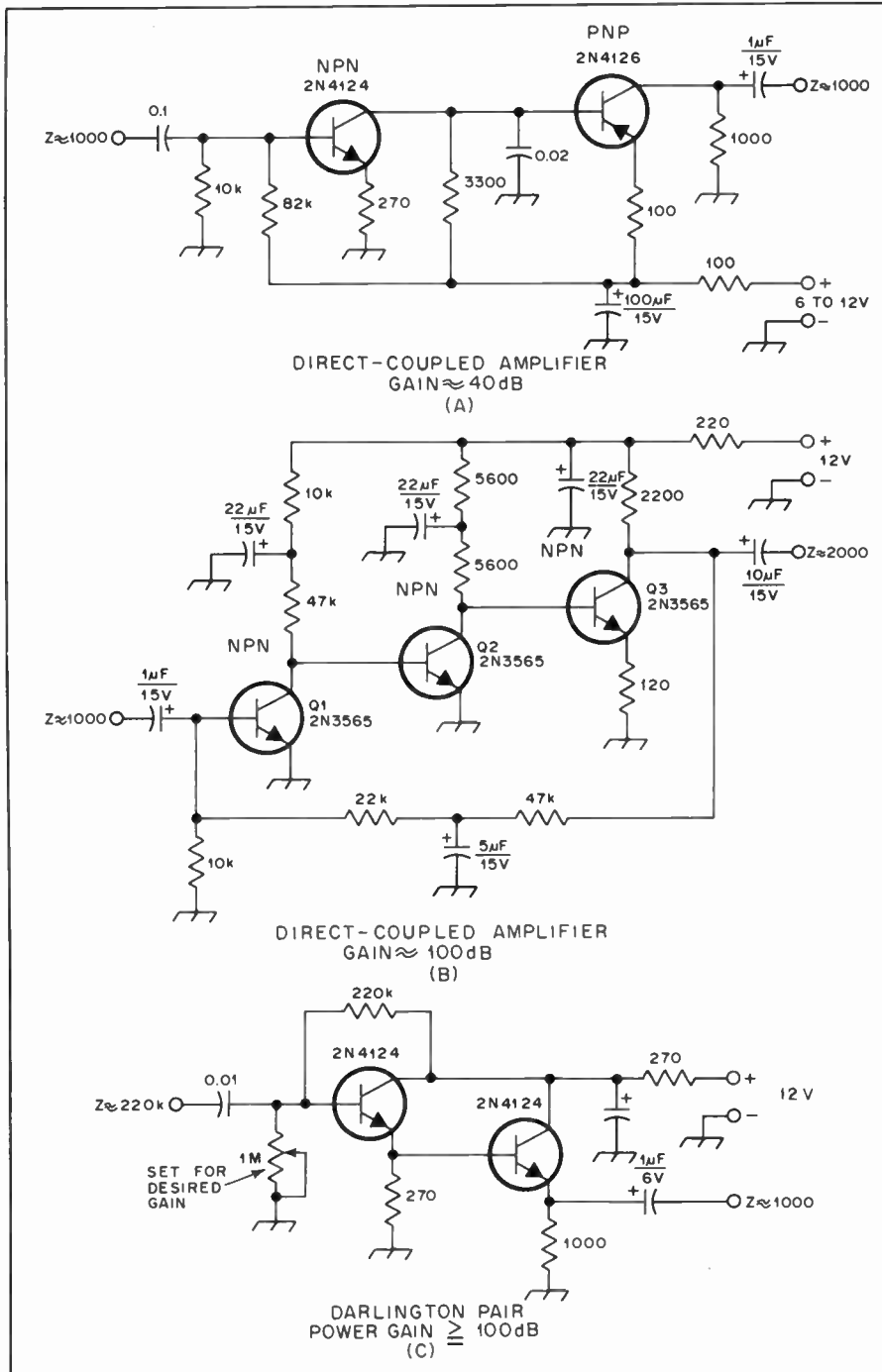


Fig. 54 — Practical examples of direct-coupled audio amplifiers.

ference in the circuits concerns returning various elements to the negative or positive sides of the power supply. The illustrations show that all one needs to do to use either type of device with the same power supply is to interchange the resistor connections. The same principle applies when using npn or pnp transistors with a power supply which has a positive ground. Knowledge of how this is done enables the designer to mix npn and pnp devices in a single circuit. This basic technique is applicable to any type of transistor circuit — rf, audio or dc.

Some basic low-level audio amplifiers are shown in Fig. 53. These stages operate in the Class A mode. The input impedance of circuits is low — typically between 500 and 1500 ohms. For the most part the output impedance is established by the value of the collector load resistor. A matching transformer can be used at the input of these stages (Fig. 53B) when it is necessary to use, for example, a high-impedance microphone with one of them. T1 serves as a step-down transformer.

Some direct-coupled audio amplifiers are shown in Fig. 54. The circuit at A combines pnp and npn devices to provide a compatible interface between them. Three npn stages are in cascade at B to provide high gain. This circuit is excellent for use in direct-conversion receivers, owing to the need for very high gain after the detector. At C is a Darlington pair — so named after the person who developed the configuration. The principle advantages of this circuit are high gain, high input impedance, and low output impedance.

### Transistor RF Amplifiers

In most respects small-signal rf amplifiers are similar in performance to those used in audio applications. However, to effect maximum stable amplification some important design measures are necessary. Furthermore, the matter of proper impedance matching becomes more important than it is in simple audio amplifiers. Other considerations are noise figure, purity of the amplified signal and dynamic range.

Although bipolar transistors can be used as rf amplifiers for receiver front ends, they are not found there in most of the high-performance receivers: Field-effect transistors are more often the designer's choice because of their high input impedance and good dynamic-range traits. A correctly designed bipolar rf input stage can exhibit good dynamic range, however. It is necessary to operate a fairly husky low-noise transistor in Class A, using a relatively high standing collector current — 50 to 100 mA, typically.

Some rf and i-f amplifier circuits which employ bipolar transistors are shown in the examples of Fig. 55. When used with the appropriate L and C networks they

are suitable for either application. At A in Fig. 55 the transistor base is tapped near the cold end of the input tuned circuit to provide an impedance match. The collector is tapped down on the output tuned circuit to provide a proper match. If it is desired, the base and collector taps can be moved even farther down on the tuned circuits. This will result in a deliberate mismatch. The technique is sometimes used to aid stability and/or lower the stage gain. The circuit at B is operated in the common-base mode. Taps are shown on the input and output coils for impedance-matching purposes.

Broadband amplifiers with heavy negative feedback are useful as small-signal rf and i-f amplifiers. An example is shown as C in Fig. 55. Not only is negative feedback applied (collector to base), but degenerative feedback is obtained by virtue of the unbypassed 10-ohm emitter resistor. The use of feedback ensures an unconditionally stable stage. As the operating frequency is decreased the negative feedback increases because the feedback-network reactance becomes lower. This is important if reasonably constant gain is desired over a wide range of frequencies, say, from 1.8 to 30 MHz. This form of gain compensation is necessary because as the operating frequency of a given transistor is decreased, the gain increases. Typically, the gain will increase on the order of 6 dB per octave. Therefore, the probability of instability (self-oscillations) becomes a major consideration at low frequencies in an uncompensated rf amplifier. The circuit of Fig. 55C operates stably and has a characteristic input and output impedance of approximately 50 ohms. The broadband 4:1 transformer in the collector circuit is required to step down the collector impedance to 50 ohms. Design information on this type of circuit is provided in the ARRL book, *Solid State Design for the Radio Amateur*. A bandpass type of filter is needed at the amplifier input. Another can be used at the output of the 4:1 transformer if desired. The transistor used in any of the amplifiers of Fig. 55 should have an  $f_T$  which is five to ten times greater than the highest operating frequency of the stage. The 2N5179 has an  $f_T$  in excess of 1000 MHz, making it a good device up to 148 MHz for this application.

### Transistor RF Power Amplifiers

Rf power amplifiers which use bipolar transistors fall into two general categories — Class C and linear. The latter is used for a-m and ssb signal amplification and the class of operation is A or AB. These amplifiers are designed for narrow or wideband applications, depending on the purpose for which the stage or stages will be used. Class C bipolar-transistor amplifiers are used for fm and cw work.

Most wideband amplifiers contain ferrite-loaded broadband transformers at the

input and output ports. The output transformer is followed by a multipole low-pass filter for each band of operation. This is necessary to attenuate harmonic currents so that they will not be radiated by the antenna system. Although this type of filtering is not always needed with a narrowband amplifier (the networks provide reasonable selectivity), filters should be used in the interest of spectral purity. Two-section filters of the half-wave or low-pass T variety are entirely suitable for harmonic reduction at the 50-ohm output ports of amplifiers.

One of the principal difficulties encountered by amateurs who design and build their own high-power, solid-state amplifiers is instability at some point in the power range. That is, an amplifier driven to its maximum rated output may be stable when terminated properly, but when the drive level is reduced it is apt to break into self-oscillation at the operating frequency, at vhf, or perhaps at very low frequencies. Part of the problem is caused by an increase in beta as the collector current is decreased. This elevates the amplifier gain to encourage instability. Also, solid-state amplifiers are designed

for a specific network impedance at a specified power-output level. When the drive is reduced the collector and base impedances increase. This causes a mismatch. An increase in the loaded Q of the networks may also result — a situation that encourages instability. Therefore, it is best to design for a specified power output and adhere closely to that level during operation.

Solid-state power amplifiers should be operated just below their saturation points for best efficiency and stability. That is the point which occurs when no additional rf output can be obtained with increased driving power. Some designers recommend that, for example, a 28-volt transistor be used for 12-volt operation: Saturation will take place at a level where the transistors are relatively safe from damage if a significant output mismatch is present. Stability is usually better under these same conditions, although the gain of the transistors will be considerably lower than would be the case if equivalent types of 12-volt devices were used.

Fig. 56 shows two single-ended amplifiers of typical design. At A there is a broadband input transformer which steps

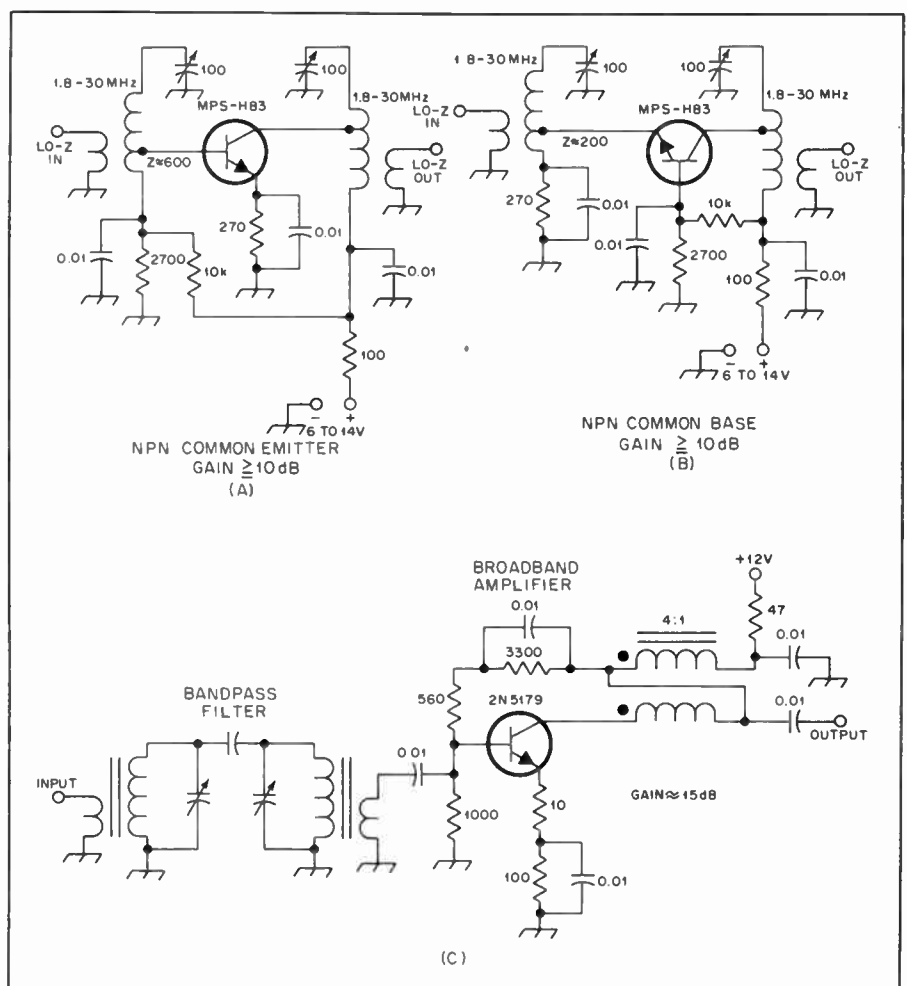


Fig. 55 — Illustrations of common-emitter and common-base rf amplifiers for narrow-band use. The circuit at C is that of a fed-back broadband amplifier which has a bandpass filter at the input.



down the 50-ohm source to the low base impedance of Q1: Most power stages have a base impedance of 5 ohms or less. Although there are a number of suitable tuned networks that can be used to effect the desired impedance match, the use of T1 eliminates components and the sometimes complex calculations required for the design of a proper network. When the actual base impedance of Q1 is unknown (it varies with respect to drive level and operating frequency), empirical adjustment of the T1 turns ratio will permit close matching. An SWR indicator can be used between T1 and the signal source to indicate a matched condition. This test should be made with the maximum intended drive applied.

To continue the discussion relating to Fig. 56A, a 10-ohm resistor (R1) is bridged across the secondary of T1 to aid stability. This measure is not always necessary. It will depend on the gain of the transistor, the layout and the loaded Q of T1. Other values of resistance can be used. A good rule of thumb is to employ only that value of resistance which cures instability. It must be remembered that R1 is in parallel with the transistor input impedance: This will have an effect on the turns ratio of T1. When excessive driving power is available, a deliberate mismatch can be introduced at the input to Q1 by reducing the number of secondary turns. If that is done, R1 can often be eliminated. The shortcoming which results from this technique is that the driving source will not be looking into a 50-ohm termination. T1 is normally a ferrite-loaded transformer — toroidal or solenoidal. The core material for operation from 1.8 to 30 MHz is typically the 950- $\mu$ ; (Initial permeability) type. The primary winding of T1 (and other broadband transformers should be approximately four times the terminal impedance with respect to reactance. Therefore, for a 50-ohm load characteristic the primary-winding reactance of T1 should be roughly 200 ohms.

Two rf chokes are shown in Fig. 56A. These are necessary to assure ample dc-lead decoupling along with the related bypass capacitors. The upper rf choke serves also as a collector load impedance. The reactance should be four or five times the collector impedance. Three values of bypass capacitors are used to ensure effective decoupling at vhf, hf and lf. If the decoupling is inadequate, rf from the amplifier can flow along the 12-volt bus to other parts of the transmitter, thereby causing instability of one or more of the stages. A simple low-pass T network is used for matching the collector to the 50-ohm load. It also suppresses harmonic energy. The loaded Q of this general type of matching network should be kept below 4 in the interest of amplifier stability. Information on this and other types of tuned matching networks is given in the *ARRL electronics data book*. Data are

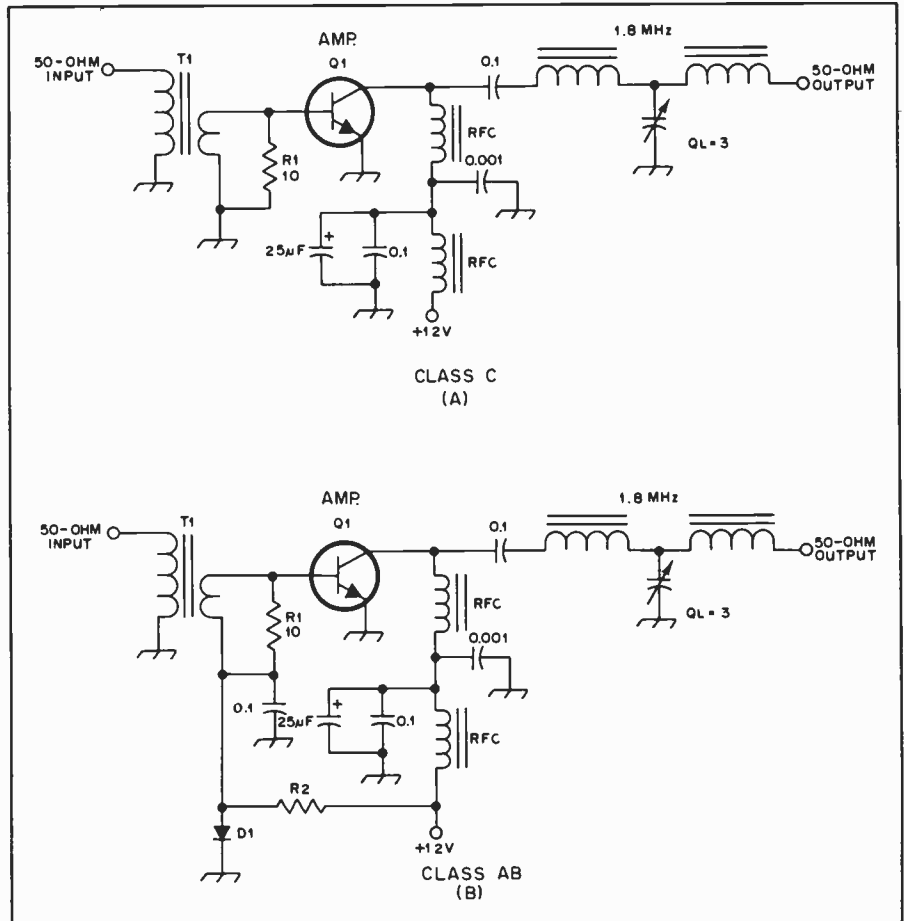


Fig. 56 — Circuits for rf power amplifiers. At A is a Class C type. The circuit at B is biased for linear amplification.

also given in that volume concerning broadband transformer design.

Fig. 56B shows the same general amplifier. The difference is in the biasing. The circuit at A is set up for Class C. It is driven into the cutoff region during operation. At B there is a small amount of forward bias applied to Q1 (approximately 0.7 volt) by means of the barrier voltage set by D1, a silicon power diode. D1 also functions as a simple bias regulator. R2 should be selected to provide fairly substantial diode current. The forward bias establishes linearity for the amplifier so that ssb and a-m driving energy can be applied to Q1 with minimum distortion resulting.

Although some transistors are designed especially for linear amplification, any power transistor can be used for the purpose. Once the proper biasing point is found for linear amplifications with a Class C type of transistor, an investigation of linearity versus output power should be undertaken. Some Class C transistors are incapable of delivering as much power (undistorted) in Class AB as they can under Class C conditions. Most power transistors intended for linear amplification have built-in, degenerative-feedback resistors at the emitter sites. This technique

aids linearity. Depending on the package style of a Class C type of transistor, an emitter-feedback resistor can be added externally. Such resistors are usually on the order of 1 ohm.

A broadband Class C amplifier is shown in Fig. 57A. T1 and T2 are 4:1 broadband transformers connected in series to provide an impedance step down of 16:1. For most applications this arrangement will provide an acceptable match between 50 ohms and the base impedance of Q1. In the example we have assumed a base impedance of approximately 3 ohms.

T3 serves as a collector load and a step-up transformer. It is useful to use a step-up transformer when the collector impedance is low (25 ohms or less). This enables the designer to work with filter-component values (FL1) that are more practical than would be the case if an attempt was made to match 10 ohms to 50 ohms with the filter network. FL1 in this example is a double pi-section low-pass type (half-wave filter). It is designed to match 40 ohms to 50 ohms and has a loaded Q of 1.

Feedback can be applied to stabilize the amplifier. This is seen in Fig. 57B. C1 and R1 are chosen to reduce the amplifier gain



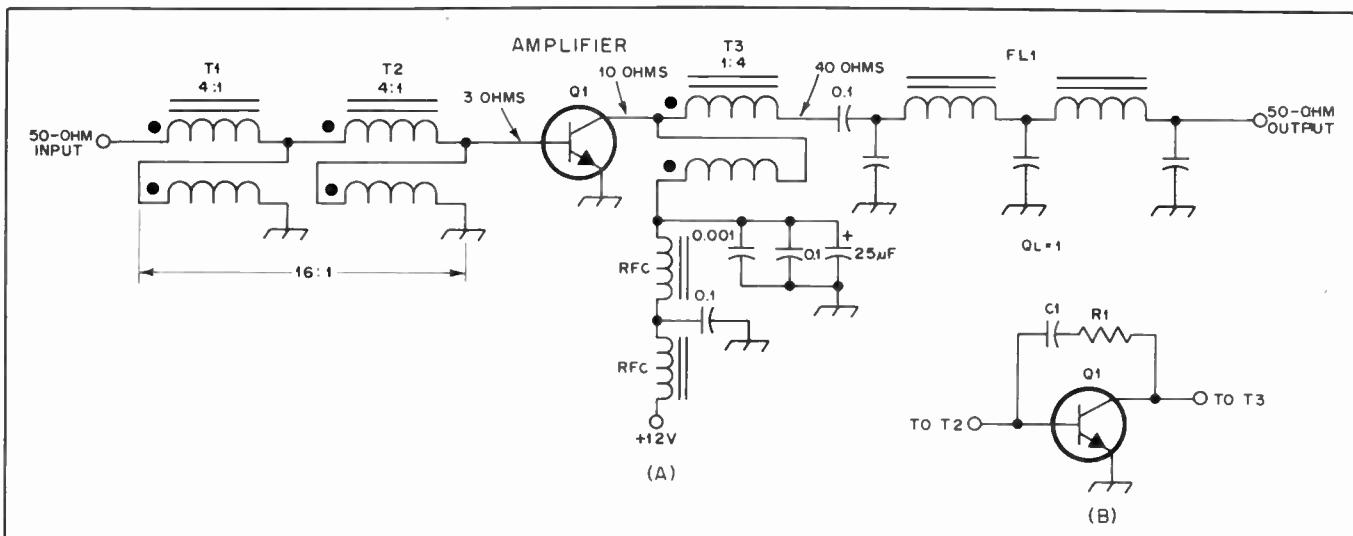


Fig. 57 — Broadband transformers are employed at A for impedance matching. FL1 suppresses harmonic currents at the amplifier output. In the example at B are feedback components C1 and R1 (see text).

by whatever amount is necessary to provide stability and the broadband characteristics desired. C1 serves as a dc blocking capacitor.

A push-pull broadband linear amplifier is illustrated at Fig. 58. When additional frequency compensation is desired (beyond that available from a negative-feedback network) L1 and R1 can be added across the amplifier input. They are selected to roll off the driving power toward the low end of the amplifier operating range. As the frequency is reduced, L1 represents a lower reactance, thereby permitting some of the drive power to be dissipated in R1.

T1 is a conventional broadband transformer (not a transmission-line type) with a turns ratio set for matching 50 ohms to the base load presented by Q1 and Q2. T2, another broadband transformer, is used to provide balanced dc feed to the collectors. T3 is another broadband transformer which is wound for lowering the collector-to-collector impedance to 50 ohms. FL1 is designed for a bilateral impedance of 50 ohms in this example.

#### Bipolar-Transistor Oscillators

Transistors function well as crystal-controlled or LC oscillators. RC oscillators are also practical when a bipolar

transistor is used as the active element. The same circuits used for tube-type oscillators apply when using transistors. The essential difference is that transistor oscillators have lower input and output impedances, operate at low voltages, and deliver low output power — usually in the mW range. The greater the oscillator power, the greater the heating of the transistor junction and other circuit elements. Therefore, in the interest of oscillator stability it is wise to keep the dc input power as low as practical. The power level can always be increased by means of subsequent amplifier stages at minor cost.

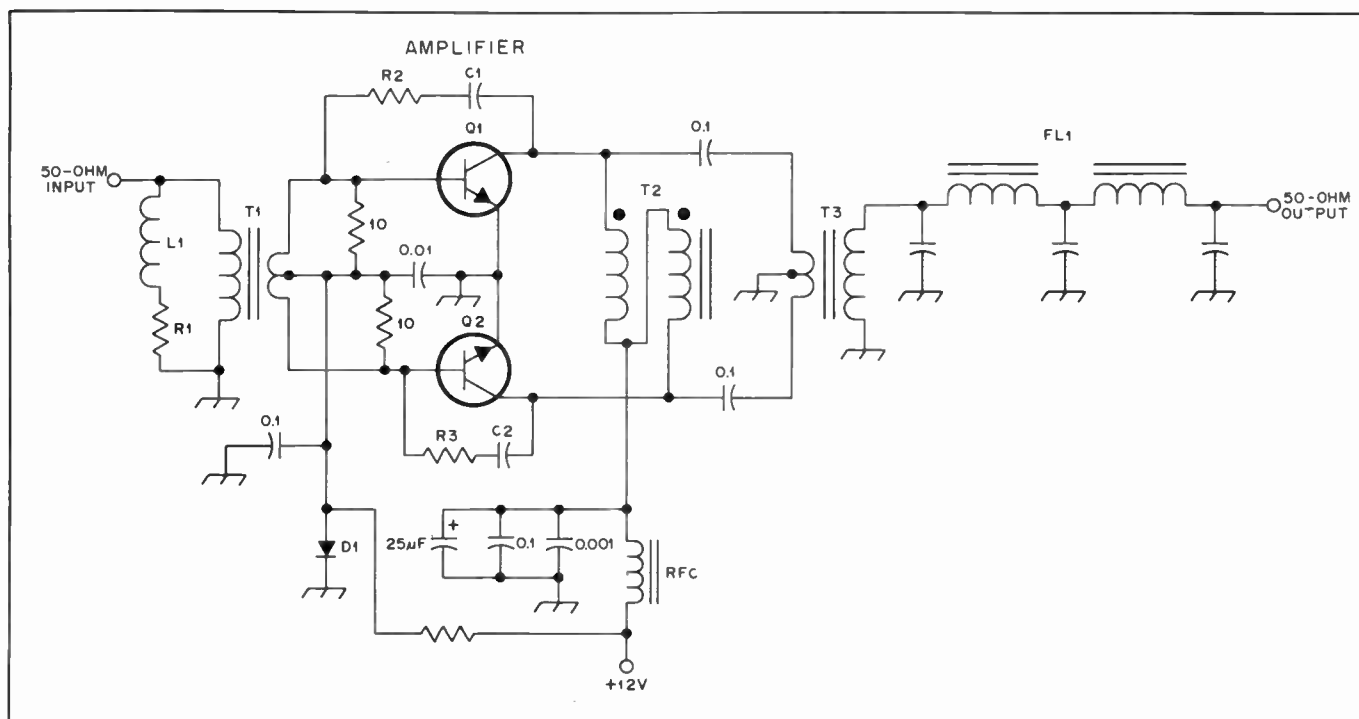


Fig. 58 — Example of a fed-back, push-pull, rf power amplifier set up for broadband service from 1.8 to 30 MHz. The circuit is biased for linear amplification.

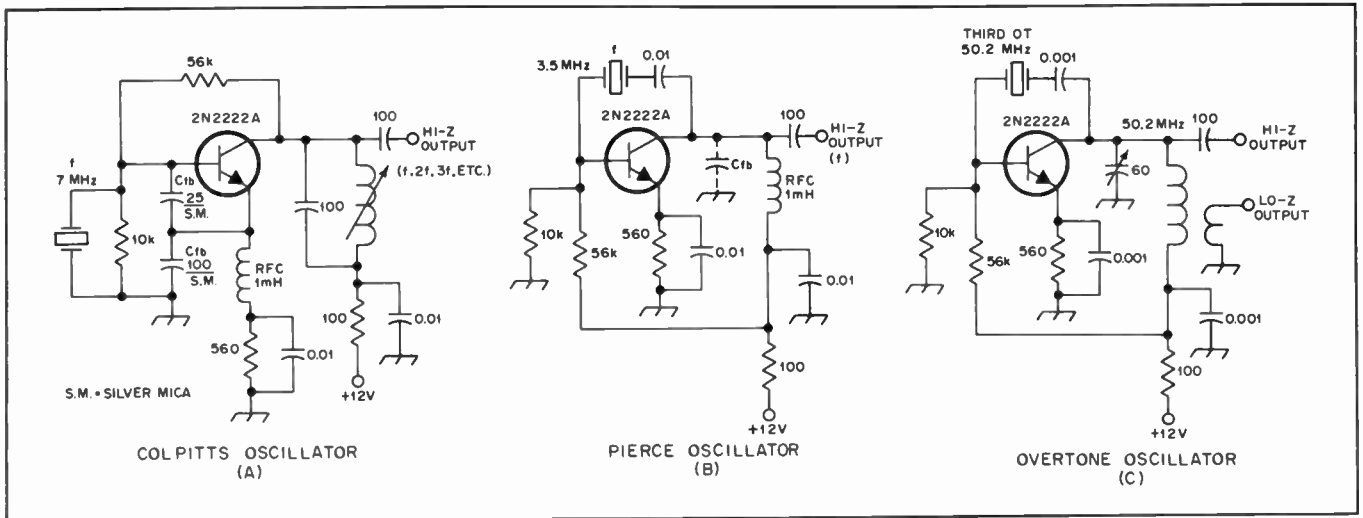


Fig. 59 — Examples of transistor oscillators which use crystal control.

Some major considerations in the selection of a transistor that is used in an oscillator are the beta and  $f_T$ . A fairly high small-signal beta is desirable, and the  $f_T$  should be high — perhaps 10 times the crystal frequency or greater. These features will help to assure oscillation, even though the crystal is sluggish or the LC network is of fairly low Q.

Some representative examples of crystal-

controlled oscillators are provided in Fig. 59. At A is an oscillator that can be used to obtain output at  $f$  (the crystal frequency), or at multiples of  $f$ . The circuit at B illustrates a Pierce type of oscillator for fundamental output at 3.5 MHz.  $C_b$  may be necessary with some crystals to provide ample feedback to cause oscillation. The value of  $C_b$  will depend on the operating frequency and the gain of the

transistor. Typically for 1.8 to 20-MHz crystals (fundamental mode) the capacitance value ranges from 25 to 200 pF. The higher values are typical at the lower end of the frequency range. In Fig. 59C is an overtone oscillator. The collector tuned circuit must be able to resonate slightly above the crystal overtone frequency in order to ensure oscillation. Low-impedance output can be had by means of the link

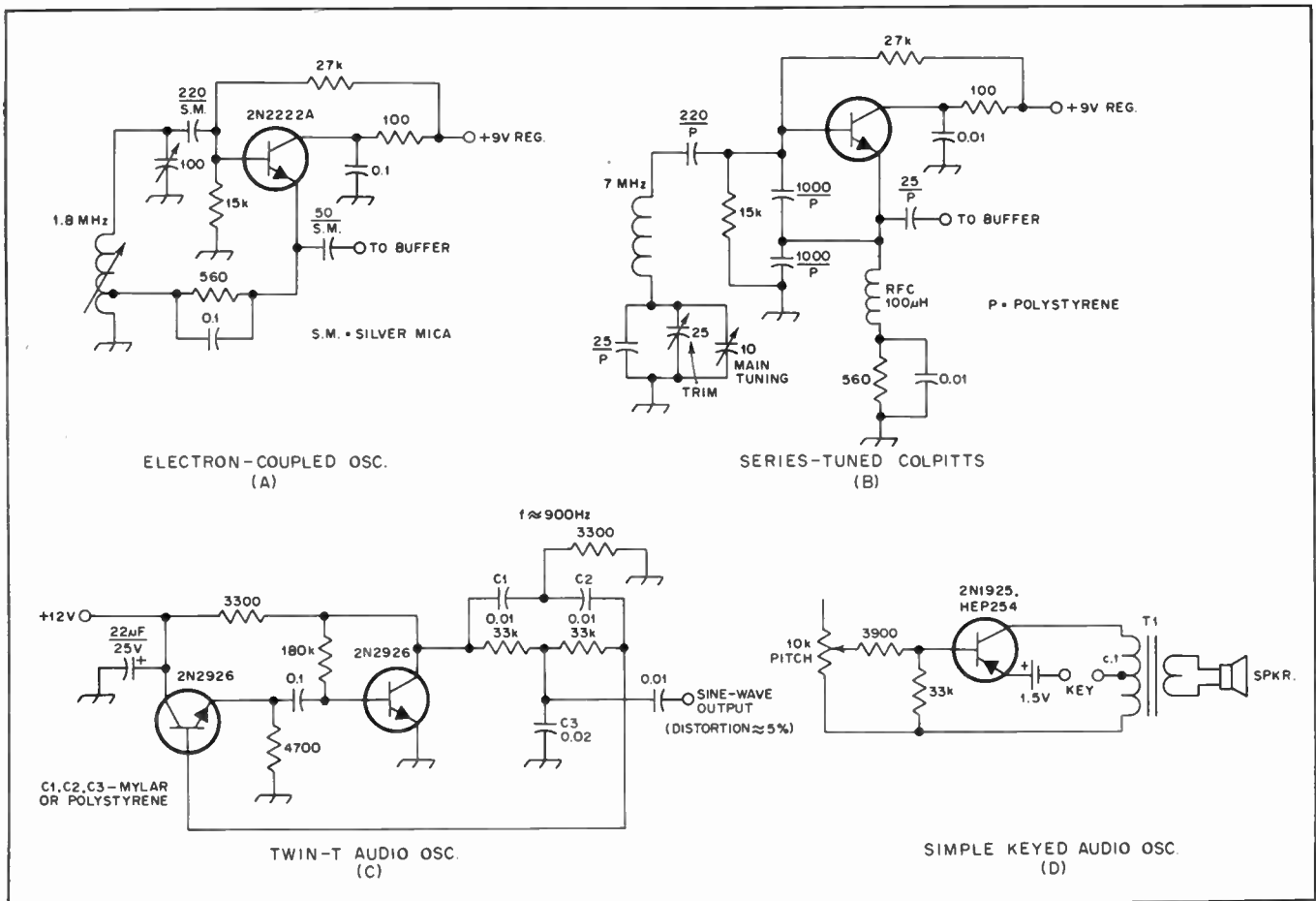


Fig. 60 — The circuits at A and B are VFOs for use in transmitters or receivers. Audio oscillators are shown at C and D.

shown. Alternatively, a capacitive divider can be placed across the inductor to provide a low-Z tap-off point. The trimmer should be retained in parallel with the inductor to permit resonating the circuit.

Some typical rf and audio oscillators are seen in Fig. 60. The circuit at A obtains feedback by means of the emitter tap on the tuned circuit. Approximately

25 percent of the oscillator rf power is used as feedback. The tap point on this type of oscillator is between 10 and 25 percent of the total coil turns. The designer should use the smallest amount of feedback that will provide reliable oscillator performance with the load connected.

Fig. 60B illustrates a series-tuned Colpitts oscillator, although this general

circuit is often referred to as a "series-tuned Clapp" oscillator. It is very stable when polystyrene capacitors are used in the feedback and tuned circuits. Silvermica capacitors can be used as substitutes at a slight sacrifice in drift stability (long term).

A twin-T audio oscillator is shown at C in Fig. 60. It is a very stable type of circuit which delivers a clean sine-wave output. Mylar or polystyrene capacitors should be used for best stability.

A simple feedback circuit is effected by means of T1 in Fig. 60D. T1 is a small transistor output transformer with a center-tapped primary and an 8-ohm secondary. This circuit is excellent for use as a code-practice or side-tone oscillator.

All of the rf oscillators described in these examples should be followed by one or more buffer stages to prevent frequency changes resulting from load variations occurring after the oscillator chain.

### Transistor Mixers

Much of the modern equipment used by amateurs contains mixers which utilize FETs or diode rings. Good dynamic range is offered by those two circuits. However, there is no reason why a bipolar mixer can't be used to obtain satisfactory results if care is taken with the operating parameters and the gain distribution in the receiver or transmitter where they are used. The bipolar transistors used in receiver mixers should be selected according to noise figure (low) and dynamic range (high). The signal applied to it should be kept as low as possible, consistent with low-noise operation. Most semiconductor manufacturers specify certain transistors for mixer service. Although this does not mean that other types of bipolar transistors can't be used for mixing, it is wise to select a device that is designed for that class of service.

Fig. 61 contains examples of three basic types of transistor mixers. At A is seen the most common one. It is found in simple circuits such as transistor a-m broadcast-band receivers. As an aid to dynamic range, the mixers of Fig. 61 can be used without rf amplifier stages ahead of them for frequencies up to and including 7 MHz: The noise in that range (ambient from the antenna) will exceed that of the mixer.

The primary limitation in the performance of the mixer of Fig. 61A is that the local-oscillator voltage is injected at the base. This does not afford good LO/input-signal isolation. The unfavorable result can be oscillator "pulling" with input load changes, and/or radiation of the LO energy via the antenna if the front-end selectivity is marginal or poor. The advantage of the circuit is that it requires less injection voltage than the one at B, where emitter injection is used.

At Fig. 61 B is the same basic mixer, but with LO voltage applied to the emitter.

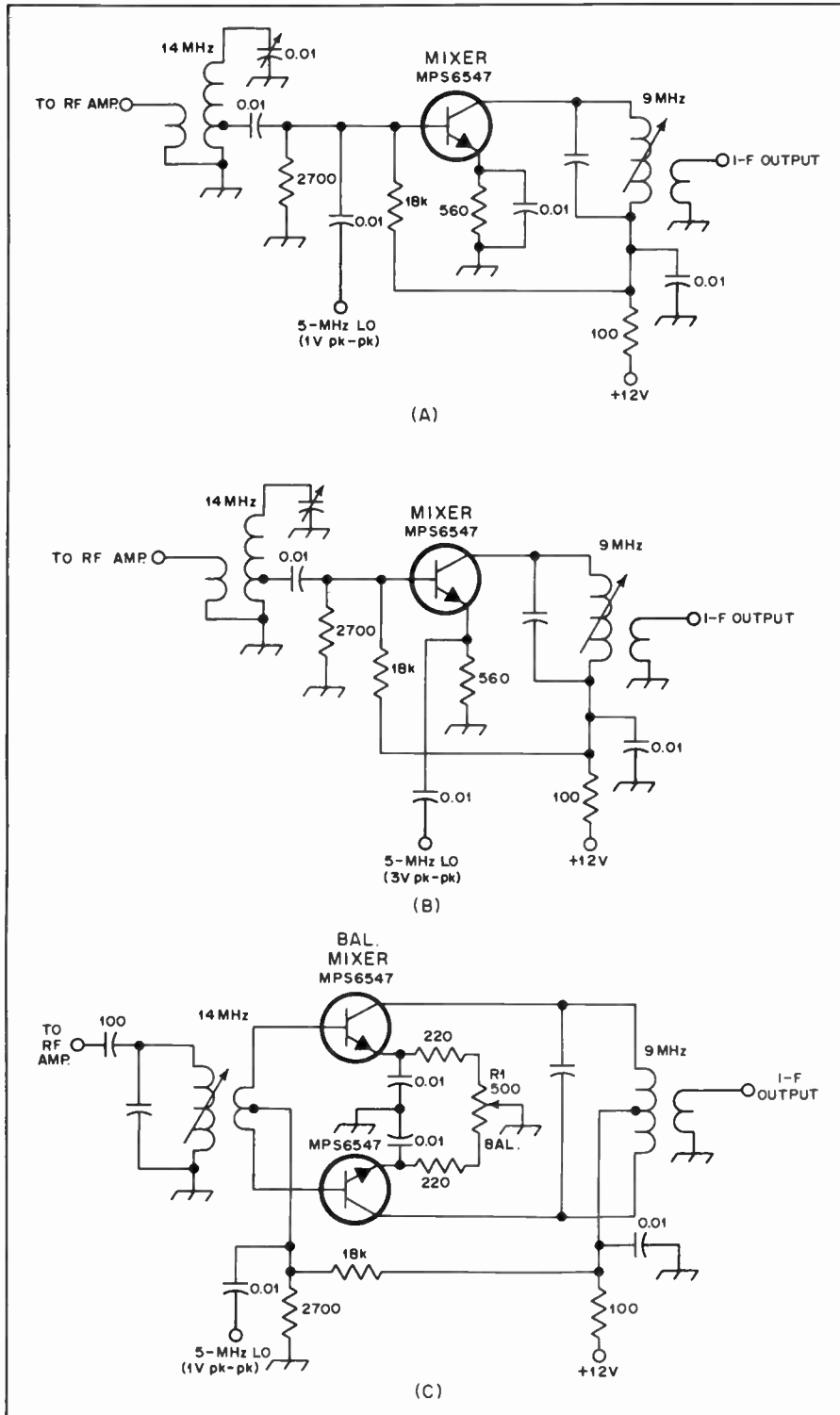


Fig. 61 — Some typical bipolar-transistor mixers are seen here. Their characteristics are discussed in the text.

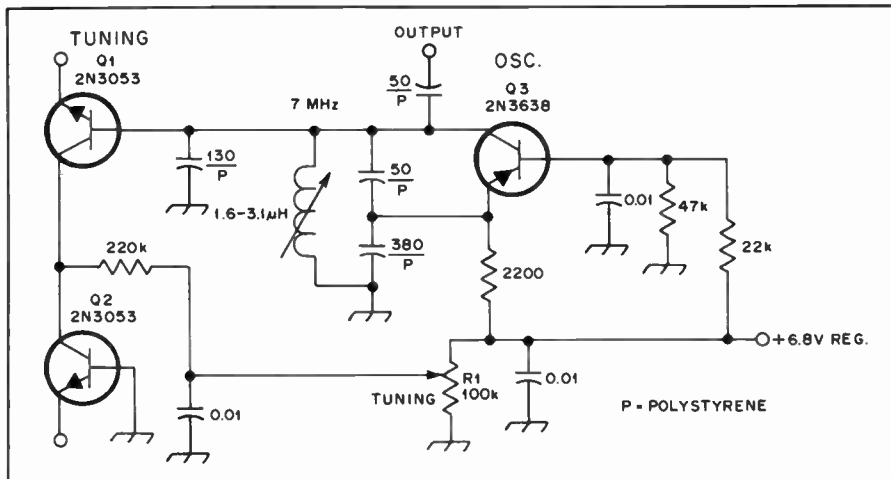


Fig. 62 — Bipolar transistors serve as varactor tuning diodes in this circuit (Q1 and Q2).

This technique requires slightly higher levels of LO energy, but affords greater LO isolation from the mixer input port.

A singly balanced bipolar-transistor mixer is illustrated in Fig. 61 at C. R1 is adjusted to effect balance. This circuit could be modified for emitter injection by changing R1 to 1000 ohms, replacing the 220-ohm resistors with 1-mH rf chokes, and injecting the LO output at the junction of the two 0.01- $\mu$ F capacitors. The center tap of the input transformer (base winding) would then be bypassed by means of a 0.01- $\mu$ F capacitor.

### Other Uses for Bipolar Transistors

It is possible to take advantage of the junction characteristics of small-signal transistors for applications which usually employ diodes. One useful technique is that of employing transistors as voltage-variable capacitors (varactors). This method is seen in Fig. 62. The collector-base junction of Q1 and Q2 serve as diodes for tuning the VFO. In this example the emitters are left floating. A single transistor could be used, but by connecting the pair in a back-to-back arrangement they never conduct during any part of the rf cycle. This minimizes loading of the oscillator. The junction capacitance is varied by adjusting the tuning control, R1. In this circuit the tuning range is approximately 70 kHz.

A bipolar-transistor junction can be used as a Zener-diode in the manner shown in Fig. 63. Advantage is taken of the reverse-breakdown characteristic of Q1 to establish a fixed reference level. Most transistors provide Zener-diode action between 6 and 9 volts. The exact value can be determined experimentally.

### Field-Effect Transistors

Field-effect transistors are assigned that name because the current flow in them is controlled by varying *electric field* which is brought about through the application of a *voltage* that controls the electrode

known as the *gate*. The analogy for a bipolar transistor is that in the latter the current flow is controlled by the *current* applied to the *base* electrode.

There are two essential types of field-effect transistors (FETs) in use today. They are the *junction FET* and the *MOSFET*. The former is most commonly called a JFET. It has no insulation between its elements, just as is the case with bipolar transistors. The MOSFET has a thin layer of oxide between the gate or gates and the drain-source junction. The term MOSFET is derived from *metal-oxide silicon* field-effect transistor. The basic characteristic of the two types are similar — high input impedance and good dynamic range. These characteristics apply to small-signal FETs. Power FETs, which will be treated later, have different characteristics. Although some MOSFETs have but one gate, others have two gates. Single-gate FETs can be equated practically to a triode vacuum tube. The gate represents the grid, the anode is similar to the drain, and the cathode is like the source. The input impedance of FETs is a megohm or greater. The noise figure of a FET is quite low, making them ideal as preamplifiers for audio and rf well into the uhf region. Nearly all of the MOSFETs manufactured today have built-in gate-protective Zener diodes. Without this provision the gate insulation can be perforated easily by small static charges on the user's hands or by the application of excessive voltages. The protective diodes are connected between the gate (or gates) and the source of the FET.

### The Junction FET

As was stated earlier, field-effect transistors are divided into two main groups: Junction FETs and MOSFETs. The basic JFET is shown in Fig. 64.

The reason for the terminal names will become clear later. A dc operating condition is set up by starting a current

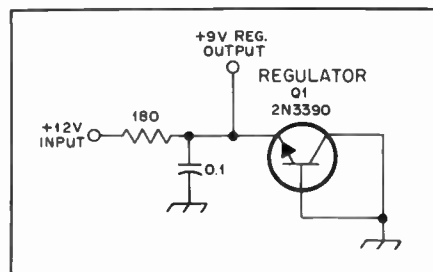


Fig. 63 — A bipolar transistor will function as a Zener diode when connected as shown here.

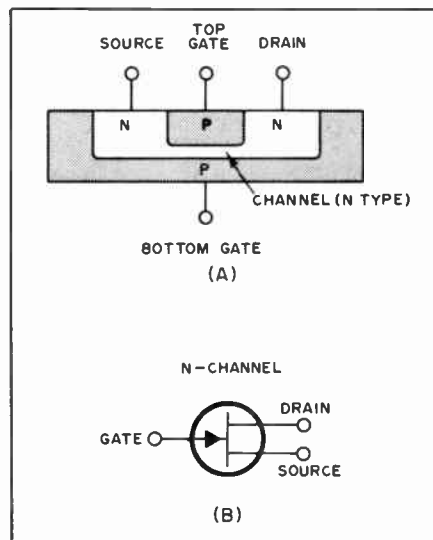


Fig. 64 — Profile and symbol for a junction field-effect transistor.

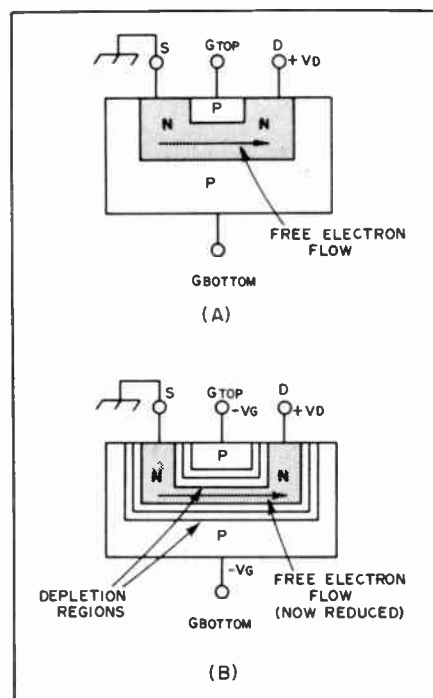


Fig. 65 — Operation of a JFET under applied bias. A depletion region (light shading) is formed, compressing the channel and increasing the resistance to current flow.



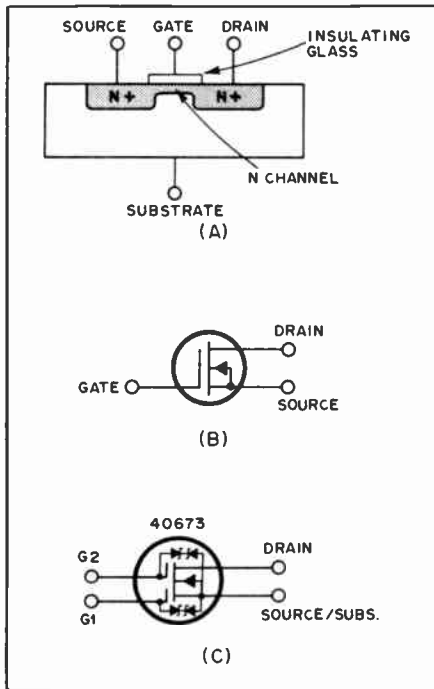


Fig. 66 — Profile and symbol for a MOSFET.

flow between source and drain. This current flow is made up of free electrons since the semiconductor is n-type in the channel, so a positive voltage is applied at the drain. This positive voltage attracts the negatively charged free electrons and the current flows (Fig. 65). The next step is to apply a gate voltage of the polarity shown in Fig. 65. Note that this reverse-biases the gates with respect to the source, channel, and drain. This reverse-bias gate voltage causes a depletion layer to be formed which takes up part of the channel, and since the electrons now have less volume in which to move the resistance is greater and the current between source and drain is reduced. If a large gate voltage is applied the depletion regions meet, causing *pinch off*, and consequently the source-drain current is reduced nearly to zero. Since the large source-drain current changed with a relatively small gate voltage, the device acts as an amplifier. In the operation of that JFET, the gate terminal is never forward biased, because if it were the source-drain current would all be diverted through the forward-biased gate junction diode.

The resistance between the gate terminal and the rest of the device is very high, since the gate terminal is always reverse biased, so the JFET has a very high input resistance. The source terminal is the *source* of current carriers, and they are *drained* out of the circuit at the drain. The gate *opens* and *closes* the amount of channel current which flows in the pinch-off region. Thus the operation of a FET closely resembles the operation of the vacuum tube with its high grid-input impedance.

### MOSFETs

The other large family which makes up field-effect transistors is the insulated-gate FET, or MOSFET, which is pictured schematically in Fig. 66. In order to set up a dc operating condition, a positive polarity is applied to the drain terminal. The substrate is connected to the source, and both are at ground potential, so the channel electrons are attracted to the positive drain. In order to regulate this source-drain current, voltage is applied to the gate contact. The gate is insulated from the rest of the device by a layer of very thin dielectric material, so this is not a p-n junction between the gate and the device — thus the name insulated gate. When a negative gate polarity is applied, positive-charged holes from the p-type substrate are attracted toward the gate and the conducting channel is made more narrow; thus the source-drain current is reduced. When a positive gate voltage is connected, the holes in the substrate are repelled away, the conducting channel is made larger, and the source-drain current is increased. The MOSFET is more flexible since either a positive or negative

voltage can be applied to the gate. The resistance between the gate and the rest of the device is extremely high because they are separated by a layer of thin dielectric. Thus the MOSFET has an extremely high input impedance. In fact, since the leakage through the insulating material is generally much smaller than through the reverse-biased p-n gate junction in the JFET, the MOSFET has a much higher input impedance. Typical values of  $R_{in}$  for the MOSFET are over a million megohms, while  $R_{in}$  for the JFET ranges from megohms to over a thousand megohms. There are both single-gate and dual-gate MOSFETs available. The latter has a signal gate, gate 1, and a control gate, gate 2. The gates are effectively in series making it an easy matter to control the dynamic range of the device by varying the bias on gate 2. Dual-gate MOSFETs are widely used as acc-controlled rf and i-f amplifiers, as mixers and product detectors, and as variable attenuators. The isolation between the gates is relatively high in mixer service. This helps lessen oscillator "pulling" and reduces oscillator radiation. The forward *transadmittance* (transconductance, or  $g_m$ ) of modern MOSFETs is as high as 18,000.

### Characteristic Curves

The characteristic curves for the FETs described above are shown in Figs. 67 and 68. The drain-source current is plotted against drain-source voltage for given gate voltages.

### Classifications

Field-effect transistors are classed into two main groupings for application in circuits, *enhancement mode* and *depletion mode*. The enhancement-mode devices are those specifically constructed so that they have *no* channel. They become useful only when a gate voltage is applied that causes a channel to be formed. IGFETs (insulated gate FET) can be used as enhancement-mode devices since both polarities can be applied to the gate without the gate becoming forward biased and conducting.

A depletion-mode unit corresponds to Figs. 64 and 66, shown earlier, where a

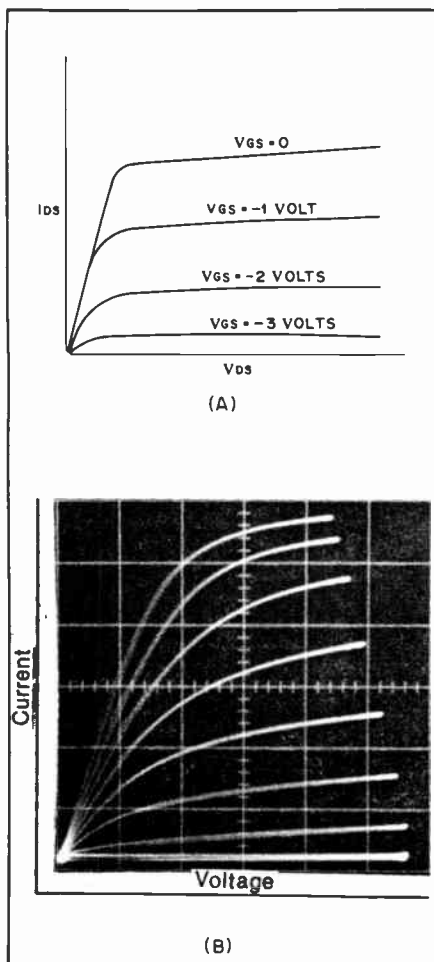


Fig. 67 — At A are typical JFET characteristic curves. The picture at B shows an actual oscilloscope picture of the family of curves produced by a curve tracer.

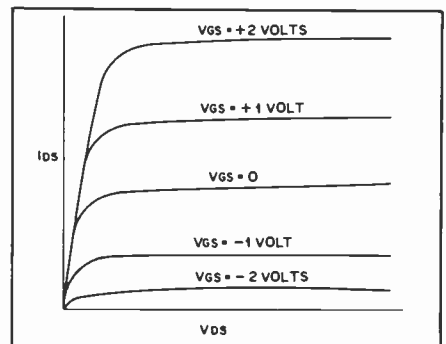


Fig. 68 — Typical characteristic curves for a MOSFET.

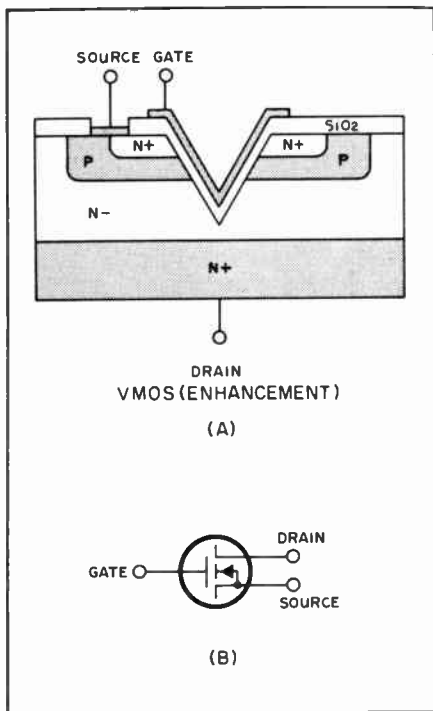


Fig. 69 — Profile and symbol for a power FET (VMOS enhancement-mode type).

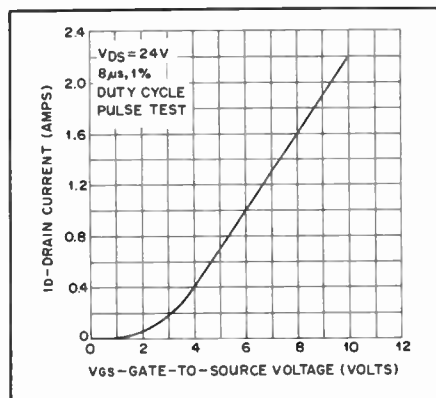


Fig. 70 — Curve showing relationship between gate-source voltage and drain current of a power FET.

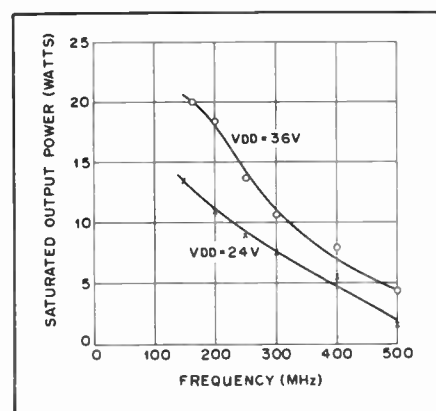


Fig. 71 — Curves for 24- and 36-volt operation of a power FET.

channel exists with no gate voltage applied. For the JFET we can apply a gate voltage and deplete the channel, causing the current to decrease. With the MOSFET we can apply a gate voltage of either polarity so the device can be depleted (current decreased) or enhanced (current increased).

To sum up, a depletion-mode FET is one which has a channel constructed; thus it has a current flow for zero gate voltage. Enhancement-mode FETs are those which have no channel, so no current flows with zero gate voltage.

### Power FETs

FETs capable of handling substantial amounts of power are available for use from dc through the vhf spectrum. They are known under more than one name — *vertical FETs*, *MOSPOWER FETs* and *VMOS FETs*. The power FET (MOSPOWER™ FET) was introduced in 1976 by Siliconix, Inc. The device enabled designers to switch a current of 1 ampere in less than four nanoseconds. The transfer characteristic of the power FET is a linear one. It can be employed as a linear power amplifier or a low-noise, small-signal amplifier with high dynamic range. With this kind of FET there is no thermal runaway, as is the case with power types

of bipolar transistors. Furthermore, there is no secondary breakdown or minority-carrier storage time. The latter makes them excellent for use in switching amplifiers (Class D service). Of particular interest to amateurs is the immunity of power FETs to damage from a high SWR (open or short condition). These devices can be operated in Class A, AB, B or C. Zero bias results in Class C operation.

Fig. 69 illustrates the manner in which a MOSPOWER FET is formed. These devices operate in the enhancement mode. The current travels vertically. The source is on top of the chip but the drain is on the backside of the chip. In this vertical structure there are four layers of material (N+, P, N- and N+). This device offers high current density, high source/drain breakdown capability and low gate/drain feedback capacitance. These features make the transistor ideal for hf and vhf use.

Fig. 70 depicts the drain current as being linearly proportional to the gate-to-source voltage. The more conventional JFET exhibits a square-law response (drain current being proportional to the square of the gate-to-source voltage).

As one example, the Siliconix VMP-4 power FET can provide a power just short of 20 watts (saturated) at 160 MHz. Fig. 71 shows curves for this device respective

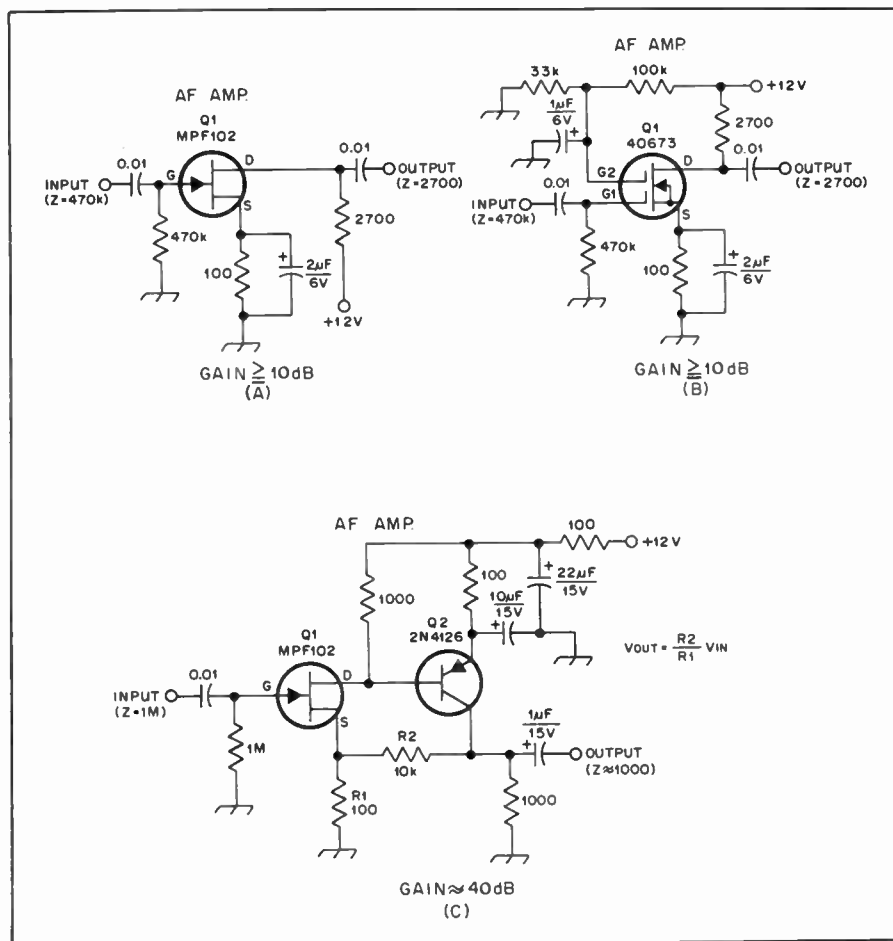


Fig. 72 — Some typical audio amplifiers which employ FETs.

to saturated output power versus frequency. In this case both the input and output impedances of the transistor are matched conjugately. An advantage to this device over the power bipolar transistor is that these impedances are barely affected by the drive levels applied. In wideband amplifier service the MOS-POWER FET can be operated with complete stability. In-depth data on these devices is given in the Siliconix application note, TA-76-1.

### Practical FET Circuits

Small-signal FETs can be used in the same general types of circuits given earlier for bipolar transistors. The primary obstacle in some types of amplifier circuits is instability. Certain precautions are necessary to prevent unwanted self-oscillations, but they do not differ markedly from those techniques applied when working with triode tubes.

In Fig. 72 are examples of FET audio amplifiers. The circuit at A shows a simple RC coupled stage with a gain of 10 dB or greater. The input and output impedances are set by the gate and drain resistors. The circuit at B in Fig. 72 is similar to that at A, except that a dual-gate MOSFET is used as the active device (Q1). A positive bias is supplied to gate 2 by means of a resistive divider. In the circuit of Fig. 72 a pnp transistor is combined with a JFET to

provide a direct-coupled pair. This configuration provides high gain. The amount of gain is set by the ratio of R1 and R2. Again, the input and output impedances are determined for the most part by the values of the input and output resistors, 1 megohm and 1000 ohms, respectively.

### RF and I-F Amplifiers

Small-signal rf and i-f amplifiers which use FETs are capable of good dynamic range and will exhibit a low noise figure. It is for these reasons that many designers prefer them to bipolar transistors. Fig. 73 contains examples of FET rf or i-f amplifiers. In the example at A the gate and drain elements of Q1 are tapped down on L2 and L3 to provide stability. This represents an intentional mismatch, which causes a slight sacrifice in stage gain. The 10-ohm drain resistor (R1) is used only if vhf parasitic oscillations occur.

At B in Fig 73 is seen a common-gate FET amplifier. The source is tapped well down on the input tuned circuit to effect an impedance match. This circuit is characterized by its excellent stability, provided the gate lead is returned to ground by the shortest path possible. This type of circuit will have slightly less gain capability than the common-source example at A.

In Fig. 73 at C is an illustration of a dual-gate MOSFET amplifier. Provided

the input and output tuned circuits are well isolated from one another there is less chance for self-oscillation than with a JFET. A positive bias is applied to gate 2, but agc voltage can be used in place of a fixed-value voltage if desired. This circuit can provide up to 25 dB of gain.

Fig. 73D shows the configuration of a cascode rf amplifier in which a dual JFET (Siliconix E420) is specified. The advantage in using the dual FET is that both transistors have nearly identical characteristics, owing to the fact that they are fabricated on a common substrate. However, well-matched single JFETs can be used in this type of circuit if desired. By using matched devices it is possible to use the direct coupling shown here. Unmatched FETs require special forward-biasing techniques and ac-coupling measures that aren't seen in this circuit.

Cascode amplifiers are noted for their high gain, good stability, and low noise figure. With the circuit shown the noise figure at 28 MHz is approximately 1.5 dB. Short leads are necessary, and shielding between the tuned circuits is recommended in the interest of stability. Careful layout will permit the use of toroidal inductors at L2 and L3. These components should be spaced apart and mounted at right angles to one another in order to reduce unwanted infringing magnetic fields. Agc can be applied to this

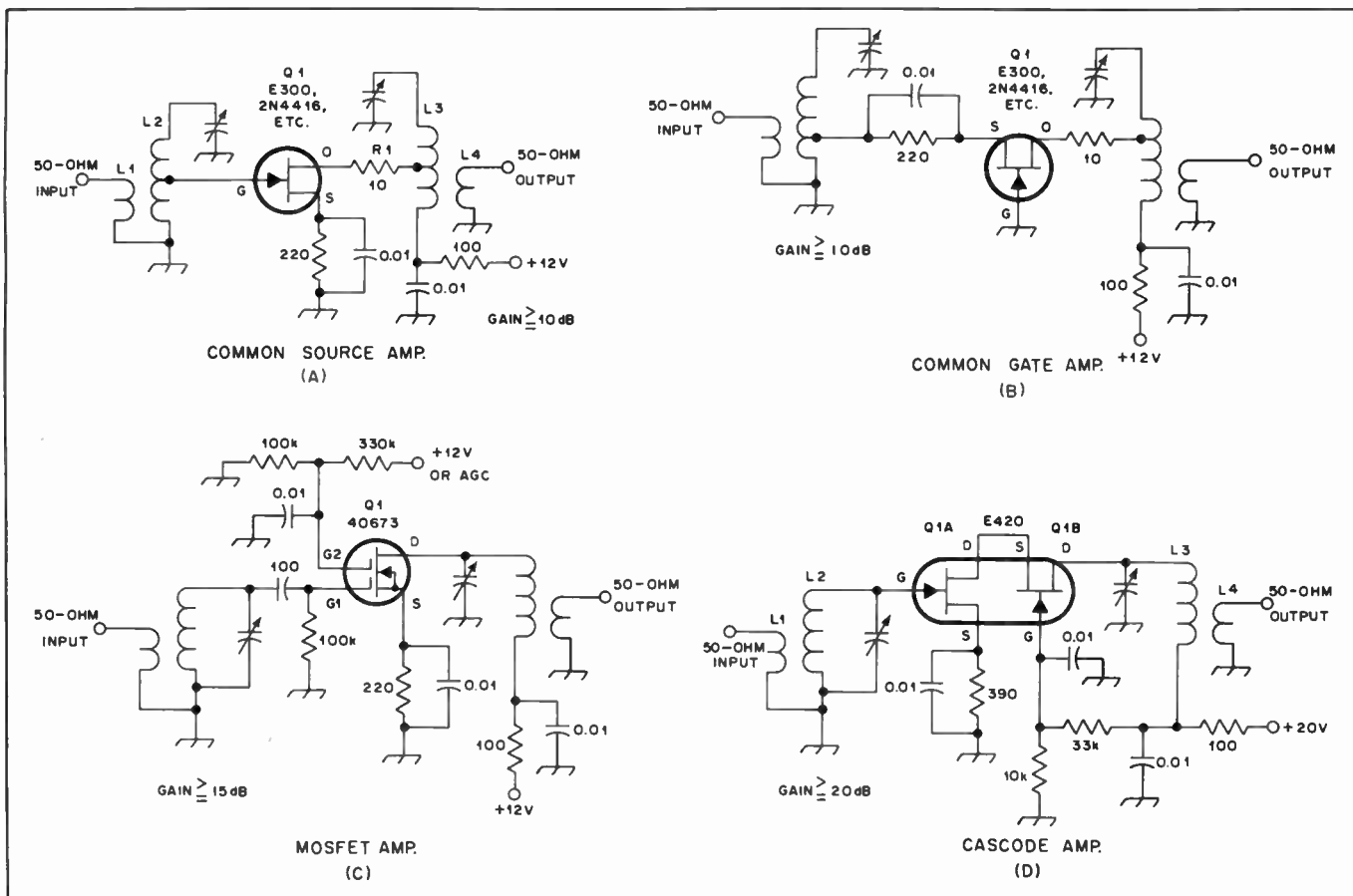


Fig. 73 — Examples of FET amplifiers suitable for rf or i-f applications.

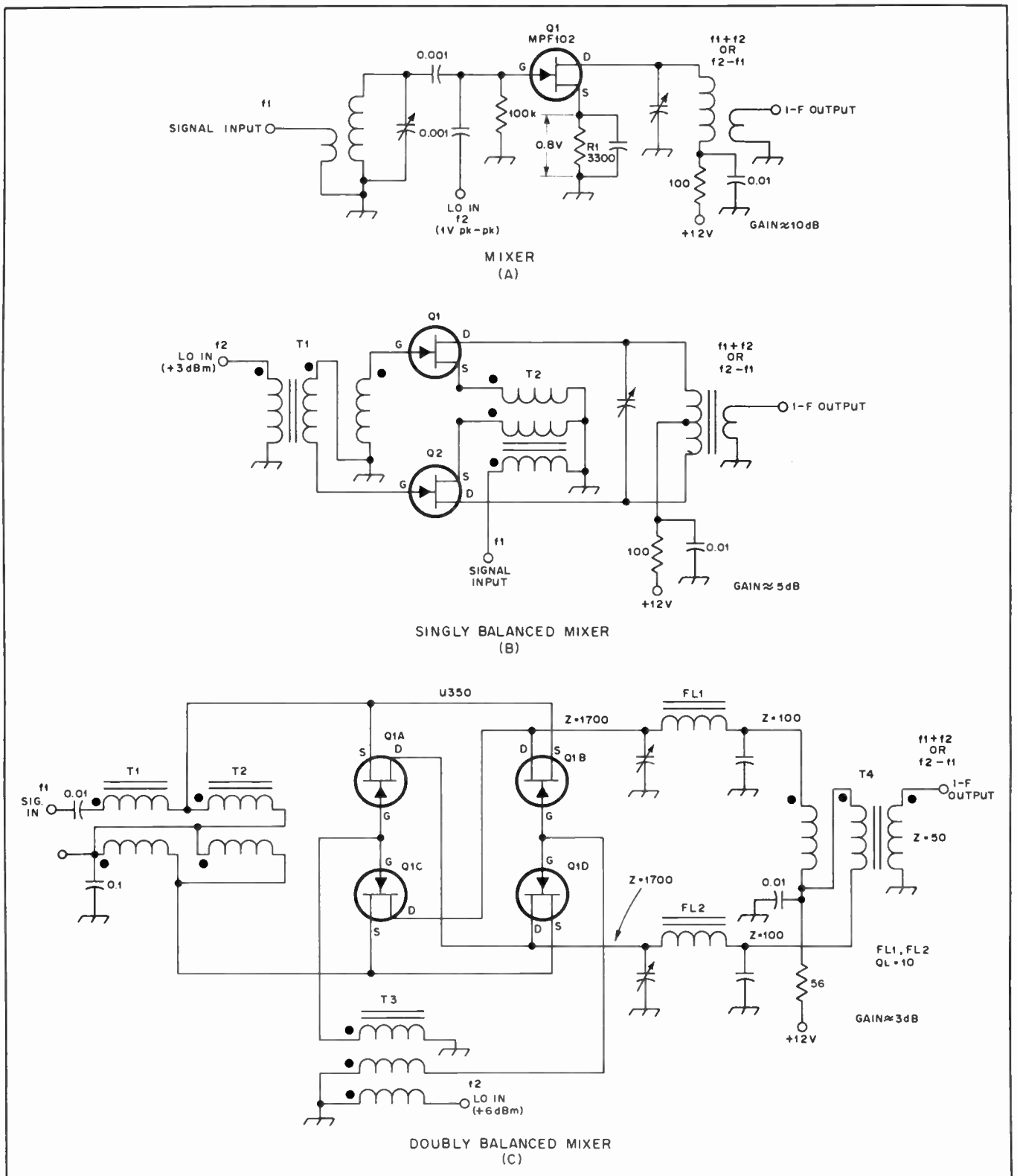


Fig. 74 — Various JFET mixers. See text for data.

amplifier by routing the control voltage to the gate of Q1B.

**FET Mixers**

There are three types of FET mixers in common use today — single-ended, singly balanced and doubly balanced. In all cases there is an advantage to using active

devices in place of passive ones (diodes). This assures a conversion gain which helps minimize the number of gain stages required in a given circuit.

A single-ended JFET mixer requires 0 dbm of LO injection power. It can provide several decades of bandwidth and has a good IMD characteristic. The latter is far

superior to most bipolar single-ended mixers. The major shortcoming is very poor isolation between the three mixer ports (rf, LO and i-f). A typical single-ended mixer using a JFET is seen in Fig. 74A. Optimum tradeoff between conversion gain and IMD occurs near the point where the self-bias is 0.8 V. LO



injection voltage will be on the order of 1 (pk-pk) to provide good mixer performance. Conversion gain with this mixer will be approximately 10 dB.

Fig. 74B illustrates a single balanced JFET mixer. A broadband transformer (T1) provides a low-impedance source for the LO and supplies injection voltage in push-pull to the gates of Q1 and Q2. The latter should be matched FETs or a dual FET such as the E430 by Siliconix. This mixer provides between 10 and 20 dB of isolation between the mixer ports. The signal is applied in parallel across the sources of Q1 and Q2 by means of broadband transformer T2. Output at the i-f is taken from a balanced tuned circuit.

A double balanced FET mixer is shown at C in Fig. 74. Broadband transformers are used throughout, with FL1 and FL2 providing low-pass selectivity at the mixer output. The filters also provide an impedance stepdown between the drains of Q1 and T4 (1700 ohms to 100 ohms). LO injection is supplied to the gates and signal input is to the sources. Port-to-port isolation with this mixer is on the order of 30 dB or greater. Bandwidth is one octave. In-depth information on this type of circuit is given in the Siliconix application note AN-72-1.

Fig. 75 contains the circuit of a typical dual-gate MOSFET single-ended mixer. Its performance characteristics are similar to those of the mixer at Fig. 74A. The primary exception is that the port-to-port isolation is somewhat better by virtue of the gate no. 2 isolation from the remainder of the electrodes. This mixer and all other active FET mixers require a fairly low drain-load impedance in the interest of good IMD. If the drain tuned circuit is made high in terms of impedance (in an effort to improve conversion gain) the drain-source peak signal swing will be high. This will lead to a change in junction capacitance (varactor effect) and the generation of harmonic currents. The result is distortion. Of primary significance is the condition called "drain-load distortion." This malady occurs when excessive signal levels overload the drain circuit. The result is degraded IMD and cross-modulation effects. R1 in Fig. 75 is used to decrease the drain-load impedance by means of swamping. A value of 10,000 ohms is suitable for a 40673 MOSFET mixer. Some JFETs require a lower drain load for optimum performance. Values as low as 5000 ohms are not unusual. This form of overloading is more pronounced at low dc drain-voltage levels, such as 6 or 8.

### FET Crystal Oscillators

A group of crystal-controlled FET oscillators is presented in Fig. 76. At A is an overtone type. The tuned circuit in the drain is resonated slightly higher than the crystal frequency to assure reliable oscillation. The circuit at B is a variation of the

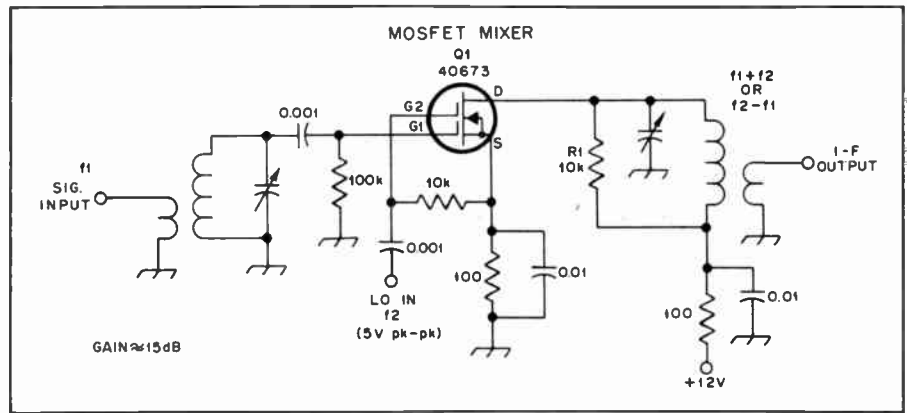


Fig. 75 — A dual-gate MOSFET single-ended mixer.

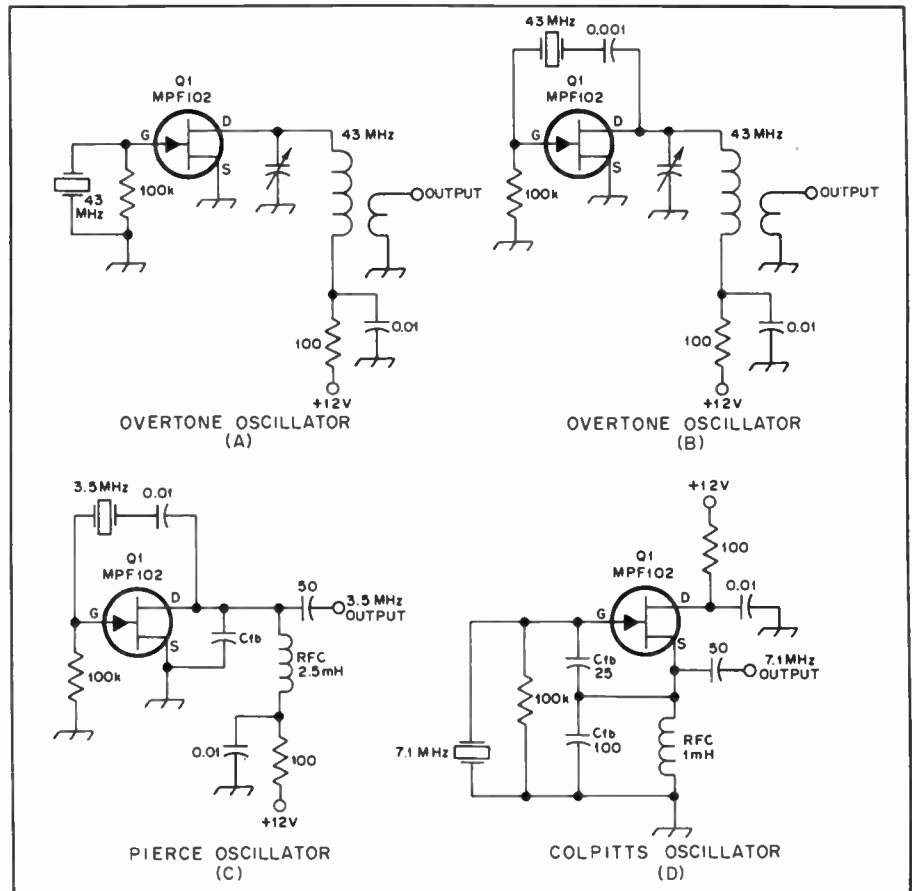


Fig. 76 — A collection of typical circuits using FETs as crystal-controlled oscillators.

one at A, but performs the same function. A Pierce type of triode oscillator is seen in Fig. 76 at C. It is suitable for use with fundamental types of crystals. A Colpitts oscillator appears at D in Fig. 76.  $C_{fb}$  in the circuits at C and D are feedback capacitors.  $C_{fb}$  in the circuit at C is chosen experimentally. Typically, it will be from 100 to 500 pF, depending on the transistor characteristics and the crystal activity.

### FET VFOs

The principle of operation for FET VFOs is similar to that which was

discussed in the section on bipolar transistor oscillators. The notable difference is the impedance level at the device input. The circuits of Fig. 77 all have high-impedance gate terminals. Furthermore, fewer parts are needed than is true of bipolar transistor equivalent circuits: There is no resistive divider for applying forward bias.

The circuits of Fig. 67A and B are identical except for the biasing of gate 2 at B. Both circuits illustrate electron-coupled oscillators. The source tap on L1 should be selected to provide approxi-

mately 25 percent of the oscillator power as feedback. D1 in each example is used to stabilize the gate bias. It acts as a diode clamp on positive-going excursions of the signal. This aids oscillator stability and reduces the harmonic output of the stage. The latter is reduced as a result of the positive swing of the sine-wave being limited by D1, which in turn limits the device transconductance on peaks. This action reduces changes in junction capacitance, thereby greatly restricting the varactor action which generates harmonic

currents. D1 is most effective when source-bias resistors are included in the circuit (R1).

Shown in Fig. 77 at C is a series-tuned Colpitts VFO which uses a JFET. This is an exceptionally stable VFO if careful design and component choice is applied. All of the fixed-value capacitors in the rf parts of the circuit should be temperature-stable. Polystyrene capacitors are recommended, but dipped silver-mica capacitors will serve adequately as a second choice. Preferably, L1 should be a rigid air-

wound inductor. A slug-tuned inductor can be used if the coil Q is high. In such cases the slug should occupy the least amount of coil space possible: Temperature changes have a marked effect on ferrite or powdered-iron slugs, which can change the coil inductance markedly.  $C_{fb}$  of Fig. 77C are on the order of 1000 pF each for 3.5-MHz operation. They are proportionally lower in capacitance as the operating frequency is increased, such as 680 pF at 7 MHz, and so on.

### Power FET Examples

Fig. 78 contains examples of three amplifiers which employ power FETs. The circuit at A is an audio amplifier which can deliver 4 watts of output. At 3 watts of output the distortion is approximately two percent. Feedback is employed to aid the reduction of distortion.

A broadband vhf amplifier is seen at B in Fig. 78. The VMP-4 device is capable of a saturated output near 20 watts at 160 MHz. In this circuit the power output is considerably less. A medium output power of 1 or 2 watts is suggested. The gain is flat within 0.5 dB over the entire bandwidth of this linear amplifier. If proper layout techniques are used this amplifier is unconditionally stable.

A narrow-band linear vhf power amplifier is shown at C in Fig. 78. Power output is 5 watts PEP. IMD is -30 dB. It is interesting to realize that this same amplifier is suitable as a high-dynamic-range preamplifier for a vhf receiver. In this application the noise figure is on the order of 2.5 dB and the gain is 11 dB. Additional data can be found in Siliconix application note AN-76-3.

### Other FET Uses

Fig. 79 contains illustrations of additional practical uses for JFETs. The circuit at A shows a Schmitt trigger. It is emitter-coupled and provides a comparator function. Q1 places very light loading on the measured input voltage. Q2 has high beta to enable the circuit to have a fast transition action and a distinct hysteresis loop. Additional applications of this type are found in *Linear Applications* by National Semiconductor Corp.

A simple FET dc voltmeter with high input impedance is seen in Fig. 79B. Multiplier resistances are given for a full-scale range of 2 or 20 volts. Meter accuracy is quite good, with a linear reading provided by M1.

A push-push frequency doubler is shown at C in Fig. 79. The input frequency (f) is applied to the gates of Q1 and Q2 in push-pull. Output from the doubler is taken with the connected drains in parallel. R1 is adjusted for best waveform purity at 2f. The efficiency of this Class C doubler is on par with that of a straight-through Class C amplifier. Careful adjustment will nearly eliminate

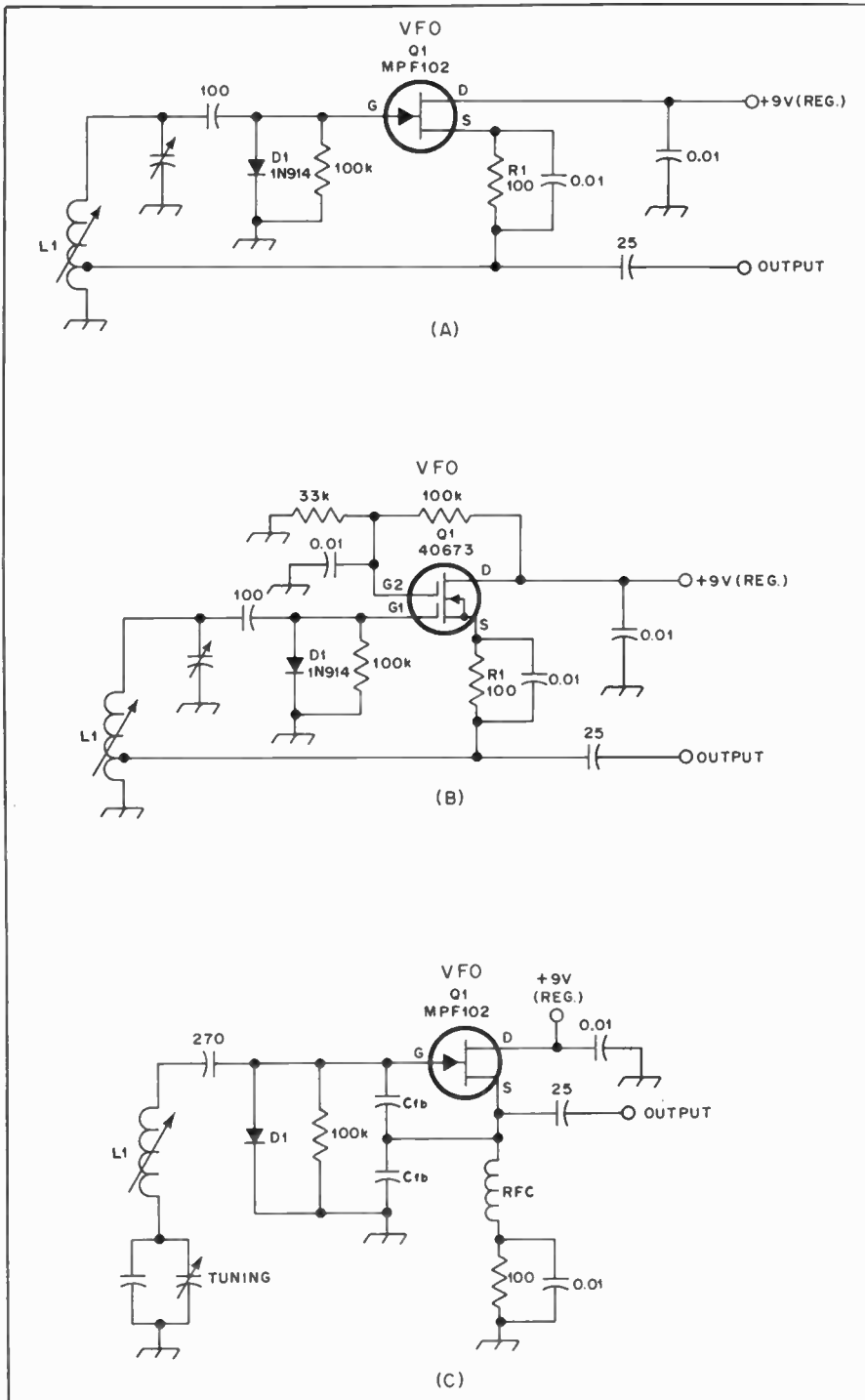


Fig. 77 — Three examples of VFO in which FETs are used.

frequency component  $f$  at the doubler output.

### Linear Integrated Circuits

There are two general types of ICs (integrated circuits). The first variety, which we are addressing at the moment, are called *linear ICs*. The other group are known generally as *logic ICs*. These devices will be discussed later in the chapter.

ICs are characterized by the term "microcircuit." In essence they are composed of numerous — sometimes hundreds — of bipolar and/or field-effect transistors on a single silicon chip (substrate). Along with the individual transistors formed on the substrate are diodes, capacitances and resistances. Some ICs contain only diodes. Others may contain only resistors. The principal advantages of ICs are their compactness over an equivalent number of discrete transistors, and the fact that all of the devices on the substrate are evenly matched in characteristics. That is the result of the manufacturing process, whereby all of the IC transistors are formed from a single slice of semiconductor material under the same environmental conditions. This provides an inherent balance in their performance traits — a condition which is nearly impossible to realize with closely matched discrete transistors. Therefore, when changes in IC temperature take place, the parameters of the transistors on the chip change in unison — a distinct advantage when the IC is used in, say, a balanced modulator, mixer or push-push doubler.

Most of the theory given earlier for bipolar transistors applies to ICs, so it will not be repeated here. Rather, the text will provide data on practical applications of ICs. Linear ICs are so-called because in most applications where they are used the performance mode is a linear one. This does not mean, however, that they can't be used in a nonlinear mode, such as Class C. The biasing will determine the operating mode, Class A through and including Class C.

### IC Structures

The basic IC is formed on a uniform chip of n-type or p-type silicon. Impurities are introduced into the chip, their depth into it being determined by the diffusion temperature and time. The geometry of the plane surface of the chip is determined by masking off certain areas, applying photochemical techniques, and providing a coating of insulating oxide. Certain areas of the oxide coating are then opened up to allow the formation of interconnecting leads between sections of the IC. When capacitors are formed on the chip, the oxide serves as the dielectric material. Fig. 80 shows a representative three-component IC in both pictorial and schematic form. Most integrated circuits are housed in TO-5 type cases, or in

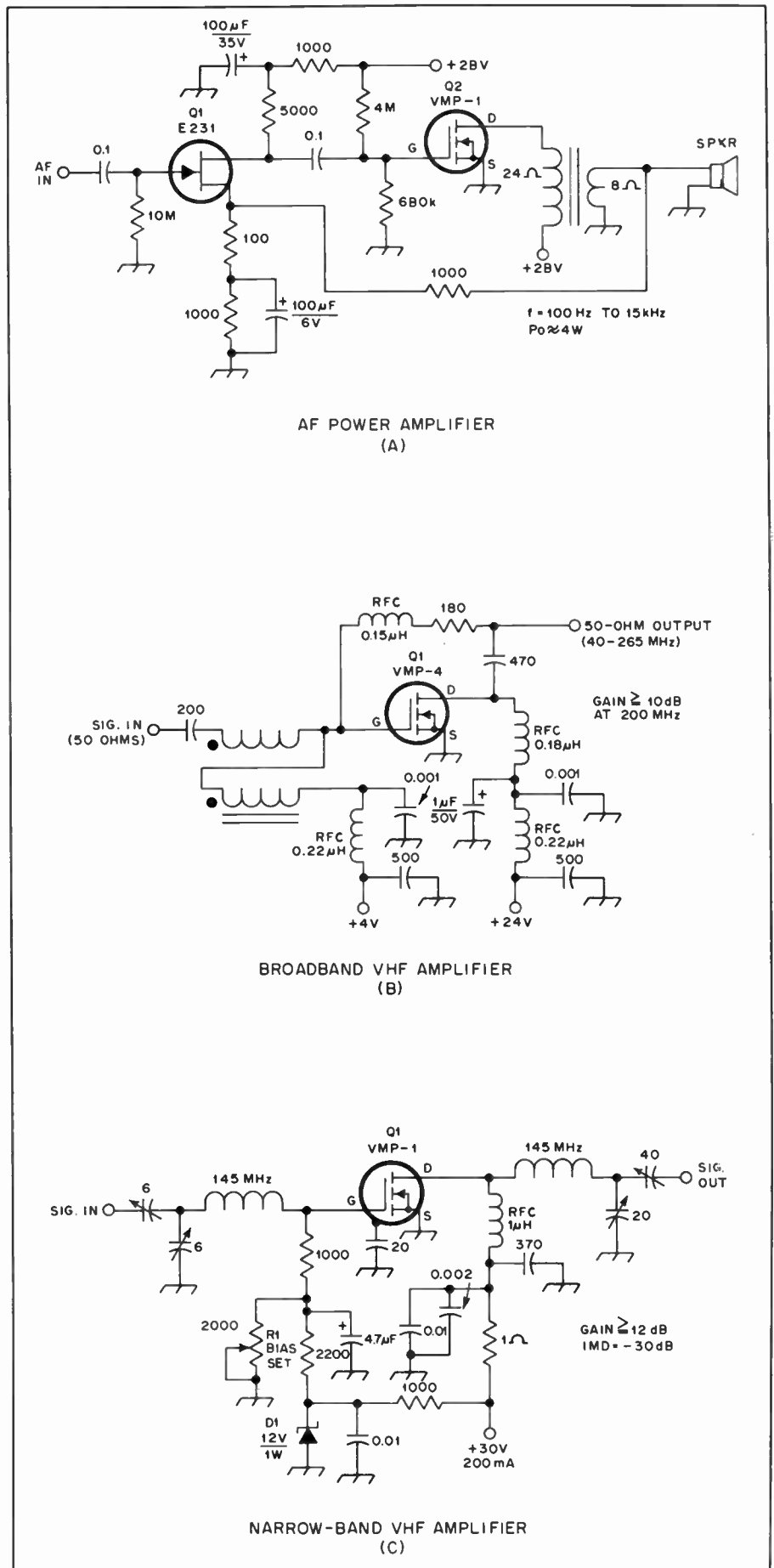


Fig. 78 — Examples of power FETs in three amplifier circuits.

flat-pack epoxy blocks. ICs may have as many as 12 or more leads which connect to the various elements on the chip.

Some of the present-day ICs are called *LSI* chips. The term LSI means *large-scale integration*. Such devices may contain the equivalent of several conventional ICs, and can have dozens of dual-in-line package (DIP) connector pins. LSI ICs are used in electronic organs, digital clocks, electronic calculators, and so on. Essentially, they are just super-size ICs.

### Some Practical Considerations

In circuits where slight extra lead lengths can be tolerated, it is prudent to install the ICs in sockets rather than solder them into the pc board directly. In

amateur work there is an occasional need to replace an IC during circuit development for a typical one-shot design. This is particularly pertinent when bargain-house ICs are purchased: Many have defects, and the task of removing an IC that is not in a socket is a task that no builder finds delightful.

When using ICs for rf work it is best to install them in a low-profile type of IC socket (minimum lead length type). The thicker sockets are suitable for dc and audio applications, where lead length is not likely to be a critical factor. Excessive lead length can cause instability. This is brought on by having numerous high-gain devices packaged physically close to one another on the common substrate: High

gain and stray lead coupling set the stage for self-oscillation!

### CMOS ICs

The term CMOS means that the IC is a *complimentary metal-oxide silicon* type of integrated circuit. Essentially, the internal workings of the device are not unlike those of MOSFETs, the latter of which were treated earlier in this chapter: MOSFETs are formed on the CMOS IC substrates.

CMOS devices consume very low power — an advantage in battery-operated equipment, especially. The transit time (propagation delay) through the FED gates of a CMOS IC is very short — ideal in logic circuits. It ranges from 25 to 50 ns in most devices. This does not imply that CMOS ICs aren't useful in linear applications: Some are designed primarily for the linear amplification of audio and rf energy (CA3600E, for one). Another salient feature of CMOS chips is low noise. Because FETs are used in these ICs the input impedance is high, making them more suitable than bipolar ICs for interfacing with comparable impedance levels outside the IC package. Fig. 81 shows the diagram of a CA3600E CMOS IC along with a block-symbol circuit for its use as a high-gain audio amplifier.

### Array ICs

One branch of the linear-IC family is known as the *IC array* group. A short course on these and other linear ICs was given by DeMaw in *QST* for January through March, 1977. Basically, the IC array is a substrate which contains a number of individual diodes or npn bipolar transistors. They differ from conventional ICs by virtue of having each of the transistors independent from one another. Each transistor base, emitter and collector is brought out of the IC package by means of its own single pin. This enables the designer to treat each transistor as a discrete device, with the advantage that each transistor has nearly identical electrical characteristics ( $f_T$ , beta,


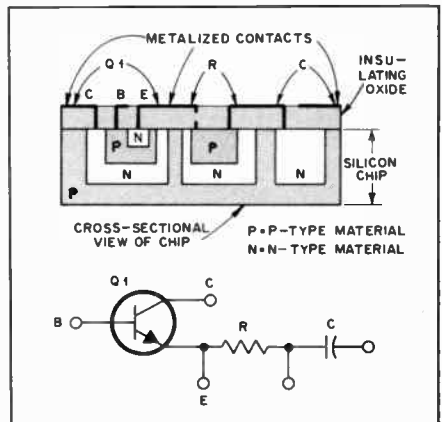


Fig. 79 — JFETs are useful in additional kinds of circuits. Here are three such examples.

Fig. 80 — Pictorial and schematic representation of a simple IC.

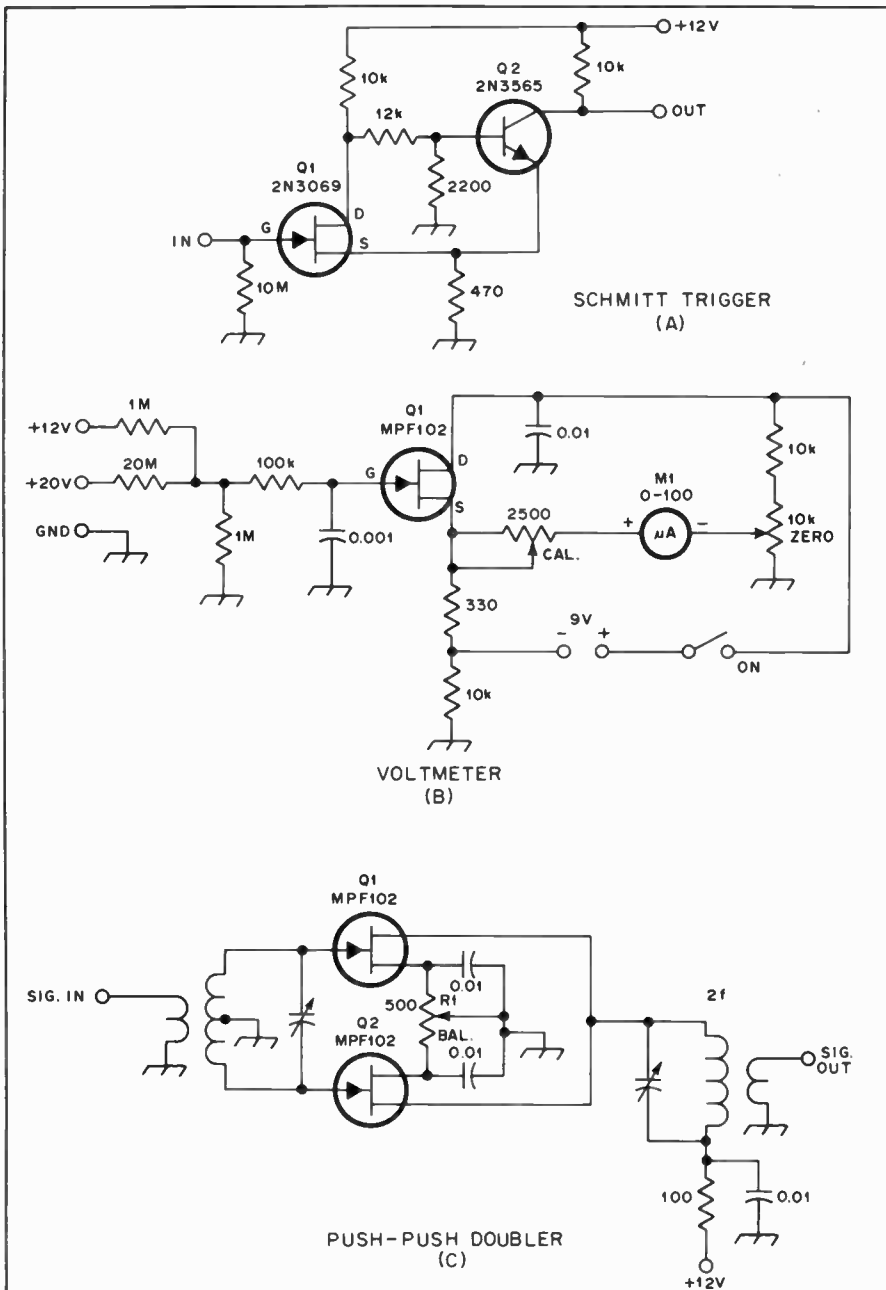

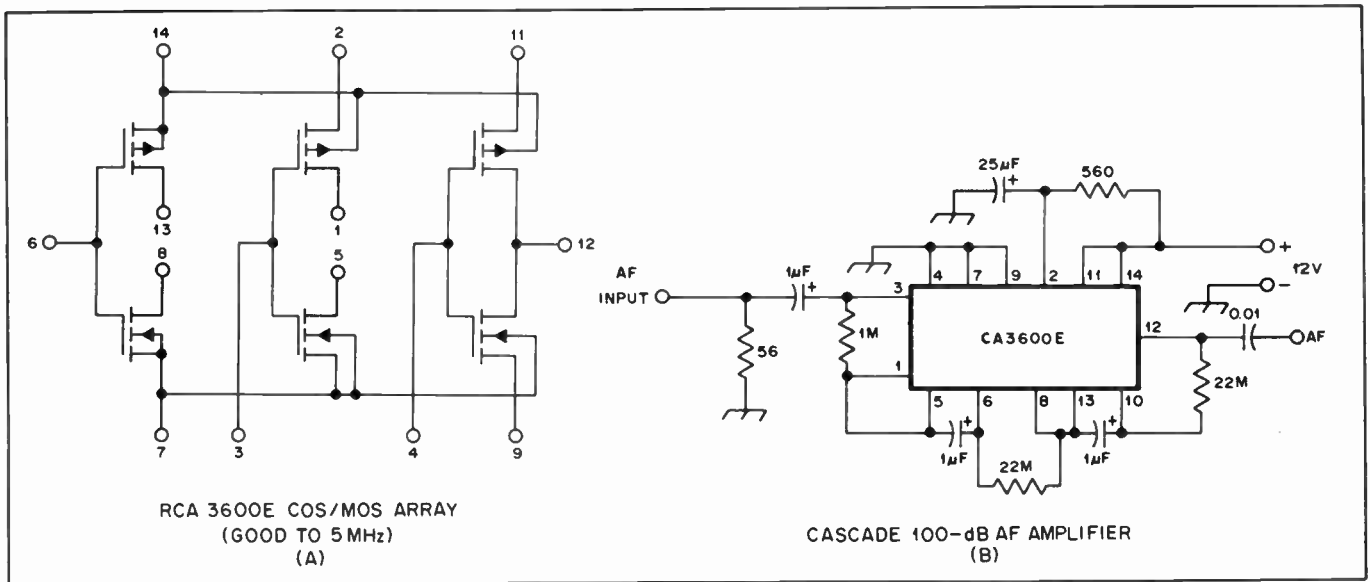


Fig. 81 — The diagram at A shows the internal workings of a CMOS IC. A 100-dB audio amplifier which employs the CA3600E is shown at B.

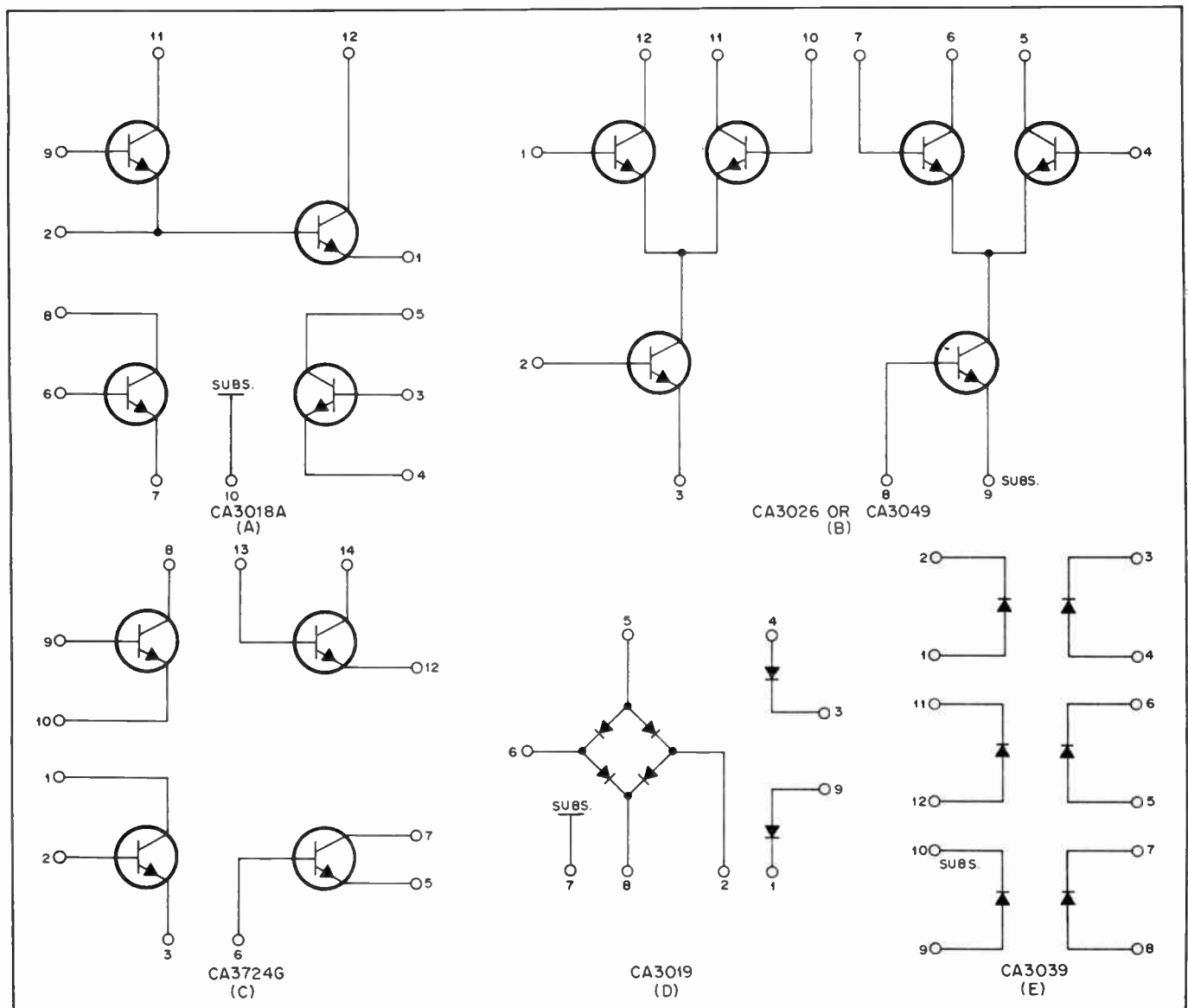


Fig. 82 — Various transistor and diode-array ICs. The configurations suggest a variety of amateur applications.

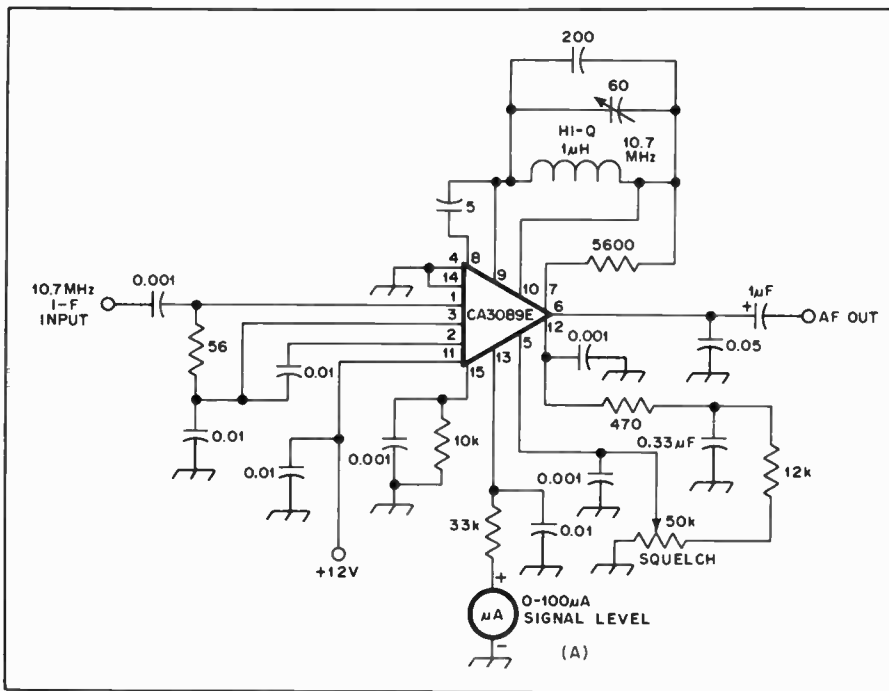


Fig. 83 — Example of a subsystem IC used as the heart of a narrow-band fm receiver.

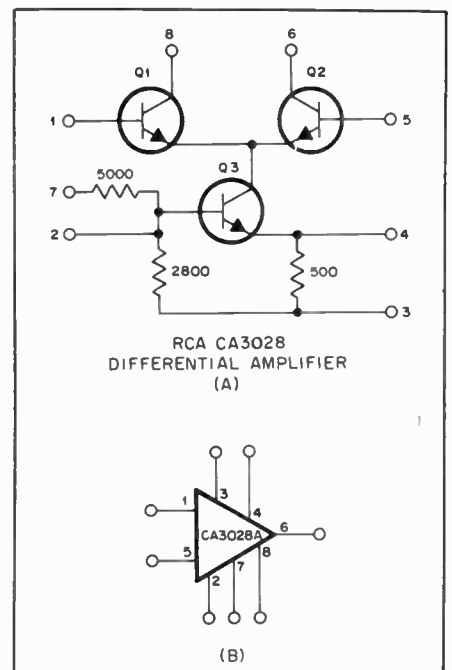


Fig. 84 — Schematic and block examples of an RCA CA3028A IC.

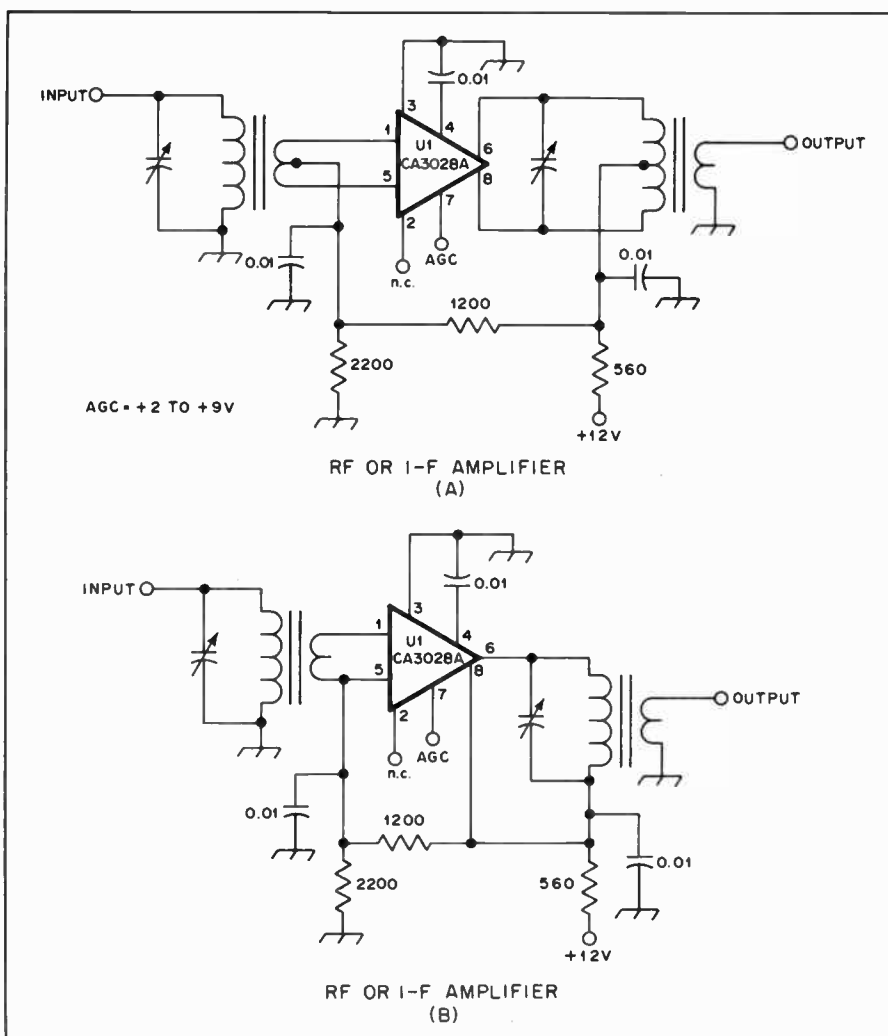


Fig. 85 — Rf and i-f amplifiers using the CA3028A IC. The example at A is balanced for ac and dc, whereas the circuit at B is balanced only for dc conditions.

dissipation rating, etc.). Some array ICs have  $f_T$  ratings as high as 1200 MHz, with maximum collector dissipation ratings as high as 1 watt. Schematic illustrations of some popular RCA array ICs are seen in Fig. 82.

**Subsystem ICs**

A branch of the linear-IC family tree is the *subsystem IC*. It is a conventional-package integrated circuit, but contains nearly as much circuitry as an LSI chip. Some of these devices represent the entire active-device circuitry for an fm or a-m radio receiver. The designer needs only to add the essential outboard components (front-end tuned circuits, i-f transformers, tuning meter, and audio power amplifier) to realize a composite piece of equipment. Other subsystem ICs may contain only the i-f amplifiers, product detectors, agc loops, and audio preamplifiers. This style of IC is sold by such manufacturers as RCA, National Semiconductor, and Plessey. Fig. 83 illustrates an example of this kind of device — the RCA CA3089E which is designed expressly for use in wide- or narrow-band fm receivers. It features a quadrature detector, and contains amplifiers, limiters, squelch circuit, metering circuit, and an af amplifier. Those interested in compact portable amateur receivers should find these devices especially interesting.

**Practical Examples**

The main disadvantage in the use of IC symbols in circuit diagrams is that the internal workings are not shown. This makes the designer work with a collection of "magic boxes." Fortunately, IC manu-

facturers publish data books which show the block symbols and pin arrangements versus the schematic diagrams of the active devices on the chips. This permits the amateur to understand what the circuit configuration is before the design work is started. It is beyond practicality to include the schematic diagrams of the ICs used in this book, but we will show the circuit of the RCA CA3028A, because it is used frequently in the following section. Fig. 84 contains the block and schematic representation of this IC.

### RF and I-F Amplifiers

Nearly every manufacturer of ICs produces chips that are suitable for use as rf/i-f amplifiers, mixers, detectors, oscillators and audio amplifiers. The circuits of Fig. 85 are examples of CA3028A rf or i-f amplifiers to which agc is applied. Maximum gain occurs when the agc voltage (IC forward bias) is at its highest potential. The IC is nearly cut off when the agc level drops below 2 volts. The circuit of Fig. 85A functions as a differential amplifier, as does the one at B. The basic difference is that dc and ac balance are featured at A, whereas only dc balance is effected at B. The gain of either stage is approximately 40 dB. Pin 2 of U1 is left floating, but is used for LO injection when the CA3028A is employed as a mixer or product detector. A Motorola MC1550G is similar to the IC shown in Fig. 85. A MC1590G is a more suitable IC for i-f amplification when greater amounts of stage gain or agc control are desired.

An example of an MC1590G amplifier is given in Fig. 86A. It is shown with agc applied to pin 2. The lower the agc voltage the higher the stage gain. This is the opposite condition from that of the CA3028A of Fig. 85, where the gain increases with elevated agc voltage. The MC1350P of Fig. 86B is a low-cost version of the MC1590G. It is shown with manual control of the gain (R1), but agc voltage can be applied instead.

### IC Mixers

Examples of IC active mixers are given in Fig. 87. At A is seen a singly balanced mixer formed by the differential transistor pair in a CA3028A. A doubly balanced mixer is illustrated at B in Fig. 87. The MC1496G contains two differential transistor pairs to permit the doubly balanced configuration. This circuit does not exactly follow the suggested one by Motorola. It has been optimized for use as a transmitting mixer by W7ZOI and KL7IAK (*Solid State Design for the Radio Amateur*, 1st edition, page 204). There are numerous other ICs which can be used as mixers. Examples of many practical circuits are given in the ARRL book just referenced.

The circuit arrangements for product detectors and balanced modulators are similar to those shown in Fig. 87. They

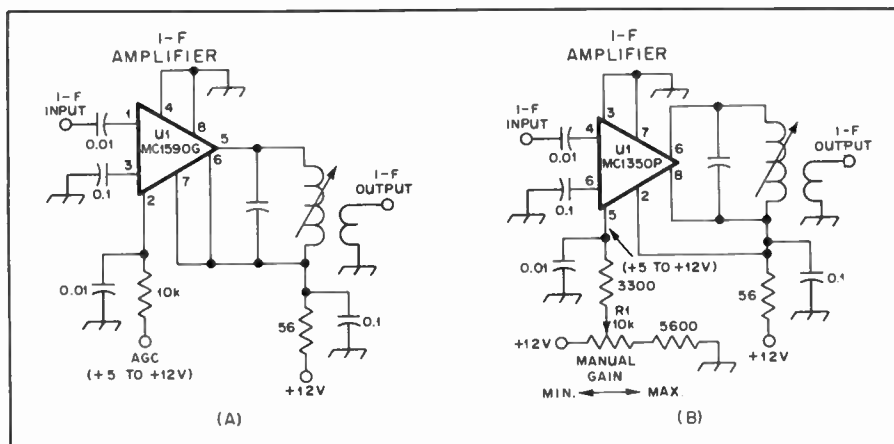


Fig. 86 — Circuit examples for Motorola IC i-f amplifiers.

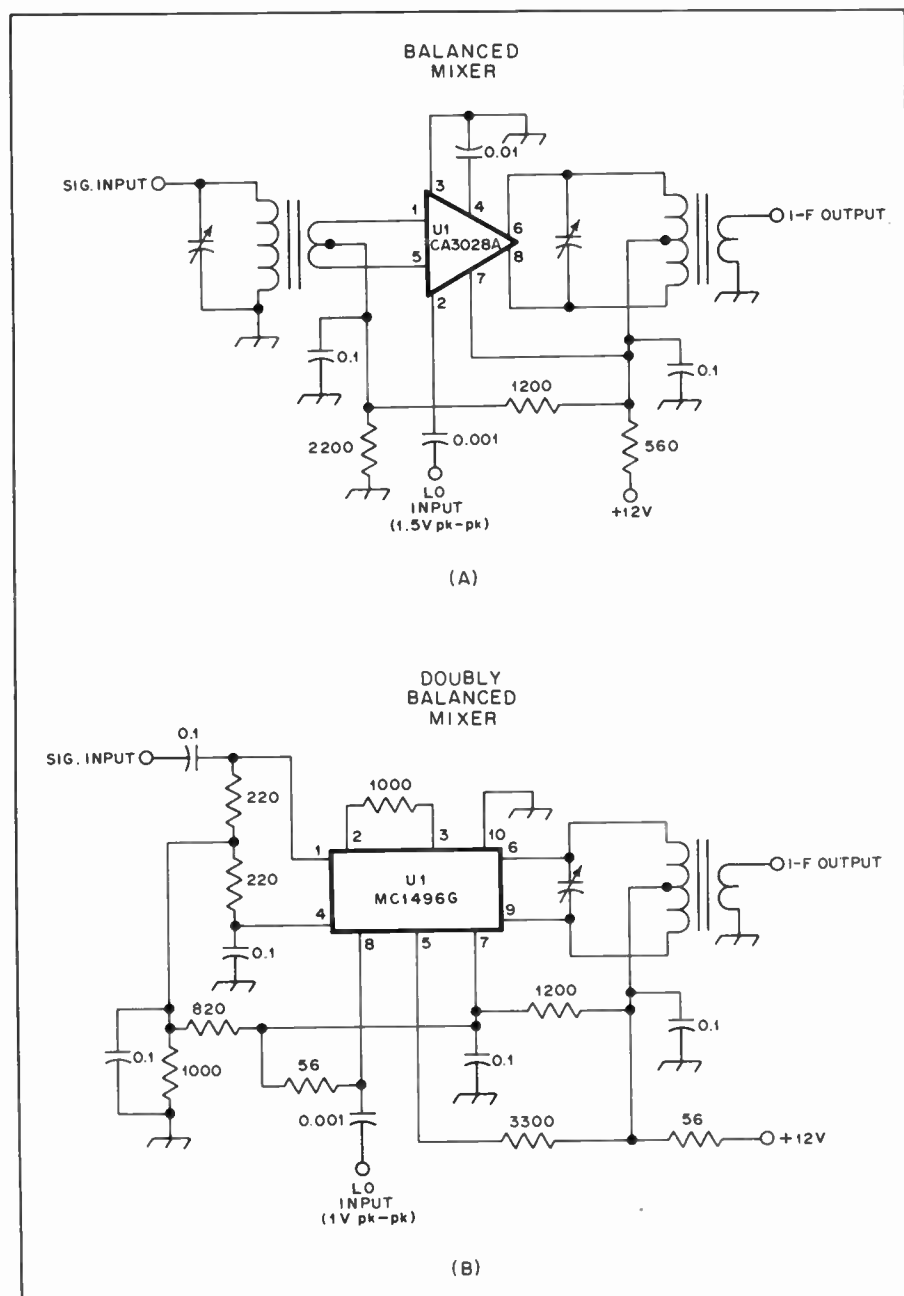


Fig. 87 — Two types of IC are shown as mixers. The one at A is a singly balanced mixer.

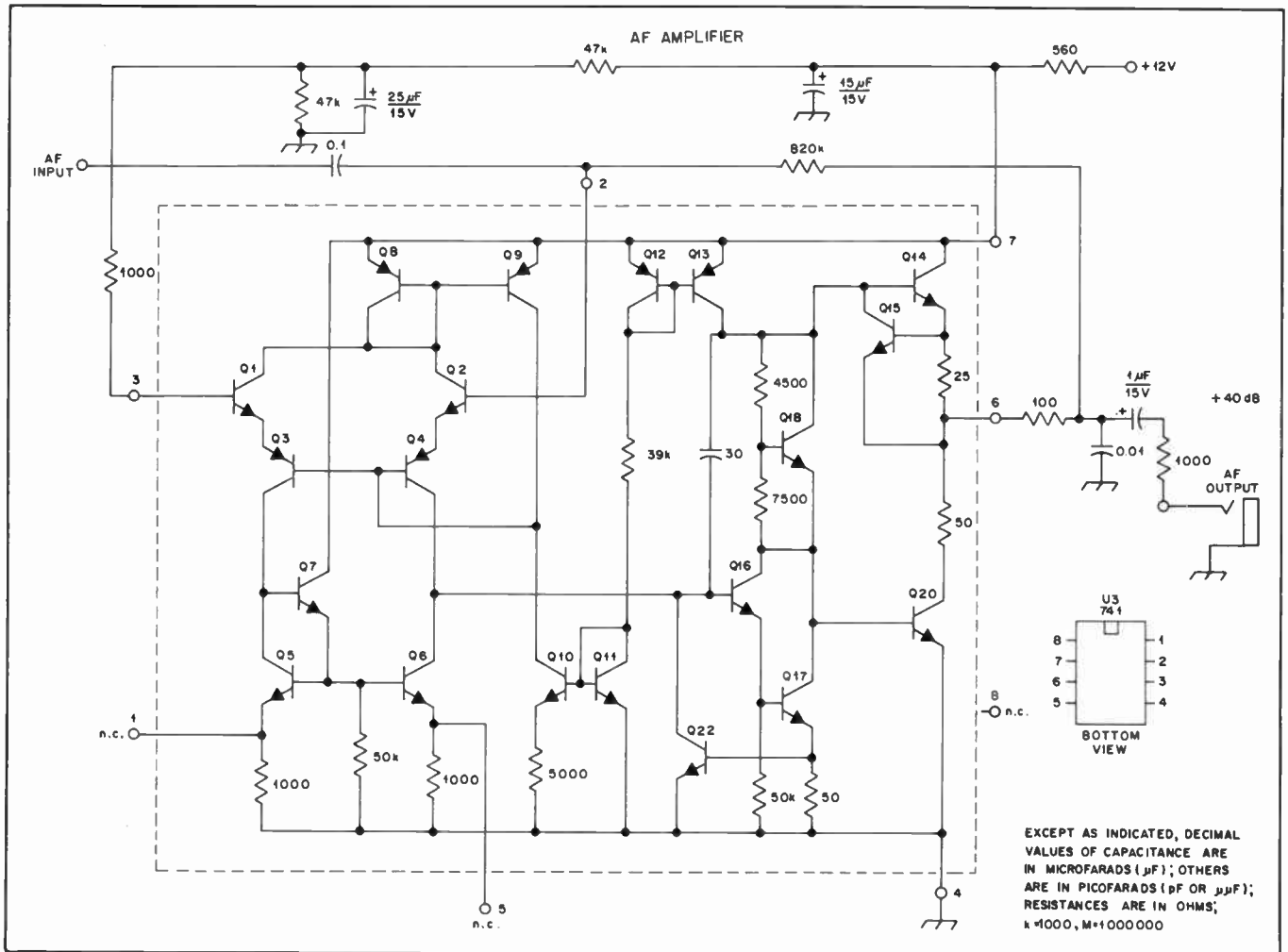


Fig. 88 — Internal circuit of a common 741 op-amp. It is shown here as a 40-dB audio amplifier.

will not be described in this text, because the primary difference between them and a regular mixer lies in the frequencies of the signals mixed (af versus rf) and the frequency of the resulting output energy.

### IC Audio Amplifiers

Practically every IC manufacturer offers a line of audio ICs. Some are for use as low-noise preamplifiers and others are capable of delivering up to a few watts of output to a loudspeaker. Most of the audio-power ICs are designed for looking directly into an 8- or 16-ohm load without the need for a matching transformer. Because these circuits are relatively mundane in nature they shall not be offered here as illustrative examples. Practical applications for audio ICs can be found in the construction projects elsewhere in this volume. Manufacturer's data sheets also provide definitive information on the use of these devices.

### Operational Amplifiers

Operational amplifiers (op amps) received their name because a host of operations can be performed with them by altering the feedback parameters. In simple terms an op amp is a device which

is capable of very high gain. It is characterized further by its differential-input dc amplifier arrangement. Basically, it can be thought of as a very precision push-pull type of amplifier. It was used at its beginning in analog computer circuits — the vacuum-tube era. The operational amplifier is perhaps the most versatile IC in the amateur and commercial field today. It would take an entire book to illustrate the many uses to which op amps can be put. Here we will merely show some basic examples. The reader is referred to Jung, *IC Op-Amp Cookbook*, by Howard Sams and Co., for an in-depth treatment of op-amp theory and practical applications.

### Some Op-Amp Basics

A theoretically perfect (ideal) op-amp would have some outstanding characteristics.

- 1) High input impedance (infinite).
- 2) Low output impedance (zero).
- 3) Infinite voltage gain.
- 4) Flat frequency response within its operating range.
- 5) With zero input signal the output is zero.

These criteria can be approached in a

practical situation, but not realized entirely.

Fig. 88 shows the circuit of a 741 op-amp. It is set up as a low-level audio amplifier with a gain of 40 dB. The components outside the dashed lines are external to the IC. This diagram clearly illustrates the complexity of the inner workings of an op amp.

Three of the more common op-amp configurations are *inverting amplifiers*, *noninverting amplifiers* and *difference amplifiers*. These modes are compared in Fig. 89. The phase relationships are compared in the examples.

Voltage gain and voltage output for an op-amp can be determined easily by means of the equations in Fig. 90. This illustrates clearly that the op-amp gain is determined by the resistors rather than by the op-amp characteristics and power supply voltage.

Fig. 91 shows the gain relationship for a noninverting op-amp. A theoretical gain of  $10^9$  is attainable from the circuits of Figs. 90 and 91. Both types of circuit find common use in amateur projects.

Fig. 92 illustrates a *difference amplifier*. A reference voltage can be applied to one



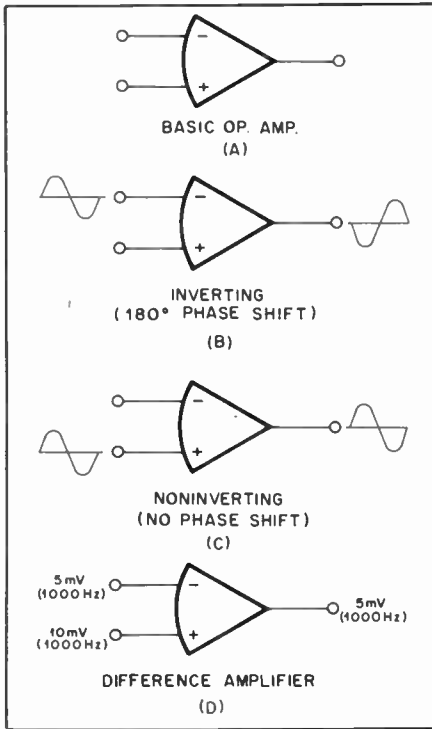


Fig. 89 — Various modes of op-amp utilization.

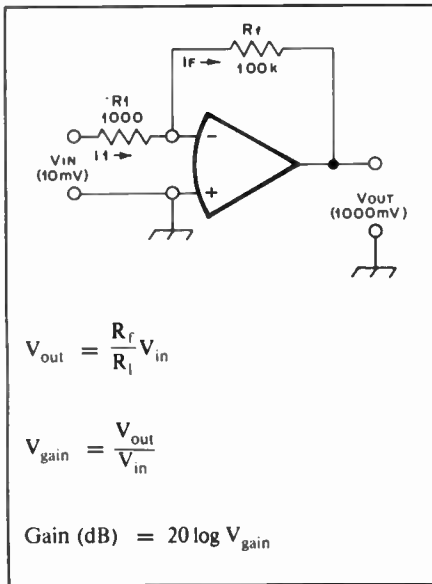


Fig. 90 — Resistance values determine the op-amp gain.

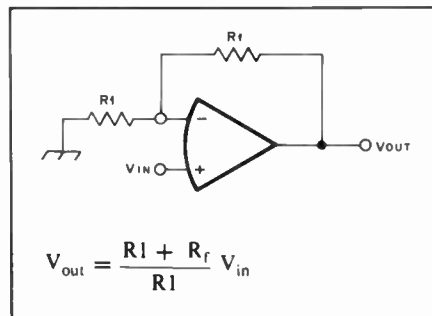


Fig. 91 — Voltage output versus voltage input for a noninverting op-amp.

of the op-amp inputs while the remaining input is fed a changing dc level (such as that which might occur across the source resistor of an FET dc amplifier). The difference in the two input voltages will appear at the op-amp output. An equation is given in Fig. 92 for determining the output voltage of this circuit.

A difference amplifier can be used to null out an unwanted ac component in a signal. Fig. 93 demonstrates how some unwanted 120-Hz energy can be removed from the desired audio voltage by deliberately feeding an equivalent amount of 120-Hz energy into the noninverting input of the op-amp. When the two 120-Hz energy levels are equal, the op-amp output at that frequency will be approximately zero. This technique is effective only when the level of the unwanted 120-Hz component remains constant.

### Op Amps as Audio Filters

One of the more common uses to which op amps are put can be seen in the RC active audio-filter field. Op amps have the distinct advantage of providing gain and variable parameters when used as audio filters. Passive filters which contain L and C elements are generally committed to some fixed-value frequency, and they exhibit an insertion loss. Finally, op amps contribute to the attainment of miniaturization which is seldom possible while employing bulky inductors in a passive type of audio filter.

Although RC active filters can be built with bipolar transistors, the modern approach is to utilize operational amplifiers (op amps). The use of an op-amp IC, such as a type 741, results in a compact filter pole which will provide stable operation. Only five connections are made to the IC, and the gain of the filter section, plus the frequency characteristic, is determined by the choice of components external to the IC.

Although there are numerous applications for RC active filters, the principal use in amateur work is that of establishing selectivity at audio frequencies. One or two poles may be used as a band-pass or low-pass section for improving the passband characteristics during ssb or a-m reception. Up to four filter poles are frequently employed to acquire selectivity for cw or RTTY reception. The greater the number of poles, up to a practical limit, the sharper the skirt response of the filter. Not only does a well-designed RC filter help to reduce QRM, it improves the signal-to-noise ratio in some receiving systems.

Considerable design data is found in the National Semiconductor Corp. application note AN72-15 in which a thorough treatment of Norton amplifiers is given, centering on the LM3900 current-differencing type of op-amp. Design information is given for high-, low-, and band-

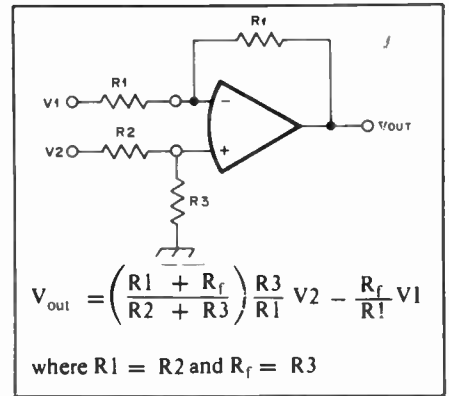


Fig. 92 — Voltage relationship for a difference amplifier.

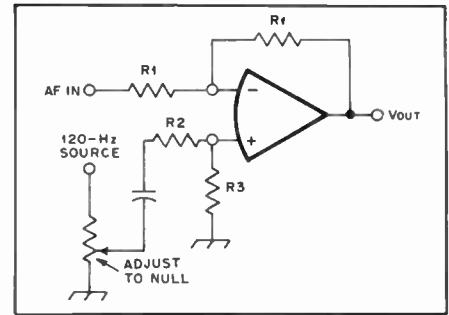


Fig. 93 — A difference amplifier can be used to null out unwanted frequency components. In this example it reduces 120-Hz hum.

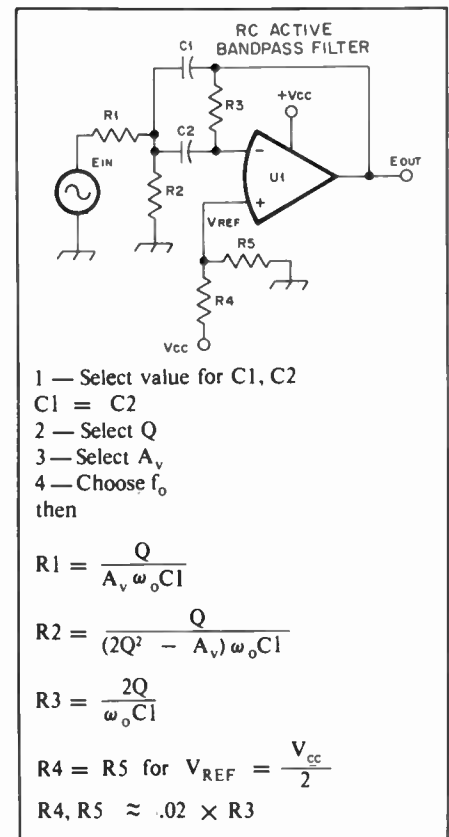


Fig. 94 — Basic circuit for an RC active bandpass filter. One pole is shown along with the fundamental equations for finding the resistance values needed.

pass types of RC active audio filters. The simplified design data presented here is based on the technique used in AN72-15.

Fig. 94 shows a single band-pass-filter pole and gives the equations for obtaining the desired values for the resistors once the gain,  $Q$ ,  $f_0$  and  $C1$ - $C2$  capacitor values are chosen.  $C1$  and  $C2$  are equal in value and should be high- $Q$ , temperature-stable components. Polystyrene capacitors are excellent for use in this part of the circuit. Disk-ceramic capacitors are not recommended.  $R4$  and  $R5$  are equal in value and are used to establish the op-amp reference voltage. This is  $V_{cc}/2$ .

$C1$  and  $C2$  should be standard values of capacitance. The filter design is less complicated when  $C1$  and  $C2$  serve as the starting point for the equations. Otherwise some awkward values for  $C1$  and  $C2$  might result. The resistance values can be "fudged" to the nearest standard value after the equations have been worked. The important consideration is that matched values must be used when more than one filter pole is employed. For most amateur work it will be satisfactory to use five percent, 1/2-watt composition resistors. If the resistor and capacitor values are not held reasonably tight in tolerance for a multipole filter, the  $f_0$  for each pole may be different, however slight. The result is a wide nose for the response, or even some objectionable passband ripple.

Fig. 95 illustrates the design of a single-pole band-pass filter. An arbitrary  $f_0$  of 900 Hz has been specified, but for cw reception the operator may prefer something much lower — 200 to 700 Hz. An  $A_v$  (gain) of 1 (unity) and a  $Q$  of 5 are stated. Both the gain and  $Q$  can be increased for a single-section filter if desired, but for a multisection RC active filter it is best to restrict the gain to 1 or 2 and use a maximum  $Q$  of 5. This will help prevent

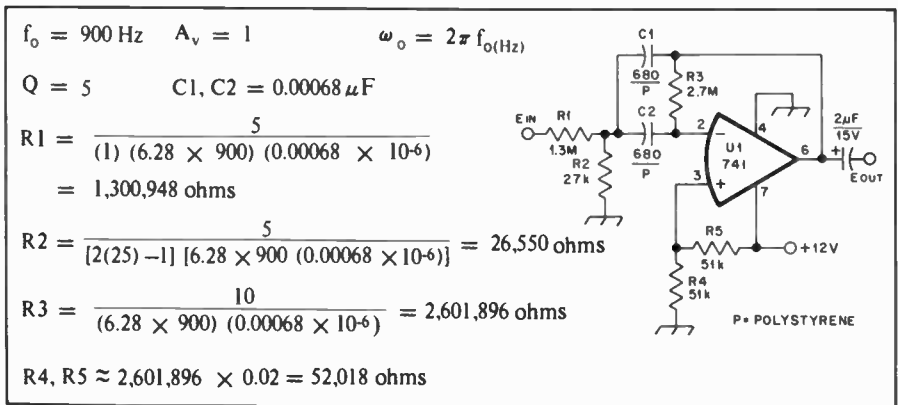


Fig. 95 — A design example based on the circuit of Fig. 94.

unwanted filter "ringing" and audio instability.

$C1$  and  $C2$  are 680-pF polystyrene capacitors. Other standard values can be used from, say, 500 to 2000 pF. The limiting factor will be the resultant resistor values. For certain design parameters and  $C1$ - $C2$  values, unwieldy resistance values may result from the equations. If this happens, select a new value for  $C1$  and  $C2$ .

The resistance values assigned to  $R1$  through  $R5$ , inclusive, are the nearest standard values to those obtained from the equations. The principal effect from this is a slight alteration of  $f_0$  and  $A_v$ .

An example of a three-pole RC active filter is seen in Fig. 96. Each filter section is a duplicate of that presented in Fig. 95.  $S1$  is used to select the number of poles required. The more poles used, the greater the selectivity. A practical limit of four poles would be typical for this style of filter.  $U1$  is a dual op amp (N5558 or equivalent). An LM747 would be useful in a four-pole filter because it is a quad op amp.

In a practical application the RC active filter should be inserted in the low-level audio stages. This will prevent overloading the filter during the reception of strong signals. Most op amps are fairly noisy, so it is recommended that the audio filter be placed after a low-noise audio preamplifier, the latter of which immediately follows the detector. The receiver af gain control should be used between the audio preamplifier and the input to the RC active filter for best results. If audio-derived agc is used in the receiver, the RC active filter will give best performance when it is contained within the agc loop.

Filters of this type are invaluable during weak-signal cw work such as scatter, moonbounce and 160-meter DXing. For that matter, the filter is an excellent adjunct to any receiver during routine cw of ssb work. The circuit of Fig. 3 can greatly enhance cw operation when it is used with receivers which do not have i-f filters for cw reception. The RC active filter is a superb low-cost substitute for a 500- or 600-Hz i-f filter.

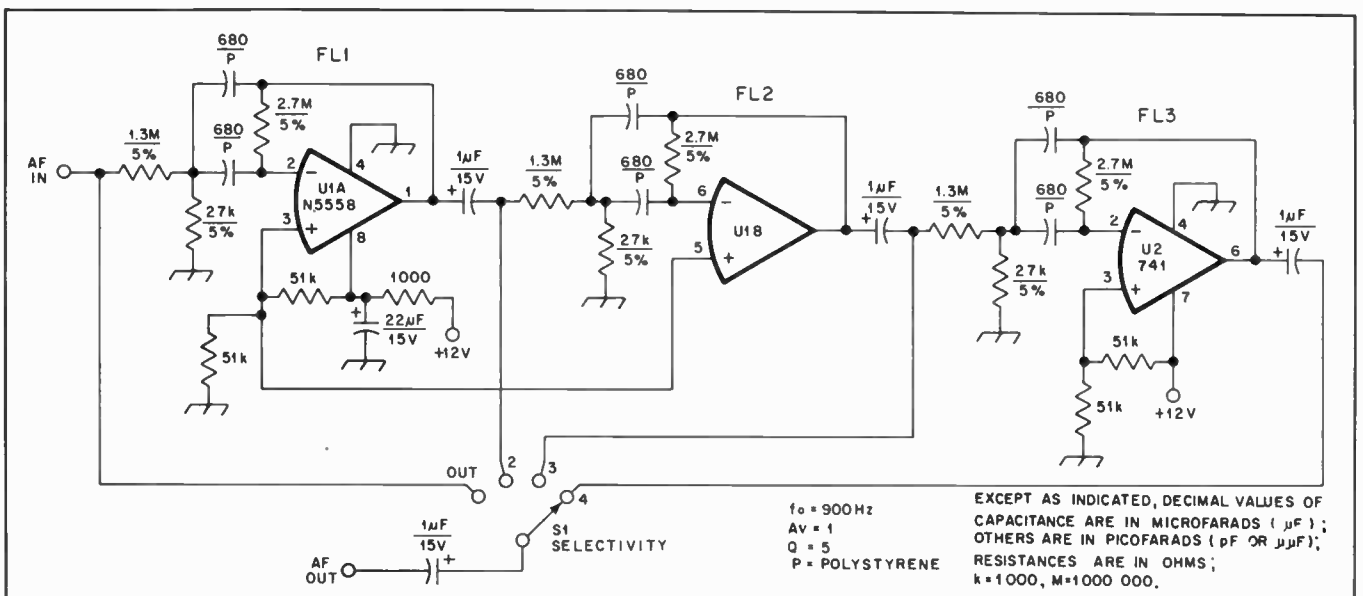


Fig. 96 — Two or more poles of RC filter can be used in cascade to increase the skirt selectivity. This illustration shows a three-pole bandpass filter. A selectivity switch has been included to permit choosing from zero to three filter sections.

# Digital-Logic Integrated Circuits

Digital logic is the term used to describe an overall design procedure for electronic systems in which "on" and "off" are the important words, not "amplification," "detection," and other terms commonly applied to most amateur equipment. It is "digital" because it deals with discrete events that can be characterized by digits or integers, in contrast with linear systems in which an infinite number of levels may be encountered. It is "logic" because it



Fig. 97 — From outward appearances, these three ICs appear to be identical. Although each is a J-K flip-flop, there are differences in their characteristics. Pictured at the left is a Texas Instruments SN74H72N integrated circuit, called a J-K master slave flip-flop. Shown in the center is a Motorola MC1927P IC which is a 120 MHz ac-coupled J-K flip-flop. Both of these ICs might be considered "universal" flip-flops, for they may be used in a variety of ways. Shown at the right is a Motorola MC726P, a simple J-K flip-flop.

follows mathematical laws in which "effect" predictably follows "cause."

Just like linear integrated circuits, digital ICs are manufactured in such a way that the internal components are interconnected for particular applications. Packaging of the digital ICs is the same for their linear counterparts, with the full package range pictured earlier being used. From outward appearances, it would be impossible to tell the difference between the two types of ICs except from the identification numbers (Fig. 97).

Linear ICs are constructed to respond to continuously variable or analog signals, such as in an amplifier. Digital devices, on the other hand, generally have active components operating only in either of two conditions — cutoff or saturation. Digital ICs find much application in on-off switching circuits, as well as in counting, computation, memory-storage, and display circuits. Operation of these circuits is based on binary mathematics, so words such as "one" and "zero" have come into frequent use in digital-logic terminology. These terms refer to specific voltage levels, and vary between manufacturers and devices. Nearly always, a "0" means a voltage near ground, while "1" means whatever the manufacturer specifies. One must distinguish between "positive logic" and "negative logic." In positive logic, a 1 is more positive than a 0, though both may be negative voltages. In negative logic, the reverse is true. Often the terms "high" and "low" are used in reference to these voltage levels. The definitions of these terms are the same for both positive and negative logic. A "high" is the most positive or least negative potential, while a "low" is the least positive or most negative.

For practical use in some applications it is desirable to convert binary data into decimal equivalents, such as in electronic counting and display systems. In other applications, such as for the graphic recording or metering of summations or products of integers, it is convenient to convert the digital data into analog equivalents. Specialized integrated circuits designed to perform these functions are also considered to be included in the digital-IC category.

## Logic Symbols

With modern microcircuit technology, thousands of components can be packaged in a single case. Rather than showing a forest of transistors, resistors, and diodes, logic diagrams show symbols based on the four distinctive shapes given in Fig. 98 at A through D. These shapes may be "modified" or altered slightly,

according to specific functions performed. Examples are shown at E through H of Fig. 98.

The square, Fig. 98D and H, may appear on logic diagrams as a rectangle. This symbol is a somewhat universal one, and thus must be identified with supplemental information to indicate the exact function. Internal labels are usually used. Common identification labels are

- FF — flip-flop
- FL — flip-flop latch
- SS — single shot
- ST — Schmitt trigger

Other logic functions may also be represented by the square or rectangle, and the label should adequately identify the function performed. Unique identifying shapes are used for gates and inverters, so these need no labels to identify the *function*. Hardware- or package-identification information may appear inside any of the symbols on logic diagrams.

## Types of Digital ICs

Digital integrated circuits perform a variety of functions, but these functions can generally be cataloged into just a few categories: Gates, inverters, flip-flops, drivers and buffers, adders and subtractors, registers, and memories, plus the special-purpose ICs as mentioned earlier — decoders and converters. Some of these types, such as adders and subtractors, registers, and memories, find use primarily in computer systems. More universally used types of ICs are the inverters, gates and flip-flops.

## Inverters

A single chip in one IC package may be designed to perform several functions, and these functions can be independent of each other. One example of an IC of this type is Texas Instruments' SN7404, which bears the name, "hex inverter." This IC contains six identical inverter sections. The schematic diagram of one section is shown in Fig. 99A. In operation, 4.5 to 5.5 volts are applied between  $+V_{cc}$  are ground. For this device in positive-logic applications, a 0 is defined as any potential less than approximately 0.7 volt, and a 1 is any value between approximately +4 and +5 volts. With a logic 0 applied at the input, Q1 will conduct current. This will cause Q2 to be near cutoff, in turn biasing the "totem pole" arrangement of Q3 into heavy conduction and Q4 near cutoff. As a result, the output will be at a potential near  $+V_{cc}$ , or a logic 1. If the 0 at the

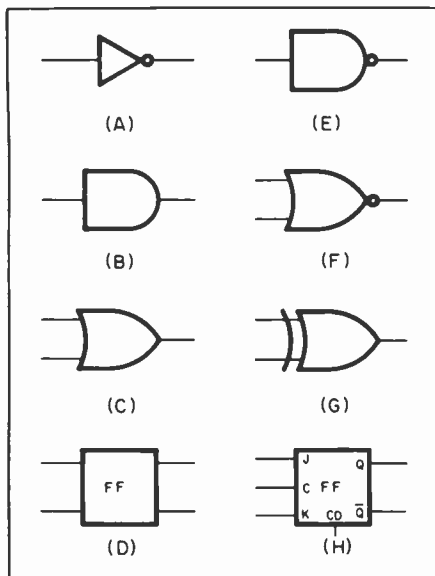


Fig. 98 — Distinctive symbols for digital logic diagrams. At A is shown an inverter, at B an AND gate, at C an OR gate, and at D a flip-flop. Additions to these basic symbols indicate specific functions performed. A small circle, for example, placed at the output point of the symbol, denotes that inversion occurs at the output of the device. Shown at E is an inverting AND or NAND gate, and at F is an inverting OR or NOR gate. At G is the symbol for an exclusive OR gate. The symbol at H represents a J-K flip-flop.

input is replaced by a 1, the conduction state of each transistor reverses and the circuit output drops nearly to ground potential; a 0 appears at the output. The input diode protects the input circuitry by clamping any negative potential to approximately  $-0.7$  V, limiting the conduction of Q1 to a safe level. The output diode is required to assure that Q3 is cut off when the output is at a logic 0.

Thus, the output of the circuit in Fig. 99A is always the opposite or *complement* of the input logic level. This is sometimes called a NOT gate, because the input and output logic levels are *not* the same, under any conditions of operation.

Shown at the right in Fig. 99A is the logic symbol for the inverter. In all logic symbols, the connections for  $+V_{cc}$  and the ground return are omitted, although they are understood to be made. The proper connections are given in the manufacturer's data sheets, and, of course, must be made before the device will operate properly. In the case of all multiple-function ICs, such as the hex inverter, a single ground connection and a single  $+V_{cc}$  connection suffice for all sections contained in the package.

### Gates

Another example of an IC containing several independent functions in one package is Texas Instruments' SN7400, a quad two-input gate. Four gates are contained in one chip. The schematic diagram and logic symbols for a gate section are shown at B in Fig. 99. As with the SN7404, a supply of 4.5 to 5.5 volts is used; for positive logic a 0 is a potential less than 0.7 volt, and a 1 is a potential between 4 and 5 volts.

It may be seen from Fig. 99 that the circuit at B is almost the same as that at A. The difference is that Q5 is a multiple-emitter transistor, with one circuit input at each emitter. If either or both inputs are at ground potential, current will flow through the 4000-ohm base resistor of Q5. The base voltage will be equal to the internal emitter-base voltage drop in Q5, and the collector will be at a low level. Through low conduction of Q6 and Q8 and heavy conduction of Q7, the output will be a logic 1. Only when both inputs, 1 and 2, are at a logic 1 level will there be base-collector current flowing in Q5 to cause a 0 (or a NOT 1) to appear at the output. The NOT functions are usually written with a bar over them, so 1 means the same thing as NOT 1, and is usually expressed as NOT 1 when reading the term.

Logic-circuit operation can be expressed with equations. *Boolean algebra* a form of binary mathematics, is used. These equations should not be confused with ordinary algebraic equations. The logic equation for the operation of the circuit in Fig. 99B is  $1 \cdot 1 = \bar{1}$ . The dot means AND. In plain words, the equa-

tion says that a 1 at input 1 and input 2 will yield a NOT 1 at the output. This is equivalent to saying the circuit is an inverting AND gate, or a NOT AND gate. This latter is usually contracted to NAND gate, the name by which the circuit is known.

If the circuit of Fig. 99B is used with negative logic, circuit operation remains the same; only the definitions of terms are changed. A logic 1, now, is a voltage level less than 0.7, and a 0 is a level between 4 and 5 volts. If a logic 1 is applied at either input, 1 or 2, the output will be near  $+V_{cc}$ , which is a logic 0 or NOT 1. The equation for this operation is  $1 \vee 1 = 1$ , where the little  $\vee$  means OR. Sometimes "+" is used instead of " $\vee$ ." In this way, with negative logic, the circuit becomes an inverting OR gate, a NOT OR gate, more commonly called a NOR gate. Some manufacturers' literature refers to this type of device as a NAND/NOR gate, because it performs either function, although the usual custom is to name the IC function based on positive-logic definitions.

### Flip-Flops

It is not necessary for the various functions on a single chip to be identical.

Texas Instruments' SN7490 IC, a decade up-counter, contains four flip-flops, a two-input AND gate, and two two-input NAND gates. These functions are interconnected to provide divide-by-10 operation, with ten input pulses required for every output pulse which appears. Intermediate outputs are also provided (in binary-coded form) so that the number of pulses which have entered the input can be determined at all times. These binary-coded decimal (BCD) outputs, after decoding, may be used to operate decimal-readout indicators.

The term, *medium-scale integration* (MSI) is frequently applied to ICs such as this decade up-counter, which contains the equivalent of 15 or more gates on a single chip. *Large-scale integration* (LSI) describes ICs containing the equivalent of 100 or more gates on a single chip. These terms, when applied to a particular IC, convey an idea of the complexity of the circuitry.

A flip-flop is a device which has two outputs that can be placed in various 1 and 0 combinations by various input schemes. Basically, one output is a 1 when the other is a 0, although situations do occur (sometimes on purpose) where both

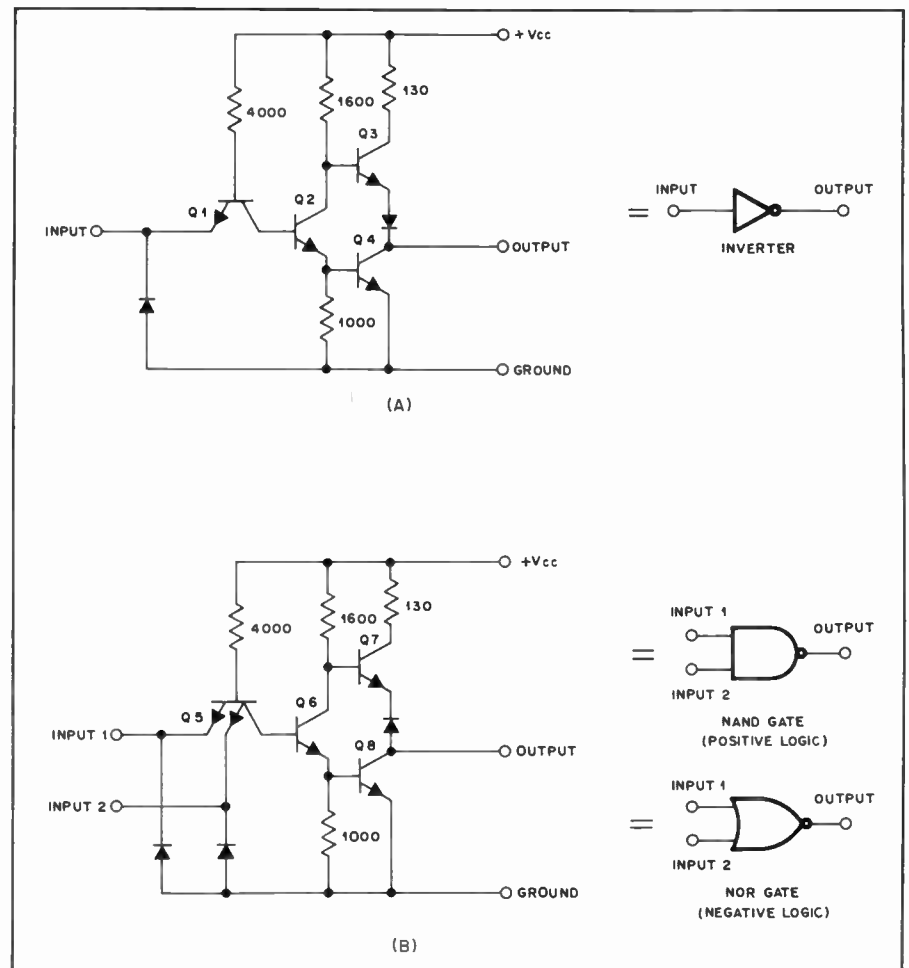


Fig. 99 — Digital circuits and their equivalent logic symbols (see text). Indicated resistor values are typical. Identification of transistors is for text reference only; these are *not* discrete components.



outputs are alike. One output is called the Q output, or "set" output, while the other is the Q(NOT Q) or "reset" output. If  $Q = 1$  and  $Q = 0$ , the flip-flop is said to be "set" or in the "1 state," while for the reverse, the flip-flop is "reset," or "cleared," or in the "0 state." A variety of inputs exist, from which the flip-flops derive their names.

The RS flip-flop is the simplest type. Its outputs change directly as a result of changes at its inputs. The type T flip-flop "toggles," "flips," or changes its state during the occurrence of a T pulse, called a clock pulse. The T flip-flop can be considered as a special case of the J-K flip-flop described later. The type D flip-flop acts as a storage element. When a clock pulse occurs, the complementary status of the D input is transferred to the Q output. The flip-flop remains in this state even though the input may change, as it can change states only when a clock pulse occurs.

Although there is some disagreement in the nomenclature, a J-K flip-flop is generally considered to be a toggled or clocked R-S flip-flop. It may also be used as a storage element. The J input is frequently called the "set" input; the K is called the "clear" input (not to be confused with the clock input). The clock input is called *c*. A clear-direct or  $C_D$  input which overrides all other inputs to clear the flip-flop to 0 is provided in most J-K flip-flop packages. The logic symbol for the J-K flip-flop is shown in Fig. 98 D.

There are essentially two types of flip-flop inputs, the dc or level-sensitive type, and the "ac" or transition-sensitive type. It should not be concluded that an ac input is capacitively coupled. This was true for the discrete-component flip-flops but capacitors of relatively large value just do not fit into microcircuit dimensions. The construction of an ac input uses the "master-slave" principle, where the actions of a master flip-flop driving a slave flip-flop are combined to produce a shift in the output level during a transit of the input.

### Digital-Logic IC Families

There are seven popular families or types of ICs that are (or were) seeing widespread use. Each family has its own inherent advantages and disadvantages. Each is geared to its own particular market, meeting a specific set of needs.

### Resistor-Transistor Logic — RTL

The RTL family was the first to gain wide usage in amateur projects, and was known primarily for its economy. This family is rapidly becoming obsolete. It is well named, since RTL ICs contain resistors and transistors exclusively.

Advantages of the RTL family were economy, ease of use in system designs, ease of interface with discrete components, and high speed-power product.

Disadvantages were low immunity to voltage noise (transients, rf pickup, and the like), and relatively low *fanout* (the number of loads that may be connected to an output before performance is degraded). The RTL family requires a supply of 3.0 to 3.6 volts.

### Diode-Transistor Logic — DTL

DTL ICs contain diodes, as well as resistors and transistors. Early DTL ICs used design criteria carried over from the use of discrete components, where diodes were inexpensive compared to transistors. These ICs required negative and positive voltage sources. Later DTL ICs are of a modified design which lends itself more easily to IC processing. Performance characteristics are also enhanced, with less input current being required, and only a single voltage source needed. Members of the DTL family are limited generally to gates. Advantages of this family are low power dissipation, compatibility with TTL (see later section), low cost, ease of use in system design, ease of interface with discrete circuits, and relatively high fanout. DTL disadvantages are low noise immunity, especially in the high state where the input impedance is relatively high, rapid change in voltage thresholds with temperature, speed slowdown with capacitive loading, and lower speed capabilities than some other families. The DTL family requires a supply voltage of 5.

### High-Threshold Logic — HTL

HTL devices are designed for high noise immunity. The circuit form is the same as DTL except that breakdown (Zener) diodes are used at the inputs. Higher supply voltages and higher power dissipations accompany the HTL family. These ICs find applications in industrial environments and locations likely to have high electrical noise levels. Advantages are high noise immunity, stable operation over very large temperature ranges, interfaces easily with discrete components, electromechanical components, and linear functions (operational amplifiers and multipliers), and a constant threshold-versus-temperature characteristic. Disadvantages are higher cost than other families, and relatively high power dissipation. The HTL family requires a supply voltage of 15.

### Transistor-Transistor Logic — TTL

TTL has characteristics that are similar to DTL, and is noted for many complex functions and the highest available speed of any saturated logic. The circuits of Fig. 99 are of the TTL family, sometimes called  $T^2L$  (T squared L). TTL may be thought of as a DTL modification that results in higher speed and driving capability. It is noted for better noise immunity than that offered by DTL, and is more effective for driving high-capacitance loads because of its low output im-

pedance in both logic states.

TTL ICs fall into five categories, relating to their speed capability and power requirements. Various manufacturing techniques are used to increase the speed, including gold doping and incorporation of high-speed Schottky diodes and diode-clamped transistors on the chips. "Plain" TTL ICs are identified by 5400- or 7400-series numbers and operate at speeds to 35 MHz. High-speed ICs are identified with the letter H, 54H00- or 74H00-series numbers. The chief schematic differences are that the H versions use a Darlington pair in place of the transistors identified as Q3 and Q7 in Fig. 99, and lower resistance values are used. These differences provide for faster operation, up to 50 MHz, but the H versions require higher current from the power supply. The letter L is used to identify low-power ICs, the 54L00 or 74L00 series. Resistance values are higher than those shown in Fig. 99, although the circuit itself is essentially identical for equivalent types. With higher resistances, less current is required from the power supply and less current at gate inputs to pull the input level down to a logic low. The speed of the L series is the lowest of the five TTL categories, only 3 MHz. Schottky-barrier, diode-clamped transistors are used in the 54S00 and 74S00 TTL series. These ICs operate at frequencies as high as 125 MHz. The use of a Darlington pair is made in each gate, as in the H series of the family. The low-power Schottky series of TTL ICs is designated by the letters LS, i.e., 54LS00 and 74LS00. In addition to using higher-value resistors than the S series, there are other significant circuit differences aimed at providing low power consumption without serious loss of operating speed; up to 45 MHz is typical. It should be noted that because of speed differences, "equivalent" types of the various series of the TTL family may not be interchangeable in all circuit applications.

In addition to TTL family advantages mentioned earlier, TTL is compatible with various other families. Multiple sources and extensive competition have resulted in very low prices for TTL devices. Disadvantages are that more care is required in the layout and mechanical design of systems because of its high speed, and additional capacitors are required for bypassing because of switching transients. The TTL family requires a supply of 5 volts.

### Emitter-Coupled Logic — ECL

ECL has the highest speed of any of the logic forms. It is sometimes called current-mode logic. This family is different from standard saturating logic in that circuit operation is analogous to that of some linear devices. In this case, the transistors do not saturate and the logic swings are reduced in amplitude. Very

## Abbreviated Semiconductor Symbol List

### Field-Effect Transfer Symbols

A	— Voltage amplification
$C_c$	— Intrinsic channel capacitance
$C_{ds}$	— Drain-to-source capacitance (includes approximately 1-pF drain-to-case and interlead capacitance)
$C_{gd}$	— Gate-to-drain capacitance (includes 0.1-pF interlead capacitance)
$C_{gs}$	— Gate-to-source interlead and case capacitance
$C_{iss}$	— Small-signal input capacitance, short circuit
$C_{rss}$	— Small-signal reverse transfer capacitance, short circuit
$g_{fs}$	— Forward transconductance
$g_{is}$	— Input conductance
$g_{os}$	— Output conductance
$I_D$	— Dc drain current
$I_{DS(OFF)}$	— Drain-to-source OFF current
$I_{GSS}$	— Gate leakage current
$r_c$	— Effective gate series resistance
$r_{DS(ON)}$	— Drain-to-source ON resistance
$r_{gd}$	— Gate-to-drain leakage resistance
$r_{gs}$	— Gate-to-source leakage resistance
$V_{DB}$	— Drain-to-substrate voltage
$V_{DS}$	— Drain-to-source voltage
$V_{GB}$	— Dc gate-to-substrate voltage
$V_{GB}$	— Peak gate-to-substrate voltage
$V_{GS}$	— Dc gate-to-source voltage
$V_{GS}$	— Peak gate-to-source voltage
$V_{GS(OFF)}$	— Gate-to-source cutoff voltage
$Y_{fs}$	— Forward transadmittance $\approx g_{fs}$
$Y_{os}$	— Output admittance
$Y_L$	— Load admittance

### Bipolar Transistor Symbols

$C_{ibo}$	— Input capacitance, open circuit (common base)
$C_{ieo}$	— Input capacitance, open circuit (common emitter)
$C_{obo}$	— Output capacitance, open circuit (common base)
$C_{oeo}$	— Output capacitance, open circuit (common emitter)
$f_c$	— Cutoff frequency
$f_T$	— Gain-bandwidth product (frequency at which small-signal forward current-transfer ratio, common emitter, is unity or 1)
$g_{me}$	— Small-signal transconductance (common emitter)
$h_{FB}$	— Static forward-current transfer ratio (common base)
$h_{fb}$	— Small-signal forward-current transfer ratio, short circuit (common base)
$h_{FE}$	— Static forward-current transfer ratio (common emitter)
$h_{fe}$	— Small-signal forward-current transfer ratio, short circuit (common emitter)
$h_{IE}$	— Static input resistance (common emitter)
$h_{ie}$	— Small-signal input impedance, short circuit (common emitter)
$I_b$	— Base current
$I_c$	— Collector current
$I_{CBO}$	— Collector-cutoff current, emitter open

### Bipolar Transistor Symbols

$I_{CEO}$	— Collector-cutoff current, base open
$I_E$	— Emitter current
MAG	— Maximum available amplifier gain
$P_{CE}$	— Total dc or average power input to collector (common emitter)
$P_{OE}$	— Large-signal output power (common emitter)
$R_L$	— Load resistance
$R_s$	— Source resistance
$V_{BB}$	— Base-supply voltage
$V_{BC}$	— Base-to-collector voltage
$V_{BE}$	— Base-to-emitter voltage
$V_{CB}$	— Collector-to-base voltage
$V_{CBO}$	— Collector-to-base (emitter open)
$V_{CC}$	— Collector-supply voltage
$V_{CE}$	— Collector-to-emitter voltage
$V_{CEO}$	— Collector-to-emitter voltage (base open)
$V_{CE(sat)}$	— Collector-to-emitter saturation voltage
$V_{EB}$	— Emitter-to-base voltage
$V_{EBO}$	— Emitter-to-base voltage (collector open)
$V_{EE}$	— Emitter-supply voltage
$Y_{fe}$	— Forward transconductance
$Y_{ie}$	— Input admittance
$Y_{oe}$	— Output admittance

high speeds can be attained because of the small voltage swings and the use of nonsaturating transistors. The input circuitry of ECL devices is of the nature of a differential amplifier, resulting in much higher input impedances than saturated logic devices. Emitter-follower outputs are of low impedance with high fanout capabilities, and are suited for driving 50-ohm transmission lines directly. Disadvantages are higher power dissipation, less noise immunity than some saturated logic, translators are required for interfacing with saturated logic, and slowed-down operation with heavy capacitive loading. The ECL family requires a supply of  $-5.2$  volts.

### Metal-Oxide Semiconductors (MOS)

Digital MOS devices are gaining significance in industrial applications. Large, complex repetitive functions, such as long shift registers, high-capacity memories, and microprocessors have proved very practical. Gates and basic logic circuits have not become as popular, because they exhibit lower drive capability than other IC families. Input impedances to these devices are essentially capacitive (an open circuit for dc). This feature allows very high fanout where speed is not a consideration. Bidirectional devices give more flexibility to the circuit designer. MOS technology results in the lowest cost per bit for memories and long shift registers, because many more functions can be contained on a given chip size than in bipolar devices. Disadvantages are that devices must be handled more carefully

than bipolar ICs because excessive static electricity can destroy the narrow gate oxide, even with internal breakdown-diode input protection. Drive capability is limited because of the high output impedances characteristic of these devices. Most MOS ICs are manufactured as p-channel devices, although microprocessors and their associated devices are usually n-channel devices.

### Complementary Metal-Oxide Semiconductor — CMOS

CMOS technology employs both p-channel and n-channel devices on the same silicon substrate. Both types are enhancement-mode devices; that is, gate voltage must be increased in the direction that inverts the surface in order for the device to conduct. Only one of the two complementary devices of a circuit section is turned on at a time, resulting in extremely low power dissipation. Dissipation is primarily from the switching of devices through the active region and the charging and discharging of capacitances. Advantages are low power dissipation, good noise immunity, very wide power supply voltage variations allowed, high fanout to other CMOS devices, and full temperature-range capabilities. Disadvantages are restricted interfacing capabilities because of high output impedance, and medium to high cost. The CMOS family requires a supply of 1.5 to 16 volts, 10 volts being nominal.

### Special Digital ICs

In addition to the logic families

mentioned above, other families are being developed (sometimes on a speculative basis) and are seeing comparatively limited use. One such family is integrated injection logic, or I<sup>2</sup>L. Other families use various techniques in the production of metal-oxide semiconductor (MOS) devices. H-MOS (for high performance) is a scaled-down silicon gate MOS process; V-MOS is an anisotropically etched double-diffused MOS process, and D-MOS is a planar double-diffused process. SOS is a complementary silicon-on-sapphire process. The proponents of each of these families claim theirs is the best way of achieving higher speeds and densities at lower power dissipation on smaller chips which cost less.

Many special-purpose digital ICs are available to accomplish specific tasks. A divide-by-10 circuit, such as the Fairchild U6B95H9059X, operates up to 320 MHz and is used as a prescaler to extend the range of a frequency counter. This IC has been designed to operate with low-level input signals, typically 100 mV at 150 MHz.

Large MOS arrays are being used for a number of applications which require the storage of logic instructions. These ICs are called memories. Instructions are stored in the memory by a process named programming. Some memories can be programmed only once; they are called ROMs (Read-Only Memory). ROMs must be read in sequence, but another group of devices called RAMs (Random-Access Memory) can be used a section at a time. Both ROMs and RAMs are also made in

reprogrammable versions, where the information stored in the memory can be changed as desired. These models are named *PROMs* and *PRAMs*, respectively.

Large memory arrays are often used for the generation and conversion of information codes. One IC can be programmed to convert the five-level RTTY code to the eight-level ASCII code popular in computer devices. National Semiconductor manufactures a single IC which generates the entire 56-character eight-level code. Several ICs are now available for character generation where letters and numerals are produced for display on an oscillograph screen.

#### **Bibliography**

##### *Articles by Amateurs*

- Blakeslee, "A Second Look at Linear Integrated Circuits," *QST*, Dec., 1968.
- DeMaw and McCoy, "Learning to Work with Semiconductors," *QST*, April through September, 1974.
- DeMaw, "Some Basics on Solid State Design," *QST*, July, 1970.
- Hanchett, "The Field-Effect Transistor as a Stable VFO Element," *QST*, Dec., 1966.
- Hayward, "Transmitting with FETs," *QST*, April, 1970.
- Hejhall, "Broadband Solid-State Power Amplifiers for SSB Service," *QST*, March, 1972.
- Pos, "Digital Logic Devices," *QST*, July, 1968.
- Stoffels, "Let's Talk Transistors," *QST*, Nov., 1969 through July, 1970 (available from ARRL as a reprint).
- Hall and Watts, "Learning to Work with Integrated Circuits," *QST*, January through July, 1976

(available as a reprint from ARRL).

DeMaw, "Understanding Linear ICs," *QST*, January through March, 1977.

##### *Technical Books*

- Cowles, *Transistor Circuit Design*, Prentice-Hall, Inc.
- Cutler, *Semiconductor Circuit Analysis*, McGraw-Hill, 1964.
- Jung, *IC Op-Amp Cookbook*, No. 20969, Howard Sams & Co., Inc.
- Linear Applications*, National Semiconductor Corp., Feb. 1973.
- Linear Integrated Circuits*, Tech. Series IC-42, by RCA.
- Solid-State Devices Manual*, Tech. Series SC-16, by RCA.
- Solid-State Design for the Radio Amateur* by Hayward and DeMaw, ARRL.
- Transistor, Thyristor and Diode Manual*, Tech. Series SC-15, by RCA.

# Ac-Operated Power Supplies

Power-line voltages have been “standardized” throughout the U.S. at 117 and 234 volts in residential areas where a single voltage phase is supplied. These figures represent nominal voltages. “Normal” line voltage in a particular area may be between approximately 110 and 125 volts, but generally will be above 115 volts. In many states the service is governed by a PUC (public utilities commission). The voltage average across the country is approximately 117.

The ac-current capability of the service is a factor of line length from the dwelling to the nearest pole transformer, plus the conductor size of the line. Many older homes are supplied with a 60-ampere service while most new homes have 100 amperes. Houses equipped with electric heat will have services ranging from 150 to 200 amperes.

The electrical power required to operate amateur radio equipment is usually taken from the ac lines when the equipment is operated where power is available. For mobile operation the source of power is almost always the car storage battery.

Dc voltages used in transmitters, receivers and other related equipment are derived from the commercial ac lines by using a transformer-rectifier-filter system. The transformer changes the ac voltage to a suitable value and the rectifier converts the ac to pulsating dc. A filter is used to smooth out these pulsations to an acceptable low level. Essentially pure direct current is required to prevent 60- or 120-Hz hum in most pieces of amateur equipment. Transmitters must be operated from a pure dc supply as dictated by federal regulations. If a constant voltage is required under conditions of changing load or ac-line voltage, a regulator is used following the filter.

When the prime power source is dc (a battery), the dc is used directly or is first changed to ac and is then followed by the transformer-rectifier-filter combination. The latter system has lost considerable popularity with the advent of low-voltage semiconductor devices.

Transformerless power supplies are

used in some applications (notably ac-dc radios and some television receivers). Supplies of this sort operate directly from the power line, making it necessary to connect the chassis or common-return point of the circuit directly to one side of the ac line. This type of power supply represents a shock hazard when the equipment is connected to other units in the amateur station or when the chassis is exposed. For safety reasons, an isolation transformer should be used with such equipment.

### Power-Line Considerations: Connections

In most residential systems, three wires are brought in from the outside to the distribution board, while in a few older systems there are only two wires. In the three-wire system, the third wire is the *neutral*, which is grounded. The voltage between the two wires normally is 234, while half of this voltage appears between each of these wires and neutral, as indicated in Fig. 1A. In systems of this type the 117-volt household load is divided as evenly as possible between the two sides of the circuit, half of the load

being connected between one wire and the neutral, while the other half of the load is connected between the other wire and neutral. Heavy appliances, such as electric stoves and heaters are designed for 234-volt operation and therefore are connected across the two ungrounded wires. While both ungrounded wires should be fused, a fuse should never be used in the neutral wire, nor should a switch be used in this side of the line. The reason for this is that opening the neutral wire does not disconnect the equipment. It simply leaves the equipment on one side of the 234-volt circuit in series with whatever load may be across the other side of the circuit, as shown in Fig. 1B. Furthermore, with the neutral open, the voltage will then be divided between the two sides in inverse proportion to the load resistance, the voltage on one side dropping below normal, while it soars on the other side, unless the loads happen to be equal.

The usual line running to baseboard outlets is rated at 15 amperes. Considering the power consumed by filaments, lamps, transmitter, receiver and other auxiliary

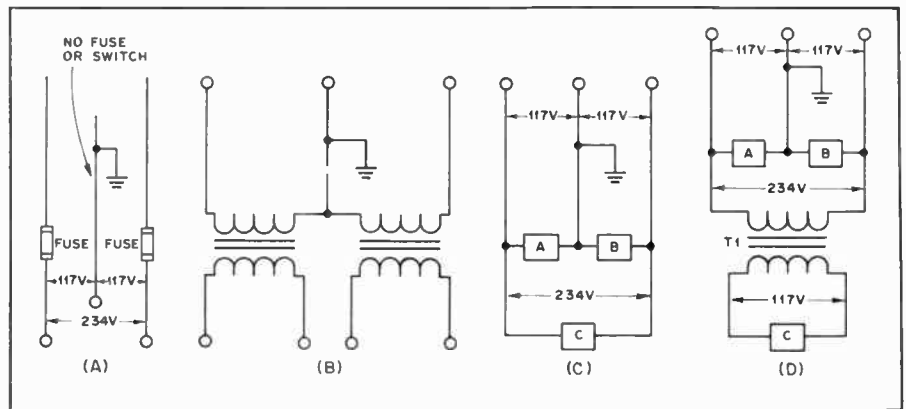


Fig. 1 — Three-wire power-line circuits. At A — Normal three-wire-line termination. No fuse should be used in the grounded (neutral) line. B — A switch in the neutral does not remove voltage from either side of the line. C — Connections for both 117- and 234-volt transformers. D — Operating a 117-volt plate transformer from the 234-volt line to avoid light blinking. T1 is a 2:1 step-down transformer.



equipment, it is not unusual to find this 15-A rating exceeded by the requirements of a station of only moderate power. It must also be kept in mind that the same branch may be in use for other household purposes through another outlet. For this reason, and to minimize light blinking when keying or modulating the transmitter, a separate heavier line should be run from the distribution board to the station whenever possible. A 3-volt drop in line voltage will cause noticeable blinking of lights.

If the system is of the three-wire, 234-V type, the three wires should be brought into the station so that the load can be distributed to keep the line balanced. The voltage across a fixed load on one side of the circuit will increase as the load current on the other side is increased. The rate of increase will depend upon the resistance introduced by the neutral wire. If the resistance of the neutral is low, the increase will be correspondingly small. When the currents in the two circuits are balanced, no current flows in the neutral wire and the system is operating at maximum efficiency.

Light blinking can be minimized by using transformers with 234-volt primaries in the power supplies for the keyed or intermittent part of the load, connecting them across the two ungrounded wires with no connection to the neutral, as shown in Fig. 1C. The same can be accomplished by the insertion of a step-down transformer with its primary operating at 234 volts and secondary delivering 117 volts. Conventional 117-volt transformers may be operated from the secondary of the step-down transformer (see Fig. 1D).

When a special heavy-duty line is to be installed, the local power company should be consulted as to local requirements. In some localities it is necessary to have such a job done by a licensed electrician, and there may be special requirements to be met. Some amateurs terminate the special line to the station at a switch box, while others may use electric-stove receptacles as the termination. The power is then distributed around the station by means of conventional outlets at convenient points. All circuits should be properly fused.

### Three-Wire 117-V Power Cords

To meet the requirements of state and national codes, electrical tools, appliances and many items of electronic equipment now being manufactured to operate from the 117-volt line, they must be equipped with a three-conductor power cord. Two of the conductors carry power to the device in the usual fashion, while the third conductor is connected to the case or frame.

When plugged into a properly wired mating receptacle, the three-contact polarized plug connects this third conductor

to an earth ground, thereby grounding the chassis or frame of the appliance and preventing the possibility of electrical shock to the user. All commercially manufactured items of electronic test equipment and most ac-operated amateur equipment are being supplied with these three-wire cords. Adapters are available for use where older electrical installations do not have mating receptacles. For proper grounding, the lug of the green wire protruding from the adapter must be attached underneath the screw securing the cover plate of the outlet box where connection is made, and the outlet box itself must be grounded.

### Fusing

All transformer primary circuits should be properly fused. To determine the approximate current rating of the fuse or circuit breaker to be used, multiply each current being drawn from the supply in amperes by the voltage at which the current is being drawn. Include the current taken by bleeder resistances and voltage dividers. In the case of series resistors, use the source voltage, not the voltage at the equipment end of the resistor. Include filament power if the transformer is supplying filaments. After multiplying the various voltages and currents, add the individual products. Then divide by the line voltage and add 10 or 20 percent. Use a fuse or circuit breaker with the nearest larger current rating.

### Line-Voltage Adjustment

In certain communities trouble is sometimes experienced from fluctuations in line voltage. Usually these fluctuations are caused by a variation in the load on the line. Since most of the variation comes at certain fixed times of the day or night, such as the times when lights are turned on at evening, they may be taken care of by the use of a manually operated compensating device. A simple arrangement is shown in Fig. 2A. A tapped transformer is used to boost or buck the line voltage as required. The transformer should have a secondary varying between 6 and 20 volts in steps of 2 or 3 volts and its secondary should be capable of carrying the full load current.

The secondary is connected in series

with the line voltage and, if the phasing of the windings is correct, the voltage applied to the primaries of the transmitter transformers can be brought up to the rated 117 volts by setting the transformer tap switch on the right tap. If the phasing of the two windings of the transformer happens to be reversed, the voltage will be reduced instead of increased. This connection may be used in cases where the line voltage may be above 117 volts. This method is preferable to using a resistor in the primary of a power transformer since it does not affect the voltage regulation as seriously. The circuit of 2B illustrates the use of a variable autotransformer (Variac) for adjusting line voltage.

### Constant-Voltage Transformers

Although comparatively expensive, special transformers called *constant-voltage transformers* are available for use in cases where it is necessary to hold line voltage and/or filament voltage constant with fluctuating supply-line voltage. These are static-magnetic voltage regulating transformers operating on principles of ferro-resonance. They have no tubes or moving parts, and require no manual adjustments. These transformers are rated over a range of less than 1 volt-ampere (VA) at 5 volts output up to several thousand VA at 117 or 234 volts. On the average they will hold their output voltages within one percent under an input voltage variation of  $\pm 15$  percent.

### Safety Precautions

All power supplies in an installation should be fed through a single main power-line switch so that all power may be cut off quickly, either before working on the equipment, or in case of an accident. Spring-operated switches or relays are not sufficiently reliable for this important service. Foolproof devices for cutting off all power to the transmitter and other equipment are shown in Fig. 3. The arrangements shown in Figs. 3A and B are similar circuits for two-wire (117-volt) and three-wire (234-volt) systems. S is an enclosed double-throw switch of the sort usually used as the entrance switch in house installations. J is a standard ac outlet and P a shorted plug to fit the outlet. The switch should be located

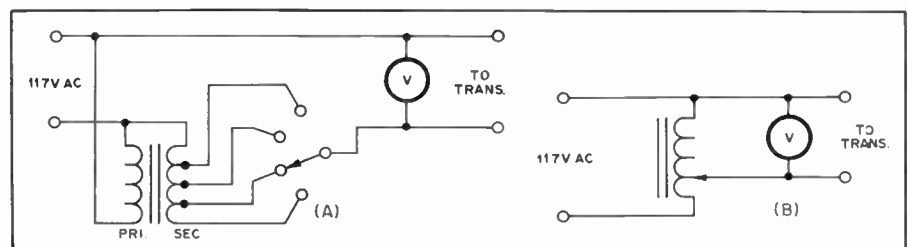


Fig. 2 — Two methods of transformer primary control. At A is a tapped transformer which may be connected so as to boost or buck the line voltage as required. At B is indicated a variable transformer or autotransformer (Variac) which feeds the transformer primaries.

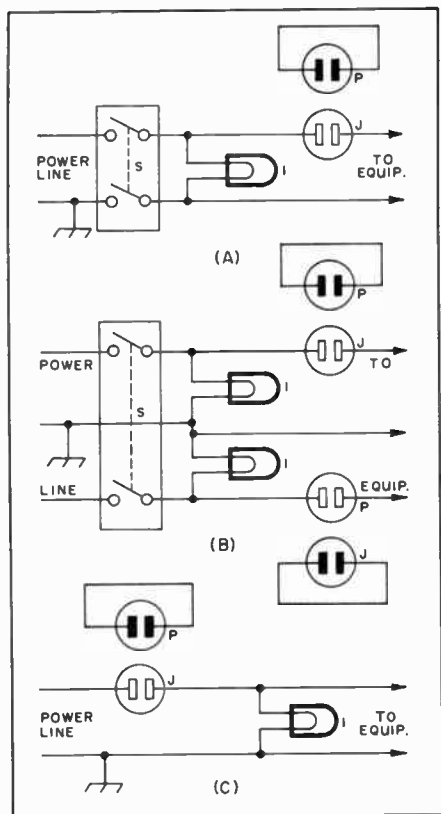


Fig. 3 — Reliable arrangements for cutting off all power to the transmitter. S is an enclosed double-pole power switch, J a standard ac outlet, P a shorted plug to fit the outlet and I a red lamp. A is for a two-wire 117-volt line, B for a three-wire 234-volt system, and C a simplified arrangement for low-power stations.

prominently in plain sight, and members of the household should be instructed in its location and use. I is a red lamp located alongside the switch. Its purpose is not so much to serve as a warning that the power is on as it is to help in identifying and quickly locating the switch should it become necessary for someone else to cut the power off in an emergency.

The outlet J should be placed in some corner out of sight where it will not be a temptation for children or others to play with. The shorting plug can be removed to open the power circuit if there are others around who might inadvertently throw the switch while the operator is working on the rig. If the operator takes the plug with him, it will prevent someone from turning on the power in his absence and either hurting himself or the equipment or perhaps starting a fire. Of utmost importance is the fact that the outlet J *must* be placed in the *ungrounded* side of the line.

Those who are operating low power and feel that the expense or complication of the switch isn't warranted can use the shorted-plug idea as the main power switch. In this case, the outlet should be located prominently and identified by a signal light, as shown in Fig. 3C.

The test bench should be fed through

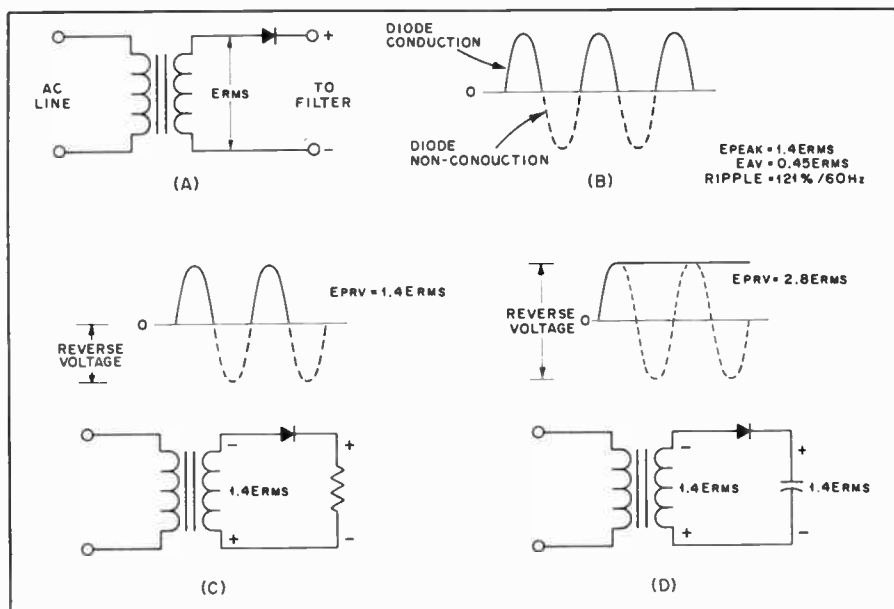


Fig. 4 — Half-wave rectifier circuit. A illustrates the basic circuit and B displays the diode conduction and nonconduction periods. The peak-reverse voltage impressed across the diode is shown at C and D with a simple resistor load at C and a capacitor load at D.  $E_{prv}$  for the resistor load is  $1.4 E_{rms}$  and  $2.8 E_{rms}$  for the capacitor load.

the main power switch, or a similar arrangement at the bench, if the bench is located remotely from the transmitter.

A bleeder resistor with a power rating which gives a considerable margin of safety should be used across the output of all transmitter power supplies, so that the filter capacitors will be discharged when the high-voltage is turned off.

### Rectifier Circuits: Half-Wave

Fig. 4 shows a simple half-wave rectifier circuit. As pointed out in the semiconductor chapter a rectifier (in this case a semiconductor diode) will conduct current in one direction but not the other. During one half of the ac cycle the rectifier will conduct and current will flow through the rectifier to the load (indicated by the solid line in Fig. 4B). During the other half cycle the rectifier is reverse biased and no current will flow (indicated by the dotted line in Fig. 4B) to the load. As shown, the output is in the form of pulsed dc and current always flows in the same direction. A filter can be used to smooth out these variations and provide a higher average dc voltage from the circuit. This idea will be covered in the next section on filters.

The average output voltage — the voltage read by a dc voltmeter — with this circuit (no filter connected) is 0.45 times the rms value of the ac voltage delivered by the transformer secondary. Because the frequency of the pulses is rather low (one pulsation per cycle), considerable filtering is required to provide adequately smooth dc output. For this reason the circuit is usually limited to applications where the current required is small, as in a transmitter bias supply.

The peak reverse voltage (PRV), the voltage that the rectifier must withstand when it isn't conducting, varies with the load. With a resistive load it is the peak ac voltage ( $1.4 E_{rms}$ ) but with a capacitor filter and a load drawing little or no current it can rise to  $2.8 E_{rms}$ . The reason for this is shown in Figs. 4C and 4D. With a resistive load as shown at C the amount of reverse voltage applied to the diode is that voltage on the lower side of the Zero-axis line or  $1.4 E_{rms}$ . A capacitor connected to the circuit (shown at D) will store the peak positive voltage when the diode conducts on the positive pulse. If the circuit is not supplying any current the voltage across the capacitor will remain at that same level. The peak reverse voltage impressed across the diode is now the sum of the voltage stored in the capacitor plus the peak negative swing of voltage from the transformer secondary. In this case the PRV is  $2.8 E_{rms}$ .

### Full-Wave Center-Tap Rectifier

A commonly used rectifier circuit is shown in Fig. 5. Essentially an arrangement in which the outputs of two half-wave rectifiers are combined, it makes use of both halves of the ac cycle. A transformer with a center-tapped secondary is required with the circuit.

The average output voltage is 0.9 times the rms voltage of half the transformer secondary; this is the maximum that can be obtained with a suitable choke-input filter. The peak output voltage is 1.4 times the rms voltage of half the transformer secondary; this is the maximum voltage that can be obtained from a capacitor-input filter.

As can be seen in Fig. 5C the PRV

impressed on each diode is independent of the type load at the output. This is because the peak reverse voltage condition occurs when diode A conducts and diode B does not conduct. The positive and negative voltage peaks occur at precisely the same time, a different condition than exists in the half-wave circuit. As diodes A and B cathodes reach a positive peak ( $1.4 E_{rms}$ ), the anode of diode B is at a negative peak, also  $1.4 E_{rms}$ , but in the opposite direction. The total peak reverse voltage is therefore  $2.8 E_{rms}$ .

Fig. 5B shows that the frequency of the output pulses is twice that of the half-wave rectifier. Comparatively less filtering is required. Since the rectifiers work alternately, each handles half of the load current: The current rating of each rectifier need be only half the total current drawn from the supply.

Two separate transformers, with their primaries connected in parallel and secondaries connected in series (with the proper polarities), may be used in this circuit. However, if this substitution is made, the primary volt-ampere rating must be reduced to about 40 percent less than twice the rating of one transformer.

### Full-Wave Bridge Rectifier

Another commonly used rectifier circuit is illustrated in Fig. 6. In this arrangement, two rectifiers operate in series on each half of the cycle, one rectifier being in the lead to the load, the other being in the return lead. As shown in Figs. 6A and B, when the top lead of the transformer secondary is positive with respect to the bottom lead diodes A and C will conduct while diodes B and D are reverse biased. On the next half cycle when the top lead of the transformer is negative with respect to the bottom diodes B and D will conduct while diodes A and C are reverse biased.

The output wave shape is the same as that from the simple center-tap rectifier circuit. The maximum output voltage into a resistive load or choke-input filter is 0.9 times the rms voltage delivered by the transformer secondary; with a capacitor filter and a light load the output voltage is 1.4 times the secondary rms voltage.

Fig. 6C shows the peak reverse voltage to be  $2.8 E_{rms}$  for each pair of diodes. Since the diodes are connected in series each diode has  $1.4 E_{rms}$  as the reverse voltage impressed across it. Each pair of diodes works alternately so each handles half of the load current. The rectifier in this circuit should have a minimum current rating of one half the total load current to be drawn from the supply.

### Filtering

The pulsating dc waves from the rectifiers are not sufficiently constant in amplitude to prevent hum corresponding to the pulsations. Filters are required be-

tween the rectifier and the load to smooth out the pulsations into an essentially constant dc voltage. Also, the design of the filter depends to a large extent on the dc voltage output, the voltage regulation of the power supply, and the maximum load current that can be drawn from the supply without exceeding the peak-current rating of the rectifier. Power supply filters are low-pass devices using series inductors and shunt capacitors.

### Load Resistance

In discussing the performance of power-supply filters, it is sometimes convenient to express the load connected to the output terminals of the supply in terms of resistance. The load resistance is equal to the output voltage divided by the total current drawn, including the current drawn by the bleeder resistor.

### Voltage Regulation

The output voltage of a power supply always decreases as more current is

drawn, not only because of increased voltage drops on the transformer, filter chokes and the rectifier (if high-vacuum rectifiers are used) but also because the output voltage at light loads tends to soar to the peak value of the transformer voltage as a result of charging the first capacitor. By proper filter design the latter effect can be eliminated. The change in output voltage with load is called *voltage regulation* and is expressed as a percentage.

$$\text{Percent regulation} = \frac{100 (E_1 - E_2)}{E_2}$$

where

$E_1$  = the no-load voltage

$E_2$  = the full-load voltage

A steady load, such as that represented by a receiver, speech amplifier or unkeyed stages of a transmitter, does not require good (low) regulation as long as the proper voltage is obtained under load conditions. However, the filter capacitors

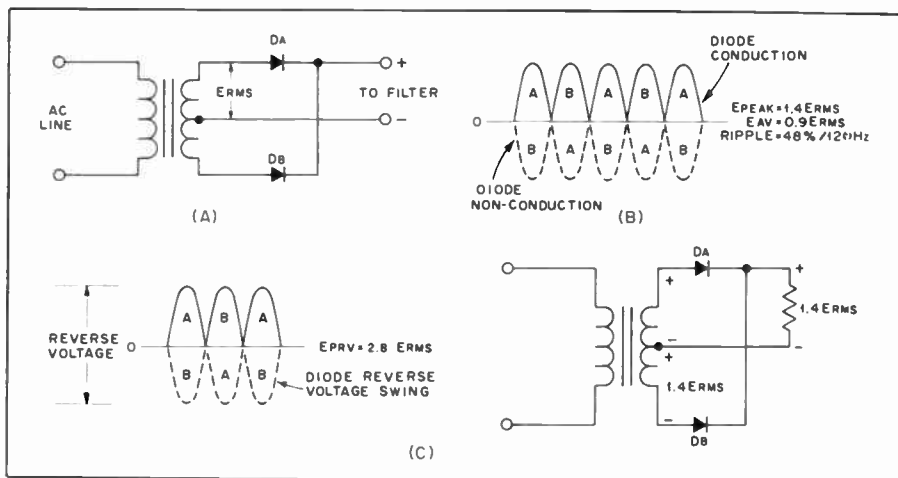


Fig. 5—Full-wave center-tap rectifier circuit. A illustrates the basic circuit. Diode conduction is shown at B with diodes A and B alternately conducting. The peak-reverse voltage for each diode is  $2.8 E_{rms}$  as depicted at C.

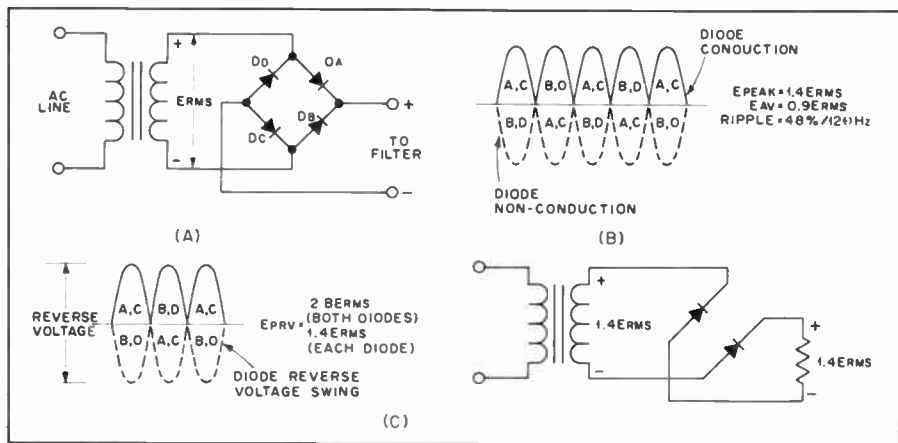


Fig. 6—Full-wave bridge rectifier circuit. The basic circuit is illustrated at A. Diode conduction and nonconduction times are shown at B. Diodes A and C conduct on one half of the input cycle while diodes B and D conduct on the other. C displays the peak-reverse voltage for one-half cycle. Since this circuit uses two diodes essentially in series, the  $2.8 E_{rms}$  is divided between two diodes, or,  $1.4 E_{rms}$  PRV for each diode.



must have a voltage rating safe for the highest value to which the voltage will soar when the external load is removed.

A power supply will show more (higher) regulation with long-term changes in load resistance than with short temporary changes. The regulation with long-term changes is often called the *static regulation*, to distinguish it from the *dynamic regulation* (short temporary load changes). A load that varies at a syllabic or keyed rate, as represented by some audio and rf amplifiers, usually requires good dynamic regulation (15 percent or less) if distortion products are to be held to a low level. The dynamic regulation of a power supply is improved by increasing the value of the output capacitor.

When essentially constant voltage regardless of current variation is required (for stabilizing an oscillator, for example), special voltage-regulating circuits described later in this chapter are used.

### Bleeder

A bleeder resistor is a resistance connected across the output terminals of the power supply. Its functions are to discharge the filter capacitors as a safety measure when the power is turned off and to improve voltage regulation by providing a minimum load resistance. When voltage regulation is not of importance, the resistance may be as high as 100 ohms per volt. The resistance value to be used for voltage-regulating purposes is discussed in later sections. From the consideration of safety, the power rating of the resistor should be as conservative as possible, since a burned-out bleeder resistor is more dangerous than none at all!

### Ripple Frequency and Voltage

Pulsations at the output of the rectifier can be considered to be the resultant of an alternating current superimposed on a steady direct current. From this viewpoint, the filter may be considered to consist of shunt capacitors which short-circuit the ac component while not interfering with the flow of the dc

component. Series chokes will readily pass dc but will impede the flow of the ac component.

The alternating component is called *ripple*. The effectiveness of the filter can be expressed in terms of percent ripple, which is the ratio of the rms value of the ripple to the dc value in terms of percentage.

$$\text{Percent ripple (rms)} = \frac{100 E_1}{E_2}$$

where

$E_1$  = the rms value of ripple voltage  
 $E_2$  = the steady dc voltage

Any multiplier or amplifier supply in a code transmitter should have less than five percent ripple. A linear amplifier can tolerate about three percent ripple on the plate voltage. Bias supplies for linear amplifiers, and modulator and modulated-amplifier plate supplies, should have less than one percent ripple. VFOs, speech amplifiers and receivers may require a ripple reduction to 0.01 percent.

Ripple frequency is the frequency of the pulsations in the rectifier output wave — the number of pulsations per second. The frequency of the ripple with half-wave rectifiers is the same as the frequency of the line supply — 60 Hz with 60-Hz supply. Since the output pulses are doubled with a full-wave rectifier, the ripple frequency is doubled — to 120 Hz with a 60-Hz supply.

The amount of filtering (values of inductance and capacitance) required to give adequate smoothing depends upon the ripple frequency, with more filtering being required as the ripple frequency is lowered.

### Type of Filter

Power-supply filters fall into two classifications, capacitor input and choke input. Capacitor-input filters are characterized by relatively high output voltage in respect to the transformer voltage. Advantage of this can be taken when silicon rectifiers are used or with any rectifier when

the load resistance is high. Silicon rectifiers have a higher allowable peak-to-dc ratio than do thermionic rectifiers. This permits the use of capacitor-input filters at ratios of input capacitor to load resistance that would seriously shorten the life of a thermionic rectifier system. When the series resistance through a rectifier and filter system is appreciable, as when high-vacuum rectifiers are used, the voltage regulation of a capacitor-input power supply is poor.

The output voltage of a properly designed choke-input power supply is less than would be obtained with a capacitor-input filter from the same transformer. Generally speaking, a choke-input filter will permit a higher load current to be drawn from a thermionic rectifier without exceeding the peak rating of the rectifier.

### Capacitive-Input Filters

Capacitive-input filter systems are shown in Fig. 7. Disregarding voltage drops in the chokes, all have the same characteristics except in respect to ripple. Better ripple reduction will be obtained when LC sections are added as shown in Figs. 7B and C.

### Output Voltage

To determine the approximate dc voltage output when a capacitive-input filter is used, the graphs shown in Fig. 8 will be helpful. An example of how to use the graph is given below.

Example:

Full-wave rectifier (use graph at B)  
 Transformer rms voltage = 350  
 Load resistance = 2000 ohms  
 Series resistance = 200 ohms  
 Input capacitance = 20  $\mu$ F

$$\frac{R}{RS} = \frac{200}{2000} = 0.1 \quad \frac{RC}{1000} = \frac{2000 \times 20}{1000} = 40$$

From curve 0.1 and  $RC = 40$ , the dc voltage is  $(350 \times 1.06) = 370$ .

In many cases it is desirable to know the amount of capacitance required for a power supply given certain performance criteria. This is especially true when designing a power supply for an application such as powering a solid-state transceiver. The following example should give the builder a good handle on how to arrive at circuit values for a power supply using a single capacitor filter.

Fig. 9 is the circuit diagram of the power supply to be used.

Requirements:

Output voltage = 12.6

Output current = 1 ampere

Maximum ripple = 2 percent

Load regulation = 5 percent

The rms secondary voltage of T1 must be the desired output voltage plus the voltage drops across D2 and D4 divided by 1.41.

$$E_{SEC} = \frac{12.6 + 1.4}{1.41} = 9.93$$

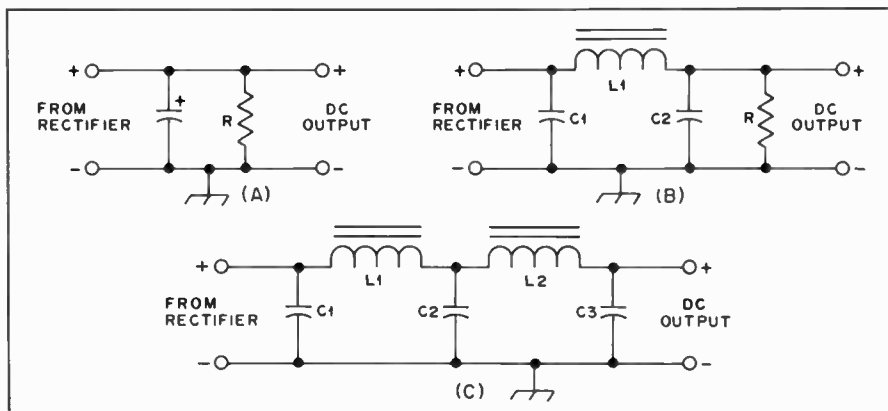


Fig. 7 — Capacitive-input filter circuits. At A is a simple capacitor filter. B and C are single- and double-section filters, respectively.



In practice the nearest standard transformer (10 V) would work fine. Alternatively, the builder could wind his own transformer, or remove secondary turns from a 12-volt transformer to obtain the desired rms secondary voltage.

A two percent ripple referenced to 12.6 volts is 0.25 V rms. The peak-to-peak value is therefore  $0.25 \times 2.8 = 0.7$  V. This value is required to calculate the required capacitance for C1.

Also needed for determining the value of C1 is the time interval (t) between the full-wave rectifier pulses which is calculated as follows:

$$T = \frac{1}{f_{(Hz)}} = \frac{1}{120} = 8.3 \times 10^{-3} \text{ sec.}$$

where T is the time between pulses and f is the frequency in Hz. Since the circuit makes use of a full-wave rectifier a pulse occurs twice during each cycle. With half-wave rectification a pulse would occur only once a cycle. Thus 120 Hz is used as the frequency for this calculation.

C1 is calculated from the following equation:

$$C_{(\mu F)} = \left[ \frac{I_L t}{E_{rip(pk-pk)}} \right] 10^6$$

$$= \left[ \frac{1A \times 8.3 \times 10^{-3}}{0.7} \right] 10^6$$

$$= 11,857 \mu F$$

where  $I_L$  is the current taken by the load.

The nearest standard capacitor value is 12,000  $\mu F$ . It will be an acceptable one to use, but since the tolerance of electrolytic capacitors is rather loose, the builder may elect to use the next larger standard value.

Diodes D1-D4, inclusive, should have a PRV rating of at least two times the transformer secondary peak voltage. Assuming a transformer secondary rms value of 10 volts, the PRV should be at least 28 volts. Four 50-volt diodes will provide a margin of safety. The forward current of the diodes should be at least twice the load current. For a 1-A load, the diodes should be rated for at least 2 A.

The load resistance,  $R_L$ , is determined by  $E_o/I_L$ , which in this example is  $12.6/1 = 12.6$  ohms. This factor must be known in order to find the necessary series resistance for five-percent regulation. Calculate as follows:

$$R_{S(max)} = \text{Load regulation} \left( \frac{R_L}{10} \right)$$

$$= 0.05 \left( \frac{12.6}{10} \right) = 0.063 \text{ ohm}$$

Therefore, the transformer secondary dc resistance should be no greater than 0.063

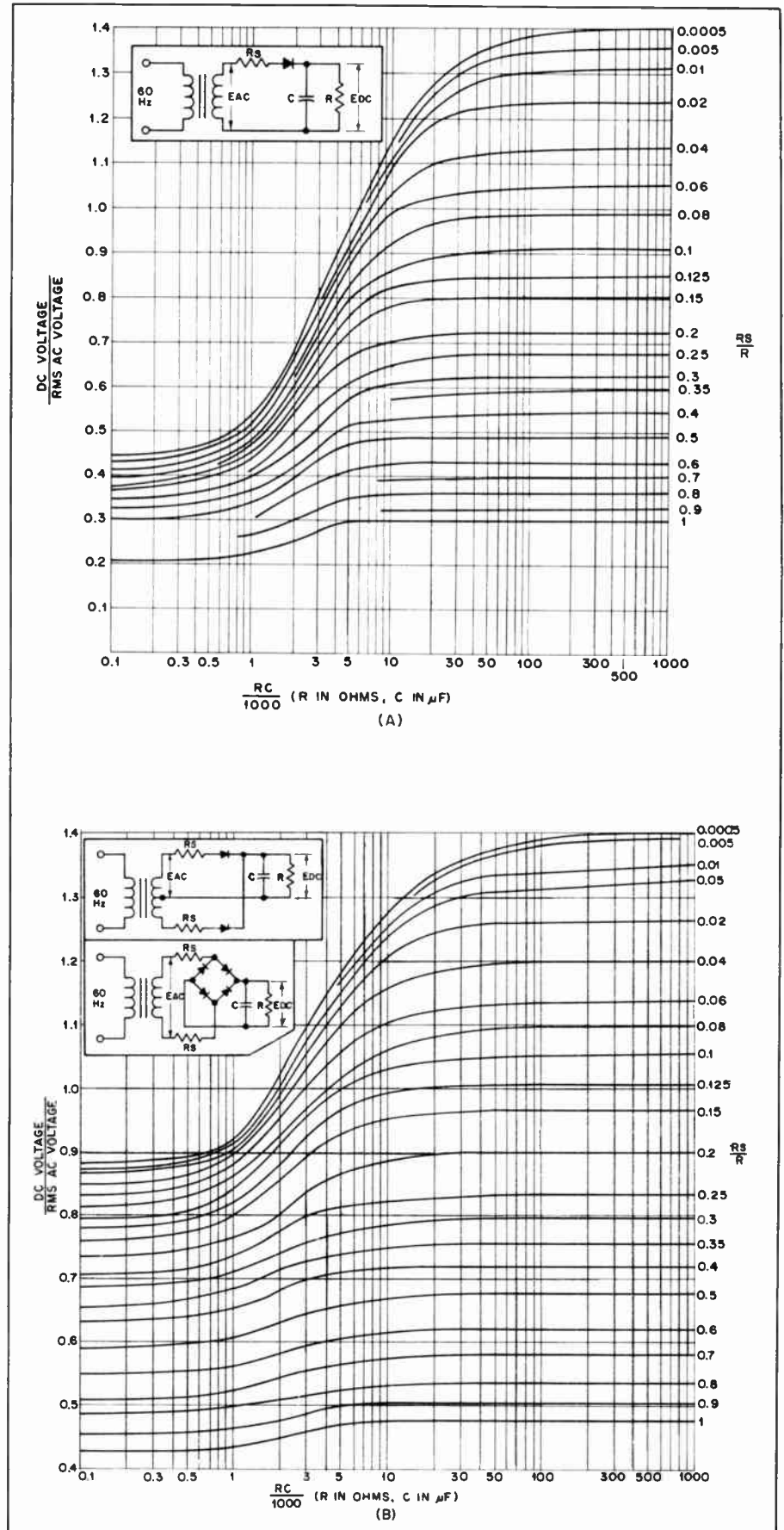


Fig. 8 — Dc output voltages from a half- and full-wave rectifier circuit as a function of the filter capacitance and load resistance (half-wave shown at A and full-wave shown at B).  $R_s$  includes transformer winding resistance and rectifier forward resistance. For the ratio  $R_s/R$ , both resistances are in ohms; for the RC product, R is in ohms and C is in  $\mu F$ .

ohm. The secondary current rating should be equal to or greater than the  $I_L = 1$  ampere.

C1 should have a minimum working voltage of 1.4 times the output voltage. In the case of this power supply the capacitor should be rated for at least 18 volts.

### Choke-Input Filters

With thermionic rectifiers better voltage regulation results when a choke-input filter, as shown in Fig. 10, is used. Choke input permits better utilization of the thermionic rectifier, since a higher load current can be drawn without exceeding the peak current rating of the rectifier.

#### Minimum Choke Inductance

A choke-input filter will tend to act as a capacitive-input filter unless the input choke has at least a certain minimum value of inductance called the *critical* value. This critical value is given by

$$L_{crit} \text{ (henrys)} = \frac{E \text{ (volts)}}{I \text{ (mA)}}$$

where  $E$  = the supply output voltage  
 $I$  = the current being drawn through the filter.

If the choke has at least the critical value, the output voltage will be limited to the average value of the rectified wave at the input to the choke when the current drawn from the supply is small. This is in contrast to the capacitive-input filter in which the output voltage tends to soar toward the peak value of the rectified wave at light loads.

#### Minimum-Load — Bleeder Resistance

From the formula above for critical inductance, it is obvious that if no current is drawn from the supply, the critical inductance will be infinite. So that a practical value of inductance may be used, some current must be drawn from the supply at all times the supply is in use. From the formula we find that this minimum value of currents is

$$I \text{ (mA)} = \frac{E \text{ (volts)}}{L_{crit}}$$

In the majority of cases it will be most convenient to adjust the bleeder resistance so that the bleeder will draw the required minimum current. From the formula, it may be seen that the value of critical inductance becomes smaller as the load current increases.

#### Swinging Chokes

Less costly chokes are available that will maintain at least the critical value of inductance over the range of current likely to be drawn from practical supplies. These chokes are called *swinging chokes*. As an example, a swinging choke may have an inductance rating of 5/25 H and a current rating of 200 mA. If the supply delivers 1000 volts, the minimum load current should be  $1000/25 = 40$  mA. When the full

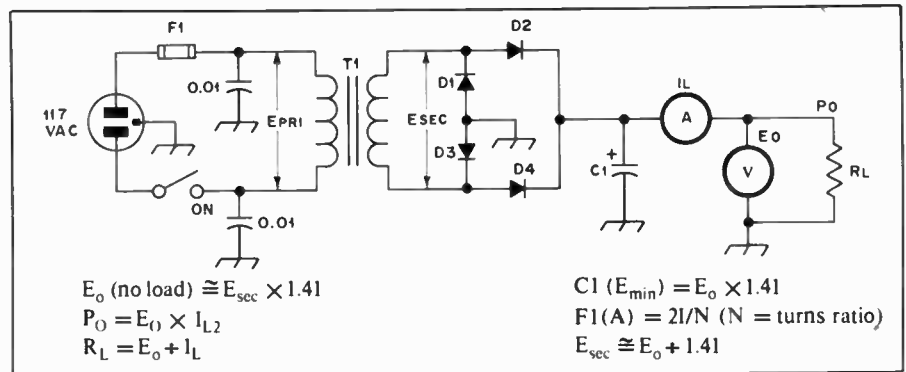


Fig. 9 — This figure illustrates how to design a simple unregulated power supply. See text for a thorough discussion.

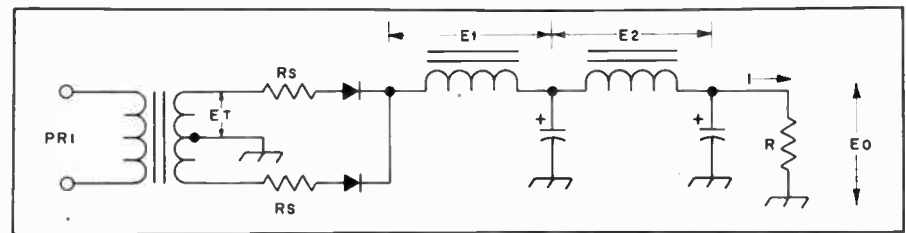


Fig. 10 — Diagram showing various voltage drops that must be taken into consideration in determining the required transformer voltage to deliver the desired output voltage.

load current of 200 mA is drawn from the supply, the inductance will drop to 5 H. The critical inductance for 200 mA at 1000 volts is  $1000/200 = 5$  H. Therefore the 5/25 H choke maintains the critical inductance at the full current rating of 200 mA. At all load currents between 40 mA and 200 mA, the choke will adjust its inductance to the approximate critical value.

#### Output Voltage

Provided the input-choke inductance is at least the critical value, the output voltage may be calculated quite close by:

$$E_o = 0.9E_t - (I_B + I_L) \times (R_1 + R_2) - E_r$$

where

- $E_o$  = output voltage
- $E_t$  = rms voltage applied to the rectifier (rms voltage between center-tap and one end of the secondary in the case of the center-tap rectifier)
- $I_B$  = bleeder current (A)
- $I_L$  = load current (A)
- $R_1$  = first filter choke resistance
- $R_2$  = second filter choke resistance
- $E_r$  = voltage drop across the rectifier.

The various voltage drops are shown in Fig. 10. At no load  $I_L$  is zero; hence the no-load voltage may be calculated on the basis of bleeder current only. The voltage regulation may be determined from the no-load and full-load voltages using the formulas previously given.

#### Output Capacitor

Whether the supply has a choke- or capacitor-input filter, if it is intended for

use with a Class A af amplifier, the reactance of the output capacitor should be low for the lowest audio frequency; 16  $\mu$ F or more is usually adequate. When the supply is used with a Class B amplifier (for modulation or for ssb amplification) or a cw transmitter, increasing the output capacitance will result in improved dynamic regulation of the supply. However, a region of diminishing returns can be reached, and 20 to 30  $\mu$ F will usually suffice for any supply subjected to large changes at a syllabic (or keying) rate.

#### Resonance

Resonance effects in the series circuit across the output of the rectifier, formed by the first choke and first filter capacitor, must be avoided, since the ripple voltage would build up to large values. This not only is the opposite action to that for which the filter is intended, but may also cause excessive rectifier peak currents and abnormally high peak-reverse voltages. For full-wave rectification the ripple frequency will be 120 Hz for a 60-Hz supply, and resonance will occur when the product of choke inductance in henrys times capacitor capacitance in microfarads is equal to 1.77. At least twice this product of inductance and capacitance should be used to ensure against resonance effects. With a swinging choke, the minimum rated inductance of the choke should be used.

#### Ratings of Filter Components

In a power supply using a choke-input filter and properly designed choke and bleeder resistor, the no-load voltage

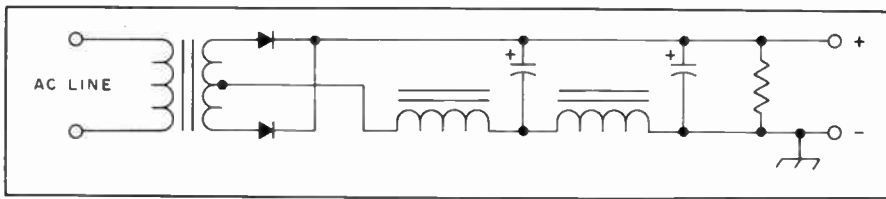


Fig. 11 — In most applications, the filter chokes may be placed in the negative instead of the positive side of the circuit. This reduces the danger of a voltage breakdown between the choke winding and core.

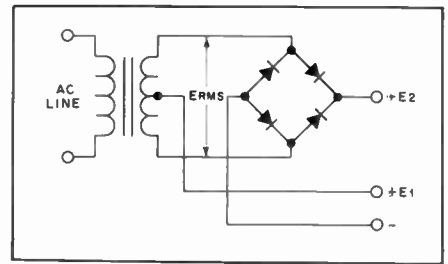


Fig. 12 — The "economy" power supply circuit is a combination of the full-wave and bridge-rectifier circuits.

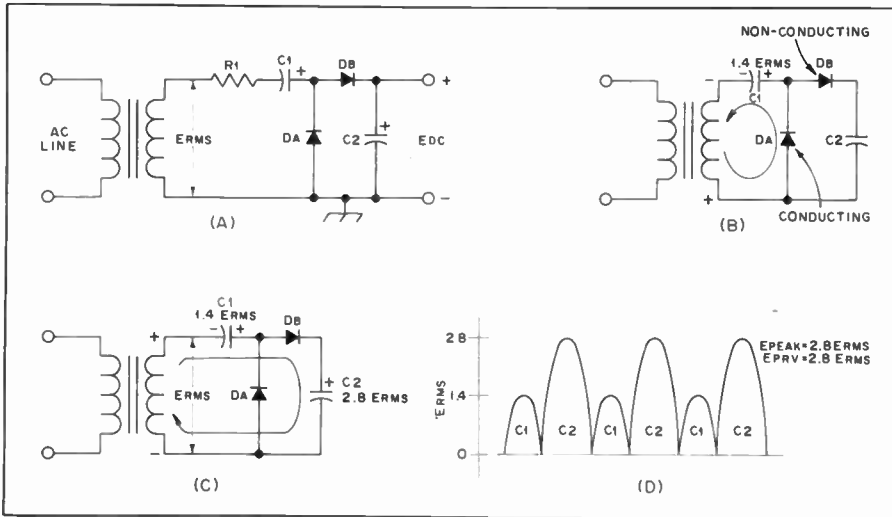


Fig. 13 — Illustrated at A is a half-wave voltage-doubler circuit. B displays how the first half cycle of input voltage charges C1. During the next half cycle (shown at C) capacitor C2 is charged with the transformer secondary voltage plus that voltage stored in C1 from the previous half cycle. D illustrates the levels to which each capacitor is charged throughout the cycle.

across the filter capacitors will be about nine-tenths of the ac rms voltage. Nevertheless, it is advisable to use capacitors rated for the *peak* transformer voltage. This large safety factor is suggested because the voltage across the capacitors can reach this peak value if the bleeder should burn out and there is no load on the supply.

In a capacitive-input filter, the capacitors should have a working-voltage rating at least as high, and preferably somewhat higher, than the peak voltage from the transformer. Thus, in the case of a center-tap rectifier having a transformer delivering 550 volts each side of the center tap, the minimum safe capacitor voltage rating will be  $550 \times 1.41$  or 775 volts. An 800-volt capacitor should be used, or preferably a 1000-volt unit.

#### Filter Capacitors in Series

Filter capacitors are made in several different types. Electrolytic capacitors, which are available for peak voltages up to about 800, combine high capacitance with small size, since the dielectric is an extremely thin film of oxide on aluminum foil. Capacitors of this type may be connected in series for higher voltages, although the filtering capacitance will be reduced to the resultant of the two capacitances in series. If this arrangement

is used, it is important that *each* of the capacitors be shunted with a resistor of about 100 ohms per volt of supply voltage applied to the individual capacitors, with an adequate power rating. These resistors may serve as all or part of the bleeder resistance. Capacitors with higher voltage ratings usually are made with a dielectric of thin paper impregnated with oil. The working voltage of a capacitor is the voltage that it will withstand continuously.

#### Filter Chokes

Filter chokes or inductances are wound on iron cores, with a small gap in the core to prevent magnetic saturation of the iron at high currents. When the iron becomes saturated its permeability decreases, and consequently the inductance also decreases. Despite the air gap, the inductance of a choke usually varies to some extent with the direct current flowing in the winding; hence it is necessary to specify the inductance at the current which the choke is intended to carry. Its inductance with little or no direct current flowing in the winding will usually be considerably higher than the value when full load current is flowing.

#### Negative-Lead Filtering

For many years it has been almost universal practice to place filter chokes in

the positive leads of plate power supplies. This means that the insulation between the choke winding and its core (which should be grounded to chassis as a safety measure) must be adequate to withstand the output voltage of the supply. This voltage requirement is removed if the chokes are placed in the negative lead as shown in Fig. 11. With this connection, the capacitance of the transformer secondary to ground appears in parallel with the filter chokes tending to bypass the chokes. However, this effect will be negligible in practical application except in cases where the output ripple must be reduced to a very low figure. Such applications are usually limited to low-voltage devices such as receivers, speech amplifiers and VFOs where insulation is no problem and the chokes may be placed in the positive side in the conventional manner. In higher-voltage applications, there is no reason why the filter chokes should not be placed in the negative lead to reduce insulation requirements. Choke terminals, negative capacitor terminals and the transformer center-tap terminal should be well protected against accidental contact, since these will assume full supply voltage to chassis should a choke burn out or the chassis connection fail.

#### The "Economy" Power Supply

In many transmitters of the 100-watt class, an excellent method for obtaining plate and screen voltages without wasting power in resistors is by the use of the "economy" power-supply circuit. Shown in Fig. 12, it is a combination of the full-wave and bridge-rectifier circuits. The voltage at E1 is the normal voltage obtained with the full-wave circuit, and the voltage at E2 is that obtained with the bridge circuit. The *total* dc power obtained from the transformer is, of course, the same as when the transformer is used in its normal manner. In cw and ssb applications, additional power can usually be drawn without excessive heating, especially if the transformer has a rectifier filament winding that isn't being used.

#### Half-Wave Voltage Doubler

Fig. 13 shows the circuit of half-wave voltage doubler. Figs. 13B, C and D illustrate the circuit operation. For clarity,



assume the transformer voltage polarity at the moment the circuit is activated is that shown at B. During the first negative half cycle (D1 conducts (D2 is in a non-conductive state), charging C1 to the peak rectified voltage ( $1.4 E_{rms}$ ). C1 is charged with the polarity shown at B. During the positive half cycle of the secondary

voltage, D1 is cutoff and diode D2 conducts charging capacitor C2. The amount of voltage delivered to C2 is the sum of peak secondary voltage of the transformer plus the voltage stored in C1 ( $1.4 E_{rms}$ ). On the next negative half cycle, D2 is nonconducting and C2 will discharge into the load. If no load is

connected across C2 the capacitors will remain charged — C1 to  $1.4 E_{rms}$  and C2 to  $2.8 E_{rms}$ . When a load is connected to the output of the doubler, the voltage across C2 drops during the negative half cycle and is recharged up to  $2.8 E_{rms}$  during the positive half cycle.

The output waveform across C2 resembles that of a half-wave rectifier circuit in that C2 is pulsed once every cycle. The drawing at Fig. 13D illustrates the levels to which the two capacitors are charged throughout the cycle. In actual operation the capacitors will not discharge all the way to zero as shown.

### Full-Wave Voltage Doubler

Shown in Fig. 14 is the circuit of a full-wave voltage doubler. The circuit operation can best be understood by following Figs. 14B, C and D. During the positive half cycle of transformer secondary voltage, as shown at B, D1 conducts charging capacitor C1 to  $1.4 E_{rms}$ . D2 is not conducting at this time.

During the negative half cycle, as shown at C, D2 conducts charging capacitor C2 to  $1.4 E_{rms}$  while D1 is nonconducting. The output voltage is the sum of the two capacitor voltages which will be  $2.8 E_{rms}$  under no-load conditions. Fig. 14D illustrates that each capacitor alternately receives a charge once per cycle. The effective filter capacitance is that of C1 and C2 in series, which is less than the capacitance of either C1 or C2 alone.

Resistors R in Fig. 14A are used to limit the surge current through the rectifiers. Their values are based on the transformer voltage and the rectifier surge-current rating, since at the instant the power supply is turned on the filter capacitors look like a short-circuited load. Provided the limiting resistors can withstand the surge current, their current-handling capacity is based on the maximum load current from the supply. Output voltages approaching twice the peak voltage of the transformer can be obtained with the voltage doubling circuit shown in Fig. 14. Fig. 15 shows how the voltage depends upon the ratio of the series resistance to the load resistance, and the product of the load resistance times the filter capacitance. The peak reverse voltage across each diode is  $2.8 E_{rms}$ .

### Voltage Tripling and Quadrupling

A voltage-tripling circuit is shown in Fig. 16A. On one half of the ac cycle C1 is charged to the source voltage through the left-hand rectifier. On the opposite half of the cycle and middle rectifier conducts and C2 is charged to twice the source voltage, because it sees the transformer plus the charge in C1 as its source. (The left-hand rectifier is cut off on this half cycle.) At the same time the right-hand rectifier conducts and, with the transformer and the charge in C2 as the source, C3 is charged to three times the transformer voltage. The positive side of the

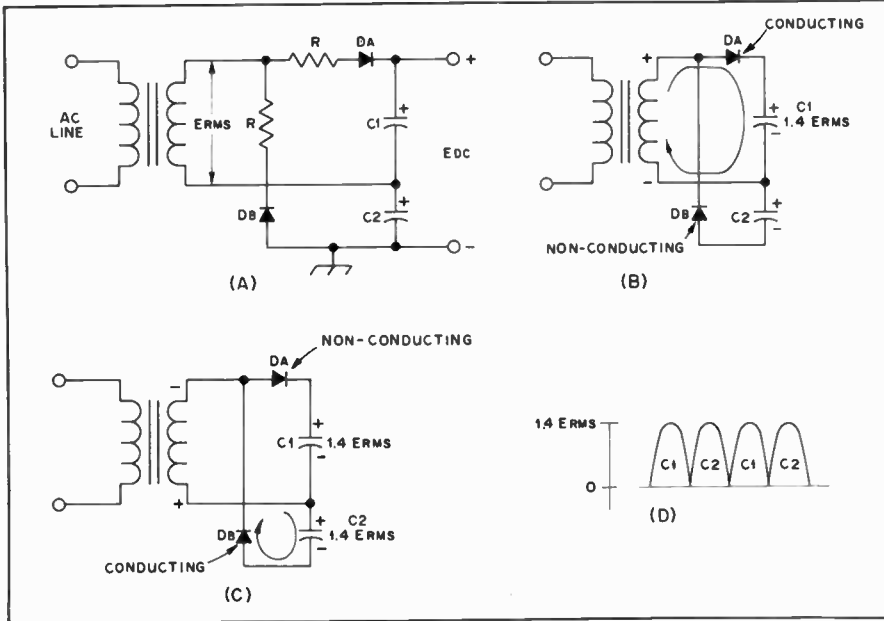


Fig. 14 — A full-wave voltage doubler is displayed at A. One half cycle is shown at B and the next half cycle at C. Each capacitor receives a charge during every cycle of input voltage. D illustrates how each capacitor is alternately charged.

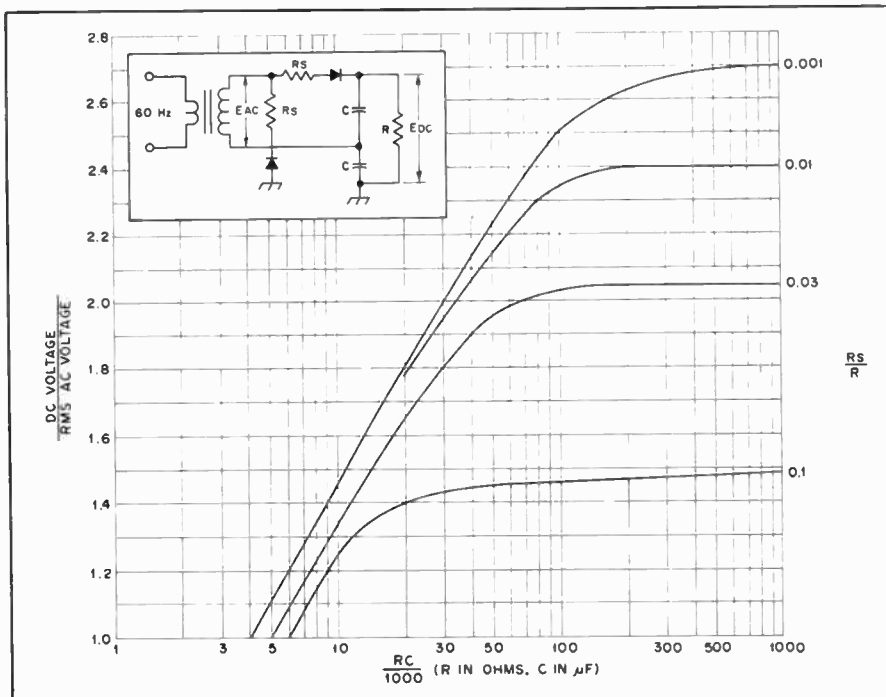


Fig. 15 — Dc output voltages from a full-wave voltage-doubling circuit as a function of the filter capacitances and load resistance. For the ratio  $R_s/R$  and for the RC product, resistances are in ohms and capacitance is in microfarads. Equal resistance values for  $R_s$  and equal capacitance values for C are assumed.



output can be grounded if the polarities of all of the capacitors and rectifiers are reversed.

The voltage-quadrupling circuit of Fig. 16B works in substantially similar fashion.

In either of the circuits of Fig. 16, the output voltage will approach an exact multiple (three or four, depending upon the circuit) of the peak ac voltage when the output current drain is low and the capacitance values are high.

### Plate and Filament Transformers: Volt-Ampere Rating

The number of volt-amperes delivered by a transformer depends upon the type of filter (capacitor or choke input) used, and upon the type of rectifier used (full-wave center tap, or full-wave bridge). With a capacitive-input filter the heating effect in the secondary is higher because of the high ratio of peak-to-average current. The volt-amperes handled by the transformer may be several times the watts delivered to the load. With a choke-input filter, provided the input choke has at least the critical inductance, the secondary volt-amperes can be calculated quite closely by the equation:

$$\text{(Full-wave ct) Sec VA} = \frac{0.707 EI}{1000}$$

$$\text{(Full-wave bridge) Sec VA} = \frac{EI}{1000}$$

where

E = total rms voltage of the secondary (between the outside ends in the case of a center-tapped winding)

I = dc output current in milliamperes (load current plus bleeder current)

The primary volt-amperes will be somewhat higher because of transformer losses.

### Broadcast and Television Replacement Transformers

Small power transformers of the type sold for replacement in broadcast and television receivers are usually designed for service in terms of use for several hours continuously with capacitor-input filters. In the usual type of amateur transmitter service, where most of the power is drawn intermittently for periods of several minutes with equivalent intervals in between, the published ratings can be exceeded without excessive transformer heating.

With a capacitor-input filter, it should be safe to draw 20 to 30 percent more current than the rated value. With a choke-input filter, an increase in current of about 50 percent is permissible. If a bridge rectifier is used, the output voltage will be approximately doubled. In this case, it should be possible in amateur transmitter service to draw the rated current, thus obtaining about twice the rated output power from the transformer.

This does not apply, of course, to amateur transmitter plate transformers, which usually are rated for intermittent service.

### Rewinding Power Transformers

Although the home winding of power transformers is a task that few amateurs undertake, the rewinding of a transformer secondary to give some desired voltage for powering filaments or a solid-state device is not difficult. It involves a matter of only a small number of turns and the wire is large enough to be handled easily. Often a receiver power transformer with a burned-out high-voltage winding or the power transformer from a discarded TV set can be converted into an entirely satisfactory transformer without great effort and with little expense. The average TV power transformer for a 17-inch or larger set is capable of delivering from 350 to 450 watts, continuous duty. If an amateur transmitter is being powered, the service is not continuous, so the ratings can be increased by a factor of 40 or 50 percent without danger of overloading the transformer.

The primary volt-ampere rating of the transformer to be rewound, if known, can be used to determine its power-handling capability. The secondary volt-ampere rating will be 10 to 20 percent less than the primary rating. The power rating may also be determined approximately from the cross-sectional area of the core which is inside the windings. Fig. 17 shows the method of determining the area, and Fig. 18 may be used to convert this information into a power rating.

Before disconnecting the winding leads from their terminals, each should be marked for identification. In removing the core laminations, care should be taken to note the manner in which the core is assembled, so that the reassembling will be done in the same manner. Most transformers have secondaries wound over the primary, while in some the order is reversed. In case the secondaries are on the inside, the turns can be pulled out from the center after slitting and removing the fiber core.

The turns removed from one of the original filament windings of known voltage should be carefully counted as the winding is removed. This will give the number of turns per volt and the same figure should be used in determining the number of turns for the new secondary. For instance, if the old filament winding was rated at 5 volts and had 15 turns, this is  $15/5 = 3$  turns per volt. If the new secondary is to deliver 18 volts, the required number of turns on the new winding will be  $18 \times 3 = 54$  turns.

In winding a transformer, the size of wire is an important factor in the heat developed in operation. A cross-sectional area of 1000 circular mils per ampere is conservative. A value commonly used in

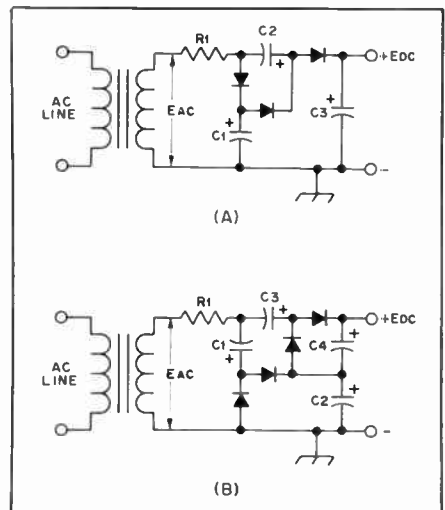


Fig. 16 — Voltage-multiplying circuits with one side of transformer secondary grounded. (A) Voltage tripler, (B) voltage quadrupler.

Capacitances are typically 20 to 50  $\mu\text{F}$  depending upon output current demand. Dc ratings of capacitors are related to  $E_{\text{peak}}$  (1.4  $E_{\text{ac}}$ ):

- C1 — Greater than  $E_{\text{peak}}$
- C2 — Greater than  $2E_{\text{peak}}$
- C3 — Greater than  $3E_{\text{peak}}$
- C4 — Greater than  $4E_{\text{peak}}$

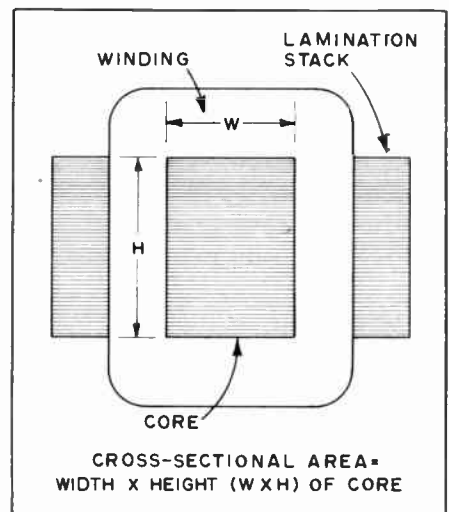


Fig. 17 — Cross-sectional drawing of a typical power transformer. Multiplying the height (or thickness of the laminations) by the width of the central core area in inches gives the value to be applied to Fig. 18.

amateur-service transformers is 700 cmil/A. The larger the cmil/A figure, the cooler the transformer will run. The current rating in amperes of various wire sizes is shown in the copper-wire table in another chapter. If the transformer being rewound is a filament transformer, it may be necessary to choose the wire size carefully to fit the small available space. On the other hand, if the transformer is a power unit with the high-voltage winding removed, there should be plenty of room for a size of wire that will conservatively

handle the required current.

After the first layer of turns is put on during rewinding, secure the ends with cellulose tape. Each layer should be insulated from the next; ordinary household waxed paper can be used for the purpose, a single layer being adequate. Sheets cut to size beforehand may be secured over each layer with tape. Be sure to bring all leads out the same side of the core so the covers will go in place when the unit is completed. When the last layer of the winding is put on, use two sheets of waxed paper, and then cover those with vinyl electrical tape, keeping the tape as taut as possible. This will add mechanical strength to the assembly.

The laminations and housing are assembled in just the opposite sequence to that followed in disassembly. Use a light coating of shellac between each lamination. During reassembly, the lamination stack may be compressed by clamping in a vise. If the last few lamination strips cannot be replaced, it is better to omit them than to force the unit together.

### Rectifier Ratings: Semiconductors

Silicon rectifiers are being used almost exclusively in power supplies for amateur equipment. Types are available to replace high-vacuum and mercury-vapor rectifiers. The semiconductors have the advantages of compactness, low internal voltage drop, low operating temperature and high current-handling capability. Also, no filament transformers are required.

Silicon rectifiers are available in a wide range of voltage and current ratings. In peak reverse voltage ratings of 600 or less, silicon rectifiers carry current ratings as high as 400 amperes, and at 1000 PRV the current ratings may be several amperes or so. The extreme compactness of silicon types makes feasible the stacking of several units in series for higher voltages. Standard stacks are available that will handle up to 10,000 PRV at a dc load current of 500 mA, although the amateur can do much better, economically, by stacking the rectifiers himself.

### Protection of Silicon Power Diodes

The important specifications of a silicon diode are

- 1) PRV (or PIV), the peak reverse (or peak inverse) voltage.
- 2)  $I_o$ , the average dc current rating.
- 3)  $I_{REP}$ , the peak repetitive forward current.
- 4)  $I_{SURGE}$ , the peak one-cycle surge current. The first two specifications appear in most catalogs. The last two often do not, but they are very important.

Since the rectifier never allows current to flow more than half the time, when it does conduct it has to pass at least twice the average direct current. With a capacitor-input filter, the rectifier conducts much less than half the time, so that when it does conduct, it may pass as much

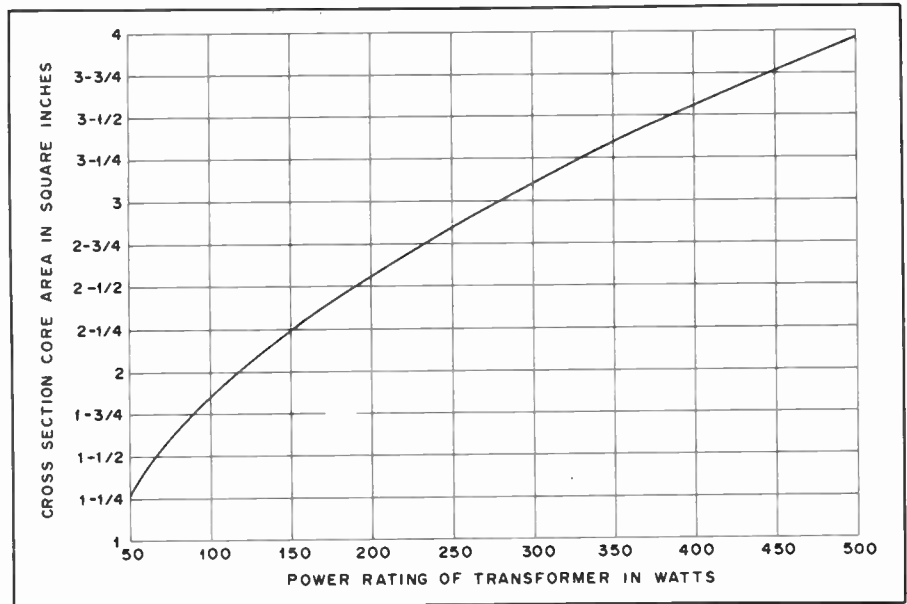


Fig. 18 — Power-handling capability of a transformer versus cross-sectional area of core.

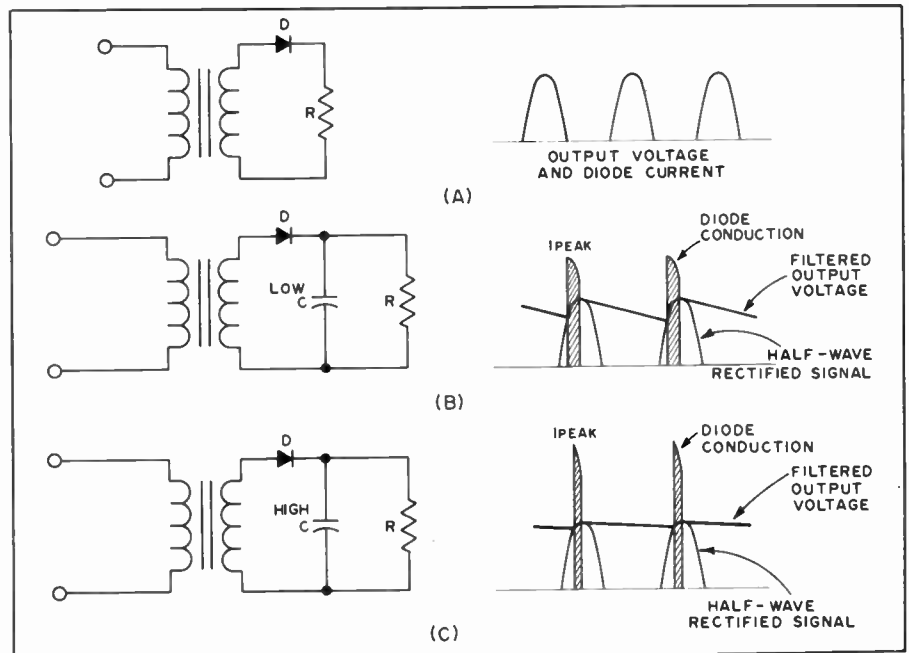


Fig. 19 — The circuit shown at A is a simple half-wave rectifier with a resistive load. The waveform shown to the right is that of output voltage and diode current. B illustrates how the diode current is modified by the addition of a capacitor filter. Since this time period is usually only a short portion of a cycle, the peak current will be quite high. C shows an even higher peak current. This is due to the larger capacitor which effectively shortens the conduction period of the diode.

as 10 to 20 times the average dc current, under certain conditions. This is shown in Fig. 19. At A is a simple half-wave rectifier with a resistive load. The waveform to the right of the drawing shows the output voltage along with the diode current. At B and C there are two periods of operation to consider. After the capacitor is charged to the peak-rectified voltage a period of diode nonconduction elapses while the output voltage discharges through the load.

As the voltage begins to rise on the next positive pulse a point is reached where the rectified voltage equals the stored voltage in the capacitor. As the voltage rises beyond that point the diode begins to supply current. The diode will continue to conduct until the waveform reaches the crest, as shown. Since the diode must pass a current equal to that of the load over a short period of a cycle the current will be high. The larger the capacitor for a given load,

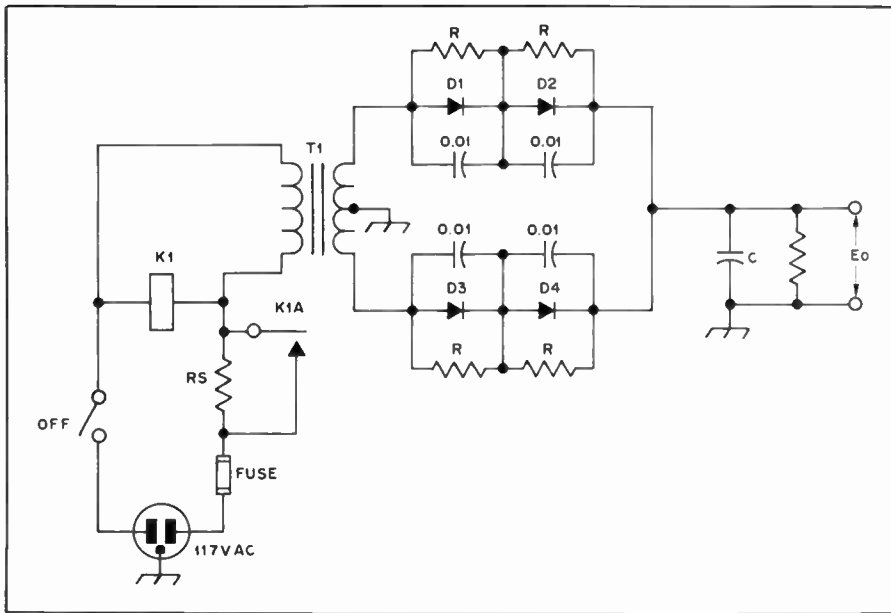


Fig. 20 — The primary circuit of T1 shows how a 117-volt ac relay and a series dropping resistor,  $R_s$ , can provide surge protection while C charges. When silicon rectifiers are connected in series for high-voltage operation, the inverse voltage does not divide equally. The reverse voltage drops can be equalized by using equalizing resistors, as shown in the secondary circuit. To protect against voltage "spikes" that may damage an individual rectifier, each rectifier should be bypassed by a 0.01- $\mu$ F capacitor. Connected as shown two 400-PRV silicon rectifiers can be used as an 800-PRV rectifier, although it is preferable to include a safety factor and call it a "750-PRV" rectifier. The rectifiers, D1 through D4, should be the same type (same type number and ratings).

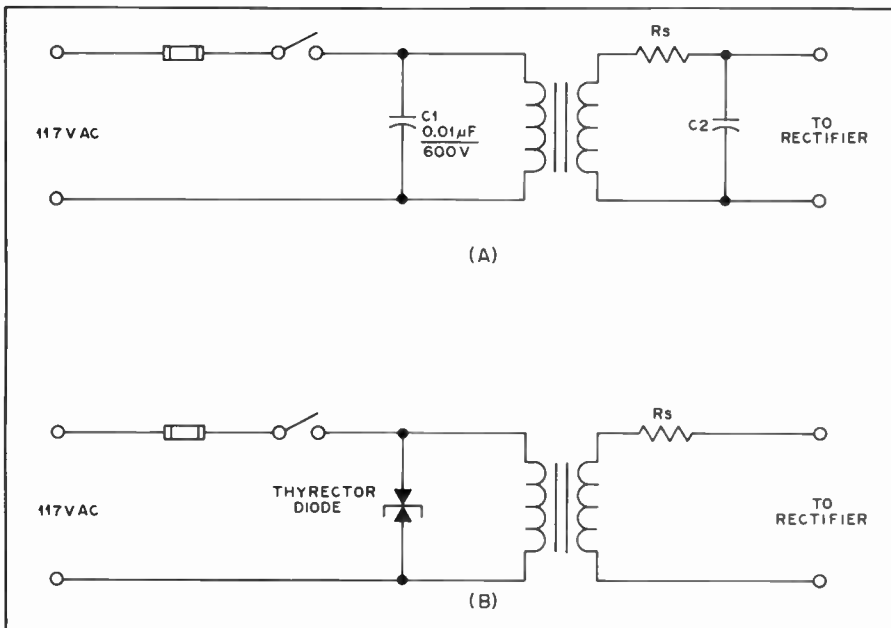


Fig. 21 — Methods of suppressing line transients. See text.

the shorter the diode conduction time and the higher the peak repetitive current ( $I_{REP}$ ).

When the supply is first turned on, the discharged input capacitor looks like a dead short, and the rectifier passes a very heavy current. This is  $I_{SURGE}$ . The maximum  $I_{SURGE}$  rating is usually for a duration of one cycle (at 60 Hz), or about 16.7 milliseconds.

If a manufacturer's data sheet is not available, an educated guess about a

diode's capability can be made by using these rules of thumb for silicon diodes of the type commonly used in amateur power supplies:

**Rule 1)** The maximum  $I_{REP}$  rating can be assumed to be approximately four times the maximum  $I_o$  rating.

**Rule 2)** The maximum  $I_{SURGE}$  rating can be assumed to be approximately 12 times the maximum  $I_o$  rating. (This should provide a reasonable safety factor.

Silicon rectifiers with 750-mA dc ratings, as an example, seldom have 1-cycle surge ratings of less than 15 amperes; some are rated up to 35 amperes or more.) From this then, it can be seen that the rectifier should be selected on the basis of  $I_{SURGE}$  and not on  $I_o$  ratings.

### Thermal Protection

The junction of a diode is quite small, hence it must operate at a high current density. The heat-handling capability is, therefore, quite small. Normally, this is not a prime consideration in high-voltage, low-current supplies. When using high-current rectifiers at or near their maximum ratings (usually 2-ampere or larger stud-mount rectifiers), some form of heat sinking is necessary. Frequently, mounting the rectifier on the main chassis — directly, or by means of thin mica insulating washers — will suffice. If insulated from the chassis, a thin layer of silicone grease should be used between the diode and the insulator, and between the insulator and the chassis to assure good heat conduction. Large high-current rectifiers often require special heat sinks to maintain a safe operating temperature. Forced-air cooling is sometimes used as a further aid. Safe case temperatures are usually given in the manufacturer's data sheets and should be observed if the maximum capabilities of the diode are to be realized.

### Surge Protection

Each time the power supply is activated, assuming the input filter capacitor has been discharged, the rectifiers must look into what represents a dead short. Some form of surge protection is usually necessary to protect the diodes until the input capacitor becomes nearly charged. Although the dc resistance of the transformer secondary can be relied upon in some instances to provide ample surge-current limiting, it is seldom enough on high-voltage power supplies to be suitable. Series resistors can be installed between the secondary and the rectifier strings, but are a deterrent to good voltage regulation. By installing a surge-limiting device in the primary circuit of the plate transformer, the need for series resistors in the secondary circuit can be avoided. A practical method for primary-circuit surge control is shown in Fig. 20. The resistor,  $R_s$ , introduces a voltage drop in the primary feed to T1 until C is nearly charged. Then, after C becomes partially charged, the voltage drop across  $R_s$  lessens and allows K1 to pull in, thus applying full primary power to T1 as K1A shorts out  $R_s$ .  $R_s$  is usually a 25-watt resistor whose resistance is somewhere between 15 and 50 ohms, depending upon the power supply characteristics.

### Transient Problems

A common cause of trouble is transient voltages on the ac power line. These are



short spikes, mostly, that can temporarily increase the voltage seen by the rectifier to values much higher than the normal transformer voltage. They come from distant lightning strokes, electric motors turning on and off, and so on. Transients cause unexpected, and often unexplained, loss of silicon rectifiers.

It's always wise to suppress line transients, and it can be easily done. Fig. 21 A shows one way. C1 looks like 280,000 ohms at 60 Hz, but to a sharp transient (which has only high-frequency components), it is an effective bypass. C2 provides additional protection on the secondary side of the transformer. It should be 0.01  $\mu$ F for transformer voltages of 100 or less, and 0.001  $\mu$ F for high-voltage transformers.

Fig. 21B shows another transient-suppression method using selenium suppressor diodes. The diodes do not conduct unless the peak voltage becomes abnormally high. Then they clip the transient peaks. General Electric sells protective diodes under the trade name, "Thyrector." Sarkes-Tarzian uses the descriptive name, "Klipvolt."

Transient voltages can go as high as twice the normal line voltage before the suppressor diodes clip the peaks. Capacitors cannot give perfect suppression either. Thus, it is a good idea to use power-supply rectifiers rated at about twice the expected PRV.

### Diodes in Series

Where the PRV rating of a single diode is not sufficient for the application, similar diodes may be used in series. (Two 500-PRV diodes in series will withstand 1000 PRV, and so on.) When this is done, a resistor and a capacitor should be placed across each diode in the string to equalize the PRV drops and to guard against transient voltage spikes, as shown in Fig. 22A. Even though the diodes are of the same type and have the same PRV rating, they may have widely different back resistances when they are cut off. The reverse voltage divides according to Ohm's Law, and the diode with the higher back resistance will have the higher voltage developed across it. The diode may break down.

If we put a swamping resistor across each diode, R as shown in Fig. 22A, the resultant resistance across each diode will be almost the same, and the back voltage will divide almost equally. A good rule of thumb for resistor size is this: Multiply the PRV rating of the diode by 500 ohms. For example, a 500-PRV diode should be shunted by 500  $\times$  500, or 250,000 ohms.

The shift from forward conduction to high back resistance does not take place instantly in a silicon diode. Some diodes take longer than others to develop high back resistance. To protect the "fast" diodes in a series string until all the diodes are properly cut off, a 0.01- $\mu$ F capacitor

should be placed across each diode. Fig. 22A shows the complete series-diode circuit. The capacitors should be non-inductive, ceramic disk, for example, and should be well matched. Use 10-percent-tolerance capacitors if possible.

### Diodes in Parallel

Diodes can be placed in parallel to increase current-handling capability. Equalizing resistors should be added as shown in Fig. 22B. Without the resistors, one diode may take most of the current. The resistors should be selected to have about a 1-volt drop at the expected peak current.

### Voltage Dropping Resistor

Certain plates and screens of the various tubes in a transmitter or receiver often require a variety of operating voltages differing from the output voltage of an available power supply. In most cases, it is not economically feasible to provide a separate power supply for each of the required voltages. If the current drawn by an electrode (or combination of electrodes operating at the same voltage) is reasonably constant under normal operating conditions, the required voltage may be obtained from a supply of higher voltage by means of a voltage-dropping resistor in series, as shown in Fig. 23A. The value of the series resistor, R<sub>1</sub>, may be obtained from Ohm's Law,

$$R = \frac{E_d}{I}$$

where

$E_d$  = voltage drop required from the supply voltage to the desired voltage.  
 $I$  = total rated current of the load

Example: The plate of the tube in one stage and the screens of the tubes in two other stages require an operating voltage of 250. The nearest available supply voltage is 400 and the total of the rated plate and screen currents is 75 mA. The required resistance is

$$R = \frac{400 - 250}{.075} = \frac{150}{.075} = 2000 \text{ ohms}$$

The power rating of the resistor is obtained from  $P$  (watts) =  $I^2R$  =  $(.075)^2 \times (2000)$  = 11.2 watts. A 20-watt resistor is the nearest safe rating to be used.

### Voltage Dividers

The regulation of the voltage obtained in this manner obviously is poor, since any change in current through the resistor will cause a directly proportional change in the voltage drop across the resistor. The regulation can be improved somewhat by connecting a second resistor from the low-voltage end of the first to the negative power-supply terminal, as shown in Fig. 23B. Such an arrangement constitutes a

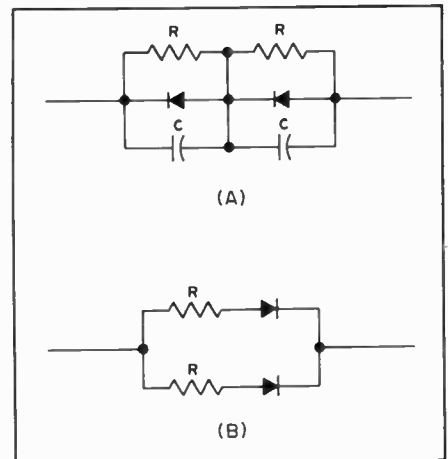


Fig. 22 — A — Diodes connected in series should be shunted with equalizing resistors and spike-suppressing capacitors. B — Diodes connected in parallel should be series current equalizing resistors.

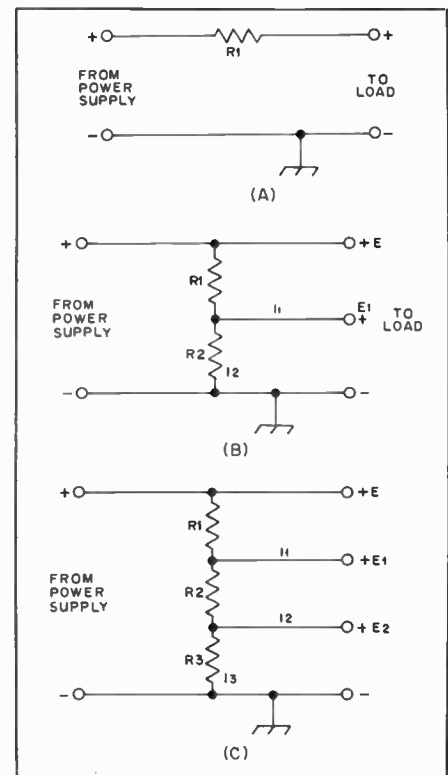


Fig. 23 — A — Series voltage-dropping resistor. B — Simple voltage divider.

$$R_2 = \frac{E_1}{I_2}, \quad R_1 = \frac{E - E_1}{I_1 + I_2}$$

$I_2$  must be assumed.

C — Multiple divider circuit.

$$R_3 = \frac{E_2}{I_3}, \quad R_2 = \frac{E_1 - E_2}{I_1 + I_3}$$

$$R_1 = \frac{E - E_1}{I_1 + I_2 + I_3}$$

$I_3$  must be assumed.



**voltage divider.** The second resistor, R2, acts as a constant load for the first, R1, so that any variation in current from the tap becomes a smaller percentage of the total current through R1. The heavier the current drawn by the resistors when they alone are connected across the supply, the better will be the voltage regulation at the tap.

Such a voltage divider may have more than a single tap for the purpose of obtaining more than one value of voltage. A typical arrangement is shown in Fig. 23C. The terminal voltage is E, and two taps are provided to give lower voltages, E1 and E2, at currents I1 and I2 respectively. The smaller the resistance between taps in proportion to the total resistance, the lower is the voltage between the taps. The voltage divider in the figure is made up of separate resistances, R1, R2 and R3. R3 carries only the bleeder current, I3; R2 carries I2 in addition to I3; R1 carries I1, I2 and I3. To calculate the resistances required, a bleeder current, I3, must be assumed; generally it is low compared with the total load current (10 percent or so). Then the required values can be calculated as shown in the caption of Fig. 23, I being in decimal parts of an ampere.

The method may be extended to any desired number of taps, each resistance section being calculated by Ohm's Law using the needed voltage drop across it and the total current through it. The power dissipated by each section may be calculated by multiplying I and E or I<sup>2</sup> and R.

### Voltage Stabilization: Gaseous Regulator Tubes

There is frequent need for maintaining the voltage applied to a low-voltage low-current circuit at a practically constant value, regardless of the voltage regulation of the power supply or variations in load current. In such applications, gaseous regulator tubes (0B2/VR105, 0A2/VR150, etc.) can be used to good advantage. The voltage drop across such tubes is constant over a moderately wide current range. Tubes are available for regulated voltages near 150, 105, 90 and 75 volts.

The fundamental circuit for a gaseous regulator is shown in Fig. 24. The tube is connected in series with a *limiting resistor*, R1, across a source of voltage that must be higher than the starting voltage. The starting voltage is about 30 to 40 percent higher than the operating voltage. The load is connected in parallel with the tube. For stable operation, a minimum tube current of 5 to 10 mA is required. The maximum permissible current with most types is 40 mA; consequently, the load current cannot exceed 30 to 35 mA if the voltage is to be stabilized over a range from zero to maximum load. A single VR tube may also be used to regulate the

voltage to a load current of almost any value as long as the *variation* in the current does not exceed 30 to 35 mA. If, for example, the average load current is 100 mA, a VR tube may be used to hold the voltage constant provided the current does not fall below 85 mA or rise above 115 mA.

The value of the limiting resistor must lie between that which just permits minimum tube current to flow and that which just passes the maximum permissible tube current when there is no load current. The latter value is generally used. It is given by the equation:

$$R = \frac{(E_s - E_r)}{I}$$

where

R = limiting resistance in ohms

E<sub>s</sub> = voltage of the source across which the tube and resistor are connected.

E<sub>r</sub> = rated voltage drop across the regulator tube.

I = maximum tube current in amperes (usually 40 mA, or 0.04 A)

Two tubes may be used in series to give a higher regulated voltage than is obtainable with one, and also to give two values of regulated voltage. Regulation of the order of one percent can be obtained with these regulator tubes when they are operated within their proper current range. The capacitance in shunt with a VR tube should be limited to 0.1 μF or less. Larger values may cause the tube drop to oscillate between the operating and starting voltages.

### Zener Diode Regulation

A Zener diode (named after Dr. Carl Zener) can be used to stabilize a voltage source in much the same way as when the gaseous regulator tube is used. The typical circuit is shown in Fig. 25A. Note that the cathode side of the diode is connected to the positive side of the supply. The electrical characteristics of a Zener diode under conditions of forward and reverse voltage are given in chapter 4.

Zener diodes are available in a wide variety of voltages and power ratings. The voltages range from less than two to a few hundred, while the power ratings (power the diode can dissipate) run from less than 0.25 watt to 50 watts. The ability of the Zener diode to stabilize a voltage is dependent upon the conducting impedance of the diode, which can be as low as one ohm or less in a low-voltage, high-power diode to as high as a thousand ohms in a low-power, high-voltage diode.

### Diode Power Dissipation

Unlike gaseous regulator tubes, Zener diodes of a particular voltage rating have varied maximum current capabilities, depending upon the power ratings of each of the diodes. The power dissipated in a diode is the product of the voltage across

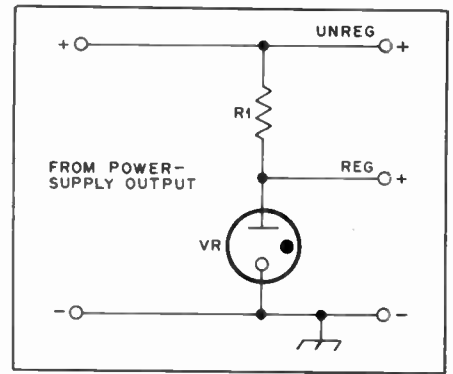


Fig. 24 — Voltage stabilization circuit using a VR tube. A negative-supply output may be regulated by reversing the polarity of the power-supply connections and the VR-tube connections from those shown here.

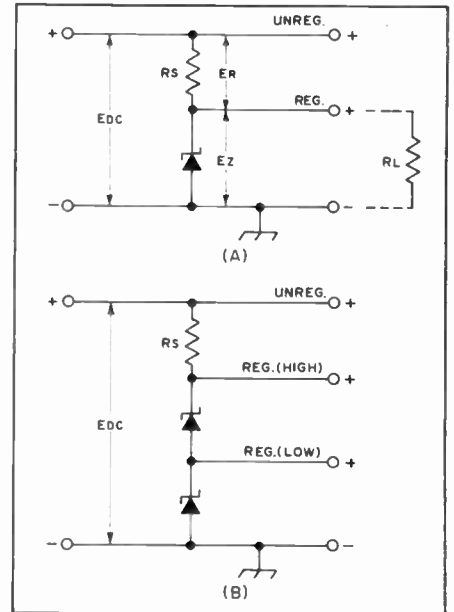


Fig. 25 — Zener-diode voltage regulation. The voltage from a negative supply may be regulated by reversing the power-supply connections and the diode polarities.

it and the current through it. Conversely, the maximum current a particular diode may safely conduct equals its power rating divided by its voltage rating. Thus, a 10-V, 50-W Zener diode, if operated at its maximum dissipation rating, would conduct 5 amperes of current. A 10-V 1-W diode, on the other hand, could safely conduct no more than 0.1 A, or 100 mA. The conducting impedance of a diode is its voltage rating divided by the current flowing through it, and in the above examples would be 2 ohms for the 50-W diode, and 100 ohms for the 1-W diode. Disregarding small voltage changes which may occur, the conducting impedance of a given diode is a function of the current flowing through it, varying in inverse proportion.

The power-handling capability of most Zener diodes is rated at 25°C, or approximately room temperature. If the diode is

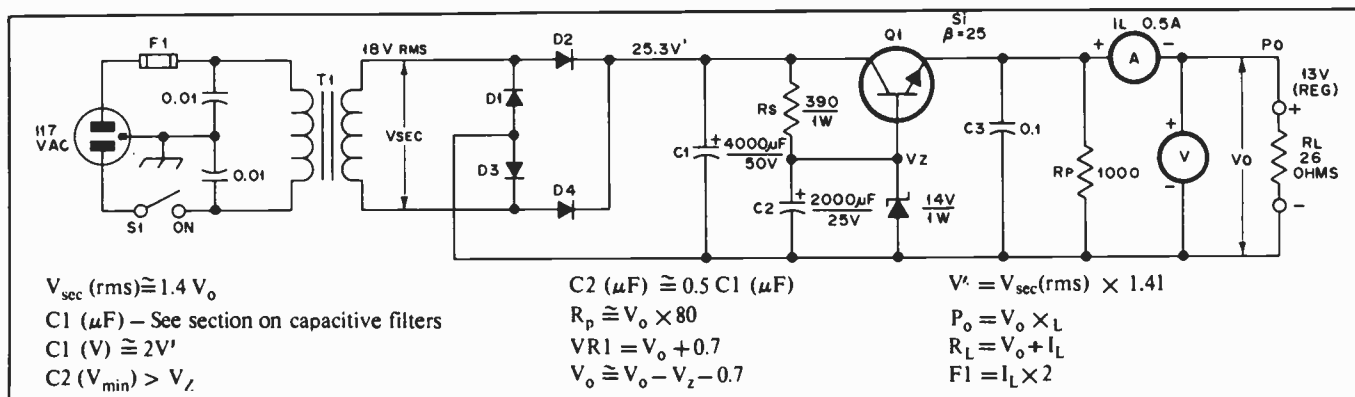


Fig. 26 — Illustration of a power supply with regulation. A pass transistor, Q1, is used to extend the range of the Zener-diode regulator.

operated in a higher ambient temperature, its power capability must be derated. A typical 1-watt diode can safely dissipate only 1/2 watt at 100°C.

### Limiting Resistance

The value of  $R_S$  in Fig. 25 is determined by the load requirements. If  $R_S$  is too large the diode will be unable to regulate at large values of  $I_L$ , the current through  $R_L$ . If  $R_S$  is too small, the diode dissipation rating may be exceeded at low values of  $I_L$ . The optimum value for  $R_S$  can be calculated by:

$$R_S = \frac{E_{DC}(\text{min}) - E_Z}{1.1 I_L(\text{max})}$$

When  $R_S$  is known, the maximum dissipation of the diode,  $P_D$ , may be determined by

$$P_D = \left[ \frac{E_{DC}(\text{max}) - E_Z}{R_S} - I_L(\text{min}) \right] E_Z$$

In the first equation, conditions are set up for the Zener diode to draw 1/10 the maximum load current. This assures diode regulation under maximum load.

Example: A 12-volt source is to supply a circuit requiring 9 volts. The load current varies between 200 and 350 mA.

$$E_Z = 9.1 \text{ V (nearest available value)}$$

$$R_S = \frac{12 - 9.1}{1.1 \times 0.35} = \frac{2.9}{0.385} = 7.5 \text{ ohms}$$

$$P_D = \left[ \frac{12 - 9.1}{7.5} - 0.2 \right] 9.1$$

$$= 0.185 \times 9.1 = 1.7 \text{ W}$$

The nearest available dissipation rating above 1.7 W is 5; therefore, a 9.1-V 5-W Zener diode should be used. Such a rating, it may be noted, will cause the diode to be in the safe dissipation range even though the load is completely disconnected [ $I_L(\text{min}) = 0$ ].

### Obtaining Other Voltages

Fig. 25B shows how two Zener diodes may be used in series to obtain regulated voltages not normally obtainable from a

single Zener diode, and also to give two values of regulated voltage. The diodes need not have equal breakdown voltages, because the arrangement is self equalizing. However, the current-handling capability of each diode should be taken into account. The limiting resistor may be calculated as above, taking the sum of the diode voltages as  $E_Z$ , and the sum of the load currents as  $I_L$ .

### Electronic Voltage Regulation

Several circuits have been developed for regulating the voltage output of a power supply electronically. While more complicated than the VR-tube and Zener-diode circuits, they will handle higher voltage and current variations, and the output voltage may be varied continuously over a wide range.

Voltage regulators fall into two basic types. In the type most commonly used by amateurs, the dc supply delivers a voltage higher than that which is available at the output of the regulator, and the regulated voltage is obtained by dropping the voltage down to a lower value through a dropping "resistor." Regulation is accomplished by varying either the current through a fixed dropping resistance as changes in input voltage or load currents occur (as in the VR-tube and Zener-diode regulator circuits), or by varying the equivalent resistive value of the dropping element with such changes. This latter technique is used in electronic regulators where the voltage-dropping element is a vacuum tube or a transistor, rather than an actual resistor. By varying the dc voltage at the grid or current at the base of these elements, the conductivity of the device may be varied as necessary to hold the output voltage constant. In solid-state regulators the series-dropping element is called a pass transistor. Power transistors are available which will handle several amperes of current at several hundred volts, but solid-state regulators of this type are usually operated at potentials below 100 volts.

The second type of regulator is a switching type, where the voltage from the dc source is rapidly switched on and off

(electronically). The average dc voltage available from the regulator is proportional to the duty cycle of the switching wave form, or the ratio of the on time to the total period of the switching cycle. Switching frequencies of several kilohertz are normally used to avoid the need for extensive filtering to smooth the switching frequency from the dc output.

The above information pertains essentially to voltage regulators. A circuit can also be constructed to provide current regulation. Such regulation is usually obtained in the form of current limitation — to a maximum value which is either preset or adjustable, depending on the circuit. Relatively simple circuits, such as described later, can be used to provide current limiting only. Current limiting circuitry may also be used in conjunction with voltage regulators.

### Discrete Component Regulators

The previous section outlines some of the limitations when using Zener diodes as regulators. Greater current amounts can be accommodated if the Zener diode is used as a reference at low current, permitting the bulk of the load current to flow through a series pass transistor (Q1 of Fig. 26). An added benefit in using a pass transistor is that of reduced ripple on the output waveform. This technique is commonly referred to as "electronic filtering."

Q1 of Fig. 26 can be thought of as a simple emitter-follower dc amplifier. It increases the load resistance seen by the Zener diode by a factor of beta ( $\beta$ ). In this circuit arrangement D5 is required to supply only the base current for Q1. The net result is that the load regulation and ripple characteristics are improved by a factor of beta. Addition of C2 reduces the ripple even more, although many simple supplies such as this do not make use of a capacitor in that part of the circuit.

The primary limitation of this circuit is that Q1 can be destroyed almost immediately if a severe overload occurs at  $R_L$ . The fuse cannot blow fast enough to protect Q1. In order to protect Q1 in case of an accidental short at the output, a

current limiting circuit is required. An example of a suitable circuit is shown in Fig. 27.

It should be mentioned that the greater the value of transformer secondary voltage, the higher the power dissipation in Q1. This not only reduces the overall efficiency of the power supply, but requires stringent heat sinking at Q1.

### Design Example

**Example:** Design a regulated, well-filtered, 13-volt dc supply capable of delivering 0.5 A, using the circuit of Fig. 26. Calculate the ratings for all components. A standard 18-volt secondary transformer is to be used.

Information on calculating the transformer, diode and input capacitor ratings were given earlier in this chapter and will not be repeated here. In order to calculate the value of  $R_S$  in Fig. 26 the base current of Q1 must be known. The base current is approximately equal to the emitter current of Q1 in amperes divided by beta. The transistor beta can be found in the manufacturer's data sheet, or measured with simple test equipment ( $\beta = I_c/I_b$ ). Since the beta spread for a particular type of transistor — 2N3055 for example, where it is specified as 25 to 70 — is a fairly unknown quantity, more precise calculations for Fig. 26 will result if the transistor beta is tested before the calculations are done. A conservative approach is to design for beta minimum of the transistor used. Calculating  $I_b$ :

$$I_b = \frac{0.5}{25} = 0.02A = 20 \text{ mA}$$

As pointed out earlier, in order for D5 to regulate properly it is necessary that a fair portion of the current flowing through  $R_S$  should be drawn by D5. The resistor will have 0.02 A flowing through it as calculated above (base current of Q1). A conservative amount of 10 mA will be used for the Zener diode current bringing the total current through  $R_S$  to 0.03 A or 30 mA. From this, the value of  $R_S$  can be calculated as follows:

$$R_S = \frac{(V' - V_Z)}{I_{R_S}} = \frac{(25.3 - 14)}{0.03} = 376 \text{ ohms}$$

The nearest standard ohmic value for  $R_S$  is 390. The wattage ratings for  $R_S$  and D5 can be obtained with the aid of the formulas given earlier for Zener-diode regulators.

The power rating for Q1 will be calculated next. The power dissipation of Q1 is equal to the emitter current times the collector-to-emitter voltage. Calculate as follows:

$$P_{Q1} = I_E \times V_{CE}$$

where

$V_{CE}$  = the desired  $V' - (V_Z - V_{BE})$ ,  
and  $V_{BE}$  is approximately 0.7 V for a silicon transistor.

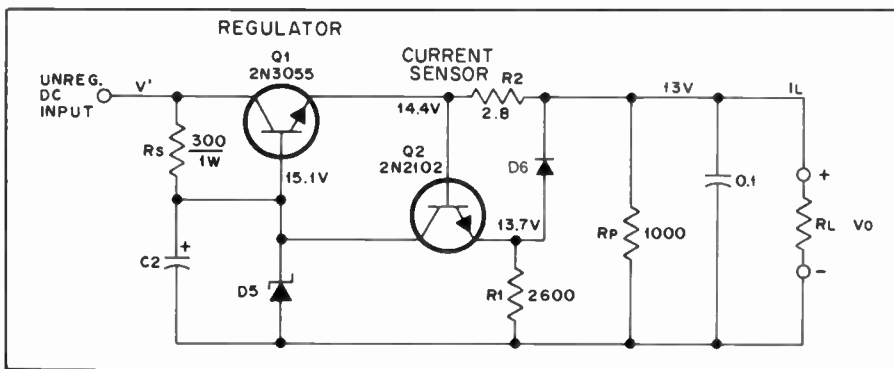


Fig. 27 — Overload protection for a regulated supply can be effected by addition of a current-overload protective circuit.

Therefore:

$$P_{Q1} = 0.5A \times 12V = 6 \text{ watts}$$

It is a good idea to choose a transistor for Q1 that has at least twice the rating calculated. In this example a transistor with a power dissipation rating 12 watts or more would be used.

The 0.01- $\mu$ F capacitors at the primary of T1 serve two functions. They act as transient suppressors and help prevent rf energy from entering the power-supply regulator.

### Current Limiting for Discrete-Component Regulators

Damage to Q1 of Fig. 26 can occur when the load current exceeds the safe amount. Fig. 27 illustrates a simple current-limiter circuit that will protect Q1. All of the load current is routed through R2. A voltage difference will exist across R2, the amount being dependent upon the exact load current at a given time. When the load current exceeds a predetermined safe value, the voltage drop across R2 will forward bias Q2 and cause it to conduct. Since D6 is a silicon diode, and because Q2 is a silicon transistor, the combined voltage drops through them (roughly 0.7 V each) will be 1.4 V. Therefore the voltage drop across R2 must exceed 1.4 V before Q2 can turn on. This being the case, R2 is chosen for a value that provides a drop of 1.4 V when the maximum safe load current is drawn. In this instance 1.4 volts will be seen when  $I_L$  reaches 0.5A.

When Q2 turns on, some of the current through  $R_S$  flows through Q2, thereby depriving Q1 of some of its base current. This action, depending upon the amount of Q1 base current at a precise moment, cuts off Q1 conduction to some degree, thus limiting the flow of current through it.

### High-Current-Output Regulators

When a single pass transistor is not available to handle the current which may be required from a regulator, the current-handling capability may be increased by connecting two or more pass transistors in parallel. The circuits at B and C of Fig. 28 show the method of connection. The

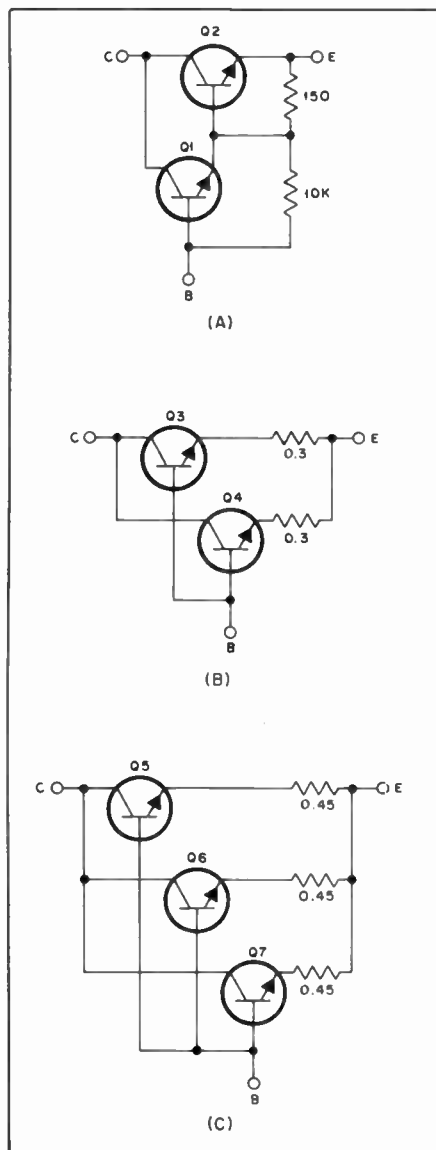


Fig. 28 — At A, a Darlington-connected pair for use as the pass element in a series-regulating circuit. At B and C, the method of connecting two or more transistors in parallel for high current output. Resistances are in ohms. The circuit at A may be used for load currents from 100 mA to 5 A, at B for currents from 6 to 10 A, and at C for currents from 9 to 15 A. Q1 — Motorola MJE 340 or equivalent. Q2-Q7, incl. — Power transistor such as 2N3055 or 2N3772.



resistances in the emitter leads of each transistor are necessary to equalize the currents.

### Fixed-Voltage IC Regulators

The modern trend in regulators is toward the use of three-terminal devices commonly referred to as three-terminal regulators. Inside each regulator is a reference, a high-gain error amplifier, sensing resistors and transistors, and a pass element. Some of the more sophisticated units have thermal shutdown, over-voltage protection and current fold-back. Many of the regulators currently on the market are virtually destruction-proof. Several supplies using these ICs are featured in the construction section of this chapter.

Three-terminal regulators (a connection for unregulated dc input, regulated dc output and ground) are available in a wide range of voltage and current ratings. Fairchild, National and Motorola are perhaps the three largest suppliers of these regulators at present. It is easy to see why regulators of this sort are so popular when one considers the low price and the number of individual components they can replace. The regulators are available in several different package styles — TO-3, TO-39, TO-66, TO-220 and dual in-line (DIP), to name just a few.

Three-terminal regulators are available as positive or negative types. In most cases, a positive regulator is used to regulate a positive voltage and a negative regulator a negative voltage. However, depending on the systems ground requirements, each regulator type may be used to regulate the "opposite" voltage.

Figs. 29A and B illustrate how the regulators are used in the conventional mode. Several regulators can be used with a common-input supply to deliver several voltages with a common ground. Negative regulators may be used in the same manner. If no other common supplies operate off the input supply to the regulator, the circuits of Figs. 29C and D may be used to regulate positive voltages with a negative regulator and vice versa. In these configurations the input supply is floated; neither side of the input is tied to the system ground.

When choosing a three-terminal regulator for a given application the important specifications to look for are maximum output current, maximum output voltage, minimum and maximum input voltage, line regulation, load regulation and power dissipation.

In use, these regulators require an adequate heat sink since they may be called on to dissipate a fair amount of power. Also, since the chip contains a high-gain error amplifier, bypassing of the input and output leads is essential to stable operation (See Fig. 30). Most manufacturers recommend bypassing the input and output directly at the leads

where they protrude through the heat sink. Tantalum capacitors are usually recommended because of their excellent bypass capabilities up into the vhf range.

### Adjustable-Voltage IC Regulators

Relatively new on the electronic scene are high-current, adjustable voltage regulators. These ICs require little more than an external potentiometer for an adjustable voltage range from 5 to 24 volts at up to 5 amperes. The unit price on these items is currently around \$6 making them ideal for a test bench power supply. An adjustable-voltage power supply using the Fairchild 78HG series of regulator is described in the construction section of this chapter. The same precautions should be taken with these types of regulators as with the fixed-voltage units. Proper heat sinking and lead bypassing is essential for proper circuit operation.

### A 12-Volt 3-Ampere Power Supply

Shown in Fig. 31 is a no-frills 12-volt supply capable of continuous operation at the 3-ampere level. Many low-power hf transceivers and most vhf-fm transceivers require voltages and currents on this order. Power supplies of this type purchased from the manufacturers can be quite costly. Described here is a very simple to build and relatively inexpensive (around \$20 using all new components) alternative.

The schematic diagram for the power supply is shown in Fig. 32. As can be seen, the circuit is simplicity itself. A transformer, two diodes, three capacitors and a regulator form the heart of the supply. Binding posts, a pilot light, fuse and on-off switch complete the design.

Ac from the mains is supplied to the transformer-primary winding through the fuse in one leg, and the on-off switch in the other. The secondary circuit feeds a full-wave rectifier circuit which is filtered by C1. This unregulated voltage is routed to the input terminal of the regulator IC which is bypassed directly at the case with a 2- $\mu$ F tantalum capacitor. The case of the IC is connected to ground. A 2- $\mu$ F tantalum capacitor is also used at the output terminal of the regulator to prevent unwanted oscillation of the error amplifier inside the IC. A pilot light attached to the regulated output indicates when the supply is in use.

The regulator has built-in thermal shut down and over-current protection. Short circuiting the output of the supply will cause no damage. A wide margin of conservative component rating was used in the design of this supply. It should be possible to run the supply for hours on end at its maximum rating.

### Construction

Rather than using an expensive cabinet, the power supply is housed on an aluminum chassis measuring 5 × 9-1/2 × 3

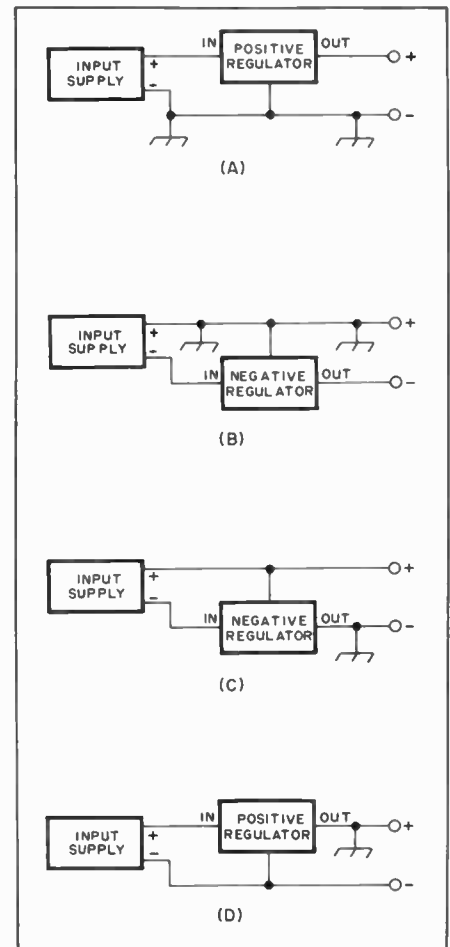


Fig. 29 — A and B illustrate the conventional manner in which three-terminal regulators are used. C and D show how one polarity regulator can be used to regulate the opposite polarity voltage.

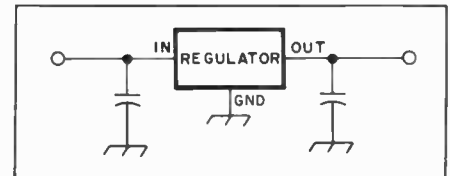


Fig. 30 — Three-terminal regulators require careful bypassing directly at the case. Here, both the input and output leads are bypassed.



Fig. 31 — Exterior view of the 12-volt, 3-ampere, no-frills power supply.



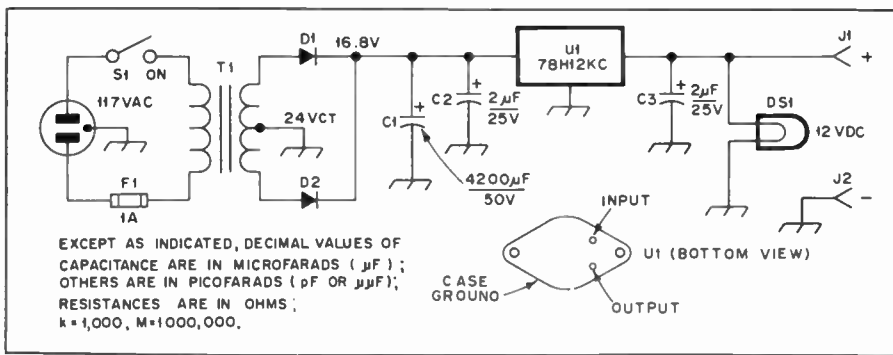


Fig. 32 — Schematic diagram of the 12-volt, 3-ampere power supply.

C1 — Electrolytic capacitor, 4200  $\mu\text{F}$ , 50 V, General Electric 86F166M or equiv.  
 C2, C3 — Tantalum capacitor, 2  $\mu\text{F}$ , 50 V.  
 D1, D2 — Silicon diode, 50 V, 6 A, HEP RO100 or equiv.  
 DS1 — Pilot light assembly, 12 V.  
 F1 — Fuse, 1 A.

J1, J2 — Binding post.  
 S1 — Spst toggle  
 T1 — Power transformer, primary 117 V, secondary 24 V ct, Stancor P-8663 or equiv.  
 U1 — Voltage regulator, Fairchild 78H12KC or equiv.

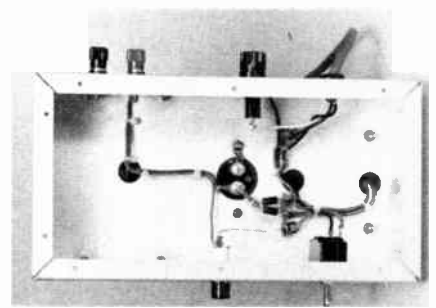


Fig. 33 — Interior view of the power supply.

inches (127 × 241 × 76 mm). Mounted atop the chassis is the power transformer, filter capacitor and regulator. The regulator is attached to a heat sink that measures 3 × 4 1/2 × inches (76 × 114 × 25 mm). Two tantalum capacitors, not visible in the pictures, are mounted at the IC terminals on the underside of the sink. Since good ground connections are required to prevent IC oscillations, remove the anodizing from the heat sink where it will contact the chassis.

The layout of the underside of the chassis can be seen in Fig. 33. Two binding posts (one red and one black) and the fuse holder are mounted on the rear apron. The on-off switch and pilot light

occupy a portion of the front panel. Dymo tape labels complete the front panel.

### A 0-25 Volt Adjustable Power Supply

The power supply shown in Fig. 34 can supply 1.5 amperes at voltages from near zero to +25. This range will cover most voltages needed for low power amateur work. Digital circuits require 5- and 12-volt supplies and most rf designs require 12 or 13 volts as a power source. On occasion there is need for voltages somewhat higher than this. The unit described here can supply voltages up to 30 volts. Voltage metering is provided to the 25-volt level since using the next larger



Fig. 34 — Front view of the 0-to 25-volt, 1.5-ampere power supply.

meter (50 volts) would give rather poor resolution of low-voltage readings.

### The Circuit

Power from the ac line is applied to the transformer primary through a single-pole, on-off switch and a fuse, F1. C1 and C2 are spike-eliminating capacitors used to protect the diodes in the transformer secondary circuit. These capacitors also

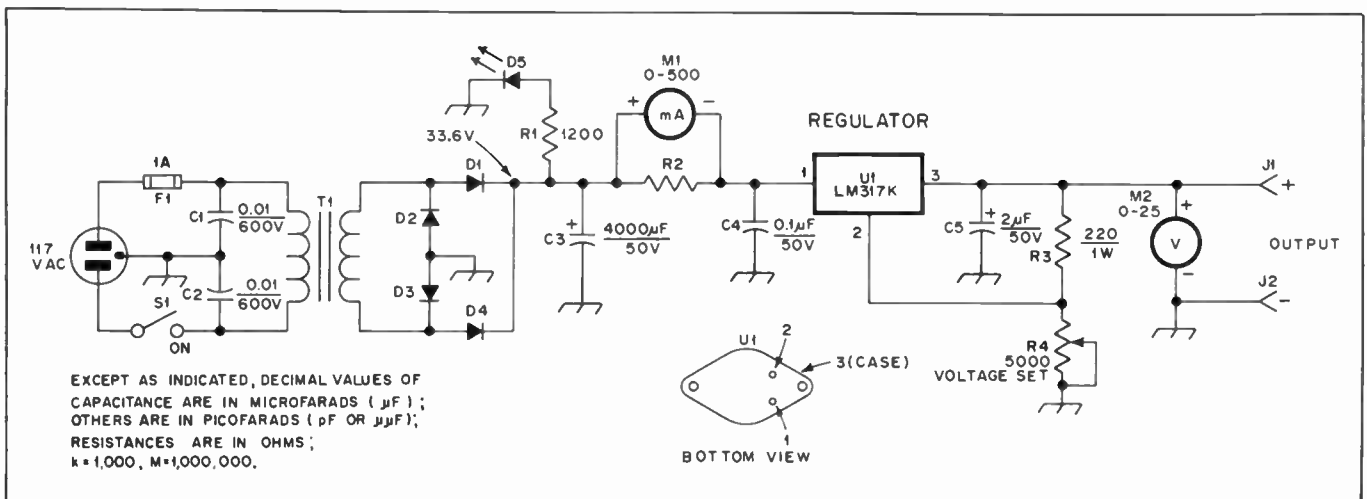


Fig. 35 — Schematic diagram of the 0-to 25-volt, 1.5-ampere power supply. Components not listed in the parts list are for text reference only. R1 is a 1/2-watt carbon type and R3 is a 1-watt carbon resistor. Capacitors are disk ceramic types unless noted otherwise.

C3 — Electrolytic capacitor, 4000  $\mu\text{F}$ , 50 V.  
 C5 — Tantalum capacitor, 2  $\mu\text{F}$ , 50 V.  
 D1 - D4, incl. — Silicon diode, 100 V, 6 ampere, HEP RO101 or equiv. Full-wave bridge assembly may be used.  
 D5 — LED, general purpose.  
 F1 — Fuse, 1 A.

J1, J2 — Binding post.  
 M1 — Panel meter, 0-500 mA. Calectro DI-916 or equiv.  
 M2 — Panel meter, 0-25 V. Calectro DI-923 or equiv.  
 R2 — Meter shunt. Wind 16- 1/2 inches (419 mm) no. 26 enam. wire on a large-value 2-watt

carbon resistor.  
 R4 — Potentiometer, 5000 ohm, 2 watt.  
 S1 — Toggle switch, spst.  
 T1 — Power transformer; primary 117 V, secondary 24 V, 3 A, Hammond HG2G or equiv.  
 U1 — Regulator, LM317K or equiv.

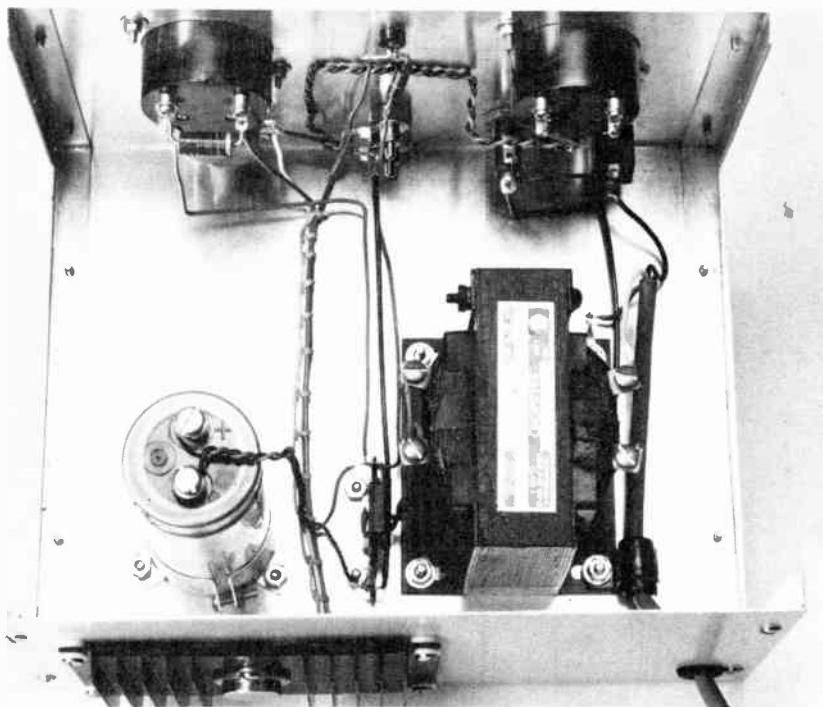


Fig. 36 — Interior view of the regulated power supply capable of delivering 1.5 amperes.

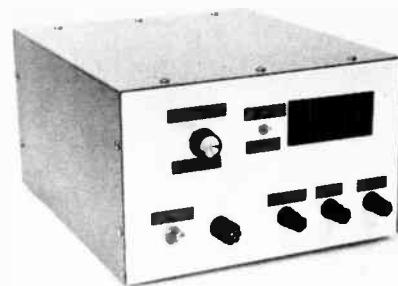


Fig. 37 — Front view of the deluxe 5- to 25-volt, 5-ampere power supply.

bypass the supply for rf energy entering or leaving the supply through the ac cord.

The voltage from the secondary of the transformer is applied to a full-wave bridge rectifier. C3, a large-value electrolytic, filters the dc. The heart of the supply is an LM317K adjustable-voltage regulator. Voltage adjustment is facilitated by the potentiometer in the voltage-divider circuit at the output of the chip. Bypass capacitors are used directly at the chip for stable operation. A 0-500 mA meter is used to measure current drawn from the supply. A meter shunt (R1) is used to multiply the meter reading by a factor of three. In other words, a reading of 100 mA on the meter face is in reality 300 mA a heading of 250 on the meter face is actually 750 mA and so on. The meter and shunt are located on the input side of the regulator so as not to compromise voltage regulation at high current levels. Idling current drawn by the '317 is very small and does not appreciably affect the meter reading.

Output voltage is measured with a 0-25 V meter placed across the output of the supply. An LED indicator is used to signal that the power supply is in operation.

#### Construction

The supply is housed in a homemade enclosure made from sheet aluminum. Overall dimensions of the cabinet are 8 × 10 × 5 inches (203 × 254 × 127 mm). Mounted to the front panel are the two meters, voltage-adjust potentiometer, binding posts, fuse holder, on-off switch and LED indicator. The general layout of the inside of the supply is shown in Fig. 36.

Point to point wiring is used throughout. The shunt resistor for M1 is located directly across the meter terminals.

Should the builder wish to limit the maximum voltage available at the output terminals of the supply, a resistor can be placed in parallel with the potentiometer. Additionally, the experimenter may wish to add a switchable voltage divider circuit for "programming" certain standard voltages into the supply. A rotary switch could be used to select, say, 5, 9, 12.6 and adjustable-voltage output.

#### A Deluxe 5-25-Volt 5-Ampere Supply

The power supply illustrated in Figs. 37 and 39 and schematically at Fig. 38 might be termed a rich man's power supply. The unit shown can supply voltages from 5 to 25 at currents up to 5 amperes. With thermal and short-circuit protection it is virtually destruction proof. A digital panel meter is used to monitor voltage and current, selectable by a front-panel switch. Although we termed this a "rich man's supply", it will cost far less to construct this unit as compared to a ready-made supply with the same features. Cost, using all new components, will be on the order of \$75. The most expensive single item in the supply is the digital panel meter, which sells in single lot quantities for around \$40 at present. As more companies start manufacturing these items the prices should drop significantly.

The digital readout, however, is not much more expensive than two high-quality meters. The prospective builder should consider this when choosing between the digital panel meters and two analog panel meters. Voltage measure-

ments are read directly off the panel meter in volts. Current is measured in amperes with a reading of 0.05 equal to 50 mA.

#### Circuit Details

The circuit diagram of the power supply is shown in Fig. 38. T1 is a 36-volt, center-tapped transformer rated at 6 amperes. D1 and D2 are used in a full-wave rectifier providing dc output to the filter capacitor, C3, a 33,000- $\mu$ F, 50-volt electrolytic of the computer-grade variety. The unregulated voltage is fed to U1, a Fairchild 78HGKC regulator, the heart of the supply. This chip is rated for 5-A continuous duty when used with an adequate heat sink. R1 and R2 form a voltage divider which sets the output voltage of the supply. R1 is a ten-turn potentiometer. U1 is bypassed with 2- $\mu$ F tantalum capacitors directly at the input and output pins.

Z1, as outlined earlier, is a digital panel meter. Connections to the meter are made through a special edge connector supplied with the readout. U2 is used to supply a regulated 5 volts for powering the digital panel meter. The input and ground leads of this regulator are attached to the input (non-regulated) side of U1.

R4, R5 and R6 form a divider circuit to supply the digital meter with an output voltage reading. R5 is made adjustable so that the meter can be calibrated. R3 is a current-sensing resistor which is placed in the negative lead of the supply. This resistor is used on the input side of the regulator (U1) so as not to affect the voltage regulation of the power supply at high load currents. Any voltage dropped across the resistor will be made up by the regulator, so the output voltage will remain unchanged. Notice that U2 is placed to the left or at the input side of the regulator. This is so the current drawn by the readout will not affect current readings taken at the load. Sections A and B of S2 are used to switch the meter between the voltage and current sensors. S3C is used to switch the decimal point in the digital panel meter to read correctly for both voltage and current.

As shown in the schematic, a single-point ground is used for the supply. Used in many commercial supplies, this tech-

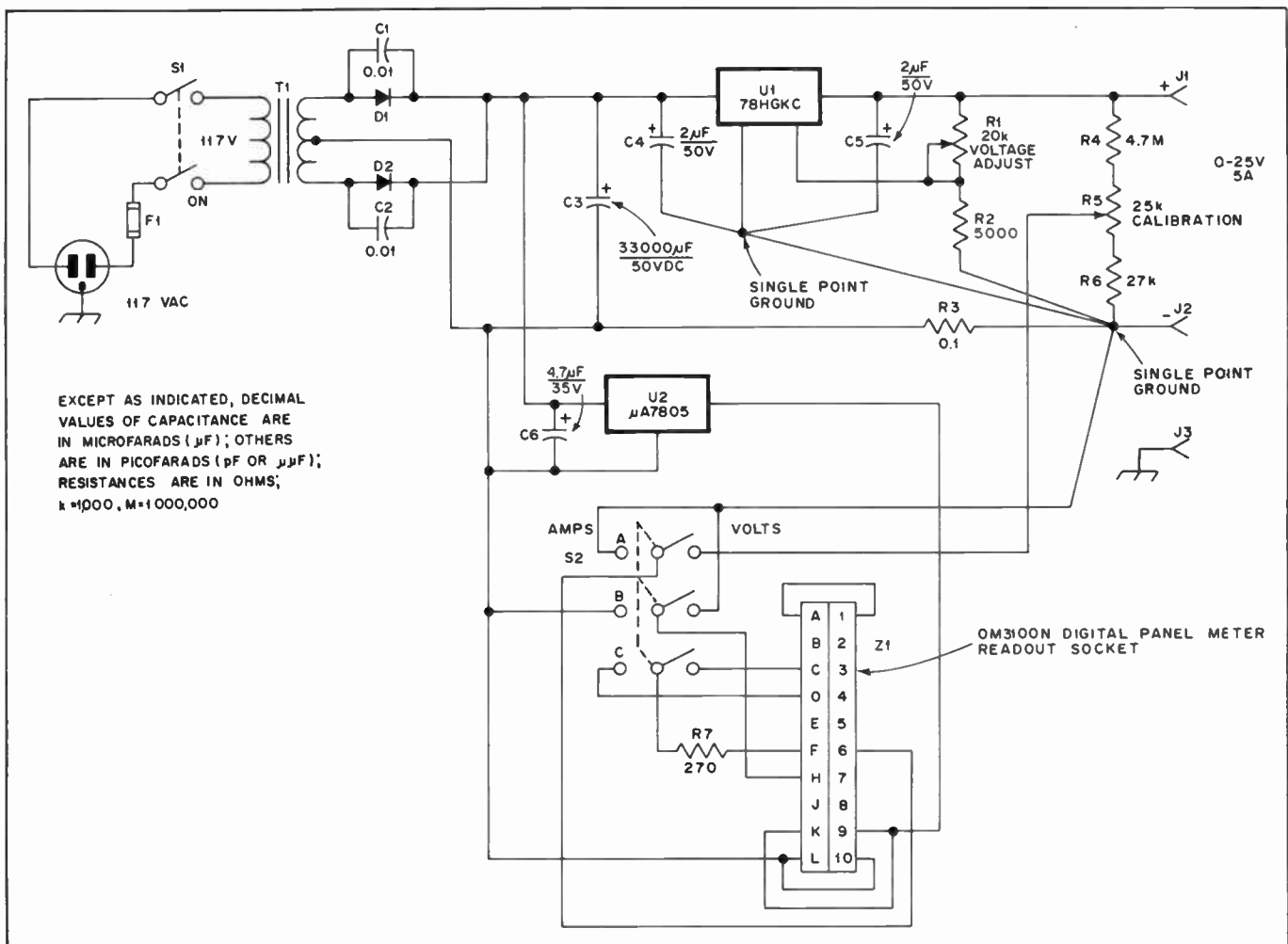


Fig. 38 — Schematic diagram of the deluxe power supply. All resistors are half-watt carbon types unless noted otherwise. Capacitors are disk ceramic unless noted otherwise. Numbered components not appearing in the parts list are for text reference only.

C3 — Electrolytic capacitor, 33,000  $\mu\text{F}$ , 35 V. Mallory CG333U035X4C or equiv.  
 C4, C5 — Tantalum capacitor, 2  $\mu\text{F}$ , 50 V.  
 C6 — Tantalum capacitor, 4.7  $\mu\text{F}$ , 35 V.  
 D1, D2 — Silicon rectifier, 100 V, 12 A. HEP RO131 or equiv.  
 F1 — Fuse, 2 A.

J1-J3, incl. — Binding post.  
 R1 — Potentiometer, 20-k $\Omega$ , linear, 10 turn. Clarostat type 731A or equiv.  
 R5 — Potentiometer, 25-k $\Omega$ , circuit board mount.  
 R3 — Resistor, 0.1 $\Omega$ , 10 W. Dale R-10 or equiv.  
 S1 — Toggle switch, spdt.  
 S2 — Toggle switch, 3pdt.

T1 — Power transformer; primary 117 V, secondary 36 V ct.; 6 A. Stancor P-8674 or equiv.  
 U1 — Regulator, Fairchild 78HGKC or equiv.  
 U2 — Regulator,  $\mu$  A7805 or equiv.  
 Z1 — Digital panel meter. Datel DM3100N or equiv.

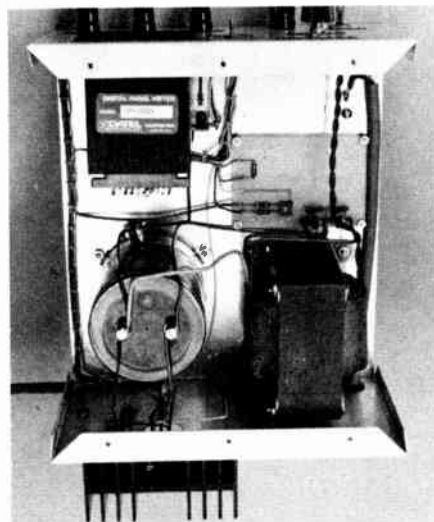


Fig. 39 — Interior view of the deluxe power supply.

nique provides better voltage regulation and stabilization than the "ground it anywhere" attitude. In this supply, the single-ground point is at the front panel binding post labelled MINUS. All leads that are to be connected to ground should go only to that point.

#### Construction

The deluxe power supply is housed in a homemade enclosure that measures 9 × 11 × 5 1/4 inches (229 × 279 × 133 mm). U1 is mounted to a large heat sink (3 × 5 × 2 inches; 76 × 127 × 51 mm) which is attached to the rear apron of the supply. The front panel sports the digital-panel meter, power switch, binding posts, fuse holder, voltage-adjust potentiometer and meter-selector switch. Although a circuit board is shown in the photograph as supporting R4, R5, R6, R7, D1, D2, C1 and C2 these items could just as well be mounted on terminal strips. For this

reason a board pattern is not supplied.

The front and rear panels are spray painted white and the cover is blue. Dymo labels are used on the front panel to identify each of the controls. Cable lacing



Fig. 40 — Front view of the heavy-duty, 3400-volt power supply.

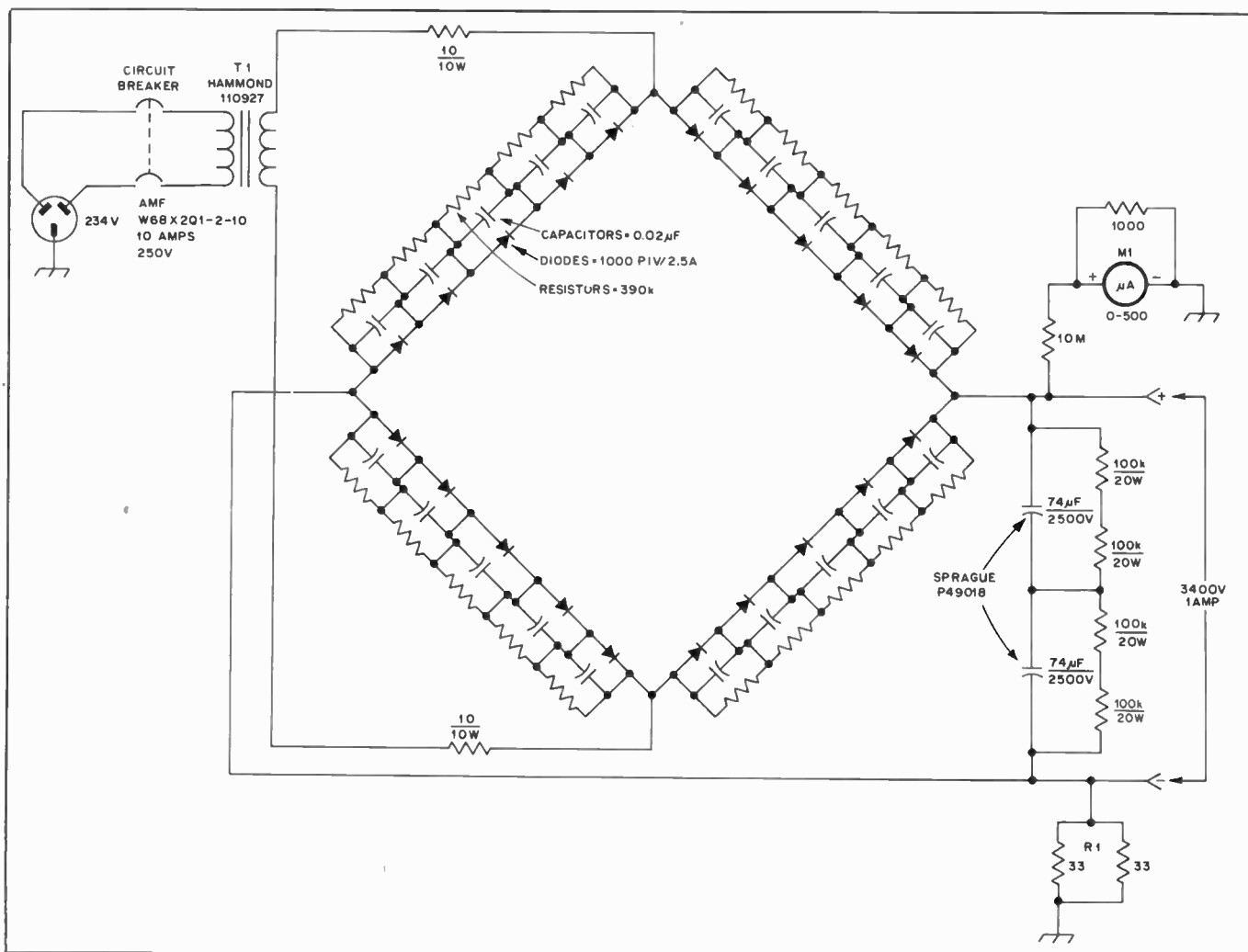


Fig. 41 — Schematic diagram of the high-voltage power supply.

of the various leads adds to the clean appearance of the supply.

### A "Sanitary" High-Voltage Supply

Power supplies aren't usually noted for adding decor to the shack. Most hams would rather hide them so that nonham visitors won't ask, "What's that ugly looking thing?" However, an attempt was made to improve the appearance of this model along with the function of providing high voltage for general amplifier purposes. Not all the additions are frivolous. For instance, the use of "rug runners" instead of the usual sharp corners on the bottom of the unit prevents gouging an easily damaged surface such as a bench or floor.

The diode bridge rectifier is mounted on a separate pc board that can be removed easily. Accidental contact is prevented by a Plexiglas sheet which also

permits viewing of the circuit board while it is still in the power supply. Although a sheet-metal cutter and bender were used to fabricate the sides, a "cut-and-file" method could result in a similar job if the builder was willing to spend the time. Either that or angle brackets (such as those on the front of the unit) could be used inside of the top and bottom covers in order to form an overlap surface for the covers.

### Circuit Details

The power supply employs a full-wave bridge rectifier and is capable of 1-A output at 3400 V dc. Primary-circuit and surge considerations are simplified by the use of 234 V ac instead of 117 V. While the addition of a 234-V line might seem like an unjustified inconvenience, experience has proven this approach to be the most acceptable method. However, additional

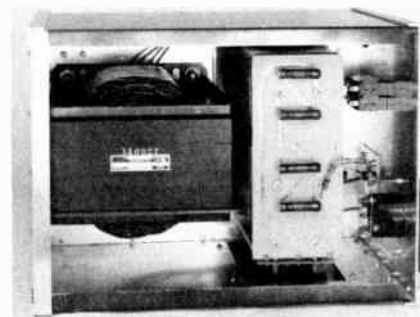


Fig. 42 — Interior view of the heavy-duty power supply. The bleeder/equalizing resistors are mounted to the circuit board which is in turn mounted directly to the capacitor terminals.

surge protection is afforded by the use of the 10-ohm, 10-watt resistors in the secondary of T1.



# HF Transmitting

Even though some modern transmitters and transceivers contain only solid-state devices, it is still practical to use a hybrid circuit that contains a mixture of tubes and active semiconductor stages. Typically, the unit has transistors, diodes and ICs up to the driver stage of the transmitter. At that point one will find a tube driver which is used to supply rf power to a tube type of amplifier. The latter might consist of a pair of 6146Bs or two sweep tubes.

The principal advantage of tube amplifiers is that they are somewhat less subject to damage from excessive drive levels and mismatched loads. However, a properly designed solid-state driver and PA section should be immune to output mismatch damage, provided an SWR-protection circuit has been included in the transmitter. A solid-state amplifier is slightly more difficult to design and have work correctly than is a tube amplifier of equivalent power. This is because purity of emissions is harder to achieve when transistor power stages are employed. Transistors generate considerably more harmonic energy than tubes do, and the former are prone to self-oscillation at lf, vlf and audio frequencies unless some careful design work is done. This is not generally true of tube amplifiers.

If one is to ignore the foregoing problems and concentrate mainly on cost and convenience, transistors may have the edge over tubes. A 13.6-volt design can be operated directly from an automotive or solar-electric supply, whereas a tube amplifier requires a high-voltage power supply for mobile, portable and fixed-station use. When an ac power source is required, the cost of a high-voltage, medium-current supply for tubes versus a low-voltage, high-current power source for transistors is similar, provided new components are used in both. At power-output levels in excess of approximately 150 watts the transistor-amplifier power

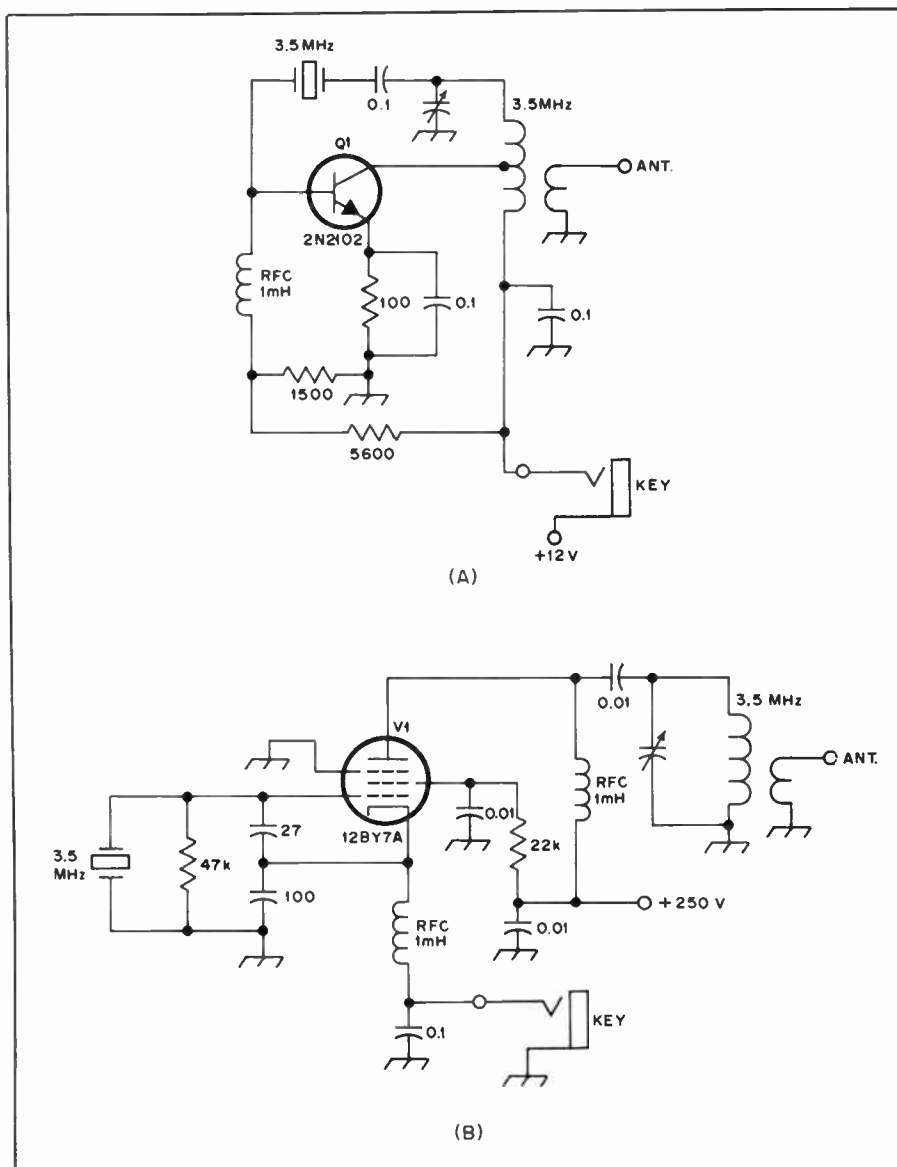


Fig. 1 — A transistor oscillator is shown at A. The example at B illustrates a tube type of crystal oscillator.

supply becomes rather expensive because of complex regulator-circuit requirements. For this reason it is the choice of most amateurs to utilize vacuum tubes in high-power hf and vhf amplifiers. The number of power transistors required (plus combiners) to generate a 1-kW signal may run considerably higher in cost than a tube or tubes for an amplifier of equivalent power. The price of large heat sinks versus a cooling fan may place the solid-state amplifier in a prohibitive class also.

The decision to buy or build a transmitter is founded on some basic considerations: Cost compared to features; professional equipment appearance contrasted to that of homemade apparatus; the knowledge and satisfaction gained from building equipment, as weighed against buying store-bought gear and simply becoming an operator. The judgment must fit the amateur's objectives and affluence. Home-built transmitters are usually easier to service than commercial ones because the builder knows the circuit layout and how each stage functions. Furthermore, the cost of maintenance is markedly lower for homemade equipment than for most factory-built gear. But the greatest significance to home-built circuits is the *knowledge* gained from constructing a project and the pride that goes with using it on the air!

### Frequency Generation

The most basic type of transmitter is one which contains a single stage, is crystal controlled, and is designed for cw operation. A circuit example is given in Fig. 1. This kind of transmitter is not especially suitable for use on the air because it is somewhat inefficient and is prone to generating a chirpy cw signal unless loaded rather lightly. But, the same circuit is entirely acceptable when followed by an isolating stage (buffer/amplifier) as shown in Fig. 2. The second stage not only builds up the power level, but it gives the oscillator a relatively constant load to look into. The latter helps to prevent oscillator pulling and attendant chirping of the cw note.

Fig. 3 illustrates the basic types of transmitters for cw and RTTY work. The drawing at A represents the general circuit given in Fig. 2. Illustration B is an expansion of that circuit and includes a frequency multiplier. A heterodyne type of generator, which is currently popular for multiband transmitters and transceivers, is shown as the exciter section of a transmitter in drawing C. A frequency synthesizer is shown as the rf generator at D.

For operation on a-m, any of the lineups given in Fig. 3 are suitable, provided a modulator is added. It is used to modulate the operating voltage to the PA stage, or in some designs the operating voltage to the PA and the stage immediately before it.

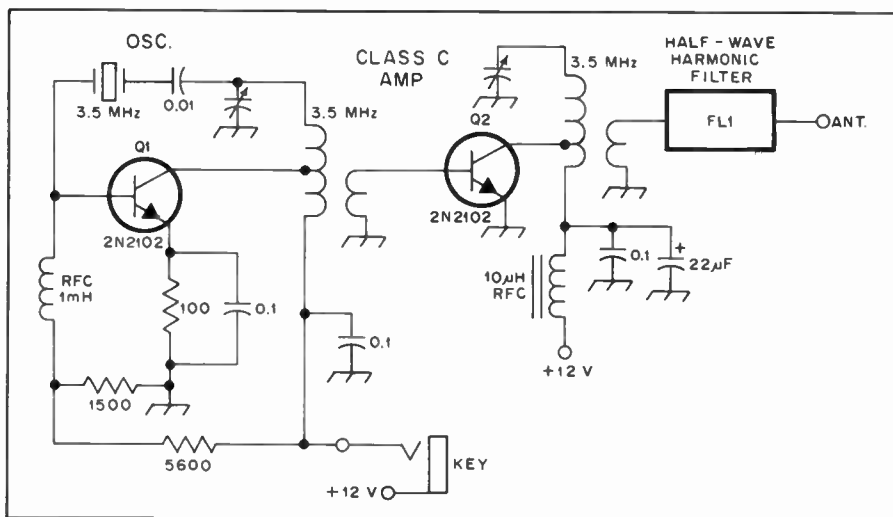


Fig. 2 — Circuit example of a simple, solid-state cw transmitter.

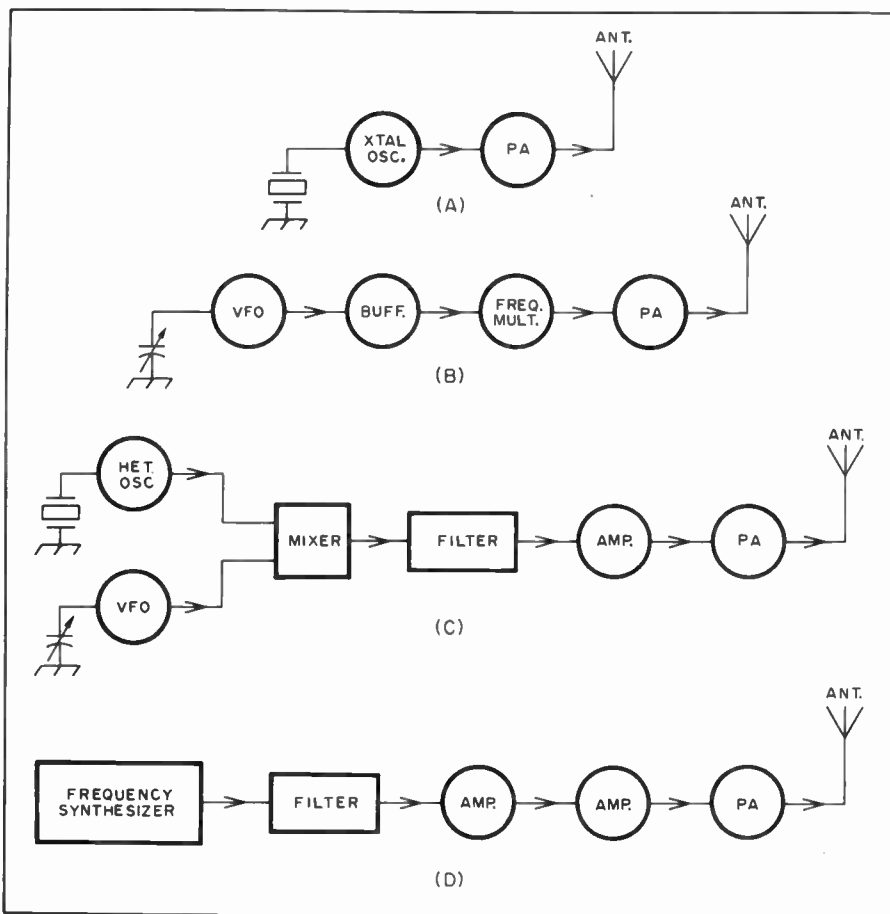


Fig. 3 — Block diagrams of various transmitters which use specific frequency-generation methods.

The block diagram of Fig. 4 outlines the functional stages of a ssb transmitter. Z1 can be a simple VFO, a heterodyne generator (Fig. 3C) or a frequency synthesizer. The essential difference between this type of transmitter and one that would be used for cw/RTTY is that the rf amplifiers must operate in the Class A, AB or B mode (linear) rather than the Class C mode which is suitable for cw

work. However, linear amplifiers are entirely satisfactory for any transmission mode at a sacrifice in efficiency. Once the ssb signal is generated it can not be passed through a frequency multiplier. All post-filter stages must operate straight through. Class C amplifiers are generally used in fm transmitters as well as in cw and RTTY transmitters. Fm operators who are heard to say, "I'm running my transceiver into a



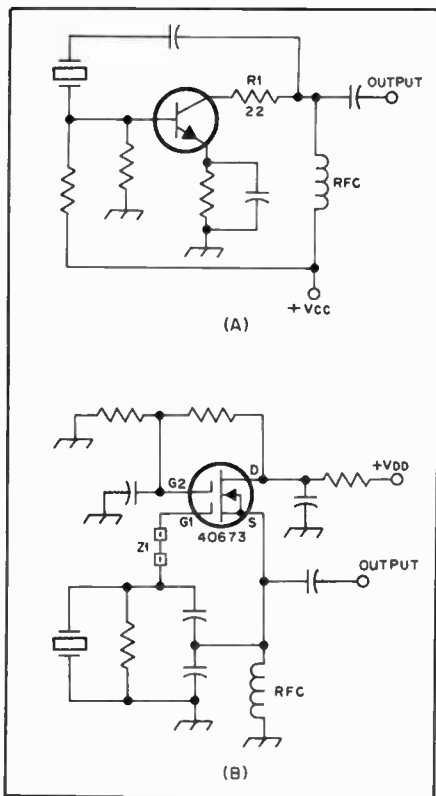


Fig. 7 — Two methods for suppressing vhf and uhf parasitic oscillations. R1 at A damps the parasitics and Z1 at B (ferrite beads) serves that purpose.

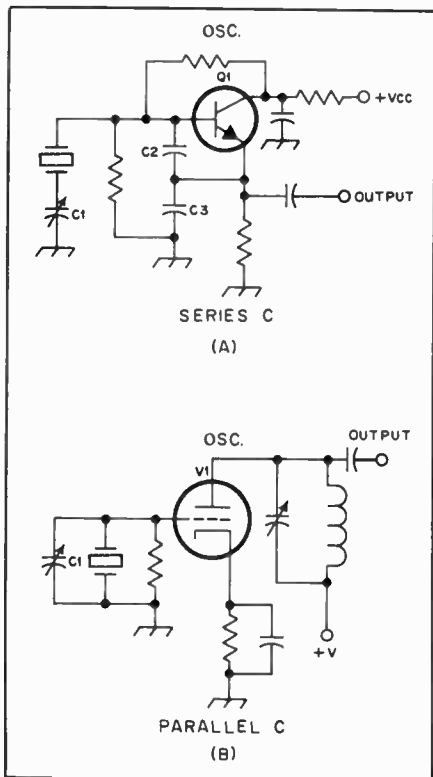


Fig. 8 — The crystal-oscillator operating frequency can be shifted slightly by means of trimmer capacitors as shown at A and B. A series hookup (A) is used with transistors to help compensate for the relatively high input capacitance of the transistor.

A Colpitts style of tube oscillator is illustrated in Fig. 6 at B. The feedback is between the grid and cathode by means of a capacitive divider (C1 and C2). The plate tank can be tuned to the crystal frequency or harmonics thereof. In the interest of good oscillator stability it is suggested that the supply voltage to the circuits of Figs. 5 and 6 be regulated. This is especially significant in the case of harmonic or overtone oscillators where small amounts of drift are multiplied by the chosen harmonic factor.

The usual cause of erratic oscillation, or no oscillation at all, is excessive loading on the oscillator output (succeeding stage of circuit), insufficient feedback, or a sluggish crystal. Concerning the latter, a crystal which is not ground to a uniform thickness and feathered carefully around the edges may be difficult to make oscillate. Attempts by inexperienced amateurs to grind their own crystals may lead to this condition.

Some crystal oscillators develop unwanted vhf self-oscillations (parasitics) even though the circuits may be functioning normally otherwise. The result will be a vhf waveform superimposed on the desired output waveform when the rf voltage is viewed by means of an oscilloscope. Parasitics can cause TVI and specific problems elsewhere in the circuit with which the oscillator is used. Two simple methods for preventing vhf parasitics are shown in Fig. 7. The technique at A calls for the insertion of a low-value resistance (R1) in the collector lead as close to the transistor body as possible. Typical resistance values are 10 to 27 ohms. The damping action of the resistor inhibits vhf oscillation. An alternative to the use of resistance for swamping vhf oscillation is illustrated at B in Fig. 7. One or two high- $\mu$  miniature ferrite beads ( $\mu_i = 950$ ) are placed near the transistor body in the lead to gate 1. The beads can be used in the drain lead when a tuned circuit or rf choke are used in that part of the circuit. However, when the drain is at ac ground, as shown at B, it does not constitute part of the feedback circuit. Ferrite beads can be used in the base or collector lead of the circuit of Fig. 7A rather than employing R1. Similarly, R1 can be used at gate 1 of the oscillator.

It is necessary in some applications of crystal oscillators to ensure spot accuracy of the operating frequency. Various reactances are present in most oscillator circuits, causing the operating frequency to differ somewhat from that for which the crystal was manufactured. Addition of a trimmer capacitor will permit "rubbering" the crystal to a specified frequency within its range. This procedure is sometimes referred to as "netting" a crystal.

Fig. 8 shows two circuits in which a trimmer capacitor might be used to compensate for differences in the operating frequency of the oscillator. At A the

series capacitor (C1) is connected between the low side of the crystal and ground. The series hookup is used to help offset the high input capacitance of the oscillator. The input capacitance consists of the series value of feedback capacitors C2 and C3 plus the input capacitance ( $C_{in}$ ) of Q1. Conversely, the input capacitance of the circuit at B in Fig. 8 is quite low because a triode tube is employed. In this kind of circuit the trimmer capacitor is used in a parallel manner as shown. The choice between series and parallel trimming will depend on the active device used and the amount of input capacitance present. This rule applies to tube oscillators as well as those which use transistors.

### Crystal Switching

Although several crystals for a single oscillator can be selected by mechanical means, a switch must be contained in the rf path. This can impose severe restrictions on the layout of a piece of equipment. Furthermore, mechanical switches normally require that they be operated from the front panel of the transmitter or receiver. That type of format complicates the remote operation of such a unit. Also, the switch leads can introduce unwanted reactances in the crystal circuit. A better technique is illustrated in Fig. 9, where D1 and D2 — high-speed silicon switching diodes — are used to select one of two or more crystals from some remote point. As operating voltage is applied to one of the diodes by means of S1, it is forward biased into "hard" conduction, thereby completing the circuit between the crystal trimmer and ground. Some schemes actually call for reverse-biasing the unused diode or diodes when they are not activated. This ensures almost complete cutoff, which may not be easy to achieve in the circuit shown because of the existing rf voltage on the anodes of D1 and D2.

### Variable-Frequency Oscillators

The theory and general application of variable-frequency oscillators is treated in chapter 8. The circuit principles are the same regardless of the VFO application.

Some additional considerations pertain to the use of VFOs in transmitters as compared to a VFO contained in a receiver. Generally, heating of the interior of a transmitter cabinet is greater than in a receiver. This is because considerably more power is being dissipated in the former. Therefore, greater care must be given to oscillator long-term stability. Temperature-compensating capacitors are often needed in the frequency-determining portion of the oscillator to level off the long-term stability factor. Some oscillators are designed for use with a temperature-control oven for the purpose of maintaining a relatively constant ambient temperature in the oscillator compartment — even while the equipment



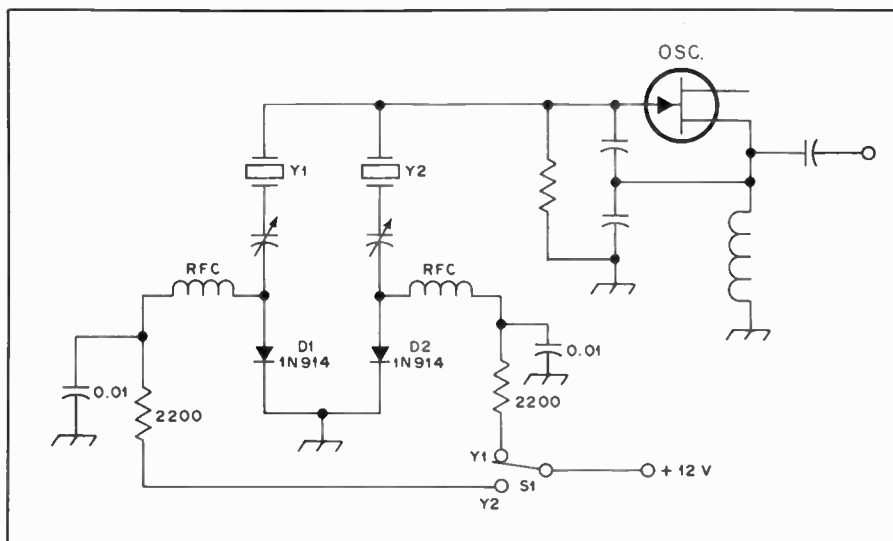


Fig. 9 — A method for selecting one of two (or several) crystals by means of diode switching. D1 and D2 are the switches.

is otherwise turned off.

Another design matter related to a transmitter-contained VFO is rf shielding of the oscillator and the attendant low-level buffer/isolation stages that follow it. Fairly high levels of stray rf can be present in a transmitter and some of that energy may migrate to the oscillator section by means of stray radiation or conduction along wiring leads or circuit-board elements. Thus, it is important to provide as much physical and electrical isolation as possible. The VFO should be housed in a rigid metal box. All dc leads entering the enclosure require rf-decoupling networks that are effective at all frequencies involved in the transmitter design. The VFO box needs to be interfaced securely with the metal chassis on which it rests to ensure good electrical contact. Excessive stray rf entering the VFO circuitry can cause severe instability and erratic oscillator operation.

#### Fundamental Stability Considerations

Apart from the recommendations given in the foregoing text for VFO stability, there are some specific measures which must be taken when designing an oscillator of this type. The form upon which the VFO coil is wound is of special significance with regard to stability. Ideally, the use of magnetic core material should be avoided. Therefore, powdered iron, brass, copper and ferrite slugs, or toroid cores for that matter, are not recommended when high stability is required. The reason is that the properties of such core materials are affected by changes in temperature and can cause a dramatic shift in the value of inductance which might not occur if an air-core coil was employed. Furthermore, some styles of slug-tuned inductors are subject to mechanical instability in the presence of vibration. This can cause severe frequency

jumping and a frequent need for recalibration of the VFO readout versus operating frequency.

Regardless of the format selected for the VFO coil, the finished product should be coated with two or three applications of polystyrene cement (Q dope) or similar low-loss dopant. This will keep the coil turns secured in a permanent position — an aid to mechanical stability.

The VFO coil should be mounted well away from nearby conducting objects (cabinet walls, shield cans, and so on) to prevent frequency shifts which are likely to occur if the chassis or cabinet are stressed during routine handling or mobile operation. Movement of the chassis, cabinet walls and other nearby conductive objects can (if the coil is close by) change the coil inductance. Furthermore, the proximity effects of the conductive objects present an undefined value of capacitance between the coil and these objects. Changes in spacing will alter that capacitance, causing frequency shifts of an abrupt nature.

It follows that all forms of mechanical stability are of paramount importance if the VFO is to be of "solid" design. Thus, the trimmer or padder capacitors that are used in the circuit should be capable of remaining at their preset values despite temperature changes and vibration. For this reason it is not wise to utilize ceramic or mica trimmers. Air-dielectric variable capacitors of the pc-board-mount sub-miniature type are recommended.

The main tuning element (capacitor or permeability tuner) needs to have substantial rigidity: It should be mounted in place in a secure manner. Variable capacitors used as main-tuning elements should be of the double-bearing variety. They should rotate easily (minimum torque) in order to minimize mechanical stress of the VFO assembly when they are

being adjusted from the front panel of the equipment. Variable capacitors with plated brass plates are preferred over those which have aluminum plates. The aluminum is more subject to physical changes in the presence of temperature variations than is the case with brass. The VFO tuning-capacitor rotor must be grounded at both ends as a preventive measure against instability. Some designers have found that a 1/8- to 1/4-inch (3.2- to 6.4-mm) thick piece of aluminum or steel plate serves as an excellent base for the VFO assembly. It greatly reduces instability which can be caused by stress on the main chassis of the equipment. The VFO module can be installed on shock mounts to enhance stability during mobile operation.

#### Concerning Electrical Stability

Apart from the mechanical considerations just discussed, the relative quality of the components used in a VFO circuit is of great importance. Fig. 10 contains three illustrations of basic solid-state tunable oscillators which are suggested for amateur applications. The numbered components have a direct bearing on the short- and long-term stability of the VFO. That is, the type of component used at each specified circuit point must be selected with stability foremost in mind. The fixed-value capacitors, except for the drain bypass, should be temperature-stable types. Polystyrene capacitors are recommended for frequencies up to approximately 10 MHz. A second choice is the silver-mica capacitor (dipped or plain versions). Silver micas tend to have some unusual drift characteristics when subjected to changes in ambient temperature. Some increase in value while others decrease. Still others are relatively stable. It is often necessary to experiment with several units of a given capacitance value in an effort to select a group of capacitors that are suitably temperature-stable. The same is not true of polystyrene capacitors. Ordinary disk-ceramic capacitors are unsuitable for use in stable VFOs. Those with specified temperature characteristics (NPO and similar) are useful, however, in compensating for drift.

The circuit of Fig. 10A is capable of very stable operation if polystyrene capacitors are used at C3 through C8, inclusive. A test model for 1.8 to 2.0 MHz exhibited only 1 hertz of drift from a cold start to a period some two hours later. Ambient temperature was 25°C. Q1 can be any high- $g_m$  JFET for use at vhf or uhf. Capacitors C1 through C4 are used in parallel as a means to distribute the rf current among them. A single fixed-value capacitor in that part of the circuit would tend to change value versus time because of the rf heating within it. Therefore, a distinct advantage exists when several capacitors can be used in parallel at such points in a VFO circuit. The same concept

is generally true of C5, C6 and C7. In the interest of stability, C5 should be the smallest value that will permit reliable oscillation. Feedback capacitors C6 and C7 are typically the same value and have an  $X_c$  of roughly 60. Therefore, a suitable value for a 1.9-MHz VFO would be 1500 pF.

C8 of Fig. 10A should be the smallest capacitance value practical with respect to ample oscillator drive to the succeeding stage — generally a buffer or amplifier. The smaller the value of C8, the less the chance for oscillator pulling during load changes. D1 is a gate-clamping diode for controlling the bias of the FET. The function of this stabilizing diode is treated in chapter four. Basically, it limits the positive swing of the sine wave. This action restricts the change in Q1 junction capacitance to minimize harmonic generation and changes in the amount of C associated with L1.

The reactance of RFC can be on the order of 10-k $\Omega$ . The drain bypass, C9, should have a maximum  $X_c$  of 10 ohms to ensure effective bypassing at the operating frequency. Ideally, an  $X_c$  of 1 ohm would be used (0.1  $\mu$ F at 1.5 MHz). D2 is used to provide 9.1 volts, regulated, at the drain of Q1. Lower operating voltages aid stability through reduced rf-current heating, but at the expense of reduced oscillator output.

An ECO (electron-coupled oscillator) is shown in Fig. 10B. This circuit offers good stability also, and is one of the better circuits to use when the tank is parallel tuned. The tap on L1 is usually between 10 and 25 percent of the total coil turns, tapped above the grounded end. This ensures adequate feedback for reliable oscillation. The higher the FET  $g_m$  the lower the tap on the coil. Only that amount of feedback which is necessary to provide oscillation should be used: Excessive feedback will cause instability and prohibitive rf heating of the components. Most of the rules for the circuit of Fig. 10A apply to the oscillator in Fig. 10B.

Parallel tuning of the kind used in Fig. 10B and C are suitable for use below, say, 6 MHz, although the circuit at B can be used successfully into the vhf region. However, the Colpitts oscillators of A and C in Fig. 10 have large amounts of shunt capacitance caused by C6 and C7 of A, and C5 and C6 of C. The smaller the coupling capacitor between L1 and the gate, the less pronounced this effect is. The net result is a relatively small value of inductance at L1, especially with respect to Fig. 10C, which lowers the tank impedance and may prevent oscillation (high C-to-L ratio). The series-tuned circuit of Fig. 10A solves the shunt-C problem nicely by requiring considerably greater inductance at L1 than would be acceptable in the circuit of Fig. 10C. The circuit at A resembles the popular "series-tuned Clapp" of the early 1950s.

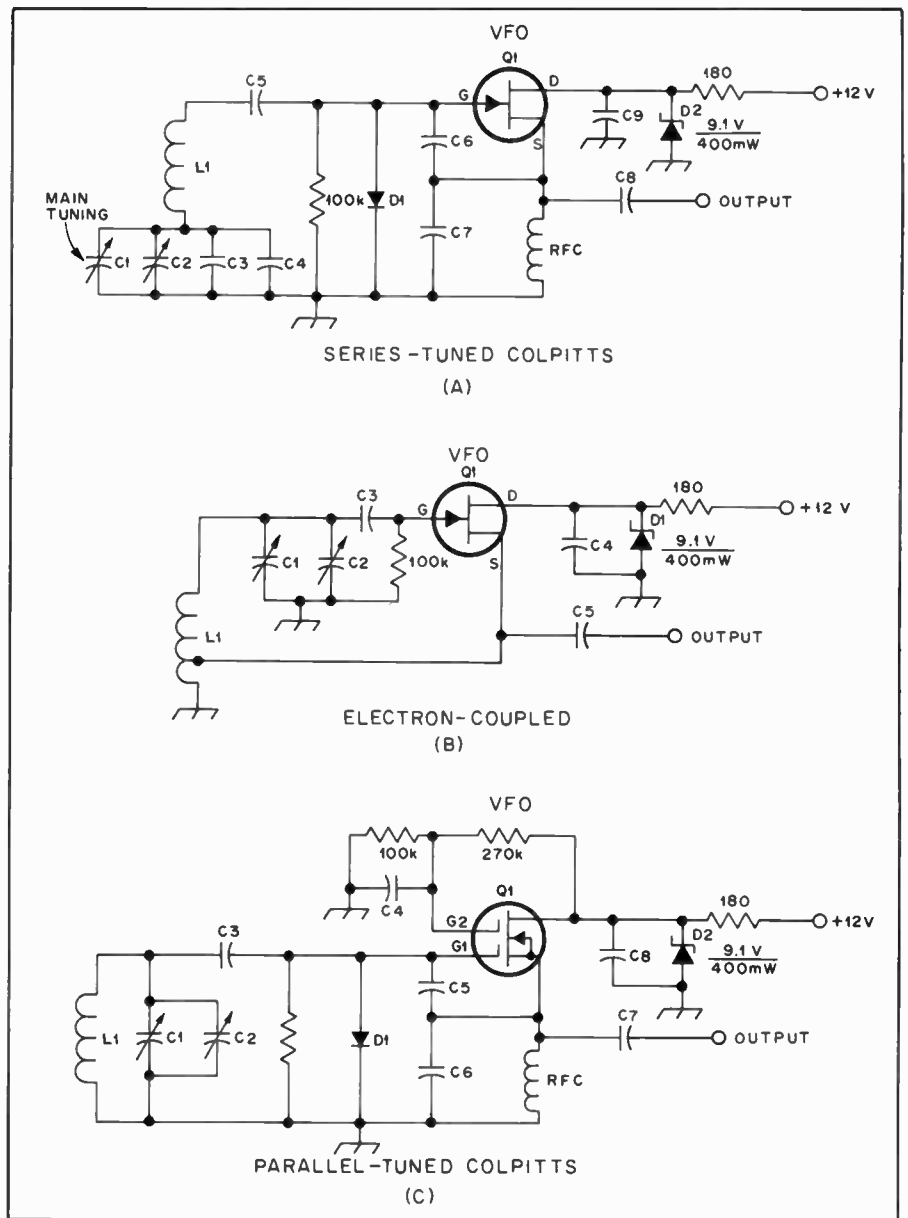


Fig. 10 — Three common types of VFOs for use in receivers and transmitters.

A suitable transistor for Q1 of Fig. 10C is an RCA 40673. The Texas Instrument 3N211 is also ideal, as it has an extremely high  $g_m$  — approximately 30,000. Dual-gate MOSFETs are suitable for the circuits of Fig. 10A and B if biased as shown at C. Also, they can be used as single-gate FETs by simply connecting gates 1 and 2 together. No external bias is required if this is done. Gate 2 of Q1 (Fig. 10C) should be bypassed with a low-reactance capacitor (C4), as is the rule for the drain bypassing of all three examples given in Fig. 10.

Bipolar transistors are satisfactory for use in the three VFOs just discussed. The principal disadvantage attendant to the use of bipolars in these circuits is the low base impedance and higher device input capacitance. Most FETs exhibit an input C of approximately 5 pF, but many bi-

polar transistors have a substantially higher capacitance, which tends to complicate a VFO design for the higher operating frequencies. The uhf small-signal transistors, such as the 2N5179, are best suited to the circuits under discussion.

#### Load Isolation for VFOs

Load changes after the oscillator have a pronounced effect on the operating frequency. Therefore, it is imperative to provide some form of buffering (isolating stage or stages) between the oscillator and the circuit to which it will be interfaced. The net effect of load changes, however minor, is a change in reactance which causes phase shifts. The latter affects the operating frequency to a considerable degree. Therefore, the more isolating stages which follow the oscillator (up to a

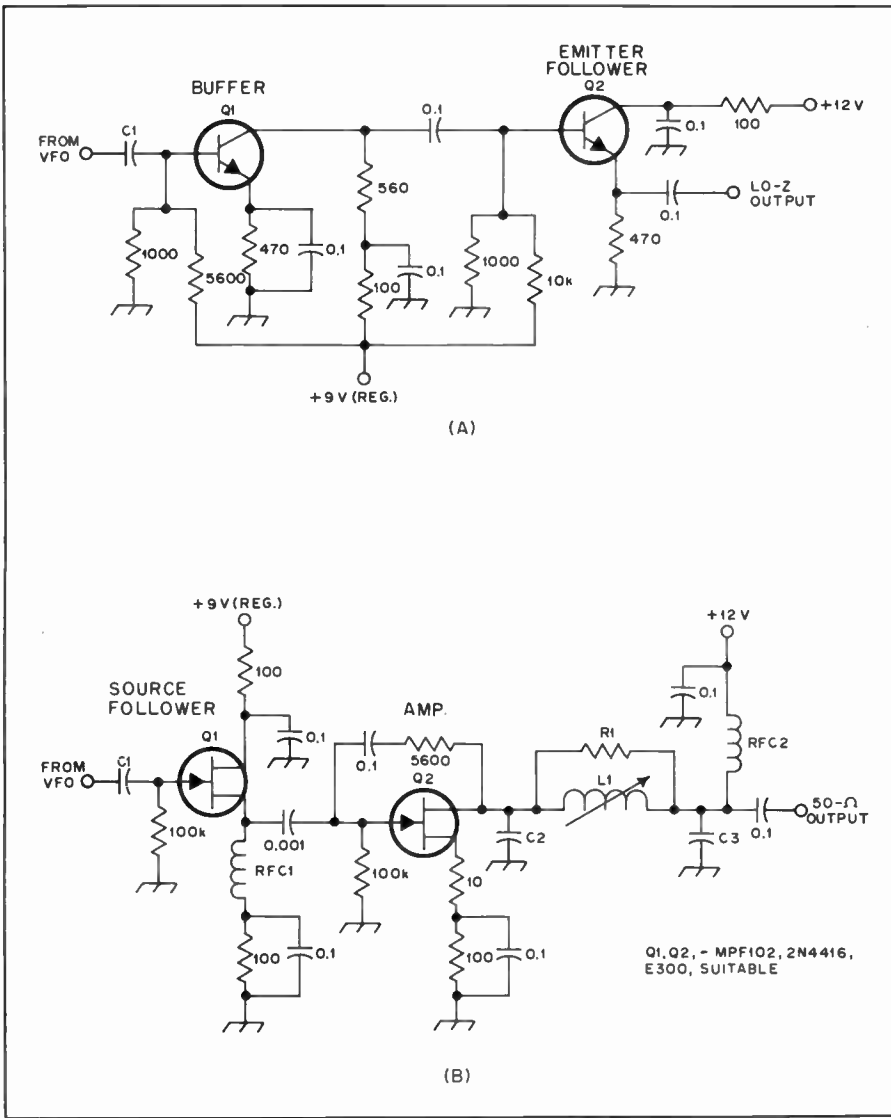


Fig. 11 — VFO buffer and buffer/amplifier sections which provide isolation between the oscillator and the VFO-chain load. The circuit at B is recommended for most applications.

practical number, of course), the less likelihood of load shifts being reflected back to the oscillator.

Buffer stages can perform double duty by affording a measure of rf amplification, as needed. But, care must be taken to avoid introducing narrow-band networks in the buffer/amplifier chain if considerable frequency range is planned, e.g., 5.0 to 5.5 MHz. If suitable broadband characteristics are not inherent in the design, the oscillator-chain output will not be constant across the desired tuning range. This could seriously affect the conversion gain and dynamic range of a receiver mixer, or lower the output of a transmitter in some parts of a given band.

Fig. 11A illustrates a typical RC coupled VFO buffer with broadband response. C1 is selected for minimum coupling to the oscillator, consistent with adequate drive to Q1. Q1 and Q2 should have high  $f_T$  and medium beta to ensure a slight rf-voltage gain. Devices such as the 2N2222A and 2N5179 are suggested.

Q2 of Fig. 11A operates as an emitter-follower. The rf-voltage output will be approximately 0.9 of that which is supplied to the base. In a typical VFO chain, using an oscillator such as the one in Fig. 10A, this buffer strip will deliver approximately 1 volt pk-pk across the 470-ohm emitter resistor of Q2.

A somewhat better circuit is offered in Fig. 11B. Q1 is a JFET which has a high input impedance (1-M $\Omega$  or greater) by virtue of the FET-device characteristic. This minimizes loading of the oscillator. RFC1 is chosen to resonate broadly with the stray circuit capacitance (roughly 10 pF) at the midrange frequency of the LO chain. Although this does not introduce significant selectivity, it does provide a rising characteristic in the rf-voltage level at the source of Q1.

Q2 functions as a fed-back amplifier with shunt feedback and source degeneration. The feedback stabilizes the amplifier and makes it broadband. The drain tank is designed as a pi network with a loaded

Q of 3. The transformation ratio is on the order of 20:1 (1000-ohm drain to 50-ohm load). R1 is placed across L1 to further broaden the network response. The 50-ohm output level is recommended in the interest of immunity to load changes: The higher the output impedance of a buffer chain the greater the chance for oscillator pulling with load changes. Pk-pk output across C3 should be on the order of 3 volts when using the oscillator of Fig. 10A.

### Other VFO Criteria

Apart from the stability considerations just treated, purity of emissions from VFOs is vital to most designers. It is prudent to minimize the harmonic output of a VFO chain and to ensure that vhf parasitic energy is not being generated within the LO system.

The pi-network output circuit of Fig. 11B helps reduce harmonics because it is a low-pass network. Additional filtering can be added at the VFO-chain output by inserting a half-wave filter with a loaded Q of 1 ( $X_L$  and  $X_C = 50$  for a 50-ohm line).

Vhf parasitics are not uncommon in the oscillator or its buffer stages, especially when high  $f_T$  transistors are employed. The best preventive measures are keeping the signal leads as short as possible and adding parasitic suppressors as required. The parasitic energy can be seen as a superimposed sine wave riding on the VFO output waveform when a high-frequency scope is used.

A low-value resistor (10 to 22 ohms) can be placed directly at the gate or base of the oscillator transistor to stop parasitic oscillations. Alternatively, one or two ferrite beads (950 $\mu_i$ ) can be slipped over the gate or base lead to resolve the problem. If vhf oscillations occur in the buffer stages, the same preventive measures can be taken.

VFO noise should be minimized as much as possible. A high-Q oscillator tank will normally limit the noise bandwidth adequately. Resistances placed in the signal path will often cause circuit noise. Therefore, it is best to avoid the temptation to control the rf excitation to a given LO stage by inserting a series resistor. The better method is to use small-value coupling capacitors.

### A Practical VFO

The circuit of Fig. 12 is for a high stability 1.8- to 1.9-MHz VFO. A circuit-board pattern and layout is included. Although the VFO frequency is for 160-meter operation, other tuning ranges up to 10 MHz are possible with this circuit. The design guidelines offered in the previous section will be useful in altering the circuit to other frequencies. A close approximation can be had by simply taking the  $X_L$  and  $X_C$  values for the components specified in Fig. 12A and determining from those reactances the new values for the frequency of interest.



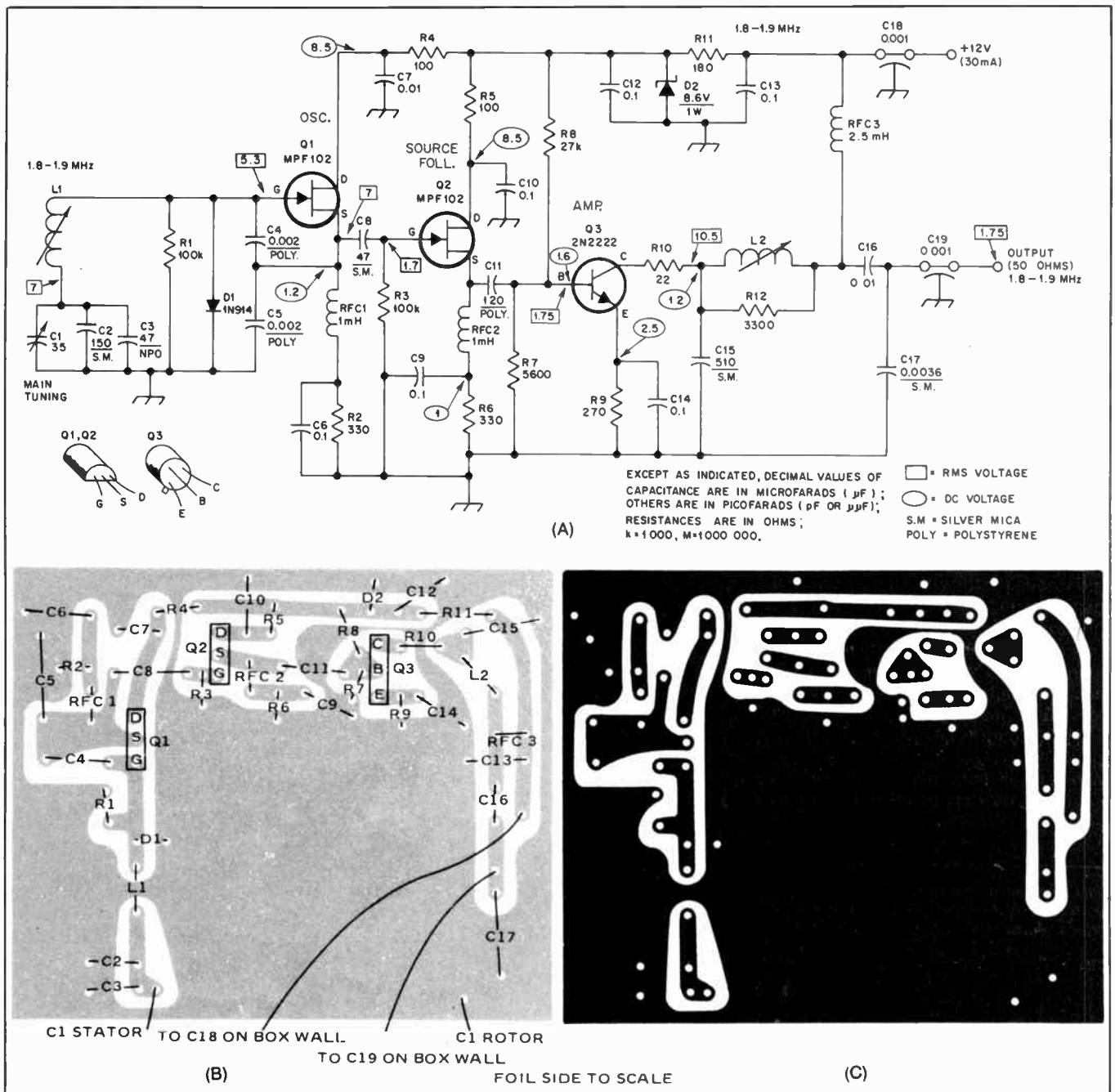


Fig. 12 — At A is the circuit of a proven VFO chain which has exceptional stability under fairly constant room temperature. Although it is shown for operation from 1.8 to 1.9 MHz, it can be modified and used as high as 10 MHz. The pc-board pattern and layout at B and C are suitable for any operating frequency. The etched side of the board is shown in both examples.

The tuning range will be determined by the capacitance value of C1. Data on precise component values for other frequency ranges are not available from the ARRL. Further information on VFO design and the general circuit of Fig. 12-A was provided by DeMaw in June 1976 *Ham Radio*.

### Premixing

It is difficult to build a variable-frequency oscillator for operation above 10 MHz with drift of only a few Hz. A scheme called premixing shown in Fig. 13A, may be used to obtain VFO output in the 10- to 50-MHz range. The output of

a highly stable VFO is mixed with energy from a crystal-controlled oscillator. The frequencies of the two oscillators are chosen so that spurious outputs generated during the mixing process do not fall within the desired output range. A band-pass filter at the mixer output attenuates out-of-band spurious energy. The charts given in chapter 8 can be used to choose oscillator combinations which will have a minimum of spurious outputs.

### PLL

Receivers and transmitters of advanced design are now using phase-locked loops (PLLs) to generate highly stable local

oscillator energy as high as the microwave region. The PLL has the advantage that no mixing stage is used in conjunction with the output oscillator, so the output energy is quite "clean." The Kenwood TS-820, the Collins 651S-1, and the National HRO-600 currently use PLL high-frequency oscillator systems.

The basic diagram of a PLL is shown in Fig. 13B. Output from a voltage-controlled oscillator (VCO) and a frequency standard are fed to a phase detector which produces an output voltage equal to the difference in frequency between the two signals. The error voltage is amplified, filtered, and applied to the VCO. The error



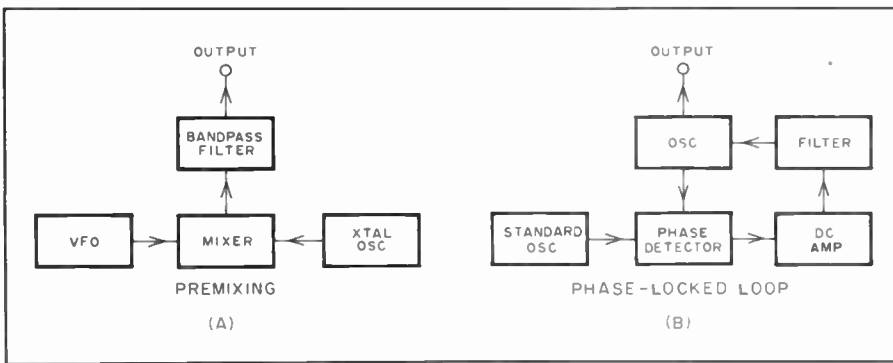


Fig. 13 — Block diagrams of the (A) premixing and (B) phase-lock loop methods.

voltage changes the frequency of the VCO until it is locked to the standard. The bandwidth of the error-voltage filter determines the frequency range over which the system will remain in phase lock.

Three types of phase-locked loops are now in use. The simplest type uses harmonics of a crystal standard to phase-lock an HFO, providing the injection for the first mixer in a double-conversion re-

ceiver. A typical circuit is given in Fig. 14. Complete construction details on this PLL were given in January 1972 *QST*. A second type of phase-locked loop uses a stable mf VFO as the standard which stabilizes the frequency of an hf or vhf VCO. This approach is used in the receiver described by Fischer in March 1970 *QST*.

The other PLL system also uses a crystal-controlled standard, but with program-

mable frequency dividers included so that the VCO output is always locked to a crystal reference. The frequency is changed by modifying the instructions to the dividers; steps of 100 Hz are usually employed for hf receivers while 10-kHz increments are popular in vhf gear.

### VFO Dials

One of the tasks facing an amateur builder is the difficulty of finding a suitable dial and drive assembly for a VFO. A dial should provide a sufficiently slow rate of tuning — 10 to 25 kHz per knob revolution is considered optimum — without backlash. Planetary drives are popular because of their low cost; however, they often develop objectional backlash after a short period of use. Several types of two-speed drives are available. They are well suited to home-made amateur equipment. The Eddystone 898 precision dial has long been a favorite with amateurs, although the need to elevate the VFO far above the chassis introduces some mechanical-stability problems. If a permeability-tuned oscillator (PTO) is used, one of the many types of turn

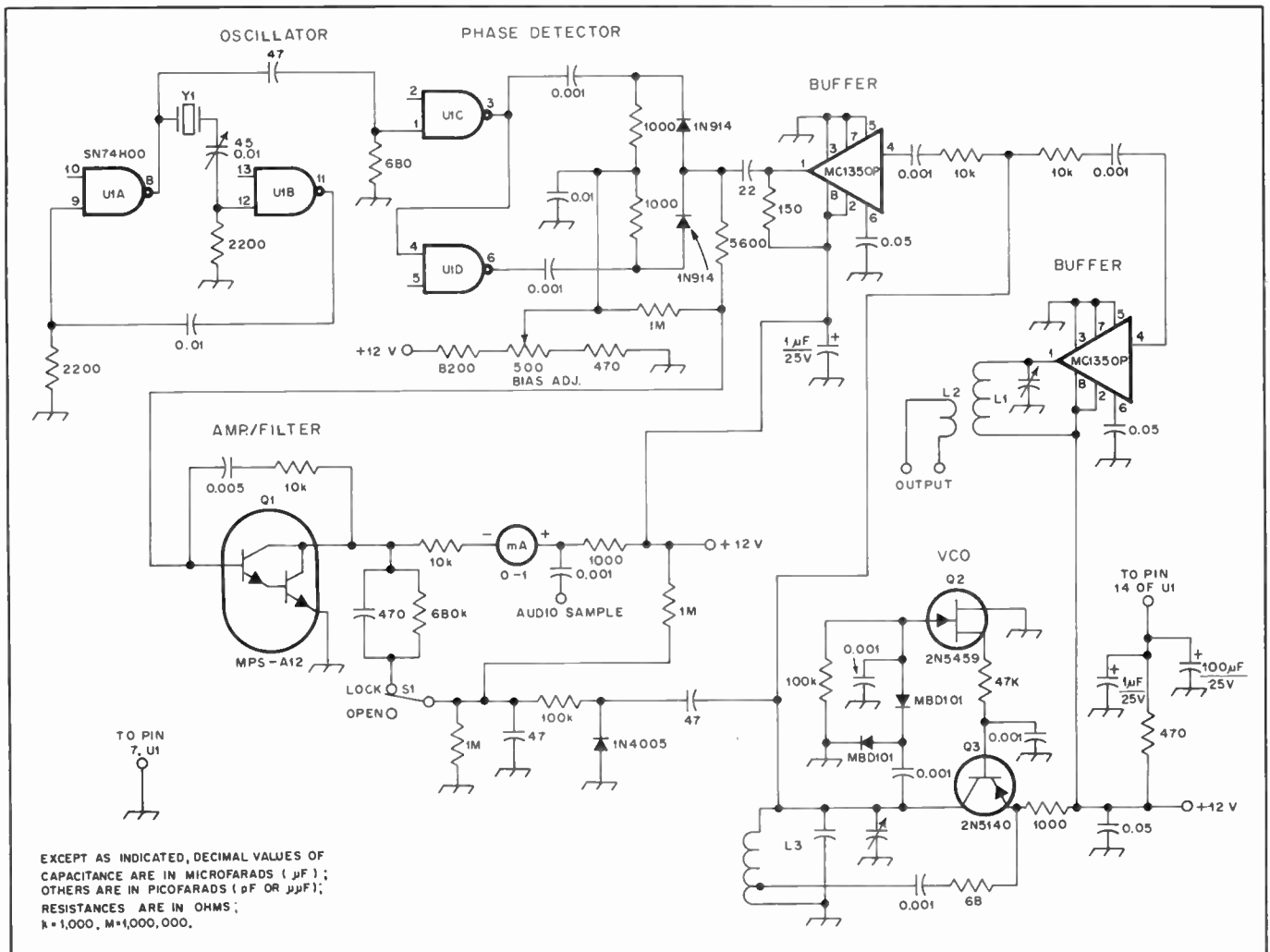


Fig. 14 — A practical PLL for a crystal-controlled HFO. Y1 is chosen so the harmonic content is ample at the desired output frequency. A 200-kHz crystal is fine to 40 MHz, a 500-kHz one is suitable to 60 MHz and a 1-MHz crystal is good for use to 80 MHz. L1 and L3 are resonant at the output frequency.



Fig. 15 — A five-digit readout that uses LEDs.

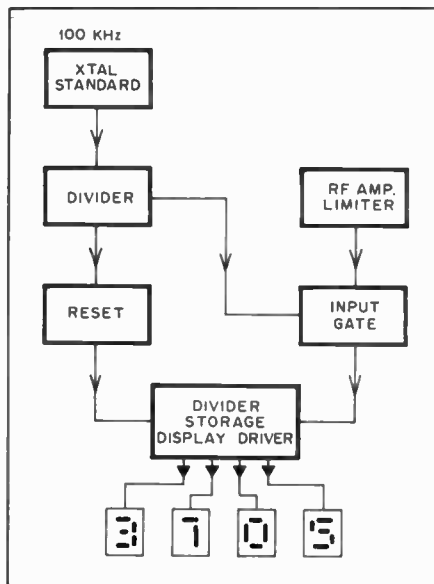


Fig. 16 — Frequency counter block diagram.

counters made for vacuum variable capacitors or rotary inductors may be employed.

### Linear Readout

If linear-frequency readout is desired on the dial, the variable capacitor must be only a small portion of the total capacitance in the oscillator tank. Capacitors tend to be very nonlinear near the ends of rotation. A gear drive providing a 1.5:1 reduction should be employed so that only the center of the capacitor range is used. Then, as a final adjustment, the plates of the capacitor must be filed until linear readout is achieved. In a PTO, the pitch of the oscillator coil winding may be varied so that linear frequency change results from the travel of the tuning slug. Such a VFO was described in July 1964 *QST*. A different approach was employed by Lee (November 1970 *QST*), using a variable-capacitance diode (Varicap) as the VFO tuning element. A meter which reads the voltage applied to the Varicap was calibrated to indicate the VFO frequency.

### Electronic Dials

An electronic dial consists of a simplified frequency counter which reads either the VFO or operating frequency of a transmitter or receiver. The advantage of an electronic dial is the excellent accuracy (to 1 hertz, if desired) and the fact that VFO tuning does not have to be linear. The readout section of the dial may

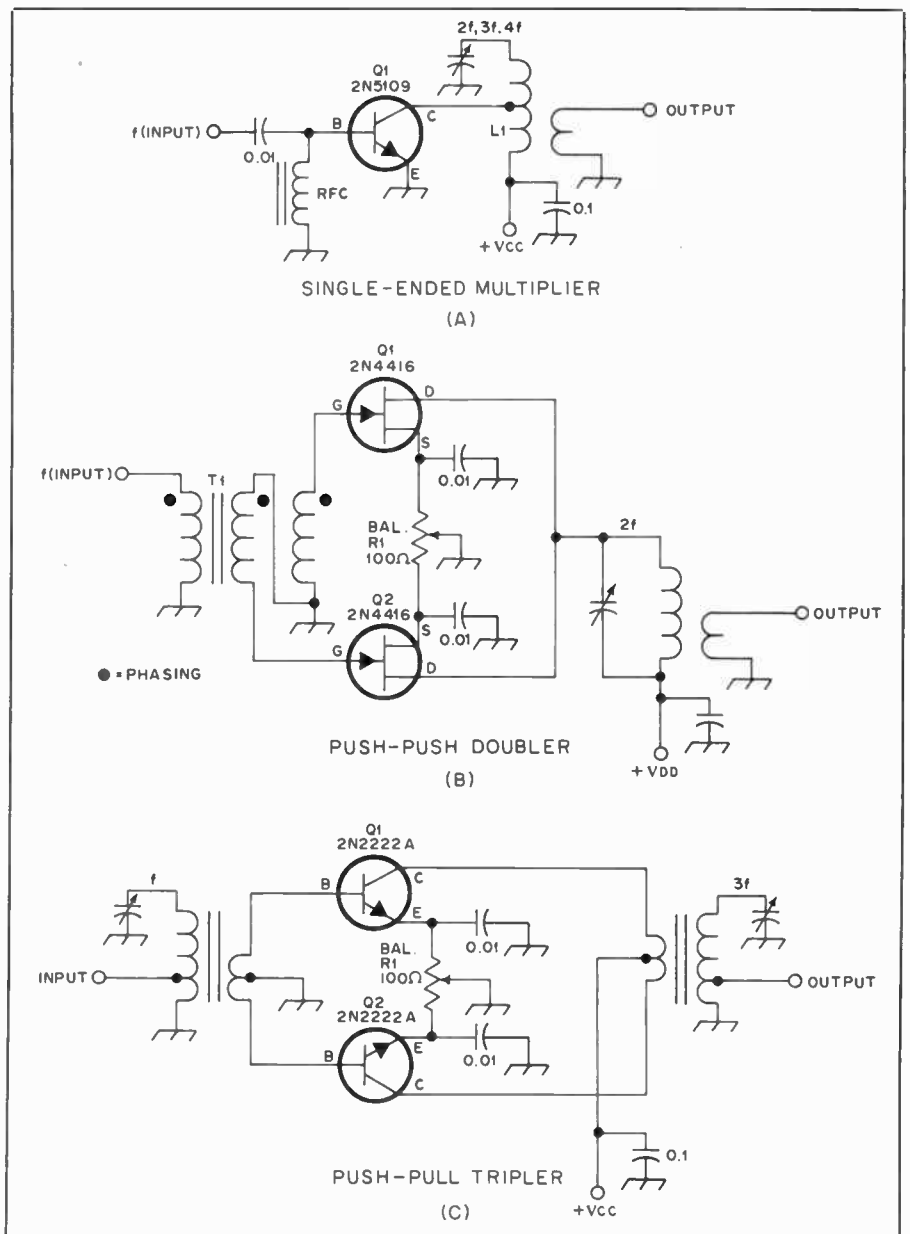


Fig. 17 — Single-ended multiplier (A), push-push doubler (B), and push-pull tripler (C).

use neon-glow tubes called *Nixies* (a trade name of the Burroughs Corp.), or a seven-segment display using incandescent lamps, filament wires in a vacuum tube, or LCDs (liquid crystal display), or LEDs (light-emitting diodes). A typical LED display is shown in Fig. 15. The use of MSI and LSI circuits, some containing as many as 200 transistors on a single chip, reduces the size required for an electronic dial to a few square inches of circuit-board space.

A typical counter circuit is given in Fig. 16. The accuracy of the counter is determined by a crystal standard which is often referred to as a *clock*. The output from a 100-kHz calibration oscillator, the type often used in receivers and transmitters, may be employed if accuracy of 100 Hz is sufficient. For readout down to 1 Hz, a 1-to-10-MHz AT-cut crystal should be chosen, because this type of

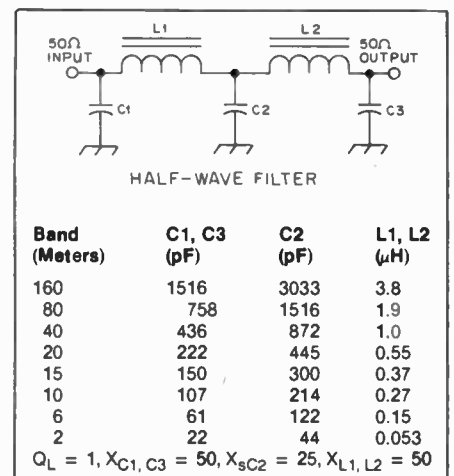


Fig. 18 — Half-wave harmonic filter and a table of values for 160 through 2 meters. This filter has a low-pass response.

high-accuracy crystal exhibits the best temperature stability. The clock output energy is divided in decade-counter ICs to provide the pulse which opens the input gate of the counter for a preset time. The number of rf cycles which pass through the gate while it is open are counted and stored. Storage is used so that the readout does not blink. At the end of each counting cycle the information that has been stored activates the display LEDs, which present the numbers counted until another count cycle is complete. A complete electronic dial arranged to be combined with an existing transmitter or receiver was described in October 1970 *QST*. Also, Macleish *et al* reported an adapter which allows a commercially made frequency counter to be mated with ham gear so that the counter performs as an electronic dial (May 1971 *QST*).

### Frequency Multiplication

It may be necessary to use frequency multipliers at some point after the VFO or other frequency generator in a transmitter. When this need is present, the circuits of Fig. 17 can be applied. Of course, vacuum-tube multipliers are entirely suitable if the design is not one which uses semiconductors. The fundamental principles for frequency multiplication are applicable to tubes and transistors alike. The requisite is that of operating the devices in Class C. Although a transistor circuit may be seen with forward bias applied to a frequency multiplier, the stage must be driven hard enough to override the bias and operate Class C. Forward bias is sometimes used in a multiplier stage (solid state) to lower the excitation requirements. Negative voltage (reverse bias) is often used on the grid of a vacuum-tube multiplier, but forward bias is not.

The circuit of Fig. 17A is probably the least suitable for frequency multiplication. Typically, the efficiency of a doubler of this type is 50 percent, a tripler is 33 percent, and a quadrupler is 25 percent. Additionally, harmonics other than the one to which the output tank is tuned will appear in the output unless effective bandpass filtering is applied. The collector tap on L1 of Fig. 17A is placed at a point which offers a reasonable compromise between power output and spectral purity: The lower the tap with respect to  $V_{CC}$ , the lighter the collector loading on L1 and the greater the filtering action of the tuned circuit. The tradeoff is, however, a reduction in output power as the mismatch of the collector to the load increases.

A push-push doubler is seen at Fig. 17B. Because of the conduction angle of this type of circuit the efficiency is similar to that of a straight amplifier which operates in Class C. Also, the driving frequency ( $f$ ) will be well attenuated at the doubler output if electrical balance and

component symmetry are ensured. A 12AU7A tube will work nicely in this type of circuit well into the vhf region. T1 in this example is a trifilar-wound, broadband toroidal transformer. It drives the gates of Q1 and Q2 in push pull (opposite phase). The drains are in parallel and are tuned to  $2f$ . R1 is used to establish electrical balance between Q1 and Q2. R1 is set while the doubler is being fully driven. Diode doublers can be used in a similar circuit, but the subject will not be treated here (see chapter four).

A push-pull tripler is illustrated in Fig. 17C. Once again the matter of electrical balance and symmetry is important to good operation. The circuit discriminates against even harmonics, thereby aiding spectral purity. The efficiency is somewhat better than a tripler using the circuit of Fig. 17A. If vacuum tubes are used in the circuits of Fig. 17, the input ports should employ high-impedance tuned circuits for best performance.

### Output Filtering

Output purity from oscillators, multipliers and amplifiers is of paramount importance to the performance of numerous circuits. In the interest of compliance with current FCC regulations, wherein all spurious emissions from a transmitter must be 40 dB or greater below the peak power of the desired signal, filtering is important. The type of filter used — band-pass, notch, low-pass or high-pass — will depend on the application. Band-pass filters afford protection against spurious responses above and below the amateur band for which they have been designed. Low-pass filters attenuate energy above the desired

output frequency, while high-pass filters reduce energy below the band of interest. It is common practice to include a harmonic filter at the output of a VFO chain to ensure purity of the driving voltage to a mixer or amplifier stage. The filter bandwidth must be adequate for the tuning range of the VFO in order to prevent attenuation of the output energy within the desired band. For this reason, a low-pass type of filter is used in preference to a bandpass one by some designers. Fig. 18 contains the circuit of a half-wave filter which can attenuate harmonics by 40 dB or more. Essentially, it consists of two pi networks in cascade, providing a low-pass response. The loaded Q is 1 and the bilateral impedance is 50 ohms. The chart provides L and C values for 160 through 2 meters, inclusive. In many cases the nearest standard capacitor value will suffice, such as 1500 pF for C2 during 80-meter use. Alternatively, a combination of fixed-value silver-mica capacitors and mica compression trimmers can be used in parallel at C1, C2 and C3 to obtain the chart values. Toroidal inductors, because of their self-shielding properties, are ideal for L1 and L2 from low to moderate power levels. Miniductor stock can be used for higher-power versions. Disk ceramic or paper capacitors are not suitable for use in rf filters. Standard mica or silver-mica capacitors are recommended. Fig. 19 contains a photograph of a 160-meter half-wave filter that was built for use at the output of a 500-watt transmitter. Transmitting micas are used for the capacitors and Miniductor stock is employed for the coils. The inductors are mounted at right angles to

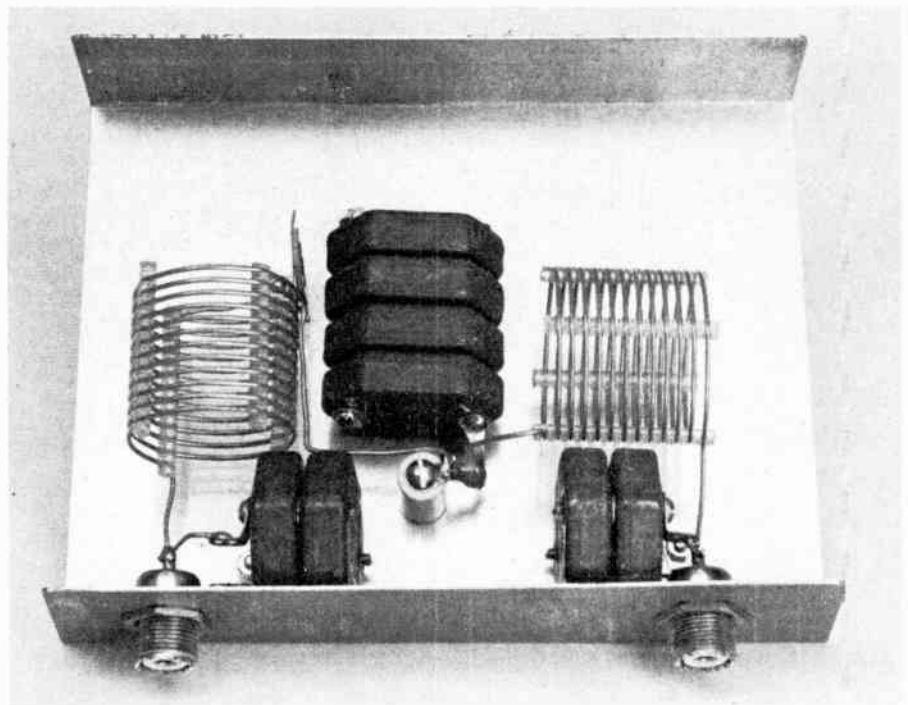


Fig. 19 — Photograph of a transmitting type of half-wave filter for use on 160 meters.



one another to discourage unwanted coupling between the input and output halves of the filter. The circuits shown in Fig. 20 can be employed where a high-pass or low-pass filter characteristic is sufficient. (In some instances, a band-pass filter may be required.)

These filters are based on a Chebyshev design and component values are given in Table 1. The filters are "normalized" to a frequency of 1 MHz and an input and output impedance of 52 ohms. In order to translate the designs to other frequencies, all that is necessary is to divide the component values by the new frequency in MHz. (The 1-MHz value represents a "cut-off" frequency. That is, the attenua-

tion increases rapidly above this frequency in the low-pass case or below  $f_c$  in the high-pass application. This effect should not be confused with the variations in attenuation in the passband.) For instance, if it was desired to eliminate harmonics from a VFO at frequencies above 5 MHz, the inductance and capacitance values would be divided by 5.0.

Other impedance levels can also be used by multiplying the inductors by the ratio  $Z_o/52$  and the capacitors by  $52/Z_o$ , where  $Z_o$  is the new impedance. This factor should be applied in addition to the ones for frequency translation. Examination of the component values in Table 1 indicates changing the impedance level to a somewhat higher one is advisable if practical. This would avoid having very small inductance values and high capacitance values which might be impractical when constructing a filter.

The choice of filter model depends mostly on the power level involved. In low-level stages, the effects of variation in insertion loss in the passband usually can be neglected in amateur applications. Consequently, the filter with a 3-dB ripple can be used. However, VSWR is closely related to insertion loss and the 0.1-dB filter should be selected in power-amplifier stages where VSWR could cause harmful effects. The 0.1-dB filter should have a maximum VSWR of approximately 1.4:1. Unfortunately, the 0.1-dB design doesn't have the rapid rolloff that the 3-dB model possesses, as can be seen by the tabulated data in Fig. 20. While other filters are possible with different ripple factors, the ones shown in Fig. 20 should cover a wide variety of applications.

amplifier. Amplifier IMD (third- and fifth-order products) in solid-state power stages which operate linearly is fully as acceptable as that which is observed in most tube types of linear amplifiers. Typically, if a design is correct, the IMD will be on the order of -33 dB from the reference power value.

The major area of concern when designing a solid-state driver or PA section is to prevent low-frequency self-oscillations. Such parasitics tend to modulate the carrier and appear as spurious responses within the amplifier passband. The low-frequency parasitics occur as a result of the extremely high gain exhibited by hf and vhf transistors at the low-frequency end of the spectrum. The theoretical gain increase for a given transistor is 6 dB per octave as the operating frequency is lowered. The same is not true of vacuum tubes. Therefore, it is necessary to employ quality decoupling and bypassing in the circuit. It is similarly important to use low-Q, low-inductance rf chokes and matching networks to discourage low-frequency tuned-base, tuned-collector oscillations. The suppression concepts just discussed are illustrated in Fig. 21 at B and C. In the circuit at B there are two 950- $\mu$  ferrite beads added over the pigtail of RFC1 to swamp the Q of the choke. Three bypass capacitors (0.001, 0.01 and 0.1  $\mu$ F) are used with RFC2 of Fig. 20B to provide effective rf decoupling from vhf to mf. A 22- $\mu$ F capacitor is used near RFC2 to bypass the +V<sub>cc</sub> line at low frequency and audio. This method is recommended for each high-gain solid-state stage in a transmitter.

### Driver Circuits

The circuits of Fig. 21A and 21B are typical of those which would be employed to excite a tube type of PA stage. The 6GK6 tube driver at A can be biased for Class C or Class AB operation, making it suitable for cw or ssb service. Of course, the AB mode would be suitable for cw and ssb, and would require considerably less excitation power than would the same stage operating in Class C. Other tubes that perform well in this circuit are the 6CL6, 12BY7A and 5763. The output tank is designed for high impedance in order to interface properly with the high-impedance grid of the PA. It may be necessary to include a neutralization circuit with this type of amplifier, especially if careful layout is not used. The high transconductance of the 6GK6 series encourages self-oscillation near the operating frequency. Z1 is a parasitic choke which should be included as a matter of course to prevent vhf parasitics.

A transistor amplifier which is suitable for driving a Class C tube PA is presented in Fig. 21B. Q1 operates Class C, so it is not satisfactory for amplifying ssb energy. However, forward bias (approximately 0.7 volt) can be added to move the

Table 1

Component values for filters shown in Fig. 20. Inductances are microhenries and capacitances are in picofarads.

Fig. 20A (LP)	L <sub>1</sub>	C <sub>2</sub>	L <sub>3</sub>	C <sub>4</sub>	L <sub>5</sub>
Fig. 20B (HP)	C <sub>1</sub>	L <sub>2</sub>	C <sub>3</sub>	L <sub>4</sub>	C <sub>5</sub>
0.1-dB LP	9.49	4197	16.4	4197	9.49
3-dB LP	28.8	2332	37.6	2332	28.6
0.1-dB HP	2669	6.04	1550	6.04	2669
3-dB HP	879	10.9	675	10.9	879

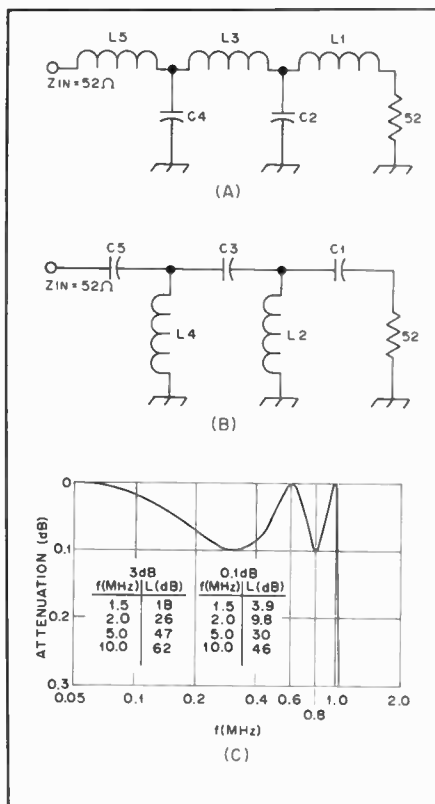


Fig. 20 — Low-pass and high-pass Chebyshev filters normalized to a frequency of 1 MHz and input/output impedance terminations of 52 ohms. Component values for 0.1- and 3-dB ripple-factor filters are given in Table 1. Passband frequency response for the 0.1-dB low-pass model is shown at C. Curve is similar in shape for the 3-dB model except for scale factor. Response for the high-pass designs can be determined by substituting  $1/f$  (MHz) for  $f$  at C.



operating curve into the Class AB (linear) region, thereby making the stage suitable for ssb signal amplification. A 1.5-ohm resistor can be added between the emitter and ground to help prevent thermal runaway and to introduce degeneration (feedback) for enhancing stability. No bypass capacitor would be used from emitter to ground if this were done. T1 is a narrow-band toroidal rf transformer that has a turns ratio suitable for transforming the collector impedance to the grid impedance (determined by the value of the grid resistor of the PA) of the final amplifier. The secondary winding of T1 is tuned to resonance at the operating frequency. Approximately 1 watt of power output can be taken from Q1 in the hf region when a 12-volt  $V_{cc}$  is used. This is ample power for driving a pair of 6146B tubes in Class AB1.

A broadband type of solid-state driver is shown in Fig. 21C. The tradeoff for broadband operation (1.8 to 30 MHz in this example) is a reduction in maximum available gain (MAG). Therefore, the output power from Q1 of Fig. 21C will be less than 1 watt. The stage operates Class A, making it linear. The emitter is unbypassed to provide emitter degeneration. Shunt feedback is used between the base and collector to enhance stability and contribute to the broadband characteristic of the circuit. T1 is a broadband conventional transformer wound on a toroid core. The turns ratio is adjusted to match the approximate 200-ohm collector impedance to the base impedance of the transistor PA stage. The latter is typically less than 5 ohms. Heat sinks are required for the transistors of Fig. 21B and C. The primary of T1 should have a reactance of roughly four times the collector impedance. This is related to the lowest proposed operating frequency. Therefore, for 1.8 MHz the primary winding would be  $70 \mu\text{H}$  ( $X_L = 800$  ohms). This can be achieved easily by using an FT-50-43 Amidon core. The primary advantage to a broadband driver is that it need not be band-switched or peaked by means of a front-panel control. The transistor selected for broadband service should have a very high  $f_T$  rating. It needs to have high beta as well. Transistors designed for uhf service are excellent as hf-band amplifiers when broadbanding is contemplated. Neutralization is not necessary when using bipolar-transistor amplifiers.

A practical three-stage broadband amplifier strip is shown schematically in Fig. 22. With an input level of 10 mW it is possible to obtain 1.4 watts of output from 3.5 to 29 MHz. A keying transistor (Q4) is included for turning the amplifier off by means of a VOX, or for keying it during cw operation.

Rms and dc voltages are noted on the diagram of Fig. 22 to aid in troubleshooting. Overall gain for the strip at 7 MHz is 31 dB, with slight gain varia-

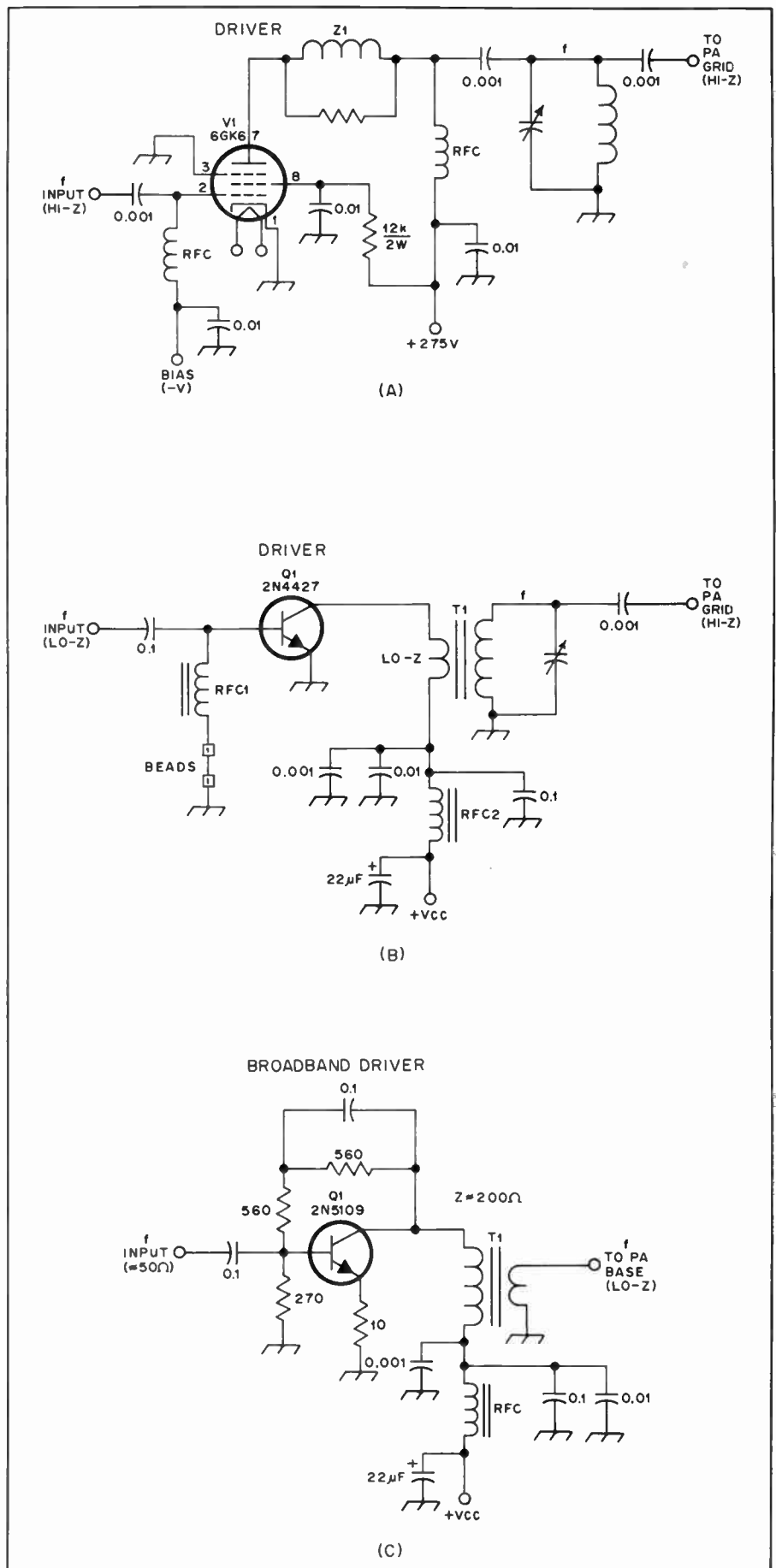


Fig. 21 — Circuit examples of transistor and tube driver stages for use in transmitters.



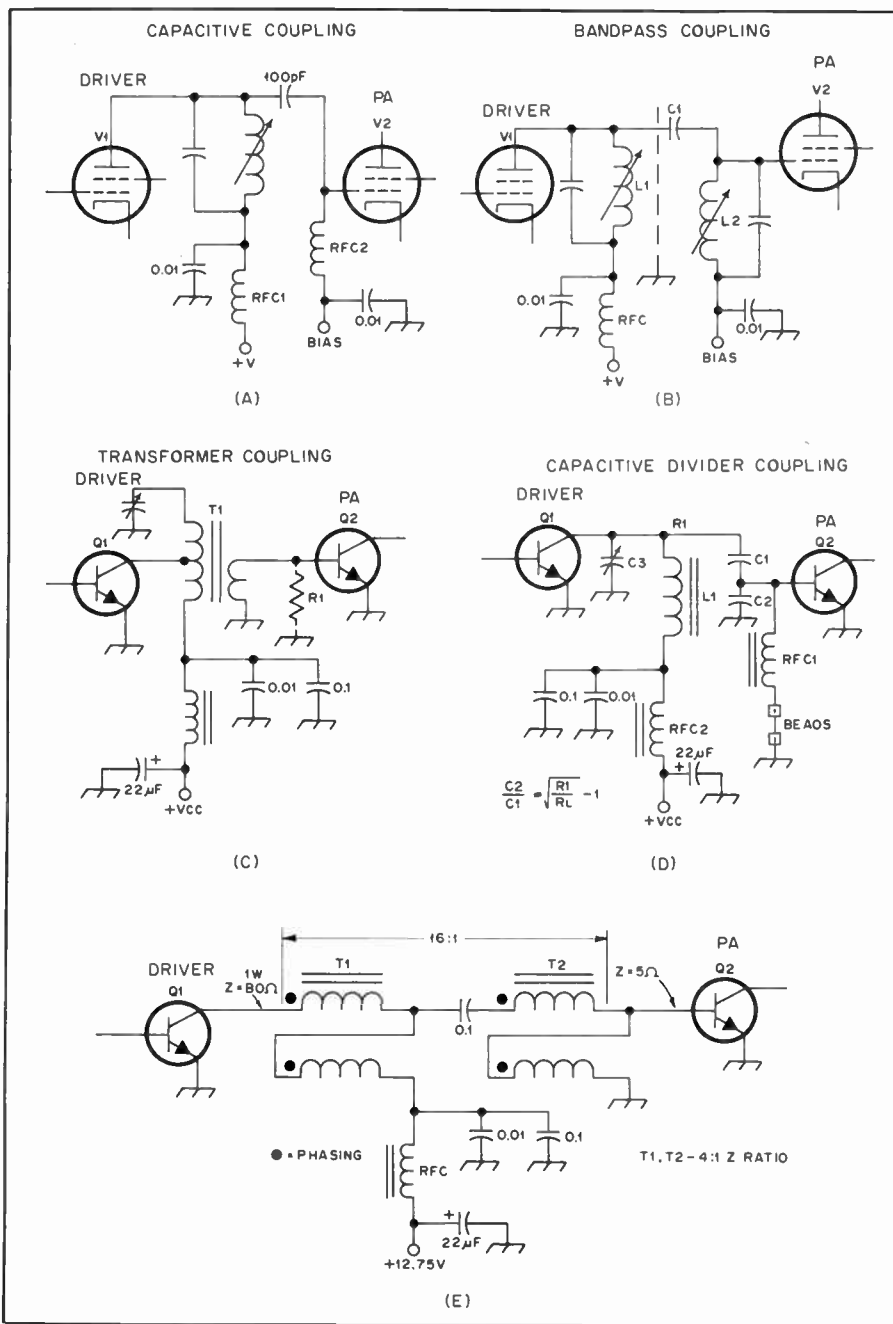


Fig. 23 — Typical coupling methods for use between amplifier stages. See text.

networks are applicable to transistor stages. The collector and base of the two stages would be tapped down on L1 and L2 to minimize loading. This helps preserve the loaded Q of the tuned circuits, thereby aiding selectivity.

A common form of transformer coupling is seen at Fig. 23C. T1 is usually a toroidal inductor for use up to approximately 30 MHz. At higher frequencies it is often difficult to provide a secondary winding of the correct impedance ratio respective to the primary winding. Depending on the total number of transformer turns used, the secondary might call for less than one turn, which is impractical. However, for most of the spectrum up to

30 MHz this technique is entirely satisfactory. The primary tap on T1 is chosen to transform the collector impedance of Q1 to the base impedance of Q2 by means of the turns ratio between the tapped section and the secondary winding of the transformer. R1 may be added in shunt with the secondary to stabilize Q2 if there is a tendency toward self-oscillation. The value used will be in the 5- to 27-ohm range for most circuits. The rule of thumb is to use just enough resistance to tame the instability.

A method for coupling between stages by means of a capacitive divider is illustrated in Fig. 23D. The net value of C1 and C2 in series must be added to the

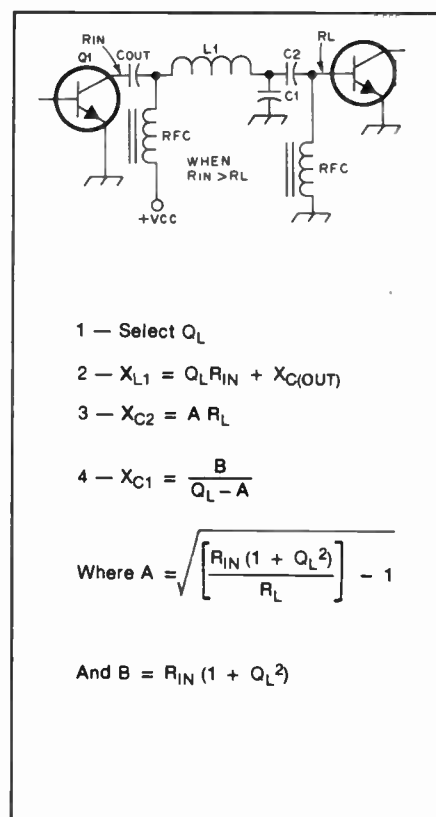


Fig. 24 — Circuit and mathematical solution for matching network no. 1.

capacitance of C3 when determining the inductance required for resonance with L1. The basic equation for calculating the capacitance ratio of C1 and C2 is included in the diagram. RFC1 serves as a dc return for the base of Q2. The Q of the rf choke is degraded intentionally by the addition of two 950-mu ferrite beads. This aids stability, as discussed earlier in this chapter. An advantage to using this type of circuit is that vhf and uhf parasitics are discouraged and harmonic currents are attenuated when C2 is fairly high in capacitance. This is not true of the circuit in Fig. 23C.

When the impedance levels to be matched are of the proper value to permit employing specific-ratio broadband transformers, the circuit of Fig. 23E is useful. In this example two 4:1 transformers are used in cascade to provide a 16:1 transformation ratio. This satisfies the match between the 80-ohm collector of Q1 and the 5-ohm base of Q2. The shortcoming of this technique is the lack of selectivity between stages, but the advantage is in the broadband characteristic of the coupling system. The phasing dots on the diagram near T1 and T2 indicate the correct electrical relationship of the transformer windings.

#### Network Equations

When the source impedance is greater than the load impedance (Fig. 24), network 1 is desirable. The output

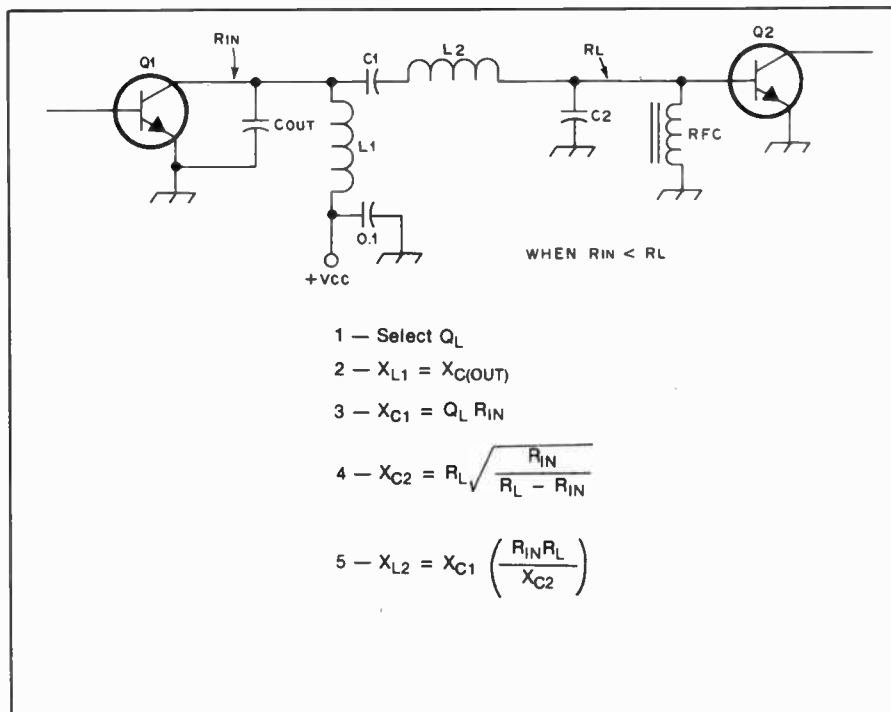


Fig. 25 — Circuit and equations for network no. 2.

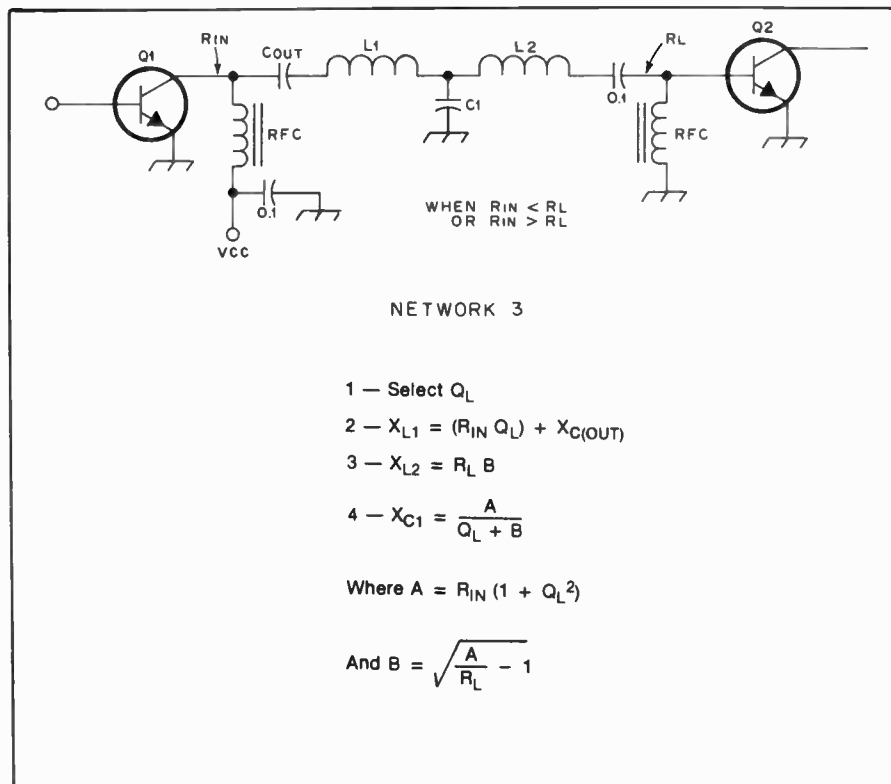


Fig. 26 — Network-solution equations and circuit for network no. 3.

capacitance of Q1 must be included in the equations. It is expressed in the network examples which follow as "C<sub>OUT</sub>." Before the equations can be worked it is necessary to choose a network loaded Q. A Q of 3, 4 or 5 is suggested for amateur work.

Network 2 (Fig. 25) can be applied when the source impedance is less than the load impedance. The rules for computing the L and C values are the same as for network 1, but with variations in the equations.

A low-pass T network is shown in Fig.

26. It has the advantage of being useful for matching a high source impedance to a low load impedance, or vice versa. Furthermore, the low-pass characteristic aids harmonic reduction. Some designers feel that of the various matching networks used in semiconductor work, the T network is the best in terms of collector efficiency.

Networks 1, 2 and 3 are entirely suitable for use between a transistor PA and the antenna, but harmonic filtering should be included between the network and the transmission line to the antenna. These three networks are covered in detail in the Motorola *Application Note AN-267*. Another excellent paper on the subject was written by Becciolini — Motorola *Application Note AN-271*. The equations for networks 1, 2 and 3 were taken from AN-267. That paper contains computer solutions to these networks and others, with tabular information for various Qs and source impedances. A fixed load value of 50 ohms is the base for the tabular data.

A design example for network 3 is given in Fig. 27. The solutions for the other two networks follow the same general trend, so examples for networks 1 and 2 will not be given. In Fig. 27 the component "C<sub>OUT</sub>" is taken from the manufacturer's data sheet. If it is not available it can be ignored at the expense of a slight mathematical error in the network determination. By making C1 variable the network can be made to approximate the correct transformation ratio. At the lower frequencies C1 will be fairly large in value. This may require a fixed-value silver-mica capacitor being used in parallel with a mica compression trimmer to obtain the exact value of capacitance needed. The equations will seldom yield standard values of capacitance.

L1 and L2 of Fig. 27 can be wound on powdered-iron toroid cores of suitable cross-sectional area for the power involved. This is explained in an earlier chapter of this book. L1 and L2 should be separated from one another by mounting them apart and at right angles. Alternatively, a shield can be used between the inductors. This will prevent unwanted capacitive and inductive coupling effects between the input and output terminals of the network. Despite the self-shielding nature of toroidal inductors, some coupling is possible when they are in close proximity.

### Stable Operating Conditions

Purity of emissions and longevity of the active devices in a tube or transistor circuit depend heavily upon stability during operation. The subject of power-lead decoupling has already been treated, wherein bypassing for vhf, hf and lf is essential in the dc leads to each transistor amplifier stage. The bypass capacitors are used in combination with low-inductance



rf chokes in most instances. Although the same concept can be applied to tube types of amplifiers, the possibility of self-oscillations at frequencies lower than vhf are not as pronounced. For the most part, tube amplifiers will operate stably if input-output shielding is provided for high-gain stages (grid circuitry shielded from plate circuitry). Depending upon the inter-electrode capacitances of tubes, a neutralization circuit may be necessary. This will cancel *positive feedback* and prevent regeneration. It involves sampling a small amount of the output energy (opposite phase of the input energy) and feeding it back to the amplifier input, thereby cancelling the unwanted in-phase (positive) feedback. A typical circuit is given in Fig. 28. L2 provides a 180-phase reversal because it is center tapped. C1 is used between the plate and the lower half of the grid tank to permit cancellation of the unwanted feedback voltage. C1 is set for the approximate value of the grid-plate capacitance of the tube, the value of which can usually be found on the tube data sheet. C1 is adjusted in one of two ways: It is set at a value which results in no change in tube grid current as the plate tank is tuned through its range. Alternatively, operating voltages are applied to the tube, but no drive is used. A scope or sensitive rf meter is connected to the plate tank and C1 is adjusted for zero output signal — indicating that self-oscillation is not taking place. *Extreme care must be exercised when the tube operating voltages are present!* Always keep the probe of the measuring instrument connected to a circuit point which does not contain dc voltage. Sampling at L4 is recommended for the circuit of Fig. 28. C1 needs to have ample plate spacing to prevent voltage breakdown when the amplifier is operating.

All leads which conduct rf energy should be kept as short as possible in an amplifier circuit, and likewise with the pigtailed bypass capacitors. This applies to tube or transistor amplifiers.

Z1 of Fig. 28 is a vhf parasitic choke. Such a network will damp self-oscillations at vhf and uhf by acting as a series impedance which breaks up the usual unwanted vhf/uhf circuit path. Z1 consists of a non-inductive resistor between 51 and 100 ohms. A coil is wound around the resistor body to provide a broadband rf choke which presents a high impedance at vhf and higher, but looks like a low reactance in the hf region and lower. A typical parasitic suppressor for a power level up to 150 watts contains 6 to 8 turns of no. 20 wire wrapped around a 56-ohm, 1-watt composition resistor. The coil ends are soldered to the resistor pigtailed near the body of the resistor. Z1 is then placed as close to the tube plate pin or cap as possible. For higher rf powers it is practical to use a high-wattage Globalbar resistor, or a 25-watt noninductive (NIT)

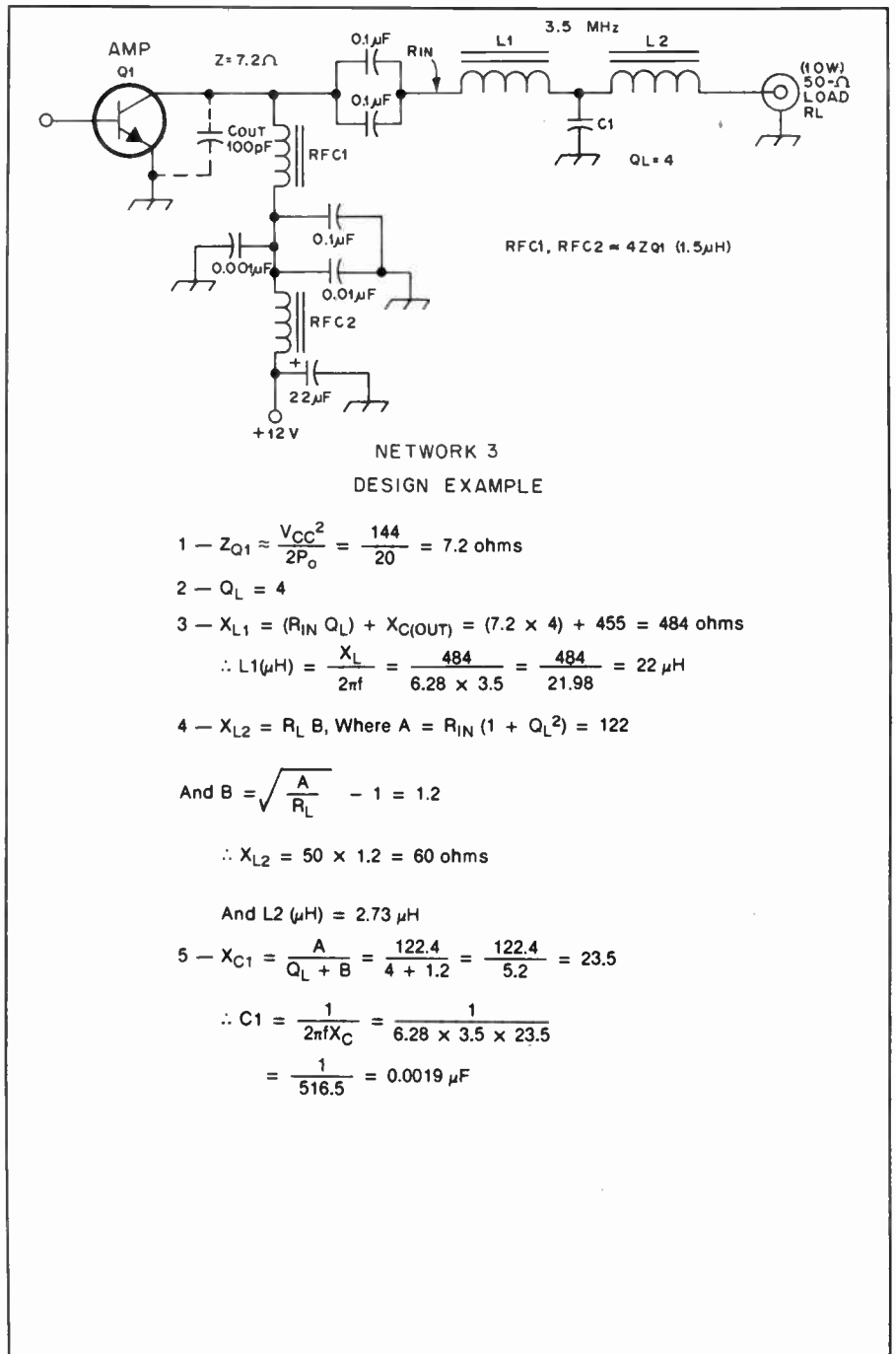


Fig. 27 — A practical example of network no. 3 and the solution to the network design.

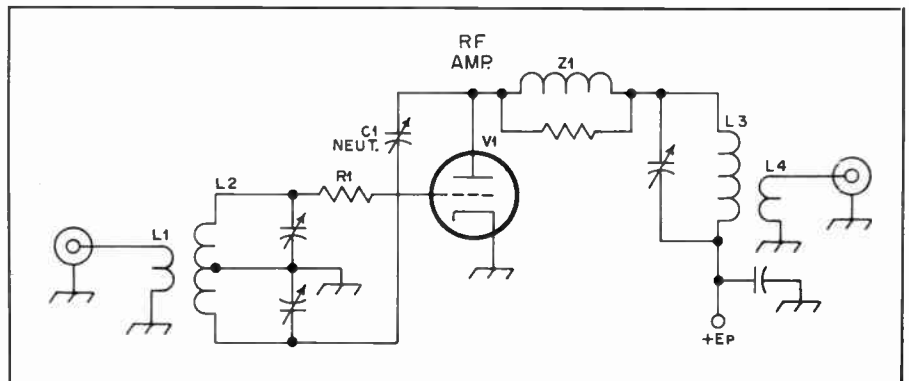


Fig. 28 — Example of neutralization of a single-ended rf amplifier.

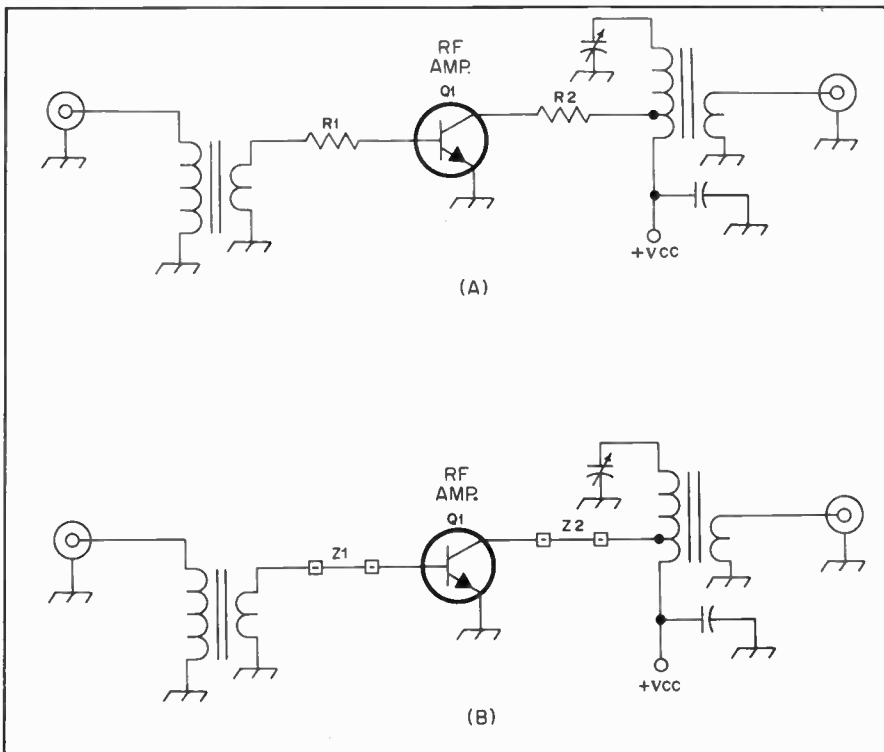


Fig. 29 — Suppression methods for vhf and uhf parasitics in solid-state amplifiers.

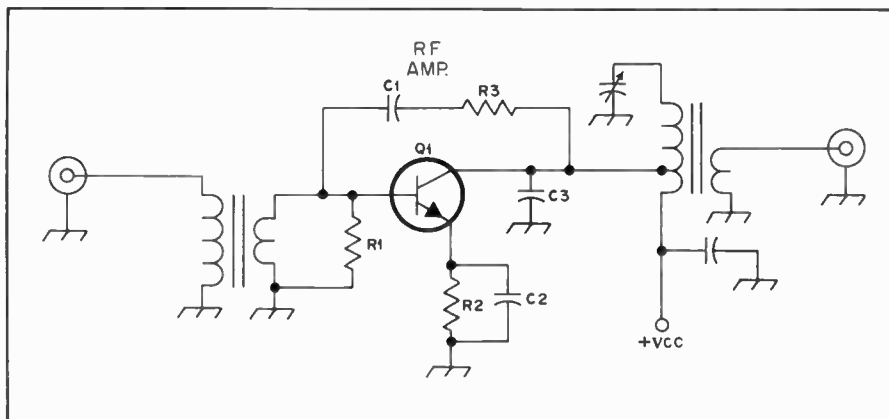


Fig. 30 — Illustration of shunt feedback in a transistor amplifier. Components C1 and R3 comprise the feedback network.

power resistor around which a suitable number of wire turns (no. 14 or 12 wire) have been wound. Additional parasitic suppression can be had by inserting a low-ohmage resistor (10 to 51 ohms) in series with the tube input, near the tube socket. This is illustrated by R1 of Fig. 28. Vhf or uhf parasitics can be detected by means of a high-frequency scope, or by probing the plate tank with a sensitive wavemeter which tunes from 30 MHz and higher.

Parasitic oscillations can be prevented in solid-state amplifiers by using a small amount of resistance in the base or collector lead of low-power amplifiers (Fig. 29A). The value of R1 or R2 is typically between 10 and 22 ohms. Resistors are seldom necessary at both points in a circuit, but can be used

effectively at either point. R1 or R2 should be located as close to the transistor as practical.

At power levels in excess of approximately 0.5 Watt, the method of parasitic suppression shown in Fig. 29B is suggested. The voltage drop across a resistor would be prohibitive at the higher power levels, so one or more ferrite beads can be substituted (Z1 and Z2). A permeability of 125 will suffice. The beads need not be used at both circuit locations. Generally, the lowest power port is best suited for the suppression devices discussed here. This means that the resistor or ferrite beads should be located at the base terminal of the transistor.

Because of the rising gain characteristic of bipolar transistors as the frequency is lowered, shunt and degenerative feedback

are often used to prevent instability. The net effect is that in the regions where low-frequency self-oscillations are most likely to occur, the feedback increases by nature of the feedback network. The heavier the feedback, the lower the amplifier gain. In the circuit of Fig. 30 C1 and R3 provide negative feedback which increases progressively as the frequency is lowered. The network has some effect at the desired operating frequency — a gain/stability tradeoff — but has a pronounced effect at the lower frequencies. The values for C1 and R3 are chosen experimentally in most instances, the precise values being dependent upon the operating frequency of the amplifier and the amount of feedback voltage available from the tap-off point. C1 will usually be between 220 pF and 0.0015  $\mu$ F for hf-band amplifiers. R3 may be a value from 51 to 5600 ohms. A rule of thumb that may prove helpful is to use a network that reduces the stage gain by approximately 1.5 dB at the lowest operating frequency.

R2 of Fig. 30 provides emitter degeneration at low frequencies when the bypass capacitor, C2, is chosen for adequate rf bypassing at the intended operating frequency. Below the desired frequency, C2 becomes progressively less effective as the frequency is lowered, thereby increasing the degenerative feedback caused by R2. This lowers the amplifier gain. R2 in a power stage is seldom greater than 10 ohms in value, and may be as low as 1 ohm. It is important to consider that under some operating and layout conditions R2 can cause instability. This form of feedback should be used only in those circuits where unconditional stability can be achieved.

Solid-state amplifiers that are built on pc boards can be made stable (in addition to the foregoing measures) by utilizing double-clad pc board material. The copper on the component side of the board is used as a ground-plane surface by removing the copper around each hole where a component is to be mounted. This ground plane is made electrically common to the ground elements on the etched side of the board. Such a technique helps prevent unwanted ac ground loops which can cause feedback and instability. Furthermore, the nonground etched elements form low-capacitance bypass capacitors against the ground-plane surface of the board. This aids in reducing the chance for vhf and uhf parasitic oscillations.

R1 of Fig. 30 is useful in swamping the input of an amplifier. This reduces the chance for low-frequency self-oscillations, but has a minor effect on the amplifier performance in the desired operating range. Values from 3 to 27 ohms are typical. When they are in shunt with the normal (low) base impedance of a power amplifier, they contribute only slightly to the lowering of the device input impedance. The rule of thumb is to use the

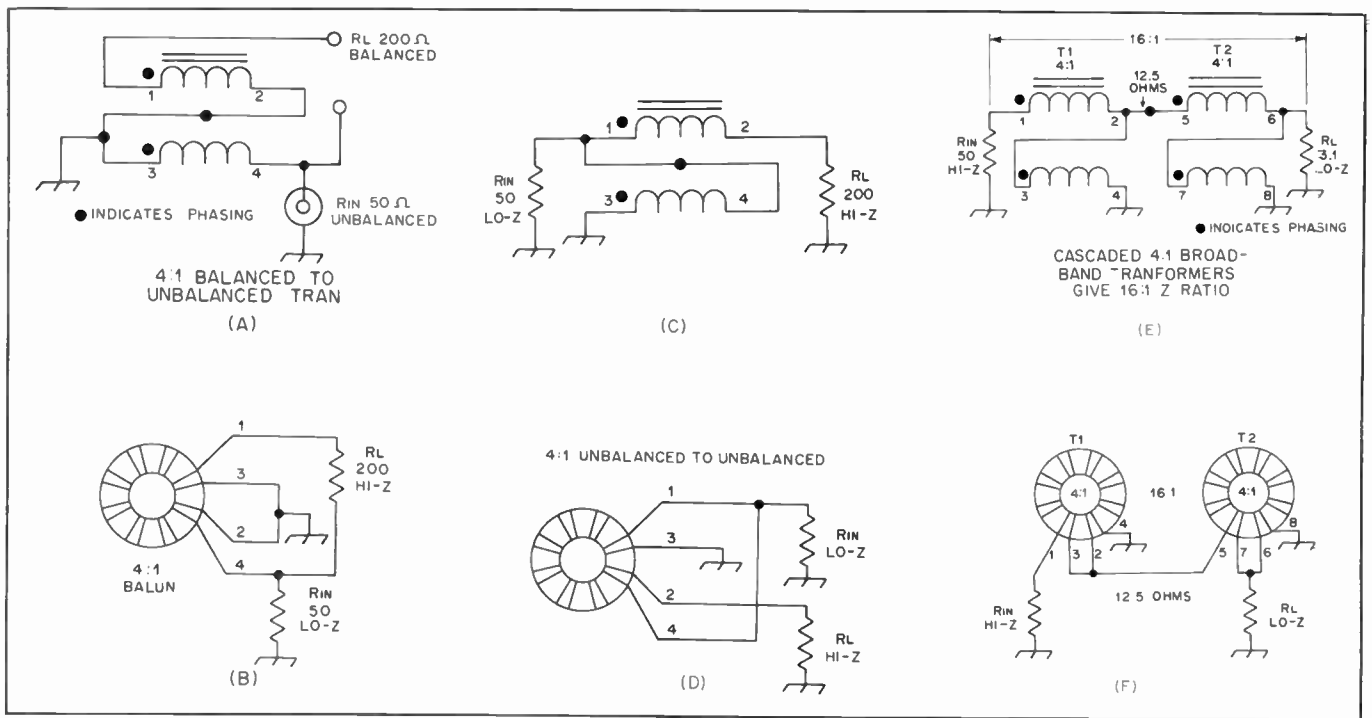


Fig. 31 — Circuit illustrations of 4:1 broadband transformers.

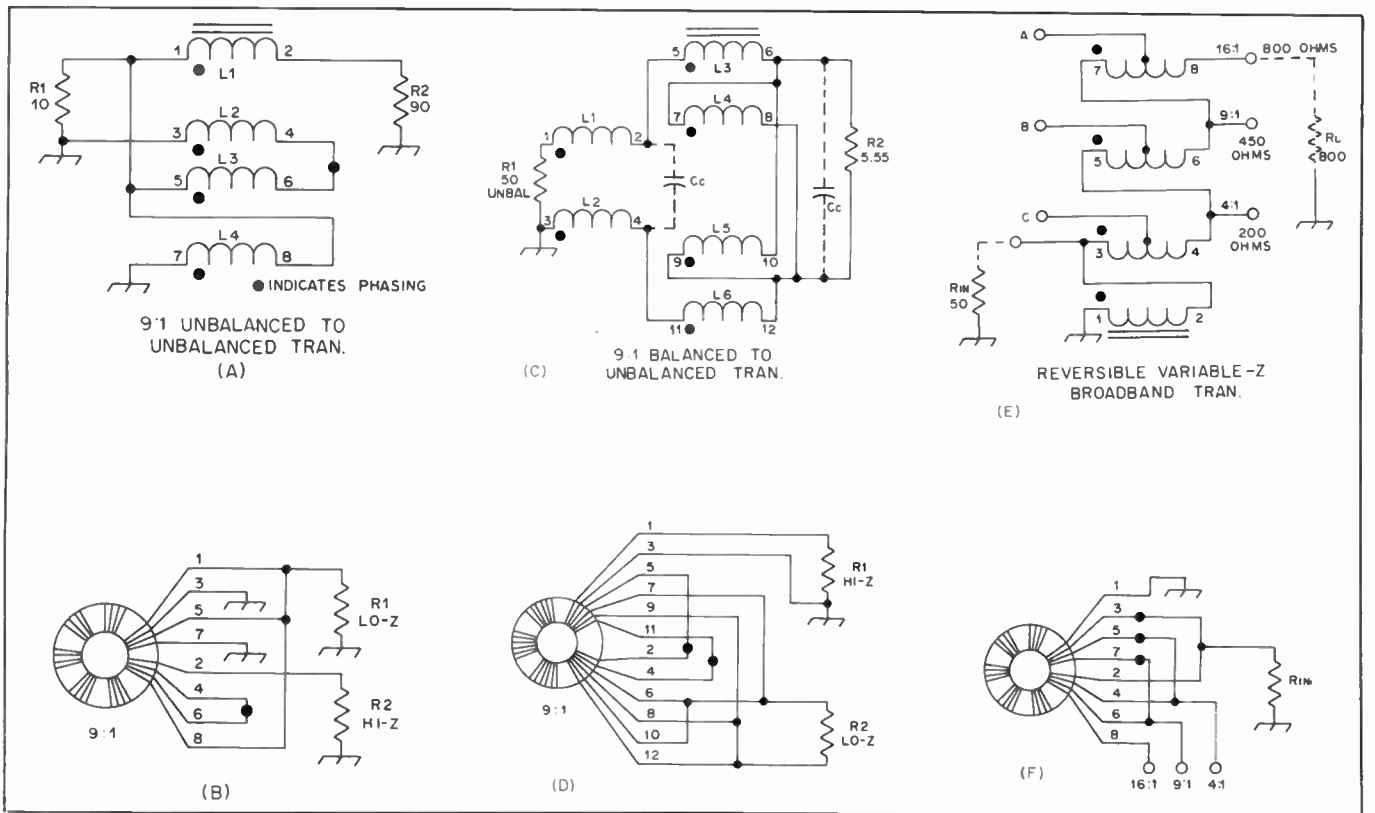


Fig. 32 — Circuit examples of 9:1 broadband transformers (A and C) and a variable-impedance transformer (E).

largest value of resistance that will ensure stability. R1 should be located as close to the transistor base terminal as possible. The pigtailed must be kept short to prevent stray inductances from forming. It is helpful to use two resistors in parallel to limit the amount of inductive reactance

introduced by a single resistor.

C3 of Fig. 30 can be added to some power amplifiers to damp vhf/uhf parasitic oscillations. The capacitor should be low in reactance at vhf and uhf, but must present a high reactance at the operating frequency. The exact value selected will

depend upon the collector impedance. A reasonable rule of thumb is to use an  $X_c$  of 10 times the collector impedance at the operating frequency. Silver-mica or ceramic-chip capacitors are suggested for this application. For example, a 3.5-MHz amplifier with a 10-ohm collector impedance

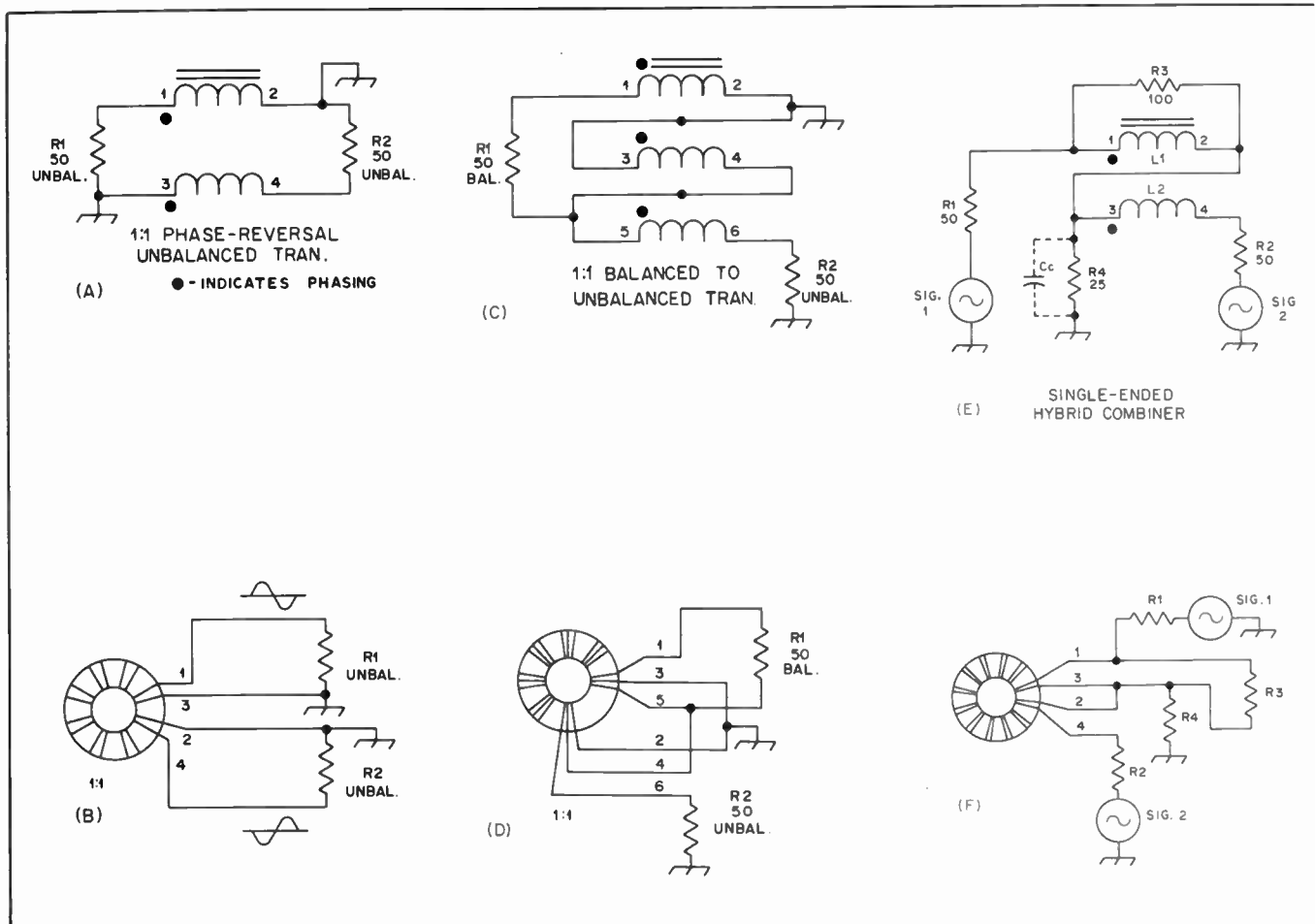


Fig. 33 — Assorted broadband transformers.

would use a capacitor with an  $X_c$  of 100 ohms.  $C_1$  would be 454 pF under this rule. At 150 MHz the same capacitor would have an  $X_c$  of only 2.3 ohms, making it an effective vhf and higher bypass element. An additional advantage is seen in the bypassing action for vhf and uhf harmonic energy in the collector circuit.  $C_3$  should be placed as close to the collector terminal as possible, using short leads. The effects of  $C_3$  in a broadband amplifier are relatively insignificant at the operating frequency. However, when a narrow-band collector network is employed, the added capacitance of  $C_3$  must be absorbed into the network design in the same manner as the  $C_{out}$  of the transistor.

### Broadband Transformers

The usefulness of toroidal broadband transformers is practically beyond description in this text. But, some of the more popular transformer configurations are presented here for those who wish to employ them in matching networks associated with solid-state devices and tubes. It is important to realize that broadband transformers are best suited to

low-impedance applications, say, up to a few hundred ohms. They should be thought of as devices which can transform one impedance to another, in terms of the transformation ratio they make possible. They should not be regarded as devices which are built for some specified pair of impedances, such as 200 ohms to 50 ohms in the case of a 4:1 transformer. The term "balun," despite its misuse, pertains only to a broadband transformer which converts a *balanced* condition to one which is *unbalanced*, or vice versa. The often-heard expressions "bal-oon" and "bal-um" are not correct.

The broadband transformers illustrated in Figs. 31, 32 and 33 are suitable for use in solid-state circuits, as matching devices between circuit modules and in antenna-matching networks. For low power levels the choice of core material is often ferrite. Powdered-iron is more often the designers preference when working with fairly high levels of power. The primary objection of some, respective to the use of ferrite at high power, is damage to the core material during saturation and overheating. This can alter the permeability factor of the

core material permanently. Powered-iron is more tolerant in this regard.

Fig. 31 shows two types of 4:1 transformers, plus a method for connecting two of them in series to effect a 16:1 transformation. The circuit at E is often used between a 50-ohm source and the base of an rf power transistor.

Two styles of 9:1 transformer are seen in Fig. 32 at A and C. They are also found at the input to transistor amplifiers and between the collector and the load. The variable-ratio transformer of Fig. 32 C is excellent for obtaining a host of impedance transformations. This transformer was developed by W2FMI for use in matching ground-mounted vertical antennas.

Phase-reversal, 1:1 balun and hybrid-combiner transformers are shown in Fig. 33. The circuit at E of Fig. 33 is useful when it is necessary to feed two signals to a single load. When the input signals are on different frequencies the power is split evenly between  $R_3$  and  $R_4$ . When the input voltages are on the same frequency (as with two transistor amplifiers feeding a single load), with the amplitudes and



phase identical, all of the power is delivered to R4.

### RF Power Amplifier Circuitry

In addition to proper tank and output-coupling circuits, an rf amplifier must be provided with suitable operating voltages and an rf driving or excitation voltage. All rf amplifier tubes require a voltage to operate the filament or heater (ac is usually permissible), and a positive dc voltage between the plate and filament or cathode (plate voltage). Most tubes also require a negative dc voltage (biasing voltage) between control grid (grid no. 1) and filament or cathode. Screen-grid tubes require in addition a positive voltage (screen voltage or grid no. 2 voltage) between screen and filament or cathode.

Biasing and plate voltages may be fed to the tube either in series or parallel with the associated rf tank circuit as discussed in the chapter on electrical laws and circuits.

It is important to remember that true plate, screen or biasing voltage is the voltage between the particular electrode and filament or cathode. Only when the cathode is directly grounded to the chassis may the electrode-to-chassis voltage be taken as the true voltage. The required rf driving voltage is applied between grid and cathode.

Plate power input is the dc power input to the plate circuit (dc plate voltage  $\times$  dc plate current). Screen power input likewise is the dc screen voltage  $\times$  the dc screen current.

Plate dissipation is the difference between the rf power delivered by the tube to its loaded plate tank circuit and the dc plate power input. The screen, on the other hand, does not deliver any output power, and therefore its dissipation is the same as the screen power input.

### Transmitting-Tube Ratings

Tube manufacturers specify the maximum values that should be applied to the tubes they produce. They also publish sets of typical operating values that should result in good efficiency and normal tube life.

The same transmitting tube may have different ratings, depending upon the manner in which the tube is to be operated and the service in which it is to be used. These different ratings are based primarily upon the heat that the tube can safely dissipate. Some types of operation, such as with grid or screen modulation, are less efficient than others, meaning that the tube must dissipate more heat. Other types of operation, such as cw or single-sideband phone are intermittent in nature, resulting in less average heating than in other modes where there is a continuous power input to the tube during transmissions. There are also different ratings for tubes used in transmitters that are in almost constant use (CCS — Continuous Commercial Service), and for

tubes that are to be used in transmitters that average only a few hours of daily operation (ICAS — Intermittent Commercial and Amateur Service). The latter are the ratings used by amateurs who wish to obtain maximum output with reasonable tube life.

### Maximum Tube Ratings

Maximum ratings, where they differ from the values given under typical operating values, are not normally of significance to the amateur except in special applications. No single maximum value should be used unless all other ratings can simultaneously be held within the maximum values. As an example, a tube may have a maximum plate-voltage rating of 2000, a maximum plate-current rating of 300 mA, and a maximum plate-power-input rating of 400 watts. Therefore, if the maximum plate voltage of 2000 is used, the plate current should be limited to 200 mA (instead of 300 mA) to stay within the maximum power-input rating of 400 watts.

### Maximum Transistor Ratings

Transistor data sheets specify a maximum operating voltage for several conditions. Of special interest to amateurs is the  $V_{ce0}$  specification (collector-to-emitter voltage, with the base open). When a transistor is called upon to handle an ac signal, the collector-to-emitter voltage can rise to twice the dc supply. Thus, if a 12-volt supply is used, the transistor should have a  $V_{ce0}$  of 24 or greater to prevent damage. If that same transistor is amplitude-modulated (as in the PA of an a-m transmitter), a collector-emitter voltage swing (theoretical) as great as four times the supply voltage can occur. A transistor chosen for this application should have a  $V_{ce0}$  of 48 or greater.

The  $f_T$  rating of a common-emitter transistor amplifier is based on the point at which the transistor gain is unity (1) with respect to operating frequency. In the interest of predictable performance and amplifier stability it is best to select a transistor that was designed for a particular frequency range. When this is not practical, the  $f_T$  should be roughly 5 to 10 times the operating frequency. Therefore, a suitable transistor for use at 3.5 MHz would have an  $f_T$  between 17.5 and 35 MHz. If a much higher  $f_T$  were selected, say, 250 MHz, the published rf performance curves for the device would be quite inaccurate at 3.5 MHz, and the transistor gain would be extremely high compared to the rated gain at the intended operating frequency of the device.

Power transistor gain is normally specified as "typical" dB. This information applies to some specified operating frequency and is by no means all-inclusive from, for example, medium frequency up to the vhf spectrum. The frequency at which a particular gain figure applies is stated on the transistor data sheet. Gene-

rally, the gain will be higher below that frequency and it will decrease above that frequency. Gain information is useful in predicting how much output power can be obtained for a given input power; i.e., a 13-dB gain transistor delivering an output of 10 watts would require a driving power of 0.5 W ( $\text{Gain}_{\text{dB}} = 10 \log [P_2/P_1]$ ).

Power dissipation for a transistor is expressed symbolically as  $P_D$ . This maximum rating is based on a case temperature of 25°C. For example, a total device dissipation of 30 watts might be specified at a case temperature of 25°C. If greater temperatures were expected, the transistor would have to be derated in mW per degree C. A Motorola MRF215 would be derated 177 mW per additional degree C. The effectiveness of the transistor heat sink plays an important role in maximum power utilization of a given device. It is not unusual to see a cooling fan used in combination with a large heat sink to aid in lowering the transistor case temperature: Heat is one of the worst enemies of power transistors.

A rule of thumb for selecting a  $P_D$  rating which is suitable for a given rf power output amount is to choose a transistor which has a maximum dissipation of twice the desired output power. Hence, a 20-watt transistor would be picked for use in a 10-watt-output amplifier. Some manufacturers push the power margin a bit harder, utilizing a transistor which delivers a power output which is as great as 3/4 the  $P_D$  rating. So close a safety margin is somewhat risky for inexperienced builders.

### Sources of Tube Electrode Voltages: Filament or Heater Voltage

The heater voltage for the indirectly heated cathode-type tubes found in low-power classifications may vary 10 percent above or below rating without seriously reducing the life of the tube. But the voltage of the higher-power, filament-type tubes should be held closely between the rated voltage as a minimum and five percent above rating as a maximum. Make sure that the plate power drawn from the power line does not cause a drop in filament voltage below the proper value when plate power is applied.

Thoriated-type filaments lose emission when the tube is overloaded appreciably. If the overload has not been too prolonged, emission sometimes may be restored by operating the filament at rated voltage with all other voltages removed for a period of 10 minutes, or at 20 percent above rated voltage for a few minutes.

### Plate Voltage

Dc plate voltage for the operation of rf amplifiers is most often obtained from a transformer-rectifier-filter system (see power-supply chapter) designed to deliver the required plate voltage at the required current. However, batteries or other dc-generating devices are sometimes used in

certain types of operation (see portable-mobile chapter).

### Bias and Tube Protection

Several methods of obtaining bias are shown in Fig. 34. At A, bias is obtained by the voltage drop across a resistor (R1) in the grid dc return circuit when rectified grid current flows. The proper value of resistance may be determined by dividing the required biasing voltage by the dc grid current at which the tube will be operated. Then, so long as the rf driving voltage is adjusted so that the dc grid current is the recommended value, the biasing voltage will be the proper value. The tube is biased only when excitation is applied, since the voltage drop across the resistor depends upon grid-current flow. When excitation is removed, the bias falls to zero. At zero bias most tubes draw power far in excess of the plate-dissipation rating. It is advisable to make provision for protecting the tube when excitation fails by accident, or by intent as it does when a preceding stage in a cw transmitter is keyed.

If the maximum cw ratings shown in the tube tables are to be used, the input should be cut to zero when the key is open. Aside from this, it is not necessary that plate current be cut off completely but only to the point where the rated dissipation is not exceeded. In this case plate-modulated phone ratings should be used for cw operation, however.

With most tubes this protection, plus the required operating bias, can be supplied by obtaining all bias from a source of fixed voltage, as shown in Fig. 34B.

Fixed bias may be obtained from dry batteries or from a power pack (see power-supply chapter). If dry batteries are used, they should be checked periodically, since even though they may show normal voltage, they eventually develop a high internal resistance.

In Fig. 34C and D, bias is obtained from the voltage drop across a Zener diode in the cathode (or filament center-tap) lead. Operating bias is obtained by the voltage drop across VR1 as a result of plate (and screen) current flow. The Zener-diode wattage rating is twice the product of the maximum cathode current times the developed bias. Therefore, a tube requiring 15 volts of bias during a maximum cathode-current flow of 100 mA would dissipate 1.5 W in the Zener diode. The diode rating, to allow a suitable safety factor, would be 3 W or greater. The circuit of Fig. 34D illustrates how D1 would be used with a cathode-driven (grounded-grid) amplifier as opposed to the grid-driven example at C.

### Transistor Biasing

Solid-state power amplifiers generally operate in Class C or Class AB. When some bias is desired during Class C

operation (Fig. 35A), a resistance of the appropriate value can be placed in the emitter return as shown. Most transistors will operate in Class C without adding bias externally, but in some instances the amplifier efficiency can be improved by means of emitter bias. Reverse bias supplied to the base of the Class C transistor should be avoided because it will lead to internal breakdown of the device during peak drive periods. The destruction is frequently a cumulative phenomenon, leading to gradual destruction of the transistor junction.

A simple method for Class AB biasing is seen in Fig. 35B. D1 is a silicon diode which acts as a bias clamp at approximately 0.7 V. The forward bias establishes linear-amplification conditions. That value of bias is not always optimum for a specified transistor in terms of IMD. Variable bias of the type illustrated in Fig. 35C permits the designer sufficient variance to locate the best operating point respective to linearity.

### Screen Voltage for Tubes

For cw and fm operation, and under certain conditions of phone operation (amplitude modulation) the screen may be operated from a power supply of the same type used for plate supply, except that voltage and current ratings should be appropriate for screen requirements. The screen may also be operated through a series resistor or voltage-divider from a source of higher voltage, such as the plate-voltage supply, thus making a separate supply for the screen unnecessary. Certain precautions are necessary, depending upon the method used.

It should be kept in mind that screen current varies widely with both excitation and loading. If the screen is operated from a fixed-voltage source, the tube should never be operated without plate voltage and load, otherwise the screen may be damaged within a short time. Supplying the screen through a series dropping resistor from a higher-voltage source, such as the plate supply, affords a measure of protection, since the resistor causes the screen voltage to drop as the current increases, thereby limiting the power drawn by the screen. However, with a resistor, the screen voltage may vary considerably with excitation, making it necessary to check the voltage at the screen terminal under actual operating conditions to make sure that the screen voltage is normal. Reducing excitation will cause the screen current to drop, increasing the voltage; increasing excitation will have the opposite effect. These changes are in addition to those caused by changes in bias and plate loading, so if a screen-grid tube is operated from a series resistor or a voltage divider, its voltage should be checked as one of the final adjustments after excitation and loading have been set.

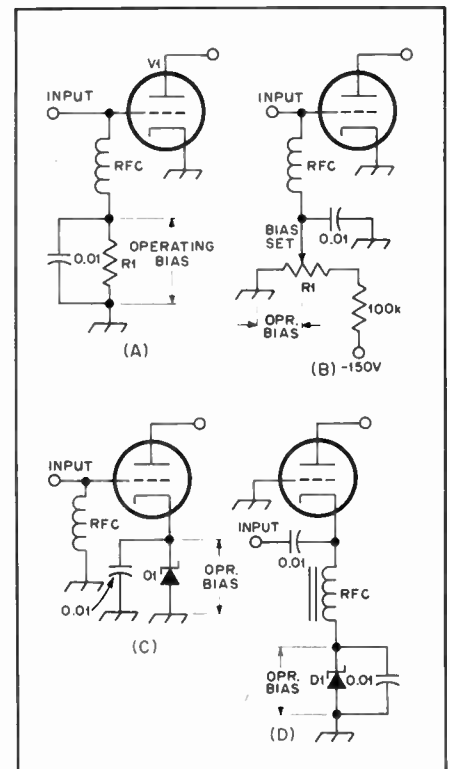


Fig. 34 — Various techniques for providing operating bias with tube amplifiers.

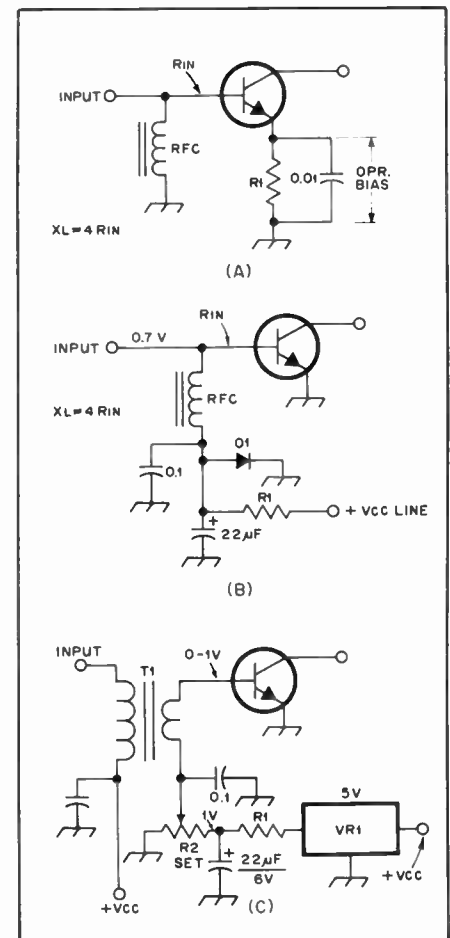


Fig. 35 — Biasing methods for use with transistor amplifiers.

An approximate value for the screen-voltage dropping resistor may be obtained by dividing the voltage drop required from the supply voltage (difference between the supply voltage and rated screen voltage) by the rated screen current in decimal parts of an ampere. Some further adjustment may be necessary, as mentioned above, so an adjustable resistor with a total resistance above that calculated should be provided.

### Protecting Screen-Grid Tubes

Considerably less grid bias is required to cut off an amplifier that has a fixed-voltage screen supply than one that derives the screen voltage through a high value of dropping resistor. When a "stiff" screen voltage supply is used, the necessary grid cutoff voltage may be determined from an inspection of the tube curves or by experiment.

### Feeding Excitation to the Grid

The required rf driving voltage is supplied by an oscillator generating a voltage at the desired frequency, either directly or through intermediate amplifiers, mixers, or frequency multipliers.

As explained in the chapter on vacuum-tube fundamentals, the grid of an amplifier operating under Class C conditions must have an exciting voltage whose peak value exceeds the negative biasing voltage over a portion of the excitation cycle. During this portion of the cycle, current will flow in the grid-cathode circuit as it does in a diode circuit when the plate of the diode is

positive in respect to the cathode. This requires that the rf driver supply power. The power required to develop the required peak driving voltage across the grid-cathode impedance of the amplifier is the rf driving power.

The tube tables give approximate figures for the grid driving power required for each tube under various operating conditions. These figures, however, do not include circuit losses. In general, the driver stage for any Class C amplifier should be capable of supplying at least three times the driving power shown for typical operating conditions at frequencies up to 30 MHz and from three to 10 times at higher frequencies.

Since the dc grid current relative to the biasing voltage is related to the peak driving voltage, the dc grid current is commonly used as a convenient indicator of driving conditions. A driver adjustment that results in rated dc grid current when the dc bias is at its rated value, indicates proper excitation to the amplifier when it is fully loaded.

In coupling the grid input circuit of an amplifier to the output circuit of a driving stage the objective is to load the driver plate circuit so that the desired amplifier grid excitation is obtained without exceeding the plate-input ratings of the driver tube.

### Driving Impedance

The grid-current flow that results when the grid is driven positive in respect to the cathode over a portion of the excitation

cycle represents an average resistance across which the exciting voltage must be developed by the driver. In other words, this is the load resistance into which the driver plate circuit must be coupled. The approximate grid input resistance is given by

$$\text{Input impedance (ohms)} = \frac{\text{driving power (watts)}}{\text{dc grid current (mA)}^2} \times 620,000$$

For normal operation, the driving power and grid current may be taken from the tube tables. Since the grid input resistance is a matter of a few thousand ohms, an impedance step-up is necessary if the grid is to be fed from a low-impedance transmission line.

### Cooling: Tubes

Vacuum tubes must be operated within the temperature range specified by the manufacturer if long tube life is to be achieved. Tubes with glass envelopes rated at up to 25 watts of plate dissipation may be run without forced-air cooling. If a moderate amount of cooling by convection can be arranged. If a perforated-metal enclosure is used, and a ring of 1/4-inch diameter holes are placed around the tube socket, normal air flow can be relied upon to remove excess heat at room temperatures.

For tubes with greater plate dissipation, or those operated with plate currents in excess of the manufacturer's ratings (often the case with TV sweep tubes) forced air cooling with a fan or blower is needed. Fans, especially those designed for cooling hi-fi cabinets, are preferred because they operate quietly. However, all fans lose their ability to move air when excessive back pressure exists. For applications where a stream of air must be directed through a tube socket, a blower is usually required. Blowers vary in their ability to work against back pressure, so this specification should be checked when selecting a particular model. Some air will always leak around the socket and through other holes in a chassis, so the blower chosen should have a capacity which is 30 to 50 percent beyond that called for by the tube manufacturer.

An efficient blower is required when using the external-anode tubes, such as the 4X150A. Such tubes represent a trade-off which allows high-power operation with a physically small device at the expense of increased complexity in the cooling system. Other types of external-anode tubes are now being produced for conductive cooling. Electrical insulators which are also excellent thermal conductors, such as AlSiMg (aluminum-silicon-magnesium compound) and Be (beryllium), couple the tube to a heat sink. Requirements for the heat dissipator are calculated in the same way as for power transistors, as outlined below. Similar



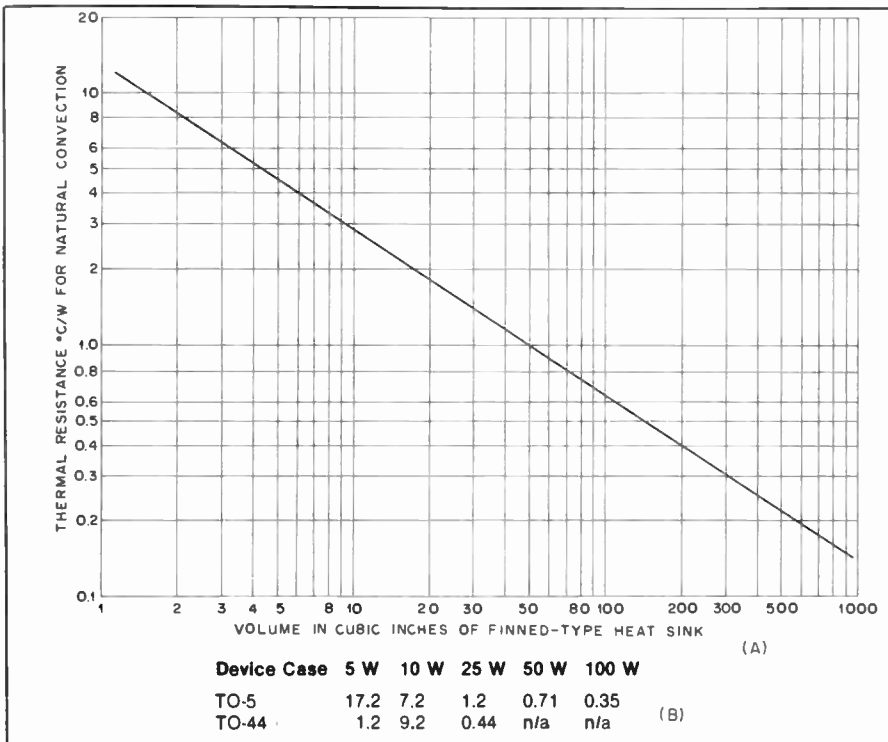


Fig. 36 — Heat-sink thermal resistance versus size. The sink volume can be determined by multiplying the height and cross-sectional area. At B are numbers which show the approximate thermal resistance needed for operating at various power levels with adequate cooling. TO-5 and TO-44 case styles are listed.

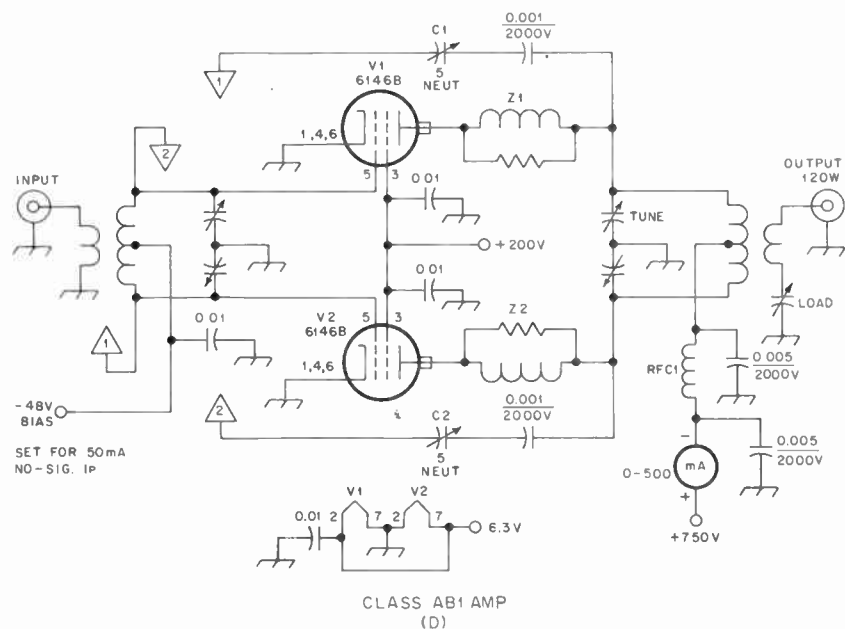

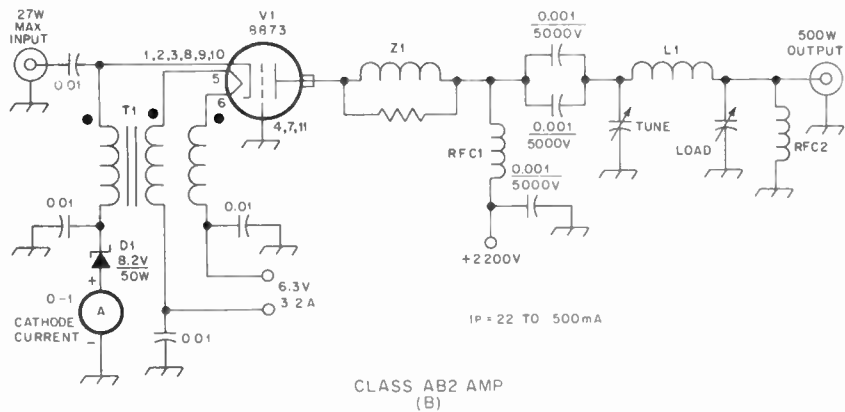





United States, a plate-modulated output stage can deliver a carrier output of 650 to 750 watts, while a screen- or control-grid-modulated output amplifier can deliver only a carrier of 300 to 350 watts.

### SSB

Only linear amplifiers can be used to amplify ssb signals without prohibitive distortion, and this limits the choice of output amplifier operation to Classes A, AB<sub>1</sub>, AB<sub>2</sub> and B. The efficiency of operation of these amplifiers runs from about 20 to 65 percent. In all but Class A operation the indicated (by plate-current meter) input will vary with the signal, and it is not possible to talk about relative inputs and outputs as readily as it is with other modes. Therefore linear amplifiers are rated by PEP (input or output) at a given distortion level, which indicates not only how much ssb signal they will deliver but also how effective they will be in

amplifying an a-m signal.

### Linear Amplifiers for A-M

In considering the practicality of adding a linear output amplifier to an existing a-m transmitter, it is necessary to know the carrier output of the a-m transmitter and the PEP output rating of the linear amplifier. Since the PEP output of an a-m signal is four times the carrier output, it is obvious that a linear with a PEP output rating of only four times the carrier output of the a-m transmitter is no amplifier at all. If the linear amplifier has a PEP output rating of eight times the a-m transmitter carrier output, the output power will be doubled and a 3-dB improvement will be obtained. In most cases a 3-dB change is just discernible by the receiving operator.

By comparison, a linear amplifier with a PEP output rating of four times an existing ssb, cw or fm transmitter will

quadruple the output, a 6-dB improvement, it should be noted that the linear amplifier must be rated for the mode (ssb, cw or fm) with which it is to be used.

### Grounded-Grid Amplifiers

The preceding discussion applies to vacuum-tube amplifiers connected in a grounded-cathode or grounded-grid circuit. However, there are a few points that apply only to grounded-grid amplifiers.

A tube operated in a given class (AB<sub>1</sub>, B, C) will require more driving power as a grounded-grid amplifier than as a grounded-cathode amplifier. This is not because the grid losses run higher in the grounded-grid configuration but because some of the driving power is coupled directly through the tube and appears in the plate load circuit. Provided enough driving power is available, this increased requirement is of no concern in cw or linear operation. In a-m operation, however, the fed-through power prevents the grounded-grid amplifier from being fully modulated (100 percent).

### Amplifier Circuits: Parallel and Push-Pull Amplifiers

The circuits for parallel-tube amplifiers are the same as for a single tube, similar terminals of tubes being connected together. The grid impedance of two tubes in parallel is half that of a single tube. This means that twice the grid tank capacitance should be used for the same Q.

The plate load resistance is halved so that the plate-tank capacitance for a single tube also should be doubled. The total grid current will be doubled, so to maintain the same grid bias, the grid-leak resistance should be half that used for a single tube. The required driving power is doubled. The capacitance of a neutralizing capacitor should be doubled and the value of the screen dropping resistor should be cut in half.

In treating parasitic oscillation, it is often necessary to use a choke in each plate lead, rather than one in the common lead. This avoids building in a push-pull type of vhf resonance, which may cause inefficient operation at higher frequencies. See Fig. 37C and D.

Two or more transistors are often operated in parallel to achieve high output power, because several medium-power devices often cost less than a single high-power type. When parallel operation is used, precautions must be taken to insure that equal drive is applied to each transistor. Otherwise, one transistor may "hog" most of the drive and exceed its safe ratings.

In practice, it is not wise or necessary to use transistors in parallel. A push-pull circuit, such as that of Fig. 41 is preferable and it tends to cancel even harmonics — a benefit. Alternatively, single-ended amplifiers can be joined to deliver power to a single load by means of hybrid combiners.

This technique was illustrated by Granberg in April and May 1976 *QST*. He used combiners to parallel the outputs of four 300-watt, push-pull, solid-state amplifiers. Fig. 33E shows the circuit of a hybrid-combiner transformer.

A typical single-ended tube amplifier which employs a 6146B in Class C is shown in Fig. 37A. Neutralization is provided by means of C1. L1 has a tap near the ac-ground end to provide a small amount of feedback voltage of the correct phase for neutralization. Meters are placed in the appropriate circuit points for monitoring the important voltage and currents.

Fig. 37B shows the circuit of a single-ended amplifier which operates Class AB2 in grounded-grid fashion. T1 is a broadband, trifilar transformer which keeps the cathode and filaments above ac ground to provide a method for driving the cathode of V1. Operating bias is developed by inserting D1 in the cathode return. Z1 is a vhf parasitic suppressor. RFC2 functions as a safety device in the event the plate blocking capacitors short and dc flows into the load (antenna or Transmatch). The rf choke permits high dc current to flow to ground, blowing the power supply fuses and destroying the choke. It should have an XL which is at least 10 times the load resistance.

TV sweep tubes used in parallel are seen at Fig. 37C. Each plate lead contains a parasitic choke (Z1 and Z2). D1 is chosen to provide the necessary idling current for the class of operation desired. The unique feature of this circuit is that the control grids of V1 and V2 are tied together and driven across a 50-ohm resistor. This method eliminates the need for a tuned circuit or matching transformer at the amplifier input. Additionally, by strapping the grids to a low impedance (50 ohms), amplifier stability can be realized without the need for neutralization. The 100-ohm resistors in the screen-grid leads are used to discourage vhf oscillations and to help equalize the screen currents of the tubes. Several sweep tubes can be parallel-connected as shown to obtain a 1-kW-dc input linear amplifier. Attention must be paid to selecting a set of tubes with nearly matched dynamic characteristics. If this is not done, one or more of the tubes may draw the major part of the current during the driven period. This would cause them to operate in excess of their safe plate-dissipation ratings and be destroyed.

An example of a push-pull amplifier is offered in Fig. 37D. Two 6146Bs are used in a Class AB1 format. C1 and C2 are the neutralizing capacitors. Join points A-A and B-B to complete the circuit. C1 and C2 are shown in series with 0.001- $\mu$ F blocking capacitors. The latter need not be used if access to the neutralizing capacitors can be had without shock hazard. The circuit concepts shown in Fig. 37 are applicable to all types of transmit-

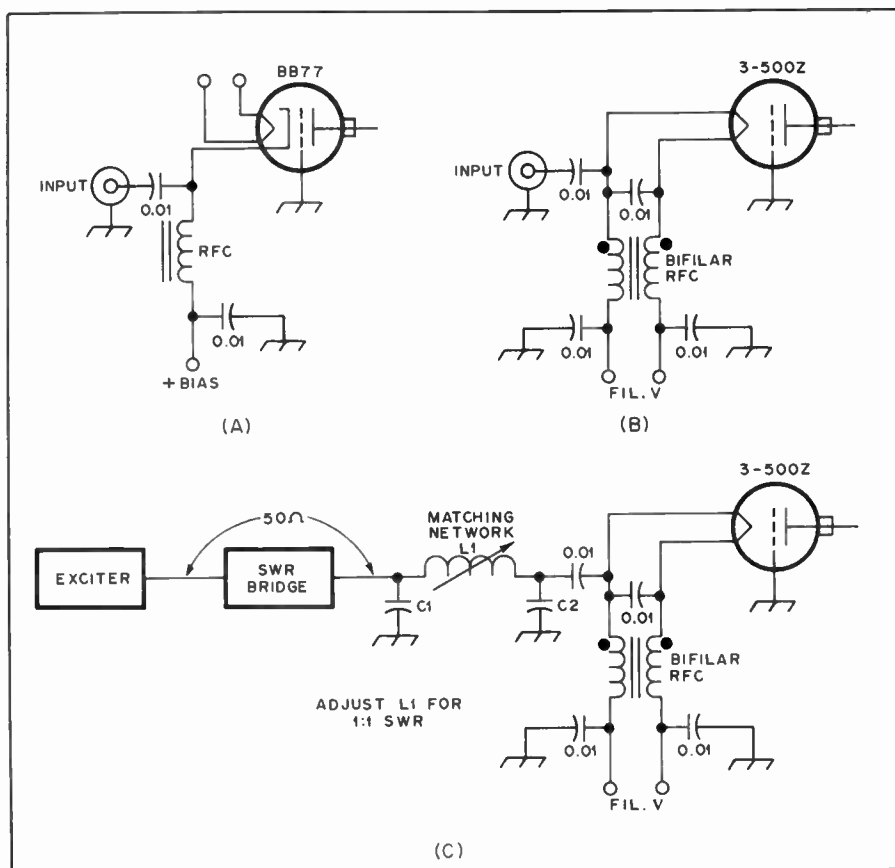


Fig. 38 — Methods for driving grounded-grid amplifiers.

ting tubes and power levels. Specific types of tubes are shown merely to provide practical examples during this treatment.

### Grounded-Grid Amplifiers

Fig. 38A shows the input circuit of a grounded-grid triode amplifier. In configuration it is similar to the conventional grounded-cathode circuit except that the grid, instead of the cathode, is at ground potential. An amplifier of this type is characterized by a comparatively low input impedance and a relatively high driver power requirement. The additional driver power is not consumed in the amplifier but is "fed through" to the plate circuit where it combines with the normal plate output power. The total rf power output is the sum of the driver and amplifier output powers less the power normally required to drive the tube in a grounded-cathode circuit.

Positive feedback is from plate to cathode through the plate-cathode capacitance of the tube. Since the grounded-grid is interposed between the plate and cathode, this capacitance is small, and neutralization usually is not necessary.

In the grounded-grid circuit the cathode must be isolated for rf from ground. This presents a practical difficulty especially in the case of a filament-type tube whose filament current is large. In plate-modulated phone operation the driver power fed through to the output is not

modulated.

The chief application for grounded-grid amplifiers in amateur work below 30 MHz is in the case where the available driving power far exceeds the power that can be used in driving a conventional grounded-cathode amplifier.

Screen-grid tubes are also used sometimes in grounded-grid amplifiers. In some cases, the screen is simply connected in parallel with the grid and the tube operates as a high- $\mu$  triode. In other cases, the screen is bypassed to ground and operated at the usual dc potential. Since the screen is still in parallel with the grid for rf, operation is very much like that of a triode except that the positive voltage on the screen reduces driver-power requirements.

In indirectly-heated cathode tubes, the low heater-to-cathode capacitance will often provide enough isolation to keep rf out of the heater transformer and the ac lines. If not, the heater voltage must be applied through rf chokes.

In a directly-heated cathode tube, the filament must be maintained above rf ground. This can be done by using a bifilar-wound filament choke (Fig. 38B and C). With this method, a double solenoid (often wound on a ferrite core) is generally used, although separate chokes can be used, or a toroid core of large cross-sectional area can be used. A typical filament choke is shown in Fig. 39.

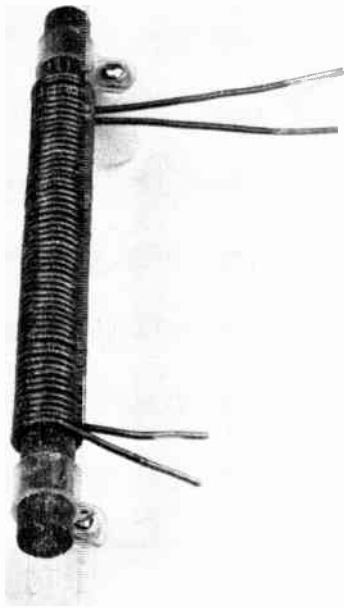


Fig. 39 — A 30-A filament choke for use with grounded-grid amplifiers. It contains 28 turns of no. 10 enameled wire, closewound in bifilar fashion on a 7-inch (178-mm) by 1/2-inch (13-mm) ferrite rod. The core permeability can be 950 or 125.

The input impedance of a grounded-grid power stage is usually between 30 and 150 ohms. A high-C, low-Q pi-section network can be used to obtain an SWR of 1:1 between the exciter and the amplifier. This is shown in Fig. 38C. The input network provides benefit other than impedance matching — a reduction in the IM distortion produced by the stage when amplifying an ssb signal.

### Transistor Amplifiers

Fig. 40 contains the circuit of a typical single-ended transistor amplifier. It is shown for Class C operation. T1 is a conventional toroidal broadband transformer which matches the 50-ohm driver load to the 5-ohm base of Q1. The primary of T1 requires sufficient reactance to look like four times the 50-ohm source impedance. A 7- $\mu$ H winding satisfies the need at 7 MHz. The collector circuit employs a T network to transform the 5.6-ohm collector to a 50-ohm load. The collector rf choke is followed by a second one, which with the associated bypass capacitors decouples the amplifier from the 13.5-volt power supply.

A push-pull, broadband, solid-state amplifier circuit is seen in Fig. 41. As shown, it is biased for Class C operation. However, if linear amplification was desired, the center tap of T1 could be lifted from ground and forward bias applied at that point. If that were done, the 10-ohm, base-swamping resistors would

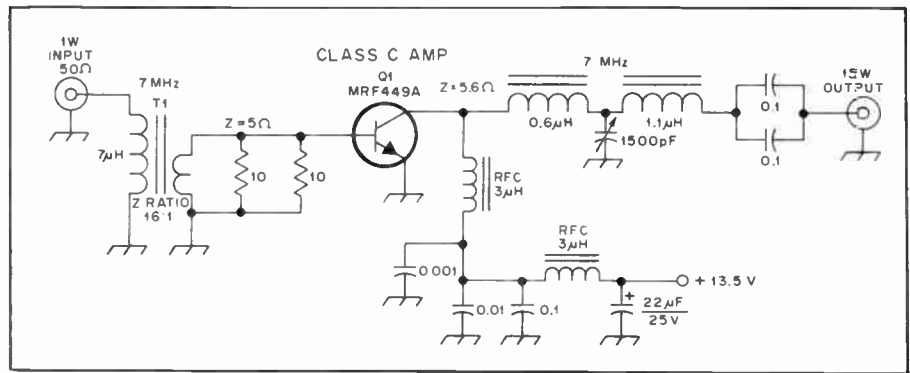


Fig. 40 — Typical circuit for a single-ended, Class C transistor power amplifier.

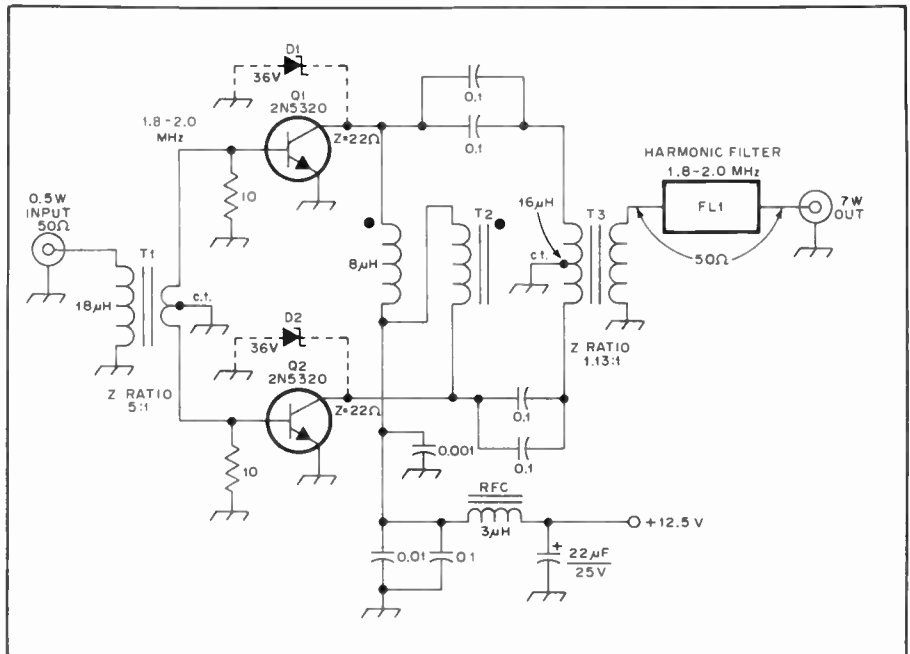


Fig. 41 — Circuit example of a broadband, push-pull, solid-state power amplifier.

be returned to the transformer center tap instead of being grounded as shown.

T2 of Fig. 41 is a phase-reversal choke which places the collectors of Q1 and Q2 in the correct phase (180 degrees apart). T3 is a conventional transformer which matches the 44-ohm collector-to-collector impedance to a 50-ohm harmonic filter, FL1. The collector coupling capacitors are pairs of 0.1- $\mu$ F capacitors in parallel. This method will pass more current with less capacitor heating than would be the case if only one capacitor were used at each point in the circuit. Ceramic chip capacitors are recommended. D1 and D2 may be added as protection against dc voltage spikes on the 13.5-V line. Also, if the amplifier should break into self-oscillation, the Zener diodes will limit the collector swing and prevent damage to the transistors. The diodes are helpful also when the amplifier is not terminated in a proper load. ARRL lab tests show that Zener diodes used in the manner indicated have no significant effect on amplifier

performance, and they do not enhance the generation of harmonic currents. The reason is that the diodes are not conducting under normal conditions. They have been proven effective as high as 30 MHz, and may function satisfactorily into the vhf region. Matching networks and their solutions can be found earlier in this chapter.

### RF Power-Amplifier Tanks and Coupling for Tubes

#### Tank Q

Rf power-amplifiers used in amateur transmitters are operated under Class C or AB conditions (see chapter on tube fundamentals). The main objective, of course, is to deliver as much fundamental power as possible into a load, R, without exceeding the tube ratings. The load resistance, R, may be in the form of a transmission line to an antenna, or the input circuit of another amplifier. A further objective is to minimize the



harmonic energy (always generated by an amplifier) fed into the load circuit. In attaining these objectives, the Q of the tank circuit is of importance. When a load is coupled inductively, the Q of the tank circuit will have an effect on the coefficient of coupling necessary for proper loading of the amplifier. In respect to all of these factors, a tank Q of 10 to 20 is usually considered optimum. A much lower Q will result in less efficient operation of the amplifier tube, greater harmonic output, and greater difficulty in coupling inductively to a load. A much higher Q will result in higher tank current with increased loss in the tank coil. Efficiency of a tank circuit is determined by the ratio of loaded Q to unloaded Q by the relationship:

$$\text{Eff.} = 100 \left( 1 - \frac{Q_L}{Q_U} \right)$$

where  $Q_L$  is the loaded Q and  $Q_U$  is the unloaded Q.

The Q is determined (see chapter on electrical laws and circuits) by the L/C ratio and the load resistance at which the tube is operated. The tube load resistance is related, in approximation, to the ratio of the dc plate voltage to dc plate current at which the tube is operated and can be computed from

Class-A Tube:

$$R_L = \frac{\text{Plate Volts}}{1.3 \times \text{Plate Current}}$$

Class-B Tube:

$$R_L = \frac{\text{Plate Volts}}{1.57 \times \text{Plate Current}}$$

Class-C Tube:

$$R_L = \frac{\text{Plate Volts}}{2 \times \text{Plate Current}}$$

Transistor:

$$R_L = \frac{(\text{Collector Volts})^2}{2 \times \text{Power Output (Watts)}}$$

### Parallel-Resonant Tank

The amount of C that will give a Q of 10 for various ratios is shown in Fig. 42. For a given plate-voltage/plate-current ratio, the Q will vary directly as the tank capacitance, twice the capacitance doubles the Q, and so on. For the same Q, the capacitance of each section of a split-stator capacitor in a balanced circuit should be half the value shown.

These values of capacitance include the output capacitance of the amplifier tube, the input capacitance of a following amplifier tube if it is coupled capacitively, and all other stray capacitances. At the higher plate-voltage/plate-current ratios, the chart may show values of capacitance,

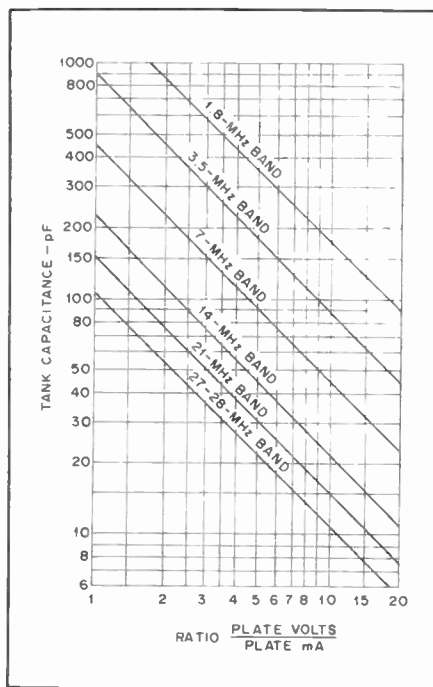


Fig. 42 — Chart showing plate tank capacitance required for a Q of 10. Divide the tube plate voltage by the plate current in milliamperes. Select the vertical line corresponding to the answer obtained. Follow this vertical line to the diagonal line for the band in question, and thence horizontally to the left to read the capacitance. For a given ratio of plate voltage/plate current, doubling the capacitance shown doubles the Q. When a split-stator capacitor is used in a balanced circuit, the capacitance of each section may be one half the value given by the chart.

for the higher frequencies, smaller than those attainable in practice. In such a case, a tank Q higher than 10 is unavoidable.

### Inductive-Link Coupling: Coupling to Flat Coaxial Lines

When the load R in Fig. 43 is located for convenience at some distance from the amplifier, or when maximum harmonic reduction is desired, it is advisable to feed the power to the load through a low-impedance coaxial cable. The shielded construction of the cable prevents radiation and makes it possible to install the line in any convenient manner without danger of unwanted coupling to other circuits.

If the line is more than a small fraction of a wavelength long, the load resistance at its output end should be adjusted, by a matching circuit if necessary, to match the impedance of the cable. This reduces losses in the cable and makes the coupling adjustments at the transmitter independent of the cable length.

Assuming that the cable is properly terminated, proper loading of the amplifier will be assured, using the circuit of Fig. 44A, if

1) The plate tank circuit has reasonably higher value of Q. A value of 10 is usually sufficient.

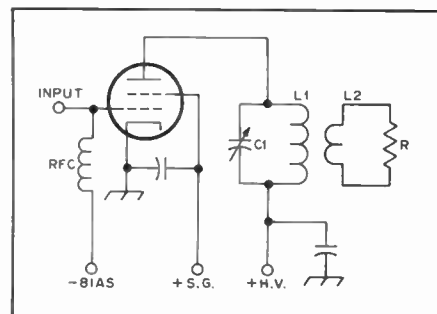


Fig. 43 — Inductive-link output coupling circuits. C1 — Plate tank capacitor — see text and Fig. 42 for capacitance.

L1 — To resonate at operating frequency with C1. See LC chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

L2 — Reactance equal to line impedance. See reactance chart and inductance formula in electrical-laws chapter, or use ARRL Lightning Calculator.

R — Representing load.

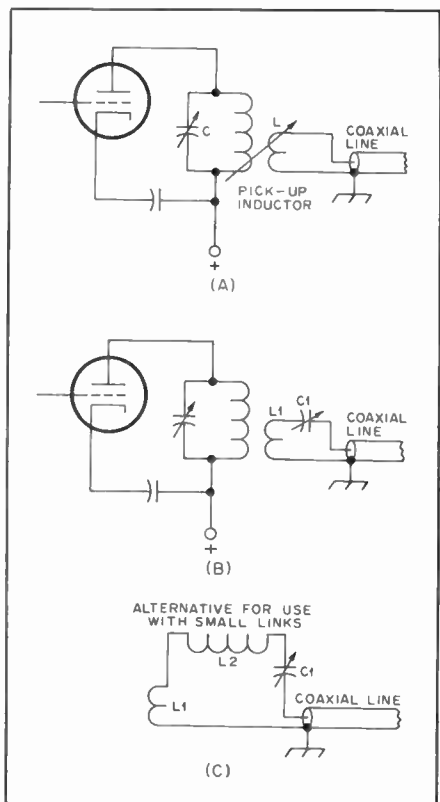


Fig. 44 — With flat transmission lines, power transfer is obtained with looser coupling if the line input is tuned to resonance. C1 and L1 should resonate at the operating frequency. See table for maximum usable value of C1. If the circuit does not resonate with maximum C1 or less, inductance of L1 must be increased or added in series at L2.

2) The inductance of the pickup or link coil is close to the optimum value for the frequency and type of line used. The optimum coil is one whose self-inductance is such that its reactance at the operating frequency is equal to the characteristic impedance,  $Z_0$ , of the line.



**Table 2**

**Capacitance in pF Required for Coupling to Flat Coaxial Lines with Tuned Coupling Circuit<sup>1</sup>**

Frequency Band (MHz)	Characteristic Impedance of Line (ohms)	
	52	75
3.5	450	300
7	230	150
14	115	75
21	80	50
28	60	40

<sup>1</sup>Capacitance values are maximum usable.

Note: Inductance in circuit must be adjusted to resonate at operating frequency.

3) It is possible to make the coupling between the tank and pickup coils very tight.

The second in this list is often hard to meet. Few manufactured link coils have adequate inductance even for coupling to a 50-ohm line at low frequencies.

If the line is operating with a low SWR, the system shown in Fig. 44A will require tight coupling between the two coils. Since the secondary (pickup coil) circuit is not resonant, the leakage reactance of the pickup coil will cause some detuning of the amplifier tank circuit. This detuning effect increases with increased coupling, but is usually not serious. However, the amplifier tuning must be adjusted to resonance, as indicated by the plate-current dip, each time the coupling is changed.

**Tuned Coupling**

The design difficulties of using "untuned" pickup coils, mentioned above, can be avoided by using a coupling circuit tuned to the operating frequency. This contributes additional selectivity as well, and hence aids in the suppression of spurious radiations.

If the line is flat the input impedance will be essentially resistive and equal to the  $Z_0$  of the line. With coaxial cable, a circuit of reasonable Q can be obtained with practicable values of inductance and capacitance connected in series with the line's input terminals. Suitable circuits are given in Fig. 44 at B and C. The Q of the coupling circuit often may be as low as 2, without running into difficulty in getting adequate coupling to a tank circuit of proper design. Larger values of Q can be used and will result in increased ease of coupling, but as the Q is increased the frequency range over which the circuit will operate without readjustment becomes smaller. It is usually good practice, therefore, to use a coupling-circuit Q just low enough to permit operation, over as much of a band as is normally used for a particular type of communication, without requiring retuning.

Capacitance values for a Q of 2 and line impedances of 52 and 75 ohms are given in the accompanying table. These are the

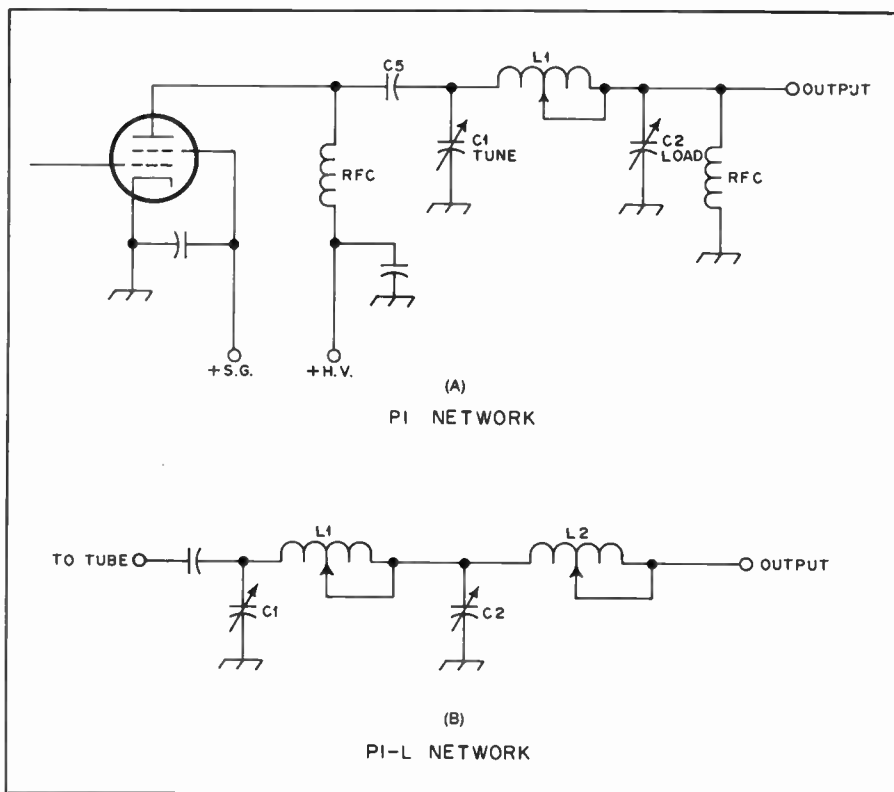


Fig. 45 — Examples of pi (A) and pi-L (B) networks.

maximum values that should be used. The inductance in the circuit should be adjusted to give resonance at the operating frequency. If the link coil used for a particular band does not have enough inductance to resonate, the additional inductance may be connected in series as shown in Fig. 44C.

**Characteristics**

In practice, the amount of inductance in the circuit should be chosen so that, with somewhat loose coupling between L1 and the amplifier tank coil, the amplifier plate current will increase when the variable capacitor, C1, is tuned through the value of capacitance given by the table. The coupling between the two coils should then be increased until the amplifier loads normally, without changing the setting of C1. If the transmission line is flat over the entire frequency band under consideration, it should not be necessary to readjust C1 when changing frequency, if the values given in the table are used. However, it is unlikely that the line actually will be flat over such a range, so some readjustment of C1 may be needed to compensate for changes in the input impedance of the line. If the input impedance variations are not large, C1 may be used as a loading control, no changes in the coupling between L1 and the tank coil being necessary.

The degree of coupling between L1 and the amplifier tank coil will depend on the coupling circuit Q. With a Q of 2, the coupling should be tight — comparable with the coupling that is typical of

"fixed-link" manufactured coils. With a swinging link it may be necessary to increase the Q of the coupling circuit in order to get sufficient power transfer. This can be done by increasing the L/C ratio.

**Pi and Pi-L Output Tanks**

A pi-section and pi-L tank circuit may also be used in coupling to an antenna or transmission line, as shown in Fig 45. The optimum values of capacitance and inductance are dependent upon values of amplifier power input and output load resistance.

Values for L and C may be taken directly from the charts of Figs. 46 and 47 if the output load resistance is the usual 52 ohms. It should be borne in mind that these values apply only where the output load is resistive, i.e., where the antenna and line have been matched.

**Output-Capacitor Ratings**

The voltage rating of the output capacitor will depend upon the SWR. If the load is resistive, receiving-type air capacitors should be adequate for amplifier input powers up to 2-kW PEP when feeding 52-75-ohm loads. In obtaining the larger capacitances required for the lower frequencies, it is common practice to switch one or more fixed capacitors in parallel with the variable air capacitor. While the voltage rating of a mica or ceramic capacitor may not be exceeded in a particular case, capacitors of these types are limited in current-carrying capacity. Postage-stamp silver-mica capacitors should

be adequate for amplifier inputs over the range from about 70 watts at 28 MHz to 400 watts at 14 MHz and lower. The larger mica capacitors (CM-45 case) having voltage ratings of 1200 and 2500 volts are usually satisfactory for inputs varying from about 350 watts at 28 MHz to 1 kW at 14 MHz and lower. Because of these current limitations, particularly at the higher frequencies, it is advisable to use as large an air capacitor as practicable, using the micas only at the lower frequencies. Broadcast-receiver replacement-type capacitors can be obtained reasonably. Their voltage insulation should be adequate for inputs of 1000 watts or more.

### More About Stabilizing Amplifiers

A straight amplifier operates with its input and output circuits tuned to the same frequency. Therefore, unless the coupling between these two circuits is brought to the necessary minimum, the amplifier will oscillate as a tuned-plate, tuned-grid circuit. Care should be used in arranging components and wiring of the two circuits so that there will be negligible opportunity for coupling external to the tube or transistor itself. Complete shielding between input and output circuits usually is required. All rf leads should be kept as short as possible, and particular attention should be paid to the rf return paths from input and output tank circuits to emitter or cathode. In general, the best arrangement using a tube is one in which the cathode connection to ground, and the plate tank circuit are on the same side of the chassis or other shielding. The "hot" lead from the input tank (or driver plate tank) should be brought to the socket through a hole in the shielding. Then when the grid tank capacitor or bypass is grounded, a return path through the hole to cathode will be encouraged, since transmission-line characteristics are simulated.

### Screen-Grid Tube Neutralizing Circuits

The plate-grid capacitance of screen-grid tubes is reduced to a fraction of a picofarad by the interposed grounded screen. Nevertheless, the power sensitivity of these tubes is so great that only a very small amount of feedback is necessary to start oscillation. To assure a stable amplifier, it is usually necessary to load the grid circuit, or to use a neutralizing circuit.

The capacitive neutralizing system for screen-grid tubes is shown in Fig. 48A. C1 is the neutralizing capacitor. The capacitance should be chosen so that at some adjustment of C1,

$$\frac{C1}{C3} = \frac{\text{Tube grid-plate capacitance (or } C_{gp})}{\text{Tube input capacitance (or } C_{in})}$$

The grid-cathode capacitance must include all strays directly across the tube capacitance, including the capacitance of the tuning-capacitor stator to ground.

### PI-Network Values

#### Tube Load Impedance (Operating Q)

	MHz	150(12)	2000(12)	2500(12)	3000(12)	3500(12)	4000(12)	5000(13)	6000(14)	8000(16)
C1	3.5	420	315	252	210	180	157	126	114	99
	7	190	143	114	95	82	71	57	52	45
	14	93	70	56	47	40	35	28	25	22
	21	62	47	37	31	27	23	19	17	15
	28	43	32	26	21	18	16	13	12	10
C2	3.5	2117	1776	1536	1352	1203	1079	875	862	862
	7	942	783	670	583	512	451	348	341	341
	14	460	382	326	283	247	217	165	162	162
	21	305	253	216	187	164	144	109	107	107
	28	210	174	148	128	111	97	72	70	70
L1	3.5	5.73	7.46	9.17	10.86	12.53	14.19	17.48	19.18	21.98
	7	3.14	4.09	5.03	5.95	6.86	7.77	9.55	10.48	12.02
	14	1.60	2.08	2.56	3.03	3.49	3.95	4.85	5.33	6.11
	21	1.07	1.39	1.71	2.02	2.34	2.64	3.25	3.56	4.09
	28	0.77	1.01	1.24	1.46	1.69	1.91	2.34	2.57	2.95

These component values are for use with the circuit of Fig. 44A and were provided by W6FFC.

Fig. 46 — A table of pi-network values for various plate impedances with a loaded Q of 12.

### Pi-L Networks Data

Z <sub>in</sub> (Ohms)	Freq. (MHz)	C1 (pF)	L1 (μH)	C2 (pF)	L2 (μH)
1500	3.50	403.	7.117	1348.	4.518
1500	4.00	318.	7.117	991.	4.518
1500	7.00	188.	3.900	596.	2.476
1500	7.30	174.	3.900	543.	2.476
1500	14.00	93.	1.984	292.	1.259
1500	14.35	89.	1.984	276.	1.259
1500	21.00	62.	1.327	191.	0.843
1500	21.45	59.	1.327	185.	0.843
1500	28.00	48.	0.959	152.	0.609
1500	29.70	43.	0.959	134.	0.609
2000	3.50	304.	9.086	1211.	4.518
2000	4.00	239.	9.086	894.	4.518
2000	7.00	142.	4.978	534.	2.476
2000	7.30	131.	4.978	490.	2.476
2000	14.00	70.	2.533	264.	1.259
2000	14.35	67.	2.533	249.	1.259
2000	21.00	47.	1.694	173.	0.843
2000	21.45	45.	1.694	167.	0.843
2000	28.00	36.	1.224	135.	0.609
2000	29.70	32.	1.224	120.	0.609
2500	3.50	244.	11.010	1115.	4.518
2500	4.00	191.	11.010	827.	4.518
2500	7.00	114.	6.033	493.	2.476
2500	7.30	105.	6.033	453.	2.476
2500	14.00	56.	3.069	240.	1.259
2500	14.35	53.	3.069	230.	1.259
2500	21.00	38.	2.053	158.	0.843
2500	21.45	36.	2.053	154.	0.843
2500	28.00	29.	1.483	127.	0.609
2500	29.70	26.	1.483	111.	0.609
3000	3.50	204.	12.903	1042.	4.518
3000	4.00	159.	12.903	777.	4.518
3000	7.00	94.	7.070	468.	2.476
3000	7.30	87.	7.070	426.	2.476
3000	14.00	47.	3.597	222.	1.259
3000	14.35	44.	3.597	217.	1.259
3000	21.00	32.	2.406	146.	0.843
3000	21.45	30.	2.406	145.	0.843
3000	28.00	24.	1.738	115.	0.609
3000	29.70	21.	1.738	105.	0.609
3500	3.50	174.	14.772	997.	4.518
3500	4.00	136.	14.772	738.	4.518
3500	7.00	81.	8.094	444.	2.476
3500	7.30	75.	8.094	404.	2.476
3500	14.00	40.	4.118	215.	1.259

Fig. 47 — Table of pi-L network values for various plate impedances and frequencies. These values

This may amount to 5 to 20 pF. In the case of capacitance coupling, the output capacitance of the driver tube must be added to the grid-cathode capacitance of the amplifier in arriving at the value of C1.

### Neutralizing a Screen-Grid Amplifier Stage

There are two general procedures available for indicating neutralization in a screen-grid amplifier stage. If the screen-grid tube is operated with or without grid current, a sensitive output indicator can be used. If the screen-grid tube is operated with grid current, the grid-current reading can be used as an indication of neutralization. When the output indicator is used, both screen and plate voltages must be removed from the tubes, but the dc circuits from the plate and screen to cathode must be completed. If the grid-current reading is used, the plate voltage may remain on

but the screen voltage must be zero, with the dc circuit completed between screen and cathode.

The immediate objective of the neutralizing process is reducing to a minimum the rf-driver voltage fed from the input of the amplifier to its output circuit through the grid-plate capacitance of the tube. This is done by adjusting carefully, bit by bit, the neutralizing capacitor or link coils until an rf indicator in the output circuit reads minimum, or the reaction of the unloaded plate-circuit tuning on the grid-current value is minimized.

The wavemeter shown in the Measurements chapter makes a sensitive neutralizing indicator. The wavemeter coil should be coupled to the output tank coil at the low-potential or "ground" point. Care should be taken to make sure that the coupling is loose enough at all times to prevent burning out the meter or the rectifier. The plate tank capacitor should be

readjusted for maximum reading after each change in neutralizing.

When the grid-current meter is used as a neutralizing indicator, the screen should be grounded for rf and dc, as mentioned above. There will be a change in grid current as the unloaded plate tank circuit is tuned through resonance. The neutralizing capacitor (or inductor) should be adjusted until this deflection is brought to a minimum. As a final adjustment, screen voltage should be returned and the neutralizing adjustment continued to the point where minimum plate current, maximum grid current and maximum screen current occur simultaneously. An increase in grid current when the plate tank circuit is tuned slightly on the high-frequency side of resonance indicates that the neutralizing capacitance is too small. If the increase is on the low-frequency side, the neutralizing capacitance is too large. When neutralization is complete, there should be a slight decrease in grid current on either side of resonance.

### Grid Loading

The use of a neutralizing circuit may often be avoided by loading the grid circuit if the driving stage has some power capability to spare. Loading by tapping the grid down on the grid tank coil (or the plate tank coil of the driver in the case of capacitive coupling), or by a resistor from grid to cathode is effective in stabilizing an amplifier.

### Low-Frequency Parasitic Oscillation

The screening of most transmitting screen-grid tubes is sufficient to prevent low-frequency parasitic oscillation caused by resonant circuits set up by rf chokes in grid and plate circuits. When rf chokes are used in both grid and plate circuits of a triode amplifier, the split-stator tank capacitors combine with the rf chokes to form a low-frequency parasitic circuit, unless the amplifier circuit is arranged to prevent it. Often, a resistor is substituted for the grid rf choke, which will produce the desired result. This resistance should be a least 100 ohms. If any grid-leak resistance is used for biasing, it should be substituted for the 100-ohm resistor.

### Component Ratings: Output Tank Capacitor Voltage

In selecting a tank capacitor with a spacing between plates sufficient to prevent voltage breakdown, the peak rf voltage across a tank circuit under load, but without modulation, may be taken conservatively as equal to the dc plate or collector voltage. If the dc supply voltage also appears across the tank capacitor, this must be added to the peak rf voltage, making the total peak voltage twice the dc supply voltage. If the amplifier is to be plate-modulated, this last value must be doubled to make it four times the dc plate voltage, because both dc and rf voltages

Z <sub>in</sub> (Ohms)	Freq. (MHz)	C1 (pF)	L1 (μH)	C2 (pF)	L2 (μH)
3500	14.35	38.	4.118	206.	1.259
3500	21.00	27.	2.755	136.	0.843
3500	21.45	25.	2.755	138.	0.843
3500	28.00	21.	1.989	106.	0.609
3500	29.70	18.	1.989	99.	0.609
4000	3.50	153.	16.621	947.	4.518
4000	4.00	119.	16.621	706.	4.518
4000	7.00	71.	9.107	418.	2.476
4000	7.30	65.	9.107	387.	2.476
4000	14.00	35.	4.633	204.	1.259
4000	14.35	33.	4.633	197.	1.259
4000	21.00	23.	3.099	137.	0.843
4000	21.45	22.	3.099	132.	0.843
4000	28.00	18.	2.238	107.	0.609
4000	29.70	16.	2.238	95.	0.609
5000	3.50	123.	20.272	872.	4.518
5000	4.00	95.	20.272	658.	4.518
5000	7.00	57.	11.108	387.	2.476
5000	7.30	52.	11.108	360.	2.476
5000	14.00	29.	5.651	186.	1.259
5000	14.35	27.	5.651	183.	1.259
5000	21.00	19.	3.780	125.	0.843
5000	21.45	18.	3.780	123.	0.843
5000	28.00	15.	2.730	95.	0.609
5000	29.70	13.	2.730	89.	0.609
6000	3.50	103.	23.873	829.	4.518
6000	4.00	80.	23.873	621.	4.518
6000	7.00	48.	13.081	368.	2.476
6000	7.30	44.	13.081	340.	2.476
6000	14.00	24.	6.655	172.	1.259
6000	14.35	22.	6.655	173.	1.259
6000	21.00	16.	4.452	117.	0.843
6000	21.45	15.	4.452	116.	0.843
6000	28.00	13.	3.215	87.	0.609
6000	29.70	11.	3.215	84.	0.609
8000	3.50	78.	30.967	747.	4.518
8000	4.00	60.	30.967	569.	4.518
8000	7.00	36.	16.968	337.	2.476
8000	7.30	33.	16.968	312.	2.476
8000	14.00	18.	8.632	165.	1.259
8000	14.35	17.	8.632	159.	1.259
8000	21.00	12.	5.775	104.	0.843
8000	21.45	11.	5.775	106.	0.843
8000	28.00	9.	4.171	86.	0.609
8000	29.70	8.	4.171	77.	0.609

Operating Q - 12. Output load - 52 ohms.

Computer data provided by Bill Imamura, JA6GW.

are based on a loaded Q of 12.

**Table 4**

**Wire Sizes for Transmitting Coils for Tube Transmitters**

Power Input (Watts)	Band (MHz)	Wire Size
1000	26-21	6
	14-7	8
	3.5-1.8	10
500	28-21	8
	14-7	12
	3.5-1.8	14
150	28-21	12
	14-7	14
	3.5-1.8	18
75	28-21	14
	14-7	18
	3.5-1.8	22
25 or less*	28-21	18
	14-7	24
	3.5-1.8	28

\*Wire size limited principally by consideration of Q.

grounded. This can be done conveniently through the use of panel shaft-bearing units.

**Tank Coils**

Tank coils should be mounted at least their diameter away from shielding to prevent a marked loss in Q. Except perhaps at 28 MHz it is not important that the coil be mounted quite close to the tank capacitor. Leads up to 6 or 8 inches are permissible. It is more important to keep the tank capacitor as well as other components out of the immediate field of the coil. For this reason, it is preferable to mount the coil so that its axis is parallel to the capacitor shaft, either alongside the capacitor or above it.

There are many factors that must be taken into consideration in determining the size of wire (see table 4) which should be used in winding a tank coil. The considerations of form factor and wire size which will produce a coil of minimum loss are often of less importance in practice than the coil size that will fit into available space or that will handle the required power without excessive heating. This is particularly true in the case of screen-grid tubes where the relatively small driving power required can be easily obtained even if the losses in the driver are quite high. It may be considered preferable to take the power loss if the physical size of the exciter can be kept down by making the coils small.

Transistor output circuits operate at relatively low impedances because the current is quite high. Coils should be made of heavy wire or strap, with connections made for the lowest possible resistance. At vhf, stripline techniques are often employed, as the small inductance values required for a lumped inductance become difficult to fabricate.

**RF Chokes**

The characteristics of any rf choke will vary with frequency, from characteristics

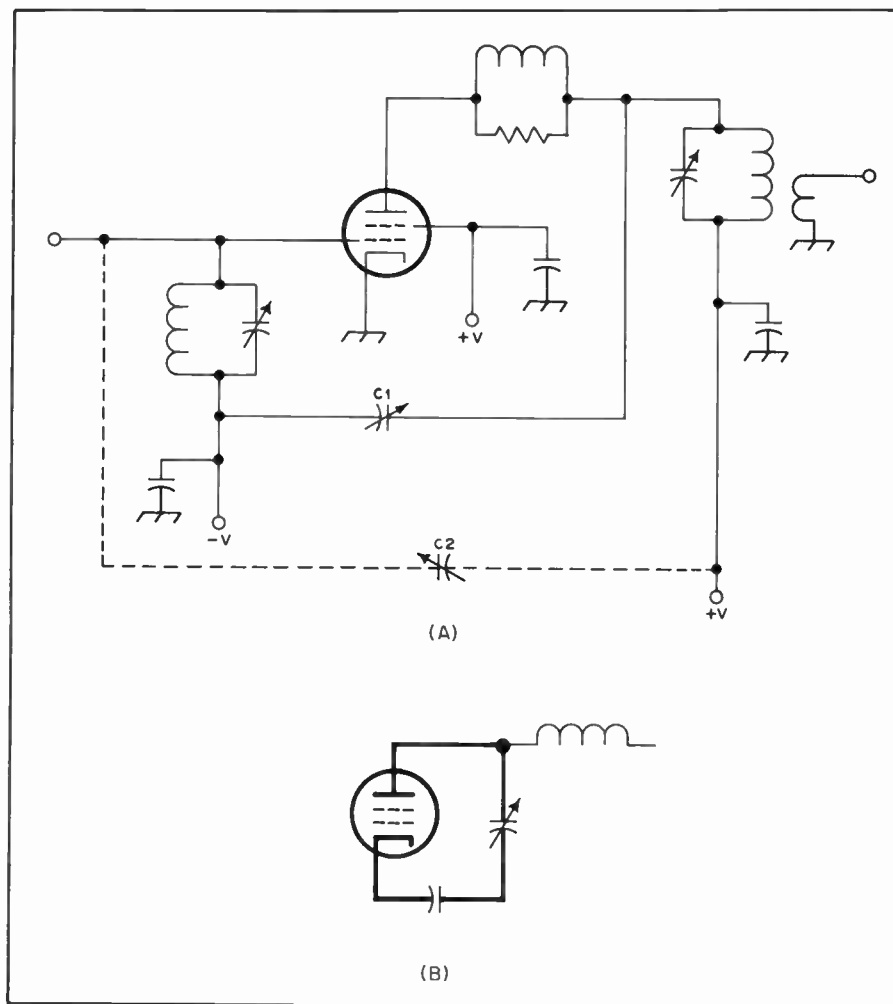


Fig. 48 — A neutralization circuit may use either C1 or C2 to cancel the effect of the tube grid-plate capacitance (A). The circuit at B shows the usual vhf-parasitic circuit in bold lines.

**Table 3**

**Typical Tank-Capacitor Plate Spacings**

Spacing Inches (mm)	Peak Voltage	Spacing Inches (mm)	Peak Voltage	Spacing Inches (mm)	Peak Voltage
0.015 (0.4)	1000	0.07 (1.8)	3000	0.175 (4.4)	7000
0.02 (0.5)	1200	0.08 (2.8)	3500	0.25 (6.3)	9000
0.03 (0.8)	1500	0.125 (3.0)	4500	0.35 (8.9)	11000
0.05 (1.3)	2000	0.15 (3.8)	6000	0.5 (12.7)	13000

double with 100-percent amplitude modulation. At the higher voltages, it is desirable to choose a tank circuit in which the dc and modulation voltages do not appear across the tank capacitor, to permit the use of a smaller capacitor with less plate spacing.

Capacitor manufacturers usually rate their products in terms of the peak voltage between plates. Typical plate spacings are shown in Table 3.

Output tank capacitors should be mounted as close to the tube as temperature considerations will permit, to make possible the shortest capacitive path

from plate to cathode. Especially at the higher frequencies, where minimum circuit capacitance becomes important, the capacitor should be mounted with its stator plates well spaced from the chassis or other shielding. In circuits where the rotor must be insulated from ground, the capacitor should be mounted on ceramic insulators of size commensurate with the plate voltage involved and — most important of all, from the viewpoint of safety to the operator — a well-insulated coupling should be used between the capacitor shaft and the dial. *The section of the shaft attached to the dial should be well*



resembling those of a parallel-resonant circuit of high impedance, to those of a series-resonant circuit, where the impedance is lowest. In between these extremes, the choke will show varying amounts of inductive or capacitive reactance.

In series-feed circuits, these characteristics are of relatively small importance because the rf voltage across the choke is negligible. In a parallel-feed circuit, however, the choke is shunted across the tank circuit, and is subject to the full tank rf voltage. If the choke does not present a sufficiently high impedance, enough power will be absorbed by the choke to cause it

to burn out.

To avoid this, the choke must have a sufficiently high reactance to be effective at the lowest frequency, and yet have no series resonances near the higher-frequency bands.

### 80-Meter QRP — The Sardine Sender

While the majority of amateur equipment produced today is composed of complex, multifunction circuitry, quality simple electronics still holds a well-established position in ham radio. QRP equipment, often very simple in design, offers outstanding portable and educational opportunities not often realized with more complicated units. The 3/4-watt output of this unit surpasses FCC spectral purity requirements while operating on the 80-meter band.

#### The Circuit

Q1 performs as a Pierce oscillator (Fig. 50). The crystal is in the feedback path from collector to base. An untuned collector is employed. Q2 functions as a Class A broadband driver which has a broadband solenoidal transformer in the collector (T1). Q3 operates Class C and is supplied with operating voltage all of the time. Q3 conducts when the 12-volt line to Q1 and Q2 is keyed at J1. Conduction is brought about by the application of driving power from Q2. R9 is used in the emitter of Q3 to prevent burnout and to aid stability through the introduction of degenerative feedback.

Additional protection is offered to Q3 by the inclusion of a Zener diode, D1.

This diode clamps on rf voltage peaks in excess of 36 volts. The collector level could exceed that amount if Q3 broke into self-oscillation, or if no load was attached at J4 during key-down conditions.

L2 and L3 are decoupling rf chokes which help prevent undesired rf energy from one stage reaching another — a condition that could cause transmitter instability and spurious output. The associated bypass capacitors are part of the decoupling networks. R8 is bridged across the secondary of T1 to help prevent self oscillation of Q3.

A fixed-tuned, low-pass T network is used as the Q3 output tank. It requires no adjustment. Operation will be satisfactory from 3.5 to 3.75 MHz with this circuit. An oscillograph is given in Fig. 51 to show the spectral purity of the transmitter. Harmonics are 54 dB or greater below the peak carrier value shown.

#### Construction

Most of the components are mounted on the printed-circuit board. A scale template with layout data is shown in Fig. 52. Point-to-point wiring is acceptable as long as the lead lengths are kept short. The chassis used here is a discarded sardine can, but any suitable metalwork will do.

#### Testing and Operation

After the components are mounted in accordance with the layout of Fig. 52, a 47- or 56-ohm 2-watt resistor can be connected across J4 to serve as a dummy load. Plug in a key at J1 (note that both

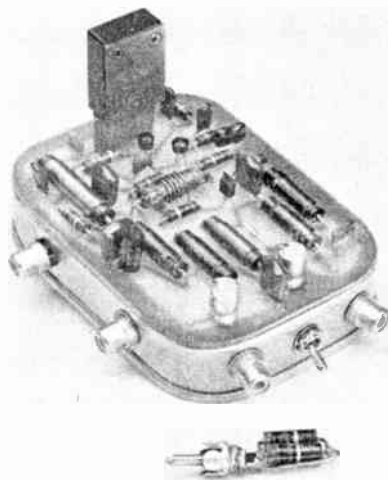


Fig. 49 — Photograph of the Sardine Sender QRP transmitter. The chassis is a sardine can. A homemade 50-ohm dummy load is in the foreground.

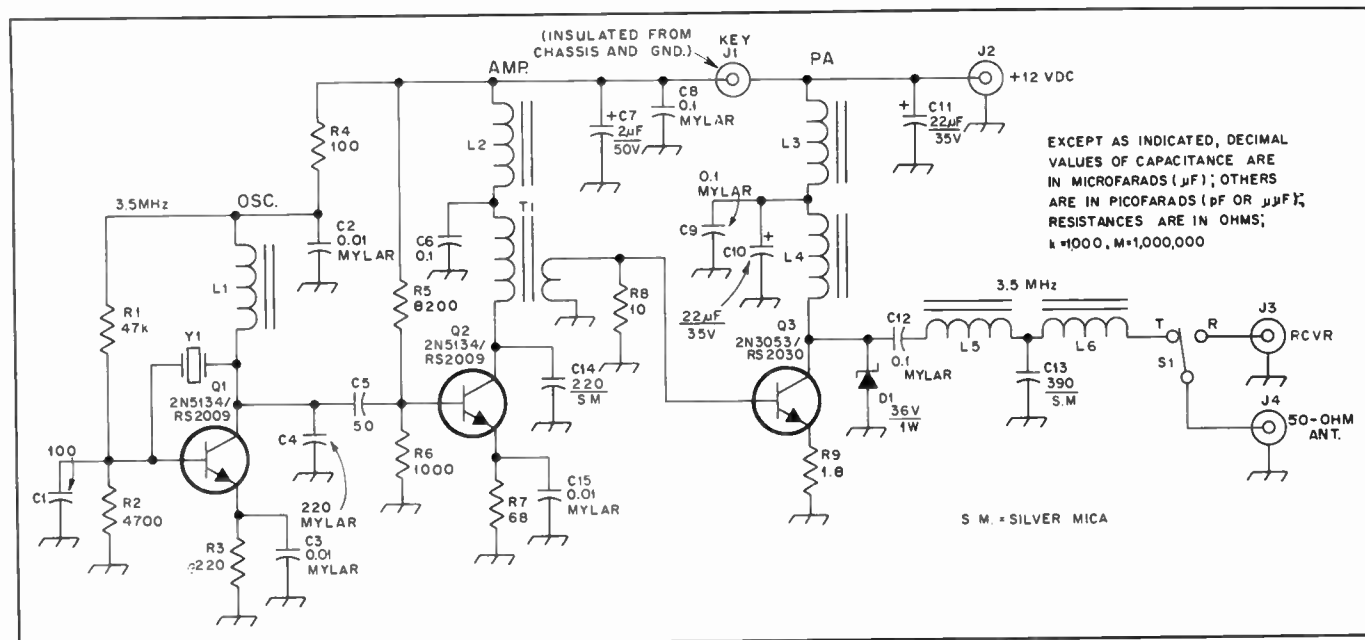


Fig. 50 — Schematic diagram of the Sardine Sender. Capacitors are disk ceramic unless otherwise noted. Resistors are 1/2-watt composition. Numbered components not appearing in the parts list are identified numerically for parts-placement information only. Polarized capacitors are electrolytic.

D1 — Zener diode, 36 V, 1 W.

J1-J4, incl. — Single-hole mount phone jack.

L1 — 100-μH choke, Radio Shack 273-102.

L2-L4, incl. — 10-μH choke, Radio Shack 273-101.

L5 — 12-μH inductor, Radio Shack 273-101 with 4 turns no. 26 enam. wire added.

L6 — 8.9-μH inductor, Radio Shack 273-101 with 3 turns removed.

T1 — Broadband transformer, Radio Shack

273-101 for primary, with 5-turn secondary of no. 26 enam. wire over C6 end of primary.

S1 — Miniature spdt toggle or slide switch.

Y1 — 80-meter fundamental type of crystal.

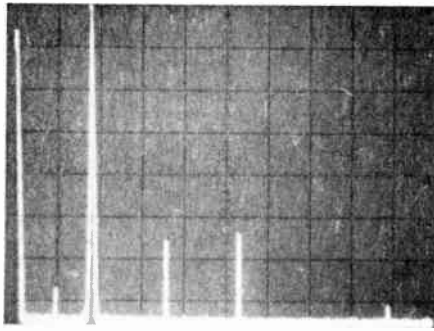


Fig. 51 — Spectrum-analyzer display of the transmitter output. The full-scale vertical line near the left is the carrier. The vertical scale is 10 dB per division. All spurious responses are in excess of 52 dB below peak carrier value, more than conforming to the FCC requirement of -40 dB or greater reduction.

contacts of J1 are above ground, thereby placing the key in series with the 12-volt line to Q1 and Q2).

A regulated dc power supply that furnishes 11 to 14 volts (not critical) is connected to J2 next. If an rf probe and VTVM are available, connect the probe from J4 to ground and key the transmitter. A power output of 3/4 watt should provide an rms voltage of 6.5 across a 56-ohm, dummy-load resistor.

Monitor the signal in a receiver and make sure there is no chirp. The principle cause of chirp with this circuit would be a sluggish crystal at Y1. Should a chirpy note result when a good crystal is used, experiment with the value of C4, the feedback capacitor.

Table 5 provides dc and rms voltage readings at check points in the circuit. This table will be helpful if difficulties with performance are encountered. Measurements should be made with a VTVM and rf probe.

### A 6-Watt Output 15-Meter Transmitter

Most QRP transmitters are designed to operate in the lower portion of the hf spectrum. This is unfortunate because 15 meters is an ideal band for low-power work. Even in periods of low solar activity the band is almost always "open" in the north/south directions and quite often in the east/west directions with transcontinental contacts commonplace. Also, it is not unusual to hear low-power stations working lots of DX. This transmitter appeared originally in January 1976 *QST*.

#### Circuit Details

Q1 and associated components (Fig. 54) comprise the Colpitts oscillator that tunes from 10.5 to 10.625 MHz. L1, an adjustable coil, is used to set the VFO on frequency at the low end of the range. C4 and C5 form an rf voltage divider which is placed across the series-tuned tank (L1 and C3). Output from Q1 is taken from the source and coupled to the gate of Q2

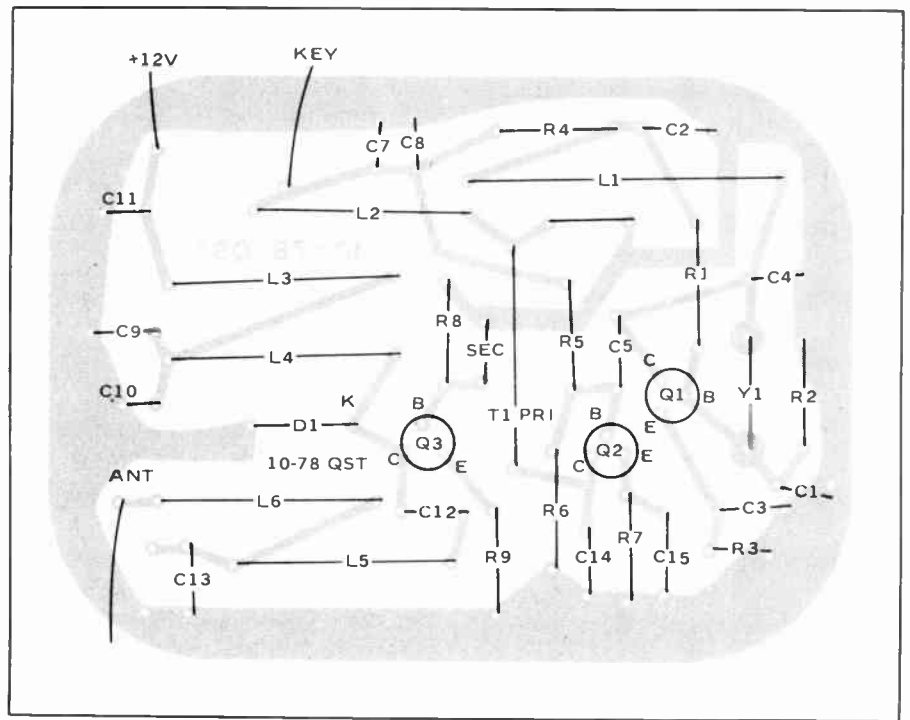


Fig. 52 — Scale template and parts placement for the Sardine Sender. Pc negatives, pc boards and parts kits for this project are available from Circuit Board Specialists, Box 969, Pueblo, CO 81002.

Table 5

	DO V (Key Up)	DC V (Key Down)	RMS V (Key Down)
Q1-E	0	+ 3.2	0
Q1-B	0	+ 1.1	2.2
Q1-C	0	+ 10.6	0.8
Q2-E	0	+ 2.0	0
Q2-B	0	+ 1.3	1.3
Q2-C	0	+ 12.0	7.7
Q3-E	- .05	+ 1.8	0
Q3-B	- .05	- .04	0.9
Q3-C	+12.0	+ 12.0	8.2

Dc and RMS voltage readings at the terminals of Q1, Q2 and Q3 as measured with a Heath VTVM and diode rf probe. Departures of 10 percent from the above readings are not indicative of problems.



Fig. 53 — The completed 15-meter transmitter.

through a small value coupling capacitor, C8.

Q2, a JFET buffer, has high input impedance, making it an ideal buffer. High input impedance is desirable because oscillator loading is minimized and therefore the frequency stability of the oscillator will not be affected significantly.

Q3 and Q4 of Fig. 54 form a push-push frequency doubler. The center tap of L3 is at ac ground and the remaining leads feed the bases of Q3 and Q4 with 10.5-MHz signals which are 180° out of phase with each other. In order to obtain a pure sine wave at the output of the doubler, the characteristics of Q3 and Q4 must be closely matched. Since transistor characteristics vary quite a bit, even with transistors of the same type, R10 is included in

the circuit to balance the two transistors. C16 and L4 make up the collector tuned circuit, and L5 couples VFO energy to the remainder of the transmitter.

Q5 operates as a Class A amplifier. R15 is a 500-ohm circuit-board potentiometer and is used to vary the bias on Q5. By varying the bias, the gain of the stage can be controlled, and thus the amount of drive applied to the succeeding stages. L6 and C22 form the tuned primary of T3.

The output stage uses a stud-mounted npn power transistor intended primarily for vhf Class C transmitters. This device is rather rugged and has more than enough gain at hf. Class C operation is used and the efficiency is on the order of 60 percent. L10, L11 and C31 make up a T network that is used to step up the low collector

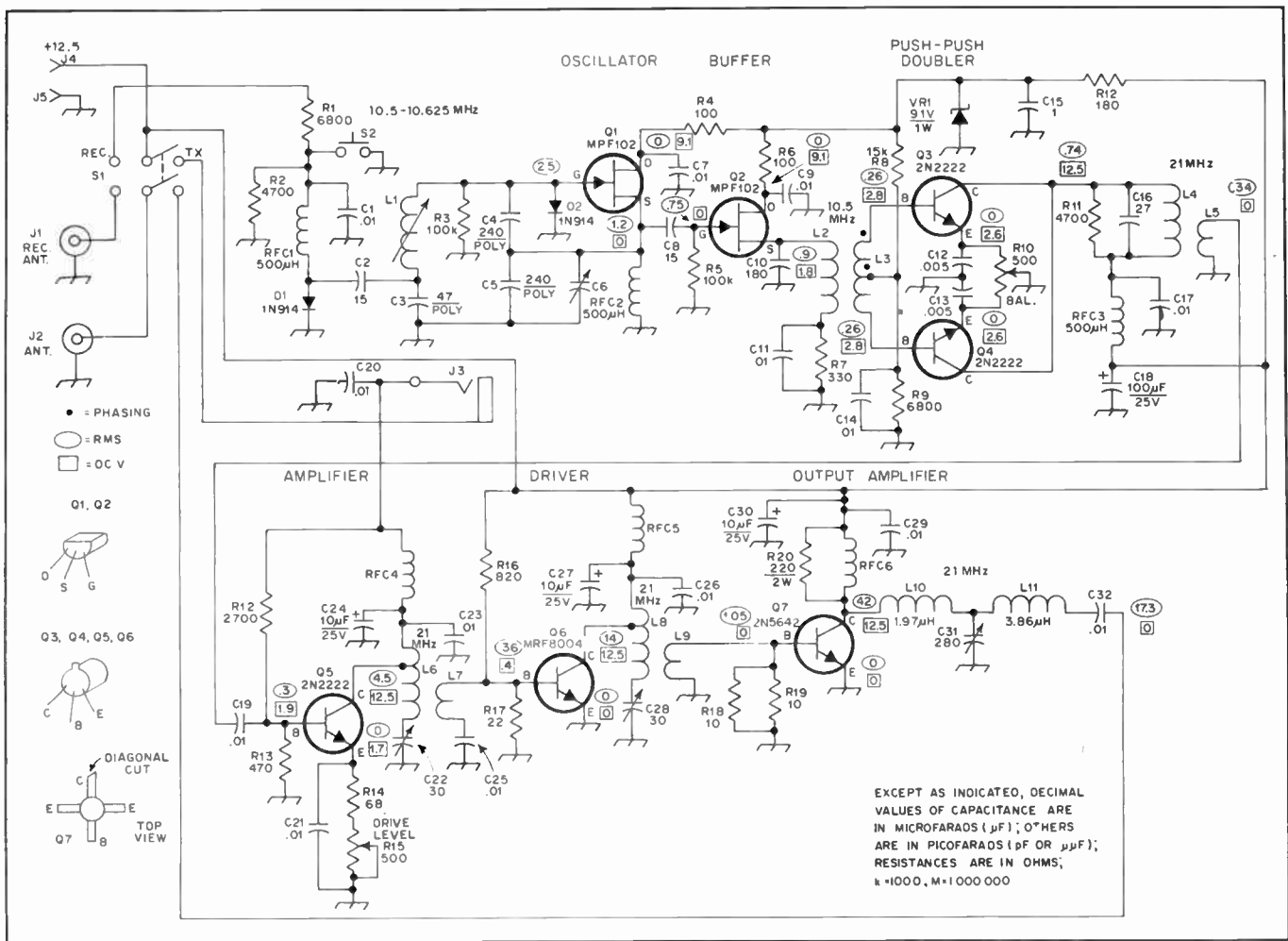


Fig. 54 — Schematic diagram of the 15-meter transmitter. Fixed-value capacitors are disk ceramic unless specified otherwise. Fixed value resistors are 1/2-W composition unless noted otherwise. Numbered components not appearing in the parts list are identified for pc-board layout purposes only.

- C3 — 47-pF polystyrene.
- C4, C5 — 240-pF polystyrene.
- C6 — 4- to 53.5-pF variable; Millen 22050 or equiv.
- C18 — 100- $\mu$ F electrolytic, 25 volts.
- C24, C27, C30 — 10 $\mu$ F tantalum or electrolytic, 25 volts.
- C22, C28 — 2.7- to 30-pF variable, Elmenco 461 or equiv.
- C31 — 25- to 280-pF variable, Elmenco 464 or equiv.
- D1, D2 — 1N914 or equiv.
- D3 — Zener Diode, 9.1 volt, 1 watt.
- J1, J2 — Coaxial connector, type SO-239.
- J3 — Phone jack, Radio Shack 274-280 or equiv.
- J4, J5 — Binding post.
- L1 — 6.05- to 12.5- $\mu$ H adjustable coil, Miller

- 42A105CB1 or equiv.
- L2 — 17 turns no. 28 enam. wire on Amidon T-50-6 core.
- L3 — 10 turns no. 28 enam. wire, center tapped, wound over L2.
- L4 — 17 turns no. 28 enam. wire on an Amidon T-50-6 core.
- L5 — 5 turns no. 28 enam. wire wound over L4.
- L6 — 30 turns no. 28 enam. wire on an Amidon T-50-6 core. Tap 10 turns above C23 end.
- L7 — 4 turns no. 28 enam. wire wound over L6.
- L8 — 30 turns no. 28 enam. wire on an Amidon T-50-6 core. Tap 7 turns above C26 end.
- L9 — 3 turns no. 28 enam. wire wound over L8.
- L10 — 20 turns no. 22 enam. wire on an Amidon T-68-6 core.
- L11 — 29 turns no. 22 enam. wire on an Amidon

- T-68-6 core.
- Q1, Q2 — Motorola MPF102 JFET or equiv.
- Q3, Q4, Q5 — 2N2222 transistor.
- Q6 — Motorola MRF8004.
- Q7 — Motorola 2N5642.
- RFC1, RFC2, RFC3 — 500- $\mu$ H rf choke, Millen J-302-500 or equiv.
- RFC4 — 16 turns no. 28 enam. wire on an Amidon FT-50-61 core.
- RFC5 — 11 turns no. 22 enam. wire on an Amidon FT-50-61 core.
- RFC6 — 6 turns no. 22 enam. wire on an Amidon FT-50-61 core.
- S1 — Dpdt miniature toggle switch.
- S2 — Spst momentary-contact push-button switch.

impedance (approximately 13 ohms) to 50 ohms.

### Construction

The transmitter is constructed on two double-sided circuit boards, one for the VFO and one for the transmitter strip. To help protect the VFO from stray rf currents, it is enclosed in a shielded box made from double-sided circuit-board material. The box measures 2 x 6 x 2 inches (51 x 152 x 51 mm), and wherever two of the panels meet they are soldered together along the entire length of the seam. The VFO circuit board is soldered

into the box near the bottom. C6, the main tuning capacitor, is attached to the front of the box and L1 is attached to the side.

The transmitter board is shown below the VFO in the photograph (Fig. 55). Both the driver and output stage require heat sinks. A Thermalloy 2215B heat sink is used for the MRF8004 driver, although any heat sink that will fit the TO-39 case may be used. The 2N5642 output transistor is mounted with the leads on the foil side of the board, thereby simplifying connection to the circuit-board foil. The stud protrudes through the circuit board, and a

homemade heat sink is attached to it on the component side of the board. A suitable heat sink consist of two U-shaped pieces of 1/16-inch (1.6-mm) aluminum sheet.

The entire transmitter, excluding power supply, is housed in an aluminum homemade enclosure that measures 6 x 8 x 2-1/2 inches (152 x 203 x 64 mm). Mounted on the rear panel are the antenna and receiver antenna output receptacles, along with two binding posts for connection to the power supply. The front panel supports the vernier dial mechanism, key jack, transmit-receive



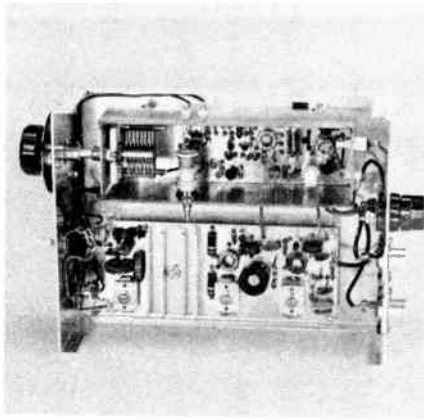


Fig. 55 — An inside view of the transmitter. The VFO is at the top of the picture and the transmitter strip is directly below it. The homemade heat sink for the output transistor can be seen at the left center of the transmitter board.

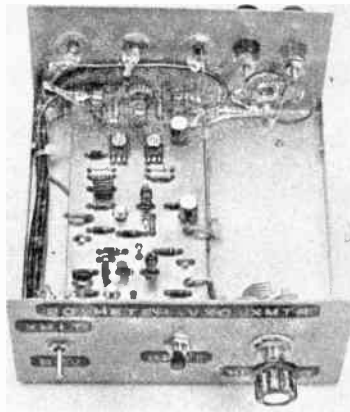


Fig. 56 — The completed 6-watt, 20-meter transmitter. C1 is mounted to the front panel at the lower right. All rf cable runs are made with RG-174/U.

switch, and spot switch. Since +12 volts is present on both the tip and ring connections of the key jack, it must be isolated from ground. This can be accomplished by drilling the hole for the jack slightly oversize and using fiber washers on each side of the panel.

### Tune-up

Connect a 12-volt power supply capable of delivering 1.3 amperes to the power supply terminals on the rear apron. Attach a 50-ohm dummy load to the antenna receptacle and insert a key into J3. The VFO must be adjusted first. Set the main tuning capacitor so that its plates are fully meshed and set the drive control, R5, to the minimum drive position (tab on control toward the edge of the circuit board). Place the transmit-receive switch

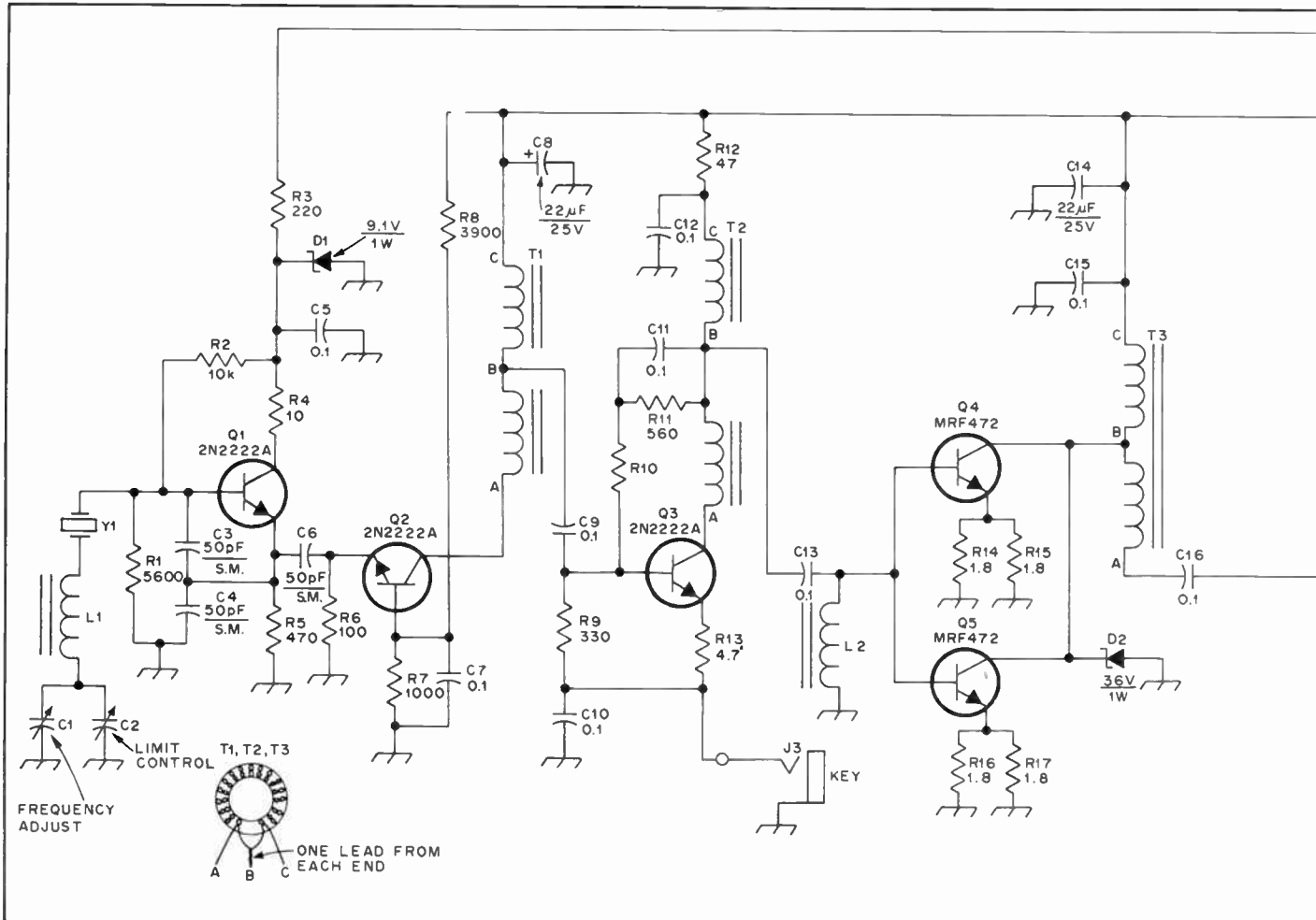


Fig. 57 — Schematic diagram of the 20-meter transmitter. All resistors are 1/4-watt carbon types unless noted otherwise. All capacitors are mylar or disk ceramic unless otherwise noted. Polarized capacitors are electrolytic or tantalum. Q4 and Q5 must be heat sunk to the circuit board.

- C1 — Variable capacitor, 50-pF maximum, panel mount.
- C2 — Variable capacitor, 10 pF maximum, miniature circuit-board mount.
- C17, C18 — Fixed capacitor, 240 pF, polystyrene.
- D1 — Zener diode, 9.1 V, 1 W.
- D2 — Zener diode, 36 V, 1 W.

- J1, J2 — Binding post.
- J3 — Key jack.
- L1 — 35 turns no. 32 enam. wire on a T-37-6 core.
- L2 — 9 turns no. 26 enam. wire on an FT-73-801 ferrite bead.
- L3, L5 — 16 turns no. 24 enam. wire on a T-50-6 core.

- L4 — 19 turns no. 24 enam. wire on a T-50-6 core.
- Q1, Q2, Q3 — Transistor, 2N2222A or equiv.
- Q4, Q5 — Transistor, MRF472 or equiv.
- R14 - R17, incl. — Fixed resistor, 1.8 ohms, 1/2 W.
- S1 — Toggle switch, 3pdt.




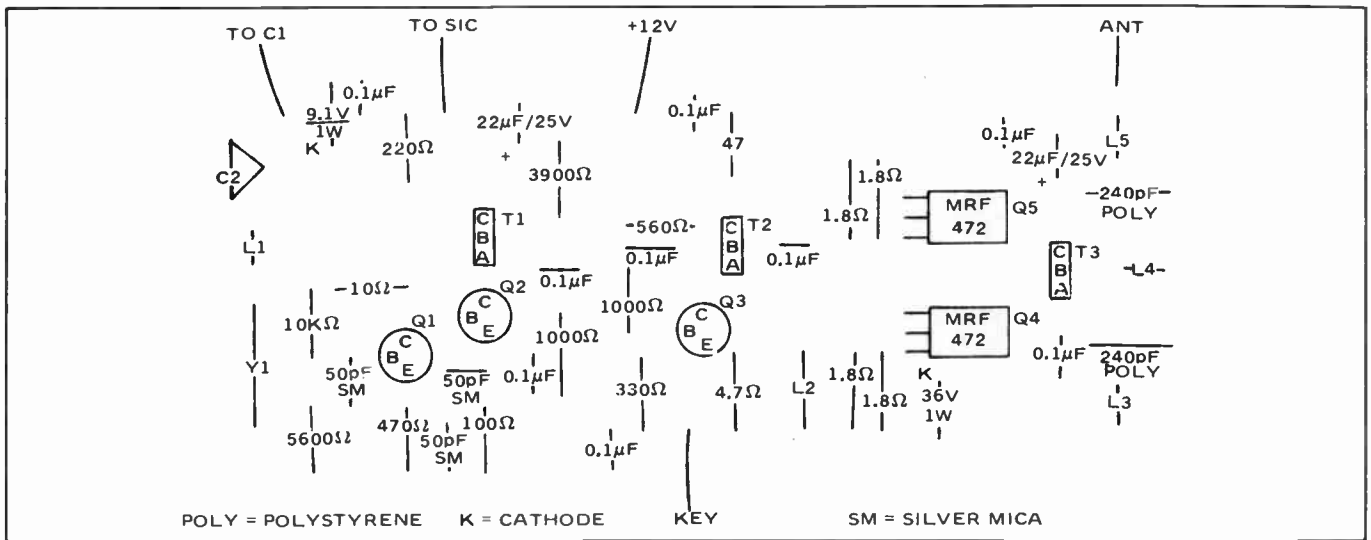


Fig. 58 — Scale etching pattern and parts layout information for the 20-meter transmitter. Gray areas represent unetched copper. One side of the board is a complete ground plane.

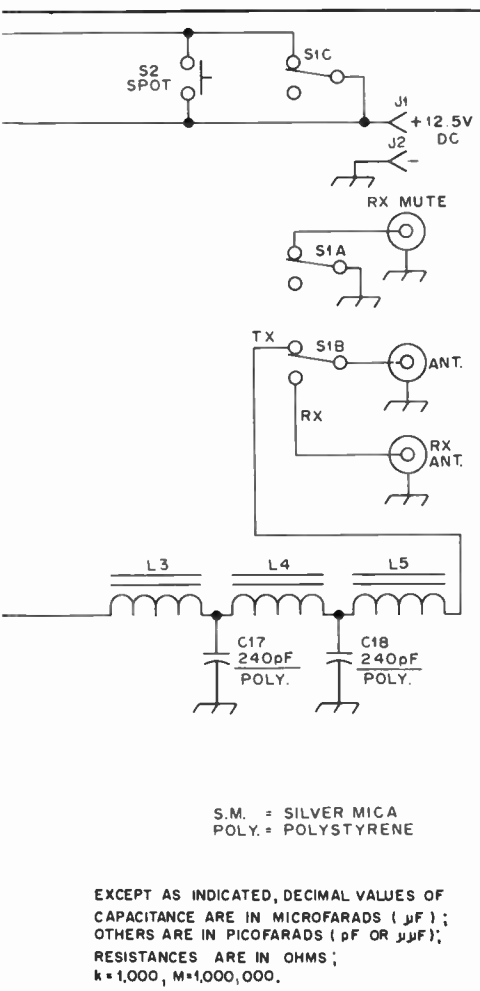

in the transmit position. While listening to the station receiver, set to approximately 20.998 MHz, adjust L1 to bring the VFO on frequency.

For the following adjustment, a general-coverage receiver, dip meter, or oscilloscope may be used. Set the VFO on the transmitter to 21.000 MHz. Insert one end of a wire into the receiver antenna jack and place the other end near L4 in the VFO. Tune the receiver to 10.5 MHz and adjust the balancing resistor, R10, for minimum signal strength. If a receiver that covers this frequency is not available, a dip meter may be used in its place. With the dip meter in the detector mode and its coil coupled to L4, tune the dip meter to 10.5 MHz. Adjust R10 for a minimum reading. If an oscilloscope is available, it may be connected across the output of the VFO. R10 should then be adjusted for the purest sine-wave curve. This completes the VFO alignment.

A VTVM or FET voltmeter with rf probe can be used for the alignment of the transmitter strip. Connect the rf probe across the dummy load. Key the transmitter and advance the drive control to the 3/4 full-drive position. Adjust C22, C28 and C31 for maximum output. As an alternative to the VTVM or FET voltmeter, an SWR indicator or wattmeter may be used. The device should be placed in the line between the transmitter and the dummy load. C22, C28 and C31 are adjusted to provide maximum output, and R15 is adjusted for a 6-watt reading.

#### Additional Comments

Circuit board templates and parts layout diagrams are available from ARRL for \$1.25. Included with the templates is a list of suppliers for all parts in this project other than fixed-value capacitors and resistors. Spectral analysis of the transmitted signal shows the second harmonic to be 45 dB down from the main signal and

the third harmonic down by 55 dB. On-the-air contacts and measurements made in the ARRL lab indicate that the transmitter is clean and chirp free.

#### A VXO-Controlled Transmitter for 20 Meters

The variable-crystal oscillator (VXO) represents a convenient method for generating a highly-stable, adjustable-frequency signal. With the circuit shown in Fig. 57 a total frequency span of 10 kHz per crystal is realized. The circuit uses 14-MHz fundamental-type crystals. Since the operator is apt to favor one portion of a band over another, a few crystals are all that are necessary for coverage of a part of the band. The transmitter, as shown, is rated for 6 watts of output while running at the 10-watt input level.

#### Circuit Description

The schematic diagram of the transmitter is displayed at Fig. 57. Q1 and associated components comprise a Colpitts variable-frequency crystal oscillator. C1 is used to adjust the frequency of the oscillator (approximately 5 kHz above

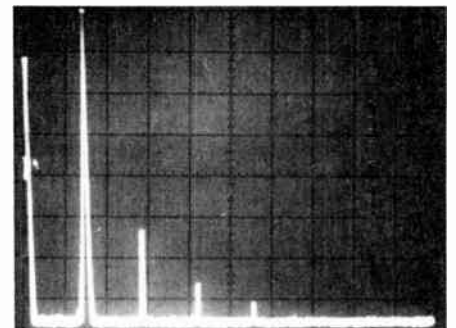


Fig. 59 — Spectral display of the VXO-controlled transmitter. The second harmonic is down 54 dB and the third is down 66 dB relative to the fundamental output. This transmitter complies with current FCC specifications regarding spectral purity.

- S2 — Push-button switch, spst, normally open.
- T1, T2 — Broadband transformer, 11 turns no. 24 enam. wire bifilar wound on an FT-37-61 core.
- T3 — Broadband transformer, 11 turns no. 24 enam. wire bifilar wound on an FT-50-61 core.
- Y1 — Crystal, 14-MHz fundamental type. International Crystal EX series.

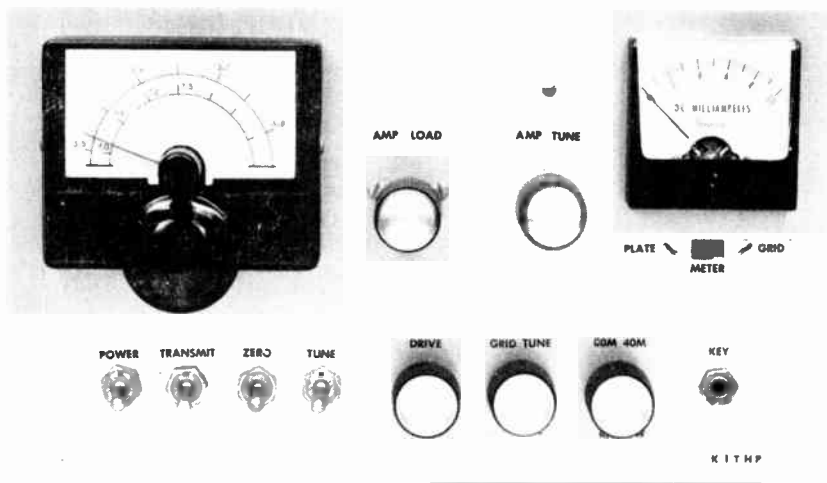


Fig. 60 — Front panel of the two-band transmitter.

and below the crystal frequency) and C2 is used to limit the span of the oscillator. If no limit is provided the oscillator can operate "on its own" and no longer be under the control of the crystal — an undesirable circumstance. Supply voltage is fed to the oscillator only during transmit and spot periods. This prevents the oscillator from interfering with received stations operating on the same frequency.

Output energy from the oscillator is routed to Q2, a grounded-base amplifier. This stage provides some gain, but more important, a high degree of isolation between the oscillator and the driver stage. Pulling and chirp are virtually non-existent.

The driver stage uses a broadband amplifier that operates Class A. Keying of this stage is accomplished by ungrounding the base and emitter resistors. C10 is used to shape the waveform. Although the

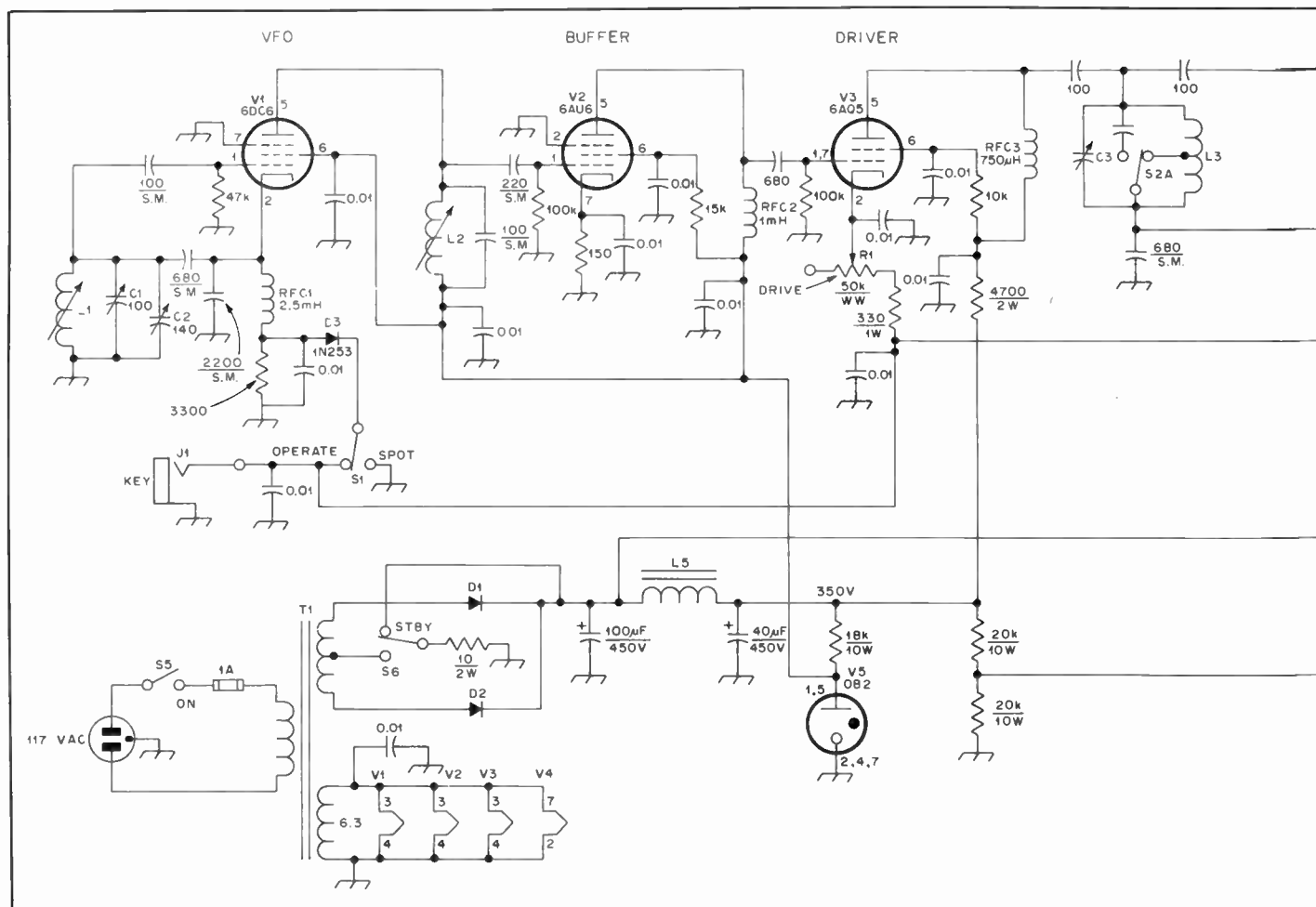


Fig. 61 — Schematic diagram of the 80- and 40-meter transmitter. Resistors are 1/2-watt carbon types unless specified otherwise. Capacitors are disk ceramic unless otherwise noted.

- C1 — 100-pF midget variable, Hammarlund MC-100.
- C2 — 140-pF midget variable, Hammarlund APC-140-B.
- C3 — 100-pF midget variable, Hammarlund APC-100-B.
- C4 — 15-pF midget variable, Hammarlund APC-15.
- C5 — 365-pF midget variable, Miller type 2111.

- C6 — 365-pF per section, three-section midget variable, three stators connected in parallel, Miller type 2113.
- D1, D2 — Silicon diode, 1000 PRV, 2.5 A. Mallory M2.5 A or equiv.
- J1 — Phone jack, open-circuit type.
- J2 — Coaxial chassis connector, type SO-239.
- L1 — 40 turns of no. 26, enameled, close-wound on 1/2-inch (12.7-mm) diameter ceramic slug-

- tuned form. Form is Millen 69046.
- L2 — Slug-tuned coil, 14.8 to 31.0 µH, Miller 4407.
- L3 — 36 turns of no. 22 enameled, close wound on 1-inch (25.4-mm) diameter form. 40-meter tap is 12 turns from the hot end of the coil, Millen coil form, no. 45000.
- L4 — 30 turns no. 20, 16 turns per inch, 1-inch (25.4-mm) diameter, 40-meter tap 16 turns

keying is rather hard there is no evidence of clicks.

Two MRF472 transistors are used in parallel for the power amplifier. These transistors were designed for the Citizen Band service and work quite nicely at 14 MHz. Each transistor is rated for 4-watts output which gives a margin of safety when operated at the 6-watt output level. L2 is used as a dc ground for the bases making the transistors operate Class C.

The low output impedance at the collectors is stepped up by a broadband transformer to the 50-ohm impedance level. A five-pole Chebyshev filter is used to assure a clean output signal. This transmitter exceeds current FCC specifications regarding spectral purity. D2 is used to clamp the collector voltage waveform should the transmitter be operated into an open circuit or high SWR antenna system. The transmitter is

designed to operate into a load that is close to 50 ohms resistive.

S1 is used as the transmit/receive switch. One section transfers the antenna to an accompanying receiver or the output of the transmitter strip. Another section is used to activate the VXO during transmit and the third section is provided for receiver muting purposes.

### Construction


The majority of the circuit components are mounted on a double-sided, printed-circuit board. One side of the board is etched with the circuit pattern and the other side is left as a ground plane. A small amount of copper is removed from around each hold on the ground-plane side of the board to prevent the leads from shorting to ground. A scale etching pattern and parts layout guide is shown in Fig. 58.

Affixed to the front panel are the transmit/receive switch, spot switch, and the tuning capacitor. The rear apron supports the antenna and mute jacks, key jack and binding posts.

A commercially available cabinet measuring 5 1/4 x 5 1/2 x 2 1/2 inches (133 x 140 x 64 mm) was used in the construction of this transmitter. The builder may elect to build his or her own cabinet from sheet aluminum or circuit-board material. The layout is not critical except that the lead from the circuit board to C1 should be kept as short as possible — an inch or two (25 to 51 mm) is fine.

The final transistors are heat sunk to the ground plane of the circuit board using mica washers and silicone compound. With the normal transmit duty cycle this heat sink is sufficient. If for some reason the prospective builder plans long key-down periods, an additional heat sink connected to the tops of the transistors would be helpful.

The only adjustment needed is that of setting the VXO limit capacitor. This can be done with the aid of a receiver. Using a 14-MHz fundamental-type crystal, adjust the capacitor for a maximum frequency spread of approximately 10 kHz. If too much frequency spread is available, increase the amount of capacitance. Make a final check with the receiver by listening to the keyed signal from the transmitter. It should be steady and chirp free. The spectral display of the transmitter is shown in Fig. 59. The second harmonic is down some 54 dB and third is down approximately 66 dB referenced to the fundamental.

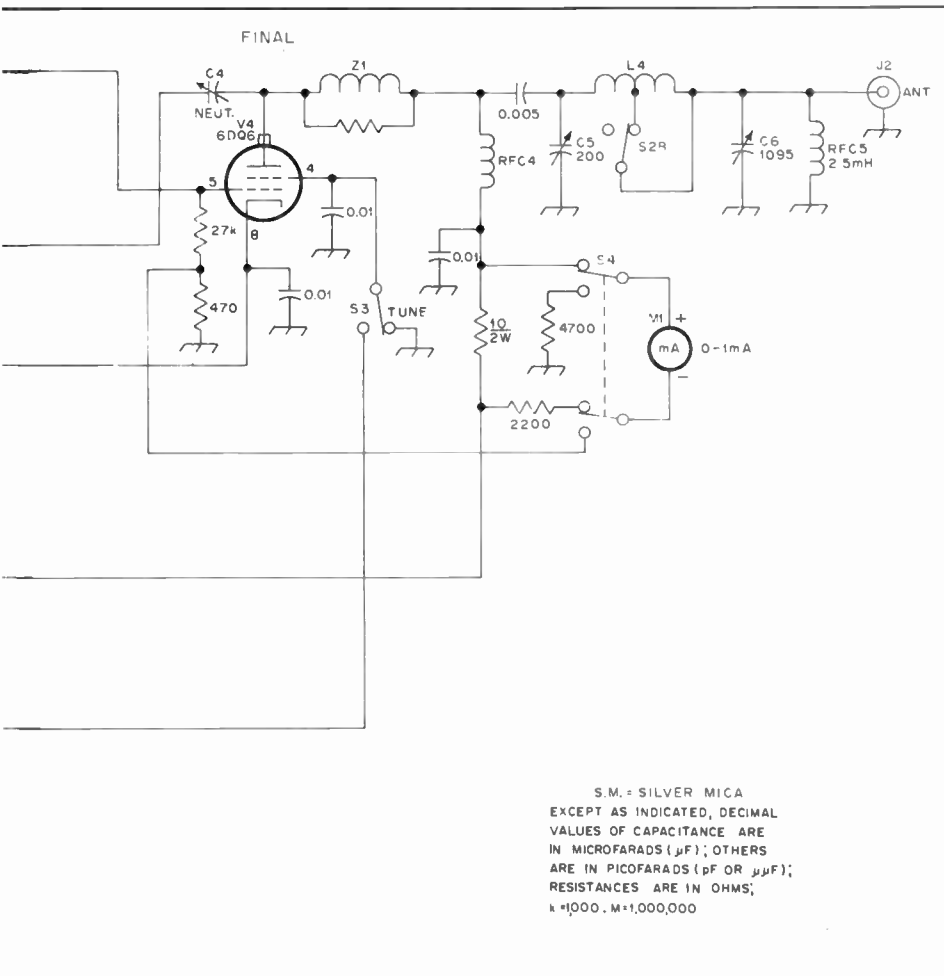

S.M. - SILVER MICA  
EXCEPT AS INDICATED, DECIMAL  
VALUES OF CAPACITANCE ARE  
IN MICROFARADS (μF); OTHERS  
ARE IN PICOFARADS (pF OR μμF);  
RESISTANCES ARE IN OHMS;  
k = 1000, M = 1,000,000

- from C5 end of coil, B & W Miniductor 3015.
- L5 — 2.5 H, 25 mA.
- M1 — 0-1 mA meter.
- R1 — 50Ω potentiometer, 1/2-watt, wire wound.
- RFC1 — 2.5-mH rf choke, Millen 34300-2500.
- RFC2 — 1-mH rf choke, Millen 34300-1000.
- RFC3, RFC4 — 750-μH rf choke, Millen 34300-750.
- RFC5 — 2.5-mH rf choke, Millen 34300-2500.

- S1, S3, S6 — Spdt toggle switch.
- S2 — 2p, 2-position rotary switch.
- S4 — Dpdt toggle switch.
- S5 — Spst toggle switch.
- T1 — Power transformer. Primary: 117 V.  
Secondaries: 540 volts, 120 mA; 6.3 volts, 3.5 A; 5 volts, 3 A (5-volt winding not used).
- Z1 — 7 turns, no. 20 enameled, close wound on 2200-ohm, 1-watt resistor.

### A 35-W, Two-Band CW Transmitter

A traditional source of components for amateur projects is the junked television set. Modern television sets are solid state, and many are pressed into service as video monitors for the home computer when they are retired from service. The older tube units, conversely, are often thrown into the garbage and hauled to the dump. The enterprising amateur can intercede and acquire enough parts for many projects.

The transmitter described here (Fig. 60) is built around used television components. While the design is far from state of the art, the performance is comparable to today's standards. Financial outlay should be minimal for anyone who is willing to invest a little time in searching for the bargains. Bands covered are 80 and 40 meters with a cw input of 35 watts. The circuit is one adapted by K1THP from an April 1965 QST article by W1ICP.

### The Circuit

The oscillator is a classic Colpitts circuit (Fig. 61). The grid circuit of the 6DC6 is tuned to the 1.75 MHz range while the plate circuit is tuned to 3.5



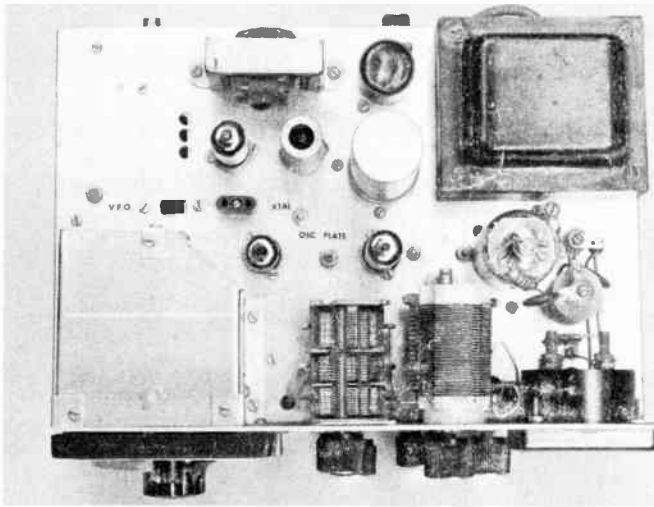


Fig. 62 — The layout on the top side of the chassis. The VFO is enclosed in an aluminum case at the left and the final stage is at the right.

MHz. V2 is an untuned buffer amplifier. This promotes stable VFO operation and chirp-free keying. Both V1 and V2 are run from a regulated power source, further enhancing transmitter stability.

The driver stage, V3, is also used as a frequency doubler for the 3.5-MHz signal during 7-MHz operation. The plate circuit, L3-C3, tunes to either 80 or 40 meters, depending on the position of S2. The cathode bias is adjustable by varying R1, allowing the proper amount of drive for the final amplifier tube.

The final amplifier of Fig. 61 is a 6DQ6 sweep tube. The high plate impedance of the tube is transformed to 50 ohms by means of a pi-network. The matching network provides harmonic attenuation. The screen of V4 can be grounded through S3 to allow tune-up at reduced power.

The cathodes of V1, V3 and V4 are all

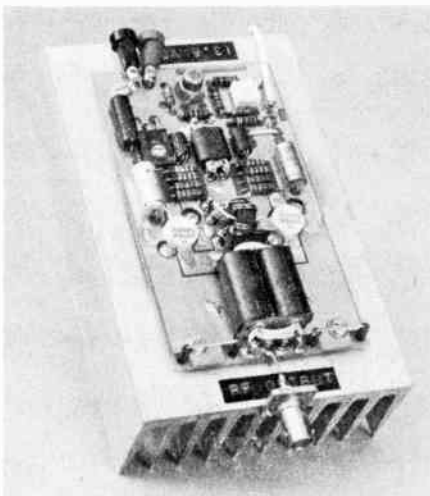


Fig. 64 — The completed 140-watt amplifier board and heat sink. D1 is mounted on the underside of the circuit board sandwiched between the board and the heat sink.

keyed. For spotting purposes the cathode of V1 can be grounded separately through S1. This turns on the oscillator without radiating a signal over the air.

The power supply uses a surplus TV-type transformer. Two silicon diodes in a full-wave circuit rectify the ac. After filtering, the unregulated power-supply output is 400V. Metering of the plate current is accomplished by use of a 0-1 mA meter connected as a volt-meter across a shunt in the B line. Grid current is measured in a similar manner.

#### Construction Details

VFO components L1, C1 and C2 should be mounted firmly to the chassis top to prevent wobble in the VFO. The leads brought down to below the chassis from the VFO components should be similarly stiff, using no. 14 solid wire. The turns of L1 are closely spaced. The wire should be wound tightly on the coil form and sprayed with a clear acrylic lacquer or coil dope to enhance mechanical stability.

The pi-network coil, L4, should be mounted on stand-off insulators at a distance from the chassis. The neutralizing arrangement requires that the shaft of C3 be insulated from the chassis. Neutralizing capacitor C4 must also be insulated from ground.

#### Tune-up and Operation

Upon warm-up, the oscillator should be tested and aligned. A receiver tuned to the operating frequency is an ideal indicator. To adjust the VFO, first fully mesh C1, the front panel control. The slug in L1 should be fully disengaged (screwed to the stop on the coil form). Slowly tune C2 through its range until the signal is heard at 3500 kHz in the receiver.

For optimum bandspread, 300 kHz of range should be available at 80 meters. Tune C1 through 180 degrees and check

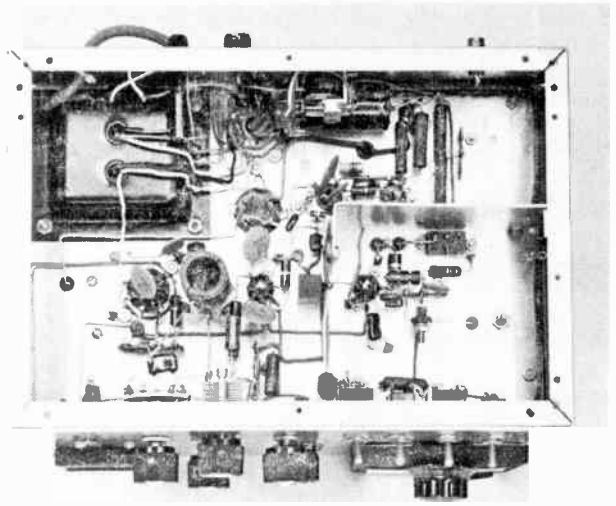


Fig. 63 — The underside of the transmitter. Layout is not especially critical. However, a clean layout will make trouble shooting much simpler, should that be necessary.

the frequency coverage. If it is less than 300 kHz, move the slug in L1. Reset C2 so that the fully meshed condition of C1 gives an oscillator output at 3500 kHz. Again check the range of C1. Repeat the process until the 300-kHz bandspread is reached. The dial can then be calibrated using the receiver as a standard.

After the VFO tuning range is adjusted, switch M1 to read final amplifier grid current. Leave the amplifier screen grounded and tune C3 for maximum grid current. Set the VFO to 3600 kHz and adjust the slug in L2 for maximum amplifier grid current. As much as 5 mA of grid current should be available at the maximum setting of R1.

Neutralizing the amplifier requires a means to sample output power. This could be in the form of an SWR indicator, a wattmeter or a dip meter set to the diode mode. Connect a dummy load to the output terminal through the SWR meter or wattmeter, if used. If neither is available, couple the grid-meter probe near to L4. (*Remember: High voltage is present in this rig. Turn off the power and allow the filter capacitors to bleed before working near any high-voltage point. Be careful!*) Adjust C3, and the plate-tuning capacitor for maximum deflection on the output indicator when the rig is keyed. Next, adjust C4 for minimum indication. It will be a sharp dip when adjusted properly.

Adjust the drive control for a key-down amplifier grid current of 2 mA. Switch the meter to read plate current. Set C6 to maximum and switch S4 so that screen voltage is applied to V4.

Tune-up procedure with a pi network consists of gradually reducing the loading capacitance (turning C6 towards minimum) while constantly retuning the plate tuning capacitor for a dip. This process is continued until a plate current of about 100 mA is attained. If an output-



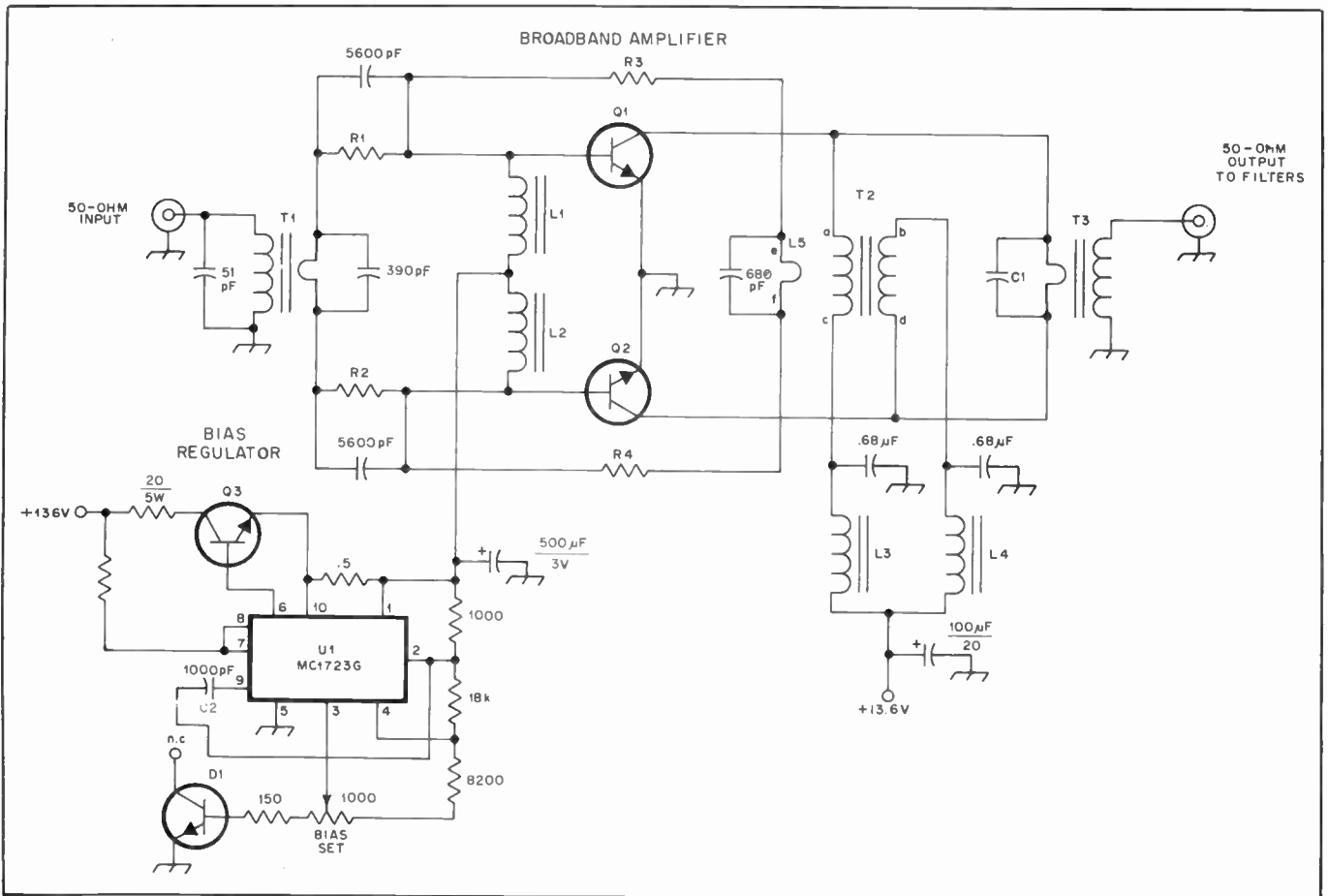


Fig. 65 — Circuit diagram of the 140-watt amplifier. All capacitors except part of C1, C2 and the electrolytic types are ceramic chips. Capacitors with values higher than 82 pF are Union Carbide type 1225 or Varadyne size 14. Others are type 1813 or size 18, respectively.

C1 — 1760 pF (two 470-pF chip capacitors in parallel with an 820-pF silver mica).

C2 — 1000-pF disk ceramic.

D1 — 2N5190 or equiv.

L1, L2 — Ferrite choke, Ferroxcube VK200 19/4B.

L3, L4 — Two Fair-Rite Products ferrite beads (2673021801 or equiv.) on no. 16 wire.

L5 — 1 turn through toroid of T2.

Q1, Q2 — MRF454.

Q3 — 2N5989 or equiv.

R1, R2 — Two 3.6 ohm, 1/2 W, in parallel.

R3, R4 — Two 5.6 ohm, 1/2 W, in parallel.

T1 — Primary: 3 turns no. 22 insulated wire.

Secondary: Braid or tubing loop. Core material: Stackpole 57-1845-24B, Fair-Rite Products 2873000201 or two Fair-Rite Products 0.375-inch OD  $\times$  0.2-inch ID  $\times$  0.4 inch (9.5  $\times$  5.1  $\times$  10.2 mm), Material-77 beads for type A (Fig. 66A) transformer.

T2 — 6 turns no. 18 enameled wire, bifilar wound. Ferrite core: Stackpole 57-9322, Indiana General F627-8 Q1 or equiv.

T3 — Primary: Braid or tubing loop. Secondary: 4 turns no. 18 insulated wire. Core material: Two Stackpole 57-3238 ferrite sleeves (7D material) or a number of toroids with similar magnetic characteristics and 0.175-inch sq. (113-mm sq.) total cross-sectional area.

U1 — Motorola MC1723G or equiv.

indicating device is in the feed line, maximum power should be observed at minimum plate current. Connecting the antenna in place of the dummy load should only require a small amount of retuning. Under operating conditions, 1.5 mA of grid current is optimum.

### A 140-W Solid-State Linear Amplifier

Solid-state technology has progressed to the point where devices capable of producing up to 100-watts output in the hf range are available at reasonable cost. This unit, designed by K7ES, applies the aforementioned technology to a broadband linear-amplifier design. Power output is 140 watts from 1.6 to 30 MHz. The amplifier described here originally appeared in *QST* for June and July 1977.

### The Circuit

The MRF454 transistor is specified for a continuous power output of 70 watts.

The maximum continuous current allowable is 15A. Maximum dissipation is limited to 250 watts. The minimum recommended collector idling current is 100 mA per device.

Fig. 65 shows the basic circuit. The bias supply uses active components rather than the common diode clamping scheme. Some advantages of this system are line-voltage regulation capability, low standby current, and a wide range of voltage adjustment. With the component values shown the bias is adjustable from 0.5 to 0.9 volt. The 0.5-ohm resistor between pins 1 and 10 of the MC1723 sets the current-limiting point of the chip at 1.35A. Temperature-compensating diode D1 is added for bias tracking as the power devices heat up. This circuit prevents thermal runaway. The base-emitter junction of a 2N5190 is used as this diode. Physical dimensions of the 2N5190 allow it to be used as the center standoff post of

the circuit board, ensuring adequate thermal bonding of the diode junction to the heat sink.

Device input impedances vary across the frequency range this amplifier is designed for. An input frequency-correction network is employed to give a gain flatness response of better than 1 dB across the band. R1, R2 and the associated 5600-pF shunt capacitors comprise the input-correction network. With the negative feedback applied via R3 and R4 through L5, the equivalent of an attenuator is formed with frequency-sensitive characteristics. At 30 MHz the input power loss is 1 to 2 dB, increasing to 10 to 12 dB at 1.6 MHz. The gain variation of the rf transistors is the reciprocal of this, resulting in a gain flatness of approximately 1 dB. Input VSWR is better than 1.75 across the band.

The input transformer, T1, and the output transformer, T3, are of the same

type. The low-impedance windings consist of two pieces of metal tubing which are shorted electrically at one end — the opposite ends being the connections of the windings (Fig. 66). The multitrans, high-impedance windings are wound through the tubing so that the low- and high-impedance winding connections are at opposite ends of the transformer. Alternatively, copper braid can be substituted for the metal tubing. The braid can be taken from coaxial cable of the proper diameter. This is exemplified in Fig. 66B.

The primary and secondary coupling coefficient is determined by the length-to-diameter ratio of the metal tubing or braid, plus the gauge and insulation thickness of the wire used for the high-impedance winding. A high coupling

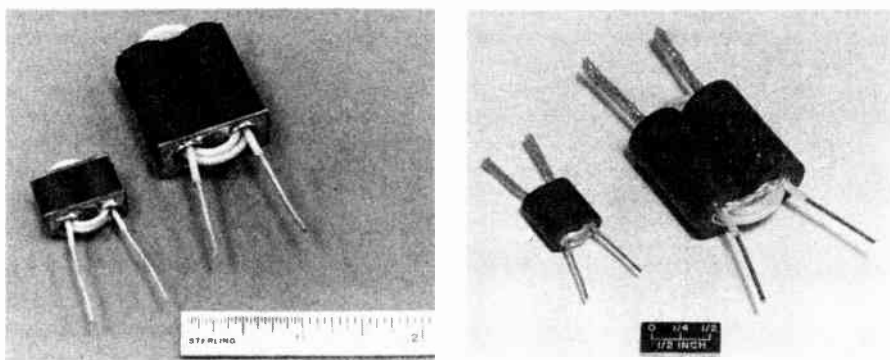


Fig. 66 — Shown at A and B are the two methods of constructing the transformers as outlined in the text. At A the one-turn loop is made from brass tubing and at B a piece of coaxial cable braid is used for the loop.

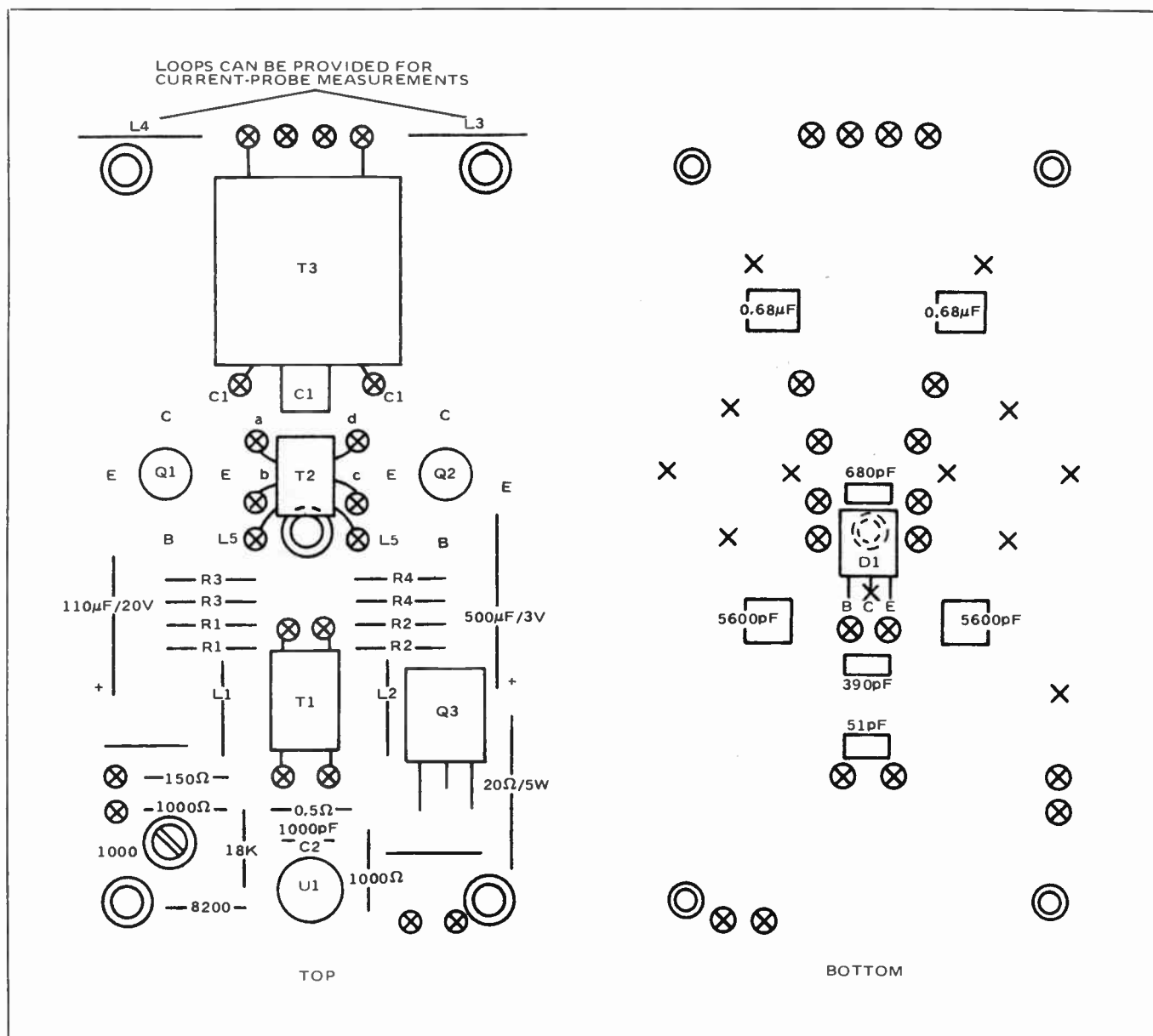


Fig. 67 — Actual-size layouts for the amplifier. Gray areas represent unetched copper. The pattern at the left is for the top side of the board and the one at the right for the bottom of the board.

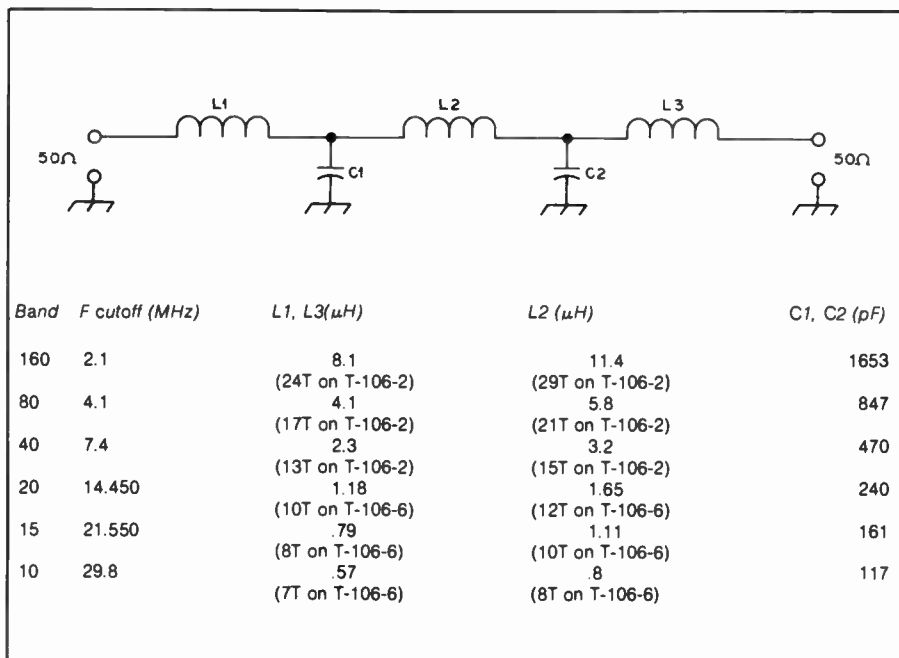


Fig. 68 — This table shows the values for five-pole Chebyshev filters suitable for use with the amplifier. Each coil is wound with no. 18 enameled wire on the core specified. The closest standard capacitor values to those given in the table should be used.

coefficient is necessary for good high-frequency response. Both transformers are loaded with ferrite material to provide sufficient low-frequency inductance.

The collector choke (T2) provides an artificial center-tap for T3. This produces even-harmonic cancellation. Additionally, T2 is a low-impedance point that supplies negative feedback voltage through a separate one-turn winding. The characteristic impedance of ac and bd (windings on T2) should be approximately equal to the collector-to-collector impedance of Q1 and Q2, but it is not critical. For physical convenience a bifilar winding is used. The center-tap of T2 is really bc, but for stabilization purposes, b and c are separated by rf chokes which are bypassed individually.

### Construction

A scale pc-board template is shown in Fig. 67. Double-sided board is used, and patterns are shown for each side of the board.

All parts are mounted on the circuit board. The MRF454s are soldered to the board, but the flanges are bolted tightly to the heat sink. Apply a thin layer of silicone grease to Q1, Q2 and D1 where they will contact the heat sink. This aids in efficient heat transfer. The board is attached to the heat sink by means of five screws. They are tapped into the heat sink: Four are at the board corners, and the fifth goes through the board, through D1, and into the heat sink.

A large heat sink is required for proper dissipation of heat. A nine-inch (229-mm) length of Thermalloy 6153 or a seven-inch (178-mm) length of Aavid Engineering 60140 extrusion is suitable for 100-percent

duty cycle operation (such as RTTY or SSTV operation).

### Tune Up and Operation

Since this is a broadband amplifier, no tuning adjustments are necessary. One need only set the bias control so that the amplifier draws 200 mA of quiescent current. A regulated power supply capable of delivering 13.6 volts dc at 25 A is required for amplifier operation.

If direct operation into an antenna is expected, filtering of the output is necessary to meet FCC regulations for spectral purity. The filters shown in Fig. 68 will provide more than sufficient harmonic attenuation with less than 1 dB of loss at the operating frequency.

Collector efficiency is in the vicinity of 50 percent. IMD products are typically 32 to 34 dB below PEP. Power gain is approximately 15 dB, which means that approximately 5 watts will drive the amplifier to the rated output of 140 watts. The spectral displays for harmonics and IMD are shown in Fig. 69.

### The Novice "1/4 Gallon"

Most Novice class licensees own transmitters that are not capable of running the maximum legal-power input for that class license — 250 watts. This amplifier was designed primarily with this in mind. Approximately 25 watts of power are required to drive the amplifier to 165-watts output on 80 meters. If a 75-watt transmitter is used to drive the amplifier, the transmitter output should be reduced to a level just sufficient to drive the amplifier to its full-power input. This can usually be accomplished by lowering the drive

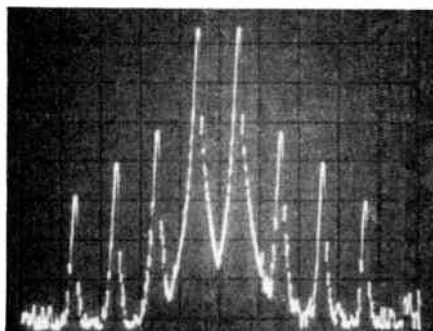
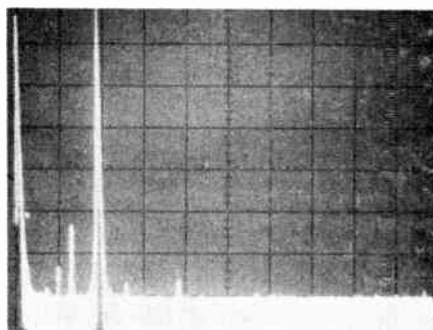


Fig. 69 — Spectral photographs of the output from the 140-watt amplifier. The display at the top was taken with the amplifier operating on the 80-meter band. At the bottom is a close in look at the IMD products generated by the amplifier. Third-order products are down some 32 to 34 dB below PEP.

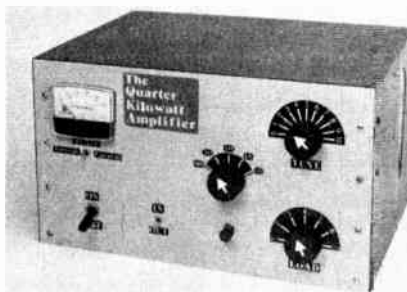


Fig. 70 — The completed quarter-kilowatt amplifier.

to the transmitter output stage and re-loading.

### The Circuit

The main ingredient in this amplifier is a pair of 6KD6 television-sweep tubes (see Fig. 71). Although the tubes are rated at 33 watts of plate dissipation, they can handle temporary overloads of at least 100 watts without sustaining permanent damage. These tubes were chosen over 811s or 572Bs because they can often be "liberated" from old television sets or can be purchased new from most TV service shops.

D11, an 11-volt Zener diode, provides cathode bias for the tubes and establishes





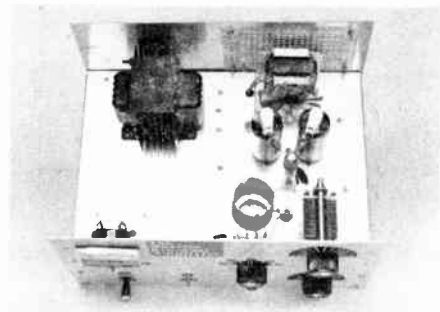


Fig. 72 — An inside view of the amplifier. C1 is located at the lower right. C2 is mounted below the chassis and is connected to L1 using a feedthrough insulator.

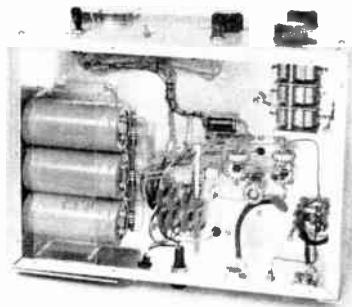


Fig. 73 — Underside of the amplifier. Component layout is not particularly critical.

build as possible. The only critical values are those for the amplifier plate-tank circuitry. Reasonable parts substitutions elsewhere in the circuit should have little or no effect on the performance of the amplifier. For example, if 330- $\mu$ F filter capacitors are not available, 250- $\mu$  or 300- $\mu$ F units could be substituted. They should be rated at 450 volts or greater to provide a margin of safety. If a 0.001- $\mu$ F plate-blocking capacitor is not on hand and a 0.005- $\mu$ F unit is, use it. Builders often attempt to match parts exactly to the type specified in a schematic or parts list. A few projects are this critical in nature, but the majority, including this one, are not.

The transformer used in this amplifier was garnered from an old TV set. Any hefty transformer with a high-voltage secondary between 550 and 700 volts should be adequate. Most of these transformers will have multiple low-voltage secondaries suitable for the tube filaments and relay requirements.

The chassis used to house the amplifier happened to be on hand and measured 3  $\times$  10  $\times$  14 inches (76  $\times$  254  $\times$  356 mm). No doubt the amplifier could be constructed on a smaller chassis. The beginner is cautioned not to attempt to squeeze too much in too small a space.

The front, rear, side and top panels are constructed from sheet aluminum and help to keep the amplifier "rf tight." Any air-flow openings are "screened" with perforated aluminum stock. The front-panel meter opening is shielded by means of an aluminum enclosure (a small

Minibox would serve quite nicely). The on-off power switch, pilot light, meter switch, band switch, tuning and loading controls, and amplifier in-out switch are all located on the front panel. On the rear panel are the amplifier input and output connections, relay control jack and the fuse holder. As can be seen from the photograph, a fan is located near the tube envelopes to keep them cool during operation.

### Setup and Operation

Attach the transmitter output to the amplifier input connection. Then, join the output of the amplifier to a 50-ohm noninductive dummy load. Connect the relay control line to the transmitter or external antenna-relay contacts. Then plug in the line cord and turn the power switch to the ON position. With the meter switch in the PLATE VOLTS position, the reading on the meter should be approximately 425, which corresponds to 850 volts. If the power transformer used has a high-voltage secondary other than 600 volts, the reading will vary accordingly. If no plate voltage is indicated by the meter, check your wiring for possible errors or defective components. Next, place the meter in the PLATE CURRENT position, the band switch to the 80-meter band, and apply a small amount of drive to the amplifier — enough to make the meter read 50 mA (5 on the meter scale). With the plate-tank loading control fully meshed, quickly adjust the plate tuning capacitor for a dip in plate current. Apply more drive (enough to make the meter read 100 mA), advance the loading control approximately one-eighth turn and readjust the plate tuning control for a dip in the plate current. Continue this procedure until the plate-current maximum dip is approximately 300 mA. The final value of plate current at which the amplifier should be run depends on what the plate voltage is under load. In our case this value was 800 volts. Therefore, the amount of current corresponding to 250 watts input is approximately 310 mA. ( $I = P/E$ ,  $I = 250/800$ ,  $I = 312.5$  mA.) The same tune-up procedure should be followed for each of the other bands. The amplifier efficiency on 80 through 20 meters is approximately 65 percent, dropping to 60 percent on 15 meters. On 10 meters, efficiency is slightly less than 50 percent. Poor efficiency on the higher bands is caused primarily by the high-output capacitance characteristics of sweep tubes.

### A "Universal" Three-Band Linear Amplifier

The cost for a project can be as important a goal as ultimate performance. The challenge of finding surplus or used electronic components for a project may be even greater than the challenge of actual construction. This amplifier was designed to make use of the many tubes

available through surplus channels and flea markets for bargain prices. Some commercial users employ these tubes and remove them from service after a prescribed period as part of preventive maintenance. These "pulls" still offer thousands of hours of satisfactory use in amateur equipment.

This amplifier is capable of running one kilowatt of dc input on the 160-, 80- and 40-meter amateur bands. The high-frequency usefulness of the 833A in the amplifier shown limits the usage to those three bands. Pi-network values are given for various surplus tubes: 4-400A, 4-250A, 304TH and 833A (Table 6).

### The Circuit

The power tube is used in the grounded-cathode configuration (Fig. 75). If the tube to be used is a tetrode, the screen and grid should be tied together to simulate a triode. The 0.01- $\mu$ F disk capacitors from each cathode terminal to ground provide a low-impedance rf path, effectively bypassing the cathode to ground. Grid voltage is developed across a low resistance, R1, which coincidentally maintains a constant load impedance for the exciter and prevents instability.

The output circuit is a pi-network. The values for the plate-tank components

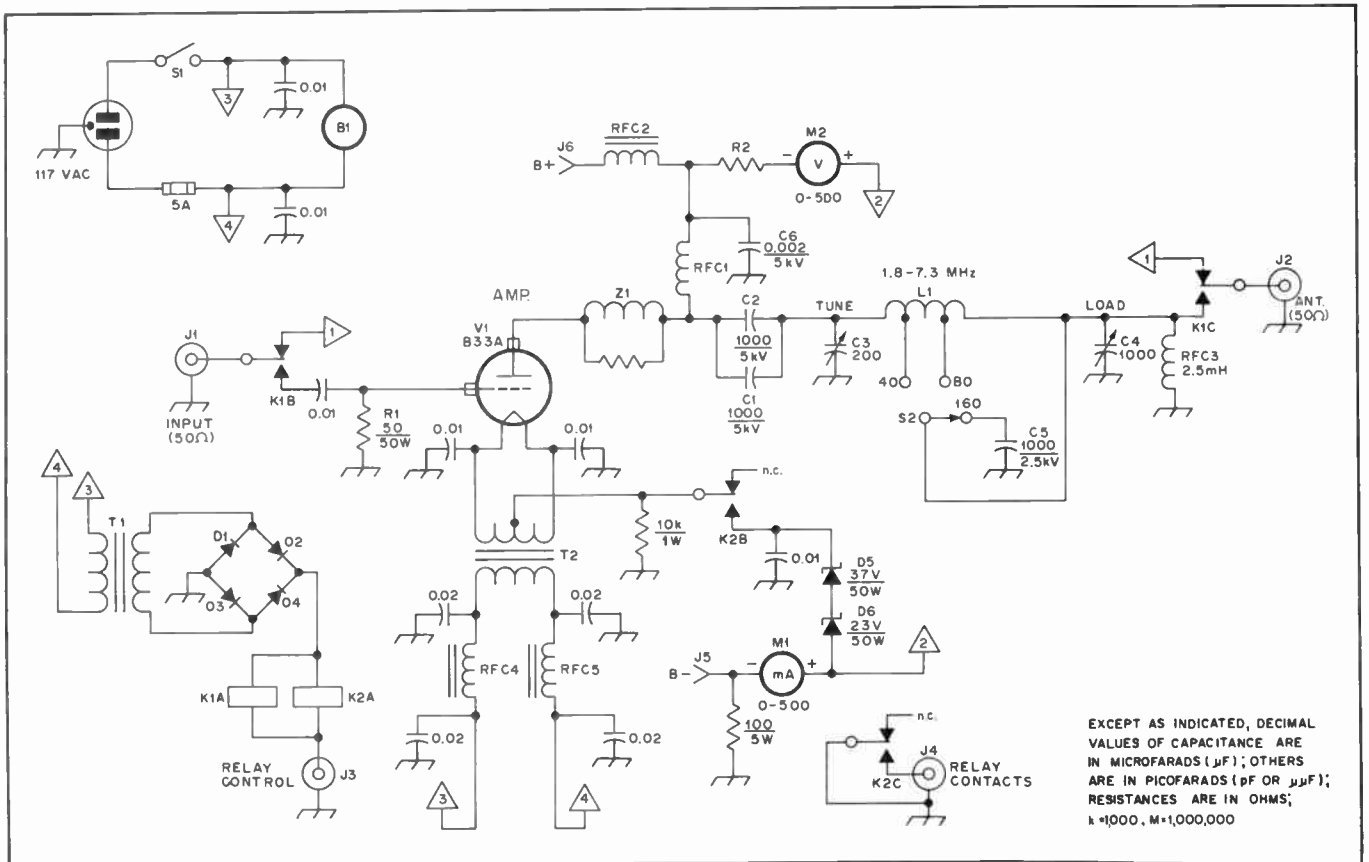


Fig. 74 — Front panel of the amplifier.

Table 6

160 meters			
Plate Voltage	C3	C4	L1
2000	490 pF	2987 pF	17.83 $\mu$ H
2500	305 pF	2098 pF	27.59 $\mu$ H
3000	222 pF	1676 pF	37.29 $\mu$ H
3500	193 pF	1676 pF	42.74 $\mu$ H
80 meters			
2000	252 pF	1536 pF	9.17 $\mu$ H
2500	157 pF	1079 pF	14.19 $\mu$ H
3000	114 pF	862 pF	19.18 $\mu$ H
3500	99 pF	862 pF	21.96 $\mu$ H
40 meters			
2000	114 pF	670 pF	5.03 $\mu$ H
2500	71 pF	451 pF	7.77 $\mu$ H
3000	52 pF	341 pF	10.48 $\mu$ H
3500	45 pF	341 pF	12.02 $\mu$ H

These values normalized for a dc power input of 1 KW



EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu\text{F}$ ); OTHERS ARE IN PICO FARADS ( $\text{pF}$  OR  $\mu\mu\text{F}$ ); RESISTANCES ARE IN OHMS; k=1,000, M=1,000,000

Fig. 75 — Schematic diagram of the three-band amplifier.

- B1 — Muffin fan, 80 to 100 CFM suitable, 117 VAC.
- C1, C2 — 1000-pF transmitting capacitor, 5000 volts (Centralab 858 series).
- C3 — Transmitting air variable, 200 pF, E. F. Johnson 154-0016-001 or equiv.
- C4 — Transmitting air variable, 1000 pF Millen 16999 or equiv.
- C5 — 1000-pF transmitting capacitor, 5000 volts, Centralab 858 series.
- C6 — 0.002- $\mu\text{F}$  transmitting capacitor, 5000 volts, Centralab 858 series.
- D1-D4, incl. — 100 PRV, 1 A.
- D5 — Zener diode, 37V, 50 W.
- D6 — Zener diode, 23V, 50 W.
- J1, J2 — SO-239 chassis-mounted coaxial

- connector.
- J3, J4 — Phono jack, panel mount.
- J5, J6 — High-voltage connection, Millen 37001.
- K1 — Dpdt, 5-A contacts. Coil voltage is 24 dc.
- K2 — Dpdt, 2-A contacts. Coil voltage is 24 dc.
- L1 — Surplus E. F. Johnson inductor in this model. Use Table 6 values. Copper tubing (0.25 inch dia.) suitable.
- M1 — 500 mA dc.
- M2 — 500 V dc.
- R1 — 50-ohm noninductive resistor, 50 W, Sage 3550M or similar.
- R2 — Meter multiplier resistor made from five 1.8 M $\Omega$ , 1-watt in series.
- RFC1 — See text and Fig. 76.
- RFC2 — 40 turns no. 24 enam. on T-80-2 Toroid

- core.
- RFC3 — 2.5-mH choke (Millen 34300-2500 or equivalent).
- RFC4, RFC5 — 6 turns no. 18 enam. on FT-37-43 Toroid core.
- S1 — Spst toggle switch.
- S2 — High voltage, single-pole, three-position rotary switch, ceramic insulation (such as from surplus BC-191 or -375E transmitter).
- T1 — 117-volt primary; secondary 24 V ac at 1.2 A.
- T2 — 117-volt primary; secondary 10 V ct at 10 A. Hammond 167510.
- V1 — 833A, see text.
- Z1 — Parasitic suppressor. 4 turns, no. 16 enam. wound around three 150-ohm, 1-watt resistors connected in parallel.

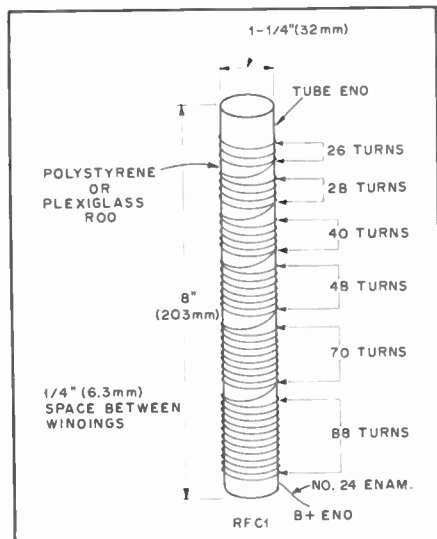


Fig. 76 — RFC1 is wound on 1-1/4 inch (32-mm) diameter polystyrene rod as depicted.

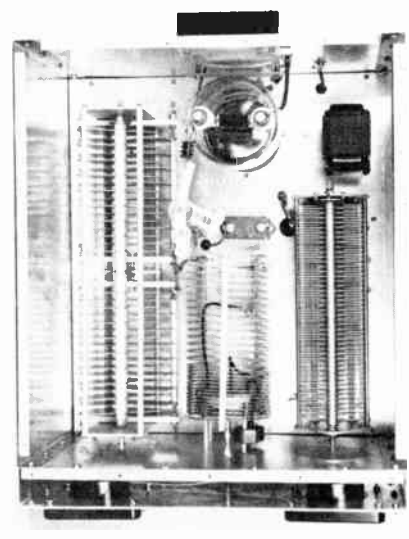


Fig. 77 — Interior view of the three-band amplifier. The band switch is mounted to the front panel inside one end of the tank coil.



Fig. 78 — External view of the 8873 amplifier and power supply.

depend on the plate load impedance of the tube. This is a function of the plate voltage and the plate current. To allow the builder flexibility in power-supply requirements, Table 6 lists the pi-network values needed for different plate voltages. The computed values assume the use of appropriate plate current for 1 kilowatt input at the plate voltage given. Observe the maximum tube ratings when choosing a power-supply voltage. High voltage goes to the plate through

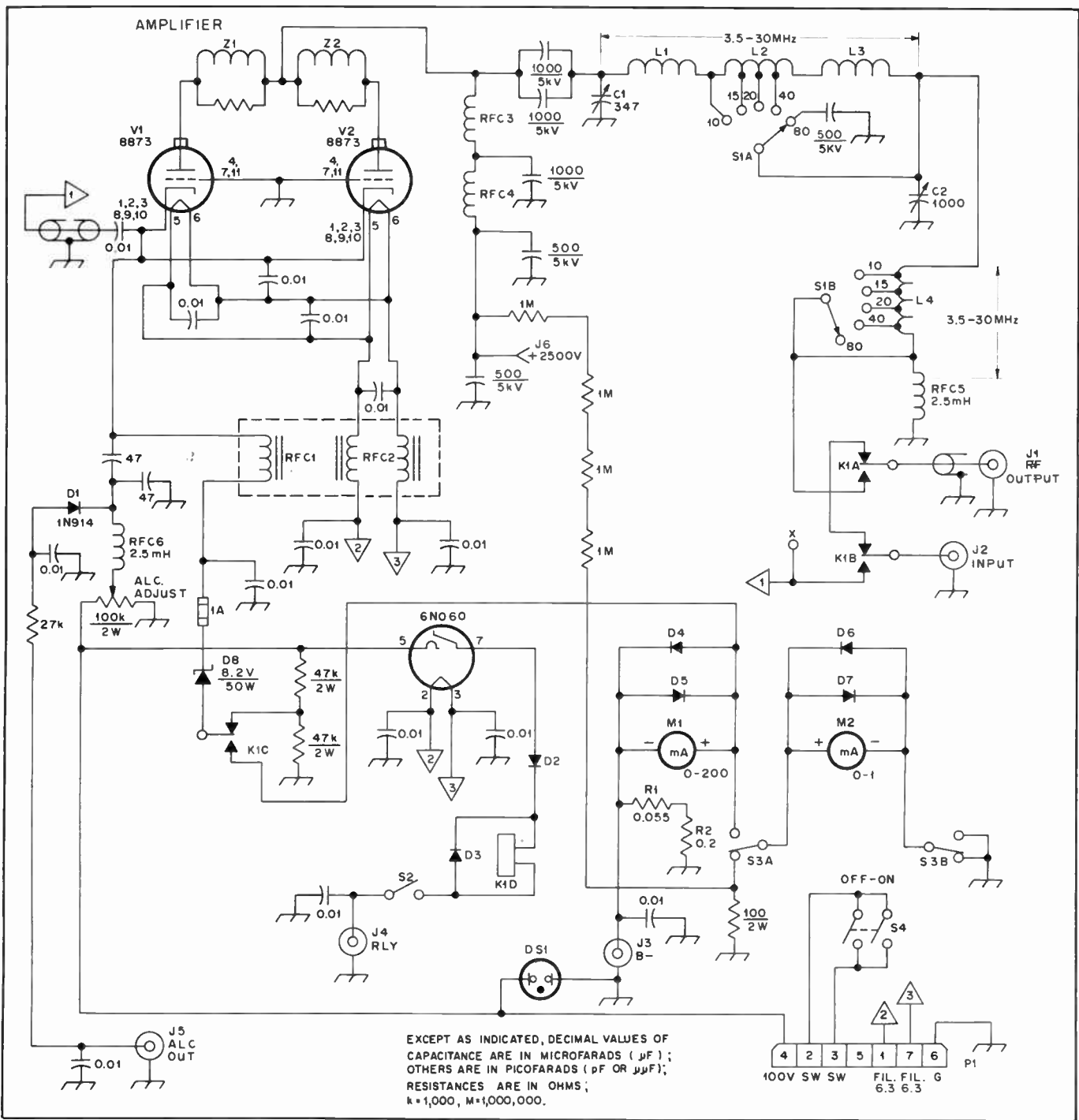


Fig. 79 — Circuit diagram for the 8873 conduction-cooled amplifier. Component designations not listed below are for text reference. RFC1 and RFC2 are wound on the same ferrite rod in the same direction; three wires are wound together (Amidon MU-125 kit). Tube sockets for V1 and V2 are E. F. Johnson 124-0311-100. The thermal links are available from Eimac with the tubes. The heat sink is part number 2559-080-A000 from Astrodyne Inc., 353 Middlesex Ave., Wilmington, MA 01887.

- C1 — Transmitting air variable, 347 pF, E. F. Johnson 154-0010-001.
- C2 — Transmitting air variable, 1000 pF, E. F. Johnson 154-30.
- D2 - D7, incl. — 1000 PRV, 2.5 A, Motorola HEP170.
- D8 — 8.2-V, 50-W Zener diodes.
- J1 — S0-239 chassis mounted coaxial connector.
- J3, J4, J5 — Phono jack, panel mount.
- J6 — High-voltage connection, Millen 37001.
- K1 — Enclosed, three-pole relay, 110-volt dc coil, Potter and Brumfield KUP14D15.
- L1 — 4-3/4 turns of 1/4-inch (6.3-mm) copper tubing, 1-3/4-inch ID, 2-1/4 inches long.
- L2 — 12-1/2 turns, 1/4-inch (6.3-mm) copper tubing, 2-3/4-inch (70-mm) ID, tap at one turn

- from connection point with L1, 2-1/2 inches (63.5-mm) for 20 meters, 7-3/4 turns for 40 meters.
- L3 — 11-1/2 turns, 2-inch (51-mm) diameter, 6 tpi, Barker and Williamson 3025.
- L4 — 10 turns, 2-inch (51-mm) diameter, 6tpi, with taps at 3 turns for 10 meters, 3-1/2 turns for 15 meters, 4-3/4 turns for 20 meters, 6-3/4 turns for 40 meters; all taps made from junction of L3, Barker and Williamson 3025.
- M1 — 200 mA full scale, 0.5-ohm internal resistance Simpson Electric Designer Series model 523.
- M2 — 1 mA full scale, 43 ohms internal resistance (Simpson Electric, same series as M1).
- R1 — Meter shunt 0.05555 ohm constructed

- from 3.375 feet of no. 22 enam. wire wound over the body of any 2-watt resistor higher than 100 ohms in value.
- R2 — Meter shunt, 0.2 ohm made from five 1-ohm, 1-watt resistors connected in parallel.
- RFC1, RFC5, RFC6 — 2.5 mH, Millen 34300-2500.
- RFC3 — Rf choke, Barker and Williamson Model 800 with 10 turns removed from the bottom end.
- RFC4 — 22 $\mu\text{H}$ , Millen 34300.
- S1 — High-voltage band-selector style, double pole, six position, James Millen 51001 style.
- Z1, Z2 — 2 turns 3/8-inch (9.5-mm) wide copper strap wound over three 100-ohm, 2-watt resistors connected in parallel.



RFC1. The choke is wound in such a way as to reduce its distributed capacitance over a conventionally wound choke. RFC3 prevents high voltage from appearing on the antenna should the plate-blocking capacitors (C1 and C2) short; it provides a dc path to ground, thereby blowing the power-supply fuse.

Operating bias for the tube sets the operation to Class AB2. D5 and D6 raise the cathode potential above ground to establish the appropriate idling current of the tube. When in the standby mode, relay contacts switch to a different bias level, reducing plate current to zero.

### Construction

Construction is straightforward. While the layout shown here proved ideal for the components on hand, many builders will use parts other than the ones shown. Physical constraints may require different layout arrangements. The main considerations are to keep lead lengths to a minimum, and to ensure adequate grounds where needed.

A homemade sealed box encloses the circuitry. Three potential problem areas dictate that in this, and all rf power amplifiers, a shielded box is necessary. Safety considerations, both due to high dc and high rf voltages, RFI reduction and adequate air cooling of the tube all necessitate a sealed box. All metal-to-metal bond areas should be cleaned carefully to guarantee good electrical contact. An abundance of fastening screws hold these seams together, further "RFI-proofing" the box. Air is blown across the tube by means of a muffin fan. Plenty of cooling air not only stabilizes the tuning of the amplifier but also lengthens tube life.

Many variations in switching, metering and power supplies are possible with a unit such as this. The methods shown here are intended to be *examples* of the various possibilities. Parts availability and in-

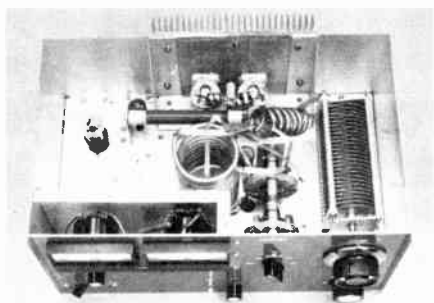


Fig. 80 — Top view of the 80-10-meter conduction-cooled amplifier. The chassis is 17 × 12 × 3 inches (432 × 305 × 76-mm) and is totally enclosed in a shield. A separate partition was fabricated to prevent rf leakage through the meter holes in the front panel. An old National Radio Company vernier dial is used in conjunction with the plate tuning capacitor to provide ease of adjustment (especially on 10 meters). The position of the dial for each band is marked on the dial skirt with a black pen and india ink.

dividual desires of the builder dictate the final design.

### Tune-up and Operation

Because of the expected variations between different amplifiers, there are no hard and fast rules for tune-up. For initial tune-up less than full plate voltage is recommended. This permits a greater safety margin (both for the amplifier and the operator) if unexpected events occur. Increase drive slowly while making adjustments, this again providing a safety margin. *Remember, hazardous voltages are present in this amplifier, and these should be respected at all times.*

A wattmeter is helpful during tune-up. A goal of maximum output power consistent with high efficiency should be sought. Efficiency on the order of 55 to 65 percent can be expected. In order to increase tube longevity, the manufacturer's maximum ratings should never be exceeded.

### A Conduction-Cooled 2-Kilowatt Amplifier

One of the major concerns when dealing with high-power amplifiers is heat and how to reduce it. The usual method has been to use a large fan or blower, but this solution is generally noisy. By using the principles of heat transfer, a noiseless amplifier can be made with the use of an adequate heat sink and conduction-cooled tubes.

The amplifier shown in the photographs and schematically in Fig. 79 uses a pair of 8873 conduction-cooled triode tubes. The circuit configuration is grounded grid and uses no tuned-input tank components. When properly adjusted, the amplifier is capable of IMD characteristics which are better than can be achieved by a typical exciter, therefore the added complexity of band switching a tuned-input circuit was deemed unnecessary.

### Construction

Building an amplifier such as this is often an exercise in adapting readily available components to a published circuit. For this reason, a blow-by-blow description of this phase of the project will not be given. An effort was made, however, to use parts which are available generally, and should the builder desire, this model could be copied verbatim.

The most difficult constructional problem is that of aligning the tube sockets correctly. It is imperative that the sockets be aligned so that when the tubes are mounted in place, the flat surfaces of the anodes fit smoothly and snugly against the thermal-link heat-transfer material. Any misalignment here could destroy the tubes (or tube) the first time full power is applied. The mounting holes for the tube sockets are enlarged to allow final positioning after the tubes are "socked" in place with the clamping hardware. Pres-



Fig. 81 — Top view of the power supply showing the technique for mounting the filter-capacitor bank. The diodes are mounted on a printed-circuit board which is fastened to the rear of the cabinet with cone insulators and suitable hardware.

sure must be applied to the anodes so that they are always snug against the thermal link. The hardware used to perform this function must be nonconducting material capable of withstanding as much as 250°C (482°F). The pressure bracket used here was fabricated from several Millen jack-bar strips (metal clips removed) mounted in back-to-back fashion. The entire assembly is held in place by means of a long piece of no. 10 threaded brass rod which passes through a small hole in the center of the heat sink. An attempt to give meaningful comments about how tight the tubes should be pressured to the copper and aluminum sink will not be given. Suffice it to say that the tubes should fit flat and snugly against the thermal hardware. The heat sink was purchased from Thermalloy and is connected to a 1/4-inch (6.3-mm) thick piece of ordinary copper plate. The total cost for the copper and the aluminum sink is somewhat more than the price of a good centrifugal blower (\$30) but the savings offered by not having to purchase special tube sockets and glass chimneys overcomes the cost-differential.

The power supply is built on a separate chassis because the plate transformer is bulky and cumbersome. A special transformer was designed for this amplifier by Hammond Transformer Co. Ltd., of Guelph, Ontario, Canada. The transformer contains two windings, one is for the plate supply to be used in a voltage-doubler circuit and the other is for the tube filaments. The power supply produces 2200 volts under a load of 500 mA, and is rated for 2000 watts. The Hammond part number is given in Fig. 82. All of the interconnections for power-supply control and the operating voltages needed by the amplifier are



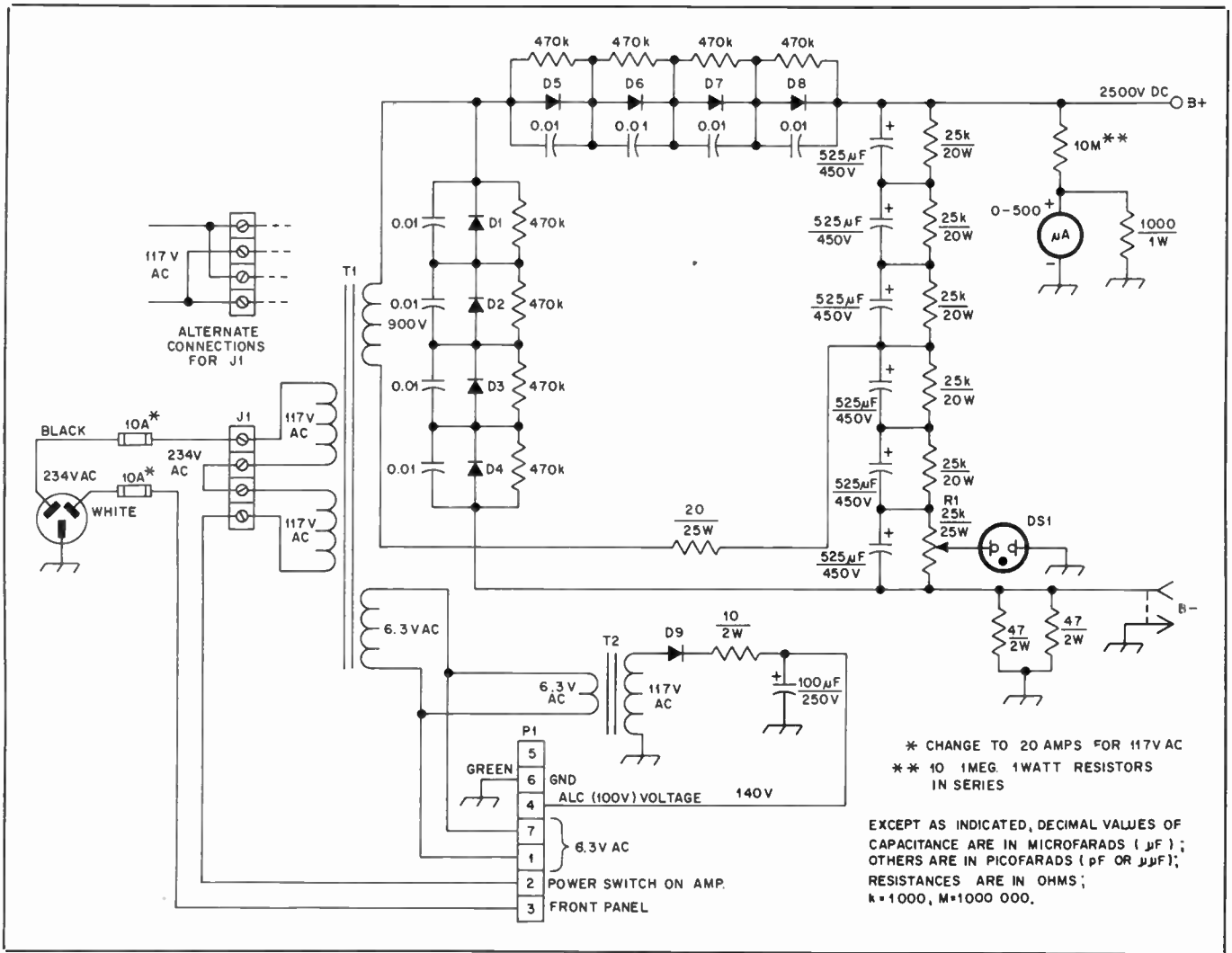


Fig. 82 — Circuit diagram for the power supply. The power transformer is available from Hammond; type no. 101165. D1 through D9 are 2.5 A, 1000 PRV; see Fig. 79 for suitable part number. T2 is Stancor part number P-8190 and is rated for 6.3 volts at 1.2 amperes. D10 is a 117-volt neon pilot lamp assembly. The tap at R1 should be set for 5000 ohms to the B minus lead. Adjustments to this tap cannot be made while voltage is applied to the power supply. If the pilot lamp does not glow properly, remove the ac cord, allow suitable time for the high-voltage to bleed to zero, and apply a screwdriver between the B-line and ground before making any adjustments!

carried by a seven-conductor cable. This excludes the B plus, however, which is connected between the units by means of a piece of test-probe wire (5-kV rating) with Millen high-voltage connectors mounted at both ends. The seven-conductor cable is made from several pieces of two-conductor household wire (no. 10) available at most hardware stores. Since the main power switch is mounted on the front panel of the amplifier, the power supply may be placed in some remote position, out of the way from the operator (not a bad idea!). A high-voltage meter was included with the power supply so that it could be used with other amplifiers. It serves no purpose with this system. The main amplifier deck has provisions for monitoring the plate voltage.

A conventional household light switch may be used for S4. If the switch is to be mounted horizontally, be sure to use a contactor device and not a mercury type (which operates in a vertical position only). A double-pole switch was used with

both poles connected in parallel. The rating is 220 volts at 10 amperes per section.

### The RF Deck

The two sections of the pi-L network are isolated from each other by placing one of them under the chassis. Although not shown in the photograph, a shield was added to prevent rf energy from entering the control section underneath the chassis. The shield divides the chassis between the tube sockets and the inductors. The loading capacitor is mounted directly beneath the plate-tuning capacitor. This scheme provides an excellent mechanical arrangement as well as a neat front-panel layout.

The 8873s require a 60-second warmup time, and accordingly, a one-minute time-delay circuit is included in the design. The amplifier IN/OUT switch is independent of the main power switch and the time delay. Once the delay circuit "times out," the amplifier may be placed

in or out of the line to the antenna, whenever desired. A safety problem exists here: There is no large blower running, and there are no brightly illuminated tubes to warn the operator that the amplifier is turned on. Except for the pilot lamp on the front panel, one might be fooled into believing the amplifier is turned off! And if the pilot lamp should burn out, there is *absolutely* no way to tell if the power is turned on (with the resultant high voltage at the anodes of the 8873s). *Beware!*

### Operation

Tuning a pi-L-output circuit is somewhat different from tuning a conventional pi-network because the grid current should be monitored closely. Grid current depends on two items — drive power and amplifier loading. The procedure found to be most effective is to tune for maximum power output with the loading sufficiently heavy to keep the grid current below the maximum level while adjusting the drive

power for the proper amount of plate current. The plate current for cw operation should be 450 mA and approximately 900 mA under single-tone tuning conditions for ssb. This presents a problem since it is not legal to operate under single-tone tuning conditions for ssb. Sixty watts of drive power will provide full input levels. For use with high-power exciter, see October 1973 *QST*.

### A 2-Kilowatt Amplifier Using the Eimac 8877 Triode

The 2-kilowatt amplifier shown here is designed for dependable service at the maximum legal power input allowed in the United States. The component ratings are generous and the construction is heavy duty. Since power-handling capability is determined typically by physical size, most of the components used here are large, and accordingly, a split arrangement has been employed allowing the placement of the power supply on a separate chassis from the amplifier compartment.

Another feature sets this amplifier apart from most others described in the literature; the air is exhausted from the top of the tube socket instead of the conventional pressurized chassis air-flow system.

#### The Circuit

The triode, a 3CX1500/8877, is connected in a grounded-grid configuration, which provides about the most simple layout possible (Fig. 84). The output tank circuit is a pi-network with vacuum-variable capacitors used for both input and output tuning. A 2.5-mH rf choke is connected between the output end of the tank and ground to prevent B+ from appearing at the antenna terminals should C1 develop a short.

A passive, untuned, capacitor-coupled circuit is used to apply rf-drive energy to the 8877 cathode. Since a moderate amount of bias is permitted, L1 is incorporated to provide isolation from rf to the bias-developing Zener diodes. The highest recommended bias voltage for use on ssb is 8.2, but for cw operation, where IMD is not relevant, 22 volts is developed which nearly places the tube at cutoff (zero no-signal plate current). A 10-k $\Omega$  resistor is included in series with the Zener-diode circuit to assure complete cutoff of the 8877, during receiving periods. It is switched out of the circuit during transmit periods by a set of contacts on K1.

Antenna transfer along with bias switching is accomplished with two relays. Sequencing can be an important factor since it is very undesirable to provide drive to the 8877, remove its bias, all before the output circuit relay has closed and stopped "bouncing." This is accomplished by the use of a vacuum relay shown as K2 in Fig. 84. K2 is many times faster in operation than K1 and accordingly, the

antenna is placed on the amplifier output circuit well ahead of drive arriving at the cathode of the 8877. Voltage to operate both relays is developed by T2. Since the relays are connected in a fashion to allow straight-through operation of an exciter or transceiver to the antenna in the de-energized position, interruption of the voltage from T2 during transmit periods with it is undesirable; to have the amplifier "on line" and developing power is all that need be done. S4 serves that function.

Metering of three operating conditions of the amplifier is accomplished with three meters instead of one or two. The purpose is first, to eliminate a switch for selection, and second, to provide continuous indication of the important parameters of the 8877. Of course, operator error is reduced since it is impossible to assume a meter is measuring one thing while a switch is selected for another. Both plate and grid current meters are direct-reading instruments — no shunts are needed. A string of resistors is used at R1 to multiply the scale of the 500- $\mu$ A meter to indicate zero through 5000 volts. R1 is constructed of 10 resistors, 1 watt in size and 1 M $\Omega$  in value. The purpose is to keep the applied voltage across each resistor below 600. A 1000-ohm resistor is included at the meter end of R1 to keep the voltage low should the meter winding become an open circuit.

Another feature of this particular amplifier is the use of a motorized Powerstat for control of the high-voltage circuit. The ability to select the operating plate voltage from the front panel of the amplifier is a feature desired by the builder of the project and need not be duplicated. If voltage control is not used, the power transformer used in the high-voltage power supply should be selected to provide about 3000 volts. This is a suitable compromise for efficient cw and ssb operation at the maximum power input levels. In actual operation, the amplifier shown in the photographs is used with 3400 volts during ssb operation and 2500 volts for cw conditions.

Several 50-ohm, 10-watt resistors have been placed at various points in the B- circuit, both in the amplifier-chassis compartment and on the power supply chassis. This prevents the B- lead from creeping above "almost ground" potential should a defect develop in the grid-current metering circuit. Also, included in the B+ lead is a 10-ohm resistor that will help prevent component damage should a direct short take place in the amplifier compartment.

#### Mechanical Construction

The split-chassis configuration offers several advantages. First, it allows the amplifier compartment to be somewhat more compact because the power supply can be located elsewhere. This consumes less space on the operating desk. It also



Fig. 83 — Front view of the 8877 amplifier. The non-sequential numbering of the band switch is discussed in the text. A switch is provided to allow the selection of proper bias for the mode in use at the time.

divides the weight into parts; the heavier section, the power supply, may be placed on the floor and equipped with wheels to give it mobility. The only disadvantage with having a two-chassis system comes when portability is desired.

The power supply has been assembled on an aluminum plate which is 1/4-inch (6.3-mm) thick. Casters are provided because the plate transformer itself weighs about 80 pounds (36.3 kg). The capacitor bank for filtering has also been mounted on the aluminum plate. A circuit board is used to interconnect the capacitors and is supported above the plate with ceramic pillar insulators. A screened covering is provided to keep unwanted objects from contacting the high-voltage system. The power supply relay (T3 primary connection) and the Powerstat have been assembled separately and may be interconnected to the power supply chassis plate via an interconnecting cable. Mounting both the plate transformer and the Powerstat on the same chassis would render it unmovable!

The power supply bleeder-resistor network must be placed in a position to allow air to flow past it and rise through the top screen cover. R2 and R3 each consist of six resistors (12 total) rated at 20 k $\Omega$  and 20 watts each. A similar bank of 12 capacitors connected in series constitutes the filter network. Each filter capacitor in the circuit has one of the bleeder resistors connected directly across it in order to assure equal voltage division. Each capacitor is rated at 200  $\mu$ F and 450 volts.

D5 and D6 consist of series diodes similar in hookup to the capacitor and resistor network described above. Each individual diode is rated at 1000 volts; the four series connected equal 4000 PRV. The current rating for each diode is two amperes.

No provisions have been made to operate this plate supply from a 117-volt ac source. Accordingly, if one wishes to have such capability, a suitable trans-

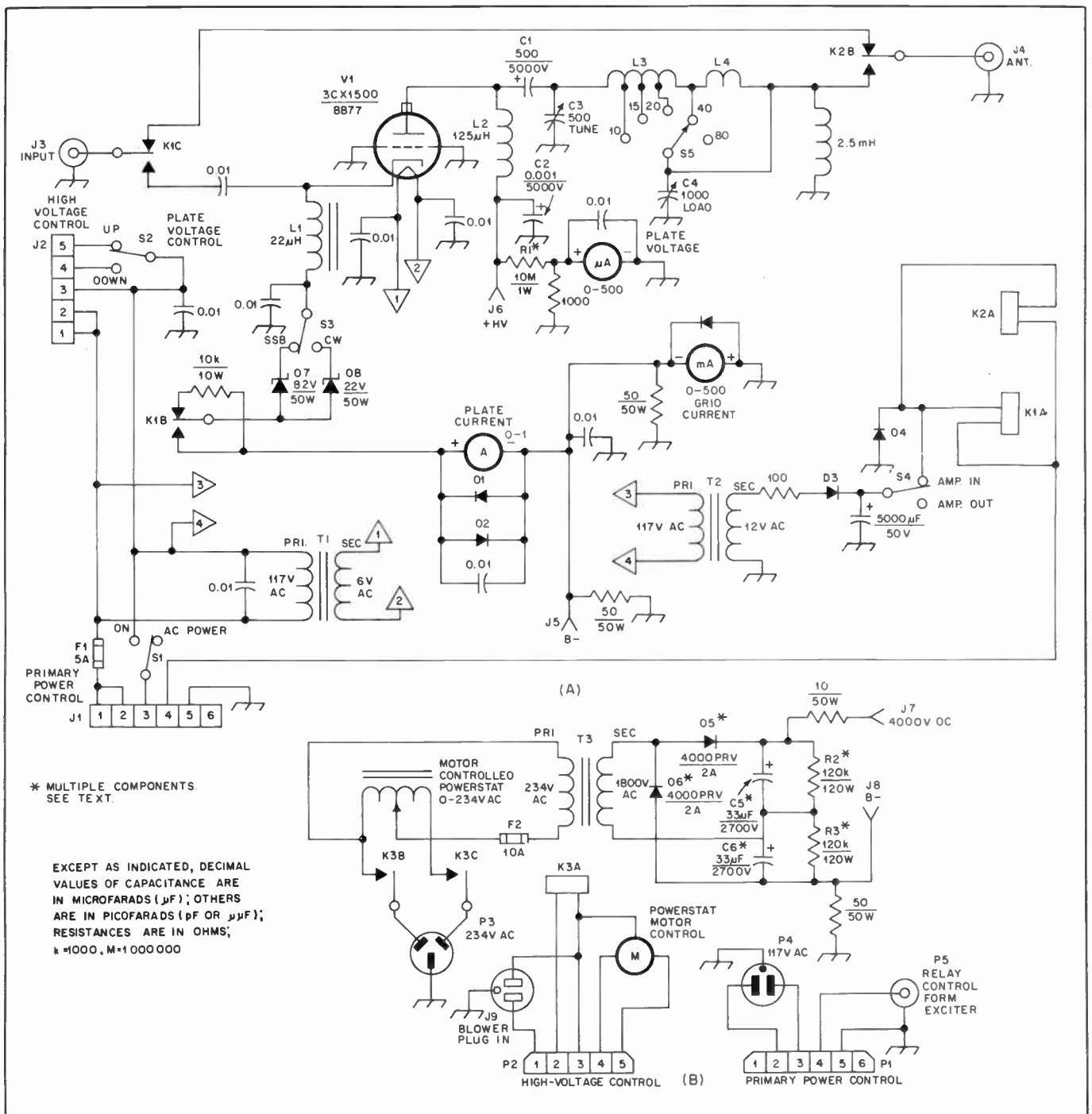


Fig. 84 — Circuit diagram for the 8877 2-kW amplifier. Component designations not listed below are for text reference only.

- C1 — 500-pF transmitting capacitor, 5000 volts Centralab 858 series.
- C2 — 0.001-μF transmitting capacitor, 5000 volts, Centralab 858 series.
- C3 — Vacuum variable, 500 pF maximum, 7500 volts.
- C4 — Vacuum variable, 1000 pF maximum, 5000 volts.
- C5, C6 — Six 200-μF units see text.
- K1 — Dpdt, 5-A contacts. Coil voltage is 12 volts dc.
- K2 — Vacuum relay, spst Torr Electronics TF1 or equiv.
- K3 — Power relay, 10-A contacts, 117-V ac coil.
- L1 — 25 turns wound on an Amidon T-50-2 toroid core.
- L2 — 125 μH, 2 A, Hammond Mfg.
- L3 — Strap-wound inductor, 12 πH total tapped at 2-1/2 turns for 10 meters, 3 turns for 15 meters, 5 turns for 20 meters and 14 turns for 40 meters, E. F. Johnson 232-626.
- L4 — 5 turns of 1/4-inch copper tubing wound the same diameter as L3.
- S1, S3, S4 — spst, 3 A, Radio Shack.
- S2 — spdt, 3 A with spring return to center off position, Radio Shack
- T1 — primary 117 V ac, secondary 5.0 V ac, 10 A, Hammond Transformer.
- T2 — primary 117 V ac, secondary 12 V ac at 3 A.
- T3 — plate transformer, 235-volt ac primary, 1770-volt (Hammond Transformer 105677).

former must be substituted for T3 shown in Fig. 84. It should be pointed out, however, that the plate supply is the only portion to operate with a 235-volt line. The amplifier filament circuit and voltage-source circuits for the relays along with

the blower all operate from 117-V ac. The amplifier portion of this system is constructed on an aluminum chassis that is 14 × 17 × 4 inches (356 × 432 × 102 mm). The 14-inch (356-mm) dimension was chosen as the front-panel size to conserve

space on the operating table. A bottom cover for the chassis is cut from a large section of aluminum perforated stock while the area above the chassis top is completely sealed and made airtight. The amplifier top cover is solid stock but has a



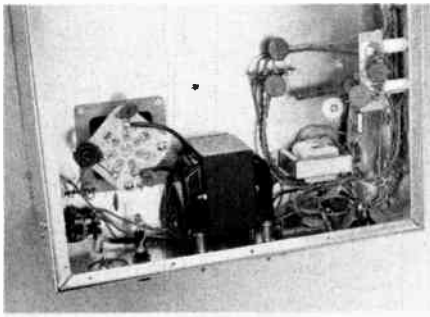


Fig. 85 — Bottom view of the amplifier chassis. L1 is shown near the tube socket. It is wound on a T-50-2 Amidon toroid core. The Zener diodes are mounted on a plate and secured to the side chassis wall.

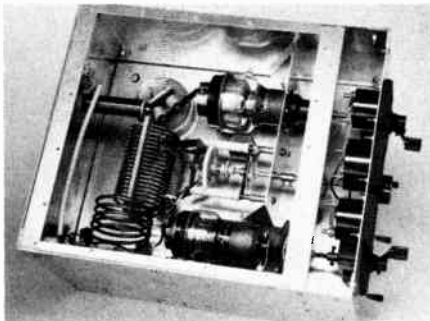


Fig. 86 — Top view of the 8877 amplifier. The three meters are separated from the rf compartment with an aluminum shield.

four-inch (102-mm) flange (stovepipe material) mounted directly above the 8877 tube. Hot air is exhausted via this port using an external "blower" which has been set up to draw air rather than force it. The procedure is simple; just connect the four-inch hose coming from the pipe flange to the blower intake port. Place the blower exhaust outlet in a position so that it will not be restricted. The cold air is drawn in under the amplifier chassis, passes through the 8877 and socket, then out the stovepipe to the blower. The air from the blower is heated and should not be directed at anything which might run normally warm (power supply components). In fact, the warm air may either be directed out of the radio shack in the event the heat is undesirable or the heat may be applied to one's feet in the winter season if the system is being used in an unheated basement atmosphere. Of course, one of the key features of a solid shield enclosure for the rf compartment is the reduction of unwanted radiation of fundamental or spurious energy which could cause TVI.

Care must be given to the mechanical installation of the high-voltage connectors and the cable used to transport 3600 volts of dc from the power supply to the anode of the 8877. Millen high-voltage connectors were used throughout. One prob-

lem developed during the testing phase of this project. A steel screw and nut were used to mount one of the connectors and apparently the Bakelite material cracked during installation. A discharge path developed across the crack creating loud noises and popping fuses. Nylon or Teflon hardware is recommended for mounting the Millen connectors if voltages above 3000 are anticipated.

### Operation

Since this project is one which should not be undertaken by an inexperienced builder, some of the basic steps of pretest will not be discussed in detail here. Suffice it to say that ordinary primary voltage checks and switching should be confirmed as being in correct working order before placing primary power to the high-voltage supply. The 3000-volt circuit *must* be treated with respect — it can seriously injure or even kill a person coming in contact with it! Operation of the motor-controlled Powerstat can be determined by operating the system on the 117-volt primary, leaving the plug to the 235-volt line disconnected.

A word of caution: *The air flow system must always be used when any power is applied to the 8877 — even filament.* And rf drive power should never reach the 8877 unless that tube has plate voltage applied. Of course, if one applies plate voltage and drive, he should be prepared to dissipate the power output from the amplifier into a dummy load of suitable rating.

One particular disadvantage of having the amplifier completely enclosed in a solid shield is the inability of the operator to visually spot any arc or component failure. During the initial testing of this amplifier, occasionally an arc would occur. While the arc was audible, the operator had to inspect the inner compartment very carefully to determine the cause of the malady. In fact, the arc had to be "encouraged" to a point where damage was easily identified!

Operation of the amplifier is quite simple. A feature that simplifies tune-up is the use of turn-counting dials for both the plate tuning and plate loading. Once the proper tuning has been established, one can log the numbers and return to them anytime. It is quite easy to touch up the dial settings for proper operating conditions once the approximate settings have been determined.

The coil-tap positions shown in the caption for Fig. 84 are given for proper operation at 3000 volts. Slightly better efficiency is possible by increasing the plate voltage to 3600 for 2-kilowatt PEP ssb operation. The same is true of lowering the voltage to 2500 during cw conditions. The actual plate current to which the amplifier is driven should be

determined in conjunction with the full-load plate voltage.

For cw tuneup and operation, the amplifier should be adjusted for maximum output power (usually determined using an externally mounted rf wattmeter) while maintaining proper grid current under conditions of 1 kW input as determined by the combination of plate current and voltage. The proper settings will have been found when the plate meters indicate 1-kW input, the grid current shows 40 mA, and maximum output power occurs in conjunction with a "dip" in plate current and a "peak" in grid current all at the same time as the plate tuning control is adjusted. A condition of high grid current is usually a result of insufficient loading or too much drive power. If a low grid current condition exists and loading control decrease doesn't correct it, more drive power is indicated.

Tune-up for single sideband at the 2-kilowatt level can be done only during dummy load conditions because it requires key-down conditions in excess of the legal-limit power restrictions. There is no way to tune this amplifier into an antenna at reduced power input and then drive it up to the 2-kW rated input point. The procedure for adjustment is identical to the one described above for cw operation. The one exception is plate-power input as indicated by the meters should be 2-kW. Then, when the proper settings have been determined, the ssb drive signal is adjusted so that peak readings of plate current show about one-half of that shown for key-down operation.

The lack of a tuned-input circuit solves several problems normally encountered when constructing an amplifier. The main advantage is that there need not be two band-switch decks with long leads (or even worse, two band switches!) nor space given to the inductors and capacitors. The driving impedance of the 8877 is very nearly 50 ohms and requires very little power to drive it to full power input. The tuned-circuit characteristics would reduce the drive requirement even further and should be considered by anyone wishing to use a 20-watt driver. For those amateurs using modern-day exciters in the 100-watt output class, some reduction in exciter gain control may be necessary. Exciters with more than about 150 watts of output power available should not be used without due consideration being given to an attenuator. The measured power required for this particular amplifier and tube shown was 50 watts to achieve a kilowatt on cw and about 70 watts for 2 kilowatts (this was in conjunction with a plate-voltage change between modes) for ssb service. Slightly more drive power was required on 10 meters.



# VHF and UHF Transmitting

The frequencies above 50 MHz were once a world apart from the rest of amateur radio, in equipment required, in modes of operation and in results obtained. Today these worlds blend increasingly. Thus, if the reader does not find what he needs in these pages to solve a transmitter problem, it will be covered in the hf transmitting chapter. This chapter deals mainly with aspects of transmitter design and operation that call for different techniques in equipment for 50 MHz and up.

### SSB/CW vs. FM

Whenever vhf operators gather, the subject of fm vs. ssb and cw is bound to come up. Because of their mode differences, the two types of operation are segregated on the lower four amateur vhf bands. Actually, both forms of communications have their advantages and disadvantages. They are better discussed subjectively among operators. Here we are only interested in the different requirements each mode places upon the transmitting equipment used. In general, equipment used for fm is of the oscillator-multiplier type. Because ssb cannot be passed satisfactorily through a frequency-multiplication stage, generation of vhf ssb signals requires the use of one or more mixer stages. Vhf cw may be generated by either method. Recently, manufacturers of synthesized as well as crystal-controlled amateur fm transceivers have been using a combination of both approaches. The multimode vhf transceiver, which offers the operator a choice of cw, ssb, fm and often a-m, is a reality. Here again we find both approaches to signal generation.

### The Oscillator-Multiplier Approach

This type of transmitter, which may be used for fm or cw, generally starts with a crystal oscillator operating in the hf range, followed by one or more frequency-multiplier stages and at least one amplifier

stage. While relatively simple to construct, such transmitters can be a cause of much grief unless the builder takes precautions to prevent undesired multiples of the oscillator and the multiplier stages from being radiated. For frequencies below 450 MHz the transmitting mixer is not difficult to construct and is recommended for most applications. Spurious-signal radiation is much easier to prevent with the latter, although it does not lend itself to compact fm equipment design. For operation on the higher amateur uhf bands, the oscillator-multiplier approach offers definite advantages and is recommended at present. Fig. 1 shows how the harmonics of a 144-MHz signal may be multiplied to permit operation on amateur microwave bands. Stability at 144 MHz is easy to achieve with the current technology, making stable microwave signals simple to generate. Varactor diodes are used as frequency-multiplying devices. They are installed in resonant cavities constructed from double-sided pc-board material. Operation will probably be crystal controlled, as even the best transceiver/transverter combination used to generate the 144-MHz signal may create problems when the output is multiplied in frequency 40 times! A frequency synthesizer with a stable reference oscillator may be used to generate the 144-MHz signal, but its output should be well filtered to eliminate noise.

Although spurious outputs of the various multiplier stages may not cause harmful interference, that is no excuse for not removing them. In most cases, the Q of successive cavities will suffice. A band-pass filter may be used to filter the final multiplier stage. Construction details of a 432-to-1296 MHz frequency multiplier using switching diodes are presented later in this chapter.

### Transmitting Mixers

With the possible exception of the

power levels involved, there is no reason to consider transmitting mixers differently than their receiving counterparts. One thing to keep in mind is that many deficiencies in the transmit mixer will show up on the air. Receiver-mixer troubles are *your* problem. Transmitter-mixer troubles become everyone's problem!

A trio of popular types of transmitting mixers is shown in Fig. 2. The doubly balanced diode mixer at A may be built using either discrete components, or the phase relationship between ports may be established using etched-circuit strip lines. Miniature DBMs are available at low cost from several manufacturers. They offer an almost-foolproof method of generating vhf ssb. Another popular mixer uses a pair of FETs in a singly balanced configuration. If care is taken in construction and adjustment, local-oscillator rejection will be adequate with this circuit. To be safe, a series-tuned trap, designed to attenuate the LO leakage even further, should follow this stage. A typical FET balanced mixer is shown in Fig. 2B.

Finally, we see a typical vacuum-tube mixer (Fig. 2C). Because it can handle more power, the tube mixer has endured at vhf. Its higher output, when compared to most solid-state mixers, reduces the number of subsequent amplifier stages

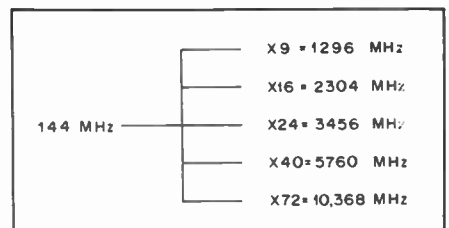


Fig. 1 — The harmonic relationships of most microwave bands to the 2-meter band are diagrammed here. The 15-mm (24 GHz) band bears no easily utilized integral relationship to 144 MHz

needed to reach a specific power level. Apart from feeling more comfortable with tubes, this is the only advantage available from using them as mixers, at least on the lower vhf bands.

### High-Level Transmitting Mixers

When designing a transmitting converter for vhf, the tradeoffs between the advantages of mixing at a low power level, such as in a diode-ring mixer, and using several stages of linear amplification must be weighed against the cost of amplifying devices. Linear uhf transistors are still relatively expensive. On 432 MHz and above, it may be desirable to mix the i-f and local-oscillator signals at a fairly high level. This method makes it unnecessary to use costly linear devices to reach the same power level. High-level mixing results in a slightly more distorted signal than it is usually possible to obtain with conventional methods, so it should be used only when essential. Fig. 3 gives the schematic diagram of a typical 432-MHz high-level mixer. V1 is the final amplifier tube of a retired commercial 450-MHz fm transmitter. The oscillator and multiplier stages now produce local-oscillator injection voltage, which is applied to the grid as before. The major change is in the cathode circuit. Instead of being directly at ground, a parallel LC circuit is inserted and tuned to the i-f. In this case a 10-meter i-f was chosen. With the exception of 144 MHz any amateur band could serve as the i-f. Two meters is unsuitable because the third harmonic of the i-f would appear at the output, where it would combine with the desired signal. In fact, some additional output filtering is needed with this circuit. A simple strip-line filter, such as appears in the ARRL *Radio Amateur's VHF Manual*, will do the job. The original crystal in the transmitter is replaced with one yielding an output at the desired local-oscillator frequency, then the intermediate stages are retuned.

One disadvantage of the high-level mixer is the relatively large amount of local-oscillator injection required. In most cases it is simpler to mix at a lower level and use linear amplifiers than to construct the local-oscillator chain. On the higher bands, it may be feasible to generate local-oscillator energy at a lower frequency and use a passive varactor mixer to reach the injection frequency. Here again, the previous caveats pertaining to diode-multiplier spurious outputs pertain. If the local-oscillator injection is impure, the mixer output will be also. Considerable theory concerning mixers is found in chapters 4 and 8 of this publication and in *Solid State Design for the Radio Amateur*, an ARRL publication.

### Designing for SSB and CW

The almost universal use of ssb for voice work in the hf range has had a major impact on equipment design for the vhf

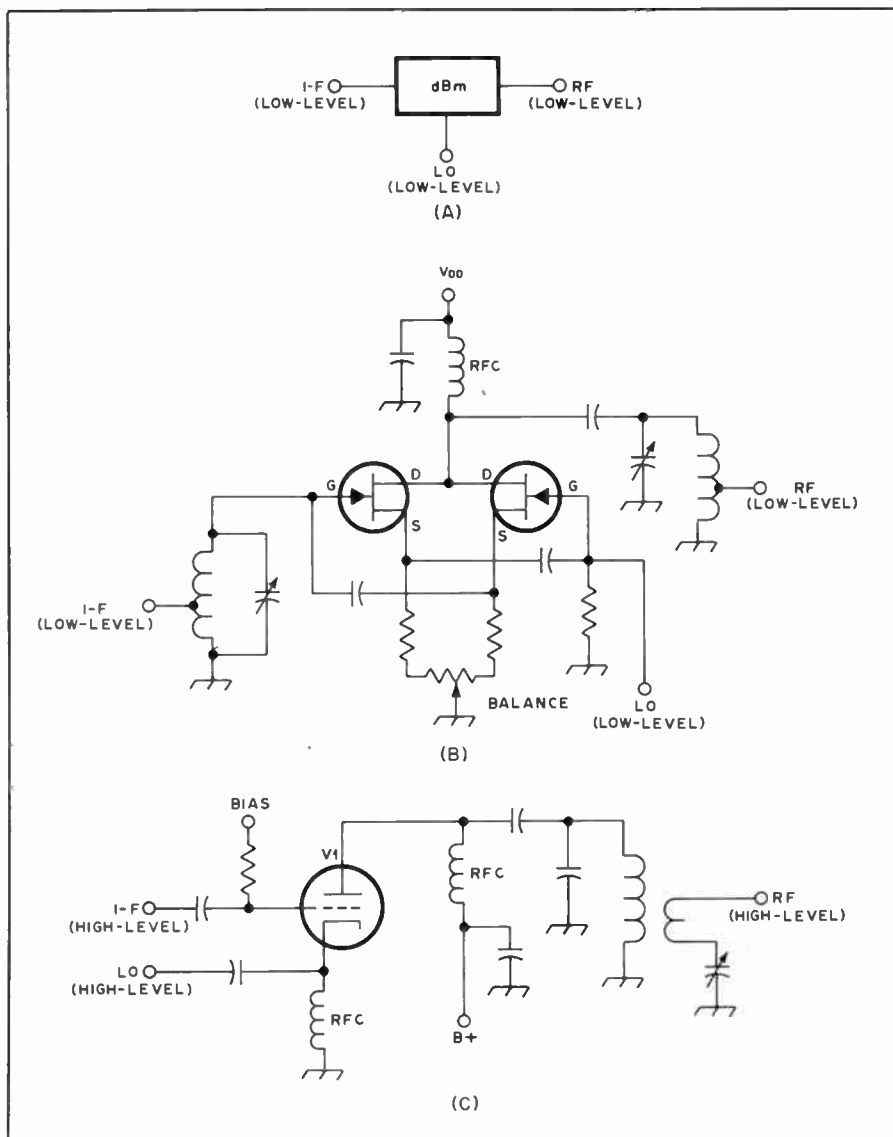


Fig. 2 — A trio of commonly used vhf transmitting mixers. At A, perhaps the simplest, a commercially available diode doubly balanced mixer. Rf output is low, requiring the use of several stages of amplification to reach a useful level. At B, a singly balanced mixer using FETs. Adjustment of this circuit is somewhat critical to prevent the local-oscillator signal from leaking through. A mixer of this type can supply slightly more output than a diode mixer. (3 dBm, as opposed to 1 dBm for the mixer shown at A). At C, a high-level mixer using a vacuum-tube triode is shown. V1 in this case might be a 2C39 or 7289. With the correct circuit constants this mixer could provide an ssb output of 15 watts on 1296 MHz. Power input would be about 100 watts! In addition, 10 watts of LO and 5 watts of i-f drive would be needed. Despite these requirements, such a circuit provides a relatively low-cost means of generating high-level microwave ssb. Spurious outputs at the LO and image frequencies will be quite strong. To attenuate them a strip-line or cavity filter should be used at the mixer output.

and even uhf bands. Many amateurs have a considerable investment in hf sideband gear. This equipment provides accurate frequency calibration and good mechanical and electrical stability. It is effective in cw as well as ssb communication: These qualities being attractive to the vhf operator, it is natural for him to look for ways to use his hf gear on frequencies above 50 MHz.

Increasing use is currently being made of vhf accessory devices, both ready made and homebuilt. This started years ago with the vhf converter, for receiving. Rather similar conversion equipment for transmitting has been widely used since

ssb began taking over the hf bands. Today the hf trend is to one-package stations, transceivers. The obvious move for many vhf operators is a companion box to perform both transmitting and receiving conversion functions. Known as *transverters*, these are offered by several manufacturers. They are also relatively simple to build, and are thus attractive projects for the homebuilder of vhf gear.

### Transverter vs. Separate Units

It does not necessarily follow that what is popular in hf work is ideal for vhf use. Our bands are wide, and piling-up in a

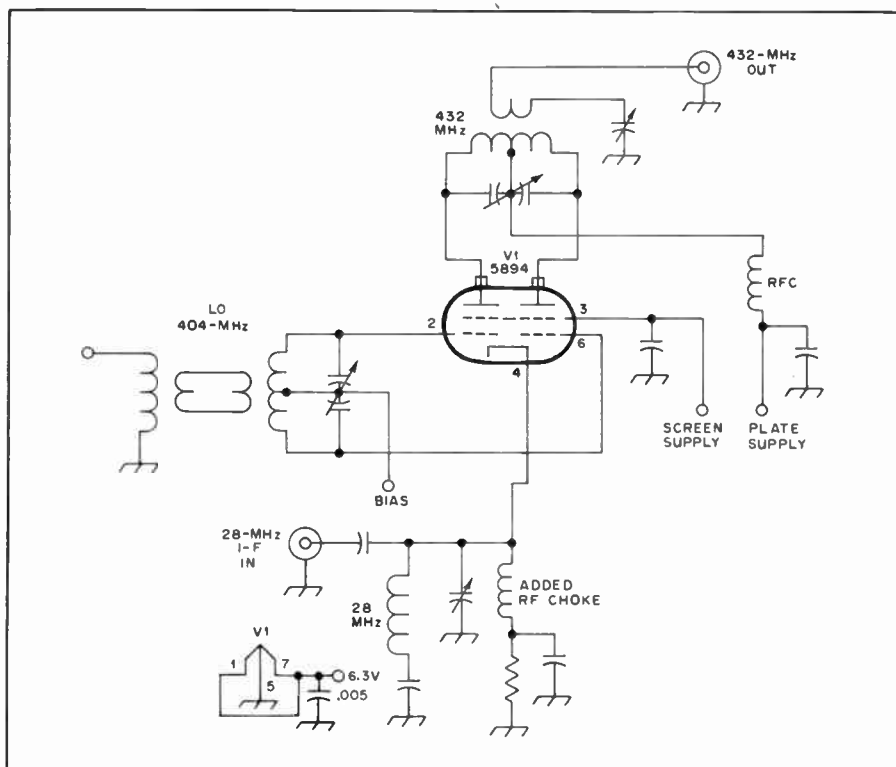


Fig. 3 — Partial schematic diagram of a 70-cm (432-MHz) mixer, built from a converted fm transmitter. The original oscillator-multiplier-driver stages of the unit now provide LO injection. A strip-line filter should be used at the output of the mixer to prevent radiation of spurious products.

narrow segment of a band, which the transceiver encourages, is less than ideal use of a major asset of the vhf bands — spectrum space. Separate ssb exciters and receivers, with separate vhf conversion units for transmitting and receiving, tend to suit our purposes better than the transceiver-transverter combination, at least in home-station service.

### Amplifier Design and Operation

All amplifiers in vhf transmitters once ran Class C, or as near thereto as available drive levels would permit. This was mainly for high-efficiency cw and quality high-level amplitude modulation. Class C is now used mostly for cw or fm, and in either of these modes the drive level is completely uncritical, except as it affects the operating efficiency. The influence of ssb techniques is seen clearly in current amplifier trends. Today Class AB1 is popular and most amplifiers are set up for linear amplification, for ssb and — to a lesser extent — a-m. The latter is often used in connection with small amplitude-modulated vhf transmitters, having their own built-in audio equipment. Where a-m output is available from the ssb exciter, it is also useful with the Class AB1 linear amplifier, for only a watt or two of driver output is required.

There is no essential circuit difference between the AB1 linear amplifier and the Class C amplifier; only the operating conditions are changed for different classes of service. Though the plate

efficiency of the AB1 linear amplifier is low in a-m service, this type of operation makes switching modes a very simple matter. Moving toward the high efficiency of Class C from AB1 for cw or fm service is accomplished by merely raising the drive from the low AB1 level. In AB1 service the efficiency is typically 30 to 35 percent. No grid current is ever drawn. As the grid drive is increased, and grid current starts to flow, the efficiency rises rapidly. In a well-designed amplifier it may reach 60 percent, with only a small amount of grid current flowing. Unless the drive is run well into the Class C region, the operating conditions in the amplifier can be left unchanged, other than the small increasing of the drive, to improve the efficiency available for cw or fm. No switching or major adjustments of any kind are required for near-optimum operation on ssb, a-m, fm or cw, if the amplifier is designed primarily for AB1 service. If high-level a-m were to be used, there would have to be major operating-conditions changes, and very much higher available driving power.

### Tank-Circuit Design

Except in compact low-powered transmitters, conventional coil-and-capacitor circuitry is seldom used in transmitter amplifiers for 144 MHz and higher frequencies. U-shaped loops of sheet metal or copper tubing, or even copper-laminated circuit board, generally give higher Q and circuit efficiency at 144 and

220 MHz. At 420 MHz and higher, coaxial tank circuits are effective. Resonant cavities are used in some applications above 1000 MHz. Examples of all types of circuits are seen later in this chapter. Coil and capacitor circuits are common in 50-MHz amplifiers, and in low-powered, mobile and portable equipment for 144 and even 220 MHz.

### Stabilization

Most vhf amplifiers, other than the grounded-grid variety, require neutralization if they are to be satisfactorily stable. This is particularly true of AB1 amplifiers, which are characterized by very high power sensitivity. Conventional neutralization is discussed in chapter 6. An example is shown in Fig. 4A.

A tetrode tube has some frequency where it is inherently neutralized. This is likely to be in the lower part of the vhf region for tubes designed for hf service. Neutralization of the opposite sense may be required in such amplifiers, as in the example shown in Fig. 4B.

Conventional screen bypassing methods may be ineffective in the vhf range. Series-tuning the screen to ground, as in 4C, may be useful in this situation. A critical combination of fixed capacitance and lead length may accomplish the same result. Neutralization of transistorized amplifiers is not generally practical, at least where bipolar transistors are used.

Parasitic oscillation can occur in vhf amplifiers, and, as with hf circuits, the oscillation is usually at a frequency considerably higher than the operating frequency, and it cannot be neutralized out. Usually it is damped out by methods illustrated in Fig. 5. Circuits A and B are commonly used in 6-meter transmitters. Circuit A may absorb sufficient fundamental energy to burn up in all but low-power transmitters. A better approach is to use the selective circuit illustrated at B. The circuit is coupled to the plate tank circuit and tuned to the parasitic frequency. Since a minimum amount of the fundamental energy will be absorbed by the trap, heating should no longer be a problem.

At 144 MHz and higher, it is difficult to construct a parasitic choke that will not be resonant at or near the operating frequency. Should uhf parasitics occur, an effective cure can often be realized by shunting a 56-ohm, 2-watt resistor across a small section of the plate end of the tuned circuit as shown in Fig. 5C. The resistor should be attached as near the plate connector as practical. Such a trap can often be constructed by bridging the resistor across a portion of the flexible strap-connector that is used in some transmitters to join the anode fitting to the plate-tank inductor.

Instability in solid-state vhf and uhf amplifiers can often be traced to oscillations in the lf and hf regions. Because the gain of the transistors is very high at the



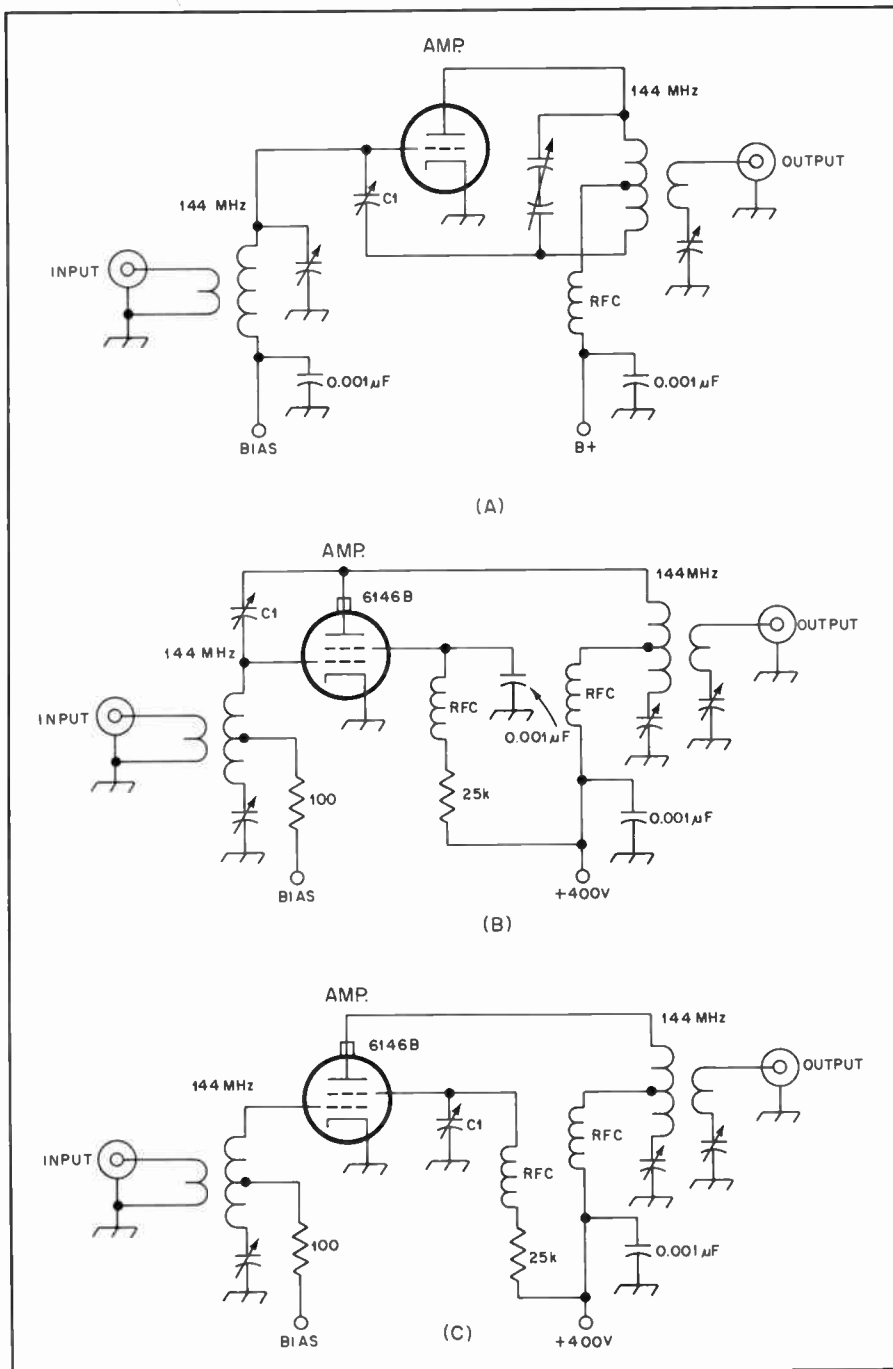


Fig. 4 — Representative circuits for neutralizing vhf single-ended amplifiers. The same techniques are applicable to stages that operate in push-pull. At A, C1 is connected in the manner that is common to most vhf or uhf amplifiers. The circuits at B and C are required when the tube is operated above its natural self-neutralizing frequency. At B, C1 is connected between the grid and plate of the amplifier. Ordinarily, a short length of stiff wire can be soldered to the grid pin of the tube socket, then routed through the chassis and placed adjacent to the tube envelope, and parallel to the anode element. Neutralization is effected by varying the placement of the wire with respect to the anode of the tube, thus providing variable capacitance at C1. The circuit at C is a variation of the one shown at B. It too is useful when a tube is operated above its self-neutralizing frequency. In this instance, C1 provides a low-Z screen-to-ground path at the operating frequency. RFC in all circuits shown are vhf types and should be selected for the operating frequency of the amplifier.

lower frequencies, instability is almost certain to occur unless proper bypassing and decoupling of stages is carried out. Low-frequency oscillation can usually be cured by selecting a bypass-capacitor value that is effective at the frequency of oscillation and connecting it in parallel with the vhf bypass capacitor in the same

part of the circuit. It is not unusual, for example, to employ a 0.1- $\mu$ F disk ceramic in parallel with a 0.001- $\mu$ F disk capacitor in such circuits as the emitter, base, or collector return. The actual values used will depend upon the frequencies involved. An additional stabilization method for solid-state amplifiers is shown in Fig. 5E.

Capacitive reactance of C is chosen to be very low at the parasitic frequency. R then appears as a swamping resistor, damping the oscillation.

### VHF TVI Causes and Cures

The principal causes of TVI from vhf transmitters are:

- 1) Adjacent-channel interference in channels 2 and 3 from 50 MHz.
- 2) Fourth harmonic of 50 MHz in channels 11, 12 or 13, depending on the operating frequency.
- 3) Radiation of unused harmonics of the oscillator or multiplier stages. Examples are 9th harmonic of 6 MHz, and 7th harmonic of 8 MHz in channel 2; 10th harmonic of 8 MHz in channel 6; 7th harmonic of 25-MHz stages in channel 7; 4th harmonic of 48-MHz stages in channel 9 or 10; and many other combinations. This may include i-f pickup, as in the cases of 24-MHz interference in receivers having 21-MHz i-f systems, and 48-MHz trouble in 45-MHz i-fs.
- 4) Fundamental blocking effects, including modulation bars, usually found only in the lower channels, from 50-MHz equipment.
- 5) Image interference in channel 2 from 144 MHz, in receivers having a 45-MHz i-f.
- 6) Sound interference (picture clear in some cases) resulting from rf pickup by the audio circuits of the TV receiver.

There are other possibilities, but nearly all can be corrected completely, and the rest can be substantially reduced.

Items 1, 4 and 5 are receiver faults, and nothing can be done at the transmitter to reduce them, except to lower the power or increase separation between the transmitting and TV antenna systems. Item 6 is also a receiver fault, but it can be alleviated at the transmitter by using fm or cw instead of a-m phone.

Treatment of the various harmonic troubles, Items 2 and 3, follows the standard methods detailed elsewhere in this *Handbook*. The prospective builder of new vhf equipment should become familiar with TVI prevention techniques and incorporate them in new construction projects.

Use as high a starting frequency as possible, to reduce the number of harmonics that might cause trouble. Select crystal frequencies which do not have harmonics in local TV channels. Example: The 10th harmonic of 8-MHz crystals used for operation in the low part of the 50-MHz band falls in channel 6, but 6-MHz crystals for the same band have no harmonic in that channel.

If TVI is a serious problem, use the lowest transmitter power that will do the job at hand. Keep the power in the multiplier and driver stages at the lowest practical level, and use link coupling in preference to capacitive coupling. Plan for complete shielding and filtering of the rf



Fig. 5 — Representative circuits for vhf parasitic suppression are shown at A, B, and C. At A, Z1 (for 6-meter operation) would typically consist of 3 or 4 turns of No. 13 wire wound on a 100-ohm 2-watt non-inductive resistor. Z1 overheats in all but very low power circuits. The circuit at B, also for 6-meter use, is more practical where heating is concerned. Z2 is tuned to resonance at the parasitic frequency by C. Each winding of Z2 consists of two or more turns of no. 14 wire — determined experimentally — wound over the body of a 100-ohm 2-watt (or larger) noninductive resistor. At C, an illustration of uhf parasitic suppression as applied to a 2-meter amplifier. Noninductive 56-ohm 2-watt resistors are bridged across a short length of the connecting lead between the tube anode and the main element of the tank inductor, thus forming Z3 and Z4.

The circuit at D illustrates how bypassing for both the operating frequency and lower frequencies is accomplished. Low-frequency oscillation is discouraged by the addition of the 0.1  $\mu$ F disk ceramic capacitors. RFC1 and RFC2 are part of the decoupling network used to isolate the two stages. This technique is not required in vacuum-tube circuits. At E, a capacitor with low reactance at the parasitic frequency is connected in series with a 1/2-watt carbon resistor. At 144 MHz, C is typically 0.001  $\mu$ F. R may be between 470 and 2200 ohms

sections of the transmitter, should these steps become necessary.

Use coaxial line to feed the antenna system, and locate the radiating portion of the antenna as far as possible from TV receivers and their antenna systems.

A complete discussion of the problems and cures for interference is in the ARRL publication, *Radio Frequency Interference*.


### A 2-Meter Transverter

This transverter is designed to be used with any 14- or 28-MHz ssb exciter capable of delivering approximately 20 watts peak output. It is stable both in terms of frequency and general operating conditions. It can provide up to 20 watts PEP output at 144 MHz — sufficient, say, for driving a pair of 4CX250 tubes in Class C for cw operation, or the same pair of tubes can be operated AB1 to provide 1200 watts PEP input with this unit as a driver. The output signal is clean and TVI should not be experienced except when receiver faults are involved.

Beginners should not attempt this project, since vhf ssb circuits require special care in their construction and operation, sometimes a requirement that is a bit beyond the inexperienced builder.
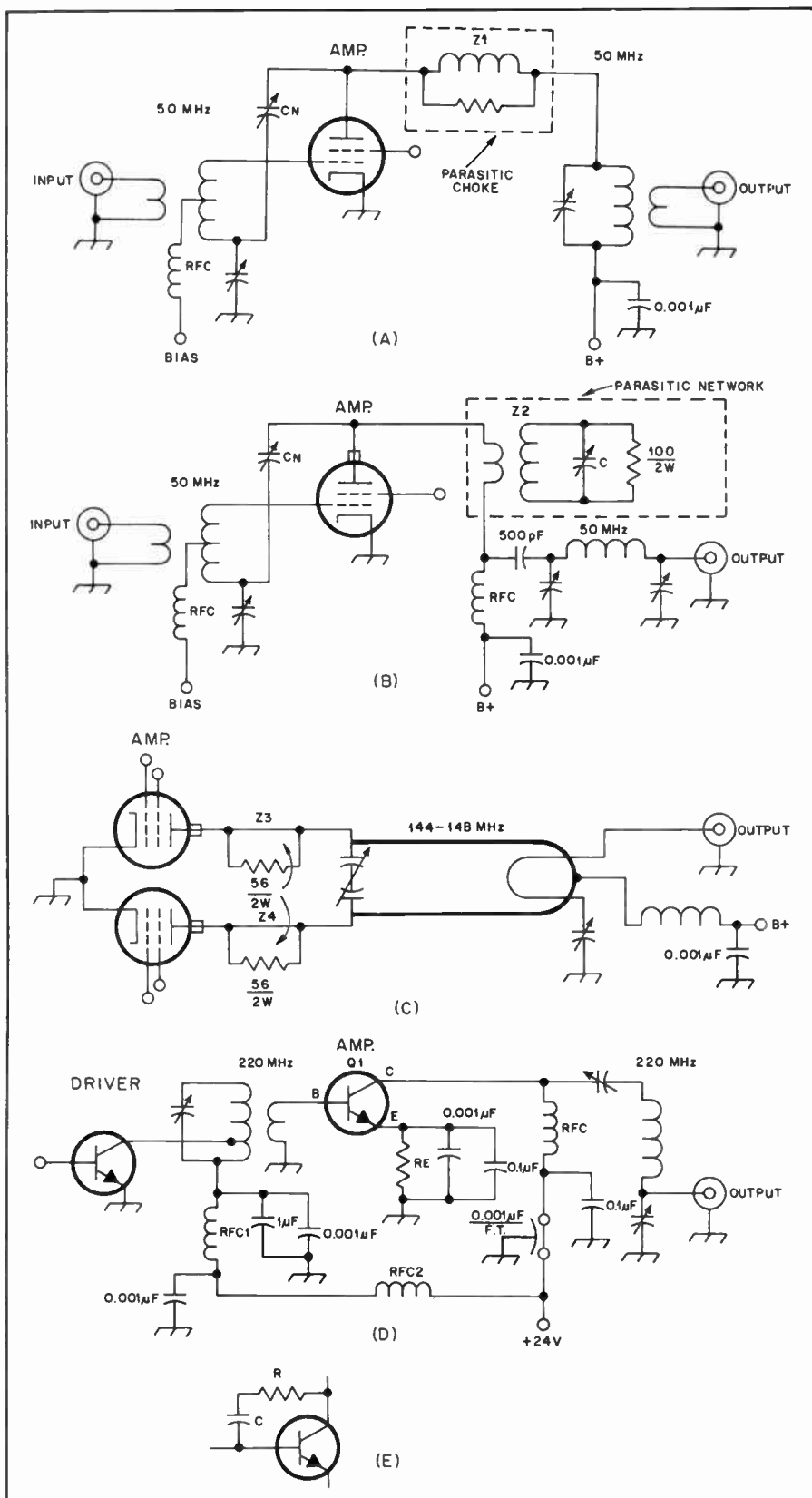
### How It Operates

Starting with VIA, the oscillator, Fig. 6, a 43.333-MHz overtone crystal is used at Y1 to provide the local-oscillator signal for the exciter. Output from VIA is amplified by V1B to a suitable level for driving the tripler, V2. 130-MHz or 116-MHz energy is fed to the grids of V3, a 6360 mixer, by means of a band-pass tuned circuit, L3-C1 and L4-C2. The selectivity of this circuit is high, thus reducing unwanted spurious energy at the mixer grids.



Output from the exciter is supplied through an attenuator pad at J1 and is injected to the mixer, V3, at its cathode circuit across a 270-ohm resistor. The attenuator pad can be eliminated if a very low-power exciter is to be used. The values shown in Fig. 6 were chosen for

operation with a Central Electronics 20A exciter operating at full input, or nearly so. The amount of driving power needed at the cathode of V3 is approximately 4 or 5 watts PEP.

After the 130-MHz and 14-MHz signals are mixed at V3, the *sum* frequency of

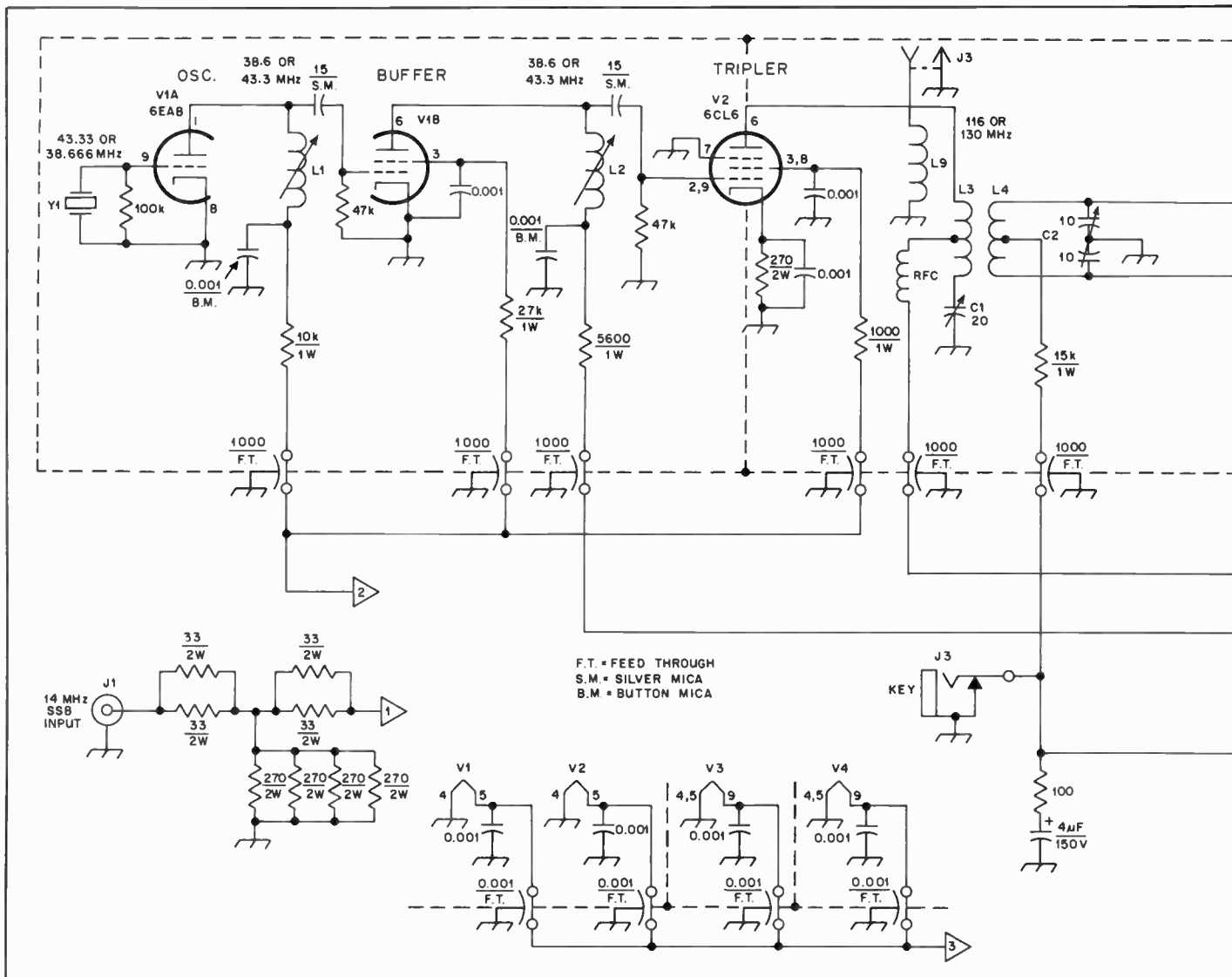


Fig. 6 — Schematic diagram of the transmitting converter portion of the transverter. Fixed-value capacitors are disk ceramic unless noted differently.

B1 — Small 15-volt battery.  
 C1 — 20-pF miniature variable, E. F. Johnson 160-110 suitable.  
 C2, C3, C5 — 10 pF per section miniature butterfly (E. J. Johnson 167-21 suitable).  
 C4 — 5-pF per section miniature butterfly, E. F. Johnson 160-205 suitable.

C6 — 20-pF miniature variable (same as C1).  
 I1, I2 — 117-V ac neon panel lamp assembly.  
 J1-J3, incl. — SO-239-coax connector.  
 J3 — Closed-circuit phone jack.  
 L1 — 15 turns no. 28 enam. wire, close-wound, on 1/4-inch dia, slug-tuned form, Millen 69058 form suitable.

L2 — 12 turns no. 28 enam. wire, close wound, on same type form as L1.  
 L3 — 5 turns no. 18 wire space-wound to 7/8-inch length, 1/2-inch dia, center-tapped.  
 L4 — 3 turns no. 18 wire, 1/2-inch dia, 3/8-inch long, center-tapped.

F.T. = FEED THROUGH  
 S.M. = SILVER MICA  
 B.M. = BUTTON MICA

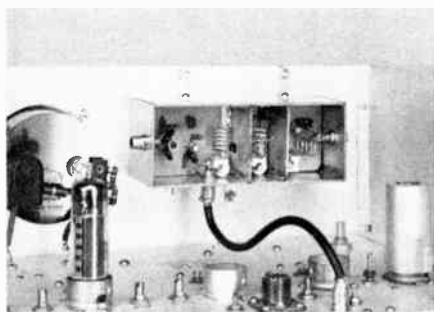


Fig. 7 — Inside view of the converter. Shields are used between the rf amplifier input and output circuits, and between the latter and the mixer input circuit. The cable entering the bottom side of the enclosure carries the oscillator injection energy. Output to the associated receiver or transceiver is taken through the jack to the left.

144-MHz is coupled to the grids of V4, the PA stage, by means of another bandpass tuned circuit — further reducing spurious output from the exciter. PA stage V4 operates in the AB1 mode. Its idling plate current is approximately 25 mA. The plate current rises to approximately 100 mA at full input.


If cw operation is desired, the grid-block keying circuit in the mixer stage (J3) can be included. If ssb operation is all that is contemplated, the minus 100-volt bias line can be eliminated along with J3, R1 and the shaping network at J3. In that case the 15-kΩ grid resistor from the center tap of L4 would be grounded to the chassis.

The receiving section uses a low-noise uhf MOSFET as the rf amplifier and a second dual-gate MOSFET as the mixer (see Fig. 8). The gate-1 and drain

connections of the rf amplifier are tapped down on the tuned circuits so that unconditional stability is achieved without neutralization. Oscillator energy is sampled with a two-turn link wound over L3. A short length of RG-58A/U carries the injection energy to Q2. The converter is built in a 5 × 2-1/4 × 2-1/4-inch (127 × 57 × 57-mm) box constructed from four pieces of double-sided circuit board which have been soldered on all abutting edges. The unit is mounted on the transverter front panel.
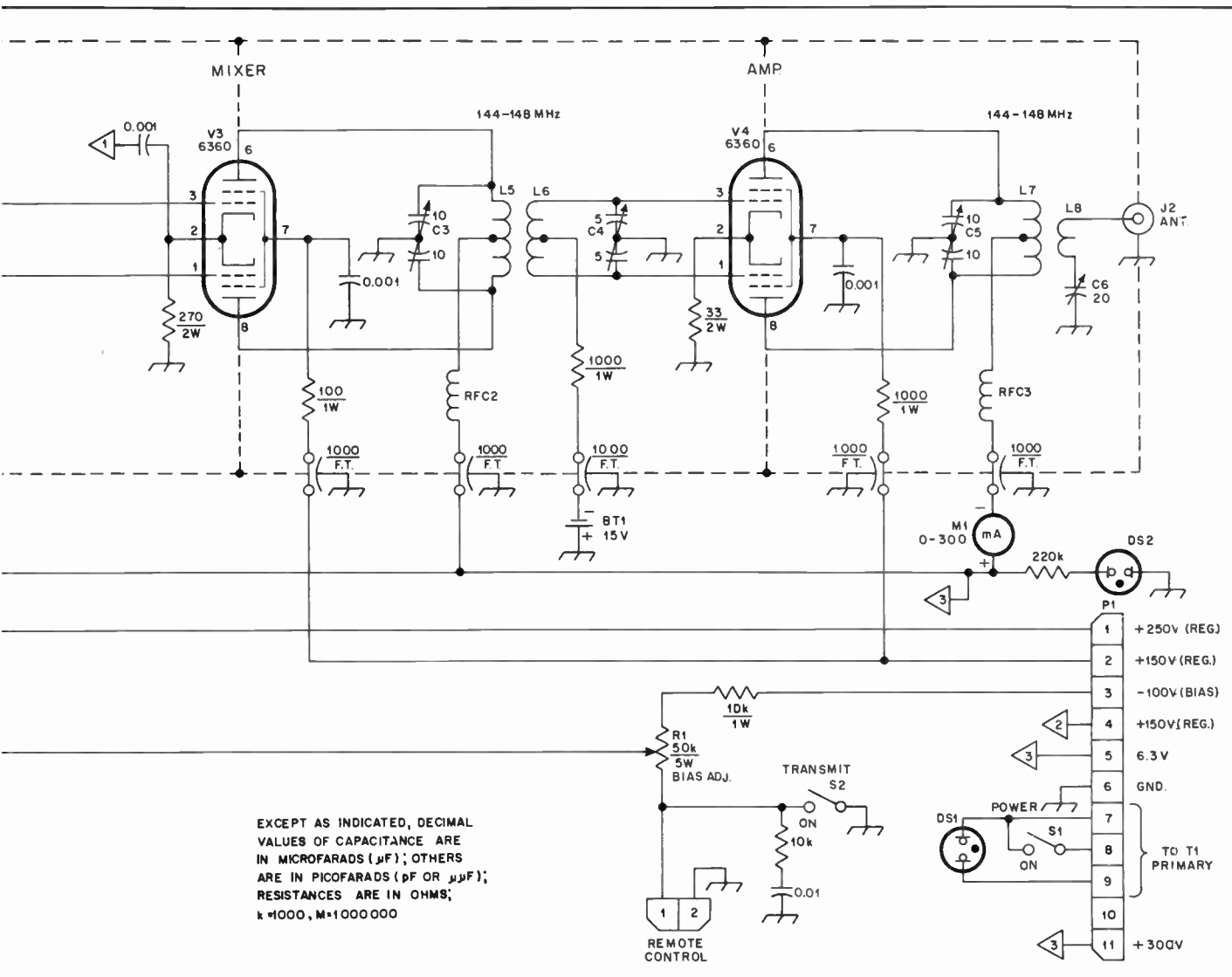
#### Construction Notes

The photographs show the construction techniques that should be followed for duplicating this equipment. The more seasoned builder should have no difficulty changing the prescribed layout to fit his



The polarized capacitor is electrolytic. Fixed-value resistors are 1/2-watt carbon unless otherwise noted. Inches × 25.4 = mm.

- L5 — 5 turns no. 18 wire, 1/2-inch dia, 5/8-inch long, center-tapped.
- L6 — 3 turns no. 18 wire, 1/2-inch dia, 5/8-inch long, center-tapped.
- L7 — 4 turns no. 18 wire, 1/2-inch dia, 1/2-inch long, center-tapped.
- L8 — 1-turn link of insulated hookup wire, 1/2-

- inch dia, inserted in center of L7.
- L9 — 2 turns of insulated hookup wire over L3.
- M1 — 0 to 200-mA dc meter.
- P1 — 11-pin chassis-mount male plug (Amphenol 86PM11).
- R1 — 50-kΩ linear-taper, 5-watt control.
- RFC1-RFC3, incl. — 2.7-μH rf choke, Millen

- 34300-2.7.
- S1, S2 — Spst rocker-type switch (Carling TIGK60).
- Y1 — 43.333-MHz, third-overtone crystal for 14-MHz input. If a 28-MHz transceiver will be used, a 38.667-MHz crystal is required

particular needs, but the shielding and bypassing methods used here should be adhered to even if changes are made.

An 8 × 12 × 3-inch (203 × 305 × 76-mm) aluminum chassis is used for this equipment. An internal chassis, 5 inches (127-mm) wide, 3 inches (76-mm) deep, and 12 inches (305-mm) long, is made from flashing copper and installed along one edge of the main chassis. This method makes it possible to solder directly to the chassis for making positive ground connections rather than rely on mechanical joints. Copper shield partitions are soldered in place as indicated on the schematic diagram and photo. An aluminum bottom plate is used to enclose the underside of the chassis for confining the rf.

Feedthrough capacitors bring power leads into the copper compartment.

Though this adds somewhat to the overall cost of the project, it provides excellent bypassing and decoupling, thus reducing unwanted interstage coupling. It also contributes to TVI reduction. Most surplus houses offer feedthrough capacitors at reasonable cost.

### Tune-Up

An antenna-changeover relay and a set of normally open relay contacts, both operated by the exciter, must be provided. The remote control leads, from P2, should be connected to the relay contacts. With power applied to the converter, L12 should be set for maximum noise input to the transceiver. Then, using a signal generator or off-the-air weak signal, peak L9, L10 and L11 for best signal-to-noise ratio.

The transmitter section can be powered by the circuit of Fig. 10, or the builder can design a supply of his own choice. Regulated voltages are recommended for best operation.

With a dummy load connected to J2, apply operating voltage. Couple a wavemeter to L1 and tune the oscillator plate for maximum output. Then, detune the slug of L1 slightly (toward minimum inductance) to assure reliable oscillator starting. Couple the wavemeter to L2 and tune for peak output. With the wavemeter applied to L4, adjust C1 and C2 for maximum indicated output.

The next step is to connect the transceiver to J1 and supply just enough drive to cause a rise in PA plate current of a few milliamperes. Tune C3 and C4 for maximum indicated plate current at M1,

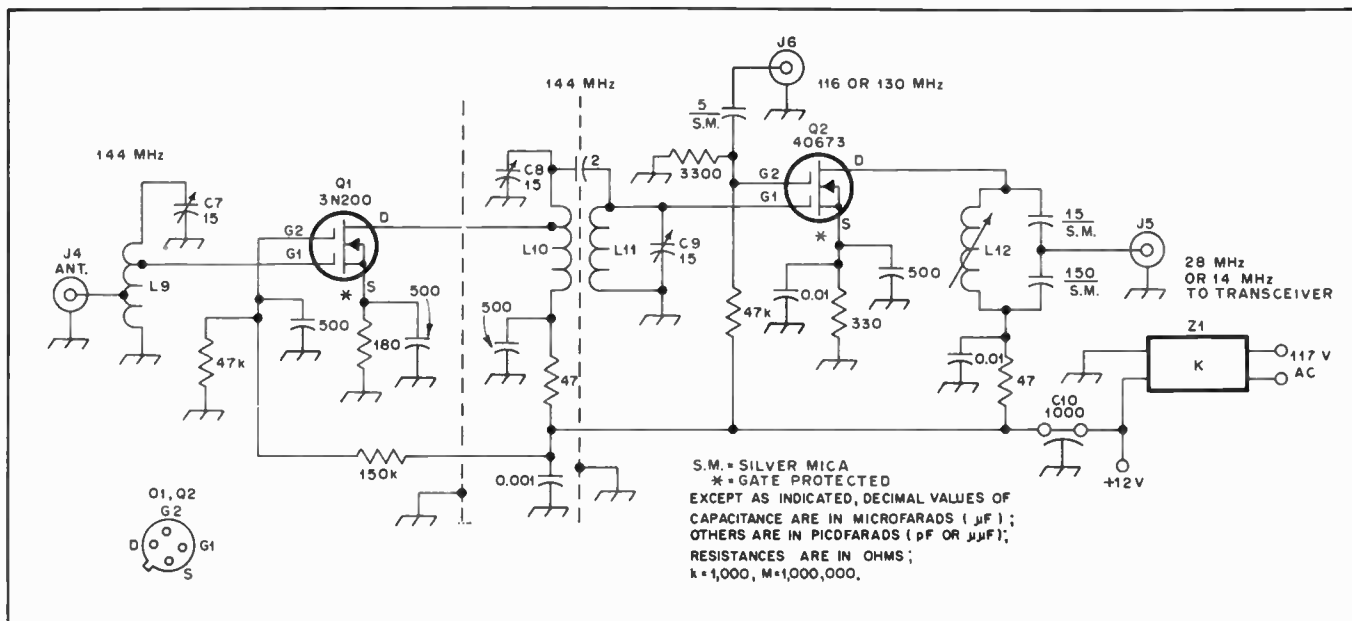


Fig. 8 — Diagram of the converter section. Resistors are 1/4-watt composition and capacitors are disk ceramic, except as noted otherwise. Inches  $\times$  25.4 = mm.

C7-C9, incl. — Air variable, pc mount, Johnson 189-505-5.  
 C10 — Feedthrough type.  
 L9 — 4-1/2 turns, no. 18 tinned wire, 1/4-inch ID. Tap at 1-1/2 turns up from the ground end for the antenna connection, and at 3 turns for the Q1 gate.

L10 — 4-1/2 turns, no. 18 tinned wire, 1/4-inch ID. Tap at 3 turns up from the cold end for the Q1 drain connection.  
 L11 — 5 turns no. 18 tinned wire, 1/4-inch ID.  
 L12 — 1.99-2.42- $\mu\text{H}$  slug-tuned coil, pc mount, for 28-MHz output, J. W. Miller 46A226CPC; or, for 14-MHz output, 7.3-8.9- $\mu\text{H}$  J. W. Miller

46A226CPC.  
 J4-J6, incl. — Phono type.  
 Q1, Q2 — RCA dual-gate MOSFET.  
 Z1 — 12-V miniature power supply, transistor radio type.

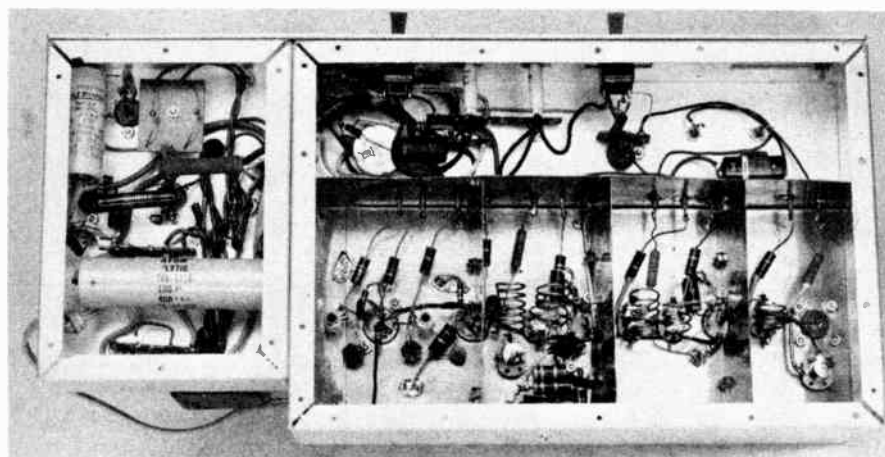


Fig. 9 — Looking into the bottom of the chassis, the rf section is enclosed in a shield compartment made from flashing copper. Additional divider sections isolate the input and output tuned circuits of the last three stages of the exciter. Feed-through capacitors are mounted on one wall of the copper compartment to provide decoupling of the power leads.

then adjust C5 and C6 for maximum power output to the dummy load. C1, C2, C3 and C4 should be readjusted at this point for maximum plate current of the PA stage. Use only enough drive to bring the PA plate current up to 100 mA at maximum dc input power.

A closed-circuit keying jack is used at J3 so that the mixer stage is not biased to cutoff during voice operation. Inserting the key permits full bias to be applied, thus cutting off V3. R1 should be adjusted

for complete cutoff of V3 when the key is open.

#### A Linear Transmitting Converter for 432 MHz

Linear transmitting converters offer several advantages over frequency multiplication schemes for the 70-cm band. Any mode in which the low-frequency exciter is capable of generating can be translated to the higher frequency. Frequency stability is similar to that of the hf

unit, and all the hf operating features are retained when using the transmitting converter. Single sideband and cw operation are prevalent on Mode B operation (70-cm transmit, 2-meter receive) of the OSCAR series, and a linear transmitting converter permits this option.

A traditional approach (using tubes) is employed here (Fig. 11 to 14). This unit is a modified version of one appearing in November 1973 *QST* by W2AIH. Detailed construction notes are described in that article. The output is 35 watts from a modified surplus Motorola T-44 transmitting module. OSCAR Mode B requires less than 10 watts erp for effective access of the satellite. Feed-line loss in a typical installation will drop the 35-watt output to the level where an omnidirectional, unity-gain antenna will be sufficient for use with OSCAR. For other applications, the most popular kilowatt amplifier for 432 MHz, a design by K2RIW (April and May 1972 *QST*), requires in excess of 20 watts of drive for maximum output. The output of this transmitting converter handily provides for both situations.

Injection to the mixer is provided by multiplication of 67.33-MHz energy from the oscillator. The 6922 dual triode is used as a Butler oscillator. The plate circuit of V1B is capacitively coupled to the input of the 6688 pentode doubler, V2. The following stage uses a 6939 as a tripler for an output frequency of 404 MHz. Inductive coupling is used between the



tripler and the 6939 mixer, V4, and between the output of the mixer and the 6939 amplifier stages (L4, L5/L6 and L7, respectively). A 6939 driver-amplifier stage runs Class AB1 for good suppression of unwanted mixing products. The final amplifier is a cathode-driven 2C39 triode. Input power to the cathode is coupled through a variable capacitor to provide an impedance match to the exciter. The plate and cathode hardware are modified components from a T-44 amplifier. A flapper type of capacitor is used to tune the plate circuit to resonance. The mica dielectric in the bypass capacitors is replaced with 5-mil (0.127-mm) Teflon sheet. This is all the modification required for the 2C39 PA.

Tune-up is simply a matter of applying voltage to the unit and adjusting the tuned circuits for maximum indication on a wavemeter. Coupling between L3, and L4/L5 and L6 should be as loose as possible while still providing adequate drive for the 6939s. Final adjustment is made by applying approximately 0.5 watt of drive and adjusting for maximum power output as indicated by a watt-meter in the feed line. For normal use, approximately 0.5 watt of 28-MHz energy is adequate for full output with minimum distortion. More drive will cause distortion in the mixer and will generate spurious signals within and out of the ham band.

#### T-44 Cavity Modification

It was felt that the inductive tuning arrangement was somewhat inefficient so this was replaced with a capacitive type instead. A "flapper" capacitor of spring brass is attached to the newly fabricated top cover. The top cover is bent from aluminum sheet stock (0.035 inch). Tuning is accomplished by means of a screw which bears against the spring-brass capacitor plate. Some adjustment of the line that forms L11 may also be needed to bring the plate tank near resonance. Final adjustment is accomplished by means of C10.

#### Optional LO Output

In some applications, rf energy at the LO frequency (404 MHz) is required. This is accomplished by mounting a BNC connector (with the pin sawed off) near L5. Refer to the bottom view of the driver stages. The connector can be seen just above C4 in the third compartment from the left.

#### A 220-MHz High-Power Amplifier

Circuits for 220-MHz power amplifiers have long been designed around the external-anode tetrode. While these tubes offer high gain, instability problems have caused many builders considerable consternation over the years. Multiple-tube amplifiers are often necessary to obtain the high power levels many moonbouncers and weak-signal specialists require. Push-pull amplifiers have been

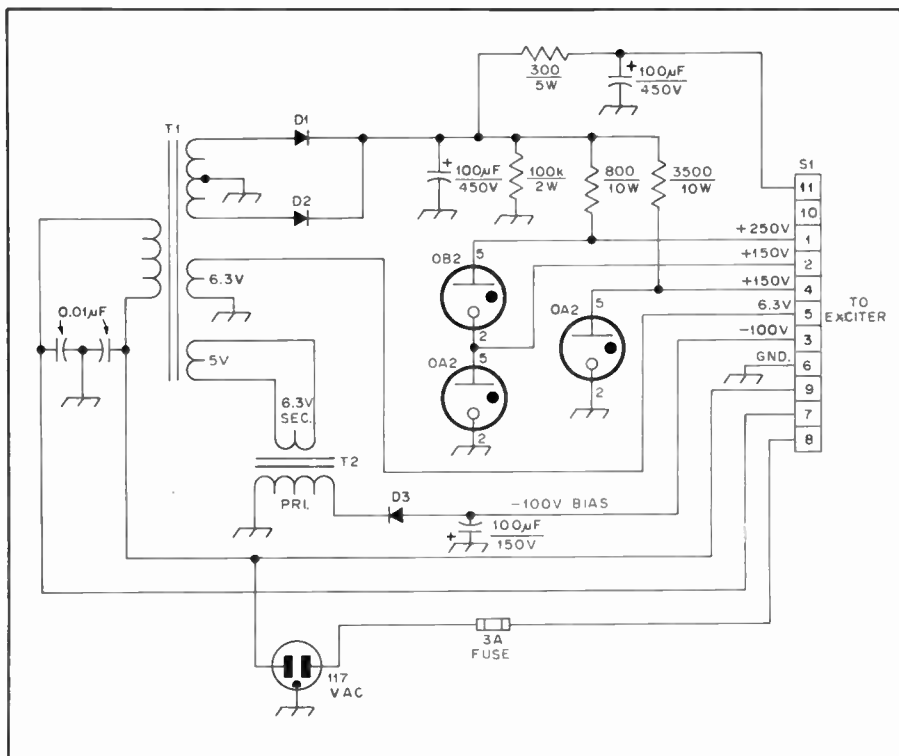


Fig. 10 — Schematic diagram of the power supply section. On-off switches for the ac and dc circuits are mounted in the rf deck along with the pilot lamps. Polarized capacitors are electrolytic, others are disk ceramic. D1 and D2 are 1000-volt, 1-ampere silicon diodes. D3 is a 200-PRV, 600-mA silicon diode. T1 is a power transformer with a 540-volt ct secondary at 120 mA. Filament windings are 5 V at 3 A, and 6.3 V at 3.5 A. T1 is a 6.3 V, 1-A filament transformer connected back to back with the 5-V winding of T1. S1 is an 11-pin socket (female). A 10-kΩ resistor and a 0.01-μF disk capacitor are connected in series between the center tap of T1's secondary and ground for transient suppression when S2 is switched to on. The suppressor is mounted at S2, in the rf deck.

tried with moderate success, and recently parallel-tube designs have found favor.<sup>1</sup>

Modern computer-aided tube designs have brought forth high-μ triodes such as the 3CX1500A7/8877, a 1500-watt dissipation external-anode triode with maximum ratings good through 250 MHz. The ceramic insulation allows a heavy flow of rf current through the tube, with no loss of stability in a properly designed circuit. Low heater requirements (5 V at 10.5 A) add to the appeal of the 8877. This amplifier employs the 3CX1500A7/8877 in a cathode-driven circuit. The grid is grounded directly to the chassis, adding to the stability. The amplifier (Figs. 15 to 21) is unconditionally stable — more so than some amplifiers built for the hf region.

#### Circuit Details

The input circuit consists of a T network. Medium values of Q were chosen to provide high efficiency. Both the cathode and the heater are operated at the same rf potential; the heater is held above rf ground by the impedance of the filament choke. The plate tank is a pair of quarter-wavelength striplines placed symmetrically about the tube.<sup>2</sup> This arrangement per-

mits a more uniform flow of current through the anode, preventing "hot spots" on the anode conducting surface. Additionally, tube output capacitance is effectively halved, as one-half the tube capacitance (13 pF) is used to load each stripline. Striplines act as low-pass circuit elements even with the high unloaded-Q conditions found at 220 MHz. Linear inductors also offer control of odd-mode harmonics. No spurious responses could be found in this amplifier up through the 900-MHz region.

A strip-line impedance can be varied by changing its width and relation to its ground planes. Physical dimensions of the tube limit the position of the stripline above one ground plane. In order to utilize commercially available chassis, the stripline was placed 1-1/4 inch (32-mm) above one side of an inverted 4-inch (102-mm) high chassis. This means that approximately 75 percent of the rf current flows through the chassis, but only 25 percent flows through the top shield cover. The small percentage flowing through the top reduces the effect of any mechanical anomalies associated with a removable cover.

For quarter-wavelength lines, the ratio of line impedance to reactance should be between 1.5 and 2.0 for the best bandwidth. Taking stray capacitance into account, expected tuning capacitance and tube output capacitance gives a value of

<sup>1</sup>Knadle, "A Strip-Line Kilowatt Amplifier for 432 MHz," *QST*, April and May, 1972.

<sup>2</sup>Barber, Rinaudo, Orr and Sutherland, "Modern Circuit Design for VHF Transmitters," *CQ*, November and December, 1965.

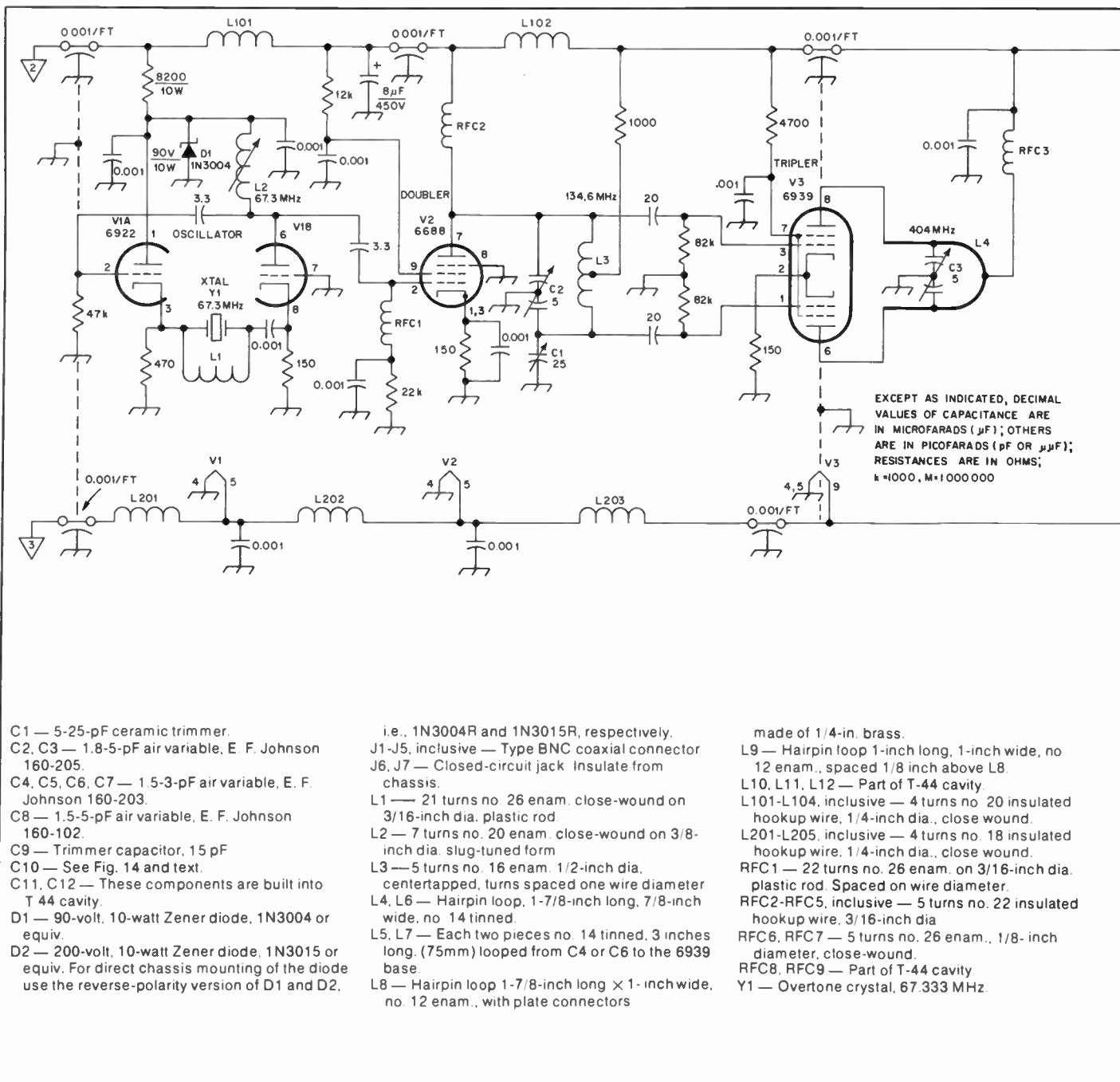


Fig. 11 — Schematic diagram of the heterodyne exciter for 432 MHz. Inches  $\times$  25.4 = mm.

55 ohms for  $X_C$ . Values of line impedance versus line length for resonance at 222 MHz were computed on a programmable calculator for impedances between 30 and 100 ohms. These were plotted on a graph. Final dimensions were determined using this system, choosing dimensions that fell into the middle of the graph, thus allowing for any unpredicted effects.

The plate blocking capacitor consists of a sandwich of brass plate and the stripline, with Teflon sheet as the dielectric. This forms a very low-loss, high-voltage capacitor. The plate bypass capacitor is built along the same principles. A piece of circuit board was once again sandwiched


with Teflon sheet to the side wall of the chassis. This technique is used effectively throughout as an inexpensive bypass or feedthrough capacitor at vhf.

Amplifier output is coupled through a capacitive probe. Transformation of the load impedance to the tube resonant-load impedance is achieved by means of a series reactance (the loading capacitor). The tuning capacitor is solidly grounded by means of a flexible strap of negligible inductance. Mechanical details were described by Sutherland.<sup>3</sup>

A rather elaborate metering system is employed. Although all of the meters provide useful data, only the plate and

grid meters are necessary for proper amplifier use. At a repeater site where key-down service is the rule rather than the exception, measurement of heater usage and voltage provide data requisite to tube replacement. The anode exhaust-temperature metering circuit takes advantage of a thermal property of semiconductors. As the temperature changes the forward resistance of a diode changes in a nearly linear manner. The diode sensor is made a part of a bridge circuit, allowing calibrated operation. Calibration may
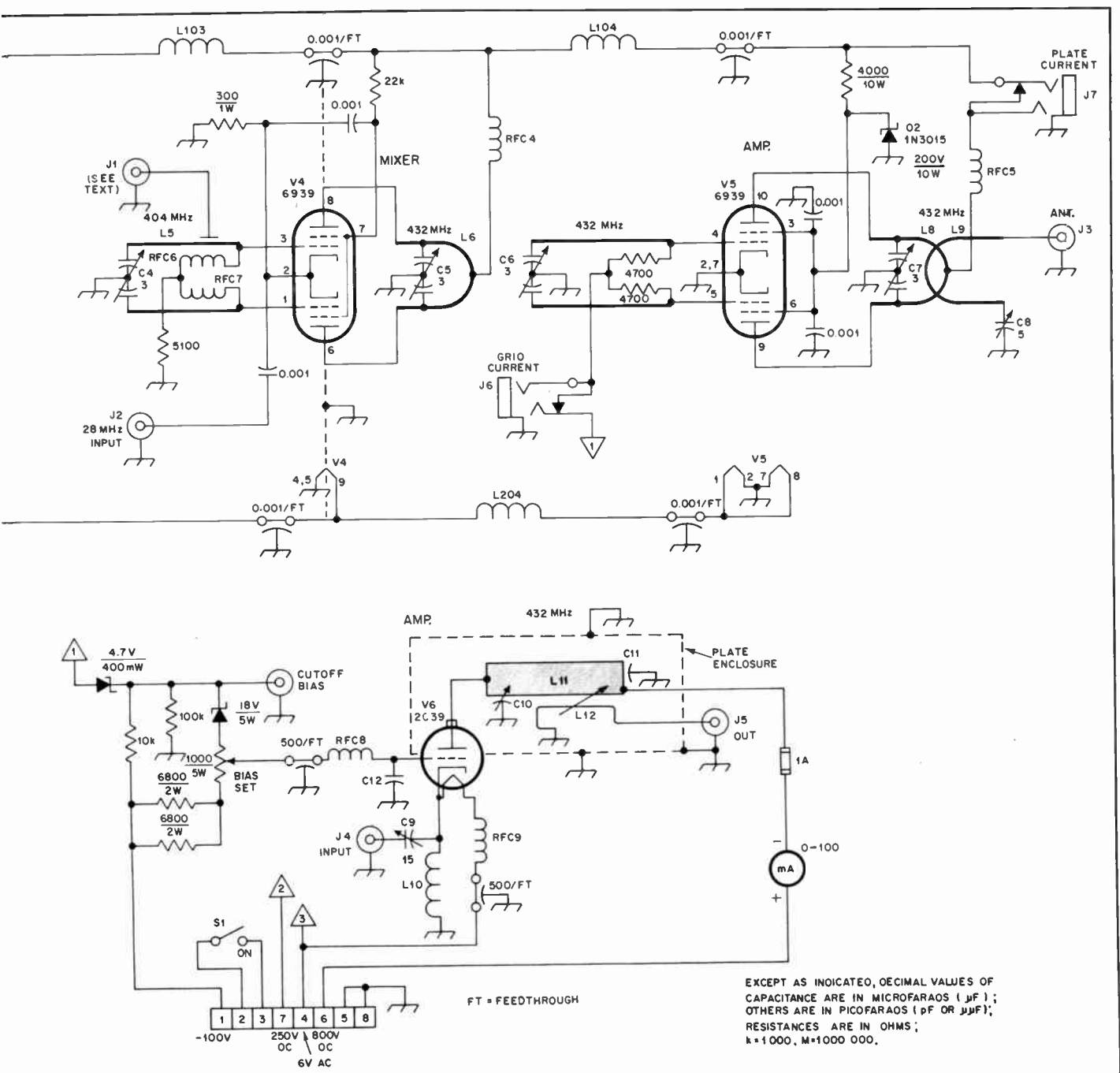
<sup>3</sup>Sutherland, "High-Performance 144 MHz Power Amplifier," *ham radio*, August, 1971.



be determined by packing the diode in ice for the low point ( $0^{\circ}\text{C}$ ) and immersing it in boiling water for the high point ( $100^{\circ}\text{C}$ ). The amount of heat dissipated by the tube is inversely proportional to the efficiency for a given power input. Low heat dissipation yields longer tube life.

High-power amplifiers require considerable attention to cooling. The plate compartment is pressurized by air from an external blower, and holes in the chassis allow a portion of this air to pass through the grid and cathode structure. Most of the air flows through the anode, a handmade Teflon chimney, then out the top cover. Aluminum screening is tightly

bonded around these two openings. No radiated rf could be detected around the chassis except within one inch of the anode exhaust hole.

To commence operation, the input should be adjusted for minimum VSWR with no voltages applied. The covers should be in place whenever voltage is present. Drive should *never* be applied without plate voltage and a load connected if the filament is energized. Cooling air must always be supplied whenever the filament is turned on.

After a 60-second warmup small amounts of drive may be applied. The plate circuit is then tuned for maximum output

indication. The drive level is then increased. Tuning and loading follow the normal procedure for any cathode-driven amplifier: Adjustments are made for maximum output and efficiency. When the desired plate output power has been achieved, the input circuit should be adjusted for minimum input VSWR.

#### Grounded-Grid 50-MHz Amplifier

Increasing use of 50-MHz transceivers and transmitters having outputs of 25 watts or more has created a demand for amplifiers to be used with such equipment as the driver. The grounded-grid amplifier of Fig. 22 is designed for this use. With 30



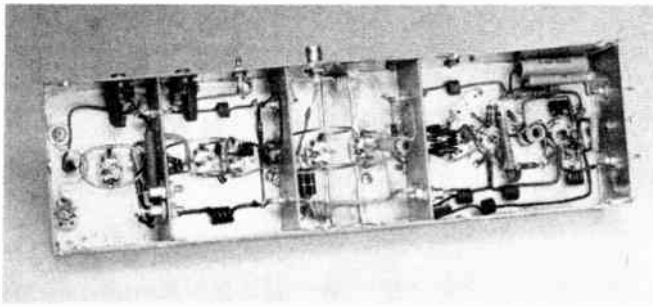


Fig. 12 — Bottom view showing stages for V1 through V5.

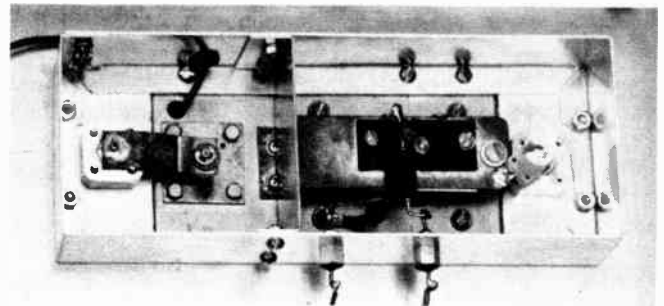


Fig. 13 — Bottom view of T-44 cavity.

watts or more of driving power it will deliver 600 watts cw output. As a Class-B linear under single-tone conditions, its rated PEP output is 750 watts.

### Circuit

The Eimac 3-500Z triode is designed for grounded-grid service. As shown in Fig. 25, driving power is applied to the filament circuit, which must be kept above rf ground by means of high-current bifilar rf chokes, RFC1 and RFC2. These are a central feature of the bottom view, Fig. 24. The input impedance is low, so the input circuit, L1, C1, tunes broadly, and the 50-ohm line from the exciter is tapped well up on L1. The plate circuit is merely a coil of copper tubing, L2, inductively tuned by means of a "shorted turn" of copper strip, rotated inside its cold end. See Fig. 23. Tuning is smooth and the rotating loop avoids many problems commonly encountered in tuning high-powered amplifiers by conventional methods. Plate voltage is shunt fed to the tube, thus preventing the high dc voltage from accidentally appearing on the output coupling loop or on the antenna line.

Most of the lower part of the schematic diagram has to do with control and metering, and is largely self-explanatory. The exciter voice-control relay shorts out R1, allowing grid current to flow, and making the amplifier operative, if the filament and primary-control switches, S1 and S2, have been closed. Feeding ac voltage to the plate-supply relay through J4, J5 and P1 prevents application of plate voltage without the filament and blower being on.

### Construction

The amplifier chassis is aluminum, 10 X 12 X 3 inches (254 X 305 X 76mm) in size, with the tube socket centered 3-1/8 inches (79 mm) from the front edge. The sheet-aluminum panel is 10 inches (254 mm) high. The decorative edging is "cove molding," used by cabinet makers for counter tops. Sides and back are also sheet aluminum. Where they need not be removable, parts are fastened together by pop-riveting. Tools and rivets for this work can be found in most hardware

stores. Perforated aluminum (cane metal) is used for the top and for covering the panel viewing hole.

Stretch the wire for the bifilar rf chokes before winding. Then, with the wires side by side, under tension, wind them on a form of wood or metal. This is left in until the choke ends are soldered in position. Then remove the form and coat the windings with coil cement to help maintain turn alignment.

Connections to the grid terminals (on opposite sides of the socket) are made with short 1/4-inch (6.3-mm) copper straps soldered to the pins and bolted to the chassis with no. 6 screws, nuts and lock-washers. Be sure that a clean, tight rf ground results.

In Fig. 23 it will be seen that the hot end of L2 is supported on the top of the two blocking capacitors, C3 and C4, which in turn, are mounted on the Teflon rod that serves as the form for RFC3. The ground end of L2 is supported on a vertical post made of 3/8-inch (9.5 mm) copper tubing, 1-3/8 inches (35mm) high. The end of the coil can be fitted with a heavy copper lug, or pounded flat. A hole is drilled in the flat portion and a 2-inch (50 mm) brass bolt runs through it and the post and chassis. Be sure that there is a permanent, solid rf ground at this point.

The shunt-feed rf choke is effectively across the tuned circuit, so it must be a good one. Handwinding as described below is strongly recommended, as no ready-made choke is likely to be as good. Teflon is slippery, so a light thread cut in the form will help keep the winding in place. If this cannot be done, prepare and wind two wires, as for the filament chokes. Feed the wire ends through one hole in the form, and wind a bifilar coil. Pull the other ends through the finish hole, bending one back tightly at the hole edge. Remove the other winding, which should leave a tight, evenly-spaced coil that makes an excellent vhf choke.

The blocking capacitors, C3 and C4, are mounted between brass plates, one of which is fastened to the top of the rf choke form with a sheet-metal screw. The other plate is connected to the hot end of L2 by means of a wrap-around clip of flashing copper. The lead to the tube plate cap is

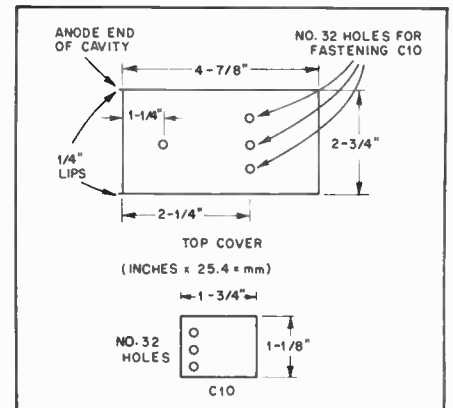


Fig. 14 — Layout details for modified top cover and brass capacitor flap. Inches X 25.4 = mm.

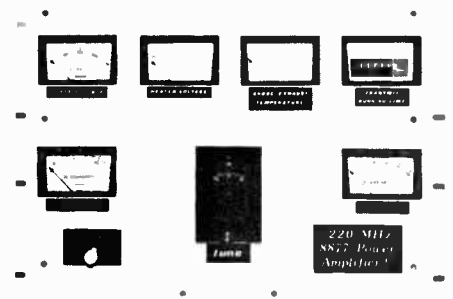


Fig. 15 — Front-panel layout of the 220-MHz kilowatt.

made with braid removed from a scrap of coax. A strip of flashing copper about 1/4 inch (6.3 mm) wide is also good for this. Use a good heat-dissipating connector such as the Eimac HR6.

The shorted-turn tuning ring is centered between the first two turns of L2. The ring is attached to a ceramic pillar, and that to a 1/4-inch (6.3-mm) shaft, the end of which is tapped for 8-32 thread. This shaft runs through a bearing mounted in a bracket 4 inches high and 2-3/4 inches (70 mm) wide, fastened to the chassis and the side of the enclosure. The output loading capacitor, C6, is also mounted on this bracket. It is one inch above the chassis, and the tuning-ring shaft is 3-1/4 inches (83 mm) above the chassis. The input



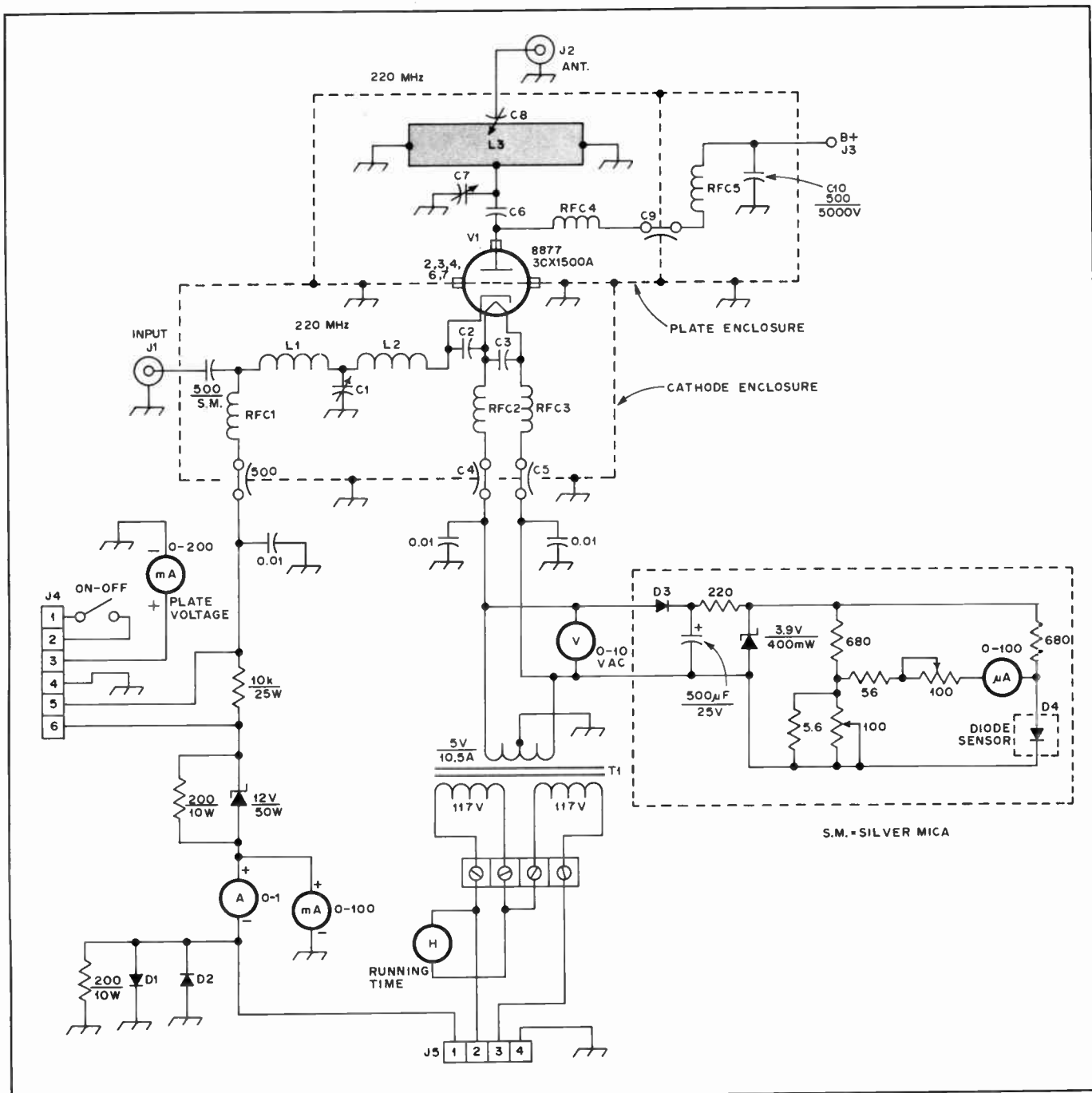


Fig. 16 — Schematic diagram of the 220-MHz amplifier. Unless otherwise specified, all capacitors are disk ceramic and resistors are 1/2-watt carbon composition. Inches  $\times$  25.4 = mm.

C1 — Air variable, 15 pF.  
 C2, C3 — Button mica, 500-pF, 500-V rating.  
 C4-C9, inclusive — Teflon capacitor (use 10-mil Teflon sheet) see Fig. 2 for dimensions.  
 C10 — Doorknob capacitor, 500 pF, 5-kV rating.  
 D1-D4 — 1000 PRV, 3A, HEP R0078 or equiv.  
 J1, J2 — Coaxial receptacle, type N.

J3 — High-voltage connector (Millen).  
 L1 — 3 turns No. 14, 1/4-inch ID, 3/4-inch long.  
 L2 — 1/4-inch wide, 2-3/8 inch long copper flashing strap.  
 L3 — Plate inductor (see Fig. 20).  
 RFC1 — 8 turns no. 18 enam. 1/2-inch dia, 3/4-inch long.

RFC2, RFC3 — 10 turns no. 18 enam. bifilar wound on 3/4-inch Teflon rod close wound.  
 RFC4 — 5 turns no. 16 enam. 1/2 inch ID, 3/4-inch long.  
 RFC5 — 12 turns no. 18 enam. wound on 1-M $\Omega$ , 2-watt composition resistor.  
 T1 — Filament transformer, 5.0 V at 10.5 A.

tuning capacitor, C1, is mounted under the chassis, with equal spacing between the three for symmetrical appearance.

The output coupling loop, L3, is just inside the cold end of L2. It can be adjusted for optimum coupling by "leaning" it slightly into or out of L2. Be sure that it clears the shorted turn throughout movement of the latter.

The coaxial output jack, J3, is on the

rear wall of the enclosure. A small bracket of aluminum grounds it to the chassis, independent of the bonding between the chassis and the enclosure. Plate voltage enters through a Millen 37001 high-voltage connector, J2, on the rear wall, and is bypassed immediately inside the compartment with a TV "doorknob" high-voltage capacitor, C5.

The blower assembly in the left rear

corner of the chassis draws air in through a hole in the back of the compartment, and forces it down into the enclosed chassis. The only air path is then back up through the socket and chimney (Eimac parts SK-410 and SK-406 recommended) and out through the top of the enclosure. The data sheet for the 3-500Z specifies an air flow of at least 13 cubic feet per minute, when the tube is operated at 500

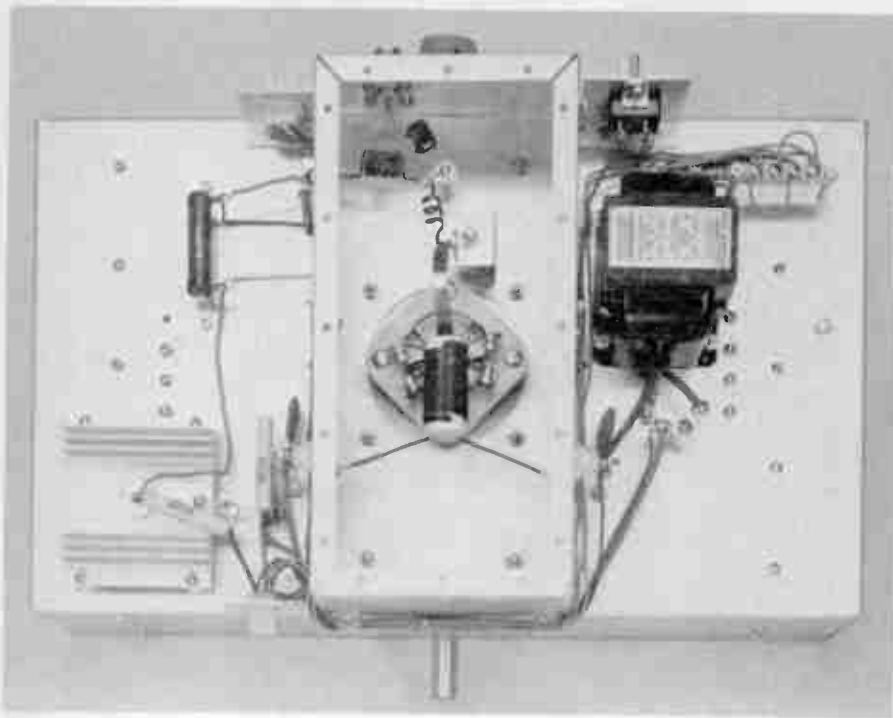


Fig. 17 — Bottom view of the amplifier. RFC2 and RFC3 can be seen above tube socket (bifilar winding). Copper strap is L2 shown connected to C1. Small coil is L1 and larger coil is RFC1. The grid of the tube should be grounded to the chassis with finger stock similar to that used in the plate line. Component mounted on the heat sink at left is the Zener diode used for biasing purposes.

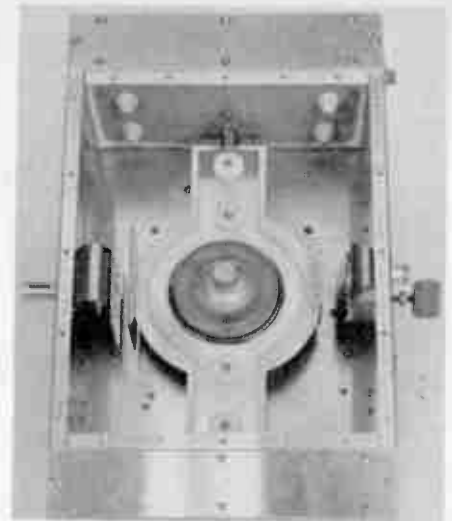


Fig. 18 — Interior view of the amplifier. Contact of the tube with "hot side" of C6 is accomplished with suitable finger stock (available from the tube manufacturer). This conductor, in conjunction with a similar one separated by the Teflon insulator, forms the L3/C6 combination. The entire assembly is sandwiched together by means of four insulated bushings (approximately 3/4-inch or 19-mm diameter). Placement of bushings is not critical. RFC4 can be seen at the right connected to C9. C8 is seen at the bottom center of the photo and has a nominal spacing of 1 inch (25 mm) to similar plate soldered to L3. Tuning capacitor, C7, can be seen in upper center of photo (see Fig. 20 for dimensions). Drive mechanism can be of builder's choice or see reference 3.

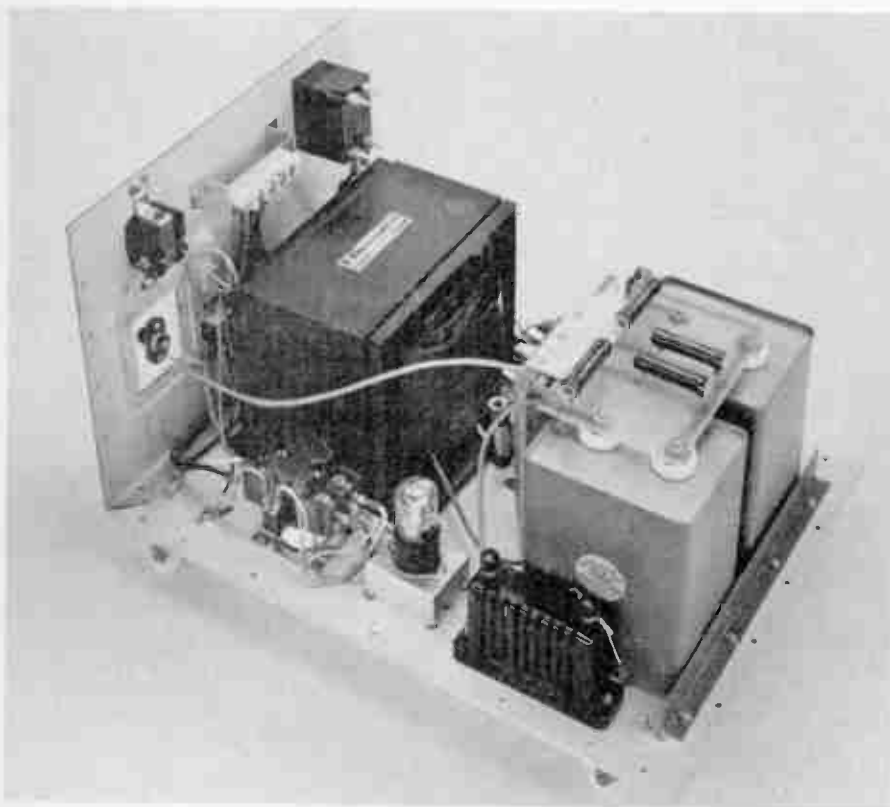


Fig. 19 — Interior view of the power supply.

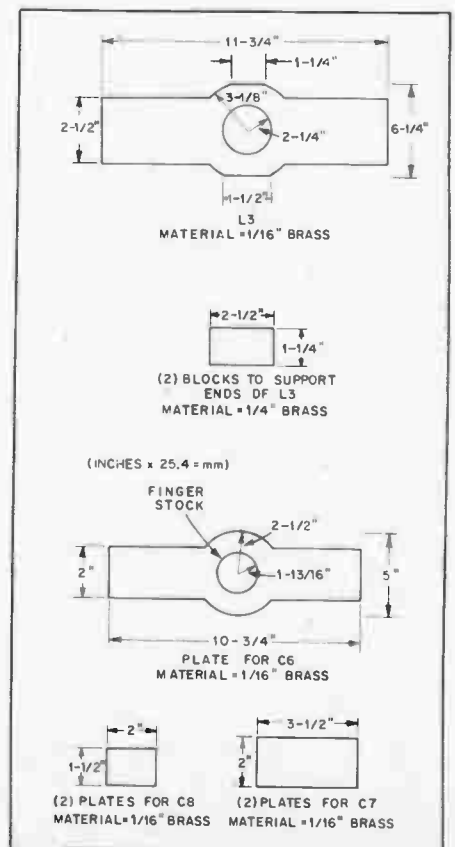


Fig. 20 — Construction details of plate line and associated components. Inches x 25.4 = mm.

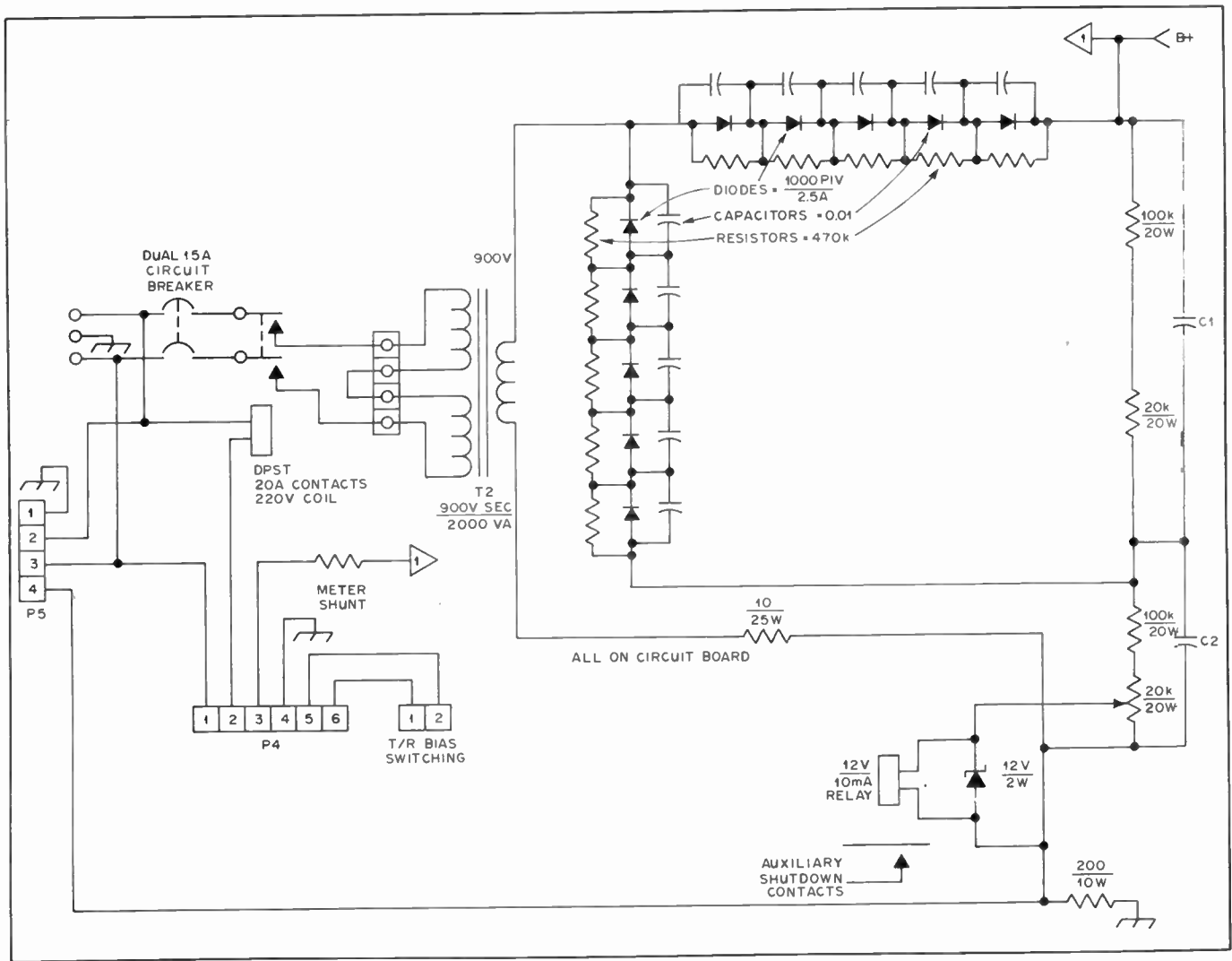


Fig. 21 — Schematic diagram of a suitable power supply for the amplifier. Unless otherwise specified, all capacitors are disk ceramic (1000 V) and resistors are 1/2-watt carbon composition.  
 C1, C2 — Filter capacitor 74  $\mu$ F at 2500 V  
 Sprague P49018.  
 Meter shunt used should be one supplied with movement for 4-kV full-scale.

watts plate dissipation. The ac leads for the blower motor come into the enclosure on feedthrough capacitors.

The meters are enclosed in a shield fastened to the front and side panels. Meter terminals are bypassed for rf inside the shield, and leads come through the chassis on feedthrough capacitors. The rocker-type switches just below the meters have built-in illumination. The high-voltage switch is not meant to control the plate supply directly, but rather through a relay, as in the 3000-volt supply shown in chapter 5. The plate meter is in the negative lead, so be sure that your supply is compatible with this arrangement. Do not use this system where a potential difference exists between the amplifier and power supply chassis. All power leads are made with shielded wire (Belden 8862) and all exposed points are bypassed to ground.

#### Adjustment and Use

Do not apply drive to the 3-500Z without the plate voltage being on. Also,

it is recommended that initial testing be done with low drive and a plate voltage of 1500 or less. With a 50-ohm load connected to J3, apply 1000 to 1500 volts through J2, and turn on the driver. Adjust the tuning ring inside L2 for a dip in plate current. Tune C1 for maximum grid current. Tune C6 and adjust the position of L3 with respect to L2 for maximum output. If the amplifier seems to be running properly, connect an SWR bridge between the driver and J1, and check reflected power. It should be close to zero. If otherwise, adjust the tap position on L1.

Tuning range of the plate circuit can be checked with a grid-dip meter, with the power off the amplifier. The range is affected by turn spacing overall, and at the cold end. The closer the first two turns are together the greater the effect of the tuning ring. No other tuning device is used, so some experimentation with diameter and length of L2 may be needed if you want other than the 49.8 to 52.7 MHz obtained with the graduated turn

spacing visible in the interior view. The highest frequency is reached with the ring in a vertical plane. Dimensions that affect tuning range are as follows: Grounded support for L2 — 1-1/8 inches (28-mm) from right side of chassis and 3-1/4 inches (83-mm) from rear. RFC3 mounting position — 4 inches (102-mm) from rear and 5-1/2 inches (140-mm) from left. Shorted turn approximately centered between turns 1 and 2 of L2. The start of L3 bends from the stator of C6 to near the start of L2. The end toward J2 passes between the first two turns of L2, clearing the tuning ring in any position of the latter.

Once the amplifier seems to work normally at moderate plate voltages, apply higher values, up to the maximum of 3000. Plate current, with no drive, should be about 160 mA. It can be lowered by inserting 0.1 to 0.4 ohm in series with R1 and the filament center-tap. A Zener diode, 2 to 9 volts, 10 watts, could do this job, as well.

Keep the amplifier tuned for maximum



Fig. 22 — Table-top 50-MHz amplifier of grounded-grid design, only 10 × 12 inches (254 × 305 mm) in size. Grid and plate current are monitored simultaneously. Knobs at the right are for input tuning, bottom; amplifier loading, center; and plate tuning, top.

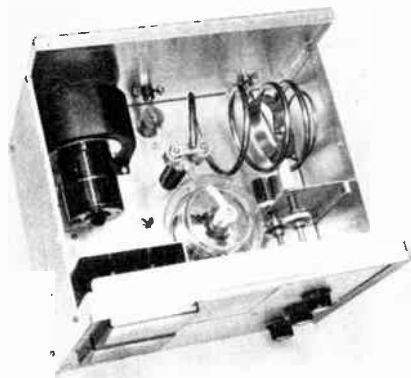


Fig. 23 — Interior view of the 50-MHz amplifier shows the shorted-turn tuning system, plate coil and output coupling, upper right. The tuning and loading controls are mounted on a bracket to the right of the 3-500Z tube and chimney. Meter shielding is partially visible in the left front corner.

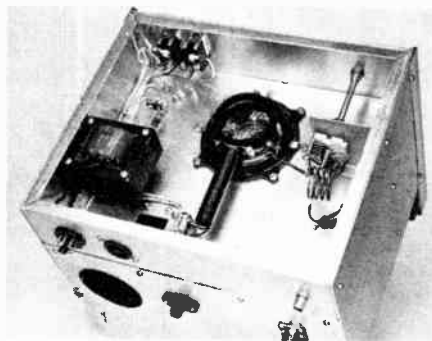


Fig. 24 — With the bottom cover removed, a look into the chassis from the rear shows the input circuit. L1, C1, right, the bifilar filament chokes, foreground, filament transformer and control switches. Opening in the rear wall is for air intake.

output. Do not decouple to reduce output; cut down drive and/or plate voltage instead. Adjustment for linear operation requires a scope. Maximum output, minimum plate current and maximum grid current should all occur at the same setting of the plate tuning. If they do not, the output loading is overcoupled, or there is regeneration in the amplifier. The plate-current dip at resonance is noticeable and smooth, but not of great magnitude.

Typical operating conditions given by the manufacturer are guides to good practice. The amplifier works well with as little as 1000 volts on the tube plate, so varying the ac voltage to the plate-supply transformer is a convenient way to control power level. It is seldom necessary to run the maximum legal power in vhf communication, so some provision for this voltage control is recommended. With just one high-voltage supply needed and no critical tuning adjustments, power variations from 100 to 600 watts output are quickly and easily made. This amplifier was built by WISL and described in *QST* for November, 1970.

#### A 2-kW PEP Amplifier for 144 MHz

Large external-anode triodes in a cathode-driven configuration offer outstanding reliability, stability and ease in obtaining high power at 144 MHz. The selection is somewhat limited and they are not inexpensive. Data on the recently introduced 3CX1500A7/8877, a high- $\mu$ , external-anode power triode, appeared very promising. A reasonable heater requirement (5 V at 10 A) and an inexpensive socket and chimney combination made the tube even more attractive.

The techniques employed in the design and construction of the cathode-driven 3CX1500A7/8877 amplifier described here (Figs. 26 to 30) have removed many of the mechanical impositions of other designs. Those interested in obtaining complete constructional details should refer to the two-part article appearing in December, 1973 and January, 1974 *QST*.

#### Input Circuit

The plate tank operates with a loaded  $Q$  on the order of 40 at 2-kW PEP and 80 at 1 kW. Typical loaded  $Q$  values of 10 to 15 are used in hf amplifiers. In comparison, we are dealing with a relatively high loaded  $Q$ , so losses in the strip-line tank-circuit components must be kept very low. To this end, small-diameter Teflon rods are used as mechanical drive for the tuning capacitor and for physical support as well as mechanical drive for the output-coupling capacitor. The tuning vane or flapper capacitor is solidly grounded through a wide flexible strap of negligible inductance, directly to the chassis in close proximity to the grid-return point. A flexible-strap arrange-

ment, similar to that of the tuning capacitor, is used to connect the output coupling capacitor to the center pin of a type-N coaxial connector mounted in the chassis base. Ceramic (or Teflon) pillars, used to support the air strip line, are located under the middle set of plate-line dc isolation bushings. This places these pillars well out of the intense rf field associated with the tube, or high-impedance end of the line. In operation, plate tuning and loading is quite smooth and stable, so a high-loaded  $Q$  is apparently not bothersome in this respect.

In this amplifier, output coupling is accomplished by the capacitive probe method. As pointed out by Knadle<sup>4</sup> "Major advantages of capacitive probe coupling are loading linearity and elimination of moving contact surfaces."

Capacitive-probe coupling is a form of "reactive transformation matching" whereby the feed-line (load) impedance is transformed to the tube resonant-load impedance ( $R_o$ ) of 1800 ohms (at the 2-kW level) by means of a series reactance (a capacitor in this case). At the 1-kW level,  $R_o$  is approximately twice that at the 2-kW PEP level. Therefore, the series coupling capacitor should be variable and of sufficient range to cover both power levels. Formulas to calculate the transformation values have been presented in *QST*.<sup>5</sup>

The electromechanical method of probe coupling used in this amplifier is easy to assemble and provides good electrical performance. Also, it has no moving-contact surfaces and enables placement of the output coupling, or loading, control on the front panel of the amplifier for ease in adjustment.

#### Support Electronics

The grid- and cathode-metering circuits employed are conventional for cathode-driven amplifiers. The multimeter, a basic 0-1 mA movement, is switched to appropriate monitoring points.

An rf-output monitor is a virtual necessity in vhf amplifiers to assure maximum power transfer to the load while tuning. Most capacitive-probe output coupling schemes presented to date do not lend themselves to built-in relative-output monitoring circuits. In this amplifier, one of these built-in circuits is achieved quite handily. The circuit consists of a 10:1 resistive voltage divider, diode rectifier, filter and adjustable indicating instrument. Two 7500-ohm, 2-watt carbon resistors are located in the plate compartment connected between the type-N rf-output connector and a BNC connector. A small wire was soldered to the center pin of the BNC connector, inside a Minibox, with the 1500-ohm,

<sup>4</sup>Knadle, "A strip-Line Kilowatt Amplifier for 432 MHz," *QST*, April and May, 1972.

<sup>5</sup>Belcher, "RF Matching Techniques, Design and Example," *QST*, October, 1972.



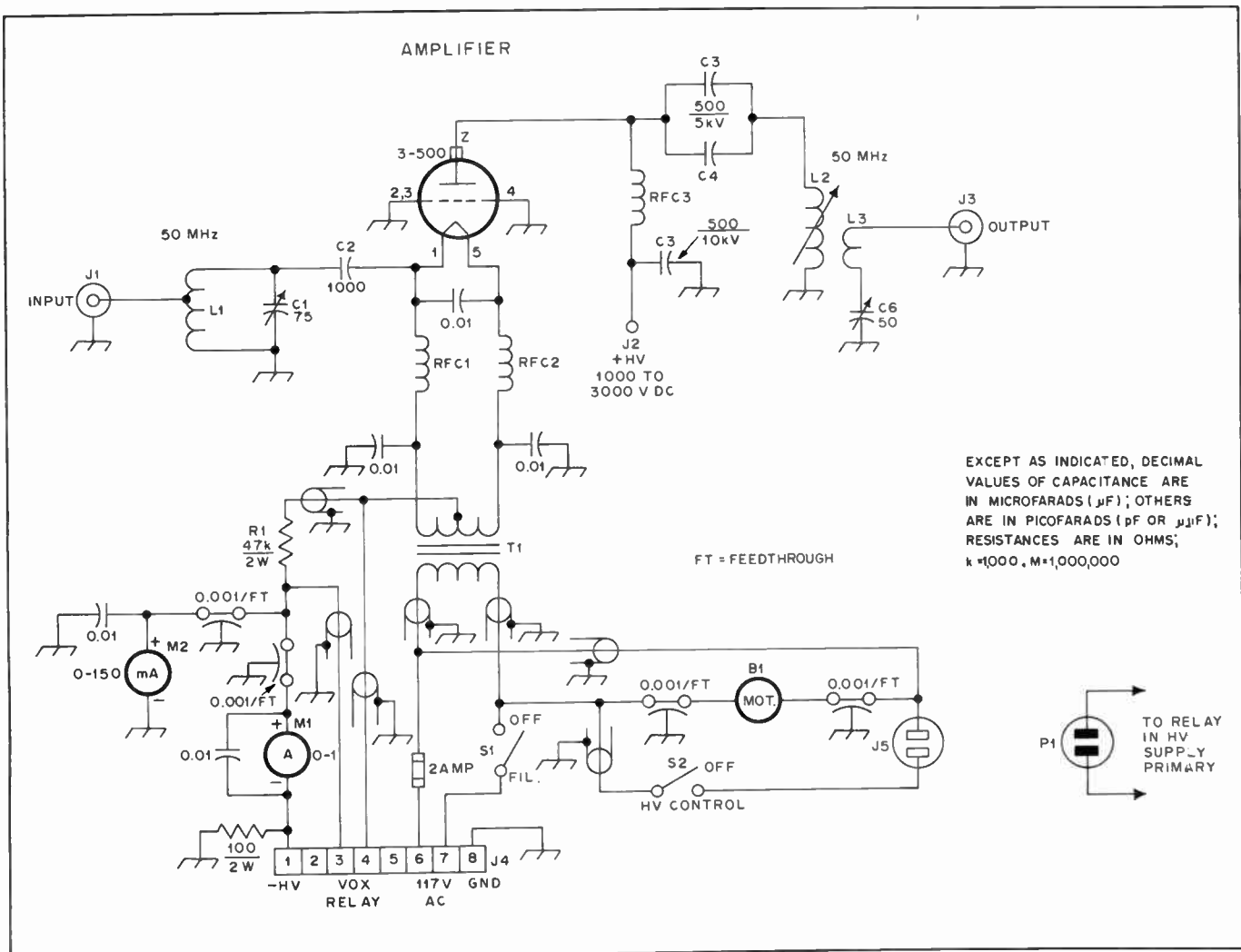


Fig. 25 — Schematic diagram and parts information for the 50-MHz grounded-grid amplifier. Inches  $\times$  25.4 = mm.

- B1 — Blower, 15 ft<sup>3</sup>/min or more.
- C1 — 75-pF variable (Johnson 167-4).
- C2 — 1000-pF dipped mica.
- C3, C4 — 500-pF 5-kV transmitting ceramic (Centralab 858S-500).
- C5 — 500-pF, 10-kV or more, TV "doorknob."
- C6 — 50-pF variable (Johnson 167-3).
- J1 — BNC coaxial receptacle.
- J2 — High-voltage connector (Millen 3700I).
- J3 — Type N coaxial receptacle.
- J4 — 8-pin male power connector, chassis-mounting.
- J5 — A receptacle, chassis mounting.

- L1 — 4 turns no. 12 enam, 1 inch long, 1 inch dia. Tap 2-1/2 turns from ground end.
- L2 — 3-1/2 turns 1/4-inch copper tubing, 3-1/2-inch dia, 5-1/4 inches long. Diameter is finished dimension, not that of form used for winding. See text and photo for turn spacing. Tuning ring is closed loop of 1/2-inch copper strip, 2-5/8-inch dia.
- L3 — 1 turn, 3-inch dia, and leads, made from one piece of 1/8-inch copper tubing or no. 8 wire.
- M1 — DC meter, 0-1 A (Simpson Wide-Vue, Model 1327).

- M2 — 0-300mA, like M1.
- P1 — A plug, on cable to power supply.
- R1 — 47 k $\Omega$ , 2-watt.
- RFC1, RFC2 — 21 turns each, no. 12 enam, 1/2-inch dia, bifilar.
- RFC3 — 30 turns no. 20 enam, spaced by same, on 3/4-inch Teflon rod, 3-3/4 inches long. Drill end holes 1/2 and 2-3/4 inches from top.
- S1, S2 — Spst, rocker-type, neon-lighted, Carling LT1L, with snap-in bracket.
- T1 — Filament transformer, 5 V, 15 A (Stancor P6433; check any electrical equivalent for fit under 3-inch chassis).

1-watt composition resistor and the rectifier diode joined at this point. Relative output voltage is fed, via feedthrough capacitors, to the level-setting potentiometer and multimeter switch.

A calibrated string of 2-watt composition resistors, totaling 5 M $\Omega$ , was installed to facilitate "on-the-spot" determination of power input, and to attest to the presence or absence of high voltage in the plate tank circuit. A full-scale range of 5000 volts is obtained with the 0-1 mA meter. If desired, the builder may use 10 500-k $\Omega$ , 2-watt, 1-percent resistors for the string, and reasonable accuracy will be obtained. Of course this monitor feature may be eliminated if other means are used

to measure and monitor plate voltage.

### Testing and Operation

The amplifier is unconditionally stable, with no parasitics. To verify this, a zero-bias check for stability was made. This involved shorting out the Zener diode in the cathode return lead, reducing bias to essentially zero volts. Plate voltage was applied, allowing the tube to dissipate about 885 watts. The input and output circuits were then tuned through their ranges with no loads attached. There was no sign of output on the relative output meter and no change in the plate and grid currents. As with most cathode-driven amplifiers, there is a slight interaction between grid and plate currents during

normal tune-up under rf-applied conditions. This should not be misconstrued as amplifier instability.

Tolerances of the Zener diode used in the cathode return line will result in values of bias voltage and idling plate currents other than those listed in Table 1. The 1N3311, a 20-percent tolerance unit, is rated at 12 volts nominal but actually operates at 10 volts in this amplifier (within the 20-percent tolerance).

All testing and actual operation of this amplifier was conducted with a Raytrack high-voltage power supply used in conjunction with the author's 6-meter amplifier. The power supply control and output cable harness was moved from one amplifier to the other, depending on the

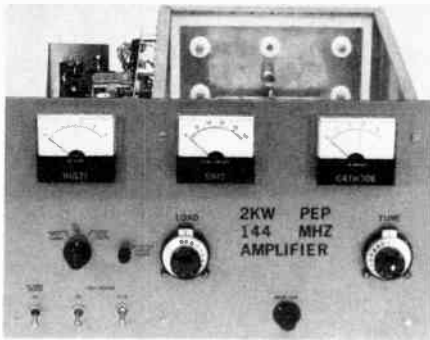


Fig. 26 — Front-panel layout of the 2-meter kilowatt amplifier.

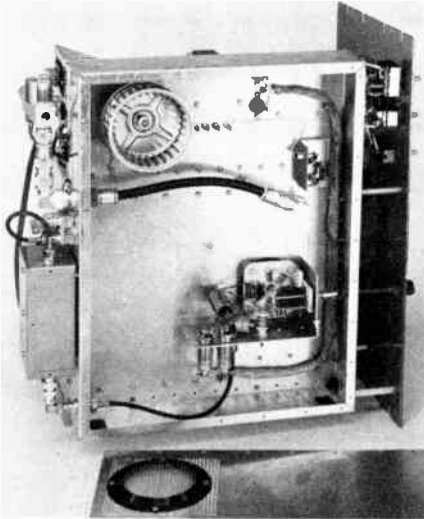


Fig. 27 — The placement of input-circuit components and supporting bracket may be seen in this bottom view. When the bottom cover is in place, the screened air inlet allows the blower to pull air in, pressurizing the entire under-chassis area. The Minibox on the rear apron is a housing for the input reflectometer circuit.

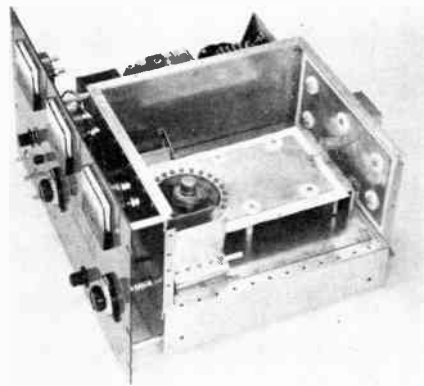


Fig. 28 — The tube and plate line is in place, with the top and side of the compartment removed for clarity. The plate-tuning vane is at bottom center. A bracket is attached to the side panel to support the rear of the Teflon rod supporting the tuning vane. The coil at the opposite end of the plate line is RFC1, connected between the high-voltage-bypass plate and the top section of the plate-line sandwich. Items outside the tube enclosure include the filament transformer, blower motor, relays, and a power supply to operate a VOX-controlled relay system.

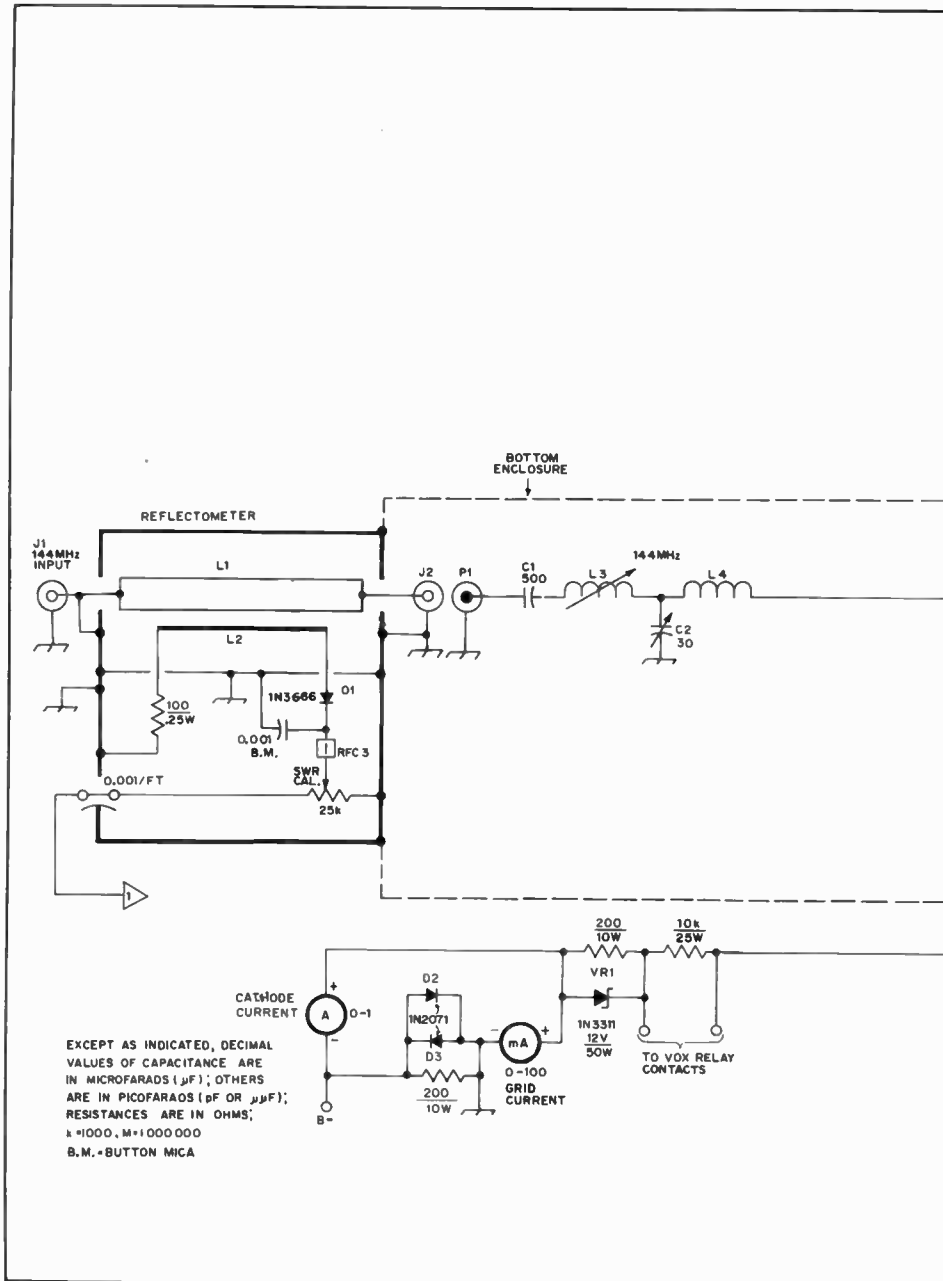


Fig. 29 — Schematic diagram of the 144-MHz amplifier. Included is information for the input reflectometer used as an aid to tuning the cathode circuit for low SWR. C7, C8, and C9 are fabricated as described in the text and Fig. 31. Inches  $\times$  25.4 = mm.

- B1 — Blower, Fasco 59752-IN or Dayton 2C610. Wheel diameter is 3-13/16 inches.
- C2 — 5- to 30-pF air variable, Hammarlund HF-30-X or equiv.
- C3, C4, C5, C6 — 0.1  $\mu\text{F}$ , 600-V, 20-A feedthrough capacitor. Sprague 80P3 or equiv.
- J1, J2, J6 — Type N.
- J3 — Type N.
- J4 — Coaxial panel jack, UG-22B/U, Amphenol 82-62 or equiv.
- J5 — HV connector, James Millen 37001 or equiv.
- L1 — Double-sided pc board, 1-1/4  $\times$  4-7/16 inches.
- L2 — 4-1/4 inches of no. 18 wire. L1 and L2 are part of the input reflectometer circuit.
- L3 — 6 turns no. 18 enam., 5/8-in. long on 3/8-in. dia form (white slug).

desired frequency of operation.

Drive requirements were measured for plate power-input levels of 1000 and 1600 watts with a Bird Model 43 Thru-line wattmeter and a plug of known accuracy. Output power was measured simultaneously with drive requirements at the 1000 and 1600 watt plate power input levels. A second Bird model 43 with a 1000-watt plug was used to measure


amplifier output into a Bird 1000-watt Terminal load. A 2500-watt plug would be necessary to determine output power at the 2-kW input level, so I stopped at the 1000-watt output point and worked backwards to calculate apparent stage gain and efficiency.

Efficiency measurements also were made employing the "tube air-stream heat-differential" method. Several runs

Table 1

Performance Data

Power input, watts	1000	1600
Plate voltage	2600	2450
Plate current (single tone)	385 mA	660 mA
Plate current (idling)	50 mA	50 mA
Grid bias	-10V	-10V
Grid current (single tone)	35 mA	54 mA
Drive power, watts	18	41
Efficiency (apparent)	59.5%	61.8%
Power gain (apparent)	15.2 dB	13.9 dB
Power output, watts	595	1000

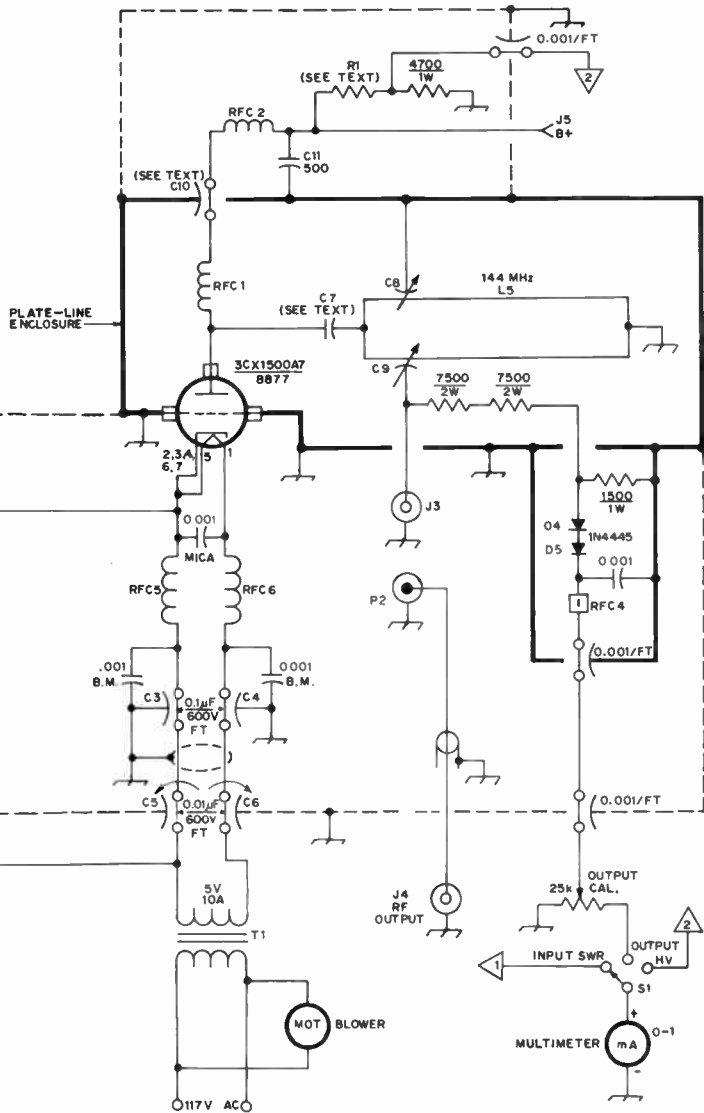

- L4 — 3 turns no. 14 enam., 5/8-in. long × 9/16-in. ID. Lead length to L3 is 5/8-in. Lead length to cathode bus is 3/4-in.
- L5 — Air-dielectric strip line. See text and Fig. 30.
- P1 — Type BNC.
- P2 — Type N.
- R1 — Meter range multiplier. Ten 500-kΩ, 2-W composition resistors in series.
- RFC1 — 7 turns no. 16 tinned, 1/2-in. ID × 1-in. long.

- RFC2 — 18 turns no. 18 enam., close wound on 1-MΩ, 2-watt composition resistor.
- RFC3, RFC4 — Each 2 ferrite beads on component leads.
- RFC5, RFC6 — 10 turns no. 12 enam., bifilar wound, 5/8-in. dia.
- S1 — Single-pole, three position rotary switch, non-shorting contacts.
- T1 — 5-V, 10-A secondary; center tap not used, Stancor P-6135 or equiv.

were made at 885 watts static dc and normal rf input. Apparent efficiencies of 62 to 67 percent were noted. These values were about five percent higher than the actual power output values given in Table 1. Both efficiency measurement schemes serve to confirm that the amplifier is operating at the upper limit of the theoretical 50 to 60 percent efficiency range for typical Class AB2 amplifiers.

To commence routine operation, the variable capacitor in the input circuit should be set at the point where lowest input VSWR was obtained during the "cold-tube" initial tube-up. The ability of the plate tank to resonate at 144-145 MHz with the top cover in place should be verified with a grid-dip meter, via a one-turn link attached to the rf output connector. Top and bottom covers are

then secured. As with all cathode driven amplifiers, excitation should never be applied when the tube heater is activated and plate voltage is removed. Next, turn on the tube heater and blower simultaneously, allowing 90 seconds for warm-up. A plate potential between 2400 and 3000 volts then may be applied and its presence verified on the multimeter. The power supply should be able to deliver 800 mA or so. With the VOX relay actuated, resting current should be indicated on the cathode meter. A small amount of drive is applied and the plate tank circuit tuned for an indication of maximum relative power output. The cathode circuit can now be resonated, tuning for minimum reflected power on the reflectometer, and not for maximum drive power transfer. Tuning and loading of the plate-tank circuit follows the standard sequence for any cathode driven amplifier. Resonance is accompanied by a moderate dip in plate/cathode current, a rise in grid current and a considerable increase in relative power output. Plate-current dip is not absolutely coincident with maximum power output, but it is very close. Tuning and output-loading adjustments should be for maximum efficiency and output as indicated on the output meter. Final adjustment for lowest VSWR at amplifier input should be done when the desired plate input-power level has been reached.

**A Conduction-Cooled Amplifier for 432 MHz**

Equipment for 432 MHz varies in style, size, complexity and ancestry. Some stations use converted uhf fm transmitters that once saw duty in taxicabs or the like. Others have been able to build up-converters using tubes such as the 6939.<sup>6</sup>

The design criteria for a desirable amplifier were simple — a table-top conduction-cooled (quiet) unit that would deliver 100-watts output at a drive level of less than 10 watts. The table-top configuration would be more attractive to many station owners than would the old reliable rack-and-panel system of days gone by. The conduction-cooling requirement was

<sup>6</sup>Moretti, "A Heterodyne Exciter for 432 MHz," QST, November, 1973 (also see Feedback, QST, March, 1974, page 83).

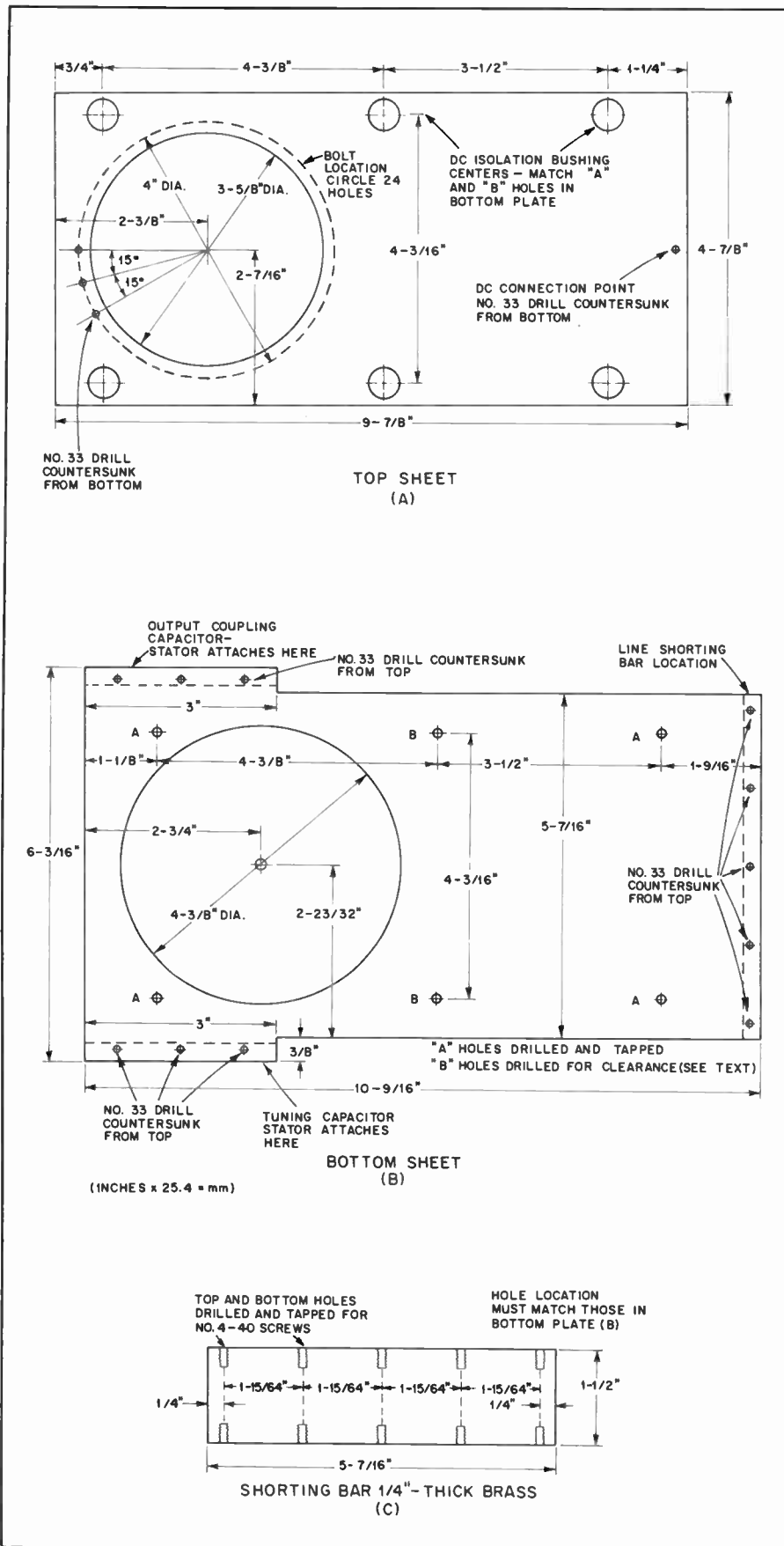


Fig. 31 — The 432-MHz amplifier built by WA1JLD and WISL.

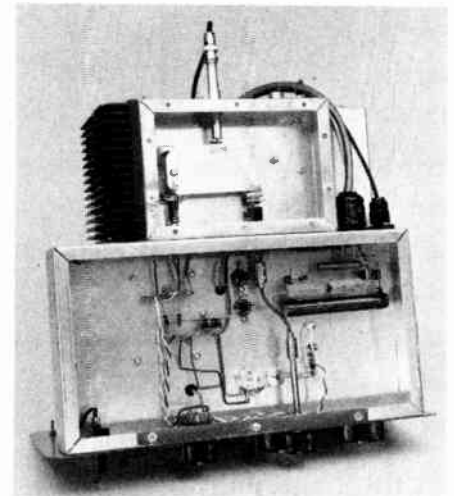


Fig. 32 — A look at the bottom of the amplifier reveals the grid compartment (top center) and the ac and dc connection cables from the power supply. A grid line is tuned by means of a butterfly type of capacitor mounted on phenolic so that the total capacitance is reduced. A small disk on the end of a coaxial section provides capacitive input coupling to the grid circuit. The flexible coupling shown here has since been replaced by two universal-joint type of connectors to remove some annoying backlash in the tuning control. A high-wattage dropping resistor, part of the screen supply circuitry, is shown at the right.

to get away from the blower/air-hose/insulated-box problems that follow the usual external-anode design. At the 100-watt output level, some transmission-line loss could be tolerated and still allow the use of a modest antenna for satellite access.

### Amplifier Circuitry

The amplifier (Figs. 31 to 35) draws heavily upon previous designs that utilized the air-cooled, external-anode tubes as shown in Fig. 33 and in the photographs. A half-wave grid line is fabricated from double-sided pc-board material. The input-coupling method departs slightly from previous examples, but only in the mechanics of adjustment. The plate line is similar to published information, with slight variations in the method of tuning.

Input coupling to the amplifier is by means of a capacitive probe to the grid line. A small tab of copper is soldered to the grid line and forms one side of the



**Table 2**  
**Operating Conditions**

432-MHz drive power watts	432-MHz output power watts
2	30
4	50
5	80
7	100
9	140

$E_p$  — 1000 V  
 $I_p$  — 60 mA, zero signal.  
 $I_p$  — 300 mA, single tone (cw), 140 W output.

capacitor. A disk on the center conductor of a coaxial section is the movable portion of the coupling. This coaxial section is fabricated from pieces of brass tubing that will slide together, telescope fashion. A BNC chassis-mount fitting with the threads filed down is soldered into the inner, movable piece of tubing to allow ease of connection from the exciter. A piece of copper wire and a couple of Teflon disks extend the center conductor for attachment of the capacitor plate inside the grid compartment. Once adjusted, the sliding portion is held in place by means of a small compression clamp.

The plate line is the familiar half-wavelength variety, with capacitive tuning provided by movable vanes or "flappers." In earlier versions using this tuning scheme, the flappers were moved by means of string that was allowed to wind or unwind around a shaft, providing front-panel control. After a few instances of loss of control, caused by the nylon fishing line melting or becoming untied, the writers decided that there had to be a better way. Accordingly, the cam-on-a-rod method was tried and found satisfactory. Both plate-tuning and output-coupling flappers are adjusted in this manner (Fig. 34).

### Cooling

Several tests were performed to check the effectiveness of the thermal-link/heat-sink cooling system. With the aid of Temprombes,<sup>7</sup> it was determined that the tube would stay within maximum temperature ratings while dissipating 100 to 200 watts of dc. A liberal coating of thermal-conducting grease was used to aid heat transfer. More on this subject later.

Early tests with only dc applied, and later ones with the full dc and rf voltages present, confirmed that at the 100-watt output level no forced-air cooling was required. At higher output levels of 175 to 200 watts, the temperatures on the anode and heat sink were still below the maximum allowed by the manufacturer, but high enough that it was felt prudent to

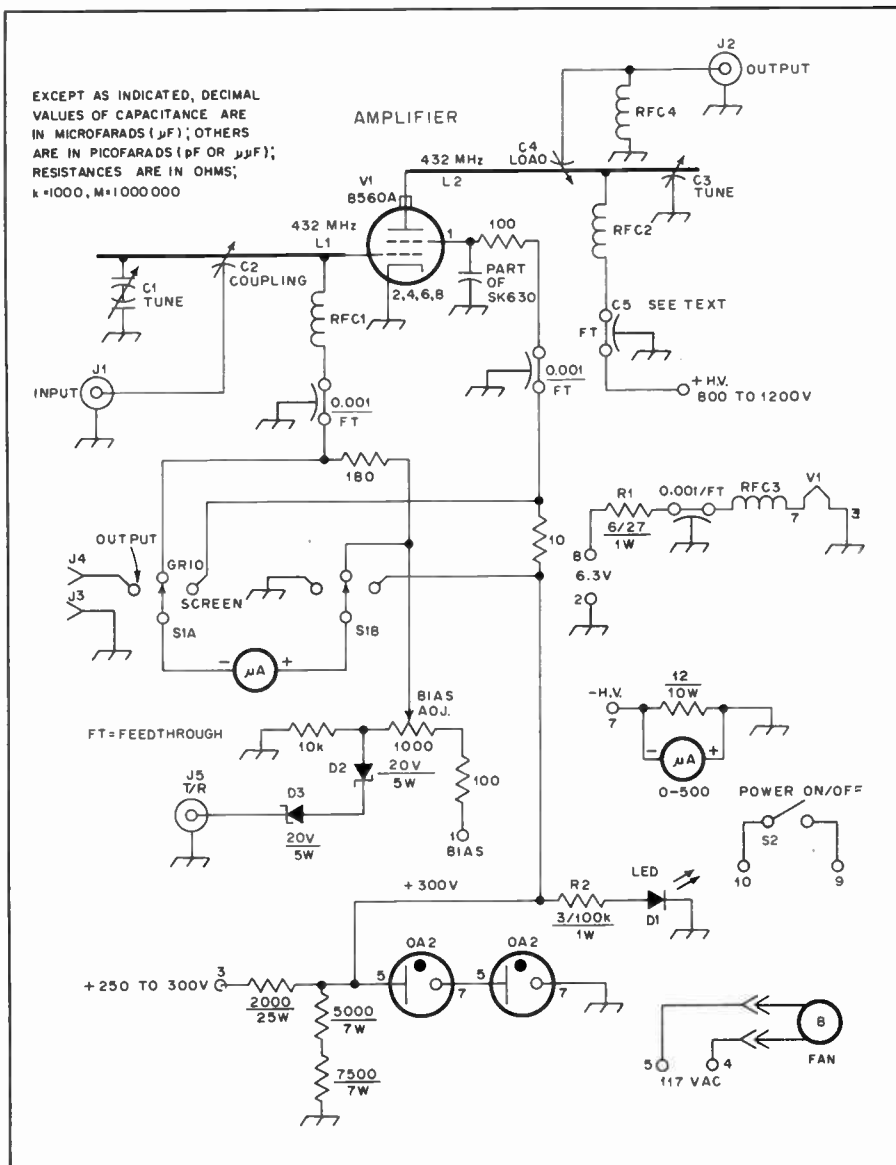


Fig. 33—Schematic diagram of the 432-MHz amplifier. Inches  $\times$  25.4 = mm.

- C1 — 1.8- to 5.1-pF air variable, E. F. Johnson 160-0205-001. Mount on phenolic bracket.
- C2 — 1/2-inch dia. disk on center conductor of coaxial extension. See text and photograph.
- C3, C4 — Spring-brass flapper type tuning capacitors. See text and Fig. 33.
- C5 — 2-1/2  $\times$  4-inch pc board, single-sided, with 0.01-inch thick Teflon sheet for insulation to chassis. Copper-foil side mounted toward the chassis wall.
- D1 — 1/4-inch dia. LED.
- J1 — BNC chassis-mount connector with threads filed to fit inside brass sleeve.
- J2 — Type "N" coaxial connector.
- J3, J4 — Tip jacks or binding posts.
- J5 — Phono-type connector. External relay contacts should be wired to short J5 for "carrier on" condition.
- J6 — High-voltage connector, James Miller 37001.
- L1 — 1-3/4  $\times$  4-inch double-sided pc board, spaced 7/8-inch from chassis.
- L2 — 3-1/2  $\times$  6-1/4-inch double-sided pc board or aluminum strip. Length from tip of line to tube center is 7-1/8 inches. See Fig. 33.
- Heat Sink — Astrodyne no. 3216-0500-A00D0, 5  $\times$  5 inches. Can be painted flat black or anodized for better dissipation.
- R1 — 27-ohm, 1-W, 6 in parallel.
- R2 — 100-k $\Omega$  1-W, 3 in parallel.

add a quiet "whisper" fan for safety. Operational tests proved that the added background noise was not distracting to the operator.

### Construction

There are several configurations possible for the package, and the constructor should feel free to mold them to fit his idea of how things should be assembled. An LMB cabinet (CO-1) was selected for

an enclosure because it matches many of the "gray boxes" found in a lot of shacks. Rather than mount the heat sink through an unsightly hole in the rear panel of the cabinet, it was decided to mount the amplifier parallel to the front panel. This places the heat sink inside, but there is adequate ventilation through the box to allow proper cooling. This mounting scheme also permits a fan to be mounted inside, so that there are no awkward

<sup>7</sup>Temprombes® Test Kit, by Tempil®, Hamilton Blvd., South Plainfield, NJ 07080.

protuberances to worry about behind the cabinet. A standard-size chassis is used to fill the gap between the panel and the amplifier proper, and incidentally to provide mounting space for peripheral electronics. As long as the parts placement within the amplifier grid and plate compartments is not changed from the design given here, it will not matter what is done externally.

The grid compartment is a 5 × 7 × 2-inch (127 × 178 × 50-mm) aluminum chassis with captive nuts in the bottom lip to permit securing the bottom plate. For the plate compartment a 5 × 10 × 3-inch (127 × 254 × 76-mm) aluminum chassis is modified to provide better mounting surfaces for the heat sink and to allow the plate-tuning flapper to be mounted on the end wall of the compartment. One end of the chassis was removed and pieces of aluminum angle stock were fastened around the open end. These pieces were drilled to accept no. 8-32 screws that thread into tapped holes in the heat sink. Tapped holes in the top surface of the heat sink and captive nuts in the top lips of the chassis permit a perforated top plate to be fastened securely for minimum rf leakage. Total dimensions are given in Fig. 34.

### Tube Placement

An Eimac SK-630 socket and SK-1920 thermal link are used in mounting the tube and conducting the heat away from the tube and conducting the heat away from the tube. The thermal link is made of toxic beryllium oxide (BeO). *The manufacturer's caution against abrasion, fractures or disposal should be heeded.* Parts placement in the anode-block area is critical if efficient heat transfer and minimum strain on the tube are to be obtained. The tube socket must have sufficient clearance in its mounting hole that some lateral movement toward or away from the heat sink is allowed. The socket is secured to the chassis with the usual toe clamps supplied. Because of the rim formed on the socket by the integral screen-bypass capacitor, a spacer is needed between the thermal link and the heat sink. A piece of copper, 1/4-inch (6.3-mm) thick and about 2-3/4 × 4-1/2-inches (70 × 114-mm) serves as the spacer, as well as providing excellent heat transfer to the inner face of the heat sink. This copper spacer and the BeO thermal link are both held in place between the tube anode and the heat sink by the pressure applied by the ceramic pillars. The anode end of the plate line is bent up to form a surface that will permit screws to thread into the insulators. In the early version of the amplifier this shaped and bent piece of aluminum was only long enough to provide some mounting surface to which the plate line (double-sided pc board in this instance) was fastened by means of five no. 6-32 screws and nuts with lock washers. The photograph shows this particular scheme in the top view. A later

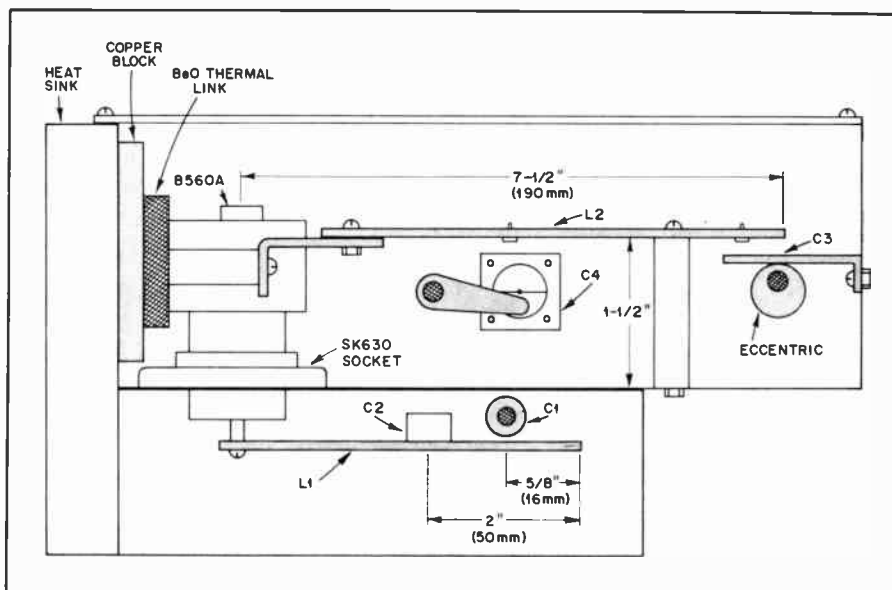


Fig. 34 — Cutaway drawing from the side of the grid and plate compartments. The plate line may be made of two pieces, as shown here, or of one single piece of aluminum strip. C4 is shown from the end-on view. The arm that moves C4 and the eccentric that moves C3 are fastened to their insulated shafts by epoxy cement. Small Teflon buttons prevent accidental shorts between the capacitors and the plate line. (Inches × 25.4 = mm).

version had the pc board replaced with an aluminum strip of the same size. A still-later test was made with the anode-clamp/plate line all constructed from one piece of aluminum. No difference in plate-circuit performance could be noticed, which was the reason for the tests of different materials.

A moderate coating of thermal-conducting grease should be applied between the copper plate, the heat sink, the thermal link, and the anode block. Don't overdo it, however. In one test a glob of the material found its way down to the screen ring, and the combination of rf and dc voltages between the screen and plate caused the material to break down.

### Power Supply

Most of the earlier testing of this unit was performed while using the Heath HP-23A to supply all voltages. The amplifier can be operated at the 80- to 100-watt output level without unduly taxing the capability of this supply. Accordingly, the wiring and plug connections were made up with this feature in mind. When a larger supply was constructed for tests at the 200-watt level, connections were made compatible with those on the Heath supply as far as practicable. When using the HP-23A, provision must be made to drop the filament potential to the nominal 6.0 V required by the 8560A heater. A voltage-dropping resistor for this purpose is located under the support chassis. Heater voltage should be measured at the tube socket, not at the power supply. The newer power supply, HP-23B, can be used if the series resistance added is sufficient to drop the potential from 12 to 6 V as

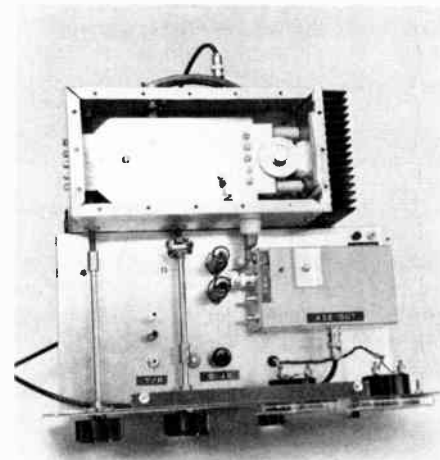


Fig. 35 — The amplifier chassis is mounted parallel to the front panel. A varactor-diode tripler is mounted on the subchassis, at the right. This view of the amplifier shows the ceramic insulators that provide pressure to hold the tube anode against the thermal link and the heat-sink assembly. A half-wavelength plate line occupies most of the length of the chassis, with a flapper type of tuning capacitor mounted on the left wall. The two VR tubes, center, are regulators for the screen voltage. Insulated shafts extend into the plate compartment, under the plate line, where they rotate eccentric disks to provide tuning control. Two tip jacks at the extreme right allow a cooling fan to be connected, if needed for higher power operation.

needed by the tube.

### Adjustment and Operation

Initial testing should be performed while operating the amplifier at reduced plate and screen voltages, if possible. Output coupling should be at maximum, and the input-coupling probe should be near maximum. Again, do not adjust the

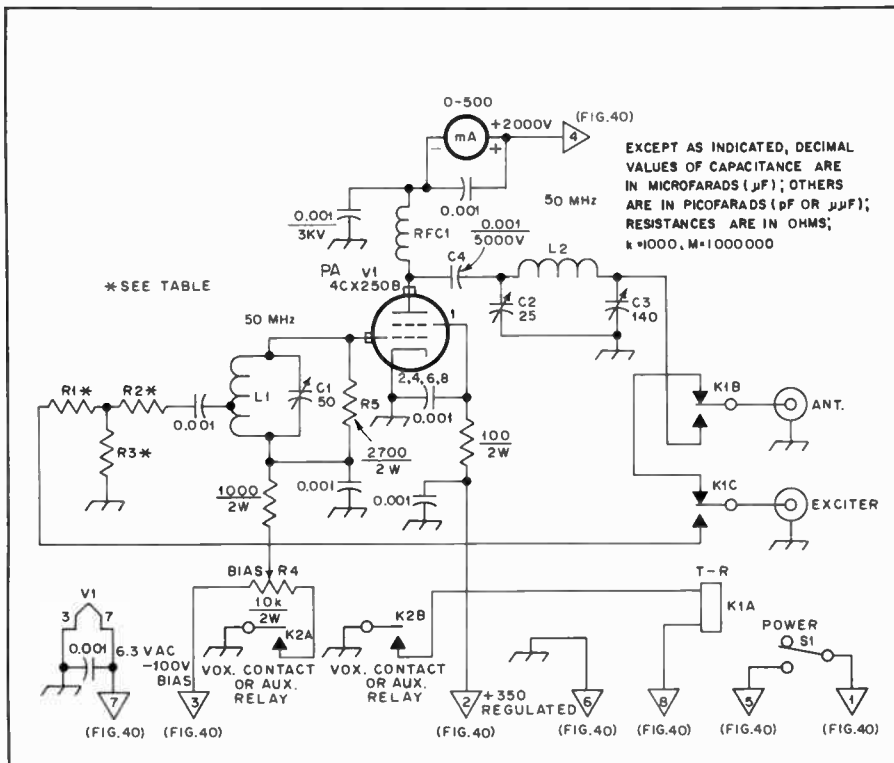


Fig. 36 — Schematic diagram of the 500-W amplifier for 6 meters. Unless otherwise specified, capacitors are disk ceramic and resistors are carbon composition. (Inches  $\times$  25.4 = mm).

- C1 — 50 pF, receive spacing.
- C2 — 25 pF, 3 kV (surplus cap. in unit).
- C3 — 140 pF, receive spacing.
- C4 — Cer. cap. 2 paralleled 500 pF, 5 kV.
- K1 — Dpdt relay, 12-V coil (can have dc/power type contacts but rf design preferable).
- K2 — Dpdt relay. Either T-R contacts in exciter or

- aux. relay if only spst option available.
- L1 — 6 turns no. 14 solid wire, 1/2-inch dia, 1-1/4 inch long. Tap 1-1/2 turns from gnd end.
- L2 — 5 turns no. 10 solid wire, 1-3/8 dia, 2 inch long (see text).
- RFC1 — 35 turns no. 22 enam. wire on 5/8-inch dia cer. ins.

exciter circuits to make up for misadjustment of the amplifier. Input power should be adjusted by increasing or decreasing the 432-MHz excitation to the amplifier. An output power indicator should be used as an aid in adjustment of the amplifier. Provisions were made in the wiring to the multi-meter switch to display a sample of rf energy, such as might be obtained from a directional coupler.<sup>8</sup> The input-probe spacing and the grid-line tuning should be adjusted for maximum drive to the tube; this should be concurrent with minimum SWR as seen by the exciter. Move the coupling probe in small increments — the proper position will tend to be somewhat difficult to find. Output coupling and plate tuning should be adjusted for maximum output. The reason for starting with maximum coupling is that with minimum coupling and reactive loads, the amplifier could be unstable. Loading should be decreased until there is a smooth, but not sharp, dip in plate current. A reading in the vicinity of 250 to 300 mA at resonance is about right, at a plate potential of 800 V. As with most tubes in this family, maximum output is seldom achieved at minimum plate current. Use the output power

as an indication of proper operation, but be sure that the screen is not abused — small amounts of negative screen current are no cause for alarm. In all cases, do not exceed the power dissipation rating of the tube element concerned.

It is not practical to operate this tube in this configuration at more than 1200-V plate potential. Tests were made at 1500 V, with disastrous results. At that dc level, with the added rf voltage, the stress across the BeO thermal link caused it to become "very unhappy." This caused it to produce frying sounds, which made the authors unhappy. The condition also caused a reduction of plate-circuit efficiency and much unwanted heating of nearby metal parts. Investigation of the phenomenon showed that the high Q of the circuit caused the fault. Rather than do a complete redesign of the plate circuit and because the initial goal was a 100-watt unit, the decision was made to leave well enough alone and recommend a 1200-volt limit. This unit was originally described by WISL and WAIJLD in *QST* for January, 1976.

#### A Low-Drive 6-Meter PA

There have been some excellent articles on 6-meter amplifiers in the 1- and 2-kW PEP levels. Usually grounded-grid design is used and the amplifiers require exciters



Fig. 37 — Designed and built by Dick Stevens, W1QWJ, this amplifier fills the need for a low-drive model usable with 10-watt exciters.

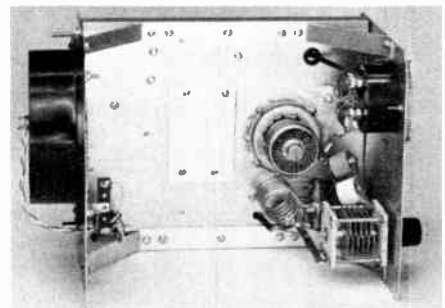


Fig. 38 — Top view of the amplifier (note paralleled ceramic capacitors for C4).

in the 100-watt class. The new popular solid-state 6-meter transceivers that develop approximately 10-watts PEP fall short of the necessary drive for grounded-grid design. This amplifier can easily be driven to 500-watts PEP input by transmitters in this power class.

#### The Circuit

A single 4CX250B is used in a conventional grounded-cathode arrangement (Fig. 36). The tuned grid circuit and the pi-network in the output is a standard design that works well on 6 meters. Driving power is fed into the tuned grid circuit through a 50-ohm T pad. Selection of the correct T-pad value will compensate for driving power of a watt or so up to 25 watts. R5 provides very heavy swamping and assures that the amplifier is completely stable. If R5 resistor is omitted for drive of less than 1 watt, the amplifier will have to be neutralized. Another advantage of the T pad and resistive input is a more constant load to the driving stage.

In the plate circuit, heavy copper-strap conductors are used to provide low inductance leads. The output capacitance of the 4CX250B (4.4 pF) plus strays and the plate tuning capacitance should be 10 to 12 pF for a reasonable circuit Q. The amplifier plate circuit should resonate at 50 MHz with the tuning capacitor (C1) as

<sup>8</sup>McMullen, "The Line Sampler," *QST*, April, 1972. Also in *FM and Repeaters for the Radio Amateur*, chapter 10, and *The Radio Amateur's VHF Manual*, chapter 14.



near minimum value as possible.

When drive is provided by a transmitter, a dpdt relay (K1) places the amplifier in the line in the transmit condition and connects the antenna to the transceiver in the receive condition. Cutoff bias is applied to the amplifier in the receive condition and is reduced to the operating value while transmitting by grounding one end of the bias potentiometer, R4. A double set of VOX send/receive contacts is required to perform these two functions (K2).

**Construction**

An LMB CO-7 cabinet is used as the

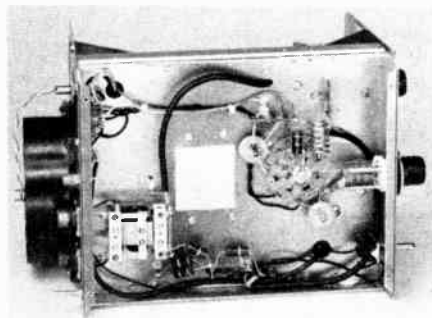


Fig. 39 — Bottom view of the amplifier.

basic amplifier housing (Fig. 37). It is necessary to add four small brackets to stiffen the front and back panels. Two pieces of 1/2 x 1/2-inch (12.7 x 12.7-mm) Reynolds aluminum angle stock are added to the sides of the built-in chassis to provide additional strength and provide an air seal between the bottom and top of the chassis. All the perforated holes above the top of the chassis *must* be covered with masking tape to make the top portion of the cabinet airtight. Directly beneath the 4CX250B tube socket, a large hole is punched in the bottom of the cabinet for an air entrance. The photograph of the amplifier shows that the 4CX250B does not have a chimney. It was later found that the chimney *must* be used to provide adequate cooling. A 4-inch diameter hole is cut in the back panel of the cabinet and a 5-inch Roton Whisper fan is mounted over the hole to exhaust air from the cabinet.

Air flow is through the bottom of the cabinet, through the socket of the 4CX250B, through the chimney into the anode and out of the cabinet through the exhaust fan. Very little blower noise is generated using this method of cooling as compared to the conventional squirrel-cage blower fan. The amplifier construction is quite simple as can be seen from

Figs. 38 and 39, and can be duplicated easily.

**Results**

A suitable power supply is shown in Fig. 40. With 2000 volts on the anode and a plate current of 250 mA, the power output as measured by a Bird Thru-line wattmeter into a Bird dummy load was 325 watts. This agrees closely with the tube specification sheets.

**A Low-Drive 2-Meter PA**

This amplifier will provide a 200-watt output with as little as 2 watts of drive in linear service. With more drive, more power output can be had (up to 350 watts), but at higher power levels the amplifier components get intolerably warm.

**The Circuit**

A 4CX250 tetrode is used in the grounded-cathode circuit. The 4CX250 is a high-mu tube, so high gain is inherent to the design. The cathode is grounded directly through tabs in the Eimac SK-630 socket, reducing feedback possibilities. The screen is grounded through a low-inductance bypass capacitor built into the tube socket. The socket also has a built-in screen-ring shield. All these measures help eliminate the greatest problem with amplifiers of this type: feedback and subsequent self oscillation.

The grid circuit is a simple tuned line made from no. 14 bus wire. A link couples power to this line. At the high-impedance, tube end of the line, bias voltage is shunt fed to the grid through a 2700-ohm resistor. This resistor also swamps the input heavily, assuring amplifier stability without neutralization.

The plate circuit is series tuned. Series tuning places the tube output capacitance in series with the tuning capacitor, effectively reducing tank circuit capacitance. This allows for a larger tank coil which might otherwise become unworkably small if parallel tuning was used. High voltage is fed to the tube at the low-impedance point of the tank coil through an rf choke. Power output is coupled

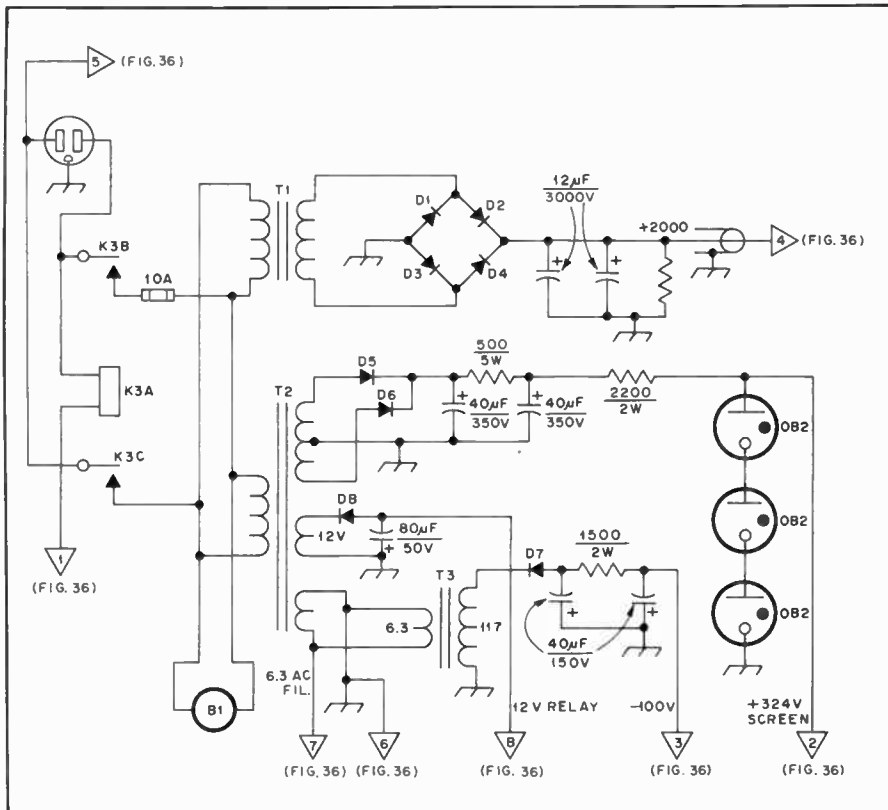


Fig. 40 — Power supply for the amplifier.  
 B1 — Blower motor (see text).  
 D1-D4, incl. — Each leg consists of 2 series silicon diodes (1 A, 1000 PRV).  
 D5, D6, D7 — Silicon diode, 1 A, 1000 PRV.  
 D8 — Silicon diode, 3 A, 100 PRV.  
 K3 — Power relay, dpdt 10 A, contacts 117-V ac

coil.  
 T1 — Power transformer, 1400 V ac, 500 mA.  
 T2 — Power transformer, 500 V at 100 mA sec. 12-V, 1-A sec. and 6.3-V, 3-A sec.  
 T3 — Filament transformer, 6.3 V, 1A.



Fig. 41 — A 500-watt amplifier for the 2-meter band, complete with power supply, is housed in this cabinet. The hole plug covers a former location of a control.



EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu\text{F}$ ); OTHERS ARE IN PICOFARADS ( $\text{pF}$  OR  $\mu\mu\text{F}$ ); RESISTANCES ARE IN OHMS; k = 1000, M = 1000 000.

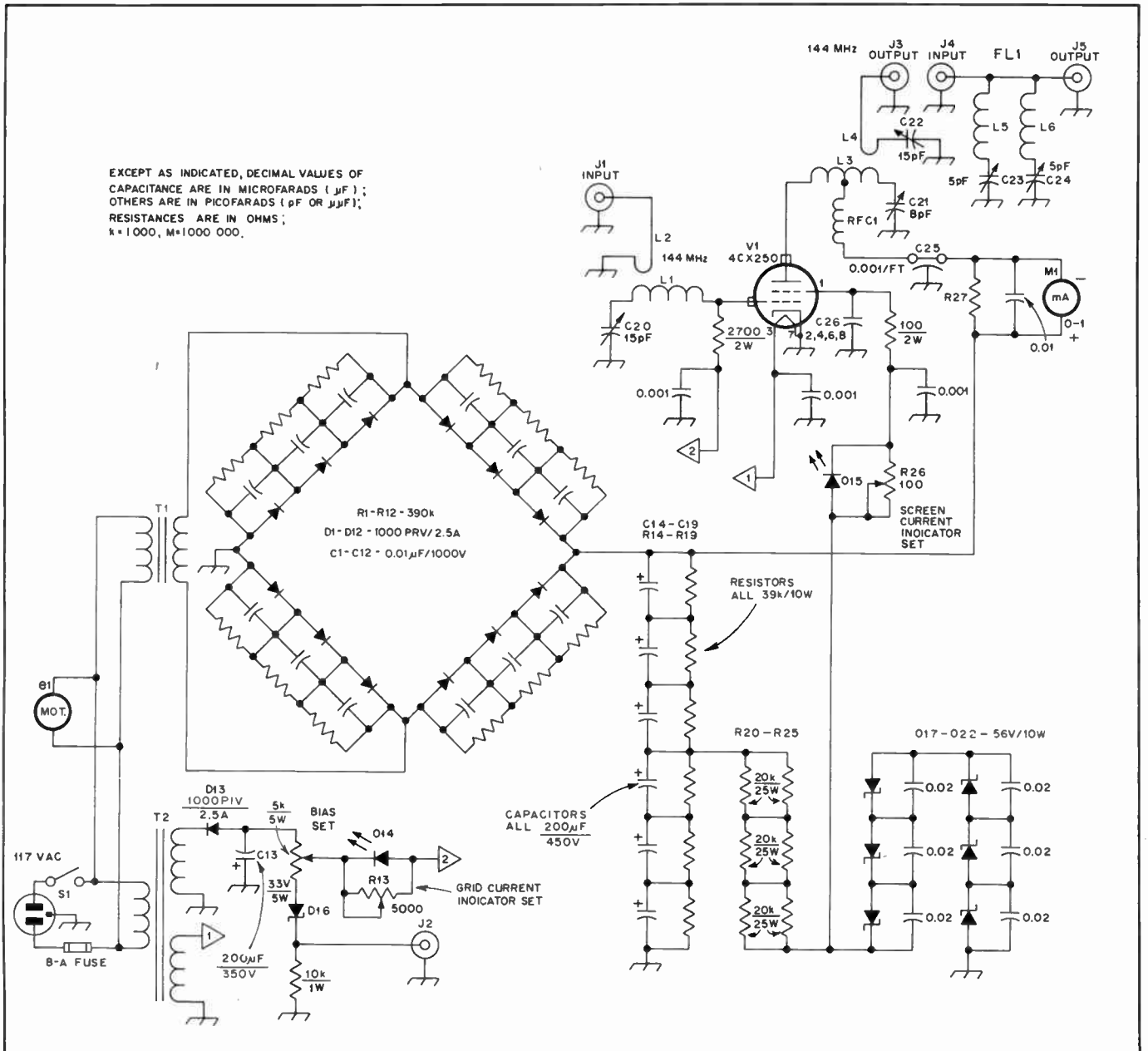


Fig. 42 — Schematic diagram and parts list of the 144-MHz amplifier. Inches  $\times$  25.4 = mm.

- B1 — Blower, 15 ft 3 min or more.
- C1-C12, incl. — 0.01  $\mu\text{F}$  disc ceramic, 1000-Vdc.
- C13 — 100  $\mu\text{F}$ , 350 Vdc.
- C14-C19, incl. — 200  $\mu\text{F}$  electrolytic, 450-Vdc.
- C20, C22 — 15-pF air variable, Hammarlund HF-15-X or equiv.
- C21 — 5-pF air variable, Hammarlund HFA-25-B with 2 middle rotor plates and two end stator plates removed, or equiv.
- C23, C24 — 5-pF air variable, E.F. Johnson 160-0104-001 or equiv.
- C25 — 0.001  $\mu\text{F}$ , 4-kV feedthrough capacitor, Erie 2498 or equiv.
- C26 — screen bypass capacitor built into EIMAC SK-630A tube socket.
- D1-D12, incl. — 1000 PIV, 2.5-A silicon diodes.

- Mallory M2.5A or equiv.
- D14, D15 — Light emitting diode Motorola HEP P2005 or equiv.
- D16 — 33-V, 5-W Zener diode, Motorola HEP Z2531 or equiv.
- D17-D22 — 56-V, 10-W Zener diode, Motorola HEP Z3530 or equiv.
- F1 — 10-A fuse.
- J1, J3, J4, J5 — Type SO-239.
- J2 — Phono jack, panel mount.
- L1, L2 — See text and Fig. 7 - 45.
- L5, L6 — 3 turns no. 18 tinned, 1/4-inch ID, 3/8 inch long.
- L3 — 3-1/2 turns no. 10, 1-1/4 inch ID, 2 inch long.
- L4 — 1 turn no. 14 enameled, 1-inch ID.

- M1 — 0-1 mA meter.
- R1 - R12, incl. — 390k  $\Omega$  1/2-W.
- R13, R26 — 5k  $\Omega$ , 2-W potentiometer.
- R14 - R19, incl. — 39k  $\Omega$ , 10-W.
- R20 - R25, incl. — 20k  $\Omega$ , 25-W.
- R27 — Meter shunt, 0.05555 ohms (3.375 feet (1.03m) no. 22 enam. wire wound on any large-value, 2-watt resistor).
- RFC1 — 20 turns no. 24, enam., wound on 100k, 1-W resistor.
- S1 — spst, 10A.
- T1 — primary 117 V ac, secondary 1250 V ac, 500 mA, Hammond 720 or equiv.
- T2 — primary 117 V ac, secondary 125 V ac, 50 mA; 6.3 V ac, 2.0 A, Stancor PA-8421 or equiv.
- V1 — Eimac 4CX250B.

through a variable link, reducing harmonic content. Series tuned traps at the second and third harmonics ensure clean spectral response, far surpassing FCC requirements.

The power supply uses a full-wave bridge rectifier circuit in the high voltage

circuit. Series-dropping resistors lower the high voltage to the correct value for the tube screen. Screen voltage is regulated by a string of Zener diodes. Series LEDs in the bias and screen-voltage lines provide warning of excess current flow. Bias is switched between cutoff (-120 volts) and

-50 volts regulated during transmit operation.

### Construction

Despite the compact design, few precautions are necessary. Caution with respect to high-voltage leads is mandatory,

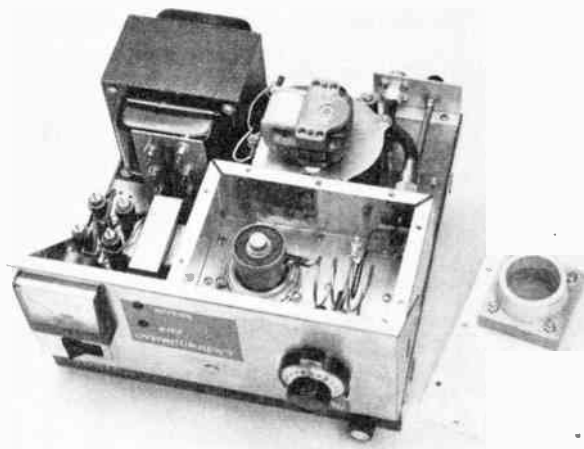


Fig. 43 — Top view of the two-meter amplifier. Voltage-dropping resistors and Zener diodes may be seen on the left-hand side of the chassis. The small transformer next to the plate compartment is T2. Details of the wood spacer may be seen at right.

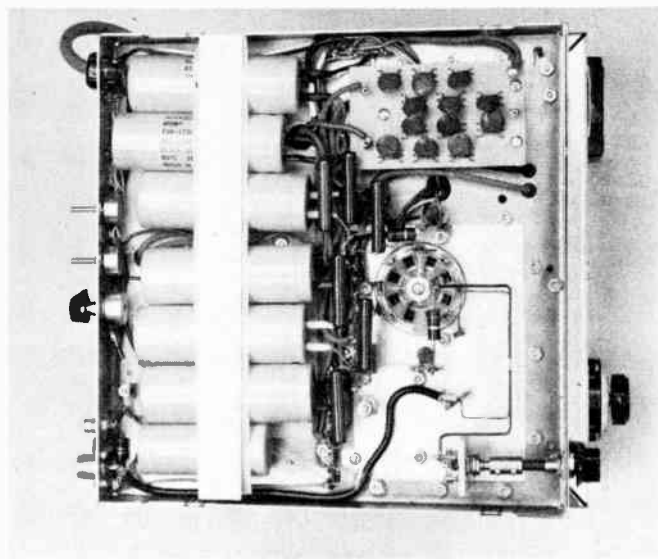


Fig. 45 — Bottom view of the amplifier. A thin sheet of Teflon has been placed between the electrolytic capacitors and their aluminum mounting strap. At upper right is the power supply rectifier board. Details of the grid circuit are also visible.

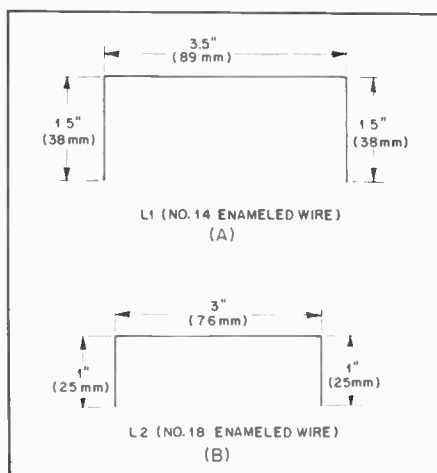


Fig. 44 — Formation details for L1 and L2.

Table 3

Pad Values for Input Attenuator

Attn (dB)	R1	R2	R3 (ohms)
0	none		
6	18	18	68
10	27	27	39
20	43	43	11

of course. The plate circuitry is entirely enclosed by a shielded box, which also prevents air leakage. The grid circuit should be installed so that no other circuit is in close proximity to the tuned line, link or tuning capacitor. Cooling air is blown into the plate compartment through a screened hole. Several screw, nut and flat-washer combinations guarantee good electrical contact to the screen. A standard Eimac ceramic tube chimney is

mounted on a wooden standoff. The chimney fits over the tube anode in an inverted style. The hole in the top cover is screened in the same way as is the fan inlet. Cool air enters through the fan hole and passes through the tube anode cooler. Tube-warmed air exits through the chimney and out the screened hole in the top. A small portion of the cooling air passes through the tube socket, cooling the tube base before flowing through the underside of the chassis.

The output traps are built into a box fabricated from copper-clad circuit board. The easiest approach to mounting it is by means of a double-male UHF-type connector to the jack on the rear of the plate compartment.

An input attenuator may be required to reduce transceiver output power down to the 2-watt level necessary to drive the amplifier. Standard composition resistors can be used in attenuator construction. The attenuator is built in a separate box from the amplifier.

#### Tune-up and Operation

Upon completion, all wiring should be thoroughly checked for mistakes. *The high voltage present can be lethal if not treated carefully.* Be sure no wires are touching anything they shouldn't.

Primary voltage should initially be applied through a variable line transformer. This allows the voltage to be brought up slowly so that if something is awry it can be noticed before any damage can occur. Once the primary has been safely brought up to its normal voltage, voltage checks on the tube should be made. Screen voltage should be about 325 and bias should be about -130 V. AC filament voltage should be about 6.

Shorting J2 places the amplifier in the

transmit mode. With no drive applied, adjust bias for an idling plate current of 50 MA. This establishes a class of operation AB2. Adjustment of the warning-LED potentiometers requires the use of temporary load resistors. Remove power from the amplifier. Temporarily connect a 150-kΩ resistor from the grid terminal to ground. Turn on the power. Do not short J2. Adjust R13 until the grid-sensing LED just comes on. Turn the power off again. Connect a string of 10 1000-ohm, 1-watt resistors from the screen terminal of the tube socket to ground. Turn the power on again. Adjust R26 until the screen sensing LED just comes on. Turn the power off and disconnect the temporary load resistors.

Connect a source of drive to J1 through an SWR indicator. A 50-ohm dummy load should be connected to J3. Applying a small amount of drive, adjust grid capacitor C for a dip in SWR on the indicator. The SWR may not be close to 1:1. If not, readjust the position of L1 with respect to L2. Recheck the SWR. Continue the process until the input SWR is close to 1:1. Since no voltage is applied to the amplifier, adjustment is very simple. In the amplifier shown, the L1 adjustment was optimum when placed approximately 1/8-inch (3-mm) from and parallel to L2.

Reconnect the system so that a power-indicating device is inserted in the line between the dummy load and J3. Apply primary power. Short J2 and apply approximately 2 watts of drive. Adjust the grid capacitor for maximum plate current. Do not key the rig for longer than about 20 seconds at a time. Peak the tuning and the loading controls alternately for maximum output. Since the amplifier is not neutralized, the plate-current dip will not coincide with maximum output.

If a calibrated wattmeter is available, output should be measured at about 200 watts with a plate current of 200 mA. Efficiency is about 58 percent. These are the normal operating parameters. If either of the indicator LEDs turns on, either the amplifier is not tuned properly, there is too much drive, or some equipment failure has taken place.

Adjustment of the traps requires use of a wavemeter or a dip meter in the wavemeter function. Coupling the wavemeter to the dummy load should indicate some harmonic energy at twice the fundamental and three times the fundamental. Adjust one trap capacitor for minimum harmonic energy at the second harmonic and the other for minimum third-harmonic energy.

### An Inexpensive Diode Multiplier for 23 cm

Instead of expensive and hard-to-find varactors this tripler, designed by G8AZM, uses computer switching diodes. It has been described in several RSGB publications.

A schematic diagram of the tripler is shown in Fig. 46. The unit is fabricated from sheet brass or copper. Construction details are shown in Fig. 47A and B. To increase the dissipation ability of the diodes a heat sink is fabricated, allowing up to 6 watts drive at 432 MHz and 2 watts output at 1296 MHz. The five diodes are connected between two 1 × 5/8-inch (25 × 16-mm) plates to form a stack, one side of which is bolted to the chassis. The other side is fastened to L1. Great care must be taken when soldering the diodes. Lead length should be as short as possible. To reduce the risk of damaging the diodes, the leads and the holes in the plates should be pretinned and a hot soldering iron used for the minimum time necessary to make each joint. The top and bottom surfaces of the stack should then be made flat by filing, and then with emery paper. It will be helpful to place the emery paper grit-side up on a hard surface, such as glass, and then draw the plate across its surface. Mating surfaces of the chassis and L1 should also be carefully flattened to ensure good thermal contact. Output loop L5 is made of no. 18 wire, 1/2-inch (13-mm) long, placed as near to L1 as possible.

The output filter, shown in Fig. 47C, is a simple cavity resonator. It may be built

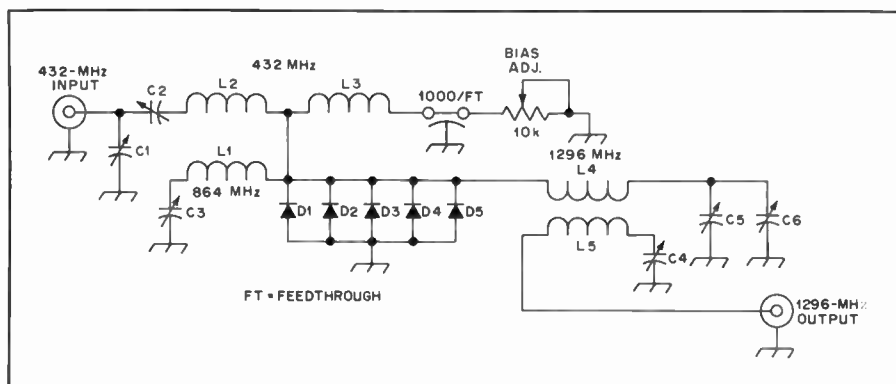


Fig. 46 — Schematic diagram and parts list for the 432-to-1296-MHz tripler.

C1-C3 — Air-variable capacitors, 3-11 pF.

D1-D5 — 1N914 diodes or equiv.

C4-C6 — Piston-trimmer capacitors, 105 pF.

R1 — 10-k $\Omega$  potentiometer, linear taper.

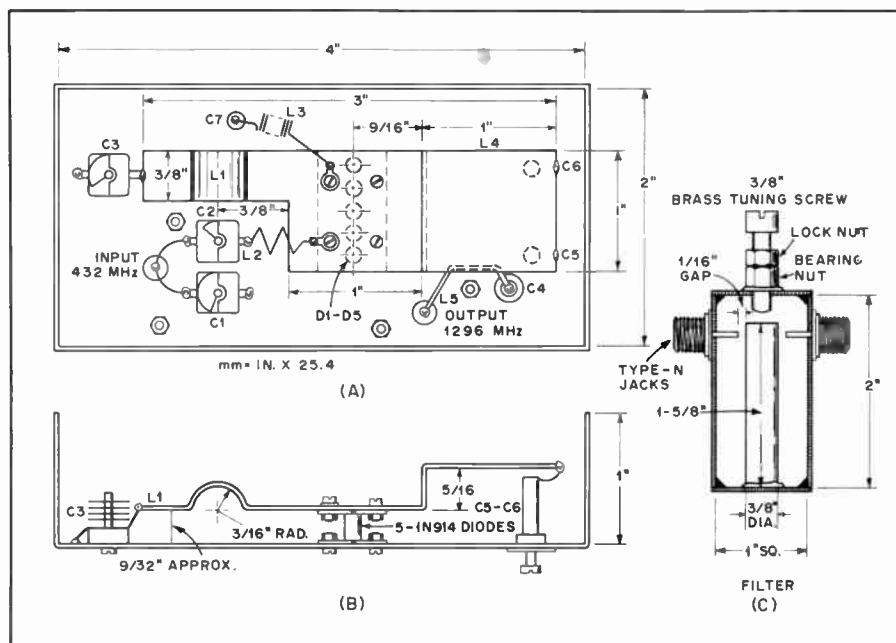


Fig. 47 — Construction information for the tripler and filter. At A, a top view of the tripler, showing the position of the components. At B, a side view of the tripler, showing the installation of D1-D5. At C, a cavity filter designed to remove undesired harmonics generated in the tripler.

from thin brass or copper sheet. Before drive is applied to the tripler, the filter should be aligned. This may be done by connecting it to a receiver and peaking on a weak signal. Insertion loss should be less than 1 dB. The lock nut should be tightened and the filter connected between the tripler and a load.

Adjust R1 to its centerpoint and connect a high-impedance dc voltmeter across it. When 5-watts drive at 432 MHz is applied to the tripler, C1, C2 and C3 should be adjusted for maximum meter deflection (about 20 volts). R1 and all tuning capacitors should then be adjusted for maximum rf output.

# Receiving Systems

How good should receiver performance be? A suitable answer might be, "As good as is possible, consistent with the state of the amateur art and the money available to the purchaser." That opens up a wide area for debate, but the statement is not meant to imply that a receiver has to be costly or complex to provide good performance: Some very basic, inexpensive homemade receivers offer outstanding performance.

For many years the evolution of commercial amateur receivers seemed to stagnate except for the window dressing and frills added to the front panels. Emphasis was placed on "sensitivity" (whatever was *really* meant by that term) in the advertising. Some amateurs concluded, as a result of the strong push for *sensitive* receivers, that the mark of a good unit was seen when atmospheric noise on the hf bands could push the S-meter needle up to an S2 or S3. Very little thought, if any, was given to the important parameters of a receiver — high dynamic range, fine readout resolution and frequency stability. Instead, countless receivers were placed on the market with 5- or 10-kHz dial increments and excessive amounts of front-end gain. The latter caused the mixer (or mixers) to collapse in the presence of moderate and strong signals. Double-conversion superheterodyne receivers were for a long time the choice of manufacturers and amateurs. The second i-f was often 100 or 50 kHz, thereby enabling the designer to get fairly reasonable orders of selectivity by means of high-Q i-f transformers. That concept predated the availability of crystal-lattice and mechanical filters. The low-frequency second i-f dictated the use of a double-conversion circuit in order to minimize image responses.

Single-conversion receivers offer much cleaner performance in terms of spurious responses and dynamic range. They are

being offered by some manufacturers, and although performance is acceptable in many instances, there is considerable room for improvement. At least there is only *one* mixer to cause intermodulation distortion (IMD) and overloading problems in a single-conversion superheterodyne receiver. A strong doubly balanced mixer (DBM) and careful gain distribution in such a receiver can yield superb performance if a proper design effort is put forth. Of course, the local oscillator should be stable and low in noise components to further enhance performance. Thus far, not many commercially built amateur receivers meet the foregoing criteria. In terms of dynamic range, some manufactured receivers exhibit an MDS (minimum discernible signal) of  $-145$  dBm (referenced to the noise floor), blocking of the desired signal does not occur (1 dB of compression) until the adjacent test signal is some 116-dB above the noise floor, and the two-tone IMD is on the order of 85 dB. Greater detail concerning this measurement technique will be given later in the chapter. A receiver with the approximate figures just given is considered to be an acceptable one for use where fairly strong signals prevail. However, it is possible to improve those numbers considerably; it has been done by amateurs who designed and built their own receivers. Examples are W7ZOI's "Competition Grade Receiver" (March and April 1974 *QST*) and the WICER receiver described in June and July 1976 *QST*.

The foregoing suggests strongly that amateurs should consider designing and building their own receivers. Certainly, such an endeavor is within the capability of many experimenters. The satisfaction derived from such an effort can't be measured. The following sections of this chapter are written for those who wish to acquire a better understanding of how a

practical receiver operates. Design data and related philosophy are included for those who are inspired toward developing a homemade receiver.

### Sensitivity

One of the least understood terms among amateurs is *sensitivity*. In a casual definition the word refers to the ability of a receiver to respond to incoming signals. It is proper to conclude from this that the better the sensitivity, the more responsive the receiver will be to weak signals. The popular misconception is that the greater the receiver front-end gain, the higher the sensitivity. An amateur who subscribes to this concept can ruin the performance of a good receiver by installing a high-gain preamplifier ahead of it. Although this will cause the S meter to read much higher on all signals, it can actually *degrade* the receiver sensitivity if the preamplifier is of inferior design (noisy).

A true measure of receiver sensitivity is obtained when the input signal is referenced to the noise generated within the receiver. Since the significant noise generated inside a receiver of good design originates in the rf and mixer stages (sometimes in the post-mixer amplifier), a low-noise front end is vital to high sensitivity. The necessary receiver gain can be developed after the mixer — usually in the i-f amplifier section. The internal noise is generated by the thermal agitation of electrons inside the tubes, transistors or ICs. It is evident from the foregoing discussion that a receiver of high sensitivity could be one with relatively low front-end gain. This thought should be kept in mind as we enter the discussion of dynamic range and noise figure.

### Noise Figure

The lower the receiver *noise figure* (NF), the more sensitive it is. Receiver noise figures are established primarily in



the rf amplifier and/or mixer stages. Low-noise active devices (tubes or transistors) should be used in the receiver front end to help obtain a low noise figure or signal-to-noise ratio (SNR). The unwanted noise, in effect, masks the weaker signals and makes them difficult to copy. Noise generated in the receiver front end is amplified in the succeeding stages along with the signal energy. Therefore, it is in the interest of sensitivity that internal noise should be kept as low as possible.

Some amateurs confuse external noise (man-made and atmospheric, which comes in on the antenna) with receiver noise during discussions of noise figure. Although the ratio of the external noise to the incoming signal level has a lot to do with reception, external noise does not relate to this general discussion. It is because external noise levels are quite high on 160, 80, 40 and 20 meters that emphasis is seldom placed on a low receiver noise figure for those bands. However, as the operating frequency is increased from 15 meters up through the microwave spectrum, the matter of receiver noise becomes a primary consideration. At these higher frequencies the receiver noise almost always exceeds that from external sources, especially at 2 meters and above.

### Noise-Figure Measurements

Amateurs can use a thermal noise source for determining receiver noise figure. The resistance of the noise-generator output must match that of the receiver input, 50 ohms to 50 ohms, for example. Fig. 1 shows a setup for making these measurements. The first reading is taken with the noise generator turned off. The receiver audio gain is adjusted for a convenient noise reading in dB, as observed on the audio power meter. The noise generator is turned on next, and its output is increased until a convenient power ratio, expressed by  $N_2/N_1$ , is observed. From these numbers the noise figure can be calculated by

$$NF = (\text{excess})_{dB} - 10 \log [(N_2/N_1) - 1]$$

where  $(\text{excess})_{dB}$  = the difference in noise power between the receiver noise and that from the noise generator.

If a thermal diode such as a 5722 tube is used as the noise source, and if the circuit is operated in the "temperature-limited mode" (portion of the tube curve where saturation occurs, dependent upon cathode temperature and plate voltage), the  $(\text{excess})_{dB}$  can be calculated by

$$(\text{excess})_{dB} = 10 \log (20R_d I_d)$$

where  $R_d$  = the noise source output resistance

$I_d$  = the diode current in amperes

Most manufacturers of amateur communications receivers rate the noise characteristics with respect to signal input. The common expression is S+ Noise

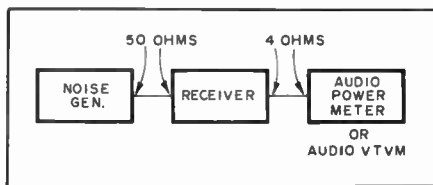


Fig. 1 — Block diagram of a noise measurement setup.

/Noise, or the signal-to-noise ratio, which is usually given in dB. Typically, this runs about 5 to 10 dB for a good receiver below 30 MHz. Lower noise figures can be obtained, but they are of no real value because of the external noise arriving from the antenna. It is important to remember also that optimum noise figure in an rf amplifier does not always coincide with maximum stage gain, especially at vhf and higher. It is for this reason that actual noise measurements are important to peak performance.

### Selectivity

Many amateurs regard the expression "selectivity" as equating to the ability of a receiver to separate signals. This is a fundamental truth, particularly with respect to i-f selectivity which has been established by means of high-Q filters (LC, crystal, monolithic or mechanical). But in a broader sense, *selectivity* can be employed to reject unwanted signal energy in any part of a receiver — the front end, i-f section, audio circuit or local-oscillator chain. Selectivity is a relative term, since the degree of bandwidth can vary from a few hertz to more than a megahertz, depending on the design objectives. Therefore, it is not uncommon to hear terms like "broadband filter" or "narrow-band filter."

The degree of selectivity is determined by the *bandwidth* of a filter network. The bandwidth is normally specified for the minus 3-dB points on the filter response curve; the frequencies where the filter output power is half the peak output power elsewhere in the passband. The difference in frequency between a minus 3-dB point and the filter center frequency is known as  $\Delta f$ . The bandwidth of the filter then becomes  $2 \Delta f$ . Fig. 2 illustrates this principle and shows how the unloaded Q of a tuned circuit or resonator relates to the bandwidth characteristic.

If a tuned circuit is used as a filter, the higher its loaded Q, the greater the selectivity. To make the skirts of the response curve steeper, several high-Q resonators can be used in cascade. This aids the selectivity by providing greater rejection of signals close in frequency to the desired one. The desirable effect of cascaded filter sections can be seen in Fig. 3. The circuit is that of a tunable Cohn type of three-pole filter for use in the front end of a 160-meter receiver. The response

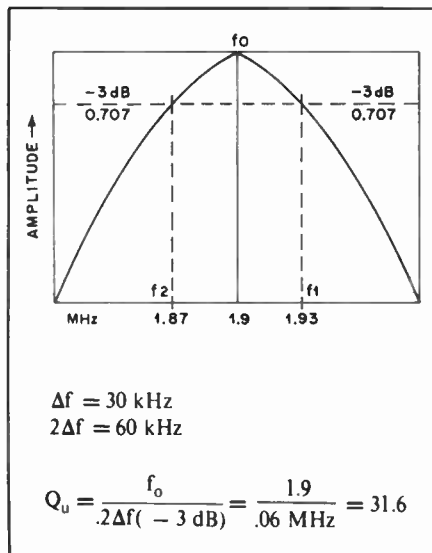


Fig. 2 — A curve and equation for determining the unloaded Q of a tuned circuit.

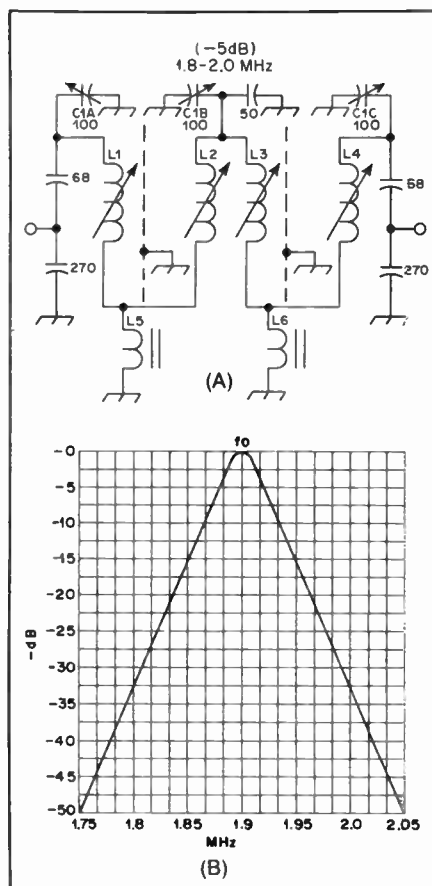


Fig. 3 — A tunable Cohn type of filter is shown at A. L5 and L6 are the bottom-coupling inductors (1.45  $\mu$ H). L1 and L4 are 70  $\mu$ H and L2, L3 are 140  $\mu$ H. A response curve for the tunable filter is given at B.

curve is included to illustrate the selectivity obtained.

An ideal receiver with selectivity applied to various significant parts of the

circuit might be structured something like this:

a) Selective front end for rejecting out-of-band signals to prevent overloading and spurious responses.

b) Selective i-f circuit (two i-f filters: one for 2.4-kHz ssb bandwidth and one for 400-Hz cw bandwidth).

c) RC active or passive audio filter for audio selectivity to reduce wideband noise and provide audio selectivity in the range from 400 to 2500 Hz (ssb), or a very narrow bandwidth, such as 650 to 750 Hz, for cw.

d) Selective circuits or filters in the local oscillator chain to reject all mixer injection energy other than the desired frequency.

This illustrates clearly that selectivity does not simply mean the ability of a receiver to separate one amateur signal from another that is nearby in frequency, or to "separate the stations." More specifically, it means that selectivity can be used to select one frequency or band of frequencies while rejecting others. Practical applications of selective circuit elements will be found later in the chapter.

### Dynamic Range

Here is another term which seems to confuse some amateurs and even some receiver manufacturers. The confusion concerns true dynamic range (as treated briefly at the start of this chapter) and the agc control range in a receiver. That is, if a receiver agc circuit has the capability of controlling the overall receiver gain by some 100 dB from a no-signal to a large-signal condition, a misinformed individual might claim that the dynamic range of the receiver is 100 dB. A receiver with a true dynamic range of 100 dB would be a very fine piece of equipment, indeed!

*Dynamic range* relates specifically to the amplitude levels of multiple signals that can be accommodated during reception.<sup>1</sup> This is expressed as a numeric ratio, generally in decibels. The present state of the receiver art provides *optimum dynamic ranges* of up to 100 dB. This is the maximum dynamic range attainable when the distortion products are at the sensitivity limit of the receiver. Simply stated, dynamic range is the dB difference (or ratio) between the largest tolerable receiver input signal (without causing audible distortion products) and the minimum discernible signal (sensitivity).

Poor dynamic range can cause a host of receiving problems when strong signals appear within the front-end passband. Notable among the maladies is cross modulation of the desired signal. Another effect is desensitization of the receiver from a strong unwanted signal. Spurious signals may appear in the receiver tuning range when a strong signal is

<sup>1</sup>Hayward, "Defining and Measuring Receiver Dynamic Range," *QST*, July, 1975.

elsewhere in the band. This is caused by IMD products from the mixer. Clearly, strong signals cause undesired interference and distortion of the desired signal when a receiver's dynamic range is poor. Design features of importance to high dynamic range receivers will be appearing in the theory sections of this chapter. The four terms which have been defined in this section were thus treated to enable the reader to better understand the material that follows.

### Detection and Detectors

Detection (demodulation) is the process of extracting the signal information from a modulated carrier wave. When dealing with an a-m signal, detection involves only the rectification of the rf signal. During fm reception, the incoming signal must be converted to an a-m signal for detection.

Detector sensitivity is the ratio of desired detector output to the input. Detector linearity is a measure of the ability of the detector to reproduce the exact form of the modulation on the incoming signal. The resistance or impedance of the detector is the resistance or impedance it presents to the circuits it is connected to. The input resistance is important in receiver design, since if it is relatively low it means that the detector will consume power, and this power must be furnished by the preceding stage. The signal-handling capability means the ability to accept signals of a specified amplitude without overloading or distortion.

### Diode Detectors

The simplest detector for a-m is the diode. A germanium or silicon crystal is an imperfect form of diode (a small current can usually pass in the reverse direction), but the principle of detection in a semiconductor diode is similar to that in a vacuum-tube diode.

Circuits for both half-wave and full-wave diodes are given in Fig. 4. The simplified half-wave circuit at Fig. 4A includes the rf tuned circuit, L2C1, a coupling coil, L1, from which the rf energy is fed to L2C1, and the diode, D1, with its load resistance, R1, and bypass capacitor, C2.

The progress of the signal through the detector or rectifier is shown in Fig. 5. A typical modulated signal as it exists in the tuned circuit is shown at A. When this signal is applied to the rectifier, current will flow only during the part of the rf cycle when the anode is positive with respect to cathode, so that the output of the rectifier consists of half-cycles of rf. These current pulses flow in the load circuit comprised of R1 and C2, the resistance of R1 and the capacitance of C2 being so proportioned that C2 charges to the peak value of the rectified voltage on each pulse and retains enough charge between pulses so that the voltage across

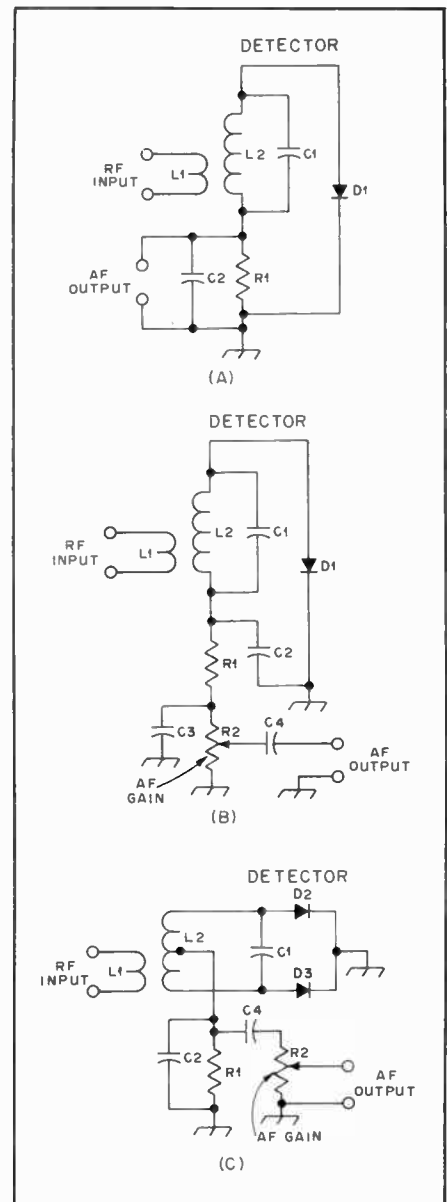


Fig. 4 — Simplified and practical diode detector circuits. A, the elementary half-wave diode detector; B, a practical circuit, with rf filtering and audio output coupling; C, full-wave diode detector, with output coupling indicated. The circuit, L2C1, is tuned to the signal frequency; typical values for C2 and R1 in A and C are 250 pF and 250 k $\Omega$ , respectively; in B, C2 and C3 are 100 pF each; R1, 50k $\Omega$ ; and R2, 250 k $\Omega$ . C4 is 0.1  $\mu$ F and R3 may be 0.5 to 1 megohm.

R1 is smoothed out, as shown in C. C2 thus acts as a filter for the radio-frequency component of the output of the rectifier, leaving a dc component that varies in the same way as the modulation on the original signal. When this varying dc voltage is applied to a following amplifier through a coupling capacitor (C4 in Fig. 4), only the *variations* in voltage are transferred, so that the final output signal is ac, as shown in D.

In the circuit at 4B, R1 and C2 have been divided for the purpose of providing a more effective filter for rf. It is important to prevent the appearance of

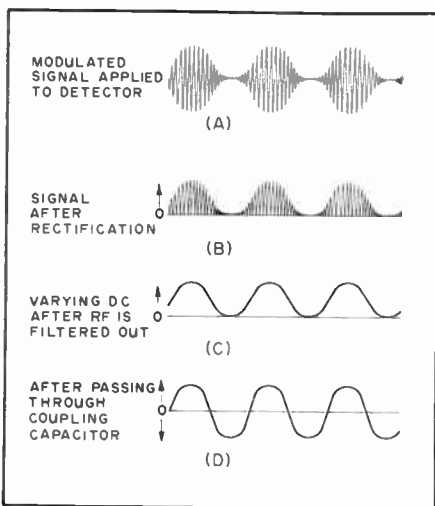


Fig. 5 — Illustrations of the detection process.

any rf voltage in the output of the detector, because it may cause overloading of a succeeding amplifier stage. The audio-frequency variations can be transferred to another circuit through a coupling capacitor, C4. R2 is usually a "potentiometer" so that the audio volume can be adjusted to a desired level.

Coupling from the potentiometer (volume control) through a capacitor also avoids any flow of dc through the moving contact of control. The flow of dc through a high-resistance volume control often tends to make the control noisy (scratchy) after a short while.

The full-wave diode circuit at Fig. 4C differs in operation from the half-wave circuit only in that both halves of the rf cycle are utilized. The full-wave circuit has the advantage that rf filtering is easier than in the half-wave circuit. As a result, less attenuation of the higher audio frequencies will be obtained for any given degree of rf filtering.

The reactance of C2 must be small compared to the resistance of R1 at the radio frequency being rectified, but at audio frequencies must be relatively large compared to R1. If the capacitance of C2 is too large, response at the higher audio frequencies will be lowered.

Compared with most other detectors, the gain of the diode is low, normally running around 0.8 in audio work. Since the diode consumes power, the Q of the tuned circuit is reduced, bringing about a reduction in selectivity. The loading effect of the diode is close to one half the load resistance. The detector linearity is good, and the signal-handling capability is high.

### Plate Detectors

The plate detector is arranged so that rectification of the rf signal takes place in the plate circuit of the tube or the collector of an FET. Sufficient negative bias is applied to the grid to bring the plate current nearly to the cutoff point, so that application of a signal to the grid

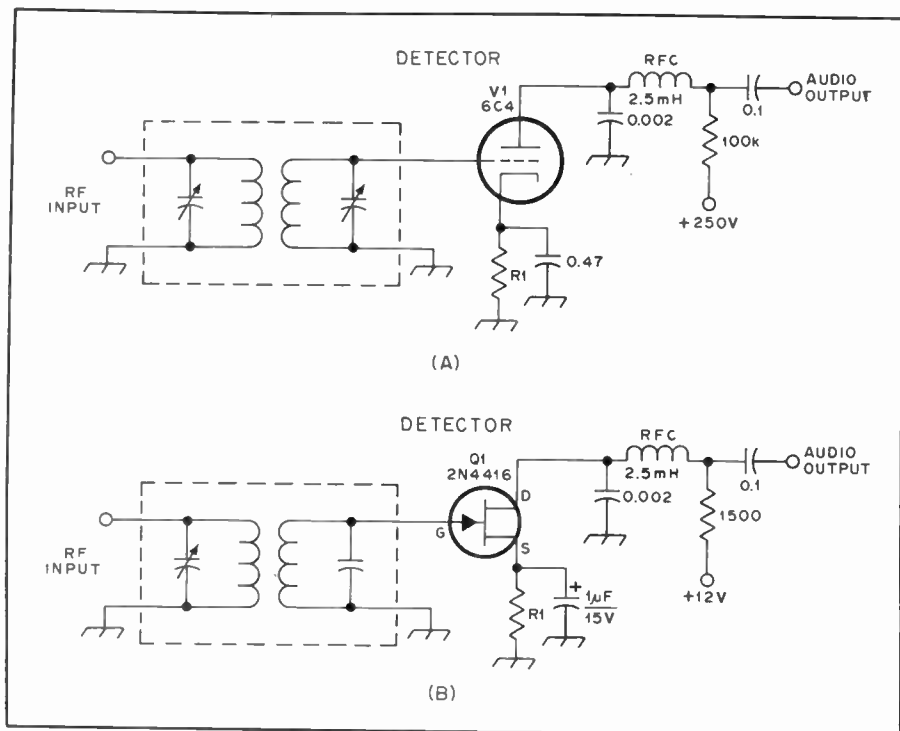


Fig. 6 — Plate-detection circuits. In each example the input circuit is tuned to the signal frequency. Typical R1 values for the tube circuit at A are 1000 to 5600 ohms. For the FET circuit at B, R1 is on the order of 100 to 3900 ohms.

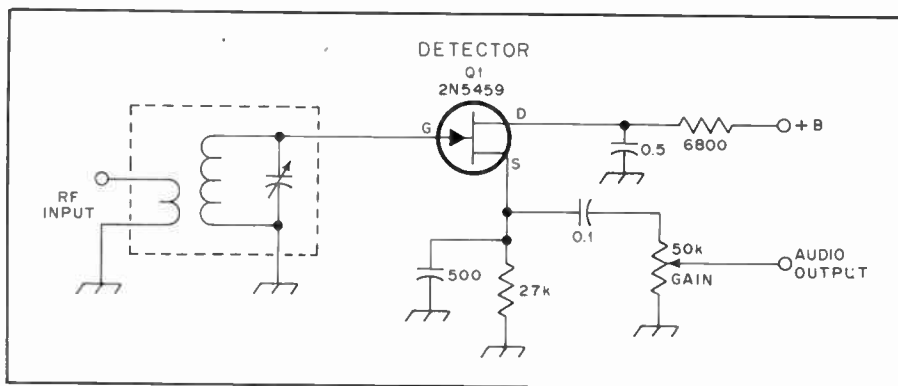


Fig. 7 — An infinite-impedance detector.

circuit causes an increase in average plate current. The average plate current follows the changes in the signal in a fashion similar to the rectified current in a diode detector.

In general, transformer coupling from the plate circuit of a plate detector is not satisfactory, because the plate impedance of any tube is very high when the bias is near the plate-current cutoff point. The same is true of a JFET or MOSFET. Impedance coupling may be used in place of the resistance coupling shown in Fig. 6. Usually 100 henrys or more of inductance is required.

The plate detector is more sensitive than the diode because there is some amplifying action in the tube or transistor. It will handle large signals, but is not so tolerant in this respect as the diode. Linearity, with the self-biased circuits

shown, is good. Up to the overload point the detector takes no power from the tuned circuit, and so does not affect its Q and selectivity.

### Infinite-Impedance Detector

The circuit of Fig. 7 combines the high signal-handling capabilities of the diode detector with the low distortion and, like the plate detector, does not load the tuned circuit it connects to. The circuit resembles that of the plate detector, except that the load resistance, 27-k $\Omega$ , is connected between source and ground and thus is common on both gate and drain circuits, giving negative feedback for the audio frequencies. The source resistor is bypassed for rf but not for audio, while the drain circuit is bypassed to ground for both audio and radio frequencies. An rf filter can be connected between the



cathode and the output coupling capacitor to eliminate any rf that might otherwise appear in the output.

The drain current is very low at no signal, increasing with signal as in the case of the plate detector. The voltage drop across the source resistor consequently increases with signal. Because of this and the large initial drop across this resistor, the gate usually cannot be driven positive by the signal.

### Product Detectors

A *product detector* is similar in function to a balanced or *product modulator*. It is also similar to a mixer. In fact, the latter is sometimes called a "first detector" in a receiver circuit. Product detectors are used principally for ssb and cw signal detection. Essentially, it is a detector whose output is approximately equal to the product of the beat-frequency oscillator (BFO) and the rf signals applied to it. Output from the product detector is at audio frequency. Some rf filtering is necessary at the detector output to prevent unwanted i-f or BFO voltage from reaching the audio amplifier which follows the detector. LC or RC rf decoupling networks are satisfactory, and they need not be elaborate. Fig. 9 illustrates this type of filtering.

### Diode Product Detectors

The product detectors shown in Fig. 8 are called "passive." The term means that the devices used do not require an operating voltage. Active devices (transistors, ICs and tubes) do require an operating voltage. Passive mixers and detectors exhibit a *conversion loss*, whereas active detectors provide a *conversion gain*. Passive detectors usually require a substantially greater level of BFO injection voltage than is the case with active detectors. Therefore, the primary drawbacks to the use of diodes in these circuits are the loss in gain and the high injection level required. A typical conversion loss for a two-diode detector (Fig. 8A) is 5 dB. The four-diode detectors have a loss of approximately 8 dB. The BFO injection level for each of the diode detectors shown in Fig. 8 is +13 dBm, or 20 mW. Since the terminal impedance of the detector is roughly 50 ohms, an rms BFO voltage of 1, or a pk-pk voltage of 2.8 is required.

The advantages to the use of diodes in a product detector are circuit simplicity, low cost, broadband characteristics, low noise figure and good port-to-port signal isolation. This type of detector is excellent at the input of a direct-conversion receiver (to be treated later in the chapter).

The transformers shown in the circuits of Fig. 8 are broadband, toroidal-wound types. The black dots near the windings of T1 and T2 indicate the phasing required. The core material is ferrite and the windings are trifilar. Core permeability can be 950 for most applications, al-

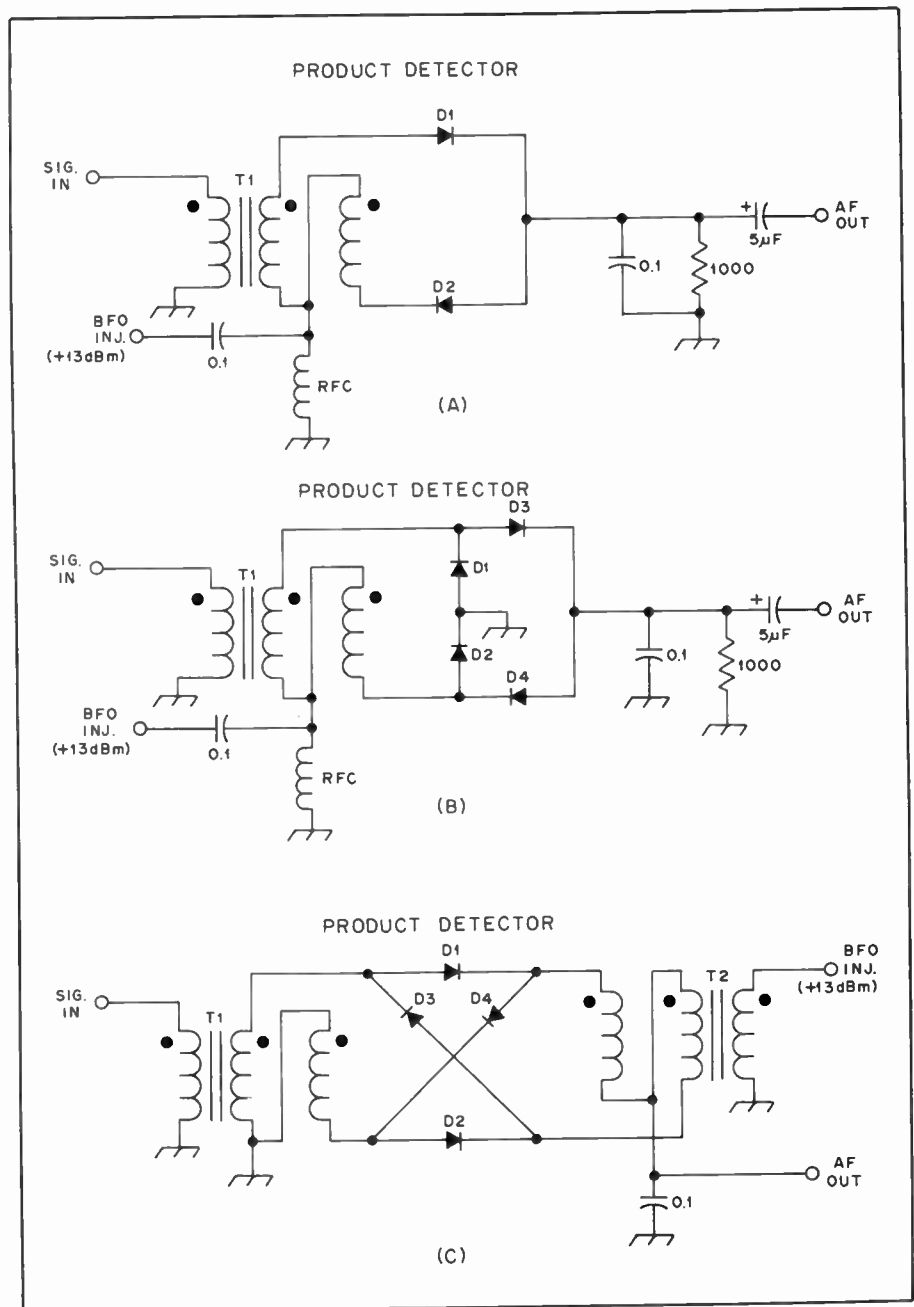


Fig. 8 — Examples of diode product detectors. Singly balanced types are shown at A and B. A doubly balanced version is illustrated at C.

though some designers use cores with less initial permeability. An Amidon FT-50-43 is entirely suitable as a transformer core for the circuits shown. Fifteen trifilar turns are ample for each transformer.

High-speed silicon switching diodes are satisfactory for use in the circuits of Fig. 8. They should be as closely matched as possible for forward and back resistance. Closely matched diodes can be had by using a diode-array IC, such as the RCA CA3019 or 3039. Hot-carrier diodes are excellent for the circuits shown. Matched 1N914s are the choice of many amateur designers.

A singly balanced detector is seen at A in Fig. 8. An improved singly balanced detector is shown at B. Two diodes have

been added to improve the circuit balance while presenting a more symmetrical load to the BFO. The result is better isolation between the BFO and i-f input ports.

Two broadband transformers are used to provide the doubly balanced detector of Fig. 8C. The advantage with this configuration is that all three ports are isolated from one another effectively.

### Simple Active Product Detectors

Fig. 9 contains two examples of single-ended active detectors which employ FETs. They are quite acceptable for use in simple receivers which do not require high performance characteristics. The circuit at A uses a JFET which has BFO injection voltage supplied across the



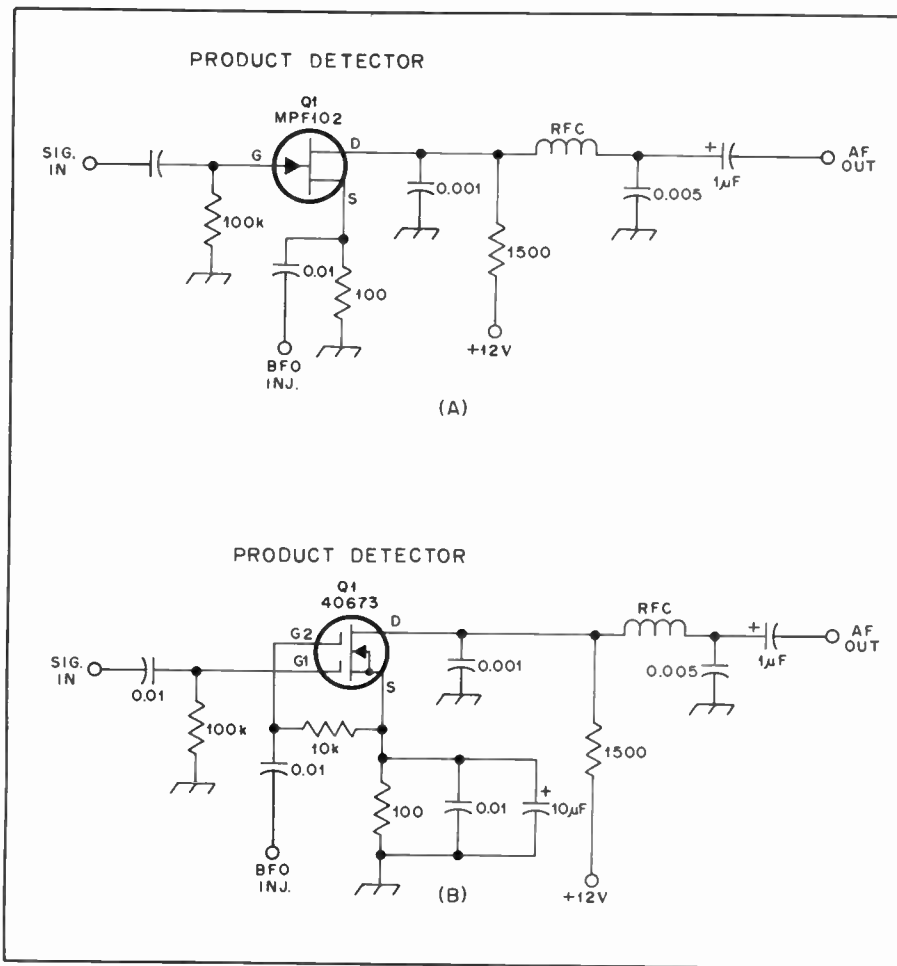


Fig. 9 — Active product detectors. A JFET example is provided at A and a dual-gate MOSFET type is at B.

source resistor. Because the source is not bypassed, instability can occur if the circuit is used as a mixer which has an i-f that is close to the signal frequency. This problem is not apt to become manifest when the output is at audio frequency. Slightly more injection power is needed for circuit A than is necessary for the detector at B. An rms voltage of roughly 0.8 is typical (6.5 mW).

The detector of Fig. 9B operates in a similar fashion to that of A, but the BFO is injected on control gate no. 2. Approximately 1 volt rms is needed (0.1 mW). FETs with proper injection levels and moderate signal-input amounts have excellent IMD characteristics. Generally, they are preferred to single-ended, bipolar-transistor detectors. The circuits at A and B contain rf chokes and bypass capacitors in the drain leads to minimize the transfer of BFO energy to the succeeding audio stage. The bypass capacitors are useful also for rolling off the unwanted high-frequency audio components.

#### Active Balanced Product Detectors

Examples of active IC product detectors are given in Fig. 10. A singly balanced version is shown at A. It uses an RCA differential-pair IC. Except for the

conversion gain it provides, it performs similarly to the singly balanced diode detector of Fig. 8B. Doubly balanced active detectors are seen at B and C of Fig. 10. These ICs contain two sets of differential amplifiers each. The "diff amps" are cross-connected in the examples shown to obtain doubly balanced circuits. The virtues of these detectors are similar to the equivalent four-diode types, but they exhibit several dB of conversion gain. The MC1496G is made by Motorola and the CA3102E is an RCA device.

#### FM Detectors

The first type of fm detector to gain popularity was the frequency discriminator. The characteristic of such a detector is shown in Fig. 11. When the fm signal has no modulation, and the carrier is at point zero, the detector has no output. When audio input to the fm transmitter swings the signal higher in frequency, the rectified output increases in the negative direction. Over a range where the discrimination is linear (shown as the straight portion of the line), the conversion of fm to a-m which is taking place will be linear.

A practical discriminator circuit is shown in Fig. 12A. The fm signal is

converted to a-m by means of transformer T1. The voltage induced in the T1 secondary is 90 degrees out of phase with the current in the primary. The primary signal is introduced through a center tap on the secondary, coupled through a capacitor. The secondary voltages combine on each side of the center tap so that the voltage on one side leads the primary signal while the other side lags by the same amount. When rectified, these two voltages are equal and of opposite polarity, resulting in zero-voltage output. A shift in input frequency causes a shift in the phase of the voltage components that result in an increase of output amplitude on one side of the secondary, and a corresponding decrease on the other side. The differences in the two changing voltages, after rectification, constitute the audio output.

RCA developed a circuit that has now become standard in entertainment radios and which eliminated the need for a preceding limiter stage. Known as the *ratio detector*, this circuit is based on the idea of dividing a dc voltage into a ratio which is equal to the ratio of the amplitudes from either side of a discriminator transformer secondary. With a detector that responds only to ratios, the input signal may vary in strength over a wide range without causing a change in the level of output voltage — fm can be detected, but no a-m. In an actual ratio detector, Fig. 12B, the dc voltage required is developed across two load resistors, shunted by an electrolytic capacitor. Other differences include the two diodes, which are wired in series-aiding rather than series-opposing, as in the standard discriminator circuit. The recovered audio is taken from a tertiary winding which is tightly coupled to the primary of the transformer. Diode-load resistor values are selected to be lower (5000 ohms or less) than for the discriminator.

The sensitivity of the ratio detector is one half that of the discriminator. In general, however, the transformer design values for Q, primary-secondary coupling, and load will vary greatly, so the actual performance differences between these two types of fm detectors are usually not significant. Either circuit can provide excellent results.

A crystal discriminator is shown in Fig. 12C. This provides an adjustment-free discriminator by virtue of the quartz resonator. The components without assigned values are selected to give the desired bandwidth. A unit of this type is sold by Spectrum International Co.

#### TRF Receivers

Tuned-radio-frequency receivers have little value in Amateur Radio today, but in the early days they were suitable for the reception of spark and a-m signals. They consisted mainly of a couple of stages of selective rf amplification, an a-m type of

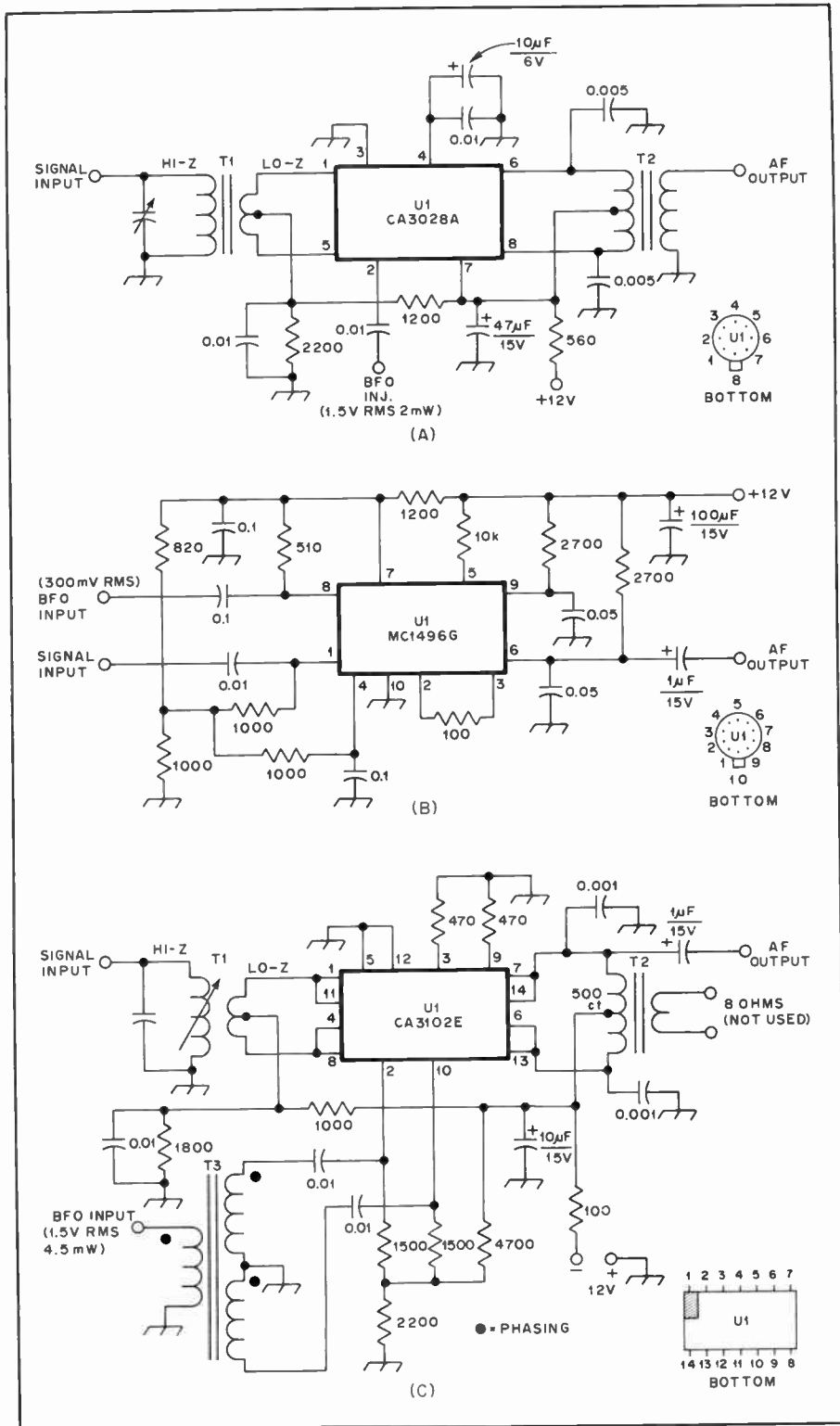


Fig. 10 — Examples of IC product detectors. At A is a singly balanced version, while those at B and C are doubly balanced.

detector and an audio amplifier. Variations were developed as *regenerative* and *superregenerative* receivers. The straight regenerative detector was simply a self-oscillating detector which provided increased sensitivity (similar in function to a product detector) and a beat note for cw reception. Amplitude-modulated signals

could be copied, if they were loud, when the regeneration control was set for a non-oscillating condition. For weak-signal a-m reception the regeneration control was advanced to increase the detector sensitivity and the signal was tuned in at zero beat, thereby eliminating the heterodyne from the carrier. Present-day

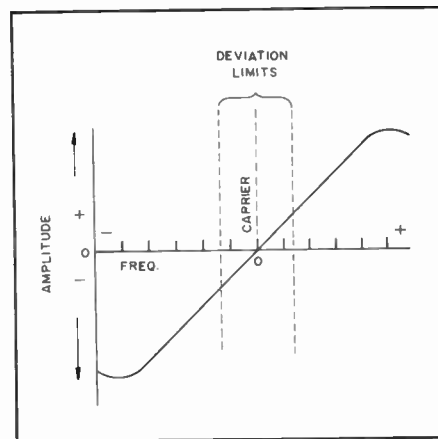


Fig. 11 — Characteristic of an fm discriminator.

uses for the TRF receiver are restricted mainly to reception of a-m broadcast signals, for hi-fi reception and for field-strength indicators of cw or a-m signals.

Superregenerative receivers were quite popular among vhf and uhf amateurs in the '30s, '40s and early '50s. The principle of operation was an oscillating detector which had its oscillation interrupted (quenched) by a low-frequency voltage slightly above the audible range (20 to 50 kHz being typical). Some superregenerative detectors employed a so-called self-quenching trait, brought about by means of an RC network of the appropriate time constant. The more esoteric "supergenny" or "rushbox" detectors used an onboard quench oscillator. This type of circuit was more sensitive than the straight regenerative detector, but was best suited for reception of a-m and wide-band fm signals. Because of the quenching action and frequency, the detector response was extremely broad, making it unsuitable for narrow-band signals versus audio recovery. High-Q input tuned circuits helped make them more selective, but a typical superregenerative receiver which used a tuned cavity at the detector input could accommodate only 10 1000-V, 30-percent modulated a-m signals in a range from 144 to 148 MHz without signal overlap. These tests were performed in the ARRL laboratory with the 10 signals separated from one another by equal amounts.

A major problem associated with the use of regenerative and superregenerative receivers was oscillator (detector) re-radiation. The isolation between the detector and the antenna was extremely poor, even when an rf amplifier was employed ahead of the detector. In many instances the radiated energy could be heard for several miles, causing intense interference to other amateurs in the community.

### Direct-Conversion Receivers

A more satisfactory type of simple receiver is called the *direct-conversion* or

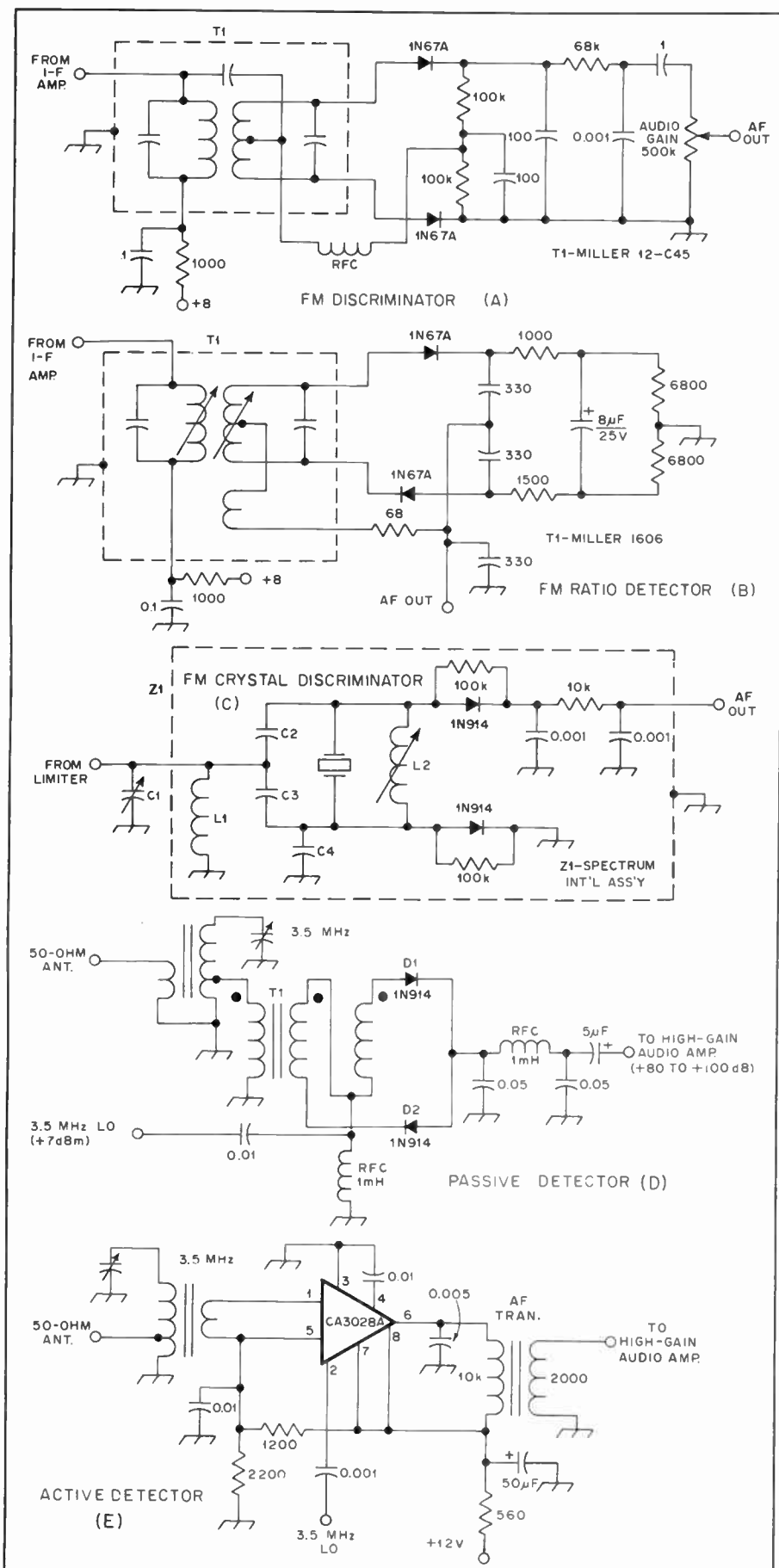


Fig. 12 — Popular types of fm detector (A, B and C) and typical detectors which can be used in the front ends of direct-conversion receivers (D and E). A passive detector is seen at D. The version at E provides considerable conversion gain.

*synchrodyne* type. Although there is a distinct possibility of signal radiation, it is considerably lower in level than with regenerative receivers. This results from better isolation between the detector and the source of the oscillation. A modern direct-conversion receiver uses a separate oscillator and a balanced or doubly balanced detector. Both features help to reduce unwanted radiation.

The detection stage of this receiver is actually a product detector that operates at the desired signal frequency. The product-detector circuits described earlier in the chapter are suitable in this kind of receiver. A tuned rf amplifier is useful ahead of the detector at 14 MHz and higher, but it is seldom necessary from 160 through 40 meters. This is because the atmospheric and man-made noise from the resonant antenna usually exceeds that of the detector below 14 MHz. When no rf stage is used, it is desirable to include a tuned network ahead of the detector.

Fig. 12 shows typical front ends for direct-conversion receivers. One circuit (D) employs a passive detector. The other (E) contains an active detector. The latter is desirable in the interest of increased gain.

The circuit of Fig. 12A shows a singly balanced passive detector. Front-end selectivity is provided by a tuned circuit. T1 is a broadband, trifilar-wound toroid transformer. It is tapped on the input tuned circuit at the approximate 50-ohm point. An rf filter is used after D1 and D2 to prevent LO energy from being passed on to the audio amplifier.

Fig. 12B illustrates an active singly balanced IC detector. The input impedance across pins 1 and 5 is roughly 1000 ohms. However, the secondary winding of the input tuned circuit can be made lower than 1000 ohms to reduce the signal amount to the detector. This will ensure improved dynamic range through a deliberate mismatch. Such a practice is useful when an rf amplifier precedes the detector. For maximum sensitivity when no rf amplifier is included, it is more practical to use a 1000-ohm transformation from the 50-ohm antenna (larger link at the detector input). An audio transformer is used at the detector output. The primary winding should have low dc resistance to provide dc balance between the collectors of the differential-amplifier pair in the IC. Alternatively, a center-tapped primary can be used. If this is done, pin 8 should be connected to one end of the winding and the B+ fed to the center tap. The impedance between pins 6 and 8 is approximately 8000 ohms.

In order to obtain ample headphone volume during reception of weak signals it is necessary to use an audio amplifier which has between 80 and 100 dB of gain. The first af amplifier should be a low-noise type, such as a JFET. The audio-gain control should follow the first

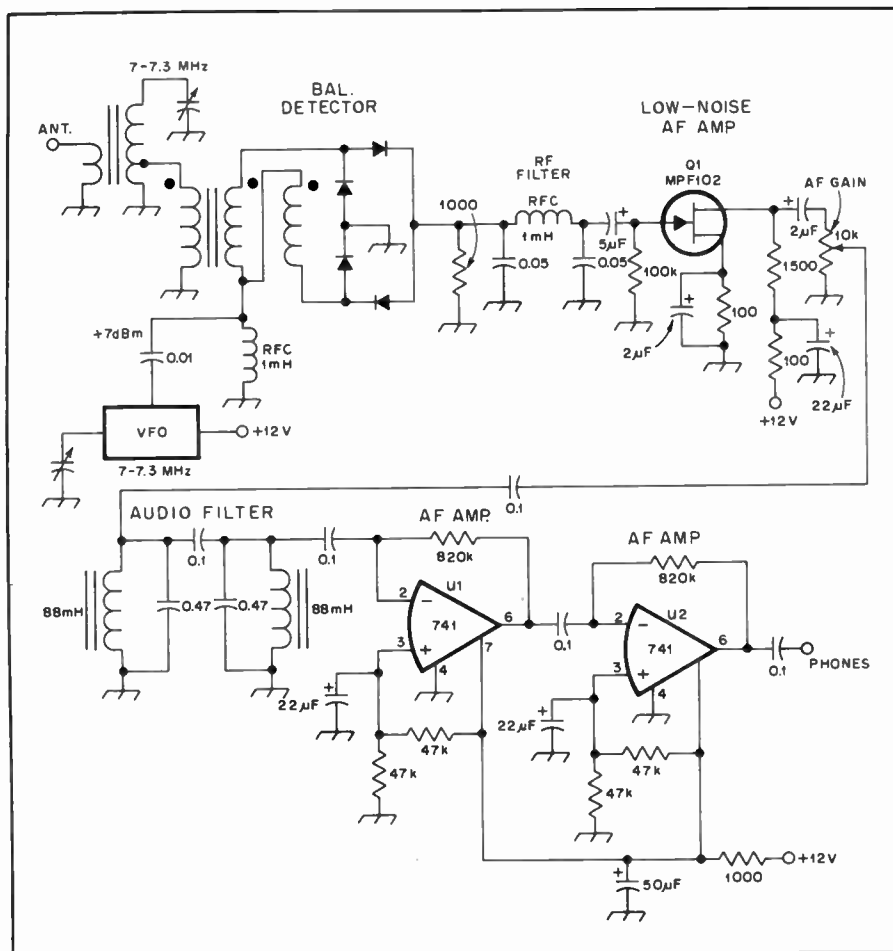


Fig. 13 — Example of a practical direct-conversion receiver for 40 meters.

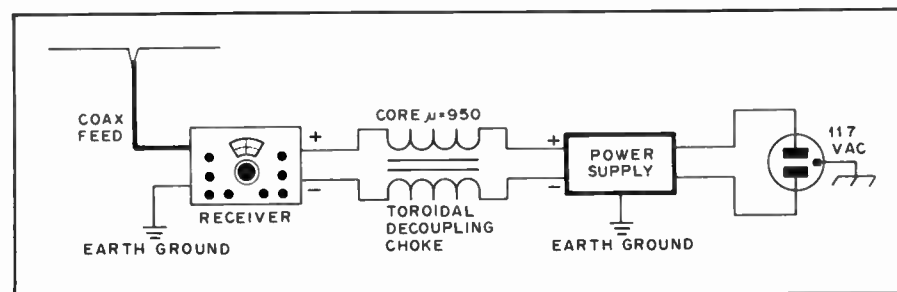


Fig. 14 — A method for eliminating common-mode hum in a direct-conversion receiver, as described by W7ZOI.

audio amplifier. Selectivity for ssb and cw reception can be had by including a passive or RC active audio filter after the gain control. Fig. 13 contains a circuit which shows a typical direct-conversion receiver in its entirety. As was stated earlier, the detector is operating as a product detector rather than a mixer, and the VFO is serving as a BFO. The difference frequency between the incoming 7-MHz signal and the 7-MHz BFO injection voltage is at audio frequency (zero i-f). This is amplified by means of Q1, filtered through a passive LC audio network, then amplified by two 40-dB op-amp stages. It is possible to copy a-m signals with this type of receiver

by tuning the signal in at zero beat.

Direct-conversion receivers of the type illustrated in Fig. 13 provide double-signal reception. That is, a cw beat note will appear either side of zero beat. This is useful during sideband reception, wherein the upper sideband is received on one side of zero beat and the lower sideband will appear on the opposite side of zero beat. QRM will be greater, of course, with this kind of receiver because there is no rejection of the unwanted sideband. Some designers have contrived elaborate circuits which, by means of phasing networks, provide single-signal reception. Unfortunately, the circuit becomes nearly as complex as that of superheterodyne. The

benefits obtained are probably not worth the effort.

Direct-conversion receivers are not especially suitable above 14 MHz because it is difficult to secure adequate BFO stability at so high a frequency. A practical solution to the problem is the employment of a heterodyne BFO chain in which a 5-MHz VFO is heterodyned with crystal-controlled oscillators. Direct-conversion receivers are ideal for use in simple transceivers because the BFO can be used also as the frequency source for the transmitter, provided the appropriate frequency offset is included between transmit and receive to permit copy of ssb and cw signals without readjusting the BFO.

### Characteristic Faults

A major difficulty connected with direct-conversion receivers is *microphonics*. The effect is noted when the operating receiver is bumped or moved. An annoying ringing sound is heard in the receiver output until the mechanical vibration ceases. The simple act of peaking the front end or adjusting the volume control can set off a microphonic response. This trait is caused by the extreme high gain needed in the audio amplifier. Slight electrical noises in the receiver front end, caused by small vibrations, are amplified many times by the time they reach the speaker or phones. The best precautionary measure to reduce microphonics is to make all of the detector and BFO circuit leads and components as rigid as possible. Addition of an rf amplifier stage ahead of the detector will also help by virtue of increasing the front-end gain. This reduces the amount of audio gain needed to copy a signal, thereby diminishing the loudness of the microphonics.

The other common problem inherent in direct-conversion receivers is hum (Fig. 14). The fault is most pronounced when an ac type of power supply is used. The hum becomes progressively worse as the operating frequency is increased. For the most part, this is caused by ac ground loops in the system. The ac modulates the BFO voltage, and the hum-modulated energy is introduced in the detector directly, as well as being radiated and picked up by the antenna. The most practical steps toward a cure are to affix an effective earth ground to the receiver chassis and power supply, use a battery power supply, and feed the antenna with coaxial cable. End-fed wire antennas increase the possibility of hum if they are voltage fed (high impedance at the receiver end). Decoupling of the ac power supply leads (dc leads to the receiver) is also an effective preventive measure for hum. This was explained by Hayward, W7ZOI, in July 1977 *QST*, page 51. The cure is to add a toroidal decoupling



choke, bifilar wound, in the plus and minus dc leads from the power supply. This will prevent high-impedance rf paths

between the power supply and receiver. The effect is to prevent BFO energy from entering the power supply, being modula-

ted by the rectifier diodes and being reradiated by the ac line. This form of buzz is called "common-mode hum."

## Superheterodyne Receivers

Nearly all of the present-day communications receivers are structured as *superheterodyne* types. Fig. 15 shows a simple block diagram of a single-conversion superheterodyne circuit. This basic design has been popular since the 1930s, and only a few general circuit enhancements have been introduced in recent years. Sophisticated versions of this type of receiver use various alternatives to the circuits indicated in the block diagram. The local oscillator, for example, might utilize a phase-locked loop or synthesizer type of LO chain rather than a straight VFO. Digital readout is used in some models in place of the more traditional analog readout method. Rf types of noise blankers (often very complex) are chosen by some designers in preference to simple

shunt audio noise limiters. An assortment of techniques is being used to improve the overall selectivity of these receivers — elaborate i-f filtering, RC active or LC passive audio filters. However, the basic circuit concept remains unchanged. The advancement of greatest significance in recent years is the changeover from vacuum tubes to semiconductors. This has increased the life span of the of the equipment, improved overall efficiency, aided stability (reduced heating), and contributed to greater ruggedness and miniaturization.

Some manufacturers still produce double- or multiconversion superheterodyne receivers, but the circuits are similar to that of Fig. 15. Multiconversion receivers have a second mixer and LO chain for the

purpose of making the second i-f lower than the first. This helps to increase the overall selectivity in some designs, but it often degrades the receiver dynamic range through the addition of a second mixer. Multiconversion receivers are more prone to spurious responses than is the case with single-conversion designs, owing to the additional oscillator and mixing frequencies involved. The "cleanest" performance is obtained from properly designed single-conversion receivers.

### Circuit Function

In the example of Fig. 15 it is assumed that the receiver is adjusted to receive the 20-meter band. Front-end selectivity is provided by the resonant networks before and after the rf amplifier stage. This part

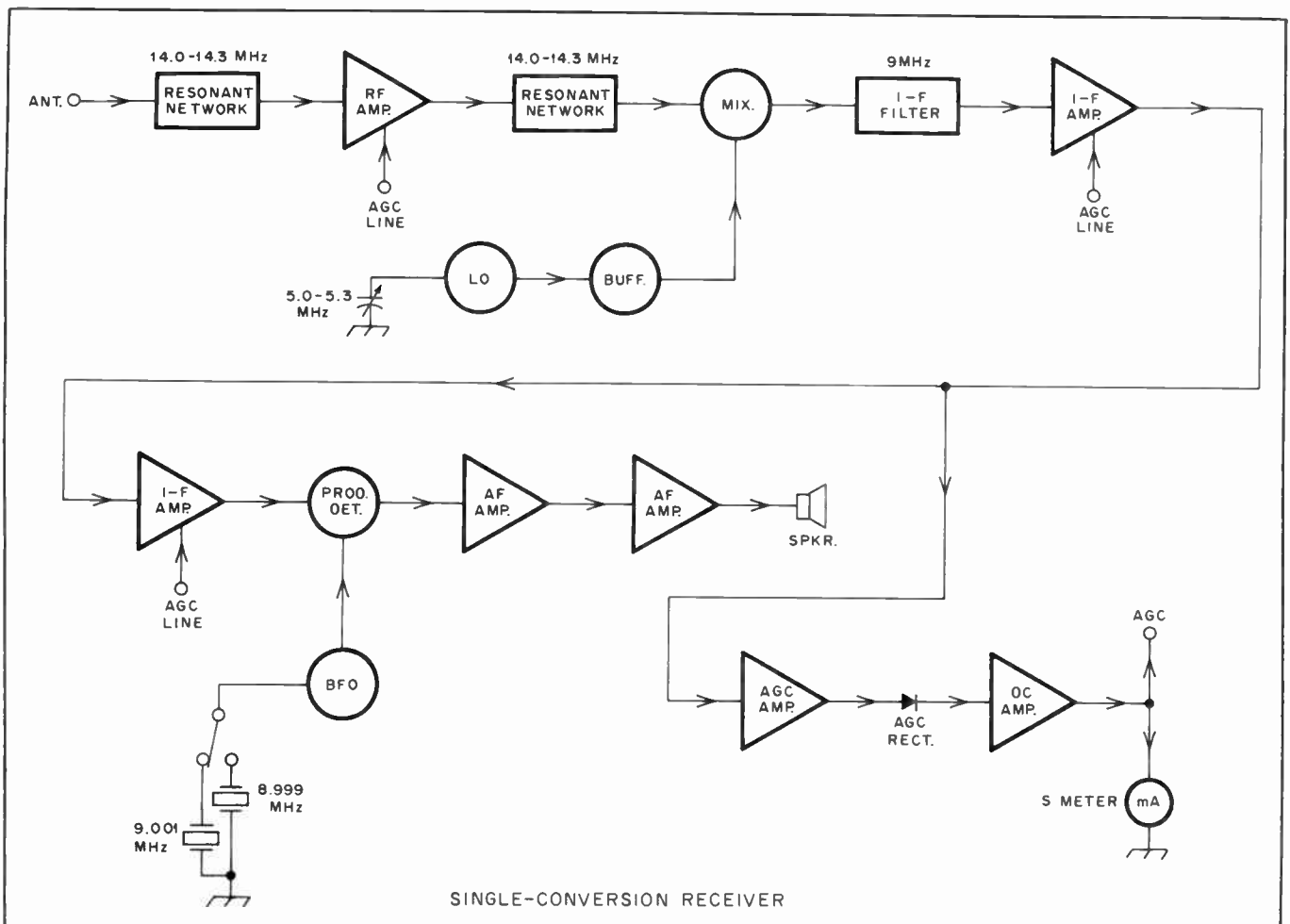


Fig. 15 — Block diagram of a single-conversion superheterodyne receiver for 20 meters. The arrows indicate the direction of signal and voltage components.

of the receiver is often called the *preselector*, meaning that it affords a specific degree of front-end selectivity at the operating frequency. The rf amplifier increases the level of the signal from the antenna before it reaches the mixer. The amount of amplification is set by the designer, consistent with the overall circuit requirements (gain distribution). Generally, the gain will be from a few dB to as much as 25 dB.

When the incoming signal reaches the mixer it is heterodyned with the local-oscillator frequency to establish an i-f (intermediate frequency). The i-f can be the *sum* or the *difference* of the two frequencies. In the example given, the i-f is the difference frequency, or 9 MHz.

An i-f filter (crystal lattice or ceramic monolithic) is used after the mixer. At low intermediate frequencies (455 kHz and similar), mechanical filters are often used. The i-f filter sets the *overall receiver selectivity*. For ssb reception it is usually 2.1 kHz wide at the 3-dB points of the filter response curve. For cw reception it is between 200 and 500 Hz in bandwidth, depending upon the design objective. Wider filters are available for a-m reception.

Output from the i-f filter is increased by one or more amplifier stages. The overall gain of most i-f strips varies from 50 to 100 dB. The amount of signal gain is determined by the design objective, the type of amplifier devices used, and the number of gain stages.

The amplified i-f energy is routed to a product detector where it is mixed with the beat-frequency oscillator output. This produces an audio-frequency voltage which is amplified and fed to a speaker or headphones. The BFO is adjusted for reception of the upper or lower sideband, depending on which is appropriate at the time. In either case the BFO frequency is offset slightly from the center frequency of the i-f filter. For ssb reception it is usually offset approximately 1.5 kHz, in which case it falls on the slope of the i-f response curve. For cw reception the BFO is offset approximately 700 Hz from the i-f filter center frequency to produce a 700-Hz peak audio tone in the speaker. Other values of cw offset are common, but 700 Hz is preferred by many cw operators.

The overall gain of the receiver can be adjusted manually (by means of a panel-mounted control) or automatically. The latter is accomplished by means of an *agc* circuit. Energy can be sampled from the i-f amplifier output or the audio amplifier. Depending on the method used, the resultant agc is called *i-f derived* or *audio derived*. There are many arguments pro and con about which method is best. They shall not be considered here. In Fig. 15 the agc voltage is sampled from the i-f strip, amplified by the agc amplifier and then rectified to provide a dc control voltage. A dc amplifier is used to drive the

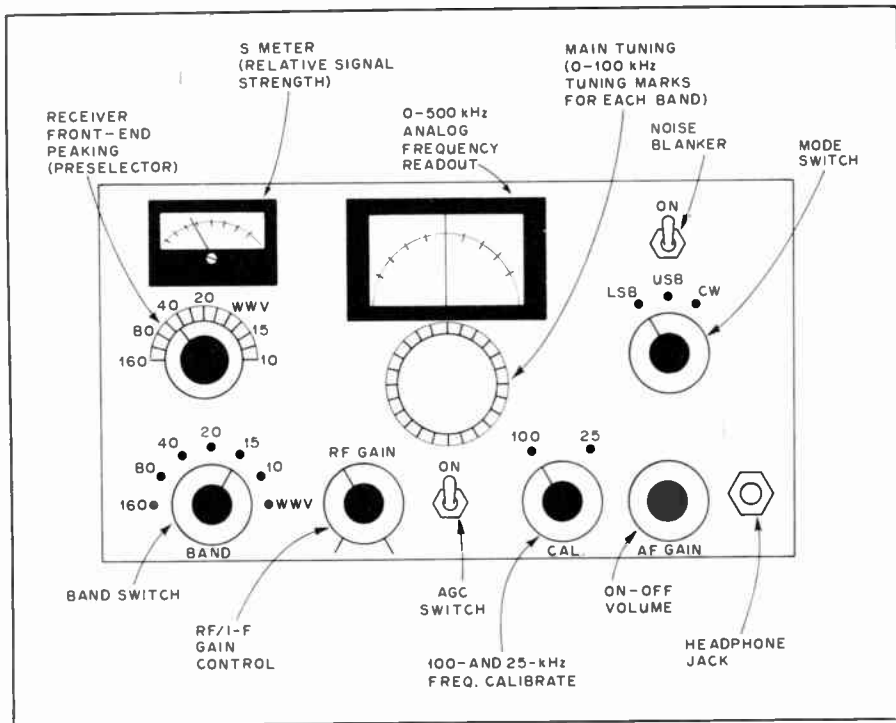


Fig. 16 — Layout of a typical modern amateur receiver.

agc terminals of the rf and i-f amplifiers. It can be used also to operate an S meter for observing relative signal-strength levels. When the incoming signal is weak the gain-controlled stages operate fully. As the incoming signal becomes stronger the agc circuit starts lowering the gain of the rf and i-f stages, thereby leveling the audio output at the speaker. A well-designed agc system will provide a uniform level of audio output (at a given af-gain control setting) over an incoming signal-level variation of 100 dB. The net effect is to prevent overloading of some of the receiver stages and to protect the operator from the startling effect of tuning from a weak signal to an extremely loud one. Fig. 16 shows the front panel and controls for a typical amateur-band superheterodyne receiver.

### Local Oscillators

A good communications receiver contains oscillators that operate in a stable and spectrally pure manner. Poor oscillator performance can spoil the best of receivers even though all other parts of the circuit are functioning in elegant fashion. Not only should the oscillator be stable with regard to short- and long-term drift, it should have minimum noise in the output (at least 80 dB below the peak value of the fundamental energy) and be reasonably free of spurious responses. Concerning the latter, it is not difficult to design an oscillator which has all harmonics attenuated by 60 or 70 dB. Another important characteristic of an oscillator is quick starting when operating

voltage is applied.

Oscillator instability can result from a host of poor design practices. To improve the stability characteristics it is useful to observe the following:

- 1) Use regulated operating voltages (well filtered).
- 2) Avoid whenever possible the use of magnetic core material in the oscillator tank coil. Air-wound or ceramic-form coils are best if they are rigid.
- 3) Use temperature-stable, fixed-value capacitors in the frequency-determining part of the circuit. Polystyrene and silver-mica capacitors are recommended.
- 4) Ensure that all mechanical and electrical components are secured rigidly in their part of the circuit. This will lessen the chance for mechanical instability.
- 5) Build the oscillator on a firm, flex-free chassis.
- 6) When practical, enclose the oscillator in its own shield compartment and use rf filtering in the dc supply leads. Needless to say, the more constant the ambient temperature surrounding the oscillator, the greater will be the frequency stability.

Precautions should be taken to ensure that the oscillator in a receiver looks into a constant load impedance. Even minute load changes will cause phase shifts which can affect the oscillator frequency. The effect is more pronounced with VFOs than it is with crystal-controlled oscillators. Because of these conditions it is good design practice to couple very lightly to the oscillator stage. The power level can be increased by adding one or more

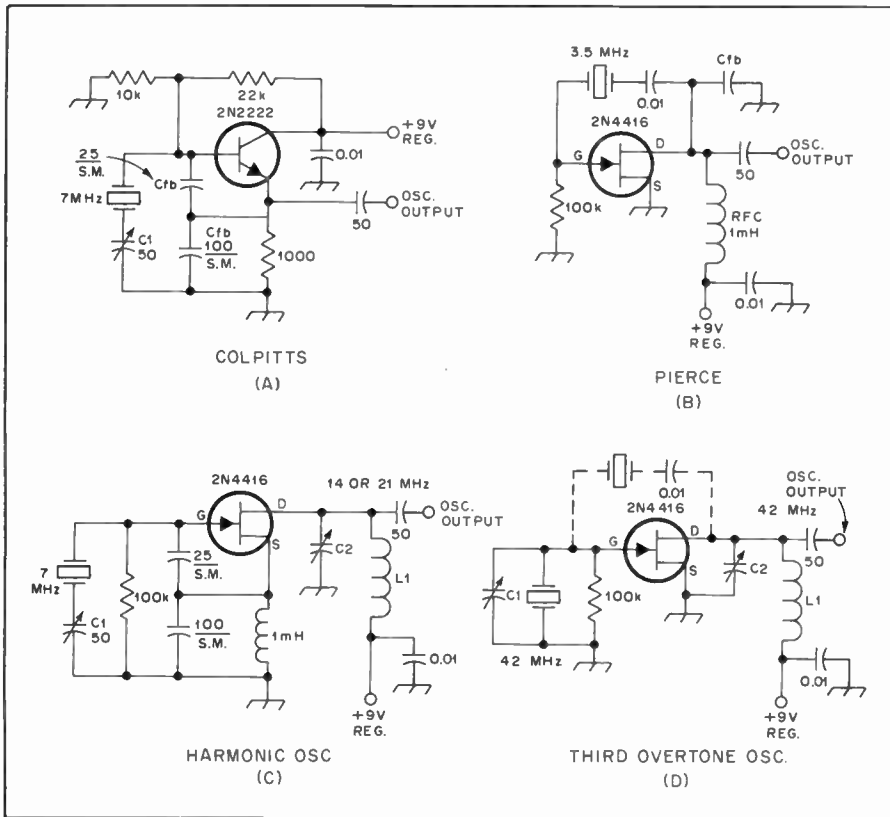


Fig. 17 — Practical examples of crystal-controlled oscillators.

buffer/amplifiers before the oscillator signal is supplied to the mixer or detector.

Changes in operating voltage will result in frequency shifts. It is for this reason that regulated voltage is recommended for oscillators. Zener diodes are adequate for the purpose.

Magnetic cores, such as those in slug-tuned coils, change their properties with variations in ambient temperature, thereby causing inductance changes which can severely affect the oscillator frequency. Furthermore, mechanical instability can result if the slugs are not affixed securely in the coil forms. Toroidal inductors are similarly unsuitable for use in stable VFOs.

Oscillator noise can be held to an acceptable level by employing high-Q tuned circuits. The higher the tank Q, the narrower the bandwidth, and hence, the lower the noise output voltage. Excessive LO noise will have a serious effect on mixer performance.

High amounts of harmonic current in the LO-chain output can cause unwanted mixer injection. If the receiver front-end selectivity is not of high magnitude, spurious signals from outside the band of interest will be heard along with the desired ones. Harmonic energy can degrade the performance of some kinds of mixers, making it worthwhile to use suitable filtering at the LO-chain output.

### Crystal Oscillators

Although there is a wide variety of

crystal-controlled oscillator circuits that provide acceptable performance in amateur equipment, only a few of the popular ones will be highlighted here. In the circuits offered as illustrations, the feedback must be ample to assure quick starting of the oscillator. Some circuits function quite well without the addition of external feedback components (internal capacitance within the transistor or tube being adequate). Other circuits need external feedback capacitors. Poor-quality (sluggish) crystals generally require larger amounts of feedback to provide operation which is comparable with that of lively crystals. Some surplus crystals are sluggish, as can be the case with those which have been reground or etched for a different operating frequency. Therefore, some experimentation with feedback voltage may be necessary when optimizing a given circuit. As a rule of thumb it is necessary to use one-fourth of the oscillator output power as feedback power, to ensure oscillation.

Fig. 17 shows four common types of oscillator. The same circuits can be used with tubes by applying the appropriate operating voltages. C1 is included for adjusting the crystal to the frequency for which it has been ground. In circuits where considerable shunt capacitance is present (Fig. 17A and C) the trimmer is usually connected in series with the crystal. When there is minimal parallel capacitance (approximately 6 pF in the circuits at B and D, Fig. 17) the netting

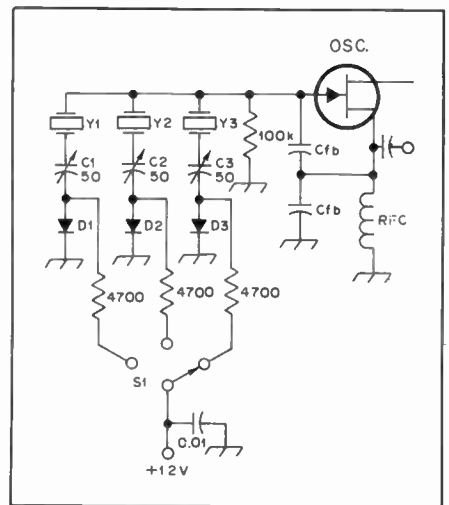


Fig. 18 — Method for changing crystals by means of diode switching.

trimmer can be placed in parallel with the crystal. Whether a series or parallel trimmer is used will depend also on the type of crystal used (load capacitance and other factors).

Feedback capacitance ( $C_{fb}$ ) for the circuit at B in Fig. 17 must be found experimentally. Generally, a value of 100 pF will suffice for operation from 3.5 to 20 MHz. As the operating frequency is lowered it may require additional capacitance. The drain rf choke should be self-resonant below operating frequency.

A third-overtone crystal is illustrated at Fig. 17D. Satisfactory operation can be had by inserting the crystal as shown by the dashed lines. This method is especially useful when low-activity crystals are used in the overtone circuit. However, C1 will have little effect if the crystal is connected from gate to drain, as shown. C2-L1 is adjusted slightly above the desired overtone frequency to ensure fast starting of the oscillator. The circuits shown in Fig. 17 can be used with dual-gate MOSFETs also, assuming that gate 2 is biased with a positive 3 to 4 volts.

A large number of crystals can be switched by means of silicon diodes in the manner shown at Fig. 18. The advantage of this technique is that the switching is done at dc, thereby permitting the control point to be a considerable distance from the oscillator circuit. D1 through D3, inclusive, are 1N914 diodes or equivalent.

### VXO Circuits

Variable-frequency crystal oscillators (VXOs) are useful in place of conventional crystal oscillators when it is necessary to "rubber" the crystal frequency a few kHz. AT-cut crystals in HC-6/U type holders seem to provide the greatest frequency change when used in a VXO. To obtain maximum frequency shift it is vital to reduce stray circuit capacitance to the smallest possible

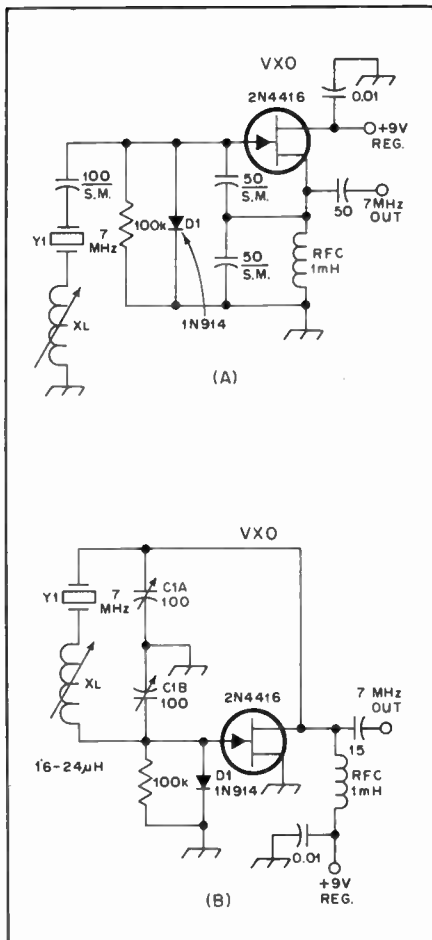


Fig. 19 — Circuits for two types of VXOs.

amount. This calls for low-capacitance switches, low minimum-capacitance variable capacitors, and the avoidance of crystal sockets. The crystals should be spaced well away from nearby metal surfaces and circuit components to further reduce capacitance effects. The higher the crystal fundamental frequency, the greater the available frequency swing. For example, a 3.5-MHz crystal might be moved a total of 3 kHz, whereas a 7-MHz crystal could be shifted 10 kHz. Although some amateurs claim shifts as great as 50 kHz at 7 MHz, the circuit under those conditions is no longer operating as a true VXO. Rather, it has gone into the VFO mode. In a situation of that kind the high-stability traits of a VXO are lost.

Fig. 19 contains a simple VXO circuit at A. By adjusting  $X_L$  the operator can shift the crystal frequency. The range will start at the frequency for which the crystal is cut and move lower. D1 in both circuits is included to stabilize the FET bias and reduce the transistor junction capacitance during the peak of the positive rf-voltage swing. It acts as a clamp, thereby limiting the transistor  $g_m$  at peak-voltage periods. This lowers the junction capacitance and provides greater VXO swing. D1 also reduces harmonic output from the VXO by restricting the nonlinear change in

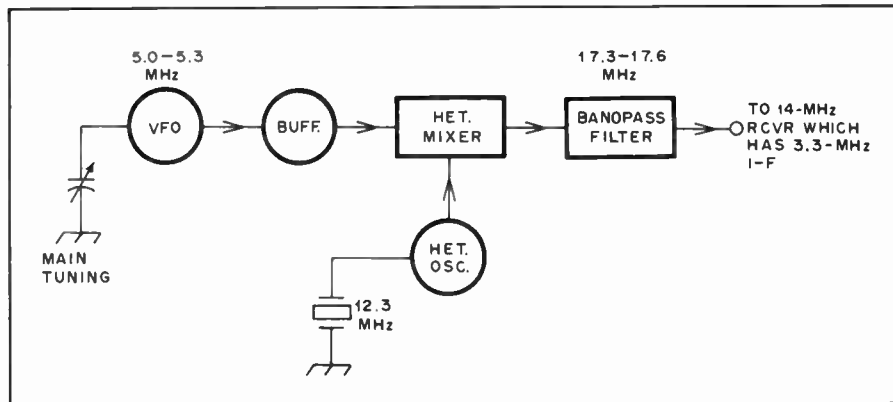


Fig. 20 — Technique for heterodyne frequency generation in a receiver.

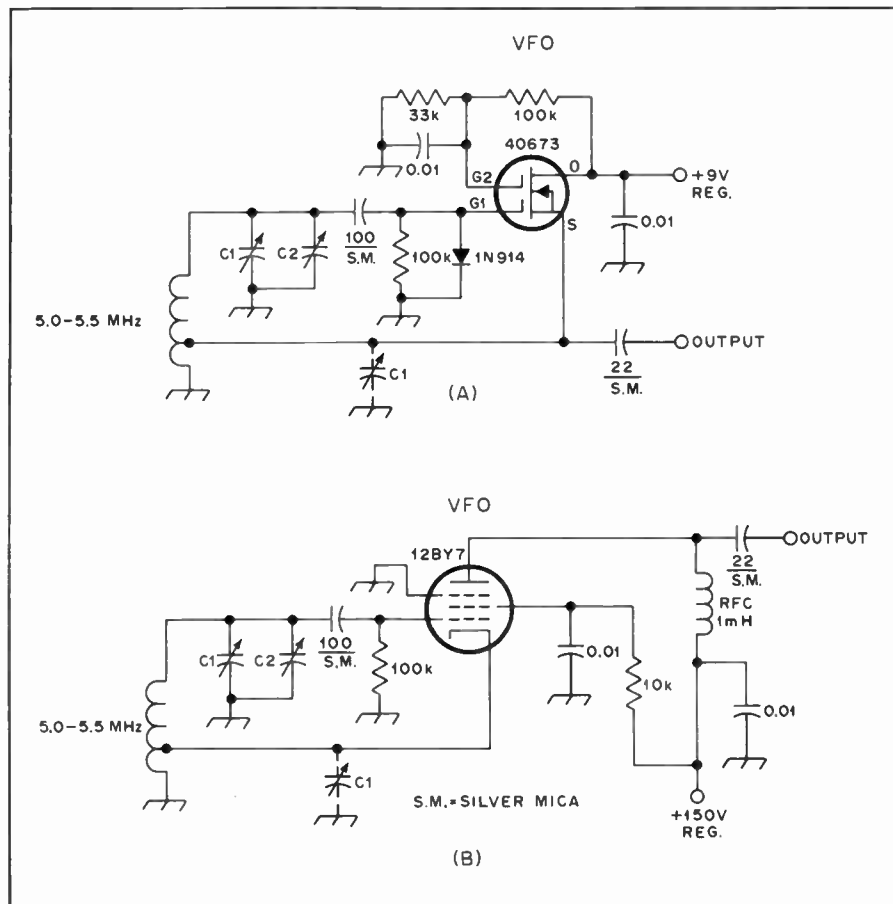


Fig. 21 — Examples of electron-coupled VFOs.

transistor junction capacitance — a contributing factor to the generation of harmonic currents. Clamp diodes are used for the same purpose in conventional FET VFOs. The circuit of Fig. 19A will provide a swing of approximately 5 kHz at 7 MHz.

An improved type of VXO is presented at B in Fig. 19. Depending upon the exact characteristics of the crystal used at Y1, swings as great as 15 kHz are possible.  $X_L$  is set initially for a reactance value that will provide the maximum possible frequency shift when C1 is tuned through its range. The frequency shift should be

only that which corresponds to true VXO control, even though greater range can be had after the circuit ceases to be a highly stable one.  $X_L$  is not adjusted again. A buffer stage should be used after either of the VXO circuits to prevent frequency pulling during load changes.

VXOs of this general type are useful in portable transmitters and receivers when full band coverage is sacrificed in exchange for stability and simplicity. Output from VXOs can be multiplied several times to provide LO energy for vhf and uhf receivers and transmitters. When that is done it is possible to realize 100 kHz or



more of frequency change at 144 MHz.

### VFO Circuits

Variable-frequency oscillators are similar in performance to the VXOs which were described in the foregoing text. The essential difference is that greater frequency coverage is possible, and no crystals are used. The practical upper frequency limits for good stability range between 7 and 10 MHz. For operation at higher frequencies it is better to employ a heterodyne type of VFO. This calls for a VFO operating at, say, 5 MHz. The VFO output is heterodyned in a mixer with energy from a crystal-controlled oscillator to provide a resultant sum or difference frequency at the desired LO-chain output frequency. A block diagram is given at Fig. 20 to illustrate the concept. Most modern receivers employ this style of local-oscillator circuit. The heterodyne

oscillator has a crystal for each amateur band accommodated by the receiver. The crystals and appropriate bandpass filters are switched by means of a panel-mounted control. The band-pass filter (Fig. 20) is desirable in the interest of preventing 5- and 12.3-MHz energy from reaching the receiver mixer. A doubly balanced mixer is recommended if minimum unwanted energy is desired at the mixer output.

Some typical VFOs are shown in Figs. 21 and 22. A vacuum-tube ECO (electron-coupled oscillator) is compared to a similar one which utilizes a dual-gate MOSFET in Fig. 21. The capacitor shown in dashed lines (C1) can be used in that part of the circuit rather than at the low end of the tank coil if greater bandwidth is desired. C1 is the main-tuning capacitor and C2 is the padder for calibrating the oscillator. The coil tap is approximately

25 percent of the total number of turns for proper feedback.

A comparison is drawn in Fig. 22 between a bipolar transistor and JFET version of a series-tuned Colpitts oscillator (some times called a "series-tuned Clapp"). This type of oscillator can be made very stable by using polystyrene capacitors in the frequency-determining part of the circuit. Silver-mica capacitors are satisfactory if they have been graded out for temperature stability, but most run-of-the-mill, silver-mica units have unpredictable characteristics in this regard. Some are very stable, while others from the same lot may exhibit positive or negative drift characteristics. Polystyrene capacitors are considerably better in this respect. These VFO circuits can be scaled to other operating frequencies by using the values shown to determine the reactances of the capacitors. This information will enable the designer to select approximate values in pF for other frequencies.

Fig. 23 illustrates a composite VFO which has a buffer stage that is followed by an amplifier. D1 can be included to provide the necessary frequency offset when switching the receiver from upper to lower ssb. This is necessary in order to eliminate the need to readjust the receiver calibration dial when changing sidebands. C1 is adjusted for the desired offset amount. The pi-network output from the amplifier stage is designed to transform 500 ohms to 50 ohms. The low-impedance output is desirable in the interest of minimum frequency pulling from load changes. A 3300-ohm swamping resistor is used across the pi-network inductor to broadband the tuned circuit and to prevent any tendency toward instability when a high-impedance load is attached to the circuit. Long-term drift measure-

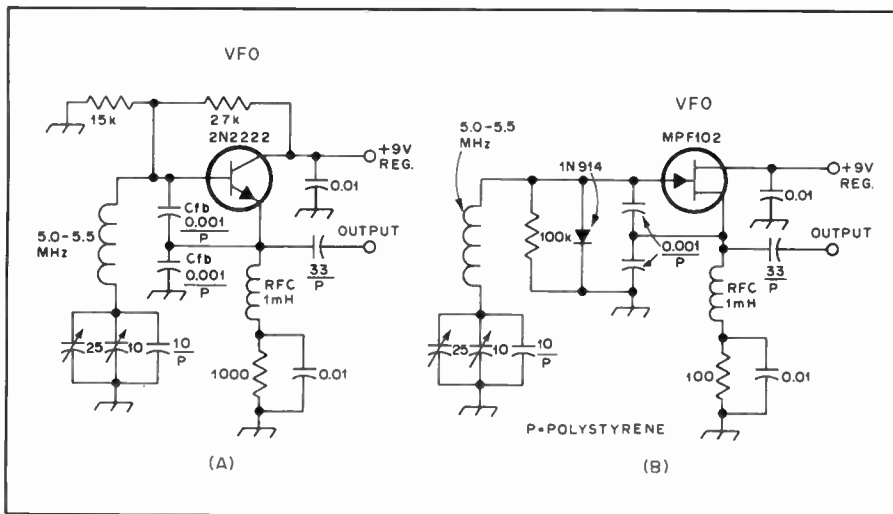


Fig. 22 — Colpitts VFOs. A bipolar transistor type is seen at A, while a FET version is given at B.

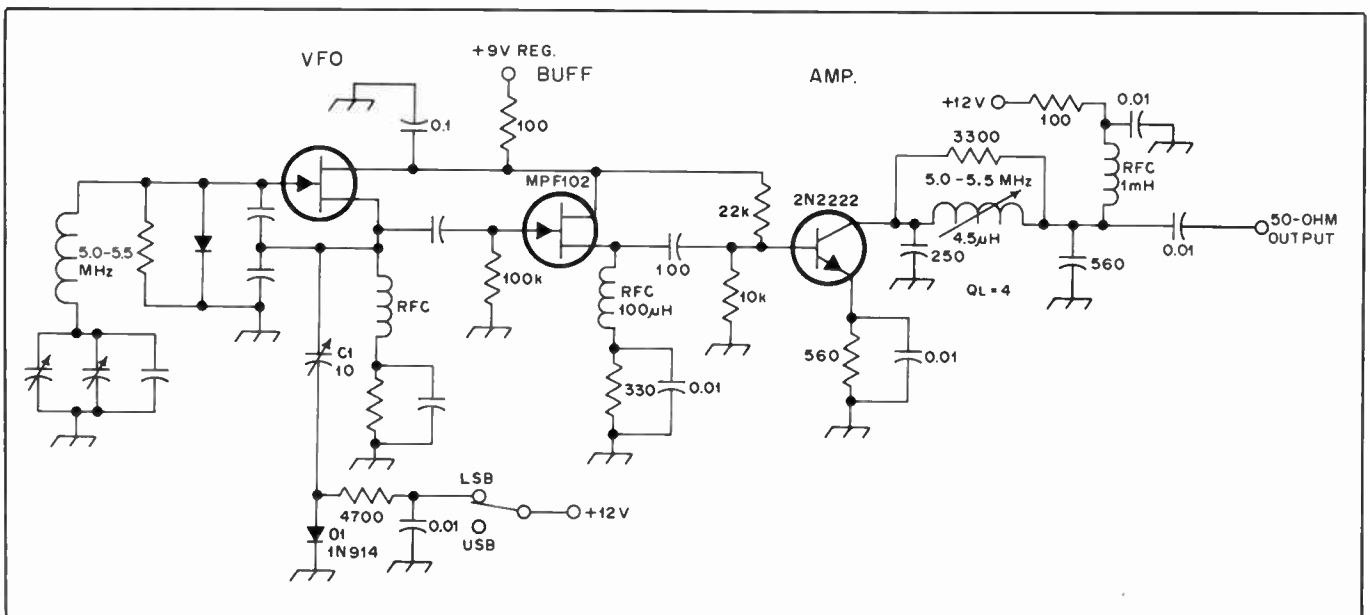


Fig. 23 — Suggested circuit for a stable series-tuned Colpitts VFO. Buffering follows the oscillator to increase the output level and provide load isolation.

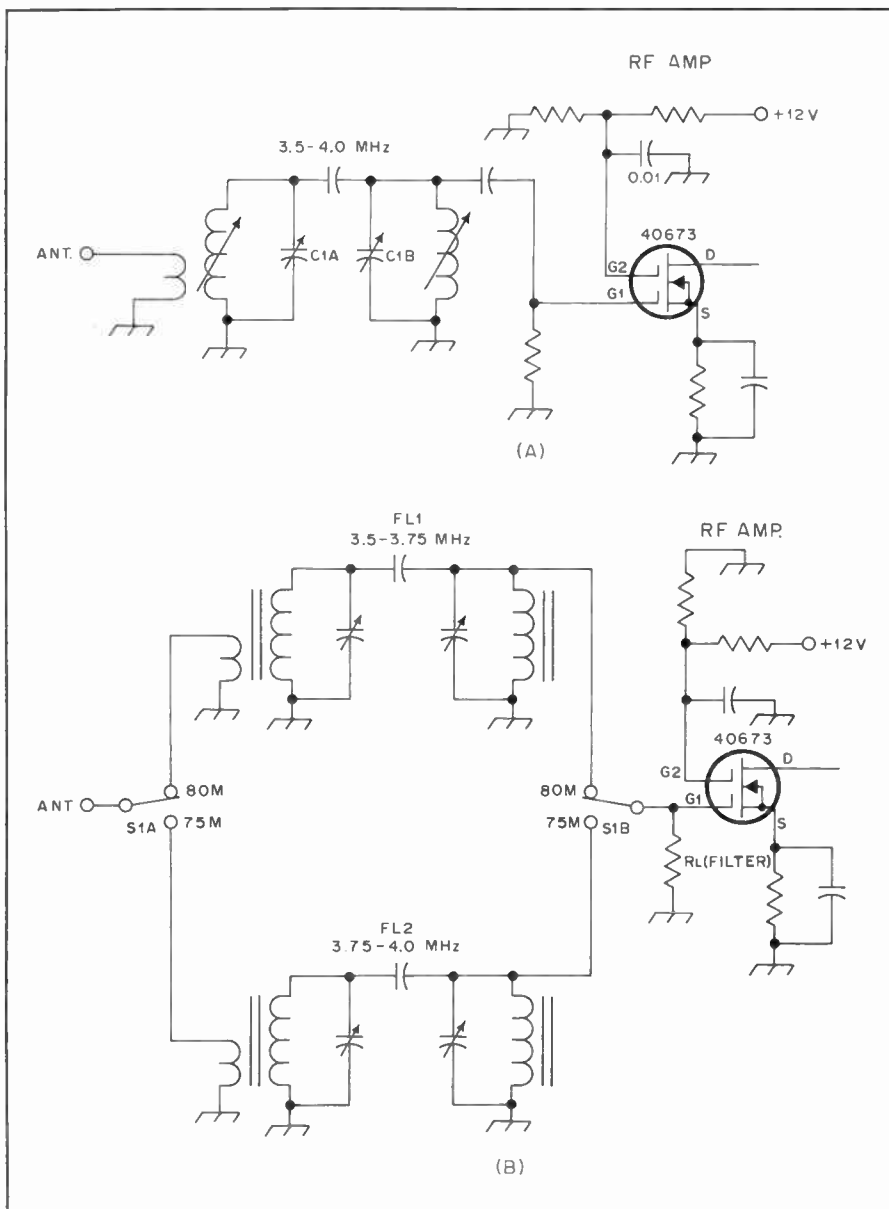


Fig. 24 — Method for selecting band-pass filters for 75 and 80 meters at the input to an rf amplifier.

ments with this type of circuit at the frequency specified indicated a maximum shift of 60 Hz over a three-hour period. Output was measured at approximately 1 volt rms across 50 ohms.

### Receiver Front Ends

The designer has a number of options available when planning the input section of a receiver. The band-pass characteristics of the input tuned circuits are of considerable significance if strong out-of-band signals are to be rejected — an ideal design criterion. Most of the commercial receivers available to the amateur use tuned circuits which can be adjusted from the front panel of the equipment. The greater the network Q, the sharper the frequency response, and hence, the better the adjacent-frequency rejection. For a given network design the bandwidth doubles for each octave higher. That is, an 80-meter

front-end network may have a 3-dB bandwidth of 100 kHz for a given Q and load factor. At 40 meters the same type of network would be 200-kHz wide at the 3-dB points of the response curve. It is for this reason that most receivers have a tunable front-end section (preselector). If fixed-tuned filters were used, at least two such filters would be necessary to cover from 3.5 to 4 MHz or 1.8 to 2.0 MHz, this would complicate the design and cost of the equipment.

Fig. 24 shows the two concepts just discussed. The circuit at A covers all of the 80-meter band, and if selective enough offers some in-band rejection. A pair of Butterworth band-pass filters might be used at FL1 and FL2 of Fig. 24 to cover all of the 80-meter band. A lot of additional components would be required, and the in-band rejection of unwanted signals would be less than in the

case of circuit A. The principal advantage to the circuit at B is that front-panel peaking adjustments would not be necessary once the trimmers in the filters were set for the desired response. A similar tuned circuit for either example in Fig. 24 would be used between the rf amplifier and the mixer.

Regardless of the type of LC input network used, a built-in step attenuator is worth considering. It can be used for measuring changes in signal level, or to reduce overloading effects when strong signals appear in the receiver passband. Fig. 25 shows how this can be done. The example at A is suitable for simple receivers when calibration in dB is not a requisite, and when maintaining an impedance match between the tuned circuit and the antenna is not vital. The circuit at B is preferred because the pads are of 50 ohm impedance. In the circuit shown there are three steps available: 6, 12 and 18 dB, depending on how the switches are thrown. The resistance values specified are the closest standard ones to the actual values needed to provide precisely 6 or 12 dB of attenuation. For amateur work the accuracy is adequate. Front-end attenuators are useful when vhf converters are used ahead of the station receiver. If the converters have a significant amount of overall gain they can degrade the dynamic range of the main receiver when strong signals are present. The attenuators can be set to simulate a condition of unity gain through the converter, thereby aiding receiver dynamic range. It is worth remembering, however, that an attenuator used at the *input* of a receiver when no converter is attached will degrade receiver sensitivity and noise figure. A receiver used frequently for antenna and received-signal dB measurements might have several 3-dB pads included, thereby providing greater resolution during measurements.

### RF Amplifiers

It was implied earlier in the chapter that rf amplifiers are useful primarily to improve the receiver noise figure. When atmospheric and man-made noise levels exceed that of the mixer it should be possible to realize better dynamic range by not having an rf amplifier. The gain of the rf stage, when one is used, should be set for whatever level is needed to override the mixer noise. Sometimes that is only a few dB. A good low-noise active device should be employed as the rf amplifier in such instances. For hf-band work 40673s, MPF102s and 2N4416s are good. Most modern receiving tubes specified for use as rf amplifiers are suitable also. For vhf work the Siliconix E300 and U310 FETs are excellent low-noise devices.

A well-designed receiver should not have agc applied to the rf amplifier. The best noise figure and rf-stage dynamic range will result when agc is not applied.

This is because the agc voltage changes the operating characteristics of the rf amplifier from Class A to a less linear mode.

Fig. 26 shows some typical rf amplifiers for use in amateur receivers. Tube-type circuits have not been included because they are not much in vogue, nor do they offer any particular advantages over solid-state amplifiers.

The circuit at A in Fig. 26 is likely to be the least subject to self-oscillation of the four examples given. The common-base hookup helps to ensure stability if the gate lead is kept as short as is physically possible. The gain from a common-gate amplifier of this type is lower than that of a common-source amplifier. However, gains up to 15 dB are entirely typical. The drain of the FET need not be tapped down on the drain coil, but if it is there will be less loading on the tuned circuit, thereby permitting somewhat greater tuned-circuit selectivity. The lower the drain tap, the less the stage gain.

All of the FET amplifiers in Fig. 26 are capable of providing low-noise operation and good dynamic range. The common-source circuits at illustrations B and C can provide up to 25 dB of gain. However,

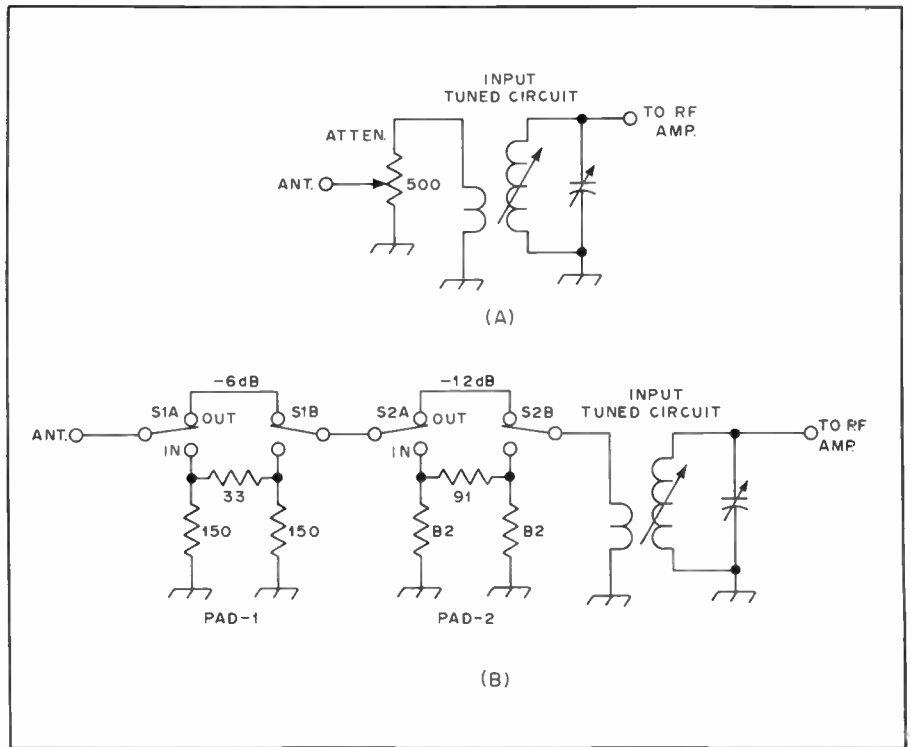


Fig. 25 — Front-end attenuators. A simple type is given at A and a step-attenuator version is seen at B.

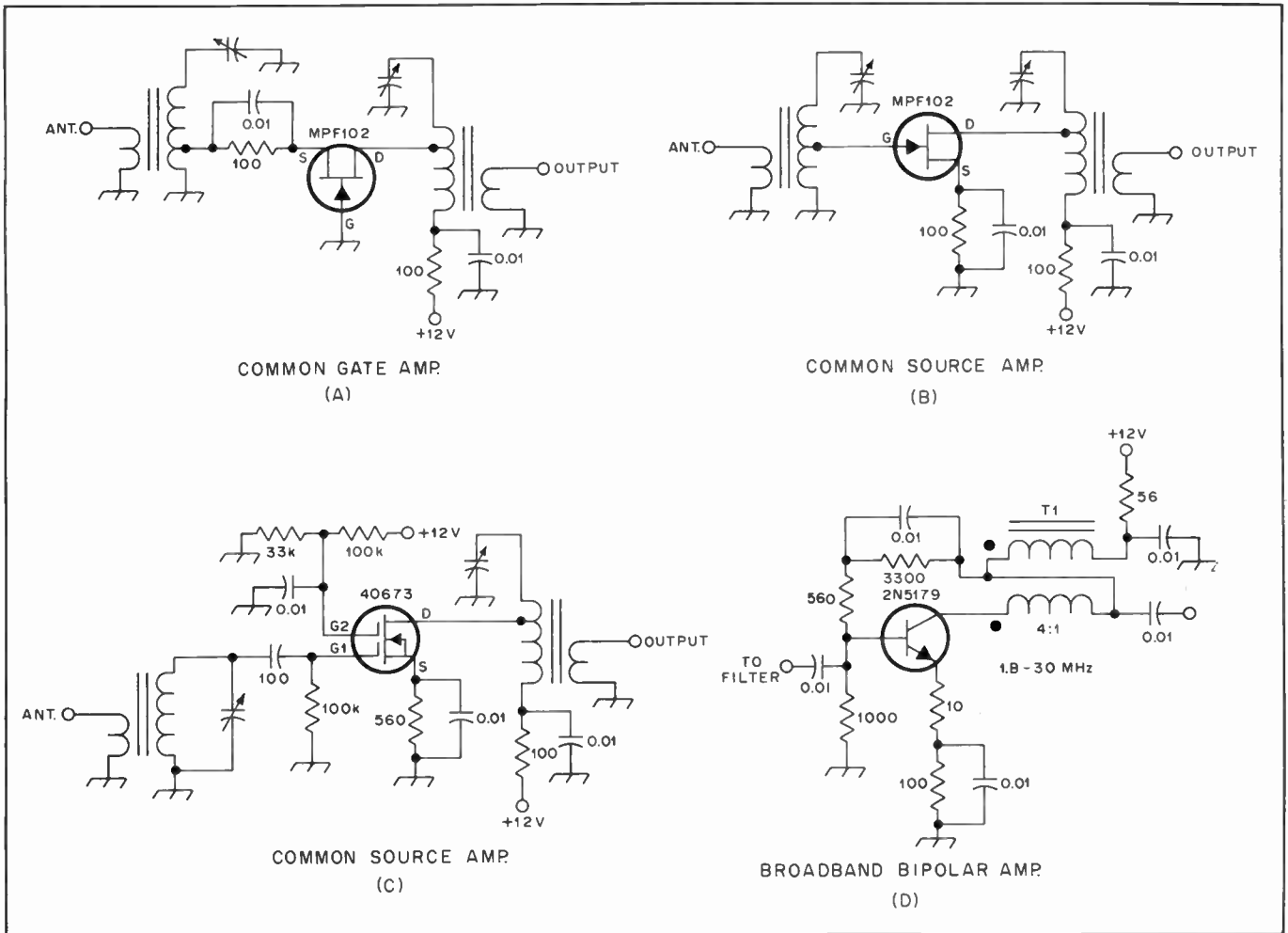


Fig. 26 — Narrowband rf amplifiers are shown from A to C. A fed-back broadband rf amplifier is seen at D.

they are more prone to instability than is the circuit at A. Therefore, the gates are shown tapped down on the gate tank: Placing the input at a low impedance point on the tuned circuit will discourage self-oscillation. The same is true of the drain tap. JFETs will hold up under considerable rf input voltage before being damaged. Laboratory tests of the MPF102 showed that 80 volts pk-pk (gate to source) were required to destroy the device. However, in the interest of good operating practices the pk-pk voltage should be kept below 10. Tapping the gate down on the input tuned circuit will result in lower levels of pk-pk input voltage, in addition to aiding stability.

A broadband bipolar-transistor rf amplifier is shown in Fig. 26 at D. This type of amplifier will yield approximately 16 dB of gain up to 148 MHz, and it will be unconditionally stable because of the degenerative feedback in the emitter and the negative feedback in the base circuit. A broadband 4:1 transformer is used in the collector to step the impedance down to approximately 50 ohms at the amplifier output. A 50-ohm characteristic exists at the input to the 2N5179 also. A band-pass filter should be used at the input and output of the amplifier to provide selectivity. The 4:1 transformer helps to assure a collector load of 200 ohms, which is preferred in an amplifier of this type. This style of amplifier is used in CATV applications where the transformation from collector to load is 300 to 75 ohms.

### Receiver Mixers

One of the most important parts of a high-performance receiver is the mixer. It is at this point where the greater consideration for dynamic range exists. For best receiver performance the mixer should receive only enough preamplifier signal to overcome the mixer noise. When excessive amounts of signal energy are permitted to reach the mixer there will be desensitization, cross-modulation and IMD products in the mixer. When these effects are severe enough the receiver can be rendered useless. Therefore, it is advantageous to utilize what is often called a "strong mixer." That is one which can handle high signal levels without being adversely affected.

Generally speaking, diode-ring passive mixers fare the best in this regard. However, they are fairly noisy and require considerably more LO injection than is the case with active mixers. For the less sophisticated types of receivers it is entirely adequate to use single-ended active mixers, provided the gain distribution between the antenna and mixer is proper for the mixer device used. Field-effect transistors are preferred by most designers; bipolar-transistor mixers are seldom used.

The primary advantage of an active mixer is that it has conversion gain rather

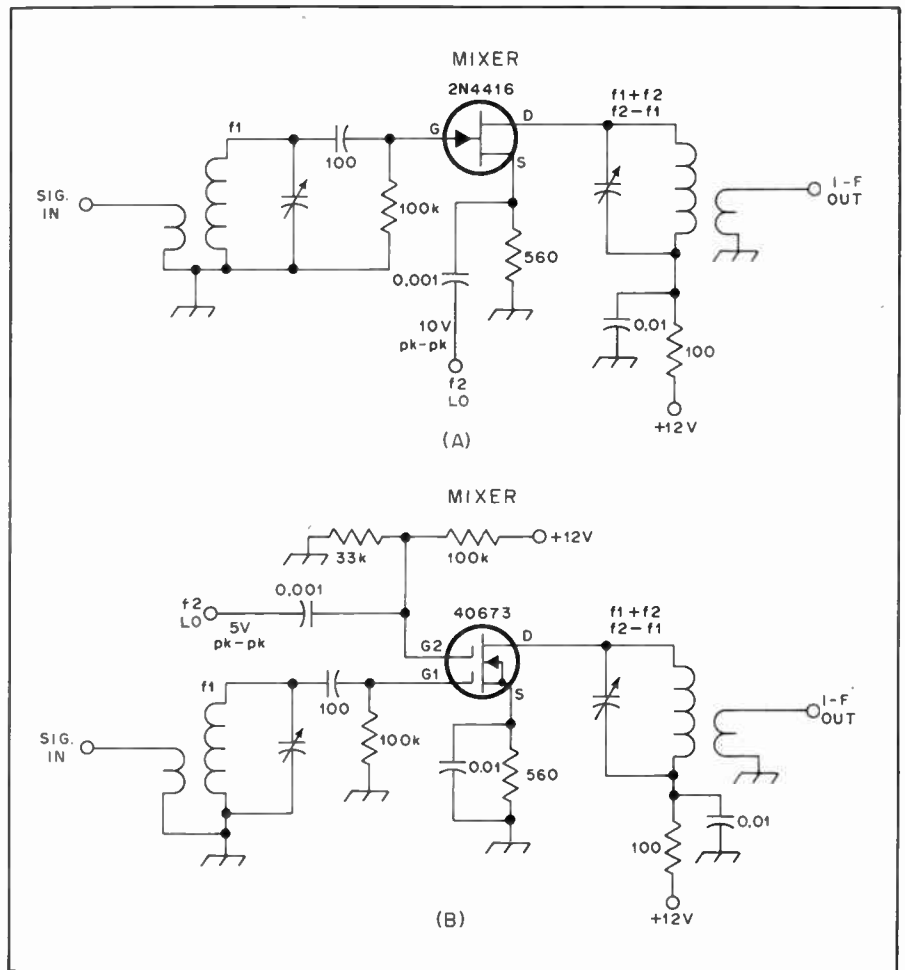


Fig. 27 — Two styles of active mixers using FETs.

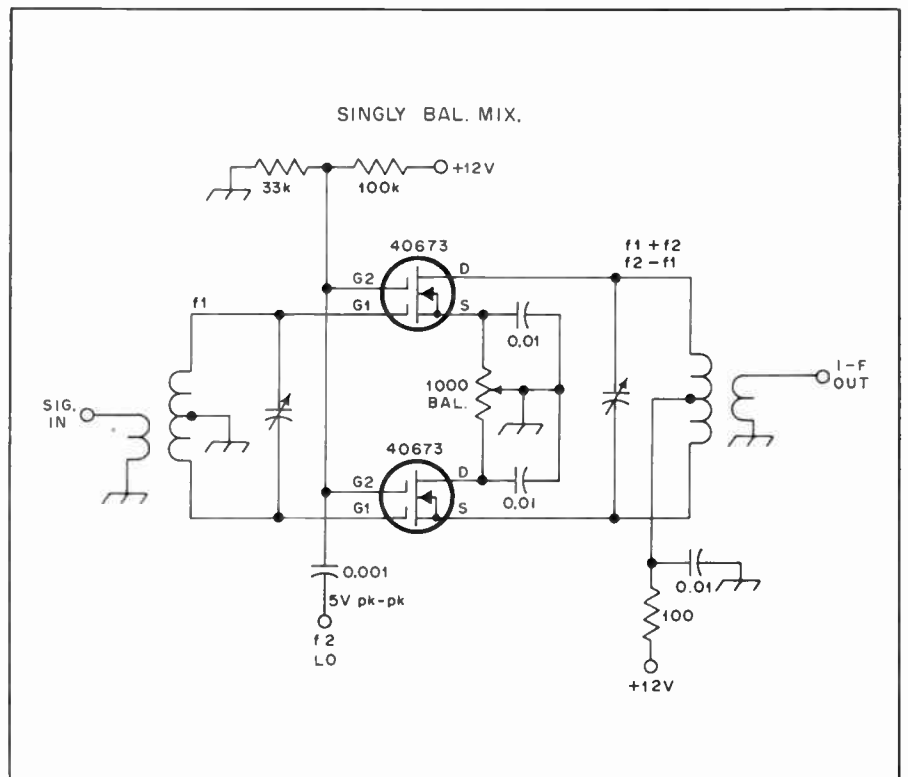


Fig. 28 — An active singly balanced FET mixer.



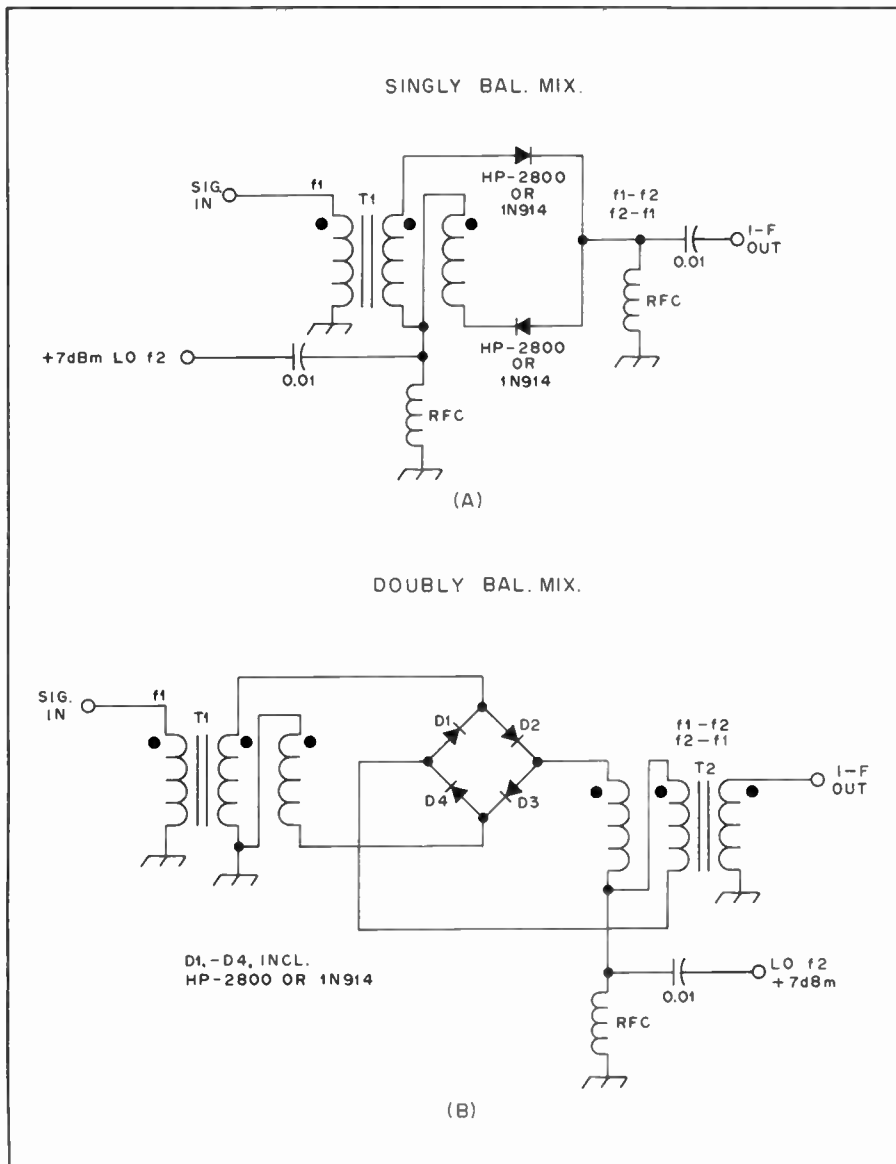


Fig. 29 — Singly and doubly balanced diode mixers.

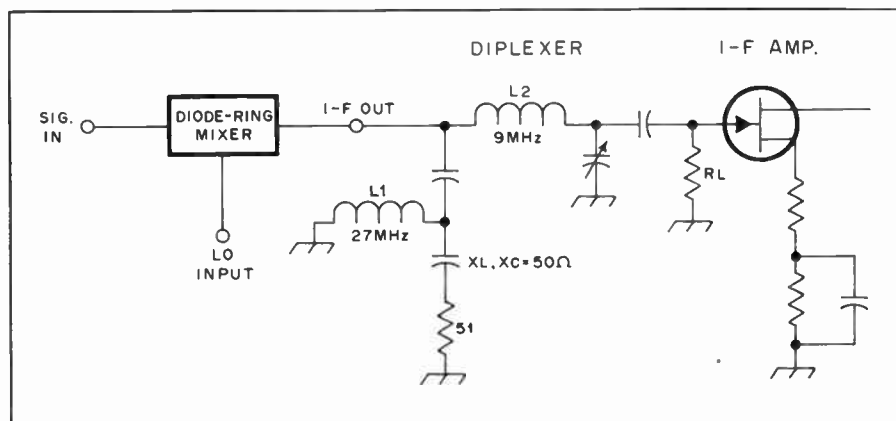


Fig. 30 — Method for diplexing the mixer output to improve the IMD characteristics.

than loss. This means that the stages following the mixer need not have as much gain as when diode mixers are used. A typical doubly balanced diode mixer will have a conversion loss of some 8 dB,

whereas an FET active mixer may exhibit a conversion gain as great as 15 dB. The cost of gain stages in this era is relatively small. This easily justifies the use of strong passive mixers in the interest of high

dynamic range.

An LC, crystal-lattice, or mechanical type of band-pass filter is almost always used after the mixer or the post-mixer amplifier. This helps to establish the overall selectivity of the receiver. It also rejects unwanted mixer products that fall outside the passband of the filter.

In the interest of optimum mixer performance, the LO energy supplied to it should be reasonably clean with respect to frequencies other than the desired LO one. Many designers, for this reason, use a band-pass filter between the LO output and the mixer input. Excessive LO noise will seriously degrade receiver performance. LO noise should be 80 dB or more below the peak level of the desired LO frequency. Excessive noise will appear as noise sidebands in the receiver output.

### Typical Mixer Circuits

Fig. 27 shows two single-ended active mixers which offer good performance. The example at A employs a JFET with LO injection supplied to the source across a 560-ohm resistor. This injection mode requires somewhat more LO power than would be used if injection was done at the gate. However, there is less occasion for LO pulling when source injection is used, and there is better isolation between the LO and antenna than would be the case with gate injection.

The circuit at B in Fig. 27 is similar to that of A with regard to general performance. The major difference is that a dual-gate MOSFET is used to permit injection of the LO energy at gate 2. Since there is considerable signal isolation between gates 1 and 2, LO pulling is minimized and antenna-LO isolation is good.

A singly balanced active mixer is illustrated at Fig. 28. Two 40673 dual-gate MOSFETs are connected in push-pull, but with the LO frequency injected in parallel at gate 2 of each device. A potentiometer is used in the sources of the transistors to permit circuit balance. This mixer offers superior performance to those shown in Fig. 27.

One of the least complicated or expensive mixers is the two-diode version (singly balanced) seen in Fig. 29A. A trifilar-wound broadband toroidal transformer is used at the mixer input. The shortcoming of this mixer over the one seen at B is that signal isolation between all three mixer ports is not possible. A better version is that a B in Fig. 29. In this case all three mixer ports are well isolated from one another. This greatly reduces the probability of spurious responses in the receiver. Conversion loss with these mixers is approximately 8 dB. The impedance of the mixer ports is approximately 50 ohms.

Improved IMD characteristics can be had from a diode-ring mixer, by placing a diplexer after the mixer as seen in Fig. 30. The diplexer consists of a

high-pass network (L1) and a low-pass one (L2). L2 is tuned to the i-f and serves as a matching network between 50 ohms and  $R_L$ , the FET gate resistor. L1 and the associated series capacitors are tuned to three times the i-f and terminated in 50 ohms. This gives the mixer a proper resistive termination without degrading the 9-MHz i-f. The high-pass network has a loaded Q of 1.

### IC Mixers

Although there are numerous ICs available for use as mixers, only two are shown here. Fig. 31 shows a CA3028A singly balanced active mixer. The diagram at B shows the inner workings of the IC. Conversion gain is on the order of 15 dB.

Fig. 32A illustrates a doubly balanced IC active mixer which employs an MC1496G. A schematic diagram of the IC is shown at B. The performance of this mixer is excellent, but it is not as strong a mixer as that of Fig. 29. However, it has good conversion gain and a fairly low noise figure.

### I-F Amplifiers

The amount of i-f amplification used in a receiver will depend upon how much signal level is available at the input to the i-f strip. Sufficient gain is needed to ensure ample audio output consistent with driving headphones or a speaker. Another consideration is the amount of agc-initiated i-f gain range. The more i-f stages used (a maximum of two is typical) the greater the gain change caused by agc action. The range is on the order of 80 dB when two CA3028A ICs are used in the i-f strip. A pair of MC1590G ICs will provide up to 120 dB of gain variation with agc applied.

Nearly all modern receiver circuits utilize ICs as i-f amplifiers. Numerous types of ICs are available to provide linear rf and i-f amplification at low cost. The CA3028A and MC1590G ICs are the most popular ones for amateur work because they are easy to obtain and are relatively low in cost. With careful layout techniques either device will operate in a stable manner. Bypassing should be done as near to the IC pins as possible. Input and output circuit elements must be separated to prevent mutual coupling which can cause unstable operation. If IC sockets are used they should be the low-profile variety with short socket conductors.

Fig. 33 contains examples of bipolar transistor and FET i-f amplifiers. Typical component values are given. A CA3028A IC, connected for differential-amplifier operation, is shown in Fig. 34 as an i-f amplifier. Up to 40 dB of gain is possible with this circuit. The IC is useful up to 120 MHz and has a low noise figure.

A Motorola MC1590G IC will provide up to 50 dB of stage gain when used as an

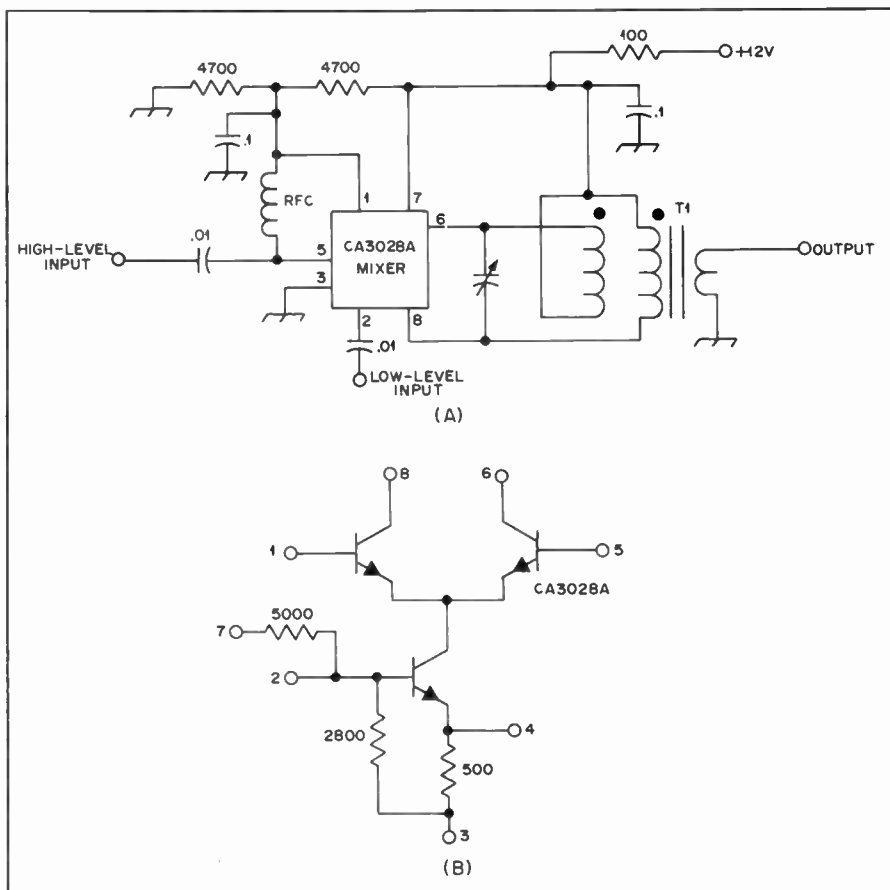


Fig. 31 — CA3028A singly balanced mixer. The circuit for the IC is given at B.

i-f amplifier. An example of the circuit is given in Fig. 35. Agc operates in the reverse of that which is applied to a CA3028A. With the latter the gain will be maximum with maximum agc voltage. An MC1590G delivers maximum gain at the low agc voltage level.

With both amplifiers (Figs. 34 and 35) the input impedance is on the order of 1000 ohms. The output impedance is close to 4000 ohms. These values are for single-ended operation, as shown. The values are doubled when either device is operated in push-pull with respect to input and output tuned circuits.

### Choice of Frequency

The selection of an intermediate frequency is a compromise between conflicting factors. The lower the i-f, the higher the selectivity and gain, but a low i-f brings the image nearer the desired signal and hence decreases the image ratio. A low i-f also increases pulling of the oscillator frequency. On the other hand, a high i-f is beneficial to both image ratio and pulling, but the gain is lowered and selectivity is harder to obtain by simple means.

An i-f of the order of 455 kHz gives good selectivity and is satisfactory from the standpoint of image ratio and oscillator pulling at frequencies up to 7 MHz. The image ratio is poor at 14 MHz

when the mixer is connected to the antenna, but adequate when there is a tuned rf amplifier between antenna and mixer. At 28 MHz and on the very high frequencies, the image ratio is very poor unless several rf stages are used. Above 14 MHz, pulling is likely to be bad without very loose coupling between mixer and oscillator. Tuned-circuit shielding also helps.

With an i-f of about 1600 kHz, satisfactory image ratios can be secured on 14, 21 and 28 MHz with one rf stage of good design. For frequencies of 28 MHz and higher, a common solution is to use double conversion, choosing one high i-f for image reduction (9 MHz is frequently used) and a lower one for gain and selectivity. A popular i-f at present is 3.3 to 3.4 MHz, which is used by some commercial designers as the last i-f in double-conversion receivers.

In choosing an i-f it is wise to avoid frequencies on which there is considerable activity by the various radio services, since such signals may be picked up directly by the i-f wiring. Shifting the i-f or better shielding are the solutions to this interference problem.

### Fidelity; Sideband Cutting

Amplitude modulation of a carrier generates sideband frequencies numerically equal to the carrier frequency plus and

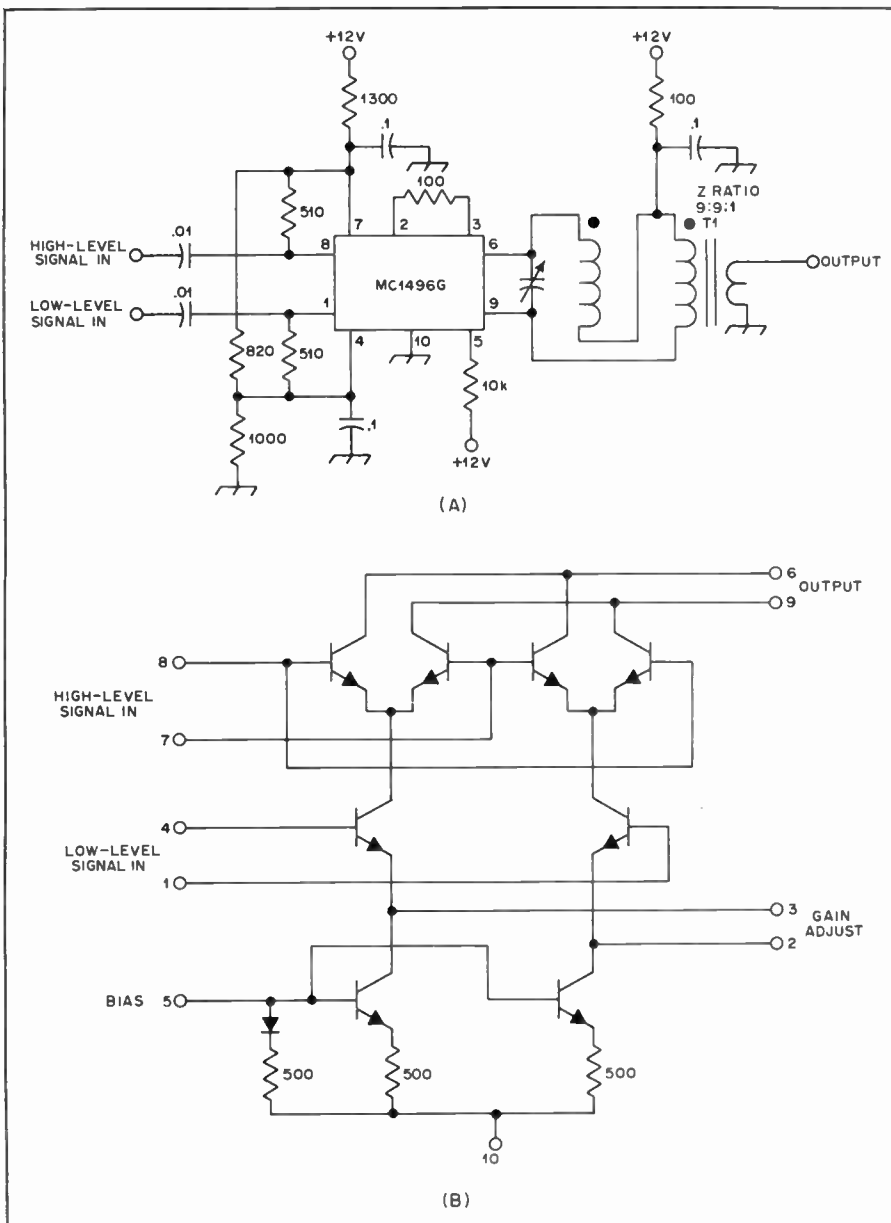


Fig. 32 — MC1496G doubly balanced mixer and circuit of the IC.

minus the modulation frequencies present. If the receiver is to give a faithful reproduction of modulation that contains, for instance, audio frequencies up to 5000 Hz, it must at least be capable of amplifying equally all frequencies contained in a band extending from 5000 Hz above or below the carrier frequency. In a superheterodyne, where all carrier frequencies are changed to the fixed intermediate frequency, the i-f amplification must be uniform over a band 5-kHz wide, when the carrier is set at one edge. If the carrier is set in the center, a 10-kHz band is required. The signal-frequency circuits usually do not have enough overall selectivity to affect materially the "adjacent-channel" selectivity, so that only the i-f amplifier selectivity need be considered.

If the selectivity is too great to permit uniform amplification over the band of frequencies occupied by the modulated signal, some of the sidebands are "cut." While sideband cutting reduces fidelity, it is frequently preferable to sacrifice reproduction naturalness in favor of communications effectiveness.

The selectivity of an i-f amplifier, and hence, the tendency to cut sidebands, increases with the number of tuned circuits and also is greater with the lower the intermediate frequency. From the communication standpoint, sideband cutting is never serious with two-stage amplifiers at frequencies as low as 455 kHz. A two-stage i-f amplifier at 85 or 100 kHz will be sharp enough to cut some of the higher-frequency sidebands if good transformers are used. However, the cutting is not at all serious, and the gain in selectivity is worthwhile in crowded amateur bands as an aid to QRM reduction.

### I-F Selectivity

The most significant selectivity in a receiver is that which separates signals

Table 1

Part & Type Numbers	Min. 3 dB BW @ 25°C (kHz)	Min. 4 dB BW OTR (kHz)	Max. 60 dB BW @ 25°C (kHz)	Max. 60 dB BW OTR (kHz)	Max. RV @ 25°C (dB)	Max. RV OTR (dB)	Max. IL @ 25°C (dB)	Max. IL COTR (dB)	Min. 60 dB SBR (kHz)	S&L —5% (ohms)	Res. Cap. +5% (pF)
526-9689-010 F455FD-04	0.375	0.375	3.5	4.0	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	350
526-9690-010 F455FD-12	1.2	1.2	8.7	9.5	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	350
526-9691-010 F455FD-19	1.9	1.9	5.4	5.9	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	330
526-9692-010 F455FD-25	2.5	2.5	6.5	7.0	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	510
526-9693-010 F455FD-29	2.9	2.9	7.0	8.0	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	510
526-9694-010 F455FD-38	3.8	3.8	9.0	10.0	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	1000
526-9695-010 F455FD-58	5.8	5.8	14.0	15.0	3.0	4.0	10.0	12.0	445-F60L F60H-465	2000	1100

OTR = Operating Temperature Range, RV = Ripple Voltage, IL = Insertion Loss, SBR = Stop Band Range, S & L = Source and Load

Courtesy of Collins Radio Co.

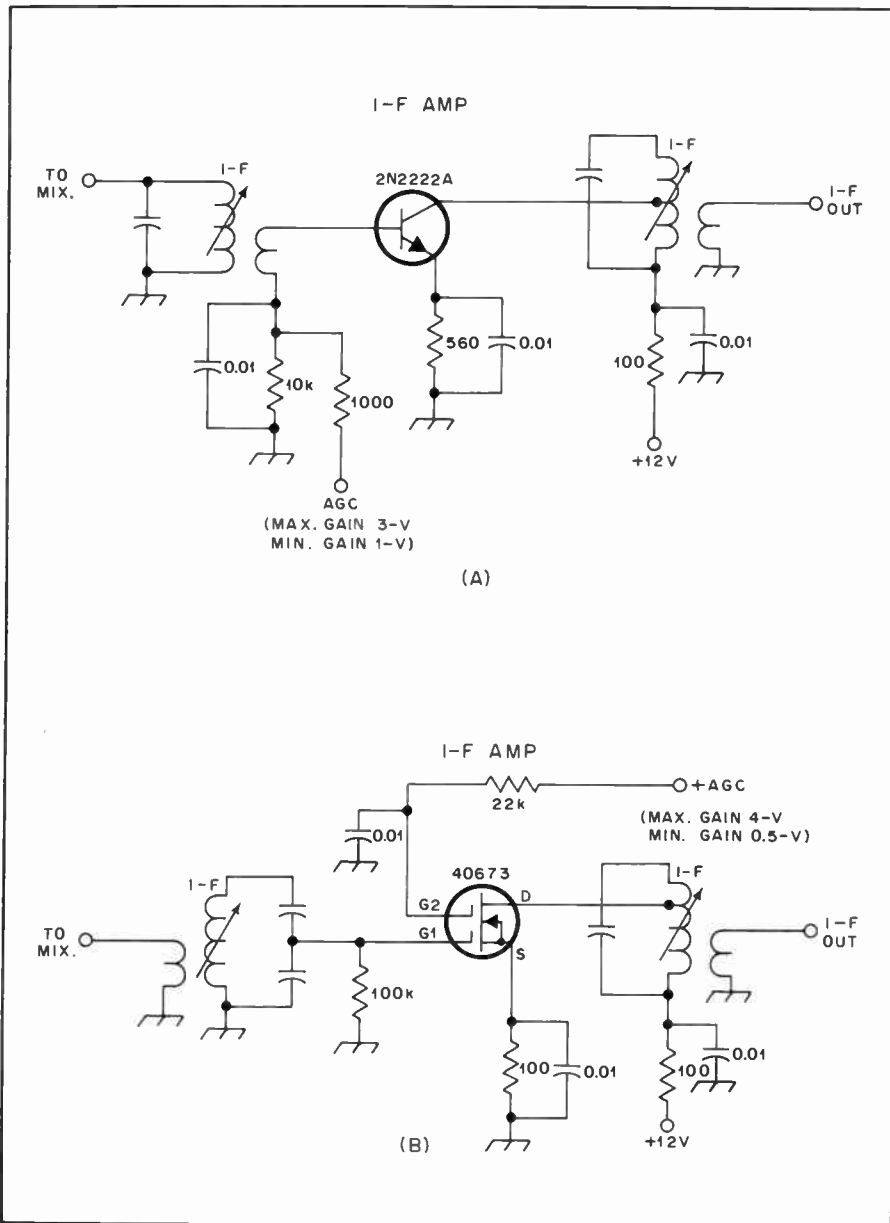


Fig. 33 — Methods for applying agc to a bipolar i-f amplifier (A) and a dual-gate MOSFET i-f stage (B).

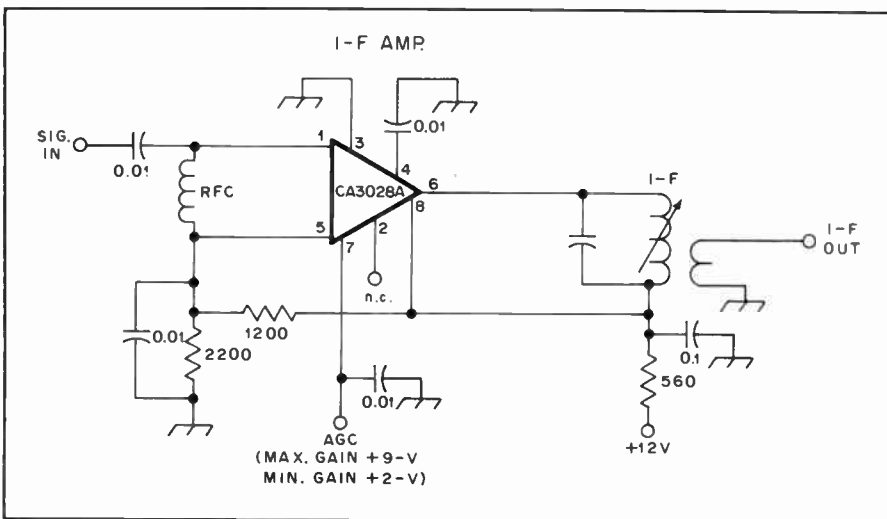


Fig. 34 — An IC type of i-f amplifier with agc applied.

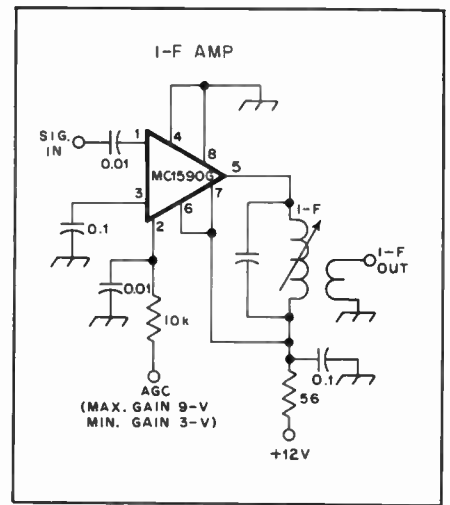


Fig. 35 — Agc is applied to an MC1590G IC.

and reduces QRM, assuming that selectivity in other parts of a receiver is ignored but correct. Narrow-response filters are used after the last mixer or post-mixer amplifier to establish the overall selectivity of a receiver. Most receivers which use a second i-f of 455 kHz contain mechanical filters. Table 1 lists various mechanical filters which are manufactured by Collins Radio Co.

At intermediate frequencies above 500 kHz it is common practice to use crystal filters. These can be designed with just one crystal (Fig. 36A), or with two or more crystals. Fig. 36B illustrates a two-crystal, half-lattice filter and a cascaded half-lattice filter is shown at C of Fig. 36.

The single-crystal example shown at A of Fig. 36 is best stated for simple receivers intended mainly for cw use. C1 is adjusted to provide the bandpass characteristic shown adjacent to the circuit. When the BFO frequency is placed on the part of the low-frequency slope (left) which gives the desired beat note respective to  $f_o$  (approximately 700 Hz), single-signal reception will result. To the right of  $f_o$  in Fig. 36A the response drops sharply to reduce output on the unwanted side of zero beat, thereby making single-signal reception possible. If no i-f filter was used, or if the BFO frequency fell at  $f_o$ , nearly equal response would exist either side of zero beat (double-signal response) as is the case with direct-conversion receivers. QRM on the unwanted-response side of the i-f passband would interfere with reception. The single-crystal filter shown is capable of at least 30 dB of rejection on the high-frequency side of zero beat. The filter termination  $R_T$  has a marked effect on the response curve. It is necessary to experiment with the resistance value until the desired response is obtained. Values can range from 1500 to 10,000 ohms.

A half-lattice filter is shown at B in Fig. 36. The response curve is symmetrical and there is a slight dip at center frequency. The dip is minimized by proper selection



**Table 2**

Application	SSB Tran.	SSB Rec.	CW or Digital Data	A-M	A-M	CW	FM
Filter type	XF-9A	XF-9B	XF-9NB	XF-9C	XF-9D	XF-9M	XF-9E
No. of crystals	5	8	8	8	8	4	8
6-dB bandwidth	2.5 kHz	2.4 kHz	0.5 kHz	3.75 kHz	5.0 kHz	0.5 kHz	12 kHz
Passband ripple	<1 dB	<2 dB	<0.5 dB	<2 dB	<2 dB	<1 dB	<2 dB
Insertion loss	<3 dB	<3.5 dB	<6.5 dB	<3.5 dB	<3.5 dB	<5 dB	<3 dB
Term. impedance	500Ω	500Ω	500Ω	500Ω	500Ω	500Ω	1200Ω
Ripple capacitors	30 pF	30 pF	30 pF	30 pF	30 pF	30 pF	30 pF
Shape factor	6:50 dB	6:60 dB	6:60 dB	6:60 dB	6:60 dB	6:60 dB	6:60 dB
Stop-band atten.	>45 dB	>100 dB	>90 dB	>100 dB	>100 dB	>90 dB	>90 dB

Courtesy of Spectrum International

of  $R_T$ .  $Y_1$  and  $Y_2$  are separated in frequency by the amount needed to obtain cw or ssb selectivity. The bandwidth at the 3-dB points will be approximately 1.5 times the crystal-frequency spacing. For upper or lower sideband reception  $Y_1$  and  $Y_2$  would be 1.5 kHz apart, yielding a 3-dB bandwidth of approximately 2.25 kHz. For cw work a crystal spacing of 0.4 kHz would result in a bandwidth of roughly 600 Hz. The skirts of the curve are fairly wide with a single half-lattice filter, which uses crystals in the hf region.

The skirts can be steepened by placing two half-lattice filters in cascade, as shown in Fig. 36C.  $R_1$  and  $R_T$  must be selected to provide minimum ripple at the center of the passband. The same rule for frequency spacing between the crystals applies.  $C_1$  is adjusted for a symmetrical response.

The circuits of Fig. 36 can be built easily and inexpensively by amateurs. The transformers shown are tuned to center frequency. They are wound bifilar or trifilar on ferrite or powdered-iron cores of appropriate frequency characteristics.

An illustration of how a mechanical filter operates is provided in Fig. 37. Perhaps the most significant feature of a mechanical filter is the high Q of the resonant metallic disks it contains. A Q figure of 10,000 is the nominal value obtained with this kind of resonator. If L and C constants were employed to acquire a bandwidth equivalent to that possible with a mechanical filter, the i-f would have to be below 50 kHz.

Mechanical filters have excellent frequency-stability characteristics. This makes it possible to fabricate them for fractional bandwidths of a few hundred hertz. Bandwidths down to 0.1 percent can be obtained with these filters. This means that a filter having a center frequency of 455 kHz could have a bandwidth as small as 45.5 Hz. By inserting a wire through the centers of several resonator disks, thereby coupling them, the fractional bandwidth can be made as great as 10 percent of the center frequency. The upper limit is governed primarily by occurrence of unwanted spurious filter responses adjacent to the desired passband.

Mechanical filters can be built for

center frequencies from 60 to 600 kHz. The main limiting factor is disk size. At the low end of the range the disks become

prohibitively large, and at the high limit of the range the disks become too small to be practical.

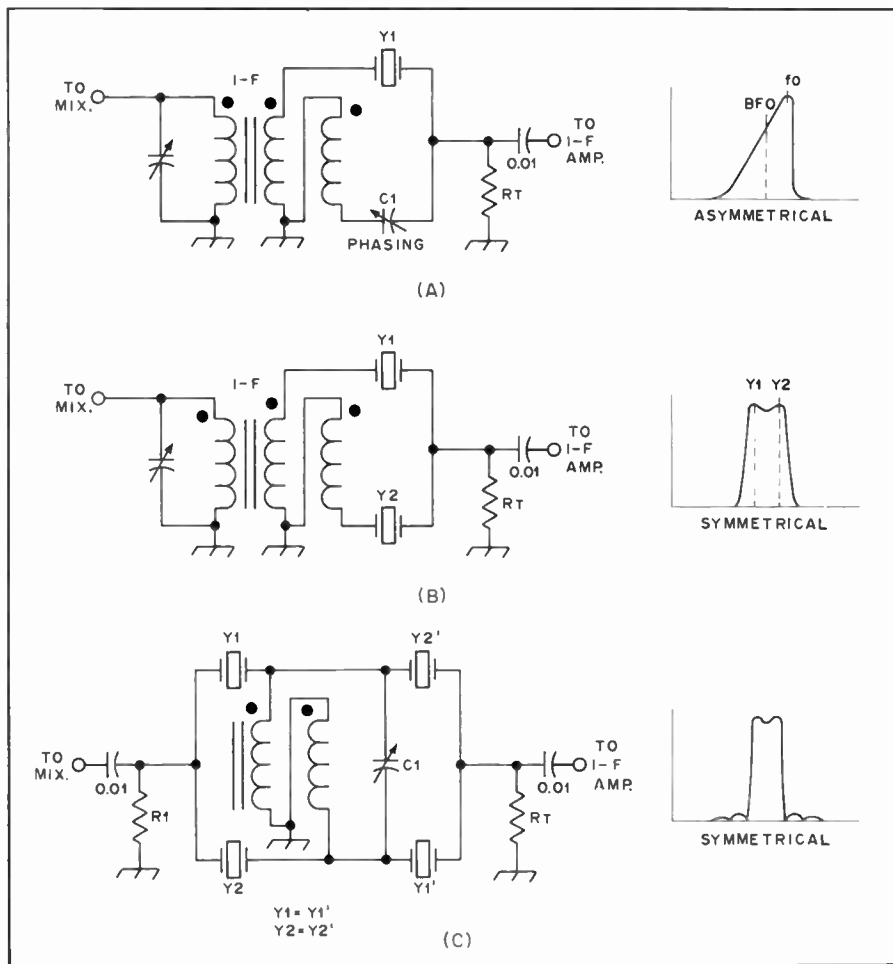


Fig. 36 — A comparison between crystal i-f filters. The selectivity is increased as crystals are added.

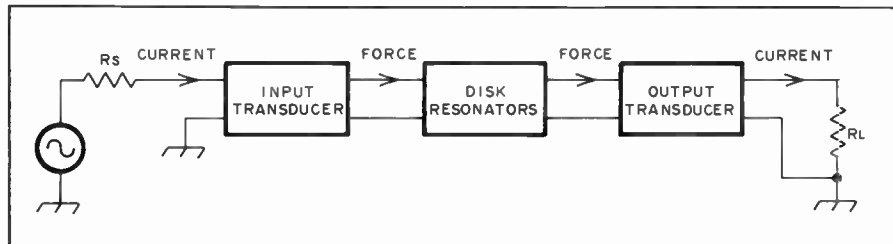


Fig. 37 — Block diagram of a mechanical filter (Collins Radio).

The principle of operation is seen in Fig. 37. As the incoming i-f signal passes through the input transducer it is converted to mechanical energy. This energy is passed through the disk resonators to filter out the undesired frequencies, then through the output transducer where the mechanical energy is converted back to the original electrical form.

The transducers serve a second function: They reflect the source and load impedances into the mechanical portion of the circuit, thereby providing a termination for the filter.

Mechanical filters require external resonating capacitors which are used across the transducers. If the filters are not resonated there will be an increase in insertion loss, plus a degradation of the passband characteristics. Concerning the latter, there will be various unwanted dips in the nose response (ripple), which can lead to undesirable effects. The exact amount of shunt capacitance will depend on the filter model used. The manufacturer's data sheet specifies the proper capacitor values.

Most bipolar transistor i-f amplifiers have an input impedance of 1000 ohms or less. There are situations where the output impedance of the stage preceding the filter is similarly low. In circuits of this variety it is best to use series-resonating capacitors in preference to parallel ones. Stray circuit capacitance, including the input and output capacitances of the stages before and after the filter, should be subtracted from the value specified by the manufacturer.

Collins mechanical filters are available with center frequencies from 64 to 500 kHz and in a variety of bandwidths. Insertion loss ranges from 2 dB to as much as 12 dB, depending on the style of filter used. Of greatest interest to amateurs are the 455-kHz mechanical filters specified as F455. They are available in bandwidths of 375 Hz, 1.2 kHz, 1.9 kHz, 2.5 kHz, 2.9 kHz, 3.8 kHz and 5.8 kHz. Maximum insertion loss is 10 dB, and the characteristic impedance is 2000 ohms. Different values of resonating capacitance are required for the various models, spreading from 350 to 1100 pF. Although some mechanical filters are terminated internally, this series requires external source and load termination of 2000 ohms. The F455 filters are the least expensive of the Collins line.

Most modern receivers have selectable i-f filters to provide suitable bandwidths for ssb and cw. Most of the commercial receivers use a 500- or 600-Hz bandwidth filter for cw and a 2.1- or 2.4-kHz bandwidth for ssb. The input and output ends of a filter should be well isolated from one another if the filter characteristics are to be realized. Leakage across a filter will negate the otherwise good performance of the unit. The problem becomes worse as the filter frequency is increased. Mechanical switches are not

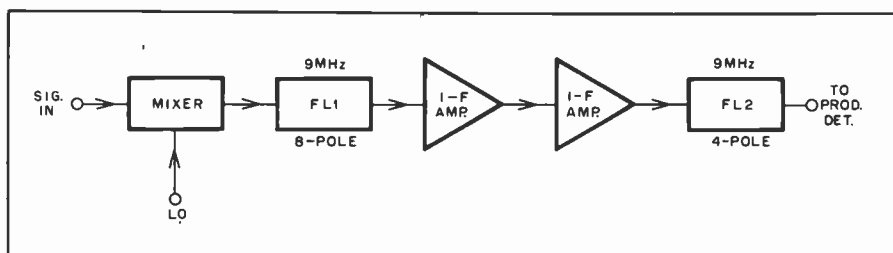


Fig. 38 — Crystal i-f filters can be used at both ends of the i-f strip. FL2 greatly reduces wideband i-f noise.

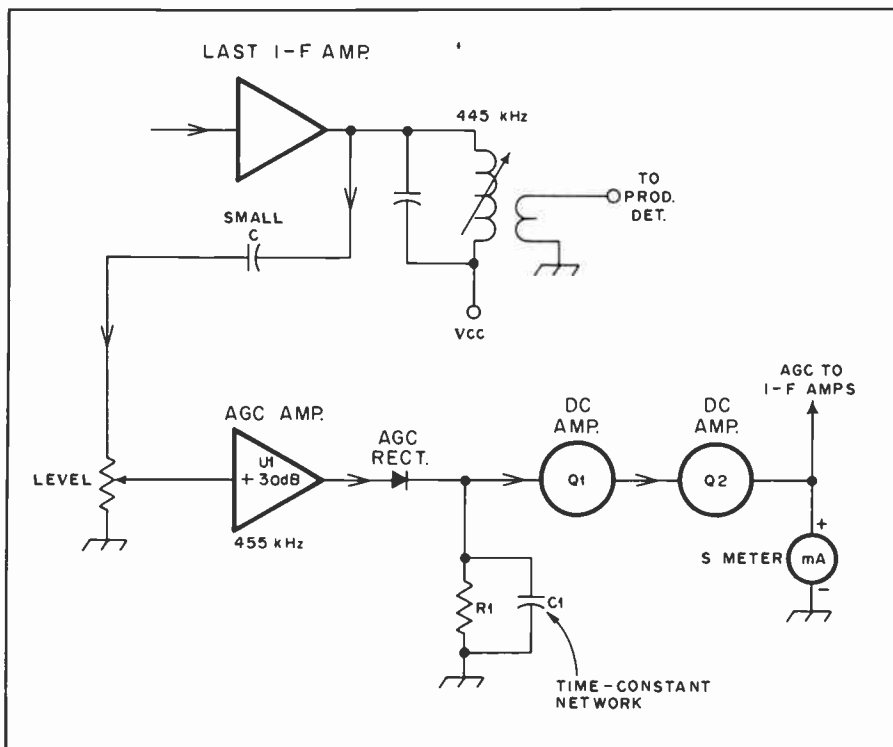


Fig. 39 — A system for developing receiver agc voltage.

recommended above 455 kHz for filter selection because of leakage across the switch wafers and sections. Diode switching is preferred by most designers. The switching diodes for the filter that is out of the circuit are usually back-biased to ensure minimum leakthrough.

In the interest of reducing wideband noise from the i-f amplifier strip it is worthwhile to use a second filter which has exactly the same center frequency as the first. The second filter is placed at the end of the i-f strip, ahead of the product detector. This is shown in Fig. 38. The technique was described by W7ZOI in March and April 1974 *QST*. The second filter, FL2, has somewhat wider skirts than the first, FL1. An RC active audio filter after the product detector has a similar effect, but the results are not quite as spectacular as when two i-f filters are used. The overall signal-to-noise ratio is greatly enhanced by this method.

#### Automatic Gain Control

Automatic regulation of the gain of the receiver in inverse proportion to the signal

strength is an operating convenience in reception, since it tends to keep the output level of the receiver constant regardless of input-signal strength. The average rectified dc voltage, developed by the received signal across a resistance in a detector circuit, is used to vary the bias on the rf and i-f amplifier stages. Since this voltage is proportional to the average amplitude of the signal, the gain is reduced as the signal strength becomes greater. The control will be more complete and the output more constant as the number of stages to which the agc bias is applied is increased. Control of at least two stages is advisable.

Various schemes from simple to extravagant have been conceived to develop agc voltage in receivers. Some perform poorly because the attack time of the circuits is wrong for cw work, resulting in "clicky" or "pumping" agc. The first significant advance toward curing the problem was presented by Goodman W1DX, "Better AVC for SSB and Code Reception," January 1957 *QST*. He coined the term, "hang" avc, and the

technique has been adopted by many amateurs who have built their own receiving equipment. The objective is to make the agc take hold as quickly as possible to avoid the ailments mentioned in the foregoing text.

For best receiver performance the i-f filters should be contained within the agc loop, which strongly suggests the use of rf-derived agc. Most commercial receivers follow this rule. However, good results can be obtained with audio-derived agc, despite the tendency toward a clicky response. If RC active audio filters are used to obtain receiver selectivity, they should be contained within the audio-agc loop if possible.

Fig. 39 illustrates the general concept of an agc circuit. Rf energy is sampled from

the output of the last i-f by means of light coupling. This minimizes loading on the tuned circuit of the i-f amplifier. The i-f energy is amplified by the agc amplifier, then converted to dc by means of an agc rectifier. R1 and C1 are selected to provide a suitable decay time constant (about 1 second for ssb and cw). Q1 and Q2 function as dc amplifiers to develop the dc voltage needed for agc control of the i-f (and sometimes, rf) amplifier stages. The developed agc voltage can be used to drive an S meter. A level control can be placed at the input of the agc amplifier to establish the signal input level (receiver front end) which turns on the agc system. Most designers prefer to have this happen when the received signal level is between 0.25 and 1  $\mu$ V. The exact

parameters are based somewhat on subjectivity.

An af-derived agc loop is shown in Fig. 40. It is suitable for use with CA3028A i-f amplifier ICs. Provision is made for manual i-f gain control. D1 functions as a gating diode to prevent the manual-control circuitry from affecting the normal agc action. This circuit was first used in a receiver described by DeMaw in June and July 1976 *QST*.

An rf-derived agc system is seen in Fig. 41. It operates on a similar principle as that of Fig. 40, except that an op-amp is used in place of the discrete bipolar dc amplifiers of Fig. 40. Current changes are sampled across the 10-k $\Omega$  FET source resistor by means of the op-amp difference amplifier. With the values of resistance given, the output dc swing of the op-amp is the desired +2 to +9 volts for controlling CA3028A i-f amplifiers. This system was also used in the DeMaw receiver.

It certainly is not essential to have agc in a receiver. If the operator is willing to adjust the gain manually, good performance is certain to result. Agc is mainly an operator convenience: It prevents loud signals from blasting out of the speaker or headphones when the operator tunes the band at a given af-gain setting.

### Beat-Frequency Oscillators

The circuits given for crystal-controlled oscillators earlier in this chapter are suitable for use in BFO circuits. A beat oscillator generates energy which is supplied to a product detector for reception of cw and ssb signals. The BFO frequency is offset by the appropriate amount with respect to the center frequency of the i-f filter. For example, a BFO used during cw reception is usually some 700 Hz above or below the i-f center frequency. During ssb reception the offset is slightly more — approximately 1.5 kHz above or below the i-f center frequency, depending upon the need for upper or lower sideband operation. Typically, the BFO is placed roughly 20 dB down on the slope of the i-f passband curve for ssb reception or transmission.

A BFO need not be crystal controlled. It can use a VFO type of circuit, or it can be tuned by means of a Varactor diode (see chapter 4 for a discussion of semiconductor theory). Elimination of the crystals represents a cost savings to the builder, but frequency stability may not be as good as when crystal control is employed.

When the BFO is operated at frequencies above 3 MHz it is helpful to use a buffer stage after the oscillator to minimize the effects of pulling. Furthermore, if a passive product detector is used in the receiver, a substantial amount of BFO output power will be required — approximately +7 dBm. The buffer/ampli-

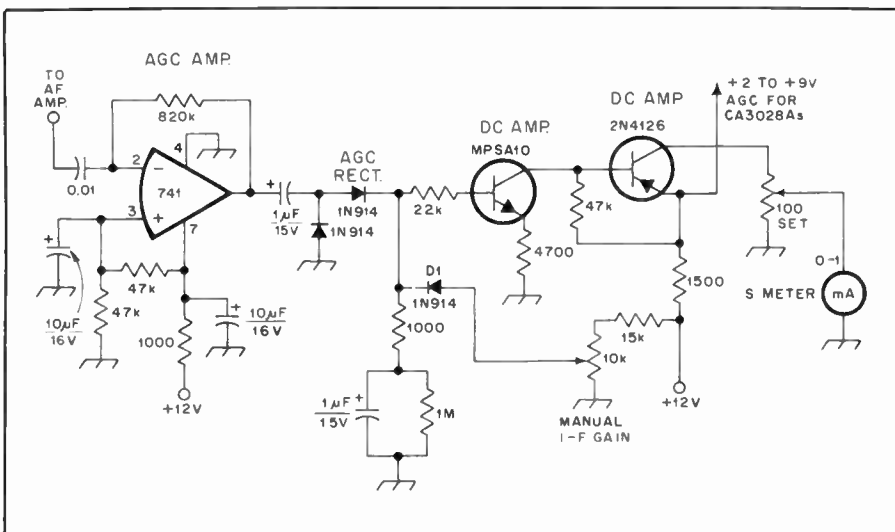


Fig. 40 — A practical circuit for developing agc voltage for a CA3028A i-f amplifier.

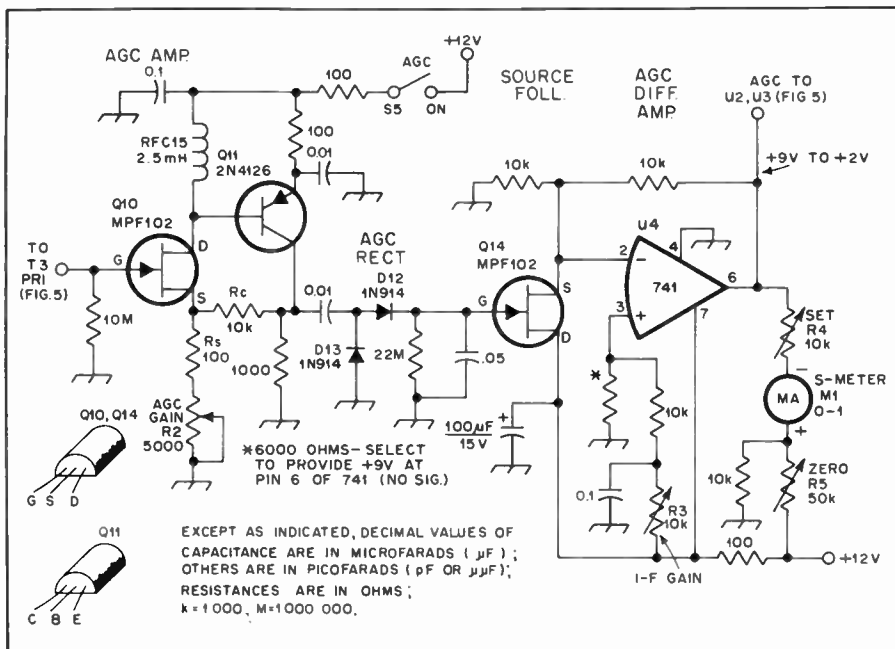


Fig. 41 — An agc system for CA3028A i-f amplifiers. An op-amp is used as difference amplifier to provide agc voltage while operating an S meter.

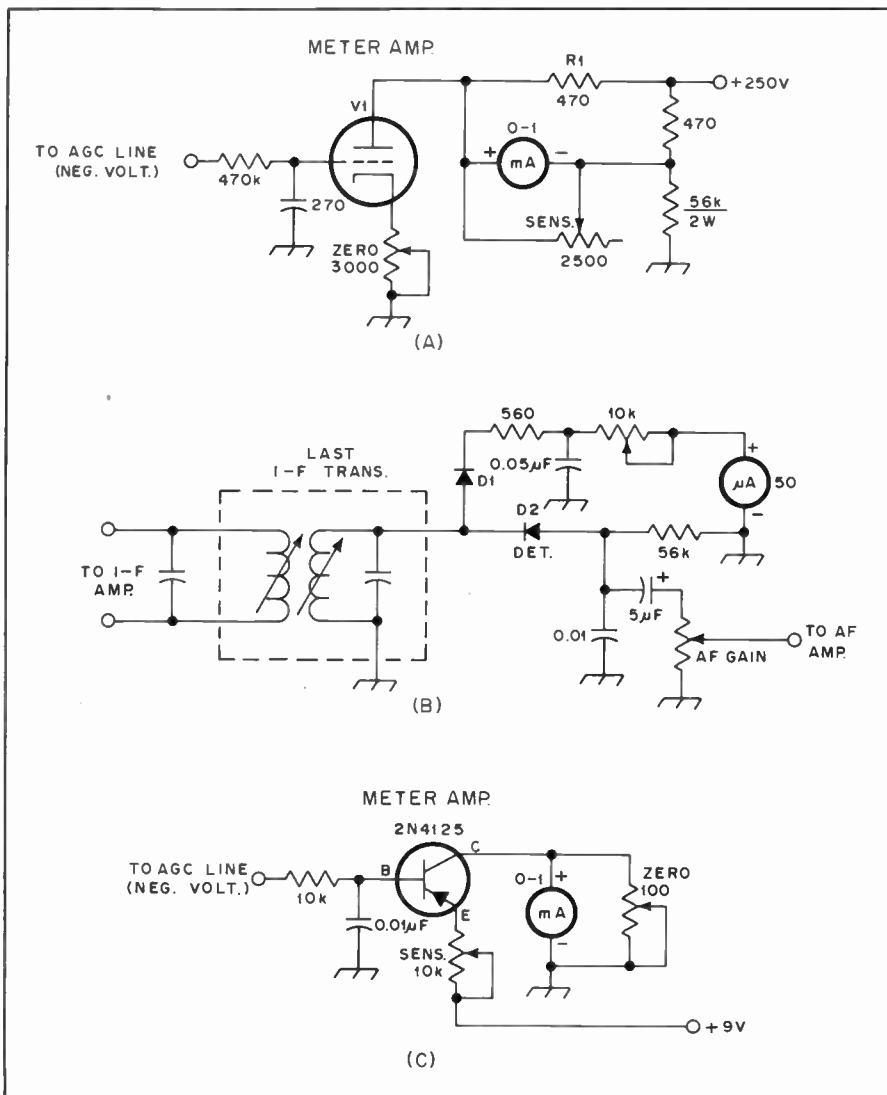


Fig. 42 — Various methods for using an S meter. At A, V1 is a meter amplifier. As the agc voltage increases the plate current decreases to lower the voltage drop across R1. An up-scale meter reading results as the current through the meter increases. At B, the i-f energy is rectified by means of D1 to deflect the meter. A 10-k $\Omega$  control sets the meter sensitivity. At C, the negative agc voltage forward biases the transistor to cause an increase in collector current, thereby deflecting the meter upwards with signal increases.

fier helps to boost the oscillator output to satisfy the requirement.

### S Meters

Signal-strength meters are useful when there is a need to make comparative readings. Such might be the case when another operator asks for a comparison between two antennas he is testing. Because S meters are relative-reading instruments, signal reporting based on the amount of needle deflection is generally without meaning. No two receivers render the same reading for a given signal, unless by coincidence. This is because the gain distribution within an amateur receiver varies from band to band. Since most S meters are activated from the agc line in a receiver, what might be S9 on one ham band could easily become S6 or 10 dB over S9 on another band. A receiver that

rendered accurate readings on each band it covered would be extremely esoteric and complex.

An attempt was made by at least one receiver manufacturer in the early 1940s to establish some significant numbers for S meters. S9 was to be equivalent to 50 V, and each S unit would have been equal to 6 dB. The scale readings above S9 were given in dB. The system never took hold in the manufacturing world, probably for the reasons given earlier in this section.

In addition to the example shown in Fig. 41, some typical S-meter circuits are offered in Fig. 42. The example at C can be used with rf- or audio-derived agc.

### Noise Reduction

In addition to active-device and circuit noise, much of the noise interference

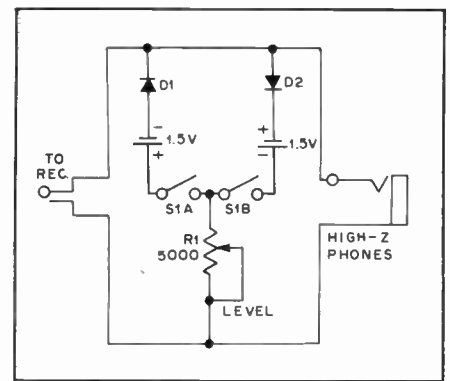


Fig. 43 — A simple audio limiter/clipper. R1 sets the bias on the diodes for the desired limiting level.

experienced in reception of high-frequency signals is caused by domestic or industrial electrical equipment and by automobile ignition systems. The interference is of two types in its effects. The first is the "hiss" type, consisting of overlapping pulses similar in nature to the receiver noise. It is largely reduced by high selectivity in the receiver, especially for code reception. The second is the "pistol-shot" or "machine-gun" type, consisting of separated impulses of high amplitude. The hiss type of interference usually is caused by commutator sparking in dc and series-wound ac motors, while the shot type results from separated spark discharges (ac power leaks, switch and key clicks, ignition sparks, and the like).

The only known approach to reducing tube, transistor and circuit noise is through the choice of low-noise, front-end, active components and through more overall selectivity.

### Impulse Noise

Impulse noise, because of the short duration of the pulses compared with the time between them, must have high amplitude to contain much average energy. Hence, noise of this type strong enough to cause much interference generally has an instantaneous amplitude much higher than that of the signal being received. The general principle of devices intended to reduce such noise is to allow the desired signal to pass through the receiver unaffected, but to make the receiver inoperative for amplitudes greater than that of the signal. The greater the amplitude of the pulse compared with its time of duration, the more successful the noise reduction.

Another approach is to "silence" (render inoperative) the receiver during the short duration time of any individual pulse. The listener will not hear the "hole" because of its short duration, and very effective noise reduction is obtained. Such devices are called "blankers" rather than "limiters."

In passing through selective receiver



circuits, the time duration of the impulses is increased, because of the bandwidth of the circuits. Thus, the more selectivity ahead of the noise-reducing device, the more difficult it becomes to secure good pulse-type noise suppression.

### Audio Limiting

A considerable degree of noise reduction in code reception can be accomplished by amplitude-limiting arrangements applied to the audio-output circuit of a receiver. Such limiters also maintain the signal output nearly constant during fading. These output-limiter systems are simple, and they are readily adaptable to most receivers without any modification of the receiver itself. However, they cannot prevent noise peaks from overloading previous stages.

### Noise-Limiter Circuits

Pulse-type noise can be eliminated to an extent which makes the reception of even the weakest of signals possible. The noise pulses can be clipped, or limited in amplitude, at either an rf or af point in the receiver circuit. Both methods are used by receiver manufacturers; both are effective.

A simple audio noise limiter is shown at Fig. 43. It can be plugged into the headphone jack of the receiver and a pair of headphones connected to the output of the limiter. D1 and D2 are wired to clip both the positive and negative peaks of the audio signal, thus removing the high spikes of pulse noise. The diodes are back-biased by 1.5-volt batteries permitting R1 to serve as a clipping-level control. This circuit also limits the amount of audio reaching the headphones. When tuning across the band, strong signals will not be ear-shattering and will appear to be the same strength as the weaker ones. S1 is open when the circuit is not in use to prevent battery drain. D1 and D2 can be germanium or silicon diodes, but 1N34As or 1N914s are generally used. This circuit is usable only with high-impedance headphones.

The usual practice in communications receivers is to use low-level limiting, Fig. 44. The limiting can be carried out at rf or af points in the receiver, as shown. Limiting at rf does not cause poor audio quality as is sometimes experienced when using series or shunt af limiters. The latter limits the normal af signal peaks as well as the noise pulses, giving an unpleasant audio quality to strong signals.

In a series-limiting circuit, a normally conducting element (or elements) is connected in the circuit in series and operated in such a manner that it becomes nonconductive above a given signal level. In a shunt limiting circuit, a non-conducting element is connected in shunt across the circuit and operated so that it becomes conductive above a given signal level, thus short-circuiting the signal and

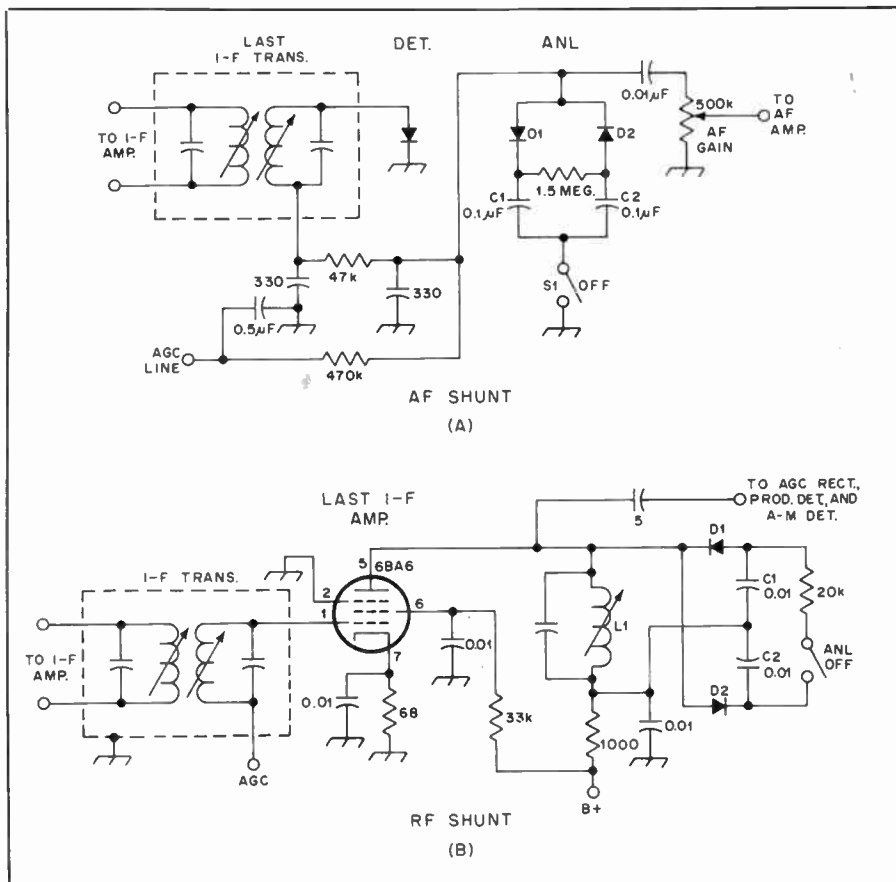


Fig. 44 — Examples of rf and audio anl circuits. Positive and negative clipping takes place in both circuits. The circuit at A is self-adjusting.

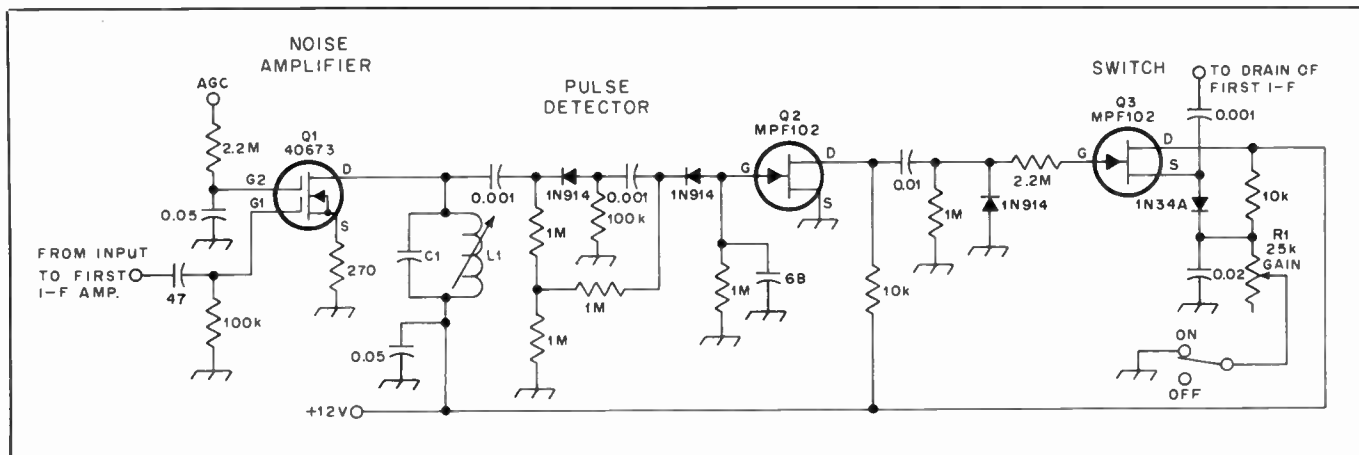


Fig 45 — Diagram of a noise blanker. C1 and L1 are tuned to the receiver i-f.

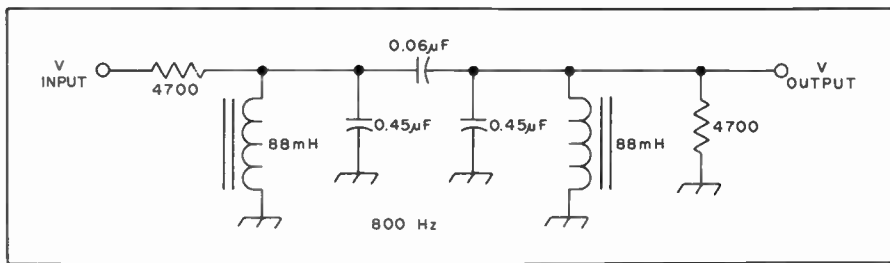


Fig. 46 — An LC bandpass filter for cw reception.

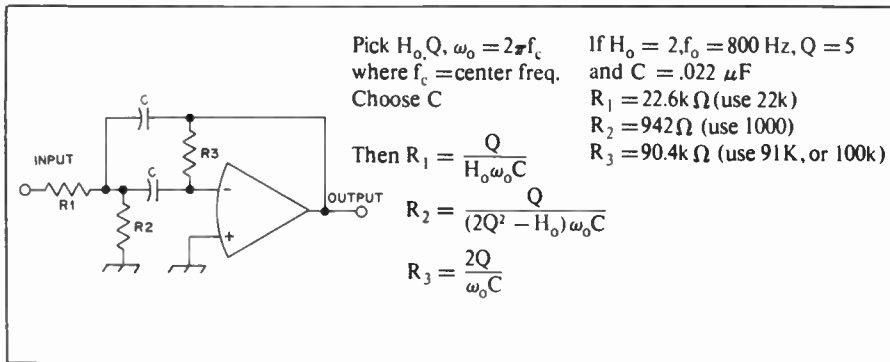


Fig. 47 — Equations for designing an RC active audio filter.

preventing its being transmitted to the remainder of the amplifier. The usual conducting element will be a forward-biased diode, and the usual nonconducting element will be a back-biased diode. In many applications the value of bias is set manually by the operator; usually the clipping level will be set at about 1 to 10 volts.

The af shunt limiter at A, and the rf shunt limiter at B operate in the same manner. A pair of self-biased diodes are connected across the af line at A, and across an rf inductor at B. When a steady cw signal is present the diodes barely conduct, but when a noise pulse rides in on the incoming signal, it is heavily clipped because capacitors C1 and C2 tend to hold the diode bias constant for the duration of the noise pulse. For this reason the diodes conduct heavily in the presence of noise and maintain a fairly constant signal output level. Considerable clipping of cw signal peaks occurs with this type of limiter, but no apparent deterioration of the signal quality results. L1 at C is tuned to the i-f of the receiver. An i-f transformer with a conventional secondary winding could be used in place

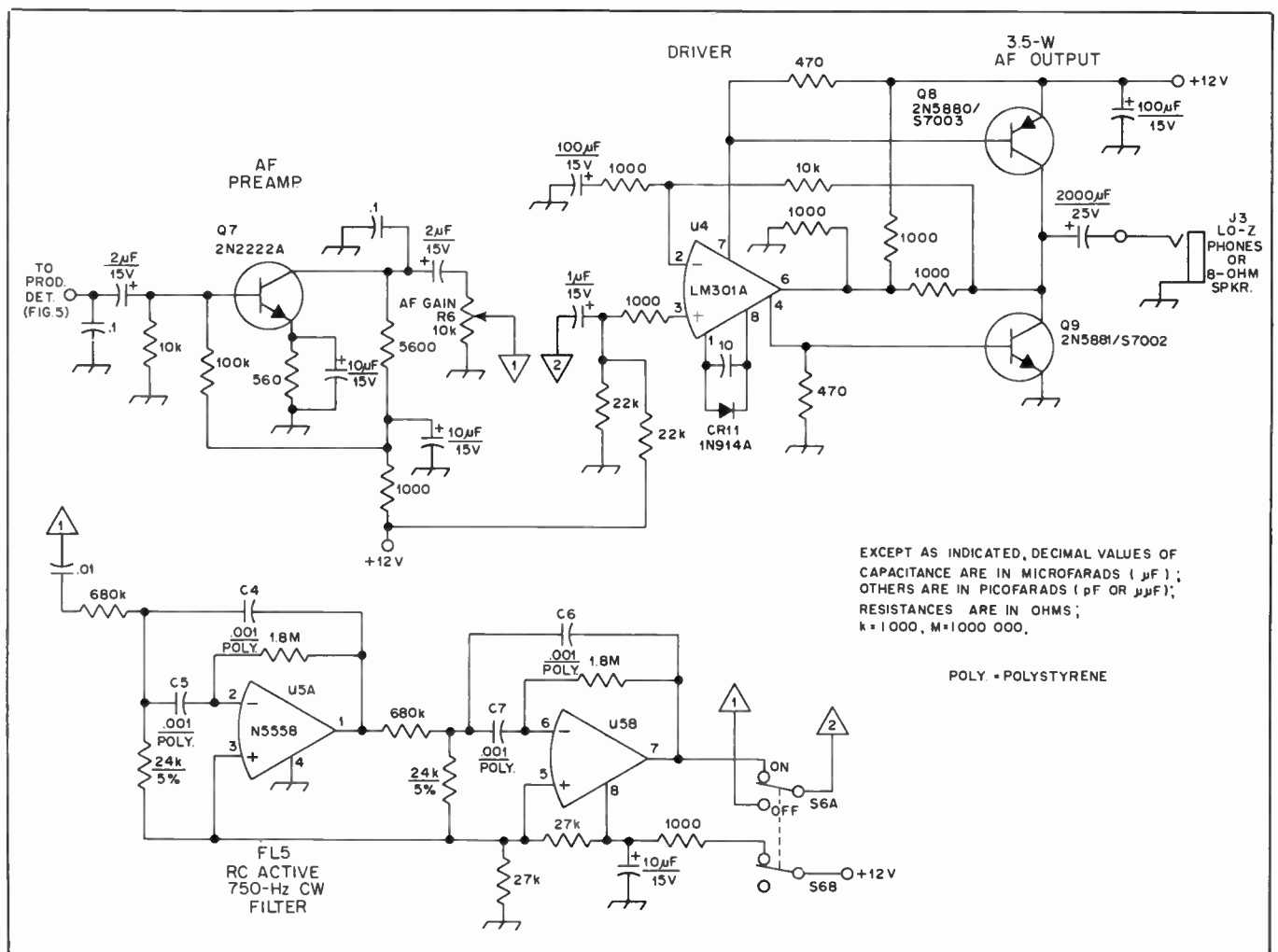


Fig. 48 — Practical circuit for a two-pole cw RC active filter, showing how it can be switched into and out of the audio channel of a receiver.

of L1, the clipper circuit being connected to the secondary winding; the plate of the 6BA6 would connect to the primary winding in the usual fashion.

### I-F Noise Silencer

The i-f noise silencer circuit shown in Fig. 45 is designed to be used ahead of the high-selectivity section of the receiver. Noise pulses are amplified and rectified, and the resulting negative-going dc pulses are used to cut off an amplifier stage during the pulse. A manual "threshold" control is set by the operator to a level that only permits rectification of the noise pulses that rise above the peak amplitude of the desired signal. The clamp transistor, Q3, short circuits the positive-going pulse "overshoots." Running the 40673 controlled i-f amplifier at zero gate 2 voltage allows the direct application of agc voltage. See July 1971 *QST* for additional details.

### Selective Audio Filters

Adding selective audio filters often improves reception. Passive types of filters made from high-Q audio inductors such as surplus telephone toroids of the 44- or 88-mH type are sometimes used. The usual configuration is that of a band-pass

filter. Several poles can be used, but the more selective the passive filter, the more prone it becomes to "ringing." This produces an annoying sound during reception.

Most modern receivers employ RC active audio filters designed around one or more op amps. These filters do not introduce an insertion loss. Rather, they are set for unity gain or slightly more than unity. They can be made adjustable in the interest of various degrees of audio skirt selectivity.

An audio filter is exceptionally beneficial in reducing wide-band receiver noise (hiss), heterodynes and low-frequency rumble. Even though the receiver may contain a narrowband i-f filter, the benefits of an audio filter are worthwhile. This is particularly significant when it is necessary to pull weak cw signals up out of the noise during vhf and uhf DX work. Some audio filters of the active variety are fairly elaborate, providing variable Q, variable peak frequency, plus band-pass, low-pass or notch characteristics. All of these features can be controlled from the front panel of the filter box.

Fig. 45 illustrates a passive LC audio filter suitable for cw reception. It is a

Butterworth type of filter which has a peak frequency of 800 Hz and a 3-dB bandwidth of 150 Hz. The filter must be terminated in its characteristic impedance to ensure the proper passband. In the example given the termination is 4700 ohms.

Design data are given in Fig. 47 for one pole of RC active bandpass filtering. A 741 or LM301 op amp is suitable. When two or more poles are used in cascade to increase the filter selectivity, a dual or quad op amp can be used. Typically, a maximum of four poles are used. The term  $H_0$  is the desired filter voltage gain. Normally it is set at unity, but gains as great as 2 are not uncommon. It is imperative that high-Q capacitors be used in this type of filter: Polystyrene capacitors are recommended. The capacitors must be matched in value as closely as possible and the resistors should be five-percent tolerance types or better.

An example of a practical RC active filter is seen in Fig. 48. It contains two poles and is designed for cw reception. It should be used in the low-level portion of the audio circuit, as shown. S1 is used to switch the filter out of the circuit during ssb reception.

## A Simple Receiver for Beginners

Good results are obtainable with the basic direct-conversion receiver presented here. The circuit is without frills, making it easy to construct and operate. Information is given for operation on 80 or 40 meters, with only four transistors, one IC and three diodes. No attempt has been made to provide cw selectivity, but reception of cw and ssb signals is entirely adequate for this first effort at receiver building.

The circuit of Fig. 50 is designed for headphone output. The overall receiver sensitivity is suitable for comfortable reception of even the weaker signals when a resonant antenna is used. The front-end filter, L1/L2/C1/C2/C3, is designed to work into a 50-ohm antenna. This network is fixed tuned, so it does not have to be adjusted across the tuning range once it has been preset for midrange in the coverage of the main-tuning dial. If a 50-ohm antenna is not available, the user can install a small antenna-matching circuit between the receiver and the antenna system (a small Transmatch) to provide the proper termination for FL1. A rough approximation of the proper settings for the tuner can be found by



Fig. 49 — Front view of the beginners receiver. The panels are made from double-sided pc board material.

**Table 3**

Band	L1, L2 ( $\mu$ H)	C1 (pF)	C2 (pF)	C3 (pF)	C4 (pF)	C5 (pF)	C6 (pF)	C7, C8 (pF)
40 M	2 20 ts. no. 20 enam. on T68-6 toroid core. Use 2- turn link on L1.	5	240 nom. Arco 427	198 nom. Arco 427	42 s.m.	10 max.	200 poly. or s.m.	560 poly. or s.m.
80 M	8.7 40 ts. no. 24 enam. on T68-6 toroid core. Use 2- turn link on L1.	7	184 nom. Arco 427	116 nom. Arco 427	68 s.m.	15 max.	300 poly. or s.m.	950 poly. or s.m.

Component data for the direct-conversion receiver. S.M. = silver mica. Poly. = polystyrene. L3 nom. inductance for 40 meters = 4.5  $\mu$ H (J. W. Miller 42A476CBI or equivalent). L3 for 80 meters has nom. inductance of 9.6  $\mu$ H (J. W. Miller 42A105CBI or equivalent). T1 consists of 15 bifilar turns of no. 24 enam. wire on an Amidon FT-50-43 toroid core. Twist wires 6 times per inch before winding. C2 and C3 are miniature mica compression trimmers.

adjusting for maximum sensitivity while listening to a weak signal. A better method is to adjust the matching network by means of a transmitter and SWR indicator. Then the receiver can be connected in place of the transmitter and FL1 adjusted as outlined later.

Q1 of Fig. 50 operates as a fed-back broadband amplifier. Output from Q1 is routed to the product detector (Q2) through T1, driving the source of Q2. VFO injection is on the detector gate. Q3 is the audio preamplifier. It is direct coupled to the drain of the product detector. An additional 40 dB of audio

gain is provided by U1, an operational-amplifier IC. A 330-ohm resistor is in series with the headphone line to permit the use of 8- and 16-ohm phones. Without the resistor the IC tends to self-oscillate at audio frequencies. The resistor is not required when the headphones have an impedance of 600 ohms or greater.

A protection diode, D2, is included to prevent accidental damage to the receiver if the power supply is attached with the wrong polarity. Positive voltage will pass through the diode, but negative voltage will be blocked.

The VFO uses only one transistor.


Voltage to the drain of the FET, Q4, is regulated at 9.1 volts by means of a Zener diode, D2. D1 helps to stabilize the oscillator by limiting the positive swing of the sine wave during oscillation. Table 3 contains the correct values for the VFO parts, respective of the operating band, which do not have specified values on the schematic diagram of Fig. 50.

**Construction**

The receiver is built from pieces of double-sided pc board, except for the etched-circuit board which is *single* sided. The overall layout is larger than need be,

Fig. 50 — Schematic diagram of the direct-conversion receiver. Capacitors are disk ceramic unless noted otherwise. Polarized capacitors are electrolytic. Resistors are 1/4- or 1/2-watt composition. Numbered components which do not have assigned values are so designated for layout purposes. Others appear in Table 3. FT indicates feedthrough type.

- C2, C3 — Mica compression trimmer, Arco 427 or equiv.
- C5 — Miniature air variable, Hammarlund HF-15 or similar for 80-meter version. HF-10 or similar for 40-meter version.
- D1 — Silicon switching diode, 1N914 or equiv.
- D2 — Zener diode, 9.1-V, 400 mW or 1 watt.
- D3 — Silicon rectifier diode, 50 PRV, 1 A suitable.
- J1 — SO-239.
- J2 — Two-circuit phone jack.
- J3 — Single-hole mount phono jack.
- Q2, Q4 — Motorola MPF102 JFET.
- R1 — 10-k $\Omega$  carbon control, audio taper preferred.
- U1 — 741 op amp, 8-pin dual in line. Mount directly on pc board or use 8-pin IC socket.

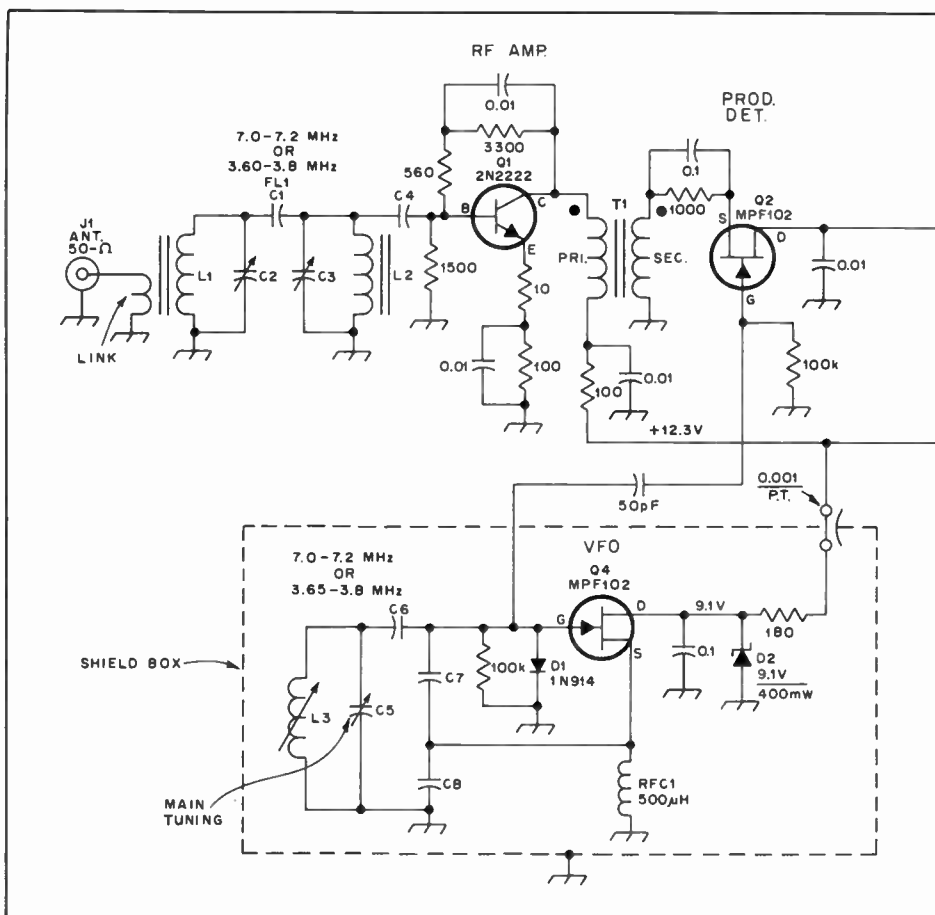



in order to make the project less difficult for inexperienced builders to assemble. The VFO is enclosed in a separate compartment made from three pieces of double-sided pc board. The side pieces measure  $2\frac{1}{2} \times 3$  inches ( $64 \times 76$  mm). The rear wall of the VFO box is  $2 \times 2\frac{1}{2}$  inches ( $51 \times 64$  mm). The rear corners of the box are joined by flowing solder along the inner seams. A  $1\frac{1}{2} \times 2$ -inch ( $38 \times 51$  mm) plate is soldered inside the front of the compartment,  $\frac{1}{2}$  inch (13 mm) from the front panel. This plate is also made from double-sided pc board. It is the mounting plate for the main-tuning capacitor. Three no. 6 spade bolts hold the VFO box to the main circuit board.

The front and rear panels of the receiver are  $4\frac{3}{4}$  inches (127 mm) high and 6 inches (625 mm) wide. The etched-circuit board is soldered to the panels  $\frac{3}{4}$  inch (19 mm) up from the lower edges of the panels. After the panels are in place (they should be drilled for the attached parts first — see photographs), the leading edges of the VFO box can be tack-soldered to the front panel at two points to ensure rigidity. The rear panel can be reinforced by connecting a small homemade bracket between the inner wall of the panel and the etched-circuit board at some convenient point.

A 1-inch (25-mm) diameter hole is made in the front panel, centered on the shaft of the tuning capacitor. This will

permit ample leeway when mounting the vernier-drive mechanism.

A blank area is provided near the rear of the etched-circuit board. This was done to allow room for accessories to be added, such as an RC active audio filter or a small crystal-controlled converter to permit reception of the 20- or 15-meter bands. Alternatively, an audio amplifier could be placed in that spot to provide speaker volume. Designs for such accessory items are left to the skills of the builder.

All solder joints must be done with care to prevent cold-solder joints and unwanted bridges (shorts) from one circuit foils to another. Final inspection with a magnifying glass is recommended. If a radio club adopts this receiver as a group project it is suggested that the members trade receivers for the purpose of inspection before applying the operating voltage.

Fig. 52 contains a scale template for the circuit board, plus a parts-placement guide. The general layout scheme of the receiver is apparent when viewing the photographs. D3 is connected between J3 and the pc board 12-volt bus.

#### Checkout and Operation

The VFO tuning range should be checked first. With operating voltage from two 6-volt lantern batteries (series connected), 10 size D flashlight cells in

series, or a 12-volt regulated dc power supply, place a short length of wire near the VFO circuit. The opposite end of the wire is connected to the antenna post of a calibrated amateur receiver. Look for the VFO signal in the 80- or 40-meter bands (depending upon which model is built). Once it is located, indicating that the oscillator is working, set C5 for maximum capacitance. Tune the receiver being used for calibration purposes to the low-frequency end of the VFO range (3.6 or 7.0 MHz) and adjust the slug of L3 in the homemade receiver until a signal is heard. When C5 is set for minimum capacitance the signal should appear at approximately 3.8 or 7.2 MHz. As an alternative to the foregoing alignment method, a frequency counter can be coupled to the gate lead of Q2 for direct VFO readout.

All that remains in the alignment procedure is to set C2 and C3 of FL1 for peak signal response in the center of the VFO tuning range. If a 50-ohm signal generator is available it should be used for the purpose. If not, a 56-ohm resistor can be connected across J1 and a random length of antenna wire attached to the antenna post of the receiver. The trimmers of FL1 should then be set for maximum response of a weak signal near the center of the VFO tuning range. The 56-ohm resistor will provide a suitable termination for FL1 if the antenna wire is not a quarter wavelength long or some multiple thereof.


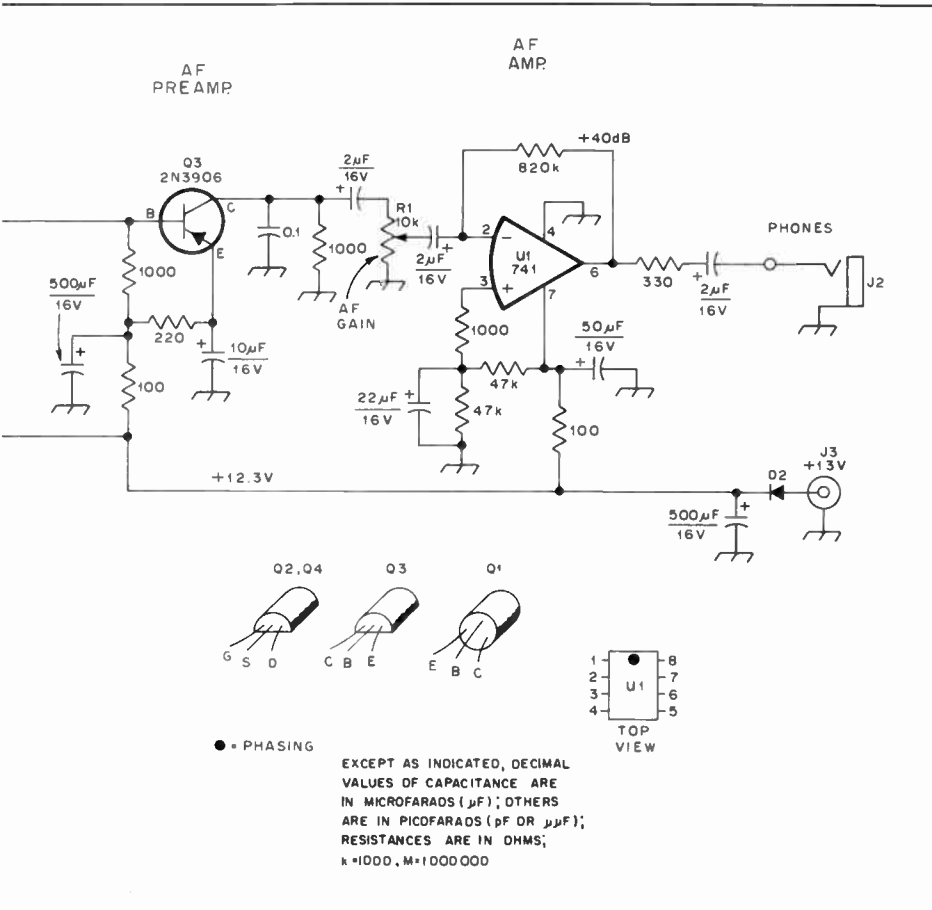


Fig. 51 — Top view of the receiver showing the input filter at the upper right, the VFO and its enclosure at the lower center and the audio-amplifier IC at the lower left. A Radio Shack vernier drive is used to turn the VFO tuning capacitor. A panel-reinforcing bracket is visible at the upper right.

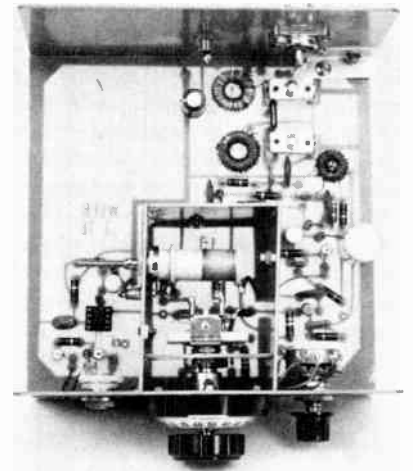

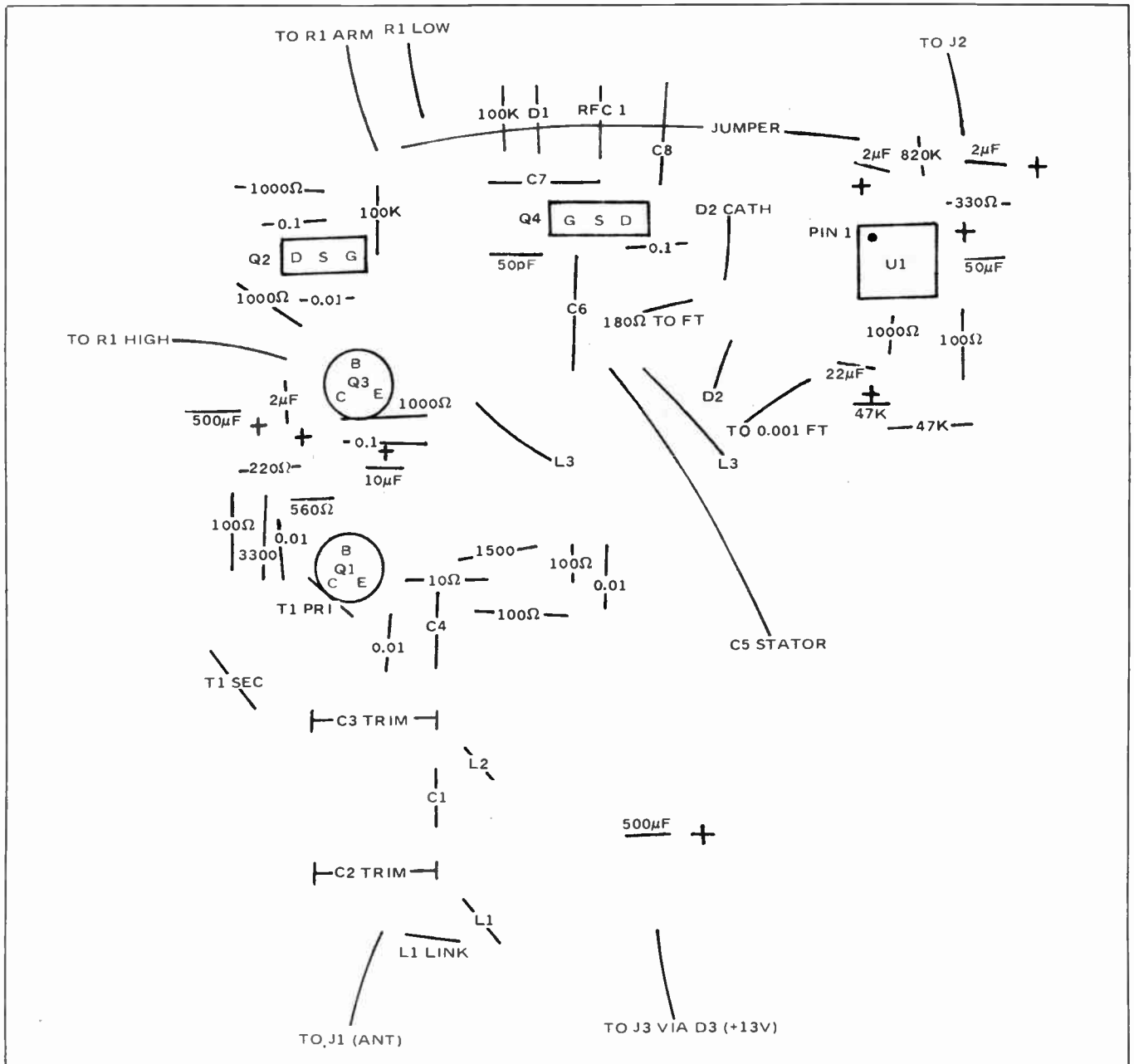


Fig. 53 — Scale pattern of the pc board showing parts placement. Shown from the component side of the board



Fig. 52 — Outside view of the simple superhet receiver. The front and rear panels are made from double-sided circuit board.

Circuit boards and negatives for this receiver are available from Circuit Board Specialists, Box 969, Pueblo, CO 81002. Complete parts kits are also available from the same supplier.

### A Simple Superhet for 75-Meter SSB

Circuit elaboration is not always essential to good receiver performance. This is particularly true when the builder desires compact equipment for portable operation. The simplicity concept is enhanced further by the low current drain which can be realized when only the bare essentials are designed into the circuit.

This superheterodyne receiver represents the most basic approach that will

provide acceptable selectivity, immunity to front-end overloading and sensitivity. Five transistors, four diodes and one IC comprise the semiconductor count in the design. A supply voltage of 11 to 14 is suitable. The current drain is on the order of 50 mA maximum.

Fig. 54 shows the schematic diagram of this receiver. A fixed-tuned Butterworth front-end filter permits coverage from 3.75 to 4.0 MHz without the need for retuning the filter. A high-transconductance dual-gate MOSFET, Q1, serves as the mixer. Conversion gain with this device (3N211) is very high, owing to the  $g_m$  of 30,000 micromhos. A Collins Radio CB-type mechanical filter is shown as the

i-f selectivity element, FL2. This part was chosen because of the low cost. However, any of the Collins 455-kHz mechanical filters designed for ssb bandwidth can be used, provided the insertion loss is low. The only circuit changes necessary would be modification of the terminating resistances, the filter resonating capacitors, and the BFO crystals (Y1 and Y2). This model calls for 2700 ohms at each end of the filter, plus two 360 pF resonating capacitors. The filter bandwidth is 2.2 kHz at the 3-dB points. The 60-dB bandwidth is 5.5 kHz. A lower-cost 455-kHz filter alternative is offered in the modification diagram of Fig. 55. A J. W. Miller 8814 transformer/filter is specified. It contains a monolithic filter that provides a 4-kHz bandwidth at the 3-dB points of the response curve. It is suggested that the Miller 8814 be used in place of a mechanical filter to ensure maximum overall receiver gain and reduced cost. An extra stage of i-f amplification may be required with some mechanical filters in order to have sufficient headphone output on weak signals.

Output from FL2 is routed to a single-stage i-f amplifier, Q2, another 3N211 FET. The gain of this amplifier, plus that of the audio-amplifier ICU1 is controlled manually by means of a dual control, R1A/R1B. The bias on gate 2 of Q2 is varied at R1A to set the i-f gain level. In order to obtain a wide range of control it is necessary to place gate 2 at a volt or two minus with respect to gate 1. This is achieved by "bootstrapping" the stage with D1, an LED which conducts at roughly 1.5 volts.<sup>2</sup> Therefore, when R1A has its arm at ground, gate 2 of Q2 is effectively at -1.5 volts (minimum gain). D1 serves purely as a reference diode in this instance. Alternatively, two 1N914 diodes can be used in series from source to ground to provide a reference of roughly 1.4 volts.

A 3N211 FET serves as the VFO. Gates 1 and 2 are connected together to simulate a single-gate transistor. Injection to the mixer is taken from the gate of Q3 in order to realize a 3-volt pk-pk level at gate 2 of Q1. A pure sine wave is available at that take-off point. Some oscillator pulling (slight) will be observed when FL1 is aligned. However, once the front-end filter is tuned the effect will not be noticed. A VFO buffer/amplifier would resolve this condition, but is not necessary in practice if circuit simplicity is to be keynoted. D2 is used as a switching diode to offset the VFO frequency when changing from upper to lower sideband. This eliminates the need to readjust the main-tuning dial of the receiver. This part of the circuit need not be included if dial calibration is not essential when changing sidebands.

<sup>2</sup>The LED should be installed so that it illuminates when R1 is set for maximum receiver gain.

A 3N211 is employed at Q4 (gates tied together) as the product detector. Output from the i-f amplifier is fed to the source of Q4. BFO energy is supplied to Q4 from another 3N211 (Q5). Y1 and Y2 are selectable to permit upper and lower sideband reception. Since lower-sideband transmissions are the general rule on 75 meters, the builder may elect to use only the lsb crystal and eliminate S1 and the VFO offset circuitry.

Audio gain is provided by U1, a 40-dB op amp. The receiver output is adequate for weak signals (1  $\mu$ V or greater) with the arrangement shown in Fig. 54. Addition of a 0.5 or 1-watt audio IC would enable the builder to employ a speaker rather than phones, but the current drain of the receiver would be considerably higher.

### Construction Notes

The etched-circuit board is the single-sided variety (copper on only one side). Double-sided pc board material is used for the front panel, rear panel and the VFO enclosure. Constructional details and dimensions follow closely those given for the direct-conversion beginner's receiver treated earlier in this chapter. Therefore, that information will not be repeated here. Pc boards, negatives and parts kits for this receiver are available from Circuit Board Specialists, listed in the text for the foregoing beginner's receiver. An adaptor pc board is available from that supplier to permit using the modification shown in Fig. 55.

Fig. 57 shows the scale pc pattern and parts placement for this receiver. The panels are soldered to the ground foil which forms the perimeter of the etched-circuit board.

### Adjustment and Use

FL1 is designed to be terminated in a 50-ohm load. The antenna or signal generator used during adjustment of C1 and C2 should provide a 50-ohm termination. Tune in a weak signal near 3875 kHz and adjust C1 and C2 for maximum signal output in the headphones. There may be some interaction, so repeat this step two or three times. This assumes that the VFO has been calibrated by means of the slug in L4 to provide mixer injection at 44 3.55 kHz when C3 is set for minimum capacitance (plates unmeshed).

T1 is peaked last for maximum signal output from the receiver, again using a weak-signal source. This transformer is adjusted for resonance at the center of the FL2 passband — 453.55 kHz.

Offset trimmer C4 of Fig. 54 should be set as follows. Tune in a weak signal for zero beat, with S1 in the upper-sideband position. Switch S2 to lower sideband and adjust C4 for zero beat as heard in the headphones. The main-tuning dial should not be moved during this part of the alignment.

The reason FL2 does not have a center

Table 4

Component	DC Voltage
<b>Q1</b>	
Gate 1	0.0
Gate 2	0.3
Drain	12.21
Source	0.26
<b>Q2</b>	
Gate	- 7.72
Drain	9.38
Source	0.0
<b>U1</b>	
Pin 2	5.96
3	5.96
4	0.0
6	6.02
7	11.90
<b>U2</b>	
Pin 2	6.0
3	6.0
4	0.0
6	6.0
7	11.96

These voltages were measured by means of a Heath VTVM while powering the receiver with a 12-volt dc source.

frequency of 455 kHz is because it was designed by Collins for use as a *lower-sideband* filter. An upper-sideband filter is used with it in CB radios. That permits the use of a single BFO crystal at 455 kHz for either sideband. The bandpass of this filter is symmetrical, just as is true of the regular 455-kHz Collins mechanical filters in amateur receivers. FL2 was chosen for this project because the price is roughly one-third that of the mechanical filters used by most amateur builders.

### A Four-Band Direct-Conversion Receiver

This direct-conversion receiver will allow a beginner to become acquainted with amateur radio. It provides cw and ssb reception of the 80-, 40-, 20- and 15-meter amateur bands. Band changing is accomplished with plug-in coil assemblies. Parts procurement — a commonly given argument against home construction — should not be a problem, as most of the components can be obtained at Radio Shack stores.

### Circuit Details

The circuit, Fig. 59, consists of a product detector (Q1) which uses an RCA 40673 dual-gate MOSFET. The combination of T1 (a plug-in coil) and C1, the peak control, determine the input frequency coverage. They are connected through C2 to gate 1 of the 40673. The oscillator is Q2. Injection to gate 2 of the product detector is through capacitor C19. Drain voltage for the oscillator is stabilized by means of D5, a 9.1-volt Zener diode. The tuning range of the oscillator is determined by plug-in assembly, L1/C18. C21, the main-tuning capacitor, connects to a tap on L1. This permits only the desired amateur band to be tuned.

Fig. 54 — Schematic diagram of the ssb receiver. Fixed-value capacitors are disk ceramic unless noted otherwise. Polarized capacitors are electrolytic. Fixed-value resistors are 1/4- or 1/2-watt composition.

- C1, C2 — Mica compression trimmer, 300 pF max. Arco 427 or equiv.  
 C3 — Miniature 25-pF air variable, Hammarlund HF-25 or similar.  
 C4 — Circuit-board mount subminiature air variable or glass piston trimmer, 10 pF mix. NP0; miniature ceramic trimmer suitable as second choice.  
 D1 — LED, any color or size. Used only as 1.5-V reference diode.  
 D2, D3 — Silicon switching diode, 1N914 or equiv.  
 D4 — Polarity-guarding diode. Silicon rectifier, 50 PRV, 1A.  
 D5 — Zener diode, 9.1 volts, 400 mW or 1 watt.  
 FL1 — Band-pass filter (see text)  
 FL2 — Collins Radio CB-type mechanical filter, Rockwell International no. 5269939010, 453.55 kHz center freq.  
 J1 — SO-239.  
 J2 — Single-hole-mount phono jack.  
 J3 — Two-circuit phone jack.  
 L1 — Two turns no. 24 insulated wire over ground end of L2.  
 L2, L3 — 40 turns no. 24 enam. wire on T-68-6 toroid core.  
 L4 — Slug-tuned inductor, 3.6 to 8.5 range, J. W. Miller 42A686CBI or equivalent suitable. Substitutes would have Q of 100 or greater at 4 MHz and be mechanically rigid.  
 Q1-Q5, incl. — Texas Instruments 3N211 FET.  
 R1 — Dual control, 10-k $\Omega$  per section, linear taper, Allen Bradley type JD1N200P or similar. Separate controls can be used by providing extra hole in front panel.  
 RFC1, RFC3 — 10-mH Miniature rf choke, J. W. Miller 70F102AI or equiv.  
 RFC2 — 1-mH Miniature rf choke, J. W. Miller 70F103AI or equiv.  
 S1 — Two-pole, two-position phenolic or ceramic wafer switch.  
 T1 — 455-kHz miniature i-f transformer (see text), J. W. Miller no. 2067.  
 U1 — 8-pin dual-in-line 741 op amp.  
 Y1, Y2 — International Crystal Co. type GP, 30-pF load capacitance, HC-6/U style of holder. Lsb 452.25 kHz, and usb 454.85 kHz.

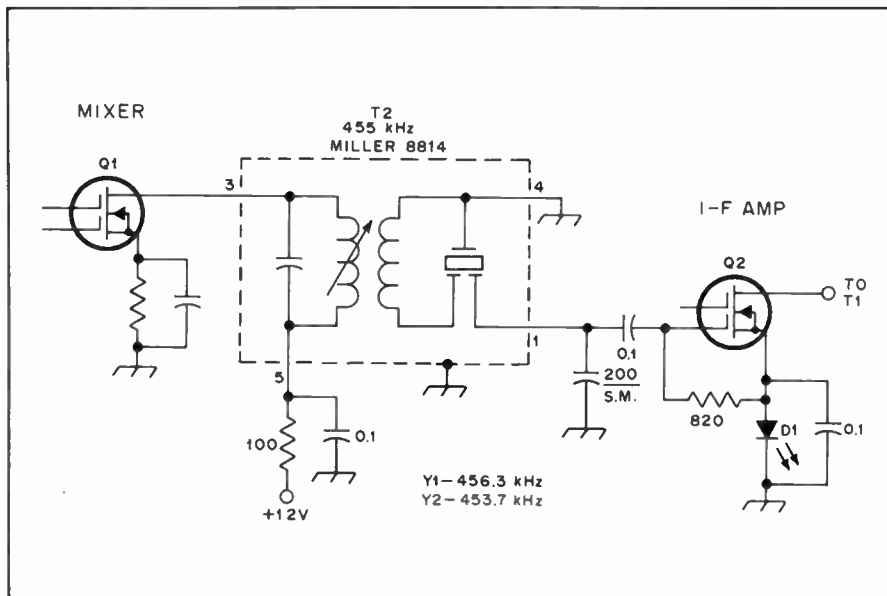
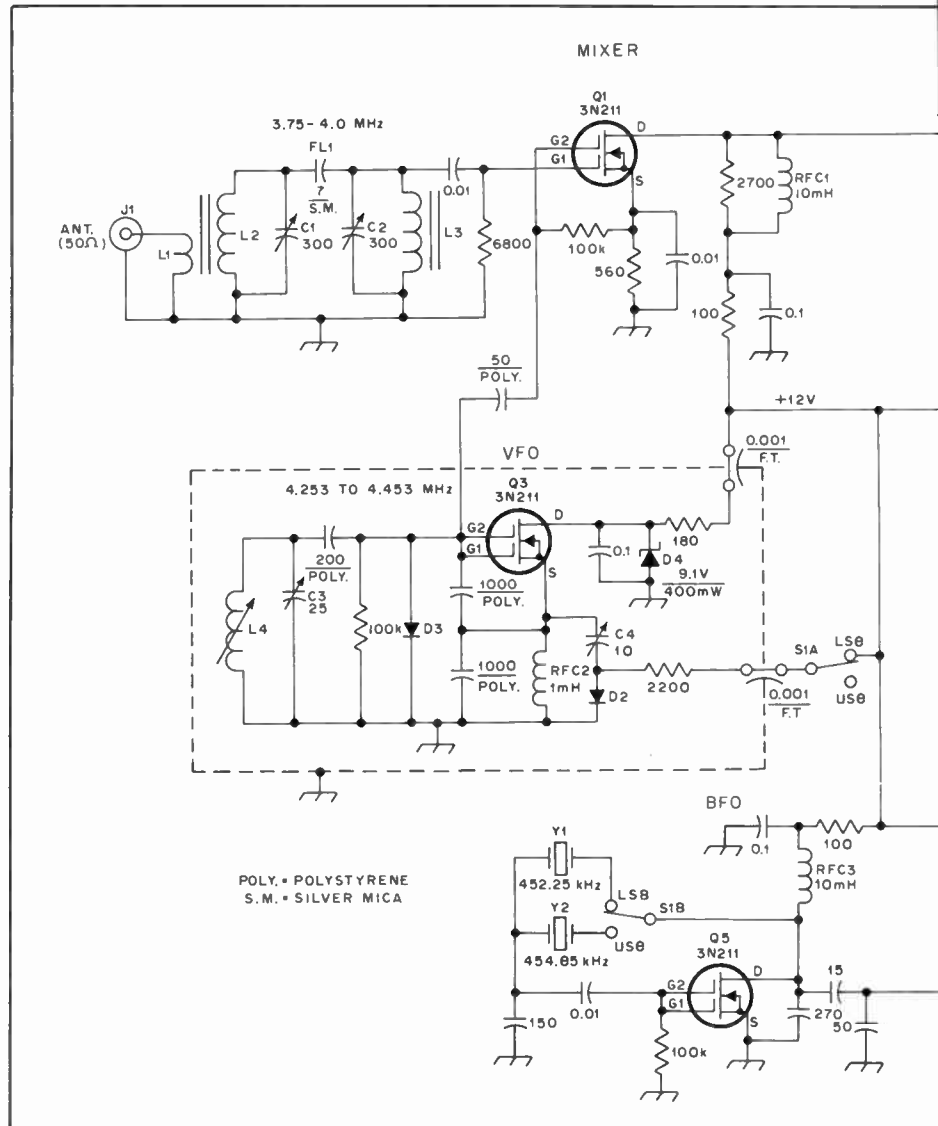


Fig. 55 — Circuit modifications for inclusion between the mixer and i-f amplifier of the circuit in Fig. 54. T2 is a J. W. Miller no. 8814 i-f filter transformer (see text).

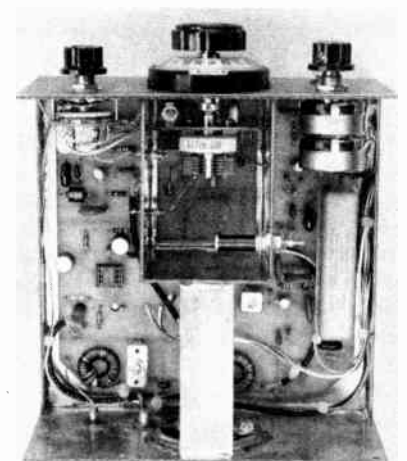


Fig. 56 — Top view of the simple superhet receiver showing the locations of the various components. The VFO and its enclosure are at the center of the etched-circuit board adjacent to the front panel. The layout seen here differs in some areas from the artwork in Fig. 57 due to late circuit changes. The speaker on the rear panel is not used.







EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu\text{F}$ ); OTHERS ARE IN PICOFARADS ( $\text{pF}$  OR  $\mu\mu\text{F}$ ); RESISTANCES ARE IN OHMS; k = 1000, M = 1,000,000.

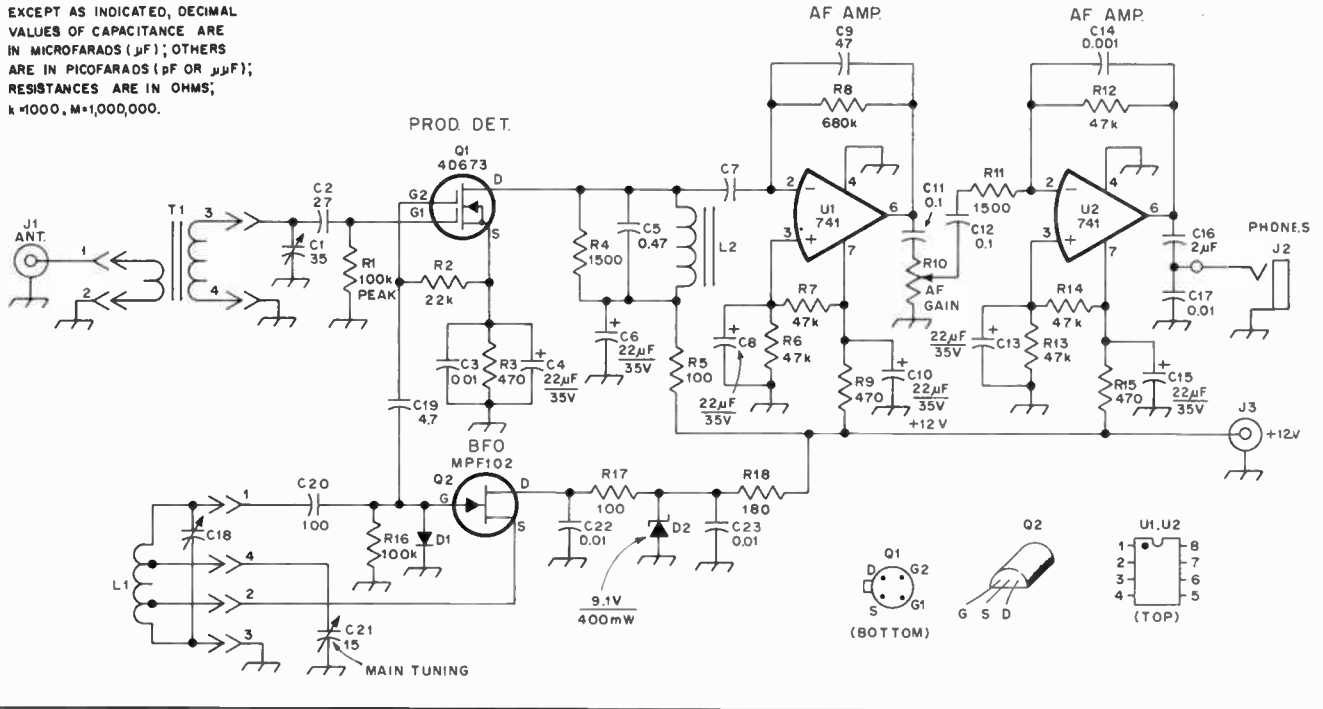


Fig. 59 — Schematic diagram for the beginner's 4-band direct conversion receiver. Fixed-value resistors are 1/4 W carbon. Capacitors marked with polarity are tantalum or electrolytic.

C1 — 35 pF, Hammarlund HF-35 or equiv.  
 C21 — 15 pF Hammarlund HF-15 or equiv.  
 C2 — 27 pF silver mica.  
 C3, C17, C22 — 0.01  $\mu\text{F}$  disk ceramic.  
 C4, C6, C8, C10, C13, C15 — 22  $\mu\text{F}$ , 35-V.  
 C9 — 47 pF, disk ceramic.  
 C14 — 0.001  $\mu\text{F}$ , disk ceramic.  
 C7, C11, C12 — 0.1  $\mu\text{F}$ .

C19 — 4.7 pF disk ceramic.  
 C20 — 100 pF polystyrene.  
 C5 — 0.47  $\mu\text{F}$  mylar.  
 C18 — See table 5.  
 C16 — 2  $\mu\text{F}$ .  
 D1 — 1N914.  
 D2 — 1N757.  
 T1 — See table 5.

L1 — See table 5.  
 L2 — 110 mH pot core.  
 J1, J3 — RCA phone jack.  
 J2 — Open-circuit phone jack.  
 Q1 — RCA 40673.  
 Q2 — Motorola MPF102.  
 R10 — 20-k  $\Omega$  potentiometer, audio taper.  
 U1, U2 — 741 operational amplifier.

scribed later in this chapter. They were designed for high performance also, and the desired characteristics were based on the dynamic-range profile of this receiver. That is, the two systems are compatible by design intent. IMD of the main-frame receiver (tested at 1.9 MHz) is -95 dB. Noise floor is -135 dBm, and blocking of 1 dB occurs at some point in excess of 123 dB above the noise floor. With the mating 20-meter converter attached, IMD = 88 dB, noise floor is -133 dBm, and blocking is in excess of 123 dB. The 20-meter tests were performed with the fixed-tuned 160-meter front-end filter in the circuit. Tests for dynamic range on 160 meters were performed with the tunable Cohn filter in the circuit. This receiver was described first by W1FB in *QST* for June and July, 1976.

#### Front-End Circuit

Fig. 64 shows the rf amplifier, mixer, and post-mixer amplifier. What may seem like excessive elaboration in design is a matter of personal whim, but the features are useful, nevertheless. For example, the two front-end attenuators aren't essential to good performance, but are useful in making accurate measurements (6, 12 or 18 dB) of signal levels during on-the-air

experiments with other stations (antennas, amplifiers and such). Also, FL2, a fixed-tuned 1.8- to 2-MHz band-pass filter, need not be included if the operator is willing to repeak the three-pole tracking filter (FL1) when tuning about in the band. The fixed-tuned filter is convenient when the down converters are in use.

The benefits obtained from a highly selective tunable filter like FL1 are seen when strong signals are in or near the 160-meter band. The rejection characteristics can be seen in Fig. 65. Insertion loss was set at 5 dB in order to narrow the filter response. In this example the high-Q slug-tuned inductors are isolated in aluminum shields, and the three-section variable capacitor which tunes them is enclosed in a shield made from pc-board sections. Bottom coupling is accomplished with small toroidal coils.

Rf amplifier Q1 was added to compensate for the filter loss. It is mismatched intentionally by means of L10 and L11 to restrict the gain to 6 dB maximum. Some additional mismatching is seen at L12, and the mixer is overcoupled to the FET tuned output tank to broaden the response (1.8 to 2 MHz). The design tradeoffs do not impair performance.

The double balanced diode-ring mixer

(U1) was chosen for its excellent reputation in handling high signal levels, having superb port-to-port signal isolation, and because of its good IMD performance. The module used in this design is a commercial one that contains two broadband transformers and four hot-carrier diodes with matched charac-

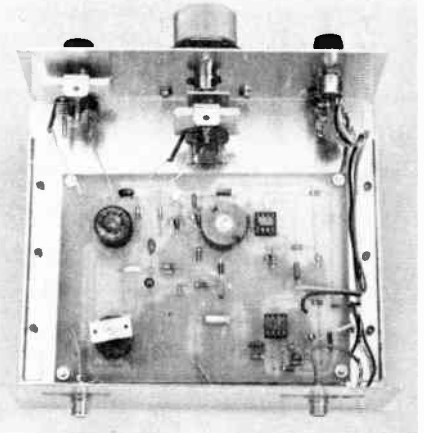


Fig. 60 — Inside view of the 4-band direct conversion receiver showing the etched-circuit board supported above the chassis on metal standoff posts. The pot-core audio inductor is at the top center of the pc board.

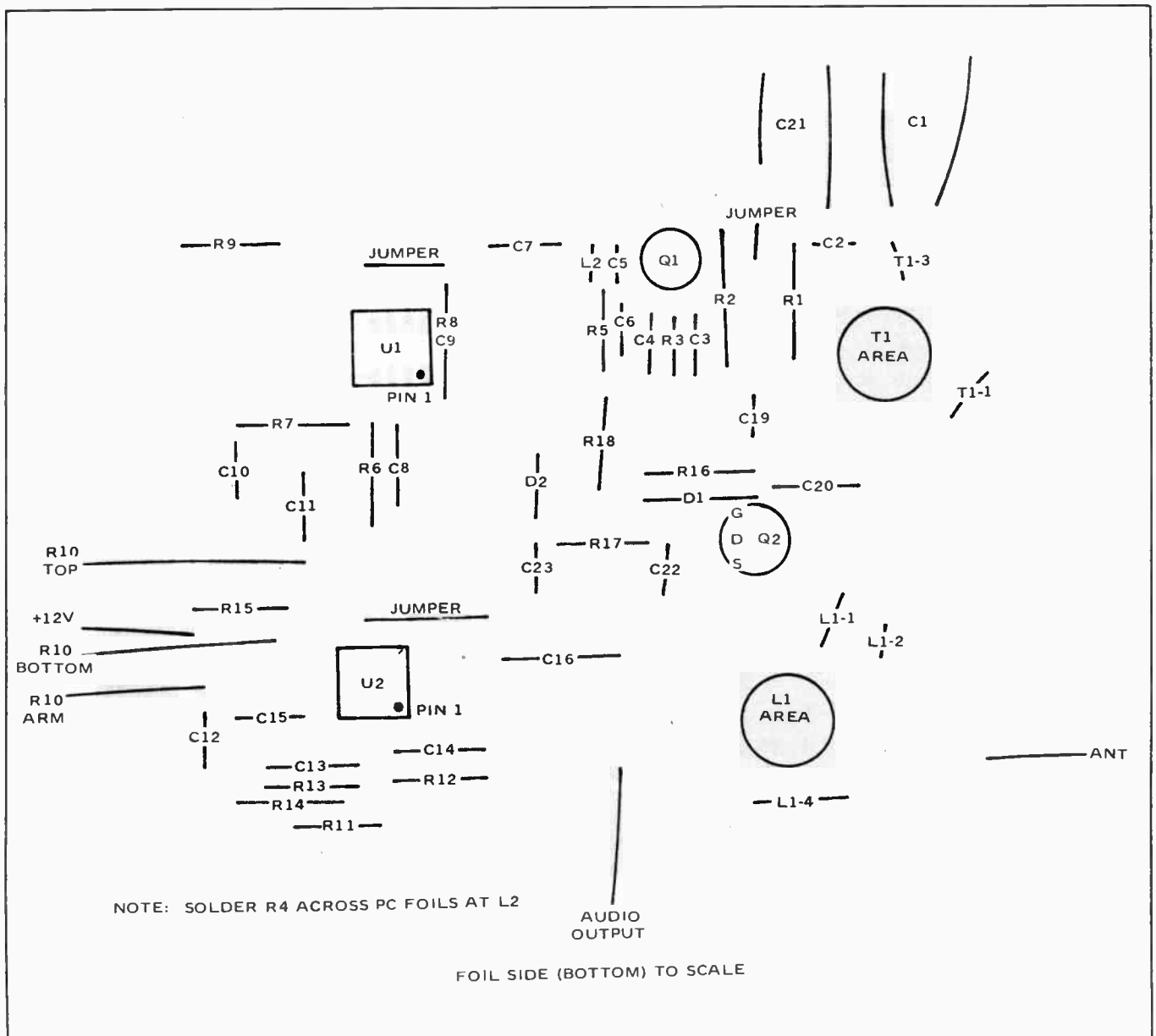


Fig. 61 — Scale template and parts layout for the 4-band direct-conversion receiver. View shown from the copper-foil side.

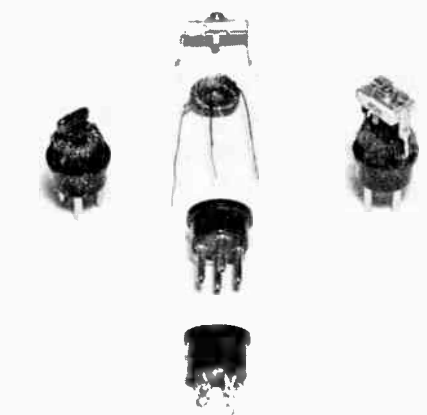


Fig. 62 — Break-down view (center) of a plug-in coil assembly for the 4-band "dc" receiver. Completed units are at the left and right of the picture.



Fig. 63 — This receiver is built in a homemade aluminum cabinet. A two-tone gray and flat-black paint job has been applied. Black Dymo tape labels are used for identifying the controls in the black area, and gray labels are affixed to the gray portion of the front panel. A cut-down Jackson Brothers vernier dial mechanism (two-speed) is used for frequency readout.

teristics. The amateur can build his own mixer assembly in the interest of reduced expense. At the frequencies involved in this example, it should not be difficult to obtain performance equal to that of a commercial mixer.

A diplexer is included at the mixer output (L13 and the related 0.002 capacitors). The addition was worthwhile, as it provided an improvement in the noise floor and IMD characteristics of the receiver. The diplexer works in combination with matching network L14, a low-pass L-type circuit. The diplexer is a high-pass network that permits the 56-ohm terminating resistor to be seen by the mixer without degrading the 455-kHz i-f. The low-pass portion of the diplexer helps reject all frequencies above 455 kHz so that the post-mixer amplifier receives only the desired information. The high-pass



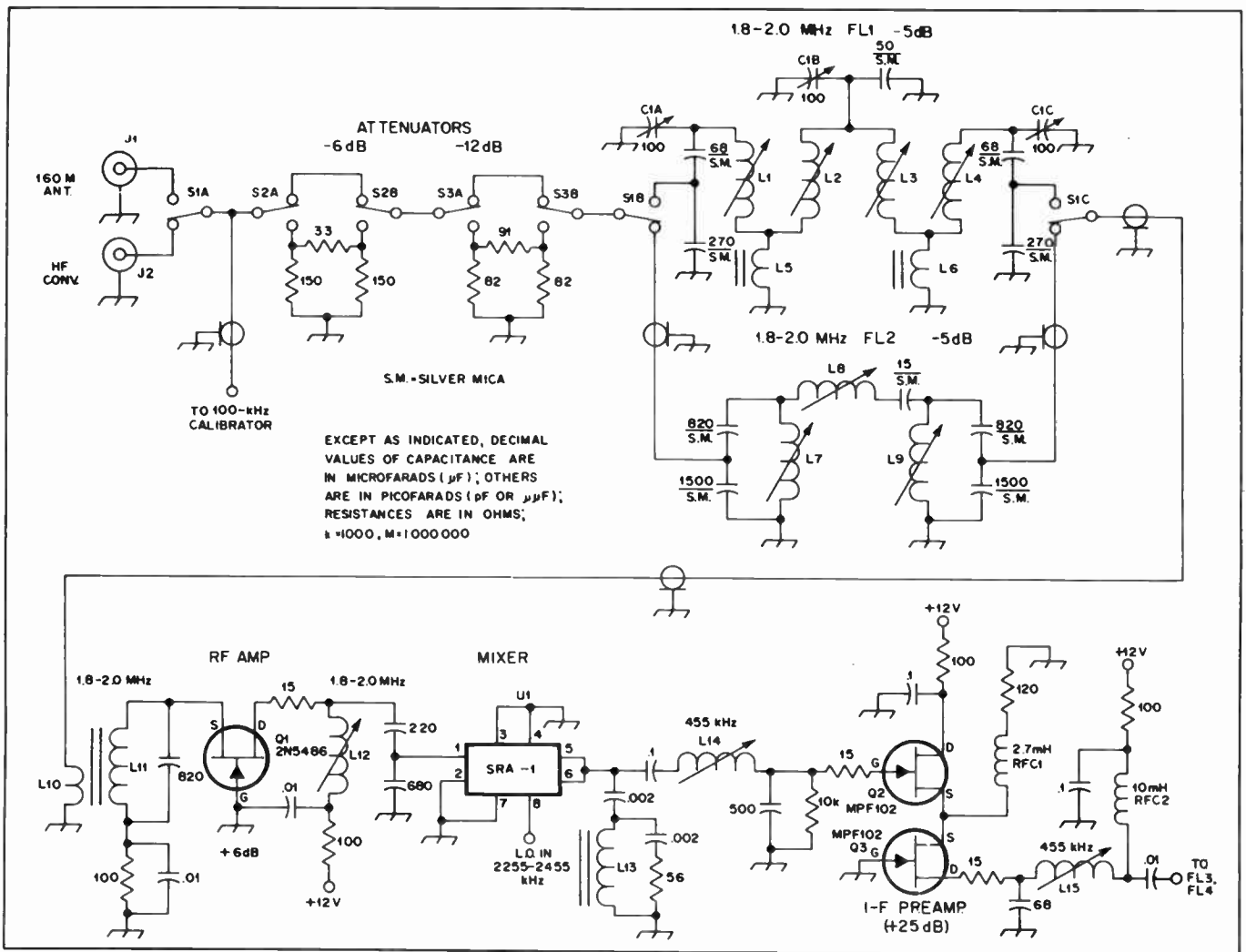


Fig. 64 — Schematic diagram of the receiver front end. Fixed-value capacitors are disk ceramic unless otherwise noted. Resistors are 1/2-W composition. All slug-tuned inductors are contained in individual shield cans which are grounded.

- C1 — Three-section variable, 100 pF per section. Model used here obtained as surplus.
- J1 — SO-239.
- J2 — Phono jack.
- L1, L4 — 38 to 68  $\mu$ H,  $Q_u$  of 175 at 1.8 MHz, slug-tuned inductor, J.W. in Miller S-74 shield can.
- L2, L3 — 95 to 187  $\mu$ H,  $Q_u$  of 175 at 1.8 MHz, slug-tuned, J. W. Miller 43A154CBI in S-74 shield can.
- L5, L6 — 1.45- $\mu$ H toroid inductor,  $Q_u$  of 250 at 1.8 MHz. 15 turns no. 26 enam. wire on Amidon T-50-2 toroid.
- L7, L9 — 13- $\mu$ H slug-tuned inductor, J. W. Miller 9052.
- L8 — 380- $\mu$ H slug-tuned inductor, J. W. Miller 9057.
- L10 — 16 turns no. 30 enam. wire over L11 winding.
- L11 — 45 turns no. 30 enam. wire on Amidon T-50-2 toroid, 8.5  $\mu$ H.
- L12 — 42- $\mu$ H slug-tuned inductor,  $Q_u$  of 50 at 1.8 MHz, J. W. Miller 9054.
- L13 — 8.7- $\mu$ H toroidal inductor. 12 turns no. 26 enam. wire on Amidon FT-37-61 ferrite core.
- L14 — 120- to 280- $\mu$ H, slug-tuned inductor, J. W. Miller 9056.
- L15 — 1.3- to 3.0-mH, slug-tuned inductor, J. W. Miller 9059.
- Q1, Q2, Q3 — Motorola JFET.
- RFC1 — 2.7-mH miniature choke, J. W. Miller 70F273AI.
- RFC2 — 10-mH miniature choke, J. W. Miller 70F102AI.
- S1 — Three-pole, two-position phenolic wafer switch.
- S2, S3 — Two-pole, double-throw miniature toggle.
- U1 — Mini-Circuits Laboratories SRA-1 doubly balanced diode mixer. (2625 East 14th St., Brooklyn, NY 11235.)

section of the diplexer starts rolling off at 1.2 MHz. A reactance of 66 ohms ( $X_C$  and  $X_L$ ) was chosen to permit use of standard-value capacitors in the low-Q network.

A pair of source-coupled JFETs is used in the post-mixer i-f preamplifier. The 10-k $\Omega$  gate resistor of Q2 sets the transformation ratio of the L network at 200:1 (50 ohms to 10 k $\Omega$ ). An L network is used to couple the preamplifier to a diode-switched pair of Collins mechanical filters which have a characteristic impedance of 2000 ohms. The terminations are built into the filters.

Gain distribution to the mixer is held to near unity in the interest of good IMD performance. The preamplifier gain is approximately 25 dB. The choice was made to compensate for the high insertion loss of the mechanical filters — 10 dB. Without the high gain of Q2 and Q3 there would be a deterioration in noise figure.

**Local Oscillator**

A low noise floor and good stability are essential traits of the local oscillator in a quality receiver. The requirements are met by the circuit of Fig. 66. Within the capabilities of the ARRL lab measuring

procedures, it was determined that VFO noise was at least 90 dB below fundamental output. Furthermore, stability at 25°C ambient temperature was such that no drift could be measured from a cold start to a period three hours later. Mechanical stability is excellent: Several sharp blows to the VFO shield box caused no discernible shift in a cw beat note while the 400-Hz i-f filter was actuated. VFO amplifier Q14 is designed to provide the recommended +7 dBm mixer injection voltage. Furthermore, the output pi tank of Q14 is of 50 ohms characteristic impedance. Though not of special signifi-

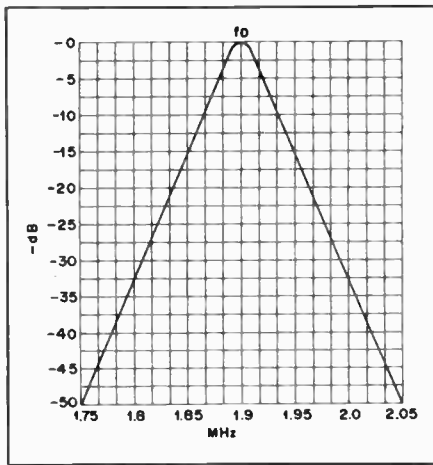


Fig. 65 — Response curve of the tunable front-end filter, centered on 1.9 MHz.

cance in this application, the measured harmonic output across 50 ohms is  $-36$  dB at the second order, and  $-47$  dB at the third order.

### Filter Module

In the interest of minimizing leakage between the filter input and output ports (Fig. 68), diode switching is used. The advantage of this method is that only dc switching is required, thereby avoiding the occasion for unwanted rf coupling across the contacts and wafers of a mechanical switch. 1N914 diodes are used to select FL3 (400-Hz bandwidth) or FL4 (2.5-kHz bandwidth). Reverse bias is applied to the nonconducting diodes. This lessens the possibility of leakage through them. Because the Collins filters have a characteristic impedance of 2000 ohms, the output coupling capacitors from each are 120 pF rather than the low-reactance 0.01- $\mu$ F units, as used at the filter inputs. Without the smaller value of capacitance the filters would see the low base impedance of Q4, the post-filter i-f amplifier. The result in this case would be one of double termination, leading to a loss in signal level. Additionally, the 120-pF capacitors help to divorce the input capacitance of the amplifier stage. The added capacitance would have to be subtracted from the 350- and 510-pF resonating capacitors at the output ends of the filters.

The apparent overall receiver gain is greatest during cw reception, owing to the selectivity of cw filter FL3. To keep the S-meter readings constant for a given signal level in the ssb and cw modes, R7 has been included in the filter/amplifier module. In the cw mode, R7 is adjusted to bias Q4 for an S-meter reading equal to that obtained in the ssb mode. Voltage for the biasing is obtained from the diode-switching line during cw reception.

### I-F Amplifier

A receiver i-f system should be capable of providing a specific gain, have an

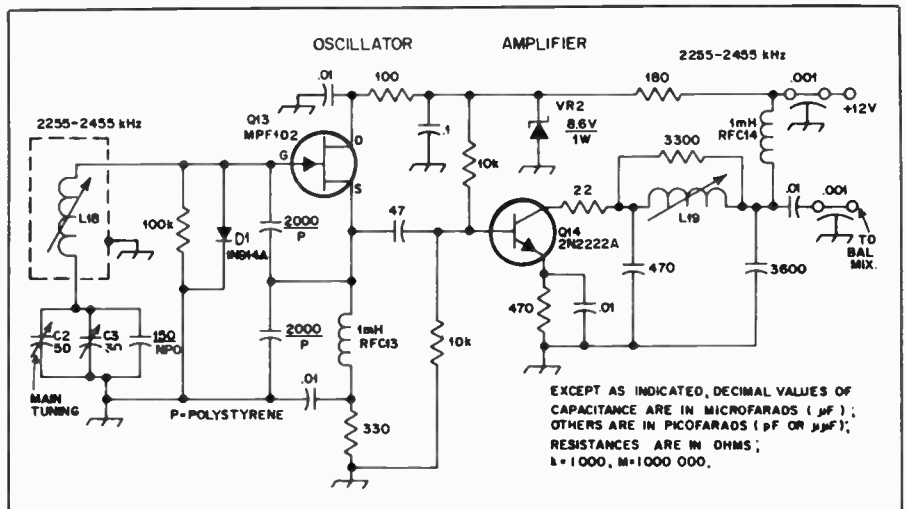


Fig. 66 — Circuit diagram of the local oscillator. Capacitors are disk ceramic unless specified differently. Resistors are 1/2-W composition. Entire assembly is enclosed in a shield box made from pc-board sections.

- C2 — Double-bearing variable capacitor, 50 pF.
- C3 — Miniature 30-pF air variable.
- D1 — High-speed switching diode, silicon type 1N914A.
- L18 — 17- to 41- $\mu$ H slug-tuned inductor,  $Q_u$  of 175, J. W. Miller 43A335CBI in Miller S-74

- shield can.
- L19 — 10- to 18.7- $\mu$ H slug-tuned pc-board inductor, J. W. Miller 23A155RPC.
- RFC13, RFC14 — Miniature 1-mH rf choke, J. W. Miller 70F103AI.
- VR2 — 8.6-V, 1-W Zener diode.

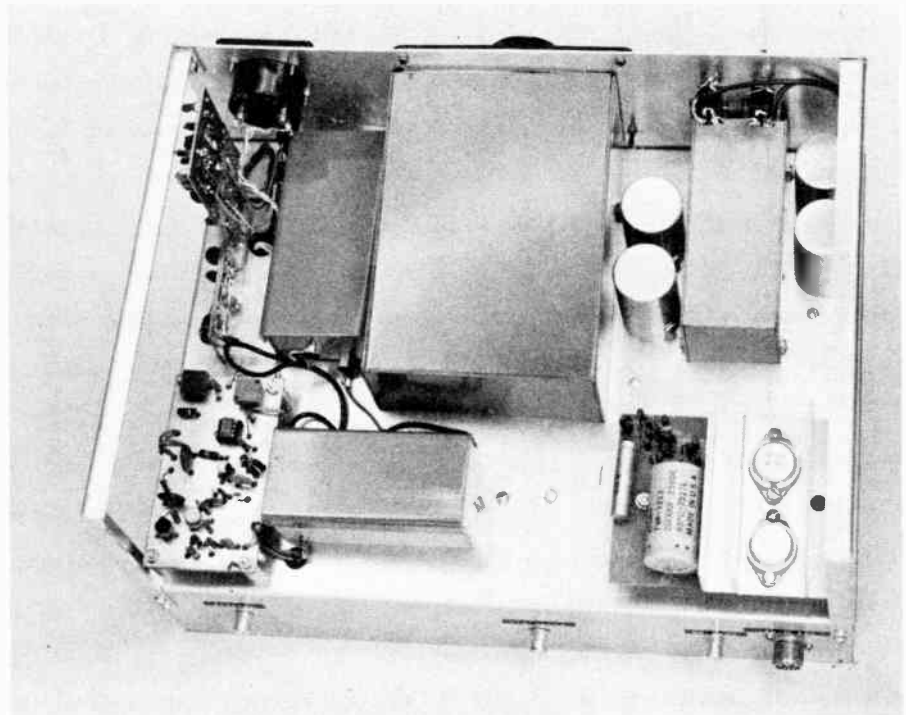


Fig. 67 — Top-chassis view of the receiver. The RC active filter and audio preamplifier are built on the pc board at the upper left. To the right is the BFO module in a shield box. The agc circuit is seen at the lower left, and to its right is the i-f strip in a shield enclosure. The large shield box at the upper center contains the VFO. To its right is the tunable front-end filter. The three-section variable capacitor is inside the rectangular shield box. The audio amplifier module is seen at the lower right. The small board (mounted vertically) at the left center contains the product detector. Homemade end brackets add mechanical stability between the panel and chassis and serve as a support for the receiver top cover.

acceptable noise figure, and respond satisfactorily to the applied agc. This almost bromidic judgment is not as true as it may seem, for some designers use a

haphazard approach to this part of a receiving system. Two of the more serious shortcomings in some designs are poor agc (clicky, pumping or inadequate range)

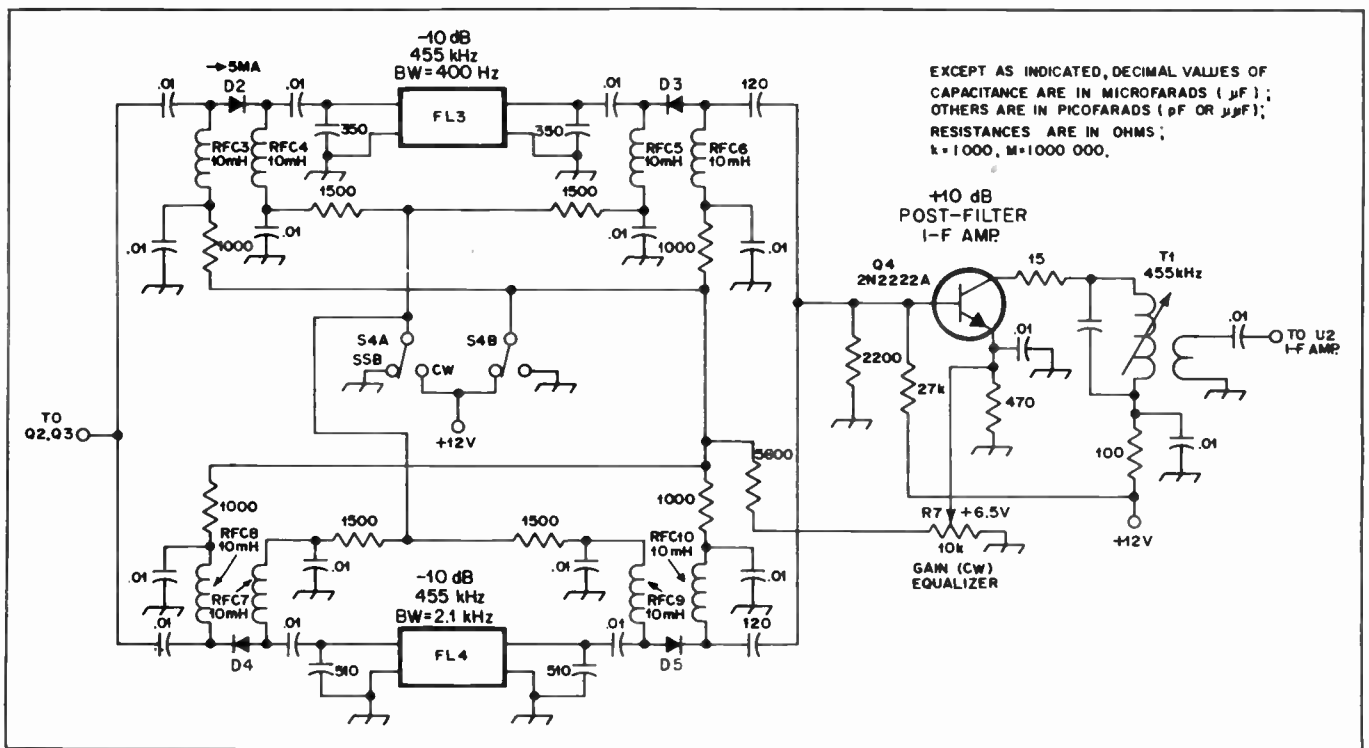


Fig. 68 — Schematic diagram of the filter and i-f post-filter amplifier. Capacitors are disk ceramic. Resistors are 1/2-W composition.  
 D1-D5, incl. — High-speed silicon switching diode, 1N914A.  
 FL3 — Collins mechanical filter F455FD-04.  
 FL4 — Collins mechanical filter F455FD-25.  
 RFC3-RFC10, incl. — 10-mH miniature rf choke, J. W. Miller 70F102A1.  
 R7 — Pc-board control, 10 k $\Omega$ , linear taper.  
 S4 — Double-pole, double-throw toggle or wafer.  
 T1 — Miniature 455-kHz i-f transformer, J. W. Miller 2067, 30 k $\Omega$  to 500 ohms.

and insufficient i-f gain.

A pair of RCA CA3028A ICs is used in the i-f strip. Somewhat greater gain and agc range is possible with Motorola MC1590G ICs, and they are the choice of many builders. However, the CA3028As, configured as differential amplifiers, will provide approximately 70 dB of gain per pair when operated at 455 kHz. This gives an agc characteristic from maximum gain to full cutoff which is entirely acceptable for most amateur work.

Fig. 69 shows the i-f amplifiers, product detector, and Varicap-tuned BFO. Transformer coupling is used between U2 and U3, and also between U3 and the product detector. The 6800-ohm resistors used across the primaries of T2 and T3 were chosen to force an impedance transformation which the transformers can't by themselves provide: Available Miller transformers with a 30-k $\Omega$  primary to 500-ohm secondary characteristic are used. U2 and U3 have 10- and 22-ohm series resistors in the signal lines. These were added to discourage vhf parasitic oscillations.

Agc is applied to pin 7 of each IC. Maximum gain occurs at +9 V, and minimum gain results when the agc voltage drops to its low value, +2 V. The agc is rf derived, with i-f sampling for the agc amplifier being done at pin 6 of U3 through a 100-pF blocking capacitor.

The 1000-ohm decoupling resistors in the 12-V feed to U2 and U3 drop the

operating voltage to +9. This aids stability and reduces i-f system noise. The amplifier strip operates with unconditional stability.

### Product Detector

A quad of 1N914A diodes is used in the product detector. Hot-carrier diodes may be preferred by some, and they may lead to slightly better performance than the silicon units. A trifilar broadband toroidal transformer, T4, couples the i-f amplifier to the detector at a 50-ohm impedance level. BFO injection is supplied at 0.7 V rms.


### BFO Circuit

In the interest of lowering the cost of this project, a Varicap (D10 of Fig. 69) is used to control the BFO frequency. Had a conventional system been utilized, three expensive crystals would have been needed to handle upper sideband, lower sideband, and cw. The voltage-variable capacitor tuning method shown in Fig. 69 is satisfactory if the operator is willing to change the operating frequency of the BFO when changing receive modes. Adjustment is done by means of front-panel control R1. Maximum drift with this circuit was measured as 5 Hz from a cold start to a time three hours later. A Motorola MV-104 tuning diode is used at D10.

Q6 functions as a Class A BFO

EXCEPT AS INDICATED, DECIMAL VALUES OF CAPACITANCE ARE IN MICROFARADS ( $\mu$ F); OTHERS ARE IN PICOFARADS (pF OR  $\mu$ pF); RESISTANCES ARE IN OHMS; k=1000, M=1000000.

### +10 dB POST-FILTER I-F AMP

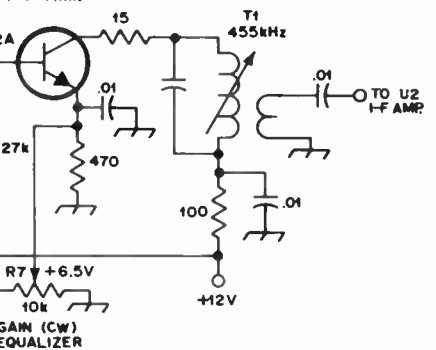

### GAIN (CW) EQUALIZER

amplifier/buffer. It contains a pi-network output circuit and has a 50-ohm output characteristic. The main purpose of the amplifier stage is to increase the BFO injection power without loading down the oscillator.

### AGC Circuit

Fig. 70 shows the agc amplifier, rectifier, dc source follower, and op-amp difference amplifier. An FET is used at Q10 because it exhibits a high input impedance and will not, therefore, load down the primary of T3 in Fig. 69. Q1 is directly coupled to a pnp transistor, Q11. Assuming that  $R_s$  and R2 are treated as a single resistance,  $R_s$ , the Q10/Q11 gain is determined as  $\text{gain (dB)} = 20 \log \frac{R_c + R_s}{R_s}$ . Control R2 has been included as part of  $R_s$  to permit adjustment of the agc loop gain. Each operator may have a preference in this regard. The agc is set so it is fully actuated at a signal-input level of 10  $\mu$ V. Agc action commences at 0.2  $\mu$ V (1 dB of gain compression).

Agc disabling is effected by removing the operating voltage from Q10 and Q11 by means of S5. Manual i-f gain control is made possible by adjusting R3 of Fig. 70. Agc delay is approximately one second. Longer or shorter delay periods can be established by altering the values of the Q14 gate resistor and capacitor. Agc amplifier gain is variable from 6 to 40 dB by adjusting R2. Agc action is smooth,



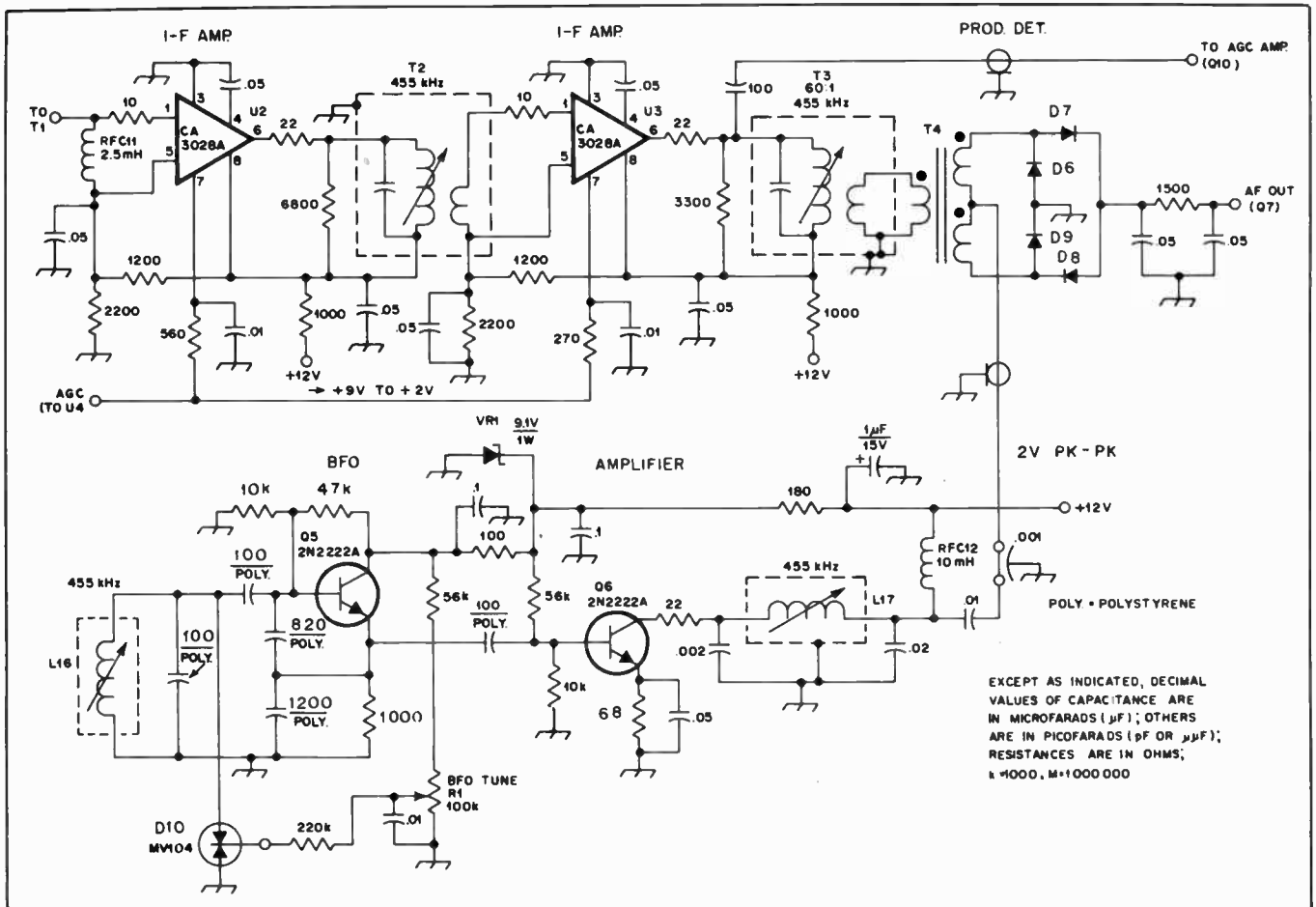


Fig. 69 — Circuit of the i-f amplifier, BFO, and product detector. Capacitors are disk ceramic unless noted differently. Fixed-value resistors are 1/2-W composition. Dashed lines show shield enclosures. The BFO and i-f circuits are installed in separate shield boxes. The RC active filter and af preamplifier are on a common circuit board, which is not shielded.

D6-D9, incl. — High-speed silicon, 1N914A or equiv.

D10 — Motorola MV-104 Varicap tuning diode.

D14 — 9.1-V, 1-W Zener diode.

L16 — Nominal 640- $\mu$ H slug-tuned inductor, J. W. Miller 9057.

L17 — Nominal 60- $\mu$ H slug-tuned inductor, J. W.

Miller 9054.

R1 — 100-k $\Omega$  linear-taper composition control (panel mount).

RFC11 — 2.5-mH miniature choke, J. W. Miller 70F253A1.

RFC12 — 10-mH miniature choke, J. W. Miller 70F102A1.

T2, T3 — 455-kHz i-f transformer. See text. J. W. Miller 2067.

T4 — Trifilar broadband transformer. 15 trifilar turns on no. 26 enam. wire on Amidon T-50-61 toroid core.

U2, U3 — RCA CA3028A.

and there is no evidence of clicks on the attack during strong-signal periods. At no time has agc "pumping" been observed.

### Audio System

A major failing of many receivers is poor-quality audio. For the most part this malady is manifest as cross-over distortion in the af-output amplifier. Moreover, some receivers have marginal audio-power capability for normal room volume when a loudspeaker is used. Some transformerless single-chip audio ICs (0.25- to 2-W class) exhibit a prohibitive distortion characteristic: This is especially prominent at low signal levels. The unpleasant effect is one of "fuzziness" when listening to low-level signals. Unfortunately, external access to the biasing circuit of such ICs is not typical, owing to the unitized construction of the chips.

Since undistorted audio is an important feature of a quality communications receiver, discrete devices have been em-

ployed in this circuit. The complementary-symmetry output transistors and the op-amp driver are configured in a manner similar to that used by Jung in his *Op Amp Cookbook*. Maximum output capability is 3.5 W into an 8-ohm load. An LM-301A driver was chosen because of its low-noise profile. There has been no aural evidence of distortion at any signal level while using the circuit of Fig. 72. The rationale in this situation is one of having considerably more audio power available than is needed — a practice used in hi-fi work.

### R-C Active CW Filters

A worthwhile improvement in signal-to-noise ratio can be realized during weak-signal reception by employing an RC active bandpass filter. A two-pole version (FL5) is shown in Fig. 72. A peak frequency of 800 Hz results from the R and C values given.

The benefits of FL5 are similar to those

when a second i-f filter (at the i-f strip output) is used to reduce wideband noise from the system. The RC active filter serves in a similar manner, but performs the signal "laundering" at audio rather than at rf. The technique has one limitation — monotony in listening to a fixed-frequency beat note, which is dictated by the center frequency of the audio filter. The RC filter should be designed to have a peak frequency that matches the cw beat-note frequency preferred by the operator. That is, if the BFO is adjusted to provide an 800-Hz cw note, the center frequency of FL5 should be 800 Hz.

Experience with FL5 in this receiver has proved in many instances that weak DX signals on 160 meters could be elevated above the noise to a Q5 copy level, while without the filter solid copy was impossible. It should be stressed that high-Q capacitors be used from C4 to C7, inclusive, to assure a sharp peak response.



Polystyrene capacitors satisfy the requirement. To ensure a well-defined (minimum ripple) center frequency, the capacitors should be matched closely in value (five percent or less). Resistors of five-percent tolerance should be employed in the circuit, where indicated in Fig. 72.

### Summary Comments

The photographs illustrate a modular construction technique. All rf-circuit assemblies are isolated from one another, and from outside energy influences, by means of shield compartments. Signal points are joined (module to module) with RG-174/U subminiature coaxial cable, the shield braids being grounded to the chassis at each end. Feedthrough-type .001- $\mu$ F capacitors are used at the 12-V entry points of the modules. The foregoing measures help to prevent birdies and unwanted stray rf pickup.

The tuning range of the receiver is 200 kHz. This means that for use with converters the builder will have to satisfy himself with the cw or ssb band segments. The alternatives are to increase the local oscillator tuning range to 500 kHz, or use a multiplicity of converters to cover the cw and ssb portions of each band.

### High-Performance Converters

This section provides circuits for a group of converters (80 through 15 meters) for use with the high-performance 160-meter receiver described in this chapter. These units were described originally in *QST* for June, 1976 by W7ZOI.

### Converter Designs

The converters should have a net gain of about 10 dB and an output intercept of approximately +17 dBm or higher. For work on the bands up through 14 MHz, a noise figure of 13 to 16 dB can be deemed acceptable. On the higher bands some compromise in dynamic range is tolerable in order to achieve lower noise figures. In studying the available circuit combinations it was decided to base the front end of the converters on a diode-ring mixer. The mixer would be preceded by a bandpass preselector filter and followed with a diplexer and dual-gate MOSFET amplifier at 1.9 MHz. A block diagram of the system is shown in Fig. 74.

The original intention was to construct separate converters for each band, 80 through 10 meters. However, after reviewing the design requirements, this was found to be redundant. Diode-ring mixers are inherently broadband and do not require tuned circuits. Furthermore, the post-mixer amplifier would be identical for all of the bands. Only the front-end preselector networks and local oscillators need be changed between bands. The final configuration chosen was to use a master board which contained the diode-ring mixer and the post amp. A family of

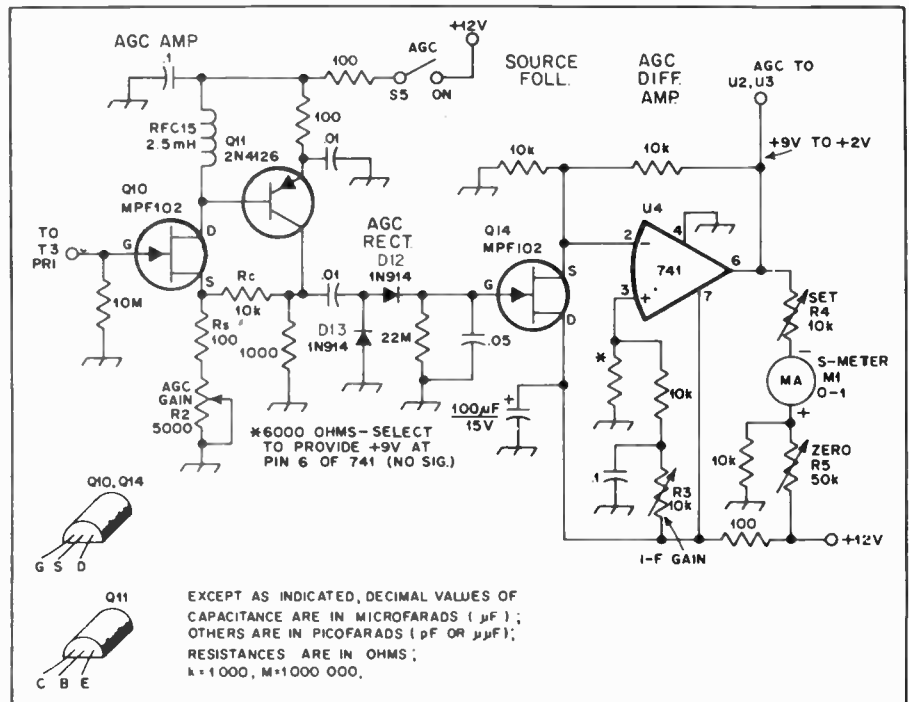


Fig. 70 — Schematic diagram of the agc system. Capacitors are disk ceramic except when polarity is indicated, which signifies electrolytic. Fixed-value resistors are 1/2-W composition. This module is not enclosed in a shield compartment.

- D12, D13 — High-speed silicon, 1N914A or equiv.
- Q10, Q12, Q14 — Motorola MPF102 JFET.
- Q11 — Motorola 2N4126.
- R2, R4, R5 — Linear-taper composition pc-board mount control.
- R3 — 10-k $\Omega$  linear-taper control, panel mounted.
- RFC15 — 2.5-mH miniature choke, J. W. Miller 70F253A1.
- S5 — Single-pole, single-throw toggle.
- U4 — Dual-in-line 741 op amp.
- M1 — 0- to 1-mA meter.

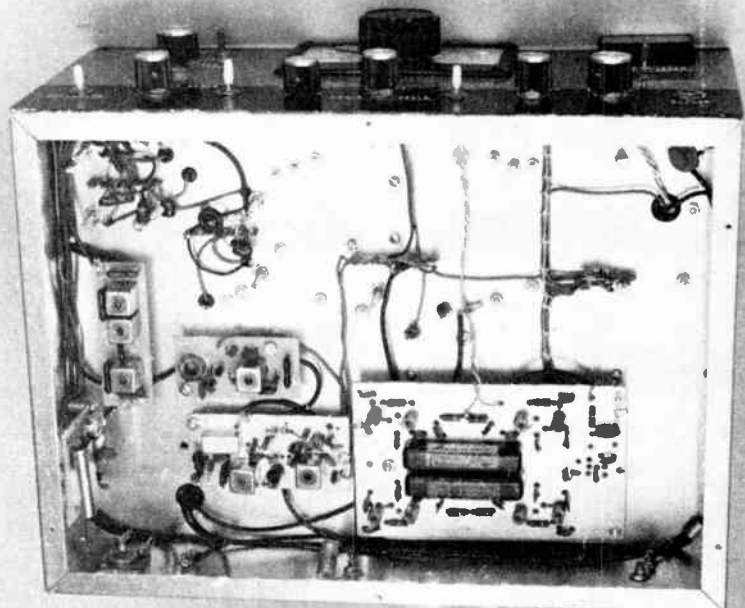


Fig. 71 — Considerable space remains beneath the chassis for the addition of accessory circuits or a set of down converters. At the upper left are the adjustment screws for the tunable filter, plus the bottom-coupling toroids. At the left center is the fixed-tuned front-end filter. To the right is the rf-amplifier module. A 100-kHz MFJ Enterprises calibrator is seen at the far lower left. Immediately to the right is the mixer/amplifier assembly. The large board at the lower center contains the i-f filters and post-filter amplifier. Most of the amplifier components have been tacked beneath the pc board because of design changes which occurred during development.

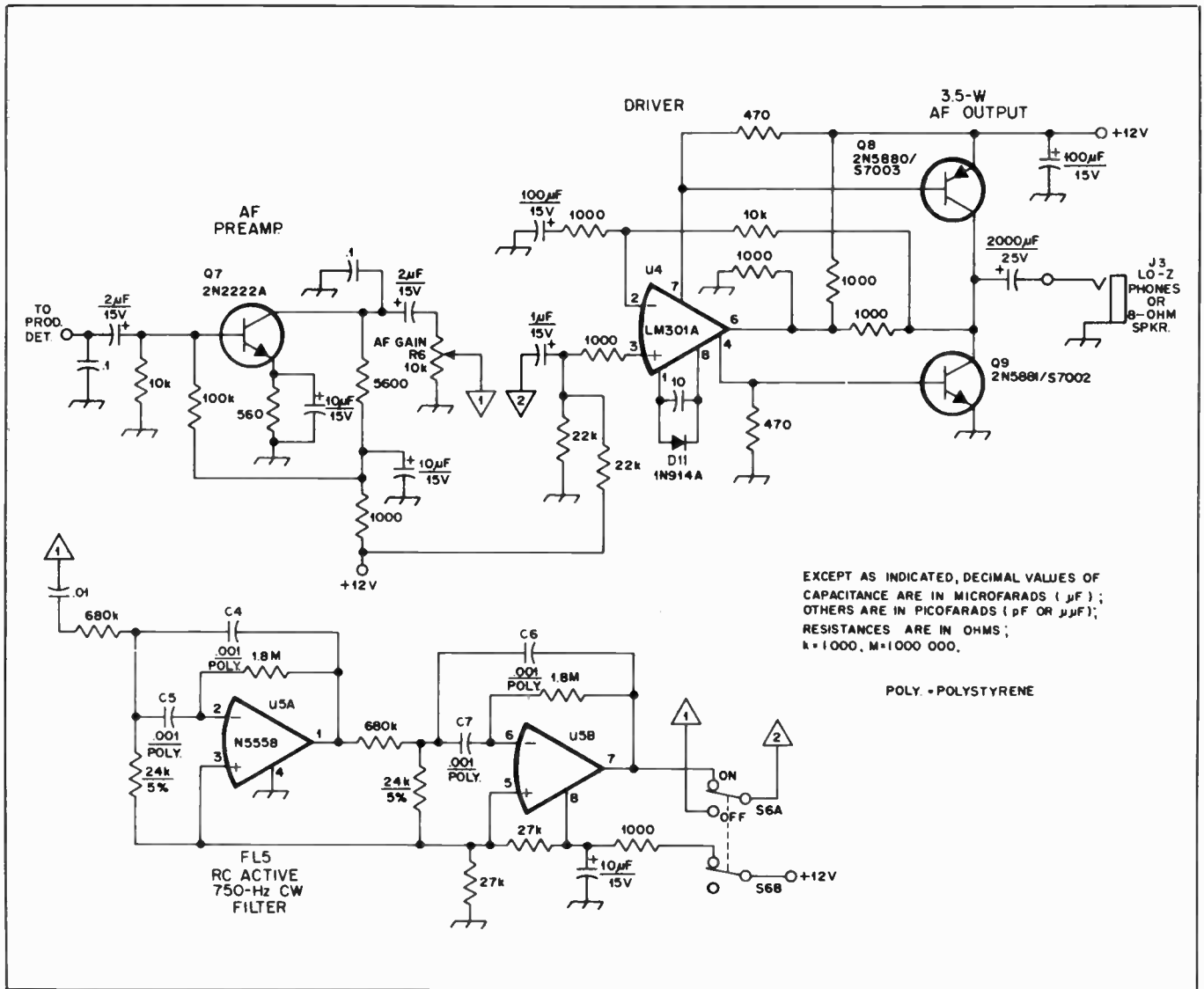


Fig. 72 — Diagram of the audio amplifier and RC active filter. Capacitors are disk ceramic unless otherwise noted. Polarized capacitors are electrolytic or tantalum. Fixed-value resistors are 1/2-W composition. This circuit is not contained in a shield box. Heat sinks are used with Q8 and Q9.  
 C4-C7, incl. — See text. R6 — 10-k $\Omega$  audio-taper composition control, panel mounted. U4 — National Semiconductor LM301A.  
 D11 — High-speed silicon, 1N914A or equiv. S6 — Dpdt, toggle. U5 — Signetics N5558 dual op-amp.  
 J3 — Phone jack.

boards was then constructed, each containing a suitable local oscillator and the preselector network for the band of interest.

### Mixer and Post-Amplifier Board

The circuit for the mixer and dual-gate MOSFET amplifier is shown in Fig. 75. There are a few departures from the typical in this design. First, a diplexer is used between the mixer and the "post amp." A 2200-ohm resistor at the gate provides a termination, causing the mixer to see 50 ohms in the 1.9-MHz frequency range.

In order to simplify the band switching, +12 volts dc is supplied through the local oscillator port of the mixer. This is realized with an rf choke and suitable capacitors.

The output of the amplifier was designed for broadband performance. To



Fig. 73 — Exterior view of the high-performance converter assembly. A gray and black spray-paint finish is applied to the homemade aluminum cabinet. Lettering is by means of a Dymo tape labeler.

obtain a large bandwidth, the output transformer (T1) is wound on a high permeability ferrite toroid. A powdered iron core should not be used for this transformer. It was found that a ferrite core with a permeability of 125 was not suitable in this position. Much better bandwidth and impedance matching was obtained with the core specified, which has a permeability of 2000. The 2200 ohm resistor in the drain circuit ensures that the output impedance presented by the amplifier is close to 50 ohms. This is important in order to assure that the input filters of the 160-meter receiver are properly terminated.

A ferrite bead is used on gate 2 of the amplifier. This may not be necessary in some cases. However, it was included to lessen the possibility of uhf oscillations occurring within the amplifier. A Fairchild FT-0601 or RCA 40673 dual-gate MOSFET can be used at Q1.

### Front-End Sections

Shown in Fig. 76 is the circuit used as the front end for each of the lower-input bands (3.5-3.7, 7.0-7.2 and 14.0-14.2 MHz). Component values are given in Tables 6 and 7.

The local oscillator for each of the converters uses a bipolar transistor and is designed to provide an output from +10 to +13 dBm. This level of LO injection is near optimum for the diode-ring mixer.

The preselector filters are fairly elaborate. However, the results are well worth the extra expense and effort. Predistorted filter-synthesis methods were used when designing the bandpass filters. They were designed for a three-pole Butterworth response.

One problem with multisection filters using capacitors as coupling elements between the resonators is that the stop-band attenuation may degrade in the vhf spectrum. This is due to slight amounts of lead inductance in the tuning capacitors, and the fact that the capacitive-intersection coupling method degenerates toward a high-pass filter response away from the passband. In order to suppress these responses, should they occur, a 5-pole low-pass filter is included at the antenna terminal.

Two methods were used for evaluation of the filter designs. First, after initial calculation of the component values, a computer program was used to determine the frequency response of the filters over a wide range. In this analysis, resistors were placed in the circuit to simulate the distortion effects caused by the losses in the cores.

After the filters were built and aligned, they were checked with laboratory instrumentation. In that case a Tektronix 7L13 spectrum analyzer and TR-502 tracking generator were used. The measured results around the passband corresponded with the computer simulation.

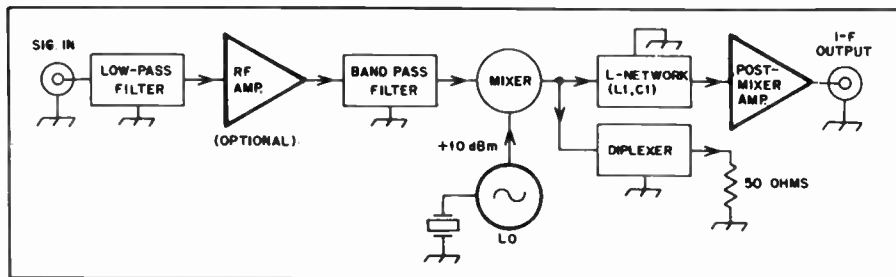


Fig. 74 — Block diagram of the hf-band converters.

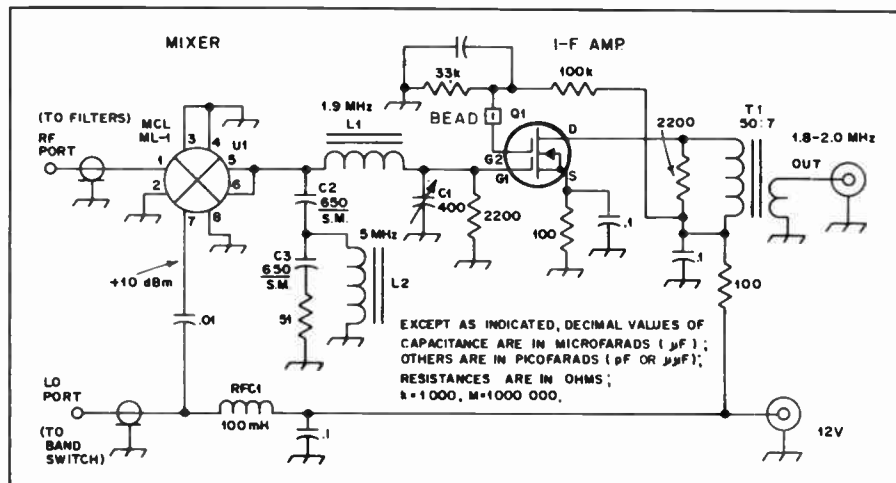


Fig. 75 — Diagram of the mixer and amplifier. Fixed-value capacitors are disk ceramic unless noted otherwise. Resistors are 1/2-W composition. See tables for component values not marked. U1 is a ML-1 or SRA-1 doubly balanced diode-ring mixer assembly. L2 (1.62  $\mu\text{H}$ ) has 18 turns of no. 22 wire on a T-50-2 toroid core. T1 primary has 50 turns of no. 22 wire on an FT-50-72 toroid core. The secondary contains 7 turns of no. 22 wire.

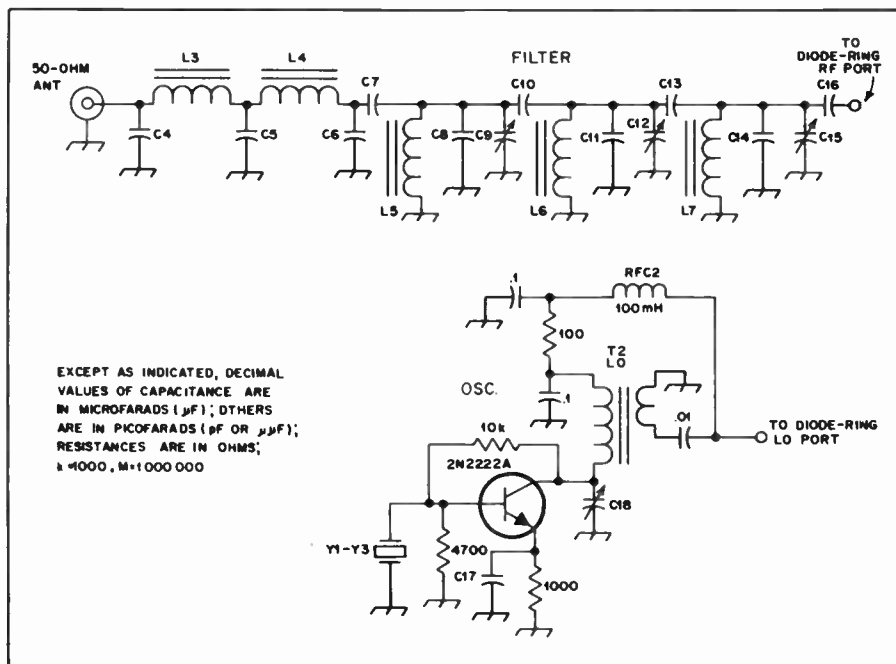


Fig. 76 — Diagram of the filter and crystal oscillator used on 20, 40 and 80 meters. Numbered fixed-value capacitors are silver micas. Resistors are 1/2-W composition. See Tables 6 and 7 for parts values.



**Table 6**

Band (MHz)	L3, L4, L8 (Turns-Core)	L9 (Turns-Core)	L5,L6,L7 L10,L11,L12 (Turns-Core)	T2,T3 (Turns-Core)
3.5 to 3.7	19, no. 22 T50-2	none	35, no. 24 T68-2	25, no. 24 T50-2, 2-t link
7.0 to 7.2	15, no. 22 T50-2	none	20, no. 22 T68-6	25, no. 24 T50-2, 2-t. link
14.0 to 14.2	12, no. 22 T50-6	none	12, no. 22 T68-6	28, no. 24 T50-6, 3-t. link
21.0 to 21.2	10, no.22 T50-6	21, no. 22 T50-6	10, no. 22 T50-6	19, no. 24 T50-6, 2-t. link

Coil and transformer data. Toroid cores are Amidon Assoc. powdered-iron type. Y1, Y2, Y3 and Y4 for 3.5 through 21 MHz, respectively, are 5.5, 5.2, 12.2 and 19.2 MHz (International Crystal Co. type GP, 30-pF load capacitance).

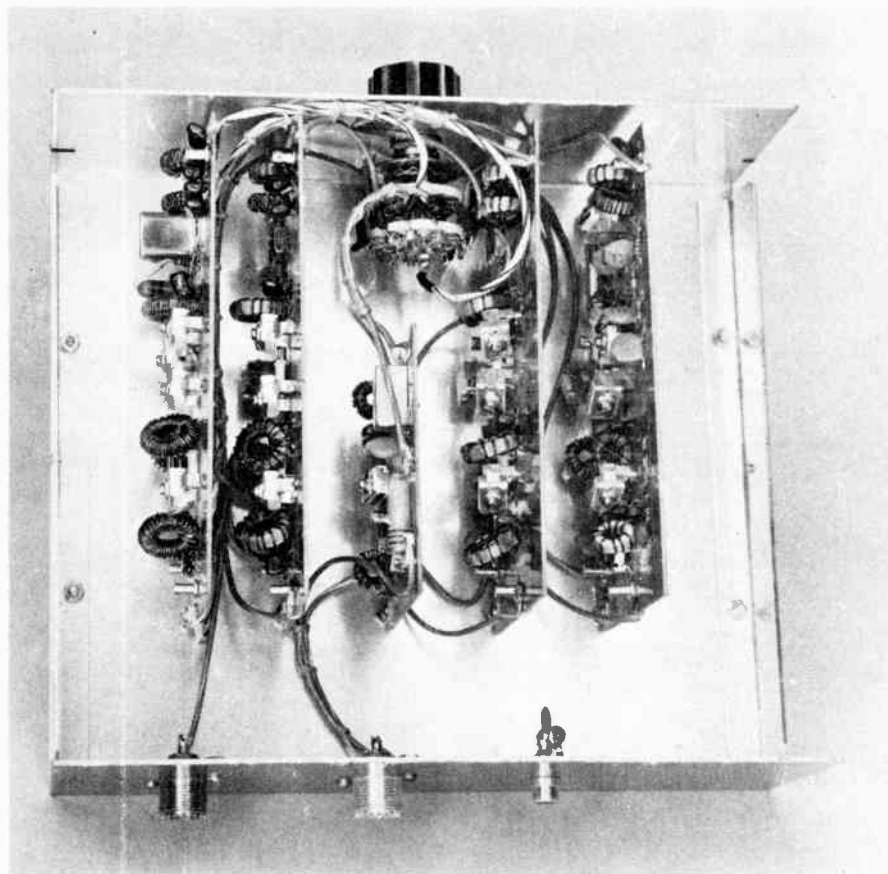


Fig. 77 — Interior view of the converter unit. The boards are mounted edgewise. The mixer module is seen at dead center. A multisection wafer switch, with shield partitions between wafers, should be used in place of the one seen in this photograph (see text).

The stopband attenuation was measured, with one exception, to be over 100 dB for all three filters evaluated. The exception was for the 80-meter filter. At about 70 MHz the attenuation degraded to about 95 dB, but returned to the better values at frequencies up through 200 MHz.

A Butterworth response was chosen because that filter shape is aligned easily with simple test equipment. Alignment is performed by driving the filter with a 50-ohm signal generator and terminating the output in a sensitive 50-ohm detector. The generator is set at the center frequency for the filter and the variable capacitors are adjusted for a maximum response. Experimentally, it was not found necessary to readjust the filters when the swept instrumentation was available.

The converter for the 15-meter band was built using the circuit in Fig. 78. On this band it was felt that a better noise figure might be useful. This was provided by inserting an rf amplifier between the low-pass filter and the bandpass circuit. The low-pass circuit was modified. The input section is a symmetrical pi network with a Q of 1. This is followed by a pi network with a Q of 10 and an impedance transformation from 50 to 2000 ohms. A 3300-ohm resistor is used in the drain circuit to ensure proper termination of the bandpass filter. In the unit built, the drain was attached directly to the "hot" end of the resonator (L10). However, it would be desirable to reduce the gain somewhat. This would be realized easily by tapping the drain down on the tuned circuit as shown. The terminating resistor should remain across L10.

Those building the converter for 80 meters may wish to also cover the 75-meter phone band. While the filter shown could probably be realigned for a range about 100 kHz higher, the shape of the filter would no doubt deteriorate if it were moved farther. A better approach would be to change the value of the inductors. Proper results should be obtained by reducing the coils from 35 to 32 turns, keeping all capacitor values the same. A 5.8-MHz crystal would be

**Table 7**

Band (MHz)	C4,C6 C19 (pF)	C5,C20 (pF)	C7 (pF)	C8 (pF)	C9,C12 C15 (pF)	C10 (pF)	C11 (pF)	C13 (pF)	C14 (pF)	C16 (pF)	C17,C31 (pF)	C18,C32 (pF)	C21 (pF)
3.5 to 3.7	790	1580	130	—	90 to 400	12	—	10	—	91	100	400	—
7.0 to 7.2	450	890	43	—	90 to 400	4.7	—	4.7	—	62	100	400	—
14.0 to 14.2	220	450	33	90	20 to 90	3.3	90	3.3	90	22	47	20 to 90	—
21.0 to 21.2	150	300 345	—	51	20 to 90	1.2	51	1.2	51	12	47	20 to 90	20 to 90

Fixed-value and trimmer capacitors. Fixed-value capacitors are silver-mica or similar high-Q, stable types. Trimmers are mica compression type. See text to obtain precise non-standard fixed-capacitance values.





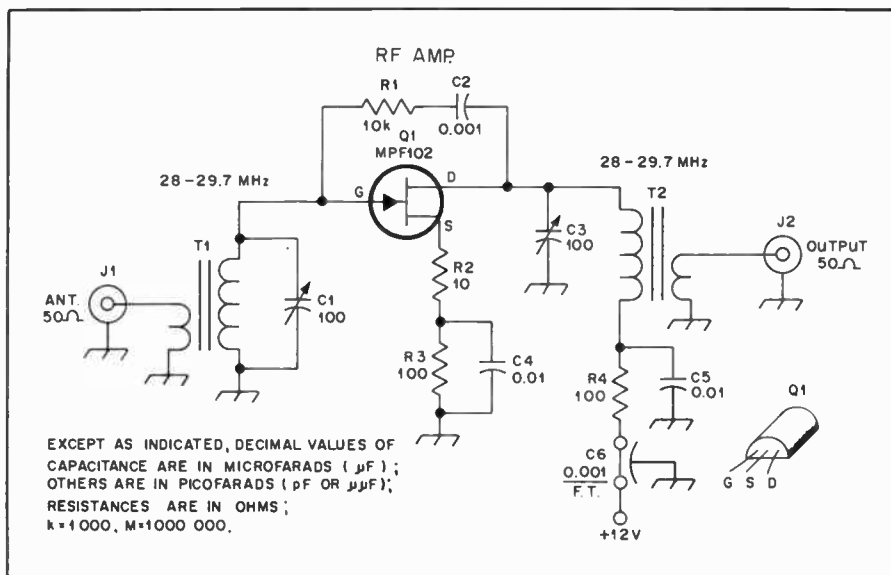


Fig. 80 — Schematic diagram of the 10-meter preamplifier. Data for 15-meter operation can be found in the text. Fixed-value capacitors are disk ceramic. Resistors are 1/4-watt composition types. Numbered components not appearing in the parts list are so identified for pc layout purposes only. C1, C3 — Mica compression trimmer, 100 pF max. Elmenco 423 suitable. J1, J2 — Coaxial connector of builder's choice. Q1 — Motorola JFET, MPF102, HEP F0015, or equiv. (see text).

used was an HP-8640B. On the three lower bands, the noise figure was 12 dB plus the loss of the input filters. Similarly, the gain of the converter was 12.5 dB, minus the loss of the input filters. It was found that the gain and noise figure could both be improved by removing the 2200-ohm resistor at the gate of Q1. There was a slight reduction in the output intercept, but not enough to cause problems. However, the low-pass part of the diplexer became much sharper in frequency response. This would make a front-panel trimmer control necessary.

The 15-meter converter performed differently. The net gain of this unit was 32.5 dB and the noise figure was about 3 dB. This is too much sensitivity to be usable at this frequency. It is recommended that the builder move the drain tap on the band-pass filter as outlined.

The two-tone dynamic range of the complete receiver was measured at 88 dB. Blocking occurred for an input over 120 dB above the MDS.

### A Stable 10-Meter Preamp

OSCAR enthusiasts and those who chase DX on 10 and 15 meters may not have the hottest receiver in town, especially if low-cost or early-design receivers are being used. When receivers run out of gas in terms of front-end gain and noise figure, it usually happens on 15 and 10 meters. A typical symptom is the need to carry the audio gain wide open to copy a weak signal. This problem can often be resolved by adding a preamplifier between the receiver input and the antenna.

Of course, it is not beneficial to add gain ahead of a receiver that has sufficient sensitivity. The end product may be excessive front-end gain, leading to the demise of good dynamic range. If the latter is degraded significantly, cross modulation, IMD and desensitization will become manifest when strong signals are present in and near the band of interest. In other words, don't use a preamp if your receiver performs satisfactorily now. All that will be achieved is a higher S meter reading and a higher ambient noise level when no signals are present.

### Circuit Description

A major problem experienced by some builders who use common-source FETs in rf amplifiers is instability. Despite careful layout and input-output isolation, instability seems to occur. A quick solution might be to change the circuit to a common-gate (grounded gate) type. Stability is relatively easy to obtain with the latter, but a tradeoff in gain will accompany modification. A common-gate JFET amplifier usually provides between 10 and 14 dB of gain, whereas a common-source version will yield up to 25 dB of gain in some circuits.

An alternative to using a common-gate configuration was highlighted in *Solid*

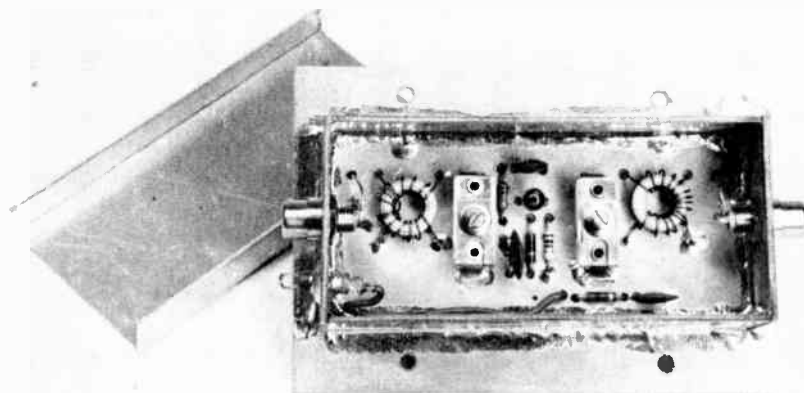


Fig. 81 — Inside view of the preamplifier, showing the layout used.

useful to build miniature equipment when there is a need for small size. However, for high-performance home-station equipment, where considerable experimentation may be required, a larger format is often desirable.

Because the pc boards shown in the photograph are quite large, the builder will probably elect to lay the circuits out for a more compact format. For this reason there are no pc-board templates and layouts available.

Care should be taken when the front-end sections are band switched. Shielding between switch wafers should have over

100 dB of isolation. Diode switching is not recommended unless the builder has equipment to evaluate the effects on IMD. The single-wafer switch shown in the photographs is not recommended.

The only converter evaluated for IMD was the 14-MHz unit. Two-tone IMD measurements were performed and it was found that the output intercept of the converter was +22 dBm. This is more than sufficient for the application, since it greatly exceeds the input intercept of the 160-meter receiver, +7.5 dBm.

The gain and MDS were measured for all four converters. The signal generator

*State Design for the Radio Amateur*, where Hayward and DeMaw illustrated and gave design data for fed-back bipolar-transistor rf amplifiers. The same principles apply to FET amplifiers, where gain is traded for bandwidth and stability.

A design objective with any amplifier should be unconditional stability — no self-oscillations at any frequency, regardless of the load connected to the amplifier. Properly applied feedback ensures unconditional stability. Circuits of this kind are ideal for amateur builders who have limited practical experience in the workshop.

Fig. 80 shows the WIFB circuit to which this project is addressed. T1 is a toroidal input transformer which is tuned to the operating frequency by means of C1. R1 and C2 form a shunt feedback-network which aids stability by lowering the gain. R2 provides additional stability by introducing degenerative feedback. R2 is not bypassed for rf.

The drain circuit contains a second tuned transformer, T2. R4 and C5 form a decoupling network in the 12-volt supply line. This helps prevent unwanted signal energy from entering the preamplifier via the power-supply leads.

#### Construction Data

A printed-circuit layout is given to scale in Fig. 82. Pc-board material (double sided) is used as a shield enclosure for the preamplifier. The outer dimensions of the box are (HWD) 1-1/2 × 1-3/4 × 3-15/16 inches (38 × 44 × 100 mm). A 3 × 4-1/2-inch (76 × 115 mm), pc-board base is used as the bottom cover, and a U-shaped, press-fit aluminum cover serves as a top shield for the assembly.

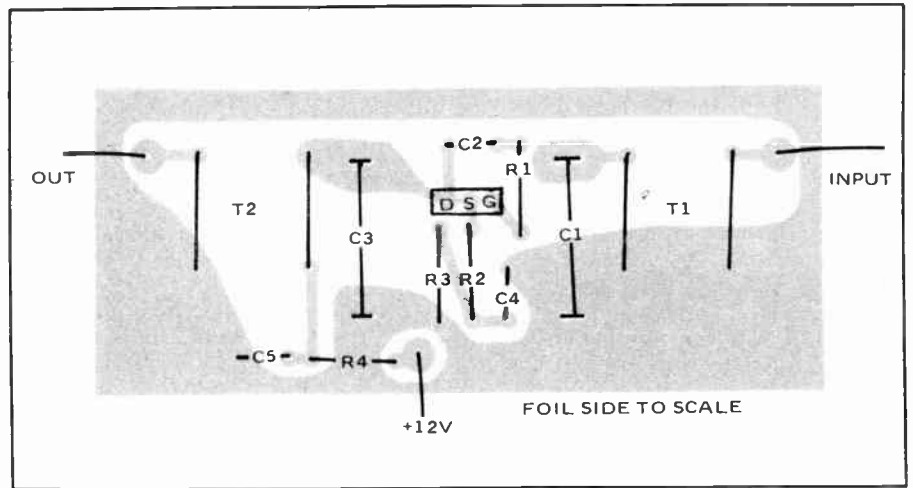


Fig. 82 — Scale pattern and layout for the pc board. See Ref. 1 for availability information.

The pc board is soldered in place inside the box after the circuit has been built and tested. A single-hole mount phono jack is used at each end of the box to provide input and output connections for the 50-ohm coaxial cables of the system. A 0.001- $\mu$ F feedthrough capacitor is mounted at one end of the box to allow routing of the 12-volt supply to the preamplifier.

#### Performance

A 3-dB bandwidth of 1 MHz is characteristic of this preamplifier. The measured gain is 15 dB. Stability is excellent under all conditions, including an open-loop situation (no termination at either end of the circuit). The noise figure is under 3 dB at 30 MHz. A slightly better noise figure and increased dynamic range

might be possible with a Siliconix E300 or U310 JFET. However, at 10 and 15 meters either the MPF102 or Motorola HEP F0015 is entirely suitable. A 2N4416 FET would be an acceptable substitute for the MPF 102.

Operation on 15 meters can be had by adding two turns of wire to the main windings of T1 and T2. No other changes are necessary. The circuit constants given in Fig. 80 are for 10-meter operation. A parts kit, pc board or pc negative are available<sup>3</sup>. This circuit is suitable for use on 20, 40 and 80 meters by merely changing the T1/C1 and T2/C3 circuits for the desired frequency.

<sup>3</sup>Circuit Board Specialists, Box 969, Pueblo CO 81002

# VHF and UHF Receiving Techniques

Adequate receiving capability is essential in vhf and uhf communications, whether the station is a transceiver or a combination of separate transmitting and receiving units, and regardless of the modulation system used. Transceivers and fm receivers are treated separately in this *Handbook*, but their performance involves basic principles that apply to all receivers for frequencies above 30 MHz. Important attributes are good signal-to-noise ratio (low noise figure), adequate gain, stability, and freedom from overloading and other spurious responses.

Except where a transceiver is used, the vhf station often has an hf-band communications receiver for lower bands, with a crystal-controlled converter for the vhf band in question ahead of it. The receiver serves as a tunable i-f system, complete with detector, noise limiter, BFO and audio amplifier. Unless one enjoys work with communications receivers, there may be little point in building this part of the station. Thus our concern here will be mainly with converter design and construction.

Choice of a suitable communications receiver for use with converters should not be made lightly, however. Several degrees of selectivity are desirable: 500 Hz or less for cw, 2 to 3 kHz for ssb, 4 to 8 kHz for a-m phone and 12 to 36 kHz for fm phone are useful. The special requirements of fm phone are discussed in chapter 13. Good mechanical design and frequency stability are important. Image rejection should be high in the range tuned for the converter output. This may rule out 28 MHz with receivers of the single-conversion type having 455-kHz i-f systems.

Broadband receiving gear of the surplus variety is a poor investment at any price, unless one is interested only in local work. The superregenerative receiver, though simple to build and economical to use, is inherently lacking in selectivity. With this general information in mind,

this section will cover vhf and uhf receiver "front end," stage by stage.

### RF Amplifiers

**Signal-to-Noise Ratio (S/N):** The limiting factor in the reception of signals is noise. Noise can be classified into two broad forms, random and nonrandom. Nonrandom noise such as interfering signals are reduced or eliminated through techniques aimed at directly filtering or otherwise suppressing detection of the unwanted signals. This is only possible because the nonrandom noises are discrete in nature and are relatively predictable.

Random noise is generated by sources both internal and external to the receiver. The external noise problem varies considerably with frequency of reception. Below about 25 MHz, man-made, atmospheric, and galactic noise picked up by the antenna is usually far greater than the noise generated within the receiver. In a majority of cases, noise output from a receiver tuned to the hf range drops dramatically when the antenna is disconnected from the receiver. When this is observed, it clearly demonstrates that reception is limited by external noise.

Since the ionosphere is less active at 50 MHz, atmospheric noise is of less concern than at hf. Even in a quiet location, however, external noise usually overrides receiver noise in a well-designed system. Above 100 MHz, external noise other than man-made is rarely a problem in weak-signal work. The noise characteristics of a receiving system become important as they are the primary limitation in weak-signal work. Unfortunately, circuit design and component choice become increasingly critical with respect to signal-to-noise ratio as the operating frequency rises.

The quantitative measure of the degradation of signal-to-noise ratio as the signal passes through the receiver is *noise*

*figure*. Noise figure is representative of the amount of noise generated within the receiver. The noise figure, *F*, is defined as

$$F = 10 \log_{10} \left( \frac{S/N \text{ at input}}{S/N \text{ at output}} \right)$$

The noise figure is expressed in dB. Decibels are often inconvenient for use in calculations, so another term, *noise factor*, is used. Noise factor, *f*, is merely the noise figure expressed in linear units rather than logarithmic units (decibels).

$$F = 10 \log_{10} f$$

A vhf receiving system consists of an interconnection of individual stages, some noisier than others. Each stage's noise contribution to the reduction of signal-to-noise ratio can be expressed as a noise figure. How much the noise figure of a particular stage affects system noise figure depends on the gain of the stages between that stage and the antenna. That is, if a stage's gain is sufficiently large, its noise figure will tend to override or "mask" the noise contribution of the stage following it. Mathematically, the noise factor of a receiving system can be expressed as

$$f = f_1 + \frac{f_2 - 1}{G_1} + \frac{f_3 - 1}{G_1 G_2} + \dots + \frac{f_n - 1}{G_n \dots G_2 G_1}$$

where

$f_n$  = noise factor of the  $n^{\text{th}}$  stage  
 $G_n$  = gain of the  $n^{\text{th}}$  stage

Brief analysis of this equation shows that the first stage of a receiving system is the most important with regard to noise figure. If the gain of this and succeeding stages is greater than unity, the denominator of each successive term becomes greater. The numerical value of terms beyond the second or third approaches zero and can be ignored.

It might seem that the more gain an rf



amplifier has, the better the signal-to-noise ratio and therefore the better the reception. This is not necessarily true. The primary function of an rf amplifier is to establish the noise figure of the system. One good rf stage is usually adequate unless the mixer is a passive type with loss instead of gain. Two rf stages are the usual maximum requirement.

Once the system noise figure is established, any further gain necessary to bring a signal to audible levels may be obtained from intermediate-frequency stages or in the audio channel. Use of the minimum gain necessary to set the overall receiver noise figure is desirable in order to avoid overloading and spurious signals in subsequent stages.

Further examination of the equation points out the desirability of mounting the first stage of the receiver system at the antenna. The transmission line from the antenna to the receiver can be considered as a stage in the receiving system. The first stage of a receiving system makes the major contribution of noise figure to the system, so it is highly desirable that the first stage be a low-noise amplifier with gain. A transmission line is a "lossy" amplifier, and if placed as the first stage of a receiving system, automatically limits the system noise figure to that of the transmission line, *at best*. If the first rf amplifier is placed before the lossy transmission line stage, at the antenna, the amplifier gain will tend to mask the noise added by the transmission line.

### Stability

Excessive amounts of gain or undesired feedback may cause amplifier instability. Oscillation may occur in unstable amplifiers under certain conditions. Damage to the active device due to overdissipation is only the most obvious effect of oscillation. Deterioration of noise figure, spurious signals generated by the oscillation, and reradiation of the oscillation through the antenna, causing interference to other services (i.e., RFI), can also occur from amplifier instability.

Neutralization or other forms of feedback may be required in rf amplifiers to reach stability. Amplifier neutralization is achieved by feeding energy from the amplifier output circuit back to the input in such an amount and phase as to cancel out the effects of device internal capacitance and other unwanted input-output coupling. Care in termination of both the input and output can produce stable results from an otherwise unstable amplifier. Attention to proper grounding and proper isolation of the input from the output by means of shielding also can yield stable operating conditions.

### Overloading and Spurious Signals

Normally, the rf amplifier is not a significant contributor to overloading problems in vhf receiving systems. The rf

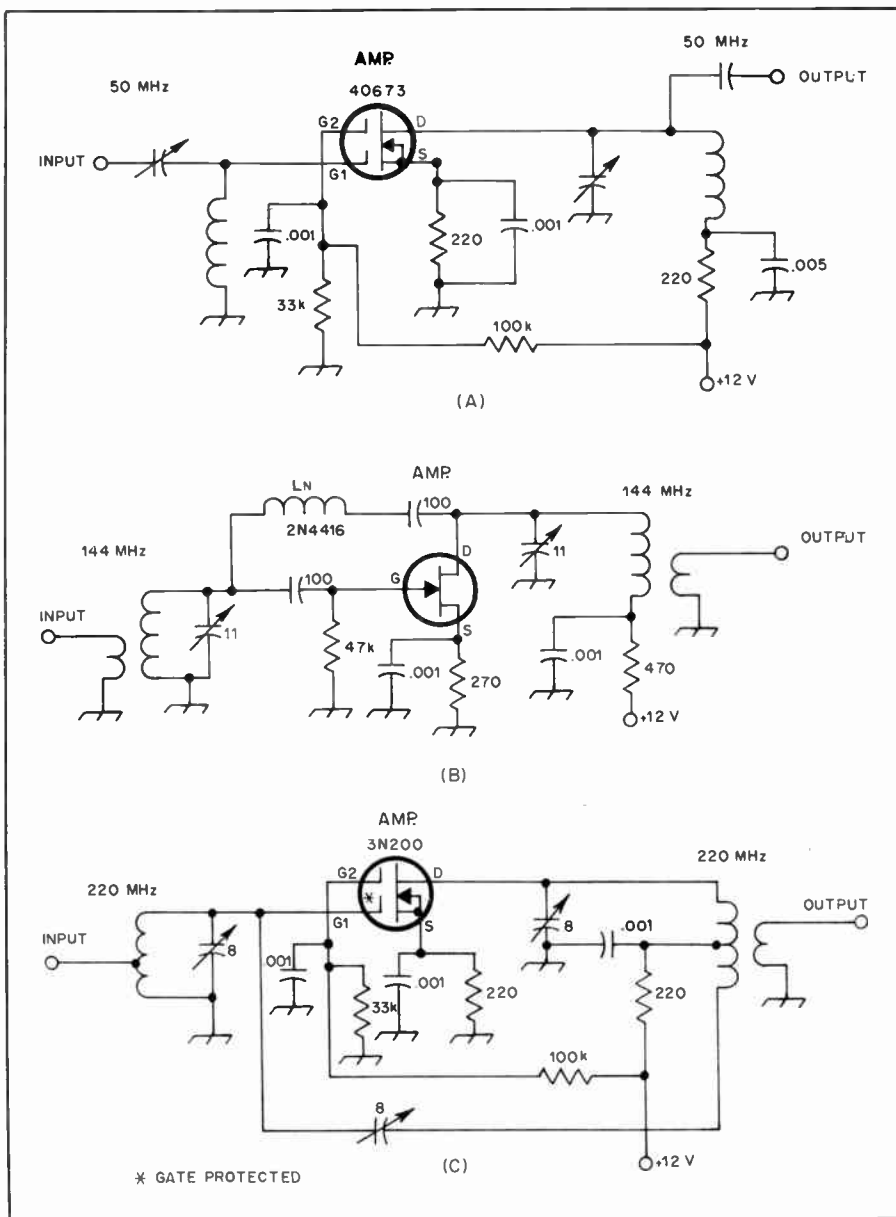


Fig. 1 — Typical grounded-source rf amplifiers. The dual-gate MOSFET, A, is useful below 500 MHz. The junction FET, B, and neutralized MOSFET, C, work well on all vhf bands. Except where given, component values depend on frequency.

amplifiers in the first or second stage of a receiving system operate in a linear service and if properly designed require a substantial signal input to cause deviation from linearity. Overloading usually occurs in the naturally nonlinear mixer stages. Images and other responses to out of band signals can be reduced or eliminated by proper filtering at the amplifier input.

In general, unwanted spurious signals and overloading increase as the signal levels rise at the input to the offending stage. Consequently, minimum gain prior to the stage minimizes overloading. Since noise figure may suffer at reduced gain, a compromise between optimum noise figure and minimum overloading must often be made. Especially in areas of high amateur activity, sacrificing noise figure

somewhat may result in increased weak-signal reception effectiveness if the lower noise-figure system is easily overloaded.

### Typical Circuits

Common circuits for rf amplifiers are illustrated in Figures 1 through 4. Examples of amplifier construction are given later in this chapter. The termination impedance of both the input and output of these examples are low impedance (50 ohms), lending them to preamplifier service. Preamplifiers are useful for improving the noise figure of existing equipment.

The choice of active device has a profound effect on the weak-signal performance of an rf amplifier. Although tubes can be used on the vhf and uhf bands, their use is seldom seen, as

solid-state devices provide far better performance at lower cost. Bipolar transistors can provide excellent noise figures up through 4 GHz if chosen and used properly. The JFET is usable through the 432-MHz band, although the most commonly available ones drop off in performance quickly beyond that frequency. Dual-gate MOSFETs also are usable through 432 MHz. The GaAs FET, though somewhat costly, provides superior noise figures past the 1296 MHz band.

Most rf amplifiers for use below the 432-MHz band use FETs rather than bipolars. Unless bipolar transistors are run at relatively high standing currents they are prone to overloading from strong signals. Additionally, their lower terminating impedances can present somewhat awkward design considerations to the builder. The FET minimizes these problems while presenting acceptable noise figure.

At 432 MHz and above, inexpensive FETs cannot provide the low noise figure attainable from bipolars. The wavelength at these higher frequencies also allows the convenient use of tuned lines rather than conventional coils, easing the possible design difficulties of the lower terminating impedances of bipolars.

The input network of an rf amplifier should be as low in loss as possible, if a low noise figure is desired. Since any loss before the first stage is effectively added to the noise figure, it is well to keep these losses to a minimum. High-selectivity circuits often have significant losses and should be avoided at the front end. L networks usually provide the least loss while assuring proper impedance matching. High-quality components should also be employed in the input circuit to further reduce the losses.

It should be pointed out that the terminating impedance of transistors for optimum noise figure is usually not the same as that for optimum power transfer (gain). This complicates the designing and tuning procedures somewhat, but careful measurements and adjustment can compensate for these shortcomings. The dual-gate MOSFET has different internal geometry, so optimum noise match is virtually identical to optimum gain match. This means that adjusting a dual-gate MOSFET amplifier for maximum gain usually provides best noise figure.

Some examples of common-source amplifiers are shown in Fig. 1. Many properly designed dual-gate MOSFET amplifiers do not require neutralization to achieve stability and best noise figure. An example of this approach is shown in Fig. 1A. Neutralization may be required; Fig. 1C shows capacitive neutralization applied to dual-gate MOSFET amplifier. Common-source JFET amplifiers usually require neutralization to attain satisfactory operation. Inductive neutralization as shown in Fig. 1B is commonly used.

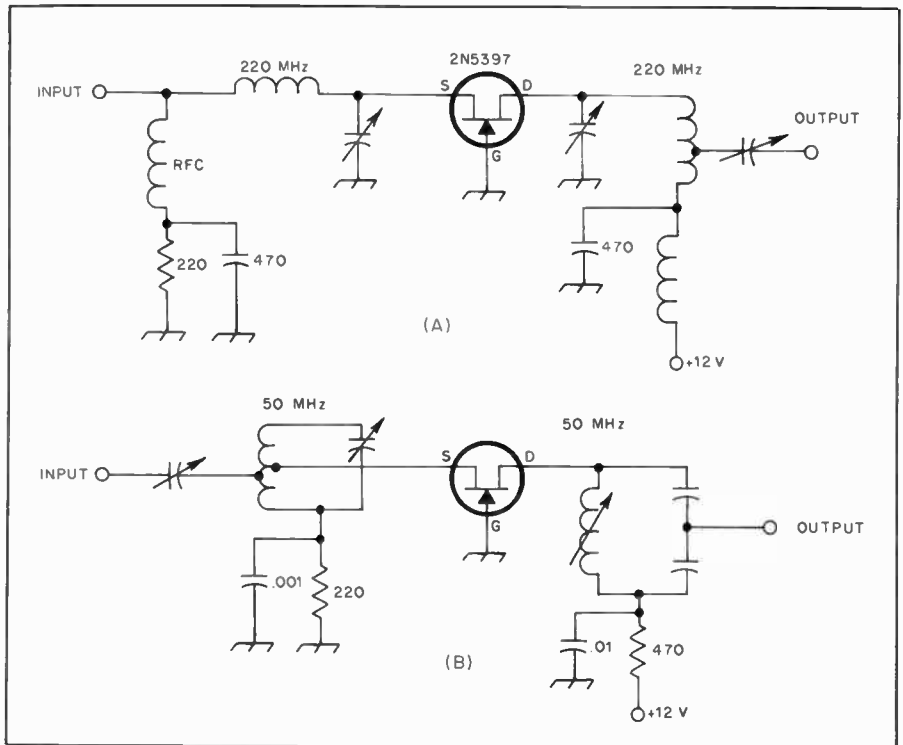


Fig. 2 — Grounded-gate FET preamplifier tends to have lower gain and broader frequency response than other amplifiers described.

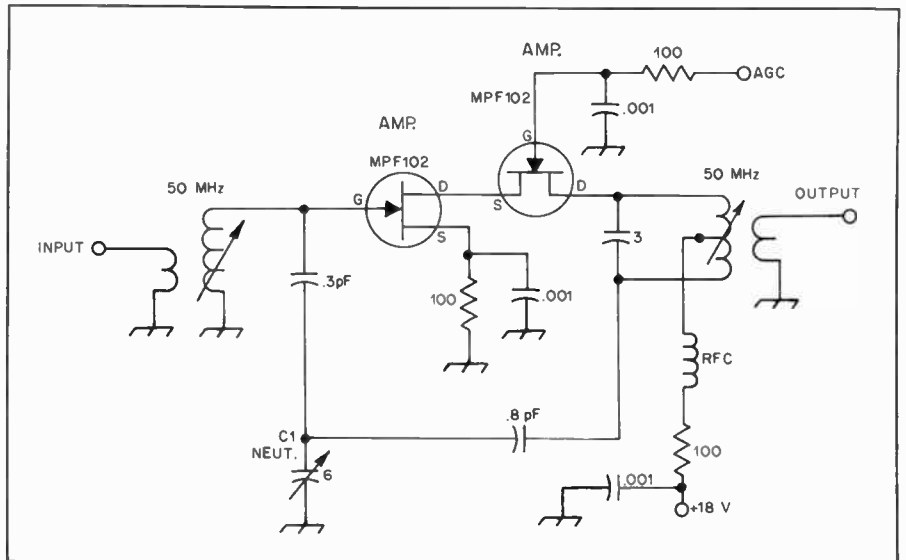


Fig. 3 — Cascode amplifier circuit combines grounded-source and grounded-gate stages, for high gain and low noise figure. Though JFETs are shown, the cascode principle is useful with MOSFETs as well.

Using the gate as the common stage element introduces negative feedback and eliminates the need for neutralization in a common-gate amplifier, shown in Fig. 2. The feedback reduces the stage gain and lowers the input impedance, increasing the bandwidth of the stage. An additional benefit of common-gate amplifiers is reduced susceptibility to overload as compared to common-source amplifiers.

The cascode circuit of Fig. 3 combines the common-source and the common-gate amplifiers, securing some of the ad-

vantages of each. Increased gain over a single stage is its greatest asset.

Fig. 4 shows typical bipolar amplifiers for the uhf range. Fig. 4A illustrates a common-emitter amplifier, analogous to the common-source FET amplifier. The common-base amplifier of Fig. 4B can similarly be compared to a common-gate FET amplifier.

#### Front-End Protection

The first amplifier of a receiver is susceptible to damage or complete burnout

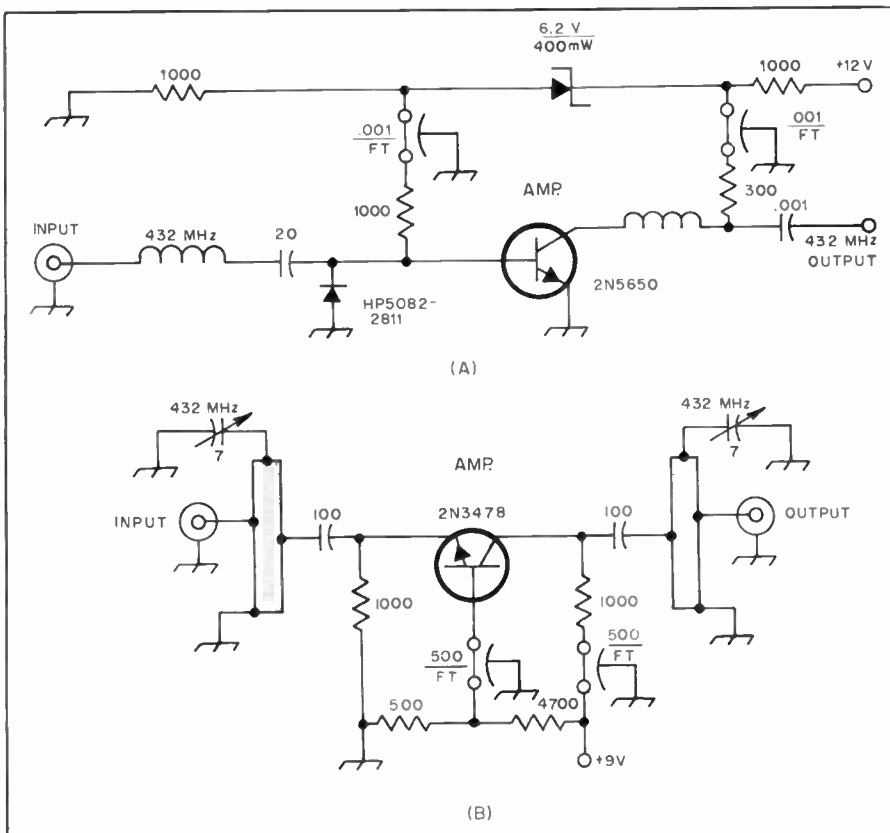


Fig. 4 — Examples of uhf amplifiers using bipolar transistors.

through application of excessive voltage to its input element by way of the antenna. This can be the result of lightning discharges (not necessarily in the immediate vicinity), rf leakage from the station transmitter through a faulty send-receive relay or switch, or rf power from a nearby transmitter and antenna system. Bipolar transistors often used in low-noise uhf amplifiers are particularly sensitive to this trouble. The degradation may be gradual, going unnoticed until the receiving sensitivity has become very poor.

No equipment is likely to survive a direct hit from lightning, but casual damage can be prevented by connecting diodes back-to-back across the input circuit. Either germanium or silicon vhf diodes can be used. Both have thresholds of conduction well above any normal signal level, about 0.2 volt for germanium and 0.6 volt for silicon. The diodes used should have fast switching times. Computer diodes such as the 1N914 and hot-carrier types are suitable. A check on weak-signal reception should be made before and after connection of the diodes.

### RF Selectivity

Ever-increasing occupancy of the radio spectrum brings with it a parade of receiver overload and spurious responses. Overloading problems can be minimized by the use of high dynamic range receiving techniques, but spurious responses such as

the receive image must be filtered out before mixing occurs. Conventional tuned circuits cannot provide the selectivity necessary to eliminate the plethora of signals found in most ham neighborhoods. Other filtering techniques must be used.

Although some amateurs use quarter-wavelength coaxial cavities on 50, 144 and 220 MHz, the helical resonators shown in Fig. 5 are usually a better choice as they are smaller and easier to build. In the frequency range from 30 to 100 MHz, where it's difficult to build high-Q inductors, and because coaxial cavities are very large, the helical resonator is an excellent choice. At 50 MHz, for example, a capacitance-tuned, quarter-wavelength coaxial cavity with an unloaded Q of 3000 would be about 4 inches (100 mm) in diameter and nearly 5 feet (1.5 m) long. On the other hand, a helical resonator with the same unloaded Q is about 8.5 inches (216 mm) in diameter and 11.3 inches (287 mm) long. Even at 432 MHz, where coaxial cavities are common, the use of a helical resonator will result in substantial size reductions. The following design information on helical resonators originally appeared in a June 1976 *QST* article by WJHR.

The helical resonator has often been described simply as a coil surrounded by a shield, but it is actually a shielded, resonant section of helically wound transmission line with relatively high characteristic impedance and low axial

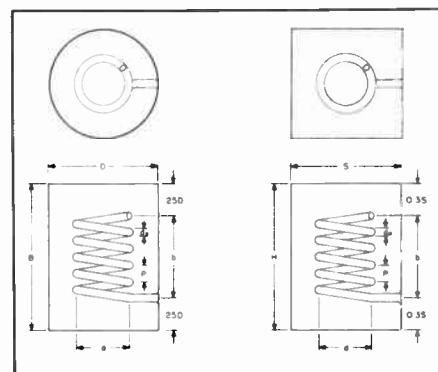


Fig. 5 — Round and square helical resonators, showing principal dimensions. Diameter, D (or side, S) is determined by the desired unloaded Q. Other dimensions are expressed in terms of D (or S) as described in the text.

propagation velocity. The electrical length is about 94 percent of an axial quarter wavelength, or 84.6 electrical degrees. One lead of the helical winding is connected directly to the shield and the other end is open circuited as shown in Fig. 5. Although the shield may be any shape, only round and square shields will be considered in this section.

### Design

The unloaded Q of a helical resonator is determined primarily by the size of the shield. For a round resonator with a copper coil on a low-loss form, mounted in a copper shield, the unloaded Q is given by

$$Q_u = 50D \sqrt{f_o}$$

where D = inside diameter of the shield in inches ( $\times 2.54 = \text{mm}$ )

$f_o$  = frequency in MHz

If the shield can is square, assume D to be 1.2 times the width of one side. This formula, which includes the effects of losses and imperfections in practical materials, yields values of unloaded Q which are easily attained in practice. Silver plating of the shield and coil will increase the unloaded Q by about three percent over that predicted by the equation. At vhf and uhf, however, it is more practical to increase slightly the shield size (i.e., increase the selected  $Q_u$  by about three percent before making the calculation). The fringing capacitance at the open-circuited end of the helix is about  $0.15D$  pF (i.e., approximately 0.3 pF for a shield two inches, or 51 mm, in diameter).

Once the required shield size has been determined, the total number of turns, N, winding pitch, P, and characteristic impedance,  $Z_o$ , for round and square helical resonators with air dielectric between the helix and shield, are given by

$$N = \frac{1908}{f_o D} \quad N = \frac{1590}{f_o S} \quad P = \frac{f_o D^2}{2312} f_o$$

$$Z_o = \frac{99,000}{f_o D} \quad Z_o = \frac{82,500}{f_o S} \quad P = \frac{f_o S^2}{1606}$$



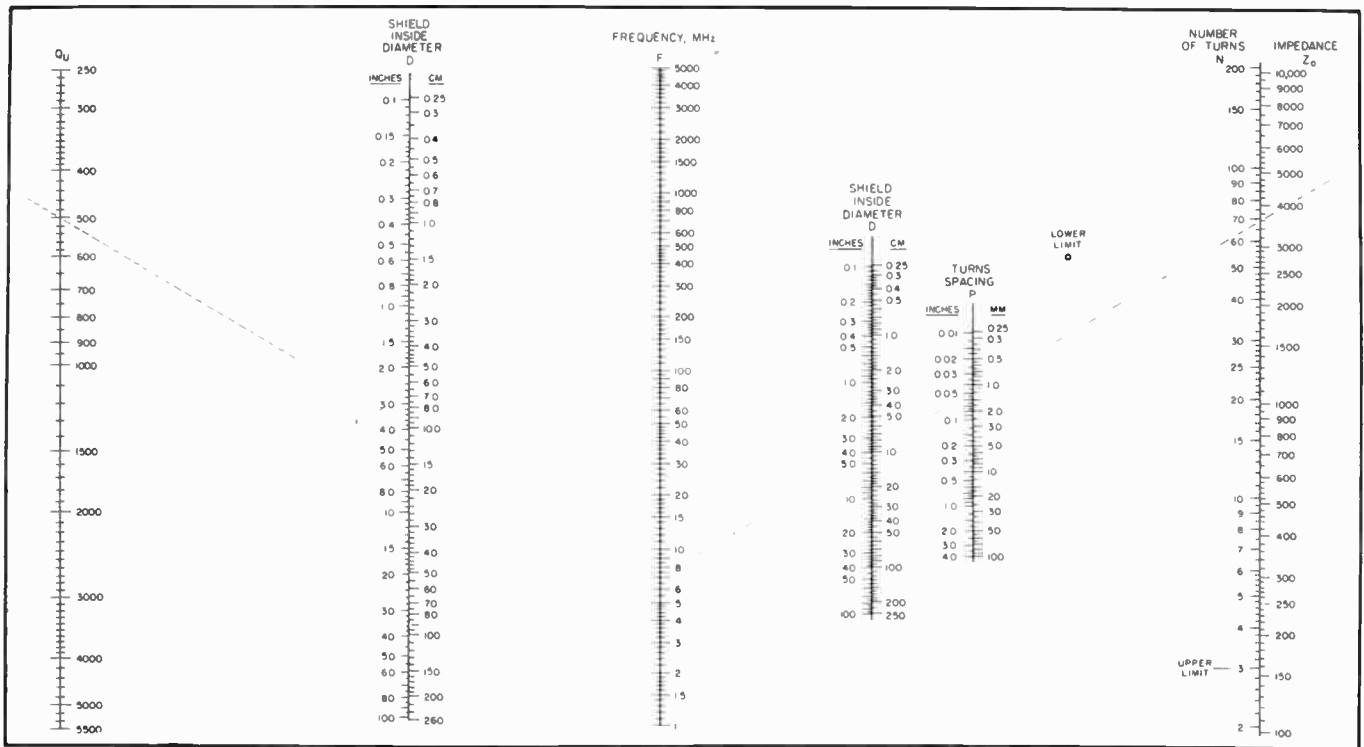


Fig. 6 — Design nomograph for round helical resonators. After selecting unloaded  $Q_u$ , required shield diameter is indicated by index line from  $Q_u$  scale to frequency scale (dashed index line shown here indicates a shield of about 3.8 inches (97 mm) for an unloaded  $Q$  of 500 at 7 MHz). Number of turns,  $N$ , winding pitch,  $P$ , and characteristic impedance,  $Z_0$ , are determined by index line from the frequency scale through previously determined shield diameter on right-hand side of the chart (index line indicates  $P = 0.047$  inch, 1 mm,  $N = 70$  turns, and  $Z_0 = 3600$  ohms).

In these equations dimensions  $D$  and  $S$  are in inches, and  $f_0$  is in MHz. The design nomograph for round helical resonators in Fig. 6, which can be used with slide-rule accuracy, is based on these formulas.

Although there are many variables to consider when designing helical resonators, certain ratios of shield size and length, and coil diameter and length, will provide optimum results. For helix diameter,  $d = 0.55D$ , or  $d = 0.66S$ . To determine helix length,  $b = 0.825E$  or ( $b = 0.99S$ ). For shield length,  $B = 1.325D$  and  $H = 1.60S$ .

Calculation of these dimensions is simplified by the design chart of Fig. 7. Note that these ratios result in a helix with a length 1.5 times its diameter, the condition for maximum  $Q$ . The shield is about 60 percent longer than the helix — although it can be made longer — to completely contain the electric field at the top of the helix and the magnetic field at the bottom.

It should be mentioned that the winding pitch,  $P$ , is used primarily to determine the required conductor size. During actual construction the length of the coil is adjusted to that given by the equations for helix length. Conductor size ranges from  $0.4P$  to  $0.6P$  for both round and square resonators and is plotted graphically in Fig. 8.

Obviously, an area exists (in terms of frequency and unloaded  $Q$ ) where the designer must make a choice between a conventional cavity (or lumped LC cir-

cuit) and a helical resonator. At the higher frequencies, where cavities might be considered, the choice is affected by shape factor; a coaxial resonator is long and relatively small in diameter, while the length of a helical resonator is not much greater than its diameter. A second consideration is that point where the winding pitch,  $P$ , is less than the radius of the helix (otherwise the structure tends to be nonhelical). This condition occurs when the helix has less than three turns ("upper limit" on the design nomograph of Fig. 6).

### Construction

To obtain as high an unloaded  $Q$  as possible, the shield should not have any seams parallel to the axis of the helix. This is usually not a problem with round resonators because large-diameter copper tubing is used for the shield, but square resonators require at least one seam and usually more. However, the effect on unloaded  $Q$  is minimal if the seam is silver soldered carefully from one end to the other.

Best results are obtained when little or no dielectric is used inside the shield. This is usually no problem at vhf and uhf because the conductors are large enough that a supporting coil form is not required. The lower end of the helix should be soldered to the inside of the shield at a point directly opposite from the bottom of the coil.

Although the external field is mini-

mized by the use of top and bottom covers, the top and bottom of the shield may be left open with negligible effect on frequency or unloaded  $Q$ . If covers are provided, however, they should make good electrical contact with the shield. In those resonators where the helix is connected to the bottom cover, that cover must be soldered solidly to the shield to minimize losses.

### Tuning

A helical resonator designed from the nomograph of Fig. 6, if carefully built, will resonate very close to the design frequency. Resonance can be adjusted over a *small* range by slightly compressing or expanding the helix. If the helix is made slightly longer than that called for in Fig. 7, the resonator can be tuned by pruning the open end of the coil. However, neither of these methods is recommended for wide frequency excursions because any major deviation in helix length will degrade the unloaded  $Q$  of the resonator.

Most helical resonators are tuned by means of a brass tuning screw or high quality air-variable capacitor across the open end of the helix. Piston capacitors also work well, but the  $Q$  of the tuning capacitor should ideally be several times the unloaded  $Q$  of the resonator. Varactor diodes have sometimes been used where remote tuning is required, but varactors can generate unwanted harmonics and other spurious signals if they are excited by strong, nearby signals.



When a helical resonator is to be tuned by a variable capacitor, the shield size is based on the chosen unloaded Q at the operating frequency. Then the number of turns, N and the winding pitch, P, are based on resonance at  $1.5f_o$ . Tune the resonator to the desired operating frequency,  $f_o$ .

### Insertion Loss

The insertion loss (dissipation loss), IL, in dB, of all tuned resonant circuits is given by

$$IL = 20 \log \left( \frac{1}{1 - Q_d/Q_u} \right) \text{ dB}$$

where  $Q_d$  = loaded Q

$Q_u$  = unloaded Q

This is plotted in Fig. 9. For most practical cases ( $Q_d > 5$ ) this can be closely approximated by  $IL \cong 9.0(Q_d/Q_u)$  dB. The selection of a loaded Q for a tuned circuit is dictated primarily by the required selectivity of the circuit. However, to keep dissipation loss to 0.5 dB or less (as is the case for low-noise vhf receivers), the unloaded Q must be at least 18 times the loaded Q. Although this may be difficult to achieve in practice, it points up the necessity of considering both selectivity and insertion loss before choosing the unloaded Q of any resonant tuned circuit.

### Coupling

Signals may be coupled into and out of helical resonators with inductive loops at the bottom of the helix, capacitive probes at the top of the helix, direct taps on the coil, or any combination of these. Although the correct tap point can be calculated easily, coupling by loops and probes must be determined experimentally. When only one resonator is used, the input and output coupling is often provided by probes. For maximum isolation the probes are positioned on opposite sides of the resonator.

When coupling loops are used, the plane of the loop should be perpendicular to the axis of the helix and separated a small distance from the bottom of the coil. For resonators with only a few turns, the plane of the loop can be tilted slightly so it is parallel with the slope of the adjacent conductor. Helical resonators with inductive coupling (loops) will exhibit more attenuation to signals above the resonant frequency (as compared to attenuation below resonance) whereas resonators with capacitive coupling (probes) exhibit more attenuation below the passband as shown for a typical 432-MHz resonator in Fig. 10. This characteristic may be a consideration when choosing a coupling method. The passband can be made more symmetrical by using a combination of coupling methods (inductive input and capacitive output, for example).

If more than one helical resonator is required to obtain a desired bandpass

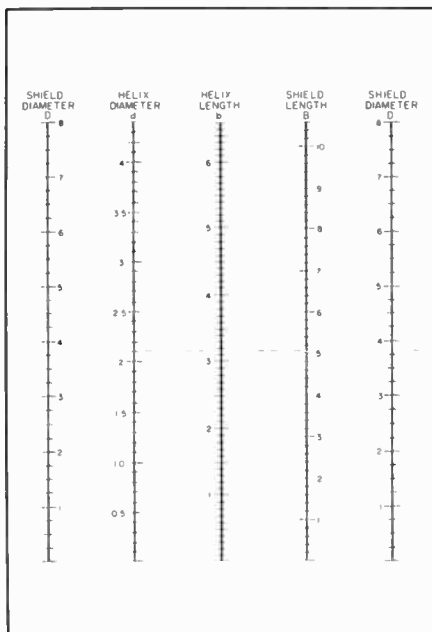


Fig. 7 — Helical-resonator design chart. After the shield diameter has been determined, helix diameter, d, helix length, b, and shield length, B, can be determined with this graph. Index line indicates that a shield diameter of 3.8 inches (97 mm) requires helix mean diameter of 2.1 inches (53 mm), helix length of 3.1 inches (79 mm), and shield length of 5 inches (127 mm).

characteristic, adjacent resonators may be coupled through apertures in the shield wall between the two resonators. Unfortunately, the size and location of the aperture must be found empirically, so this method of coupling is not very practical unless you're building a large number of identical units.

Since the loaded Q of a resonator is determined by the external loading, this must be considered when selecting a tap (or position of a loop or probe). The ratio of this external loading,  $R_b$ , to the characteristic impedance,  $Z_o$ , for a quarter-wavelength resonator is calculated from

$$K = \frac{R_b}{Z_o} = 0.785 \left( \frac{1}{Q_d} - \frac{1}{Q_u} \right)$$

Even when filters are properly designed and built, they may be rendered totally ineffective if not installed properly. Leakage around a filter can be quite high at vhf and uhf where wavelengths are short. Proper attention to shielding and good grounding is mandatory for minimum leakage. Poor coaxial cable shield connection into and out of the filter is one of the greatest offenders with regard to filter leakage. Proper dc lead bypassing throughout the receiving system is good practice, especially at vhf and above. Ferrite beads placed over the dc leads may help to reduce leakage even further.

Proper termination of a filter is a necessity if minimum loss is desired from the filter. Most vhf rf amplifiers optimized for noise figure do not have a 50-ohm

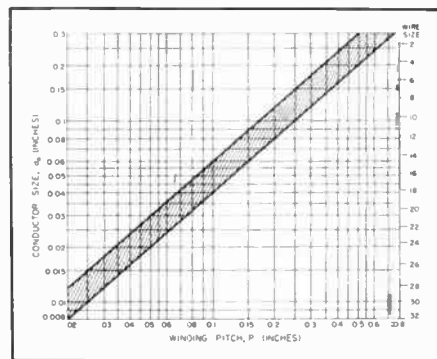


Fig. 8 — Helix conductor size vs. winding pitch, P. A winding pitch of 0.047 inch (1 mm), for example, dictates a conductor diameter between 0.019 and 0.028 inch (number 22 or 24 AWG).

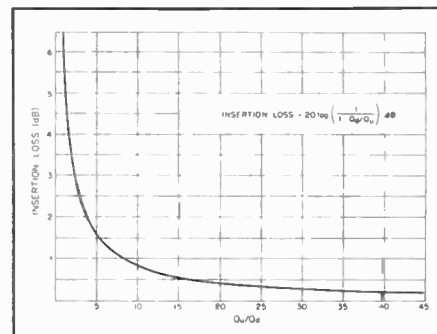


Fig. 9 — Insertion loss of all tuned resonant circuits is determined by the ratio of loaded to unloaded Q as shown here.

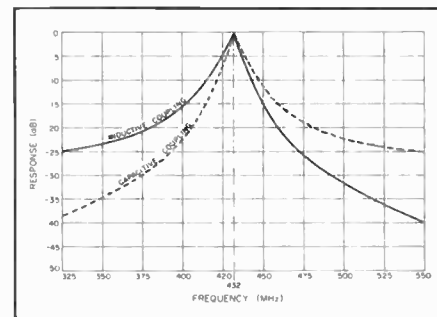


Fig. 10 — Response curve for a single-resonator 432-MHz filter showing the effects of capacitive and inductive input/output coupling. Response curve can be made symmetrical on each side of resonance by combining the two methods (inductive input and capacitive output or vice versa).

terminating input impedance. As a result, any filter attached to the input of an rf amplifier optimized for noise figure will not be properly terminated, and the filter's loss may rise substantially. As this loss is directly added to the rf amplifier's noise figure, prudent consideration should be made of filter choice and placement in the receiver.

### Mixers

Conversion of the received energy to a lower frequency, so that it can be amplified more efficiently than would be

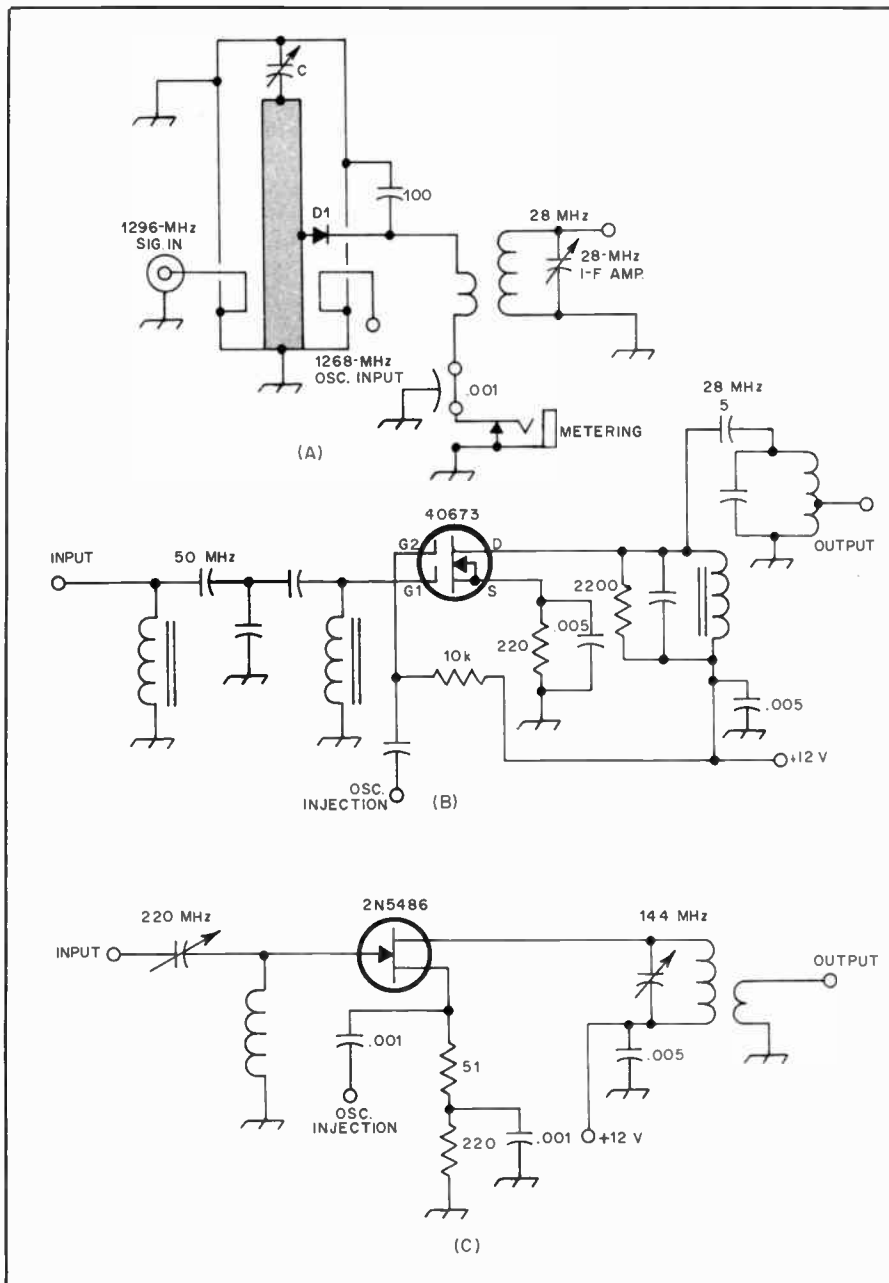


Fig. 11 — Examples of single-ended mixers. The diode mixer, A, is usable through the microwave region. FET mixers, B and C, offer conversion gain and low noise figure.

possible at the signal frequency, is a basic principle of the superheterodyne receiver. The stage in which this is done may be called a "converter," or "frequency converter," but we will use the more common term, *mixer*, to avoid confusion with *converter*, as applied to a complete vhf receiving accessory. Mixers perform similar functions in both transmitting and receiving circuits, and mixer theory and practice are treated in considerable detail elsewhere in this *Handbook*.

A receiver for 50 MHz or higher usually has at least two such stages; one in the vhf or uhf converter, and usually two or more in the communications receiver that follows it. We are concerned here with the first mixer.

The ideal mixer would convert any

signal input to it to another chosen frequency with no distortion, and would have a noise figure of 0 dB. Unfortunately a mixer such as that only exists in a dream world. The mixer that has a 0 dB noise figure (or equivalent loss) has yet to be conceived. This means that the proper use of rf amplification and perhaps post-mixer amplification is necessary for maximum receiver performance with regard to sensitivity. Improving sensitivity is the less difficult of the mixer failings to mend.

Because the mixer operates in a nonlinear mode, reduction of distortion becomes a major design problem. As the mixer input level is increased, a point is reached where the output no longer increases linearly with input. A phe-

nomenon known as *compression* occurs. When the compression point is reached, the sensitivity of the mixer is reduced for every signal in the passband. This is manifested as desensing. Different types of mixers characteristically reach their compression points at different input levels, so proper mixer choice can minimize this type of distortion. Any amplifier before the mixer will increase the input levels to the mixer, lowering the point where the input level to the receiving system will cause compression. It behooves the builder not to use more gain than is necessary to establish system noise figure prior to the mixer.

If more than one signal is present in the passband going into the mixer, they may mix with each other to produce spurious responses known as intermodulation distortion (IMD) products. As the input levels further increase, higher-order IMD products may appear, seemingly filling the passband. Proper mixer operating conditions will alleviate IMD problems, and also reduce gain-compression problems.

A third type of distortion is *cross modulation*. This is most readily observed on a-m signals. When the carrier is on, cross modulation is evidenced by modulation characteristics of another signal being superimposed on the received carrier. Techniques to improve IMD characteristics also improve cross modulation performance.

A problem inherent to all mixing systems is *image* generation. Whenever two signals are mixed, components are produced at the sum and difference of the two signal frequencies, and at multiples of these frequencies. For receiving applications, amateurs typically want to detect only one of the mixing products, usually the first order mixing product. Filtering must be applied to separate the desired signal from the rest. Post-mixer filtering is not adequate, as input images can be mixed to the same intermediate frequency as the desired signal. Input filtering discriminates against these images and prevents unwanted out-of-band signals from possibly overloading the mixer.

### Single-ended Mixers

Most mixers are single-ended. The simplest type of mixer is the diode mixer. The signal and the heterodyning frequency are fed into the mixer and the mixer output includes both the sum and difference frequencies of the two. In the case of the circuit shown in Fig. 11A the difference frequency is retained, so the 1296-MHz input signal is converted down to 28 MHz. The sum frequency is filtered out by the 28-MHz tuned circuits.

A quality diode (such as the hot-carrier type) has a fairly low noise figure up through the microwave region. Since most active mixers fall off in performance above 500 MHz, the diode mixer is the

one most commonly found in amateur microwave service. Unfortunately, all diode mixers have conversion loss. The loss must be added to the noise figure of the stage following the mixer to determine the system noise figure. A low-noise stage following the mixer is necessary for good weak-signal reception. The noise figure of most communications receivers is far higher than what is needed for a low noise figure system, if no rf amplification is used.

Bipolar transistors are not good square-law type devices, and thus are not favored for single-ended applications. Their major use is in switching-type mixers of the balanced variety.

Field-effect transistors have good square-law response and are very popular vhf mixers. The dual-gate MOSFET is probably the most common mixer found in vhf amateur equipment. The MOSFET can provide considerable conversion gain, while at the same time maintaining a reasonable noise figure. MOSFET overload characteristics are suitable for the vast majority of applications. Local-oscillator energy can be applied at one of the MOSFET gates, effectively isolating the local oscillator from the other signals. The gate impedance is high, so relatively little injection is needed for maximum conversion gain. A typical example is shown in Fig. 11B.

JFETs are close to the MOSFET in mixer performance but are more difficult to apply in practical hardware. As with the MOSFET, input impedance to a JFET mixer is high, and substantial conversion gain is available. JFET bias for mixer service is critical and must be adjusted for best results. The output impedance of a JFET is lower than a dual-gate MOSFET; typically around 10 k $\Omega$ . Although other possibilities exist, local-oscillator injection should be made at the JFET source for best results. The source is a low-impedance point, so considerably more local-oscillator power is required than if a dual-gate MOSFET were used as mixer. Noise figures as low as 4 dB are possible with circuits like that shown in Fig. 11C.

The injection level of the local oscillator affects mixer performance. Raising LO level increases conversion gain in an FET mixer. The local-oscillator signal should be as large as possible without pushing the FET into its pinchoff region. The gate junction of the FET should never conduct in mixer applications. Increased IMD products result from either of the aforementioned conditions and should be carefully avoided. The local-oscillator energy should be as pure as possible. Distorted injection energy not only increases IMD production but also increases stage noise figure.

Proper termination of the output of an FET mixer optimizes overload performance. If the impedance seen at the drain of an FET mixer is too high at any of

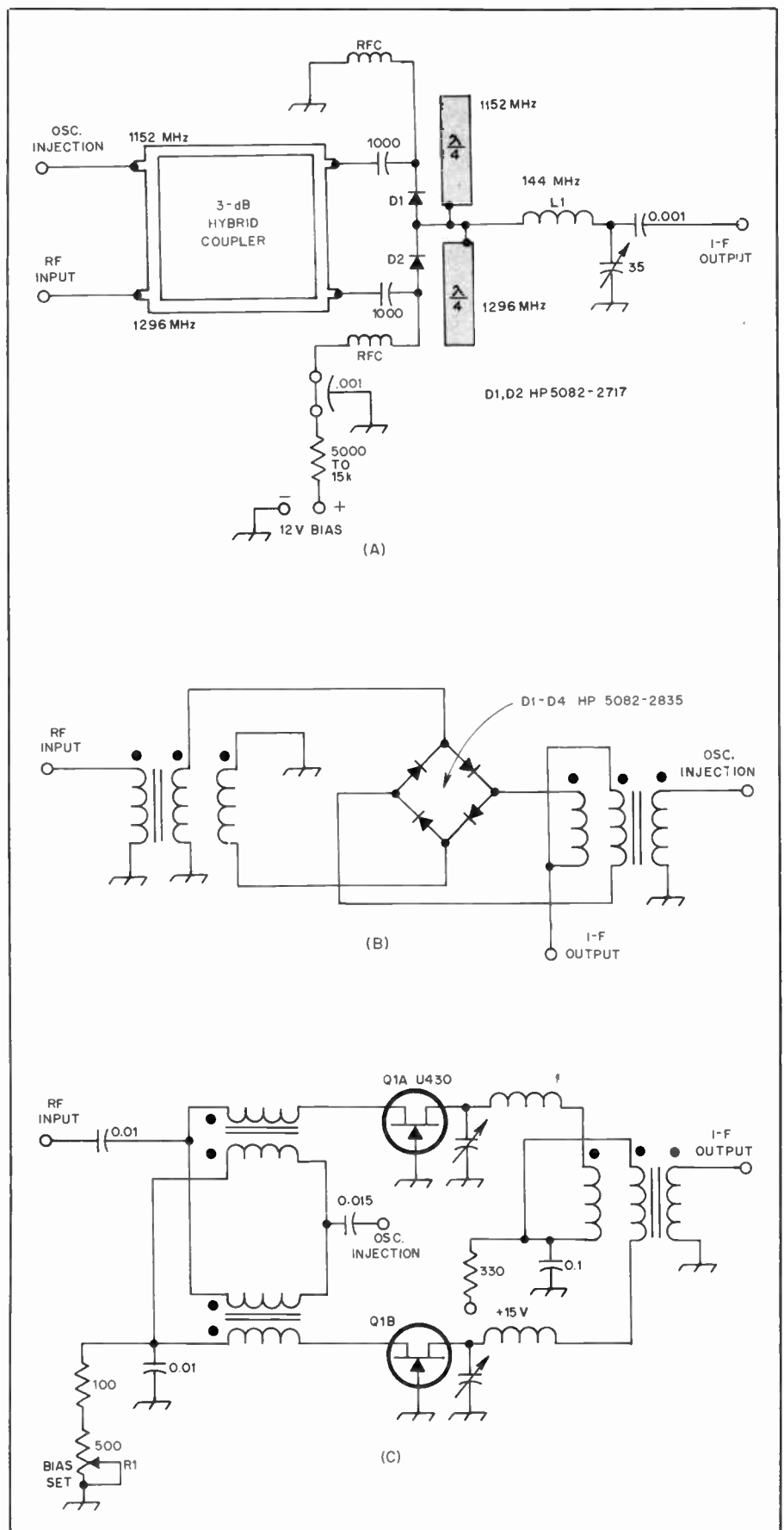


Fig. 12 — Balanced mixers for vhf and uhf. The singly balanced mixer, A, provides isolation of the local oscillator from the output. The doubly balanced diode mixer, B, has all ports isolated from each other, and is broadband throughout vhf. A special dual JFET is used in C to give high dynamic range with low noise figure.



the mixer product frequencies, large voltage excursions can occur on the FET drain. If the voltage excursion on the drain is large enough, output distortion will be evident. Often these high-voltage excursions occur at frequencies outside the desired passband, causing distortion from signals not even detectable by the receiver. A resistor within the output matching network is often used to limit the broadband impedance to a suitably low level.

### Balanced Mixers

Use of more than one device in either a singly or doubly balanced mixer offers many advantages over a single-ended mixer. The balance prevents energy injected into a mixer port from re-appearing at another port. The implications of this are significant when minimum mixer distortion is sought. The port-to-port isolation inhibits any signals other than the mixing products from reaching any other stages further along in the system where they might be mixed, causing undesirable signals. The usually large local-oscillator signal is kept away from the rf amplifier stages where it might cause gain compression because of its magnitude. Any amplitude-modulated noise found on the local-oscillator signal is suppressed from the mixer output, where it might be later detected. In a singly balanced mixer only one port, usually the local-oscillator input, is isolated from the other two. A doubly balanced mixer isolates all three ports from each other.

The most common balanced mixer uses diodes. The disadvantages presented earlier with respect to single-ended diode mixers apply here also. A singly balanced diode mixer is shown in Fig. 12A. Hot-carrier diodes are normally used for D1 and D2, as they can handle high currents, have a low noise figure, and are available for use up through several gigahertz.

The doubly balanced mixer is more common today. Commercial modules, very reasonably priced, are often used instead of homemade circuits. Large-scale manufacturing can usually offer electrical balance not so easily attained with the homemade units. Isolation of 35 to 40 dB is typical at vhf, with only 6 to 7 dB of conversion loss. High local-oscillator injection is needed to reach optimum performance with these mixers. Proper broadband termination of all the mixer ports is necessary to prevent unwanted signals from being reflected back into the mixer "rat race," only to emerge at another port. The i-f port (shown in Fig. 12B) is the most critical with respect to termination and should be terminated at  $50 + j0$  ohms. Transmission line transformers provide the necessary phase shift, as half the bridge is fed 180 degrees out of phase with respect to the other half. These can be wound on ferrite toroid forms to

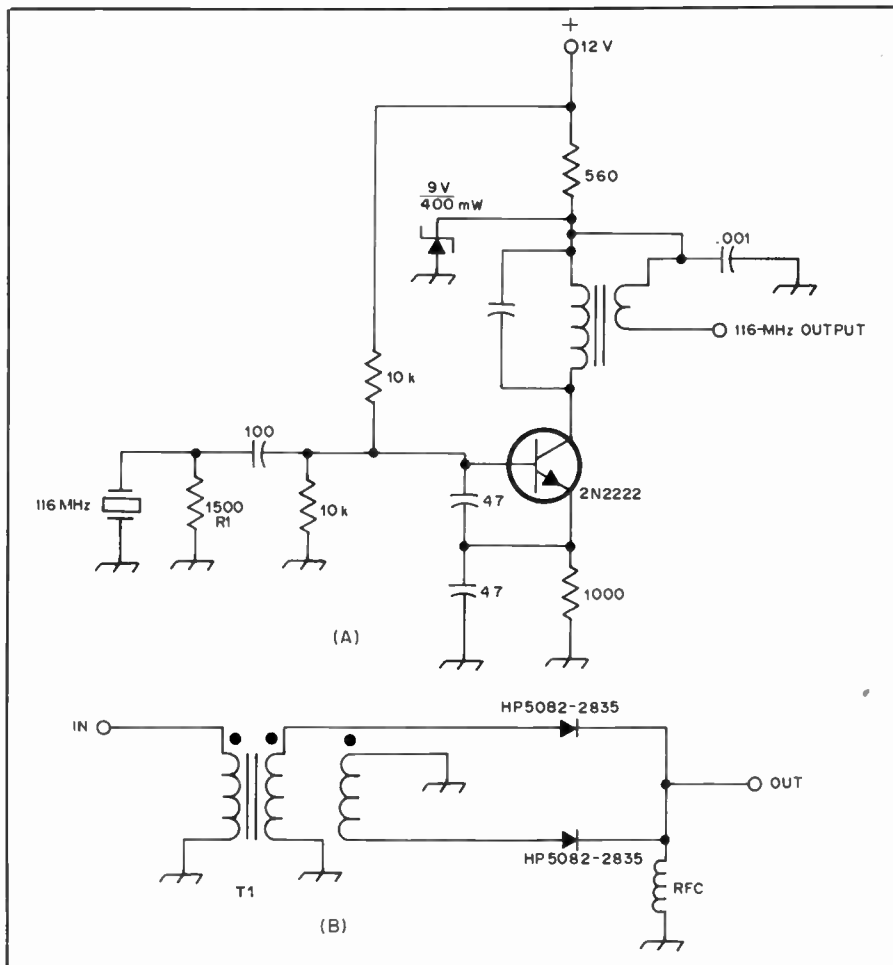


Fig. 13 — Typical crystal oscillator for vhf use. A. The diode frequency doubler. B. provides good rejection of the fundamental signal.

effect a broadband response. Careful winding of the transformers improves balance in the circuit, which in turn improves port-to-port isolation.

Active devices can be used very effectively in balanced mixers. Both FETs and bipolars can be used successfully. Active balanced mixers offer all the benefits of balanced diode mixers plus the added advantage of conversion gain rather than loss. Less rf amplification is needed to establish low system noise figure because of this conversion gain than would be needed with a diode mixer. Low gain prior to the mixer keeps mixer input levels low, maximizing mixer overload resistance. High dissipation active devices can be used, yielding better mixer performance than is available from diode balanced mixers. Fig. 12C shows a dual FET which has been specially designed for mixer applications. R1 allows for electrical balance adjustment in the circuit. A sharp null in local oscillator output at the mixer output can be observed when R1 is set to the optimum point, showing electrical balance has been achieved.

### Injection Stages

Oscillator and multiplier stages supplying heterodyning energy to the mixer

should be as stable and free of unwanted frequencies as possible. Proper application of crystal control gives stability pursuant to needs. Two major influencing factors control oscillator stability, temperature and operating voltage. As the temperature of a component changes, its internal geometry changes somewhat as the constituent materials expand or contract. When the geometry changes, the internal capacitance often changes, affecting the resonant frequency of the tuned circuits controlling oscillator frequency. Use of quality components which have good temperature characteristics helps in this regard. Minimum power should be extracted from the oscillator as excessive heat dissipation within either the crystal or the transistor will cause internal capacitance changes in those units, moving the resonant frequency. Voltage to the transistor should be regulated for best stability. Simple Zener diode regulation is sufficient or a three-terminal regulator IC can be used.

Any unwanted injection frequencies will mix with signals present in the mixer, creating spurious outputs at the mixer output. A clean local oscillator will prevent these unwanted outputs. The oscillator chain output can be heavily



filtered to cut down the harmonic content of the oscillator, but good planning and design will minimize the unwanted energy, making the filter job less demanding. A high-frequency crystal in the oscillator minimizes the number of times the fundamental oscillator frequency has to be multiplied to reach the converter injection frequency. Proper use of doublers rather than triplers can eliminate any odd oscillator frequency multiples, so a low-pass filter at the output only has to filter the fourth harmonic and beyond. A band-pass filter would be needed at the output of a tripler to eliminate the second harmonic and the higher ones. Finally, good shielding and power-line filtering should be used throughout to prevent any stray radiation from reaching the mixer or causing RFI problems elsewhere.

Fig. 13A shows a typical circuit useful for providing the 116-MHz injection energy necessary to convert a 144-MHz signal down to 28 MHz. R1 dampens the crystal action somewhat, assuring that the proper overtone is the actual oscillation frequency. The collector tank network is parallel tuned and can be wound on a toroid core to reduce radiation. The output is link coupled from the tank, minimizing harmonic coupling. This oscillator would be followed by a buffer to bring the signal up to that level needed and to purify the oscillator signal further.

A similar oscillator could be used in a 220-MHz converter. Since crystals are not available at 192 MHz, the frequency required for conversion to 28-MHz converter output, the most logical approach is to use a 96-MHz oscillator and double its output. Fig. 13B shows a diode frequency doubler suitable for the application. The phase-shifting transformer can be made from a trifilar winding on a ferrite core. Hot-carrier diodes allow the use of a doubler like this up through at least 500 MHz. There is a loss of about 8 dB through the doubler, so amplification is needed to bring the injection signal to the appropriate level. Fundamental energy is down by as much as 40 dB from the second harmonic with a balanced diode doubler such as this. All the odd harmonics are well down in amplitude also, all without tuned circuits. A low-pass filter can be used to eliminate the undesired harmonics from the output.

### MOSFET Preamplifiers for 10, 6 and 2 Meters

If an hf or vhf receiver lacks gain, or has a poor noise figure, an external preamplifier can improve its ability to detect weak signals. This preamplifier uses an RCA 40673 dual-gate MOSFET. Designs for using this device as a mixer or as a preamplifier abound and many of them are excellent.

When it comes to simplicity, small size, good performance, low cost, and flexibility, a design by Gerald C. Jenkins,

W4CAH, certainly qualifies.

The preamplifier really shines in pepping up the performance of some of the older 10-meter receivers that many have pressed into service. A 6-meter version is also very useful for any of the modes of communication available on that band.

In Fig. 15 the voltage dropping resistor, R4 and the Zener diode, D1, may be of the value necessary to obtain 9 to 12 V dc for operation of the unit. By increasing the resistance and dissipation rating of R4 and D1, the preamplifier may be operated from the 150- to 200-V supply found in many tube-type receivers.

The layout of the board is so simple that it is hardly worth the effort of making a negative for the photo-etch process. A Kepro resist-marking pen was used with

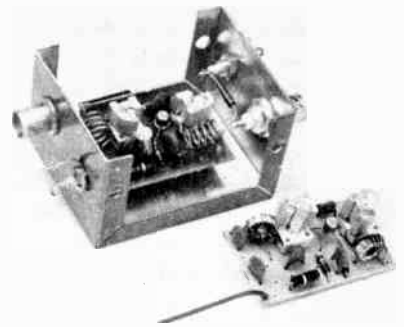


Fig. 14 — Two versions of the preamplifier. The one in the box is for 2-meter use. Toroids are used in the six-meter version (right) and in the ten-meter preamplifier (not shown). Input is at the right on both units. The extra rf choke and feedthrough capacitor on the right end of the Minibox are for decoupling a crystal-current metering circuit that is part of a 2304-MHz mixer.

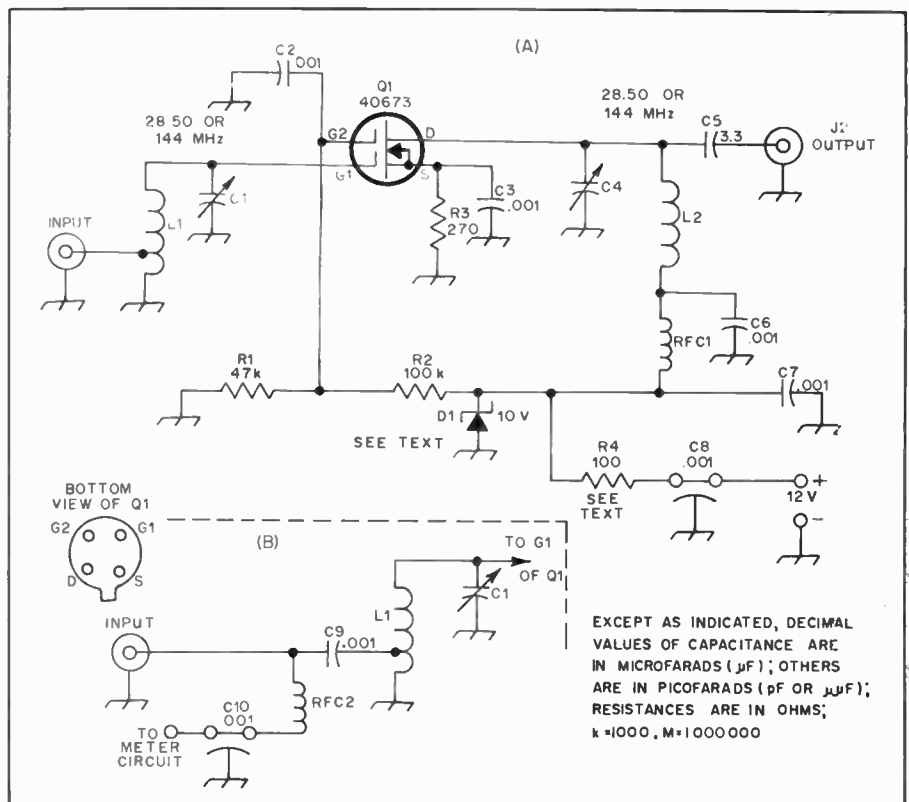


Fig. 15 — Schematic diagram for the preamplifier. Part designations not listed below are for pc: board placement purposes. Alternative input circuit for use with microwave diode mixer is shown at B.

- C1, C4 — See Table 1.  
 C2, C3, C5, C6, C7, C9 — Disk ceramic.  
 C8 — 0.001 feedthrough capacitor.  
 J1, J2 — Coaxial connectors. Phono-type, BNC or SO-239 acceptable.  
 L1, L2 — See Table 1.  
 R4 — 3 turns no. 28 enam. on ferrite bead. A 220-ohm, 1/2-watt resistor may be substituted.  
 RFC2 — 33 µH, iron-core inductor. Millen J300-33 or J. W. Miller 70F335A1.

Table 1

	28 MHz	50 MHz	144 MHz
L1	17 turns No. 28 enam. on Amidon T-50-6 core. Tap at 6 turns from ground end.	12 turns No. 26 enam. on Amidon T-37-10 core. Tap at 5 turns from ground end.	5 turns No. 20 tinned 1/2-inch ID × 1/2-inch long. Tap at 2 turns from ground end.
L2	Same as L1, without tap.	Same as L1, without tap.	4 turns No. 20 tinned like L1, without tap.
C1	15 to 60-pF ceramic	1.8- to 16.7-pF air variable.	1.5- to 11.6-pF air variable.
C4	trimmer. Erie 538-002F.	E. F. Johnson 189-506-005.	E. F. Johnson 189-504-005.

success on several boards. Another approach — and one that is highly recommended — is to cover the copper with masking tape, transfer the pattern with carbon paper, then cut away the tape to expose the part to be etched. On small, simple boards the masking-tape method is hard to beat.

The pc board may be mounted in almost any small enclosure. Construction is not tricky or difficult. It should take only a few minutes to complete the unit after the board is prepared. The board is fastened in the enclosure by means of one metal standoff post and a no. 4 screw and nut. Input and output connectors are not critical; phono-type jacks may be used in the interest of low cost.

Adjustment is so easy that it almost needs no description. After connecting the amplifier to a receiver, simply tune the input (C1) and the output (C4) for maximum indication on a weak signal. One possible area of concern might be that the toroids used in the 10- and 6-meter versions are not always uniform in permeability, as purchased from various suppliers. However, it is an easy matter to add capacitance or remove a turn as required to make the circuits resonate at the correct frequency.

### Low-Noise 220-MHz JFET Preamp

At 220 MHz cosmic noise is below 1.4 dB, so very low noise receiving systems are effective at that frequency. This preamplifier uses a 2N5245 or 2N5486 JFET to achieve a noise figure as low as 1.3 dB. The JFET operates grounded-

source with inductive neutralization. The preamplifier was first described by WB6-NMT in March 1972 *QST*.

The preamplifier is built on double-clad circuit board, mounted on spacers inside an LMB T-F770 aluminum box, 2-3/4 × 2-1/8 × 1-5/8 (70 × 54 × 42 mm) inches in size. A shield of circuit board stock divides the amplifier as indicated by the broken line in the circuit diagram. SMA or N-type fittings are recommended for the input and output connectors. E. F. Johnson manufactures an inexpensive line of SMA connectors which are highly desirable for low-noise connections at vhf and uhf. Top grade glass trimmers or miniature air variables should be used for C1, C2 and C4 for best results.

The dc voltage for the preamplifier is fed through one arm of a coaxial T fitting at the receiver input. This assumes use of some sort of blocking capacitor in the receiver input, to prevent grounding the dc through a coupling loop or tap on a grounded tuned circuit. The rf choke in the preamplifier circuit, RFC1, and the one used at the receiver input (to isolate the dc from the rf) are not critical. Any reasonably good vhf choke should do. If you're still willing to take the losses involved in the line, and you want to use the preamp at the receiver input, leave RFC1 out of the circuit, and connect the dc as shown in Fig. 17.

### Adjustment

First set R1 for about 5 mA current drain, at 12 to 15 volts dc. Touch the neutralizing coil, L2. If there is any

change in current, the stage is oscillating. Keeping contact with L2 (to prevent oscillation), readjust R1 for 5 mA. Using a strong 220-MHz test signal, adjust C4 for maximum signal indication. Set C1 to minimum capacitance, and peak C2. Increase C1 slowly until signal no longer rises, then back off one turn and readjust C2 and C4 for maximum signal.

Now reverse the preamplifier, connecting J1 to the receiver input, and feeding the signal to J2. With the dc still applied, tune L2 to minimum signal feed-through. If L2 has an ungrounded brass slug, the amplifier attenuation should be about 50 dB. Drain current

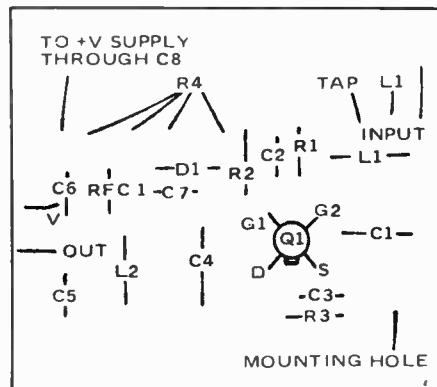


Fig. 16 — Full-scale layout and parts placement guide for the pc board. Foil side shown.


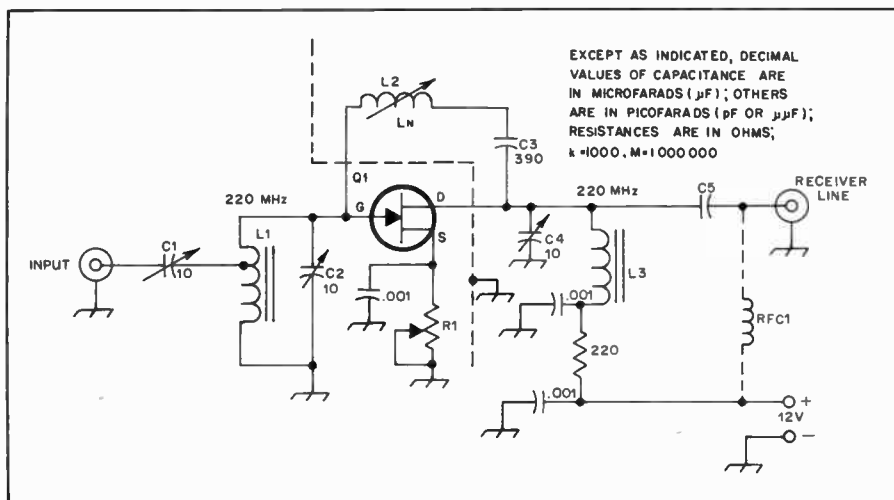



Fig. 17 — Circuit and parts information for the WB6NMT 220-MHz preamplifier.

- C1 — 0.8 or 1 to 10 pF glass trimmer, Johanson 2950 or JFD VAM or MVM series.
- C2 — Like C1, or Corning Direct Traverse CGW, 0.8 to 10 pF.
- C3 — 390-pF silver mica.
- C4 — Like C1, C2, or less-expensive type with 1 to 10-pF range.
- C5 — Experiment with values 1 to 5 pF, for maximum gain in system as it will be used.
- J1, J2 — SMA or N-type connector.
- L1 — 4 turns no. 22 enam. on Micrometals T-30-0 toroidal core (Amidon Associates). Tap 1 turn

- from top, subject to adjustment for lowest nf. Air-wound coils also usable, but toroids preferred.
- L2 — 9 turns no. 28 enam. on 1/4-in. (6.3 mm) slug-tuned form (Miller 4500, brass slug). Do not ground the slug.
- L3 — Like L1, but no tap.
- Q1 — 2N5245, 2N5486, MPF-107, TIS-88.
- R1 — 200- or 250-ohm control.
- RFC1 — Vhf rf choke, 0.8 to 3 μH. Use only when preamp is antenna mounted (see text).

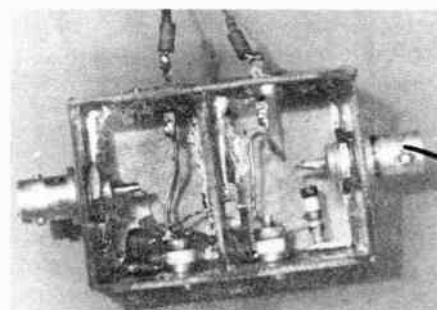

(A)

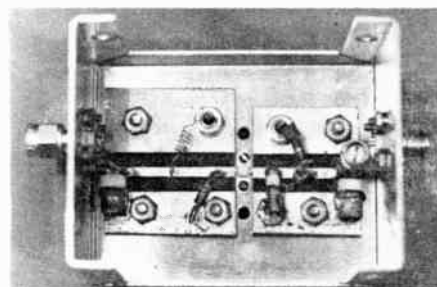

(B)

Fig. 18 — At A, 432-MHz GaAs FET preamplifier built by K2UYH. The transistor is mounted to the central shield by soldering the source lead directly to the copper foil. The drain lead of the transistor passes through a hole in the shield. At B, a 1296-MHz GaAs FET preamplifier built by WA2ZZF. In this model, the transistor is connected to striplines etched on glass-epoxy board. SMA-type coaxial connectors are shown although type N or BNC connectors may be used.

should remain at 5 mA.

Connect the amplifier normally, and repeat the process outlined above, until the tuning of C4 remains nearly constant. Finally, adjust C1 for best signal-to-noise ratio (lowest noise figure) and readjust C2. This should yield a noise figure of 1.5 to 2 dB, and gain of 12 to 18 dB, depending on the transistor used. Often the lower-gain condition will also give the best noise figure.

### Low-Noise GaAs FET Preamplifiers for 432 and 1296 MHz

Gallium-arsenide field-effect transistors (GaAs FETs) have recently come into use as low-noise microwave amplifiers. Amateur experimentation has shown that they can provide excellent performance on the uhf and lower microwave amateur bands. These devices are rather expensive, particularly the ones characterized as C-band and X-band (4-12 GHz) microwave low-noise amplifiers. However, other GaAs FETs, characterized as *power amplifiers* for low and medium-power (up to 1/4 watt) microwave applications will provide almost the same noise figure at uhf and are being made available to amateurs. The power devices also have wide dynamic range, providing less intermodulation distortion and lower susceptibility to burnout. The receiver preamplifiers to be described are relatively simple to construct and have sufficient tuning range for almost any GaAs FET available. They were first described by K2UYH and WA2ZZF in June 1978 *QST*.

### Construction

These preamps for 432 MHz (Fig. 18A) and 1296 MHz (Fig. 18B) use power GaAs FETs made by Microwave Semiconductor Corp.; however, devices made by NEC (Nippon Electric Co.) perform at least as well, and many similar devices will also certainly work. Construction details are shown in the photographs and schematic diagrams. The 432-MHz preamp is built in a 2-1/4 × 1-1/2 × 1-inch (57 × 38 × 25-mm) box made of double-sided printed-circuit board. A cover plate is recommended but does not significantly affect tuning. The GaAs FET source is soldered to the central shield board with the drain lead projecting through a hole. Several other versions have been constructed; in one of these, the wire inductors are replaced by straps placed parallel to the bottom plate, and spaced approximately 1/8 inch (3 mm) above it; a typical strap dimension would be 3 inches (76.2 mm) long by 1/2 inch (13 mm) wide. The 1296-MHz preamp is constructed in a 2-3/4 × 2-1/8 × 1-5/8-inch (70 × 54 × 41-mm) Minibox (BUD CU-3000A or equivalent). The GaAs FET is bolted between two pieces of 1/16-inch (1.6-mm) printed-circuit board, using 0-80 screws (available at many hobby shops). The lead height is just right to sit on top of the

50-ohm lines printed on these boards. The ground connection for the tuning capacitors is provided by mounting screws and by copper foil soldered around one edge of each board. The ground plane sides of the board are smoothly tinned to reduce copper-to-aluminum corrosion.

### Handling Precautions

The MSC GaAs FETs have static-resistant gold gates, and are only susceptible to damage from overvoltage or excess heating. Some other types, particularly those of Japanese manufacture, have aluminum gates which are very sensitive to static burnout, and should be handled in the same manner as unprotected MOS devices. In any case, work quickly when soldering the devices and use a grounded or cordless soldering iron. After assembly, the Zener diodes shown should protect the device in normal operation. Of course, it should be realized that these devices are physically small and require reasonably careful handling.

### Adjustment and Performance

Normal operating voltages are  $V_{DS} = 1.5$  to 3V,  $V_{GS} = -0.5$  to  $-2V$ ; gate current is negligible and may be supplied from a battery. Peak the tuning capacitors on a strong signal, then trim them and adjust the drain and gate voltages with the aid of a noise-figure meter or weak-signal source. Minimum noise figure occurs near the tuning for maximum gain. Output tuning should have little effect, but the noise figure is sensitive to the input tuning and gate voltage; varying the drain voltage should give a broad peaking of noise figure. Drain current is controlled by gate voltage. After peaking up the preamp, drain current will probably be between 20 and 100 mA.

It should be emphasized that these devices have extremely high gain at uhf and will readily oscillate unless adequate precautions are taken. Stability is obtained *directly* from the drain to ground, at the expense of some gain reduction. The values shown should provide adequate stability if good bypassing is used; gain will be around 20 dB at 432 MHz and 15 dB at 1296 MHz. Any increase in the value of these stabilizing resistors is at your own risk!

Typical noise figures to be expected with these preamps are on the order of 1 dB at 432 MHz and 3 dB or less at 1296 MHz. The devices are capable of even better performance than this; significant improvements are obtainable at 1296 MHz with attention to good uhf construction techniques and low-loss circuitry. However, the circuits shown are easily reproduced and still provide excellent performance.

### Doubly Balanced Mixer

Advances in technology have, in recent years, provided the amateur builder with

many new choices of hardware to use in the building of receivers, converters, or preamplifiers. The broadband doubly balanced mixer package is a fine example of this type of progress, and as amateurs gain an understanding of the capabilities of this device, they are incorporating this type of mixer in many pieces of equipment, especially receiving mixers. The combined mixer/amplifier described here was presented originally in March 1975 *QST* by KIAGB.

### Mixer Comparisons

Is a DBM really better than other types? What does it offer, and what are its disadvantages? To answer these questions, a look at more conventional "active" (voltages applied) mixing techniques and some of their problems is in order. The reader is referred to an article in *QST*<sup>1</sup> dealing with mixers. Briefly reiterated, common single-device active mixers with gain at vhf and uhf are beset with problems of noise, desensitization and small local-oscillator (LO) isolation from the r-f and i-f "ports." As mixers, most devices have noise figures in excess of those published for them as rf amplifiers and will not provide sufficient sensitivity for weak-signal work. To minimize noise, mixer-device current is generally maintained at a low level. This can reduce dynamic range, increasing overload potential, as defined in the terminology appendix. Gain contributions of rf amplifiers (used to establish a low system noise figure) further complicate the overload problem. LO-noise leakage to the rf and i-f ports adversely affects system performance. Mixer dynamic range can be limited by conversion of this noise to i-f, placing a lower limit on mixer system sensitivity. Generally 20 dB of mixer midband interport isolation is required, and most passive DBM can offer greater than 40 dB.

A commercially manufactured doubly balanced diode mixer offers performance predictability, circuit simplicity and flexibility. Closely matched Schottky-barrier hot-carrier diodes, commonly used in most inexpensive mixers of this type, provide outstanding strong-signal mixer performance (up to about 0 dBm at the rf input port) and add little (0.5 dB or so) to the mixer noise figure. Essentially, diode conversion loss from rf to i-f, listed in Table 2 on page 9-13 represents most of the mixer contribution to system noise figure. Midband isolation between the LO port and the rf and i-f ports of a DBM is typically > 35 dB — far greater than that achievable with conventional single device active-mixing schemes. This isolation is particularly advantageous in dealing with low-level local-oscillator harmonic and noise content. Of course, selection of LO devices with low audio noise figures, and proper rf filtering in the LO output, will

<sup>1</sup>DeMaw and McCoy; "Learning to Work With Semiconductors," Part IV, *QST*, July, 1974.



reduce problems from this source.

Often-listed disadvantages of a diode DBM are (a) conversion loss, (b) LO power requirements, and (c) i-f-interface problems. The first two points are closely interrelated. Conversion loss necessitates some low-noise r-f amplification to establish a useful weak-signal system noise figure. Active mixers also have this requirement, as will be demonstrated later. Additional LO power is fairly easy to generate, filter, and measure. If we accept the fact that more LO power is necessary for the DBM than is used in conventional single-device active mixing circuits, we leave only two real obstacles to be overcome in the DBM, those of conversion loss and i-f output interfacing.

To minimize conversion loss in a DBM, the diodes are driven by the LO beyond their square-law region, producing an output spectrum which in general includes the terms<sup>2</sup>:

- 1) Fundamental frequencies  $f_{LO}$  and  $frf$
- 2) All of their harmonics
- 3) The desired i-f output,  $f_{LO} \pm frf$
- 4) All higher order products of  $nf_{LO} \pm mfrf$ , where  $n$  and  $m$  are integers.

The DBM, by virtue of its symmetry and internal transformer balance, suppresses a large number of the harmonic modulation products. In the system described here,  $f_{LO}$  is on the low side of  $frf$ , therefore, numerically, the desired i-f output is  $frf - f_{LO}$ . Nonetheless, the term  $f_{LO} \pm frf$  appears at the i-f-output port equal in amplitude to the desired i-f signal, and this unused energy must be effectively terminated to obtain no more than the specified mixer-conversion loss. This is not the image frequency,  $f_{LO} - fi-f$ , which will be discussed later.

In any mixer design, all rf port signal components must be bypassed effectively for best conversion efficiency (minimum loss). Energy not "converted" by mixing action will reduce conversion gain in active systems, and increase conversion loss in passive systems such as the diode DBM. Rf bypassing also prevents spurious resonances and other undesired phenomena from affecting mixer performance. In this system, rf bypassing at<sup>2</sup>See appendix.

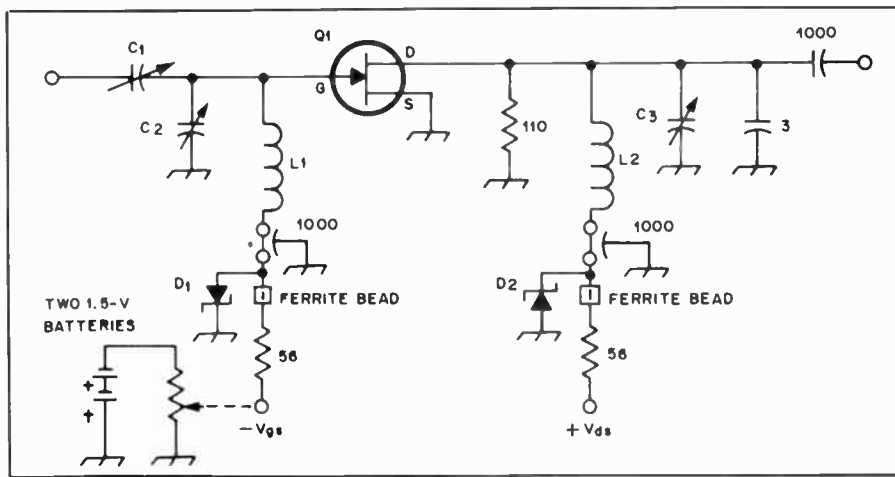


Fig. 19 — Schematic diagram of the 432-MHz preamplifier.  
 C1 — 0.0.3- to 3.5-pF piston trimmer (Johanson or JFD).  
 C2, C3 — 0.8- to 10-pF piston trimmer (Johanson or JFD).  
 D1, D2 — Zener diode, 5.6 volts (4.7 to 6.2 volts usable).  
 L1 — 1 turn no. 18 wire (see photo) or strip-line (see text).  
 L2 — no. 18 wire, 0.9 in. (23 mm) long  
 Q1 — GaAs FET (see text).

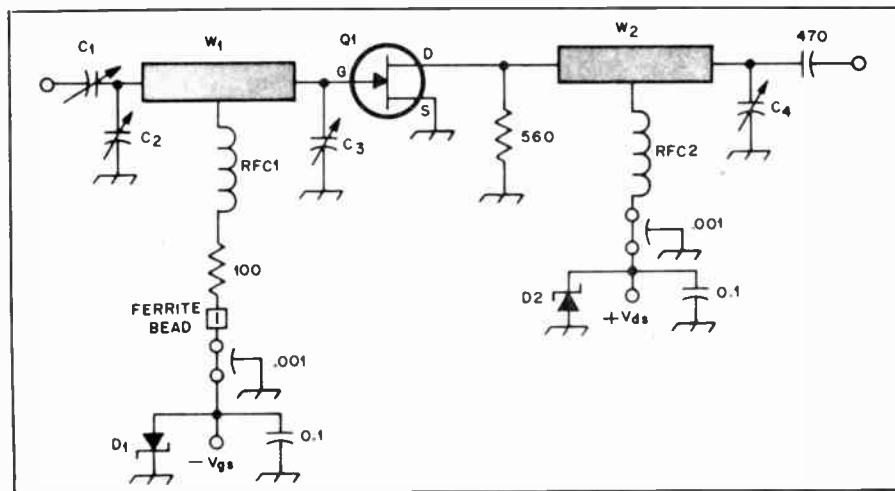


Fig. 20 — Schematic diagram of the 1296-MHz preamplifier.  
 C1, C2, C4 — 0.8- to 10-pF piston trimmer (Johanson or JFD). Note: C1 may be replaced by a fixed low-inductance capacitor of 10-pF or more.  
 C3 — 0.3- to 3.5-pF piston trimmer (Johanson or JFD).  
 D1, D2 — Zener diode, 5.6 V (4.7 to 6.2 V usable).  
 Q1 — GaAs FET (see text)  
 RFC1 — 3 turns, 1/16-in. (1.6-mm) ID, in lead of resistor, spaced wire diameter.  
 RFC2 — 5 turns no. 32 wire, 1/16-in. (1.6 mm) ID, spaced two wire diameters.  
 W1 — 50-ohm microstripline, 0.105 in. (2.7 mm) wide by 0.9 in. (23 mm) long on 1/16-in. (1.6-mm) thick double-sided G-10 printed-circuit board.  
 W2 — 50-ohm microstripline, 0.105 in. (2.7 mm) wide by 1.1-in. (28-mm) long on 1/16-in. (1.6-mm) thick double-sided G-10 printed-circuit board.

Table 2

Manufacturer:	Relcom	Anzac	MCL	MCL	MCL	MCL
Model	M6F	MD-108	SRA-1	SRA-1H	RAY-1	MA-1
Frequency range, LO MHz	2-500	5-500	.5-500	.5-500	5-500	1-2500
rf	2-500	5-500	.5-500	.5-500	5-500	1-2500
i-f	DC-500	DC-500	DC-500	DC-500	DC-500	1-1000
Conversion loss,	9 dB max.	7.5 dB max.	6.5 dB typ.	6.5 dB typ.	7.5 dB typ.	8.0 dB typ.
Mid-range						1-2.5 GHz.
Isolation, LO-RF	35,40 dB min.	40 dB min.	45 dB typ.	45 dB typ.	40 dB typ.	40 dB typ.
mid-range LO-i-f	25-35 dB min.	35 dB min.	40 dB typ.	40 dB typ.	40 dB typ.	40 dB typ.
Total input power:	50 mW	400 mW	500 mW	500 mW	1 W	50 mW
LO power requirement:	+7 dBm (5 mW)	+7 dBm (5 mW)	+7 dBm (5 mW)	+17 dBm (50 mW)	+23 dBm (200 mW)	+10 dBm (10 mW)
Signal 2-dB compression level	Not spec.	Not spec.	+1 dBm	+10 dBm	+15 dBm	+7 dBm
Impedance, all ports:	50 ohms	50 ohms	50 ohms	50 ohms	50 ohms	50 ohms

All specifications apply only at stated LO power level.

Relcom, Division of Watkins-Johnson, 3333 Hillview Ave., Palo Alto, CA 94304.  
 Anzac Electronics, 39 Green Street, Waltham, MA 02154.  
 MCL — Mini-Circuits Laboratory, 2625 East 14th St., Brooklyn, NY 11235.



the i-f-output port will be provided by the input capacitance of the i-f interface. The DBM is not a panacea for mixing ills, and

its effectiveness can be reduced drastically if all ports are not properly terminated.

### DBM Port Terminations

Most DBM-performance inconsistencies occur because system source and load impedances presented to the mixer are not matched at all frequencies encountered in normal operation. The terminations (attenuator pads) used in conjunction with test equipment by manufacturers to measure published performance characteristics are indeed "broadband" matched. Reactive mixer terminations can cause system problems, and multiple reactive terminations can usually compound these problems to the point where performance is very difficult to predict. Let's see how we can deal with reactive terminations.

### The I-F Port

The i-f port is very sensitive to mismatch conditions. Reflections from the mixer/i-f amplifier interface (the pi network in Fig. 23) can cause the conversion loss to vary as much as 6 dB. Also greatly affected are third-order inter-modulation-product ratio and the suppression of spurious signals, both of which may vary  $\pm 10$  dB or more. It is ironic that the i-f port is the most sensitive to a reactive termination, as this is a receiving system point where sharp-skirted filters are often desired.

Briefly, here is what happens with a reactive i-f port termination. Fig. 22 shows a DBM with "high side" LO injection and an i-f termination matched at  $f_{LO} - f_{RF}$  but reactive at  $f_{LO} + f_{RF}$ . The latter term re-enters the mixer, again combines with the LO and produces terms that exit at the rf port, namely  $2f_{LO} + f_{RF}$ , a dc term, and  $f_{LO} + f_{RF} - f_{LO}$  (the

original rf-port input frequency). This condition affects conversion loss, as mentioned earlier, in addition to rf-port VSWR, depending on the phase of the reflected signal. The term  $2f_{LO} + f_{RF}$  also affects the harmonic modulation-products spectrum resulting in spurious responses.

One solution to the i-f-interface problem is the use of a broadband 50-ohm resistive termination, like a pad, to minimize reflections. In deference to increased post-conversion system noise figure, it seemed impractical to place such a termination at the mixer i-f output port. While a complimentary filter or diplexer (high-pass/low-pass filters appropriately terminated) can be used to terminate both  $f_{RF} + f_{LO}$  and  $f_{RF} - f_{LO}$ , a simpler method can be used if  $f_{RF} + f_{LO}$  is less

<sup>3</sup>Presentation and calculation format of these terms is based on "low-side" LO injection. See the appendix for explanation.

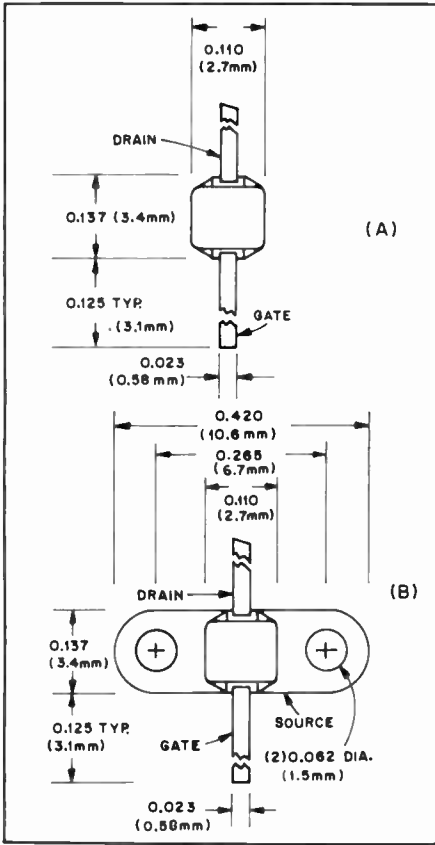


Fig. 21 — Dimensional information for the GaAs FET packages supplied by MSC. At A, case style 98, top view, and at B, top view of case style 97. Drain and source leads are spaced 0.065 in. (1.65 mm) above the bottom of the case. MSC designation for these case styles is Flipac.

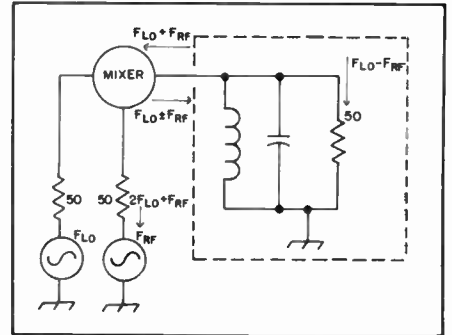


Fig. 22 — The i-f port of a double-balanced mixer is matched at  $f_{LO} - f_{RF}$  and reactive at  $f_{LO} + f_{RF}$ . In this configuration conversion loss, rf compression and desensitization levels can vary  $\pm 3$ dB while harmonic modulation and third-order IMD products can vary  $\pm 20$  dB.

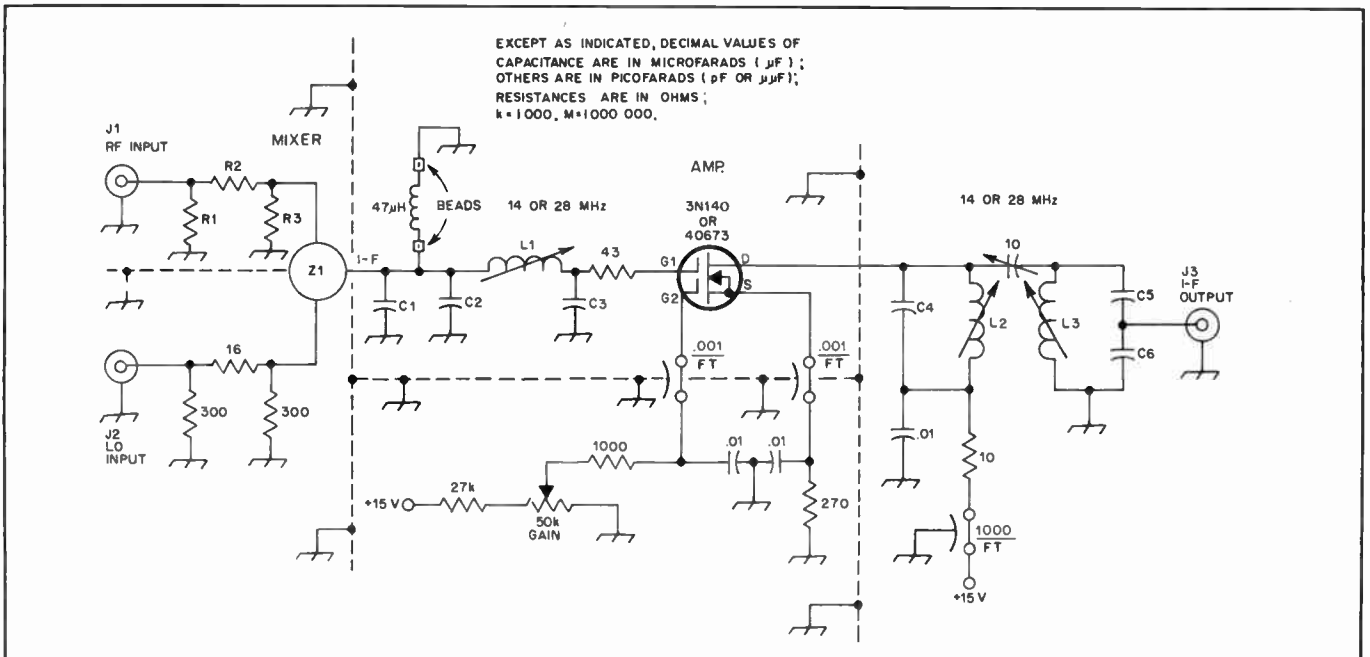


Fig. 23 — A schematic diagram for the double-balanced mixer and i-f post amplifier. The i-f can be either 14 or 28 MHz. Parts values are given in Table 3.

than 1 GHz and  $frf + (fLO)/(frf - fLO) \geq 10$ . Place a short-circuit termination to  $frf + fLO$ , like a simple lumped capacitance, directly at the mixer i-f terminal. This approach is easiest for the amateur to implement and duplicate, so a form of it was tried — with success. In our circuit, C1 serves a dual purpose. Its reactance at  $frf + fLO$  is small enough to provide a low-impedance “short-circuit” condition to this term for proper mixer operation. Additionally, it is part of the input reactance of the mixer i-f-amplifier interface. Fortunately the network impedance-transformation ratio is large enough, and in the proper direction, to permit a fairly large amount of capacitance (low reactance) at the mixer i-f-output port. The capacitor, in its dual role, must be of good quality at vhf/uhf (specifically  $frf + fLO$ ), with short leads, to be effective. The mixer condition  $(frf + fLO)/(frf - fLO) \geq 10$  is met at 432 and 220 MHz with a 404/192-MHz LO (28-MHz i-f) and on 14 MHz with a 130-MHz LO (14-MHz i-f). At 50 MHz, with a 36 MHz LO, we are slightly shy of the requirement, but no problems were encountered in an operating unit. The pi-type interface circuit assures a decreasing impedance as i-f operation departs from midband, thereby lessening IMD problems.

### The LO Port

The primary effect of a reactive LO source is an increase in harmonic modulation and third-order IMD products. If the drive level is adequate, no effect is noted on conversion loss, rf compression and desensitization levels. A reactive LO source can be mitigated by simply padding the LO port with a 3- or 6-dB pad and increasing the LO drive a like amount. If excess LO power is not available, matching the LO source to the mixer will improve performance. This method is acceptable for single-frequency LO applications, when appropriate test equipment is available to evaluate matching results. For simplicity, a 3-dB pad was incorporated at the LO-input port as an interface in both versions of the mixer. Thus the LO port is presented with a reasonably broadband termination, and is relatively insensitive to applied frequency, as long as it is below about 500 MHz. This implies that frequencies other than amateur assignments may be covered — and such is indeed the case when appropriate LO frequencies and rf amplifiers are used. Remotely located LOs, when adjusted for a 50-ohm load, can be connected to the mixer without severe SWR and reflective-loss problems in the transmission line.

Broadband mixers exhibit different characteristics at different frequencies, due to circuit resonances and changes in diode impedances resulting from LO power-level changes. Input impedances of the various ports are load dependent, even though they are isolated from each other

Table 3

### DBM I-F Amplifier Parts List

C1	14 MHz i-f output 470 pF JFD 471J or equal.	28 MHz i-f output 300 pF JFD 301J or equal.
C2	390 pF SM	not used
C3	180 pF SM	51 pF SM
C4	39 pF SM	18 pF SM
C5	56 pF SM	27 pF SM
C6	300 pF SM	150 pF SM
L1	9 turns no. 18 enam., close wound on a 3/8- inch (9.5 mm) diameter red-slug coil form.	9 turns no. 24 enam., close wound on a 1/4- inch (6.3mm) diameter green-slug coil form.
L2	18 turns no. 26 enam., close wound on a 3/8- inch diameter red-slug coil form.	12 turns no. 26 enam., close wound on a 1/4- inch diameter green- slug coil form.
	Tap down 7 turns from top for 3N140 drain connection. See text.	No tap used.
L3	Same as L2 but no tap. spaced 1 1/8-inch (29mm) center-to- center with L2.	Same as L2, spaced 1 inch (25mm) center-to- center with L2.
R1,	300 ohm 1/4 W, carbon.	430 ohm, 1/4 W,
R3		carbon.
R2	16 ohm, 1/4 W, carbon.	11 ohm, 1/4 W, carbon.

Ferrite beads can be replaced by a 10-ohm,  
1/4 W carbon resistor at one end of the choke,  
if desired.

SM = Silver Mica.

physically, and by at least 35 dB electrically. At higher frequencies, this effect is more noticeable, since isolation tends to drop as frequency increases. For this reason, it is important to maintain the LO power at its appropriate level, once other ports are matched.

### The RF Port

A reactive rf source is not too detrimental to system performance. This is good, since the output impedance of most amateur preamplifiers is seldom 50 ohms resistive. A 3-dB pad is used at the rf port in the 50- and 144-MHz mixer to 14 MHz, and a 2-dB pad is used in the 220/432-MHz to 28 MHz, although they add directly to mixer noise figure. Rf inputs between about 80 and 200 MHz are practical in the 14-MHz i-f-output model, while the 28-MHz-output unit is most useful from 175 to 500 MHz. Mixer contribution to system noise figure will be almost completely overcome by a low-noise rf amplifier with sufficient gain and adequate image rejection.

### Image Response

Any broadband mixing scheme will have a potential image-response problem. In most amateur vhf/uhf receiver systems (as in these units) single-conversion techniques are employed, with the LO placed below the desired rf channel for non-inverting down-conversion to i-f. Conversion is related to both i-f and LO

frequencies and, because of the broadband nature of the DBM, input signals at the rf image frequency (numerically  $fLO - fi-f$  in our case) will legitimately appear inverted at the i-f-output port, unless proper filtering is used to reduce them at the mixer rf-input port. For example, a 144-MHz converter with a 28-MHz i-f output (116-MHz LO) will have rf image-response potential in the 84 to 88-MHz range. TV channel 6 wideband-fm audio will indeed appear at the i-f-output port near 28 MHz unless appropriate rf-input filtering is used to eliminate it. While octave-bandwidth vhf/uhf “imageless mixer” techniques can improve system noise performance by about 3 dB (image noise reduction), and image signal rejection by 20 dB — and much greater with the use of a simple gating scheme — such a system is a bit esoteric for our application. Double or multiple-conversion techniques can be used to advantage, but they further complicate an otherwise simple system. Image noise and signal rejection will depend on the effectiveness of the filtering provided in the rf-amplifier chain.

### Mixer Selection

The mixer used in this system is a Relcom M6F, with specifications given in Table 2. Suitable substitute units are also presented. The M6F is designed for printed-circuit applications (as are the recommended substitutes), and the lead pins are rather short. While mixers are available with connectors attached, they are more expensive. The simple package is suggested as, aside from less expense, improved interface between mixer and i-f amplifier is possible because of the short leads. The combining of mixer and i-f amplifier in one converter package was done for that reason. Along these lines, the modular-construction approach permits good signal isolation and enables the mixer-amplifier/i-f system to be used at a variety of rf and LO-input frequencies, as mentioned earlier.

Most commonly available, inexpensive DBM are not constructed to take advantage of LO powers much above +10 dBm (10 mW). To do so requires additional circuitry which could degrade other mixer characteristics, specifically conversion loss and interport isolation. The advantage of higher LO power is primarily one of improved strong-signal-handling performance. At least one manufacturer advertises a moderately priced “high-level” receiving DBM that can use up to +23 dBm (200 mW) LO power, and still retain excellent conversion loss and isolation characteristics, shown in Table 1. The usefulness of mixers with LO power requirements above the commonly available +7 dBm (5 mW) level in amateur receiving applications may be a bit moot, as succeeding stages in most amateur receivers will likely over-

load before the DBM. Excessive over-design is not necessary.

In general, mixer selection is based on the lowest practical LO level requirement that will meet the application, as it is more economical and results in the least LO leakage within the system. As a first-order approximation, LO power should be 10 dB greater than the highest anticipated input-signal level at the rf port. Mixers with LO requirements of +7 dBm are quite adequate for amateur receiving applications.

### Application Design Guidelines

While the material just presented only scratches the surface in terms of DBM theory and utilization in amateur vhf/uhf receiving systems, some practical solutions to the non-ideal mixer-port-termination problem have been offered. To achieve best performance from most commercially manufactured broadband DBM in amateur receiver service, the following guidelines are suggested:

- 1) Choose i-f and LO frequencies which will provide maximum freedom from interference problems. Don't "guesstimate"; go through the numbers!
- 2) Provide a proper i-f-output termination (most critical).
- 3) Increase the LO-input power to rf-input power ratio to a value that will provide the required suppression of any in-band interfering products. The specified LO power (+7 dBm) will generally accomplish this.
- 4) Provide as good an LO match as possible.
- 5) Include adequate pre-mixer rf-image filtering at the rf port.

When the mixer ports are terminated properly, performance usually in excess of published specifications will be achieved — and this is more than adequate for most amateur vhf/uhf receiver mixing applications.

### The Combined DBM/I-F Amplifier

A low-noise i-f amplifier (2 dB or less) following the DBM helps ensure an acceptable system noise figure when the mixer is preceded by a low-noise rf amplifier. A pi-network matching system used between the mixer i-f-output port and gate 1 of the 3N140 transforms the nominal 50-ohm mixer-output impedance to a 1500-ohm gate-input impedance (at 28 MHz) specifically for best noise performance. The network forms a narrow-band mixer/i-f-output circuit which serves two other important functions: It helps achieve the necessary isolation between rf- and i-f signal components, and serves as a 3-pole filter, resulting in a monotonic decrease in match impedances as the operating i-f departs from mid-band. This action aids in suppression of harmonic-distortion products.

The combined DBM/i-f amplifier is shown schematically in Fig. 23 and

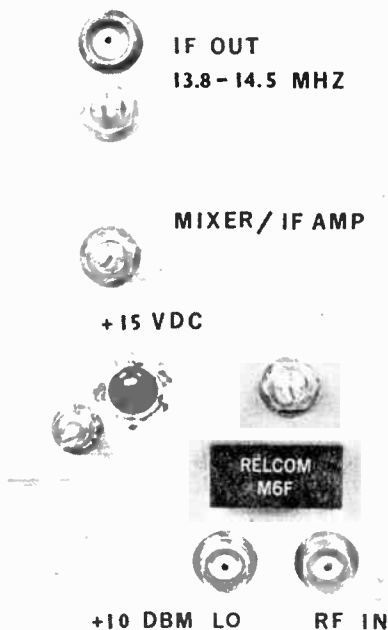


Fig. 24 — This top view of the DBM/i-f amplifier shows the plastic mixer package plus rf/LO inputs and i-f output jacks clearly marked for cabling. The unit is mounted on the open face of a standard 6 × 4 × 2-inch (152 × 102 × 51-mm) aluminum chassis. This shielding is necessary to prevent the 3N140 from picking up external signals in the 14-MHz region.

pictorially in the photographs. In the 14-MHz model, the 3N140 drain is tapped down on its associated inductance to provide a lower impedance for better strong-signal-handling ability. The 3N140 produces about 19 dB gain across a 700-kHz passband, flat within 1 dB between 13.8 and 14.5 MHz. A 2-MHz passband is used for the 28-MHz model, and the device drain is connected directly to the high-impedance end of its associated inductance. Both amplifiers were tuned independently of their respective mixers, and checked for noise figure as well as gain. With each i-f amplifier pretuned and connected to its mixer, signals were applied to the LO and rf-input ports. The pi-network inductance in the i-f interface was adjusted carefully to see if performance had been altered. No change was noted. I-f gain is controlled by the externally accessible potentiometer. Passband tuning adjustments in the drain circuit are best made with a sweep generator, but single-signal tuning techniques will be adequate. While there should be no difficulty with the non-gate-protected 3N140, a 40673 may be substituted directly if desired.

### DBM/I-F Amplifier IMD Evaluation

Classical laboratory IMD measurements were made on the DBM/i-f amplifier, using the test setup shown in Fig. 27, from both tones of a two-equal-tone rf-input test signal consisting of -10 dBm each tone. The tones were closely spaced

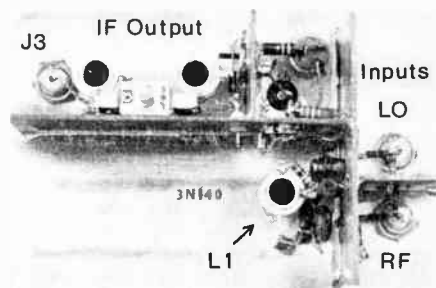


Fig. 25 — The bottom view of the DBM/i-f amplifier shows component and shielding layout. L1, the mixer-amplifier interface inductance and associated components are indicated. C1, with its wide silver-strap leads, is connected directly between the mixer i-f output pin and the copper-clad ground plane with essentially zero lead length. Connection between the mixer output pin and other components (L1, C2 and the rf choke for d-c return) is made by using excess lead from C1. The 43-ohm, 1/4-W resistor in the 3N140 gate 1 lead is connected between the high-impedance end of L1 and a spare terminal on the coil form. The device gate no. 1 lead and resistor are joined at this point. It is important that input/output isolation of the 3N140 be maintained as it is operating at high gain. Mixer packages other than the M6F may have different pin connections and require slightly different input-circuit layout and shielding. Double-sided copper-clad board was used throughout.

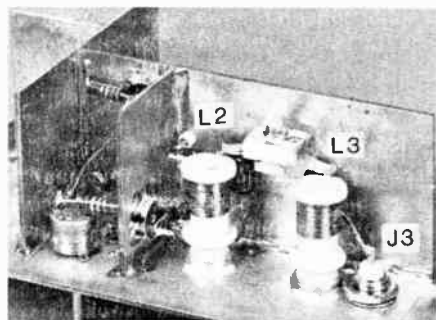


Fig. 26 — This is a side view showing construction details for the double-tuned i-f output circuit. The 3N140 drain lead passes through the shield wall via a small Teflon press-fit bushing and is connected directly to L2. A dc-input isolation compartment along with device gate 2 biasing components (bias configuration modified slightly after photograph was taken), can be seen to the left of the i-f-output components. L2 and L3 are spaced 1-1/8-inch (29 mm) center-to-center in the 14-MHz model shown, and 1 inch (25 mm) apart in the 28-MHz unit.

in the 144-MHz range, and converted to 14 MHz LO. Close spacing was necessary to ensure third-order products would appear essentially unattenuated within the relatively narrow i-f-output passband. In operation, as simulated by these test conditions, equivalent output signal levels at J3 would be strong enough to severely overload most amateur receivers. Perhaps the early Collins 75A series R390A and those systems described by Sabin<sup>4</sup> and Hayward<sup>5</sup> would still be functioning well.

<sup>4</sup>Sabin, "The Solid-State Receiver," *QST*, July, 1970.

<sup>5</sup>Hayward, "A Competition-Grade CW Receiver," *QST*, March and April 1974.



A high-performance, small-signal, vhf/uhf receiving amplifier optimized for IMD reduction and useful noise figure is only as good as any succeeding receiving-system stage, in terms of overload. The DBM/i-f-amplifier combination presented significantly reduces common first-mixer overload problems, leaving the station receiver as the potentially weak link in the system. When properly understood and employed, the broadband DBM followed by a selective low-noise i-f amplifier can be a useful tool for the amateur vhf/uhf receiver experimenter.

### Appendix

#### Mixer Terminology

*frf* — rf input frequency

*fLO* — local-oscillator input frequency

*fi-f* — i-f output frequency

By convention, mixing signals and their products are referred to the LO frequency for calculations. In the mixer system presented, *frf* is always above *fLO*, so we will refer our signals to *frf*, with the exception of Fig. 22 which uses the *fLO* reference.

#### Overload

A generic term covering most undesired operating phenomena associated with device non-linearity.

#### Harmonic Modulation Products

Output responses caused by harmonics of *fLO* and *frf* and their mixing products.

#### RF Compression Level

The absolute single-signal rf input-power level that causes conversion loss to increase by 1 dB.

#### RF Desensitization Level

The rf input power of an interfering signal that causes the small-signal conversion loss to increase by 1 dB, i.e., reducing a weak received signal by 1 dB.

#### Intermodulation Products

Distortion products caused by multiple rf signals and their harmonics mixing with each other and the LO, producing new output frequencies.

#### Mixer Intermodulation Intercept Point

Because mixers are nonlinear devices, all signals applied will generate others. When two signals (or tones), *F1* and *F2*, are applied simultaneously to the rf-input port, additional signals are generated and appear in the output as  $f_{LO} \pm (nF1 + mF2)$ . These signals are most troublesome when  $n \pm m$  is a low odd number, as the resulting product will lie close to the desired output. For  $n = 1$  (or 2) and  $m = 2$  (or 1), the result is three (3), and is called the two-tone/third-order intermodulation products. When *F1* and *F2* are separated by 1 MHz, the third-order products will lie 1 MHz above and below the desired outputs. Intermodulation is generally specified under anticipated operating

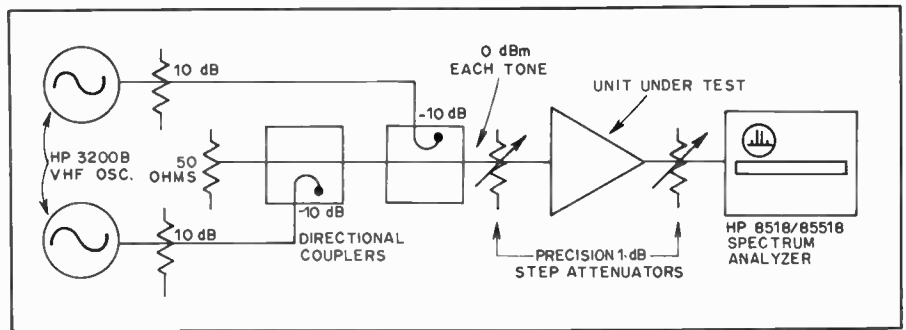


Fig. 27 — A test setup used to measure IMD. The first attenuator adjusts the input level to the unit under test. The second one provides a means of staying within the linear range of the spectrum analyzer.

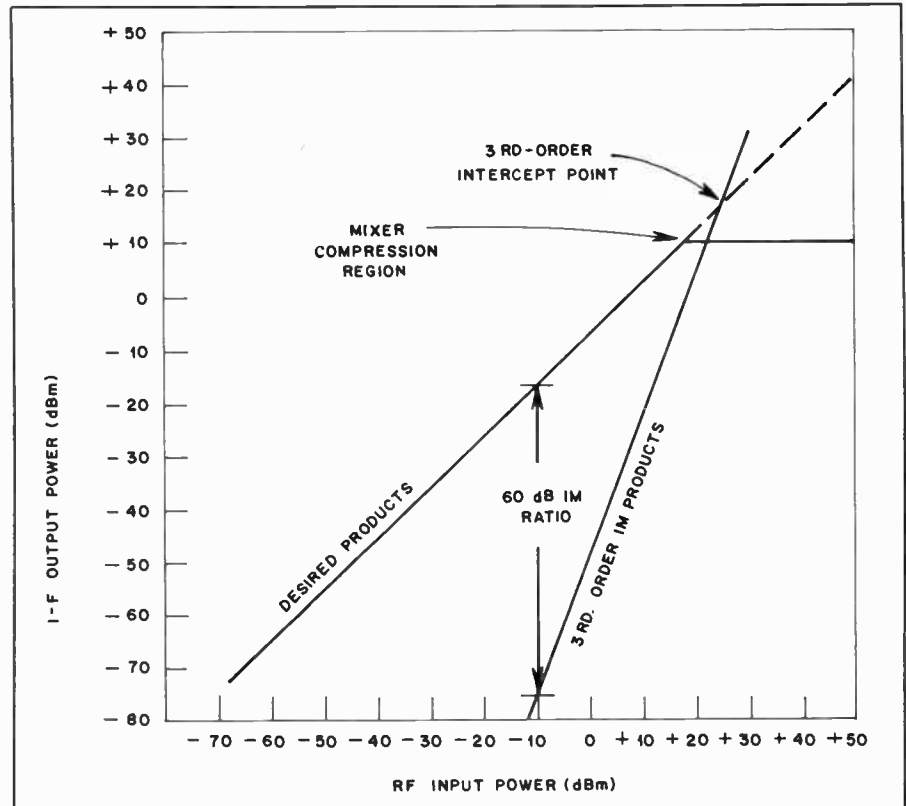


Fig. 28 — A third-order intercept point is determined by extrapolating the desired product curve beyond the mixer compression point and intersecting with the third-order IM-product curve. In this case LO power is +7 dBm, conversion loss is 5 dB.

conditions since performance varies over the broad mixer-frequency ranges. Intermodulation products may be specified at levels required (i.e., 50 dB below the desired outputs for two 0-dBm input signals) or by the intercept point.

The intercept point is a fictitious point determined by the fact that an increase of level of two input tones by 10 dB will cause the desired output to increase by 10 dB, but the third-order output will increase by 30 dB. If the mixer exhibited no compression, there would be a point at which the level of the desired output would be equal to that of the third-order product. This is called the third-order intercept point and is the point where the

desired-output slopes and third-order slopes intersect (Fig. 28).

#### Noise Figure

Noise figure is a relative measurement based on excess noise power available from a termination (input resistor) at a particular temperature (290° K). When measuring the NF of a double balanced mixer with an automatic system, such as the HP-342A, a correction may be necessary to make the meter reading consistent with the accepted definition of receiver noise figure.

In a broadband DBM, the actual noise bandwidth consists of two i-f passbands, one on each side of the local-oscillator



frequency ( $f_{LO} + f_i - f$  and  $f_{LO} - f_i - f$ ). This double sideband (dsb) i-f response includes the rf channel and its image. In general, only the rf channel is desired for further amplification. The image contributes nothing but receiver and background noise.

When making an automatic noise-figure measurement using a wideband noise source, the excess noise is applied through both sidebands in a broadband DBM. Thus the instrument meter indicates NF as based on both sidebands. This means that the noise in the rf and image sidebands is combined in the mixer i-f-output port to give a double contribution (3 dB greater than under ssb conditions). For equal rf-sideband responses, which is a reasonable assumption, and in the absence of preselectors, filters, or other image rejection elements, the automatic NF meter readings are 3 dB lower than the actual NF for DBM measurements.

The noise figure for receivers (and most DBM) is generally specified with only one sideband for the useful signal. As mentioned in the text, most DBM diodes add no more than 0.5 dB (in the form of NF) to conversion loss, which is generally measured under single-signal rf-input (ssb) conditions. Assuming DBM conversion efficiency (or loss) to be within specifications, there is an excellent probability that the ssb NF is also satisfactory. Noise figure calculations in the text were made using a graphical solution of the well known noise-figure formula:

$$F_T = f_1 + \frac{f_2 - 1}{g_1}$$

converted to dB.

### Improved Wide Band I-F Responses

The following information was developed in achieving broad-band performance in the mixer-to-amplifier circuitry. In cases where only a small portion of a band is of interest the original circuit values are adequate. For those who need to receive over a considerable portion of a band, say one to two MHz, a change of some component will provide improved performance over a broad range while maintaining an acceptable noise figure.

The term "nominal 50-ohm impedance" applied to diode DBM ports is truly a misnomer, as their reflective impedance is rarely 50 ohms + j0 and a VSWR of 1 is almost never achieved. Mixer performance specified by the manufacturer is measured in a 50-ohm broadband system, and it is up to the designer to provide an equivalent termination to ensure that the unit will meet specifications. Appropriate matching techniques at the rf and LO ports will reduce conversion loss and low-power requirements. Complex filter synthesis can improve the i-f output match. However, if one does not have the necessary equip-

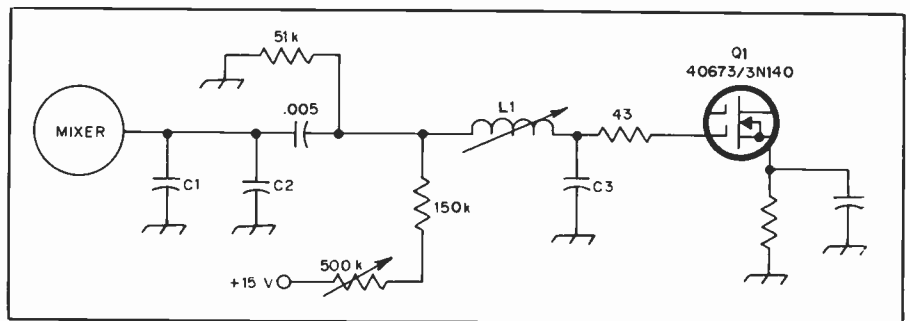


Fig. 29 — Suggested changes in the mixer-to 3N140 pi-network interface circuit, producing lower  $Q_L$  and better performance.

ment to evaluate his efforts, they may be wasted. Simple, effective, easily reproduced reduced circuitry was desired as long as the trade-offs were acceptable, and measurements indicate this to be the case.

The most critical circuit in the combined unit is the interface between mixer and i-f amplifier. It must be low-pass in nature to satisfy vhf signal component bypassing requirements at the mixer i-f port. For best mixer IMD characteristics and low conversion loss, it must present to the i-f port a nominal 50-ohm impedance at the desired frequency, and this impedance value must not be allowed to increase as i-f operation departs from midband. The impedance at the i-f amplifier end of the interface network must be in the optimum region for minimum cross-modulation and low noise. A dual-gate device offers two important advantages over most bi-polars. Very little, if any, power gain is sacrificed in achieving best noise figure, and both parameters (gain and NF) are relatively independent of source resistance in the optimum region. As a result, the designer has a great deal of flexibility in choosing a source impedance. In general, a 3:1 change in source resistance results in only a 1-dB change in NF. With minimum cross-modulation as a prime system consideration, this 3:1 change (reduction) in source resistance implies a 3:1 improvement in cross-modulation and total harmonic distortion.

Tests on the 3N201 dual-gate MOSFET have shown device noise performance to be excellent for source impedances in the 1000- to 2000-ohm region. For optimum noise and good cross-modulation performance, the nominal 50-ohm mixer i-f output impedance is stepped up to about 1500 ohms for i-f amplifier gate 1, using the familiar low-pass pi network. This is a mismatched condition for gate 1, as the device input impedance for best gain in the hf region is on the order of 10kΩ. Network loaded-Q values in the article are a bit higher than necessary, and a design for lower  $Q_L$  is preferred. Suggested modified component values are listed in Fig. 29. High-frequency attenuation is reduced somewhat, but satisfactory noise and bandwidth performance is more

easily obtained. Coil-form size is the same, so no layout changes are required for the modification. Components in the interface must be of high Q and few in number to limit their noise contribution through losses. The 28-MHz values provide satisfactory interface network performance over a 2-MHz bandwidth. A higher  $Q_L$  in the 28-MHz interface can be useful if one narrows the output network and covers only a few hundred kilohertz bandwidth, as is commonly done in 432-MHz weak-signal work.

Device biasing and gain control methods were chosen for simplicity and adequate performance. Some sort of gain adjustment is desirable for drain-circuit overload protection. It is also a handy way to "set" the receiver S meter. A good method for gain adjustment is reduction of the gate-2 bias voltage from its initial optimum-gain bias point (greater than +4 V dc), producing a remote-cutoff characteristic (a gradual reduction in drain current with decreasing gate bias). The initial gain-reduction rate is higher with a slight forward bias on gate 1, than for  $V_{g1s} = 0$ . Input and output circuit detuning resulting from gain reduction (Miller effect) is inconsequential as the gate-1 and drain susceptances change very little over a wide range of  $V_{g2s}$  and  $I_D$  at both choices of i-f. Best intermodulation figure for the 3N201 was obtained with a small forward bias on gate 1, and the bias-circuit modification shown may be tried, if desired.

### Converters for 50, 144 and 220 MHz

The converters here were originally designed by the Rochester VHF Group and appeared in August 1973 *QST*. The design was the basis for a club project so the same board is used for all three converters, with only slight modifications for each band. Design features include

- 1) Low noise figure.
- 2) State-of-the-art freedom from cross modulation.
- 3) Sufficient gain to override the front-end-noise of most receivers.
- 4) Double-tuned bandpass interstage and output circuits to achieve a flat response over a 2-MHz portion of either band.
- 5) Filtering of the local oscillator chain

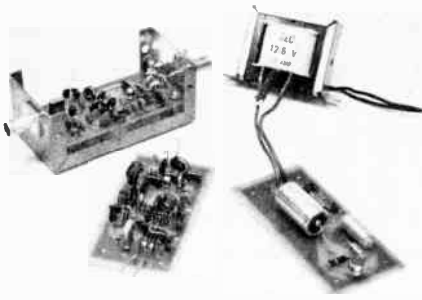


Fig. 30 — Completed 6- and 2-meter converters (left and center) with power supply.

in the 144- and 220-MHz models to reduce spurious responses.

6) Small size and low power consumption.

7) Freedom from accidental mistuning during the life of the converter.

Other points considered were such things as freedom from the necessity of neutralization and the use of moderately priced transistors.

Several breadboard models were constructed and tested as the design evolved. Fig. 30 shows two completed converters and a power supply.

### Circuit Design

A schematic diagram for the three versions are shown in Figs. 31, 32 and 33. The configuration of the rf and mixer portions of the circuit are virtually identical for all three with the values of the frequency-determining components

being scaled appropriately. The major difference between the converters is a change in the local oscillator chain. A minor change in the method of interstage coupling was necessary to prevent stray-capacitance effects from making the alignment critical on the 50-MHz converter.

All inductors in the 50-MHz model and the 28-MHz output circuit are wound on Amidon toroid cores. The tuned circuits are aligned by spreading or compressing the turns around the toroid core. After alignment the coils are glued in place with Silastic compound (sold as bathtub caulk).

The rf amplifier, Q1, is used in a grounded-gate configuration. The input circuit is tapped to provide a proper match between the antenna and source of the FET while maintaining a reasonable Q. The 50-MHz interstage coupling network consists of C3, C5, L2 and L3. Band-pass coupling is controlled by the capacitive T network of C3 and C5 in ratio with C6. A 40673 dual-gate MOS-FET is used in the mixer circuit (Q2). Gate 1 receives the signal, while gate 2 has the local-oscillator injection voltage applied to it through C7. A slight amount of positive bias is applied to gate 2 through R2. A top-coupled configuration, using toroid inductors, serves as the 28-MHz output circuit of both converters.

The oscillator circuit in the 50-MHz model is straightforward, relying on the drain-to-gate capacitance of the FET for feedback. A tap at four turns from the hot end of the toroid winding provides the

injection to the mixer through capacitor C7. In the 144- and 220-MHz converter the rf stage is identical to the 50-MHz version except for the tuning networks. L1, L2, and L3 are air wound, self-supporting, and are formed initially by winding wire around the threads of a 1/4-20 bolt. The turns of L1 are spread to permit adding taps prior to mounting on the board. The degree of interstage coupling in the two-meter model is controlled by the positions of L2 and L3. Since they are mounted at right angles, the coupling is very light. By changing the angle between these two coils, the passband may be optimized.

In the 144- and 220-MHz converter oscillator stages, Q3 is changed to an oscillator/tripler by replacing the source bias resistor with L6. Replace bypass capacitor, C13, with a suitable value to resonate L6 near the crystal frequency. Source-to-gate capacitance provides the feedback in this case. The drain tank is modified to provide output at the third harmonic, thus eliminating the need for a separate tripler stage. Q4 is used as an isolation amplifier running at very low current level (as controlled by R9) to provide attenuation of the adjacent harmonics. This stage is not needed for amplification of the oscillator signal but without the additional filtering, severe "birdies" may result from nearby fm or TV stations. In all three versions, a number of printed-circuit pads will be left over when construction is completed. These are the result of providing both bands on a common pc layout. For

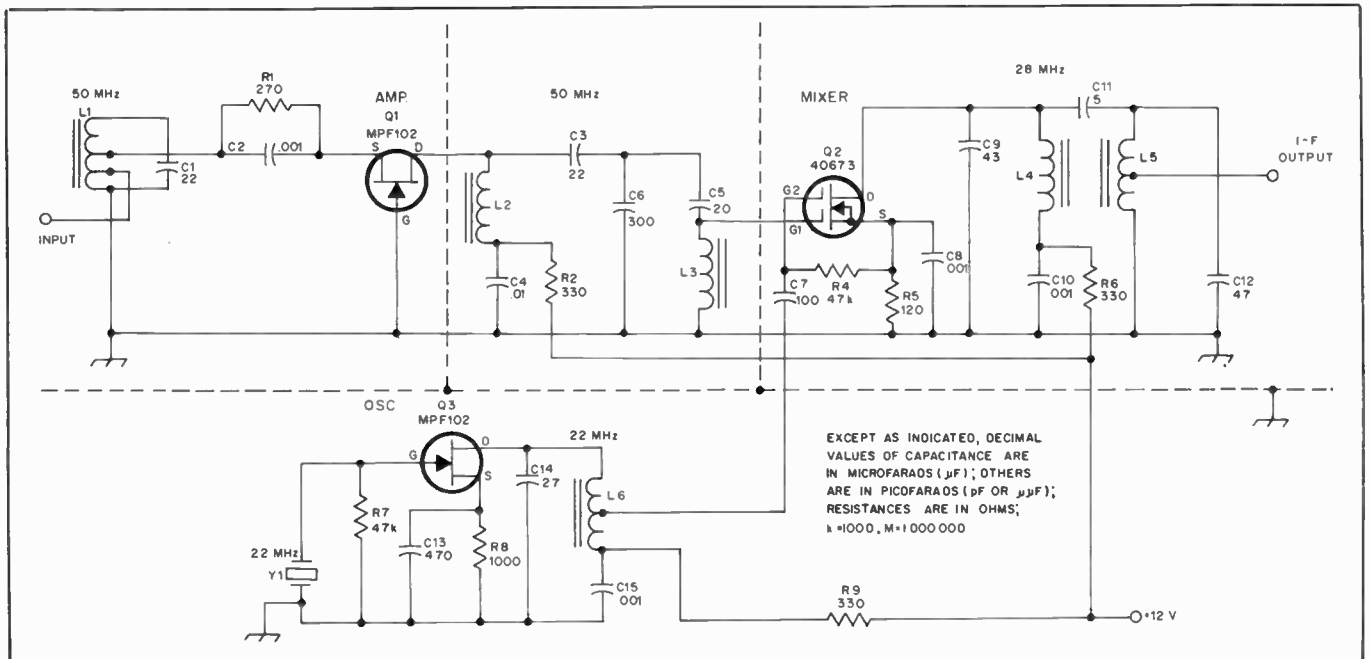


Fig. 31 — Schematic diagram of the 50-MHz converter. All resistors are 1/4-watt composition. C2, C8, C10 and C15 are 0.001  $\mu$ F disk ceramic. C4 is 0.01  $\mu$ F disk ceramic. All other capacitors are dipped mica

L1-L6, incl. — All no. 28 enam. wire wound on Amidon T-25-6 cores as follows: L1, 14 turns tapped at 4 turns and 6 turns; L2, 13 turns; L3,

12 turns; L4, 18 turns; L5, 18 turns tapped at 4 turns from hot end; L6, 26 turns tapped at 6 turns from hot end.

Y1 — 22-MHz crystal. International Crystal Mfg. Co. type EX.

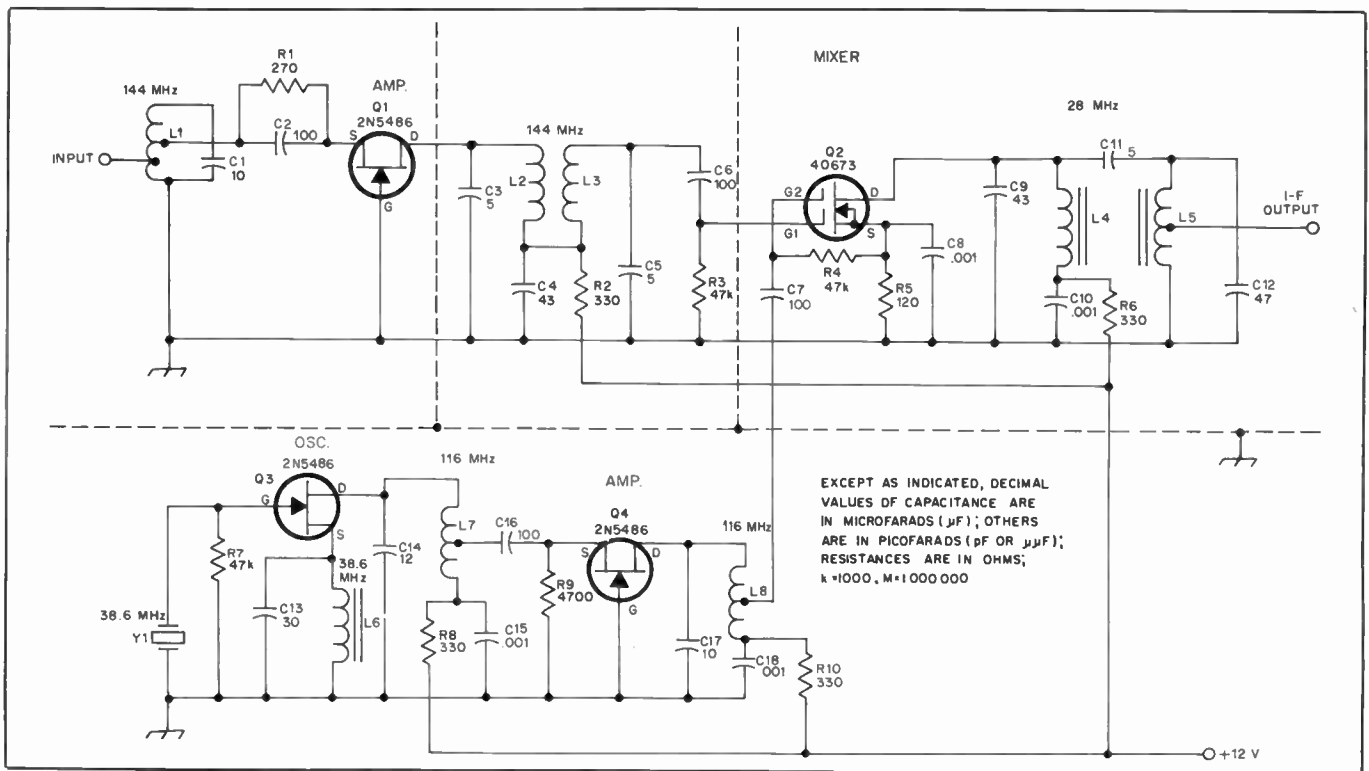


Fig. 32 — Schematic diagram of the 144-MHz converter. All resistors are 1/4-watt composition. C8, C10, C15 and C18 are 0.001- $\mu$ F disk ceramic. All other capacitors are dipped mica units.

L1, L2, L3, L7, L8 — All no 20 enam. wire formed by using the threads of a 1/4-20 bolt as a guide. L1, 5 turns tapped at 1-3/4 turns and 3/4 turn from cold end; L2, 5 turns; L3, 4 turns; L7, and L8, 5 turns tapped at 2 turns from hot end.

L4 — 18 turns no. 28 enam. wound on Amidon T-25-6 core.  
 L5 — 18 turns like L4, tapped at 4 turns from cold end.  
 L6 — 16 turns no. 28 enam wound on Amidon T-25-10 core

Y1 — 38.666-MHz crystal. International Crystal Mfg. Co. type EX.

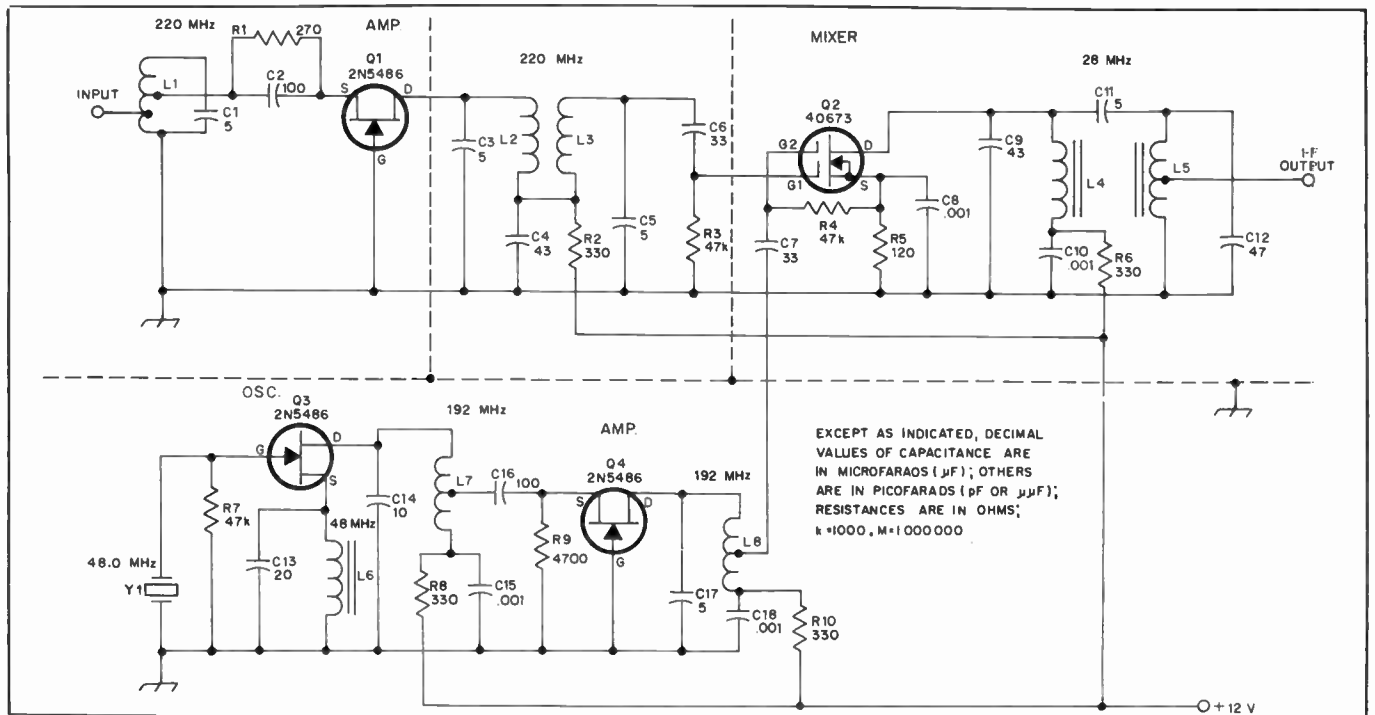


Fig. 33 — Schematic diagram of the 220-MHz converter. All resistors are 1/4-watt composition. C8, C10, C15 and C18 are 0.001- $\mu$ F disk ceramic. All other capacitors are dipped mica units.

L1, L2, L3, L7, L8 — All no. 20 enam. wire formed by using the threads of a 1/4-20 bolt as a guide. L1, 4 turns tapped at 1-1/2 turns and 3/4 turn from cold end; L2, 4 turns; L3, 2 turns; L7, 3 turns tapped at 1-1/2 turns from cold end, and

L8, 4 turns tapped at 2-1/2 turns from hot end.  
 L4 — 18 turns no. 28 enam. wound on Amidon T-25-6 core.  
 L5 — 18 turns like L4, tapped at 4 turns from cold end.

L6 — 18 turns no. 28 enam. wound on Amidon T-25-10 core.  
 Y1 — 48.000 MHz crystal International Crystal Mfg. Co. type EX.

example, the isolation amplifier following the oscillator is not used on 50 MHz. Therefore, this stage is bypassed by a jumper wire from L6 to C7. Five additional holes are located in the ground area along the centerline of the board and between rf and mixer stages. Component lead clippings are soldered into these holes to provide a mounting for the shield partitions, which are soldered to the wires where they extend through the board. Fig. 35 shows the parts layout for the three converters. Notice that one lead of C3 must reach past the ground hole and connect to the foil. R3 is not used on the 50-MHz converter.

### Alignment and Test

Perhaps the most difficult task in the project was the test and tune-up of the finished converter. A single test setup using a sweep generator, diode probe, and oscilloscope is a necessity to assure the flat response over the tuning range. Commercial attenuators can be used to calibrate each converter by the substitution method.

Tuning of the air-wound rf circuit for 144 and 220 MHz is accomplished by spreading or compressing the turns of the coils. After alignment, the windings are secured by a bead of Silastic compound along the coil to hold the turns in place.

The transistors used in the rf stage are also subject to some variation in noise figure. When this occurs, an rf FET should be carefully traded with an oscillator FET, since performance of the FET as an oscillator usually is satisfactory.

Small ceramic trimmers can be used in place of the fixed-value mica capacitors in the tuned circuits of these converters. The midrange of the trimmer should be approximately the value of the mica capacitors replaced. This procedure may simplify the tuning process of the converters where a sweep generator setup is not available. A little careful tweaking should give a reasonably flat response.

If trimmers are used, the rf input circuit should be tuned to the center of the desired response, 50.5 MHz as an example. This circuit tunes broadly and is not too critical. The rf interstage circuits should be stagger tuned, one at 50.0 MHz and the other at 51.0 MHz. As an example, the output i-f circuits can be tuned in a manner similar to the interstage circuits.

### A High-Performance 2-Meter Converter

Top performance is a requisite for vhf receivers during contests and when the operator is engaged in weak-signal work. The criteria are low noise, frequency stability and freedom from unwanted spurious responses in the overall receiver. The latter can be assured by using an LO chain which has proper spectral purity, and by using narrow-band filtering at the receiver front end. Additional benefits are

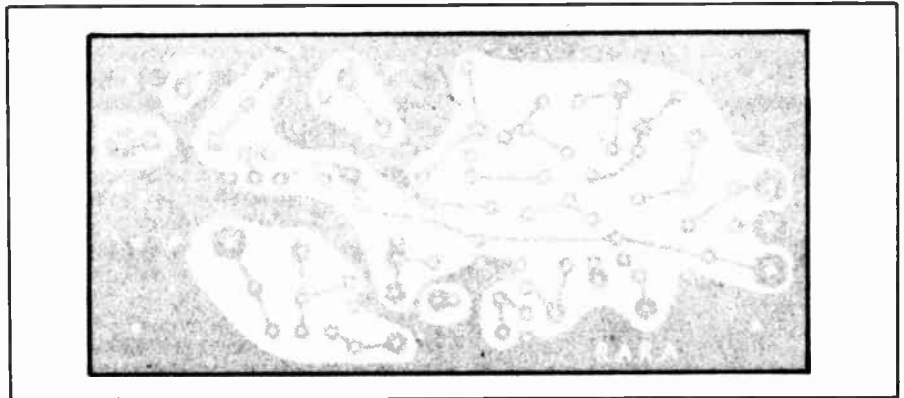


Fig. 34 — Scale-size layout for the pc board. The same pattern is used for each band. Foil side shown here.

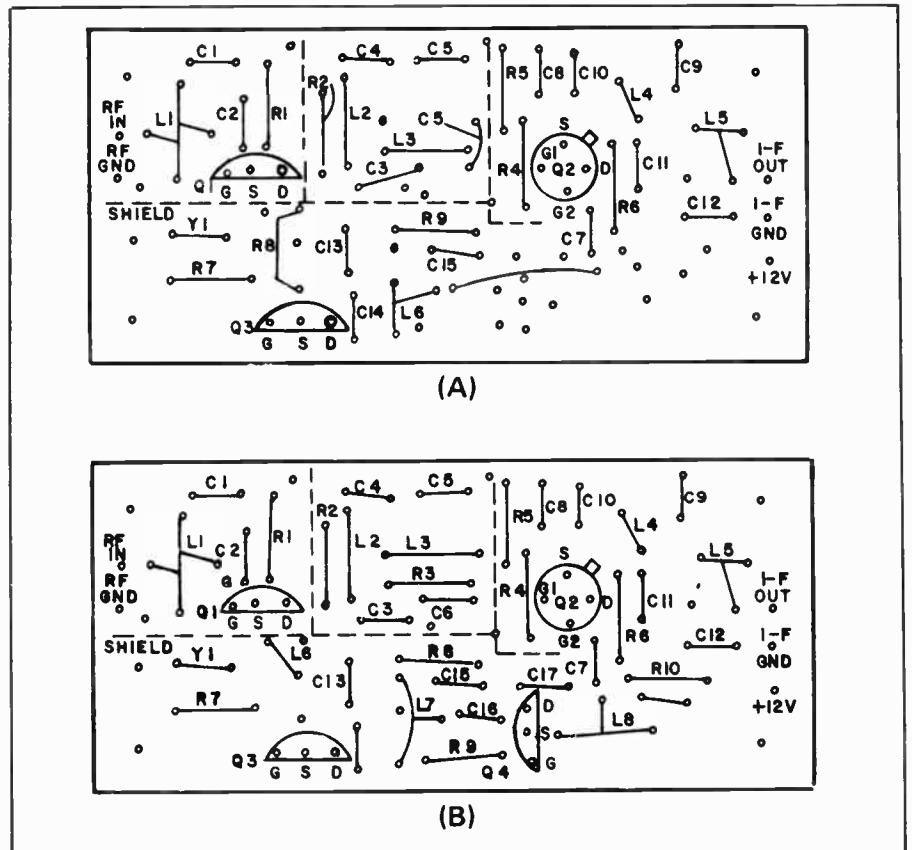


Fig. 35 — Parts-placement guide for the 50-MHz converter, A, and the 144- and 220-MHz converters, B. View is from the foil side of the board. Dashed lines show the location of shields that are soldered to short pieces of wire which project through holes in the pc board. The shields may be fabricated from sheet brass or copper, or scraps of copper-clad board material.

obtained when utilizing filtering at the i-f output of a vhf converter. This circuit, developed by W1FB, complies with the foregoing design and performance objectives. It is intended for use on ssb, cw and a-m, notably below 146 MHz. The dynamic range of this converter is excellent, owing in part to the use of a doubly balanced diode-ring mixer that is followed by a diplexer. The diplexer assures that the mixer is terminated in its characteristic impedance — 50 ohms.

An overall gain of 15 dB was measured

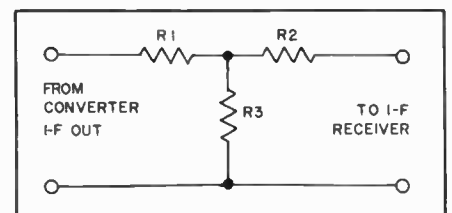


Fig. 36 — An i-f attenuator may be necessary if the receiver following the converter is exceptionally hot. Values for 6 dB: R1, R2 — 18 ohms; R3 — 68 ohms. For 10 dB: R1, R2 — 27 ohms; R3 — 39 ohms.



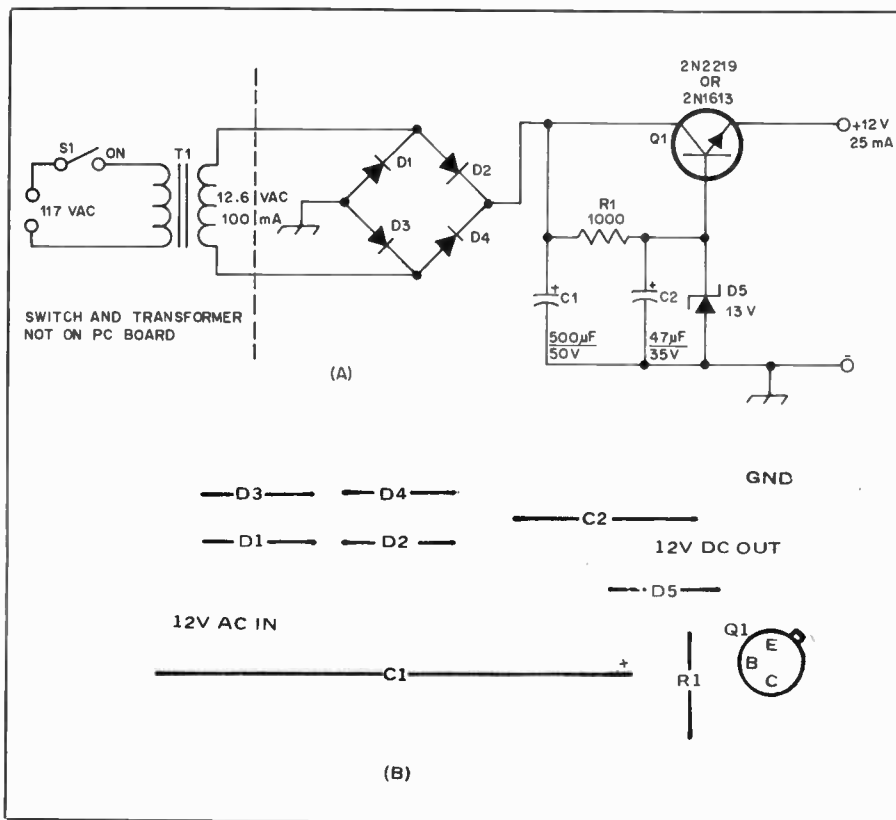


Fig. 37 — Schematic diagram and parts-placement guide for the power supply to the converters. The transformer is mounted external to the board. Pc board size is identical to the one used for the converters.

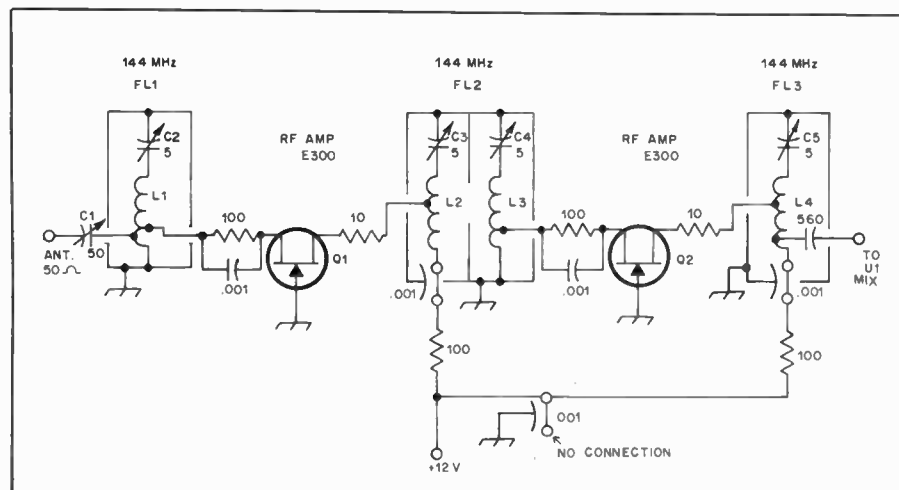


Fig. 38 — Schematic diagram of the converter front end. Fixed-value capacitors are disk ceramic. Feedthrough types are used where indicated. Resistors are 1/2-watt composition.  
 C1 — 50-pF ceramic trimmer (see text).  
 C2-C5, incl. — 5-pF capacitor. Subminiature air variable of glass piston trimmer of high-Q type.  
 E. F. Johnson 160-102 suitable. Johnson 193-4-1 (13 pF max.) used in this model.  
 L1-L4, incl. — 4 turns no. 16 bare or silver-plated copper wire, 5/8-inch ID × 1-1/4 inches (16 × 32 mm) long. Q1, Q2 sources tapped 1/2 turn above ground. Input and output taps are 1/4 turn from ground. Drain taps are 1/2 turn from high end of coils.  
 Q1, Q2 — Siliconix E300 JFET. 2N4416 suitable at slight reduction in performance.

for the composite converter. All spurious energy at the LO-chain output is -72 dB or greater below the desired output (116 MHz). A two-pole Butterworth filter is used at the i-f output of the converter. This 28-MHz filter prevents unwanted energy from the converter from reaching

the tunable i-f main receiver — a further aid to the elimination of birdies. The converter has a 3-dB bandwidth of 200 kHz. This is established by the highly selective four-resonator input filter which is similar to a helical resonator. The converter can be adjusted for any 200-kHz

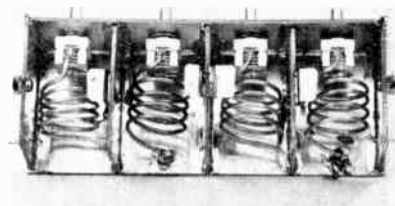


Fig. 39 — Closeup view of the interior of the rf front-end amplifier and bandpass filters. Spring-brass tabs are soldered to the divider walls to assure good electrical contact with the aluminum side plate (see text). A third 0.001-μF feedthrough capacitor was added to the lower edge of the third compartment from the left after this photograph was taken. It serves as a tie point for the 100-ohm decoupling resistors (see Fig. 38).

segment of the 2-meter band. The example given here was designed primarily for use from 144.0 to 144.2 MHz. In this case the tunable i-f is 28.0 to 28.2 MHz.

### RF Amplifiers and Filter

Fig. 38 shows the front-end section of the converter. C1 was not needed in the prototype model, but can be included in the interest of obtaining the lowest possible noise figure. The tap point to which C1 is connected is approximately 50 ohms without C1 in the circuit. L1 and C2 comprise the input resonator, FL1. Q1 operates in the common-gate mode. The source is tapped on L1 to provide an impedance match. A Siliconix E300 JFET is used at Q1 and Q2 in the interest of low noise and high dynamic range. It is rated by the manufacturer as having a typical noise figure of 1.3 dB at 100 MHz. The dynamic range is specified as 100 dB or greater. Power gain is listed as 17 to 20 dB in the common-gate mode. In this circuit the gain is set at approximately 10 dB per stage by means of the tap points on the resonators and the value of source-bias resistance. The 10-ohm resistors used in the drain leads of each transistor reduce the gain slightly. They are included for suppression of parasitic oscillations.

FL2 consists of two aperture-coupled resonators. The aperture is set for an insertion loss of roughly 5 dB in order to obtain the desired 200-kHz overall front-end selectivity. FL3 is the fourth resonator. Output is taken at 50 ohms by means of a 560-pF coupling capacitor. This circuit is unconditionally stable. The gate lead must be made as short as possible to ensure stability. It is returned to ground on the inner conductor of the pc-board double-clad module wall. Three 0.001-μF feedthrough capacitors and two 100-ohm resistors serve as the 12-volt decoupling elements. Q1 and Q2 are

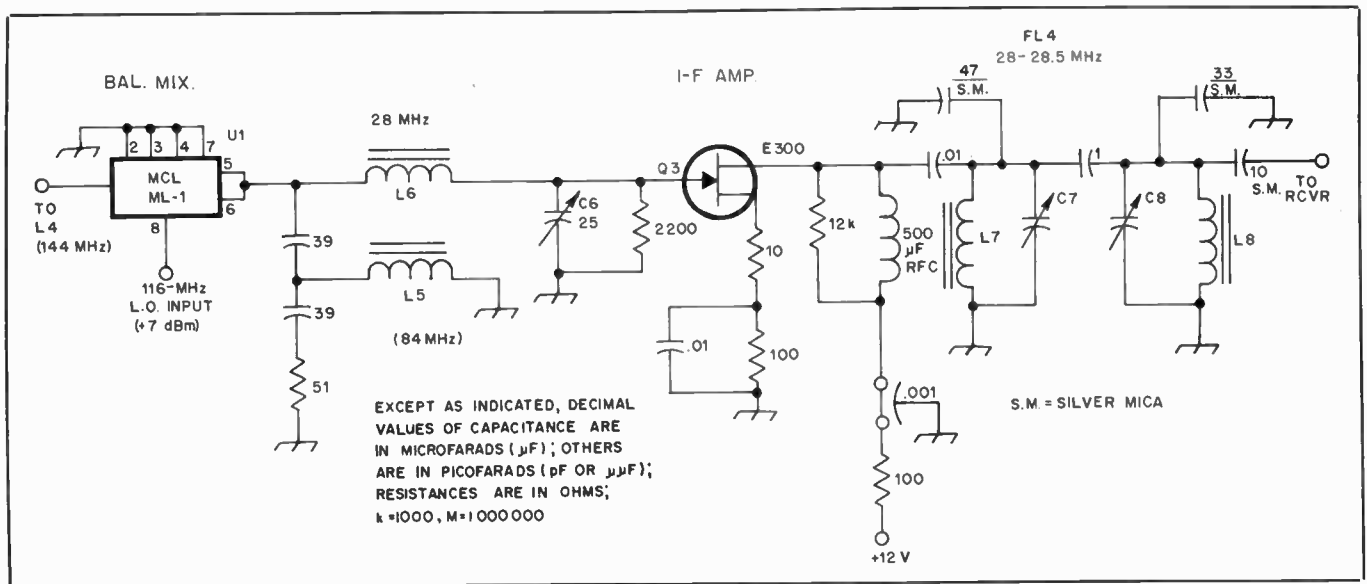


Fig. 40 — Schematic diagram of the passive mixer, diplexer and post-mixer amplifier. Fixed-value capacitors are disk ceramic except those shown as feedthrough types. Resistors are 1/2-watt composition.

C6-C8, incl. — 35-pF ceramic or Mylar trimmer. Solder 47- and 33-pF silver mica capacitors across pc foils for C7 and C8, respectively. L5 — 5 turns no. 24 enam. wire on T-50-6 toroid core (0.09 μH).

L6 — 21 turns no. 24 enam. wire on T-50-6 toroid core (1.8 μH). L7, L8 — 10 turns no. 24 enam. wire on T-50-6 toroid core (0.48 μH). Q3 — Siliconix E300 JFET or 2N4416.

U1 — Diode-quad doubly balanced mixer. MCL SRA-1 or SBL1, or Cimarron CM-1 suitable.

mounted on the outside wall of the rf-amplifier module.

### Mixer and Post-Mixer Amplifier

U1 and Q3 of Fig. 40 are contained in the second module. U1 is a four-diode doubly balanced mixer assembly. It has a conversion loss of approximately 8 dB. This requires the inclusion of a post-mixer i-f amplifier, Q3. The latter is set for a gain of roughly 8 dB. LO injection is supplied to U1 at 116 MHz. The LO power is +7 dBm (approximately 0.5 volt rms across 50 ohms).

L5, the 51-ohm resistor and two 39-pF capacitors form the diplexer in combination with the L network (L6/C6). L5 and the 39-pF capacitors comprise a high-pass network with a loaded Q of 1 ( $X_L$  and  $X_C = 50$ ). The cutoff frequency of the network is three times the i-f (84 MHz). The 51-ohm resistor serves as a termination for the mixer. L6 and C6, by virtue of the low-pass characteristic, help prevent 116- and 144-MHz energy from reaching Q3. This network is designed to match 50 ohms to 2200 ohms.

Q3 is another E300 FET, chosen for the low-noise characteristic. An unbypassed 10-ohm resistor is used in the source to cause degeneration in the interest of stability. A two-pole Butterworth band-pass filter is used at the output of Q3. It has a 3-dB bandwidth of 500 kHz and is tuned for a center frequency of 28.250 MHz. The filter input characteristic is 12,000 ohms. The 10-pF output coupling capacitor provides a 50-ohm terminal impedance for looking into a 50-ohm tunable i-f receiver. The circuit of Fig. 40 is contained in a module fashioned from

single-sided pc board. The copper surfaces are inside the box.

### Local-Oscillator Section

A simple overtone oscillator is used at the beginning of the LO chain (Fig. 41). C9 can be adjusted to shift the oscillator frequency by a small amount. Greater range for netting the crystal can be obtained by inserting a small amount of inductive reactance between C6 and Y1.

A tuned toroidal transformer, T1, is adjusted for resonance at approximately 58 MHz. C10 is set for reliable starting of the oscillator (consistent with high output) when the operating voltage is turned on. Zener-diode regulation (D1) is used to aid oscillator stability.

Output from Q4 is routed to a fed-back, broadband, Class A amplifier, Q5. The feedback provides a 50-ohm input characteristic and contributes to excellent stability of the 58-MHz amplifier. Negative feedback and emitter degeneration are used at Q5 and Q6 for this purpose. T2 is a broadband 4:1 toroidal transformer. It transforms the collector impedance of Q5 to 50 ohms. Output is taken at this point and fed to a separate module which contains T3 through FL5.

The output from Q5 is used to drive a two-diode balanced doubler, D2 and D3. A trifilar-wound broadband toroidal transformer (T3) couples the energy to the doubler. L9 and C11 comprise a 116-MHz resonator which serves as an impedance transformer between the diodes and Q6. This resonator also suppresses energy at other than 116 MHz. The diodes and the base of Q6 are tapped close to ground on L9 to effect an impedance match. The

stage gain from L9 to the output of FL5 was measured as 16 dB. The gain is needed to ensure a +7-dBm injection level at U1, the mixer.

Another broadband step-down transformer, T4, is used to effect an impedance match. It transforms the collector impedance of Q6 to the 50-ohm input impedance of band-pass filter FL5. The latter greatly suppresses the 58-MHz energy passing through Q6. It also rejects the harmonics of the 116-MHz LO chain. Fig. 42 shows the spectral output of the LO chain as viewed on an HP analyzer. It can be seen that all spurious responses are 72 dB or greater below the desired 116-MHz energy level. Imagine that the carrier amplitude is full scale when comparing the levels of the spurs. The 116-MHz carrier has been suppressed by means of a trap to prevent front-end overloading of the analyzer. This has no effect on the accuracy of the spur-level readings. The full-scale line at the far left in Fig. 42 is the zero-reference blip from the analyzer. It should be ignored.

Q4, Q5 and the related circuitry are contained in a module made from single-sided pc board. The copper foil is on the inside of the box. D2, D3, Q6 and related components are in a separate container. Double-sided pc board is used.

### Construction Data

Modular construction is used in this design so that various portions of the circuit can be isolated from one another in an effective manner. Another benefit to this style of construction is that the builder can experiment with other circuits (substitutes) and install them without

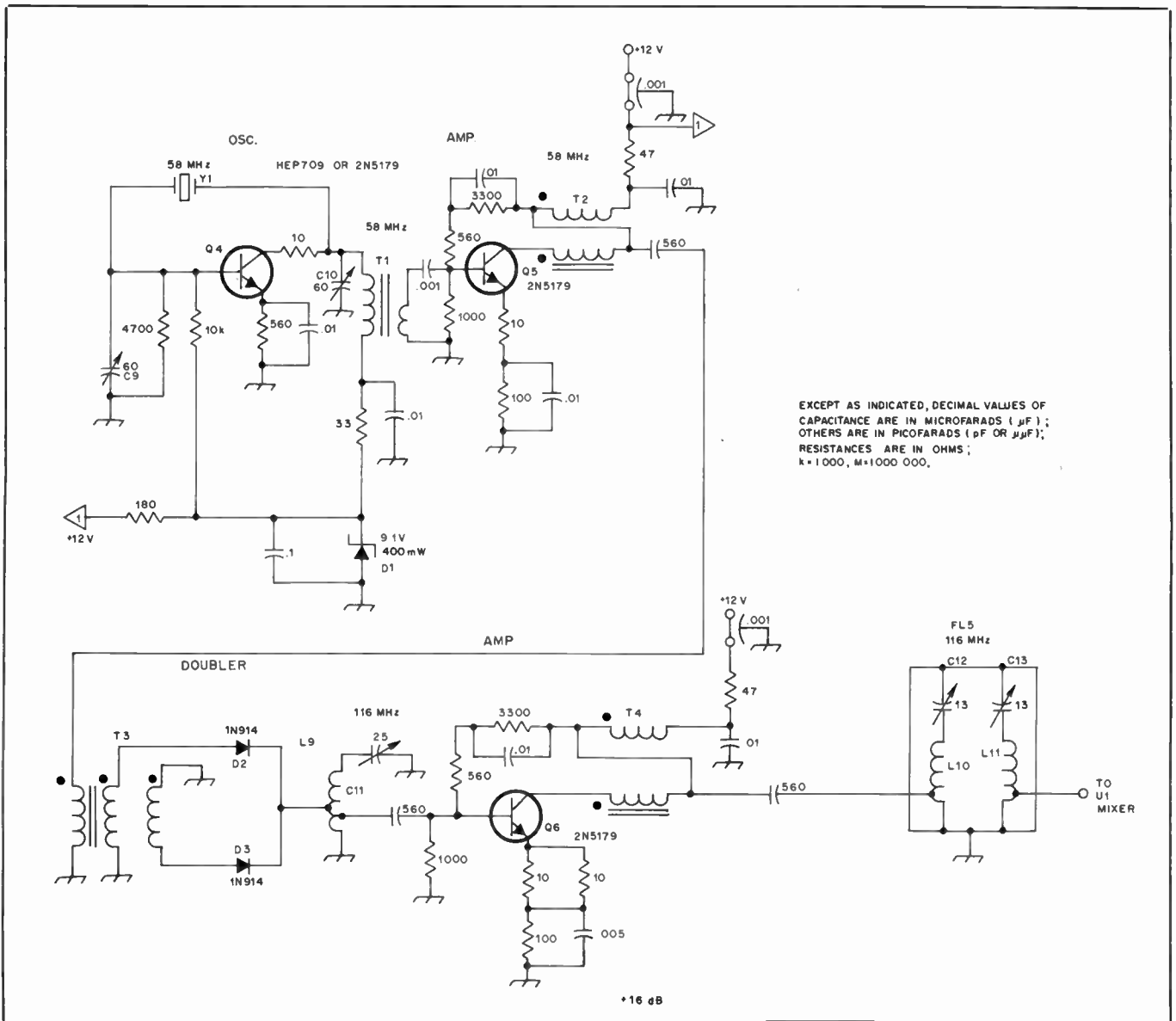


Fig. 41 — Schematic diagram of the local-oscillator chain. Fixed-value capacitors are disk ceramic except those shown as feedthrough types. Resistors are 1/2-watt composition.

C9, C10 — Miniature 60-pF ceramic or Mylar trimmer.

C11 — 25-pF miniature ceramic or Mylar trimmer.

C12, C13 — 13-pF subminiature trimmer or glass-piston type, high Q. E. F. Johnson 193-4-1 used in this model.

D1 — Zener diode, 9.1 V, 400 mW or 1 watt.

D2, D3 — High-speed silicon switching diode or

hot-carrier diode. 1N914 used here.

L9 — 7 turns no. 16 bare wire, 1/4-inch ID  $\times$  1/2 inch long (6.3  $\times$  12.7 mm). Tap diodes 1-3/4 turns above ground. Tap Q6 1-1/4 turns from ground.

L10, L11 — 7 turns no. 16 bare wire, 1/4-inch ID  $\times$  3/4 inch long (6.3  $\times$  19 mm). Tap 1 turn above ground. Center-to-center spacing is 3/4 inch (19 mm).

Q4-Q6, incl. — 2N5179 or Motorola HEP709 npn transistor.

T1 — 8 turns no. 24 enam. wire on T-50-6 toroid core (0.25  $\mu\text{H}$ ). Secondary has 3 turns over primary winding, no. 24 enam.

T2, T4 — 6 bifilar turns no. 30 enam. wire on Amidon FT-23-43 toroid core.

T3 — 7 trifilar turns no. 30 enam. wire on FT-23-43 toroid core.

disrupting the complete converter. Most of the circuit boards are much larger than necessary. This was done with a view toward possible revisions to the circuits of the first model. Those who are skilled at layout work may want to compress the circuits somewhat.

Small Teflon press-fit feedthrough bushings are used as input and output terminals for the various modules. They were purchased at a flea market, so the original source is not known. Any low-loss miniature bushing should be

suitable as a substitute. Alternatively, the RG-174 miniature coaxial cables can be routed directly into and out of the modules for connection to the circuits. For attachment to the +12-volt supply, each module has 0.001- $\mu\text{F}$  feedthrough capacitors. These components are mounted on the box walls. Small Teflon feedthrough bushings are used at Q1 and Q2 to permit circuit connections for the FET leads inside the module. The FETs are installed on the outer wall of the front-end module.

All of the modules are affixed to the main chassis 7  $\times$  11  $\times$  2 inches (180  $\times$  280  $\times$  50 mm) by means of no. 6 spade bolts. The latter are bolted to the side walls of the modules. The rf amplifier assembly uses the chassis surface as part of the box shield. An aluminum plate is attached to the side wall of the module by means of spade bolts. This type of construction was used to ease assembly of the front end filter and amplifiers. Spring-brass fingers are soldered to the compartment dividers to assure solid contact to the aluminum



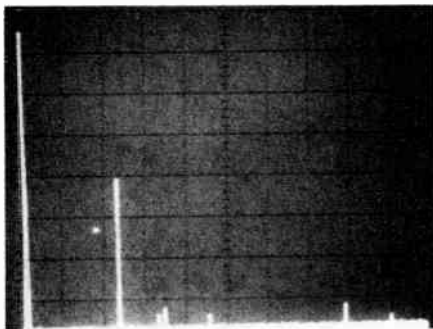


Fig. 42 — Spectral output of the 116-MHz LO chain showing all spurious responses at  $-72$  dB or greater. The carrier has been suppressed by means of a 116-MHz trap to prevent front-end overload of the analyzer. In effect, it is at full scale. The vertical line at the far left is a zero-reference response from within the analyzer. Vertical scale is 10 dB/div. and the horizontal scale is 50 MHz/div.

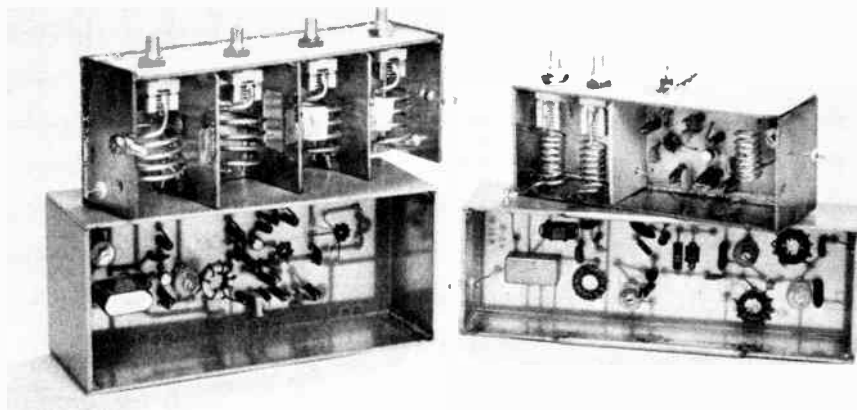


Fig. 43 — View of the assembled modules before the mounting bolts and other final touches were added. The LO assembly is at the lower left, with the LO amplifier and filter at the upper right. The mixer and i-f filter module is at the lower right.

side plate (see Fig. 43). The aperture size between L2 and L3 of FL2 is  $1 \times 5/8$  inch ( $25 \times 16$  mm). Each resonator compartment measures  $1-1/4 \times 1-1/4 \times 2$  inches ( $32 \times 32 \times 50$  mm). The coils are centered in the compartments.

Dimensions for the mixer/post-mixer amplifier assembly are  $5-3/4 \times 1-7/8$  inches ( $155 \times 50$  mm), length and width. The box height is  $1-1/2$  inches (3.8 cm). This container and the one for the low-level stages of the LO chain do not have copper on the outside. Therefore it is necessary to provide a grounding contact for the press-fit U-shaped aluminum covers. Shim-brass or flashing-copper strips are located opposite one another on the upper lips of the side walls. The strips are approximately  $1-1/2$  inches long (38 mm) and  $3/4$  inch (19 mm) wide. They are soldered to the inner walls of the box, then bent over the edges and down the outside of the box walls. This provides a ground contact for the box covers.

Single-sided glass-epoxy pc-board material is used for all of the etched circuits. A ground-bus copper strip is retained around the entire perimeter of each board. This permits the builder to solder the boards into the shield boxes.

The low-level section of the LO chain is housed in a box which is  $5-1/4$  inches (135 mm) long,  $2-1/4$  inches (58 mm) wide and 2 inches (51 mm) high. The last half of the LO circuit is contained in an enclosure which is  $4-1/8$  inches (105 mm) long,  $1-1/2$  inches (38 mm) wide and  $1-1/4$  inches (32 mm) high. The end compartment houses the bandpass filter. It is  $1-1/2 \times 1-1/2$  inches ( $38 \times 38$  mm) square. The depth of the compartment is 1 inch (25 mm). The lower surface of the filter compartment is part of the main pc board, the end of which has not been stripped of copper.

The inner and outer copper surfaces of the modules which use double-clad pc board sides should be connected together

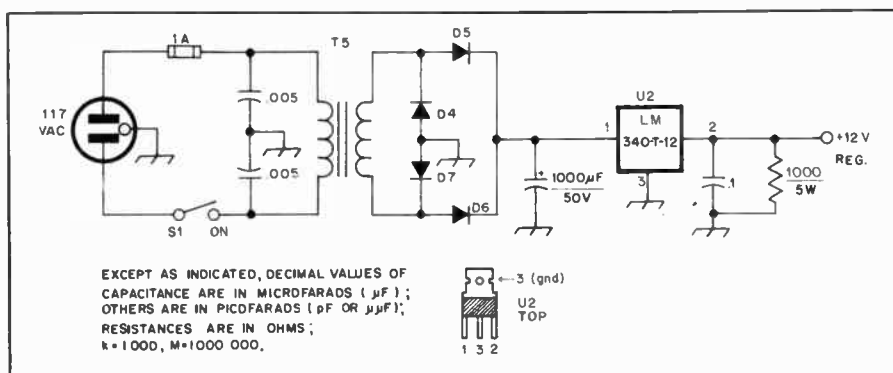


Fig. 44 — Schematic diagram of the regulated 12-volt power supply used with the 2-meter converter. Capacitors are disk ceramic except the one with polarity marked, which is electrolytic. D4-D7, incl., are 1-A, 50-PRV silicon diodes. S1 is a spst toggle switch. T5 delivers 24V ac at 1 A, and U2 is a National Semiconductor three-terminal regulator.

to assure electrical contact. This can be done by running short lengths of bare wire through the box walls at four points per wall, then soldering the wires in place on each surface (inner and outer). Alternatively, angle stock can be made of flashing copper and soldered across each corner of the box. The U-shaped lids will complete the electrical contacts when installed.

#### Alignment

Choose a 200-kHz segment of the 2-meter band that suits your purposes. Place a 2-meter signal at the midpoint of that tuning range (144.1 MHz for coverage from 144.0 to 144.2 MHz). Connect the converter to a receiver tuned and peaked at 28.1 MHz. Apply power to the converter and locate the 2-meter signal in the receiver tuning range. It should fall close to 28.1 MHz. Observe the receiver S meter and adjust all of the converter tuned circuits for maximum meter reading. This procedure should be repeated two or three times again, using the weakest 2-meter signal that will provide needle deflection on the S meter.

This circuit should provide a noise figure of less than 4 dB with careful adjustment. C1 of Fig. 38 may be required to achieve this result. It was not used in the ARRL model because accurate noise-figure measuring equipment was not available. However, without the input capacitor, a 0.1- V signal into the converter provided a loud cw response in the tunable i-f receiver, roughly equivalent to an RST of 559. The test receiver was a Kenwood TS-820 with a 500-Hz i-f filter. A similar front end was built earlier, using 2N4416 FETs. When used with a 2-meter fm receiver it provided 20 dB of quieting with a  $0.18 \mu\text{V}$  input signal.

#### Power Supply

A well-filtered 12-volt regulated dc supply is recommended for use with this converter. It should be capable of accommodating a load current of 100 mA or greater. The unit shown here contains a 12-volt regulated supply under the main chassis. A red LED is used as the on-off indicator. The circuit is shown in Fig. 44. A bottom plate can be added to the chassis. Adhesive-backed plastic feet (four)



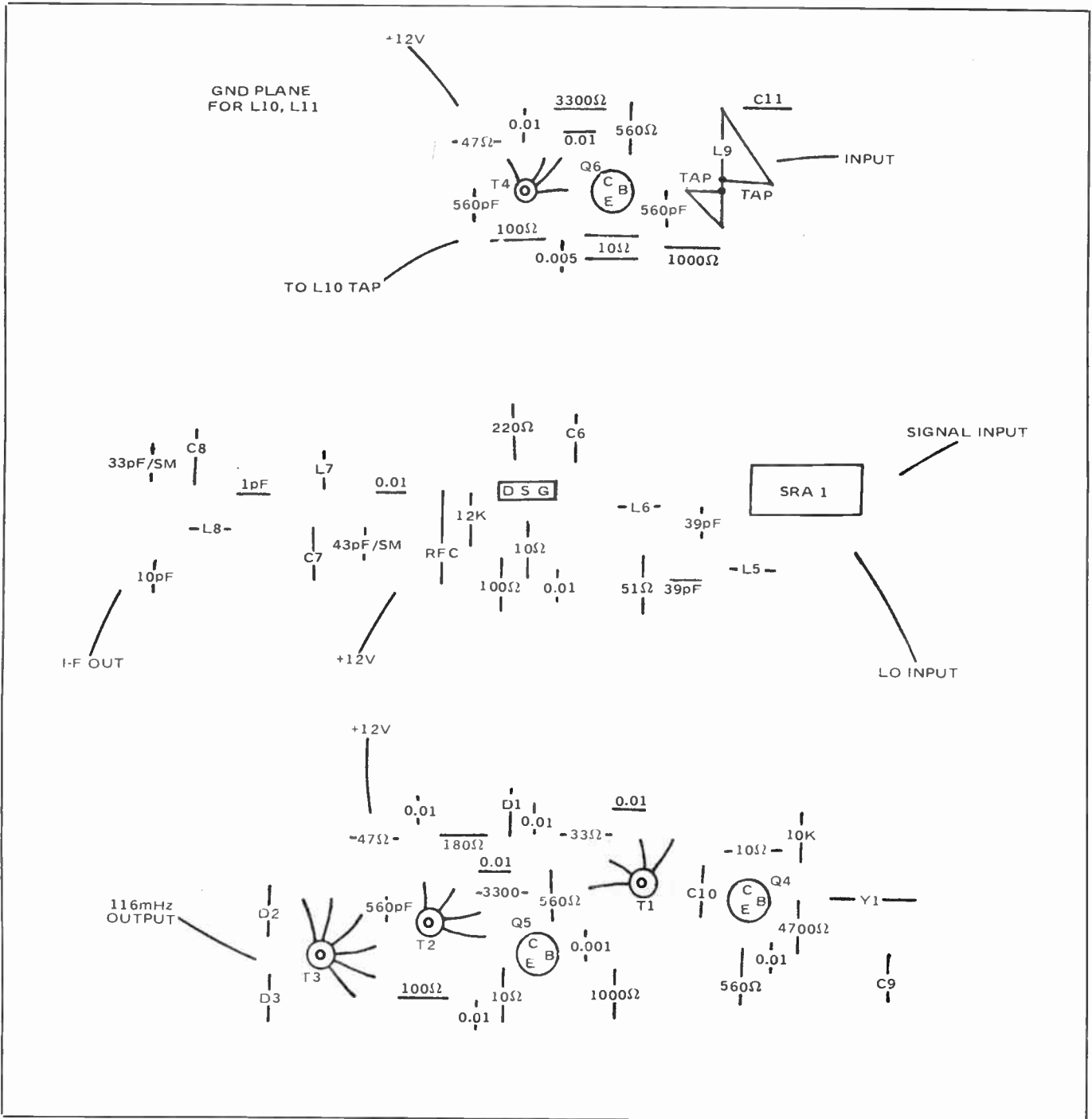


Fig. 45 — Scale layouts and parts-placement guides for the three circuit boards. Views are shown from the bottom (etched sides) of the boards.

should be affixed to the bottom plate to prevent scratching the operating desk.

Pc-board layouts and parts-placement guides are given in Fig. 45. The drawings show the etched sides of the boards. Each board is illustrated to scale.

### Interdigital Converter for 1296 or 2304 MHz

In a world where rf spectrum pollution is becoming more serious, even into the microwave region, it is almost as important to keep unwanted signals out of a

receiver as it is to prevent radiation of spurious energy. An interdigital filter was described some years ago, featuring low insertion loss, simplicity of construction, and reasonable rejection to out-of-band signals. It could be used in either transmitters or receivers.

This twice-useful principle has now been put to work again — as a mixer. Again, the ease of construction and adaptation leads many to wonder that it had not been thought of before. It was first described by W2CQH in January

1974 *QST*.

### A Filter and Mixer

A layout of the microwave portions of both converters is shown in Fig. 46. The structure consists of five interdigitated round rods, made of 3/8-inch (9.5 mm) OD brass or copper tubing. They are soldered to two sidewalls and centrally located between two ground-planes made of 1/16-inch (1.6 mm) sheet brass or copper-clad epoxy fiberglass. One ground plane is made larger than the microwave

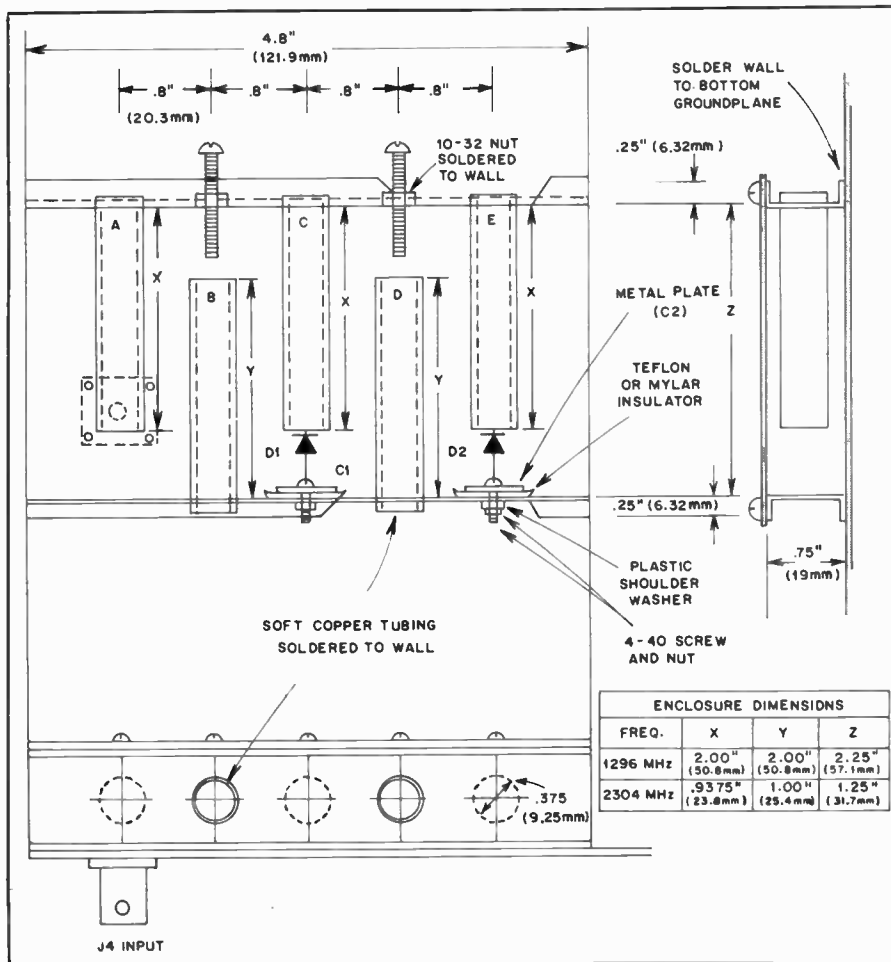


Fig. 46 — Dimensions and layout for the filter and mixer portions of the interdigital converters. The signal input is to the left rod, labeled "A." Local-oscillator injection is through the diode to rod "E." D1 is the mixer diode, connected to the center rod in the assembly.

assembly and thus provides a convenient mounting plate for the remainder of the converter components.

The sidewalls are bent from 0.032-inch thick sheet brass or they can be made from 1/4 × 3/4-inch (6 × 19 mm) brass rod. One edge of each sidewall is soldered to the larger ground plane. The other edge is fastened to the smaller ground plane by 4-40 machine or self-tapping screws, each located over the centerline of a rod. The sidewall edges should be sanded flat, before the ground plane is attached, to assure continuous electrical contact. Note that no end walls are required since there are no electric fields in these regions.

Electrically, rods A, B, and C comprise a one-stage, high-loaded-Q ( $Q_L = 100$ ), interdigital filter<sup>6</sup> which is tuned to the incoming signal frequency near 1296 or 2304 MHz. The ungrounded end of rod A is connected to a BNC coaxial connector and serves as the coupling section to the filter input. Rod B is the high-Q resonator and is tuned by a 10-32 machine screw. Rod C provides the filter output-coupling section to the mixer diode, D1.

The mixer diode is a Hewlett-Packard

<sup>6</sup> Fisher, "Interdigital Bandpass Filters for Amateur VHF/UHF Applications," *QST*, March, 1968.

5082-2577 Schottky-barrier type which is available from distributors for about \$4. The cheaper 5082-2835, selling for 90 cents, can be used instead, but this substitution will increase the 2304-MHz mixer noise figure by approximately 3 dB.

One pigtail lead of the mixer diode is tack-soldered to a copper disk on the ungrounded end of rod C. Care should be taken to keep the pigtail lead as short as possible. If rod C is machined from solid brass stock, then it is feasible to clamp one of the mixer-diode leads to the rod end with a small setscrew. This alternative method facilitates diode substitution and was used in the mixer models shown in the photographs.

Fig. 46 also shows that the other end of D1 is connected to a homemade 30-pF bypass capacitor, C1, which consists of a 1/2-inch-square copper or brass plate clamped to the sidewall with a 4-40 machine screw. The dielectric material is a small sheet of 0.004-inch (0.1 mm) thick Teflon or mylar. A 4-40 screw passes through an oversize hole and is insulated from the other side of the wall by a small plastic shoulder washer.

In the first converter models constructed by the author and shown in the

Table 4

Converter Specifications

	1296 MHz	2304 MHz
Noise figure	5.5 dB	6.5 dB
Conversion gain	20 dB	14 dB
3-dB bandwidth	2 MHz	7 MHz
Image rejection	18 dB	30 dB
I-F output	28 MHz	144 MHz

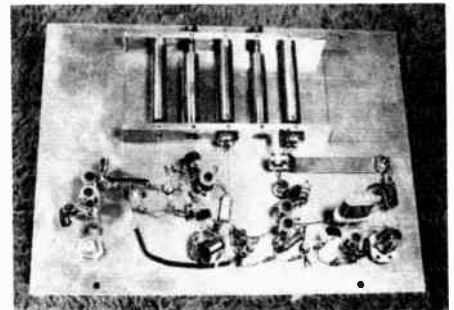


Fig. 47 — The converter for 1296 MHz. This unit was built by R. E. Fisher, W2CQH. While the mixer assembly (top center) in this model has solid brass walls, it can be made from lighter material, as explained in the text and shown in Fig. 46. The i-f amplifier is near the center, just above the mixer-current-monitoring jack, J1. A BNC connector at the lower left is for 28-MHz output. The local oscillator and multiplier circuits are to the lower right. Note that L6 is very close to the chassis, just above the crystal. The variable capacitor near the crystal is an optional trimmer to adjust the oscillator to the correct frequency.

photographs, C1 was a 30-pF button mica unit soldered to the flange of a 3/8-inch diameter threaded panel bearing (H. H. Smith No. 119). The bearing was then screwed into a threaded hole in the sidewall. This provision made it convenient to measure the insertion loss and bandwidth of the interdigital filters since the capacitor assembly could be removed and replaced with a BNC connector.

Rods C, D, and E comprise another high loaded-Q ( $Q_L = 100$ ) interdigital filter tuned to the local oscillator (LO) frequency. This filter passes only the fourth harmonic (1268 or 2160 MHz) from the multiplier diode, D2. The two filters have a common output-coupling section (rod C) and their loaded Qs are high enough to prevent much unwanted coupling of signal power from the antenna to the multiplier diode and LO power back out to the antenna.

The multiplier diode is connected to the driver circuitry through C2, a 30-pF bypass capacitor identical to C1. D2 is a Hewlett-Packard 5082-2811 although the 5082-2835 works nearly as well. Fifty milliwatts drive at one-quarter of the LO frequency is sufficient to produce 2 mA of mixer diode current, which represents

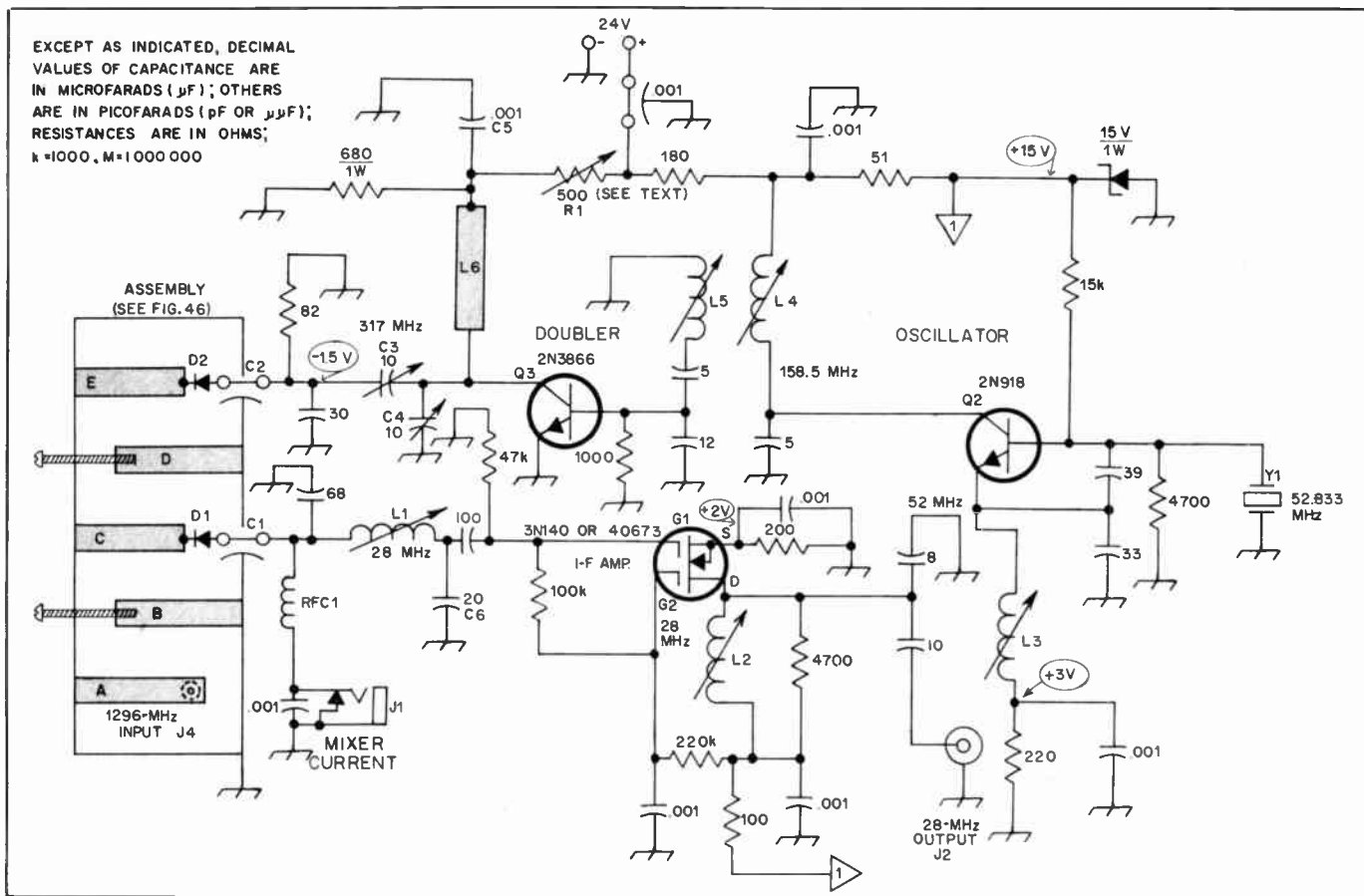


Fig. 48 — Schematic diagram of the 1296-MHz converter with oscillator and multiplier sections included. Dimensions for the filter and mixer assembly are given in Fig. 46.

- C1, C2 — 30-pF homemade capacitor. See text and Fig. 1.
- C3, C4 — 0.8- to 10-pF glass trimmer, Johanson 2945 or equiv.
- C5 — 0.001- $\mu\text{F}$  button mica.
- C6 — 2- to 20-pF air variable, E. F. Johnson 189-507-004 or equiv.

- D1 — Hewlett Packard 5082-2577 or 5082-2835.
- D2 — Hewlett Packard 5082-2811 or 5082-2835.
- J1 — Closed-Circuit jack.
- J2 — Coaxial connector, type BNC acceptable.
- L1, L2 — 18 turns no. 24 enam. on 1/4-inch (6.3-mm) OD slug-tuned form (1.5  $\mu\text{H}$  nominal).
- L3 — 10 turns like L1 (0.5  $\mu\text{H}$ ).

- L4, L5 — 6 turns like L1 (0.2  $\mu\text{H}$ ).
- L6 — Copper strip, 1/2-inch wide  $\times$  2-1/2-inches (127  $\times$  635 mm) long. See text and photographs.
- RFC1 — 33  $\mu\text{H}$ , J. W. Miller 74F33SA1 or equiv.

about 1 milliwatt of the local-oscillator injection. A Schottkey-barrier was chosen over the more familiar varactor diode for the multiplier because it is cheaper, more stable, and requires no idler circuit.

Fig. 48 shows the schematic diagram of the 1296 to 28 MHz converter. All components are mounted on a 7  $\times$  9-inch (178  $\times$  229 mm) sheet of brass or copper-clad epoxy-fiberglass board. As mentioned earlier, this mounting plate also serves as one ground plane for the microwave mixer. When completed, the mounting plate is fastened to an inverted aluminum chassis which provides a shielded housing.

**Oscillator and Multipliers**

The nonmicrowave portion of the converter is rather conventional. Q1, a dual-gate MOSFET, was chosen as the 28-MHz i-f amplifier since it can provide 25 dB of gain with a 1.5-dB noise figure. The mixer diode is coupled to the first

gate of Q1 by a pi-network matching section. It is most important that the proper impedance match be achieved between the mixer and i-f amplifier if a low noise figure is to be obtained. In this case, the approximately 30-ohm output impedance of the mixer must be stepped up to about 1500 if Q1 is to yield its rated noise figure of 1.5 dB. It is for this reason that a remote i-f amplifier was not employed, as is the case with many contemporary uhf converters.

Q2 functions in an oscillator-tripler circuit which delivers about 10 milliwatts of 158.5-MHz drive to the base of Q3. The emitter coil, L3, serves mainly as a choke to prevent the crystal from oscillating at its fundamental frequency. Coils L4 and L5, which are identical, should be spaced closely such that their windings almost touch.

Q3 doubles the frequency to 317 MHz, providing about 50 milliwatts drive to the multiplier diode. It is important that the emitter lead of Q3 be kept extremely

short; 1/4-inch (6.3 mm) is probably too long. L6, the strip-line inductor in the collector circuit of Q3, consists of a 1/2  $\times$  2-1/2-inch (127  $\times$  635-mm) piece of flashing copper spaced 1/8-inch (3-mm) above the ground plane. The cold end of L6 is bypassed to ground by C5, a 0.001- $\mu\text{F}$  button mica capacitor.

The multiplier circuits are tuned to resonance in the usual manner by holding a wavemeter near each inductor being tuned. Resonance in the Q3 collector circuit is found by touching a VTVM probe (a resistor must be in the probe) to C2 and adjusting the Johanson capacitors until about -1.5 volts of bias is obtained. The 317- to 1268-MHz multiplier cavity is then resonated by adjusting the 10-32 machine screw until maximum mixer current is measured at J1. When resonance is found, R1 should be adjusted so that about 2 mA of mixer current is obtained. As an alternative to mounting a potentiometer in the converter, once a value of resistance has been found that

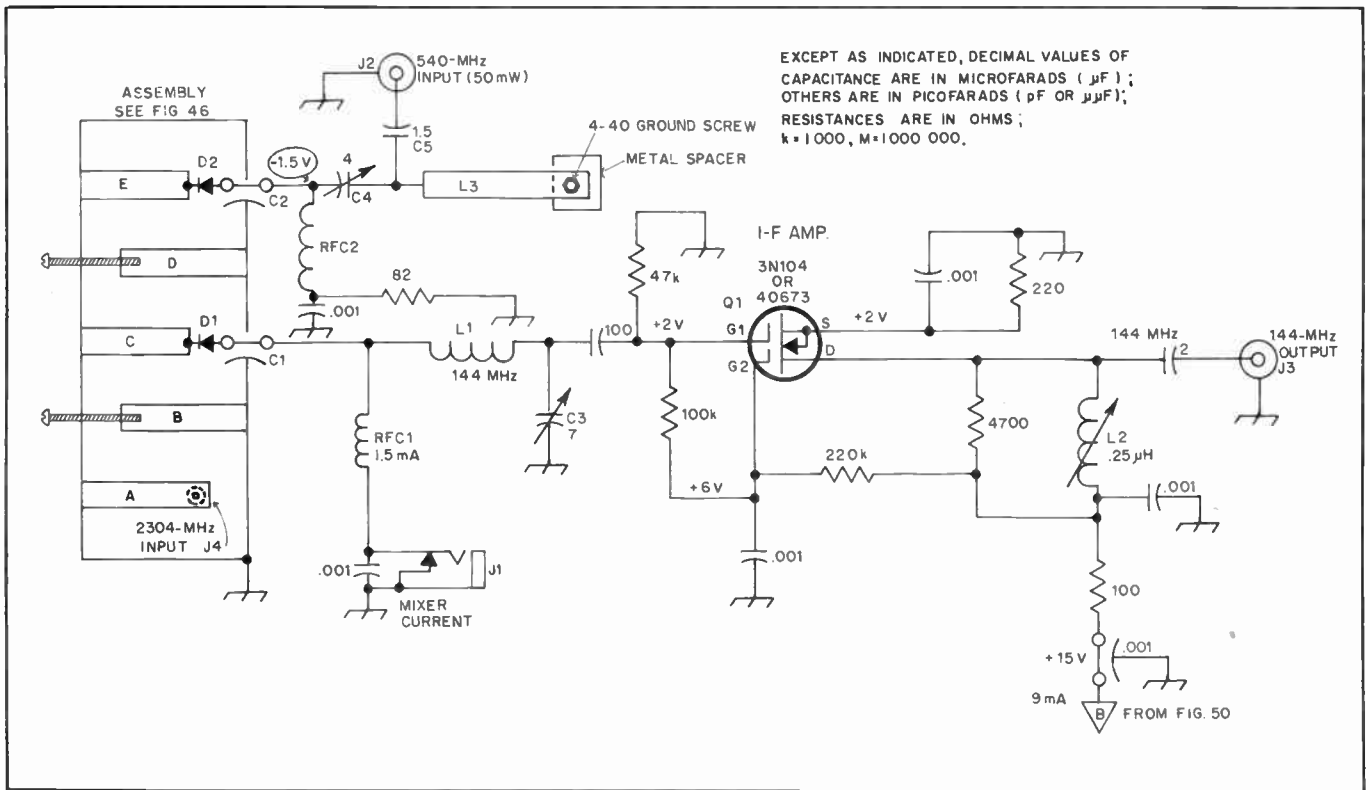


Fig. 49 — Schematic diagram of the 2304-MHz version of the converter, with the i-f amplifier. The oscillator and multiplier circuits are constructed separately.

C1, C2 — 30-pF homemade capacitor (see text).  
 C3, C4, C5 — 0.8- to 10-pF glass trimmer, Johanson 2945 or equiv.  
 D1 — Hewlett Packard 5082-2577 or 5082-2835.  
 D2 — Hewlett Packard 5082-2811 or 5082-2835.

J1 — Closed-circuit jack.  
 J2, J3, J4 — Coaxial connector, type BNC.  
 L1 — 5 turns no. 20 enam., 1/4-inch ID  $\times$  1/2-inch long. (6.35  $\times$  12.7 mm).  
 L2 — 6 turns no. 24 enam., on 1/4-inch OD slug-tuned form (0.25  $\mu\text{H}$ ).  
 L3 — Copper strip 1/2  $\times$  2-11/16 inches (13  $\times$  69 mm). See text and photographs.  
 RFC1 — Ohmite Z-144 or equiv.  
 RFC2 — Ohmite Z-460 or equiv.

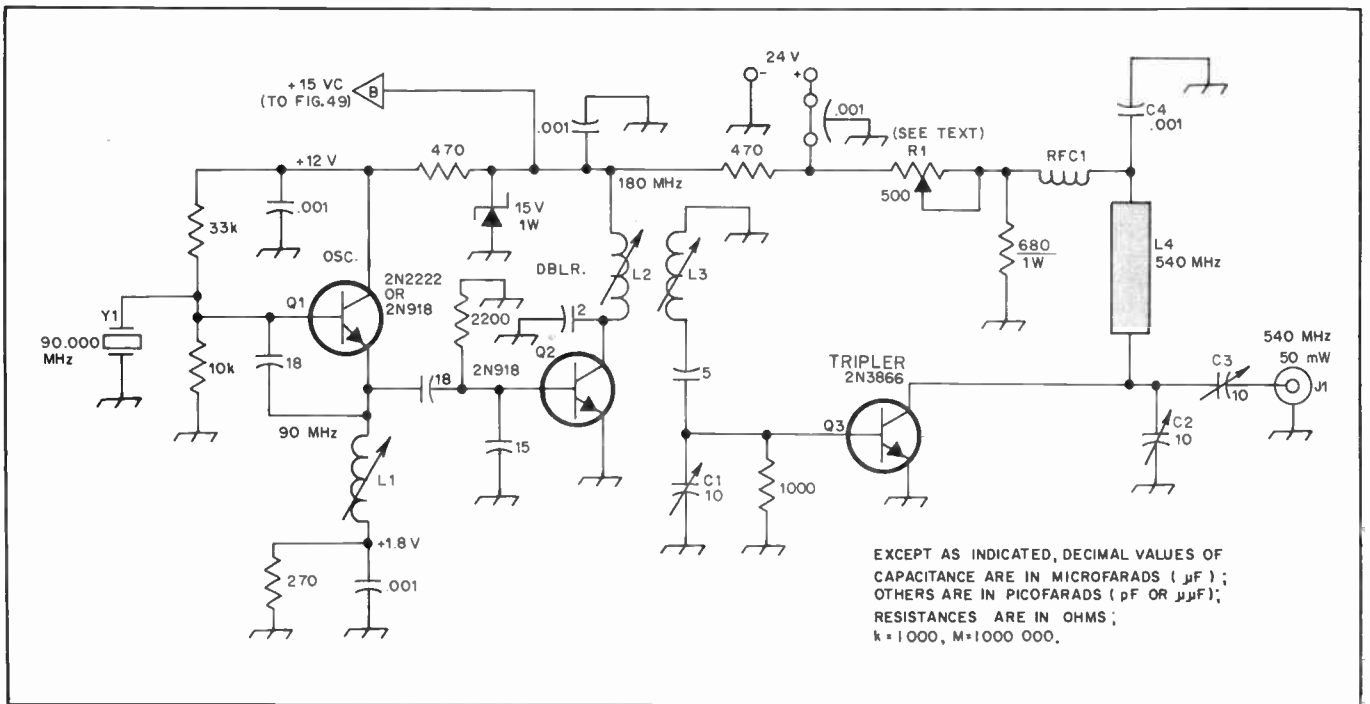


Fig. 50 — Schematic diagram of the oscillator and multiplier for the 2304 MHz converter. As explained in the text, a fixed-value resistor may be substituted for R1 after the value that provides proper performance has been found.

C1, C2, C3 — 0.8- to 10-pF glass trimmer, Johanson 2945 or equiv.  
 C4 — 0.001- $\mu\text{F}$  button mica.  
 J1 — Coaxial connector, type BNC or equiv.

L1 — 10 turns no. 24 enam. on 1/4-in. OD slug-tuned form.  
 L2, L3 — 3 turns like L1.  
 L4 — Copper strip 1/2  $\times$  1-1/2 in. (13  $\times$  38 mm).  
 Space 1/8 inch (3.2 mm) from chassis.  
 RFC1 — 10 turns no. 24 enam. 1/8-in. ID, close wound.



provides correct performance it can be measured and the nearest standard fixed-value resistor substituted. Some means of adjusting the collector voltage on the multiplier stage must be provided initially to allow for the nonuniformity of transistors.

#### A 2304-MHz Version

Fig. 49 and 50 show the schematic diagrams of the 2304-MHz converter and multiplier. The mixer and i-f preamplifier

was built on a separate chassis since, at the time of their construction, a multiplier chain from another project was available. An i-f of 144 MHz was chosen, although 50 MHz would work as well. An i-f output of 28 MHz, or lower, should not be used since this would result in undesirable interaction between the mixer and multiplier interdigital filters.

The 2304-MHz mixer and i-f amplifier section, shown in Fig. 49, is very similar to its 1296-MHz counterpart. Q1, the dual-


gate MOSFET, operates at 144 MHz and thus has a noise figure about 1-dB higher than that obtainable at 28 MHz.

The multiplier chain, Fig. 50, has a separate oscillator for improved drive to the 2N3866 output stage. Otherwise the circuitry is similar to the 1296-MHz version.

#### References

- Fisk, "Double-Balanced Mixers," *ham radio*, March, 1968.
- Ress, "Broadband Double-balanced Modulator," *ham radio*, March, 1970.
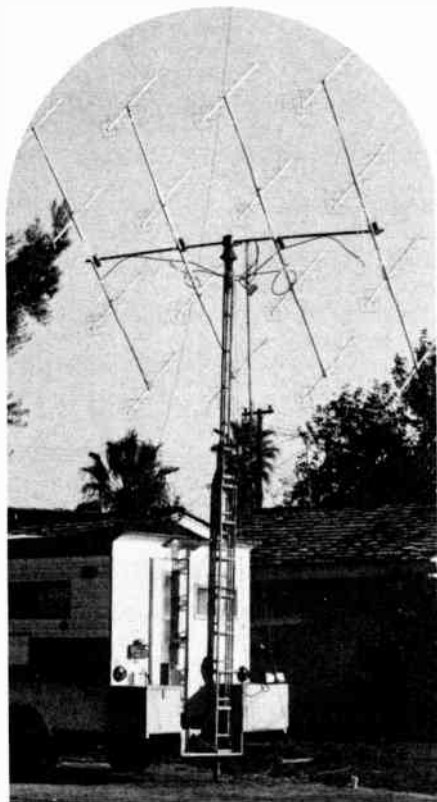
# Mobile, Portable and Emergency Equipment



A major justification for the existence of amateur radio in the USA is to provide a pool of experienced operators in time of national or community need. When the call for emergency communications is voiced by cities, towns, counties, states or the federal government, mobile and portable radio equipment is pressed into service where needed. Aside from the occasional need for disaster and emergency communications provided by amateurs, a great deal of pleasure and challenge can reward the amateur when operating portable or mobile under normal conditions. In this regard, most mobile operation is carried out today by means of narrow-band fm and repeaters. The major repeater frequencies are 146, 220 and 440 MHz. It is expected that this reliable service mode will soon include widespread occupancy of the 1215-MHz band and higher.

Mobile hf-band operation still appeals to numerous amateurs because it eliminates the constrictions imposed by vhf and uhf repeaters, their operators and their normal coverage contours. When operating mobile on ssb or cw with hf transceivers, worldwide contacts are possible for those who enjoy that style of communication.

High-power mobile operation has become entirely practical from the automotive 13.6-volt dc battery system. This results from the use of transistorized equipment. With only two transistors, a linear power amplifier can deliver 150 watts or more of rf output. For the most part, dynamotors, vibrator packs and dc-to-dc converters are things of the past, making mobile and portable operation

much less expensive and much more efficient.

## QRP Operation

Low-power operation has taken a significant jump forward in recent years and the ardent core of the movement almost qualifies as a cult. The basic concept is to do things the "hard way," proving that power levels of less than 10 watts are entirely effective when reasonably good antennas are used. A widespread and somewhat mistaken notion prevails in some areas that any power level below 100 watts is QRP. The ARRL definition is that 10 watts or less is more descriptive of true "QRP." The expression "QRP<sub>p</sub>" has been adopted by some low-power enthusiasts to define very low power. It is not a term recognized by the ARRL. Rather, it is suggested that *QRP-1* be used to signify a 1-watt output power, *QRP-5* be used for 5 watts and *QRP-10* be the identifier for a 10-watt rig (see "Operating News," July 1978 *QST*). This approach provides a clear definition of the power class and preserves the International Q Code symbol, "QRP." It should be said that QRP in its proper use means "Decrease power" or "Shall I decrease power?" Thus, going from 800 watts to 500 watts is an act of QRP. Conversely, QRO means "increase power."

Power levels as low as a few milliwatts are often suitable for emergency work when the cw mode is employed in the hf bands (Fig. 27). Similarly, ssb and fm transmissions on vhf and uhf at the mW level are effective over line-of-sight paths. The advantage of this type of QRP equipment is long-term operation from batteries. Numerous examples of equipment designed for QRP work are provided in the League's book, *Solid State Design for the Radio Amateur*.

## Electrical-Noise Elimination

One of the most significant deterrents to effective signal reception during mobile or portable operation is electrical impulse noise from the automotive ignition system. The problem also arises during the use of gasoline-powered portable ac



Fig. 1 — This may represent the ultimate in portable vhf operation. The aggregate antenna gain represented by this setup could be very effective in time of emergency. This installation was built and operated by N6NB/K6YNB, who with a similar system, set a single-operator national record during a vhf contest, earning more than 60,000 points. The antenna shown is effective also for e.m.e. work.

Fig. 2 — WB5MKX and K5GM demonstrate the practicality of portable operation from a remote site as they operate W5KA/5 during an ARRL Field Day contest.

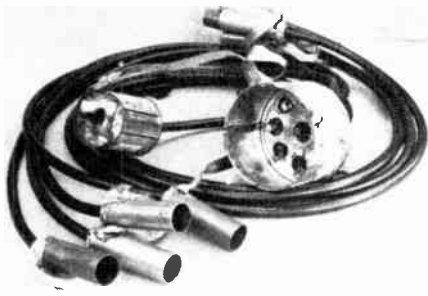


Fig. 3 — A typical homemade shielding kit for an automotive ignition system. Tin cans have been put to use as shields for the spark coil and distributor. Additional shields have been mounted on the plug ends of the wires for shielding the spark plugs. The shield braid of the cabling protrudes at each end of the wires and is grounded to the engine block.



Fig. 5 — Gasoline-driven alternators are excellent as sources for 117 or 235 volts ac during field operations. In this picture is WB5YWQ yanking the starter rope of the WA5CXG power plant.



Fig. 4 — A close-up view of the distributor shield can. The shield braid over each spark-plug wire is soldered to the top of the can, and the can is grounded to the engine block.

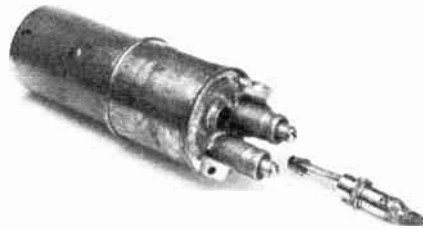


Fig. 6 — The automobile ignition coil should be shielded as shown here. A small tin can has been soldered to the metal coil case, and coaxial feed through capacitors have been soldered to the top of the can. The "hot" lead of the coil enters the shield can through a modified audio connector.

generators. This form of interference can completely mask a weak signal, thus rendering the station ineffective. Most electrical noise can be eliminated by taking logical steps toward suppressing it. The first step is to clean up the *noise source* itself, then utilize the receiver's built-in noise-reducing circuit as a last measure to knock down any noise pulses from passing cars, or from other man-made sources (Fig. 3).

### Spark-Plug Noise

Spark-plug noise is perhaps the worst offender when it comes to ignition noise. There are three methods of eliminating this type of interference — resistive spark-plug suppressors, resistor spark plugs, or resistance-wire cabling. By installing resistor plugs a great deal of the noise can be stopped. Tests have proved, however, that suppressor cable between the plugs and the distributor, and between the distributor and ignition coil, is the

most effective means of curing the problem. Distributed-resistance cable has an approximate resistance of 5000 ohms per foot, and consists of a carbon-impregnated sheath followed by a layer of insulation, then an outer covering of protective plastic sheathing. Some cars come equipped with suppressor cable. Those which do not can be so equipped in just a matter of minutes. Automotive supply stores sell the cable, and it is not expensive. It is recommended that this wiring be used on all mobile units. The same type of cable can be installed on gasoline-powered generators for field use. A further step in eliminating plug noise is the addition of shielding over each spark-plug wire, and over the coil lead. It should be remembered that each ignition cable is an antenna by itself, thus radiating those impulses passing through it. By fitting each spark-plug and coil lead with the shield braid from a piece of RG-59/U coax line, grounding the braid

at each end to the engine block, the noise reduction will be even greater. An additional step is to encase the distributor in flashing copper, grounding the copper to the engine block (Fig. 4). This copper is quite soft and can be form-fit to the contour of the distributor. (Commercially manufactured shielded ignition cable kits are also available.) The shield braid of the spark-plug wires should be soldered to the distributor shield if one is used. Also, the ignition coil should be enclosed in a metal shield since the top end of many of these coils is made of plastic. A small tin can can often be used as a top cover for the coil or distributor. It should be soldered to the existing metal housing of the coil. Additional reduction in spark-plug noise can be effected by making certain that the engine hood makes positive contact with the frame of the car when it is closed, thus offering an additional shield over the ignition system. The engine block should also be bonded to the frame at several points. This can be done with the shield braid from coax cable. Feedthrough (hi-pass) capacitors should be mounted on the coil shield as shown in Fig. 6 to filter the two small leads leaving the assembly.

### Other Electrical Noise

The automotive generator system can create an annoying type of interference which manifests itself as a "whine" when heard in the receiver. This noise results from the brushes sparking as the commutator passes over them. A dirty commutator is frequently the cause of excessive sparking, and can be cleaned up by polishing its surface with a fine grade of emery cloth. The commutator grooves should be cleaned out with a small, pointed instrument. A coaxial feedthrough capacitor of 0.1- to 0.5- $\mu$ F capacitance, should be mounted on the generator frame and used to filter the generator *armature* lead. In stubborn cases of generator noise a parallel L/C tuned trap can be used in place of the capacitor, or in addition to it, tuned to the receiver's operating frequency. This is probably the most effective measure used for curing generator noise.

Voltage regulators are another cause of mobile interference. They contain relay contacts that jitter open and closed when the battery is fully charged. The noise shows up in the receiver as a ragged, "hashy" sound. Coaxial feedthrough capacitors can be mounted at the *battery* and *armature* terminals of the regulator box to filter those leads. The *field* terminal should have a small capacitor and resistor, series-connected, from it to chassis ground. The resistor prevents the regulator from commanding the generator to charge constantly in the event the bypass capacitor short-circuits. Such a condition would destroy the generator by causing overheating.

Alternators should be suppressed in a



similar manner as dc generators. Their slip rings should be kept clean to minimize noise. Make sure the brushes are making good contact inside the unit. A coaxial feedthrough capacitor and/or tuned trap should be connected to the output terminal of the alternator. Make certain that the capacitor is rated to handle the output current in the line. The same rule applies to dc generators. *Do not connect a capacitor to the alternator or generator field terminals.* Capacitor values as high as 0.5- $\mu$ F are suitable for alternator filtering.

Some alternator regulator boxes contain solid-state circuits, while others use single or double contact relays. The single-contact units require a coaxial capacitor at the *ignition* terminal. The double-contact variety should have a second such capacitor at the *battery* terminal. If noise still persists, try shielding the field wire between the regulator and the generator or alternator. Ground the shield at both ends.

#### Instrument Noise

Some automotive instruments are capable of creating noise. Among these gauges and senders are the heat- and fuel-level indicators. Ordinarily, the addition of a 0.5- $\mu$ F coaxial capacitor at the sender element will cure the problem.

Other noise-gathering accessories are turn signals, window-opener motors, heating-fan motors and electric windshield-wiper motors. The installation of a 0.25- $\mu$ F capacitor will usually eliminate their interference noise.

#### Frame and Body Bonding

Sections of the automobile frame and body that come in contact with one another can create additional noise. Suspected areas should be bonded together with flexible leads such as those made from the shield braid of RG-8/U coaxial cable. Trouble areas to be bonded are

- 1) Engine to frame.
- 2) Air cleaner to engine block.
- 3) Exhaust lines to car frame and engine block.
- 4) Battery ground terminal to frame.
- 5) Steering column to frame.
- 6) Hood to car body.
- 7) Front and rear bumpers to frame.
- 8) Tail pipe to frame.
- 9) Trunk lid to frame.

#### Wheel and Tire Static

Wheel noise produces a ragged-sounding pulse in the mobile receiver. This condition can be cured by installing static-collector springs between the spindle bolt of the wheel and the grease-retainer cap. Insert springs of this kind are available at automotive supply stores.

Tire static has a ragged sound, too, and can be detected when driving on hard-surface highways. If the noise does not appear when driving on dirt roads it will

be a sure indication that tire static exists. This problem can be resolved by putting antistatic powder inside each tire. This substance is available at auto stores, and comes supplied with an injector tool and instructions.

#### Corona-Discharge Noise

Some mobile antennas are prone to corona build-up and discharge. Whip antennas which come to a sharp point will sometimes create this kind of noise. This is why most mobile whips have steel or plastic balls at their tips. But, regardless of the structure of the mobile antenna, corona buildup will frequently occur during or just before a severe electrical storm. The symptoms are a high-pitched "screaming" noise in the mobile receiver, which comes in cycles of one or two minutes duration, then changes pitch and dies down as it discharges through the front end of the receiver. The condition will repeat itself as soon as the antenna system charges up again. There is no cure for this condition, but it is described here to show that it is not of origin within the electrical system of the automobile.

#### Electronic Noise Limiters

Many commercially built mobile transceivers have some type of built-in noise clipping or cancelling circuit. Those which do not can be modified to include such a circuit. The operator has a choice of using af or rf limiting. Circuits of this type are described in the theory section of the hf receiving chapter.

Simple superregenerative receivers, by nature of their operation, provide noise-limiting features, and no additional circuit is needed. Fm receivers, if operating properly, do not respond to noise pulses of normal amplitude; hence no additional circuitry is required.

#### Mobile and Portable Power Supplies

Most present-day mobile equipment is powered by solid-state dc-to-dc converters. They use power transistors to switch the primary voltage of the transformer. This technique eliminates sparking in the switching circuit, as would be the situation if a mechanical switch (vibrator) was used, and offers greater reliability and efficiency. The switching transistors can be made to oscillate by means of a feedback winding on the transformer, and by application of forward bias on the bases of the switching transistors. The switching rate can be set for any frequency between 50 Hz and several thousand Hz. The choice depends upon the inductance of the transformer windings. The switching waveform is a square wave. Therefore, the supply is capable of causing a buzzing sound in transmitter or receiver output in much the same fashion as with the old-style vibrator supply. Rf filtering should be employed as a corrective measure. At higher switching rates the buzz becomes a whine. High-frequency switching rates are preferred for dc-to-dc converters because smaller transformer cores can be used and because less output filtering is required. The efficiency

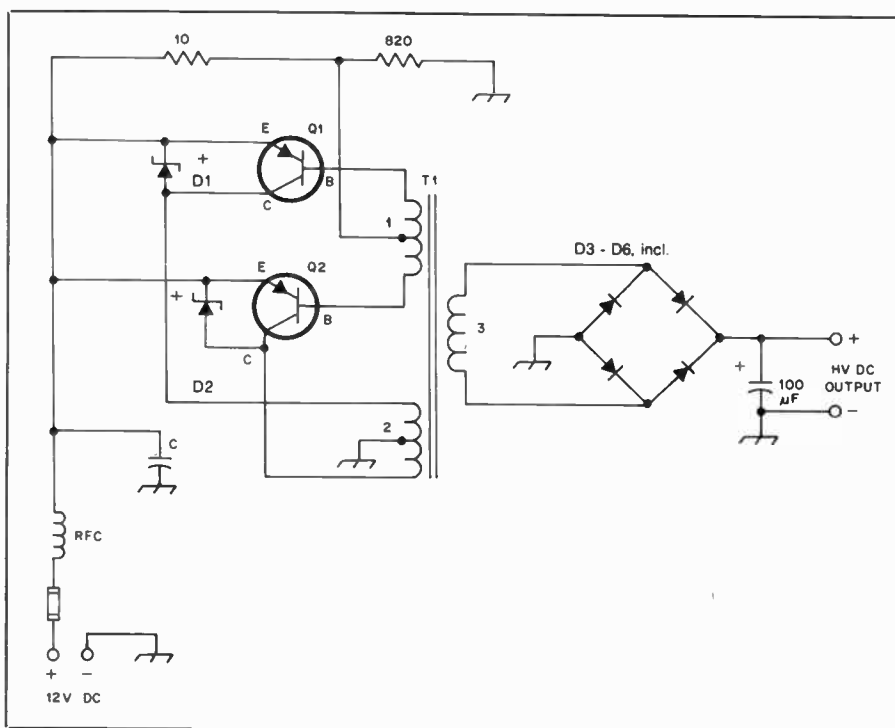


Fig. 7 — Representative circuit of a dc-to-dc converter which uses power transistors (Q1 and Q2) as electronic switches in the primary of T1. D3-D6, inclusive, rectify the ac voltage from the transformer secondary.



of a well-designed solid-state power supply is on the order of 80 percent, an improvement over the usual 60 to 70 percent of vibrator supplies, or the miserable 30 to 40 percent of dynamotors.

A typical transistorized supply is shown in Fig. 7. The supply voltage is fed into the emitter circuit of Q1-Q2. A resistive divider is used to obtain forward bias for the transistors through base-feedback winding 1. The primary switching takes place between the emitter and collector of each transistor. Q1 and Q2 are connected in push-pull and conduct on alternate half cycles. As each transistor is driven into conduction it saturates, thus forming a closed contact in that leg of the circuit. The induced voltage is stepped up by means of T1, and high-voltage appears across winding 3. Zener diodes D1 and D2 protect Q1 and Q2 from voltage spikes. They should be rated at a voltage slightly lower than the  $V_{CE}$  of the transistors. Diodes D3 through D6 form a bridge rectifier to provide dc output from winding 3. Some supplies operate at a switching rate of 2000 to 3000 Hz. It is possible to operate such units without using output rectifiers, but good filtering

is needed to remove the ripple from the dc output.

### Transistor Selection

The switching transistors should be able to handle the primary current of the transformer. Since the feedback will diminish as the secondary load is increased, the beta of the transistors, plus the design of the feedback circuit, must be sufficient to sustain oscillation under full-load conditions. During no-load conditions, the feedback voltage will reach its highest peak at the bases of Q1 and Q2. Therefore, the transistors must be rated for whatever base-emitter reverse voltage that occurs during the cutoff period. Since the transistors must be able to handle whatever peak voltage occurs during the switching process, it is wise to stay on the safe side. Choose transistors that have a  $V_{CEO}$  rating of three or four times the supply voltage, keeping in mind that fully charged automobile batteries can deliver as much as 14 volts. Heat sinks should be used on Q1 and Q2 to prevent damage from excessive heating. The larger the heat sink, the better. Under full-load conditions the transistors should only be

slightly warm to the touch. If they are running hot, this will indicate inadequate heat sinking, too great a secondary load, or too much feedback. *Use only enough feedback to sustain oscillation under full loading, and to assure rapid starting under the same conditions.*

### Mobile Power Supply for Transceivers

Transceivers such as the Heath SB-102 and the Drake TR-4 require a separate power supply when operated from 12 volts dc. Additionally, linear amplifiers can be run from a separate dc supply to allow increased power operation from relatively low-power transceivers. The unit described here, when operated from 12 volts dc, will deliver approximately 900 volts dc at 300 mA, 250 volts dc at 200 mA, -150 volts dc at 40 mA, and an adjustable bias voltage from 10 to 150 volts of dc.

### The Circuit

A common-emitter configuration is used with diodes to provide a return path for the feedback winding, as shown in Fig. 8. Assuming that Q2 conducts first, the base is driven negative by the feedback

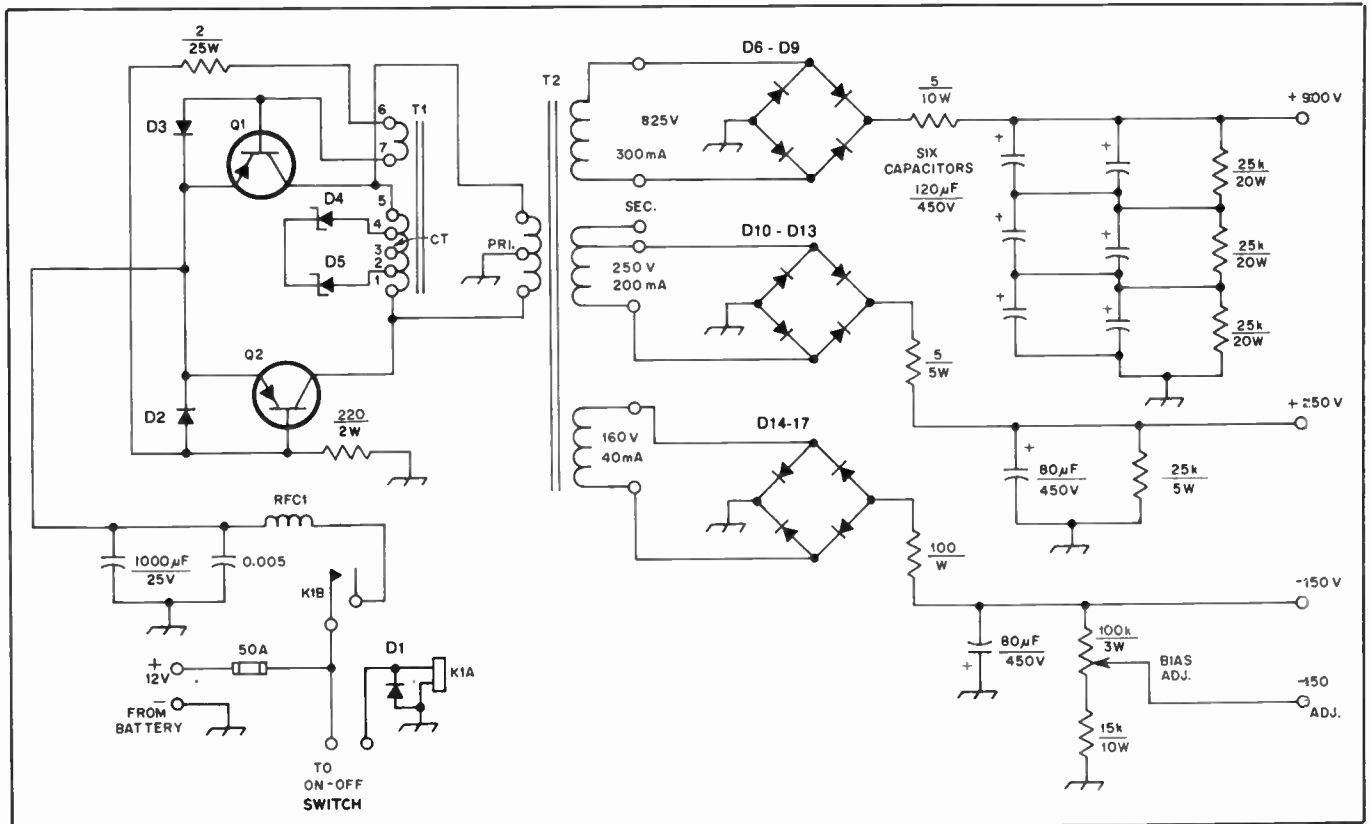


Fig. 8 — Circuit diagram of the mobile power supply. Polarized capacitors are electrolytic, others are paper or mica. Resistances are in ohms. Component designations not listed below are for text reference.

D1, D6-17 — 1000-PRV, 1.5-A silicon diode.  
 D2, D3 — 50-PRV, 3-A silicon diode.  
 D4, D5 — 18-V, 1-W Zener diode.  
 K1 — Spst contactor relay, 60-A, 12-volt dc coil (Potter and Brumfield MB3D).  
 Q1, Q2 — Delco 2N1523 transistor (substitutions not

recommended). Delco insulator kits (no. 7274633) are required. The heat sinks are Delco part no. 7281366.  
 R3 — 100 k $\Omega$ , 3W, linear-taper control.  
 RFC1 — 20 turns, no. 10 enam. wire on a 1/4-

inch dowel.  
 T1 — Feedback transformer, 1000-Hz Osborne 6784.  
 T2 — Hipersil transformer, 1000-Hz, Osborne 21555.

winding (connections 6 and 7 on T1). D3 then conducts, thereby protecting the base of Q1. D2 is back-biased to an open circuit when Q2 is conducting. When T1 saturates producing a square wave, the voltage at pins 6 and 7 of T1 reverses turning on Q1. When Q2 conducts, current flows through the primary of T2 in one direction and as Q1 conducts, current flows through the primary of T2 in the other direction. This reversal of current in the primary of T2 provides an alternating square-wave voltage which is stepped up by the secondary winding. Full-wave rectification with current limiting is used with each secondary winding.

The supply oscillates at about 1000 Hz and audible noise is low. The main power to the supply is applied through K1B. K1A can be connected in parallel with the filament supply in the transceiver.

Hash filtering is provided by RFC1 and its associated bypass capacitors in the primary lead. Transient suppression is assured by D1, D4 and D5. Bleeder resistors are used on each supply leg to provide a constant minimum load for the circuit. The supply can be operated without fear of damaging the diodes or transistors should no load be connected, although this is not considered good practice. Input and output connectors for interconnection to the battery and the transceiver can be selected to meet the needs of the particular installation.

### Construction

This circuit requires that the transistors be insulated from the heat sink. Suitable insulators are included with the devices. Silicone grease should be used to help conduct the heat away from the transistors.

No attempt has been made to make the

supply small. It is built on a 12 × 6 × 3-inch (305 × 152 × 76-mm) chassis, which allows plenty of room for the heavy conductors. The capacitors are mounted in a row along one side of the chassis. The heat sinks, shown in the photograph, are mounted on a 1/8-inch (3-mm) thick aluminum back plate.

The leads from the battery to the relay, and from the relay to the transistors and T1, should be no. 6 or no. 8 conductors. All ground leads should be connected to one point on the chassis. The wiring layout is uncritical and no other special precautions are necessary.

### Operation

The power supply should be mounted as close to the battery terminals as possible to minimize voltage drop. If the supply is trunk mounted, 1/4-inch (6-mm) conductors should be used to connect it to the battery. A 300-volt tap is available on the secondary of T2. If the transceiver requires more than 250 volts for proper operation, this tap can be used.

### Solar-Electric Power

Although solar-electric arrays are quite expensive when purchased new, surplus individual cells and groups of cells (arrays) can be bought inexpensively on occasion. Photons from the sun strike the p-n junctions of the cells to generate 0.5

volt per cell (see chapter 4). The current rating of an individual cell is dependent upon the diameter of the cell. Typical production units deliver 100 mA, 600 mA, 1 A or 1.5 A. Cells with higher current ratings are manufactured, but are quite costly.

A solar-electric panel generally contains 36 cells wired in series. This provides approximately 18 volts dc (no-load conditions) at peak sunlight. The current capability of the panel is determined by the diameter of the cells. Greater amounts of current output can be had by paralleling like panels. That is, two 1.5-A panels can be operated in parallel to deliver 3 amperes of current, and so on.

The usual operating system has the array output routed through a regulator to a storage battery. The regulator prevents overcharging of the battery. The station equipment takes its power from the battery. Most automotive 12-volt batteries are suitable for use with solar-electric panels. NiCad batteries are satisfactory also. Fig. 9 shows two solar arrays in a frame. The cells are wired in series. Semicircular cells are seen at the right. They deliver approximately half the dc current available from the circular cells at the left in the picture. A Ten-Tec Argonaut transceiver is at the lower right in Fig. 9. It is a good example of the type of amateur equipment which can be operated by

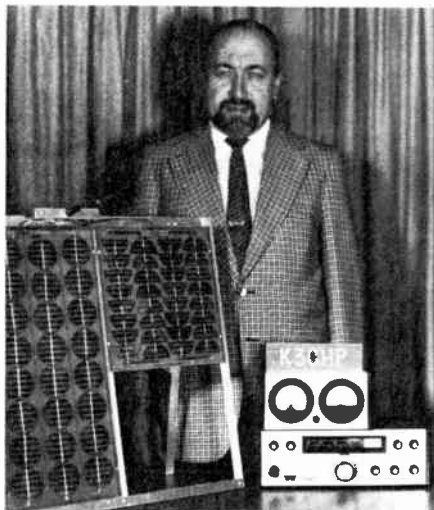


Fig. 9 — Solar-electric arrays are excellent for short- or long-term field and emergency use to power amateur stations. A 14-volt, 1.5-A solar panel and two automobile batteries in parallel can provide many after-dark hours of operation with typical 100-watt hf-band transceivers of the solid-state variety.

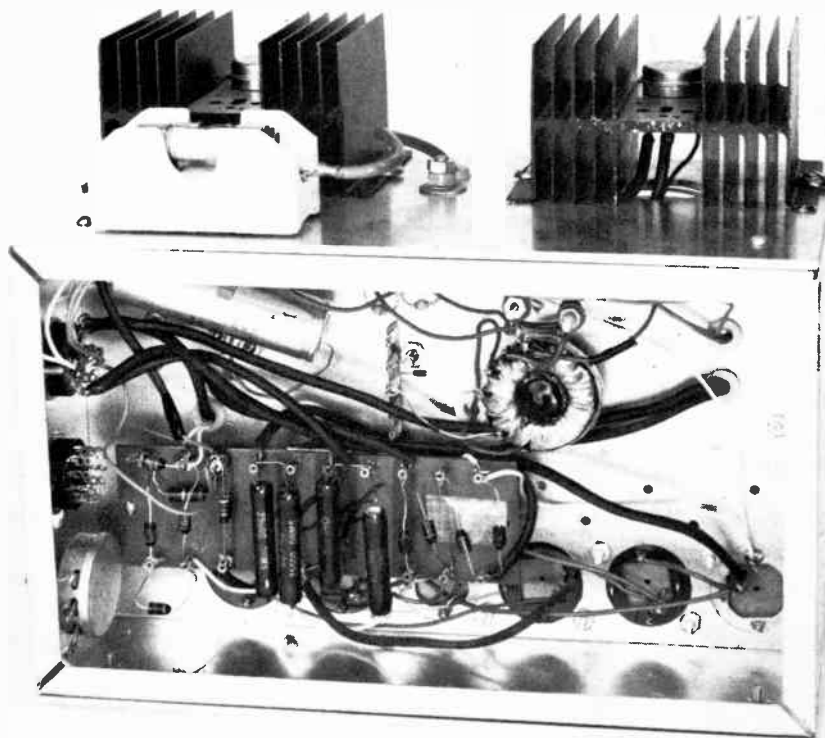


Fig. 10 — The heat sinks are mounted on an aluminum panel. When installing a power supply of this type, be sure to keep the heat sink fins in a vertical position to provide best air circulation. All of the filter capacitors are mounted in a row across the front of the chassis. RFC1 is located next to the transformer. Two sockets are mounted on the chassis side wall to accept an interconnecting cable from the transceiver. To the left of these sockets is the bias voltage adjustment control, R3. This model of the power supply was built by W8HS.



means of solar power. A feature article on solar-electric power appeared in August 1977 *QST*.

### Portable AC Power Sources

There are two popular sources of ac power for use afield. The first is what is referred to as a dc-to-ac converter, or more commonly, an *inverter*. For the most part it is a unit not significantly unlike the mobile power supply of Fig. 8. The essential difference is that the inverter delivers 117 volts ac, rather than dc voltages (Fig. 11).

The ac output voltage is a square wave. Therefore, some types of equipment can not be operated satisfactorily from the inverter. Certain types of motors are among those items which require a sine-wave output. Fig. 11 shows a picture of one style of commercial inverter. Heat sinks are used to cool the switching transistors. The unit shown is available from Heath Company in kit form. It delivers 117 volts of ac at 175 watts continuous power rating. The primary voltage is 6 or 12 dc.

When sine-wave output is required from a portable ac power supply, gasoline-engine alternators are used. They are available with ratings of several kilowatts, or as little as 500 watts. One of the larger units is seen in Fig. 12 where WB9QPI has just completed a maintenance run for the W0OHU/0 Field Day group.

Alternators powered by internal-combustion engines have been used for years to supply 117/235 ac independently of the commercial mains. Such combinations range from tiny units powered by two-cycle or four-cycle gasoline engines in the low-wattage class to giant multicylinder diesels capable of supplying megawatts of power. Perhaps the most practical power range for most purposes would be in the neighborhood of 2 kW. Larger units tend to become too heavy for one person to lift and handle easily while smaller generators lack sufficient power output for many applications. A 2-kW alternator is quite heavy but it is capable of supplying power for just about any large power tool. It is roughly the equivalent of having a single 15-A outlet in an ordinary electric service. Of course, it will handle moderate-power amateur equipment with ease.

### Maintenance Checklist

Although more complicated maintenance chores should be performed by qualified service personnel, many simple measures which will prolong the life of the alternator can be done at home or afield. Perhaps the best plan is to log the dates of when the unit was used and the operating time in hours. Also included in the log would be dates of maintenance and type of service performed. Oil changes, when gasoline was purchased for emergency purposes, and similar data would fall under this category.

Important points that are common to all types of generators are indicated for a typical one in Fig. 13. (Consult the manufacturer's manual for additional instructions that might apply to a particular model.) The following checklist relates to the numbers on the drawing.

1) Use the proper grade of fuel. Newer models will burn either "no-lead" or regular leaded gasoline. Do not use premium or so-called "hi-test" grades unless the owner's manual recommends it. Such fuels have a high lead content for proper burning in high-compression automobile engines and are generally unsuitable for small, low-compression engines found in most alternator combinations. Check the owner's manual to determine whether oil must be mixed with the gasoline. While *two-cycle* models require an oil-gas mixture, most generators have a *four-cycle* engine that burns ordinary gasoline with no extra additives. Gasoline for emergency purposes should only be stored in small amounts and rotated on a regular basis. Older stock can be burned in a car (that uses the same grade of gas as the generator) since storing gasoline for any length of time is inadvisable. The more volatile components evaporate, leaving excess amounts of a varnish-like substance that will clog carburetor passages. Also, be sure gasoline containers are of an approved type with a clean interior, free of rust or other foreign matter. Similar considerations apply to the gas tank on the engine itself.

The majority of difficulties with small engines are related to fuel problems in some way. Dirty fuel or water in the gasoline is one source, with carburetor trouble because of the use of old gas being another common cause. Except for minor adjustments recommended in the instruction manual, it is seldom necessary to touch the carburetor controls. Avoid the temptation to make such adjustments in the case of faulty operation. *Follow the recommendations* in this guide so that more complicated maintenance procedures (such as carburetor overhaul) are not required.

2) Another important factor often neglected in maintenance of alternator engines is oil. While lubrication is one job oil has to perform, there are other considerations as well. The engine oil in the crankcase also collects a large amount of solid combustion products, bits of metal worn away by the moving parts, and any dust or other foreign matter that enters the carburetor intake. For instance, it is especially important to observe the manufacturer's recommendations concerning the length of time the engine may be operated before an oil change is required during the break-in period. If you ever have the opportunity to examine the oil from a new engine, you will note a metallic sheen to it. This is from the excessive amount of metal that is worn

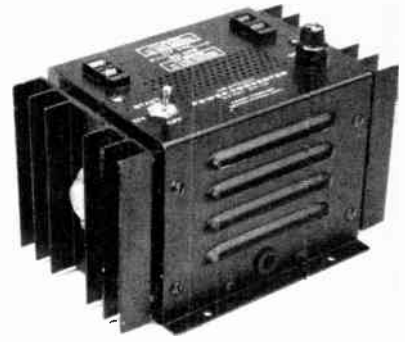


Fig. 11 — Photograph of a commercial dc-to-ac inverter that operates from 6 or 12 volts dc and delivers 117 volts ac (square wave) at 175 watts.



Fig. 12 — Large gasoline generators of the kW and higher class are excellent for powering several amateur stations from a complex field site. Maintenance, as discussed in the text, is a vital matter to ensure reliable operation. Here, WB9QPI has just finished a maintenance check of the group's Field Day power plant.

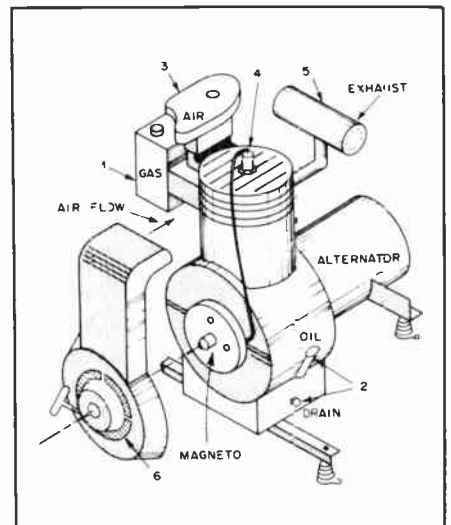


Fig. 13 — The numbers indicate the primary maintenance points of a large power generator (see text for details).

away. After the break-in period, much less metal is abraded and the oil doesn't have to be replaced as often.

The oil level should be checked frequently during engine operation. Each time fuel has to be added the oil should be checked also. When storing an alternator, it is also wise to drain the oil and replace it with fresh stock. This is because one of the combustion products is sulfur which forms sulfuric acid with water dispersed in the oil. The acid then attacks the special metal in the bearing surfaces causing pitting and premature replacement.

Also note the grade and weight of oil recommended by the manufacturer. Unlike their larger counterparts in the automobile, most small engines do not have oil filters, which is another reason why required changes are more frequent. Some manufacturers recommend a high-detergent oil that comes in various service grades such as MS, SD, and similar types. Examine the top or side of the cans in which the oil is sold and see if the letters correspond to those recommended by the engine manufacturer.

3) The carburetor mixes gasoline with air, which is then burned in the engine. Before entering the carburetor, the air must be filtered so that it is free of dust and other foreign matter that might otherwise be drawn into cylinder(s). Particles that do get by the air filter are picked up by the oil. That should be changed more often if the alternator is operated in a dusty location. Also, it is important to clean the air filter frequently. It contains a foam-like substance which can be cleaned in kerosene and then soaked in fresh motor oil. Squeeze excess oil from the filter before replacing. Also, consult the instruction manual for further recommendations.

4) Once the gas/air mixture enters the cylinder, it is compressed by the piston into a very small volume and ignited by the spark plug. During the rapid burning that then occurs, the expansion caused by the resulting heat forces the piston down and delivers the mechanical power to the alternator.

As might be expected, proper operation of the ignition system is an important factor in engine performance. Power for the spark is supplied by a device called a magneto that is normally installed on the front of the engine. The magneto seldom requires servicing and such work should only be done by those qualified to do so. (This is one reason why the magneto is often located under a flywheel that is difficult to remove by the inexperienced.)

On the other hand, faulty spark plugs are the usual cause of ignition problems. Special equipment is required to test a spark plug properly, but an easier solution is to have a new one handy. In fact, keep two spare plugs on hand. Spark plug life can be notoriously short on occasion. However, repeated plug failure is also

abnormal and other causes such as a poor gas/air mixture might be the culprit.

Replace the spark plug with a type similar to the one that came with the alternator or a substitute recommended by the manufacturer. Some models have resistor-type plugs which are desirable for ignition-noise suppression. Resistor plugs are usually indicated by an R prefix. For instance the resistor version of a Champion CJ-8 would be an RC-J8.

5) Little maintenance is required in regard to the exhaust system. In some forested areas, a spark-arrester type of muffler is required, so be sure that your unit is so equipped *before* contemplating operation in such a location. "Quiet hours" may also be imposed in some places during the nighttime hours if generator exhaust noise is too loud.

Two very important safety precautions should be observed with regard to the exhaust system. *Never* operate an alternator in closed surroundings such as a building. Dangerous gases are emitted from the exhaust which are highly toxic. Secondly, *never* refuel an engine while it is running or if the exhaust system is still very hot. Unfortunately, this last precaution is disregarded by many, which is extremely foolish. (Experienced service-station operators will refuse to refuel an automobile with the motor running, which is often prohibited by law.) Don't become an unnecessary statistic.

6) Most alternators are air-cooled as opposed to the water-cooled radiator system of the automobile. A fan on the front of the engine forces air over the cylinder and an unobstructed entrance for this air flow is necessary. Avoid operating the alternator in areas where obstruction to this flow might result (such as in tall grass). Alternators should be operated such that a sufficient amount of air circulation is present for cooling, carburetion and exhaust.

### Storage

Proper maintenance of an alternator when it is not being used is just as important as during the time it is in operation. The usual procedure is to run the engine dry of gasoline, drain the crankcase and fill it with fresh oil, and remove the spark plug. Then pour a few tablespoons of oil into the cylinder and turn the engine over a few times with the starter and replace the plug. But *never* crank the engine with the plug removed and the *ignition* or *start* switch in the *on* or *run* position. The resulting no-load high voltage might cause damage to the magneto. It is also a good idea to ground the spark-plug wire to the engine frame with a clip lead in case the switch is accidentally activated.

Moisture is the greatest enemy of an iron product — such as a generator, in storage. The coating of oil helps retard rust formation here which might actually

weld the two surfaces together or cause pitting. Also, rust particles abrade the surfaces when the engine is restarted, resulting in premature wear. Consequently, it is important to store the alternator in an area of low humidity.

Although the maintenance procedures outlined may seem like a chore, the long-term benefits include low repair costs and like-new performance. Engines for alternator combinations must be able to handle a variety of loads while maintaining a constant speed in order to keep the output frequency constant. A mechanical governor performs this latter function by metering the fuel supplied to the engine under different load conditions. However, the system cannot function properly with an engine in poor mechanical condition because of lack of proper maintenance.

### Grounds

Newer generators are supplied with a three-wire outlet and the ground connection should go to the plug as shown in Fig. 14. On older types, the ground would have to be connected separately to the generator frame and then to the common terminal in the junction box. A pipe or rod can then be driven into the ground and a wire connection made to either a clamp supplied with the rod or by means of a C-clamp for larger sizes of pipe. From an ignition-noise-suppression standpoint, the ground is desirable along with safety considerations when power tools are being used.

The ground connection goes to the green wire in commercially made three-wire conduit. Conduit purchased from an electrical store comes with a color-coded insulation and the colored wires should be connected as shown in Fig. 14. Consult

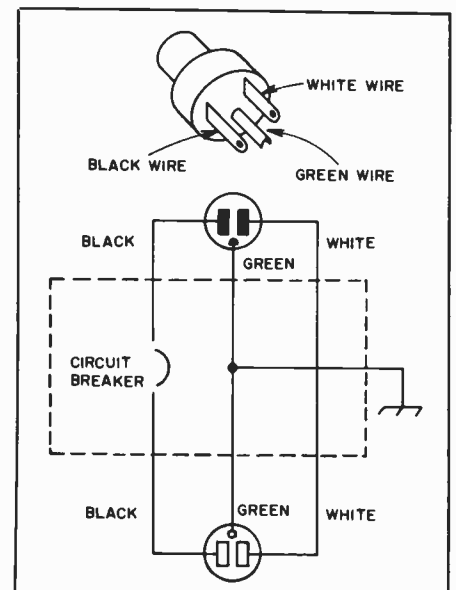


Fig. 14 — A simple accessory that provides overload protection for generators that do not have such provisions built in.



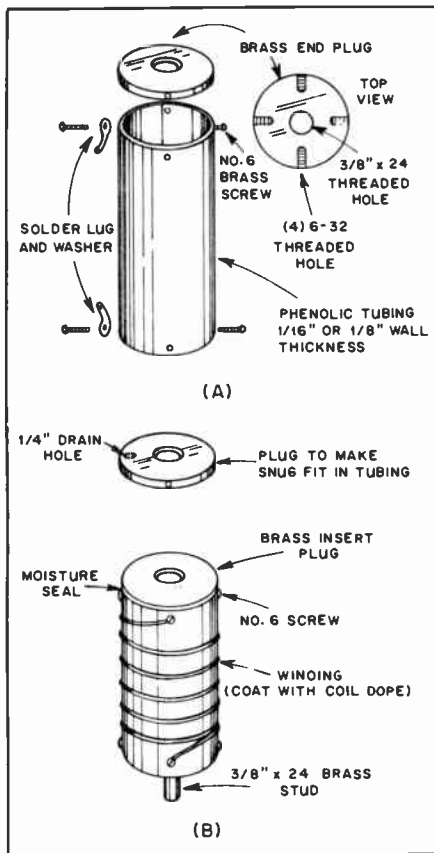


Fig. 15 — Details for making a home-built mobile loading coil. A breakdown view of the assembly is given at A. Brass end plugs are snug-fit into the ends of the phenolic tubing, and each is held in place by four 6-32 brass screws. Center holes in the plugs are drilled and tapped for 3/8-24 thread. The tubing can be any diameter from one to four inches (25 to 100-mm). The larger diameters are recommended. Illustration B shows the completed coil. Resonance can be obtained by installing the coil, applying transmitter power, then pruning the turns until the lowest SWR is obtained. Pruning the coil for maximum field-strength-meter indication will also serve as a resonance indication.

the owner's manual for the generator for further details on power hookup that might apply to your particular model.

### HF Mobile Antennas

The antenna is perhaps the most important item in the successful operation of a mobile installation. Mobile antennas, whether designed for single or multiband use, should be securely mounted to the automobile, as far from the engine compartment as possible (for reducing noise pickup), and should be carefully matched to the coaxial feed line connecting them to the transmitter and receiver. All antenna connections should be tight and weatherproof. Mobile loading coils should be protected from dirt, rain and snow if they are to maintain their Q and resonant frequency. The greater the Q of the loading coil, the better the efficiency, but the narrower will be the bandwidth of the antenna system.

Though bumper-mounted mobile antennas are favored by some, it is better to place the antenna mount on the rear deck of the vehicle, near the rear window. This locates the antenna high and in the clear, assuring less detuning of the system when the antenna moves to and from the car body. *Never use a base-loaded antenna on a bumper mount.* Many operators avoid cutting holes in the car body for fear of devaluation when selling the automobile. Such holes are easily filled, and few car dealers lower the trade-in price because of the holes.

The choice of base or center loading a mobile antenna has been a matter of controversy for many years. In theory, the center-loaded whip presents a slightly higher base impedance than does the base-loaded antenna. However, with proper impedance-matching techniques employed there is no discernible difference in

Table 2

### Suggested Loading-Coil Dimensions

Req'd L(μH)	No. Turns	Wire Size	Dia In.	Length In.
700	190	22	3	10
345	135	18	3	10
150	100	16	2-1/2	10
77	75	14	2-1/2	10
77	29	12	5	4-1/4
40	28	16	2-1/2	2
40	34	12	2-1/2	4-1/4
20	17	16	2-1/2	1-1/4
20	22	12	2-1/2	2-3/4
8.6	16	14	2	2
8.6	15	12	2-1/2	3
4.5	10	14	2	1-1/4
4.5	12	12	2-1/2	4
2.5	8	12	2	2
2.5	8	6	2-3/8	4-1/2
1.25	6	12	1-3/4	2
1.25	6	6	2-3/8	4-1/2

To obtain dimensions in millimeters, multiply inches by 25.4.

performance between the two methods. A base-loading coil requires fewer turns of wire than one for center loading, and this is an electrical advantage because of reduced coil losses. A base-loaded antenna is more stable during wind loading and sway. If a homemade antenna system is contemplated, either system will provide good results, but the base-loaded antenna may be preferred for its mechanical advantages.

### Loading Coils

There are many commercially built antenna systems available for mobile operation, and some manufacturers sell the coils as separate units. Air-wound coils of large wire diameter are excellent for use as loading inductors. Large Miniductor coils can be installed on a solid phenolic rod and used as loading coils. Miniductors, because of their turns spacing, are easy to adjust when resonating the mobile antenna, and provide excellent Q. Phenolic-impregnated paper or fabric tubing of large diameter is suitable for making homemade loading coils. It should be coated with liquid fiber glass, inside and out, to make it weatherproof. Brass insert plugs can be installed in each end, their centers drilled and tapped for a standard 3/8 x 24 (9.5 mm x 24) thread to accommodate the mobile antenna sections. After the coil winding is pruned to resonance it should be coated with a high-quality, low-loss compound to hold the turns securely in place, and to protect the coil from the weather. Liquid polystyrene is excellent for this. Hobby stores commonly stock this material for use as a protective film for wall plaques and other

Table 1

### Approximate Values for 8-foot Mobile Whip

#### Base Loading

f(kHz)	Loading L(μH)	RC(Q50) Ohms	RC(Q300) Ohms	RR Ohms	Feed R* Ohms	Matching L(μH)
1800	345	77	13	0.1	23	3
3800	77	37	6.1	0.35	16	1.2
7200	20	18	3	1.35	15	0.6
14,200	4.5	7.7	1.3	5.7	12	0.28
21,250	1.25	3.4	0.5	14.8	16	0.28
29,000	—	—	—	—	36	0.23

#### Center Loading

1800	700	158	23	0.2	34	3.7
3800	150	72	12	0.8	22	1.4
7200	40	36	6	3	19	0.7
14,200	8.6	15	2.5	11	19	0.35
21,250	2.5	6.6	1.1	27	29	0.29

RC = Loading-coil resistance; RR = Radiation resistance.

\* Assuming loading coil Q = 300, and including estimated ground-loss resistance.

Suggested coil dimensions for the required loading inductance are shown in a following table.

artwork. Details for making a home-built loading coil are given in Fig. 15.

### Impedance Matching

Fig. 16 illustrates the shunt-feed method of obtaining a match between the antenna and the coaxial feed line. For operation on 75 meters with a center-loaded whip, L2 will have approximately 18 turns of no. 14 wire, spaced one wire thickness between turns, and wound on a 1-inch (25-mm) diameter form. Initially, the tap will be approximately 5 turns above the ground end of L2. Coil L2 can be inside the car body, at the base of the antenna, or it can be located at the base of the whip, outside the car body. The latter method is preferred. Since L2 helps determine the resonance of the overall antenna, L1 should be tuned to resonance in the desired part of the band with L2 in the circuit. The adjustable top section of the whip can be telescoped until a maximum reading is noted on the field-strength meter. The tap is then adjusted on L2 for the lowest reflected-power reading on the SWR bridge. Repeat these two adjustments until no further increase in field strength can be obtained; this point should coincide with the lowest SWR. The number of turns needed for L2 will have to be determined experimentally for 40- and 20-meter operation. There will be proportionately fewer turns required.

### Matching with an L Network

Any mobile antenna that has a feed-point impedance less than the characteristic impedance of the transmission line can be matched to the line by means of a simple L network, as shown in Fig. 17. The network is composed of  $C_M$  and  $L_M$ . The required values of  $C_M$  and  $L_M$  may be determined from the following:

$$C_M = \frac{\gamma R_A (R_O - R_A) \times 10^9}{2\pi f (\text{kHz}) R_A R_O} \text{ pF}$$

and

$$L_M = \frac{\gamma R_A (R_O - R_A) \times 10^3}{2\pi f (\text{kHz})} \text{ } \mu\text{H}$$

where  $R_A$  = the antenna feed-point impedance

$R_O$  = the characteristic impedance of the transmission line.

As an example, if the antenna impedance is 20 ohms and the line is 50-ohm coaxial cable, then at 4000 kHz,

$$C_M = \frac{\gamma 20(50 - 20) \times 10^9}{(6.28)(4000)(20)(50)}$$

$$= \frac{\gamma 600 \times 10^4}{(6.28)(4)(2)(5)}$$

$$= \frac{24.1}{251.2} \times 10^4 = 974 \text{ pF}$$

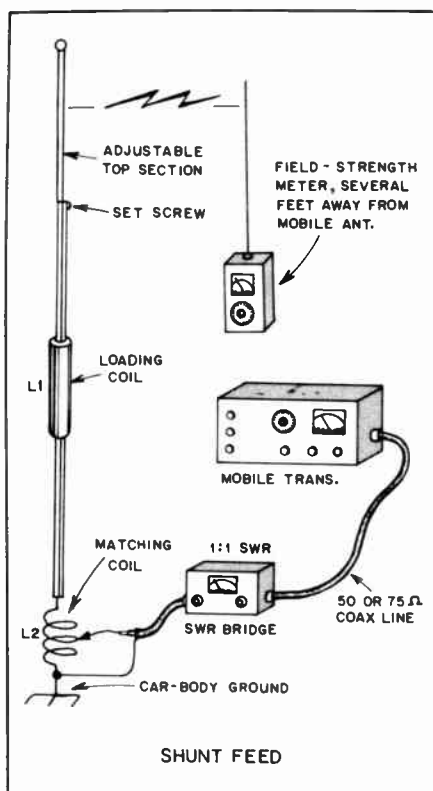


Fig. 16 — A mobile antenna using shunt-feed matching. Overall antenna resonance is determined by the combination of L1 and L2. Antenna resonance is set by pruning the turns of L1, or adjusting the top section of the whip, while observing the field-strength meter or SWR indicator. Then, adjust the tap on L2 for lowest SWR.

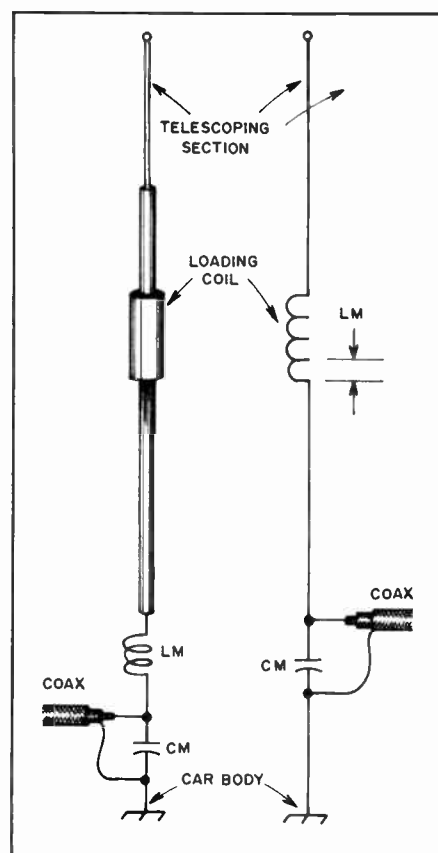


Fig. 17 — A whip antenna may also be matched to coax line by means of an L network. The inductive reactance of the L network can be combined in the loading coil, as indicated at the right.

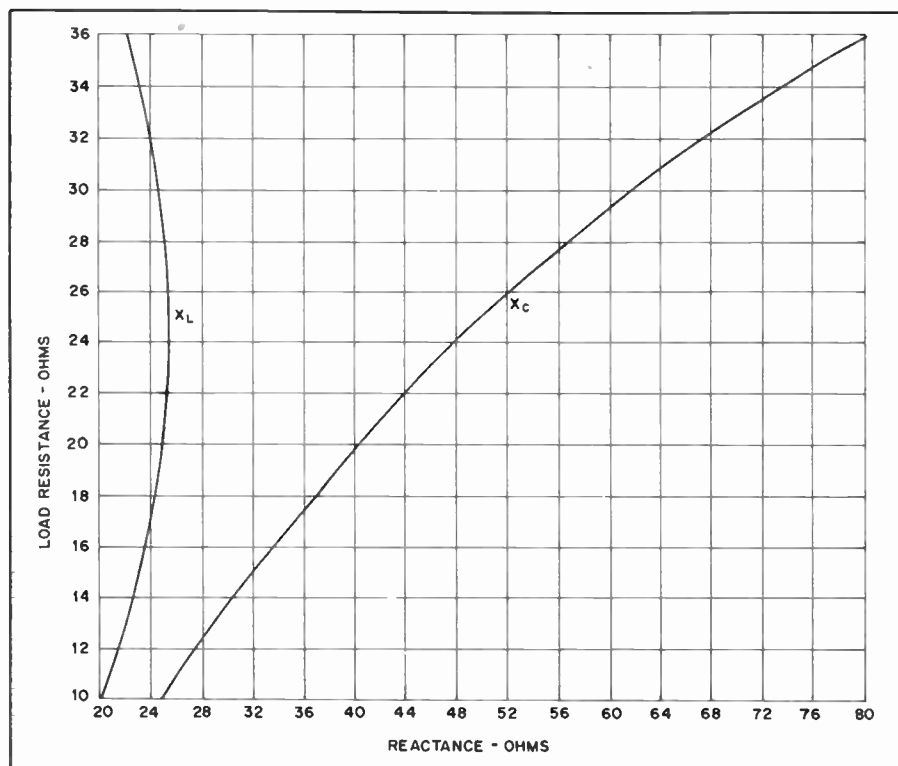


Fig. 18 — Curves showing inductive and capacitive reactances required to match a 50-ohm coaxial line to a variety of antenna resistances.

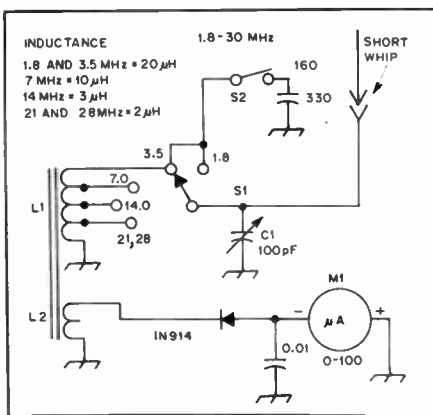


Fig. 19 — A band-switched field-strength meter for tuning up the hf-band mobile antenna. It should be assembled into a metal box. In use, it should be placed several feet from the antenna under test. C1 is tuned for a peak meter reading at the operating frequency. It can be detuned for varying the sensitivity. L1 is a 22- $\mu$ H inductor. It consists of 70 turns of no. 26 enam. wire on a T80-6 toroid core. Taps are chosen for the desired amateur bands. L2 is 10 turns of no. 26 enam. over the ground end of L1.

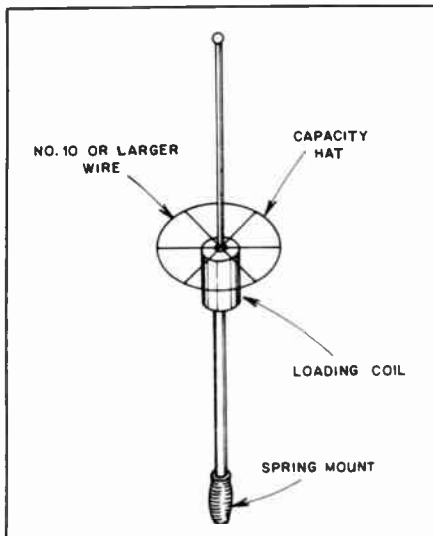


Fig. 20 — A capacitance "hat" can be used to improve the performance of base- or center-loaded whips. A solid metal disk can be used in place of the skeleton disk shown here.

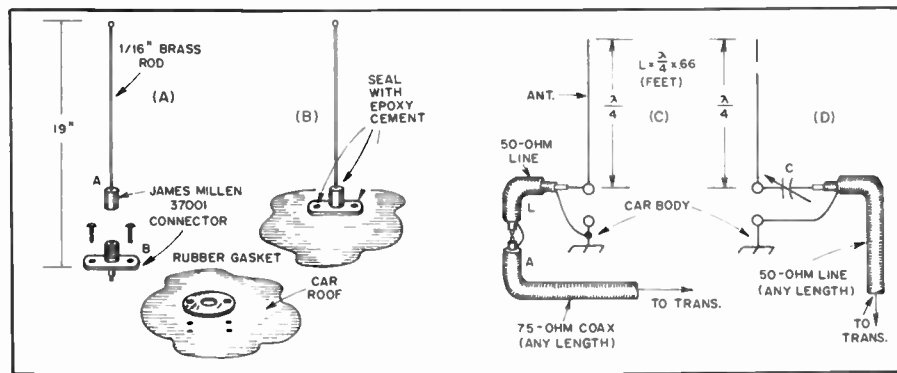


Fig. 21 — At A and B, an illustration of how a quarter-wavelength vertical antenna can be mounted on a car roof. The whip section should be soldered into the cap portion of the Millen connector, then screwed to the base socket. This handy arrangement permits removing the antenna when desired. Epoxy cement should be used at the two mounting screws to prevent moisture from entering the car. Diagrams C and D are discussed in the text.

$$L_M = \frac{\gamma 20(50 - 20) \times 10^3}{(6.28)(4000)}$$

$$= \frac{\gamma 600}{25.12} = \frac{24.5}{25.12} = 0.97 \mu\text{H}$$

The chart of Fig. 18 shows the capacitive reactance of  $C_M$  and the inductive reactance of  $L_M$  necessary to match various antenna impedances to 50-ohm coaxial cable.

In practice,  $L_M$  need not be a separate inductor. Its effect can be duplicated by adding an equivalent amount of inductance to the loading coil, regardless of whether the loading coil is at the base or at the center of the antenna.

### Adjustment

In adjusting this system, at least part of  $C_M$  should be variable, the balance being made up of combinations of fixed mica capacitors in parallel as needed.

A small, one-turn loop should be connected between  $C_M$  and the chassis of the car, and the loading coil should then be adjusted for resonance at the desired frequency as indicated by a dip meter coupled to the loop at the base. Then the transmission line should be connected, and a check made with an SWR indicator connected at the transmitter end of the line.

With the line disconnected from the antenna again,  $C_M$  should be readjusted and the antenna returned to resonance by readjustment of the loading coil. The line should be connected again, and another check made with the SWR bridge. If the SWR is less than it was on the first trial,  $C_M$  should be readjusted in the same direction until the point of minimum SWR is found. Then the coupling between the line and the transmitter can be adjusted for proper loading. It will be noticed from Fig. 18 that the inductive reactance varies only slightly over the range of antenna resistances likely to be

encountered in mobile work. Therefore, most of the necessary adjustment is in the capacitor.

The one-turn loop at the base should be removed at the conclusion of the adjustment and slight compensation made at the loading coil to maintain resonance. Fig. 19 shows a field-strength meter circuit that is useful when adjusting mobile antennas.

### Top-Loading Capacitance

Because the coil resistance varies with the inductance of the loading coil, the resistance can be reduced, beneficially, by reducing the number of turns on the coil. This can be done by adding capacitance to that portion of the mobile antenna that is above the loading coil (Fig. 20). To achieve resonance, the inductance of the coil is reduced proportionally. "Capacity hats," as they are often called, can consist of a single stiff wire, two wires or more, or a disk made up from several wires, like the spokes of a wheel. A solid metal disk can also be used. The larger the capacity hat, in terms of volume, the greater the capacitance. The greater the capacitance, the smaller the amount of inductance needed in the loading coil for a given resonant frequency.

There are two schools of thought concerning the attributes of center-loading and base-loading. It has not been established that one system is superior to the other, especially in the lower part of the hf spectrum. For this reason both the base- and center-loading schemes are popular. Capacity-hat loading is applicable to either system. Since more inductance is required for center-loaded whips to make them resonant at a given frequency, capacity hats should be particularly useful in improving their efficiency.

### VHF Quarter-Wavelength Vertical

Ideally, the vhf vertical antenna should be installed over a perfectly flat plane reflector to assure uniform omnidirectional radiation. This suggests that the center of the automobile roof is the best place to mount it. Alternatively, the flat portion of the auto rear-trunk deck can be used, but will result in a directional pattern because of car-body obstruction. Fig. 21 illustrates at A and B how a Millen high-voltage connector can be used as a roof mount for a 144-MHz whip. The hole in the roof can be made over the dome light, thus providing accessibility through the upholstery. RG-59/U and matching section L, Fig. 21C, can be routed between the car roof and the ceiling upholstery and brought into the trunk compartment, or down to the dashboard of the car. Some operators install an SO-239-type coax connector on the roof for mounting the whip. The method is similar to that of Fig. 21.

It has been established that quarter-wavelength vertical antennas for mobile



work through repeaters are not as effective as 5/8-wavelength verticals are. The 1/4-wavelength types cause considerably more "picket fencing" (rapid flutter) of the signal than is the case with the 5/8-wavelength type of antenna. The flutter that takes place when vertical polarization is used is caused by vertical conductive objects being between the mobile antenna (near field) and the station being worked (or the repeater). As the vehicle moves past these objects there is a momentary blockage or partial blockage of the signal path.

## 2-Meter 5/8-Wavelength Vertical

Probably the most popular antenna used by the fm group is the 5/8-wavelength vertical. As stated previously, this antenna has some gain when compared to a dipole. The antenna can be used in either a fixed location with radials or in a mobile installation. An inexpensive antenna of this type can be made from a modified CB whip. The antenna shown in Figs. 22 and 23 is a 5/8-wavelength, 2-meter whip.

There are a number of different types of CB mobile antennas available. This antenna to be modified consists of a clamp-on trunk mount, a base loading coil, and a 39-inch (0.99m) spring-mounted, stainless-steel whip.

The modification consists of removing the loading-coil inductance, winding a new coil, and mounting a 3-30 pF trimmer in the bottom housing. The capacitor is used for obtaining a precise match in conjunction with the base coil tap.

The first step is to remove the weatherproof phenolic covering from the coil. Remove the base housing and clamp the whip side of the antenna in a vise. Insert a knife blade between the edge of the whip base and the phenolic covering. Gently tap the knife edge with a hammer to force the housing away from the whip section.

Next, remove the coil turns and wind a new coil using no. 12 wire. The new coil should have nine turns, equally spaced. The tap point is two turns up from the base (ground) end on the antenna as modified. The trimmer capacitor is mounted on a terminal strip that is installed in the base housing. A hole must be drilled in the housing to allow access to the capacitor adjustment screw.

Initially, the tap on the coil was tried at three turns from the bottom. The antenna was mounted on the car, an SWR indicator was inserted in the feed line, and C1 and the whip height were adjusted for a match. A match was obtained, but when the phenolic sleeve was placed over the coil, it was impossible to obtain an adjustment that proved a match. Apparently the dielectric material used in the coil cover has an effect on the coil. After some experimenting it was found that with the tap two turns up from the bottom, and

with the cover over the coil, it was possible to get a good match with 50-ohm line.

This antenna can be used in a fixed location by adding radials. The radials (four) should be slightly longer than 1/4-wave and should be attached to the base mounting section.

## A 5/8-Wavelength 220-MHz Mobile Antenna

This antenna, Figs. 24 and 25, was developed to fill the gap between a homemade 1/4-wavelength mobile antenna and a commercially made 5/8-wavelength model. There have been other antennas made using modified CB models. This still presents the problem of cost in acquiring the original antenna. The major cost in this setup is the whip portion. This can be any tempered rod that will spring easily.

## Construction

The base insulator portion is constructed of 1/2-inch (13-mm) Plexiglas rod. A few minutes work on a lathe was sufficient to shape and drill the rod. The bottom 1/2-inch (13-mm) of the rod is turned down to a diameter of 3/8 inch (9.5-mm). This portion will now fit into a PL-259 uhf connector. A hole, 1/8-inch (3-mm) diameter, is drilled through the center of the rod. This hole will contain the wires that make the connections between the center conductor of the connector and the coil tap. The connection between the whip and the top of the coil is also run through this opening. A stud is force-fitted into the top of the Plexiglas rod. This allows the whip to be detached from the insulator portion.

The coil should be initially wound on a form slightly smaller than the base insulator. When the coil is transferred to the Plexiglas rod it will keep its shape and will not readily move. After the tap point has been determined, a longitudinal hole is drilled into the center of the rod. A no. 22 wire can then be inserted through the center of the insulator into the connector. This method is also used to attach the whip to the top of the coil. After the whip has been fully assembled a coating of epoxy cement is applied. It seals the entire



Fig. 22 — The new coil is tapped two turns from the base end. It may be necessary to file the coil ends so that the assembly will fit in the phenolic covering.

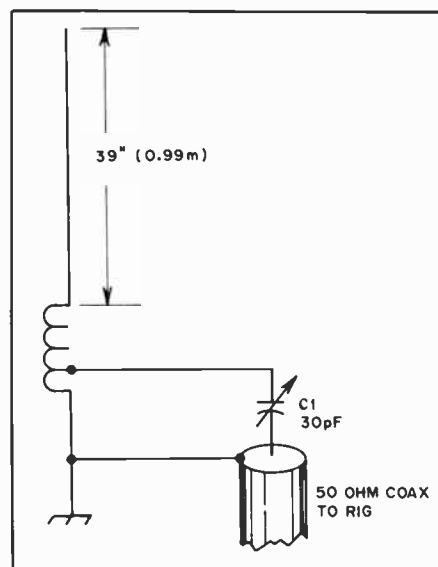


Fig. 23 — Circuit details of the 5/8-wavelength antenna for mobile use. C1 is a 3-30 pF mica compression trimmer.



Fig. 24 — Photograph of the 220-MHz 5/8-wavelength mobile antenna. The bottom end of the coil is soldered to the coaxial connector.

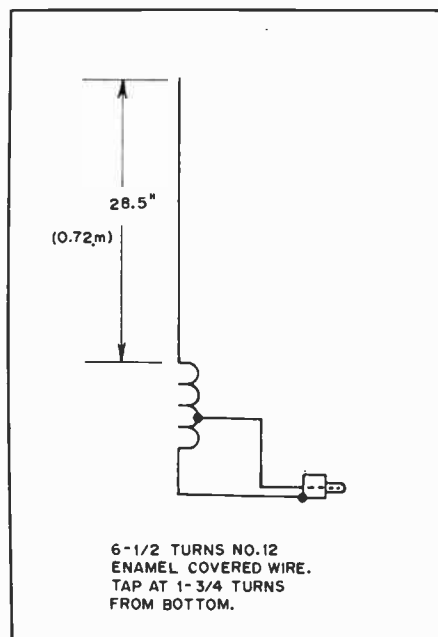


Fig. 25 — Diagram of the 220-MHz mobile antenna.



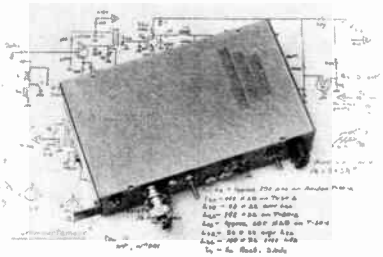


Fig. 26 — Exterior view of the tiny 40-meter CW transceiver built by W7ZOI. The key paddle protrudes from the box at the lower left in the picture.

assembly and provides some additional strength. During a full winter's use, there was not any sign of cracking or mechanical failure.

### Adjustment

Prior to final assembly of the whip antenna, the correct tap point should be determined. This will produce the least

reflected power. The whip length should be cut initially for the desired operating frequency.

### An Ultra-Portable CW Transceiver for 7 MHz

For portable operation it is desirable that the equipment be physically small. A major criterion for miniaturization is simplicity. This forms the basis of the W7ZOI transceiver described in this section.

Shown in Fig. 27 is the circuit. Q1 functions as a crystal-controlled oscillator operating at 7 MHz. This stage serves a dual role. It drives Q2, the power output amplifier of the transmitter. Second, it provides BFO injection for the direct-conversion receiver.

Initially, it may seem limiting to utilize crystal control for both the transmitter and the receiver. But, if the transmitter is to be crystal controlled it is generally unnecessary for the receiver to have the ability to receive on different frequencies. On the hf bands contacts occur rarely on

a split-frequency basis. It is mandatory though that the crystal oscillator have capability for slight adjustment. If this were not present, it would be possible for another station to be exactly zero beat with the transceiver without the operator realizing its presence. This tuning is achieved by moving the crystal frequency slightly by switching in series inductors, L1 or the series combination of L1 and L2. With the component values shown in Fig. 27 the shift is  $\pm 0.5$  or  $\pm 1$  kHz. The shift will vary with different crystals: Experimentation may be required.

An RCA CA3028A serves as a product detector. The output is transformer coupled to a two-stage audio amplifier that utilizes a pair of bipolar transistors. In the interest of simplicity, no audio-gain control is included. The only selectivity in the receiver is that which is provided by the low-pass characteristic of the audio amplifier and the limited bandwidth of T1.

The transmitter portion of the circuit consists of the crystal oscillator (Q1) and

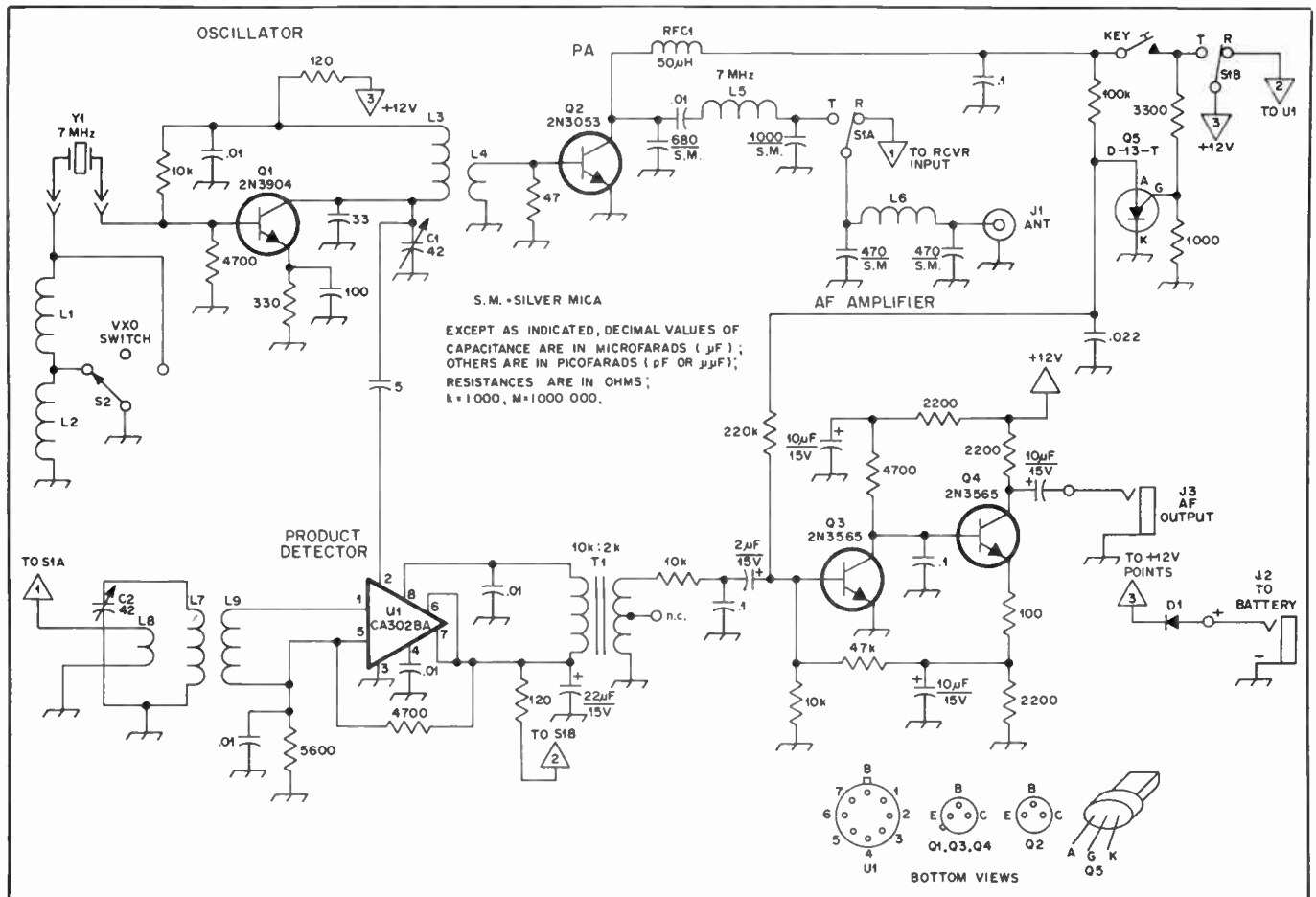


Fig. 27 — Schematic diagram of the ultra-portable transceiver. Fixed-value capacitors are discussed in the text. Resistors are 1/4-watt composition.

- C1, C2 — Subminiature ceramic trimmer, 42pF maximum.
- D1 — Silicon rectifier diode, 50 PRV, 500 mA.
- J1 — BNC chassis-mount coax connector.
- J2, J3 — Phone jack.
- L1, L2 — 20 turns no. 22 enam. on Amidon

- T-50-2 toroid core (Amidon Assoc.).
- L3 — 44 turns no. 28 enam. on T-50-2 core.
- L4 — 4 turns no. 22 enam. over L3 winding.
- L5, L6 — 14 turns no. 22 enam. on T-50-2 core.
- L7 — 60 turns no. 28 enam. on T-50-2 core.
- L8 — 5 turns no. 22 enam. over L7 winding.

- L9 — 10 turns no. 22 enam. over L7 winding.
- T1 — Miniature 10,000-ohm to 2000-ohm transformer. Center tap not used.
- U1 — RCA CA3028A.
- Y1 — 7-MHz crystal.

the keyed power amplifier (Q2). Keying is by means of a microswitch in series with the supply to the collector. The microswitch is activated by a strip of pc board which serves as a paddle. The details may be seen in the photographs. Keying is clean, although with this method the backwave is only suppressed by approximately 30 dB. Owing to the low power output of the transmitter (0.5 watt), the backwave presents no problem.

A General Electric D13-T type of programmable unijunction transistor (PUT) serves as a sidetone oscillator. The output is injected into the input of the two-stage audio amplifier.

Transmit-receive switching is realized with a double-pole, double-throw toggle switch, S1. One section switches the antenna while the other controls the power-supply output. Receiver muting is done by removing the operating voltage from the detector during transmit periods.

A low-pass filter section (L6) is included at the antenna jack of the transceiver. This provides harmonic suppression at the transmitter output. Additionally, it adds preselection to the receiver front end. This was found to be helpful when the transceiver was operated in close proximity to TV broadcast stations.

The station is built on a 2 × 5-inch (51 × 127 mm) double-sided pc board. The side containing the components is the ground foil, with the interconnecting runs on the back of the board. The box size is 1-1/2 × 3 × 5 inches (38 × 76 × 127 mm). Locations of the components may be seen in the photographs (Figs. 26 and 28). Placing all of the controls on one side of the chassis permits convenient operation. The transceiver is normally held in the left hand, with the right hand activating the controls and key. The battery pack is composed of AA-size NiCads, and usually resides in a parka pocket.

This rig has been available for emergency communications when needed. A deficiency of the design, as presented here, is the need for plug-in crystals. Not only are loose crystals lost easily, but the pins are subject to corrosion. The builder's version of this transceiver could contain switched crystals. No pc board information is available for this project.

#### The Mini-Miser's Dream Receiver

A receiver that featured good performance with a modest outlay of building time and components appeared in the 45th edition of *The Radio Amateur's Handbook*. The original design was that of Byron Goodman, W1DX, and incorporated vacuum tubes in the construction.

This updated version (Fig. 29) by Doug DeMaw, W1FB, utilizes the same principle of going directly into a mixer in the front end which is followed by a simple crystal filter. Solid-state construction is used throughout the design and audio

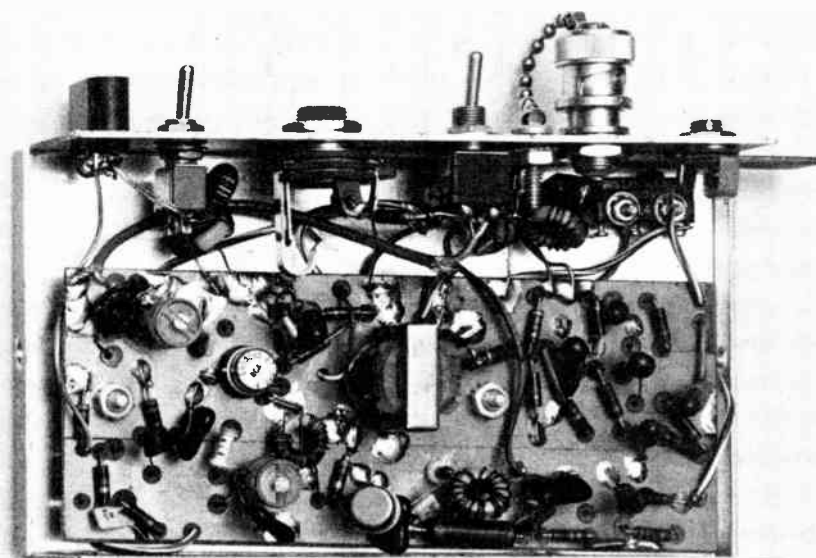


Fig. 28 — Interior of the portable mini-transceiver. Double-clad pc board is used.

output is sufficient to drive a small speaker. This receiver should fill the need for a simple, compact unit where low current drain is also a requirement.

#### Circuit Description

There are some departures from the W1DX design, mainly to minimize cost and package size. The major compromise was the elimination of agc and multiband coverage. There is ample room inside the cabinet of this receiver to accommodate one or two small converters for reception of bands other than 40 meters. This main frame is designed for 7- to 7.175-MHz coverage.

Fig. 30 shows an IC being used as the receiver front end — a CA3028A which is configured as a balanced mixer. The input tuned circuit, T1, is designed to match a 50-ohm antenna to the 2000-ohm base-to-base impedance of the mixer IC. The transformer is broadband in nature (300 kHz at the 3-dB points), and has a loaded Q of 23. This eliminates the need for a front-panel peaking control — a cost-cutting aid to simplicity.

The output tuned circuit, L1, is a bifilar-wound toroid which is tuned approximately to resonance by means of a mica trimmer, C2. The actual setting of C2 will depend upon the degree of i-f selectivity desired, and typically the point of resonance will not be exactly at 3300.5, the i-f center frequency.

Goodman used a half-lattice filter (two crystals) in his design, but this requires two crystals which are related properly in addition to a BFO crystal. For this reason, an older circuit was employed — a single crystal filter with a phasing capacitor, C3. The latter approach pro-



Fig. 29 — Front view of the assembled 40-meter miniature receiver. A 20-meter converter is seen in the foreground. Pc boards and parts kits for this project are available from Circuit Board Specialists, Box 969, Pueblo, CO 81002. Boards and kits for a mating transmitter (May 1978 QST, page 16) are available from the same supplier.

vides reasonably good single-signal reception (at least 30 dB rejection of the unwanted response), and assures much better performance than is possible with simpler direct-conversion receivers.

A single i-f amplifier, U2, is used to provide up to 40 dB of gain. R1 serves as a manual i-f gain control, and will completely cut off the signal output when set for minimum i-f gain. No audio gain control is used. T2 is designed to transform the 8000-ohm collector-to-collector impedance of U2 down to 500 ohms, and has a bandwidth of 100 kHz. The loaded Q is 33.

A two-diode product detector converts the i-f energy to audio. BFO injection voltage is obtained by means of a crystal-controlled oscillator, Q2. RFC2

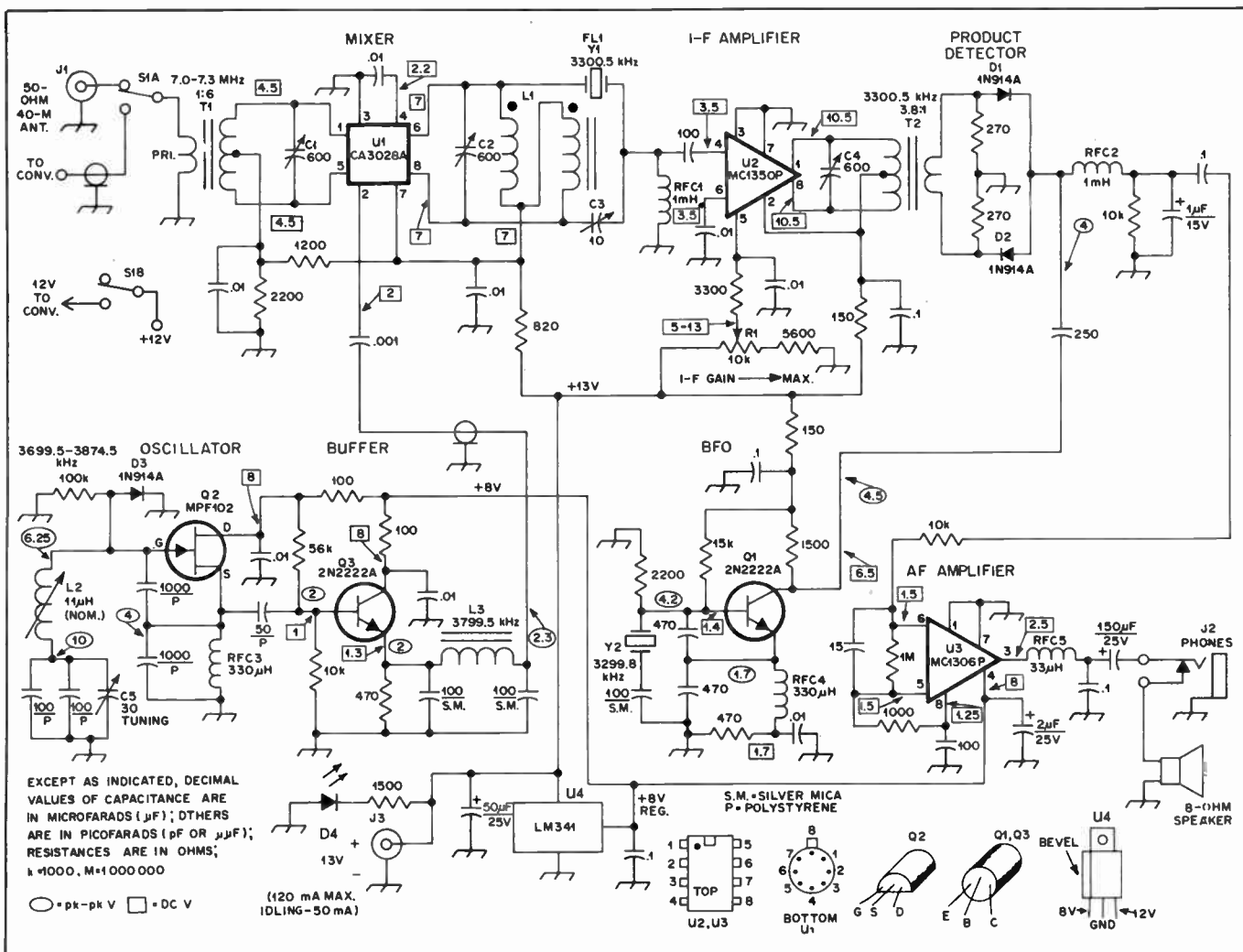


Fig. 30 — Schematic diagram of the 40-meter receiver. Fixed-value capacitors are chip or disk ceramic unless noted otherwise. Capacitors with polarity marked are electrolytic. S.M. indicates silver mica, and P is for polystyrene. Fixed-value resistors are 1/4- or 1/2-W composition.

C1, C2, C4 — 170- to 600-pF mica trimmer (Arco 4213).  
 C3 — 10-pF subminiature trimmer. Ceramic or pc-mount air variable suitable.  
 C5 — Miniature air variable, 30 pF maximum (Millen 25030E or similar).  
 D1-D3, incl. — High-speed silicon switching diode. 1N914A or equiv.  
 J1, J3 — Single-hole-mount phono jack.  
 J2 — Closed-circuit phone jack.  
 L1 — Toroidal bifilar-wound inductor. L = 5.8 µH. 8 turns no. 28 enam., bifilar wound on Amidon FT-37-61 ferrite core. Note polarity marks.  
 L2 — Slug-tuned inductor (see text), 11 µH nominal. J.W. Miller 42A105CBI or equiv.

Q<sub>U</sub> = 125.  
 L3 — Toroidal inductor, 17 µH, 19 turns no. 26 enam. wire on Amidon FT-50-61 ferrite core.  
 R1 — 10,000-ohm miniature composition control, linear taper.  
 RFC1, RFC2 — Miniature 1-mH rf choke, Millen J302-1000 or equiv.  
 RFC3, RFC4 — Miniature 330-µH rf choke (Millen J302-330 or equiv.).  
 RFC5 — Miniature rf choke, 33 µH, Millen J302-33 or equiv.  
 S1 — Miniature dpdt toggle.  
 T1 — Toroidal transformer. Primary has 2 turns no. 24 enam. wire. Secondary has 14 turns no. 24 enam. wire on Amidon T50-2 core.

T2 — Toroidal transformer. Primary has 9 turns no. 26 enam. wire on Amidon FT-37-61 core. Secondary has 3 turns no. 26 enam. wire. Primary winding has center tap.  
 U1 — RCA CA3028A. Bend pins to fit 8-pin dual-in-line IC socket.  
 U2 — Motorola MC1350P.  
 U3 — Motorola MC1306P.  
 U4 — Eight-volt regulator, National Semiconductor LM341.  
 Y1, Y2 — Surplus crystal in HC-6/U case or International Crystal Co. type GP with 32-pF load capacitance.

and the 1-µF bypass capacitor filter the rf, keeping it out of the audio line to U3.

Audio-output IC U3 contains a pre-amplifier and power-output system. It will deliver approximately 300 mW of af energy into an 8-ohm load. RFC5 is used to prevent rf oscillations from occurring and being radiated to the front end and i-f system of the receiver. The 0.1-µF bypass at RFC5 also helps prevent oscillations.

A three-terminal voltage regulator, U4, supplies the required operating voltage to U3. It also provides regulated voltage for

the VFO and buffer stages of the local oscillator (Q2 and Q3). The latter consists of a stable series-tuned Clapp VFO and an emitter-follower buffer stage. A single-section pi network is placed between the emitter of Q3 and the injection terminal of U1. It has a loaded Q of 1, and serves as a filter for the VFO output energy. It is designed for a bilateral impedance of approximately 500 ohms. The recommended injection-voltage level for a CA3028A mixer is 1.5 rms. Good performance will result with as little as 0.5 volt

rms. A 1-volt level is available with the circuit shown in Fig. 30.

A red LED is used at D4 as an on-off indicator. Since it serves mainly as "window dressing," it need not be included in the circuit.

### Construction Notes

Front panel, rear panel, side brackets, and chassis are made from double-sided circuit-board material. The chassis is an etched circuit board, the pattern for which is given in Fig. 33. There is no reason



why the top and bottom covers for the receiver can not be made of the same material by soldering six pieces of pc board together to form two U-shaped covers.

The local oscillator is housed in a compartment made from pc-board sections. It measures (HWD) 1-3/8 × 1-5/8 × 2-3/4 inches (35 × 41 × 70mm). A 1/4-inch (6-mm) high pc-board fence of the same width and depth is soldered to the bottom side of the pc board (opposite the top partition) to prevent rf energy from entering or leaving the local-oscillator section of the receiver. Employment of the top and bottom shields stiffens the main pc board, and that helps prevent mechanical instability of the oscillator, which can result from stress on the main assembly.

Silver plating has been applied to the main pc board and to the front and rear panels. This was done to enhance the appearance and discourage tarnishing of the copper. It is not a necessary step in building the receiver. The front panel has been sprayed with green paint, then baked for 30 minutes by means of a heat lamp. A coarse grade of sandpaper was used to abrade the front panel before application of the paint. The technique will prevent the paint from coming off easily when the panel is bumped or scratched. Green Dymo tape labels are used to identify the panel controls.

There is ample room inside the cabinet, along the rear inner panel surface, to install a small crystal-controlled converter for some other hf band. A switch, S1, is located on the front panel to


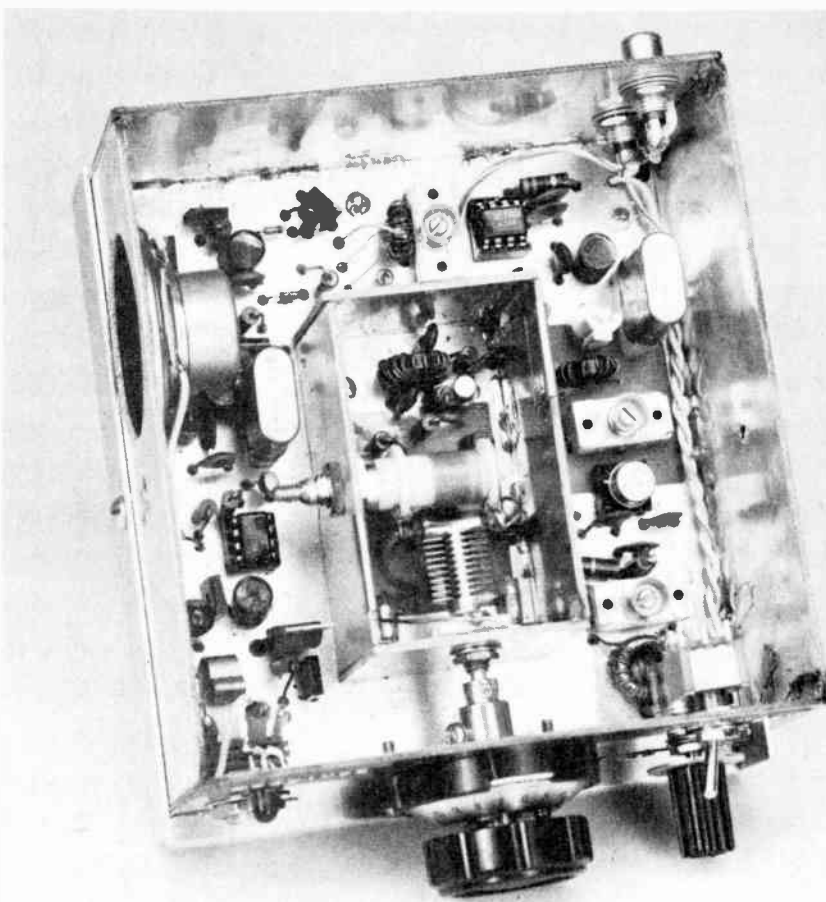


Fig. 31 — Interior view of the receiver. The front end is at the lower right. The leads of U1 are bent to align with an 8-pin dual-in-line IC socket. The rim of the speaker is tack-soldered to the pc-board side wall at two points. The 20-meter converter mounts on the rear wall inside the receiver (upper left corner).

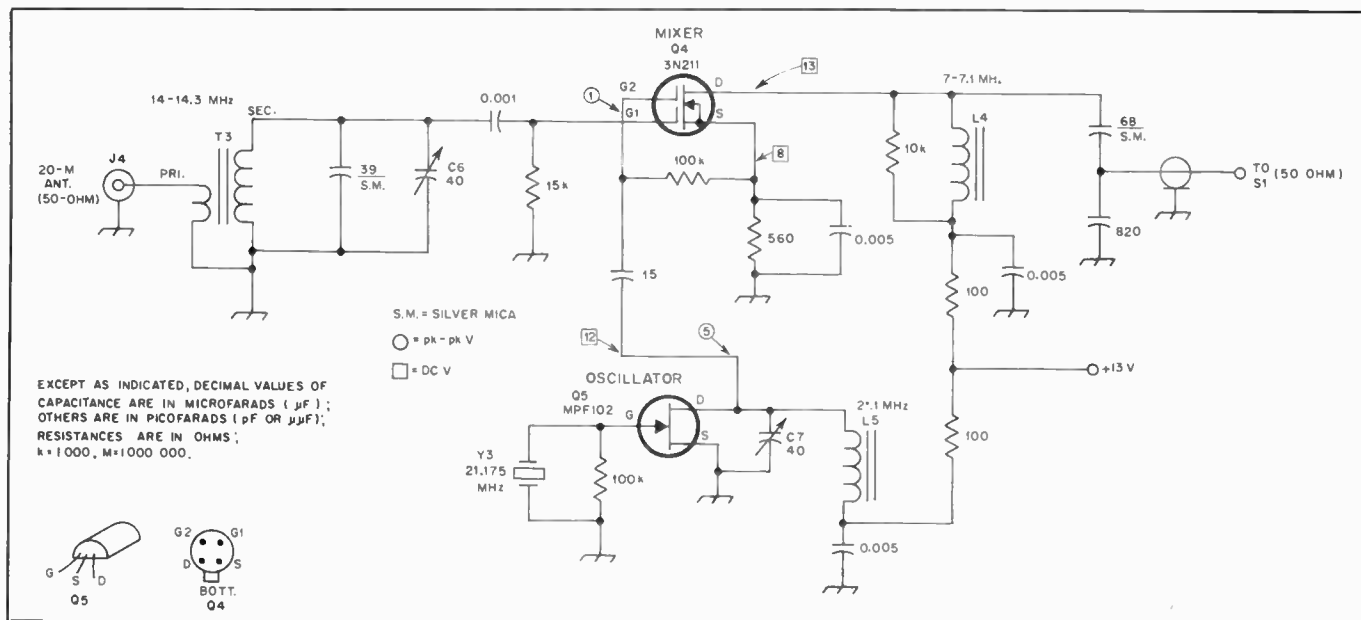



accommodate a planned 20-meter converter. A suitable circuit is given in Fig. 32.

All of the toroidal inductors are coated several times with Q dope after they are installed in the circuit. The VFO coil is treated in a like manner. The polystyrene VFO capacitors should be cemented to the pc board after a circuit is tested. This will help prevent mechanical instability. Hobby cement or epoxy glue is OK for the job. Use only a drop or two of cement at each capacitor — just enough to affix it to the pc board.

**Alignment and Operation**

The VFO should be aligned first. This can be done by attaching a frequency counter to pin 2 of U1 or by monitoring the output on a receiver tuned to the 75-meter band. Coverage should be from 3699.5 to 3874.5 kHz for reception from 7.0 to 7.175 MHz. Actual coverage may be more or less than the spread indicated, depending on the absolute values of the VFO capacitors and stray circuit inductance and capacitance. Greater coverage can be had by using a larger capacitance value at C5, the main tuning control. Those interested only in phone-band coverage can align the VFO accordingly and change Y2 to 3301.8 kHz.

Final tweaking is effected by attaching an antenna and peaking C1, C2 and C4 for maximum signal response at 7085 kHz. To obtain the selectivity characteristics desired (within the capability of the circuit), adjust C2 and C3 experimentally. C2 will provide the major effect. C3 should be set for minimum response on the unwanted side of zero beat. A fairly strong signal will be needed to hear the unwanted response.

For reception of lower sideband, it will be necessary to use a different BFO frequency — 3301.8 kHz. The crystal indicated in Fig. 30 was used because it was the only one available at the time of construction. Those wishing to shift the BFO frequency a few hundred hertz can place a trimmer in series with Y2 rather than use the 100-pF capacitor shown.

Because there is no agc in this receiver, the i-f gain should be set low for comfortable listening. Too much gain will cause the audio circuit to be overdriven, and distortion will result. To prevent earsplitting signal levels, one can install a pair of 1N34A diodes (back to back) across the output jack, J2.

**Bits and Pieces**

The photograph shows some fancy looking components on the circuit board. Tantalum capacitors are seen where electrolytics are indicated on the diagram. Either type will work nicely. Tantalums were found at a flea market for 10 cents each, so they were used. Similarly, the 0.1-μF capacitors used are the high-class kind (Aerovox CK05BX), which sell for roughly 70 cents each. Mylar or disk

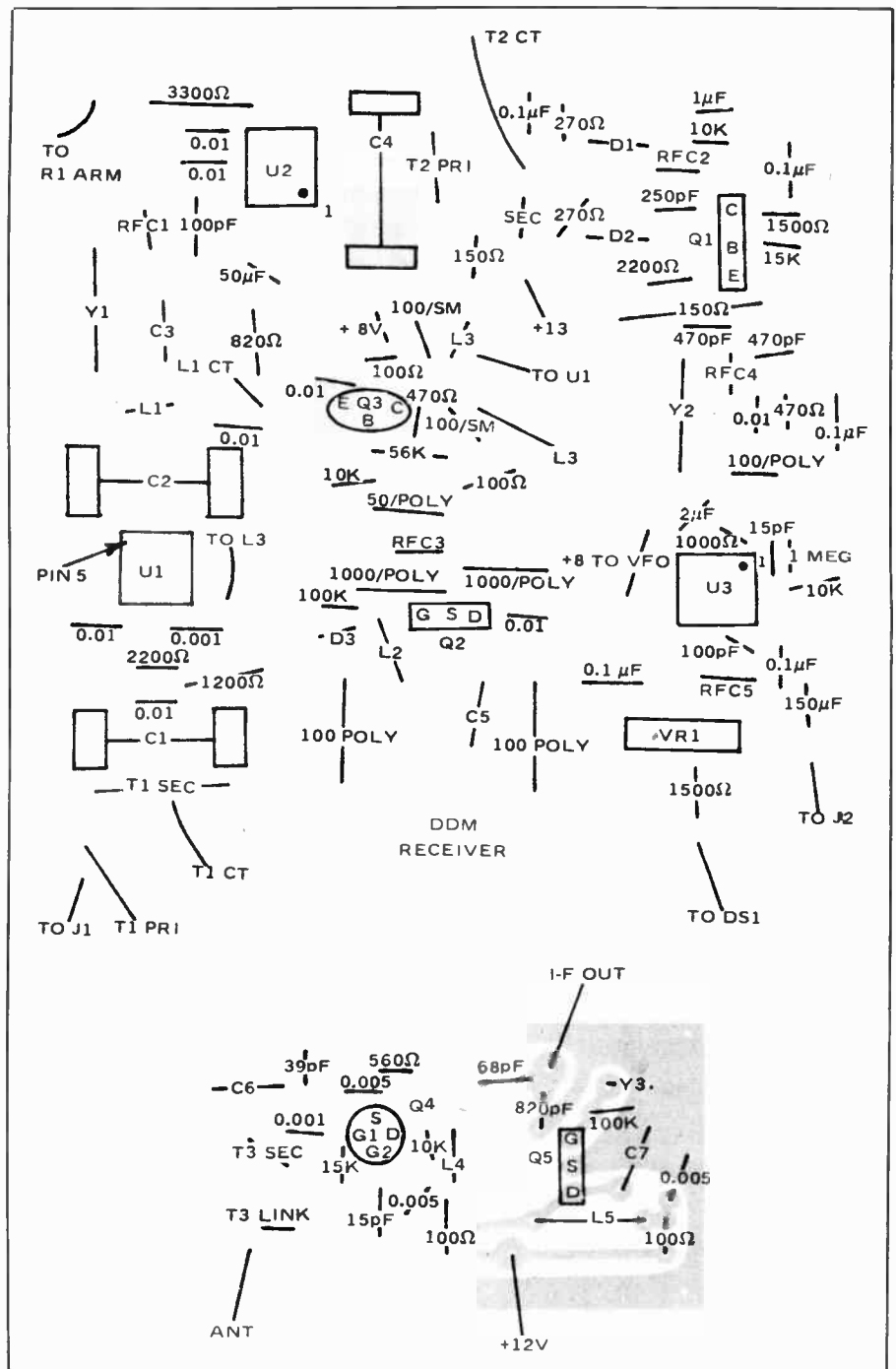


Fig. 33 — Foil-side scale pattern of the pc board. Circuit board is double-sided glass-epoxy material. Ground-plane copper should be removed directly opposite Q2 and related components (oscillator) for an area of 1-1/2 x 1-1/2 inches (38 x 38-mm). Remove copper in similar manner on ground-plane side of board opposite L1, C3 and Y1 (1 x 1-1/4 inch (25 x 32-mm) area). Removal of foil will prevent unwanted capacitive effects in those critical parts of the circuit. Ground-plane side of board should be electrically common to the ground foils on opposite side of board at several points.

ceramic 0.1-μF units will be fine as substitutes.

The polystyrene capacitors were obtained from Radio Shack in an assortment pack. New units are made by Centralab, and they sell for less than 20 cents each in single lots. Since they are more stable than silver micas, they are recommended for the VFO circuit.

All of the toroid cores were purchased by mail from Amidon Associates. A J.W.

Miller 42-series coil is used in the VFO, but any slug-tuned ceramic form can be used if it has good high-frequency core material. The unloaded Q of the inductor should be at least 150 at 3.5 MHz. L2 in this design has 3/8-inch (9.5-mm) diameter body. The winding area is 5/8-inch (16-mm) long.

The metal cases of both crystals should be connected to ground by means of short lengths of wire. This will prevent un-

wanted radiation from the BFO crystal, and will help keep the filter crystal from picking up stray energy. A metal cover should be placed on the VFO compartment for reasons of isolation.

James Millen encapsulated rf chokes are used in the receiver. Any subminiature choke of the approximate inductance indicated will be suitable and it need not be encapsulated. The VFO tuning capacitor is also a Millen part. Ample room exists between the VFO box and the front panel to allow making the box longer. That will permit use of a larger variable capacitor. A double-bearing capacitor is recommended for best mechanical stability of the VFO.

The i-f system and BFO can be tailored to frequencies other than those indicated. The VFO, mixer, and i-f amplifier tuned circuits will have to be altered accordingly, if crystals of other frequencies

in the 2- to 3-MHz range are chosen.

Performance of this receiver is quite good. A 0.1- $\mu$ V signal from a generator is plainly audible. No hum or distortion is heard in the output of this receiver at normal listening levels. VFO drift is 45 Hz from a cold start to stabilization, and strong signals do not pull the oscillator.

Extremely strong local signals (1000  $\mu$ V or greater) will cause desensitization of the receiver when they appear off frequency from where the operator is listening. Under ordinary conditions this will not be a problem. At some sacrifice in noise figure and sensitivity, those living in areas where other amateurs are nearby can modify T1 to aid the situation. C1 should remain across all of the T1 secondary, and a 2200-ohm resistor should be connected across C1. Pins 1 and 5 of U1 should be connected to two turns each side of the center tap of the

secondary. This will require cutting the pc board elements to divorce pins 1 and 5 from C1. This design trade-off is quite acceptable at 40 meters, as the atmospheric noise level will mask the reduction in receiver noise performance. With the circuit change there was no desensing evident below approximately 8000  $\mu$ V.

Agc could be used in this receiver by applying the audio-derived "hang" type used by Goodman in his *Handbook* design. If the feature was adopted, agc voltage would be applied to pin 5 of U2 and the manual gain control would be eliminated. In such a case, it would be necessary to add an af gain control between the product detector and U3. It should be remembered that minimum gain results when 13 volts are applied to pin 5 of U2. The lower the voltage at that point, the greater the gain.

# Code Transmission

Keying a transmitter properly involves much more than merely turning it on and off with a fast manually operated switch (the key). If the output is permitted to go from zero to full instantaneously (zero "rise" time), side frequencies, or *key clicks*, will be generated for many kilohertz either side of the transmitter frequency, at the instant the key is closed. Similarly, if the output drops from full to zero instantaneously (zero "decay" time), side frequencies will be generated at the instant of opening the key. The amplitude of the side-frequency energy decreases with the frequency separation from the transmitter frequency. To avoid key clicks and thus to comply with the FCC regulations covering spurious radiations, the transmitter output must be "shaped" to provide finite rise and decay times for the envelope. The longer the rise and decay times, the less will be the side-frequency energy and extent.

Since the FCC regulations require that "... the frequency of the emitted wave shall be as constant as the state of the art permits," there should be no appreciable change in the transmitter frequency while energy is being radiated. A *slow* change in frequency is called a *frequency drift*; it is usually the result of thermal effects on the oscillator. A *fast* frequency change, observable during each *dit* or *dah* of the transmission, is called a *chirp*. Chirp is usually caused by a nonconstant load on the oscillator or by dc voltage changes on the oscillator during the keying cycle. Chirp may or may not be accompanied by drift.

If the transmitter output is not reduced to zero when the key is up, a *backwave* (sometimes called a "spacing wave") will be radiated. A backwave is objectionable to the receiving operator if it is readily apparent; it makes the signal slightly harder to copy. However, a slight backwave, 40 dB or more below the key-down signal, will be discernible only when the signal-to-noise ratio is quite high. Some operators listening in the shack to their own signals and hearing a

backwave think that the backwave can be heard on the air. It isn't necessarily so, and the best way to check is with an amateur a mile or so away. If he doesn't find the backwave objectionable on the S9+ signal, you can be sure that it won't be when the signal is weaker.

When any circuit carrying dc or ac is closed or opened, the small or large spark (depending upon the voltage and current) generates rf during the instant of make or break. This rf click covers a frequency range of many megahertz. When a transmitter is keyed, the spark at the key (and relay, if one is used) causes a click in the receiver. *This click has no effect on the transmitted signal.* Since it occurs at the same time that a click (if any) appears on

the transmitter output, it must be eliminated if one is to listen critically to his own signal within the shack. A small rf filter is required at the contacts of the key (and relay); typical circuits and values are shown in Fig. 2. To check the effectiveness of the rf filter, listen on a band lower in frequency than the one the transmitter is tuned to, with a short receiving antenna and the receiver gain backed off.

### What Transmitter Stage To Key

A satisfactory code signal, free from chirp and key clicks, can be amplified by a *linear* amplifier without affecting the keying characteristics in any way. If, however, the satisfactory signal is amplified by one or more nonlinear stages (e.g.,

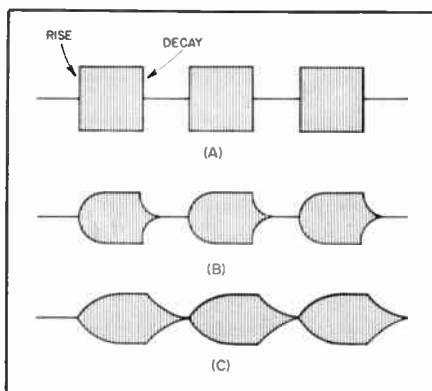


Fig. 1 — Typical oscilloscope displays of a code transmitter. The rectangular-shaped dots or dashes (A) have serious key clicks extending many kHz either side of the transmitter frequency. Using proper shaping circuits increases the rise and decay times to give signals with the envelope form of B. This signal would have practically no key clicks. Carrying the shaping process too far, as in C, results in a signal that is too "soft" and is not quite as easy to copy as B.

Oscilloscope displays of this type are obtained by coupling the transmitter rf to the vertical plates and using a slow sweep speed synchronized to the dot speed of an automatic key.

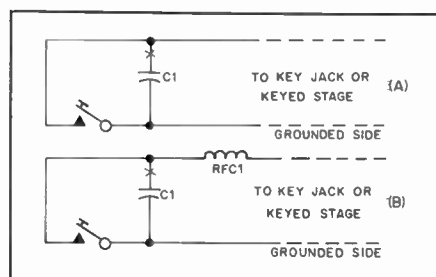


Fig. 2 — Typical filter circuits to apply at the key (and relay, if used) to minimize rf clicks. The simplest circuit (A) is a small capacitor mounted at the key. If this proves insufficient, an rf choke can be added to the ungrounded lead (B). The value of C1 is 0.001 to 0.01  $\mu\text{F}$ ; RFC1 can be 0.5 to 2.5 mH, with a current-carrying ability sufficient for the current in the keyed circuit. In difficult cases another small capacitor may be required on the other side of the rf choke. In all cases the rf filter should be mounted right at the key or relay terminals; sometimes the filter can be concealed under the key. When cathode or center-tap keying is used, the resistance of the rf choke or chokes will add cathode bias to the keyed stage, and in this case a high-current low-resistance choke may be required, or compensating reduction of the grid-leak bias (if it is used) may be needed. Shielded wire or coaxial cable makes a good keying lead.

A visible spark on "make" can often be reduced by the addition of a small (10- to 100-ohm) resistor in series with C1 (inserted at point "x"). Too high a value of resistance reduces the arc-suppressing effect on "break".

a Class C multiplier or amplifier), the signal envelope will be modified. The rise and decay times will be decreased, possibly introducing significant key clicks that were not present on the signal before amplification. It is possible to compensate for the effect by using longer-than-normal rise and decay times in the excitation and letting the amplifier(s) modify the signal to an acceptable one.

Many two-, three- and even four-stage

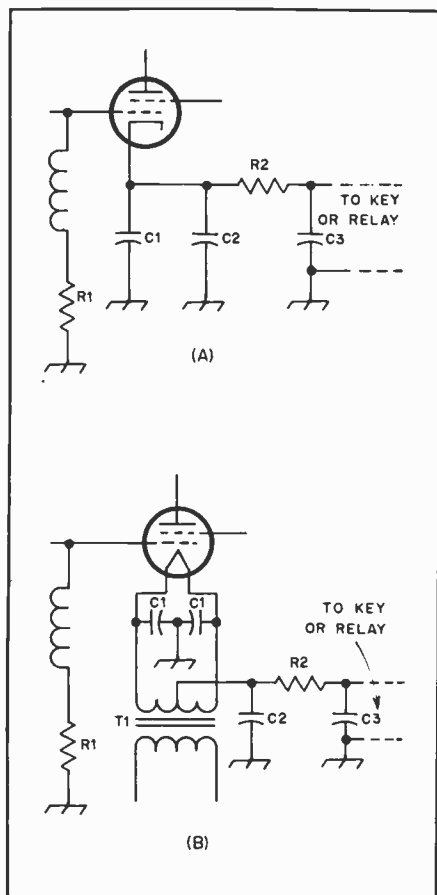


Fig. 3 — The basic cathode (A) and center-tap (B) keying circuits. In either case C1 is the rf return to ground, shunted by a larger capacitor, C2, for shaping. Voltage ratings at least equal to the cutoff voltage of the tube are required. T1 is the normal filament transformer. C1 and C3 can be about 0.01  $\mu$ F.

The shaping of the signal is controlled by the values of R2 and C2. Increased capacitance at C2 will make the signal softer on break; increased resistance at R2 will make the signal softer on make.

Values at C2 will range from 0.5 to 10  $\mu$ F, depending upon the tube type and operating conditions. The value of R2 will also vary with tube type and conditions, and may range from a few to 100 ohms. When tetrodes or pentodes are keyed in this manner, a smaller value can sometimes be used at C2 if the screen-voltage supply is fixed and not obtained from the plate supply through a dropping resistor. If the resistor decreases the output (by adding too much cathode bias) the value of R1 should be reduced.

Oscillators keyed in the cathode can't be softened on break indefinitely by increasing the value of C2 because the grid-circuit time constant enters into the action.

VFO-controlled transmitters are incapable of chirp-free output-amplifier keying because keying the output stage has an effect on the oscillator frequency and "pulls" it. Keying the amplifier presents a variable load to its driver stage, which in turn is felt as a variable load on the previous stage, and so on back to the oscillator. Chances of *pulling* are especially high when the oscillator is on the same frequency as the keyed output stage, but frequency multiplication is no guarantee against pulling. Another source of reaction is the variation in oscillator supply voltage under keying conditions, but this can usually be handled by stabilizing the oscillator supply with a VR tube. If the objective is a completely chirp-free transmitter, the first step is to make sure that keying the amplifier stage (or stages) has no effect on the frequency. This can be checked by listening on the oscillator frequency while the amplifier stage is keyed. Listen for chirp on either side of zero beat, to eliminate the possibility of a chirpy receiver (caused by line-voltage changes or BFO pulling).

An amplifier can be keyed by any method that reduces the output to zero. Neutralized stages can be keyed in the cathode circuit, although where powers over 50 or 75 watts are involved it is often desirable to use a keying relay or vacuum tube keyer, to minimize the chances for electrical shock. Tube keying drops the supply voltages and adds cathode bias, points to be considered where maximum output is required. Blocked-grid keying is applicable to many neutralized stages, but it presents problems in high-powered amplifiers and requires a source of negative voltage. Output stages which are not neutralized, such as many of the tetrodes and pentodes in widespread use, will usually leak a little and show some backwave regardless of how they are keyed. In a case like this it may be necessary to key two stages to eliminate backwave. They can be keyed in the cathodes with blocked-grid keying or in the screens. When screen keying is used, it is not always sufficient to reduce the screen voltage to zero; it may have to be taken to some negative value to bring the key-up plate current to zero, unless fixed negative control-grid bias is used. It should be apparent that where two stages are keyed, keying the earlier stage must have no effect on the oscillator frequency if completely chirp-free output is the goal.

Shaping of the keying is obtained in several ways. Vacuum-tube keyers, blocked-grid and cathode-keyed systems get suitable shaping with proper choice of resistor and capacitor values, while screen-grid keying can be shaped by using inductors or resistors and capacitors. Sample circuits are shown in Figs. 3, 4 and 5, together with instructions for their adjustment. There is no "best" adjustment, since this is a matter of personal

preference and what you want your signal to sound like. Most operators seem to like the make to be heavier than the break. All of the circuits shown here are capable of a wide range of adjustment.

If the negative supply in a grid-block keyed stage fails, the tube will draw excessive key-up current. To protect against tube damage in this eventuality, an overload relay can be used or, more simply, a fast-acting fuse can be included in the cathode circuit.

### Oscillator Keying

One may wonder why oscillator keying has not been mentioned earlier, since it is widely used. A sad fact of life is that excellent oscillator keying is infinitely more difficult to obtain than is excellent amplifier keying. If the objective is no detectable chirp, it is probably *impossible* to obtain with oscillator keying, particularly on the higher frequencies. The reasons are simple: Any keyed-oscillator transmitter requires shaping at the oscillator, which

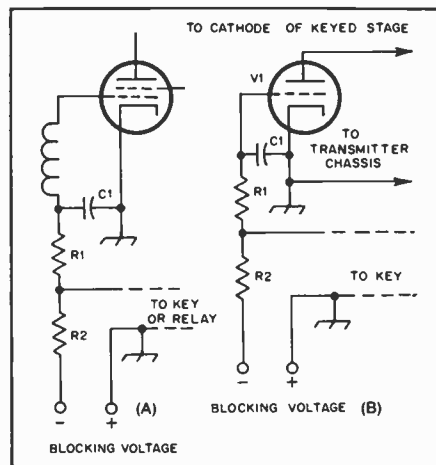


Fig. 4 — The basic circuit for blocked-grid keying is shown at A. R1 is the normal grid leak, and the blocking voltage must be at least several times the normal grid bias. The click on make can be reduced by making C1 larger, and the click on break can be reduced by making R2 larger. Usually the value of R2 will be 5 to 20 times the resistance of R1. The power supply current requirement depends upon the value of R2, since closing the key circuit places R2 across the blocking voltage supply.

An allied circuit is the vacuum-tube keyer of B. The tube V1 is connected in the cathode circuit of the stage to be keyed. The values of C1, R1 and R2 determine the keying envelope in the same way that they do for blocked-grid keying. Values to start with might be 0.47 M $\Omega$  for R1, 4.7 M $\Omega$  for R2 and 0.0047  $\mu$ F for C1.

The blocking voltage supply must deliver several hundred volts, but the current drain is very low. A 6Y6 or other low plate-resistance tube is suitable for V1. To increase the current-carrying ability of a tube keyer, several tubes can be connected in parallel.

A vacuum-tube keyer adds cathode bias and drops the supply voltages to the keyed stage and will reduce the output of the stage. In oscillator keying it may be impossible to use a VT keyer without changing the oscillator dc grid return from ground to cathode.



involves changing the operating conditions of the oscillator over a significant period of time. The output of the oscillator does not rise to full value immediately, so the drive on the following stage is changing, which in turn may reflect a variable load on the oscillator. No oscillator has been devised that has no change in frequency over its entire operating voltage range and with a changing load. Furthermore, the shaping of the keyed-oscillator envelope usually has to be exaggerated, because the following stages will tend to sharpen up the keying and introduce clicks unless they are operated as linear amplifiers.

### Break-in Keying

The usual argument for oscillator keying is that it permits break-in operation. If break-in operation is not contemplated and as near-perfect keying as possible is the objective, then keying an amplifier or two by the methods outlined earlier is the solution. For operating convenience, an automatic transmitter "turner-onner" (see Campbell, August 1956 *QST*), which will turn on the power supplies and switch antenna relays and receiver muting devices, can be used. The station switches over to the complete "transmit" condition when the first dot is sent, and it holds for a length of time dependent upon the setting of the delay. It is equivalent to voice-operated phone of the type commonly used by ssb stations. It does not permit hearing the other station whenever the key is up, as does full break-in.

Full break-in with excellent keying is not easy to come by, but it is easier than many amateurs think. Many use oscillator keying and put up with a second-best signal.

### Differential Keying

The principle behind "differential" keying is to turn the oscillator on fast before a keyed amplifier stage can pass any signal and turn off the oscillator fast after the keyed amplifier stage has cut off. A number of circuits have been devised for accomplishing the action. The simplest, which should be applied *only* to a transmitter using a voltage-stable (crystal-controlled) oscillator is shown in Fig. 6. Many "simple" and kitted Novice transmitters can be modified to use this system, which approaches the performance of the "turner-onner" mentioned above insofar as the transmitter performance is concerned. With separate transmitting and receiving antennas, the performance is comparable.

A simple differential-keying circuit that can be applied to any grid-block keyed amplifier or tube-keyed stage by the addition of a triode and a VR tube is shown in Fig. 7. Using this keying system for break-in, the keying will be chirp-free if it is chirp-free with the VR tube

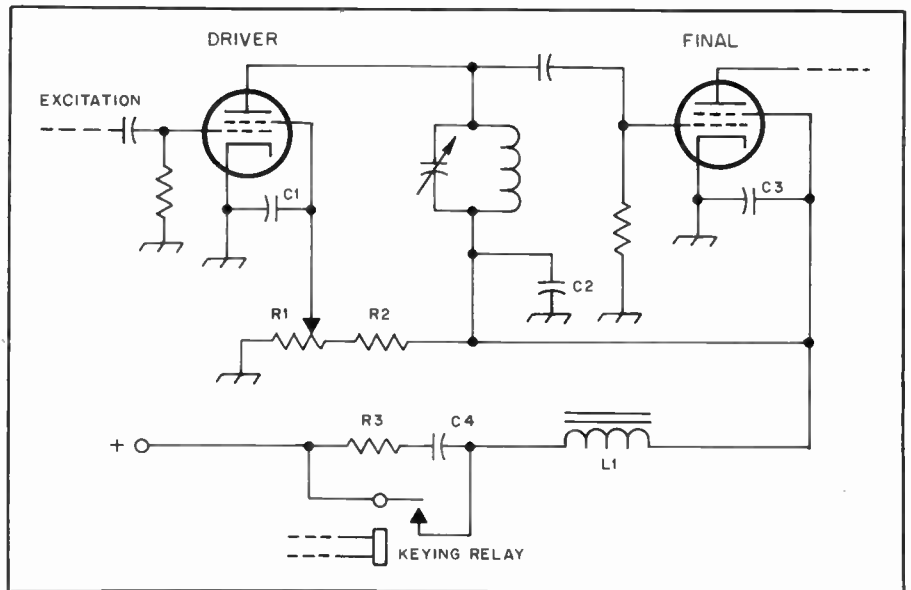


Fig. 5 — When the driver-stage plate voltage is roughly the same as the screen voltage of a tetrode final amplifier, combined screen and driver keying is an excellent system. The envelope shaping is determined by the values of L1, C4 and R3, although *rf* bypass capacitors C1, C2 and C3 also have a slight effect. R1 serves as an excitation control for the final amplifier by controlling the screen voltage of the driver stage. If a triode driver is used, its plate voltage can be varied for excitation control.

The inductor L1 will not be too critical, and the secondary of a spare filament transformer can be used if a low-inductance choke is not available. The values of C4 and R3 will depend upon the inductance and the voltage and current levels, but good starting values are 0.1  $\mu$ F and 50 ohms.

To minimize the possibility of electrical shock, it is recommended that a keying relay be used in this circuit, since both sides of the circuit are "hot." As in any transmitter, the signal will be chirp-free only if keying the driver stage has no effect on the oscillator frequency. (The Sigma 41FZ-35-ACS-SIL 6-volt ac relay is well-suited for keying applications.)

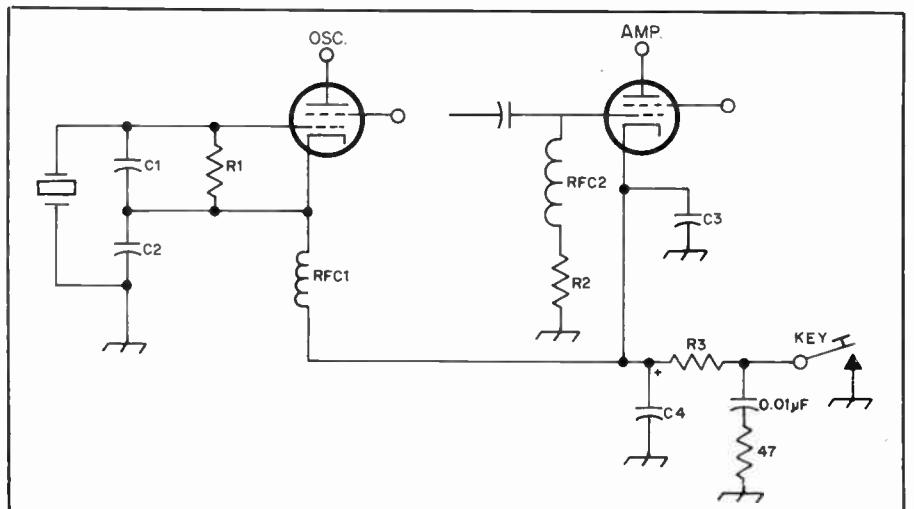


Fig. 6 — Simple differential-keying circuit for a crystal-controlled oscillator and power-amplifier transmitter.

Most simple crystal-controlled transmitters, commercial or homebuilt, return the oscillator grid-leak resistor, R1, to chassis, and "cathode keying" is used on the oscillator and amplifier stages. By returning the oscillator grid leak to the cathode, as shown here, negative power-supply-lead keying is used on the oscillator. A good crystal oscillator will operate with only 5 to 10 volts applied to it.

Using the above circuit, the signal is controlled by the shaping circuit, C4-R3. Increasing the value of R3 will make the signal "softer" on make; increasing the capacitance of C4 will make the signal softer on make and break. The oscillator will continue to operate after the amplifier has cut off, until the charge in C4 falls below the minimum operating voltage for the oscillator.

The 0.01- $\mu$ F capacitor and 47-ohm resistor reduce the spark at the key contacts and minimize "key clicks" heard in the receiver and other nearby receivers. They do not control the key clicks associated with the signal miles away; these clicks are reduced by increasing the values of R3 and C4.

Since the oscillator may hold in between dits and dahs, a back wave may be present if the amplifier stage is not neutralized.

C1, C2 — Normal oscillator capacitors.

C3 — Amplifier *rf* cathode bypass capacitor.

C4 — Shaping capacitor, typically 1 to 10  $\mu$ F, 250

V, electrolytic.

R1 — Oscillator grid leak; return to cathode

instead of chassis ground.

R2 — Normal amplifier grid leak; no change.

R3 — Typically 47 to 100 ohms.

RFC1, RFC2 — As in transmitter, no change.

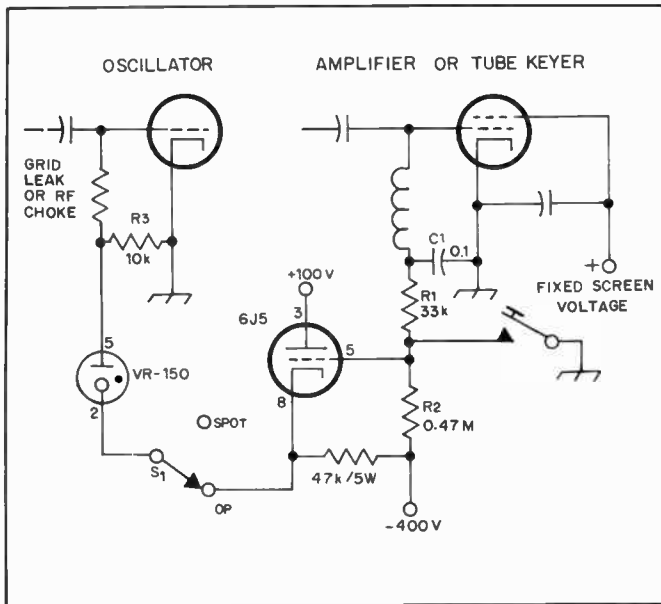


Fig. 7 — When satisfactory blocked-grid or tube keying of an amplifier stage has been obtained, this VR-tube break-in circuit can be applied to the transmitter to furnish differential keying. The constants shown here are suitable for blocked-grid keying of a 6146 amplifier; with a tube keyer the 6J5 and VR tube circuitry would be the same.

With the key up, sufficient current flows through R3 to give a voltage that will cut off the oscillator tube. When the key is closed, the cathode voltage of the 6J5 becomes close to ground potential, extinguishing the VR tube and permitting the oscillator to operate. Too much shunt capacity on the leads to the VR tube and too large a value of grid capacitance in the oscillator may slow down this action, and best performance will be obtained when the oscillator (turned on and off this way) sounds "clicky." The output envelope shaping is obtained in the amplifier, and it can be made softer by increasing the value of C1. If the keyed amplifier is a tetrode or pentode, the screen voltage should be obtained from a fixed voltage source or stiff voltage divider, not from the plate supply through a dropping resistor.

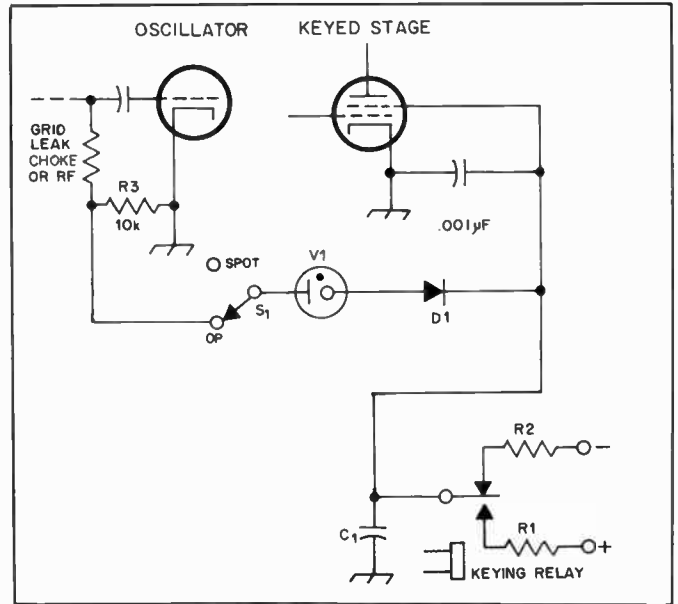


Fig. 8 — VR-tube differential keying in an amplifier screen circuit.

With key up and current flowing through V1 and D1, the oscillator is cut off by the drop through R3. The keyed stage draws no current because its screen grid is negative. C1 is charged negatively to the value of the — source. When the relay is energized, C1 charges through R1 to a positive value. Before reaching zero (on its way positive) there is insufficient voltage to maintain ionization in V1, and the current is broken in R3, turning on the oscillator stage. As the screen voltage goes positive, the VR tube cannot reignite because the diode, D1, will not conduct in that direction. The oscillator and keyed stage remain on as long as the relay is closed. When the relay opens, the voltage across C1 must be sufficiently negative for V1 to ionize before any bleeder current will pass through R3. By this time the screen of the keyed stage is so far negative that the tube has stopped conducting. (See Fig. 5 for suitable relay.)

removed from its socket to permit the oscillator to run all of the time. If the transmitter can't pass this test, it indicates that more isolation is required between keyed stage and oscillator.

Another VR-tube differential-keying circuit, useful when the screen-grid circuit of an amplifier is keyed, is shown in Fig. 8. The normal screen keying circuit is made up of the shaping capacitor C1, the keying relay (to remove dangerous voltages from the key), and the resistors R1 and R2. The + supply should be 50 to 100 volts higher than the normal screen voltage, and the — voltage should be sufficient to ignite the VR tube, V1, through the drop in R2 and R3. Current through R2 will be determined by the voltage required to cut off the oscillator; if 10 volts will do it the current will be 1 mA. For a desirable keying characteristic, R2 will usually have a higher value than R1. Increasing the value of C1 will soften both "make" and "break".

The tube used at V1 will depend upon the available negative supply voltage. If it is between 120 and 150, a 0A3/VR75 is recommended. Above this a 0C3/VR105 can be used. The diode, D1, can be any unit operated within its ratings. A type 1N4005, for example, may be used with

screen voltages under 600 and with far greater bleeder currents than are normally encountered — up to 1 ampere.

#### Clicks in Later Stages

It was mentioned earlier that key clicks can be generated in amplifier stages following the keyed stage or stages. This can be a puzzling problem to an operator who has spent considerable time adjusting the keying in his exciter unit for clickless keying, only to find that the clicks are bad when the amplifier unit is added. There are two possible causes for the clicks; low-frequency parasitic oscillations and amplifier "clipping."

Under some conditions an amplifier will be momentarily triggered into low-frequency parasitic oscillations, and clicks will be generated when the amplifier is driven by a keyed exciter. If these clicks are the result of low-frequency parasitic oscillations, they will be found in "groups" of clicks occurring at 50- to 150-kHz intervals either side of the transmitter frequency. Of course low-frequency parasitic oscillations can be generated in a keyed stage, and the operator should listen carefully to make sure that the output of the exciter is clean before he

blames a later amplifier. Low-frequency parasitic oscillations are usually caused by poor choice in rf choke values, and the use of more inductance in the plate choke than in the grid choke for the same stage is recommended.

When the clicks introduced by the addition of an amplifier stage are found only near the transmitter frequency, amplifier "clipping" is indicated. It is quite common when fixed bias is used on the amplifier and the bias is well past the "cut-off" value. The effect can usually be minimized by using a combination of fixed and grid-leak bias for the amplifier stage. The fixed bias should be sufficient to hold the key-up plate current only to a low level and not to zero.

A linear amplifier (Class AB1, AB2 or B) will amplify the excitation without adding any clicks, and if clicks show up a low-frequency parasitic oscillation is probably the reason.

#### Keying Speeds

In radiotelegraphy the basic code element is the dot, or unit pulse. The time duration of a dot and a space together is that of two unit pulses. A dash is three unit pulses long. The space between letters is three unit pulses long. The space between

letters is three unit pulses; the space between words or groups is seven unit pulses. A speed of one *baud* is one pulse per second.

Assuming that a speed key is adjusted to give the proper dot, space and dash values mentioned above, the code speed can be found from

$$\text{Speed (wpm)} = \frac{\text{dots/min.}}{2.5} = 2.4 \times \text{dots/sec.}$$

For example, a properly adjusted electronic key gives a string of dots which are counted at 10 dots per second. Speed =  $2.4 \times 10 = 24$  wpm.

Many modern electronic keyers use a clock or pulse-generator circuit which feeds a flip-flop dot generator. For these keyers the code speed may be determined directly from the clock frequency

$$\text{Speed (wpm)} = 1.2 \times \text{clock frequency (Hz)}$$

For a quick and simple means of determining the code speed, send a continuous string of dashes and count the number of dashes which occur in a five second period. This number, to a close approximation, is the code speed in words per minute.

### Break-In Operation

Smooth cw break-in operation involves protecting the receiver from permanent damage by the transmitter power and assuring that the receiver will "recover" fast enough to be sensitive between dots and dashes, or at least between letters and words.

### Separate Antennas

Few of the available antenna transfer relays are fast enough to follow keying, so the simplest break-in system is the use of a separate receiving antenna. If the transmitter power is low (25 or 50 watts) and the isolation between transmitting and receiving antennas is good, this method can be satisfactory. Best isolation is obtained by mounting the antennas as far apart as possible and at right angles to each other. Feed-line pickup should be minimized, through the use of coaxial cable or 300-ohm twin-lead. If the receiver recovers fast enough but the transmitter clicks are bothersome (they may be caused by the receiver overload and so exist only in the receiver) their effect on the operator can be minimized through the use of input and output limiters.

### Electronic Transmit-Receive Switches

When powers above 25 or 50 watts are used, where two antennas are not available, or when it is desired to use the same antenna for transmitting and receiving (a "must" when directional antennas are used), special treatment is required for quiet break-in operation on the transmitter frequency. A means must be provided for limiting the power that reaches the

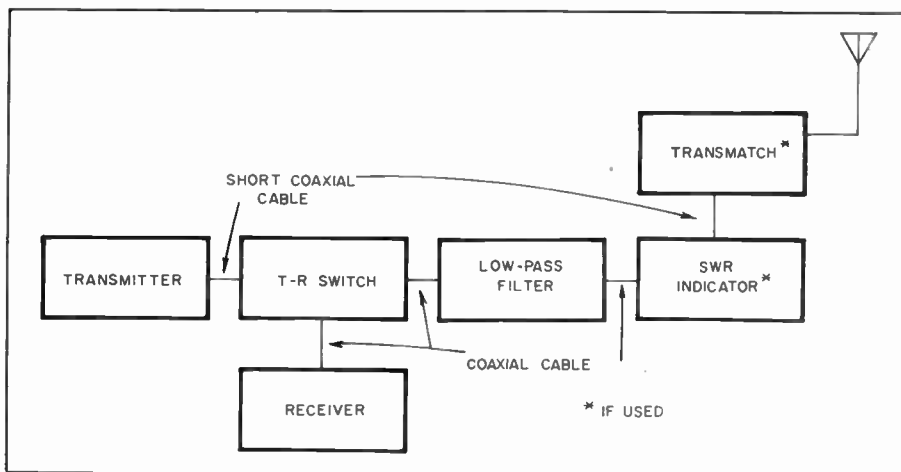


Fig. 9 — Proper method of interconnecting T-R switch with various other station accessory equipment.

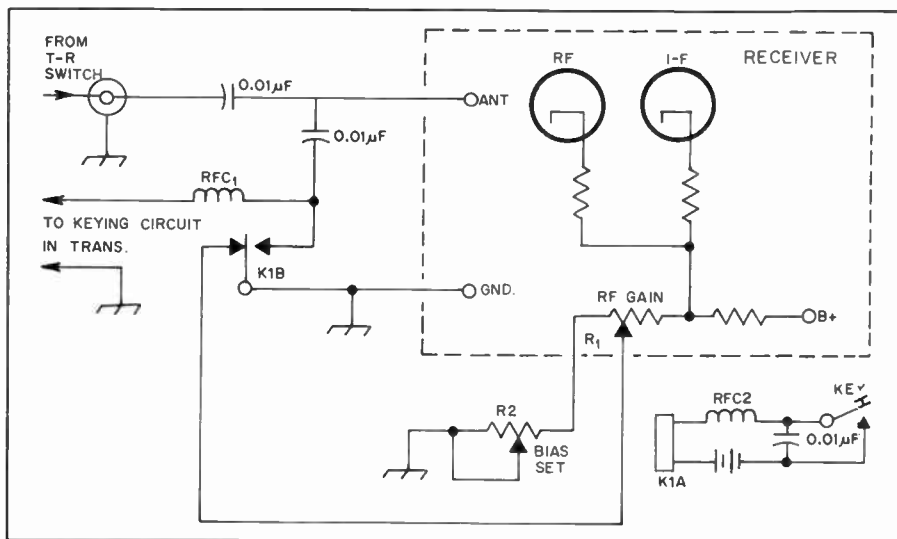


Fig. 10 — Circuit for smooth break-in operation, using an electronic T-R switch. The leads shown as heavy lines should be kept as short as possible, to minimize direct transmitter pickup.

K1 — Spdt keying relay, Sigma 41FZ-10000-ACS-SIL or equiv. Although battery and dc relay are shown, any suitable ac or dc relay and power source can be used.

R1 — Receiver manual gain control.

R2 — 5000- or 10,000-ohm wire-wound potentiometer.  
RFC1, RFC2 — 1- to 2-1/2-mH rf choke, current rating adequate for application.

receiver input. This can be either a direct short-circuit, or may be a limiting device like an electronic switch used in the antenna feed line. The word "switch" is a misnomer in this case; the transmitter is connected directly to the antenna at all times. The receiver is connected to the antenna through the T-R switch, which functions to protect the receiver's input from transmitted power. In such a setup, all the operator need do is key the transmitter, and all the switching functions are taken care of by the T-R switch.


With the use of a T-R switch some steps should be taken to prevent receiver blocking. Turn off the agc or avc, decrease the rf gain setting, and advance the audio gain control. Use the rf gain control for obtaining the desired listening level. A little experimenting with the controls will provide the receiver settings best suited to individual operating preferences. A range

of settings can usually be found, just on the threshold of receiver blocking, where comfortable levels of received signals are heard, and where, without adjusting the controls, the receiver can be used as a monitor during transmission. Usually, no modification to the receiver is required, but if annoying clicks and thumps or excess volume occur at all settings of the receiver controls during transmission, their effect can be reduced with output audio limiting.

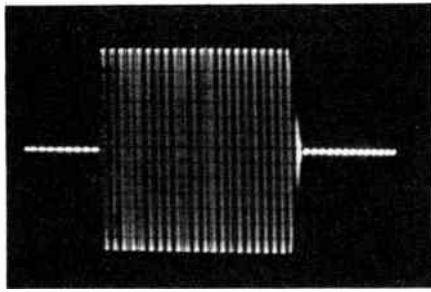
### TVI and T-R Switches

T-R switches generate harmonics of the transmitted signal because of rectification of the energy reaching the switch input. These harmonics can cause TVI if steps are not taken to prevent it. Any T-R switch should be very well shielded, and should be connected with as short as possible cable length to the transmitter.







(A)

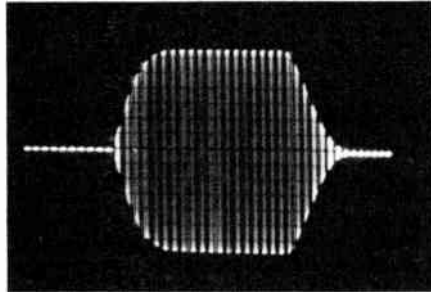

(B)

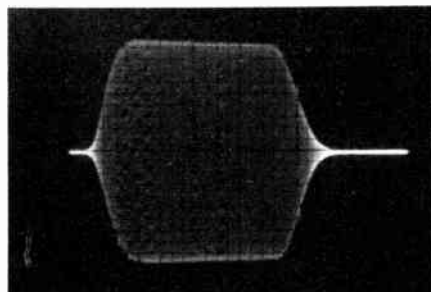

(C)

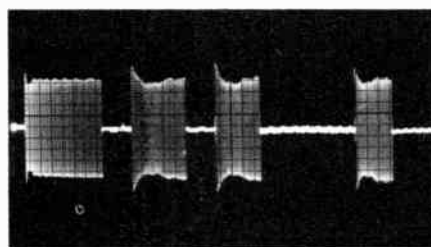

(D)

Fig. 11 — These photos show cw signals as observed on an oscilloscope. At A is a dot generated at a 46-baud rate with no intentional shaping, while at B the shaping circuits have been adjusted for approximately 5-ms rise and decay times. Vertical lines are from a 1-kHz signal applied to the Z or intensity axis for timing. Shown at C is a shaped signal with the intensity modulation of the pattern removed. For each of these photos, sampled rf from the transmitter was fed directly to the deflection plates of the oscilloscope.

A received signal having essentially no shaping is shown at D. The spike at the leading edge is typical of poor power-supply regulation, as is also the immediate y following dip and rise in amplitude. The clicks were quite pronounced. This pattern is typical of many observed signals, although not by any means a worst case. The signal was taken from the receiver's i-f amplifier (before detection) using a hand-operated sweep circuit to reduce the sweep time to the order of one second. (Photos from October and November 1966 QST.)

In addition, a low-pass filter may be required in the transmission line between the T-R switch and the antenna. Fig. 9 shows the proper method of interconnecting the various station accessory equipment.

### Reduction of Receiver Gain During Transmission

For absolutely smooth break-in operation with no clicks or thumps, means must be provided for momentarily reducing the gain through the receiver. The system shown in Fig. 10 permits quiet break-in operation of high-powered stations. It may require a simple operation on the receiver, although many commercial receivers already provide the connection and require no internal modification. The circuit is for use with a T-R switch and a single antenna. R1 is the regular receiver rf and i-f gain control. The ground lead is run to chassis ground through R2. A wire from the junction ground runs to the keying relay, K1. When the key is up, the ground side of R1 is connected to ground through the relay arm, and the receiver is in its normal operating condition. When the key is closed the relay closes, which breaks the ground connection from R1 and applies additional bias to the tubes in the receiver. This bias is controlled by R2. When the relay closes, it also closes the circuit to the transmitter keying circuit. A simple rf filter at the key suppresses the local clicks caused by the relay current. This circuit is superior to any working on the agc line of the receiver because the cathode circuit(s) have shorter time constants than the agc circuits and will recover faster. A similar circuit may be used in the emitters or source leads of transistorized receivers.

### Testing and Monitoring of Keying

In general, there are two common methods for monitoring one's "fist" and signal. The first type involves the use of an audio oscillator that is keyed simultaneously with the transmitter.

The second method is one that permits receiving the signal through one's receiver, and this generally requires that the receiver be tuned to the transmitter (not always convenient unless working on the same frequency) and that some method be provided for preventing overloading of the receiver, so that a good replica of the transmitted signal will be received. Except where quite low power is used, this usually involves a relay for simultaneously shorting the receiver input terminals and reducing the receiver gain.

An alternative is to use an rf-powered audio oscillator. This follows the keying very closely (but tells nothing about the quality — chirps or clicks — of the signal).

The easiest way to find out what your keyed signal sounds like on the air is to trade stations with a near-by ham friend some evening for a short QSO. If he is a

half mile or so away, that's fine, but any distance where the signals are still S9 will be satisfactory.

After you have found out how to work his rig, make contact and then have him send slow dahs, with long spacing (the letter "T" at about 5 wpm). With minimum selectivity, cut the rf gain back just enough to avoid receiver overloading (the condition where you get crisp signals instead of mushy ones) and tune slowly from out of beat-note range on one side of the signal through to zero and out the other side. Knowing the tempo of the dashes, you can readily identify any clicks in the vicinity as yours or someone else's. A good signal will have a thump on "make" that is perceptible only where you can also hear the beat note, and the click on "break" should be practically negligible at any point. If your signal is like that, it will sound good, provided there are no chirps. Then have your friend run off a string of fast dits with the bug — if they are easy to copy, your signal has no "tails" worth worrying about and is a good one for any speed up to the limit of manual keying. Make one check with the selectivity in, to see that the clicks off the signal frequency are negligible even at high signal level.

If you don't have any friends with whom to trade stations, you can still check your keying, although you have to be a little more careful. The transmitter output should be fed into a shielded dummy load. Ordinary incandescent lamps are unsatisfactory as lamp resistance varies too much with current. The thermal lag may cause the results to be misleading.

The first step is to get rid of the rf click at the key. This requires an rf filter (mentioned earlier). With no clicks from a spark at the key, disconnect the antenna terminals with a short piece of wire. Tune in your own signal and reduce the rf gain to the point where your receiver doesn't overload. Detune any antenna trimmer the receiver may have. If you can't avoid overload with the rf gain-control range, pull out the rf amplifier tube and try again. If you still can't avoid overload, listen to the second harmonic as a last resort. An overloaded receiver can generate clicks.

Describing the volume level at which you should set your receiver for these "shack" tests is a little difficult. The rf filter should be effective with the receiver running wide open and with an antenna connected. When you turn on the transmitter and take the steps mentioned to reduce the signal in the receiver, run the audio up and the rf down to the point where you can just hear a little "rushing" sound with the BFO off and the receiver tuned to the signal. This is with the selectivity in. At this level, a properly adjusted keying circuit will show no clicks off the rushing-sound range. With the



BFO on and the same gain setting, there should be no clicks outside the beat-note range. When observing clicks, make the slow-dah and dit tests outlined previously.

Now you know how your signal sounds on the air, with one possible exception. If keying your transmitter makes the lights blink, you may not be able to tell too accurately about the chirp on your signal. However, if you are satisfied with the absence of chirp when tuning *either side of zero beat*, it is safe to assume that your receiver isn't chirping with the light flicker and that the observed signal is a true representation. No chirp either side of zero beat is fine. Don't try to make these tests without first getting rid of the rf click at the key, because clicks can mask a chirp.

The least satisfactory way to check your keying is to ask another ham on the air how your keying sounds. It is the least satisfactory because most hams are reluctant to be highly critical of another amateur's signal. In a great many cases they don't actually know what to look for or how to describe any aberrations they may observe.

#### A Memory for the Deluxe Keyer

The system described here permits storage of up to 200 letters of text organized in one, two, three or four messages. A digital display provides an indication of the message being sent or loaded (no. 1, 2, 3 or 4) and the message bit being addressed (0 to 512). Any number of pauses may be programmed into a message to allow manual insertion of changeable text (such as RST or contest serial number). After manual insertion a touch of the RUN button allows the remainder of the programmed message to continue. The message being sent may be aborted by pressing the STOP button (the "I didn't mean to press the button!" button). Unlike some programmable keyers, the use of a free-running (asynchronous) clock in the load mode has been avoided, greatly simplifying the loading process. All features of the original Accu-Keyer have been retained. The dit and dah memories of the Accu-Keyer and its automatic character-space feature are used to good advantage in the Accu-Memory.

In addition to the Accu-Keyer board, three printed-circuit boards make up the Accu-Memory: a memory board, a display board, and a display-driver board. The power supply provides 5 volts at 0.8 ampere to power all the circuitry.

The Accu-Memory has been "battle tested" in contests and has been found to be very effective in reducing operator fatigue. It is of use whenever there is a requirement for repeatedly sending the same cw sequences, such as in contests, DX pileups, and net-control operations. Experience has shown that the digital

displays are far more useful than originally anticipated.

#### Construction

As shown in Fig. 12, the Accu-Memory is constructed in an aluminum box made by cutting and bending sheet aluminum. The front-panel dimensions are deliberately made small because depth in most ham shacks is more abundant than frontal-area space. This method also gives a neat, streamlined appearance. The overall outside dimensions are 4-1/4 × 3-1/2 × 10-1/2 inches (108 × 89 × 267 mm), with the length dimension measured across the bottom plate, less knobs and heat sink. The heat sink for the LM309 is attached to the rear panel, along with the key jack, the output jack, and a fuse holder (*safety first!*). Power supply components are located on the bottom plate near the rear. Two terminal strips are used to mount the power supply diodes and filter capacitor. All the other electronic parts are mounted on four printed-circuit cards.

One word of caution: Do not increase the filter capacitor value in the power supply. It has been chosen for minimum dissipation by the LM309 regulator.

Fig. 13 is a schematic diagram of the circuitry on the driver and display board. Wires that interconnect the boards are shown as numbers or lower case letters in triangles on the figures. Selectable jump-

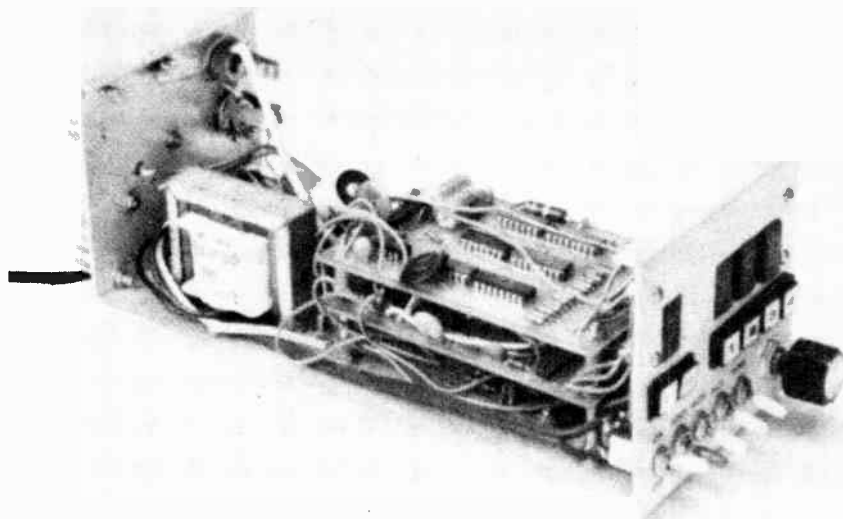


Fig. 12 — A look at the inside of the Accu-Memory. The power supply components are shown at the left, and the three "stacked" circuit boards to their right. The fourth circuit board, containing the readout, is mounted behind the sloping portion of the front panel. The board at the bottom of the "stack" is that of the original Accu-Keyer.

ers allow the use of one or two RAM ICs. The jumper points are shown as capital letters in circles. Table 1 is a list of interconnecting wires. Table 2 gives a parts list for each board. Fig. 15 is a diagram of the power supply.

To send, place the LOAD/SEND switch in the SEND position and press the proper message button. The STOP button will halt sending, but the message can be continued from the halted point if the RUN button is depressed.

If it is desired to use the insert feature, load the first part of the message as described above. Then after the memory stops advancing, press the RUN button once, wait until the count stops, and then load the second half of the message. In the SEND mode the memory will send the first part, stop and allow insertion of manual input such as signal reports, and then, when the RUN button is depressed, continue with the second half. This procedure may be repeated as many times as necessary.

The readout indicates the message number and the location within the message starting at 000 and continuing through either 256 or 512, depending on whether one or two memories are installed. A decimal point lights when the keyer is sending either manually or automatically.

#### Helpful Advice

After a lot of correspondence with amateurs who built the Accu-Keyer, it is apparent that some do not know that there is a difference between a 7400, a 74H00, a 74L00 and a 74C00. These are all members of a family of quad two-input gates that are different internally and are

<sup>1</sup>The heat sink for the LM-309 is available from D. J. Manson, Ph.D., KØTVO, Alpha Electronic Laboratories, 2302 Oakland Gravel Road, Columbia, MO 65201, 314-449-1362.

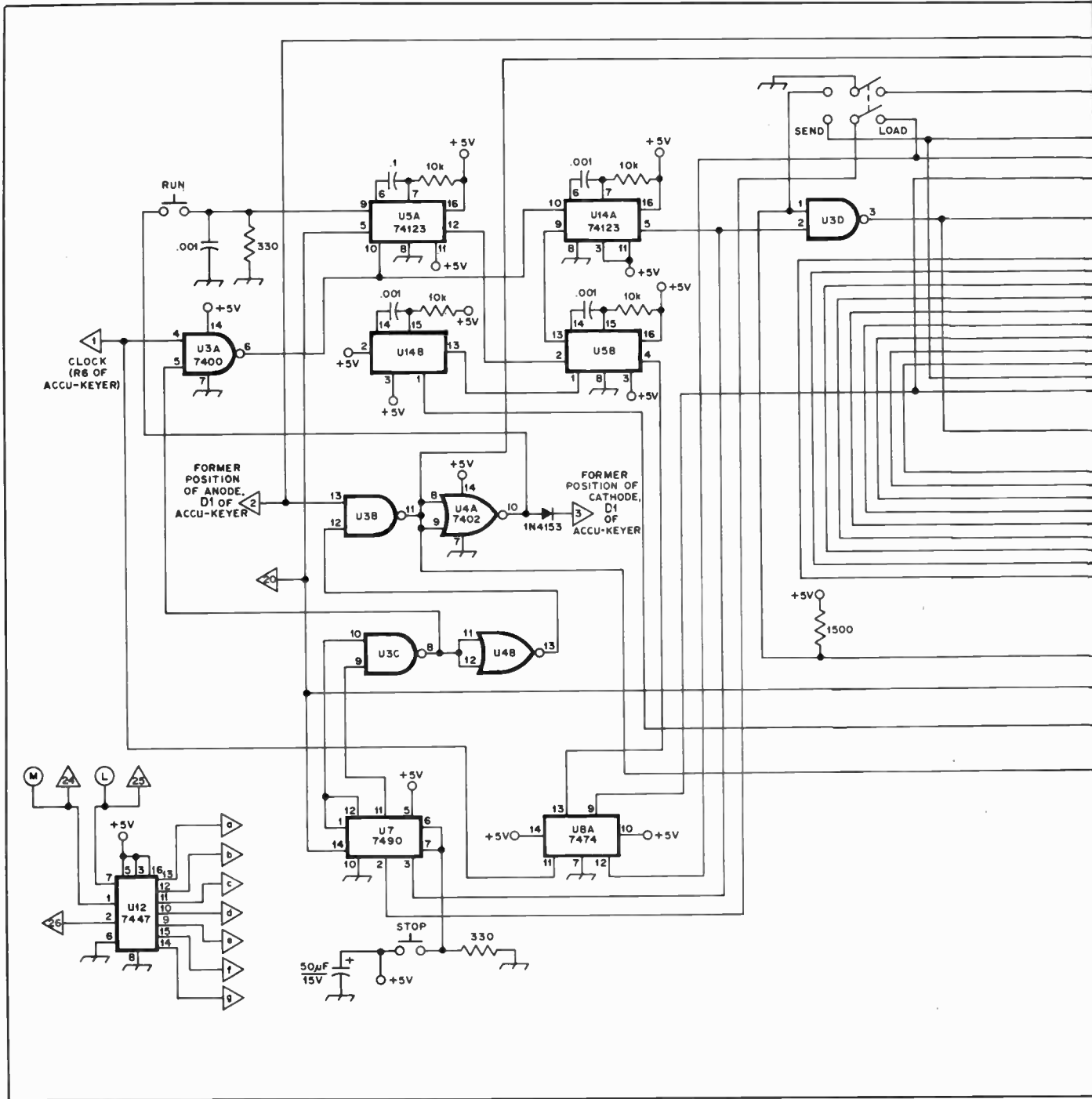


Fig. 13 — Diagram of memory circuitry of the Accu-Memory. See Table 2 for list of parts. Numbers and letters in triangles identify inter-connections to other parts of the Accu-Memory, as listed in Table 1. Letters in circles indicate terminals for jumpers to be wired for either one or two RAM ICs. This wiring information is also listed in Table 1.

not interchangeable (in almost all cases). Some IC distributors tend to be haphazard about which type they send.

As with the Accu-Keyer, ready-made boards are available for the memory through Garrett.<sup>2</sup> A business-size self-

addressed stamped envelope is mandatory to reduce addressing time to a minimum. If any problems develop or changes occur in the circuit, a data sheet showing corrections will be included with the boards.

#### Deluxe All-Solid-State Keyer

The Accu-Keyer is a modern keying device with deluxe features available on only the most expensive of commercially available instruments, but it may be built for less than \$25.


The basic circuit uses seven TTL

integrated circuits which may be purchased from "bargain" suppliers for less than \$3. Optional features which may be incorporated at the builder's discretion are a stiffly regulated power supply, a keying monitor, and provisions for solid-state keying of cathode-keyed transmitters.

The Accu-Keyer was designed with these features in mind:

- 1) Self-completing dits and dahs
- 2) Dit and dah memories
- 3) Iambic operation
- 4) Dit and dah insertion

<sup>2</sup>As a service to those who wish to avail themselves, ready-made circuit boards may be obtained through James Garrett, WB4VVF, 126 W. Buchanan Ave., Orlando, FL 32809. All boards are glass epoxy and drilled. At the time of this printing, the Accu-Keyer board is \$3.50. The memory, readout and readout-driver boards are \$12 as a set. The memory board, if ordered alone, is \$6.

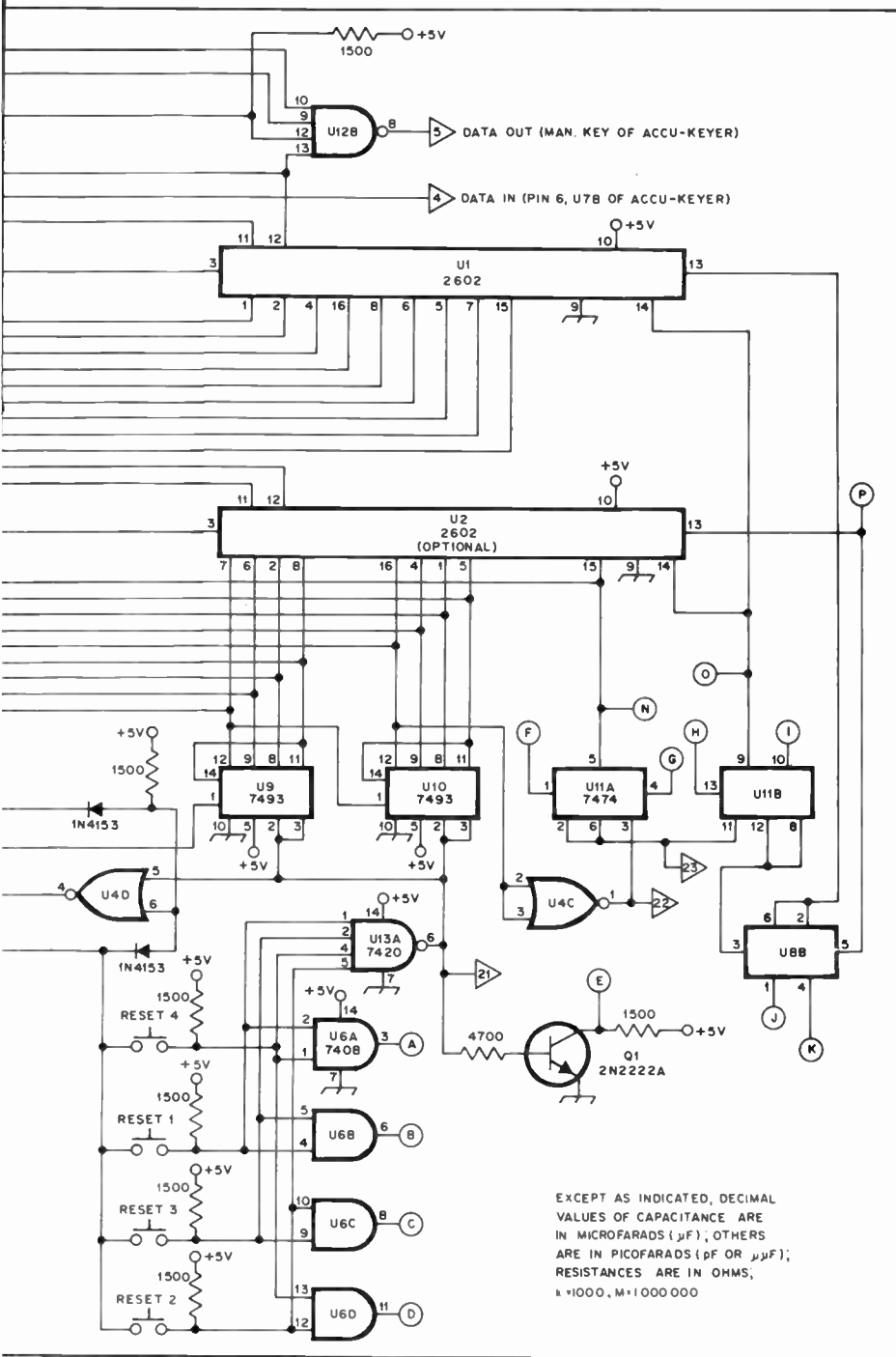

**Table 1 — Interconnections**

Wire Number	Function
<i>Keyer-to-memory interconnections</i>	
1	Clock — connect to R6
2	Anode D1
3	Cathode D1 (Remove D1 in keyer and connect as shown.)
4	Data in (Connect to U7B in keyer and tone oscillator on driver board.)
5	Data out (Connect to manual key input, U7 pin 5 in keyer.)
<i>Memory-to-control switches</i>	
6	Send 1
7	Send 2
8	Load 1
9	Load 2
10	Common 1
11	Common 2
<i>Memory to readout</i>	
12	Insert
13	Insert return
14	Reset 1
15	Reset 2
16	Reset 3
17	Reset 4
Dpdt switch	
Push buttons	
18	Reset common
19	Stop
a,b,c,d,e,f,g	Quadrant readout
<i>Memory to driver</i>	
20	Readout count
21	Readout reset
22	Readout quadrant reset (use with one 2601)
23	Readout quadrant reset (use with two 2602s)
24	NOR 1
25	NOR 2
26	NOR out
<i>Driver to readout</i>	
27-33 (a-g, LSB)	Least-significant digit
34-40 (a-g, CSB)	Center-significant digit
41-47 (a-g, MSB)	Most-significant digit
48-49	Pitch control (snort if no control desired)
50	Speaker
<i>Memory interconnections</i>	
For one memory IC connect: A to H, B to G, C to I, D to F, J to ground, K to +5V, L to N, and M to O.	
For two memory ICs connect: A to J, B to I, C to K, D to H, E to F, G to +5V, L to O, and M to P.	

Connect DP (decimal point) on readout board to wire 13.

- 5) Automatic character space (with switching provided to defeat this feature)
- 6) 5-50 wpm speed range
- 7) Low cost

### The Circuit

The schematic diagram of the Accu-Keyer is shown in Fig. 17. The voltage applied to D2 for powering the keyer may be either 8 to 10 volts dc or 6.3 volts ac, such as from the filament supply of a transmitter or receiver. If dc is applied, C6 is not required. If ac is applied to D2, D3 functions more to protect the ICs from

overvoltage by limiting the amplitude of the ripple than it does for voltage regulation. If a well-filtered and regulated supply is desired, the circuit of Fig. 18A may be used in place of D2, R13, and D3 and associated capacitors. Constructed with the components shown, that supply will handle the keyer requirements with power to spare.

Should a keying monitor be desired, the diagram of Fig. 18B may be used to construct a circuit which will afford plenty of volume and a stable, pleasing tone. Equipped with such a monitor, the

Accu-Keyer becomes ideal for conducting code practice sessions for small and medium-sized groups.

Fig. 18C shows a circuit which may be used for cathode-keyed or solid-state "QRP" transmitters. The Delco ampere transistor will safely handle two amperes of current and a collector-to-emitter potential of 800 V, and yet its cost is less than that of a new mercury-wetted relay. The use of a transistor offers advantages over both vacuum-tube keying and relay keying of cathode-keyed rigs; the voltage drop across the transistor when saturated

**Table 2 — Accu-Memory Parts List**

2	7474 ICs	U8, U11
2	7493 ICs	U9, U10
1	7408 IC	U6
2	74123 ICs	U5, U14
1	7400 IC	U3
1	7490 IC	U7
1	7402 IC	U4
1	7420 IC	U13
1	7447 IC	U12 (optional)
2	2102 or 2602 ICs	U1, U2 (U2 optional)
1	2N2222A transistor	
3	1N4148 silicon diodes or equivalent	
8	1500- $\Omega$ 1/4-W resistors	
4	10-k $\Omega$ 1/4-W resistors	
2	330- $\Omega$ resistors	
1	4700- $\Omega$ resistor	
4	.001- $\mu$ F disk ceramic capacitors	
4	.1- $\mu$ F disk ceramic capacitors	
1	50- $\mu$ F 15-V electrolytic capacitor	

**Driver Board**

3	7490 ICs
3	7447 ICs
1	7402 IC
1	NE555 IC
22	330- $\Omega$ resistors
1	5600- $\Omega$ resistor
1	2200- $\Omega$ resistor
1	4700- $\Omega$ resistor (33 K $\Omega$ with no pitch control)
1	27- $\Omega$ resistor
1	0.001- $\mu$ F disk ceramic capacitor
1	0.022- $\mu$ F disk ceramic capacitor
2	0.1 $\mu$ F disk ceramic capacitors
2	50- $\mu$ F 15-V electrolytic capacitors

**Readout Board**

4	SLA-1 readouts
6	Push buttons
8	330- $\Omega$ resistors

introduces negligible grid-cathode bias to the keyed stage, and the keying is softened somewhat over relay keying because the transistor cannot go from cutoff to saturation (or vice versa) instantaneously. For QRP transmitters, Q6 may be a 300- or 500-mW silicon npn transistor, such as a 2N2222 or 2N4123.

**Construction and Operation**

A ready-made circuit board is available for the basic circuit of the Accu-Keyer.<sup>3</sup> Fig. 19 is an actual-size board layout and parts-placement guide. If the builder elects to use none of the optional circuit features of Fig. 18, the complete keyer can be built into a 3 × 2 × 5-inch (76 × 51 × 127-mm) Minibox. The board pattern in Fig. 19 contains all parts of Fig. 17 except the controls, the filter capacitor, and the rectifier in the power supply.

It is essential that all leads to the keyer be shielded from rf. RG-174/U coax can be used. A 0.01- $\mu$  F bypass capacitor is provided on the power input to remove rf. As shown on the diagram, the inputs from the paddle are filtered by 150-ohm

<sup>3</sup>A glass-epoxy board, pre-drilled, is available for \$3.50 from James M. Garrett, WB4VVF, 126 W. Buchanan, Orlando, FL 32809.

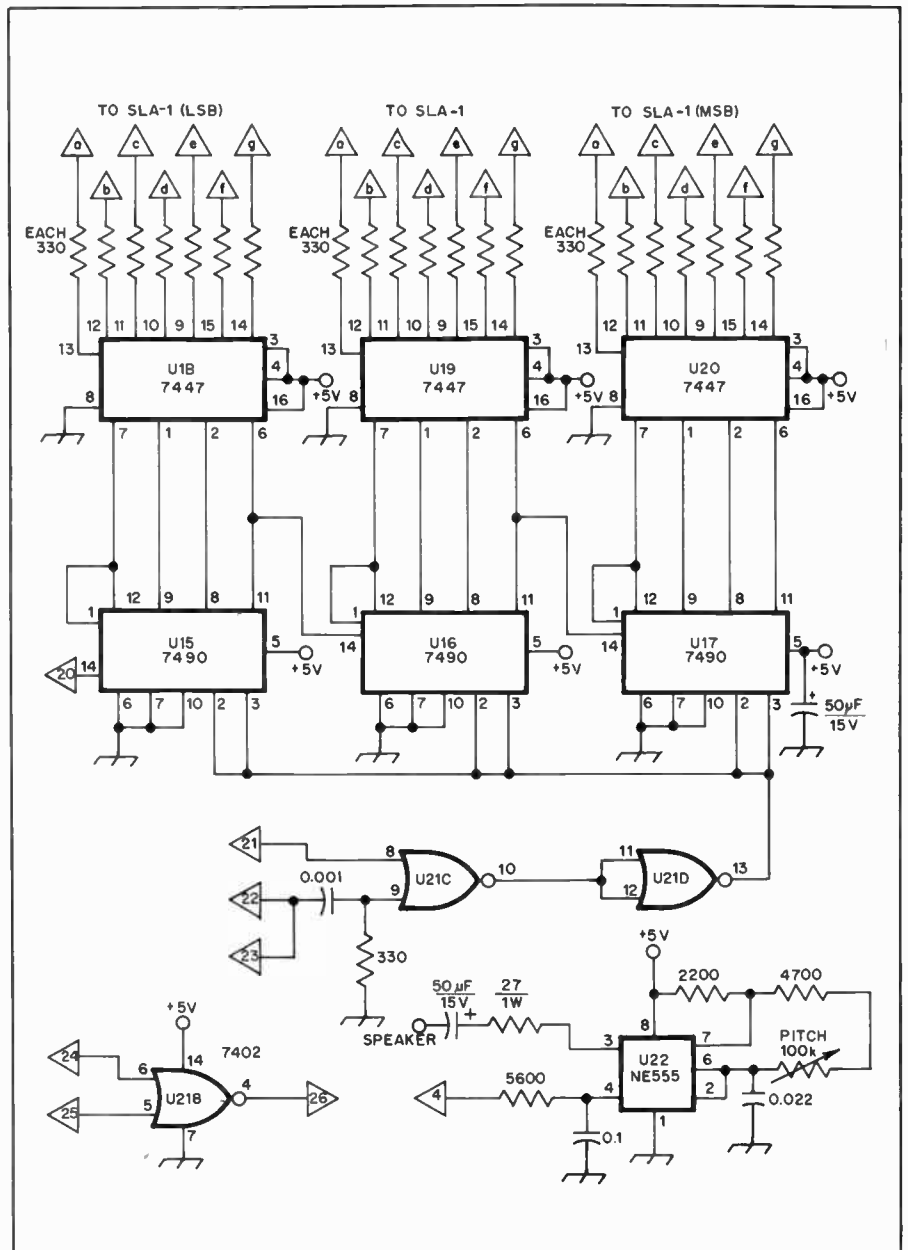


Fig. 14 — Diagram of driver and display. See Table 2 for list of parts. Numbers inside triangles identify interconnections to other parts of the Accu-Memory, as listed in Table 1.

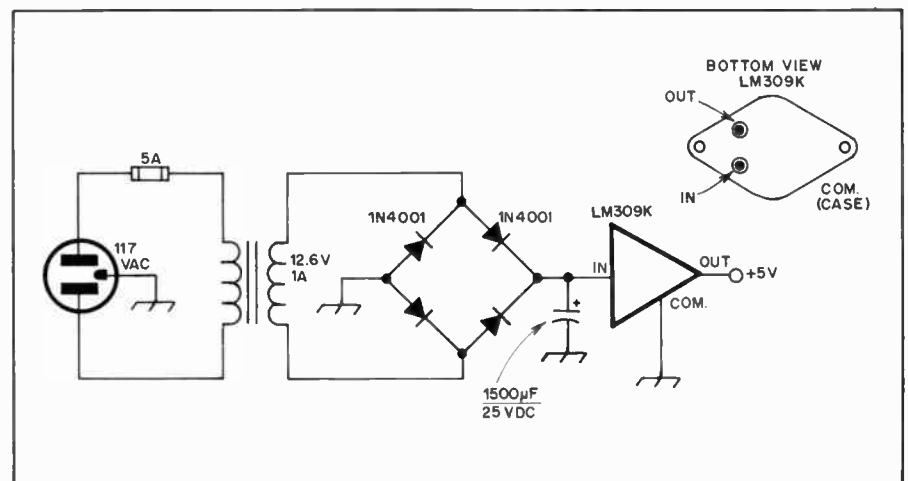


Fig. 15 — Power supply for Accu-Memory and display circuits.



resistors bypassed by 0.001- $\mu$ F capacitors. In stubborn cases it may be necessary to bypass the paddle contacts at the paddle itself.

Substitution of transistors for Q1 and Q2 may require changing the value of R5 to make the first clock pulse the same length as the rest. Both should be transistors with a beta of at least 60. Q3 is noncritical, and any good silicon transistor should work. Q4 should be capable of withstanding the transmitter key-up voltage. Any pnp silicon device having a reasonable beta and meeting this requirement should work. The value of C1 may be juggled to change the range of the speed control. The value specified gives a range of approximately 5 to 50 wpm.

### A Single-IC Keyer

The 8043 integrated electronic keyer IC is a space-age component, designed specifically for the cw operator. A product of the latest design and processing technology available in the integrated circuit industry, the 8043 represents the same advancements which make possible the one-chip electronic calculator and the digital electronic wristwatch. The 8043 is available from Curtis Electro Devices, Box 4090, Mountain View, CA 94040.

A good keyer exhibits no idiosyncrasies. The 8043 incorporates filters which eliminate the effects of key bounce on both make and break. Another intangible quality is rf immunity. To protect false triggering by rf on the paddle leads, the 8043 dit and dah inputs are equipped with active pull-up resistors (a system which reflects a few hundred ohms during quiescence and zero ohms during key down) which exhibit only a few hundred ohms impedance to the power supply when the key is open. In order to assure that the 8043 dissipates as little power as possible, CMOS (complementary metal-oxide semiconductor) circuit techniques are used. As a result, the quiescent current required is only 50 microamperes at 0.5 volts. This makes an on-off switch unnecessary even when using a battery supply. The key-down current is about 30 mA with only 99.9 percent of this current being required for sidetone output and drive for the output transistor.

Once a dit, dah or space is commenced, there is no way to prevent it from transmitting at the exact standard length. It may be neither cut short nor extended by improper key action. When the dit paddle is depressed, a continuous string of dits is produced; when the dah paddle is depressed, continuous dahs are produced. When both paddles are closed, an alternate (iambic) series of dits and dahs is made. The series can be started with either a dit or a dah, depending on which key side is closed first. Iambic operation allows squeeze keying if a

twin-lever paddle is used.

The self-completing function of electronic keyers can cause dits to get lost because the operator, attempting to initiate a dit before the last character has been completed, tends to lead the keyer. Since dahs are naturally held longer they seldom get lost. To prevent lost dits, the 8043 employs a memory to remember when a dit is called for and to insert it at the proper time. The dit memory also helps in squeeze keying, where a tap on the dit paddle will insert a dit into a series of dahs. Although a dit-space ratio of 1:1 is correct timing, some operators like heavier keying. The 8043 has provision for a weight control if desired.

The 8043 has a built-in sidetone generator with pitch adjustable to your preference. This sidetone also functions when a straight key is used or the tune switch is closed. The keying output voltage from the 8043 is low for a key-up condition; key down is represented by high output of sufficient level to drive an npn keying transistor. The speed range is normally about 8 to 50 words per minute, but by selecting timing components, you can get almost any speed range you like.

The 8043 is contained in a 1-3/4  $\times$  2-1/4  $\times$  4-3/4-inch (44  $\times$  57  $\times$  121-mm) metal box. There is no on-off switch because of the low quiescent current drain. Jacks for the paddle and output keying are located on the rear of the enclosure and are not visible in the photograph.

### An Inexpensive Morse Keyboard

Many radio amateurs who have used a keyboard for transmitting Morse code

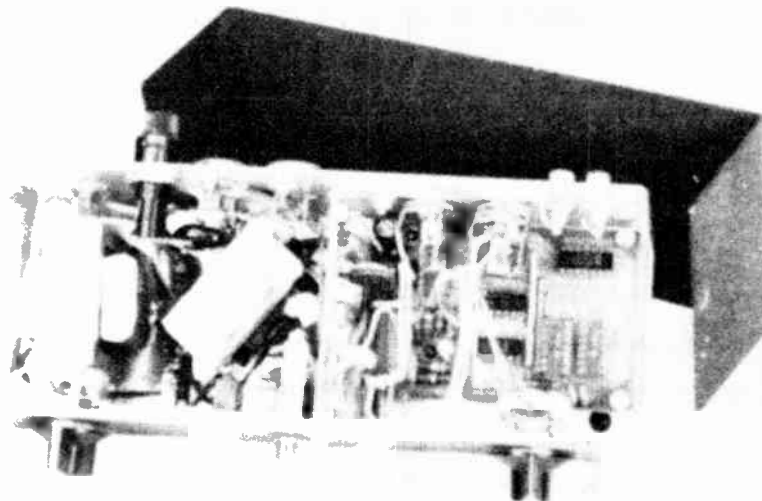


Fig. 16 — A peek inside the Accu-Keyer shows compact construction in this deluxe version built by W1VV. The ac-operated power supply components are located at the left, and the basic keyer board at the right. The keying monitor is constructed on a separate vertically mounted circuit board positioned near the center of the enclosure. The pitch control is mounted inside the keyer on this circuit board as it is not adjusted frequently. The speaker is mounted over a "grille" formed by drilling many holes at the bottom of the enclosure, and is nearly hidden by the filter capacitor in this view. On the rear panel, in TO-3 style cases, are the 5-volt regulator IC and the cathode keying transistor.

find the device most satisfying and delightful for communication. The near-perfect code sent by keyers of this type does much to reduce operator fatigue and increase accuracy of copy. Oddly enough, and over the objections of some purists, machine-sent code does tend to improve one's fist. Any device that improves the quality of radio communication deserves attention and use.

Until recently, the price of commercially available keyboards and the cost of many homebuilt units have made the keyboard keyer an expensive station accessory. But, with the explosive growth of home computers, large supplies of surplus keyboards and digital-logic material have been made available at reasonable prices. By careful shopping and acquisition of a used keyboard, the keyer described in this article can cost less than \$30.

After designing and building two previous keyboard keyers, the writer decided upon a few guidelines for any future construction. First, diode matrices for keyswitch encoding are to be avoided. With all sorts of LSI chips and dynamic systems for encoding switch closures, there is no justification for using literally hundreds of diodes. Secondly, CMOS logic is used. CMOS devices are widely available at reasonable cost. They have excellent noise immunity and allow the use of simple power supplies. Finally, any unnecessary frills will be avoided such as buffer memories, baudot operation, and canned messages.

These extras, although often useful, are not worth the added cost and complexity. What evolved is an inexpensive, easy-

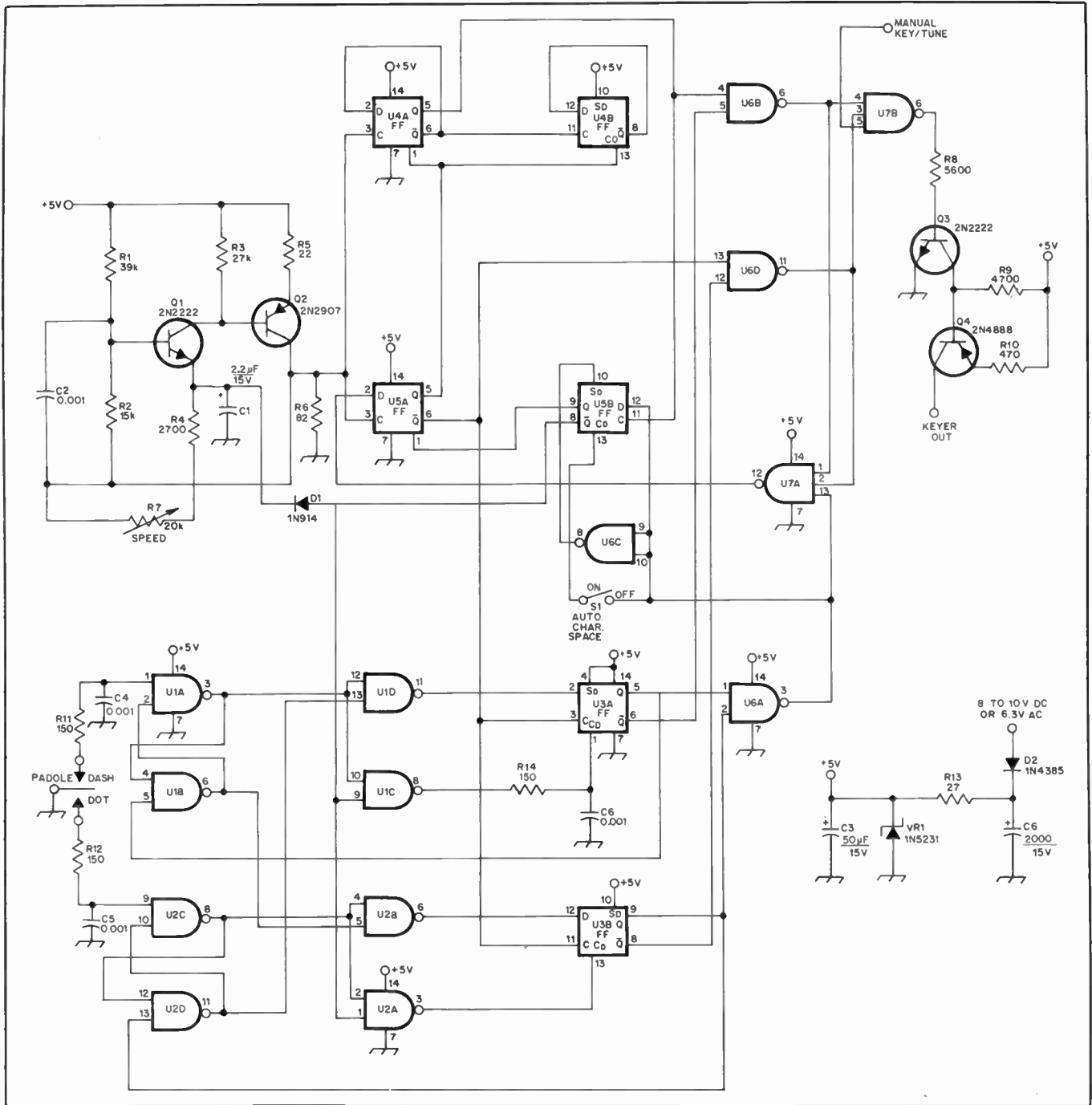


Fig. 17 — Schematic diagram of the Accu-Keyer. Resistances are in ohms; k = 1000. All capacitances are in microfarads. All resistors may be 1/4 watt except R13, which should have a 2-W rating. Capacitors with polarity indicated are electrolytic; all others are disk ceramic. Parts not listed below are for text reference and circuit-board identification.

D1 — Small-signal silicon diode.  
 D2 — Rectifier diode, 1/2 A or greater.  
 D3 — 5.1-V, 0.4-W Zener diode.  
 Q1, Q3 — Silicon npn, 250-mW, high-speed switching or rf-amplifier transistor.  
 Q2 — Silicon pnp, 250-mW, high-speed switching or rf-amplifier transistor.  
 Q4 — Silicon pnp, 250-mW, high-voltage af-amplifier transistor.

R7 — Reverse-log-taper control; Mallory U-28 suitable.  
 S1 — spst toggle.  
 U1, U2, U6 — Quad 2-input NAND gate, type 7400.\*  
 U3, U4, U5 — Dual type D flip-flop, type 7474.  
 U7 — Triple 3-input NAND gate, type 7410.\*

\*All ICs are dual-in-line package, 14 pin. Note: All ICs are available from various manufacturers or as surplus. Motorola part numbers are prefixed by MC and suffixed by P. Texas Instruments parts have an SN prefix and N suffix. Signetics ICs have an N prefix and an A suffix. For example, Motorola's MC7400P is equivalent to Texas Instruments' SN7400N or Signetics' N7400A.

to-build, keyboard keyer constructed from readily available parts. It includes a completely interlocked keyboard with two-key rollover. The unit has the capability to transmit all letters, numbers, punctuation and special symbols in-

cluding  $\overline{AR}$ ,  $\overline{SK}$ ,  $\overline{DN}$ ,  $\overline{AS}$  and  $\overline{BT}$ . The secret to the diodeless encoding scheme is the use of a scanned keyboard. The heart of the scanning circuitry is composed of three CMOS analog multiplexers. An analog multiplexer is com-

parable to eight electronic switches as shown in Fig. 24, arranged so that only one of the eight switches is closed at any time. The switch that is closed depends on the binary number presented to the decoder. For example, if binary 010

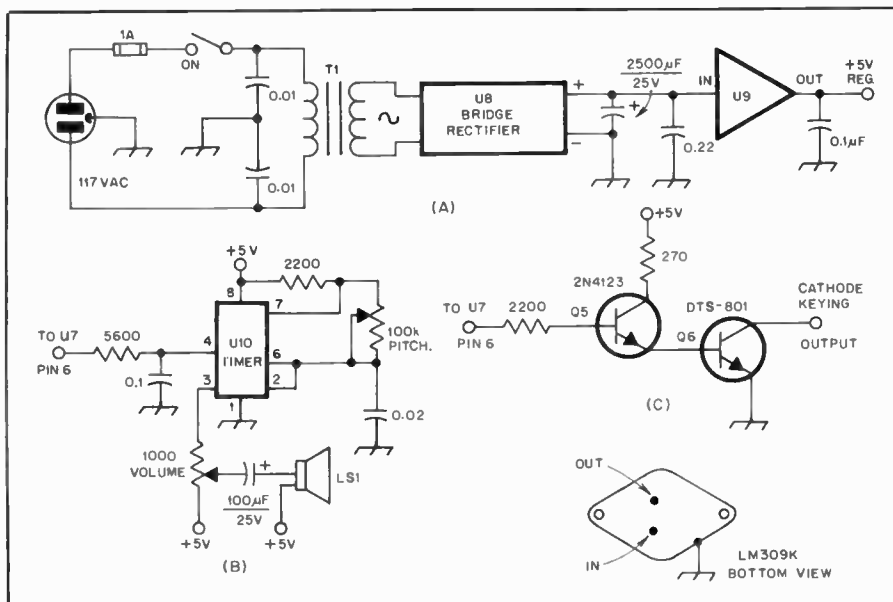


Fig. 18 — At A, optional ac-operated power supply circuit for the Accu-Keyer; at B, an optional monitor, and at C a circuit for cathode keying.  
 LS1 — Miniature speaker, 4-, 8- or 16-ohm impedance.  
 Q6 — High-voltage high-current silicon npn power transistor, Delco DTS-801, -802, or -804 or equiv.  
 T1 — Surplus filament transformer, 12.6-V 1-A secondary rating.

U8 — Full-wave rectifier bridge, 1-A, 50-V, Motorola 920-2, HEP 175, or equiv. Four rectifier diodes in a bridge arrangement may be used instead.  
 U9 — Voltage-regulator IC, 5-volt National Semiconductor LM309K or equiv.  
 U10 — Signetics NE555 timer.



Fig. 20 — Exterior view of IC Keyer.

used in the keyboard keyer as a multiplexer and demultiplexer.

### The Scanned Keyboard

Fig. 25 shows a simplified schematic diagram of a scanned keyboard. It may be viewed as an electronic maze or puzzle. If one of the keyboard switches is closed, the scanning system must find it and generate the proper code assigned to that switch without being fooled by switch bounce or multiple-switch closures. When a keyboard switch closes, there will be a current path from the demultiplexer to the multiplexers. The scanning circuitry attempts to find this current path by closing one electronic switch after another, going through all possible combinations until the circuit is completed.

The current through the demultiplexer, the keyboard switch, the multiplexer and finally resistance R, in that order, causes a voltage drop across R and stops the scanning oscillator. The binary number contained in the seven-bit counter when the oscillator stops is the binary code assigned to the keyswitch. Since the counter is seven bits long, there is the possibility of encoding any binary number from 0000000 to 1111111 and producing 128 different combination possibilities. For example, if switch A in Fig. 25 is closed, the counter will stop at 1111001. If switch B is closed, then the counter stops at 1101110. If no switches are closed, then the circuit will continue to scan all 128 different possibilities until a closed switch is found. When this happens the counter will stop until the detected switch is released, whether or not any other keyboard switches are closed. This produces interlocking so that if more than one keyboard switch is closed, only the first will be decoded.

The scanning oscillator in this keyboard keyer operates at about 64 kHz. At this frequency the operator has a feeling of instantaneous operation. This frequency provides a worst-case decoding time of about 2 ms. Although possible, operating the oscillator at a higher frequency is not

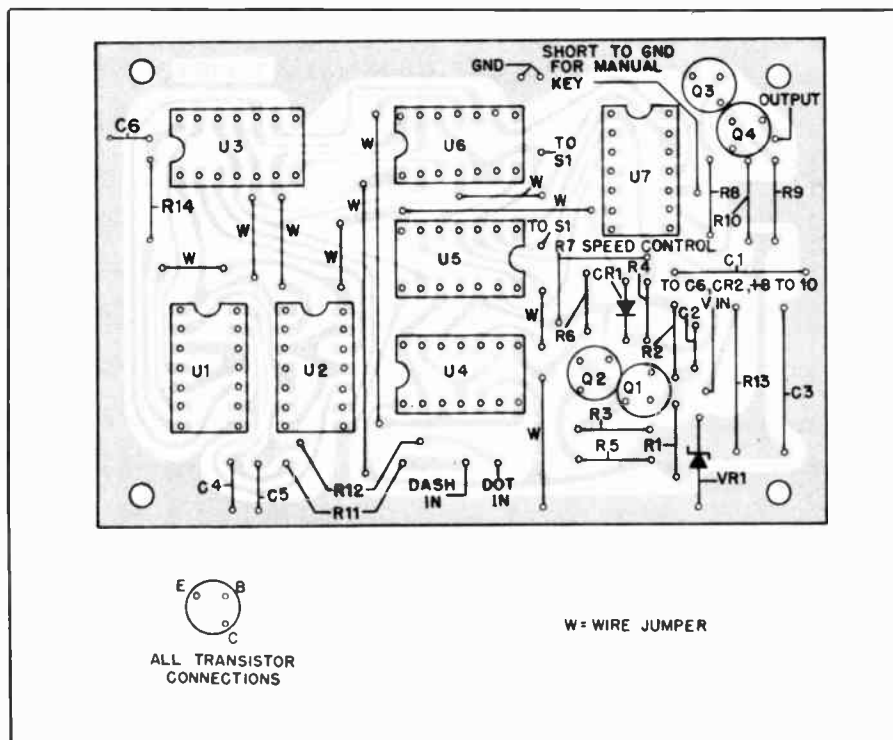


Fig. 19 — Etching pattern and parts-layout diagram for the Accu-Keyer. Pattern is actual size, shown from *fail* side of board.

appears at the decoder, switch number two will be closed. If 000 appears, then switch number zero will be closed. If the input to the decoder is connected to the output of a binary counter, then the switches will close in succession (zero

through seven and back to zero).

If the analog inputs and outputs are reversed the device becomes a demultiplexer, allowing one common input to be applied to any one of eight outputs. The same monolithic integrated circuit is



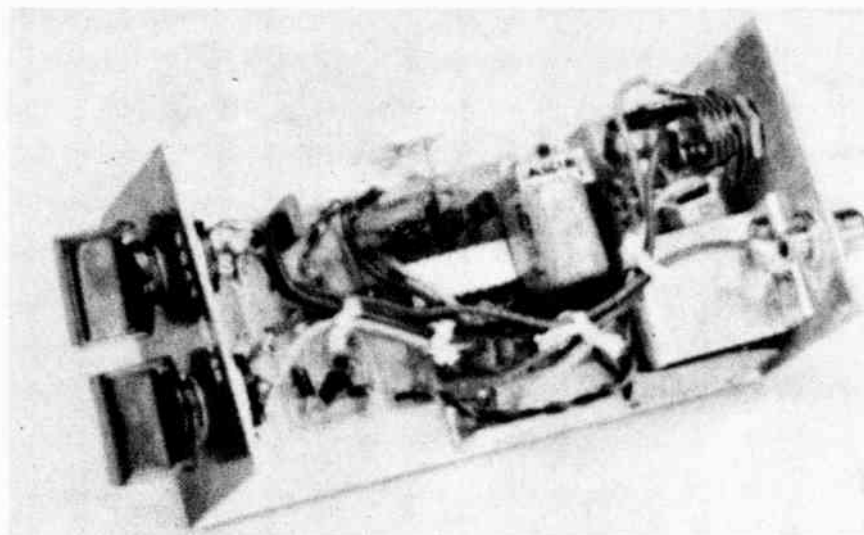


Fig. 21 — Inside view of the one-IC keyer.



Fig. 23 — The designer, K2BLA, operating his keyboard in its intended environment. For field operation, the Gonset twins have been "solid-stated," and run 8 watts to an FET power amplifier.

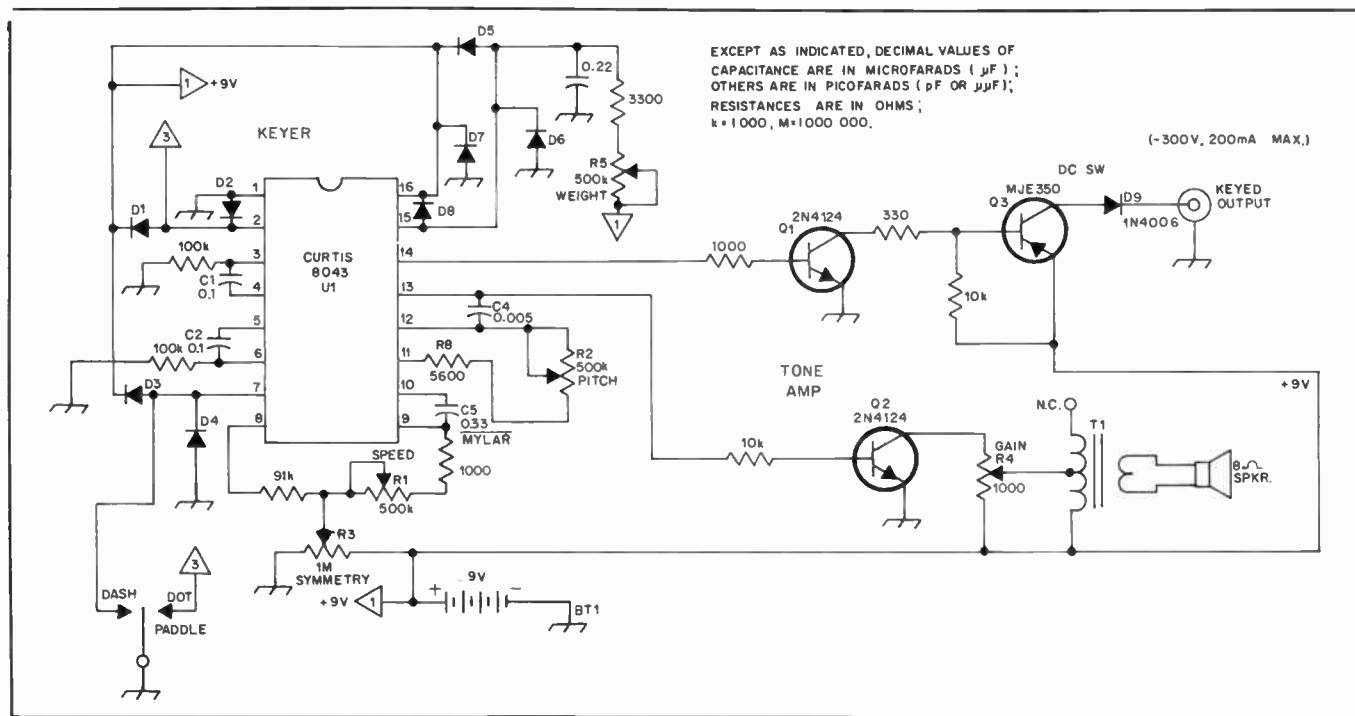


Fig. 22 — Circuit diagram for the keyer. D1-D8, incl., 1N270 or equiv. D9, 1N4006 or equiv. All potentiometers are linear taper and resistors are 1/2- or 1/4-watt. T1, 500 ohms, ct, 8-ohm secondary.

desirable. The 2-ms time is fast enough for practically any keyboard action. Higher scanning frequencies tend to place stronger, low-order harmonics of the scanning oscillator in the hf radio spectrum, causing possible interference problems.

Because the keyboard scanner can only encode seven-bit binary numbers, some scheme is required to convert these binary numbers into valid Morse code characters. In this keyer, binary one represents the dit and binary zero the dah. An extra

zero is added as an "end" bit and the characters are sent from right to left. All of the letters, numbers or special characters must be represented by seven-bit binary numbers where all of the unused bits to the left of the "end" bit are binary 1s. For example, the letter A is represented by 1111001. The right-hand digit, a one, represents a dit. The next digit is zero, representing a dah. The following zero represents the end bit and is not sent, but signifies the end of the Morse

character. The remaining digits are ignored. To illustrate further, the letter B is thus encoded 1101110, and the number seven as 1011100.

### The Shift Register

A shift register is used to temporarily store the decoded binary number and to shift the number to the right one digit at a time (see Fig. 26). The binary output from the keyboard scanning encoder is parallel-loaded into the seven-bit shift register.



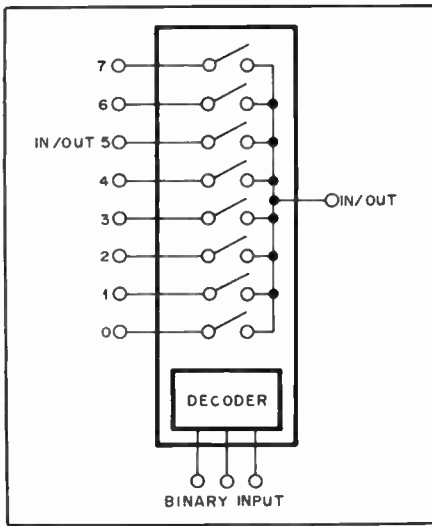


Fig. 24 — An analog multiplexer with an internal decoder. The decoder allows only one of the eight switches to be closed at a time.

Table 3

**Keyswitch Connections**

Connect keyswitches as indicated. Connecting wires are kept short to minimize rf susceptibility. The longest wire in the author's keyboard is about 200 mm (7-7/8 inches). It causes no difficulties.

Character	From	Connect To	Character	From	Connect To
A	A7	B1	X	A4	B6
B	A5	B6	Y	A4	B2
C	A5	B2	Z	A5	B4
D	A6	B6	1	A0	B1
E	A7	B5	2	A0	B3
F	A5	B3	3	A0	B7
G	A6	B4	4	A1	B7
H	A5	B7	5	A3	B7
I	A7	B3	6	A3	B6
J	A4	B1	7	A3	B4
K	A6	B2	8	A3	B0
L	A5	B5	9	A2	B0
M	A7	B0	0	A0	B0
N	A7	B2	AS	A3	B5
O	A6	B0	AR	A2	B5
P	A5	B1	BT	A1	B6
Q	A4	B4	DN	A2	B6
R	A6	B5	SK	A9	B7
S	A6	B7	comma	A8	B4
T	A7	B4	period	A9	B5
U	A6	B3	?	A10	B3
V	A4	B7			
W	A6	B1			

The state of the right-hand stage of the shift register will determine whether a dit or dah is to be sent by the dit/dah circuitry.

Presume that 1111010 has been parallel-loaded into the shift register from the keyboard encoder. Because the right-hand stage of the shift register contains a zero, the dit/dah circuitry will send a dah. The falling edge of the dah shifts the register one step to the right, and places a 1 in the left-hand stage. The number now in the register is 1111101, with the right-hand stage containing a one, the dit/dah circuitry sends a dit.

When the falling edge of the dit shifts the register again, the digital content is 1111110. The dit/dah circuitry generates a dah because the last digit is zero. However, the dah will not be sent because the inhibit line will go low and not allow the dah to appear on the output line. After shifting, the register now contains all ones. This causes the "stop" line to go high, indicating the end of the Morse character. In this example, the letter N has been sent and a space of one dah duration was generated. The shift register is now free to be parallel-loaded with the next encoded Morse character. Notice that a space of one dah duration, included between any two Morse characters, is required for letter spacing and is thus automatically generated.

**About the Electronic Package**

In the keyboard keyer constructed by the writer, these simplified circuits took on a somewhat different form in order to contend with problems of real hardware. See Fig. 29. Extra gating was required to suppress false decoding which resulted from switching glitches in the scanning circuitry. A flip-flop was added to allow automatic spacing of repeated letters.

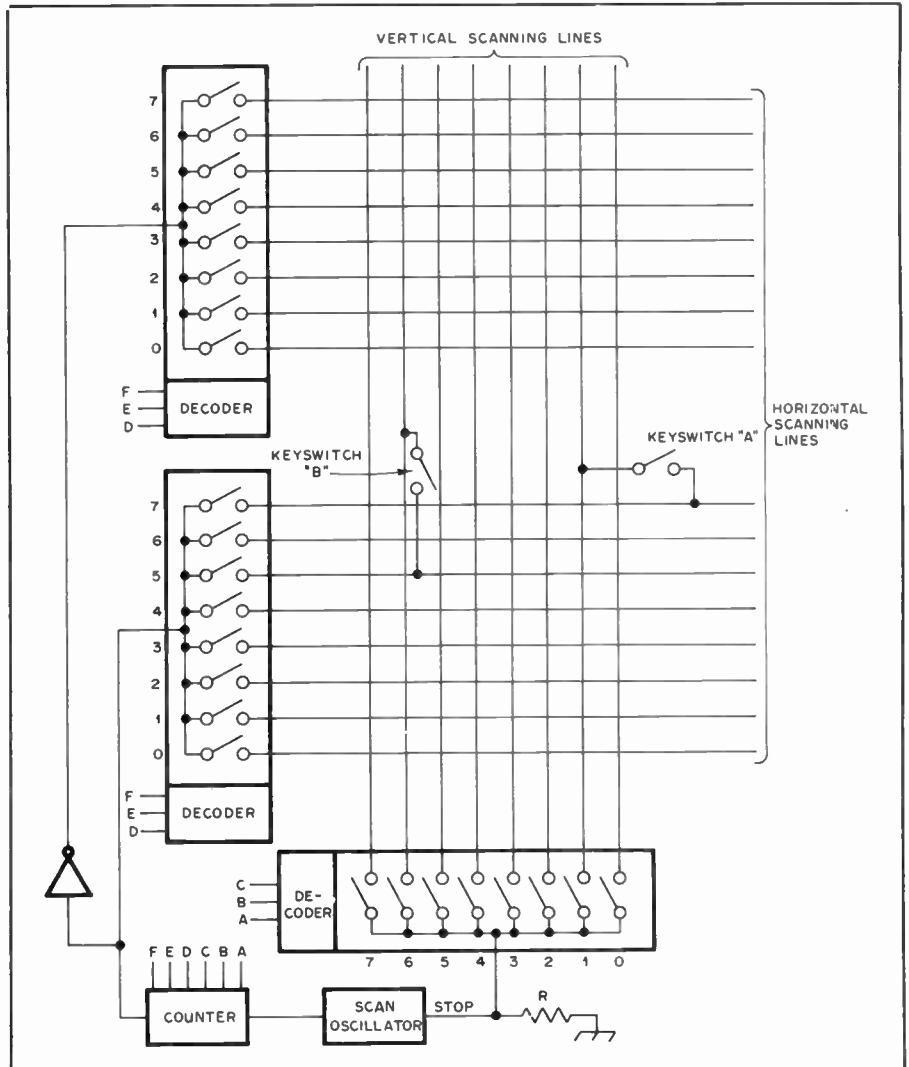


Fig. 25 — A scanned keyboard. Switches are connected between any horizontal wire to any vertical wire as desired. An intersection without a switch implies that these binary codes are unnecessary or invalid for the system.

If the reader wishes to understand thoroughly how the circuit functions, a careful study should be made of the data sheets for each device, especially the complex functions. By doing so, one may gain an in-depth understanding of the keyboard keyer from the moment a switch closure has been detected until the unit is ready for another key closure.

The entire electronics package is assembled on a universal DIP pc board. Wire-wrap techniques could be used, but would require the board to be deeper. Because of the noise immunity of CMOS devices, layout is not critical.

The scanned keyboard circuits are inherently debounced and interlocked. Therefore, almost any type of key contact or keyboard will work. No electronics are required for the keyboard. Consequently,

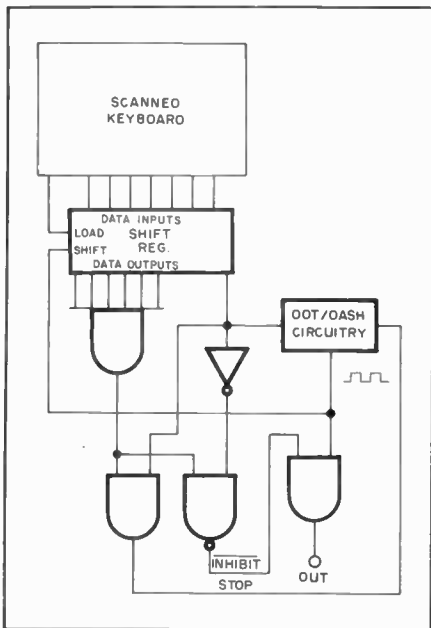


Fig. 26 — A simplified diagram of the Morse keyboard. Each Morse code character has a unique seven-bit binary number. The binary number encoded by a keyboard switch is determined by which horizontal and vertical scanning lines the switch is connected to.

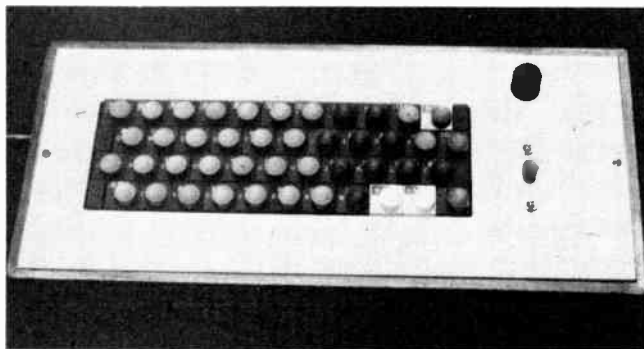
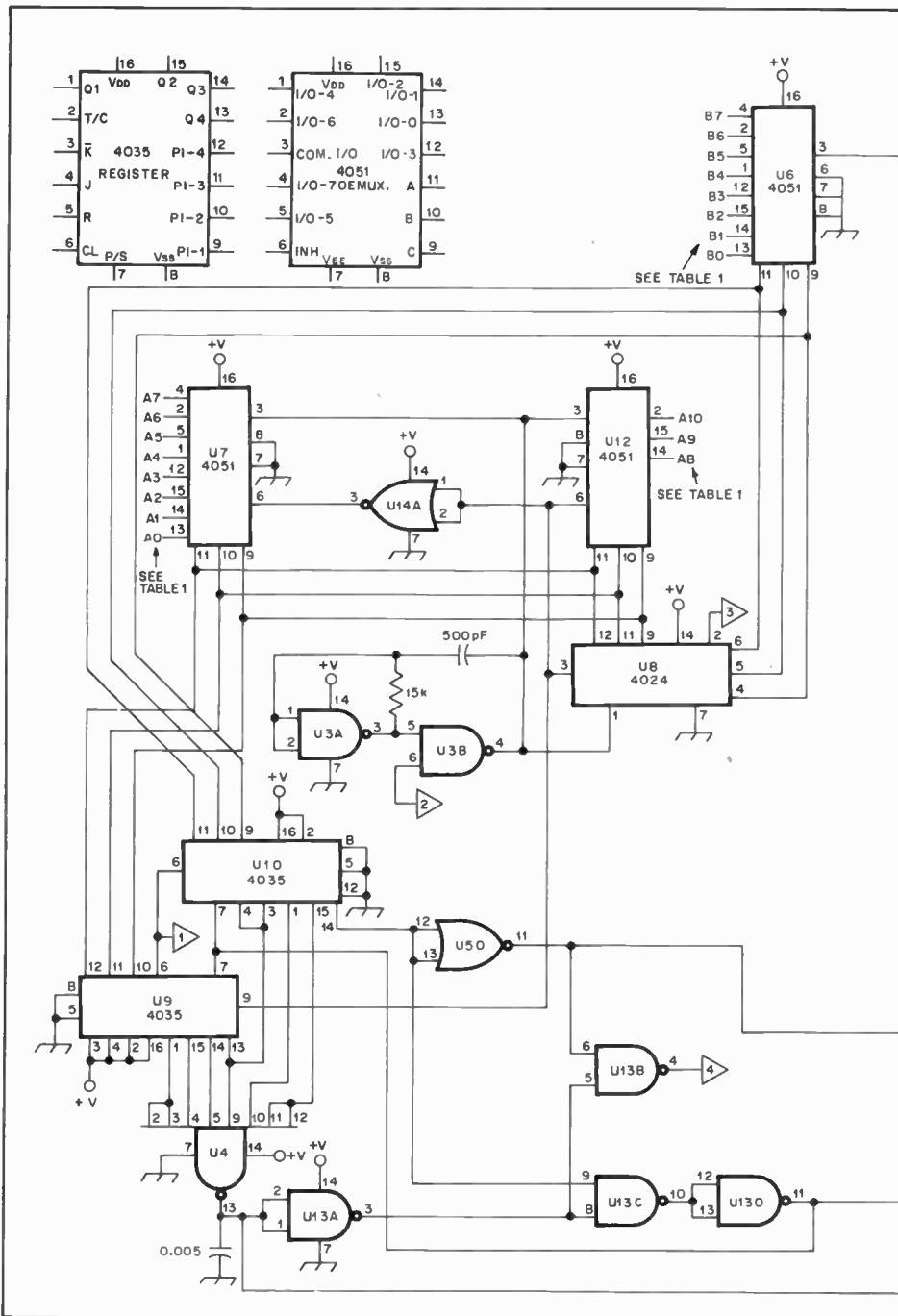


Fig. 27 — Operator's view of the Morse keyboard. The enclosure is home constructed. The top panel is made with 1/8-inch (3 mm) aluminum while the sides are wood. Some keys are relabeled to include noncomputer symbols such as AR, BT or SK.

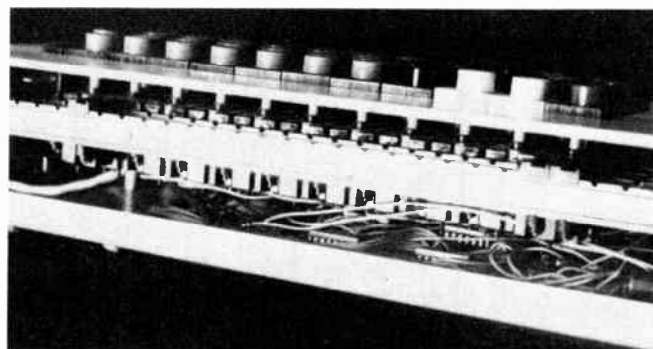


Fig. 28 — The electronics are contained on a single 4- x 6-inch (102 x 152-mm) prototype board attached to a shallow aluminum channel. The keyboard frame, the panel and the electronic channel are secured with long machine screws and spacers.

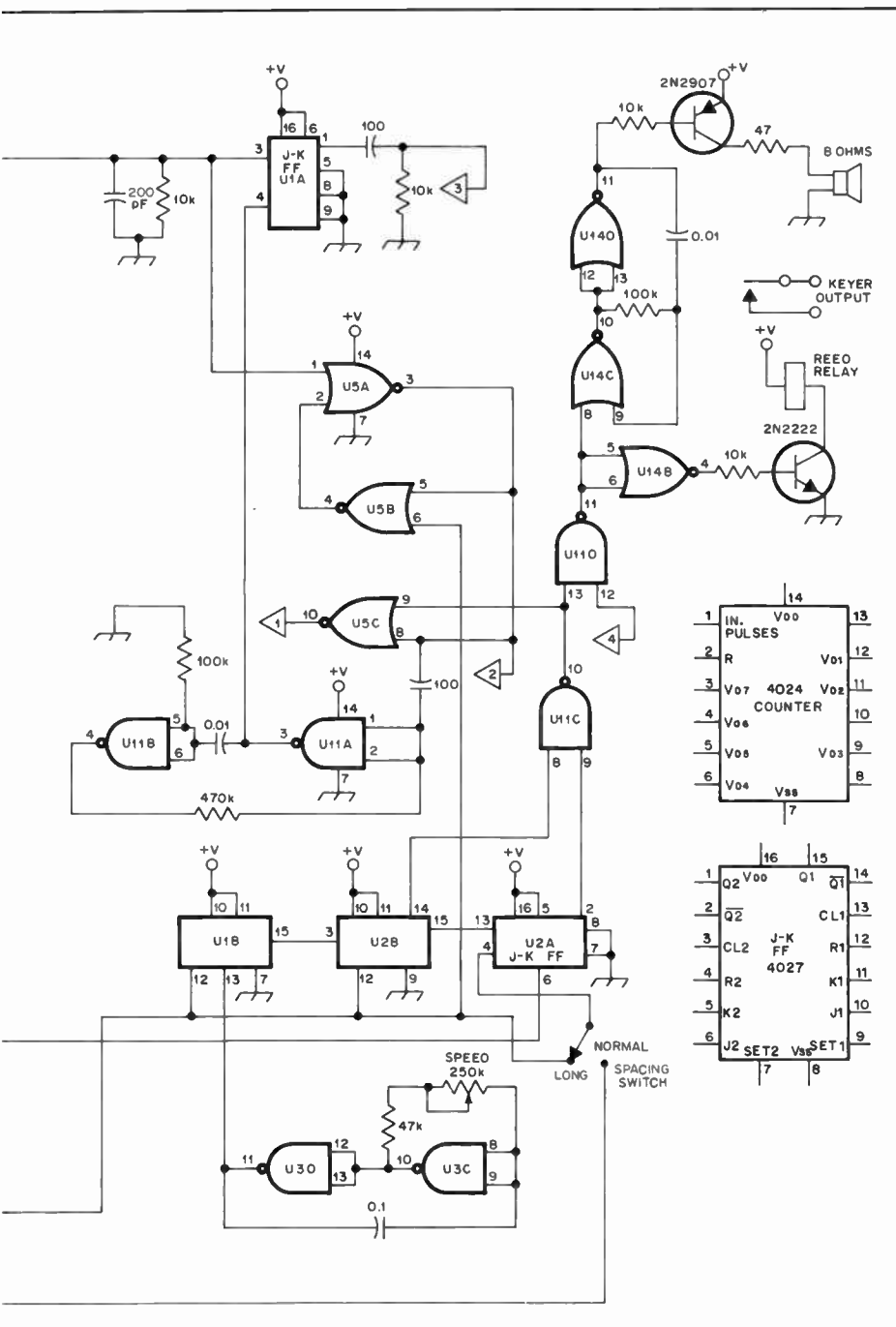


Fig. 29 — The inexpensive Morse keyboard using a diodeless encoding scheme. All capacitors are Mylar or polystyrene, 20V. U1, U2 — Monolithic silicon digital MOS IC, dual J-K flip-flop type 4027. U3, U11, U13 — Monolithic silicon digital MOS IC, quad 2-input NAND gate, type 4011. U4 — Monolithic silicon digital MOS IC, 8-input NAND gate, type 4068. U5, U14 — Monolithic silicon digital MOS IC, quad 2-input NOR gate, type 4001. U6, U7, U12 — Monolithic silicon digital MOS IC, multiplexer/demultiplexer, type 4051. U8 — Monolithic silicon digital MOS IC, 7-stage binary counter, type 4024. U9, U10 — Monolithic silicon digital MOS IC, 4-stage parallel-in/parallel-out shift register, type 4035.

the builder can save considerably by shopping around for a keyboard with nonstandard encoding, or no encoding at all.<sup>4</sup> These keyboards are the least desirable for the computer enthusiast, but are ideal for a Morse keyboard. If the keyboard has any circuit connected to it, the circuitry must be removed.

#### A Sidetone Oscillator and Key Switches

A sidetone oscillator was added and a switch was provided for turning off the sidetone to reduce power drain. A power

drain problem exists for the keying stage. The use of a reed relay is the most foolproof keying method, but costs the most in terms of power drain. If an ac supply is used, power drain is no problem, allowing the use of pilot lamps, monitors and relays. The power supply may range from 5 to 15 volts dc. A regulated supply is not essential. The writer's keyboard keyer is powered by six penlight cells. There is no keying stage because the keyboard is used with a portable transmitter having a CMOS-compatible key input.

#### In Conclusion

The keyboard is easy to use and requires very little skill to send perfect

code. Being familiar with a typewriter keyboard is helpful. Because the keyboard keyer automatically spaces each letter, the operator may press one letter and before the letter has been completed press another letter and still have both letters sent with correct spacing. For example, to send CQ, press the C key and then immediately press the Q key. Hold the Q until the keyer starts sending Q. A perfectly spaced CQ will be transmitted.

One word of caution is in order. Sitting in front of a keyboard is like sitting in the wheel of a Ferrari — one is tempted to go very fast. Remember that copying the keyboard with a pencil is like racing a Model A against the Ferrari!

<sup>4</sup>To purchase a keyboard, the builder should refer to Ham Ads in *QST* and advertisements for surplus equipment.

# Single-Sideband Transmission

A fully modulated a-m signal has two-thirds of its power in the carrier and only one-third in the sidebands. The sidebands carry the intelligence to be transmitted; the carrier “goes along for the ride” and serves only to demodulate the signal at the receiver. By eliminating the carrier and transmitting only the sidebands, or just one sideband, the available transmitter power is used to greater advantage. To recover the intelligence being transmitted, the carrier must be reinserted at the receiver, but this is no great problem with a proper detector circuit.

Assuming that the same final-amplifier tube or tubes are used either for normal a-m or for single sideband, carrier suppressed, it can be shown that the use of ssb can give an effective gain of up to 9 dB over a-m — equivalent to increasing the transmitter power eight times. Eliminating the carrier also eliminates the heterodyne interference that so often spoils communication in congested phone bands.

### Generating the SSB Signal: Filter Method

Two basic systems for generating ssb signals are shown in Fig. 2. One involves the use of a band-pass filter having sufficient selectivity to pass one sideband and reject the other. Mechanical filters are available for frequencies below 1 MHz. From 0.2 to 10 MHz, good sideband rejection can be obtained with filters using

four or more quartz crystals. Oscillator output at the filter frequency is combined with the audio signal in a balanced modulator, and only the upper and lower sidebands appear in the output. One of the sidebands is passed by the filter and the other rejected, so that an ssb signal is fed to the mixer. The signal is mixed with the output of a high-frequency rf oscillator to produce the desired output frequency. For additional amplification a linear rf amplifier must be used.

When the ssb signal is generated around 500 kHz it may be necessary to convert twice to reach the operating frequency, since this simplifies the problem of rejecting the “image” frequencies re-

sulting from the heterodyne process. The problem of image frequencies in the frequency conversions of ssb signals differs from the problem in receivers because the beating-oscillator frequency becomes important. Either balanced mixers or sufficient selectivity must be used to attenuate these frequencies in the output and hence minimize the possibility of unwanted radiations. (Examples of filter-type exciters can be found in various issues of *QST* and in *Single Sideband for the Radio Amateur*.)

### High-Frequency Crystal Filters for SSB

Many articles have appeared in *QST* describing crystal filters for ssb



Fig. 1 — Practical example of a homemade SSB transceiver. (Designed and built by K1ZJH).

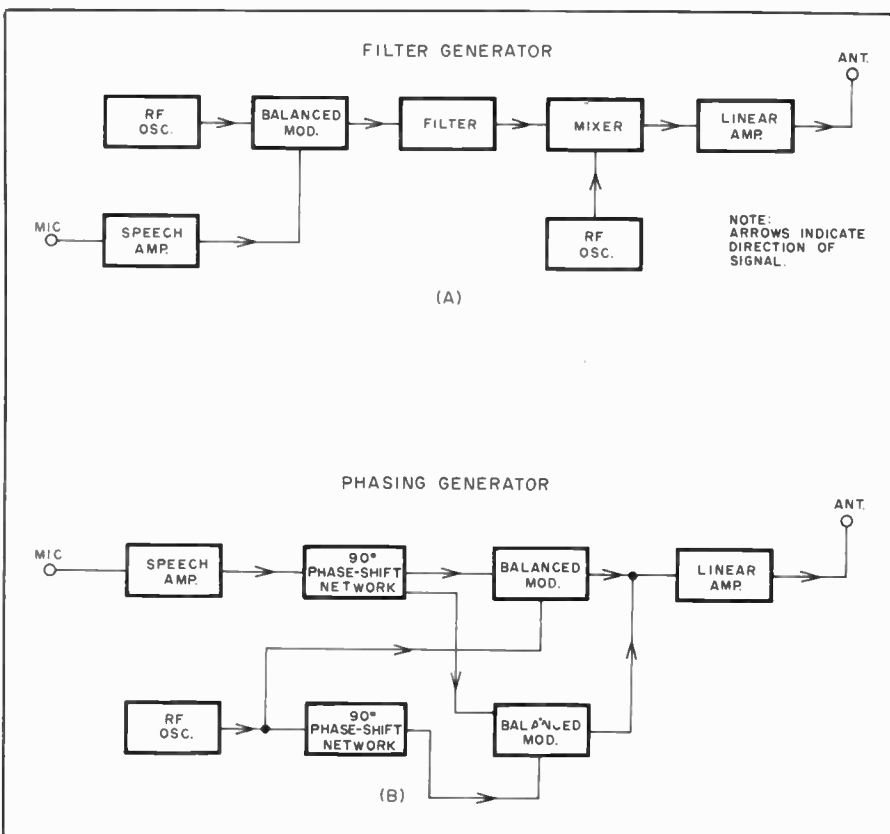


Fig. 2 — Two basic systems for generating single-sideband suppressed carrier signals



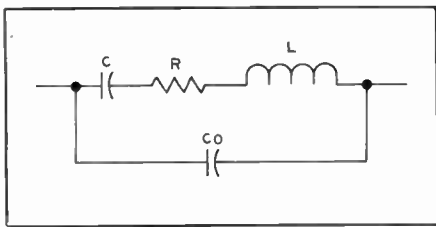


Fig. 3 — Equivalent circuit of a crystal. C and L are the motional capacitance and inductance of the crystal, and R represents the frictional loss. C<sub>0</sub> is the electrode and holder capacitance shunting the crystal.

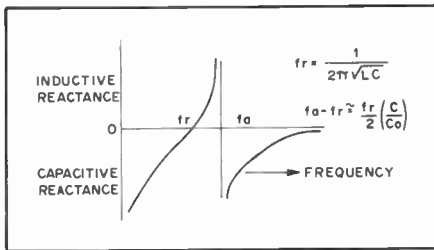


Fig. 4 — Reactance vs. frequency characteristics of a crystal. The series-resonant frequency,  $f_r$ , is that of C and L. The anti-(parallel) resonant frequency,  $f_a$ , is that of the circuit formed by C and L in one branch and C<sub>0</sub> in the other.

operations.<sup>1-5</sup> However, none of these supplied a design procedure or gave the precise performance of the resulting filters. This presentation describes a particular type of filter that was built for a homemade transceiver. [Editor's Note: This section was written by D. J. Healey, W3HEC].

The theoretical shape of the selectivity characteristic attainable with simple crys-

tal-filter arrangements was calculated first and found to be inadequate for good sideband suppression. The effect of mismatch when filter sections are cascaded without vacuum-tube isolation improved the steepness of the selectivity characteristic but at the expense of ripple in the passband. By inserting a small resistance between two sections of a three-section filter, the ripple was reduced without greatly affecting the shape factor (ratio of the bandwidth at some high attenuation to the bandwidth at low attenuation) of the selectivity curve. A filter constructed according to this design from FT-243 surplus crystals performed as predicted.

In filters such as the one used in the transceiver described by W3TLN<sup>6</sup> it is not

unusual to obtain spurious responses as close as 15 kHz to the passband which are suppressed by only about 20dB. In the filter described here the spurious responses are attenuated more than 50 dB, even with a crystal whose principal spurious frequency was only 7 dB down from the main response.

### Simple Filter Sections

Fig. 3 shows the equivalent circuit of a crystal neglecting its spurious modes. This circuit has the reactance vs. frequency curve shown in Fig. 4. L and C are series resonant at  $f_r$ , and  $f_a$  is the antiresonant frequency of C<sub>0</sub> and the LC combination. A selective filter is obtained by utilizing crystals in a lattice structure, as shown in Fig. 5. The lattice is a bridge, and it is obvious that maximum unbalance of the bridge will occur when one arm has an impedance which is capacitive while the other arm is inductive. When the impedances are equal, the bridge will be balanced. The reactance vs. frequency curves of the crystals can then be used to indicate the regions of the passband and the stopband. Fig. 6 shows what happens when the antiresonant frequency of one pair of crystals is made equal to the resonant frequency of the other pair. It is observed that the passband of a simple lattice is limited to the region between the antiresonant frequency of the higher-frequency crystals and the resonant

<sup>1</sup>Weaver and Brown, "Crystal Lattice Filters," *QST*, June, 1951.  
<sup>2</sup>Good, "A Crystal Filter for Phone Reception," *QST*, October, 1951.  
<sup>3</sup>Burns, "Sideband Filters Using Crystals," *QST*, November, 1954.  
<sup>4</sup>Morrison, "Cascaded Half-Lattice Crystal Filters for Phone and C. W. Reception," *QST*, May, 1954.  
<sup>5</sup>Vester, "Surplus-Crystal High Frequency Filters," *QST*, January, 1959.  
<sup>6</sup>Vester, "Mobile S.S.B. Transceiver," *QST*, June, 1959.

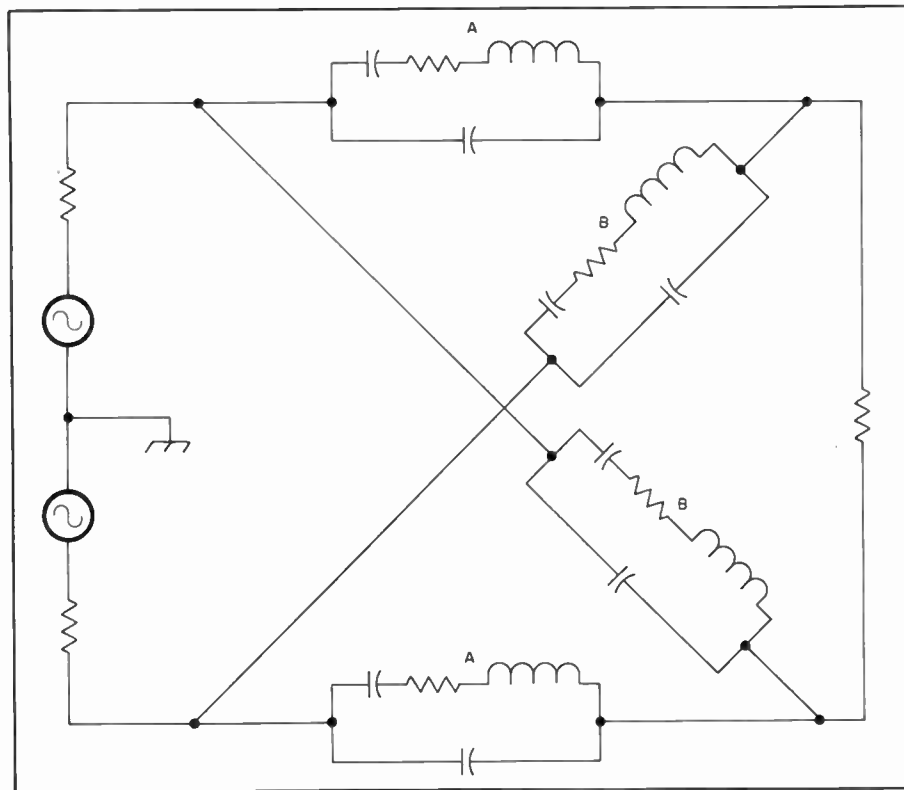


Fig. 5 — Equivalent circuit of a full lattice crystal filter. The series crystals, A, are the same frequency, as are the shunt crystals, B. Note that the lattice could be redrawn as a bridge circuit.

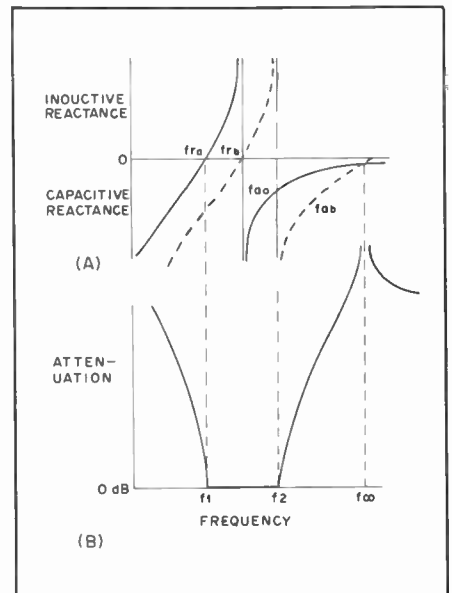


Fig. 6 — (A) Reactance characteristics of crystals A and B in the lattice of Fig. 5. In the type of filter described in this article, the series-resonant frequency of the higher-frequency crystal,  $f_{aB}$ . (B) Attenuation curve of a filter using the crystals of (A). In the passband between  $f_1$  and  $f_2$  the series and shunt reactances are opposite, the bridge is unbalanced, and nearly all of the input signal appears at the output. At other frequencies the reactances are similar, and the bridge approaches balance and shows little output.

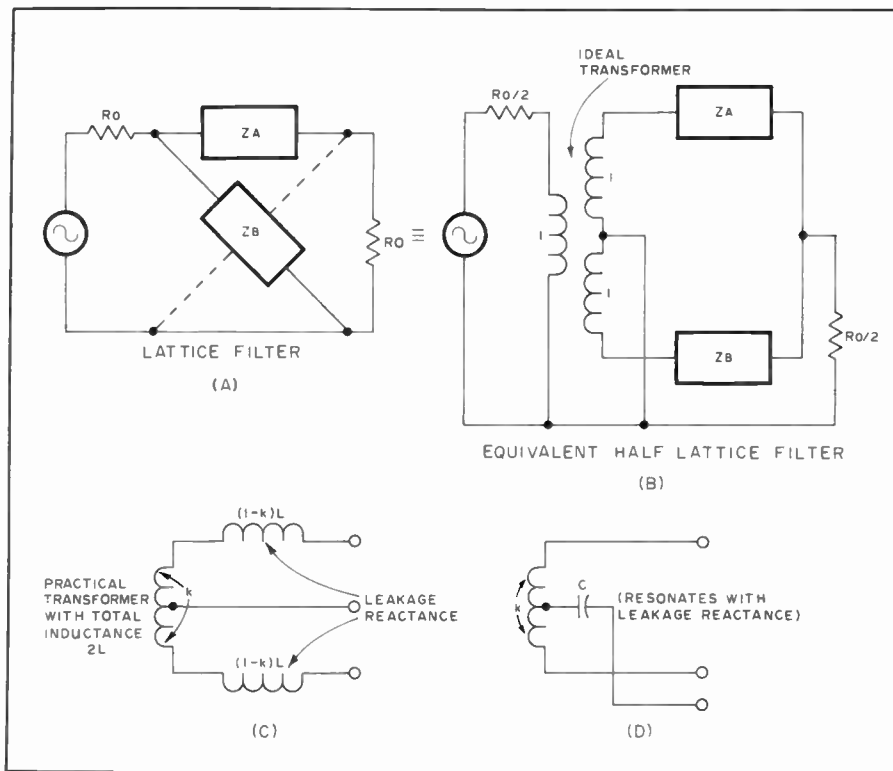


Fig. 7 — (A) Basic circuit of a lattice filter and (B) an equivalent half-lattice filter. The transformer is an ideal one with unity coupling between windings. (C) Diagram of a practical transformer showing the leakage inductance which results from a coupling coefficient,  $k$ , less than unity. (D) How the leakage reactance may be tuned out by inserting capacitor,  $C$ , in the center-tap lead.

frequency of the lower-frequency crystals. For the case where the reactance curves in the stopband are equal only at zero frequency and infinite frequency, analysis of the circuit shows that the frequency difference  $f_2 - f_1$  corresponds to the bandwidth at which the attenuation is approximately 7 dB.

The resistive component of the crystal may be transformed to an equivalent parallel resistance shunting the crystal, which is essentially constant for the small frequency range of concern. If all crystals have the same  $Q$  and inductance, then the equivalent resistance shunting the crystals is the same, and if one considers the resistive bridge thus formed, it is balanced under these conditions. The loss resistance can then be neglected except as it modifies the termination of the filter and affects insertion loss. The point is that the filter behaves essentially as though its elements had infinite  $Q$ .

Identical results can be obtained with half as many crystals in a half-lattice circuit. As shown in Fig. 7, this is the equivalent of a full lattice in which the impedances of the elements are one-half those of the half lattice. The basic circuit, Fig. 7B, shows two crystals and an ideal transformer that does not have unity coupling can be represented by the circuit of Fig. 7C. Leakage reactance appears in series with the crystals of the lattice and will lower their resonant frequencies. In narrow-band filters, this can be prevented by connecting a capacitor which resonates

with the leakage inductance at the center frequency of the filter in series with the center tap<sup>7</sup> as in Fig. 7D. This allows a simple center-tapped coil to be used for the ideal transformer.

### Designing An SSB Filter

In building a filter for a transceiver, an intermediate frequency of 5500 kHz was selected. This choice is satisfactory for 100-dB suppression of spurious signals in the receiver except on 15 meters. There, a fifth-order intermodulation product falls in the passband so that with a simple mixer the spurious response is only attenuated 75 dB. However, by using a simple balanced mixer, the desired suppression of 100 dB is realized. The balanced mixer also reduces the pre-selection requirements on other bands.

Since the passband is on the order of twice  $f_z - f_r$ , this frequency difference must be about 1500 Hz for a filter capable of passing the voice frequencies. The second formula in Fig. 4 shows that  $f_a - f_r$  depends on the ratio of the capacitance shunting the crystal to the motional capacitance of the crystal. For AT-cut crystals (the ones you get inexpensively), this ratio is about 250 minimum. Therefore, AT-cut crystals above 750 kHz meet the requirements, and capacitive terminations are feasible. For example, the shunt capacitance  $C_o$ , of a typical AT-cut crystal is about 3 pF. If it is desired to terminate a half-lattice filter with a circuit

<sup>7</sup>Kosovsky, Patent no. 2,913,682.

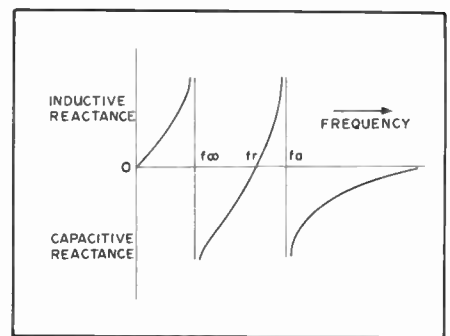


Fig. 8 — Reactance vs. frequency characteristics of a crystal and inductance,  $L_o$ , in parallel.  $f_r$ , the resonant frequency of  $C$  and  $L$ , the motional capacitance and inductance of the crystal, is the same as in Fig. 4.  $f_a$ , however, is higher than the antiresonant frequency of the crystal alone, since  $L_o$  decreases the effective inductance across shunt capacitance  $C_o$  at frequencies above  $f_r$ .  $L_o$  is also antiresonant with the total effective capacitance of the crystal at some lower frequency,  $f_{oo}$ .

capacitance of, say, 15 pF, this will reflect as a total shunt  $C$  of  $15/2 + 3 = 10.5$  pF across each crystal. Under such conditions, AT-cut crystals can be used for amateur ssb applications at any frequency above 2625 kHz.

Surplus FT-243 crystals (BT-cut) are available for 5500 kHz and their use is economically attractive. These crystals, however, have  $C_o/C$  ratios around 4000 minimum<sup>8</sup> which is too high to allow the desired passband to be obtained. The passband can be widened by paralleling inductance with the crystals. This will raise their antiresonant frequencies and leave their resonant frequencies unchanged. One must be cautious in doing this since the inductance will also be antiresonant with the total effective capacitance of the crystal at some lower frequency,  $f_{oo}$  in Fig. 8. If this new frequency of infinite attenuation is too close to the center frequency of the filter, the passband characteristics may be distorted.

Measurements made on an FT-243 crystal resonant at 5502.195 kHz showed a motional capacitance,  $C$ , of 0.0038 pF and a shunt capacitance,  $C_o$ , of 14.7 pF. The spacing between the resonant and antiresonant frequencies is therefore

$$\frac{5502195}{2} \left( \frac{0.0038}{14.7} \right) \text{ or } 711 \text{ Hz}$$

To provide a desired spacing of, say, 1422 Hz, the effective shunt capacitance must be reduced to one half the value of  $C_o$ .

<sup>8</sup>Herman Shall, W3BWK, has pointed out that the high ratios measured on FT-243 surplus crystals result from the nature of their mounting. Actually, BT-cut crystals can exhibit ratios as low as 400. Some of the FT-243s on the surplus market may be AT cut, and may have ratios around 2000. AT-cut crystals which are plated can have ratios as low as 250. If the ratio is other than indicated in the article (around 4000) the termination tuning will be slightly different. However, the range of tuning available with the specified coils should be adequate for any surplus crystals available. — Ed.

This would require the addition of a *negative* capacitance of  $14.7/2 = 7.35$  pF. If an inductance,  $L_o$  in parallel with capacitance  $C_o$  is considered, the susceptance of the parallel combination is

$$B = 2\pi f \left( C_o - \frac{1}{4\pi^2 f^2 L_o} \right)$$

$$= 2\pi f C_o \left( 1 - \frac{f_{\infty}^2}{f^2} \right)$$

where  $f_{\infty}$  is the antiresonant frequency of  $L_o$  and  $C_o$ . (The capacitive contribution of the motional capacitance and inductance below their resonant frequency is small enough to be neglected.) For the case above, it is desired to reduce the susceptance of  $C_o$  alone,  $2\pi f C_o$ , by a factor of one half. This means that

$$1 - \frac{f_{\infty}^2}{f^2}$$

must equal 1/2, so  $L_o$  and  $C_o$  must be antiresonant at 0.707 times the filter frequency or about 3889 kHz for the 5500-kHz filter. Higher values of  $f_{\infty}$  will also work as long as they are not too close to the center frequency.

For convenience, the filter was built with input and output coils which resonate with 56 pF plus about 10 pF tube and circuit capacitance. This is equivalent to about 33 pF across each crystal, or a total effective  $C_o$  of 47.7 pF. Since the effective  $C_o$  desired is only 7.35 pF,

$$1 - \frac{f_{\infty}^2}{f^2} = 7.35/47.7 = 0.154$$

and  $f_{\infty}$  is 0.92 times the filter frequency, or 5060 kHz. This new frequency of infinite attenuation, due to resonance between the coil paralleling the crystal and the total capacitance, is sufficiently removed from the center frequency so that it has negligible effect on the passband shape. Design equations for narrow-band capacitor-only filter circuits should therefore be sufficiently accurate for a filter built around FT-243 crystals at 5500 kHz.

For narrow-band filters of this type it is convenient to describe the selectivity characteristic in terms of a normalized frequency variable,  $Z$ .

$$\text{Let } f = f_o + Z \left( \frac{f_2 - f_1}{2} \right)$$

where  $f_1$  is the resonant frequency of the lower-frequency crystal,  $f_2$  is the antiresonant frequency of the higher-frequency crystal as modified by the circuit, and  $f_o = 1/2 (f_1 + f_2)$ , the center frequency of the filter.

Fig. 9 shows the selectivity characteristics of two- and three-section filters (each section being two crystals in a half lattice) when the effects of mismatch between sections<sup>9</sup> are neglected. Note that

these are normalized curves, plotted in terms of the variable  $Z$ .

If we consider only two sections and a 6-dB bandwidth of 2400 Hz, the upper curve of Fig. 9 tells us that  $Z = 0.7$  corresponds to 1200 Hz. In these plots,  $Z$  is proportional to the separation from the center of the passband. If we assume a low audio cutoff of 300 Hz, the carrier must be  $1200 + 300 = 1500$  Hz from the center frequency. Therefore, the carrier must lie at

$$Z = \frac{1500}{1200} \cdot 0.7 = 0.875$$

At this frequency the carrier attenuation would only be about 10.5 dB. The undesired sideband would extend from

$$Z = 0.7 \frac{1800}{1200} = 1.05 \text{ to}$$

$$Z = \frac{4200}{1200} \cdot 0.7 = 2.45$$

The corresponding sideband suppression would vary between 15.4 and 43.2 dB.

This is not adequate for our purpose, so three sections must be considered. Here, the 6-dB down frequencies correspond to  $Z = 0.617$ . Carrier rejection would be 11.6 dB and sideband suppression varies between 17.9 and 58.4 dB. This still does not meet our requirement, which is 30- to 40-dB suppression of the undesired sideband with a low audio cutoff of 300 Hz, and about 20-dB carrier rejection due to filter selectivity.

Fortunately, the interaction which occurs due to mismatch between cascaded identical filter sections will help us achieve this goal. Fig. 10 shows the selectivity characteristics of two- and three-section filters when effects of mismatch are taken into account. As can be seen, these curves are much steeper than those of Fig. 9.

Consider as before a 6-dB bandwidth of 2400 Hz. For three sections, 1200 Hz corresponds to  $Z = 0.91$ , and at the carrier frequency

$$Z = 0.91 \times \frac{1500}{1200} = 1.138$$

At this value of  $Z$ , the rejection is 26.5 dB.

<sup>9</sup>The classical method of filter design uses the notion of a characteristic impedance for a filter section. When several filter sections having the same characteristic impedance are cascaded, the over-all selectivity characteristic should be the product of characteristics of the individual sections (or the sum of their responses in decibels). The difficulty is that the image impedance required to terminate the filter in its characteristic impedance is not realizable with ordinary resistive terminations. As a result, there is reflection at the termination which is a function of frequency, and the filter section does not provide the correct image impedance for an identical section which may precede it. In practical filters a match is obtained only on the average over the frequency range of interest. The input impedance, therefore, varies from the image impedance value, and it is this variation which causes a practical multisection filter to have a response which is different from that which would be expected from the characteristics of the individual sections.

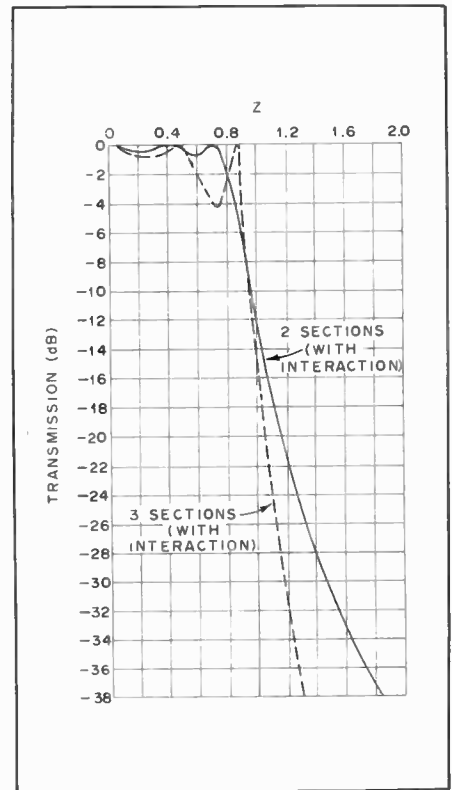


Fig. 9 — Theoretical selectivity characteristics of two and three cascaded identical filter sections when interaction due to mismatch between the sections is ignored.  $Z$  is the normalized frequency variable defined in the text. It is proportional to the frequency difference from the center of the passband.

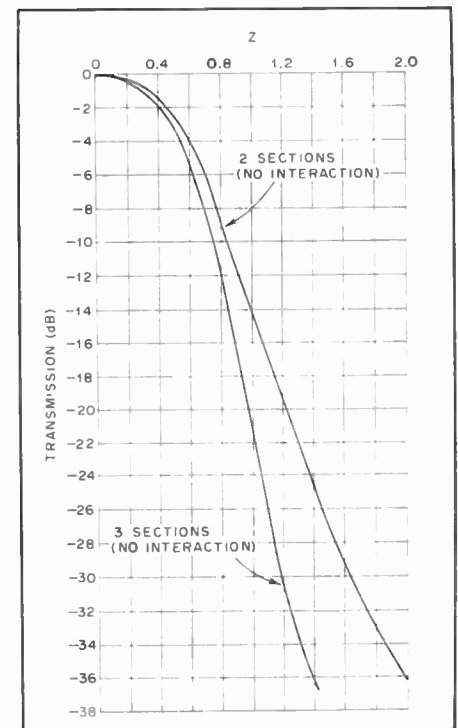


Fig. 10 — Theoretical selectivity characteristics of two and three cascaded identical filter sections when interaction is taken into account. These curves are steeper than those of Fig. 9, but there is considerable ripple in the passband.



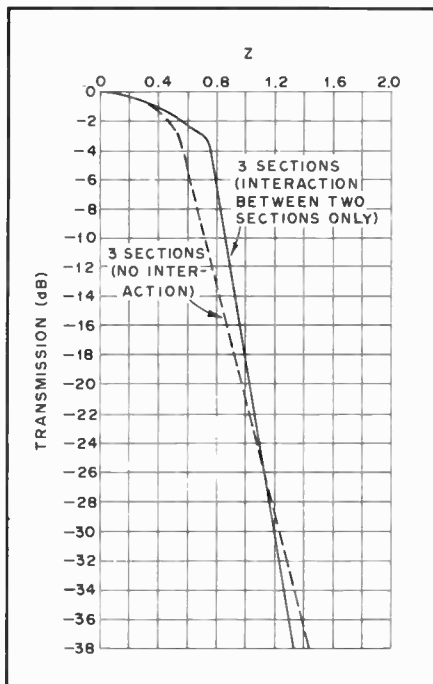


Fig. 11 — The solid curve shows the selectivity of a three-section filter with interaction between two sections only. This design is an excellent compromise between those of Figs. 9 and 10. The dashed curve drawn for comparison is for a three-section filter without interaction.

At the low audio end of the undesired sideband,

$$Z = 0.91 \times \frac{1800}{1200} = 1.36$$

and the attenuation is 40.5 dB. Thus, the three identical crystal filter sections satisfy our requirements.

If we build three sections and reduce the interaction of one section, the attenuation characteristic becomes that shown in Fig. 11. The large pass-band ripple of Fig. 10 is reduced, and by allowing some interaction but not the full interaction of one section, the passband can be made nearly flat. In Fig. 11,  $Z = 0.8$  when the response is 6 dB down. If we again consider a 2400-Hz bandwidth and 300-Hz audio cut-off,  $Z = 0.8 \times 1500/1200 = 1.0$  at the carrier frequency; the corresponding attenuation from Fig. 11 is 19 dB. The undesired sideband extends from  $Z = 1.2$  to  $Z = 2.8$ , so sideband attenuation will range from 30.3 to greater than 60 dB. Such a filter will meet the requirements as well as provide a flat passband. The shape factor for 30 dB/6 dB is 1.49 and for 60 dB/6 dB, about 2.5.

Since  $Z = 0.8$ , 1200 Hz from the center frequency, these values can be substituted into the equation which defined  $Z$ . Solving for  $f_2 - f_1$  gives a value of  $2 \times 1200/0.8$  or 3000 Hz. The resonant and effective antiresonant frequencies of each crystal should therefore be separated by half this amount or 1500 Hz. The resonant frequencies of the two sets of crystals should also differ by 1500 Hz. Table 1 lists

Table 1

Measured characteristics of the crystals used for the filter described below.  $f_{rs1}$  and  $f_{rs2}$  are spurious frequencies.

No.	$f_r$ (Hz)	$C_0$ (pf.)	$C_o$ (pf.)	$f_{rs1}$ (Hz)	atten. $f_{rs1}$ (dB.)	$f_{rs2}$ (Hz)	atten. $f_{rs2}$ (dB)
1	5502195	0.00380	14.7	5516800	>9	5559800	12
2	5502227	0.00356	12.3	5519900	13.5	5552000	15.5
3	5502212	0.00290	12.7	1	>15 <sup>2</sup>	1	>15 <sup>2</sup>
4	5503960	0.00334	12.3	5523000	9	5547200	9
5	5503927	0.00348	14.0	5536200	7	5570200	7.5
6	5503860	0.00311	13.8	1	>20 <sup>2</sup>	1	>20 <sup>2</sup>

<sup>1</sup>These frequencies were not recorded.

<sup>2</sup>Attenuation greater than figures shown.

the measured characteristics<sup>10</sup> of the crystals actually used. Crystals 1-3 are resonant near 5502.2 kHz; crystals 4-6 are near 5503.9 kHz, giving a separation of 1700 Hz.

The impedance of a filter such as this is given by the expression.<sup>11</sup>

$$R_o = \frac{1}{2\pi C_o'} \left( \frac{f_1}{f_1 f_2 - f_o^2} \right)$$

$C_o'$  is the shunt capacitance of the crystal plus the reflected circuit and tuning capacitance or about 47.7 pF as shown earlier.  $f_1$  is the resonant frequency of the lower-frequency crystals, 5502.2 kHz  $f_2$  is the antiresonant frequency of the higher-frequency crystals, which is 5503.9 kHz plus about 1500 Hz or 5505.4 kHz.  $f_o$  is 5060 kHz as calculated above. Putting these values into the equation gives a value of 3920 ohms for  $R_o$ . In a half lattice the termination should be  $R_o/2$  or 1960 ohms.

2000-ohm terminations are used with the filter that was built. Slight variations in the terminations from these values will affect the selectivity only a small amount and can be used to get almost flat passband response.

The effective parallel resistance of the coils is about ten times the filter impedance and has negligible effect on the filter characteristics.<sup>12</sup>

Fig. 12 is a diagram of the complete filter. The first two sections are connected "back-to-back," and full interaction takes place. The 300-ohm resistor between sections two and three reduces interaction and smooths the passband response as shown above. The leakage reactance between the two halves of L2 and L3 is tuned out by the capacitors connected in series with the center taps of these coils. L1 and L4, the input and output coils, resonant with the calculated value of terminating capacitance at 5060 kHz and effectively reflect the needed inductance across the crystals. The 2000-ohm resistors complete the termination called for by the design equations.

All the crystals were purchased as 5500-kHz FT-243s and etched to the desired frequencies with hydrofluoric acid. It is best to wash each crystal with soap and water and measure its frequency before etching. The crystals in each set of

three should be as close to each other in frequency as possible, and the separation between the two groups should be about 1500 Hz. A simple comparator circuit<sup>13</sup> will allow two crystals to be checked simultaneously and compared, using an oscilloscope and audio oscillator to measure the frequency separation.

Tuning the filter is quite simple since all four adjustments can be peaked for maximum output at a fixed alignment frequency. This frequency should be on the high side of the passband and can be the carrier frequency used for lower sideband transmission (5505.5 Hz in the case of the filter described). Using the carrier frequency it is only necessary to unbalance the balanced modulator to obtain a cw alignment signal. Of course, a signal generator and rf probe-equipped VTVM can also be used. C1, C2, L1 and L4 are simply adjusted for maximum output.

<sup>10</sup>Shunt capacitance  $C_o$  can be found by connecting a small capacitance,  $C_1$ , in series with the crystal and measuring the shift in resonant frequency. The resonant frequency of the crystal alone is

$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

If  $f_{r1}$  is the resonant frequency of the crystal and C combined, then

$$f_{r1} = f_r^2 \left( 1 + \frac{C}{C_1 + C_o} \right)$$

Since  $\frac{C}{C_1 + C_o}$  is much less than 1,

$$f_{r1} - f_r \approx \frac{f_r}{2} \left( \frac{C}{C_1 + C_o} \right)$$

or

$$C = 2 \frac{\Delta f}{f_r} (C_1 + C_o)$$

where  $\Delta f$  is the difference ( $f_{r1} - f_r$ ) between the resonant frequencies.

<sup>11</sup>A simpler expression can actually be used for the filter under consideration.

$$R_o = \frac{1}{2\pi f_o C_o}$$

where  $f_o$  is the center frequency of the filter, and  $C_o$  is the effective capacitance required (7.35 pF in this case) so that the correct  $f_a - f_r$  is exhibited by the crystal.

<sup>12</sup>The input and output coils will have little effect on the impedance of the filter if  $2\pi Q f_o L$  or  $(Q/2f_o C)$  is large compared to  $R_o/2$ .  $Q$  and  $L$  are the  $Q$  and inductance of the coil,  $C$  is the capacitance across the coil,  $f_o$  is the center frequency and  $R_o/2$  is the terminating resistance. This requirement is usually met in hf filters such as the one described. At lower frequencies such as 450 Hz, the required  $R_o/2$  is higher. Then the terminating resistor must be chosen so that it and the effective resistance of the coil in parallel will give the desired termination.

<sup>13</sup>Clark, "Hints & Kinks," QST, December, 1959.



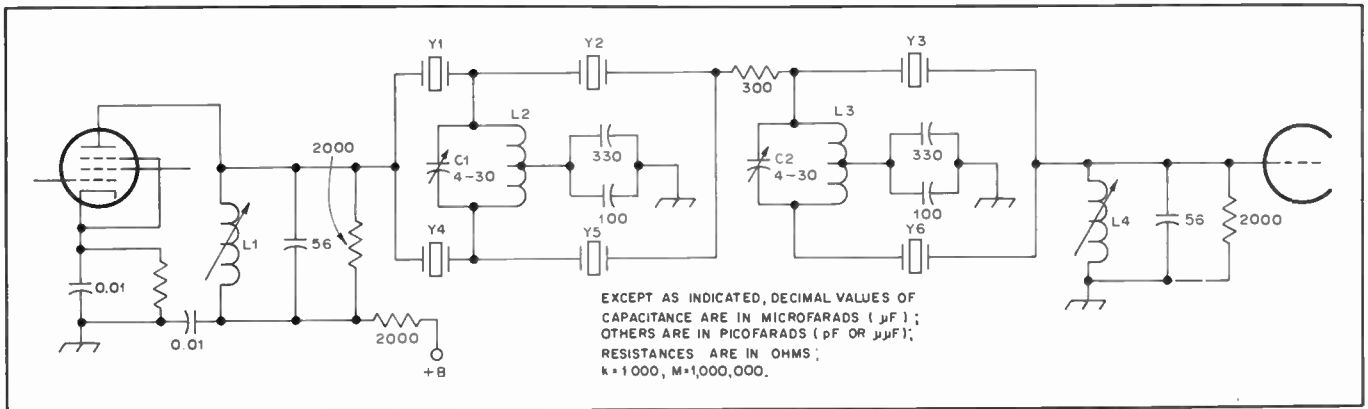


Fig. 12 — Circuit diagram of a filter designed according to the methods of this article. Resistances are in ohms, and resistors are 1/2-watt composition; capacitors are disk ceramic except at noted. C1, C2 — 4-30-pF mica trimmer. L1, L4 — 50 turns no. 38 enamel, close-wound on 17/64-inch (6.7-mm) diam. ceramic slug-tuned form, CTC LS-6, National XR-81 or similar. L2, L3 — 60 turns no. 38 enamel, close-wound on 17/64-inch (6.7-mm) ceramic form, CTC LS-6, National XR-81 or similar with powdered-iron core removed, center tapped. Y1, Y2, Y3 — All same frequency (near 5500 kHz). Y4, Y5, Y6 — All same frequency and 1500 to 1700 Hz different from Y1, Y2, Y3.

A slightly better shape factor can be had by detuning the carrier oscillator to a lower alignment frequency corresponding to about the 4-dB-down point on the high-frequency side of the passband. Fig. 13 shows the measured performance of the filter when aligned at 5502.2 kHz. The 6-dB bandwidth is 2750 Hz, somewhat greater than the 2400-Hz design figure because the average spacing of the crystal pairs used was 1700 Hz instead of 1500 Hz. At 30 dB down, the bandwidth is 3950 kHz, so the 30 dB/6 dB-shape factor is 1.44. This agrees well with the theoretical value of 1.49 from Fig. 10.

The spurious crystal responses occur as indicated in Table 1, but the overall filter exhibited more than 52-dB attenuation at the nearest spurious frequency (5516.800 kHz). The others could not be measured since they were attenuated more than 60 dB, which attenuation level was beyond the capability of the measuring setup used.

It should be noted that this filter is better used to pass the lower sideband than the upper one. When aligned at the 5505.5-kHz carrier frequency, the filter provides 20 dB of carrier attenuation with a 6-dB down audio passband which extends from 300 to 2800 Hz. The undesired upper sideband is attenuated more than 40 dB for all audio frequencies above 350 Hz.

If the filter is aligned at 5505.2 kHz, and the carrier set at 5505.6 kHz, carrier suppression is 19 dB for a 6-dB audio passband of 300-3050 Hz. Upper-sideband suppression is better than 40 dB for audio above 300 Hz.

The cutoff on the low-frequency side of the band is somewhat less steep than on the high side. This is believed to be due to the use of less than ideal coupling coils between the filter sections. Using an alignment frequency of 5505.5 kHz and a carrier frequency of 5502.2 kHz, the upper

sideband audio pass band is 450-2950 Hz for 20-dB carrier suppression. Undesired sideband attenuation is greater than 30 dB for audio above 350 Hz and greater than 40 dB for audio above 750 Hz.

When the filter is aligned at 5505.2 kHz and the carrier is placed at 5502.1 kHz, the audio passband is 400-3200 Hz for 20-dB carrier attenuation. Lower-sideband suppression will be more than 30 and 40 dB for audio frequencies above 300 and 700 Hz, respectively.

### Surplus-Crystal High-Frequency Filters

This treatise, which was written by Vester, W3TLN, shows how to reduce costs when building homemade filters. The techniques apply, of course, when new crystals are used as well.

An article by Kosowsky<sup>14</sup> boils a lot of "long-hair" literature on crystal-lattice theory into a fairly simple and understandable form. One of the most interesting points was the fact that the crystal filter designer considers the narrow-band high-frequency crystal filter for ssb to be the "easy" design — the problem getting much more exotic for the wide-band high-frequency filter. Since W3HEC was already tackling the tough problem of making a good low-frequency filter with the FT-243 crystals, the author took the easy way out by trying the high-frequency unit.

### Some Background

If you're planning to try your hand at it, it will help if you grab a few fundamental concepts on crystal lattice filters first. The properties of the crystal itself are pretty well known, the approximate equivalent circuit being shown in Fig. 14 and the change of reactance or impedance being shown in Fig. 15. The crystal has two resonances very close together, L and C

being in series resonance at  $f_s$ , and L, C and  $C_0$  being parallel resonant at  $f_p$ . These resonances have been given names by the network theory boys, the series resonance being called a "zero" of impedance (for obvious reasons) and the

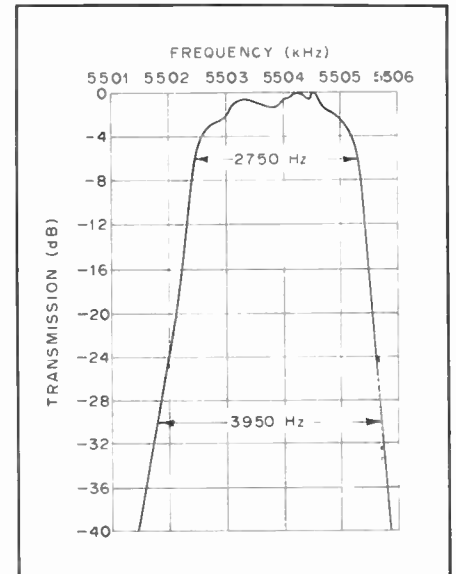


Fig. 13 — Measured selectivity characteristic of the filter described in this article when aligned at 5505.2 kHz. The 6-dB bandwidth is 2750 Hz and the 30 dB/6 dB shape factor is 1.44.

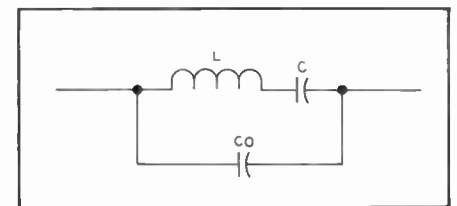


Fig. 14 — The equivalent circuit of a crystal. L and C are the electrical equivalents of mechanical constants of the crystal, while  $C_0$  is the shunting capacitance of the electrodes and holder.

<sup>14</sup>Kosowsky, "High Frequency Crystal Filter Design Techniques and Applications," *Proceedings of the IRE*, February, 1958.

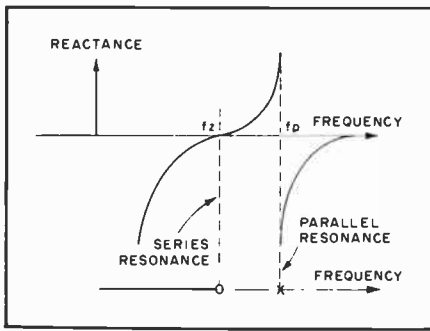


Fig. 15 — Reactance characteristics of a crystal. The series-resonant frequency,  $f_z$ , is that of L and C (Fig. 14) in series; the parallel-resonant frequency,  $f_p$ , is the resonant frequency of the parallel circuit formed by L and C in one branch and  $C_0$  in the other.

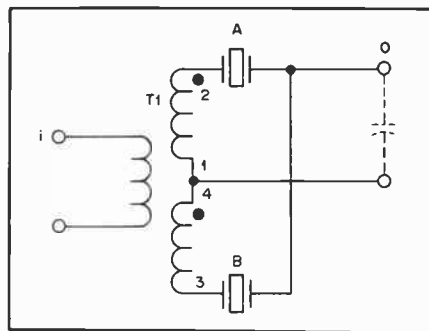


Fig. 16 — The half-lattice crystal filter. Crystals A and B should be chosen so that the parallel-resonant frequency of one is the same as the series-resonant frequency of the other. Very tight coupling between the two halves of the secondary of T1, is required for optimum results.

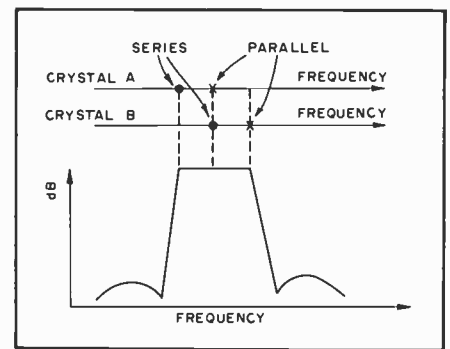


Fig. 17 — The theoretical attenuation-vs.-frequency curve of a half-lattice filter shows a flat passband between the lower series-resonant frequency and higher parallel-resonant frequency of the pair of crystals.

parallel resonance being called a "pole" of impedance. The symbols used for these are shown on Fig. 15. These poles and zeros are mighty convenient little symbols for handling networks, the most convenient part being the fact that if you have a circuit with several poles and zeros, you can often manipulate the circuit values so as to get some of the zeros each to cancel out a pole. Hence, a circuit with a multitude of resonances (or poles and zeros) can be arranged to have its response equivalent to only a few resonances.

The universal crystal filter is a lattice circuit. The lattice is usually developed in full "four-arm" form (i.e., as a bridge circuit) and then the equivalence of the half-lattice is proved. The reader is referred to Kosowsky's article and its bibliography for the full treatment on this. We will settle for a few statements on crystal lattice filters which have been adequately proven by others. Consider the simple one-section half lattice shown in Fig. 16. The first important point to consider is that the only way in which the lattice can give a high insertion loss between input and output is for the impedances of A and B to be about equal, so that the voltage at their common connection (point 0) is equal to the voltage at the coil center tap. Our crystals will meet the requirement pretty well if they have the same holder capacitance, so the primary problem is to build the coil so that the voltage from Terminals 1 to 2 is exactly the same as the voltage from 3 and 4. The method for realizing this will be discussed a little later.

Crystals A and B are chosen to be different in frequency for the half lattice. Thus it is obvious that if we are at a zero (series resonant) frequency of, say, crystal A, the impedance balance of A and B is spoiled and there is a voltage showing up between point 0 and the center of the coil. This will also occur at the pole (parallel resonant) frequency of crystal A. The same can be said for crystal B, only the unbalance is in the opposite direction.

This leads us directly into the statement that the passband of the crystal filter will be as wide as the spacing of all the poles and zeros. This says nothing about the ripple or variation in transmission in the passband, however, and if A and B are far apart the ripple or dip may be tremendous. Here's where the network theory boys' trick of pairing off poles and zeros comes in handy. A little study with Fig. 15 of the way in which the impedance change around a zero differs from that around a pole will give an idea how the lattice crystals can be arranged to give a flat passband. Fig. 17 shows the desired arrangement. The series-resonant frequency of crystal B is arranged to coincide with the parallel-resonant frequency of crystal A. This will theoretically give a perfectly flat passband from the zero of crystal A to the pole of crystal B.

The problem is now resolved down to determining the pole-zero spacing for the available crystals. The surplus FT-243 crystals in the 5-MHz range (this choice of frequency was obviously based on the excellent results being obtained with the popular HT-32 transmitter) have a measured spacing of about 2.2 kHz between their series- and parallel-resonant frequencies. Thus, two of them spaced 2.2 kHz apart in frequency are theoretically capable of giving a 4.4-kHz bandwidth. Practically, it is very difficult to get quite this much bandwidth.

If we examine the effects that the external coupling circuitry has on the pole-zero spacing, it can be shown that both an increase and a decrease in the spacing can be accomplished by shunting inductance or capacitance, respectively, across the crystal. The most familiar example of this to most of us is in pulling a crystal oscillator's frequency by shunting a capacitor across the crystal. This technique, you will remember, only works where the crystal is being used in its parallel-resonant mode. Referring back to Fig. 14, it is easily seen that a parallel capacitor makes  $C_0$  larger and lowers the parallel-resonant frequency (pole). It will

not affect the series-resonant frequency (zero), so the effect of the parallel capacitor is to move the pole closer to the zero. Similarly, it can be shown that an inductance shunted around the crystal will push the pole away from the zero; unfortunately, however, this also introduces a second parallel-resonant frequency. Even the network theory boys begin to sweat a little when they begin to manipulate this many poles and zeros in a lattice circuit, so we hams had better avoid the complications, and shy away from trying to add tuned inductors on the input and output of the filter. If we are forced to use an inductor, we will make its inductance large enough to avoid its resonating with  $C_0$  anywhere near the desired passband.

#### Preliminary Measurements

Now that we have some ideas as to how crystal filters work, we will get more specific and look at the procedure by which one may be evolved. To measure the spacing between the series- and parallel-resonant frequencies, we must be careful to avoid having the test circuit put shunt capacitance across the crystal and give erroneous results. The circuit in Fig. 18 was used by the writer. To eliminate the extra shunt capacitance that a socket would add, the crystal holders were soldered directly into the circuit. The signal generator can be most any kind, so long as it has a slow tuning rate — the author used one of the Command transmitters (WW II surplus). The measurement detector can be a scope, a VTVM (with rf probe), or the station receiver. The low resistance, R2 across it should swamp out any small amount of input capacitance it might have. If a receiver is used, a 1000 or 2000-ohm resistor should probably be put in series with its input to isolate the crystal from the receiver front-end tuned circuits. The series- and parallel-resonant frequencies are, of course, at the peak and null of the signal across R2. Any decent communications receiver will measure the frequency difference; best

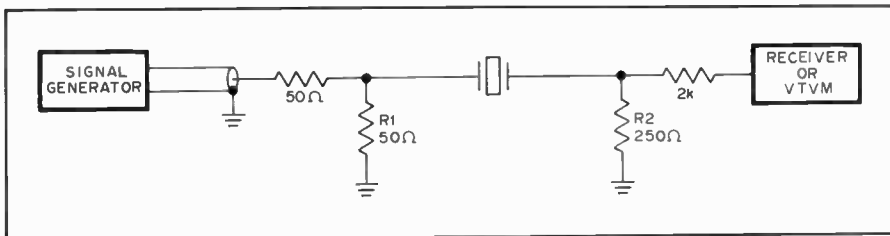


Fig. 18 — Setup for measuring the series- and parallel-resonant frequencies (or pole-zero spacing) of a crystal.

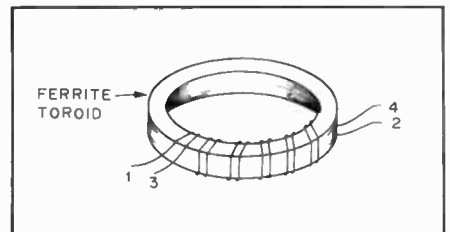


Fig. 19 — Bifilar winding on a toroidal core.

accuracy is obtained by measuring the harmonics of the generator with the receiver in the sharp crystal-filter position.<sup>15</sup>

Initial measurements of the two 5645-kHz crystals showed a pole-to-zero spacing of 2.2 kHz on one and 2.4 kHz on the other. Their series-resonant frequencies were about 500 hertz apart. It was decided to try these first to get a bearing on the problem.

As indicated earlier, the push-pull coil must have very tight coupling between its two secondaries and should be chosen with a high enough inductance to avoid resonance with the crystal shunt capacitance near the passband. A 3/4-inch (19-mm) ferrite toroid was used (origin and properties unknown), with the secondaries wound bifilar. The bifilar winding is illustrated in Fig. 19. The enclosed LS series coils made by CTC probably would work just as well. (It would probably be very difficult to get tight enough coupling with air-wound coils, however.) The writer arbitrarily made each half of the secondary coil with an inductance of 50 microhenrys; this required 25 bifilar turns, to 50 turns total. The exact inductance is not at all crucial — the important thing is the tight coupling.

#### Experimental Results

A filter was constructed with the circuit shown in Fig. 16. It was fed from a low impedance and its output was fed into a 6AK5 mixer grid, the mixer grid effectively shunting some capacitance across the crystals. This mixer was used to beat the filter output signal into a range which was covered by the author's receiver (a 75A-3) so it could be used for both dB and frequency measurements. The initial response was as shown by curve A in Fig. 20. A 10-kΩ resistor was then added to

terminate the filter and the response squared up (as shown by curve B) to give a passable 1-kHz high-frequency filter.

This was sufficiently encouraging, so an ammonium bifluoride<sup>16</sup> etching bath was dug out from its hiding place and the upper-frequency crystals were moved to a frequency 1500 Hz above the lower frequency (W2IHW's technique for etching crystals is really simple).

The initial results with this were anything but encouraging. Curve C in Fig. 21 illustrates the results. It was obvious that the capacitance across the lattice output had shoved the poles too close to the zeros, or else the 0.5-MΩ terminating resistor was improper. The writer tried tuning the capacitance out with a slug-tuned coil and got all kinds of interesting results (curve D in Fig. 21 is typical), none of them usable. When the writer terminated the filter with lower values of resistance, however, the results improved markedly. With just the right resistor, 1500 ohms in this case, the passband was flat over a reasonable width. Curve E in Fig. 22 shows the final results. The bandwidth is just barely great enough for phone use.

Since this writer had one other 5645-kHz crystal which was 300 Hz from one of the original crystals, it was substituted and curve F in Fig. 22 was obtained. This time a 3900-ohm terminating resistor gave the flattest passband.

If greater rejection off the skirts is required, there are several ways in which these sections can be cascaded. A simple technique is to connect them back-to-back as shown in Fig. 23. This method of connection will minimize spurious off-frequency response since the probability of getting the spurious responses of crystals A and B to line up with those of crystals A' and B' is pretty small. The coil, L1 is again would bifilar and R1 and R2 are chosen experimentally for the best passband. The crystals should be matched as closely as you can read their frequency — this is pretty easy with the etching technique. Fig. 24 shows the response received from four 7300-kHz crystals, connected like Fig. 23 (crystals A and A' were 1.5 kHz higher than B and B'). The same bifilar coil was used.

By measuring the spacing between series and parallel resonance of a few of the other surplus crystals that were lying

around the following results were obtained:

Crystal Freq. kHz	Type	Pole-Zero Spacing kHz
8725	FT-243	2.7 kHz
7250	FT-243	2.3 kHz
7380	Plated-surplus	5 kHz
7010	Plated-surplus	6 kHz
8900	Plated-harmonic cut	20 kHz

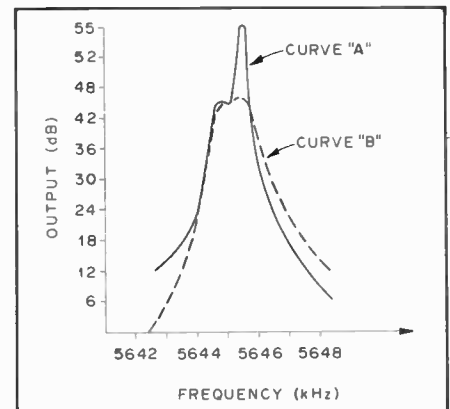


Fig. 20 — Measured attenuation curves of a half-lattice filter using two nominal 5645-kHz crystals having series-resonant frequencies separated by 560 Hz. A — without resistance termination; B — with 10-kΩ terminating resistor. In taking the data for these curves and those shown in Figs. 21, 22 and 24, the attenuation was based on the manufacturer's calibration of the receiver used in the tests.

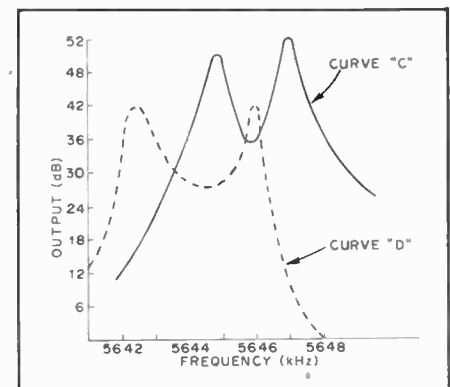


Fig. 21 — Attenuation curves of half-lattice filter with crystals of the same nominal frequency as in Fig. 20 but with 1.5-kHz separation. C — with 0.5-megohm terminating resistor; D — shunt coil added across the output to resonate with capacitance present at that point.

<sup>15</sup>i.e., after adjusting the generator to the series-resonant frequency, let the generator alone and shift the receiver to some higher range where a generator harmonic can be heard and its frequency measured. Then shift back to the fundamental frequency, adjust the generator to the parallel-resonant frequency, shift the receiver again and then measure the generator harmonic adjacent to the first one. The frequency separation between the crystals is of course equal to the frequency difference between the harmonics divided by the order of the harmonic. This method usually will give improved accuracy only if the receiver calibration can be read to the same accuracy — e.g., 1 kHz per dial division — on the harmonic range as on the fundamental. — Ed. <sup>16</sup>Newland, "A Safe Method for Etching Crystals" *QST*, January, 1958.



The plated crystals will give wider-band filters.

If you're interested in an asymmetrical filter which has a gradual fall-off on one side, then the circuit shown in Fig. 25 can be used. Here both the crystals are on exactly the same frequency. The coils are again bifilar and C is tuned to give the desired passband. The potential bandwidth here is only half that obtained with the half-lattice. It should work nicely with the plated crystals, however.

### Phasing Method

The second system is based on the phase relationships between the carrier and sidebands in a modulated signal. As shown in Fig. 2, the audio signal is split into two components that are identical except for a phase difference of 90 degrees. The output of the rf oscillator (which may be at the operating frequency, if desired) is likewise split into two separate components having a 90-degree phase difference. One rf and one audio component are combined in each of two separate

balanced modulators. The carrier is suppressed in the modulators, and the relative phases of the sidebands are such that one sideband is balanced out and the other is augmented in the combined output. If the output from the balanced modulators is high enough, such an ssb exciter can work directly into the antenna, or the power level can be increased in a following amplifier.

Generally, the filter-type exciter is easier to adjust than is the phasing exciter. Most home-built ssb equipment uses commercially made filters these days. The alignment is done at the factory, thus relieving the amateur of the sometimes tedious task of adjusting the filter for suitable band-pass characteristics. Filter-type exciters are more popular than phasing units and offer better carrier suppression and alignment stability. It is still practical for the builder to fabricate his own crystal-lattice filter by utilizing low-cost surplus crystals. This possibility should not be overlooked if the builder is interested in keeping the overall cost of the home-built exciter at a minimum.

### Balanced Modulators

The carrier can be suppressed or nearly eliminated by using a balanced modulator or an extremely sharp filter. In ssb transmitters it is common practice to use both devices. The basic principle of any balanced modulator is to introduce the carrier in such a way that it does not appear in the output, but so that the sidebands will. The type of balanced-modulator circuit chosen by the builder will depend upon the constructional considerations, cost, and whether diodes or transistors are to be employed.

In any balanced-modulator circuit there will be no output with no audio signal. When audio is applied, the balance is upset, and one branch will conduct more than the other. Since any modulation process is the same as "mixing" in receivers, sum and difference frequencies

(sidebands) will be generated. The modulator is not balanced for the sidebands, and they will appear in the output.

In the rectifier-type balanced modulators shown in Fig. 26, at A and B, the diode rectifiers are connected in such a manner that, if they have equal forward resistances, no rf can pass from the carrier source to the output circuit via either of the two possible paths. The net effect is that no rf energy appears in the output.

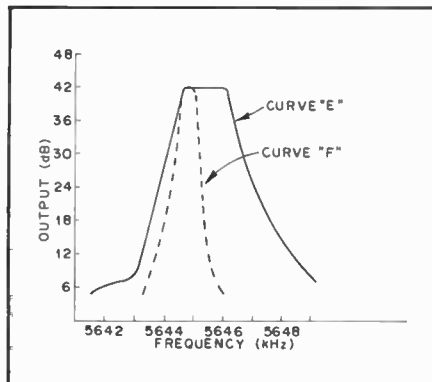


Fig. 22 — E — half-lattice filter using same crystals as in Fig. 21, with 1500-ohm terminating resistor. F — using two nominal 5645-kHz crystals separated 300 Hz, with 3900-ohm terminating resistor.

Fig. 23 — Half-lattice filters cascaded in a back-to-back arrangement. The theoretical curve of such a filter has increased skirt selectivity and fewer spurious responses, as compared with a simple half lattice, but the same passband as the simple circuit.



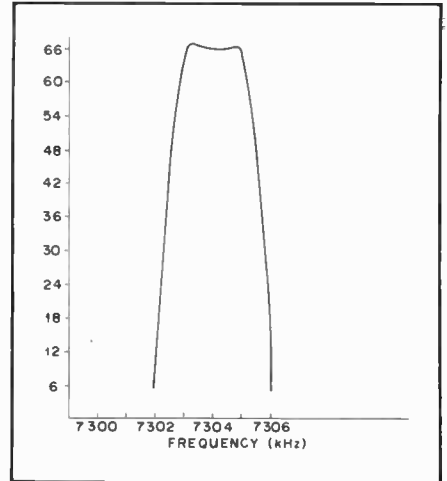


Fig. 24 — Attenuation curve of filter using four nominal 7300-kHz crystals, pairs separated 1.5 kHz, in the circuit of Fig. 23.

Fig. 25 — An asymmetrical filter and theoretical attenuation curve.

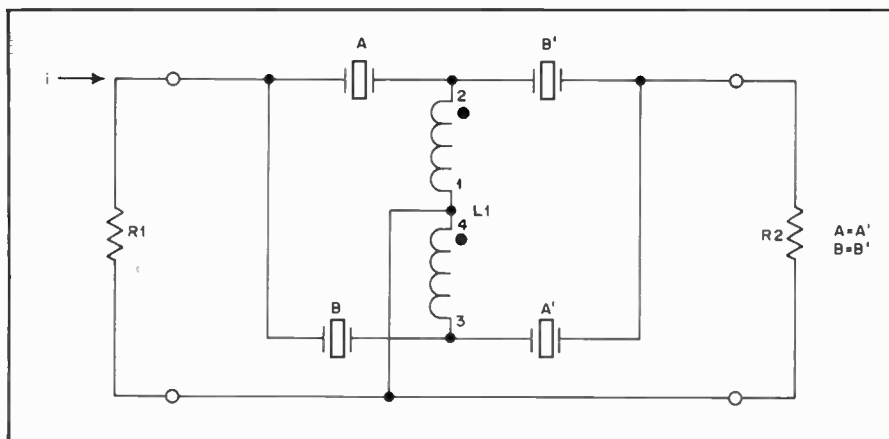

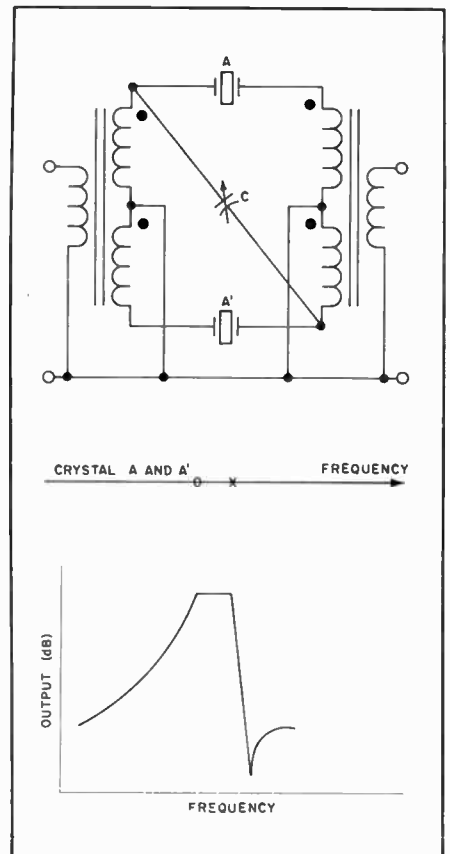

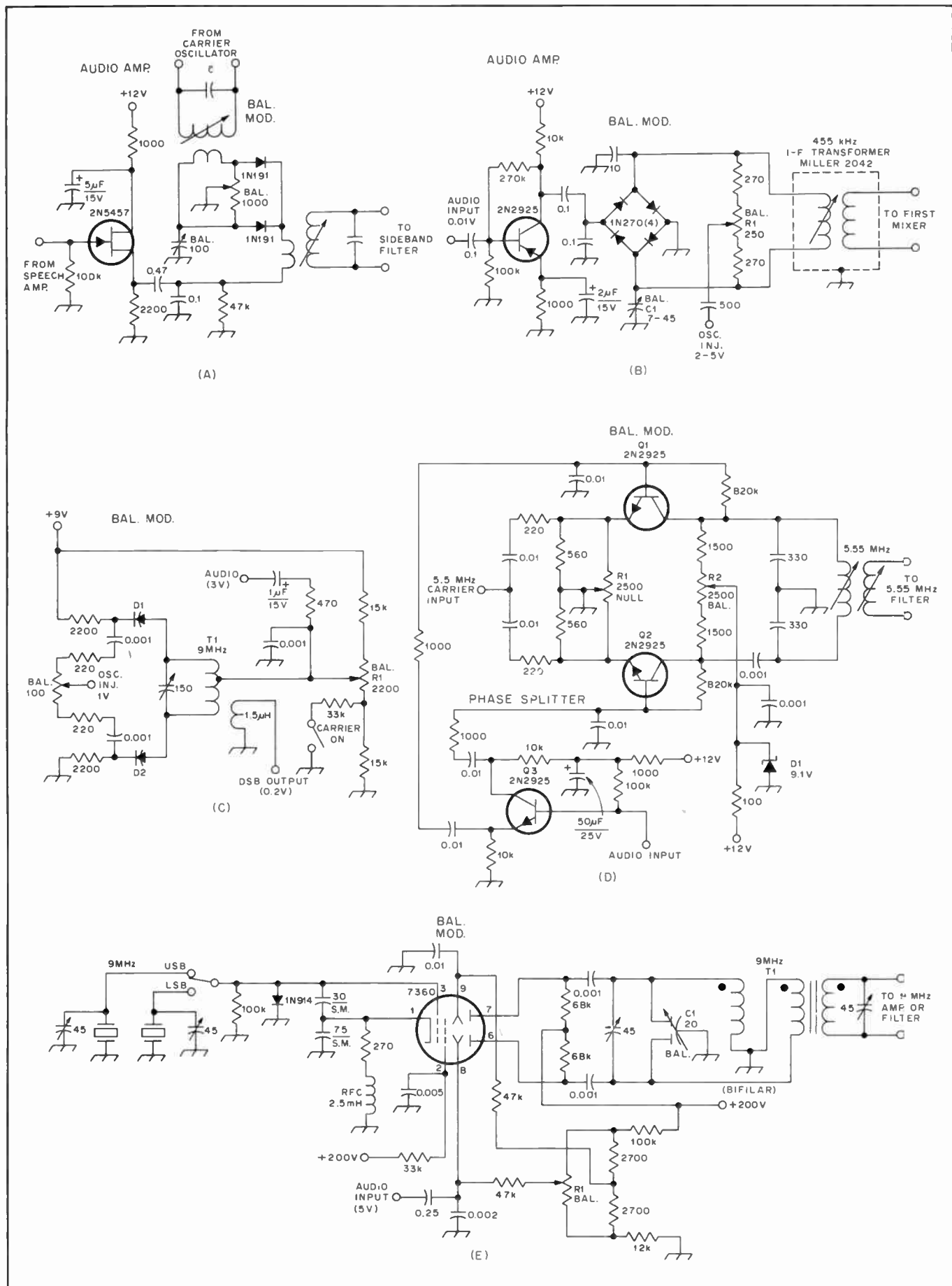


Fig. 26 — Typical circuits of balanced modulators. Representative parts values are given and should serve as a basis for designing one's own equipment.

When audio is applied, it unbalances the circuit by biasing the diode (or diodes) in one path, depending upon the instantaneous polarity of the audio, and hence some rf will appear in the output. The rf in the output will appear as a double-sideband suppressed-carrier signal.

In any diode modulator, the rf voltage should be at least six to eight times the peak audio voltage for minimum dis-

tortion. The usual operation involves a fraction of a volt of audio and several volts of rf. Desirable diode characteristics for balanced modulator and mixer service include: low noise, low forward resistance, high reverse resistance, good temperature stability, and fast switching time (for high-frequency operation). Fig. 27 lists the different classes of diodes, giving the ratio of forward-to-reverse resistance of each. This ratio is an important criterion in the selection of diodes. Also, the individual diodes used should have closely matched forward and reverse resistances; an ohmmeter can be used to select matched pairs or quads.

One of the simplest diode balanced modulators in use is that of Fig. 26A. Its use is usually limited to low-cost portable equipment in which a high degree of carrier suppression is not vital. A ring balanced modulator, shown in Fig. 26B, offers good carrier suppression at low cost. Diodes D1 through D4 should be well matched and can be 1N270s or similar. C1 is adjusted for best rf phase

balance as evidenced by maximum carrier null. R1 is also adjusted for the best carrier null obtainable. It may be necessary to adjust each control several times to secure optimum suppression.

Varactor diodes are part of the unusual circuit shown in Fig. 26C. This arrangement allows single-ended input of near-equal levels of audio and carrier oscillator. Excellent carrier suppression, 50 dB or more, and a simple method of unbalancing the modulator for cw operation are features of this design. D1 and D2 should be rated at 20 pF for a bias of -4 V. R1 can be adjusted to cancel any mismatch in the diode characteristics, so it isn't necessary that the varactors be well matched. T1 is wound on a small-diameter toroid core. The tap on the primary winding of this transformer is at the center of the winding.

A bipolar-transistor balanced modulator is shown in 26D. This circuit is similar to one used by Galaxy Electronics and uses closely matched transistors at Q1 and Q2. A phase splitter (inverter) Q3, is used to feed audio to the balanced modulator in push-pull. The carrier is supplied to the circuit in parallel and the output is taken in push-pull. D1 is a Zener diode and is used to stabilize the dc voltage. Controls R1 and R2 are adjusted for best carrier suppression.

The circuit at E offers superior carrier suppression and uses a 7360 beam-deflection tube as a balanced modulator. This tube is capable of providing as much as 60 dB of carrier suppression. When used with mechanical or crystal-lattice filters the total carrier suppression can be as great as 80 dB. Most well-designed balanced modulators can provide between 30 and 50 dB of carrier suppression; hence the 7360 circuit is highly desirable for optimum results. The primary of transformer T1 should be bifilar wound for best results.

Diode Type	Ratio M = 1,000,000
Point-contact germanium (1N98)	500
Small-junction germanium (1N270)	0.1 M
Low-conductance silicon (1N457)	48 M
High-conductance silicon (1N645)	480 M
Hot-carrier (HPA-2800)	2000 M

Fig. 27 — Table showing the forward-to-reverse resistance ratio for the different classes of solid-state diodes.


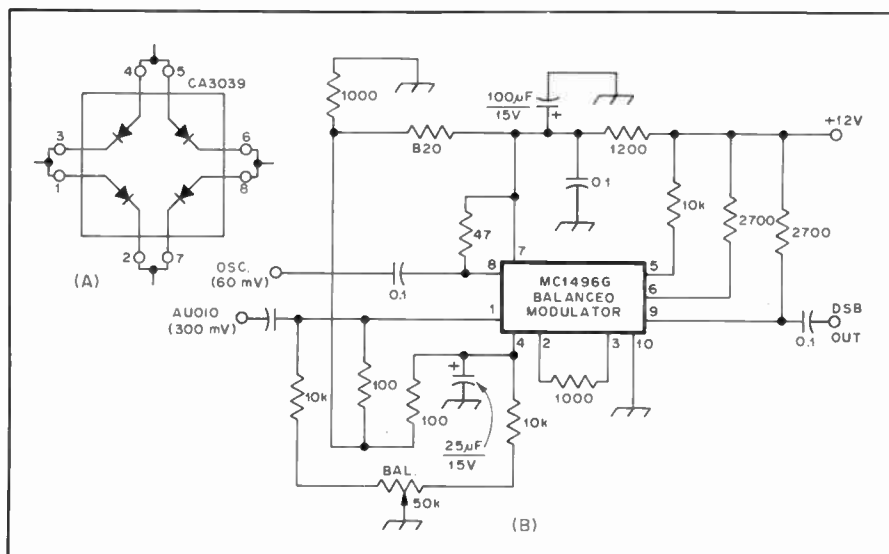


Fig. 28 — Additional balanced-modulator circuits in which integrated circuits are used.

Fig. 29 — Balanced modulator design using hot-carrier diodes.

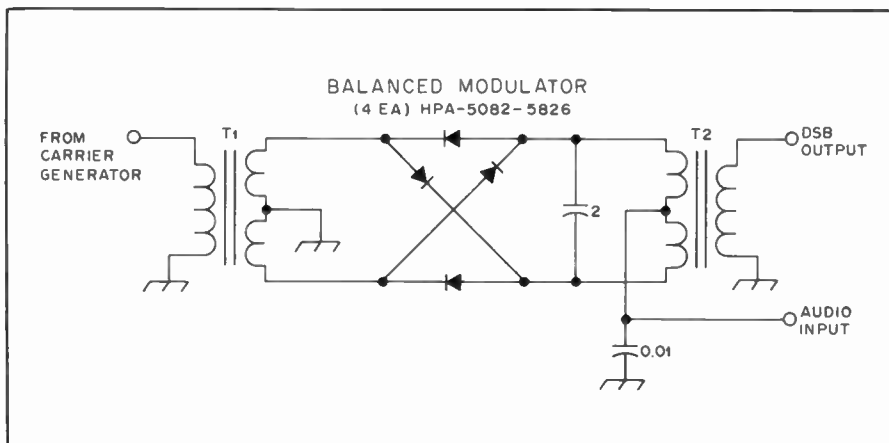

### IC Balanced Modulators

Integrated circuits (ICs) are presently available for use in balanced-modulator and mixer circuits. A diode array such as the RCA CA3039 is ideally suited for use in circuits such as that of Fig. 28A. Since all diodes are formed on a common silicon chip, their characteristics are extremely well matched. This fact makes the IC ideal in a circuit where good balance is required. The hot-carrier diode also has closely matched characteristics and excellent temperature stability. Using broadband toroidal-wound transformers, it is possible to construct a circuit similar to that of Fig. 29 which will have 40 dB of carrier suppression without the need for balance controls. T1 and T2 consist of trifilar windings, 12 turns of no. 32 enam. wire wound on a 1/2-inch (13-mm) toroid core. Another device with good inherent balance is the special IC made for modulator/mixer service, such as the

Motorola MC1496G or Signetics S5596. A sample circuit using the MC1496 can be seen in Fig. 28B. R1 is adjusted for best carrier balance. The amount of energy delivered from the carrier generator effects the level of carrier suppression; 100 mV of injection is about optimum, producing up to 55 dB of carrier suppression. Additional information on balanced modulators and other ssb-generator circuits is given in the texts referenced at the end of this chapter.

### Using Commercial Crystal Filters

Some builders may not have adequate testing facilities for building and aligning their own filters. In such instances it is possible to purchase ready-made units which are prealigned and come equipped with crystals for upper-and lower-sideband use. Spectrum International<sup>17</sup> has two types for use at 9 MHz. Another manufacturer, McCoy Electronics Co.,<sup>18</sup> sells 9-MHz models for amateur use, and other filters are available surplus.<sup>19</sup>

### Mechanical Filters

Mechanical filters contain elements that vibrate and establish resonance mechanically. In crystal filters the coupling between filter sections is achieved by electrical means. In mechanical filters, mechanical couplers are used to transfer the vibrations from one resonant section to the next. At the input and output ends of the filter are transducers which provide for electrical coupling to and from the filter. Most mechanical filters are designed for use from 200 to 600 kHz, the range near 455 kHz being the most popular for amateur use. Mechanical filters suitable for Amateur Radio circuits are manufactured by the Collins Radio Co. and can be purchased from some dealers in Amateur Radio equipment.

### Filter Applications

Methods for using typical sideband filters are shown schematically in Fig. 30. In the circuit of Fig. 30A a 455-kHz mechanical filter is coupled to the balanced modulator by means of two dc isolating capacitors. C1 is used to tune the input of FL1 to resonance (if a Collins type 455-FB-21 is used). Frequently, a fixed-value 120-pF capacitor will suffice at each end of the filter. C2 tunes the output of the filter. A stage of i-f amplification usually follows the filter, as shown, to compensate for the insertion loss of the filter and to provide a stage to which agc can be applied for alc (automatic level control) purposes. In the circuit shown the operator can ground R1 if alc is not used. R2 can be lifted from ground and a 5000-ohm control can be

placed between it and ground to provide a means of manual gain control for providing the desired signal level to the mixer.

The circuit of Fig. 30B uses a 9-MHz crystal filter, followed by an IC i-f amplifier. Either the McCoy or Spectrum International filters are suitable. Most commercial ssb filters are supplied with a data sheet which shows recommended input and output circuits for matching the impedance of the filter. All are adaptable to use with tubes or transistors.


Another circuit which uses an hf crystal filter, preceded by a dual-gate MOSFET

operating as an rf speech clipper, is shown in Fig. 30C. The advantages of rf clipping are explained later in this chapter. A second MOSFET amplifies the signal from the filter and provides a variable level of output which is controlled by the alc line.

### Carrier Oscillator

The ssb-generation process starts with a crystal-controlled oscillator, as shown in Fig. 2. In a filter-type generator, the oscillator frequency is set on the low-frequency side of the filter bandpass to produce upper sideband and on the upper

Fig. 30 — Typical circuits showing how ssb filters are connected in the circuit.

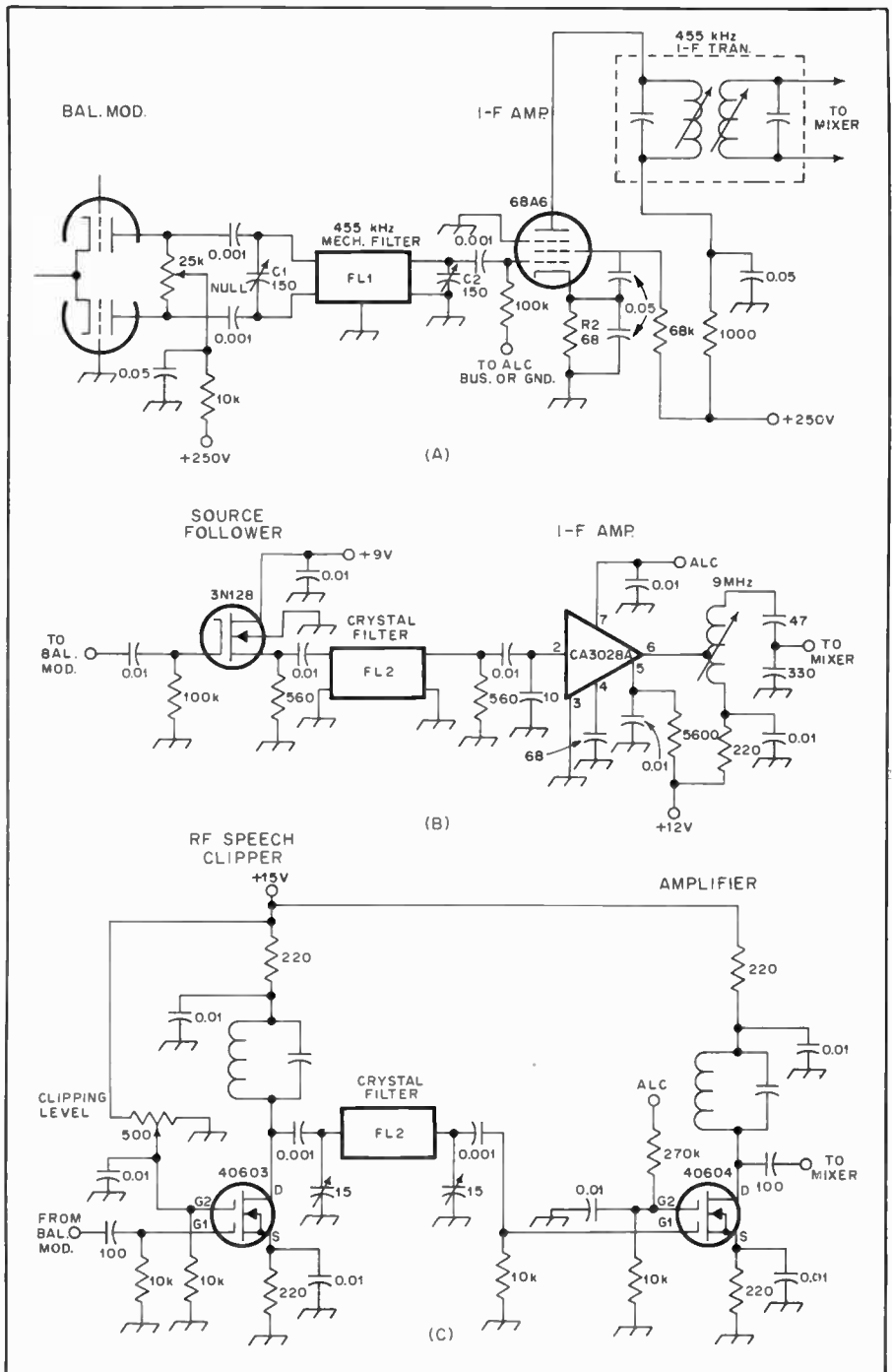

<sup>17</sup>Spectrum International, P.O. Box 1084, Concord, MA 01742. Tel. 617-263-2145.

<sup>18</sup>McCoy Electronics Co., Mt. Holly Springs, PA 17065. Tel. 717-486-3411.

<sup>19</sup>E. S. Electronic Labs, Box 434, Excelsior Springs, MO 64024.

side when lower-sideband operation is desired. Suitable oscillator circuits are shown in chapter 6.

### Mixer

A single-sideband signal, unlike fm or cw, cannot be frequency multiplied. One or more mixer stages are employed in an ssb exciter to heterodyne the output of a fixed-frequency ssb generator to the desired operating frequency. See chapter 8 for details of mixer design and sample mixer circuits.

### The Speech Amplifier

The purpose of a speech amplifier is to raise the level of audio output from a microphone to that required by the modulator of a transmitter. In ssb and fm transmitters the modulation process takes place at low levels, so only a few volts of audio are necessary. One or two simple

voltage-amplifier stages will suffice. A-m transmitters often employ high-level plate modulation requiring considerable audio power, compared to ssb and fm. The microphone-input and audio voltage-amplifier circuits are similar in all three types of phone transmitters, however.

When designing speech equipment it is necessary to know (1) the amount of audio power the modulation system must furnish, and (2) the output voltage developed by the microphone when it is spoken into from normal distance (a few inches) with ordinary loudness. It then becomes possible to choose the number and type of amplifier stages needed to generate the required audio power without overloading or undue distortion anywhere in the system.

### Microphones

The level of a microphone is its electrical output for a given sound intensity. The level varies somewhat with the type. It depends to a large extent on the distance from the sound source and the intensity of the speaker's voice. Most commercial transmitters are designed for the median level. If a high-level mic is used, care should be taken not to overload the input amplifier stage. Conversely, a microphone of too low a level must be boosted by a preamplifier.

The frequency response (fidelity) of a microphone is its ability to convert sound uniformly into alternating current. For high articulation it is desirable to reproduce a frequency range of 200-3500 Hz. When all frequencies are reproduced equally, the microphone is considered "flat." Flat response is highly desirable as peaks (sharp rises in the reproduction curve) limit the swing or modulation to the maximum drive voltage, whereas the usable energy is contained in the flat part of the curve.

Microphones are generally omnidirectional, and respond to sound from all directions, or unidirectional, picking up sound from one direction. If a microphone is to be used close to the operator's mouth, an omnidirectional microphone is ideal. If, however, speech is generated a foot (0.31 m) or more from the microphone, a unidirectional microphone will reduce reverberation by a factor of 1.7:1. Some types of unidirectional microphones have proximity effect in that low frequencies are accentuated when the microphone is too close to the mouth.

### Carbon Microphones

The carbon microphone consists of a metal diaphragm placed against a cup of loosely packed carbon granules. As the diaphragm is actuated by the sound pressure, it alternately compresses and decompresses the granules. When current is flowing through the button, a variable dc will correspond to the movement of the

diaphragm. This fluctuating dc can be used to provide grid-cathode voltage corresponding to the sound pressure.

The output of a carbon microphone is extremely high, but nonlinear distortion and instability has reduced its use. The circuit shown in Fig. 31 will deliver 20-30 volts at the transformer secondary.

### Piezoelectric Microphones

Piezoelectric microphones make use of the phenomena by which certain materials produce a voltage by mechanical stress or distortion of the material. A diaphragm is coupled to a small bar of material such as Rochelle salt or ceramic made of barium titanate or lead zirconium titanate. The diaphragm motion is thus translated into electrical energy. Rochelle-salt crystals are susceptible to high temperatures, excessive moisture, or extreme dryness. Although the output level is higher, their use is declining because of their fragility.

Ceramic microphones are impervious to temperature and humidity. The output level is adequate for most modern amplifiers. They are capacitive devices and the output impedance is high. The load impedance will affect the low frequencies. To provide attenuation, it is desirable to reduce the load to 0.25 megohm or even lower, to maximize performance when operating ssb, thus eliminating much of the unwanted low-frequency response.

### Dynamic Microphones

The dynamic microphone somewhat resembles a dynamic loudspeaker. A lightweight coil, usually made of aluminum wire, is attached to a diaphragm. This coil is suspended in a magnetic circuit. When sound impinges on the diaphragm, it moves the coil through the magnetic field, generating an alternating voltage.

### Electret Microphones

The electret microphone has recently appeared as a feasible alternative to the carbon, piezoelectric or dynamic microphone. An electret is an insulator which has a quasi-permanent static electric charge trapped in or upon it. The electret operates in a condenser fashion which uses a set of biased plates whose motion, caused by air pressure variations, creates a changing capacitance and an accompanying change in voltage. The electret acts as the plates would, and being charged, it requires no bias voltage. A low voltage provided by a battery used for an FET impedance converter is the only power required to produce an audio signal.

Electrets traditionally have been susceptible to damage from high temperatures and high humidity. New materials and different charging techniques have lowered the chances of damage, however. Only in extreme conditions

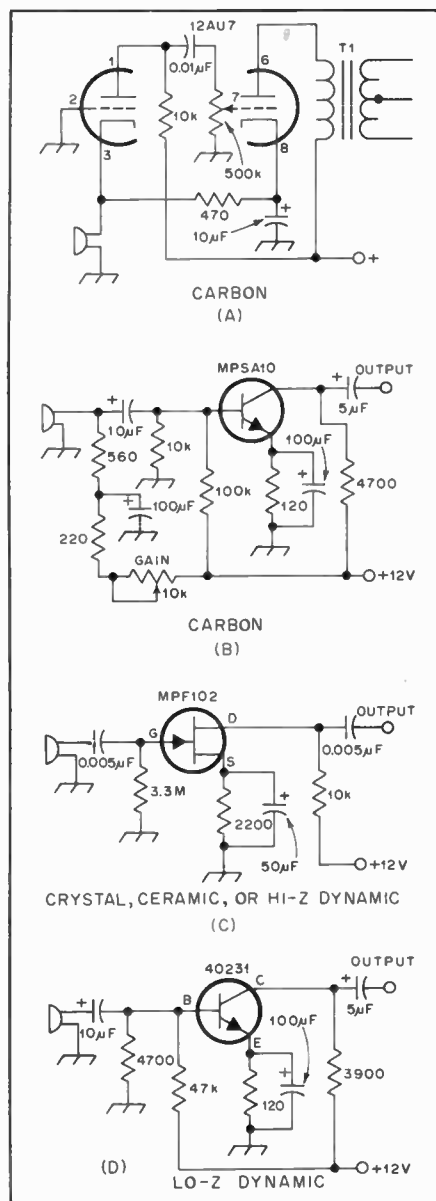


Fig. 31 — Speech circuits for use with standard-type microphones. Typical parts values are given.



(such as 120°F or 49°C at 90 percent humidity) are problems present. The output level of a typical electret is higher than that of a standard dynamic microphone.

### Voltage Amplifiers

The important characteristics of a voltage amplifier are its *voltage gain*, maximum undistorted *output voltage*, and its *frequency response*. The voltage gain is the voltage-amplification ratio of the stage. The output voltage is the maximum voltage that can be secured from the stage without distortion. The amplifier frequency response should be adequate for voice reproduction; this requirement is easily satisfied.

The voltage gain and maximum undistorted output voltage depend on the operating conditions of the amplifier. The output voltage is in terms of *peak* voltage rather than rms; this makes the rating independent of the waveform. Exceeding the peak value causes the amplifier to distort, so it is more useful to consider only peak values in working with amplifiers.

### Resistance Coupling

Resistance coupling generally is used in voltage-amplifier stages. It is relatively inexpensive, good frequency response can be secured, and there is little danger of hum pick-up from stray magnetic fields. It is the most satisfactory type of coupling for the output circuits of pentodes and high- $\mu$  triodes, because with transformers a sufficiently high load impedance cannot be obtained without considerable frequency distortion. A typical circuit is given in Fig. 32.

### Phase Inversion

Push-pull output may be secured with resistance coupling by using *phase-inverter* or *phase-splitter* circuits as shown in Fig. 33. In this circuit the voltage developed across the emitter resistor of Q1 is equal to, but 180 degrees out of phase with, the voltage swing across the collector resistor. Thus, the following two stages are fed equal af voltages. The gain of Q1 will be quite low, if indeed the stage exhibits any gain at all.

### Transformer Coupling

Transformer coupling between stages ordinarily is used only when power is to be transferred (in such a case resistance coupling is very inefficient), or when it is necessary to couple between a single-ended and a push-pull stage.

Several types of ICs have been developed for use in speech amplifiers. The Motorola MFC8040 features very low noise, typically  $1\mu\text{V}$  (Fig. 34A), while the RCA CA3020 has sufficient power output — 500 mW — to drive low-impedance loads (Fig. 34B). A transistor IC array can also be put to work in a speech amplifier,

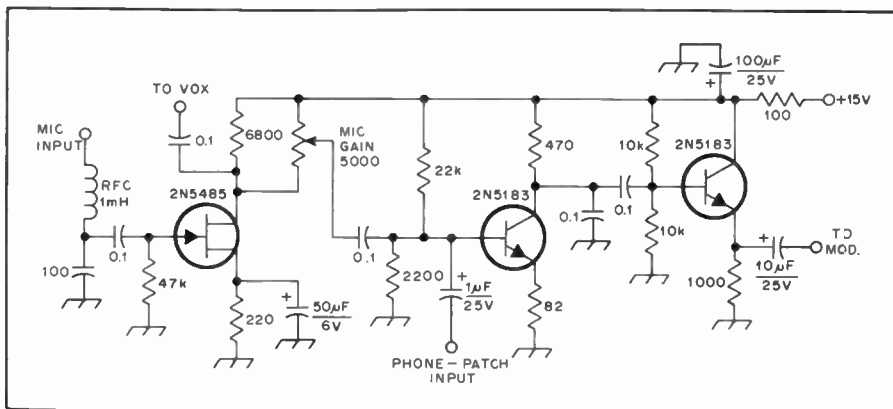


Fig. 32 — A resistance-coupled speech amplifier. Component values are representative of a typical circuit.

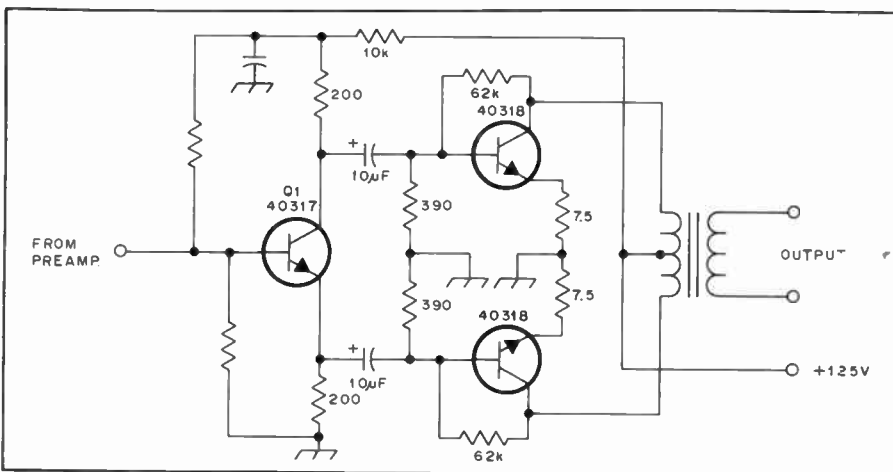


Fig. 33 — Typical phase-inverter circuits for transistor amplifier applications.

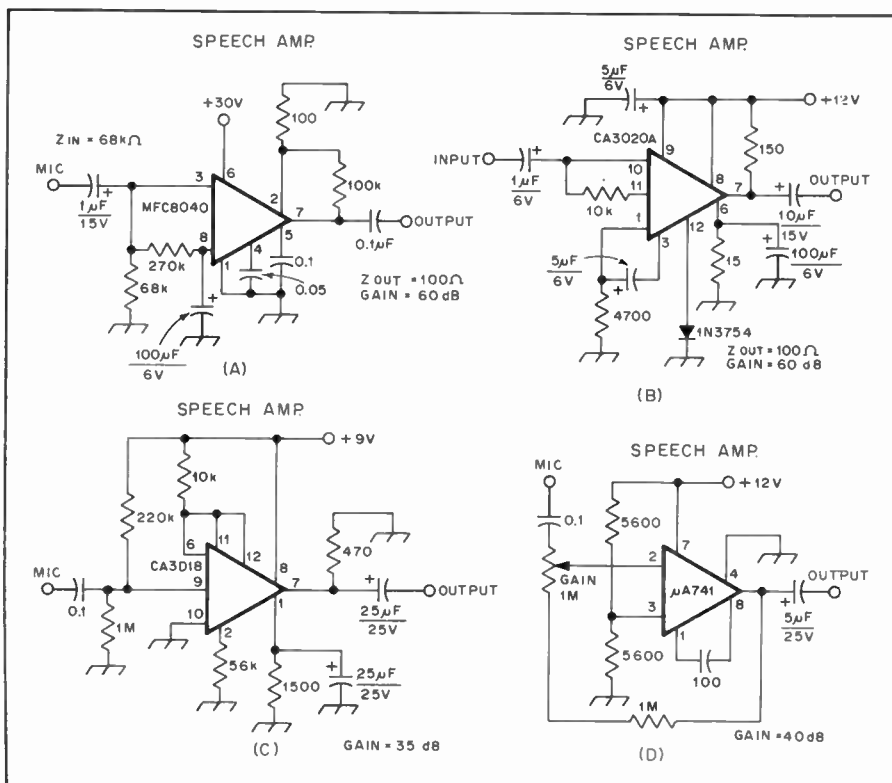


Fig. 34 — Typical speech amplifier using integrated circuits.

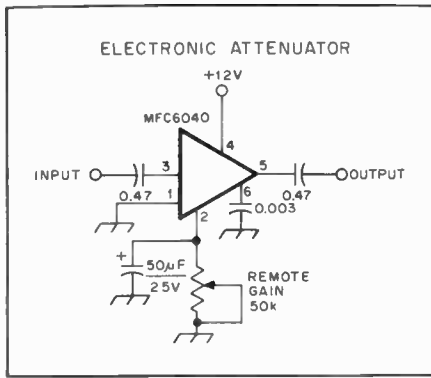


Fig. 35 — A dc voltage controls the gain of this IC, eliminating the need for shielded leads to the gain control.

as shown in Fig. 34C. This circuit uses an RCA CA3018, with a high-gain Darlington pair providing high gain and high input impedance. A second transistor within the IC functions as an emitter follower for low-impedance output. Most of the operational-amplifier ICs will work as high-gain speech amplifiers, using a minimum of external parts as shown in Fig. 34D. The type 741 has internal frequency compensation, but the popular 709 series of operational amplifiers requires external frequency compensation to prevent self-oscillation.

### Gain Control

A means for varying the overall gain of the amplifier is necessary for keeping the final output at the proper level for modulating the transmitter. The common method of gain control is to adjust the value of ac voltage applied to the base or grid of one of the amplifiers by means of a voltage divider or potentiometer.

The gain-control potentiometer should be near the input end of the amplifier, at a point where the signal voltage level is so low there is no danger that the stages ahead of the gain control will be overloaded by the full microphone output. In a high-gain amplifier it is best to operate the first stage at maximum gain, since this gives the best signal-to-hum ratio. The control is usually placed in the input circuit of the second stage.

Remote gain control can also be accomplished with an electronic attenuator IC, such as the Motorola MFC6040. A dc voltage varies the gain of the IC from +6 to -85 dB, eliminating the need for shielded leads to a remotely located volume control. A typical circuit is shown in Fig. 35.

### Speech-Amplifier Construction

Once a suitable circuit has been selected for a speech amplifier, the construction problem resolves itself into avoiding two difficulties — excessive hum, and unwanted feedback. For reasonably humless operation, the hum voltage should not exceed about 1 percent of the maximum

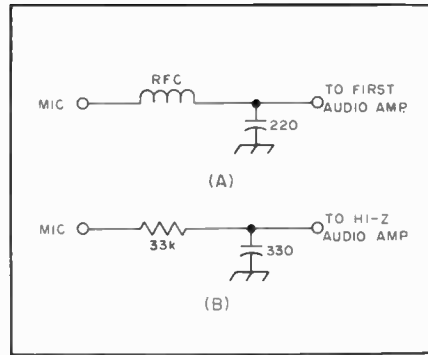


Fig. 36 — Rf filters using LC (A) and RC (B) components, which are used to prevent feedback caused by rf pickup on the microphone lead.

audio output voltage — that is, the hum and noise should be at least 40 dB below the output level.

Unwanted feedback, if negative, will reduce the gain below the calculated value; if positive, is likely to cause self-oscillation or “howls.” Feedback can be minimized by isolating each stage with decoupling resistors and capacitors, by avoiding layouts that bring the first and last stages near each other, and by shielding of “hot” points in the circuit, such as high-impedance leads in low-level stages.

If circuit-board construction is used, high-impedance leads should be kept as short as possible. All ground returns should be made to a common point. A good ground between the circuit board and the metal chassis is necessary. Complete shielding from rf energy is always required for low-level solid-state audio circuits. The microphone input should be decoupled for rf with a filter, as shown in Fig. 36. At A, an rf choke with a high impedance over the frequency range of the transmitter is employed. For high-impedance inputs, a resistor may be used in place of the choke.

When using paper capacitors as bypasses, be sure that the terminal marked “outside foil,” often indicated with a black band, is connected to ground. This utilizes the outside foil of the capacitor as a shield around the “hot” foil. When paper or mylar capacitors are used for coupling between stages, always connect the outside foil terminal to the side of the circuit having the lower impedance to ground.

### Driver and Output Stages

Few ssb transmitting mixers have sufficient output to properly drive an output stage of any significant power level. Most modern-day linear amplifiers require at least 30 to 100 watts of exciter output power to drive them to their rated power input level. It follows, then, that an intermediate stage of amplification should be used between the mixer and the PA stage of the exciter.

The vacuum-tube mixers of chapter 8 will provide 3 to 4 peak volts of output into a high-impedance load. Since most AB1 exciter output stages need from 25 to 50 volts of swing on their grids for normal operation, it is necessary to employ a driver stage to amplify the mixer output. There are several high-transconductance pentode tubes that work well as drivers. Among them are the 6CL6, 12BY7, 6EH7 and 6GK6. Since all of these tubes are capable of high gain, instability is sometimes encountered during their use. Parasitic suppression should be included as a matter of course, and can take the form of a low-value, noninductive resistor in series with the grid, or a standard parasitic choke installed directly at the plate of the tube. Some form of neutralization is recommended and is preferred to resistive loading of the tuned circuits. The latter method lowers the tuned-circuit Q. This in turn lowers the stage selectivity and permits spurious responses from the mixer to be passed on to the following stage of the exciter.

A typical driver and PA stage for modern exciters is shown in Fig. 37. The PA is set up for AB1 amplification. The AB1 mode is preferred because it results in less distortion than does the AB2 or Class-B modes, and because driving power is not needed for AB1 operation. A 6146 tube is used but an inexpensive TV sweep tube may be employed if a higher level of IMD is permissible. Some sweep tubes are capable of producing less IMD than others, but if not overdriven most of them are satisfactory for ham use. Among the sweep tubes useful as AB1 amplifiers are 6DQ5, 6GB5, 6GE5, 6HF5, 6JE6, 6JS6, 6KD6, 6KG6, 6LF6 and 6LQ6.

### A Practical Circuit

In the circuit of Fig. 37, a 6GK6 and a 6146 are shown in a typical driver-amplifier arrangement. Each stage is stabilized by means of R1 in the driver grid, and Z1 in the PA plate, both for parasitic suppression. C2 and C5 are neutralizing capacitors and can take the form of stiff wires placed adjacent to and in the same plane as the tube anode. Varying the spacing between the neutralizing stubs and the tube envelopes provides the adjustment of these capacitors. Parallel dc feed is used in the mixer and driver stages to prevent the tuned-circuit Q from being lowered by dc current flow through L1 and L2. C1A and C1B are ganged, and slug-tuned inductors are used at L1 and L2 to permit tracking of the mixer and driver plate tanks. C3 and C4 form part of the neutralizing circuits. The values shown are suitable for operation on 3.5 MHz but may require modification for use on the other bands. Regulated dc voltage is recommended for the screen grids of the driver and rf stages. Typical rf voltages (measured with a diode rf probe and VTVM) are identified with an

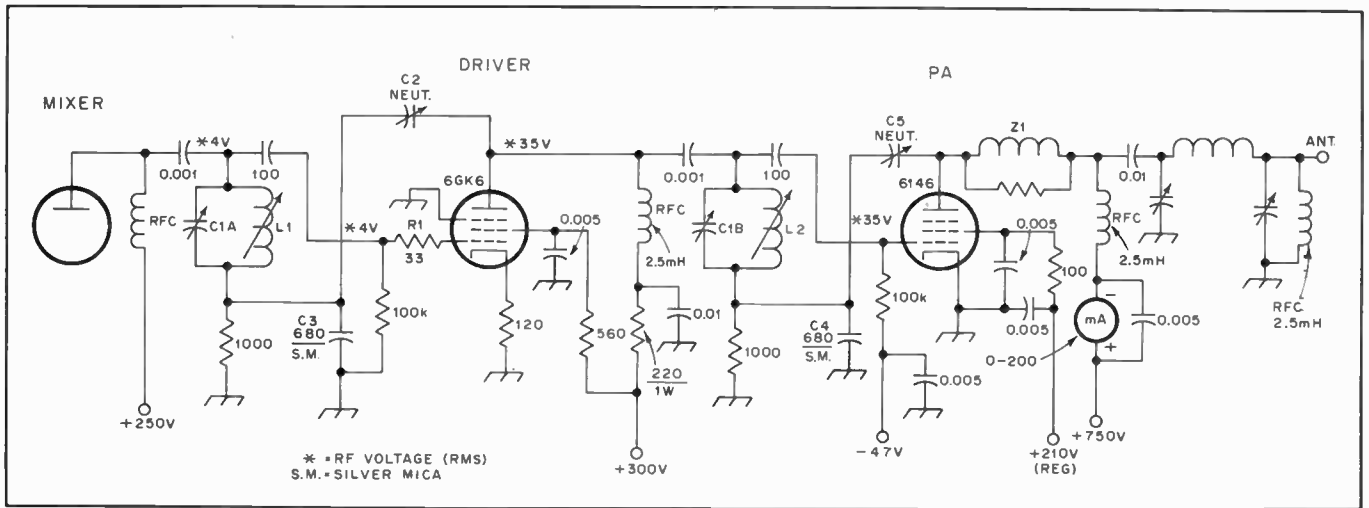


Fig. 37 — Schematic diagram of a typical driver and final stage for ssb exciter. Neutralization and parasitic-suppression circuits have been included.

asterisk. A circuit of this type is capable of up to 60 watts PEP output. For more information on linear amplifiers for sideband service, see chapter 6.

### Power Ratings of SSB Transmitters

Fig. 38 is more or less typical of a few voice-frequency cycles of the modulation envelope of a single-sideband signal. Two amplitude values associated with it are of particular interest. One is the *maximum peak amplitude*, the greatest amplitude reached by the envelope at any time. The other is the *average amplitude*, which is the average of all the amplitude values contained in the envelope over some significant period of time, such as the time of one syllable of speech.

The power contained in the signal at the maximum peak amplitude is the basic transmitter rating. It is called the *peak-envelope power*, abbreviated PEP. The peak-envelope power of a given transmitter is intimately related to the distortion considered tolerable. The lower the signal-to-distortion ratio the lower the attainable peak-envelope power, as a general rule. For splatter reduction, an S/D ratio of 25 dB is considered a border-line minimum, and better figures are desirable.

The signal power,  $S$ , in the standard definition of S/D ratio is the power in *one* tone of a two-tone test signal. This is 3 dB below the peak-envelope power in the same signal. Manufacturers of amateur ssb equipment usually base their published S/D ratios on PEP, thereby getting an S/D ratio that looks 6 dB better than one based on the standard definition. In comparing distortion-product ratings of different transmitters or amplifiers, first make sure that the ratios have the same base.

When the output of an ssb transmitter is viewed on a spectrum analyzer, the display shows the power in the two tones separately, so that the level of distortion

products is 6 dB below the level of either tone. However, commercial analyzers usually have a scale over the display tube which is calibrated directly in dB below a single-tone test. Readings may be converted to dB below the PEP level by subtracting 6 dB from the indicated distortion levels.

### Peak vs. Average Power

Envelope peaks occur only sporadically during voice transmission, and have no direct relationship with meter readings. The meters respond to the amplitude (current or voltage) of the signal averaged over several cycles of the modulation envelope. (This is true in practically all cases, even though the transmitter rf output meter may be *calibrated* in watts. Unfortunately, such a calibration means little in voice transmission since the meter can be calibrated in watts only by using a sine-wave signal — which a voice-modulated signal definitely is not.)

The ratio of peak-to-average amplitude varies widely with voice of different characteristics. In the case shown in Fig. 38A the average amplitude, found graphically, is such that the peak-to-average ratio of amplitudes is almost 3:1. The ratio of *peak power* to *average power* is something else again. There is no simple relationship between the meter reading and actual average power, for the reason mentioned earlier.

### DC Input

FCC regulations require that the transmitter power be rated in terms of the dc input to the final stage. Most ssb final amplifiers are operated Class AB1 or AB2, so that the plate current during modulation varies upward from a "resting" or no-signal value that is generally chosen to minimize distortion. There will be a peak-envelope value of plate current that, when multiplied by the dc plate voltage, represents the instantaneous tube

power input required to produce the peak-envelope output. This is the "peak-envelope dc input" or "PEP input." It does not register on any meter in the transmitter. Meters cannot move fast enough to show it — and even if they did, the eye couldn't follow. What the plate meter *does* read is the plate current averaged over several modulation-envelope cycles. This multiplied by the dc plate voltage is the number of watts input required to produce the *average* power output described earlier.

In voice transmission the power input and power output are both continually varying. The power input peak-to-average

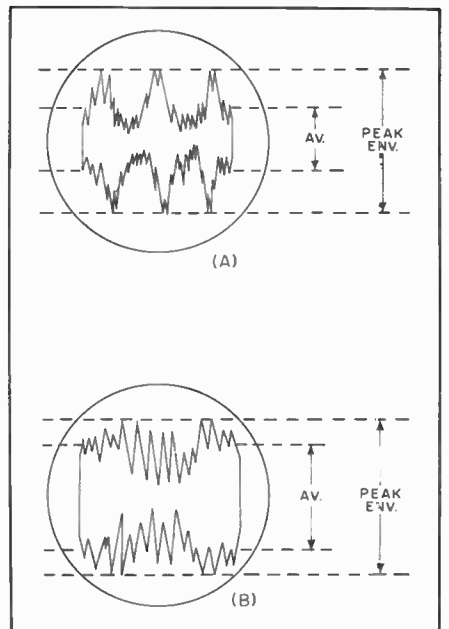


Fig. 38 — (A) Typical ssb voice-modulated signal might have an envelope of the general nature shown, where the rf amplitude (current or voltage) is plotted as a function of time, which increases to the right horizontally. (B) Envelope pattern after speech processing to increase the average level of power output.



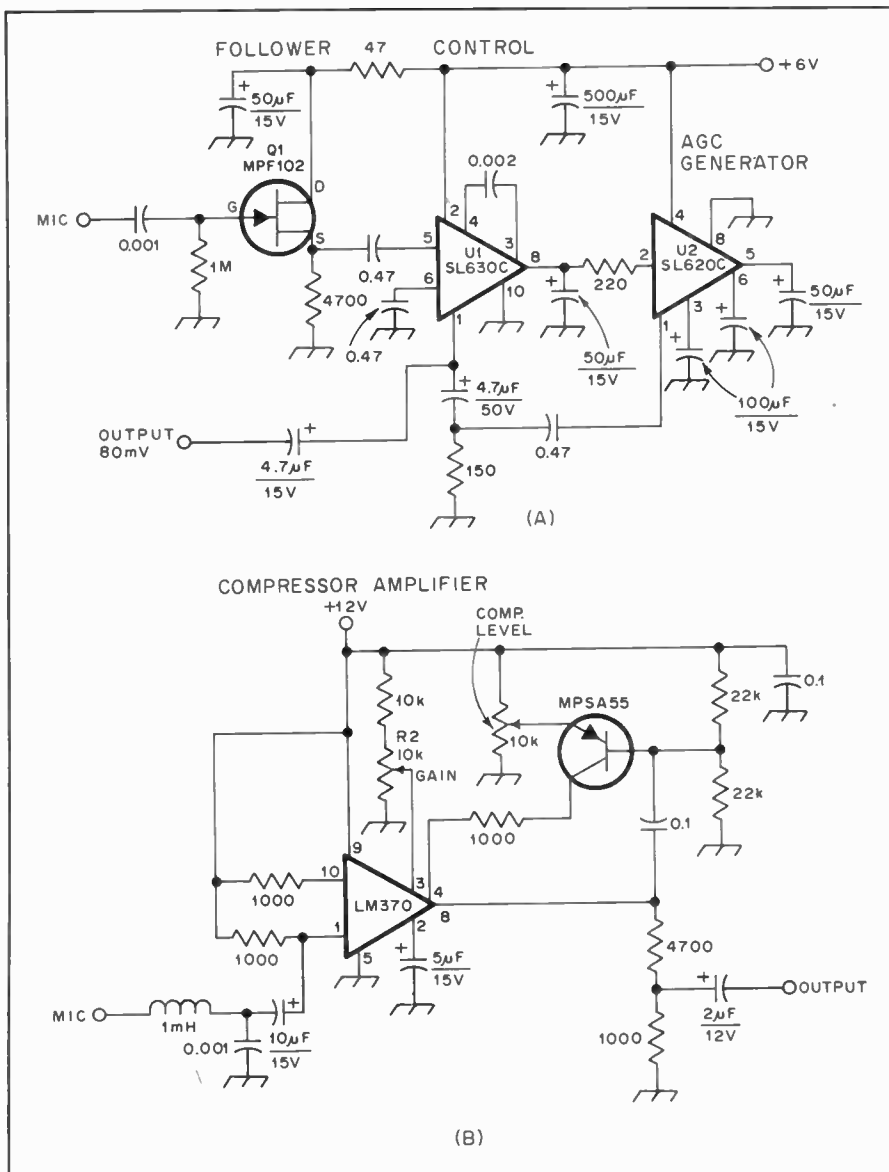


Fig. 39 — Typical solid-state compressor circuit.

ratio, as the power-output peak-to-average ratio, depends on the voice characteristics. Determination of the input ratio is further complicated by the fact that there is a resting value of dc plate input even when there is no rf output. *No exact figures are possible.* However, experience has shown that for many types of voices and for ordinary tube operating conditions where a moderate value of resting current is used, the ratio of PEP input to average input (during a modulation peak) will be in the neighborhood of 2:1. That is why many amplifiers are rated for a PEP input of 2 kilowatts even though the maximum legal input is 1 kilowatt.

#### PEP Input

The 2-kW PEP input rating can be interpreted in this way: The amplifier can handle dc peak-envelope inputs of 2 kW, presumably with satisfactory linearity.

But it should be run up to such peaks if — and *only* if — in doing so the dc plate current (the current that shows on the plate meter) multiplied by the dc plate voltage does not at any time exceed 1 kW. On the other hand, if your voice has characteristics such that the dc peak-to-average ratio is, for example, 3:1, you should not run a greater dc input during peaks than 2000/3, or 660 watts. Higher dc input would drive the amplifier into nonlinearity and generate splatter.

If your voice happens to have a peak-to-average ratio of less than 2:1 with this particular amplifier, you cannot run more than 1 kW dc input even though the envelope peaks do not reach 2 kW.

It should be apparent that the dc input rating (based on the *maximum* value of dc input developed during modulation, of course) leaves much to be desired. Its principal virtues are that it can be measured with ordinary instruments, and

that it is consistent with the method used for rating the power of other types of emission used by amateurs. The meter readings offer no assurance that the transmitter is being operated within linearity limits, unless backed up by oscilloscope checks using *your* voice.

It should be observed, also, that in the case of a grounded-grid final amplifier, the 1-kW input permitted by FCC regulations must include the input to the driver stage as well as the input to the final amplifier itself. Both inputs are measured as described above.

#### Speech Processing

Four basic systems, or a combination thereof, can be used to reduce the peak-to-average ratio, and thus, to raise the average power level of an ssb signal. They are compression or clipping of the af wave before it reaches the balanced modulator, and compression or clipping of the rf waveform after the ssb signal has been generated. One form of rf compression, commonly called *alc* (automatic level control) is almost universally used in amateur ssb transmitters. Audio processing is also used to increase the level of audio power contained in the sidebands of an a-m transmitter and to maintain constant deviation in an fm transmitter. Both compression and clipping are used in a-m systems, while most fm transmitters employ only clipping.

#### Volume Compression

Although it is obviously desirable to keep the voice level as high as possible, it is difficult to maintain constant voice intensity when speaking into the microphone. To overcome this variable output level, it is possible to use automatic gain control that follows the *average* (not instantaneous) variations in speech amplitude. This can be done by rectifying and filtering some of the audio output and applying the rectified and filtered dc to a control electrode in an early stage in the amplifier.

A practical example of an audio compressor circuit is shown in Fig. 39A. Q1 is employed as an impedance converter, providing coupling between a high-impedance microphone and the input terminal of the Plessey SL630C audio-amplifier IC. Low-impedance microphones can be connected directly to the input of the SL630C. U1 has an agc terminal which allows logarithmic control of the output level with a variable dc voltage. High-frequency cutoff is accomplished by connecting a 0.002-μF capacitor between pins 3 and 4. Manual gain control is effected by applying a dc voltage to pin 8.

Agc voltage for U1 is developed by the SL620C. A suitable time constant for voice operation is established by the capacitors connected to pins 3, 4 and 6, respectively. The IC provides a fast-



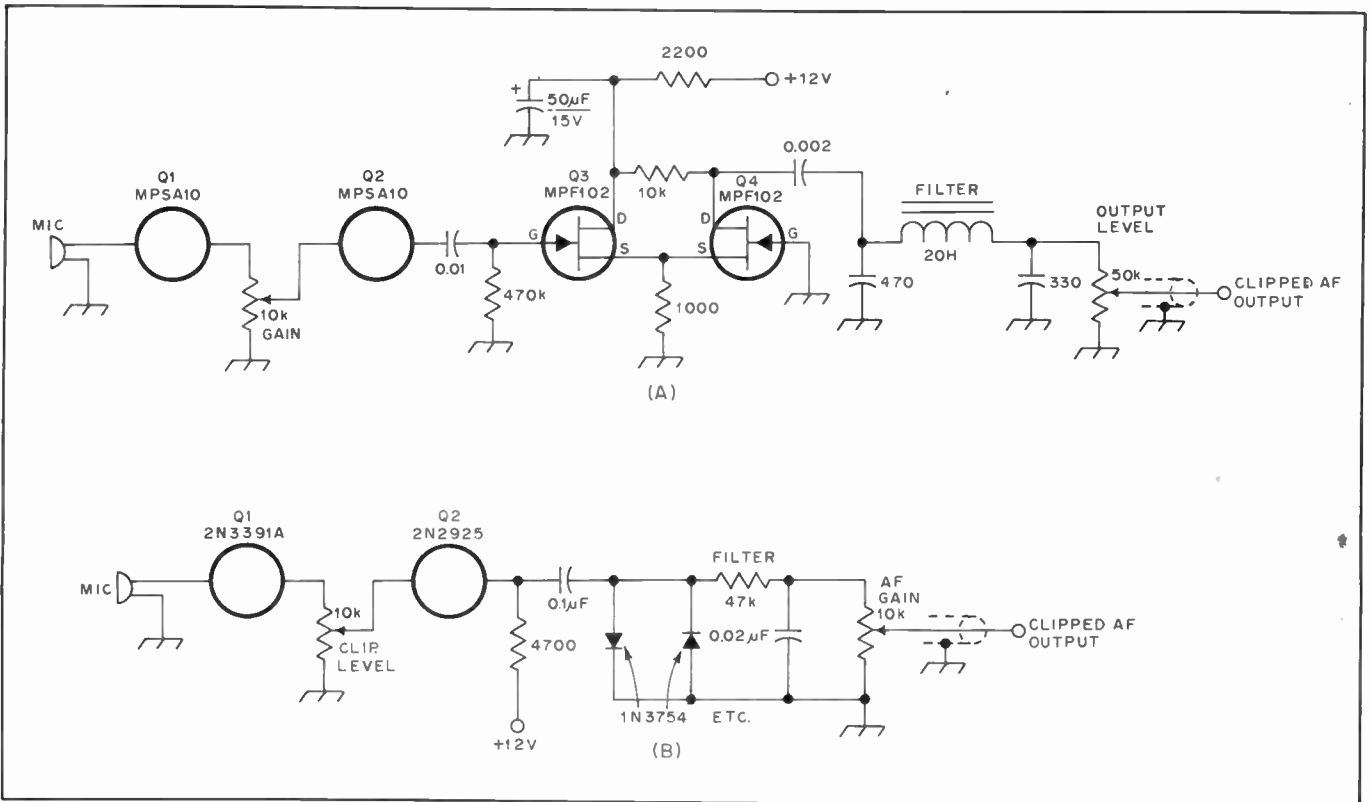


Fig. 40— This drawing illustrates use of JFETs or silicon diodes to clip positive and negative voice peaks.

attack, slow-decay characteristic for the agc voltage when voice signals are applied and a short burst of agc voltage when a short noise burst occurs. Twenty transistors and four diodes are used in U2.

The compressor will hold the output level constant within 2 dB over a 40-dB range of input signal. The nominal output level is 80 mV; the microphone used should develop at least 3 mV at the gate of Q1.

Fig. 39B shows an IC audio compressor circuit using the National Semiconductor LM-370. This IC has two gain-control points, pins 3 and 4; one is used for the input gain adjustment while the other receives agc voltage whenever the output

level exceeds a preset norm. R2 establishes the point at which compression starts.

### Speech Clipping and Filtering

In speech waveforms the average power content is considerably less than in a sine wave of the same peak amplitude. If the low-energy peaks are clipped off, the remaining waveform will have a considerably higher ratio of average power to peak amplitude. Although clipping distorts the waveform and the result

therefore does not sound exactly like the original, it is possible to secure a worthwhile increase in audio power without sacrificing intelligibility. Once the system is properly adjusted it will be impossible to overdrive the modulator stage of the transmitter because the maximum output amplitude is fixed.

By itself, clipping generates high-order harmonics and therefore will cause splatter. To prevent this, the audio frequencies above those needed for intelligible speech

Fig. 42— Two-tone envelope patterns with various degrees of rf clipping. All envelope patterns are formed using tones of 600 and 1000 Hz. (A) At clipping threshold; (B) 5 dB of clipping; (C) 10 dB of clipping; (D) 15 dB of clipping.


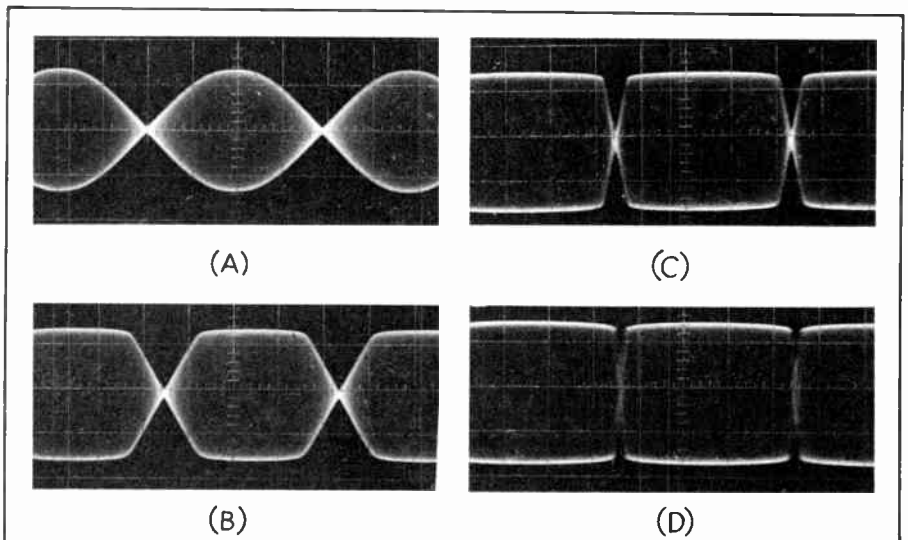


Fig. 41— The improvement in received signal-to-noise ratio achieved by the simple forms of signal processing.

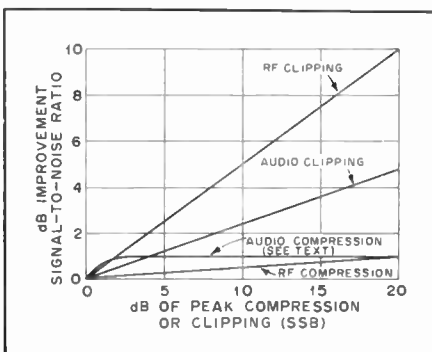

must be filtered out *after* clipping and *before* modulation. The filter required for this purpose should have relatively little attenuation below about 2500 Hz, but high attenuation for all frequencies above 3000 Hz.

The values of L and C should be chosen to form a low-pass filter section having a cutoff frequency of about 2500 Hz, using the value of the terminating resistor load

resistance. For this cutoff frequency the formulas are

$$L1 = \frac{R}{7850}$$

$$C1 = C2 = \frac{63.6}{R}$$

where R = ohms

L1 = henrys

C1 =  $\mu$ F

C2 =  $\mu$ F

There is a loss in naturalness with "deep" clipping, even though the voice is highly intelligible. With moderate clipping levels (6 to 12 dB) there is almost no change in "quality" but the voice power is increased considerably.

Before drastic clipping can be used, the speech signal must be amplified several times more than is necessary for normal modulation. Also, the hum and noise

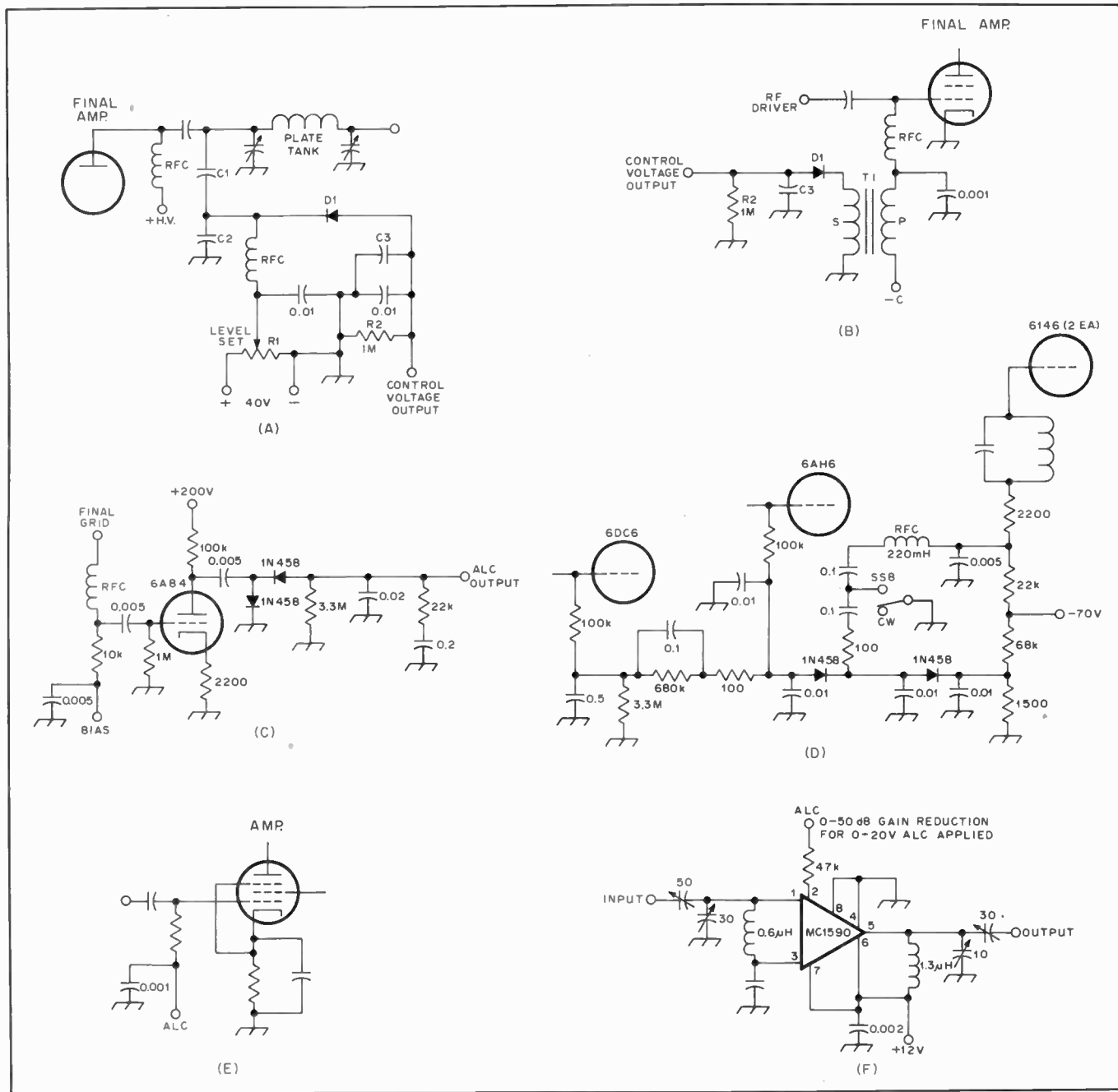


Fig. 43 — (A) Control voltage obtained by sampling the rf output voltage of the final amplifier. The diode back bias, 40 volts or so maximum, may be taken from any convenient positive voltage source in the transmitter. R1 may be a linear control having a maximum resistance of the order of 50 k $\Omega$ . D1 may be a 1N34A or similar germanium diode.  
 (B) Control voltage obtained from grid circuit of a Class AB1 tetrode amplifier. T1 is an interstage audio transformer having a turns ratio, secondary to primary, of 2 or 3 to 1. An inexpensive transformer may be used, since the primary and secondary currents are negligible. D1 may be a 1N34A or similar; time constant R2C3 is discussed in the text.  
 (C) Control voltage is obtained from the grid of a Class AB1 tetrode amplifier and amplified by a triode audio stage.  
 (D) ALC system used in the Collins 32S-3 transmitter.  
 (E) Applying control voltage to the tube or (F) linear IC controlled amplifier.

must be much lower than the tolerable level in ordinary amplification, because the noise in the output of the amplifier increases in proportion to the gain.

In the circuit of Fig. 40B a simple diode clipper is shown following a two-transistor preamplifier section. The 1N3754s conduct at approximately 0.7 volt of audio and provide positive- and negative-peak clipping of the speech waveform. A 47-k $\Omega$  resistor and a 0.02- $\mu$ F capacitor follow the clipper to form a simple R-C filter for attenuating the high-frequency components generated by the clipping action, as discussed earlier. Any top-hat or similar silicon diodes can be used in place of the 1N3754s. Germanium diodes (1N34A type) can also be used, but will clip at a slightly lower peak audio level.

### SSB Speech Processing

Compression and clipping are related, as both have fast attack times, and when the compressor release is made quite



Fig. 44 — Exterior view of the audio speech processor.

short, the effect on the waveform approaches that of clipping. Speech processing is most effective when accomplished at radio frequencies, although a combination of af clipping and compression can produce worthwhile results. The advantage of an outboard audio speech processor is that no internal modifications are necessary to the ssb transmitter with which it will be used.

To understand the effect of ssb speech processing, review the basic rf waveforms shown in Fig. 38A. Without processing, they have high peaks but low average power. After processing, Fig. 38B, the amount of average power has been raised considerably. Fig. 41 shows an advantage of several dB for rf clipping (for 20 dB of processing) over its nearest competitor.

Investigations by W6JES reported in January 1969 *QST* show that, observing a transmitted signal using 15 dB of audio clipping from a remote receiver, the intelligibility threshold was improved nearly 4 dB over a signal with no clipping. Increasing the af clipping level to 25 dB gave an additional 1.5 dB improvement in intelligibility. Audio compression was found to be valuable for maintaining relatively constant average-volume speech, but such a compressor added little to the intelligibility threshold at the receiver, only about 1-2 dB.

Evaluation of rf clipping from the receive side with constant-level speech, and filtering to restore the original bandwidth, resulted in an improved intelligibility threshold of 4.5 dB with 10 dB of clipping. Raising the clipping level to 18 dB gave an additional 4-dB improvement at the receiver, or 8.5-dB

total increase. The improvement of the intelligibility of a weak ssb signal at a distant receiver can thus be substantially improved by rf clipping. The effect of such clipping on a two-tone test pattern is shown in Fig. 42.

Automatic level control, although a form of rf speech processing, has found its primary application in maintaining the peak rf output of an ssb transmitter at a relatively constant level, hopefully below the point at which the final amplifier is overdriven when the audio input varies over a considerable range. These typical alc systems, shown in Fig. 43, by the nature of their design time constants offer a limited increase in transmitted average-to-PEP ratio. A value in the region of 2-5 dB is typical. An alc circuit with shorter time constants will function as an rf syllabic compressor, producing up to 6 dB improvement in the intelligibility threshold at a distant receiver. The Collins Radio Company uses an alc system with dual time constants (Fig. 43D) in their S/Line transmitters, and this has proven to be quite effective.

Heat is an extremely important consideration in the use of any speech processor which increases the average-to-peak power ratio. Many transmitters, in particular those using television sweep tubes, simply are not built to stand the effects of increased average input, either in the final-amplifier tube or tubes or in the power supply. If heating in the final tube is the limiting factor, adding a cooling fan may be a satisfactory answer.

### An Audio Speech Processor

Over the years, different speech pro-

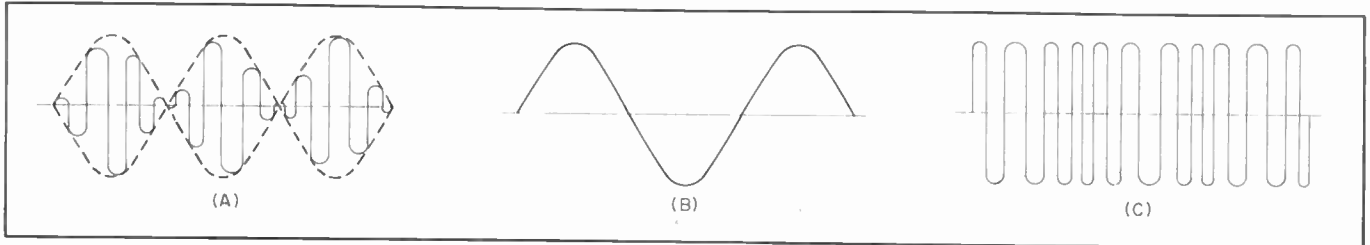


Fig. 45 — A voice signal can be represented as an a-m waveform, which results from multiplication of a relatively slowly varying envelope (B) with a carrier (C). Note the carrier peak amplitude is constant. The speech processor separates components B and C, and filters out B, leaving the carrier portion only.

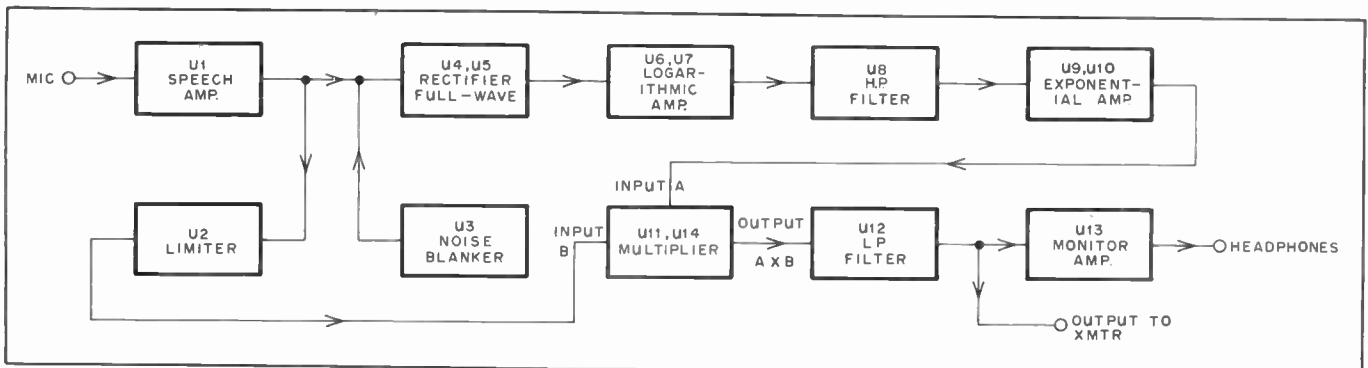


Fig. 46 — Block diagram for the processor.

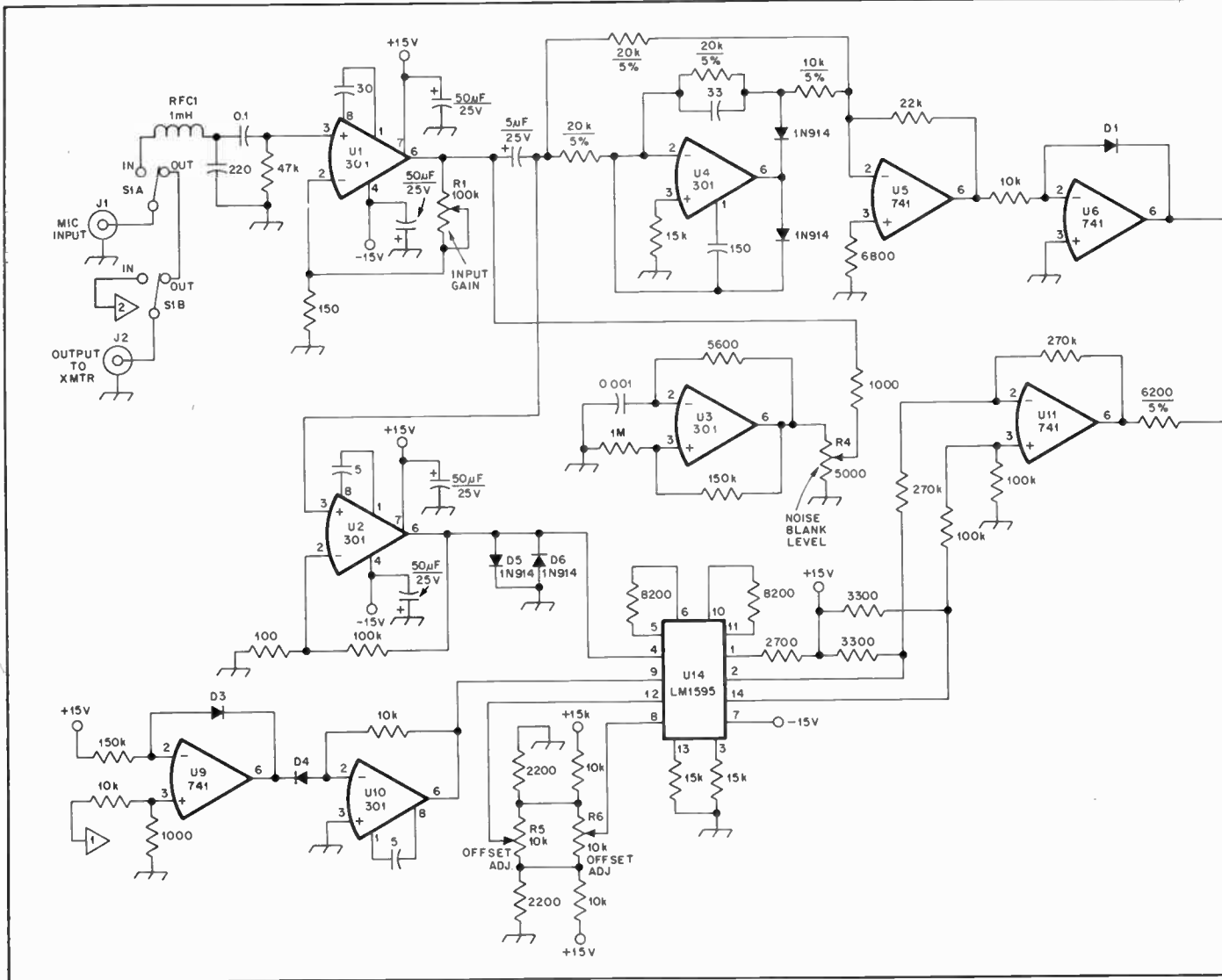


Fig. 47 — Circuit diagram for the speech processor.  
 D1, D2 — Pair of matched silicon diodes (see text).  
 D3, D4 — Same as D1, D2.  
 R1, R4, R5, R6, R7 — Use circuit-board type pots.  
 S1 — Dpdt toggle switch.

T1 — 1000-ohm to 8-ohm audio transformer, 250 milliwatts.  
 U1, U5, U6, U8, U9, U10, U11, U12, U13 — Type 741 op amp, 8-pin DIP package.

U2, U3, U4, U7, U10 — National Semiconductor LM301 op amp, 8-pin DIP package.  
 U14 — National Semiconductor LM1595 (or Motorola MC1595), 14-pin DIP package.

cessing schemes have been employed, with varying degrees of success, to raise the average-to-peak power ratio of a voice signal and improve communications effectiveness. The various methods generally fall into one of two categories — compression or clipping. Described here is a processor which represents a departure from these standard approaches. Processing is done at audio frequencies, but in a unique fashion. The unit is used between the microphone and the transmitter so that no modification to the transmitter is required.


#### Technical Description

Operation is a consequence of the fact that speech energy resembles an amplitude-modulated signal. The speech waveform represents multiplication of a slowly varying envelope containing energy

below 100 Hz with a voice-frequency signal contained mostly between 300 and 3000 Hz. In an analogous fashion, a conventional a-m modulator multiplies an amplitude-varying low-frequency signal (the applied modulation) with a constant-amplitude higher-frequency carrier. Thus the speech waveform envelope corresponds to the a-m modulation and the voice-frequency portion to the carrier. Note that the voice carrier actually varies continuously in frequency, unlike the conventional fixed-frequency a-m case, but is constant in amplitude. The object of this speech processor is to reproduce only the carrier portion of speech. The voice envelope is separated from the voice carrier, and because their respective frequency spectrums are nonoverlapping, the envelope can be filtered leaving only the carrier. (See Fig. 45.)

To separate the envelope and carrier, the speech signal is passed through a logarithmic amplifier which performs the mathematical operation of taking logarithms. By analogy to the a-m model, this signal can be represented as the mathematical product  $EV$ , where  $E$  represents the envelope and  $V$ , the voice carrier, both of which are functions of time. Taking the logarithm produces  $\log EV$ , but  $\log EV = \log E + \log V$  (a well-known property of the logarithm). The envelope and carrier components are then separated in terms of their logarithms and it is now a relatively simple matter to process the two components independently. This is something which could not be done up to this point. A high-pass filter with an appropriately chosen cutoff frequency attenuates the envelope waveform but passes the higher-frequency



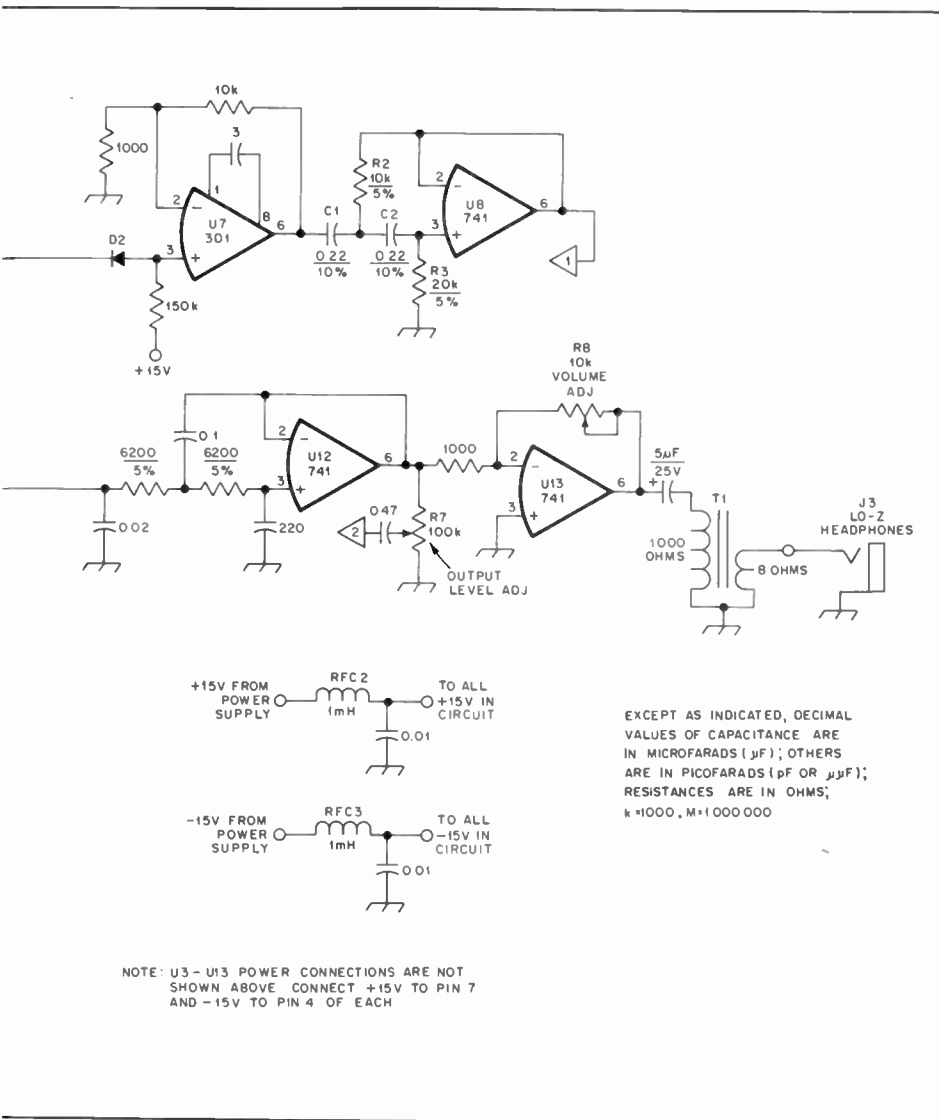

voice carrier. The remaining signal is  $\log V$ . It goes through an inverse-logarithm amplifier which produces at its output the signal  $V$ . The result is the desired constant-amplitude voice carrier.

### Circuit Description

Some additional issues arise when one tries to implement the preceding scheme. These will be considered now in a stage-by-stage operational description of the processor. The reader is referred to the block diagram in Fig. 46 and the circuit in diagram Fig. 47. Speech amplifier U1 first boosts the incoming audio signal to a convenient and usable level. Before taking logarithms, however, output from U1 must be full-wave rectified to be all positive since the logarithmic amplifier works only for positive signal input. The logarithm of a

number is defined only for positive numbers. U4 and U5 serve as a full-wave rectifier and precedes the logarithmic amplifier, U6 and U7. Matched silicon diodes are recommended for D1 and D2. If none is available, individual 1N914 diodes may be substituted. The logarithmic stage separates the voice-frequency and envelope components of the speech waveform, as described above, and the envelope is filtered by an active RC high-pass filter, U8.<sup>20</sup> A two-pole Butterworth configuration is used with the lower half-power frequency set at approximately 50 Hz. Those who are experimentally inclined may wish to try lower or higher cutoff frequencies. The expression for cutoff frequency,  $f_c$ , in terms of the filter components is

$$f_c = \frac{1}{2\pi\sqrt{R_3 R_2 C_1 C_2}}$$

where it is required that  $C_1 = C_2$  and  $R_3 = 2 \times R_2$  for proper filter response. Varying the cutoff frequency corresponds to changing the compression level setting on a conventional speech compressor. Lower cutoff frequencies result in reduced "compression." In the original model of this processor, it was found that a filter cutoff frequency of about 400 Hz or higher produced essentially constant-amplitude output from the processor. Harmonic distortion was quite noticeable, however. Thus, 50 Hz was chosen as a compromise between maximum "compression" and minimum distortion. The distortion that is inherent in this unit occurs for signals that have considerable energy in the neighborhood of the high-pass filter cutoff frequency. With a setting of 50 Hz, the distortion is quite low. The filtered signal proceeds to an exponential amplifier, U9 and U10. As with the logarithmic amplifier, matched diodes for D3 and D4 will produce the best results, but individual 1N914s will serve satisfactorily. The signal at the output of U10 is still in rectified form (all positive). To be converted back to its bipolar form, the signal is multiplied by the correct sign information (either positive or negative). The effect is to invert (make negative) portions of the signal which should be negative, leaving the remaining parts positive. The correct sign information is obtained by hard-limiting the voice signal at the processor input. Output from U1 is further amplified by U2 and then limited by a diode clipper, D5 and D6. Because of the very high gain of the U1-U2 cascade, the clipper produces almost pure square-wave output. Thus, any positive input to U1 produces a level of approximately 1 volt at the output of U2, and any negative input produces a level of about -1 volt. The square-wave output is multiplied with the signal from the exponential amplifier by an analog multiplier, U14. The LM1595 used at U14 produces an output voltage equal to the mathematical product of its two input signals, which in this case are the signals from U2 and U10. The result, then, is to multiply the rectified signal from the exponential amplifier by plus or minus one volt to produce the desired bipolar signal. Output is taken from buffer amplifier U11. The processed signal is passed through a low-pass filter with sharp cutoff above 3 kHz to eliminate unwanted high-frequency energy.

Because the processor is inherently sensitive to even the smallest input signals,

<sup>20</sup>Because the rectification and logarithmic operations performed upon the original speech signal are nonlinear, the frequency spectrums of the actual envelope and voice carrier signals are, strictly speaking, not exactly the same as those of the signals appearing at the output of the logarithmic amplifier. The main result of these operations is to introduce additional higher-frequency components not present in the original signal. It has been determined, however, that the logarithm of the rectified speech envelope is still primarily low-frequency in nature (mostly far below 100 Hz). This is sufficient to allow the processor to operate as originally described.

undesired background noise or induced ac hum will be processed along with the speech and will appear as a loud disturbance at the output. To help eliminate this problem, noise blanker U3 is included in the design. It consists of a free-running multivibrator with square-wave output at about 20 kHz, which is beyond audibility. When this signal is added to the output of the speech amplifier, the effect is to mask, before processing, any noise which is lower in amplitude than the 20-kHz signal.

An audio amplifier, U13, at the output, provides a convenient means of monitoring the processed audio output with low-impedance (eight-ohm) headphones. If high-impedance headphones are to be used, T1 may be omitted and output can be taken directly from pin 6 of U13 through a 5- $\mu$  F coupling capacitor.

### Construction Information

An etched circuit board template pattern is available from ARRL, 225 Main Street, Newington, CT 06111. Please include 50 cents and a self-addressed, stamped envelope. Builders who use this layout should experience no problems. Those attempting their own layout, however, should be cautioned that because of the relatively large number of active devices, some operating with high gain, the potential for instability (oscillation) exists in a haphazard layout. Arrangement of circuit components should be generally in a straight line from input to output. The shortest possible leads should be used in all cases. Particular attention should be paid to the positions of U1 and U2 with respect to each other. Because of the very high gain the input of U1 should be kept physically as far apart as possible from the output of U2. Mounting the circuit board inside a metal chassis, such as a suitable Minibox, is recommended for rf shielding.

Procurement of parts should present no particular problems. As of the time of this writing, the 741 and LM301 operational amplifiers used in the circuit can be purchased from mail order houses for about 30 cents apiece. The LM1595 integrated circuit, probably the single most expensive item in the processor, was bought for under \$2. Matched diodes for D1, D2, D3 and D4 should cost less than a dollar.

The circuit is powered by a dual dc power supply that provides plus and minus 15 volts, as is typically used with most operational amplifiers. Current consumption is approximately 50 mA from each side of the supply.

### Initial Adjustments

If an oscilloscope and audio sine wave generator are available, the following alignment procedure should be followed: Set R4 to minimum resistance. Connect a microphone to J1 and the oscilloscope

probe to pin 6 of U1. Adjust R1, the input gain control, while speaking into the microphone so that the voice peaks viewed on the oscilloscope are slightly below the output clipping level of U1 (approximately 14 volts peak). Remove the microphone and connect the signal generator to J1. Set the generator frequency to about 1000 Hz and adjust its output level to produce about 10 volts peak at pin 6 of U1. Place the oscilloscope probe on pin 6 of U12. Adjust offset controls R5 and R6 for the best-looking sine wave. It should be possible to produce a nearly perfect sine wave. Disconnect the generator, reconnect the microphone, and plug headphones into J3. Advancing volume control R8, one should now be able to hear himself talking, although background noise and ac hum will probably be very high. Adjust noise blanking control R4 for the desired degree of background noise suppression.

Those who do not have access to test equipment may do the following: Set R4 to the center of its range. Connect a microphone to J1 and headphones to J3. Speaking into the microphone, advance input gain control R1 and monitor volume control R8 to the point where the speech becomes audible in the headphones. Adjust offset controls R5 and R6 for minimum distortion as monitored in the headphones. The final setting of R1 is not critical. It should be high enough so that the circuit functions properly (if set too low, the audio output will sound broken up and "grainy") but not so high that the speech amplifier itself distorts the signal by clipping. Adjust R4 to suppress background noise as desired.

Finally, connect the processor output at J2 to the transmitter's microphone jack. Switch the processor out of the line by means of S1. If a Monitoroscope is available to view rf output, speak into the microphone and note the level of the voice peaks. Switch the unit "in" and adjust output level control R7 for the same peak voice output level. If a monitoroscope is not available, the transmitter's alc meter readings may be used. With the processor switched "out," speak into the microphone and increase the transmitter's microphone gain control until the alc meter starts to deflect. Note the peak readings. Switch the processor "in" and adjust R7 to obtain the same peak reading.

### Single-Sideband Transceivers

A *transceiver* combines the functions of transmitter and receiver in a single package. In contrast to a packaged "transmitter-receiver," it utilizes many of the active and passive elements for both transmitting and receiving. Ssb transceiver operation enjoys widespread popularity for several justifiable reasons. In most designs the transmissions are on the same (suppressed-carrier) frequency as the

receiver is tuned to. The only practical way to carry on a rapid multiple-station "roundtable" or net operation is for all stations to transmit on the same frequency. Transceivers are ideal for this, since once the receiver is properly set the transmitter is also. Transceivers are by nature more compact than separate transmitter and receiver setups and thus lend themselves well to mobile and portable use.

Although the many designs available on the market differ in detail, there are of necessity many points of similarity. All of them use the filter type of sideband generation, and the filter unit furnishes the receiver i-f selectivity as well. The carrier oscillator doubles as the receiver (fixed) BFO. One or more mixer or i-f stage or stages will be used for both transmitting and receiving. The receiver S meter may become the transmitter plate-current or output voltage indicator. The VFO that sets the receiver frequency also determines the transmitter frequency. The same signal-frequency tuned circuits may be used for both transmission and reception, including the transmitter pi-network output circuit.

Usually the circuits are switched by a multiple-contact relay, which transfers the antenna if necessary and also shifts the biases on several stages. Most commercial designs offer *VOX* (voice-controlled operation) and *MOX* (manual operation). Which is preferable is a controversial subject; some operators like *VOX* and others prefer *MOX*.

### Circuits

The use of a filter-amplifier combination common to both the transmitter and receiver is shown in Fig. 48A. This circuit is used by the Heath Company in several of their transceiver kits. When receiving, the output of the hf mixer is coupled to the crystal filter, which, in turn, feeds the first i-f amplifier. The output of this stage is transformer coupled to the second i-f amplifier. During transmit, K1 is closed, turning on the isolation amplifier that links the balanced modulator to the band-pass filter. The single-sideband output from the filter is amplified and capacitance-coupled to the transmitter mixer. The relay contacts also apply alc voltage to the first i-f stage and remove the screen voltage from the second i-f amplifier, when transmitting.

Bilateral amplifier and mixer stages, first used by Sideband Engineers in their SBE-33, also have found application in other transceiver designs. The circuits shown in Fig. 48B and C are made to work in either direction by grounding the bias divider of the input transistor, completing the bias network. The application of these designs to an amateur transceiver for the 80-10 meter bands is given in the Fifth Edition of *Single Sideband for the Radio Amateur*.

The complexity of a multiband ssb transceiver is such that most amateurs buy them fully built and tested. There are, however, some excellent designs available in the kit field, and any amateur able to handle a soldering iron and follow instructions can save himself considerable money by assembling an ssb transceiver kit.

Some transceivers include a feature that permits the receiver to be tuned a few kHz either side of the transmitter frequency. This consists of a voltage-sensitive capacitor, which is tuned by varying the applied dc voltage. This can be a useful

device when one or more of the stations in a net drift slightly. The control for this function is usually labeled RIT for receiver incremental tuning. Other transceivers include provision for a crystal-controlled transmitter frequency plus full use of the receiver tuning. This is useful for "DXpeditions" where net operation (on the same frequency) may not be desirable.

#### SSB Bibliography

*Single Sideband for the Radio Amateur*, American Radio Relay League, Fifth Edition, 1970.  
 Hennebury, *Single Sideband Handbook*, Technical Material Corporation, 1964.  
 Pappenfus, Bruene and Schoenike, *Single Sideband*

*Principles and Circuits*, McGraw-Hill, 1964.  
*Amateur Single Sideband*, by Collins Radio Company, 1962.

#### Testing a Sideband Transmitter

There are three commonly used methods for testing an ssb transmitter. These include the wattmeter, oscilloscope, and spectrum-analyzer techniques. In each case, a two-tone test signal is fed into the mic input to simulate a speech signal. From the measurements, information concerning such quantities as PEP and intermodulation-distortion-product (IMD) levels can be obtained. Depending upon the technique used, other aspects of

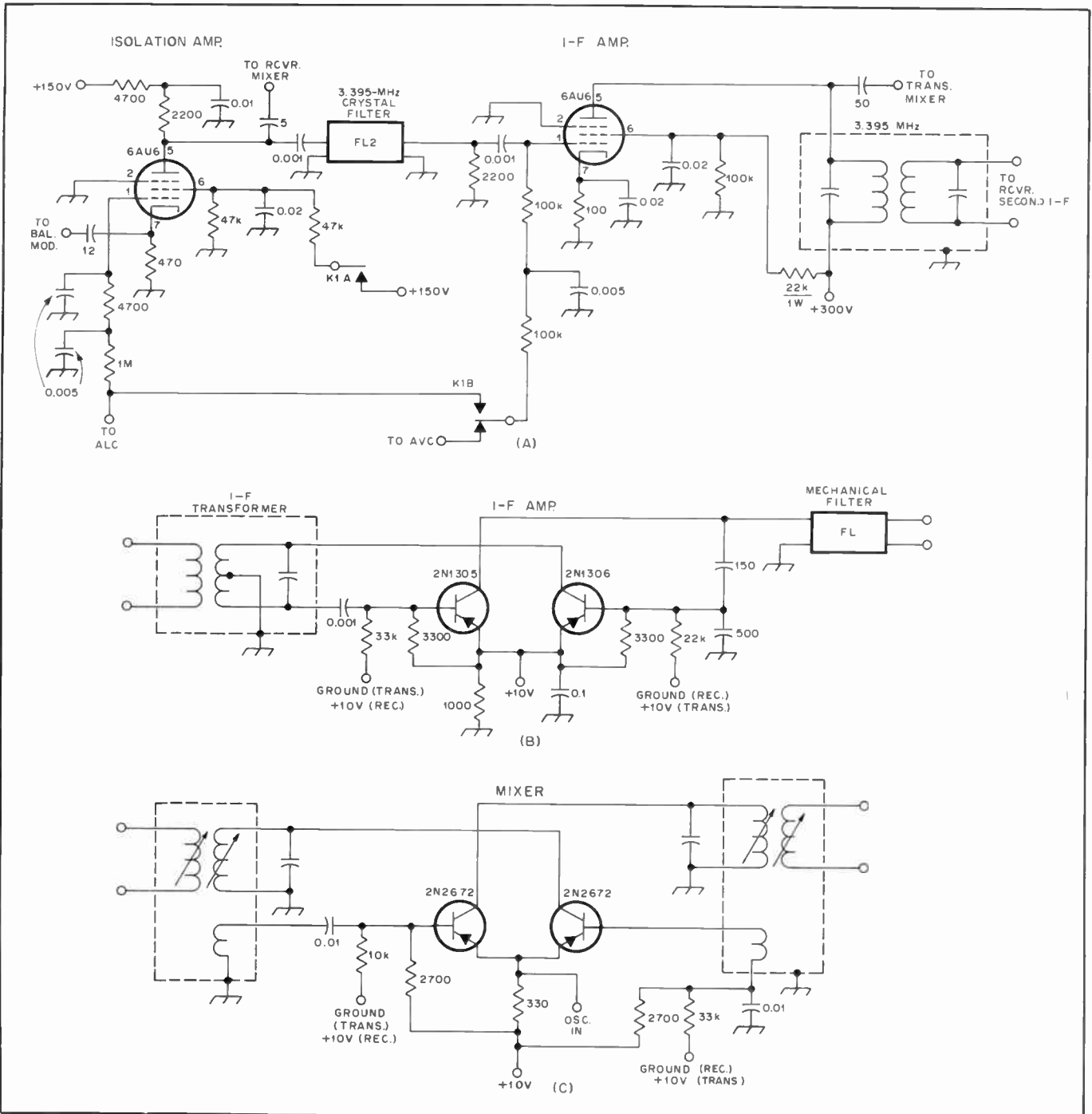


Fig. 48 — Transceiver circuits where a section is made to operate on both transmit and receive. See text for details.



transmitter operation (such as hum problems and carrier balance) can also be checked.

As might be expected, each technique has both advantages and disadvantages and the suitability of a particular method will depend upon the desired application. The wattmeter method is perhaps the simplest one but it also provides the least

amount of information. Rf wattmeters suitable for single-tone or cw operation may not be accurate with a two-tone test signal. A suitable wattmeter for the latter case must have a reading that is proportional to the actual power consumed by the load. The reading must be independent of signal waveform. A thermocouple ammeter connected in series

with the load would be a typical example of such a system. The output power would be equal to  $I^2R$ , where  $I$  is the current in the ammeter and  $R$  is the load resistance (usually 50 ohms). In order to find the PEP output with the latter method (using a two-tone test input signal), the power output is multiplied by two.

A spectrum analyzer is capable of giving the most information (of the three methods considered here), but it is also the most costly method and the one with the greatest chance of misinterpretation. Basically, a spectrum analyzer is a receiver with a readout which provides a plot of signal amplitude vs. frequency. The readout could be in the form of a paper chart but usually it is presented as a trace on a CRT. A sweep voltage which is applied to the horizontal-deflection amplifiers of the CRT is also used to control the frequency of the LO for the first mixer (there may be other mixers but these are fixed-frequency types) in the analyzer. (See the block diagram in Fig. 49.) In order to give a meaningful output waveform, the first mixer has to have a broadband and "flat" response. It also has to have very good IMD suppression characteristics, otherwise, the mixer may generate spurious signals itself. Unfortunately, these signals fall on the same frequencies as those being measured in the transmitter output and it may be difficult to tell whether or not the spurious products are being generated in the transmitter or in the spectrum analyzer. Other precautions that should be taken would be to ensure that good RFI-prevention practices are observed. In effect, the problem is similar to trying to listen to one's own signal in the station receiver. Quite often a signal may not be as bad or as good in the latter as it is at a distant station.

### Two-Tone Tests and Scope Patterns

A very practical method for amateur applications is to use a two-tone test signal (usually audio) and sample the transmitter output. The waveform of the latter is then applied directly to the vertical-deflection plates in an oscilloscope. An alternative method is to use an rf probe and detector to sample the waveform and apply the resulting audio signal to the vertical-deflection amplifier input.

If there are no appreciable nonlinearities in the amplifier, the resulting envelope will approach a perfect sine-wave pattern (see Fig. 50A). As a comparison, a spectrum-analyzer display for the same transmitter and under the same conditions is shown in Fig. 50B. In this case, spurious products can be seen which are approximately 30 dB below the amplitude of each of the tones.

As the distortion increases, so does the level of the spurious products and the resulting waveform departs from a true

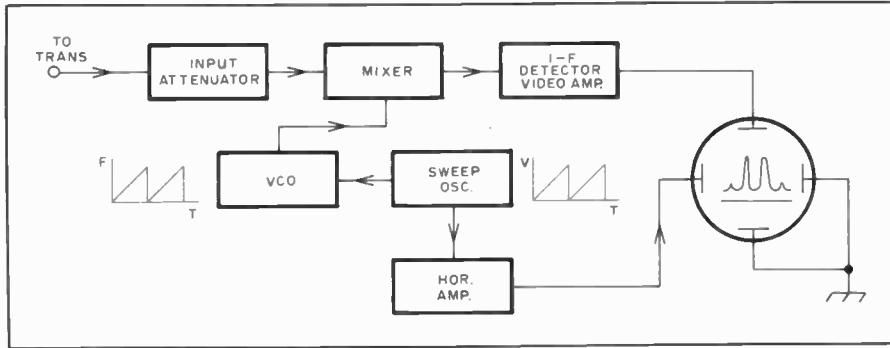


Fig. 49 — Block diagram of a spectrum analyzer.

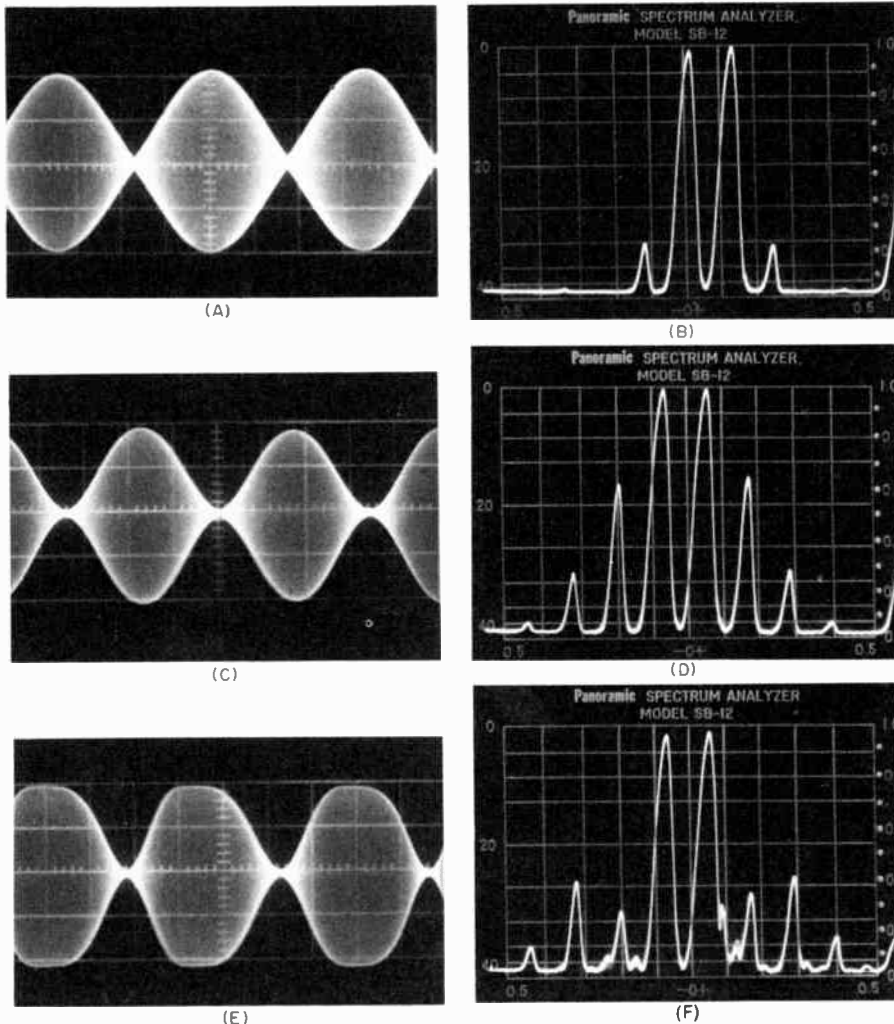


Fig. 50 — Scope patterns for a two-tone test signal and corresponding spectrum-analyzer displays. The pattern in A is for a properly adjusted transmitter and consequently the IMD products are relatively low as can be seen on the analyzer display. At C, the PA bias was set to zero idling current and considerable distortion can be observed. Note how the pattern has changed on the scope and the increase in IMD level. At E, the drive level was increased until the flattopping region was approached. This is the most serious distortion of all since the width of the IMD spectrum increases considerably causing splatter (F).



sine-wave function. This can be seen in Fig. 50C. One of the disadvantages of the scope and two-tone test method is that a relatively high level of IMD-product voltage is required before the waveform seems distorted to the eye. For instance, the waveform in Fig. 50C doesn't seem too much different than the one in Fig. 50A but the IMD level is only 17 dB below the level of the desired signal (see analyzer display in Fig. 50D). A 17- to 20-dB level corresponds to approximately 10-percent distortion in the voltage waveform. Consequently, a "good" waveform means the IMD products are at least 30 dB below the desired tones. Any noticeable departure from the waveform in Fig. 50A should be suspect and the transmitter operation should be checked.

The relation between the level at which distortion begins for the two-tone test signal and an actual voice signal is a rather simple one. The maximum deflection on the scope is noted (for an acceptable two-tone test waveform) and the transmitter is then operated such that voice peaks are kept below this level. If the voice peaks go above this level, a type of distortion called "flattopping" will occur and the results are shown for a two-tone test signal in Fig. 50E. IMD-product levels raise very rapidly when flattopping occurs. For instance, third-order product levels will increase 30 dB for every 10-dB increase in desired output as the flattopping region is approached, and fifth-order terms will increase by 50 dB (per 10 dB).

### Interpreting Distortion Measurements

Unfortunately, considerable confusion has grown concerning the interpretation and importance of distortion in ssb gear. Distortion is a very serious problem when high spurious-product levels exist at frequencies removed from the passband of the desired channel but is less serious if such products fall within the bandwidth of operation. In this former case, such distortion may cause needless interference to other channels ("splatter") and should be avoided. This can be seen quite dramatically in Fig. 50F when the flattopping region is approached and the fifth and higher order terms increase drastically.

On the other hand, attempting to suppress in-band products more than necessary is not only difficult to achieve but may not result in any noticeable increase in signal quality. In addition, measures required to suppress in-band IMD often cause problems at the expense of other qualities such as efficiency. This can lead to serious difficulties such as shortened tube life or transistor heat-dissipation problems.

The two primary causes of distortion can be seen in Fig. 51. While the waveform is for a single-tone input signal, similar effects occur for the two-tone case.

As the drive signal is increased, a point is reached where the output current (or voltage) cannot follow the input and the amplifier saturates. This condition is often referred to as flattopping (as mentioned previously). It can be prevented by ensuring that excessive drive doesn't occur and the usual means of accomplishing this is by alc action. The alc provides a signal that is used to lower the gain of earlier stages in the transmitter.

The second type of distortion is called "cross-over" distortion and occurs at low signal levels. (See Fig. 51.) Increasing the idling plate or collector current is one way of reducing the effect of cross-over distortion in regards to producing undesirable components near the operating frequency. Instead, the components occur at frequencies considerably removed from the operating frequency and can be eliminated by filtering.

As implied in the foregoing, the effect of distortion, frequencywise, is to generate components which add or subtract in order to make up the complex waveform. A more familiar example would be the harmonic generation caused by the nonlinearities often encountered in amplifiers. However, a common misconception which should be avoided is that IMD is caused by fundamental-signal components beating with harmonics. Generally speaking, no such simple relation exists. For instance, single-ended stages have relatively poor second-harmonic suppression but with proper biasing to increase the idling current, such stages can have very good IMD-suppression qualities.

However, a definite mathematical relation does exist between the desired components in an ssb signal and the "distortion signals." Whenever nonlinearities exist, products between the individual components which make up the desired signal will occur. The mathematical result of such multiplication is to generate other signals of the form  $(2f_1 - f_2)$ ,  $(3f_1)$ ,  $(5f_2 - f_1)$  and so on. Hence the term intermodulation-distortion products. The "order" of such products is equal to the sum of the multipliers in front of each frequency component. For instance, a term such as  $(3f_1 - 2f_2)$  would be called a fifth-order term since  $3+2$  is equal to 5. In general, the third, fifth, seventh, and similar "odd-order" terms are the most important ones since some of these fall near the desired transmitter output frequency and can't be eliminated by filtering. As pointed out previously, such terms do not normally result from fundamental components beating with harmonics. An exception would be when the fundamental signal along with its harmonics is applied to another nonlinear stage such as a mixer. Components at identical frequencies as the IMD products will result.

When two equal tones are applied to an amplifier and the result is displayed on a spectrum analyzer, the IMD products

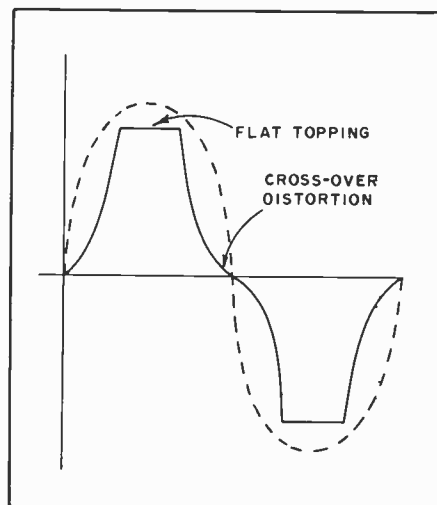


Fig. 51 — Waveform of an amplifier with a single-tone input showing flattopping and cross-over distortion.

appear as "pips" off to the side of the main signal components (Fig. 50). The amplitudes associated with each tone and the IMD products are merely the dB difference between the particular product and one tone. However, each desired tone is 3 dB down from the average power output and 6 dB down from the PEP output.

Since the PEP represents the most important quantity as far as IMD is concerned, relating IMD-product levels to PEP is one logical way of specifying the "quality" of a transmitter or amplifier in regard to low distortion. For instance, IMD levels are referenced to PEP in "Product Review" specifications of commercially made gear in QST. PEP output can be found by multiplying the PEP input by the efficiency of the amplifier. The input PEP for a two-tone test signal is given by

$$PEP = E_p I_p \left[ 1.57 - 0.57 \frac{I_o}{I_p} \right]$$

where  $E_p$  = the plate voltage  
 $I_p$  = the average plate current  
 $I_o$  = the idling current

Generally speaking, most actual voice patterns will look alike (in the presence of distortion) except in the case where severe flattopping occurs. This condition is not too common since most rigs have an alc system which prevents overdriving the amplifiers. However, the voice pattern in a properly adjusted transmitter usually has a "Christmas tree" shape when observed on a scope and an example is shown in Fig. 52.

### Mathematical Relation Between Amplifier Nonlinearity and IMD Products

The term *intermodulation-distortion product* is often used and the following derivation shows how it is related to

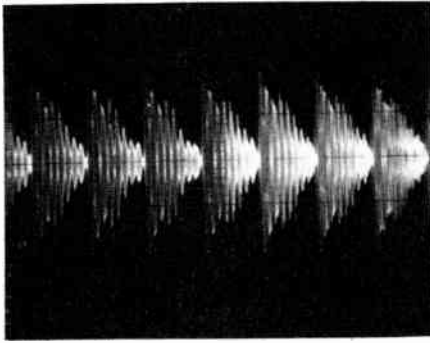


Fig. 52 — Speech pattern of the word "X" in a properly adjusted ssb transmitter.

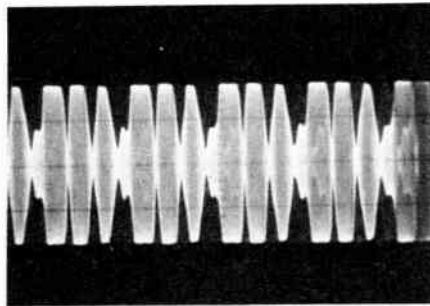


Fig. 53 — Severe clipping (same transmitter as Fig. 52 but with high drive and alc disabled).

amplifier nonlinearity. The output of an amplifier can be related to the input by means of a power series of the form:

$$S = A + Br + Cr^2 + Dr^3 + Er^4 + \dots$$

where

s = some parameter such as output voltage or current

r = some input quantity (voltage or current)

A, B, C, and other constants are primarily determined by the amplifier nonlinearity. A represents a dc term and can be neglected. In an ideal amplifier with no distortion, C, D, and the constants for the higher exponent terms will be zero and only the constant for the "linear" term, B, will exist. Consequently, the output quantity will be an exact replica of the input.

If the output is plotted against the input, a straight line will result, hence the term "linear operation." On the other hand, if distortion is present, the C, D and other constants will not be zero. The values of the constants will be such that as r increases, the higher order terms will add (or subtract) so that s follows the input-output curve of the amplifier.

For a two-tone test signal, r can be represented by the following formula:

$$r = R_0 (\cos \omega_1 t + \cos \omega_2 t); \quad \omega_1 = 2\pi f_1 \\ \omega_2 = 2\pi f_2$$

where f<sub>1</sub> and f<sub>2</sub> are the frequencies of the two tones. If this equation for r is substituted into the power series, many

terms will result and the algebra involved to find each one would be rather tedious. However, the purpose here is only to show how the IMD products come about. For instance, some terms will yield products such as

$$(\cos^2 \omega_1 t) (\cos \omega_2 t)$$

The squared term can be expanded by a trigonometric formula:

$$\cos 2 \omega_1 t = \frac{1 + \cos 2 \omega_1 t}{2}$$

This gives rise to a term  $\cos 2\omega_1 t \cos \omega_2 t$  which can be expanded by another trigonometric formula to give:

$$\cos 2 \omega_1 t \cos \omega_2 t = \frac{1}{2} \left[ \cos (2\omega_1 + \omega_2) t + \cos (2\omega_1 - \omega_2) t \right]$$

The second term in the bracket represents a third-order IMD "product" which falls close to the ssb passband. Notice that the exponents of the product functions which gave rise to this term are 2 and 1, respectively, hence the term "third-order" product. The manner in which the terms increase will depend upon the distortion curve but generally speaking, the amplitude will follow a law which is proportional to r raised to a power x, where x is the order of the term.

### A Modern Solid-State VOX

In March 1964 *QST*, Campbell<sup>21</sup> described a simple and inexpensive voice-operated relay (VOX) device which he called "a VOX in a box." Today, most manufactured ssb transceivers include a VOX function. It would seem that insufficient time or effort has gone into the design of some commercial VOX circuits, because performance is often poor. The VOX unit described here retains Campbell's concepts of a small, low-cost device, but ICs and modern circuit techniques have been employed to improve operational characteristics.

### Circuit Description

Two integrated circuits, an LM3900 (a quad of Norton operational amplifiers) and a type 555 timer have been used in the VOX circuit. Each IC is currently priced at 50 cents. A description of the 555 has previously appeared in *QST*<sup>22</sup> and will not be repeated here. The Norton circuit is an unusual type of operational amplifier in which the differential input transistors of a conventional op amp have been replaced by a "current mirror" circuit to obtain a noninverting input directly from

<sup>21</sup>Campbell, "A VOX in a Box," *QST*, March, 1964.

<sup>22</sup>Technical Topics, "Time — IC Controlled", *QST*, June, 1972.

<sup>23</sup>Blakeslee, "Some Thoughts on Station Control," *QST*, January, 1966.

<sup>24</sup>Blakeslee, "A Solid-State VOX," *QST*, September, 1970.

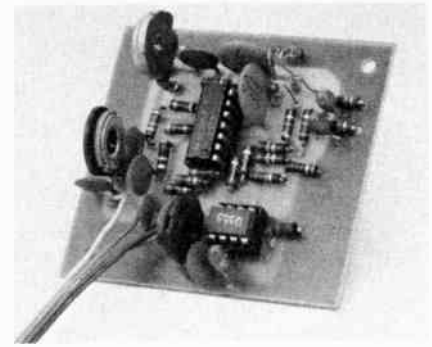


Fig. 54 — The unit shown here was designed and built by N1RM. It originally appeared in March 1976 *QST*.

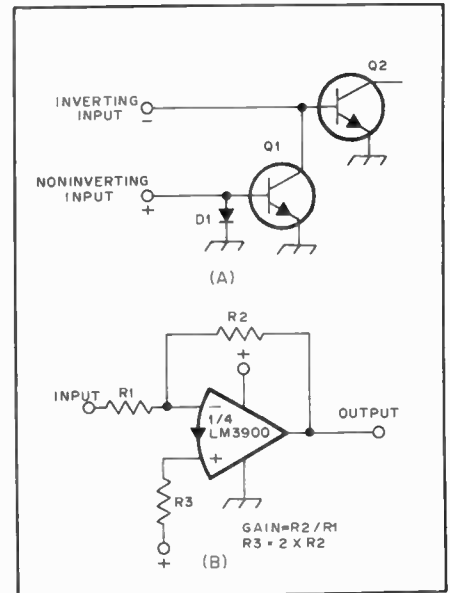


Fig. 55 — (A) Simplified input circuit for a Norton operational amplifier, such as used in the National Semiconductor LM3900. (B) Design equations for an audio amplifier using the LM3900.

the inverting input. One advantage of this circuit arrangement is operation from a single supply voltage. A simplified diagram of the input portion of the Norton amplifier is shown in Fig. 55A. D1 and the base-emitter junction of Q2 clamp the maximum input voltages at approximately 0.5 volt. External series resistors are employed to convert voltage changes to current differences which are applied to the input terminals. D1 and Q1 form the mirror circuit which assures that the bias current at both inputs will be the same; whatever bias voltage is applied to the noninverting input will be reproduced for the inverting input.

The basic design data for the LM3900 amplifiers are given in Fig. 55B. At audio frequencies, the maximum gain of a single stage is 40 dB, while the open-loop gain is specified at approximately 70 dB. Input bias current is rated at 30 nanoamperes (nA). Each of the four op amps in the LM3900 may be operated independently.

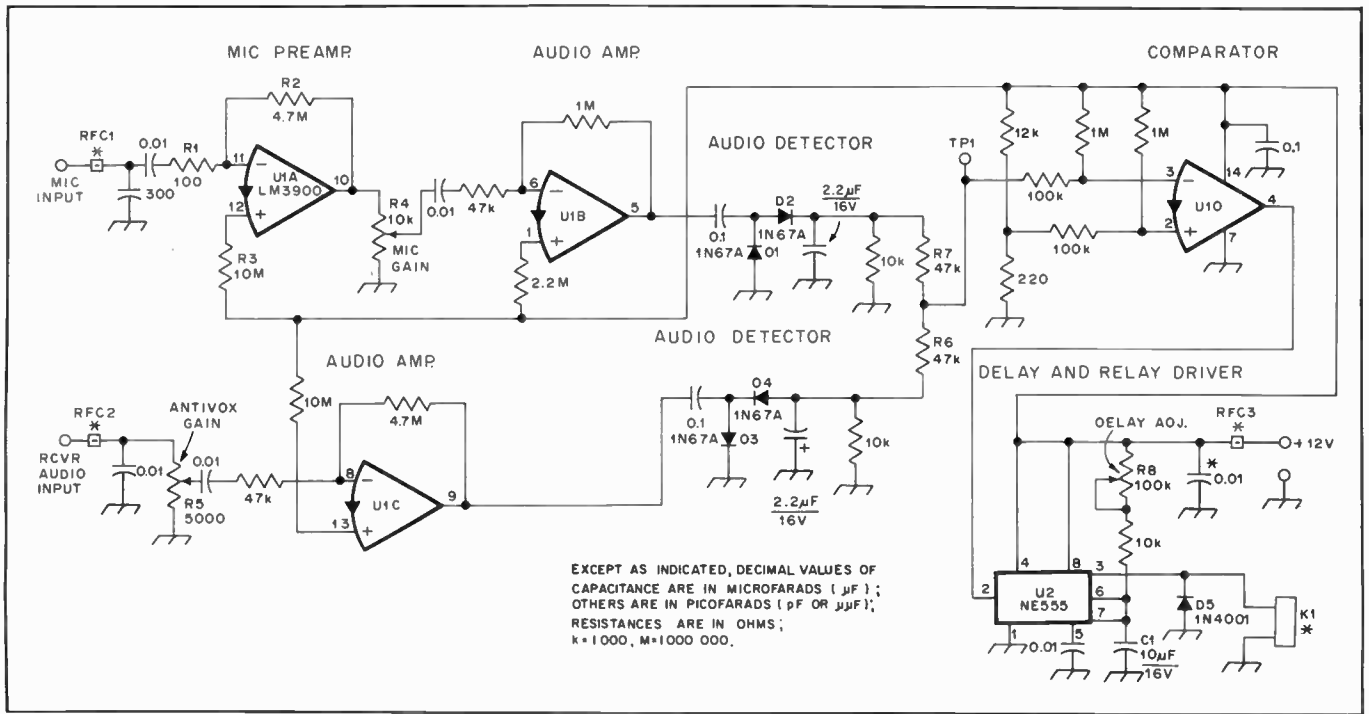


Fig. 56 — Schematic diagram of the VOX unit. Unless otherwise specified, resistors are 1/4-watt composition. Capacitors with polarity marked are plastic-encapsulated tantalum; others are disk ceramic.

C1 — For text reference.  
 D1 to D4, incl. — Germanium diode, 1N34A, 1N67 or equivalent.  
 D5 — Silicon diode, 50 PRV or more, 1N4001 or

similar.  
 K1 — Miniature type, 12-volt coil (see text).  
 R1-R3, incl., R6, R7 — For text reference.  
 R4, R5, R8 — Miniature control (see text).

RFC1-RFC3, incl. — Ferrite bead.  
 U1 — National Semiconductor LM3900.  
 U2 — Type 555 timer

The schematic diagram of the VOX device is shown in Fig. 56. Three of the LM3900 sections have been configured as high-gain audio amplifiers. U1A and U1B amplify the signal from the microphone. When a high-output microphone is employed, or when the audio signal is sampled after a preamplifier stage, the builder may wish to reduce the gain of U1A. This can be accomplished by changing the values of R1 and R2 in accordance with the design equations in Fig. 55B. If R2 is changed, the value of R3 must be modified so that R3 is twice the resistance of R2. U1C functions as an amplifier for audio sampled at the station speaker. Coupling capacitors in the audio stages have been chosen to reduce response below 300 Hz. This will minimize hum problems.

Outputs from the microphone and speaker amplifiers are capacitively coupled to rectifier stages which convert the audio signals to varying dc voltages. Germanium diodes, because of the lower threshold voltage, have been used as audio rectifiers instead of silicon units. The outputs of the two rectifier stages are summed resistively by means of R6 and R7, and applied to the inverting input of a voltage comparator, U1D. The output of U1D remains high (approximately 0.5 volt less than the supply voltage) so long as the voltage at the noninverting input is less than the 0.2-volt reference applied to the inverting input. Whenever the input

exceeds the reference, the output of the comparator goes low — to near the ground or common potential. Voltage output from the microphone-signal rectifier is positive and, thus, will cause the comparator to switch as soon as the reference is exceeded. Because the speaker-signal rectifier produces negative voltage, it will not trigger the comparator. If the outputs of the two rectifiers are equal, as will happen when the microphone is picking up audio from the speaker, the resulting voltage from the summing network will be zero and the comparator will not trigger. The ability to reject speaker audio is usually called the *antivox* function.

The positive-to-ground transition of the comparator output starts the timing cycle of the 555. The length of the time cycle is determined by the values used for R9 and C1. The time delay produced is identical each time the microphone signal stops. One of the major difficulties of earlier VOX circuits was that capacitor discharge circuits were used where the capacitor would not always be fully charged, so the time delay produced would vary. Operators compensated for the uncertain time delay by using a modified version of the English language; an *ahhh*, *oohh*, or *errr* was inserted after each word to assure that the VOX relay would not drop out prematurely.

The 555 has a current-switching capability of 200 mA, sufficient to directly

drive either a relay or a solid-state switching arrangement. D5 is included to protect the IC from transients generated when switching an inductive load such as a relay coil.

#### Components and Construction

The VOX unit is constructed on a 2-3/8 × 2-3/4-inch (60 × 70-mm) etched circuit board. The photo indicates that one-third of the board real estate is unused, so a smaller version is possible. The type of controls and relay employed will be determined by the builder's individual requirements. This writer's unit uses pc-mount controls which are aligned on the board so that they may be accessed through small holes in the rear panel of the transceiver. If panel-mount controls are desired, Mallory MLC units may be used for R4, R5 and R8.

The VOX device is small enough so it can be mounted inside most rigs. If a separate VOX unit is needed, a small utility box or Minibox will make an appropriate housing. Rf interference can cause trouble, so the unit should be shielded in any application where rf fields may be present. The bypass capacitors for the audio inputs are located on the circuit board. If the leads from the audio connectors are more than a few inches long, the bypass capacitors and their associated ferrite-bead chokes should be mounted at the connectors.

No provision has been made for



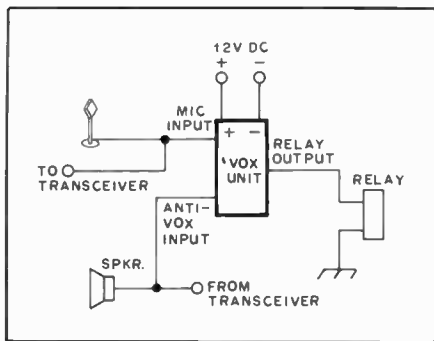


Fig. 57 — Typical connections to the VOX unit.

mounting the relay on the circuit board, as the type of relay will depend on how the VOX device will be used. Any 12-volt relay which requires less than 200 mA of current can be employed. When the VOX relay must drive a second relay, such as the antenna relay in a transceiver, the fast

operating time of a reed relay is needed to prevent clipping of the first syllable spoken. The total close time of all relays connected in tandem should be 10 milliseconds or less. If the VOX relay will perform all switching functions directly, a miniature control relay such as the Potter & Brumfield R10 series is appropriate. These relays are available in 2-, 4- and 6-pole versions, part numbers R10-E1-Y2-185, R10-E1-Y4-V185 and R10-E1-Y6-V90, respectively.

The circuit board is designed for 1/4-watt resistors which are mounted flat. If 1/2-watt units are used, they must be positioned vertically. Care must be employed when mounting and soldering the germanium diodes. If the leads are bent too close to the body of the diode, breakage can result. If excessive heat is applied to the diode, it can be damaged, so use a heat sink (such as a small alligator clip) when soldering. Assure that proper

polarity is observed when installing the diodes and tantalum capacitors.

### Installation and Operation

Typical connections for the VOX unit are shown in Fig. 57. Shielded cable should be used for all audio connections. Audio for the antivox function can be sampled at the station speaker or at the phone-patch output (which is a feature of many commercial transceivers). If VOX operation of a cw rig is desired, connect the output of a sidetone monitor to the microphone input of the VOX unit. The mic gain control should be set so that the VOX relay closes each time a word is spoken. The delay control should be adjusted to fit individual speech patterns and operating habits. The delay time must be long enough that the VOX relay will drop out only during a pause in speech. There are two methods of setting the antivox gain control. The first way is

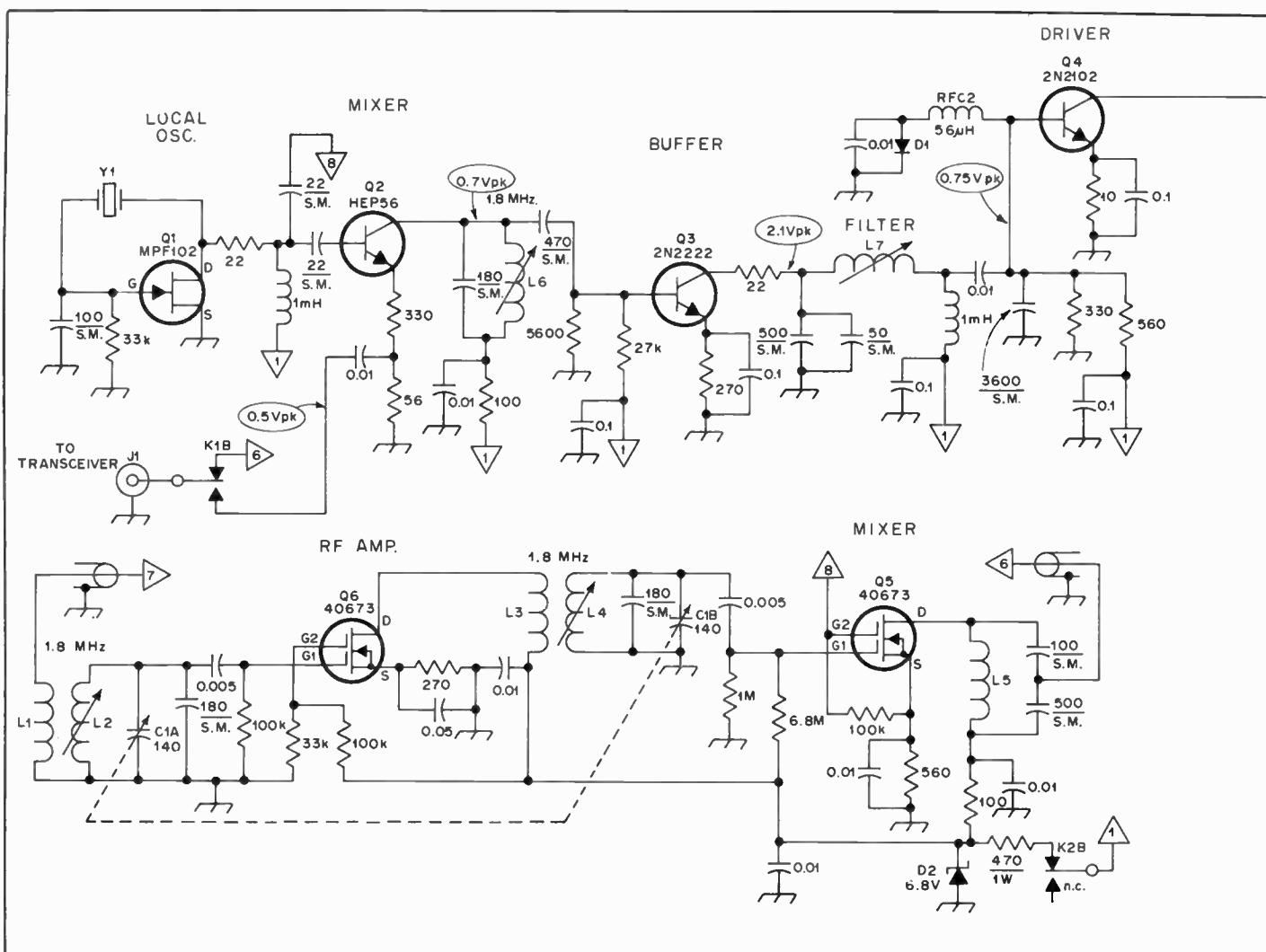


Fig. 59 — Schematic diagram for the transverter. Resistors are 1/2-watt composition and capacitors are disk ceramic, unless otherwise noted.

- C1 — Dual-section air variable, 140 pF per section, or two 150 pF air variable units.
- C2 — Air variable, Millen 19280.
- C3 — Dual-section broadcast variable, 365 pF per section, both sections connected in parallel.
- D1 — Silicon, 50 PRV, 100 mA.

- D2 — Zener diode, 6.8-volt, 1-watt (1N4736).
- J1 — Phono type, chassis mount.
- J2 — Coaxial receptacle, chassis mount.
- K1, K2 — 12-V dc, 2-A contacts, dpdt relay (Radio Shack 275-206).
- L1 — 11 turns of no. 28 enam. wire wound over L2.

- L2, L4 — 19.5 to 24.3- $\mu$ H variable inductor (Miller 46A 225CPC).
- L3 — 22 turns of no. 28 enam. wire wound on L4 coil form.
- L5 — 18.8 to 41.0- $\mu$ H variable inductor, Miller 42A335CPC.



simply to advance the control until audio from the speaker does not trip the VOX unit. A more scientific approach is to connect a voltmeter to TPI. With no audio input, the meter should read only the comparator reference voltage, approximately 0.1 volt. Tune the receiver to provide a steady tone signal, such as the heterodyne note from a crystal calibrator. Advance the antivoix control until the voltmeter registers only the reference voltage. The antivoix gain should be set with the audio from the speaker slightly louder than is necessary during normal operation.

VOX control can be a helpful operating aid. It can speed up traffic handling and contest operation. It might make roundtable discussions more natural. The unit described here will help to eliminate some of the operator idiosyncrasies that have become associated with VOX operation. The operators themselves can

cure the rest.

### A Transverter for 1.8 MHz

Owners of five-band transceivers often get the urge to try "top band." Converting a transceiver to cover a frequency range for which the rig was not designed is difficult indeed. A far better approach is to build an outboard transverter, such as the one described here. This particular system requires one watt of drive power at either 21 or 28 MHz. Many transceivers can provide this low-level output along with the power supply voltages through an accessory socket.

### The Circuit

A schematic diagram of the transverter is given in Fig. 59. Q1 operates as a crystal oscillator, to produce the local-oscillator energy for the receive (Q5) and transmit (Q2) mixing stages, which runs continuously. During transmit 21.1 MHz ssb


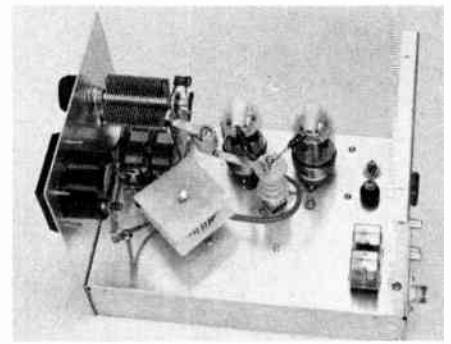


Fig. 58— Top view of transverter with cover removed. Final amplifier circuit is at the left. The rear apron has an accessory socket for an external power supply (transceiver), rf, and remote-keying connectors. The plate meter is at the lower left

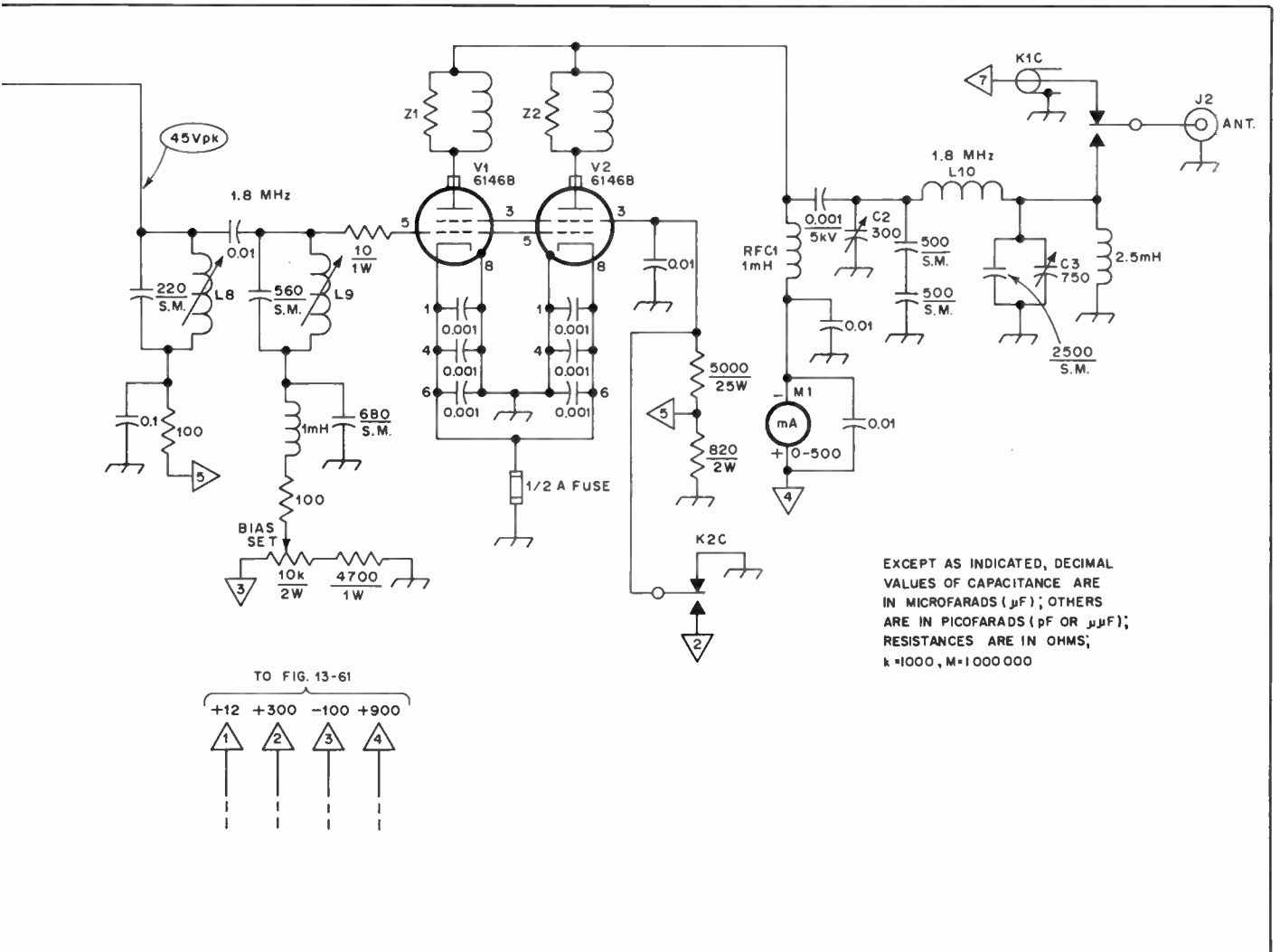or cw energy is supplied to the emitter of Q2 through a power divider network. This signal is mixed with the 19.3-MHz output



- L6, L8 — 35 to 43.0- $\mu$ H variable inductor, Miller 46A395CPC.
- L7 — 13.2 to 16.5- $\mu$ H variable inductor, Miller 46A155CPC.
- L9 — 10.8 to 18.0- $\mu$ H adjustable coil, Miller 21A155RBI.

- L10 — 42 turns, no. 16 enam. wire equally spaced on a T-200 Amidon core.
- M1 — 500 mA, panel mount, Simpson 17443 or similar.
- Q5, Q6 — RCA 40673 MOSFET.
- RFC1 — 1-mH, 500-mA rf choke, Johnson

- 102-572.
- RF2 — 56- $\mu$ H rf choke, Millen J-302-56.
- Y1 — 19.3-MHz crystal is used for a 21-MHz i-f, 26.5-MHz crystal for a 28-MHz i-f.
- Z1, Z2 — 2 turns, no. 18 enam. wound over 47-ohm, 2-watt composition resistor.

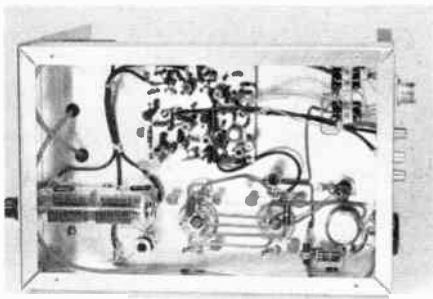


Fig. 60 — The bottom view of the chassis, the sockets for the 6146B tubes are at the lower center. The etched-circuit board is above the final amplifier tube sockets and the T-R relays at the upper right. The different supply voltages are obtained from the associated transceiver.

from the LO producing 1.8 MHz power, which is amplified by Q3, followed by a filter network. Q4 provides adequate drive to the pair of 6146Bs. The PA stage operates Class AB1, which will deliver in excess of 100 watts PEP output.

During receive, an incoming signal is amplified by Q6, a dual-gate, diode-protected MOSFET. The output from the rf amplifier is mixed with local-oscillator energy at Q5 to produce a receiving i-f of 21 MHz. The crystal frequency is the only change required to make this system

usable at 28 MHz. Changeover from transmit to receive is accomplished by K1 and K2 which are controlled by the associated transceiver. If the LO frequency is 19.3 MHz, the 1.8 to 2.0 MHz band will correspond with 21.1 to 21.3 MHz on the transceiver dial. Likewise, with a 26.5 MHz crystal in the LO circuit, the 160-meter band will appear between 28.3 and 28.5 MHz.

If the various supply voltages can not be obtained from the transceiver, an economy power supply shown in Fig. 61 can be used. The 6.3- and 5-volt windings of T1 are series-connected to provide 11.5 volts to power K1 and K2, the receiving converter and the predriver stages of the transmitting section. The windings must be phased properly to prevent voltage cancellation. If no output is obtained when the windings are connected, reverse the leads of one winding. The 11.3-volt ac is rectified by D6.

Bias voltage is obtained for V1 and V2 by connecting a 6.3-volt filament transformer in back-to-back fashion with the 6.3-volt winding of T1. The 125-volt ac output from T2 is rectified, filtered, and then routed to the bias-adjust control, R1, to establish a PA resting plate current of 50 mA.

The metering circuit consists of a 500 mA meter connected in the plate voltage

line. Other meters may be employed by using the proper shunts, as described in the Measurements Chapter.

### Construction

An aluminum chassis that measures 7 × 11 × 2 inches (178 × 279 × 51 mm) is used as the base for the transverter. A homemade panel and cabinet enclose the unit. The front panel is 8 × 7-1/4 inches (203 × 184 mm). The layout employed should be apparent from the photographs. All long runs of rf wiring should be made with subminiature coaxial cable (RG-174/U or similar).

The receiver section, driver stages and local oscillator are constructed on a double-sided printed-circuit board measuring 3 × 3-1/2 inches (76 × 89 mm). Inductors L1 and L2 are mounted on the chassis close to C1. Short leads are used from the circuit board to the "pre-selector" capacitor and L1-L2 which are located on the underside of the chassis. The final tank inductor is wound on an Amidon T-200 toroid core. It is supported above the chassis by a ceramic standoff insulator and two pieces of Plexiglas.

### Tune Up

Provision must be made to reduce the power output of most transceivers used with the transverter since only about one watt of drive power is required. Too much rf voltage can damage the HEP S0016 and will "smoke" the input resistors. Some transceivers are capable of delivering sufficient drive by removing the screen voltage from the PA stage. Or, it may be practical to disable the PA and obtain a sample of driver output by a link-coupling circuit.

Before testing the transverter, assure that the changeover relays, K1 and K2, are connected to the remote-keying terminals of the transceiver. Then connect an antenna to J2 and listen for signals. Peak the incoming signals with the preselector

Fig. 61 — Diagram of the power-supply section. Resistors are 1/2-watt composition. Capacitors are disk ceramic, except those with polarity marked which are electrolytic.  
 D2-D5, incl. — Silicon, 1000 PRV, 1 A.  
 D6, D7 — Silicon, 400 PRV, 1 A.  
 J3 — Phono type, chassis mount.  
 K1, K2 — See Fig. 59.  
 L11 — Power choke, 130 mA, Allied 6X24HF or equiv.

- S1 — Spst toggle.
- T1 — Power transformer, 117-V primary; secondary windings 740 V ct at 275 mA, 6.3 V at 7 A, and 5 V at 3 A, Stancor P-6315 or equiv.
- T2 — Filament transformer, 117-V primary; 6.3-V, 1-A secondary.


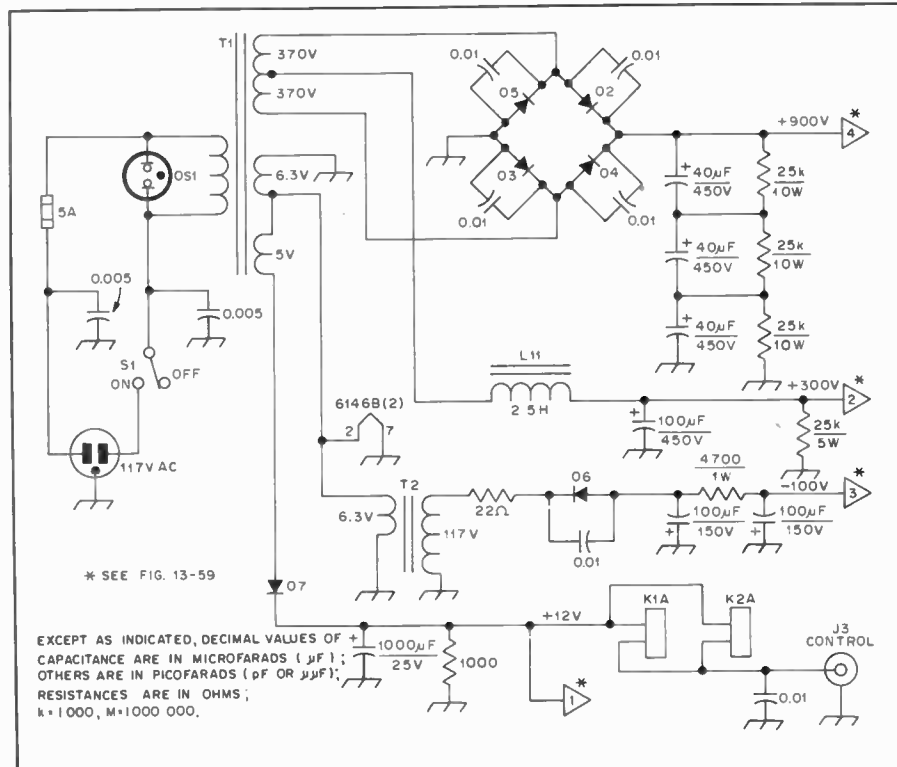


Fig. 62 — Close-up view of the printed-circuit board. This board has the local oscillator, receiver, and low-level driver stages. The crystal socket and crystal for the LO are shown at the lower left.

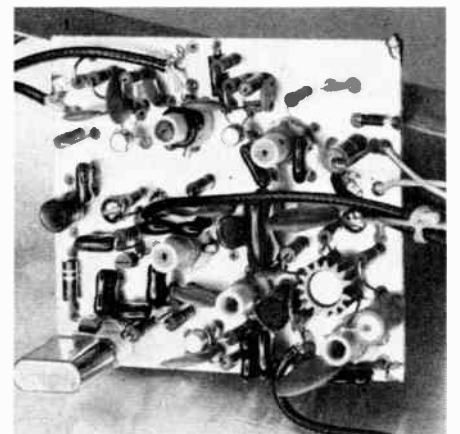

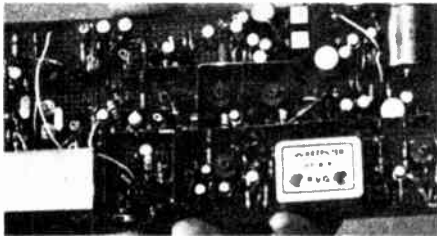


Fig. 63 — The small size of the module built by ON5FE is evident from this photograph. It contains a complete transceiver i-f system, including speech amplifier/balanced modulator for transmitting and product detector/audio amplifier for receiving along with VOX and clipping circuits.

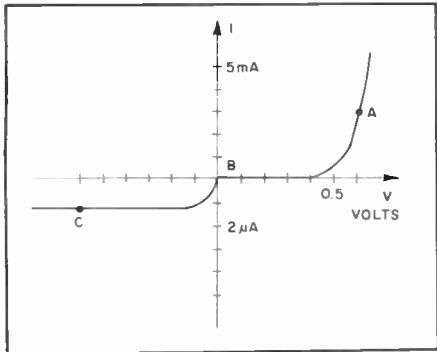


Fig. 64 — Typical current-vs. voltage characteristic of a silicon diode. Note change in current scale below horizontal axis.

control. The slugs of L2 and L4 should be adjusted for the highest S-meter reading on the transceiver. L5 should be set for maximum output at 21 or 28 MHz. If the receiving converter is functioning properly, it will be possible to copy a 0.1  $\mu$ V signal without difficulty in areas where atmospheric and man-made noise are at a minimum. If no signals can be heard, check Q1 to make certain that it is working properly. A wavemeter or general-coverage receiver can be employed to

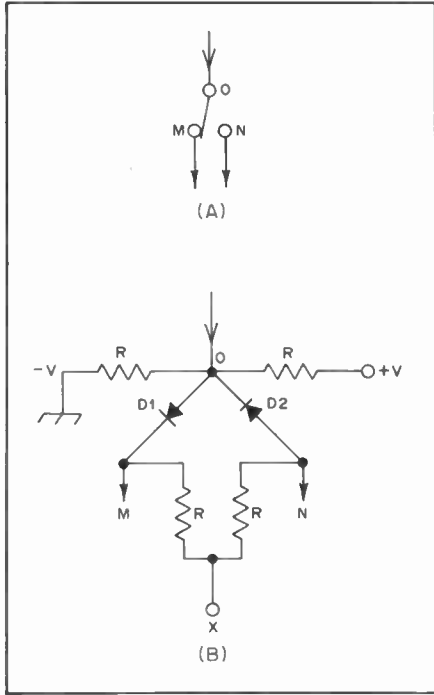


Fig. 65 — Conventional switch (A) and corresponding diode switch (B). V is the source of voltage required for biasing the diodes, forward for conduction, reverse for nonconduction. Resistors R are needed for isolating the switched circuit from the dc source.

see if the crystal oscillator is operating. Attach a 50-ohm load to J2 before testing the transmitter section. Set R1 for an indicated resting plate current of 50 mA on M1. This adjustment should be made without drive applied but with K1 and K2 energized. Next, apply about one watt of 21.1-MHz cw drive power at J1. Tune L6, L7, L8 and L9 for maximum meter reading. While monitoring the plate current, tune C2 for a dip. C3 is the PA loading control. When the PA capacitors

are properly adjusted, the plate current will be about 220 mA.

### Transistor Module for SSB Transceivers: A Complete I-F/Audio System


Because of the many advantages to be gained with a transceiver, separate receiver-transmitter configurations are used less often these days. Economy may be the most important reason; obviously, one circuit is cheaper than two, and there is needless duplication in separate units. Some other advantages are weight and size reduction, especially for mobile use, and ease of operation. However, a transceiver must often be more sophisticated because of the switching problems.

These switching problems are not to be minimized, particularly when switching a "hot" lead from receive to transmit. Spurious signals can be induced in the wiring going to relay contacts. Also, energizing the relay may change such circuit parameters as stray capacitance and lead coupling. For example, the load capacitance on a crystal filter may change appreciably when switching from receive to transmit. These troubles can be avoided by diode switching. Briefly, this is how it works:

A diode forward-biased by a few milliamperes dc (point A on Fig. 64) loses its rectifying property for small alternating currents. That is, a small reduction  $\Delta i$  in the polarization current may be interpreted as a current  $\Delta i$  passing through the diode in the reverse direction. For this  $\Delta i$ , the diode acts as a dynamic resistance of about 50 ohms.

In order to make the diode look like an open circuit, it is usually only necessary to reduce the bias voltage to zero, which results in a dynamic resistance of about 100 k $\Omega$  (operating point B). However, the diode is usually back-biased to point C to avoid eventual rectification problems and

Fig. 66 — Block diagram of the sss module (part enclosed in dashed lines) together with the remaining essentials for a complete transceiver. The module includes i-f, balanced modulator and audio circuits, and provides 9-MHz sss output for transmitting.

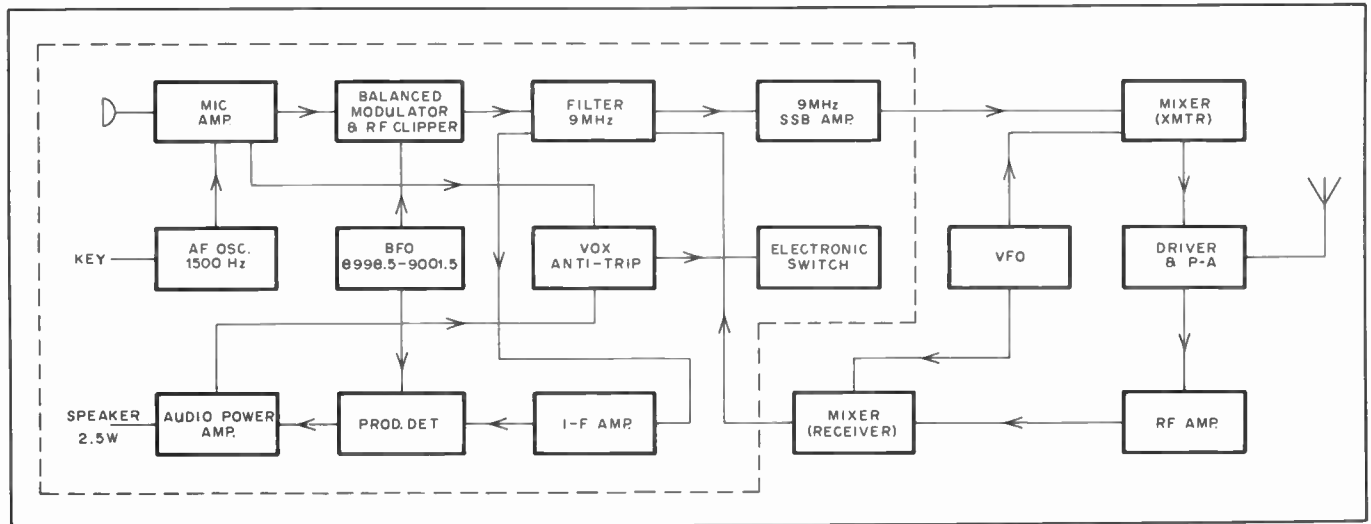

to reduce the effective junction capacitance. This results in a more positive switching action.

Fig. 65A shows a conventional spdt switch, while Fig. 65B is the diode equivalent. If X is connected to  $-V$ , D1 conducts and D is off. The ac signal passes through D1 from point O to M as in the conventional switch. Switching is accomplished by changing X from  $-V$  to  $+V$  ( $V$  is the power-supply voltage) which turns D1 off and D2 on. The signal current must be small compared to the dc bias current to avoid nonlinearity.

### Overall System

A block diagram of the complete transceiver is given in Fig. 66. This section covers only the blocks within the dotted outline. Design problems with the VFO, driver and power amplifier will not be treated here. Note that there are separate channels for transmitting and receiving; only the filter is switched.

This approach is different from the one often taken in commercial transceivers where, for instance, the i-f amplifier is used for transmit as well as for receive. It may seem that components are being duplicated, and it is true that this circuit arrangement does not offer any advantage if only a simple transceiver is being designed. However, if features such as VOX and rf clipping are desired, the circuit results in a simpler overall design because only one pair of switching points is needed.

### Microphone Amplifier and VOX System

The gain of the microphone amplifier in Fig. 67 is 45 dB, and its input impedance is about 150 k $\Omega$ . This high impedance can be obtained with a transistor if it is operated at very low collector current (30  $\mu$ A), providing it retains a high  $h_{fe}$  at this current. The approximate formula is

$$Z_{in} = \frac{26}{i_c} h_{fe}$$

where  $i_c$  = collector current (mA)  
 $h_{fe}$  = small-signal current gain

Since noise has an effect at this first stage, a low-noise transistor is used and the emitter-follower configuration must be avoided.

There is no microphone gain control, as it was found to be useless because of the rf clipping in later stages. The output is from the emitter and collector of Q3; the balanced modulator gets the emitter signal while the collector output is rectified in a voltage doubler to operate VOX. The amplifier supplies 4 V pk-pk output before clipping. Heavy clipping, by talking too loud, must be avoided, but light clipping on higher voice peaks will cause no trouble. The clipping level can be varied from linear (no clipping) to 30 dB

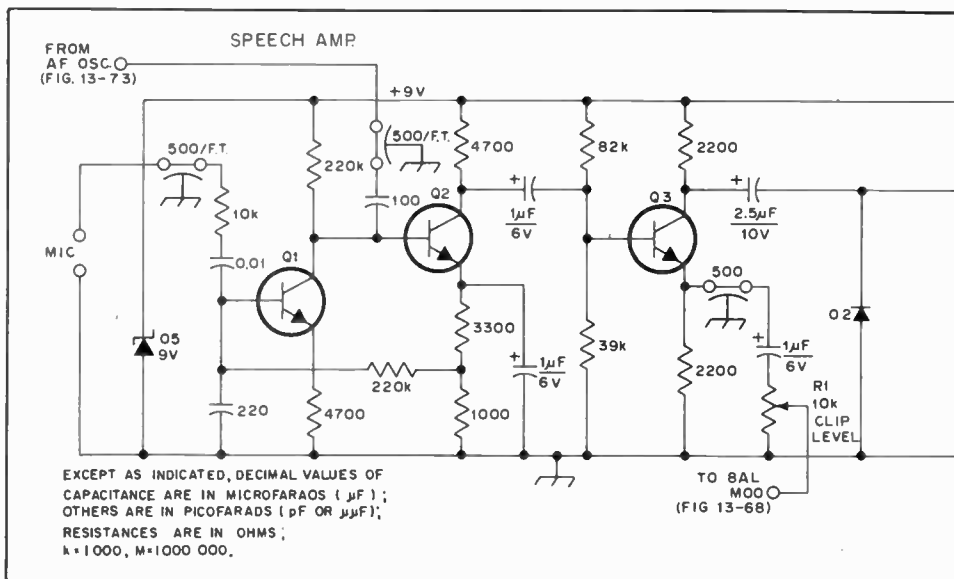


Fig. 67 — Microphone amplifier, VOX circuit, and electronic send-receive switch. Capacitors with polarity marked are electrolytic; others are ceramic. Fixed resistors are 1/4 or 1/2 watt. Labeled components not listed are for text reference.

by adjustment of potentiometer R1 in the emitter output circuit. Complete rf decoupling of the microphone amplifier is indispensable.

The VOX circuit is straightforward. Its sensitivity is adjusted by potentiometer R3, which sets the forward-bias level at

the base of Q4 when the microphone amplifier is operating. During reception Q4 is cut off, which in turn cuts off Q5. Under these conditions Q6 is saturated since it is biased for heavy conduction through R5. The point labeled R is at nearly +12 V when Q6 is on; this voltage


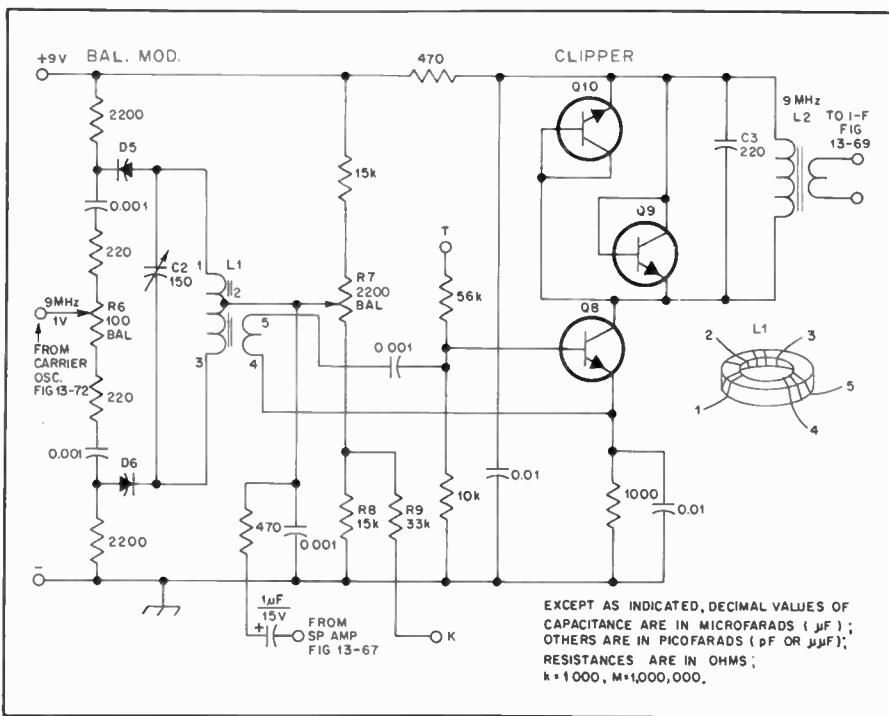


Fig. 68 — Balanced modulator and rf clipper circuit. Inset shows construction of  $L_1$  toroid with terminal numbers. Capacitor with polarity marked is electrolytic; other fixed capacitors are ceramic. Fixed resistors are 1/4 or 1/2 watt. Labeled components not listed below are for text reference.  
 C2 — 150-pF miniature variable.  
 C3 — Mica.  
 L1, L2 — Toroid, pri./sec. turns ratio 14:4; primary to resonate at 9 MHz with C2 and C3 respectively (app 3  $\mu$ H and 1.5  $\mu$ H, respectively). Terminal 2 on primary is a center tap.  
 D5, D6 — Varactor diode; see text.  
 Q8, Q9, Q10 — 2N706, 2N708.  
 R6, R7 — Linear-taper potentiometer.  
 R9 — App. 33,000 ohms; see text.

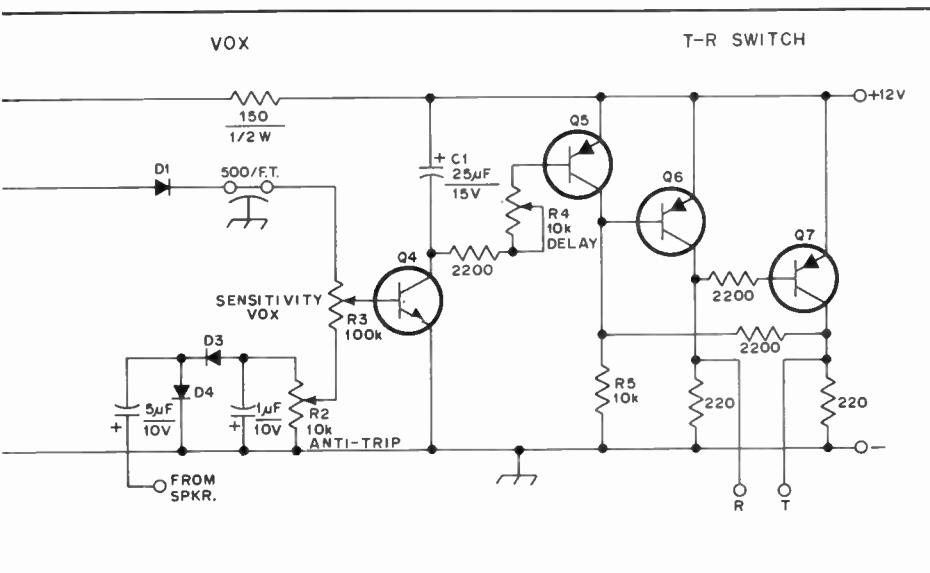



D1 — Zener, 9 volts, 1/2 watt.  
 D2-D5, incl. — Germanium, any type.  
 Q1, Q2, Q4 —  $I_{CBO}$  0.1  $\mu$ A (max) npn,  $h_{FE}$  100 (min.), C450, BC113 or equivalent.

Q3 — 2N706, 2N708.  
 Q5 — AC125, AC126, 2N1301 or equivalent.  
 Q6, Q7 — AC128, 2N1496 or equivalent.  
 R1-R4, incl. — Linear-taper potentiometer.

operates the diode switching circuit for receive, as mentioned earlier. When the rectified VOX signal applies positive bias to the base of Q4 this transistor saturates, turning on Q5, which then cuts off Q6 because the voltage at the base of Q6 rises to nearly +12 V. Q6 and Q7 form a bistable flip-flop, and with Q6 off Q7 goes on, supplying 12 V for the transmit circuits at point T. C1 and R4 hold Q5 on during momentary pauses in speaking.

Feedback from the speaker to the microphone is avoided by means of the antitrip circuit, which also uses a rectifying voltage doubler but with the diodes connected for negative dc output voltage. Adjustment is by R2. The three adjustments, VOX, antitrip and delay, are nearly independent.

### Balanced Modulator and RF Clipper

The balanced modulator, Fig. 68, uses two varactor diodes, back-biased at 4.5 volts through potentiometer R7, which is adjusted to cancel any mismatch in the diodes' characteristics. The 9-MHz carrier is applied to the arm of R6, and due to symmetry, no voltage will be developed across the 9-MHz resonant circuit, LIC2. The audio voltage is applied to the arm of R7, causing the capacitance of the varactors to vary in opposite directions and thus aiding each other in the unbalancing. An interesting feature of this circuit is that the input is asymmetric — i.e., single-ended — for both the high-frequency and audio signals. Also, the input impedances are much greater than those of the classical four-diode modulator.

Inductor L1 is constructed on a toroidal core because the coupling must be purely magnetic if a high carrier-rejection ratio is to be obtained. Note that the modulator

can be easily unbalanced by connecting a resistance in parallel with R8 (point K grounded). In this way, cw or a-m signals can be produced. The a-m signal could be taken from the open secondary of L1 with point K at ground, although this possibility of producing a-m is not used in the present circuit.

European coil forms were used throughout this transceiver so information on the number of turns would be nearly useless if different coil forms are used. The turns ratio will provide sufficient information. One can easily construct suitable coils with his own material with the help of a grid-dip meter. The requirements are

- Audio: 4 V pk-pk max.
- Carrier: 1 V rms.
- Carrier rejection: Better than 50 dB.
- Turns ratio on L1:  $n_p/n_s = 14/4$ .
- Varactor diodes:  $C = 20$  pF at  $-4$  V (not critical).
- Output: 200 mV pk-pk rf for 2.8 V pk-pk audio input.

Distortion seems to be less than with the four-diode modulator. It is not necessary to have well-matched varactors; their differences may be cancelled by adjustment of R7.

### RF Clipper

It is well known that speech remains intelligible even with infinite clipping; in other words, the amplitude contains relatively little information regarding intelligibility. However, keep in mind that in the absence of noise at the receiver a clipped signal will always be less intelligible than a normal signal without clipping. It is only under marginal conditions (high noise level) that clipping presents an appreciable improvement. Consequently, the operator must maintain control of the clipping level. Using

the peak power as reference (and this is a good approach to the problem, because ssb transmitters are limited by their peak power rather than their average power dissipation) it has been found that the following degrees of improvement can be obtained:

	Clipping Amount	Improvement
Audio clipping	15 dB	4 dB
	25 dB	5.5 dB
Rf ssb clipping	10 dB	4 dB
	20 dB	8 dB

The table indicates, for example, that during marginal conditions an rf ssb clipping level set at 20 dB can have a peak power 8 dB under the peak power of an unclipped signal and maintain the same intelligibility. The table also shows that rf clipping has greater efficiency than audio clipping. This is because in rf clipping most of the spurious signals created fall outside the passband. However, a crystal filter must always follow rf clipping in order to eliminate spurious signals near the edge of the band and to avoid transmitting an excessively broad spectrum. Unfortunately, the crystal filter is presently the most expensive item in a single-sideband transmitter. To economize, we decided to clip the dsb signal and use only one filter to extract ssb and to follow the clipping stage. But "you get what you pay for," and dsb clipping creates more intermodulation products inside the transmitted bandwidth than ssb clipping does.

The rf clipper is a standard clipping circuit, except that two transistors in diode configuration are used instead of two diodes. The clipping action is slightly better. Two examples of rf clipping at different levels can be seen in the photographs taken at the collector of Q8. The third picture, taken at the output of Q12, Fig. 69, is two-tone test modulation with strong clipping, after passing through the crystal filter. It shows some distortion, but at an acceptable level. When using a high clipping level, note that the plate of the power amplifier must dissipate a significantly higher average power.

### Crystal Filter

A commercial European filter (KVG type XF-9A) was used. Its characteristics are

- Bandwidth: 2.5 kHz at  $-6$  dB.
- Passband irregularities: Less than 1 dB.
- Insertion loss: Less than 3 dB.
- Spurious response: Less than 45 dB.
- Shape factor: 1/1.7, 6 dB/50 dB.
- Input and output impedances: R = ohms, C = 30 pF.

If this low-cost German filter is not available,<sup>25</sup> any filter can be used with minor changes in R10, R11 and R13.

<sup>25</sup>KVG filters are available in the U.S. from Spectrum International, P.O. Box 1084, Concord, MA 01742.

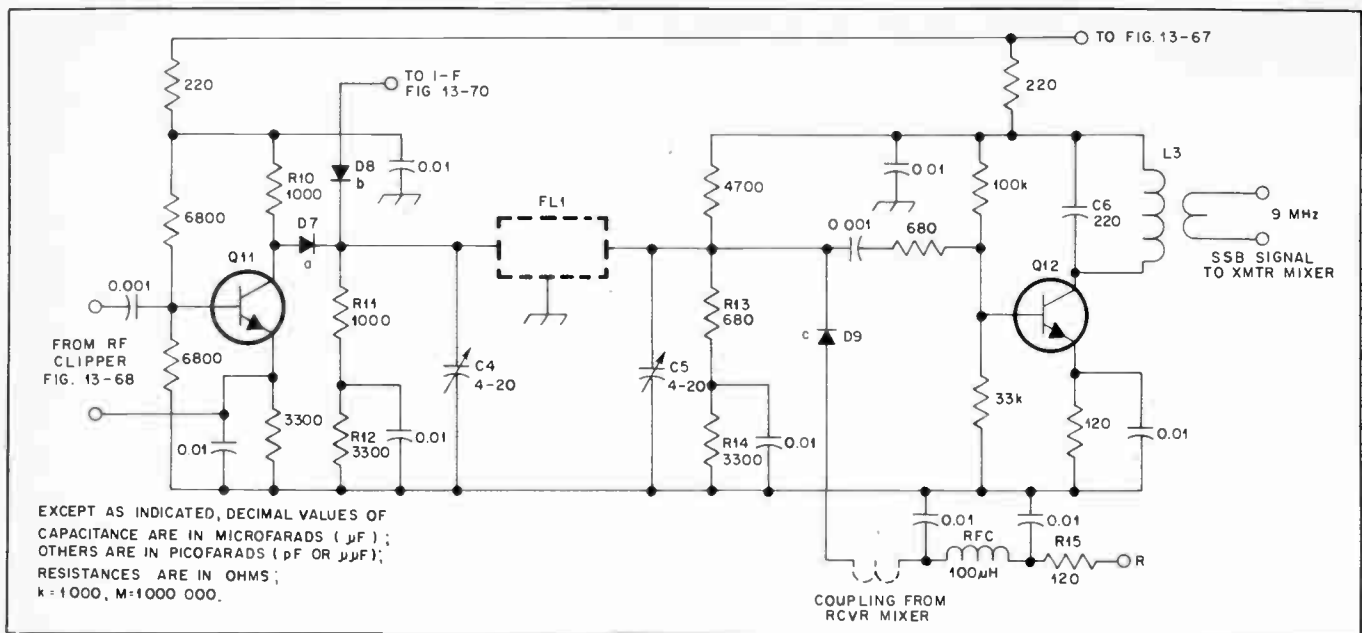


Fig. 69 — Crystal filter and diode switching circuit. Fixed capacitors are ceramic, fixed resistors are 1/4 or 1/2 watt. Labeled components not listed below are for text reference.

C4, C5 — Trimmer, 4-20 pF.

C6 — Mica.

D7, D8, D9 — Silicon, fast recovery (Fairchild

FD-100).

L3 — Same as L2, Fig. 68.

Q11, Q12 — 2N706, 2N708.

FL1 — 9-MHz crystal filter, 2.5-kHz bandwidth; see text.

Q11 provides the correct input impedance for the filter. Q12 is a buffer stage providing 12 V pk-pk on its collector. This signal is large enough to feed a vacuum-tube mixer. If a transistorized mixer is desired, suitable matching is needed and it is recommended that a balanced mixer be used.

### Filter Switching

During transmit, point T is at 12 volts and point R is at about 1 volt. D8 then conducts through R10, R11 and R12. D9 and D10 are back-biased.

During receive, T is at about 1 volt and R is at 12 volts. D10 now is forward-biased through R13, R14 and R15. The signal from the mixer is applied to the filter through D10, D8 is back-biased; D9 conducts through R16 and R17 (see i-f schematic, Fig. 70) passing the filtered ssb to the i-f amplifier.

### I-F Amplifier and Product Detector

The traditional transistorized hf amplifier (common-emitter circuit) does not respond to agc as well as its vacuum-tube counterpart. The LC circuit is detuned and the Q varies when the agc acts. In Fig. 70 these troubles are avoided by using two transistors per stage in a cascode arrangement. The first transistor is stable because its load is the very low input impedance of the next transistor, which is in a common-base configuration. The second transistor is stable in this common-base arrangement, so the LC circuit is practically independent of agc action. The gain of a cascode amplifier is slightly greater than that of a single transistor in

the common-emitter mode. At 9 MHz the gain may be 50 dB or more per stage. Unfortunately, 80 dB cannot be obtained with one cascode stage and two stages provide too much gain. In order to reduce the gain, R18 must be decreased until the gain is reduced to the optimum 80-dB figure.

The agc amplifier is Q17, which also controls the S meter. The agc dynamic range is 0 to -70 dB without distortion. When no signal is present, the collector

current of Q17 is zero. When a signal is received, the transistor begins to conduct, causing a voltage drop in R19 and reducing bias current in the cascade stages. The agc has a fast action and slow decay due to C7. Q17 can discharge C7 very rapidly, but the capacitor must recharge through R19. The time constant is 1/2 second. Note that C7 is not grounded; this prevents the S meter from responding to momentary peak currents.

The RCA 3N141 dual-gate MOSFET is

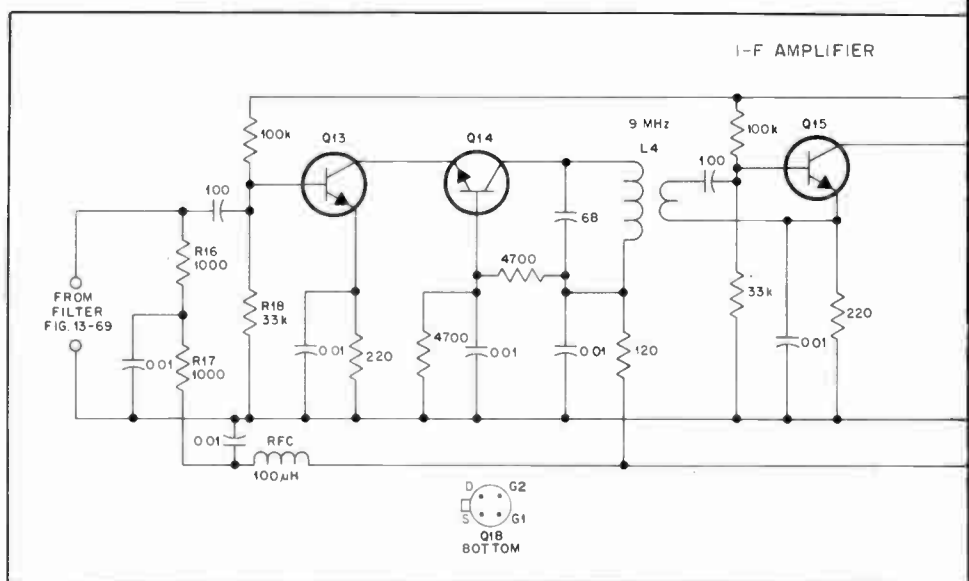


Fig. 70 — I-f amplifier and product detector. capacitors with polarity are electrolytic; others are ceramic. Fixed resistors are 1/4 or 1/2 watt. Labeled components not listed below are for text reference.

D10 — Germanium, f-m detector type.

L4, L5 — Toroid pri./sec. turns ratio 10:1; primary


to resonate at 9 MHz with 68 pF (app. 4.5  $\mu\text{H}$ ).

M1 — 0-1 dc milliammeter.









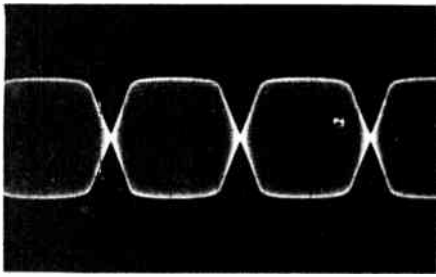

(A)

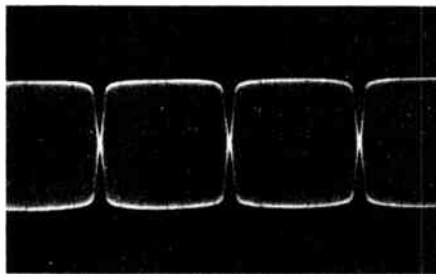

(B)

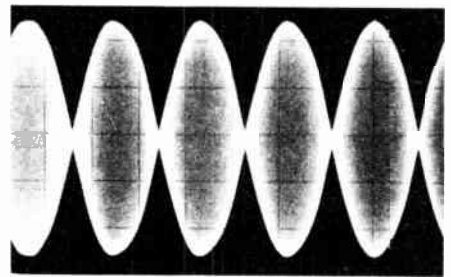

(C)

Fig. 75 — A: Single-tone signal with moderate clipping, measured at the input to the 9-MHz sideband filter. B: Same with heavy clipping. C: Heavily-clipped two-tone signal after passing through the sideband filter. Post-clipping filtering restores the original modulation envelope with little distortion.

# Frequency Modulation and Repeaters

Methods of radiotelephone communication by frequency modulation were developed in the 1930s by Major Edwin Armstrong in an attempt to reduce the problems of static and noise associated with receiving a-m broadcast transmissions. The primary advantage of fm, the ability to produce a high signal-to-noise ratio when receiving a signal of only moderate strength, has made fm the mode chosen for mobile communications services and quality broadcasting. The disadvantages, the wide bandwidth required and the poor results obtained when an fm signal is propagated via the ionosphere (because of phase distortion), has limited the use of frequency modulation to the 10-meter band and the vhf/uhf section of the spectrum.

Fm has some impressive advantages for vhf operation, especially when compared to a-m. With fm the modulation process takes place in a low-level stage and remains the same, regardless of transmitter power. The signal may be frequency multiplied after modulation, and the PA stage can be operated Class C for best efficiency, as the "final" need not be linear.

In recent years there has been increasing use of fm by amateurs operating around 29.6 MHz in the 10-meter band. The vhf spectrum now in popular use includes 52 to 54 MHz, 146 to 148 MHz, 222 to 225 MHz, and 440 to 450 MHz. The subject of fm and repeaters is covered in great depth in the ARRL publication, *FM and Repeaters for the Radio Amateur*.

## Frequency and Phase Modulation

It is possible to convey intelligence by modulating any property of a carrier, including its frequency and phase. When the frequency of the carrier is varied in accordance with the variations in a modulating signal, the result is *frequency modulation* (fm). Similarly, varying the phase of the carrier current is called *phase modulation* (pm).

Frequency and phase modulation are not independent, since the frequency

cannot be varied without also varying the phase, and vice versa.

The effectiveness of fm and pm for communication purposes depends almost entirely on the receiving methods. If the receiver will respond to frequency and phase changes but is insensitive to amplitude changes, it will discriminate against most forms of noise, particularly impulse noise such as that set up by ignition systems and other sparking devices. Special methods of detection are required to accomplish this result.

Modulation methods for fm and pm are simple and require practically no audio power. Also, since there is no amplitude variation in the signal, interference to broadcast reception resulting from rectification of the transmitted signal in the audio circuits of the bc receiver is substantially eliminated.

## Frequency Modulation

Fig. 2 is a representation of frequency modulation. When a modulating signal is applied, the carrier frequency is increased during one half cycle of the modulating signal and decreased during the half cycle of opposite polarity. This is indicated in the drawing by the fact that the rf cycles occupy less time (higher frequency) when the modulating signal is positive, and more time (lower frequency) when the modulating signal is negative. The change in the carrier frequency (*frequency deviation*) is proportional to the instantaneous amplitude of the modulating signal. Thus, the deviation is small when the instantaneous amplitude of the modulating signal is small, and is greatest when the modulating signal reaches its peak, either positive or negative.

As shown in the drawing, the amplitude of the signal does not change during modulation.

## Phase Modulation

If the phase of the current in a circuit is changed there is an instantaneous frequency change during the time the phase is being shifted. The amount of frequency



Fig. 1 — The most effective repeaters are situated well above average terrain and obstacles which could be in the signal path.

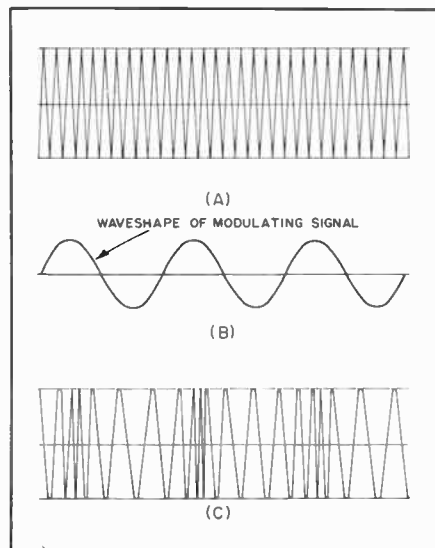


Fig. 2 — Graphical representation of frequency modulation. In the unmodulated carrier at A, each rf cycle occupies the same amount of time. When the modulating signal, B, is applied, the radio frequency is increased and decreased according to the amplitude and polarity of the modulating signal.

change, or deviation, depends on how rapidly the phase shift is accomplished. It is also dependent upon the total amount of the phase shift. In a properly operating pm system the amount of phase shift is proportional to the instantaneous amplitude of the modulating signal. The rapidity of the phase shift is directly proportional to the frequency of the modulating signal. Consequently, the frequency deviation in pm is proportional to both the amplitude and frequency of the modulating signal. The latter represents the outstanding difference between fm and pm, since in fm the frequency deviation is proportional only to the amplitude of the modulating signal.

### FM and PM Sidebands

The sidebands set up by fm and pm differ from those resulting from a-m in that they occur at integral multiples of the modulating frequency on either side of the carrier rather than, as in a-m, consisting of a single set of side frequencies for each modulating frequency. An fm or pm signal therefore inherently occupies a wider channel than a-m.

The number of "extra" sidebands which occur in fm and pm depends on the relationship between the modulating frequency and the frequency deviation. The ratio between the frequency deviation, in hertz, and the modulating frequency, also in hertz, is called the *modulating index*. That is

$$\text{Modulation index} = \frac{\text{carrier frequency deviation}}{\text{modulating frequency}}$$

Example: The maximum frequency deviation in an fm transmitter is 3000 Hz either side of the carrier frequency. The modulation index when the modulation frequency is 1000 Hz is

$$\text{Modulation index} = \frac{3000}{1000} = 3$$

At the same deviation with 3000 Hz modulation the index would be 1; at 100 Hz it would be 30, and so on.

In pm the modulation index is constant regardless of the modulating frequency; in fm it varies with the modulating frequency, as shown in the above example. In an fm system the ratio of the *maximum* carrier-frequency deviation to the *highest* modulating frequency used is called the *deviation ratio*.

Fig. 3 shows how the amplitudes of the carrier and the various sidebands vary with the modulation index. This is for single-tone modulation; the first sideband (actually a pair, one above and one below the carrier) is displaced from the carrier by an amount equal to the modulating frequency, the second is twice the modulating frequency away from the carrier, and so on. For example, if the modulating frequency is 2000 Hz and the carrier

frequency is 29,500 kHz, the first sideband pair is at 29,498 kHz and 29,502 kHz, the second pair is at 29,496 kHz and 29,504 kHz, the third at 29,494 kHz and 29,506 kHz, and so on. The amplitudes of these sidebands depend on the modulation index, not on the frequency deviation.

Note that as shown in Fig. 3, the carrier strength varies with the modulation index. (In amplitude modulation the carrier strength is constant; only the sideband amplitude varies.) At a modulation index of approximately 2.4, the carrier disappears entirely. It then becomes "negative" at a higher index, meaning that its phase is reversed compared to the phase without modulation. In fm and pm the energy that goes into the sidebands is taken from the carrier, the *total* power remaining the same regardless of the modulation index.

Since there is no change in amplitude with modulation, an fm or pm signal can be amplified without distortion by an ordinary Class C amplifier. The modulation can take place in a very low-level stage and the signal can then be amplified by either frequency multipliers or straight-through amplifiers.

If the modulated signal is passed through one or more frequency multipliers, the modulation index is multiplied by the same factor that the carrier frequency is multiplied. For example, if modulation is applied on 3.5 MHz and the final output is on 28 MHz, the total frequency multiplication is eight times, so if the frequency deviation is 500 Hz at 3.5 MHz it will be 4000 Hz at 28 MHz. Frequency multiplication offers a means for obtaining practically any desired amount of frequency deviation, whether or not the modulator itself is capable of giving that much deviation without distortion.

### Bandwidth

FCC amateur regulations (97.61) limit the bandwidth of F3 (frequency and phase modulation) to that of an a-m transmission having the same audio characteristics below 29.0 MHz and in the 50.1- to 52.5-MHz frequency segment. Greater bandwidths are allowed from 29.0 to 29.7 MHz and above 52.5 MHz.

If the modulation index (with single-tone modulation) does not exceed 0.6 or 0.7, the most important extra sideband, the second, will be at least 20 dB below the unmodulated carrier level. This should represent an effective channel width about equivalent to that of an a-m signal. In the case of speech, a somewhat higher modulation index can be used. This is because the energy distribution in a complex wave is such that the modulation index for any one frequency component is reduced as compared to the index with a sine wave having the same peak amplitude as the voice wave.

The chief advantage of fm or pm for

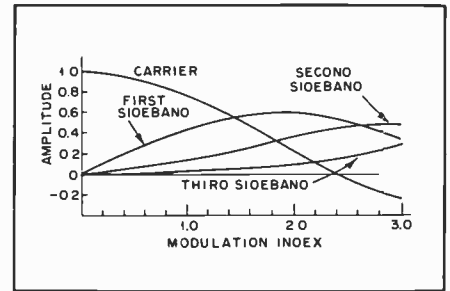


Fig. 3 — How the amplitude of the pair of sidebands varies with the modulation index in an fm or pm signal. If the curves were extended for greater values of modulation index the carrier amplitude would go through zero at several points. The same statement also applies to the sidebands.

frequencies below 30 MHz is that it eliminates or reduces certain types of interference to broadcast reception. Also, the modulating equipment is relatively simple and inexpensive. However, assuming the same unmodulated carrier power in all cases, narrow-band fm or pm is not as effective as a-m with the methods of reception used by many amateurs. To obtain the benefits of the fm mode, a good fm receiver is required. As shown in Fig. 3, at an index of 0.6 the amplitude of the first sideband is about 25 percent of the unmodulated-carrier amplitude; this compares with a sideband amplitude of 50 percent in the case of a 100 percent modulated a-m transmitter. When copied on an a-m receiver, a narrow-band fm or pm transmitter is about equivalent to a 100-percent modulated a-m transmitter operating at one-fourth the carrier power. On a suitable (fm) receiver, fm is as good or better than a-m, watt for watt.

The deviation standard now is  $\pm 5$  kHz, popularly known as *narrow band*. For a while after WW II, 2.5- to 3-kHz deviation ("sliver band") was used on 10 meters and the vhf bands. During the '60s and early '70s 15 kHz was extensively used since many amateur rigs were commercial surplus. Narrow-band deviation developed as a middle ground between audio quality and spectrum conservation. The rule-of-thumb for determination of bandwidth requirements for an fm system is

$$2(\Delta F) + F_{A \max}$$

where

$$\Delta F = 1/2 \text{ total frequency deviation}$$

$$F_{A \max} = \text{maximum audio frequency (3 kHz for communication purposes)}$$

Thus, for narrow-band fm, the bandwidth equals  $(2)5 + 3$  or 13 kHz. Wide-band systems need a 33-kHz receiver bandwidth.

### Comparison of FM and PM

Frequency modulation cannot be applied to an amplifier stage, but phase modulation can; pm is therefore readily adaptable to transmitters employing oscillators of high stability such as the

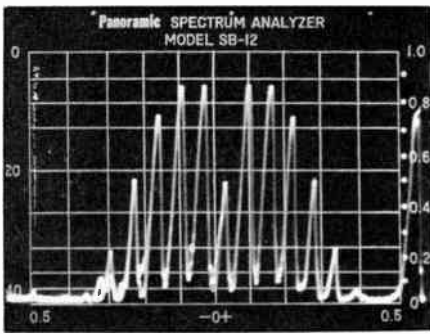


Fig. 4 — Output frequency spectrum of a narrow-band fm transmitter modulated by a 1-kHz tone.

crystal-controlled type. The amount of phase shift that can be obtained with good linearity is such that the maximum practicable modulation index is about 0.5. Because the phase shift is proportional to the modulating frequency, this index can be used only at the highest frequency present in the modulating signal, assuming that all frequencies will at one time or another have equal amplitudes. Taking 3000 Hz as a suitable upper limit for voice work, and setting the modulation index at 0.5 for 3000 Hz, the frequency response of the speech-amplifier system above 3000 Hz must be sharply attenuated, to prevent excess splatter. (See Fig. 4.) Also, if the "tinny" quality of pm as received on an fm receiver is to be avoided, the pm must be changed to fm, in which the modulation index decreases in inverse proportion to the modulating frequency. This requires shaping the speech-amplifier frequency-response curve in such a way that the output voltage is inversely proportional to frequency over most of the voice range. When this is done the maximum modulation index can only be used to some relatively low audio frequency, perhaps 300 to 400 Hz in voice transmission, and must decrease in proportion to the increase in frequency. The result is that the maximum linear frequency deviation is only one or two hundred Hz, when pm is changed to fm. To increase the deviation for narrow band requires a frequency multiplication of eight or more.

It is relatively easy to secure a fairly large frequency deviation when a self-controlled oscillator is frequency-modulated directly. (True frequency modulation of a crystal-controlled oscillator results in only very small deviations and so requires a great deal of frequency multiplication.) The chief problem is to maintain a satisfactory degree of carrier stability, since the greater the inherent stability of the oscillator the more difficult it is to secure a wide frequency swing with linearity.

#### Frequency Modulation Methods: Direct FM

A simple, satisfactory device for producing fm in the amateur transmitter is

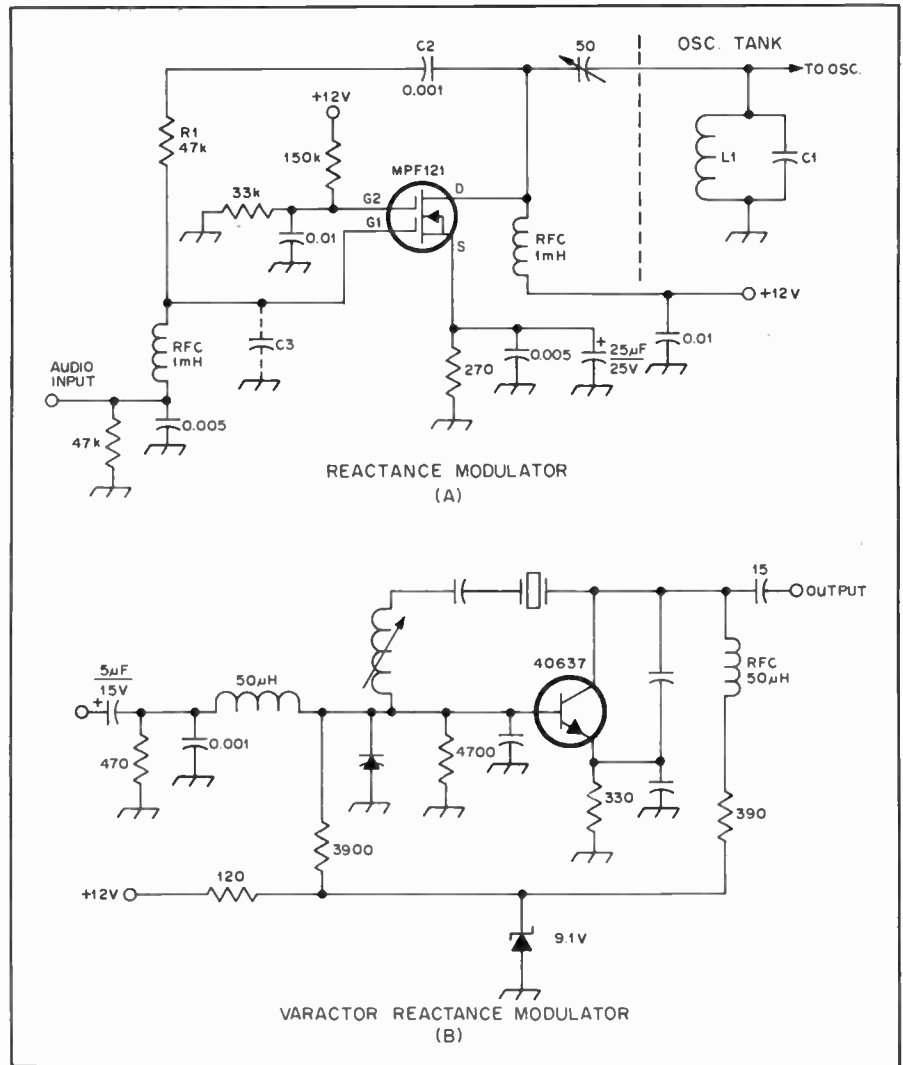


Fig. 5 — Reactance modulators using (A) a high-transconductance MOSFET and (B) a varactor diode.

the reactance modulator. This is a vacuum tube or transistor connected to the rf tank circuit of an oscillator in such a way as to act as a variable inductance or capacitance.

Fig. 5A is a representative circuit. Gate 1 of the modulator MOSFET is connected across the oscillator tank circuit, C1/L1, through resistor R1 and blocking capacitor C2. C3 represents the input capacitance of the modulator transistor. The resistance of R1 is made large compared to the reactance of C3, so the rf current through R1/C3 will be practically in phase with the rf voltage appearing at the terminals of the tank circuit. However, the voltage across C3 will lag the current by 90 degrees. The rf current in the drain circuit of the modulator will be in phase with the grid voltage, and consequently is 90 degrees behind the current through C3, or 90 degrees behind the rf tank voltage. This lagging current is drawn through the oscillator tank, giving the same effect as though an inductance were connected across the tank. The frequency increases in proportion to the amplitude of the lagging plate current of the modulator. The audio voltage, introduced through a

radio-frequency choke, varies the transconductance of the transistor and thereby varies the rf drain current.

The modulated oscillator usually is operated on a relatively low frequency, so that a high order of carrier stability can be secured. Frequency multipliers are used to raise the frequency to the final frequency desired.

A reactance modulator can be connected to a crystal oscillator as well as to the self-controlled type as shown in Fig. 5B. However, the resulting signal can be more phase-modulated than it is frequency-modulated, for the reason that the frequency deviation that can be secured by varying the frequency of a crystal oscillator is quite small.

The sensitivity of the modulator (frequency change per unit change in grid voltage) depends on the transconductance of the modulator transistor. It increases when R1 is made smaller in comparison with C3. It also increases with an increase in L/C ratio in the oscillator tank circuit. However, for highest carrier stability it is desirable to use the largest tank capacitance that will permit the desired devia-



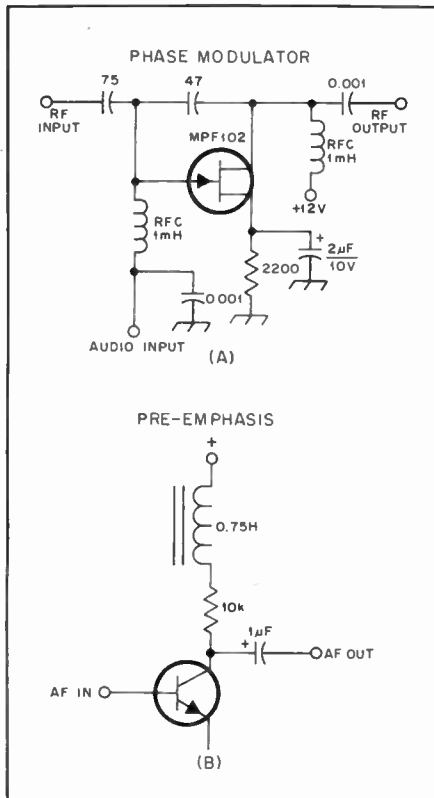


Fig. 6 — (A) The phase-shifter type of phase modulator. (B) preemphasis and (C) deemphasis circuits.

tion to be secured while keeping within the limits of linear operation.

A change in *any* of the voltages on the modulator transistor will cause a change in rf drain current, and consequently a frequency change. Therefore it is advisable to use a regulated power supply for both modulator and oscillator.

### Indirect FM

The same type of reactance-tube circuit that is used to vary the tuning of the oscillator tank in fm can be used to vary the tuning of an amplifier tank and thus vary the phase of the tank current for pm. Hence the modulator circuit of Fig. 5A or

6A can be used for pm if the reactance transistor or tube works on an amplifier tank instead of directly on a self-controlled oscillator. If audio shaping is used in the speech amplifier, as described above, fm instead of pm will be generated by the phase modulator.

The phase shift that occurs when a circuit is detuned from resonance depends on the amount of detuning and the Q of the circuit. The higher the Q, the smaller the amount of detuning needed to secure a given number of degrees of phase shift. If the Q is at least 10, the relationship between phase shift and detuning (in kHz either side of the resonant frequency) will be substantially linear over a phase-shift range of about 25 degrees. From the standpoint of modulator sensitivity, the tuned circuit Q on which the modulator operates should be as high as possible. On the other hand, the effective Q of the circuit will not be very high if the amplifier is delivering power to a load since the load resistance reduces the Q. There must therefore be a compromise between modulator sensitivity and rf power output from the modulated amplifier. An optimum Q figure appears to be about 20; this allows reasonable loading of the modulated amplifier and the necessary tuning variation can be secured from a reactance modulator without difficulty. It is advisable to modulate at a low power level.

Reactance modulation of an amplifier stage usually results in simultaneous amplitude modulation because the modulated stage is detuned from resonance as the phase is shifted. This must be eliminated by feeding the modulated signal through an amplitude limiter or one or more "saturating" stages — that is, amplifiers that are operated Class C and driven hard enough so that variations in the amplitude of the input excitation produce no appreciable variations in the output amplitude.

For the same type of reactance modulator, the speech-amplifier gain required is the same for pm as for fm. However, as

pointed out earlier, the fact that the actual frequency deviation increases with the modulating audio frequency in pm makes it necessary to cut off the frequencies above about 3000 Hz before modulation takes place. If this is not done, unnecessary sidebands will be generated at frequencies considerably away from the carrier.

### Speech Processing for FM

The speech amplifier preceding the modulator follows ordinary design, except that no power is taken from it and the af voltage required by the modulator grid usually is small — not more than 10 or 15 volts, even with large modulator tubes, and only a volt or two for transistors. Because of these modest requirements, only a few speech stages are needed; a two-stage amplifier consisting of two bipolar transistors, both resistance-coupled, will more than suffice for crystal ceramic or Hi-Z dynamic microphones.

Several forms of speech processing produce worthwhile improvements in fm system performance. It is desirable to limit the peak amplitude of the audio signal applied to an fm or pm modulator, so that the deviation of the fm transmitter will not exceed a preset value. This peak limiting is usually accomplished with a simple audio clipper placed between the speech amplifier and modulator. The clipping process produces high-order harmonics which, if allowed to pass through to the modulator stage, would create unwanted sidebands. Therefore, an audio low-pass filter with a cut-off frequency between 2.5 and 3 kHz is needed at the output of the clipper. Excess clipping can cause severe distortion of the voice signal. An audio processor consisting of a compressor and a clipper, such as described in chapter 12, has been found to produce audio with a better sound (i.e., less distortion) than a clipper alone.

To reduce the amount of noise in some fm communications systems, an audio shaping network called *preemphasis* is

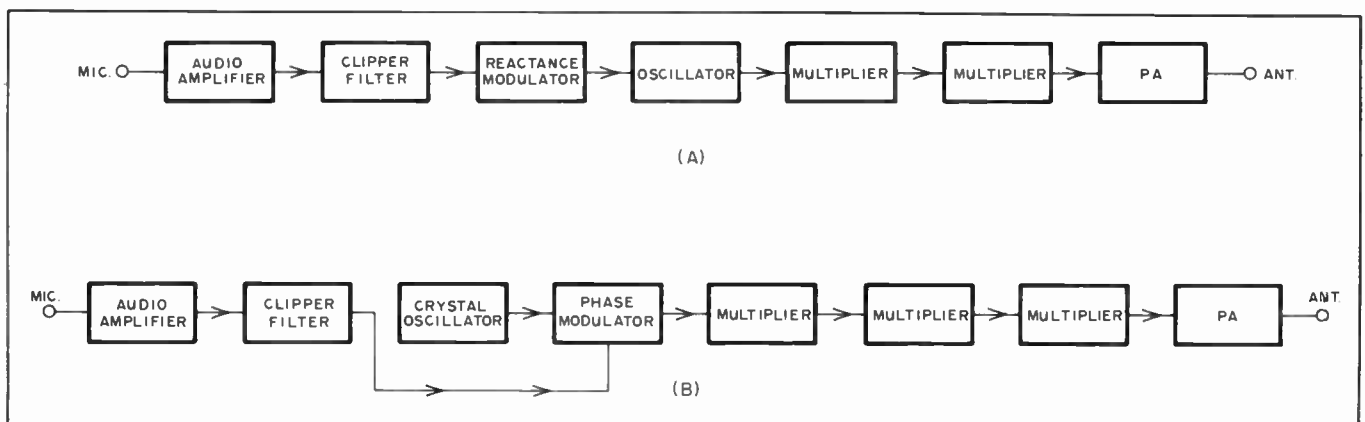


Fig. 7 — Block diagrams of typical fm exciters.

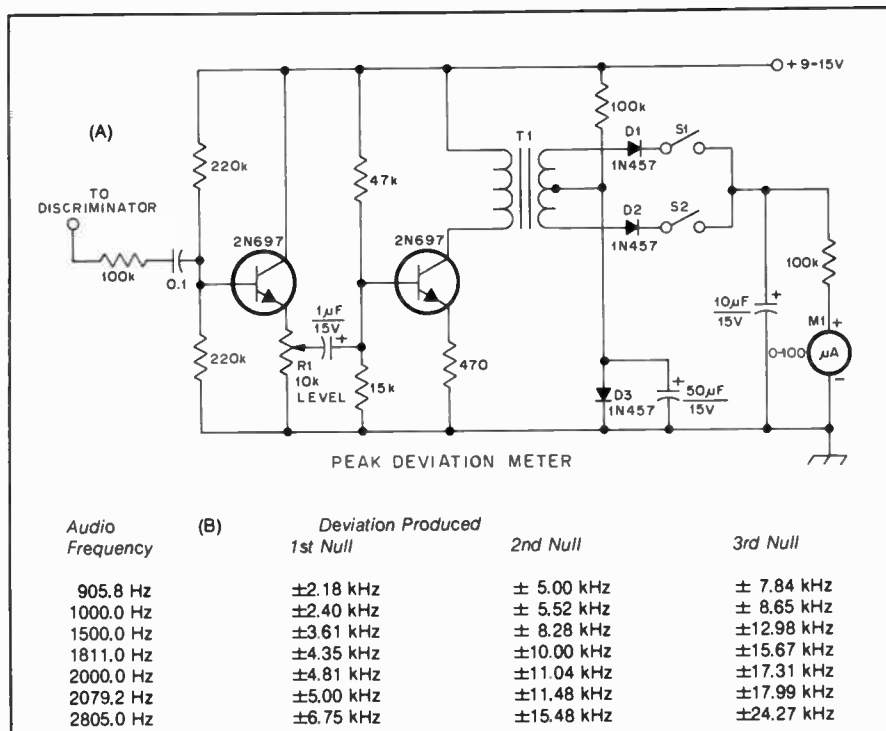


Fig. 8 — (A) Schematic diagram of the deviation meter. Resistors are 1/2-watt composition and capacitors are ceramic, except those with polarity marked, which are electrolytic. D1-D3, incl., are high-speed silicon switching diodes. R1 is a linear-taper composition control, and S1, S2 are spst toggle switches. T1 is a miniature audio transformer with 10-kΩ primary and 20-kΩ center-tapped secondary (Triad A31X). (B) Chart of audio frequencies which will produce a carrier null when the deviation of an fm transmitter is set for the values given.

added at the transmitter to proportionally attenuate the lower audio frequencies, giving an even spread to the energy in the audio band. This results in an fm signal of nearly constant energy distribution. The reverse process, called *deemphasis*, is accomplished at the receiver to restore the audio to its original relative proportions. Sample circuits are shown in Fig. 6.

### FM Exciters

FM exciters and transmitters take two general forms. One, shown at Fig. 7A, consists of a reactance modulator which shifts the frequency of an oscillator to generate an fm signal directly. Successive multiplier stages provide output on the desired frequency, which is amplified by a PA stage. This system has a disadvantage in that, if the oscillator is free running, it is difficult to achieve sufficient stability for vhf use. If a crystal-controlled oscillator is employed, because the amount that the crystal frequency is changed is kept small, it is difficult to achieve equal amounts of frequency swing.

The indirect method of generating fm shown in Fig. 7B is currently popular. Shaped audio is applied to a phase modulator to generate fm. Since the amount of deviation produced is very small, a large number of multiplier stages is needed to achieve wide-band deviation at the operating frequency. In general, the system shown at A will require a less complex circuit than that at B, but the

indirect method (B) often produces superior results.

### Testing an FM Transmitter

Accurate checking of the operation of an fm or pm transmitter requires different methods than the corresponding checks on an a-m or ssb set. This is because the common forms of measuring devices either indicate amplitude variations only (a millimeter, for example), or because their indications are most easily interpreted in terms of amplitude.

The quantities to be checked in an fm transmitter are the linearity and frequency deviation and the output frequency, if the unit uses crystal control. The methods of checking differ in detail.

### Frequency Checking

Crystal-controlled, channelized fm operation requires that a transmitter be held within a few hundred hertz of the desired channel even in a wide-band system. Having the transmitter on the proper frequency is particularly important when operating through a repeater. The rigors of mobile and portable operation make a frequency check of a channelized transceiver a good idea at three-month intervals.

Frequency meters generally fall into two categories, the heterodyne type and the digital counter. For amateur use, the vhf/uhf counterparts of the popular BC-221 frequency meter, the TS-174 and

TS-175, will provide sufficient accuracy. Frequency counters that will work directly up to 500 MHz and higher are available, but their cost is high. The less expensive low-frequency counters can be employed using a *prescaler*, a device which divides an input frequency by a preset ratio, usually 10 or 100. Many prescalers may be used at 148 MHz or higher, using a counter with a 2-MHz (or more) upper frequency limit. If the counting system does not have a sufficient upper frequency limit to measure the output of an fm transmitter directly, one of the frequency-multiplier stages can be sampled to provide a signal in the range of the measurement device. Alternatively, a crystal-controlled converter feeding an hf receiver which has accurate frequency readout can be employed, if a secondary standard is available to calibrate the receiving system.

### Deviation and Deviation Linearity

A simple deviation meter can be assembled following the diagram of Fig. 8A. This circuit was designed by K6VKZ. The output of a wide-band receiver discriminator (before any deemphasis) is fed to two amplifier transistors. The output of the amplifier section is transformer coupled to a pair of rectifier diodes to develop a dc voltage for the meter, M1. There will be an indication on the meter with no signal input because of detected noise, so the accuracy of the instrument will be poor on weak signals.

To calibrate the unit, signals of known deviation will be required. If the meter is to be set to read 0-15 kHz, then a 7.5-kHz deviation test signal should be employed. R1 is then adjusted until M1 reads half scale, 50μA. To check the peak deviation of an incoming signal, close both S1 and S2. Then, read the meter. Opening first one switch and then the other will indicate the amount of positive and negative deviation of the signal, a check of deviation linearity.

### Measurement of Deviation Using Bessel Functions

Using a mathematical relationship known as the *Bessel Function* it is possible to predict the points at which, with certain audio-input frequencies and predetermined deviation settings, the carrier output of an fm transmitter will disappear completely. Thus, by monitoring the carrier frequency with a receiver, it will be possible to identify by ear the deviation at which the carrier is nulled. A heterodyne signal at either the input or receiver i-f is required so that the carrier will produce a beat note which can easily be identified. Other tones will be produced in the modulation process, so some concentration is required by the operator when making the test. With an audio tone selected from the chart (Fig. 8B), advance the deviation control slowly until the first

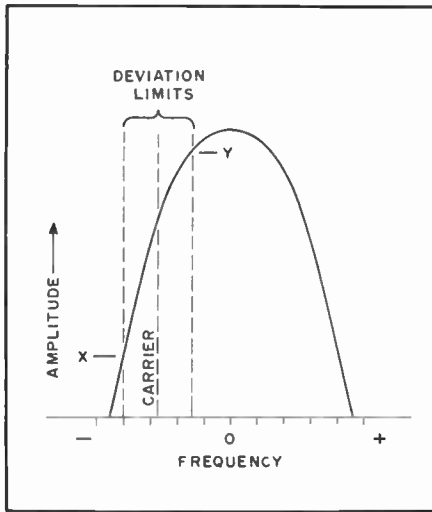


Fig. 9 — Fm detector characteristics. Slope detection, using the sloping side of the receiver's selectivity curve to convert fm to a-m for subsequent detection.

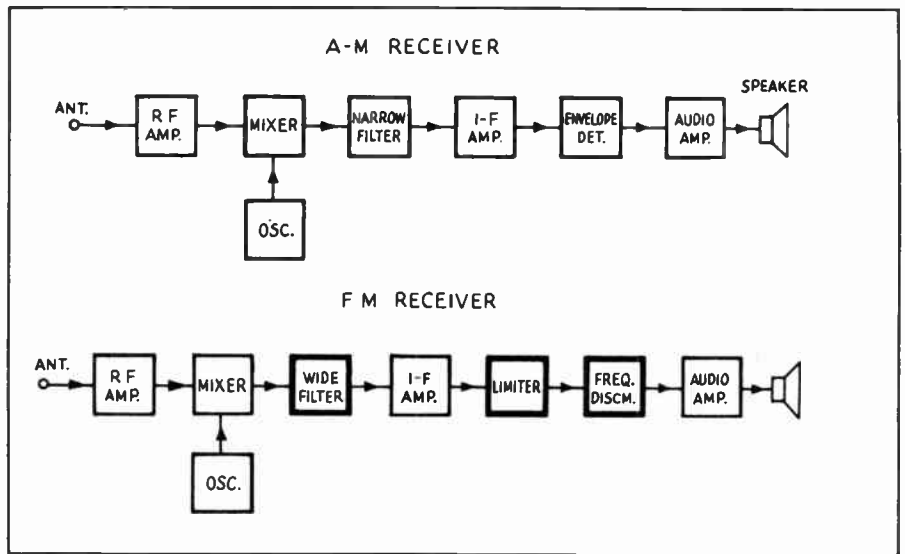


Fig. 10 — Block diagrams of (A) an a-m, (B) an fm receiver. Dark borders outline the sections that are different in the fm set.

FM Filters		Center Frequency	Normal Bandwidth	Ultimate Rejection	Impedance (r)	Insertion Loss	Crystal Discriminator
Manufacturer	Model				In	Out	
KVG (1)	XF-9E	9.0 MHz	12 kHz	90 dB	1200	1200	XD9-02
KVG (1)	XF-107A	10.7 MHz	12 kHz	90 dB	820	820	XD107-01
KVG (1)	XF-107B	10.7 MHz	15 kHz	90 dB	910	910	XD107-01
KVG (1)	XF-107C	10.7 MHz	30 kHz	90 dB	2000	2000	XD107-01
Heath Dynamics (2)		21.5 MHz	15 kHz	90 dB	550	550	-
Heath Dynamics (2)		21.5 MHz	30 kHz	90 dB	1100	1100	-
Clevite (3)	TCF4-12D3CA	445 kHz	12 kHz	60 dB	40k	2200	-
Clevite (3)	TCF4-18G45A	455 kHz	18 kHz	50 dB	40k	2200	-
Clevite (3)	TCF6-30D55A	455 kHz	30 kHz	60 dB	20k	1000	-

Fig. 11 — A list of fm-bandwidth filters that are available to amateurs. Manufacturer's addresses are as follows: (1) Spectrum International, P. O. Box 1084, Concord, MA 01742; (2) Heath Dynamics, Inc., 6050 N. 52nd Ave., Glendale, AZ 85301, tel. 602-934-5234; (3) Semiconductor Specialists, Inc., P. O. Box 66125, O'Hare International Airport, Chicago, IL 60666.

null is heard. If a higher-order null is desired, continue advancing the control further until the second, and then the third, null is heard. Using a carrier null beyond the third is generally not practical.

For example, if a 905.8-Hz tone is used, the transmitter will be set for 5-kHz deviation when the second null is reached. The second null achieved with a 2805-Hz audio input will set the transmitter deviation at 15.48 kHz. The Bessel-function approach can be used to calibrate a deviation meter, such as the unit shown in Fig. 8A.

### Reception of FM Signals

Receivers for fm signals differ from others principally in two features — there is no need for linearity preceding detection (it is, in fact, advantageous if amplitude variations in signal and background noise can be "washed out") and the detector must be capable of converting frequency variations of the incoming signal into amplitude variations.

Frequency-modulated signals can be received after a fashion on any ordinary receiver. The receiver is tuned to put the carrier frequency partway down on one

side of the selectivity curve. When the frequency of the signal varies with modulation it swings as indicated in Fig. 9, resulting in an a-m output varying between X and Y. This is then rectified as an a-m signal.

With receivers having steep-sided selectivity curves, the method is not very satisfactory because the distortion is quite severe unless the frequency deviation is small, since the frequency deviation and output amplitude is linear over only a small part of the selectivity curve.

### The FM Receiver

Block diagrams of an a-m/ssb and an fm receiver are shown in Fig. 10. Fundamentally, to achieve a sensitivity of less than 1  $\mu$ V, an fm receiver requires a gain of several million — too much total gain to be accomplished with stability on a single frequency. Thus, the use of the superheterodyne circuit has become standard practice. Three major differences will be apparent from a comparison of the two block diagrams. The fm receiver employs a wider-bandwidth filter, a different detector, and has a limiter stage added between the i-f amplifier and the detector.

Otherwise the functions, and often the circuits, of the rf, oscillator, mixer and audio stages will be the same in either receiver.

In operation, the noticeable difference between the two receivers is the effect of noise and interference on an incoming

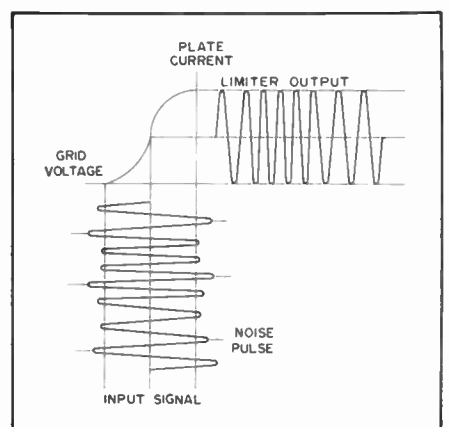


Fig. 12 — Representation of limiter action. Amplitude variations on the signal are removed by the diode action of the grid- and plate current saturation.

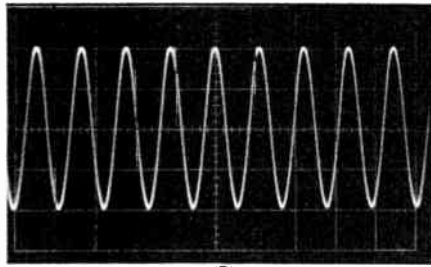
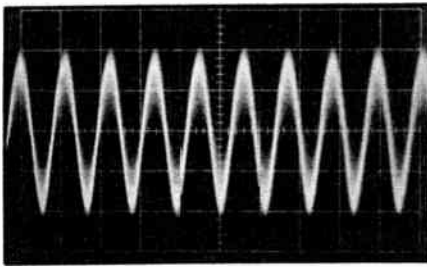


Fig. 13 — (A) Input wave form to a limiter stage shows a-m and noise. (B) The same signal, after passing through two limiter stages, is devoid of a-m components.

signal. From the time of the first spark transmitters, "rotten QRN" has been a major problem for amateurs. The limiter and discriminator stages in an fm set can eliminate a good deal of impulse noise, except noise which manages to acquire a frequency-modulation characteristic. Accurate alignment of the receiver i-f system and phase tuning of the detector are required to achieve good noise suppression. Fm receivers perform in an unusual manner when QRM is present,

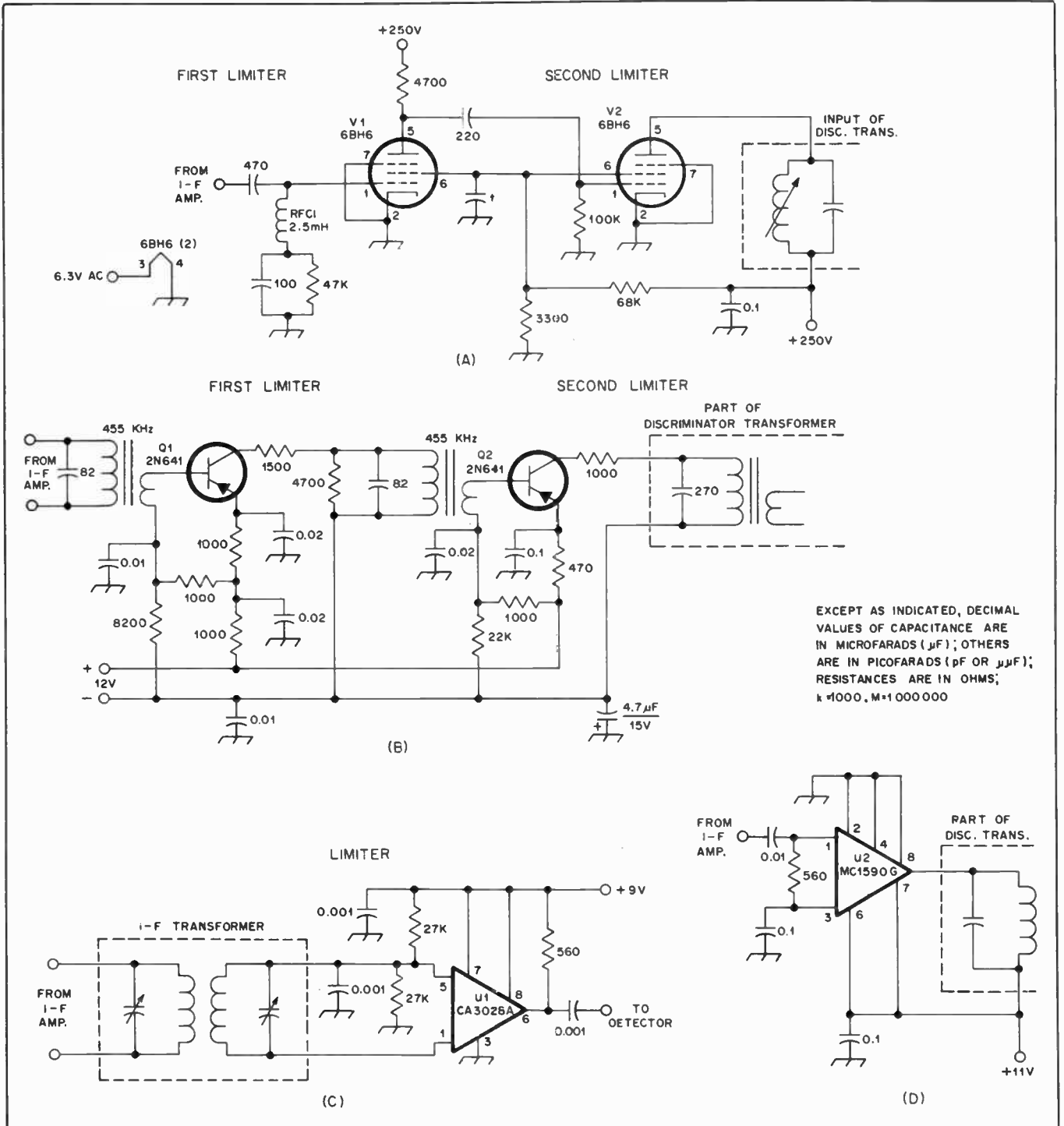


Fig. 14 — Typical limiter circuits using (A) tubes, (B) transistors, (C) a differential IC, (D) a high-gain linear IC.



exhibiting a characteristic known as the *capture effect*. The loudest signal received, even if it is only two or three times stronger than other stations on the same frequency, will be the only transmission demodulated. By comparison, an S9 a-m or cw signal can suffer noticeable interference from an S2 carrier.

### Bandwidth

Most fm sets that use tubes achieve i-f selectivity by using a number of over-coupled transformers. The wide bandwidth and phase-response characteristic needed in the i-f system dictate careful design and alignment of all interstage transformers.

For the average ham, the use of a high-selectivity filter in a homemade receiver offers some simplification of the alignment task. Following the techniques used in ssb receiver, a crystal or ceramic filter should be placed in the circuit as close as possible to the antenna connector — at the output of the first mixer, in most cases. Fig. 11 lists a number of suitable filters that are available to amateurs. Prices for these filters are in the \$50 range. Experimenters who wish to “roll their own” can use surplus hf crystals, as outlined in ARRL’s *Single Sideband for the Radio Amateur*, or ceramic resonators.

One item of concern to every amateur fm user is the choice of i-f bandwidth for his receiver. Deviation of 5 kHz is now standard on the amateur bands. A wide-band receiver can receive narrow-band signals, suffering only some loss of audio in the detection process. Naturally, it also will be subject to adjacent-channel interference, especially in congested areas.

### Limiters

When fm was first introduced, the main selling point used for the new mode was the noise-free reception possibilities. The circuit in the fm receiver that has the task of chopping off noise and amplitude modulation from an incoming signal is the *limiter*. Most types of fm detectors respond to both frequency and amplitude

variations of the signal. Thus, the limiter stages preceding the detector are included to “cleanse” the signal so that only the desired frequency modulation will be demodulated. This action can be seen in Fig. 13.

Limiter stages can be designed using tubes, transistors, or ICs. For a tube to act as a limiter, the applied B voltages are chosen so that the stage will overload easily, even with a small amount of signal input. A sharp-cutoff pentode such as the 6BH6 is usually employed with little or no bias applied. As shown in Fig. 12, the input signal limits when it is of sufficient amplitude so that diode action of the grid and plate-current saturation clip both sides of the input signal, producing a constant-amplitude output voltage.

Obviously, a signal of considerable strength is required at the input of the limiter to assure full clipping, typically several volts for tubes, 1 volt for transistors, and several hundred microvolts for ICs. Limiting action should start with an rf input of 0.2  $\mu$ V or less, so a large amount of gain is required between the antenna terminal and the limiter stages. For example, the Motorola 80D has eight tubes before the limiter, and the solid-state receivers use nine transistor stages to get sufficient gain before the first limiter. The new ICs offer some simplification of the i-f system, as they pack a lot of gain into a single package.

When sufficient signal arrives at the receiver to start limiting action, the set *quiets* — that is, the background noise disappears. The sensitivity of an fm receiver is rated in terms of the amount of input signal required to produce a given amount of quieting, usually 20 dB. Use of solid-state devices allow receivers to achieve 20 dB quieting with 0.15 to 0.5  $\mu$ V of input signal.

A single tube or transistor stage will not provide good limiting over a wide range of input signals. Two stages, with different input time constants, are a minimum requirement. The first stage is set to handle impulse noise satisfactorily while

the second is designed to limit the range of signals passed on by the first. At frequencies below 1 MHz it is useful to employ untuned RC-coupled limiters which provide sufficient gain without a tendency toward oscillation.

Fig. 14A shows a two-stage limiter using sharp-cutoff tubes, while 14B has transistors in two stages biased for limiter service. The base bias on either transistor may be varied to provide limiting at a desired level. The input-signal voltage required to start limiting action is called the *limiting knee*, referring to the point at which collector (or plate) current ceases to rise with increased input signal. Modern ICs have limiting knees of 100 mV for the circuit shown in Fig. 14C, using the RCA CA3028A or Motorola MC1550G, or 200 mV for the MC1590G of Fig. 14D. Because the high-gain ICs such as the CA3076 and MC1590G contain as many as six or eight active stages which will saturate with sufficient input, one of these devices provides superior limiter performance compared to a pair of tubes or transistors.

### Detectors

The first type of fm detector to gain popularity was the frequency discriminator. The characteristic of such a detector is shown in Fig. 15. When the fm signal has no modulation, and the carrier is at point 0, the detector has no output. When audio input to the fm transmitter swings the signal higher in frequency, the rectified output increases in the positive direction. When the frequency swings lower the output amplitude increases in the negative direction. Over a range where the discriminator is linear (shown as the straight portion of the line), the conversion of fm to a-m that is taking place will be linear.

A practical discriminator circuit is shown in Fig. 16. The fm signal is converted to a-m by transformer T1. The voltage induced in the T1 secondary is 90 degrees out of phase with the current in the primary. The primary signal is

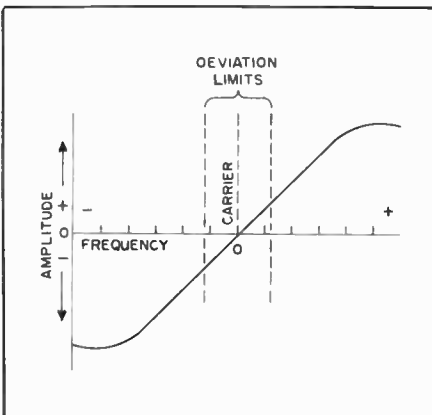


Fig. 15 — The characteristic of an fm discriminator.

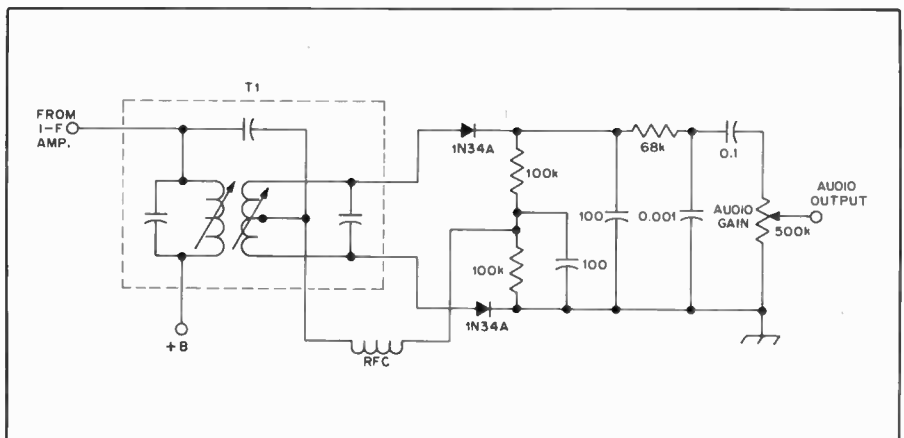


Fig. 16 — Typical frequency-discriminator circuit used for fm detection. T1 is a Miller 12-C45.

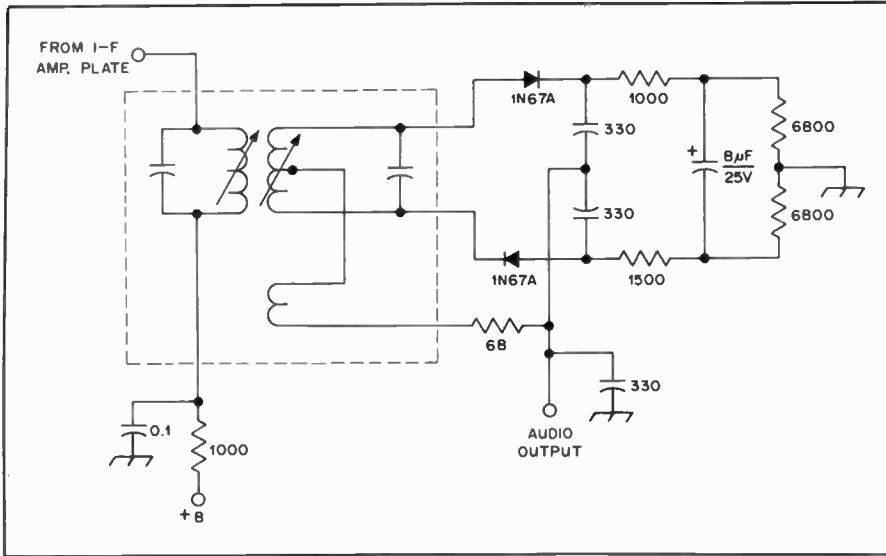


Fig. 17 — A ratio detector of the type often used in entertainment radio and TV sets. T1 is a ratio-detector transformer such as the Miller 1606.

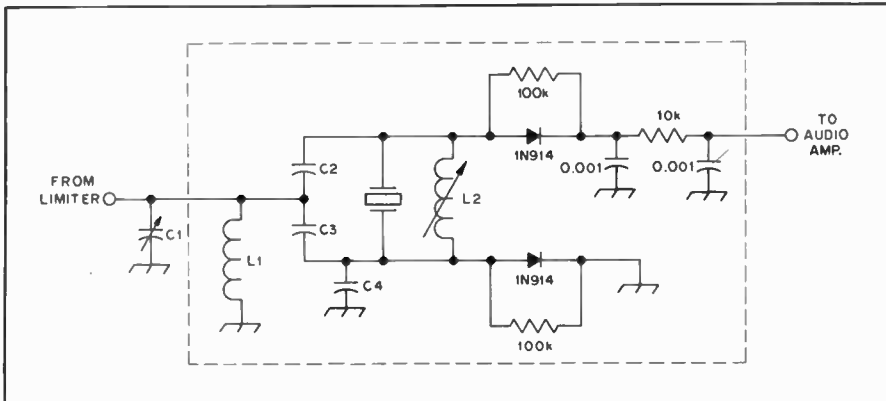


Fig. 18 — Crystal discriminator, C1 and L1 are resonant at the intermediate frequency. C2 is equal in value to C3. C4 corrects any circuit imbalance so that equal amounts of signal are fed to the detector diodes.

introduced through a center tap on the secondary, coupled through a capacitor. The secondary voltages combine on each side of the center tap so that the voltage on one side leads the primary signal while the other side lags by the same amount. When rectified, these two voltages are equal and of opposite polarity, resulting in zero-voltage output. A shift in input frequency causes a shift in the phase of the voltage components that results in an increase of output amplitude on one side of the secondary, and a corresponding decrease on the other side. The differences in the two changing voltages, after rectification, constitute the audio output.

In the search for a simplified fm detector, RCA developed a circuit that has now become standard in entertainment radios which eliminated the need for a preceding limiter stage. Known as the *ratio detector*, this circuit is based on the idea of dividing a dc voltage into a ratio which is equal to the ratio of the amplitudes from either side of a dis-

criminator-transformer secondary. With a detector that responds only to ratios, the input signal may vary in strength over a wide range without causing a change in the level of output voltage — fm can be detected, but not a-m. In an actual ratio detector, Fig. 17, the dc voltage required is developed across two load resistors, shunted by an electrolytic capacitor. Other differences include the two diodes, which are wired in series aiding rather than series opposing, as in the standard discriminator circuit. The recovered audio is taken from a tertiary winding which is tightly coupled to the primary of the transformer. Diode-load resistor values are selected to be lower (5000 ohms or less) than for the discriminator.

The sensitivity of the ratio detector is one-half that of the discriminator. In general, however, the transformer design values for Q, primary-secondary coupling, and load will vary greatly, so the actual performance differences between these two types of fm detectors are usually not

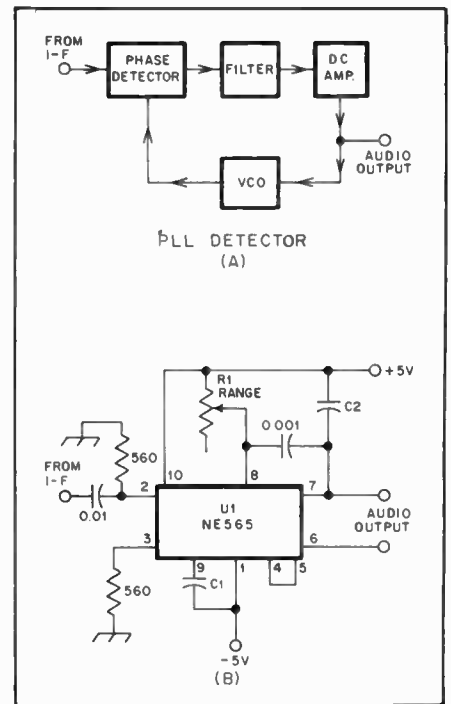


Fig. 19 — (A) Block diagram of a PLL demodulator. (B) Complete PLL circuit.

significant. Either circuit can provide excellent results. In operation, the ratio detector will not provide sufficient limiting for communications service, so this detector also is usually preceded by at least a single limiting stage.

#### Other Detector Designs

The difficulties often encountered in building and aligning LC discriminators have inspired research that has resulted in a number of adjustment-free fm detector designs. The *crystal discriminator* utilizes a quartz resonator, shunted by an inductor, in place of the tuned-circuit secondary used in a discriminator transformer. A typical circuit is shown in Fig. 18. Some commercially made crystal discriminators have the input-circuit inductor, L1, built in (C1 must be added) while in other types both L1 and C2 must be supplied by the builder. Fig. 18 shows typical component values; unmarked parts are chosen to give the desired bandwidth. Sources for crystal discriminators are listed in Fig. 11.

#### The PLL

Since the *phase-locked loop* (PLL) was reduced to a single IC package, this circuit is revolutionizing some facets of receiver design. Introduction by Signetics of a PLL in a single flat-pack IC, followed by Motorola and Fairchild (who are making the PLL in separate building-block ICs), allows a builder to get to work with a minimum of bother.

A basic phase-locked loop consists of a phase detector, a filter, a dc amplifier, and a voltage-controlled oscillator (VCO). The VCO runs at a



Fig. 20 — The solid-state fm adapter is constructed on a 6 × 2-inch (152 × 51-mm) etched-circuit board, mounted on a homemade chassis.

frequency close to that of an incoming signal. The phase detector produces an error voltage if any frequency difference exists between the VCO and the i-f signal. This error voltage is applied to the VCO. Any changes in the frequency of the incoming signal are sensed at the detector and the error voltage readjusts the VCO frequency so that it remains locked to the intermediate frequency. The bandwidth of the system is determined by a filter on the error-voltage line.

Because the error voltage is a copy of the audio variations originally used to shift the frequency of the transmitter, the PLL functions directly as an fm detector. The sensitivity achieved with the Signetics NE565 PLL is good — about 1 mV for a typical circuit. No transformers or tuned circuits are required. The PLL bandwidth is usually two to ten percent of the i-f for fm detection. Components R1/C1 set the VCO to near the desired frequency. C2 is the loop-filter capacitor which determines the capture range — that range of frequencies over which the loop will acquire lock with an input signal, initially starting out of lock. The NE565 has an upper frequency limit of 500 kHz; for higher frequencies, the NE561, which is usable up to 30 MHz, can be employed.

#### A Solid-State Adapter

Since tubes are seldom used in current designs, a solid-state version of the 455-kHz adapter was constructed. Using an IC limiter/amplifier and miniature i-f transformers, the unit requires only 25

mA at 12 V for power. See Fig. 21A. The Motorola MC1590G provides 70 dB gain and hard limiting action superior to that obtained with the tube version.

The unit is built on a 2 × 6-1/2-inch (51 × 165 mm) circuit board; a template is given in Fig. 21B. Because of the high gain of the IC stage, a shield is required across pins 4 and 6 to isolate the input from the output. Alignment and installation are the same as for the tube version. The bandwidth of the miniature transformers restricts this adapter to narrow-band reception. However, builders wishing a wideband version can use the J. W. Miller 8811 miniature coils, which are combined with a 12-pF coupling capacitor to form a wide-band transformer.

#### Repeaters

A repeater is a device which retransmits received signals in order to provide improved communications range and coverage. This communications enhancement is possible because the repeater can be located at an elevated site which has coverage that is superior to that

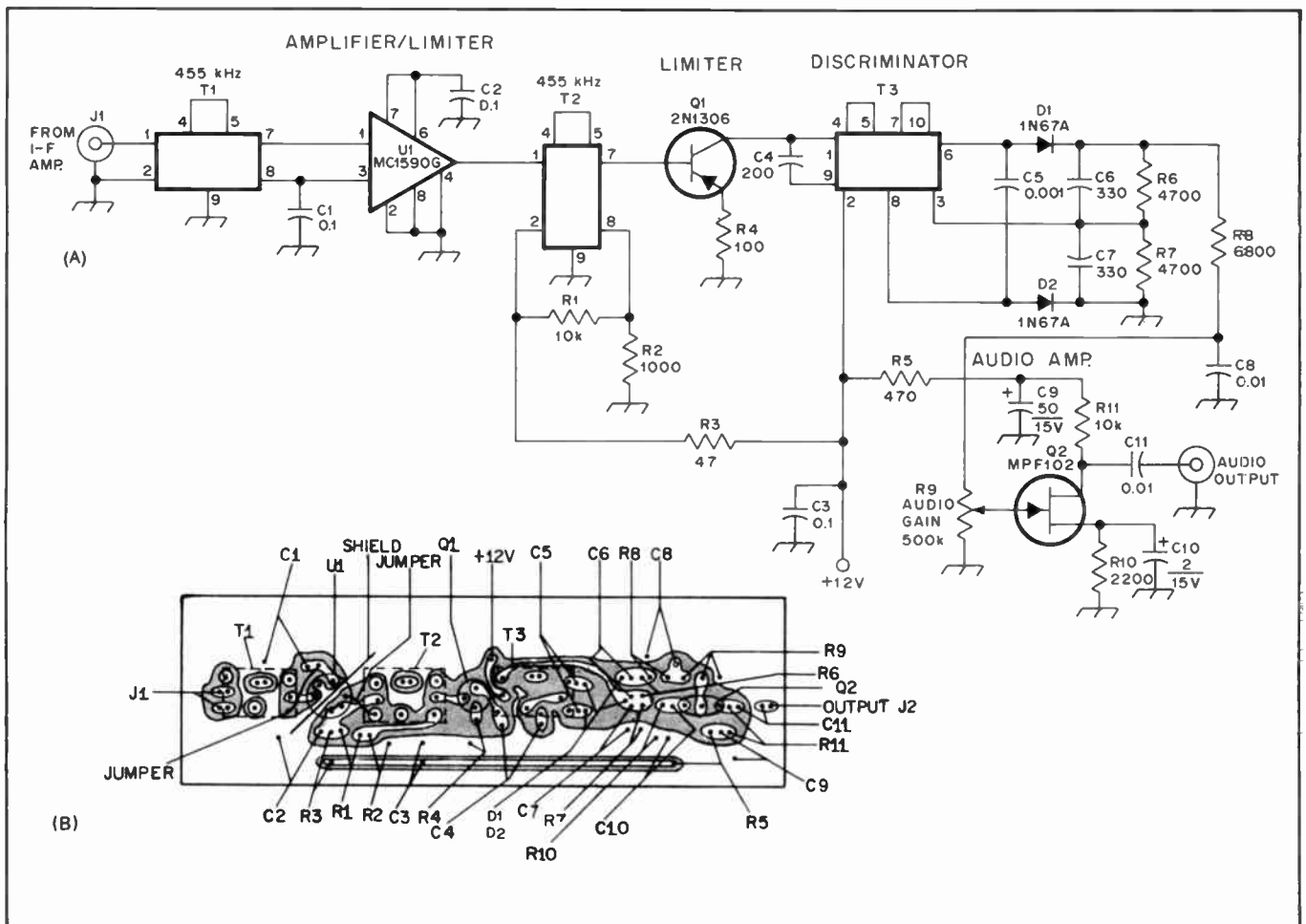


Fig. 21 — (A) Diagram of the 455-kHz narrow-band adapter. Resistors are 1/4- or 1/2-watt composition and capacitors are disk ceramic, except those with polarity marked, which are electrolytic. Components with reference numbers that are not listed below are noted for circuit-board location. (B) Template for the solid-state adapter (not to scale). 8807.

- J1, J2 — Phono receptacle, panel mount.
- R1 — Miniature 1/2-watt composition control.
- T1 — Miniature 455-kHz i-f transformer, Miller
- T2 — Miniature discriminator transformer, 455 kHz, Miller 8806.
- U1 — Motorola MC1590G.



obtained by most stations. A major improvement is usually found when a repeater is used between vhf mobile stations, which normally are severely limited by their low antenna heights and resulting short communications range. This is especially true where rough terrain exists.

The simplest repeater consists of a receiver with its audio output directly connected to the audio input of an associated transmitter tuned to a second frequency. But, certain additional features are required to produce a workable repeater. These are shown in Fig. 23A. The "COR" or carrier-operated relay is a device connected to the receiver squelch circuit which provides a relay contact closure to key the transmitter when an input signal of adequate strength is present. As all amateur transmissions require a licensed operator to control the emissions, a "control" switch is provided in the keying path so that the operator can exercise his duties. This repeater, as shown, is suitable for installation where an operator is present, such as the home of a local amateur with a superior location, and would require no special licensing under existing rules.

In the case of a repeater located where no licensed operator is available, provisions must be made to control the equipment over a telephone line or a radio circuit on 220 MHz or higher. Fig. 23B shows the simplest system of this type. The control decoder may be variously designed to respond to simple audio tones, dial pulsed tones, or even "Touch-Tone" signals. If a leased telephone line with dc continuity is used, control voltages may be sent directly, requiring no decoder. A three-minute timer to disable the repeater transmitter is provided for fail-safe operation. This timer resets during pauses between transmissions and does not interfere with normal communications. The system just outlined is suitable where all operation is to be through the repeater and where the frequencies to be used have no other activity.

### Remote Base Stations

The remote base, like the repeater, utilizes a superior location for transmission and reception, but is basically a simplex device. That is, it transmits and receives on a single frequency in order to communicate with other stations also operating on that frequency. The operator of the remote base listens to his hilltop receiver and keys his hilltop transmitter over his 220-MHz or higher control channels (or telephone line). Fig. 24A shows such a system. Control and keying features have been omitted for clarity. In some areas of high activity, repeaters have all but disappeared in favor of remote bases because of the interference to simplex activity caused by repeaters

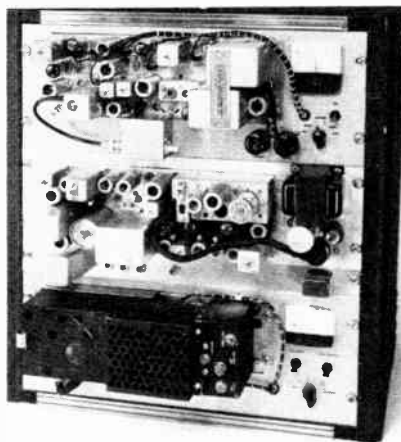


Fig. 22 — This typical 144-MHz amateur repeater uses GE Progress-Line transmitter and receiver decks. Power supplies and metering circuits have been added. The receiver located on the middle deck is a 440-MHz control receiver, also a surplus GE unit. A preamplifier, similar to that shown in Fig. 30, has been added to the 2-meter receiver to improve the sensitivity so that a 0.2- $\mu$ V input signal will produce 20 dB of quieting.

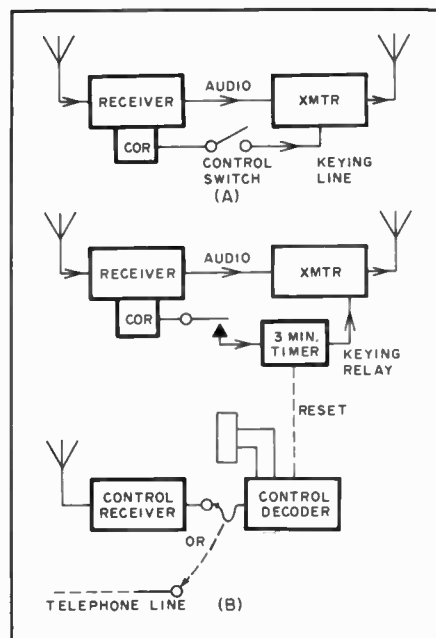


Fig. 23 — Simple repeaters. The system at A is for local control; remote control is shown at B.

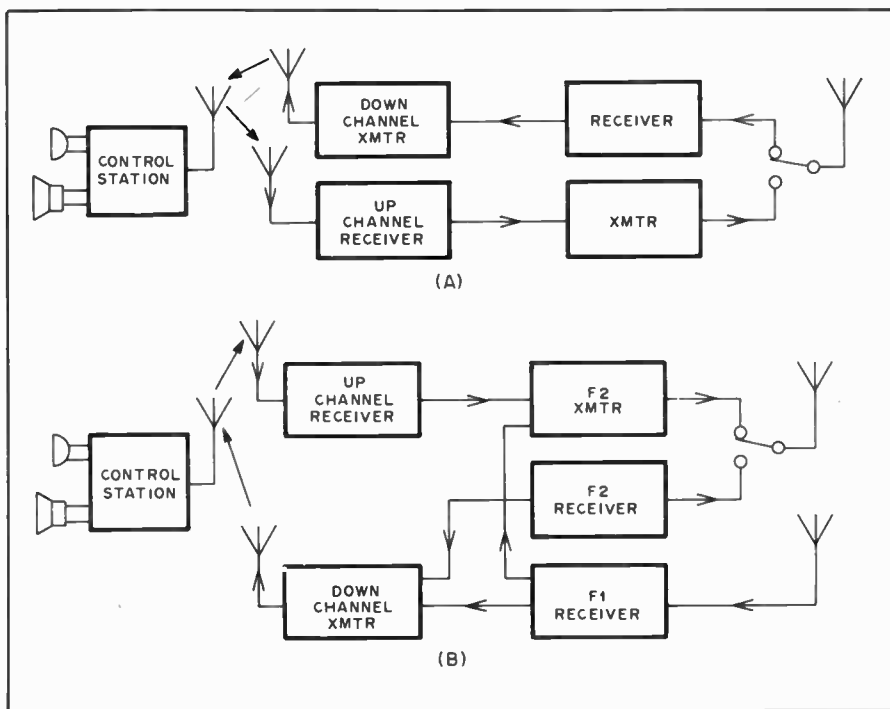


Fig. 24 — A remote base is shown at A. A repeater with remote-base operating capability is shown at B. Control and keying circuits are not shown. Telephone-line control may be substituted for the radio-control channels shown.

unable to monitor their output frequency from the transmitter location.

### A Complete System

Fig. 24B shows a repeater that combines the best features of the simple repeater and the remote base. Again, necessary control and keying features have not been shown in order to simplify the drawing, and make it easier to follow. This repeater is compatible with simplex

operation on the output frequency because the operator in control monitors the output frequency from a receiver at the repeater site between transmissions. The control operator may also operate the system as a remote base. This type of system is almost mandatory for operation on one of the national calling frequencies, such as 146.52 MHz, because it minimizes interference to simplex operation and permits simplex communications through



**Table 1**  
EIA Standard Subaudible Tone Frequencies

Reed	Freq. (Hz)	Reed	Freq. (Hz)
L1	67.0	2A	114.8
WZ	69.3	2B	118.8
L2	71.9	3	123.0
WA	74.4	3B	131.8
L3	77.0	4	136.5
WB	79.7	4A	141.3
L4	82.5	4B	146.2
YA	85.4	5	151.4
L4A	88.5	5A	156.7
ZZ	91.5	5B	162.2
L5	94.8	6	167.9
1	100.0	6A	173.8
1A	103.5	6B	179.9
1B	107.2	7	186.2
2	110.9	7A	192.8

the system with passing mobiles who may not have facilities for the repeater-input frequency.

The audio interface between the repeater receivers and transmitters can, with some equipment, consist of a direct connection bridging the transmitter microphone inputs across the receiver speaker outputs. This is not recommended, however, because of the degradation of the audio quality in the receiver-output stages. A cathode follower connected to each receiver's first squelch-controlled audio amplifier stage provides the best results. A repeater should maintain a flat response across its audio passband to maintain the repeater intelligibility at the

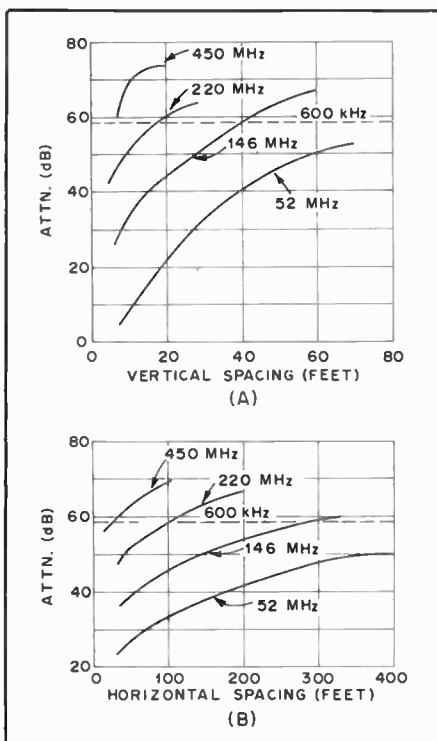


Fig. 25 — Charts to calculate the amount of isolation achieved by (A) vertical and (B) horizontal spacing of repeater antennas. If 600-kHz separation between the transmitted and received frequencies is used, approximately 58-dB attenuation (indicated by the dotted line) will be needed. (Feet  $\times$  0.3048 = meters.)

same level as direct transmissions. There should be no noticeable difference between repeated and direct transmissions. The intelligibility of some repeaters suffers because of improper level settings which cause excessive clipping distortion. The clipper in the repeater transmitter should be set for the maximum system deviation, 5 kHz, usually. Then the receiver level driving the transmitter should be set by applying an input signal of known deviation below the maximum, and adjusting the receiver audio gain to produce the same deviation at the repeater output. Signals will then be repeated linearly up to the maximum desired deviation. The only incoming signal that should be clipped in a properly adjusted repeater is an overdeviated signal.

The choice of repeater input and output frequencies must be carefully made. In general, check with the appropriate volunteer frequency coordinator, who is listed in the *ARRL Repeater Directory*, since about 4000 repeaters are operating across the U.S. and Canada. Some 10-meter repeaters are operational, and most use 100-kHz separation. A popular arrangement on 6 meters uses 52.525 MHz as either the input or output, with several choices for the other half. Many stations, however, are moving toward either a 600-kHz or 1-MHz offset. On 2 meters the standard is 600 kHz. The 220-MHz band uses 1.6-MHz separation. On the 450-MHz band it is 5 MHz. The choice and usage is a matter for local agreement.

In some cases where there is overlapping geographical coverage of repeaters using the same frequencies, special methods for selecting the desired repeater have been employed. One technique requires the user to transmit automatically a 0.5-second burst of a specific audio tone

at the start of each transmission. Different tones are used to select different repeaters. Standard tone frequencies are 1800, 1950, 2100, 2250 and 2400 Hz.

Because of growing congestion among same- and adjacent-channel repeaters, an increasingly popular access method is a continuous subaudible tone. Popularly known as PL (Motorola trademark for Private Line), it must be applied to a transmitter after the clipper/filter stage has shaped the voice audio. Table 1 lists the EIA-standard frequencies.

### Practical Repeater Circuits

Because of their proven reliability, commercially made transmitter and receiver decks are generally used in repeater installations. Units designed for repeater or duplex service are preferred because they have the extra shielding and filtering necessary to hold mutual interference to a minimum when both the receiver and transmitter are operated simultaneously.

Wide-band noise produced by the transmitter is a major factor in the design of any repeater. The use of high-Q tuned circuits between each stage of the transmitter, plus shielding and filtering throughout the repeater installation, will hold the wideband noise to approximately 80 dB below the output carrier. However, this is not sufficient to prevent *desensitization* — the reduction in sensitivity of the receiver caused by noise or rf overload from the nearby transmitter — if the antennas for the two units are placed physically close together.

Desensitization can easily be checked by monitoring the limiter current of the receiver with the transmitter switched off, then on. If the limiter current increases when the transmitter is turned on, then the problem is present. Only physical isolation of the antennas or the use of

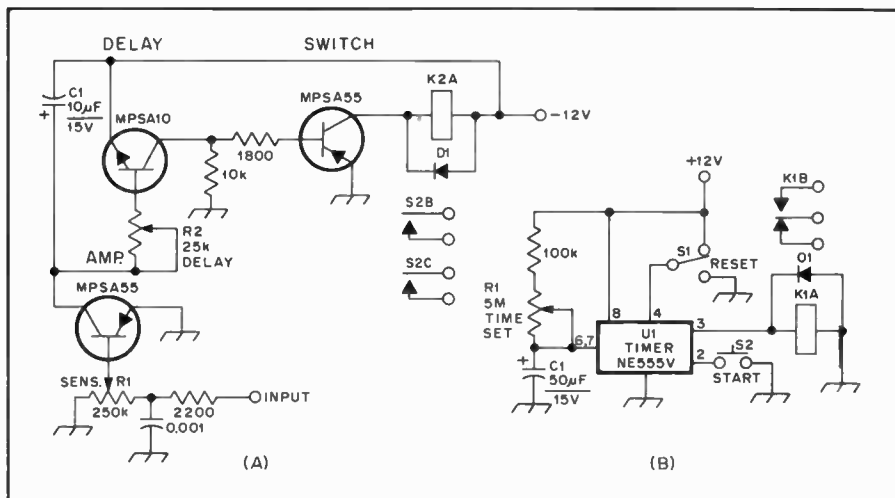


Fig. 26 — (A) COR circuit for repeater use. R2 sets the length of time that K1 will stay closed after the input voltage disappears. K1 may be any relay with a 12-volt coil, although the long-life reed type is preferred. D1 is a silicon diode. (B) Timer circuit using a Signetics NE555. R1, C1 set the timer range. C1 should be a low-leakage type capacitor. S1, S2 could have their contacts paralleled by the receiver COR for automatic START and RESET controlled by an incoming signal.

high-Q tuned cavities in the transmitter and receiver antenna feedline will improve the situation.

### Antenna Considerations

The ultimate answer to the problem of receiver desensing is to locate the repeater transmitter a mile or more away from the receiver. The two can be interconnected by telephone line or uhf link. Another effective approach is to use a single antenna with a *duplexer*, a device that provides up to 120 dB of isolation between the transmitter and receiver. High-Q cavities in the duplexer prevent transmitted signal energy and wideband noise from degrading the sensitivity of the receiver, even though the transmitter and receiver are operating on a single antenna simultaneously. A commercially made duplexer is very expensive, and constructing a unit requires extensive metal-working equipment and test facilities.

If two antennas are used at a single site, there will be a minimum spacing of the two antennas required to prevent desensing. Fig. 25 indicates the spacing necessary for repeaters operating in the 50-, 144-, 220- and 420-MHz bands. An examination of Fig. 25 will show that vertical spacing is far more effective than is horizontal separation for vertically polarized antennas. The chart assumes unity-gain antennas will be used. If some type of gain antenna is employed the pattern of the antennas will be a modifying factor. A rugged repeater antenna was described in January 1970 *QST*.

### Control

Two connections are needed between the repeater receiver and transmitter, audio and transmitter control. The audio should be fed through an impedance-matching network to ensure that the receiver output circuit has a constant load while the transmitter receives the proper input impedance. Filters limiting the audio response to the 300- to 3000-Hz band are desirable, and with some gear an audio-compensation network may be required. A typical COR (carrier-operated relay) circuit is shown in Fig. 26A. This unit may be operated by the grid current

of a tube limiter or the dc output of the noise detector in a solid-state receiver.

Normally, a repeater is given a "tail"; a timer holds the repeater transmitter on for a few seconds after the input signal disappears. This delay prevents the repeater from being keyed on and off by a rapidly fading signal. Other timers keep each transmission to less than three minutes duration (an FCC requirement), turn on identification, and control logging

functions. A simple timer circuit is shown in Fig. 26B.

### A Scanning Touch-Tone Digit and Word Decoder

The Touch-Tone encoding system, used extensively in autopatch operations on fm repeaters across the country, offers a ready-made source for dual-tone codes, and advances in microcircuitry design have produced a single device that can be

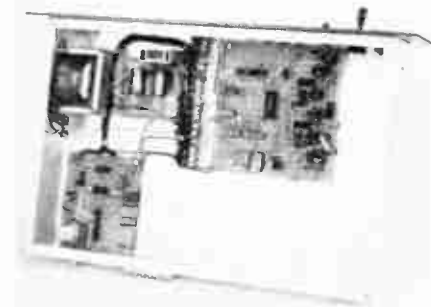


Fig. 27 — Shown here is the decoder built by W1GNP as described in January 1976 *QST*.

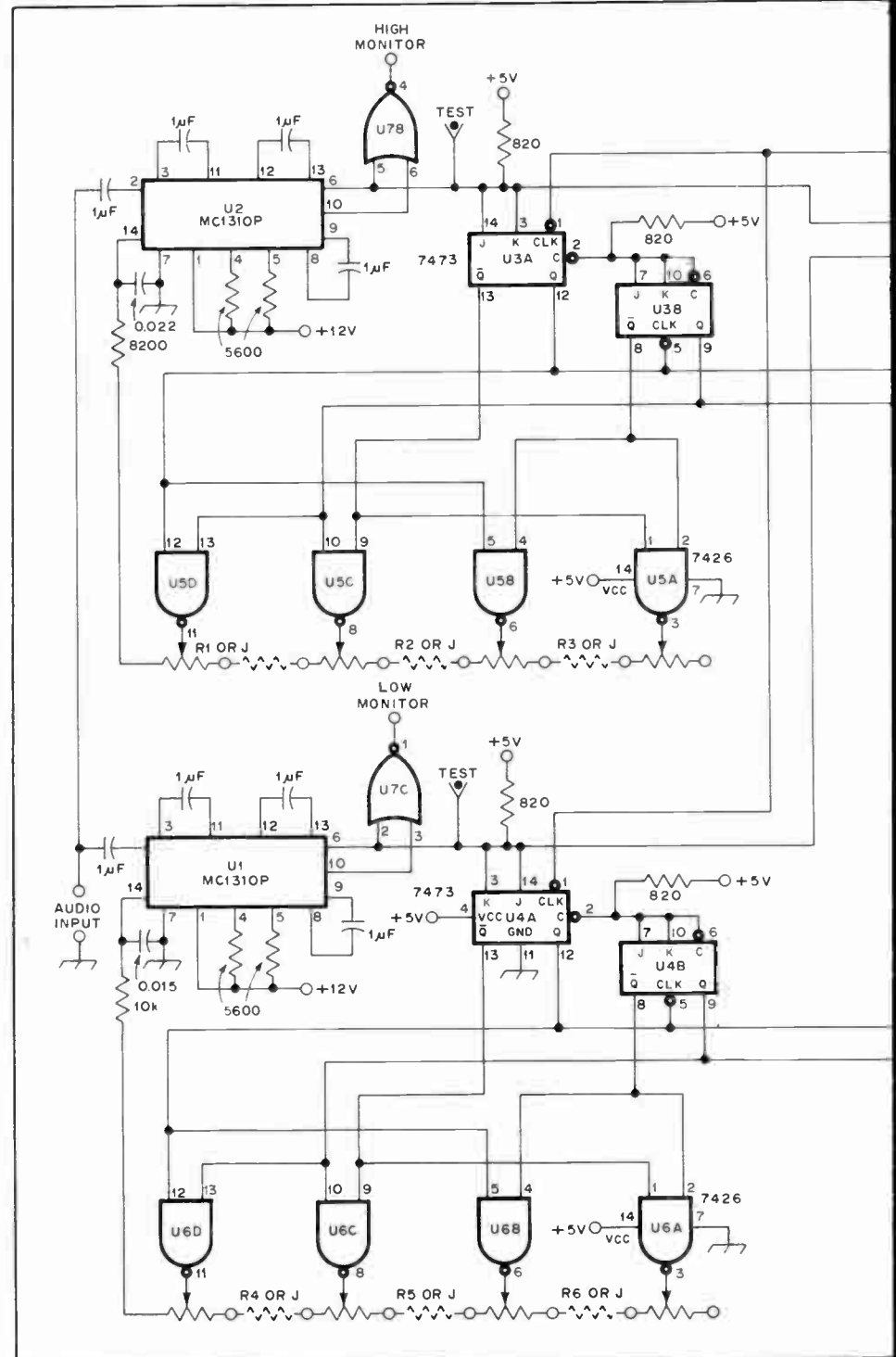



Fig. 28 — Schematic diagram of the tone and digit decoder. Parts placement is not critical, but standard construction practice should be followed when fabricating these circuits.

used to decode these dual-tone codes for a variety of remotely controlled functions. However, one device is required to decode each tone. This section describes how a scanning decoder evolved as an attempt to avoid using seven of these decoder ICs, and how a simple counter circuit can recognize specific four-digit word sequences to provide a unique approach to a remote-control decoder.

There are 16 tone pairs possible —

selecting one from the low group, 697, 770, 852 and 941 Hz, and one from the high group, 1209, 1336, 1477 and 1633 Hz. Two phase-locked-loop types of tone decoders should therefore be sufficient if each one sequentially scans the four tones of one group. In this way two decoders with some added scanning circuits take the place of eight. Parts of the scanning circuit such as the clock oscillator and digit decoder would be required in any

case for word decoding, and the parts' cost of the present system using primarily low cost TTL logic is reasonable. One disadvantage of the scanning decoder is the slow response time resulting from the need to wait for each decoder to find the received tone. Also, a delay is built in which requires both decoders to halt for at least one full clock period before a digit is registered. The operation is thus relatively immune to spurious responses from voice

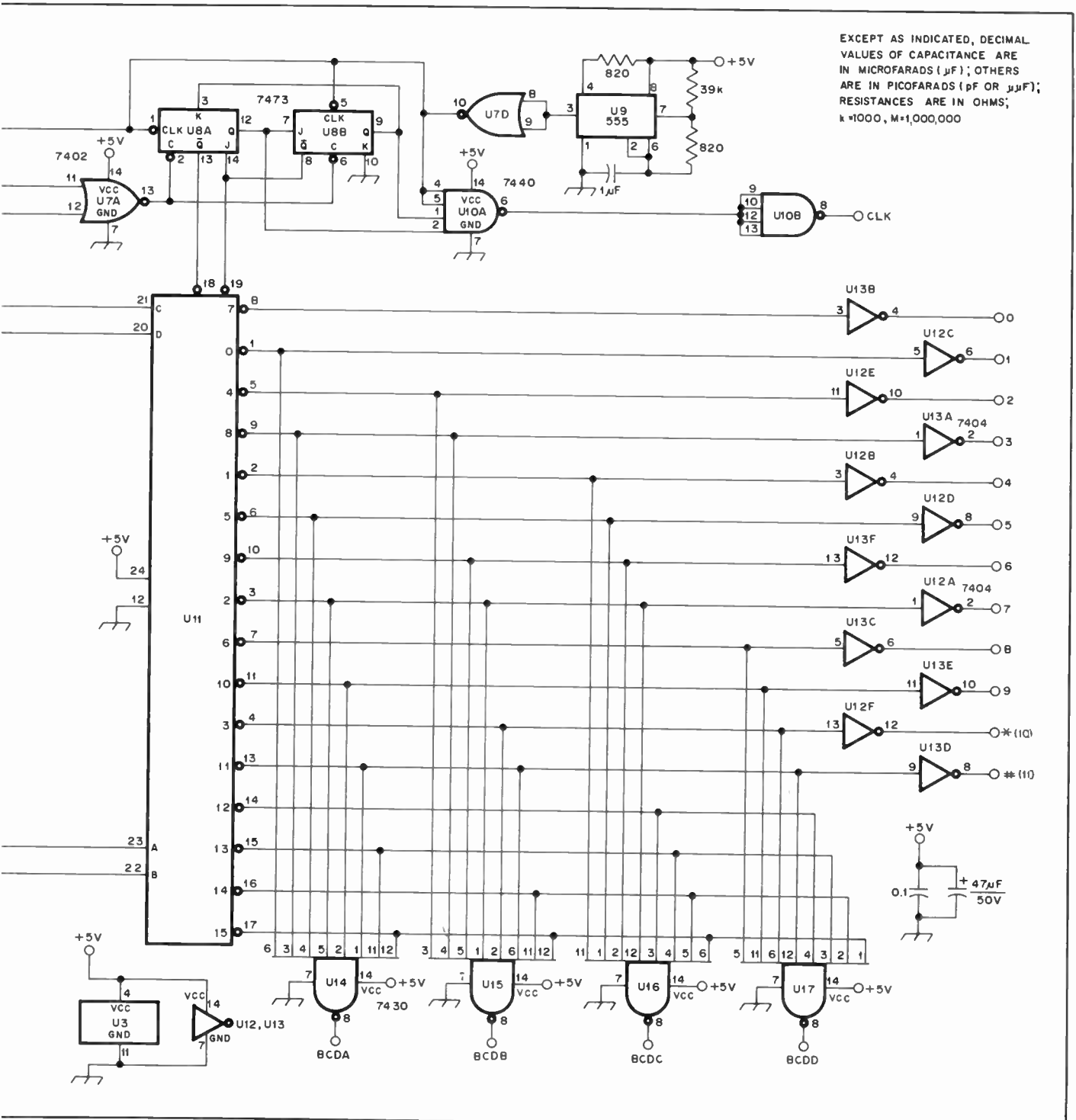





and become stopped in state 2 (U8A off, U8B on) until reset when one or the other tone detector drops out. Its purpose is to provide a two-clock-period double check on the decoder operation and yield a single clock pulse (CLK) just before the end of state 3 if the tone signal is so validated. Also, during state 3 (U8A and U8B on) the decoder U11 is enabled, and one of the digit outputs from U12 or U13 comes on.

The decoder makes use of the counter states of U3 and U4 when they are stopped by an incoming two-tone signal. Since the tones are scanned from low to high and the low group (top to bottom rows on a standard pad) is wired to the two least-significant-digit inputs on U11, the output states of U11 would correspond to the tone button assignments of a standard Touch-Tone pad. In order that the digit outputs are correct for the actual assignment on the tone pad, the U11 outputs are reordered and the 12 corresponding to the commonly used 12-button pad are inverted to the positive logic form by U12 and U13. The four gates U14, U15, U16 and U17 are optional and are used to obtain the binary equivalent of the standard digit assignment of the Touch-Tone pad.

### Word Decoding

The word-decoding circuitry shown in Fig. 29 consists of two, three-digit prefix decoders and an output flip-flop U22. Each prefix decoder consists of a dual J-K flip-flop (U18) two AND gates (U20A and B) and two NAND gates (U21A and B). The prefix or first three digits of the four-letter word being decoded are selected by connecting inputs digit 1 (DG1), digit 2 (DG2), digit 3 (DG3) and digit 4 (DG4) to the desired outputs from U12 and U13. Likewise, the other word-decoder inputs DH1, DH2, DH3 and DH4 are connected to four outputs from U12 and U13. The first four-letter word such as the sequence 4639 would turn U22 on, and the second such as 1 \* 8 # would turn it off.

This sequence detection is achieved by the gating used on the J-K inputs of U18 and U19. Each is a two-stage counter which will advance in the state sequence 0 — 1 — 3 — 2 — 0 only if the correct digit input is on in proper sequence. That is, in order to advance from 0 — 1 DG1 must be on, to advance from 1 — 3 DG2 must be on, and to advance from 3 — 2 DG3 must be on. If any are off when they should be on, the state goes directly to zero. When state 2 is reached, U18A is off and U18B is on, and two of the three AND J inputs of U22 are on. At this point the three-digit prefix has been received successfully. If the fourth digit received corresponds to DG4, the clock pulse (CLK) will also turn on U22 since all its J inputs will then be on. Similarly, the second four-digit-word sequence will turn off U22. Further

interfacing between the TTL output of U22 and a controlled system will depend upon its nature. A simple relay driver using two parallel-connected 15-volt open-collector buffer inverters (1/3 of a 7416) and a 12-volt, 150-ohm relay is shown. A small silicon diode connected as shown helps to avoid transient problems.

The on-off function of Fig. 29 can be simplified by using the same prefix decoder for both turn on and turn off; only the fourth digit need be different. One must be sure the word decoder is reset before it will respond properly to a four-digit word. This is just a matter of being sure that any code such as 4639 is not preceded by a 4, a 46, or a 463. If in doubt about what the last digit may have been in the system, an extra random digit other than 4 is generally sufficient. Alternatively, the reset inputs of U18 and U19 can be wired to some completely independent source of a reset such as the carrier-input detector.

A few words about the choice of codes. For most amateur radio applications, the four-digit word provides adequate security. If a great deal of phone patch activity is present on the channel, the characters \* or # should be used in the code, as these do not appear in phone numbers. The four additional characters generated only by a 16 button pad can be used if four additional inverters are added to the group in U12 and U13. When a number of four-digit codes are used to operate a remote system of some sort, it becomes difficult to remember them all, and ease of use becomes an important factor in choosing codes. Often a single digit is better to turn something off because it's quicker and less likely to be forgotten. In any case, all system codes must be mutually compatible.

### Construction

The unit was constructed on double-sided, copper-clad pc board. The tone and digit decoder circuit of Fig. 28 was constructed on a 6 × 6-inch (152 × 152-mm) pc board. All of the components are mounted on the top side of the board and are soldered on both sides of the pc board. The value for R1 through R6 in each tone-selection line should be selected so that the potentiometer will tune the circuit to the proper tone in the middle of its resistance range. The values shown in the circuit diagram of Fig. 28 are typical and can be used as a starting point for selecting the final value. The word decoders are also constructed on pc board with a double-sided layout. The decoder board is 4 × 4 inches (102 × 102 mm) with all of the components installed on the top side. Several of these decoder boards can be stacked and will make the addition of control functions a simple task.

### Alignment

Alignment is a matter of setting the

scanned frequencies to the correct values using a frequency counter connected to a monitor point. The associated test point is grounded, and with no input to the decoder one of the frequencies can be adjusted, depending on which of the four tones in any group happened to be on when it was stopped manually. It is best to stop the highest tone first and adjust the first potentiometer, along with R9 if necessary, to get 941 Hz. Then select the second potentiometer and value of R1 until 852 Hz can be tuned. In a like manner, adjust all eight frequencies to the correct values. After several months of operation the response became sluggish and finally the unit stopped working, but original performance was restored by retuning R1 through R6. Satisfactory operation is obtained with input levels between 0.1 and 1 volt ac.

### Preamplifiers for Increased Sensitivity

Some surplus, homemade and commercial new equipment for the vhf and uhf fm bands need additional receiver gain and noise-figure improvement for weak-signal work. Too much gain can seriously degrade the receiver dynamic range, so care must be exercised when adding a preamplifier ahead of an existing receiver front end. The temptation of some inexperienced amateurs is to use a preamp which has a gain of 25 dB or greater. As a result, strong local signals can overload the receiver and cause severe mixer IMD. The two preamplifiers described here are tailored for useful but not excessive gain amounts. They should enhance the performance of receivers or converters that are marginal in terms of overall gain and noise figure. They should not have a serious effect on the receiver dynamic range.

The 2-meter version shown in Fig. 30 utilizes a single Siliconix U310 JFET in a common-gate circuit. This helps to ensure stability and provide a gain of over 10 dB. The U310 is well known for its low noise up to 450 MHz (about 3 dB at 450 MHz and 1.5 dB at 144 MHz). This transistor also has excellent dynamic-range characteristics (in excess of 100 dB). A less costly substitute is the Siliconix E300, which comes in a plastic case. The performance traits are approximately the same, but stability may be harder to realize because the E300 has no metal case which can be grounded automatically when the gate is grounded.

C1 of Fig. 30 is adjusted for lowest noise figure. The C1 coil tap can be adjusted also if further improvement is needed. C2 and C3 should be high-Q trimmers for best performance. Miniature ceramic trimmers should be suitable for use at C1, C2 and C3. Ideally, Teflon trimmers or small air variables would be used at those circuit points.

If L1 and L2 are at right angles to one another and spaced well apart, it may not

be necessary to use a shield divider across Q1 as shown in Fig. 30. However, a small piece of copper, brass or double-sided pc board should be easy to add to the circuit board.

A strip-line preamplifier for use at 440 MHz is shown in Figs. 31 and 32. The maximum attainable gain is roughly 20 dB with the circuit shown. Noise figure should be better than 5 dB when the taps onto L1 are optimized. Some experimenting will be necessary. The loaded Q of the three resonators can be increased by moving the Q1/Q2 taps closer to the ground ends of each line. The tradeoff is in preamplifier gain. The increased Q may be important when gain requirements

aren't too great (as in a repeater installation), but when rejection of out-of-band commercial signals are vital to good performance. L1, L2 and L3 are silver plated in this model. The double-sided pc-board housing for the amplifier is also silver plated, as are the two internal divider walls which isolate the tuned circuits from one another.

Amplifier stability is excellent when the gate leads of Q1 and Q2 are made as short as possible. Additional insurance against instability is provided by the decoupling circuits in the drain leads of Q1 and Q2. A press-fit aluminum or brass cover (U-shaped) is used to enclose the open side of the preamplifier case. Craftsmen may

elect to make the housing and divider walls from sections of 1/16-inch (1.6-mm) brass, using silver solder to join the mating surfaces. This unit is suitable for use anywhere in the 420- to 450-MHz band.

### A Selective 2-Meter Preamplifier

A preamplifier used ahead of a surplus receiver as part of a repeater must be based on something more than casual design if good performance is to be realized. Special attention must be paid to selectivity, and the noise figure should be low enough to assure the kind of sensitivity desired by most repeater operators — 0.2 V or less for 20 dB of quieting. Transient and rf-burnout protection are the other criteria for successful use at the repeater site.

While some groups have had success with solid-state preamplifiers, others have decried the reliability of transistorized preamps, mainly because of overloading, IMD, and susceptibility to device damage from static discharges and line transients. Certainly tube-type equipment is less subject to catastrophic failure from the foregoing causes, but a properly designed solid-state preamplifier can hold its own when competing against a vacuum-tube equivalent. The unit treated here (designed by WIFB) meets the design specifications of most amateur repeaters. Precautions have been taken to prevent the usual problems inherent in homemade preamps.

### Design

JFETs were chosen for use in the preamp over gate-protected MOSFETs because the former can sustain up to 80 volts pk-pk, gate to source, before being damaged. Protected MOSFETs are rated

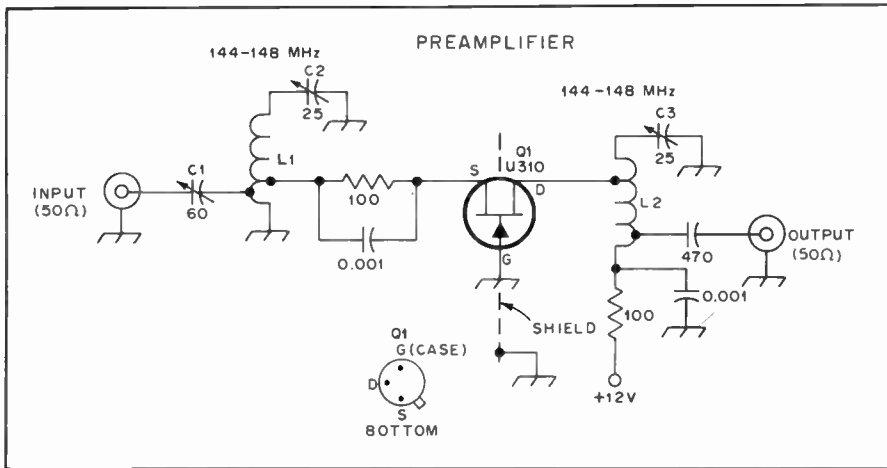


Fig. 30 — Schematic diagram of the low-noise 2-meter preamp. Fixed-value capacitors are disk ceramic. Resistors are 1/4- or 1/2-watt composition. See text for data on the trimmers. L1 has 5 turns of no. 20 wire, 3/4-inch (19-mm) long with an ID of 1/4 inch (6.3 mm). C1 tap approx. 1/2 turn from ground. Q1 tap approx. 1 turn from ground. L2 has same dimensions except for Q1 tap, which is approx. 1 turn from C3 end. See text for Q1 data.

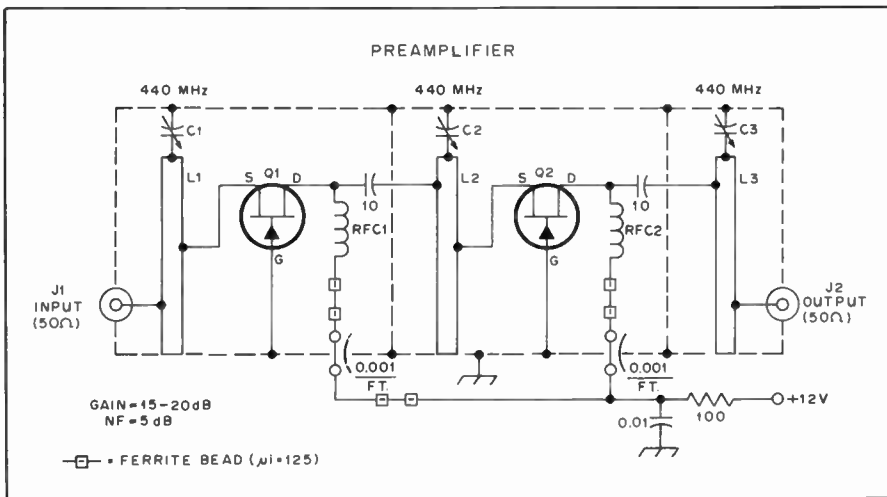


Fig. 31 — Schematic diagram of the 440-MHz preamp. The 10-pF capacitors are silver mica. FT indicates feedthrough capacitor. C1-C3, incl. — 1.4 to 9.2-pF miniature air variable, Johnson 189-0563-001 or equiv. J1, J2 — BNC-type connector soldered to case outer wall. L1-L3, incl. — 2-5/8 × 1/4-inch (67 × 6.3-mm) brass strip. Input and output taps on L1 and L3 are approx. 1/2 inch (13 mm) up from ground (see text). Attach Q1/Q2 drain taps approx. 1/4 inch (6.3 mm) below C2 and C3 ends of line. Q1, Q2 source taps on L1 and L2 are approx. 3/4 inch (19 mm) up from ground. Q1, Q2 — Siliconix JFET. RFC1, RFC2 — 420-MHz choke J. W. Miller 4584 or equiv. Ferrite beads assoc. with these chokes are Amidon miniature type.

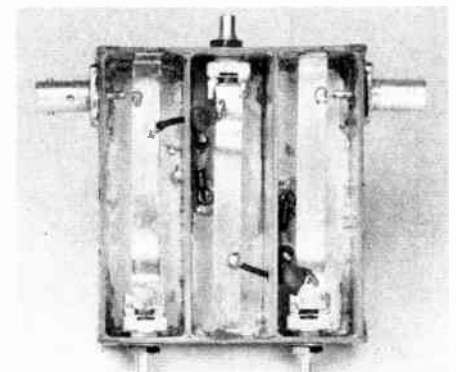


Fig. 32 — Interior view of the 440-MHz preamplifier. The center strip line is reversed from the end ones to prevent excessive lead lengths from Q1 and Q2. The box dimensions are 3 × 3-1/2 × 1 inch (76 × 89 × 25 mm). The internal shields are 3 × 15/16 inches (76 × 24 mm). All mating surfaces of the box walls are soldered inside and outside. Both sides of the dividers are soldered to the inner surface of the box.

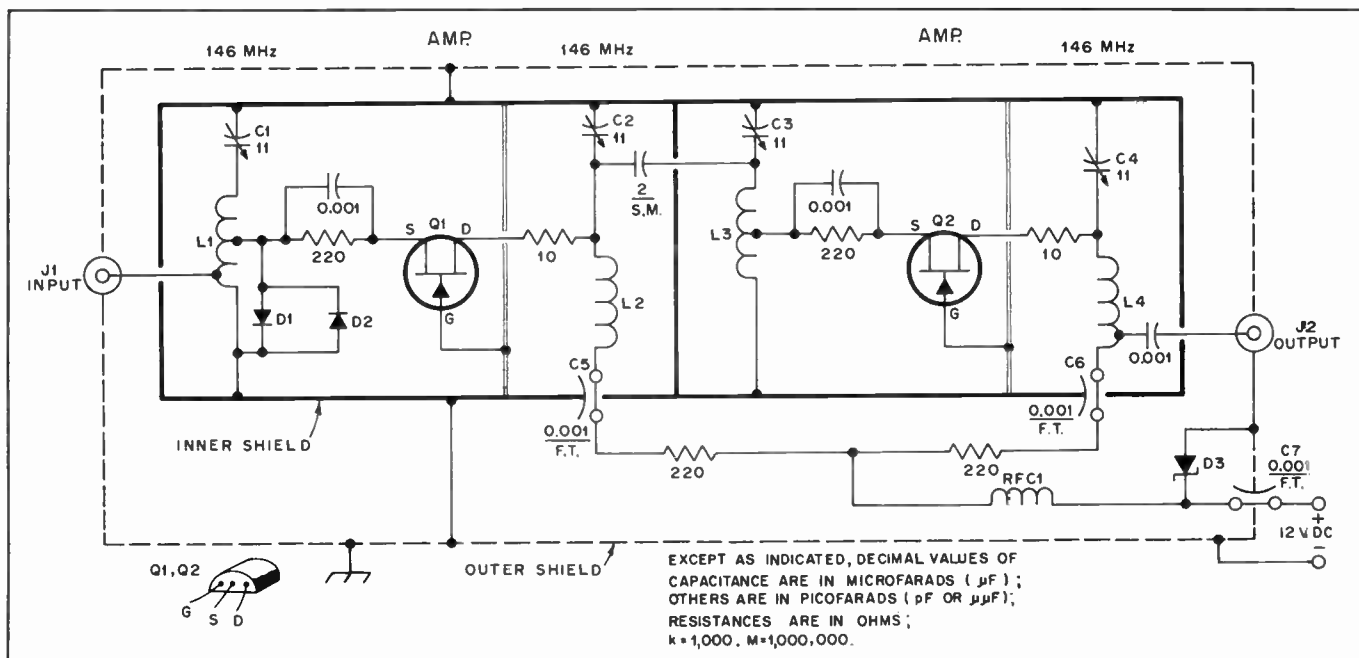


Fig. 33 — Circuit diagram of the preamplifier. Heavy lines indicate the pc-board shield box and dividers. The outer shield box is shown in dashed lines. Fixed-value capacitors are disk ceramic unless otherwise noted. S.M. indicates silver mica. Resistors are 1/2 watt carbon.

C1-C4, incl. — 11-pF subminiature air variable, E. F. Johnson 189-564. Piston trimmers or Johnson 160-0104-001 suitable also.  
 C5-C7, incl. — Feedthrough capacitor.  
 D1, D2 — High-speed silicon switching diode, 1N914 or equivalent.  
 D3 — 15-volt, 1-watt Zener diode.  
 J1, J2 — Coaxial connector of builder's choice.

(Type BNC used in this model.)

L1, L3 — 3-1/2 turns no. 14 tinned bus wire, 1/2-inch ID  $\times$  3/4-inch (13  $\times$  19 mm) long. Tap source at 1-3/4 turns from trimmer end. Tap L1 also at 1/2 turn from ground.  
 L2, L4 — 3-1/3 turns No. 14 tinned bus wire, 1/2-inch ID  $\times$  3/4-inch (13  $\times$  19 mm) long. Tap L4 1/2 turn above C6.

Q1, Q2 — Vhf or uhf JFET (see text). Keep gate lead as short as possible, 1/8 inch (3 mm) or less.

RFC1 — 144-MHz rf choke, approximately 2.7  $\mu\text{H}$ . James Millen 34300-2.7 or equivalent. Alternatively, wind 20 inches (508 mm) of no. 30 enam. wire on the body of a 2700-ohm 1-watt carbon resistor. Use pigtails as anchor points for ends of winding.

at 20 volts maximum. Furthermore, the employment of JFETs eliminated four resistors and two capacitors, all of which would have been required in the gate-2 biasing circuits of the MOSFETs.

In the interest of eliminating the need for those sometimes-tricky neutralization circuits, the common-gate configuration was chosen. Common-gate amplifiers provide somewhat less gain than do the common-source types — approximately 10 dB less gain per stage, but by using two stages in common-gate the gain of the preamplifier is more than adequate for most applications. The circuit of Fig. 33 should exhibit a gain of between 15 and 20 dB, depending upon the transconductances of the two FETs picked from the supplier's shelf.

Motorola 2N5484s (MPF106) are used at Q1 and Q2. Alternatively, U310, E300, 2N4416 or 2N4417 devices can be used if one is willing to pay a bit more money. MPF102s would probably do a good job in the circuit of Fig. 33. Since the 2N5484s are designed for use into the 400-MHz region, they seemed likewise choices for low-noise operation. To assure good selectivity and thereby offer reasonable immunity to nearby out-of-band commercial signals, high-Q tuned circuits were employed. The section between Q1 and Q2 is a bandpass type, lightly coupled by means of a 2-pF silver-mica capacitor. Lighter coupling will provide greater selectivity, but with an attendant loss in

gain. Aperture coupling can be used in place of the method shown. If so, the aperture size must be adjusted to establish the gain and selectivity desired by the user.

Source bias is used in each stage to prevent the amplifiers from saturating in the presence of strong signals. The sources are tapped down on their respective tuned circuits to provide impedance matching.

In the prototype unit the drains were tapped down on the tuned circuits — a method used to achieve stability. As an aid to stability each stage has a 10-ohm resistor between its drain and the related tuned circuit. However, the gain of the preamplifier was somewhat less when using the 10-ohm resistors and connecting them to the stators of C2 and C4.

Decoupling networks are used between the stages (220-ohm resistors and 0.001- $\mu\text{F}$  bypass capacitors) to prevent inter-stage coupling along the 12-volt supply line. Filtering at rf is provided by using RFC1 and another 0.001- $\mu\text{F}$  feedthrough capacitor, thus helping to prevent unwanted rf from entering the preamplifier on the dc supply line.

Rf burnout protection is offered by two 1N914 diodes connected from the source tap on L1 to ground. The diodes are located at an impedance point which is higher than that of the 50-ohm antenna tap. This means the diodes will conduct sooner at the source tap because the rf-voltage level from static discharge or abnormally strong signals will always be

greater at the tap point than at the 50-ohm terminal. No change in amplifier performance could be noted after adding the diodes.

Protection from any abrupt increase in supply voltage brought about by ac-line transients is afforded by the use of a 15-volt, 1-watt Zener diode (D3) which is connected between the 12-volt supply line and chassis ground.

### Construction Information

To provide for adequate shielding against RFI two boxes are used in the construction of the preamp. The inner box is made from double-sided copper-clad pc board. It measures 4-1/2  $\times$  1-7/8  $\times$  1-1/4 inches (114  $\times$  48  $\times$  32 mm). The box walls and the partitions are soldered in place by using a 100-watt soldering iron with a small-diameter tip. The metal surfaces of the pc-board sections are silver plated, though the plating is not necessary as far as circuit performance is concerned. The plating does, however, retard tarnishing and make soldering somewhat easier.

The input and output rf connections, and those between the compartments, are made by means of small Teflon push-in feedthrough terminals which were obtained as surplus. The source-bias resistors and bypass capacitors are attached to Teflon standoff posts. Satisfactory substitutes for the feedthrough bushings can be fashioned from short lengths of



RG-59/U coax with the vinyl jacket and shield braid removed. Epoxy cement can be used to hold the homemade bushings in place.

Once the circuit is assembled in its pc-board enclosure the subassembly can be installed in a Minibox which measures 5-1/4 x 3 x 2-1/8 inches (133 x 76 x 54 mm).

### Adjustment and Use

Connect the preamplifier ahead of the fm receiver with which it is to be used. Apply 12 volts dc to the preamp, then supply a low-level signal to Q1 via J1. Peak each tuned circuit for maximum response by observing the 1st-limiter current reading of the fm receiver. The unit should then be ready to use.

This preamplifier was used ahead of a Motorola five-pipe Sensicon receiver during all tests. The "barefoot" fm receiver provided 20 dB of quieting with a 0.4- $\mu$ V input signal. With the preamp installed it was possible to obtain 20 dB of quieting with somewhat less than 0.1  $\mu$ V of input signal.

### A Practical Synthesizer

With so many amateurs working toward developing a synthesizer for use on 146-MHz fm, it is inevitable that the results are beginning to appear, each showing the builder's unique approach to the aforementioned problems. One practical synthesizer, contributed by K2CBA, represents a basic PLL circuit with a minimum of frills. The compromise between lockup time and spectral purity is a good one. It takes less than 0.5 second to lock to a new channel or to switch from transmit to receive. Spurious responses on the carrier are better than 35 dB down as seen on a spectrum analyzer. By using programming switches that do not read directly in frequency, considerable circuit complexity and expense is avoided. The output provides 15-kHz steps at 146 MHz, which allows working through a repeater input or "splitting the channel" to find a spot for simplex. Receiving and transmitting frequencies are selected independently by the use of separate thumbwheel switches.

The output frequency for transmitting is in the 6-MHz range, which is compatible with many of the surplus transmitters available. For receiving, the output is near 5.5 MHz as required for the RCA Carfone equipment for which the synthesizer was designed. Other makes of receivers might require modification of their local oscillator and frequency multiplication circuitry to work with this synthesizer.

### Circuit Features

A block diagram of the PLL synthesizer is shown in Fig. 34. It consists of a crystal-controlled oscillator and frequency-divider chain from which a reference

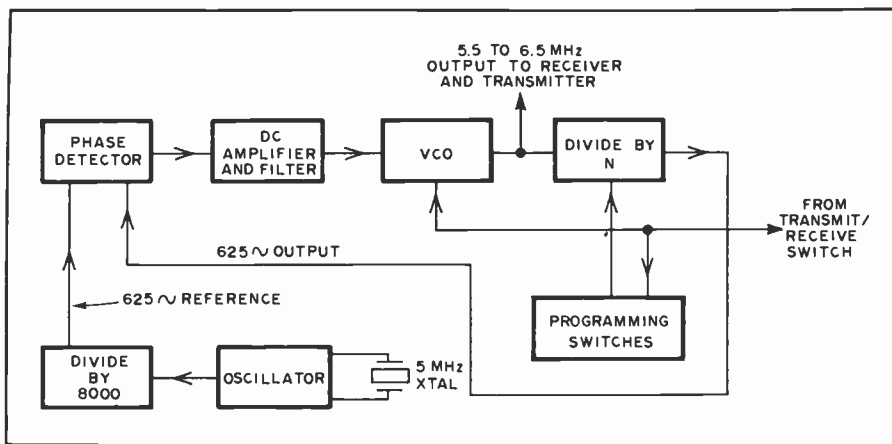


Fig. 34 — Block diagram of the synthesizer described in the text.

frequency is derived, a voltage-controlled oscillator whose output frequency is divided by programmable circuits, and a phase detector that compares the resultant signals from the divider chains and develops a correction voltage for the VCO.

The crystal oscillator generates a 5-MHz signal, which is divided by 8000 to produce a 625-Hz reference signal. A total of six ICs perform the oscillator and division functions. The VCO operates in the 5.5- to 6.5-MHz range and the output frequency of the VCO is divided down to 625 Hz to be compared with the output from the crystal-controlled source. Four programmable (divide-by-N) ICs are used following the output of the VCO. Thumbwheel switches are used to program the frequency-dividing circuit.

A single IC is used to compare the phase of the two 625-Hz signals, and, with the help of an external transistor, develops a voltage that is proportional to the phase difference between these signals. This voltage is applied to the VCO in such a manner as to cause a frequency change in the direction that will reduce the phase difference.

### VCO Circuit

The circuit for the VCO is shown in Fig. 37. It is simply a series-tuned Colpitts VFO with D1 providing the variable capacitance to adjust the frequency. The capacitance of this diode varies with a change in voltage applied to it, causing a corresponding change in the frequency of oscillation. Two small chokes, L2 and L3, along with C2 and C3, filter the correction voltage from the phase detector circuit. The value of this LC filter network influences the lockup time of the VCO, in addition to reducing the amplitude of any 625-Hz energy present. Values for L1 and D1 are selected so as to cause Q4 to oscillate on the frequency needed for transmitting, in this case 6 MHz.

A trimmer capacitor, C1, is added to the circuit to adjust the oscillator to the frequency needed for receiving. In the

receive mode, a positive voltage is applied to D2, causing it to conduct and effectively place C1 in parallel with D1. This lowers the frequency of oscillation to 5.5 MHz, which is multiplied by external circuits to the frequency needed for receiver mixing. At the same time that a voltage is applied to D2, the divide-by-N counter is reprogrammed to provide a 625-Hz signal for comparison with the reference, thus keeping the VCO stabilized. Q5, Q6, and Q7 are buffers to isolate the oscillator from any load and to provide two output connections. Output from Q7 is connected to the divider chain. Q6 provides output to the frequency multipliers in the transmitter or receiver.

### Frequency Dividers

A stable 625-Hz reference signal is derived from the 5-MHz oscillator and a frequency divider chain, as shown in Fig. 38. A hex inverter, SN74H04, is used as a crystal controlled oscillator. C5 is a trimmer capacitor to provide a means of adjusting the frequency to zero beat with WWV. The oscillator is followed by three divide-by-10 stages, then a divide-by-4 and a divide-by-2 stage for a total division of 8000. The 625-Hz output from this circuit is applied to one input of the phase detector.

The 5.5- to 6.5-MHz output from the VCO buffer, Q7, is divided by four programmable stages, called divide-by-N (Fig. 35). The divisor, N, is selected by setting the thumbwheel switches to the proper positions. These switches have the necessary binary-coded output connections to program the divided circuits. Two separate sets of thumbwheel switches are connected to the divider chain through isolating diodes. A positive voltage, applied to Q2, causes the diodes to conduct, thereby connecting the receive thumbwheel to the chain. When there is no voltage applied to Q2 and the transmit-receive bus is grounded, Q1 will conduct, causing the transmit channel selector switches to be connected to the divider chain. The 625-Hz output from



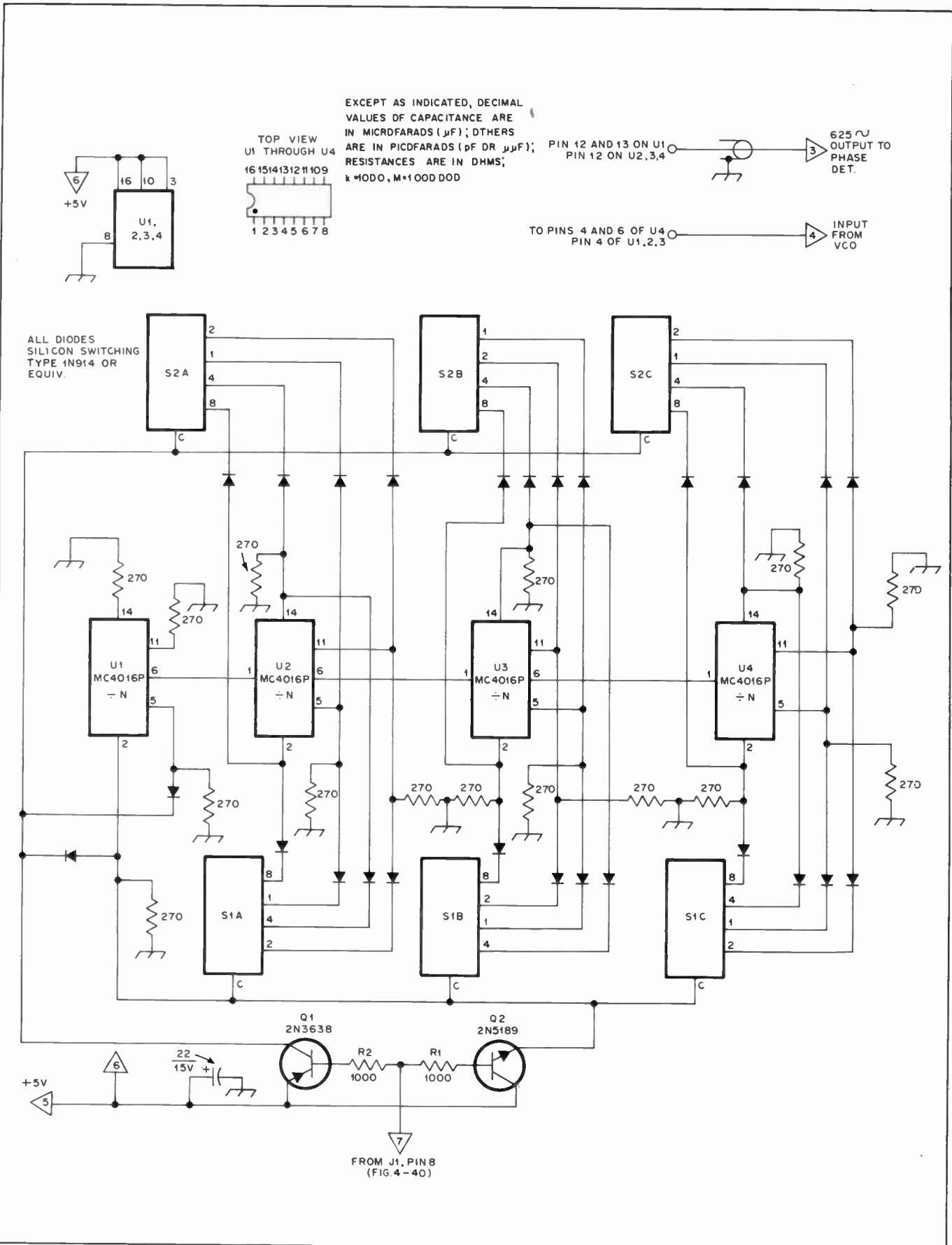


Fig. 35 — Schematic of the divide-by-N portion of the synthesizer.  
S1, S2 — Printed-circuit thumb-wheel switch,  
10-position, BCD, single-pole, EECo type  
1776 or equiv. U1-U4, incl. — TTL programmable modulo-N  
decade counter IC, Motorola MC4016P or  
equiv.



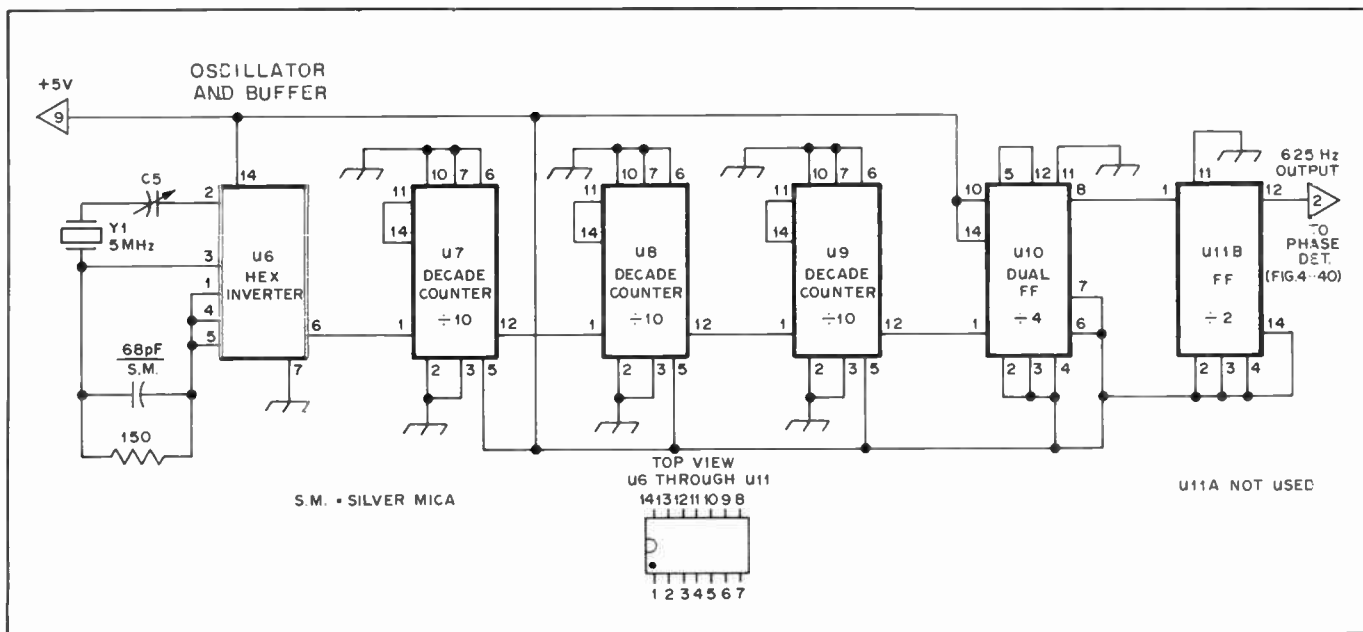


Fig. 38 — The reference oscillator and divider chain. C5 — 9- to 60-pF compression trimmer, Arco 404 or equiv. U6 — TTL high speed hex-inverter, IC, Texas Instrument SN74H0AN or equiv.

U7, U8, U9 — TTL decade-counter, IC, Texas Instr. SN7490 or equiv. U10 — TTL dual J-K master-slave flip-flop, Texas Instr. SN7473 or equiv. U11 — Same as U10 but one section not

used. Y1 — 5-MHz crystal, calibrated for 32-pF load capacitance. (International Crystal Co. part).

stressed. The coil, voltage-variable capacitor, and the trimmer capacitors associated with the frequency-determining parts of the circuit should be mounted securely to eliminate microphonic effects. The leads carrying dc supply voltages should be well filtered and shielded. Since it takes only millivolts of change to cause a wide excursion of frequency, the leads carrying the correction voltage to the VCO should be well shielded against hum and noise.

In the model described here, the VCO coil, L1, is wound on a 2-watt resistor of high ohmic value, thus obtaining a mechanically rigid mount. Dipped silver-mica capacitors are used in the oscillator circuits for temperature stability. All dc and correction voltages are connected to the pc boards via feedthrough capacitors of the solder-in variety. A blank copper-clad board, to provide shielding, is mounted between the frequency divider board and the one containing the VCO and phase detector. The boards are fastened securely to each other and to the chassis by threaded metal posts at the corners.

#### Adjustment and Operation

As complex as the circuitry for the synthesizer is, it requires few adjustments during operation. The 5-MHz oscillator can be set to zero beat with WWV by adjusting C5. If the reference-oscillator divider chain is working properly, a check with an oscilloscope or audio oscillator should show that a 625-Hz signal is present on pin 1 of the phase detector. The VCO should be oscillating at approximately 6 MHz with the correction voltage

removed from L3. If it is not, turns may be added or removed from L1 to correct the frequency. A small trimmer could be installed between the bottom of L1 and ground for exact frequency correction, but it will limit the effectiveness of D1 in maintaining lockup. C1 is adjusted to set the oscillator to the correct frequency for receiving.

The thumbwheel switches set the programming for the divide-by-N counters. S1 sets the division necessary for receiving, and S2 sets that needed for transmitting. With the particular switches used in this unit, the numbers are *not* channel numbers or the output frequency, but are the *divisor* numbers applied to the frequency out of the VCO. Direct-frequency readout would require a much more complex circuit. In either case, transmitting or receiving, the first digit of the four-number divisor is preprogrammed into the counter, with the last three numbers being selected by the thumbwheels. As an example, the VCO frequency required for transmitting on 146.34 MHz is 6097.5 kHz. To obtain 625 Hz for comparison with the reference, it is necessary to divide 6097.5 kHz by 9756. The 756 part of the divisor is set by the switches with the 9 part being preset in the wiring of the divide-by-N circuit.

For use in receiving, the output of the VCO is near 5.5 MHz. The equipment this synthesizer was designed to work with requires a local-oscillator injection frequency in the 130-MHz range for the first mixer. To receive 146.97 MHz, the output from the VCO must be 5561.875 kHz. Reducing this to 625 Hz requires a division

of 8899. The 8 part of the divisor is preset in the wiring and the 899 part is set by the thumbwheel switches.

For receivers that require a different injection frequency, it will be necessary to adjust the VCO output frequency and change the programming of the divide-by-N counters to obtain the correct combination. Additional information concerning the counters is available in the data sheets for the Motorola MC4016P Programmable Modulo-N decade counter. Motorola application notes AN438 and AN532A are suggested reading for those who would like to learn more about active filters and frequency synthesizers using the MC4044P phase detector.

To keep the noise problem to a minimum, it is recommended that modulation not be applied directly to the

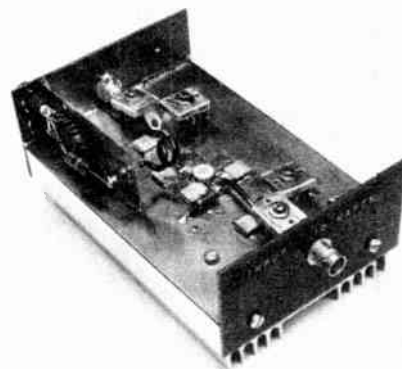


Fig. 39 — An end view of the breadboard version of the 50-watt 2-meter amplifier. The input circuit is at the lower right, and the output network is at the upper left.

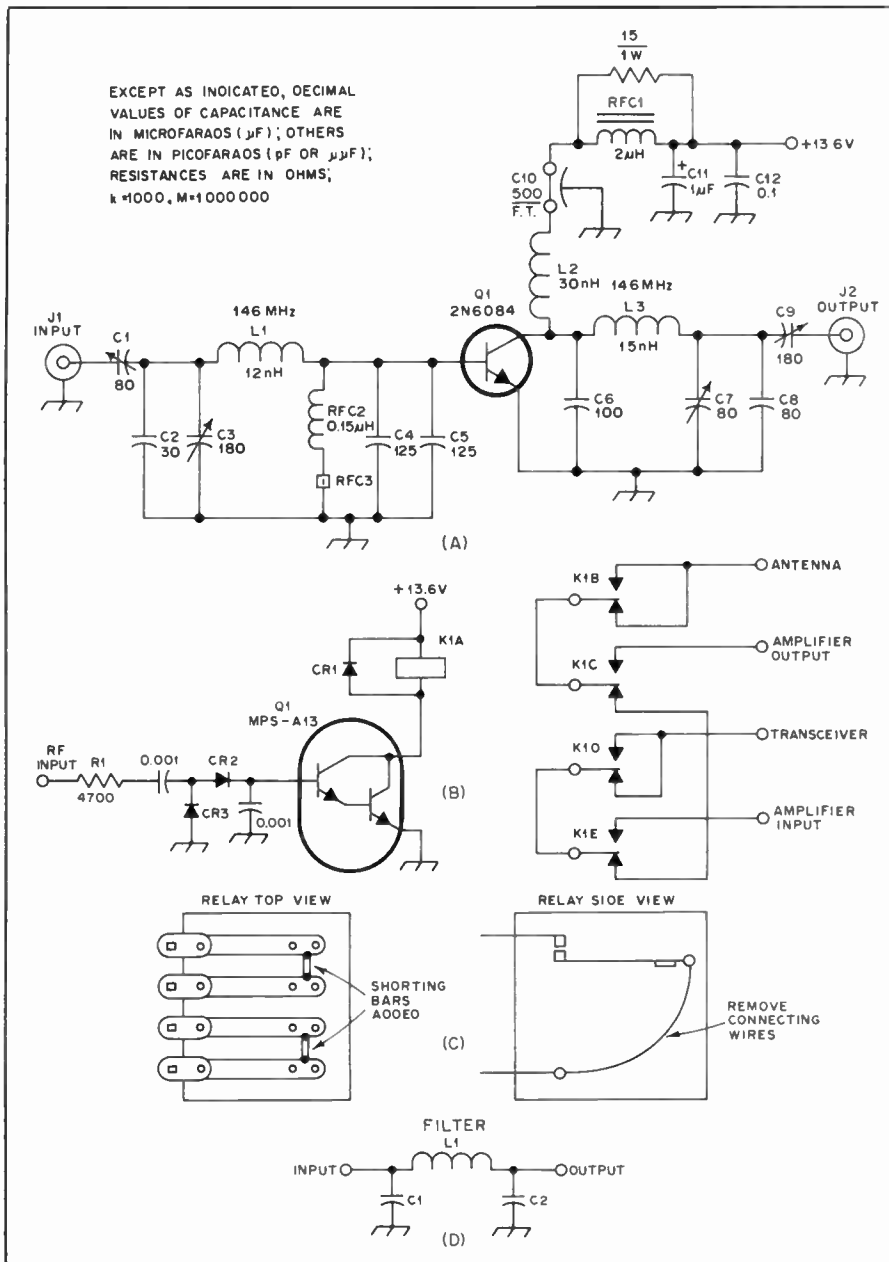


Fig. 40 (A) — Diagram of the amplifier which provides 40 to 50 watts output. Capacitors are mica unless otherwise noted. The heat sink is a Thermalloy 6169B, Allied Electronics no. 957-2890. (B) COR circuit. Capacitors are disk ceramic. (C) The COR relay is modified by removing the connecting wires from all four wiper arms and adding two shorting bars, as shown. Only the stationary-contact connections are used. (D) Pi-section output filter, C1 and C2 are 39-pF mica capacitors, Elemenco 6ED390J03 or equiv. and L1 consists of 2 turns of no. 18 tinned wire, 1/4 inch ID, 0.2 inch (61 × 5 mm) long (approximately 44 nH).

C1, C7 — 5- to 80-pF compression trimmer, Alco 462 or equiv.  
 C2, C4-C, C8, incl. — Mica button, Underwood J-101.  
 C3, C9 — 9- to 180-pF compression trimmer, Arco 463 or equiv.  
 C10 — Feedthrough type.  
 C11 — Tantalum.  
 C12 — Ceramic disk.  
 D1 — 100-PRV or more, 500-mA or more silicon diode (Motorola 1N4001 or equiv.).  
 D2, D3 — High-speed, low-capacitance 100-PRV silicon diode (Motorola MSD7000 dual package used here).  
 J1, J2 — Coaxial connector, panel mount.  
 K1 — 4pdt open-frame relay, 12-V contacts (Comar CRD-1603-4S35 or equiv., Sigma 67R4-12D also suitable), modified as described above.

L1 — 12 nH, no. 10 tinned wire, 1-1/4-inch (32-mm) long straight conductor.  
 L2 — 30 nH, 1-3/4 turns, no. 10 tinned wire, 3/8-inch ID, 3/4 inch (10 × 19 mm) long.  
 L3 — 15 nH, no. 14 tinned wire, 3/4-inch (19-mm) long straight conductor.  
 L4 — 2 turns of no. 18 tinned wire 1/4-inch ID, 0.2-inch (6 × 5 mm) long (approximately 44 nH).  
 Q1 — Motorola silicon power transistor.  
 Q2 — Npn silicon Darlington transistor,  $H_{FE}$  of 5000 or more, Motorola MPS-A13 or equiv.

synthesizer. A phase modulator stage following the output buffer will provide good results. Many of the commercially manufactured units with which the synthesizer can be used will have such a phase modulator as part of their original circuitry.

## 2-Meter Solid-State RF Power Amplifiers

The majority of the commercially made 2-meter fm transceivers available today have rf power-output levels of 1 to 15 watts. There are many occasions when an fm operator would like to have a little more power to be able to work over greater distances. Described here are two amplifiers, one for 25 watts and another for 50 watts output for the 2-meter band. Both amplifiers use a single transistor and operate directly from a 13.6-volt vehicular electrical system.

### Circuit Description

The amplifier circuit shown in Fig. 40 utilizes a single 2N6084 transistor operated in a Class C, zero-bias configuration. This mode of operation has the advantages of high collector efficiency at full output and zero dc current drain when no rf driving signal is applied. The reader should note that zero-bias operation yields an amplifier that is not a "linear." It operates Class C and is designed for fm or cw operation only; it would produce objectional distortion and splatter if used to amplify a-m or ssb signals.

The amplifier operates directly from an automobile electrical system, so no additional power supply is required for mobile operation. The input and output tuned circuits are designed to match the impedances of the transistor to a 50-ohm driving source and to a 50-ohm antenna system, respectively. Since both the input and output impedances of the transistor are extremely low (in the 1- to 5-ohm region), the matching networks employed are somewhat different than those used with tubes. The networks chosen for the amplifier are optimized for low-impedance matching.

The elaborate decoupling network used in the collector dc feed is for the purpose of assuring amplifier stability with a wide variety of loads and tuning conditions. The 2N6084 transistor is conservatively rated at 40 watts output (approximately 60 watts dc input). The amplifier can be driven to power-output levels considerably higher than 40 watts, but it is recommended that it be kept below 50 watts output. If the transmitter or transceiver has more than 10 watts of output, an attenuator should be used at the amplifier input to keep the power output below 50 watts.

### Construction Details

The usual precautions for building a solid-state amplifier are followed. These include proper mechanical mounting of



the transistor, emitter grounding, heat sinking, and decoupling of the supply-voltage leads. The fixed-value mica capacitors, Underwood type J-101, are special mica units designed for high-frequency applications. The core for RFC1 and the rf bead used for RFC3 are Ferroxcube products.<sup>2</sup>

The amplifier is constructed on a pc board that is bolted to a heat sink. A few islands can be etched on the board for tie points. A complex foil pattern is not required. In the amplifier shown in the photograph and pictorial layout (Figs. 39 and 41) islands were etched only for input and output tie points. Circuit-board islands may also be etched for the transistor base and collector leads. However, an interesting alternative method was used in the author's breadboard amplifier. The base and collector islands were formed by attaching small pieces of pc board to the top of the main board. This procedure added a few tenths of a pF of capacitance at the connection points, so if you choose to etch islands directly on the main board you may want to increase the value of C6 slightly. (The values of C4 and C5 are not critical.)

A word about the care of a stud-mount rf power transistor: Two of the most important mounting precautions are (1) to assure that there is no upward pressure (in the direction of the ceramic cap) applied to the leads, and (2) that the nut on the mounting stud is not overtightened. The way to accomplish item 1 is to install the nuts *first* and solder the leads to the circuit later. For item 1, the recommended stud torque is 6 inch-pounds. For those who don't have a torque wrench in the shack, remember that it is better to undertighten than to overtighten the mounting nut.

The transistor stud is mounted through a hole drilled in the heat sink. A thermal compound, such as Dow Corning 340 heat-sink grease, should be used to decrease the thermal resistance from transistor case to heat sink. See the excellent article by White in April 1971 *QST* for details of heat-sink design.

Series impedance in the emitter circuit can drastically reduce the gain of the amplifier. Both transistor emitter leads should be grounded as close to the transistor body as is practical.

The wiring for the dc voltage feeder to the collector should have extremely low dc resistance. Even a drop of 1 volt can significantly reduce the power output of the amplifier. A good goal is less than 0.5-volt drop from the car battery to the transistor collector. With operating currents of several amperes, the total dc resistance should be only a fraction of an ohm. A standard commercially made heat sink is used for the 50-watt amplifier, and it is adequate for amateur communications. Forced-air cooling across the heat sink should be used for any application


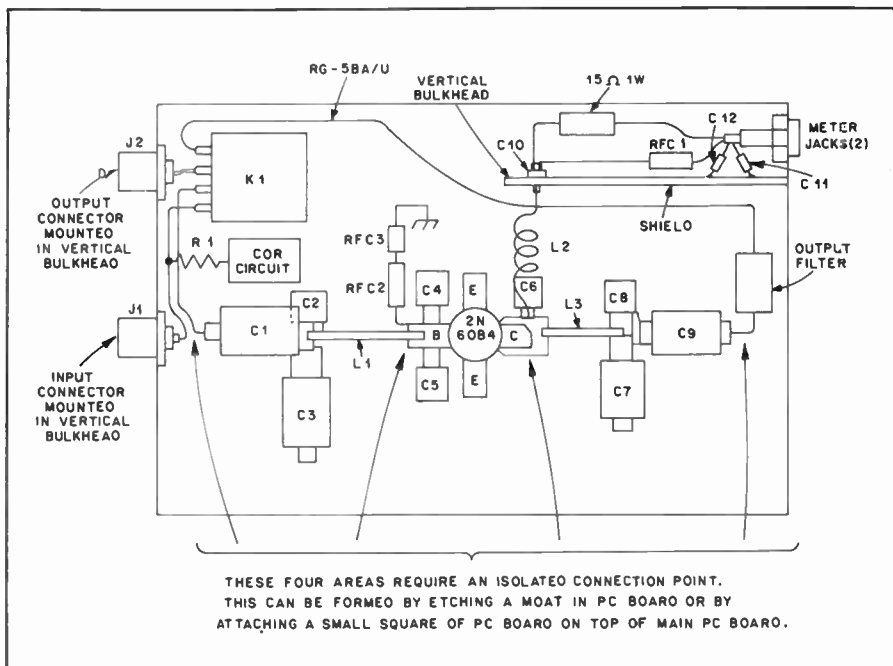


Fig. 41 — Parts-layout diagram for the 50-watt amplifier (not to scale). A 4 x 6-inch (102 x 152-mm) pc board is used as the base.

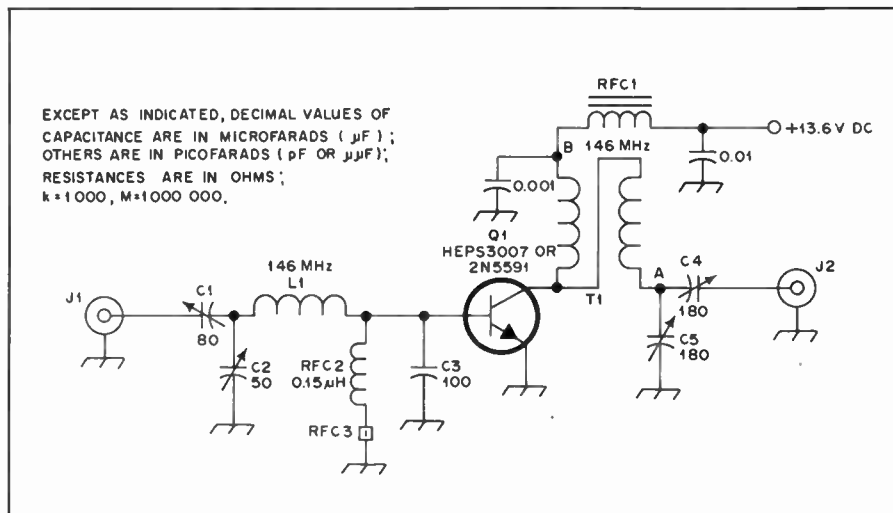

level, not by detuning the final. In the case of an outboard PA stage, such as described here, both the input and output networks can be tuned for maximum rf output, if the driving source has an output impedance of approximately 50 ohms. However, a better procedure consists of tuning the output tank circuit for maximum rf output and tuning the input circuit for minimum SWR as measured between the exciter and the final amplifier. This tune-up procedure has the added advantage of assuring that the amplifier presents a 50-ohm load to the exciter. A dc ammeter to check collector current is a useful tune-up aid. Since tuning is for peak output, a Monimatch-type SWR bridge is adequate for the job. The best tuning procedure is to monitor simultaneously both output power (absolute or relative) and the SWR between the exciter and amplifier.

First, apply dc voltage with no rf drive. No collector current should flow. Then apply a low level of rf drive — perhaps 25 percent or less of the rated 10 watts maximum drive — and tune the input network for maximum indicated collector current. The networks may not tune to resonance at this low drive level, but you should at least get an indication of proper operation by smooth tuning and lack of any erratic behavior in the collector-current reading. Gradually increase the drive until full rated output is reached.

### An Additional Design

For those who own a low-power fm transceiver, an intermediate amplifier stage or a final amplifier providing 10 to 25 watts may be desired. The circuit of Fig. 42 is suitable for the 2N5591 or HEP S3007 transistors (25 watts), and the 2N5590 or HEP S3006 transistors (10 watts). An unusual feature of this circuit is the use of a transmission-line transformer in the output network (Fig. 43). The construction and tuneup procedures for the amplifier of Fig. 42 is similar to that described earlier for the 50-watt amplifier.

### Accessories

When an amplifier stage is used with an fm transceiver, a method of automatic transmit/receive switching is needed. A simple carrier-operated relay (COR), such as that of Fig. 40B, can be employed for the amplifiers described in this section. The level of input rf required to operate the COR is determined by the value of R2. One to two watts of 2-meter energy will operate K1 when a 4700-ohm resistor is employed. The rf signal is rectified by two high-speed switching diodes; the dc output from the rectifier is applied to Q2, a Darlington-connected transistor pair. When sufficient current is developed in the base circuit, Q2 will turn on, activating K1. A transient-suppression diode is included across the relay coil to prevent voltage-spike damage to Q2.

The switching circuits needed to take the amplifier in and out of the circuit are somewhat complex. The cost of four coaxial relays would be prohibitive. But, an open-frame relay can cause sufficient loss at 146 MHz to severely degrade the sensitivity of the associated receiver. To get around this problem the designer modified an inexpensive relay. The long leads to the wiper arms were removed and discarded. Two shorting bars were added, as shown in the drawing (Fig. 40C). External connections were made only to the stationary contacts. Received signal loss through the modified relay measured 0.4 dB.

### Appendix

<sup>1</sup>Amidon toroid cores are available from Amidon Associates, 12033 Otsego St., North Hollywood, CA 91607.

<sup>2</sup>Ferroxcube components can be purchased from Elna Ferrite Laboratories, Inc., 9 Pine Grove St., Woodstock, NY 12498.

<sup>3</sup>J. W. Miller chokes are available from distributors, or directly from J. W. Miller, 19070 Reyes Ave., Compton, CA 90224.

<sup>4</sup>Underwood mica capacitors are available from Alpha Electronic Laboratories, 2302 Oakland Gravel Rd., Columbia, MD 65201.

<sup>5</sup>A circuit board for the 50-watt amplifier is available from Circuit Board Specialists, P. O. Box 969, Pueblo, CO 82002.

### Touch-Tone Control

From the inception of automatic dialing, signaling from telephone instruments was accomplished using dc pulses. This signaling method required direct wired connections, as a dc path was needed. For transmission via a radio circuit, the dc pulses had to be converted to a keyed audio tone. In the early 1960s the Bell Telephone Companies introduced a new, faster tone-coded dialing system which was given the registered trade name *Touch-Tone*. Because the tone signals of the Touch-Tone system could be transmitted over any audio carrier or radio circuit, many amateurs have adopted the telephone-company system for control of fm remote-base stations and repeaters.

Because two tones are used for each function in the Touch-Tone system, reliability is excellent even when used on radio circuits that are noisy or fading. Another factor that has made Touch-Tone popular with repeater groups is that many use autopatch connections to the public telephone network. By ordering a Touch-Tone line for the repeater autopatch, the same encoders and decoders can be used for the phone patch and repeater control.

### Encoders

Touch-Tone information is coded in tone pairs, using two of eight possible tones for digits zero through nine and six special functions. The audio frequencies used are given in Fig. 44. The tones are divided into the low group, 697, 770, 852 and 941 Hz; and the high group, 1209, 1336, 1447 and 1633 Hz. One tone from each group is used for each function. For residential and business telephones, a

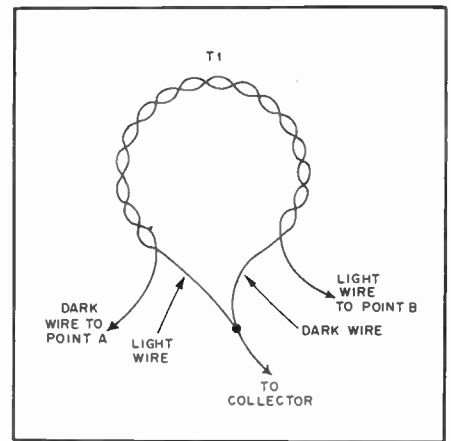


Fig. 43 — Transmission-line output transformer consisting of two 4-inch (102-mm) long conductors, No. 20 enam. wire, twisted to 16 crests per inch, using an electric drill. The conductors should be color coded, one with one color and one with a second color. Form the twisted pair into a 1/2-inch (13-mm) dia circle. Unwind the leads so that only the portion of the pair forming the circle remains twisted. Connect the leads of each color as shown.

Low Tone (Hz)	High Tone				
	1209 Hz	1336 Hz	1477 Hz	1633 Hz	
697	1	2	3		F <sub>0</sub>
770	4	5	6		F
852	7	8	9		I
941	*	0	#		P

Fig. 44 — Frequencies used in the Touch-Tone signaling system.



Fig. 45 — This Western Electric Touch-Tone encoder has been mounted in a 4 x 4 x 2-inch (102 x 102 x 51-mm) utility box (Bud AU-1083). Encoders are sold by most telephone supply houses, including Telephone Equipment Co., P. O. Box 596, Leesburg, FL 32748. Tel. 904-728-2730.

12-button encoder pad consisting of digits zero through nine and symbols pound # and star \* are employed. A typical encoder is shown in Fig. 45, and the connections for pads manufactured by Western Electric and Automatic Electric are shown in Fig. 46. The telephone pads will work with as little as nine volts or as much as 24 volts dc applied. Either high- or low-impedance output may be em-

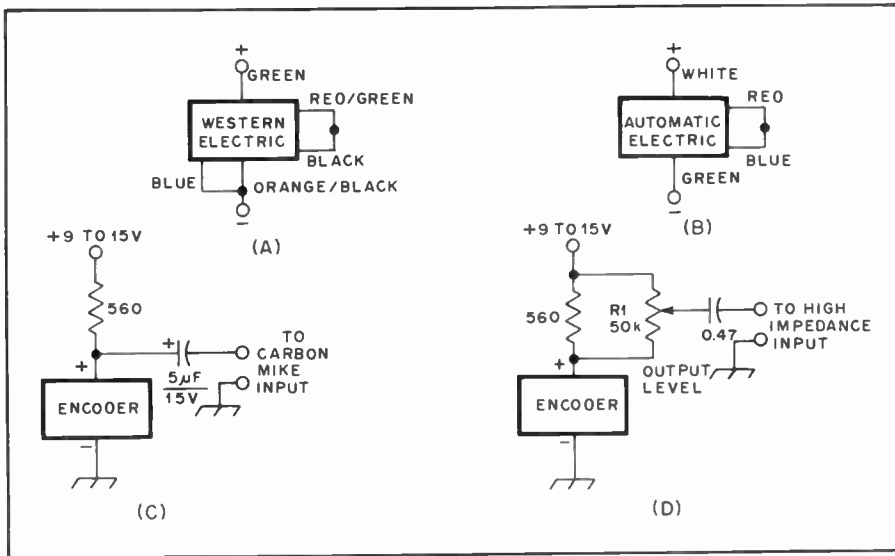


Fig. 46 — Typical connections for the encoders manufactured by Western Electric (A) and Automatic Electric (B). If low-impedance output is needed to drive a carbon-microphone input, the circuit at C can be employed for either encoder. Likewise, the circuit at D will provide a high-impedance output. R1 can be any miniature composition control; the types made for mounting on circuit boards are ideal.

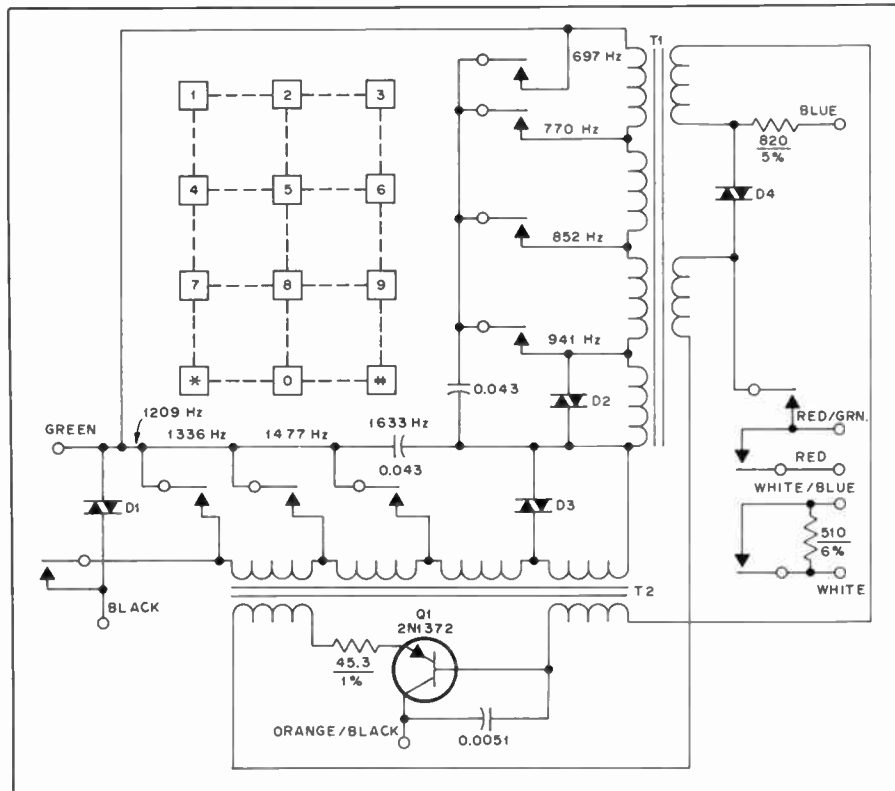


Fig. 47 — Diagram of a typical Western Electric Touch-Tone generator. T1 and T2 are special multi-winding transformers manufactured by Sangamo Electric and others. D1-D4, incl., are silicon varistors.

employed, as shown in Figs. 46C and D. A circuit diagram of a typical telephone-company pad is given in Fig. 47. Individual models will vary slightly, but the basic circuit used in all models is the same. A single transistor produces two tones. Two LC circuits are used, one for the high tone group and one for the low tones. Some people are bothered by the use of a single transistor to generate two

audio frequencies, so the lower tone can be considered the frequency of oscillation while the high tone is called a parasitic oscillation, for purposes of explanation.

#### A Homemade Touch-Tone Encoder

To generate the Touch-Tone codes, two special integrated-circuit function generators can be used. The ICs are Signetics NE566s, voltage-controlled oscillators that

were outgrowths of phase-lock-loop technology. The circuit shown here was developed by Jim Wyland of Signetics. This design, Fig. 49, provides 11 number codes. If the additional frequency of the 12-button telephone pad, or the five additional frequencies of the 16-button generator are needed, one can add appropriate timing resistors. The operating frequency of an NE566 is approximately:

$$F_0 = \frac{2}{R1C1} \times \frac{V8 - V5}{V8 - V1}$$

where V8, V5 and V1 are the voltages at pins 8, 5 and 1, respectively.

In the practical circuit shown in Fig. 49, the value of the timing resistors in each oscillator, R1 and R2, are selected to generate the highest frequency desired. Additional resistors are switched in to lower the frequency of oscillation to the other Touch-Tone frequencies. Both oscillators use a 0.022 µF capacitor for timing. Calibration is needed only at one frequency for each oscillator since the other tones are set by the resistor used.

The keyboard is a Chromerics EF-20271 which is Touch-Tone encoded. Similar keyboards are available from other vendors. The resistors used in the frequency-determining networks must be one-percent values if the audio produced is to be on the correct frequency. The ICs and the other small components can be mounted on a pc board or electronic pegboard. Sockets are recommended for the ICs.

For those who require Touch-Tone signals that meet the telephone-company specifications, a simple encoder can be constructed using a hybrid IC. The integrated circuit is manufactured by Microsystems International, a Canadian firm, and has excellent specifications: operating voltage from 4.5 to 45, maximum frequency drift of 1.5 percent, amplitude stability of plus or minus one dB, and total distortion of less than eight percent. Designated the ME8900, the IC is contained in a 1-1/8 × 1-3/8-inch (29 × 35 mm) plastic package with 16 leads brought out in dual-in-line fashion.

A typical circuit using the ME8900 is shown in Fig. 50. A 9-V transistor radio battery supplies dc potential. If the encoder is to be powered by an automotive electrical system, a 36-V Zener diode should be connected from pin 16 to pin 13 to prevent high-voltage transients from damaging the IC. If a supply voltage of 12 or more is used, the 1-µF capacitor connected to pin 1 may be eliminated. Any Touch-Tone encoded button pad may be employed — the Chromerics EF 20271 is used in this design. The small size and low profile of U1 and U2 allow the





Fig. 48 — This homemade Touch-Tone generator is housed in a Western Electric sloping-front plastic box.

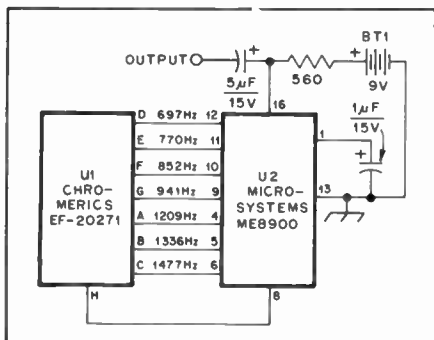


Fig. 50 — Circuit for a simple Touch-Tone encoder. The capacitors are electrolytic and the resistor is 1/4-watt composition.

BT1 — Miniature 9-V battery.

U1 — Chromerics EF-20271 (See Fig. 49 for address).

U2 — Microsystems International ME8900 (Microsystems International, 800 Dorchester Blvd., Montreal, PQ. Tel. 514-861-7626.)

encoder to be constructed on the side of a hand-held transceiver.

### A Decoder

The Touch-Tone decoders used by the telephone company system consist of input filters which separate the high- and low-tone groups, followed by additional LC filters that separate the individual tones. The output control section uses relays. For amateur applications a decoder can be constructed using modern phase-lock loop (PLL) ICs which will allow a decoder to be constructed which is smaller, lighter and less costly than the Western Electric model.

The circuit of the IC Touch-Tone decoder is shown in Fig. 51. This design was developed by Jim Wyland of Signetics Corp., with a few modifications added by WASCJG. Seven NE567 ICs are used in the decoder section and four TTL quad gate packages are used in the logic portion. Each IC is tuned to a Touch-Tone frequency by a resistor and a

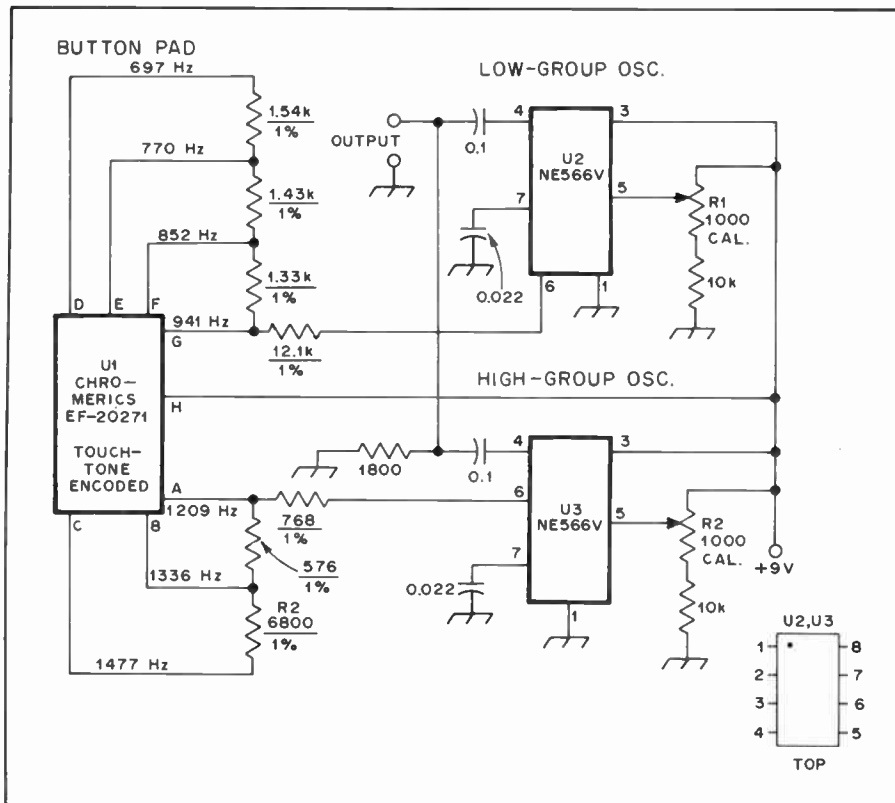


Fig. 49 — Schematic diagram of the tone generator. All resistors are 1/2-watt composition.

Capacitors are mylar.

BT1 — 9-V miniature battery.

R1, R2 — Linear-taper, 1/2-watt composition control.

U1 — Chromerics EF-20271 keyboard (available from Chromerics, 77 Dragon Ct., Woburn, MA

01801. Tel. 617-935-4850).

U2, U3 — Signetics NE566V. Alpha Elect. Labs, 2302 Oakland Gravel Rd., Columbia, MO 65201. Tel. 314-449-1362.

capacitor. The approximate frequency is given by the relationship

$$f \approx \frac{1}{RC}$$

The bandwidth of the PLL has been set so that a tone no more than four percent high or low in frequency will be demodulated. When a tone is received, the PLL output goes from a logic high to a logic low. When a Touch-Tone encoded pair is present, 796 and 1209 Hz representing the number 1 for example, PLLs U1 and U5 will have logic low outputs. These two lows appear at the input to NOR gate U8A, changing its output to a high. The output of the NOR gate can be used to drive a relay (using a switching transistor) or a function decoder.

### A Control-Function Decoder

The control decoder shown in Fig. 53 was designed by WSPCX for the Texas Inter-City Repeater System. The decoder is compatible with any seven-tone system such as Touch-Tone. The Touch-Tone signals must be decoded to a TTL-compatible output, one output for each

tone combination, similar to the decoder shown in Fig. 51.

The control decoder allows 32 stations, each having 32 control functions, to work in the same relay system; all stations are capable of independent control.

A control transaction is initiated by the Touch-Tone star (\*) button which resets the decoder to a known starting point. The first five Touch-Tone digits are designated as the address field. The station address is predetermined by straps on the control card. The next five Touch-Tone digits (6 through 0) are designated as the control-function field. When the desired address and control digits have been entered, the control transaction is executed by the Touch-Tone pound (#) button. If the entered address agrees with the station address, the control field is then stored and decoded to one of 32 control functions. The control decoder has provisions for an external clear function, and an external control disable function to inhibit any input.

The control decoder consists of two levels of parallel storage, a parallel four-bit comparator, and two binary (four-bit) to one-out-of-sixteen decoders. The first level of storage consists of two five-bit universal shift registers to store the



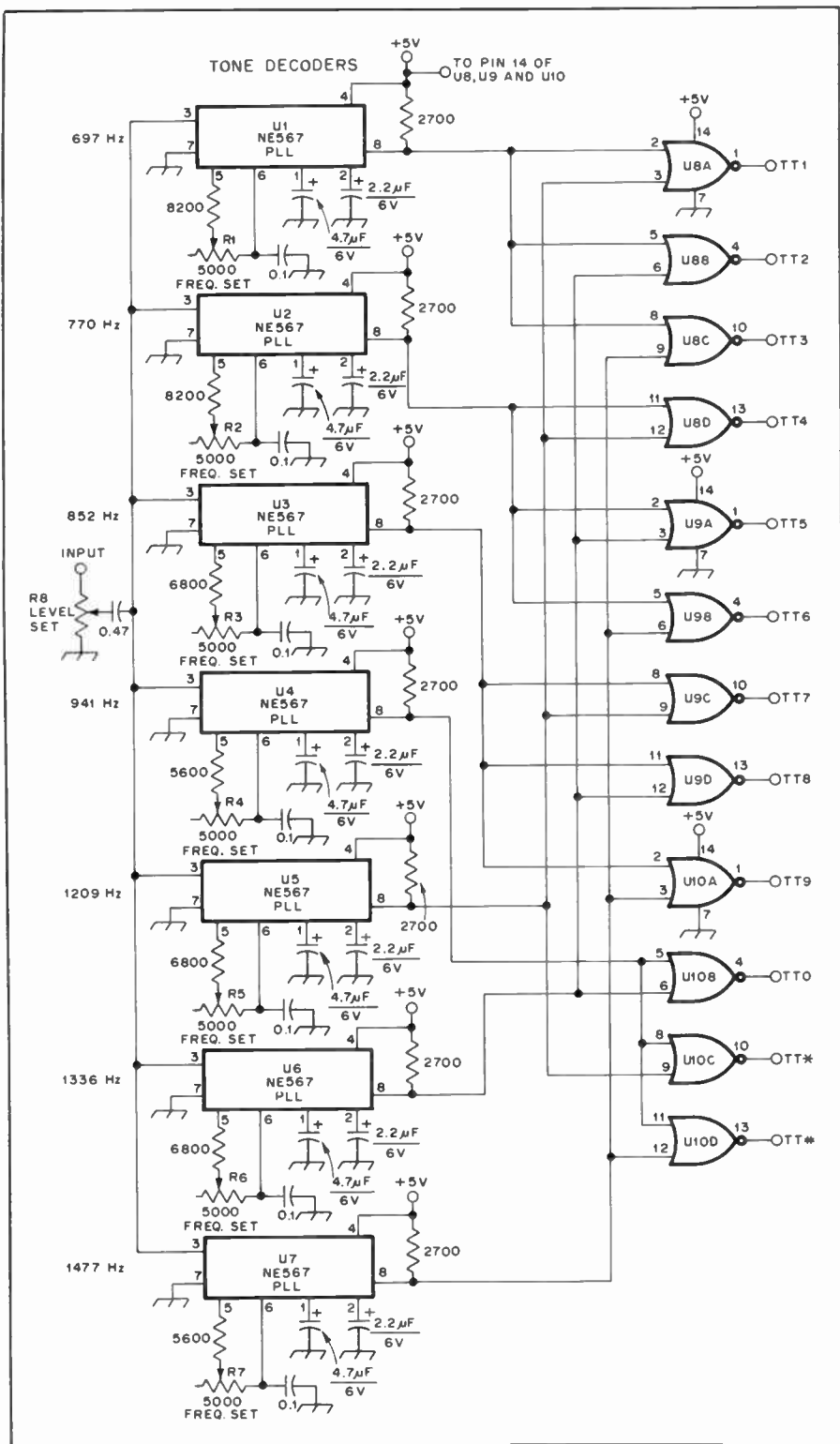


Fig. 51 — Touch-Tone decoder. Resistors are 1/2-watt composition and capacitors are mylar. R1-R8, incl., are 1/2-watt, pc-mount composition controls. Final adjustment of the frequency of each PLL should be made by adjusting the control as needed to center each phase-locked loop on the telephone-company frequency. A frequency counter facilitates the adjustment procedure. U1-U7, incl., are Signetics type NE 567V, and U8-U10, incl., are Motorola MC7402Ls.

address and function entries as they are generated and decoded. The shift registers are used in the parallel mode. The unique features of these storage elements are the individual direct set and the common reset modes of parallel data entry. The Touch-

Tone star line is connected to the common reset line and is used to set the ten bits of storage to the zero state. The reset action also erases any logic ones that remain from any previous control transaction. The desired pattern is entered by genera-

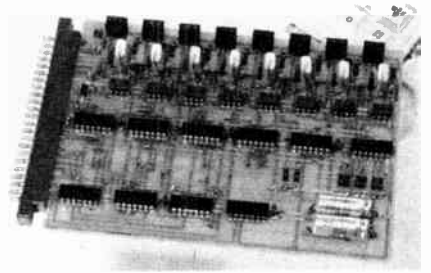


Fig. 52 — A commercially manufactured version of the circuit shown in Fig. 51.

ting only those Touch-Tone signals that correspond to the required logic ones; the logic zeros are already present because of the reset action. Each Touch-Tone digit provides direct set to the storage-register location assigned to the particular digit; when the digit is pressed, a logic one is stored in that location; if an error is made, the star button must be pushed and the entire sequence repeated.

The station address is assigned by jumpers on the control-decoder pc card. The address is then resident in a particular system and is compared to every Touch-Tone entered address. The address recognition hardware consists of a five-bit register (U1) and a four-bit magnitude comparator (U3) with cascading capability. The address field is five bits, four bits used as the compare inputs, and one bit used as the cascading input. When the entered address, temporarily stored in U1, compares with the system resident address, a logic one is generated by the magnitude comparator, thus enabling the data field to be permanently stored and decoded when the pound button is pressed. The five-bit address field will allow  $2^5$  or 32 address combinations. It is advisable that the null set (00000) not be a valid address field; so, there are 31 valid system addresses.

The control-function digits are temporarily stored in the other five-bit register, U2. When the address has been entered, the pound function will cause the control data in U2 to be permanently stored in storage registers U4 and U5.

The five-bit data field allows  $2^5$  or 32 control functions to be decoded. Only one decoded control function is available at any given time; so, some form of latching relay or other electronic storage element must be provided to implement the control capability available at the decoder output. A decoded output function will appear as a TTL logic low. Typical addresses are shown in Fig. 54.

The output-function decoding is accomplished by two binary-to-one-out-of-sixteen decoders, U6 and U9. These binary decoders have two enabling inputs which allow either one or the other decoders to be active at a specific time; this allows the same four bits of control function to be used on both decoders, plus

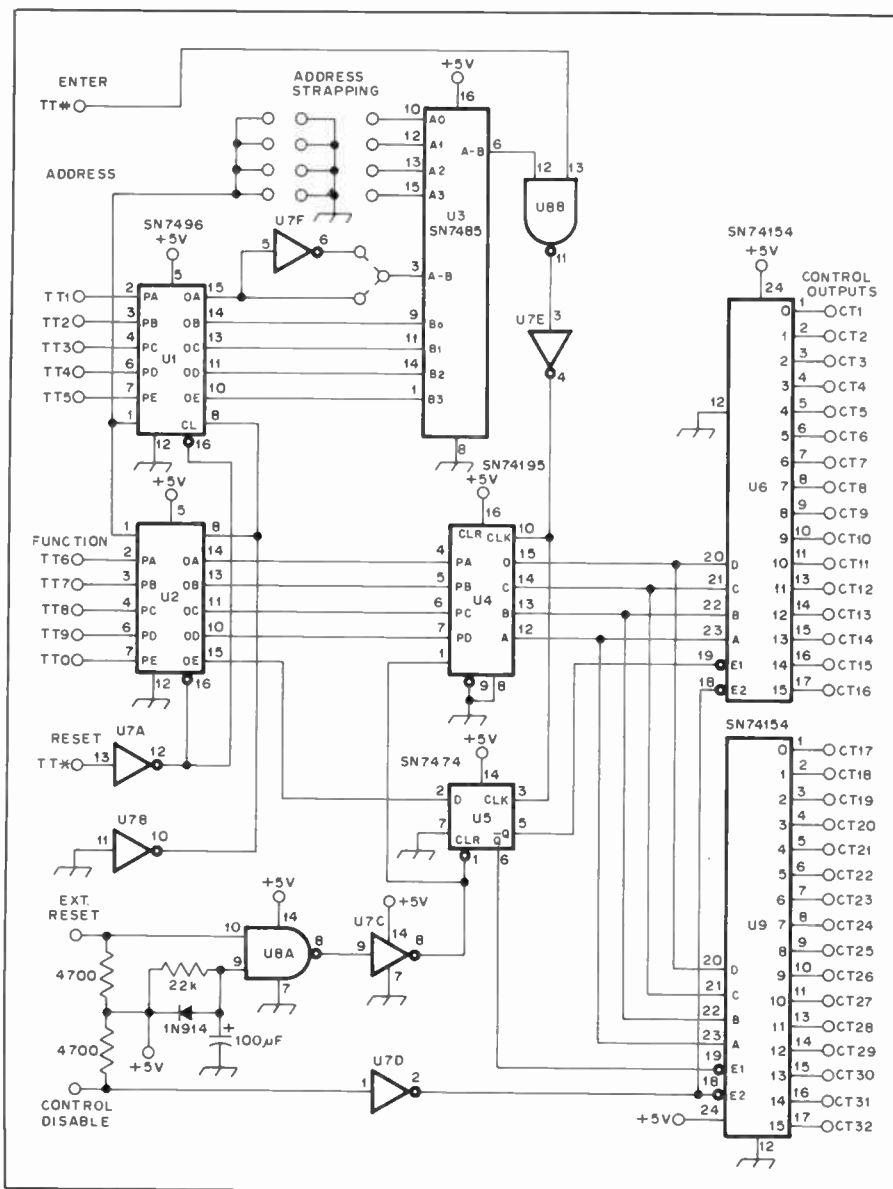


Fig. 53 — Circuit of the function and command decoder. Resistors are 1/2-watt composition and the capacitor is electrolytic.  
 U1, U2 — 5-bit shift resistor, type 7496.  
 U3 — 4-bit comparator, type 7485.  
 U4 — 4-bit shift register, type 74195.  
 U5 — Dual flip-flop, type 7474.  
 U6, U9 — 4-line to 16-line decoder, type 74154.  
 U7 — Hex inverter type 7404.  
 U8 — Quad 2-input NAND gate, type 7400.

the fifth control function bit used to select which control decoder will be active. In this manner, five encoded (binary) control function bits are decoded to 32 output functions. It is advisable to define the null set (00000) control code as the primary system reset code; so, there are only 31 valid functions. The null function is decoded in any event, and is there to be used by wiring to the decoded output, if desired.

There are three ways to enter the null set. The first is by Touch-Tone signal. A second null set occurs whenever the system power is turned on. The network of R1, C1 and D1 with sections of U7 and U8 automatically generate a reset signal to the secondary storage elements, U4 and U5. When U4 and U5 are reset, the stored data exactly correspond to the null data

field, and are decoded in exactly the same manner. The third way is by use of the external reset function. This input allows external generation of a reset signal for storage registers U4 and U5; the external reset forces a null data pattern to be stored in U4 and U5 and is decoded as that function. A logic 0 on the external reset line (or a contact closure from that connection to ground) will cause the reset signal to be generated.

To provide a local inhibit of any further control functions being decoded, a control-disable function is designed into the decoder logic. A logic low (or a contact closure to ground) will disable all the outputs of U6 and U9; these outputs will remain in the logic high state as long as the disable function is energized. When the disable function is released, the

### Sample Control Code Assignments

Address	Number
Repeater 1	2
Repeater 2	3
Repeater 3	2,3
Repeater 4	4
Repeater 5	2,4
Repeater 6	3,4
Repeater 7	2,3,4
Repeater 8	5

Control function	Number
CT2 — Cross link on	0
CT3 — Down link on	9
CT4 — Up link on	9,0
CT5 — Autopatch on	8
CT6 — Autopatch off	8,0
CT7 — Timer reset	8,9
CT8 — Antenna 1 on	8,9,0
CT9 — Antenna 2 on	7
CT10 — Main transmitter on	7,0
CT11 — Backup transmitter on	7,9
CT12 — Direct repeat start	7,9,0
CT13 — Backup receiver on	7,8

Fig. 54 — An example of some of the remote switching and control operations which can be handled by the control-function decoder. A system such as this can be very useful in emergency situations when it might be necessary to link several repeaters to extend the capability beyond an immediate trouble area.



Fig. 55 — This dual-tone encoder is built in a surplus housing which was sold with the rotary dial no. TEL from John Meshna, P. O. Box 62, E. Lynn, MA 01904.

outputs will assume the state of the last encoded function entered in registers U4 and U5. This disable function can be used as an overriding local control of a system via another control link or to lock the system into a particular operational mode. The external-reset and control-disable functions may remain unused by leaving the respective input pins unconnected.

### References

- FM and Repeaters for the Radio Amateur*, an ARRL publication.
- Goldsmith, et al. *Frequency modulation*, in two volumes, RCA Review, RCA, 1948.
- Hund, *Frequency Modulation*, McGraw-Hill Book Company, 1942.
- Kiver, *FM Simplified*, D. Van Nostrand Company, Inc., N.Y.
- Lytel, *Two-Way Radio*, McGraw-Hill Book Company, 1959.
- Rider and Uslan, *FM Transmission and Reception*, John I. Rider Publisher, 1948.
- Wolf, *FM Schematic Digest*, Two-Way Radio Engineers, 1970.07 *Pre-Progress Line Diagrams*, in two volumes. Mobile Radio Department, General Electric Company, 1968.

# Narrow-Band Voice Modulation

The December 1977 issue of QST<sup>1</sup> heralded a new and unique system for conserving communications bandwidth. Unlike other systems developed previously, this one provides very high-quality voice transmission. This technique, now implemented and in the production stage, works at baseband (audio) rather than at intermediate or radio frequencies (i-f or rf). Thus it is applicable to virtually all types of analog and digital transmission systems. The system includes the newly developed frequency compandor<sup>2</sup> and the well-known, but not extensively used, ampli-

tude compandor.<sup>3</sup> Use of both devices within the same baseband system offers significant improvements in adjacent channel rejection and signal-to-noise ratio (SNR).

The transceive baseband system operates on the audio waveform just after the microphone but before the speaker. The frequency compandor filters the essential parts of speech and down converts this information electronically on transmission, thus providing a significant reduction in transmitted bandwidth. A narrower bandwidth signal causes less interference to others operating in the same band. It also allows the use of a sharper and narrower receive filter, which

greatly reduces adjacent-channel interference. Tests of the baseband system conducted for the FCC<sup>4</sup> indicate that an interfering signal only 2-kHz off frequency can be 40-dB stronger than the desired on-frequency signal and yet be essentially eliminated.

A significant advantage of the narrower bandwidth (BW) is that less noise power competes with the signal. Comparing the frequency compandor noise bandwidth with a "typical" amateur receiver indicates that up to 3 dB greater SNR can be achieved.

The amplitude compandor, known since the 1930s but only recently made

<sup>1</sup>Harris, R. W. and Gorski, J. C., "A New Era in Voice Communications," QST, December 1977.

<sup>2</sup>A frequency compandor compresses signal bandwidth on transmission and expands signal bandwidth on reception.

<sup>3</sup>An amplitude compandor compresses signal amplitude on transmission and expands signal amplitude on reception.

<sup>4</sup>Wilmore, R.M. and Lusignan, B.B., "Spectrum-Efficient Technology for Voice Communication," UHF Task Force Report, Office of Plans and Policy, FCC, Washington, DC, February 1978.

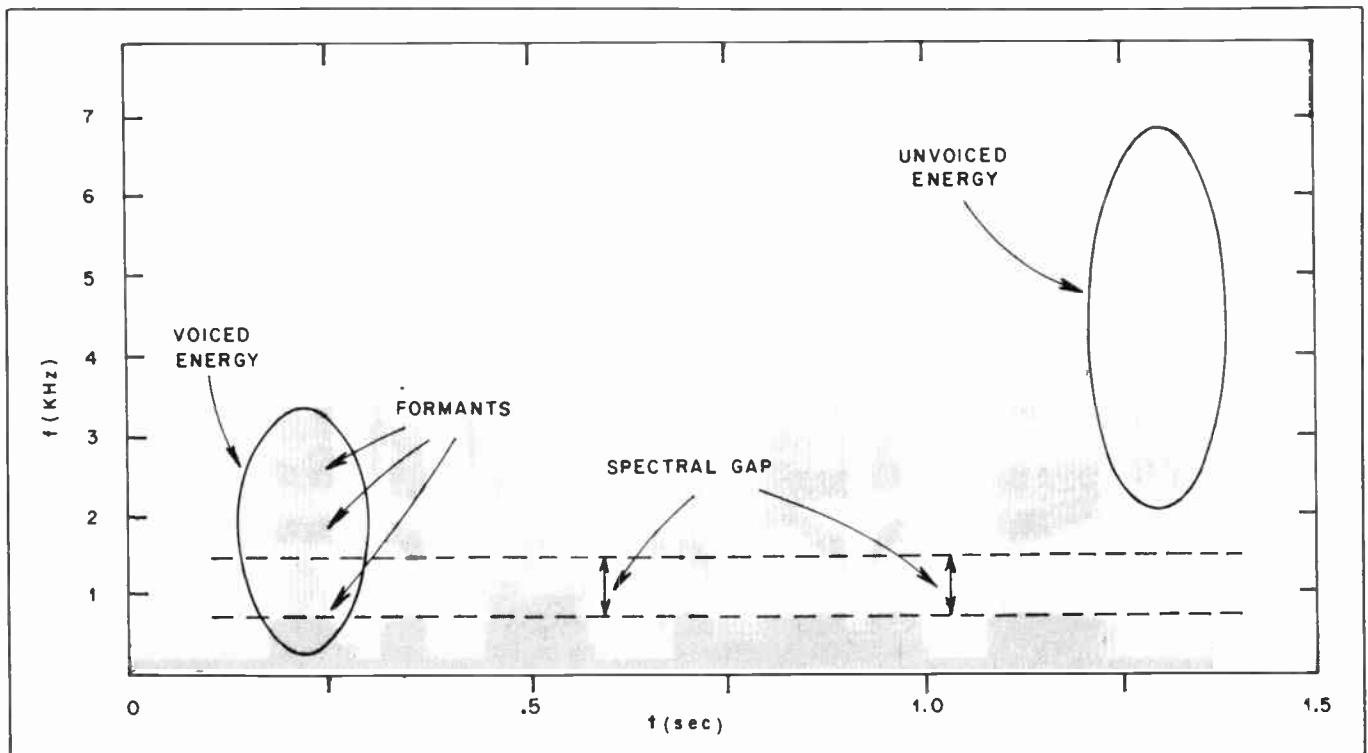


Fig. 1 — A spectrogram or voice print of the utterance "digital communication." The vertical axis represents frequency (80-8000 Hz), and the horizontal axis represents time 0-1.5 sec.)

practical and economical, provides some significant advantages. It compresses the amplitude on transmission, well-known to most amateurs. But significantly, on reception it expands the signal back to its original proportions. As long as the received signal is a few dB above the noise, all of the circuit and channel noise which might corrupt the signal during transmission is greatly reduced.

The FCC tests indicate that the SNR improvement is at least 13 dB and as high as 15 dB in some cases. Addition of the amplitude compandor allows a higher quality voice transmission over the usable communications range of currently designed ssb transceivers; alternatively, future designs may require less transmitter power to achieve the currently available voice quality.

### What Is Speech?

One can better understand how the frequency compandor works by considering the composition of speech. Acoustically, human speech consists predominantly of two types of sounds—voiced and unvoiced.

Voiced sounds originate by passing air from the speaker's lungs through the larynx (voice box), a passage in the human throat with the opening obstructed by vocal cords.<sup>5</sup> As air is passed by these cords, they vibrate, causing puffs of air to escape into the aural cavity, which consists of the throat, nasal cavity and mouth. Studies indicate that the acoustic waveform produced by the vocal cords has many harmonics of the fundamental vibration. Because of the irregular shape of the aural cavity, the spectral-amplitude distribution of the harmonics tends to show peaks at distinct points. As speech is produced, changes occur in the aural cavity shape, thus changing the spectral location of these peaks.

Fig. 1 shows a spectrogram, or voice print, of the utterance "digital communication." The vertical axis represents frequency (80-8000 Hz), and the horizontal axis represents time (0-1.5 s). Darkness of the bands indicates amplitude or voice strength. The fine structure of amplitude peaks that are very close together in the horizontal dimension is a measurement of vocal-cord vibration (fundamental frequency).

Notice the rather strong amplitude concentrations below 4000 Hz. These are the spectral peaks referred to above and are called formants. The first three formants are shown in Fig. 1 at the beginning of the utterance. Proper processing of these three formants is a major concern of bandwidth conservation in speech.

<sup>5</sup>Flanagan, J. L., *Speech Analysis Synthesis and Perception*, 2nd Ed., Springer-Verlag, 1972.

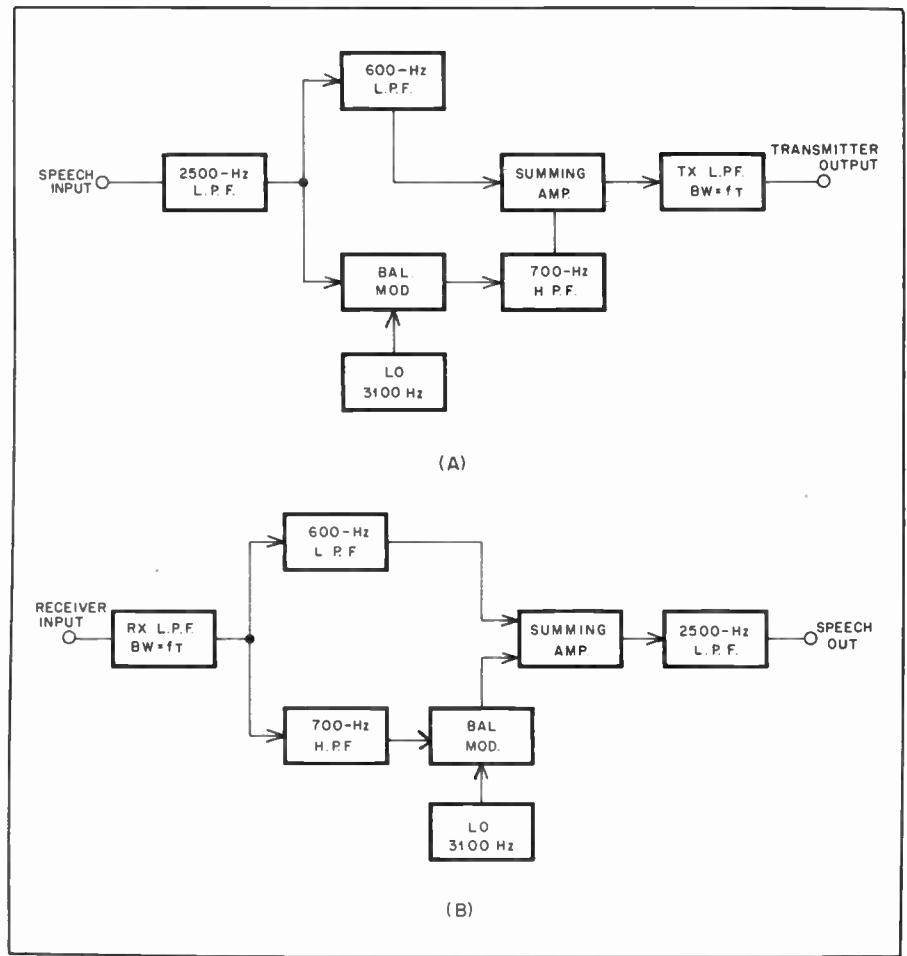


Fig. 2 — Block diagram of the basic frequency compandor scheme. The circuit at A is used to compress the audio bandwidth on transmit. The circuit at B expands this signal for receive.

Unvoiced sounds occur when there is no vocal-track excitation. Sounds such as clicks, hisses and popping are caused by the speaker using his tongue, lips and teeth. These sounds, or evidence of their occurrence by formant extensions into or from a voiced sound, are very important to the intelligibility of speech. Spectral-amplitude distributions of unvoiced sounds are generally above 1500 Hz and are "noise-like," in that very little periodic structure is present (see Fig. 1).

One other important aspect of speech is the pause between acoustic sounds. Juncture pauses carry meaning and cannot be eliminated without impairing intelligibility. Some long pauses can, however, be shortened and thereby reduce message length.

Briefly, speech is the continuous production of voiced and unvoiced sounds, with appropriate pauses to add clarity and distinctness. Measurements performed on voices from different speakers indicate that the first three formants lie predominantly below 2500 Hz. Speech consisting of these three formants is of good quality, both from an intelligibility and "listenability" standpoint. Sufficient information as to the existence of some

unvoiced sounds appears to lie in this range. For example, to produce an "s" sound, the frequency range must extend to approximately 4000 Hz, but this is not usually required for intelligibility since contextual clues provide sufficient evidence for the listener to "hear" an "s."

Evidence from theory and that gained through practice (amateur communications) indicate a bandwidth of 300 to 2500 Hz is adequate for good quality speech. Tests using single, coherent-tone interference indicate a dynamic range of 40 dB is quite adequate for good quality speech. Many communications channels only allow 10-30 dB of SNR so equipment designed to preserve more than 40-dB dynamic range is not warranted.

How can we take advantage of the structure of speech and transmit it more efficiently, and yet preserve the essentials to allow acceptable-sounding speech with high intelligibility? Let us first consider bandwidth conservation and then power. Bandwidth can be conserved at rf and baseband. Rf-bandwidth conservation involves the choice of modulation type such as a-m, fm, ssb or dsb. Amateur users have played a significant role in popularizing ssb which is the most efficient



with respect to bandwidth. Rf modulation types more efficient than ssb are not known. Thus to conserve even greater signal bandwidth it appears that audio-bandwidth reduction prior to rf modulation and transmission is the last possibility.

### Audio Bandwidth Reduction and the Frequency Compandor

The idea of conserving bandwidth at baseband is not new. Many techniques have been used such as vocoders, transform coding, waveform iteration, time sampling, variable-band vocoding, and analytic signal rooting. Two of the more useful of these techniques are vocoders and time sampling. These two systems are explained briefly in November 1978 *QST*.

Bandwidth-efficient techniques investigated by the writers have been only those which are of high quality from a communications standpoint, and can be produced in large quantities with current technology at a reasonable cost. With these constraints in mind a goal of a factor of two in bandwidth reduction was set. Based on past experience with speech processing, another goal was to transmit as much of the available speech as possible without disruption and yet conserve bandwidth. At each stage of investigation voice quality has been carefully considered. The system devised allows flexibility in transmission and reception bandwidth so the quality can be tailored to some extent and yet allow bandwidth reduction of up to a factor of two.

To explain the approach taken, consider the spectrogram in Fig. 1. Notice that there are natural gaps between the first and second, and second and third formants. There is little energy present in these gaps.

After extensive listening tests and consideration of various filtering and mixing combinations it was found that the first formant is not as essential to intelligibility as the second and third. Furthermore, the gap between the first and second formants is wider than between the second and third and it is more constant with time. As a result the system shown in Fig. 2 was developed.

To understand how the system works note that two bands of speech are preserved, the first from dc to 600 Hz, (most communications transceivers limit the low end to 350 Hz) and second from  $f_1$  to 2500 Hz;  $f_1$  corresponds to the low end of the second formant and is variable depending on the transmission and reception low-pass filter (LPF) cutoff frequency  $f_T$ . In equation form

$$f_1 = 3100 - f_T$$

For example, the two filter options provided by the first commercial system will be  $f_T = 1600$  Hz and  $f_T = 2100$  Hz. Both the transmission and reception filters have a 1.3 shape factor. Thus the narrow system with a transmission bandwidth of

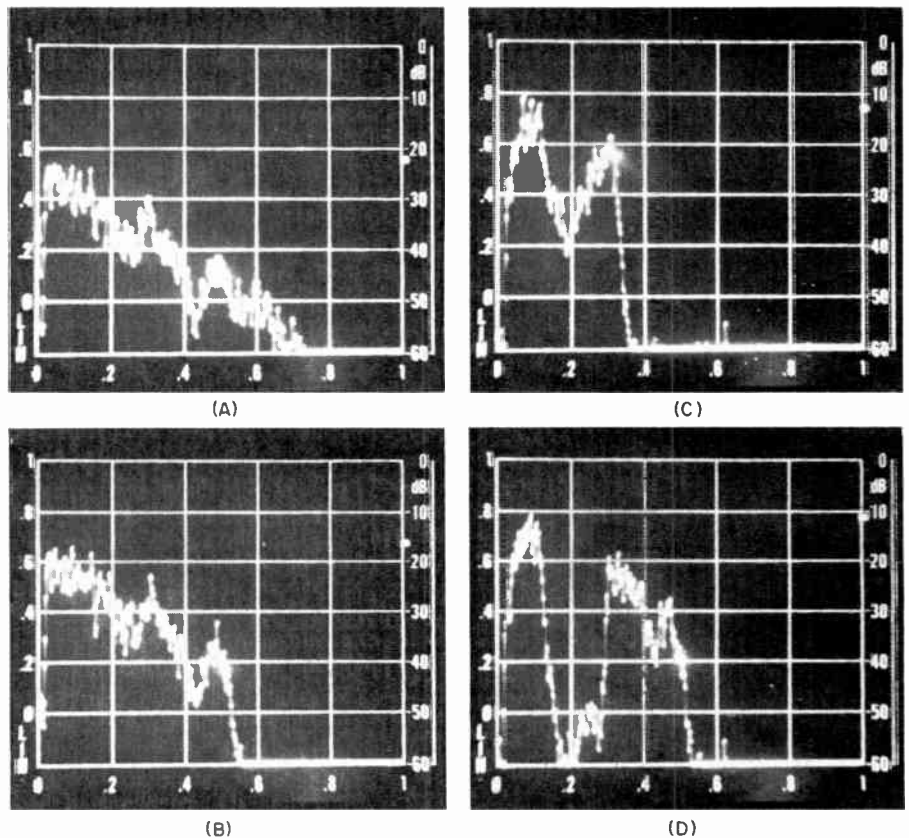


Fig. 3 — In this sequence of photographs the vertical axis represents amplitude at 10 dB/division and the horizontal axis represents frequency at 500 Hz/division. A depicts a long-time, amplitude spectrum of speech. The 2500-Hz LPF at the input to the processor modifies the waveform as shown at B. Final transmitted spectra using the  $f_T = 1600$ -Hz filter is shown at C. The recovered compandor audio output for the 1600-Hz system is depicted at D.

1600 Hz is designed to preserve speech from 350-600 Hz, which is the first formant approximation, and from 1500-2500 Hz, which is the band of contiguous second and third formants. The wider system with a 2100-Hz transmission bandwidth preserves speech from 350-600 Hz as before in the narrower 1600-Hz system, but also preserves the region from 1000-2500 Hz which includes more of the lower end of the second formant.

Operationally, the first formant 350-600 Hz passes essentially straight through the system. The second and third formants are inverted and down converted for transmission, then reinverted and up converted on reception. Use of the 700-Hz high-pass filter (HPF) aids in eliminating potential distortion products due to high frequencies mixed low on transmit and low frequencies mixed high on receive.


The various facets of baseband audio processing are more clearly understood by considering the following sequence of spectra in the system. Fig. 3A shows a long-time, amplitude spectrum of input speech. The amplitude scale (vertical) is calibrated at 10 dB/division and the frequency scale (horizontal) is calibrated at 500 Hz/division in all cases. Note the presence of the first three formants and that speech components above 2500 Hz are 20 to 25 dB lower in amplitude than

those below 2500 Hz. The 2500-Hz LPF at the input to the processor modifies the waveform as shown in Fig. 3B. For communication purposes, the quality of this speech is very good. The goal of the baseband processor is to transmit this speech in a very narrow band and recover it on reception.


Final transmitted spectra using an  $f_T = 1600$  Hz LPF is shown in Fig. 3C. Notice the extremely sharp rolloff above 1600 Hz. This signal has much less chance of interfering with other communicators close by in frequency and allows the use of an identical, very narrow, 1600-Hz LPF to be used on receive. This filter eliminates adjacent channel interference.

The recovered compandor audio output for the 1600-Hz system is shown in Fig. 3D. Notice that the spectrum has been expanded and approximates the shape shown in Fig. 3B. Although a gap does exist in the final-output spectrum, the speech is of high intelligibility, as discussed later, and it has high recognizability.

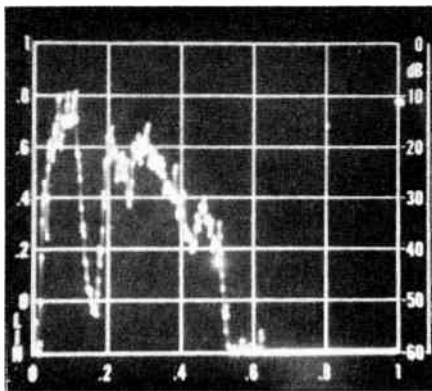If the user desires additional speech features and can tolerate a 500 Hz wider transmission bandwidth, the gap can be narrowed by using the 2100-Hz audio filter in place of the 1600. This expanded output is shown in Fig. 4A. Comparing Fig. 4A with 3D it is obvious that more speech is present in the second formant



(A)

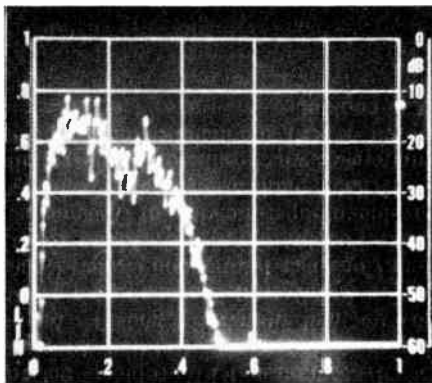

(B)

Fig. 4 — In these photographs the calibration of the display is the same as that in Fig. 3. At A is the recovered audio output for the 2100-Hz compandor system. Shown at B is ordinary speech which is passed through only the final 2100-Hz LPF.

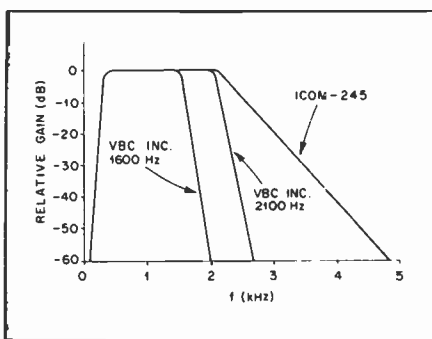


Fig. 5 — Typical response curves for the two compandor LPFs and an amateur transceiver.

region. The question is often asked, "What would happen if we just used only the final transmission LPF and listened to that speech?" A spectral output picture of speech filtered by only the 2100-Hz LPF is shown in Fig. 4B. Notice the absence of the third formant in comparison with Fig. 4A. This formant is essential to clear enunciation of words and is preserved by the 2100-Hz compandor system. Loss of the third formant is, perhaps, the major reason why communicators in the past have not been able to simply continue to

cut the voice spectrum down from the high end.

A comparison of the rolloff characteristics of the 1600- and 2100-Hz final LPF with respect to a typical amateur receiver (ICOM-245) is shown in Fig. 5. It is obvious that both systems (1600 and 2100 Hz) provide extremely sharp audio filtering and are capable of significantly attenuating adjacent-channel interference and nonlinearities not eliminated by the i-f filter. As pointed out in a recent study, audio filtering has significant advantages over i-f filtering for eliminating nonlinearities.

Bandwidth conservation for the two systems can be estimated from Fig. 5 by computing the bandwidth reduction at several points along the rolloff characteristics. Performing these calculations for the 1600-Hz system yields a 50 percent bandwidth savings and for the 2100-Hz system a 33 percent savings. Converting the bandwidth savings to noise-power reduction and computing the increase in SNR yields a 3-dB increase for the 1600-Hz system and a 1.5-dB increase for the 2100-Hz system. Laboratory measurements for the FCC\* using actual speech did verify that a net SNR increase is achieved. However, no extensive on-the-air testing has been performed.

### Amplitude Compandor

Compressing the audio signal prior to modulation to achieve more efficient use of the transmitter power has been widely used by amateurs. However, by compressing only the amplitude peaks, the background noise increases relative to the peaks. A significant advantage can be achieved by expanding the compressed audio at the receiver.

The positive effects of this expansion are illustrated in Fig. 6. A short segment of the speech time waveform is shown in Fig. 6A. When compressed and transmitted this waveform becomes noisy due to the compression and also due to the added circuit and radio channel noise. This is shown in Fig. 6B. Notice the increased noise between the two passages of speech. After the waveform is processed by an amplitude expander (the receiving portion of an amplitude compandor), the waveform appears as shown in Fig. 6C. The noise during the quiet passage has been reduced relative to the high-level passages. Although the SNR during the loud passage is not as good as the input waveform, the SNR of the overall passage is much better than the passage would be if it had not been expanded. Noise during loud passages is not nearly as objectionable as noise between passages of speech.

Using a two-to-one amplitude compandor\* (Signetics NE571N), tests performed for the FCC indicate a measurable 12- to 15-dB improvement with the full

amplitude compandor (compression on transmit and expansion on receive). When only compression was used, significant SNR reduction resulted, even though a higher average transmitter power was being used.

It is important to realize that the amplitude compandor will improve SNR but only when sufficient signal is present for use as a reference. Thus it has a thresholding effect. As long as the received signal is a few dB above the noise, the expander can expand on the basis of the reference to provide a communications channel with a cleaner signal over a wider dynamic range. However, when the signal level drops into the noise, the expander will not operate properly. SNR improvement is limited, but the improvement over the useful range is worthwhile.

If we consider that a certain SNR and corresponding voice quality were required, use of an amplitude compandor would allow the achievement of this goal using less transmitter power. In this respect the amplitude compandor can achieve the same quality SNR with 12-15 dB less transmitted power. This is a significant power savings and can have a definite impact on the quality of communications, per watt of transmitter power.

It is important to note before discussing speech quality measures, that the frequency compandor, unlike the amplitude compandor, does extend communications into the noise because there is no threshold effect inherent in the frequency compandor. Thus, use of both devices will save even more transmitter power and thereby provide more efficient communications.

### What Is Good-Quality Speech?

Whether or not speech is of "good" quality ultimately depends on the user's opinion of the quality available for his specific use of speech communications equipment.

In speech communications perhaps the two most important measures of quality are intelligibility and acceptability. Intelligibility appears to be the most important in radiotelephony since if it is high, the message gets through. A reasonable measure of intelligibility is simply the percentage of correctly received words or phrases. This aspect of speech-communications quality is fairly easy to measure. Extensive statistical tests are available such as the Harvard P-B Word Test, the Fairbanks Rhyme Test, the Modified Rhyme Test, Harvard Test Sentences and

\*A compandor with a compression of 1 dB out for every 2 dB in and an expander with an expansion of 2 dB out for every 1 dB in.



the Diagnostic Rhyme Test. The test which is best suited for a particular application is a matter of opinion of the researchers in the field. Each has its advantages and limitations.

An intelligibility test widely accepted by the military, and perhaps one of the hardest tests to score well on, is the Diagnostic Rhyme Test (DRT) designed by Dr. W. D. Voiers of Dynastat, Inc.<sup>8</sup> By using a team of listeners, statistically significant, repeatable results can be obtained which allow the intelligibility score to be measured. For example, a prototype system which uses approximately 60 percent less transmission bandwidth than normal baseband-communications system scored 90 percent on a male speaker and 87 percent on a female speaker. (Typical long distance telephone conversations score about 93 percent.) An ssb system tested (ICOM-245) scored 95 percent using the same male speaker under ideal conditions. It is interesting to note the military has accepted DRT scores above 85 percent as being adequate from an intelligibility point of view.

Reliable, generally accepted measures of voice acceptability are very hard to obtain. Acceptability, which involves tone quality, speaker recognizability and general measures, is very much a matter of user opinion. Dynastat, Inc. is beginning to establish a data base from which acceptability measures may be available in the future.<sup>9</sup>

To aid in the establishment of a data base as to the acceptability of the system described here a demonstration tape has been prepared.<sup>10</sup> This tape presents male and female speakers in actual communications using ssb with and without baseband processing.

### Radio Communication Uses

The frequency and amplitude compandor baseband system is designed as an add-on baseband package. It will be useful for virtually all modulation types of transceivers including a-m, fm, ssb and dsb. It can be used also as an input to digital communication devices, which, if they have an adjustable sample rate, will save approximately 50 percent in transmitted bandwidth.

Because the system has not been extensively used in actual practice, although preliminary tests are very promising, considerable flexibility has been designed into the baseband system. For example, the user will be able to switch between frequency companding modes (2100-Hz and 1600-Hz bandwidth) and will be able to use the transmit and

receive LPFs as stand-alone audio filters. The amplitude compandor can be used in the expansion only or compression only modes. Combination of the various filters also provide a good band-pass filter for cw use.

### System Options

During the hardware evolution it became apparent that several optional modes of operation could be made available to enhance the overall capability of the baseband system. Through on-the-air tests it has become apparent that a 1600-Hz transmission bandwidth with a shape factor of 1.3 to 1 is a very narrow system indeed. In some cases a wider system in between the narrow 1600-Hz audio and the typical 2400-Hz audio as used in the ICOM-245 and the Kenwood TS-820 would be desirable. Thus, the system developed uses two frequency compandor modes — 1600 Hz (50 percent BW savings) and 2100 Hz (33 percent BW savings).<sup>11</sup> With the 2100-Hz option it becomes obvious that use of a 2100-Hz stand-alone audio filter may be very useful, particularly if the transceiver in use does not already have a very narrow i-f or audio filter.

Use to date has shown the 2100-Hz frequency compandor and stand-alone audio filter modes to be valuable additions. Although the frequency compandor has a very sharp transmission filter which eliminates interference higher in frequency than the desired signal, elimination of undesired signals on the lower side is dependent primarily upon the receiver i-f filter. Some transceivers do not have sufficient opposite-sideband rejection. Use of the 700-Hz HPF within the frequency compandor in conjunction with either the 1600-Hz or 2100-Hz LPFs provides a very narrow band-pass filter (BPF) while allowing reasonable intelligibility (700 Hz to 2100 Hz is preferable) and significantly reducing opposite sideband interference.

Many amateurs compress their audio level on transmission to allow higher average transmitter power, but few amateurs take advantage of audio expansion on reception. As long as the amplitude expander has sufficient signal level to use as a reference, suppression of channel noise and interference significantly improves on the received audio SNR. Independent switches for the amplitude compressors and for the expander seem to be very desirable. This feature has been included in the baseband system and allows the use of the expander as a stand-alone feature on receive to allow expansion of amplitude-compressed signals.

The narrow BPF option (700 Hz to 1600 Hz) offers the user a moderate

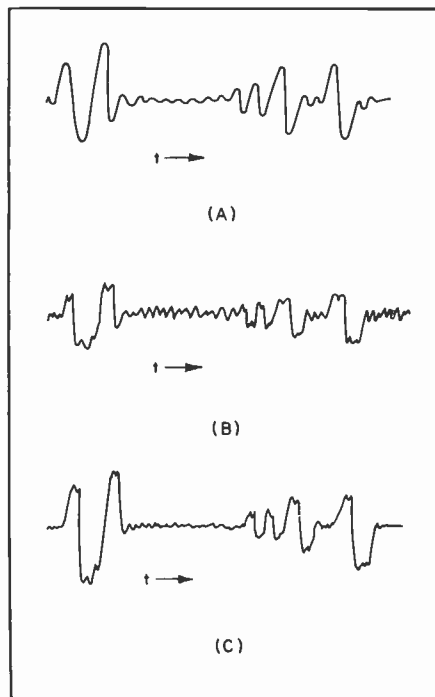


Fig. 6 — Amplitude compandor waveforms are shown above. A is a portion of unmodified speech. B illustrates this same passage of speech after amplitude compression. C illustrates the passage after expansion.

bandwidth with a sharp skirted band-pass response for cw use. Furthermore, preliminary tests using the amplitude expander in conjunction with the BPF indicate that exceptionally quiet cw reception can be achieved. This increased SNR provides fewer decoding errors and less annoyance, particularly for weak-signal cw contacts.

The baseband system developed has evolved over a period of three years. It provides many options for communications improvement so that, depending upon the environment, the user may select several modes for optimizing radio communications.

The baseband system developed uses six high-performance hybrid chips with laser-trimmed 1-percent resistors, very stable, long-life capacitors, and low-noise operational amplifiers. This modular system provides flexibility in interconnections for future improvements. The hybrid chips operate over a wide temperature range (0-70°C), dissipate very little power (the largest being 0.25 watt), occupy very little volume (1.25 cubic inches including all six hybrid chips), and provide excellent reliability.

### Hardware System

A block diagram of the voice processing accessory developed specifically for amateur use is shown in Fig. 7. Five custom hybrid integrated circuits make up the basic frequency-compandor circuitry which includes provision for baseband

<sup>8</sup>Voiers, W. D., *Intelligibility Testing at Dynastat: The Diagnostic Rhyme Test*, Dynastat, Inc., Austin, TX.

<sup>9</sup>Voiers, W. D., *Speech Acceptability Evaluation at Dynastat: The Diagnostic Acceptability Measure (DAM)*, Dynastat, Inc., Austin, TX.

<sup>10</sup>To obtain a demonstration tape send \$5 to VBC Tape Request, P. O. Box 1289, San Mateo, CA, 94401.

<sup>11</sup>Compared to a 2 to 1 shape factor audio filter of 2400 Hz.





transceiver operation and system bypass (provided by sections of S1 and S2). A sixth hybrid IC plus an amplitude compandor and other peripheral circuitry have been added to increase the usefulness and flexibility of the overall device for the amateur under varying operating conditions. Since a considerable amount of audio-signal switching takes place, CMOS analog-switch elements (CD4053) are used wherever possible to minimize signal path lengths and therefore audio crosstalk. Dc control of the switch elements allows a much simpler logic-oriented selection of system functions and helps keep control-panel wiring manageable.

Referring again to the block diagram, the seven sections of S1 provide the transceiver switching and it is shown in the receive mode. S2 allows receive and transmit audio to be connected directly through the system, thus bypassing the frequency compandor for standard voice operation.

In the transmit mode, S1 is in the position *opposite* to that shown in Fig. 7. Low-level audio from the station microphone is fed to a 40-dB gain preamplifier. Output from the preamplifier is summed with high-level audio energy (tape playback as an example), if present, and fed through S1d to the 2500L LPF which limits the input bandwidth to 2500 Hz. The band-limited signal then passes through S1g to the input of the 0600L LPF and also through S1a to the input of the TL442 balanced mixer. The 600-Hz LPF passes the first speech formant to input 2 of summer  $\Sigma 2$ .

The 3100-Hz oscillator is the second input to the TL442 and causes the output of the mixer to contain a double-sideband audio signal with sidebands extending 2500 Hz either side of the suppressed 3100-Hz carrier. This signal passes through S1c to the 0700H HPF which rolls off the audio components below 700 Hz. Output from the 0700H filter passes through S1b to input number 1 of summer  $\Sigma 2$ . The output of the summer contains the original audio up to 600 Hz, the inverted audio from 700 to 3100 Hz, plus the

opposite sideband above 3100 Hz.

One final step remains — that of cutting off this composite signal at an appropriate frequency. The output of summer  $\Sigma 2$  feeds the 1600L and 2100L LPFs through S1e. The 1600L cuts off sharply above 1600 Hz and the 2100L does likewise above 2100 Hz. If the 1600L filter is selected, the complete transmission signal includes the original components of the speech up to 600 Hz and the original components between 1500 and 2500 Hz which are now inverted and transmitted between 600 and 1600 Hz. Operation with the 2100L filter is the same except that original speech components between 1000 and 2500 Hz are inverted and transmitted between 600 and 2100 Hz. Some rolloff does begin on the upper (inverted) segment below 700 Hz due to the 0700H filter.

This signal is fed through S1f and S2a to an output buffer amplifier. Neglecting the amplitude compressor momentarily, the signal is finally fed through S3 to a high-level line output and through a 40-dB pad to the low-level microphone output.

Examination of the diagram will allow the reader to follow the reconstruction sequence from the narrow bandwidth received audio at the transceiver audio output to the speaker. The process is essentially just the reverse of that on transmission. The recovered voice spectrum has a gap in energy between 600 and 1000 Hz or 600 and 1500 Hz depending on which transmission filter is used (1600L or 2100L). As explained previously, this spectral gap occurs in the region where less vital voice energy is present.

Listed in Table 1 are the basic specifications of the frequency compandor portion of the baseband device operating as a stand-alone unit. Note that although the device will respond to 50-Hz signals, moderate voice energy rolloff below 400 Hz (as performed by the radio transceiver) is not only acceptable but highly desirable to achieve a pleasing tone balance in the recovered voice. Thus, the effective audio bandwidth at the input to the transceiver is approximately 350 to

1600 Hz using the 1600L system. Linearity of subsequent rf stages in the transmitter affects the ultimate rf transmission bandwidth.

The basic operation of the Signetics NE570/571 amplitude compandor has been dealt with previously,<sup>12</sup> except that major emphasis was not placed on the primary design purpose of the IC, that of design purpose of the IC, that of amplitude compression and expansion. The NE571 has two identical halves, each of which can serve as an amplitude compressor or expander. The basic transfer function is 2:1, that is, in the compression mode, every 2-dB change in amplitude at the input is compressed to a 1-dB change in amplitude at the output. The expander performs the inverse function. The transfer curve is highly linear in nature except where purposely distorted as discussed below. This feature keeps harmonic distortion products to insignificant levels. The 0-dB gain point in the NE571 is set at 0.775-volt rms input (0 dBm in 600-ohm systems) and its range extends plus 20 and minus 80 dB from that point. A 50-dB dynamic range is deemed adequate for voice communications and is also easily realized with the frequency compandor circuitry. This range is then reduced to approximately 25 dB for transmission and is expanded back to 50 dB at the receiving station. Noise picked up via the transmission path is not compressed, but since it is lower in level than the desired signal, is expanded to an even lower level by the amplitude expander.

The excess dynamic range capability of the NE571 at very low amplitudes is not used in this system. Borrowing from telephone industry practices, the compressor is essentially turned off below a certain input level so that ambient acoustical noise at the microphone is not amplified to an annoying level by the compression process. Another interesting phenomenon occurs with the expander. If the full

<sup>12</sup>Jung, Walter G., "Gain Control IC For Audio Processing." *ham radio*, July 1977, page 47

**Table 1**  
**Frequency Compandor Specifications**

Parameter	Input		Output	
	Transmit	Receive	Transmit	Receive (Recovered Voice)
Cutoff Frequencies (Hz)				
1600 System	50-2500	50-1600	50-1600	50-600 and 1500-2500
2100 System	50-2500	50-2100	50-2100	50-600 and 1000-2500
Stopband Attenuation, min. (dB)				
1600 System		-50 @2000 Hz	-50 @2000 Hz	
2100 System		-50 @2000 Hz	-50 @2650 Hz	
Maximum Voice Levels, (dB)				
(0 dB = .775 vrms)	line in, +10 mic in, -30*	+10	lineout, +10 mic out, -30	line, +10 dB earphone, +10 dB (Zk $\Omega$ load) speaker, 1.5 watts (8 $\Omega$ load)
Signal Port Impedances, ( $\Omega$ )	line, 10 k mic, 50 k	10k	line, 1k mic, 600 line, -35	line, 1k phone, 50 line, -55
Suppression of 3100 Hz carrier, min. (dB)				

\*Mic level set at maximum

**Table 2**  
**Overall System Features**

Mode	Transceive	Transmit Only	Receive Only
Frequency Compandor			
1600 Hz	X		
2100 Hz	X		
Amplitude Compandor			
Compressor	X	X	
Expander	X		X
Receive Filters			
1600 Low Pass (Fig 2)			X
2100 Low Pass (Fig 3)			X
700-2100 Bandpass (Fig 4)			X
700-1600 Bandpass (Fig 5)			X
Straight-Through	X		

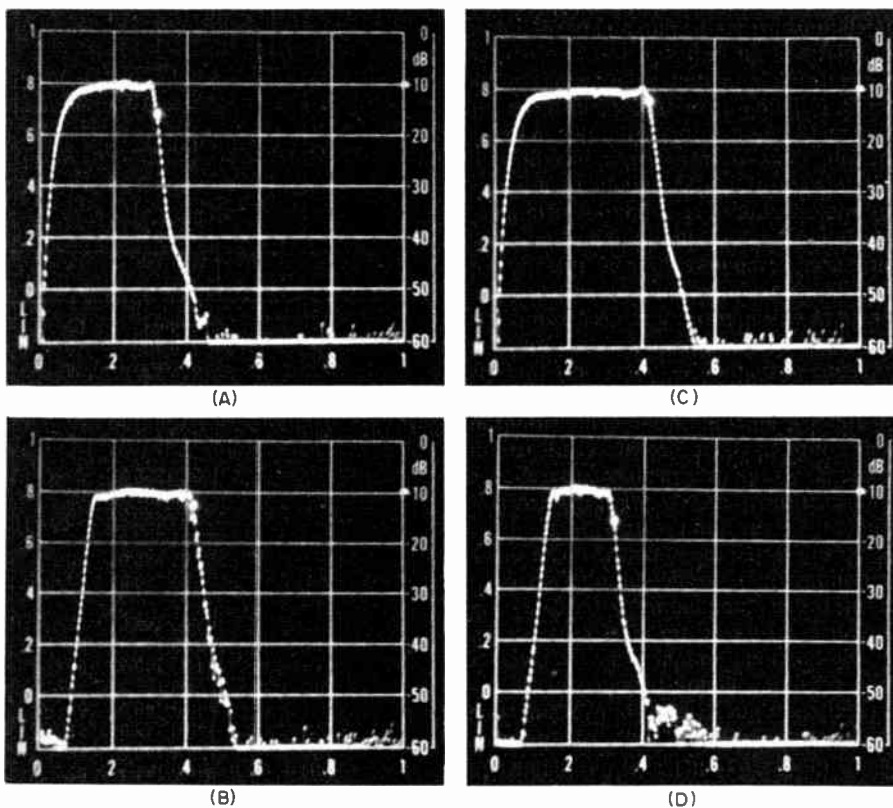


Fig. 8 — Bode plots of the A) 350-1600 Hz frequency compandor response B) 700-2100 Hz band-pass filter C) 350-2100 Hz frequency compandor response and D) 700-1600 band-pass filter

dynamic range is used and the signal input is quite low, the expander decreases this level to the point of inaudibility. In early telephone companding experiments the called party could hear nothing between voice passages and was inclined to prematurely hang up on the caller. So it appears that the expander should cease to expand signals below a certain level input so that a feeling of presence is maintained. This is accomplished by distorting the expander transfer curve so that little or no expansion occurs below a certain input level. The NE571 compandor allows this to be easily accomplished.

The compressor/expander continuously measures the level of the incoming voice

signal in order to develop a gain-control signal to vary the amplification (or attenuation) factor. The level measurement responds at a maximum 100-Hz rate which corresponds to the shortest segment of typical speech at 10 ms duration. Faster response provides less compression advantage and slower response distorts the time relationship of the speech passages. The process depends upon an amplitude modulation envelope to provide SNR improvement, therefore the amplitude compandor is "transparent" to constant amplitude signals or signals which have modulation envelopes greater than 100 Hz. Fortunately, the typical on-off keyed cw modulation envelope

falls within this range and the amplitude expander can provide an SNR advantage in this mode.

As shown in the block diagram, additional switching has been added to allow the use of some of the active filters when the unit is not in the frequency compandor mode. The additional switching is active only in the receive mode; the transmit signal is passed unmodified to the amplitude compressor or output. S7 places the unit in the filters-only mode. S5 selects between the 1600- and 2100-Hz LPFs and S6 allows addition of the 700-Hz HPF for a band-pass characteristic. Control lines are fed to the front panel switches.

Not shown on the block diagram is a voice feed-around switch operated by the keying circuit during frequency compandor VOX operation. Since the frequency compandor is normally in the receive mode except when the operator speaks, the microphone audio is fed directly to the compandor output where the transceiver sensing circuits energize the transmitter. The transmitter key line is fed back to the voice processor transceive control and places the unit into the transmit mode. In actual operation, this occurs so rapidly that the transition is not noticed by either station of the link.

The overall features of the amateur voice-processing accessory are listed in Table 2. Note that the amplitude compressor, amplitude expander, and frequency compandor can all be selected to operate simultaneously or independently. Assuming reception of standard ssb transmissions, the receive-filter options allow suppression of upper or lower adjacent-channel interference with voice degradation increasing with decreasing bandwidth. The 700- to 1600-Hz band-pass combination appears to be very useful in conjunction with the amplitude expander for cw reception. Bode plots of the receive filters taken on a Spectral Dynamics Model SD340 analyzer are shown in Fig. 8A-D. The plots include the typical low end rolloff due to the radio equipment.

The reader may question the existence of high level input and output connections in the system. One obvious use is for easy interface with a tape recorder for recording and playback of radio messages.

### Detailed Hardware Discussion

Four active audio filters are basic to the frequency compandor. All are based on 0.1-dB ripple Chebyshev low-pass prototypes. Increased magnitude ripple could be tolerated to obtain faster cutoff rates than those achieved with these filters; however, another important factor must be considered. It is well known that all filters exhibit delay and this delay is not constant across the passband of a Chebyshev filter. The delay variation (also known as the differential-delay distortion)

across the passband of the filter can be quite large for audio filters as compared to similar filters at radio frequencies. Voice information can only tolerate up to approximately 10-ms delay distortion over its spectrum before garbling begins to occur. Since the voice information must pass through the four filters of the frequency compressor at the transmit end and four more filters at the receive end, each end can have approximately 5-ms total differential-delay distortion. The filters used here each exhibit an average of about 1-ms delay distortion so the total is 4 ms on transmit and 4 ms of receive. Thus the 10-ms maximum is adhered to.

Listed in Table 3 are the typical performance characteristics for five filters used. Note that the 1600L and 2100L are not used simultaneously. The two 16-pole filters each consist of two identical cascaded eight-pole designs to minimize delay distortion. Each two-pole pair of the LPF requires a stage such as shown in Fig. 9.

The advantages of the hybrid implementation of these circuits cannot be overstated. High-order discrete filters can certainly be built, and were built by the authors in early stages of development, but they can be very difficult to tame. Problems which arise with discrete layouts are the unavailability of an infinite variety of resistor values, feedback causing oscillation, inadequate ultimate rejection and excessive noise. Size is also important when one is talking about a total of 26 active filter stages, not to mention the oscillator, mixer and switches.

The hybrid approach allows the total prototype system, minus external control, to be contained on a standard 4-1/2 × 6-inch (114 × 152 mm) plug-in printed circuit card (see Fig. 10). The 16-pole active 50 mm) and the other filters are 1 inch square. Texas Instruments TL074 low-noise, bi-FET quad op amps are used throughout. Since the audio passes through 20 op amps in each direction, low-noise amplifiers are critical. Typical ultimate rejection was improved from 50 dB in the discrete version to 65 dB in the hybrid version. Feedback and oscillation is easily controlled and power supply decoupling is less critical. Dc offsets in the direct coupled stages are minimized by the low input currents of the TL074 op amp.

Laser trimming of the thick-film hybrid resistors assures reliable reproduction of the desired filter characteristics in quantity production. The low temperature coefficients of the thick film resistors and COG dielectric capacitors insure that the filter will remain in specification over a wide temperature range (limited only by the op-amp performance with temperature). All filters have passband gains near 0 dB and can handle +10-dBm input with a total supply voltage of 10. They were designed for so-called single supply

**Table 3.**  
**Active Filters**

Filter	Type	Number of Poles	Cutoff freq. Hz	Shape Factor (-6 to -60 dB)
VBC0600L	Low Pass	6	600	2.50
VBC0700H	High Pass	6	700	2.50
VBC1600L	Low Pass	16	1600	1.29
VBC2100L	Low Pass	16	2100	1.29
VBC2500L	Low Pass	8	2500	1.29

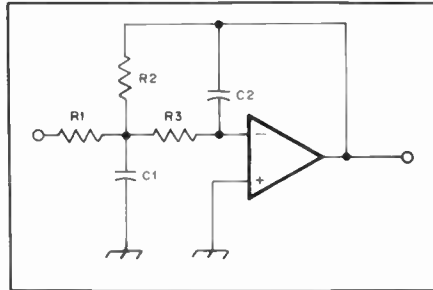


Fig. 9 — This is a basic diagram of one, two-pole, low-pass filter section.

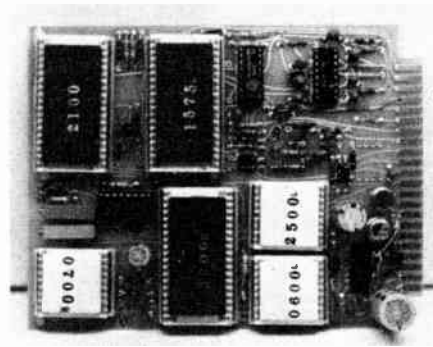


Fig. 10 — Photograph of a completed frequency and amplitude compandor board. Connections to the board are made through the edge connector at the right-hand side of the board.

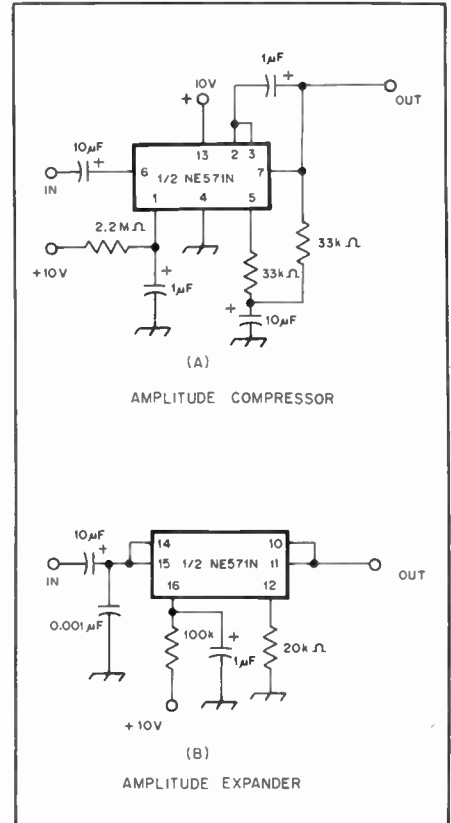


Fig. 11 — Amplitude compressor and expander circuitry.

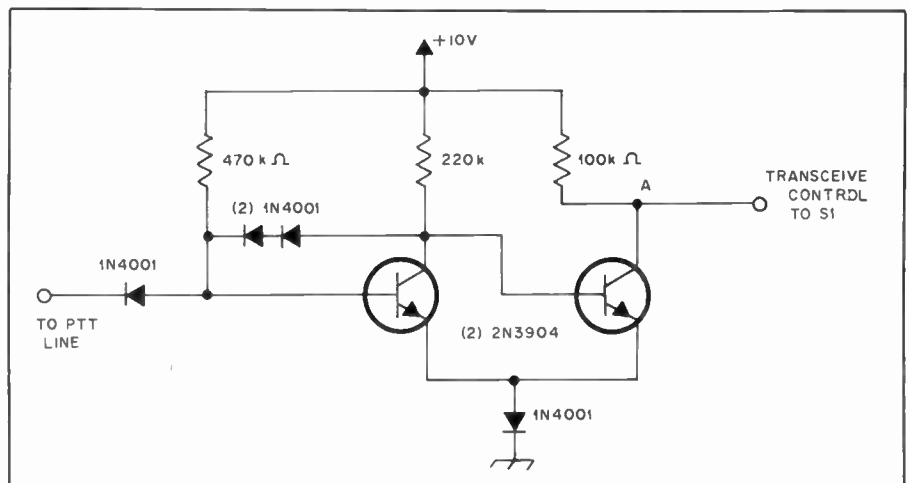


Fig. 12 — Details of the transmit/receive switching system as presented in the text.



operation. Supply voltages used in the processor are regulated +10 and +5 V dc. Supply sources must exhibit very low impedance at audio frequencies.

### Control Circuitry

The control hybrid (VBC3000C) contains the 3100-Hz oscillator, balanced mixer, mic preamplifier, CMOS analog switches and buffer amplifiers for the basic frequency compander. The oscillator uses two op amps and has amplitude limiting to minimize harmonic distortion. Frequency trim and output connections are externally available. The doubly balanced mixer is a Texas Instruments TL442 which operates reasonably well at audio frequencies. Signal input is approximately -20 dBm at the rf port, -10 dBm at the LO port, and output is approximately -20 dBm at the i-f port. Most voice signals throughout the control chip are at -10 dBm to allow plenty of headroom below the +10-dBm saturation limit of the filters. In addition to the filter input and output connections shown in the block diagram, other external connections allow for additional carrier balance, buffer gain and logic-reference adjustment.

The peripheral circuitry includes an extension of the switching capability for receive-only filtering. Spare op amps in the 0600L and 0700H filters are used for the additional buffer amplifiers. An LM380N provides approximately 1 watt of audio output into 8 ohms. The gain of this device is reduced to 10 with negative feedback from the speaker terminal to the inverting input. This reduces positive feedback problems and microphonics inherent with the LM380 when used at its maximum gain of 50.

Shown in Fig. 11 is a schematic of the actual connections to the NE571 amplitude compander. The 100-Hz time constant for the internal rectifier is set with an internal resistor and the external 1- $\mu$ F capacitor. The 2.2-M $\Omega$  resistors provide the transfer curve mistracking at low levels as described earlier. The two 33-k $\Omega$  resistor and capacitor combinations set the dc gain of the internal compressor op amp and the 20-k $\Omega$  resistor biases the expander internal op amp to +5 V dc for maximum signal handling capability.

The total system is powered from a 12.5 to 20 V dc source at 75 mA idle current and approximately 300 mA at 1-watt audio output. All circuitry excluding the LM380 is powered from +10 and +5 V dc regulators (LM340LAH-10 and -5).

One last circuit was devised to provide interface between the radio transmitter key line and the transceiver. Since transmitters of different manufacture use a variety of voltage and impedance key lines, the circuit in Fig. 12 was developed to handle most situations. The circuit looks for a low-impedance ground closure for the transmit mode. If the impedance


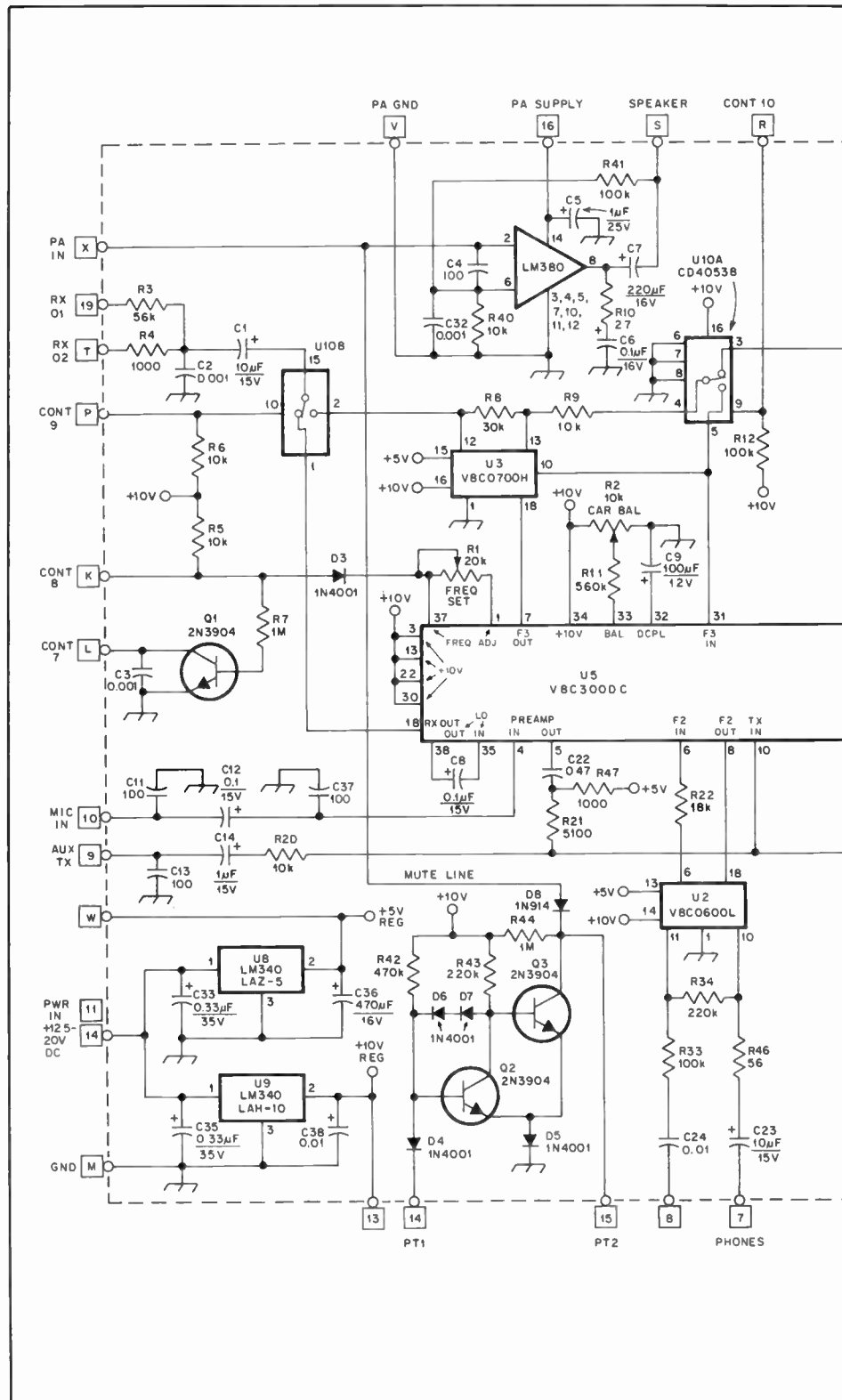


Fig. 13 — The schematic diagram of the compandor system. All numbered circles represent circuit board foils which mate with a standard edge connector.

- C1, C15, C17, C19, C23, C29 — Capacitor, 10  $\mu$ F, 15 volt, electrolytic or tantalum.
- C2, C3, C10, C20, C21, C25, C30, C31, C32 — Capacitor, 0.001  $\mu$ F, 50 volt, disk ceramic.
- C4, C11, C13, C37 — Capacitor, 100 pF, disk ceramic.
- C6, C8, C12 — Capacitor, 0.1  $\mu$ F, 15 volt, tantalum.
- C7 — Capacitor, 220  $\mu$ F, 16 volt, electrolytic.
- C9 — Capacitor, 100  $\mu$ F, 15 volt, electrolytic.
- C14, C16, C18, C28 — Capacitor, 1  $\mu$ F, 15 volt, tantalum.
- C22 — Capacitor, 0.47  $\mu$ F, nonpolarized, ceramic.
- C24, C38, C40 — Capacitor, 0.01  $\mu$ F, 50 volt, ceramic.
- C27 — Capacitor, 0.047  $\mu$ F, 15 volt, nonpolarized.
- C33, C35 — Capacitor, 0.33  $\mu$ F, 35 volt, tantalum.
- C36 — Capacitor, 470  $\mu$ F, 16 volt, electrolytic.
- C39 — Capacitor, 22  $\mu$ F, 15 volt, tantalum.
- C41 — Capacitor, 1000  $\mu$ F, 25 volt, electrolytic.

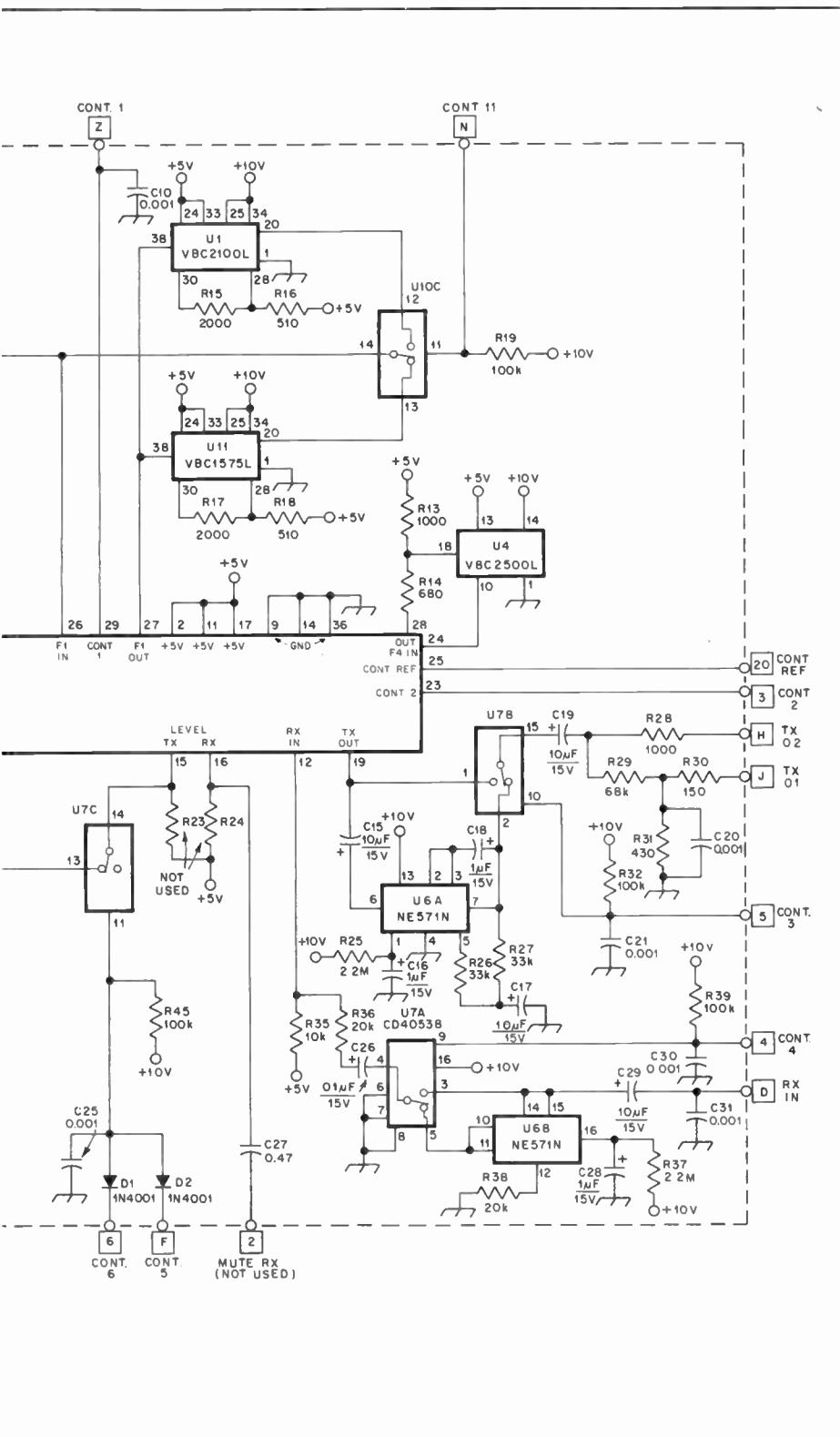



- D1-D8, incl. — Diode, 1N4001.
- D9 — LED
- J1 — Edge connector, 22 pin, 44 contact.
- J2-J12, incl. — Builder's choice.
- Q1-Q3, incl. — Switching transistor, 2N3904.
- R48 — Potentiometer, 50 k $\Omega$ .
- R49 — Potentiometer, 25 k $\Omega$ .
- S1 — Toggle switch, dpdt.
- S2-S5, incl. — Toggle switch, spdt.
- S6 — Toggle switch, spst.
- U1 — Hybrid circuit, VBC2100L.

- U2 — Hybrid circuit, VBC0600L.
- U3 — Hybrid circuit, VBC0700H.
- U4 — Hybrid circuit, VBC2500L.
- U5 — Hybrid circuit, VBC3000C.
- U6 — IC, Signetics NE571N.
- U7, U10 — IC, CD4053B.
- U8 — Voltage regulator, LM340LAH-5.
- U9 — Voltage regulator, LM340LAH-10.
- U11 — Hybrid circuit, VBC1575L.
- U12 — Audio amplifier, LM380.



Fig. 14 — Front-panel view of a prototype compandor system. As outlined in the text, considerable flexibility has been designed into the system. Various modes of operation can be selected at a flip of the switch.


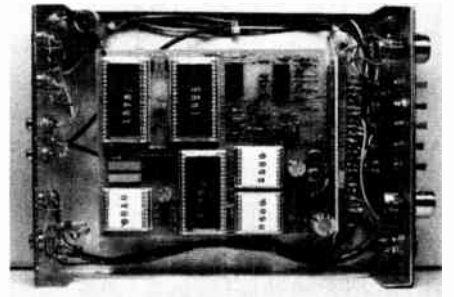


Fig. 15 — Interior view of the compandor system prototype. As can be seen, an edge connector is used for connection to the circuit board to facilitate easy removal.

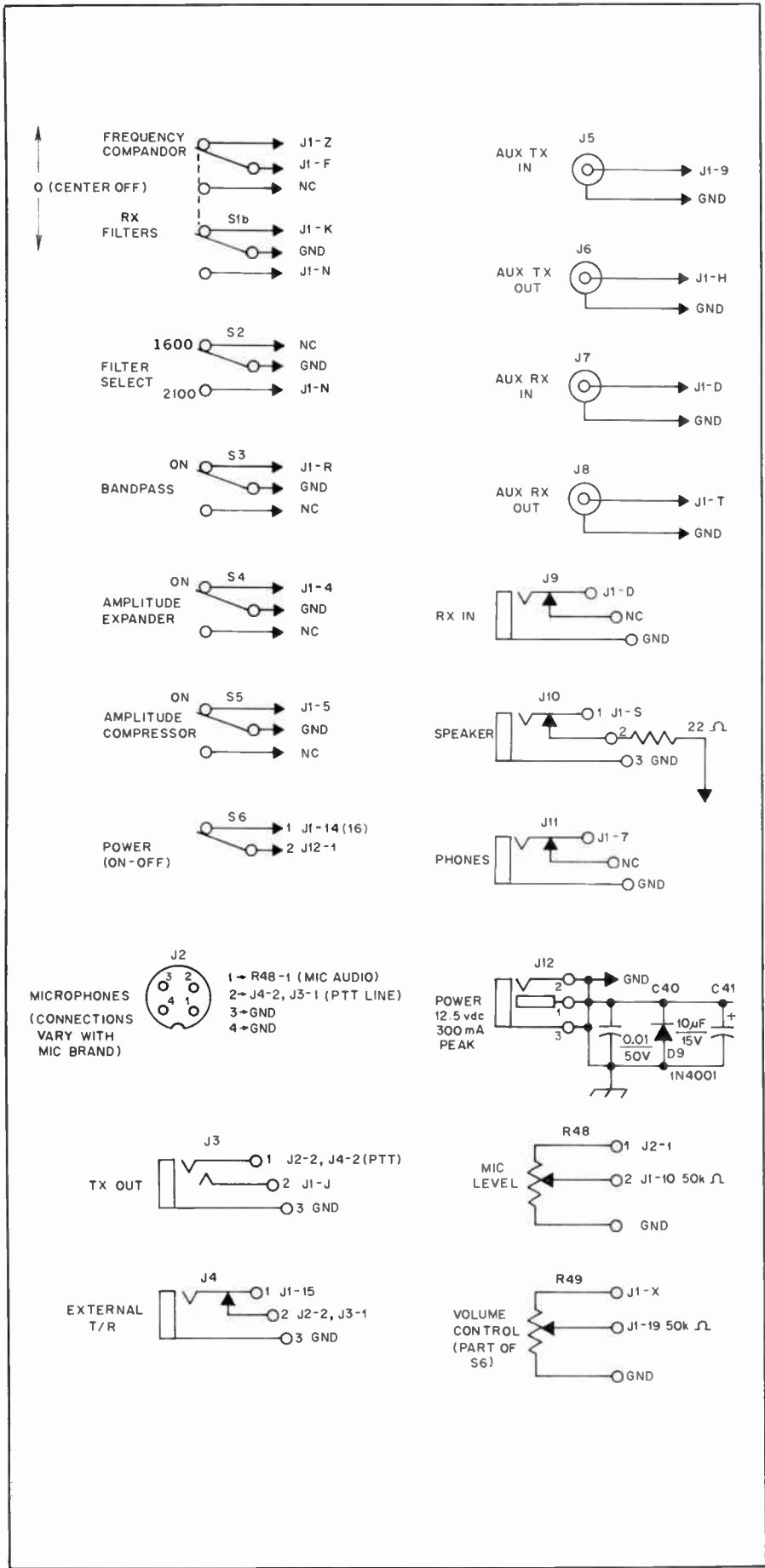

Fig. 16 — Here is a photograph of the rear panel of the processor. Layout is not particularly critical, but leads should be kept as short as possible. The use of a completely shielded enclosure is mandatory.

becomes very high or the voltage exceeds  $\pm 0.5$  volts from ground, the unit returns to the receive mode. This allows positive or negative key-up voltages and assumes a grounded line during transmit. There is no load on positive key lines and an approximate 100-k $\Omega$  load on negative key lines. Key line voltages must remain within the reverse breakdown voltage of the diode-transistor combination (ap-



proximately 60 volts as shown here).

**Construction and Operation**

Layout of the printed circuit board is tricky at best. Ground loops are hard to avoid and can make the unit sound akin to a squawking chicken. Keeping the local oscillator signal out of where it doesn't belong is most difficult since it is a coherent tone and is audible at levels lower than normal voice sounds. Additional power-supply decoupling of the oscillator stages is helpful. Rf-bypass capacitors are used liberally on the audio input and output lines. The unit must be mounted in a well-shielded enclosure since stray rf currents entering any of the audio circuitry can cause gravelly sounding audio or even blocking.

The schematic diagram of the voice processor is shown in Fig. 12. An etched circuit board with all necessary parts to complete a basic processor board is available commercially.<sup>13</sup> Shown in Figs. 13-15 is a prototype unit including control switches, microphone input connector, level control, and receive volume/on-off switch. The rear panel houses phono and phone jacks for the various other input and output connections. Power is provided by an external dc power pack such as those used for calculator recharging. A 13-volt automobile system is also suitable.

Interface with a radio transceiver is quite simple. The unit is connected in the line permanently since its function can be bypassed if desired. The station microphone is connected to the front-panel microphone jack. The push-to-talk line is routed directly to the transceiver microphone jack (and is tapped by the audio processor control circuit). A shielded cable is installed between the processor microphone and PTT terminals and the equivalent transceiver connections. The receive audio is taken from the transceiver speaker or earphone output (after the transceiver volume control) and connected to the receive input on the voice processor. A speaker or earphone is connected to the appropriate audio output jack. In operation, the processor volume control is preset to a desirable listening level. The receiver af-gain control is adjusted to keep the input level to the voice processor fairly constant with varying signal strengths. If the station receiver has very good agc characteristics, volume adjustments will be minimal. If not, the af-gain control will need periodic adjustment to keep strong signals from overdriving the amplitude expander, since a 1-dB increase in level at the input is expanded to a 2-dB increase at the output.

**Amateur Participation**

Although tests to date have been successful, many more tests are desired on

<sup>13</sup>Contact Ham Radio Outlet at the following locations for details: 2620 W. LaPalma, Anaheim, CA 92801; 990 Howard Ave., Burlingame, CA 94010; 5375 Kearny Villa Rd., San Diego, CA 92123 and 13754 Victory Blvd., Van Nuys, CA 91401.

Fig. 17 — Details of how the circuit board connects with control and input/output lines.

other bands by a large number of amateurs under varying conditions. Only then will a sufficient data base be established as to the full usefulness of the baseband system and provide guidance for future improvements.

As currently designed, the baseband internal local oscillator is fixed at 3100 Hz. This choice was made to allow use of a wide range of transmission and reception filters with cutoff frequencies between 1500 and 2500 Hz. Hardware for amateur use now provides filters of 1600 Hz and 2100 Hz. VBC, Inc. is also producing an 1850-Hz filter for mobile radio bands, which can be obtained as an option for amateur use. Amateurs are an inventive group of communicators, with a desire to find practical and useful communications features. Many amateurs may wish to experiment by using their own transmission and reception filter designs. It is suggested that amateurs be heavily involved in the evolution of the system. Results of their experimental work will prove very valuable for future efforts in bandwidth and power conservation.

Important to amateur users, will be the potential use of the narrow-band technology in vhf and uhf amateur bands. In these bands a channelized format similar to that of mobile bands is used.

The combination of these newly developed baseband technologies in several bands is expected to continue to evolve for many years to come. The ultimate goal is a better and larger number of communications opportunities for all users.

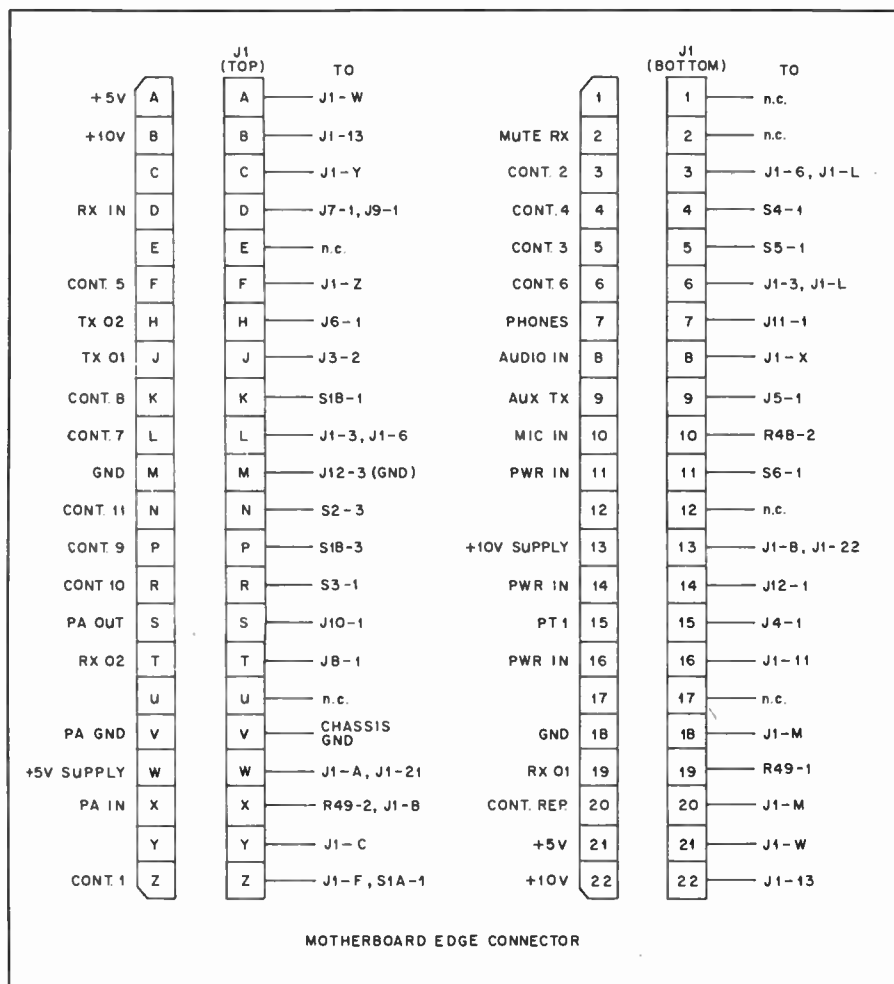


Fig. 18 — Edge connector information. Use in conjunction with Fig. 17.

# Interference with other Services

**R**adio Frequency Interference (RFI) has probably been with us since the first amateur stations came on the air some 70 years ago. Fed by the technology that developed during and following WW II, the problem has become an increasing source of irritation between radio operators and their neighbors. Home-entertainment electronics devices now abound, with most families owning at least one television receiver, an a-m or fm radio, and any one of several audio devices (such as a phonograph, an intercom, an electronic guitar, or an electronic organ). Given the innate perversity of these objects to intercept radio signals, it should surprise no one to learn that RFI is one of the most difficult problems amateurs face in their day-to-day operations.

### How Serious is the RFI Problem?

In 1978, the FCC received 150,000 RFI complaints, up more than 200 percent from the number of complaints received in 1970. Of these, the great majority involved interference to home-entertainment equipment. Most important, nearly all of these would never have come to the Commission's attention if the manufacturers had corrected design deficiencies in their home-entertainment products at the time of manufacture. It is of interest to note that more than 60 percent of the interference cases reported were related to television interference (TVI).

In the case of television interference, FCC experience shows that 90 percent of the problems experienced can only be cured at the television receiver. Further, when it comes to audio equipment, the *only* cure for RFI is to treat the audio device experiencing the interference. There is nothing an amateur can do to his transmitter which will stop a neighbor's phonograph from acting as a short-wave receiver. It should be emphasized that phonographs and hi-fi units are not designed to be receivers, but simply audio devices.

It is clear, therefore, that almost all RFI problems experienced with home-entertainment devices result from basic design deficiencies in this equipment. The few small components or filters which would prevent RFI are often left out of otherwise well-designed products as manufacturers attempt to reduce costs, and hence, to reduce the prices of their products.

### The Solution — Consumer Protection

Given the present unacceptable situation, what can we as amateurs do to help the consumer resolve the RFI problem? One step which should certainly be taken is to advise our friends and neighbors to inquire, before they make a purchase of an electronic device, whether the product has been certified for operation in the presence of a radio transmitter. Manufacturers must be made to recognize that RFI protection of their home-entertainment equipment has become essential. Further, where interference is being experienced, the consumer should be encouraged to contact the manufacturer of his equipment and to request that the *manufacturer* furnish the components or services necessary to eliminate RFI.

### What Are Manufacturers Doing Today?

Many responsible manufacturers have a policy of supplying filters for eliminating television interference when such cases are brought to their attention. A list of those manufacturers, and a more thorough treatment of the RFI problem, can be obtained by writing the ARRL. If a given manufacturer is not listed, it is still possible that he can be persuaded to supply a filter; this can be determined by writing either directly to him or to the Electronic Industries Association (EIA).<sup>1</sup>

With respect to audio devices, some manufacturers will supply modified sche-

matic diagrams showing the recommended placement of bypass capacitors and other components to reduce rf susceptibility. One large American manufacturer of hi-fi equipment has in some cases supplied the necessary components free of charge, although no consistent policy has been evident and the consumer must still pay to have a serviceman install the components.

While these are encouraging developments, it appears likely that meaningful and widespread corrective action by equipment designers will require both pressure from consumers and establishment of suitable government standards.

Voluntary after-the-fact measures on the part of manufacturers simply are not enough. It is a foregone conclusion that as long as the inclusion of additional components for susceptibility reduction increases a manufacturer's cost, however slightly, there will be reluctance to take steps to improve equipment designs by the manufacturers themselves. What appears to be necessary, therefore, is federal legislation giving the FCC the authority to regulate the manufacture of home-entertainment devices and thus protect the consumer.

### It's Up to Us

If requests to manufacturers of home-entertainment equipment for those components and installation services necessary to relieve RFI problems are to be successful, each of us, when faced with an RFI problem, must make known our position to the manufacturers involved. While a respectful request for assistance will bring more cooperation than a blunt demand, do not hesitate to let the manufacturers know that they have a responsibility to the consumer for correcting the design deficiencies that are causing the problem. Before casting the first stone, however, make sure you're not sitting in a glass house. Certainly, if your own television receiver experiences no interference while you are on the air, it is

<sup>1</sup>Electronic Industries Association, 2001 Eye Street, N.W., Washington, DC 20006. Attention: Director of Consumer Affairs.



most likely that interference to a more distant television receiver is not the fault of your transmitter.

All of the above is not to say, however, that we should not continue to assist in resolving RFI problems. Radio amateurs have typically sought to assist their neighbors in correcting RFI problems, even where those problems were in no way attributable to the performance of the transmitter. Ultimately, of course, it is the manufacturers' responsibility to correct those deficiencies which lead to the interception of radio signals. But in the interest of good neighborhood relations, we must continue to provide this assistance wherever older equipment designs are in use.

### Clean House First

In approaching an RFI problem, the first step obviously is to make sure that the transmitter has no radiations outside the bands assigned for amateur use. The best check on this is your own a-m or TV receiver. It is always convincing if you can demonstrate that you do not interfere with reception in your own home.

### Don't Hide Your Identity

Whenever you make equipment changes — or shift to a hitherto unused band or type of emission — that might be expected to change the interference situation, check with your neighbors. If no one is experiencing interference, so much the better; it does no harm to keep the neighborhood aware of the fact that you are operating without bothering anyone.

Should you change location, make your presence known and conduct occasional tests on the air, requesting anyone whose reception is being spoiled to let you know about it so steps may be taken to eliminate the trouble.

### Act Promptly

The average person will tolerate a limited amount of interference, but the sooner you take steps to eliminate it, the more agreeable the listener will be; the longer he has to wait for you, the less willing he will be to cooperate.

### Present Your Story Tactfully

Whenever a device intercepts your signals, it is natural for the complainant to assume that your transmitter is at fault. If you are certain that the trouble is not in your transmitter, explain to the listener that the reason lies in the receiver design, and that some modifications may have to be made in the receiver if he is to expect interference-free reception.

### Arrange for Tests

Most listeners are not very competent observers of the various aspects of interference. If at all possible, enlist the help of another amateur and have him operate your transmitter while you see for

yourself what happens at the affected receiver.

### In General

In this "public relations" phase of the problem a great deal depends on your own attitude. Most people will be willing to meet you half way, particularly when the interference is not of long standing, if you as a person make a good impression. Your personal appearance is important. So is what you say about the receiver — no one takes kindly to hearing his possessions derided. If you discuss your interference problems on the air, do it in a constructive way — one calculated to increase listener cooperation, not destroy it.

### VHF Television

For the amateur who does most of his transmitting on frequencies below 30 MHz, the TV band of principal interest is the low vhf band between 54 and 88 MHz. If harmonic radiation can be reduced to the point where no interference is caused to channels 2 to 6, inclusive, it is almost certain that any harmonic troubles with channels above 174 MHz will disappear also.

The relationship between the vhf television channels and harmonics of amateur bands from 14 through 28 MHz is shown in Fig. 1. Harmonics of the 7- and 3.5-MHz bands are not shown because they fall in every television channel. However, the harmonics above 54 MHz from these bands are of such high order that they are usually rather low in amplitude, although they may be strong enough to interfere if the television receiver is quite close to the amateur transmitter. Low-order harmonics — up to about the sixth — are usually the most difficult to eliminate.

Of the amateur vhf bands, only 50 MHz will have harmonics falling in a vhf television channel (channels 11, 12 and 13). However, a transmitter for any amateur vhf band may cause interference if it has multiplier stages either operating in or having harmonics in one or more of the vhf TV channels. The rf energy on such frequencies can be radiated directly from the transmitting circuits or coupled by stray means to the transmitting antenna.

### Frequency Effects

The degree to which transmitter harmonics or other undesired radiation actually in the TV channel must be suppressed depends principally on two factors: The strength of the TV signal on the channel or channels affected, and the relationship between the frequency of the spurious radiation and the frequencies of the TV picture and sound carriers within the channel. If the TV signal is very strong, interference can be eliminated by comparatively simple methods. However, if the TV signal is very weak, as in

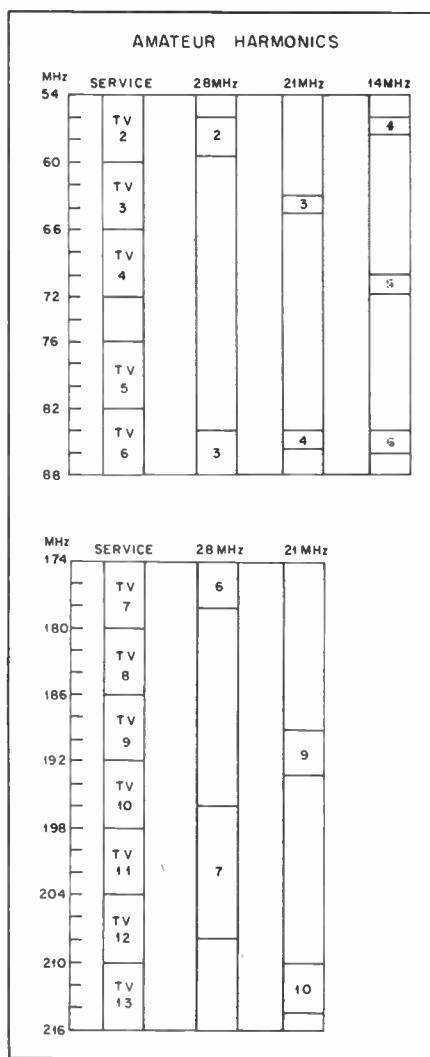


Fig. 1 — Relationship of amateur-band harmonics to vhf TV channels. Harmonic interference from transmitters operating below 30 MHz is likely to be serious in the low-channel group (54 to 88 MHz).

"fringe" areas where the received picture is visibly degraded by the appearance of set noise or "snow" on the screen, it may be necessary to go to extreme measures.

In either case the intensity of the interference depends very greatly on the exact frequency of the interfering signal. Fig. 2 shows the placement of the picture and sound carriers in the standard TV channel. In channel 2, for example, the picture carrier frequency is  $54 + 1.25 = 55.25$  MHz and the sound carrier frequency is  $60 - 0.25 = 59.75$  MHz. The second harmonic of 28,010 kHz (56,020 kHz or 56.02 MHz) falls  $56.02 - 54 = 2.02$  MHz above the low edge of the channel and is in the region marked "severe" in Fig. 2. On the other hand, the second harmonic of 29,500 kHz (59,000 kHz or 59 MHz) is  $59 - 54 = 5$  MHz from the low edge of the channel and falls in the region marked "mild." Interference at this frequency has to be about 100 times as strong as the 56,020 kHz to cause effects of equal intensity. Thus an operating

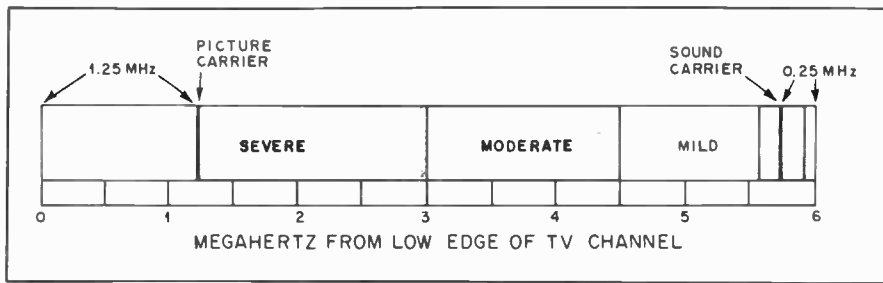


Fig. 2 — Location of picture and sound carriers in a monochrome television channel, showing the relative intensity of interference as the location of the interfering signal within the channel is varied without changing its strength. The three regions are not actually sharply defined as shown in this drawing, but merge into one another gradually.

frequency that puts a harmonic near the picture carrier requires about 40 dB more harmonic suppression in order to avoid interference, as compared with an operating frequency that puts the harmonic near the upper edge of the channel.

For a region of 100 kHz or so either side of the sound carrier there is another "severe" region where a spurious radiation will interfere with reception of the sound program and this region also should be avoided. In general, a signal of intensity equal to that of the picture carrier will not cause noticeable interference if its frequency is in the "mild" region shown in Fig. 2, but the same intensity in the "severe" region will utterly destroy the picture.

### Interference Patterns

The visible effects of interference vary with the type and intensity of the interference. Complete "blackout," where the picture and sound disappear completely, leaving the screen dark, occurs only when the transmitter and receiver are quite close together. Strong interference ordinarily causes the picture to be broken up, leaving a jumble of light and dark lines, or turns the picture "negative" — the normally white parts of the picture turn black and the normally black parts turn white. "Cross-hatching" — diagonal bars or lines in the picture — accompanies the latter, usually, and also represents the most common type of less severe interference. The bars are the result of the beat between the harmonic frequency and the picture carrier frequency. They are broad and relatively few in number if the beat frequency is comparatively low — near the picture carrier — and are numerous and very fine if the beat frequency is very high — toward the upper end of the channel. Typical cross-hatching is shown in Fig. 3. If the frequency falls in the mild region in Fig. 2, the cross-hatching may be so fine as to be visible only on close inspection of the picture, in which case it may simply cause the apparent brightness of the screen to change when the transmitter carrier is thrown on and off.

Whether or not cross-hatching is visible, an amplitude-modulated transmitter may cause "sound bars" in the picture. These

look about as shown in Fig. 4. They result from the variations in the intensity of the interfering signal when modulated. Under most circumstances modulation bars will not occur if the amateur transmitter is frequency- or phase-modulated. With these types of modulation the cross-hatching will "wiggle" from side to side with the modulation.

Except in the more severe cases, there is seldom any effect on the sound reception when interference shows in the picture, unless the frequency is quite close to the sound carrier. In the latter event the sound may be interfered with even though the picture is clean.

Reference to Fig. 1 will show whether or not harmonics of the frequency in use will fall in any television channels that can be received in the locality. It should be kept in mind that not only harmonics of the final frequency may interfere, but also harmonics of any frequencies that may be present in buffer or frequency-multiplier stages. In the case of 144-MHz transmitters, frequency-multiplying combinations that require a doubler or tripler stage to operate on a frequency actually in a low-band vhf channel in use in the locality should be avoided.

### Harmonic Suppression

Effective harmonic suppression has three separate phases:

- 1) Reducing the amplitude of harmonics generated in the transmitter. This is a matter of circuit design and operating conditions.
- 2) Preventing stray radiation from the transmitter and associated wiring. This requires adequate shielding and filtering of all circuits and leads from which radiation can take place.
- 3) Preventing harmonics from being fed into the antenna.

It is impossible to build a transmitter that will not generate *some* harmonics, but it is obviously advantageous to reduce their strength, through circuit design and choice of operating conditions, by as large a factor as possible before attempting to prevent them from being radiated. Harmonic radiation from the transmitter itself or from its associated wiring obviously will cause interference just as readily as



Fig. 3 — "Cross-hatching," caused by the beat between the picture carrier and an interfering signal inside the TV channel.

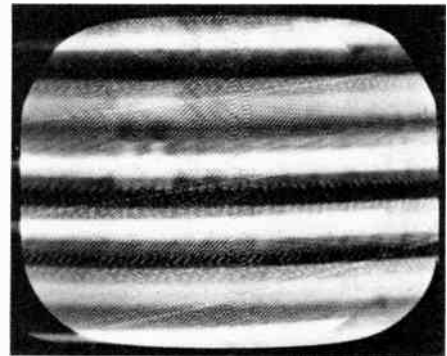


Fig. 4 — "Sound bars" or "modulation bars" accompanying amplitude modulation of an interfering signal. In this case the interfering carrier is strong enough to destroy the picture, but in mild cases the picture is visible through the horizontal bars. Sound bars may accompany modulation even though the unmodulated carrier gives no visible cross-hatching.

radiation from the antenna, so measures taken to prevent harmonics from reaching the antenna will not reduce TVI if the transmitter itself is radiating harmonics. But once it has been found that the transmitter itself is free from harmonic radiation, devices for preventing harmonics from reaching the antenna can be expected to produce results.

### Reducing Harmonic Generation

Since reasonably efficient operation of rf power amplifiers always is accompanied by harmonic generation, good judgment calls for operating all frequency-multiplier stages at a very low power level. When the final output frequency is reached, it is desirable to use as few stages as possible in building up to the final output power level and to use tubes that require a minimum of driving power.

### Circuit Design and Layout

Harmonic currents of considerable amplitude flow in both the grid and plate circuits of rf power amplifiers, but they will do relatively little harm if they can be effectively bypassed to the tube cathode. Fig. 5 shows the paths followed by harmonic currents in an amplifier circuit;

because of the high reactance of the tank coil there is little harmonic current in it, so the harmonic currents simply flow through the tank capacitor, the plate (or grid) blocking capacitor, and the tube capacitances. The lengths of the leads forming these paths is of great importance, since the inductance in this circuit will resonate with the tube capacitance at some frequency in the vhf range (the tank and blocking capacitances usually are so large compared with the tube capacitance that they have little effect on the resonant frequency). If such a resonance happens to occur at or near the same frequency as one of the transmitter harmonics, the effect is just the same as though a harmonic tank circuit had been delib-

erately introduced; the harmonic at that frequency will be tremendously increased in amplitude.

Such resonances are unavoidable, but by keeping the path from plate to cathode and from grid to cathode as short as is physically possible, the resonant frequency usually can be raised above 100 MHz in amplifiers of medium power. This puts it between the two groups of television channels.

It is easier to place grid-circuit vhf resonances where they will do no harm when the amplifier is link-coupled to the driver stage, since this generally permits shorter leads and more favorable conditions for bypassing the harmonics than is the case with capacitive coupling. Link coupling also reduces the coupling between the driver and amplifier at harmonic frequencies, thus preventing driver harmonics from being amplified.

The inductance of leads from the tube to the tank capacitor can be reduced not only by shortening but by using flat strip instead of wire conductors. It is also better to use the chassis as the return from the blocking capacitor or tuned circuit to cathode, since a chassis path will have less inductance than almost any other form of connection.

The vhf resonance points in amplifier tank circuits can be found by coupling a grid-dip meter covering the 50-250 MHz range to the grid and plate leads. If a resonance is found in or near a TV channel, methods such as those described above should be used to move it well out of the TV range. The grid-dip meter also should be used to check for vhf resonances in the tank coils, because coils made for 14 MHz and below usually will show such resonances. In making the check, disconnect the coil entirely from the transmitter and move the grid-dip meter coil along it while exploring for a dip in the 54- to 88-MHz band. If a resonance falls in a TV channel that is in use in the locality, changing the number of turns will move it to a less-troublesome frequency.

conditions, there is little or no difference between single-ended and push-pull amplifiers in respect to harmonic generation. Push-pull amplifiers are frequently trouble-makers on even-order harmonics because with such amplifiers the even-harmonic voltages are in phase at the ends of the tank circuit and hence appear with equal amplitude across the whole tank coil if the center of the coil is not grounded. Under such circumstances the even harmonics can be coupled to the output circuit through stray capacitance between the tank and coupling coils. This does not occur in a single-ended amplifier having an inductively coupled tank if the coupling coil is placed at the cold end or with a pi-network tank.

### Some TVI Tests

One of the difficulties in solving TVI problems, particularly in fringe areas, is the number of possible causes and their elusive nature. A "cure" seems to be found only to have the problem return with renewed severity the next day. Consequently, some tests were performed by the ARRL in order to isolate the causes, if possible. Although the results weren't encouraging in regard to certain aspects, one bright spot was some "fall-out" in the way of additional suppression measures previously neglected.

### Test Procedures

A ham experiencing some TVI in a fringe area (on his own set) generously agreed to be the "patient" in the tests. A large screened enclosure was transported to his location. It could contain the TV set along with a smaller version of the screen enclosure (Fig. 6) for the transmitter. Other equipment included a gasoline-powered generator that could power either the TV set or transmitter. There is always the possibility that feedback of rf energy through the power line (or "conducted interference") is a factor in a TVI problem. By running the equipment on separate power systems, some idea of the importance of this type of coupling would be ascertained.

Various low-pass filters, high-pass filters, and power harnesses made up the rest of the equipment list. Checks on various TV channels indicated the most serious problem resulted from third-harmonic energy on channel 3 during 15-meter operation. Tests were performed with the rig inside and out of its shielded enclosure, the TV set inside and out of the larger enclosure, and with either the TV set or transmitter on independent power.

### Test Results

Previous checks in the lab revealed that almost all currently manufactured amateur transmitters and transceivers emit harmonics in the form of "chassis radiation" to varying degrees. It should be pointed out that no outstanding "saints"

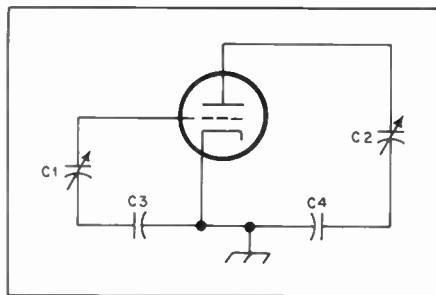


Fig. 5 — A vhf resonant circuit is formed by the tube capacitance and the lead inductances through the tank and blocking capacitors. Regular tank coils are not shown, since they have little effect on such resonances. C1 is the grid tuning capacitor and C2 is the plate tuning capacitor. C3 and C4 are the grid and plate blocking or bypass capacitors, respectively.

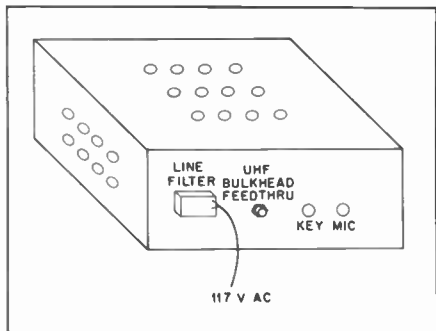


Fig. 6 — Construction details of the rf enclosure. For the model shown, thin aluminum sheet metal was used to form a box 12 × 28 × 20 inches (HWD) (304 × 711 × 508 mm). Small holes were drilled for ventilation and a fan might be advisable if temperature rise is considered a problem. Feed-through connectors can be of the builder's choice but ac conduits and control leads should be filtered. For key and mic leads, bypass with 0.001-μF disk-ceramic capacitors and install a small ferrite bead (if available). A commercially manufactured line filter was used, although a homemade one of the "brute force" type would also be suitable.

Although dimensions and material are not critical, the cabinet should be deep enough to form as much of an overlap as possible between the front of the equipment panel and the front of the cabinet. It is important that all leads be run through the rear of the cabinet.

### Operating Conditions

Grid bias and grid current have an important effect on the harmonic content of the rf currents in both the grid and plate circuits. In general, harmonic output increases as the grid bias and grid current are increased, but this is not necessarily true of a particular harmonic. The third and higher harmonics, especially, will go through fluctuations in amplitude as the grid current is increased, and sometimes a rather high value of grid current will minimize one harmonic as compared with a low value. This characteristic can be used to advantage where a particular harmonic is causing interference, remembering that the operating conditions that minimize one harmonic may greatly increase another. For equal operating



were found in this area but mostly "sinners." Once this energy escapes from the transmitter cabinet, it can be conducted to the antenna or back through the power line via a single-conductor waveguide type of mode. This mode is very similar to the propagation of rf energy over a two-dimensional conducting surface in the form of a ground wave. But the important thing to keep in mind is that devices such as filters, traps and grounds are ineffective since the rf energy flows *around* the suppression network. The only effective measure is adequate shielding.

As might be expected, the field tests verified the importance of this aspect. *The*



Fig. 7 — Lab simulation of TVI tests discussed in the text. A dummy load placed next to the "rabbit ears" served as the transmitting antenna.

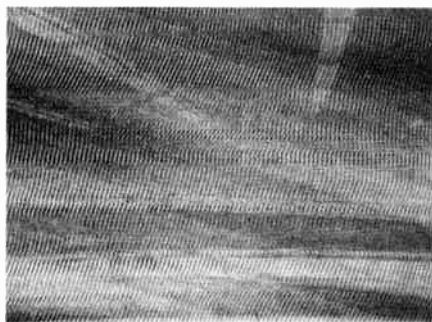


Fig. 8 — Severe interference occurred with the setup shown above with the transmitter out of the enclosure. Interference was about the same with the leads running from the front of the cabinet instead of through the rear connectors.

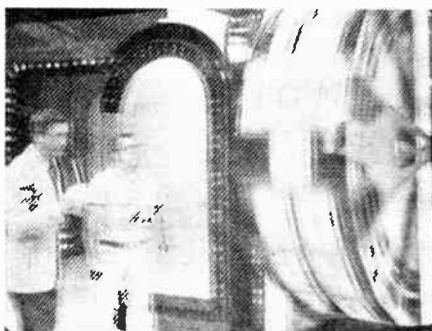


Fig. 9 — The interference was either reduced considerably (as shown in this photo) or eliminated completely, depending upon TV signal strength, with all the leads exiting from the rear of the cabinet.

*only test that indicated appreciable reduction of TVI was the one with the transmitter placed inside of its shielded enclosure.* In all other tests, there was no improvement or the change was so slight as to be inconclusive. Some residual interference still remained with the rig enclosed in the shield. This was likely caused by rectification in the external environment. One unexpected result was that no noticeable difference was observed with the door of the enclosure opened or closed. In fact, with the door partially closed and touching the shield at only a few points the TVI became worse!

### Conclusions

The transmitter power for these tests was approximately 180 watts. Considerable work has yet to be performed to determine the important factors at higher levels. However, there is hope for the ham experiencing TVI because of chassis radiation. With the door open, it is believed that the enclosure acts as a waveguide below cutoff and still offers some measure of suppression while permitting access to the controls. In discussing the tests with other amateurs experiencing TVI, reports from the field were favorable when similar measures were tried.

Some further experimentation along these lines is in order. For instance, former shielding theory advocated the use of *high-conductivity* materials. Newer methods often rely on the dissipation of unwanted rf energy in lower conductivity materials such as steel. Although rf energy can penetrate deeper into low-conductivity metals, and greater thicknesses are required to provide the same isolation (as that of copper, for example), other problems are simplified. Unwanted rf energy must be dissipated *somewhere* and when a good conductor is used for a shielding enclosure there is a greater tendency for this energy to leak out through doors, conduits and other points of entry. By dissipating energy internally on the shield walls, there is less chance for it to leak out. (However, if the unexpected attenuation with the door open was actually caused by a waveguide-below-cutoff effect as speculated, high-conductivity material near the door opening would be advisable.)

### Other Results

With the TV set in its shielded enclosure and with power fed through a commercially manufactured line filter, there was no difference in TVI with the rig *or* TV set on independent power. Rf signal energy from the TV antenna was fed into the shield enclosure through a commercially manufactured high-pass filter. Little change was noted when these measures were eliminated and the set operated on the same power service as the transmitter, without a high-pass filter and outside of the shield.

It should not be concluded that such

measures will be equally ineffective under all circumstances. However, the claims of some manufacturers are open to question. Items such as power supplies that eliminate TVI, and similar nostrums have come to our attention. Consequently, common sense is in order in judging whether or not a particular device will prove effective in eliminating interference or how it should be employed.

### Suppression Practices

As the test results reported in the previous section reveal, complete elimination of TVI is often not a simple process. It seldom happens that a single measure such as installing a high-pass filter at the TV set will cure the problem. Rather, a number of methods must be applied simultaneously. The principal factor in any TVI situation is the ratio of TV signal strength to interference level. This includes interference of all types such as ignition noise, random or thermal noise (which isn't really interference but sets the minimum signal that permits "snow-free" reception), and unwanted signals that fall within the TV channel. A signal-to-interference ratio greater than approximately 35 to 40 dB is required for good picture quality.

In this regard, an area frequently overlooked in TVI difficulties is the TV-set antenna. A poor antenna with little gain in the direction of the TV station, old and corroded wire and connections (which can *cause* the harmonic generation by rectification of a "clean" signal generated in a nearby amateur transmitter), may result in a TVI situation that is impossible to solve. For instance, the "simulated" lab tests illustrated in the photographs were performed with a dummy load next to a set of "rabbit ears," which comprised the TV-set antenna. With a good outdoor system, the TVI would not have been present even though there was a leakage from the transmitter cabinet. Generally speaking, if the picture quality on the TV set experiencing the interference is poor to begin with, even sophisticated suppression measures are likely to prove futile.

### Grounds

Grounding of equipment has long been considered to be a first step in eliminating interference. While the method is very effective in the mf range and below, for all practical purposes it is useless in suppressing vhf energy. This is because even short lengths of wire have considerable reactance at vhf. For instance, suppose a length of wire by itself has an inductance of  $1\ \mu\text{H}$ . At 550 kHz, the reactance would be about 3.46 ohms. On the other hand, the same wire would have a reactance of over 300 ohms at 56 MHz, which is the frequency range of TV channel 2. (Actually, the impedance of a wire becomes a more complicated entity to define at vhf.



The delay effects along the wire are similar to those on the surface of an antenna. Consequently, the wire might even appear as an open circuit rather than as a ground as the electrical length approaches a quarter wavelength.)

From a shock-hazard point of view, grounding is important. *However, never connect a ground for any reason to the chassis of a TV set.* This is because many TV sets derive their operating voltages directly from the ac-service line. Although a schematic diagram of a TV set may indicate a "power transformer" is being used, caution should be exercised to be sure it is actually being employed for this purpose. Quite often, the only voltage the transformer is supplying is for the TV picture tube filament.

### Shielding

Effective shielding is perhaps the single most important measure in preventing or curing any RFI problem. However, as pointed out in previous sections, unwanted rf energy must be dissipated. The task becomes harder to perform when the spacing between the source of energy and the boundaries of the shield diminish. Consequently, the use of a double shield (as used in the tests) is one way of reducing residual radiation from the primary shielding surface.

In order to obtain maximum effectiveness of a particular shielding measure, no breaks or points of entry should be permitted. Small holes for ventilation purposes usually do not degrade shielding effectiveness. But even here, a honeycomb type of duct is often employed when maximum isolation is required. (A parallel bundle of small tubing has very high attenuation since each tube by itself acts as a waveguide below cutoff.)

The isolation of a coaxial cable can be degraded considerably unless the ends of the shield are terminated properly. A braid should be soldered so that it completely encloses the inner conductor(s) at the connector junction. For instance, the practice of twisting the braid and point soldering it to the base of a connector may result in a 20-dB degradation in isolation. Normally, this effect is not serious if the cable is run through an area where sensitive circuits don't exist. However, the isolation afforded by a filter can be reduced considerably in circuits where such cable breaks occur.

One instance where a shield break causes a serious problem is in the connection between the antenna terminals on a TV set and the tuner. Newer sets have a 75-ohm coaxial input along with a balun for 300-ohm line. However, because many TV sets have direct connections to the ac line, a decoupling network is used. The shielded lead to the tuner is broken and a capacitor is connected in series with the braid. This provides a low-impedance path for rf energy while presenting a high

impedance at 60 Hz. Consequently, because of the cable break, high-pass filters at the antenna input terminals are not as effective as those built into the tuner itself.

### Capacitors at RF

Capacitors are common elements found in almost any piece of electronics gear. However, some precautions are necessary when they are employed in RFI-preventive purposes such as in filters and bypassing applications. In particular, lead inductance may be sufficient to resonate with the capacitor proper and cause the entire combination to have a high inductive reactance rather than the desired capacitive reactance.


This effect is illustrated in the accompanying photographs. The response curve shown in Fig. 10A is for a 10-MHz low-pass filter arranged in a "pi" configuration. However, this particular circuit realization required some large-valued capacitors. Using ordinary capacitor types resulted in an unwanted resonance as evidenced by the sharp dip in the response curve at approximately 15 MHz. However, by going to the equivalent "T" configuration (see the section on filters in the chapter on electrical laws and circuits), a circuit realization for the desired response required much smaller capacitance values. The curve shown in Fig. 10B approximated this response quite closely and no effects of parasitic inductance were noticeable. When designing filters, it is advisable to compute the component values for as many

configurations as possible in order to determine which one results in the most practical elements. If large capacitance values are unavoidable, either special low-inductance types should be used or a number of ordinary smaller-valued capacitors can be paralleled to reduce the effect of lead inductance.


A very desirable capacitor (C2) from an RFI point of view is shown in Fig. 11. Instead of having two or more plates arranged in a parallel fashion, the conductors are coaxial and are separated by the dielectric. Such feedthrough capacitors are highly recommended for conducting leads in and out of circuits where the radiation of harmonic energy is possible. In addition, the rfc illustrated in Fig. 11 could either consist of a small coil wound over a composition resistor as shown or it could be a ferrite bead on a straight piece of wire.
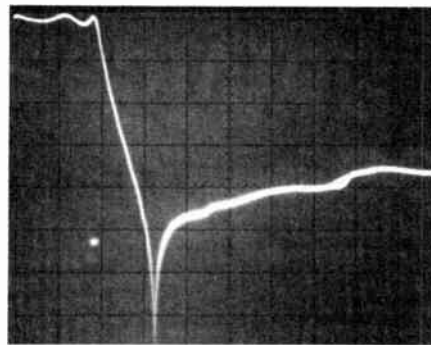
### Decoupling from the AC Line

Direct feedback of rf energy into the ac power service is usually not a problem with modern transmitting equipment. However, currents induced on the antenna feed line may flow on the transmitter chassis and back into the ac line. A rig "hot" with rf or even the presence of "broadcast harmonics" while receiving may mean a problem of this sort. In the case where an antenna is being used that requires a ground (such as an end-fed wire), never use any part of the ac conduits, water systems, or other conductors in a building. It is always



(A)

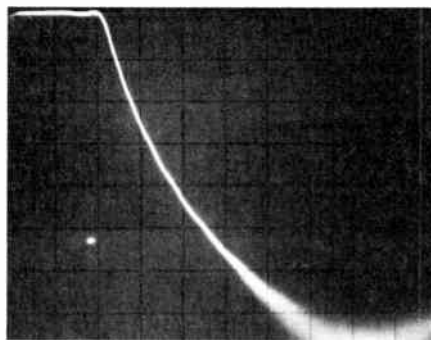

(B)

Fig. 10 — Stray lead inductance of a capacitor can degrade filter performance.

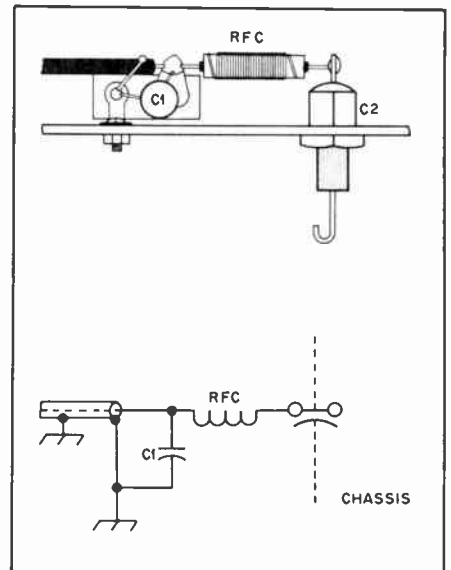


Fig. 11 — Additional lead filtering for harmonics or other spurious frequencies in the high vhf TV band (174-216 MHz).  
C1 — 0.001- $\mu$ F disk ceramic.  
C2 — 500- or 1000-pF feed-through bypass (Centralab FT-1000 Above 500 volts, substitute Centralab 858S-500.)  
RFC — 14 inches (35.6-mm) no. 26 enamel close-wound on 3/16-inch (4.76-mm) dia. form or composition resistor body.

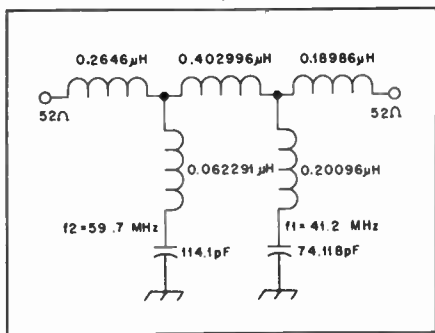


Fig. 12 — Schematic diagram showing component values of an experimental elliptic function filter.

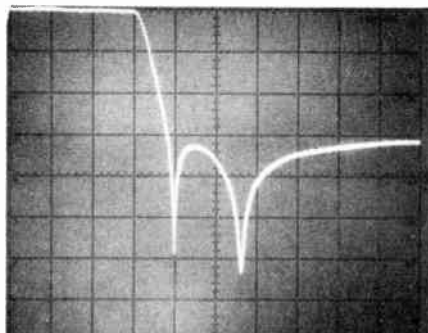


Fig. 13 — Response curve of the filter shown in Fig. 12. Vertical scale represents 10 dB/div. and horizontal scale is 10 MHz/div.

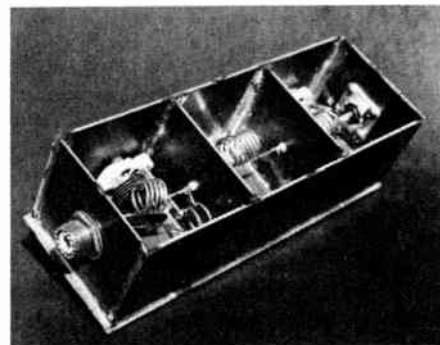


Fig. 14 — Pc board serves as an enclosure for this elliptic function filter.

advisable to have a separate ground system for the antenna itself.

It is also good practice to use an antenna-matching network with no direct connection between the transmitter and antenna feed line. Any matching network that uses mutual-magnetic coupling exclusively will fulfill this requirement. Antenna pattern is another factor to consider and if possible, a type should be used that directs the minimum possible signal into other dwellings. For instance, ground-mounted vertical antennas have considerable low-angle radiation while a dipole directs energy at angles *below* the horizontal plane. A vertical ground plane or beam mounted on as high a tower as practical will generally be better from an RFI and TVI standpoint than antennas closer to the ground.

### Filters and Interference

The judicious use of *filters*, along with other suppression measures such as shielding, has provided solutions to interference problems in widely varying applications. As a consequence, considerable attention has been given to the subject over the years that has resulted in some very esoteric designs. Perhaps the most modern approach is the optimization and/or realization for a particular application of a filter by means of a digital computer. However, there are a number of other types with component values cataloged in tabular form. Of these, the most important ones are the so-called Chebyshev and elliptic-function filters. (Butterworth filters are often considered a special case of Chebyshev types with a ripple factor of zero.)

Elliptic-function filters might be considered optimum in the sense that they provide the sharpest rolloff between the passband and stopband. Computed values for a low-pass filter with a 0.1-dB ripple in the passband and a cutoff frequency of 30.6 MHz are shown in Fig. 12. The filter is supposed to provide an attenuation of 35 dB above 40 MHz. An experimental model was built and the response is shown in Fig. 13. As can be seen, the filter came quite close to the design goals. Unfortu-

nately, as with most of the designs in this section, alignment of the more complicated filters requires some sort of sweep-generator setup. This is the only practical way of "tweaking" a filter to the desired response. While building a sweep setup is not beyond the talents of an advanced experimenter, the lack of one is an obstacle in the home construction of filters.

### Chebyshev Filters

Chebyshev low-pass filters (and Butterworth filters) have the same ladder-network circuit as the elliptic-function filter in Fig. 12 except that the inductors in the shunt arms are omitted. Tables for the element values are quite common and can be found in any number of references. However, how to determine the attenuation at a particular frequency is often not included in such tables and some explanation is in order. It will be recalled that a ripple factor was mentioned in conjunction with the elliptic-function filter in the previous section. This factor specifies the allowable amount of attenuation in the passband and represents a tradeoff from steepness of the attenuation between the passband and stopband. Larger ripple factors result in greater rolloff; however, the input impedance and consequently the VSWR of the filter become larger also. For moderate-power-transmitting applications, a ripple factor of 0.1 dB is about the maximum permissible amount. This results in a VSWR of approximately 1.4:1. For low-level stages, VSWR is often not a problem and higher ripple factors can be used.

The attenuation (or insertion loss in the case of equal resistive terminations at the input and output of the filter) is given by

$$L = 10 \log_{10} \frac{1}{1 + \epsilon^2 T_n^2(\omega)}$$

where  $T_n(\ )$  represents a Chebyshev polynomial of degree  $n$ , and  $n$  represents the number of inductors and capacitors in the filter (for instance, for an ordinary pi or T network,  $n$  would be 3). The term  $\omega$  is just  $2\pi f$  ( $f$  is the frequency in Hz and  $\epsilon^2$  will be discussed shortly). Chebyshev polynomials can be expressed in terms of

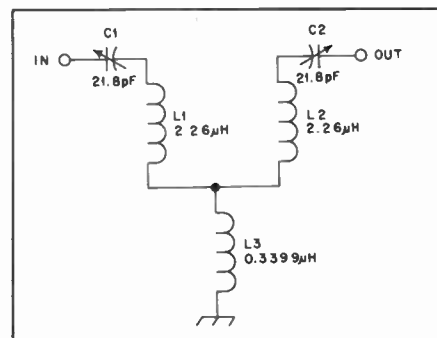


Fig. 15 — Schematic diagram of the "Citation Eliminator." Component values shown are theoretical computed inductances and capacitances for a band-pass filter resonant at 21.14 MHz with a bandwidth of 4.5 MHz. C1, C2 — 4.5 to 25 pF, ceramic trimmer. L1, L2 — 13 turns 3/4-inch (19-mm) dia., 16 tpi (B & W 3011). L3 — 5 turns no. 16 solid wire 3/4-inch (19-mm) dia., approx. 1-inch (25-mm) long.

ordinary trigonometric and hyperbolic functions by

$$T_n(\omega) = \begin{cases} \cos(n \arccos \omega) & 0 \leq \omega \leq 1 \\ \cosh(n \operatorname{arcosh} \omega) & \omega > 1 \end{cases}$$

For values of  $\omega$  less than one, the polynomial oscillates between  $\pm 1$ , while for greater values it increases rapidly. Consequently, the value for  $\omega$  equal to 1 represents the cutoff frequency of the filter. While the polynomial could be tabulated from tables of functions, the problem could be easily solved on many current calculator models. In fact, with programmable models such as the Hewlett Packard HP-25, finding the attenuation at any frequency only requires entry of the frequency, ripple factor and number of elements (number of poles). For those interested, a copy of such a program is available from ARRL for 25 cents and an s.a.s.e.

The term  $\epsilon^2$  is the ripple factor and is related to the ripple factor in decibels by the equation:

$$\epsilon^2 = 10^{\frac{\text{ripple (dB)}}{10}} - 1$$



This concept represents the most important aspect of current filter design. Limits or tolerances are set on the amount of ripple in either the passband or stopband (or both in the case of elliptic-function filters) and the filter is designed around these limits.

### A Citation Eliminator

Quite often, some insight into the qualitative manner in which a filter works is useful. For example, consider the filter shown in Fig. 15. If the 2.26- $\mu$ H coils were omitted, a high-pass configuration would result. By including the coils, the filter will possibly have a rolloff above the high-pass cutoff frequency and provide an unsymmetrical bandpass characteristic.

This is shown in Fig. 16 and an application of a filter of this type is as follows. Many older rigs suitable for cw work are often acquired by Novice operators because of their low cost. Unfortunately, operation on the higher bands such as 15 meters can be somewhat tricky and it is possible that the rig is tuned up on 20 meters instead. The aforementioned filter eliminates that possibility by providing rejection at 14 MHz and also at harmonics above the operating frequency of 21 MHz. It is relatively easy to align since all that is necessary is to grid-dip L1 to 21.14 MHz (with the input shorted and the output open) by means of C1. The process is repeated with L2 and C2, only the input is opened and the output terminal shorted. Further tweaking can be accomplished by adjusting the capacitors for minimum SWR with the output circuit connected to a dummy load. Some adjustment of L3, which controls the coupling, may be necessary. Spreading or squeezing the coil turns farther apart or closer together decreases or increases the inductance (and hence the coupling) accordingly.

### An Absorptive Filter

The filter shown in Fig. 18 not only provides rejection by means of a low-pass section, it also includes circuitry that absorbs harmonic energy. A high-pass section consisting of L1, L2, C1 and C2 is terminated in a 50-ohm "idler load" and this combination performs the latter function. The advantages of this technique are that degradation of filter rejection caused by antenna mismatch at the harmonic frequency are not as severe (with a filter of this type) and the transmitter is terminated in a resistive load at the harmonic.

### Construction and Test Techniques

If good performance above 100 MHz is not a necessity, this filter can be built using conventional fixed capacitors. Copper-clad Teflon board may not be readily available in small quantities from many supply houses. Regular fiberglass-insulated board is satisfactory for low power. One

such filter has been used with an SB-100 transceiver running 100 watts. Although the Q of the fiberglass capacitors will be lower than that of Teflon-dielectric capacitors, this should not greatly affect the type of filter described here.

Test equipment needed to build this filter at home includes a reasonably accurate grid-dip oscillator, an SWR bridge, a reactance chart or the ARRL Lightning Calculator (for L, C and f), a 50-ohm dummy load, and a transmitter.

Once the value of a given capacitor has been calculated, the next step is to determine the capacitance per square inch of the double-clad circuit board you have. This is done by connecting one end of a coil of known inductance to one side of the circuit board, and the other coil lead to the other side of the circuit board. Use the grid-dip oscillator, coupled lightly to the coil, to determine the resonant frequency of the coil and the circuit-board capacitor. When the frequency is known, the total capacitance can be determined by working the Lightning Calculator or by looking the capacitance up on a reactance chart. The total capacitance divided by the number of square inches on one side of the circuit board gives the capacitance per square inch. Once this figure is determined, capacitors of almost any value can be laid out with a ruler!

High voltages can be developed across capacitors in a series-tuned circuit, so the copper material should be trimmed back at least 1/8 inch (3-mm) from all edges of a board, except those that will be soldered to ground, to prevent arcing. This should not be accomplished by filing, since the copper filings would become imbedded in the board material and just compound the problem. The capacitor surfaces should be kept smooth and sharp corners should be avoided.

If the filter box is made of double-clad fiberglass board, both sides should be bonded together with copper stripped from another piece of board. Stripped copper foil may be cleaned with a razor blade before soldering. To remove copper foil from a board, use a straight edge and a sharp scribe to score the thin copper foil. When the copper foil has been cut, use a razor blade to lift a corner. Careful heating with a soldering iron will reduce the effort required to separate the copper from the board. This technique of bonding two pieces of board or two sides of a piece of board can also be used to interconnect two capacitors when construction in one plane would require too much area. Stray inductance must be minimized and sufficient clearance must be maintained for arc-over protection.

Capacitors with Teflon dielectric have been used in filters passing up to 2 kW PEP. One further word of caution: No low-pass filter will be fully effective until the transmitter with which it is used is properly shielded and all leads filtered.

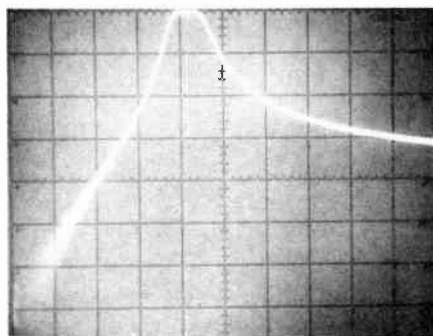


Fig. 16 — Response of the "Citation Eliminator." Attenuation and frequency scale 10 dB/div. (vertical) and 5 MHz/div. (horizontal).

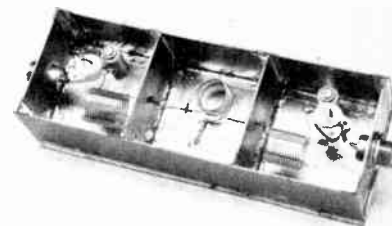


Fig. 17 — Pc-board construction is shown here for the "Citation Eliminator." Approximate dimensions are 2 x 2-3/4 x 2-3/4-inches (51 x 70 x 70 mm) HWD. A top cover with a hole for capacitor adjustment should be soldered on after the filter is initially aligned. The power rating is suitable for transmitters in the 75-watt input class.

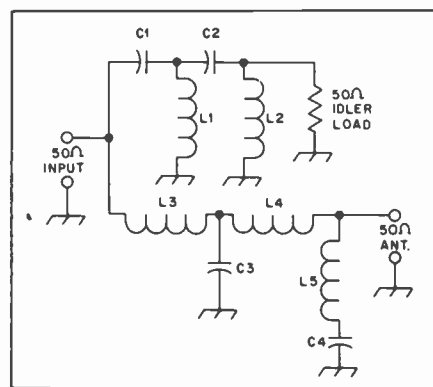


Fig. 18 — Schematic diagram of the absorptive filter. The pc-board used is MIL-P-13949D, FL-GT-.062 in., C-2/2-11017, Class 1, Grade A. Polychem Bud Division. Capacitance between copper surfaces is 10-pF per square inch. Values are as follows for a design cutoff frequency of 40 MHz and rejection peak in channel 2:  
C1 — 52 pF    C4 — 21.6 pF    L3 — 0.3  $\mu$ H  
C2 — 73 pF    L1 — 0.125  $\mu$ H    L4 — 0.212  $\mu$ H  
C3 — 126 pF    L2 — 0.52  $\mu$ H    L5 — 0.24  $\mu$ H

The terminating loads for the high-pass section of the filter can be made from 2-watt, 10-percent tolerance composition resistors. Almost any dissipation rating can be obtained by suitable series-parallel combinations. For example, a 16-watt, 50-ohm load could be built as shown in Fig. 19. This load should handle the harmonic energy of a signal with peak

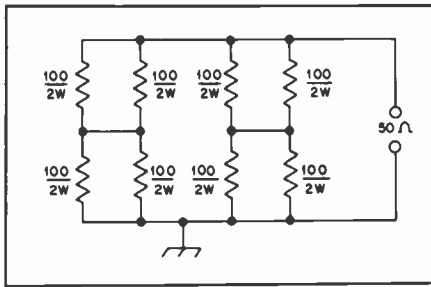


Fig. 19 — Dummy load for the high-pass section of the filter.

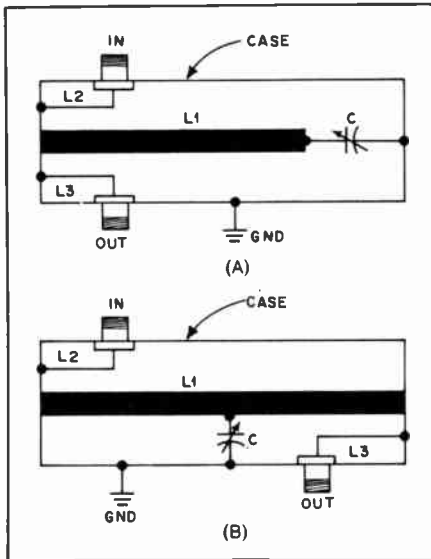


Fig. 20 — Equivalent circuits for the strip-line filters. At A, the circuit for the 6- and 2-meter filters are shown. L2 and L3 are the input and output links. These filters are bilateral, permitting interchanging of the input and output terminals.

At B, the representative circuit for the 220- and 432-MHz filters. These filters are also bilateral.

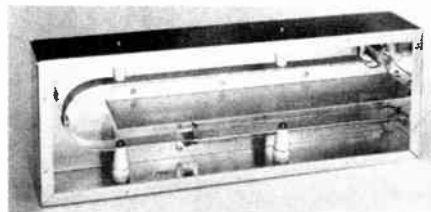


Fig. 21 — Interior of the 50-MHz strip line filter. Inner conductor of aluminum strip is bent into U shape, to fit inside a standard 17-inch (432-mm) chassis.

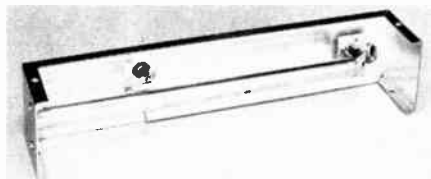


Fig. 22 — The 144-MHz filter has an inner conductor of 1/2-inch (13-mm) copper tubing 10 inches (254-mm) long, grounded to the left end of the case and supported at the right end by the tuning capacitor.

fundamental power of 2 kilowatts. With this load, the harmonic energy will see an SWR under 2:1 up to 400 MHz. For low power (under 300 watts PEP), a pair of 2-watt, 100-ohm resistors is adequate.

In the model shown the high-pass filter series capacitors are bonded and mounted on Teflon standoff insulators.

#### Filters For VHF Transmitters

High rejection of unwanted frequencies is possible with the tuned-line filters of Fig. 20. Examples are shown for each band from 50 through 450 MHz. Construction is relatively simple, and the cost is low. Standard boxes are used for ease of duplication.

The filter of Fig. 21 is selective enough to pass 50-MHz energy and attenuate the seventh harmonic of an 8-MHz oscillator that falls in TV channel 2. With an insertion loss at 50 MHz of about 1 dB, it can provide up to 40 dB of attenuation to energy at 57 MHz in the same line. This should be more than enough attenuation to take care of the worst situations, provided that the radiation is by way of the transmitter output coax only. The filter will not eliminate interfering energy that gets out from power cables, the ac line, or from the transmitter circuits themselves. It also will do nothing for TVI that results from deficiencies in the TV receiver.

The 50-MHz filter, Fig. 21, uses a folded line in order to keep it within the confines of a standard chassis. The case is a 6 × 17 × 3-inch (152 × 432 × 76-mm) chassis (Bud AC-433) with a cover plate that fastens in place with self-tapping screws. An aluminum partition down the middle of the assembly is 14 inches (356-mm) long, and the full height of the chassis, 3 inches (76-mm).

The inner conductor of the line is 32 inches (813-mm) long and 13/16-inch (21-mm) wide, of 1/16-inch (2-mm) brass, copper or aluminum. This was made from two pieces of aluminum spliced together to provide the 32-inch (813-mm) length. Splicing seemed to have no ill effect on the circuit Q. The sides of the "U" are 2-7/8 inches (73-mm) apart, with the partition at the center. The line is supported up with sections of hard wood or bakelite rod, to give the required 1-1/2-inch (38-mm) height.

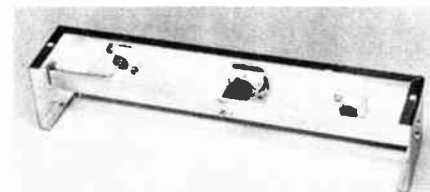


Fig. 23 — A half-wave strip line is used in the 220-MHz filter. It is grounded at both ends and tuned at the center.

The tuning capacitor is a double-spaced variable (Hammarlund HF-30-X) mounted 1-1/2 inches (38-mm) from the right end of the chassis. Input and output coupling loops are of no. 10 or 12 wire, 10 inches (254-mm) long. Spacing away from the line is adjusted to about 1/4 inch (6-mm).

The 144-MHz model is housed in a 2-1/4 × 2-1/2 × 12-inch (57 × 64 × 305-mm) Minibox (Bud CU-2114-A).

One end of the tubing is slotted 1/4-inch (6-mm) deep with a hacksaw. This slot takes a brass angle bracket 1-1/2-inches (38-mm) wide, 1/4-inch (6-mm) high, with a 1/2-inch (13-mm) mounting lip. This 1/4-inch (6-mm) lip is soldered into the tubing slot, and the bracket is then bolted to the end of the box, so as to be centered on the end plate.

The tuning capacitor (Hammarlund HF-15-X) is mounted 1-1/4 inches (32-mm) from the other end of the box, in such a position that the inner conductor can be soldered to the two stator bars.

The two coaxial fittings (SO-239) are 11/16 inch (17-mm) in from each side of the box, 3-1/2 inches (89-mm) from the left end. The coupling loops are no. 12 wire, bent so that each is parallel to the center line of the inner conductor, and about 1/8 inch (3-mm) from its surface. Their cold ends are soldered to the brass mounting bracket.

The 220-MHz filter uses the same size box as the 144-MHz model. The inner conductor is 1/16-inch (2-mm) brass or copper, 5/8-inch (16-mm) wide, just long enough to fold over at each end for bolting to the box. It is positioned so that there will be 1/8 inch (3-mm) clearance between it and the rotor plates of the tuning capacitor. The latter is a Hammarlund HF-15-X, mounted slightly off-center in the box, so that its stator plates connect to the exact mid-point of the line. The 5/16-inch (8-mm) mounting hole in the case is 5-1/2 inches (140-mm) from one end. The SO-239 coaxial fittings are 1 inch (25-mm) in from opposite sides of the box, 2 inches (51-mm) from the ends. Their coupling links are no. 14 wire, 1/8 inch (3-mm) from the inner conductor of the line.

The 420-MHz filter is similar in design, using a 1-5/8 × 2 × 10-inch (41 × 51 × 254-mm) Minibox (Bud CU-2113-A). A half-wave line is used, with disk tuning at the center. The disks are 1/16-inch (2-mm) brass, 1-1/4-inch (32-mm) diameter. The fixed one is centered on the inner conductor, the other mounted on a no. 6 brass lead-screw. This passes through a threaded bushing, which can be taken from the end of a discarded slug-tuned form. An advantage of these is that usually a tension device is included. If there is none, use a lock nut.

Type N coaxial connectors were used on the 420-MHz model. They are 5/8 inch (16-mm) in from each side of the box, and



1-3/8 inches (35-mm) in from the ends. Their coupling links of no. 14 wire are 1/16 inch (2-mm) from the inner conductor.

### Adjustment and Use

If you want the filter to work on both transmitting and receiving, connect the filter between antenna line and SWR indicator. With this arrangement you need merely adjust the filter for minimum reflected power reading on the SWR bridge. This should be zero, or close to it, if the antenna is well-matched. The bridge should be used, as there is no way to adjust the filter properly without it. If you insist on trying, adjust for best reception of signals on frequencies close to the ones you expect to transmit on. This works only if the antenna is well matched.

When the filter is properly adjusted (with the SWR bridge) you may find that reception can be improved by retuning the filter. Don't do it if you want the filter to work best on the job it was intended to do: The rejection of unwanted energy, transmitting or receiving. If you want to improve reception with the filter in the circuit, work on the receiver input circuit. To get maximum power out of the transmitter and into the line, adjust the transmitter output coupling, not the filter. If the effect of the filter on reception bothers you, connect it in the line from the antenna relay to the transmitter only.

### Summary

The methods of harmonic elimination outlined here have been proved beyond doubt to be effective even under highly unfavorable conditions. It must be emphasized once more, however, that the problem must be solved one step at a time, and the procedure must be in logical order. It cannot be done properly without two items of simple equipment: A grid-dip meter and wavemeter covering the TV bands, and a dummy antenna.

To summarize:

1) Take a critical look at the transmitter on the basis of the design considerations outlined under "Reducing Harmonic Generation."

2) Check all circuits, particularly those connected with the final amplifier, with the grid-dip meter to determine whether there are any resonances in the TV bands. If so, rearrange the circuits so the resonances are moved out of the critical frequency region.

3) Connect the transmitter to the dummy antenna and check with the wavemeter for the presence of harmonics on leads and around the transmitter enclosure. Seal off the weak spots in the shielding and filter the leads until the wavemeter shows no indication at any harmonic frequency.

4) At this stage, check for interference with a TV receiver. If there is interference, determine the cause by the methods

described previously and apply the recommended remedies until the interference disappears.

5) When the transmitter is completely clean on the dummy antenna, connect it to the regular antenna and check for interference on the TV receiver. If the interference is not bad, a Transmatch or matching circuit installed as previously described should clear it up. Alternatively, a low-pass filter may be used. If neither the Transmatch nor filter makes any difference in the interference, the evidence is strong that the interference, at least in part, is being caused by receiver overloading because of the strong fundamental-frequency field about the TV antenna and receiver. A Transmatch and/or filter, installed as described above, will invariably make a difference in the intensity of the interference if the interference is caused by transmitter harmonics alone.

6) If there is still interference after installing the Transmatch and/or filter, and the evidence shows that it is probably caused by a harmonic, more attenuation is needed. A more elaborate filter may be necessary. However, it is well at this stage to assume that part of the interference may be caused by receiver overloading. Take steps to alleviate such a condition before trying highly elaborate filters and traps on the transmitter.

### Harmonics by Rectification

Even though the transmitter is completely free from harmonic output it is still possible for interference to occur because of harmonics generated outside the transmitter. These result from rectification of fundamental-frequency currents induced in conductors in the vicinity of the transmitting antenna. Rectification can take place at any point where two conductors are in poor electrical contact, a condition that frequently exists in plumbing, downspouting, BX cables crossing each other, and numerous other places in the ordinary residence. It also can occur at any exposed vacuum tubes in the station, in power supplies, speech equipment, or other items which may not

be enclosed in the shielding about the rf circuits. Poor joints anywhere in the antenna system are especially bad, and rectification also may take place in the contacts of antenna changeover relays. Another common cause is overloading the front end of the communications receiver when it is used with a separate antenna (which will radiate the harmonics generated in the first tube) for break-in.

Rectification of this sort will not only cause harmonic interference but also is frequently responsible for cross-modulation effects. It can be detected in greater or less degree in most locations, but fortunately the harmonics thus generated are not usually of high amplitude. However, they can cause considerable interference in the immediate vicinity in fringe areas, especially when operation is in the 28-MHz band. The amplitude decreases rapidly with the order of the harmonic, the second and third being the worst. It is ordinarily found that even in cases where destructive interference results from 28-MHz operation the interference is comparatively mild from 14-MHz, and is negligible at still lower frequencies.

Nothing can be done at either the transmitter or receiver when rectification occurs. The remedy is to find the source and eliminate the poor contact either by separating the conductors or bonding them together. A crystal wavemeter (tuned to the fundamental frequency) is useful for hunting the source by showing which conductors are carrying rf and, comparatively, how much.

Interference of this kind is frequently intermittent since the rectification efficiency will vary with vibration, weather and so on. The possibility of corroded contacts in the TV receiving antenna should not be overlooked, especially if it has been up a year or more.

### TV Receiver Deficiencies

When a television receiver is quite close to the transmitter, the intense rf signal from the transmitter's fundamental may overload one or more of the receiver circuits to produce spurious responses

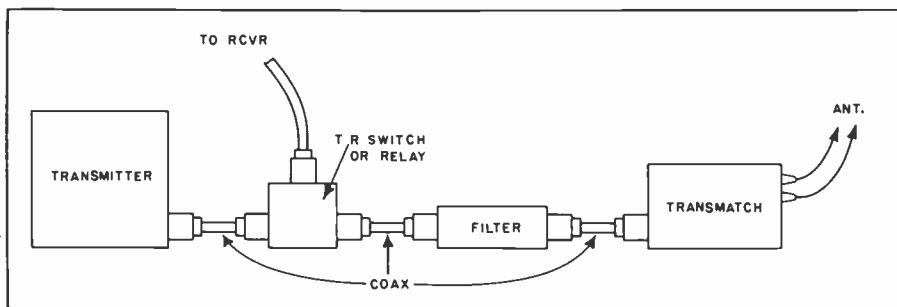


Fig. 24 — The proper method of installing a low-pass filter between the transmitter and a Transmatch. If the antenna is fed through coax, the Transmatch can be eliminated, but the transmitter and filter must be completely shielded. If a TR switch is used, it should be installed between the transmitter and low-pass filter. TR switches can generate harmonics themselves, so the low-pass filter should follow the TR switch.

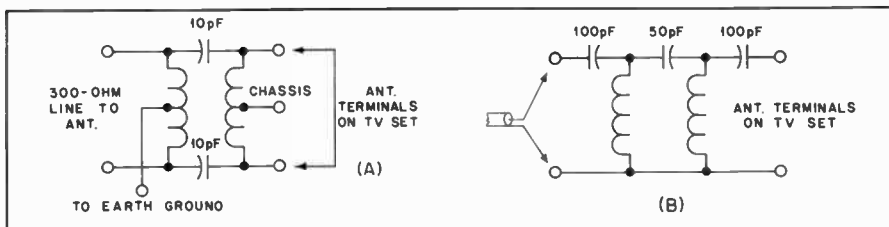


Fig. 25 — High-pass filters for installation at the TV receiver antenna terminals. Each coil 8 turns no. 14, 3/4-in. dia, 1-in. long (19 × 25 mm) tapped at center. B — For 75-ohm coaxial line. Each coil 3 turns no. 14, 3/4-in. (19-mm) dia, 8 turns per inch. *Important:* Do not use a direct ground on the chassis of a transformerless receiver. Ground through a 0.001- $\mu$ F mica capacitor.

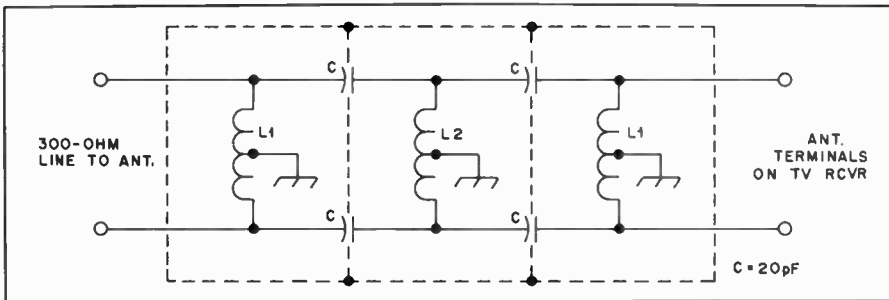


Fig. 26 — Another type of high-pass filter for 300-ohm line. The coils may be wound on 1/8-inch (3-mm) diameter plastic knitting needles. L1 = 40 turns no. 30 enam. close wound, 1/8-in. (3-mm) dia. L2 = 22 turns no. 30 enam. close wound, 1/8-inch. (3-mm) dia. *Important:* Do not use a direct ground on the chassis of a transformerless receiver. Ground through a 0.01- $\mu$ F mica capacitor.

which cause interference.

If the overload is moderate, the interference is of the same nature as harmonic interference; it is caused by harmonics generated in the early stages of the receiver and, since it occurs only on channels harmonically related to the transmitting frequency, it is difficult to distinguish from harmonics actually radiated by the transmitter. In such cases additional harmonic suppression at the transmitter will do no good, but any means taken at the receiver to reduce the strength of the amateur signal reaching the first tube will effect an improvement. With very severe overloading, interference also will occur on channels *not* harmonically related to the transmitting frequency, so such cases are easily identified.

### Cross-Modulation

Under some circumstances overloading will result in cross-modulation or mixing of the amateur signal with that from a local fm or TV station. For example, a 14-MHz signal can mix with a 92-MHz fm station to produce a beat at 78 MHz and cause interference in channel 5, or with a TV station on channel 5 to cause interference in channel 3. Neither of the channels interfered with is in harmonic relationship to 14 MHz. Both signals have to be on the air for the interference to occur, and eliminating either at the TV receiver will eliminate the interference.

There are many combinations of this type, depending on the band in use and the local frequency assignments to fm and TV stations. The interfering frequency is

equal to the amateur fundamental frequency either added to or subtracted from the frequency of some local station, and when interference occurs in a TV channel that is not harmonically related to the amateur transmitting frequency, the possibilities in such frequency combinations should be investigated.

### i-f Interference

Some TV receivers do not have sufficient selectivity to prevent strong signals in the intermediate-frequency range from forcing their way through the front end and getting into the i-f amplifier. The once-standard intermediate frequency of, roughly, 21 to 27 MHz, is subject to interference from the fundamental-frequency output of transmitters operating in the 21-MHz band. Transmitters on 28 MHz sometimes will cause this type of interference as well.

A form of i-f interference peculiar to 50-MHz operation near the low edge of the band occurs with some receivers having the standard "41-MHz" i-f, which has the sound carrier at 41.25 MHz and the picture carrier at 45.75 MHz. A 50-MHz signal that forces its way into the i-f system of the receiver will beat with the i-f picture carrier to give a spurious signal on or near the i-f sound carrier, even though the interfering signal is not actually in the nominal passband of the i-f amplifier.

There is a type of i-f interference unique to the 144-MHz band in localities where certain uhf TV channels are in operation. I affects only those TV receivers in which double-conversion type plug-in uhf tuning

strips are used. The design of these strips involves a first intermediate frequency that varies with the TV channel to be received and, depending on the particular strip design, this first i-f may be in or close to the 144-MHz amateur band. Since there is comparatively little selectivity in the TV signal-frequency circuits ahead of the first i-f, a signal from a 144-MHz transmitter will "ride into" the i-f, even when the receiver is at a considerable distance from the transmitter. The channels that can be affected by this type of i-f interference are

Receivers with 21-MHz second i-f	Receivers with 41-MHz second i-f
Channels 14-18, incl.	Channels 20-25, incl.
Channels 41-48, incl.	Channels 51-58, incl.
Channels 69-77, incl.	Channels 82 and 83.

If the receiver is not close to the transmitter, a trap of the type shown in Fig. 27 will be effective. However, if the separation is small the 144-MHz signal will be picked up directly on the receiver circuits and the best solution is to readjust the strip oscillator so that the first i-f is moved to a frequency not in the vicinity of the 144-MHz band. This has to be done by a competent technician.

I-f interference is easily identified since it occurs on all channels — although sometimes the intensity varies from channel to channel — and the cross-hatch pattern it causes will rotate when the receiver's fine-tuning control is varied. When the interference is caused by a harmonic, overloading or cross modulation, the structure of the interference pattern does not change (its intensity may change) as the fine-tuning control is varied.

### High-Pass Filters

In all of the above cases the interference can be eliminated if the fundamental signal strength can be reduced to a level that the receiver can handle. To accomplish this with signals on bands below 30 MHz, the most satisfactory device is a high-pass filter having a cutoff frequency between 30 and 54 MHz installed at the tuner input terminals of the receiver. Circuits that have proved effective are shown in Figs. 25 and 26. Fig. 26 has one more section than the filters of Fig. 25 and thus has somewhat better cutoff characteristics. All the circuits given are designed to have little or no effect on the TV signals, but will attenuate all signals lower in frequency than about 40 MHz. These filters preferably should be constructed in some sort of shielding container, although shielding is not always necessary. The dashed lines in Fig. 26 show how individual filter coils can be shielded from each other. The capacitors can be tubular ceramic units centered in holes in the partitions that separate the coils.

Simple high-pass filters cannot always

be applied successfully in the case of 50-MHz transmissions, because they do not have sufficiently sharp cutoff characteristics to give both good attenuation at 50-54 MHz and no attenuation above 54 MHz. A more elaborate design capable of giving the required sharp cutoff has been described (Ladd, "50-MHz TVI — Its Causes and Cures," *QST*, June and July, 1954). This article also contains other information useful in coping with the TVI problems peculiar to 50-MHz operation. As an alternative to such a filter, a high-Q wave trap tuned to the transmitting frequency may be used, suffering only the disadvantage that it is quite selective and therefore will protect a receiver from overloading over only a small range of transmitting frequencies in the 50-MHz band. A trap of this type is shown in Fig. 27. These "suck-out" traps, while absorbing energy at the frequency to which they are tuned, do not affect the receiver operation otherwise. The assembly should be mounted near the input terminals of the TV tuner and its case should be grounded to the TV set chassis. The traps should be tuned for minimum TVI at the transmitter operating frequency. An insulated tuning tool should be used for adjustment of the trimmer capacitors, since they are at a "hot" point and will show considerable body-capacitance effect.

High-pass filters are available commercially at moderate prices. In this connection, it should be understood by all parties concerned that while an amateur is responsible for harmonic radiation from his transmitter, it is no part of his responsibility to pay for or install filters, wave traps or other devices that may be required at the receiver to prevent interference caused by his fundamental frequency. Proper installation usually requires that the filter be installed right at the input terminals of the rf tuner of the TV set and not merely at the external antenna terminals, which may be at a considerable distance from the tuner. The question of cost is one to be settled between the set owner and the organization with which he deals. Don't overlook the possibility that the manufacturer of the TV receiver may supply a high-pass filter free of charge.

If the fundamental signal is getting into the receiver by way of the line cord a line filter such as those shown in Fig. 28 may help. To be most effective it should be installed inside the receiver chassis at the point where the cord enters, making the ground connections directly to the chassis at this point. It may not be so helpful if placed between the line plug and the wall socket unless the rf is actually picked up on the house wiring rather than on the line cord itself.

### Antenna Installation

Usually, the transmission line between the TV receiver and the actual TV antenna will pick up a great deal more energy from

a nearby transmitter than the television receiving antenna itself. The currents induced on the TV transmission line in this case are of the "parallel" type, where the phase of the current is the same in both conductors. The line simply acts like two wires connected together to operate as one. If the receiver's antenna input circuit were perfectly balanced it would reject these "parallel" or "unbalanced" signals and respond only to the true transmission-line ("push-pull") currents; that is, only signals picked up on the actual antenna would cause a receiver response. However, no receiver is perfect in this respect, and many TV receivers will respond strongly to such parallel currents. The result is that the signals from a nearby amateur transmitter are much more intense at the first stage in the TV receiver than they would be if the receiver response were confined entirely to energy picked up on the TV antenna alone. This situation can be improved by using shielded transmission line — coax or, in the balanced form, "twinax" — for the receiving installation. For best results the line should terminate in a coax fitting on the receiver chassis, but if this is not possible the shield should be grounded to the chassis right at the antenna terminals.

The use of shielded transmission line for the receiver also will be helpful in reducing response to harmonics actually being radiated from the transmitter or transmitting antenna. In most receiving installations the transmission line is very much longer than the antenna itself, and is consequently far more exposed to the harmonic fields from the transmitter. Much of the harmonic pickup, therefore, is on the receiving transmission line when the transmitter and receiver are quite close together. Shielded line, plus relocation of either the transmitting or receiving antenna to take advantage of directive effects, often will reduce overloading, as well as harmonic pickup, to a level that does not interfere with reception.

### UHF Television

Harmonic TVI in the uhf TV band is far less troublesome than in the vhf band. Harmonics from transmitters operating below 30 MHz are of such high order that they would normally be expected to be quite weak; in addition, the components, circuit conditions and construction of low-frequency transmitters are such as to tend to prevent very strong harmonics from being generated in this region. However, this is not true of amateur vhf transmitters, particularly those working in the 144-MHz and higher bands. Here the problem is quite similar to that of the low vhf TV band with respect to transmitters operating below 30 MHz.

There is one highly favorable factor in uhf TV that does not exist in the most of the vhf TV band: If harmonics are radiated, it is possible to move the

**Table 1**  
**Harmonic Relationship — Amateur VHF Bands and UHF TV Channels**

Amateur Band	Harmonic	Fundamental Freq. Range	Channel Affected		
144 MHz	4th	144.0-144.5	31		
		144.5-146.0	32		
		146.0-147.5	33		
		147.5-148.0	34		
		144.0-144.4	55		
		144.4-145.6	56		
	5th	145.6-146.8	57		
		146.8-148.0	58		
		6th	144.0-144.33	79	
			144.33-145.33	80	
			145.33-147.33	81	
			147.33-148.0	82	
220 MHz	3rd	220-220.67	45		
		220.67-222.67	46		
		222.67-224.67	47		
		224.67-225	48		
	4th	220-221	82		
		221-222.5	83		
		420 MHz	2nd	420-421	75
				421-424	76
424-427	77				
427-430	78				
430-433	79				
433-436	80				

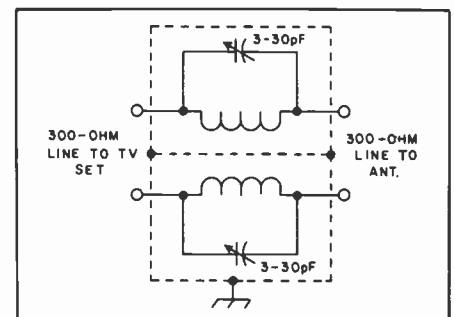


Fig. 27 — Parallel-tuned traps for installation in the 300-ohm line to the TV set. The traps should be mounted in an aluminum Minibox with a shield partition between them, as shown. For 50 MHz, the coils should have nine turns of no. 16 enamel wire, close wound to a diameter of 1/2 inch (13-mm). The 144-MHz traps should contain coils with a total of six turns of the same type wire, close-wound to a diameter of 1/4 inch (6 mm). Traps of this type can be used to combat fundamental-overload TVI on the lower-frequency bands as well.

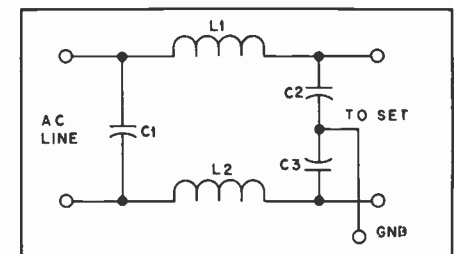


Fig. 28 — "Brute-force" ac line filter for receivers. The values of C1, C2 and C3 are not generally critical; capacitances from 0.001 to 0.01  $\mu$ F can be used. L1 and L2 can be a 2-inch (51-mm) winding of no. 18 enameled wire on a 1/2-inch (13-mm) diameter form. In making up such a unit for use external to the receiver, make sure that there are no exposed conductors to offer a shock hazard.



transmitter frequency sufficiently (within the amateur band being used) to avoid interfering with a channel that may be in use in the locality. By restricting operation to a portion of the amateur band that will not result in harmonic interference, it is possible to avoid the necessity of taking extraordinary precautions to prevent harmonic radiation.

The frequency assignment for uhf television consists of 70 channels (14 to 83, inclusive) in 6-MHz steps, beginning at 470 MHz and ending at 890 MHz. The harmonics from amateur bands above 50 MHz span the uhf channels as shown in Table 1. Since the assignment plan calls for a minimum separation of six channels between any two stations in one locality, there is ample opportunity to choose a fundamental frequency that will move a harmonic out of range of a local TV frequency.

### Color Television

The color TV signal includes a subcarrier spaced 3.579545 MHz from the regular picture carrier (or 4.83 MHz from the low edge of the channel) for transmitting the color information. Harmonics which fall in the color subcarrier region can be expected to cause break-up of color in the received picture. This modifies the chart of Fig. 2 to introduce another "severe" region centering around 4.8 MHz measured from the low-frequency edge of the channel. Hence with color television reception there is less opportunity to avoid harmonic interference by choice of operating frequency. In other respects the problem of eliminating interference is the same as with black-and-white television.

### Interference from TV Receivers

The TV picture tube is swept horizontally by the electron beam 15,734.264 times per second, using a wave shape that has very high harmonic content. The harmonics are of appreciable amplitude even at frequencies as high as 30 MHz, and when radiated from the receiver can cause considerable interference to reception in the amateur bands. While measures to suppress radiation of this nature are required by FCC in current receivers, many older sets have had no such treatment. The interference takes the form of rather unstable, ac-modulated signals spaced at intervals of 15.734 kHz.

Studies have shown that the radiation takes place principally in three ways. In order of importance: (1) from the ac line, through stray coupling to sweep circuits; (2) from the antenna system, through similar coupling; (3) directly from the picture tube and sweep-circuit wiring. Line radiation often can be reduced by bypassing the ac line cord to the chassis at the point of entry, although this is not completely effective in all cases since the coupling may take place outside the

chassis beyond the point where the bypassing is done. Radiation from the antenna is usually suppressed by installing a high-pass filter on the receiver. The direct radiation requires shielding of high-potential leads and, in some receivers, additional bypassing in the sweep circuit; in severe cases, it may be necessary to line the cabinet with screening or similar shielding material.

Incidental radiation of this type from TV and broadcast receivers, when of sufficient intensity to cause serious interference to other radio services (such as amateur), is covered by Part 15 of the FCC rules. When such interference is caused, the user of the receiver is obligated to take steps to eliminate it. The owner of an offending receiver should be advised to contact the source from which the receiver was purchased for appropriate modification of the receiving installation. TV receiver dealers can obtain the necessary information from the set manufacturer.

It is usually possible to reduce interference very considerably, without modifying the TV receiver, simply by having a good amateur-band receiving installation. The principles are the same as those used in reducing "hash" and other noise — use a good antenna, such as the transmitting antenna, for reception; install it as far as possible from ac circuits; use a good feeder system such as a properly balanced two-wire line or coax with the outer conductor grounded; use coax input to the receiver, with a matching circuit if necessary; and check the receiver to make sure that it does not pick up signals or noise with the antenna disconnected.

### Hi-Fi Interference

Since the introduction of stereo and high-fidelity receivers, interference to this type of home-entertainment device has become a severe problem for amateurs. Aside from placing the amateur antenna as far as possible from any hi-fi installation, there is little else that can be done at the amateur's ham shack. Most of the hi-fi gear now being sold has little or no filtering to prevent rf interference. In other words, corrective measures must be done at the hi-fi installation.

### Hi-Fi Gear

Hi-fi gear can consist of a simple amplifier, with record or tape inputs and speakers. The more elaborate installations may have a tape deck, record player, fm and a-m tuners, an amplifier and two or more speakers. These units are usually connected together by means of shielded leads, and in most cases the speakers are positioned some distance from the amplifier via long leads. When such a setup is operated near an amateur station, say within a few hundred feet, there are two important paths through which rf energy can reach the hi-fi installation to cause

interference.

Step number one is to try determining how the interference is getting into the hi-fi unit. If the volume control has no effect on the level of interference or very slight effect, the audio rectification of the amateur signal is taking place past the volume control, or on the output end of the amplifier. This is by far the most common type. It usually means that the amateur signal is being picked up on the speaker leads, or possibly on the ac line, and is then being fed back into the amplifier.

Experience has shown that most of the rf gets into the audio system via the speaker leads or the ac line, mostly the speaker leads. The amateur may find that on testing, the interference will only show up on one or two bands, or all of them. In hi-fi installations speakers are sometimes set up quite some distance from the amplifier. If the speaker leads happen to be resonant near an amateur band in use, there is likely to be an interference problem. The speaker lead will act as a resonant antenna and pick up the rf. One

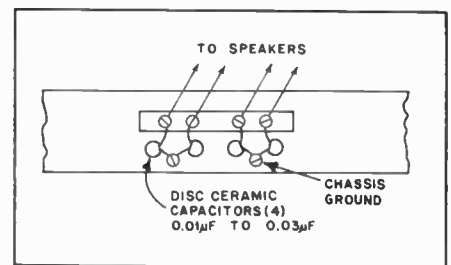


Fig. 29 — The disk capacitors should be mounted directly between the speaker terminals and chassis ground, keeping the leads as short as possible.

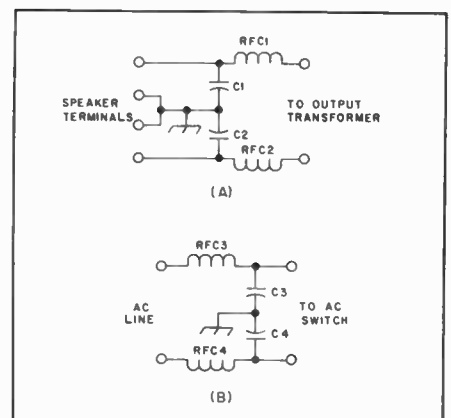


Fig. 30 — At A, the method for additional speaker filter, and at B, filtering and ac-line input. In both cases, these installations should be made directly inside the amplifier chassis, keeping the leads as short as possible. C1, C2 — 0.01- to 0.03- $\mu$ F disk ceramic. C3, C4 — 0.01 disk ceramic, ac type. RFC1 through RFC4 — 24 turns no. 18 enamel-covered wire, close-spaced and wound on a 1/4-inch (6-mm) diameter form (such as a pencil).



easy cure is to bypass the speaker terminals at the amplifier chassis. Use 0.01- to 0.03- $\mu$ F disk capacitors from the speaker terminals directly to chassis ground; see Fig. 29. Try 0.01  $\mu$ F and see if that does the job. In some amplifiers 0.03  $\mu$ F is required to eliminate the rf. Be sure to install bypasses on *all* the speaker terminals. In some instances, it may appear that one of each of the individual speaker terminals is grounded to the chassis. However, some amplifiers have the speaker leads above ground on the low side, for feedback purposes. If you have a circuit diagram of the amplifier you can check, but in the absence of a diagram, bypass all the terminals. If you can get into the amplifier, you can use the system shown in Fig. 30A.

In this system, two rf chokes are installed in series with the speaker leads from the output transformers, or amplifier output, to the speakers. These chokes are simple to make and help keep rf out of the amplifier. In particularly stubborn cases, use shielded wire for the speaker leads, grounding the shields at the amplifier chassis and still using the bypasses on the terminals. When grounding, all chassis used in the hi-fi installation should be bonded together and connected to a good earth ground (such as a water pipe) if at all possible. It has been found that grounding sometimes eliminates the interference. On the other hand, don't be discouraged if grounding doesn't appear to help. Even with the bypassing and filtering grounding may make the difference.

Fig. 30B shows the method for filtering the ac line at the input of the amplifier chassis. The choke dimensions are the same as those given in Fig. 30A. Be sure that the bypasses are rated for ac because the dc types have been known to short out.

### Antenna Pickup

If the hi-fi setup includes an fm installation, and many of them do, there is the possibility of rf getting into the audio equipment by way of the fm antenna. Chances for this method of entry are very good and precautions should be taken here to prevent the rf from getting to the equipment. A TV-type high-pass filter can prove effective in some cases.

### Turntables and Tape Decks

In the more elaborate hi-fi setups, there may be several assemblies connected together by means of patch cords. It is a good idea when checking for RFI to disconnect the units, one at a time, observing any changes in the interference. Not only disconnect the patch cords connecting the pieces together, but also unplug the ac line cord for each item as you make the test. This will help you determine which section is the culprit.

Patch cords are usually, *but not always*,

made of shielded cable. The lines *should* be shielded, which brings up another point. Many commercially available patch cords have poor shields. Some have wire spirally wrapped around the insulation, covering the main lead, rather than braid. This method provides poor shielding and could be the reason for RFI problems.

Record-player tone-arm connections to the cartridge are usually made with small clips. The existence of a loose clip, particularly if oxidation is present, offers an excellent invitation to RFI. Also, the leads from the cartridge and those to the amplifier are sometimes resonant at vhf, providing an excellent receiving antenna for rf. One cure for unwanted rf pickup is to install ferrite beads, one on each cartridge lead. Check all patch-cord connections for looseness or poor solder joints. Inferior connections can cause rectification and subsequent RFI.

Tape decks should be treated the same as turntables. Loose connections and bad solder joints all can cause trouble. Ferrite beads can be slipped over the leads to the recording and play-back pickup heads. Bypassing of the tone-arm or pickup-head leads is also effective, but sometimes it is difficult to install capacitors in the small area available. Disk capacitors (0.001  $\mu$ F) should be used as close to the cartridge or pickup head as possible. Keep the capacitor leads as short as possible.

### Preamplifiers

There are usually one or more preamplifiers used in a hi-fi amplifier. The inputs to these stages can be very susceptible to RFI. Fig. 31 illustrates a typical preamplifier circuit. In this case the leads to the bases of the transistors are treated for RFI with ferrite beads by the addition of RFC2 and RFC4. This is a very effective method for stopping RFI when vhf energy is the source of the trouble.

Within the circuit of a solid-state audio system, a common offender can be the emitter-base junction of a transistor. This junction operates as a forward-biased diode, with the bias set so that a change of base current with signal will produce a linear but amplified change in collector current. Should rf energy reach the junction, the bias could increase, causing nonlinear amplification and distortion as the result. If the rf level is high it can completely block (saturate) a transistor, causing a complete loss of gain. Therefore, it may be necessary to reduce the transmitter power output in order to pinpoint the particular transistor stage that is affected.

In addition to adding ferrite beads it may be necessary to bypass the base of the transistor to chassis ground, C1 and C2, Fig. 31. A suitable value is 100 pF, and keep the leads short! As a general rule, the capacitor value should be as large as possible without degrading the high-frequency response of the amplifier. Values up to 0.001  $\mu$ F can be used. In severe cases, a series inductor (RFC1 and RFC3) may be required, such as the Ohmite Z-50 or Z-144, or their equivalents (7 and 1.8  $\mu$ H, respectively). Fig. 31 shows the correct placement for an inductor, bypass capacitor, and ferrite bead. Also, it might help to use a ferrite bead in the plus-B lead to the preamplifier stages (RFC5 in Fig. 31). Keep in mind that Fig. 31 represents only one preamplifier of a stereo set. *Both* channels may require treatment.

### FM Tuners

There is often an fm tuner used in a hi-fi installation. Much of the interference to tuners is caused by fundamental overloading of the first stage (or stages) of the tuner, effected by the amateur's signal. The cure is the installation of a high-pass

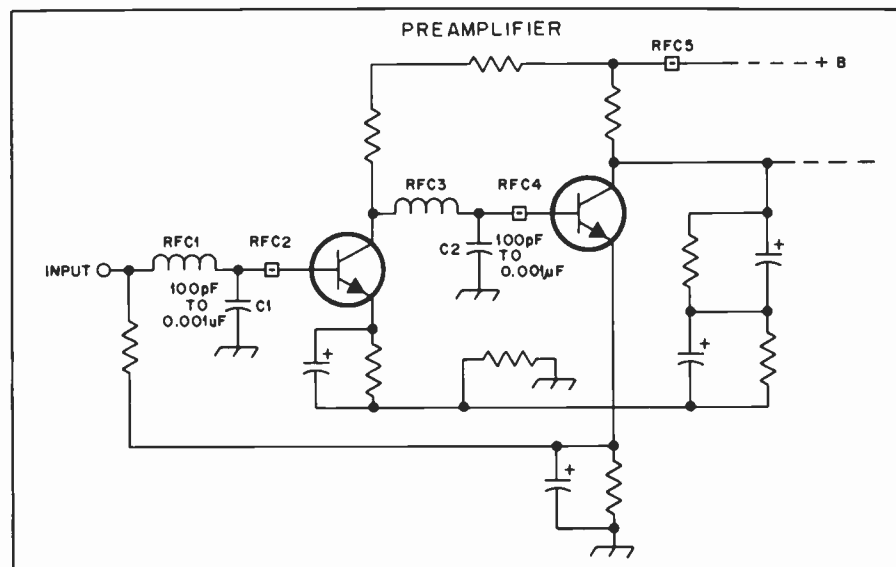


Fig. 31 — Typical circuit of a solid-state preamplifier.

filter, the same type used for TVI. The filter should be installed as close as possible to the antenna input of the tuner. The high-pass filter will attenuate the amateur *fundamental* signal, thus preventing overloading of the front end.

### Shielding

Lack of shielding on the various components in a hi-fi installation can permit rf to get into the equipment. Many units have no bottom plates, or are installed in plastic cases. One easy method of providing shielding is to use aluminum foil. Make sure the foil doesn't short circuit the components, and connect it to chassis ground.

### Interference with Standard Broadcasting

Interference with a-m broadcasting usually falls into one or more rather well-defined categories. An understanding of the general types of interference will avoid much cut-and-try in finding a cure.

### Transmitter Defects

Out-of-band radiation is something that must be cured at the transmitter. Parasitic oscillations are a frequently unsuspected source of such radiations, and no transmitter can be considered satisfactory until it has been thoroughly checked for both low- and high-frequency parasitics. Very often parasitics show up only as transients, causing key clicks in cw transmitters and "splashes" or "burps" on modulation peaks in a-m transmitters. Methods for detecting and eliminating parasitics are discussed in the transmitter chapter.

In cw transmitters the sharp make and break that occurs with unfiltered keying causes transients that, in theory, contain frequency components through the entire radio spectrum. Practically, they are often strong enough in the immediate vicinity of the transmitter to cause serious interference to broadcast reception. Key clicks can be eliminated by the methods detailed in the chapter on keying.

BCI is frequently made worse by radiation from the power wiring or the rf transmission line. This is because the signal causing the interference, in such cases, is radiated from wiring that is nearer the broadcast receiver than the antenna itself. Much depends on the method used to couple the transmitter to the antenna, a subject that is discussed in the chapters on transmission lines and antennas. If it is at all possible the antenna itself should be placed so that it is not in close proximity to house wiring, telephone and power lines, and similar conductors.

### The BC Set

Most present day receivers use solid-state active components, rather than tubes. A large number of the receivers in use are battery powered. This is to the amateur's advantage because much of the

bc interference an amateur encounters is due to ac line pickup. In the case where the bc receiver is powered from the ac line, whether using tube or solid-state components, the amount of rf pickup must be reduced or eliminated. A line filter such as is shown in Fig. 28 often will help accomplish this. The values used for the coils and capacitors are in general not critical. The effectiveness of the filter may depend considerably on the ground connection used, and it is advisable to use a short ground lead to a cold-water pipe if at all possible. The line cord from the set should be bunched up to minimize the possibility of pick-up on the cord. It may be necessary to install the filter inside the receiver, so that the filter is connected between the line cord and the set wiring, in order to get satisfactory operation.

### Cross-Modulation

With phone transmitters, there are occasionally cases where the voice is heard whenever the broadcast receiver is tuned to a bc station, but there is no interference when tuning between stations. This is cross-modulation, a result of rectification in one of the early stages of the receiver. Receivers that are susceptible to this trouble usually also get a similar type of interference from regular broadcasting if there is a strong local bc station and the receiver is tuned to some *other* station.

The remedy for cross modulation in the receiver is the same as for images and oscillator-harmonic response — reduce the strength of the amateur signal at the receiver by means of a line filter.

The trouble is not always in the receiver, since cross modulation can occur in any nearby rectifying circuit — such as a poor contact in water or steam piping, gutter pipes, and other conductors in the strong field of the transmitting antenna — external to both receiver and transmitter. Locating the cause may be difficult, and is best attempted with a battery-operated portable broadcast receiver used as a "probe" to find the spot where the interference is most intense. When such a spot is located, inspection of the metal structures in the vicinity should indicate the cause. The remedy is to make a good electrical bond between the two conductors having the poor contact.

### Handling BCI Cases

Assuming that your transmitter has been checked and found to be free from spurious radiations, get another amateur to operate your station, if possible, while you make the actual check on the interference yourself. The following procedure should be used.

Tune the receiver through the broadcast band to see whether the interference tunes like a regular bc station. If so, image or oscillator-harmonic response is the cause. If there is interference only when a bc station is tuned in, but not between

stations, the cause is cross-modulation. If the interference is heard at all settings of the tuning dial, the trouble is pickup in the audio circuits. In the latter case, the receiver's volume control may or may not affect the strength of the interference, depending on the means by which your signal is being rectified.

Having identified the cause, explain it to the set owner. It is a good idea to have a line filter with you, equipped with enough cord to replace the set's line cord, so it can be tried then and there. If it does not eliminate the interference, explain to the set owner that there is nothing further that can be done without modifying the receiver. Recommend that the work be done by a competent service technician, and offer to advise the service man on the cause and remedy. Don't offer to work on the set yourself, but if you are asked to do so use your own judgment about complying; set owners sometimes complain about the overall performance of the receiver afterward, often without justification. If you work on it, take it to your station so the effect of changes you make can be seen. Return the receiver promptly when you have finished.

### Miscellaneous Types of Interference

The operation of amateur phone transmitters occasionally results in interference on telephone lines and in audio amplifiers used in public-address work, plus other audio devices. The cause is rectification of the signal in an audio circuit.

### Organs

The electronic organ is an RFI problem area. All of the techniques outlined for hi-fi gear hold true in getting rid of RFI in an organ. Two points should be checked — the speaker leads and the ac line. Many organ manufacturers have special servicemen's guides for taking care of RFI. However, to get this information you or the organ owner must contact the manufacturer, not the dealer or distributor. Don't accept the statement from a dealer or serviceman that there is nothing that can be done about the interference.

### P-A Systems

The cure for RFI in p-a systems is almost the same as that for hi-fi gear. The one thing to watch for is rf on the leads that connect the various stations in a p-a system. These leads should be treated the same as speaker *leads* and bypassing and filtering should be done at *both* ends of the lines. Also, watch for ac-line pickup of rf.

### Telephone Interference

Telephone interference may be cured by connecting a bypass capacitor (about 0.001  $\mu$ F) across the microphone unit in the telephone handset. The telephone companies have capacitors for this pur-

pose. When such a case occurs, get in touch with the repair department of the phone company, giving the particulars. Section 500-150-100 of the Bell System Practices *Plant Series* gives detailed instructions. This section discusses causes and cures of telephone interference from radio signals. It points out that interference can come from corroded connections, unterminated loops, and other sources. It correctly points out that the rf can be picked up on the drop wire coming into the house, and also on the wiring within the house, but the rf detection usually occurs inside the phone. The detection usually takes place at the varistors in the compensation networks, and/or at the receiver noise suppressor and the carbon microphone. But interference suppression should be handled two ways: Prevent the rf from getting to the phone, and prevent it from being rectified.

The telephone companies (Bell System) have two devices for this purpose. The first is a 40BA capacitor, which is installed at the service entrance protector, and the second is the 1542A inductor, which is installed at the connector block. According to the practices manual, the 40BA bypasses rf picked up on the drop wire coming into the house from the phone, and the 1542A suppresses rf picked up on the inside wiring. These are mentioned because in very stubborn cases they may be necessary. But the telephone should be modified first.

Since there are several different series of phones, they will be discussed separately:

**500 series** — These are the desk and wall phones most commonly in use. They come in several different configurations, but all use 425-series compensation network. The letter designation can be A, B, C, D, E, F, G or K, and all these networks contain varistors. The network should be replaced with a 425J, in which the varistors are replaced by resistors. Also, 0.01- $\mu$ F disk-ceramic capacitors should be placed across the receiver suppressor. The suppressor is a diode across the receiver terminals. The carbon microphone in the handset should be bypassed with a 0.01- $\mu$ F ceramic capacitor.

**Series 1500, 1600, 1700** — These are the "Touch-Tone" phones, and the cure is similar to that for the 500 series, except that the network is a 4010B or -D, and should be replaced with a 4010E.

**Trimline series** — These are the "Princess" series phones. The practice manual says that these should be modified by installing bypass capacitors across *all* components in the set which may act as demodulators. This statement is rather vague, but evidently the telephone company is aware of a solution.

At the end of section 500-150-100 is an ordering guide for special components and sets, as follows:

*Ordering Guide*  
Capacitor, 40BA  
Inductor, 1542A

-49 Gray, -50 Ivory  
Set, Telephone, -rf Modified  
Set, Telephone Hand, 220A, -rf Modified  
Set, Telephone Hand, 2220B, -rf Modified  
Set, Hand G, -rf Modified  
Dial — (Touch-Tone dial only), -rf Modified.

The type "G" handset is the one used with the 500 and Touch-Tone series phones. Also, Mountain Bell has put out an "Addendum 500-150-100MS, Issue A, January 1971" to the practices manual, which states that items for rf modified phones should be ordered on nonstock form 3218, as follows:

(Telephone Set type)  
Modified for BSP 500-150-100  
for Radio Signal Suppression

### The FCC's Role

In response to the many hundreds of thousands of RFI-related complaints it has received in recent years, the FCC has produced a booklet designed to show how to solve common RFI problems before they become serious. Entitled *How to Identify and Resolve Radio-TV Interference Problems*, it is available for \$1.50 from Consumer Information Center, Dept. 051F, Pueblo, CO 81009. Make check payable to Superintendent of Documents. The ARRL publication *Radio Frequency Interference* which sells for \$3, covers all aspects of RFI and includes the complete FCC booklet.



# Test Equipment and Measurements



**M**easurement and testing seemingly go hand in hand, but it is useful to make a distinction between “measuring” and “test” equipment. The former is commonly considered to be capable of giving a meaningful quantitative result. For the latter a simple indication of “satisfactory” or “unsatisfactory” may suffice; in any event, the accurate calibration associated with real measuring equipment is seldom necessary, for simple test apparatus.

Certain items of measuring equipment that are useful to amateurs are readily available in kit form, at prices that represent a genuine saving over the cost of

identical parts. Included are volt-ohm-milliammeter combinations, vacuum-tube and transistor voltmeters, oscilloscopes and the like. The coordination of electrical and mechanical design, components, and appearance make it far preferable to purchase such equipment than to attempt to build one's own.

However, some test gear is either not available or can easily be built. This chapter considers the principles of the more useful types of measuring equipment and concludes with the descriptions of several pieces that not only can be built satisfactorily at home but which will facilitate operation of the amateur station.

### The Direct-Current Instrument

In measuring instruments and test equipment suitable for amateur purposes the ultimate “readout” is generally based on a measurement of direct current. A meter for measuring dc uses electromagnetic means to deflect a pointer over a calibrated scale in proportion to the current flowing through the instrument.

In the *D'Arsonval* type a coil of wire, to which the pointer is attached, is pivoted between the poles of a permanent magnet. When current flows through the coil it sets up a magnetic field that interacts with the field of the magnet to cause the coil to turn. The design of the instrument is usually such as to make the pointer deflection directly proportional to the current.


A less expensive type of instrument is the *moving-vane* type, in which a pivoted soft-iron vane is pulled into a coil of wire by the magnetic field set up when current flows through the coil. The farther the vane extends into the coil the greater the

magnetic pull on it, for a given change in current. This type of instrument thus does not have “linear” deflection — the intervals of equal current are crowded together at the low-current end and spread out at the high-current end of the scale.
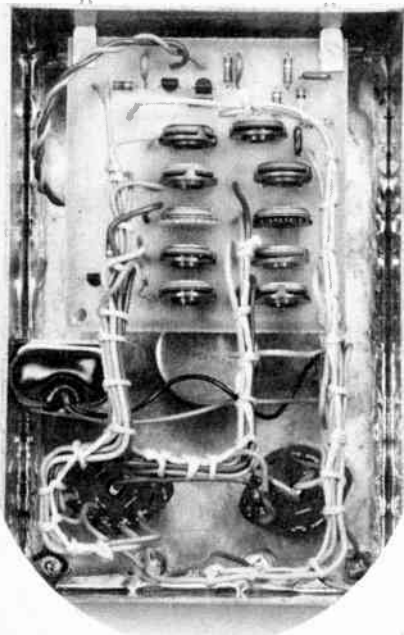
### Current Ranges

The *sensitivity* of an instrument is usually expressed in terms of the current required for full-scale deflection of the pointer. Although a very wide variety of ranges is available, the meters of interest in amateur work have basic “movements” which will give maximum deflection with currents measured in microamperes or milliamperes. They are called *microammeters* and *milliammeters*, respectively.

Thanks to the relationships between current, voltage and resistance expressed by Ohm's Law, it becomes possible to use a single low-range instrument — e.g., 1 milliampere or less full-scale pointer deflection — for a variety of direct-current measurements. Through its ability to measure current, the instrument can also be used indirectly to measure voltage. Likewise, a measurement of *both* current



You can build this FET Volt-Ohmmeter with the information that appears in this chapter. See page 16-5.



and voltage will obviously yield a value of resistance. These measurement functions are often combined in a single instrument — the *volt-ohm-milliammeter* or "VOM," a multirange meter that is one of the most useful pieces of measuring and test equipment an amateur can possess.

### Accuracy

The accuracy of a dc meter of the D'Arsonval type is specified by the manufacturer. A common specification is "2 percent of full scale," meaning that a 0-100 microammeter, for example, will be correct to within 2 microamperes at any part of the scale. There are very few cases in amateur work where accuracy greater than this is needed. However, when the instrument is part of a more complex measuring circuit, the design and components of which all can cause error, the overall accuracy of the complete device is always less.

### Extending the Current Range

Because of the way current divides between two resistances in parallel, it is possible to increase the range (more specifically, to decrease the sensitivity) of a dc micro- or milliammeter to any desired extent. The meter itself has an inherent resistance — its *internal resistance* — which determines the full-scale current through it when its rated voltage is applied. (This rated voltage is of the order of a few millivolts.) By connecting an external resistance in parallel with the internal resistance, as in Fig. 1, the current will divide between the two, with the meter responding only to that part of the current which flows through the internal resistance of its movement. Thus it reads only part of the total current; the effect is to make more total current necessary for a full-scale meter reading. The added resistance is called a shunt.

It is necessary to know the meter's internal resistance before the required value for a shunt can be calculated. It may vary from a few ohms to a few hundred, with the higher resistance values associated with higher sensitivity. When known, it can be used in the formula below to determine the required shunt for a given current multiplication:

$$R = \frac{R_m}{n - 1}$$

where:

R = the shunt

$R_m$  = internal resistance

n = the factor by which the original meter scale is to be multiplied

Quite often the internal resistance of a particular meter will be unknown. This is usually the case when the meter is purchased at a flea market or is obtained from a commercial piece of equipment. Unfortunately, the internal resistance of the meter can not be directly measured with a VOM or VTVM without risk of

injury to the meter movement. In most cases, the currents in the measuring equipment are high enough to damage the delicate meter movement.

Fig. 2 illustrates a method that can be used to safely determine the internal resistance of a meter. A calibrated meter capable of measuring the same current as the unknown meter is required. The system works as follows: S1 is placed in the open position and R2 is set for maximum resistance. A supply of constant voltage is connected to the terminals + and - (a battery will work fine) and R2 is adjusted so that the unknown meter reads exactly full scale. Note the current shown on M2. Close S1 and alternately adjust R1 and R2 so that the unknown meter (M1) reads exactly half scale and the known meter (M2) reads the same value as in the step above. At this point the current in the circuit is divided in half. Half of the current flows through M1 and half through R1. To determine the internal resistance of the meter simply open S1 and read the resistance of R1 with a VTVM, VOM or digital volt-ohmmeter.

The values for R1 and R2 will depend on the meter sensitivity and the voltage of the supply. The maximum resistance value for R1 should be approximately twice the expected internal resistance of the meter. For highly sensitive meters (100  $\mu$ A and less) 1000 ohms should be adequate. For less sensitive meters 100 ohms should suffice.

The value for minimum resistance at R2 can be calculated using Ohm's Law. For example, if the meter is a 0-1 mA type and the supply is a 1.5-volt battery, the minimum resistance required at R2 will be

$$R_2 = \frac{1.5}{0.001}$$

$$R_2(\text{min}) = 1500 \text{ ohms}$$

In practice a 2000- or 2500-ohm potentiometer would be used.

### Making Shunts

Homemade shunts can be constructed from any of various special kinds of resistance wire, or from ordinary copper wire if no resistance wire is available. The copper wire table in this handbook gives the resistance per 1000 feet (305 m) for various sizes of copper wire. After computing the resistance required, determine the smallest wire size that will carry the full-scale current (250 circular mils per ampere is a satisfactory figure for this purpose). Measure off enough wire to provide the required resistance. A 1- or 2-watt carbon resistor makes an excellent form on which to wind the wire.

### The Voltmeter

If a large resistance is connected in series with a current-reading meter, as in Fig. 3, the current multiplied by the resistance will be the voltage drop across

the resistance. This is known as a *multiplier*. An instrument used in this way is calibrated in terms of the voltage drop across the multiplier resistor and is called a *voltmeter*.

### Sensitivity

Voltmeter sensitivity is usually expressed in *ohms per volt*, meaning that the meter *full-scale* reading multiplied by the sensitivity will give the total resistance of the voltmeter. For example, the resistance of a 1000-ohms-per-volt voltmeter is 1000 times the full-scale calibration voltage, and by Ohm's Law the current required for full-scale deflection is 1 milliampere. A sensitivity of 20,000 ohms per volt, a commonly used value, means that the instrument is a 50-microampere meter.

The higher the resistance of the

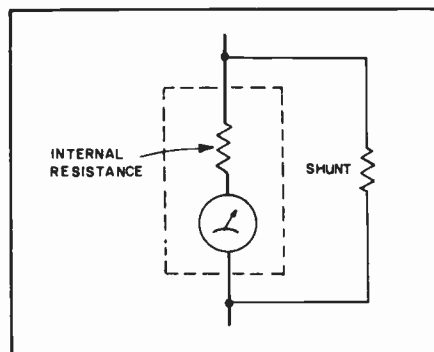


Fig. 1 — Use of a shunt to extend the calibration range of a current-reading instrument.

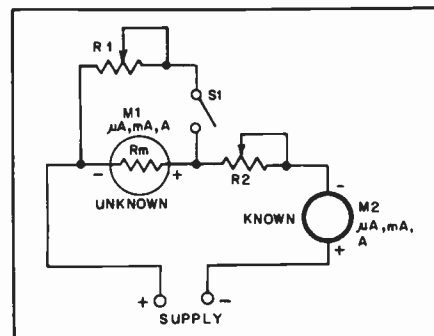


Fig. 2 — A safe method for determining the internal resistance of a meter.

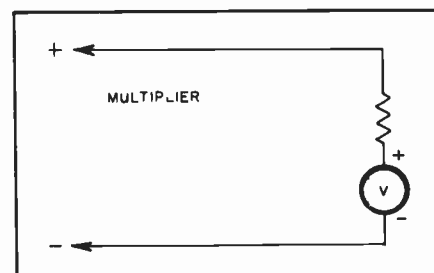


Fig. 3 — A voltmeter is a current-indicating instrument in series with a high resistance, the "multiplier."

voltmeter, the more accurate the measurements, especially in high-resistance circuits. Current flowing through the voltmeter will cause a change in the voltage between the points where the meter is connected, compared with the voltage with the meter absent. This is illustrated in Fig. 4.

### Multipliers

The required multiplier resistance is found by dividing the desired full-scale voltage by the current, in amperes, required for full-scale deflection of the

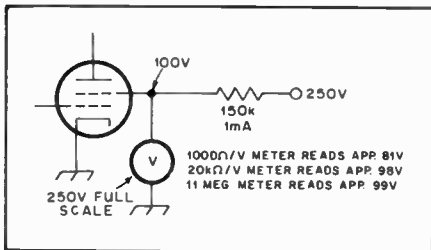


Fig. 4 — Effect of voltmeter resistance on accuracy of readings. It is assumed that the dc resistance of the screen circuit is constant at 100 kilohms. The actual current and voltage without the voltmeter connected are 1 mA and 100 volts. The voltmeter readings will differ because the different types of meters draw different amounts of current through the 150-kilohm resistor.

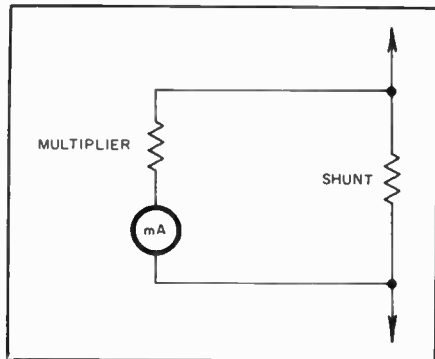


Fig. 5 — Voltmeter method of measuring current. This method permits using relatively large values of resistance in the shunt, standard values of fixed resistors frequently being usable. If the multiplier resistance is 20 (or more) times the shunt resistance, the error in assuming that all the current flows through the shunt will not be of consequence in most practical applications.

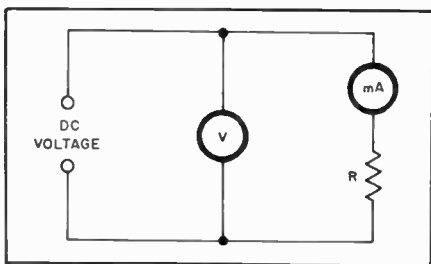


Fig. 6 — Measurement of power requires both current and voltage measurements; once these values are known the power is equal to the product  $P = EI$ . The same circuit can be used for measurement of an unknown resistance.

meter alone. Strictly, the internal resistance of the meter should be subtracted from the calculated value but this is seldom necessary (except perhaps for very low ranges), since the meter resistance will be negligibly small compared with the multiplier resistance. An exception is when the instrument is already a voltmeter and is provided with an internal multiplier, in which case the multiplier resistance required to extend the range is  $R = R_m (n - 1)$

where

$R_m$  = total resistance of the instrument itself

$n$  = factor by which the scale is to be multiplied

For example, if a 1000-ohms-per-volt voltmeter having a calibrated range of 0-10 volts is to be extended to 1000 volts,  $R_m$  is  $1000 \times 10 = 10,000$  ohms,  $n$  is  $1000/10 = 100$ , and  $R = 10,000 (100 - 1) = 990,000$  ohms.

When extending the range of a voltmeter or converting a low-range meter into a voltmeter, the rated accuracy of the instrument is retained only when the multiplier resistance is precise. Precision wire-wound resistors are used in the multipliers of high-quality instruments. These are relatively expensive, but the home constructor can do quite well with 1-percent tolerance composition resistors. They should be "derated" when used for this purpose — that is, the actual power dissipated in the resistor should not be more than 1/4 to 1/2 the rated dissipation — and care should be used to avoid overheating the body of the resistor when soldering to the leads. These precautions will help prevent permanent change in the resistance of the unit.

Ordinary composition resistors are generally furnished in 10- or 5-percent tolerance ratings. If possible errors of this order can be accepted, resistors of this type may be used as multipliers. They should be operated below the rated power dissipation figure, in the interests of long-time stability.

### DC Measurement Circuits: the Voltmeter

A current-measuring instrument should have very low resistance compared with the resistance of the circuit being measured; otherwise, inserting the instrument will cause the current to differ from its value with the instrument out of the circuit. The resistance of many circuits in radio equipment is high and the circuit operation is affected little, if at all, by adding as much as a few hundred ohms in series. In such cases the voltmeter method of measuring current, shown in Fig. 5, is frequently convenient. A voltmeter (or low-range milliammeter provided with a multiplier and operating as a voltmeter) having a full-scale voltage range of a few volts is used to measure the voltage drop across a suitable value of resistance acting as a shunt.

The value of shunt resistance must be calculated from the known or estimated maximum current expected in the circuit (allowing a safe margin) and the voltage required for full-scale deflection of the meter with its multiplier.

### Power

Power in direct-current circuits is determined by measuring the current and voltage. When these are known, the power is equal to the voltage in volts multiplied by the current in amperes. If the current is measured with a milliammeter, the reading of the instrument must be divided by 1000 to convert it to amperes.

The setup for measuring power is shown in Fig. 6, where  $R$  is any dc "load," not necessarily an actual resistor.

### Resistance

Obviously, if both voltage and current are measured in a circuit such as that in Fig. 6 the value of resistance  $R$  (in case it is unknown) can be calculated from Ohm's Law. For accurate results the internal resistance of the ammeter or milliammeter, mA, should be very low compared with the resistance,  $R$ , being measured, since the voltage read by the voltmeter,  $V$ , is the voltage across mA and  $R$  in series. The instruments and the dc voltage should be chosen so that the readings are in the upper half of the scale, if possible, since the percentage error is less in this region.

### The Ohmmeter

Although Fig. 6 suffices for occasional resistance measurements, it is inconvenient when frequent measurements over a wide range of resistance are to be made. The device generally used for this purpose is the *ohmmeter*. This consists fundamentally of a voltmeter (or milliammeter, depending on the circuit used) and a small battery, the meter being calibrated so the value of an unknown resistance can be read directly from the scale. Typical ohmmeter circuits are shown in Fig. 7. In the simplest type, shown in Fig. 7 A, the meter and battery are connected in series with the unknown resistance. If a given deflection is obtained with terminals A-B shorted, inserting the resistance to be measured will cause the meter reading to decrease. When the resistance of the voltmeter is known, the following formula can be applied:

$$R = \frac{eR_m}{E} - R_m$$

where

$R$  = resistance to be found

$e$  = voltage applied (A-B shorted)

$E$  = voltmeter reading with  $R$  connected, and

$R_m$  = resistance of the voltmeter.

The circuit of Fig. 7A is not suited to measuring low values of resistance (below a hundred ohms or so) with a high-resistance voltmeter. For such measure-

ments the circuit of Fig. 7B can be used. The unknown resistance is

$$R = \frac{I_2 R_m}{I_1 - I_2}$$

The formula is based on the assumption that the current in the complete circuit will be essentially constant whether or not the "unknown" terminals are short-circuited. This requires that  $R_1$  be very large compared with  $R_m$  e.g., 300 ohms for a 1-mA meter having an internal resistance of perhaps 50 ohms. A 3-volt battery would be necessary in this case in order to obtain a full-scale deflection with the "unknown" terminals open.  $R_1$  can be an adjustable resistor, to permit setting the open-terminals current to exact full scale.

A third circuit for measuring resistance is shown in Fig. 7C. In this case a high-resistance voltmeter is used to measure the voltage drop across a reference resistor,  $R_2$ , when the unknown resistor is connected so that current flows through it,  $R_2$  and the battery in series. By suitable choice of  $R_2$  (low values for low-resistance, high values for high-resistance unknowns) this circuit will give equally good results on all resistance values in the range from one ohm to several megohms, provided that the voltmeter resistance,  $R_m$ , is always very high (50 times or more) compared with the resistance of  $R_2$ . A 20,000-ohm-per-volt instrument (50- A movement) is generally used. Assuming that the current through the voltmeter is negligible compared with the current through  $R_2$ , the formula for the unknown is

$$R = \frac{eR_2}{E} - R_2$$

where

$R$  and  $R_2$  are as shown in Fig. 7C.

$e$  = the voltmeter reading with A-B open circuited

$E$  = voltmeter reading with  $R$  connected

The "zero adjuster,"  $R_1$ , is used to set the voltmeter reading exactly to full scale when the meter is calibrated in ohms. A 10,000-ohm variable resistor is suitable with a 20,000-ohms-per-volt meter. The battery voltage is usually 3 volts for ranges up to 100,000 ohms or so and 6 volts for higher ranges.

### Bridge Circuits

An important class of measurement circuits is the bridge. A desired result is obtained by balancing the voltages at two different points in the circuit against each other so that there is zero potential difference between them. A voltmeter bridged between the two points will read zero (*null*) when this balance exists, but will indicate some definite value of voltage when the bridge is not balanced.

Bridge circuits are useful both on direct current and on ac of all frequencies. The majority of amateur applications are at radio frequencies, as shown later in this chapter. However, the principles of bridge

operation are most easily introduced in terms of dc, where the bridge takes its simplest form.

### The Wheatstone Bridge

The simple resistance bridge, known as the Wheatstone bridge, is shown in Fig. 8. All other bridge circuits — some of which are rather elaborate, especially those designed for ac — derive from this. The four resistors,  $R_1$ ,  $R_2$ ,  $R_3$ , and  $R_4$  shown in A, are known as the bridge *arms*. For the voltmeter reading to be zero, the voltages across  $R_3$  and  $R_4$  in series must add algebraically to zero; that is,  $E_1$  must equal  $E_2$ .  $R_1R_3$  and  $R_2R_4$  form voltage dividers across the dc source, so that if

$$\frac{R_3}{R_1 + R_3} = \frac{R_4}{R_2 + R_4}$$

$$E_1 = E_2$$

The circuit is customarily drawn as shown at 8B when used for resistance measurement. The equation above can be rewritten

$$R_x = R_s \frac{R_2}{R_1}$$

to find  $R_x$ , the unknown resistance.  $R_1$  and  $R_2$  are frequently made equal; then the calibrated adjustable resistance (the *standard*),  $R_s$ , will have the same value as  $R_x$  when  $R_s$  is set to show a null on the voltmeter.

Note that the resistance *ratios*, rather than the actual resistance values, determine the voltage balance. However, the values do have important practical effects on the sensitivity and power consumption. The *bridge sensitivity* is the readiness with which the meter responds to small amounts of unbalance about the null point; the "sharper" the null the more accurate the setting of  $R_s$  at balance.

The Wheatstone bridge is rarely used by amateurs for resistance measurement, the ohm-meter being the favorite instrument for that purpose. However, it is worthwhile to understand its operation because it is the basis of more complex bridges.

### Electronic Voltmeters

It has been pointed out that for many purposes the resistance of a voltmeter must be extremely high in order to avoid "loading" errors caused by the current that necessarily flows through the meter. This tends to cause difficulty in measuring relatively low voltages (under perhaps 1000 volts) because a meter movement of given sensitivity takes a progressively smaller multiplier resistance as the voltage range is lowered.

The voltmeter resistance can be made independent of the voltage range by using vacuum tubes or field-effect transistors as electronic dc amplifiers between the circuit being measured and the actual indicator, which is usually a conventional

meter movement. As the input resistance of the electronic devices is extremely high — hundreds of megohms — they have essentially no loading effect on the circuit to which they are connected. They do, however, require a closed dc path in their input circuits (although this path can have very high resistance) and are limited in the amplitude of voltage that their input circuits can handle. Because of this, the

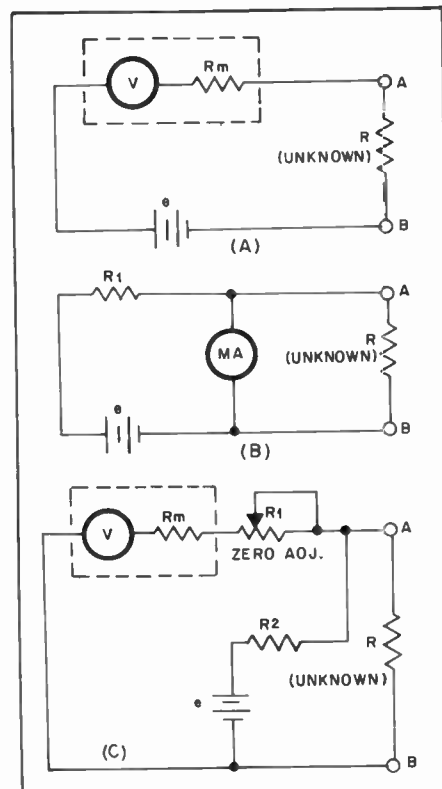


Fig. 7 — Ohmmeter circuits. Values are discussed in the text.

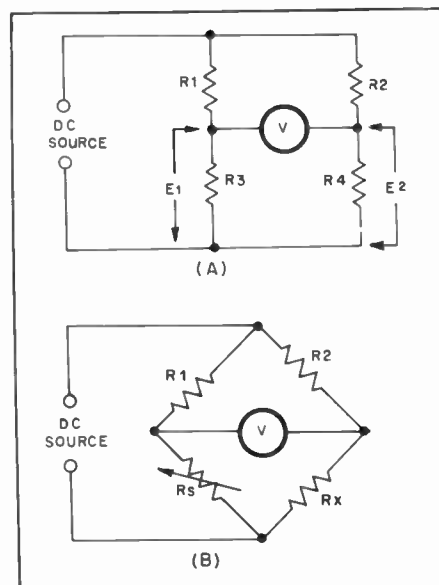


Fig. 8 — The Wheatstone bridge circuit. It is frequently drawn as at (B) for emphasizing its special function.



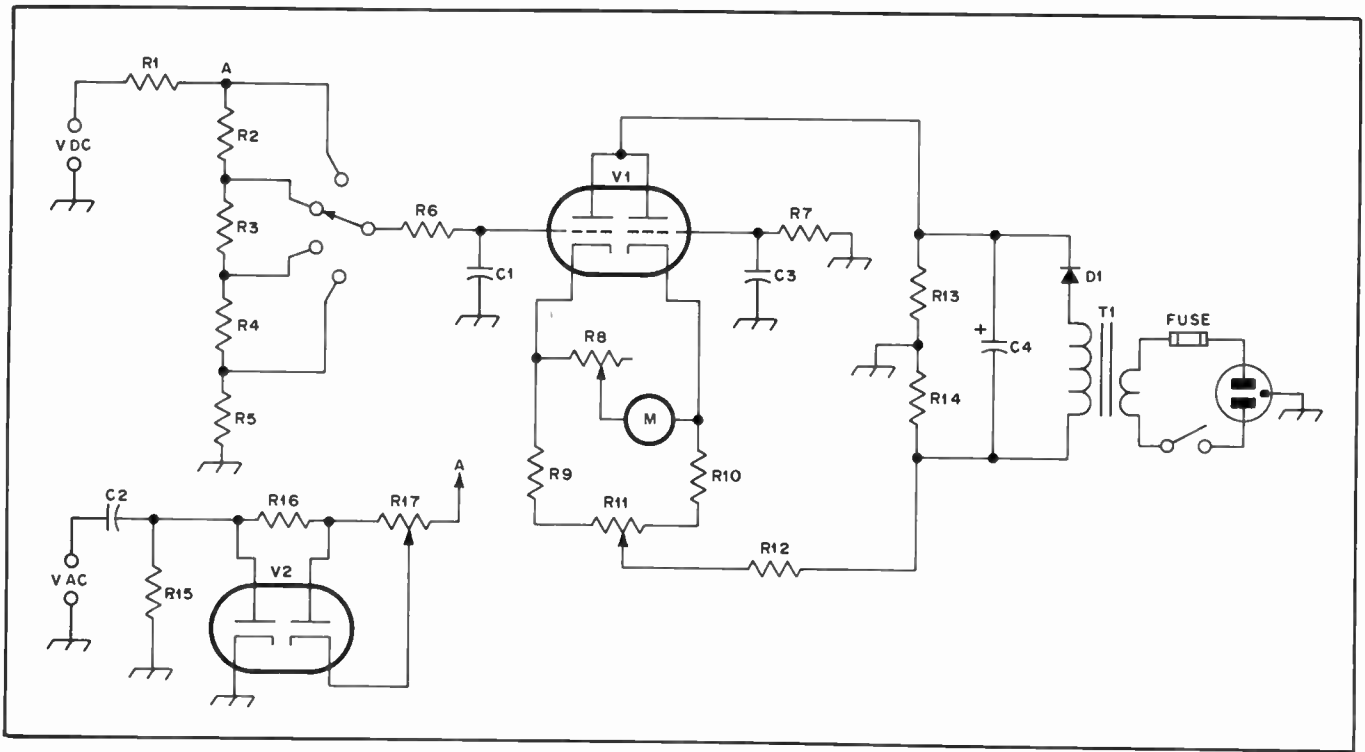


Fig. 9— Vacuum-tube voltmeter circuit.  
 C1, C3— 0.002- to 0.005- $\mu$ F mica.  
 C2— 0.01  $\mu$ F, 1000 to 2000 volts, paper or mica.  
 C4— 16  $\mu$ F, 150 V electrolytic.  
 D1— 400 PRV rectifier.  
 M— 0-200 microammeter.  
 R1— 1 m $\Omega$ , 1/2 watt.  
 R2-R5, incl.— To give desired voltage ranges, totaling 10 m $\Omega$ .

R6, R7— 2 to 3 M $\Omega$ .  
 R8— 10-k $\Omega$ , variable (calibrate).  
 R9, R10— 2000 to 3000 ohms.  
 R11— 5000- to 10,000-ohm control (zero set).  
 R12— 10 to 50 k $\Omega$ .  
 R13, R14— Approx 25 k $\Omega$ . A 50-k $\Omega$  slider-type wire-wound can be used.

R15— 10 M $\Omega$ .  
 R16— 3 M $\Omega$ .  
 R17— 10-M $\Omega$  variable.  
 T1— 120-V, 15-mA transformer (only secondary shown).  
 V1— Dual triode, 12AU7A.  
 V2— Dual diode, 6AL5.

device actually measures a small voltage across a portion of a high-resistance voltage divider connected to the circuit being measured. Various voltage ranges are obtained by appropriate taps on the voltage divider.

In the design of electronic voltmeters it has become practically standard to use a

voltage divider having a resistance of 10 megohms, tapped as required, in series with a 1-megohm resistor incorporated in a probe that makes the actual contact with the "hot" side of the circuit under measurement. The total voltmeter resistance, including probe, is therefore 11 megohms. The probe resistor serves to isolate the voltmeter circuit from the "active" circuit.

#### A Vacuum-Tube Voltmeter

A typical vacuum-tube voltmeter (VTVM) circuit is given in Fig. 9. A dual triode, V1, is arranged so that, with no voltage applied to the left-hand grid, equal currents flow through both sections. Under this condition the two cathodes are at the same potential and no current flows through M. The currents can be adjusted to balance by potentiometer, R11, which takes care of variations in the tube sections and in the values of cathode resistors R9 and R10. When a positive dc voltage current through that tube section increases, so the current balance is upset and the meter indicates. The sensitivity of the meter is regulated by R8, which serves to adjust the calibration. R12, common to the cathodes of both tube sections, is a feedback resistor that stabilizes the system and makes the readings linear. R6 and C1 form a filter for any ac component that may be present, and R6 is balanced

by R7 connected to the grid of the second tube section.

Values to be used in the circuit depend considerably on the supply voltage and the sensitivity of the meter, M. R12 and R13-R14, should be adjusted by trial so that the voltmeter circuit can be brought to balance, and to give full-scale deflection on M with about 3 volts applied to the left-hand grid (the voltage chosen for this determines the lowest voltage range of the instrument). The meter connections can be reversed to read voltages that are negative with respect to ground. The small circuit associated with V2 is for ac measurements.

As compared with conventional dc instruments, the VTVM has the disadvantages of requiring a source of power for its operation, and generally must have its "cold" terminal grounded in order to operate reliably. It is also somewhat susceptible to erratic readings from rf pickup when used in the vicinity of a transmitter, and in such cases may require shielding. However, its advantages outweigh these disadvantages in many applications.

#### An FET Volt-ohmmeter

The circuit shown in Fig. 11 makes use of two field-effect transistors in a balanced circuit. Since no two active devices have exactly the same characteristics,



Fig. 10— Exterior view of the FET Volt-ohmmeter.



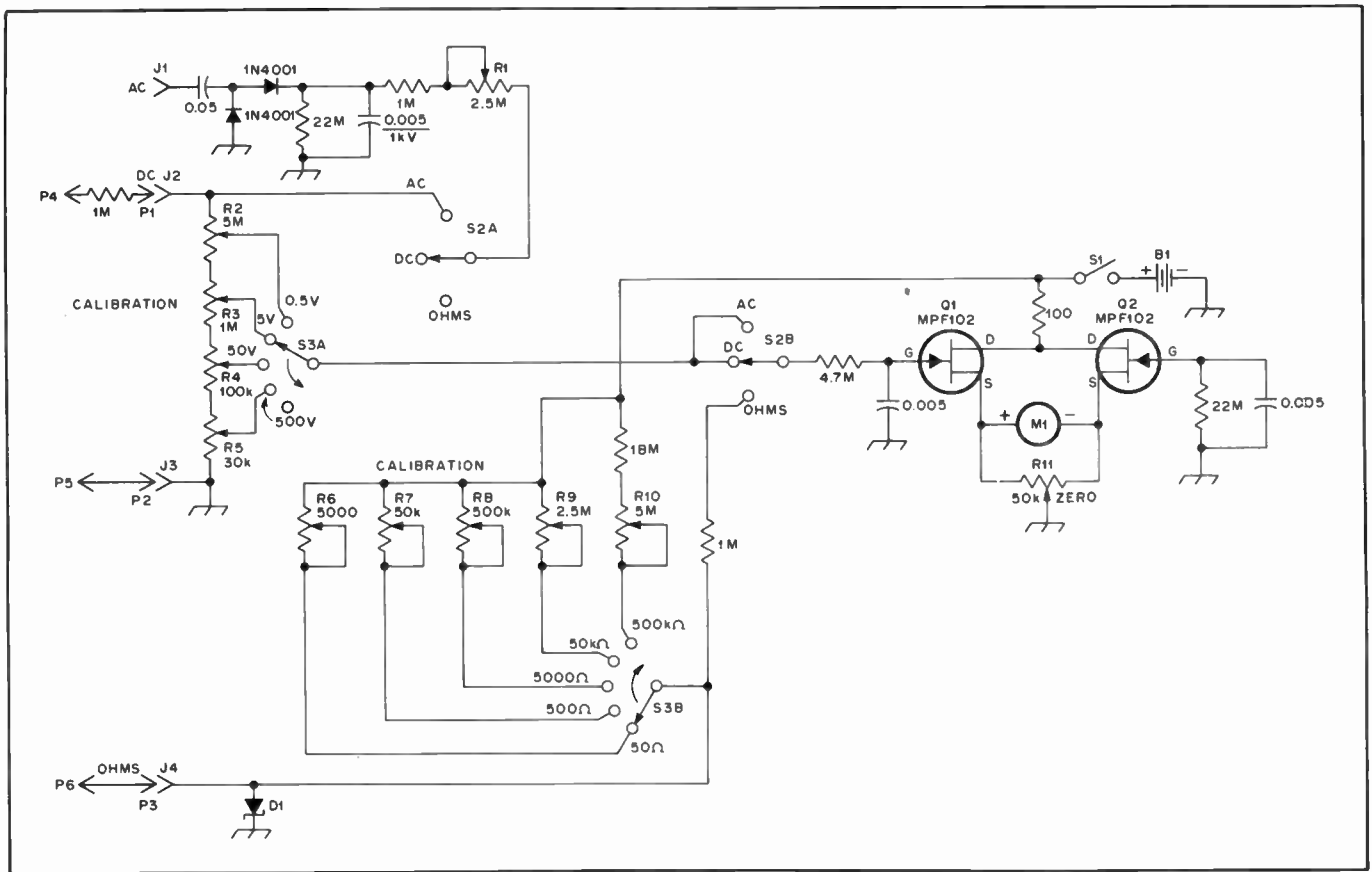


Fig. 11 — Schematic diagram of the FET VOM. All resistors are 1/4-watt carbon types except for the potentiometers. Numbered components not appearing in the parts list are for text callout only. All controls except R11 are for calibration.  
 BT1 — Battery, 9-volt rectangular.  
 D1 — Zener diode, 6.2-V.  
 J1-J4, incl. — Standard tip jacks.  
 M1 — Panel meter, 0-50  $\mu$ A dc; Radio Shack 22-051 or equiv.  
 P1-P3, incl. — Standard tip plugs.  
 P4 — Standard test probe. Mount 1-M $\Omega$  1/4-watt resistor inside probe tip.  
 P5, P6 — Standard test probe.  
 Q1, Q2 — Motorola MPF102; do not substitute.  
 S1 — Spst toggle.  
 S2 — 2-pole, 3-position rotary.  
 S3 — 2-pole, 5-position rotary.

some means must be incorporated to balance the circuit under static conditions. The ZERO potentiometer does just that since the meter will read exactly "0" when the circuit is balanced. Any imbalance causes the meter to deflect, the amount of deflection proportional to the degree of imbalance.

Voltage scales for both ac and dc are 0-0.5, 0-5, 0-50 and 0-500. A series of dividers (R2 through R5) feed a portion of the voltage being measured to the bridge circuitry. A 1-M $\Omega$  resistor is used in the tip of the dc probe bringing the total input impedance to approximately 7 megohms. The use of potentiometers in the divider alleviates the need for precision, special-value resistors, thereby reducing the cost of the unit.

Measurements of ac voltage are facilitated by rectifying the ac and reading the resulting dc directly. Two 1N4001 diodes, a 22-M $\Omega$  resistor, and a 0.05- $\mu$ F capacitor form the rectifier circuit. R1 is used to calibrate the instrument for ac measurements.

Resistance measurements are made in ohms using five ranges: 0-50, 0-500, 0-5000, 0-50k and 0-500k. This circuit makes use of a linear ohms-readout

system. Conventional VTVMs and VOMs use scales that are cramped on the high end and expanded on the low resistance end. This logarithmic system is impractical for a home-constructed instrument since special meter faces are not generally available. Linear readout of resistance allows the user to read the value of resistance directly from a standard meter face.

Potentiometers R6 through R10 are used in place of precision, nonstandard-value resistors. Each potentiometer controls the voltage division for its associated range.

Under normal circuit conditions with the instrument placed in the ohms position, the meter will rest gently against the peg, off scale at the high end. When the ohmmeter leads are connected together, the zero potentiometer is adjusted so that the meter indicates zero resistance. Separating the leads causes the pointer to return to its position resting against the high-end peg. D1 is used to limit the voltage fed to the bridge so that the pointer does not slam against the peg.

#### Construction

The enclosure is made from pieces of

double-sided, glass-epoxy circuit board material with the overall dimensions measuring 4  $\times$  6  $\times$  2-1/4 inches (100  $\times$  150  $\times$  60 mm). All seams are soldered together along their entire length to ensure a rigid construction. The battery is held between two pieces of circuit board material soldered to the sides at several locations.

All components other than the meter switches, battery and zero potentiometer are mounted on a circuit board that measures 2-7/8  $\times$  3-1/8 inches (73  $\times$  79 mm). A suitable foil pattern with parts layout is shown in Fig. 12.

The schematic shows a number of connections to ground. In this particular circuit, ground is not the cabinet of the instrument but rather a "floating" ground. By not connecting any of the circuitry to the cabinet there is no chance of having dangerous voltages on the case. *This means that the circuit-board ground foil should not be allowed to contact the cabinet.*

Although the unit shown in the photographs was left natural (tarnished copper) with a clear acrylic coating, there is no reason why the builder should not paint the finished VOM. Treat the copper

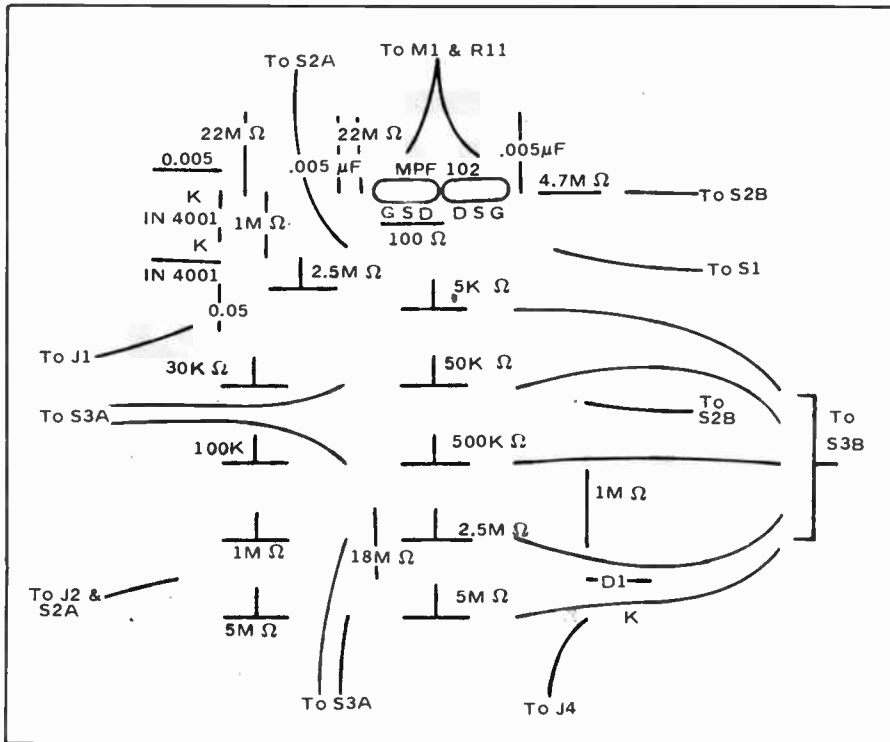


Fig. 12 — Circuit-board layout with parts overlay for the FET VOM. Shaded areas represent unetched copper areas of circuit board. This view is from the foil side of the board.

like any other metal surface when painting. Any type of labeling that suits the builder's fancy may be used. Dry transfer-type labels were used on the unit shown.

**Calibration**

Adjustment of the completed FET VOM is simple. However, it does require the use of a calibrated meter and a source of variable-voltage dc. The dc ranges should be adjusted first. Connect the calibrated voltmeter in parallel with the FET VOM and attach these connection points to the variable-voltage dc supply. Start with the lowest range (0-0.5) and set the supply voltage for a midscale reading (0.25 volt). Adjust R2 so that the FET VOM reading conforms with the reading

on the calibrated meter. Do the same for each of the other ranges using a voltage that will allow the meter to read near midscale. Should 250 volts not be available for the high-range calibration, 50 volts could be used, yielding only a small difference in accuracy. *Care should be taken to touch only the plastic insulation on the potentiometers since potentially dangerous voltages are present in the circuit.*

Ac calibration is somewhat simpler since the basic voltage dividers have already been calibrated. The ac line voltage should be used for calibration, again conforming the reading on the FET VOM with the calibrated meter. R1 is provided for this adjustment.

Calibration of the ohmmeter circuitry is

**AC INSTRUMENTS AND CIRCUITS**

Although purely electromagnetic instruments which operate directly from alternating current are available, they are seen infrequently in present-day amateur equipment. For one thing, their use is not feasible above power-line frequencies.

Practical instruments for audio and radio frequencies generally use a dc meter movement in conjunction with a rectifier. Voltage measurements suffice for nearly all test purposes. Current, as such, is seldom measured in the af range. When rf

current is measured the instrument used is a thermocouple milliammeter or ammeter.

**The Thermocouple Meter**

In a *thermocouple meter* the alternating current flows through a low-resistance heating element. The power lost in the resistance generates heat that warms a "thermocouple," a junction of certain dissimilar metals which has the property of developing a small dc voltage when

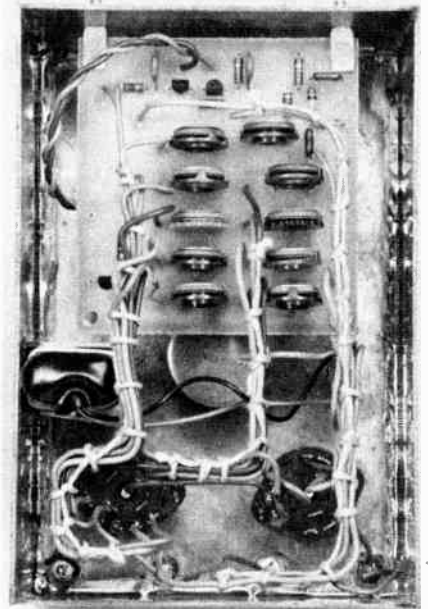


Fig. 13 — The inside of the FET VOM. Leads are dressed with wire-tying twine to provide a neat appearance.

done in a similar manner. A resistor that will allow the meter to read approximately midscale for each range will be required. If the resistors are of the precision variety, a calibrated ohmmeter will not be required. However, if the resistors used for calibration are of five-percent tolerance or greater, it would be wise to use a calibrated meter. For example, a 27-ohm precision resistor could be used for the lowest frequency range. R6 would be adjusted for a reading of exactly 27 ohms on the FET VOM. A 10- or 20-percent tolerance resistor could be used provided a calibrated meter is available. In that case the FET VOM reading should be made the same as the calibrated meter. Simply do the same for the remainder of the resistance ranges. That completes the calibration of the instrument. It is now ready for use in those many applications around your shack.



Fig. 14 — Rf ammeter mounted in a Minibox, with connectors for placing the meter in series with a coaxial line. A bakelite-case meter should be used to minimize shunt capacitance (which introduces error) although a metal-case meter can be used if mounted on bakelite sheet with a large cut-out in the case around the rim. The meter can be used for rf power measurements ( $P = I^2R$ ) when connected between a transmitter and a nonreactive load of known resistance.

delivered to the load. A suitable mounting for this is shown in Fig. 14, for use in coaxial lines.

### Rectifier Instruments

The response of a rectifier-type meter is proportional (depending on the design) to either the peak amplitude or average amplitude of the rectified ac wave, and never directly responsive to the rms value. The meter therefore cannot be calibrated in rms without preknowledge of the relationship that happens to exist between the "real" reading and the rms value. This relationship, in general, is not known, except in the case of single-frequency ac (a sine wave). Very many practical measurements involve nonsinusoidal wave forms, so it is necessary to know what kind of instrument you have, and what it is actually reading, in order to make measurements intelligently.

### Peak and Average with Sine-Wave Rectification

Fig. 15 shows the relative peak and average values in the outputs of half- and full-wave rectifiers (see power-supply chapter for further details). As the positive and negative half cycles of the sine wave have the same shape (A), half-wave rectification of either the positive half (B) or the negative half (C) gives exactly the same result. With full-wave rectification (D) the peak is still the same, but the average is doubled, since there are twice as many half cycles per unit of time.

### Unsymmetrical Wave Forms

A nonsinusoidal waveform is shown in

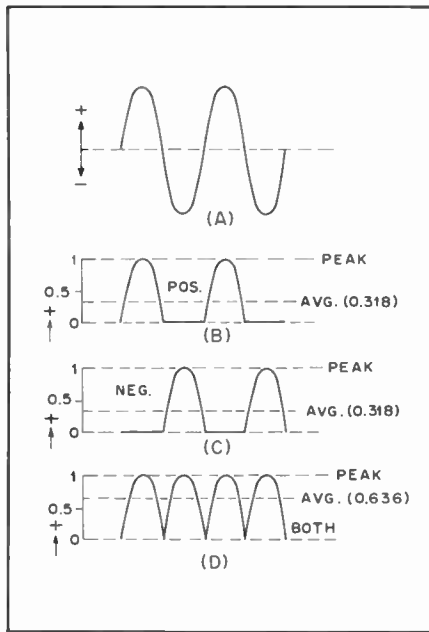


Fig. 15 — Sine-wave alternating current or voltage (A), with half-wave rectification of the positive half cycle (B) and negative half cycle (C). D — full-wave rectification. Average values are shown with relation to a peak value of 1.

Fig. 16A. When the positive half cycles of this wave are rectified the peak and average values are as shown at B. If the polarity is reversed and the negative half cycles are rectified, the peak value is different but the average value is unchanged. The fact that the average of the positive side is equal to the average of the negative side is true of *all* ac waveforms, but different waveforms have different averages. Full-wave rectification of such a "lop-sided" wave doubles the average value, but the peak reading is always the same as it is with the half cycle that produces the *highest* peak in half-wave rectification.

### Effective-Value Calibration

The actual scale calibration of commercially made rectifier-type voltmeters is very often (almost always, in fact) in terms of rms values. For sine waves this is satisfactory, and useful since rms is the standard measure at power-line frequency. It is also useful for many rf applications where the waveform is often closely sinusoidal. But in other cases, particularly in the af range, the error may be considerable when the waveform is not pure.

### Turn-Over

From Fig. 16 it is apparent that the calibration of an average-reading meter will be the same whether the positive or negative sides are rectified. A half-wave *peak*-reading instrument, however, will indicate different values when its connections to the circuit are reversed (*turn-over effect*). Very often readings are

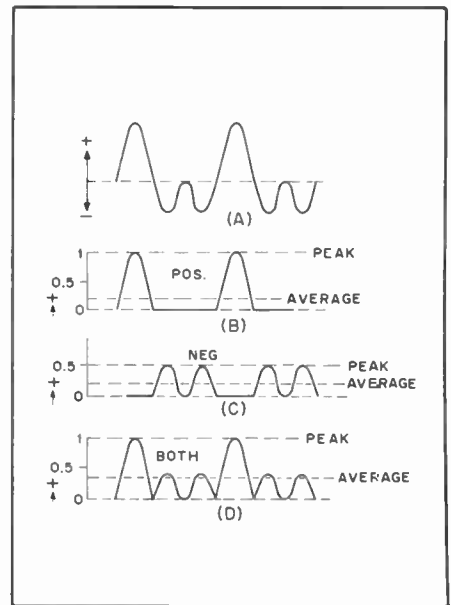


Fig. 16 — Same as Fig. 15 for an unsymmetrical waveform. The peak values are different with positive and negative half-cycle rectification.

taken both ways, in which case the sum of the two is the *peak-to-peak* (pk-pk) value, a useful figure in much audio and video work.

### Average- and Peak-Reading Circuits

The basic difference between average- and peak-reading rectifier circuits is that in the former the output is not filtered while in the latter a filter capacitor is charged up to the peak value of the output voltage. Fig. 17A shows typical average-reading circuits, one half-wave and the other full-wave. In the absence of dc filtering the meter responds to wave forms such as are shown at B, C and D in Figs. 15 and 16, and since the inertia of the pointer system makes it unable to follow the rapid variations in current, it averages them out mechanically.

In Fig. 17A D1 actuates the meter; D2 provides a low-resistance dc return in the meter circuit on the negative half cycles. R1 is the voltmeter multiplier resistance. R2 forms a voltage divider with R1 (through D1) which prevents more than a few ac volts from appearing across the rectifier-meter combination. A corresponding resistor can be used across the full-wave bridge circuit.

In these two circuits no provision is made for isolating the meter from any dc voltage that may be on the circuit under measurement. The error caused by this can be avoided by connecting a large capacitance in series with the "hot" lead. The reactance must be low compared with the meter impedance (see next section) in order for the full ac voltage to be applied to the meter circuit. As much as 1 may be required at line frequencies with some meters. The capacitor is not usually included in a VOM.



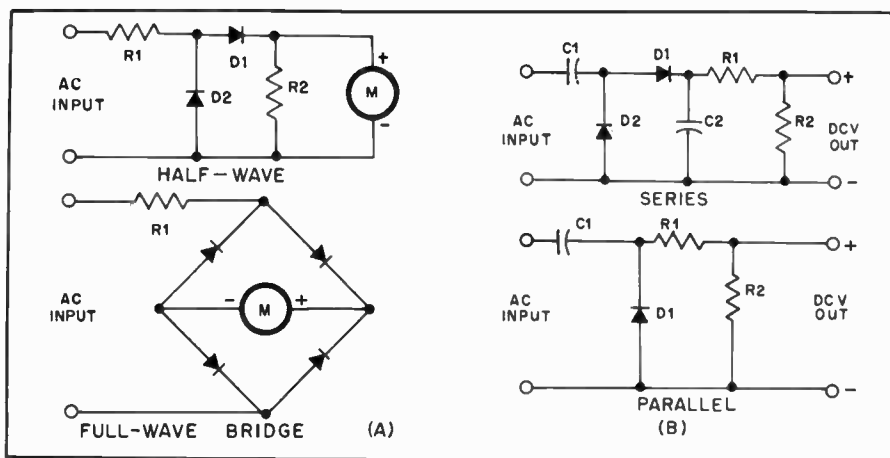


Fig. 17 — At A, half-wave and full-wave rectification for an instrument intended to operate on average values. At B, half-wave circuits for a peak-reading meter.

Series and shunt peak-reading circuits are shown in Fig. 17B. Capacitor C1 isolates the rectifier from dc voltage on the circuit under measurement. In the series circuit (which is seldom used) the time constant of the C2-R1-R2 combination must be very large compared with the period of the lowest ac frequency to be measured; similarly with C1-R1-R2 in the shunt circuit. The reason is that the capacitor is charged to the peak value of voltage when the ac wave reaches its maximum, and then must hold the charge (so it can register on a dc meter) until the next maximum of the same polarity. If the time constant is 20 times the ac period the charge will have decreased by about five percent by the time the next charge occurs. The *average* drop will be smaller, so the error is appreciably less. The error will decrease rapidly with increasing frequency, assuming no change in the circuit values, but will increase at lower frequencies.

In Fig. 17B R1 and R2 form a voltage divider which reduces the peak dc voltage to 71 percent of its actual value. This converts the peak reading to rms or sine-wave ac. Since the peak-reading circuits are incapable of delivering appreciable current without considerable error, R2 is usually the 11-megohm input resistance of an electronic voltmeter. R1 is therefore approximately 4.7 megohms, making the total resistance approach 16 megohms. A capacitance of 0.05  $\mu$ F is sufficient for low audio frequencies under these conditions. Much smaller values of capacitance suffice for radio frequencies, obviously.

#### Voltmeter Impedance

The impedance of the voltmeter at the frequency being measured may have an effect on the accuracy similar to the error caused by the resistance of a dc voltmeter, as discussed earlier. The ac meter acts like a resistance in parallel with a capacitance,

and since the capacitive reactance decreases with increasing frequency, the impedance also decreases with frequency. The resistance is subject to some variation with voltage level, particularly at very low voltages (of the order of 10 volts or less) depending upon the sensitivity of the meter movement and the kind of rectifier used.

The ac load resistance represented by a diode rectifier is approximately equal to one-half its dc load resistance. In Fig. 17A the dc load is essentially the meter resistance, which is generally quite low compared with the multiplier resistance R1, so the total resistance will be about the same as the multiplier resistance. The capacitance depends on the components and construction, test lead length and disposition, and other such factors. In general, it has little or no effect at power-line and low audio frequencies, but the ordinary VOM loses accuracy at the higher audio frequencies and is of little use at rf. For radio frequencies it is necessary to use a rectifier having very low inherent capacitance.

Similar limitations apply to the peak-reading circuits. In the parallel circuit the resistive component of the impedance is smaller than in the series circuit, since the dc load resistance, R1/R2, is directly across the circuit being measured, and is therefore in parallel with the diode ac load resistance. In both peak-reading circuits the effective capacitance may range from 1 or 2 to a few hundred pF. Values of the order of 100 pF are to be expected in electronic voltmeters of customary design and construction.

#### Linearity

Fig. 18, a typical current/voltage characteristic of a small semiconductor rectifier, indicates that the forward dynamic resistance of the diode is not constant, but rapidly decreases as the forward voltage is increased from zero.

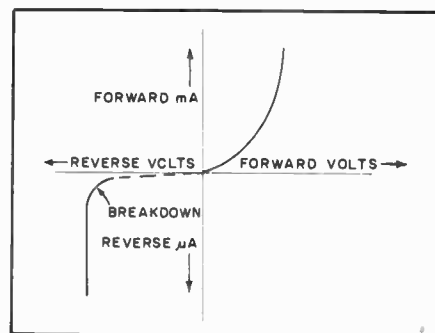


Fig. 18 — Typical semiconductor diode characteristic. Actual current and voltage values vary with the type of diode, but the forward-current curve would be in its steep part with only a volt or so applied. Note change in current scale for reverse current. Breakdown voltage, again depending on diode type, may range from 15 or 20 volts to several hundred.

The transition from high to low resistance occurs at considerably less than 1 volt, but is in the range of voltage required by the associated dc meter. With an average-reading circuit the current tends to be proportional to the *square* of the applied voltage. This crowds the calibration points at the low end of the meter scale. For most measurement purposes, however, it is far more desirable for the output to be "linear;" that is, for the reading to be *directly* proportional to the applied voltage.

To achieve linearity it is necessary to use a relatively large load resistance for the diode — large enough so that this resistance, rather than the diode's own resistance, will govern the current flow. A linear or equally spaced scale is thus gained at the expense of sensitivity. The amount of resistance needed depends on the type of diode; 5000 to 50,000 ohms usually suffices for a germanium rectifier, depending on the dc meter sensitivity, but several times as much may be needed for silicon. The higher the resistance, the greater the meter sensitivity required; i.e., the basic meter must be a microammeter rather than a low-range milliammeter.

#### Reverse Current

When voltage is applied in the reverse direction there is a small leakage current in semiconductor diodes. This is equivalent to a resistance connected across the rectifier, allowing current to flow during the half cycle which should be completely nonconducting, and causing an error in the dc meter reading. This "back resistance" is so high as to be practically unimportant with silicon, but may be less than 100 kilohms with germanium.

The practical effect of back resistance is to limit the amount of resistance that can be used in the dc load resistance. This in turn affects the linearity of the meter scale.

The back resistance of vacuum-tube



diodes is infinite, for practical purposes.

### RF Voltage

Special precautions must be taken to minimize the capacitive component of the voltmeter impedance at radio frequencies. If possible, the rectifier circuit should be installed permanently at the point where the rf voltage to be measured exists, using the shortest possible rf connections. The dc meter can be remotely located, however.

For general rf measurements an *rf probe* is used in conjunction with an electronic voltmeter, substituted for the dc probe mentioned earlier. The circuit of Fig. 20, essentially the peak-reading shunt circuit of Fig. 17B, is generally used. The series resistor, installed in the probe close to the rectifier, prevents rf from being fed through the probe cable to the electronic voltmeter, being helped in this by the cable capacitance. This resistor, in conjunction with the 10-M $\Omega$  divider resistance of the electronic voltmeter, also reduces the peak rectified voltage to a dc value equivalent to the rms of the rf signal, to make the rf readings consistent with the regular ac calibration.

Of the diodes readily available to amateurs, the germanium point-contact type is preferred for rf applications. It has low capacitance (of the order of 1 pF) and in the high-back-resistance types the reverse current is not serious. The principal limitation is that its safe reverse voltage is only about 50-75 volts, which limits the rms applied voltage to 15 or 20 volts, approximately. Diodes can be connected in series to raise the overall rating.

### An RF Probe for Electronic Voltmeters

The isolation capacitor, C1, crystal diode, and filter/divider resistor are mounted on a bakelite five-lug terminal strip, as shown in Fig. 22. One end lug should be rotated 90 degrees so that it extends off the end of the strip. All other lugs should be cut off flush with the edge of the strip. Where the inner conductor connects to the terminal lug, unravel the shield three-quarters of an inch, slip a piece of spaghetti over it, and then solder the braid to the ground lug on the terminal strip. Remove the spring from the tube shield, slide it over the cable, and crimp it to the remaining quarter inch of shield braid. Solder both the spring and a 12-inch (305-mm) length of flexible copper braid to the shield.

Next, cut off the pins on a seven-pin miniature shield-base tube socket. Use a socket with a cylindrical center post. Crimp the terminal lug previously bent out at the end of the strip and insert it into the center post of the tube socket from the top. Insert the end of a phone tip or a pointed piece of heavy wire into the bottom of the tube socket center post, and solder the lug and tip to the center post.

Insert a half-inch grommet at the top of the tube shield, and slide the shield over the cable and flexible braid down onto the tube socket. The spring should make good contact with the tube shield to insure that the tube shield (probe case) is grounded. Solder an alligator clip to the other end of the flexible braid and mount a phone plug on the free end of the shielded wire.

Mount components close to the terminal strip, to keep lead lengths as short as possible and minimize stray capacitance. Use spaghetti over all wires to prevent accidental shorts.

The phone plug on the probe cable plugs into the dc input jack of the electronic voltmeter and rms voltages are read on the voltmeter's negative dc scale.

The accuracy of the probe is within  $\pm 10$  percent from 50 kHz to 250 MHz. The approximate input impedance is 6000 ohms shunted by 1.75 pF (at 200 MHz).

### RF Power

Power at radio frequencies can be measured by means of an accurately calibrated rf voltmeter connected across the load in which the power is being dissipated. If the load is a known pure resistance the power, by Ohm's Law, is equal to  $E^2/R$ , where E is the rms value of the voltage.

The method only indicates *apparent* power if the load is not a pure resistance. The load can be a terminated transmission line tuned, with the aid of bridge circuits such as are described in the next section, to act as a known resistance. An alternative load is a "dummy" antenna, a known pure resistance capable of dissipating the rf power safely.

### AC Bridges

In its simplest form, the ac bridge is exactly the same as the Wheatstone bridge discussed earlier. However, complex impedances can be substituted for resistances, as suggested by Fig. 23A. The same bridge equation holds if Z is substituted for R in each arm. For the equation to be true, however, *the phase angles as well as the numerical values of the impedances must balance*; otherwise, a true null voltage is impossible to obtain. This means that a bridge with all "pure" arms (pure resistance or reactance) cannot measure complex impedances; a combination of R and X must be present in at least one arm besides the unknown.

The actual circuits of ac bridges take many forms, depending on the type of measurement intended and on the frequency range to be covered. As the frequency is raised, stray effects (unwanted capacitances and inductances, principally) become more pronounced. At radio frequencies special attention must be paid to minimizing them.

Most amateur-built bridges are used for rf measurements, especially SWR measure-



Fig. 19 — Rf probe for use with an electronic voltmeter. The case of the probe is constructed from a seven-pin ceramic tube socket and a 2-1/4-inch (57-mm) tube shield. A half-inch (13-mm) grommet at the top of the tube shield prevents the output lead from chafing. A flexible copper-braid grounding lead and alligator clip provide a low-inductance return path from the test circuit.

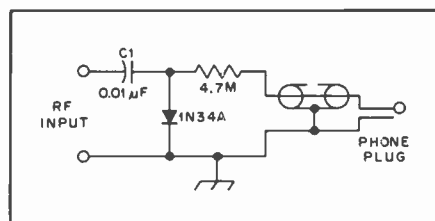


Fig. 20 — The rf probe circuit.

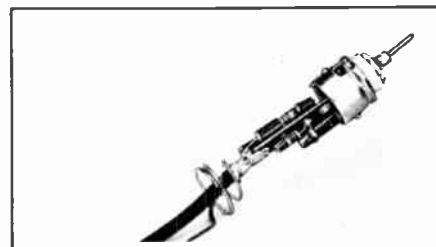


Fig. 21 — Inside the probe. The 1N34A diode, calibrating resistor, and input capacitor are mounted tight to the terminal strip with shortest leads possible. Spaghetti tubing is placed on the diode leads to prevent accidental short circuits. The tube-shield spring and flexible-copper grounding lead are soldered to the cable braid (the cable is RG-58/U coax). The tip can be either a phone tip or a short pointed piece of heavy wire.

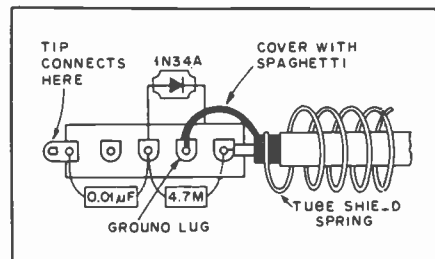


Fig. 22 — Component mounting details.

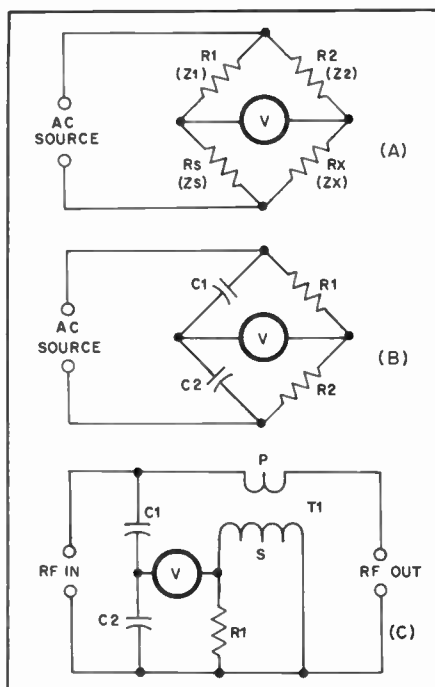


Fig. 23 — (A) Generalized form of bridge circuit for either ac or dc. (B) One form of ac bridge frequently used for rf measurements. (C) SWR bridge for use in transmission lines. This circuit is often calibrated in power rather than voltage.

ments on transmission lines. The circuits at B and C, Fig. 23, are favorites for this purpose.

Fig. 23B is useful for measuring both transmission lines and "lumped constant" components. Combinations of resistance and capacitance are often used in one or more arms; this may be required for eliminating the effects of stray capacitance.

Fig. 23C is used only on transmission lines, and only on those lines having the characteristic impedance for which the bridge is designed.

### SWR Measurement — the Reflectometer

In measuring standing-wave ratio advantage is taken of the fact that the voltage on a transmission line consists of two components traveling in opposite directions. The power going from the transmitter to the load is represented by

one voltage (designated "incident" or "forward") and the power reflected from the load is represented by the other. Because the relative amplitudes and phase relationships are definitely established by the line's characteristic impedance, its length and the load impedance in which it is terminated, a bridge circuit can separate the incident and reflected voltages for measurement. This is sufficient for determining the SWR. Bridges designed for this purpose are frequently called *reflectometers*.

Referring to Fig. 20A, if R1 and R2 are made equal, the bridge will be balanced when  $R_X = R_S$ . This is true whether  $R_X$  is an actual resistor or the input resistance of a perfectly matched transmission line, provided  $R_S$  is chosen to equal the characteristic impedance of the line. Even if the line is not properly matched, the bridge will still be balanced for power traveling *outward* on the line, since outward-going power sees only the  $Z_0$  of the line until it reaches the load. However, power reflected back from the load does not "see" a bridge circuit, and the reflected voltage registers on the voltmeter. From the known relationship between the incident and reflected voltages the SWR is easily calculated:

$$SWR = \frac{V_0 + V_r}{V_0 - V_r}$$

### The "Reflected Power Meter"

Fig. 23C makes use of mutual inductance between the primary and secondary of T1 to establish a balancing circuit. C1 and C2 form a voltage divider in which the voltage across C2 is in the same phase as the voltage at that point on the transmission line. The relative phase of the voltage across R1 is determined by the phase of the *current* in the line. If a pure resistance equal to the design impedance of the bridge is connected to the "RF Out" terminals, the voltages across R1 and C2 will be out of phase and the voltmeter reading will be minimum; if the *amplitudes* of the two voltages are also equal (they are made so by bridge adjustment) the voltmeter will read zero. Any other value of resistance or impedance connected to the "RF Out"

terminals will result in a finite voltmeter reading. When used in a transmission line this reading is proportional to the reflected voltage. To measure the incident voltage the secondary terminals of T1 can be reversed. To function as described, the secondary leakage reactance of T1 must be very large compared to the resistance of R1.

Instruments of this type are usually designed for convenient switching between forward and reflected, and are often calibrated to read power in the specified characteristic impedance. The net power transmission is equal to the incident power minus the reflected power.

### Sensitivity vs. Frequency

In all of the circuits in Fig. 23 the sensitivity is independent of the applied frequency, within practical limits. Stray capacitances and couplings generally limit the performance of all three at the high-frequency end of the useful range. Fig. 23A will work right down to dc, but the low-frequency performance of Fig. 23B is degraded when the capacitive reactances become so large that voltmeter impedance becomes low in comparison (in all these bridge circuits, it is assumed that the voltmeter impedance is high compared with the impedance of the bridge arms). In Fig. 23C the performance is limited at low frequencies by the fact that the transformer reactance decreases with frequency, so that eventually the reactance is not very high in comparison with the resistance of R1.

### The "Monimatch"

A type of bridge which is quite simple to make, but in which the sensitivity rises directly with frequency, is the *Monimatch* and its various offspring. The circuit cannot be described in terms of lumped constants, as it makes use of the distributed mutual inductance and capacitance between the center conductor of a transmission line and a wire placed parallel to it. The wire is terminated in a resistance approximating the characteristic impedance of the transmission line at one end and feeds a diode rectifier at the other. A practical example is shown later in this chapter.

## Frequency Measurement

The regulations governing amateur operation require that the transmitted signal be maintained inside the limits of certain bands of frequencies.<sup>1</sup> The exact frequency need not be known, so long as it is not outside the limits. On this last point there are no tolerances: It is up to the

individual amateur to see that he stays safely "inside."

This is not difficult to do, but requires some simple apparatus and the exercise of some care. The apparatus commonly used is the *frequency-marker generator*, and the method involves use of the station receiver, as in Fig. 24.

### The Frequency Marker

The marker generator in its simplest

form is a high-stability oscillator generating a series of signals which, when detected in the receiver, mark the exact edges of the amateur assignments. It does this by oscillating at a low frequency that has harmonics falling on the desired frequencies.

U.S. amateur band limits are exact multiples of 25 kHz, whether at the extremes of a band or at points marking the subdivisions between types of emis-

<sup>1</sup>These limits depend on the type of emission and class of license held, as well as on international agreements. See the latest edition of *The Radio Amateur's License Manual* for current status.

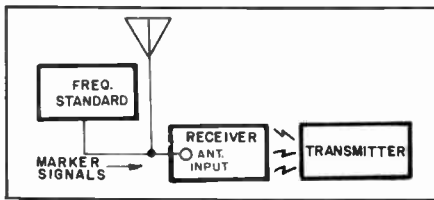


Fig. 24 — Setup for using a frequency standard. It is necessary that the transmitter signal be weak in the receiver — of the same order of strength as the marker signal from the standard. This requirement can usually be met by turning on just the transmitter oscillator, leaving all power off any succeeding stages. In some cases it may also be necessary to disconnect the antenna from the receiver.

sion, license privileges, and so on. A 25-kHz fundamental frequency therefore will produce the desired marker signals if its harmonics at the higher frequencies are strong enough. But since harmonics appear at 25-kHz intervals throughout the spectrum, along with the desired markers, the problem of identifying a particular marker arises. This is easily solved if the receiver has a reasonably good calibration. If not, most marker circuits provide for a choice of fundamental outputs of 100 and 50 kHz as well as 25 kHz, so the question can be narrowed down to initial identification of 100-kHz intervals. From these, the desired 25-kHz (or 50-kHz) points can easily be spotted. Coarser frequency intervals are rarely required; there are usually signals available from stations of known frequency, and the 100-kHz points can be counted off from them.

### Transmitter Checking

In checking one's own transmitter frequency the signal from the transmitter is first tuned in on the receiver and the dial setting at which it is heard is noted. Then the nearest marker frequencies above and below the transmitter signal are tuned in and identified. The transmitter frequency is obviously between these two known frequencies.

If the marker frequencies are accurate, this is all that needs to be known — except that the transmitter frequency must not be so close to a band (or subband) edge that sideband frequencies, especially in phone transmission, will extend over the edge.

If the transmitter signal is "inside" a marker at the edge of an assignment, to the extent that there is an audible beat note with the receiver's BFO turned off, normal cw sidebands are safely inside the edge. (This statement does not take into account abnormal sidebands such as are caused by clicks and chirps.) For phone the "safety" allowance is usually taken to be about 3 kHz, the nominal width of one sideband. A frequency difference of this order can be estimated by noting the receiver dial settings for the two 25-kHz markers which bracket the signal and dividing 25 by the number of dial

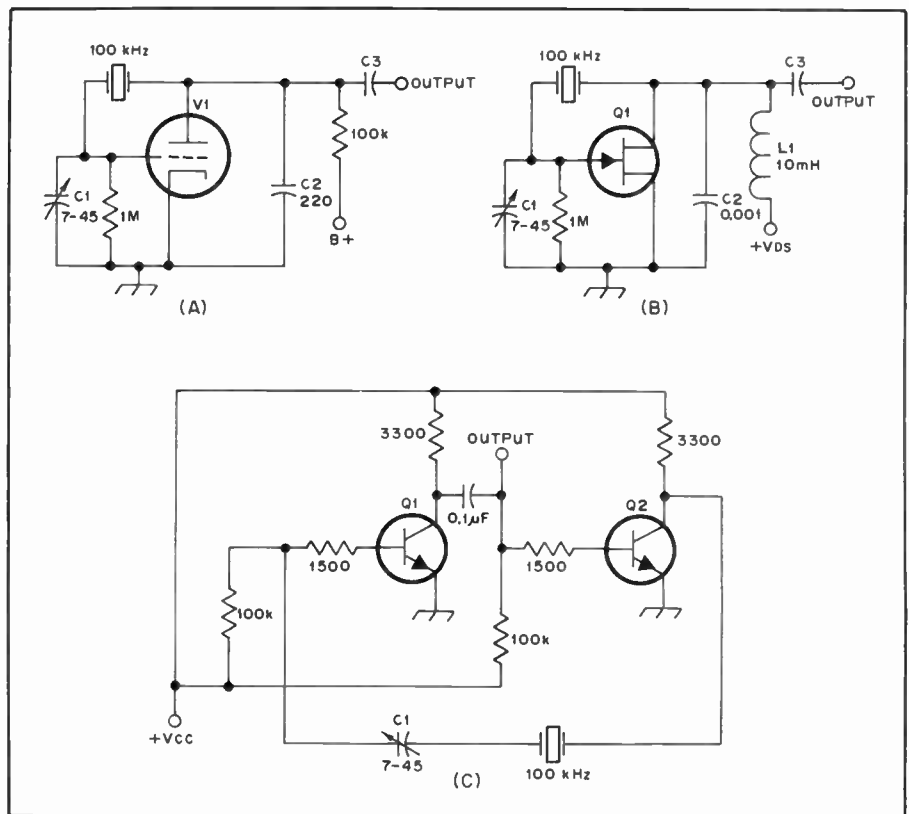


Fig. 25 — Three simple 100-kHz oscillator circuits. C is the most suitable of available transistor circuits (for marker generators) and is recommended where solid-state is to be used. In all three circuits C1 is for fine frequency adjustment. The output coupling capacitor, C3, is generally small — 20 to 50 pF — a compromise to avoid loading the oscillator by the receiver antenna input while maintaining adequate coupling for good harmonic strength.

divisions between them. This will give the number of kHz per dial division.

### Transceivers

The method described above is applicable when the receiver and transmitter are separate pieces of equipment. When a transceiver is used and the transmitting frequency is automatically the same as that to which the receiver is tuned, setting the tuning dial to a spot between two known marker frequencies is all that is required.

The proper dial settings for the markers are those at which, with the BFO on, the signal is tuned to zero beat — the spot where the beat disappears as the tuning makes the beat tone progressively lower. Exact zero beat can be determined by a very slow rise and fall of background noise, caused by a beat of a cycle or less per second.

### Frequency-Marker Circuits

The basic frequency-determining element in most amateur frequency markers is a 100-kHz crystal. Although the marker generator should produce harmonics at 25-kHz and 50-kHz intervals, crystals (or other high-stability devices) for frequencies lower than 100 kHz are expensive and difficult to obtain. However, there is really no need for them, since it is easy to divide the basic frequency down to any

figure one desires; 50 and 25 kHz require only two successive divisions, each by two. In the division process, the harmonic output of the generator is greatly enhanced, making the generator useful at frequencies well into the vhf range.

### Simple Crystal Oscillators

Fig. 25 illustrates a few of the simpler circuits. Fig. 25A is a long-time favorite where vacuum tubes are used and is often incorporated in receivers. C1 in this and the other circuits is used for exact adjustment of the oscillating frequency to 100 kHz, which is done by using the receiver for comparing one of the oscillator's harmonics with a standard frequency transmitted by WWV, WWVH or a similar station.

Fig. 25B is a field-effect transistor analog of the vacuum-tube circuit. However, it requires a 10-mH coil to operate well, and since the harmonic output is not strong at the higher frequencies the circuit is given principally as an example of a simple transistor arrangement. A much better oscillator is shown at C. This is a cross-connected pair of transistors forming a multivibrator of the "free-running" or "asynchronous" type, locked at 100 kHz by using the crystal as one of the coupling elements. While it can use two separate bipolar transistors as shown, it is much simpler to use an integrated-circuit



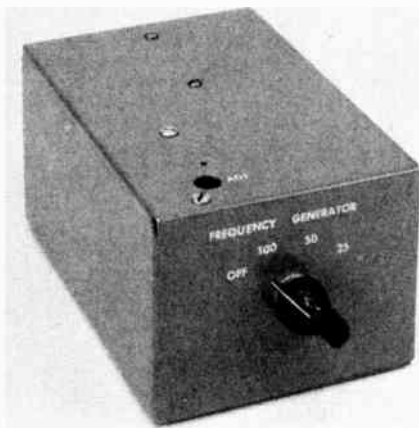


Fig. 26 — Frequency marker generating 100-, 50- or 25-kHz intervals. Battery power supply (two "D" cells) is inside the cabinet, a 3 × 4 × 6-inch (17 × 102 × 152 mm) aluminum chassis with bottom plate. The trimmer capacitor for fine adjustment of frequency is available through the hole in the top near the left front.

*dual gate*, which will contain all the necessary parts except the crystal and capacitors and is considerably less expensive, as well as more compact, than the separate components. An example is shown later in the chapter.

### Frequency Dividers

Electronic division is accomplished by a "bistable" *flip-flop* or cross-coupled circuit which produces one output change for every two impulses applied to its input circuit, thus dividing the applied frequency by two. All division therefore must be in terms of some power of two. In

practice this is no handicap since with modern integrated-circuit flip-flops, circuit arrangements can be worked out for division by any desired number.

As flip-flops and gates in integrated circuits come in compatible series — meaning that they work at the same supply voltage and can be directly connected together — a combination of a dual-gate version of Fig. 25C and a dual flip-flop make an attractively simple combination for the marker generator.

There are several different basic types of flip-flops, the variations having to do with methods of driving (dc or pulse operation) and control of the counting function. Information on the operating principles and ratings of a specific type usually can be obtained from the manufacturer. The counting-control functions are not needed in using the flip-flop in a simple marker generator, although they come into play when dividing by some number other than a power of two.

### Marker Generator for 100, 50 and 25 kHz

The frequency generator in the accompanying illustrations will deliver marker signals of usable strength well into the vhf region when its output is connected to the antenna input terminals of a communications receiver. It uses a 100-kHz crystal in an integrated-circuit version of the solid-state multivibrator oscillator shown earlier. The oscillator is followed by a two-stage IC divider which produces 50- and 25-kHz marker intervals. Two inexpensive ICs are used, an MC724P quad gate and an MC790P dual J-K flip-flop. Two of the gates in the MC724P are used for the oscillator and a third

serves as a following buffer amplifier and "squarer" for driving the first divide-by-two circuit in the MC790P. This divider then drives the second divide-by-two flip-flop. Outputs at the three frequencies are taken through a three-position switch from taps as shown in the circuit diagram, Fig. 27.

Two of the three poles of the four-position switch are used for controlling the collector voltage for the ICs. Voltage is on the MC724P in all active positions of the switch, but is applied to the MC790P only when 50- and 25-kHz markers are required. This saves battery power, since the MC790P takes considerably more current than the MC724P.

The outputs on all three frequencies are good square waves. To assure reasonably constant harmonic strength through the hf spectrum the output is coupled to the receiver through a small capacitance which tends to attenuate the lower-frequency harmonics. This capacitance, C3, is not critical as to value and may be varied to suit individual preferences. The value shown, 22 pF, is satisfactory for working into a receiver having an input impedance of 50 ohms.

At 3 volts dc input the current taken in the 100-kHz position of S1 is 8 mA. In the 50- and 25-kHz positions the total current (both ICs) is 35 mA. The generator continues to work satisfactorily when the voltage drops as low as 1.5 volts. The oscillator frequency is subject to change as the voltage is lowered, the frequency shift amounting to approximately 30 Hz at 15 MHz on going from 3 to 2 volts. There is a slight frequency shift between the 100-kHz and 50/25-kHz positions, but this amounts to only 6 or 7 Hz at 15 MHz. Frequency changes resulting from temperature variations are larger; they may be as much as a few hundred Hz at 15 MHz in normal room-temperature variations. All such frequency changes can be compensated for by adjusting C2, and it is good practice to check the frequency occasionally against one of the WWV transmissions, readjusting C2 if necessary.

### Layout and Construction

The physical layout of the circuit can be varied to suit the builder's tastes. The size of the box containing the generator shown in the photographs makes the batteries easily accessible for replacement. The method of mounting the crystal and C2 allows the latter to be reached through the top of the box for screwdriver adjustment, and makes possible the easy removal of the crystal since it plugs into a standard crystal socket. There is ample room for soldering the various wires that lead to the switch from the etched board on which the ICs, resistors, and C1 are mounted. The output jack is placed at the rear where it is convenient when the unit is alongside a receiver.

An etched board does not have to be

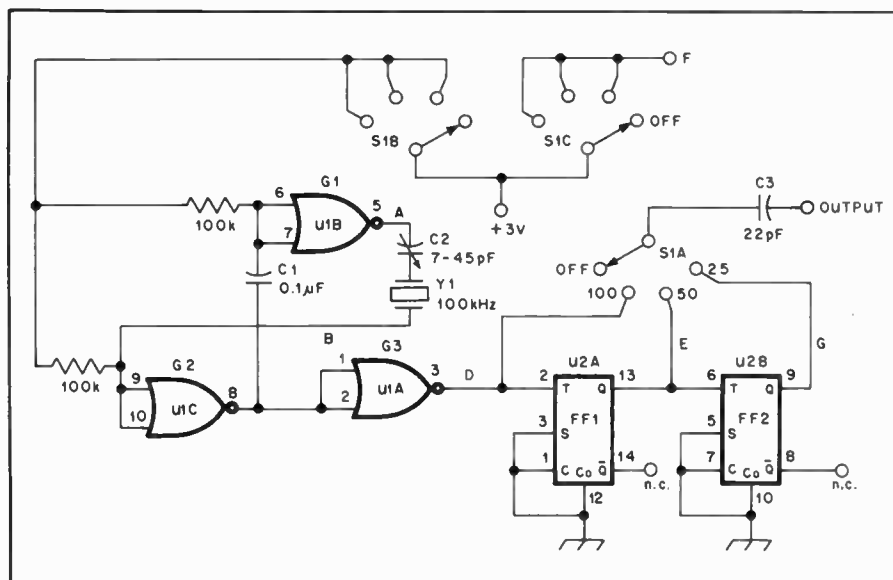


Fig. 27 — Marker generator circuit. Ground pin 4 of both ICs. Connect pin 11 of U1 to point C, and pin 11 of U2 to point F.

- C1 — 0.1µF paper, low voltage.
- C2 — 7.45-pF ceramic trimmer.
- C3 — 22-pF dipped mica (ceramic also satisfactory).

- S1 — 3-pole, 4-position rotary (Mallory 3134J).
- U1 — Quad 2-input NOR gate, 1 section unused, Motorola MC724P.
- U2 — Dual J-K flip-flop, Motorola MC790P.



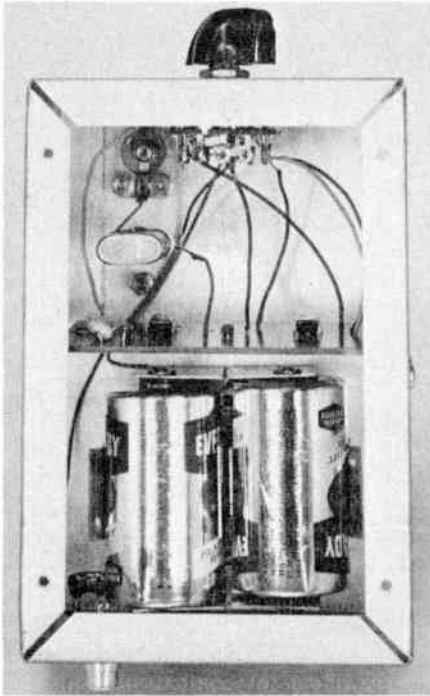


Fig. 28 — Integrated circuits and associated fixed-value capacitors and resistors are mounted on an etched board measuring 3-3/4 × 2-1/2 inches (95 × 63 mm) supported from one wall by an aluminum bracket. The 100-kHz crystal and trimmer capacitor are on a 1 × 2-inch (25 × 51 mm) plastic strip supported below the top on 1/2-inch (13-mm) spacers, with the capacitor facing upward so it can be adjusted from outside. The two dry cells are in a dual holder (available from electronics supply stores). The output connector is a phone jack, mounted on the rear wall (upper left in this view) with C3.

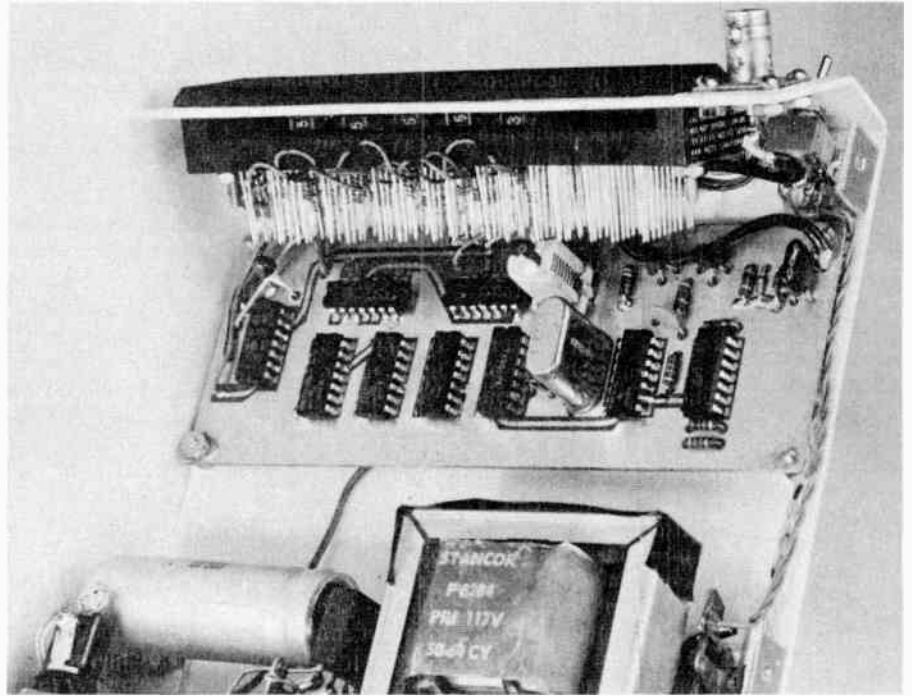


Fig. 31 — The use of a bezel and a single pc board allows very compact packaging in this counter. Leads that interconnect between the bezel and the circuit board have been made extra long. This excess length is tucked under the bezel and allows the pc board to be removed and worked on while still connected to the counter.

used for wiring the ICs and associated parts, although it makes for neatness in construction.

sometimes is when using a marker generator.

#### Other Methods of Frequency Checking

#### Absorption Circuit

The simplest possible frequency-measuring device is a parallel LC circuit, tunable over a desired frequency range of having its tuning dial calibrated in terms of frequency. It can be used only for checking circuits in which at least a small amount of rf power is present, because the energy required to give a detectable indication is not available in the LC circuit itself; it has to be extracted from the circuit being measured; hence the name *absorption frequency meter*. It will be observed that what is actually measured is the frequency of the rf energy, not the frequency to which the circuit in which the energy is present may be tuned.

A typical absorption frequency-meter circuit is shown in Fig. 29. In addition to the adjustable tuned circuit, L1-C1, it includes a pickup coil, L2, wound over L1, a high-frequency semiconductor diode, D1, and a microammeter or low-range (usually not more than 0-1 mA) milliammeter. A phone jack is included so the device can be used for listening to the signal.

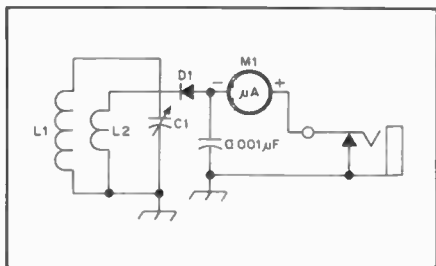


Fig. 29 — Absorption frequency-meter circuit. The closed-circuit phone jack may be omitted if listening is not wanted; in that case the positive terminal of M1 goes to common ground.

The measurement accuracy of such an instrument is low, compared with the accuracy of a marker generator, because the Q of a practicable LC circuit is not high enough to make precise reading of the dial possible. Also, any two circuits coupled together react on each others' tuning. (This can be minimized by using the loosest coupling that will give an adequate indication.)

The sensitivity of the frequency meter depends on the sensitivity of the dc meter movement and the size of L2 in relation to L1. There is an optimum size for this coil which has to be found by experiment. An alternative is to make the rectifier connection to an adjustable tap on L1, in which case there is an optimum tap point. In general, the rectifier coupling should be a little *below* (that is, less tight) the point that gives maximum response, since this will make the indications sharper.

#### Calibration

The absorption frequency meter has one useful advantage over the marker generator — it will respond *only* to the frequency to which it is tuned, or to a band of frequencies very close to it. Thus there is no harmonic ambiguity, as there

The absorption frequency meter must be calibrated by taking a series of readings on various frequencies from circuits carrying rf power, the frequency of the rf energy first being determined by some other means such as a marker generator and receiver. The setting of the dial that gives the highest meter indication is the calibration point for that frequency. This

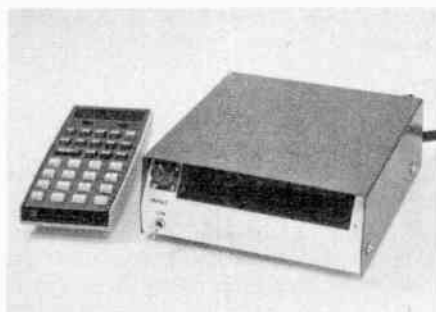


Fig. 30 — The counter is built into a homemade enclosure that measures 2 × 6 × 6 inches (50 × 153 × 153 mm).

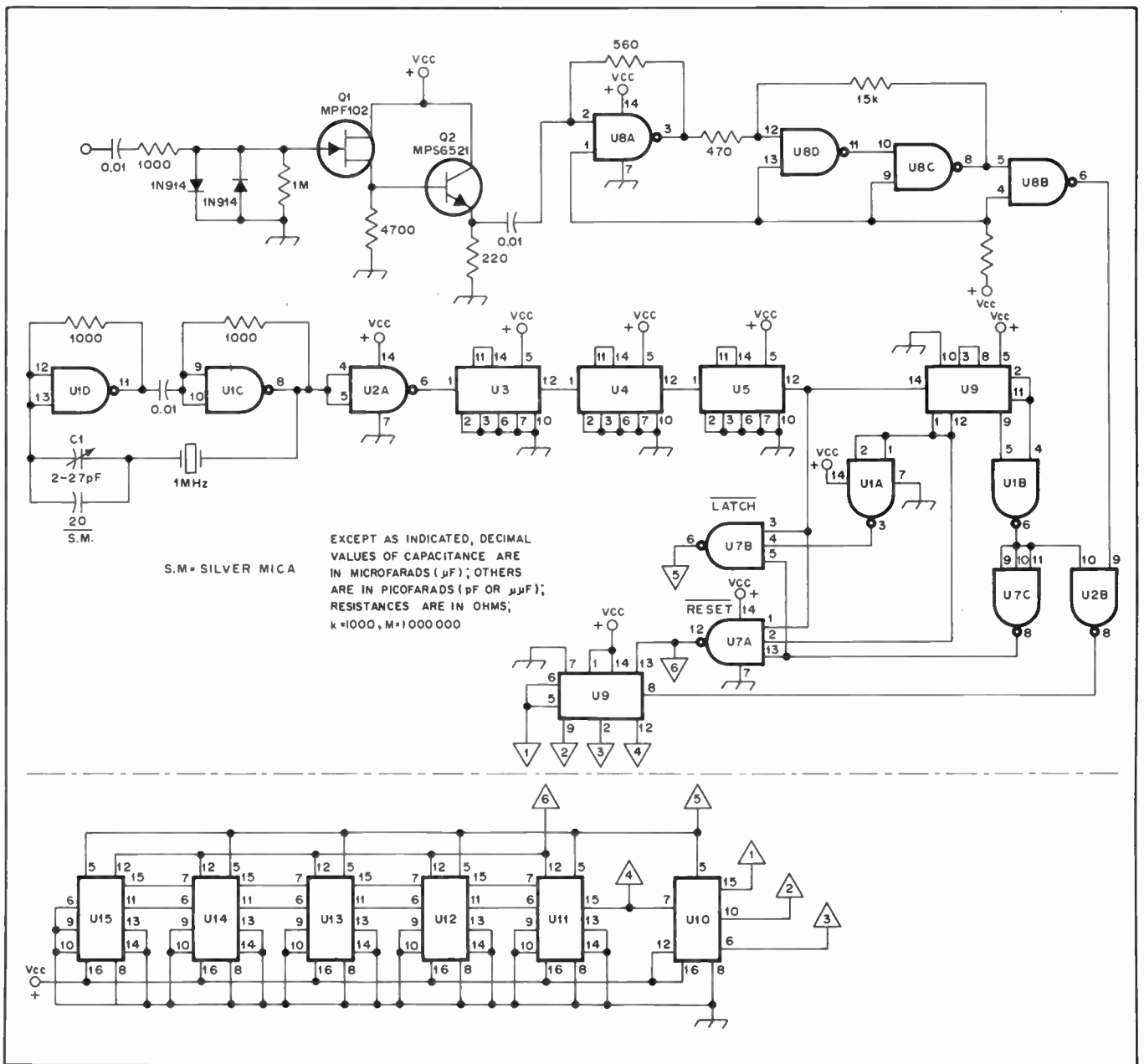


Fig. 32 — Schematic diagram of the counter and bezel wiring.

C1 — Johnson 193-8-5 trimmer 2-27 pF.

Q1 — 2N5486.

Q2 — MPS3563.

U1 — SN7400.

U2 — SN74S00.

U3, U4, U5 — SN74LS90.

U6 — SN7493.

U7 — SN74LS10.

U8 — SN74S00.

U9 — N82S90 (Signetics).

U10 — TIL 308.

U11-U15, incl. — TIL 306.

point should be determined by tuning through it with loose coupling to the circuit being measured.

### Frequency Standards

The difference between a marker generator and a *frequency standard* is that in the latter special pains are taken to make the oscillator frequency as stable as possible in the face of variations in temperature, humidity, line voltage, and other factors which could cause a small change in frequency.

While there are no definite criteria that distinguish the two in this respect, a

circuit designated as a "standard" for amateur purposes should be capable of maintaining frequency within at least a few parts per million under normal variations in ambient conditions, without adjustment. A simple marker generator using a 100-kHz crystal can be expected to have frequency variations 10 times (or more) greater under similar conditions. It can of course be adjusted to exact frequency at any time the WWV (or equivalent) signal is available.

The design considerations of high-precision frequency standards are outside the scope of this chapter, but information

is available from time to time in periodicals.

### Frequency Counters

One of the most accurate means of measuring frequency is the frequency counter. This instrument is capable of displaying numerically the frequency of the signal supplied to its input. For example, if an oscillator operating at 8.244 MHz is connected to the counter input, 8.244 would be displayed. At present, there are counters that are usable well up into the GHz range. Most counters that are to be used at high

frequencies make use of a prescaler ahead of a basic low-frequency counter. Basically, the prescaler divides the high-frequency signal by 10, 100, 1000 or some other amount so that the low-frequency counter can display the operating frequency.

The accuracy of the counter depends on an internal crystal reference. The more accurate the crystal reference, the more accurate will be the readings. Crystals for frequency counters are manufactured to close tolerances. Most counters have a trimmer capacitor so that the crystal can be set exactly on frequency. A crystal frequency of 1 MHz has become more or less standard. The 10th harmonic of the crystal can be compared to the 10-MHz signal of WWV or WWVH and adjusted for zero beat.

**A 50-MHz Frequency Counter**

As the complexity of amateur radio equipment increases, the sophistication of the test equipment needed to effectively troubleshoot failures also increases. The following counter was developed to fulfill this need and will also certainly complement the station itself. This counter as a whole is very basic in design and some interesting features are its size and the displays. Each display (except for the Least Significant Digit) contains four sections: the counter, latch, decoder and the display. The LSD does not have a counter included.

**Circuit Description**

The counter uses a crystal-controlled time base to generate the gating pulses. A 1-MHz oscillator is counted down to provide 1 kHz for the SN7493 (U6). U6 is connected to divide by 12. The outputs of this divide-by-12 counter are gated to provide the count, latch and reset gates. The timing relationships are shown in Fig. 33.

Displays are Texas Instruments TIL-306 devices and a single TIL-308. Each TIL-306 contains the four units necessary to display a counter frequency. The internal counter has an upper frequency limit of approximately 18 MHz. Following the counter is a latch, which is used to hold the data while the counter is operating. The frequency information, in BCD format, is decoded and it then drives the correct segments of the display. The maximum count output is used to drive the successive displays. Each display contains a feature called ripple blanking.

**Other Instruments and Measurements**

Many measurements require a source of ac power of adjustable frequency (and sometimes adjustable amplitude as well) in addition to what is already available from the transmitter to receiver. Rf and af test oscillators, for example, provide signals for purposes such as receiver

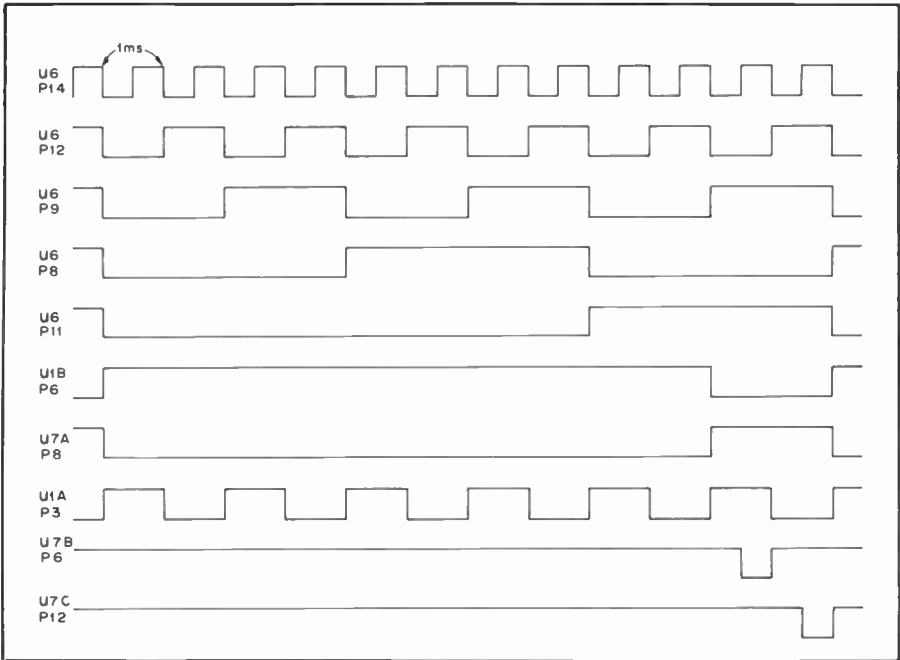


Fig. 33 — Timing diagram of the counter.

If the number zero is detected in the latches and ripple blanking has been enabled, the display will be blanked. This function was incorporated to give leading zero blanking in the counter. Starting from left to right (MSD to LSD), if zero is detected that display will be blanked and the blanked data will be passed to the right. This means that 455.2 kHz will be displayed as 455.2, not 00455.2. The LSD is not connected for leading zero blanking. It was a bit disconcerting to turn the counter on and not have the display light up. Therefore, the LSD was not connected for leading zero blanking and zero will be displayed when the counter is on with no input.

The LSD, a TIL-308, does not have the internal counter. This allows a faster counter, greater than 18 MHz, to be used for the LSD. The N82590, used as the counter for the LSD, is rated for 100-MHz operation.

Signal input is applied to a source follower, Q1. For the sake of simplicity, it was decided to use this form of input configuration instead of an amplifier for the input. An input signal of 0.25 V will be sufficient to trigger the counter, up to 50 MHz. Following the input network is an SN74S00 connected to act as a level translator. The signal from the input

alignment, testing of phone transmitters, and so on. Another valuable adjunct to the station is the oscilloscope, especially useful for checking phone modulation.

**RF Oscillators for Circuit Alignment**

Receiver testing and alignment, covered

network is made TTL compatible by this circuit.

**Construction**

One of the features of this counter is that its construction is not critical. The entire counter is built on a small circuit board and in the bezel. Instead of using a bezel, a circuit board could be etched and mounted behind the front panel. The foil on the top of the pc board is the ground interconnection for all the integrated circuits and the builder should liberally install bypass capacitors on the 5-volt line. This will prevent any transients on the line from showing up in the counted frequency. Construction techniques and added features are left entirely to individual preferences.

**Operation and Adjustment**

The only adjustment required is the crystal oscillator. This should be checked and set against a frequency standard. An error as small as 100 Hz in the crystal frequency can cause a frequency measurement to be off as much as 5 kHz at 50 MHz. This counter will function with signals as high as 65 MHz in its present configuration. The limiting factors are the selection of integrated circuits and the input network.

in an earlier chapter, uses equipment common to ordinary radio service work. Inexpensive rf signal generators are available, both complete and in kit form. However, any source of signal that is weak enough to avoid overloading the receiver usually will serve for alignment



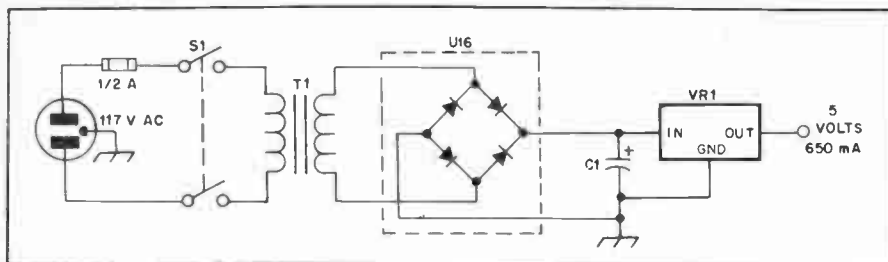


Fig. 34 — Schematic diagram of the power supply.  
 C1 — 2000  $\mu$ F, 25 V.  
 T1 — 12.6 Vac, 1 A.  
 U16 — 50 PRV, 1-A encapsulated bridge

rectifier.  
 U1 — 5-V, 1-A voltage regulator, LM309K.

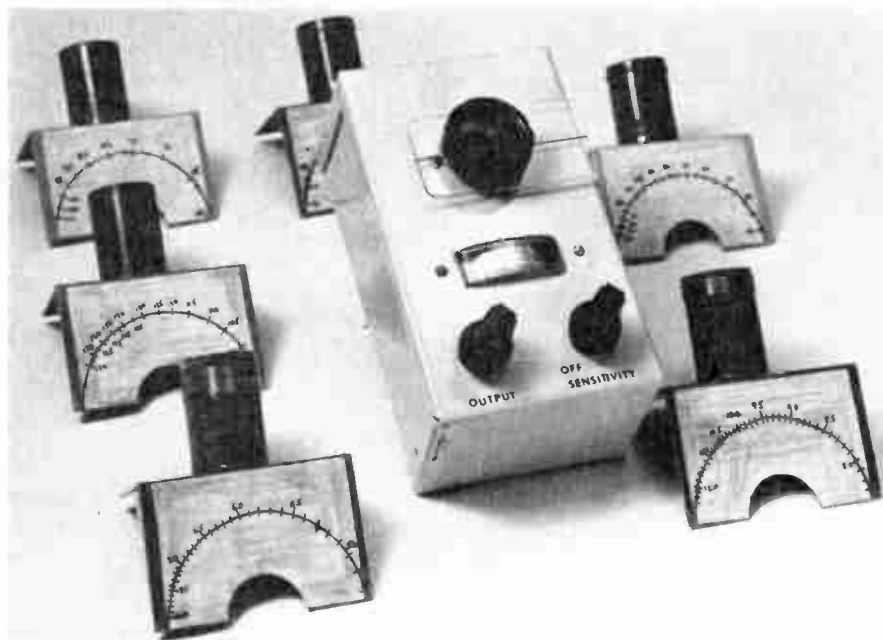


Fig. 35 — Exterior view of the dual-gate MOSFET dip meter with plug-in coils.

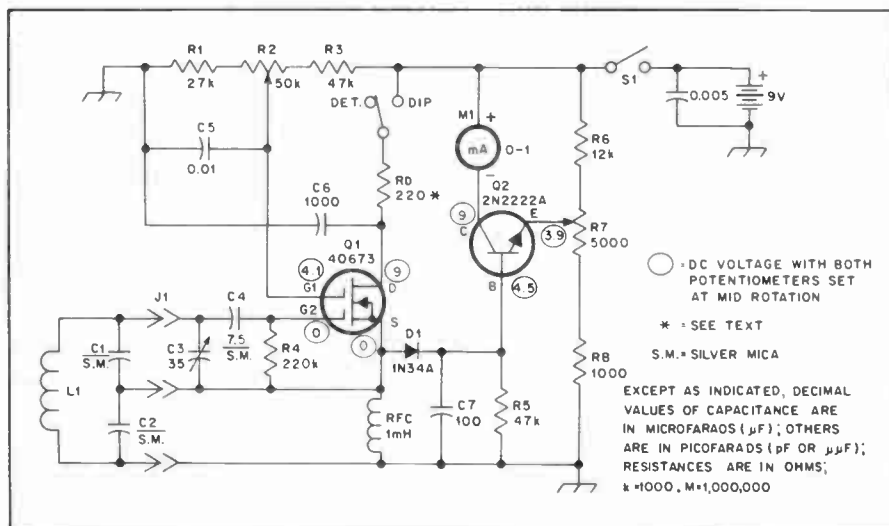


Fig. 36 — Schematic diagram of the dual-gate MOSFET dip meter. All resistors are 1/2-watt composition type. Capacitors are disk ceramic unless noted otherwise.  
 C1, C2 — See Table 1.  
 C3 — Variable capacitor, 35 pF, Millen 20035 or equiv.  
 D1 — 1N34A or equiv.  
 J1 — Socket, Amphenol type S4.  
 L1 — See Table 1 for values. All coils wound on Millen 45005 coil forms.  
 M1 — Edgewise panel meter, 0-1 mA, Calectro DI-905 or equiv.  
 Q1 — Dual-gate MOSFET, RCA 40673.  
 Q2 — Npn transistor, 2N2222A.  
 R2 — Potentiometer, 50 k $\Omega$ .  
 R7 — Potentiometer, 5000 ohms.  
 S1 — Spst on-off switch mounted on R7.

work. The frequency marker generator is a satisfactory signal source. In addition, its frequencies, although not continuously adjustable, are known far more precisely, since the usual signal-generator calibration is not highly accurate. For rough work the dip meter described in the next section will serve.

### A Dual-Gate MOSFET Dip Meter

The dip meter reverses the absorption-wave-meter procedure in that it supplies the rf power by incorporating a tunable oscillator from which the circuit being checked absorbs energy when this circuit and the oscillator are tuned to the same frequency and coupled together. In the vacuum-tube version the energy absorption causes a decrease or "dip" in the oscillator's rectified grid current, measured by a dc microammeter.

Described here and shown in Figs. 35 and 38 is a simple-to-build dip meter that covers 2.3 to 200 MHz. By opening switch S2 the circuit will function as a wave-meter, eliminating the need for two separate test instruments. The layout is not especially critical; however, you should try to keep the leads from the coil socket to the remainder of the circuitry as short as possible. This will help prevent unwanted resonances in the higher frequency ranges. Such parasitic resonances can cause false dips and erratic operation.

### Circuit Details

The circuit shown in Fig. 36 is a grounded-drain Colpitts oscillator employing an RCA n-channel, dual-gate MOSFET. The oscillation level, detected by a diode and amplified by a 2N2222A transistor, is displayed on a 0- to 1-mA meter. Transconductance of the MOSFET, and hence the output signal, is controlled by potentiometer R2 and reaches a maximum of 10-volts pk-pk at the source when  $V_{G2}$  (voltage from gate 2 to source) is set to +5 volts. The meter is adjusted for the desired deflection by R7. R8 must be selected according to the meter used and should be 100 ohms for a 1-mA meter movement. Frequency of oscillation depends on C1, C2, C3 and L1, and may reach 250 MHz or so when L1 is reduced to a hairpin.

Higher frequencies may be obtained by using a uhf D-MOSFET, such as a Signetics SD300, and by plugging C3 and L1 in series in a Clapp-oscillator configuration. The circuit is designed to operate from a 12-volt supply, but it also works fine with a 9-volt transistor-radio type of battery if the drain resistor ( $R_C$ ) is shorted. In either case the unit draws approximately 20 mA.

### Construction

Most of the components that comprise the oscillator and meter-driver circuits are mounted on a circuit board that measures approximately 1-1/4  $\times$  2-1/2 (32  $\times$  63



**Table 1**

Freq. Range MHz	C1 pF	C2 pF	L1 Turns
2.3-4	15	15	71-1/2
3.4-5.1	33	10	39-1/2
4.8-8	10	33	25-1/2
7.9-13	10	33	14-1/2
12.8-21.2	10	33	6-1/2
21-34	10	33	4-1/2
34-60	10	33	2-1/2
60-110	10	33	••
90-200	not used	not used	••

\*denotes a 1-1/2-turn coil of no. 18 enam. wire wound on a 1/2-inch (13-mm) form spaced 1/8 inch (3 mm) between turns. It should be placed so that the coil is near the top of the coil form.

\*\*denotes a hairpin loop made from flashing copper, 3/8-inch (9.5-mm) wide × 1-7/8-inch (89 mm) total length.

All other coils are wound with no 24 enam. wire.

mm) inches. The foil pattern is shown in Fig. 37. A Minibox that measures 5-1/2 × 3 × 2-1/2 inches (140 × 76 × 63 mm) contains the circuit board, variable capacitor, meter, controls and four-pin coil socket. Nine plug-in coils are used to cover the frequency range from 2.3 to 200 MHz. The coils are wound on Millen 45004 coil forms to which L brackets are mounted for the dial scale. Winding information is given in Table 1. Epoxy cement holds the aluminum brackets to the forms. The use of nine separate coils instead of five or six greatly expands the calibration scales so more accurate frequency measurements may be made. To reduce the fast tuning rate of the variable capacitor, a reduction vernier is used. It was removed from a Japanese vernier dial assembly. An aluminum bracket supports the variable capacitor inside the box. A rectangular piece of thin Plexiglas is used for the dial. A thin line is scribed down the center of the dial and is colored with a permanent-marking felt pen.

**Alignment**

A general-coverage receiver or another dip meter (calibrated) will be required to align the instrument. Plug in the appropriate coil for the range to be calibrated and turn the power switch to the ON position and advance R7 to approximately one-third scale. If a receiver is being used to calibrate the instrument, tune it to the lowest frequency covered by the particular coil in use. With the coil of the dip meter in close proximity to the receiver antenna terminal and the variable capacitor fully meshed, the dip-meter oscillator should be heard somewhere close to that frequency. Start by marking this frequency on the paper of thin cardboard dial attached to the plate. Next tune the receiver higher in frequency (approximately 100 kHz on the lower range coils and 1 MHz on the higher frequency ranges) and mark this frequency

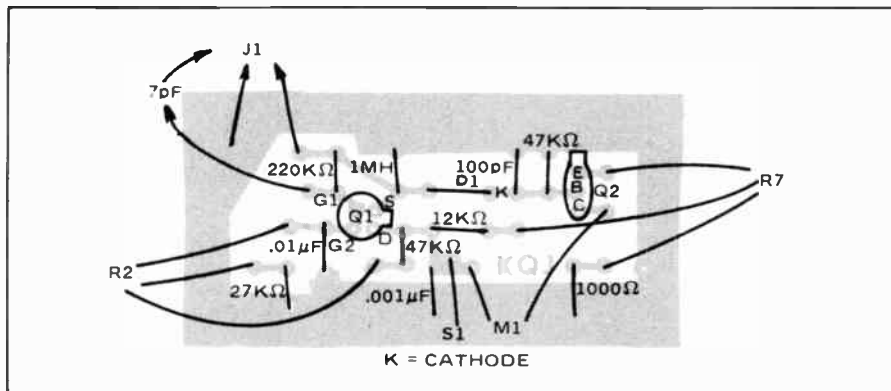


Fig. 37 — Here is the circuit board pattern for the dip meter — foil side of board. Grey areas represent the unetched copper pattern.

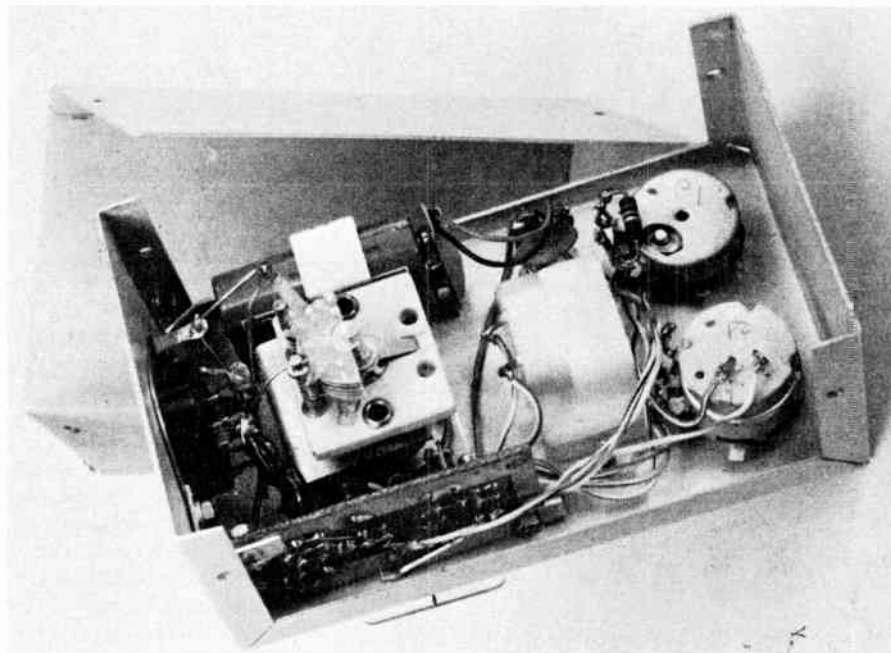


Fig. 38 — Interior view of the MOSFET dip meter. Just to the right of the variable capacitor is the edgewise panel meter. The battery can be seen just above the variable capacitor.

on the dial. Continue this procedure until the complete range of the particular coil has been marked. Do the same for each of the other coils. If another dip meter is used for the calibration process, it should be placed in the DETECTOR mode and used in a similar fashion as that of the receiver outlined above.

**Operating the Dip Meter**

The dip meter will check only resonant circuits, since nonresonant circuits or components will not absorb energy at a specific frequency. The circuit may be either lumped or linear (a transmission-line type circuit) provided only that it has enough Q to give sufficient coupling to the dip-meter coil for detectable absorption of rf energy. Generally the coupling is principally inductive, although at times there may be sufficient capacitive coupling between the meter and a circuit point that is at relatively high potential with

respect to ground to permit a reading. For inductive coupling, maximum energy absorption will occur when the meter is coupled to a coil (the same coupling rules which apply to any two coils are operative here) in the tuned circuit being checked, or to a high-current point in a linear circuit.

Because of distributed capacitance (and sometimes inductance) most circuits resonant at the lower amateur frequencies will show quasi-linear-type resonances at or close to the vhf region. A vhf dip meter will uncover these, often with beneficial results since such "parasitic" resonances can cause unwanted responses at harmonics of the intended frequency, or be responsible for parasitic oscillations in amplifiers. Caution must be used in checking transmission lines or antennas — and, especially, combinations of antenna and line — on this account, because these linear circuits have well-defined

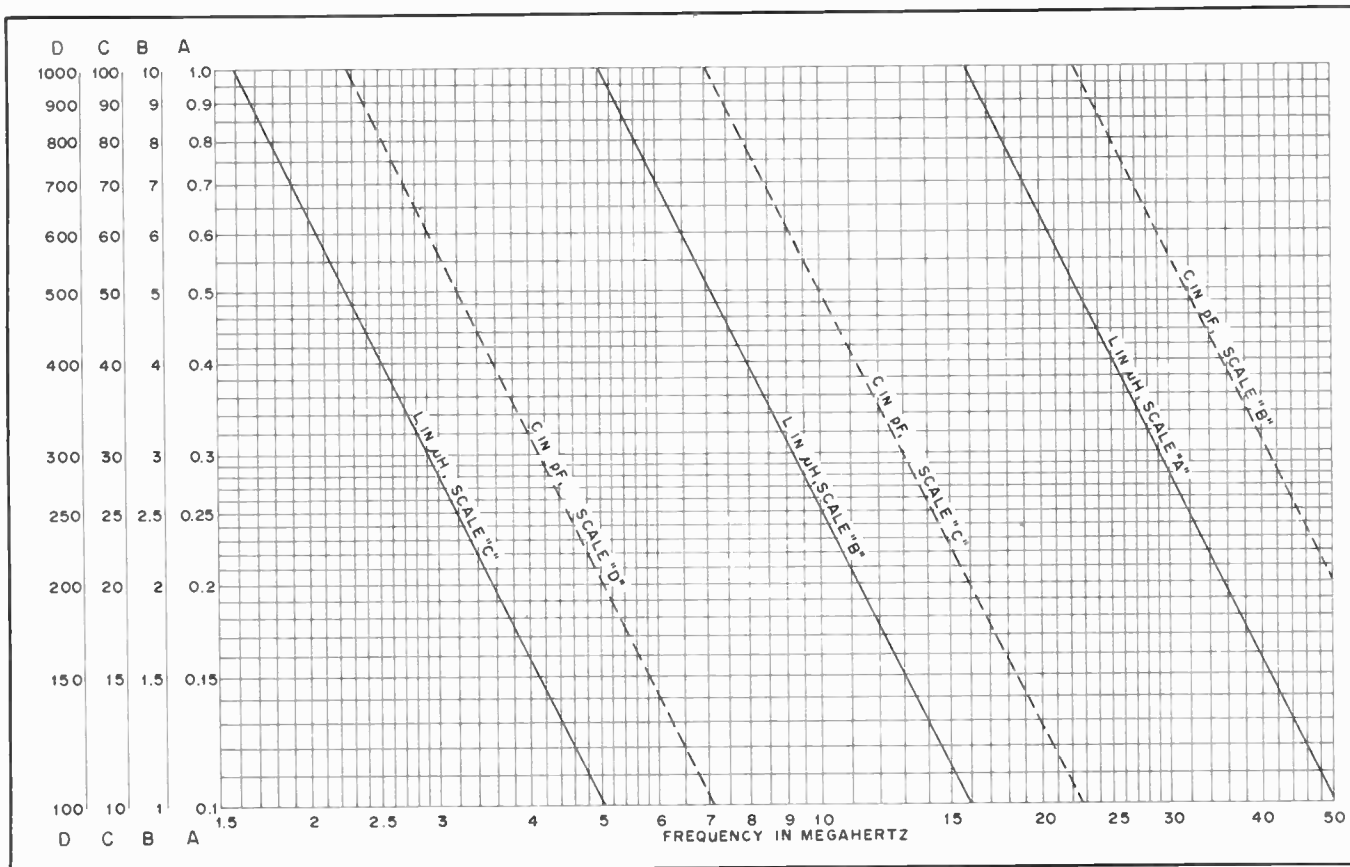


Fig. 39 — Chart for determining unknown values of L and C in the range of 0.1 to 100  $\mu\text{H}$  and 2 to 1000 pF, using standards of 100 pF and 5  $\mu\text{H}$ .

series of harmonic responses, based on the lowest resonant frequency, which may lead to false conclusions respecting the behavior of the system.

Measurements with the dip meter are essentially frequency measurements, and for best accuracy the coupling between the meter and circuit under checking must be as loose as will allow a perceptible dip. In this respect the dip meter is similar to the absorption wavemeter.

#### Measuring Inductance and Capacitance with the Dip Meter

With a carefully calibrated dip meter,

properly operated, inductance and capacitance in the values ordinarily used for the 1.5-50 MHz range can be measured with ample accuracy for practical work. The method requires two accessories: an inductance "standard" of known value, and a capacitance standard also known with reasonable accuracy. Values of 100 pF for the capacitance and 5  $\mu\text{H}$  for the inductance are convenient. The chart of Fig. 39 is based on these values.

The L and C standards can be quite ordinary components. A small silver-mica capacitor is satisfactory for the capacitance, since the customary tolerance

is  $\pm 5$  percent. The inductance standard can be cut from commercial machine-wound coil stock; if none is available, a homemade equivalent in diameter, turn spacing, and number of turns can be substituted. The inductance will be 5  $\mu\text{H}$  within amply close tolerances if the specifications in Fig. 40 are followed closely. In any case, the inductance can easily be adjusted to the proper value; it should resonate with the 100-pF capacitor at 7100 kHz.

The setup for measuring an unknown is shown in Fig. 41. Inductance is measured with the unknown connected to the standard capacitance. Couple the dip meter to the coil and adjust the meter for the dip, using the loosest possible coupling that will give a usable indication. Similar procedure is followed for capacitance measurement, except that the unknown is connected to the standard inductance. Values are read off the chart for the frequency indicated by the dip meter.

#### Coefficient of Coupling

The same equipment can be used for measurement of the coefficient of coupling between two coils. This simply requires two measurements of inductance (of one of the coils) with the coupled coil first open-circuited and then short-circuited. Connect the 100-pF standard capacitor to one coil and measure the inductance with the terminals of the

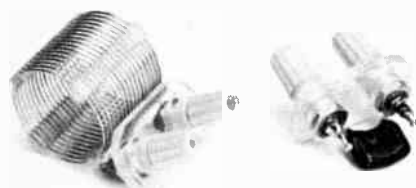


Fig. 40 — A convenient mounting, using binding-post plates, for L and C standards made from commercially available parts. The capacitor is a 100-pF silver mica unit, mounted so the lead length is as nearly zero as possible. The inductance standard, 5  $\mu\text{H}$ , is 17 turns of coil stock, 1-inch (25 mm) diameter, 16 turns per inch.

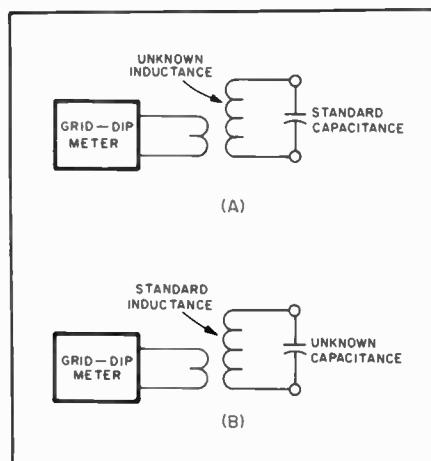


Fig. 41 — Setups for measuring inductance and capacitance with the dip meter.

second coil open. Then short the terminals of the second coil and again measure the inductance of the first. The coefficient of coupling is given by

$$k = \sqrt{1 - \frac{L_2}{L_1}}$$

where  
 k = coefficient of coupling  
 L1 = inductance of first coil with terminals of second coil open  
 L2 = inductance of first coil with terminals of second coil shorted

### Audio-Frequency Oscillators

Tests requiring an audio-frequency signal generally call for one that is a reasonably good sine wave, and best oscillator circuits for this are RC-coupled, operating as nearly Class A amplifiers as possible. Variable frequency covering the entire audio range is needed for determining frequency response of audio amplifiers, but this is a relatively unimportant type of test in amateur equipment. The variable-frequency of signal generator is best purchased complete; kits are readily available at prices that compare very favorably with the cost of parts.

For most phone-transmitter testing, and for simple trouble shooting in af amplifiers, an oscillator generating one or two frequencies with good wave form is adequate. A "two-tone" (dual) oscillator is particularly useful for testing sideband transmitters, and adjusting them for on-the-air use.

The circuit of a simple RC oscillator useful for general test purposes is given in Fig. 42. This "Twin-T" arrangement gives a wave form that is satisfactory for most purposes, and by choice of circuit constants the oscillator can be operated at any frequency in the usual audio range. R1, R2 and C1 form a low-pass type network, while C2C3R3 is high-pass. As the phase shifts are opposite, there is only one frequency at which the total phase shift from collector to base is 180 degrees, and oscillation will occur at this frequency. Optimum operation results when C1 is approximately twice the capacitance of C2 or C3, and R3 has a resistance about 0.1 that of R1 or R2 (C2 = C3 and R1 = R2). Output is taken across C1, where the harmonic distortion is least. A relatively high-impedance load should be used — 0.1 megohm or more.

A small-signal af transistor is suitable for Q1. Either npn or pnp types can be used, with due regard for supply polarity. R4, the collector load resistor, must be large enough for normal amplification, and may be varied somewhat to adjust the operating conditions for best waveform.

### A Wide-Range Audio Oscillator

A wide-range audio oscillator that will provide a moderate output level can be

built from a single 741 operational amplifier (Fig. 43). Power is supplied by two 9-volt batteries, from which the circuit draws 4 mA. The frequency range is selectable from 15 Hz to 150 kHz, although a 1.5- to 15-Hz range can be included with the addition of two 5-μF nonpolarized capacitors and an extra switch position. Distortion is approximately one percent. The output level under a light load (10 k ohms) is 4 to 5 volts. This can be increased by using higher battery voltages, up to a maximum of plus and minus 18 volts, with a corresponding adjustment of Rf.

Pin connections shown are for the TO-5 case. If another package configuration is used, the pin connections may be different. Rf (220 ohms) is trimmed for an output level about five percent below clipping. This should be done for the temperature at which the oscillator will normally operate, as the lamp is sensitive to ambient temperature. Note that the output of this oscillator is direct coupled. If you are connecting this unit into circuits where dc voltage is present, use a coupling capacitor. As with any solid-state equipment, be cautious around plate circuits of tube-type equipment, as the voltage spike caused by charging a coupling capacitor may destroy the IC. This unit was originally described by Schultz in November 1974 *QST*.

### Resistors at Radio Frequencies

Measuring equipment, in some part of its circuit, often requires essentially pure resistance — that is, resistance exhibiting only negligible reactive effects on the frequencies at which measurement is intended. Of the resistors available to amateurs, this requirement is met only by small composition (carbon) resistors. The inductance of wire-wound resistors makes them useless for amateur frequencies.

The reactances to be considered arise from the inherent inductance of the resistor itself and its leads, and from small stray capacitances from one part of the resistor to another and to surrounding conductors. Although both the inductance and capacitance are small, their reactances become increasingly important as the frequency is raised. Small composition resistors, properly mounted, show negligible capacitive reactance up to 100 MHz or so in resistance values up to a few hundred ohms; similarly, the inductive reactance is negligible in values higher than a few hundred ohms. The optimum resistance region in this respect is in the 50 to 200-ohm range, approximately.

Proper mounting includes reducing lead length as much as possible, and keeping the resistor separated from other resistors and conductors. Care must also be taken in some applications to ensure that the resistor, with its associated components, does not form a closed loop into which a

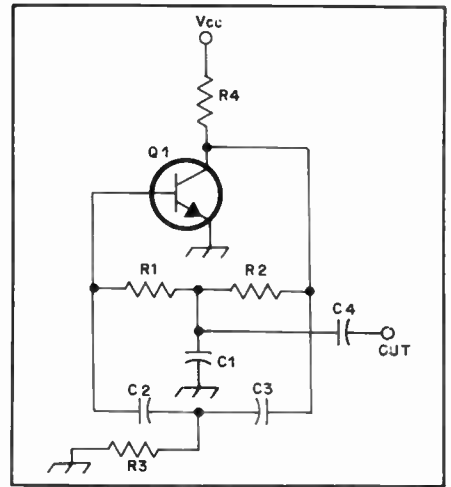


Fig. 42 — Twin-T audio oscillator circuit. Representative values for R1-R2 and C1 range from 18 kΩ and 0.05 μF for 750 Hz to 15 kΩ and 0.02 μF for 1800 Hz. For the same frequency range, R3 and C2-C3 vary from 1800 ohms and 0.02 μF to 1500 ohms and 0.01 μF. R4 should be approximately 3300 ohms. C4, the output coupling capacitor, can be 0.05 μF for high-impedance loads.

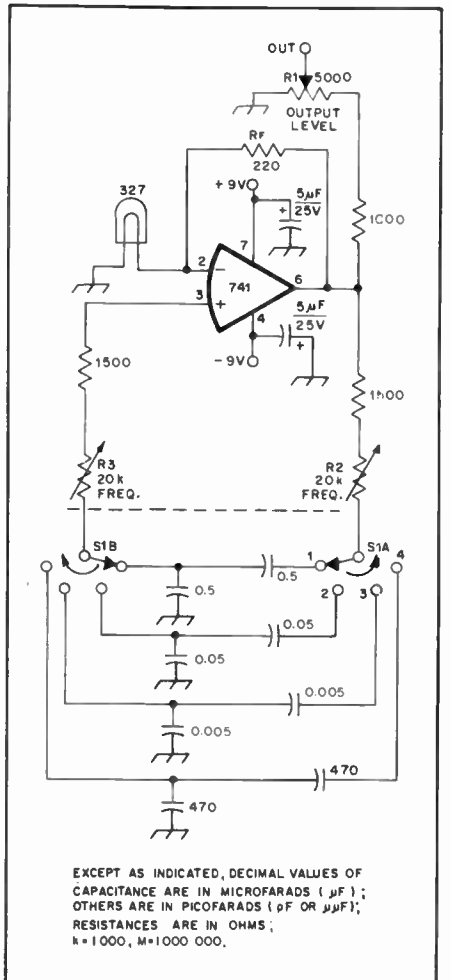


Fig. 43 — A simple audio oscillator that provides a selectable frequency range. R2 and R3 control the frequency and R1 varies the output level.



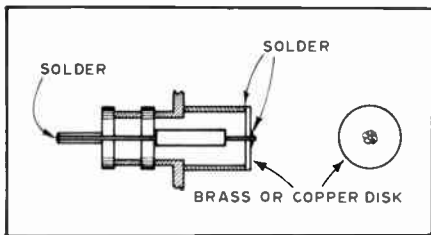


Fig. 44 — Dummy antenna made by mounting a composition resistor in a PL-259 coaxial plug. Only the inner portion of the plug is shown; the cap screws on after the assembly is completed.

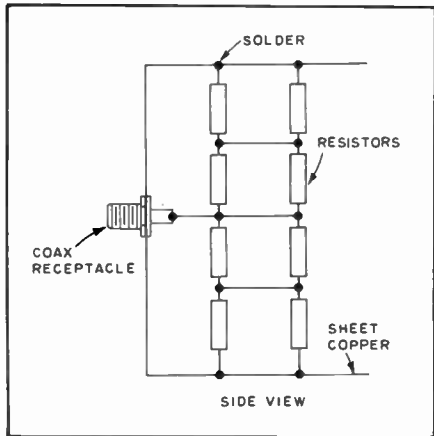


Fig. 45 — Using resistors in series-parallel to increase the power rating of a small dummy antenna. Mounted in this way on pieces of flat copper, inductance is reduced to a minimum. Eight 100-ohm 2-watt composition resistors in two groups, each four resistors in parallel, can be connected in series to form a 50-ohm dummy. The open construction shown permits free air circulation.

voltage could be induced magnetically.

So installed, the resistance is essentially pure. In composition resistors the skin effect is very small, and the rf resistance up to vhf is very closely the same as the dc resistance.

### Dummy Antennas

A *dummy antenna* is simply a resistor that, in impedance characteristics, can be substituted for an antenna or transmission line for test purposes. It permits leisurely transmitter testing without radiating a signal. (The amateur regulations strictly limit the amount of "on-the-air" testing that may be done.) It is also useful in testing receivers, in that electrically it resembles an antenna, but does not pick up external noise and signals, a desirable feature in some tests.

For transmitter tests the dummy antenna must be capable of dissipating safely the entire power output of the transmitter. Since for most testing it is desirable that the dummy simulate a perfectly-matched transmission line, it should be a pure resistance, usually of approximately 52 or 73 ohms. This is a severe limitation in home construction, because nonreactive resistors of more than a few watts rated

safe dissipation are very difficult to obtain. (There are, however, dummy antenna kits available that can handle up to a kilowatt).

For receiver and minipower transmitter testing an excellent dummy antenna can be made by installing a 51- or 75-ohm composition resistor in a PL-259 fitting as shown in Fig. 44. Sizes from one half to two watts are satisfactory. The disk at the end helps reduce lead inductance and completes the shielding. Dummy antennas made in this way have good characteristics through the vhf bands as well as at all lower frequencies.

### Increasing Power Ratings

More power can be handled by using a number of 2-watt resistors in parallel, or series-parallel, but at the expense of introducing some reactance. Nevertheless, if some departure from the ideal impedance characteristics can be tolerated this is a practical method for getting increased dissipations. The principal problem is stray inductance which can be minimized by mounting the resistors on flat copper strips or sheets, as suggested in Fig. 45.

The power rating on resistors is a *continuous* rating in free air. In practice, the maximum power dissipated can be increased in proportion to the reduction in duty cycle. Thus with keying, which has a duty cycle of about one half, the rating can be doubled. With sideband the duty cycle is usually not over about one-third. The best way of judging is to feel the resistors occasionally (with power off); if too hot to touch, they may be dissipating more power than they are rated for.

### The Oscilloscope

The electrostatically deflected cathode-ray tube, with appropriate associated equipment, is capable of displaying both low- and radio-frequency signals on its fluorescent screen, in a form which lends itself to ready interpretation. (In contrast, the magnetically deflected television picture tube is not at all suitable for measurement purposes.) In the usual display presentation, the fluorescent spot moves across the screen horizontally at some known rate (*horizontal deflection* or *horizontal sweep*) and simultaneously is moved vertically by the signal voltage being examined (*vertical deflection*). Because of the retentivity of the screen and the eye, a rapidly deflected spot appears as a continuous line. Thus a varying signal voltage causes a *pattern* to appear on the screen.

Conventionally, oscilloscope circuits are designed so that in vertical deflection the spot moves upward as the signal voltage becomes more positive with respect to ground, and vice versa (there are exceptions, however). Also, the horizontal deflection is such that with an ac sweep voltage — the simplest form —

positive is to the right; with a *linear sweep* — one which moves the spot at a uniform rate across the screen and then at the end of its travel snaps it back very quickly to the starting point — *time* progresses to the right.

Most cathode-ray tubes for oscilloscope work require a deflection amplitude of about 50 volts per inch. For displaying small signals, therefore, considerable amplification is needed. Also, special circuits have to be used for linear deflection. The design of amplifiers and linear deflection circuits is complicated, and extensive texts are available. For checking modulation of transmitters, a principal amateur use of the scope, quite simple circuits suffice. A 60-Hz voltage from the power line makes a satisfactory horizontal sweep, and the voltage required for vertical deflection can easily be obtained from transmitter rf circuits without amplification.

For general measurement purposes amplifiers and linear deflection circuits are needed. The most economical and satisfactory way to obtain a scope having these features is to assemble one of the many kits available.

### Simple Oscilloscope Circuit

Fig. 46 is an oscilloscope circuit that has all the essentials for modulation monitoring: controls for centering, focusing, and adjusting the brightness of the fluorescent spot; voltage dividers to

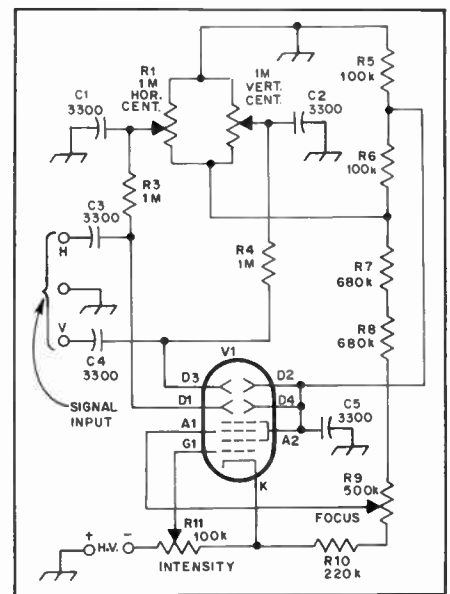


Fig. 46 — Oscilloscope circuit for modulation monitoring. Constants are for 1500- to 2500-volt high-voltage supply. For 1000 to 1500 volts, omit R8 and connect the bottom end of R7 to the top end of R9. C1-C5, incl. — 1000-volt disk ceramic. R1, R2, R9, R11 — Volume-control type, linear taper. R9 and R11 must be well insulated from chassis. R3, R4, R5, R6, R10 — 1/2 watt. R7, R8 — 1 watt. V1 — Electrostatic-deflection cathode-ray tube, 2- to 5-inch (51 to 127-mm). Base connections and heater ratings vary with type chosen.



supply proper electrode potentials to the cathode-ray tube; and means for coupling the vertical and horizontal signals to the deflection plates.

The circuit can be used with electrostatic-deflection tubes from two to five inches in face diameter, with voltages up to 2500. Either set of deflecting electrodes (D1-D2, or D3-D4) may be used for either horizontal or vertical deflection, depending on how the tube is mounted.

In Fig. 46, the centering controls are not too high above electrical ground, so they do not need special insulation. However, the focusing and intensity controls are at a high voltage above ground and therefore should be carefully insulated. Insulated couplings or extension shafts should be used.

The tube should be protected from stray magnetic fields, either by enclosing it in an iron or steel box or by using one of the special CR tube shields available. If the heater transformer (or other transformer) is mounted in the same cabinet, care must be used to place it so the stray field around it does not deflect the spot. The spot cannot be focused to a fine point when influenced by a transformer field. The heater transformer must be well insulated, and one side of the heater should be connected to the cathode. The high-voltage dc can be taken from the transmitter plate supply; the current required is negligible.

Methods for connecting the oscilloscope to a transmitter for checking or monitoring modulation are given in earlier chapters.

### Quasi-Linear Sweep

For wave-envelope patterns that require a fairly linear horizontal sweep, Fig. 47 shows a method of using the substantially linear portion of the 60-Hz sine wave — the "center" portion where the wave goes through zero and reverses polarity. A 60-Hz transformer with a center-tapped secondary winding is required. The voltage should be sufficient to deflect the spot well off the screen on both sides — 250 to 350 volts, usually. With such "over-deflection" the sweep is fairly linear, but it is as bright on retrace as on left-to-right. To blank it in one direction, it is necessary to couple the ac to the no. 1 grid of the CR tube as shown.

### Lissajous Figures

When sinusoidal ac voltages are applied to both sets of deflecting plates in the oscilloscope the resultant pattern depends on the relative amplitudes, frequencies and phases of the two voltages. If the ratio between the two frequencies is constant and can be expressed in integers, a stationary pattern will be produced.

The stationary patterns obtained in this way are called *Lissajous figures*. Examples of some of the simpler Lissajous figures are given in Fig. 48. The frequency ratio is

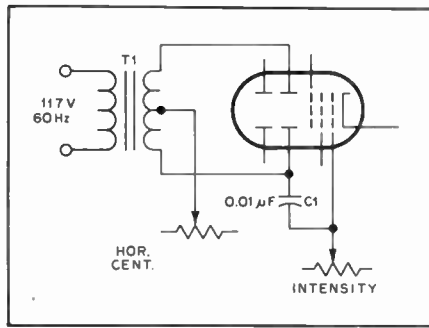


Fig. 47 — A quasi-linear time base for an oscilloscope can be obtained from the "center" portion of a sine-wave. Coupling the ac to the grid gives intensity modulation that blanks the retrace.

C1 — Ceramic capacitor of adequate voltage rating.

T1 — 250- to 350-volt center-tapped secondary. If voltage is too high, use dropping resistor in primary side.

found by counting the number of loops along two adjacent edges. Thus in the third figure from the top there are three loops along a horizontal edge and only one along the vertical, so the ratio of the vertical frequency to the horizontal frequency is 3:1. Similarly, in the fifth figure from the top there are four loops along the horizontal edge and three along the vertical edge, giving a ratio of 4:3. Assuming that the known frequency is applied to the horizontal plates, the unknown frequency is

$$f_2 = \frac{n_2}{n_1} f_1$$

where  $f_1$  = known frequency applied to horizontal plates

$f_2$  = unknown frequency applied to vertical plates

$n_1$  = number of loops along a vertical edge

$n_2$  = number of loops along a horizontal edge.

An important application of Lissajous figures is in the calibration of audio-frequency signal generators. For very low frequencies the 60-Hz power-line frequency is held accurately enough to be used as a standard in most localities. The medium audio-frequency range can be covered by comparison with the 440- and 600-Hz modulation on the WWV transmissions. It is possible to calibrate over a 10:1 range, both upward and downward from each of the latter frequencies and thus cover the audio range useful for voice communication.

An oscilloscope having both horizontal and vertical amplifiers is desirable, since it is convenient to have a means for adjusting the voltages applied to the deflection plates to secure a suitable pattern size.

### A Tester for FET and Bipolar Transistors

The circuit shown is intended solely as a

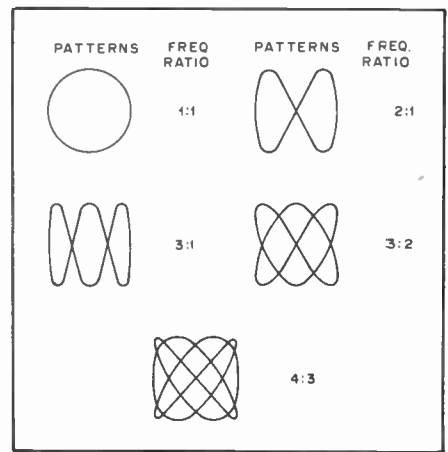


Fig. 48 — Lissajous figures and corresponding frequency ratios for a 90-degree phase relationship between the voltages applied to the two sets of deflecting plates.

tester for npn and pnp transistors, junction FETs, and dual-gate MOSFETs. This equipment is not for use in checking audio or high-power rf transistors.

The circuit of Fig. 50 is an oscillator which is wired so that it will test various small-signal transistors by switching the battery polarity and bias voltage. A crystal for the upper range of the hf spectrum is wired into the circuit permanently, but could be installed in a crystal socket if the builder so desires. A 20-MHz crystal was chosen for this model. Any hf crystal cut for fundamental mode operation can be used.

When testing FETs the bias switch, S3, is placed in the FET position, thus removing R2 from the circuit. However, when testing bipolar transistors the switch position must be changed to BIPOL so that forward bias can be applied to the base of the bipolar transistor under test. R1 is always in the circuit, and serves as a gate-leak resistor for FETs being evaluated. It becomes part of the bias network when bipolars are under test. C1 is used for feedback in combination with the internal capacitances of the transistors being checked. Its value may have to be changed experimentally if crystals for lower frequencies are utilized in the circuit. Generally speaking, the lower the crystal frequency, the greater the amount of capacitance needed to assure oscillation. Use only that amount necessary to provide quick starting of the oscillator.

Components R3 and R4 are used as a voltage divider to provide bias for dual-gate MOSFETs. C2 is kept small in value to minimize loading of the oscillator by the low-impedance voltage doubler, D1 and D2. Rectified rf from the oscillator is monitored on M1. Meter deflection is regulated manually by means of control R5. S1 is used to select the desired supply voltage polarity — negative ground for testing n-channel FETs



Fig. 49 — Exterior view of the transistor/FET tester.



Fig. 51 — The completed crystal/transistor checker.

and npn bipolars, and a positive ground when working with p-channel and pnp devices.

When testing MOSFETs which are not gate protected (3N140 for one), make certain that the transistor leads are shorted together until the device is seated in the test socket. Static charges on one's hands can be sufficiently great to damage the insulation within the transistor. Use a single strand of wire from some no. 22 or 24 stranded hookup wire, wrapping it two or three times around the pigtailed of the FET as close to the transistor body as possible. After the FET is plugged into the socket, unwrap the wire and perform the tests. (It's not a bad idea to have an earth ground connected to the case of the tester when checking unprotected FETs.) Put the shorting wire back on the FET leads before removing the unit from the tester.

The meter indication is significant in checking any type of transistor. If the device is open, shorted, or extremely leaky, no oscillation will take place, and the meter will not deflect. The higher the meter reading, the greater the vigor of the transistor at the operating frequency. High meter readings suggest that the transistor is made for vhf or uhf service, and that its beta is medium to high. Lower readings may indicate that the transistor is designed for hf use, or that it has very low gain. Transistors that are known to be good but will not cause the circuit to oscillate are most likely made for low-frequency or audio applications.

#### A Tester for Crystals and Bipolar Transistors

The circuit of Fig. 52 is intended primarily to test surplus crystals and bipolar transistors. It uses a Pierce oscillator. Battery polarity can be switched to allow testing of npn or pnp transistors. Crystal quality is indicated on M1. The greater the crystal activity, the higher the meter reading. A suitable transistor for use at Q1 (when testing crystals) is the 2N4124, MPS3563, HEP S0014, or Radio Shack 276-2009. All have  $f_T$  ratings well into the vhf spectrum, and each has reasonably high beta. The two characteristics make the devices ideal as general-purpose oscillators.

This tester will work well from the upper hf range down to at least 455 kHz. S1 is used to change the value of feedback capacitance. The lower the frequency of operation, the greater the amount of capacitance required.

A transistor can be checked by plugging the unknown type into the panel socket while using a crystal of known frequency and condition. Both testers can be used as calibrators by inserting crystals for band-edge checking. The frequencies of unknown crystals can be checked by listening to the output from the test oscillators on a calibrated receiver or while using a frequency counter connected

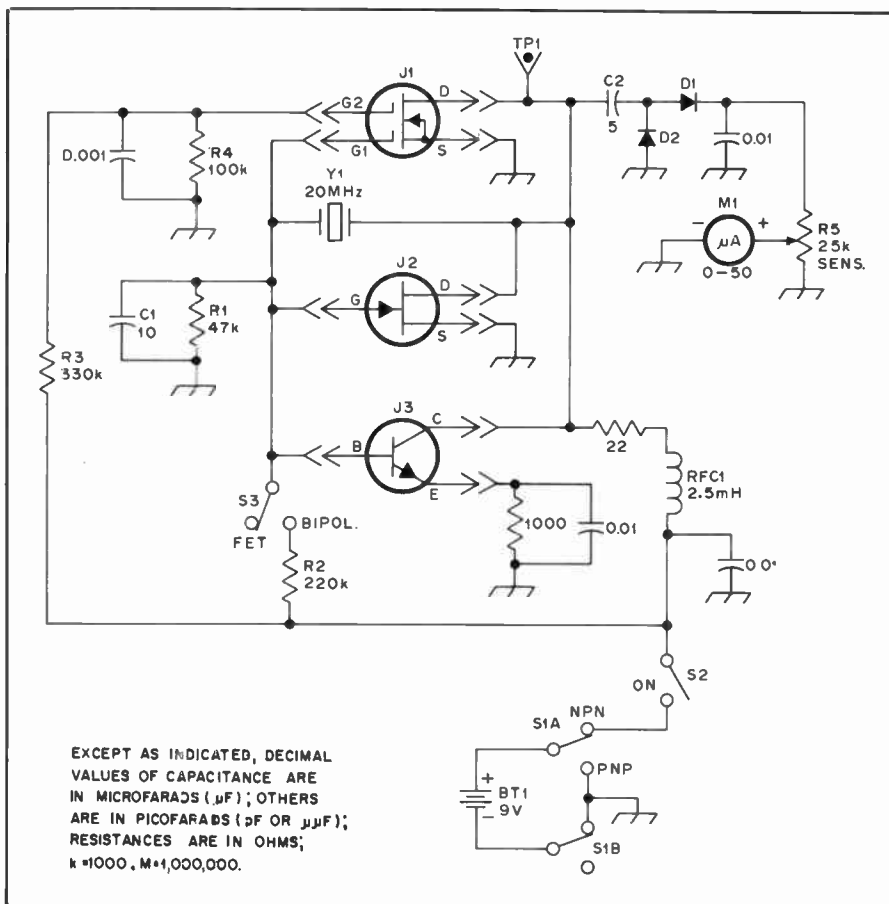


Fig. 50 — Schematic diagram of the transistor tester. Capacitors are disk ceramic or mica. Resistors are 1/2- or 4-watt composition except for R5. Numbered components not appearing in parts list are so designated for text discussion.

BT1 — Small 9-V transistor-radio battery.  
D1, D2 — 1N34A germanium diode or equiv.  
J1 — Four-terminal transistor socket.  
J2, J3 — Three-terminal transistor socket.  
M1 — Microampere meter. Calectro D1-910 used here.

R5 — 25-k $\Omega$  linear-taper composition control with switch.  
RFC1 2.5-mH rf choke  
S1 — Two-pole double-throw miniature toggle.  
S2 — Part of R5.  
S3 — Spst miniature toggle.  
Y1 — Surplus crystal (see text).





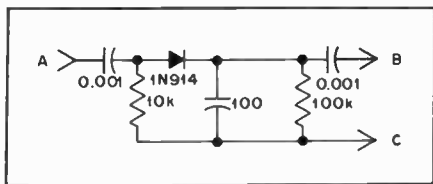


Fig. 54 — A simple detector which can be used when aligning ssb and fm receivers (see text for details).

around the diode itself should follow good vhf practices with short leads and direct placement.

### Theory of Operation

Q1 and Q2 are used in a cross-coupled multivibrator circuit, operating at approximately 700 Hz. The value of C1 is greater than C2 to cause the duty cycle to favor the conduction of Q2 slightly. When Q2 conducts, the pulse is coupled to Q3 via C3, turning on Q3 and causing current flow through R7, CR1 and R8.

The diode generates broadband noise which is passed through R9 to the output. R7, C4 and C5 form a low-pass filter to prevent high-order harmonics of the switching pulses from appearing in the output.

The influence of stray rf signals entering the device under test through the generator may be minimized by shielding the components shown. A simple box may be built by using pc-board scraps. For best match, this source should be connected directly to the input of the device under test; therefore, the unit is equipped with a male connector. This matching becomes a

greater consideration as the frequency of interest increases.

### Addendum

The gated noise source was first developed in November, 1975. Subsequently, some interesting things have been learned regarding its application. Some contemporary receivers and transceivers cannot be operated in the a-m mode, and consequently the noise source seems not to operate. The detection of noise is the process by which the noise source operates; therefore, it will not work through an fm detector, nor will it work through a product detector since one of the terms of the detection (the noise) is not coherent.

The "scope" jack on most receivers is loosely coupled to the i-f amplifier, preceding the detector. A wide-band scope connected to this point will show the train of pulses and eliminate the need for aural detection. The alignment of the later i-f stages of a system should have the least impact on the noise performance, and maximum signal response will always occur at the same setting. With this thought in mind, the simple prototype detector will generally work for aural a-m detection. Connect point A to the last i-f amplifier plate or collector. Connect point B to the audio amplifier, at or near the volume control and ground point C. With this arrangement the normal detector output is turned down with the volume control, and the temporary detector provides a-m detection.

The gated noise source has been used for literally hundreds of applications and

has proved to be a powerful yet simple addition to the test bench. While no guarantee of duplication may be made, these units develop approximately 18 dB of excess noise in the region of 50-300 MHz. This unit was originally described by Hartsen in January 1977 *QST*.

### RF Impedance Bridge for Coax Lines

The bridge shown in Figs. 55 through 57 may be used to measure unknown complex impedances at frequencies below 30 MHz. Measured values are of equivalent series form,  $R + jX$ . The useful range of the instrument is from about 5 to 400 ohms if the unknown load is purely resistive, or 10 to 150 ohms resistive component in the presence of reactance. The reactance range is from 0 to approximately 100 ohms for either inductive or capacitive loads. Although the instrument cannot indicate impedances with the accuracy of a laboratory type of bridge, its readings are quite adequate for the measurement and adjustment of antenna systems for amateur use, including the taking of line lengths into account with a Smith chart or Smith transmission-line calculator.

The bridge incorporates a differential capacitor, C1, to obtain an adjustable ratio for measurement of the resistive component of the load. The capacitor consists of two identical sections on the same frame, arranged so that when the shaft is rotated to increase the capacitance of one section, the capacitance of the other section decreases. The capacitor is adjusted for a null reading on M1, and its settings are calibrated in terms of resistance at J3 so the unknown value can be read off the calibration. A coil-and-capacitor combination is used to determine the amount and type of reactance, inductive or capacitive. L1 and C2 in the bridge circuit are connected in series with the load. The instrument is initially balanced at the frequency of measurement with a purely resistive load connected at J3, so that the reactances of L1 and of C2 at its midsetting are equal. Thus, these reactances cancel each other in this arm of the bridge. With an unknown complex-impedance load then connected at J3, the setting of C2 is varied either to increase or decrease the capacitive reactance, as required, to cancel any reactance present in the load. If the load is inductive more capacitive reactance is required from C2 to obtain a balance, indicated by a null on M1, with less reactance needed from C2 if the load is capacitive. The settings of C2 are calibrated in terms of the value and type of reactance at J3. Because of the relationship of capacitive reactance to frequency, the calibration for the dial of C2 is valid at only one frequency. It is therefore convenient to calibrate this dial for equivalent reactances at 1 MHz, as shown in Fig. 58. Frequency corrections



Fig. 55 — An RCL bridge for measuring unknown values of complex impedances. A plug-in coil is used for each frequency band. The bridge operates at an rf input level of about 5 volts; pickup-link assemblies for use with a grid-dip oscillator are shown. Before measurements are made, the bridge must be balanced with a nonreactive load connected at its measurement terminals. This load consists of a resistor mounted inside a coaxial plug, shown in front of the instrument at the left. The aluminum box measures 4-1/4 x 10-3/4 x 6-1/8 inches (108 x 273 x 156 mm) and is fitted with a carrying handle on the left end and self-sticking rubber feet on the right end and bottom. Dials are Millen no. 10009 with skirts reversed and calibrations added.



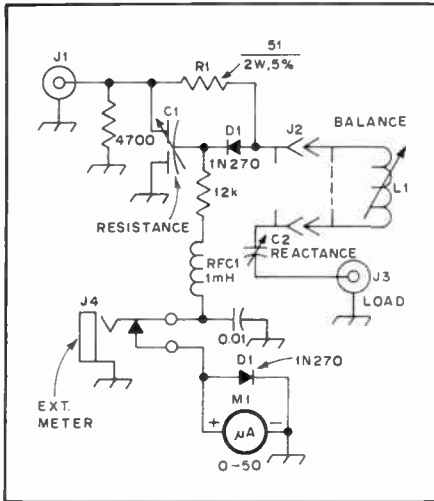


Fig. 56 — Schematic diagram of the impedance bridge. Capacitance is in microfarads, resistances are in ohms. Resistors are 1/2-W, 10-percent tolerance unless otherwise indicated.

- C1 — Differential capacitor, 11-161 pF per section Millen 28801.
- C2 — 17.5-327 pF with straight-line capacitance characteristic, Hammarlund RMC-325-S.
- D1, D2 — Germanium diode, high back resistance.
- J1, J3 — Coaxial connectors, chassis type.
- J2 — To mate plug of L1, ceramic.
- J4 — Phone jack, disconnecting type.
- L1 — See text and Table 1.
- M1 — 0-50  $\mu$ A dc, Simpson Model 1223 Bold-Vue, Cat. No. 15580 or equiv.
- R1 — For text reference.
- RFC1 — Subminiature rf choke, Miller 70F103AI or equiv.

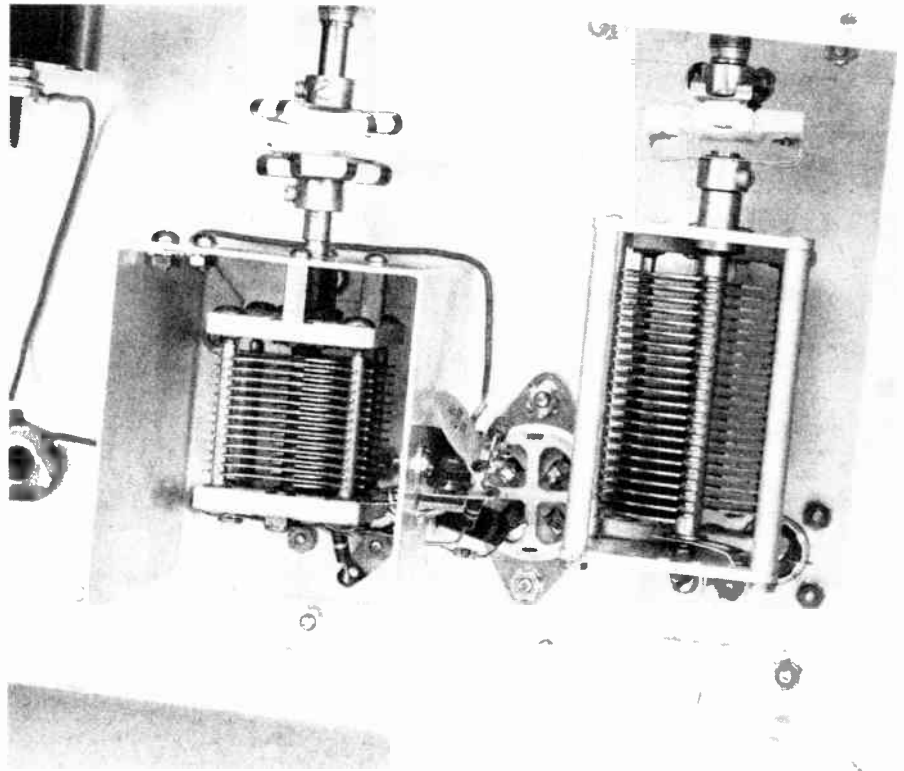


Fig. 57 — All components except the meter are mounted on the top of the box. C1 is visible inside the shield at the left, with C2 at the right and J2 mounted between them. J1 is hidden beneath C1 in this view, a part of J3 may be seen in the lower right corner of the box. Components for the dc metering circuit are mounted on a tie-point strip which is affixed to the shield wall for C1; all other components are interconnected with very short leads. The 4700-ohm input resistor is connected across J1.

may then be made simply by dividing the reactance dial reading by the measurement frequency in megahertz.

### Construction

In any rf-bridge type of instrument, the leads must be kept as short as possible to reduce stray reactances. Placement of component parts, while not critical, must be such that lead lengths greater than about 1/2 inch (13 mm) (except in the dc metering circuit) are avoided. Shorter leads are desirable, especially for R1, the "standard" resistor for the bridge. In the unit photographed, the body of this resistor just fits between the terminals of C1 and J2 where it is connected. C1 should be enclosed in a shield and connections made with leads passing through holes drilled through the shield wall. The frames of both variable capacitors, C1 and C2, must be insulated from the chassis, with insulated couplings used on the shafts. The capacitor specified for C1 has provisions for insulated mounting. C2 is mounted on 1-inch (25 mm) ceramic insulating pillars.

Band-switching arrangements for L1 complicate the construction and contribute to stray reactances in the bridge circuit. For these reasons plug-in coils are used at L1, one coil for each band over which the instrument is used. The coils must be adjustable, to permit initial

balancing of the bridge with C2 set at the zero-reactance calibration point. Coil data are given in Table 2. Millen 45004 coil forms with the coils supported inside provide a convenient method of constructing these slug-tuned plug-in coils. A phenolic washer cut to the proper diameter is epoxied to the top or open end of each form, giving a rigid support for mounting of the coil by its bushing. Small knobs for 1/8-inch (3.2 mm) shafts, threaded with a no. 6-32 tap, are screwed onto the coil slug-tuning screws to permit ease of adjustment without a tuning tool. Knobs with setscrews should be used to prevent slipping. A ceramic socket to

mate with the pins of the coil form is used for J2.

### Calibration

The resistance dial of the bridge may be calibrated by using a number of 1/2- or 1-watt 5-percent-tolerance composition resistors of different values in the 5- to 400-ohm range as loads. For this calibration, the appropriate frequency coil must be inserted at J2 and its inductance adjusted for the best null reading on the meter when C2 is set with its plates half meshed. For each test resistor, C1 is then adjusted for a null reading. Alternate adjustment of L1 and C1 should be made

Table 2  
Coil Data for RFI Impedance Bridge

Band	Nominal Inductance Range ( $\mu$ H)	Frequency Coverage (MHz)	Coil Type or Data
80	6.5 - 13.8	3.2 - 4.8	28 turns no. 30 enam. wire close-wound on Miller form 42A000CBI.
40	2.0 - 4.4	5.8 - 8.5	Miller 42A336CBI or 16 turns no. 22-enam. wire close-wound on Miller form 42A000CBI.
20	0.6 - 1.1	11.5 - 16.6	8 turns no. 18 enam. wire close-wound on Miller form 42A000CBI.
15	0.3 - 0.48	18.5 - 23.5	4-1/2 turns no. 18 enam. wire close-wound on Miller form 42A000CBI.
10	0.18 - 0.28	25.8 - 32.0	3 turns no. 16 or 18 enam. or tinned bus wire spaced over 1/4-inch (6.3-mm) winding length on Miller form 42A000CBI.





Fig. 61 — The deviation meter is constructed in a Calectro aluminum box. A four-position switch is at the lower right. The crystal plugs in on the left, with the frequency adjusting trimmer just below. A short whip or pickup wire can be plugged into the phono connector that is mounted on the back wall of the box.

used to check the audio deviation of an fm transmitter, or to determine how far off frequency the transmitter carrier may be. It can also be used as a signal source to aid in setting a receiver on frequency, if a crystal of known accuracy is plugged into the oscillator.

### The Circuit

As shown in Fig. 62 a transistor oscillator is used to feed energy to a mixer diode, D1. A small pickup antenna is connected to the diode also, thereby coupling a signal from a transmitter to the mixer. The output from the diode, in the audio range, is amplified by U1, a Dual 747 operational amplifier. The Dual 747 amplifies and clips the audio, providing a square wave of nearly constant amplitude at the output. This square wave is applied to a rectifier circuit through variable coupling capacitors and a selector switch. A meter is connected to the rectifier circuit to read the average current. Since the amplitude of the input is constant, a change in frequency will produce a change of average current. Three ranges are selected by S1, with individual trimmers being placed in the circuit for calibration.

### Construction

An aluminum box is used for the enclosure, 6-1/4 × 3-1/2 × 2 inches (159 × 89 × 51 mm). A meter switch, variable capacitor, and crystal socket are all mounted on the top panel. A small pc board is fastened to the meter terminals as a convenient support. This board contains the IC and associated circuit components, as well as the rectifier diodes.

The oscillator is constructed on a separate pc board which mounts behind the crystal socket and variable capacitor. Metal spacers and 4-40 screws and nuts are used to fasten the oscillator board in place. A shield of pc board is placed between the oscillator and the amplifier to provide isolation. Power for the instrument is furnished by a 9-volt transis-

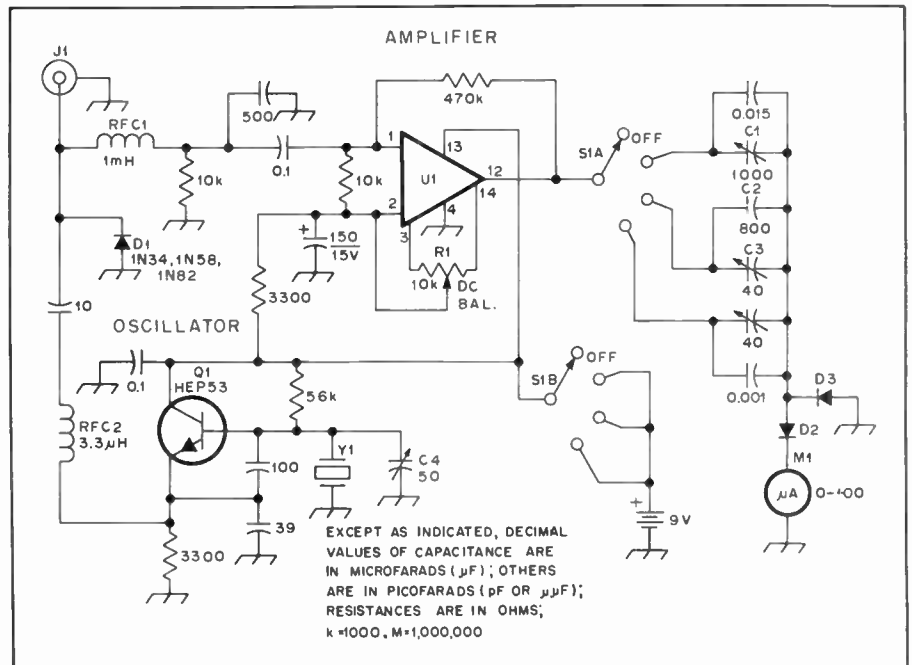


Fig. 62 — Circuit of the deviation meter. Connections shown are for a 747 dual op amp. A 741 may be substituted with appropriate changes in pin numbers.

- C1 — 360 to 1000 pF mica trimmer, J. W. Miller 160-A or equiv.
- C2, C3 — 3 to 30 pF mica trimmer, J. W. Miller 86 MA 2 or equiv.
- C4 — 50-pF miniature air variable, Hammarlund MAPC 50 or equiv.
- D1 — Germanium diode, 1N34, 1N58, or 1N82 suitable.
- D2, D3 — Silicon diode, 1N914 or equiv.
- J1 — Coax connector, BNC or phono type suitable.
- M1 — Microammeter, 0 to 1000  $\mu$ A, Simpson Model 1212 Wide-Vue or equiv.
- Q1 — Motorola transistor.
- R1 — 10k $\Omega$  miniature control, pc mount.
- S1 — 2-pole, 4-position rotary switch, nonshorting.
- U1 — Dual operational amplifier IC, Type 2747, one half not used.
- Y1 — Crystal to produce harmonic on desired transmitter or receiver frequency. Fundamental range 6 to 20 MHz.

tor radio battery that is held by a clip inside the box.

### Testing and Use

Before calibrating the meter, the dc balance should be adjusted. A voltmeter should be connected to the output of U1, (pin 12) and R1 adjusted until the potential at this pin in one half of the supply voltage.

A low-level audio signal can be used to test the amplifier and meter circuit. As little as 10 mV, applied to pin 1, will produce a square wave at the output of the amplifier. Three ranges are provided in this meter; 0-1000 Hz, 0-10 kHz, and 0-20 kHz. Each position can be calibrated by adjustment of the associated trimmer capacitor. The amount of capacitance needed may vary with different diodes, so fixed ceramic capacitors may be placed in parallel with the trimmers to bring the adjustment within range. As the frequency of the input to U1 is varied, the meter reading should correspond to that frequency over most of its range. On the upper frequency range, 0-20 kHz, a multiplication factor must be applied to the reading on the meter.

In use, a short whip or piece of wire is connected to J1, and the meter placed near a transmitter. A crystal that will produce a harmonic on the correct

frequency is plugged into the socket. The selector switch should be in the first (0-1000 Hz) position. When the transmitter is turned on, the meter will indicate the difference in frequency between the transmitter and the harmonic from the oscillator. The trimmer, C4, should be adjusted for a minimum reading. Any hum, noise, or power-supply whine will cause a residual reading that could mask true zero beat. Modulation can be applied to the transmitter and the deviation control adjusted for the amount desired as indicated on the meter. Note that there is a difference between the indications obtained from a sine wave and those from voice. Readings will be lower with voice, the amount being dependent on the meter that is used and upon the individual voice.

Several transmitters can be netted to a system by setting the crystal in the device to the correct frequency at first, then adjust the frequency of each transmitter for an indication of zero beat.

Since there is some energy from the oscillator present at the input, J1, the same procedure can be used to align receivers to the correct frequency. When the deviation meter is acting as a signal source for checking either receivers or transmitters, the crystal should be checked for frequency drift several times during the test.

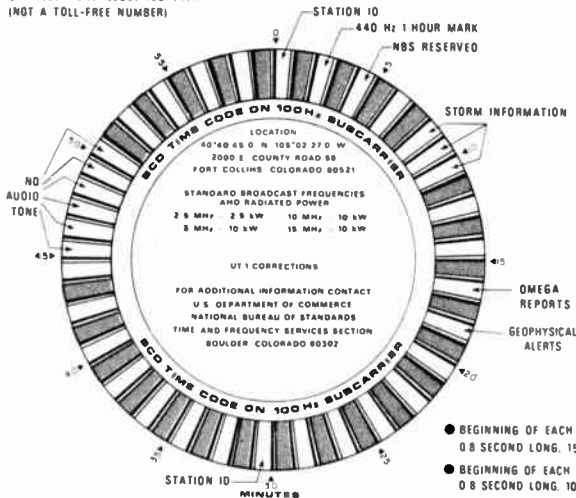


Table 3


**WWV BROADCAST FORMAT**

VIA TELEPHONE (303) 499-7111  
(NOT A TOLL-FREE NUMBER)

U.S. DEPARTMENT OF COMMERCE  
National Bureau of Standards



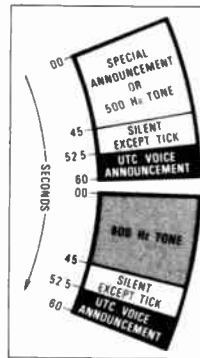- BEGINNING OF EACH HOUR IS IDENTIFIED BY 0.8 SECOND LONG, 1500 HZ TONE
- BEGINNING OF EACH MINUTE IS IDENTIFIED BY 0.8 SECOND LONG, 1000 HZ TONE
- THE 29th & 59th SECOND PULSE OF EACH MINUTE IS OMITTED



**Standard Frequencies and Time Signals**

The National Bureau of Standards maintains two radio transmitting stations, WWV at Ft. Collins, CO, and WWVH near Kekaha, Kauai, HI, for broadcasting standard radio frequencies of high accuracy. WWV and WWVH broadcast are on 2.5, 5, 10 and 15 MHz. The broadcasts of both stations are continuous, night and day. Standard audio frequencies of 440, 500 and 600 Hz on each radio-carrier frequency by WWV and WWVH. The duration of each tone is approximately 45 seconds. A 500-Hz tone is broadcast during even alternate minutes unless voice announcements or silent periods are scheduled. A 440-Hz tone is broadcast beginning one minute after the hour by WWVH and two minutes after the hour by WWV. The 440-Hz tone period is omitted during the first hour of the UTC day.

Transmitted frequencies from the two stations are accurate to  $\pm 1$  part in  $10^9$ . Atomic frequency standards are used to maintain this accuracy. Voice announcements of the time, in English, are given every minute. WWV utilizes a male voice, and WWVH features a female voice to distinguish between the two stations. WWV time and frequency broadcasts can be heard by telephone also. The number to call is 303-499-7111, Boulder, CO.


All official announcements are made by voice. Time announcements are in UTC (Universal Coordinated Time). One-second markers are transmitted throughout all programs except that the 29th and 59th markers of each minute are omitted. Detailed information on hourly broadcast schedules is given in the accompanying format chart. Complete information on the services can be found in NBS Special Publication 432, *NBS Frequency and Time Dissemination Services*, available for 60 cents from the Superintendent of Documents, U.S. Government Printing Office, Washington, DC 20402.

**Geophysical Alerts**

"Geoalerts" are broadcast in voice during the 18th minute of each hour from WWV. The messages are changed each day at 0400 UT with provisions to schedule immediate alerts of outstanding occurring events. Geoalerts tell of geophysical events affecting radio propagation, stratospheric warming, and related events.

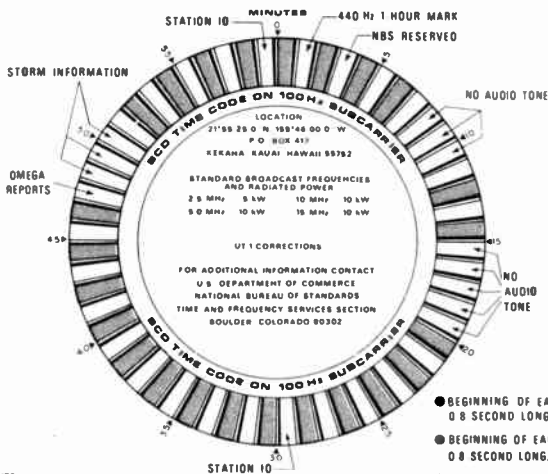**WWVH BROADCAST FORMAT**

VIA TELEPHONE (808) 335-4363 (NOT A TOLL-FREE NUMBER)



- BEGINNING OF EACH HOUR IS IDENTIFIED BY 0.8 SECOND LONG, 1500 HZ TONE
- BEGINNING OF EACH MINUTE IS IDENTIFIED BY 0.8 SECOND LONG, 1200-HZ TONE
- THE 29th & 59th SECOND PULSE OF EACH MINUTE IS OMITTED


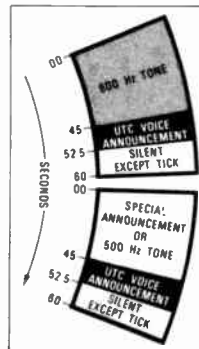


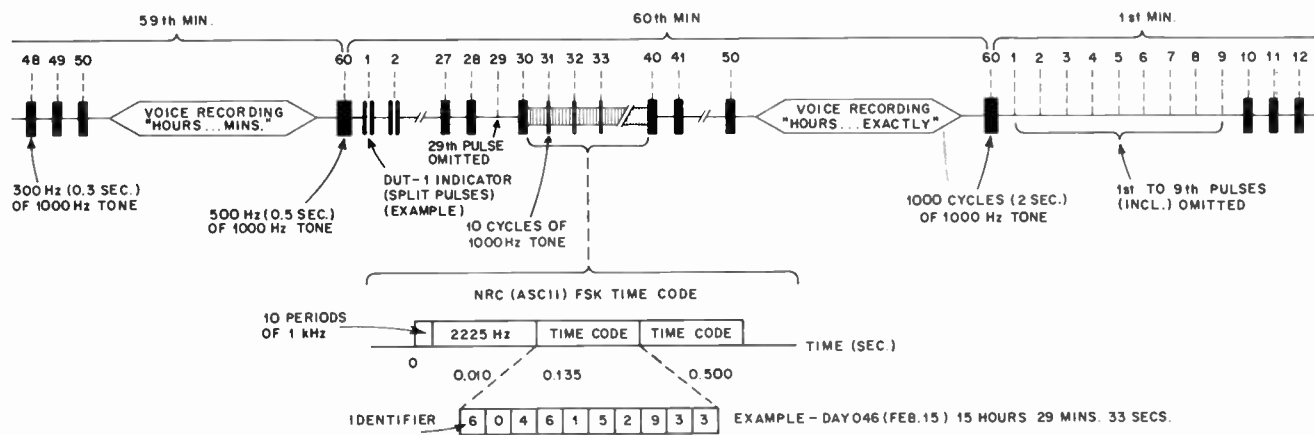

Table 4

CHU DATA TRANSMISSION SEQUENCE




**CHU**

The time service of Canada, CHU, transmits on three frequencies, 3330 kHz (power output 3 kW), 7335 kHz (power output 10 kW) and 14,670 kHz (power output 3 kW). All signals are transmitted with vertical antennas.

Transmitter frequencies and time signals are derived from a cesium frequency standard which is referred daily to the Canadian primary standard.

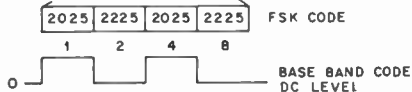Transmission mode is A3H, which is a form of single sideband. The lower sideband is attenuated but full carrier is transmitted.



# Construction Practices and Data Tables

**W**hile a better job can be done with a variety of tools, by taking a little care it is possible to turn out a fine piece of equipment with only a few common hand tools. A list of tools which are indispensable in the construction of radio equipment is found on this page. To convert English dimensions in the list to millimeters, multiply inches  $\times$  25.4. With these tools it should be possible to prepare panels and metal chassis for assembly and wiring. It is an excellent idea for the amateur who builds gear to add to his supply of tools from time to time as finances permit.

### Recommended Tools and Materials

- Long-nose pliers, 6- and 4-inch
- Diagonal cutters, 6- and 4-inch
- Combination pliers, 6-inch
- Screwdriver, 6- to 7-inch, 1/4-inch blade
- Screwdriver, 4- to 5-inch, 1/8-inch blade
- Phillips screwdriver, 6- to 7-inch
- Phillips screwdriver, 3- to 4-inch
- Long-shank screwdriver with holding clip on blade
- Scratch awl or scribe for marking metal
- Combination square, 12-inch, for layout work
- Hand drill, 1/4-inch chuck or larger
- Soldering pencil, 30-watt, 1/8-inch tip
- Soldering iron, 200-watt, 5/8-inch tip
- Hacksaw and 12-inch blades
- Hand nibbling tool, for chassis-hole cutting
- Hammer, ball-peen 1-lb. head
- Heavy-duty jackknife
- File set, flat, round, half-round, and triangular. Large and miniature types recommended
- High-speed drill bits, no. 60 through 3/8-inch diameter
- Set of "Spintite" socket wrenches for hex nuts
- Adjustable wrenches, 6- and 10-inch
- Machine-screw taps, 4-40 through 10-32 thread
- Socket punches, 1/2", 5/8", 3/4", 1-1/8", 1-1/4", and 1-1/2"
- Tapered reamer, T-handle, 1/2-inch maximum width
- Bench vise, 4-inch jaws or larger

- Medium-weight machine oil
- Tin shears, 10-inch size
- Motor-driven emery wheel for grinding Solder, *rosin core only*
- Contact cleaner, liquid or spray can
- Duco cement or equivalent
- Electrical tape, vinyl plastic

Radio-supply houses, mail-order retail stores and most hardware stores carry the various tools required for building or servicing amateur radio equipment. While power tools (electric drill or drill press, grinding wheel, etc.) are very useful and will save a lot of time, they are not essential.

### Twist Drills

Twist drills are made of either high-speed steel or carbon steel. The latter type is more common and will usually be supplied unless specific request is made for high-speed drills. The carbon drill will suffice for most ordinary equipment construction work and costs less than the high-speed type.

While twist drills are available in a number of sizes, those listed in *italic type* in Table I will be most commonly used in construction of amateur equipment. It is usually desirable to purchase several of each of the commonly used sizes rather than a standard set, most of which will be used infrequently, if at all.

### Care of Tools

The proper care of tools is not only a matter of pride to a good worker. He also recognizes the energy saved and the annoyance avoided by possessing a full kit of well-kept, sharp-edged tools.

Drills should be sharpened at frequent intervals so that grinding is kept at a minimum each time. This makes it easier to maintain the rather critical surface angles required for best cutting with least wear. Occasional oilstoning of the cutting edges of a drill or reamer will extend the time between grindings.

The soldering iron can be kept in good condition by keeping the tip well tinned with solder and not allowing it to run at

**Table 1**  
**Numbered Drill Sizes**

No.	Diameter (Mils)	Will Clear Screw	Drilled for Tapping from Steel or Brass*
1	228.0	-	-
2	221.0	12-24	-
3	213.0	-	14-24
4	209.0	12-20	-
5	205.0	-	-
6	204.0	-	-
7	201.0	-	-
8	199.0	-	-
9	196.0	-	-
10	193.5	10-32	-
11	191.0	10-24	-
12	189.0	-	-
13	185.0	-	-
14	182.0	-	-
15	180.0	-	-
16	177.0	-	12-24
17	173.0	-	-
18	169.5	8-32	-
19	166.0	-	12-20
20	161.0	-	-
21	159.0	-	10-32
22	157.0	-	-
23	154.0	-	-
24	152.0	-	-
25	149.5	-	10-24
26	147.0	-	-
27	144.0	-	-
28	140.0	6-32	-
29	136.0	-	8-32
30	128.5	-	-
31	120.0	-	-
32	116.0	-	-
33	113.0	4-40	-
34	111.0	-	-
35	110.0	-	6-32
36	106.5	-	-
37	104.0	-	-
38	101.5	-	-
39	99.5	3-48	-
40	98.0	-	-
41	96.0	-	-
42	93.5	-	4-40
43	89.0	2-56	-
44	86.0	-	-
45	82.0	-	3-48
46	81.0	-	-
47	78.5	-	-
48	76.0	-	-
49	73.0	-	2.56
50	70.0	-	-
51	67.0	-	-
52	63.5	-	-
53	59.5	-	-
54	55.0	-	-

\*M.T.

full voltage for long periods when it is not being used. After each period of use, the tip should be removed and cleaned of any scale which may have accumulated. An oxidized tip may be cleaned by dipping it in sal ammoniac while hot and then wiping it clean with a rag. If the tip becomes pitted it should be filed until smooth and bright, and then tinned immediately by dipping it in solder.

### Useful Materials

Small stocks of various miscellaneous materials will be required in constructing radio apparatus. Most of these are available from hardware or radio-supply stores. A representative list follows:

Sheet aluminum, solid and perforated, 16 or 18 gauge, for brackets and shielding.

1/2 × 1/2-inch (12 × 13-mm) aluminum angle stock.

1/4-inch (6-mm) diameter round brass or aluminum rod for shaft extensions.

Machine screws: Round-head and flat-head, with nuts to fit. Most useful sizes: 4-40, 6-32 and 8-32, in lengths from 1/4-inch (6 mm) to 1-1/2 inches (38 mm). (Nickel-plated iron will be found satisfactory except in strong rf fields, where brass should be used.)

Bakelite, Lucite and polystyrene scraps.

Soldering lugs, panel bearings, rubber grommets, terminal-lug wiring strips, varnished-cambric insulating tubing.

Shielded and unshielded wire.

Tinned bare wire, nos. 22, 14 and 12.

Machine screws, nuts, washers, soldering lugs, etc., are most reasonably purchased in quantities of a gross. Many of the radio-supply stores sell small quantities and assortments that come in handy.

### Triac Motor-Speed Control

Most electric hand drills operate at a single high speed; however, from time to time, the need arises to utilize low or medium speeds. Low speeds are useful when drilling in tight spaces or on exposed surfaces where it is important that the drill bit doesn't slip, and when drilling bakelite, Plexiglas and similar materials. Medium speeds are useful for drilling non-ferrous metals such as aluminum and brass. One way to accomplish these ends with a single-speed electric drill is to use a silicon bidirectional thyristor (Triac) speed control.

The circuit for the Triac speed control is shown in Fig. 3. This type of circuit provides some degree of regulation with varying loads.

### Construction

Because of the small complement of parts, the Triac speed control can be constructed inside a very small container. The model described was built in a 2-3/4 × 2-1/8 × 1-5/8-inch (70 × 54 × 41-mm) Minibox. Since the mounting stud and main body of the Triac are common with the anode, care should be used to mount



Fig. 1 — The SCR motor-speed control is housed in a small cabinet.

the Triac clear from surrounding objects. In the unit shown, two soldering lugs were soldered together and the narrow ends connected to one side of the female output connector; the large ends were used as a fastening point for the Triac anode stud.

### Operation

Although the circuit described is intended to be used to reduce the speed of electric hand drills that draw 6 amperes or less, it has many other applications. It can be used to regulate the temperature of a soldering iron, which is being used to wire a delicate circuit, or it may be used for dimming lamps or for controlling the cooking speed of a small hot plate. Note, however, if the circuit is used with a device drawing from 3 to 6 amperes for a continuous period of over 10 minutes, it will be necessary to provide a heat sink (insulated from the chassis) for the Triac anode case.

### Chassis Working

With a few essential tools and proper procedure, building radio gear on a metal

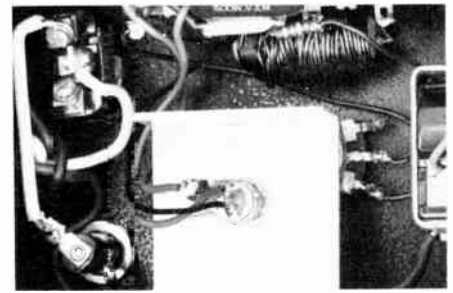


Fig. 2 — The working parts of the motor-speed control. The triac is centered on its aluminum heat-sink, with the terminals of the speed-control resistor protruding from underneath. The rf-hash-suppression filter and components in the gate-triggering circuit are mounted on a tie-point strip, visible at the bottom of the enclosure. The triac is barely discernible at the right end of the fixed resistor. Terminals of the strip which are associated with the mounting feet are unused and are bent down to prevent accidental shorts to other parts of the circuit.

chassis is a relatively simple matter. Aluminum is preferred to steel, not only because it is a superior shielding material, but because it is much easier to work and provides good chassis contacts.

The placement of components on the chassis is shown quite clearly in the photographs in this *Handbook*. Aside from certain essential dimensions, which usually are given in the text, exact duplication is not necessary.

Much trouble and energy can be saved by spending sufficient time in planning the job. When all details are worked out beforehand the actual construction is greatly simplified.

Cover the top of the chassis with a piece of wrapping paper, or, preferably, cross-section paper, folding the edges down over the sides of the chassis and fastening with adhesive tape. Then assemble the parts to be mounted on top of the chassis and move them about until a satisfactory arrangement has been found, keeping in mind any parts which are to be mounted underneath, so interferences in mounting

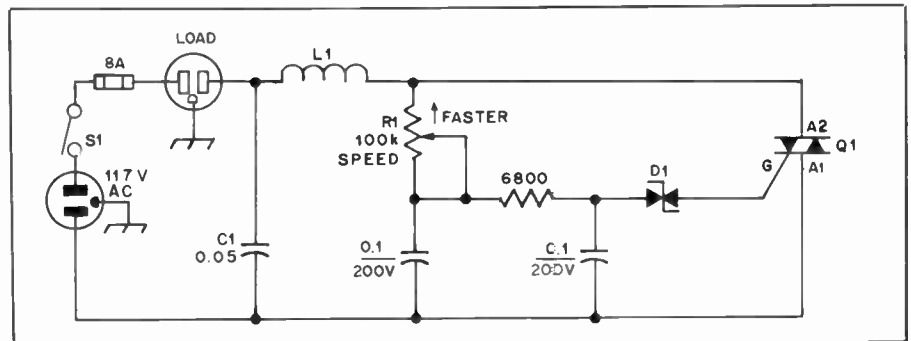


Fig. 3 — Schematic diagram of motor-speed control. Resistances are in ohms (k = 1000) and capacitances are in microfarads. Important note: The basing diagram for Q1 is correct as shown here.

- C1 — 0.05- $\mu$ F, 600-V paper.
- D1 — Diac (silicon bilateral trigger), 2-A, 300-mW (Motorola MPT28 or HEP311 or equiv.).
- L1 — Approx. 70  $\mu$ H; made with 18 ft. (5.49 m) no. 18 enam. wire scramble-wound on body of C1, or on a 1-1/2-inch (38-mm) length of 1/2-inch (13-mm) dia. rod.
- Q1 — Tnac (silicon bidirectional thyristor), 8-A, 200-V (Motorola MAC2-4 or HEP340 or equiv.).
- R1 — Linear-taper composition control, 2-W.
- S\* — Spst toggle.

can be avoided. Place capacitors and other parts with shafts extending through the panel first, and arrange them so that the controls will form the desired pattern of the panel. Be sure to line up the shafts squarely with the chassis front. Locate any partition shields and panel brackets next, and then the tube sockets and any other parts, marking the mounting-hole centers of each accurately on the paper. Watch out for capacitors whose shafts are off center and do not line up with the mounting holes. Do not forget to mark the centers of socket holes and holes for leads under i-f transformers and other such components, as well as holes for wiring leads. The small holes for socket-mounting screws are best located and center-punched, using the socket itself as a template, after the main center hole has been cut.

By means of the square, lines indicating accurately the centers of shafts should be extended to the chassis front and marked on the panel at the chassis line, the panel being fastened on temporarily. The hole centers may then be punched in the chassis with the center punch. After drilling, the parts which require mounting underneath may be located and the

mounting holes drilled, making sure by trial that no interferences exist with parts mounted on top. Mounting holes along the front edge of the chassis should be transferred to the panel by once again fastening the panel to the chassis and marking it from the rear.

Next, mount on the chassis the capacitors and any other parts with shafts extending to the panel, and measure accurately the height of the center of each shaft above the chassis, as illustrated in Fig. 4. The horizontal displacement of shafts having already been marked on the chassis line on the panel, the vertical displacement can be measured from this line. The shaft centers may now be marked on the back of the panel, and the holes drilled. Holes for any other panel equipment coming above the chassis line may then be marked and drilled, and the remainder of the apparatus mounted. Holes for terminals and other parts in the rear edge of the chassis should be marked and drilled at the same time that they are done for the top.

#### Drilling and Cutting Holes

When drilling holes in metal with a hand drill it is important that the centers first be located with a center punch, so

that the drill point will not "walk" away from the center when starting the hole. When the drill starts to break through, special care must be used. Often it is an advantage to shift a two-speed drill to low gear at this point. Holes more than 1/4-inch (6-mm) in diameter should be started with a smaller drill and reamed out with the larger drill.

The check on the usual type of hand drill is limited to 1/4-inch (6-mm) drills. The 1/4-inch (6-mm) hole may be filed out to larger diameters with round files. Another method possible with limited tools is to drill a series of small holes with the hand drill along the inside of the circumference of the large hole, placing the holes as close together as possible. The center may then be knocked out with a cold chisel and the edges smoothed with a file. Taper reamers which fit into the carpenter's brace will make the job easier. A large rat-tail file clamped in the brace makes a very good reamer for holes up to the diameter of the file.

For socket holes and other large holes in an aluminum chassis, socket-hole punches should be used. They require first drilling a guide hole to pass the bolt that is turned to squeeze the punch through the

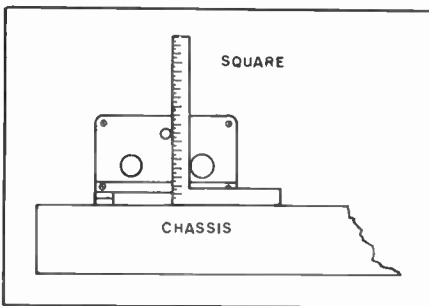


Fig. 4 — Method of measuring the heights of capacitor shafts. If the square is adjustable, the end of the scale should be set flush with the face of the head.

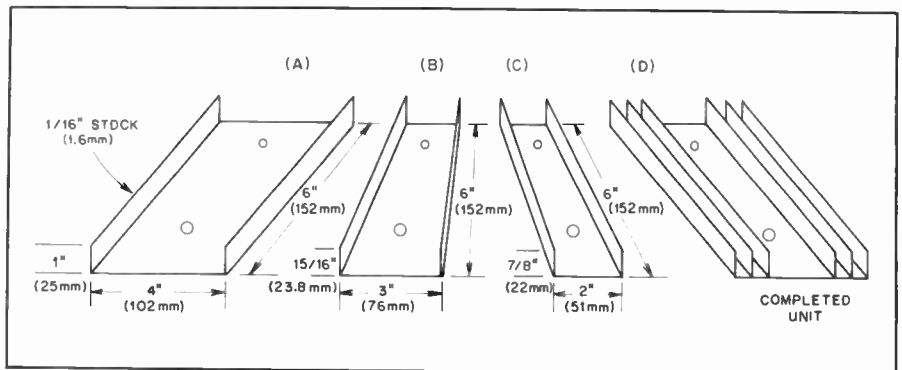


Fig. 6 — Details for forming channel-type heat sinks.

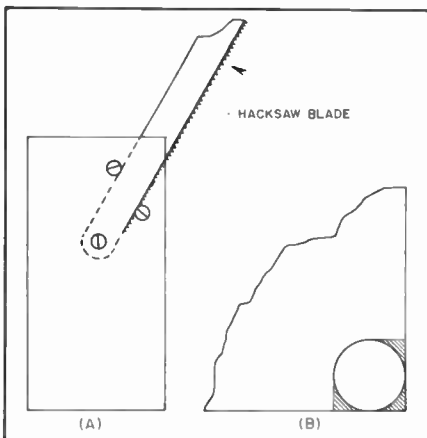


Fig. 5 — To cut rectangular holes in a chassis corner, holes may be filed out as shown in the shaded portion of B, making it possible to start the hacksaw blade along the cutting line. A shows how a single-ended handle may be constructed for a hacksaw blade.

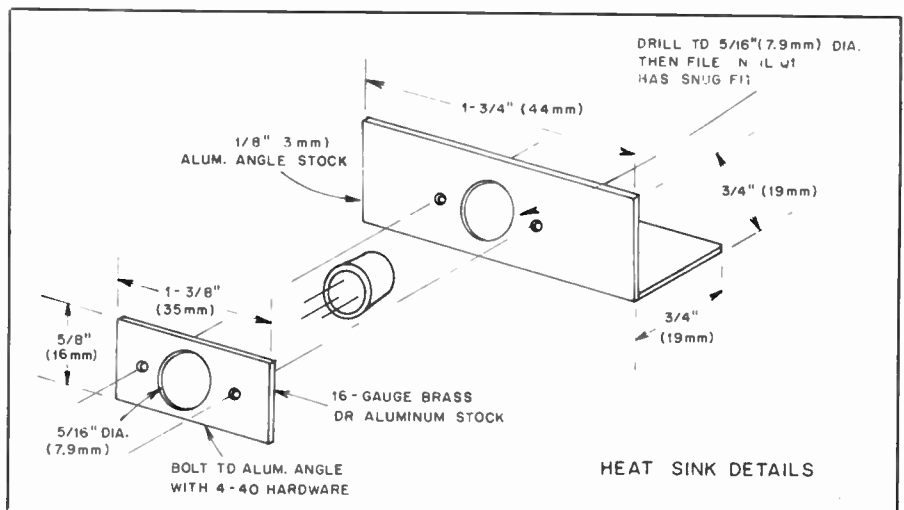


Fig. 7 — Layout and assembly details of another homemade heat sink. The completed assembly can be insulated from the main chassis of the transmitter by using insulating washers.



chassis. The threads of the bolt should be oiled occasionally.

Large holes in steel panels or chassis are best cut with an adjustable circle cutter. Occasional application of machine oil in the cutting groove will help. The cutter first should be tried out on a block of wood, to make sure that it is set for the right diameter.

The burrs or rough edges which usually result after drilling or cutting holes may be removed with a file, or sometimes more conveniently with a sharp knife or chisel. It is a good idea to keep an old wood chisel sharpened and available for this purpose.

### Rectangular Holes

Square or rectangular holes may be cut out by making a row of small holes as previously described, but is more easily done by drilling a 1/2-inch (13-mm) hole inside each corner, as illustrated in Fig. 5, and using these holes for starting and turning the hacksaw. The socket-hole punch and the square punches which are now available also may be of considerable assistance in cutting out large rectangular openings.

### Semiconductor Heat Sinks

Homemade heat sinks can be fashioned from brass, copper or aluminum stock by employing ordinary workshop tools. The dimensions of the heat sink will depend upon the type of transistor used and the amount of heat that must be conducted away from the body of the semiconductor.

Fig. 6 shows the order of progression for forming a large heat sink from aluminum or brass channels of near-equal height and depth. The width is lessened in parts B and C so that each channel will fit into the preceding one as shown in the completed model at D. The three pieces are bolted together with 8-32 screws and nuts. Dimensions given are for illustrative purposes only.

Heat sinks for smaller transistors can be fabricated as shown in Fig. 8. Select a drill bit that is one size smaller than the diameter of the transistor case and form the heat sink from 1/16-inch (1.6-mm) thick brass, copper or aluminum stock as shown in steps A, B and C. Form the stock around the drill bit by compressing it in a vise (A). The completed heat sink is press-fitted over the body of the semiconductor as illustrated at D. The larger the heat sink area, the greater will be the amount of heat conducted away from the transistor body. In some applications, the heat sinks shown in Fig. 8 may be two or three inches in height (power transistor stages).

Another technique for making heat sinks for TO-5 type transistors and larger models is shown in Fig. 7. This style of heat sink will dissipate considerably more heat than will the type shown in Fig. 6. The main body of the sink is fashioned

**Table 2**  
**Standard Metal Gauges**

Gauge No.	American or BS <sup>1</sup>	U.S. Standard <sup>2</sup>	Birmingham or Stubs <sup>3</sup>	Gauge No.	American or BS <sup>1</sup>	U.S. Standard <sup>2</sup>	Birmingham or Stubs <sup>3</sup>
1	0.2893	0.28125	0.300	24	0.02010	0.025	0.022
2	0.2576	0.265625	0.284	25	0.01790	0.021875	0.020
3	0.2294	0.25	0.259	26	0.01594	0.01875	0.018
4	0.2043	0.234375	0.238	27	0.01420	0.0171875	0.016
5	0.1819	0.21875	0.220	28	0.01264	0.015625	0.014
6	0.1620	0.203125	0.203	29	0.01126	0.0140625	0.013
7	0.1443	0.1875	0.180	30	0.01003	0.0125	0.012
8	0.1285	0.171875	0.165	31	0.008928	0.0109375	0.010
9	0.1144	0.15625	0.148	32	0.007950	0.01015625	0.009
10	0.1019	0.140625	0.134	33	0.007080	0.009375	0.008
11	0.09074	0.125	0.120	34	0.006350	0.00859375	0.007
12	0.08081	0.109375	0.109	35	0.005615	0.0078125	0.005
13	0.07196	0.09375	0.095	36	0.005000	0.00703125	0.004
14	0.06408	0.078125	0.083	37	0.004453	0.006640625	-
15	0.05707	0.0703125	0.072	38	0.003965	0.00625	-
16	0.05082	0.0625	0.065	39	0.003531	-	-
17	0.04526	0.05625	0.058	40	0.003145	-	-
18	0.04030	0.05	0.049				
19	0.03589	0.04375	0.042				
20	0.03196	0.0375	0.035				
21	0.02846	0.034375	0.032				
22	0.02535	0.03125	0.028				
23	0.02257	0.028125	0.025				

<sup>1</sup>Used for aluminum, copper, brass and nonferrous alloy sheets, wire and rods.

<sup>2</sup>Used for iron, steel, nickel and ferrous alloy sheets, wire and rods.

<sup>3</sup>Used for seamless tubes; also by some manufacturers for copper and brass.

from a piece of 1/8-inch (3-mm) thick aluminum angle bracket — available from most hardware stores. A hole is bored in the angle stock to allow the transistor case to fit snugly into it. The transistor is held in place by a small metal plate whose center hole is slightly smaller in diameter than the case of the transistor. Details are given in Fig. 7.

A thin coating of silicone grease, available from most electronics supply houses, can be applied between the case of the transistor and the part of the heat sink with which it comes in contact. The silicone grease will aid the transfer of heat from the transistor to the sink. This practice can be applied to all models

shown here. In the example given in Fig. 6, the grease should be applied between the three channels before they are bolted together, as well as between the transistor and the channel it contacts.

### Construction Notes

If a control shaft must be extended or insulated, a flexible shaft coupling with adequate insulation should be used. Satisfactory support for the shaft extension, as well as electrical contact for safety, can be provided by means of a metal panel bearing made for the purpose. These can be obtained singly for use with existing shafts, or they can be bought with a captive extension shaft included. In either

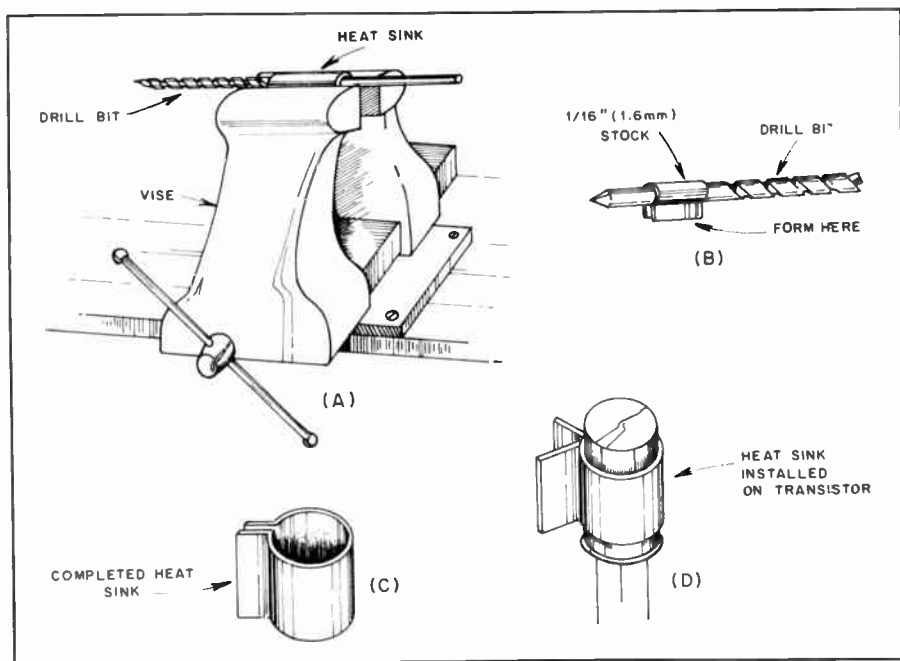


Fig. 8 — Steps used in constructing heat sinks for small transistors.

case the panel bearing gives a "solid" feel to the control.

The use of fiber washers between ceramic insulation and metal brackets, screws or nuts will prevent the ceramic parts from breaking.

### Cutting and Bending Sheet Metal

If a metal sheet is too large to be cut conveniently with a hacksaw, it may be marked with scratches as deep as possible along the line of the cut on both sides of the sheet, and then clamped in a vise and worked back and forth until the sheet breaks at the line. Do not carry the bending too far until the break begins to weaken; otherwise the edge of the sheet may become bent. A pair of iron bars or pieces of heavy angle stock, as long or longer than the width of the sheet, to hold it in the vise, will make the job easier. C clamps may be used to keep the bars from spreading at the ends. The rough edges may be smoothed with a file or by placing a large piece of emery cloth or sandpaper on a flat surface and running the edge of the metal back and forth over the sheet. Bends may be made similarly.

### Finishing Aluminum

Aluminum chassis, panels and parts may be given a sheen finish by treating them in a caustic bath. An enameled or

plastic container, such as a dishpan or infant's bathtub, should be used for the solution. Dissolve ordinary household lye in cold water in a proportion of one-quarter to one-half can of lye per gallon of water. The stronger solution will do the job more rapidly. Stir the solution with a stick of wood until the lye crystals are completely dissolved. Be very careful to avoid any skin contact with the solution. It is also harmful to clothing. Sufficient solution should be prepared to cover the piece completely. When the aluminum is immersed, a very pronounced bubbling takes place and ventilation should be provided to disperse the escaping gas. A half hour to two hours in the solution should be sufficient, depending upon the strength of the solution and the desired surface.

Remove the aluminum from the solution with sticks and rinse thoroughly in cold water while swabbing with a rag to remove the black deposit. When dry, finish by spraying on a light coat of clear lacquer.

Raw aluminum can be prepared for painting by abrading the surface with medium-grade sandpaper, making certain the strokes are applied in the same direction (not circular or random). This process will create tiny grooves on the otherwise smooth surface. As a result,


paint or lacquer will adhere well. Before painting, wash the abraded aluminum with soap and hot water, dry thoroughly: Avoid touching the prepared surface before painting it.

### Soldering


The secret of good soldering is to use the right amount of heat. Too little heat will produce a "cold-soldered joint"; too much may injure a component. The iron and the solder should be applied simultaneously to the joint. Keep the iron clean by brushing the hot tip with a paper towel. Always use rosin-core solder; never acid-core. Solders have different melting points, depending upon the ratio of tin to lead. A 50-50 solder melts at 425°F (218°C), while 60-40 melts at 371°F (188°C). When it is desirable to protect from excessive heat the components being soldered, the 60-40 solder is preferable to the 50-50. (A less-common solder, 63-37, melts at 361°F or 182°C.)

When soldering transistors, crystal diodes or small resistors, the lead should be gripped with a pair of pliers up close to the unit so that the heat will be conducted away. Overheating of a transistor or diode while soldering can cause permanent damage. Also, mechanical stress will have a similar effect. Therefore, a small unit should be mounted so that there is no

#### 83-58FCP

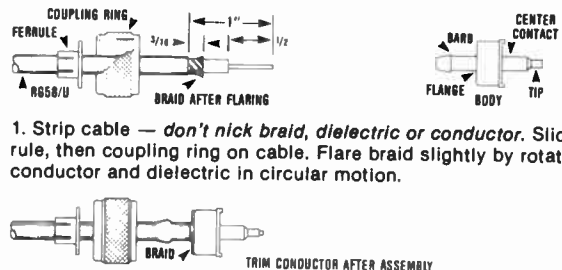


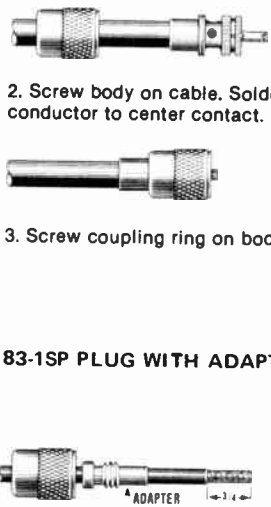1. Strip cable — *don't nick braid, dielectric or conductor*. Slide ferrule, then coupling ring on cable. Flare braid slightly by rotating conductor and dielectric in circular motion.
2. Slide body on dielectric, barb going under braid until flange is against outer jacket. Braid will fan out against body flange.




2. Screw body on cable. Solder braid through solder holes. Solder conductor to center contact.
3. Screw coupling ring on body.

#### 83-1SP PLUG (PL-259)

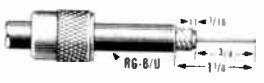

1. Strip cable, *don't nick braid, dielectric or conductor*. Tin exposed braid and conductor. Slide coupling ring on cable.

#### 83-1SP PLUG WITH ADAPTERS



1. Strip jacket. *Don't nick braid*. Slide coupling ring and adapter on cable. Note — use 83-168 adapter for RG-58/U and 83-185 for RG-59/U.
2. Fan braid slightly, fold back over adapter and trim to 3/8". Strip dielectric and tin exposed conductor. *Don't nick conductor*.
3. Screw body on adapter. Follow 2 and 3 under 83-1SP plug.

Fig. 10 — Cable stripping dimensions and assembly instructions for several popular coaxial cable connectors. This material courtesy of Amphenol® Electronic Components, RF Division, Bunker Ramo Corp. (Dimensions on this drawing are in English inches. Multiply inches  $\times 25.4$  to obtain mm).

appreciable mechanical strain on the leads.

Trouble is sometimes experienced in soldering to the pins of coil forms or male cable plugs. It helps if the pins are first cleaned on the inside with a suitable twist drill and then tinned by flowing rosin-core solder into them. Immediately clear the surplus solder from each hot pin by a whipping motion or by blowing through the pin from the inside of the form or plug. Before inserting the wire in the pin, file the nickel plate from the tip. After soldering, round the solder tip off with a file.

When soldering to the pins of polystyrene coil forms, hold the pin to be soldered with a pair of heavy pliers to form a "heat sink" and insure that the pin does not heat enough in the coil form to loosen and become misaligned.

### Wiring

The wire used in connecting amateur equipment should be selected by considering both the maximum current it will be called upon to handle and the voltage its insulation must stand without breakdown. Also, from the consideration to TVI, the power wiring of all transmitters should be done with wire that has a braided shielding cover. Receiver and

audio circuits may also require the use of shielded wire at some points for stability or the elimination of hum.

No. 20 stranded wire is commonly used for most receiver wiring (except for the high-frequency circuits) where the current does not exceed 2 or 3 amperes. For higher-current heater circuits, no. 18 is available. Wire with cellulose acetate insulation is good for voltages up to about 500. For higher voltages, Teflon-insulated or other special HV wire should be used. Inexpensive wire strippers that make the removal of insulation from hookup wire an easy job are available on the market.

When power leads have several branches in the chassis, it is convenient to use fiber-insulated multiple tie points as anchorages or junction points. Strips of this type are also useful as insulated supports for resistors, rf chokes and capacitors. Exposed points of high-voltage wiring should be held to a minimum; those which cannot be avoided should be made as inaccessible as possible to accidental contact or short-circuit.

Where shielded wire is called for and capacitance to ground is not a factor, Belden type 8885 shielded grid wire may be used. If capacitance must be minimized, it may be necessary to use a piece of car-radio low-capacitance lead-in wire or coaxial cable.


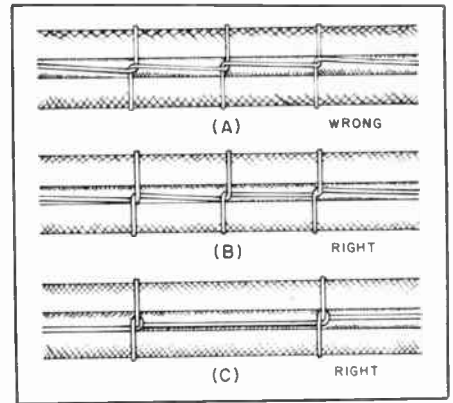


Fig. 9 — Methods of lacing cables. The method shown at C is more secure, but takes more time than the method of B. The latter is usually adequate for most amateur requirements.

For wiring high-frequency circuits, rigid wire is often used. Bare soft-drawn tinned wire, size 22 (depending on mechanical requirements) is suitable. Kinks can be removed by stretching a piece of 10 or 15 feet (3 or 4.5 m) long and then cutting it into short lengths that can be handled conveniently. Rf wiring should be run directly from point to point with a minimum of sharp bends and the wire kept well spaced from the chassis or other grounded metal surfaces. Where the

### BNC CONNECTORS (STANDARD CLAMP)

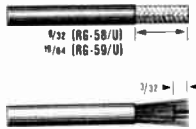

1. Strip jacket. Fray braid and strip dielectric. *Don't nick braid or conductor.* Tin conductor.




2. Taper braid. Slide nut, washer, gasket and clamp over braid. Clamp inner shoulder should fit squarely against end of jacket.



3. With clamp in place, comb out braid, fold back smooth as shown. Trim 3/32" from end.





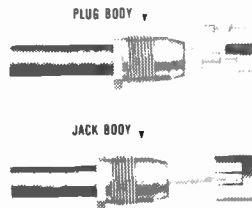4. Solder contact on conductor through solder hole. Contact should butt against dielectric. Remove excess solder from outside of contact. Avoid excess heat to prevent swollen dielectric which would interfere with connector body.



5. Push assembly into body. Screw nut into body with wrench until tight. *Don't rotate body on cable to tighten.*

### BNC CONNECTORS (IMPROVED CLAMP)

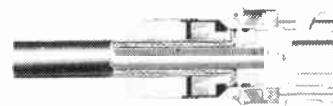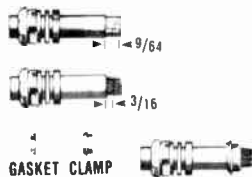

1. Follow 1, 2, 3 and 4 in BNC connectors (standard clamp) except as noted. Strip cable as shown. Slide gasket on cable *with groove facing clamp*. Slide clamp on cable *with sharp edge facing gasket*. Clamp should cut gasket to seal properly.



wiring must pass through the chassis or a partition, a clearance hole should be cut and lined with a rubber grommet. In case insulation becomes necessary, varnished cambric tubing (spaghetti) can be slipped over the wire.

In transmitters where the peak voltage does not exceed 2500, the shielded grid wire mentioned above should be satisfactory for power circuits. For higher voltages, Belden type 8656, Birnbach type 1820, or shielded ignition cable can be used. In the case of filament circuits carrying heavy current, it may be necessary to use no. 10 or 12 bare or enameled wire, slipped through spaghetti, and then covered with copper braid pulled tightly over the spaghetti. The chapter on TVI shows the manner in which shielded wire should be applied. If the shielding is simply slid back over the insulation and solder flowed into the end of the braid, the braid usually will stay in place without the necessity for cutting it back or binding it in place. The braid should be cleaned first so that solder will take with a minimum of heat.

Rf wiring in transmitters usually follows the method described above for receivers, with due respect to the voltages involved.

Where power or control leads run together for more than a few inches, they will present a better appearance when bound together in a single cable. The correct technique is illustrated in Fig. 9; both plastic and waxed-linen lacing cords are available. Plastic cable clamps are available to hold the laced cable.

To give a "commercial look" to the wiring of any unit, run any cabled leads along the edge of the chassis. If this isn't possible, the cabled leads should then run parallel to an edge of the chassis. Further, the generous use of tie points mounted parallel to an edge of the chassis, for the support of one or both ends of a resistor or fixed capacitor, will add to the appearance of the finished unit. In a similar manner, "dress" the small components so that they are parallel to the panel or sides of the chassis.

### *Winding Coils*

Close-wound coils are readily wound on the specified form by anchoring one end of a length of wire (in a vise or to a doorknob) and the other end to the coil form. Straighten any kinks in the wire and then pull to keep the wire under slight tension. Wind the coil to the required number of turns while walking toward the anchor, always maintaining a slight tension on the wire.

To space-wind the coil, wind the coil simultaneously with a suitable spacing medium (heavy thread, string or wire) in the manner described above. When the winding is complete, secure the end of the coil to the coil-form terminal and then carefully unwind the spacing material. If

the coil is wound under suitable tension, the spacing material can be easily removed without disturbing the winding. Finish the space-wound coil by judicious applications of Duco cement to hold the turns in place.

The "cold" end of a coil is the end at or close to chassis or ground potential. Coupling links should be wound on the cold end of a coil to minimize capacitive coupling.

### *Circuit-Board Fabrication*

Modern-day builders prefer the neatness and miniaturization made possible by the use of etched or printed circuit boards. There are additional benefits to be realized from the use of circuit boards: Low lead inductances, excellent physical stability of the components and interconnecting leads, and good repeatability of the basic layout of a given project. The latter attribute makes the use of circuit boards ideal for group projects.

### *Methods*

Perhaps the least complicated approach to circuit-board fabrication is the use of unclad perforated board into which a number of push-in terminals have been installed. The perforated board can be obtained with one of many hole patterns, dependent upon the needs of the builder. Perforated terminal boards are manufactured by several companies. Their products are available from most mail-order houses.

Once the builder plots the layout of his circuit on paper, push-in terminals can be installed in the "perf" board to match the layout which was done on paper. The terminals serve as tie points and provide secure mounting-post anchors for the various components. Selected terminals can be wired together to provide ground and B+ lines. Although this technique is the most basic of the methods, it is entirely practical.

### *Planning and Layout*

The constructor should first plan the physical layout of the circuit by sketching a pictorial diagram on paper, drawing it to scale. Once this has been done, the interconnecting leads can be inked in to represent the copper strips that will remain on the etched board. The Vector Company sells layout paper for this purpose. It is marked with the same patterns that are used on their perforated boards.

After the basic etched-circuit design has been completed the designer should go over the proposed layout several times to insure against errors. When the foregoing has been done, the pattern can be painted on the copper surface of the board to be etched. Etch-resistant solutions are available from commercial suppliers and can be selected from their catalogs. Some builders prefer to use India ink for this

purpose. Perhaps the most readily available material for use in etch-resist applications is ordinary exterior enamel paint. The portions of the board to be retained are covered with a layer of paint, applied with an artist's brush, duplicating the pattern that was drawn on the layout paper. The job can be made a bit easier by tracing over the original layout with a ballpoint pen and carbon paper while the pattern is taped to the copper side of the unetched circuit board. The carbon paper is placed between the pattern and the circuit board. After the paint has been applied, it should be allowed to dry for at least 24 hours prior to the etching process. The Vector Company produces a rub-on transfer material that can also be used as etch-resist when laying out circuit-board patterns. Thin strips of ordinary masking tape, cut to size and firmly applied, serve nicely as etch-resist material too.

When making "one-shot" pc boards it is convenient to cover the copper surface with masking tape, transfer the circuit pattern by means of carbon paper, then cut out and remove the sections of masking tape where the copper is to be etched away. An X-acto hobby knife is excellent for the purpose. Masking tape, securely applied, serves as a fine etch-resist material.

### *The Etching Process*

Almost any strong acid bath will serve as an etchant, but the two chemical preparations recommended here are the safest to use. A bath can be prepared by mixing one part ammonium persulphate crystals with two parts clear water. A normal quantity of working solution for most amateur radio applications is composed of one cup of crystals and two cups of water. To this mixture add 1/4 teaspoon of mercuric chloride crystals. The latter serves as an activator for the bath. Ready-made etchant kits which use these chemicals are available from Vector. Complete kits which contain circuit boards, etchant powders, etch-resist transfers, layout paper, and plastic etchant bags are also available from Vector at moderate prices.

Another chemical bath that works satisfactorily for copper etching is made up from one part ferric chloride crystals and two parts water. No activator is required with this bath. Ready-made solutions (one-pint and one-gallon sizes) are available through some mail-order houses at low cost. They are manufactured by Kepro Company and carry stock numbers E-IPT and E-IG, respectively.

Etchant solutions become exhausted after a certain amount of copper has been processed. Therefore, it is wise to keep a quantity of the bath on hand if frequent use is anticipated. With either chemical bath, the working solution should be maintained at a temperature between 90



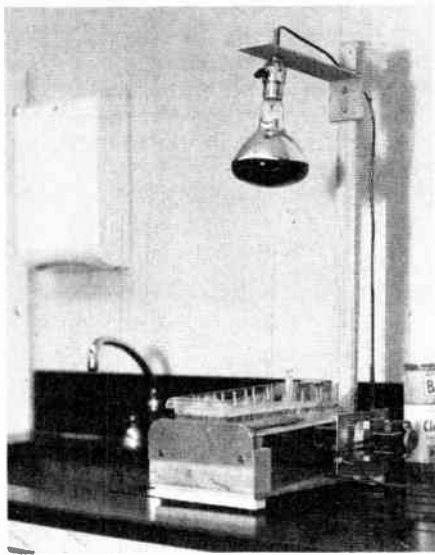


Fig. 11 — A homemade stand for processing etched-circuit boards. The heat lamp maintains the etchant-bath temperature between 90 and 115°F (32 and 46°C) and is mounted on an adjustable arm. The tray for the bath is raised and lowered at one end by the action of a motor-driven eccentric disk, providing the necessary agitation of the chemical solution. A dark-room thermometer monitors the temperature of the bath.

and 115°F (32 and 46°C). A heat lamp can be directed toward the bath during the etching period, its distance set to maintain the required temperature. A darkroom thermometer is handy for monitoring the temperature of the bath.

While the circuit board is immersed in the solution, it should be agitated continuously to permit uniform reaction to the chemicals. This action will also speed up the etching process somewhat. Normally, the circuit board should be placed in the bath with the copper side facing down, toward the bottom of the tray. The tray should be non-metallic preferably a Pyrex dish or a photographic darkroom tray.

The photograph, Fig. 11, shows a homemade etching stand made up from a heat lamp, some lumber, and an 8-rpm motor. An eccentric disk has been

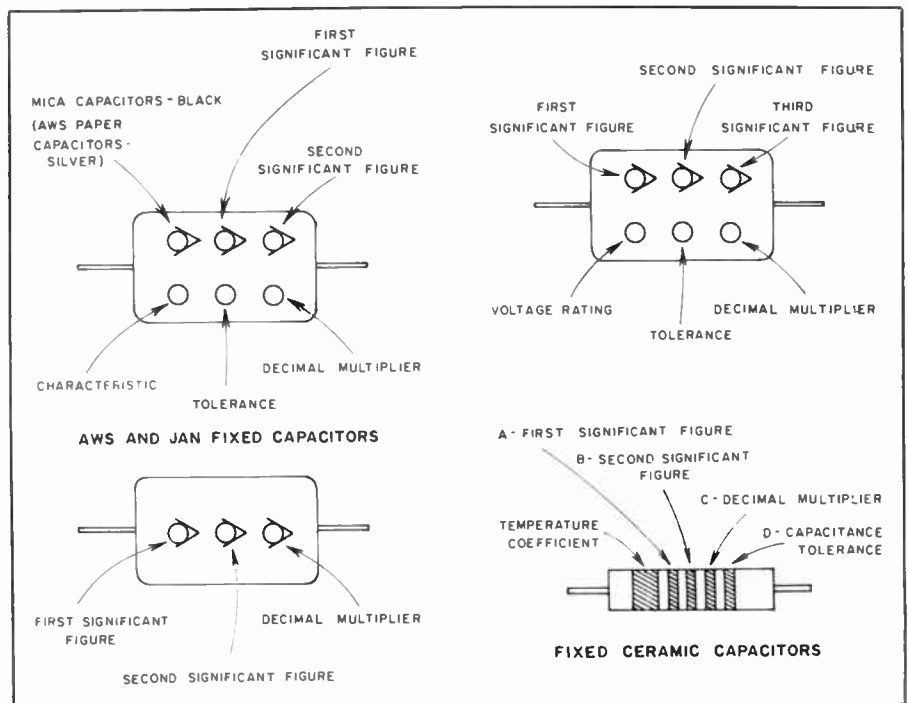


Fig. 12 — Color coding of fixed mica, molded paper and tubular ceramic capacitors. The color code for mica and molded paper capacitors is given in Table 4. Table 5 gives the color code for tubular ceramic capacitors.

mounted on the motor shaft and butts against the bottom of the etchant tray. As the motor turns, the eccentric disk raises and lowers one end of the tray, thus providing continuous agitation of the solution. The heat lamp is mounted on an adjustable, slotted wooden arm. Its height above the solution tray is adjusted to provide the desired bath temperature. Because the etching process takes between 15 minutes and one hour — dependent upon the strength and temperature of the bath — such an accessory is convenient.

After the etching process is completed, the board is removed from the tray and washed thoroughly with fresh, clear water. The etch-resist material can then be rubbed off by applying a few brisk strokes with medium-grade steel wool. **WARNING: Always use rubber gloves when working with etchant powders and solu-**

*tions. Should the acid bath come in contact with the body, immediately wash the affected area with clear water. Protect the eyes when using acid baths.*

### Component Values

Values of composition resistors and small capacitors (mica and ceramic) are specified throughout this *Handbook* in terms of "preferred values." In the preferred-number system, all values represent (approximately) a constant-percentage increase over the next lower value. The base of the system is the number 10. Only two significant figures are used.

"Tolerance" means that a variation of plus or minus the percentage given is considered satisfactory. For example, the actual resistance of a "4700-ohm" 20-percent resistor can lie anywhere between 3700 and 5600 ohms, approximately. The

**Table 3**  
Approximate Series-Resonance Frequencies of Disk Ceramic Bypass Capacitors

Capacitance	Freq. <sup>1</sup>	Freq. <sup>2</sup>
0.01 μF	13 MHz	15 MHz
0.0047	18	22
0.002	31	38
0.001	46	55
0.0005	65	80
0.0001	135	165

<sup>1</sup>Total lead length of 1 inch (25-mm)

<sup>2</sup>Total lead length of 1/2-inch (13-mm)

**Table 4**  
Resistor-Capacitor Color Code

Color	Significant Figure	Decimal Multiplier	Tolerance (%)	Voltage Rating*
Black	0	1	-	-
Brown	1	10	1*	100
Red	2	100	2*	200
Orange	3	1,000	3*	300
Yellow	4	10,000	4*	400
Green	5	100,000	5*	500
Blue	6	1,000,000	6*	600
Violet	7	10,000,000	7*	700
Gray	8	100,000,000	8*	800
White	9	1,000,000,000	9*	900
Gold	-	0.1	5	1000
Silver	-	0.01	10	2000
No color	-	-	20	500

\*Applies to capacitors only.

**Table 5**

**Color Code for Ceramic Capacitors**

Color	Significant Figure	Decimal Multiplier	More than 10 pF (in %)	Less than 10 pF (in pF)	Temp. Coeff. ppm/deg. C.
Black	0	1	±20	2.0	0
Brown	1	10	±1		-30
Red	2	100	±2		-80
Orange	3	1000			-150
Yellow	4				-220
Green	5				-330
Blue	6		±5	0.5	-470
Violet	7				-750
Gray	8	0.01		0.25	30
White	9	0.1	±10	1.0	500

**Table 6**

**Capacitor Characteristic Code**

Color	Temperature Coefficient	Capacitance
Sixth Dot	ppm/deg. C.	Drift
Black	±1000	±5% +1 pF
Brown	±500	±3% +1 pF
Red	±200	±0.5%
Orange	±100	±0.3%
Yellow	-20 to +100	±0.1% +0.1 pF
Green	0 to +70	±0.05% +0.1 pF

**Table 7**

**Color Code for Hookup Wire**

Wire Color	Type of Circuit
Black	Grounds, grounded elements, and returns
Brown	Heaters or filaments, off ground
Red	Power supply B plus
Orange	Screen grids and Base 2 of transistors
Yellow	Cathodes and transistor emitters
Green	Control grids, diode plates, and Base 1 of transistors
Blue	Plates and transistor collectors
Violet	Power supply, minus leads
Gray	Ac power line leads
White	Bias supply, B or C minus, agc

Wires with tracers are coded in the same manner as solid-color wires, allowing additional circuit identification over solid-color wiring. The body of the wire is white and the color band spirals around the wire lead. When more than one color band is used, the widest band represents the 1st color.

permissible variation in the same resistance value with 5-percent tolerance would be in the range from 4500 to 4900 ohms, approximately.

In the component specifications in this *Handbook*, it is to be understood that when no tolerance is specified the *largest* tolerance available in that value will be satisfactory.

Values that do not easily fit into the preferred-number system (such as 500, 25,000) can be substituted. It is obvious, for example, that a 5000-ohm resistor falls well within the tolerance range of the 4700-ohm 20-percent resistor used in the example above. It would not,

**Table 8**

**Metric Multiplier Prefixes**  
**Multiples and submultiples of fundamental units (e.g., ampere, farad, gram, meter, watt) may be indicated by the following prefixes.**

Prefix	Abbreviation	Multiplier
tera	T	10 <sup>12</sup>
giga	G	10 <sup>9</sup>
mega	M	10 <sup>6</sup>
kilo	k	10 <sup>3</sup>
hecto	h	10 <sup>2</sup>
deci	d	10 <sup>-1</sup>
centi	c	10 <sup>-2</sup>
milli	m	10 <sup>-3</sup>
micro	μ	10 <sup>-6</sup>
nano	n	10 <sup>-9</sup>
pico	p	10 <sup>-12</sup>

**Table 9**

**Pilot-Lamp Data**

Lamp No.	Bead Color	Base (Miniature)	Bulb Type	Rating Volts	Rating Amp.
40	Brown	Screw	T-3 1/4	6-8	0.15
40A <sup>1</sup>	Brown	Bayonet	T-3 1/4	6-8	0.15
41	White	Screw	T-3 1/4	2.5	0.5
42	Green	Screw	T-3 1/4	3.2	**
43	White	Bayonet	T-3 1/4	2.5	0.5
44	Blue	Bayonet	T-3 1/4	6-8	0.25
45	*	Bayonet	T-3 1/4	3.2	**
46 <sup>2</sup>	Blue	Screw	T-3 1/4	6-8	0.25
47 <sup>1</sup>	Brown	Bayonet	T-3 1/4	6-9	0.15
48	Pink	Screw	T-3 1/4	2.0	0.06
49 <sup>3</sup>	Pink	Bayonet	T-3 1/4	2.0	0.06
49A <sup>3</sup>	White	Bayonet	T-3 1/4	2.1	0.12
50	White	Screw	G-3 1/2	6-8	0.2
51 <sup>2</sup>	White	Bayonet	G-3 1/2	6-8	0.2
53	-	Bayonet	G-3 1/2	14.4	0.12
55	White	Bayonet	G-4 1/2	6-8	0.4
292 <sup>5</sup>	White	Screw	T-3 1/4	2.9	0.17
292A <sup>5</sup>	White	Bayonet	T-3 1/4	2.9	0.17
1455	Brown	Screw	G-5	18.0	0.25
1455A	Brown	Bayonet	G-5	18.0	0.25
1487	-	Screw	T-3 1/4	12-16	0.20
1488	-	Bayonet	T-3 1/4	14	0.15
1813	-	Bayonet	T-3 1/4	14.4	0.10
1815	-	Bayonet	T-3 1/4	12-16	0.20

<sup>1</sup>40A and 47 are interchangeable.

<sup>2</sup>Have frosted bulbs.

<sup>3</sup>49 and 49A are interchangeable.

<sup>4</sup>Replace with no. 48.

<sup>5</sup>Use in 2.5-volt sets where regular bulb burns out too frequently.

\*White in G.E. and Sylvania; green in National Union, Raytheon and Tung-Sol.

\*\*0.35 in G.E. and Sylvania; 0.5 in National Union, Raytheon and Tung-Sol.

however, be usable if the tolerance were specified as 5 percent.

**Color Codes**

Standardized color codes are used to mark values on small components such as composition resistors and mica capacitors, and to identify leads from transformers and other large components. The resistor-capacitor number color code is given in Table 4.

**Fixed Capacitors**

The methods of marking "postage-stamp" mica capacitors, molded paper capacitors and tubular ceramic capacitors

are shown in Fig. 12.

Capacitors made to American War Standards (AWS) or Joint Army-Navy (JAN) specifications are marked with the six-dot code shown at the top. Practically all surplus capacitors are in this category.

The three-dot EIA code is used for capacitors having a rating of 500 volts and ±20 percent tolerance only; other ratings and tolerances are covered by the six-dot EIA code.

Example: A capacitor with a six-dot code has the following markings: Top row, left to right, black, yellow, violet; bottom row, right to left, brown, silver, red. Since the first color in the top row is black (significant figure zero) this is the AWS code and the capacitor has mica dielectric. The significant figures are 4 and 7, the decimal multiplier 10 (brown, at right of second row), so the capacitance is 470 pF. The tolerance is ±0 percent. The final color, the characteristic, deals with temperature coefficients and methods of testing (see Table 6).

A capacitor with a three-dot code has the following colors, left to right: brown, black, red. The significant figures are 1, 0 (10) and the multiplier is 100. The capacitance is therefore 100 pF.

A capacitor with a six-dot code has the following markings: Top row, left to right, brown, black, black; bottom row, right to left, black, gold, blue. Since the first color in the top row is neither black nor silver, this is the EIA code. The significant figures are 1, 0, 0 (100) and the decimal multiplier is 1 (black). The capacitance is therefore 100 pF. The gold dot shows that the tolerance is ±5 percent and the blue dot indicates 600-volt rating.

**Ceramic Capacitors**

Conventional markings for ceramic capacitors are shown in the lower drawing of Fig. 12. The colors have the meanings indicated in Table 4. In practice, dots may be used instead of the *narrow* bands indicated in Fig. 12.

Example: A ceramic capacitor has the following markings: Broad band, violet; narrow bands or dots, green, brown, black, green. The significant figures are 5, 1 (51) and the decimal multiplier is 1, so the capacitance is 51 pF. The temperature coefficient is — 750 parts per million per degree celsius, as given by the broad band, the capacitance tolerance is ±5 percent

**Fixed Composition Resistors**

Composition resistors (including small wire-wound units molded in cases identical with the composition type) are color-coded as shown in Fig. 13. Colored bands are used on resistors having axial leads; on radial-lead resistors the colors are placed as shown in the drawing. When bands are used for color coding the body color has no significance.

Examples: A resistor of the type shown in the lower drawing of Fig. 13 has the

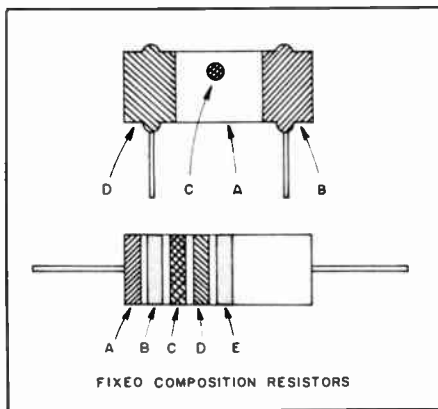


Fig. 13 — Color coding of fixed composition resistors. The color code is given in Table 4. The colored areas have the following significance:  
 A — First significant figure of resistance in ohms.  
 B — Second significant figure.  
 C — Decimal multiplier.  
 D — Resistance tolerance in percent. If no color is shown the tolerance is  $\pm 20\%$ .  
 E — Relative percent change in value per 1000 hours of operation; Brown, 1%; Red, 0.1%; Orange, 0.01%; Yellow, 0.001%.

following color bands: A, red; B, red; C, orange; D, no color. The significant figures are 2, 2 (22) and the decimal multiplier is 1000. The value of resistance is therefore 22,000 ohms and the tolerance is  $\pm 20$  percent.

A resistor of the type shown in the upper drawing has the following colors: Body (A), blue; end (B), gray; dot, red; end (D), gold. The significant figures are 6, 8 (68) and the decimal multiplier is 100, so the resistance is 6800 ohms. The tolerance is  $\pm 5$  percent.

#### I-F Transformers

- Blue — plate lead.
- Red — B+ lead.
- Green — grid (or diode) lead.
- Black — grid (or diode) return.

Note: If the secondary of the i-f transformer is center-tapped, the second diode plate lead is green-and-black striped, and black is used for the center-tap lead.

#### Audio Transformers

- Blue — plate (finish) lead of primary
- Red — B+ lead (this applies whether the primary is plain or center-tapped).
- Brown — plate (start) lead on center-tapped primaries. (Blue may be used for this lead if polarity is not important.)
- Green — grid (finish) lead to secondary.
- Black — grid return (this applies whether the secondary is plain or center-tapped).
- Yellow — grid (start) lead on center-tapped secondaries. (Green may be used for this lead if polarity is not important.)

Note: These markings apply also to line-to-grid and tube-to-line transformers.

#### Power Transformers

- 1) Primary Leads: black  
If tapped:

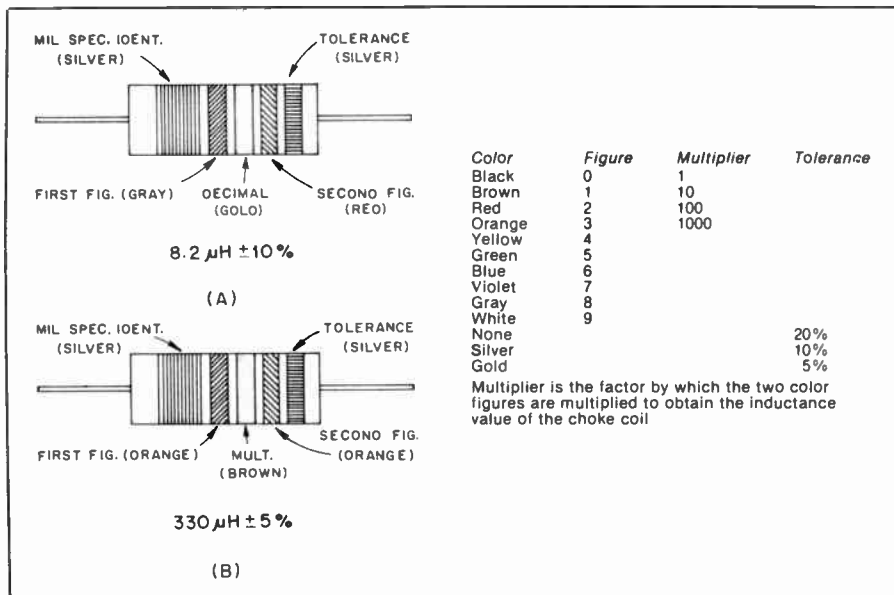


Fig. 14 — Color coding for tubular encapsulated rf chokes. At A, an example of the coding for an 8.2- $\mu$ H choke is given. At B, the color bands for a 330- $\mu$ H inductor are illustrated.

- Common: black
- Tap: black and yellow striped
- Finish: black and red striped
- 2) High-Voltage Plate Winding: red  
Center-Tap: red and yellow striped
- 3) Rectifier Filament Winding: yellow  
Center-Tap: yellow and blue striped
- 4) Filament Winding no. 1: green  
Center-Tap: green and yellow striped

- 5) Filament Winding no. 2: brown  
Center-Tap: brown and yellow striped
- 6) Filament Winding no. 3: slate  
Center-Tap: slate and yellow striped

#### Finding Parts

No chapter on construction would be complete without information on where to buy parts. Amateurs, on a dwarfed

Table 10

#### Frequency-Spectrum Reference Chart of nonamateur channel assignments and other frequency data.

Frequency (kHz)	Frequency (MHz)
15.734264 $\pm 0.000044$ : TV hor. scan freq.	1.8 - 2.0: Loran A (pulse transmission)
17.8 (0.5) <sup>1</sup> : NAA Cutler, ME	2.5 (0.5) <sup>1,2</sup> : WWV, Ft. Collins, CO; WWVH Kekaha, HI
18.6 (0.5) <sup>1</sup> : NPG/NLK Jim Creek, WA	3.33 (50) <sup>1,2</sup> : CHU, Ottawa, Canada
21.4 (0.5) <sup>1</sup> : NSS Annapolis, MD	3.395: Transceiver i-f (Heath, Kenwood)
24.0 (0.5) <sup>1</sup> : NBA Balboa, Panama, CZ	3.579545 $\pm 10^{-5}$ : TV chrominance subcarrier
26.1 (0.5) <sup>1</sup> : NPM, HI	5.0 (0.5) <sup>1,2</sup> : WWV, WWVH
60.0 (0.5) <sup>1,2</sup> : WWVB Ft. Collins, CO	5.645: receiver i-f (Drake)
85: Receiver i-f (command set or "Q5er")	7.335 (50) <sup>1,2</sup> : CHU
100.0 (0.5) <sup>1</sup> : Loran C (regional)	9.0: Xtal filters (KVG)
179: WGU20 CD Station, East Coast. Bc of WX and time (a-m)	10.0 (0.5) <sup>1,2</sup> : WWV, WWVH
285 - 325: Marine RDF band. Two cw tones 1020-Hz apart	10.7: Receiver i-f (fm bc)
285 - 405: Aero RDF; aero WX (a-m) 325 - 405.	14.67 (50) <sup>1,2</sup> : CHU
415 - 490: Marine (cw)	
455: Receiver i-f/mech. filters (Collins)	
535 - 1605: bc (a-m), 107 chans. every 10 kHz from 540 (carrier)	
	15.0 (0.5) <sup>1,2</sup> : WWV
	26.965 - 26.985: Citizens Band chan. 1-3 (10-kHz sep.)
	27.005 - 27.035: CB chan. 4-7
	27.055 - 27.085: CB chan. 8-11
	27.105 - 27.135: CB chan. 12-15
	27.155 - 27.185: CB chan. 16-19
	27.205 - 27.225: CB chan. 20-22
	27.235 - 27.255: CB chan. 24, 25, 23
	27.265 - 27.405: CB chan. 26-40
	41.25: TV sound carrier (location in receiver i-f)
	42.17: TV color subcarrier (location in receiver i-f)
	45.75: TV picture carrier (location in receiver i-f)
	54 - 72: TV chan. 2-4. (Three 6-MHz chans. starting from 54)
	72, 75: RC chans.
	76 - 88: TV chan. 5-6
	88.1 - 107.9: Bc (fm) 100 chan. from 88.1 (carrier) in 200-kHz steps
	120 - 130: Aero, RDF WX
	137.5, 137.62: WX Sat. (A4). Ref. W1AW Bul. for orbital data
	162.4: Marine WX bc (fm, regional)
	174 - 216: TV chan. 7-13
	470 - 890: TV chan. 14-83 (70 chan. 6-MHz wide)

<sup>1</sup>Standard-frequency transmission figure in brackets is error in parts  $10^{10}$  (Electronics Engineers' Handbook, McGraw Hill, pp. 1-48).

<sup>2</sup>Standard time station. A3 transmissions include time, weather and propagation on WWV/WWVH. A3 time transmission on CHU (English/French). WWVB has no A3; info in BCD format generated by reducing carrier by 10-dB (binary 0).



**Table 11**  
**ARRL PARTS SUPPLIER LIST**

E	Active Electronics Fasken Drive Malton, ON CANADA	M,N **\$5	Fair Radio Sales Box 1105 Lima, OH 45802	E,M *free	Poly Paks Box 942 Lynnfield, MA 01940
H	Airway Products P. O. Box 337A Princeton, MN 55371	L	Genessee Radio & Parts Co., Inc. 2550 Delaware Avenue Buffalo, NY 14216 716-873-9661 or Enterprise 2745	M,N **\$2	Precision Systems P. O. Box 6 Murray Hill, NJ 07974
E *stamp **10	Aldelco 2281 Babylon Tpk. Merrick, NY 11566	N	Paul A. Greenfield 9715 Tulsemere Road Randallstown, MD 21133	E	S.D. Sales P. O. Box 28810 Dallas, TX 75228
L *\$1 **&15	Allied Electronics 401 East 8th Street Ft. Worth, TX 76102 Att. Dept. QST	P	Gregory Electronics Corp. 249 Rte. 46 Saddle Brook, NJ 07662	D	Savoy Electronics, Inc. Box 5727 Ft. Lauderdale FL 33310
E,L	Alpha Electronic Laboratories 2302 Oakland Gravel Road Columbia, MO 65201 Att. Don Manson, KØTV0 314-874-1514	L	Gull Electronics, K3DPJ 12690 Route 30 North Huntingdon, PA 15642	C	Semtronics Rte. 3, Box 1 Bellaire, OH 43906
B	Amidon Associates 12033 Otsego Street N. Hollywood, CA 91607	A,H,O	Hal Devices Box 365 Urbana, IL 60801	D	Sentry Mfg. Co. Crystal Park Chickasha, OK 73108
O	Atlantic Surplus Sales 3730 Nautilus Avenue Brooklyn, NY 11224	E	Hamilton Avnet 4445 Sigma Road Dallas, TX 75240	F,V	Skylane Products 406 Bon Air Avenue Temple Terrace, FL 33617
A,E,I T,U	ATV Research 13th & Broadway Dakota City, NE 68731		Hammarlund Manufacturing Co. Div. of Pax Manufacturing Corp. 100 E. Montauk Highway Lindenhurst, NY 11757 (516) 888-5561 (Inst. Manuals - \$15, Schematics - \$5)	A,P	Spectronics 1009 Garfield Street Oak Park, IL 60304
B	Barken Electronics 274 Mt. Pleasant Avenue Livingston, NJ 07039	I,K **\$25	Hammond Manufacturing, Ltd. 394 Edinburgh Rd. N. Guelph, ON CANADA N1H 1E5	A,J	Spectrum International P. O. Box 1084 Concord, MA 01742 (617) 263-2145
A	Barker & Williamson, Inc. Canal Street Bristol, PA 19007		Hammond Manufacturing Co., Inc. (U.S.) 385 Nagel Drive Buffalo, NY 14225	M,N **\$4	Star Tronics P. O. Box 683 McMinnville, OR 97128
M,N *stamp **\$10	Budget Electronics 2704 W. North Avenue Chicago, IL 60647	L	Harrison Radio 20 Smith Street Farmingdale, L.I., NY 11735	B,O **\$10	Teletypewriter Comm. Specialists 550 Springfield Avenue Berkeley Heights, NJ 07922
L,A **\$50	Cambridge Thermionic Corp. 445 Concord Avenue Cambridge, MA 02138	L *\$.25 **\$1	HI Inc. Box 864 Council Bluffs, IA 51501 (send 25 cents and s.a.s.e. for manual list)	K,A	Ten-Tec Inc. Highway 411, E. Sevierville, TN 37862
H	Caywood Electronics (Millen Capacitors) 67 Maple Avenue Malden, MA 02148 MILLEN PARTS, EXC. MILLEN CAPACITORS Electronic Instrument and Specialty Corp. MC Division Lowell Street Winchester, MA 01890 Circuit Board Specialists P. O. Box 969 Pueblo, CO 81002 (Circuit Boards and ARRL Projects, Kits)	D **\$5	International Crystal Co. 10 North Lee Street Oklahoma City, OK 73102	O *s.a.s.e.	Typetronics Box 8873 Ft. Lauderdale, FL 33110 (305) 583-1340
A,E	Circuit Specialists P. O. Box 3047 Scottsdale, AZ 85257	D	JAN Crystals 2400 Crystal Drive Ft. Myers, FL 33907	E,M	Weinschenker Box 353 Irwin, PA 15642
M,N,R	Theodore E. Dames Co. 308 Hickory Street Arlington, NJ 07032	D	Kepro Circuit Systems 3630 Scarlet Oak Blvd. St. Louis, MO 63122	A,B,E	G. R. Whitehouse 11 Newberry Drive Amherst, NH 03031
I,M,N	Delta Electronics Co. P. O. Box 1 Lynn, MA 01903	C	Kirk Electronics 73 Ferry Road Chester, CT 06412	E,G,H D	Workman Electronic Prod. Inc. Box 3828 Sarasota, FL 33578 (314) 449-1362 (will refer indiv. to their nearest distr.)
R	Dennis Brothers RFD 1 Potter, NE 69156	F **\$10	Lafayette Radio Elect. 111 Jericho Tpk. Syosset, L.I. NY 11791		
L	Dominion Radio & Elect. Co. 535 Yonge Street Toronto, ON CANADA	L *free	John Meshna, Jr. Box 62 E. Lynn, MA 01904		
B,J	E. S. Electronic Labs Box 434 Excelsior Springs MO 64024	M,N **\$5	MFJ Enterprises P. O. Box 494 Mississippi State, MS 39762		
L **\$5	Electro-Sonic Supply 1100 Gordon Baker Road Willowdale, ON CANADA M2H 3B3 416-494-1555	A,B,H	J. W. Miller Co. 19070 Reyes Avenue Compton, CA 90224		
L	Electronics Distributors, Inc. 1960 Peck Street Muskegon, MI 49441	B	Palomar Engineers Box 455 Escondido, CA 92025		
		C	PBI Electronics P. O. Box 5 Azusa, CA 91702		
		L	C. M. Peterson Co. Ltd. 220 Adelaide St. N. London, ON CANADA N6B 3H4		
		J	Piezo Technology, Inc. P. O. Box 7859 Orlando, FL 32804		

**Chart Coding**

- A - New Components
- B - Toroids and Ferrites
- C - Etched Circuit Board Materials
- D - Transmitting and Receiving Materials
- E - Solid State Devices
- F - Antenna Hardware
- G - Dials and Knobs
- H - Variable Capacitors
- I - Transformers
- J - I-f Filters
- K - Cabinets and Boxes
- L - General Supplier
- M - Surplus Parts
- N - Surplus Assemblies
- O - RTTY Equipment & Parts
- P - Surplus FM gear and Parts
- R - Service of Collins Equipment
- T - Amateur TV Cameras & Components
- U - Microcomputer Peripheral Equipment
- V - Towers
- \*Catalog Price
- \*\*Minimum Order

To the best of our knowledge the suppliers shown are willing to sell components to amateurs in small quantities by mail. This listing does not necessarily indicate that these firms have the approval of ARRL.



scale, must function as purchasing agents in these perplexing times. A properly equipped buyer maintains as complete a catalog file as possible. Many of the companies listed in Table 11 will provide free catalogs upon written request. Others may charge a small fee for catalogs. Mail

ordering, especially for those distant from metropolitan areas, is today's means to the desired end when collecting component parts for an amateur project. Prices are, to some extent, competitive. A wise buyer will study the catalogs and select his merchandise accordingly.

Delays in shipment can be lessened by avoiding the use of personal checks when ordering. Bank or postal money orders are preferred by most distributors. Personal checks often take a week to clear, thereby causing frustrating delays in the order reaching you.

Table 12

Copper-Wire Table

Wire Size A.W.G. (B&S)	Diam. in Mils <sup>1</sup>	Circular Mil Area	Turns per Linear Inch (25.4-mm) <sup>2</sup> Enamel	S.C.E.	D.C.C.	Cont.-duty current <sup>3</sup> single wire in open air	Cont.-duty current <sup>3</sup> wires or cables in conduits or bundles	Feet per Pound (0.45 per kg) Bare	Ohms 1000 ft. 25°C	Current Carrying Capacity <sup>4</sup> at 700 C.M. per Amp.	Diam. in mm.	Nearest British S.W.G. No.
1	289.3	83690	—	—	—	—	—	3.947	.1264	119.6	7.348	1
2	257.6	66370	—	—	—	—	—	4.977	.1593	94.8	6.544	3
3	229.4	52640	—	—	—	—	—	6.276	.2009	75.2	5.827	4
4	204.3	41740	—	—	—	—	—	7.914	.2533	59.6	5.189	5
5	181.9	33100	—	—	—	—	—	9.980	.3195	47.3	4.621	7
6	162.0	26250	—	—	—	—	—	12.58	.4028	37.5	4.115	8
7	144.3	20820	—	—	—	—	—	15.87	.5080	29.7	3.665	9
8	128.5	16510	7.6	—	7.1	73	46	20.01	.6405	23.6	3.264	10
9	114.4	13090	8.6	—	7.8	—	—	25.23	.8077	18.7	2.906	11
10	101.9	10380	9.6	9.1	8.9	55	33	31.82	1.018	14.8	2.588	12
11	90.7	8234	10.7	—	9.8	—	—	40.12	1.284	11.8	2.305	13
12	80.8	6530	12.0	11.3	10.9	41	23	50.59	1.619	9.33	2.053	14
13	72.0	5178	13.5	—	12.8	—	—	63.80	2.042	7.40	1.828	15
14	64.1	4107	15.0	14.0	13.8	32	17	80.44	2.575	5.87	1.628	16
15	57.1	3257	16.8	—	14.7	—	—	101.4	3.247	4.65	1.450	17
16	50.8	2583	18.9	17.3	16.4	22	13	127.9	4.094	3.69	1.291	18
17	45.3	2048	21.2	—	18.1	—	—	161.3	5.163	2.93	1.150	18
18	40.3	1624	23.6	21.2	19.8	16	10	203.4	6.510	2.32	1.024	19
19	35.9	1288	26.4	—	21.8	—	—	256.5	8.210	1.84	.912	20
20	32.0	1022	29.4	25.8	23.8	11	7.5	323.4	10.35	1.46	.812	21
21	28.5	810	33.1	—	26.0	—	—	407.8	13.05	1.16	.723	22
22	25.3	642	37.0	31.3	30.0	—	5	514.2	16.46	.918	.644	23
23	22.6	510	41.3	—	37.6	—	—	648.4	20.76	.728	.573	24
24	20.1	404	46.3	37.6	35.6	—	—	817.7	26.17	.577	.511	25
25	17.9	320	51.7	—	38.6	—	—	1031	33.00	.458	.455	26
26	15.9	254	58.0	46.1	41.8	—	—	1300	41.62	.363	.405	27
27	14.2	202	64.9	—	45.0	—	—	1639	52.48	.288	.361	29
28	12.6	160	72.7	54.6	48.5	—	—	2067	66.17	.228	.321	30
29	11.3	127	81.6	—	51.8	—	—	2607	83.44	.181	.286	31
30	10.0	101	90.5	64.1	55.5	—	—	3287	105.2	.144	.255	33
31	8.9	80	101	—	59.2	—	—	4145	132.7	.114	.227	34
32	8.0	63	113	74.1	62.6	—	—	5227	167.3	.090	.202	36
33	7.1	50	127	—	66.3	—	—	6591	211.0	.072	.180	37
34	6.3	40	143	86.2	70.0	—	—	8310	266.0	.057	.160	38
35	5.6	32	158	—	73.5	—	—	10480	335	.045	.143	38-39
36	5.0	25	175	103.1	77.0	—	—	13210	423	.036	.127	39-40
37	4.5	20	198	—	80.3	—	—	16660	533	.028	.113	41
38	4.0	16	224	116.3	83.6	—	—	21010	673	.022	.101	42
39	3.5	12	248	—	86.6	—	—	26500	848	.018	.090	43
40	3.1	10	282	131.6	89.7	—	—	33410	1070	.014	.080	44

<sup>1</sup>A mil is 0.001 inch. <sup>2</sup>Figures given are approximate only; insulation thickness varies with manufacturer. <sup>3</sup>Max. wire temp. of 212°F (100°C) and max. ambient temp. of 135°F (57°C). <sup>4</sup>700 circular miles per ampere is a satisfactory design figure for small transformers, but values from 500 to 1000 c.m. are commonly used.

Semiconductor Diode Color Code

The "1N" prefix is omitted. A double-width band, which also identifies the cathode terminal end of the diode, is usually used as the first band. (An alternative method uses equal band widths with the set clearly grouped toward the cathode end.) The code is read starting at the cathode end.

Diodes having two-digit numbers are coded with a black band followed by second and third bands. A suffix letter is indicated by a fourth band.

Diodes with three-digit numbers are coded with the sequence numbers in the first, second and third bands. Any suffix letter is indicated by a fourth band.

The color code (numbers) is the same as the resistor-capacitor code. The suffix-letter code is A — brown, B — red, C — orange, D — yellow, E — green, and F — blue.

# Wave Propagation

Though great advances have been made in recent years in understanding the many modes of propagation of radio waves, variables affecting long-distance communication are very complex, and not entirely predictable. Amateur attempts to schedule operating time and frequencies for optimum results may not always succeed, but familiarity with the nature of radio propagation can reduce the margin of failure and add greatly to one's enjoyment of the pursuit of any kind of DX.

The sun, ultimate source of life and energy on earth, dominates all radio communication beyond the local range. Conditions vary with such obvious sun-related earthly cycles as time of day and season of the year. Since these differ for appreciable changes in latitude and longitude, almost every communications circuit is unique in some respects. There are also short- and long-term solar cycles which influence propagation in less obvious ways. Furthermore, the state of the sun at a given moment is critical to long-distance communication, so it is understandable that propagation forecasting is still a rather inexact science.

With every part of the radio spectrum open to our use differing in its response to solar phenomena, amateurs have been, and still are, in a position to contribute to advancement of the art, both by accident and by careful investigation.

## Solar Phenomena

Man's interest in the sun is older than recorded history. Sunspots were seen and discussed thousands of years ago, and they have been studied since Galileo observed them with one of the first telescopes ever made. Records of sunspot observations translatable into modern terms go back nearly 300 years. Current observations are statistically "smoothed" to maintain a continuous record, in the form of the *Zurich sunspot number*, on which propagation predictions mentioned later are based.

A useful modern indication of overall solar activity is the solar flux index. Solar flux noise is measured on various frequencies in many places. A 2800-MHz

measurement made several times daily in Ottawa is transmitted hourly by WWV. Because it is essentially current information, directly related to the sunspot number (see Fig. 1) and more immediately useful, it tends to displace the latter as a means of predicting propagation conditions.

## Sunspot Cycles

Even before their correlation with radio propagation variations was well-known, the periodic rise and fall of sunspot numbers had been studied for many years. These cycles average roughly 11 years in length, but have been as short as 9 and as long as 13 years. The highs and lows of the cycles also vary greatly. Cycle 19 peaked

in 1958 with a sunspot number of over 200. Cycle 20, of nearer average intensity, reached 120 in 1969. By contrast, one of the lowest, Cycle 14, peaked at only 60 in 1907.<sup>1</sup> Several cycle lows have not reached zero levels on the Zurich scale for any appreciable period, while others have had several months of little or no activity.

Sunspot cycles should not be thought of as having sine-wave shape. There can be isolated highs during the normally low years. A remarkable example was a run of several days in October, 1974, less than two years from the end of Cycle 20, when the solar flux reached 145, a level well

<sup>1</sup>Tilton, "The DXer's Crystal Ball," *QST*, June, August and September, 1975. WWV bulletin form changed in 1976, but basic principles apply.

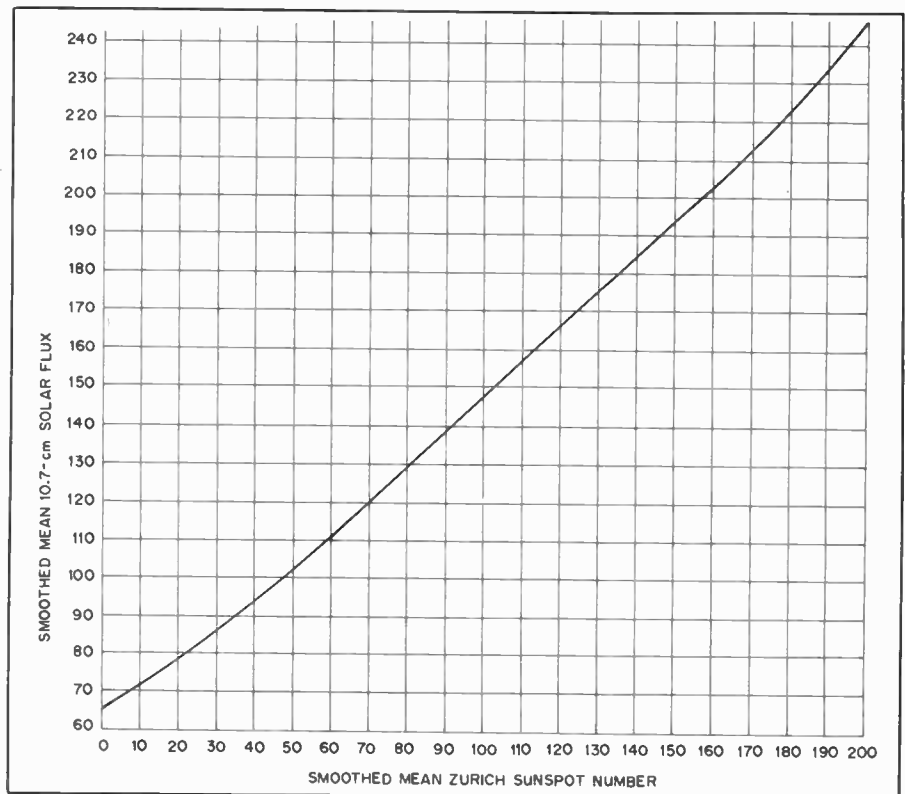


Fig. 1 — Relationship between smoothed mean Zurich sunspot number and the 2800-MHz solar flux. Highest solar flux recorded in 1974, October 12, was 145, the equivalent of a sunspot number of 100. Lowest flux value in 1975 and 1976 was 66, equating with a sunspot number very close to zero. Flux values in early 1978 ran from 87 to 197.



Fig. 2 — W1KXZ of the ARRL hq. staff looks for sunspots with a simple projection system. The baffle at the top end of the small telescope provides a shaded area for viewing the sun's image (light circle) on the projection surface. Sunspots large enough to affect radio propagation are easily seen with this viewing system.

above the highs of several cycles on record. Only five months later, several days of solar flux below 70 were recorded.

### Solar Radiation

Insofar as it affects most radio propagation, solar radiation is of two principal kinds: ultraviolet light and charged particles. The first travels at just under 300,000,000 meters (186,000 miles) per second, as does all electromagnetic radiation, so UV effects on wave propagation develop simultaneously with increases in observed solar noise, approximately eight minutes after the actual solar event. Particle radiation moves more slowly, and by varying routes, so it may take up to 40 hours to affect radio propagation. Its principal effects are high absorption of radio energy and the production of auroras, both visual and the radio variety.

Variations in the level of solar radiation can be gradual, as with the passage of some sunspot groups and other long-lived activity centers across the solar disk, or sudden, as with solar flares. An important clue for anticipating variations in solar radiation levels and radio propagation changes resulting from them is the rotational period of the sun, approximately 27 days. Sudden events (flares) may be short-lived, but active areas capable of influencing radio propagation may recur at four-week intervals for four or five solar rotations. Evidence of the "27-day cycle" is most marked during years of low solar activity.

Information on the condition of the sun, as it affects radio propagation, can be obtained in several ways. Projection of the sun's image as in Fig. 2 is particularly useful in the low years of the "11-year" cycle. At other times visible evidence of

solar activity may be more difficult to sort out. Enough definition for our purposes is possible with the simplest telescopes. Low-cost instruments, 10 to 30-power, are adequate. A principal requirement is provision for mounting on a tripod having a pan-tilt head.<sup>2</sup>

Adjust the aiming to give a circular shadow of the scope body, then move the scope slowly until a bright spot appears on the projection surface. Put a baffle on the scope to enlarge the shaded area and adjust the focus to give a sharp-edged image of the solar disk. If there are any sunspots you will see them now. Draw a rough sketch of what you see, every time an observation is made, and keep it with your record of propagation observations.

Spots move across the image from left to right, on the projected image, as it is viewed with the sun at the observer's back. The line of movement is parallel to the solar equator. Not all activity capable of affecting propagation can be seen, but any spots seen have significance. Active areas may develop before spots are visible and may persist after spots associated with them are gone, but once identified by date they are likely to recur about 27 days later, emphasizing the worth of detailed records.

Variations in solar noise may be observed by aiming the antenna at the rising or setting sun. Sudden large increases may be heard regardless of the antenna position. Such bursts are often heard, but seldom recognized for what they are — warnings of imminent changes in propagation.

Vhf or uhf arrays capable of movement in elevation as well as azimuth are useful for solar noise monitoring. With a good system, the "quiet sun" can be "heard" at a low level.<sup>3</sup> Bursts that can be many dB higher indicate the start of a major event, such as a solar flare capable of producing an hf blackout and possibly vhf auroral propagation.

### Characteristics of Radio Waves

All electromagnetic waves are moving fields of electric and magnetic force. Their lines of force are at right angles, and are mutually perpendicular to the direction of travel. They can have any position with respect to the earth. The plane containing the continuous lines of electric and magnetic force is called the *wave front*.

The medium in which electromagnetic waves travel has a marked influence on their speed of movement. In empty space the speed, as for light, is just under 300,000,000 meters per second. It is

slightly less in air, and it varies with temperature and humidity to a degree, depending on the frequency. It is much less in dielectrics, where the speed is inversely proportional to the square root of the dielectric constant of the material.

Waves cannot penetrate a good conductor to any extent because the electric lines of force are practically short-circuited. Radio waves travel through dielectric materials with ease.

### Polarization

If the lines of force in the electric field are perpendicular to the surface of the earth, the wave is said to be *vertically polarized*. If parallel with the earth, the polarization is said to be *horizontal*. It is possible to generate waves with rotating field lines. Known as *circular polarization*, this is useful in satellite communication, where polarization tends to be random. When the earth's surface is not available as a reference, polarization not of a rotating nature is described as linear or plane polarization, rather than vertical or horizontal, which become meaningless. Circular polarization is usable with plane-polarized antennas at the other end of the circuit, though with some small loss on most paths.

### Types of Propagation

Depending on the means of propagation, radio waves can be classified as *ionospheric*, *tropospheric*, or *ground waves*. The ionospheric or *skywave* is that main portion of the total radiation leaving the antenna at angles somewhat above the horizontal. Except for the reflecting qualities of the ionosphere, it would be lost in space. The tropospheric wave is that portion of the radiation kept close to the earth's surface as the result of bending in the lower atmosphere. The ground wave is that portion of the radiation directly affected by the surface of the earth. It has two components, an earth-guided *surface wave*, and the *space wave*. The latter is the resultant of two components, direct and ground-reflected. The terms "tropospheric wave" and "ground wave" are often used interchangeably, though this is not strictly correct.

### The Ionosphere

Long-distance communication and much over shorter distances, on frequencies below 30 MHz, is the result of bending of the wave in the *ionosphere*, a region between about 60 and 200 miles above the earth's surface where free ions and electrons exist in sufficient quantity to affect the direction of wave travel. Without the ionosphere, DX as we know it would be impossible.

Ionization of the upper atmosphere is attributed to ultraviolet radiation from the sun. The result is not a single region, but several layers of varying densities at

<sup>2</sup>Projection of the sun and interpretation of results are discussed in reference 1, and in *QST*, December, 1974, p. 83; January, 1975, p. 84 and October, 1976, p. 11. A black-box viewing device (Tomcik, K4HYF) for sun projection is shown in July, 1964, *QST*. (Photocopy from ARRL, 75 cents and stamped envelope.)

<sup>3</sup>Bray and Kirchner, "Antenna Patterns from the Sun," *QST*, July, 1960. Wilson, "432-MHz Solar Patrol," *QST*, August, 1967.



various heights surrounding the earth. Each layer has a central region of relatively dense ionization that tapers off both above and below.

### ***Ionospheric Layers***

The lowest useful region of the ionosphere is called the E layer. Its average height of maximum ionization is about 70 miles. The atmosphere here is still dense enough so that ions and electrons set free by solar radiation do not have to travel far before they meet and recombine to form neutral particles: The layer can maintain its ability to bend radio waves only when continuously in sunlight. Ionization is thus greatest around local noon, and it practically disappears after sundown.

In the daylight hours there is a still lower area called the D region where ionization is proportional to the height of the sun. Wave energy in the two lowest frequency amateur bands, 1.8 and 3.5 MHz, is almost completely absorbed by this layer. Only the highest-angle radiation passes through it and is reflected back to earth by the E layer. Communication on these bands in daylight is thus limited to short distances, as the lower-angle radiation needed for longer distances travels farther in the D region and is absorbed.

The region of ionization mainly responsible for long-distance communication is called the F layer. At its altitude, about 175 miles at night, the air is so thin that recombination takes place very slowly. Ionization decreases slowly after sundown, reaching a minimum just before sunrise. The obvious effect of this change is the early disappearance of long-distance signals on the highest frequency that was usable that day, followed by loss of communication on progressively lower frequencies during the night. In the daytime the F layer splits into two parts, F1 and F2, having heights of about 140 and 200 miles, respectively. They merge again at sunset.

Scattered patches of relatively dense ionization develop seasonally at E-layer height. Such *sporadic E* is most prevalent in the equatorial regions, but it is common in the temperate latitudes in late spring and early summer, and to a lesser degree in early winter. Its effects become confused with those of other ionization on the lower amateur frequencies, but they stand out above 21 MHz, especially in the low-activity years of the solar cycle, when other forms of DX are not consistently available.

Duration of openings decreases and the length of skip increases with progressively higher frequencies. Skip distance is commonly a few hundred miles on 21 or 28 MHz, but multiple hop propagation can extend the range to 2500 miles or more. June and July are the peak months in the northern hemisphere. Es propagation is most common in midmorning and early

evening, but may extend almost around the clock at times. The highest frequency for Es is not known, but the number of opportunities for using the mode drops off rapidly between the amateur 50- and 144-MHz bands, whereas 28 and 50 MHz are quite similar.

The greater the intensity of ionization in a layer, the more the wavepath is bent. The bending also depends on wavelength; the longer the wave the more its path is modified for a given degree of ionization. Thus, for a given level of solar radiation, ionospheric communication is available for a longer period of time on the lower-frequency amateur bands than on those near the upper limit of hf spectrum. The intensity and character of solar radiation are subject to many short-term and long-term variables, the former still predictable with only partial success.

### ***Absorption***

In traveling through the ionosphere, a radio wave gives up some of its energy by setting the ionized particles in motion. When moving particles collide with others, this energy is lost. Such *absorption* is greater at lower frequencies. It also increases with the intensity of ionization, and with the density of the atmosphere. This leads to a propagation factor often not fully appreciated: *Signal levels and quality tend to be best when the operating frequency is near the maximum that is reflected back to earth at the time.*

### ***Virtual Height***

An ionospheric layer is a region of considerable depth, but for practical purposes it is convenient to think of it as

having finite height, from which a simple reflection would give the same effects (observed from the ground) as result from the gradual bending that actually takes place. It is given several names, such as *group height*, *equivalent height*, and *virtual height*.

The virtual height of an ionospheric layer for various frequencies and vertical incidence is determined with a variable-frequency sounding device that directs pulses of energy vertically and measures the time required for the round-trip path shown in Fig. 3. As the frequency rises, a point is reached where no energy is returned vertically. This is known as the *critical frequency* for the layer under consideration. A representation of a typical *ionogram* is shown in Fig. 4.<sup>4</sup> In this sounding the virtual height for 3.5 to 4 MHz was 400 km. Because the ionogram is a graphical presentation of wave travel time, double-hop propagation appears as an 800-km return for the same frequency. The critical frequency was just over 5 MHz on this occasion. Such a clear F-layer ionogram is possible only under magnetically quiet conditions, and at night, when little or no E- and D-layer ionization is present.

### ***Effects of the Earth's Magnetic Field***

The ionosphere has been discussed thus far in terms of simple bending, or refraction, a concept useful for some explanatory purposes. But an understanding of long-distance propagation must take the earth's magnetic field into

<sup>4</sup>Davies, "Ionospheric Radio Propagation," NBS Monograph 80, out of print. Available in some technical libraries.

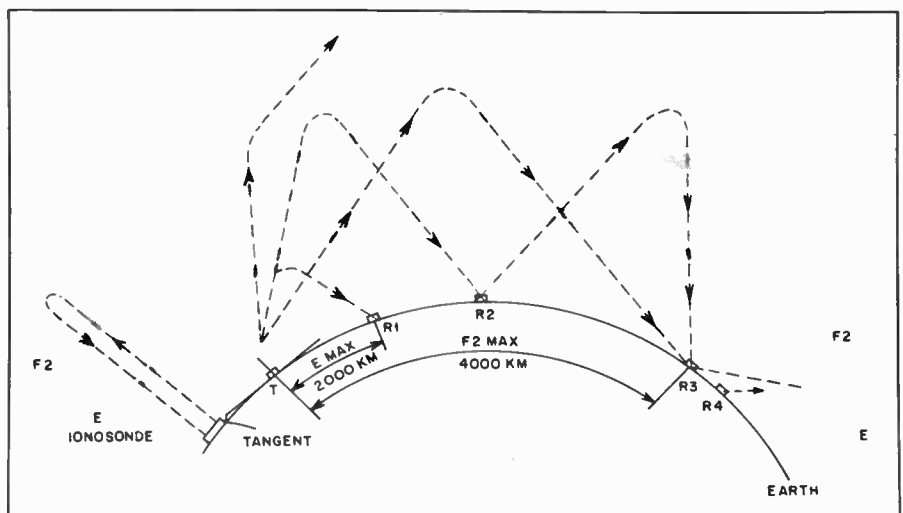


Fig. 3 — Three types of ionospheric propagation. Sounder, left, measures virtual height and critical frequency of F2 layer. Transmitter T is shown radiating at three different angles. Highest passes through the ionosphere after slight refraction. Lower-angle wave is returned to earth by the E layer, if frequency is low enough, at a maximum distance of 2000 km. The F-layer reflection returns at a maximum distance of about 4000 km, depending on the radiation angle. It is shown traversing a second path (double hop) from R2 to R4, the latter beyond single-hop range. The lowest-angle wave reaches the maximum practical single-hop distance at R3.



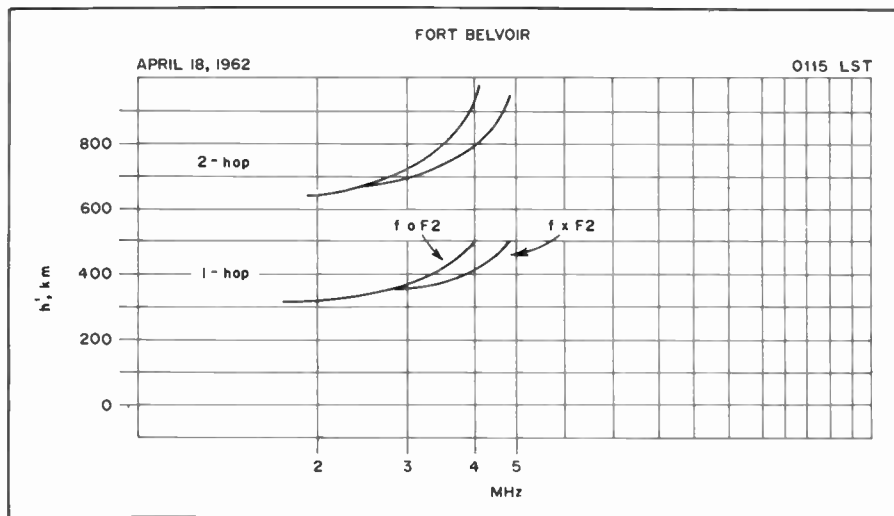


Fig. 4 — F-layer ionogram taken at night during magnetically quiet conditions. The traces show the breaking up into ordinary and extraordinary waves. Because it required twice the travel time, the double-hop return appears as having come from twice the height of the single-hop.

account. Because of it, the ionosphere is a birefringent medium (double refracting) which breaks up plane-polarized waves into what are known as the *ordinary* and *extraordinary waves*,  $f_o F2$  and  $f_x F2$  in the ionogram. This helps to explain the dispersal of plane polarization encountered in most ionospheric communication.<sup>5</sup>

Sudden marked increases in solar radiation, such as with solar flares, trigger instantaneous effects in the F, E and D regions; slightly delayed effects, mainly in the polar areas; and geomagnetic effects, delayed up to 40 hours.

Onset of the D-region absorption is usually sudden, lasting a few minutes to several hours, leading to use of the term SID (sudden ionospheric disturbance). Shortwave fadeouts (SWFs) and SIDs exhibit wide variations in intensity, duration and number of events, all tending to be greater in periods of high solar activity. Though their effects on radio propagation are of great importance, solar flares and associated disturbances are among the least predictable of solar-induced communications variables.

### Radiation Angle and Skip Distance

The lower the angle above the horizon at which a wave leaves the antenna, the less refraction in the ionosphere or troposphere is required to bring it back, or to maintain useful signal levels in the case of tropospheric bending. This results in the emphasis on low radiation angles in the pursuit of DX, on the hf or vhf bands. It is rarely possible to radiate energy on a line tangent to the earth's surface, but even when this is done some bending is still required for communication over appreciable distances because of earth curvature.

<sup>5</sup>See reference 4.

Some of the effects of radiation angle are illustrated in Fig. 3. The high-angle wave at the left is bent only slightly in the ionosphere, and so goes through it. The wave at the somewhat lower angle is just capable of being returned by the ionosphere. In daylight it might be returned via the E layer. Its area of return from the F layer, R2, is closer to the transmitting point, T, than is that of the lowest-angle wave. If R2 is at the shortest distance where returned energy is usable, the area between R1 and the outer reaches of the ground wave, near the transmitter, is called the *skip zone*. The distance between R2 and T is called the *skip distance*. The distances to both R1 and R2 depend on the ionization density, the radiation angle at T, and the frequency in use. The maximum distance for single-hop propagation via the F layer is about 2500 miles (4000 kilometers). The maximum E-layer single hop is about 1250 miles (2000 kilometers).

The maximum usable frequency (muf) for F-layer communication is about three times the critical frequency for vertical return, as in Fig. 3. For E-layer propagation it is about five times.

### Multiple-Hop Propagation

On its return to earth, the ionosphericly propagated wave can be reflected back upward near R1 or R2, travel again to the ionosphere, and be refracted back to earth. This process can be repeated several times under ideal propagation conditions, leading even to communication over distances well beyond halfway around the world. Ordinarily ionospheric absorption and ground-reflection losses exact tolls in signal level and quality, so multiple-hop propagation usually yields lower signal levels and more distorted modulation than single-hop. This is not always the case, and under ideal condi-

tions even long-way-around communication is possible with good signals. There is evidence to support the theory that signals for such communications, rather than hopping, may be ducted through the ionosphere for a good part of the distance.

### Fading

Two or more parts of the wave may follow different paths, causing phase differences between wave components at the receiving end. Total field strength may be greater or smaller than that of one component. Fluctuating signal levels also result from the changing nature of the wave path, as in the case of moving air-mass boundaries, in tropospheric propagation on the higher frequencies. Changes in signal level, lumped under the term *fading*, arise from an almost infinite variety of phenomena; some natural, some man-made. Aircraft reflections are in the latter category.

Under some circumstances the wave path may vary with very small changes in frequency, so that modulation sidebands arrive at the receiver out of phase, causing distortion that may be mild or severe. Called *selective fading*, this problem increases with signal bandwidth. Double-sideband a-m signals suffer much more than single-sideband signals with suppressed carrier do.

### The Scatter Modes

Much long-distance propagation can be described in terms of discrete reflection, though the analogy is never precise since true reflection would be possible only with perfect mirrors, and in a vacuum. All electromagnetic wave propagation is subject to scattering influences which alter idealized patterns to a great degree. The earth's atmosphere and ionospheric layers are scattering media, as are most objects that intervene in the wave path as it leaves the earth. Strong returns are thought of as reflections and weaker ones as scattering, but both influences prevail. Scatter modes have become useful tools in many kinds of communication.

### Forward Scatter

We describe a skip zone as if there were no signal heard between the end of useful ground-wave range and the points R1 or R2 of Fig. 3, but actually the transmitted signal can be detected over much of the skip zone, with sufficiently sensitive devices and methods. A small portion of the transmitted energy is scattered back to earth in several ways, depending on the frequency in use.

*Tropospheric scatter* extends the local communications range to an increasing degree with frequency, above about 20 MHz, becoming most useful in the vhf range. *Ionospheric scatter*, mostly from the height of the E region, is most marked at frequencies up to about 60 or 70 MHz.

Vhf tropospheric scatter is usable within the limits of amateur power levels and antenna techniques, out to nearly 500 miles. Ionospheric forward scatter is discernible in the skip zone at distances up to 1200 miles or so.

A major component of ionospheric scatter is that contributed by short-lived columns of ionization formed around meteors entering the earth's atmosphere. This can be anything from very short bursts of little communications value to sustained periods of usable signal level, lasting up to a minute or more. Meteor scatter is most common in the early morning hours, and it can be an interesting adjunct to amateur communication at 21 MHz and higher, especially in periods of low solar activity. It is at its best during major meteor showers.<sup>6</sup>

### **Backscatter**

A complex form of scatter is readily observed when working near the maximum usable frequency for the F layer at the time. The transmitted wave is refracted back to earth at some distant point, which may be an ocean area or a land mass where there is no use of the frequency in question at the time. A small part of the energy is scattered back to the skip zone of the transmitter via the ionospheric route.

Backscatter signals are generally rather weak, and subject to some distortion from multipath effects. But with optimum equipment they are usable at distances from just beyond the reliable local range out to several hundred miles. Under ideal conditions backscatter communication is possible over 3000 miles or more, though the term "sidescatter" is more descriptive of what probably happens on such long paths.

The scatter modes contribute to the usefulness of the higher parts of the DX spectrum, especially during periods of low solar activity when the normal ionospheric modes are less often available.

### **MF and HF Propagation**

The 1.8-MHz band offers reliable communication over distances up to about 25 miles during daylight. On winter nights ranges up to several thousand miles are possible.

The 3.5-MHz band is seldom usable beyond 200 miles in daylight, but long distances are not unusual at night, especially in years of low solar activity. Atmospheric noise tends to be high in the summer months on both 3.5 and 1.8 MHz.

The 7-MHz band has characteristics similar to 3.5 MHz, except that much greater distances are possible in daylight,

and more often at night. In winter dawn and dusk periods it is possible to work the other side of the world, as signals follow the darkness path.

The 14-MHz band is the most widely used DX band. In the peak years of the solar cycle it is open to distant parts of the world almost continuously. During low solar activity it is open mainly in the daylight hours, and is especially good in the dawn and dusk periods. There is almost always a skip zone on this band.

The 21-MHz band shows highly variable propagation depending on the level of solar activity. During sunspot maxima it is useful for long-distance work almost around the clock. At intermediate levels it is mainly a daylight DX band. In the low years it is useful for transequatorial paths much of the year, but is open less often to the high latitudes. Sporadic-E skip is common in early summer and midwinter.

The 28-MHz band is excellent for DX communication in the peak solar-cycle years, but mostly in the daylight hours. The open time is shorter in the intermediate years, and is more confined to low-latitude and transequatorial paths as solar activity drops off. For about two years near the solar minimum, F-layer openings tend to be infrequent, and largely on north-south paths, with very long skip.

Sporadic-E propagation keeps things interesting in the period from late April through early August on this band, and on 21 MHz, providing single-hop communication out to 1300 miles or so, and multiple-hop to 2600 miles. Effects discussed in the following section on vhf propagation also show up in this band, though tropospheric bending is less than on 50 MHz.

### **The World Above 50 MHz**

It was once thought that frequencies above 50 MHz would be useful only locally, but increased occupancy and improved techniques turned up many forms of long-distance vhf propagation. What follows supplements information given earlier in this chapter. First, let us consider the nature of our bands above 50 MHz.

#### *50 to 54 MHz*

This borderline region has some of the characteristics of both higher and lower frequencies. Just about every form of wave propagation is found occasionally in the 50-MHz band, which has contributed greatly to its popularity. Its utility for service-area communication should not be overlooked. In the absence of any favorable condition, the well-equipped 50-MHz station should be able to work regularly over a radius of 75 to 100 miles or more, depending on terrain and antenna size and height.

Changing weather patterns extend coverage to 300 miles or more at times, main-

ly in the warmer months. Sporadic-E skip provides seasonal openings for work over 400 to 2500 miles in seasons centered on the longest and shortest days of the year. Auroral effects afford vhf operators in the temperate latitudes an intriguing form of DX up to about 1300 miles. During the peak of "11-year" sunspot cycle 50-MHz DX of worldwide proportions may be workable by reflections of waves by the ionospheric F2 layer. Various weak-signal scatter modes round out the 50-MHz propagation fare.

#### *144 to 148 MHz*

Ionospheric effects are greatly reduced at 144 MHz. F-layer propagation is unknown. Sporadic-E skip is rare and much more limited in duration and coverage than on 50 MHz. Auroral propagation is quite similar to that on 50 MHz, except that signals tend to be somewhat weaker and more distorted at 144. Tropospheric propagation improves with increasing frequency. It has been responsible for 144-MHz work over distances up to 2500 miles, and 500 mile contacts are fairly common in the warmer months. Reliable range on 144 is slightly less than on 50 under minimum conditions.

#### *220 MHz and Higher*

Ionospheric propagation of the sorts discussed above is virtually unknown above about 200 MHz. Auroral communication is possible on 220 and 420 MHz, but probably not on higher frequencies, with amateur power levels. Tropospheric bending is very marked, and may be better on 432 than on 144 MHz, for example. Communication has been carried on over paths far beyond line of sight, on all amateur frequencies up through 10,000 MHz. Under minimum conditions, signal levels drop off slightly with each higher band.

### **Propagation Modes**

Known means by which vhf signals are propagated beyond the horizon are described below.

#### *F2-Layer Reflection*

Most communication on lower frequencies is by reflection of the wave in the F region, highest of the ionized layers. Its density varies with solar activity, the maximum usable frequency (muf) being highest in peak years of the sunspot cycle. Cycle 19 hit an all-time high (in the recorded history of sunspot activity) in the fall of 1958, which may never be equaled within the lifetime of some of us. Cycle 20 produced 50-MHz F2 DX in 1968 to 1970, but less than Cycle 18 (1946 to 1949), and far less than Cycle 19.

The muf for F2-layer propagation follows daily, monthly and seasonal cycles, all related to conditions on the sun, as with the hf bands. Frequent checks will show if the muf is rising or falling, and the times and directions for which it is

<sup>6</sup>Bain, "VHF Propagation by Meteor Trail Ionization," *QST*, May, 1974. Table of major meteor showers, *Radio Amateurs VHF Manual*, Ch. 2.

highest. Two-way work has been done over about 1800 to 12,500 miles; even greater, if daylight routes around the earth the long way are included. The muf is believed to have reached about 70 MHz in 1958.

#### The TE Mode

Also associated with high solar activity is a transequatorial mode, having an muf somewhat higher than the F2. This is observed most often between points up to 2500 miles north and south of the geomagnetic equator, mainly in late afternoon or early evening.<sup>7</sup> Work done by amateurs, beginning in 1976, has shown that the TE mode works in the 144-MHz band, and possibly on even higher frequencies.

#### Sporadic-E Skip

Patchy ionization of the E region of the ionosphere often propagates 28- and 50-MHz signals over 400 to 1300 miles or more. Often called "short skip," this is most common in May, June and July, with a shorter season around year end. Seasons are reversed in the southern hemisphere. E skip can occur at any time or season, but is most likely in mid-morning or early evening. Multiple-hop effects may extend the range to 2500 miles or more.

Es propagation has been observed in the 144-MHz band, and on TV channels up to about 200 MHz. Minimum skip distance is greater, and duration of openings much shorter, on 144 MHz than on 50. Reception of strong Es signals from under 300 miles on 50 MHz indicates some possibility of skip propagation on 144, probably to 800 miles or more.

#### Aurora Effect

High-frequency communication may be wiped out or seriously impaired by absorption in the ionosphere, during disturbances associated with high solar activity and variations in the earth's magnetic field. If this occurs at night in clear weather, there may be a visible aurora; but the condition also develops in daylight, usually in late afternoon. Weak wavy signals in the 3.5- and 7-MHz bands are good indicators.

Vhf waves can be returned to earth from the auroral region, but the varying intensity of the aurora and its porosity as a propagation medium impart a multipath distortion to the signal, which garbles or even destroys any modulation. Distortion increases with signal frequency and varies, often quite quickly, with the nature of the aurora. Single-sideband is preferred to modes requiring more bandwidth. The most effective mode is cw, which may be the only reliable communications method at 144 MHz and higher, during most auroras.

Propagation is generally from the north, but probing with a directional array is recommended. Maximum range is about 1300 miles, though 50-MHz signals are heard occasionally over greater distances, usually with little or no auroral distortion.

How often auroral communication is possible is related to the *geomagnetic* latitude of participating stations, auroras being most frequent in northeastern USA and adjacent areas of Canada. They are rare below about 32°N in the Southeast and about 38 to 40°N in the Southwest. The highest frequency for auroral returns depends on equipment and antennas, but auroral communication has been achieved up to at least 432 MHz.

#### Tropospheric Bending

An easily-anticipated extension of normal vhf coverage results from abrupt changes in the refractive index of the atmosphere, at boundaries between air masses of differing temperature and humidity characteristics. Such warm-dry over cool-moist boundaries often lie along the southern and western edges of stable slow-moving areas of fair weather and high barometric pressure. Tropospheric bending can increase signal levels from within the normal working range, or bring in more distant stations, not normally heard.

A condition known as *ducting* or *trapping* may simulate propagation within a waveguide, causing vhf waves to follow earth curvature for hundreds or even thousands of miles. Ducting incidence increases with frequency. It is rare on 50 MHz, fairly common on 144, and more so on higher frequencies. It occurs most often in temperate or low latitudes. It was the medium for the W6NLZ-KH6UK work on 144, 220 and 432 MHz, over a 2540-mile path. Gulf Coast states see it often, the Atlantic Seaboard, Great Lakes and Mississippi Valley areas occasionally, usually in September and October.

Many local conditions contribute to tropospheric bending. Convection in coastal areas in warm weather; rapid cooling of the earth after a hot day, with upper air cooling more slowly; warming of air aloft with the summer sunrise; subsidence of cool moist air into valleys on calm summer evenings — these familiar situations create upper-air conditions which can extend normal vhf coverage.

The alert vhf enthusiast soon learns to correlate various weather signs and propagation patterns. Temperature and barometric-pressure trends, changing cloud formations, wind direction, visibility and other natural indicators can give him clues as to what is in store in the way of tropospheric propagation.

The 50-MHz band is more responsive to weather effects than 28, and 144 MHz is much more active than 50. This trend continues into the microwave region, as

evidenced by tropospheric records on all our bands, up to and including work over a 275-mile path on 10,000 MHz.

#### The Scatter Modes

Though they provide signal levels too low for routine communication, several scatter modes attract the advanced vhf operator.

Tropospheric scatter offers marginal communication up to 500 miles or so, almost regardless of conditions and frequency, when optimum equipment and methods are used.

Ionospheric scatter is useful mainly on 50 MHz, where it usually is a composite of meteor bursts and a weak residual scatter signal. The latter may be heard only when optimum conditions prevail. The best distances are 600 to 1200 miles.

Backscatter, common on lower frequencies, is observed on 50 MHz during ionospheric propagation, mainly of the F2 variety. Conditions for 50-MHz backscatter are similar to those for the hf bands, detailed earlier in this chapter.

Scatter from meteor trails in the E region can cause signal enhancement, or isolated bursts of signal from a station not otherwise heard. Strength and duration of meteor bursts decrease with increasing signal frequency, but the mode is popular for marginal communication in the 50- and 144-MHz bands. It has been used on 220 MHz, and, more marginally, on 432 MHz.

Random meteor bursts can be heard by cooperating vhf stations at any time or season, but early-morning hours are preferred. Major meteor showers (August Perseids and December Geminids) provide frequent bursts. Some other showers have various periods, and may show phenomenal burst counts in peak years. Distances are similar to other E-layer communication.

All scatter communication requires good equipment and optimum operating methods. The narrow-band modes are superior to wide-band systems.

#### Communication Via the Moon

Though amateurs first bounced signals off the moon in the early 1950s, real communication via the earth-moon-earth (EME) route is a fairly recent accomplishment. Requirements are maximum legal power, optimum receiving equipment, very large high-gain antennas, and precise aiming. Sophisticated tracking systems, narrow bandwidth (with attendant requirements for receiver and transmitter stability) and visual signal-resolution methods are desirable. Lunar work has been done on all amateur frequencies from 50 to 2400 MHz, over distances limited only by the ability of the stations to "see" the moon simultaneously.

For more detailed vhf propagation information and references, see *The Radio Amateur's VHF Manual*, chapter 2.

<sup>7</sup>World Radio and TV Handbook, Billboard Publications, London W1V 1PG England; 2160 Patterson Street, Cincinnati, OH 45124. Gilfer Associates, Box 239, Park Ridge, NJ 07656.



## Propagation Prediction

Information on the prediction of maximum usable frequencies (muf) and optimum working frequencies for F-layer propagation was formerly available from the U.S. Government Printing Office. The material took several forms, as methods developed for military communications use were adapted to worldwide civilian needs. Though the service was terminated in 1975, the basic methods are still of interest. A full description may be found in *QST* for March, 1972.<sup>8</sup> The government information is available in some technical libraries. The propagation charts which appear regularly in *QST* are computer-derived from information similar to that described in reference 8.

Other means are available to amateurs who wish to make their own predictions, both short- and long-term. An appreciable amount of observing and record-keeping time is involved at first, but the work can be streamlined with practice. Many amateurs who try it find the task almost as interesting as any operational success that may result from it. Properly organized, data collection and propagation prediction can become an ideal group project.

### Getting Started

Because most factors have well-defined cyclical trends, the first step in propagation prediction is to become familiar with the rhythm of these trends for the geographical location and season under consideration. This job is made easier if we understand the causes of the ups and downs, so familiarity with basic information given earlier in this chapter is helpful.

What frequencies are "open," and where the cutoff in ionospheric propagation lies in the spectrum can be determined quite readily by tuning upward in frequency with a general-coverage receiver, until ionospherically propagated signals are no longer heard. The muf for the day and the times that a given frequency band opens or closes can be found in this way. A daily log will show if conditions are improving or deteriorating.

Listening in the amateur bands and on immediately adjacent frequencies may be the only way to do this, if the receiver is the amateur-bands-only variety. Most DX bands are narrower in other parts of the world than in the Americas, so there is no lack of round-the-clock occupancy by other services, ordinarily. Most receivers also cover somewhat more than the actual amateur assignments, at their widest, so some commercial and governmental signals can be found close by our band edges. A worldwide listing of stations, by frequency, is useful in identifying signals for

Table 1

Some time and frequency stations useful for propagation monitoring.

Call	Frequency (kHz)	Location
WWV	2500; 5000; 10,000; 15,000	Ft. Collins, Colorado
WWVH	Same as WWV	Kekaha, Kauai, Hawaii
CHU	3330; 7335; 14,670	Ottawa, Ontario, Canada
RID	5004; 10,004; 15,004	Irkutsk, USSR*
RWM	4996; 9996; 14,996	Novosibirsk, USSR*
ZUO	2500; 5000	Pretoria, South Africa
VNG	7500	Lyndhurst, Australia
BPV	5000; 10,000; 15,000	Shanghai, China
JJY	2500; 5000; 10,000; 15,000	Tokyo, Japan
LOL	5000; 10,000; 15,000	Buenos Aires, Argentina

\*Call, from international table, may not check with actual reception. Locations and frequencies appear to be as given.

propagation monitoring purpose. Don't overlook WIAW; frequencies and schedule are listed in every *QST*.

Ability to tune to 5 MHz and multiples thereof, to receive the standard time-and-frequency stations now operating in many parts of the world, is a great aid. See Table 1. Most such stations operate continuously, with appreciable power and omnidirectional antennas. WWV and WWVH are excellent indicators, at any suitable distance from Colorado or Hawaii. Their signal behavior can tell the experienced observer at least as much about propagation — at the moment — as does the content of their propagation bulletins. Many receivers can be made to tune some of these frequencies by detuning their front-panel tracking controls. See September 1975 *QST*, page 23, for suggestions. Simple crystal-controlled converters for the standard frequencies offer another possibility (June 1976 *QST*, page 25).

### Recurring Phenomena

Because the sun is responsible for all radio-propagation variables, their rhythmic qualities are related to time, season and other sun-earth factors. Some are obvious. Others, particularly the rotational period of the sun, about 27.5 days, show best in long-term chart records kept on a monthly or four-week basis. Recurrence data are used in nearly all prediction work done presently, and the data can yield fair accuracy.

If the muf is high and conditions are generally good for several days, a similar condition is likely to prevail four weeks later, when the same area of the sun will be in view from the earth. Ionospheric disturbances also generally follow the 27-day cycle, though there may be marked differences in level from one period to the next.

Some solar-activity centers are short-lived, lasting less than a full rotation. Others go on and on, recognizable from their propagation effects for a year or more. Recurring phenomena are more apparent in the low-activity years of the solar cycle, most of them being far enough apart to be clearly identifiable. In April and May, 1976, for example, there were

three well-separated areas affecting radio propagation. All were of "the old cycle." There were also three new-cycle areas seen briefly, but with no recognizable radio-propagation influence. The WWV propagation bulletins described will be seen to show recurring effects, if their content is charted for extended periods.

### WWV Propagation Bulletins

The National Bureau of Standards radio station WWV, Ft. Collins, CO, transmits hourly bulletins on solar activity and the condition of the earth's magnetic field. This information is essentially current, and thus invaluable to any student of radio propagation. Putting it into simple chart form and using it in conjunction with visual observation of the sun provides an excellent base for propagation understanding and prediction. The WWV (and WWVH) signals themselves are also very useful in gathering propagation data, as the stations are on the air continuously, using constant power levels and omnidirectional antennas. It should be stated here that WWVH (Kekaha, HI) does not carry the bulletin service, but its signals provide valuable propagation evidence. Other time-and-frequency stations, some of which are listed in Table 1, can be used similarly.

In order of their presentation, the WWV bulletins give the solar flux and A-index for the previous Universal Coordinated Time (UTC) day; the Boulder K-index (changed every 6 hours); the state of solar activity and the condition of the earth's magnetic field for the previous 24 hours, and the same factors predicted for the coming 24 hours. The bulletin starts after the time announcement at 18 minutes after each hour.

The solar flux is a measure of the sun's radiation at 2800 MHz, taken daily at 1700 UTC in Ottawa. Similar measurements are made on many different frequencies at other observatories. The 2800-MHz flux is given because this value correlates well with the ionization density of the ionospheric F region, with the Zurich sunspot number (see Fig. 1), and with the maximum usable frequency for long-

<sup>8</sup>Hall, "High-Frequency Propagation Estimations for the Radio Amateur," *QST*, March, 1972.



distance communication.

A solar flux value of 66 represents "quiet sun" conditions. It will be heard only in the years near the minimum of the solar cycle, most recently 1975 and 1976. At such times any flux variation is worthy of note, as it will produce an observable change in long-distance propagation in the hf range. Large increases in flux values come from large new active areas on the sun, which will be apparent to the regular viewer of the sun. The short-term effects of flares do not appear in the solar flux values, unless they are very large and numerous. Flares are mentioned in the bulletins, if they are major events capable of affecting radio propagation.

A steady rise or fall in solar flux will show clearly in radio propagation effects, and also in the observer's view of sunspot activity. Trends either way are important to the propagation student. They often run for several days, during which the associated changes in muf, and in the duration and geographical distribution of openings on frequencies above about 15 MHz, are easily observed. Flux readings of 80 or higher will make the 21- and 28-MHz bands come alive, even near the bottom of the solar cycle.

In the intermediate years of the cycle, as in 1977 to 1979, flux values tend to range between about 100 and 200, the latter being high enough to make even the 50-MHz band worth watching for worldwide communication on the more favored paths. When values above 200 come, the 21- and 28-MHz bands are open almost around the clock during the cooler months of the year. Sustained periods above 250, particularly in spring and fall, will bring widespread 50-MHz openings.

The *A-index* is a 24-hour figure for the activity of the geomagnetic field, on a scale of 0 to 400 or so, though values of 100 or more are rare. A quiet field (*A* indices of 10 or lower) is characteristic of the best propagation conditions. Absorption of wave energy is low at such times, so signals are strong on long paths. This effect is most noticeable on circuits crossing the higher latitudes, where very low *K* values must prevail or propagation will be very poor or nonexistent. The effect of geomagnetic activity is very slight on low-latitude paths or any circuit crossing the equator. In fact, it is observed that north-south or transequatorial propagation may *improve* briefly at the onset of a period of high *A* (and *K*) indices, especially on the highest frequency that is usable at all.

The *K-index* is similar to the *A-index*, except that it is as near to a current figure as can be given in bulletin form. It is also given on a different mathematical scale, in order to make short-term changes more apparent. The information given by WWV is for Boulder, Colorado. It is likely to be higher for Boston, and lower for San Francisco or New Orleans, both

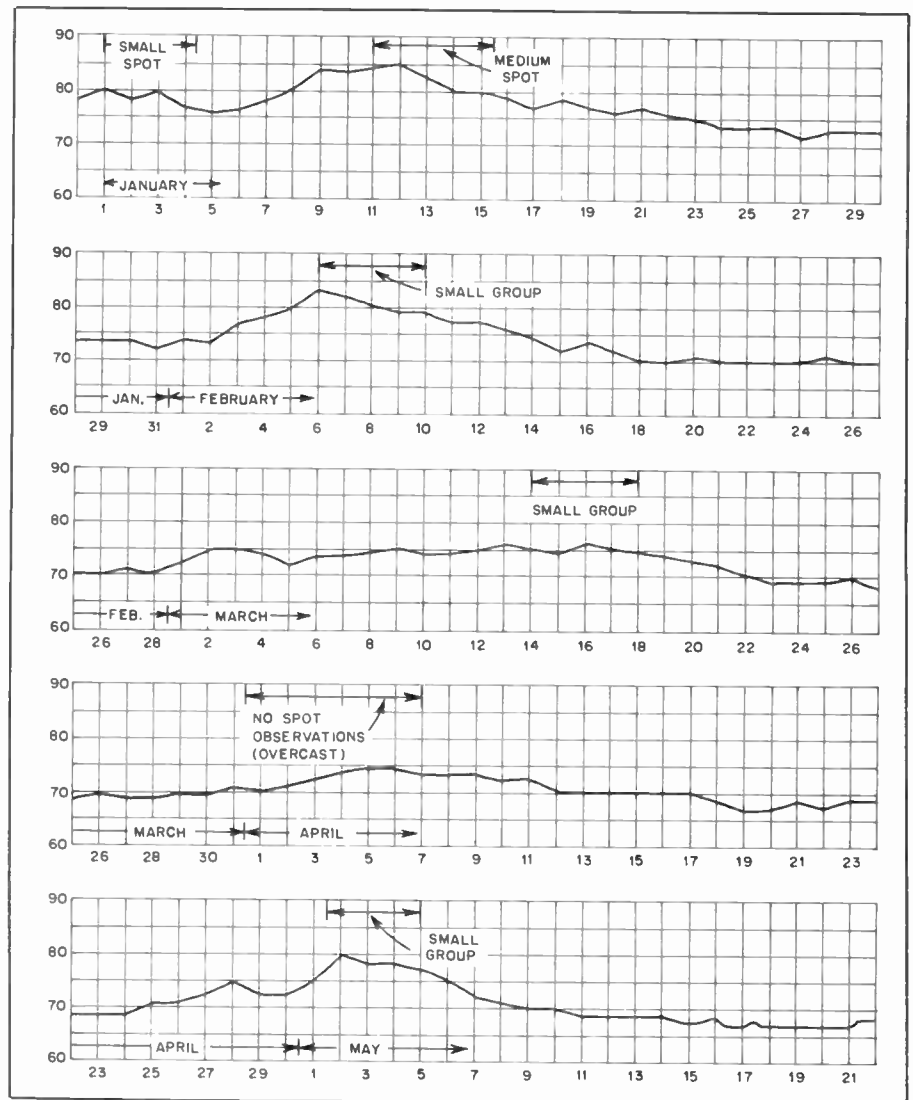


Fig. 5 — Graphs of 2800-MHz solar-flux information, as transmitted by WWV, for five consecutive four-week periods in early 1975. It will be seen that, even in this period of relatively low solar activity, the flux readings rise and fall with the passage of small spots. The rise in muf is mainly in the first half of the spot or group's passage across the solar disk. Observation in this period was with the system shown in Fig. 2

the latter cities having much lower geomagnetic latitude than either Boulder or Boston, while Boston's is higher than Boulder's.

The *K-index* is given for six-hour periods beginning at 0000, 0600, 1200 and 1800 UTC. It represents the conditions during the last three hours just before the bulletin's time of issue. Thus, it is close to a *now* statement of a factor of vital importance to any user of the hf radio spectrum. It may interest vhf operators as well, when the values go above 3. The *trend* is important — a rising trend means degraded hf propagation; values of 4 and up may mean auroral conditions on the vhf bands.

*Solar Activity*, as the term is used in the final portion of the WWV bulletins, relates to fast-changing conditions that affect propagation adversely. Activity is given as *very low*, *low*, *moderate*, *high* or *very high*.

*Geomagnetic field* conditions are termed *quiet*, *unsettled* or *active*. These relate roughly to *K* indices of 0 to 1 for *quiet*, 1 to 3 for *unsettled*, and 4 or higher for *active*. These three words rather aptly describe the propagation conditions associated with them and with the *K* indices. Often any *K* value of 4 or higher will be associated with a "geomagnetic storm," usually described as "minor" or "major." Either is bad news for the amateur interested in high-latitude hf communication. "Major" may include a total or near-total interruption of all communication on the lower hf bands. It is likely to be accompanied by auroral conditions on the vhf bands, at least in the higher latitudes.

*K* values are used to derive the *A-index* for the whole UTC day. The manner in which this is done is rather involved. It is spelled out in detail in reference 1. Explanation of the bulletin data in greater detail is also given, though the form of the

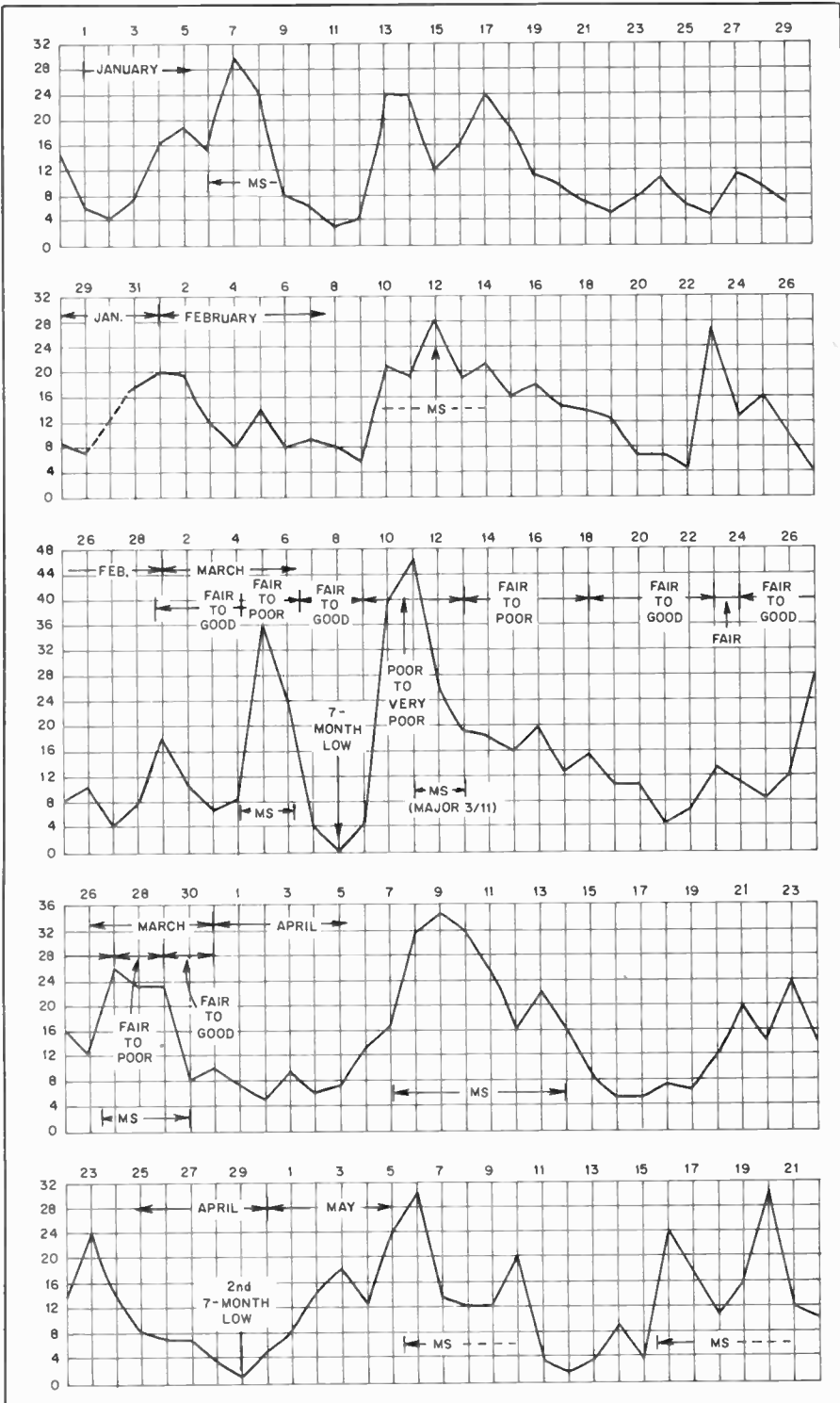


Fig. 6 — A-index information as transmitted by WWV, for the same four-week periods as Fig. 5. Propagation conditions as to level of absorption are indicated for the month of March, normally the most disturbed period of the year. Periods of geomagnetic storms are indicated by MS. It will be seen that disturbed periods show very marked 27-day recurrence effects, though the severity of disturbance is not necessarily consistent.

bulletins is now different from that described in the three 1975 *QST* articles. Information on all WWV services can be had by writing the National Bureau of Standards, Boulder, CO 80302.

### Keeping Records

In a group project, or for the individual

observer who has the time for it, charting all WWV information is very useful. A less time-consuming effort, since it requires logging only a single bulletin each day, is a chart record of the solar flux and A-index only. Depending on the time available, this record can take many forms. In the interest of readability here, Figs. 5 and 6

are separate records of the solar flux and A-index. Both are plotted in four-week periods, lined up vertically to show recurrent effects resulting from the solar rotational period.

For his own purposes the author developed a compact form containing much more detail than could be reproduced clearly. Graph paper having five blocks to the inch is cut to just over 54 blocks high and 73 blocks wide. This format was chosen to fit a standard binder 11-1/2 × 15-1/2 inches (292 × 394-mm) in size. Two blocks per day are used horizontally, the record beginning a day or two before the first of the month, and running over up to three days at the end, for better continuity in the total information. Solar flux values are plotted in the upper portion of the sheet, using two squares for each five flux units. The A and K indices share the lower portion, using different scales. The A-index is plotted at two units per block and the K-index at one unit per block. Using a different color for each item helps to keep them sorted out visually.

Much more information can be added. Brief propagation notes, drawings of the sun for the more significant dates, and a record of the solar flux and A-index values for the corresponding day four weeks before are commonly used. If the record for the previous solar rotation is inked in lightly (solar flux and A-index only) when the chart is first set up, it will make anticipation of recurring effects much easier. It should be emphasized that solar rotation time is by no means the whole story. Clearly there are occasional surprises which are not explained by this factor alone. Activity centers die out and new ones are born, seemingly without reason. Prediction of these seeming anomalies presents a challenge not yet met fully by anyone, including professionals. It is a wide-open field.

### Solar Observation

Regular viewing of the sun should be a part of any major propagation-prediction effort. Even simple projection with a low-cost telescope, as shown in Fig. 2, is well worthwhile, if it is done regularly and drawings are made to record what is seen. Improvements in technique need not be costly. A desirable first step is a light-exclusion box. An example, shown in use in Fig. 7, uses a corrugated-paper box sprayed dull black, inside and out, with a white viewing surface cemented in the bottom. The observer should position himself so as to see as little light other than that of the solar image as possible. A wide-brim hat is useful in this. For a complete black-box viewing system that can be built from plywood and simple optical components, see reference 2.

The telescope shown in Fig. 2 is a low-priced model which has a power of 10. Target scopes and the like in this general



Fig. 7 — Projection viewing of the sun's image with a 4-inch (102-mm) reflector-type telescope. White-paper viewing surface is cemented in the bottom of a black-sprayed cardboard box.



Fig. 8 — Direct viewing of the sun should be done only with a telescope equipped with an aperture filter known to be safe for this purpose. Telescope is a Celestron 5 with the maker's solar filter, which passes 0.01 percent of impinging light. A brimmed hat shading the observer's eyes from direct rays of the sun helps to improve visual acuity.

range work well, especially with the light-exclusion methods described above. Many radio amateurs are also interested in astronomy, and thus may already have much better instruments available. Moderately priced 2- or 3-inch (51- or 76-mm) refractors give beautiful detail with light-exclusion viewing. Telescopes with more than 4-inch (102-mm) aperture are not recommended for projection, as they may develop enough internal heating to damage optical components. Large telescopes also introduce mechanical stability problems, unless mounted on permanent supports or tripods of exceptional sturdiness.

Better definition is available with larger telescopes when they are used for direct viewing, as shown in Fig. 8. *This requires a safe solar filter*, mounted over the telescope aperture. Never look at the sun directly, with the naked eye, binoculars or any telescope, except through a solar filter known to be safe. Such a filter should pass no more than 0.01 percent of the impinging light, and it should be reasonably uniform across the whole solar spectrum. Do not use eyepiece filters. Be sure

### WIAW Propagation Bulletins

For those who may not have time or interest to do their own predicting, short-term predictions of propagation conditions are carried daily on the Headquarters station, WIAW. (See schedule in every issue of *QST*.) These bulletins are designed to supplement the propagation charts given in *QST*, and to provide the best available information on the conditions to be expected in the next few days after the bulletin date. Normally the text is chang-

ed weekly, but new information is included whenever it becomes available.

The bulletin contents are made up from a combination of daily monitoring and charting of all WWV information, observation of the sun with advanced equipment, and frequent monitoring of the amateur hf and vhf bands. Interesting propagation events of recent days are reported, in order to put new information in proper perspective.

that the aperture filter is mounted firmly, so that it cannot come off while the telescope is in use. *Never* look at the sun without it.

Visual acuity is very important. Even people who think they have satisfactory eyesight, with or without glasses, may find that keener eyes will see much solar surface detail that they miss. Have a younger helper, if you are middle aged or older.

### Interpreting What You See and Hear

In viewing the sun with a celestial telescope equipped with a star diagonal and a vertical eyepiece, one sees the solar disk with the east limb on the right and the west limb on the left. This is the opposite of the view obtained with the setup of Fig. 2, but is more natural since it simulates a map. Visible solar activity moves across the disk from right to left, on a line parallel with the solar equator. The apparent position of the equator varies with the time of day and the position of the viewer, but it can be determined readily if drawings are made during each observation. Knowing the position of the equator is important in identifying activity as belonging to the old or new cycle, in times of transition. Old-cycle spots move near the equator. New-cycle activity appears some 30° above or below.

In good projection, or with properly safeguarded direct viewing, bright patches may be seen, especially near the east or west limbs. Known as plage, faculae, or flocculi, these patches identify active areas that may or may not include visible spots. When seen on the east limb, they may be advance notice of spots due in another day or two. They serve as warning of propagation changes several days away, and their appearance may coincide with the start of a steady rise in solar flux and in the muf as well. Faculae may identify new activity in which spots will appear four weeks later, or they may be the residue of declining activity that contained spots last time around. They can be a vital part of visual records, and their significance will increase as records accumulate.

In their first or last day on the east or west limb, respectively, sizeable spots or

groups usually show as fine lines on or close to the edge of the image. Some detail will begin to show on the second day of new or recurring activity, and sketches should be made as accurately as possible. Note any changes in additional sketches, marked with date and time. Changes in appearance and growth or decay are significant indicators, becoming more so on consecutive rounds of long-lived activity centers.

Increasing size and number of spots will be reflected in a rise in solar flux on the WWV bulletins, particularly the one for 0000 UTC, and in rising F-layer muf. Sudden large growth, or a major breakup of a large spot or group, may show radio effects at once — a rise in muf and perhaps a considerable increase in noise level. The latter is more obvious when using a directive array that can be aimed at the sun.

The noise burst and visible change will almost certainly be accompanied by particle radiation increase, the radio effects of which will be increased absorption of hf signal energy, and possibly auroral conditions on 28 MHz or the vhf bands, one to four days later. (Rising K-index on WWV, possibly without warning on previous bulletins.)

Slower growth, barely distinguishable from day to day, will be accompanied by rising solar-flux numbers, probably a point or two daily, and a gradual improvement in hf conditions that will last as long as the K-index remains low. A rise in muf will be apparent at such times, and propagation will remain good on all frequencies for several days, barring sudden solar change which is always a possibility.

If, on the first attempt at solar viewing, one sees sizeable spots or groups, it is well to remember that these may represent activity in a declining phase. If so, they may move across the disk with only minor apparent change. Keep watch though — the area could be brought back to active state again by forces not yet fully understood. This is why long-term predictions are doomed to occasional abject failure and why short-term prediction, using all the tools available, is such an exciting and useful pursuit.



# Transmission Lines

Transmission lines, and the theory behind them, play an important role in many phases of radio communication. This is because the basic principles involved can be applied to a wide variety of problems. Types of transmission lines include simple two-conductor configurations such as the familiar coaxial cable and TV parallel-wire line. Such lines are useful from power frequencies to well up into the microwave region and form perhaps the most important class. The waveguide is representative of a second type. Here, the conductor configuration is rather complex and ordinary concepts such as voltage and current tend to become obscure. As a consequence, various parameters are expressed in terms of the electric and magnetic fields associated with the line. Finally, the propagation of electromagnetic energy through space itself is closely related to similar phenomena in wave guides and transmission lines. In fact, the only significant physical difference is that the power density in a wave propagated in space decreases with increasing distance while it is possible to transmit power over long distances with conventional lines with little attenuation. This is because power flow is essentially confined to one dimension in the latter case while the three-dimensional aspect of space does not permit such confinement.

## Transmission Lines and Circuits

A transmission line differs from an ordinary circuit in one very important aspect. Delay effects associated with the finite propagation time of electromagnetic energy are often neglected in network design since the dimensions involved are normally small compared to the wavelength of any frequencies present in the circuit. This is not true in transmission-line considerations. The finite propagation time becomes a factor of paramount importance. This can be illustrated with the aid of Fig. 1. A transmission line separates a source at point g from a load at point a by a distance l. If the line is uniform (same conductor shape at any cross

section along the line), only two parameters are required to express the line properties completely. These are the phase velocity,  $v_p$  and the characteristic impedance,  $Z_0$ . If the line can be considered lossless as well,  $Z_0$  becomes a pure resistance,  $R_0$ .

Assume that a very short burst of power is emitted from the source. This is represented by the vertical line at the left of the series of lines in Fig. 2. As the pulse voltage appears across the load  $Z_a$ , all the energy may be absorbed or part of it may be reflected in much the same manner energy in a wave in water is reflected as the wave hits a steep breakwater or the end of a container. This reflected wave is represented by the second line in the series and the arrow above indicates the direction of travel. As the latter wave reaches the source, the process is again repeated with either all of the energy being absorbed or partially reflected.

The back-and-forth cycle is actually an infinite one but after a few reflections, the intensity of the wave becomes very small. If, instead of a short pulse, a continuous voltage is applied to the terminals of a transmission line, the voltage at any point along the line will consist of a sum of voltages of the composite of waves traveling toward the right and a composite of waves traveling toward the left. The total sum of the waves traveling toward the right is called the *forward wave* or *incident wave* while the one traveling toward the left is called the *reflected wave*. Provided certain conditions concerning  $Z_a$  are met, there will be a net flow of energy from the source to the load, with a fraction of the energy being stored in the "standing" waves on the line. This phenomenon is identical to the case of a coupled resonator with ordinary circuit elements. Sections of transmission line are often used for this purpose, especially in the vhf/uhf region. The duplexer found in many vhf repeaters is a common example.

## Line Factors and Equations

Since transmission lines are usually connected between lumped or discrete

circuitry, it is convenient to be able to express the input impedance of a line in terms of the output or load impedance. A line treated this way is then similar to a filter or matching network with a given load impedance. One caution should be kept in mind in applying such relations and that is the manner in which the source and load are connected to the line can be important. There are always some "parasitic" effects arising from connectors and post-connector circuit configuration that may cause the line to "see" a different impedance than if measurements were made at the load terminals directly. This is indicated by the abrupt change in line dimensions at points a and g in Fig. 1. Even though the short line connecting the generator to the main transmission line (and the one connecting the load to the line) might have the same characteristic

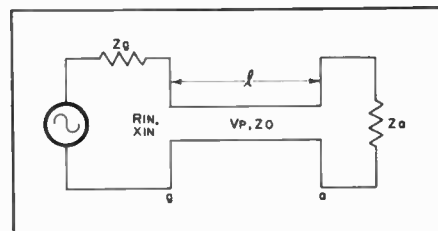


Fig. 1 — Source and load connected by means of a transmission line.

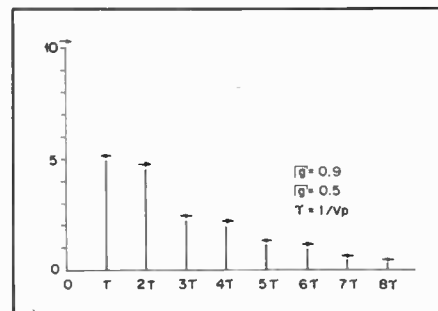


Fig. 2 — Magnitudes of components for forward and reverse traveling waves of a short pulse on a transmission line.



impedance, if the sizes are different a mismatch will still occur. Normally, this effect can be neglected at hf but becomes important as the frequency of operation is extended into the vhf region and above.

In referring to the previous example shown in Fig. 2, the ratio of the voltage in the reflected wave to that of the voltage in the incident wave is defined as the voltage reflection coefficient designated by the Greek letter,  $\Gamma$ , or by  $\rho$ . The relation between the output resistance,  $R_a$ , the output reactance,  $X_a$ , the line impedance,  $Z_o$ , and the magnitude of the reflection coefficient is

$$\Gamma = \sqrt{\frac{(R_a - R_o)^2 + X_a^2}{(R_o + R_a)^2 + X_a^2}}$$

Note that if  $R_z$  is equal to  $R_o$ , and if  $X_a$  is 0 the reflection coefficient is 0, which represents "matched" conditions. All the energy in the incident wave is transferred to the load. In effect, it was as if there were an infinite line of characteristic impedance  $Z_o$  connected at a. On the other hand, if  $R_a$  is 0, regardless of the value of  $X_a$  the reflection coefficient is 1.0. This means all the power is reflected in much the same manner as radiant energy is reflected from a mirror.

If there are no reflections from the load, the voltage distribution along the line is constant or "flat" while if reflections exist, a standing-wave pattern will result. The ratio of the maximum voltage on the line to the minimum value (provided the line is longer than a quarter wavelength) is defined as the voltage standing-wave ratio (VSWR). The VSWR is related to the reflection coefficient by

$$VSWR = \frac{1 + \Gamma}{1 - \Gamma}$$

This latter definition is a more general one, valid for any line length. Quite often, the actual load impedance is unknown. An alternate way of expressing the reflection coefficient is

$$\Gamma = \sqrt{\frac{P_r}{P_f}}$$

where

$P_r$  = the power in the reflected wave and  
 $P_f$  = the power in the forward wave.

The parameters are relatively easy to measure with power meters available commercially or with homemade designs. However, it is obvious there can be no other power sources at the load if the foregoing definition is to hold. For instance, the reflection coefficient of the generator in the example shown in Fig. 2 is 0.9. This value could have been obtained by substituting the generator resistance and reactance into a previous formula for reflection coefficient, but not by measurement if the source were activated.

Fortunately, it is possible to determine the input resistance and reactance of a terminated line if the load resistance and reactance are known, along with the line length and characteristic impedance. (With actual lines, the physical length must be divided by the velocity factor of the cable which gives the value of  $l$  in the following formula.) The equations are

$$r_{in} = \frac{r_a(1 + \tan^2 \beta l)}{(1 - x_a \tan \beta l)^2 + (r_a \tan \beta l)^2}$$

$$x_{in} = \frac{x_a(1 - \tan^2 \beta l) + (1 - r_a^2 - x_a^2) \tan \beta l}{(1 - x_a \tan \beta l)^2 + (r_a \tan \beta l)^2}$$

for a 1-ohm line. Equations are often "normalized" this way in order to make universal tables or plots that cover a wide range of values. If characteristic impedances ( $Z_o$ ) other than 1.0 are to be used, the following set of conversions apply where  $R_a$  and  $X_a$  are the load resistance and reactance and  $R_{in}$  and  $X_{in}$  represent the resistance and reactance at the input end of the line.

$$r_a = \frac{R_a}{Z_o} \quad R_{in} = Z_o r_{in}$$

$$x_a = \frac{X_a}{Z_o} \quad X_{in} = Z_o x_{in}$$

In order to determine the value of the tangent function, either the line length in meters or feet, along with the frequency in MHz, can be substituted into the following expressions:

$$\beta l (\text{degrees}) = 1.2 f_{(\text{MHz})} \times l_{(\text{meters})}$$

$$\beta l (\text{degrees}) = 0.367 f_{(\text{MHz})} \times l_{(\text{feet})}$$

Since the foregoing transmission-line equations are somewhat awkward to work with, various plots have been devised that permit a graphical solution. However, with modern programmable calculators, even those in a moderate price class, it takes approximately four seconds to solve both equations. The plots shown in Fig. 3A and Fig. 3B were computed in this manner. The curves are for  $r_{in}$  and  $x_{in}$  for various values of  $r_a$  ( $x_a$  equal to 0) and line length in degrees. Note that 90 degrees appears to be a "critical" value and represents a line length of a quarter wavelength. As this value is approached, the transmission-line equations can be approximated by the formulas:

$$r_{in} \approx \frac{r_a}{r_a^2 + x_a^2}$$

$$x_{in} = \frac{-x_a}{r_a^2 + x_a^2}$$

If  $x_a$  is zero, the formula for a quarter-wavelength transformer is obtained which is

$$R_{in} = Z_o^2 / R_a$$

Quite often, it is mistakenly assumed that power reflected from a load represents power "lost" in some way. This is only true if there is considerable loss in the line itself and the power is dissipated on the way back to the source. On the other hand, the quarter-wavelength transformer is an example where reflections on a lossless line can actually be used to advantage in matching a load impedance that is different from the source impedance.

If the terminating resistance is zero, the input resistance is also zero. In effect, the line and load act as a pure reactance which is given by the formula:

$$x_{in} = \frac{x_a + \tan \beta l}{1 - x_a \tan \beta l}$$

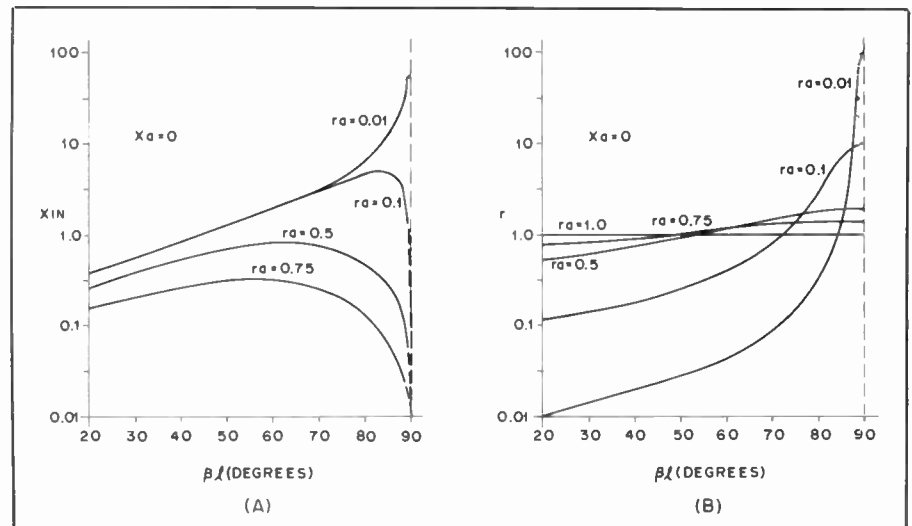


Fig. 3 — Normalized input reactance and resistance vs. line length for various values of  $r_a$  ( $x_a = 0$ ).

The special cases in which the terminating reactance is either zero or infinity are given by the respective formulas

$$x_{in} = \tan \beta l$$

$$x_{in} = \cot \beta l$$

A short length of line with a short circuit as a terminating load appears as an inductor while an open-circuited line appears as a capacitance.

### Matching the Antenna to the Line

The load for a transmission line may be any device capable of dissipating rf power. When lines are used for transmitting applications the most common type of load is an antenna. When a transmission line is connected between an antenna and a receiver, the receiver input circuit (not the antenna) is the load, because the power taken from a passing wave is delivered to the receiver.

Whatever the application, the conditions existing at the load, and *only* the load, determine the standing-wave ratio on the line. If the load is purely resistive and equal in value to the characteristic impedance of the line, there will be no standing waves. In case the load is not purely resistive, and/or is not equal to the line  $Z_0$ , there will be standing waves. No adjustments that can be made at the input end of the line can change the SWR, nor is it affected by changing the line length.

Only in a few special cases is the load inherently of the proper value to match a practicable transmission line. In all other cases it is necessary either to operate with a mismatch and accept the SWR that results, or else to take steps to bring about a proper match between the line and load by means of transformers or similar devices. Impedance-matching transformers may take a variety of physical forms, depending on the circumstances.

Note that it is essential, if the SWR is to be made as low as possible, that the load at the point of connection to the transmission line be purely resistive. In general, this requires that the load be tuned to resonance. If the load itself is not resonant at the operating frequency the tuning sometimes can be accomplished in the matching system.

### The Antenna as a Load

Every antenna system, no matter what its physical form, will have a definite value of impedance at the point where the line is to be connected. The problem is to transform this *antenna input impedance* to the proper value to match the line. In this respect there is no one "best" type of line for a particular antenna system, because it is possible to transform impedances in any desired ratio. Consequently, any type of line may be used with any type of antenna. There are frequently reasons other than impedance matching that dictate the use of one type of line in preference to

another, such as ease of installation, inherent loss in the line, and so on, but these are not considered in this section.

Although the input impedance of an antenna system is seldom known very accurately, it is often possible to make a reasonably close estimate of its value.

Matching circuits can be built using ordinary coils and capacitors, but are not used very extensively because they must be supported at the antenna and must be weatherproofed. The systems to be described use *linear transformers*.

### The Quarter-Wave Transformer or "Q" Section

As mentioned previously, a quarter-wave transmission line may be used as an impedance transformer. Knowing the antenna impedance and the characteristic impedance of the transmission line to be matched, the required characteristic impedance of a matching section such as is shown in Fig. 4 is

$$Z = \sqrt{Z_1 Z_0}$$

where  $Z_1$  = antenna impedance  
 $Z_0$  = characteristic impedance of the line to which it is to be matched.

Example: To match a 600-ohm line to an antenna presenting a 72-ohm load, the quarter-wave matching section would require a characteristic impedance of

$$\sqrt{72 \times 600} = \sqrt{43,200} = 208 \text{ ohms}$$

The spacing between conductors and the conductor size determines the characteristic impedance of the transmission line. As an example, for the 208 ohm transmission line required above, the line could be made from 1/2-inch (13-mm) diameter tubing spaced 1.5 inches (38-mm) between conductors.

The length of the quarter-wave matching section may be calculated from

$$\text{Length (feet)} = \frac{246V}{f}$$

$$\text{Length (meters)} = \frac{75V}{f}$$

where  $V$  = velocity factor  
 $f$  = frequency in MHz

Example: A quarter-wave transformer of RG-11/U is to be used at 28.7 MHz. From table 6 of chapter 21,  $V = 0.66$ .

$$\text{Length} = \frac{246 \times 0.66}{28.7} = 5.65 \text{ feet}$$

$$= 5 \text{ feet } 8 \text{ inches (1.72m)}$$

The antenna must be resonant at the operating frequency. Setting the antenna length by formula is amply accurate with single-wire antennas, but in other systems, particularly close-spaced arrays, the antenna should be adjusted to resonance before the matching section is connected.

When the antenna input impedance is not

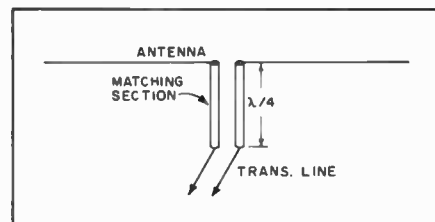


Fig. 4 — "Q" matching section, a quarter-wave impedance transformer.

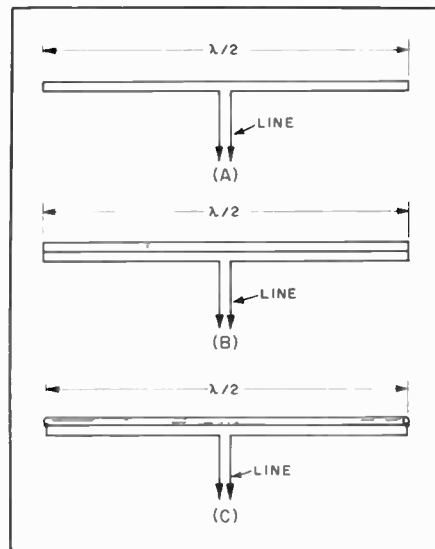


Fig. 5 — The folded dipole, a method for using the antenna element itself to provide an impedance transformation.

known accurately, it is advisable to construct the matching section so that the spacing between conductors can be changed. The spacing then may be adjusted to give the lowest possible SWR on the transmission line.

### Folded Dipoles

A half-wave antenna element can be made to match various line impedances if it is split into two or more parallel conductors with the transmission line attached at the center of only one of them. Various forms of such "folded dipoles" are shown in Fig. 5. Currents in all conductors are in phase in a folded dipole, and since the conductor spacing is small the folded dipole is equivalent in radiating properties to an ordinary single-conductor dipole. However, the current flowing into the input terminals of the antenna from the line is the current in one conductor only, and the entire power from the line is delivered at this value of current. This is equivalent to saying that the input impedance of the antenna has been raised by splitting it up into two or more conductors.

The ratio by which the input impedance of the antenna is stepped up depends not only on the number of conductors in the folded dipole but also on their relative diameters, since the distribution of cur-

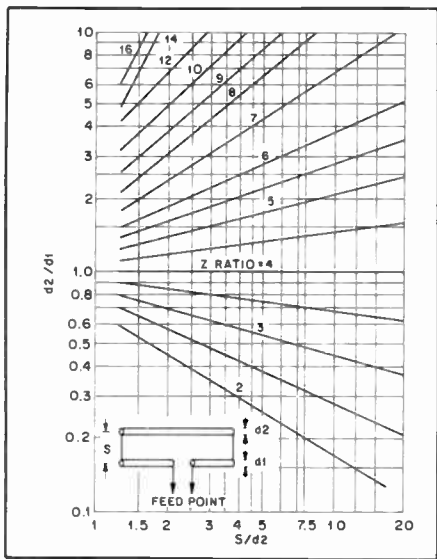


Fig. 6 — Impedance transformation ratio, two-conductor folded dipole. The dimensions  $d_1$ ,  $d_2$  and  $s$  are shown on the inset drawing. Curves show the ratio of the impedance (resistive) seen by the transmission line to the radiation resistance of the resonant antenna system.

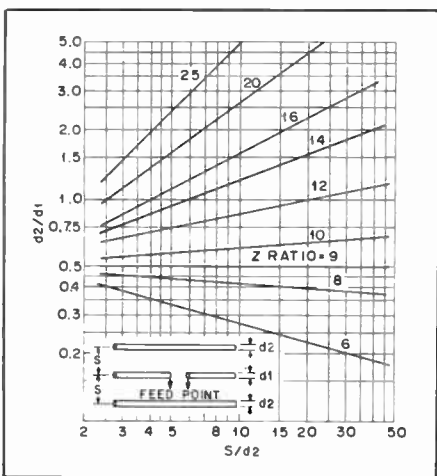


Fig. 7 — Impedance transformation ratio, three-conductor folded dipole. The dimensions  $d_1$ ,  $d_2$  and  $s$  are shown on the inset drawing. Curves show the ratio of the impedance (resistive) seen by the transmission line to the radiation resistance of the resonant antenna system.

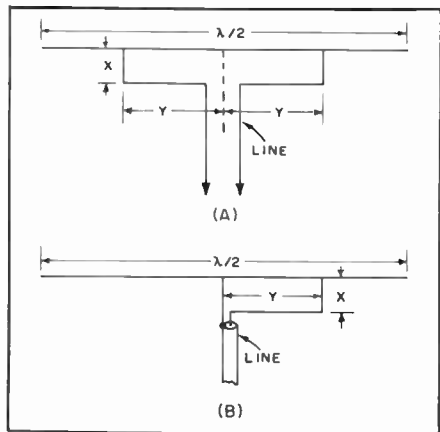


Fig. 8 — The "T" match and "gamma" match.

rent between conductors is a function of their diameters. (When one conductor is larger than the other, as in Fig. 5, the larger one carries the greater current.) The ratio also depends, in general, on the spacing between the conductors, as shown by the graphs of Figs. 6 and 7. An important special case is the two-conductor dipole with conductors of equal diameter; as a simple antenna, not a part of a directive array, it has an input impedance close enough to 300 ohms to afford a good match to 300-ohm twin-lead.

The required ratio of conductor diameters to give a desired impedance ratio using two conductors may be obtained from Fig. 6. Similar information for a three-conductor dipole is given in Fig. 7. This graph applies if all three conductors are in the same plane. The two conductors not connected to the transmission line must be equally spaced from the fed conductor, and must have equal diameters. The fed conductor may have a different diameter, however. The unequal-conductor method has been found particularly useful in matching to low-impedance antennas such as directive arrays using close-spaced parasitic elements.

The length of the antenna element should be such as to be approximately self-resonant at the median operating frequency. The length is usually not highly critical, because a folded dipole tends to have the characteristics of a "thick" antenna and thus has a relatively broad frequency-response curve.

### "T" and "Gamma Matching Sections"

The method of matching shown in Fig. 8A is based on the fact that the impedance between any two points along a resonant antenna is resistive, and has a value which depends on the spacing between the two points. It is therefore possible to choose a pair of points between which the impedance will have the right value to match a transmission line. In practice, the line cannot be connected directly at these points because the distance between them is much greater than the conductor spacing of a practical transmission line. The T arrangement in Fig. 8A overcomes this difficulty by using a second conductor paralleling the antenna to form a matching section to which the line may be connected.

The T is particularly suited to use with a parallel-conductor line, in which case the two points along the antenna should be equidistant from the center so that electrical balance is maintained. The operation of this system is somewhat complex. Each T conductor ( $y$  in the drawing) forms with the antenna conductor opposite it a short section of transmission line. Each of these transmission-line sections can be considered to be terminated in the impedance that exists at the point of connection to the antenna. Thus the part of the antenna between the

two points carries a transmission-line current in addition to the normal antenna current. The two transmission-line matching sections are in series, as seen by the main transmission line.

If the antenna by itself is resonant at the operating frequency, its impedance will be purely resistive. In such case the matching-section lines are terminated in a resistive load. However, since these sections are shorter than a quarter wavelength, their input impedance — i.e., the impedance seen by the main transmission line looking into the matching-section terminals — will be reactive as well as resistive. This prevents a perfect match to the main transmission line, since its load must be a pure resistance for perfect matching. The reactive component of the input impedance must be tuned out before a proper match can be secured.

One way to do this is to detune the antenna just enough, by changing its length, to cause reactance of the opposite kind to be reflected to the input terminals of the matching section, thus cancelling the reactance introduced by the latter. Another method, which is considerably easier to adjust, is to insert a variable capacitor in series with the matching section where it connects to the transmission line, as shown in chapter 20. The capacitor must be protected from the weather.

The method of adjustment commonly used is to cut the antenna for approximate resonance and then make the spacing  $x$  some value that is convenient constructionally. The distance  $y$  is then adjusted, while maintaining symmetry with respect to the center, until the SWR on the transmission line is as low as possible. If the SWR is not below 2:1 after this adjustment, the antenna length should be changed slightly and the matching section taps adjusted again. This procedure may be continued until the SWR is as close to 1:1 as possible.

When the series-capacitor method of reactance compensation is used, the antenna should be the proper length to be resonant at the operating frequency. Trial positions of the matching-section taps are then taken, each time adjusting the capacitor for minimum SWR, until the standing waves on the transmission line are brought down to the lowest possible value.

The unbalanced ("gamma") arrangement in Fig. 8B is similar in principle to the T, but is adapted for use with single coax line. The method of adjustment is the same.

### Balancing Devices

An antenna with open ends, of which the half-wave type is an example, is inherently a balanced radiator. When opened at the center and fed with a parallel-conductor line, this balance is maintained throughout the system, so long as the causes of unbalance discussed



in this chapter are avoided.

If the antenna is fed at the center through a coaxial line, as indicated in Fig. 9A, this balance is upset because one side of the radiator is connected to the shield while the other is connected to the inner conductor. On the side connected to the shield, a current can flow down over the *outside* of the coaxial line. The fields thus set up cannot be canceled by the fields from the inner conductor because the fields *inside* the line cannot escape through the shielding afforded by the outer conductor. Hence these "antenna" currents flowing on the outside of the line will be responsible for radiation.

### Linear Baluns

Line radiation can be prevented by a number of devices whose purpose is to detune or decouple the line for "antenna" currents and thus greatly reduce their amplitude. Such devices generally are known as *baluns* (a contraction for "balanced to unbalanced"). Fig. 9B shows one such arrangement, known as a *bazooka*, which uses a sleeve over the transmission line to form, with the outside of the outer line conductor, a shorted quarter-wave line section. As described earlier in this chapter, the impedance looking into the open end of such a section is very high, so that the end of the outer conductor of the coaxial line is effectively isolated from the part of the line below the sleeve. The length is an

electrical quarter wave, and may be physically shorter if the insulation between the sleeve and the line is other than air. The bazooka has no effect on the impedance relationships between the antenna and the coaxial line.

Another method that gives an equivalent effect is shown at C. Since the voltages at the antenna terminals are equal and opposite (with reference to ground), equal and opposite currents flow on the surfaces of the line and second conductor. Beyond the shorting point, in the direction of the transmitter, these currents combine to cancel out. The balancing section "looks like" an open circuit to the antenna, since it is a quarter-wave parallel-conductor line shorted at the far end, and thus has no effect on the normal antenna operation. However, this is not essential to the line-balancing function of the device, and baluns of this type are sometimes made shorter than a quarter wavelength to provide the shunt inductive reactance required in certain matching systems.

Fig. 9D shows a third balun, in which equal and opposite voltages, balanced to ground, are taken from the inner conductors of the main transmission line and half-wave phasing section. Since the voltages at the balanced end are in series while the voltages at the unbalanced end are in parallel, there is a 4:1 impedance from the balanced to the unbalanced side. This arrangement is

useful for coupling between a 300-ohm balanced line and a 75-ohm coaxial line, for example.

### Other Loads and Balancing Devices

The most important practical load for a transmission line is an antenna which in most cases, will be "balanced" — that is, symmetrically constructed with respect to the feed point. Aside from considerations of matching the actual impedance of the antenna at the feed point to the characteristic impedance of the line (if such matching is attempted) a balanced antenna should be fed through a balanced transmission line in order to preserve symmetry with respect to ground. This will avoid difficulties with unbalanced currents on the line and consequent undesirable radiation from the transmission line itself.

If, as is often the case, the antenna is to be fed through coaxial line, (which is inherently unbalanced) some method should be used for connecting the line to the antenna without upsetting the symmetry of the antenna itself. This requires a circuit that will isolate the balanced load from the unbalanced line while providing efficient power transfer. Devices for doing this are called *baluns*. The types used between the antenna and transmission line are generally linear, consisting of transmission-line sections.

The need for baluns also arises in coupling a transmitter to a balanced transmission line, since the output circuits of most transmitters have one side grounded. (This type of output circuit is desirable for a number of reasons, including TVI reduction.) The most flexible type of balun for this purpose is the inductively coupled matching network described in a subsequent section in this chapter. This combines impedance matching with balanced-to-unbalanced operation, but has the disadvantage that it uses resonant circuits and thus can work over only a limited band of frequencies without readjustment. However, if a fixed impedance ratio in the balun can be tolerated, the coil balun described below can be used without adjustment over a frequency range of about 10:1 — 3 to 30 MHz, for example.

### Coil Baluns

The type of balun known as the "coil balun" is based on the principles of linear-transmission-line balun as shown in the upper drawing of Fig. 10. Two transmission lines of equal length having a characteristic impedance ( $Z_0$ ) are connected in series at one end and in parallel at the other. At the series-connected end the lines are balanced to ground and will match an impedance equal to  $2Z_0$ . At the parallel-connected end the lines will be matched by an impedance equal to  $Z_0/2$ . One side may be connected to ground at the parallel-connected end, provided the

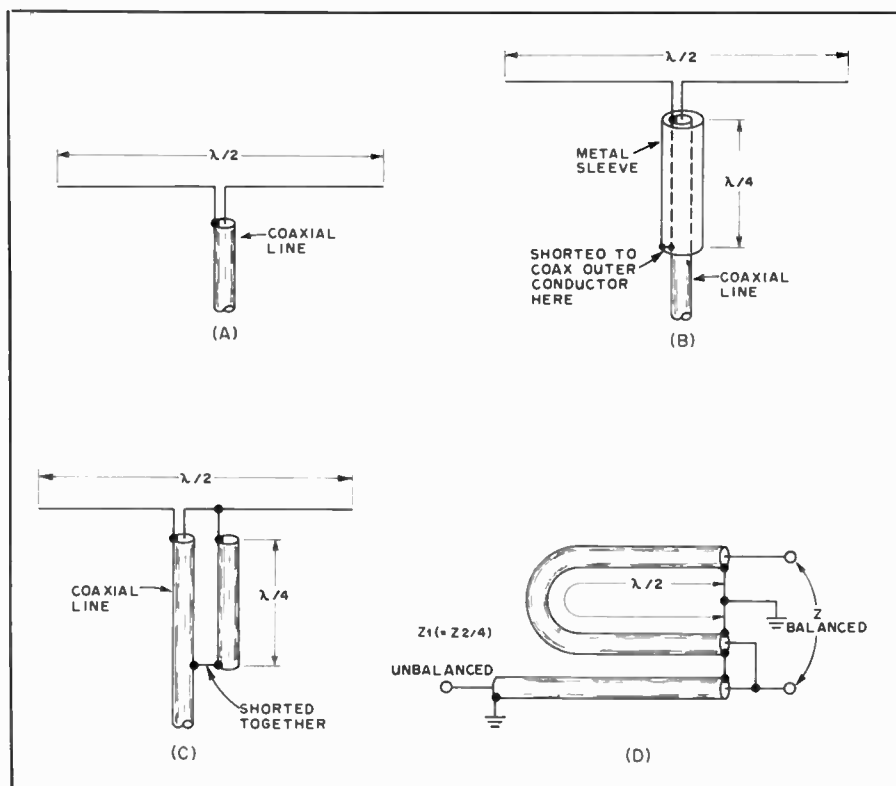


Fig. 9 — Radiator with coaxial feed (A) and methods of preventing unbalanced currents from flowing on the outside of the transmission line (B and C). The half-wave phasing section shown at D is used for coupling between an unbalanced and a balanced circuit when a 4:1 impedance ratio is desired or can be accepted.

two lines have a length such that, considering each line as a single wire, the balanced end is effectively decoupled from the parallel-connected end. This requires a length that is an odd multiple of 1/4 wavelength.

A definite line length is required only for decoupling purposes, and so long as there is adequate decoupling the system will act as a 4:1 impedance transformer regardless of line length. If each line is wound into a coil, as in the lower drawing, the inductances so formed will act as choke coils and will tend to isolate the series-connected end from any ground connection that may be placed on the parallel-connected end. Balun coils made in this way will operate over a wide frequency range, since the choke inductance is not critical. The lower frequency limit is where the coils are no longer effective in isolating one end from the other; the length of line in each coil should be about equal to a quarter wave-length at the lowest frequency to be used.

The principal application of such coils is in going from a 300-ohm balanced line to a 75-ohm coaxial line. This requires that the  $Z_0$  of the lines forming the coils be 150 ohms.

A balun of this type is simply a fixed-ratio transformer, when matched. It cannot compensate for inaccurate matching elsewhere in the system. With a "300-ohm" line on the balanced end, for example, a 75-ohm coax cable will not be matched unless the 300-ohm line actually is terminated in a 300-ohm load.

### Two Broadband Toroidal Baluns

Air-wound balun transformers are somewhat bulky when designed for operation in the 1.8- to 30-MHz range. A more compact broadband transformer can be realized by using toroidal ferrite core material as the foundation for bifilar-wound coil balun transformers. Two such baluns are described here.

In Fig. 11 at A, a 1:1 ratio balanced-to-unbalanced-line transformer is shown. This transformer is useful in converting a 50-ohm balanced line condition to one that is 50 ohms, unbalanced. Similarly, the transformer will work between balanced and unbalanced 75-ohm impedances. A 4:1 ratio transformer is illustrated in Fig. 11 at B. This balun is useful for converting a 200-ohm balanced condition to one that is 50 ohms, unbalanced. In a like manner, the transformer can be used between a balanced 300-ohm point and a 75-ohm unbalanced line. Both balun transformers will handle 1000 watts of rf power and are designed to operate from 1.8 through 60 MHz.

Low-loss high-frequency ferrite core

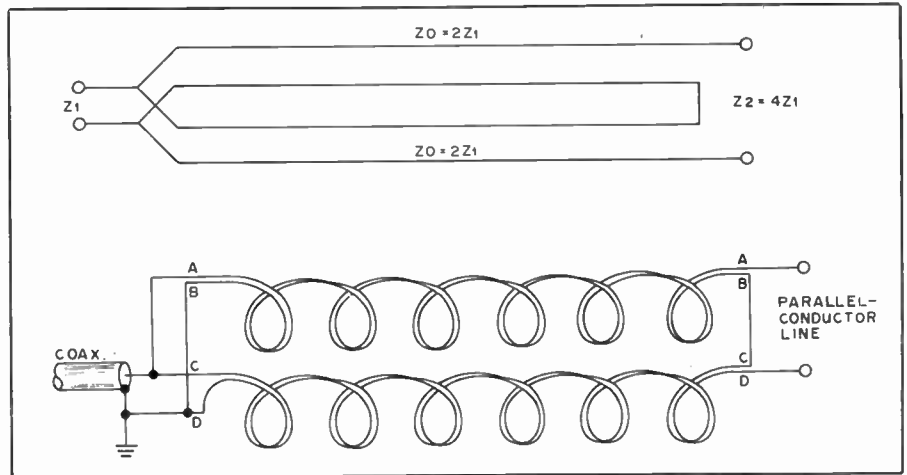


Fig. 10 — Baluns for matching between push-pull and single-ended circuits. The impedance ratio is 4:1 from the push-pull side to the unbalanced side. Coiling the lines (lower drawing) increases the frequency range over which satisfactory operation is obtained.

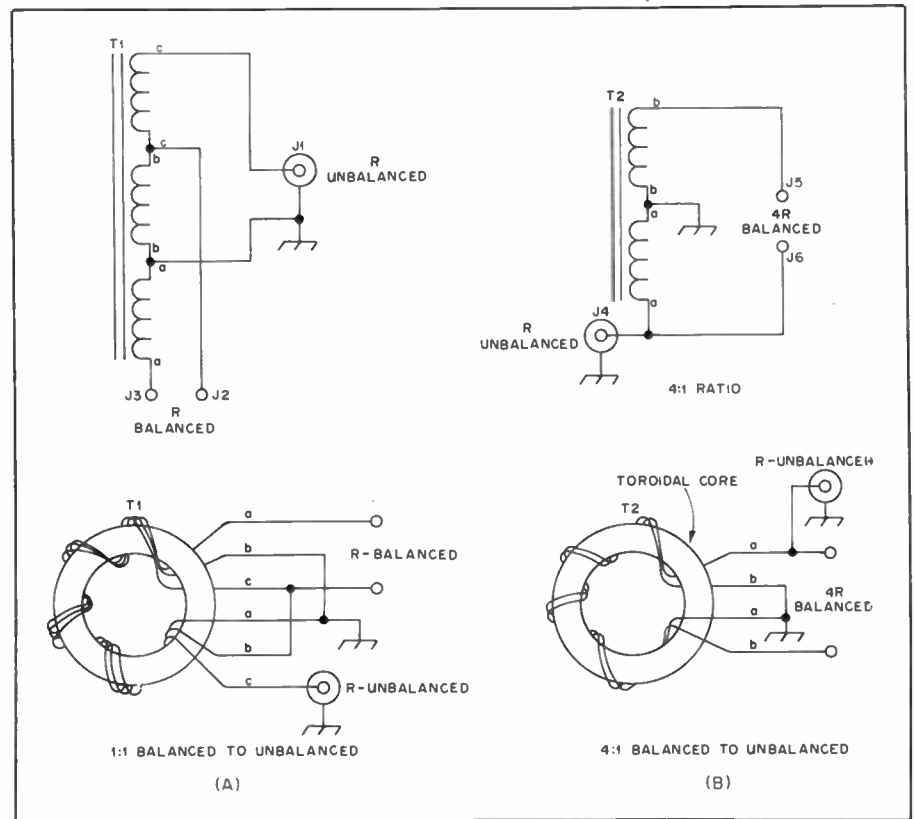


Fig. 11 — Schematic and pictorial representations of the balun transformers. T1 and T2 are wound on CF-123 toroid cores (see footnote 4 and the text). J1 and J4 are SO-239-type coax connectors, or similar. J2, J3, J5, and J6 are steatite feedthrough bushings. The windings are labeled a, b and c to show the relationship between the pictorial and schematic illustrations.

material is used for T1 and T2.<sup>1,2</sup> The cores are made from Q-2 material and cost approximately \$5.50 in single-lot quantity. They are 0.5 inches (13-mm) thick, have an OD of 2.4 inches (61-mm) and the ID is 1.4 inches (36-mm). The permeability rating of the cores is 40. A packaged 1-kilowatt balun kit, with winding instructions for 1:1 or 4:1 impedance transformation ratios, is available, but uses a core of slightly different dimensions.<sup>3</sup>

### Winding Information

The transformer shown in Fig. 11 at A has a trifilar winding consisting of 10 turns of No. 14 formvar-insulated copper wire. A 10-turn bifilar winding of the same type of wire is used for the balun of Fig. 11 at B. If the cores have rough edges, they should be carefully sanded until smooth enough to prevent damage to the

<sup>1</sup>Available in single-lot quantity from Permag Corp., 88-06 Van Wyck Expy, Jamaica, N.Y. 11418.

<sup>2</sup>Toroid cores are also available from Ferroxcube Corp. of America, 5083 Kings Hwy, Saugerties, N.Y. 12477.

<sup>3</sup>Amidon Associates, 12033 Otsego St., North Hollywood, CA 91601.

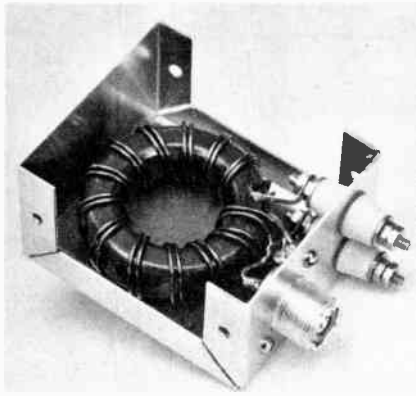


Fig. 12 — Layout of a kilowatt 4:1 toroidal balun transformer. Phenolic insulating board is mounted between the transformer and the Minibox wall to prevent short-circuiting. The board is held in place with epoxy cement. Cement is also used to secure the transformer to the board. For outdoor use, the Minibox cover can be installed, then sealed against the weather by applying epoxy cement along the seams of the box.

wire's Formvar insulation. The windings should be spaced around the entire core as shown in Fig. 12. Insulation can be used between the core material and the windings to increase the power handling capabilities of the core.

### Using the Baluns

For indoor applications, the transformers can be assembled open style, without benefit of a protective enclosure. For outdoor installations, such as at the antenna feed point, the balun should be encapsulated in epoxy resin or mounted in a suitable weatherproof enclosure. A Minibox, sealed against moisture, works nicely for the latter.

### Nonradiating Loads

Typical examples of nonradiating loads for a transmission line are the grid circuit of a power amplifier (considered in the chapter on transmitters), the input circuit of a receiver, and another transmission line. This last case includes the "antenna tuner" — a misnomer because it is actually a device for coupling a transmission line to the transmitter. Because of its importance in amateur installations, the antenna coupler is considered separately in a later part of this chapter.

### Coupling to a Receiver

A good match between an antenna and its transmission line does not guarantee a low standing-wave ratio on the line when the antenna system is used for receiving. The SWR is determined wholly by what the line "sees" at the receiver's antenna-input terminals. For minimum SWR the receiver input circuit must be matched to the line. The rated input impedance of a receiver is a nominal value that varies over a considerable range with frequency. Most hf receivers are sensitive enough

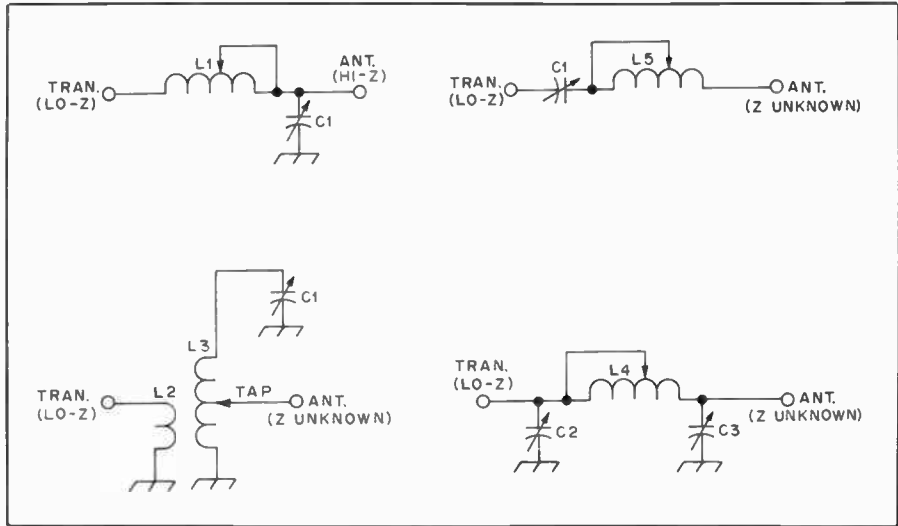


Fig. 13 — Networks for matching a low-Z transmitter output to random-length end-fed wire antennas.

that exact matching is not necessary. The most desirable condition is when the receiver is matched to the  $Z_0$  and the line in turn is matched to the antenna. This transfers maximum power from the antenna to the receiver with the least transmission line loss.

### Coupling to Random-Length Antennas

Several impedance-matching schemes are shown in Fig. 13, permitting random-length wires to be matched to normal low-Z transmitter outputs. The circuit used will depend upon the length of the antenna wire and its impedance at the desired operating frequency. Ordinarily, one of the four methods shown will provide a suitable impedance match to an end-fed random wire, but the configuration will have to be determined experimentally. For operation between 3.5 and 30 MHz, C1 can be a 200-pF type with suitable plate spacing for the power level in use. C2 and C3 should be 500-pF units to allow for flexibility in matching. L1, L4 and L5 should be tapped or rotary inductors with sufficient L for the operating frequency. L3 can be a tapped Miniductor coil with ample turns for the band being used. An SWR bridge should be used as a match indicator.

### Coupling the Transmitter to the Line

The type of coupling system that will be needed to transfer power adequately from the final rf amplifier to the transmission line depends almost entirely on the input impedance of the line. As shown earlier in this chapter, the input impedance is determined by the standing-wave ratio and the line length. The simplest case is that where the line is terminated in its characteristic impedance so that the SWR is 1:1 and the input impedance is equal to the  $Z_0$  of the line, regardless of line length.

Coupling systems that will deliver power into a flat line are readily designed. For all practical purposes the line can be

considered to be flat if the SWR is no greater than about 1.5:1. That is, a coupling system designed to work into a pure resistance equal to the line  $Z_0$  will have enough leeway to take care of the small variations in input impedance that will occur when the line length is changed, if the SWR is higher than 1:1 but no greater than 1.5:1.

Current practice in transmitter design is to provide an output circuit that will work into such a line, usually a coaxial line of 50 to 75 ohms characteristic impedance. The design of such output circuits is discussed in the chapter on high-frequency transmitters. If the input impedance of the transmission line that is to be connected to the transmitter differs appreciably from the impedance value that the transmitter output circuit is designed to operate, an impedance-matching network must be inserted between the transmitter and the line input terminals.

### Impedance-Matching Circuits for Transmission Lines

As shown earlier in this chapter, the input impedance of a line that is operating with a high standing-wave ratio can vary over quite wide limits. The simplest type of circuit that will match such a range of impedances to 50 to 75 ohms is a simple series- or parallel-tuned circuit, approximately resonant at the operating frequency. If the load presented by the line at the operating frequency is low (below a few hundred ohms), a series-tuned circuit should be used. When the load is higher than this, the parallel-tuned circuit is easier to use.

Typical simple circuits for coupling between the transmitter with 50- to 75-ohm coaxial-line output and a balanced transmission line are shown in Fig. 14. The inductor L1 should have a reactance of about 60 ohms when adjustable inductive coupling is used (Figs. 14A and 14B). When a variable series capacitor is used,



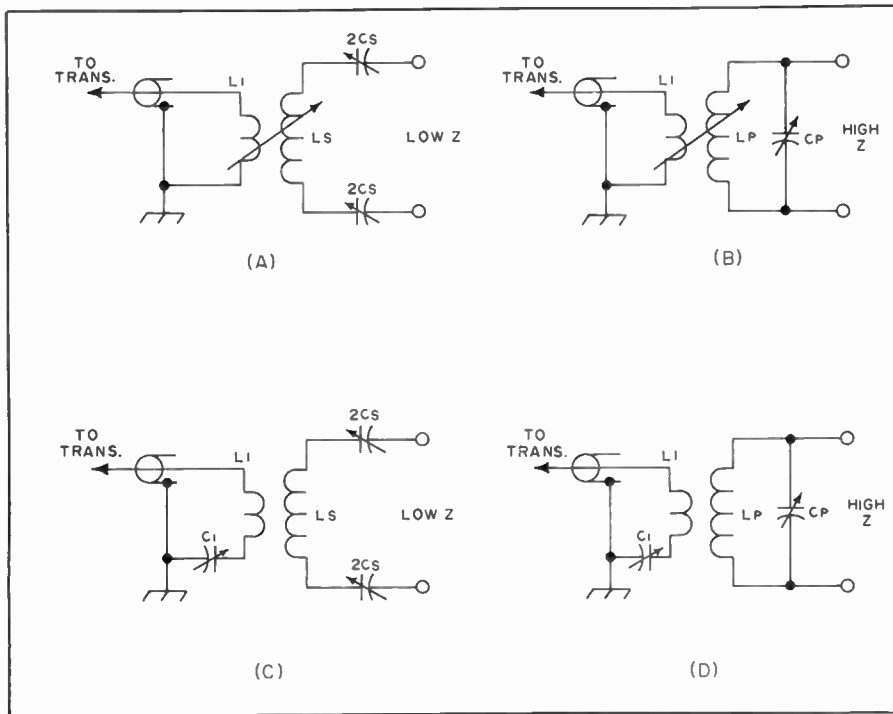


Fig. 14 — Simple circuits for coupling a transmitter to a balanced line that presents a load different than the transmitter output impedance. (A) and (B) respectively are series- and parallel-tuned circuits using variable inductive coupling between coils, and (C) and (D) are similar but use fixed inductive coupling and a variable series capacitor, C1. A series-tuned circuit works well with a low-impedance load; the parallel circuit is better with high-impedance loads (several hundred ohms or more).

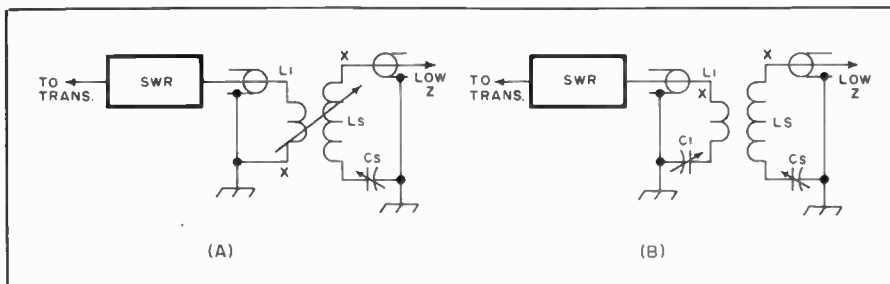


Fig. 15 — Coupling from a transmitter designed for 50- to 75-ohm output to a coaxial line with a 3 or 4:1 SWR is readily accomplished with these circuits. Essential difference between the circuits is (A) adjustable inductive coupling and (B) fixed inductive coupling with variable series capacitor. In either case the circuit can be adjusted to give a 1:1 SWR on the meter in the line to the transmitter. The coil ends marked "x" should be adjacent, for minimum capacitive coupling.

L1 should have a reactance of about 120 ohms. The variable capacitor, C1, should have a reactance at maximum capacitance of about 100 ohms.

On the secondary side, L<sub>s</sub> and C<sub>s</sub> should be capable of being tuned to resonance at about 80 percent of the operating frequency. In the series-tuned circuits, for a given low-impedance load, looser coupling can be used between L1 and L<sub>s</sub> as the L<sub>s</sub>-to-C<sub>s</sub> ratio is increased. In the parallel-tuned circuits, for a given high-impedance load looser coupling can be used between L1 and L<sub>p</sub> as the C<sub>p</sub>-to-L<sub>p</sub> ratio is increased. The constants are not critical; the rules of thumb are mentioned to assist in correcting a marginal condition where sufficient transmitter loading cannot be

obtained.

Coupling to a coaxial line that has a high SWR, and that consequently may present a transmitter with a load it cannot couple to, is done with an unbalanced version of the series-tuned circuit, as shown in Fig. 15. The rule given above for coupling ease and L<sub>s</sub>-to-C<sub>s</sub> ratio applies to these circuits as well.

The most satisfactory way to set up initially any of the circuits of Fig. 14 or 15 is to connect a coaxial SWR bridge in the line to the transmitter, as shown in Fig. 15. The "Monimatch" type of bridge, which can handle the full transmitter power and may be left in the line for continuous monitoring, is excellent for this purpose. However, a simple resistance bridge is

perfectly adequate, requiring only that the transmitter output be reduced to a very low value so that the bridge will not be overloaded. To adjust the circuit, make a trial setting of the coupling (coil spacing in Figs. 14A and B and 15A, C1 setting in others) and adjust C<sub>s</sub> or C<sub>p</sub> for minimum SWR as indicated by the bridge. If the SWR is not close to practically 1:1, readjust the coupling and return C<sub>s</sub> or C<sub>p</sub>, continuing this procedure until the SWR is practically 1:1. The settings may then be logged for future reference.

In the series-tuned circuits of Figs. 14A and 14C, the two capacitors should be set at similar settings. The "2C<sub>s</sub>" indicates that a balanced series-tuned coupler requires twice the capacitance in each of two capacitors as does an unbalanced series-tuned circuit, all other things being equal.

It is possible to use circuits of this type without initially setting them up with an SWR bridge. In such a case it is a matter of cut-and-try until adequate power transfer between the amplifier and main transmission line is secured. However, this method frequently results in a high SWR in the link, with consequent power loss, "hot spots" in the coaxial cable, and tuning that is critical with frequency. The bridge method is simple and gives the optimum operating conditions quickly and with certainty.

#### A Transmatch for Balanced or Unbalanced Lines

Nearly all commercially made transmitters are designed to work into a 50- to 70-ohm load, and they are not usually equipped to handle loads that depart far from these values. However, many antenna systems (the antenna plus its feed line) have complex impedances that make it difficult, if not impossible, to load and tune a transmitter properly. What is required is a coupling method to convert the reactive/resistive load to a non reactive 50-ohm load. This task can be accomplished with a *Transmatch*, a device that consists of one or more LC circuits. It can be adjusted to tune out any load reactance plus, when necessary, transforming the load impedance to 50 or 70 ohms.

As has been discussed earlier in this chapter, losses in transmission lines depend on several factors: The size of the conductors, the spacing between conductors, the dielectric material used in the construction of the feed line, and the frequency at which the line is used. Coaxial lines can be classed as lossy lines when compared to a low-loss line such as open-wire feeders, at least below 100 MHz. Because losses increase as the SWR increases, the type of line used to feed an antenna should be chosen carefully. If the transmission line has very low-loss characteristics, high standing wave ratios can be tolerated with no practical loss of power in the line.

A wire antenna, fed at the center with



Fig. 16 — The universal Transmatch shown here will couple a transmitter to almost any antenna system. If the amateur already has a matching indicator, the Monimatch section of the circuit can be eliminated. The counter dial and knobs are James Millen & Co. components.

open-wire line, is the most efficient multiband antenna devised to date. For all practical purposes, the feed line is lossless, so extremely high SWRs can be tolerated. This should not be construed to mean that coaxial feed lines cannot be used because of a high SWR, but only the very expensive types are really suitable in this application.

The Transmatch shown in Figs. 16 and 17 is designed to handle practically any mismatch that an amateur is likely to encounter. The unit can be used with either open-wire feeders, balanced lines, coaxial lines, or even an end-fed single wire. Frequency range of the unit is from 3 to 30 MHz, accomplished without the use of bandswitching. Basically, the circuit is designed for use with unbalanced lines, such as "coax." For balanced lines, a 1.4 (unbalanced-to-balanced) balun is connected to the output of the Transmatch.

The chassis used for the Transmatch is made of a 16 × 25-inch (406 × 635-mm) sheet of aluminum. When bent to form a U, the completed chassis measures 16 × 13 × 6 inches (406 × 330 × 152-mm). When mounting the variable capacitors, the roller inductor and the balun, allow at least 1/2-inch (13-mm) clearance to the chassis and adjoining components. The capacitors should be mounted on insulated standoff insulators. The balun can be mounted on a cone insulator or piece of Plexiglas.

The balun requires three ferrite cores stacked for 2-kW or two cores for 1-kW power levels. Amidon type T-200-2 cores are used in making the balun.\* Each core should be covered with two layers of 3M no. 27 glass-cloth insulating tape. Next, the cores are stacked and covered with another layer of the tape. The winding consists of 15 bifilar turns of no. 14, Teflon-covered wire. Approximately 20 feet (6.10 m) of wire (two 10-foot — 3.1-m — lengths) are required.

A template for the etched-circuit Monimatch is shown in Fig. 20. Details for making etched circuits are given in the \*Amidon Associates, Palomar Engineers and G. R. Whitehouse (see QST advertisements)

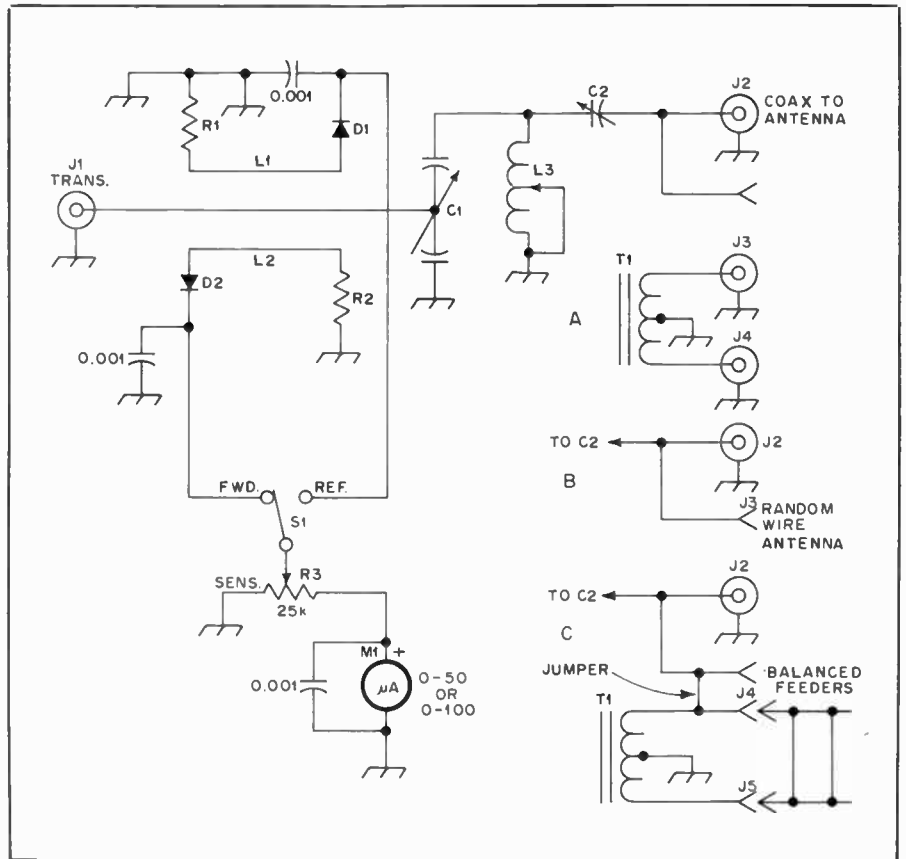


Fig. 17 — Circuit diagram of the Transmatch. The 0.001- $\mu$ F capacitors used are disk ceramic. C1 — Dual-section or air variable, 200 pF per section (E. F. Johnson 154-507 or Millen 16250). C2 — Air variable 350 pF, (E. F. Johnson 154-10 or Millen 16520A). D1, D2 — 1N34A germanium diode. J1, J2 — Coax chassis connector, type SO-239. J3, J4, J5 — Isolantite feedthrough insulators. L1, L2 — See Fig. 20. L3 — Roller inductor, 28  $\mu$ H (E. F. Johnson 229-203). M1 — 50 or 100  $\mu$ A. R1, R2 — 68-ohm, 1/2-watt carbon or composition. R3 — 25-k $\Omega$  control, linear taper. S1 — Spst toggle. T1 — Balun transformer, see text and Fig. 18.

Construction Practices chapter. If the builder desires, a power-type bridge can be substituted. Such a unit is described in the Measurements chapter. In addition to providing standing-wave indications for Transmatch adjustment purposes, the power bridge will accurately measure transmitter output power.

For coax-to-coax feeder matching, the antenna feed line should be connected to J2 of Fig. 17. C1 and C2 should be set at maximum capacitance and power applied to the transmitter. The SWR indicator should be switched to read reflected power. Then, adjust L3 until there is a drop in the reflected reading. C1 and C2 should then be reset, along with L3, until a perfect match is obtained. It will be found that with many antenna systems, several different matching combinations can be obtained. Always use the matching setting that uses the most capacitance from C1 and C2, as maximum C provides the best harmonic attenuation.

End-fed wires should be connected to J3. Use the same adjustment procedures for setting up the Transmatch as outlined above. For balanced feeders, the feed line

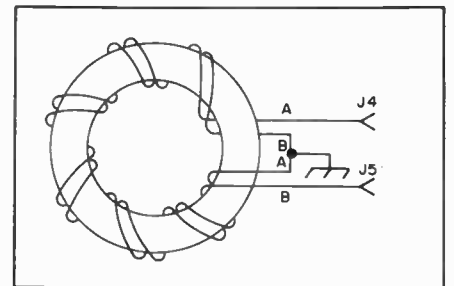


Fig. 18 — Details of the balun bifilar windings. The drawing shows the connections required. In the actual balun, the turns should be close spaced on the inside of the core and spread evenly on the outside.

should be connected to J4 and J5, and a jumper must be connected between J3 and J4 (see Fig. 17 at C).

A slight modification will permit this Transmatch to be used on the 160-meter band. Fixed capacitors, 100 pF each (Centralab type 850S-100N), can be installed across each of the stator sections of C1, providing sufficient C to tune to 1.8 MHz. But, the fixed capacitors must be

**Table 1**

**80- and 40-meter link-coupled matching network.**

Center Section	Each End Section	
Band	(No. turns)	(No. turns)
80 M	12	18
40 M	8	10

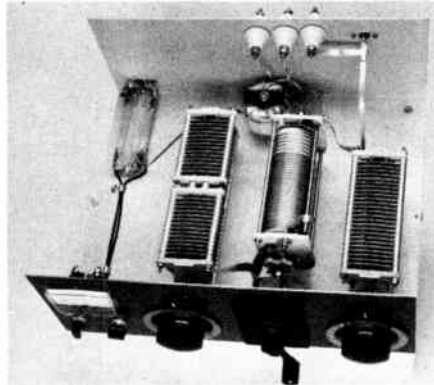


Fig. 19 — Interior view of the Transmatch. The etched-circuit Monimatch is mounted 1/2 inch (13 mm) above the chassis. Both C1 and C2 must be mounted on insulated stand-offs and insulated shaft couplers used between the capacitors and the panel knobs. Likewise, T1 should be installed on an insulated mounting. An isolantite cone is used in the unit shown (the balun could be mounted on a piece of Plexiglas). Feedthrough isolantite insulators, mounted through the rear deck, are used for the antenna connectors.

removed when using the Transmatch on the other hf bands.

**A Link-Coupled Matching Network**

Link coupling offers many advantages over other types of systems where a direct connection between the transmitter and antenna is required. This is particularly true on 80 meters, where commercial broadcast stations often induce sufficient voltage to cause either rectification or front-end overload. Transceivers and receivers that show this tendency can usually be cured by using only magnetic coupling between the transceiver and antenna system. There is no direct connection and better isolation results

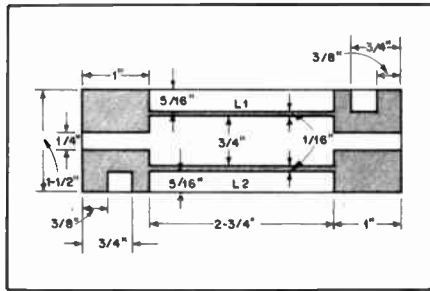


Fig. 20 — Template for the etched-circuit Monimatch, foil side shown, etched portion shaded. (Inches  $\times$  25.4 = mm)

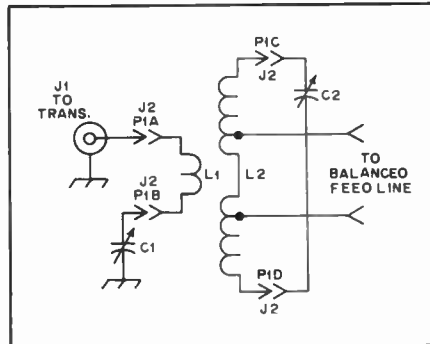


Fig. 21 — Schematic diagram of the 80- and 40-meter link-coupled matching network.  
 C1 — Variable capacitor, 244 pF, 2000 V Johnson 154-0001-001 or equiv.  
 C2 — Variable capacitor, 145 pF, 4500 V Johnson 154-0015-001 or equiv.  
 J1 — Coaxial fitting.  
 J2 — Millen 41305.  
 L1 — Barker & Williamson 3034. See Table 1 for details.  
 L2 — Millen 40305.  
 P1 — Millen 40305.

along with the inherent band-pass characteristics of magnetically coupled tuned circuits.

Although link coupling can be used with either single-ended or balanced antenna systems, its most common application is with balanced feed. The model shown here is designed for 80- and 40-meter operation, since antennas for these bands are the most likely ones to require a matching network.

**Construction**

An additional bonus of this type of matching network is that it is very simple to build and requires only a few hours time. The layout is not critical and the

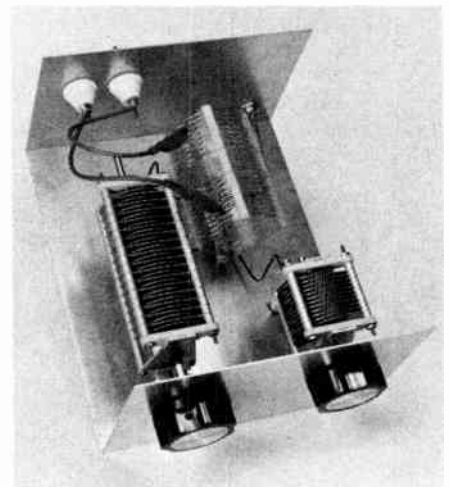


Fig. 22 — Interior view of the link-coupled matching network.

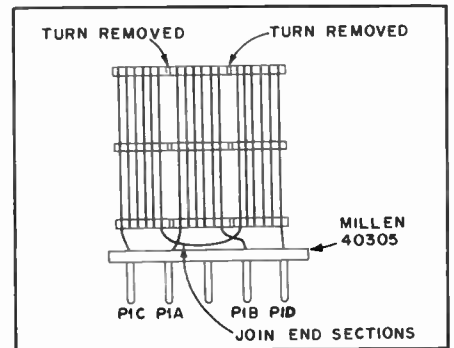


Fig. 23 — Pictorial view of L1 and L2 showing manner in which coils are connected to P1.

general approach can be seen in the photograph. Also, components such as capacitors are not critical and just about any type with ratings similar to those specified in Fig. 21 can be substituted. A homemade hand-wound coil could also be used instead of the one specified for L1.

This matching network is capable of handling up to 2 kW PEP, provided the voltage rating of C2 is sufficient. Also, instead of C1, a variable link might be employed. This would improve the matching capability of the network over one with a fixed coil. But, even a fixed-link coil might be used if one is willing to experiment with determining the correct number of turns for the link.



# Antennas for High Frequency

An antenna system is comprised of all the components which are used between the transmitter or receiver and the actual radiator. Therefore, such items as the antenna proper, transmission line, matching transformers, baluns and Transmatch qualify as parts of an antenna system.

Only the antenna does the radiating in a well-designed system. It is noteworthy that any type of feed line can be utilized with a given antenna, provided a suitable matching device is used to ensure a low standing-wave ratio (SWR) between the feed line and the antenna, and again between the feed line and the transmitter and/or the receiver. Some antennas possess a characteristic impedance at the feed point close to that of certain transmission lines. For example, a half-wavelength center-fed dipole, placed a correct height above ground, will have a feed impedance of approximately 75 ohms. In such a case it is practical to use 75-ohm coaxial or balanced line to feed the antenna. But few amateur half-wavelength dipoles actually exhibit a 75-ohm impedance. This is because at the lower end of the high-frequency spectrum the typical height above ground is rarely more than 1/4 wavelength. The 75-ohm characteristic is most likely to be realized in a practical installation when the horizontal dipole is approximately one-half, three-quarters or one wavelength above ground. At other heights the feed impedance may vary from roughly 58 to 95 ohms (see Fig. 1). This general principle applies to nearly all antennas which are erected horizontally above an earth ground. Furthermore, the precise conductivity of the earth at one location may differ markedly at another site, and this phenomenon has a direct effect on the electrical height of the radiator above ground. A curve (dotted line) is included in Fig. 1 to demonstrate the radiation resistance of a vertical dipole at various feed-point heights above ground.

## The Antenna Choice

Paramount among the factors to consider when selecting an antenna is the matter of available space. Those who live

in urban areas have frequent need to accept a compromise type of antenna for the hf bands because the city lot won't accommodate full-size wire dipoles, end-fed systems or high supporting structures. Other constrictions are imposed by the amount of money available for an antenna system (inclusive of supporting hardware), the number of amateur bands to be worked, and local zoning ordinances. Finally, the operational objective comes into play: To dedicate one's self to DXing, or settle for a general type of operation that will yield short- and long-haul QSOs during periods of good propagation. Because of the foregoing influences, it is impossible to suggest one type of antenna system over another. Perhaps a general rule of thumb might be to erect the biggest and best antenna collection that space and finances will allow. If a modest system is the order of the day, then use whatever is practical and accept a tradeoff between elaboration and performance. Practically any radiator will enable the operator to make good contacts under some conditions of propagation, assuming that the radiator is able to accept power and radiate it at some useful angle respective to earth.

In general, the height of the antenna above ground is the most critical factor at the higher end of the hf spectrum — 20, 15 and 10 meters. This is because the antenna should be clear of conductive objects such as power lines, phone wires, gutters and the like, plus high enough to have a low radiation angle. This is not nearly as important at 160, 80 and 40 meters, but it is still recommended that lower-frequency antennas be well away from conductive objects and as high above ground as possible in the interest of good performance. The exception is a ground-mounted vertical antenna. Ground-plane verticals, however, should be installed as high above ground as possible so that their performance will not be degraded by conductive objects.

## Antenna Polarization

Most hf-band antennas are either vertically or horizontally polarized, al-

though circular polarization is possible, just as it is at vhf and uhf. The polarization is determined by the position of the radiating element or wire with respect to earth. Thus, a radiator that is parallel to earth radiates horizontally, while an antenna at a right angle to earth (vertical) radiates a vertical wave. If a wire antenna is slanted above earth, it radiates waves which are between vertical and horizontal in nature. During line-of-sight communications, maximum signal strength will be realized when the antennas at both ends of the circuit have the same polarity. Cross polarization results in many decibels of signal reduction. However, during propagation via the ionosphere (sky wave) it is not essential to have the same polarization as the station at the opposite end of the circuit. This is because the radiated wave is bent and tumbled considerably during its travel from the atmospheric layer from which it is refracted. At the far end of the communications path the wave may be horizontal, vertical or somewhere in between at a given instant. On multihop transmissions, where the signal is refracted more than once from the atmosphere, and similarly reflected from the earth's surface during its travel (skip), considerable polarization shift will occur. Therefore, the main consideration for a good DX antenna is a low angle of

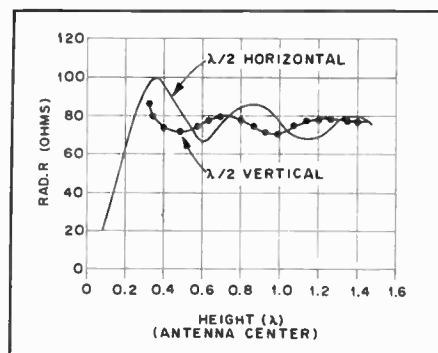


Fig. 1 — Curves showing the radiation resistance of vertical and horizontal half-wavelength dipoles at various heights above ground.

radiation rather than the polarization. It should be said, however, that most DX antennas for hf work are horizontally polarized. The major exception is the ground-plane vertical and phased vertical arrays.

### Impedance

The impedance at a given point in the antenna is determined by the ratio of the voltage to the current at that point. For example, if there were 100 rf volts and 1.4 amperes of current at a specified point in an antenna, the impedance would be approximately 71 ohms. The impedance is significant with regard to matching the feeder to the feed point: Maximum power transfer takes place under a perfectly matched condition. As the mismatch increases so does the reflected power. If the feed line is not too lossy or long, good performance can be had at hf when the standing-wave ratio (SWR) is 3:1 or less. When feeder loss is very low — such as with open-wire transmission line — much higher SWR is not particularly detrimental to performance provided the transmitter is able to lead into the mismatched condition satisfactorily. In this regard, a *Transmatch* (matching network between the transmitter and the feed line) is often employed to “disguise” the mismatch condition, thereby enabling the operator to load the transmitter to its full rated power.

Antenna impedance can be either resistive or complex. This will depend upon whether or not the antenna is resonant at the operating frequency. Many operators believe that a mismatch, however small, is a serious matter, and that their signals won't be heard well even if the SWR is as low as 1.3:1. This unfortunate fallacy has cost many man-hours and dollars among some amateur groups as individuals attempted to obtain a “perfect” match: A perfect match, however ideal the concept may be, is not necessary. The significance of a perfect match becomes more pronounced at vhf and higher, where feeder losses are a major problem.

### Antenna Bandwidth

The bandwidth of an antenna refers generally to the range of frequencies over which the antenna can be used to obtain good performance. The bandwidth is usually referenced to some SWR value, such as “The 2:1 SWR bandwidth is 3.5 to 3.8 MHz.” Some more specific bandwidth terms are used also, such as the *gain bandwidth* and the *front-to-back ratio bandwidth*. The gain bandwidth is significant because the higher the antenna gain the narrower the gain bandwidth will be, for a given gain-bandwidth product.

For the most part, the lower the operating frequency of a given antenna design, the narrower the bandwidth. This

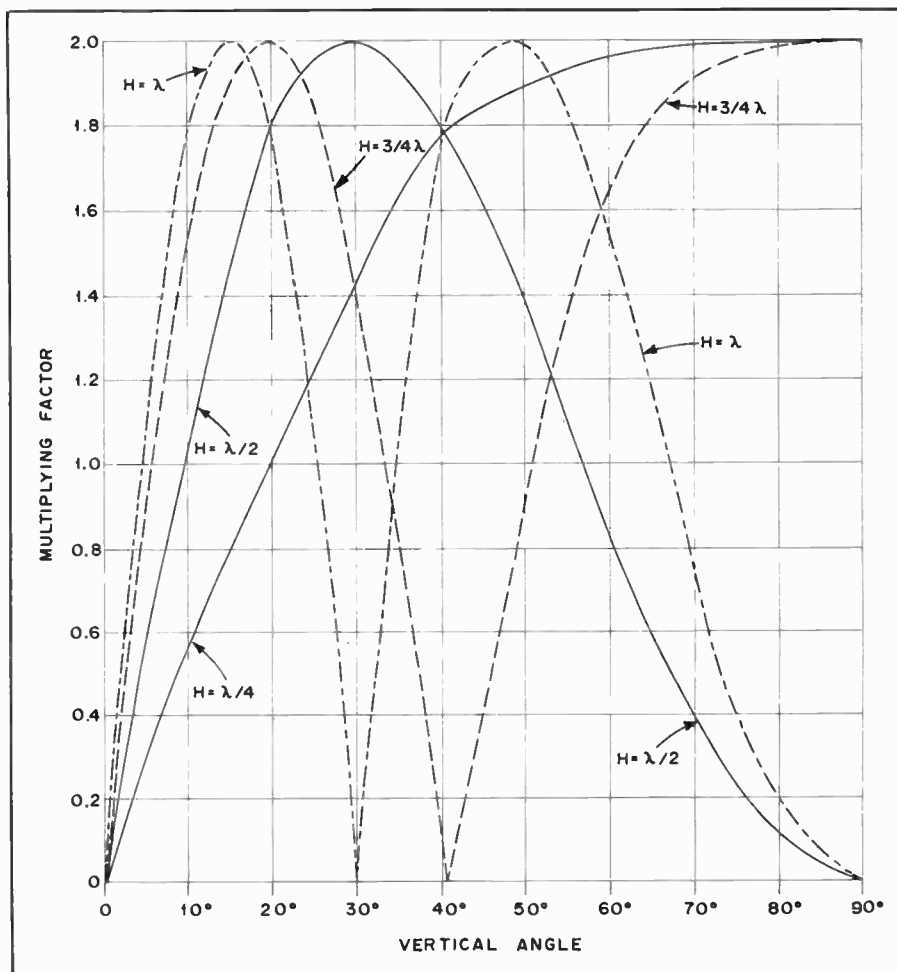


Fig. 2 — Effect of ground on the radiation of horizontal antennas at vertical angles for four antenna heights. These data are based on perfectly conducting ground.

follows the rule where the bandwidth of a resonant circuit doubles as the frequency of operation is increased one octave (doubled) assuming the Q is the same for each case. Therefore, it is often difficult to achieve sufficient bandwidth to cover all of the 160- and 80-meter bands with a dipole antenna cut for each of those bands. The situation can be aided by applying broadbanding techniques, such as fanning the far ends of a dipole to simulate a conical type of dipole.

### Radiation Angle

The vertical angle of maximum radiation is of primary importance, especially at the higher frequencies. It is advantageous, therefore, to erect the antenna at a height that will take advantage of ground reflection in such a way as to reinforce the space radiation at the most desirable angle. Since low angles usually are most effective, this generally means that the antenna should be high — at least one-half wavelength at 14 MHz, and preferably three-quarters or one wavelength, and at least one wavelength, and preferably higher, at 28 MHz. The physical height required for a given height in wavelengths decreases as the frequency

is increased, so that good heights are not impracticable; a half wavelength at 14 MHz is only 35 feet, approximately, while the same height represents a full wavelength at 28 MHz. At 7 MHz and lower frequencies the higher radiation angles are effective, so that again a useful antenna height is not difficult to attain. But, greater height is important at 7 MHz and lower when it is desired to work DX consistently. Heights between 35 and 70 feet are suitable for the upper bands, the higher figures being preferable. It is well to remember that most simple horizontally polarized antennas do not exhibit the directivity they are capable of unless they are one-half wavelength above ground, or greater, at their operating frequency. Therefore, with dipole-type antennas it is not important to choose a favored broadside direction unless the antenna is *at least one-half wavelength above ground*.

### Imperfect Ground

Fig. 2 is based on ground having perfect conductivity, whereas the earth is not a perfect conductor. The principal effect of actual ground is to make the curves inaccurate at the lowest angles; appreciable high-frequency radiation at

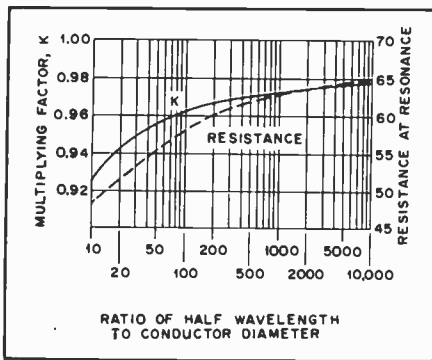


Fig. 3 — Effect of antenna diameter on length for half-wavelength resonance, shown as a multiplying factor, K, to be applied to the free-space, half-wavelength equation (Eq. 1). The effect of conductor diameter on the center impedance is shown also.

angles smaller than a few degrees is practically impossible to obtain over horizontal ground. Above 15 degrees, however, the curves are accurate enough for all practical purposes, and may be taken as indicative of the result to be expected at angles between 5 and 15 degrees.

The effective ground plane — that is, the plane from which ground reflections can be considered to take place — seldom is the actual surface of the ground but is a few feet below it, depending upon the characteristics of the soil.

#### Current and Voltage Distribution

When power is fed to an antenna, the current and voltage vary along its length. The current is maximum (*loop*) at the center and nearly zero (*node*) at the ends, while the opposite is true of the rf voltage. The current does not actually reach zero at the current nodes, because of the end effect; similarly, the voltage is not zero at its node because of the resistance of the antenna, which consists of both the rf resistance of the wire (*ohmic resistance*) and the *radiation resistance*. The radiation resistance is an *equivalent* resistance, a convenient conception to indicate the radiation properties of an antenna. The radiation resistance is the equivalent resistance that would dissipate the power the antenna radiates, with a current flowing in it equal to the antenna current at a current loop (maximum). The ohmic resistance of a half-wavelength antenna is ordinarily small enough, compared with the radiation resistance, to be neglected for all practical purposes.

#### Conductor Size

The impedance of the antenna also depends upon the diameter of the conductor in relation to the wavelength, as indicated in Fig. 3. If the diameter of the conductor is increased, the capacitance per unit length increases and the inductance per unit length decreases. Since the radiation resistance is affected

relatively little, the decreased L/C ratio causes the Q of the antenna to decrease, so that the resonance curve becomes less sharp. Hence, the antenna is capable of working over a wide frequency range. This effect is greater as the diameter is increased, and is a property of some importance at the very high frequencies where the wavelength is small.

#### The Half-Wave Wavelength Antenna

A fundamental form of antenna is a single wire whose length is approximately equal to half the transmitting wavelength. It is the unit from which many more-complex forms of antennas are constructed. It is known as a *dipole antenna*.

The length of a half-wave in free space is

$$\text{Length (ft)} = \frac{492}{f(\text{MHz})} \quad 1a$$

$$\text{Length (m)} = \frac{150}{f(\text{MHz})} \quad 1b$$

The actual length of a half-wavelength antenna will not be exactly equal to the half-wavelength in space, but depends upon the thickness of the conductor in relation to the wavelength as shown in Fig. 3, where K is a factor that must be multiplied by the half wavelength in free space to obtain the resonant antenna length. An additional shortening effect occurs with wire antennas supported by insulators at the ends because of the capacitance added to the system by the insulators (end effect). The following formula is sufficiently accurate for wire antennas for frequencies up to 30 MHz.

Length of half-wave antenna (ft) =

$$\frac{492 \times 0.95}{f(\text{MHz})} = \frac{468}{f(\text{MHz})} \quad 2a$$

$$\frac{150 \times 0.95}{f(\text{MHz})} = \frac{143}{f(\text{MHz})} \quad 2b$$

Example:

A half-wave antenna for 7150 kHz (7.15 MHz) is  $\frac{468}{7.15} = 65.45$  ft, or 65 ft 5 in. (19.9m).

Above 30 MHz the following formulas should be used, particularly for antennas constructed from rod or tubing. K is taken from Fig. 3.

Length of half-wave antenna (ft) =

$$\frac{492 \times K}{f(\text{MHz})} \quad 3a$$

$$\text{Length (in.)} = \frac{5905 \times K}{f(\text{MHz})} \quad 3b$$

$$\text{Length (m)} = \frac{150 \times K}{f(\text{MHz})} \quad 3c$$

$$\text{Length (mm)} = \frac{150,000 \times K}{f(\text{MHz})} \quad 3d$$

Example: Find the length of a half-wavelength antenna at 28.7 MHz, if the antenna is made of 1/2-inch (12.7mm) diameter tubing. At 28.7 MHz, a half-wavelength in space is

$$\frac{492}{28.7} = 17.14 \text{ ft (5.3m)}$$

from Equation 1. The ratio of half wavelength to conductor diameter (changing wavelength to inches) is

$$\frac{(17.14 \times 12)}{0.5} = 411$$

From Fig. 3, K = 0.97 for this ratio. The length of the antenna, from Equation 3a is

$$\frac{(492 \times 0.97)}{28.7} = 16.63 \text{ ft (5.06 m)}$$

or 16 feet 7-1/2 inches. The answer is obtained directly in inches by substitution of Equation 3b.

$$\frac{(5905 \times 0.97)}{28.7} = 199.6 \text{ inches (5.06 m)}$$

The length of a half-wavelength antenna is affected also by the proximity of the dipole ends to nearby conductive and semiconductive objects. In practice, it is often necessary after cutting the antenna to the computed length to do some experimental "pruning" of the wire, shortening it in increments to obtain a low SWR. This can be done by applying rf power through an SWR indicator and observing the reflected-power reading. When the lowest SWR is obtained for the desired part of an amateur band, it does not necessarily follow that the antenna is resonant at that frequency. However, a matched condition will have been secured — the basic objective in preparing an antenna for use.

#### Radiation Characteristics

The classic radiation pattern of a dipole antenna is most intense perpendicular to the wire. A figure-8 pattern (Fig. 4) can be assumed off the broad side of the antenna (bidirectional pattern) if the dipole is 1/2 wavelength or greater above earth and not degraded by nearby conductive objects. This assumption is based also on a symmetrical feed system. In practice, a coaxial feed line will distort this pattern slightly. Minimum horizontal radiation occurs off the ends of the dipole. The foregoing relates to a half-wavelength antenna which is parallel to the earth. However, if the dipole is erected vertically, uniform radiation in all compass directions (a doughnut pattern if it could be viewed from above the antenna) will result.

One of the greatest errors made by some beginners is to assume that a dipole



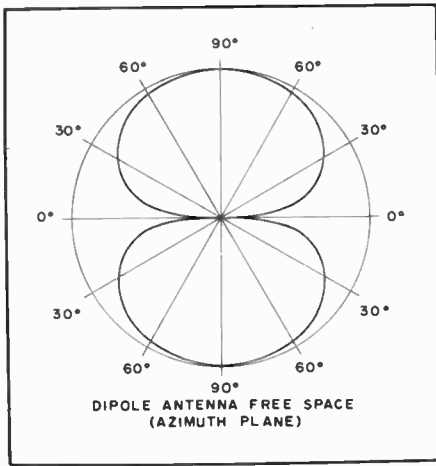


Fig. 4 — Azimuth-plane response of a half-wavelength dipole in free space.

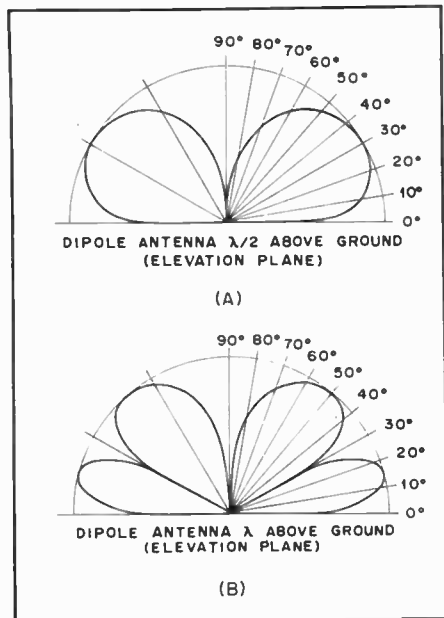


Fig. 5 — Elevation-plane response of a dipole antenna placed 1/2-wavelength above a perfectly conducting ground (A), and the pattern for the same antenna (B) when it is raised to one-wavelength above ground.

antenna will exhibit a "broadside pattern" at any height above ground. As the antenna is brought closer to ground, the radiation pattern deteriorates until the antenna is, for the most part, an omnidirectional radiator of high-angle waves. Many are tempted to use any convenient height, such as 20 or 30 feet above ground for an 80-meter dipole, only to learn that the system is effective in all directions over a relatively short distance (out to 500 or 1000 miles under good conditions). It can be seen from this that height above ground is important for a host of reasons. Fig. 5A and B illustrate clearly the advantage gained from antenna height. The radiation angle of Fig. 5A is roughly 35 degrees, whereas at a height of one wavelength (Fig. 5B) the lobes split and the lower ones provide a good

DX-communications angle of approximately 15 degrees. The higher-angle lobes (50°) are useful for short-haul communications and compare favorably in practice with the lobe angle seen in Fig. 5A. At heights appreciably lower than 1/2 wavelength, the lobe angle becomes higher, and eventually the two lobes converge to create a discrete "ball of radiation" which has a very high-angle nature (poor for long-distance communications).

### Feed Methods for Half-Wavelength Antennas

Most amateur single-wire dipole antennas (half wavelength) have a feed impedance between 50 and 75 ohms, depending on the installation. Therefore, standard coaxial cable is suitable for most installations. The smaller types of cable (RG-58/U and RG-59/U) are satisfactory for power levels up to a few hundred watts if the SWR of the system is low. For high-power stations it is recommended that the larger cables be employed (RG-8/U or RG-11/U). These cables can be connected at the center of the antenna, as shown in Fig. 6. A plastic insulating block is used as a central reinforcement for the cable and the dipole wires. The coax shield braid connects to one leg of the dipole and the center conductor is soldered to the remaining leg. The exposed end of the cable should be sealed against dirt and moisture to prevent degradation of the transmission line.

Symmetrical feed can be achieved by inserting a 1:1 balun transformer at the dipole feed point. If one is not used, it is unlikely that the slight pattern skew resulting from nonsymmetrical feed will be noticed. The effects of unbalanced feed are most significant in beam antennas at vhf and higher. The narrower the beam pattern the more annoying the condition will be.

The characteristic impedance of a dipole antenna can be increased by using a two-wire or folded dipole of the type seen in Fig. 7. This antenna offers a good match to 300-ohm feed line. In fact, the dipole itself can be fashioned from a length of 300-ohm TV ribbon. Alternatively, two pieces of wire can be used to form the equivalent of the TV-line dipole. If this is done it will be necessary to locate insulating spacers every few feet along the length of the dipole to keep the wires spaced apart uniformly and to prevent short circuiting. Open-wire TV "ladder line" is excellent for use in a 300-ohm folded-dipole antenna, both for the radiator and the feed line. Feeder losses with this type of construction will be very low as opposed to molded TV twin-lead.

A dipole antenna can be used as an "all-band" radiator by using tuned open-wire feed line. This principle is seen in Fig. 8A. In this example the dipole is cut to a

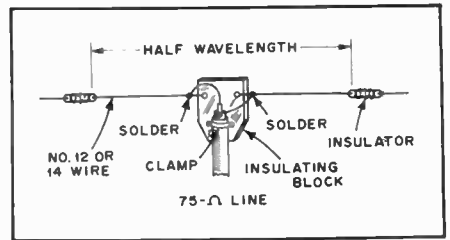


Fig. 6 — Method for affixing the feed line to the center of a dipole antenna. A plastic block is used as a center insulator. The coaxial cable is held in place by means of a metal clamp.

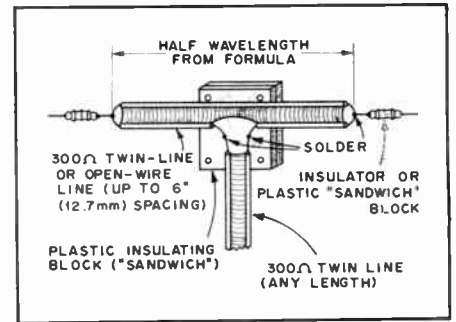


Fig. 7 — Construction details for a folded-dipole antenna. TV ribbon line is used as the dipole and feed line. Two pieces of plastic form an insulator/sandwich at the center to hold the conductor junction secure.

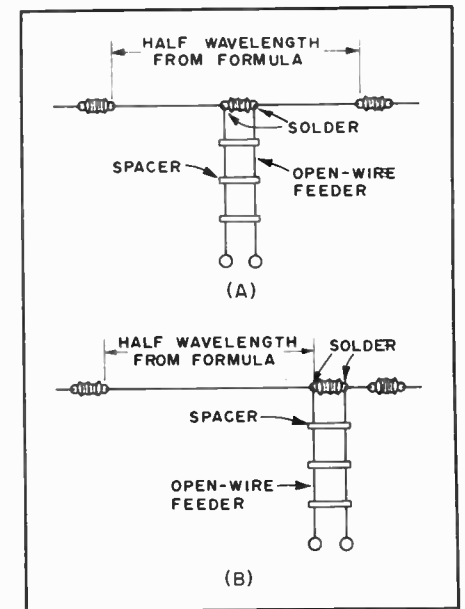


Fig. 8 — Center-fed Zepp antenna (A) and an end-fed Zepp at B.

half wavelength for the lowest desired amateur band. It is operated on its harmonics when used for the other chosen amateur bands. A typical antenna of this type might be utilized from 80 through 10 meters. This style of radiator is known by some amateurs as the "center-fed Zepp." An end-fed version (end-fed Zepp) is shown in Fig. 8 at B. The latter is not quite as desirable as the center-fed version

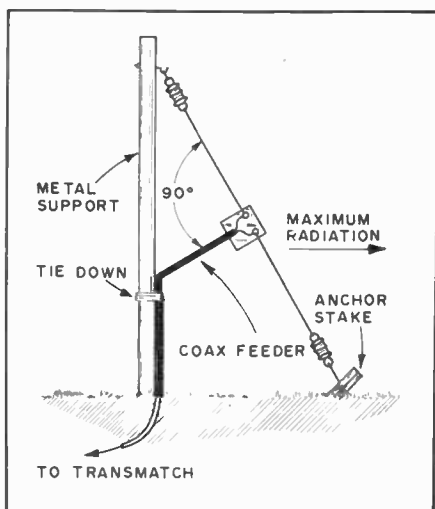


Fig. 9 — Example of a sloping half-wavelength dipole. Maximum directivity is as shown provided a metal mast is used. If a tree or nonconducting mast is employed the pattern will be similar to that of a vertical ground-plane antenna.

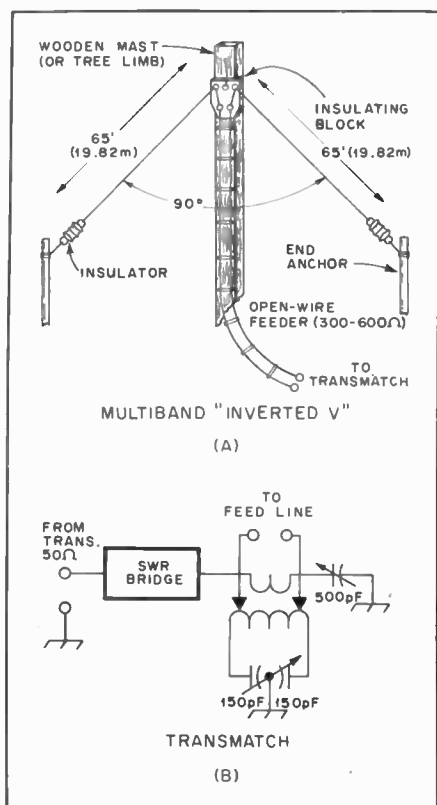


Fig. 10 — Details for an inverted-V dipole which can be used for multiband hf operation (A). A Transmatch is seen at B. It is suitable for matching the antenna to the transmitter over a wide frequency range.

because the feed system is not symmetrical. This can cause feeder radiation and a distortion of the antenna radiation pattern. Both types of Zepp antenna require a matching network (Transmatch) at the transmitter end of the line to convert the feeder impedance to 50 ohms, and to change the balanced condition to an

unbalanced one. Although the feed line may be anything from 200 ohms up to 600 ohms (not critical), losses will be insignificant when open-wire line is used. This is true despite the variations in dipole feedpoint impedance from band to band. The feed impedance will be high at even harmonics and will be low at the lowest operating frequency and at odd harmonics thereof. For example, if the dipole is cut for 40 meters, the feed impedance will be low on 40 and 15 meters, but it will be high at 20 and 10 meters.

When using any dipole antenna it is recommended that the feed line be routed away from the antenna at a right angle for as great a distance as possible. This will help prevent current unbalance in the line caused by rf pickup from the dipole. A right-angle departure of 1/4 wavelength or greater is suggested.

Under some circumstances it may be necessary to experiment with the length of the open-wire feeders when using an all-band Zepp. This is because at some operating frequencies the line may present an "awkward" impedance to the Transmatch, making it impossible to obtain a suitable load condition for the transmitter. This will depend essentially on the capability of the Transmatch being used.

### Dipole Variations

The physical application of dipoles can be varied to obtain radiation properties which differ from those of the more conventional "horizontal dipole." Furthermore, the nature and amount of property at the installation site will often dictate certain departures from the conventional when erecting a dipole.

A sloping dipole can be useful for DX work because of the low angle of radiation which results when it is erected as shown in Fig. 9. The higher the feed point is above ground the lower the radiation angle will be. However, excellent results can be had when the ground end of the antenna is only a few feet above the earth. Maximum directivity is off the sloped front of the antenna, as shown. This characteristic is obtained when the "sloper" is supported by a metal mast or tower: The metal structure tends to act as a reflector, actually providing a slight amount of gain. Some amateurs install four slopers for a given amateur band, spaced equidistantly around the tower. A feed-line switching system is used to obtain directivity in the chosen direction.

Another popular type of dipole antenna is the so-called *inverted V*, or *drooping doublet*. An inverted V is shown in Fig. 10. Newcomers to amateur radio are frequently led to regard this antenna as a panacea, but there is nothing magical or superior about an inverted-V dipole. The main attributes are that it radiates more or less omnidirectionally at typical heights above ground, requires only one supporting structure, and can be used for

single or multiband use. As is true of a horizontal dipole, the higher the inverted V is mounted above ground (feed point), the better it will perform relative to long-distance communications.

Best results seem to be obtained when the enclosed angle of the inverted V is between 90 and 120 degrees. At angles less than 90 degrees considerable cancellation is likely, resulting in reduced antenna performance. At angles greater than 120 degrees, the antenna begins to function as a horizontal dipole.

When the ends of the inverted V are relatively close to the earth, pruning of the dipole legs may be necessary to compensate for the capacitive effect to ground. Thus, if the dipole is cut to length by means of the standard half-wavelength dipole equation, it may be too long as an inverted V. Incremental trimming of each end of the dipole can be done while using an SWR indicator. This will show when the lowest SWR is obtained. A 50-ohm feed line offers a good match for inverted Vs when single-band operation is desired. For multiband use, the inverted V can be fed by means of open-wire line and matched to the transmitter by means of a Transmatch.

The most ideal supporting structure for an inverted V is a wooden or other nonconductive one. This type of support will have the least effect on antenna pattern and performance. When a metal structure is used, the mast of tower is in the field of the antenna and will affect the radiation pattern considerably. The effect is similar to that of the sloping dipole, where maximum directivity is off the sloping front of the antenna (Fig. 9). In the case of an inverted V, two prominent lobes result — off two sides of the tower, as if two sloping dipoles were being used.

Inverted Vs are most effective when used for a single band — the one for which the dipole has been cut. As the operating frequency is increased, the radiation angle deteriorates: Results with DX are often mediocre. Good results can be had when using an inverted V for two-band operation, however. An 80-meter inverted V can be fed with open-wire line and used also on 40 meters as two half waves in phase. Although ARRL tests have not been made to verify the effect, some gain seems to be realized when operating the inverted V on its second harmonic.

Tests performed with an inverted V on 80 meters showed that with an apex height of 60 feet (18 m) and an enclosed angle of 90 degrees, no directivity could be observed during ground-wave signal evaluation. The test stations were 10 miles apart during daylight, and the inverted V was rotated through the various compass headings while the signal level was monitored at the far end of the communications circuit. The supporting structure was a 60-foot (18 m) tower in an open

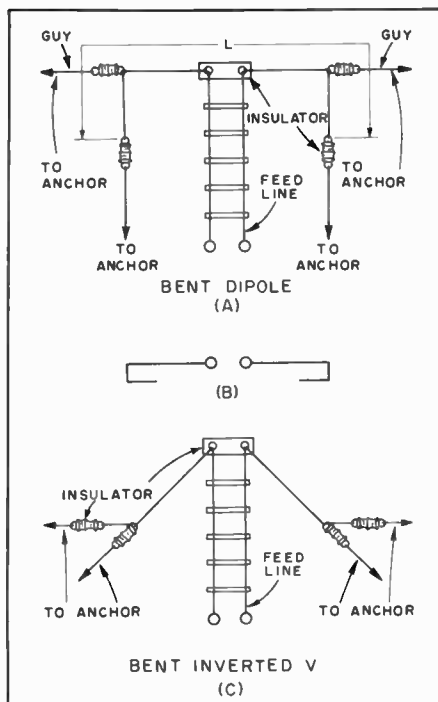


Fig. 11 — When limited space is available for a dipole antenna the ends can be bent downward (A), or back on the radiator as shown at B. The inverted V at C can be erected with the voltage ends bent parallel with the ground when the available supporting structure is not high enough to permit an enclosed angle of approximately 90 degrees.

20-acre field. This verified the omnidirectional property mentioned earlier.

### Bent Dipoles and Trap Dipoles

When there is insufficient real estate to permit the erection of a full-size horizontal or inverted-V dipole, certain compromises are possible in the interest of getting an antenna installed. The voltage ends (far ends) of a dipole can be bent downward toward earth to effect resonance, and the performance will not be reduced markedly. Fig. 11 illustrates the technique under discussion. At A the dipole ends are bent downward and secured to anchors by means of guy line. Some pattern distortion will result from bending the ends. The dipole ends can also be bent back over the wire halves of the antenna, as seen at B in Fig. 11. This causes some signal cancellation (more severe than with the system of Fig. 11A), so it is not a preferred technique.

Fig. 11C demonstrates a bending technique for inverted Vs when the available supporting mast or tree is too short to permit normal installation. The ends of the dipole are guyed off by means of insulators and wires, as shown. Alternatively, but not preferred, is the fold-back method at B in Fig. 11.

All of the shortening systems highlighted in Fig. 11 will have an effect on the overall length of the dipole. Therefore, some cutting and testing will be necessary

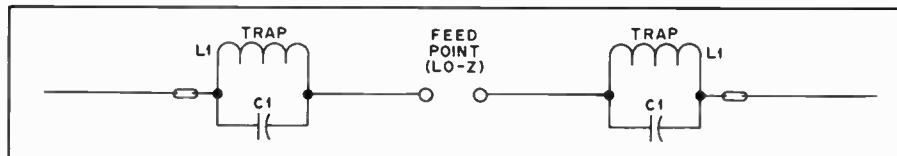


Fig. 12 — Example of a trap dipole antenna. L1 and C1 can be tuned to the desired frequency by means of a dip meter before they are installed in the antenna.

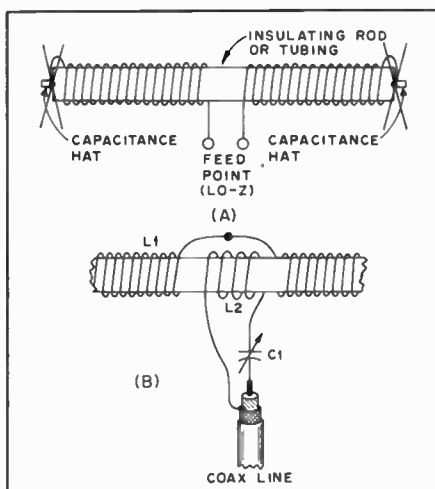


Fig. 13 — A helically wound dipole is illustrated at A. As shown, the radiation resistance will be very low and will require a broadband matching transformer. The coupling method seen at B is more satisfactory for providing a matched condition.

to ensure a low SWR in the favored part of the amateur band for which the antenna is built. If open-wire feeders and a Transmatch are used, the dipole length will not be a critical factor, provided it is close to the length required for a fully extended half-wavelength dipole. Pruning will be required if single-band operation with coaxial feed line is planned.

Trap dipoles offer one solution to multiband operation with a shortened radiator. The concept is seen in Fig. 12. In this example the dipole is structured for two-band use. Assuming in this case that the antenna is made for operation on 80 and 40 meters, the overall radiator (inclusive of the traps) must be resonant at the center of the chosen section of the 80-meter band. The traps add loading to the dipole, so the length from the feed point to the far end of each leg will be somewhat shorter than normal. During 40-meter operation the traps present a high impedance to the signal and "divorce" the wires beyond the traps. Therefore, the wire length from the feed point to each trap is approximately what it would be if the dipole were cut for just 40 meters, with no traps in the line. This principle can be extended for additional bands, using a new set of traps for each additional band. Since there is considerable interaction between the various segments of a multiband trap dipole, considerable experimentation with the

wire lengths between the traps and beyond will be necessary.

The trap capacitors should be high-voltage and-current units (C1). Transmitting mica capacitors offer good performance. Transmitting ceramic capacitors are usable, but change value with extreme changes of temperature. Therefore, they are more suitable for use in regions where the climate is fairly constant throughout the year. The coils (L1) should be of reasonably heavy wire gauge to minimize I<sup>2</sup>R losses. The X<sub>L</sub> and X<sub>C</sub> values in the traps are not critical. Generally the reactance can be on the order of 100 to 300 ohms. The traps are checked for resonance before they are installed in the antenna system. This can be accomplished by means of a dip meter and a calibrated receiver. Weatherproofing should be added to the traps as a measure against detuning and damage from ice snow and dirt.

### Helically-Wound Dipoles

The overall length of a half-wavelength dipole can be reduced considerably by employing helically-wound elements. Fig. 13A shows the general form taken with this type of antenna. A length of insulating rod or tubing (fiberglass or phenolic) is used to contain the wire turns of the dipole. The material should be of high dielectric quality. Varnished bamboo has been used successfully by some in lieu of the more expensive materials. A hardwood pole from a lumber yard can be used after being coated one or more times with exterior spar varnish.

To minimize losses, the wire used should be of the largest diameter practical. The turns can be close wound or spaced apart with little difference in performance. The ends of the helical dipole should contain capacitance hats (disks or wire spokes preferred) of the largest size practical. The hats will lower the Q of the antenna and broaden its response. If no disks are used, extremely high rf voltage can appear at the ends of the antenna. At medium power levels and higher the insulating material can burn when no hats are used. The voltage effect is similar to that of a Tesla coil.

The feed impedance of helical dipoles or verticals is quite low. Therefore, it may be necessary to employ some form of matching network to interface the antenna with 50-ohm coaxial cable. A broadband, variable-impedance transformer is convenient for determining the turns ratio of the final transformer used. The feed



method shown at B of Fig. 13 can be used to secure a matched condition. L2 is wound over L1, or between the two halves of L1, as illustrated. C1 is adjusted for an SWR of 1 at the center of the desired operating range. The bandwidth of this type of antenna is quite narrow. A 40-meter version with an 18-foot (5.5-m) overall length exhibited a 2:1 SWR bandwidth of 50 kHz. The capacitance hats on that model were merely 18-inch (457-mm) lengths (spikes) of no. 8 copperweld wire. Greater bandwidth would result with larger capacitance hats.

To obtain half-wavelength performance it is necessary to wind approximately one wavelength of wire on the tubing. Final pruning can be accomplished while observing an SWR indicator placed in the transmission line. Proximity to nearby conductive objects and the earth will have a significant effect on the resonance of the antenna. Ideally, final adjustments should be made with the antenna situated where it will be during use. Marine spar varnish should be painted on the elements after all tuning is finished. This will protect the antenna from the weather and will lock the turns in place so that detuning will not occur later on.

A reasonably linear current and voltage distribution will result when using a helically wound dipole or vertical. The same is not true of center-, mid- or end-loaded (lumped inductance) dipoles. The efficiency of this antenna will be somewhat less than a full-size dipole. The performance will degrade as the helices are made shorter. Despite the gain-length tradeoff, this antenna is capable of good performance when there is no room for a full-size dipole.

### Gain Types of Wire Antennas

Perhaps one of the most misused antenna expressions in amateur radio is "long wire." The fact that a relatively long piece of wire (physical dimensions) is erected for use as an antenna does not qualify it as a classic *long wire* in the true definition. A real long wire (electrical dimensions) must be one wavelength or more in size. This section of the chapter deals with actual long wires. All references thereto are based on the assumption that the length of the antenna is at least one wavelength.

The basic concepts related to height above ground and wave angles discussed in the section on dipoles applies to long wires. Fig. 14 shows the relationship of height to wave angle. Therefore, the greater the antenna height the more favorable the wave angle for DX work.

### Single Long Wire

A long-wire antenna can be operated with or without a resistive termination. When no terminating resistor is used, the maximum-response pattern will be bidirectional off the ends of the wire. Some

minor lobes will occur off the broadside of the antenna. When a long wire is terminated at the far end (Fig. 15B and C), maximum directivity is off the terminated ends, as illustrated in Fig. 18. Therefore, the antenna should be pointed toward the DX area of interest, such as NE from the New England area for working Europe. The addition of a terminating resistor does not decrease the antenna gain in the favored direction, but it does consume 3 dB of power. Thus, the terminating resistor needs to be capable of dissipating one half the power fed to the antenna, without excessive heating. Furthermore, the resistor ( $R_t$  of Fig. 15) must be noninductive so that a pure resistance exists. The optimum value of the termination cannot be calculated by means of a simple equation. The best value depends on the length of the long wire, the height above ground and some less significant factors. Generally, the value of  $R_t$  is determined experimentally by probing the long wire with an rf ammeter to establish that uniform current distribution exists. The entire length of the antenna should be probed in this manner. In practice, the correct termination requires

a complex impedance, not purely a resistance. For most amateur work a termination of 400 to 600 ohms will be entirely suitable. The reactance values normally lie between  $j150$  and  $j250$ .

The most effective method of terminating the long wire is by means of a buried or above-ground system of radial wires. Although some amateurs have simply returned the terminating resistor to a pipe driven into the earth, the effectiveness of the ground is poor. Also, the quality of such a ground system will change with the seasons. The same is true

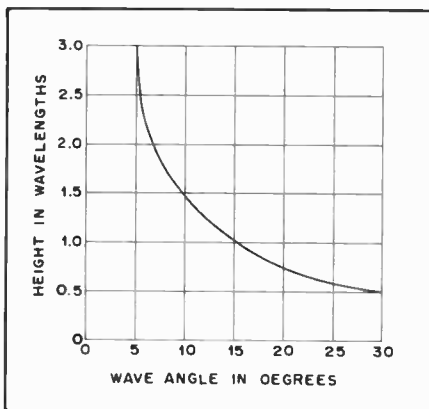


Fig. 14 — Antenna height to be used for securing maximum radiation at a desired wave angle. This curve applies to any type of horizontal antenna.

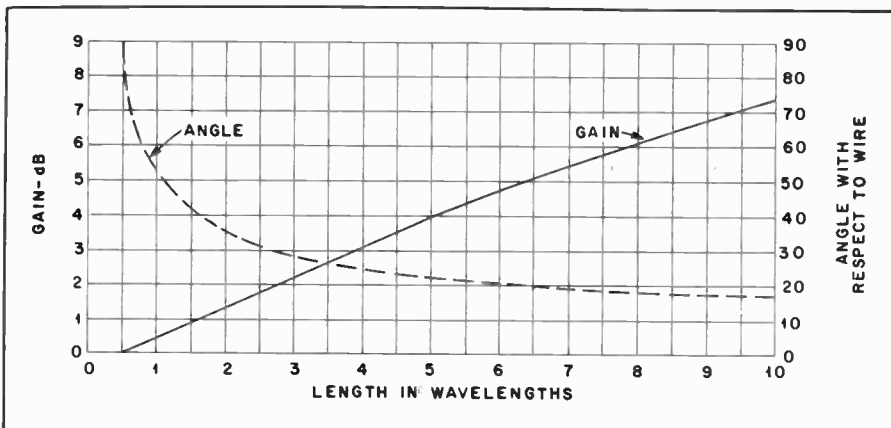


Fig. 16 — Theoretical gain of a true long-wire antenna over a reference dipole as a function of wire length. The angle, with respect to the wire, at which the radiation intensity is maximum is shown also.

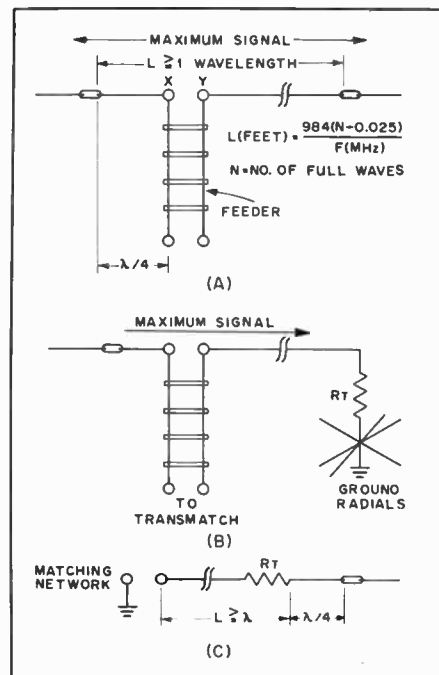


Fig. 15 — A long-wire antenna is fed  $1/4$  wavelength off one end at A. Minimum pattern distortion will be observed when using this feed technique. The same antenna is shown at B with a termination to provide unidirectional radiation. A termination can be used without returning it to ground, as shown at C. The simulated ground in this case consists of a quarter-wavelength piece of wire.

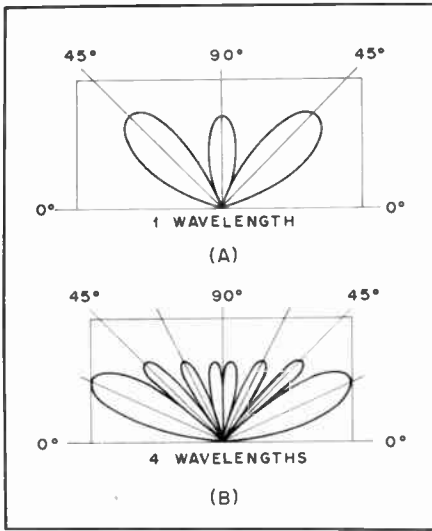


Fig. 17 — Elevation-plane radiation characteristic of a one-wavelength long wire (A) compared to that of a four-wavelength long wire. The patterns are for unterminated wires erected over a perfectly conducting ground.

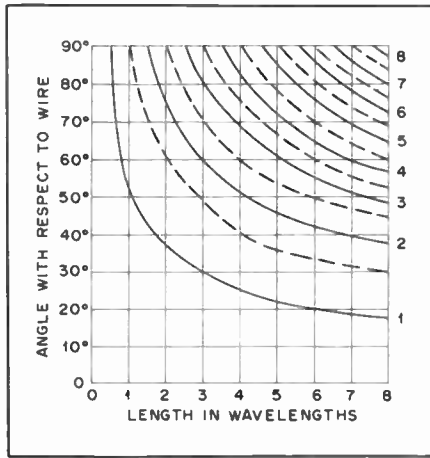


Fig. 19 — Angles from which long-wire radiation is maximum (solid curves) and zero (dashed curves). The major lobe has the power gains given in Fig. 16. Secondary lobes have lower amplitude, but the maxima may exceed the radiation intensity of a half-wavelength dipole.

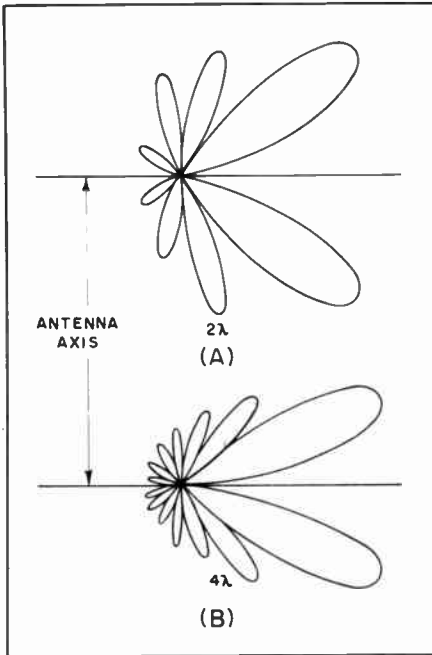


Fig. 18 — Typical radiation patterns (azimuth) for two-wavelength and four-wavelength terminated long wires. In practice, the pattern is somewhat distorted by the wire attenuation.

of buried radials, but the effects are not nearly so pronounced. Fig. 15B shows an illustration of radial-wire termination. An alternative which has been applied by some antenna designers is shown in Fig. 15C, where a 1/4-wavelength extension is added to the long wire.  $R_1$  is inserted between the antenna and the 1/4-wavelength extension. It is assumed in this case that the long wire consists of a multiple of half waves.

The theoretical gain of a long-wire antenna is given in terms of wavelengths at Fig. 16. Data are provided to show the

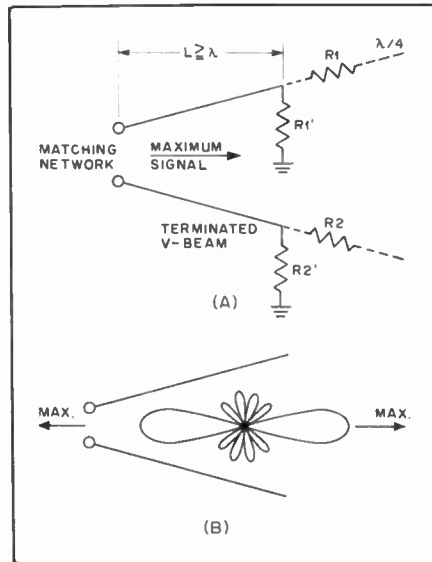


Fig. 20 — Two long-wire antennas can be combined to form a V beam as seen at A. Greater gain and directivity can be had when using this scheme. The V can be operated as resonant (unterminated) for bidirectional response, or terminated (nonresonant) for unidirectional response. Terminations  $R_1$  and  $R_2$  can connect to quarter-wavelength extensions (Fig. 15C) or as shown by  $R_1'$  and  $R_2'$  to an earth ground. The azimuthal pattern at B is for an unterminated V beam.

wave angles also. A comparison of the approximate wave angles for an unterminated one-wavelength and an unterminated four-wavelength long wire is provided in Fig. 17. It is apparent that the greater the number of wavelengths the lower the angle of radiation for the major lobes. Owing to the increased number of high-angle minor lobes of the longer antennas (Fig. 17B), good results can be obtained in the favored antenna direction under a variety of sky-wave conditions. In an actual situation, a long wire of several wavelengths can be capable of effective

long-distance communications when Yagi or quad beams are useless. It depends on the propagation conditions at a given period of the day. The major limitation is, of course, the inability of the operator to rotate the antenna toward the compass point of interest. If one were able to look down upon a long wire and see the radiation pattern, the lobes illustrated in Fig. 18 would be typical. The comparison is between a two- and a four-wavelength long wire. It can be seen that the longer the antenna the more directional it becomes as the major lobes compress. The examples are for terminated long wires. Fig. 19 shows curves for the wave angle versus length in wavelengths.

### Wire Combinations

Two long-wire antennas can be combined as shown in Fig. 20 to form what is called a *V beam*. The radiation properties are similar to those of single long wires, respective to being terminated or unterminated. The terminations,  $R_1$  and  $R_2$ , can be returned to a radial ground system or to a 1/4-wavelength wire extension at the far ends of the V. If a proper termination is made, the system has a feed-point impedance roughly equivalent to the termination value. This requires a matching circuit between the feed point and the transmission line, or between the transmission line and the station equipment, to provide a 50-ohm unbalanced load for the transmitter and receiver. A Transmatch is the better choice for most installations. The feeder can be a length of 600-ohm open-wire line to the Transmatch, assuming a 600-ohm termination is used.

Fig. 21 shows the relationship between the apex (enclosed) angle of a V beam and the leg size in wavelengths. Two wave angles (0 and 15 degrees) are provided. A V beam is designed primarily for one band, but it can be used effectively on several amateur bands when the leg length is at least one wavelength on the lowest operating band. However, the apex angle will be optimum only for the band it is designed for.

### Rhombic Antennas

Four long-wire antennas can be combined in a rhomboid configuration to develop a *rhombic antenna*. The basic structure is illustrated in Fig. 22. The system can be used with or without the termination,  $R_1$ . The decision is based on whether or not bidirectional radiation is desired. This follows the rule for long wires and V beams. A typical terminating resistance is 600 ohms for amateur work. This makes the system compatible with 600-ohm open-wire transmission line. Sides a, b, c and d all have the same length (Fig. 22). The opposite corner angles are equal. In effect, this antenna is two V beams which are joined end to end. Maximum directivity is off the terminated

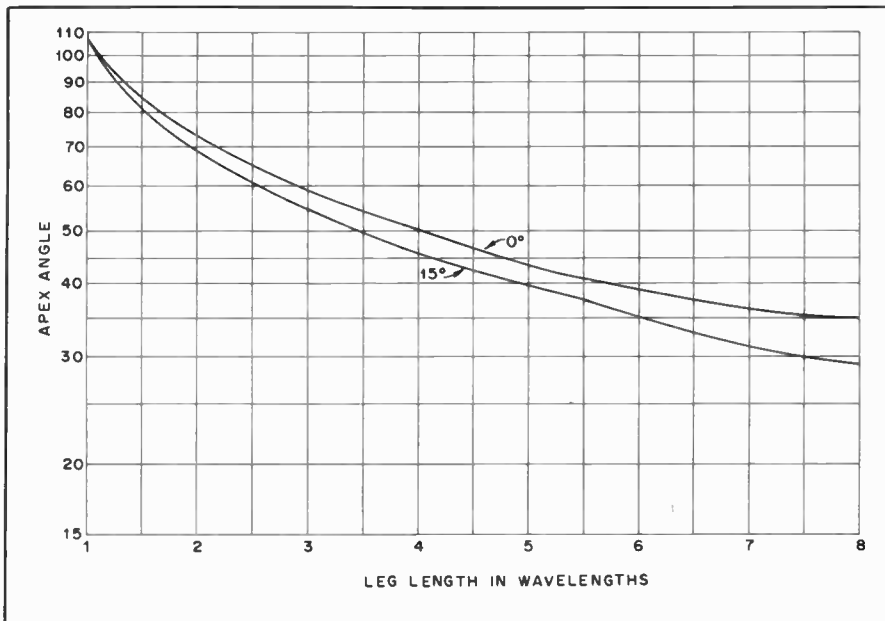


Fig. 21 — Apex angle of a V beam for alignment of the primary lobe at different wave angles, as a function of leg size in wavelengths.

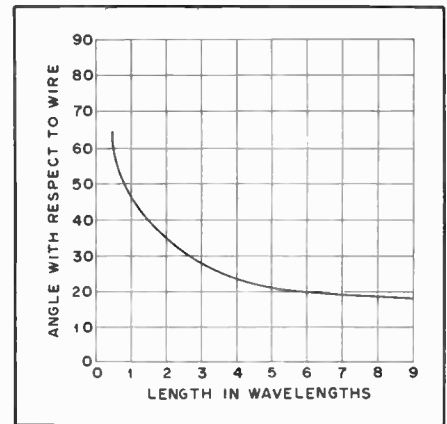


Fig. 23 — Angle with respect to wire axis at which radiation from a nonresonant long-wire antenna is maximum.

DX work. Additionally, the space occupied by vertical antennas is relatively small, making them ideal for city-lot property and apartment buildings. The principal limitation in performance is the omnidirectional pattern. This means that QRM can't be nulled out from the directions which are not of interest at a given period. The exception is, of course, when phased arrays of vertical elements are used. Despite the limitation of a single vertical element with a ground screen or radial system, cost versus performance is an incentive that inspires many antenna builders.

For use on the lower-frequency amateur bands — notably 160 and 80 meters — it is not always practical to erect a full-size vertical. In such instances it is satisfactory to accept a shorter radiating element and employ some form of *loading* to obtain an electrical length of one's choice. Most constructors design a system that contains a 1/4-wavelength driven element. However, good results and lower radiation angles are sometimes realized when using a 3/8- or 1/2-wavelength vertical. At the lower amateur frequencies the larger verticals become prohibitive, especially in urban areas where zoning ordinances may exist, and where limited acreage may rule out the installation of guy-wire systems.

Fig. 26 provides curves for physical height of verticals in wavelength versus radiation resistance and reactance. The plots are based on perfectly conducting ground, a condition which is seldom realized in practical installations. It can be seen that the shorter the radiator the lower the radiation resistance, with 6 ohms being typical for a 0.1-wavelength antenna. The lower the radiation resistance the more the antenna efficiency becomes. Also, the bandwidth decreases markedly as the length is reduced toward the left of the scale in Fig. 26. Difficulty is also experienced in developing a suitable matching network when the radiation resistance is very low.

Illustrations of some vertical-antenna

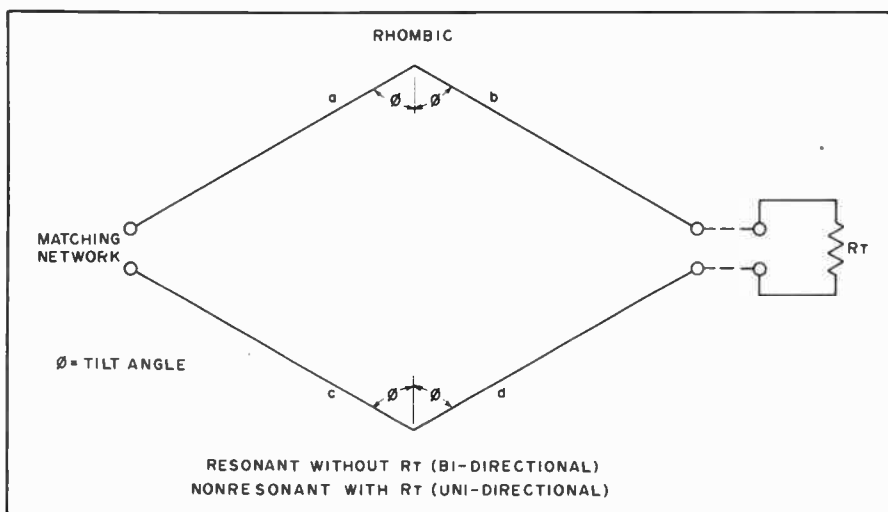


Fig. 22 — Four long-wire antennas can be combined as shown to form a high-gain system called a rhombic antenna. This antenna can be operated with or without a termination (see text).

end when  $R_t$  is used. Without a termination the bidirectional pattern extends off the open ends of the diamond.

The angle of maximum radiation for a rhombic antenna is called the *tilt angle*. This is derived by subtracting the angle of maximum radiation from 90 degrees. When a rhombic antenna is designed for a wave angle of zero, the tilt angle is 90° minus the values specified in Fig. 23. The tilt angle is shown as a function of antenna leg length in Fig. 24. The curve marked 0° is for a wave angle of zero degrees (maximum radiation in the plane of the antenna). The dashed curve shows the "optimum length" at which maximum gain is obtained for a selected wave angle. Increasing the leg length beyond the optimum will cause a decrease in gain.

Leg lengths greater than six wave-

lengths are not suggested because the directivity becomes so sharp that antenna performance is highly variable with small changes in the angle, both vertical and horizontal, at which the incoming wave reaches the antenna. These angles change with propagation, so it does not pay to employ too great a degree of directivity.

The theoretical gain of a terminated (nonresonant) rhombic is characterized by the curve in Fig. 25. The gain is referenced to a half-wavelength dipole. An allowance of 3 dB has been made for the terminating resistor.

### The Vertical Antenna

One of the more popular amateur antennas is the vertical type. With this style of antenna it is possible to obtain low-angle radiation for ground-wave and



radiation patterns are given in Fig. 27. The example at A is for a quarter-wavelength radiator over a theoretically ideal ground. The dashed lines show the current distribution, inclusive of the *image* portion below ground. The image can be equated to one half of a dipole antenna, with the vertical radiator representing the remaining dipole half. The illustration at B characterizes the pattern of a half-wavelength vertical. It can be seen that the radiation angle is somewhat lower than that of the quarter-wavelength version at A. The lower angles enhance the DX capability of the antenna. Two half wavelengths in phase are shown in Fig. 27 at C and D. From a practical point of view, few amateurs could erect such an antenna unless it was built for use on the higher hf bands, such as 20, 15 or 10 meters. The very low radiation angle is excellent for DXing, however.

### Full-Size Vertical Antennas

When it is practical to erect a full-size vertical antenna, the forms shown in Fig. 28 are worthy of consideration. The example at A is the well-known *vertical ground plane*. The ground system consists of four or more above-ground radial wires against which the driven element is worked. The driven element length in feet is derived from the standard equation

$$L \text{ (feet)} = \frac{234}{f(\text{MHz})}$$

$$L \text{ (meters)} = \frac{71.3}{f(\text{MHz})}$$

The radial wires are slightly longer, approximately  $\lambda/3.9$ , yielding the dimension in feet. It has been established generally that with four equidistant radial wires drooped at approximately 45 degrees (Fig. 28A) the feed impedance is roughly 50 ohms. When the radials are at right angles to the radiator (Fig. 28B) the feed impedance approaches 30 ohms. The major advantage in this type of vertical antenna over a ground-mounted type is that the system can be elevated well above nearby conductive objects (power lines, trees, buildings, etc.). When drooping radials are utilized they can be used as guy wires for the mast which supports the antenna. The coaxial cable shield braid is connected to the radials and the center conductor is common to the driven element.

The Marconi antenna seen in Fig. 28 at C is the classic form taken by a ground-mounted vertical. It can be grounded at the base and shunt fed, or it can be isolated from ground, as shown, and series fed. This antenna depends upon an effective ground system for efficient performance. The subject of ground screens is treated later in this section. If a perfect ground were located below the

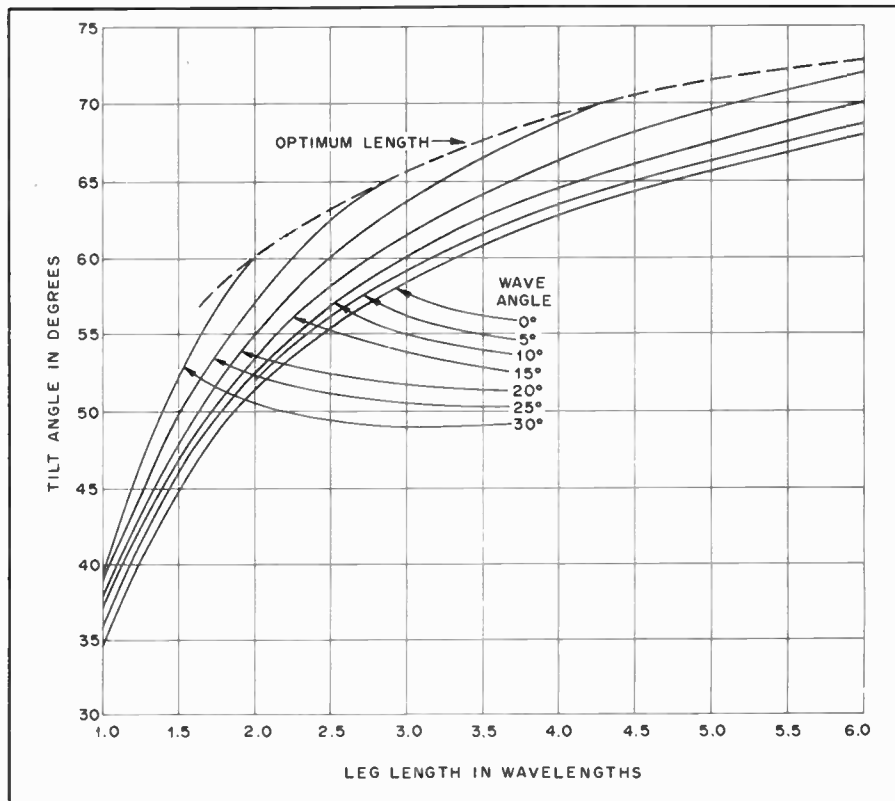


Fig. 24 — Rhombic-antenna design chart. For any given leg length, the curves show the proper tilt angle to give maximum radiation at the selected wave angle. The broken curve marked "optimum length" shows the leg length that gives the maximum possible output at the selected wave angle. The optimum length as given by the curves should be multiplied by 0.74 to obtain the leg length for which the wave angle and main lobe are aligned.

antenna, the feed impedance would be near 30 ohms. In a practical case, owing to imperfect ground, the impedance is more apt to be in the vicinity of 5 to 15 ohms.

A gamma-feed system for a grounded 1/4-wavelength vertical is presented in Fig. 28D. Some rules of thumb for arriving at workable gamma-arm and capacitor dimensions are to make the rod length 0.04 to 0.05 wavelength, its diameter 1/3 to 1/2 that of the driven element and the center-to-center spacing between the gamma arm and the driven element roughly 0.007 wavelength. The capacitance of C1 at a 50-ohm matched condition will be some 7 pF per meter. The absolute value at C1 will depend upon whether the vertical is resonant and the precise value of the radiation resistance. Generally, best results can be had when the radiator is approximately three percent shorter than the resonant length. Amateur antenna towers lend themselves well to use as shunt fed verticals, even though an hf-band beam antenna may be mounted on the tower. The overall system should be close to resonance at the desired operating frequency if gamma feed is to be used. The hf-band beam will contribute somewhat to top loading of the tower. The natural resonance of such a system can be checked by dropping a no. 12 or 14 wire down from the top of the tower (making it common to the tower top) to

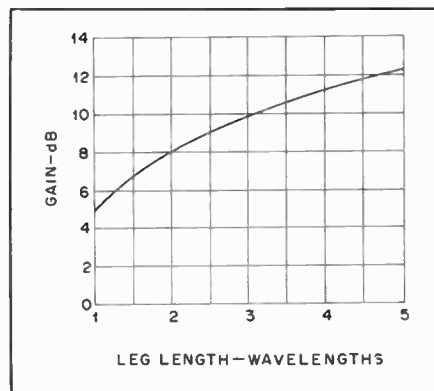


Fig. 25 — Theoretical gain of a nonresonant rhombic antenna over a half-wave dipole in free space. This curve includes an allowance of 3 dB for loss in the terminating resistor.

form a folded unipole (Fig. 28E). A four- or five-turn link can be inserted between the lower end of the drop wire and the ground system, then a dip meter inserted in the link to observe the resonant frequency. If the tower is equipped with guy wires, the latter should be broken up with strain insulators to prevent unwanted loading of the vertical. In such cases where the tower and beam antenna are not able to provide 1/4-wavelength resonance, portions of the top guy wires can be used as top-loading capacitance. It

will be necessary to experiment with the guy-wire lengths (using the dip-meter technique) while determining the proper dimensions.

A folded-unipole type of vertical is depicted at E of Fig. 28. This system has the advantage of increased feed-point impedance. Furthermore, a Transmatch can be connected between the bottom of the drop wire and the ground system to permit operation on more than one band. For example, if the tower is resonant on 80 meters, it can be used as shown on 160 and 40 meters with reasonable results, even though it is not electrically long enough on 160. The drop wire need not be a specific distance from the tower, but spacings between 12 and 30 inches are suggested.

The method of feed seen at Fig. 28F is commonly referred to as "slant-wire feed." The guy wires and the tower combine to provide quarter-wave resonance. A matching network is placed between the lower end of one guy wire and ground and adjusted for an SWR of 1. It does not matter at which level on the tower the guy wires are connected, assuming that the Transmatch is capable of effecting a match to 50 ohms.

**Physically Short Verticals**

A group of short vertical radiators is presented in Fig. 29. Illustrations A and B are for top and center loading. A capacitance hat is shown in each example. It should be as large as practical to increase the radiation resistance of the antenna and improve the bandwidth. The wire in the loading coil is chosen for the largest gauge consistent with ease of winding and coil-form size. The larger wire diameters will reduce the  $I^2R$  losses in the system. The coil-form material should be of the medium- or high-

voltage breakdown resistance dielectric type. Phenolic or fiberglass tubing is entirely adequate.

A base-loaded vertical is shown at C of Fig. 29. Since this is the least effective method of loading in terms of antenna

performance, it should be used only as a last choice. The primary limitation is that the current portion of the vertical exists in the coil rather than the driven element. With center loading the portion of the antenna below the coil carries current,

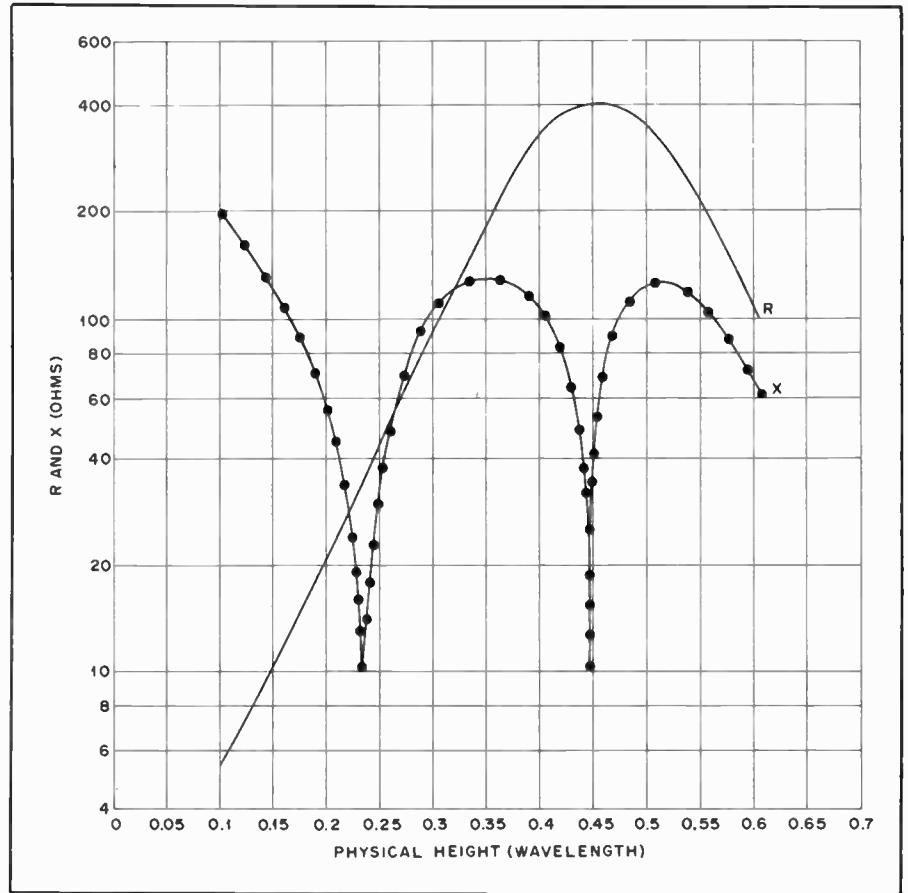


Fig. 26 — Radiation resistance (solid curve) and reactance (dotted curve) of vertical antennas as a function of physical height.

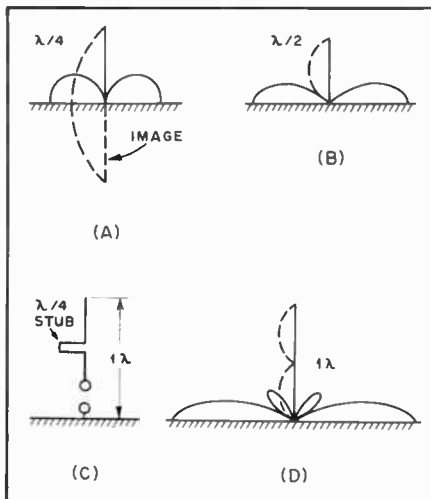


Fig. 27 — Elevation plane responses for a quarter-wavelength vertical antenna (A), a 1/2-wavelength type (B) and two half waves in phase (C and D). It can be seen that the examples at B and D provide lower radiation angles than the version at A.

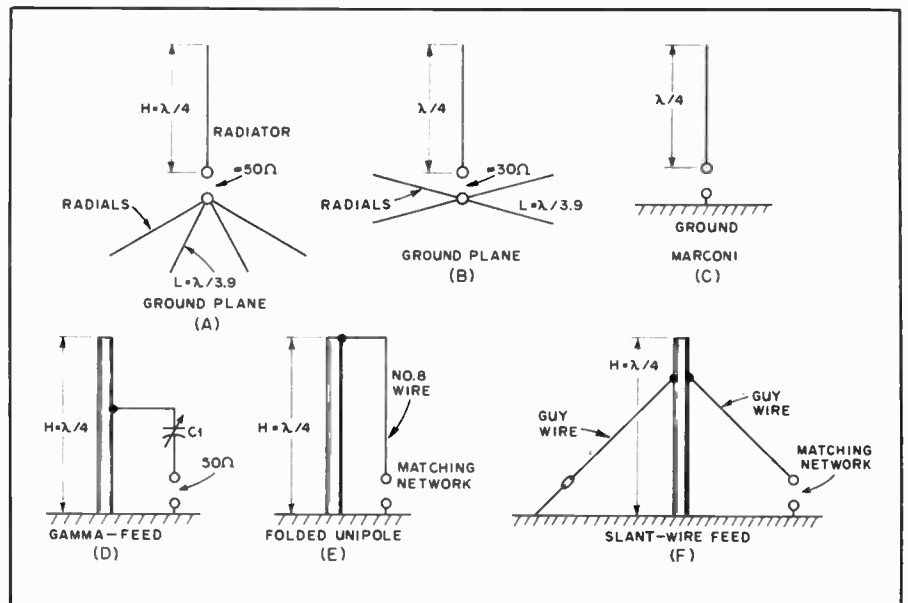


Fig. 28 — Various types of vertical antennas.

and with the top-loading version the entire vertical element carries current. Since the current part of the antenna is responsible for most of the radiating, base loading is the least effective of the three methods. The radiation resistance of the coil-loaded antennas shown is usually less than 15 ohms.

A method for using guy wires to top load a short vertical is illustrated in Fig. 29D. This system works well with gamma feed. The loading wires are trimmed to provide an electrical quarter wavelength for the overall system. This method of loading will result in a higher radiation resistance and greater bandwidth than the systems seen in Fig. 29A, B and C. If an hf-band or vhf array is atop the tower, it will simply contribute to the top loading.

A tri-wire unipole is shown at E of Fig. 29. Two no. 8 drop wires are connected to the top of the tower and brought to ground level. The wires can be spaced any convenient distance from the tower — normally 12 to 30 inches (0.3 to 0.76 m) from one side. C1 is adjusted for an SWR of 1. This type of vertical has a fairly narrow bandwidth, but because C1 can be motor-driven and controlled from the operating position, QSYing is accomplished easily. This technique will not be suitable for matching to 50-ohm line unless the tower is less than an electrical quarter wavelength.

A different method for top loading is shown at F of Fig. 29. W9UCW described this system in December 1974 *QST* as "The Minooka Special." An extension is used at the top of the tower to effect an electrical quarter-wavelength vertical. L1 is a loading coil with sufficient inductance to provide antenna resonance. This type of antenna lends itself nicely to operation on 160 meters. L1 and the pipe extension above the hf-band beam can be tuned at ground level against the ground system. It should be made resonant approximately 100 kHz higher than the desired operating frequency for use on 160 meters. After it is in place on the tower, the overall system resonance will drop some 100 kHz. Final adjustment can be accomplished by trimming the capacitance-hat spokes.

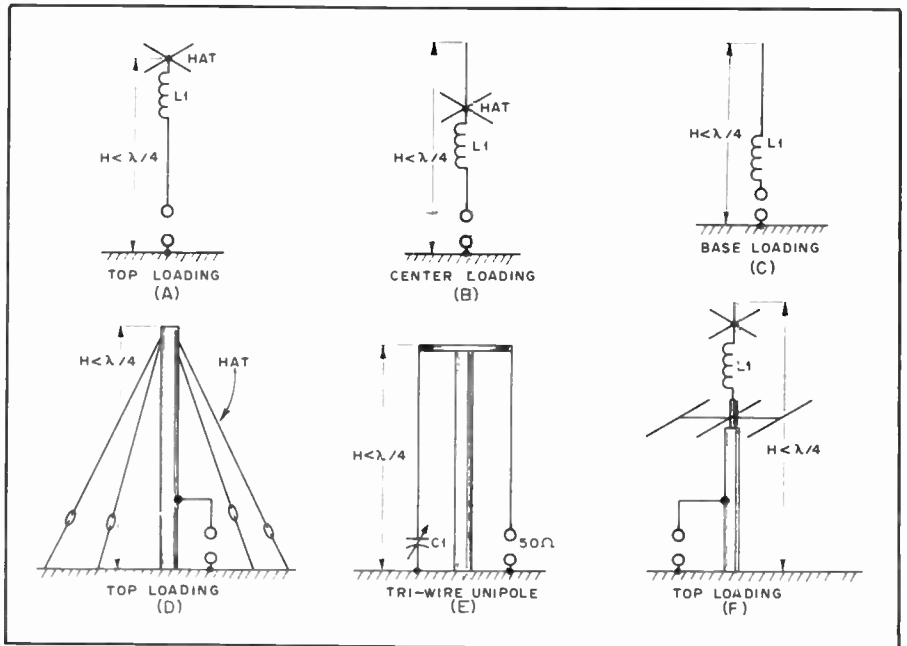


Fig. 29. — Vertical antennas which are less than wavelength in height.

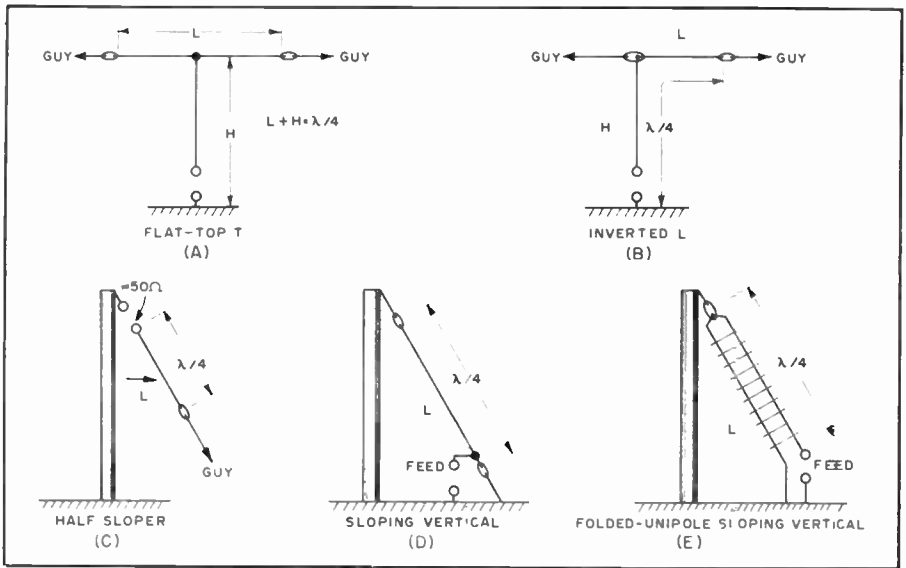


Fig. 30 — Some variations in vertical antennas which offer excellent performance.

### Cables and Control Wires on Towers

Most vertical antennas of the type shown in Fig. 29 consist of towers and hf or vhf beam antennas. The rotator control wires and the coaxial feeders to the top of the tower will not affect antenna performance adversely. In fact, they become a part of the composite antenna. To prevent unwanted rf currents from following the wires into the shack, simply dress them close to the tower legs and bring them to ground level. This decouples the wires at rf. The wires should then be routed along the earth surface (or buried underground) to the operating position. It is not necessary to use bypass capacitors or rf chokes in the rotator

control leads if this is done, even when maximum legal power is employed.

### Variations in Verticals

A number of configurations qualify for use as vertical antennas even though the radiators are fashioned from lengths of wire. Fig. 30A shows a flat-top T vertical. Dimension H should be as tall as possible for best results. The horizontal section, L, is adjusted to a length which provides resonance. Maximum radiation is polarized vertically despite the horizontal top-loading wire. A variation of the T antenna is depicted at B of Fig. 30. This antenna is commonly referred to as an "inverted L." Again, vertical member H

should be as long as possible. L is added to provide an electrical quarter wavelength overall. Some amateurs believe that a 3/8-wavelength version of this antenna is more effective, since the current portion of the wire is elevated higher above ground than is the case with a 1/4-wavelength wire.

A "half sloper" is shown at Fig. 30C. The antenna is one half of a dipole. The unique feature is that the current portion of the radiator is elevated well above ground. This antenna is fed with 50-ohm coaxial cable, the center conductor of which connects to L. The coax shield braid is affixed electrically to the tower at the antenna feed point. The wire, L, is



trimmed for an SWR of 1 at the desired operating frequency. Excellent DX results are reported with this antenna. Maximum radiation is in the direction of the arrow because of the reinforcing effect of the tower support. The enclosed angle of the antenna is usually between 45 and 60 degrees, depending upon the available tower height.

It is often possible to realize a full-size quarter-wavelength vertical type of radiator by using the technique illustrated at D of Fig. 30. A tall tree or a tower can be used as a support. When a metal support is available, the system at C is preferable.

A folded-unipole slanting vertical can be fashioned from open-wire line or TV ribbon line as shown at Fig. 30E. This method provides a higher radiation resistance than that of Fig. 30D. If TV ribbon is used the velocity factor of the line must be included when cutting L to length.

### Ground Systems

The importance of an effective ground system for vertical antennas cannot be emphasized too strongly. However, it is not always possible to install a radial network that approaches the ideal. It might be said that "a poor ground is better than no ground at all," and therefore the amateur should experiment with whatever is physically possible rather than exclude vertical antennas from his or her construction plans. It is often possible to obtain excellent DX results with practically no ground system at all. Although the matter of ground systems could be debated almost endlessly, some practical rules of thumb are in order for those wishing to erect vertical antennas. Generally, if the physical height of the vertical is a quarter wavelength, the radial wires should be of the same length and dispersed uniformly from the base of the tower. In this example approximately 60 radial wires will suffice. The conductor size of the radials is not especially significant. Wire gauges from no. 4 to no. 20 have been used successfully by amateurs. Copper wire is preferred, but where soil acid or alkali is not high in level, aluminum wire can be used. The wires can be bare or insulated, and they can be laid on the earth surface or buried a few inches below ground. The insulated wires will have greater longevity by virtue of reduced corrosion and dissolution from soil chemicals.

The shorter the vertical antenna the fewer and shorter the radials need be. For example, a vertical which is 1/8 wavelength high will provide maximum field strength with 16 to 18 radial wires, and the wires need be only as long as the vertical is high. If time and expense are not a prime consideration, the amateur should bury as much ground wire as possible. Some operators have literally *miles* of wire buried radially beneath their vertical

antennas.

When property dimensions do not allow a classic installation of equally spaced radial wires, they can be placed in the ground wherever space will permit. They may run away from the antenna in only one or two compass directions. Results will still exceed those of when no ground system is used.

A single ground rod, or a group of them bonded together, is seldom as effective as a collection of random-length radial wires. In some instances a group of short radial wires can be used in combination with ground rods driven into the soil near the base of the antenna. The power-company ground can be tied in also, and if a metal fence skirts the property it can also be used as part of the ground system. A good rule is to use anything that will serve as a ground when developing a radial-ground system.

All radial wires must be connected together at the base of the vertical antenna. The electrical bond needs to be of low resistance. Best results will be obtained when the wires are soldered together at the junction point. When a grounded vertical is used, the ground wires should be affixed securely to the base of the driven element. A lawn-edging tool is excellent for cutting slits in the soil when laying radial wires.

### A 360° Steerable Vertical Phased Array for 7 MHz

The original design information for the array presented here appeared in April 1976 *QST* in an article written by Atchley, Stinehelfer and White. That article featured a system designed for use in the 3.5- to 4.0-MHz range.

The configuration shown here makes use of four 1/4 wavelength vertical elements in a square, with quarter-wave spacing between adjacent elements, as shown, with its predicted pattern, in Fig. 32. All elements are fed with equal amplitudes, the rear element at 0°, the two side elements at -90° and the lead element at -180°. The beam is transmitted along the diagonal from the rear to the lead element. Gain due to horizontal beam formation alone is approximately 5.3 dB. Front-to-back ratio is on the order of 25 dB. Front-to-side ratio is 12 dB at 90° either side, increasing to much higher levels at 135° either side. Since most of the vertical energy is concentrated at low angles, as much as 4 dB of gain additional to the predicted 5.3 dB in the horizontal plane can be achieved in theory, with perfectly conducting ground. With a good radial system and less-than-perfect ground one can expect an approximate additional gain of 2 dB, or a total gain just over 7 dB for the system described.

A computer program calculation predicts the half-power beamwidth to be 97°. A suitable switching matrix is used to direct the beam pattern to four different

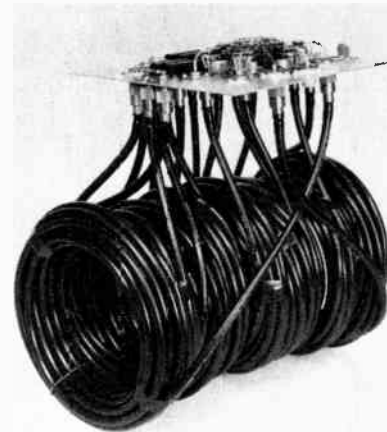


Fig. 31 — Photograph of the assembled phase system.

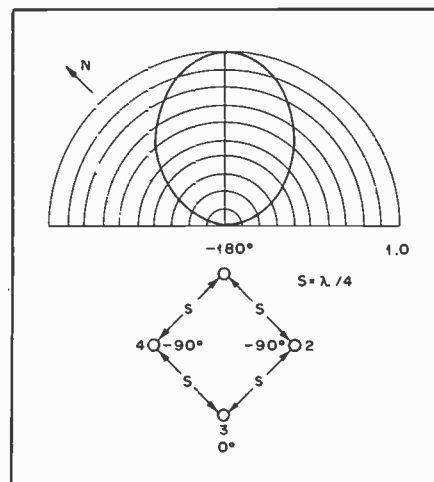


Fig. 32 — Polar plot of relative power, and planar view of the four-element diamond array showing the pattern obtained with no dc voltage on the switching relays, as in Fig. 33. Minor lobes are too far down to show on this scale.

quadrants, with only a slight loss of forward gain at the cross-over points, and virtually no deterioration of the front-to-back and front-to-side suppression.

### RF Power Dividers

Good power splitters are essential to the operation of phased arrays. The system described here makes use of 2-way Wilkinson Power Dividers<sup>1</sup>. Those readers versed in microwave technology are no doubt familiar with these devices. As shown in Fig. 33, power from the transmitter is fed through 50-ohm line of any length to a T connection, feeding two quarter-wavelength lines, W1 and W2. The two inner conductors of the 70-ohm lines are connected through a 100-ohm

<sup>1</sup>Wilkinson, "An N-Way Hybrid Power Divider," *IRE Transactions on Microwave Theory and Techniques*, January, 1960.

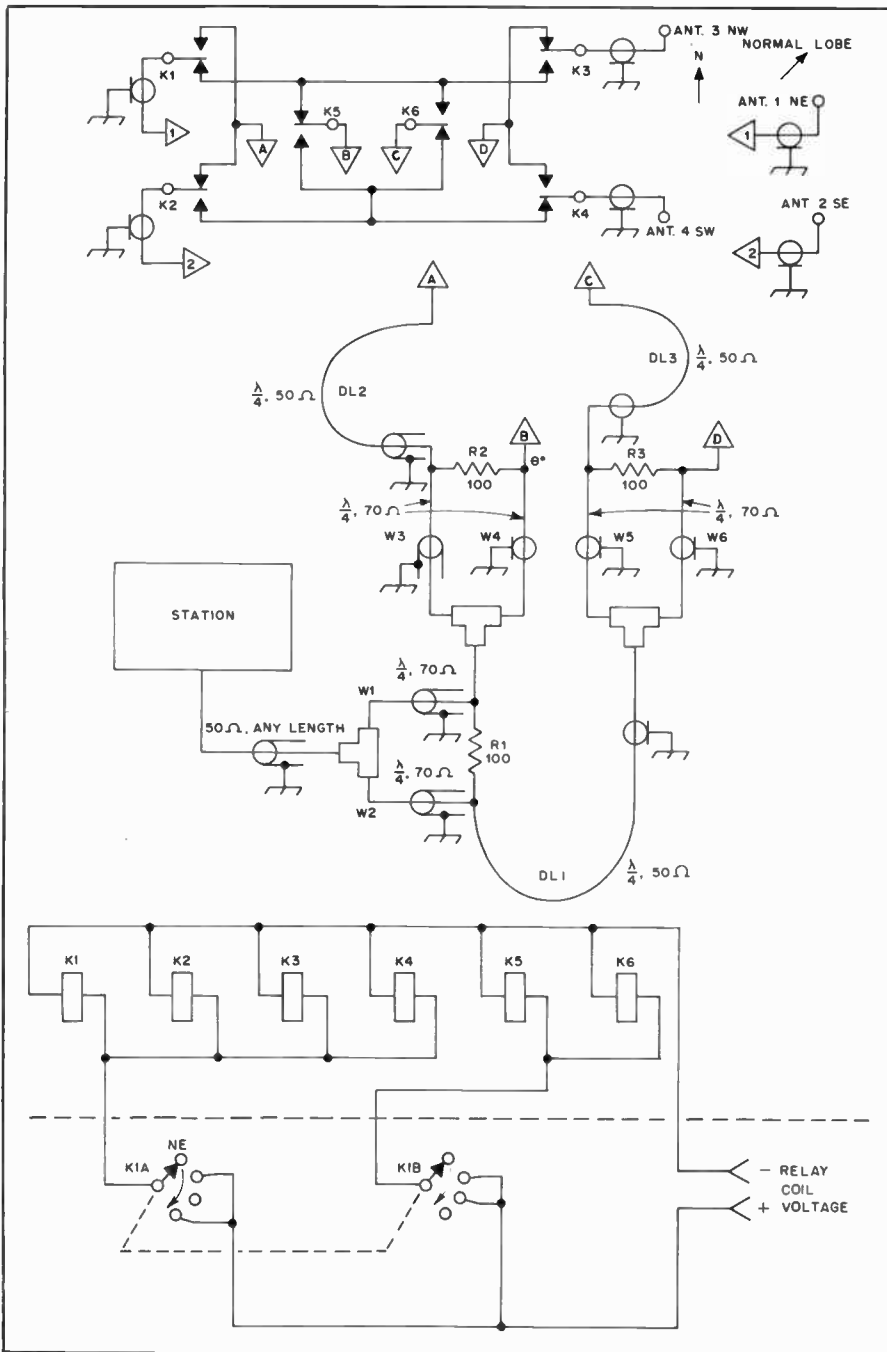


Fig. 33 — Schematic diagram of the phased array. Relays K1 through K6 are three-pole, double-throw units with all three sections of each relay connected in parallel. Each of the 100-ohm resistances are comprised of two 200-ohm noninductive 50-watt resistors manufactured by Nytronics. The quarter wavelength lines should be adjusted for 7.1 MHz with the aid of a noise bridge, RX bridge or similar device. Calculated lengths of line for the velocity factors of 0.81 and 0.66 are 28.1 feet and 22.9 feet respectively. (Feet  $\times$  0.3048 = M.)

noninductive resistance, R1. This type of divider gives an equal power split, matches to 50-ohm loads at the two outputs, and has the unique property that any energy returning to the two outputs out of phase, due to mismatches or mutuals, is absorbed in the 100-ohm resistor.

The 90-degree phase-delay cable (DL) used in one side of each of the three power-splitting hybrids serves to assure that equal power reflections from the antennas are absorbed. Theoretically the

resistors absorb none of the forward power. This technique provides approximately 30 dB of isolation from one output terminal to the other, to unwanted energy. The Wilkinson Power Divider, when used to feed phased arrays, reduces the problems associated with element interaction due to mutual impedances between elements.

#### Feeding, Switching and Phasing

The four-element system shown here uses three Wilkinson 2-way power di-

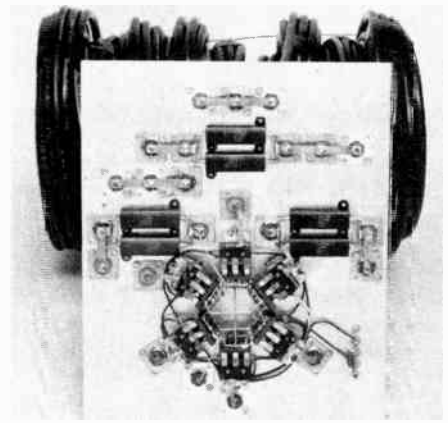


Fig. 34 — Close-up view of the relay and resistor assembly.

viders, as shown in Fig. 33. Proper element phasing is accomplished with three 90-degree sections of RG-8/U cable: DL1, DL2 and DL3. The four outputs are at 0°, -90°, -90° and -180°, respectively in phase relationship, with power from the transmitter divided into four equal parts. Special attention should be paid to preserving symmetry throughout the system, in the hybrids, phase shifters, rf switching, feeds and antenna placement, in order to have the array perform uniformly as it is switched between the four headings.

The switching was done with six relays as shown in Fig. 33 and the accompanying photograph. With no voltage applied to the relay coils, the arms are in the positions shown in Fig. 33, giving northeasterly directivity — a convenient heading for operation from New England. The three Wilkinson power divider resistor networks along with the switching relays are mounted on a piece of sheet aluminum measuring 10  $\times$  12 inches (254  $\times$  305 mm). Each of the three phasing lines and quarter-wavelength lines associated with the power dividers connect to coaxial fittings also mounted to the piece of sheet aluminum. The entire phasing/switching system can be transported or worked on as a single unit. Basic layout of this system is shown in Figs. 34 and 36. Measured phase errors due to unequal lead lengths in the switching system are less than two degrees. The builder need not follow the layout shown here — generally speaking, if the leads are kept short and direct the system should function according to specifications listed earlier.

The relays used in this system were surplus 3-pole double-throw units. Each of the three sections were connected in parallel to assure that the relays would handle the transmitter power. A three-wire control system is used to steer the array. Four different commands are required for four different directions as shown in the relay truth table in Fig. 33.

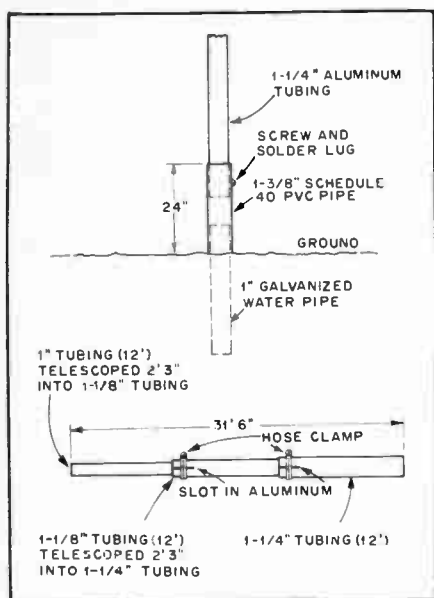


Fig. 35 — Details of element construction and mounting method. The water pipe should be driven into the ground so that approximately one foot of the pipe extends above ground level. Feet  $\times 0.3048 = m$  and inches  $\times 25.4 = mm$ .

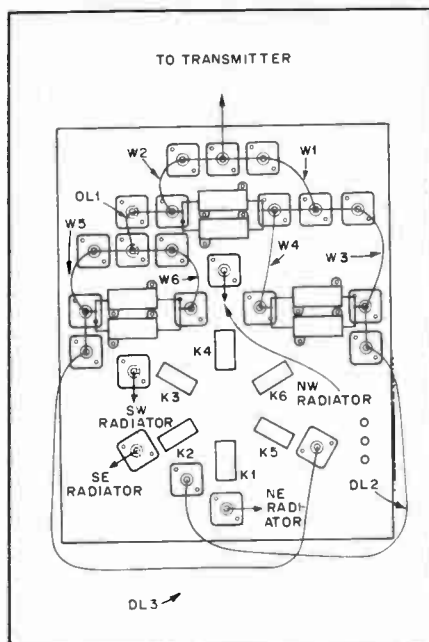


Fig. 36 — This drawing shows where each of the phasing and delay lines are connected to the divider/switching system.

An aluminum chassis measuring  $10 \times 12 \times 3$  inches ( $254 \times 305 \times 76$  mm) placed over the piece of aluminum on the resistor/relay side protects these components from the weather. Silicon seal is used to fill any holes or slots in the chassis.

#### Radiators and Radials

Relays K1 through K4 (Fig. 33) connect to their respective radiators through equal lengths of 50-ohm line. The radiators are constructed from 6061-T6 aluminum tubing which is available in 12 foot (3.7 m) lengths. Three pieces are required for each radiator: one each 1-1/4 inches (32 mm), 1-1/8 inches (28 mm), and 1 inch (25 mm) diameter. Constructional details are shown in Fig. 32. Base insulators are made from schedule 40 PVC pipe measuring 1-3/8 inch (35-mm) diameter. The 1-1/4-inch aluminum tubing does not fit securely inside the PVC pipe necessitating the use of shims between the aluminum tubing and PVC. One simple way of solving this problem is to cut thin strips (about 1/2 inch or 13 mm) of sheet aluminum and wind them over the aluminum tubing, sliding both the tubing and shim material into the PVC pipe. See Fig. 35 for details.

The radiators are supported at the base by 4-foot (1.2-m) long pieces of 1-inch galvanized water pipe driven approximately 3 feet into the ground. Care should be taken to ensure that the pipe is kept true vertical when inserted into the ground. Although the radiators are self supporting, it is highly recommended that

at least one set of guy wires be used for each radiator. Moderate winds have no difficulty bending the radiators if guys are not used. With the system described here, one set of guys, located at the 24-foot (7.3 m) point are used. Heavy nylon cord was used for this purpose.

Though 120 radials are considered to be the optimum number, only 40 per element are used with this system. All are 35 feet (10.66 m) long, no. 15 aluminum fence wire, lying directly on the ground. The radials at the center of the array, in addition to providing considerable symmetry of the mutuals, allows a higher packing density for the radials, reducing ground losses.

#### Testing the System

Before power is applied to the array a quick resistance check should be made. One person should go to each element and short the input, while another person watches an ohmmeter placed across the main line at the station end. Make sure that a very low dc resistance is measured. Then, with the array in the normal position, that shown in the schematic, make sure that the resistance across the input is high. If it is low, check for moisture in the cables or connectors or for other leakage resistance. Silicone grease in the connectors is a good moisture preventive measure. It is recommended that these resistance checks be repeated periodically to be sure that all is well.

When the array is ready for use, go easy at first, as any reflected energy will be dissipated in the 100-ohm resistances. If

they become hot, there is either a problem with the system or better matching of the elements will be necessary. Each 100-ohm resistance is made of two Sage 200-ohm, 50-watt resistors connected in parallel.

#### Using the System

When receiving in the "search" mode, one hand tunes the receiver while the other operates the lobe selector switch, to see which position "listens" best. Large rotary arrays typically take 45 to 60 seconds to rotate 360°, which tends to discourage frequent directional checks. With the phased array a complete scan takes but a few seconds. The high front and side rejection eliminates most of the interference from signals in unwanted directions, and in transmitting the clean pattern helps to prevent interference to stations off the lobe of the beam that might be on the same frequency.

One useful by-product of this system has been the reduced atmospheric noise pickup from unwanted directions. In particular, when listening toward Europe, atmospheric noise coming from electrical storms in the southwest is greatly reduced, improving the signal-to-noise ratio on signals arriving from the favored direction.

#### Yagi and Quad Directive Antennas

Most of the antennas described earlier in this chapter have unity gain or just slightly more. The notable exception is the phased vertical array. For the purpose of obtaining gain and directivity it is convenient to use the *Yagi-Uda* or *cubical-quad* types of hf-band beam antennas. The former is commonly called a "Yagi" and the latter is referred to as a "quad" in the amateur vernacular.

Most operators prefer to erect these antennas for horizontal polarization, but they can be used as vertically polarized arrays as well by merely rotating the feed point 90 degrees. In effect, the beam antenna is turned on its side for vertical polarity. The number of elements employed will depend on the gain desired and the capability of the supporting structure to contain the array safely. Many amateurs obtain satisfactory results with only two elements in a beam antenna, while others have several elements operating for a single amateur band. Regardless of the number of elements used, the height-above-ground rule shown earlier for dipole antennas remains valid with respect to the angle of radiation. This is demonstrated in Fig. 37 at A and B where a comparison of radiation characteristics is given for a three-element Yagi at one-half and one wavelength above a perfectly conducting ground. It can be seen that the higher antenna has a lobe that is more favorable for DX work (roughly 15 degrees) than the larger lobe of Fig. 37A (approximately 30 degrees). The pattern at B shows that some useful



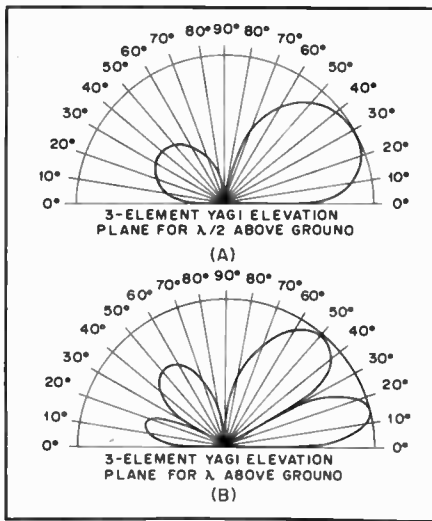


Fig. 37 — Elevation-plane response of a three-element Yagi placed  $\lambda/2$  wavelength above a perfect ground (A) and the same antenna spaced one wavelength above ground (B).

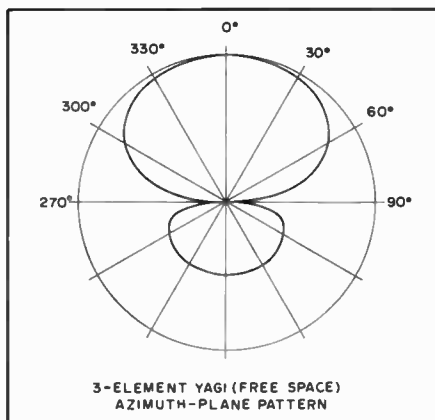


Fig. 38 — Azimuth-plane pattern of a three-element Yagi in free space.

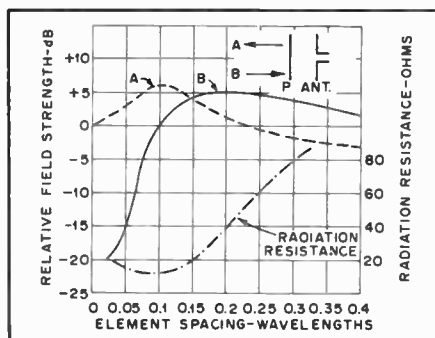


Fig. 39 — Gain vs. element spacing for an antenna and one parasitic element. The reference point, 0 dB, is the field strength from a half-wave antenna alone. The greatest gain is in the direction A at spacings of less than 0.14 wavelength, and in direction B at greater spacings. The front-to-back ratio is the difference in dB between curves A and B. Variation in radiation resistance of the driven element is also shown. These curves are for a self-resonant parasitic element. At most spacings the gain as a reflector can be increased by slight lengthening of the parasitic element; the gain as a director can be increased by shortening. This also improves the front-to-back ratio.

high-angle radiation exists also, and the higher lobe is suitable for short-skip contacts when propagation conditions dictate the need. A free-space azimuth pattern for the same antenna is provided in Fig. 38. The back-lobe pattern reveals that most of the power is concentrated in the forward lobe. The power difference dictates the front-to-back ratio in dB. It is infrequent that two three-element Yagis with different element spacings will yield the same lobe patterns. The data in Fig. 38 are given only for illustrative purposes.

### Parasitic Excitation

In most of these arrangements the additional elements receive power by induction or radiation from the driven element, generally called the "antenna," and reradiate it in the proper phase relationship to achieve the desired effect. These elements are called *parasitic* elements, as contrasted to the driven elements which receive power directly from the transmitter through the transmission line.

The parasitic element is called a *director* when it reinforces radiation on a line pointing to it from the antenna, and a *reflector* when the reverse is the case. Whether the parasitic element is a director or reflector depends upon the parasitic-element tuning, which usually is adjusted by changing its length.

### Gain vs. Spacing

The gain of an antenna with parasitic elements varies with the spacing and tuning of the elements and thus for any given spacing there is a tuning condition that will give maximum gain at this spacing. The maximum front-to-back ratio seldom, if ever, occurs at the same condition that gives maximum forward gain. The impedance of the driven element also varies with the tuning and spacing, and thus the antenna system must be tuned to its final condition before the match between the line and the antenna can be completed. However, the tuning and matching may interlock to some extent, and it is usually necessary to run through the adjustments several times

to insure that the best possible tuning has been obtained.

### Two-Element Beams

A two-element beam is useful where space or other considerations prevent the use of the larger structure required for a three-element beam. The general practice is to tune the parasitic element as a reflector and space it about 0.15 wavelength from the driven element, although some successful antennas have been built with 0.1-wavelength spacing and director tuning. Gain vs. element spacing for a two-element antenna is given in Fig. 39 for the special case where the parasitic element is resonant. It is indicative of the performance to be expected under maximum-gain tuning conditions.

### Three-Element Beams

A theoretical investigation of the three-element case (director, driven element and reflector) has indicated a maximum gain of slightly more than 7 dB. A number of experimental investigations have shown that the optimum spacing between the driven element and reflector is in the region of 0.15 to 0.25 wavelength, with 0.2 wavelength representing probably the best overall choice. With 0.2-wavelength reflector spacing, Fig. 40 shows the gain variation with director spacing. It is obvious that the director spacing is not especially critical, and that the overall length of the array (boom length in the case of a rotatable antenna) can be anywhere between 0.35 and 0.145 wavelength with no appreciable difference in gain.

Wide spacing of both elements is desirable not only because it results in high gain but also because adjustment of tuning or element length is less critical and the input resistance of the driven element is higher than with close spacing. The latter feature improves the efficiency of the antenna and makes a greater bandwidth possible. However, a total antenna length, director to reflector, of more than 0.3 wavelength at frequencies of the order of 14 MHz introduces considerable difficulty from a constructional standpoint. Lengths of 0.25 to 0.3 wavelength

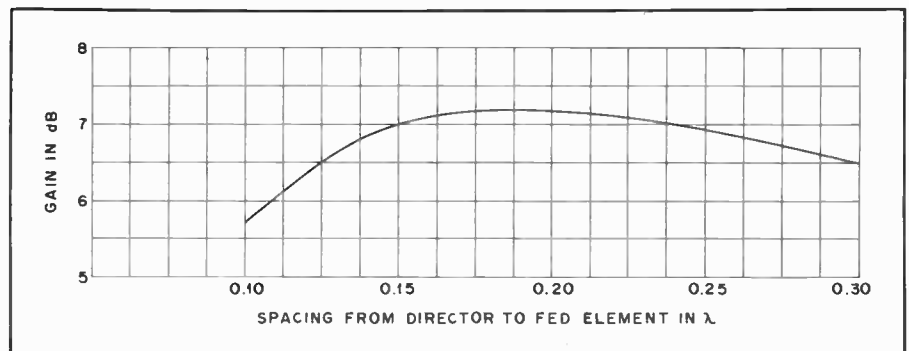


Fig. 40 — Gain of three-element Yagi versus director spacing, the reflector spacing being fixed at 0.2 wavelength.

are therefore frequently used for this band, even though they are less than optimum.

In general, the antenna gain drops off less rapidly when the reflector length is increased beyond the optimum value than it does for a corresponding decrease below the optimum value. The opposite is true of a director. It is therefore advisable to err, if necessary, on the long side for a reflector and on the short side for a director. This also tends to make the antenna performance less dependent on the exact frequency at which it is

operated, because an increase above the design frequency has the same effect as increasing the length of both parasitic elements, while a decrease in frequency has the same effect as shortening both elements. By making the director slightly short and the reflector slightly long, there will be a greater spread between the upper and lower frequencies at which the gain starts to show a rapid decrease.

When the over all length has been decided upon, the element lengths can be found by referring to Fig. 41. The lengths determined by these charts will vary slightly in actual practice with the element diameter and the method of supporting the elements. The tuning of a beam should always be checked after installation. However, the lengths obtained by the use of the charts will be close to correct in practically all cases, and they can be used without checking if the beam is difficult to access.

In order to make it even easier for the Yagi builder, Table 1 can be used to determine the element lengths needed. Both cw and phone lengths are included for the three bands, 20, 15 and 10 meters. The 0.2 wavelength spacing will provide greater bandwidth than the 0.15 spacing. Antenna gain is essentially the same with either spacing. The element lengths given will be the same whether the beam has two, three or four elements. It is recommended that "plumber's delight" type construction be used where all the elements are mounted directly on and grounded to the boom. This puts the entire array at dc ground potential, affording better lightning protection. A gamma section can be used for matching the feed line to the array.

### Tuning Adjustments

The preferable method for checking the beam is by means of a field-strength meter or the S meter of a communications receiver, used in conjunction with a dipole antenna located at least 10 wavelengths away and as high as or higher than the

beam that is being checked. A few watts of power fed into the antenna will give a useful signal at the observation point, and the power input to the transmitter (and hence the antenna) should be held constant for all the readings.

Preliminary matching adjustments can be done on the ground. The beam should be set up so the reflector element rests on earth, with the remaining elements in a vertical configuration. In other words, the beam should be aimed straight up. The matching system is then adjusted for 1:1 SWR between the feed line and driven element. When the antenna is raised into its operating height, only slight touch-up of the matching network will be required.

A great deal has been printed about the need for tuning the elements of a Yagi-type beam. However, experience has shown that lengths given in Fig. 41 and Table 1 are close enough to the desired length that no further tuning should be required. This is true for Yagi arrays made from metal tubing. However, in the case of quad antennas, made from wire, the reflectors and directors *should* be tuned with the antenna in its operating location. The reason is that it is practically impossible to cut and install wire to the *exact* dimensions required for maximum gain or front-to-back.

### Simple Systems: the Rotary Beam

Two- and three-element systems are popular for rotary-beam antennas, where the entire antenna system is rotated, to permit its gain and directivity to be utilized for any compass direction. They may be mounted either horizontally (with the plane containing the elements parallel to the earth) or vertically.

A four-element beam will give still more gain than a three-element one, provided the support is sufficient for about 0.2 wavelength spacing between elements. The tuning for maximum gain involves many variables, and complete gain and tuning data are not available.

The elements in close-spaced (less


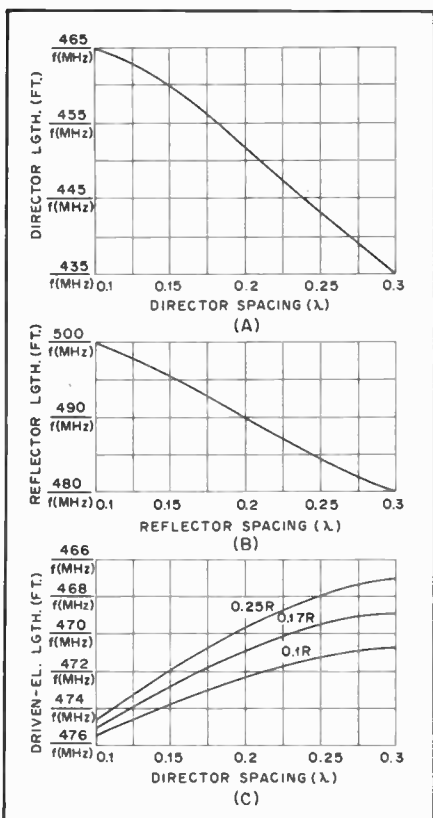
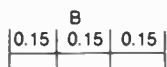


Fig. 41 — Element lengths for a three-element beam. These lengths will hold closely for tuning elements supported at or near the center.

Table 1

Freq.	Driven Element		Reflector		First Director		Second Director	
	A	B	A	B	A	B	A	B
14050	33' 5-3/8"	33' 8"	35' 2-1/2"	35' 5-1/4"	31' 9-3/8"	31' 11-5/8"	31' 1-1/4"	31' 3-5/8"
14250	32' 11-3/4"	33' 2-1/4"	34' 8-1/2"	34' 11-1/4"	31' 4"	31' 6-3/8"	30' 8"	30' 10-1/2"
21050	22' 4"	22' 5-5/8"	23' 6"	23' 7-3/4"	21' 2-1/2"	21' 4"	20' 9-1/8"	20' 10-7/8"
21300	22' 3/4"	22' 2-3/8"	23' 2-5/8"	23' 4-1/2"	20' 11-1/2"	21' 1"	20' 6-1/4"	20' 7-3/4"
28050	16' 9"	16' 10-1/4"	17' 7-5/8"	17' 8-7/8"	15' 11"	16'	15' 7"	15' 9-1/2"
28600	16' 5-1/4"	16' 6-3/8"	17' 3-1/2"	17' 4-3/4"	15' 7-1/4"	15' 8-1/2"	15' 3-3/8"	15' 4-1/2"

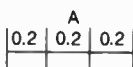

Element lengths for 20, 15 and 10 meters, phone and cw. These lengths are for 0.2 or 0.15 wavelength element spacing.

To convert ft to meters multiply ft  $\times$  0.3048.  
Convert in. to mm by multiplying in.  $\times$  25.4.

than 1/4-wavelength element spacing) arrays preferably should be made of tubing of 1/2 to 1 inch (13 to 25-mm) diameter. A conductor of large diameter not only has less ohmic resistance but also has lower Q; both these factors are important in close-spaced arrays because the impedance of the driven element usually is quite low compared to that of a simple dipole antenna. With three- and four-element close-spaced arrays the radiation resistance of the driven element may be so low that ohmic losses in the conductor can consume an appreciable fraction of the power.

### Feeding the Rotary Beam

Any of the usual methods of feed (described later under "Matching the Antenna to the Line") can be applied to

the driven element of a rotary beam. The popular choices for feeding a beam are the gamma match with series capacitor and the T match with series capacitors and a half-wavelength phasing section, as shown in Fig. 42. These methods are preferred over any others because they permit adjustment of the matching and the use of coaxial-line feed. The variable capacitors can be housed in small plastic cups for weatherproofing; receiving types with close spacing can be used at powers up to a few hundred watts. Maximum capacitance required is usually 140 pF at 14 MHz and proportionately less at the higher frequencies.

If physically possible, it is better to adjust the matching device after the antenna has been installed at its ultimate height, since a match made with the antenna near the ground may not hold for the same antenna in the air.

### Sharpness of Resonance

Peak performance of a multielement parasitic array depends upon proper phasing or tuning of the elements, which can be exact for one frequency only. In the case of close-spaced arrays, which because of the low radiation resistance, usually are quite sharp-tuning, the frequency range over which optimum results can be secured is only of the order of one or two percent of the resonant frequency, or up to about 500 kHz at 28 MHz. However, the antenna can be made to work satisfactorily over a wider frequency range by adjusting the director or directors to give maximum gain at the *highest* frequency to be covered, and by adjusting the reflector to give optimum gain at the

lowest frequency. This sacrifices some gain at all frequencies, but maintains more uniform gain over a wider frequency range.

The use of large-diameter conductors will broaden the response curve of an array because the larger diameter lowers the Q. This causes the reactances of the elements to change rather slowly with frequency, with the result that the tuning stays near the optimum over a considerably wider frequency range than is the case with wire conductors.

### Combination Arrays

It is possible to combine parasitic elements with driven elements to form arrays composed of collinear driven and parasitic elements and combination broadside-collinear-parasitic elements. Thus, two or more collinear elements might be provided with a collinear reflector or director set, one parasitic element to each driven element. Or, both directors and reflectors might be used. A broadside-collinear array can be treated in the same fashion.

### Delta Loops and Quad Beams

One of the more effective DX arrays is called the "cubical quad" or, simply, "quad" antenna. It consists of two or more square loops of wire, each supported by a bamboo or fiberglass cross-arm assembly. The loops are a quarter wavelength per side (full wavelength overall) one loop being driven, and the other serving as a parasitic element — usually a reflector. A variation of the quad is called the delta loop. The electrical properties of both antennas are

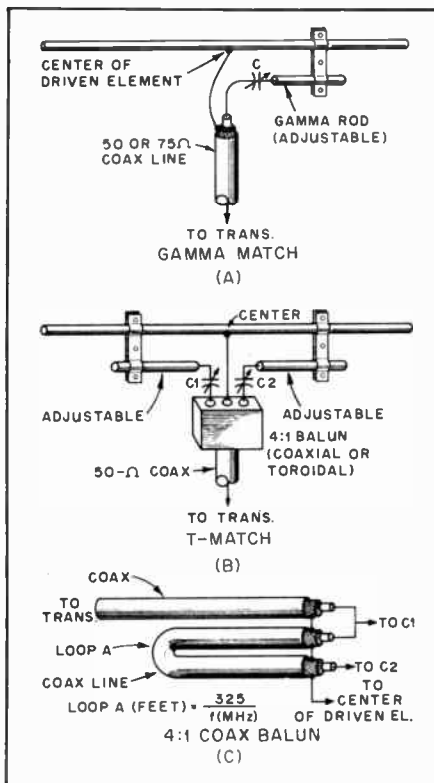


Fig. 42 — Illustrations of gamma and T-matching systems. At A, the gamma rod is adjusted along with C until the lowest SWR is obtained. A T-match is shown at B. It is the same as two gamma-match rods. The rods and C1 and C2 are adjusted alternately for a 1:1 SWR. A coaxial 4:1 balun transformer is shown at C. A toroidal balun can be used in place of the coax model shown. The toroidal version has a broader frequency range than the coaxial one. The T-match is adjusted for 200 ohms and the balun steps this *balanced* value down to 50 ohms, *unbalanced*. Or, the T-match can be set for 300 ohms, and the balun used to step this down to 75 ohms, unbalanced. Dimensions for the gamma and T-match rods are not given by formula. Their lengths and spacing will depend upon the tubing size used, and the spacing of the parasitic elements of the beam. Capacitors C, C1 and C2 can be 140 pF for 14-MHz beams. Somewhat less capacitance will be needed at 21 and 28 MHz.

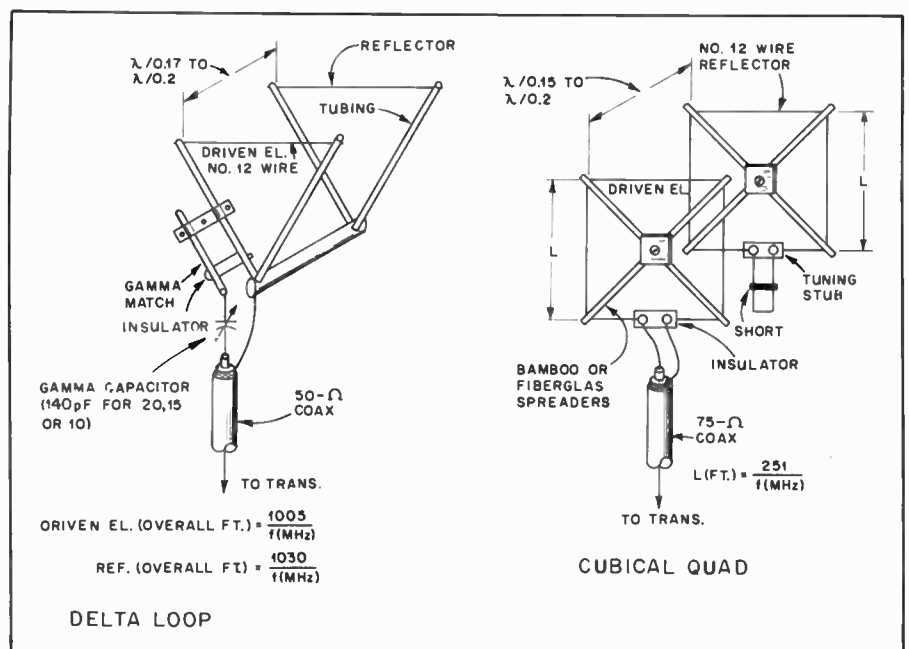


Fig. 43 — Information on building a quad or a delta-loop antenna. The antennas are electrically similar, but the delta-loop uses "plumber's delight" construction.



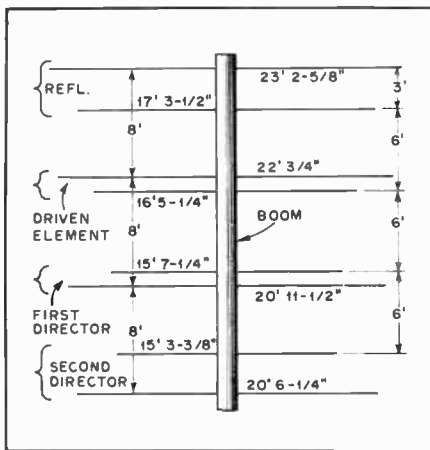


Fig. 45 — The element lengths shown are for the phone sections of the bands. Table 1 provides the dimensions for cw frequencies.

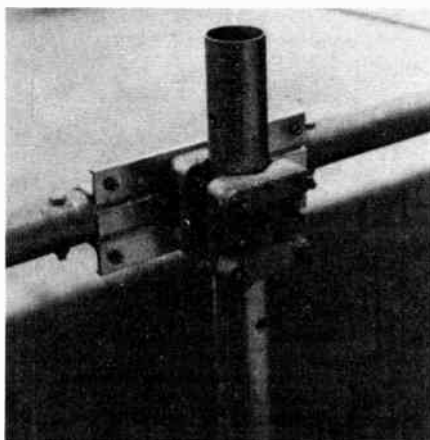


Fig. 46 — The boom-to-mast fixture that holds the two 12-foot boom sections together. The unit is made by Hy-Gain Electronics.

the same, generally speaking, though some operators report better DX results with the delta loop. Both antennas are shown in Fig. 43. They differ mainly in their physical properties, one being of plumber's delight construction, while the other uses insulating support members. One or more directors can be added to either antenna if additional gain and directivity is desired, though most operators use the two-element arrangement.

It is possible to interlace quads or "deltas" for two or more bands, but if this is done the formulas given in Fig. 43 may have to be changed slightly to compensate for the proximity effect of the second antenna. For quads the length of the full-wave loop can be computed from

$$\text{Full-wave loop (ft)} = \frac{1005}{f(\text{MHz})}$$

$$\text{Full-wave loop (m)} = \frac{306}{f(\text{MHz})}$$

If multiple arrays are used, each antenna should be tuned up separately for maximum forward gain as noted on a

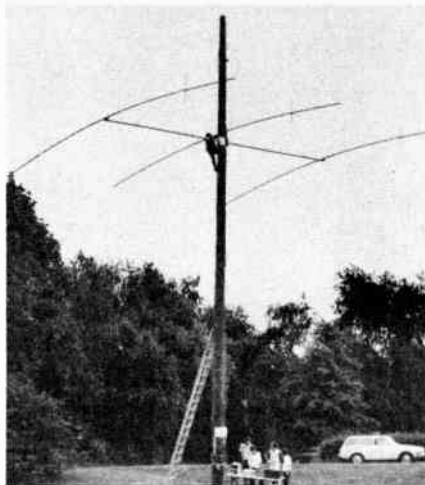


Fig. 47 — The shortened 40-meter Yagi beam closely approximates the size of a standard 20-meter Yagi. It is shown on a 60-foot (18-m) telephone pole.

field-strength meter. The reflector stub on the quad should be adjusted for the foregoing condition. The delta loop gamma match should be adjusted for a 1:1 SWR. No reflector tuning is needed. The delta loop antenna has a broader frequency response than the quad, and holds at an SWR of 1.5:1 or better across the band it is cut for.

The resonance of the quad antenna can be found by checking the frequency at which the lowest SWR occurs. The element length (driven element) can be adjusted for resonance in the most-used portion of the band by lengthening or shortening it.

A two-element quad or delta loop antenna compares favorably with a three-element Yagi array in terms of gain (see *QST*, May, 1963 and January, 1969, for additional information). The quad and delta-loop antennas perform very well at 50 and 144 MHz. A discussion of radiation patterns and gain, quads vs. Yagis, was presented by Lindsay in May 1968 *QST*.

#### An Optimum-Gain Two-Band Yagi Array

If optimum performance is desired from a Yagi, the dual four-element array shown in Fig. 45 will be of interest. This antenna consists of four elements on 15 meters interlaced with the same number for 10. Wide spacing is used, providing excellent gain and good bandwidth on both bands. Each driven element is fed separately with 50-ohm coax; gamma-matching systems are employed. If desired, a single feed line can be run to the array and then switched by a remotely controlled relay.

The element lengths shown in Fig. 45 are for the phone portions of the band, centered at 21,300 and 28,600 kHz. If desired, the element lengths can be changed for cw operation, using the dimensions given in Table 1. The spacing

of the elements will remain the same for both phone and cw.

#### Construction Details

The elements are supported by commercially made U-bolt assemblies. Muffler clamps also make excellent element supports. The boom-to-mast support is also a manufactured item that is designed to hold a 2-inch (51-mm) diameter boom and that can be used with mast sizes up to 2-1/2 inches (63.5 mm) in diameter. Another feature of this device is that it permits the beam to be tilted after it is mounted in place on the tower, providing access to the elements if they need to be adjusted once the beam has been mounted on the tower.

The elements are made from 6061-T6 aluminum tubing, which is available from metal suppliers. The tubing comes in 12-foot (3.66-m) lengths and can be purchased in telescoping sizes. The center sections of the 15-meter beam elements are 1-inch (25-mm) outside diameter and the 10-meter sections are 3/4-inch (19 mm). The ends of the tubing are slit with a hack saw, and hose clamps are used to hold the telescoping portions.

#### A Small Yagi for 40 Meters

A 7-MHz antenna for most amateur installations consists of a half-wavelength dipole attached between two convenient supports and fed power at the center with coaxial cable. When antenna gain is a requirement on this frequency, the dimensions of the system can become overwhelming. A full-size three-element Yagi typically would have 68-foot (20.7-m) elements and a 36-foot (10.9-m) boom. Accordingly, half-size elements present some distinct mechanical as well as economical advantages. Reducing the spacing between elements is not recommended since it would severely restrict the bandwidth of operation and make the tuning critical. This array features good directivity and reasonable gain, yet the mechanical design allows the use of a "normal" heavy-duty rotator and a conventional tower support. Element loading is accomplished by lumped inductance and capacitance hats along the 38-foot (11.6-m) elements. This design concept can be applied on any of the amateur hf bands.

#### Construction

The system described here uses standard sizes and lengths of aluminum tubing available through most aluminum suppliers. For best mechanical and electrical performance, 6061-T6 alloy should be used. All three elements are the same length; the tuning of the inductor is slightly different on each element, however. The two parasitic elements are grounded at the center with the associated boom-to-element hardware. A helical hairpin match is used to provide a proper

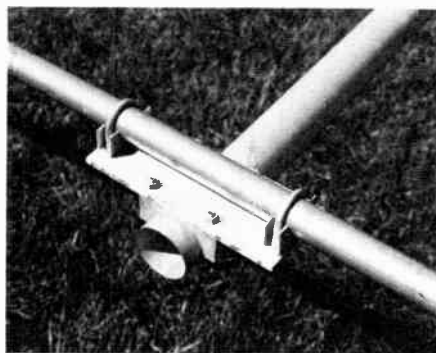


Fig. 48 — An aluminum plate and four automotive muffler clamps are used to affix the parasitic beam elements to the boom.

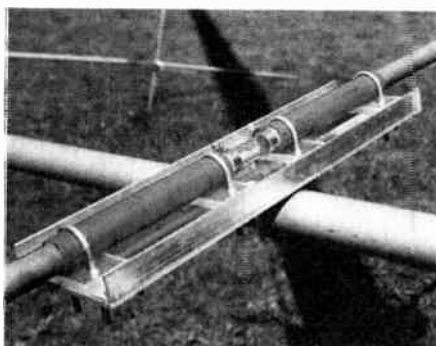


Fig. 49 — The driven element of the antenna is insulated from the boom by means of PVC tubing, as shown.

match to the split and insulated driven element. Two sections of steel angle stock are used to reinforce the driven-element mounting plate since the Plexiglas center insulating material is not rigid and element sag might otherwise result. The parasitic element center sections are continuous sections of aluminum tubing and additional support is not needed here. Figs. 48 and 49 show the details clearly.

The inductors for each element are wound on 1-1/8-inch (28-mm) diameter solid Plexiglas cast rod. Each end of the coil is secured in place with a solder lug and the Plexiglas is held in position with an automotive compression clamp. The total number of turns needed to resonate the elements correctly is given in Fig. 51. The capacitance hats consist of 1/2-inch (13-mm) tubing 3 feet (0.9 m) long (two pieces used) attached to the element directly next to the coil on each parasitic element and 2 inches (51 mm) away from the coil for the driven element. Complete details are given in Fig. 50.

The boom is constructed from three sections of aluminum tubing which measures 2-1/2 inches (63.5 mm) diameter and 12 feet (3.65 m) long. These pieces are joined together with inner tubes made from 2-1/4-inch (57 mm) stock shimmed with aluminum flashing. Long strips, approximately one inch wide, are wound on the inner tubing before it is placed

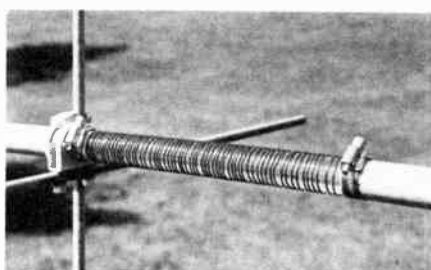


Fig. 50 — Each loading coil is wound on Plexiglas rod. The capacitance hats for the parasitic elements are mounted next to the coil, as shown here. The hose clamps compress the tubing against the Plexiglas rod. Each capacitance hat consists of two sections of tubing and associated muffler clamps.

Table 2

Quantity	Length (ft)	Diameter (in.)	Reynolds No.
2	8	1	9A
4	8	3/4	8A
1	8	1-1/4	10A
1	6	7/8	4231

2 U-bolts, TV antenna to mast type, 1 variable capacitor, 150 pF maximum, any type, 1 plastic freezer container, approximately 5 × 5 × 5 inches, to house gamma capacitor.

Gamma rod, 3/8- to 1/2-inch diameter aluminum tubing, 36 inches long. (Aluminum curtain rod or similar.)

Rt × 0.3048 = m. In. × 25.4 = mm.

inside the boom sections. A pair of 3/8 × 3-1/2 inch (9.5 × 89 mm) steel bolts are placed at right angles to each other at every connection point to secure the boom. Caution: Do not overtighten the bolts since this will distort the tubing making it impossible to pull apart sections, should the need arise. It is much better to install locking nuts over the original ones to assure mechanical security.

The helical hairpin details are given in Fig. 52. Quarter-inch copper tubing is formed into seven turns approximately 4 inches long and 2-1/4 inches (102 mm) ID.

### Tuning and Matching

The builder is encouraged to carefully follow the dimensions given in Fig. 51. Tuning the elements with the aid of a dip oscillator has proved to be somewhat unreliable and accordingly, no resonant frequencies will be given.

The hairpin matching system may not resemble the usual form but its operation and adjustment are essentially the same. For a detailed explanation of this network see *The ARRL Antenna Book*, 13th edition. The driven element resonant frequency required for the hairpin match is determined by the placement of the capacitance hats with respect to the ends of the coils. Sliding the capacitance hats

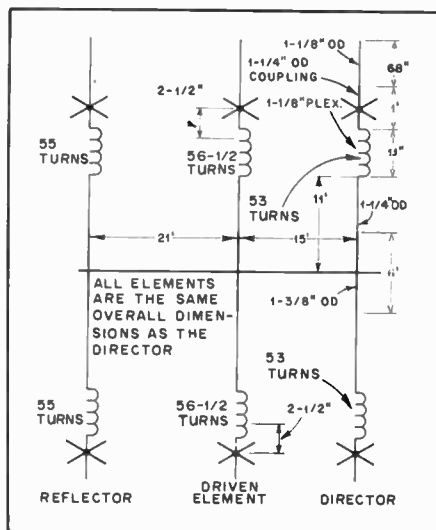


Fig. 51 — Mechanical details and dimensions for the 40-meter Yagi. Each of the elements uses the same dimensions; the difference is only the number of turns on the inductors and the placement of the capacitance hats. Feet × 0.3048 = m. Inches × 25.4 = mm. See the text for more details.

away from the ends of the coils increases the resonant frequency (capacitive reactance) of the element to cancel the effect of the hairpin inductive reactance. The model shown here had capacitance hats mounted 2-1/2 inches (63.5 mm) out from the ends of the coils (on the driven element only). An SWR indicator or wattmeter should be installed in series with the feed line at the antenna. The hairpin coil may be spread or compressed with an insulated tool (or by hand if power is removed!) to provide minimum reflected power at 7.050 MHz. The builder should not necessarily strive for a perfect match by changing the position of the capacitance hats since this may reduce the bandwidth of the matching system. An SWR of less than 2:1 was achieved across the entire 40-meter band with the antenna mounted atop an 80-foot tower.

The tuning of the array can be checked by making front-to-back ratio measurements across the band. With the dimensions given here, the best figures of front-to-back (approximately 25 to 30 dB) should be noticed in the cw portion of the band. Should the builder suspect the tuning is incorrect or if the antenna is mounted at some height greatly different than 80 feet (24.3 m) retuning of the elements may be necessary.

### Optimized Yagi Dimensions

Yagi beams for other amateur bands can be designed for effective performance by using the data compiled and published by P. Viezbicke in the National Bureau of Standards *Technical Note 688*, December, 1976. Table 3 provides the information needed to design Yagi antennas of various boom lengths and element numbers. This basic design criterion is valid over a large

**Table 3**

**Optimized lengths of parasitic elements for Yagi antennas of six different lengths.**

Lengths of Yagi in Wavelengths		0.4	0.8	1.20	2.2	3.2	4.2
Reflector Length ( $\lambda$ )		0.482	0.482	0.482	0.482	0.482	0.475
Director length, ( $\lambda$ )	1st	0.442	0.428	0.428	0.432	0.428	0.424
	2nd		0.424	0.420	0.415	0.420	0.424
	3rd		0.428	0.420	0.407	0.407	0.420
	4th			0.428	0.398	0.398	0.407
	5th				0.390	0.394	0.403
	6th				0.390	0.390	0.398
	7th				0.390	0.386	0.394
	8th				0.390	0.386	0.390
	9th				0.398	0.386	0.390
	10th				0.407	0.386	0.390
	11th					0.386	0.390
	12th					0.386	0.390
	13th					0.386	0.390
	14th					0.386	0.390
	15th					0.386	0.390
Spacing between directors ( $\lambda$ )		0.20	0.20	0.25	0.20	0.20	0.308
Gain relative to half-wave dipole in dB		7.1	9.2	10.2	12.25	13.4	14.2

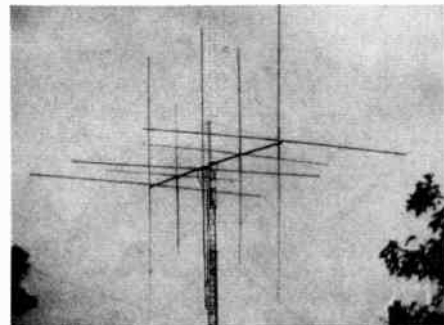


Fig. 53 — The assembled and installed three-band cubical-quad beam antenna.

to support the three-element 20-meter, four-element 15-meter, and five-element 10-meter wire-loop system. The spacing between elements has been chosen to provide optimum performance consistent with boom length and mechanical construction. Each of the parasitic loops is closed (ends soldered together) and requires no tuning. All of the loop sizes are listed in Table 4 and are designed for a center frequency of 14.1, 21.1 and 28.3 MHz. Since quad antennas are rather broad-tuning devices excellent performance is achieved in both cw and ssb band segments of each band (with the possible exception of the very high end of 10 meters). Changing the dimensions to favor a frequency 200 kHz higher in each band to create a "phone" antenna is not necessary.

One question which comes up quite often is whether to mount the loops in a diamond or a square configuration. In other words, should one spreader be horizontal to the earth, or should the wire be horizontal to the ground (spreaders mounted in the fashion of an X)? From the electrical point of view, it is probably a trade-off. While the square configuration has its lowest point higher above ground than a diamond version (which may lower the angle of radiation slightly), the top is also lower than that of a diamond shaped array. Some authorities indicate that separation of the current points in the diamond system gives slightly more gain than is possible with a square layout. It should be pointed out, however, that there never has been any substantial proof in favor of one or the other, electrically.

Spreader supports (sometimes called spiders) are available from many different manufacturers. If the builder is keeping the cost at a minimum, he should consider building his own. The expense is about half that of a commercially manufactured equivalent and, according to some authorities, the homemade arm supports described below are less likely to rotate on the boom as a result of wind pressure.

A 3-foot (0.9-m) long section of 1-inch (25-mm)-per-side steel angle stock is used to interconnect the pairs of spreader arms. The steel is drilled at the center to accept a muffler clamp of sufficient size to clamp

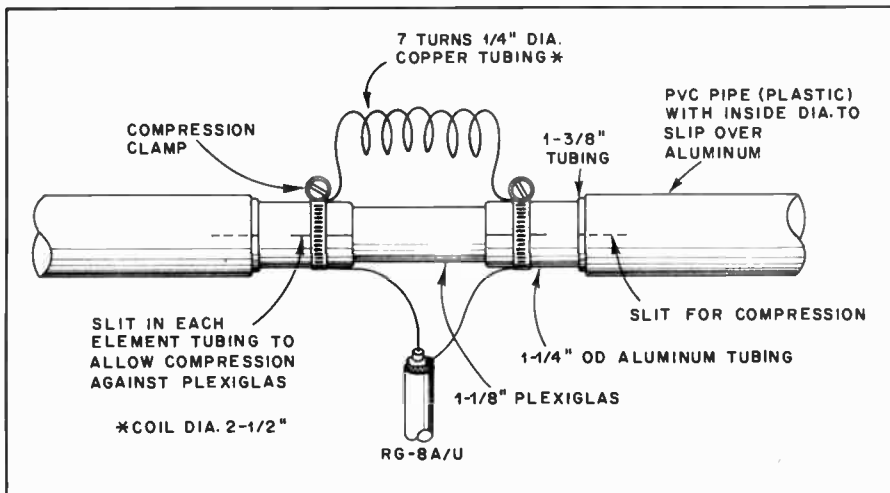


Fig. 52 — Details of the hairpin matching network on the driven element. See Fig. 51 for metric conversion.

**Table 4**  
**Three-Band Quad Loop Dimensions**

Band	Reflector	Driven Element	First Director	Second Director	Third Director
20 meters	(A) 72'8"	(B) 71'3"	(C) 69'6"	—	—
15 meters	(D) 48'6 1/2"	(E) 47'7 1/2"	(F) 46'5"	(G) 46'5"	—
10 meters	(H) 36' 2 1/2"	(I) 35'6"	(J) 34'7"	(K) 34'7"	(L) 34'7"

Letters indicate loops identified in Fig. 54. Feet  $\times$  0.3048 = m. Inches  $\times$  25.4 = mm.

range of frequencies, provided the element diameter to wavelength ratio,  $d/\lambda$ , is contained within the limits indicated in the table. The data were compiled at a frequency of 400 MHz. Element diameter factor is 0.0085 and the reflector was spaced 0.2 wavelength behind the driven element. (This information is provided through the courtesy of the U.S. Department of Commerce/NBS.)

**A Three-Band Quad Antenna System**

Quads have been popular with ama-

teurs during the past few decades because of their light weight, relatively small turning radius, and their unique ability to provide good DX performance when mounted close to the earth. A two-element three-band quad, for instance, with the elements mounted only 35 feet (10.7 m) above the ground, will give good performance in situations where a triband Yagi will not. Fig. 53 shows a large quad antenna which can be used as a basis for design for either smaller or larger arrays.

Five sets of element spreaders are used



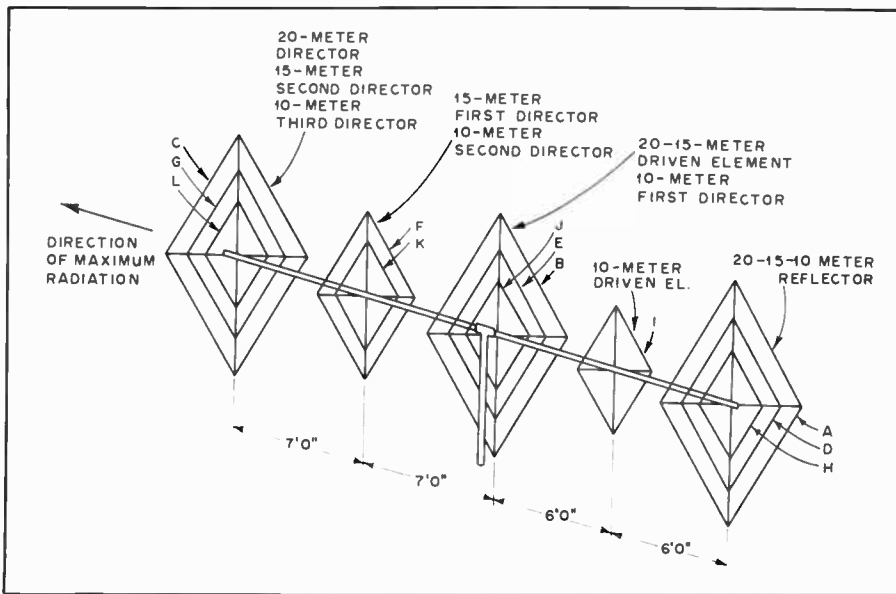


Fig. 54 — Dimensions of the three-band cubical quad. See Table 4 for the dimensions of the lettered wires. Note: Feet  $\times$  0.3048 = meters.

the assembly to the boom. The fiberglass is attached to the steel angle stock with automotive hose clamps, two per pole. Each quad-loop spreader frame consists of two assemblies of the type shown in Fig. 55.

#### Assorted Antenna Data

The question often arises concerning which type of wire is best for building antennas. Perhaps the major considerations are the conductivity of the wire, strength of the conductor and immunity to corrosion. With respect to conductivity, copper (solid or stranded) is excellent. The wire size should be great enough to withstand the strain of the span under conditions of wind and ice. Generally, no. 12 or 14 gauge is suitable for spans up to 150 feet (51 m). Soft-drawn copper is not especially good for the application because the weight of the wire will stretch it, causing sag and a change in resonant frequency. Hard-drawn copper is better and Copperweld (steel-core copper wire) is best, particularly for lengths in excess of 150 feet. Aluminum wire is also suitable if one is able to make good electrical connections to it. However, aluminum will tend to corrode quickly in areas where chemical pollution and salt air are common. Aluminum will also crystalize and break under continual stress from the wind.

To minimize the effects of the natural elements on an antenna, enamel or Formvar insulation is suggested. The insulation will have no apparent effect on the performance of the wire antenna in the hf bands. Plastic-covered wire has also been used with good results.

#### Beam-Antenna Elements

Most Yagi antennas are made from

sections of aluminum tubing which has been extruded or drawn. Compromise beams have been fashioned from less-expensive materials such as electrical conduit (iron) or bamboo poles wrapped with conductive tape or aluminum foil. The iron conduit is heavy, a poor conductor and is subject to rust. Therefore, it is best suited to experimental antennas or emergency use. Similarly, bamboo with conducting material affixed to it will deteriorate rapidly when exposed to the natural elements for a period of time. For the foregoing reasons it is wise to use aluminum tubing for Yagi elements and booms.

Table 5 lists standard sizes of aluminum round tubing stocked by most dealers in the USA and Canada. All of the tubing comes in 12-foot (3.65-m) lengths. Also, any specified diameter of tubing will fit inside the next larger size, provided the larger of the two has a 0.058-inch (1.47 mm) wall thickness. The 6061-T6 type of tubing in Table 5 has high strength and is easy to work with. It is highly resistant to corrosion and will bend without taking a "set." Check the local telephone directory for the nearest dealer.

#### Transmission Lines

Each type of line has a characteristic *velocity factor*, owing to the insulating-material properties. The velocity factor must be taken into account when cutting a transmission line to a specific part of a wavelength — such as with a quarter-wavelength transformer. For example, if RG-8A/U were employed to make a quarter-wavelength line at 3.5 MHz, the line dimension should be  $234/f(\text{MHz}) \times 0.66$ . Thus, the line would be 44.1 feet (13.44 m) long instead of the free-space length of 66.85 feet (20.37 m). Table 6

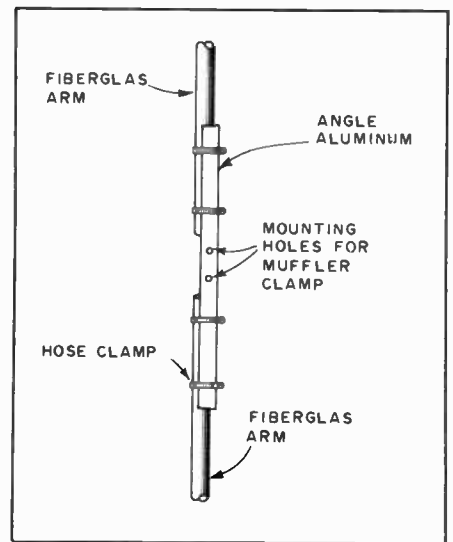


Fig. 55 — Details of one of two assemblies for a spreader frame. The two assemblies are jointed to form an X with a muffer clamp mounted at the position shown.

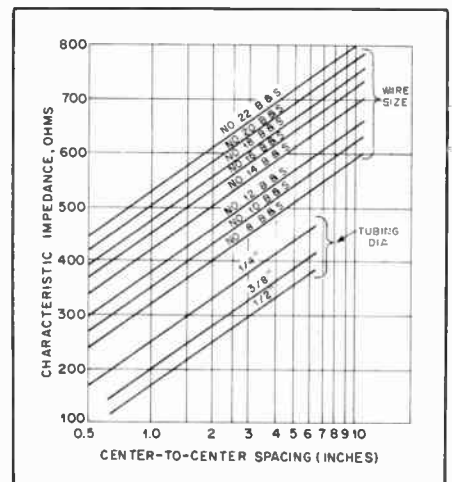


Fig. 56 — Chart showing the characteristic impedance of spaced-conductor parallel transmission lines with air dielectric. Tubing sizes given are for outside diameters.

shows various velocity factors for the transmission lines used by amateurs. Open-wire line has no appreciable velocity factor because it lacks a substantial amount of insulating material. Conversely, molded 300-ohm TV line has a velocity factor of 0.80 to 0.82. The higher cost of the larger coaxial lines is often worth the expenditure in terms of reduced feeder losses.

Amateurs can construct their own parallel transmission lines by following the chart contained in Fig. 56. When using wire conductors it is an easy matter to fabricate open-wire feed lines. Spacers made of high-dielectric material need to be affixed to the conductors at appropriate distances apart to maintain the spacing between the wires (constant impedance) and to prevent shorting of the conductors.

**Table 5**

**6061-T6 (61S-T6) Round Aluminum Tube  
In 12-Foot Lengths**

OD Wall Thickness				Approx. Weight		In 12-Foot Lengths				Approx. Weight	
Inches	Inches	Stubs Ga.	ID Inches	Per Foot	Per Length	Inches	Inches	Stubs Ga.	ID Inches	Per Foot	Per Length
3/16"	0.035	(no. 20)	0.117	0.019 lbs.	0.228 lbs.	1"	0.083	(no. 14)	0.834	0.281 lbs.	3.372 lbs.
	0.049	(no. 18)	0.089	0.025 lbs.	0.330 lbs.	1 1/8"	0.035	(no. 20)	1.055	0.139 lbs.	1.668 lbs.
1/4"	0.035	(no. 20)	0.180	0.027 lbs.	0.324 lbs.		0.058	(no. 17)	1.009	0.228 lbs.	2.736 lbs.
	0.049	(no. 18)	0.152	0.036 lbs.	0.432 lbs.	1 1/4"	0.035	(no. 20)	1.180	0.155 lbs.	1.860 lbs.
5/16"	0.035	(no. 20)	0.242	0.036 lbs.	0.423 lbs.		0.049	(no. 18)	1.152	0.210 lbs.	2.520 lbs.
	0.049	(no. 18)	0.214	0.047 lbs.	0.564 lbs.		0.058	(no. 17)	1.134	0.256 lbs.	3.072 lbs.
	0.058	(no. 17)	0.196	0.055 lbs.	0.660 lbs.		0.065	(no. 16)	1.120	0.284 lbs.	3.408 lbs.
3/8"	0.035	(no. 20)	0.305	0.043 lbs.	0.516 lbs.		0.083	(no. 14)	1.084	0.357 lbs.	4.284 lbs.
	0.049	(no. 18)	0.277	0.060 lbs.	0.720 lbs.	1 3/8"	0.035	(no. 20)	1.305	0.173 lbs.	2.076 lbs.
	0.058	(no. 17)	0.259	0.068 lbs.	0.816 lbs.		0.058	(no. 17)	1.259	0.282 lbs.	3.384 lbs.
	0.065	(no. 16)	0.245	0.074 lbs.	0.888 lbs.	1 1/2"	0.035	(no. 20)	1.430	0.180 lbs.	2.160 lbs.
7/16"	0.035	(no. 20)	0.367	0.051 lbs.	0.612 lbs.		0.049	(no. 18)	1.402	0.260 lbs.	3.120 lbs.
	0.049	(no. 18)	0.339	0.070 lbs.	0.840 lbs.		0.058	(no. 17)	1.384	0.309 lbs.	3.708 lbs.
	0.065	(no. 16)	0.307	0.089 lbs.	1.068 lbs.		0.065	(no. 16)	1.370	0.344 lbs.	4.128 lbs.
1/2"	0.028	(no. 22)	0.444	0.049 lbs.	0.588 lbs.		0.083	(no. 14)	1.334	0.434 lbs.	5.208 lbs.
	0.035	(no. 20)	0.430	0.059 lbs.	0.708 lbs.		*0.125	1/8"	1.250	0.630 lbs.	7.416 lbs.
	0.049	(no. 18)	0.402	0.082 lbs.	0.984 lbs.		*0.250	1/4"	1.000	1.150 lbs.	14.832 lbs.
	0.058	(no. 17)	0.384	0.095 lbs.	1.040 lbs.	1 5/8"	0.035	(no. 20)	1.555	0.206 lbs.	2.472 lbs.
	0.065	(no. 16)	0.370	0.107 lbs.	1.284 lbs.		0.058	(no. 17)	1.509	0.336 lbs.	4.032 lbs.
5/8"	0.028	(no. 22)	0.569	0.061 lbs.	0.732 lbs.	1 3/4"	0.058	(no. 17)	1.634	0.363 lbs.	4.668 lbs.
	0.035	(no. 20)	0.555	0.075 lbs.	0.900 lbs.		0.083	(no. 14)	1.584	0.510 lbs.	6.120 lbs.
	0.049	(no. 18)	0.527	0.106 lbs.	1.272 lbs.	1 7/8"	0.058	(no. 17)	1.759	0.389 lbs.	4.356 lbs.
	0.058	(no. 17)	0.509	0.121 lbs.	1.452 lbs.	2"	0.049	(no. 18)	1.902	0.350 lbs.	4.200 lbs.
	0.065	(no. 16)	0.495	0.137 lbs.	1.644 lbs.		0.065	(no. 16)	1.870	0.450 lbs.	5.400 lbs.
3/4"	0.035	(no. 20)	0.680	0.091 lbs.	1.092 lbs.		0.083	(no. 14)	1.834	0.590 lbs.	7.080 lbs.
	0.049	(no. 18)	0.652	0.125 lbs.	1.500 lbs.		*0.125	1/8"	1.750	0.870 lbs.	9.960 lbs.
	0.058	(no. 17)	0.634	0.148 lbs.	1.776 lbs.		*0.250	1/4"	1.500	1.620 lbs.	19.920 lbs.
	0.065	(no. 16)	0.620	0.160 lbs.	1.920 lbs.	2 1/4"	0.049	(no. 18)	2.152	0.398 lbs.	4.776 lbs.
	0.083	(no. 14)	0.584	0.204 lbs.	2.448 lbs.		0.065	(no. 16)	2.120	0.520 lbs.	6.240 lbs.
7/8"	0.035	(no. 20)	0.805	0.108 lbs.	1.308 lbs.		0.083	(no. 14)	2.084	0.660 lbs.	7.920 lbs.
	0.049	(no. 18)	0.777	0.151 lbs.	1.810 lbs.	2 1/2"	0.065	(no. 16)	2.370	0.587 lbs.	7.044 lbs.
	0.058	(no. 17)	0.759	0.175 lbs.	2.100 lbs.		0.083	(no. 14)	2.334	0.740 lbs.	8.880 lbs.
	0.065	(no. 16)	0.745	0.199 lbs.	2.399 lbs.		*0.125	1/8"	2.250	1.100 lbs.	12.720 lbs.
1"	0.035	(no. 20)	0.930	0.123 lbs.	1.476 lbs.		*0.250	1/4"	2.000	2.080 lbs.	25.440 lbs.
	0.049	(no. 18)	0.902	0.170 lbs.	2.040 lbs.	3"	0.065	(no. 16)	2.870	0.710 lbs.	8.520 lbs.
	0.058	(no. 17)	0.884	0.202 lbs.	2.424 lbs.		*0.125	1/8"	2.700	1.330 lbs.	15.600 lbs.
	0.065	(no. 16)	0.870	0.220 lbs.	2.640 lbs.		*0.250	1/4"	2.500	2.540 lbs.	31.200 lbs.

\*These sizes are extruded. All other sizes are drawn tubes.  
Inches × 25.4 = mm.  
Pounds × 0.4536 = kilograms.

**Table 6**  
**Characteristics of Commonly Used Transmission Lines**

Type of Line	Z <sub>0</sub> Ohms	Vel. %	pF per ft.	OD	Attenuation in dB per 100 feet							
					3.5	7	14	21	28	50	144	420
RG-58A/U	53	66	28.5	0.195	0.68	1.0	1.5	1.9	2.2	3.1	5.7	10.4
RG-58/U Foam Diel.	50	79	25.4	0.195	0.52	0.8	1.1	1.4	1.7	2.2	4.1	7.1
RG-59A/U	73	66	21.0	0.242	0.64	0.90	1.3	1.6	1.8	2.4	4.2	7.2
RG-59/U Foam Diel.	75	79	16.9	0.242	0.48	0.70	1.0	1.2	1.4	2.0	3.4	6.1
RG-8A/U	52	66	29.5	0.405	0.30	0.45	0.66	0.83	0.98	1.35	2.5	4.8
RG-8/U Foam Diel.	50	80	25.4	0.405	0.27	0.44	0.62	0.76	0.90	1.2	2.2	3.9
RG-11A/U	75	66	20.5	0.405	0.38	0.55	0.80	0.98	1.15	1.55	2.8	4.9
Aluminum Jacket, Foam Diel. <sup>1</sup>												
3/8 inch	50	81	25.0	—	—	—	0.36	0.48	0.54	0.75	1.3	2.5
1/2 inch	50	81	25.0	—	—	—	0.27	0.35	0.40	0.55	1.0	1.8
3/8 inch	75	81	16.7	—	—	—	0.43	0.51	0.60	0.80	1.4	2.6
1/2 inch	75	81	16.7	—	—	—	0.34	0.40	0.48	0.60	1.2	1.9
Open-wire <sup>2</sup>	—	97	—	—	0.03	0.05	0.07	0.08	0.10	0.13	0.25	—
300-ohm Twin-lead	300	82	5.8	—	0.18	0.28	0.41	0.52	0.60	0.85	1.55	2.8
300-ohm tubular	300	80	4.6	—	0.07	0.25	0.39	0.48	0.53	0.75	1.3	1.9
Open-wire, TV type												
1/2 inch	400	95	—	—	0.028	0.05	0.09	0.13	0.17	0.30	0.75	—
1 inch	450	95	—	—	0.028	0.05	0.09	0.13	0.17	0.30	0.75	—

<sup>1</sup>Polyfoam dielectric type line information courtesy of Times Wire and Cable Co.  
<sup>2</sup>Attenuation of open-wire based on no. 12 conductors, neglecting radiation.  
Feet × 0.3048 = m. Inches × 25.4 = mm.

# VHF and UHF Antennas

Improving his antenna system is one of the most productive moves open to the vhf enthusiast. It can increase transmitting range, improve reception, reduce interference problems, and bring other practical benefits. The work itself is by no means the least attractive part of the job. Even with high-gain antennas, experimentation is greatly simplified at vhf and uhf because an array is a workable size, and much can be learned about the nature and adjustment of antennas. No large investment in test equipment is necessary.

Whether we buy or build our antennas, we soon find that there is no one "best" design for all purposes. Selecting the antenna best suited to our needs involves much more than scanning gain figures and prices in a manufacturer's catalog. The first step should be to establish priorities.

### Objectives: *Gain*

Shaping the pattern of an antenna to concentrate radiated energy, or received-signal pickup, in some directions at the expense of others is the only way to develop gain. This is best explained by starting with the hypothetical *isotropic antenna*, which would radiate equally in all directions. A point source of light illuminating the inside of a globe uniformly, from its center, is a visual analogy. No practical antenna can do this, so all antennas have "gain over isotropic" (*dBi*). A half-wave dipole in free space has 2.1 dBi. If we can plot the radiation pattern of an antenna in all planes, we can compute its gain, so quoting it with respect to isotropic is a logical base for agreement and understanding. It is rarely possible to erect a half-wave antenna that has anything approaching a free-space pattern, and this fact is responsible for much of the confusion about true antenna gain.

Radiation patterns can be controlled in various ways. One is to use two or more driven elements, fed in phase. Such *collinear* arrays provide gain without markedly sharpening the frequency response, compared to that of a single element. More gain per element, but with

a sacrifice in frequency coverage, is obtained by placing *parasitic* elements, longer and shorter than the driven one, in the plane of the first element, but not driven from the feedline. The reflector and directors of a *Yagi* array are highly frequency sensitive and such an antenna is at its best over frequency changes of less than one percent of the operating frequency.

### *Frequency Response*

Ability to work over an entire vhf band may be important in some types of work. The response of an antenna element can be broadened somewhat by increasing the conductor diameter, and by tapering it to something approximating a cigar shape, but this is done mainly with simple antennas. More practically, wide frequency coverage may be a reason to select a collinear array, rather than a Yagi. On the other hand, the growing tendency to channelize operations in small segments of our bands tends to place broad frequency coverage low on the priority list of most vhf stations.

### *Radiation Pattern*

Antenna radiation can be made omnidirectional, bidirectional, practically unidirectional, or anything between these conditions. A vhf net operator may find an omnidirectional system almost a necessity, but it may be a poor choice otherwise. Noise pickup and other interference problems tend to be greater with such antennas, and those having some gain are especially bad in these respects. Maximum gain and low radiation angle are usually prime interests of the weak-signal DX aspirant. A clean pattern, with lowest possible pickup and radiation off the sides and back, may be important in high-activity areas, or where the noise level is high.

### *Height Gain*

In general, the higher the better in vhf antenna installations. If raising the antenna clears its view over nearby obstructions, it may make dramatic im-

provements in coverage. Within reason, greater height is almost always worth its cost, but height gain must be balanced against increased transmission-line loss. The latter is considerable, and it increases with frequency. The best available line may be none too good, if the run is long in terms of wavelength. Give line-loss information, shown in table form in chapter 19, close scrutiny in any antenna planning.

### *Physical Size*

A given antenna design for 432 MHz will have the same gain as one for 144 MHz, but being only one-third the size it will intercept only one-third as much energy in receiving. Thus, to be equal in communication effectiveness, the 432-MHz array should be at least equal in size to the 144-MHz one, which will require roughly three times as many elements. With all the extra difficulties involved in going higher in frequency, it is well to be on the big side in building an antenna for the higher bands.

### *Design Factors*

Having sorted out objectives in a general way, we face decisions on specifics, such as polarization, type of transmission line, matching methods and mechanical design.

### *Polarization*

Whether to position the antenna elements vertically or horizontally has been a moot point since early vhf pioneering. Tests show little evidence on which to set up a uniform polarization policy. On long paths there is no consistent advantage, either way. Shorter paths tend to yield higher signal levels with horizontal in some kinds of terrain. Man-made noise, especially ignition interference, tends to be lower with horizontal. Verticals are markedly simpler to use in omnidirectional systems, and in mobile work.

Early vhf communication was largely vertical, but horizontal gained favor when directional arrays became widely used. The major trend to fm and repeaters,



particularly in the 144-MHz band, has tipped the balance in favor of verticals in mobile work and for repeaters. Horizontal predominates in other communication on 50 MHz and higher frequencies. It is well to check in advance in any new area in which you expect to operate, however, as some localities still use vertical almost exclusively. A circuit loss of 20-dB or more can be expected with cross-polarization.

### Transmission Lines

There are two main categories of transmission lines: balanced and unbalanced. The former include open-wire lines separated by insulating spreaders, and twin-lead, in which the wires are embedded in solid or foamed insulation. Line losses result from ohmic resistance, radiation from the line and deficiencies in the insulation. Large conductors, closely spaced in terms of wavelength, and using a minimum of insulation, make the best balanced lines. Impedances are mainly 300 to 500 ohms. Balanced lines are best in straight runs. If bends are unavoidable, the angles should be as obtuse as possible. Care should be taken to prevent one wire from coming closer to metal objects than the other. Wire spacing should be less than  $1/20$  wavelength.

Properly built, open-wire line can operate with very low loss in vhf and even uhf installations. A total line loss under 2 dB per hundred feet at 432 MHz is readily obtained. A line made of no. 12 wire, spaced  $3/4$  inch (19 mm) or less with Teflon spreaders, and running essentially straight from antenna to station, can be better than anything but the most expensive coax, at a fraction of the cost. This assumes the use of baluns to match into and out of the line, with a short length of quality coax for the moving section from the top of the tower to the antenna. A similar 144-MHz setup could have a line loss under 1 dB.

Small coax such as RG-58/U or -59/U should never be used in vhf work if the run is more than a few feet. Half-inch (13-mm) lines (RG-8 or -11) work fairly well at 50 MHz, and are acceptable for 144-MHz runs of 50 feet or less. If these lines have foam rather than solid insulation they are about 30 percent better. Aluminum-jacket lines with large inner conductors and foam insulation are well worth their cost. They are readily waterproofed, and can last almost indefinitely. Beware of any "bargains" in coax for vhf or uhf uses. Lost transmitter power can be made up to some extent by increasing power, but once lost, a weak signal can never be recovered in the receiver.

Effects of weather should not be ignored. A well-constructed open-wire line works well in nearly any weather, and it stands up well. Twin-lead is almost useless in heavy rain, wet snow

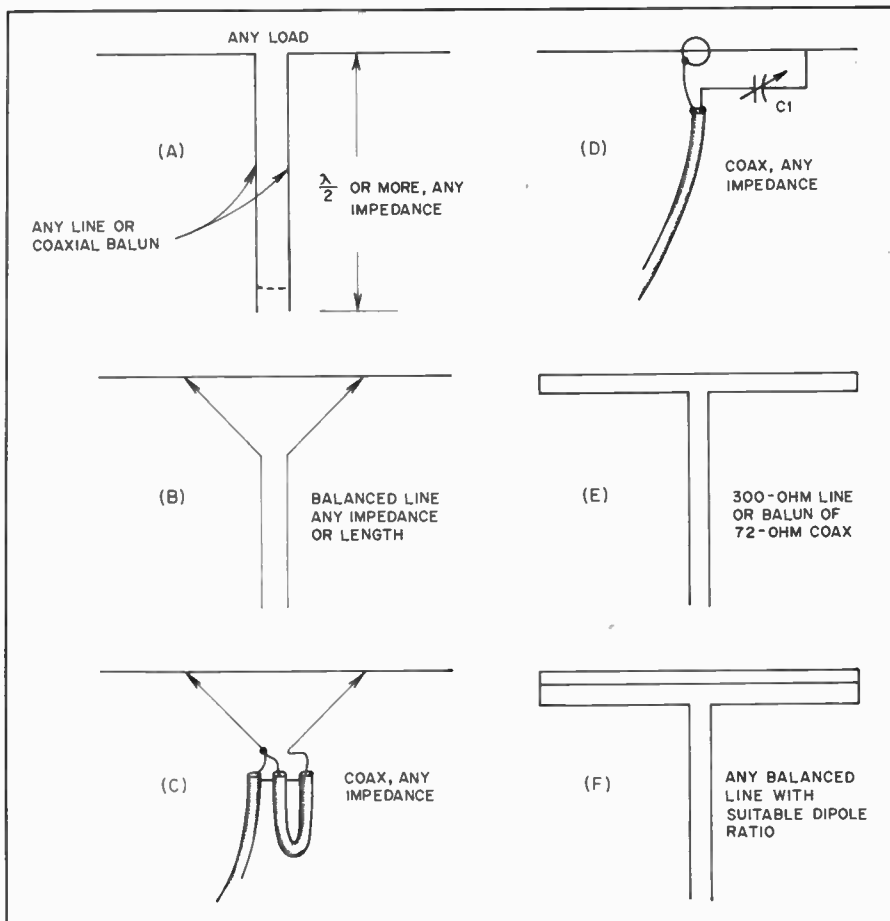


Fig. 1 — Matching methods commonly used in vhf antennas. The universal stub, A, combines tuning and matching. The adjustable short on the stub, and the points of connection of the transmission line, are adjusted for minimum reflected power in the line. In the delta match, B and C, the line is fanned out to tap on the dipole at the point of best impedance match. Impedances need not be known in A, B and C. The gamma-match, D, is for direct connection of coax. C.1 tunes out inductance in the arm. Folded dipole of uniform conductor size, E, steps up antenna impedance by a factor of four. Using a larger conductor in the unbroken portion of the folded dipole, E, gives higher orders of impedance transformation.

or icing. The best grades of coax are impervious to weather. They can be run underground, fastened to metal towers without insulation, or bent into any convenient position, with no adverse effects on performance.

### Impedance Matching

Theory and practice in impedance matching are given in detail in earlier chapters, and theory, at least, is the same for frequencies above 50 MHz. Practice may be similar, but physical size can be a major modifying factor in choice of methods. Only the matching devices used in practical construction examples later in this chapter will be discussed in detail here. This should not rule out consideration of other methods, however, and a reading of relevant portions of chapters 19 and 20 is recommended.

### Universal Stub

As its name implies, the double-adjustment stub of Fig. 1A is useful for many matching purposes. The stub length is varied to resonate the system,

and the transmission line and stub impedances are equal. In practice this involves moving both the sliding short and the point of line connection for zero reflected power, as indicated on an SWR bridge connected in the line.

The universal stub allows for tuning out any small reactance present in the driven part of the system. It permits matching the antenna to the line without knowledge of the actual impedances involved. The position of the short yielding the best match gives some indication of amount of reactance present. With little or no reactive component to be tuned out, the stub will be approximately a half-wavelength from load to short.

The stub should be stiff bare wire or rod, spaced no more than  $1/20$  wavelength. Preferably it should be mounted rigidly, on insulators. Once the position of the short is determined, the center of the short can be grounded, if desired, and the portion of the stub no longer needed can be removed.

It is not necessary that the stub be connected directly to the driven

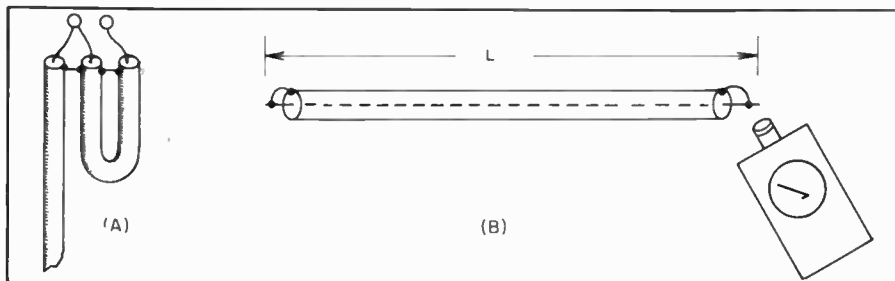


Fig. 2 — Conversion from unbalanced coax to a balanced load can be done with a half-wave coaxial balun, A. Electrical length of the looped section should be checked with a dip-meter, with ends shorted, B. The half-wave balun gives a 4:1 impedance step up.

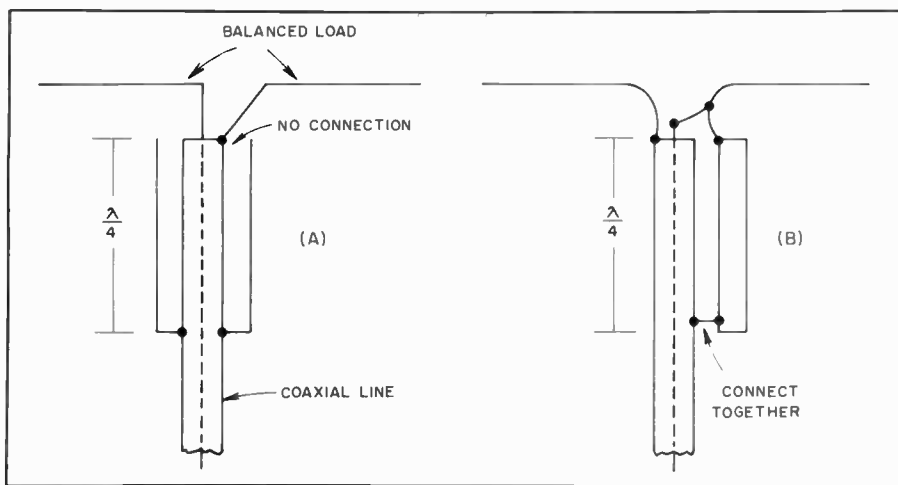


Fig. 3 — The balun conversion function, with no impedance change, is accomplished with quarter-wave lines, open at the top and connected to the coax outer conductor at the bottom. The coaxial sleeve, A, is preferred.

element. It can be made part of an open-wire line, as a device to match into or out of the line with coax. It can be connected to the lower end of a delta match, or placed at the feedpoint of a phased array. Examples of these uses are given later.

#### Delta Match

Probably the first impedance match was made when the ends of an open line were fanned out and tapped onto a half-wave antenna at the point of most efficient power transfer, as in Fig. 1B. Both the side length and the points of connection either side of the center of the element must be adjusted for minimum reflected power in the line, but as with the universal stub, the impedances need not be known. The delta makes no provision for tuning out reactance, so the universal stub is often used as a termination for it, to this end.

Once thought to be inferior for vhf applications because of its tendency to radiate if improperly adjusted, the delta has come back to favor, now that we have good methods for measuring the effects of matching. It is very handy for phasing multiple-bay arrays with open lines, and its dimensions in this use are not particularly critical. It should be

checked out carefully in applications like that of Fig. 1C, having no tuning device.

#### Gamma Match

An application of the same principle to direct connection of coax is the gamma match, Fig. 1D. There being no rf voltage at the center of a half-wave dipole, the outer conductor of the coax is connected to the element at this point, which may also be the junction with a metallic or wooden boom. The inner conductor, carrying the rf current, is tapped out on the element at the matching point. Inductance of the arm is tuned out by means of C1, resulting in electrical balance. Both the point of contact with the element and the setting of the capacitor are adjusted for zero reflected power, with a bridge connected in the coaxial line.

The capacitor can be made variable temporarily, then replaced with a suitable fixed unit when the required capacitance value is found, or C1 can be mounted in a waterproof box. Maximum should be about 100 pF for 50 MHz and 35 to 50 pF for 144. The capacitor and arm can be combined in one coaxial assembly, with the arm connecting to the driven element by

means of a sliding clamp, and the inner end of the arm sliding inside a sleeve connected to the inner conductor of the coax. A commercially supplied assembly of this type is used in a 50-MHz array described later, or one can be constructed from concentric pieces of tubing, insulated by plastic sleeving. Rf voltage across the capacitor is low, once the match is adjusted properly, so with a good dielectric, insulation presents no great problem, if the initial adjustment is made with low power level. A clean, permanent high-conductivity bond between arm and element is important, as the rf current is high at this point.

#### Folded Dipole

The impedance of a half-wave antenna broken at its center is 72 ohms. If a single conductor of uniform size is folded to make a half-wave dipole as shown in Fig. 1E, the impedance is stepped up four times. Such a folded dipole can thus be fed directly with 300-ohm line with no appreciable mismatch. Coaxial line of 70 to 75 ohms impedance may also be used if a 4:1 balun is added. (See balun information presented later in this chapter.) Higher impedance step up can be obtained if the unbroken portion is made larger in cross-section than the fed portion, as in Fig. 1F. For design information, see chapter 19.

#### Baluns and Transmatches

Conversion from balanced loads to unbalanced lines, or vice versa, can be performed with electrical circuits, or their equivalents made of coaxial line. A balun made from flexible coax is shown in Fig. 2A. The looped portion is an electrical half-wavelength. The physical length depends on the propagation factor of the line used, so it is well to check its resonant frequency, as shown at B. The two ends are shorted, and the loop at one end is coupled to a dip-meter coil. This type of balun gives an impedance stepup of 4:1 in impedance, 50 to 200 ohms, or 75 to 300 ohms, typically.

Coaxial baluns giving 1:1 impedance transfer are shown in Fig. 3. The coaxial sleeve, open at the top and connected to the outer conductor of the line at the lower end (A) is the preferred type. A conductor of approximately the same size as the line is used with the outer conductor to form a quarter-wave stub, in B. Another piece of coax, using only the outer conductor, will serve this purpose. Both baluns are intended to present an infinite impedance to any rf current that might otherwise tend to flow on the outer conductor of the coax.

The functions of the balun and the impedance transformer can be handled by various tuned circuits. Such a

**Table 1**

**Dimensions for VHF Arrays in Inches**

Freq. (MHz)*	50*	144*	220*	432*
Driven element	111	38-5/8	25-7/16	13
Change per MHz	2	1/4	1/8	1/32
Reflector	116-1/2	40-1/2	26-3/4	13-1/2
1st director	105-1/2	36-5/8	24-1/8	12-11/32
2nd director	103-1/2	36-3/8	24	12-9/32
3rd director	101-1/2	36-1/8	23-7/8	12-7/32
1.0 wavelength	236	81-1/2	53-5/8	27-1/4
0.625 wavelength	149	51	33-1/2	17
0.5 wavelength	118	40-3/4	26-13/16	13-5/8
0.25 wavelength	59	20-3/8	13-7/8	6-13/16
0.2 wavelength	47-3/4	16-1/4	10-3/4	5-7/16
0.15 wavelength	35-1/2	12-1/4	8	4
Inches × 25.4 = mm				

\*Dimensions are for the most-used section of each band: 50 to 50.6 MHz, 144 to 145.5 MHz, 220 to 222 MHz, and 432 to 434 MHz. The element lengths should be adjusted for each megahertz difference in frequency by the amount given in the third line of the table. Example: If optimum performance is wanted much above 145 MHz, shorten all elements by about 1/4 inch. For above 146 MHz, shorten by 1/2 inch. See text.

Element spacings are not critical, and table figures may be used, regardless of element lengths chosen. Parasitic element lengths are optimum for collinear arrays and small Yagis, having 0.2-wavelength spacing.

device, commonly called an antenna coupler or Transmatch, can provide a wide range of impedance transformations. Additional selectivity inherent to the Transmatch can reduce RFI problems.

**The Q Section**

The impedance transforming property of a quarter-wave line is treated in chapter 19. The parallel-bar Q section is not useful in low-impedance vhf matching situations, but Q sections of flexible coaxial line may be handy in phasing and matching vhf and uhf arrays. Such sections can be any odd multiple of a quarter-wavelength. An example of two 3/4-wave 75-ohm Q sections, used to phase and match a pair of Yagi bays, each of which has 50 ohms impedance, is given later in this chapter.

**Mechanical Design**

The small size of vhf and, especially, uhf arrays opens up a wide range of construction possibilities. Finding components is becoming difficult for home constructors of ham gear, but it should not hold back antenna work. Radio and TV distributors have many useful antenna parts and materials. Hardware stores, metals suppliers, lumber yards, welding-supply and plumbing-supply houses and even junkyards should not be overlooked. With a little imagination, the possibilities are endless.

**Wood or Metal?**

Wood is very useful in antenna work. It is available in a great variety of shapes and sizes. Rug poles of wood or bamboo make fine booms. Round wood stock (doweling) is found in many hardware stores in sizes suitable for small arrays. Square or rectangular boom and frame materials can be cut to order in most lumber yards if they are not available

from the racks in suitable sizes.

There is no rf voltage at the center of a half-wave dipole or parasitic element, so no insulation is required in mounting elements that are centered in the support, whether the latter is wood or metal. Wood is good for the framework of multibay arrays for the higher bands, as it keeps down the amount of metal in the active area of the array.

Wood used for antenna construction should be well-seasoned and free of knots or damage. Available materials vary, depending on local sources. Your lumber dealer can help you better than anyone else in choosing suitable materials. Joining wood members at right angles is often done advantageously with gusset plates. These can be of thin outdoor-grade plywood or Masonite. Round materials can be handled in ways similar to those used with metal components, with U clamps and with other hardware.

Metal booms have a small "shorting effect" on elements that run through them. With materials sizes commonly employed, this is not more than one percent of the element length, and may not be noticeable in many applications. It is just perceptible with 1/2-inch (13-mm) tubing booms used on 432 MHz, for example. Formula lengths can be used as given, if the matching is adjusted in the frequency range one expects to use. The center frequency of an all-metal array will tend to be 0.5 to 1 percent higher than a similar system built of wooden supporting members.

**Element Materials and Dimensions**

Antennas for 50 MHz need not have elements larger than 1/2-inch diameter, though up to 1 inch (25 mm) is used occasionally. At 144 and 220 MHz the elements are usually 1/8 to 1/4 inch (3 to 6 mm) in diameter. For 420, elements as small as 1/16 inch (1.6 mm) in diameter

work well, if made of stiff rod. Aluminum welding rod, 3/32 to 1/8 (2.4 to 3 mm) inch in diameter is fine for 420-MHz arrays, and 1/8 inch or larger is good for the 220 band. Aluminum rod or hard-drawn wire works well at 144 MHz. Very strong elements can be made with stiff-rod inserts in hollow tubing. If the latter is slotted, and tightened down with a small clamp, the element lengths can be adjusted experimentally with ease.

Sizes recommended above are usable with formula dimensions given in Table 1. Larger diameters broaden frequency response; smaller ones sharpen it. Much smaller diameters than those recommended will require longer elements, especially in 50-MHz arrays.

The driven element(s) of a vhf array may be cut from the formula

$$L \text{ (inches)} = \frac{5600}{\text{freq. (MHz)}}$$

$$\text{or } L \text{ (mm)} = \frac{142,250}{\text{freq. (MHz)}}$$

This is the basis for Table 1 driven-element information. Reflectors are usually about five percent longer, and directors five percent shorter, though element spacing and desired antenna bandwidth affect parasitic-element lengths. The closer the reflector and director (especially the latter) are to the driven element the nearer they must be to the driven-element length to give optimum gain. This is another way of saying that close-spaced arrays tend to work effectively over narrower bandwidths than wide-spaced ones, though maximum gain may be possible with many different combinations of lengths and spacings.

Parasitic-element lengths of Table 1 are based on spacings of about 0.2 wavelength, common in relatively short Yagis and collinear arrays. Dimensions given later in the individual descriptions of antennas may be at variance with those of the table. Where this is evident, the length differences result from use of different element spacings, for the most part. Some designs are for maximum gain, without consideration of bandwidth. Still others have slightly modified spacings, to give optimum results with a particular boom length.

**Antennas for 50 MHz**

Simple antennas such as dipoles, ground-planes, mobile whips and the like are covered adequately elsewhere in this *Handbook*. Adaptation of them to vhf work involves mainly reference to Table 1 for length information. We will be concerned here with arrays that give appreciable gain, or other properties needed in vhf communication.

**Yagis, Short and Long**

The Yagi array is practically standard for 50-MHz directive use. Usual sizes are three to six elements, though up to eight or nine in line are seen in ambitious



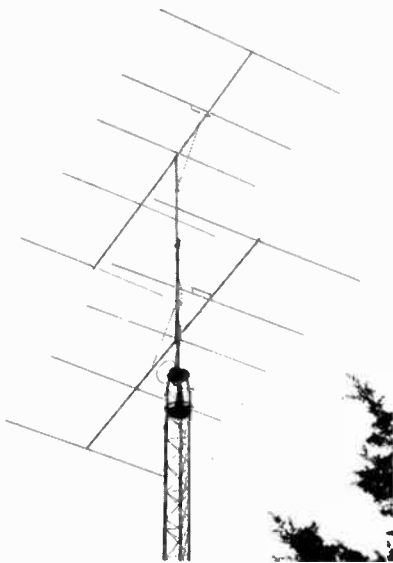


Fig. 4 — 5-over-5 stacked-Yagi array for 50 MHz, with all-coax feed.

installations. Director spacing, after the first three, must be very wide to be worthwhile, so boom lengths of 30 feet (9.1 m) or more are needed for more than 6 elements. Though long Yagis certainly are desirable, it should be emphasized that the first two or three elements provide very high gain per unit of space. Even a three-element Yagi, on as short a boom as 6 feet (1.8 m) is good for 7.5 dB over a dipole. To double the gain (add 3 dB) requires going to only six elements — but it takes a boom more than 20 feet (6.1 m) long. If it is possible to put up a rotatable antenna at all, there is usually room for at least a 3-element structure, and the gain such an antenna provides is very helpful. Dimensions can follow those given for the first three elements of larger arrays described here.

### Stacking Yagis

Where suitable provision can be made for supporting them, two Yagis mounted one above the other and fed in phase may be preferable to one long Yagi having the same theoretical or measured gain. The pair will require a much smaller turning space for the same gain, and their lower radiation angle can provide interesting results. On long ionospheric paths a stacked pair occasionally may show an *apparent* gain much greater than the 2 to 3 dB that can be measured locally as the gain due to stacking.

Optimum spacing for Yagis of five elements or more is one wavelength, but this may be too much for many builders of 50-MHz antennas to handle. Worthwhile results can be obtained with as little as one half-wavelength (10 feet 3 m), and 5/8 wavelength (12 feet/3.66 m) is markedly better. The difference between 12 and 20 feet may not be worth the added structural problems involved in the wider

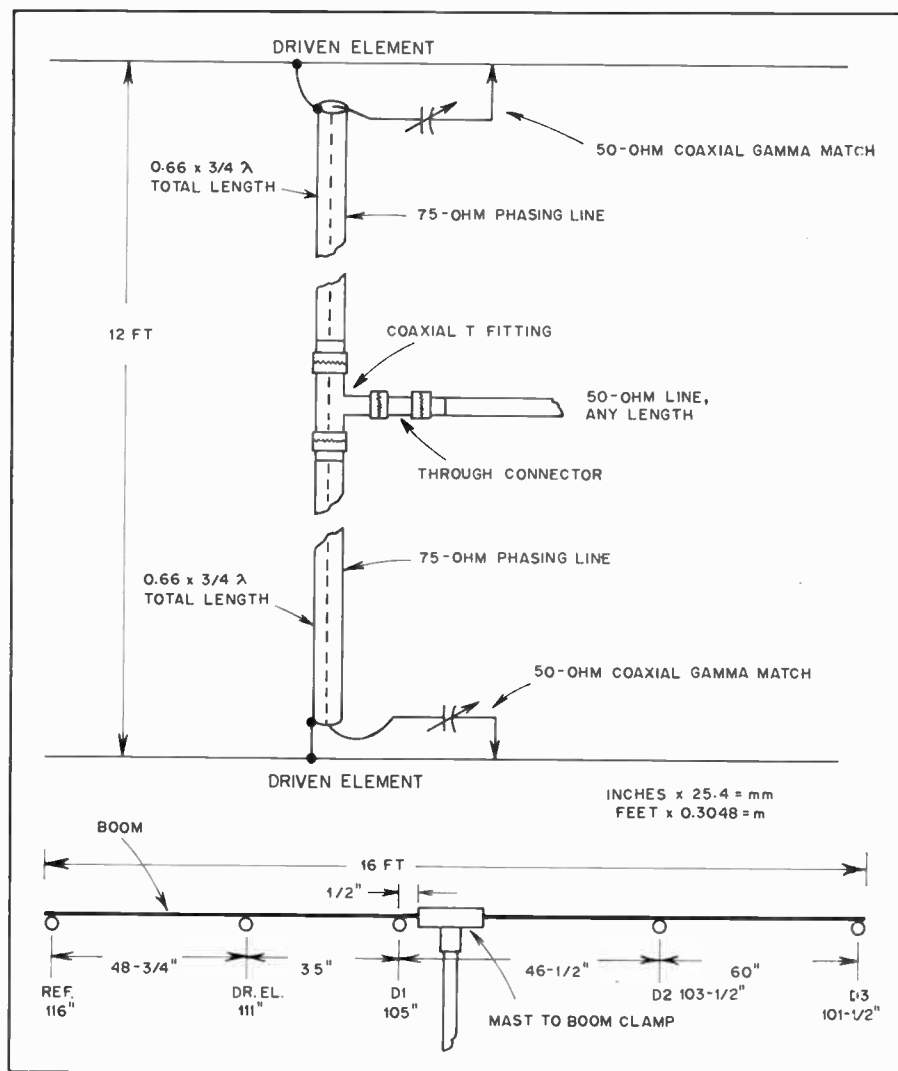


Fig. 5 — Principal dimensions of the 50-MHz 5-over-5, with details of the 3/4-wavelength Q-section matching system. The propagation factor of 0.66 applies only with solid-dielectric coax. Gamma-matching assemblies are coaxial-capacitor units (Kirk Electronics C6M).

spacing, at 50 MHz, at least. The closer spacings give lower measured gain, but the antenna patterns are cleaner than will be obtained with one-wavelength spacing. The extra gain with wider spacings is usually the objective on 144 MHz and higher bands, where the structural problems are not severe.

### 5-Over-5 for 50 MHz

The information provided in Fig. 5 is useful for a single five-element Yagi, or for the stacked pair of Fig. 4, either to be fed with a 50-ohm line. The phasing and matching arrangement may be used for any pair of Yagis designed for 50-ohm feed individually. With slight modification it will serve with Yagis designed for 200-ohm balanced feed.

### Mechanical Details

Construction of the single Yagi bay or a stacked pair is simplified by use of components which should be available to most builders. Element-to-boom and boom-to-mast mounts are aluminum

castings designed for these applications by Kirk Electronics, 73 Ferry Rd., Chester, CT 06412. The gamma matches shown schematically in Fig. 5 are of coaxial construction, waterproofed for long life, and available from the same supplier.

Booms are made of two 8-foot (2.4-m) lengths of 1-1/4-inch (32-mm) aluminum (Reynolds) found in many hardware stores. Reynolds makes a special fitting for joining sections of the tubing, but these are not widely available from the usual hardware-store stocks, so a hand-made splice was substituted. A piece of the same-diameter tubing as the booms, 12 inches (305 mm) or more in length, is slotted with a hacksaw, and then compressed to fit inside the ends of the two 8-foot (2.44-m) lengths, as shown in Fig. 6. If the splice is held in the compressed position with large pipe pliers or a hose clamp, the ends will slide inside the boom sections readily. When the splice is released from compression, the two tubes can be driven together. Self-tapping screws should be run through the tubes and the splice, to

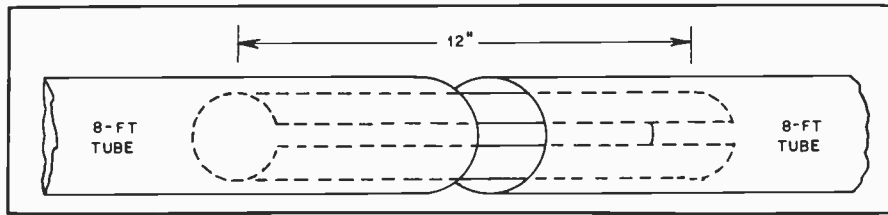


Fig. 6 — Details of the boom splices used in the five-element 50-MHz Yagis. Two 8-foot (2.4-m) lengths of 1-1/4-inch (32-mm) tubing are joined to make the 16-foot (4.8 m) booms.

hold the assembly firm. Use at least two on each side of the splice.

Elements are 1/2-inch (13-mm) aluminum tubing, Alcoa alloy 6061-T6. Almost any aluminum should be suitable. Kirk Yagi clamps, one-piece aluminum castings designed for this job, are available for 3/8 (1.5 mm) as well as 1/2-inch (13-mm) elements, and 1-1/4-inch (32-mm) boom. The eyes through which the elements pass are drilled, but must be tapped for 10-32 setscrews to tighten the elements firmly in place, two screws per element. The portion of the clamp that surrounds the boom can be spread slightly to allow the clamp to slide along the boom to the desired point. The interior surface is slightly rough, so tightening the yoke with the screw provided with the clamps makes the element set firmly on the boom. The reflector, driven element and first director are all in back of the boom splice.

The vertical member of the stacked array is 1-1/4 inch (32 mm) thick-wall anodized steel tubing, commonly used in large antenna installations for home TV. Do not use thin-wall aluminum or light galvanized steel masting. The aluminum is not strong enough, and inexpensive steel masting rusts inside, weakening the structure and inviting failure.

Spacing between bays can be a half wavelength (10 feet/3 m), 5/8 wavelength (12 feet/3.6 m), or a full wavelength (20 feet/6 m), though the wide spacing imposes mechanical problems that may not be worth the effort for most builders. The 5/8-wave spacing is a good compromise between stacking gain and severe support problems, and is recommended with the materials used here.

The 10-foot (3-m) lengths of steel masting could be used, with the bottom 8 feet (2.4 m) running through the tower bearing to the rotator. A heavier main support is preferable, however, and it is "1-inch (25 mm) water pipe" in this installation. This is iron, about 1-3/8 inch (35 mm) outside diameter, extending about 8 feet out of the tower. The steel masting between the Yagi bays is fastened to the pipe with four TV-type U-clamps, spaced evenly in the overlapping area of the two supports.

The booms are braced to the mast fore and aft, using the longest pieces of element stock left over when the forward directors are cut from 12-foot (3.6-m) lengths. Ends of the braces are flattened

about 1 inch (25 mm), and bent to the proper angle. Outer ends fasten to the booms with two self-tapping screws each. The mast ends are clamped to the support with one TV U-clamp for each pair. This bracing is good insurance against fluttering of the booms and elements, which can cause failures after long periods, even though a structure appears adequately strong.

#### Phasing and Matching

A single five-element Yagi can be fed directly with 50-ohm coax, through the Kirk coaxial gamma-match assembly (Type C6M). This has an adjustable coaxial capacitor, and an arm that connects to the driven element with a sliding clip. Both the capacitor and the point of connection should be adjusted for minimum reflected power, at the center of the frequency range most used. Doing this between 50.2 and 50.4 MHz is suitable for most operators, other than those using fm above 52.5 MHz. Each bay of the stacked pair should be set in this way. The pair can then be fed through a double Q-section of 75-ohm coax, as shown in Fig. 5.

The Kirk gamma-match assembly has an SO-239 coaxial fitting built in, so the phasing lines are fitted with PL-259 coaxial connectors at both ends. The inner ends attach to a matching coaxial T fitting. The main run of 50-ohm line connects to the center of the T, with a coaxial through-connector and a PL-259 fitting. When the antenna is installed all connectors should be wrapped tightly with plastic tape, and sprayed with Krylon or other protective spray. Dow-Corning Silastic RTV-732 sealant is also good for this use. If the coaxial phasing sections are wrapped around the booms and vertical support a few times, they will just reach the T-fitting, when 12-foot (3.6-m) spacing is used.

The lines should be any odd multiple of a quarter-wavelength. If both are the same length the gamma arms should attach to the same side of the driven elements. If there is a half-wavelength difference in the lines, the arms should connect to opposite sides. The length given in Fig. 5 is nominal for solid-dielectric coax. If foam-dielectric line is used, the propagation factor given by the maker should be substituted for the 0.66 figure. It is best to grid-dip the line sections for resonant frequency, in any

case. Cut the line three inches or more longer than the expected length. Solder a loop of wire between the center pin and the mounting flange of an SO-239 connector. Attach this to the PL-259 connector at one end of the line, and couple it to the dip-meter coil. Trim the line length until resonance at the midpoint of the intended frequency range is indicated. This will not change appreciably when the other coaxial connector is attached.

The line used in the model described is RG-59A/U, which is satisfactory for any amateur power level, so long as the SWR is kept low. Larger coax, such as RG-11A/U, is recommended for a greater margin of safety.

#### Adjustment and Testing

An individual Yagi can be tested and matched properly by mounting it a half-wavelength above ground, in a large area that is clear of obstructions for many wavelengths. The boom can also be tilted up, until the ground-reflected wave is not a factor in the field-strength meter reading. The SWR bridge should be connected at the gamma match, or an electrical half-wavelength therefrom. Apply low power (not over 10 watts) and adjust the gamma capacitor and the point of connection to the driven element for zero reflected power, at the desired frequency range. The model was flat from 50.2 to 50.4 with just perceptible reflected power showing at 50.1 to 50.5. Adjusted in this way the array should work well up to about 51 MHz.

The best way to check operation of the stacked pair is to support the array with the reflectors resting on the ground and the booms pointing straight up. A 6-foot (2-m) step-ladder can be used for a temporary support. The bays can be fed separately with 50-ohm line, in this position, and the gamma settings should be the same as obtained in the first check, described above. Now connect the two 75-ohm phasing lines, and insert the SWR bridge in the 50-ohm line to the T fitting. The SWR should be the same as when the bays are fed separately through the 50-ohm line; close to 1:1. The array can be dismantled and reassembled atop the tower, and matching should remain correct.

The matching-phasing system described is useful for any two loads designed for 50-ohm feed. The 5/8-wave spacing is usable with up to at least six-element bays, though wider bay spacing is needed for maximum gain with long Yagis. Individual antennas intended for 200-ohm balanced feed can be matched with 75-ohm coax in the phasing harness and baluns at each load.

Bay spacing is not critical. Close spacing gives somewhat lower gain, but a very clean pattern. The main lobe gets sharper and larger as spacing is increased,

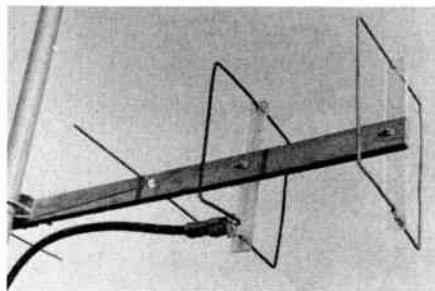


Fig. 7 — A close-up view of the feed method used on a 432-MHz quagi. This arrangement produces an excellent SWR and an actual measured gain in excess of 13 dB over an isotropic antenna with a 4-foot 10-inch (1.5 m) boom! The same basic arrangement is used on lower frequencies, but wood may be substituted for the Plexiglas spreaders. The boom is 1/2-inch (13 mm) exterior plywood.

but minor lobes also increase. These take over from the main lobe if spacing of bays is carried too far.

### The VHF Quagi

First described by K6YNB in April 1977 *QST*, the quagi has become a very popular antenna for use on 144 MHz and above. The long-boom quagi was presented by K6YNB/N6NB in February 1978 *QST*.

### How to Build a Quagi

There are a few tricks to quagi building. The designer mass produced as many as 16 in one day. Table 2 gives the dimensions for various frequencies.

The boom is *wood* or any other nonconductor (e.g., fiberglass). If a metal boom is used, a new design and new element lengths will be required. Many vhf antenna builders go wrong by failing to follow this rule: If the original uses a metal boom, use the same size and shape metal boom when you duplicate it. If it calls for a wood boom, use a non-conductor. Many amateurs dislike wood booms, but in a salt-air environment they outlast aluminum (and surely cost less). Varnish the boom for added protection.

The 2-meter version is usually built on a 14-foot (4.3-m), 1 × 3 inch (20 × 60 mm) boom, with the boom cut down to taper it to one inch at both ends. Clear pine is best because of its light weight, but construction grade Douglas fir works well. At 220 MHz, the boom is under 10 feet (3 m) long and most builders use 1 × 2 (20 × 40 mm) or (preferably) 3/4 by 1-1/4-inch (19 × 32 mm) pine molding stock. On 432 MHz the boom must be 1/2-inch (13-mm) thick or less. Most builders use strips of 1/2-inch (13-mm) exterior plywood for 432.

The quad elements are supported at the current maxima (the top and bottom, the latter beside the feed point) with Plexiglas or small strips of wood. The quad elements are made of no. 12 copper wire,

**Table 2**  
Dimensions, Eight-Element Quagi

Element Lengths	144.5 MHz	147 MHz	222 MHz	432 MHz	446 MHz
Reflector (all no. 12 TW wire, closed)	86-5/8" (loop)	85"	56-3/8"	28"	27-1/8"
Driven element (no. 12 TW, fed at bottom)	82" (loop)	80"	53.5"	26-5/8"	25-7/8"
Directors	35-15/16" to 35" in 3/16" steps	35-5/16" to 34-3/8" in 3/16" steps	23-3/8" to 22-3/4" in 1/8" steps	11-3/4" to 11-7/16" in 1/16" steps	11-3/8" to 11" in 1/16" steps
<b>Spacing</b>					
R-DE	21"	20-1/2"	13-5/8"	7"	6.8"
DE-D1	15-3/4"	15-3/8"	10-1/4"	5-1/4"	5.1"
D1-D2	33"	32-1/2"	21-1/2"	11"	10.7"
D2-D3	17-1/2"	17-1/8"	11-3/8"	5.85"	5.68"
D3-D4	26.1"	25-5/8"	17"	8.73"	8.46"
D4-D5	26.1"	25-5/8"	17"	8.73"	8.46"
D5-D6	26.1"	25-5/8"	17"	8.73"	8.46"
<b>Stacking Distance Between Bays</b>					
	11'	10'10"	7'1-1/2"	3'7"	3'5-5/8"
Inches × 25.4 = mm      Feet × 0.3048 = m					

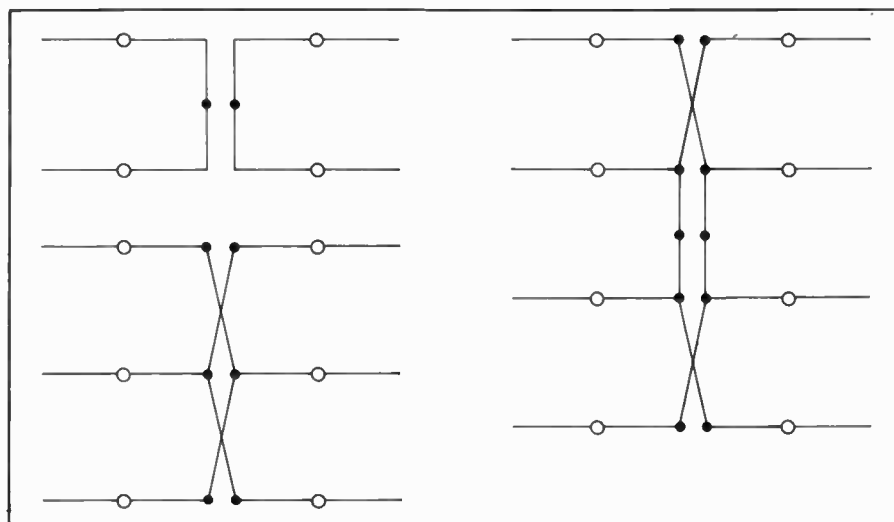


Fig. 8 — Element arrangements for 8-, 12- and 16-element collinear arrays. Parasitic reflectors, omitted here for clarity, are 5 percent longer and 0.2 wavelength in back of the driven elements. Feed points are indicated by black dots. Open circles are recommended support points. The elements can run through wood or metal booms, without insulation, if supported at their centers in this way. Insulators at the element ends (points of high rf voltage) tend to detune and unbalance the system.

commonly used in house wiring. Some builders may elect to use no. 10 wire on 144 MHz and no. 14 wire on 432 MHz, although this will change the resonant frequency slightly. Solder a type-N connector (an SO-239 is often used at 2 meters) at the midpoint of the driven element bottom side, and close the reflector loop.

The directors are mounted through the boom. They can be made of almost any metal rod or wire of about 1/8-inch (3 mm) diameter. Welding rod or aluminum clothesline wire will work well if straight. (The designer used 1/8-inch stainless-steel rod secured from an aircraft surplus store.)

A TV-type U-bolt mounts the antenna

on a mast. The author uses a single machine screw, washers and nut to secure the spreaders to the boom so the antenna can be quickly "flattened" for travel. In permanent installations two screws are recommended.

### Construction Reminders

Here are a couple of hints based on the experiences of some who have built the quagi. First, remember that at 432 MHz even a 1/8-inch measuring error will deteriorate performance. Cut the loops and elements as carefully as possible. No precision tools are needed but be careful about accuracy. Also, make sure to get the elements in the right order. The longest director goes closest to the driven element.



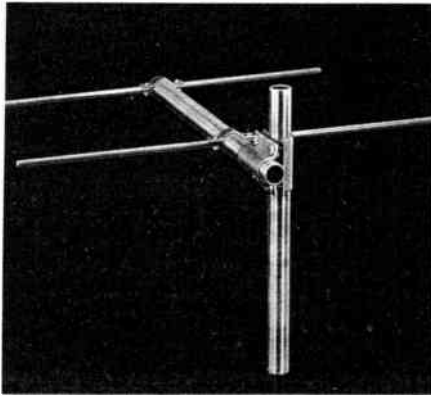


Fig. 9 — Model showing recommended method for assembling all-metal arrays. Suitable assembling clips can be cut and bent from sheet aluminum. Supporting structure should be in back of all active elements of the array.

Finally, remember that a balanced antenna is being fed with an unbalanced line. Every balun the designer tried introduced more losses than the feed imbalance problem. Some builders have tightly coiled several turns of the feed line near the feed point to limit radiation further down the line. In any case, the feed line should be kept at right angles to the antenna. Run it from the driven element directly to the supporting mast and then up or down perpendicularly for best results.

### Collinear Antennas

Information given thus far is mainly on parasitic arrays, but the collinear antenna has much to recommend it. Inherently broad in frequency response, it is a logical choice where coverage of an entire band is wanted. This tolerance also makes a collinear easy to build and adjust for any vhf application, and the use of many driven elements is popular in very large phased arrays, such as may be required for moonbounce (EME) communication.

### Large Collinear Arrays

Bidirectional curtain arrays of four, six, and eight half-waves in phase are shown in Fig. 8. Usually reflector elements are added, normally at about 0.2 wavelength in back of each driven element, for more gain and a unidirectional pattern. Such parasitic elements are omitted from the sketch in the interest of clarity. Dimensions are not critical, and may be taken from Table 1.

When parasitic elements are added, the feed impedance is low enough for direct connection to open line or twin-lead, connected at the points indicated by black dots. With coaxial line and a balun, it is suggested that the universal stub match, Fig. 1A, be used at the feedpoint. All elements should be mounted at their electrical centers, as indicated by open circles in Fig. 8. The framework can be metal or insulating material, with equally

Table 3

### 432-MHz, 15-Element, Long-Boom Quagi Construction Data

Element Lengths — Inches		Interelement Spacing — Inches	
R — 28" loop	D7 — 11-3/8	R-DE — 7	D6-D7 — 12
DE — 26-5/8" loop	D8 — 11-5/16	DE-D1 — 5-1/4	D7-D8 — 12
D1 — 11-3/4	D9 — 11-5/16	D1-D2 — 11	D8-D9 — 11-1/4
D2 — 11-11/16	D10 — 11-1/4	D2-D3 — 5-7/8	D9-D10 — 11-1/2
D3 — 11-5/8	D11 — 11-3/16	D3-D4 — 8-3/4	D10-D11 — 9-3/16
D4 — 11-9/16	D12 — 11-1/8	D4-D5 — 8-3/4	D11-D12 — 12-3/8
D5 — 11-1/2	D13 — 11-1/16	D5-D6 — 8-3/4	D12-D13 — 13-3/4
D6 — 11-7/16			

Boom — 1 x 2-inch x 12-ft Douglas fir, tapered to 5/8 inch at both ends.

Driven element — No. 12 TW copper-wire loop in square configuration, fed at center bottom with

type N connector and 52-ohm coax.

Reflector — No. 12 TW cooper-wire loop, closed at bottom.

Directors — 1/8-inch rod passing through boom.

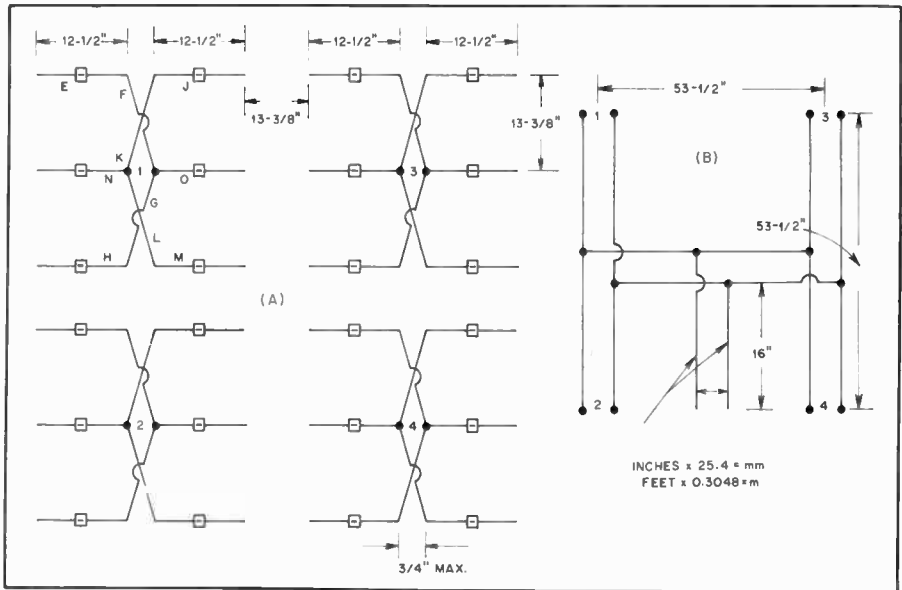


Fig. 10 — Large collinear arrays should be fed as sets of no more than eight driven elements each, interconnected by phasing lines. This 48-element array for 432 MHz (A) is treated as if it were four 12-element collinear arrays. Reflector elements are omitted for clarity. Phasing harness is shown at B.

good results. A model showing the preferred method of assembling an all-metal antenna is pictured in Fig. 9. Note that the metal supporting structure is entirely in back of the plane of the reflector elements. Sheet-metal clamps can be cut from scraps of aluminum to make this kind of assembly, which is very light in weight and rugged as well. Collinear elements should always be mounted at their centers, where rf voltage is zero — never at their ends, where the voltage is high and insulation losses and detuning can be very harmful.

Collinear arrays of 32, 48, 64 and even 128 elements can be made to give outstanding performance. Any collinear should be fed at the center of the system, for balanced current distribution. This is very important in large arrays, which are treated as sets of six or eight driven elements each, and fed through a balanced harness, each section of which is a resonant length, usually of open-wire line. A 48-element collinear array for 432

MHz, Fig. 10, illustrates this principle.

### Plane and Parabolic Reflectors

A reflecting plane, which may be sheet metal, wire mesh, or even closely spaced elements of tubing or wire, can be used in place of parasitic reflectors. To be effective, the plane reflector must extend on all sides to at least a quarter-wavelength beyond the area occupied by the driven elements. The plane reflector provides high front-to-back ratio, a clean pattern, and somewhat more gain than parasitic elements, but large physical size rules it out for amateur use below 420 MHz. An interesting space-saving possibility lies in using a single plane reflector with elements for two different bands mounted on opposite sides. Reflector spacing from the driven element is not critical. About 0.2 wavelength is common.

The reflector can be formed into parabolic shape for a focussing effect, similar to that in a searchlight. Parabolic reflectors must be very large in terms of

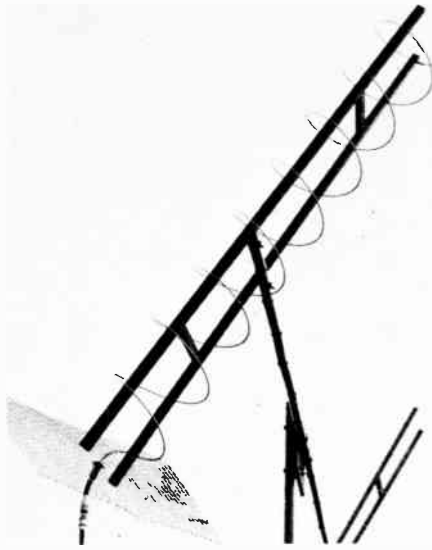


Fig. 11 — An eight-turn 432-MHz helical array, wound from aluminum clothesline wire. Left-hand polarization is shown. Each turn is one wavelength, with a pitch of 0.25 wavelength. Feed is with 50-ohm coax, through an 84-ohm Q section.

wavelength. Principles involved in parabolic reflector design are discussed by WA9HUV in June 1971 *QST*, page 100.

#### Circular Polarization

Polarization is described as "horizontal" or "vertical," but these terms have no meaning once the reference of the

earth's surface is lost. Many propagation factors can cause polarization change: reflection or refraction, passage through magnetic fields (Faraday rotation) and satellite rolling, for example. Polarization of vhf waves is often random, so an antenna capable of accepting any polarization is useful. Circular polarization, generated with helical antennas or with crossed elements fed 90 degrees out of phase, has this quality.

The circularly polarized wave, in effect, threads its way through space, and it can be left- or right-hand polarized. These polarization "senses" are mutually exclusive, but either will respond to any plane polarization. A wave generated with right-hand polarization comes back with left-hand, when reflected from the moon, a fact to be borne in mind in setting up EME circuits. Stations communicating on direct paths should have the same polarization sense.

Both senses can be generated with crossed dipoles, with the aid of a switchable phasing harness. With helical arrays, both senses are provided with two antennas, wound in opposite directions.

#### Helical Antenna for 432 MHz

The eight turn helix of Fig. 11 is designed for 432 MHz, with left-hand polarization. It is made from 213 inches (5.4 m) of aluminum clothesline wire, including 6 inches (152 mm) that is used for cutting back to adjust the

feed impedance.

Each turn is one wavelength long, and the pitch is about 0.25 wavelength. Turns are stapled to the wooden supports, which should be waterproofed with liquid fiberglass or exterior varnish. The reflecting screen is one wavelength square, with a type-N coaxial fitting soldered at its center, for connection of the required coaxial Q section.

The nominal impedance of a helical antenna is 140 ohms, calling for an 84-ohm matching section to match to a 50-ohm line. This can be approximated with copper tubing of 0.4-inch (10-mm) inside diameter, with no. 10 inner conductor, both 6-1/2 inches (165 mm) long. With the antenna and transformer connected, apply power and trim the outer end of the helix until reflected power approaches zero.

The support arms are made from sections of 1 × 1 inch (25 × 25mm) wood and are each 60 inches (1.52 m) long. The spacing between them is 8-1/4 inches (210 mm), outer dimension. The screen of the antenna in Fig. 11 is tacked to the support arms for temporary use. A wooden framework for the screen would provide a more rugged antenna structure. The theoretical gain of an eight-turn helical is approximately 14 decibels. Where both right- and left-hand circularity is desired, two antennas can be mounted on a common framework, a few wavelengths apart, and wound for opposite sense.

# Operating a Station

The rest of this Handbook serves primarily the technical phases of amateur radio — and indeed radio/electronics in general. But as far as hamming is concerned, only about half the game deals with how you handle the soldering iron. The other half is concerned with what you do with all that junk once you get it operating. This is the subject of this chapter.

It's a pretty big subject, one which we can't hope to cover in these few pages, so at the very start we urge that you obtain the two principal operating publications put out by ARRL. They're both free. *Operating an Amateur Radio Station* covers basic and intermediate operating, details all the League's awards, contests and other operating activities, the complete ARRL operating organization and how it works, abbreviations and a lot more. The *Public Service Communications Manual* goes into even further detail on ARRL's most important operating organization, the Amateur Radio Public Service Corps, comprising the Amateur Radio Emergency Service (ARES) and the National Traffic System. These two booklets are free on request.

If you are just beginning in ham radio, you should spring for a copy of the *Ham Radio Operating Guide*. This has all the

operating information in basic form for the beginning amateur, written in a style anyone can follow.

But we'll try to cover the essentials of operating in these few pages. Here goes.

### Operating Standards

Amateur radio through the years has developed a number of operating standards and procedures. Some of these are borrowings from other services, such as commercial or military. Some have been coined by amateurs for our particular use, as a part of "ham jargon." Still others have been innovated by the League to fulfill a need. All of them together make up a "standard operating procedure" for amateurs differing, at least in part, from the procedures used in any other radio service. We hams are a service; we aren't just a bunch of licensed operators randomly pursuing a "hobby." We have standard procedures, and these procedures are recommended by ARRL but based on our particular needs. If we all use different procedures, we will have difficulty, at times, in communicating with each other. If we all use the same procedures, even though the ARRL recommendation may not be our personal preference, we will communicate effectively. And, since ARRL is ultimately

controlled by its members, any procedure you don't like can be changed if members share your opinion.

So let's all use the same standards. Let's be a single, organized, operating *service*.

### Establishing Contact

If you are looking for a contact with *anyone*, then the thing to do is to call CQ. Make sure the frequency is unoccupied, then go to it. These days, few amateurs tune away from their frequencies very far, so you don't need a long CQ — just a 3 × 3, for example. Listen around a minute or so. If no answer, it means one of two things: either no one heard you or no one listening wants to contact you. Try it again, another 3 × 3. If still no answer, that's enough. Move to another (clear) frequency before you try it again; or try calling someone else. A CQ call on cw might go like this: CQ CQ CQ DE WINJM WINJM WINJM K. On voice, "CQ CQ, this is WINJM, W One November Juliett Mike, go."

If you call CQ, it means you are willing to talk to anyone. If you want to be fussy, don't CQ. Find someone you would like to talk to and call *him*. In this case, you can observe the same principle; zero beat his frequency and give him a short call, such as: WINJM WINJM WINJM DE N4KB N4KB N4KB AR, or even shorter. On voice, "WINJM, WINJM from N4KB, November Four Kilo Bravo, over."

Notice the "ending signals." These aren't just happenstance; each one of them means something. On cw, for example, K at the end of a transmission means "anyone go ahead," while AR means "I have just called another station and want only him to reply." On voice, "go" or "go ahead" refers to anybody listening, while "over" refers to a specific station. And so on. There is a complete list of ending prosigns and prowords. Use them properly, even if others you hear do not.

Now, about the QSO itself. You are introducing yourself to a brand-new acquaintance. Don't bore him. The usual procedure is to give him a signal report



Operating is the name of the game. Operate well, using time-tested procedures, and you'll enjoy it even more.



(see RST system), and tell him your name and location. After that, tell him the things about yourself that you would like to know about him, but make your transmission short; don't go on and on. Start each transmission with your own call, i.e., DE WINJM or "This is WINJM," and end it with both calls, i.e., N4KB DE (or from) WINJM. Most voice contacts today use "VOX" or "push to talk," which makes it possible to talk back and forth rapidly, much like a telephone conversation. When you do this, identification of each transmission is unnecessary. But be sure your station identification is completed at least every 10 minutes, and at the end of the contact identify both stations; that is, each station must identify not only itself but the station with which contact is being made.

Repeater operating uses somewhat different procedures because of special circumstances, but we'll discuss that a little later.

### The ARRL QSL Bureaus

Only one thing is left to do before you can consider the contact complete — confirm it with a "QSL" card. The QSL is considered the final courtesy of a contact and is an amateur radio tradition. Most amateurs have printed cards, some personalized (at greater cost), some using standard setups provided by printers for the purpose. Whatever form you adopt, be sure your QSL card shows very clearly the *correct* call of the station contacted, the date (including year) and time (preferably in UTC/GMT), the band on which contact was made and the mode. Most awards based on QSL cards require at least these essentials, along with, of course, your street address, city, state or province, and country. Some awards include county as well. Other interesting data might include some details of your equipment, antennas, former calls held, class of license, signal report and any friendly comments.

If everybody waited to receive a card before sending one, there would be no QSLing. Admittedly, printing and postage are expensive and if you are very active on the air QSLing every contact may seem like a needless expense. If you want a QSL from your contact, send him your card; and as a matter of common courtesy, send a card to everyone who sends you one.

### Receiving DX QSLs

Within the U.S. and Canada, the ARRL DX QSL Bureau System is made up of 22 call area bureaus. Most of the cards from DX bureaus go directly to the individual bureaus.

At the individual bureaus, the incoming cards are sorted by the first letter of the suffix. This sorting divides the work load into portions that can be handled by a single individual.

To claim your cards, send a 5 × 7 1/2-inch self-addressed stamped envelope

### Some Facts about Time Conversion

The chart below has been arranged to show time zones used by most amateurs in the North American continent and Universal Coordinated Time, used universally as a standard. The advantage of UTC is that it is the universally understood reference throughout the world. ARRL recommends that all amateur logging be done in UTC.

All times shown are in 24-hour time for convenience. To convert to 12-hour time; for times between 0000 and 0059, change the first two ciphers to 12, insert a colon and add a.m.; for time between 0100 and 1159, insert a colon and add a.m.; for times between 1200 and 1259, insert a colon and add p.m.; for times between 1300 and 2400, subtract 12, insert a colon and add p.m.

Time zone letters may be used to identify the kind of time being used. For example, UTC is designated

UTC	EDT/AST	CDT/EST	MDT/CST	PDT/MST	PST
0000*	2000	1900	1800	1700	1600
0100	2100	2000	1900	1800	1700
0200	2200	2100	2000	1900	1800
0300	2300	2200	2100	2000	1900
0400	0000*	2300	2200	2100	2000
0500	0100	0000*	2300	2200	2100
0600	0200	0100	0000*	2300	2200
0700	0300	0200	0100	0000*	2300
0800	0400	0300	0200	0100	0000*
0900	0500	0400	0300	0200	0100
1000	0600	0500	0400	0300	0200
1100	0700	0600	0500	0400	0300
1200	0800	0700	0600	0500	0400
1300	0900	0800	0700	0600	0500
1400	1000	0900	0800	0700	0600
1500	1100	1000	0900	0800	0700
1600	1200	1100	1000	0900	0800
1700	1300	1200	1100	1000	0900
1800	1400	1300	1200	1100	1000
1900	1500	1400	1300	1200	1100
2000	1600	1500	1400	1300	1200
2100	1700	1600	1500	1400	1300
2200	1800	1700	1600	1500	1400
2300	1900	1800	1700	1600	1500
2400	2000	1900	1800	1700	1600

Time changes one hour with each change of 15° in longitude. The five time zones in the U.S. proper and Canada roughly follow these lines.

\*0000 and 2400 are interchangeable. 2400 is associated with the date of the day ending, 0000 with the day just starting.

to the bureau serving your district. Addresses for the U.S. and Canadian bureaus are normally shown every other month in *QST*, usually on a page closely following "How's DX?".

These envelopes should have your call sign printed neatly in the upper left corner of the envelope to assist the sorter of your cards. Some bureaus will sell envelopes or postage credits as well as handling s.a.s.e.s. The bureau will provide the proper-size envelope and affix appropriate postage upon prepayment of a certain fee. The exact arrangement of your area bureau can be obtained by sending your bureau an s.a.s.e. with your inquiry.

Since many of the DX stations use the bureau system, this area bureau can be very important to someone who works DX. But, it is a complex volunteer arrangement requiring good cooperation on the part of the DXers to function properly.

### Sending Your DX QSLs

Each month, every member of the ARRL (except family and sightless mem-

bers) is mailed a copy of *QST*. The address label on the wrapper of *QST* is the member's "ticket" for use of the Overseas QSL Service. Twelve times per year, an ARRL member may send as many QSL cards as he wants for amateurs overseas. With each mailing the member must include the address label from the current copy of *QST*, \$1 (check or money order) and an s.a.s.e. QSLs must be presorted by prefix. Nothing but the cards, address label, \$1 and s.a.s.e. may be included in the package. Wrap the package securely and address it to ARRL-Membership Overseas QSL Service, 225 Main Street, Newington, CT 06111.

"Family" members of ARRL, to whom only one copy of *QST* is sent, may send cards in the same package but must include \$1 for each member sending cards and indicate that the *QST* address label includes a "family membership."

Sightless members, who do not receive a copy of *QST*, need only include \$1 with a note indicating that the cards are from a sightless member, and an s.a.s.e. Associate (unlicensed) members may use the Over-

DATE TIME	STATION CALLED	CALLED BY	HIS SIGNAL RST	MY SIGNAL RST	FREQ	EMIS-ION TYPE	POWER INPUT WATTS	TIME OF ENDING OSO	OTHER DATA	OSLs	
										NAME	S
3/16											
2300	KIEIR	X	-	-	3.6	A1	100	2320	QNI CN, RCY3		
2330	ZFIMA	X	59	47	14.2	A33	250	2332	BOX 459, GR. CAYMAN	JOE	✓
2345	WA9BWX	X	59	59				2359		MIKE	
	W9LT	X	59	59				0065		LAPAR	
3/17											
0015	HC5EE	X	599	599	14	A1	500	0016	YIA WA8TBY		✓
0030	N6SF	X	569	579				0055	S.F.	RUSTY	
0100	W1QYY	X	-	-	3.6	A1	100	0110	QNI IRN, SENT 3		
0130	CQ	UA90H	589	569	14	A1	500	0139	MOYOSIBIRSK	VLADIS	✓

seas QSL Service to send SWL reports to overseas amateur stations. No cards will be sent to individual QSL managers.

Additional information is available from ARRL. Send an s.a.s.e. and request the QSL Bureau reprint.

### Your Station Record — Logging

“Official” logging requirements have been eased in recent years, but an accurate, complete and neat log book should be a matter of personal pride. It can also be a strong form of protection for you against possible claims by others of intentional interference or against troubles caused by unauthorized use of your call by “bootleggers.”

A log should be convenient to use and a bound one is best so pages will not be lost. The ARRL log is designed to make it as easy as possible for you to comply legally with FCC requirements. This becomes a written diary of your amateur operation and should include everything that will be of interest to you in years to come. FCC requires you to retain your log for only a year, but most amateurs retain theirs indefinitely because your log reflects your personality.

### The Voice Modes

The use of proper procedure to get best results is very important. Voice operators say what they want to have understood, cw operators have to spell it out or abbreviate . . . since on phone the speed of transmission is generally between 150 and 200 words per minute, the matter of readability and understandability is critical to good communications. The good voice operator uses operating habits that are beyond reproach.

### Phone Operating Practices

*Listen with care.* It is very natural to answer the loudest station that calls, but with a little digging, if need be, answer the best signal instead. Not all amateurs can run a kilowatt, but there is no reason why every amateur cannot have a signal of the highest quality. Do not reward the operator who cranks up the transmitter

gain and splatters by answering him if another station is calling.

*Use VOX or push-to-talk.* If you use VOX, don't defeat its purpose by saying “ahhh” to keep the relay closed. If you use push-to-talk, let go of the mic button every so often to make sure you are not “doubling” with the other station. Don't be a monologist.

*Listen before transmitting.* Make sure the frequency isn't being used before you come barging into it. If you don't hear any station on the frequency, make this announcement: “Is the frequency in use? WICKK” If it is still clear, you are ready to make your call.

Interpose your call frequently. In distinct, measured tones say your call often. Use approved phonetics if your call sign is hard to understand or conditions are poor. Remember you can be cited for improper identification if it cannot be understood.

*Keep modulation constant.* Don't “ride” the microphone gain. Try to speak in an even amplitude the same distance from the microphone, keeping the gain down to eliminate room noise. Follow the manufacturers' instructions for use of the microphone; some require close-talking, some need to be turned at an angle to the speaker's mouth.

*Have a pencil and paper always handy, avoid repetition and inanities, and steer clear* of such controversial or suggestive subjects as politics and sex, and of profanities, even those considered acceptable in today's society.

The speed of radiotelephone transmission (with perfect accuracy) depends almost entirely on the skill of the two operators concerned. One must use a rate of speech allowing perfect understanding as well as permitting the receiving operator to record the information.

*Round table* operation has advantages. Ordinarily it clears frequencies of interference, especially if all stations are on the same frequency. Round tables can become very unpopular if not conducted properly. The monologist, off on a long spiel about nonsensical matters, cannot be interrupt-

ed. *Make your transmissions short and to the point.*

### Voice Operating Hints

- 1) Listen before calling.
- 2) Make short calls with breaks to listen. Avoid long CQs; do not answer overlong CQs.
- 3) Use push-to-talk or voice control (VOX). Give data concisely in first transmissions.
- 4) Make reports honest. Use definitions of strength and readability for reference. Make your reports informative and useful. Honest reports and full word description of signals save operators from FCC trouble.
- 5) Limit transmission length. Two minutes or less will convey much information. When three or more stations converse in round tables, brevity is essential.
- 6) Display sportsmanship and courtesy. Bands are congested . . . make transmissions meaningful . . . give others a break.
- 7) Check transmitter adjustment . . . avoid a-m overmodulation and splatter. On ssb, check carrier balance carefully. Do not radiate when moving VFO frequency or checking nbfm swing. Use receiver BFO to check stability of signal on a-m. Complete testing before busy hours — use a dummy load!

### Repeater Operating

A repeater is a device which receives a signal on one frequency and simultaneously transmits (“repeats”) the received signal on another frequency. The device is often

Table 1

### Voice Equivalents to Code Procedure

Voice	Code	Meaning
over	K	after call to specific station
end of message	AR	self-explanatory
wait, stand by	AS	self-explanatory
roger	R	all received correctly
go	K	any station transmit
go only	KN	addressed station only
clear	SK	end of contact
closing station	CL	going off the air

located atop a tall building or high mountain and, in this way, greatly extends the operating coverage of amateurs using mobile and handheld transceivers.

To use a repeater you must have a transceiver with the capability of transmitting on the repeater's *input frequency* (the frequency that the repeater listens on) and receiving on the repeater's *output frequency* (the frequency the repeater transmits on). This capability can be acquired by installing the correct crystals in your transceiver or, if you have a synthesized rig, by dialing the current frequency and selecting the proper *offset* (frequency difference between input and output).

When you have the frequency capability, all that you need do is press the microphone button and you will turn on ("access") the repeater. (Some repeaters have limited access requiring the transmission of a sub-audible tone, series of tones or bursts in order to access the repeater.) Most repeaters briefly transmit a carrier ("squelch tail") after a user has stopped transmitting to inform the user that he is actually accessing a repeater.

After acquiring the ability to access a repeater you should become acquainted with the operating practices that are inherent to this unique mode of amateur radio:

1) Monitor the repeater to become familiar with any peculiarities in its operation.

2) To initiate a contact simply indicate that you are on frequency. Various geographical areas have different practices on making yourself heard, but, generally, "This is W1XZ monitoring" will suffice. One practice that is looked upon with disfavor throughout the U.S. and Canada is calling a long CQ on a repeater.

3) Identify legally; you must transmit your call sign at the beginning and end of each contact and every 10 minutes in between. At the end you must also identify the station you were in QSO with. It is illegal to key a repeater without identification.

4) Pause between transmissions. This allows other hams to use the repeater (someone may have an emergency). On most repeaters a pause is necessary to reset the timer.

5) Keep transmissions short and thoughtful. Your monologue may prevent someone with an emergency from using the repeater. If your monologue is long enough, you may *time out* the repeater. Your transmissions are being heard by many listeners including nonhams with "public service band" monitors; don't give a bad impression of our hobby.

6) Use simplex whenever possible. If you can complete your QSO on a direct frequency, there is no need to tie up the repeater and prevent others from using it.

7) Use the minimum amount of power necessary to maintain communications. This FCC regulation minimizes the

Table 2

International Telecommunication Union Phonetics

A — Alpha	J — Juliett	S — Sierra
B — Bravo	K — Kilo	T — Tango
C — Charlie	L — Lima	U — Uniform
D — Delta	M — Mike	V — Victor
E — Echo	N — November	W — Whiskey
F — Foxtrot	O — Oscar	X — X-Ray
G — Golf	P — Papa	Y — Yankee
H — Hotel	Q — Quebec	Z — Zulu
I — India	R — Romeo	

possibility of accessing distant repeaters on the same frequency.

8) Don't break into a contact unless you have something to add. Interrupting is no more polite on the air than it is in person.

9) Many repeaters are equipped with autopatch facilities which, when properly accessed, connect the repeater to the telephone system to provide a public service. The FCC forbids using an autopatch for anything that could be construed as business communications. Nor should an autopatch be used to avoid a toll call. Do not use an autopatch where regular telephone service is available. Abuses of autopatch privileges may lead to their loss.

10) All repeaters are assembled and maintained at considerable expense and inconvenience. Usually an individual or a

## REPEATER TIPS

### DO'S

**DO KEEP ALL TRANSMISSIONS SHORT.** Emergencies don't wait for monologues to be finished. If you talk to hear your own voice what you want is a tape recorder, not an fm rig.

**DO THINK BEFORE YOU TRANSMIT.** If you can't think of anything worth saying, don't say anything.

**DO PAUSE A COUPLE OF SECONDS BETWEEN EXCHANGES.** Someone with a high-priority need for the repeater may want to break in; also, some repeaters are configured so that a brief pause in transmissions is necessary to reset the three-minute timer.

**DO IDENTIFY PROPERLY** You must give your call at the beginning of a contact and every 10 minutes thereafter. At the end of the contact you must also give the call of the station with whom you were in contact.

**DO BE COURTEOUS.** A repeater is like a telephone party line, and requires the same kind of cooperation in its use.

**DO USE SIMPLEX WHENEVER POSSIBLE.** Leave the repeaters available for those who need them.

**DO USE THE MINIMUM POWER NECESSARY** to maintain communication. Not only is this an FCC requirement, it's also common courtesy.

**DO SUPPORT YOUR LOCAL REPEATER CLUB** even if it doesn't require all users to be members. Maintaining a good machine is an expensive undertaking, and you should do your share.

### DON'TS

#### DON'T ABUSE AUTOPATCH PRIVILEGES.

Business messages are not permitted in the amateur service. Don't force the control operator to terminate your call in order to avoid a violation.

**DON'T BREAK INTO A CONTACT** unless you have something to add. Interrupting is no more polite on the air than it is in person.

**DON'T FORGET THAT AMATEUR RADIO IS ALLOCATED FREQUENCIES BECAUSE IT IS A SERVICE** not just a hobby. Don't neglect the public service aspects of Vhf-fm communication, such as accident reporting, emergency preparedness, etc.

**DON'T TRY TO PROVE WHAT A GREAT OPERATOR YOU ARE** by criticizing the operating techniques of others on the air. Instead, set an example which others will be proud to follow.

**DON'T MONOPOLIZE A REPEATER.** The best repeater users are the ones who do a lot of listening, and little transmitting.



**REMEMBER, WHAT YOU SAY OVER A REPEATER CAN BE HEARD OVER THOUSANDS OF SQUARE MILES** by anyone with an inexpensive "public service band" monitor. These people are potential hams; if they like what they hear on the air, they will want to get licenses and join us. Don't leave them with a bad impression of our hobby by making thoughtless or off-color remarks.



group is responsible and it behooves those who are regular users of a repeater to support the efforts of keeping the repeater on the air.

An annually revised directory listing all registered repeaters is available from the ARRL. For details on how to obtain a copy, check recent issues of *QST*.

### CW Operating

If you spend your entire amateur radio career on phone, once you have mastered enough cw to pass the necessary tests, you are missing out on at least 50 percent of the fun of hamming. Mastering the art of cw communication is ten times easier than learning to talk, and you did this when you were two years old. All it takes is some basic learning principles, then practice, practice and more practice. This is not so much drudgery as you might think, because you can combine learning with listening to actual signals on the band, and even with operating, since the Novice Class license requires only 5 wpm.

But listening is the best way to go, in the beginning. You don't need a license for this. Once you have learned the basic sounds of code, you will soon start recognizing common words — the, and, for, and so on. You will hear a lot of CQ. This is always followed by DE (from) and then a set of call letters, in the Novice bands usually starting with a W, but elsewhere you might hear an A, K or N as the first letter of a call. Practicing copying calls is an excellent means of getting prelicense practice. You can even get good sending practice by pretending to call the CQing station on your code practice oscillator. Sending practice is important, even though we do now have machines that will do it for you. The things are expensive and not needed for slow speeds, at which you will be starting. Buy a simple "straight" key for \$5 or less, mount it on a piece of heavy plywood, or directly onto your operating table. The time to "graduate" to a "bug" (semi-automatic key), or an electronic keyer is later.


There are many pitfalls to developing

into a finished cw operator, not the least of which is the acquisition of bad habits. Many of these come from mimicking your peers or elders, some of whom themselves are the victims of bad cw habits. Don't let them rub off on you. Most of these unfavorable traits of beginner cw operators are called the "Novice accent," things which identify you as a beginner.

Probably the worst of these is carelessness about spacing. Your early cw training should have taught you that spacing length is just as important as dit and dah length. All we can say about this is that if you have a tendency to stumble all over yourself when you talk, you will tend to do so when you send; but try to curb it. One way to do this is to practice sending in step with WIAW or other code practice each month lists the source of the text of certain transmissions. If you can send "in step" with WIAW, your sending is perfect. Lacking that (and very few can achieve it), the closer you can come to it the better you are.

On phone it is unnecessary and therefore improper to use jargon and abbreviations, but on cw abbreviations are a necessity. Without them, it takes a long time to say what you want to say, especially at beginner speeds. Most of the abbreviations we hams use have developed within the fraternity, some of them are borrowed from or are carryovers from old-time telegraphy abbreviations. Which is which doesn't matter; it is all ham radio to us. Learn to use ham cw abbreviations liberally and you will get much more said in much less time. When you reach a high-proficiency level, you will find that cw is almost as fast as talking, thus all but eliminating one of its principal disadvantages while still retaining its many advantages.

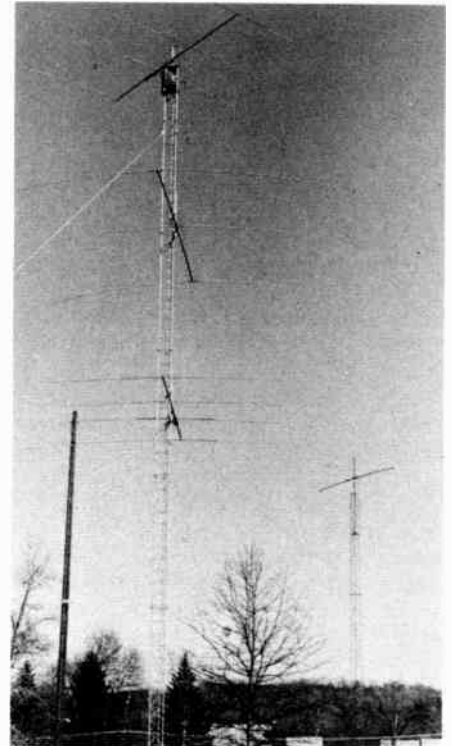Despite the fact that learning cw is easier than learning to talk, nearly everybody can talk but few people can communicate by cw. Thus, there is considerable pride of accomplishment in cw operating. Regardless of your level of proficiency, chances are that you still have



This W1AW 120 foot tower holds phased 4-element 20-meter Yagis at 60 and 120 feet and a 3-element 40-meter Yagi at 90 feet. The 5-element 10-meter Yagi in the background is on a 60-foot tower.

### The R-S-T System

#### Readability

- 1 — Unreadable.
- 2 — Barely readable, occasional words distinguishable.
- 3 — Readable with considerable difficulty.
- 4 — Readable with practically no difficulty.
- 5 — Perfectly readable.

#### Signal Strength

- 1 — Faint signals, barely perceptible.
- 2 — Very weak signals.
- 3 — Weak signals.
- 4 — Fair signals.
- 5 — Fairly good signals.
- 6 — Good signals.
- 7 — Moderately strong signals.
- 8 — Strong signals.
- 9 — Extremely strong signals.

#### Tone

- 1 — Sixty cycle ac or less, very rough and broad.
- 2 — Very rough ac very harsh and broad.
- 3 — Rough ac tone, rectified but not filtered.
- 4 — Rough note, some trace of filtering.
- 5 — Filtered rectified ac but strongly ripple-modulated.
- 6 — Filtered tone, definite trace of ripple modulation.
- 7 — Near pure tone, trace of ripple modulation.
- 8 — Near perfect tone, slight trace of modulation.
- 9 — Perfect tone, no trace of ripple or modulation of any kind.

If the signal has the characteristic steadiness of crystal control, add the letter X to the RST report. If there is a chirp, the letter C may be added to so indicate. Similarly for a click, add K. The above reporting system is used on both cw and voice, leaving out the "tone" report on voice.

### ARRL Ending Signals

Meaning	CW	Use
End of transmission	AR	After call to a specific station, before contact has been established. W6ABC DE W9LMN AR
End of message	AR	After transmission of a radiogram, following the signature.
Invitation to transmit (any station)	K	After CQ and at the end of a transmission during QSO when there is no objection to another station breaking in.
Invitation to transmit (specific station, only)	KN	At the end of any transmission when only the specific station called or being contacted is invited to answer.
End of contact	SK	At the end of a QSO. SK W8LMN DE W5BCD.
Closing station	CL	When going off the air to indicate no calls will be listened for or answered. W7HIJ DE W2JKL CL



The main operating room is shown on the W1AW QSL. The equipment in the racks is used for code practice and bulletin transmissions.



The SSTV position at W1AW as operated by ARRL Deputy Communications Manager Jim La Porta, N1CC. The operating controls are placed so that the operator has easy access to the receiver, input controls and video character generator. The lens cap is kept within reach of the camera making it easy to "cap up" at the end of a transmission to protect the vidicon. A cassette tape recorder is also kept on line to record noteworthy pictures for future use.



The modern RTTY position at W1AW, operated by ARRL Public Service Communications Assistant Stan Horzepa, WA1LOU. Note the neat order of equipment. This permits the operator to select all RTTY converter functions while tuning the transceiver. The proximity of the keyboard to transmit controls and the visibility of the equipment operating parameters (plate current and frequency) make for convenient operating. The required cw identification is accomplished by changing mode on the HAL keyboard at the end of transmissions. Many stations have an fsk identification technique that uses a very small shifting network across the keyboard contacts.

something to learn about cw operating, additional proficiency goals you can achieve. ARRL offers a series of awards in this field, starting at 10 wpm and progressing all the way through 40 wpm, in 5-wpm increments. You will find more details elsewhere in this chapter and full details in the operating booklet.

Copying cw and comprehending it are not the same thing. The word "copy" implies something written, so "if you don't put it down, that ain't copying." On the other hand, for conversational cw purposes, copying really isn't necessary and can be quite cumbersome. Most beginners on cw learn by copying everything down, and some find this habit hard to break as they achieve higher levels of proficiency. However, it does involve a "translation" process that can and should be eliminated for conversational purposes. Sooner or later, in order to realize the full value of cw communication, you must learn to just listen to it, as you do the spoken word, rather than to "copy" it. It should not be necessary to translate the cw into written copy and then translate the written copy into intelligence by reading it. Eventually, the sound of code should directly trigger your consciousness just as the spoken word does, and then the "copy" and understanding functions are reversed; that is, you understand it first, then you copy it. If written copy is unnecessary, the function stops at understanding it.

No indeed, Cw is not just something that has been imposed on us to make passing the amateur test a little more difficult. It is an entirely different method of communication, and a long way from obsolete. Learn it well and you will enjoy ham radio much more.

### SSTV Procedures

The popularity of slow-scan television (SSTV) continues growing with more and more of the newer amateurs getting on this mode. To operate SSTV, first listen around the calling frequencies, then either respond on voice to a station calling "CQ SSTV" or call CQ SSTV yourself after first ascertaining that the frequency is not in use. Call CQ on voice in the normal manner adding "SSTV" to your call: "CQ SSTV CQ SSTV CQ SSTV this is K1WJ K1WJ K1WJ over." Once contact on voice is established, an exchange of video is undertaken. You should identify your video as you start your transmission and as you end transmission of video as follows: "K1KI this is K1WJ, video follows. SSTV pictures sent. OK, how do you like that one? K1KI this is K1WJ over." Questionable matter, visual as well as aural, should be reserved for the local coffee get-together, and not be put on the air. (Recently the FCC determined that amateur experimentation with another exotic mode would not be permitted and cited abuses of SSTV as the reason.)

SSTV operators should carefully moni-

tor their station audio to insure that they are not overmodulating (allowing the SSTV signal to exceed normal voice bandwidth limitations). It is possible to store properly modulated signals on ordinary cassette tape, so that you can play back some rare DX QSO, or a nice series of shack pictures to visitors in your shack when the band is dead, and you're not on the air.

### RTTY Procedures

Technical advances, availability of equipment, and lowering of the costs to get into RTTY have resulted in an increased interest among amateurs in RTTY operation. RTTY equipment operates at different speeds ranging from 60 to 100 words per minute. The standard speeds are 60, 67, 75 and 100 wpm, with the most common amateur speed being 60 wpm. The machine code used is the Baudot code.

Two methods of keying are generally used: First, frequency-shift-keying (fsk) utilizes either 170- or 850-hertz shift from mark to space; and secondly, audio-frequency-shift-keying (afsk) is referenced on a 2975-hertz mark tone shifting downward for space at either 170 or 850 hertz. The most common practices are for 170 hertz on fsk and 850 hertz on afsk. Because of these wide variations in practices and the multitude of mechanical and electronic machines on the market today, some standardization of procedures is helpful.

As in other modes of operation, the best thing to do is listen first! The typically pulsating tones of RTTY can easily be recognized by the beginner and tuned in on the station receiver (when interfaced with a demodulator) to detect the RTTY signal and change it into pulses usable by the teleprinter. The "RY" test signal, "CQ" (as well as your own call sign) can, after a brief period of listening, be easily identified aurally without looking at the printed page or display screen. The procedure for establishing contact is much the same as for cw — zero your vfo while copying and call the station on the same frequency. When using a transceiver be sure that the offset for transmitting your afsk through the ssb mode is pure and stable enough so that your signal will not exceed bandwidth limitations. Even though the other station finishes his CQ with a carriage return (CR) and line feed (LF), it is a good idea to get into the habit of transmitting these functions, to "clear the machine." Thus: (2CR) (LF) WAILOU WAILOU DE WIEH\*WIEH K (2CR) (LF). On hf at this time you must identify on cw at no more than 20 words per minute. If you are on vhf you have the option of identification on cw as above or voice identification.

To initiate a CQ, find an unused frequency in the band near the calling frequency and activate your transmitter,



sending: (2CR) (LF) CQ CQ CQ DE WAILOU WAILOU WAILOU K (CR) (LF).

During the QSO, when you come to the end of a line (or the end-of-line indicator on tape equipment), send (2CR) (LF) (2LTRS). That is, after your carriage return and line feed at the end of a line, the two nonprinting "letter" pulses serve to allow sluggish machines to get ready for the next line. This takes less than a second to send.

Most RTTY stations are also set up to send tape and many, as well, to reoperate tape from on-the-air signals. This enables the operator to prepare tape in advance with basic station information on the tape. Loops for calling CQ can be made up in advance. Storage on paper tape of received signals permits reference back to something sent by another station, such as a "teleprinter art form" for future use. When using automatic tape distributors to send your message, you eliminate the somewhat irksome pauses and jerkiness evident in a signal transmitted by an operator who does not type as fast as the machine (or who thinks a lot between words!). Many operators have the capability to send faster or slower. If you hear a signal that is too fast for your machine, try calling the station on cw (hf) or voice (vhf) and asking for a QRS. If the station has the capability, as on cw or voice, that request should be granted.

### OSCAR Procedures

OSCAR has been around a long time now, and procedures for operation have evolved. Notwithstanding the unique mode of operation of the OSCAR spacecraft, operating procedures are similar to those used on other modes. At this writing, two Phase II spacecraft, the AMSAT-OSCAR 7 and the ARRL-OSCAR 8, are in operation. They will be joined soon by the first Russian RS amateur spacecraft. All of these devices require the same procedures. The Phase III elliptical orbit satellites will require some changes in procedures as practices develop.

As with all types of communications on the amateur bands, begin by listening. The easiest listening is to the Mode A transponders in use on both OSCAR 7 and OSCAR 8. These transponders transmit on 29.4 through 29.5 MHz. Tune in the beacons after determining the spacecraft orbit time, equatorial crossing and bearing in relation to earth by using your OSCARLOCATOR from the ARRL publication *Getting to Know OSCAR*. You are now ready to look for signals in the downlink passband from 29.4 through 29.5 MHz. Some practice is needed to learn to follow the effects of Doppler shift on the signals. Cw operation is generally accomplished between 29.400 and 29.450 MHz, and ssb operation from 29.450 MHz up. However, you may find a cw or



During the final countdown phase OSCAR 8 was "mated" to the second stage of the launch vehicle. ARRL Satellite Coordinator Bernie Glassmeyer, (far right) W9KDR/1 and Southwestern Division Director Jay Holladay, W6EJJ, look on as solar array protective covers are mounted for prelaunch protection.

ssb signal anywhere in the passband of the transponder.

Now that you have learned to listen to OSCAR, the time to find out if you can transmit through the spacecraft has arrived. More than in any other situation the OSCAR user must use no more power necessary than that required to establish and maintain communications. In most cases an effective radiated power (erp) of 100 watts is more than adequate to access the spacecraft on Mode A. Tracking of the spacecraft, azimuth-elevation control of directional antennas and other details are treated in the above-referenced *Getting to Know OSCAR*. Once your station is ready to transmit you should select a frequency in the passband downlink that is devoid of signals. Interpolate the required uplink frequency and send a string of dits interspersed with your call sign for identification. While you are sending the dits, listen to the downlink for your signal, tuning at least plus and minus 10kHz from your computed downlink frequency to allow for Doppler effects and possible calibration error on your uplink transmitter. Once you have found your signal you have two choices. The first, and least desirable, is to call CQ. Calling CQ is done a bit differently on OSCAR than the other amateur modes. Your CQ should be a continuous call, and you should listen on your downlink frequency and nearby that point for stations calling you. When someone zeroes your signal or calls you, stop sending and reply to the station. This is full break-in operation at its very best, an almost duplex-type operation. The same procedures apply for voice and cw. A contact on OSCAR might go like this: CQ OSCAR CQ OSCAR CQ OSCAR this is N1CC N1CC November One Charlie Charlie CQ OSCAR CQ OSCAR CQ OSCAR this is N1CC November one . . . At this point a "ditter" zero beats the downlink signal. N1CC this is W2BXA 58 New York (without pause). W2BXA this is N1CC 59 Connecticut,

name is Jim. Contact established, signal reports exchanged. At this point contact can end or more details can be exchanged. This contact would take about 20 seconds on voice and 2 minutes on cw. With an average time of 15 minutes on a pass, many contacts can be made when efficient operating habits are displayed.

The use of RTTY, SSTV, a-m, fm and other steady-state carrier modes is not permitted on OSCAR, unless prior coordination is made with AMSAT for OSCAR 7 or ARRL for OSCAR 8 (as applicable for special experimental transmissions). Stations heard calling "CQ LOS" are looking for real DX, and are trying for over-the-horizon QSO via satellite. You should not reply to a station looking for loss-of-signal (LOS) contacts unless the obvious range on your OSCAR-LOCATOR places the calling station outside your normal range. Short, crisp, to-the-point contacts are very characteristic of OSCAR users. Numerous awards are available to OSCAR users and the spacecraft are acquiring more and more users. Now let's see, the next pass is in 30 minutes, so point your antennas, sharpen your pencil, and get ready for space-age fun with amateur radio.

### Working DX

Most amateurs at one time or another make "working DX" a major aim. As in every other phase of amateur work, there are right and wrong ways to go about getting best results in working foreign stations. This section will outline a few of them.

The ham who has trouble raising DX stations readily may find that poor transmitter efficiency is not the reason. He may find that his sending is poor, his call ill-timed, or his judgment in error. Working DX requires the know-how that comes with experience. If you just call CQ DX you may get a call from a foreign station, but it isn't likely to be a "rare one." On the other hand, unless you are experienced enough to know that conditions are right, your receiver is sensitive and selective enough, and your transmitter and antenna properly tuned and oriented, you may get no calls at all and succeed only in causing some unnecessary QRM.

The call CQ DX means slightly different things to amateurs on different bands:

a) On vhf, CQ DX is a general call ordinarily used only when the band is open, under favorable "skip" conditions. For vhf work, such a call is used for looking for new states and countries, also for distances beyond the customary "line-of-sight" range on most vhf bands.

b) CQ DX on our 7-, 14-, 21- and 28-MHz bands may be taken to mean "general call to any foreign station." The term "foreign station" usually refers to any station on a different continent. If you



do call CQ DX, remember that it implies you will answer any DX who calls. If you don't mean "general call to any DX station," then listen and call the station you do want.

### Codes and Ethics

One of the most effective ways to work DX is to know the operating habits of the DX stations sought, and to abide by the procedures they use. Know when and where to call, and for how long, and when to remain silent while waiting your chance. DXing has certain understood codes of ethics and procedures that will make this popular amateur pursuit more fun for everybody if everybody follows them. One of the sad things about DXing is to listen to some of the abuse that goes on, mostly by stations on "this" side, as they trample on each other trying to raise their quarry. DX stations have been known to go off the air in disgust at some of the tactics.

If W and VE stations will use the procedure in the "DX Operating Code" detailed elsewhere on these pages, we can all make a good impression on the air. ARRL has also recommended some operating procedures for DX stations aimed at controlling some of the thoughtless practices used by W/VE amateurs. A copy of these recommendations (CD-215) can be obtained free of charge from ARRL headquarters.

### Snagging the Rare Ones

Once in a while a CQ DX will result in snagging a rare DX contact, if you're lucky. This seldom happens, however; usually, what you have to do is listen — and listen — and then listen some more. You gotta hear 'em before you can work 'em! If everybody transmits, nobody is going to hear anything. Be a snooper. Usually, unless you are lucky enough to be among the first to hear him, a rare DX station will be found under a pileup, with stations swarming all over him like worker bees over a queen. The bedlam will subside when the DX station is transmitting (although some stations keep right on calling him), and you can hear him. Don't immediately join the pack; be a little cagey. Listen a while, get an idea of his habits, find out where he is listening (if not zero on himself), bide your time, and wait your chance.

Make your calls short, snappy and distinct. No need to repeat his call (he knows it very well, all he needs to know is that you are calling him), but send your own call a couple of times. Try to find a time when few stations are calling him and he is not transmitting; then get in there! With experience, you'll learn all kinds of tricks, some of them clever, some just plain dirty. You'll have no trouble discerning which is which. Learn to use the clever ones, and shun the dirty ones. More than you think depends on the

impressions we make on our foreign friends!

### Choosing Your Band

If it does nothing else in furthering your education, striving to work DX will certainly teach you a few things about propagation. You will find that four principal factors determine propagation characteristics: (1) the frequency of the band on which you do your operating, (2) the time of day or night, (3) the season of the year, and (4) the sunspot cycle. The proper choice of band depends pretty much on the other three factors. For example, the 3.5- to 4.0-MHz band at high noon in the summertime at the "node" part of the sunspot cycle is the poorest possible choice, while the same band at midnight during the wintertime at the "null" part of the cycle might produce some very exciting DX. Similarly, you will learn by experience when to operate on which band for the best DX by juggling the above factors using both long-range and other indications of band conditions. WWV transmissions can also be helpful in indicating both current and immediate-forecast band conditions.

On some bands, such as 10 and 6 meters, beacons have been established to give an indication of band openings. Listen between 28.2 and 28.3 MHz on 10 meters and around 50.110 MHz on 6 meters. Commercial stations near ham-band edges are also a fair indication of openings. But remember that many of these run many times the maximum amateur power, and consequently may be heard well before skip improves to the point necessary to sustain amateur communications.

Conditions in the transmission medium often make it possible for the signals from low-powered transmitters to be received at great distances. In general, the higher the frequency band, the less important power considerations become, for occasional DX work. This accounts in part for the relative popularity of the 14-, 21- and 28-MHz bands among amateurs who like to work DX.

### DX Century Club Award

The DXCC is one of the most popular and sought-after awards in all of amateur radio, and among the more difficult to acquire. Its issuance is carefully supervised at ARRL headquarters by three staff members.

To obtain DXCC, an amateur must make two-way contact with 100 "countries" on the ARRL DXCC List. Written confirmations are required for proof of contact. These must show clearly your call sign, date, time, frequency and mode. Such confirmations must be sent to ARRL headquarters, where each one is carefully scrutinized to make sure it actually confirms a contact with the applying amateur, that it was not altered or tampered with,



and that the "country" claimed is actually on the ARRL list. Further safeguards are applied to maintain the high standards of this award. A handsome, king-size certificate and "DXCC" pin are sent to each amateur qualifying.

The term "country" is an arbitrary one, not necessarily agreeing with the dictionary definition. For DXCC purposes, many bodies of land not having independent status politically are classified as countries. For example, Alaska and Hawaii, while states of the U.S., are considered separate "countries" because of their distance from the mainland. There are over 300 such designations on the ARRL list. Once a basic DXCC is issued, the certificate can be endorsed, by sticker, for additional countries by sending the additional cards in to headquarters for checking.

Separate DXCC awards are available for mixed modes, all phone, call cw, RTTY, 160 meters and satellite.

Before applying, familiarize yourself with full information. Application forms (CD164) and the ARRL DXCC List (detailing rules) may be obtained from Headquarters for a stamped addressed envelope.

### Five-Band DXCC

Entirely separate from DXCC, ARRL also offers a Five-Band DXCC (5BDXCC) Award for those amateurs who submit written proof of having made two-way contact with 100 or more countries on each of five amateur bands since January 1, 1969.

For a copy of the complete rules, drop a line to ARRL Headquarters, 225 Main St., Newington, CT 06111.

### DX Operating Code (For W/VE Amateurs)

The points below, if observed by all W/VE amateurs, will go a long way toward making DX more enjoyable for everybody.

1) Call DX only after he calls CQ, QRZ?, signs  $\overline{SK}$ , or phone equivalent thereof.

2) Do not call a DX station.

a) on the frequency of the station he is working until you are sure the QSO is over. This is indicated by the ending signal  $\overline{SK}$  on cw and any indication that the operator is listening, on phone.



b) because you hear someone else calling him.

c) when he signs  $\overline{KN}$ ,  $\overline{AR}$ ,  $\overline{CL}$  or phone equivalents.

d) exactly on his frequency.

e) after he calls a directional CQ, unless of course you are in the right direction or area.

3) Keep within frequency-band limits. Some DX stations operate outside. Perhaps they can get away with it, but you cannot.

4) Observe calling instructions of DX stations. "10U" means call 10 kHz up from his frequency, "15D" means 15 kHz down, etc.

5) Give honest reports. Many foreign stations depend on W and VE reports for adjustment of station and equipment.

6) Keep your signal clean. Key clicks, chirps, hum or splatter give you a bad reputation and may get you a citation from FCC or DOC.

7) Listen for and call the station you want. Calling CQ DX is not the best assurance that the rare DX will reply.

8) When there are several W or VE stations waiting to work a DX station, avoid asking him to "listen for a friend." Let your friend take his chances with the rest. Also avoid engaging DX stations in rag chews against their wishes.

### WAC Award

The ever-popular Worked All Continents Award (WAC), sponsored by the International Amateur Radio Union (IARU), can be yours by simply submitting proof of contacts with each of the six continents. Two-way confirmed contacts must be made with amateurs in each of six continental areas of the world: Africa, Asia, Europe, North America, Oceania and South America. Confirmations submitted with all cw or mixed cw and phone will receive the basic award. Special endorsements include 1.8 MHz, 3.5 MHz, 50 MHz, RTTY, SSTV, ssb and phone. A unique version of the award is available for working all continents on each of five or six bands after January 1, 1974. Amateurs residing in the USA or its possessions and Canadian amateurs may obtain full details about the WAC Awards from ARRL headquarters. QSLs (not copies) must be sent to ARRL headquarters for checking. Applicants in other

countries must send QSLs to their IARU amateur society, the latter of which will certify their eligibility to the IARU headquarters society (ARRL) for issuance of the award on behalf of the Union. Applicants in countries not belonging to the IARU society may send their QSLs direct to ARRL headquarters for checking. IARU member-society addresses will be sent, upon request, to those amateurs who do not reside within continental limits of the USA, its possessions or Canada.

### Awards

League-sponsored operating activities have useful objectives and provide much enjoyment for members of the fraternity. Achievement in amateur radio is also recognized by various awards offered by ARRL and detailed below. Basic rules require that sufficient funds be included with all submission of cards to ensure their safe return. A basic fee for return postage is included with each award application. Applications in the U.S., its possessions and Canada must be ARRL members to participate in the WAS and DXCC programs. (Novices and DX stations are exempted from this requirement.)

### WAS Award

"WAS" means Worked All States. This award is universal and may be obtained by any amateur who has worked each of the U.S. states and submits original proof of contacts to ARRL headquarters for examination. Contacts may be made over any period of time on any or all of the amateur bands.


Special endorsements are also available for WAS on cw, ssb, phone, all on one band, and so on — confirmations must clearly state that contact took place under circumstance of desired endorsement. QSLs must be accompanied by sufficient postage for their safe return. Please send an s.a.s.e. to the ARRL. Communications Department before mailing QSLs, and request a copy of the rules and application, which will include a guideline for postage fees for return of cards.

### 5B WAS Award

A handsome, specially engraved plaque will be issued to all amateurs who submit original proof of contact with all of the 50 states on each of five amateur bands, made after January 1, 1970 (only contacts made after that day will be eligible). Rules require applicants in the U.S., its possessions and Canada to be full ARRL members. Standard WAS rules apply. Write to ARRL for the application, full rules and QSL postage fee return.
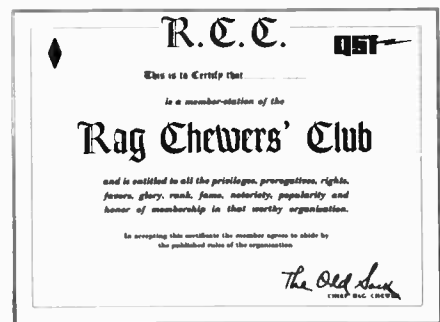
### 6-Meter "600 Club"

The 6-Meter "600 Club" award counts contacts made on 6 meters on or after January 1, 1977. A total of 600 points is



required. Scoring is based on the sum of QSOs (times 2), ARRL sections (times 6) and countries (times 25). Some of the scoring areas are complex so be sure to send in for a form before you apply. Applicants must include sufficient postage for safe return of QSLs. Applicants in the



U.S., its possessions and Canada must be full members to apply.

### **Satellite "1000" Award**

This award, known also as the Satellite Achievement Award, is gaining in popularity as more amateurs are mastering the art of using the OSCAR communications satellites. Contacts count if made on or after December 15, 1972. Only one contact per station is accepted, regardless of mode. Each contact with a new station counts 10 points, with a new country 50 points and with a new continent 250 points. To qualify for this award, amass 1000 points. An s.a.s.e. to the League will provide you with complete rules and an application form.

### **A-1 Operator Club**

The A-1 Operator Club should include in its ranks every good operator. To become a member one must be nominated by two persons who already belong. General keying (not speed) or voice technique, procedure, copying ability, judgment and courtesy all count in rating candidates under the club rules. These are detailed at length in the booklet *Operating an Amateur Radio Station*. Aim to make yourself a fine operator and one of these days you will be pleasantly surprised when your mailman arrives at your QTH with your certificate of membership in the A-1 Operators Club.

### **Old-Timers Club**

If you held an amateur radio license 20 or more years ago and are licensed at the present time, you are eligible to become a member of the Old Timers Club. Lapses in activity during intervening years are permitted. OTC members may sign "OTC" after their call to indicate their seniority. An s.a.s.e. (legal-size, at least 10 × 4 inches) will expedite your certificate.

### **Rag Chewers Club**

Your first contact as a licensed amateur may very well earn your first award. The Rag Chewers Club is designed to encourage friendly contacts and discourage the "contest" type of QSO with nothing more than an exchange of calls, signal reports, and so on. It furthers fraternalism through amateur radio.

Membership certificates are awarded to amateurs who report a fraternal-type contact with another amateur lasting a half hour or longer. This does not mean a half hour spent trying to work a rare DX station, but a solid half hour of pleasant "visiting" with another amateur, discussing subjects of mutual interest, and getting to know each other. If nominating someone for RCC, please send the information to the nominee who will (in turn) apply to Headquarters for membership. Or if you know you qualify for the RCC, just report the conversation to ARRL (c/o RCC) and back will come

your member certificate. A legal-size envelope (at least 10 × 4 inches) is appreciated when requesting this award.

### **Code Proficiency Award**

Many hams can follow the general idea of a contact "by ear," but when pressed to "write it down" they "muff" the copy. The Code Proficiency Award permits each amateur to prove himself as a proficient operator, and sets up a system of awards for step-by-step gains in copying proficiency. It enables every amateur to check his code proficiency, to better that proficiency, and to receive a certification of his receiving speed.

This program is a lot of fun. The League will award a certificate to any interested individual who demonstrates that he can copy perfectly for at least one minute, plain-language Continental code at 10, 15, 20, 25, 30, 35 or 40 words per minute, as transmitted twice monthly from WIAW and once a month from W6OWP.

As part of the ARRL Code Proficiency program WIAW transmits plain-language practice material several times daily at speeds from 5 to 35 wpm, occasionally in reverse order. All amateurs are invited to use these transmissions to increase their code-copying ability. Nonamateurs are invited to utilize the lower speeds, 5, 7-1/2 and 10 wpm, which are transmitted for the benefit of persons studying the code in preparation for the amateur license examination. Check the WIAW material earlier in this chapter and/or refer to any issue of *QST* for details.

### **Contesting**

Contesting is to amateur radio what the Olympic Games are to worldwide amateur athletic competition: a showcase to display talent and learned skills, as well as a stimulus for further achievement through competition. Increased operating skills and greater station efficiency are the predominant end results of amateur radio contesting, whether the operator is a serious contender or a casual participant.

Don't believe it? Tune across the band, any band, and listen for the most efficient operators. Chances are better than even that they are avid testers or at least have contesting as one of their favorite amateur radio activities. How can one tell who is a tester just by listening to a particular operator's style? It is easier to tell who is *not* interested in contesting by listening. The tester is *not* likely to be the one, who (while thousands on frequency are gnashing their teeth in anger) asks the operator of the rarest DXpedition in two decades what the weather is like in "Lower Slobbovia." The tester is *not* likely to be the operator who, when working a much-sought-after station on one of the many awards nets, punctuates his repeating of the needed exchange 37 times with a long series of



A typical contest station (WA3WIK shown here) will vary in equipment configuration from operator to operator, but in all cases the underlying themes of efficiency and ease of operation will be apparent.

"uhhs, duhs" and assorted other noises for the lack of anything better to say. The contest operator knows from experience that conciseness and brevity are aids in efficient and courteous operating.

The contest operator is also likely to have one of the better signals on the band — not necessarily the most elaborate station equipment, but a signal enhanced by the most efficient use of station components available. Contest operation encourages optimization of station and operator efficiency.

The ARRL Contest Program is so diverse that it holds appeal for almost every operator — the beginning tester and the old hand, the newest Novice and the oldest Extra-Classer, "Top Band" buff and microwave enthusiast.

A thumbnail sketch of each contest sponsored by the ARRL (grouped according to the month of occurrence) follows. Complete entry rules and details appear in *QST*, usually the month before the contest occurs.

### **January**

**Straight Key Night.** A low-key operating event. Twenty-four hours of cw operating, no automatic or semi-automatic keys/keyers allowed. Participants nominate each other for "Best Fist" and "Most Interesting QSO" honors.

**CD (Communications Department) Party.** One weekend each of phone and cw, where CD appointees only work each other in a QSO party format.

**VHF Sweepstakes.** Premier vhf operating event. All bands, 50 MHz and up. ARRL affiliated-club competition, based on members' aggregate total scores. \*

### **February**

**Novice Roundup.** Competition geared for the beginning (Novice and Technician) amateur. Increase code speed through operating, work stations needed for WAS, and other achievements. Awards for ARRL Section winners. Fun for all.

### **March**

**International DX Competition.** W/VE amateurs work the rest of the world for individual section, country and ARRL





Some of the various awards given high-score participants in ARRL-sponsored contests. Included above are several of the individual certificates, the Affiliated Club gavel and the plaque awarded to the highest-scoring single-operator stations on each continent in the ARRL International DX Competition.

affiliated club honors. During two weekends; one is phone only, the other for cw.

#### April

**"Open" CD Party.** One weekend each of phone and cw. Open to all ARRL members, as well as CD appointees. Same format as "closed" parties in January and October. Exchange appointment and/or membership status (i.e. member, life member, charter life member) and ARRL Section.

**EME Contest.** First weekend of two for moonbounce enthusiasts. Listeners reports as well as active participants' entries are welcomed.

#### May

**EME Contest.** Second part of same contest, begun in April.

#### June

**VHF QSO Party.** One of two vhf QSO parties. This one (and the September party) lends itself to multioperator expedition operations. Use all bands above 50 MHz. ARRL sections and DXCC "countries" are scoring multipliers.

**Field Day.** The *number one* operating event of the year. Upwards of 20,000 participants take to the fields to operate some 1500 emergency stations for informal competition, a score listing in *QST* and an all-around good time. Don't miss this one.

#### July

**Straight Key Night.** Second of two such events held each year (see January).

**IARU Radiosport Championship.** World-wide competition. Everybody works everybody else for continental, country and ARRL section honors. Varying point scale, ITU zones are scoring multipliers. Some of those hard-to-work DXCC countries turn out for this contest.

#### August

**UHF Contest.** Similar to the vhf contests, but utilizes the 220 MHz and above bands. Scoring multipliers are determined by the longitude/latitude

co-ordinates of the participants. The uhf bands come alive for this contest weekend.

#### September

**VHF QSO Party.** Second of two vhf QSO parties (see June also).

#### October

**CD Party.** Same as the January CD Party. For CD appointees only.

#### November

**Sweepstakes.** The A number 1 most prestigious domestic contest. Two weekends (actually separate contests and separate listings), one weekend for phone and one weekend for cw. Twenty-four hour time limit on each mode. W and VE operators work each other. ARRL sections are the scoring multipliers. Awards for both high and low power ARRL section winners. An ARRL-affiliated club competition highlights the Sweepstakes activity.

#### December

**160-Meter Contest.** A gathering of "top band" enthusiasts. W/VE types work each other and DX stations for contest credit.

**10-Meter Contest.** The last (but certainly not least) one on the year's contest calendar. A 10-meter operator's dream come true as 28 MHz springs to life and everyone, worldwide, tries to work everyone else for top scorer (in country, continent and ARRL section) honors.

That's the ARRL Contest Program in a nutshell. Of course, more detailed rules and descriptions of the award structure (certificates and plaques awarded to designated top scorers) are announced in *QST* for each of these events. The monthly "Operating Events" column of *QST* also details the entry rules for many contests other than those sponsored directly by ARRL including the very popular state QSO parties and most other major contests.

#### Public Service

Tens of thousands of U.S. and Canadian amateurs are involved with public service. Where do you fit in? Just about wherever you want to. There's a place for every ham in the League's Amateur Radio Public Service Corps. ARPSC has two principal divisions: the Amateur Radio Emergency Service (ARES) is an emergency-preparedness group of approximately 50,000 amateurs who have signed up voluntarily to keep amateur radio in the forefront of public service operating. The National Traffic System (NTS) functions as a message-handling network operating 365 days a year for the systematic handling of third-party traffic.

Also recognized by ARRL as a part of the organized public service effort are the Radio Amateur Civil Emergency Service

(RACES), a part of the Amateur Service serving civil defense under a separate subpart of the amateur regulations; the Military Affiliate Radio System (MARS), sponsored by the armed forces to provide military communications training for amateurs; and the numerous amateur groups organized into nets or monitoring services by individuals, clubs or other amateur entities for public service. The detailed workings of the League's emergency and traffic programs are covered briefly herein and in more depth in the *Public Service Communications Manual* and *Operating an Amateur Radio Station*, available from ARRL hq.

#### ARES and NTS — How it Applies to You

As a member of the local ARES group, you'll be training to provide communications at the city or county level. Each group is headed by an ARRL Emergency Coordinator. Most ARES activities are centered on 2-Meter fm, so it's advantageous to have your own emergency-powered vhf gear. However, you really don't need any equipment to join; it's the training and practice that are most important. All you really need is an interest in serving your community through amateur radio. Full members pledge to participate actively in periodic tests of readiness capability, while limited members participate only as time permits. What kinds of tests? Well, they run the gamut from serious simulated emergencies to providing communications for parades and walkathons, or conducting a message-handling service at a shopping center during the Christmas season. Many hams have trained with the National Weather Service to become tornado and storm spotters. All these activities exist, so that when a flood or an ice storm disrupts



WA6VRK was one of 40 amateurs who provided communications for the five-day National Wheelchair Games in San Jose, CA. Roy used a unique rig; it consisted of two lead-acid motorcycle batteries built into a backpack. The rig was an ICOM IC-3211 into a modified discone antenna that strongly resembled a broken umbrella.

The ARRL Communications Department makes available the following free operating aids for public service communications:

### Operating an Amateur Radio Station

Public Service Communications Manual	CD-235
Net Directory	CD-50
ARRL numbered radiograms	CD-3
Sample emergency plan	CD-27
ARES registration form	CD-98
Emergency reference information	CD-209
Before/during/after emergency	CD-214
Amateur message form	CD-218
Ready reference information	CD-219

This entire Public Service Package can be had by sending a large (9 × 12-inch) envelope with postage for seven ounces, first class.


Information concerning the Military Affiliate Radio Service (MARS) may be obtained directly from the individual branches at the addresses listed below:

Air Force MARS:  
Chief, USAF MARS  
HQ AFCS/DOYR  
Scott AFB, IL 62225

Army MARS:  
Commander  
USAAC  
ATTN: CC OPS OM  
Ft. Huachuca, AZ 85613

Navy-Marine Corps MARS:  
Chief, Navy-Marine Corps  
MARS  
Eight & Courthouse Road  
Building 17  
Arlington, VA 22204

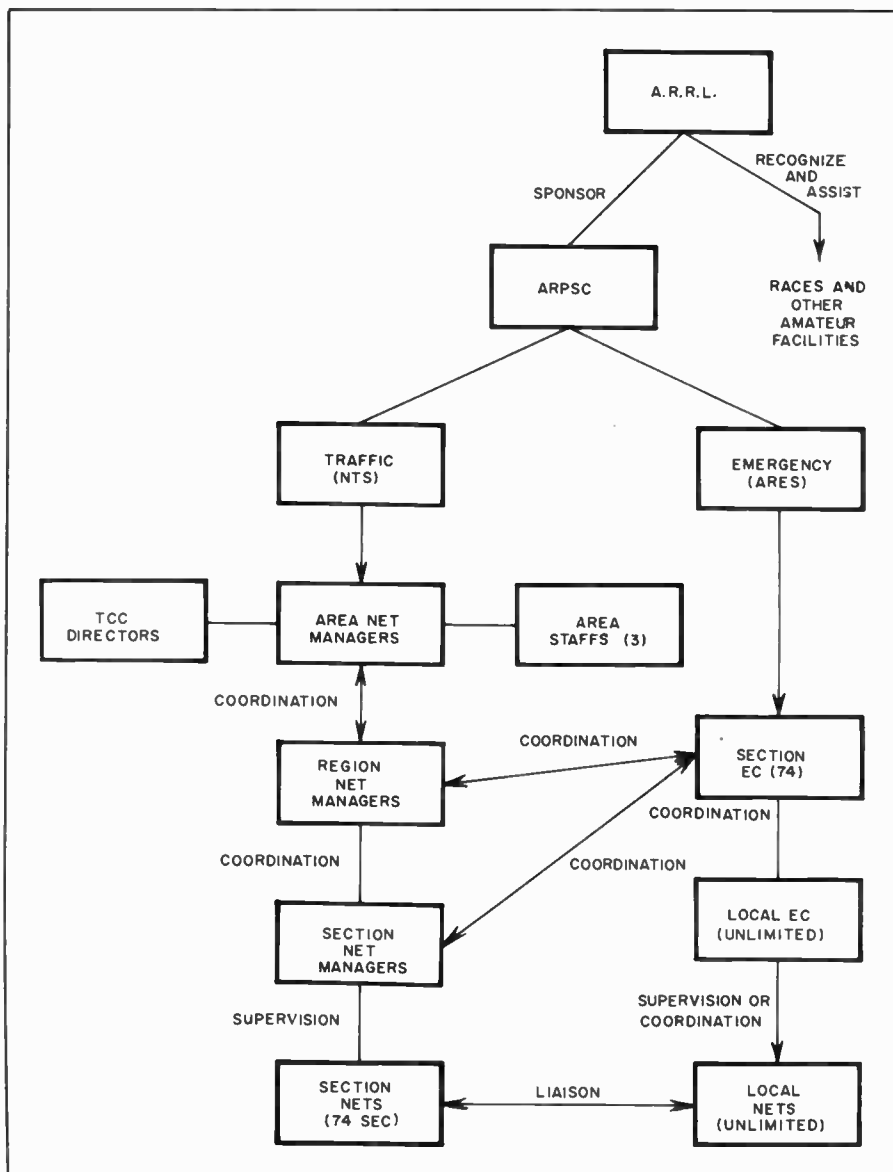Information on the RACES program is available from the Defence Civil Preparedness Agency, Washington, DC 20301.



the community, experienced hams will know exactly what to do.

Becoming involved is as simple as requesting a registration card (CD-98) from the ARRL Communications Department and filling it out. These cards are turned over to the local EC, who registers you in the local ARES organization. Should your community not have an EC, why not volunteer yourself? You qualify if you are a licensed amateur of Technician class or higher, an ARRL member, have a sincere interest in public service and a willingness to put in the time and effort to fulfill the appointment. If this sounds like you, contact your Section Communications Manager. His name, address and telephone number appear on page 8 of each issue of *QST*.

The bulk of recent localized emergency communications have been handled vhf. Much has involved repeater operation. The reason is simple: Repeaters can be accessed with low-cost and lightweight equipment, handheld or mobile. Best of

all, they provide clear, reliable communications up to 100 miles or so. Many repeaters have emergency power capabilities as well, making them the mainstay of any widespread emergency.

What's the National Traffic System all about, then? NTS serves a dual purpose: The rapid movement of long-haul traffic from origin to destination and the training of amateur operators in the handling of formal radiogram traffic in efficient directed nets. A rundown of the NTS schedule of nets and functions can be found in the *Public Service Manual*. However, in the overview, NTS can be visualized as somewhat of a pony express of the airwaves, with assigned amateurs (rather than cowboys) carrying traffic to and from the next higher (or lower) level in the system. NTS operations are concentrated mainly on the high frequencies (hf), but local nets on 2 meters are becoming more and more popular as the ideal place to distribute traffic for delivery after the long journey.

Most ARRL sections have section nets on 80 meters, both phone and cw. You can find the traffic and emergency nets that serve your area in the annual *ARRL Net Directory* (free with an s.a.s.e.). Directed net procedures, especially on cw, take a little getting used to, but if you consult the League's reference material and do a little monitoring beforehand, you shouldn't have much problem. In fact, there are many slow speed nets which meet on the Novice frequencies, which are a boon to learning the simple procedures.

Each day, hams enjoy the challenge of these activities. Why not check into a net and check it out!

### What You Should Do

Before an emergency occurs, prepare for it by keeping your station and emergency power supply (if you have one) in good working order. Participate in the annual nationwide Simulated Emergency Test, contests and Field Day.

Register your station with your local

# AMATEUR MESSAGE FORM

Every message originated and handled should contain the following component parts in the order given:

**I PREFAMBLE**

a. Number (begin with 1 each month or year)  
 b. Precedence (R, Q, P or EMERGENCY)  
 c. Handling Instructions (optional, see text)  
 d. Station of Origin (first amateur handler)  
 e. Check (number of words/groups in text only)  
 f. Place of Origin (not necessarily location of station of origin)  
 g. Time Filed (optional with originating station)  
 h. Date (must agree with date of time filed)

**II ADDRESS** (as complete as possible, include zip code and telephone number)

**III TEXT** (limit to 25 words or less, if possible)

**IV SIGNATURE**

## CW MESSAGE EXAMPLE

I NR I R HXA WIAW B NEWINGTON CONN 1830Z July 1  
a b c d e f g h

II DONALD R SMITH AA  
 164 EAST SIXTH AVE AA  
 NORTH RIVER CITY MO 00789 AA  
 PHONE 733-3968 BT

III HAPPY BIRTHDAY X SEE YOU SOON X LOVE BT

IV DIANA AR

**CW:** Note that X, when used in the text as punctuation, counts as a word. The prosign AA separates the parts of the address. BT separates the address from the text and the text from the signature. AR marks end of message; this is followed by B if there is another message to follow, by N if this is the only or last message. It is customary to copy the preamble, parts of the address, text and signature on separate lines.

**RTTY:** Same as cw procedure above, except (1) use extra space between parts of address, instead of AA; (2) omit cw procedure sign BT to separate text from address and signature, using line spaces instead; (3) add a CFM line under the signature, consisting of all names, numerals and unusual words in the message in the order transmitted.

**PHONE:** In general, use *prowords* in place of procedural signals or *prosigns*. The above message on phone would go something like this: "Message Follows Number one, routine, HX Alpha, WIAW, check eight, Newington, Connecticut, one eight thuhree zero zulu, July one, to Donald Initial R Smith, Figures one six fower, East Sixth Avenue, North River City, Missouri zero zero seven eight nine, Fone sev-ven thuhree thuhree, thuhree niyen six eight. Break Happy Birthday X-ray see you soon X-ray love Break Diana, End of Message. Over." Speak in measured tones, emphasizing every syllable. Spell out phonetically all difficult or unusual words, but do not spell out common ones.

## PRECEDENCES

The precedence will follow the message number. For example, on cw 207R or 207 EMERGENCY. On phone, "Two Zero Seven, Routine (or Emergency)."

**EMERGENCY** - Any message having life and death urgency to any person or group of persons, which is transmitted by amateur radio in the absence of regular commercial facilities. This includes official messages of welfare agencies during emergencies requesting supplies, materials or instructions vital to relief of stricken populace in emergency areas. During normal times, it will be very rare. On cw, this designation will always be spelled out. When in doubt, do not use it.

**PRIORITY** - Important messages having a specific time limit. Official messages not covered in the "Emergency" category. Press dispatches and other emergency-related traffic not of the utmost urgency. Notification of death or injury in a disaster area, personal or official. Use the abbreviation P on cw.

**INQUIRY** - Messages pertaining to the health or welfare of persons in a disaster should carry this precedence, which is abbreviated to Q on cw. These messages are handled after PRIORITY traffic but before ROUTINE.

**ROUTINE** - Most traffic in normal times will bear this designation. In disaster situations, traffic labeled "Routine" (R on cw) should be handled last, or not at all when circuits are busy with emergency, priority or inquiry traffic. Most traffic handled on amateur circuits in normal times will fall in this category.

## W1AW Special Emergency Bulletin Schedule

Phone on the hour: 1835, 3990, 7290, 14290, 21390, 28590, 50190, 147555 kHz. RTTY 15 minutes past the hour: 3625, 7095, 14905, 21095, 28095, 147555 kHz. Cw on the half hour: 1835, 3580, 7080, 14080, 21080, 28080, 50080, 147555 kHz.



Hundreds of amateurs assisted the relief efforts during the Johnstown Flood. Pictured here is one of the command posts, at the Conemaugh Valley Memorial Hospital.

the 5 - 15 wpm transmissions. Two code proficiency qualifying runs are sent each month; details are in the operating news column in QST.

## EST/EDST PST/PDST

Speeds  
5, 7-1/2, 10, 13, 15

9 A.M. MWF 6 A.M. MWF  
7 P.M. MWF 7 P.M. MWF  
4&10 P.M. TTHSSU 1&7 P.M. TTHSSU

Speeds  
35, 30, 25, 20, 15, 13, 10

9 A.M. TTH 6 A.M. TTH  
7 P.M. TTHSSU 4 P.M. TTHSSU  
4 and 10 P.M. MWF 1 and 7 P.M. MWF

## Bulletins

Cw bulletins at 18 wpm are sent daily at 5, 8 and 11 P.M. EST/EDST, and Monday through Friday at 10 A.M. Frequencies are the same as those used for code practice.

Teletype bulletins, at 60 WPM with 170-Hz shift, are daily at 6, 9 and 12 P.M. EST/EDST and Monday through Friday at 11 A.M. Frequencies are 3.625, 7.095, 14.095, 21.095, 28.095 and 147.555 MHz.

Voice bulletins are daily at 9:30 P.M. and 12:30 A.M. EST/EDST on 1.835, 3.990, 7.290, 14.290, 21.390, 28.590, 50.19 and 147.555 MHz.

A complete W1AW schedule is available from ARRL headquarters for s.a.s.e.

## General Operation

W1AW is equipped for operation on all bands from 1.8 to 144 MHz, and for RTTY, SSTV and satellite communication as well as for cw, ssh, and nbfm. Schedules for contact with W1AW can be arranged.

EC. During an emergency, report to him at once and follow his suggestions.

Monitor your local emergency net frequency, but don't transmit unless you are specifically requested to or are certain you can be of assistance.

Copy special W1AW bulletins for latest developments.

Use your receiver more, your transmitter less. Interference can be intense during an emergency.

After an emergency, tell your EC or net manager of your activities, so he can submit a timely report to ARRL hq. Each month, QST chronicles amateur radio's emergency communications efforts. Participants in the reported events receive the "Public Service Award."

The Amateur Radio Service has been a vital part of emergency communications for more than 50 years, whether it be relaying medical traffic into an earthquake-ravaged village in South America, answering a "Mayday" from a ship in the Pacific Ocean, or finding out if a neighbor's relative survived a blizzard in the Midwest.

Why not become a part of it!

## W1AW: ARRL Hq. Station

The Maxim Memorial Station, W1AW, is dedicated to service to the amateur fraternity. It is adjacent to the Headquarters offices and is operated by the Headquarters Operators Club. Operating hours are 7:30 A.M. to 1:00 A.M. Monday through Friday and 3:30 P.M. to 1:00 A.M. Saturday and Sunday. The station is open to visitors at all times it is in operation. If you wish to operate W1AW while visiting, the period between 1:00 and 4:00 P.M. Monday through Friday is available. Be sure to bring your original FCC license with you if you plan to operate.

## W1AW Code Practice

Code practice is sent on approximately 1.835, 3.58, 7.08, 14.08, 21.08, 28.08, 50.08 and 147.555 MHz. Texts are from recent issues of QST and checking references are sent several times in each session. For practice purposes, the order of words in each line of text may be reversed during



# OSCAR Data Sheet

The year 1978 was a banner year for the Amateur Satellite Program. AMSAT (Radio Amateur Satellite Corporation) and ARRL joined forces to design, build and test OSCAR 8. It was the first amateur spacecraft built by the combined forces of AMSAT, Project OSCAR and ARRL. Nations contributing to the effort included Canada, Japan, the U.S.A. and West Germany.

The primary missions of OSCAR 8 are to continue the OSCAR Educational Program, further amateur radio space communications technology and provide an active satellite well into the upcoming Phase III program.

OSCAR 8 was launched by NASA March 5, 1978, from Vandenberg AFB, CA, aboard a Thor-Delta rocket.

Following its "textbook" launch, OSCAR 8 was tested thoroughly by

AMSAT and ARRL. After a brief period of performance testing, Operational Management duties were assumed by ARRL hq. to enable AMSAT to devote full time to the first Phase III satellite. AMSAT is planning a Phase III elliptical orbit satellite and a transponder to bolt onto a geostationary satellite.

Anyone, amateur radio operator or not, can receive a commemorative, multi-color QSL card by sending a report of telemetry received from OSCAR 8. (See beacon frequencies elsewhere on this page.) Mail reports to ARRL hq.

For further information about the satellite program, contact ARRL hq.

## Nets and Bulletins Schedules

The following AMSAT nets meet regularly to disseminate information about amateur radio satellites and general

vhf-uhf operating (times and days are in UTC):

East Coast Net — 0100 Wed.,

3850 kHz, lsb

Mid-Continent Net — 0200 Wed.,

3850 kHz, lsb

West Coast Net — 0300 Wed.,

3850 kHz, lsb

International Net — 1800 Sun.,

14280 kHz, usb.

All amateur radio operators holding the proper class of license are welcome to participate.

Bulletins of general interest are transmitted regularly on OSCAR 7 and OSCAR 8 reference orbits. Special demonstrations or experiments can be arranged for OSCAR 7 and OSCAR 8. Contact AMSAT (P. O. Box 27, Washington, DC 20044) for OSCAR 7 operations and ARRL hq. for OSCAR 8 operations.

## OSCAR 7 Orbital Parameters

Period: 114.945255 minutes.  
 Increment: 28.737647 degrees  
 Eccentricity: 0.0012052 degrees.  
 Inclination: 101.5230 degrees.  
 Maximum Height: 1443.0 km.  
 Minimum Height: 1478.4 km.  
 Measured Reference Orbit:

Orbit Date	Hr.Min.Sec.	Long. W.
17531 15 Sept. 78	0121:14.4 UTC	79.42°

## OSCAR 8 Orbital Parameters

Period: 103.232620 minutes.  
 Increment: 25.808461 degrees.  
 Eccentricity: 0.0008316 degrees.  
 Inclination: 98.9635 degrees.  
 Maximum Height: 910.372 km.  
 Minimum Height: 898.259 km.  
 Measured Reference Orbit:

Orbit Date	Hr.Min.Sec.	Long. W.
2697 15 Sept. 78	0130:09.6 UTC	63.30°

## Spacecraft Frequencies

Mode	OSCAR 7		OSCAR 8	
	Uplink (MHz)	Downlink (MHz)	Uplink (MHz)	Downlink (MHz)
A	145.850 to 145.950	29.400 to 29.500	145.850 to 145.950	29.400 to 29.500
B	432.125 to 432.175	145.975 to 145.925		
J			145.900 to 146.000	435.100 to 435.200
Beacons	Mode A:	29.502	Mode A:	29.402
	Mode B:	145.972	Mode J:	435.095

Notes: (1) OSCAR 7 operates on Mode A on days of the year evenly divisible by 3 (e.g. February 2 is day 33), and in Mode B on other days. Wednesdays are reserved for experimental purposes. (2) OSCAR 8 operates in Mode A on Monday, Tuesday, Thursday and Friday, and in Mode J on Saturday and Sunday. Wednesdays, experimental days, vary in mode. (3) Both the Mode B and Mode J transponders invert signals, that is, turn them "upside down." A signal from the ground transmitted on the low end of the uplink passband will return to your station on the high end of the downlink passband and vice versa. Thus, an upper sideband signal returns as a lower sideband signal. Mode A does not invert. (4) Mondays UTC have been designated QRP orbits — use a maximum of 10 watts erp when transmitting.

# INDEX

- Absorption: 18-3
- Absorption frequency meter: 16-14
- Acceptors: 4-2
- Accu-Keyer: 11-8
- Accu-Memory: 11-7
- Accuracy:
  - Bridge: 16-10
  - Instruments: 16-2, 16-7
  - Line decoupling: 15-6
- Ac-operated power supplies: 5-1
- Active: 3-19
  - Networks: 3-13
  - Region, transistor: 4-19
- Admittance: 2-34
- A-Index: 18-8
- Alpha: 4-17
  - Cutoff: 4-17
- Alternating current: 2-17
- Alternator: 10-2, 10-6
- Aluminum, finishing: 17-5
- Aluminum tubing: 20-22
- Amateur Radio: 1-1
- Amateur Radio Emergency Service: 22-11
- Amateur Radio history: 1-3
- American Radio Relay League: 1-4
- American War Standard: 17-9
- Ampere: 2-2, 2-5
- Amplifier:
  - Amplification factor: 3-15
  - Audio: 4-20, 4-39
  - Broadband: 4-22
  - Common-source rf: 9-2
  - Conduction-cooled 2-kW: 6-48
  - Conduction-cooled, 432-MHz: 7-19
  - Cooling: 7-11, 7-24
  - Design: 6-1
  - Efficiency: 7-3, 7-27
  - Efficiency measurement: 7-18
  - Gain: 3-15
  - Grounded-grid: 6-25
  - Grounded-grid 50-MHz: 7-11
  - Instability: 3-16
  - Intermediate frequency: 8-19
  - Linear, a-m: 6-25
  - Low-drive 2-meter PA: 7-24
  - Low-drive 6-meter PA: 7-23
  - Nonlinearity: 12-26
  - Novice "1/4 gallon": 6-43
  - Parallel: 6-25
  - Push-pull: 6-25, 15-4
  - Rf: 8-15
  - Rf power circuitry: 6-21
  - Rf, transistor: 4-20
  - Speech: 12-13
  - Stabilizing: 6-30
  - Transistor: 4-18, 6-27
  - Triode: 3-14
  - "Universal" three-band linear: 6-45
  - Voltage: 12-14
  - 2-kW PEP, 144 MHz: 7-16
  - 2-kW, 8877: 6-50
  - 2-meter, rf power: 13-23
  - 140-W solid-state linear: 6-41
  - 220-MHz high-power: 7-9
  - Amplitude compandor: 14-1, 14-4
  - Amplitude modulation: 6-24
  - Analog: 3-19
  - AND gate: 4-42
  - Antenna:
    - Assorted data: 20-22
    - Base-loaded: 10-8
    - Center-loaded: 10-8
    - Collinear: 21-8
    - Conductor size: 20-3
    - Dipole: 20-3
    - Dummy: 16-21
    - Folded dipole: 19-3, 20-4, 21-3
    - Half-wavelength: 20-3
    - Helical, 432 MHz: 21-9
    - Hf: 20-1
    - Hf mobile: 10-8
    - Load: 19-3
    - Matching: 19-3
    - Optimum-gain two-band Yagi: 20-19
    - Random-length, coupling: 19-7
    - Repeater: 13-13
    - Separate: 11-5
    - Small Yagi, 40 meters: 20-19
    - Three-band quad: 20-21
    - Vertical: 20-9
    - Vertical, 7-MHz steerable: 20-13
    - Vhf quagi: 21-7
    - Vhf/uhf: 21-1
    - Vhf vertical: 10-10
    - Wire: 20-7
    - Yagis and quads: 20-15
    - 2-meter vertical: 10-11
    - 220-MHz mobile: 10-11
    - 50 MHz: 21-4
  - Anti-resonant crystal: 2-39
  - Armature: 10-2
  - Arsenic: 4-2
  - Atoms: 2-1, 4-1
  - Attenuation: 15-7
    - Effective: 2-34
  - Attenuator: 7-5, 7-26
  - Audio amplifier, IC: 4-39
  - Audio derived agc: 8-11
  - Audio-frequency oscillator: 16-20
  - Audio rectification: 15-13
  - Audio speech processor: 12-20
  - Aurora: 18-2, 18-6
  - Automatic gain control: 8-11, 8-23
  - Automotive battery: 10-1
  - Automotive generator: 10-2
  - Autotransformer: 2-24
  - Avalanche-diode oscillator: 4-11
  - Average-reading circuit: 16-8
  - Awards: 22-8
  
  - Back bias: 4-3
  - Back emf: 2-10, 2-16, 2-18
  - Backscatter: 18-5
  - Backwave: 10-12, 11-1
  - Balanced mixer: 10-13
  - Balanced modulator: 12-9
  - Balancing devices: 19-4
  - Balun: 3-13, 13-19, 19-5, 21-3
    - Broadband toroidal: 19-6
    - Coil: 19-5
    - Linear: 19-5
  - Bandpass: 3-19
  - Band-reject: 3-19
  - Bandwidth: 3-19
    - Antenna: 20-2
    - Limitation: 2-41
    - NBVM: 14-1
    - Reduction: 14-3
  - Bank wound: 3-19
  - Base: 4-17
  - Base loading: 3-19
  - Base-loaded antenna: 10-8
  - Battery:
    - Automotive: 10-1
    - NiCad: 10-5
  - Bazooka: 19-5
  - Beat-frequency oscillator: 8-11, 8-24
  - Beryllium oxide: 7-22
  - Bessel function: 13-5
  - Beta: 4-17
  - BFO injection: 10-12
  - Bias: 3-19, 6-22
    - Diode: 4-4
    - Grid: 15-4
    - Stabilization device: 4-7
    - Zener: 7-17
  - Bifilar: 3-19
    - Rf choke: 7-12
    - Winding: 2-27, 2-33, 3-9
  - Bilateral: 3-19
  - Binary: 3-19
  - Binder: 2-14
  - Bit: 3-19
  - Blanker: 3-19
  - Bleeder resistor: 5-3, 5-5
  - Blocked-grid keying: 11-2
  - Blocking, receiver: 11-5
  - Breakdown: 4-1
  - Break-in keying: 11-3
  - Bridge: 3-19
    - Ac: 16-10
    - Circuits: 16-4
  - Broadband amplifier: 4-22
  - Broadband transformer: 3-8, 6-20
  - Broadcast harmonics: 3-3
  - Broadcast interference: 15-15
  - Buffer, VFO: 6-7
  - Bumper mount: 10-8
  - Butler oscillator: 7-8
  - Butterworth filter: 2-36, 2-37, 15-7
  - Bypass: 3-2, 10-14, 15-3, 15-14, 15-17
  - Byte: 3-19
  
  - Cable and control wires: 20-12
  - Canadian amateur bands: 1-4
  - Capacitance: 2-1, 2-8
    - Distributed: 3-3
    - Formula: 2-9
    - "Hat": 10-10
    - Measurement: 16-19
    - Parallel: 2-10
    - Series: 2-10
    - Time constant: 2-16
    - Top-loading: 10-10
  - Capacitive:
    - Input filter: 5-5
    - Probe: 7-10, 7-20
    - Probe coupling: 7-16
    - Reactance: 2-18
  - Capacitor: 2-3, 2-8, 17-9
    - Bypass: 7-10, 7-24
    - Coaxial feedthrough: 10-2
    - Dielectric: 2-8
    - Diodes: 4-7
    - Disk-ceramic resonance: 17-8
    - Electrolytic: 2-9, 5-8

- Feedthrough: 7-7, 15-6
- Flapper: 7-21
- Output-coupling: 7-16
- Output loading: 7-12
- Output ratings: 6-29
- Output tank voltage rating: 6-31
- Screen-bypass: 7-22
- Series: 5-8
- Variable: 2-9
- Capture effect: 13-8
- Carbon microphone: 12-13
- Carrier-operated relay: 13-11
- Carrier oscillator: 12-12
- Cascade: 3-19
- Cascode: 3-19
- Cascode amplifier: 9-3
- Cathode bias: 3-16
- Cavity resonator: 7-27
- Center-loaded antenna: 10-8
- Charge: 2-2
- Charged particles: 18-2
- Chassis working: 17-2
- Chip: 3-19
- Chirp: 11-1
- Choke:
  - Input filter: 5-7
  - Rf: 6-32
- CHU: 16-30
- Circuit: 2-1
  - Board, double-sided: 3-11, 6-18
  - Board fabrication: 17-7
- Circular polarization: 18-2
- "Citation Eliminator": 15-8
- Clamp: 3-19
  - Diode: 4-7
- Class:
  - AB1 linear amplifier: 7-3
  - C: 4-22
  - C amplifier: 7-3
- Clicks, key: 11-4
- Clipping: 3-19, 4-7, 11-4
  - Speech: 12-18
- Closed loop: 3-19
- Clubs: 1-2
- CMOS: 4-35, 4-45
- Coax, rf impedance bridge: 16-25
- Coaxial cable: 19-1, 20-23
- Code transmission: 11-1
- Coefficient of coupling: 3-4
- Coil: 2-10
  - Baluns: 19-5
  - Winding: 17-7
- Cold end: 3-19
- Collector: 4-17
- Collinear antenna: 21-8
- Color code, resistor-capacitor: 17-9
- Colpitts oscillators: 3-17
- Common:
  - Base: 4-19
  - Collector: 4-19
  - Emitter: 4-19
  - Source rf amplifier: 9-2
- Commutator: 10-2
- Compandor, amplitude: 14-1, 14-4
- Compandor, frequency: 14-3
- Complex waves: 2-22
- Components: 3-1
- Component values: 17-7
- Composite: 3-19
- Compression:
  - Mixer: 9-7
  - Volume: 12-17
- Conductance: 2-5
- Conduction cooling: 7-19
- Connector assembly: 17-5
- Construction practices: 17-1
- Contesting: 22-10
- Continuous Commercial Service: 6-21
- Control-function decoder: 13-27
- Control, repeater: 13-11, 13-13
- Conversion loss/gain: 3-19
- Converter:
  - High-performance hf: 8-42
  - High-performance 2-meter: 9-21
  - Interdigital, 1296 or 2304 MHz: 9-26
  - Vhf/uhf: 9-7
  - 50, 144 and 220 MHz: 9-18
- Copper-wire table: 17-12
- Cores, high-permeability: 3-9
- Corona-discharge noise: 10-3
- Coulomb: 2-1
- Counter, frequency: 16-15
- Coupled circuits: 2-33
- Coupled resonators: 2-38
- Coupling:
  - Coefficient: 2-39, 16-19
  - Directional: 3-10
  - Inductive: 7-8
  - Inductive-link: 6-28
  - Link: 3-6, 15-4
  - Mutual-magnetic: 15-7
  - Output: 7-22
  - Receiver: 19-7
  - Resistance: 12-14
  - Transformer: 12-14
  - Transmitter stages: 6-14
  - Transmitter to line: 19-7
  - Tubes: 6-27
  - Tuned: 6-29
- CQ: 22-1
- Critical inductance: 5-7
- Critical frequency: 18-3
- "Cross-hatching": 15-3
- Cross modulation: 9-7, 15-11, 15-15
- Crystal: 2-38
  - Controlled oscillator: 4-25
  - Discriminator: 13-9
  - Filter, commercial: 12-12
  - Filter, ssb: 12-1
  - Oscillator: 6-3, 8-12
  - Switching: 6-4
  - Tester: 16-23
- Current: 2-1, 2-3
  - Amplification factor: 4-17
  - And voltage distribution: 20-3
  - Density: 2-3
  - Limiting: 5-16
  - Ratio: 2-29
  - Regulation: 5-15
  - Reverse: 16-9
- Curve tracer: 4-18
- Cutoff, transistor: 4-19
- Cw operating: 22-5
- Cycle: 2-17
- Dah: 11-1
- Damping: 3-19
- Darlington pair: 5-16
- D'Arsonval: 16-1
- Data tables: 17-1
- DBM/i-f amplifier, combined: 9-16
- Dc input power: 12-16
- Dc-to-dc converters: 10-3
- Decay time: 3-19
- Decibel (dB): 2-29
- Decibel chart: 2-30
- Decoder, Touch-Tone: 13-27
- Deemphasis: 13-5
- Degenerative feedback: 6-18
- Degrees: 2-17
- Delta loop: 20-18
- Delta match: 21-3
- Depletion mode: 4-28
- Depletion region: 4-17
- Desensitization: 8-17, 13-12
- Design, radio: 3-1
- Detection: 8-3
- Detector:
  - Diode: 4-8, 8-3
  - Fm: 8-6, 13-8
  - Infinite-impedance: 8-4
  - Plate: 8-4
  - Product: 8-5
  - Ratio: 8-6
- Deviation:
  - Frequency: 13-1
  - Linearity: 13-5
  - Meter, heterodyne: 16-27
- Dial, electronic: 6-10
- Dial, VFO: 6-9
- Dielectric: 2-8, 18-2
  - Constant: 2-2
  - Loss: 3-2
- Difference amplifier: 4-39
- Differential:
  - Amplifier: 3-19
  - Keying: 11-3
- Digital: 3-19
  - Logic IC: 4-42
  - Meter: 5-19
- Diode: 4-4
  - Capacitors: 4-7
  - Clamp: 4-7
  - Clipper: 4-7
  - Detector: 4-8, 8-3
  - Dissipation: 5-14
  - Gates: 4-6
  - Gunn: 4-11
  - Hot carrier: 4-10
  - Light-emitting (LED): 4-13
  - In parallel: 5-13
  - In series: 5-13
  - Mixer: 4-8
  - Multiplier: 4-8
  - PIN: 4-13
  - Protection: 5-11
  - Protective: 5-13
  - Solar-electric: 4-14
  - Switching: 4-6
  - Transistor logic: 4-44
  - Varactor: 4-11
  - Voltage reference: 4-6
  - Zener: 4-15
- Dip meter, Dual-gate MOSFET: 16-17
- Diplexer: 3-19
- Dipole: 20-3
  - Folded: 19-3, 20-4, 21-3
- Direct-conversion receiver: 8-7
- Direct-current instrument: 16-1
- Directional coupling: 3-10
- Discrete: 3-19
- Discriminator:
  - Crystal: 13-9
  - Frequency: 13-8
- Dish: 3-19



- Dissipationless network: 2-34
- Distortion measurements: 12-26
- Dit: 11-1
- Divider, frequency: 16-13
- Donors: 4-2
- Double-tuned circuits: 3-4
- Doubly balanced mixer: 4-9, 7-1, 9-12
- D region: 18-3
- Drift, Gunn-diode: 3-18
- Drive: 3-20
- Driver stages: 6-12
- Dummy antenna: 16-21
- Duplexer: 3-20, 13-13
- DX Century Club: 22-8
- Dynamic:
  - Range: 3-20, 8-3
  - Microphone: 12-13
  - Regulation: 5-5
- Earth's magnetic field: 18-3
- "Economy" power supply: 5-8
- Eddy currents: 2-15
- Effective attenuation: 2-34
- Efficiency: 2-8
- E layer: 18-3
- Electret microphone: 12-13
- Electrical laws and circuits: 2-1
- Electrical-noise: 10-1
- Electric-field strength: 2-2
- Electrodes: 2-3
- Electromagnetic fields: 2-1
- Electromagnetic waves: 18-2
- Electromotive force (emf): 2-3
- Electronic:
  - Industries Association (EIA): 15-1
  - Organ: 15-15
  - T-R switch: 11-5
  - Voltage regulation: 5-15
  - Voltmeter: 16-4
- Electrons: 2-1, 4-1
- Electrostatic fields: 2-1
- Electrostatic shield: 2-3
- EME: 18-6
- Emergency operation: 22-11
- Emitter: 4-17
- Emitter-coupled logic: 4-44
- Empirical: 3-20
- Enabling: 3-20
- Encoder: 3-20
- Encoder, Touch-Tone: 13-25
- Energy: 2-7, 2-8
- Enhancement mode: 4-28
- Equipotential: 2-2
- Etching, circuit-board: 17-7
- Ethics: 22-8
- Excitation: 3-20
- External-anode triodes: 7-16
- External-anode tube: 7-20
- Faculae: 18-10
- Fading: 18-4
- Farad: 2-9
- Feedback: 3-15, 3-16, 3-20
- Feed methods, antenna: 20-4
- Feedthrough: 3-20
- Feedthrough capacitor: 7-7, 15-6
- Fermi level: 4-3
- Ferrite bead: 2-27, 3-2, 15-6, 15-14
- Ferromagnetic: 2-25, 3-20
- FET volt-ohmmeter: 16-5
- Field-effect transistor (FET): 4-27
- FET:
  - Balanced mixer: 7-1
  - Crystal oscillator: 4-32
  - Insulated-gate: 4-28
  - Mixer: 4-31
  - Power: 4-29
  - VFO: 4-32
  - Voltmeter: 4-33
- Field: 2-3
  - Magnetic: 2-10
  - Strength: 2-2
  - Strength meter: 10-10
- Filament voltage: 6-21
- Filter: 2-33
  - Absorptive: 15-8
  - "Brute-force" ac line: 5-12
  - Butterworth: 2-36, 15-7
  - Chebyshev: 6-12
  - Chokes: 5-8
  - Crystal: 8-21
  - Fm-bandwidth: 13-6
  - Full-lattice crystal: 12-1, 12-2
  - Elliptic-function: 15-7
  - Half-lattice: 8-21, 10-13
  - High-pass: 15-5, 15-11
  - Intermediate frequency: 8-11
  - Line: 15-15
  - Low-pass: 15-7
  - Mechanical: 8-22, 12-12
  - NBVM: 14-9
  - Op amp: 4-40
  - Oscillator output: 6-11
  - Ssb generation: 12-1
  - Surplus crystal hf: 12-6
  - Tables: 2-36
  - Transistor: 4-22
  - Vhf transmitters: 15-9
- Filtering: 5-4
- Finite: 3-20
- F layer: 18-3
- Flip-flop: 3-20, 4-42, 4-43, 16-13
- Flux density: 2-14
- Flux lines: 2-40, 3-9
- Floating: 3-20
- Frequency modulation: 13-1
  - Bandwidth: 13-2
  - Control-function decoder: 13-25
  - Detector: 8-6, 13-8
  - Direct method: 13-2
  - Indirect fm: 13-4
  - Limiter: 13-8
  - Receiving: 13-6
  - Transmitter testing: 13-5
- Folded dipole: 19-3, 20-4, 21-3
- Forward-biased diode: 4-4
- Forward scatter: 18-4
- Forward wave: 19-1
- Fractions: 2-5
- Frame and body bonding: 10-3
- Frequency: 13-5
  - Compondor: 14-3
  - Counter: 16-15
  - Generation: 6-2
  - Marker generator: 16-11
  - Measurement: 16-11
  - Meter, absorption: 16-14
  - Multiplication: 6-11
  - Multiplier: 7-1, 15-3
  - Response: 2-42
  - Sealing: 2-36
  - Spectrum: 17-10
- Standard: 16-15
- Station: 16-29, 18-7
- Synthesizer: 7-1
- Front-end overload: 15-10
- Front-end protection: 9-3
- Front end, receiver: 8-15
- Front-to-back bandwidth: 20-2
- Full-wave bridge rectifier: 5-4
- Full-wave center-tap rectifier: 5-3
- Full-wave voltage doubler: 5-9
- Fusing: 5-2
- Gain:
  - Amplifier: 3-15
  - Bandwidth: 20-2
  - Bandwidth product: 4-17
  - Control: 12-15
- Gallium arsenide (GaAs): 3-18
- Gamma match: 19-4, 21-3
- Gate: 3-20
- Gate, IC: 4-43
- GDO: 3-20
- Gated noise source: 16-24
- Geomagnetic field: 18-8
- Germanium: 4-2
- Germanium diode: 4-5
- Glossary of terms: 3-19
- Gradient, potential: 2-2
- Grid:
  - Blas: 15-4
  - Current: 15-4
  - Excitation: 6-23
  - Loading: 6-31
- Ground: 2-3, 10-7, 15-5
- Grounded-gate FET preamplifier: 9-3
- Grounded-grid amplifier: 6-25
- Ground loop: 3-20
- Ground system: 20-13
- Ground wave: 18-2
- Gunn diode: 4-11
- Gunn-diode microwave oscillator: 3-18
- Half-power point: 3-20
- Half-wavelength antenna: 20-4
- Half-wave rectifier: 5-3
- Half-wave voltage doubler: 5-8
- Harmonics: 7-4, 15-2
  - Broadcast: 3-3
  - Current: 15-3
  - Frequency generation: 3-13
  - Modulation products: 9-17
  - Pick-up: 15-12
  - Suppression: 15-3
- Hartley oscillator: 3-17
- "Hash": 15-13
- Hash filtering: 10-5
- Heater voltage: 6-21, 7-22
- Heat sink: 5-12, 5-17, 10-5
- Heat-sink design: 6-24
- Heat sinks, semiconductor: 17-4
- Heat transfer: 7-21
- Helically-wound dipole: 20-6
- Helical antenna, 432 MHz: 21-9
- Helical resonator: 9-4
- Henry: 2-10
- Heterodyne deviation meter: 16-27
- HF mobile antennas: 10-8
- Hi-fi interference: 15-13
- High end: 3-20
- High-frequency antennas: 20-1

- High-frequency filter, ssb: 12-6
- High-frequency transmitting: 6-1
- High level: 3-20
- High-level transmitting mixers: 7-2
- High-pass: 3-20
- High-pass filter: 2-37, 15-5
- High-permeability cores: 3-9
- High-Q circuits: 2-39
- High-threshold logic: 4-44
- High-Z: 3-20
- Hole: 2-1
- Hole flow: 4-3
- Holes, drilling and cutting: 17-3
- Hot end: 3-20
- Hybrid: 3-20
- Hybrid combiner: 3-11
- Hysteresis: 2-15
  
- Ideal: 3-20
- Ignition-noise-suppression: 10-7
- Image generation: 9-7
- Image-parameter theory: 2-36
- Impedance: 2-21
  - Antenna: 20-2
  - Bridge, coax: 16-25
  - Driving: 6-23
  - Matching: 2-24
  - Matching, vhf: 21-2
  - Normalized: 2-36
  - Ratio: 2-23
  - Transformation: 2-33
  - Transmission lines: 20-23
  - Voltmeter: 16-9
- Impulse noise: 8-25
- Incidental radiation: 15-13
- Incremental parameters: 3-15
- Indirect coupling: 3-3
- Induced emf: 2-10
- Inductance: 2-1, 2-10
  - Formula: 2-11
  - Index: 2-28
  - Lead: 15-4, 6
  - Measurement: 16-19
  - Mutual: 2-15
  - Parallel: 2-15
  - Parasitic: 15-6
  - Series: 2-15
- Inductive coupling: 7-8
- Inductive reactance: 2-18
- Inductors: 3-3
- Injection locking: 3-18
- Injection stages: 9-9
- Insertion loss: 2-34, 3-20
- Instability, amplifier: 3-16
- Instrument noise: 10-3
- Instrument, test: 16-1
- Insulated-gate FET: 4-28
- Insulators: 2-1
- Integrated circuit:
  - Array: 4-35
  - Audio amplifier: 4-39
  - CMOS: 4-35
  - Digital-logic: 4-42, 4-44
  - Gate: 4-43
  - I-f amplifier: 4-38
  - Inverter: 4-42
  - Linear: 4-34
  - Mixer: 4-38, 8-19
  - Operational amplifier: 4-39
  - Rf amplifier: 4-38
  - Structure: 4-34
- Subsystem: 4-37
- Interference patterns: 15-3
- Intermediate frequency: 3-5
  - Amplifier: 4-38, 8-19, 10-13
  - Derived agc: 8-11
  - Filter: 8-11
  - Improved wide-band responses: 9-18
- Interference: 15-1, 15-11
  - Selectivity: 8-20
  - Ssb, complete i-f audio: 12-32
- Intermittent Commercial
  - Amateur Service: 6-21
- Intermodulation distortion: 9-7
- Intermodulation distortion product: 12-26
- Interpolate: 3-20
- Intrinsic: 4-13
- Intrinsic semiconductor: 4-2
- Inverted V: 20-5
- Inverter: 10-6
- Inverter, IC: 4-42
- Inverting: 4-39
- Ionization: 4-1, 18-2
- Ionogram: 18-3
- Ionospheric scatter: 18-4
- Ionospheric wave: 18-2
- Iron-core coil: 2-14
- Isolation: 15-6
  
- JFET mixer: 9-8
- J-K flip-flop: 4-42
- Joint Army-Navy: 17-9
  
- Keyboard, inexpensive Morse: 11-11
- Keyboard, scanned: 11-13
- Key clicks: 15-15
- Keyer:
  - Deluxe all-solid-state: 11-8
  - Memory: 11-7
  - Single-IC: 11-11
- Keying:
  - Break-in: 11-3
  - Differential: 11-3
  - Oscillator: 11-2
  - Speed: 11-4
  - Testing and monitoring: 11-6
  - Transmitter: 11-2
- Kilo (k): 2-5
- K-Index: 18-8
- Klystron oscillator, reflex: 3-17
  
- Ladder networks: 2-34
- Laminations: 2-15
- Large-scale integration: 4-43
- Lead inductance: 15-4, 15-6
- Leakage: 3-1, 3-20, 9-6
- Leakage reactance: 2-23
- Light blinking: 5-2
- Light-emitting diode (LED): 4-13
- Limiting: 13-8
- Limiting, audio: 8-26
- Limiting resistor: 5-9, 5-14
- Linear
  - Amplification: 3-20, 6-25
  - Approximation: 3-14
  - Baluns: 19-5
  - Transformers: 19-3
  - Transmitting converter, 432 MHz: 7-8
- Line:
  - Impedance: 7-10
- Radiation: 15-13
- Voltage: 5-2
- Link coupling: 3-6, 19-10
- Lissajous figures: 16-22
- L network: 10-9
- Load: 3-20
  - Antenna: 19-3
  - Isolation, VFO: 6-6
  - Nonradiating: 19-7
  - Resistance: 5-4
  - Terminating: 15-8
- Loaded circuit Q: 2-33
- Local oscillator: 7-2, 7-9, 8-11
- Logarithmic response: 2-29
- Logging: 22-3
- Logic: 3-20
- Logic symbols: 4-42
- Long wire: 3-20, 20-7
- Loop, circuit: 2-4
- Low end: 3-20
- Low-frequency oscillation: 7-4
- Low level: 3-20
- Low pass: 3-20
- Low-pass filter: 15-7
- Low-Q circuits: 2-28, 2-32
- Low Z: 3-20
  
- Magnetic field: 2-10
- Magnetizing current: 2-22
- Majority carrier: 4-3
- Marker, frequency: 16-11
- Marker generator: 16-13
- Master oscillator: 3-20
- Matching, antenna: 19-3
- Matching, link-coupled: 19-10
- Matching networks: 2-40
- Matching sections: 19-4
- Maxim, Hiram Percy: 1-3
- Maximum usable frequency: 18-4
- Mean: 3-20
- Measurements: 16-1
- Mechanical filter: 12-12
- Medium-scale integration: 4-43
- Mega: 2-5
- Memory, keyer: 11-7
- Meteor scatter: 18-5
- Metal-oxide semiconductor: 4-28, 4-45
- Metric multiplier prefixes: 17-9
- Micro: 2-5
- Microammeter: 16-1
- Microphone: 12-13
- Microphonics: 8-9
- Microstripline 2-GHz oscillator: 3-18
- Microwave oscillators: 3-17
- Military Affiliate Radio System: 22-12
- Milli: 2-5
- Milliammeter: 16-1
- Minimum discernable signal: 8-1
- Mix, Don: 1-3
- Mixer
  - Balanced: 10-13
  - Balanced, vhf and uhf: 9-8
  - Diode: 4-8
  - Doubly balanced: 4-9, 7-1, 9-12
  - FET: 4-31
  - IC: 4-38, 8-19
  - Intermodulation intercept point: 9-17
  - MOSFET: 9-8
  - Premixing: 6-8
  - Receiver: 8-17

- Singly balanced: 4-9, 9-7
- Transistor: 4-26
- Terminology: 9-17
- Transmitting: 7-1
- Vacuum-tube: 7-1
- Vhf/uhf: 9-6
- Mho: 2-5
- Mobile practices: 10-1
- Modulation, amplitude: 6-24
- Modulation bars: 15-3
- Modulation, frequency: 13-1
- Modulation, phase: 13-1
- Monimatch: 16-11
- Moonbounce: 18-6
- Moving-vane instrument: 16-1
- Multiple-hop propagation: 18-4
- Multiples: 2-5
- Multiplication, frequency: 6-11
- Multiplier, diode: 4-8
- Multiplier, voltmeter: 16-3
- Mutually coupled inductors: 2-39
- Mutual-magnetic coupling: 3-3
  
- NAND gate: 4-42
- National Traffic System: 22-11
- Narrow-band voice modulation: 14-1
- NBVM filters: 14-9
- Negative feedback: 3-16
- Negative-lead filtering: 5-8
- Network: 2-1, 3-20
- Network reactance: 2-41
- Neutralization: 7-3, 7-24, 9-2
- Neutralizing, screen-grid: 6-30
- Neutrons: 2-1
- NiCad battery: 10-5
- Noise
  - Corona discharge: 10-3
  - Electrical: 10-1
  - Figure: 8-1, 9-1, 9-17
  - Impulse: 8-25
  - Instrument: 10-3
  - Limiter: 8-26, 10-3
  - Reduction: 8-25
  - Source, gated: 16-24
  - Spark plug: 10-2
- Nominal: 3-20
- Noninverting: 4-39
- Nonlinear networks: 3-13
- Nonlinear transfer characteristics: 3-14
- Npn transistor: 4-17
- N-type semiconductor: 4-2
  
- Ohm: 2-4
- Ohmmeter: 16-3
- Ohm's Law: 2-5
- Ohm's Law Impedance: 2-21
- Ohm's Law reactance: 2-19
- Ohms per volt: 16-2
- Op amp filter: 4-40
- Open loop: 3-20
- Operating: 22-1
- Operating conditions: 15-4
- Operational amplifier: 3-20, 4-39
- OR gate: 4-42
- OSCAR: 1-2, 22-7, 22-14
- Oscillator: 3-16, 7-2
  - Audio-frequency: 16-20
  - Carrier: 12-12
  - Colpitts: 3-17
  - Crystal: 4-25, 4-32, 6-3, 8-12, 10-12
  - Hartley: 3-17
  - Keying: 11-2
  - Local: 7-2, 7-9, 8-11
  - Microwave: 3-17
  - Rf generator: 16-16
  - Siditone: 10-13
  - Stability: 6-5
  - Tuned plate tuned grid: 3-16
  - Variable-frequency: 6-4
  - Voltage-controlled: 6-8
- Oscilloscope: 16-21
- Output-capacitor ratings: 6-29
- Output filtering: 6-11
- Output coupling: 7-22
- Overlay transistor: 4-17
- Overload: 9-2, 9-17
- Overload protection: 5-16
- Parabolic reflector: 21-8
- Parallel amplifier: 6-25
- Parallel impedance: 2-21, 2-32
- Parallel reactance: 2-19
- Parallel resistance: 2-6
- Parallel resonance: 2-32
- Parallel-resonant crystal: 2-39
- Parallel-wire line: 19-1
- Parameter: 3-20
- Parametric amplifier: 3-20
- Parasitic choke: 7-3
- Parasitic inductance: 15-6
- Parasitic, low-frequency: 6-31
- Parasitic, low-frequency: 6-31
- Parts suppliers: 17-11
- Passband: 15-7
- Passive: 3-20
- Pass transistor: 5-15
- Patch cords: 15-14
- Peak envelope power: 3-20, 6-24, 12-16
- Peak reverse voltage: 4-5, 5-3
- Peak-to-peak value: 16-8
- Permeability: 2-14, 3-20
- Permittivity: 2-1
- Phase difference: 2-17
- Phase inversion: 12-14
- Phase-locked loop: 3-20, 6-8, 13-9
- Phase modulation: 13-1
- Phasing method, ssb: 12-9
- Phone operating practices: 22-3
- Phonetics, ITU: 22-4
- Photovoltaic conversion: 4-14
- Picture carrier frequency: 15-2
- Piezoelectric crystals: 2-38
- Piezoelectric microphone: 12-13
- Pill: 3-20
- PIN diode: 4-13
- Pi output tanks: 6-29
- Planck's constant: 4-1
- Plane reflector: 21-8
- Plate-circuit efficiency: 7-23
- Plate voltage: 6-21
- PN junction: 4-2
- Pnp transistor: 4-17
- Point-contact diode: 4-5
- Polarization: 18-2, 20-1, 21-9
- Port: 3-20
- Portable/emergency equipment and practices: 10-1
- Positive feedback: 3-16, 4-18
- Pot core: 2-25
- Potential: 2-2
- Powdered iron: 2-25
- Power: 2-7
  
- Dissipation: 19-2
- Divider, rf: 20-13
- Factor: 2-21
- Gain: 2-34
- Input: 6-21
- Measurement: 16-3
- Peak vs. average: 12-16
- Rating, ssb: 12-16
- Rf: 16-10
- Relationships: 2-23
- Ratio: 2-29
- Power cord: 5-2
- Power company: 5-2
- Power FET: 4-29
- Power line: 5-1
- Power supplies, ac: 5-1
  - Deluxe 5-25 volt 5-ampere: 5-19
  - Mobile, Transceivers: 10-4
  - "Sanitary" high-voltage supply: 5-21
  - Voltage-adjustable: 5-17
- PRAM: No. 4-46
- Preamplifier
  - Low-noise GaAs FET: 9-12
  - Low-noise 220-MHz JFET: 9-11
  - Stable 10-meter: 8-47
  - 2-meter: 13-16
  - 10, 6 and 2 meters: 9-10
  - 440-MHz: 13-17
- Predistortion: 2-39
- Preemphasis: 13-4
- Premixing: 6-8
- Prescaler: 13-5
- Preselector: 8-11
- Primary coil: 2-22
- Private Line: 3-20, 13-12
- Processing, ssb speech: 12-20
- Product detector: 8-5, 10-12
- PROM: 4-46
- Propagation: 18-1
- Propagation bulletins: 18-7, 18-10
- Propagation prediction: 18-7
- Protons: 2-1
- Prototype: 3-20
- P-type semiconductor: 4-2
- Public-address system: 15-15
- Public service: 1-3, 22-11
- Pulling: 11-2
- Push-pull amplifier: 6-25, 15-4
  
- Q: 2-31, 3-4
- Q<sub>L</sub>: 3-20
- Q section: 19-3, 21-4
- QSL Bureau, ARRL: 22-2
- QST: 1-5
- Q, tank: 6-27
- Q<sub>u</sub>: 3-20
- Quad arrays: 20-15
- Quagi, vhf: 21-7
- Quasi-linear sweep: 16-22
  
- Radiation angle: 18-4, 20-2
- Radiation characteristics: 20-3
- Radio design: 3-1
- Radio frequency: 2-31
  - Amplifier: 4-38, 8-15
  - Amplifier, neutralization: 9-2
  - Amplifier, vhf/uhf: 9-1
  - Bypass: 7-15
  - Choke: 6-32
  - Compression levels: 9-17



- Desensitization level: 9-17, 10-17
- Leakage: 3-1
- Oscillator: 16-16
- Power amplifier: 6-21
- Power dividers: 20-13
- Resistors: 16-20
- Radio frequency interference: 15-1
- Random-access memory: 4-45
- Random-length antenna: 19-7
- Ratio: 2-22, 2-29
- Ratio detector: 8-6, 13-9
- Ratio, deviation: 13-2
- RC filter: 4-41
- Reactance: 2-18, 2-23
- Reactance chart: 2-19
- Reactive power: 2-20
- Reactive transformation matching: 7-16
- Read-only memory: 4-45
- Receiver
  - Beginners': 8-28
  - Coupling: 19-7
  - Desensing: 9-17, 10-17
  - Direct-conversion: 8-7
  - Direct-conversion, four-band: 8-32
  - Fm: 13-6
  - Front end: 8-15
  - High-dynamic range, 160-15: 8-35
  - Mini-Miser's Dream Receiver: 10-13
  - Mixer: 8-17
  - Simple superhet, 75-meter: 8-31
  - Superheterodyne: 8-10
- Receiving fm: 13-6
- Receiving systems: 8-1
- Receiving, vhf and uhf: 9-1
- Rectification, stray: 15-5
- Rectifier: 5-3
- Rectifier instruments: 16-8
- Rectifier mounting: 5-12
- Rectifier rating: 5-11
- Reflected wave: 19-1
- Reflection coefficient: 19-2
- Reflectometer: 16-11
- Reflex klystron oscillator: 3-17
- Recurring phenomena: 18-7
- Regeneration: 7-16
- Regenerative feedback: 3-16
- Regulation, voltage: 5-4
- Remote base: 13-11
- Repeater: 13-10
  - Complete system: 13-11
  - Control: 13-11, 13-13
  - Operating: 22-3
  - Practical circuits: 13-12
- Resistance: 2-1, 2-4, 2-7
- Coupling: 12-14
  - Internal: 16-2
  - Measurement: 16-3
  - Metals: 2-4
  - Parallel: 2-6
  - Phase: 2-18
  - Series: 2-6
  - Series-parallel: 2-7
  - Time constant: 2-16
- Resistance-wire cabling: 10-2
- Resistive spark-plug suppressors: 10-2
- Resistors: 2-3, 2-5, 5-14
  - Color code: 17-9
  - Rf: 16-20
- Resistor swamping: 5-13
- Resistor spark plugs: 10-2
- Resistor-transistor logic: 4-44
- Resonator: 3-20
- Resonance: 2-31, 5-7
- Resonant frequency: 2-31
- Return: 3-21
- Resultant: 2-18
- Reverse-biased diode: 4-4
- Rf probe, voltmeter: 16-10
- Rhombic antenna: 20-8
- Ringing: 3-21
- Ripple: 3-21, 5-5, 15-7
- Rise time: 3-21
- RLC network: 2-42
- Root mean square: 3-21
- Rotor: 3-21
- RST system: 22-5
- Safety: 5-2, 17-4
- Saturation: 2-14, 3-21, 4-19
- Schematic diagram: 2-1
- Schmitt trigger: 4-33, 4-42
- Screen bypassing: 7-3
- Screen current, negative: 7-23
- Screen-grid neutralizing: 6-30
- Screen-grid tube protection: 6-23
- Screen voltage: 6-22
- Secondary coil: 2-22
- Selective fading: 18-4
- Selectivity: 2-31, 3-21, 8-2
- Self-inductance: 2-16
- Self-oscillation: 7-24
- Semiconductor: 2-1, 4-1
- Semiconductor symbol list: 4-45
- Sensitivity: 8-1
- Sensitivity, instrument: 16-1
- Sensitivity, transformer: 3-8
- Sensitivity, voltmeter: 16-2
- Series: 2-4
- Series impedance: 2-21
- Series-parallel: 2-7
- Series reactance: 2-19
- Series resistance: 2-6
- Series resonance: 2-31
- Series-tuned trap: 7-25
- Shaping, keying: 11-2
- Sheet metal, cutting and bending: 17-5
- Shield, electrostatic: 2-3
- Shielding: 15-6, 15-12, 15-15
- "Shorted turn": 7-12
- Short-wave fadeout: 18-4
- Shunt: 3-21, 10-9
- Shunt-fed rf choke: 7-12
- Sidebands, fm and pm: 13-2
- Sidetone oscillator: 10-13
- Signal-to-noise ratio: 8-2
- Silicon: 4-2
- Silicon diode: 4-5
- Single-ended amplifiers: 7-4
- Single-meshed transformed network: 3-8
- Single sideband: 6-25, 12-1
  - Balanced modulator: 12-9
  - Bibliography: 12-24
  - Driver and output: 12-15
  - Filter design: 12-3
  - Generation: 12-1
  - I-f audio system: 12-32
  - Modern solid-state VOX: 12-27
  - Phasing method: 12-9
  - Power rating: 12-16
  - Transceiver: 12-23
  - Transmitter testing: 12-24
- Single-tuned circuits: 3-5, 3-7
- Singly balanced mixer: 4-9, 9-7
- Skin effect: 2-5
- Skip distance: 18-3
- Skip zone: 18-4
- Sky wave: 18-2
- Slug, coil: 2-14
- Small-signal parameters: 3-15
- S meter: 2-29, 8-25
- Solar activity: 18-8
- Solar-electric diode: 4-14
- Solar-electric power: 10-5
- Solar filter: 18-10
- Solar flux: 18-1, 18-7
- Solar noise: 18-2
- Solar radiation: 18-2
- Solar observation: 18-9
- Soldering: 17-5
- Solenoidal: 2-25, 3-21
- Solid-state: 2-1, 4-1
- Sound carrier frequency: 15-2
- Space wave: 18-2
- Spark arrester: 10-7
- Spark plug noise: 10-2
- Spectral purity: 3-21
- Spectrum, frequency: 17-10
- Speech: 14-2
- Speech amplifier: 12-13
- Speech-amplifier construction: 12-15
- Speech clipping and filtering: 12-18
- Speech processing: 12-17, 13-4, 12-20
- Speed, keying: 11-4
- Sporadic E: 18-3, 18-6
- Spurious radiation: 15-2
- Spurious response: 15-10
- Stabilization: 7-3
- Stability, oscillator: 6-5
- Stabilizing amplifier: 6-30
- Standard, frequency: 16-15
- Standing wave: 19-1
- Standing-wave ratio: 3-21
- Static regulation: 5-5
- Stopband: 15-7
- Stray radiation: 15-3
- Strip: 3-21
- Strip-line: 7-9, 7-16, 7-21
- Strip-line filter: 7-2
- Subaudible tones, EIA: 13-12
- Subharmonic: 3-21
- Subsystem IC: 4-37
- Sudden ionospheric disturbance: 18-4
- S unit: 2-29
- Sunspot cycles: 18-1
- Sunspot number, Zurich: 18-1
- Surface wave: 18-2
- Superheterodyne receivers: 8-9
- Superregenerative receiver: 8-7
- Susceptance: 2-34
- Surge current: 5-11
- Surge protection: 5-12
- Swamping resistor: 5-13
- Sweep, quasi-linear: 16-22
- Swinging choke: 5-7
- Sweep tubes: 6-26
- Switching diodes: 4-6
- Switching regulator: 5-15
- SWR measurement: 16-11
- Synchrodyne receiver: 8-8
- Synthesizer, practical 2-meter: 13-19
- Systeme International d'Unites: 2-1
- Tank circuit design: 7-3
- Tank coil: 6-32

- Tank, parallel-resonant: 6-28
- Tank Q: 6-27
- Technical developments: 1-4
- Telephone interference: 16-15
- Telescope: 18-10
- Television, color: 15-13
- Television receiver: 15-10
- Television, vhf: 15-2
- Television, uhf: 15-12
- Temperature effect, wire: 2-5
- Test equipment: 16-1
- Thermal-conducting grease: 7-21
- Thermal motion: 4-2
- Thermal protection: 5-12
- Thermal resistance: 6-24
- Thermal runaway: 4-19
- Thermocouple meter: 16-7
- Three-terminal regulators: 5-17
- Time constant: 2-16
- Time conversion: 22-2
- Time interval: 2-17
- Time station: 16-29, 18-7
- T match: 19-4
- T network: 7-9
- Tools: 17-1
- Toroidal: 2-25, 3-21
- Toroid core specifications: 2-27
- Touch-Tone control: 13-25
- Touch-Tone decoder: 13-13, 13-27
- Transceiver: 3-21, 12-23
- Transceiver, ssb: 12-23
- Transceiver, ultra-portable cw, 7-MHz: 10-12
- Transducer: 3-21
- Transequatorial propagation: 18-6
- Transferred-electron oscillator: 4-11
- Transformers: 2-22
  - Autotransformer: 2-24
  - Baluns: 3-13
  - Broadband: 2-26, 6-20
  - Color code: 17-10
  - Conventional: 2-26
  - Constant-Voltage: 5-2
  - Construction: 2-24
  - Core: 2-22, 2-25
  - Cross-section: 2-24
  - Coupling: 12-14
  - Efficiency: 2-23
  - 1-f: 3-5
  - Iron-core: 2-22
  - Load: 2-23
  - Losses: 2-23
  - Low-frequency: 3-11
  - Narrow-band: 2-26
  - Quarter-wave: 19-3
  - Replacement: 5-10
  - Rewinding: 5-10
  - Sensitivity: 3-8
  - Toroid: 2-25
  - Transmission-line: 2-27, 3-11
  - Types: 2-26
- Transient voltages: 5-12
- Transition region: 4-17
- Transit time: 4-17
- Transistors: 4-16
  - Active region: 4-19
  - Amplifiers: 4-18, 6-27
  - Balanced-emitter: 4-17
  - Ballast: 4-17
  - Base: 4-17
  - Bipolar amplifier: 4-24
  - Bipolar switch: 4-19
- Characteristics: 4-17
- Collector: 4-17
- Common-base: 4-19
- Common-collector: 4-19
- Common-emitter: 4-19
- Cooling: 6-24
- Cutoff: 4-19
- Darlington pair: 5-16
- Emitter: 4-17
- Field-effect (FET): 4-27
- Filter: 4-22
- Instability: 4-22
- Junction FET: 4-27
- Mixer: 4-26
- MOSFET: 4-28
- Npn: 4-17
- Overlay: 4-17
- Pass: 5-25
- Programmable unijunction: 10-13
- Power amplification: 4-17
- Pnp: 4-17
- Ratings: 6-21
- Rf amplifier: 4-20, 4-30
- Saturation: 4-19
- Tester: 16-22
- VFO: 4-25
- Transistor-transistor logic: 4-44
- Transmatch: 3-21, 19-8, 21-3
- Transmission line: 19-1, 20-22, 21-2
- Transmission-line transformer: 2-27, 3-11
- Transmitter:
  - Defects: 15-15
  - Diode Multiplier For 23 cm: 7-27
  - Linear converter, 432-MHz: 7-8
  - Power output: 6-24
  - Sardine Sender: 6-33
  - 15-meter, 6-watt: 6-34
  - 20 meters, VXO: 6-37
  - 35-W, two-band cw: 6-39
- Transmitting, hf: 6-1
- Transmitting mixers: 7-1
- Transmitting, stable conditions: 6-16
- Transmitting, vhf/uhf: 7-1
- Transverter: 3-21, 7-2
- Transverter, 1.8 MHz: 12-30
- Transverter, 2-meter: 7-5
- Trap: 3-21, 7-3
- Trap dipole: 20-6
- Triac motor-speed control: 17-2
- Trifilar winding: 2-27, 3-21
- Trigger: 3-21
- Triode amplifier: 3-14
- Tropospheric propagation: 18-2, 18-4, 18-6
- T-R switch: 11-5
- Tube ratings, transmitting: 6-21
- Tubes, cooling: 6-23
- Tube voltages: 6-21
- Tuned-plate tuned-grid oscillator: 3-16
- Tunnel-diode oscillator: 4-11
- Tuska, Clarence: 1-4
- TVI: 7-4, 15-1
- TVI and T-R switches: 11-5
- Twin-lead: 19-4, 20-23
- Twist drills: 17-1
- Twisted-pair windings: 3-9
- Two-tone tests: 12-25
- U: 3-21
- Uemera, Naomi: 1-3
- Ultraviolet light: 18-2
- Universal stub: 21-2
- U.S. amateur bands: 1-5
- Vacuum-tube mixer: 7-1
- Vacuum-tube voltmeter: 16-5
- Varactor: 3-21
- Varactor diode: 4-11, 4-27
- Variable crystal oscillator: 8-12
- Variable-frequency oscillator: 6-4, 8-14
  - Buffer: 6-7
  - Dial: 6-9
  - FET: 4-32
  - Load isolation: 6-6
  - Transistor: 4-25
- V beam: 20-8
- Velocity factor: 2-2, 20-22
- Vertical antenna: 20-9
- Vertical, 2-meter: 10-11
- Vhf quagi: 21-7
- Vhf quarter-wavelength vertical: 10-10
- Vhf/uhf antennas: 21-1
- Vhf/uhf receiving: 9-1
- Vhf/uhf transmitting: 7-1
- Virtual height: 18-3
- Voice-operated control: 12-23
- Volt: 2-2, 2-5
- Voltage: 2-1
  - Amplifier: 12-14
  - Breakdown: 2-9
  - Dividers: 5-13
  - Dropping resistor: 5-13
  - Quadrupler: 5-9
  - Ratio: 2-29
  - Regulation: 5-4, 5-14, 5-17, 10-2
  - Resonance: 2-32
  - Tripler: 5-9
- Voltage-controlled oscillator: 3-21, 6-8
- Voltage reflection coefficient: 19-2
- Voltage-reference diode: 4-6
- Voltage-standing-wave ratio: 3-10, 3-21, 19-2
- Voltmeter: 16-2, 16-4, 16-9
- Voltmeter, rf probe: 16-10
- Volume compression: 12-17
- Volume unit: 3-21
- VOX, solid-state: 12-27
- Watt: 2-7
- Wattmeter, low-power: 16-27
- Wave form, unsymmetrical: 16-8
- Wave front: 18-2
- Wavepath: 18-3
- Wave propagation: 18-1
- Wheel and tire static: 10-3
- Whine: 10-2
- Windings: 3-9
- Wire antenna: 20-7
- Wire, copper table: 17-12
- Wire, resistance: 2-4
- Wiring: 17-6
- WWV/WWVH: 16-29, 18-1, 18-7
- WIAW: 22-13
- Yagi array: 20-15, 21-4
- Z: 3-21
- Zener diode: 3-21, 4-4, 4-15, 5-14
- Z ratio: 3-21
- Zurich sunspot number: 18-1





