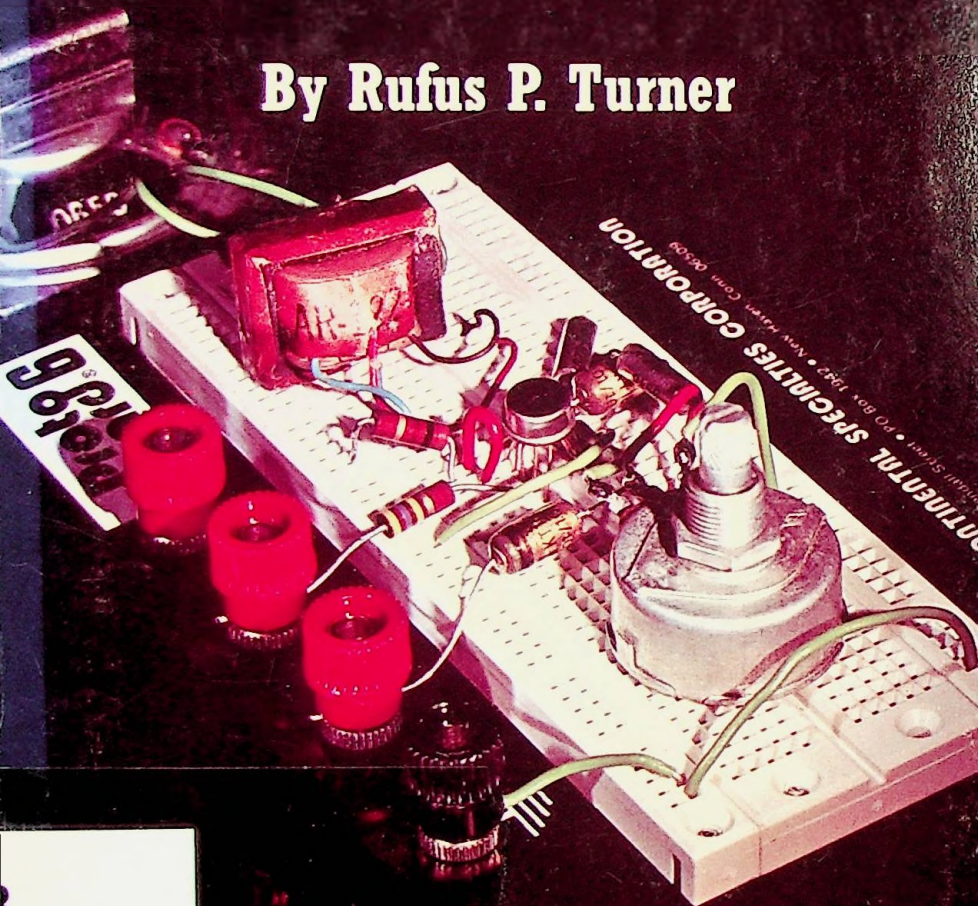


106 EASY ELECTRONICS PROJECTS— Beyond the Transistor

By Rufus P. Turner



Historie v/d Radio

...to the world of sophisticated semiconductors by building practical projects using FETs, MOSFETs, ICs, UJTs, tunnel diodes, varactors, zener diodes, diacs, triacs, and SCRs.

BRAND NEW BOOKS—JUST PUBLISHED!

Practical Solid-State DC Power Supplies	196 p. 151 il.	\$6 95
Optoelectronics Guidebook—with tested projects	196 p.	\$5 95
Master Transistor Substitution Handbook	504 p.	\$7 95
How To Make Your Own Built-In Furniture	336 p. 758 il.	\$5 95
Transistor Lighting Systems	252 p. 162 il.	\$5 95
TV Ignition Handbook	228 p. 261 il.	\$12 95
Building Model Ships From Scratch	378 p. 84 il.	\$7 95
How To Make News & Influence People	140 p.	\$3 95
Homeowner's Handy "Do-It" Manual	280 p., 84 il.	\$7 95
How to Repair Home Kitchen Appliances	294 p. 205 il.	\$5 95
Fun With Electronics	140 p. 88 il.	\$3 95
How to Hear & Speak CB in a Short-Short	172 p. 85 il.	\$3 95
The Complete Handbook of Model Railroading	350 p. 238 il.	\$6 95
Talk-Back TV: Two-Way Cable Television	238 p. 64 il.	\$5 95
Understanding Use Modern Signal Generators	294 p.	\$6 95
Numbers, Shortcuts & Pastimes	336 p. 80 il.	\$6 95
Using Modern Electronic Projs. Beyond Transistors	224 p.	\$5 95
Easy Modern Electronic Serv. Test Eqp. 252 p.	177 il.	\$5 95
Mathematics Unveiled—New Commonsense Approach		\$6 95
Master Tube Substitution Handbook	322 p. 548 il.	\$4 95
Modern Guide to Digital Logic	294 p. 222 il.	\$6 95
VHF/UHF Fire, Police, Ham Scanners	Man. 250 p., 114 il.	\$6 95
OP AMP Circuit Design & Applications	280 p. 235 il.	\$5 95
Master Handbook of Digital Logic Applications	392 p. 287 il.	\$7 95
CET License Handbook 2nd ed.	448 p. 381 il.	\$8 95
The Electronic Musical Instrument Manual	210 p. 385 il.	\$6 95
Microprocessor Microprogramming Handbook	294 p. 176 il.	\$6 95
Sourcebook of Electronic Organ Circuits	168 p. 101 il.	\$4 95
Build Your Own Working Robot	238 p. 83 il.	\$5 95
CBer's Handbook of Simple Hobby Projects	168 p. 114 il.	\$3 95
Fire & Theft Security Systems 2nd ed.	192 p. 114 il.	\$5 95
How to Repair Home Laundry Appliances	280 p. 137 il.	\$5 95
Piloting Navigation With the Pocket Calculator	392 p. 233 il.	\$8 95

HOBBY ELECTRONICS

How to Read Electronic Circuit Diagrams	192 p. 140 il.	\$4 95
21 Simple Transistor Radios You Can Build	140 p. 122 il.	\$3 95
Basic Electricity & Beginning Electronics	252 p. 191 il.	\$5 95
Radio Control for Models	358 p. 417 il.	\$6 95
MOSFET Circuits Guidebook	196 p. 104 il.	\$4 95
Practical Circuit Design for the Experimenter	196 p. 119 il.	\$4 95
111 Digital & Linear IC Projects	210 p. 275 il.	\$5 95
Radio Astronomy for the Amateur	252 p. 96 il.	\$5 95
Build-It Book of Mini Test Measurement Instr.	238 p. 151 il.	\$4 95
RF & Digital Test Equipment You Can Build	252 p. 217 il.	\$5 95
Miniature Projects For Electronic Hobbyists	168 p. 77 il.	\$3 95
Practical Triac/SCR Projects For The Exp.	192 p. 146 il.	\$4 95
Integrated Circuits Guidebook	196 p. 119 il.	\$5 95
Solid State Circuits Guidebook	252 p. 227 il.	\$5 95
Electronics For Shutterbugs	204 p. 109 il.	\$5 95
Practical Test Instruments You Can Build	204 p. 157 il.	\$4 95
How to Build Solid-State Audio Circuits	320 p. 190 il.	\$5 95
Radio-Electronics Hobby Projects	192 p. 214 il.	\$4 95
Handbook of IC Circuit Projects	224 p. 136 il.	\$4 95
Solid State Projects for the Experimenter	224 p. 228 il.	\$4 95
Electronic Experimenter's Guidebook	182 p. 86 il.	\$4 95
125 One-Transistor Projects	192 p. 125 il.	\$4 95
104 Easy Projects for Electronic Gadgeteers	160 p. 105 il.	\$4 95
64 Hobby Projects for Home & Car	192 p. 159 il.	\$4 95

AUDIO, HI-FI & ELECTRONIC MUSIC

Electronic Music Circuit Guidebook	224 p. 180 il.	\$6 95
Questions & Answers About Tape Recording	264 p. 102 il.	\$5 95
Handbook of Multichannel Recording	322 p. 196 il.	\$7 95
Auto Stereo Service & Installation	252 p. 245 il.	\$5 95
Servicing Cassette & Cartridge Tape Players	294 p. 196 il.	\$6 95
Electronic Music Production	156 p. 79 il.	\$3 95
Experimenting With Electronic Music	180 p. 103 il.	\$4 95
Cassette Tape Recorders. How Work/Care/Repair	204 p.	\$4 95
Acoustic Techniques for Home & Studio	224 p. 168 il.	\$5 95
Pictorial Guide to Tape Recorder Repairs	256 p. 320 il.	\$4 95
How to Repair Musical Instrument Amplifiers	288 p. 50 il.	\$5 95
Japanese Radio Record, Tape Player Svcg. Manual	228 p.	\$6 95
Servicing Electronic Organs	196 p. 158 il.	\$7 95
Tape Recording for Fun & Profit	224 p. over 200 il.	\$5 95

ALL-IN-ONE COLOR & B&W TV SCHEMATIC/SERVICING MANUALS

Each Vol. has complete service data, parts lists, full-size schematics, and all other info needed. Each 8 1/2" x 11", 196 pps. Each only \$5.95 unless marked. COLOR TV: Adm. Vol. 1 Vol. 2 \$8.95 GE Vol. 1 Vol. 2 Val. 3 Jap. Vol. 1 \$7.95 Vol. 2 \$4.95 Vol. 3 \$4.95 Vol. 4 Val. 5 Magnavox Vol. 1 \$4.95 Vol. 2 Vol. 3 Airlite Motorola Vol. 1 \$4.95 Vol. 2 Philco RCA Vol. 1 Vol. 2 Val. 3 Vol. 4 Vol. 5 Sears Serv. Modular Rec'r Vol. 1 \$6.95 Vol. 2 \$4.95 Syl. Vol. 1 Vol. 2 Toshiba Zenith Vol. 1 Vol. 2 Vol. 3 Vol. 4 B&W TV: Adm. \$7.95 GE \$7.95 Jap. \$6.95 Mag. \$4.95 Mot. \$4.95 Philco \$4.95 RCA \$7.95 Syl. \$4.95 Zenith \$7.95

DO-IT YOURSELF: AUTOMOTIVE & APPLIANCES

Homeowner's Guide to Saving Energy	196 p. 183 il.	\$5 95
Customizing Your Van	192 p. 150 il.	\$3 95
The Woodworker's Bible	434 p. 1151 il.	\$5 95
Motorcycle Repair Handbook	392 p. 260 il.	\$6 95
The Complete Handbook of Locks & Locksmithing	392 p.	\$6 95
Step-By-Step Guide: Carburetor Tuneup/Overhaul	224 p.	\$4 95
Homeowner's Guide to Solar Heating & Cooling	196 p.	\$4 95
Do-It-Yourself's Guide: Home Planning Constr.	238 p.	\$4 95
Step-By-Step Guide to Brake Servicing	238 p. 248 il.	\$4 95
Step-By-Step Guide: Chrysler Eng. Maint. Rpr.	256 p. 195 il.	\$5 95
Subcontract Your Home. Bldg. Remodeling	196 p. 63 il.	\$4 95
Auto Electronics Simplified	256 p. 202 il.	\$5 95
The Complete Auto Electric Handbook	210 p. 139 il.	\$5 95
Concrete & Masonry	392 p. 213 il.	\$5 95
Home Appliance Clinic: Controls, Timers, Wiring Rpr.	195 p.	\$4 95
Practical Home Constr. Carpentry Hdbk.	448 p. 180 il.	\$5 95
How to Repair Diesel Engines	308 p. 237 il.	\$5 95
Central Heating & Air Cond. Repair Guide	320 p. 285 il.	\$6 95
Small Appliance Repair Guide—Vol. 2	210 p. 115 il.	\$4 95
Electrical Wiring/Lighting For Home/Office	204 p. 155 il.	\$4 95
How to Repair Small Gasoline Engines, 2nd Ed.	392 p.	\$6 95
How to Repair Home Auto Air Cond.	208 p. over 100 il.	\$4 95

CB, COMMUNICATIONS & HAM RADIO

CB Schematic Svcing. Manuals each 200 p.	\$5 95	<input type="checkbox"/> Vol 1 <input type="checkbox"/> Vol 2 <input type="checkbox"/> Vol 3
Browning, Hy-gain, Penney's	<input type="checkbox"/> Vol 2 <input type="checkbox"/> Teafear, Unimetrics, Pearce-Simpson, Siltronix,	<input type="checkbox"/> Vol 3 <input type="checkbox"/> E.F. Johnson, SBE-Linear, Sonar, Royce
<input type="checkbox"/> Val. 4 Pace Fanon/Courier		
2nd Class FCC Encyclopedia	602 p. 445 il.	\$7 95
The Complete Shortwave Listener's Hdbk.	288 p. 101 il.	\$6 95
CB Radio Operator's Guide—2nd ed.	256 p. 139 il.	\$5 95
Pictorial Guide to CB Radio Install. Repair	256 p. 304 il.	\$5 95
Practical CB Radio Troubleshooting & Repair	238 p. 108 il.	\$5 95
The Complete FM 2-Way Radio Handbook	294 p. 111 il.	\$6 95
Amateur FM Conversion & Construction Projs.	256 p. 187 il.	\$5 95
Broadcast Annnc'r. 3rd Class FCC Study Guide	168 p. 19 il.	\$3 95
How To Be A Ham—including Latest FCC Rules	192 p. 25 il.	\$3 95
Commercial FCC License Handbook	444 p. 150 il.	\$5 95
The 2-Meter FM Repeater Circuits Handbook	312 p. 194 il.	\$6 95
RTTY Handbook	320 p. 230 il.	\$6 95
Citizens Band Radio Service Manual	228 p. 84 il.	\$5 95
AMATEUR RADIO STUDY GUIDES	<input type="checkbox"/> Novice <input type="checkbox"/> \$5.95 <input type="checkbox"/> General <input type="checkbox"/> \$7.95 <input type="checkbox"/> Advanced <input type="checkbox"/> \$5.95 <input type="checkbox"/> Extra <input type="checkbox"/> \$5.95 <input type="checkbox"/> Incentive <input type="checkbox"/> \$4.95	

RADIO & TV SERVICING

Color TV Trouble Facts—Problems/Solutions	3rd ed. 434 p.	\$5 95
Solid State Color TV Photo Symptom Guide	224 p. 169 il.	\$5 95
Beginner's Guide to TV Repair	176 p. 50 il.	\$4 95
Troubleshooting With the Dual-Trace Scope	224 p. 252 il.	\$5 95
TV Troubleshooter's Handbook—3rd ed.	448 p. over 300 il.	\$4 95
Color TV Case Histories Illustrated	238 p. 219 il.	\$5 95
TV Schematics: Read Between the Lines	252 p. 188 il.	\$5 95
Logical Color TV Troubleshooting	240 p. 151 il.	\$5 95
TV Bench Servicing Techniques	228 p. 177 il.	\$4 95
Modern Radio Repair Techniques	260 p. 36 il.	\$4 95
How to Interpret TV Waveforms	256 p. 250 il.	\$4 95
All-In-One TV Alignment Handbook	304 p. 145 il.	\$5 95
TV Tuner Schematic/Servicing Manual	224 p. 287 il.	\$6 95
195 Color TV Troubles & Solutions	224 p. 178 il.	\$4 95
How to Use Color TV Test Instruments	256 p. 230 il.	\$5 95
Home-Call TV Repair Guide	144 p. 20 il.	\$3 95
Pinpoint TV Troubles in 10 Minutes	327 p. 294 il.	\$5 95


ELECTRONICS TECHNOLOGY/COMPUTERS/CALCULATORS

Modern Electronics Math	686 p. 424 il.	\$9 95
Master Hdbk of 1001 Prac. Electronic Circ.	602 p. 1250 il.	\$9 95
Impedance	196 p. 90 il.	\$5 95
Intro to Medical Electronics 2nd ed.	320 p. 126 il.	\$7 95
Computer Programming Handbook	518 p. 114 il.	\$8 95
Computer Technician's Handbook	480 p. over 400 il.	\$8 95
Microelectronics	266 p. 228 il.	\$5 95
Basic Digital Electronics	210 p. 117 il.	\$4 95
Switching Regulators & Power Supplies	252 p. 128 il.	\$6 95
Advanced Applications for Pocket Calculators		
Tower's International Transistor Selector	140	
Electronic Conversions, Symbols & Formulas		
Effective Troubleshooting With EVM & Scope		
Getting the Most Out of Electronic Calculators		
Aviation Electronics Handbook	406 p. 227 il.	\$7 95
How to Test Almost Everything Electronic	160	
Digital/Logic Electronics Handbook	308 p. 22	
Modern Applications of Linear IC's	276 p. 30	
10-Minute Test Techniques For PC Servicing		
Electr. Unveiled—New Commonsense Appr		
How To Tshoot/Repair Electronic Test Eqp.	252	
Understanding & Using the Oscilloscope	272	
Industrial Electronics: Principles & Practice	4	
Dictionary of Electronics	420 p. 487 il.	\$5 95

Bibliotheek Ned.

Send for Free TAB Catalog describing over 4000 titles

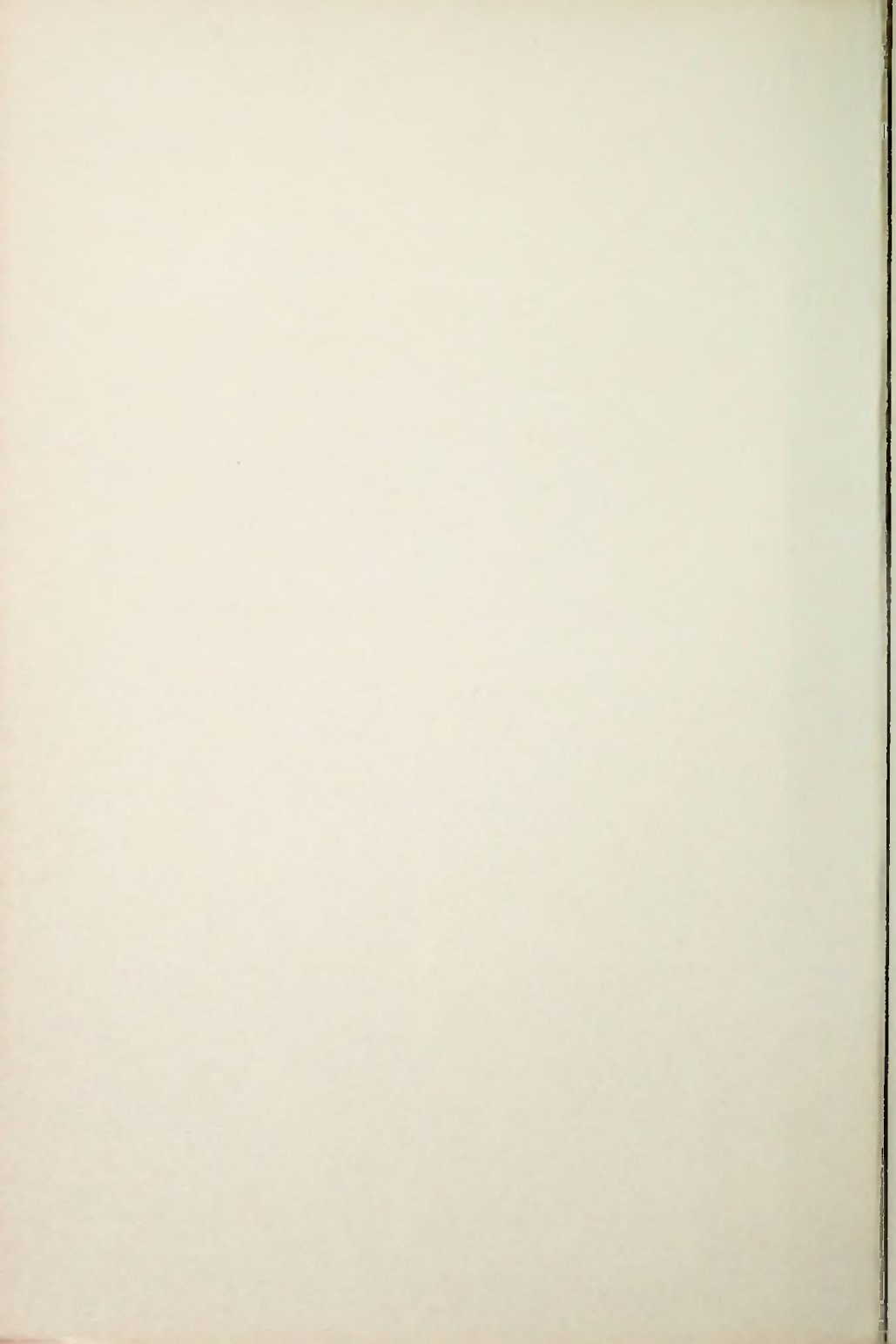Color TV Schematics - Blue Ribbon Service - Radio Shack 1724



BIBLIOTHEEK
N.V.H.R.

**106 EASY
ELECTRONICS PROJECTS—
Beyond the Transistor**

By Rufus P. Turner



TAB BOOKS

Blue Ridge Summit, Pa. 17214

FIRST EDITION

FIRST PRINTING—DECEMBER 1976

Copyright © 1976 by TAB BOOKS

**Printed in the United States
of America**

Reproduction or publication of the content in any manner, without express permission of the publisher, is prohibited. No liability is assumed with respect to the use of the information herein.

Hardbound Edition: International Standard Book No. 0-8306-6887-X

Paperbound Edition: International Standard Book No. 0-8306-5887-4

Library of Congress Card Number: 76-45059

Preface

This book is addressed to experimenters, technicians, students, and others who are already familiar with bipolar transistors and conventional diodes and who now want to work with other semiconductor devices. Fully tested circuits are given for FETs, MOSFETs, ICs, UJTs, tunnel diodes, varactors, zener diodes, diacs, triacs, and SCRs. No rectifiers, conventional diodes, or bipolar transistors appear except where they serve as auxiliary components in the main circuits.

The presentation is practical, save for an introduction, in each chapter, which describes in simple terms the device featured in that chapter. This format should enable the reader to learn the theory of the device quickly and should prepare him to use the circuits to better advantage.

In each chapter, the applications shown have been chosen because they seem best to exploit the advantages of the particular device. Electronic components are listed with each circuit diagram. But secondary parts—such as sockets, chassis, enclosures, miscellaneous hardware, and so on—are not specified, since the reader is free to choose these noncritical items according to his own preferences and demands.

While it is assumed that the reader is experienced in building, testing, and operating electronic equipment, he nonetheless should read carefully Chapter 1, "Good Semiconductor Practice," if for no other reason than to reinforce his knowledge of the special precautions needed in handling semiconductor devices safely and successfully.

The author and publisher hope that this book will prove both instructive and entertaining.

RUFUS P. TURNER

Contents

-
- 1 Good Semiconductor Practice 9**
- 2 Field-Effect Transistor FET 14**
 FET Theory—Audio Preamplifier—Two-Stage AF Amplifier—
 Untuned Crystal Oscillator—Tuned Crystal Oscillator—Phase-
 Shift Audio Oscillator—Product Detector—All-Wave
 Regenerative Receiver—Superregenerative Receiver—
 Electronic DC Voltmeter—Direct-Reading Capacitance Meter—
 Initial Calibration
- 3 Metal Oxide Semiconductor Field-Effect Transistor MOSFET 39**
 MOSFET Theory—General Purpose RF Amplifier—Ten-Meter
 Preamplifier—Wideband Instrument Amplifier—Source
 Follower—Q Multiplier—Wide-Range LC Checker—Interval
 Timer—Capacitance Relay—Touch-Plate Relay—
 Electroscopie—Ultrasonic Pickup
- 4 Integrated Circuit IC 64**
 IC Theory—Complete Audio Amplifier—Audio Power Amplifier
 With MOSFET Input—2½-Watt Intercom—Very Low-Resistance
 DC Milliammeter—Electronic DC Millivoltmeter—Low-Pass Ac-
 tive Filter—High-Pass Active Filter—Combination High-Pass.
 Low-Pass Active Filter—Bandpass (Peak) Active Filter—Active
 Bandstop (Notch) Filter—Conventional Bandpass Active
 Filter—Signal Tracer—Group Code-Practice Oscillator
- 5 Unijunction Transistor UJT 89**
 UJT Theory—Pulse Generator—Pulse and Timing Generator—
 Free-Running Multivibrator—One-Shot Multivibrator—
 Relaxation Oscillator—Standard-Frequency Oscillator—CW
 Monitor—Metronome—Tone-Identified Signal System—Trigger
 for SCR
- 6 Tunnel Diode TD 107**
 TD Theory—General-Purpose AF-RF Oscillator—Crystal
 Oscillator—Voltage-Controlled RF Oscillator—Frequency Con-
 verter—Citizens' Band Converter—Audio Amplifier—Dip
 Meter—Regenerative Receiver—Flea-Powered CW Transmitter—
 Remote-Control Transmitter—Triggered Switch

7 Variable-Capacitance Diode VCD 128

VCD Theory—Voltage-Variable Capacitor—VCD-Tuned LC Circuits—Remotely Controlled Tuned Circuit—Voltage-Tuned RF Oscillator—Automatic Frequency Control for FM Receiver—Frequency Modulators—Frequency Multipliers—RF Harmonic Intensifier

8 Zener Diode 148

Zener Diode Theory—Simple DC Voltage Regulator—Simple, Higher Voltage DC Regulators—Multiple-Output DC Voltage Regulator—Light-Duty Regulated DC Supply—5-Volt, 1.25 Ampere Regulated DC Supply—18-Volt, 1-Ampere Regulated DC Supply—Voltage-Regulated Dual DC Supply—Regulated Voltage Divider—Transistor-Bias Regulator—Voltage Regulator for Tube Heater—Simple AC Voltage Regulator—Automatic Volume Limiter—DC-Equipment Protector—DC Voltage Standard

9 Diac 170

Diac Theory—Amplitude-Sensitive Switch—Static DC Switch—Electrically Latched Relay—Latching Sensor Circuit—DC Overload Circuit Breaker—AC Overload Circuit Breaker—Phase-Controlled Trigger Circuit

10 Triac 184

Triac Theory—Simple Triac Switch—General-Purpose Controller—Controller Using Combination Thyristor—DC-Controlled Solid-State AC Relay—Sensitive DC-Controlled Triac Switch—Motor Controls—Light Dimmers—Variable Dual DC Power Supply—Automatic Equipment Power Switch

11 Silicon Controlled Rectifier SCR 200

SCR Theory—Basic SCR Switches—Light-Controlled SCR—SCR Light Dimmer—SCR Motor Control—Photoelectric Burglar Alarm—Switch-Type Burglar Alarm—Photoelectric Garage-Door Opener—Variable DC Power Supply (115 Volts)—Variable DC Power Supply (High-Voltage)—DC-To-AC Inverter—Solid-State Timer

1

Good Semiconductor Practice

Modern solid-state devices are remarkably well built, considering their smallness and complexity, and many of them are surprisingly inexpensive. Moreover, their performance is consistent. However, their electrical and mechanical ruggedness, easy availability, and reproducible performance should not be taken for granted. Careless handling, installation, and operation of these devices and misguided application of them can still cause damage or poor performance.

The following paragraphs offer guidance in working with semiconductor devices, and these hints and precautions are offered for the benefit of *all* readers. Observance of good engineering practice here will pay off in increased success with semiconductor devices.

This material applies directly or indirectly to all of the circuits in this book. By presenting it in this one place, we avoid taking space and time to repeat hints and precautions with individual circuits.

Avoid Rough Handling. This includes dropping, hammering, vibrating, or forcibly squeezing or tensing the device; pulling, twisting, or repeatedly flexing its pigtailed or lugs; and mounting the device under severe pressure or tension.

Mechanical Assembly. The reader is free to use his favorite method of construction: simple breadboard, perforated board, open chassis, metal box, printed circuit. Employ the same techniques and precautions that would apply to any other electronic circuit.

Install The Semiconductor Last. In this way, the device will not be subjected to repeated heatings caused by soldering in the circuit. It is important to check the circuit wiring thoroughly before installing the semiconductor device, to insure that the device will not be heated by unsoldering and resoldering to correct mistakes in the wiring. When the device is a standard MOSFET, keep the short-circuiting ring (that comes attached to this device) in place until the MOSFET is completely installed in the *completed* circuit; then remove it. The gate-protected MOSFET needs no such protecting ring.

Remove Semiconductor First. When dismantling a circuit, remove the semiconductor device *first*. This procedure, which protects the device from heat caused by unsoldering, is the opposite of that recommended when building the circuit (see item above).

Semiconductor Mounting. All methods of device mounting are permitted, as long as the mounting is solid. These include use of socket, soldering or welding directly into circuit, use of clips, use of mounting screws, and use of terminal studs. The pigtailed or lugs of the mounted device must be under no stress.

Soldering Or Welding. To prevent internal damage to the semiconductor device, use a suitable heat sink in the regular manner when soldering or welding the device into the circuit. Keep the heat sink in place for a reasonable time *after* the joint has cooled.

Keep Leads Straight. If a semiconductor device is to be inserted into a socket, straighten its pigtailed or lugs beforehand. To drive the device home into the socket, push firmly, but gently and straight down, on the top of the case. When leads must be bent for a particular installation, avoid a sharp right-angle bend, since such a bend tends to break easily. Use care when removing a semiconductor device from its socket.

Hot Case. The metal case of some semiconductors is "hot;" that is, the case is internally connected to one of the electrodes of the device. If the manufacturer's literature or the circuit diagram and/or the text in this book indicates this condition, keep the case free from contact with other components, metal chassis, and wiring.

Use Specified Components. Employ the exact values of components specified in the circuit diagrams. If you wish to experiment, start first with the specified value. Make adjustments exactly as instructed in the text. Where the manufacturer and model number are given for a component, this is either the only such component available or is the one that at the time of the writing was the one easily available to experimenters on a single-unit retail basis.

Wiring And Isolation. Use the shortest and most direct leads practicable; this will minimize stray pickup, undesired coupling, and undesired feedback. When long leads are unavoidable, lead dress and adequate separation are important. With high-gain devices, such as the FET, MOSFET, and IC, the input and output circuits sometimes must be shielded from each other, especially if they employ inductors or transformers. In all RF and high-gain AF circuits, shield and bypass all susceptible parts of the circuit in the same way that tube circuits are safeguarded.

Grounds. In some of the circuit diagrams, a dashed line runs to the ground symbol. This means that the connection to chassis or to earth is optional and depends upon how the circuit will be used by the reader. When, instead, a solid line runs to the ground symbol, the connection *must* be made.

Connect Power Last. Connect the power supply last, whether it is AC or DC, and then only after the circuit wiring has been double checked and verified as correct. In an experimental application—where voltages are not specified as they are in this book—start with a low voltage and gradually increase it.

Type of Power Supply. In many of the circuits, batteries are shown for DC supply, as a matter of

simplicity; however, a *well-filtered* transformer-rectifier type of supply also may be used.

Complexity of Power Supply. Some IC circuits function best with a dual power supply and accordingly are shown with two batteries; others get along with a single battery. Readers who already are expert with ICs may have favorite schemes for converting the two-battery circuit to single battery; however, it is best for all others to wire and test the circuit first as it is given in the book, and then to experiment later.

Use Specified Voltages. Employ the voltages specified in the circuit diagrams. Although a variation of a few percent, plus or minus, should not drastically affect operation of a circuit, a very large change in voltage can alter performance markedly from that reported in the text.

DC Polarity. Reversing the DC supply voltage can damage some semiconductor devices and cause others to switch off. Carefully observe polarity.

Avoid Excessive Supply. Do not subject the semiconductor device to excessive currents or voltages. Be guided by the values given in the circuit diagrams and in the text. Never allow the combined current or voltage (that is, DC plus peak AC) to exceed the maximum value given in the manufacturer's literature or warned against in the text.

Avoid Heat. Protect the semiconductor device from excessive heat, either external or internal. Where a heat sink is specified, it *must* be used. Keep the device clear of hot tubes, rectifiers, and other such components.

Avoid External Fields. The semiconductor device and its circuit must be protected from strong, external magnetic fields. Common sources of such fields are transformers, chokes, motors, generators, relays, circuit breakers, and loudspeakers.

Avoid Overdriving. Excessive signal amplitude can degrade the performance of some semiconductor devices and in some instances may even damage them. The maximum signal voltage permissible in a susceptible circuit is given in the circuit diagram or in the text, and should not be exceeded.

Testing And Troubleshooting. Employ standard test procedures when checking circuits or shooting trouble:

- 1—Use high-resistance (preferably electronic) voltmeter
- 2—Use low-resistance current meter
- 3—Monitor with an oscilloscope any AC circuit
- 4—Use low-distortion AC test signals
- 5—Be certain that your test procedure does not itself introduce excessive voltages, or transients
- 6—Test semiconductor devices with an appropriate instrument (transistor tester, IC tester, etc.) or with a foolproof laboratory setup (that is, one in which the test itself does not damage the semiconductor).

In most instances, a service-type ohmmeter will be accurate enough for testing resistors and making leakage or continuity tests. Ohmmeter tests of semiconductor devices, however, are not recommended, since some ohmmeters can apply a damaging voltage to these devices.

SAFETY NOTICE. Some semiconductor circuits—especially those employing diacs, triacs, and silicon controlled rectifiers—are operated from the AC power line and can be dangerous if not carefully built and installed and cautiously handled. To avoid electric shock or damage to equipment when working with such circuits, observe all of the usual precautions that apply to high voltages. For maximum safety with some circuits, a 1:1 isolating transformer should be inserted between the power line and the circuit (as recommended, for example, in Figures 10-6 and 10-7, Chapter 10): this will prevent the circuit from being connected directly to the power line. In other instances, the isolating transformer is desirable, but not mandatory.

2

Field-Effect Transistor FET

The *field-effect transistor (FET)* exhibits high input impedance (in the megohms) and accordingly presents negligible loading to a signal source or preceding stage. In this respect, the FET, unlike the conventional bipolar transistor, behaves more like a vacuum tube than a semiconductor device. FET transconductance is high (1000 to 12,000 micromhos, depending upon make and model) and maximum operating frequency likewise is high (up to 500 MHz for some types). This device is useful in all kinds of electronic circuits and can directly replace the tube in some of them.

The kind of FET featured in this chapter is the junction type (JFET). It is composed of junctions in a silicon chip, but is quite different from a junction-type bipolar transistor, as is explained below.

Before working with FETs, read the hints and precautions in Chapter 1.

FET THEORY

Figure 2-1 (A) shows the cross section of a FET. A manufactured unit is somewhat more complex in structure, but the illustration given here is functionally correct and will demonstrate the basic structure and behavior of the device. In this FET, P-regions are processed into opposite faces of an N-type chip and are connected together to form the control

electrode (called the *gate*, G) which corresponds to the grid of a tube or the base of a bipolar transistor.


An ohmic connection is made at each of the two ends of the chip. One of these is termed the *drain* (D) and corresponds to the plate of a tube or the collector of a bipolar transistor, and the other is termed the *source* (S) and corresponds to the cathode of a tube or the emitter of a bipolar transistor. The region extending internally from drain to source and passing between the two halves of the gate electrode is termed the *channel*.

Although Fig. 2-1 (A) shows P-type gate electrodes in an N-type chip, the opposite arrangement is also possible; that is, N-type gate electrodes can be processed into a P-type chip. An FET employing an N-type chip is termed an N-channel FET or an *NFET*, and its circuit symbol appears in Fig. 2-1 (B), whereas a FET employing a P-type chip is termed a P-channel FET or a *PFET*, and its circuit symbol appears in Fig. 2-1 (C).


Figure 2-2 illustrates FET operation. Here, a DC supply (V_{DD}) provides operating voltage (V_{DS}) between drain and source, with drain positive and source negative; and a second DC supply (V_{GG}) provides a bias voltage (V_{GS}) between gate and source, with gate negative and source positive. In Fig. 2-2 (A), the gate voltage is zero, and under this condition, a maximum value of drain current (I_D) flows from supply V_{DD} , through the channel, and back to V_{DD} . In Fig. 2-2 (B), the gate voltage has a low negative value.

The application of this voltage causes a depletion layer—a region in which no current carriers exist—to appear around each of the P-regions of the gate electrode, as shown by the dotted lines. These layers penetrate deep into the chip and narrow the channel, thereby reducing drain current I_D . When the gate voltage is increased to a sufficiently high negative value, the depletion layers meet and block the channel, cutting off the flow of drain current.


Between these limits of maximum current and cutoff, the drain current may be set to any intermediate value by appropriately setting the gate voltage. Because the drain current is controlled by gate *voltage*, the FET possesses transconductance and is a good amplifier. And because the control (gate) electrode is a reverse biased PN junction, any control current is negligible; that is, the input resistance of the device is very high. Figure 2-2 (C) shows FET performance in

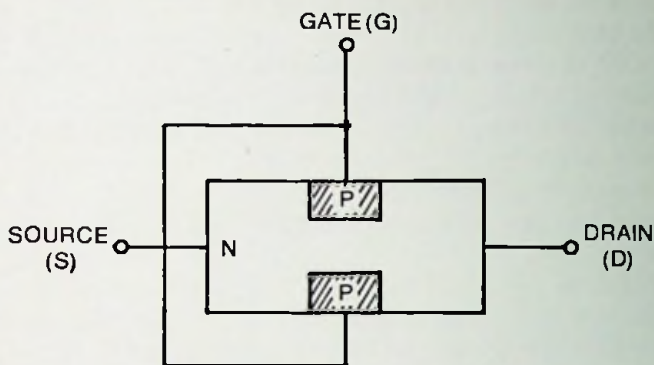

(A) BASIC STRUCTURE

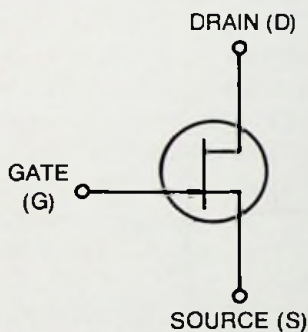

(B) NFET SYMBOL

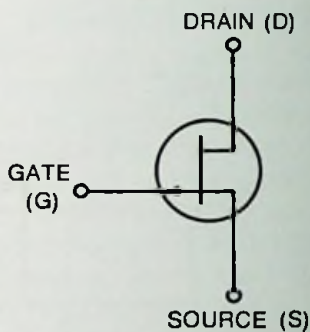


(C) PFET SYMBOL

Fig. 2-1. Details of junction FET.


a family of curves resembling those for a pentode tube. An NFET is shown in Fig. 2-2; for a PFET, reverse the polarity of V_{DD} and V_{GG} . The performance curves will remain substantially the same as in Fig. 2-2 (C).

AUDIO PREAMPLIFIER

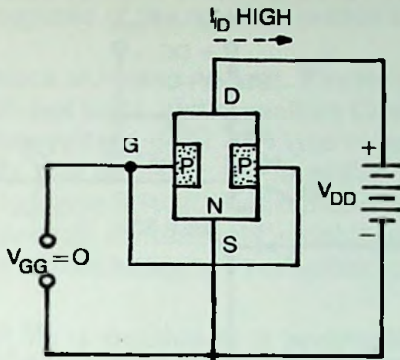
The FET is admirably suited to miniature AF amplifiers because it is small, it possesses high input impedance, it needs only a small amount of DC power, and it provides good frequency response. Such AF amplifiers, employing simple



(A) ZERO GATE VOLTAGE

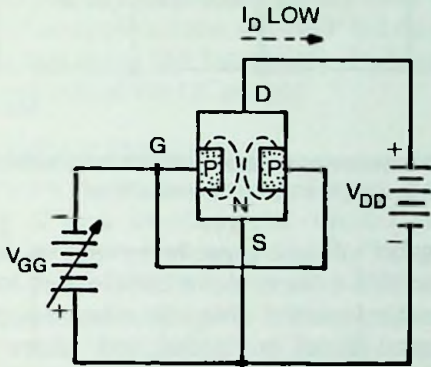

(B) NEGATIVE GATE VOLTAGE

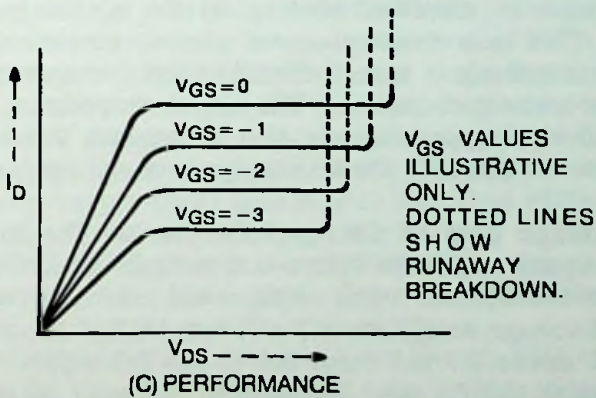

(C) PERFORMANCE

Fig. 2-2. JFET action.

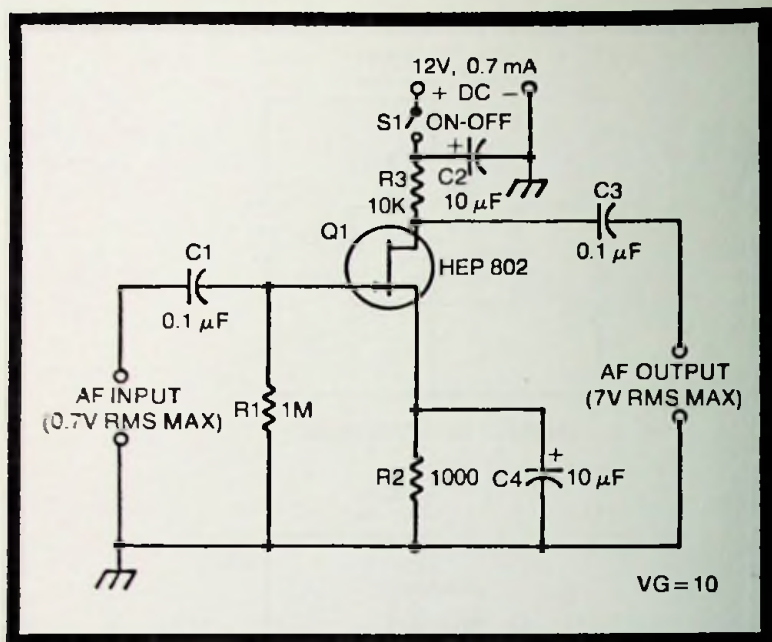


Fig. 2-3. Single-stage AF preamplifier.

circuits. provide good voltage gain and may be built tiny enough to be contained in a microphone handle or in an AF test probe. They are easily inserted also into other equipment at points where a signal boost is needed and where existing circuitry must not be appreciably loaded.

Figure 2-3 shows the circuit of a single-stage, one-transistor amplifier offering all the advantages of the FET. This is a common-source circuit, equivalent to the common-cathode tube circuit and common-emitter bipolar-transistor circuit. The input impedance of the amplifier is approximately the 1 megohm presented by resistor R1. The HEP 802 is an inexpensive and easily obtained FET.

Voltage gain of the amplifier is 10. The maximum input-signal amplitude before output-signal peak clipping is approximately 0.7 volt rms, and the corresponding output-voltage amplitude is 7 volt rms. At full operation, the circuit draws 0.7 mA from the 12-volt DC supply. With an individual FET, the input-signal voltage, output-signal voltage, and DC operating current may differ somewhat from

the values given above. Between 100 Hz and 25 kHz, the frequency response of the circuit is within 1 dB of the 1000 Hz reference.

All resistors are $\frac{1}{4}$ - or $\frac{1}{2}$ -watt. Electrolytic capacitors C2 and C4 are 35-volt units, and capacitors C1 and C3 may be any convenient low-voltage units. Any type of battery or other DC power supply can be used; the amplifier may even be sun powered by two type SP4C40B silicon solar modules connected in series. If desired, continuously variable gain control may be obtained by substituting a 1-megohm potentiometer for resistor R1.

This circuit is suitable as a preamplifier or as a main amplifier in all applications requiring a 20 dB signal boost throughout the audio spectrum. The high input impedance and medium output impedance will satisfy most requirements. For very low-noise applications, the HEP 802 may be replaced with a 2N3578; however, the latter is a P-channel FET and will demand reversal of the DC supply.

TWO-STAGE AF AMPLIFIER

Figure 2-4 shows the circuit of a two-stage FET amplifier consisting of two identical RC-coupled stages of the type discussed in the previous section. This unit will give a substantial boost (40 dB) to a small AF signal, and can be used either alone or as a stage in other equipment. The HEP 802 transistors are low-priced and readily available. The input impedance of the amplifier is approximately 1 megohm, the resistance of the input-stage resistor, R1.

Overall voltage gain of the amplifier is 100, but this figure may vary somewhat—up or down—with individual FETs. The maximum input-signal amplitude before output-signal peak clipping is 70 mV rms, and the corresponding output-signal amplitude is 7 volts rms. At full operation, the circuit draws approximately 1.4 mA from the 12-volt DC supply, but this current may vary a small amount with individual FETs. (No need was found for a decoupling filter between stages, and such a filter will decrease the current of one stage.) The frequency response of the amplifier is flat within ± 1 dB of the 1 kHz level, from 100 Hz to better than 20 kHz.

All resistors in the circuit are $\frac{1}{4}$ - or $\frac{1}{2}$ -watt. Electrolytic capacitors C2, C4, and C6 are 25-volt units, and capacitors C1, C3, and C5 may be any convenient low-voltage units. The

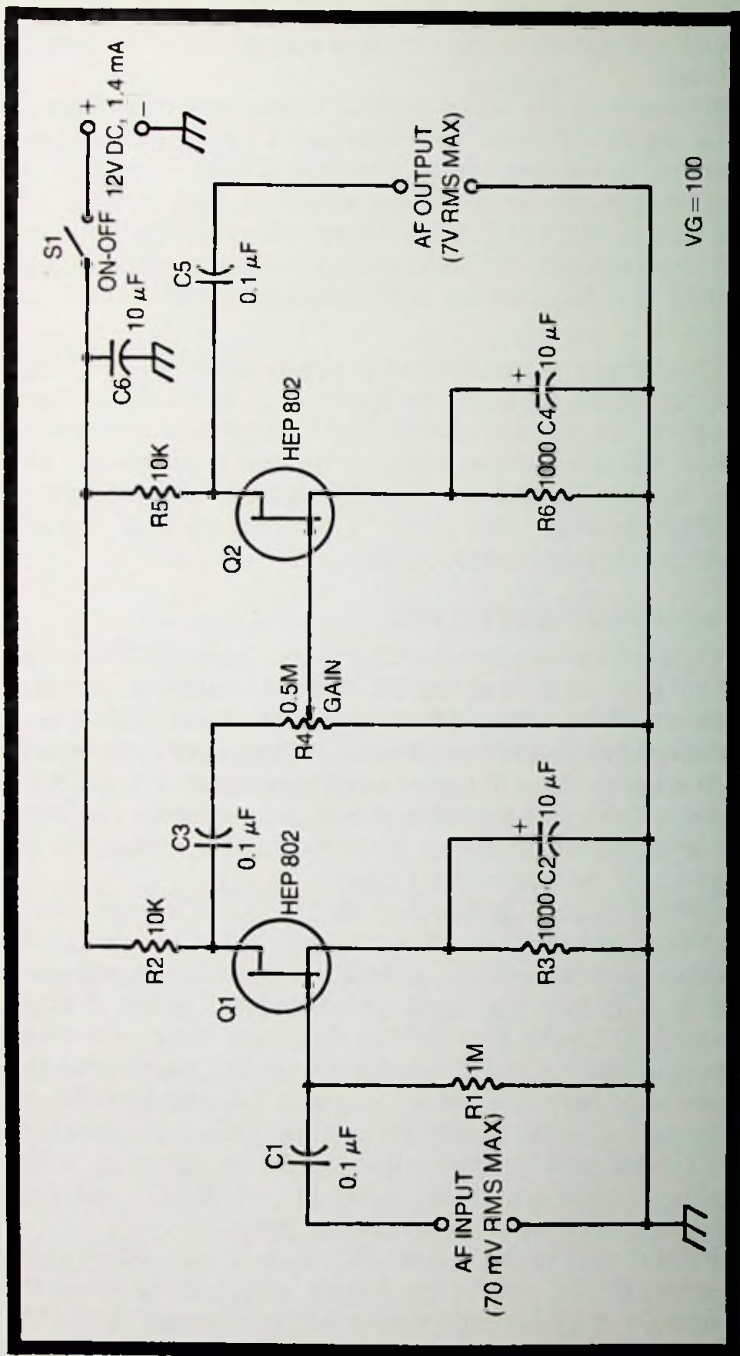


Fig. 2-4 Two-stage AF amplifier

amplifier can be operated from a self-contained 12-volt battery or from an external battery or line-operated power supply.

Since the input stage runs "wide open," there may be some tendency to pick up hum and noise unless this stage and the input leads are well shielded. In stubborn cases, R1 may be reduced to 0.47 Meg. Where the amplifier must introduce only small loading of the signal source, R1 may be increased to as high a value as 22 megohms, provided the input stage is very well shielded. However, resistance higher than this value tends to approach the FET junction resistance. For very low noise applications, the input HEP 802 FET (Q1) may be replaced with a 2N3578; however, the latter is a P-channel FET and will demand reversal of the DC supply.

UNTUNED CRYSTAL OSCILLATOR

A Pierce-type crystal oscillator has the advantage that it requires no tuning; plug in the crystal, switch on the DC supply, and obtain RF output. A circuit of this type, employing a single HEP F0015 field-effect transistor, is shown in Fig. 2-5. The untuned crystal oscillator finds use in transmitters, markers, receiver front ends, clock generators, crystal testers, RF signal generators, signal spotters (secondary frequency standards), and many similar devices. With most crystals, the circuit is a quick starter that is easy on crystals.

The untuned oscillator draws approximately 2 mA from the 6-volt DC supply. At this supply voltage, the open-circuit RF output voltage is approximately 4½ volts rms. DC supply

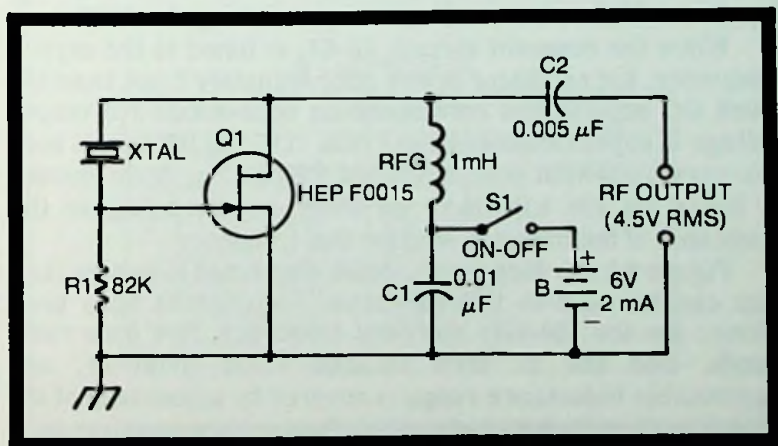


Fig. 2-5. Untuned crystal oscillator.

voltages up to 12 volts can be used, with proportionately higher RF output.

To determine if the oscillator is operating, close switch S1 and connect an RF voltmeter to the *RF Output* terminals. (A high-resistance DC voltmeter shunted by a general-purpose germanium diode will suffice if an electronic voltmeter with RF probe is not available.) Deflection of the meter indicates oscillation. Alternatively, the oscillator may be connected to the *Antenna* and *Ground* terminals of a CW receiver which may be tuned through the crystal frequency to detect oscillation.

To prevent erroneous operation, the user must remember that the Pierce oscillator operates at the labeled frequency of a crystal only when the crystal is a fundamental-frequency cut. When overtone crystals are used, the oscillator output will not be the labeled frequency, but the lower frequency determined by the crystal dimensions. For operation at the labeled frequency of an overtone crystal, the oscillator must be of the tuned type.

TUNED CRYSTAL OSCILLATOR

Figure 2-6 (A) shows the circuit of a general-purpose crystal oscillator which will operate with all types of crystals. The FET is an inexpensive and readily available HEP 801. The circuit is tuned by means of the screwdriver-adjusted slug in inductor L1. This oscillator is readily adapted to communications, instrumentation, and control applications. It may even be used as a flea-powered transmitter (DC power input, 12 mW) for communications or radio model control.

When the resonant circuit, L1-C1, is tuned to the crystal frequency, the oscillator draws approximately 2 mA from the 6-volt DC supply. The corresponding open-circuit RF output voltage is approximately 4 volts rms. (DC and RF values both will vary somewhat with individual FETs.) The drain current is lower on 100 kHz than on other bands, owing to the resistance of the inductor used for that frequency.

Figure 2-6 (B) lists commercial, slug-tuned inductors (L1) that can be used in this oscillator. Inductances have been chosen for the 100 kHz standard frequency, five ham radio bands, and the 27 MHz citizens' band; however, an appreciable inductance range is covered by adjustment of the slug of each inductor, and a wider frequency range than each band indicated in the table can be obtained with each inductor.

The oscillator may be tuned to a crystal frequency by adjusting the slug of the corresponding inductor (L1) for maximum deflection of an RF voltmeter connected to the *RF Output* terminals. (If an electronic voltmeter with an RF probe is not available, a high-resistance DC voltmeter shunted by a general-purpose germanium diode will suffice.) Alternatively, the oscillator may be tuned with a 0-5 DC millimeter inserted temporarily at point X: Adjust the slug of inductor L1 for deepest dip in the meter reading.

All resistors are 1/4- or 1/2-watt. For best results, especially at the higher frequencies, the capacitors all should be of the mica type; for low frequency drift, C2 should be silvered mica.

The slug tuning arrangement provides fine-tuned operation. In applications where it is necessary to tune the oscillator continuously with a resettable dial, a 100 pF variable

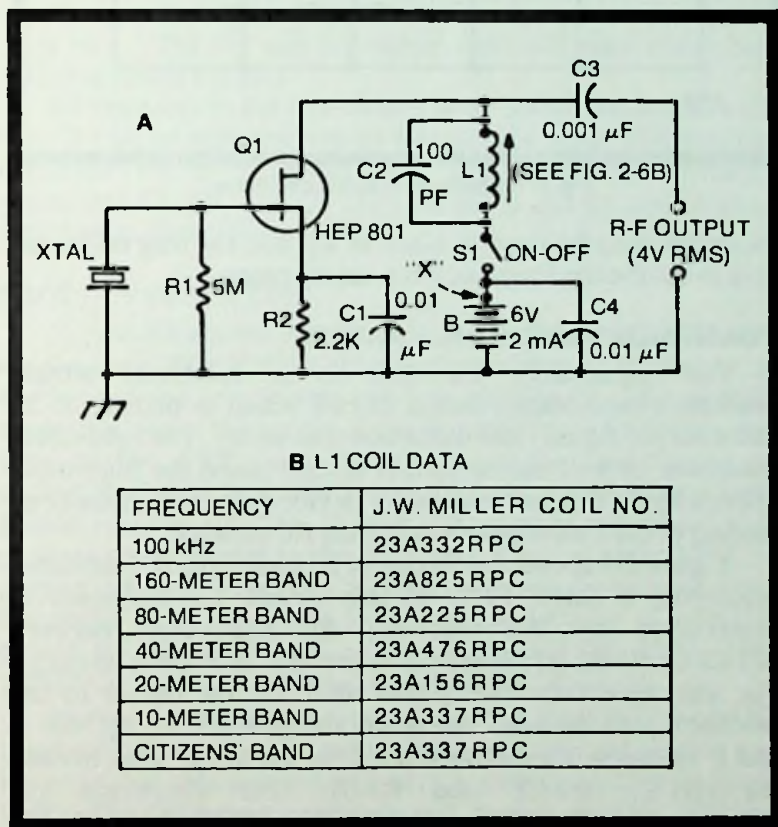


Fig. 2-6. Tuned crystal oscillator.

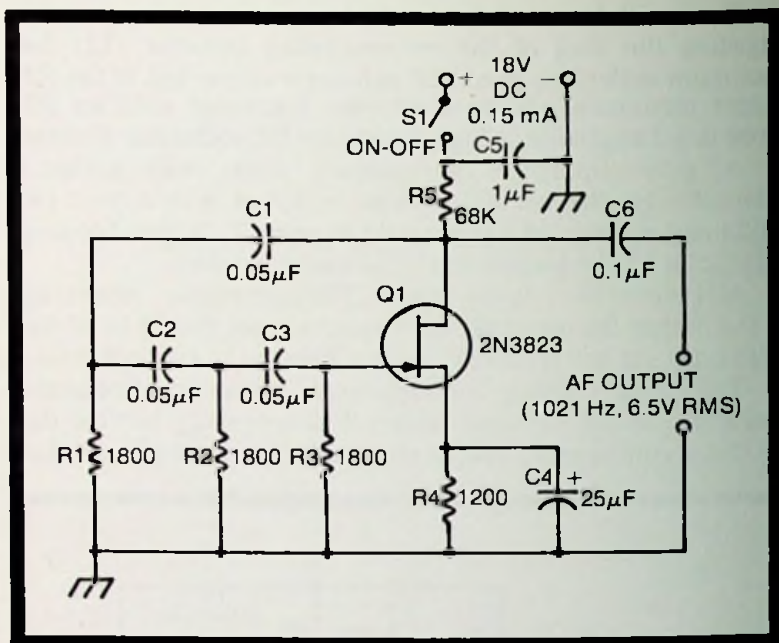


Fig. 2-7. Phase-shift audio oscillator.

capacitor may be used in place of C2, and the slug employed only to set the top frequency of a tuning range.

PHASE-SHIFT AUDIO OSCILLATOR

The phase-shift oscillator is a relatively simple resistance-capacitance tuned circuit which is prized for its clean output signal (low-distortion sine wave). The field-effect transistor is well suited to this circuit, since the high input impedance of this semiconductor device results in virtually no loading of the frequency-determining RC network.

Figure 2-7 shows the circuit of a phase-shift AF oscillator employing a single FET. In this circuit, the frequency is determined by the three-leg RC phase-shift network (C1-C2-C3-R1-R2-R3) from which the oscillator takes its name. For the necessary 180° phase shift for oscillation in the feedback path between the drain and gate of FET Q1, the R and C values in the network are selected for 60° shift in each leg (R1-C1, R2-C2, and R3-C3). For simplicity, the capacitances are kept equal ($C1 = C2 = C3$) and the resistances are kept equal ($R1 = R2 = R3$). The frequency of

the network (and accordingly the oscillation frequency of the circuit) then is $f = 1/(10.88 RC)$, where f is in hertz, R in ohms, and C in farads. With the network values given in Fig. 2-7, the frequency therefore is 1021 Hz (for exactly 1000 Hz with the 0.05 μF capacitors, R_1 , R_2 , and R_3 each must be 1838 ohms). When experimenting with a phase-shift oscillator, it will be easier to work with the resistors than with the capacitors. For an available capacitance (C), the required resistance (R) for a desired frequency (f) is $R = 1/(10.88 f C)$, where R is in ohms, f in hertz, and C in farads. Thus, with the 0.05 μF capacitors shown in Fig. 2-7, the resistance required for 400 Hz = $1/(10.88 \times 400 \times 5 \times 10^{-8}) = 1/0.0002176 = 4596$ ohms.

The 2N3823 FET provides the high transconductance (6500 μmho) required for good operation of a phase-shift oscillator. The circuit draws approximately 0.15 mA from the 18-volt DC supply, and the open-circuit AF output is approximately 6.5 volts rms. (The DC and AF values both will vary somewhat with individual FETs.)

All resistors in the circuit are $\frac{1}{4}$ - or $\frac{1}{2}$ -watt. Capacitors C_5 and C_6 can be any convenient low-voltage units. Electrolytic capacitor C_4 is a 25-volt unit. For frequency stability, capacitors C_1 , C_2 , and C_3 must be of top quality and closely matched in capacitance.

PRODUCT DETECTOR

Figure 2-8 shows the circuit of a simple product detector employing a HEP F0015 field-effect transistor. This detector is easily included in compact receiver circuits for CW and SSB reception. Here, the output of the IF amplifier is applied to the gate of the FET, and the output of the beat-frequency oscillator (BFO) is applied to the source across unbypassed source resistor R_4 . The IF and BFO signals are mixed and produce an AF signal in the drain output circuit of the FET. A pi-type low-pass filter (C_4 - C_5 -RFC1) removes the intermediate frequency from the audio output of the detector (a suitable 91-mH RF choke for use in this filter is J. W. Miller No. 70F912AF, having an internal resistance of 250 ohms).

The circuit draws approximately 1 mA from the 18-volt DC supply which may be obtained from any convenient point in the receiver, but this current will vary somewhat with individual FETs. The AF output amplitude will depend upon the relative amplitudes of the IF and BFO signal voltages. For

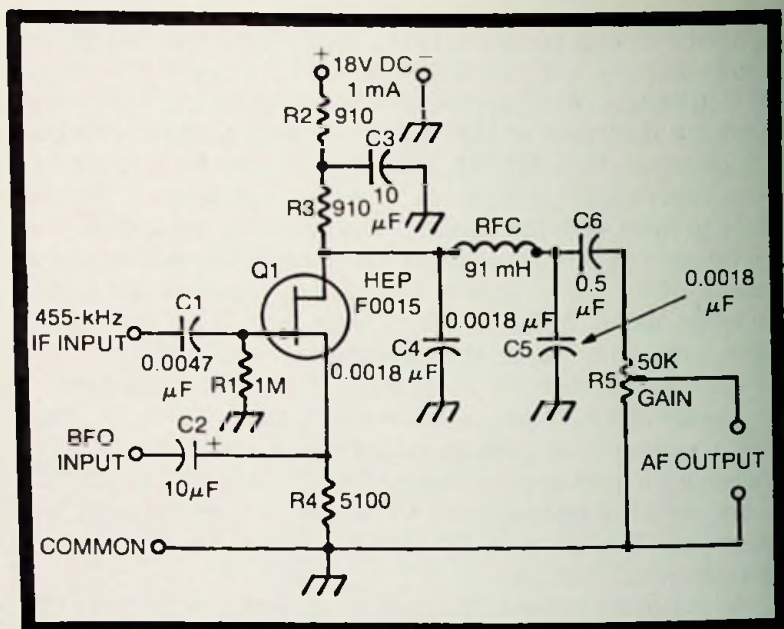


Fig. 2-8. Product detector.

low-distortion operation, i.e., linear detection, it is recommended that the amplitude of the BFO signal be not less than five times that of the IF signal. Ideally, there is no output unless the IF and BFO signals are both applied. The resulting output signal is the product of the two input signals, hence the name *product* detector.

In construction, the IF and BFO input sections of the detector should be kept as clear of each other as practicable, to minimize stray coupling; shielding is advisable. Electrolytic capacitors C2 and C3 are rated at 35 volts or higher; capacitors C1, C4, and C5 are mica or good-grade ceramic units; and capacitor C6 may be any convenient low-voltage unit. All resistors are 1/4- or 1/2-watt.

ALL-WAVE REGENERATIVE RECEIVER

The regenerative receiver is a perennial favorite of radio experimenters. A reasonably sensitive device, it has a simple circuit and is easy to operate. It works over a wide frequency range and responds to either modulated or continuous-wave signals, and for a long time was the only receiver used by many radio hams and short-wave listeners. As an emergency

receiver. the regenerative set can be quickly assembled at low cost.

Figure 2-9 shows the circuit of a tickler-coil type of regenerative receiver which covers the frequency range 440 kHz to 30 MHz in five overlapping bands: 440-1200 kHz, 1-3.5 MHz, 3.4-9 MHz, 8-20 MHz, and 18-30 MHz. Plug-in coils provide a separate tuning inductor (L1) and tickler (L2) for each band. The single FET is an inexpensive HEP 802. In this circuit, positive (regenerative) feedback is obtained by inductively coupling energy back from the drain output circuit of the FET to the gate input circuit via the coupling between tickler coil L2 and tuning coil L1.

The regeneration control is the 50K wirewound potentiometer, R2, by means of which the DC drain voltage is adjusted. At the highest-voltage setting of R2, the circuit will break into oscillation. A pi-type filter (RFC-C4-C5) removes the RF component from the output circuit. Resistor R1 is a 1/4- or 1/2-watt unit, and capacitors C3, C4, C5, and C6 should be mica or good-grade ceramic units.

The audio-frequency output signal is coupled from the circuit by transformer T. This may be any convenient interstage coupling transformer, preferably having a secondary-to-primary turns ratio of 1:1, 2:1, or 3:1. The receiver may be coupled to an audio amplifier, or high-impedance headphones may be connected directly to the *AF output* terminals.

Table 2-1 gives specifications and winding instructions for the plug-in coils. These coils are wound on 1-inch diameter 4-pin plastic forms and are plugged into a 4-contact socket.

Table 2-1. Coil-Winding Data For All-Wave Regenerative Receiver

BAND A 440-1200 kHz	L1. 187 turns No. 32 enameled wire closewound on 1 in. diameter form.
	L2. 45 turns No. 32 enameled wire closewound on same form as L1. Space 1/16" from top of L1.
BAND B 1-3.5 MHz	L1. 65 turns No. 32 enameled wire closewound on 1 in. diameter form.
	L2. 15 turns No. 32 enameled wire closewound on same form as L1. Space 1/16" from top of L1.
BAND C 3.4-9 MHz	L1. 27 turns No. 26 enameled wire closewound on 1 in. diameter form.
	L2. 8 turns No. 26 enameled wire closewound on same form as L1. Space 1/16" from top of L1.
BAND D 8-20 MHz	L1. 10 turns No. 22 enameled wire closewound on 1 in. diameter form.
	L2. 4 turns No. 22 enameled wire closewound on same form as L1. Space 1/16" from top of L1.
BAND E 18-30 MHz	L1. 5 1/2 turns No. 22 enameled wire airwound 1/2 in. in diameter. Space to winding length on 1/2 in.
	L2. 4 turns No. 22 enameled wire airwound 1/2 in. in diameter. Space to winding length of 1/4 in. Mount 1/16" from top of L1.

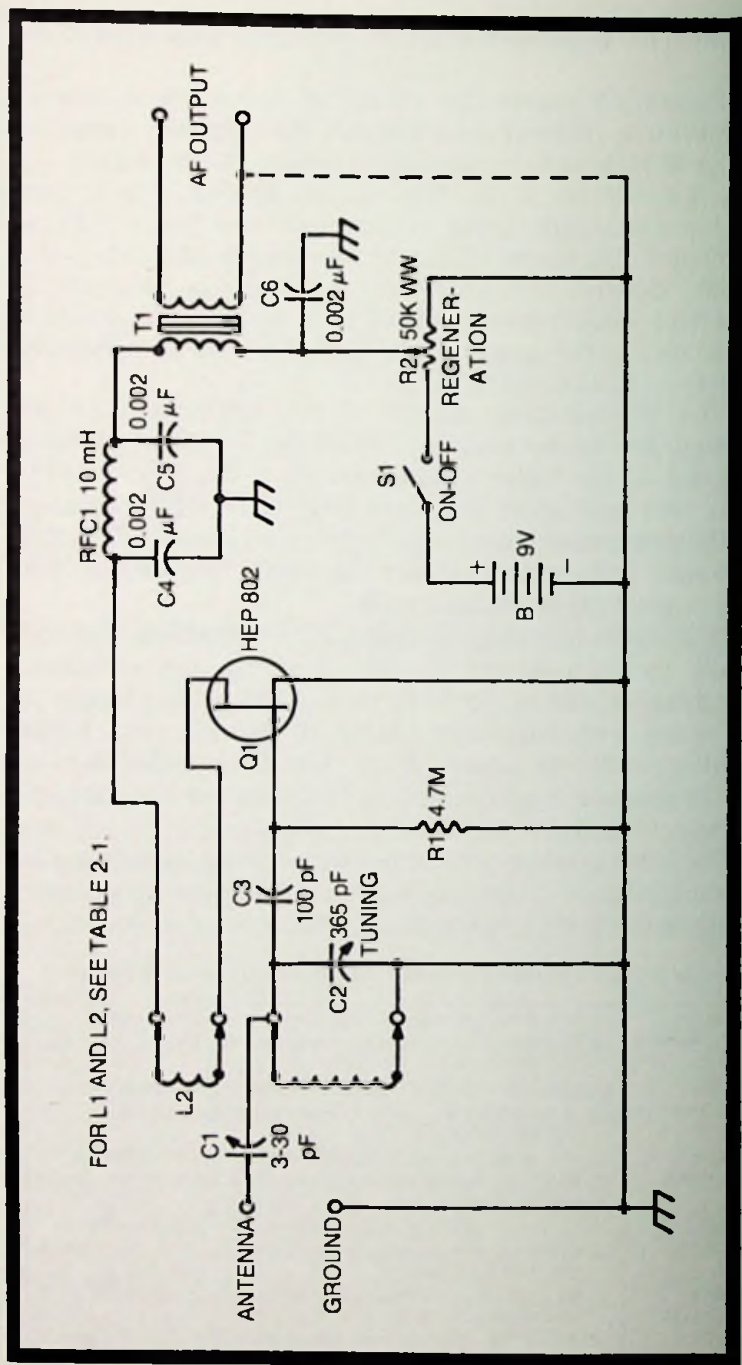


Fig. 2-9. All-wave regenerative receiver.

To test the regenerative circuit initially:

- 1—Connect high-impedance headphones to *AF output* terminals.
- 2—Set potentiometer R2 to its lowest-voltage position.
- 3—Set tuning capacitor C2 to maximum capacitance.
- 4—Close switch S1.
- 5—Slowly advance setting of R2; as maximum-voltage setting is approached, circuit should break into oscillation evidenced by beat-note whistle in headphones. If oscillation fails to occur, reverse leads to L1 or L2, but not both.
- 6—Connect antenna and ground, adjust C2 to tune-in signals, and adjust R2 for maximum weak-signal sensitivity without causing sustained oscillation of receiver. With some FETs, it may be necessary to experiment with the resistance of R1 to obtain maximum sensitivity.
- 7—The 3–30 pF antenna coupling capacitor, C1, is a screwdriver-adjusted trimmer capacitor. Set this trimmer for minimum capacitance that will give a strong signal. The adjustment should be optimum for all five frequency bands, so that C1 need not be readjusted.

The receiver tuning may be calibrated with the aid of an AM signal generator connected to the *antenna* and *ground* terminals. For this purpose, connect high-impedance headphones or *AF* voltmeter to *AF output* terminals, and at each setting of the signal generator, tune C2 for audio peak and inscribe the frequency on the C2 dial. The top frequency in each band may be placed at the same point on the dial by setting the generator to that frequency and adjusting the trimmer on the frame of C2 (most 365 pF capacitors have this trimmer) for audio peak at that point. No volume control has been included in the circuit; but if it is desired, a 50K potentiometer may easily be added at the *AF output* terminals.

The current drawn by the receiver from the 9-volt DC source (B) depends upon the setting of potentiometer R2 and will be of the order of 1 mA at the highest setting (maximum regeneration).

SUPERREGENERATIVE RECEIVER

For its small size, low cost, and simplicity, the superregenerative detector has no equal in sensitivity to signals. Especially useful at ultra-high frequencies, the superregenerator is broad enough in response to "hold onto" a floppy signal, and it has a built-in AGC action.

Figure 2-10 shows the circuit of a self-quenching type of superregenerative receiver built around a 2N3823 VHF field-effect transistor. With four coils, the circuit covers the 2-, 6-, and 10-meter ham bands and the 27 MHz region (see Table 2-2). The frequency coverage allows the receiver to be used for general communications and for radio model control. All coils are single, two-terminal units. The 27 MHz and 6- and 10-meter coils are commercial, slug-tuned units which must be mounted on two-pin plugs for easy insertion and removal (for singleband receivers, these coils may be soldered permanently into the circuit). However, the 2-meter coil must be wound by the reader, and it too must be provided with a plug-in base, except in a single-band receiver. A filter system (RFC1-C5-R3) removes the RF component from the receiver output circuit, and a second filter (R4-C6) attenuates the quench frequency. A suitable 2.4 μ H inductor for the RF filter is J. W. Miller No. 4406.

To test the superregenerative circuit initially:

- 1—Connect high-impedance headphones to *AF output* terminals.
- 2—Set volume-control potentiometer R5 to its maximum-output position.
- 3—Set regeneration-control potentiometer R2 to its bottom end.
- 4—Set tuning capacitor C3 to maximum capacitance.
- 5—Close switch S.

Table 2-2. Coil Data For Superregenerative Receiver

TUNING Capacitance = 15 pF

- A. 10-Meter Amateur Band. J. W. Miller No. 4405. Adjust core.
- B. 6-Meter Amateur Band. J. W. Miller No. 4403. Adjust core.
- C. 2-Meter Amateur Band. 4 turns No. 14 bare wire airwound $\frac{1}{2}$ in. in diameter. Space to hit band.
- D. 27-MHz Range. J. W. Miller No. 4405. Adjust core.

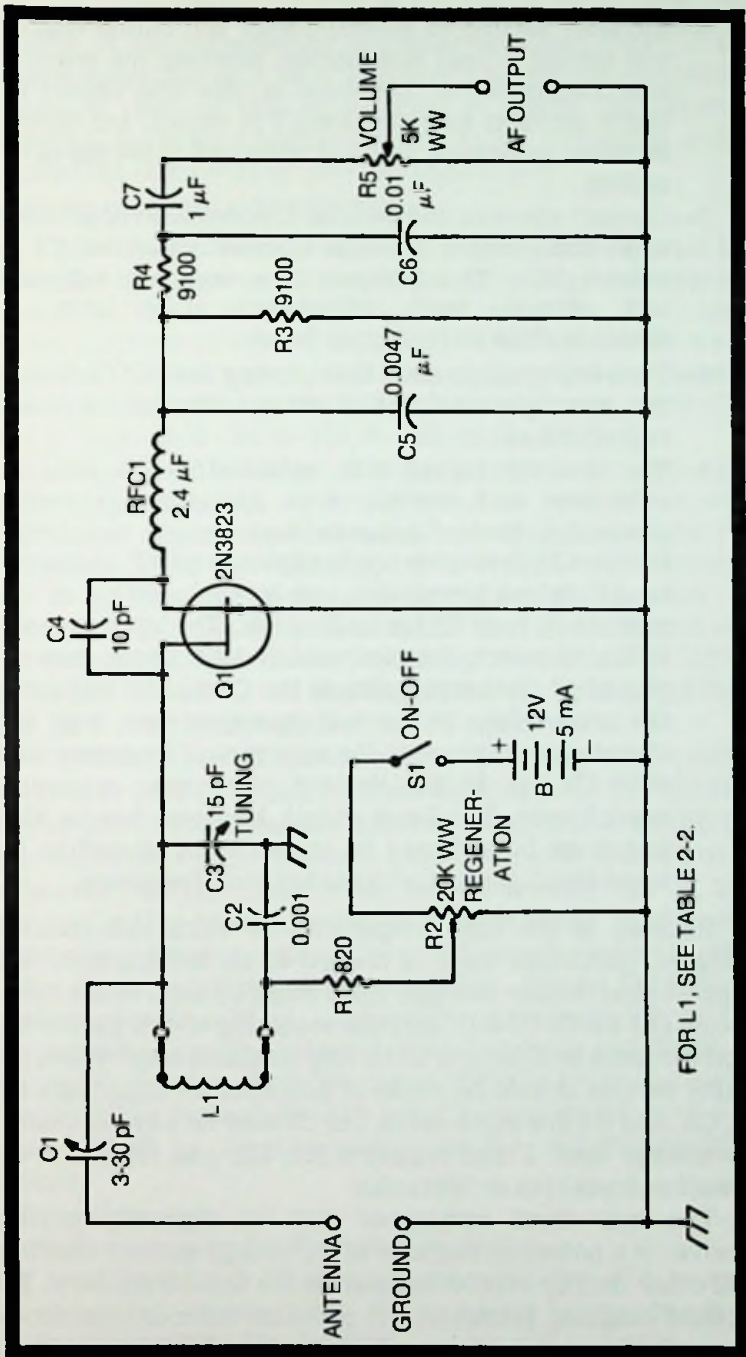


Fig. 2-10. Superregenerative receiver.

- 6—Advance setting of potentiometer R2, noting that at one setting a loud hiss begins, marking the onset of superregeneration. Loudness of this hiss should be fairly uniform as capacitor C3 is varied, but should increase somewhat as R2 is advanced to the top of its setting.
- 7—Connect antenna and ground. If connection of antenna stops hiss, adjust antenna trimmer capacitor C1 to restore this. This trimmer is screwdriver adjusted and should need adjustment only once to accommodate all frequency bands.
- 8—Tune-in signals in each band, noting the AGC action of the receiver and the nasal quality of its voice reproduction.
- 9—The receiver tuning dial, attached to C3, may be calibrated with the aid of an AM signal generator connected to the *antenna* and *ground* terminals. Connect high-impedance headphones or AF voltmeter to *AF output* terminals, and at each setting of the generator, tune C3 for audio peak. The top frequency in the 10-meter, 6-meter, and 27 MHz bands may be placed at the same point on the C3 dial by adjusting the screw slugs in the corresponding coils, with the signal generator set to the appropriate frequency and with C3 set to the desired point near minimum capacitance. The 2-meter coil, however, has no slug and must be adjusted by squeezing or spreading its turns for alignment with the top-band frequency.

Because of the high frequencies at which this receiver operates, particular care is needed in its construction. The shortest practicable straight leads must be used in the tuned circuit (L1-C1-C2-C3-R1), and the mounting of this part of the receiver must be firm and solid. Any subpanel employed in the tuning section should be made of polystyrene. Capacitors C2, C4, C5, and C6 are mica units, but C7 may be any convenient low-voltage unit. Fixed resistors R1, R3, and R4 are $\frac{1}{4}$ - or $\frac{1}{2}$ -watt composition or film units.

The user must remember that the superregenerative receiver is a notorious radiator of RF energy and can interfere with other nearby receivers tuned to the same frequency. The antenna coupling trimmer, C1, provides some attenuation of this radiation and so does reduction of the battery voltage to

the lowest value that will still afford good sensitivity and audio volume. A radio-frequency amplifier operated ahead of the superregenerator is a very effective medium for minimizing radiation; but at the frequencies at which the receiver operates, such an amplifier is not easily fabricated and it negates the simplicity of the superregenerator.

ELECTRONIC DC VOLTMETER

Figure 2-11 shows the circuit of a balanced electronic DC voltmeter having an input resistance (including the 1-megohm resistor in the shielded probe) of 11 megohms. The circuit draws approximately 1.3 mA from a self-contained 9-volt battery, B, hence can be left running for extended periods. This instrument covers 0–1000 volts in eight ranges: 0–0.5, 0–1, 0–5, 0–10, 0–50, 0–100, 0–500, and 0–1000 volts.


In the input voltage divider (range switching), the required resistances are made up of series-connected stock-value resistors which must be selected carefully for resistance close to the indicated values. If precision instrument-type resistors are available, the number of resistors in this string can be halved. That is, for R2 and R3, substitute 5 Meg.; for R4 and R5, 4 Meg.; for R6 and R7, 500 K; for R8 and R9, 400 K; for R10 and R11, 50 K; for R12 and R13, 40K; for R14 and R15, 5 K; and for R16 and R17, 5 K.

A balanced circuit such as this has virtually no zero drift; any drift in FET Q1 is balanced out automatically by a similar drift in Q2. The internal drain-to-source circuits of the FETs, in conjunction with resistors R20, R21, and R22, form a resistance bridge. Indicating microammeter M1 is the detector in this bridge circuit. With zero signal input to the electronic voltmeter, meter M1 is set to zero by balancing this bridge with the aid of potentiometer R21. When a DC voltage subsequently is applied to the input terminals, the bridge unbalances—since the internal drain-to-source resistance of the FETs changes—and the meter deflects proportionately. The RC filter formed by R18 and C1 removes AC hum and noise picked up by the probe and the voltage-switching circuits.

Initial Calibration

With zero voltage at the input terminals:

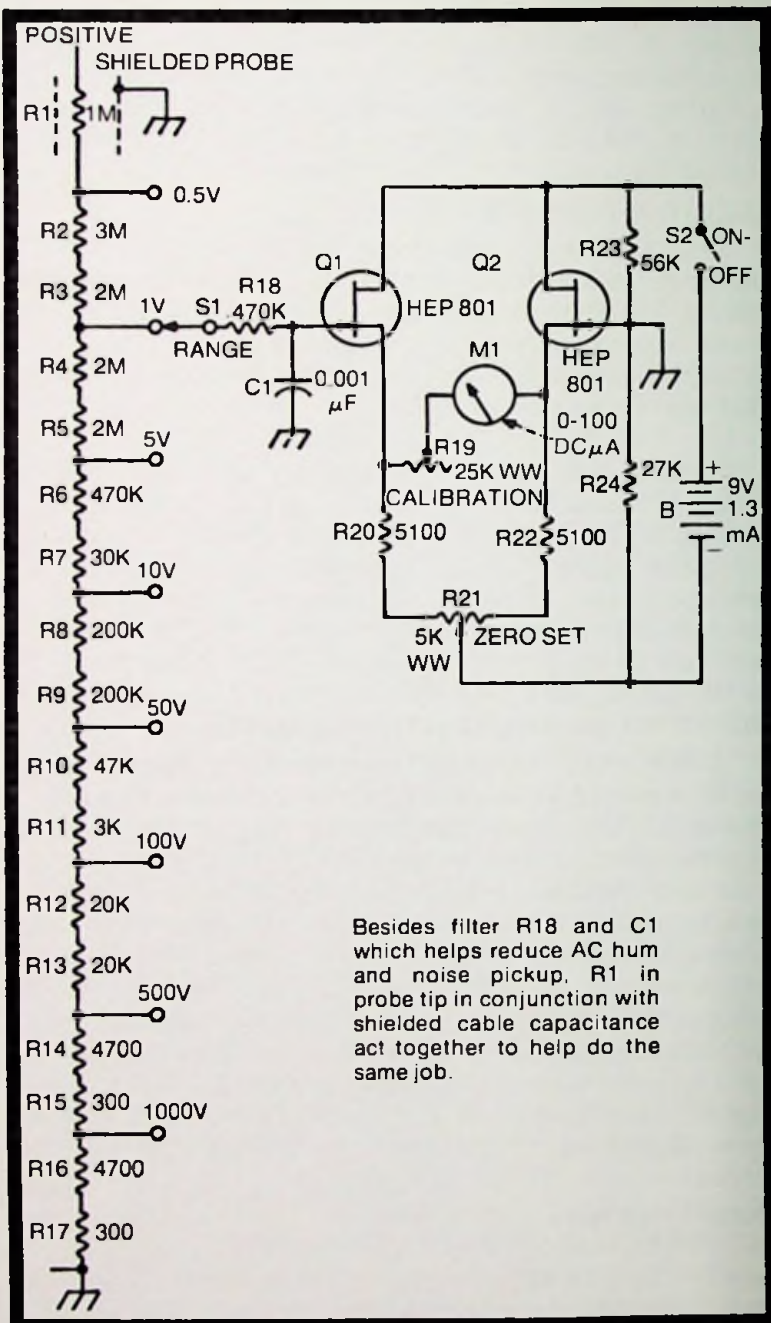- 1—Close switch S2 and set potentiometer R21 to zero pointer of meter M1. Range switch S1 may be set to any position for this step.



Besides filter R18 and C1 which helps reduce AC hum and noise pickup, R1 in probe tip in conjunction with shielded cable capacitance act together to help do the same job.

Fig. 2-11. Electronic DC voltmeter.

- 2—Set range switch to its 1-volt position.
- 3—Connect an accurately known 1-volt DC source to input terminals.
- 4—Adjust calibration control R19 for exact full-scale deflection of meter M1.
- 5—Temporarily remove input voltage and note if meter still is zeroed. If it is not, reset R21.
- 6—Work back and forth between steps 3, 4, and 5 until a 1-volt input deflects meter to full scale, and meter remains zeroed when input is removed.

Rheostat R19 will need no readjustment after this process unless its setting is disturbed or the instrument later needs recalibration. Zero-set potentiometer R21 will need only occasional resetting.

If range resistors R2 to R17 are accurate, this single-range calibration will be sufficient; all other ranges will automatically be in calibration. A special voltage card can be drawn for the meter, or the existing 0–100 μA scale may be read in volts by mentally applying the appropriate multiplier on all but the 0–100 volt range.

DIRECT-READING CAPACITANCE METER

Quick, direct reading of capacitance is afforded by the circuit shown in Fig. 2-12. This instrument covers 0–0.1 μF in four ranges: 0–200 μF , 0–1000 μF , 0–0.01 μF , and 0–0.1 μF . Operation of the circuit is linear, so the scale of the 0–50 DC microammeter, M1, can be graduated in picofarads and microfarads. An unknown capacitance connected to terminals X-X then may be read directly from the meter, without calculations or balancing adjustments. The circuit draws approximately 0.2 mA from a self-contained 18-volt battery, B.

In this circuit, the two FETs (Q and Q2) are operated in a conventional drain-coupled multivibrator. The multivibrator output, taken from the drain of Q2, is a constant-amplitude square wave whose frequency is determined principally by the values of capacitors C1 to C8 and resistors R2 to R7. On each test range, the selected capacitances are identical and so are the selected resistances. A 6-pole, 4-position, rotary switch (S1-S2-S3-S4-S5-S6) selects the correct multivibrator capacitors and resistors and the meter-circuit resistance combination required for the test frequency for a selected

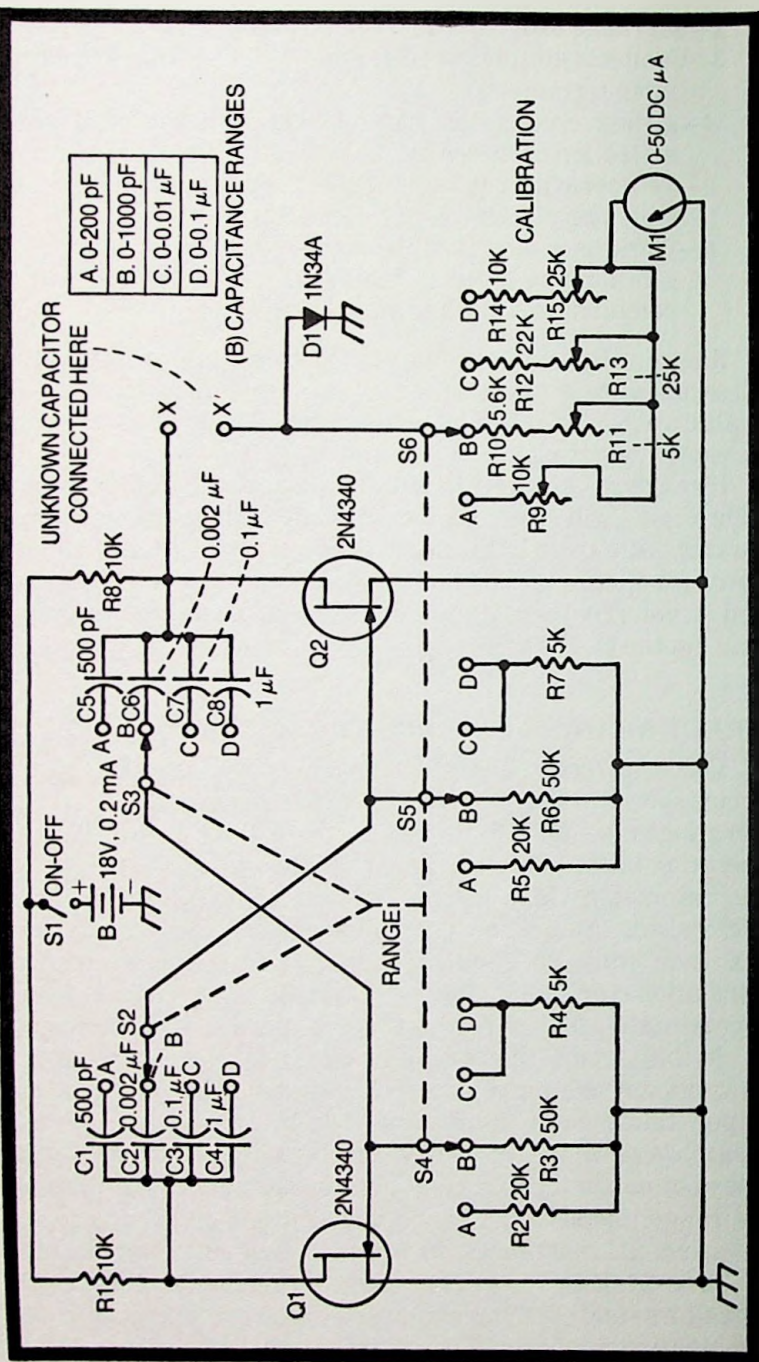


Fig. 2-12. Direct-reading capacitance meter.

capacitance range. The square-wave output is coupled through the unknown capacitor (connected to terminals X-X) to the meter circuit (diode D1, one of the resistance legs selected by switch section S6, and 0–50 DC microammeter M1). No zero setting of the meter is needed; the pointer remains at zero until an unknown capacitor is connected to terminals X-X.

For a given square-wave frequency, the meter deflection is directly proportional to unknown capacitance C, and the meter response is linear. Thus, if in the initial calibration of the circuit an accurately known 1000 pF capacitor is connected to terminals X-X, the range switch is set to its position B, and calibration rheostat R11 is set for exact full-scale deflection of M1, then the meter will indicate 1000 pF at full scale. Owing to its linear response, the meter will indicate 500 pF at half scale, 100 pF at 1/10 scale, and so on.

The multivibrator frequency is switched to the following values for the four capacitance ranges: 50 kHz (0–200 pF), 5 kHz (0–1000 pF), 1000 Hz (0–0.01 μ F), and 100 Hz (0–0.1 μ F). For this purpose, switch sections S2 and S3 switch the multivibrator capacitors in identical pairs at the same time that switch sections S4 and S5 switch the multivibrator resistors in identical pairs.

The frequency-determining capacitors must be capacitance-matched in pairs: C1 = C5, C2 = C6, C3 = C7, and C4 = C8. Likewise, the frequency-determining resistors must be resistance-matched in pairs: R2 = R5, R3 = R6, and R4 = R7. The drain load resistors, R1 and R8, also should be matched. The calibration rheostats—R9, R11, R13, and R15—must be wirewound units; and since they are adjusted only during calibration, they may be mounted inside the instrument case and provided with slotted shafts for screwdriver adjustment. All fixed resistors (R1 to R8, R10, R12, R14) must be 1-watt units.

Initial Calibration

For calibration, four accurately known, very-low-leakage capacitors will be required: 0.1 μ F, 0.01 μ F, 1000 pF, and 200 pF.

- 1—With the range switch in its position D, connect the 0.1 μ F capacitor to terminals X-X.
- 2—Close switch S1.

- 3—Adjust calibration rheostat R15 for exact full-scale deflection of meter M1.
- 4—Open switch S1.
- 5—Connect the 0.01 μF capacitor to terminals X-X in place of the 0.1 μF unit.
- 6—Set the range switch to Position C.
- 7—Close switch S1.
- 8—Adjust calibration rheostat R13 for exact full-scale deflection of the meter.
- 9—Open switch S1.
- 10—Connect the 1000 pF capacitor in place of the 0.01 μF unit.
- 11—Set the range switch to position B.
- 12—Close switch S1.
- 13—Adjust calibration rheostat R11 for exact full-scale deflection of the meter.
- 14—Open switch S1.
- 15—Connect the 200 pF capacitor in place of the 1000 pF unit, using the shortest and straightest leads practicable.
- 16—Set the range switch to position A.
- 17—Close switch S1.
- 18—Adjust calibration rheostat R9 for exact full-scale deflection of the meter.
- 19—Open switch S1.
- 20—Disconnect the 200-pF capacitor from terminals X-X.

A special meter card may be drawn, or figures may be inscribed on the present microammeter scale to show capacitance ranges of 0–200 pF, 0–1000 pF, 0–0.01 μF , and 0–0.1 μF . In subsequent use of the instrument, it will be necessary only to connect an unknown capacitor to terminals X-X, close switch S1, and read the capacitance from the meter. For best accuracy, use the range that will give the deflection in the upper part of the meter scale.

3

Metal Oxide Semiconductor Field-Effect Transistor MOSFET

The *metal oxide semiconductor field-effect transistor* (MOSFET) is a special type of field-effect transistor in which the gate electrode is not the junction found in the conventional field-effect transistor (see Chapter 2), but is a small metal plate insulated from the rest of the structure by a thin film of silicon dioxide. Any gate current in this device therefore is the leakage current of this insulation, and is as low as 10 picoamperes (10^{-11} ampere) in some models. This gate gives the MOSFET extremely high input resistance, superior to that of the FET. This feature of the MOSFET is responsible for the alternate name of the device: *insulated-gate field-effect transistor* (IGFET).

MOSFETs are now available, as discrete units, in a wide variety of ratings and types. Before working with MOSFETs, read the hints and precautions in Chapter 1, especially items 3, 10, and 19.

MOSFET THEORY

Figure 3-1(A) shows the cross section of a MOSFET. Although this representation may not be the exact picture of a particular manufactured unit, it is functionally correct and will serve to illustrate the main differences between MOSFETs and conventional junction FETs. (The various regions shown in the substrate are not to scale.) The

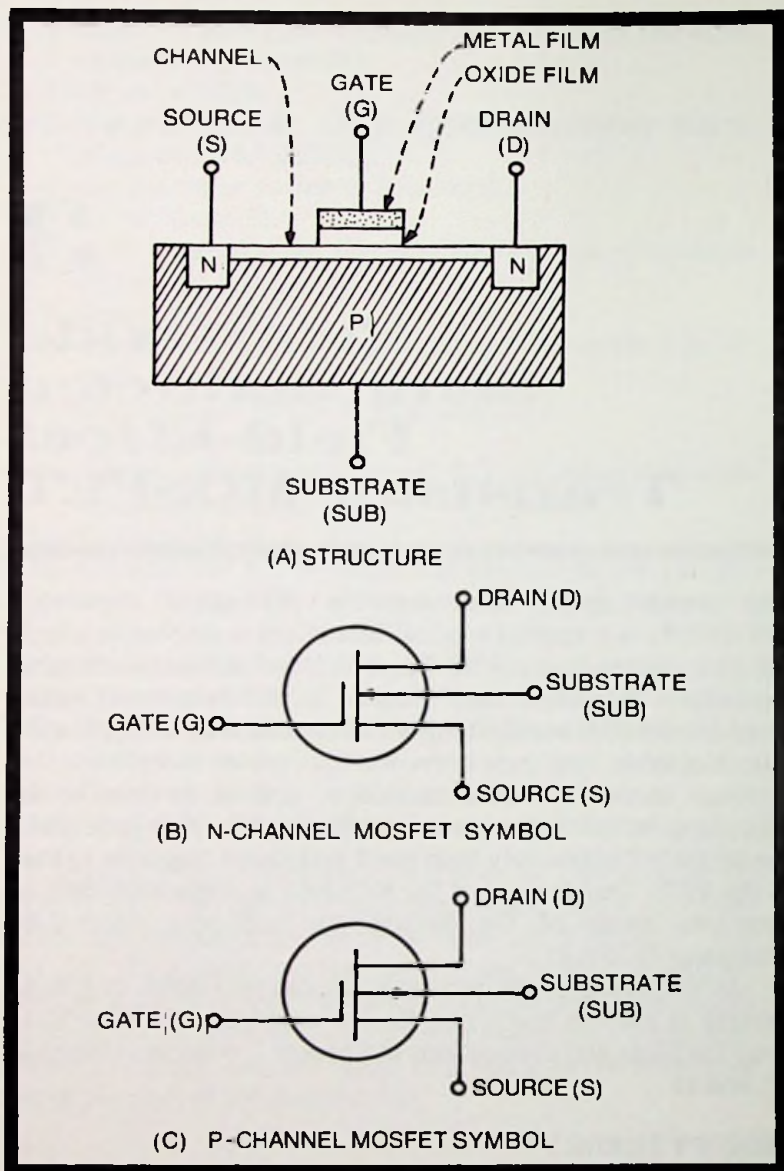


Fig. 3-1. Details of MOS field-effect transistor.

electrodes of the MOSFET are *drain*, D (corresponding to the plate of a tube or the collector of a bipolar transistor), *source*, S (corresponding to the cathode of a tube or the emitter of a bipolar transistor), and *gate*, G (corresponding to the grid of a

tube or the base of a bipolar transistor). The drain and source consist of small N-regions processed into a P-type substrate. Connecting the drain and source is a thin N-type *channel* lying just under the top face of the substrate. The metal gate electrode rests on the channel and is insulated from it by a very thin film of silicon dioxide (the insulating film is grown on the substrate, and the gate is deposited on the film).

This particular type of device is termed an N-channel MOSFET, and its circuit symbol is shown in Fig. 3-1(B). If, instead of this structure, we have an N-type substrate, the drain, source, and channel are P type. The resulting device is termed a P-channel MOSFET, and its circuit symbol is shown in Fig. 3-1(C). For the N-channel MOSFET, the external DC voltages are: drain positive, source negative. For the P-channel MOSFET, the voltages are: drain negative, source positive.

Figure 3-2 illustrates MOSFET operation. Here, a DC supply (V_{DD}) provides an operating voltage (V_{DS}) between drain and source, with drain positive and source negative; and a second DC supply (V_{GG}) provides a bias voltage (V_{GS}), with gate negative and source positive. The electric field of the gate penetrates the channel. Note that a gate-to-source resistor, R , is needed, since the gate insulation might be damaged if the gate floats.

In Fig. 3-2(A), the gate voltage is zero; and under this condition, a maximum value of drain current (I_D) flows from supply V_{DD} through the channel, and back to V_{DD} , since there is no field from the gate to affect current flowing through the channel. In Fig. 3-2(B), the gate voltage is negative; and the resulting field narrows the channel, reducing drain current I_D . When the gate voltage is raised to a sufficiently high negative value, the channel is depleted completely and the drain current is cut off.

Between these limits of maximum and cutoff, the drain current may be set to any intermediate value by appropriately setting the gate voltage. Figure 3-2(C) shows MOSFET performance in a family of curves resembling those for a pentode tube. An N-channel MOSFET is shown in Fig. 3-2; for a P-channel MOSFET, reverse the polarity of V_{DD} and V_{GG} .

Because the gate voltage acts to deplete the channel of current carriers, this type of MOSFET is termed *depletion type*. Other types are *enhancement type* and

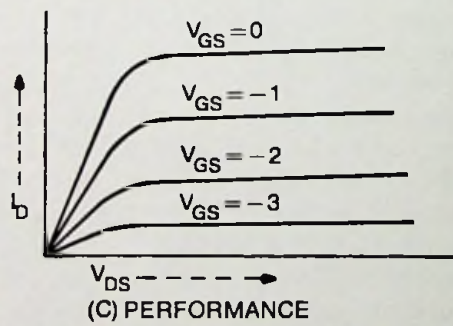
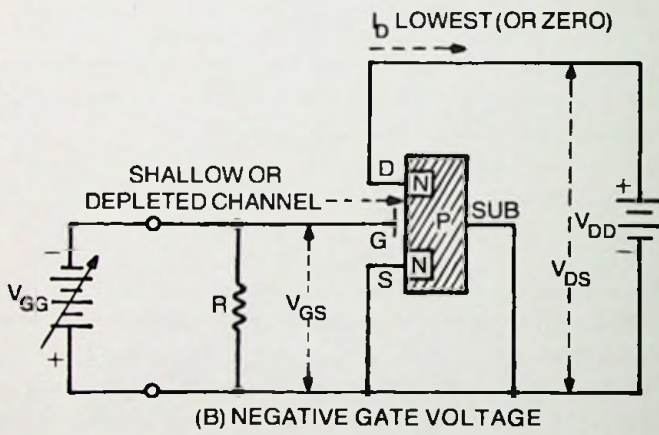
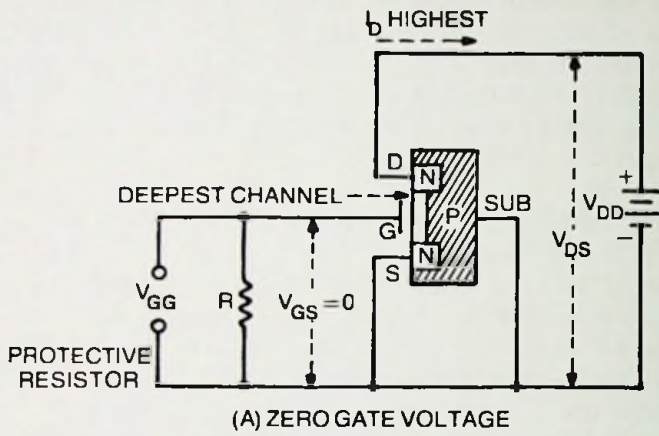


Fig. 3-2. MOSFET action.

depletion/enhancement type, but are not described here because all units mentioned in this chapter are of the depletion type.

Because the drain current of the MOSFET is controlled by gate *voltage*, the MOSFET possesses transconductance (up to 15,000 μ mhos typical) and is a good amplifier. It also, like the tube and superior to the junction FET, has a very high input resistance (in some devices, up to 100 million megohms). Depending upon make and model, MOSFETs operate at frequencies up to 500 MHz.

In addition to the single-gate MOSFET shown in Fig. 3-1 and 3-2, there are dual-gate units (see Fig. 3-3A). Also available is the *gate-protected* MOSFET (see Fig. 3-3B); in this type, internal, integrated back-to-back zener diodes (D1, D2, D3, D4) automatically protect the two gates from insulation damage resulting from static electric or excessive signal voltages. Single-gate, dual-gate, and gate-protected MOSFETs all are used in projects in this chapter.

GENERAL PURPOSE RF AMPLIFIER

Outrigger RF amplifiers are convenient as preselectors for boosting the sensitivity and selectivity of receivers. They also find use as signal boosters in electronic equipment other than receivers. The circuit shown in Fig. 3-4 may be used as an outrigger amplifier or as an RF amplifier stage which is built into an existing receiver or instrument. The circuit employs a

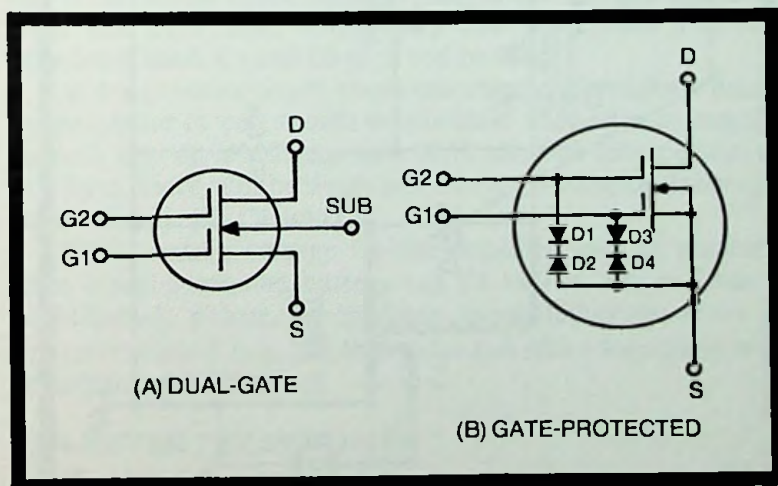


Fig. 3-3. Special MOSFETs

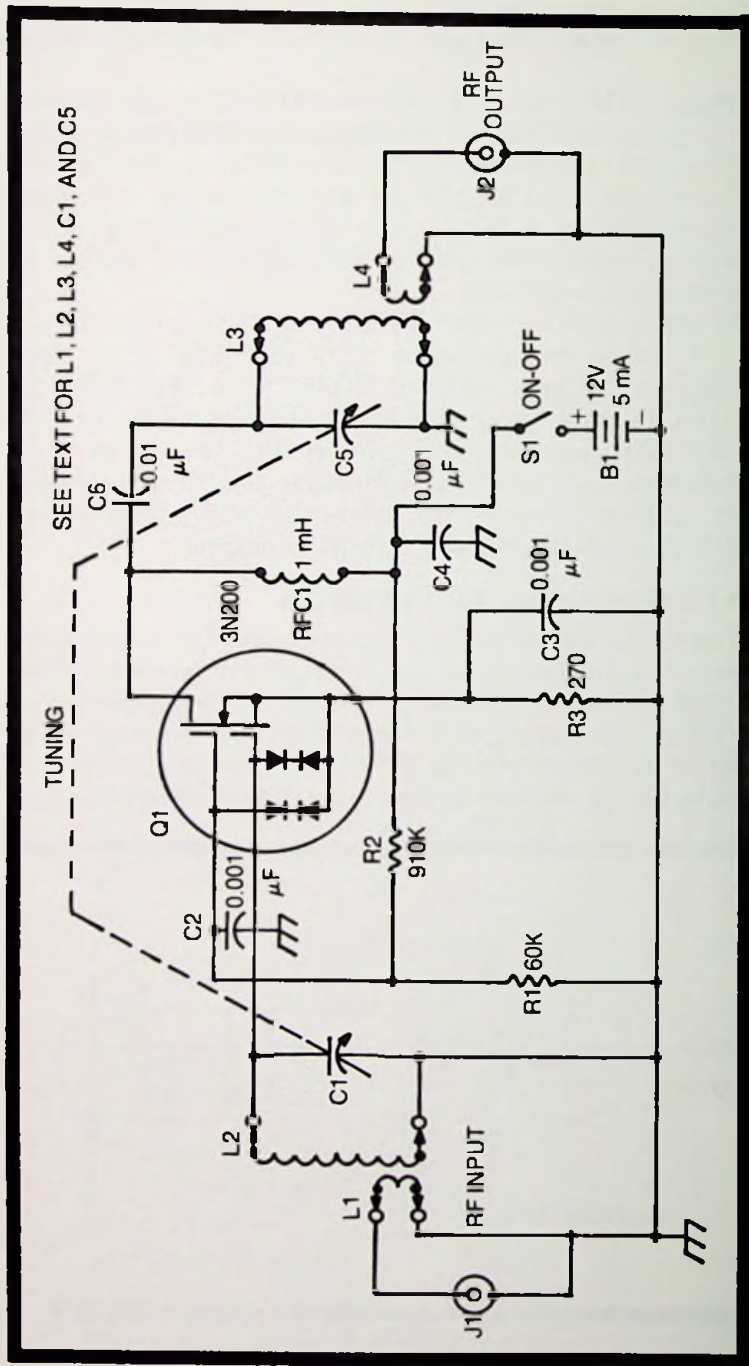


Fig. 3-4. General-purpose RF amplifier.

3N200 gate-protected MOSFET, a device which is operable to 400 MHz.

This is a standard tuned-gate, tuned-drain circuit; but, because of the low interelectrode capacitance of the 3N200, no neutralization is required. In this circuit, the incoming RF signal, selected by the input tuned circuit (L1-L2-C1) is presented to gate 1 of the MOSFET. The output signal is developed by drain current in the output tuned circuit (L3-L4-C5). Coaxial jacks (J1 and J2) or other suitable terminals permit easy input and output of the signal. The negative gate-1 bias is provided by the voltage drop resulting from the flow of drain current through source resistor R3. Required positive gate-2 bias is produced by voltage divider R1-R2. With an individual MOSFET, resistor R2 may require some adjustment for maximum amplification.

Commercial plug-in coil sets with end links may be used when the amplifier must cover a wide tuning range. The per-section capacitance of the ganged tuning capacitor, C1-C5, then will be the value recommended by the coil manufacturer for the selected coils. When the amplifier is to be used exclusively in the standard broadcast band, L2 and L3 each must be 130 turns of No. 32 enameled wire closewound on a 1-inch diameter form. L1 will be 10 turns of No. 32 enameled wire closewound around the bottom end of L2, and L4 will be 12 turns of No. 32 enameled wire closewound around the bottom end of L3. These link-coupling coils (L1 and L4) are insulated from the coils with which they are associated. For the broadcast band, C1 and C5 each will be 365 pF.

At frequencies much above the standard broadcast band, the amplifier circuit should be shielded. The unit may readily be built into an aluminum box. With shielded construction of this kind, there will be some advantage in using feed through capacitors for C2, C3, and C4.

DC operating voltage for the amplifier may be obtained from a self-contained battery (as B1 in Fig. 3-4) or from a well-filtered, power-line-operated supply. Current drain is approximately 5 mA, but this value can differ somewhat with an individual 3N200.

TEN-METER PREAMPLIFIER

Figure 3-5 shows the circuit of a preamplifier (preselector) expressly for the 10-meter ham band. Employing

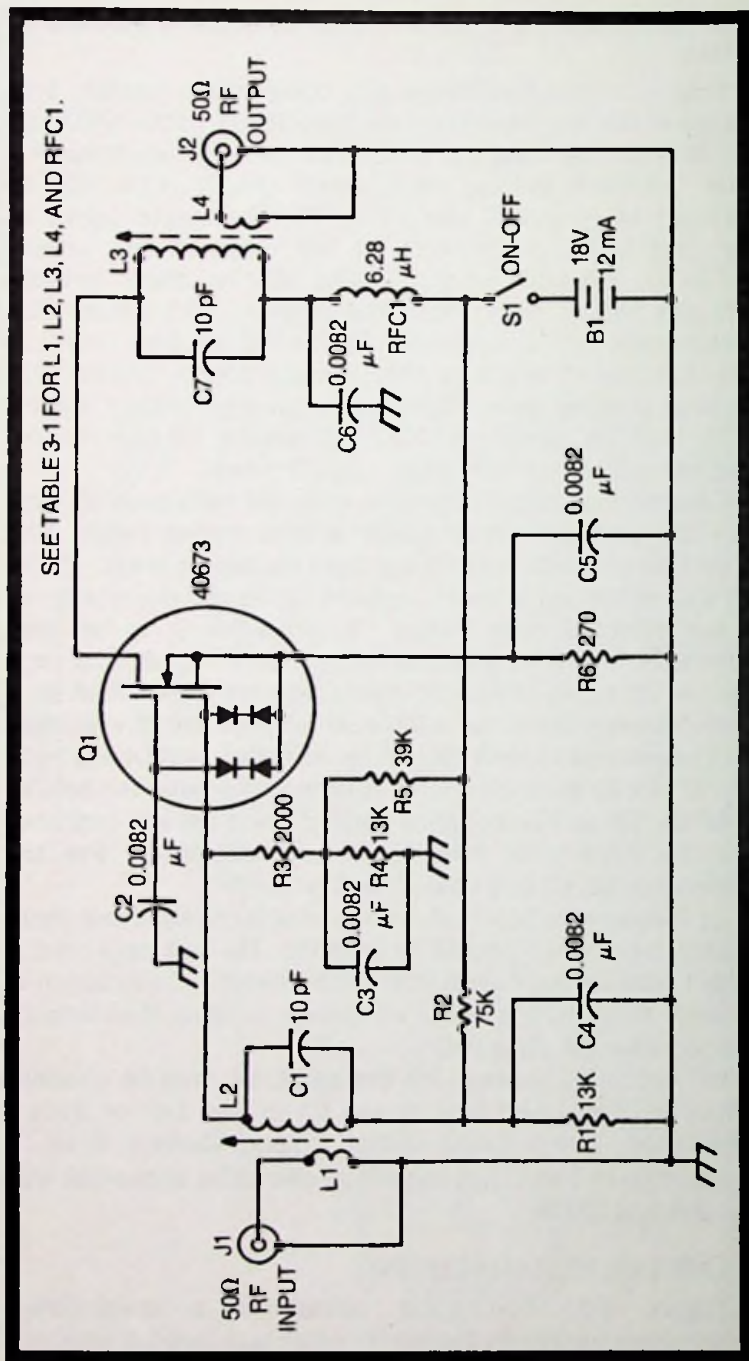


Fig. 3-5. Ten-meter preamplifier.

permeability input and output tuning, this circuit is adapted from an original RCA design. Operation of the circuit is reasonably wide band, especially if input and output are stagger tuned, so that it can function as an aperiodic amplifier. Table 3-1 gives coil data.

A gate-protected 40673 MOSFET is used with dual bias to provide substantial signal boost. The DC bias on the signal gate (gate 1) is the combination of the negative voltage developed by the flow of drain current through source resistor R6 and the positive voltage developed by voltage divider R1-R2 (the net voltage at gate 1 is negative). The required positive voltage on gate 2 is developed by voltage divider R4-R5. With an individual MOSFET, resistors R2 and R5 may require some adjustment for maximum signal output.

The circuit is fix-tuned by means of the slug-adjusted coils, L2 and L3 (see Table 3-1). While, owing to the very low interelectrode capacitance of the 40673, no neutralization is required, the mechanical assembly must be arranged to keep the input and output coils well separated and preferably at right angles to each other. A very small amount of coupling between input and output will induce oscillation.

The input and output accommodate low antenna and receiver-input impedance. For a high-impedance antenna, connect the antenna to the top of L2 through a 10 pF capacitor. Impedances other than 50 ohms may be accommodated by suitably changing the number of turns in L1 or L2.

All capacitors are silvered mica. All resistors are 1/2-watt. The circuit draws approximately 12 mA from the 12-volt DC supply which may be either battery (as B1 in Fig. 3-5) or a well-filtered power-line-operated supply.

The circuit may be aligned in the conventional manner, with a signal generator (tunable between the 28- and 29.7-MHz limits of the 10-meter band) connected to input jack J1, and a suitable indicator (such as an electronic RF voltmeter or the

Table 3-1. Coil Data For 10-M Preampifier

L1	2 turns No. 20 enameled wire closewound around ground end of L2.
L2 and L3	Each subminiature, slug-tuned, ceramic-form coil. Inductance range 1.6 to 2.4 μ H (J. W. Miller No. 4306)
L4	2 turns No. 20 enameled wire closewound around ground (bottom) end of L3.
REC1	6.28 μ H microminiature RF choke, DC resistance 2 ohms (J. W. Miller No. 9230-40).

receiver itself into which the preamplifier is to operate) connected to output jack J2. Adjust the L2 and L3 slugs first for peak output at 28.8 MHz (approximate midband); then detune both input and output coils, one above this frequency and one below, for the desired bandwidth.

Also usable in this circuit are MOSFET types 3N187 and 3N200.

WIDEBAND INSTRUMENT AMPLIFIER

A video amplifier, such as shown in Fig. 3-6, exhibits wideband response, by operating from low audio frequencies well into the high radio frequencies. Such amplifiers are widely used in electronics, and are known mainly for their role in TV picture channels, oscilloscope horizontal and vertical channels, and sampling systems. The circuit in Fig. 3-6 is offered, however, especially as an instrument amplifier; that is, as a signal booster for oscilloscopes, electronic voltmeters, and other test instruments requiring an amplifier that needs no tuning. The MOSFET is a 40820, having high transconductance (12,000 μ mhos typical).

Frequency response of this circuit extends from 60 Hz to 10 MHz. The input impedance is approximately 1 Meg., determined principally by the resistance of the input resistor, R1. Output impedance is approximately 2800 ohms. These input and output values hold at 1000 Hz. The open-circuit voltage gain of the circuit is approximately 10 at 1000 Hz, and is down approximately 3 dB at 60 Hz and down approximately 6 dB at 10 MHz. The maximum input-signal voltage before output-signal peak clipping is approximately 100 mV rms, and the corresponding maximum output-signal voltage is approximately 1 volt rms.

The peaking elements are trimmer capacitor C3 (55–300 pF) and slug-tuned inductor L1 (24–35 μ H, J. W. Miller No. 4508 or equivalent). Both of these components are adjusted carefully for maximum gain of the amplifier at 10 MHz. Successful high-frequency performance of the circuit demands that all wiring be short, rigid, and direct, and that leads be dressed for optimum performance and minimum cross coupling.

In this circuit, the MOSFET receives its negative gate-1 bias from the voltage drop resulting from the flow of drain current through source resistors R4 and R5 in series, and its

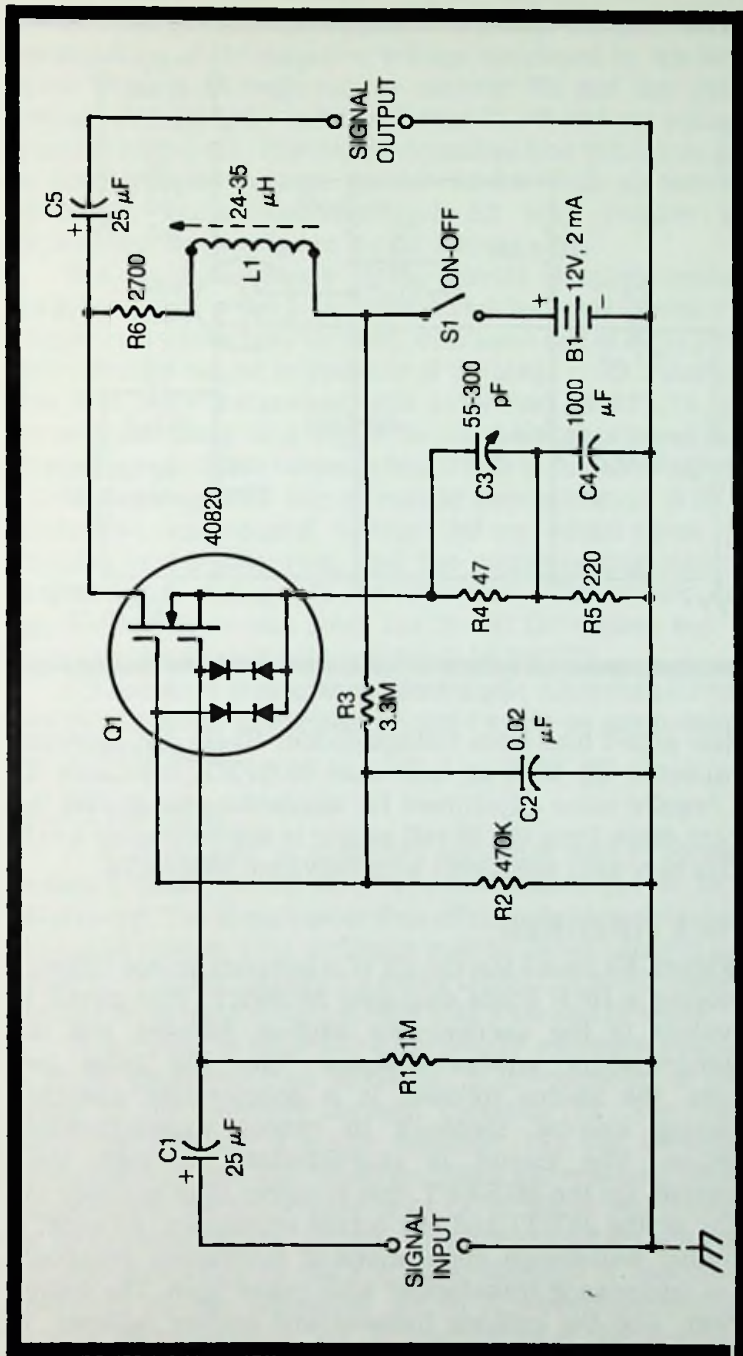


Fig. 3-6. Wide-band instrument amplifier.

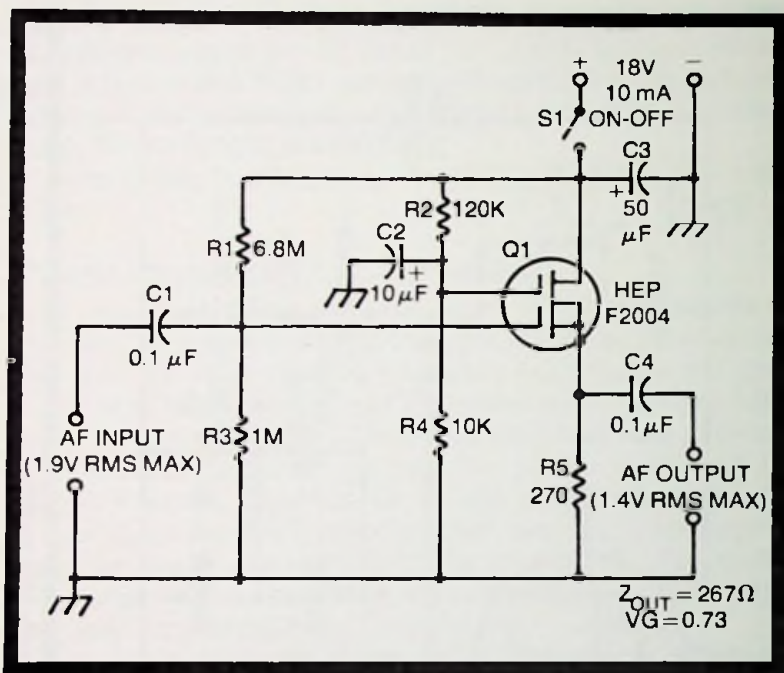


Fig. 3-7. Source follower.

positive gate-2 bias from voltage divider R2-R3, RF-bypassed by capacitor C2. With an individual MOSFET, resistance R3 may require some adjustment for maximum gain at 1000 Hz. Current drain from the 12-volt supply is approximately 2 mA, but this may vary somewhat with individual MOSFETs.

SOURCE FOLLOWER

Figure 3-7 shows the circuit of a compact source follower employing a HEP F2004 dual-gate MOSFET. This circuit is equivalent to the vacuum-tube cathode follower and the bipolar-transistor emitter follower. Like the latter two circuits, the source follower is a degenerative amplifier employing current feedback to cancel stage-introduced distortion. The circuit is characterized by high input impedance (in the MOSFET, this is higher than in either the bipolar or the JFET) and low output impedance. As such, it has many well-known applications in electronics, especially that of impedance transformer with power gain. The source follower, like the cathode follower and emitter follower, is noted also for its wide frequency response and low distortion.

In this circuit, the negative DC bias on gate 1 is the combination of the negative voltage developed by the flow of drain current through source resistor R5 and the positive voltage developed by voltage divider R1-R3 (the net voltage at gate 1 is negative). The required positive bias voltage on gate 2 is developed by voltage divider R2-R4. With an individual MOSFET, resistances R1 and R2 may require some adjustment for maximum signal output.

The input resistance of the circuit is approximately 1 megohm, and is largely determined by input resistor R1. Higher resistance may be used, with some risk of stray pickup. The effective output impedance of the stage is 267.2 ohms; but this will vary somewhat with individual MOSFETs, since transconductance is a factor in the determination of output impedance, and this varies in MOSFETs of the same type.

Voltage gain of the circuit is approximately 0.73. The maximum input-signal voltage before output-signal peak clipping is 1.9-volts rms, and the corresponding maximum output-signal voltage is 1.4-volts rms. The circuit draws approximately 10 mA from the 18-volt DC source, but this may vary somewhat with individual MOSFETs.

All resistors are 1/2-watt. Electrolytic capacitors C2 and C3 are 25-volt units; capacitors C1 and C4 may be any convenient low-voltage units..

Q MULTIPLIER

A Q multiplier is a special oscillator that is connected across a tuned circuit in a receiver to increase the latter's selectivity. The Q multiplier thus effectively increases the Q of the tuned circuit. This oscillator may be added either to an RF stage or IF stage. Figure 3-8 shows the circuit of a Q multiplier which can be used in conjunction with a 455 kHz IF stage.

This circuit is basically a Colpitts IF oscillator employing a 3N187 gate-protected MOSFET; it is connected to the IF stage in the receiver through capacitor C2. The Colpitts oscillator employs a single inductor (L1) and split tuning capacitor (C5 and C6) in series. With the resulting 0.005 μ F capacitance, the inductance of L1 (J. W. Miller No. 21A224RBI or equivalent) can be set, by means of the tuning slug, to 244 μ H for oscillation at 455 kHz. The strength of oscillation is governed by the setting of the 25 K wirewound *oscillation control* potentiometer, R4. At one setting of this control, the

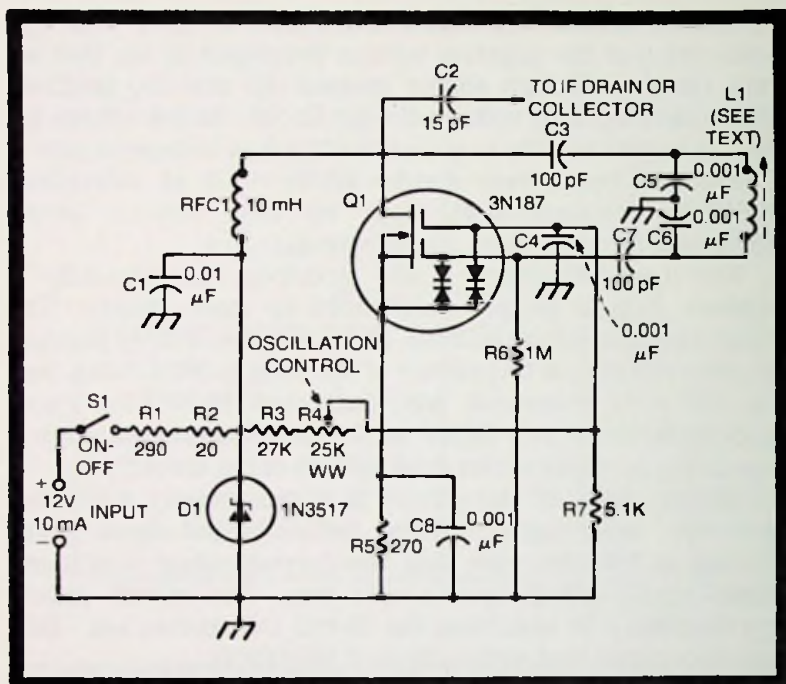


Fig. 3-8. Q multiplier (455 kHz IF).

signal in the receiver is caused to peak sharply; at another setting of R4, a slot is created, and the signal is eliminated.

In this circuit, gate 1 of the MOSFET receives its negative bias as the voltage developed by the flow of drain current through source resistor R5. Gate 2 receives its positive bias from voltage divider R3-R4-R7. The DC voltage presented to the circuit is regulated by a 1N3517 zener diode in conjunction with resistors R1 and R2 at the constant value of 9.1 volts. (See Chapter 8 for treatment of zener diodes.) When fully oscillating, the circuit draws approximately 10 mA from the 12-volt DC supply.

RF output from the circuit is coupled to the drain or collector of the IF stage in the receiver through 15 pF capacitor C2. All wiring within the Q multiplier and in the receiver to which it is connected must be as short and direct as possible. If the Q multiplier is an external unit, it must be enclosed in a metal shield box inside which all grounds must be returned to a single point. The Q-multiplier ground must be the same as the receiver ground. For stability, all capacitors in

the Q multiplier must be silvered mica, and all resistors should be 1-watt.

Also usable in this circuit is the 40820 MOSFET.

WIDE-RANGE LC CHECKER

Figure 3-9 shows an inductance-capacitance checker circuit employing a HEP F2005 MOSFET. This circuit allows a variable-frequency audio generator (tuning from 20 Hz to 20 kHz) to be used to measure inductance from 6.3 mH to 6329 H and capacitance from 0.0632 μF to 63,291 μF . Other capacitance ranges may be obtained by changing the value of inductance L1, and other ranges of inductance may be obtained by changing the value of capacitance C2.

The MOSFET is connected in a source follower circuit which drives a series-resonant circuit containing the unknown capacitance connected in series with a known inductance, L1, or the unknown inductance connected in series with a known capacitance, C2. The generator is tuned for peak deflection of meter M1, which is part of an AC milliammeter circuit connected in the series-resonant circuit. At that point, the generator frequency is noted, and the unknown component calculated in terms of the known values. Thus,

$$C_x = 1/(39.5 f^2 L^1)$$

and

$$L_x = 1/(39.5 f^2 C^2).$$

The unknown component is connected to terminals X-X. Resonant current flowing through 100-ohm resistor R3 develops a voltage drop across this resistor, and this voltage is rectified by diode D to deflect meter M1. The standard inductor (L1) is a 1 mH, slug-tuned coil (J. W. Miller No. 22A103RBI or equivalent) which may be set exactly to 1 mH with the aid of an inductance bridge. Standard capacitor C2 is a 0.01 μF silvered-mica unit which must be obtained with the highest accuracy possible.

Capacitance Measurement

To use the instrument for determining capacitance values, follow this procedure:

- 1—Connect the signal generator to the AF input terminals.

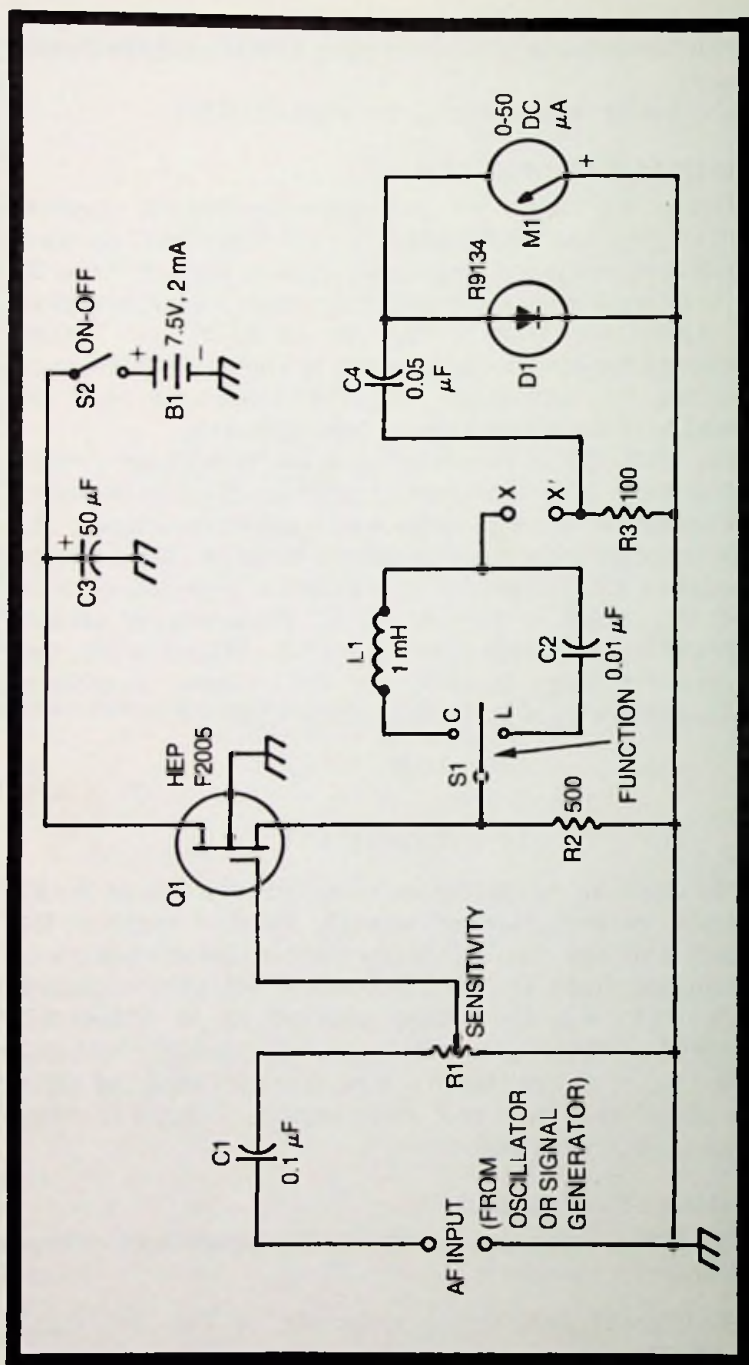


Fig. 3-9. Wide-range LC checker.

- 2—Connect the unknown capacitor to terminals X—X.
- 3—Set switch S1 to C.
- 4—Close switch S2 and turn on generator.
- 5—Tune generator throughout its range, watching for a peak deflection of meter M1.
- 6—At peak, read frequency from generator dial.
- 7—Calculate the capacitance: $C = 1/(0.0395 f^2)$, where C is a farads and f in hertz. Note that the formula is simplified, since the inductance of L1 is constant.

Inductance Measurement

To use the instrument for determining inductance values, follow this procedure:

- 1—Connect the signal generator to the *AF input* terminals.
- 2—Connect the unknown inductor to terminals X—X.
- 3—Set switch S1 to L.
- 4—Close switch S2 and turn on generator.
- 5—Tune generator throughout its range, watching for a peak deflection of meter M1.
- 6—At peak, read frequency f from generator dial.
- 7—Calculate the inductance: $L = 1/(3.95 f^2 \times 10^{-7})$, where L is in henrys and f in hertz. Note that the formula is simplified, since the capacitance of C2 is constant.

In this circuit, the MOSFET receives its negative gate bias from the voltage drop resulting from the flow of drain current through source resistor R2. The *sensitivity control* potentiometer, R1, is set for best deflection of meter M1. Electrolytic capacitor C3 is a 25-volt unit. C2 is silvered mica, and C1 and C4 may be any convenient low-voltage units. For best stability, resistors R2 and R3 should be 1-watt.

The circuit draws approximately 2 mA from the 7.5-volt DC supply, but this current may vary somewhat with individual MOSFETs.

INTERVAL TIMER

Figure 3-10 shows the circuit of a conventional interval timer in which the very high input resistance of the 3N142 MOSFET affords performance comparable to that of the usual vacuum-tube timer. Because of the smallness of the MOSFET,

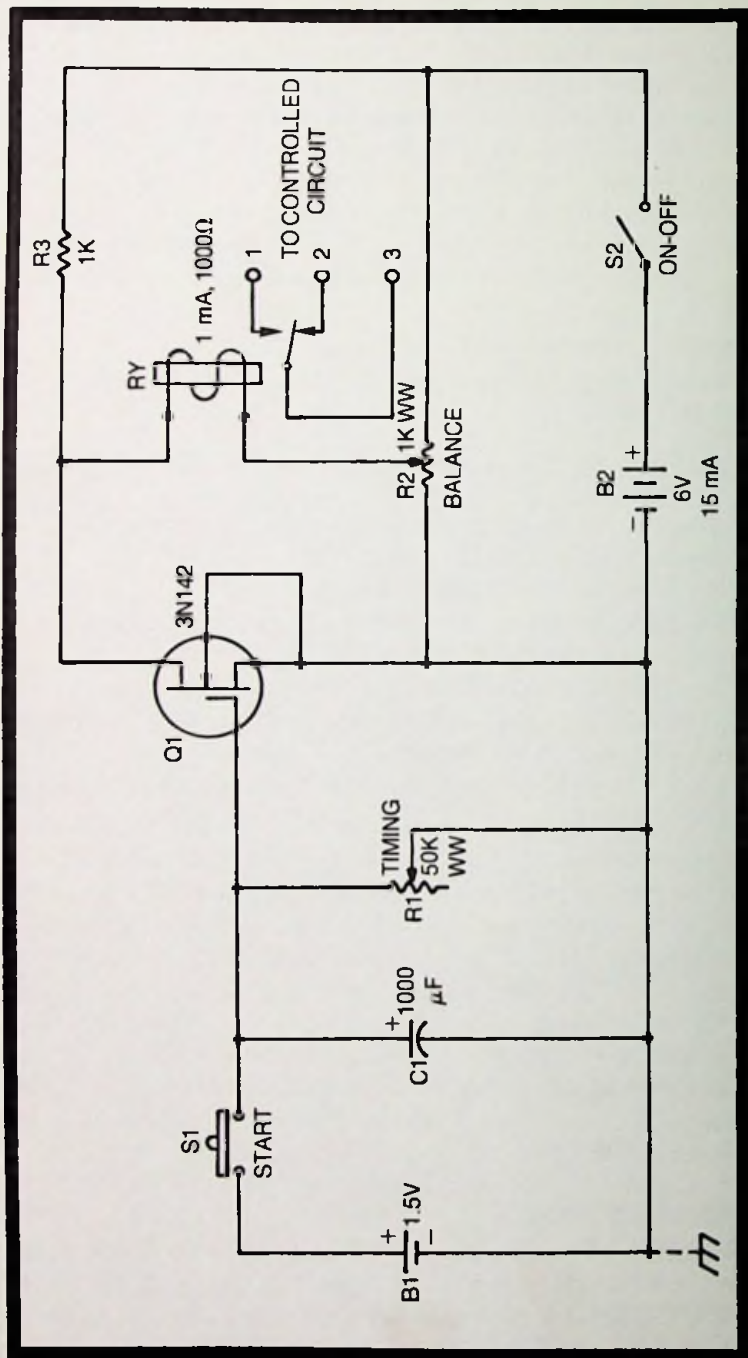


Fig. 3-10. Interval timer.

the relay, the 1000 μF (3V) capacitor, and other components, the entire unit can be very small and compact.

In this arrangement, the single-gate, 3N42 MOSFET serves as a simple DC amplifier driving relay RY in its drain output circuit. When pushbutton switch S1 is depressed momentarily, capacitor C1 is charged from 1.5-volt cell B1. At the same time, relay RY closes. When S1 then is released, capacitor C1 discharges at a rate determined by capacitance C1 and the resistance setting of R1 (the time interval before the relay drops out is closely equal to the time constant of the circuit where $t = R1C1$ seconds).

The time instant at which the relay drops out may be controlled by proper setting of rheostat R1. With the 50,000-ohm rheostat and 1000 μF capacitor shown, the maximum time interval is 50 seconds. Other maximum values may be obtained by appropriate selection of C1 and R1 values in accordance with the time-constant formula.

The relay is a 1 mA, 100-ohm device (Sigma 5F-1000 or equivalent) operated in a four-arm bridge in the drain circuit of the MOSFET. The bridge—consisting of resistor R3, the two “halves” of *balance control* potentiometer R2, and the internal drain-to-source resistance of the MOSFET—allows the static drain current to be balanced out of the relay (by adjustment of potentiometer R2) before the timer is ready to operate.

When the relay is closed, current drawn from the 6-volt DC supply is approximately 15 mA, but this may vary somewhat with individual MOSFETs. Controls R1 and R2 both are wirewound. Resistor R3 is $\frac{1}{2}$ -watt. The 1.5-volt cell, B1, is used only intermittently, to supply charging current to capacitor C1, and should enjoy long life, especially if a size-D cell is used.

CAPACITANCE RELAY

Capacitance relays are found in a number of electronic systems. They are found also in nonelectronic areas, where they serve as object- or people-counters, intrusion alarms, proximity detectors, safety switches, crowd stoppers in exhibitions and displays, and so on. A solid-state capacitance relay is both small and fast-acting.

Figure 3-11 shows the circuit of a capacitance relay employing a 3N128 MOSFET in the sensitive RF oscillator stage and a 2N2716 silicon bipolar transistor in the high-gain DC relay-amplifier stage. In this arrangement, MOSFET Q1

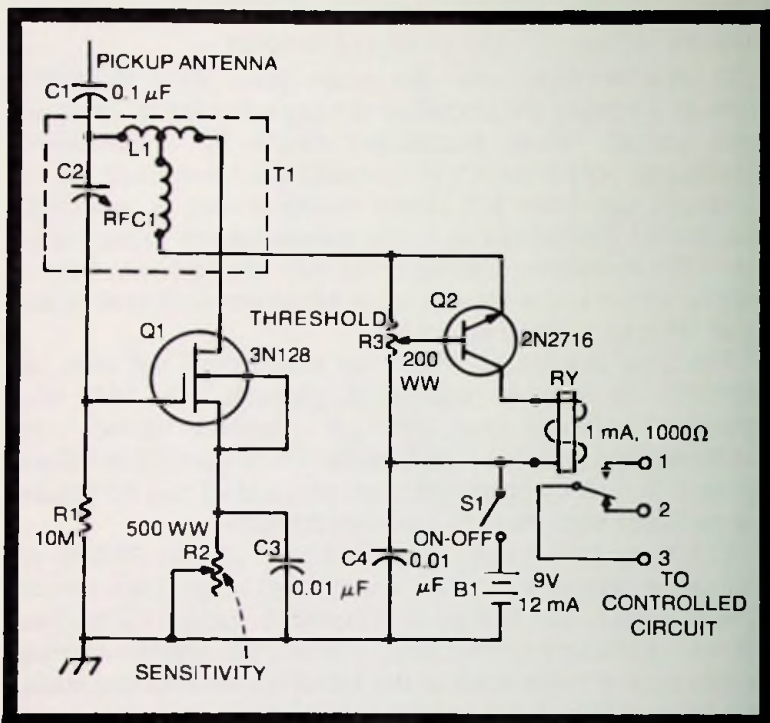


Fig. 3-11. Capacitance relay.

operates as an oscillator in conjunction with inductor L1, trimmer capacitor C2, and radio-frequency choke RFC1 (the inductor, trimmer, and RF choke are self-contained in a commercial *capacitance relay coil*, J. W. Miller No. 695 or equivalent). The MOSFET stage oscillates lightly; and when a hand or other part of the human body comes near the pickup antenna (a short piece of wire with or without a metal plate on its end), the drain current of the MOSFET undergoes a slight change. This change is coupled to the input circuit of the 2N2716 DC amplifier which, in turn, closes the relay. When the hand is withdrawn, the events reverse and the relay opens.

To set up the device initially, protect the pickup antenna from any nearby bodies, including the operator's. Then, work back and forth between adjustments of *threshold control* R3 and *sensitivity control* R2 until the relay just opens. Next, bring one of your hands close to the antenna and alternately adjust trimmer C2 and rheostat R2 with the other hand until the relay just closes. Withdrawing your hand from the vicinity

of the antenna should then cause the relay to open. When the circuit is correctly adjusted, bringing the hand to a desired distance from the antenna should close the relay, and moving the hand away should reopen it. The circuit must not be so sensitively adjusted that it self-operates.

For reliable operation, the device should be built solidly and should be completely enclosed in a shield box, except for the pickup antenna. The assembly should be grounded to earth. The antenna must be steady. Capacitor C3 should be a mica or good-grade ceramic unit, but capacitors C1 and C4 can be any convenient low-voltage units. Controls R2 and R3 both are wirewound.

The relay is a 1 mA, 1000-ohm device (Sigma 5F-1000 or equivalent). When the relay is closed, current drain from the 9-volt DC supply, B1, is approximately 12 mA, but this may vary somewhat with individual 3N128s and 2N2716s. Use output terminals 1 and 3 when relay closure must close an external circuit; use output terminals 2 and 3 when relay closure must open an external circuit.

TOUCH-PLATE RELAY

The high input resistance, high transconductance, and low input capacitance of the MOSFET suit this device for use as a DC amplifier in touch-plate relay circuits. Figure 3-12 shows a simple touch-plate circuit that responds to a light touch of a finger. Such relays have become common for operating all sorts of electrical gear, from sophisticated electronic circuits to elevators. A 3N152 low-noise MOSFET is employed in the circuit shown here. The gate almost floats, being 22 megohms above ground through resistor R1, and is connected to a small, metal, pickup disc. The gate thus is highly susceptible to pickup, so that merely touching it with a finger tip couples in enough random energy from stray fields to drive the MOSFET.

The MOSFET serves as a simple DC amplifier with a milliampere-type DC relay in its drain circuit. The relay is connected in a four-arm bridge circuit—consisting of resistor R3, the two “halves” of potentiometer R2, and the internal drain-to-source resistance of the MOSFET—which allows the static drain current of the 3N152 to be balanced out of the relay (by adjustment of R2). The relay is a 1 mA, 1000-ohm device (Sigma 5F-1000 or equivalent).

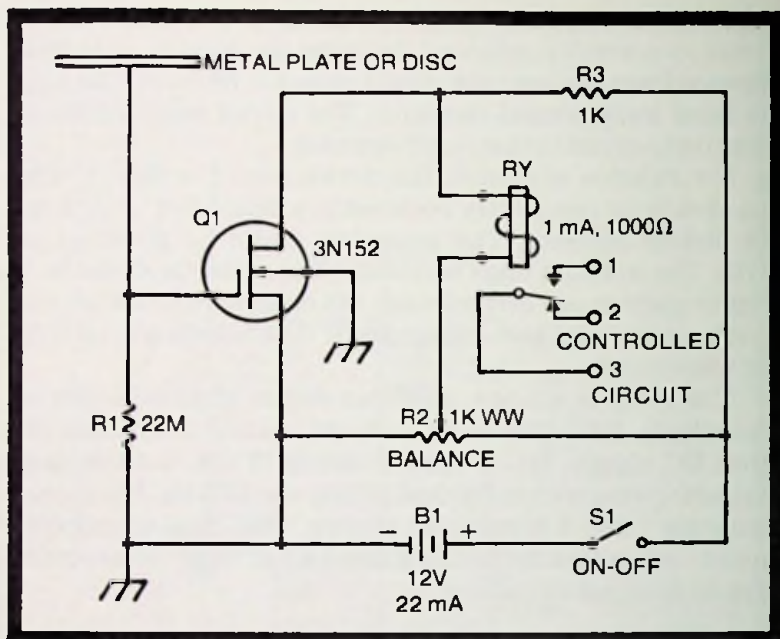


Fig. 3-12. Touch-plate relay.

With the pickup disc protected from any nearby bodies, initially set *balance control* potentiometer R2 to the point at which the relay opens. The circuit will then remain in this balanced, or "zero," condition indefinitely, unless the setting of R2 subsequently is disturbed. When the pickup disc is touched, the resulting change in drain current will change the internal resistance of the MOSFET, unbalancing the bridge and causing the relay to close.

Use output terminals 1 and 3 for operations in which the external controlled circuit must be closed by the relay closure; use 2 and 3 for operations in which the external controlled circuit must be opened. When the relay is closed, current drain from the 12-volt DC supply is approximately 22 mA, but this may vary somewhat with individual MOSFETs.

ELECTROSCOPE

An instrument for detecting the presence of electric charges is indispensable in many situations, in and out of the electronic field. For instance, it may be used to "smell out" dangerous charges of fields, or to detect the presence of high voltage without making connections to a conductor.

The old fashioned gold-leaf electroscope has a long record of usefulness as such a detector, but this device must be held upright at all times. An electronic electroscope (see circuit in Fig. 3-13) is not so restricted; it may be held in any position and, like the gold-leaf unit, it needs no connection to the source of high voltage.

This arrangement is similar to an electronic DC voltmeter. The gate of the 3N128 MOSFET is 22 megohms above ground and therefore very susceptible to nearby electric charges which are picked up by a polished brass ball on the end of a short rod attached to the gate. The picked-up energy is amplified by the MOSFET, and the latter drives miniature microammeter M1.

As in an electronic voltmeter circuit, the indicating meter is connected in a four-arm bridge circuit in the output of the MOSFET. The arms of this bridge consist of rheostat R4, the internal drain-to-source resistance of the MOSFET, and resistors R2 and R3. With the pickup ball clear of any electric fields and pointed away from the operator's body, potentiometer R4 is set to zero the meter. The device then will

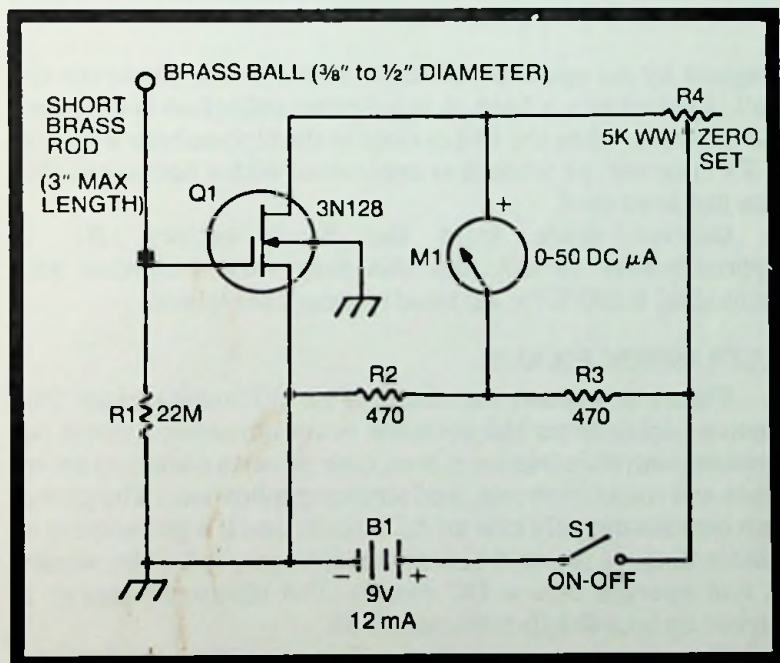


Fig. 3-13. Electroscope (charge detector).

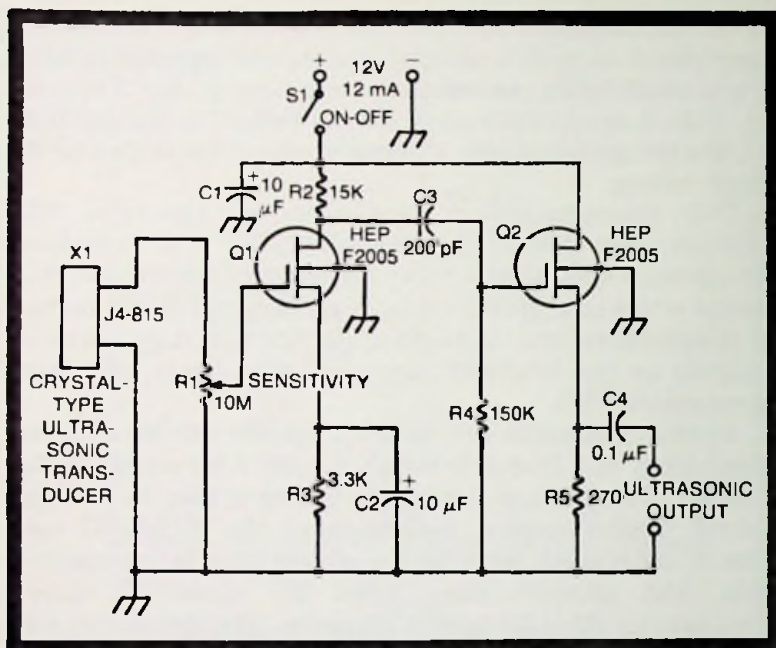


Fig. 3-14. Ultrasonic pickup.

respond by an upward deflection of the meter whenever the ball is poked into a field. A substantial deflection is obtained, for example, when the ball is close to the high-voltage wiring in a TV receiver, or when it is confronted with a hair comb that has just been used.

Current drain from the 9-volt battery, B1, is approximately 12 mA, but this may vary somewhat with individual MOSFETs. All fixed resistors are ½-watt.

ULTRASONIC PICKUP

Figure 3-14 shows the circuit of an ultrasonic pickup. This device functions as the receptor in an ultrasonic system for remote control, intrusion alarm, code or voice communication, tests and measurements, and similar applications. The pickup can operate directly into an AC circuit; and if a germanium or silicon diode is shunted across the *ultrasonic output* terminals, it can operate into a DC circuit. The ultrasonic energy is picked up by a 40 kHz transducer, X1.

The circuit consists of a voltage amplifier employing a HEP F2005 single-gate MOSFET (Q1) in a common-source

arrangement, and a source follower also employing a HEP F2005 MOSFET (Q2). The voltage gain of the input stage is approximately 30, and that of the output stage approximately 0.7; the gain of the entire pickup circuit thus is approximately 21. The maximum transducer signal, with *sensitivity control* potentiometer R1 set for maximum sensitivity, is approximately 50 mV rms before peak clipping in the output signal. The corresponding maximum output-signal voltage is approximately 1.05 V rms. In construction of this device, solid mounting and rigid wiring should be employed, to prevent vibration at very high frequencies.

All fixed resistors in this circuit are $\frac{1}{2}$ -watt. Electrolytic capacitors C1 and C2 are 25-volt units; capacitors C3 and C4 can be any convenient low-voltage units. The circuit draws approximately 12 mA from the 12-volt DC supply, but this may vary somewhat with individual MOSFETs.

4

Integrated Circuit IC

The *integrated circuit (IC)* consists of a tiny silicon chip which houses a series of components—such as transistors, diodes, resistors, and capacitors—and the interconnecting conductive paths which serve as wiring. These components and paths are formed by a combination of diffusion, photoprinting, and etching. Thus, the chip can contain an entire complicated circuit, such as a multistage amplifier, and the IC will be no larger than a discrete transistor.

The type CA3010 integrated circuit, for example, is a direct-coupled operational amplifier containing 10 transistors, 2 diodes, and 18 resistors; it has 12 leads for external connections and is housed in a T0-5 transistor package. Depending upon type, the IC is provided with pigtail leads or with terminal tabs, allowing the IC to be inserted into a socket or to be wired directly into an external circuit.

The IC, being a complete, miniaturized circuit package, saves much time and labor for the designer and builder of equipment: an entire pre-wired stage (or full circuit) can be plugged in or removed from a piece of equipment with the ease of handling a transistor or tube. While a large number of ICs contain complicated circuits, some contain only separate components (for example, 2 diodes or 4 transistors) which, being fabricated close together in the same substrate, are excellently matched. Integrated circuits are available in a

very large number of types in both linear and digital categories.

Before working with ICs, read the hints and precautions in Chapter 1, especially items 3, 4, 6, 8, 10, and 14.

IC THEORY

Figure 4-1(A) shows the structure of a possible integrated circuit; Fig. 4-1(B) shows the corresponding internal circuit. While this arrangement is not necessarily one that can be found in a manufactured unit, it is true to the nature of the IC and is simple enough for illustrative purposes.

In Fig. 4-1(A), N- and P-regions are diffused into the substrate (silicon chip) to form the diode (D1), transistor (Q1), resistor (R1), and capacitor (C1) of the circuit. Next, a silicon dioxide dielectric film is grown on the face of the chip. Then this dielectric is etched away at those places, such as points 4 and 10, where connections must be made to the N- and P-regions. Next, a metal film is deposited on top of the dielectric to extend through the etched windows to make contact with the regions and to provide the "wiring" between the components. The matching numbers in Fig. 4-1(A) and 4-1(B) allow these contacts and interconnections to be identified by the reader.

In this example, the various components are formed in a P-type chip; and since each component has an "outside" N-layer, the resulting PN junction offers very high resistance, being reverse biased, and thus prevents the components from being short-circuited together through the substrate. The resistor consists only of a P-region, connections being made to the latter at points 7 and 8. One "plate" of the capacitor is the N-region, to which a connection is made at point 10, and the other plate is the portion "X" of the metal film. This general construction is characteristic of all ICs, although the geometry of a specific manufactured unit may differ considerably from the structure in Fig. 4-1(A).

The various functional types of ICs are too numerous to list here. However, some familiar examples are DC, AF, IF, RF, video, differential, and operational amplifiers; balanced modulators; product detectors; mixers; and amplifier/discriminators in the *linear* category; and flip-flops; gates; latches; inverters; Schmitt triggers; and scalars in the *digital* category.

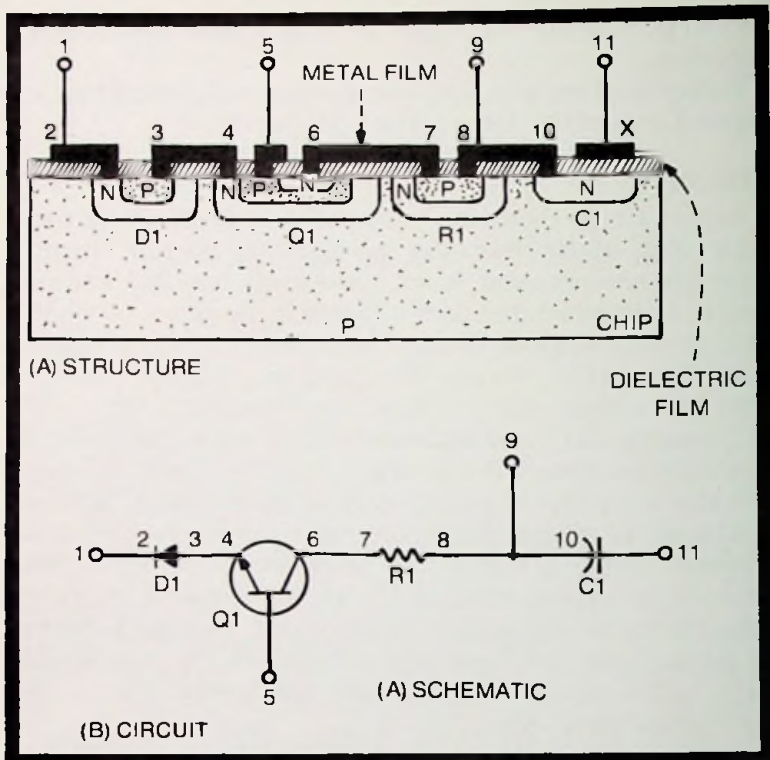


Fig. 4-1. Details of integrated circuit.

Figure 4-2 shows circuit symbols for various types of IC. In circuit diagrams in which these symbols appear, up to 14 numbered leads (not shown in Fig. 4-2) are drawn to these symbols. The numbering corresponds to the lead or terminal numbering of the particular IC package. Figures 4-2 (A) and (B) are linear-type ICs; Figs. 4-2(C), (D), (E), (F), and (G) are digital type; Fig. 4-2(H) may be either linear or digital and represents any other undesignated type such as a type voltage regulator or interval timer.

Figure 4-3(A) shows the internal circuit of a type CA3002 IF amplifier IC, and Fig. 4-3(B) shows the corresponding circuit symbol with leads numbered according to the terminal numbering of the actual IC package.

COMPLETE AUDIO AMPLIFIER

One of the attractions of the IC to experimenters and some audiophiles is the ability of some ICs to supply a complete

audio amplifier in a small transistor-type case. An amplifier of this type is shown in Fig. 4-4. Here, the CA3020 integrated circuit contains three intermediate stages and a push-pull, class-B output stage. The only "outboard" components required are four capacitors, two fixed resistors, one potentiometer, and one output transformer. The circuit operates from a single battery.



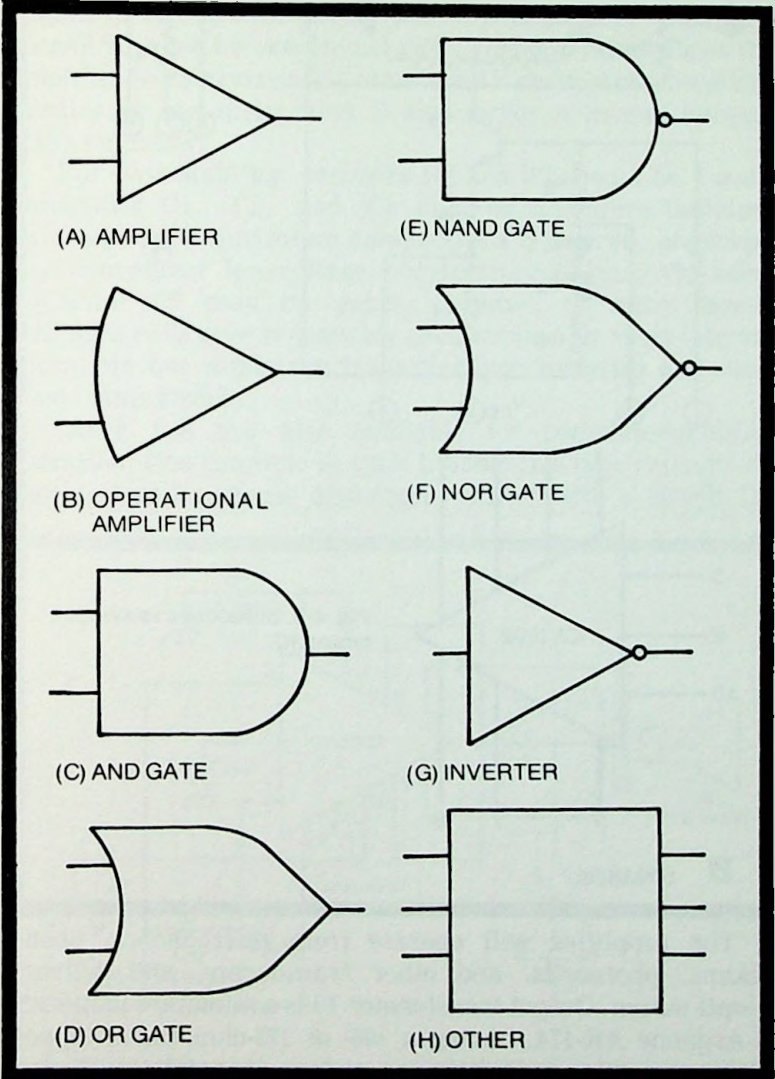


Fig. 4-2. IC circuit symbols.

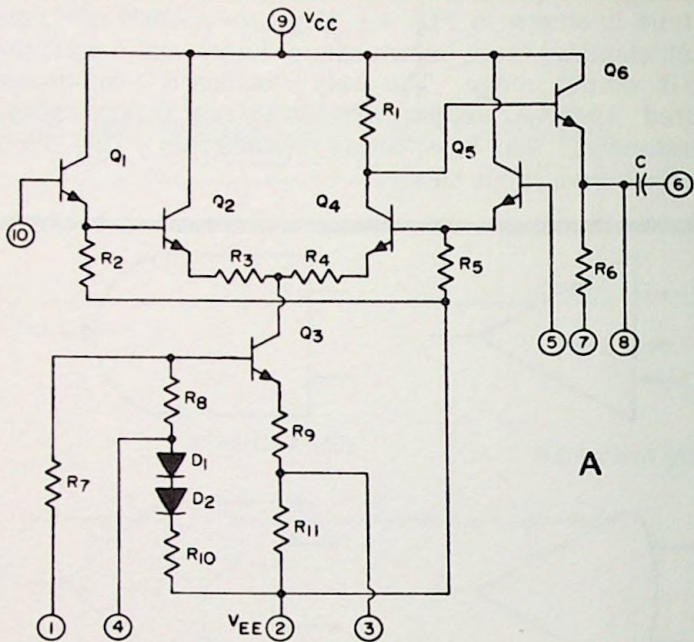

A

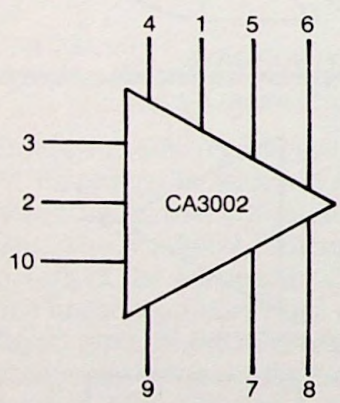

B SYMBOL

Fig. 4-3. Schematic vs symbol, typical IC.

The amplifier will operate from microphones, phono pickups, photocells, and other transducers, and delivers 1/4-watt output. Output transformer T1 is a miniature unit, such as Argonne AR-174, having a 100- or 125-ohm center-tapped primary winding and 3.2-ohm secondary, to match the 3.2-ohm speaker to the IC.

The class-B output stage uses most of the DC input power; thus, the idling current drain from the 6-volt battery is approximately 4 mA, and the maximum-signal current is 77 mA. At a battery voltage of 9 volts, the current drains are somewhat higher, and the power output is approximately 0.3 watt. With either 6- or 9-volts input, however, the IC must be supplied with a suitable heat sink.

The amplifier exhibits good gain. An input of 50 mV rms results in full ¼-watt output with low distortion, when gain control R is set for maximum gain. This operation allows the amplifier to function as the complete AF channel of a receiver, monitor, or test instrument. It also serves as its own integral audio amplifier.

For best stability, resistors R2 and R3 should be 1 watt. Capacitors C1, C3, and C4 can be miniature tantalum electrolytics, if maximum compactness is desired; otherwise any convenient low-voltage nonelectrolytics may be used. Capacitor C2 may be paper, ceramic, or mica. Size-D flashlight cells give reasonably good service for short-interval operation, but miniature transistor-type batteries are short lived in this circuit.

Other ICs are also available for complete-amplifier operation. One example is type LM380. This type delivers 2½ watts (total harmonic distortion = 0.2%) with a 22-volt DC

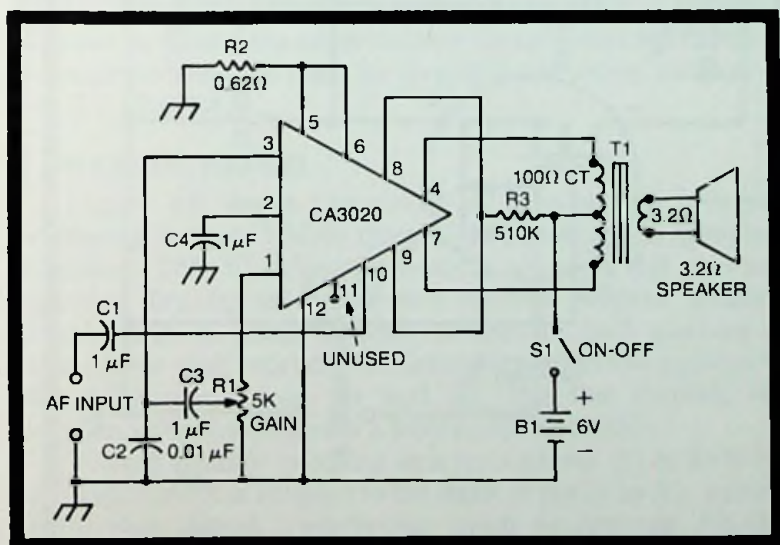


Fig. 4-4. Complete audio amplifier.

supply, and operates directly into an 8-ohm speaker without output transformer.

AUDIO POWER AMPLIFIER WITH MOSFET INPUT

The versatility of the complete audio amplifier described in the preceding section can be widened by providing it with a high-impedance input stage. Figure 4-5 shows how a 3N87 MOSFET is employed as a simple source follower to provide this high impedance. (See Chapter 3 for MOSFET theory and application.)

The voltage gain of the input stage is approximately 0.51, and this requires that the input signal amplitude be 98 mV rms for a full $\frac{1}{4}$ -watt output into the speaker. For this circuit, the zero-signal current from the 6-volt battery is 14 mA, and the maximum-signal current is 87 mA. These are approximate figures and will vary somewhat with individual ICs and MOSFETs.

Five outboard components are required for the MOSFET: Capacitor C2 is a 25-volt electrolytic unit, while C1 may be any convenient low-voltage unit. Resistors R1 and R2 are $\frac{1}{2}$ -watt. All outboard components in the IC portion of the circuit correspond to those in the same positions in the basic IC circuit. Fig. 4-4.

For ease of handling and installation, a gate-protected MOSFET has been chosen; however, a conventional MOSFET also can be used if the experimenter is experienced in handling the unprotected type (see, for example, the source follower in Fig. 3-7, Chapter 3).

2 $\frac{1}{2}$ -WATT INTERCOM

Figure 4-6 shows the circuit of a miniature intercom employing a type LM380 integrated circuit as the complete amplifier. This IC delivers 2 $\frac{1}{2}$ -watts output at full gain and operates directly into an 8-ohm speaker, without coupling transformer. A small speaker is used at both stations as microphone and reproducer, depending upon the position of the *talk-listen* switch, S1 and S3. The two stations are interconnected by means of a 3-wire, shielded cable.

When a speaker is acting as a microphone (S1 or S3 in the *talk* position), it is coupled to the input of the IC by T1, a small 4000:8 ohm output transformer (such as Argonne AR-134) connected backward. The other speaker then is automatically

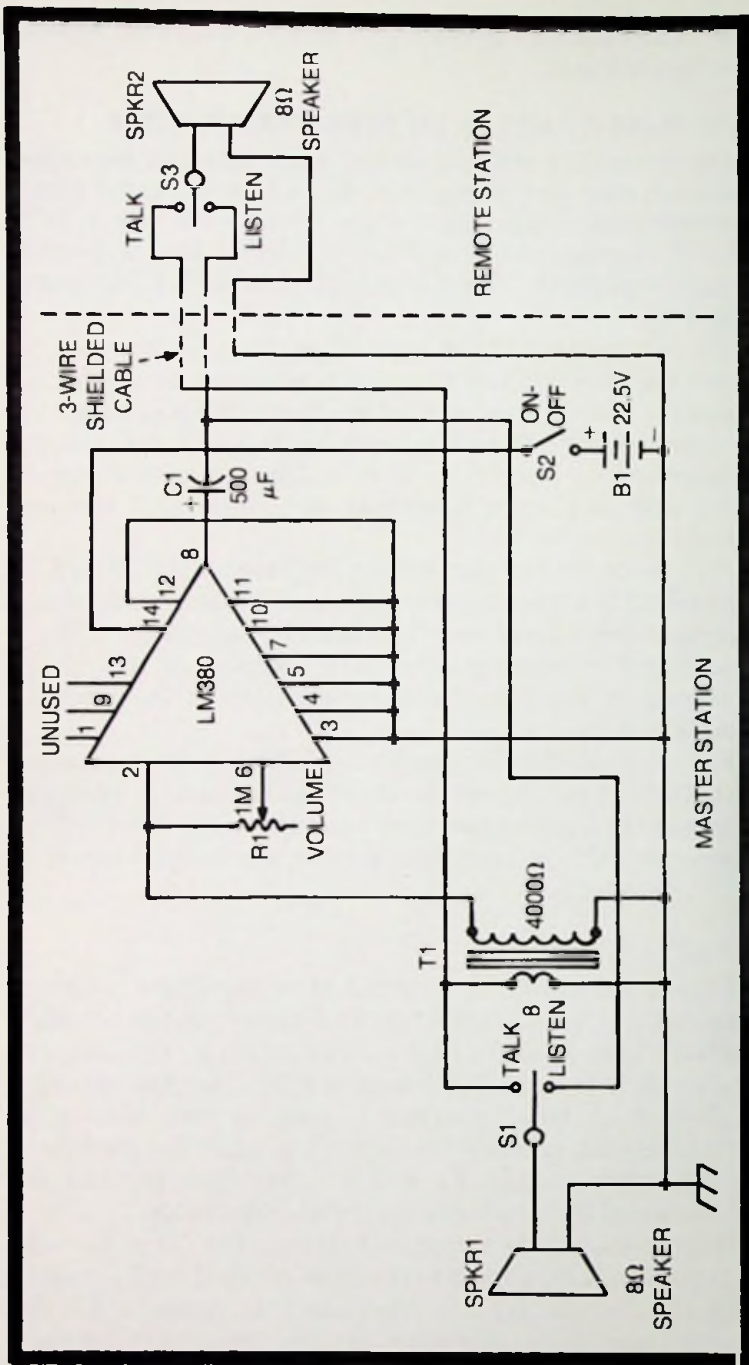


Fig. 4-6. 2 1/2-watt intercom.

connected to the output of the IC and serves as a reproducer. The 2¹/₂-watt output will be adequate in all except very noisy places.

Construction of the intercom should be entirely straight-forward. Take special precautions to keep the input and output circuits of the IC as isolated as well as practicable, to prevent unwanted electrical feedback, and to provide the IC with a heat sink. Aside from the input coupling transformer, the only outboard components are the 1-megohm rheostat (R1) and 500 μ F output capacitor (C1).

Current drain from the 22.5-volt DC source, B1, is approximately 25 mA zero-signal, and 220 mA maximum signal. These currents may vary somewhat with individual ICs.

VERY LOW-RESISTANCE DC MILLIAMMETER

Low resistance is desired in a current meter, in order to minimize the voltage drop introduced by the meter into a circuit where it is inserted. The more closely the internal resistance of the meter approaches zero, the less the instrument upsets the circuit. Even though the resistance of many current meters is low, it still is too high for some applications unless it is painstakingly taken into account in all measurements and calculations. For example, the common resistance of the useful 0–1 DC milliammeter is 55 ohms, corresponding to a voltage drop of 55 mV.

Figure 4-7 shows the circuit of an electronic DC milliammeter giving a full-scale deflection of 1 mA and having a resistance of only 2.7 ohms. In this circuit, the type μ A776 integrated circuit functions as a DC voltage amplifier with a voltage gain of approximately 40, and boosts the 2.7 mV developed by the 1 mA input current across resistor R1 to the 100 mV required to deflect the 0–50 DC microammeter (M1) to full scale. If this microammeter—whose internal resistance is 2000 ohms—were simply shunted to convert it into a 0–1 milliammeter, a shunt resistance of 105 ohms would be required, and the resulting instrument resistance would be 99.8 ohms, approximately 37 times the input resistance of the electronic circuit.

In this circuit, resistors R1, R2, and R4 must be selected to have resistance as close as practicable to the specified values. If precision instrument resistors are available to the builder,

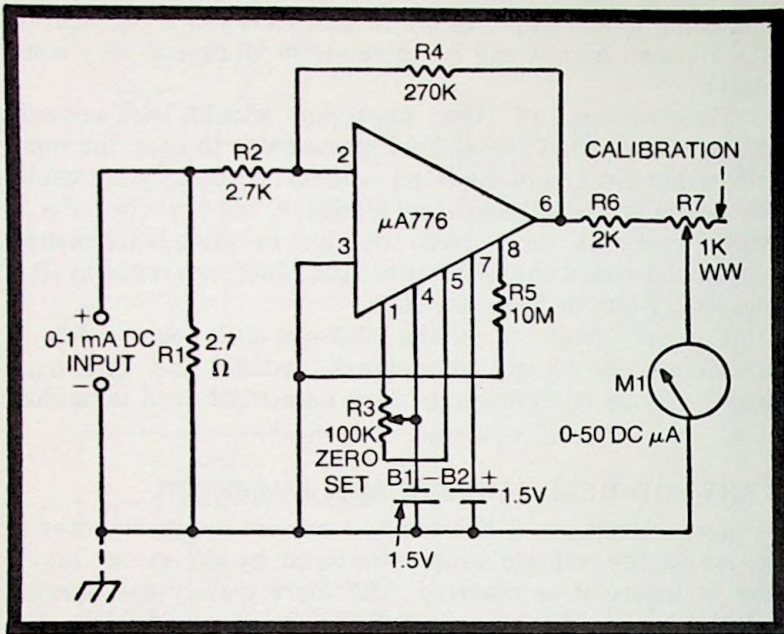


Fig. 4-7. Very low-resistance DC milliammeter.

R1 can be 2 ohms, R2 2 K, and R4 200 K; the input resistance then will be 2 ohms. Meter M1 is initially set to zero by adjustment of potentiometer R3 which adjusts the offset of the IC. Rheostat R7 allows the meter to be set for exact full-scale deflection when an accurately known 1 mA current is applied to the *DC input* terminals. For best stability, resistors R1, R2, and R4 should be 1-watt each. Resistors R5 and R6 may be ½-watt. Rheostat R7 must be wirewound.

Initial adjustment of the instrument is simple:

- 1—With the *DC input* terminals open, set rheostat R7 to its zero-resistance position and set potentiometer R3 to zero the microammeter.
- 2—Apply an accurately known 1 mA direct current to the *DC input* terminals.
- 3—Adjust rheostat R7 for exact full-scale deflection of the meter.
- 4—The instrument response is linear, and may be checked by applying successively lower currents (such as ½ mA, ¼ mA, etc.) to the *DC input* terminals.

A special 0–1 mA card may be drawn for the meter, or the 0–50 μ A card may be retained and the readings in mA interpreted from the μ A deflections.

An added advantage of this circuit is its low power demand. Size-D flashlight cells at B1 and B2 will give shelf life, so no *on-off* switch is required.

ELECTRONIC DC MILLIVOLTMETER

Figure 4-8 shows the circuit of an electronic DC millivoltmeter covering 0–1000 mV in three ranges: 0–10 mV, 0–100 mV, and 0–1000 mV. Readings are displayed on the scale of a 0–1 DC milliammeter. In this circuit, a type HEP S3001 integrated circuit functions as a DC voltage amplifier to boost the input-signal voltage to the 55 mV required for full-scale deflection of the milliammeter.

The circuit is relatively uncomplicated. The input portion contains only the three multiplier-type range resistors (R1, R2, R3) and the range selector switch (S1). Negative feedback through the 100K resistor, R4 sets the gain of the amplifier and also linearizes response of the milliammeter. A dual DC supply (22.5-volt batteries B1 and B2) is required; the current

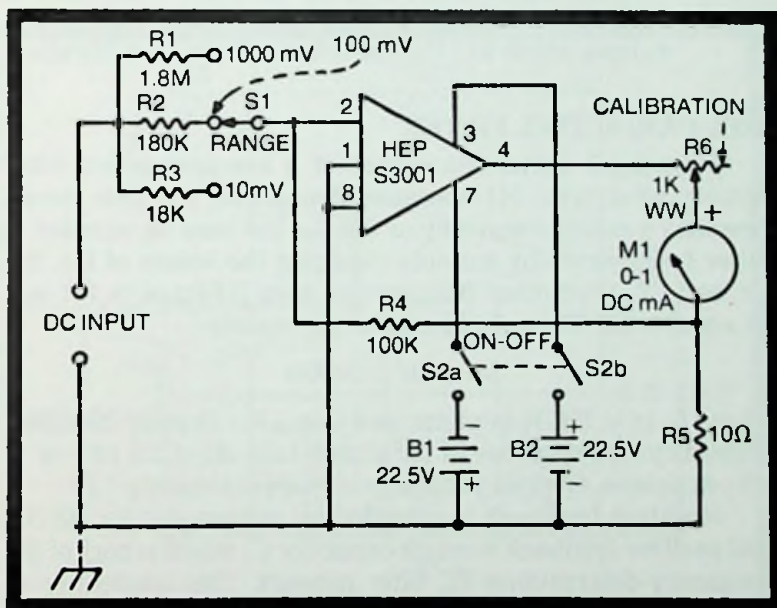


Fig. 4-8. Electronic DC millivoltmeter.

drain from each battery is approximately 5 mA, but this may vary with individual ICs. No zero-set potentiometer is needed.

For best stability, all fixed resistors in the circuit should be 1-watt. Resistors R1, R2, and R3 must be selected as close as practicable to specified values (they may depart from these values, so long as all three vary by the same ratio). Rheostat R6 must be wirewound. All wiring should be kept as short and direct as possible. Unused terminals of the IC may be left floating.

To calibrate the instrument initially:

- 1—Set switch S1 to its 1000 mV position.
- 2—Set *calibration* rheostat R6 to its zero-resistance position. Close switch S2.
- 3—Apply an accurately known 1-volt DC to the *DC input* terminals, observing correct polarity.
- 4—Adjust rheostat R6 for exact full-scale deflection of milliammeter M1.
- 5—Operation of the circuit is linear, and this may be checked by applying successively lower voltages (with S1 still set to the 1000 mV range), such as 1/2-volt, 1/4-volt, etc., while observing deflection of the meter.
- 6—If resistors R1, R2, and R3 are accurate, this one calibration will serve also for the 100 mV and 10 mV ranges which will then be automatically in calibration.

LOW-PASS ACTIVE FILTER

Figure 4-9 shows the circuit of a low-pass active filter employing a type 741 operational-amplifier IC. This circuit provides a cutoff frequency of 500 Hz, but may be adapted to other frequencies by suitably changing the values of R1, R2, C1, and C2. (For other frequencies, keep R1 equal to R2, and C1 equal to C2. The cutoff frequency f_c equals:

$$f_c = 10^6 / (2\pi RC)$$

where f_c is in Hz, R in ohms, and C in μF .) Beyond the cutoff frequency, the response of the circuit falls off at the rate of 12 dB per octave. Overall voltage gain is approximately 1.59.

Negative feedback is provided by voltage divider R3-R4, and positive feedback through capacitor C1 which is part of the frequency-determining FC filter network. This application of feedback, provided by the amplifier, sharpens the response of the filter beyond that of the simple RC circuit (R1-R2-C1-C2).

A dual DC supply is required, represented here by 12-volt batteries B1 and B2. The drain from each battery is approximately 3 mA, but this can be expected to vary somewhat with individual ICs.

All wiring must be kept as short and well separated as practicable, to prevent signal transfer around the IC; in other respects, however, construction of this filter offers no special problems. Resistances R1 and R2 must be accurate, as must also capacitances C1 and C2. The $0.032 \mu\text{F}$ capacitance can be obtained by connecting one 0.03 and one $0.002 \mu\text{F}$ capacitor in parallel. These capacitors must be of good quality. All resistors should be 1-watt. DC coupling is shown in Fig. 4-9, but AC coupling may be obtained by connecting one $10 \mu\text{F}$ capacitor in series with the high AF input lead, and another in series with the high AF output lead.

HIGH-PASS ACTIVE FILTER

Figure 4-10 shows the circuit of a high-pass active filter employing a type 741 operational-amplifier IC. This circuit, like the low-pass filter described in the preceding section, provides a cutoff frequency of 500 Hz, but may be adapted to other frequencies by suitably changing the values of R1, R2, C1,

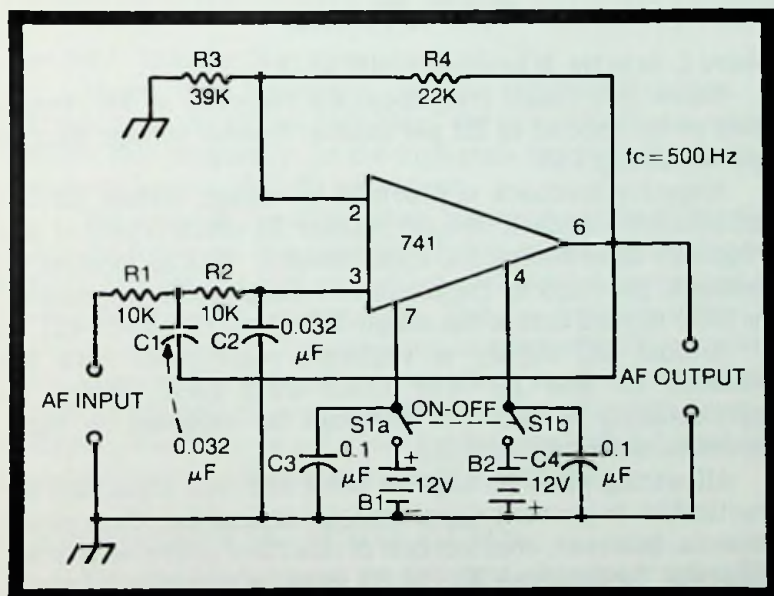


Fig. 4-9. Low-pass active filter.

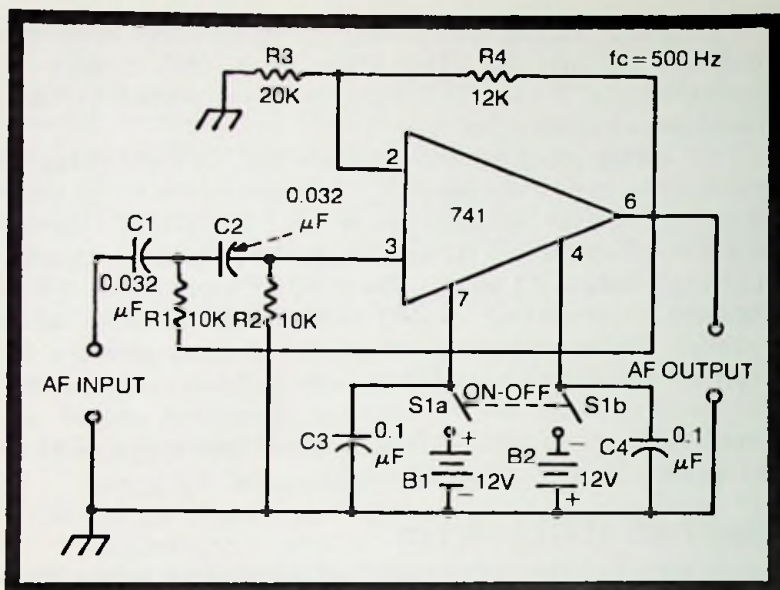


Fig. 4-10. High-pass active filter.

and C2. For other frequencies, keep R1 equal to R2, and C1 equal to C2. The cutoff frequency f_c equals:

$$f_c = 10^6 / (2\pi RC)$$

where f_c is in Hz, R in ohms, and C in μF .

Below this cutoff frequency, the response of the circuit rises at the rate of 12 dB per octave. Overall voltage gain is approximately 1.59.

Negative feedback is provided by voltage divider R3-R4, and positive feedback through resistor R1 which is part of the frequency-determining RC filter network. This application of feedback, provided by the amplifier, sharpens the response of the filter beyond that of the simple RC circuit (R1-R2-C1-C2).

A dual DC supply is required, represented here by batteries B1 and B2. The drain from each battery is approximately 3 mA, but this can be expected to vary somewhat with individual ICs.

All wiring must be kept as short and well separated as practicable, to prevent signal transfer around the IC; in other respects, however, construction of this filter offers no special problems. Resistances R1 and R2 must be accurate, as must also capacitances C1 and C2. The $0.032 \mu\text{F}$ capacitance can be

obtained by connecting one 0.03 and one 0.002 μF capacitor in parallel. These capacitors must be of good quality. All resistors should be 1-watt. The input is AC coupled by the first filter capacitor, C1, but the output is DC coupled. If desired, the output can be AC coupled by inserting a 10 μF capacitor in the high *AF output* lead.

COMBINATION HIGH-PASS, LOW-PASS ACTIVE FILTER

The active filter circuit shown in Fig. 4-11 is, in effect, a combination of a low-pass filter and high-pass filter. A single pair of resistors (R1-R2) and a single pair of capacitors (C1-C2) are arranged into a low-pass RC filter circuit when the 4-pole, double-throw changeover switch (S1_{A-D}) is in its LP position, and are arranged into a high-pass RC filter circuit when the switch is in its HP position.

With the R1-R2 and C1-C2 values given in Fig. 4-11, the cutoff frequency is 500 Hz for both the low-pass and high-pass functions. The cutoff frequency may be changed to some other desired value—and will be the same for low-pass and high-pass—by suitably changing the values of R1, R2, C1, and C2. For other frequencies, keep R1 equal to R2, and C1 equal to C2. The cutoff frequency f_c equals:

$$f_c = 10^6 / (2\pi RC)$$

where f_c is in Hz, R in ohms, and C in μF .

Above this frequency, in the low-pass function, the response of the circuit falls off at the rate of 12 dB per octave; below this frequency, in the high-pass function, the response rises at the rate of 12 dB per octave.

The general characteristics and construction of this filter are the same as those separately described for the low-pass filter and for the high-pass filter. See earlier sections of this chapter for this information. The combination filter has DC-coupled output, but the input is inherently DC coupled on low-pass and AC coupled on high-pass. If AC coupling is desired for both high-pass and low-pass and for both input and output, insert one 10 μF capacitor into the high *AF input* lead, and another 10 μF into the high *AF output* lead.

BANDPASS (PEAK) ACTIVE FILTER

Figure 4-12(A) shows the circuit of a bandpass active filter of the sharp-peak type employing a type 741 operational-

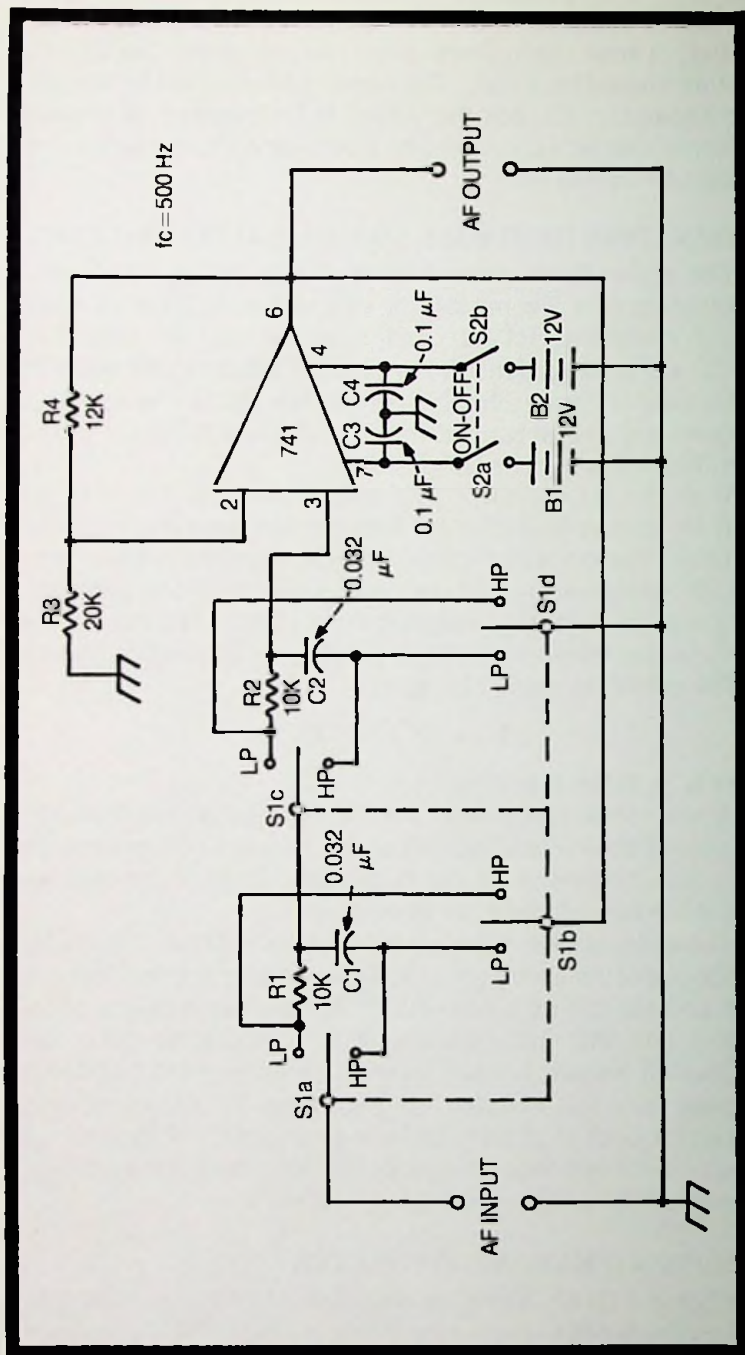


Fig. 4-11. Combination high-pass, low-pass active filter.

amplifier IC. A parallel-T RC network (R3-R4-R5-C2-C3-C4) in the negative-feedback loop determines the peak frequency of this filter. This is a null network, but it makes a *pass* amplifier out of the circuit, as it cancels gain of the amplifier on all frequencies except the null frequency. Positive feedback is adjustable by means of rheostat R7, and serves to sharpen the response of the circuit, thus effectively increasing the Q of the parallel-T network.

Figure 4-12(B) shows the response of the circuit: The solid curve depicts minimum selectivity (low Q) when positive feedback is minimum (R7 set to maximum resistance), whereas the dotted curve shows maximum selectivity (high Q) when positive feedback is maximum (R7 set to low or zero resistance). Voltage gain of the circuit at the peak of the response is approximately 100.

The resistance and capacitance values in the parallel-T network have been chosen for a filter peak of 1000 Hz. The peak frequency may be changed to some other desired value, however, by suitably changing the values of C2, C3, C4, R3, R4, and R5.

For other frequencies, keep $R_3 = R_5 = R_4$, and $C_2 = C_3 = \frac{1}{2}C_4$. The peak frequency f equals:

$$f = 10^6 / (2\pi R_3 C_2)$$

where f is in Hz, R_3 in ohms, and C_2 in μF .

A dual DC supply is required, represented here by 15-volt batteries B1 and B2. The drain from each battery is approximately 4 mA, but this can be expected to vary somewhat with individual ICs.

All wiring must be kept as short and well separated as possible, to prevent signal transmission around the IC; in other respects, however, construction of the filter offers no special problems. Resistances R3, R4, and R5 must be accurate, as must capacitances C2, C3, and C4. The off-standard values for R3 and R5 can be obtained by connecting one 3000- and one 180-ohm resistor in series, and for R4 by connecting one 1500- and one 91-ohm resistor in series. Capacitors C2, C3, and C4 must be of excellent quality.

It is interesting to note that the filter becomes a sine-wave oscillator when the positive feedback is advanced sufficiently (that is, when *selectivity* control R7 is set for excessive regeneration).


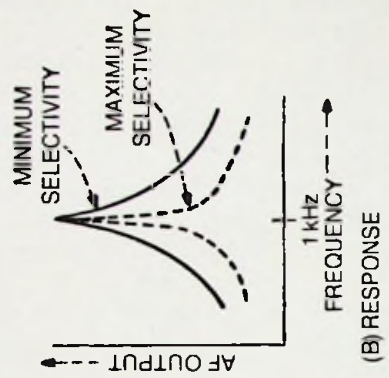
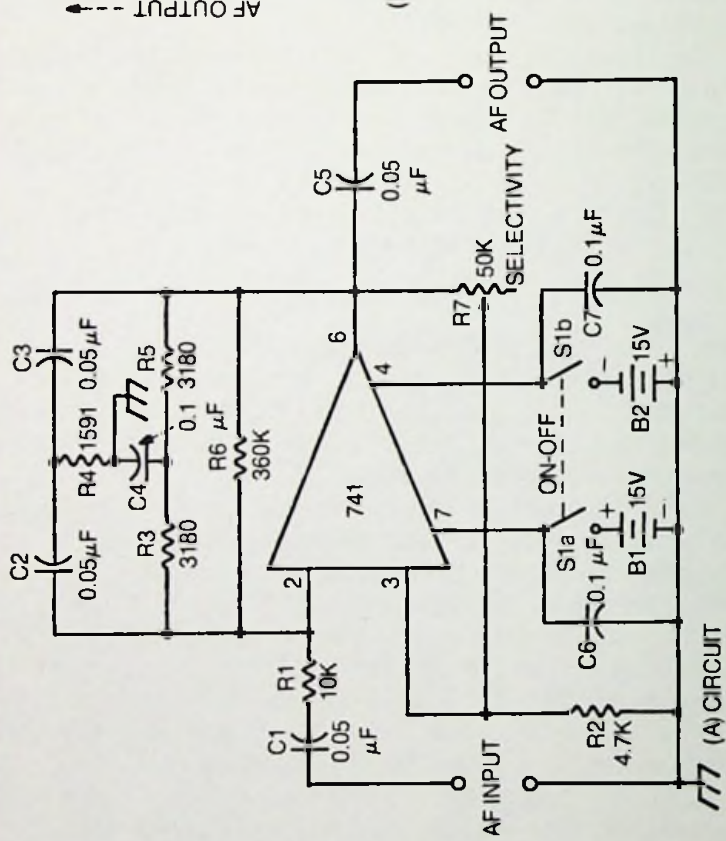


Fig. 4-12. Bandpass (peak) active filter.

ACTIVE BANDSTOP (NOTCH) FILTER

Figure 4-13(A) shows the circuit of a bandstop active filter of the sharp-notch type, employing a type 741 operations-amplifier IC. A parallel-T RC network (R1-R2-R3-C1-C2-C3) in the input circuit determines the notch frequency of this filter. This is a null network. Positive feedback is introduced at the common point of this network (junction of C3 and R3) to sharpen the response of the parallel-T. Figure 4-13(B) shows typical response.

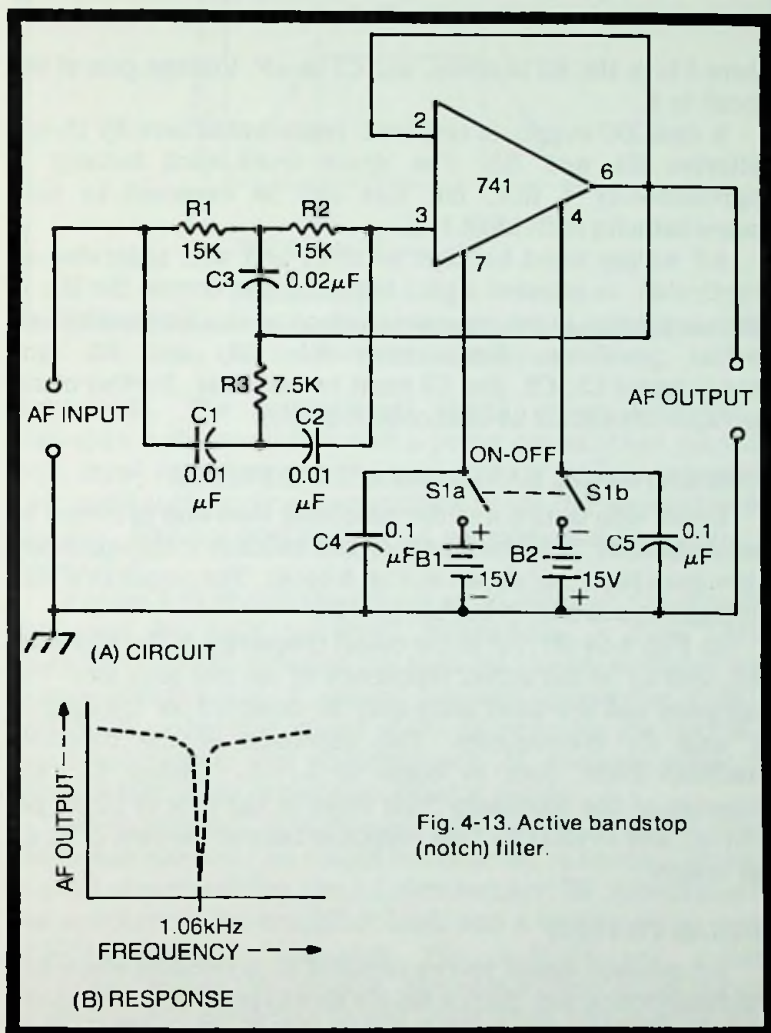

The resistance and capacitance values in the parallel-T network are stock, and the resulting notch frequency is 1061 Hz. For exactly 1000 Hz, $R_1 = R_2 = 15,915$ ohms, $R_3 = 7957$ ohms; and the capacitances remain the same as shown in the circuit. The notch frequency may be changed to any other desired value, by suitably changing the resistance or capacitance values.

For other frequencies, keep $C_1 = C_2 = \frac{1}{2}C_3$, and $R_1 = R_2 = 2R_3$. The notch frequency f equals:

$$f = 106 / (2\pi R_1 C_1)$$

where f is in Hz, R_1 in ohms, and C_1 in μF . Voltage gain of the circuit is 1.

A dual DC supply is required, represented here by 15-volt batteries B1 and B2. The drain from each battery is approximately 4 mA, but this can be expected to vary somewhat with individual ICs.

All wiring must be kept as short and well separated as practicable, to prevent signal transmission around the IC; in other respects, however, construction of the filter offers no special problems. Resistances R_1 , R_2 , and R_3 , and capacitances C_1 , C_2 , and C_3 must be accurate. Furthermore, the capacitors must be of excellent quality.

CONVENTIONAL BANDPASS ACTIVE FILTER

Users who desire a wider passband than that provided by the notch filter described earlier can cascade a high-pass and a low-pass filter, as shown in Fig. 4-14(A). The response of this arrangement is shown in Fig. 4-14(B).

In Fig. 4-14(B), f_{c1} is the cutoff frequency of the high-pass unit, and f_{c2} is the cutoff frequency of the low-pass unit. The high-pass and low-pass units may be designed for the desired f_{c1} and f_{c2} frequencies. The passband of the complete bandpass filter then is equal to $f_{c2} - f_{c1}$. Below f_{c1} , the response of the bandpass filter rises at the rate of 12 dB per octave; and beyond f_{c2} , the response falls at the rate of 12 dB per octave.

SIGNAL TRACER

An untuned signal tracer remains an invaluable electronic troubleshooting aid. Such a device should provide a reasonable amount of signal sensitivity and visual, as well as aural

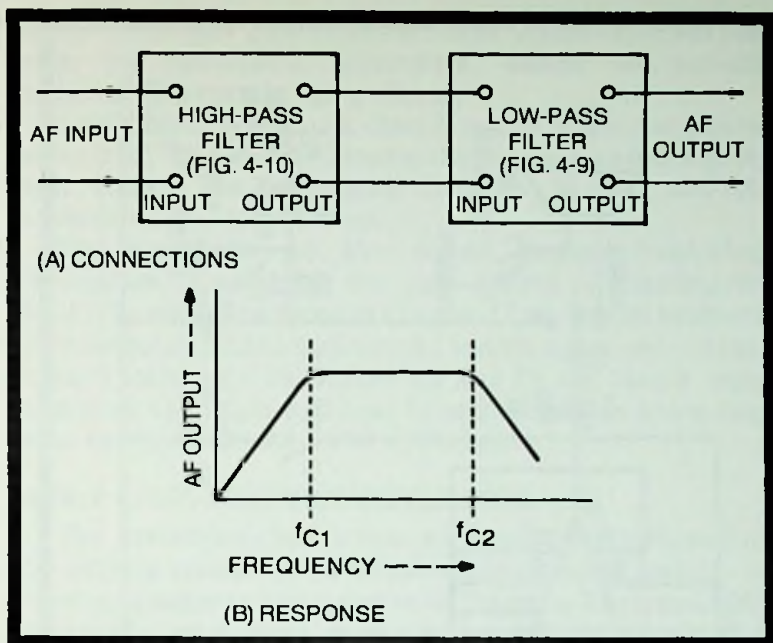


Fig. 4-14. Conventional bandpass active filter.

indications. The conventional signal tracer embodies a high-gain audio amplifier with a power output stage, provides high input impedance, and works from a straight test probe (for audio testing) or a demodulator probe (for modulated-RF testing). Battery operation gives complete isolation from the power line.

Figure 4-15 shows the circuit of an efficient signal tracer that can be built to small dimensions. A type LM380 integrated circuit supplies the high-gain audio amplifier with power-output stage. A source follower, employing a 3N128 MOSFET, connected ahead of the IC provides the very high input impedance. The shielded jack, J1, receives either the straight test probe or the demodulator probe.

When switch S2 is in its *aural* position, the amplifier drives the 8-ohm speaker; no output transformer is needed. When S2 is in its *visual* position, the 8.2-ohm resistor, R4, substitutes for the speaker as the amplifier load, and a rectifier-type meter (C5-D1-D2-R5-M1) indicates the output-signal voltage developed across this resistor. Rheostat R5 may be set initially to confine the deflection to full scale when *gain* control R3 is

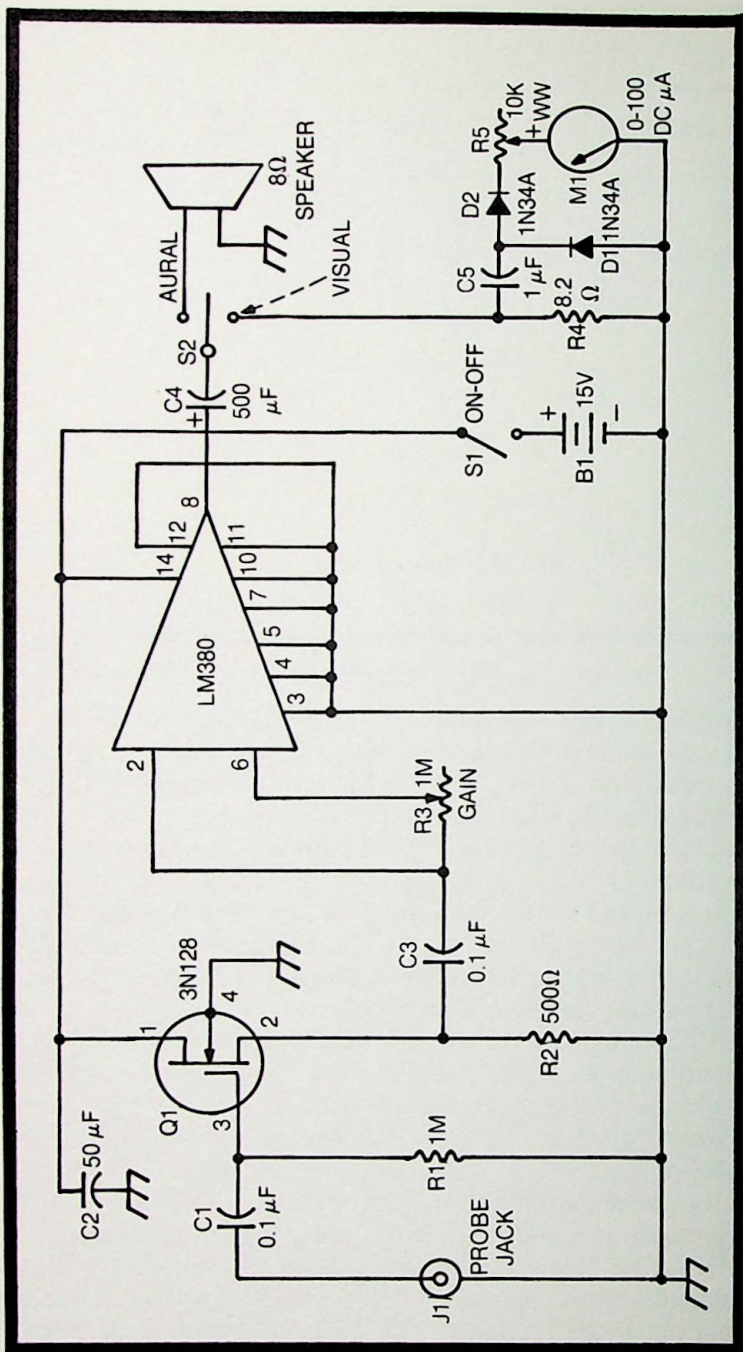


Fig. 4-15. Signal tracer

set for maximum gain (highest tracer sensitivity); R5 then needs no subsequent adjustment, except for periodic realignment to correct aging effects.

Since the IC contains a class-B output stage, the current drawn from the 15-volt DC source (battery B1), varies with the input signal: the zero-signal level is 10 mA, and the maximum-signal level 150 mA.

The simplicity of the circuit insures troublefree construction. Except for the care needed in handling the MOSFET (see precautions in Chapter 1), no special problems are introduced. Fixed resistors R1 and R2 are 1/2-watt; R4 is 5 watts. Electrolytic capacitors C2 and C4 are 25-volt units; capacitors C1, C3, and C5 may be any convenient low-voltage units, except C5 should not be electrolytic.

GROUP CODE-PRACTICE OSCILLATOR

The resistance-capacitance AF oscillator shown in Fig. 4-16 delivers enough audio output—approximately 2-watts—to an 8-ohm speaker to serve a group of listeners. The type LM380 integrated circuit operates as a phase-shift oscillator with a

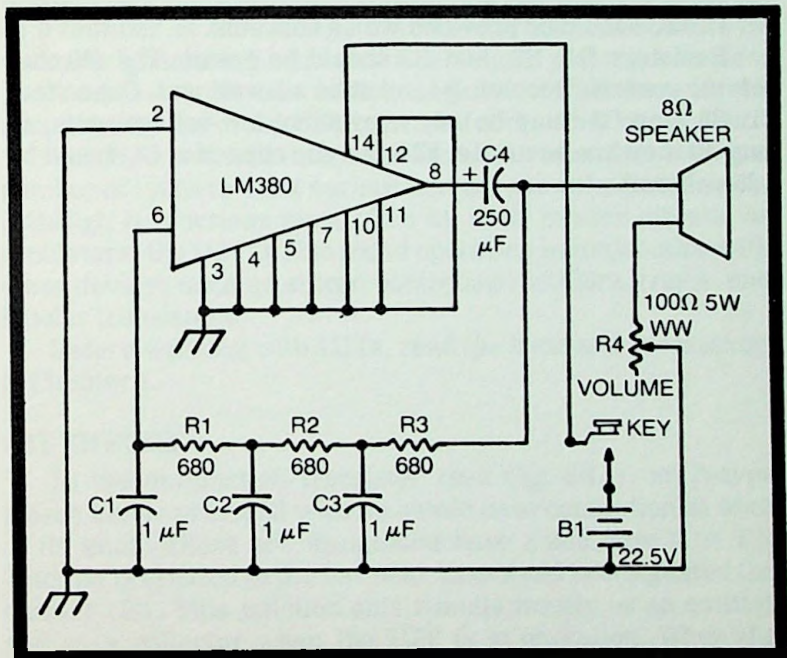


Fig. 4-16. Group code-practice oscillator.

phase-lag-type frequency-determining network (R1-R2-R3-C1-C2-C3) inserted into its positive-feedback loop.

With the stock resistance and capacitance values in the network, the frequency is 406 Hz. For exactly 400 Hz, with the 1 μ F capacitors shown, the resistors would each need to be 688.7 ohms. The frequency of approximately 400 Hz was chosen for its easy "readability." However, the frequency of the oscillator can be changed to any other desired value by suitably changing the resistance or capacitance values in the phase-shift network. For any frequency, keep $R1 = R2 = R3$, and $C1 = C2 = C3$, the oscillation frequency f equals:

$$f = 10^6 / (3.63 f C)$$

and

$$C = 10^6 / (3.63 f R)$$

The R and C values thus obtained will always produce the required total phase shift of 180 degrees. Resistors R1, R2, and R3 must be accurate, as must also capacitors C1, C2, and C3.

When the key is down, the circuit draws approximately 220 mA from the 22.5-volt DC supply, represented here by battery B1. The IC should be provided with a heat sink.

Resistors R1, R2, and R3 should be 1-watt. The 100-ohm *volume control* rheostat, R4, must be a 5-watt unit. Capacitors C1, C2, and C3 may be any convenient low-voltage units, so long as they are accurate. Electrolytic capacitor C4 should be a 25-volt unit.

5

Unijunction Transistor UJT

The *unijunction transistor (UJT)* is a 3-terminal device which, unlike the bipolar transistor, has only one PN junction. Because the UJT exhibits negative input resistance, it is useful in a number of low-voltage devices—such as multivibrators, sawtooth generators, threshold detectors, pulse generators, and timers—which can exploit negative resistance and are simplified by use of the UJT instead of some other component.

The UJT is small and versatile and is manufactured in a number of types to meet various current and voltage demands. Although it functions most often by itself in such circuits as oscillators, the UJT is also found operating in conjunction with other devices such as silicon controlled rectifiers, triacs, and bipolar transistors.

Before working with UJTs, read the hints and precautions in Chapter 1.

UJT THEORY

In the unijunction transistor (see Fig. 5-1A), an N-type silicon bar is provided with an ohmic base connection at each of its ends. These are designated *base 1* and *base 2*. A PN junction is created in the bar near base 2 and is designated the emitter (E). This junction acts simultaneously as an emitter and as a collector when the UJT is in operation. When the device is biased in the manner shown in Fig. 5-1 (A), the

portion of the bar between base 1 and the junction provides the emitter action, whereas the portion between the junction and base 2 acts as a collector. This action is detailed in the following paragraphs.

When switch S is open, current I_{B2} from DC supply V_{BB} flows—from base 1 to base 2—through the silicon bar. In this state, the bar acts only as a resistance, and an approximately linear voltage gradient is set up; that is, the voltage drop between base 1 and any point along a straight line between the bases is proportional to the distance from base 1 to that point. The voltage opposite the PN junction is higher than $\frac{1}{2}V_{BB}$, since the junction is more than halfway along the bar.

The DC supply V_{EE} is poled such that the P part of the emitter junction is positive with respect to base 1. When switch S is closed, forward current therefore flows through the junction, and holes are injected into the bar. Thus, the PN junction becomes an emitter. This hole current lowers the resistance of the bar between the emitter and base 1 and alters the voltage gradient.


If V_{EE} and V_{BB} are correctly proportioned, the P-region then will be biased positive over its half nearest base 1, and this half will act as an emitter; and the P-region will be biased negative over its half nearest base 2, and this half will act as a collector. In this way, the single junction functions simultaneously as emitter and collector.

When emitter current I_E is varied by adjusting voltage V_{EE} from a small negative value, through zero, to the maximum allowable positive value, a response characteristic similar to Fig. 5-1 (B) is obtained: The resulting emitter-to-base-1 voltage (V_E) increases with I_E from zero at point 1 to the *peak point* at 2, then decreases to the *valley point* at 3, and finally increases (as from 3 to 4) as I_E further increases. The portion of the curve between 2 and 3 shows negative resistance, since here an increasing current produces a decreasing voltage drop. It is this negative-resistance characteristic that suits the UJT to its classic applications. On each side of the negative-resistance region, there is a conventional, positive-resistance region (1 to 2, and 3 to 4).


Figure 5-1 (C) shows the UJT circuit symbol.

PULSE GENERATOR


Figure 5-2 shows the circuit of a simple pulse generator comprised by a UJT oscillator (type 2N2420, Q) and a silicon

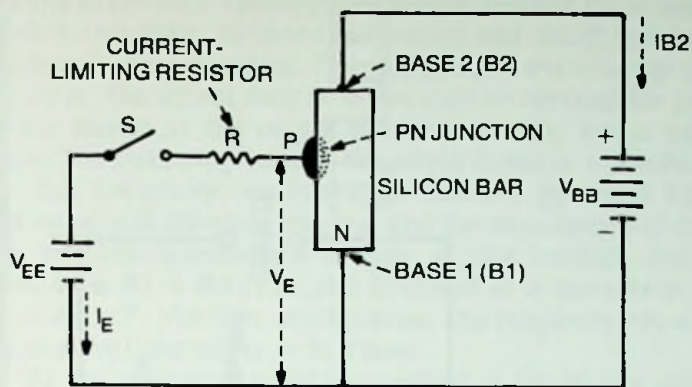

(A) STRUCTURE

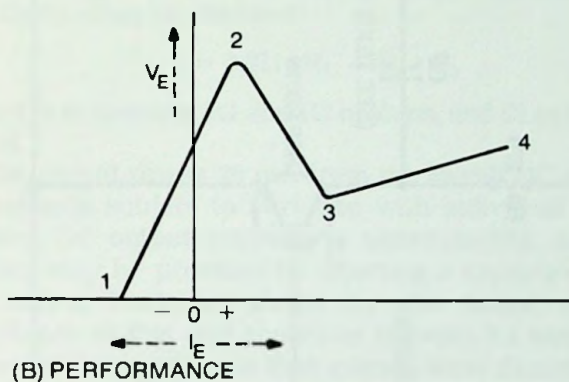

(B) PERFORMANCE

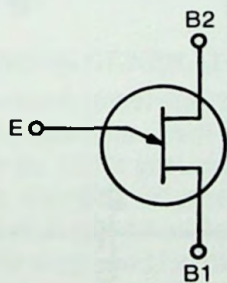

(C) CIRCUIT SYMBOL

Fig. 5-1. Details of unijunction transistor.

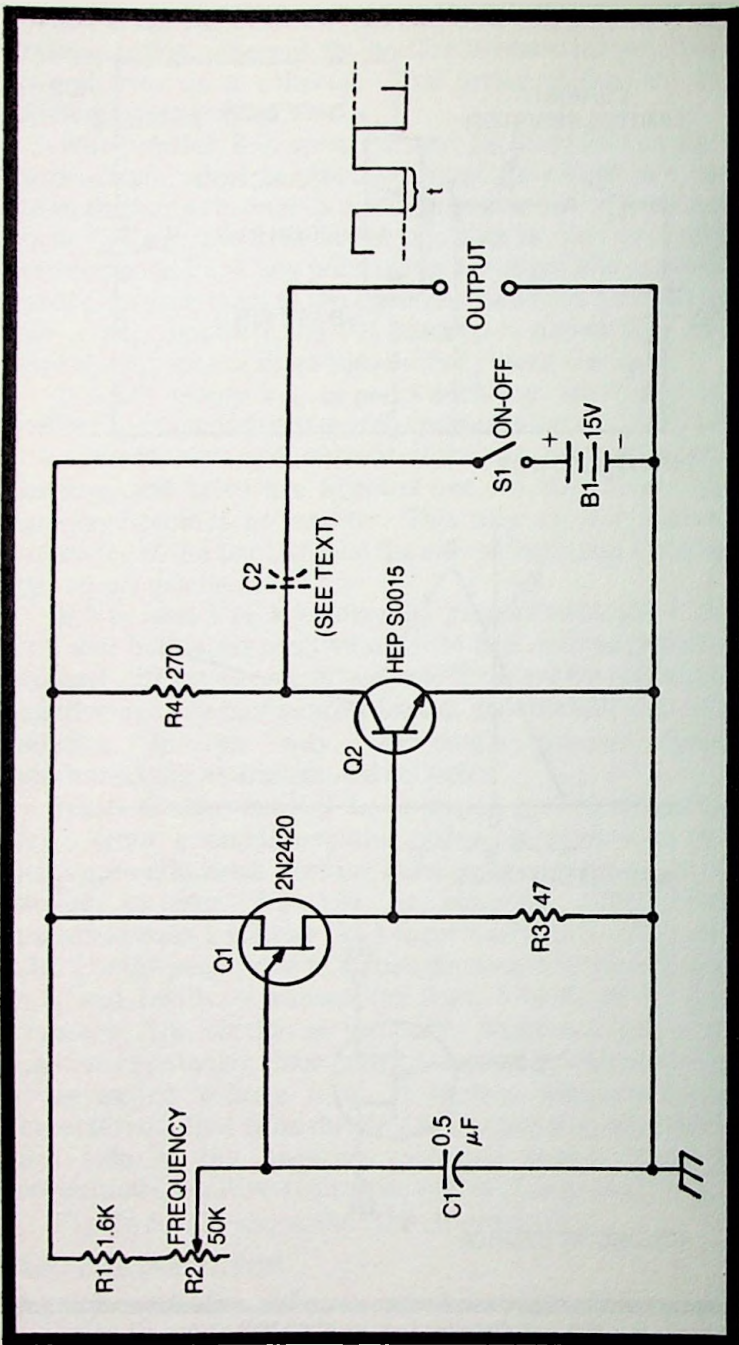


Fig. 5-2. Pulse generator.

bipolar output transistor (type HEP 50015, Q2). The output voltage of the UJT, taken across 47-ohm resistor R3, drives the bipolar transistor between saturation and cutoff, producing flat-topped output pulses. Depending upon the *time off* (t) of the wave, the output may be either narrow rectangular pulses or (as shown at the *output* terminals in Fig. 5-2) a square wave. The peak amplitude of the output signal is +15 volts.

The frequency, or repetition rate, is governed by the setting of a 50,000-ohm rheostat and the capacitance of C1. At the maximum-resistance setting of this control, the full resistance $R1 + R2$ (i.e., 51.6 kilohms) is in the circuit with $C1 = 0.5 \mu\text{F}$. For this combination, the frequency (f) = 47.2 Hz, and the time off (t) = 21.2 msec.

At the minimum-resistance setting of R2, ideally only R1 (1.6 K) is in the circuit; and for this condition, $f = 1522$ Hz, and $t = 0.66$ msec. For other frequency ranges, R1, R2, or C1—or all of them—may be changed:

$$t = 0.821 (R_1 + R_2) C_1$$

where t is in seconds, R1 and R2 in ohms, and C1 in farads, and $f = 1/t$.

The circuit draws 20 mA from the 15-volt DC supply, but this value is subject to variation with individual UJTs and bipolars. DC output coupling is shown in Fig. 5-2, but AC coupling may be provided by inserting a capacitor C2 in the high *output* lead, as shown by the dotted symbol. The capacitance of this unit should be between 0.1 and 1 μF , the best value being the one that causes least distortion of the output wave when the generator is operated into a particular desired load device.

PULSE AND TIMING GENERATOR

A simple sawtooth generator with sharp spikes is useful in a variety of applications involving timing, synchronizing, sweeping, and so on. UJTs generate such waveforms in simple and inexpensive circuits. Figure 5-3 shows such a circuit which, though not a precision instrument, will give a good account of itself in shops and low-budget laboratories.

This circuit is essentially a relaxation oscillator, with outputs taken from the emitter and both bases. The 2N2646 UJT is connected in the classic oscillator circuit for these devices. The frequency, or repetition rate, is governed by the

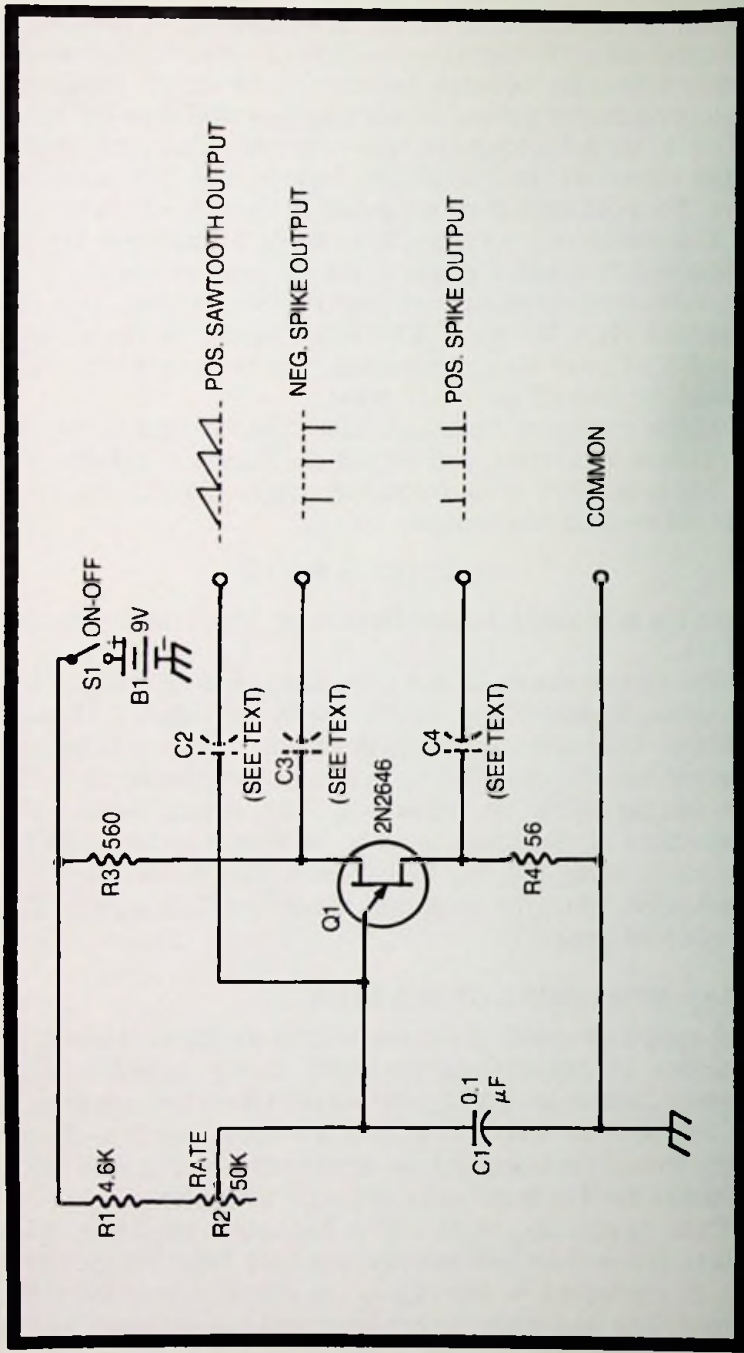


Fig. 5-3. Pulse and timing generator.

setting of the *rate* control rheostat, R2. When this control is set to its maximum-resistance point, the total resistance in series with timing capacitor C1 is the sum of the rheostat and the limiting resistance, R1 (that is, 54.6 kilohms), and the frequency is 219 Hz.

When R2 is set to its lower end, the total resistance ideally is that of resistor R1, or 5600 ohms, and the frequency is 2175 Hz. Other frequency limits and tuning ranges may be obtained by changing R1, R2, C1, or all three.

Positive-spike output is obtained from base 1 of the UJT, negative-spike output from base 2, and positive sawtooth output from the emitter. While DC output coupling is shown in Fig. 5-3, AC coupling may be obtained by inserting capacitors C2, C3, and C4 in the output leads, as shown by the dotted symbols. These capacitances will be between 0.1 and 10 μF , the value selected being determined by the maximum capacitance which can be tolerated with a given load device without degrading the output waveform.

The circuit draws approximately 1.4 mA from the 9-volt DC supply, B1. All resistors are $\frac{1}{2}$ -watt.

FREE-RUNNING MULTIVIBRATOR

The UJT circuit shown in Fig. 5-4 is similar to the relaxation oscillator circuits described in the two preceding sections, except that its constants have been chosen to give quasi-square-wave output resembling that of a conventional astable multivibrator employing transistors or tubes. The type 2N2646 unijunction transistor is a good performer in this arrangement.

Two output signals are provided: a negative-going pulse at base 2 of the UJT (see A in Fig. 5-4), and a positive-going pulse at base 1 (see B). The open-circuit peak amplitude of each of these signals is approximately 0.56-volt, but this may vary somewhat with individual UJTs. The 10,000-ohm rheostat, R2, must be adjusted for desired tilt or flatness of the top of the output wave. This control also affects the frequency, or repetition rate. With the values given here for R1, R2, and C1, the frequency is approximately 5 kHz for a flat-topped peak. For other frequencies, change R1 or C1:

$$f = 1/0.821 RC$$

where f is in Hz, R in ohms, and C in farads.

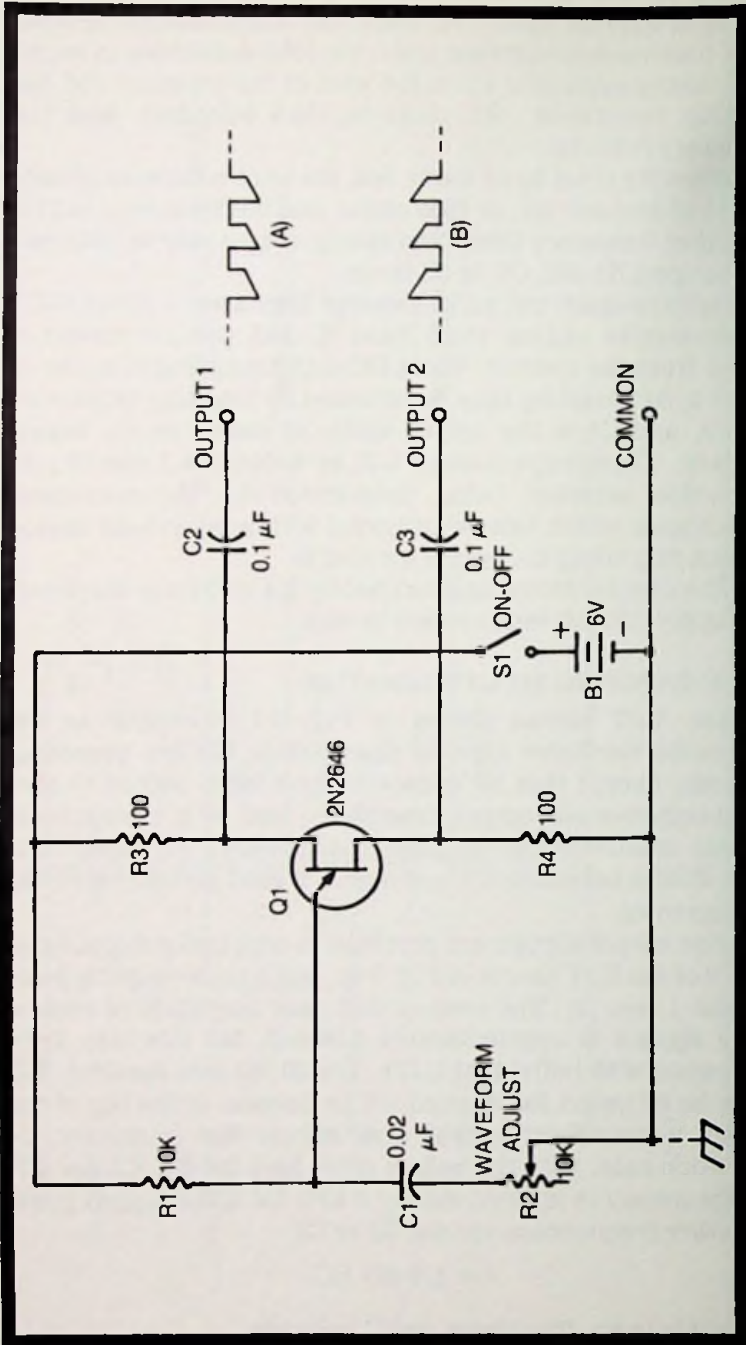


Fig. 5-4. Free-running multivibrator.

The circuit draws approximately 2 mA from the 6-volt DC supply, B1. All fixed resistors are 1/2-watt.

ONE-SHOT MULTIVIBRATOR

Figure 5-5 shows the circuit of a one-shot multivibrator (this device is also called a *single-shot multivibrator* or *monostable multivibrator*). A type 2N2420 unijunction transistor and type 2N2712 silicon bipolar transistor are combined to give a single, constant-amplitude output pulse each time the circuit is triggered by an input pulse. This circuit is adapted from a design by W. Sowa and J. Toole.

In this arrangement, the voltage divider formed by R2, R3, and the base-to-emitter resistance of transistor Q2 charges capacitor C1 making its Q2 end negative and its Q1 end positive. This divider also applies to the emitter of Q1 a positive voltage that is a little lower than the peak voltage of the 2N2420 (see point 2 in Fig. 5-1B).

Initially, Q2 is in the conducting state; therefore, the resulting voltage drop across resistor R4 reduces the voltage at the *output* terminals substantially to zero. When a 20-volt negative pulse is applied to the *pulse input* terminals, Q1 "fires," pulling the emitter side of C1 down to ground and biasing the Q2 base negative. This action cuts off Q1, and the Q1 collector voltage rises rapidly to +20 volts (see the pulse at the *output* terminals in Fig. 5-5).

The voltage remains at this level for the time t taken for capacitor C1 to discharge through resistor R3. The output then falls back to zero, and the circuit rests until another pulse arrives. Time t , and accordingly the width (duration) of the output pulse, depend upon the setting of the *pulse width* control, R3; with the values of R3 and C1 given in Fig. 5-5, the range is 2 μ sec to 0.1 msec, assuming that R3 covers the resistance range 100 to 5000 ohms. Other time ranges may be obtained by changing C1, R3, or both:

$$t = R_3 C_1$$

where t is in seconds, R3 in ohms, and C1 in farads.

The circuit draws approximately 11 mA from the 22.5-volt DC supply, B1, but this may be expected to vary somewhat with individual UJTs and bipolars. All fixed resistors are 1/2-watt.

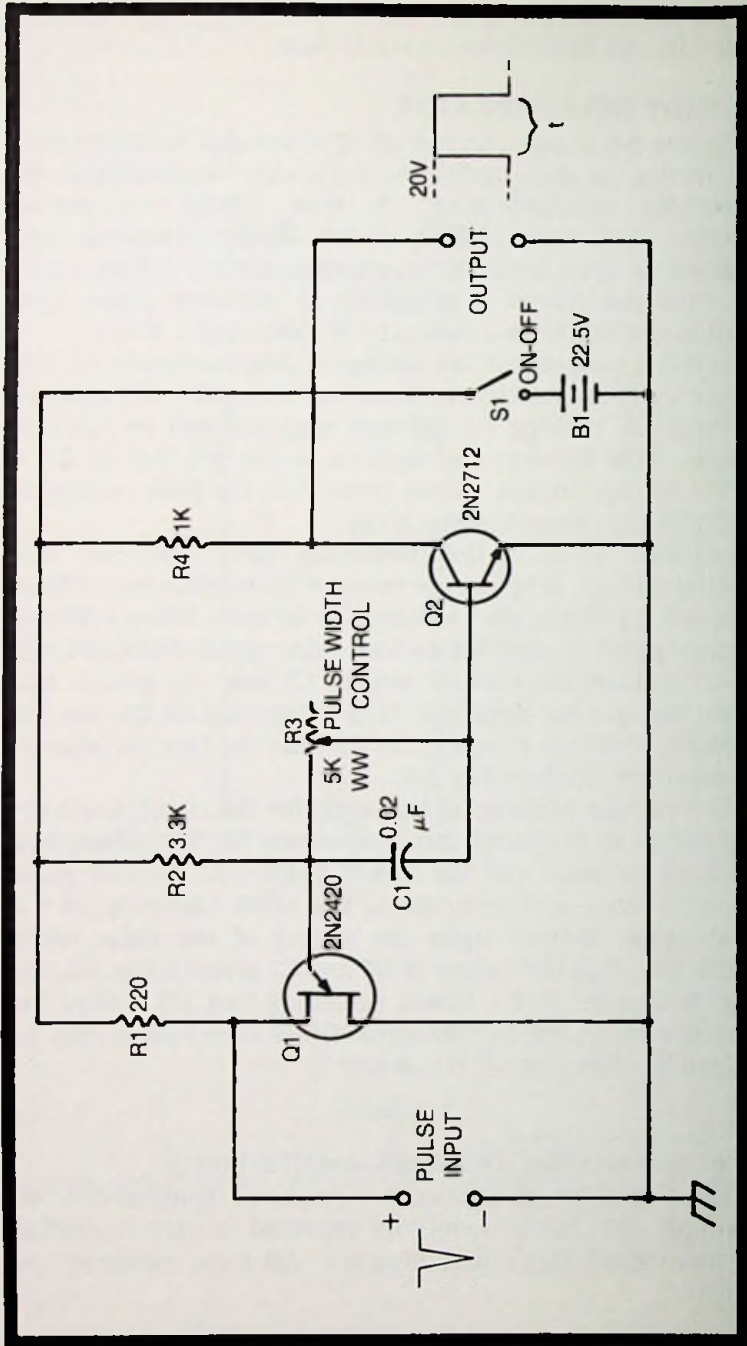


Fig. 5-5. One-shot multivibrator.

RELAXATION OSCILLATOR

A simple relaxation oscillator has a multitude of applications well known to all electronics persons. The unijunction transistor is a notably rugged and dependable active component for use in such oscillators. Fig. 5-6A shows the basic UJT relaxation-oscillator circuit, employing a type 2N2646 unit. The output is a slightly rounded sawtooth wave (Fig. 5-6B) whose peak amplitude is approximately equal to the supply voltage (here, 22.5 volts).

In this arrangement, current flowing from the DC source, B1, through resistor R1 charges capacitor C1. A voltage V_{EE} therefore gradually builds up across C1. When this voltage equals the peak voltage of the 2N2646 (see point 2 in Fig. 5-1B), the UJT "fires." This discharges the capacitor, and the UJT cuts off. The capacitor then recharges, and the events are repeated.

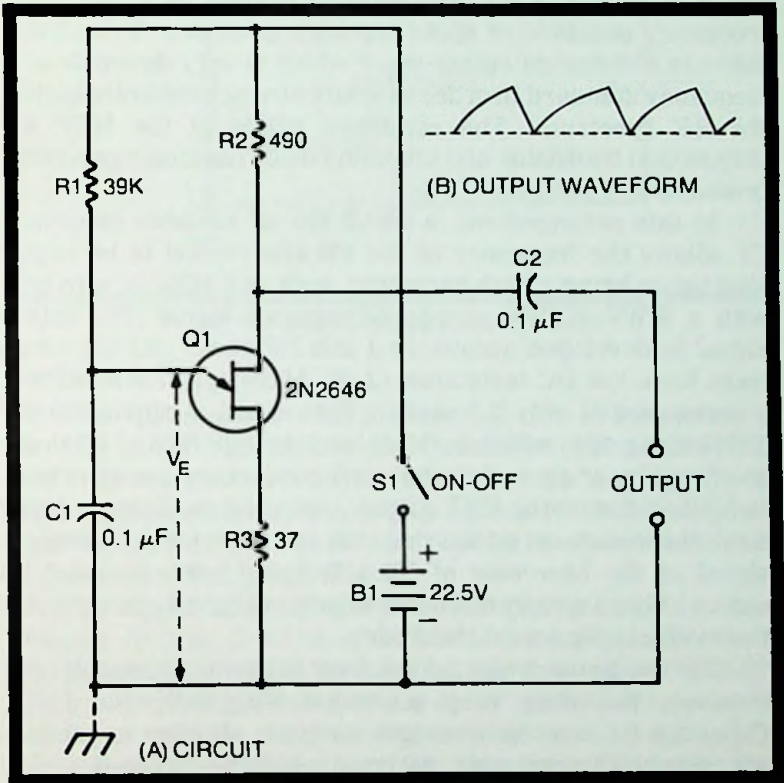


Fig. 5-6. Relaxation oscillator.

The charging and discharging of the capacitor and the resulting switching of the UJT on and off occur at a rate determined by the values of R_1 and C_1 (for the values given in Fig. 5-6, the frequency $f = 312$ Hz). For any other frequency,

$$f = 1 / (0.821 R_1 C_1),$$

where f is in Hz, R_1 in ohms, and C_1 in farads. A rheostat of suitable resistance may be substituted for the fixed resistor, R_1 , if continuously variable frequency control is desired.

All resistors are $\frac{1}{2}$ -watt. Capacitors C_1 and C_2 may be any convenient low-voltage units; however, for good stability, C_1 must be of good quality. The circuit draws approximately 6 mA from the 22.5-volt DC supply, B_1 .

STANDARD-FREQUENCY OSCILLATOR

Figure 5-7 shows the circuit of a 100-kHz crystal oscillator which is usable in the conventional manner as a secondary frequency standard or spot-frequency generator. This circuit delivers a distorted output wave which is very desirable in a frequency standard in order to insure strong harmonics high in the RF spectrum. The combined action of the HEP 310 unijunction transistor and the 1N914 diode harmonic generator produces this distorted wave.

In this arrangement, a small 100 pF variable capacitor, C_1 , allows the frequency of the 100 kHz crystal to be varied slightly, to bring a high harmonic, such as 5 MHz, to zero beat with a WWV/WWVH standard-frequency signal. The output signal is developed across the 1 mH RF choke (RFC1) which must have low DC resistance (J. W. Miller type 73F103AF has a resistance of only 7.5 ohms). This signal is applied to the 1N914 diode (D_1) which is DC-biased through R_3 and R_4 to the most nonlinear part of its forward conduction characteristic, to further distort the UJT output. When the oscillator is being used, the *waveform adjust* rheostat, R_3 , is set for the strongest signal at the harmonic of 100 kHz being used. Resistor R_3 serves only as a current limiter to prevent direct connection of the 9-volt supply across the diode.

The oscillator draws 2.5 mA from the 9-volt DC supply, B_1 ; however, this may vary somewhat with individual UJTs. Capacitor C_1 must be a midget air-type; all other capacitors are mica or silvered mica. All fixed resistors are 1-watt.

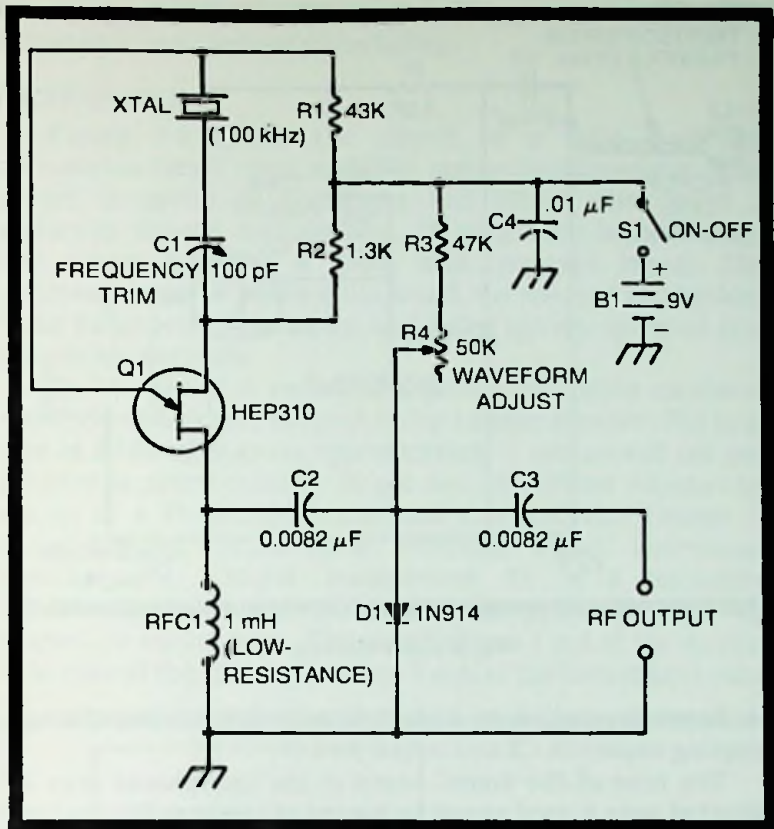


Fig. 5-7. Standard-frequency oscillator.

CW MONITOR

The CW monitor circuit shown in Fig. 5-8 is powered directly by RF pickup from the transmitter being monitored, and delivers an adjustable-tone audio signal to high-impedance headphones. The volume of this tone depends upon the strength of the RF, but will be found adequate even with low-powered transmitters.

The signal is sampled by the RF pickup coil, L1, which consists of 2 or 3 turns of *insulated* hookup wire mounted *rigidly* near the output tank coil of the transmitter. The RF energy is rectified by a shunt-diode circuit, consisting of blocking capacitor C1, diode D1, and filter resistor R1, and the resulting DC is used to power the HEP 310 unijunction transistor in a relaxation oscillator circuit. The output of this

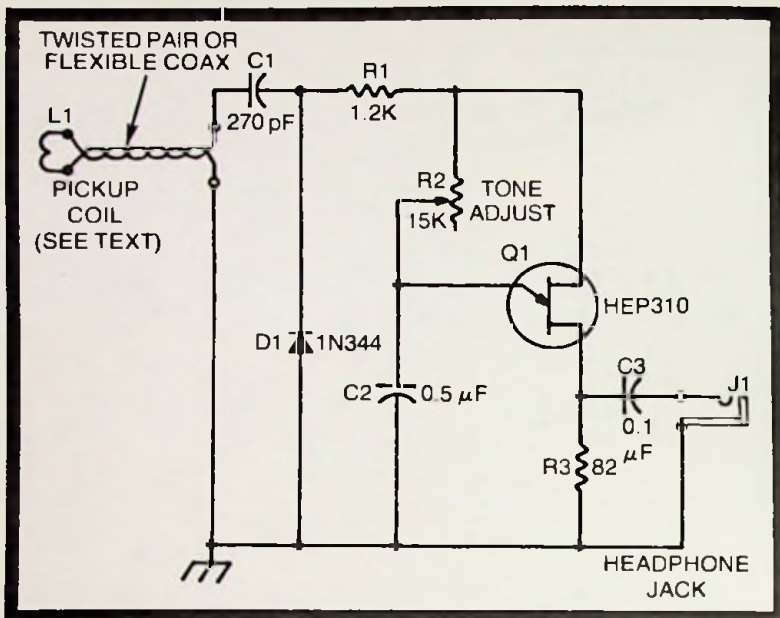


Fig. 5-8. CW monitor.

oscillator is applied to high-resistance headphones through coupling capacitor C3 and output jack J1.

The tone of the signal heard in the headphones may be adjusted over a good range by means of rheostat R2; the tone frequency is approximately 162 Hz when R2 is set to 15,000 ohms, and is approximately 2436 Hz when R2 is set to 1000 ohms. The volume may be controlled by moving L1 nearer to or farther from the transmitter tank; usually, a location will be found that gives satisfactory volume for all general use.

The device may be assembled in a small, grounded metal box. In general, it may be located at any reasonable distance from the transmitter, if good-grade twisted pair or flexible coaxial cable is used and if L1 is coupled to the low end of the tank coil. All fixed resistors are $\frac{1}{2}$ -watt. Capacitor C1 should be rated to withstand safely the maximum DC voltage that might accidentally be encountered in the transmitter; C2 and C3, however, may be any convenient low-voltage units.

This type of RF-powered monitor has some advantage over the usual sine-wave type in that the distorted signal delivered by the UJT circuit is often more pleasing to the ear

over long periods than is the flute-like sinusoidal tone. The distorted tone is certainly less lulling.

METRONOME

Figure 5-9 shows the circuit of a fully electronic metronome based upon a 2N2646 unijunction transistor. This device is useful to musicians and others who desire a uniformly spaced audible beat. Driving a 2½-inch speaker, this circuit provides a good, loud, pop-type signal. The metronome can be made quite small, the speaker and battery being its largest components, and, being battery-operated, it is completely portable.

The circuit is a variable-frequency relaxation oscillator which is transformer coupled to the 3.2-ohm speaker. The beat rate is adjustable from approximately 1 per second (60 per minute) to approximately 10 per second (600 per minute) by means of a 10,000-ohm wirewound rheostat, R2. Volume is adjustable by means of a 1000-ohm, 5-watt, wirewound rheostat, R4. Output transformer T1 is a miniature 125:3.2-ohm unit (Argonne AR-174 with primary center tap unused, or equivalent). The circuit draws 4 mA at the slowest beat rate of the metronome and 7 mA at the fastest beat rate,

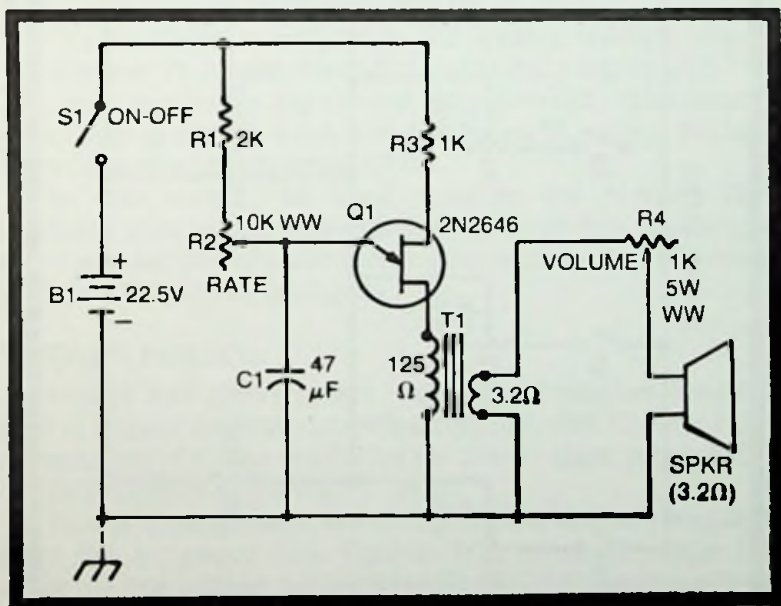


Fig. 5-9. Metronome.

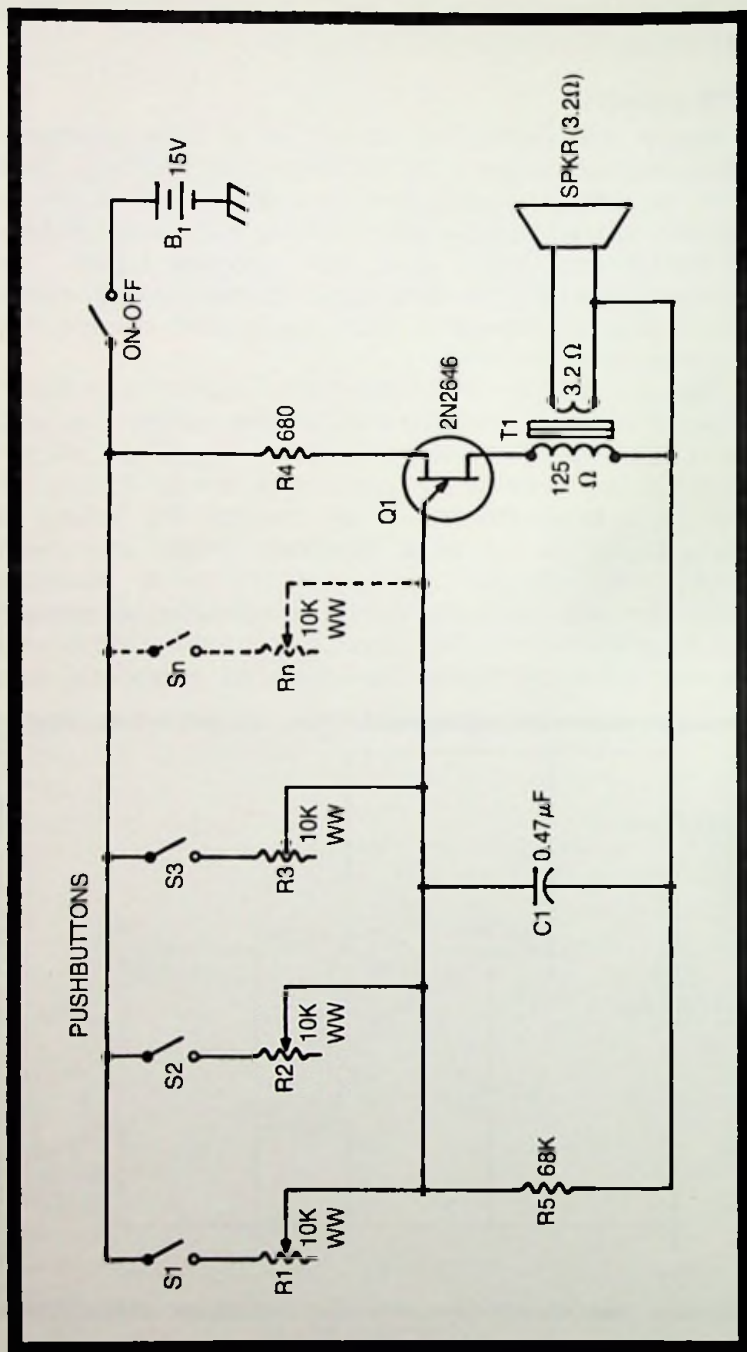


Fig. 5-10. Tone-identified signal system.

but this can vary with individual UJTs. A 22.5-volt battery (B1) will give good service at this low current drain.

Electrolytic capacitor C1 is a 50-volt unit. Resistors R1 and R3 are ½-watt, and rheostats R2 and R4 are wirewound (R4 is 5-watts).

TONE-IDENTIFIED SIGNAL SYSTEM

The circuit in Fig. 5-10 enables a separate tone signal to be obtained from each of several stations. These stations may consist of different doors in a building, different desks in an office, different rooms in a house, or any other places at which pushbuttons may be installed. The place that is signaling can be recognized from its distinctive tone, provided there are not too many stations and that the tones are far enough apart (for example, 400 Hz and 1000 Hz) that they are easily distinguishable by ear.

The circuit is a simple relaxation oscillator employing a type 2N2646 unijunction transistor to produce the signal and drive a loudspeaker. The tone frequency is set by capacitor C1 and one of the 10,000-ohm wirewound rheostats (R1 to Rn). When the rheostat is set to 10,000 ohms, the frequency is approximately 259 Hz; when the rheostat is set to 1000 ohms, the frequency is approximately 2591 Hz.

The oscillator is coupled to the speaker through output transformer T1, a miniature 125:3.2-ohm unit (Argonne AR-174 with primary center tap unused, or equivalent). The circuit draws approximately 9 mA from the 15-volt DC source, B1, but this will vary with individual UJTs.

In this circuit, all fixed resistors are ½-watt. The capacitor may be any convenient low-voltage unit. The wires to the pushbuttons will add some capacitance to C1, but in most instances this will be negligible.

TRIGGER FOR SCR

Figure 5-11 shows how a unijunction transistor may be used to trigger a silicon controlled rectifier. (See Chapter 1 for a discussion of silicon controlled rectifiers.) Here, a type HEP 310 UJT triggers a type HEP R1243 SCR.

In this arrangement, the UJT and SCR both are supplied from the AC power line. Current flow through resistor R4 drops the line voltage sufficiently that the UJT operates within voltage specifications. The timing circuit (R1-R2-C1) likewise

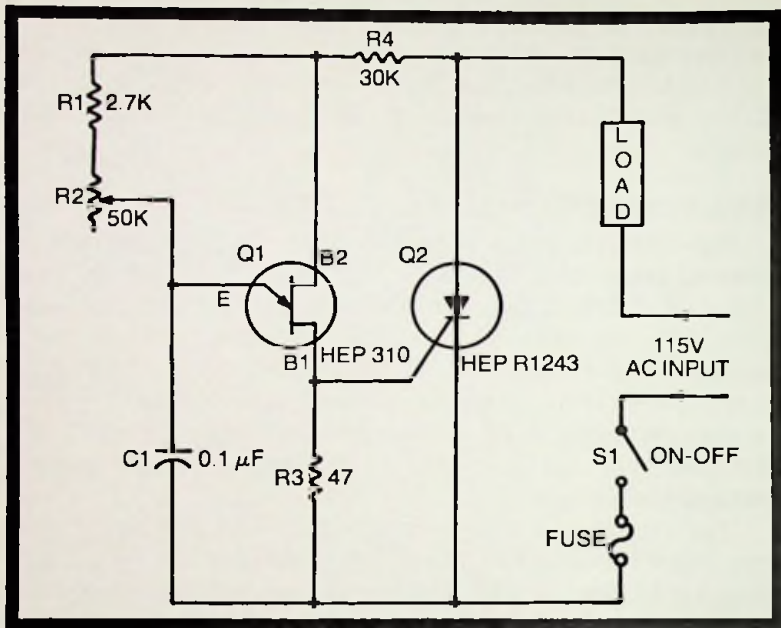


Fig. 5-11. Trigger for SCR.

is operated from the line. The load may be a motor or any other device which is to be operated on the DC output of the SCR.

On the positive half-cycle of line voltage, Q1 "fires" at any instant determined by the time constant of the R1-R2-C1 section and the characteristics of the UJT and switches Q2 into conduction. At the end of this half-cycle, Q2 switches off because of the zero line voltage and remains off during the negative half-cycle. At the same time, capacitor C1 discharges through the internal emitter-to-base-1 path of the UJT. The circuit is then ready to repeat the events.

Adjustment of rheostat R2 allows selection of the instant (point in the positive half-cycle) at which the SCR turns on (the SCR then conducts until the end of the positive half-cycle and all during the negative half-cycle). This phase-controlled action allows easy adjustment of the output current flowing through the load.

In this circuit, all fixed resistors are 1 watt. Capacitor C1 must withstand safely the peak value of the line voltage, and for maximum safety and dependability should be a 600-volt unit.

6

Tunnel Diode TD

The *tunnel diode (TD)* is a 2-terminal negative-resistance device that is simpler than the unijunction transistor. It reduces the complexity of some oscillators, amplifiers, flip-flops, and pulse generators. TDs have greatly simplified the design and construction of dip meters. Tunnel diodes are manufactured in a number of types to meet various demands of current, voltage, and power. Operation at frequencies of 2.2 GHz and higher has been attained with TDs.


Tunnel diodes as negative-resistance devices are always operated with forward bias, that is, with anode positive and cathode negative, and must be biased by a low-resistance DC source. Aside from this requirement, their installation and use impose few special demands.

The single prominent short-coming of the TD is its lack of input-output isolation, and this fault probably accounts for its widespread use in many places where it might dramatically simplify circuits.

Before working with TDs, read the hints and precautions in Chapter 1.


TD THEORY

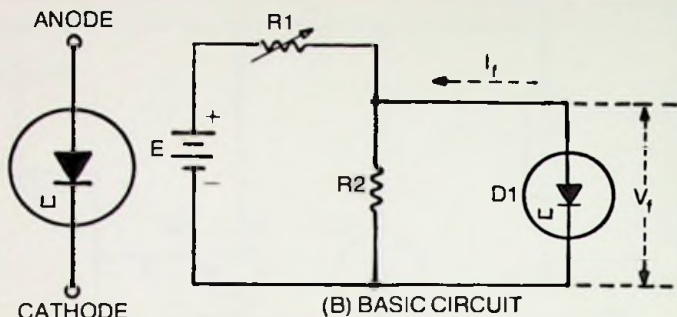The tunnel diode consists of a single, specially processed, highly doped PN junction having an extremely thin depletion layer. It takes its name from the fact that current carriers in



(A) CIRCUIT SYMBOL

(B) BASIC CIRCUIT

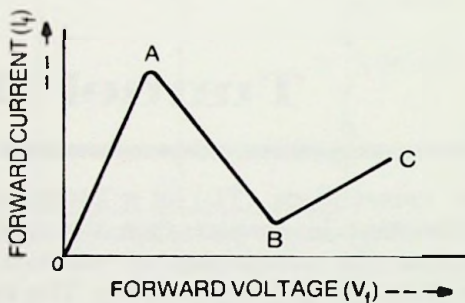

(C) RESPONSE

Fig. 6-1. TD basics.

this device behave as if they tunnel under the barrier, rather than surmounting it electrically, to appear almost instantly on the other side.

This effect is observable at low forward voltage; but at higher voltage, the TD behaves as a conventional forward-biased diode. In the tunneling region, the fast movement of the current carriers enables the TD to be used at very high frequencies and rapid switching speeds. TDs have been made from silicon, germanium, gallium arsenide, and indium antimonide. Figure 6-1(A) shows the TD circuit symbol.

Advanced mathematics and physics are required for a thorough-going explanation of TD action; however, a simple description of TD behavior can be given with the aid of Fig. 6-1(B) and (C). In Fig. 6-1(B), tunnel diode D1 is forward biased through a voltage divider, R1-R2, operated from the DC supply, E. This is a stiff divider—that is, R2 is very small

(usually not higher than 10 ohms) and the divider current is high—to prevent R1 from masking the negative resistance of the diode, and to provide good voltage regulation.

As the forward voltage, V_f , is increased by adjustment of R1, the forward current, I_f , increases from zero, as shown by Fig. 6-1(C), reaching the *peak point* (A) when V_f is several tens of millivolts. As the forward voltage is increased further, the current decreases from A to the *valley point* (B). And as the voltage is increased still further, the current again increases, as from B to C.

At the peak point, the current may be a fraction of a milliampere to several tens of mA, depending upon make and model of the diode. The portion of the curve from A to B depicts negative resistance, since here an increasing voltage produces a decreasing current. It is this negative-resistance characteristic that enables the TD to oscillate in a suitable circuit, and also to amplify. The TD is the simplest device that can amplify or oscillate without being DC overloaded.

At very low forward voltage, the diode current results from the tunneling action described above, and increases from zero to A in Fig. 6-1(C). After the peak voltage is reached, the current decreases with further increase in voltage, as the tunneling action diminishes (A to B in Fig. 6-1C). And as the voltage is increased still further, normal forward current flows through the diode (B to C and beyond).

GENERAL-PURPOSE AF-RF OSCILLATOR

The tunnel diode permits a very simple oscillator circuit, consisting merely of the biased diode in series with a tuned tank. Figure 6-2 shows such an oscillator, which can operate on either audio or radio frequencies, depending upon the inductance and capacitance of the tuned circuit. The 1N3720 tunnel diode in this circuit is useful to 1.6 GHz.

In this arrangement, the frequency is determined by the values of inductor L1 and capacitor C2. These may be selected with the aid of the following relationships:

$$L_1 = 1/(39.5f^2 C_2)$$

$$C_2 = 1/(39.5f^2 L_1)$$

and

$$f = 1/(6.28\sqrt{L_1 C_2})$$

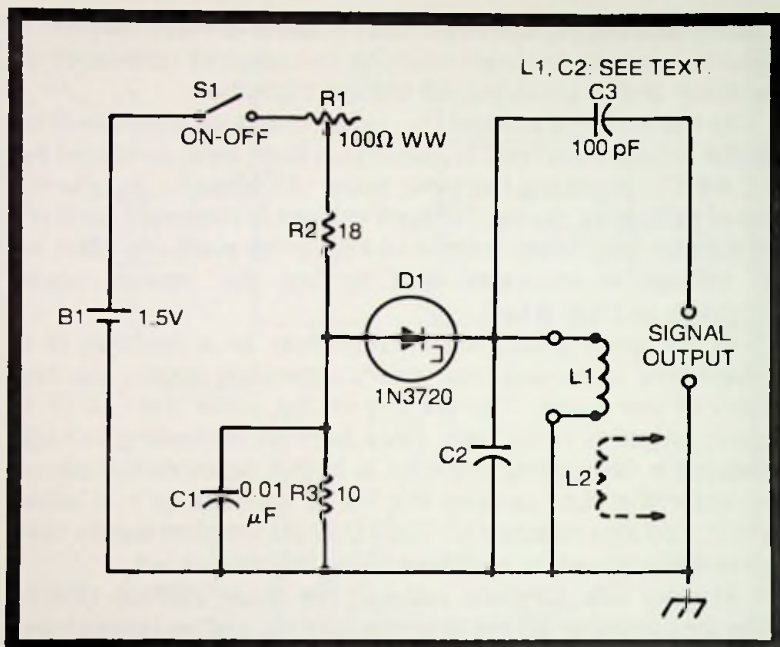


Fig. 6-2. General-purpose AF-RF oscillator.

where in each instance $C2$ is in farads, $L1$ in henrys, and f in hertz. In general, $L1$ will be coreless (or provided with a special HF core of ferrite or other material) for radio frequencies, and will be iron-cored for audio frequencies. Any inductor used in this circuit must have low DC resistance, in order that the negative-resistance characteristic of the tunnel diode will not be affected by this resistance.

The waveform of the output signal is approximately sinusoidal. Simple capacitance coupling is shown in Fig. 6-2. The 100 pF capacitor ($C3$) is a good compromise value for AF and RF. But this value may be varied to suit individual requirements. Light loading of the oscillator is imperative for two reasons: to prevent pulling the circuit out of oscillation, and to prevent shifting the frequency.

For these reasons, use the lowest capacitance ($C3$) that will allow the desired output voltage to be obtained.

The circuit is adjusted by carefully reducing the resistance setting of rheostat $R1$ to set the TD voltage to a point midway between the peak and valley points on the diode characteristic (see points A and B in Fig. 6-1C). At this point,

the circuit will oscillate most vigorously (as shown by an electronic AC voltmeter or similar indicator connected to the *signal output* terminals) and will also go readily in and out of oscillation as switch S1 is opened and closed.

In this circuit, all fixed resistors are ½-watt. Rheostat R1 is wirewound. Capacitors C1 and C3 may be any convenient low-voltage units, but C2 must be of good quality (use silvered mica for radio frequencies) for frequency stability.

If inductive, rather than capacitance, coupling is desired, use a secondary coil, such as L2 shown in dotted lines.

CRYSTAL OSCILLATOR

Figure 6-3 shows the circuit of a TD crystal oscillator employing a 1N3712. This circuit offers good stability and low-impedance output.

In this circuit, the inductance of slug-tuned inductor L1 and the capacitance of capacitor C2 must be chosen for resonance at the crystal frequency:

$$L_1 = 1/(39.5f^2 C_2)$$

and

$$C_2 = 1/(39.5f^2 L_1)$$

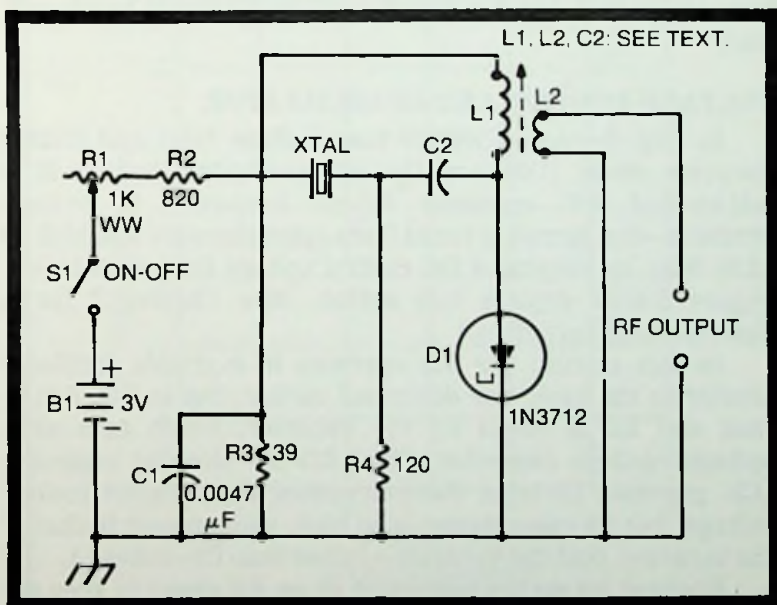


Fig. 6-3. Crystal oscillator.

where L_1 is in henrys, C_2 in farads, and f in hertz. The output coupling coil, L_2 , consists of 2 turns of insulated wire closewound around the bottom end of L_1 . It is convenient to use commercial coils for L_1 , since these units offer a wide variety of inductance ranges. Thus for a crystal frequency of 3500 kHz and a C_2 value of 100 pF, L_1 must be adjusted to 20 μH , and a satisfactory coil would be one such as J. W. Miller No. 20A225RBI which has an inductance adjustment range of 15.2–26.4 μH . The DC resistance of any inductor used must be low, since the TD current must flow through this unit, and a high coil resistance could cancel the negative resistance of the TD. The coil cited above has a maximum DC resistance of 2.1 ohms.

To adjust the circuit, close switch S_1 and adjust rheostat R_1 for strong oscillation, as indicated by an electronic AC voltmeter connected to the *RF Output* terminals. Adjust inductor L_1 for peak deflection of the meter. The oscillations should start readily when switch S_1 is closed; if starting is sluggish, readjust R_1 to correct this condition (the optimum setting will vary with individual TDs).

In this circuit, all fixed resistors are $\frac{1}{2}$ -watt; rheostat R_1 is wirewound. Capacitor C_1 may be any convenient low-voltage unit, but, for circuit stability, C_2 should be silvered mica.

VOLTAGE-CONTROLLED RF OSCILLATOR

In Fig. 6-4(A), a 1N3929 tunnel diode (D_1) and 1N2939 varactor diode (D_2) are the semiconductor devices in a self-excited RF oscillator whose frequency is voltage sensitive—the circuit is tuned from approximately 6.98 MHz to 12.58 MHz by varying a DC control voltage from zero to +6. Figure 6-4(B) depicts this action. (See Chapter 7 for a description of varactors.)

In this circuit, the TD operates in a simple oscillator similar to the basic one described earlier; but in Fig. 6-4(A) tank coil L_1 is tuned by the varactor, which acts as a voltage-variable capacitor. The 0.025 μF blocking capacitor (C_2) prevents L_1 from short-circuiting the varactor control voltage, but its capacitance is so high, with respect to that of the varactor, that the varactor—rather than C_2 —tunes L_1 .

Resistor R_4 serves somewhat as an RF choke to keep the radio-frequency energy from the oscillator out of the DC

control voltage supply. Varying the control voltage from zero to 6 volts varies the capacitance of the 1N2939 varactor diode from approximately 260 pF to 82 pF. (Note that increasing the DC voltage reduces the 1N2939 capacitance.) Inductor L1 is a

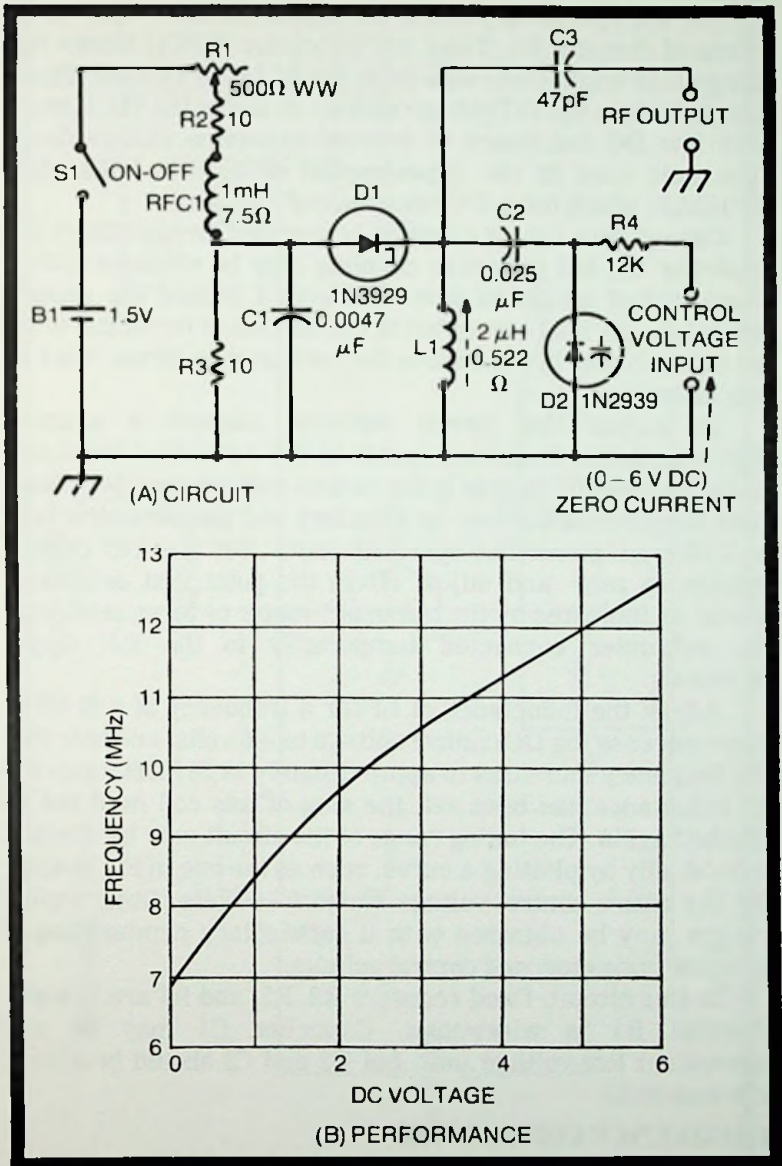


Fig. 6-4. Voltage-controlled RF oscillator.

slug-tuned coil adjustable to $2 \mu\text{H}$. The DC resistance of the coil must be low; otherwise, this resistance will mask the negative resistance of the tunnel diode and the circuit will not oscillate. (Miller No. 20A226RBI coil has a DC resistance of only 0.522 ohm.)

The DC operating point of the tunnel diode is adjusted by means of rheostat R1. The 1 mH RF choke (RFC1) blocks RF energy that might otherwise enter the B1 battery circuit. Since this choke is in the DC voltage divider circuit of the TD, it must have low DC resistance to prevent excessive voltage drop. (The unit used in the experimental setup was Miller No. 73F103AF, which has a DC resistance of 7.5 ohms.)

Capacitance output coupling is provided through the 47 pF capacitor C3, but inductive coupling may be obtained with a 2-turn coil of insulated wire closewound around the ground end of L1. Any load connected to the *RF output* terminals must not be such that it will detune the oscillator or throw it out of oscillation.

To adjust the circuit initially, connect a suitable high-impedance frequency meter to the *RF output* terminals and a variable DC supply to the *control voltage input* terminals (this supply should either be a battery and potentiometer or a *well-filtered* power-line-operated unit). Set the DC control voltage to zero and adjust R1 to the point that oscillation starts, as indicated by the frequency meter or by an electronic AC voltmeter connected temporarily to the *RF output* terminals.

Adjust the inductance of L1 for a frequency of 6.98 MHz. Then increase the DC control voltage to +6 volts, and note that the frequency increases to approximately 12.58 MHz. Once the L1 inductance has been set, the slug of this coil need not be touched again. The tuning range of the circuit may be checked individually by plotting a curve, such as the one in Fig. 6-4(B), for the entire control-voltage range 0–6 volts. Other tuning ranges may be obtained with a satisfactory combination of inductor, varactor, and control voltage.

In this circuit, fixed resistors R2, R3, and R4 are $\frac{1}{2}$ -watt; rheostat R1 is wirewound. Capacitor C1 may be any convenient low-voltage unit, but C2 and C3 should be stable, low-loss units.

FREQUENCY CONVERTER

Figure 6-5 shows the circuit of a simple converter (mixer) for use in receivers and test instruments. It is conventional,

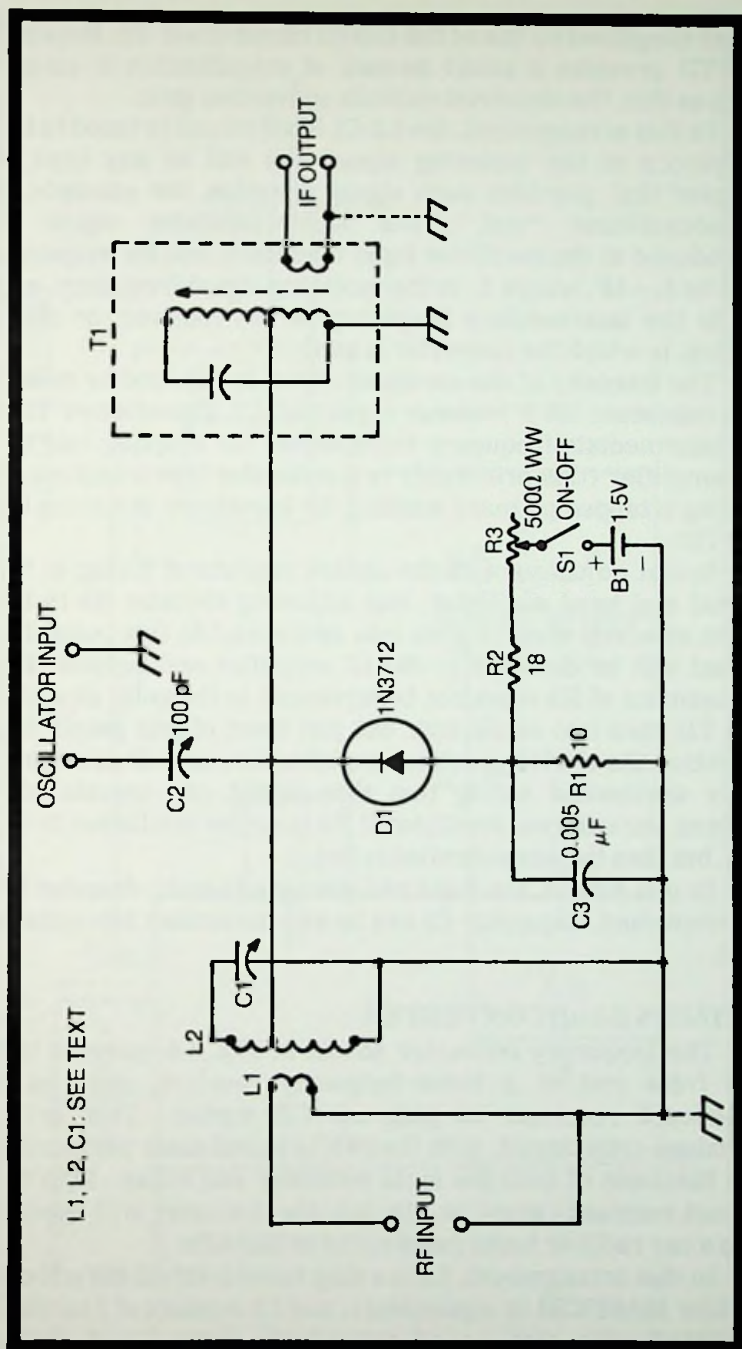


Fig. 6-5. Frequency converter.

but is simplified by use of the 1N3712 tunnel diode, D1. Because the TD provides a small amount of amplification in circuit such as this, the converter exhibits conversion gain.

In this arrangement, the L2-C1 input circuit is tuned to the frequency of the incoming signal and will be any type of coupler that provides such signal selection, for example, a broadcast-band "coil." The local oscillator signal is introduced at the *oscillator input* terminals, and its frequency will be $f_i - IF$, where f_i is the incoming-signal frequency, and IF is the intermediate frequency of the receiver, or other device, in which the converter is used.

The intensity of the oscillator signal is adjusted by means of a miniature 100 F trimmer capacitor, C2. Transformer T1 is an intermediate-frequency transformer for coupling into the IF amplifier (this preferably is a transistor-type transformer having a tapped primary winding for impedance matching for the TD).

Initial adjustment of the circuit consists of tuning-in the signal and local oscillator, and adjusting rheostat R3 to the point at which the TD goes into operation. At this point, the signal will be detected in the IF amplifier and beyond. The adjustment of R3 must not be advanced to the point at which the TD goes into oscillation, but just short of this point; it is then that the 1N3712 provides amplification, as well as mixing. It is worthwhile noting that this circuit can operate also without the external oscillator if R3 is set for oscillation in the TD, but then the amplification is lost.

In this circuit, the fixed resistors are ½-watt; rheostat R3 is wirewound. Capacitor C3 can be any convenient low-voltage unit.

CITIZENS BAND CONVERTER

The frequency converter shown in Fig. 6-6 operates into the front end of a lower-frequency receiver, such as a broadcast receiver, to pick up CB signals. This is an autodyne-type circuit, with the 1N3714 tunnel diode performing the functions of both the local oscillator and mixer. With the circuit constants given in Fig. 6-6, the converter will operate into a car radio or home radio tuned to 1500 kHz.

In this arrangement, L1 is a slug-tuned 0.482–0.680 μ H coil (Miller 40A687CBI or equivalent), and L2 consists of 2 turns of insulated wire closewound around the ground end of L1.

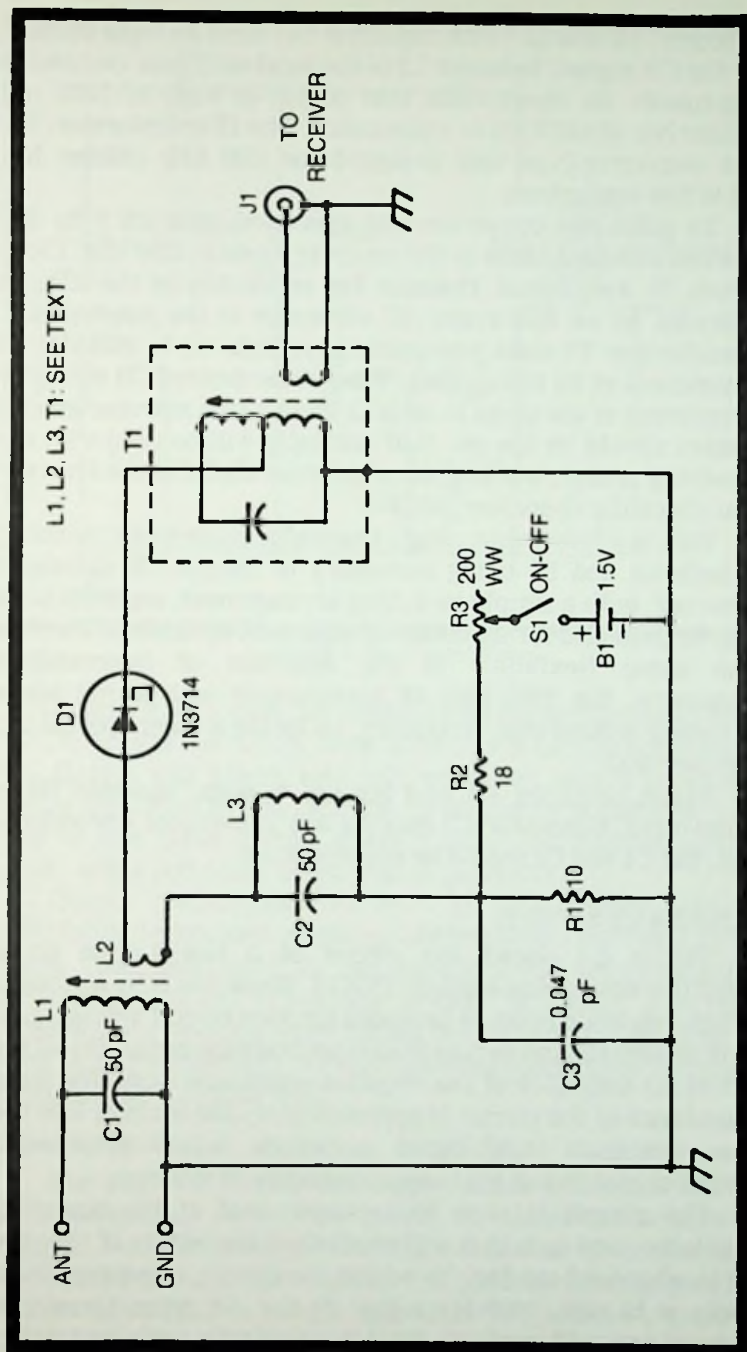


Fig. 6-6. Citizens band converter.

Together, L2 and L2 (with capacitor C1) form an input coupler for the CB signal. Inductor L3 is the local-oscillator coil and is slug-tuned: its range—like that of L1—is 0.482 to 0.680 μH (Miller No. 40A687CBI or equivalent). The IF transformer, T1, is a converter-type unit designed for 1500 kHz (Miller No. 512-WT or equivalent).

To place the converter into operation, connect it by the shortest shielded cable to the receiver tuned to 1500 kHz. Close switch S1 and adjust rheostat for oscillation of the TD, as indicated by an electronic AC voltmeter to the anode of D1. Transformer T1 must previously have been set to 1500 kHz by adjustment of its tuning slug. Tune in the desired CB signal by adjustment of the slugs in coils L1 and L3 (the antenna/ground system should be the one that normally will be used with the receiving setup), working for maximum signal in the receiver into which the converter feeds.

This is a fixed-tune, single-channel arrangement, retuning of both L1 and L3 being necessary to change CB channels. However, with a simple switching arrangement, separate coils may be provided for a number of channels, as desired. There is also some flexibility in the selection of intermediate frequency: the 1500 kHz IF transformer will permit some variation around that frequency, to locate a quiet spot on the receiver dial.

Fixed resistors R1 and R2 are $\frac{1}{2}$ -watt; rheostat R3 is wirewound. Capacitor C3 may be any convenient low-voltage unit, but C1 and C2 should be silvered mica.

AUDIO AMPLIFIER

Figure 6-7 shows the circuit of a tunnel-diode audio amplifier employing a single 1N3712. While this is by no means a high-fidelity circuit, it provides an open-circuit voltage gain of 10 at 1000 Hz and serves to demonstrate the capability of the TD as an amplifier of the negative-resistance type. The input impedance of the circuit is approximately 200 ohms at 1000 Hz. The maximum input-signal amplitude before pronounced output-signal distortion is approximately 10 mV rms.

The circuit is seen to resemble that of the basic TD oscillator; and in fact it will oscillate if the setting of rheostat R3 is advanced too far. To adjust the circuit, close switch S1, apply a 10 mV, 1000 Hz signal to the *AF input* terminals, connect an oscilloscope to the *AF output* terminals, and adjust

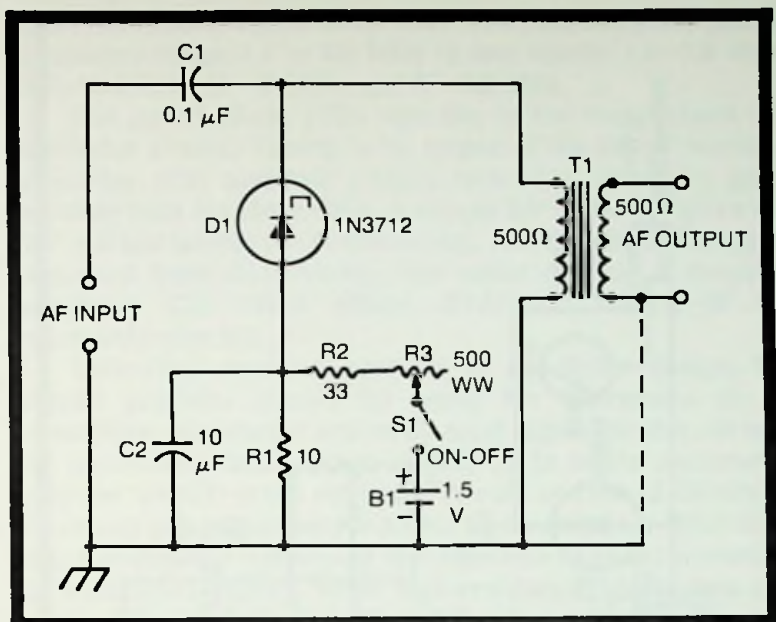


Fig. 6-7. Audio amplifier.

R3 for an output signal, as displayed by the oscilloscope. When the DC bias of the tunnel diode is incorrect for this application, the circuit will break into self-oscillation, which is usually easily identified by the fact that its frequency is different from that of the input signal. Correct bias—and highest voltage gain—is the point just below that of oscillation.

Output transformer T1 is a 1:1 unit having low DC resistance to prevent masking the negative resistance of the diode (the unit used in the experimental setup—Argonne AR-152—has a DC resistance of only 18 ohms). The fixed resistors are ½-watt; rheostat R3 is wirewound. Capacitor C1 may be any convenient low-voltage unit; electrolytic capacitor C2 should be a 25-volt unit.

DIP METER

The vigorous oscillation of the tunnel diode over a wide radio-frequency range, the ability of this device to operate with a 1½-volt battery, and the small size of components associated with the TD—itsself tiny—combine to make possible a dip meter that is simple and small. Figure 6-8 shows the circuit of a dip meter employing a 1N3720 tunnel diode (D1)

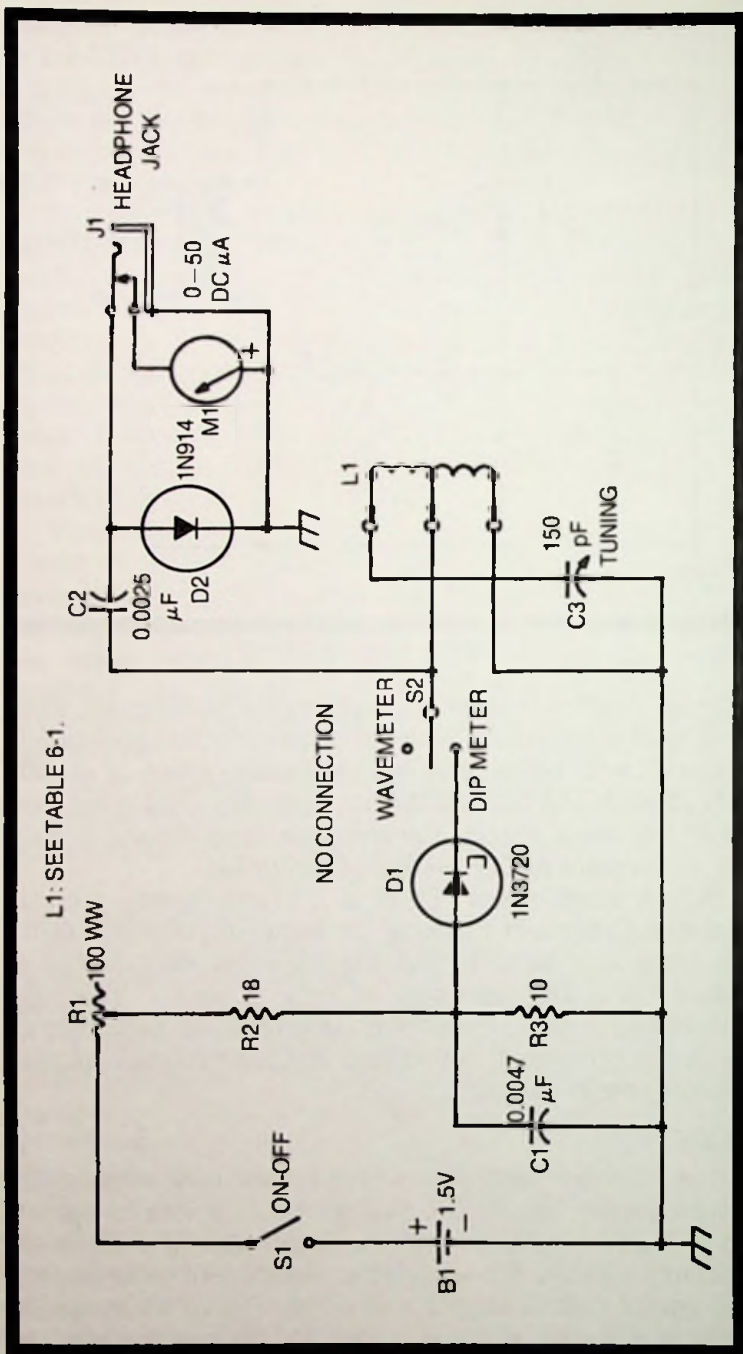


Fig. 6-8. Dip meter.

and 1N914 conventional diode (D2). This instrument covers the frequency range 1.1 to 150 MHz in four bands: 1.1–3.8 MHz, 3.7–12.5 MHz, 12–39 MHz, and 37–150 MHz.

The tunnel diode (TD) operates in the conventional TD oscillator circuit. Tuning is by means of the 150 pF variable capacitor (C3) and four plug-in coils (L1). Table 6-1 gives winding data for these coils. A simple RF meter monitors the RF voltage across the tuned circuit, and dips when energy is absorbed from this circuit. This meter consists of coupling capacitor C2, 1N914 silicon diode D2, and 0–50 DC microammeter M1.

Following standard practice in dip meter design, the circuit provides means for using the instrument as an absorption wavemeter and as an aural signal monitor, as well as dip meter. Thus, when switch S2 is in its *wavemeter* position, the TD is cut out of the circuit, and the L1-C3 circuit functions as a wavemeter with M1 as the indicator. With S2 in this position, the instrument also functions as an aural monitor of modulated signals when high-resistance headphones are plugged into jack J1 (insertion of the phone plug into this jack automatically disconnects the microammeter from the circuit). When switch S2 is in its *dip meter* position and headphones are plugged into jack J1, the instrument functions as a heterodyne frequency meter or CW monitor, with the oscillating TD beating the signal picked up by L1.

In this circuit, both fixed resistors are ½-watt. Capacitors C1 and C2 are mica. Rheostat R1 is wirewound. Jack J1 is a closed-circuit unit, its contacts opening automatically when the phone plug is inserted.

The dip meter may be calibrated in any one of the conventional ways. One of the most often used methods is to couple an unmodulated RF signal source to L1, set the source to a number of selected frequencies, insert headphones, throw S2 to *dip meter*, and tune-in each signal by the zero-beat

Table 6-1. Coil-Winding Data For Dip Meter

BAND A 1.1–3.8 MHz	72 turns No. 32 enameled wire closewound on 1 in. diameter form. Tap 36th turn.
BAND B 3.7–12.5 MHz	21 turns No. 22 enameled wire closewound on 1 in. diameter form. Tap 10th turn.
BAND C 12–39 MHz	6 turns No. 22 enameled wire on 1 in. diameter form. Space to winding length of 7/16 in. Tap 3rd turn.
BAND D 37–150 MHz	Hairpin loop of No. 14 bare copper wire, 2 in. long from end to end, ½ in. spacing between straight sides of hairpin. Tap center of loop.

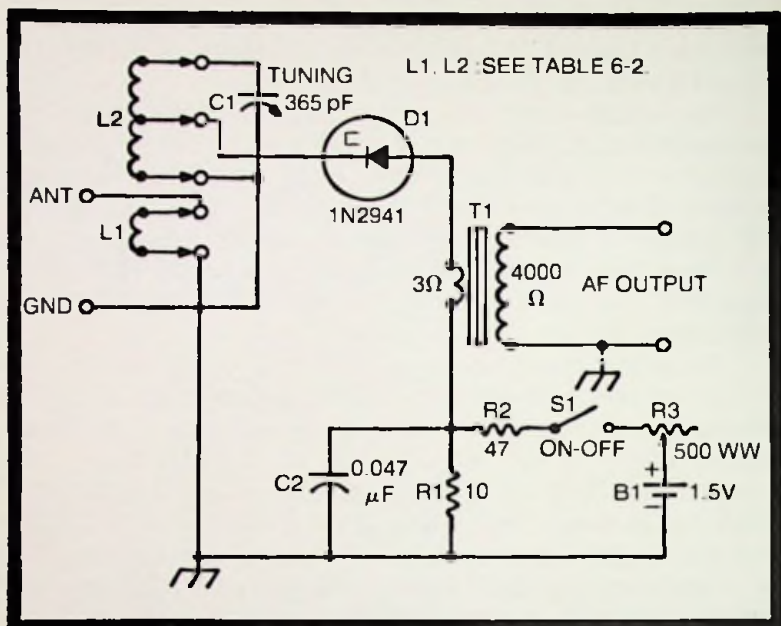


Fig. 6-9. Regenerative receiver.

method. The corresponding frequency then is inscribed on the dial of C3.

REGENERATIVE RECEIVER

The regenerative receiver has a simple circuit, is relatively easy to build and use, and is a quickly assembled emergency device. An all-wave receiver of this type has already been described in Chapter 2, but a somewhat simpler version—employing a 1N2941 tunnel diode (D1)—is presented in Fig. 6-9. This TD circuit requires only a 1.5-volt battery and is capable of extreme miniaturization.

Employing a 365 pF variable capacitor (C1) for tuning, this receiver covers the frequency range 440 kHz to 30 MHz in five bands: 440–1200 kHz, 1–3.5 MHz, 3.4–9 MHz, 8–20 MHz, and 18–30 MHz. Table 6-2 gives winding instructions for the five plug-in coils that are required.

The circuit is basically that of a TD oscillator. The tunnel diode is a tapped down coil L1 for better impedance match and minimum broadening of the tuning. Rheostat R3 can be used to some extent as a regeneration control by using it to adjust operation of the circuit to a point just short of oscillation. The

nonoscillating state is desired for reception of modulated signals. while the oscillating state must be used for CW reception.

Audio output is coupled from the detector by a miniature 3:4000-ohm transformer, T1. The DC resistance of the primary winding of this unit must be very low—otherwise it will mask the negative resistance of the tunnel diode (the transformer used in the experimental setup, Argonne AR-125, has a DC resistance of only 14 ohms). The secondary of the transformer can feed high-resistance headphones or an audio amplifier.

The receiver can be calibrated in the conventional manner, with a signal generator connected to the *antenna* and *ground* terminals, and the dial of tuning capacitor C1 marked off according to selected generator frequencies. Either modulated or CW signals may be used.

In this circuit, the two fixed resistors are ½-watt; rheostat R3 is wirewound. Capacitor C2 may be any convenient low-voltage unit.

FLEA-POWERED CW TRANSMITTER

Figure 6-10 shows the circuit of a very low-power CW transmitter employing a 1N3720 tunnel diode. In spite of its low power (approximately 1.3 milliwatts DC input), this little transmitter can perform surprisingly well when connected to a good outside antenna and operated on a clear channel.

Table 6-2. Coil-Winding Data For Regenerative Receiver

BAND A 440 - 1200 kHz	L1 5 turns No. 32 enameled wire closewound on same form as L2. Space 1/16 in. from ground end of L2.
	L2 187 turns No. 32 enameled wire closewound on 1 in. diameter form. Tap 90th turn from ground end.
BAND B 1 - 3.5 MHz	L1 5 turns No. 32 enameled wire closewound on same form as L2. Space 1/16 in. from ground end of L2.
	L2 65 turns No. 32 enameled wire closewound on 1 in. diameter form. Tap 30th turn from ground end.
BAND C 3.4 - 9 MHz	L1 4 turns No. 26 enameled wire closewound on same form as L2. Space 1/16 in. from ground end of L2.
	L2 27 turns No. 26 enameled wire closewound on 1 in. diameter form. Tap 9th turn from ground end.
BAND D 8 - 20 MHz	L1 2 turns No. 22 enameled wire closewound on same form as L2. Space 1/16 in. from ground end of L2.
	L2 10 turns No. 22 enameled wire closewound on 1 in. diameter form. Tap 5th turn.
BAND E 18 - 30 MHz	L1 2 turns No. 22 enameled wire airwound ½ in. in diameter. Space to winding length of ⅓ in. and mount firmly 1/16 in. from ground end of L2.
	L2 4 turns No. 22 enameled wire airwound ½ in. in diameter. Space to winding length of ¼ inch. Tap 2nd turn.

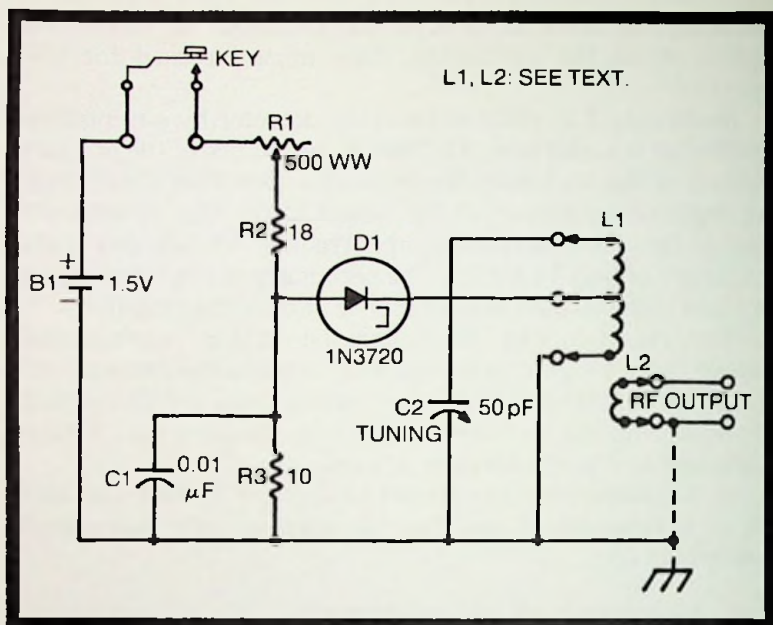


Fig. 6-10. Flea-powered CW transmitter.

The circuit is that of the basic self-excited TD radio-frequency oscillator. The diode is tapped down tuning coil L1 for improved impedance match. Rheostat R1 is adjusted to the point that the TD oscillates vigorously, as indicated by an RF voltmeter connected temporarily to the *RF Output* terminals or by a CW receiver coupled to L1 or connected to the *RF Output* terminals. For the amateur bands, commercial plug-in coils are available for L1 and L2; these should be the center-tapped, end-link type, designed for 50 pF tuning capacitance.

Fixed resistors R2 and R3 are ½-watt; rheostat R1 is wirewound. Capacitor C1 should be mica. All construction and wiring must be solid to guarantee a steady signal.

For better stability than that provided by the self-excited oscillator, the crystal oscillator shown in Fig. 6-3 can be used. For this purpose, substitute the telegraph key for switch S1 in the crystal-oscillator circuit.

REMOTE-CONTROL TRANSMITTER

Figure 6-11 shows a remote-control transmitter that can be built small enough to conceal in the palm of the hand and

which can be used for working radio-controlled models, garage-door openers, and similar devices. This unit is a 27.255 MHz crystal oscillator employing a 1N3716 tunnel diode. A detachable whip antenna (this can be a 1 foot length of stiff copper wire) radiates the control signal when pushbutton switch S1 is depressed. Alternatively, the antenna can consist of several turns of insulated hookup wire wound around the inside of the nonmetallic case of the controller.

The oscillator is tuned to crystal frequency by adjusting the slug in the 0.265–0.330 μH coil, L1. This coil must have very low DC resistance, to prevent masking the negative resistance of the diode (the coil used in the experimental model, Miller No. 40A337CBI, has a DC resistance of only 0.029 ohm).

To adjust the circuit initially, depress S1 and work alternately between the settings of R1 and L1 until the circuit

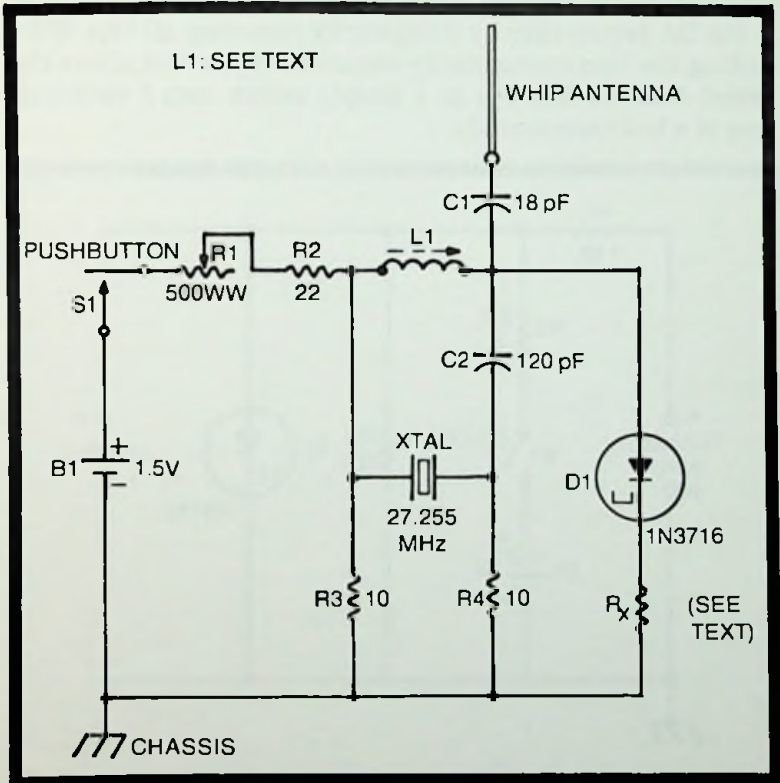


Fig. 6-11. Remote-control transmitter.

oscillates vigorously, as indicated by a CW monitor (see Chapter 5) or receiver. When R1 is correctly adjusted, oscillation will occur readily each time S1 is depressed.

When desired, the oscillator may be amplitude modulated by applying the audio modulating signal to resistor R_x, shown dotted in series with the diode. This resistance will range between 1 and 4.7 ohms, depending upon the available audio power and the characteristics of an individual TD.

TRIGGERED SWITCH

The tunnel diode exhibits two stable states, lying on opposite sides of the negative-resistance region. These stable states lie in the region OA and the region BC in Fig. 6-1(C). If the diode is biased normally in the OA region, then a momentary increase in this bias will switch operation to the BC region, and the diode will continue to operate here even after the bias is reduced to normal. Operation may be returned to the OA region only by temporarily removing all bias or by making the bias momentarily negative. This action allows the tunnel diode to function as a simple switch with a switching time of a few nanoseconds.

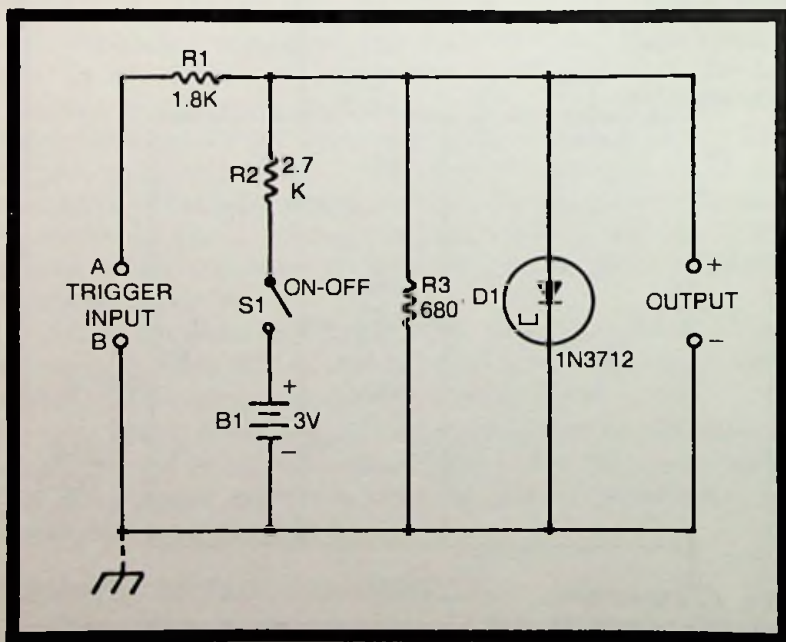


Fig. 6-12. Triggered switch.

Figure 6-12 shows the circuit of a tunnel-diode switching circuit employing a 1N3712 unit. The voltage divider, R1-R2, initially biases the TD to its low-voltage state, and the voltage at the *output* terminals is approximately 55 mV. Then, when a fast, 2-volt pulse is applied at the *trigger input* terminals to make A positive and B negative, the circuit switches rapidly to its high-voltage state, and the voltage at the *output* terminals increases to approximately 250 mV. The output voltage remains at this level until a 2-volt negative pulse is applied to the *trigger input* terminals, whereupon the output voltage is switched back to 55 mV.

An electronic switch of this type has many applications in switching and control systems, logic devices, and memories, where its simplicity recommends it.

In this circuit, all three resistors are $\frac{1}{2}$ -watt. All wiring should be kept as well separated as practicable to prevent pickup and coupling of interference via capacitance between leads.

7

Variable-Capacitance Diode VCD

The *variable-capacitance diode* (VCD) is a junction diode that has been specially processed to make useful the inherent voltage-variable capacitance of reverse-biased PN junctions. The VCD therefore can act as a tiny DC voltage-tuned capacitor in various electronic circuits, such as LC tuners and automatic frequency control systems.

All reverse-biased semiconductor diodes exhibit voltage-variable capacitance, but this capacitance is very small in conventional diodes. In the VCD, capacitance is provided in useful amounts. The VCD is also called a *varactor* or a *voltage-variable-capacitance diode* (VVCD). It is also known by several trade names, such as *Epicap*, *Semicap*, and *Varicap*.

Because the VCD junction is reverse biased, it draws very little current (in some instances less than 1 nanoampere) from the DC control-voltage source, and therefore is to all practical purposes a voltage-controlled—i.e., “zero voltage”—device. Increasing the control voltage to its nominal value (as given by the VCD manufacturer) will decrease the capacitance to one-half its initial (zero-voltage) value. Up to a 10:1 capacitance change is readily obtainable at voltages higher than nominal, however. Depending upon make and model, the Q of a variable-capacitance diode is several hundred at frequencies of several hundred megahertz. Figure 7-1 shows the circuit symbol of the VCD.

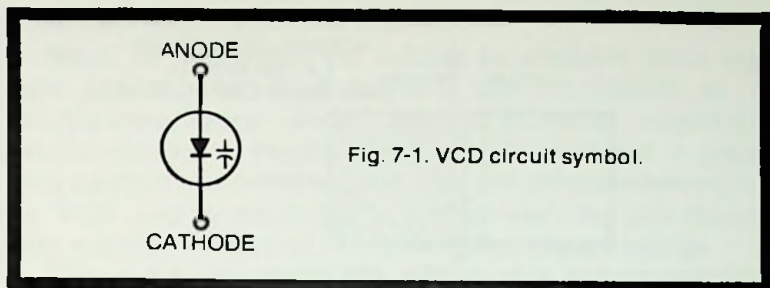


Fig. 7-1. VCD circuit symbol.


Before working with VCDs, read the hints and precautions in Chapter 1.

VCD THEORY


The variable-capacitance diode contains an abrupt PN junction. In every junction, there is a *depletion layer* about the junction, that is, a region in which no current carriers (or, at least, only a trace of them) are present. This layer thus is equivalent to a thin dielectric. The N- and P-regions, which are good conductors, face each other on opposite sides of the depletion layer and act as the two plates of a capacitor with the depletion layer acting as the dielectric of this capacitor.

When no external voltage is applied to the diode, the depletion layer is thin and the junction capacitance is highest (see Fig. 7-2A). But when a reverse DC voltage is applied to the diode (that is, anode negative and cathode positive), the depletion layer widens by an amount proportional to the voltage, and the capacitance decreases (see Fig. 7-2B). It is in this way that a variable DC voltage makes the diode a variable capacitor. The junction being reverse biased, any direct current flowing through the diode from the control-voltage source is minute (usually in the nanoamperes), so virtually no power is required to tune this semiconductor capacitor.

Figure 7-2 (C) shows typical performance of the VCD. From this plot, notice that an increase in voltage from zero to $1\frac{1}{2}$ times the nominal value decreases the capacitance from approximately 260% of nominal capacitance value to approximately 80% of nominal capacitance. This means that a VCD rated at 100 pF at 4 volts would show a capacitance change from 260 pF at zero volts to 80 pF at 6 volts. Common nominal capacitance values for VCDs are given in steps from 6.8 pF to 100 pF, although values of several hundred picofarads

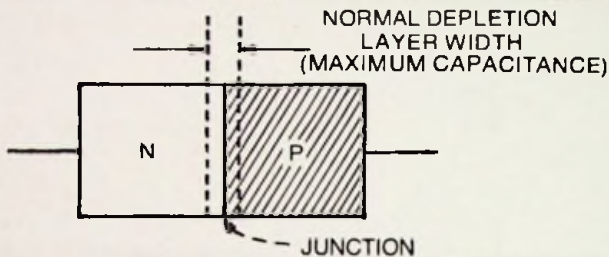

(A) ZERO APPLIED VOLTAGE

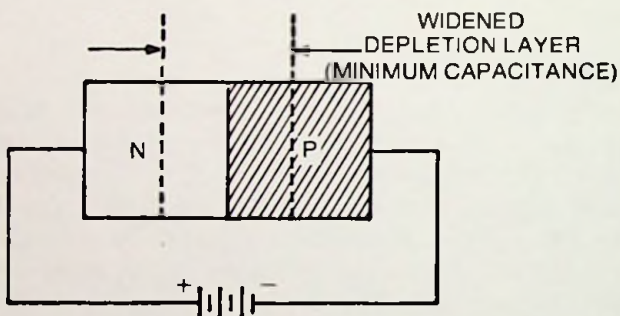

(B) HIGH APPLIED VOLTAGE

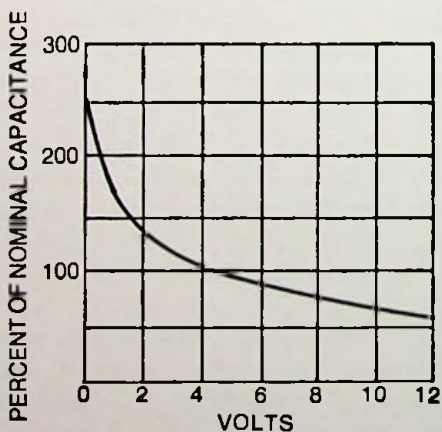


Fig. 7-2. VCD action.

are sometimes manufactured. A common nominal voltage is 4 VDC, and maximum permissible voltages are given in steps from 15 VDC to 150 VDC.

VOLTAGE-VARIABLE CAPACITOR

When an adjustable DC voltage is available from any source, it can be used to vary the capacitance of a variable-capacitance diode, and a DC-tuned miniature variable capacitor results. Such a component has a great many applications in communications and general electronics. Any VCD may be employed in this manner, the unit chosen being selected for desired voltage and capacitance ratings.

Figure 7-3 (A) shows the circuit of a voltage-variable capacitor offering a 4:1 capacitance range. The capacitance seen at the *capacitance* terminals varies from approximately 260 pF to 65 pF as the DC control voltage varies from zero to +12 volts. Figure 7-3(B) details this performance.

In this circuit, the 1-megohm, $\frac{1}{2}$ -watt resistor (R1) isolates AC energy applied to the *capacitance* terminals in applications in which the voltage-variable capacitor is used, keeping it out of the DC voltage source. This resistor replaces the usual choke coil in this function; and since the VCD draws virtually no current in its reverse-biased condition, there is practically no voltage drop across R1.

The 0.01 μ F capacitor (C1) protects the V100EB variable-capacitance diode (D1) from any DC component in the external circuit in which this arrangement is used. Since the capacitance of C1 is large, with respect to that of diode D1, the capacitance seen at the *capacitance* terminals is principally that of the diode. The V100EB diode is rated to withstand a maximum bias of 10 VDC, and at this voltage the reverse leakage current is only 100 nanoamperes.

The AC voltage presented to the *capacitance* terminals must be small, with respect to the DC control voltage; otherwise the AC voltage, instead of the DC, will determine the diode capacitance. In most instances, this will occasion little difficulty, since the signal voltage will ordinarily be small, compared with the 1 to 12 volts for control voltage.

Several VCDs may be connected in parallel to increase the maximum obtainable capacitance. It must be remembered however, that the parallel connection will also increase the minimum capacitance. Thus, five type V100EB units connected in parallel in the circuit of Fig. 7-3 (A) will provide a maximum capacitance (zero VDC) of approximately 1300 pF, and a minimum capacitance (12 VDC) of approximately 325 pF.

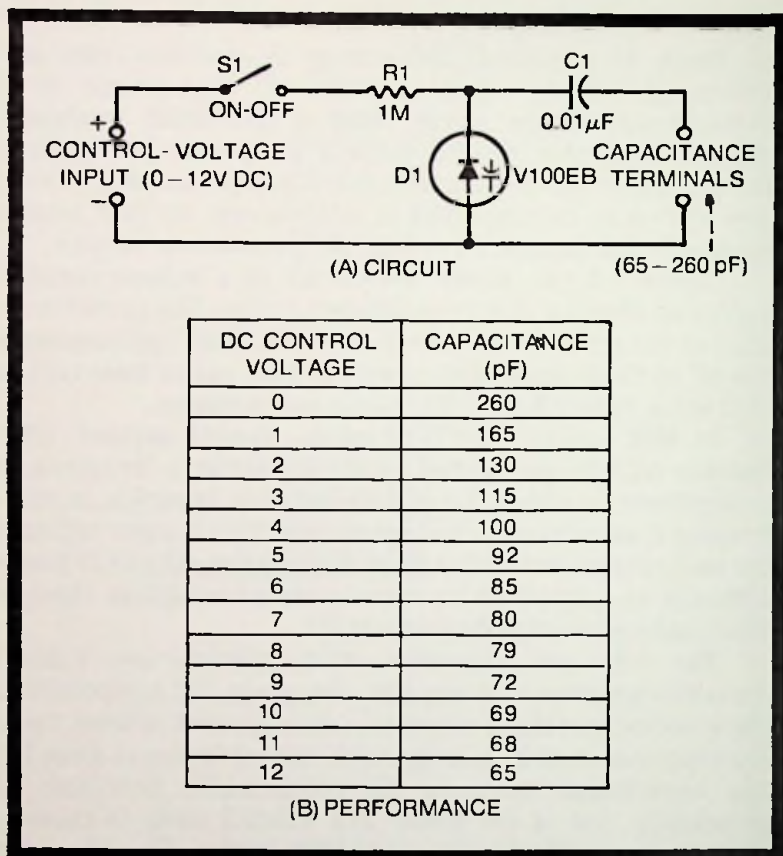


Fig. 7-3. Voltage-variable capacitor.

In short, all of the capacitance values in Fig. 7-3 (B) will be multiplied by 5. At the same time, the leakage current will be 1/5 of the rated value for a single VCD (in this case 20 nanoamperes).

The electronic-type variable capacitor is smaller than the tiniest manually variable capacitor of the same capacitance. Obviously, if a potentiometer is used to vary the capacitance-controlling DC voltage, this potentiometer may well be as large as—or even larger than—an equivalent plate-type capacitor; however, this may be of no moment when the electronic capacitor is to be remotely controlled. In many applications, the variable DC voltage will already be available in a circuit in which the electronic capacitor is used.

VCD-TUNED LC CIRCUITS

Figure 7-4 shows several circuits in which the voltage-variable-capacitance of a VCD is employed to tune an inductance-capacitance (LC) circuit. In these examples, a type V100EB diode is shown. The capacitance of this unit varies from 260 pF when the DC control voltage is zero, to 65 pF when the voltage is 12 (see Fig. 7-3B). Table 7-1 shows the resonant frequencies corresponding to the DC control-voltage value (in steps of 1 volt from zero to 12 volts) for five different values of inductance, L1.

Figure 7-4 (A) is the basic circuit, which is used as is in most applications of VCDs. Here, capacitor C1 prevents short circuit of the DC control voltage by inductor L1. This capacitance is so large, with respect to that of the VCD, that the VCD rather than C1 tunes the inductor. Resistor R1 acts somewhat as an RF choke, blocking the AC signal in the tuned circuit from the DC supply.


Figure 7-4(B) shows how two circuits may be gang-tuned simultaneously by a single DC control voltage. Each of the halves in this circuit is identical with the one in Fig. 7-4(A). While two circuits are shown in Fig. 7-4(B), the method may be extended to as many stages as required, all being tuned by a single potentiometer or by a single available variable DC voltage. Figure 7-4(C) contains an additional tuning capacitor, C2. Whereas the VCD is the lone tuning capacitor in 7-4A and (B), in 7-4C it is a voltage-controlled trimmer for fine-tuning the frequency in response to a DC error signal or manually adjusted DC voltage. Here, the circuit is tuned principally by

Table 7-1. VCD-Tuned Circuit Data


Type V100EB Diode

DC CONTROL VOLTAGE	RESONANT FREQUENCY				
	L1 = 10 mH	L1 = 1 mH	L1 = 100 μ H	L1 = 10 μ H	L1 = 1 μ H
0	98.7 kHz	312 kHz	987 kHz	3.12 MHz	9.87 MHz
1	124 kHz	392 kHz	1.24 MHz	3.92 MHz	12.4 MHz
2	139 kHz	441 kHz	1.39 MHz	4.41 MHz	13.9 MHz
3	148 kHz	469 kHz	1.48 MHz	4.69 MHz	14.8 MHz
4	159 kHz	503 kHz	1.59 MHz	5.03 MHz	15.9 MHz
5	166 kHz	525 kHz	1.66 MHz	5.25 MHz	16.6 MHz
6	173 kHz	546 kHz	1.73 MHz	5.46 MHz	17.3 MHz
7	178 kHz	563 kHz	1.78 MHz	5.63 MHz	17.8 MHz
8	179 kHz	566 kHz	1.79 MHz	5.66 MHz	17.9 MHz
9	187 kHz	593 kHz	1.87 MHz	5.93 MHz	18.7 MHz
10	192 kHz	606 kHz	1.92 MHz	6.06 MHz	19.2 MHz
11	193 kHz	610 kHz	1.93 MHz	6.10 MHz	19.3 MHz
12	197 kHz	624 kHz	1.97 MHz	6.24 MHz	19.7 MHz

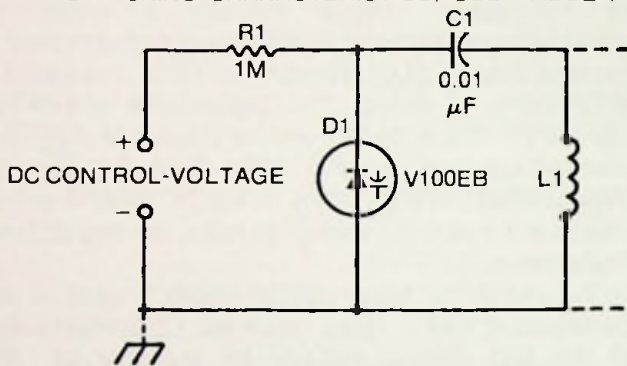
FOR TUNING CHARACTERISTICS, SEE TABLE 7-1.



(A) SINGLE TUNED CIRCUIT

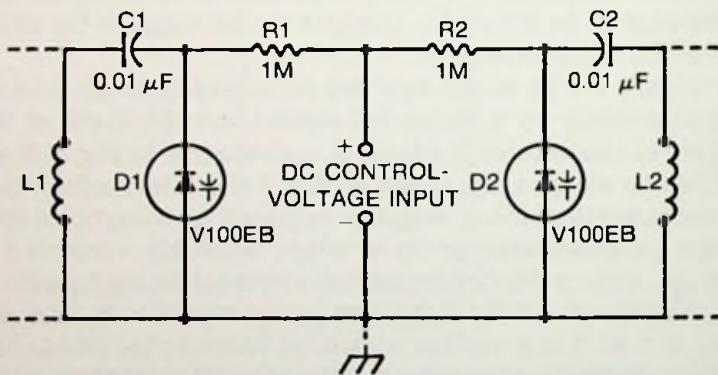

(B) TUNED CIRCUIT PAIR

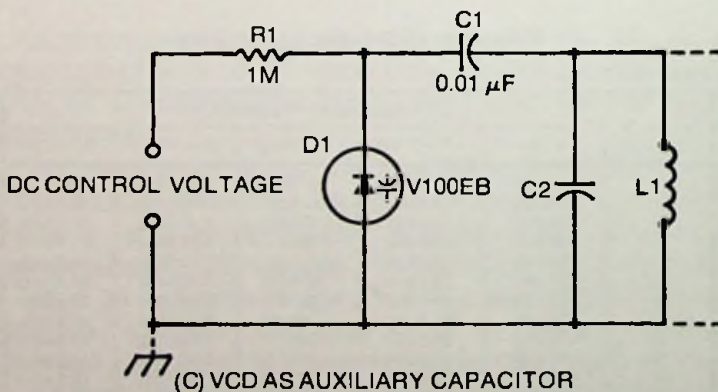

(C) VCD AS AUXILIARY CAPACITOR

Fig. 7-4. VCD-tuned LC circuits.

means of conventional variable capacitor C2. The capacitance of the diode is effectively in parallel with C2 and therefore can retune the circuit above and below the point established by the setting of C2. In practice, the diode capacitance is chosen considerably lower than that of capacitor C2, thus insuring that C2 is the dominant frequency-determining capacitance.

The circuits in Fig. 7-4, and logical modifications of them, find use in receivers, transmitters, instruments, and control devices. When the scheme in Fig. 7-4(B) is extended to several stages, a small voltage-controlling potentiometer can take the place of a bulky multigang tuning capacitor. Because of the low capacitance of VCDs, these circuits are usually limited to radio frequencies. However, it is possible to parallel-connect two or more VCDs for higher capacitance.

While the V100EB diode is shown here as a practical example, other VCDs may be selected for particular applications.

REMOTELY CONTROLLED TUNED CIRCUIT

One of the obvious applications of the DC tuning of an LC circuit is the tuning of a distant device, such as a receiver or instrument. This technique has been used, for example, to tune a field-strength meter located out of the near zone of an antenna under test, the output current from the instrument being sent back by cable to the test shack to operate an indicating meter. It has been used also to tune a distant transmitter.

Figure 7-5 shows an example of this application. In this arrangement, the DC control voltage is transmitted through a shielded cable to the voltage-variable capacitor (D1) at the remote location. This voltage is adjustable from zero to 12 volts by means of a 10,000-ohm wirewound potentiometer (R1). The V9000EB diode shown here has a capacitance of approximately 260 pF at zero VDC and 65 pF at 12 volts, and is a low-leakage type (5 nA at 20 volts), but other VDCs may be employed, as desired.

The 470 K resistors (R2 and R3) and the associated 0.001 μ F capacitors (C1 and C2) effectively block the AC signal associated with the L1 tuned circuit from the DC supply. The 0.01 μ F capacitance of C3 is so large with respect to that of the diode that the latter, rather than C3, tunes inductor L1. The inductance of L1 is governed by the frequency of the device in which this remotely tuned circuit operates.

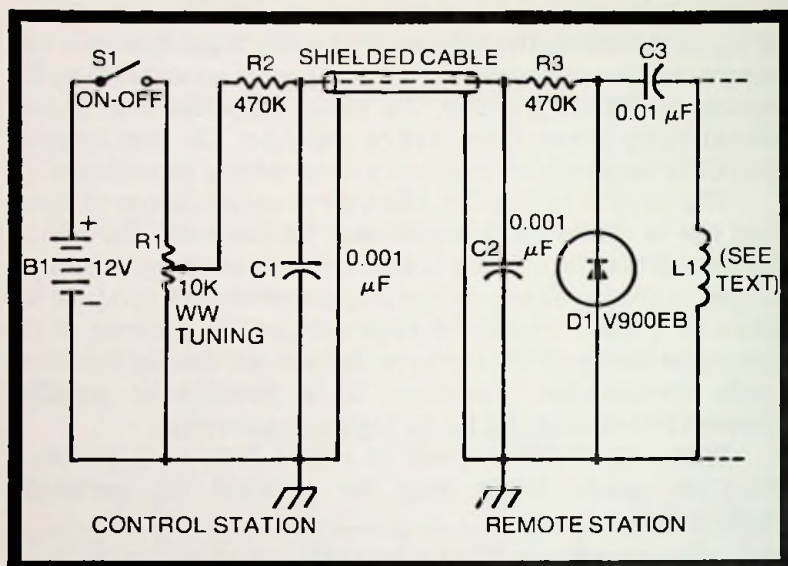




Fig. 7-5. Remotely controlled tuned circuit.

Table 7-1 lists five common inductor values and shows the frequencies corresponding to control voltages between zero and 12 volts for each of these inductances. The dial of potentiometer R1 may be graduated in kHz or MHz on the basis of an initial calibration of the circuit. Although a continuously variable DC control voltage is at work in the circuit as shown in Fig. 7-5, the control voltage may instead be applied in discrete steps for step-tuning of the resonant circuit.

VOLTAGE-TUNED RF OSCILLATOR

Figure 7-6 shows how a VCD can be used to DC voltage-tune a radio-frequency oscillator. Figure 7-6(A) gives the circuit, and Fig. 7-6(B) the tuning performance. The oscillator is a tapped-coil Hartley circuit employing a type HEP F0015 field-effect transistor (Q1), but any similar circuit can also be used. The oscillator tank coil (L1) is tuned by the type V1000EB variable-capacitance diode (D1), which is connected across the coil through 0.01 μF capacitor C1. (The capacitance of C1 is so high, with respect to that of the VCD that the latter rather than C1 tunes the coil.) For the 600–1078 kHz range (see Fig. 7-6B), L1 must be a slug-adjusted 0.04–0.24 mH coil with a tap at 1/3 of its turns (J. W. Miller No. 9011, or equivalent).

Fig. 7-6. Voltage-tuned RF oscillator.

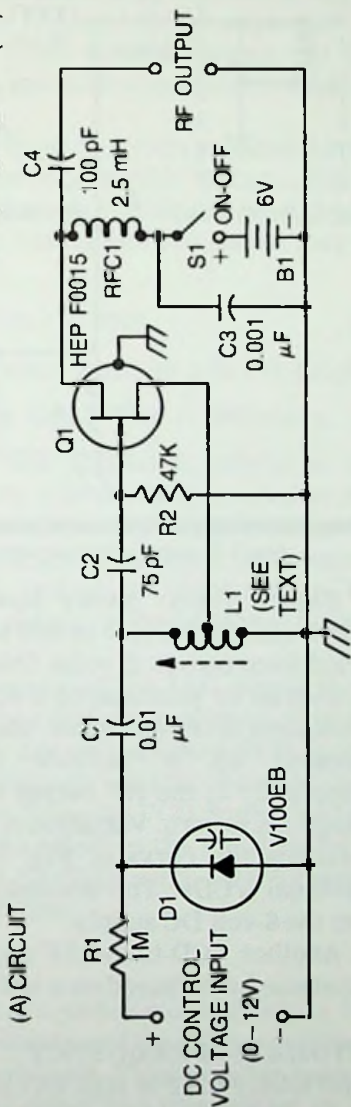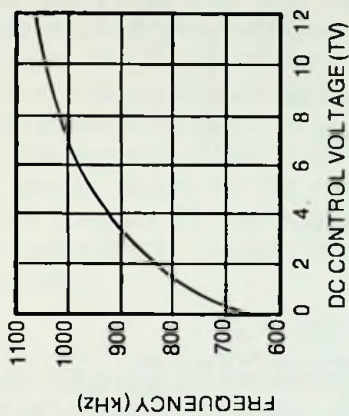

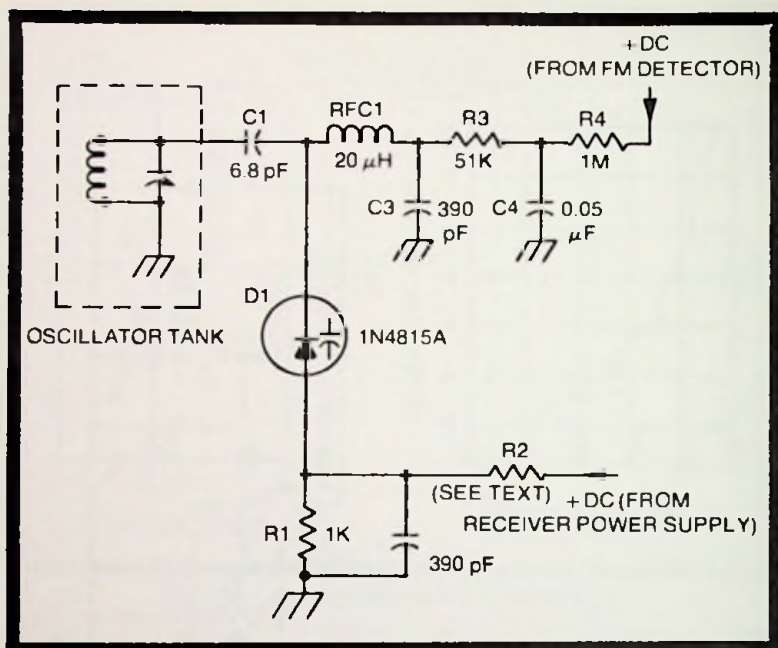


Fig. 7-7. Automatic frequency control for FM receiver.

Figure 7-6(B) shows how the frequency varies from approximately 645 kHz to 1078 kHz as the DC control voltage is varied from zero to 12 volts. Other frequencies and ranges may be covered by substituting a suitable coil for L1. In the initial adjustment of the oscillator, the slug of L1 is set for 645 kHz (as indicated by a suitable frequency meter connected temporarily to the *RF output* terminals) with the DC control voltage set to zero. Variation of the control voltage then should reproduce the curve of Fig. 7-6(B), within the tolerance of individual VCDs. The oscillator draws approximately 5 mA from the 6-volt DC supply.

Another VCD-tuned RF oscillator is described in Chapter 6, that one being based on a tunnel-diode oscillator.

AUTOMATIC FREQUENCY CONTROL FOR FM RECEIVER

The DC output of an FM detector may be used as an error voltage to vary the capacitance of a VCD which, in turn, will automatically reset the tuning of the front end. The basic circuit for accomplishing this action is shown in Fig. 7-7. In

principle, this is the same arrangement used with tubes or transistors for automatic frequency control (AFC). As shown here, the VCD acts as a trimmer in the front-end oscillator tank (see Fig. 7-4C and the attendant discussion for a description of the VCD as a trimmer), and capacitor C1 prevents the oscillator coil from short-circuiting the DC control voltage. The 1N4815A variable-capacitance diode is rated at 100 pF at 4 VDC.

The operating point of the diode is 5 volts provided by the DC power supply of the receiver through voltage divider R1-R2. Resistor R1 must be 1000 ohms, but R2 will depend upon the power-supply voltage, and the correct resistance may be calculated:

$$R_2 = (200 E_s) - 1000$$

where R2 is in ohms and E_s in volts. Thus, for a 35-volt supply,

$$R_2 = (200 \times 35) - 1000 = 7000 - 1000 = 6000 \text{ ohms.}$$

The DC voltage must be well regulated; otherwise, the diode capacitance will fluctuate with the voltage (and so will the receiver tuning). The FM detector has no DC output, as long as the receiver is tuned sharply to a station. On detuning, however, a proportional DC voltage is delivered by the detector, and it is this voltage acting on the VCD that retunes the receiver to the station.

To compensate for the presence of the AFC circuit in the oscillator, the receiver must be carefully realigned after the AFC circuit has been installed. For an individual VCD, it may be necessary to adjust R2 critically around the calculated value, for optimum AFC action. Since the VCD draws virtually no DC, its presence will have no effect on the FM detector. A substantial RF filter (RFC1-R3-R4-C3-C4 in the detector output line) provides essential RF isolation.

FREQUENCY MODULATORS

When a VCD is used as a frequency-varying device in a radio-frequency oscillator, modulation of the VCD capacitance will frequency modulate the oscillator. This provides a simple way of obtaining an FM signal either in a transmitter or in a signal generator.

In most applications, an audio modulating voltage is applied to the VCD which is DC biased to a point along its

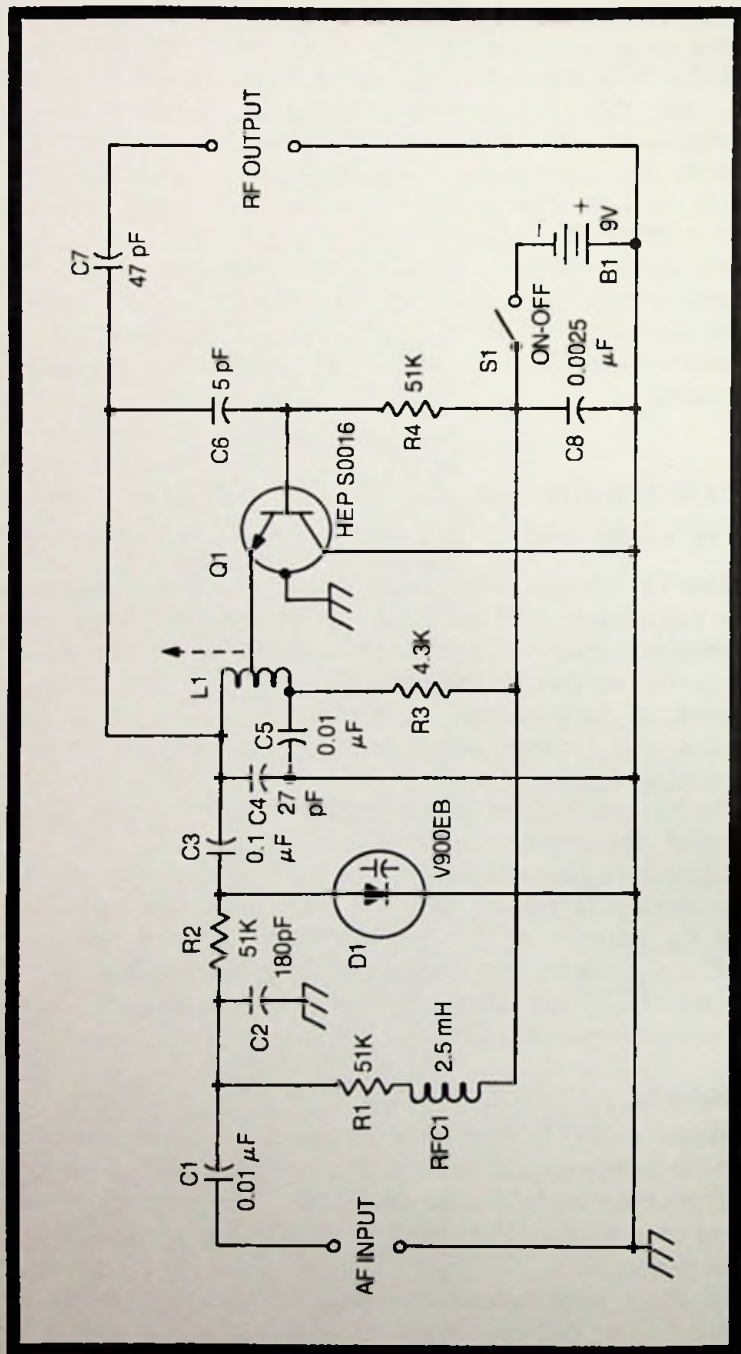


Fig. 7-8. Frequency modulator (self-excited oscillator).

voltage/capacitance curve that affords linear operation. The radio frequency then varies at the audio rate, and the deviation is proportional to the peak audio-voltage swing. By adjusting the audio amplitude, the operator may easily obtain either narrow-band or wideband FM, as desired.

Figure 7-8 shows how an audio-modulated VCD may be employed to frequency modulate a self-excited oscillator. The oscillator is a tapped-coil Hartley arrangement using a HEP S0016 bipolar transistor (Q1). For this type of oscillator, the tank coil (L1) must be tapped one-third of the way from the ground end, and such a tap is normally provided in the commercial coil (Miller No. 9012) used in the author's circuit.

The oscillator is tuned principally by coil L1 and capacitor C4; the variable-capacitance diode (D1) serves as a DC-variable trimmer, and is biased by the same 9-volt battery that energizes the transistor. The RF filter (RFC1-R-R2-C2) isolates the DC supply with respect to RF, and the series capacitor (C3) prevents coil L1 from short-circuiting the DC.

The tuned circuit of the oscillator has been chosen for 1000 kHz operation, but operation may be obtained at any other carrier frequency by suitably choosing the L1 or C4 values. (The higher the carrier frequency, the greater will be the FM swing per audio volt.) For initial adjustment of the circuit, slug-tone coil L1 for the carrier frequency with zero audio volts at the *AF input* terminals. Then apply the audio modulating voltage, and note the FM deviation for various audio amplitudes.

Figure 7-9 shows how an audio-modulated VCD may be used to fluctuate the frequency of a quartz crystal in an oscillator stage and so to frequency modulate the oscillator. The crystal frequency can be varied only a few hertz in this way, but when the oscillator is followed by several frequency-multiplier stages, this variation is multiplied along with the carrier frequency, and a useful amount of frequency modulation may be obtained in the output stage.

Thus, in Fig. 7-9, the oscillator is followed by three triplers, and here a crystal-frequency variation fluctuation of only 100 Hz would result in a fluctuation of 2.7 kHz at the final output. The circuit given here is designed to operate in the 220 MHz amateur band, the final output based upon the 8240 kHz crystal being 222.48 Mhz. Varactor-type (i.e., VCD type) triplers are described in the following sections.

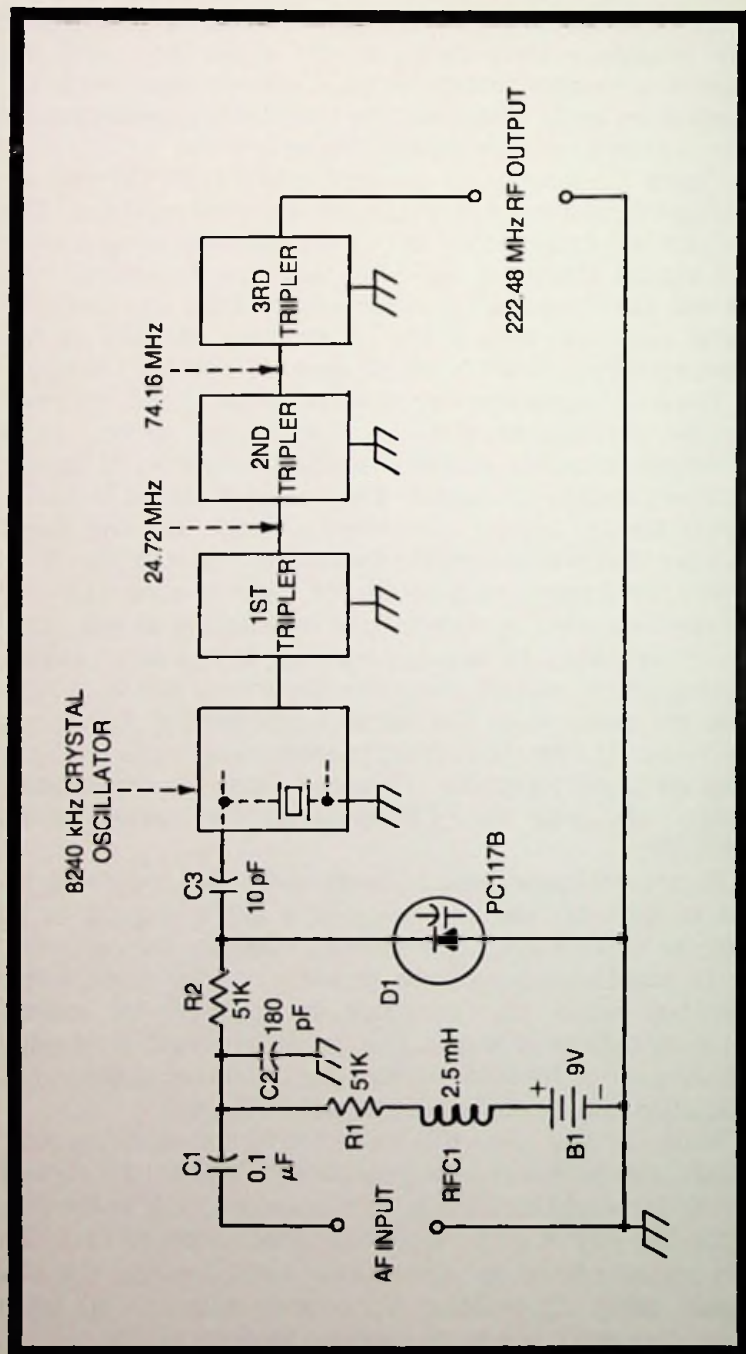


Fig. 7-9. Frequency modulator (crystal oscillator).

In this arrangement, a type PC117B, high-Q, variable-capacitance diode (D1) operates in parallel with the crystal through DC-blocking capacitor C3. Audio modulating voltage is applied to the VCD against the operating-point-setting DC bias provided by DC source B1 through the RF filter RFC1-R1-R2-C2. The resulting variation of the VCD capacitance at the audio rate fluctuates the frequency of the crystal. The deviation of the crystal frequency is proportional to the audio amplitude, and this deviation is multiplied successively by the triplers.

While the scheme shown here utilizes a 8240 kHz crystal to obtain frequency-modulated operation at 22.48 MHz, the same general arrangement may be applied for other output frequencies by suitably choosing crystal frequency and the number and type of multipliers. (The higher the final carrier frequency, the greater will be the FM swing per audio volt.)

In both the self-excited and the crystal circuit, some experimentation with the DC operating point of the VCD is necessary in order to obtain the most linear modulation. The purpose of this bias, in each circuit, is to set the operating point of the VCD to the most linear part of the diode voltage vs-capacitance characteristic.

VCD-type frequency modulators, whether employed with self-excited or crystal oscillators offer the advantages of simplicity and ease of adjustment. Moreover, the VCD requires no audio power for its operation, so the modulating source can be simply a voltage amplifier. The VCD modulator may easily be built into an existing oscillator and will occasion only the slightest readjustment of the oscillator alignment or tuning.

It is informative to note the frequencies at which FM is authorized in the ham bands. For wide-band FM: 29–29.7, 52.5–54, 144.1–148, 220–225, and 420–450 MHz. For narrow-band FM: 3775–4000 kHz, 7150–7300 kHz, 14.2–14.35, 21.25–21.45, 28.5–29.7, and 50.1–54 MHz.

FREQUENCY MULTIPLIERS

It is clear in the capacitance/voltage characteristic curve of the VCD (Fig. 7-2C) that a considerable portion of the operation of this device is nonlinear. Because of this nonlinearity, the VCD can distort an alternating current flowing through it, and accordingly can act as a harmonic

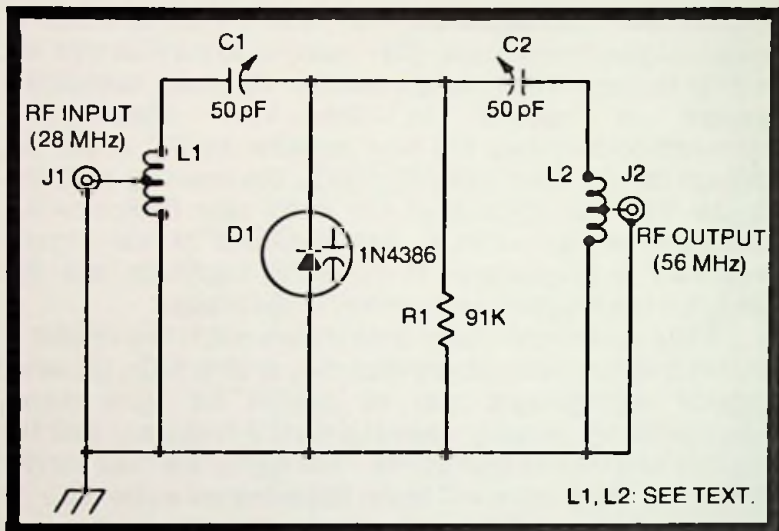


Fig. 7-10. Frequency doubler.

generator. Indeed, the attractiveness of the VCD as a harmonic generator is now well exploited in frequency doublers and triplers.

In this application, in which the VCD is called a *varactor*, no DC supply is needed, so the frequency multiplier is both simple and economical. Furthermore, it is efficient (90% is typical for varactor-type doublers, compared with 50% for the tube-type), since the VCD—a reactive device—draws very little power from its driving source. Figure 7-10 shows one type of varactor doubler, and Fig. 7-11 a varactor tripler.

In the doubler, Fig. 7-10, the input circuit is tuned to the frequency of the driver, and the output circuit to twice that frequency. In this instance, inductor L1 and capacitor C1 are tuned to 28 MHz, and inductor L2 and capacitor C2 to 56 MHz.

For these frequencies, the coils have the following specifications:

L1—7 turns No. 14 enameled wire airwound 1 in. in diameter. Space to winding length of 1 inch. Tap 2½ turns from ground end.

L2—5 turns No. 14 enameled wire airwound 1 in. in diameter. Space to winding length of 1¼ inch. Tap second turn from ground end. Other capacitor and inductor combinations may be employed for desired input and output frequencies. A 1N4386, 50-watt, varactor (D1) is used in this circuit.

In the tripler—Fig. 7-11, the input circuit is tuned to the frequency of the driver, an *idler circuit* to twice that frequency, and the output circuit to three times the driver frequency. The purpose of the idler (L3-C2) is to reinforce the tripler action and increase the overall efficiency of the circuit.

In this instance, inductor L2 and capacitor C1 are tuned to 74 MHz, inductor L3 and capacitor C2 to 148 MHz, and inductor L4 and capacitor C3 to 222 MHz. The coil specifications for these frequencies are given in Table 7-2. Other capacitor and inductor combinations may be employed for desired input and output frequencies. A 1N4386, 50-watt, varactor (D1) is used in this circuit.

Varactor doublers and triplers can be operated in cascade in various combinations to obtain desired output frequencies from available driver frequencies. While doublers and triplers are usual in varactor multiplier stages, frequency quadrupler action also has been reported.

RF HARMONIC INTENSIFIER

The nonlinearity of the VCD, so useful in frequency multipliers, can be enlisted to accentuate the harmonics of a

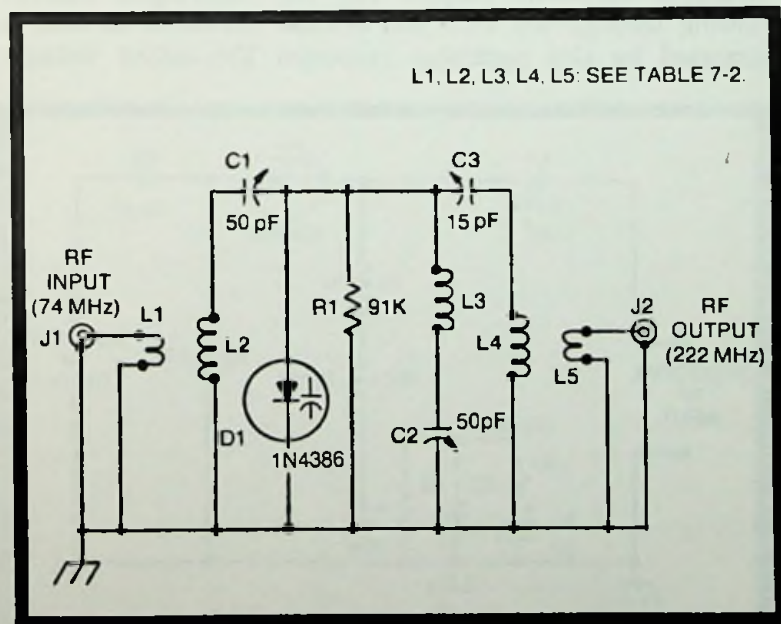


Fig. 7-11. Frequency tripler.

Table 7-2. Coil-Winding Data For Frequency Tripler

- L1. 3 turns No. 22 enameled wire closewound on same form as L2. Space $\frac{1}{8}$ in. from ground end of L2.
- L2. 35 turns No. 22 enameled wire closewound on 1 in. diameter form.
- L3. 16 turns No. 14 enameled wire airwound 1 in. in diameter. Space to winding length of $1\frac{1}{4}$ inch.
- L4. 3 turns No. 14 enameled wire airwound 1 in. in diameter. Space to winding length of 1 inch.
- L5. 1 turn No. 14 enameled wire solidly mounted $\frac{1}{8}$ in. from ground end of L4.

signal source, such as a frequency standard. The very high-order harmonics from such a source are often too weak to be useful, and can be brought up to useful amplitude by means of a simple, untuned intensifier circuit.

Figure 7-12 shows the circuit of a harmonic intensifier designed primarily for use with a 100 kHz crystal oscillator used as a secondary frequency standard bandspotter. In this arrangement, a 1N4799A diode is biased by means of the DC circuit (B1-R2) to the most nonlinear point in the diode capacitance/voltage characteristic, as evidenced by the strongest harmonic output. The RF input-signal current flowing through the VCD and resistor R3 in series then is distorted by this nonlinear response. The output voltage,

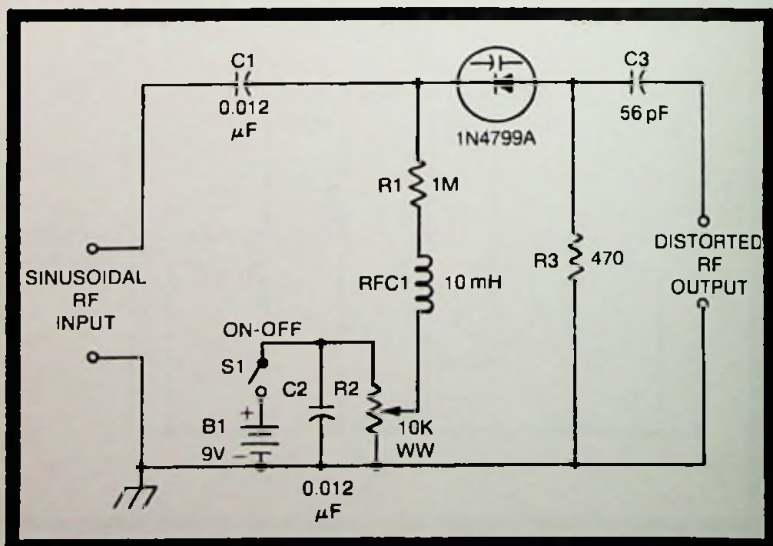


Fig. 7-12. RF harmonic intensifier.

developed across resistor R3, accordingly contains a high percentage of harmonics. The intensifier circuit produces negligible loading of the signal source.

Use of the circuit is straightforward: Close switch S1 and adjust potentiometer R2 for the strongest signal, as heard in the receiver, monitor, frequency meter, or other device with which the signal source is used. The proper setting of R2 can mean, for example, hearing or not hearing the 15 MHz harmonic of a 100 kHz oscillator.

The intensifier can be built into a small case. Battery drain is 0.9 mA DC.

8

Zener Diode

The *zener diode*, also called *avalanche diode* or *breakdown diode*, is a silicon junction diode. It is specially processed to give a nondestructive breakdown (sudden large increase in current) at a specified value of reverse voltage. Around this point—termed the *zener voltage*, *avalanche voltage*, or *breakdown voltage*—a small change in voltage produces a large change in current, and vice versa.

This action is enlisted in numerous ways in voltage regulators, control circuits, pulse generators, threshold devices, amplitude limiters, and related applications. In some instances, the zener diode—a simple 2-terminal device—performs functions which are otherwise obtainable only with more complex devices.

Zener diodes are available in a wide range of current, breakdown voltage, and power dissipation ratings. The conventional unit (see circuit symbol in Fig. 8-1) is a single diode which is DC operated; however, special AC units, consisting of a back-to-back connected zener pair, also are available. Also, two conventional zener diodes may be connected in series back-to-back for AC service.

Before working with zener diodes, read the hints and precautions in Chapter 1.

ZENER DIODE THEORY

Figure 8-2(A) shows the basic zener-diode circuit. In this arrangement, the adjustable DC source (B1) biases the diode

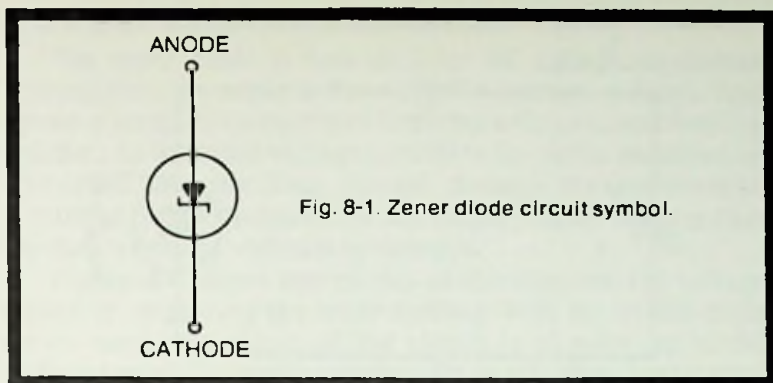



Fig. 8-1. Zener diode circuit symbol.

(DI) in the reverse direction (anode negative, cathode positive), causing a reverse current (I_R) to flow through the diode and series resistor R_s . Over much of the range of the reverse voltage (V_R) the current is tiny, as shown in Fig. 8-2(B), owing to the normally high reverse resistance of the silicon junction. At a critical value (V_B , the *breakdown voltage*), the reverse current begins to increase sharply, and for a very small increase in voltage beyond point V_B it will increase rapidly, as to point I_M .

The breakdown point is rounded to some extent, this curvature being referred to as the "knee." The sharper the knee, the better the diode performs in most applications. In zener diodes of some types, the knee is so sharp that no curvature is visible unless the scale is expanded sufficiently to reveal it.

In most applications, the zener diode is DC biased to a point (such as zener voltage V_Z and the corresponding zener current I_Z in Fig. 8-2(B)) somewhere in the breakdown region. The forward conduction characteristic is usually of no interest, so it is shown by a dotted line in Fig. 8-2(B). With the diode operating in the zener region, a large change in current produces a small (virtually zero) change in diode voltage drop. Conversely, a small change in voltage produces a large change in current.

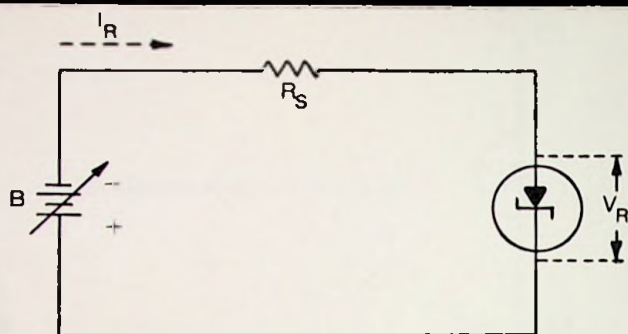In applications of the zener diode, the input (applied, or signal) voltage corresponds to the adjustable-voltage battery, B1 in Fig. 8-2(A), and the output voltage is chosen either as the voltage drop across the diode or the voltage drop across the resistor. For a given change in input voltage and therefore in



(A) BASIC CIRCUIT

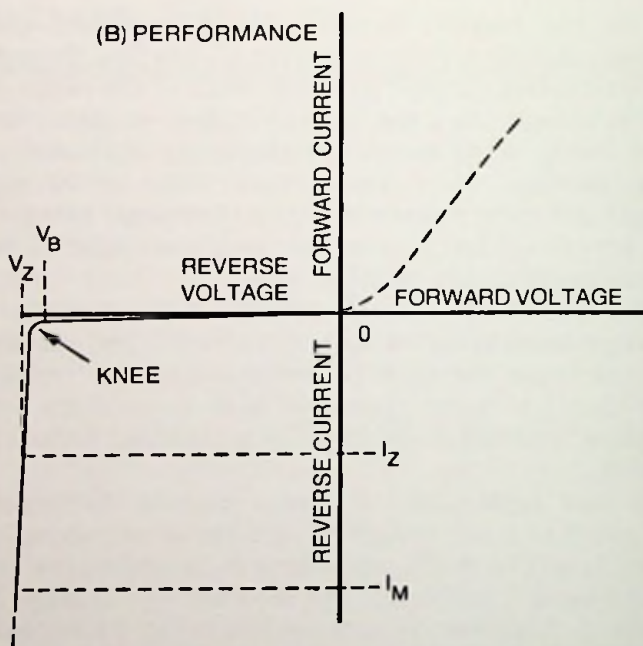


Fig. 8-2. Zener diode action

diode current (I_R), the diode voltage drop is virtually constant because of the shape of the conduction characteristic (Fig. 8-2B), and the voltage drop across the resistor changes rapidly for the same reason. The constant diode voltage in the face of considerable input-voltage changes suits the zener circuit to constant-output applications, such as voltage regulation, peak clipping, and amplitude limiting.

SIMPLE DC VOLTAGE REGULATOR

The zener diode is best used for DC voltage regulation. This application exploits the virtually constant voltage drop across a zener diode operated in series with a current-limiting resistor. As the input voltage applied to the series combination fluctuates, the resulting current through the combination fluctuates proportionately, but the output voltage taken across the diode remains virtually unchanged.

Figure 8-3 shows the circuit of the simplest DC voltage regulator employing the zener method. With the 1N4020 diode shown here, the output of the circuit is 12 volts, up to 105 milliamperes. The series resistor, R1, is a 95-ohm, 2-watt unit; and because this is not a stock resistance, it must be made up by connecting a 75-ohm and a 20-ohm unit in series (individual zeners may require some adjustment of this resistance for best voltage regulation).

When the circuit is unloaded, the full current of 105 mA flows through the diode; but when the circuit is loaded, the current divides proportionately between diode and load, the total always being 105 mA. But as the load current fluctuates, the output voltage undergoes only a tiny change (see Fig. 8-2B). Similarly, when the input voltage fluctuates, the diode current correspondingly fluctuates; but large current fluctuations of this sort produce virtually no change in output (diode) voltage (again, see Fig. 8-2B). In this way, the simple

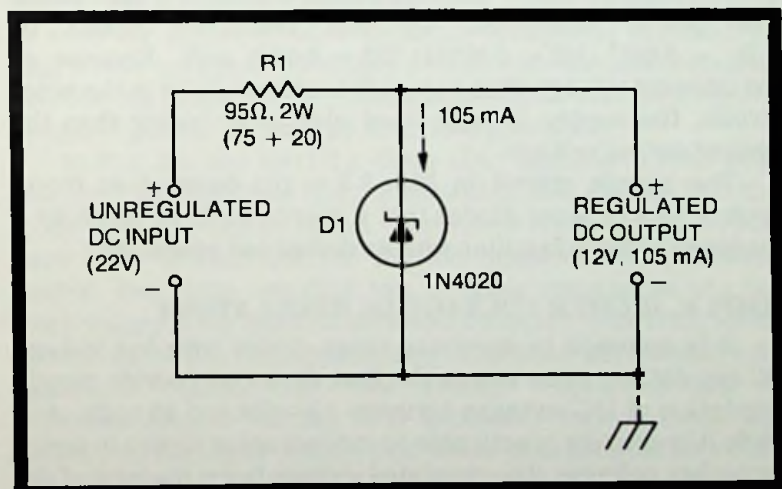


Fig. 8-3. Typical simple DC voltage regulator.

circuit regulates output voltage against both input-voltage fluctuations and load fluctuations.

A simple arrangement such as that in Fig. 8-3 is often employed as a compact voltage regulator for the power supply in an electronic device. It is used also to stabilize the DC supply voltage at a single point in a circuit (as at the collector of a sensitive transistor). Occasionally, it is used in conjunction with a battery-type power supply to provide constant DC voltage as the battery ages. For an example of the convenience of the simple zener-diode regulator, see D1 in Fig. 3-8 (Chapter 3).

The output voltage is determined by the zener-diode ratings, and so is the output current. The 1N4020 unit shown in Fig. 8-3 is a 12-volt, 105 mA diode. A wide variety of ratings may be found in the diode manufacturer's literature, so that a zener diode is available for every standard output voltage and many currents. For a particular diode and an available input voltage, the series resistance (R_1) must be calculated:

$$R_1 = (E_i - E_o) / I$$

where E_i is the available input voltage (volts), E_o is the output voltage (diode voltage, volts), and I is the rated zener current (amperes).

Thus, for 18 volts output, a 1N3795A diode is available and is rated at 21 mA; and for this diode to be operated with a 25-volt supply, $R_1 = (25 - 18) / 0.021 = 7 / 0.021 = 333$ ohms. The power dissipated by this resistance would be $I^2 R_1 = 0.021^2 / 333 = 0.000441 / 333 = 0.0013$ mW. Because of the inherent voltage drop across the series resistor in the zener circuit, the supply voltage must always be higher than the desired output voltage.

The simple circuit in Fig. 8-3 is the basis of so many applications of zener diodes that it merits the time taken by a reader to become familiar with its design and operation.

SIMPLE, HIGHER VOLTAGE DC REGULATORS

It is common to associate zener diodes with low-voltage DC regulation, since it was the first device to provide simple regulation of DC voltages between 1.8 volts and 50 volts. And while it is entirely practicable to connect zener diodes in series for higher voltages (the regulated voltage being the total of the separate rated zener voltages) so long as the diode current

ratings are identical, there are available single zener diodes that will do the job by themselves. Thus, in some applications where current requirements are the same for both devices, a single higher voltage zener diode can replace a gaseous regulator tube such as OA3/VR75 (75 volts), OA2/VR150 (150 volts), OB2/VR105 (105 volts), or OB3/VR90 (90 volts).

Figure 8-4 shows six DC voltage regulators of the simple type, each employing a single zener diode. Except for the use of a higher voltage diode, each of these circuits is identical with the basic regulator circuit discussed in the preceding section, and that section should be studied for familiarity with the circuits. In each instance, the series resistor (R_1) has been worked out for a typical input voltage; but since most of these resistances are not stock values, they must be obtained by series connecting lower values.

Electronic equipment of various types—including control devices, communications systems, test instruments, and data processing devices—can utilize simple DC voltage regulators of the zener type, such as are depicted by Fig. 8-4.

MULTIPLE-OUTPUT DC VOLTAGE REGULATOR

It is often convenient to obtain several regulated output voltages from a single supply voltage. In the parallel circuit shown in Fig. 8-5, three such outputs (10, 18, and 30 volts) are obtained from a single 48-volt unregulated supply. While three outputs are shown in this arrangement, the same scheme may be used for as many more separate voltages as required, as long as the unregulated supply can provide the total required current. An examination of the circuit shows that each leg is a simple regulator of the type described previously.

In Fig. 8-5, the 1N1771A diode (D_1) supplies 10 volts at 50 mA, the 1N3795A diode (D_2) 18 volts at 21 mA, and the 1N1782A diode (D_3) 30 volts at 15 mA. The series resistors (R_1 - R_2 - R_3) have been worked out for the individual currents of these diodes; but since the first two of these resistances are not stock values, they must be obtained by series connecting lower values. All of the resistances may need some adjustment with individual diodes, for best voltage regulation. For a grounded-positive circuit, it is necessary only to invert the diodes and the input voltage; do not change the position of the series resistors.

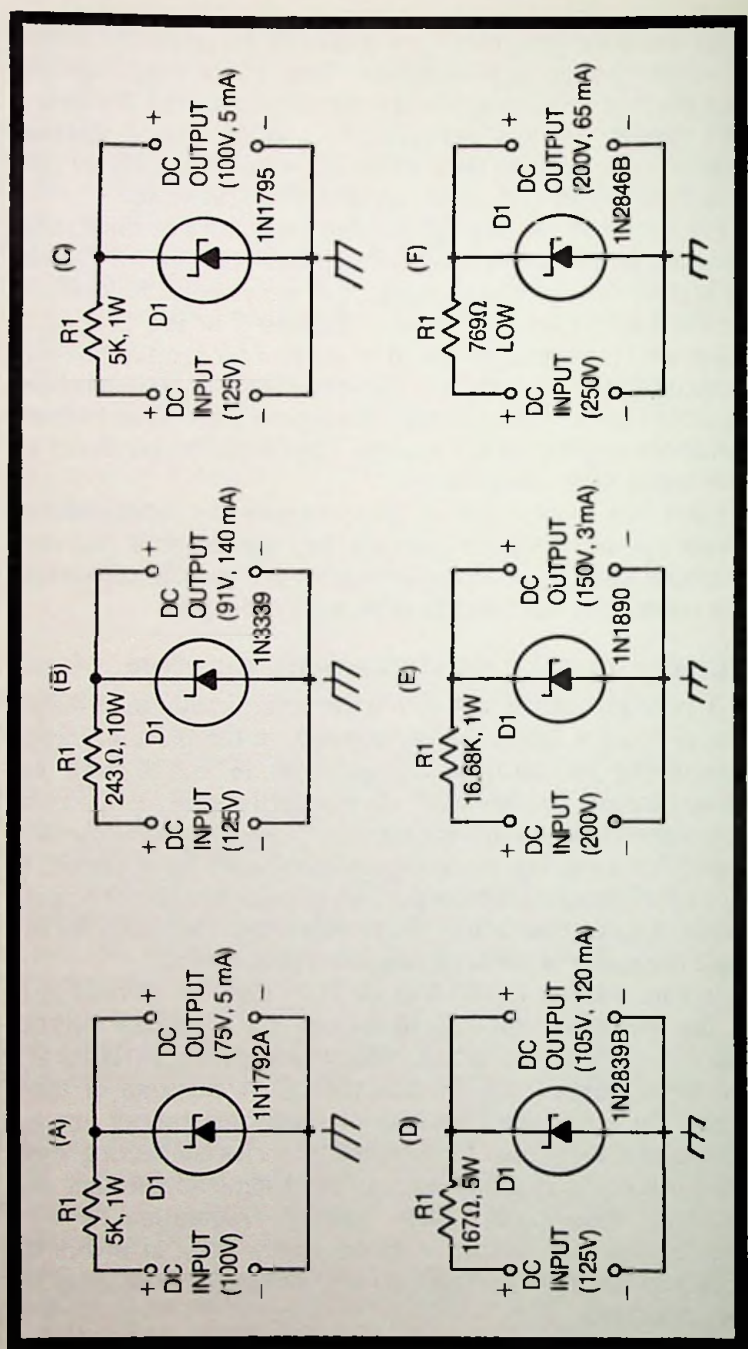


Fig. 8-4. Simple higher-voltage DC regulators.

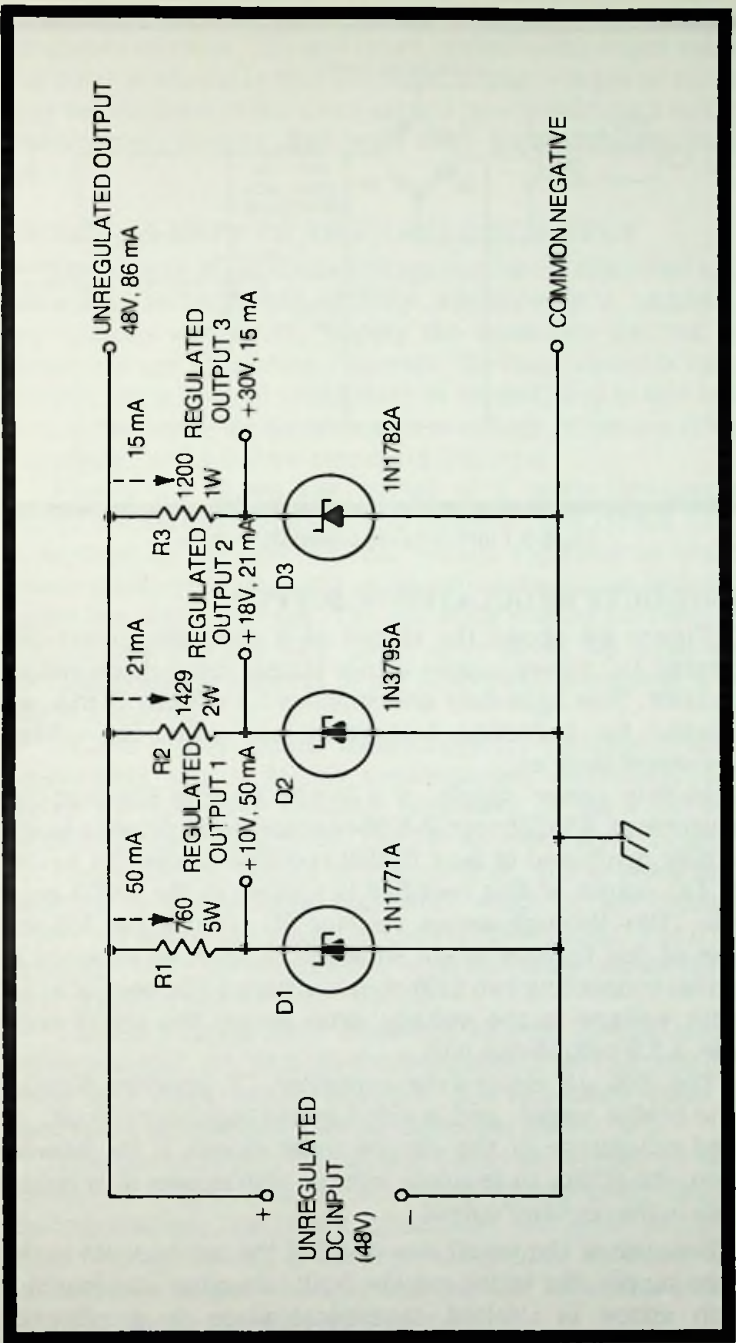


Fig. 8-5. Multiple-output DC voltage regulator.

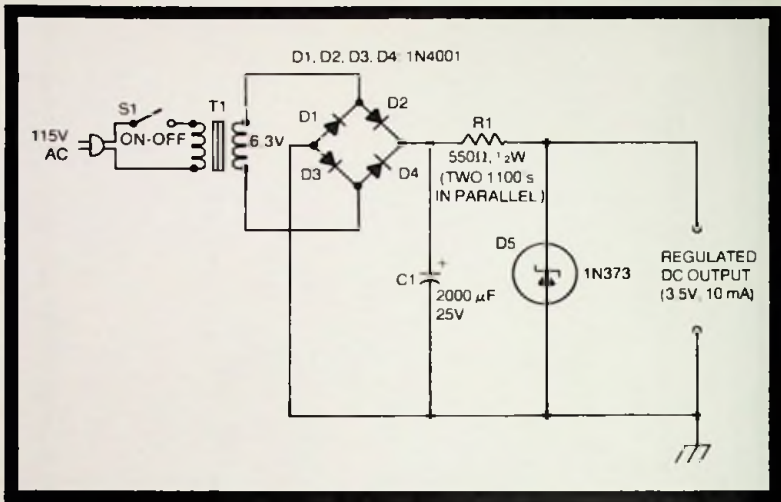


Fig. 8-6. Light-duty regulated DC supply.

LIGHT-DUTY REGULATED DC SUPPLY

Figure 8-6 shows the circuit of a complete, power-line-operated DC power supply with a simple zener-diode voltage regulator. This light-duty unit supplies 3.5 volts at 10 mA, and is useful for operating transistors and other low-voltage, low-current devices.

In this power supply, a 6.3-volt, 1.2-amp filament-type transformer, T1 (Stancor P-8190 or equivalent) drives a bridge rectifier composed of four 1N4001 rectifier diodes (D1 to D4). The DC output of this rectifier is applied to the 1N373 zener diode (D5) through series resistor R1. (Since the 550-ohm value of this resistor is not standard, it must be obtained by parallel connecting two 1100-ohm resistors.) The regulated DC output voltage is the voltage drop across the 1N373 zener diode, a 3.5-volt, 10-mA unit.

The 2000 μF electrolytic capacitor, C1, provides filtering of the bridge output, and is aided by the regulator circuit: An added advantage of the simple zener circuit is its filtering action. Its ability to regulate voltage also causes it to reduce ripple in the rectifier output.

Because of the small size of all of the components in this power supply, the latter may be built into other equipment in which space is limited. A typical place is a universal breadboard used for "dry wiring" circuits for transistors and

integrated circuits. The unit is not limited to the output voltage and current shown in this example; higher voltage or current may be obtained in the same circuit by substituting a suitable transformer, resistor, and zener diode for those shown in Fig. 8-6.

5-VOLT, 1.25-AMPERE REGULATED DC SUPPLY

The simple zener-diode voltage regulators described in the preceding sections are entirely adequate in a number of applications where they supply the constancy desired. For closer voltage regulation, however, the more complex circuit (employing a control transistor) is needed, and in this latter circuit the zener diode serves as a voltage reference device. Figures 8-7 and 8-8 show circuits of this type.

Figure 8-7 shows the circuit of a power-line-operated supply delivering 5 volts at 1.25 ampere. This circuit will be recognized as the conventional voltage regulator in which a power transistor (Q1) acts as an automatic series resistor to adjust the output voltage. The operating point of the transistor is established by the HEP Z0408 zener diode, D3. Because of the high collector current of the HEP S7002 transistor, a heat sink is required.

In this supply, power transformer T1 (Stancor P-6377 or equivalent) has a 24-volt center-tapped secondary, which drives the full-wave rectifier consisting of the HEP R0090 rectifier diodes, D1 and D2. The 250 μF electrolytic capacitor, C1, filters the DC output of the rectifier, and is aided in this function by the voltage regulator, which by its regulating action smoothes the ripple in the rectifier output. The 0.1 μF capacitor (C2), in conjunction with the zener series resistor (R1) provides still further filtering.

The HEP Z0408 zener diode is a 6.2-volt, 100-mA unit. The series resistor, R1, sets the diode current to 100 mA, and its 180 ohms is a stock value; however, this resistance value may need some adjustment with an individual diode.

This power supply circuit may easily be adapted for higher voltage or higher current service by appropriately changing the transformer, rectifiers, transistor, and zener diode. The zener voltage rating of the new diode must be equal to the desired new output voltage, and the new transistor must be able to pass the new current safely.

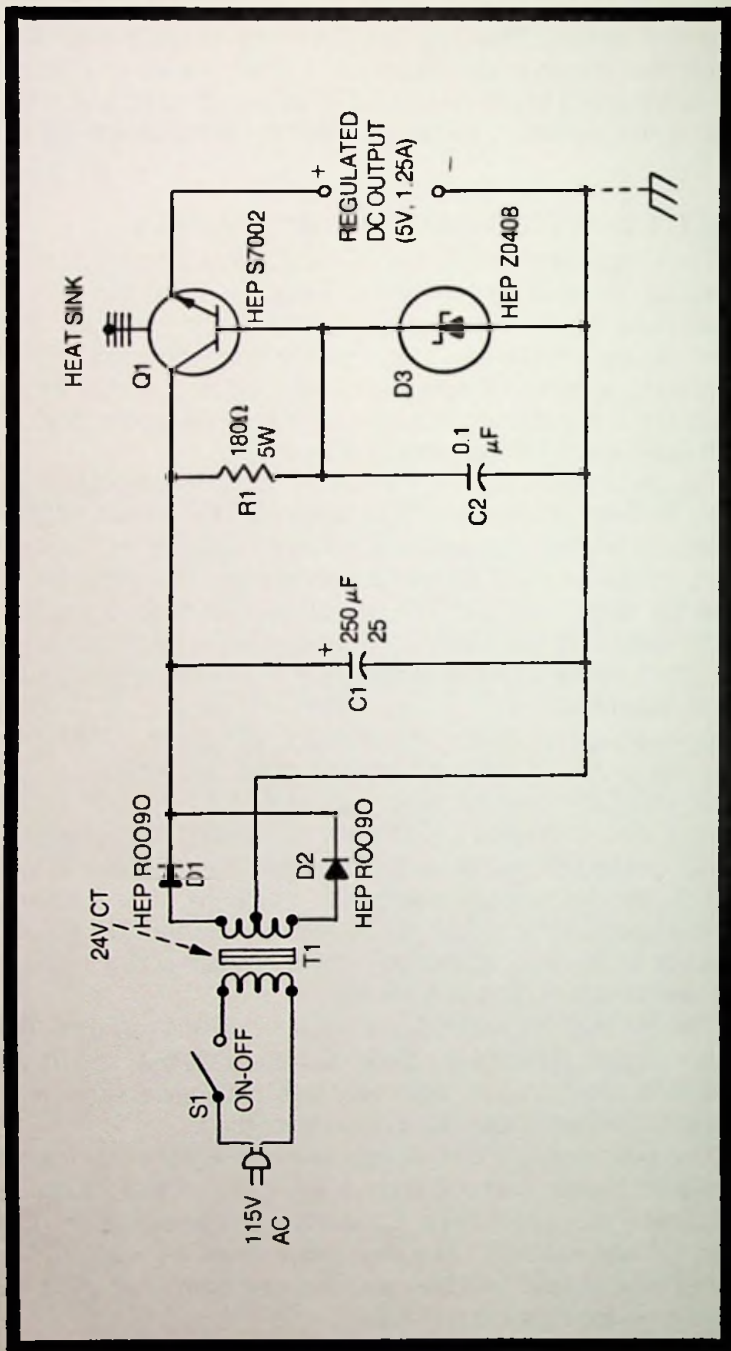


Fig. 8-7. 5-volt 1.25-ampere regulated DC supply.

18-VOLT, 1-AMPERE REGULATED DC SUPPLY

Figure 8-8 shows the circuit of a conventional voltage-regulated power supply which is operated by an AC power line and delivers 18 volts at 1 ampere. This unit is similar to the one described in the preceding section, but employs a bridge rectifier (RECT1) instead of a full-wave, center-tapped rectifier.

In this arrangement, transformer T1 (Stancor P-6469 or equivalent) delivers 25.2 volts to the bridge rectifier which is rated at 50 PRV. The DC output of the rectifier is filtered by 2200 μ F electrolytic capacitor C1 and by the ripple-reducing action of the voltage regulator. Additional filtering action is provided by 0.01 μ F capacitor C2.

The HEP S7000 power transistor (Q) serves as the automatic resistance element in the regulator, and the HEP Z2522 zener diode (D1) serves as the voltage reference. This diode applies a constant +18-volt potential to the base of the transistor. For correct diode operation, the 330-ohm series resistor, R1, establishes a current of 21 mA in the diode. (R1 may need some resistance adjustment with an individual diode.) Because of the high current (1 ampere) flowing through the transistor and the external load, Q1 requires a heat sink.

This solid-state power supply is entirely conventional and demands no special techniques in its construction, except that adequate ventilation should be provided for the rectifier and transistor.

VOLTAGE-REGULATED DUAL DC SUPPLY

The power-line-operated supply shown in Fig. 8-9 provides separate +12-volt and -12-volt outputs, each at 80 mA. A unit of this type is useful for powering devices, such as integrated circuits, that require two identical positive and negative voltages. For regulation of the output voltages, two circuits of the simple zener type, each based upon a HEP Z0415 zener diode, are operated from the rectifier.

The rectifier itself (RECT 1) is of bridge construction (type HEP R0801), but is not used as a bridge. Instead, each half of the rectifier functions as a full-wave, center-tapped unit in conjunction with the center-tapped secondary of transformer T1, the right half delivering positive voltage, and the left half negative voltage. The power transformer has a

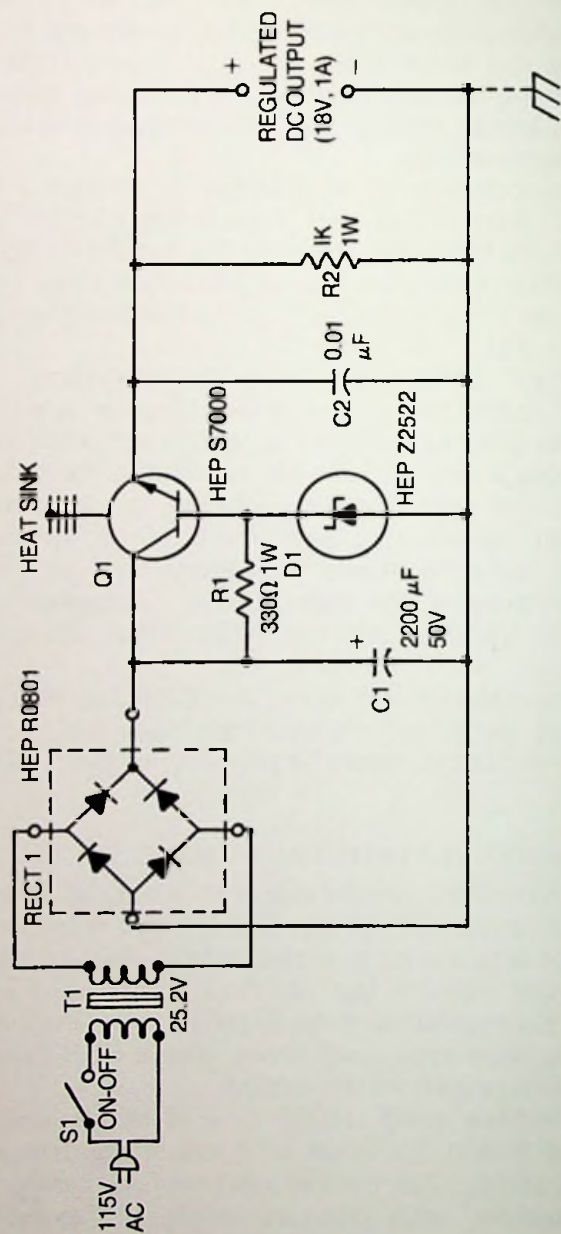


Fig. 8-8. 18-volt, 1-ampere regulated DC supply.

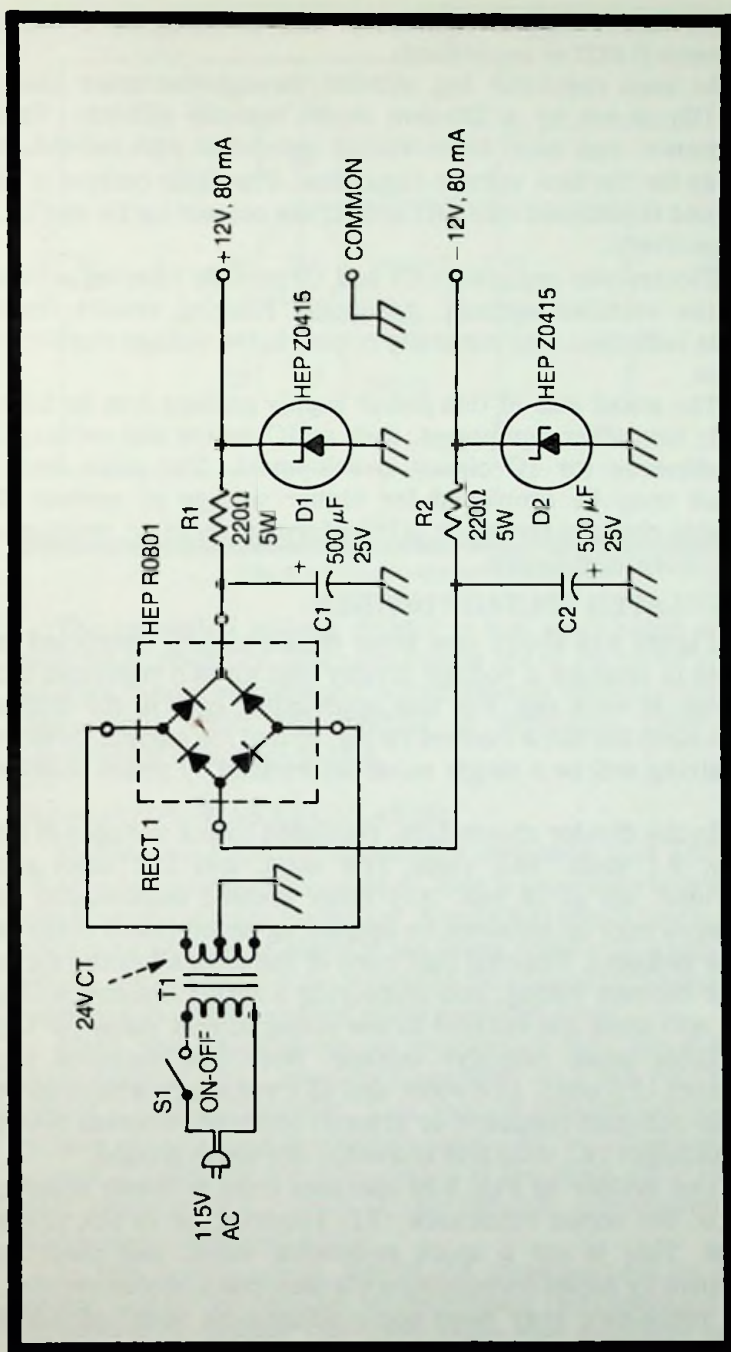


Fig. 8-9. Voltage-regulated dual DC supply.

24-volt center-tapped secondary and is rated at 2 amps (Stancor P-6377 or equivalent).

In each regulator leg, current through the zener diode (D1-D2) is set by a 220-ohm series resistor (R1-R2). This resistance may need to be varied somewhat with individual diodes for the best voltage regulation. The diode current is 80 mA and is obtained when R1 and R2 are correct for D1 and D2, respectively.

Electrolytic capacitors C1 and C2 provide filtering action for the rectifier outputs. Additional filtering results from ripple reduction that naturally occurs in the voltage regulator action.

The small size of this power supply enables it to be built easily into other equipment, such as IC testers and universal breadboards for IC circuit development. The same basic circuit may be employed for higher voltage or current if suitable changes are made in transformer, rectifier, resistors, capacitors, and diodes.

REGULATED VOLTAGE DIVIDER

Figure 8-10 shows how zener diodes may be connected in series to produce a voltage divider that gives a regulated DC voltage at each tap. For this application, each of the diodes must have the same current rating, so that the current through the string will be a single value determined by series resistor R1.

In the divider shown here, regulated output voltages of 3.5 volts, 9.1 volts, 10.5 volts, 12.6 volts, and 23.1 volts are provided, all at 10 mA. Any other desired combination of voltages may be obtained by employing zener diodes rated at those voltages, insuring that each of the diodes has the same zener current rating, and employing a series resistance (R) that will limit the current in the string to that value for the available input (supply) voltage. Note that three of the voltages (3.5 volts, 12.6 volts, and 23.1 volts) are with respect to the common (negative or ground) terminal, whereas two of the voltages (9.1 volts and 10.5 volts) are above ground.

The divider in Fig. 8-10 operates from a 28-volt supply; hence, the series resistance (R1) required for 10 mA is 490 ohms. This is not a stock resistance value, and must be obtained by series connecting a 470-ohm and a 20-ohm resistor. The resistance may need some adjustment with individual diodes, for best voltage regulation.

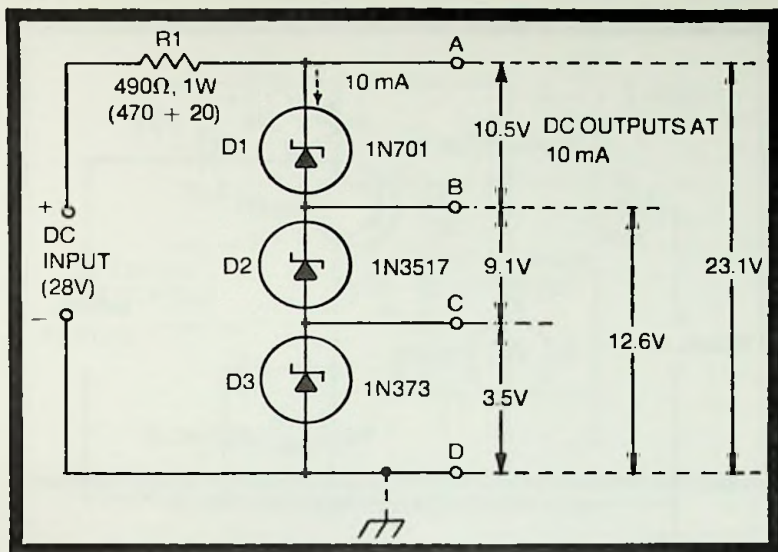


Fig. 8-10. Regulated voltage divider.

The regulated voltage divider is just as compact as one made up of resistors, since the diodes are of the same size as resistors. And it eliminates the troublesome voltage shifts that often occur when the loading of individual taps in a conventional divider is varied.

TRANSISTOR-BIAS REGULATOR

Stable operation of transistors demands that DC bias voltages be maintained constant. This is especially true of the base bias of a bipolar transistor. Figure 8-11 shows how a zener diode may be used in place of the lower resistor in a base-bias voltage divider to provide regulated DC voltage to the base of a transistor in an RC-coupled audio amplifier stage.

Here, the 1N370 diode, in conjunction with the 510-ohm series resistor (R1), supplies a constant -1.8 -volt bias to the base of a 2N414 transistor. This voltage remains constant in the face of variations in supply voltage (B1) or transistor base current. Except for the substitution of the zener diode for the usual resistor, the circuit is the familiar common-emitter RC-coupled voltage amplifier.

In this arrangement, the 20 mA zener current for D1 is determined by the 510-ohm series resistor (R1) operated from the 12-volt DC supply (B1). For other bias values or supply

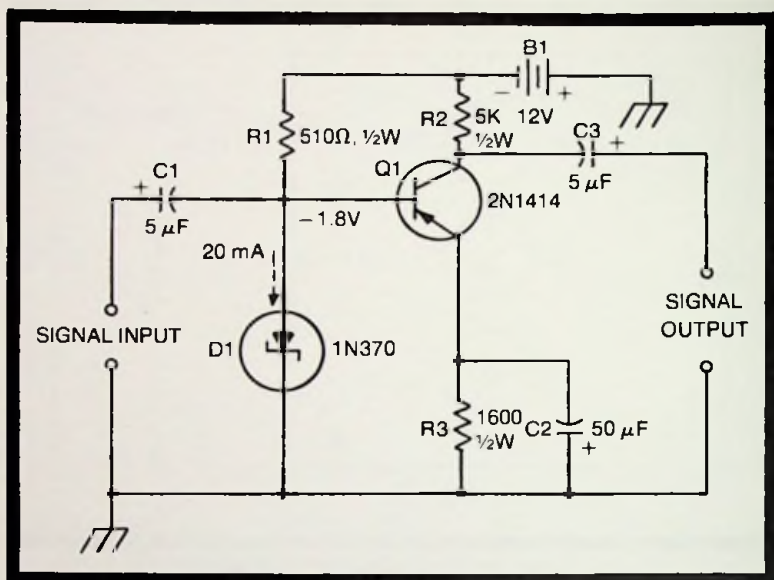


Fig. 8-11. Transistor-bias regulator.

voltages, select the zener diode that will supply that bias, and calculate the resistance needed to obtain the required zener current from the available supply voltage.

VOLTAGE REGULATOR FOR TUBE HEATER

Vacuum tubes in sensitive locations—such as variable-frequency oscillators, electrometers, Q meters, and so on—often give improved performance if their heater (filament) voltage is held constant. Figure 8-12 shows how a zener diode voltage regulator may be used to stabilize the DC heater voltage of a type 8628 high- μ triode. The heater of this tube requires 6.3 volts at 0.1 ampere. The 1N1766 zener diode supplies 6.2 volts. The slightly reduced heater voltage often results in better operation of the circuit in which the tube is used.

In this arrangement, the 100 mA current of the diode is determined by the 58-ohm series resistor (R1) operated from a 12-volt supply. Since this is not a stock resistance, it must be obtained by series connecting a 36-ohm and a 22-ohm resistor. Some slight adjustment of this resistance may be needed with an individual diode for best voltage regulation. For initial adjustment, temporarily disconnect the heater, and adjust R1

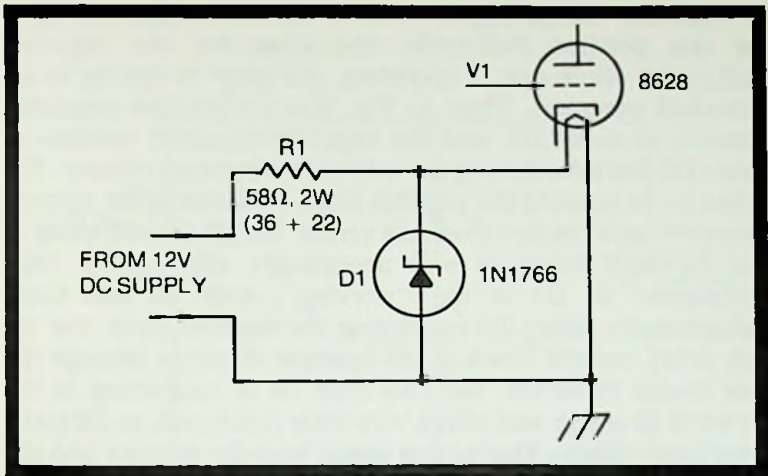


Fig. 8-12. Voltage regulator for tube heater.

(if necessary) for a diode current of 100 mA. Then, reconnect the heater.

SIMPLE AC VOLTAGE REGULATOR

Two zener diodes may be connected in series back-to-back to regulate the two half-cycles of an AC voltage. Figure 8-13 shows such an arrangement. Operating from 115 volts, this circuit delivers 105 volts at 120 milliamperes.

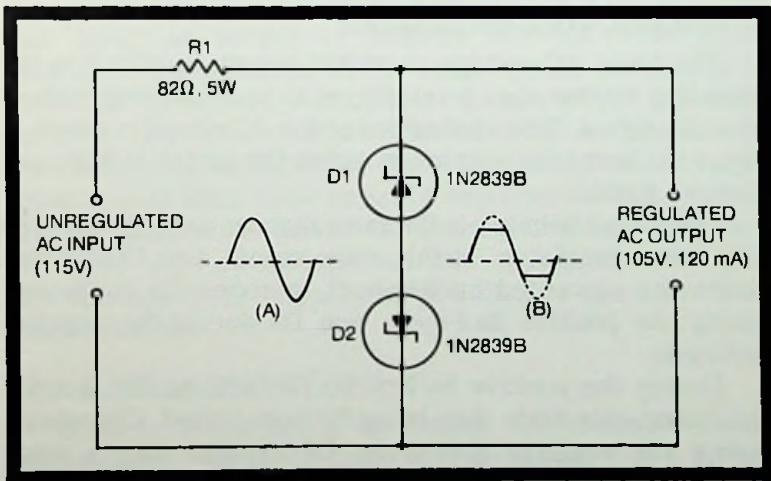


Fig. 8-13. Simple AC voltage regulator.

The AC voltage regulator is in effect two regulators, one for the positive half-cycle, the other for the negative half-cycle. When one is operating, the other is resting to all practical purposes. Thus, in Fig. 8-13 the positive regulator consists of diode D1, and the negative regulator consists of diode D2. Both diodes are served by the one series resistor, R1. When D1 is limiting the positive peak, a 120 mA zener current flows through the two diodes in series; but D2 is conducting in the forward direction and accordingly offers very little resistance, so D1 is the "working" diode at this time. Subsequently, when D2 is limiting the negative peak, the 120 mA zener current flows in the opposite direction through the two diodes in series; but this time D1 is conducting in the forward direction and offers very little resistance, so D2 is the "working" diode. This action limits both the positive and the negative peak to 105 volts, resulting in the clipped output waveform shown at (B).

For best results, D1 and D2 should be a matched pair. The common series resistor (R1) is 82 ohms, a stock resistance, but this resistance may require some slight adjustment for best voltage regulation.

The 105-volt, 120 mA regulated output shown here is typical. Other values of voltage and current may be obtained from the 115-volt input and from other input voltages by suitably choosing zener diodes and the required R1 value. The 1N2839B zener diode shown here is a 12.6-watt unit.

AUTOMATIC VOLUME LIMITER

The basic AC voltage regulator circuit described in the preceding section may be employed to limit the amplitude of an audio signal. This application of the AC circuit is shown in Fig. 8-14; here, the maximum value the output voltage can have is 1.8 volts.

The circuit behaves in the same manner as the power-type AC voltage regulator. In this audio circuit, two 1N370 zener diodes are connected back-to-back in series, D1 conducting during the positive half-cycle and D2 during the negative half-cycle.

During the positive half-cycle, D2 behaves like a small resistance, this diode then being forward biased. Conversely, during the negative half-cycle, D1 behaves like a small resistance, this diode then being the forward-biased one.

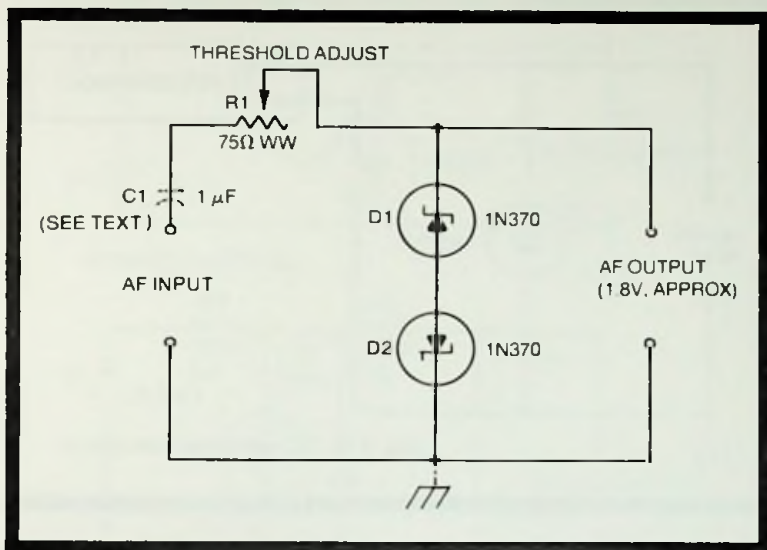


Fig. 8-14. Automatic volume limiter.

The threshold at which the output-signal clipping begins is adjustable to some extent by means of the 75-ohm wirewound rheostat, R1. If there is direct current in the output of the signal source that drives this limiter, the zener diodes must be protected from it by insertion of a 1 μ F nonpolarized capacitor, C1.

Because this is a clipper circuit, it introduces distortion in the output signal (see output waveform in Fig. 8-13). However, this distortion serves to indicate that excessive signal amplitude has occurred in the audio system and it can be corrected by needed reduction of gain, and the automatic action of the zener circuit protects the circuit and components from overdrive damage. The zener current of 20 mA is rather substantial in some audio systems, which means that the zener type of automatic limiter is most practicable in power systems. An advantage of the zener system over conventional diode clippers is its ability to operate without bias batteries.

DC-EQUIPMENT PROTECTOR

Because of its sharp breakdown and attendant heavy current drain, the zener diode may be used to clip a voltage transient or nullify a rise in supply voltage, thus protecting

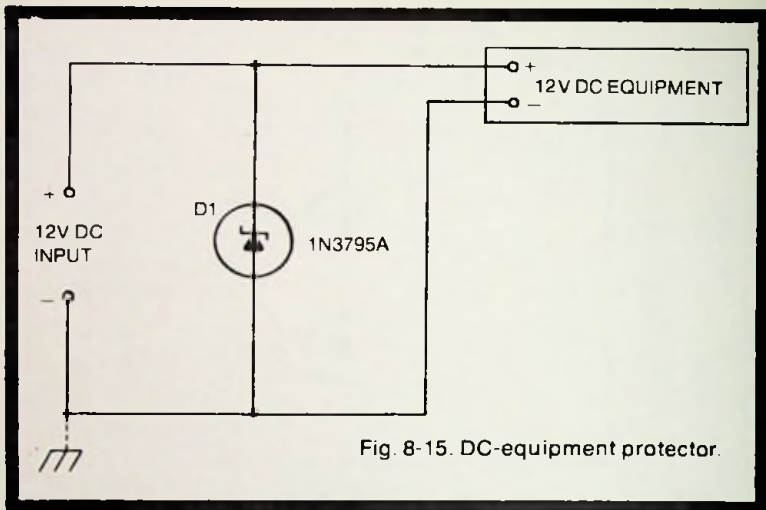


Fig. 8-15. DC-equipment protector.

equipment from overvoltage damage. Figure 8-15 shows how an 18-volt zener diode may be connected simply in parallel with a 12-volt DC supply and the equipment (such as a receiver) that the latter powers. As long as the supply remains at 12 volts, the 1N3795A diode is in its nonconducting condition and appears as a very high resistance shunting the supply. When, however, the voltage rises to 18 volts or when a transient of that voltage value appears, D1 conducts heavily and pulls the voltage down.

The same arrangement may be employed for voltages higher or lower than 18 volts simply by selecting a zener diode having that voltage rating.

DC VOLTAGE STANDARD

The constant voltage drop across a biased zener diode may be used for calibration and standardization purposes. Figure 8-16 shows two circuits, each of which provides 1.8 volts. This voltage was chosen because it is close to the voltage of a common dry cell and of a Weston standard cell. A zener voltage standard may be powered by any convenient source—e.g., a battery, powered-line-operated supply, or generator.

Figure 8-16(A) shows a single-diode circuit. Employing a 1N370 diode, this circuit delivers 1.8 volts when it is powered by 3 volts input. The required series resistance (for 20 mA

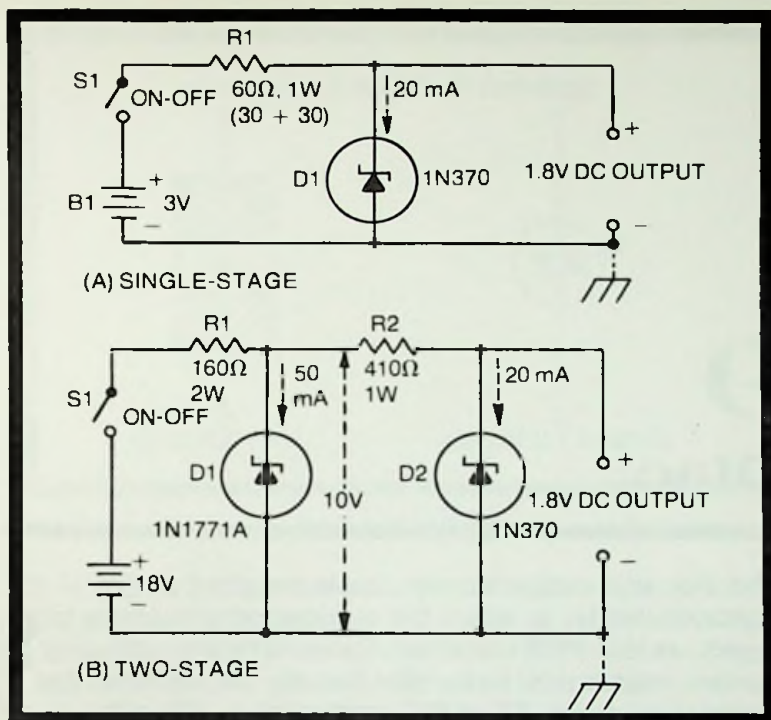


Fig. 8-16. DC voltage standard.

diode current) is the nonstock value of 60 ohms which may be obtained by series connecting two 30-ohm resistors.

Greater constancy of output voltage, against input-voltage fluctuations, is obtained with a 2-stage circuit. The output stage then smooths out the fluctuations that normally are too low for the first stage to remove. Figure 8-16(B) shows such a cascade circuit. Here, the first stage, embodying a 1N1771A diode, delivers 10 volts from an 18-volt input. Any fluctuations in this 10-volt output then are removed by the second stage, which embodies a 1N370 diode. The output of this final diode is the required 1.8 volts. In this circuit, the first series resistance (R1) is a stock value; however, the second series resistance (R2) is a nonstock and may be obtained by parallel connecting two 820-ohm resistors.

DC voltage standards may be used for calibrating such devices as meters, DC oscilloscopes, potentiometric recorders, millivolt potentiometers, thermocouple systems, and similar apparatus.

9

Diac

The *diac* is a comparatively simple switching device of the thyristor family, in which the semiconductor contains three layers, as in a PNP transistor. Connections are made only to the two outer layers, so the diac has only two terminals and it operates on either AC or DC, conducting in either direction. Like other thyristors, the diac behaves somewhat in the manner of a thyatron tube.

The diac finds application principally in control, switching, and trigger circuits where a bidirectional, 2-terminal switching device is advantageous. It may be used by itself or in conjunction with a triac or a silicon controlled rectifier.

Before working with diacs, read the hints and precautions in Chapter 1.

DIAC THEORY

Figure 9-1(A) shows the basic structure of the diac, and Fig. 9-1(B) the circuit symbol. In this device, the doping concentration, unlike that of the junction transistor, is the same for both junctions, and this enables symmetrical operation. Neither terminal is exclusively anode or cathode. Because of the series arrangement of P and N layers inside the device, the diac can never conduct in the forward direction, but always behaves as a reverse-biased avalanche diode, regardless of the direction of an applied voltage.


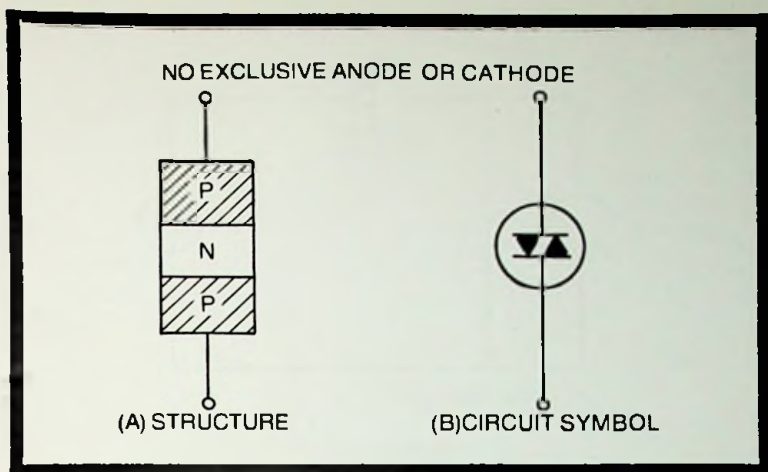


Fig. 9-1. Details of diac.


Figure 9-2 illustrates behavior of the diac. When a voltage is applied to the device, as in Fig. 9-2(A), a very small leakage current flows: this is the *off* state of the diac. As the voltage is increased, a critical value termed the *breakover voltage* eventually is reached (V_{BO}^+ when the voltage is positive, V_{BO}^- when it is negative) and at this point avalanche breakdown occurs and a heavy current suddenly flows; this is the *on* state of the diac. Once the diac is thus switched *on* by a positive or a negative voltage, the device will continue to conduct current until the voltage is removed or reduced to zero.

Figure 9-2(B) depicts diac action. Here, a small leakage current (I_{BO}^+ for a positive voltage, or I_{BO}^- for a negative voltage) flows until the applied voltage reaches the breakover value (V_{BO}^+ or V_{BO}^- , as the case may be). When the breakover voltage is reached, the current increases sharply, as from I_+ or I_- . A negative-resistance effect sets in—as shown by the backward bend of the curve—and consequently the current increases as the applied voltage is subsequently decreased.

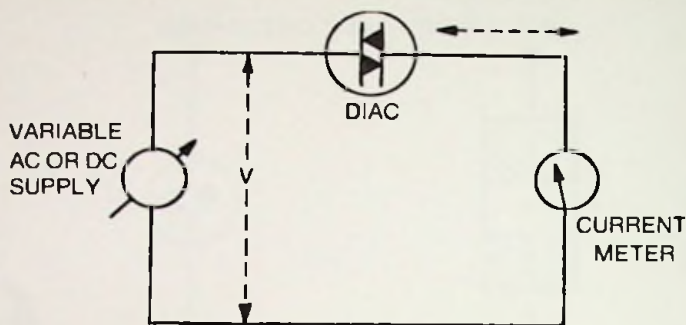At this writing, the principal use of the diac is to supply a trigger pulse to a triac, and this application is illustrated in a number of ways in Chapter 10. However, the triggered response of the diac itself and the bilateral conduction of this device also suit it to certain applications other than triac



(A) BASIC CIRCUIT

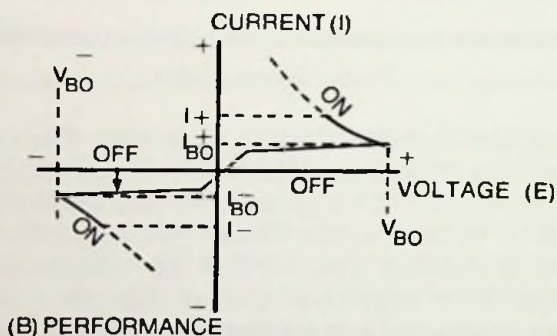

(B) PERFORMANCE

Fig. 9-2. Diac action.

operation. Several of these are described in this chapter and possibly will suggest still others to the experimenter.

AMPLITUDE-SENSITIVE SWITCH

The simplest application of the diac by itself is automatic switching. A diac appears to either AC or DC as a high resistance (almost an open circuit) until the impressed voltage reaches the critical V_{BO} value. The diac conducts when this value is reached or exceeded. Thus, this simple 2-terminal device may be switched *on* simply by raising the amplitude of the applied control voltage, and it will continue to conduct until the voltage has been reduced to zero.

Figure 9-3 shows a simple amplitude-sensitive switch circuit employing a 1N5411 diac. An applied voltage of 35 volts DC or peak AC will switch the diac into conduction, whereupon

it will pass a current of approximately 14 mA through the output resistor, R2. Individual diacs may switch on at voltages lower than 35 volts. With 14 mA on current, the output voltage developed across the 1000-ohm resistor will be 14 volts. If the voltage source has an internal conductive path in its output circuit, resistor R1 may be omitted.

In operating the circuit, adjust the input voltage upward slowly from zero while monitoring the output. Up to approximately 30 volts, there will be little or no output voltage, owing to the very low leakage current of the diac. At approximately 35 volts, however, the diac will suddenly break down and an output voltage will appear across resistor R2. Reduce the input voltage, and note that the output voltage also decreases, eventually reaching zero when the input voltage is zero. At zero, the diac is "extinguished," and is in condition to be triggered again by the 35-volt amplitude.

STATIC DC SWITCH

The simple switch described in the preceding section may be triggered also by means of a change in voltage. Thus, a steady voltage of say 30 volts may be applied continuously to the 1N5411 diac without conduction taking place; but if an additional voltage of say 5 volts is added in series, the

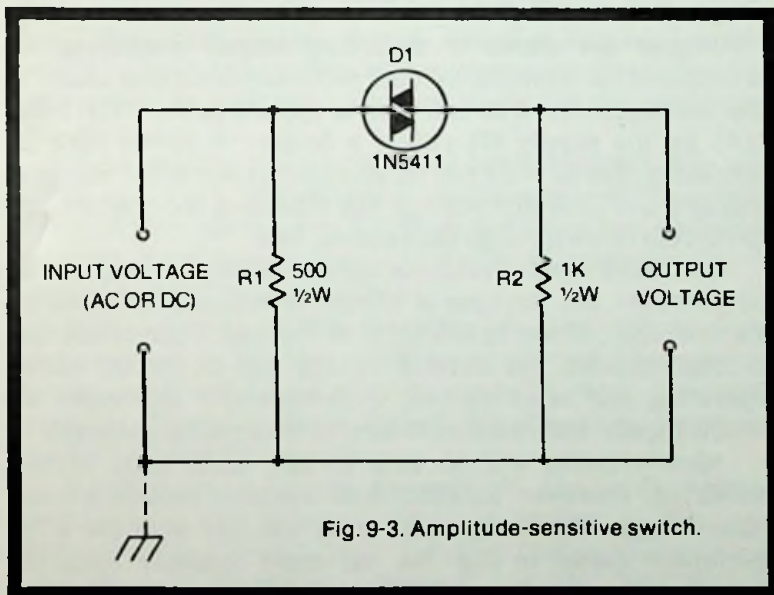


Fig. 9-3. Amplitude-sensitive switch.

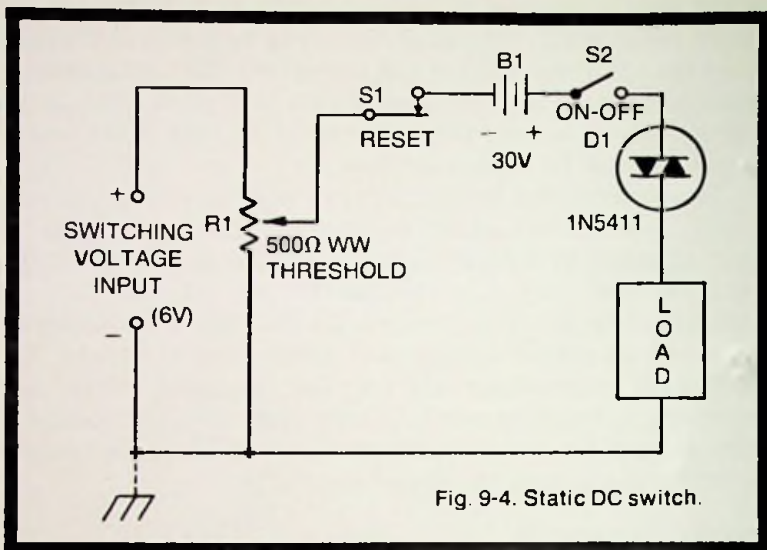


Fig. 9-4. Static DC switch.

breakdown voltage of 35-volts is reached and the diac "fires." Removal of the 5-volt "signal" then will have no effect on the conduction which will continue until the 30-volt supply voltage is reduced to zero. This behavior is somewhat similar to that of a thyratron tube, but in this instance is obtained with the simple 2-terminal diac.

Figure 9-4 shows a switching circuit employing the principle of incremental-voltage switching described above. In this arrangement, a 30-volt bias is applied to the 1N5411 diac (D1) by the supply B1 (while a battery is shown here for simplicity, the 30 volts can be supplied by any other source of steady DC). With this voltage, the diac does not conduct, and no current flows through the external load.

When the input voltage is applied through potentiometer R1, however, the increase in voltage is sufficient to switch the diac on, and current is delivered to the load. Once conduction is thus initiated, the control voltage has no further effect. Operating the *reset* switch, S, temporarily interrupts the 30-volt supply and restores control to the switching voltage.

Most 1N5411s will be able to idle at 30 volts without self-firing. However, an individual unit may require a lower bias voltage. Similarly, most units will fire with the 6-volt increment shown in Fig. 9-4, but more sensitive units will operate with a smaller switching voltage which may easily be

selected by means of the 500-ohm wirewound potentiometer, R1.

The maximum load resistance recommended for use in this circuit is 1000 ohms. The load current at this resistance is approximately 14.3 milliamperes.

This circuit will find use wherever a simple electrical latching action is desired without the complexity of 3-element thyristors and where the current demand is not severe. Individual diacs show surprising sensitivity in this simple arrangement.

ELECTRICALLY LATCHED RELAY

Figure 9-5 shows the circuit of a DC relay that will remain closed (latched) once it has been actuated by a control signal, and has the dependability of a mechanically latched relay. This circuit employs the principle described in the preceding section; that is, the IRD54-C diac here is biased at 30 volts, a potential too low for conduction. But when a 6-volt increment is applied to the diac, the latter passes current which picks up the relay (the diac then continues to conduct, holding in the relay, although the 6-volt control voltage ceases).

In this circuit, most IRD54-Cs will be able to idle at 30 volts without self-firing; however, an individual unit may require a lower voltage. Similarly, most units will fire readily with the 6-volt increment (control signal) shown in Fig. 9-5, but more sensitive units will operate with a lower control voltage which may easily be selected by means of the 500-ohm wirewound potentiometer, R1.

In its *on* state, the diac passes a current of 2 mA. The relay (RY1) is a 1 mA, 1000-ohm unit, so the extra 1 milliamperes is diverted through resistor R2. Since the latter is a wirewound rheostat, it can be adjusted—along with potentiometer R1—for desired sensitivity of response.

While a 6-volt potential is required in series with the 30-volt bias to switch *on* the diac, a higher-voltage control signal may be employed, and R1 adjusted for the 6-volt value. The 30-volt supply is shown here as a battery, for simplicity, but can be any well-filtered DC source.

When R1 and R2 are properly set, the relay picks up readily when the control signal is applied to the input terminals of the circuit. Then, the relay continues to hold even when the control signal is removed, and holds until the *reset*

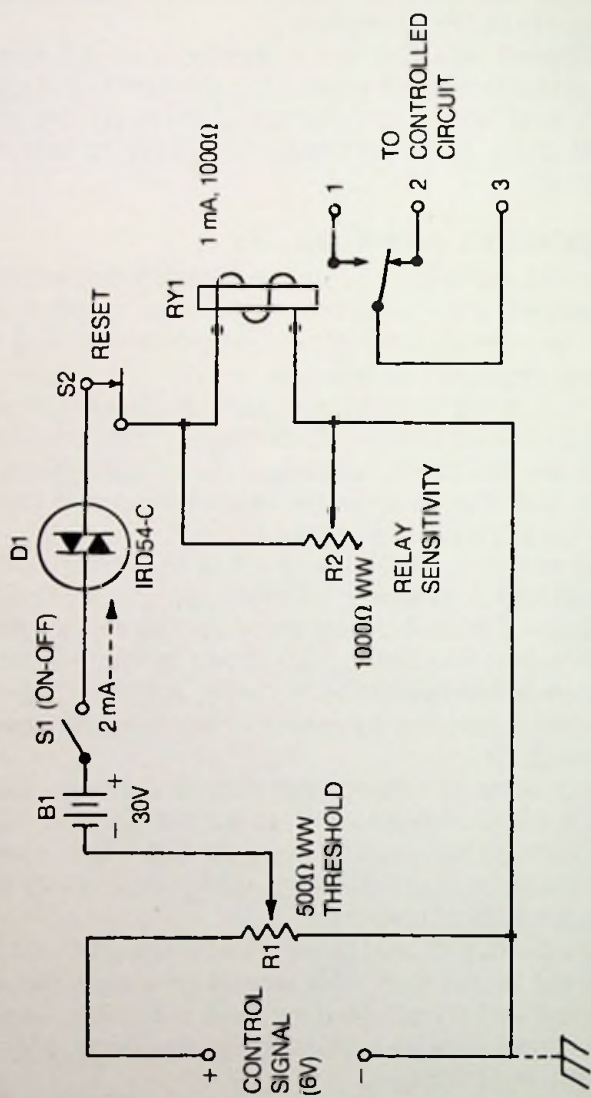


Fig. 9-5. Electrically latched relay.

switch, S2, is depressed momentarily. The relay is a 1 mA, 1000-ohm unit (Sigma 5F or equivalent) having ¼-ampere contacts. Use terminals 1 and 3 when the external circuit must be closed by relay closure; use 2 and 3 when the external circuit must be opened. If the ¼-ampere contact rating is too low for the power to be handled in the controlled circuit, a higher-wattage auxiliary relay may be operated from this circuit.

LATCHING SENSOR CIRCUIT

Some systems, such as burglar alarms and process controllers, require an actuating signal that remains *on* after it has been initiated and ceases only when operation is reset from a central control point. Once available, this signal can be used to drive circuitry for alarms, recorders, shutoff valves, safety devices, and so on.

Figure 9-6 shows a circuit of this type. Here, a HEP R2002 diac is the switching device. In this arrangement, the diac idles at 30 volts, supplied by B2, and passes such a low current that virtually no voltage appears across the 1000-ohm output resistor, R2. However, closure of switch S1, which may be a "sensor" on a door or window, adds 6 volts (from B1), to the 30-volt bias, and the resulting 35 volts fire the diac and produce approximately 1-volt output across R2. The diac then remains *on* in spite of any subsequent opening of S1 (as by closing of the door or window) until the *reset* switch (S2, at a secret location) is temporarily opened. Any number of "sensor"

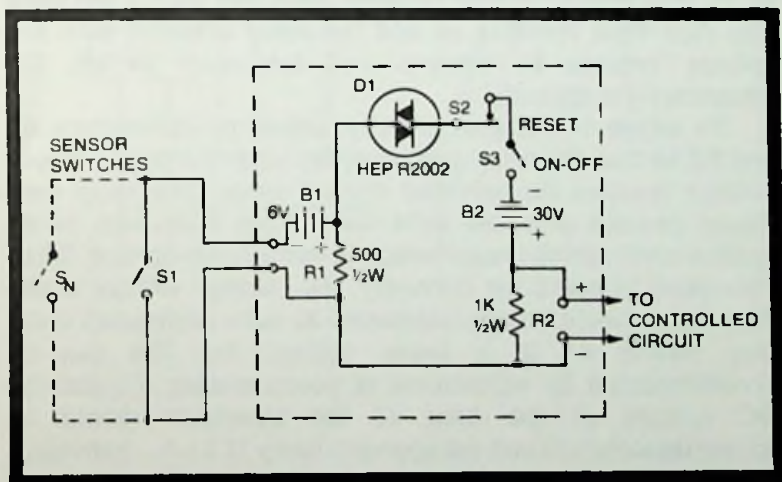


Fig. 9-6. Latching sensor circuit.

switches, such as S_n , may be operated in parallel, but this system requires that switches close when actuated, whereas the common burglar alarm system requires that they open.

While batteries are shown for simplicity, both the B1 and B2 voltages may be obtained from any other source of well-filtered DC. The 30 volts may be obtained with any convenient combination of batteries (one selection is two 15-volt units: Eveready 417, or equivalent).

For output voltage of the opposite polarity, simply reverse the connections to B1 and B2; the diac, being bilateral, requires no reversal.


DC OVERLOAD CIRCUIT BREAKER

Figure 9-7 shows a circuit that automatically disconnects a load device from its power supply when the DC operating voltage exceeds a predetermined value. The device then remains disconnected until the voltage is reduced *and* the circuit is reset.

In this arrangement, employing an IRD54-C diac and 2N2712 silicon bipolar transistor, the diac (D1) is normally in its *off* state, and the static current of the transistor (Q1) is too tiny to actuate the sensitive relay (RY1). When the power supply voltage exceeds a critical value determined by the setting of potentiometer R1, the diac switches *on* and its DC output is applied to the transistor through potentiometer R2. The resulting increase in collector current actuates the relay which then opens the lead between the power supply and load. The diac then remains *on* and the relay actuated until the voltage returns to normal *and* the *reset* switch, S1, temporarily is opened.

To adjust the circuit initially, adjust potentiometers R1 and R2 so that the relay just operates when the power-supply voltage reaches the selected critical value. The relay then should remain actuated until the voltage falls back to its normal level and the *reset* switch is temporarily opened. When the circuit is operating correctly, the "firing" voltage at the diac input should be approximately 35 volts (individual diacs may switch *on* at a lower voltage, but this can be accommodated by adjustment of potentiometer R), and the DC voltage at the base of the transistor should be approximately 0.57 volt (at approximately 12.5 μ A). Individual transistors may require higher or lower voltage here, but this can be accommodated by means of potentiometer R2.

Fig. 9-7. DC overload circuit breaker.

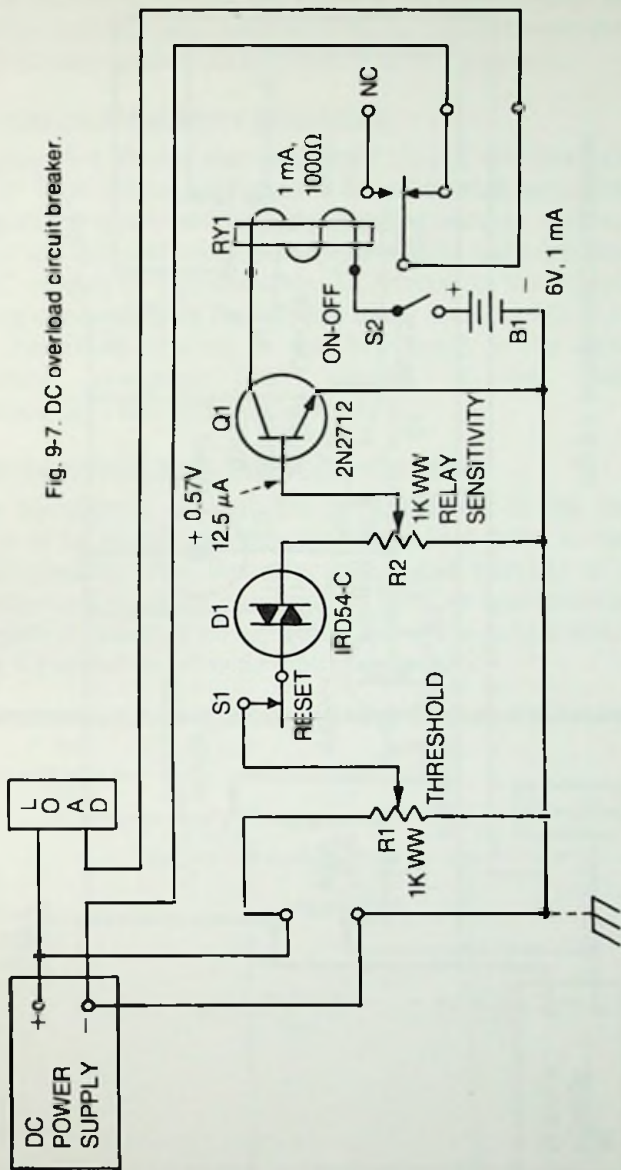

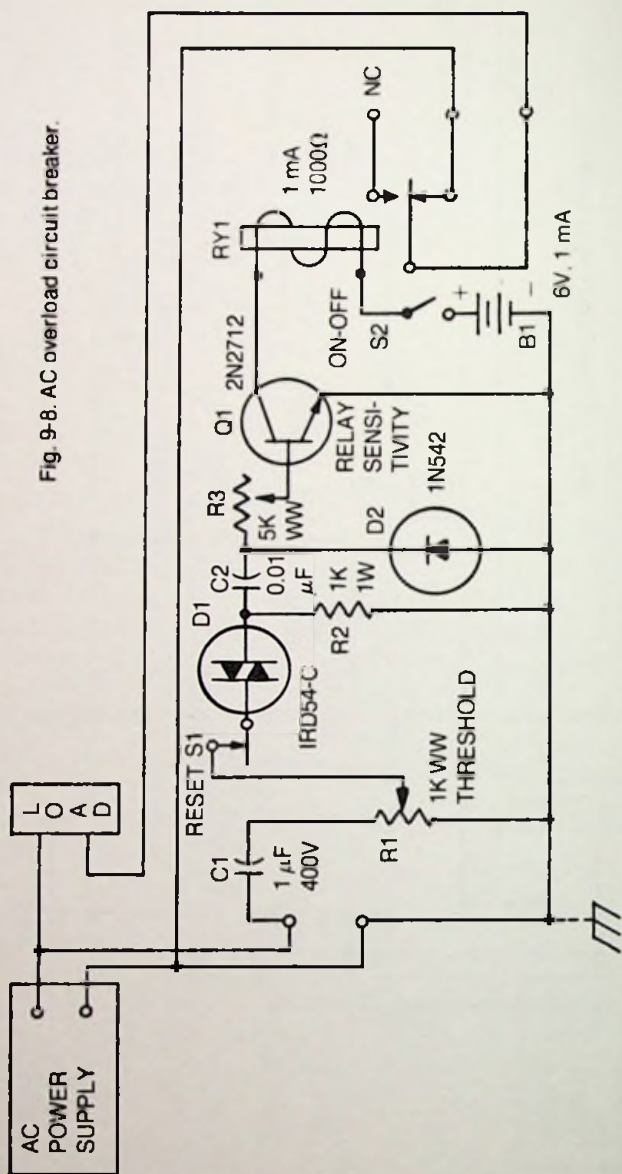


Fig. 9-8. AC overload circuit breaker.

The relay is a 1 mA, 1000-ohm unit (Sigma 5F, or equivalent). As shown in the diagram, only two of the relay contacts are used, giving the relay a normally closed status. The relay contacts are rated $\frac{1}{4}$ -watt; for higher power service, relay RY1 can actuate an auxiliary heavier duty unit.

AC OVERLOAD CIRCUIT BREAKER

Figure 9-8 shows the circuit of an AC overload circuit breaker. This circuit performs in the same manner as the DC arrangement described in the preceding section, and may be read for the general description of operation and performance. The AC circuit differs from the DC circuit in the addition of blocking capacitors C1 and C2 and diode rectifier D2; also, the *relay sensitivity* control in the AC circuit is the 5000-ohm wirewound rheostat (R3) instead of the 1000-ohm potentiometer (R2) in the DC circuit.

PHASE-CONTROLLED TRIGGER CIRCUIT

As mentioned earlier, the principal use of the diac at present is to supply a trigger voltage to a triac in various control circuits. The diac circuit for this purpose is phase controlled and by itself can find use in other applications than triac control, where a phase-adjustable pulse output is needed. Figure 9-9 shows the classic diac trigger circuit.

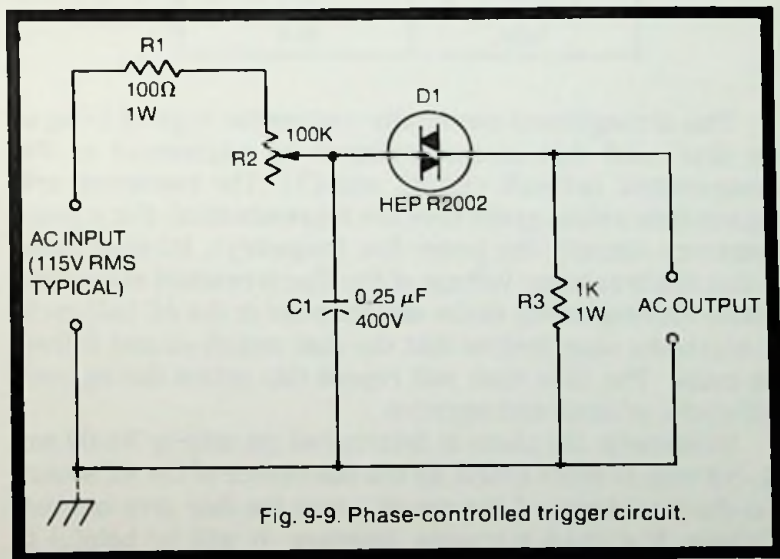


Fig. 9-9. Phase-controlled trigger circuit.

Table 9-1. Phase Angles For Various Resistances When $C = 0.25 \mu F$

$f = 60 \text{ Hz}$ $C = 0.25 \mu F$

RESISTANCE (R, ohms)	PHASE ANGLE (degrees lag)
100	0.5
200	1.1
300	1.6
400	2.2
500	2.7
600	3.3
700	3.8
800	4.3
900	4.9
1000	5.4
2K	10.7
3K	15.8
4K	20.7
5K	25.2
6K	29.5
7K	33.4
8K	37.1
9K	40.3
10K	43.3
20K	62.1
30K	70.5
40K	75.2
50K	78.1
60K	80
70K	81.4
80K	82.5
90K	83.3
100K	84.0

This arrangement essentially controls the angle of firing of the diac, and this is accomplished by adjustment of the phase-control network (R1-R2 and C1). The resistance and capacitance values given here are representative. For a given frequency (usually the power-line frequency), R2 is adjusted so that the breakover voltage of the diac is reached at the time instant corresponding to the desired point in the AC half-cycle at which the user desires that the diac switch *on* and deliver the pulse. The diac then will repeat this action during each half-cycle, positive and negative.

Ultimately, the phase is determined not only by R1-R2 and C1, but also to some extent by the impedance of the AC source and the impedance of the circuit which the diac arrangement triggers. For most purposes, however, it will be helpful to

examine the phase of the diac-circuit resistance and capacitance to determine performance of the circuit.

Table 9-1, for example, shows the phase angles corresponding to various settings of the resistance against the $0.25 \mu\text{F}$ capacitance in Fig. 9-9. The data are given for 60 Hz, the frequency at which the diac trigger circuit is so often used. Note from these data that as the resistance is lowered, the trigger pulse appears earlier and earlier in the supply-voltage cycle, thereby enabling the diac to "fire" earlier in the cycle and to conduct longer. Because the RC circuit consists of series resistance and shunt capacitance, the phase is, of course, lagging—which means that the trigger pulse *follows* the supply-voltage cycle in time sequence.

10

Triac

The *triac* is a 3-electrode device of the thyristor family, which can switch either AC or DC. Unlike the diac (Chapter 9), it has a separate control (gate) electrode which allows selection of the voltage level at which the triac begins to conduct. Like other thyristors, the triac behaves somewhat in the manner of the thyatron tube.

The triac finds application principally in control, switching, and trigger circuits. It is used singly or in conjunction with diacs, transistors, or silicon controlled rectifiers. The ratings of triacs cover a wide range, typical values being 100 volts to 600 volts and 0.5 amps to 40A.

Before working with triacs, read the hints and precautions in Chapter 1.

TRIAC THEORY

Figure 10-1A shows the basic internal structure of the triac, and Fig. 10-1B the circuit symbol. In this device, main terminals 1 and 2 are the *output* and *common* terminals, and the gate is the *input* or control terminal. Because of the series P and N layers in the triac pellet, this device—like the diac—can never pass current from terminal 1 to terminal 2 in the forward direction, regardless of the polarity of the applied voltage, but always behaves as a reverse-biased diode.

Figure 10-2 depicts performance of the triac. When a voltage is applied to this device, as from the main power


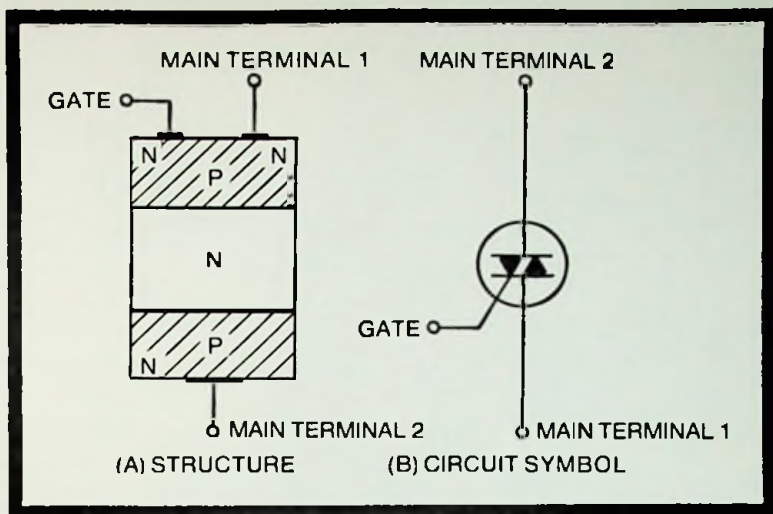


Fig. 10-1. Details of triac.


source as shown in Fig. 10-2A, a very small leakage current flows (as from 0 to A, or 0 to D in Fig. 10-2B); this is the *off* state of the triac. As the voltage is increased, a critical value eventually is reached (V_{BO}^+ in the positive direction, or V_{BO}^- in the negative direction) at which avalanche breakdown occurs and a heavy current suddenly flows (B to C and beyond, or E to F and beyond); this is the *on* state of the triac. The breakover voltage (V_{BO}^+ or V_{BO}^-) is determined by the amplitude of a positive or negative current pulse supplied to the gate electrode; the higher this amplitude, the lower the breakover voltage.

Figure 10-2B shows that the triac *snaps* to its *on* state, positive or negative. As in a thyatron tube, once PC conduction has been initiated in the triac, the gate electrode under ordinary conditions exerts no further control until the voltage from terminal 1 to terminal 2 is interrupted or otherwise reduced to zero.

Unlike the diac, the triac has exclusive terminals which must not be interchanged. Thus, in the circuit diagrams in this chapter, Main Terminal 1 is labeled MT1, Main Terminal 2 is labeled MT2, and the gate is labeled G. The gate electrode is at the Main Terminal-1 end of the triac structure (see Fig. 10-1A) and is so indicated in the circuit symbol (see Fig. 10-1B and the circuit diagrams in this chapter).

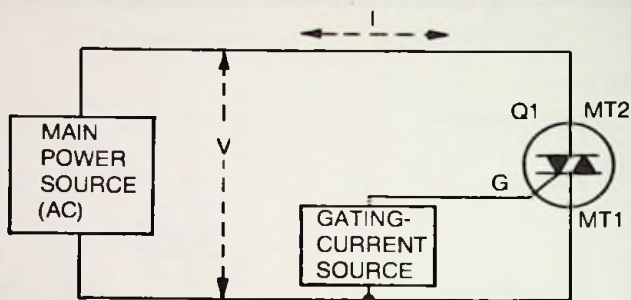

(A) BASIC CIRCUIT

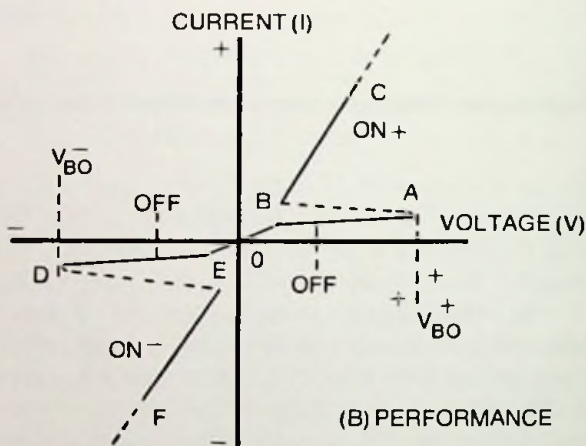

(B) PERFORMANCE

Fig. 10-2. Triac action.

Some Triacs may be worked harder than usual if a heat sink is provided for them. An immediate example is the triac motor control: In some instances, a $\frac{1}{4}$ -horsepower motor is the largest machine that can be accommodated by a certain control circuit; but if the triac is provided with a suitable heat sink, a $\frac{1}{2}$ -horsepower motor can be safely controlled.

For light dimmers, RCA advises that with small units built into the socket of the controlled lamp and handling up to 2 amps rms, sufficient heat sinking can be obtained from the lead wires to which the triac is attached. But up to 6 amps in a wall-mounted unit, the triac must be fastened to the metal wall box and face plate for sinking, and for still higher current, the

face plate must be of a type that can be mounted clear of the wall for air flow underneath.

SIMPLE TRIAC SWITCH

In the simplest application of triac theory, an AC-powered triac may be turned off by removal of the gate current. In this way, a large AC current (amperes) can be switched on and off through a load by means of a very small gate current (milliamperes). The ratio of controlled power (a characteristic somewhat similar to power amplification) can have a value of several thousand to one. The load can be any device—such as a motor, lamp, or heater—operating within the current rating of the triac, that ordinarily would be operated by means of a switch, heavy-duty relay, high-current thermostat, or similar control.

Figure 10-3A shows the circuit of a simple switch employing a 2N5754 triac. The latter is rated at 2.5 amps, and a heavier-duty triac may be used in its place if higher-current operation is desired. The adjustable trigger current is supplied by the resistance combination R1-R2 connected back to the supply voltage. Rheostat R1 is a 200,000-ohm, 1-watt, linear-taper unit (Mallory Midgetrol or equivalent). Fixed resistor R2 protects the rheostat from direct connection to the high voltage. Normally open switch S2 (SPST) is the triggering device. Instead of a simple switch, however, the light-duty contacts of a sensitive relay, a photoconductive cell, or a temperature sensor might be used. Closing the contacts or reducing the resistance of the sensor passes approximately 10 mA into the triac gate section and switches the triac *on* to pass up to 2.5 amps through the load.

Figure 10-3B depicts operation of the circuit. The plot shows the angle of start and the duration of main current flow. Because of the simple resistive control circuit, the gate current is in phase with the triac voltage. When the gate current is low at the beginning of the AC cycle, however, the triac acts as a very high resistance and virtually no current flows through the load.

When R1 is appropriately set for a given triac and AC voltage, the gate current reaches the trigger value for the 2N5754 when the supply voltage is at the maximum point in the cycle, and the triac is abruptly switched *on*. Conduction then continues until the end of the positive half-cycle, whereupon Q1

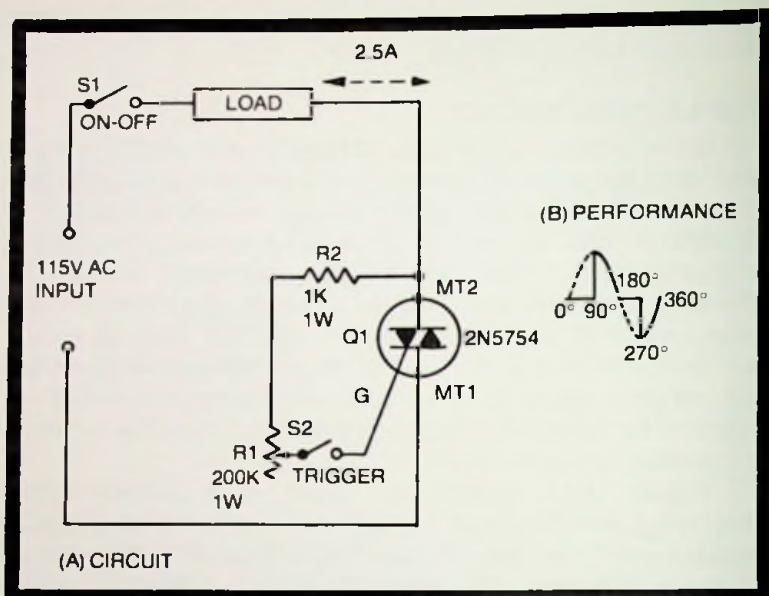


Fig. 10-3. Simple triac switch.

switches *off* as the supply-voltage cycle passes through zero, and remains *off* until the maximum-voltage point in the negative half-cycle is reached. At that point, Q1 again switches *on* and remains *on* until the zero point at the end of the cycle. Thus, the trigger voltage and current determine the instant at which the triac is switched *on* and the interval of current flow through the load, in this instance the flow being from 90° to 180° and from 270° to 360°.

If rheostat R1 is adjusted to a lower resistance, the trigger-voltage value will be reached earlier in the cycle and the load current will flow for a greater part of each half-cycle. This is essentially an *off-on* circuit and might invite the question of why it should be used in lieu of a simple switch, such as S1. The answer is that a switch such as S1 must handle the full 2.5 amps, whereas S2 (in whatever form) need handle only a few milliamperes. Any pair of light-duty contacts—or equivalent device—can serve as S2.

GENERAL-PURPOSE CONTROLLER

Figure 10-4 shows the circuit of an AC controller which, though very small by comparison, may be used in the manner

of a Variac to adjust the AC input to any device connected to the *load* socket that is capable of control by a triac. The 40429 triac shown here provides a maximum output current of 6 amps and may be operated up to 200 volts. The range of control, from maximum output to very nearly complete cutoff, is provided by a simple, volume-control-type rheostat (R1).

The triac is triggered by means of a 40583 diac (D1) operated from a "tuned" phase-shift network, R1C1. (See Chapter 9 for a general discussion of the diac trigger circuit.) The point in the AC supply-voltage cycle at which the diac triggers the triac is determined by the setting of R1 which, in turn, adjusts the phase of the trigger with respect to that of the supply voltage.

In this way, the rheostat setting determines the angle of flow and consequently the output current (once the triac has been triggered, output current continues to flow until the end of that half-cycle, and is retriggered at the corresponding point in the succeeding half-cycle: See Fig. 10-3B). The lower the resistance setting of R1, the higher the output current of the circuit.

Because no practical capacitor (C1) can give the full 90° phase shift attributed to capacitance, the phase shift of the R1C1 network is never sufficient to cut the triac completely off: nevertheless, the control range is wide and very useful.

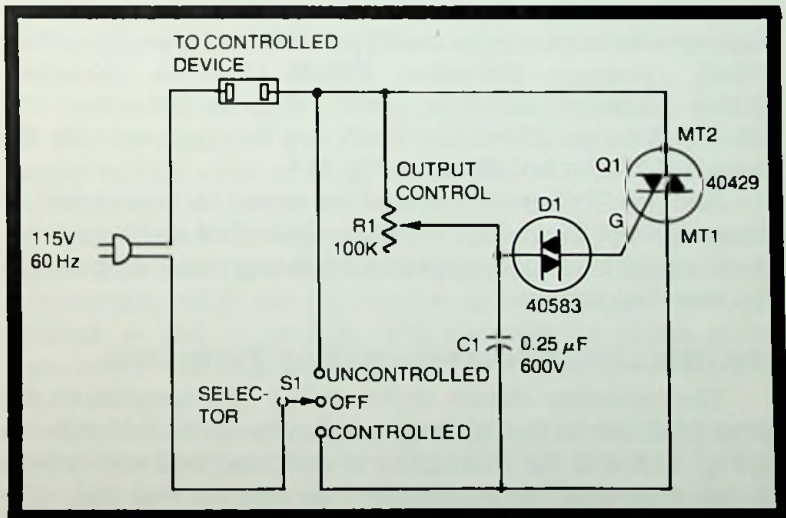


Fig. 10-4. General-purpose controller.

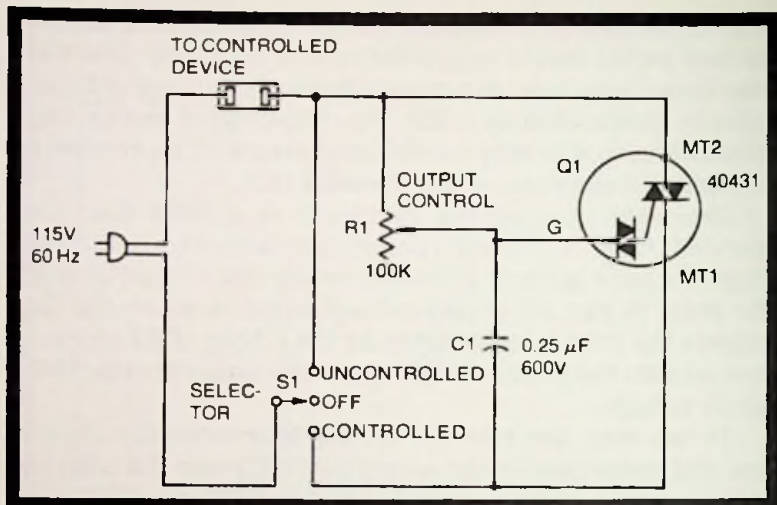


Fig. 10-5. Controller using combination thyristor.

For complete turn-on and turn-off, switch S1 acts as a mode selector. In the *uncontrolled* position of this switch, the full line voltage is applied to the load without benefit of the controller circuit which then stands idle. With S1 in the *controlled* position, the load is supplied with adjustable current delivered by the triac. With S1 in its *off* position, the load is deenergized.

For heavier-duty service than that afforded by the 6-amp triac shown in Fig. 10-4, higher-powered triacs are available. Representative examples are Types 40668 (8-amperes, 200-volts), 2N5567 (10-amperes, 200-volts), 2N5568 (10-amperes, 400-volts), 2N5571 (15-amperes, 200-volts), 40707 (30-amperes, 200-volts), and 2N5444 (40-amperes, 200-volts). Each may be triggered with the same R1C1D1 circuit shown in Fig. 10-4.

Some of the familiar uses of the circuit include control of lamps (except fluorescent), motors (universal and induction), electric heater or oven elements, soldering irons, AC-powered electronic apparatus.

CONTROLLER USING COMBINATION THYRISTOR

The controller circuit shown in Fig. 10-5 operates on the same principle as that of the general-purpose controller shown in Fig. 10-4, and the description of operation and applications in the preceding section applies as well to Fig. 10-5. The difference is that the latter circuit employs a 40431

combination thyristor (Q1) which contains both the diac and triac units. This combination unit somewhat simplifies assembly, wiring, and replacement.

The 40431 thyristor is rated at 6-amps, 200-volts. A similar unit—Type 40432—is rated at 6A, 400V. Type HEP R1725 is equivalent to 40431, and HEP S0015 is equivalent to 40432. All may be operated with either resistive or inductive loads.

DC-CONTROLLED SOLID-STATE AC RELAY

In electrical and electronic installations, it is often necessary to switch high AC voltage and current with a low-current DC control signal. At least two electromechanical relays operating in cascade usually are required for this purpose, since the contacts of a sensitive (low-voltage, low-current) DC relay cannot handle the high AC current.

For this application, an all solid-state relay circuit—with no moving parts whatever—may be achieved with a suitable triac, since a triac may be switched with a DC gate trigger of either polarity and requires only a few milliamperes to switch several amperes.

Figure 10-6 shows such a circuit. The 40773 triac (Q1) shown here is rated at 2.5-amps, 200-volts. A similar unit—Type 40774—is rated at 2.5-amps, 400-volts. In this arrangement, the triac is triggered *on* by a DC gate voltage (1.5 to 2 volts at 20 milliamperes) applied to the DC *control-signal input* terminals. The trigger-voltage and current values may differ somewhat from these figures with individual triacs.

Once the triac has switched *on*, it will continue to conduct for the remainder of the AC half-cycle, extinguishing as the supply-voltage cycle crosses the zero line, and retriggering at the corresponding point in the succeeding half-cycle. AC will continue to flow through the load as long as the DC control signal is present at the gate, and will cease when the DC is interrupted. While the DC *control-signal input* terminals are labeled + and - in Fig. 10-6, the polarity shown is not mandatory; the triac triggers on either a positive or a negative gate voltage.

This relay circuit allows 2.5 amps at 115-volts AC to be switched with approximately 20 mA at 1.5–2 volts DC. This represents a current-control ratio of 9583:1 when the DC control voltage is 1.5. For increased sensitivity, a transistor or

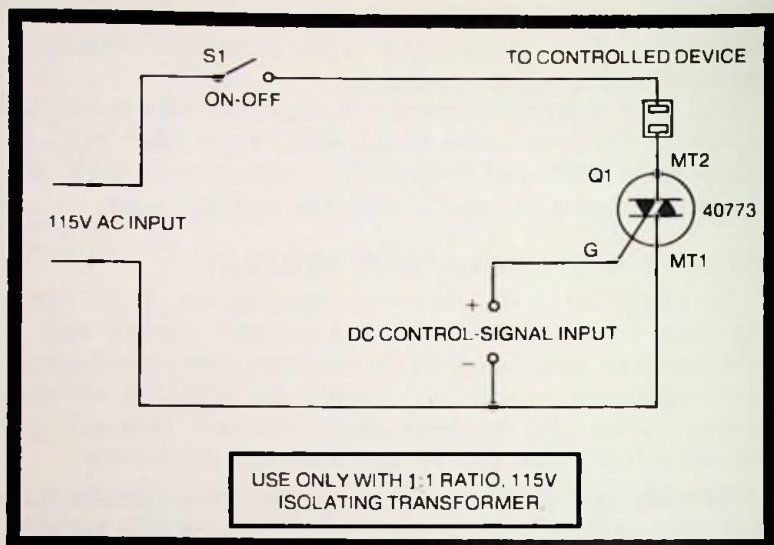


Fig. 10-6. DC-controlled solid-state AC relay.

IC direct-current amplifier may be operated between a millivolt/microampere type of DC signal source and the DC *control-signal input* terminals (see, for example, Fig. 10-7).

Because this type of relay circuit is often operated from an external DC signal source which must be returned to main terminal 1 of the triac as shown in Fig. 10-6, this source will automatically be connected *dangerously* to one side of the AC power line. Therefore, to avoid electric shock or damage to the equipment, it is advisable to insert a 1:1 isolating transformer between the power line and the circuit in Fig. 10-6.

When this solid-state relay must switch higher current than the 2.5-amp rating of the 40773 triac, employ a heavier-duty triac at Q1. Higher-current triacs include Types 40733 (4.2-amps, 200-volts), 40429 (6-amps, 200-volts), 40668 (8-amps, 200-volts), 2N5567 (10-amps, 200-volts), 40662 (30-amps, 200-volts), and 40688 (40-amps, 200-volts).

SENSITIVE DC-CONTROLLED TRIAC SWITCH

Figure 10-7 shows an all solid-state circuit that can switch 0.5 ampere at 115-volts AC in response to a DC control signal of 47 μA at 1.5-volts. This performance represents a current-control ratio of 10,638:1, and a power-control ratio of 815,603:1.

In this circuit, the DC control signal is amplified by a single-stage DC amplifier based upon the 2N2716 silicon bipolar transistor (Q1) to an output current of 10 mA which is applied as a gate current to trigger the 40769 triac (Q2) into conduction. The triac conducts AC through the load as long as the DC is present at the *DC control-signal input* terminals, and ceases when the DC is interrupted. The 2N2716 provides very low-drift operation, insuring against self-triggering of the circuit.

With individual transistors and triacs, the DC signal requirement may differ somewhat from the 1.5-volts and $47\ \mu\text{A}$ indicated in Fig. 10-7. The DC control signal can be obtained from a rectifying diode, self-generating photocell, photoconductive cell, thermocouple, light-duty contacts making and breaking a $47\ \mu\text{A}$ input current, and so on.

The floating 12-volt transistor DC supply (B1) is shown here as a battery, and a small battery will be preferred in many installations; however, a well-filtered, power-line-operated supply may be used instead. This type of relay circuit is often operated from an external DC signal source which must be returned to the emitter of the transistor and main terminal 1 of the triac, as shown in Fig. 10-7. The source thus will be automatically connected *dangerously* to one side of the

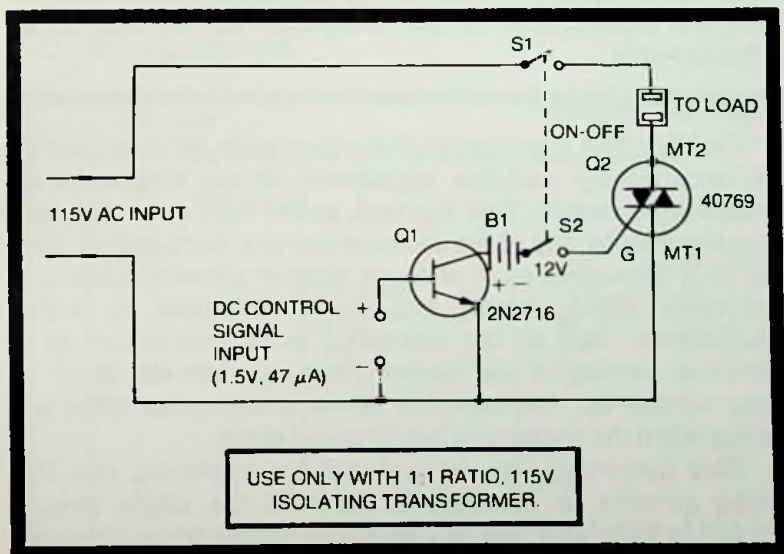


Fig. 10-7. Sensitive, DC-controlled triac switch.

AC power line. Therefore, to avoid electric shock or damage to the equipment, it is advisable to insert a 1:1 isolating transformer between the power line and the circuit in Fig. 10-7.

When this solid-state relay must switch higher current than the 0.5-amp rating of the 40769 triac, use a heavier-duty triac at Q2. Higher-current triacs include types 40767 (1.6-amps, 100-volts), 40509 (2.2-amps, 200-volts), 40691 (2.5-amps, 200-volts), 40733 (4.2-amps, 200-volts), 40429 (6-amps, 200-volts), 40668 (8-amps, 200-volts), 2N5567 (10-amps, 200-volts), 2N5571 (15-amps, 200-volts), 40662 (30-amps, 200-volts), and 40688 (40-amps, 200-volts).

For use with negative control voltage, substitute a PNP transistor for the 2N2716, and reverse both B1 and the DC control-signal input terminals.

MOTOR CONTROLS

Diac/triac circuits are very popular for controlling the speed of electric motors. The circuits given in Fig. 10-4 and 10-5 are ideal for this purpose. As the resistance setting of rheostat R1 in each of these circuits is reduced, the angle of conduction of the triac increases and so does the motor speed. These circuits will not operate satisfactorily with motors of the capacitor-start, synchronous, repulsion-induction, and shaded-pole types, but are entirely useful with universal and induction motors. Both circuits will handle motors rated up to $\frac{3}{4}$ horsepower.

LIGHT DIMMERS

One familiar application of the diac/triac AC controller is the continuously variable adjustment of the brightness of incandescent lamps. This function, called *light dimming*, can be performed by any of the common circuits, such as Figs. 10-4 and 10-5. However, each of these simpler circuits exhibits a hysteresis effect which can be troublesome in some installations; that is, the controlled lamp switches *on* at a particular setting of the control rheostat when the latter is being turned up, but switches *off* at a somewhat different setting when the rheostat is being turned down.

This hysteresis can be reduced by employing two RC timing circuits in cascade, in place of the single circuit (R1-C1) in Figs. 10-4 and 10-5, an arrangement which provides two time constants. This improvement is shown in the

light-dimmer circuits in Figs. 10-8 and 10-9. In each of these arrangements, adapted from a basic RCA circuit, the first timing leg is R2-C2, and the second leg is R3-C3.

During triggering, capacitor C3 discharges into the triac gate; but C2, being charged to a higher voltage than is C3 and having a longer discharge time, is able to replenish the C3 charge to some extent, and this reduces the hysteresis and extends the adjustment range of dimmer-control rheostat R2. The rheostat is a 200,000-ohm, 1-watt, linear-taper unit (Mallory Midgetrol or equivalent).

The two improved circuits are functionally identical. However, Fig. 10-8 employs a separate triac (type IRT82) and diac (type IRD54-C), whereas Fig. 10-9 employs a single thyristor (type 40431) which incorporates both diac and triac in the same package. Where needed, the latter arrangement somewhat simplifies construction, wiring, and replacement. The circuit given in Fig. 10-8 may be used in either 115- or 220-volt service (up to 6 amps). The circuit in Fig. 10-9 is intended solely for 115-volt service, but may be modified for 220-volt service by substituting a type 40432 unit for 40431.

A further refinement in the improved light-dimmer circuits is the inclusion of a low-pass filter (L1-C1) to suppress radio/TV interference which might otherwise result from the rapid triggering of the triac. This filter requires a high-current (5-amp) 100 μ H inductor of the smallest obtainable size (Dale IH5-100 or equivalent).

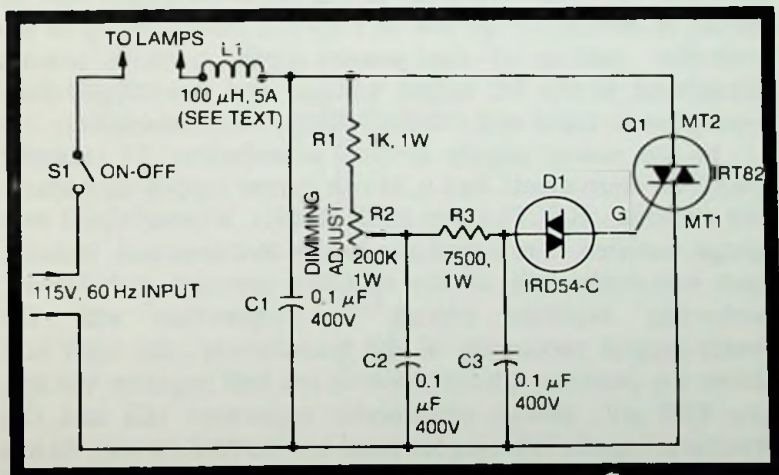


Fig. 10-8. Improved light dimmer No. 1.

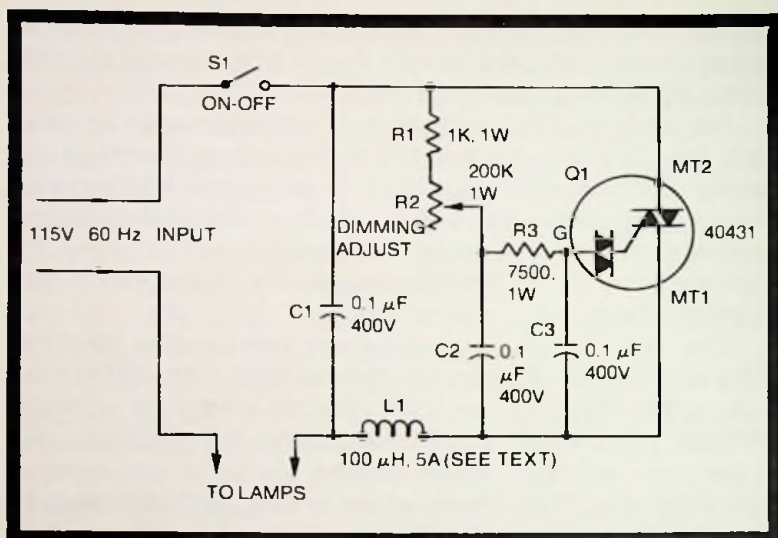


Fig. 10-9. Improved light dimmer No. 2.

VARIABLE DUAL DC POWER SUPPLY

In Fig. 10-10, a continuously variable, dual-output, DC power supply is obtained by using a triggered triac AC controller to vary the primary current of the power transformer, T1. The circuit delivers two separate maximum DC voltages: +17-volts and -17-volts, each at a maximum of 80 mA. The controller employs a type 40431 combination thyristor, Q1 (diac and triac in the same package), and its circuit is similar to the one in Fig. 10-9. Rheostat R2 in the controller section of the power supply permits smooth adjustment of the DC output voltage, and is a 200,000-ohm, 1-watt, linear-taper unit (Mallory Midgetrol or equivalent).

In the power supply section, transformer T1 (Stancor P-6377 or equivalent) has a 24-volt center-tapped secondary. The rectifier, RECT1 (type HEP RO801), although built as a bridge rectifier, is not used as a bridge in this circuit. Instead, each two-diode half of the rectifier provides a full-wave, center-tap rectifier circuit in conjunction with the center-tapped secondary of the transformer, the right half delivering positive voltage, and the left half negative voltage. The 2200 μF , 35-volt electrolytic capacitors (C3 and C4) provide adequate filtering for most low-current service. At low output-current drain, these capacitors charge to very nearly

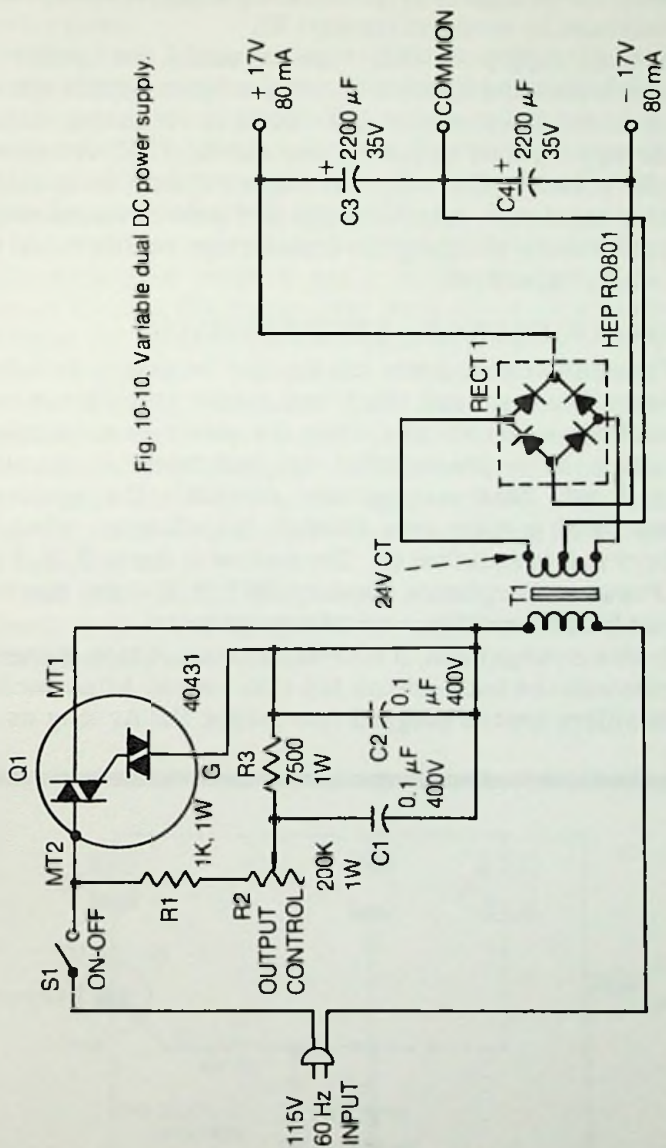


Fig. 10-10. Variable dual DC power supply.

the peak value of the 12-volt half-secondary voltage of the transformer, that is, to approximately 17 volts. At higher currents, the voltage is proportionately lower, but may easily be readjusted by means of rheostat R2.

A dual supply of this type is useful for generating adjustable plus and minus DC voltages for integrated circuits during circuit development and circuit or IC testing, and for similar applications requiring two identical DC voltages of opposite polarity. The same arrangement may be employed for other maximum output voltage and current values simply by appropriately changing the transformer, rectifier, and two electrolytic capacitors.

AUTOMATIC EQUIPMENT POWER SWITCH

Figure 10-11 shows how a triac may be used to switch off the power to a main unit (such as a master amplifier or main transmitter) automatically when the power to an auxiliary unit (such as a preamplifier or modulator) is manually switched off. This arrangement forestalls the accidental leaving on of a main unit, through forgetfulness, when the auxiliary unit is switched off. The method is due to T. N. Tyler (see *Popular Electronics*, January 1973, p. 52), and has been adapted here for readily available components.

In this arrangement, a HEP R1723 triac (Q1) is connected in series with the main-unit socket (P2) and the AC power line. The auxiliary unit is plugged into socket P1. As long as the

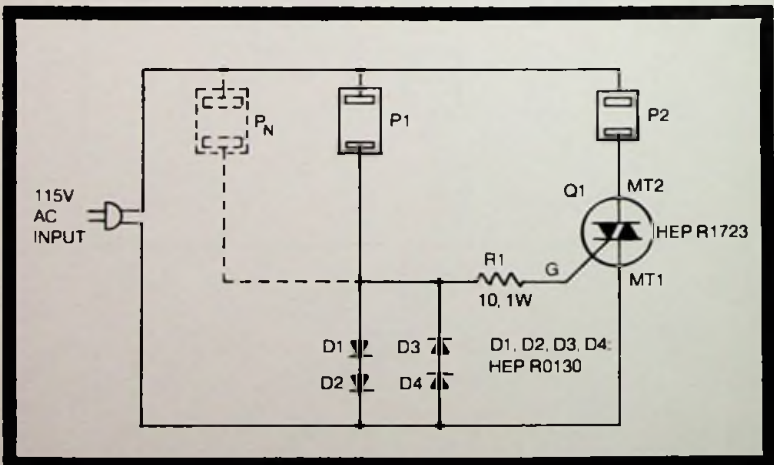


Fig. 10-11. Automatic equipment power switch.

auxiliary unit is operating, it draws its power through diodes D1 to D4, developing a voltage drop across these diodes; and this voltage triggers the triac *on*, allowing the main unit to receive power.

When later, the auxiliary unit is switched *off*, the diode voltage drop disappears, the triac switches *off*, and the main unit likewise is switched *off* even though its switch may absent-mindedly have been left *on*. If more than one auxiliary unit is used, separate sockets for them—such as P_N—may be connected in parallel with P1 and P2.

This "equipment minder" works well when the plugged-in units contain no reactive paths which can draw significant current through the diodes even when the units are manually switched *off*. Such a reactive path might be provided by a large suppressor capacitor connected across the power-line-input terminals inside the unit. The resulting capacitor current would maintain a voltage drop across the diodes and this would keep the main unit running in defeat of the whole idea. In some instances—but not all—such capacitors may be removed without degrading performance of the equipment.

The HEP R1723 triac shown in Fig. 10-11 is a 6-amp, 200-volt unit. A heavier-duty triac may be selected for higher power drain by the main unit.

11

Silicon Controlled Rectifier SCR

The *silicon controlled rectifier (SCR)* is a 3-electrode device of the thyristor family, which can switch or control DC and rectify AC with controllable angle of conduction. Like the triac (Chapter 10), it has a separate gate (control) electrode; and like other thyristors, the SCR behaves in a manner analogous to that of the thyatron tube—even more so than does the triac. Unlike the triac, the SCR can conduct in only one direction; its anode must be made positive and its cathode negative.

The SCR finds application principally in controlled rectification, and in inverters and control and switching circuits. It is used singly, in pairs or groups, and in conjunction with diacs, triacs, conventional transistors, unijunction transistors, or neon lamps. The ratings of SCRs cover a wide range, typical values being 1.7-amps to 35-amps and 100-volts to 700-volts.

Before working with SCRs, read the hints and precautions in Chapter 1.

SCR THEORY

The SCR is a 4-layer (PNPN) device; the arrangement of P and N layers within the pellet is shown in Fig. 11-1A. This PNPN arrangement is equivalent to an internally connected PNP transistor and NPN transistor, as shown by Fig. 11-1B. The circuit symbol for the SCR is given in Fig. 11-1C. The electrodes of the SCR are *anode* (normally positive biased),


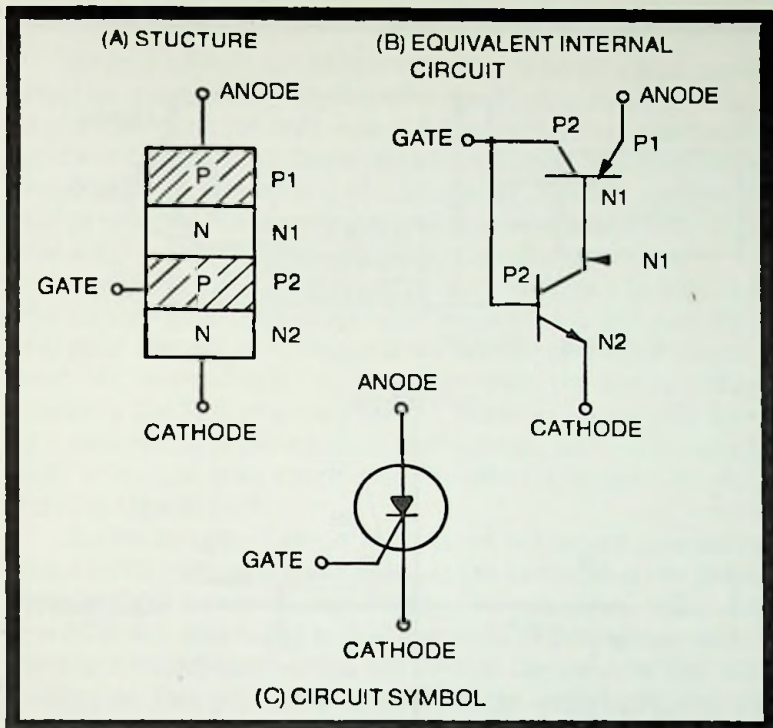


Fig. 11-1. Details of SCR.

cathode (normally negative biased), and *gate* or *control electrode*.

The basic SCR circuit is shown in Fig. 11-2A. Fig. 11-2B shows performance of the device. The SCR normally operates with anode positive, as shown here. If the anode is biased negative with respect to the cathode, only a small leakage current flows from D to E (as in a reverse-biased silicon diode).

When the reverse breakdown voltage— V_B —is reached, however, a large, potentially destructive current flows, as from E to F and beyond. When the anode is properly positive, a very small leakage current flows (as from O to A); this is the *off* state of the SCR. When the anode voltage reaches the *breakover voltage* (V_{BO}) at A, the current, due to avalanche breakdown, increases sharply (B to C and beyond); this is the *on* state of the SCR. The current at point I_h is the *holding current*. The breakover voltage (V_{BO}) is determined by the

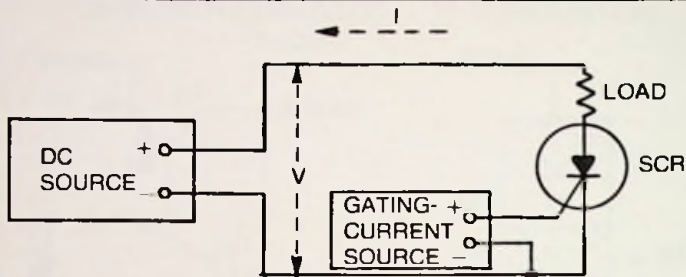

(A) BASIC CIRCUIT

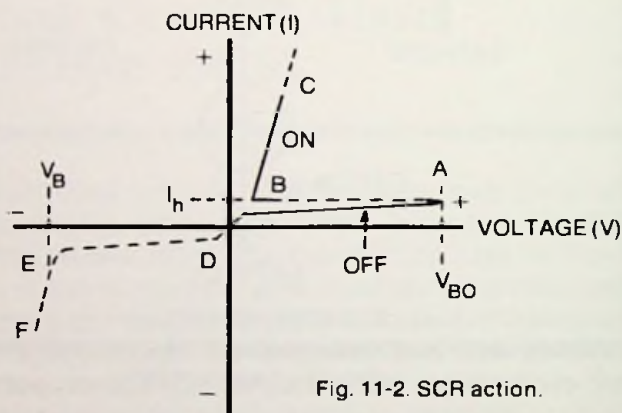


Fig. 11-2. SCR action.

(B) PERFORMANCE

value of the positive gating voltage applied to the gate electrode; the higher the gating voltage, the lower the breakover voltage, and vice versa. When the gate voltage is zero, the SCR blocks current in both directions (*off state*). From the curve in Fig. 11-2B, it is seen that the SCR *snaps* to its *on state*.

As in a thyatron tube, once conduction has been triggered in the SCR, the gate electrode—under ordinary conditions—exerts no further control of anode current until the anode-to-cathode is interrupted or temporarily reduced to zero, whereupon control is restored to the gate. Since the SCR, unlike the triac, is not a bidirectional device, it will cut off automatically and restore control to the gate at each reversal of the cycle when an AC voltage is applied to the anode (as in controlled rectification).

BASIC SCR SWITCHES

With a silicon controlled rectifier, a large anode current may be switched by means of a small gate current. Thus, a 5 mA gate current will switch 2.5 amps in a type 40810 SCR, and 8 mA will switch 35 amps in type 2N3650. The gate current can be obtained from any of a number of different sources, and many types of load devices can be operated by the SCR. This is the simplest application of silicon controlled rectifiers.

Figure 11-3 shows basic SCR static switches. In Fig. 11-3A, the IR122B SCR (Q1) is operated from the 115-volt power line. AC gate current is obtained from the line through resistors R1 and R2, accordingly, is in phase with the anode voltage. Because the SCR is a rectifier, it conducts current only during the positive half-cycles of anode voltage, and it can conduct only when the gate current has reached a critical amplitude for that type of SCR.

In this circuit, if rheostat R1 is set so that the gate current reaches its critical trigger value at the instant that the positive half-cycle of anode voltage reaches its maximum value (90°), the SCR will fire at 90° and will remain in conduction—even if switch S1 is opened—until the end of the positive half-cycle (180°). At this point, the anode voltage being zero, the SCR switches *off* and remains *off* throughout the negative half-cycle (180° to 360°), since the SCR cannot conduct when its anode is negative.

During the succeeding positive half-cycle, however, the SCR is again triggered *on* at the 90° point (if the trigger voltage is still present at the gate) and conducts to the end of that half-cycle (180°). This performance is depicted by Fig. 11-3B, which shows that the anode current flows during the last half of each positive half-cycle. If R1 is set so that the gate current reaches its trigger value earlier in the AC half-cycle, then the SCR will switch *on* earlier and anode current will flow during a longer part of the positive half-cycle. In this AC circuit, once the SCR switches *off*, when the AC cycle passes through zero, control is restored to the gate.

In Fig. 11-3C, the IR106Y1 SCR (Q1) is operated from a 35-volt DC source; otherwise, the circuit is of the same type as the one in Fig. 11-3A. In the DC circuit, if rheostat R1 is set so that the gate current has the critical trigger value required by that type of SCR, Q switches *on* when S is closed. The SCR then conducts anode current through the load and will remain

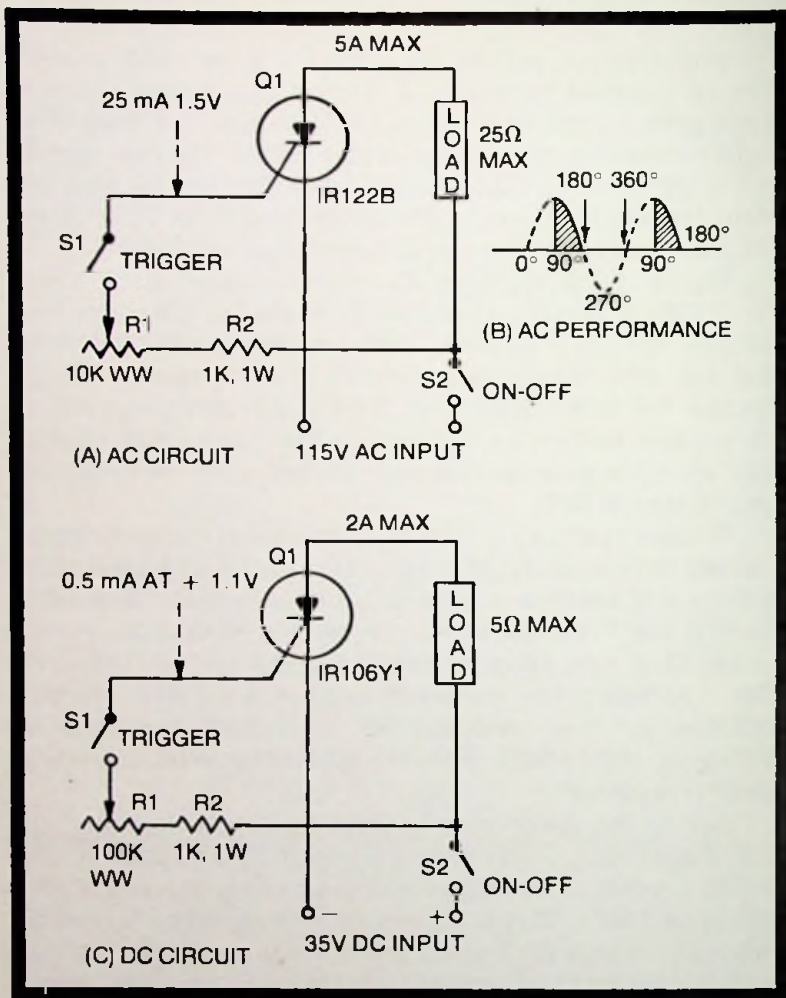


Fig. 11-3. Basic SCR switches.

on—even if S1 is opened—until the DC anode voltage is interrupted, as by momentarily opening switch S2. Thus, S2 always must be opened to reset the circuit to respond to subsequent trigger signals.

The advantage of the SCR switch, AC or DC, is that it allows a low current and voltage to be used to switch a much higher current and voltage. Thus, in Fig. 11-3A, a gate current of 25 mA at 1.5-volts switches 5-amperes at 11-volts; and in Fig. 11-3C, 0.5 mA at 1.1-volts switches 2-amperes at 35-volts. Various

SCRs afford other levels of sensitivity and other maximum anode voltages and currents. Because of the comparatively low gate current and voltage, the contacts of the control switch, S1, may be light. Also, S1 need not be a switch *per se*, but may be light-duty relay contacts or in some applications a thermostat, photocell, thermocouple, humidity sensor, thermistor, or other similar device that will deliver a low DC voltage.

LIGHT-CONTROLLED SCR

Figure 11-4 shows how the DC output of a self-generating silicon photocell can supply the gate trigger current to an SCR. The type S6M-C photocell (PC1) delivers approximately 1.5 volts (at a maximum current of 8 mA) when actuated by 100 footcandles illumination, and this DC output will trigger the HEP R1220 SCR (Q1) to a maximum of 2-amps anode current through the load. Either AC or DC supply may be used; with DC terminal A must be positive, and B negative. The photocell must be poled such that its positive DC output is applied to the SCR gate (see color coding in Fig. 11-4).

To set up the circuit initially, illuminate the photocell and adjust rheostat R1 to the point at which the SCR switches *on* and passes current through the load. With DC supply, the photocell then will exert no further control until switch S1 is momentarily opened to restore control to the gate. With AC

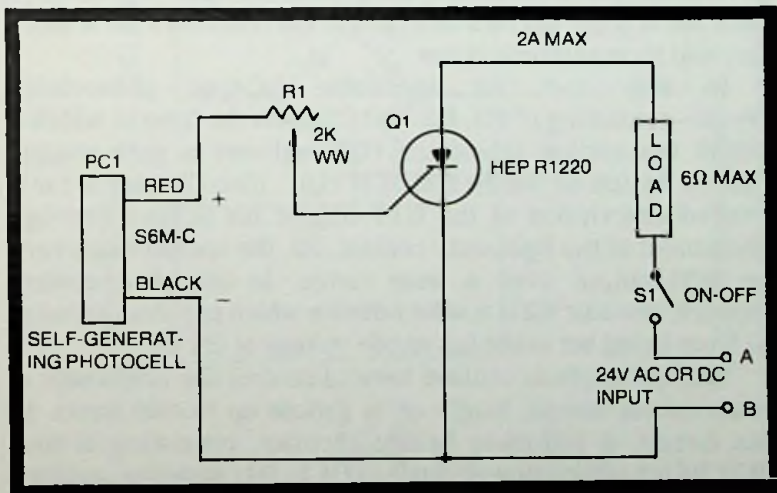


Fig. 11-4. Light-controlled SCR.

supply, however, control automatically returns to the gate each time the supply-voltage cycle passes through zero. This means that with AC supply the SCR will switch *on* each time that light is shined on the cell, and will switch *off* each time the light is interrupted; but with DC supply, the SCR will switch *on* each time the cell is illuminated and then will remain *on* when the light is removed.

This is a relatively simple arrangement, which is useful in many setups requiring a switch that closes on application of a light beam. While the circuit is not so sensitive as some similar ones, the self-generating photocell requires no bias supply, and this further simplifies the circuit. Insertion of the load device into the anode circuit of the SCR obviates the need for an auxiliary electromechanical relay. While a 2-amp SCR operated at 24 volts is shown here, the same circuit may be used with a heavier-current SCR and at higher anode voltage, provided the gate current for the new SCR is within the 8 mA output range of the photocell.

SCR LIGHT DIMMER

The output of a silicon controlled rectifier can be varied smoothly by varying the phase of the gate trigger, with respect to the anode voltage. The earlier the trigger arrives in the positive half-cycle of anode voltage, the longer the anode current flows and, therefore, the greater its value. Conversely, when the trigger arrives late, anode current flows for a short time and its magnitude is low.

In Fig. 11-5, an adjustable RC-type phase-delay circuit—consisting of R2, R3, and C1—sets the time at which a 2N2646 unijunction transistor (Q2) delivers a gate trigger pulse to switch on the 2N3228 SCR (Q1). (See Chapter 5, for a detailed description of the UJT trigger for SCRs.) Through adjustment of the light-duty control, R3, the operator can vary the SCR output over a wide range. In the phase-control network, resistor R2 is a safety device which prevents rheostat R1 from being set to the full anode voltage of the UJT.

This principle is utilized here to control the brightness of incandescent lamps, singly or in groups up to 1000 watts. In this circuit, a full-wave bridge rectifier, consisting of four HEP R0162 silicon power diodes (D1 to D4) supplies rectified power-line voltage to the SCR and lamp load. Because of the

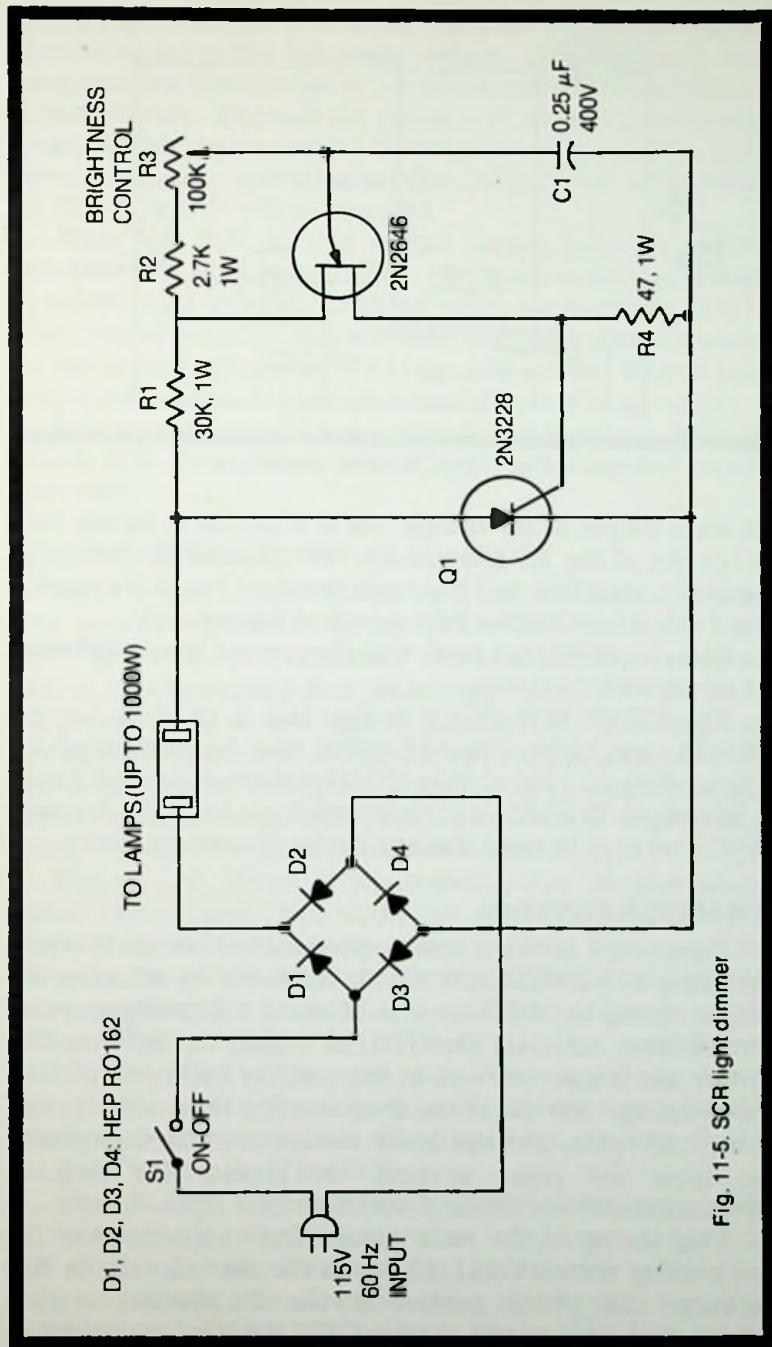


Fig. 11-5. SCR light dimmer

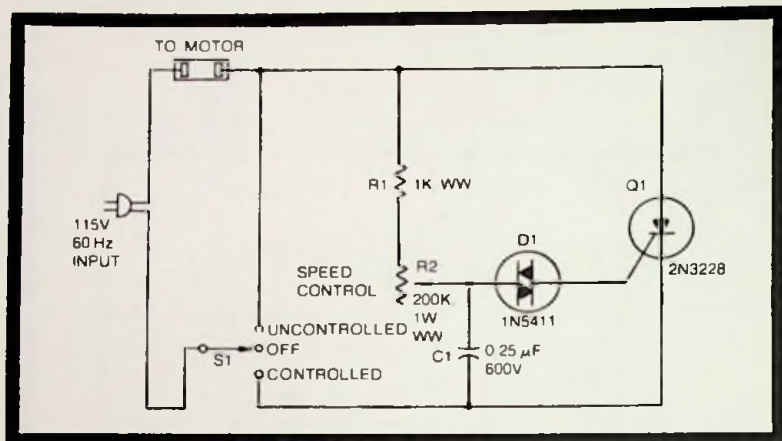


Fig. 11-6. SCR motor control.

full-wave output of the bridge. the SCR is able to handle both half-cycles of the AC line voltage. The phase-shift network is frequency sensitive and has been designed for 60 Hz service (see Table 9-1 in Chapter 9 for details of this network).

The circuit will not work with fluorescent lamps and must not be connected to them.

The 2N3228 SCR shown in Fig. 11-5 is rated at 5-amps. 200-volts. but higher-powered SCRs may be substituted for heavier-duty service. and the 2N2646 portion of the circuit may be left intact. In addition to its intended use as a light dimmer. this circuit may be used also as a heater or oven controller.

SCR MOTOR CONTROL

Figure 11-6 shows a motor-speed-control circuit in which the output of a 2N3228 SCR (Q1) is controlled by adjusting the instant during the AC half-cycle at which a gate-trigger pulse arrives from a 1N5411 diac (D1) to trigger the SCR on. The earlier the trigger arrives in the positive half-cycle of SCR anode voltage. the longer the anode current flows until the end of the half-cycle. and the faster the motor runs. Conversely. the later the pulse arrives. the shorter the time of anode-current flow and the slower the motor runs.

This timing of the pulse results from adjustment of the phase-delay network (R1-R2-C1) in the diac circuit. In this network. the phase control is the 200,000-ohm. 1-watt. linear-taper. wirewound rheostat, R1 (Mallory Midgetrol or

equivalent); and R1 is a safety resistor which prevents R2 from being set to the full anode voltage. (See Chapter 9, for a more detailed description of the phase-controlled-diac type of trigger circuit.) Because the phase-shift network is frequency sensitive, this motor-control circuit is recommended for 60 Hz service only. For operation at other frequencies, other values for R1, R2, and C1 will be required.

Since the SCR in this circuit passes only the positive half-cycles of AC supply voltage, the motor cannot be brought up to full speed. For full-speed operation, throw switch S1 to its *uncontrolled* position; this connects the motor directly across the power line without benefit of the SCR circuit. With S1 in its *controlled* position, the speed-control circuit is in operation.

The circuit is useful only with universal motors. With the 2N3228 SCR shown here, motors up to $\frac{3}{4}$ horsepower can be controlled.

PHOTOELECTRIC BURGLAR ALARM

Battery-operated burglar alarms are very desirable, since they remain operable during power-line blackouts when house breakins are very likely and in other times of power failure. It is important that the idling current of the device be low, so that one or two hotshot batteries will give long-time service in its operation. Two SCR-type burglar alarm circuits are included in this chapter; one (Fig. 11-7) employs a light beam; the other (Fig. 11-8) uses the familiar arrangement of closed "sensor" switches connected in series.

Figure 11-7 shows a photoelectric-type burglar alarm circuit which goes into operation when a light beam is interrupted, and continues to operate without break after the beam is restored. In this arrangement, a HEP R1103 SCR (Q1) is triggered by the DC output of a CS120-C cadmium-sulfide photoconductive cell (PC1). The circuit leg, consisting of resistor R1 and the photocell, constitutes a voltage divider (operated from the 12-volt battery, B1) in which the cell acts as a light-controlled resistor. The output of the voltage divider is applied to the gate of the SCR.

When the cell is illuminated, its resistance is low, and the DC output of the voltage divider then is too low to trigger the SCR into conduction. But when the light beam is interrupted, as by an intruder, the dark resistance of the cell is very high and the output of the R1-PC1 voltage divider rises high enough

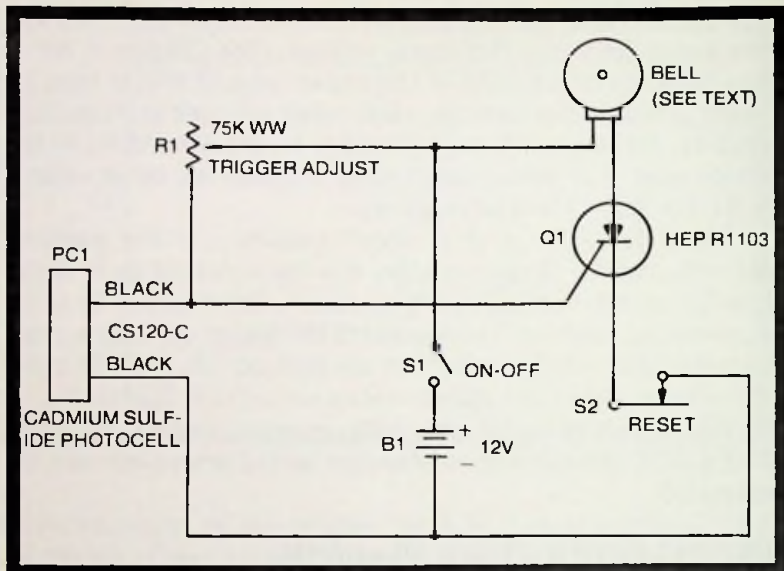


Fig. 11-7. Photoelectric burglar alarm.

to trigger the SCR *on*. The resulting flow of anode current through the bell causes the latter to go into operation. Once the SCR has thus been switched *on*, the gate loses control, and restoration of the light beam has no effect. The bell may be silenced only by momentarily opening the normally closed switch, S2 (installed at a secret location) which resets the circuit.

To set up the circuit initially, close switch S1 and illuminate the photocell, with R1 set to maximum resistance. Then, darken the cell and adjust R1 to the point at which the bell starts ringing. Depress S2 to silence the bell. This is the correct operating point of the circuit, R1 requiring no subsequent adjustment. Note that the photocell has no exclusive output polarity (see identical color coding of its leads in Fig. 11-7). The bell must be a loud one able to operate efficiently on the SCR anode current (a satisfactory unit is Audiotex 30-9100). Aside from a bell, a siren, horn, or lamp also can be used.

SWITCH-TYPE BURGLAR ALARM

The circuit in Fig. 11-8 employs a series of normally closed switches (S2, S3, S4) the momentary opening of any one of

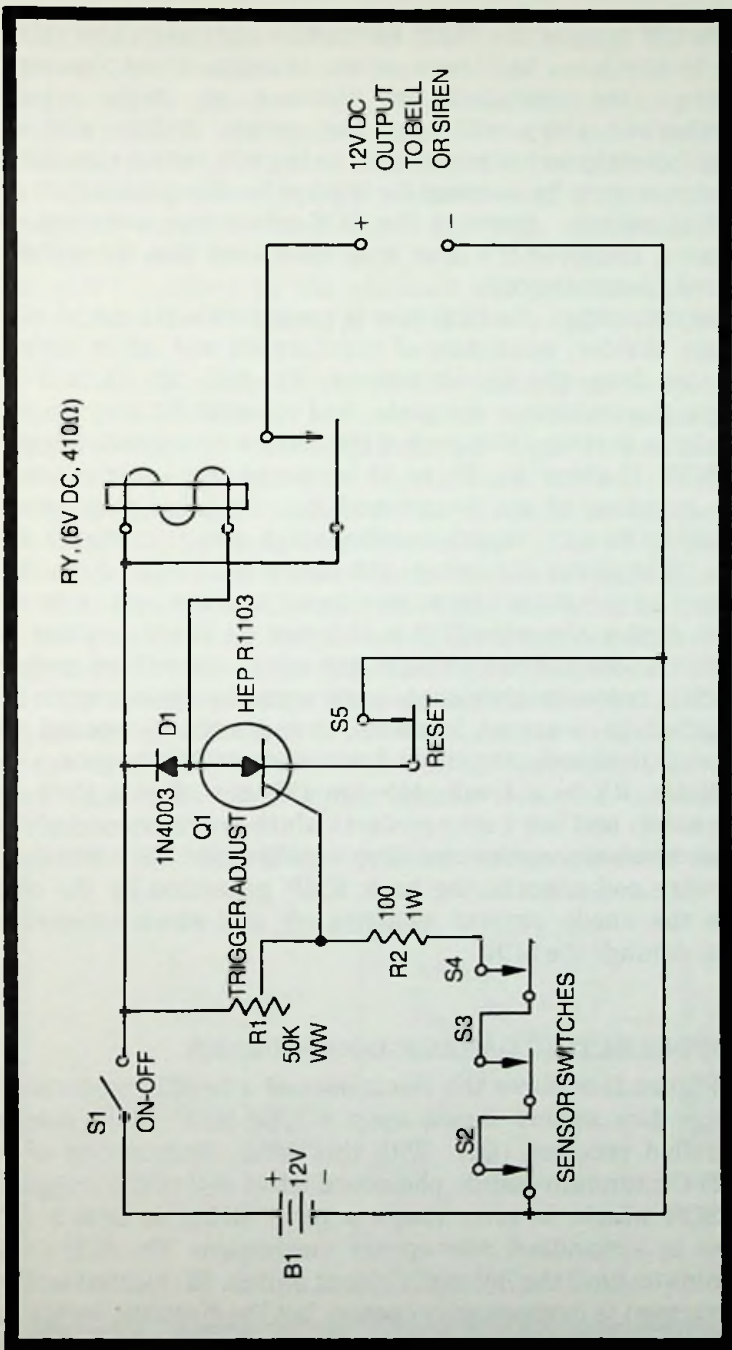


Fig 11-8 Switch-type burglar alarm.

which will trigger the HEP R1103 SCR (Q1) and close relay RY1 to operate a bell, horn, siren, or lamp. These "sensor" switches are installed on windows or doors where unauthorized entry will open the switch. A thin wire or metal-foil strip sometimes is used in lieu of a switch (breaking the wire or strip by opening the window has the same effect as opening switch). Because the SCR when once switched *on* stays *on*, reclosing the door or window (and thus the switch) will not silence the bell.

In this circuit, the SCR gate is connected to the output of a voltage divider, consisting of resistors R1 and R2 in series, operated from the 12-volt battery, B1. With S2, S3, and S4 closed, the divider is complete, and rheostat R1 may be set initially so that the DC output of the divider is too low to trigger the SCR. If either S2, S3, or S4 is opened, the lower resistor (R2) is cut out of the divider and then the gate signal, being limited by R1 only, rises to a voltage high enough to trigger the SCR. This closes the relay and connects 12 volts from the battery to the output terminals to actuate the bell or other alarm device. Once the SCR is switched *on*, it will continue to conduct anode current through the relay—even if the sensor switch is immediately closed—until normally closed switch S5 (installed at a secret location) is momentarily opened to interrupt the anode current and restore control to the gate.

Relay RY is a 6-volt, 410-ohm DC unit (Sigma 65F1 or equivalent) and has 1-amp contacts which are heavy enough to switch most alarm devices. The 1N4003 diode (D1) shunting the relay coil absorbs the back EMF generated by the coil when the anode current switches *off* and which otherwise might damage the SCR.

PHOTOELECTRIC GARAGE-DOOR OPENER

Figure 11-9 shows the electronics of a headlight-operated garage-door opener based upon a type HEP R1103 silicon controlled rectifier (Q1). With this setup, illumination of a CS120-C cadmium-sulfide photoconductive cell (PC1) triggers the SCR which, in turn, closes a relay (RY1) to switch AC power to a standard door-opener mechanism. The SCR then remains *on* until the normally closed switch, S2 (located inside the garage) is momentarily opened, but the disabling switch in the opener mechanism automatically removes the AC power

from the mechanism when the door is fully open. To achieve reasonably foolproof service and to avoid accidental triggering by ambient light, the photocell must be provided with a suitable lens system and must be properly hooded so that only the bright light of high beams will actuate the circuit.

In this circuit, the photocell functions as a light-controlled variable resistor exhibiting very high resistance when darkened and low resistance when illuminated. A voltage divider is formed by the photocell and potentiometer R1 in series, and the DC output of this divider is applied to the gate of the SCR.

When the cell is darkened, the output is too low to affect the SCR. When the cell is illuminated, however, its resistance drops considerably, the output of the voltage divider rises, and the SCR is triggered *on*, closing the 6-volt, 410-ohm relay, RY1 (Sigma 65F or equivalent). When switch S2 subsequently is momentarily opened, the anode voltage is instantly removed from the SCR, and control is restored to the SCR gate. The 1N4003 diode (D1) shunting the relay coil absorbs the back EMF generated by the coil when the anode current switches off and which otherwise might damage the SCR.

To set the circuit initially, darken the photocell, turn potentiometer R1 down to its lowest point, and close switch S1. Next, illuminate the photocell with the headlights that will be used and with these lights spaced from the cell as they

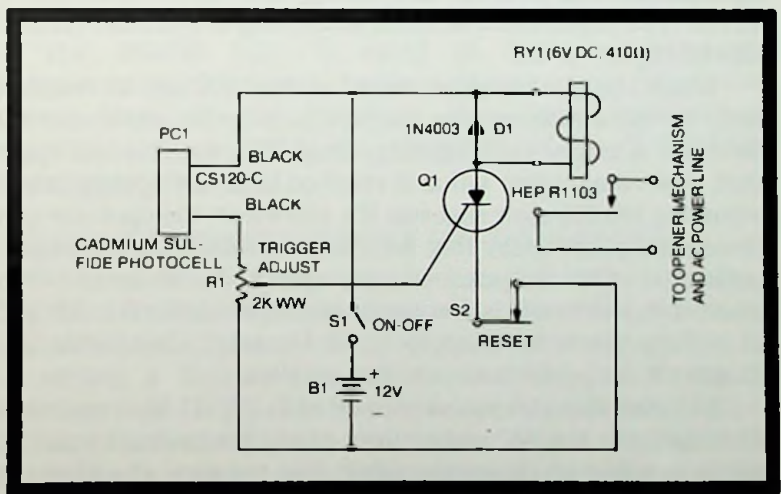


Fig. 11-9. Photoelectric garage-door opener.

normally will be. Then, advance the setting of R1 to the point at which the relay just closes. This is the correct operating point of the circuit, and R1 will require no further adjustment except to compensate from time to time for drift and aging. Finally, darken the photocell again, noting that the relay remains closed. Then, momentarily open switch S2, noting that the relay opens. Note that the photocell has no exclusive polarity; both leads are color-coded black, as shown in Fig. 11-9.


VARIABLE DC POWER SUPPLY (115 VOLTS)

Through phase control of the gate voltage, the DC output of an AC-operated SCR may be varied smoothly over a useful range. Figure 11-10 shows a half-wave rectifier circuit of this kind operated directly from the 115-volt AC power line. The average value of the DC output voltage of this circuit can be varied from close to zero to approximately 51 volts by adjustment of the light-duty 100,000-ohm rheostat, R2. The 2N3228 SCR (Q1) is rated at 5-amps, 200-volts. Because this is a half-wave circuit, substantial filtering of the DC output is required, and the resulting DC voltage may be higher than the maximum value given above, depending upon the type of filter used.

The sinusoidal gate signal is derived from the 2.5-volt center-tapped winding of transformer T1 (Stancor P-8629 or equivalent). The phase of this voltage is adjusted by means of an RC-type phase-shift network consisting of resistors R1 and R2 and capacitor C1.

When the gate-trigger value of this voltage is reached early in the anode-voltage positive half-cycle, anode current flows for a longer time (greater angle) during this half-cycle than when the trigger value is reached later. By appropriately adjusting 100,000-ohm rheostat R2, therefore, the operator can choose the phase delay that will result in minimum DC output, maximum DC output, or any point in between. The phase-delay network is frequency sensitive, so the R1, R2, and C1 values given here apply to 60 Hz only. (See Table 9-1, Chapter 9, for performance of this network.)

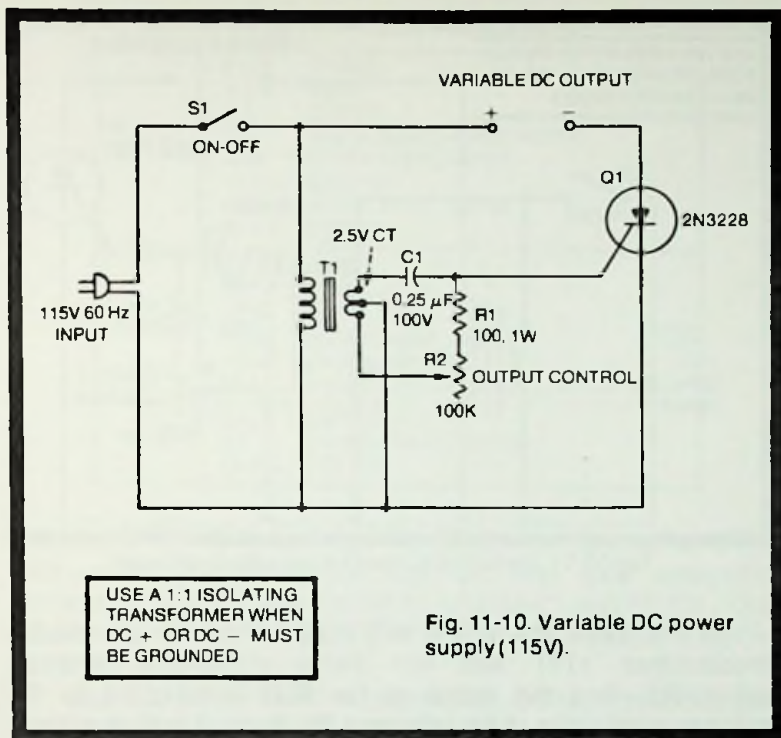Because this circuit, as presented in Fig. 11-10, is operated directly from the AC power line, safety precautions must be taken in some of its applications. For instance, if either the DC+ or DC- terminal is to be grounded, a 1:1 isolating



transformer must be inserted between the power line and the input portion (S1-T1) of the circuit, to prevent electric shock or damage to the circuit or to the powered equipment.

The 2N3228 SCR is rated at 5 amps; however, higher-current units may be used in the same circuit for heavier-duty service, provided that their gate-voltage requirements are within the capability of the T-C1-R1-R2 gate-trigger circuit.

VARIABLE DC POWER SUPPLY (HIGH-VOLTAGE)

The variable DC power supply described in the preceding section is limited to the AC voltage of the power line. However, the same principle may be applied to a higher-voltage supply by adding a high-voltage transformer and substituting a higher-voltage SCR. The same delayed-phase gate-trigger circuit may be used as in the simpler circuit. Figure 11-11 shows how a suitable high-voltage transformer (T1) may be added to the original circuit.

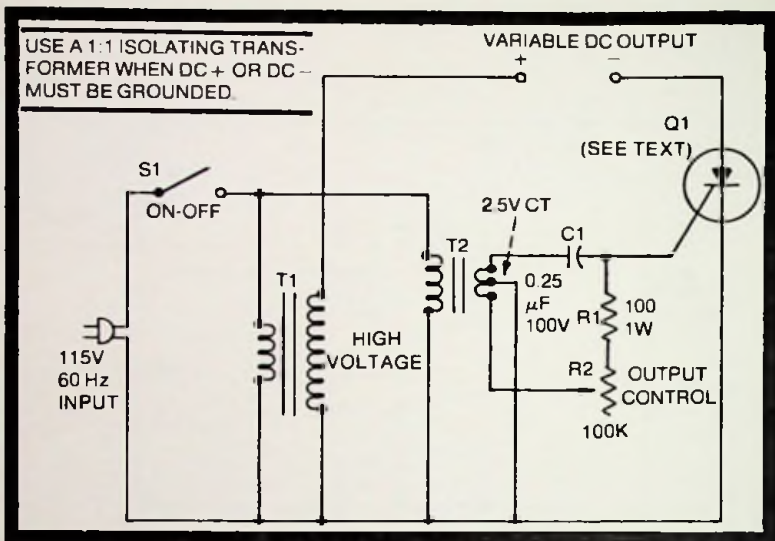


Fig. 11-11. Variable DC power supply (high-voltage).

In Fig. 11-11, the SCR is still triggered by the low-voltage transformer (T2) and the same phase-shift network (C1-R1-R2), but the anode of the SCR is supplied by the secondary winding of transformer T1. Typical higher voltage SCRs are listed in Table 11-1. The average value of the unfiltered DC output voltage of the high-voltage circuit will be equal to approximately 0.45 times the rms value of the secondary voltage of transformer T1.

Because this circuit, like the earlier one, has a direct connection to the AC power line, special safety precautions must be taken in some of its applications. For instance, to prevent electric shock or damage to the circuit or to the powered equipment, if either the DC+ or DC- terminal is to be grounded, a 1:1 isolating transformer must be inserted between the power line and the input portion (S1-T1-T2) of the circuit.

DC-TO-AC INVERTER

Figure 11-12 shows the circuit of an SCR inverter which runs from a 12-volt battery and delivers 115-volts, 60-Hz AC at 100-watts continuous service and up to 150-watts intermittent service. SCRs give efficient performance in inverters. This circuit employs two 2N3650 SCRs in push-pull, each being

Table 11-1. Higher-Voltage SCRs

400 V	2 A	2N3529
	3.3 A	40659
	5 A	2N3525
	7 A	40379, 40508, 40655, 40657
	10 A	40739, 40743, 40747
	12.5 A	2N3670
	20 A	40751, 40755, 40759
	35 A	2N3653
600 V	2.5 A	40813
	5 A	40640, 40641
	10 A	40740, 40744, 40748
	16 A	2N1842A, 2N1850A
	25 A	2N681, 2N690
	35 A	2N3873, 2N3899, 40216, 40683, 40735
700 V	2 A	2N4102
	5 A	2N4101, 40553, 40555
	12.5 A	2N4103

triggered by a relaxation oscillator employing a 2N493 unijunction transistor (Q2 and Q3) and their associated frequency-determining networks (R4-R5-C1 and R6-C2). (See Chapter 5, for an explanation of the unijunction relaxation oscillator.)

The 2N3650s are fast-turnoff SCRs recommended especially for inverter service. The upper UJT (Q2) operates at 120 Hz, and the lower one (Q3) at 60 Hz. Once rheostats R4 and R6 are set for these frequencies, they will not ordinarily need readjustment, hence may be provided with slotted shafts for screwdriver adjustment.

In circuits of this type, some means must be included for automatically switching off the SCRs at the proper time. Ordinarily they will continue to conduct, once switched on, and there would consequently be no AC output from the circuit. When this automatic switch-off is accomplished, the SCRs supply pulses alternately to the transformer, T1. This needed commutation is provided by capacitor C4 and inductor L1. As one SCR is switched on, C4 applies a negative voltage momentarily to the anode of the opposite SCR, switching the latter off.

In general, construction of the inverter is straightforward. T1 is a special inverter transformer (Triad TY-75A or equivalent). Choke inductor L1 is a 1-millihenry, 8-amp unit; and since such a heavy-current unit may not easily be located in commercial stocks, winding a simple one should be both

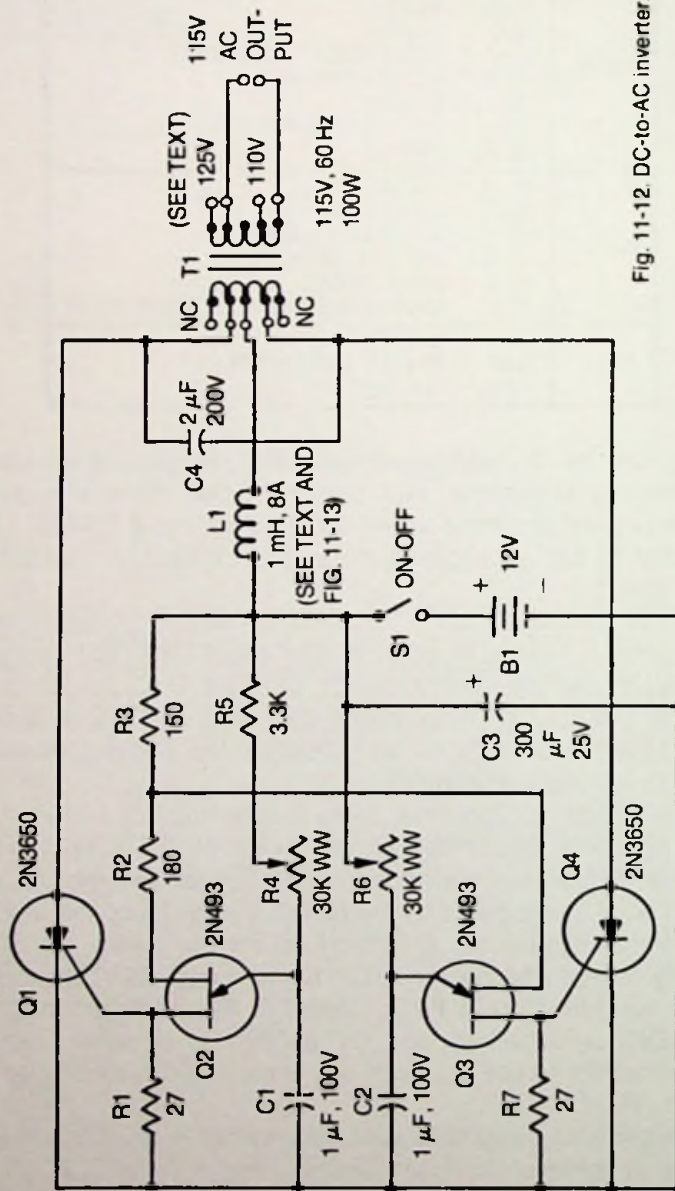


Fig. 11-12. DC-to-AC inverter.

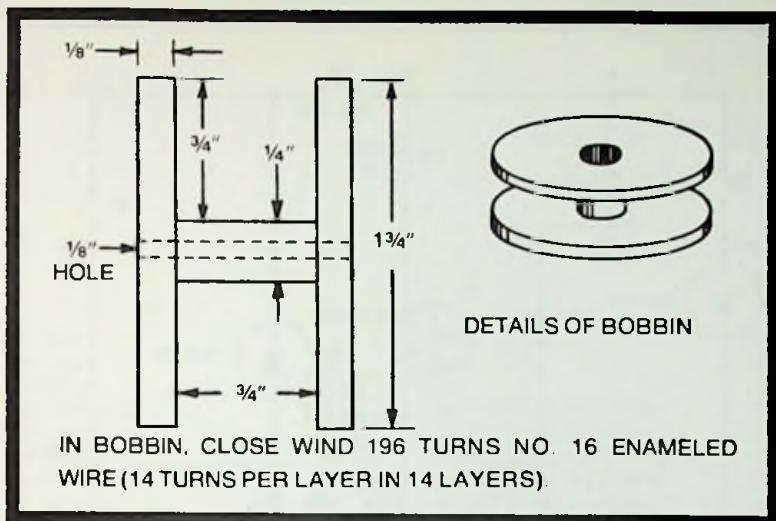


Fig. 11-13. Details of inverter choke coil.

economical and time saving. A suitable inductor may be made by closewinding 196 turns of No. 16 enameled wire in 14 layers at 14 turns per layer. Figure 11-13 shows details of a 1 $\frac{3}{4}$ in. diameter bobbin for this coil; the bobbin may be turned from wood and later impregnated with insulating varnish—or, if preferred, it can be made from some other dielectric material. The SCRs should be heat-sinked, and the UJTs should be mounted in a cool part of the inverter assembly.

SOLID-STATE TIMER

Figure 11-14 shows the circuit of an all-solid-state timer based on a 2N3228 SCR (Q2) which will switch as high as 5 amps through a load device, such as a motor, actuator, heater, lamp, and so on. This is a delayed-make type of timer; that is, the SCR switches *on* at a selected instant *after* switch S1 has been closed. Setting of the 500,000-ohm rheostat, R2, allows selection of any interval between 0.1 and 50.1 seconds. While a 28-volt battery (B1) is shown here, a well-filtered, power-line-operated supply also can be used.

In this circuit, the SCR is triggered by a pulse from a 2N2419B unijunction transistor (Q1). The anode supply voltage of this UJT, which is also the DC voltage applied to the timing circuit (R1-R2-C1) is regulated by the 1N1777 zener diode (D1) and 200-ohm resistor (R4).

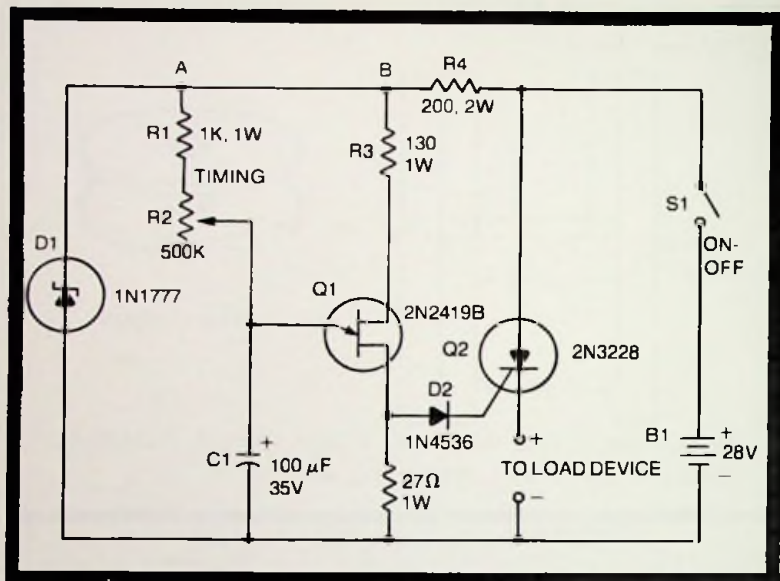


Fig. 11-14. Solid-state timer.

Operation of the circuit is simple: When switch S1 is closed, a regulated +12-volt DC potential is applied to the UJT anode circuit (point B) and the timing circuit (point A). Capacitor C1 then charges through resistors R1 and R2, the voltage across this capacitor increasing according to the time constant of the R1-R2-C1 circuit and thus according to the setting of rheostat R2. When the capacitor voltage eventually reaches the critical value of the UJT, Q1 fires and delivers a positive pulse which passes through steering diode D2 to the gate of the SCR. This triggers the SCR and causes it to conduct current through the load. The SCR then remains *on* until switch S1 subsequently is opened. Rheostat R2 may be provided with a dial reading directly in seconds on the basis of a calibration of the circuit.

Index

A			
Active filter.			
bandpass	79		
bandstop	83		
high/low pass	79		
high pass	77		
low pass	76		
AF preamplifier	16		
Alarm, burglar	209		
Amplifier.			
audio	66. 71. 118		
FET	16. 19		
IC	65		
instrument	48		
RF	43		
sensitive switch	172		
wideband	48		
Anode, SCR	200		
Audio			
amplifier	19. 66. 118		
oscillator	24		
power amplifier	71		
preamplifier	16		
Automatic			
frequency control	138		
volume limiter	166		
B			
Bandpass active filter	79		
Bandstop active filter	83		
Base, UJT	89		
Breakdown			
voltage, SCR	201		
voltage, zener	149		
Burglar alarm, photoelectric	209		
C			
Capacitance			
measurement	53		
meter	35		
relay	57		
VCD	128		
Capacitor, voltage variable	128		
Case, semiconductor	11		
Cathode, SCR	200		
Channel, FET	15		
Circuit.			
active filter, bandpass	79		
active filter, bandstop	83		
active filter, high/low pass	79		
active filter, high pass	77		
active filter, low pass	76		
alarm, burglar	209		
all-wave receiver	26		
amplitude-sensitive switch	172		
audio amplifier	66. 118		
audio power amplifier	71		
audio preamplifier	16		
automatic frequency control	138		
automatic power supply switch	198		
automatic volume limiter	166		
burglar alarm	209		
capacitance meter	35		
Citizen's Band converter	116		
code-practice oscillator	87		
controller	187. 190		
converter, Citizen's Band	116		
converter, frequency	114		
crystal oscillator	21. 111		
CW monitor	100		
DC-to-AC inverter	216		
dip meter	118		
equipment protector	167		
free-running multivibrator	95		
frequency converter	114		
frequency modulator	139		
frequency multiplier	143		
garage door opener	212		
intercom	71		
inverter	216		
interval timer	55		
LC checker	53		
light-controlled SCR	205		
light dimmer	194		
metronome	103		
milliammeter	73		

U

UJT	89
base	89
CW monitor	100
emitter	89
free-running multivibrator	95
metronome	103
oscillator, standard freq.	100
pulse generator	90
pulse/timing generator	93
relaxation oscillator	99
SCR trigger	105
tone identification	105
Unijunction transistor (UJT)	89
Ultrasonic pickup	63

V

Varactor	128
Variable	
capacitance diode (VCD)	128
power supply	196, 214
VCD	128
automatic frequency control	138
frequency multiplier	143
frequency modulator	139
RF harmonic intensifier	145
tuned LC circuit	133, 135
voltage-tuned oscillator	136
Voltage	
breakdown	149
controlled oscillator	112
divider, zener	162

regulator	151
regulator, AC	165
regulator, divider	162
regulator, 18V 1A	159
regulator, 5V 1.25A	157
regulator, 3.5V	156
regulator, tube heater	164
regulator, $\pm 12V$	159
semiconductor	12
standard, DC	168
tuned circuit	133, 135
tuned oscillator	136
zener	149
Voltmeter	33
FET	33
Volume limiter	166

W

Wiring, semiconductor	11
-----------------------	----

Z

Zener diode	148
automatic volume limiter	166
breakdown voltage	149
transistor-bias regulator	163
voltage regulator	151
voltage regulator, AC	165
voltage regulator, tube heater	164
equipment protector	167
voltage standard, DC	168

BIBLIOTHEEK
N.V.H.R.