

# electronics today international

SEPTEMBER 1976

30p

SOUTH AFRICA 60c  
CANADA \$1

## 100W DISCO

COMPLETE  
PCB KIT OFFER  
save 34%

## LOW COST VDU



TWO METER POWER AMP  
BREAKDOWN BEACON  
CMOS TO MAINS  
TOSHIBA ST910 REVIEW

# 15 — 240 Watts!

## HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone controls merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack — Multi function equalization — Low noise — Low distortion — High overload — Two simply combined for stereo

**APPLICATIONS:** Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV Ceramic Pick-up 30mV Tuner 100mV Microphone 10mV

Auxiliary 3 100mV input impedance 47k $\Omega$  at 1kHz


**OUTPUTS:** Tape 100mV, Main output 500mV R.M.S.

**ACTIVE TONE CONTROLS:** Treble  $\pm$  12dB at 10kHz Bass  $\pm$  at 100Hz

**DISTORTION:** 0.1% at 1kHz Signal/Noise Ratio 6dB

**OVERLOAD:** 38dB on Magnetic Pick-up **SUPPLY VOLTAGE:**  $\pm$  16-50V

**Price £4.75 + 59p VAT P&P free.**

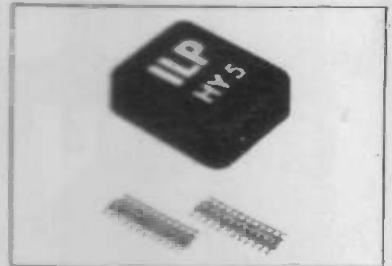

## HY30 15 Watts into 8 $\Omega$

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete Kit — Low Distortion — Short, Open and Thermal Protection — Easy to Build

**APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — audio oscillator

**SPECIFICATIONS:**

**OUTPUT POWER:** 15W R.M.S. into 8 $\Omega$ , **DISTORTION:** 0.1% at 15W

**INPUT SENSITIVITY:** 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB

**SUPPLY VOLTAGE:**  $\pm$  18V

**Price £4.75 + 59p VAT P&P free.**

Available  
June '76

## HY50 25 Watts into 8 $\Omega$

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

**APPLICATIONS:** Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 25W RMS into 8 $\Omega$ ! **LOAD IMPEDANCE:** 4-16 $\Omega$ ! **DISTORTION:** 0.04% at 25W at 1kHz

**SIGNAL/NOISE RATIO:** 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

**SUPPLY VOLTAGE:**  $\pm$  25V **SIZE:** 105 50 25mm

**Price £6.20 + 77p VAT P&P free.**



## HY120 60 Watts into 8 $\Omega$

The HY120 is the baby of I.L.P.'s new high power range, designed to meet the most exacting requirements including load line and thermal protection this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion — Integral heatsink — Load line protection — Thermal protection — Five connections — No external components

**APPLICATIONS:** Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

**SPECIFICATIONS:**


**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 60W RMS into 8 $\Omega$ ! **LOAD IMPEDANCE:** 4-16 $\Omega$ ! **DISTORTION:** 0.04% at 60W at 1kHz

**SIGNAL/NOISE RATIO:** 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**  $\pm$  35V

**SIZE:** 114 50 85mm

**Price £14.40 + £1.16 VAT P&P free.**

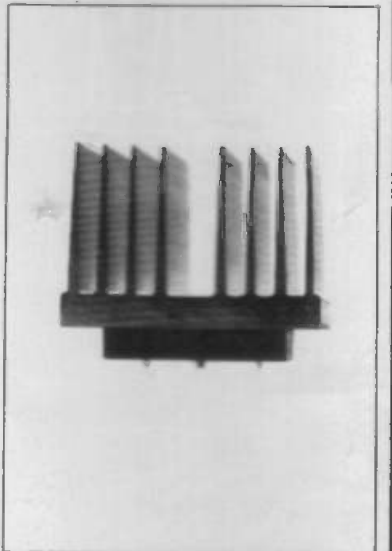

## HY200 120 Watts into 8 $\Omega$

The HY200 now improved to give an output of 120 Watts has been designed to stand the most rugged conditions such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — Integral heatsink — No external components

**APPLICATIONS:** Hi-Fi — Disco — Monitor — Power slave — Industrial — Public Address

**SPECIFICATIONS:**

**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 120W RMS into 8 $\Omega$ ! **LOAD IMPEDANCE:** 4-16 $\Omega$ ! **DISTORTION:** 0.05% at 100W at 1kHz

**SIGNAL/NOISE RATIO:** 96 dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**  $\pm$  45V

**SIZE:** 114 100 85mm

**Price £21.20 + £1.70 VAT P&P free.**

## HY400 240 Watts into 4 $\Omega$

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4 $\Omega$ ! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — No external components

**APPLICATIONS:** Public address — Disco — Power slave — Industrial


**SPECIFICATIONS:**

**OUTPUT POWER:** 240W RMS into 4 $\Omega$ ! **LOAD IMPEDANCE:** 4-16 $\Omega$ ! **DISTORTION:** 0.1% at 240W at 1kHz

**SIGNAL/NOISE RATIO:** 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:**  $\pm$  45V

**INPUT SENSITIVITY:** 500mV, **SIZE:** 114x100x85mm

**Price £29.25 + £2.34 VAT P&P free.**

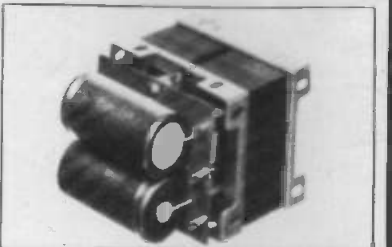

## POWER SUPPLIES

PSU36 suitable for two HY30's £4.75 plus 59p VAT P/P free  
 PSU50 suitable for two HY50's £6.20 plus 77p VAT P/P free  
 PSU70 suitable for two HY120's £12.50 plus £1.00 VAT P/P free  
 PSU90 suitable for one HY200 £11.50 plus £0.92 VAT P/P free  
 PSU180 suitable for two HY200's or one HY400 £21.00 plus £1.68 VAT P/P free

TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd  
 Crossland House  
 Nackington, Canterbury  
 Kent CT4 7AD  
 Tel (0227) 63218

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number \_\_\_\_\_  
 Name & Address \_\_\_\_\_  
 Signature \_\_\_\_\_

# electronics today

international

SEPTEMBER 1976

VOL 5, No. 9

## Features

OPTO-ELECTRONICS.....	26
<i>Plastics and their part in electronics</i>	
CAPACITORS: PART TWO.....	28
<i>Codings in use and how to use them</i>	
CMOS-TO MAINS.....	38
<i>Interfacing micropower CMOS to high power A.C.</i>	
TOSHIBA ST 910 TUNER REVIEWED.....	50
<i>Top flight tuner considered</i>	
MIRCOFILE PART SEVEN.....	58
<i>I/O, I/O, it's off to work we go!</i>	
ELECTRONICS IT'S EASY.....	64
<i>Continuing digital display techniques</i>	
TECH TIPS.....	72
<i>Three more pages of your ideas</i>	

## Projects

LOW COST VDU — PART TWO.....	10
<i>Constructional details</i>	
TWO METRE POWER AMP.....	19
<i>Boosting outpower to higher levels</i>	
ETI CLOCK MODS.....	37
<i>Addition of a 'radio alarm'</i>	
100W DISCO UNIT PART ONE.....	42
<i>Power amps and power supply constructional details</i>	
BREAKDOWN BEACON.....	52
<i>Could save you repairs, and perhaps a life!</i>	
RF ATTENUATOR.....	62
<i>Precision step unit for use to 150 MHz</i>	

## Data Sheet

LM 3909 IC FLASHER.....	55
<i>Ultra-versatile IC with millions of applications</i>	
MK 50075/50103/50104 SCIENTIFIC CALCULATOR SET.....	56
<i>The heart of a very sophisticated machine for you to build around</i>	

## News

NEWS DIGEST.....	6
ELECTRONICS TOMORROW.....	70

## Information

SUBSCRIPTIONS.....	33
BOOK SERVICE.....	34
OCTOBER ETI PREVIEW.....	36
SPECIALS.....	41
ETI CLOCK OFFER.....	49
DIGITAL WATCH.....	49
READER SERVICES INFORMATION.....	82

## Special Offers

DECON PCB KIT.....	35
<i>34% off the most convenient way yet to etch PCB's!</i>	

## EDITORIAL AND ADVERTISEMENT OFFICES

36 Ebury Street  
London SW1W 0LW  
Telephone: 01-730 5282  
Telex 8811896

HALVOR W. MOONSHEAD  
Editor

ROBERT C. EVANS  
Advertisement Manager

LES BELL, G4CFM

RON HARRIS B.Sc.  
Editorial Assistants

JEAN BUTTERWORTH  
Production

## INTERNATIONAL EDITIONS

COLLYN RYIERS  
Editorial Director

AUSTRALIA  
STEVE BRAIDWOOD  
Assistant Editor

Modern Magazines (Holdings) Ltd  
Ryrie House, 15 Boundary Street  
Rushcutters Bay 2011  
Sydney, Australia.

FRANCE  
DENIS JACOB  
Editor in chief  
CHRISTIAN DARTEVILLE  
Editor  
Electroniques Pour Vous International  
17 Rue de Bucy  
Paris, France

Electronics Today International is normally published on the first Friday of the month prior to the cover date.

PUBLISHED BY  
Modriags Ltd.  
36 Ebury Street, London SW1W 0LW.



DISTRIBUTED BY  
Aurus Distribution Ltd (British Isles)  
Gordon & Gotch Ltd. (Canada and South Africa)

PRINTED BY  
QB Newspapers Limited, Colchester

READERS' QUERIES: These can only be answered if they relate to recent articles published in the magazine. Rarely can we supply information in addition to that published. Written queries must be accompanied by a stamped addressed envelope, and telephone queries must be brief, not before 4pm and can only be answered subject to the availability of technical staff.

BACK NUMBERS: Back numbers of some issues are available for 40p each, plus 15p postage.

SUBSCRIPTIONS: Great Britain £5.00 per annum. Overseas £5.50. Payment in sterling only.

COPYRIGHT: All material is subject to world wide Copyright protection. All reasonable care is taken in the preparation of the magazine to ensure accuracy but ETI cannot be held responsible for it legally. Where errors do occur, a correction will be published as soon as possible afterwards in the magazine.

AN OFFER YOU CAN'T REFUSE — P.41

# BI-PAK SEMICONDUCTORS

### TRANSISTORS

BRAND NEW, FULLY GUARANTEED

TYPE	PRICE	TYPE	PRICE	TYPE	PRICE	TYPE	PRICE
AC117K	+0.10	BC170	+0.09	BF271	+0.31	2N939	+0.21
AC125	+0.10	BC171	+0.09	BF272	+0.31	2N1131	+0.18
AC126	+0.11	BC172	+0.09	BF273	+0.36	2N1132	+0.18
AC127	+0.11	BC173	+0.08	BF274	+0.31	2N1133	+0.18
AC128	+0.11	BC174	+0.15	BFV19	+0.61	2N1303	+0.15
AC129	+0.11	BC175	+0.22	BFX29	+0.23	2N1304	+0.18
AC132	+0.15	BC177	+0.16	BFX29A	+0.19	2N1305	+0.18
AC134	+0.15	BC178	+0.16	BFX35	+0.25	2N1306	+0.21
AC137	+0.15	BC179	+0.16	BFX46	+0.22	2N1307	+0.21
AC141	+0.19	BC180	+0.16	BFX57	+0.22	2N1308	+0.24
AC141K	+0.38	BC181	+0.25	BFX88	+0.22	2N1309	+0.21
AC142	+0.16	BC182	+0.09	BFY50	+0.13	2N1613	+0.16
AC142K	+0.16	BC182L	+0.09	BFY51	+0.13	2N1711	+0.16
AC151	+0.26	BC183	+0.09	BFY52	+0.13	2N1719	+0.32
AC153K	+0.24	BC183L	+0.09	BFY53	+0.13	2N1890	+0.46
AC154	+0.20	BC184	+0.09	BSX19	+0.16	2N1893	+0.36
AC155	+0.20	BC184L	+0.09	BSX20	+0.16	2N2147	+0.73
AC156	+0.20	BC185	+0.29	BSY25	+0.18	2N2148	+0.56
AC157	+0.25	BC187	+0.29	BSY26	+0.18	2N2192	+0.36
AC165	+0.20	BC207	+0.11	BSY27	+0.18	2N2193	+0.36
AC166	+0.20	BC208	+0.11	BSY28	+0.16	2N2194	+0.36
AC167	+0.20	BC209	+0.12	BSY29	+0.16	2N2217	+0.22
AC168	+0.25	BC212	+0.10	BSY38	+0.19	2N2218	+0.22
AC176	+0.16	BC212L	+0.10	BSY39	+0.19	2N2218A	+0.18
AC176K	+0.21	BC213	+0.10	BSY40	+0.29	2N2220	+0.22
AC177	+0.25	BC214	+0.10	BSY95	+0.13	2N2221	+0.18
AC178	+0.20	BC221	+0.10	BSY95A	+0.13	2N2222	+0.18
AC179	+0.20	BC225	+0.26	BU105	+1.90	2N2388	+0.18
AC180	+0.20	BC226	+0.38	MAT100	+0.19	2N2389	+0.12
AC181	+0.20	BC251	+0.18	MAT101	+0.20	2N2389A	+0.18
AC181K	+0.30	BC252	+0.18	MAT102	+0.18	2N2392	+0.12
AC187	+0.22	BC303	+0.31	MJE251	+0.58	2N2646	+0.34
AC187K	+0.23	BC304	+0.37	MJE255	+0.88	2N2711	+0.21
AC188	+0.19	BC327	+0.12	MJE305S	+0.57	2N2712	+0.21
AC188K	+0.23	BC328	+0.12	MJE340	+0.51	2N2714	+0.21
AC189	+0.18	BC337	+0.12	MPF102	+0.28	2N2904	+0.14
AC190	+0.20	BC338	+0.12	MPF105	+0.28	2N2904A	+0.18
AC191	+0.20	BC440	+0.31	MPF105S	+0.28	2N2905	+0.18
AC192	+0.20	BC460	+0.37	OC19	+0.36	2N2905A	+0.18
AC193	+0.20	BC460	+0.37	OC20	+0.36	2N2906	+0.12
AC194	+0.20	BC460	+0.37	OC21	+0.36	2N2906A	+0.18
AC195	+0.20	BC460	+0.37	OC22	+0.47	2N2906B	+0.18
AC196	+0.19	BCY32	+0.31	OC23	+0.49	2N2907	+0.15
AC197	+0.19	BCY33	+0.31	OC24	+0.37	2N2907A	+0.18
AC198	+0.19	BCY34	+0.26	OC25	+0.29	2N2923	+0.15
AC199	+0.20	BCY34	+0.26	OC26	+0.38	2N2924	+0.15
AC200	+0.20	BCY35	+0.20	OC27	+0.60	2N2925	+0.15
AC201	+0.20	BCY36	+0.15	OC28	+0.60	2N2926	+0.15
AC202	+0.20	BCY37	+0.20	OC29	+0.60	2N2926A	+0.18
AC203	+0.20	BCY38	+0.15	OC30	+0.45	2N2926B	+0.09
AC204	+0.20	BCY39	+0.26	OC31	+0.51	2N2926C	+0.18
AC205	+0.20	BCY40	+0.26	OC32	+0.51	2N2926D	+0.18
AC206	+0.20	BCY41	+0.26	OC33	+0.51	2N2926E	+0.18
AC207	+0.20	BCY42	+0.26	OC34	+0.51	2N2926F	+0.18
AC208	+0.20	BCY43	+0.26	OC35	+0.51	2N2926G	+0.18
AC209	+0.20	BCY44	+0.26	OC36	+0.51	2N2926H	+0.18
AC210	+0.20	BCY45	+0.26	OC37	+0.51	2N2926I	+0.18
AD130	+0.39	BD121	+0.61	OC40	+0.12	2N2926J	+0.18
AD140	+0.49	BD123	+0.67	OC41	+0.20	2N2926K	+0.18
AD142	+0.55	BD124	+0.78	OC42	+0.25	2N2926L	+0.18
AD143	+0.49	BD131	+0.36	OC43	+0.25	2N2926M	+0.18
AD149	+0.45	BD132	+0.40	OC44	+0.20	2N2926N	+0.18
AD150	+0.45	BD133	+0.67	OC45	+0.25	2N2926P	+0.18
AD162	+0.39	BD136	+0.41	OC46	+0.20	2N2926Q	+0.18
AD161 & AD162(MP)	+0.69	BD137	+0.46	OC47	+0.15	2N2926R	+0.18
AD163	+0.51	BD138	+0.51	OC48	+0.15	2N2926S	+0.18
AD164	+0.22	BD140	+0.61	OC49	+0.15	2N2926T	+0.18
AD165	+0.22	BD155	+0.61	OC50	+0.15	2N2926U	+0.18
AD166	+0.22	BD175	+0.61	OC51	+0.15	2N2926V	+0.18
AD167	+0.22	BD176	+0.61	OC52	+0.15	2N2926W	+0.18
AD168	+0.22	BD177	+0.61	OC53	+0.15	2N2926X	+0.18
AD169	+0.22	BD178	+0.61	OC54	+0.15	2N2926Y	+0.18
AD170	+0.22	BD179	+0.61	OC55	+0.15	2N2926Z	+0.18
AD171	+0.22	BD180	+0.61	OC56	+0.15	2N2926AA	+0.18
AD172	+0.22	BD181	+0.61	OC57	+0.15	2N2926AB	+0.18
AD173	+0.22	BD182	+0.61	OC58	+0.15	2N2926AC	+0.18
AD174	+0.22	BD183	+0.61	OC59	+0.15	2N2926AD	+0.18
AD175	+0.22	BD184	+0.61	OC60	+0.15	2N2926AE	+0.18
AD176	+0.22	BD185	+0.61	OC61	+0.15	2N2926AF	+0.18
AD177	+0.22	BD186	+0.61	OC62	+0.15	2N2926AG	+0.18
AD178	+0.22	BD187	+0.61	OC63	+0.15	2N2926AH	+0.18
AD179	+0.22	BD188	+0.61	OC64	+0.15	2N2926AI	+0.18
AD180	+0.22	BD189	+0.61	OC65	+0.15	2N2926AJ	+0.18
AD181	+0.22	BD190	+0.61	OC66	+0.15	2N2926AK	+0.18
AD182	+0.22	BD191	+0.61	OC67	+0.15	2N2926AL	+0.18
AD183	+0.22	BD192	+0.61	OC68	+0.15	2N2926AM	+0.18
AD184	+0.22	BD193	+0.61	OC69	+0.15	2N2926AN	+0.18
AD185	+0.22	BD194	+0.61	OC70	+0.15	2N2926AO	+0.18
AD186	+0.22	BD195	+0.61	OC71	+0.15	2N2926AP	+0.18
AD187	+0.22	BD196	+0.61	OC72	+0.15	2N2926AQ	+0.18
AD188	+0.22	BD197	+0.61	OC73	+0.15	2N2926AR	+0.18
AD189	+0.22	BD198	+0.61	OC74	+0.15	2N2926AS	+0.18
AD190	+0.22	BD199	+0.61	OC75	+0.15	2N2926AT	+0.18
AD191	+0.22	BD200	+0.61	OC76	+0.15	2N2926AU	+0.18
AD192	+0.22	BD201	+0.61	OC77	+0.15	2N2926AV	+0.18
AD193	+0.22	BD202	+0.61	OC78	+0.15	2N2926AW	+0.18
AD194	+0.22	BD203	+0.61	OC79	+0.15	2N2926AX	+0.18
AD195	+0.22	BD204	+0.61	OC80	+0.15	2N2926AY	+0.18
AD196	+0.22	BD205	+0.61	OC81	+0.15	2N2926AZ	+0.18
AD197	+0.22	BD206	+0.61	OC82	+0.15	2N2926BA	+0.18
AD198	+0.22	BD207	+0.61	OC83	+0.15	2N2926BB	+0.18
AD199	+0.22	BD208	+0.61	OC84	+0.15	2N2926BC	+0.18
AD200	+0.22	BD209	+0.61	OC85	+0.15	2N2926BD	+0.18
AD201	+0.22	BD210	+0.61	OC86	+0.15	2N2926BE	+0.18
AD202	+0.22	BD211	+0.61	OC87	+0.15	2N2926BF	+0.18
AD203	+0.22	BD212	+0.61	OC88	+0.15	2N2926BG	+0.18
AD204	+0.22	BD213	+0.61	OC89	+0.15	2N2926BH	+0.18
AD205	+0.22	BD214	+0.61	OC90	+0.15	2N2926BI	+0.18
AD206	+0.22	BD215	+0.61	OC91	+0.15	2N2926BJ	+0.18
AD207	+0.22	BD216	+0.61	OC92	+0.15	2N2926BK	+0.18
AD208	+0.22	BD217	+0.61	OC93	+0.15	2N2926BL	+0.18
AD209	+0.22	BD218	+0.61	OC94	+0.15	2N2926BM	+0.18
AD210	+0.22	BD219	+0.61	OC95	+0.15	2N2926BN	+0.18
AD211	+0.22	BD220	+0.61	OC96	+0.15	2N2926BO	+0.18
AD212	+0.22	BD221	+0.61	OC97	+0.15	2N2926BP	+0.18
AD213	+0.22	BD222	+0.61	OC98	+0.15	2N2926BQ	+0.18
AD214	+0.22	BD223	+0.61	OC99	+0.15	2N2926BR	+0.18
AD215	+0.22	BD224	+0.61	OC100	+0.15	2N2926BS	+0.18

### \*74 SERIES T.T.L. I.C.'s

BI-PAK STILL LOW PRICE. FULL SPECIFICATION GUARANTEED

Type	Quantities	Type	Quantities
	1 25 100+		1 25 100+
7400	0.09	0.09	0.05
7401	0.10	0.09	0.08
7402	0.11	0.10	0.09
7403	0.11	0.10	0.09
7404	0.13	0.12	0.11
7405	0.13	0.12	0.11
7406	0.15	0.14	0.13
7407	0.15	0.14	0.13
7408	0.15	0.14	0.13
7409	0.15	0.14	0.13
7410	0.09	0.09	0.08
7411	0.23	0.22	0.21
7412	0.26	0.25	0.24
7413	0.26	0.25	0.24
7414	0.26	0.25	0.24
7415	0.28	0.27	0.26
7416	0.28	0.27	0.26
7417	0.28	0.27	0.26
7418	0.28	0.27	0.26
7419	0.28	0.27	0.26
7420	0.28	0.27	0.26
7421	0.28	0.27	0.26
7422	0.38	0.38	0.38
7423	0.38	0.38	0.38
7424	0.38	0.38	0.38
7425	0.38	0.38	0.38
7426	0.38	0.38	0.38
7427	0.38	0.38	0.38
7428	0.42	0.42	0.42
7429	0.42	0.42	0.42
7430	0.42	0.42	0.42
7431	0.42	0.42	0.42
7432	0.30	0.28	0.26
7433	0.39	0.37	0.35
7434	1.10	1.05	1.00
7435	1.10	1.05	1.00
7436	0.95	0.90	0.85
7437	0.95	0.90	0.85
7438	0.95	0.90	0.85
7439	0.95	0.90	0.85
7440	0.95	0.90	0.85
7441	0.64	0.62	0.60
7442	0.64	0.62	0.60
7443	1.10	1.05	1.00
7444	1.10	1.05	1.00
7445	0.95	0.90	0.85
7446	1.10	1.05	1.00
7447	0.95	0.90	0.85
7448	0.80	0.78	0.76
7449	0.95	0.90	0.85
7450	0.12	0.11	0.10
7451	0.12	0.11	0.10
7452	0.12	0.11	0.10
7453	0.12	0.11	0.10
7454	0.12	0.11	0.10
7455	0.12	0.11	0.10
7456	0.12	0.11	0.10
7457	0.12	0.11	0.10
7458	0.12	0.11	0.10
7459	0.12	0.11	0.10
7460	0.12	0.11	0.10
7461	0.12	0.11	0.10
7462	0.12	0.11	0.10
7463	0.12	0.11	0.10
7464	0.12	0.11	0.10
7465	0.1		

# BI-PAK

High quality modules for stereo, mono and other audio equipment.



**NEW**

PUSH-BUTTON

## STEREO FM TUNER

## MPA 30



Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

**£2.65**

OUR PRICE ONLY

**£19.95** Fitted with Phase Lock-loop Decoder

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

Typical Specification:  
Sensitivity 3µ volts  
Stereo separation 30db  
Supply required 20-30v at 90 Ma max.

**VAT ADD 12 1/2%**

**POSTAGE & PACKING**  
Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

## STEREO PRE-AMPLIFIER



**PA 100**  
OUR PRICE **£13.50**


A top quality stereo pre-amplifier and tone control unit. The six push-button selector switch provides a choice of inputs together with two really effective filters for high and low frequencies, plus tape output.

Frequency Response + 1dB 20Hz - 20KHz. Sensitivity of inputs  
1. Tape Input 100mV into 100K ohms  
2. Radio Tuner 100mV into 100K ohms  
3. Magnetic P.U. 3mV into 50K ohms  
P.U. input equalises to R1AA curve with 1dB from 20Hz to 20KHz.  
Supply - 20-35V at 20mA.

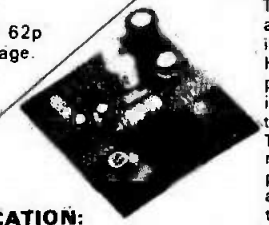**MK. 60 AUDIO KIT:** Comprising 2 x AL60's, 1 x SPM80, 1 x BTM80, 1 x PA100, 1 front panel and knobs, 1 Kit of parts to include on/off switch, neon indicator, stereo headphone sockets plus instruction booklet. **COMPLETE PRICE £27.55.**

Dimensions 299mm x 89mm x 35mm.

**TEAK 60 AUDIO KIT:** plus 62p postage. Comprising: Teak veneered cabinet size 16 3/4" x 11 1/2" x 3 3/4", other parts include aluminium chassis, heatsink and front panel bracket plus back panel and appropriate sockets etc. **KIT PRICE £9.20** plus 62p postage.



## AUDIO AMPLIFIER MODULES

The AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 5 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

- SPECIFICATION:**
- Harmonic Distortion Po=3 watts f=1KHz 02.5%
  - Load Impedance 8-16ohm
  - Frequency response ±3dB Po=2 watts 50Hz-25Hz
  - Sensitivity for Rated O/P - Vs=25v. RL=8ohm f=1KHz 75mV.RMS

**AL20 5w R.M.S. £2.65 AL30 10w R.M.S. £2.95**



## AL 60 25 Watts (RMS)

- ★ Max Heat Sink temp 90C.
- ★ Frequency response 20Hz to 100KHz
- ★ Distortion better than 0.1 at 1KHz
- ★ Supply voltage 15-50v
- ★ Thermal Feedback
- ★ Latest Design Improvements
- ★ Load - 3,4,8, or 16 ohms
- ★ Signal to noise ratio 80db
- ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

**£3.95**

**NEW**

## PA12

**NEW PA12 Stereo Pre-Amplifier** completely redesigned for use with AL 20/30 Amplifier.

Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB): Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V.5mA. Size 152mm x 84mm x 33mm.

**£6.50**

## PS12

Power supply for AL20/30, PA12, SA450 etc.

Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output current 800 mA Max. Size 60mm x 43mm x 26mm.

Transformer T538 £2.30

**OUR PRICE £1.20**

## Stabilised Power Supply Type SPM80

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

Transformer BMT80 £2.60 + 62p postage

**£3.00**

# BI-PAK

P.O. BOX 6, WARE, HERTS.

# news digest

## YOU'RE NEVER ALONE WITH AN MPU




The world's largest ever ship, the 550,000 ton 'Batillus' is under MPU control! All engine control monitoring and alarm systems are now run from the system shown in the picture. The video monitors are hooked to the MPU 'Alphaprom' units — one per engine — which each have 225 alarm points throughout its system.

The control room has an alpha-
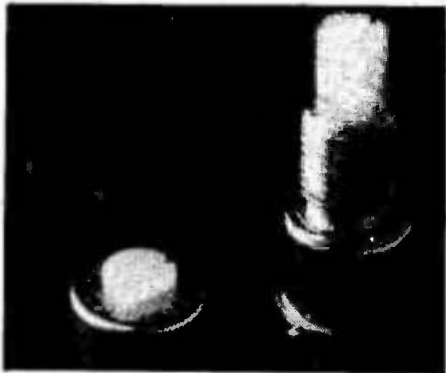
## VERY SUBMIN SWITCH

Roxburgh Electronics have a new subminiature rotary switch which is sealed in an industry-standard TO-5 can. Designated the Series 30, the switch offers a wide range of configurations, and from 2 to 8 switch positions.



Nominally rated at 0.5A, 125V AC, the switch contacts are capable of handling up to 3A, and the Series has been designed for direct mounting to PCB's, or for panel-mounting by means of an optional bush.

A thumbwheel switch is also available.

Roxburgh Electronics Limited, 22 Winchelsea Road, Rye, Sussex.

numeric printer, which reads out to the operator any deviation in levels considered significant, along with precise time codes. New alarms appear as red type, and faults rectified as black. Naturally a loud acoustic alarm is also provided. After all the controller might be colour-blind!

CSI Bv, P. O. Box 174 Vlaardingen, Holland.

## SINGLE-CHIP JFET PREAMPLIFIER

The first monolithic JFET preamplifiers types T100/300 by Siliconix will serve as single-device replacements for the discrete component assemblies generally used to buffer high-impedance signals from piezo-electric and capacitive microphones/transducers. They operate at low power levels from single DC power supplies of 1.3 to 30V. Applications include hearing aids, microphone preamplifiers and general purpose impedance converters. Two versions have been introduced, both in TO-72 metal can packages.

No external components are required for operation with devices such as ceramic electret-condenser, and air-condenser, microphones, or piezo-electric capacitive transducers.

Each chip contains an N-channel depletion-mode, junction field effect transistor (JFET), with a diffused source resistor and back-to-back Schottky diodes. The diodes from the high-impedance, gate-bias resistance. The circuit is self biasing.

Siliconix Limited, 30A High Street, Thatcham, Newbury, Berks RG13 4JG.


## TRUTH TABLE DETECTOR CLIP

The 548A Logic Chip from H.P. is designed to clip on to a 16-pin DIP-pack IC, when its light-emitting diodes show the logic states of each of the IC's pins simultaneously.

It is automatic for all logic families from 4 to 18V DC. Three volt CMOS is tested by connecting a 4.5V supply to an auxiliary power pin.

With internal, self-seeking logic circuitry, the 548A locates the supply and ground pins automatically; it can be placed on the IC 'upside down' or 'rightside up'. Total current drawn by the clip is less than 40mA with 15 LEDs on. Input current is less than 15mA, assuring virtually no circuit loading. Inputs are protected to 30V DC for 1 minute. Price is £77.

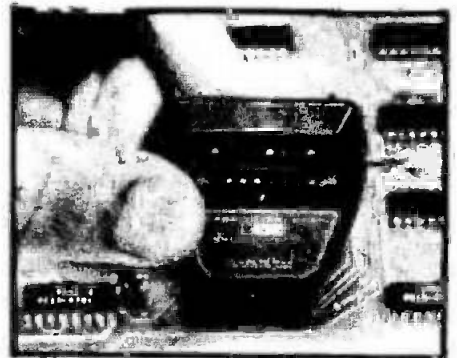Hewlett-Packard Limited, King Street Lane, Winnersh, Wokingham, Berkshire RG11 5AR.



## SHARP PRACTICES IN WATCHES?


One very interesting little snippet caught our eye last month — Gillette, the well known face scraping company, are advertising in the USA for digital watch engineers. Both LCD and LED men are required, as are I<sup>2</sup>L logic designers. With their past history Gillette can't fail to carve themselves a good chunk of the market, (literally!).

## GAMES FOR HIRE

Later this year Fairchild Semiconductors who have recently taken a hand in digital watches, will be introducing their long awaited TV games chips into Europe. These are based on the F8 microprocessor, and according to Fairchild, can handle teletext as well. In order to assure themselves of a market, the company plans to do a deal with a TV rental company so that games could be hired with the set. The cost to the user would be about £1 extra on top of a colour rental.
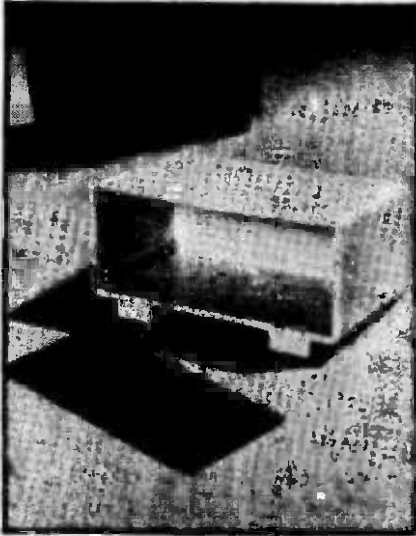
## TIME BOX

Not for pursuit of Daleks, but ideal for digital clocks, this new case from West Hyde is moulded in anti-static ABS with 3½mm walls. It has high impact strength, and integral front feet which lift the case to good viewing angle. Two positions for PCB's are provided.



Available in white, red, orange and blue in any quantity, all have 3mm thick red acrylic window panels.

Dimensions: 56mm x 131mm x 71.5mm deep. Prices: 1 off £1.79 – 100 off less 25%.

West Hyde Developments Limited, Ryefield Crescent, Northwood Hills, Middlesex HA6 1NN.

## NEW CATALOGUE FROM MARSHALL'S

One of the catalogues which we at ETI refer to most has just been updated: that from Marshall's. The new edition has 160 pages – considerably larger than the previous one. More information of semiconductor lead-outs are included as is a new listing of Japanese equivalents.

For callers the price is 30p but it's also available by post for 40p from A. Marshall, 42 Cricklewood Broadway, London NW2 3ET.

## CLOCK MODULE SHRINKS

The interest generated by the MA1001 series of clock module subsystems has encouraged National to introduce a further series, designated MA1002. This new series miniaturises the complete module to a package only 7.5mm x 3.5mm,


Various versions are available for 12/24 hours formats and input frequencies, and further details are available on request from National Semiconductor, 19 Goldington Road, Bedford, MK40 3LF.

## HOME ON THE (TEXAS) RANGE

The consumer electronics fields is about to be asked to hear the weight of yet another giant. Texas Instruments are placing their highly digital boots firmly in the earth of the home market, and expect them to take root there, and grow to 93% of their total business in 1978.


Whether or not they achieve the full bloom of this success depends entirely as to whether you and I take to the gifts the giant comes bearing. It almost gives one a feeling of power does it not?

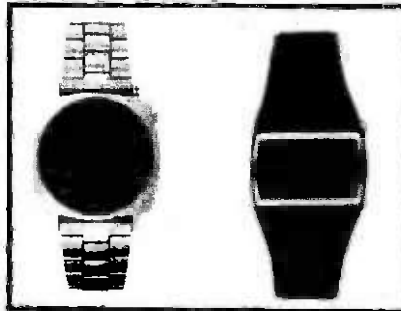As a starter T.I. have introduced 16 digital watches, 12 of which are in plastic cases. Technology is I<sup>2</sup>L, not



the ubiquitous MOS – a move to newer pastures, broken by Sinclair. The range is priced from £15.95 to around £32. Yer pays yer money and takes yer choice – of case and strap, the modules are the same in all the watches, and give 5 functions as usual. The styling is certainly carefully thought out, and new types will be dropped onto the public as and when T.I. deem it timely to do so.

A calendar feature is incorporated,

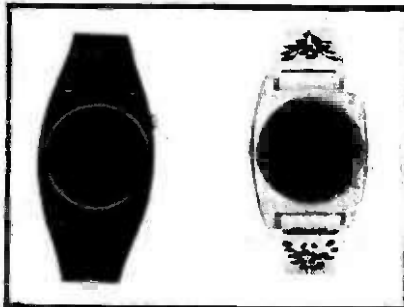

preset to 4 years of correct month length. However since the batteries last you at most a year, and date info is lost on switch-off (battery change) so don't get *too* excited with the idea.

Marketing is to be through anybody and everybody who will sell the watches, so they will be around very quickly. The displays are all LED but Texas are expending many hours of toil in the LCD field, and expect to bring to fruition a watch with this display sometime during 1977.

Calculators are the other channel from which T.I. hopes our money


will flow. In order to speed this flood, they have an extensive new range with several very ingenious machines. At the low cost end we have the TI 1600, a slimline rechargeable at £17.95. Especially for the student, the TI 30 possess no less than FIFTEEN levels of parenthesis. It also has full scientific facilities, and will turn off the display if you're wasting battery power.



Price £19.95.

The TI 5050 and 5040 are thermal printing machines, the former portable at £99, and the latter desk-bound for £109. Perhaps the most amazing of all is the SR-60. Defined as a calculator only because it requires no peripherals to work, it has a possible 1920 programme steps and 100 memories! The display is alphanumeric, and can interrogate the user if programmed to!

Well, it prompts him anyway, (It is

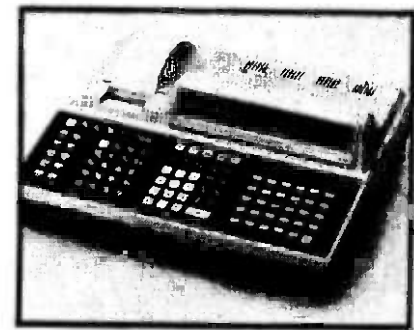


to be hoped we *don't* get an SS machine just yet! Ve hav vays of making you compute and all that). The tings the SR 60 won't do are very few indeed, but for circa £1500 perhaps this is not too surprising. Before we are deafened by crys of 'MPU's rule OK' let us add hastily that this is *not* an MPU machine, but is calculator chip based.

The range all use T.I.'s new (?) Arithmetic Operating Logic, said to be truly arithmetic in operation. In practice it looks like an improvement on ordinary arithmetic logic certainly, and *anything* is an improvement on RPN!
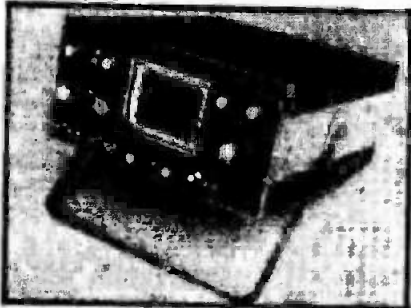
## COLOUR OSCILLOSCOPE

The Scopex 4D25 now includes a special 'Glaresheq' graticule for 'reflection-free' measurement. This does not decrease the brilliance of the trace or increase the spot size but acts to down extraneous reflection.



As a 'reaction against drabness in instrumentation', a pleasant shade of blue has been selected for the front panel, and the controls and bezel have been colour matched.

Technically the 4D25 offers 3% accuracy on both time and voltage measurements, and incorporates a 25MHz bandwidth with Y-amplifier signal delay. Apart from which think how well it will match the wallpaper! Price £245.

Scopex Instruments Limited, Pixmore Industrial Estate, Pixmore Avenue, Letchworth, Herts SG6 1Jd.

## IN 3 x 10<sup>6</sup> YEARS TIME, IT WILL BE ONE SECOND SLOW!

RCA are working for the US Navy to determine the feasibility of using hydrogen maser clocks -- precise to one second in three million years -- in Global Positioning Systems (GPS) satellites.

These satellites are part of a tri-service programme under Air Force direction. NTS-1 was launched in July 1974 and tested rubidium clocks. NTS-2 will test cesium clocks; NTS-3 will test hydrogen maser clocks.

A planned constellation of 24 GPS satellites will be continuously transmitting time synchronized signals. A ship, airplane or land craft suitably equipped to receive the signals, will be able to determine its exact position anywhere on the globe.

Hydrogen atoms are employed because of an extremely stable fixed frequency generated under certain controlled conditions. The atoms are produced from hydrogen gas molecules by an electrical discharge and beamed into a special container in a microwave cavity. The hydrogen atoms undergo an energy state change and emit a frequency that can be used to very accurately control the output frequency.

Can you just see the thing ticking away merrily on your mantelpiece? The BBC would have to phone you for a time check -- about 5976 AD!

## £37.286 PER DIGIT!

The Data Precision 175 is a full function, 32 range battery and line operated instrument, whose basic sensitivity is 100mV.

With 5 ranges of DC/AC voltage measurement and 100% overrange capability per range, the 175 measures from 100µV to 1000V, protected to ±1000V on any range (including 100mV). Basic instrument accuracy is 0.1%, and this is a 1 year specification over a ±50 temperature range.

Resistance measurements are catered for from 100mΩ to 20MΩ in 6 ranges (basic accuracy of better than 0.1%).

A 'low voltage' mode is provided having the same ranges as the normal resistance measurement, but with only 300mV of open circuit excitation. This enables resistance measurements to be made on circuits while still connected to semiconductor devices.

The £120 the Model 175 costs brings, in addition to the basic instrument, its rechargeable battery module, a pair of fuse protected test leads, mains lead with charger, alligator clip adaptors and a complete certificate of traceability.



Farnell International Instruments Limited, Sandbeck Way, Wetherby, West Yorkshire LS22 4DH.

## FIRST LIVE 4-CHANNEL BROADCAST

Live quadrasonic broadcasting experiments have been conducted by Radio Clyde (the commercial station servicing the Glasgow area). Four and a half hours of the "Proms 76" concerts, by the Scottish National Orchestra, were broadcast in four-channel mode, direct from Kelvin Hall, Glasgow, on June 26 and July 2, using encoded signals. The encoding system used for this experiment was the Sansui QS Matrix.

The experiment follows one by Piccadilly Radio -- in April -- where, apart from certain records already encoded, the Station's output for two days was synthesized via the QS system into 4-channel. The Independent Broadcasting Authority monitored and transmissions. We can only hope for the experiments to spread, with perhaps good ole Auntie taking a hand (or four!).

## NO, THE WHISTLE ISN'T DIGITAL



This hand-held battery-powered stopwatch measure time to 50 minutes, 59.9 seconds in one-tenth second intervals. Controls allow simple start/stop, Time IN/Time Out, and include safeguard against accidental reset.

Accuracy is controlled by a quartz crystal, and the display LED. Weighing 6oz., the ET105 is approximately 4½ x 2½ x 1½ ins, and will slip into a jacket pocket.

Price to be announced. Newitt and Company Limited, 81 Goodramgate, York YO1 2LU.

## IC IN CAMERA

Contained in a 16 pin DIP the ZNA134 is a complete system, requiring only a single 5V supply. An on-chip oscillator (which can be over-driven) externally permits multiple SPG unit usage.

The ZNA134 incorporates such features as synchronising between units, direct reset to horizontal and vertical counters, facilities for adding and subtracting lines, automatic interlacing and a field reference output. Perhaps its most novel feature is its ability to provide both CCIR and EIA equalisation by changing the voltage on a single pin.

The ZNA134 generates all the horizontal, vertical, mixed blanking and synchronising pulses necessary for raster generation in 625 or 525 line commercial, industrial or military TV systems. It can be supplied to operate over the military temperature ranges.

Ferranti Limited, Electronic Components Division, Gem Mill, Chadderton, Oldham OL9 8NP.



# Get a great deal from Marshall's

A. Marshall (London) Ltd Dept: ETI  
40/42 Cricklewood Broadway London NW2 3ET  
Tel: 01-452 0161/2 Telex: 21492  
& 85 West Regent St Glasgow G2 2QD  
Tel: 041-332 4133  
& 1 Straits Parade Fishponds Bristol BS16 2LX  
Tel: 0272-654201/2  
& 27 Rue Danton Issy Les Moulineaux Paris 92

Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat

Trade and export enquiries welcome. Catalogue price 40p (30p to callers).

## Top 500 Semiconductors from the largest range in the UK — All devices manufacturers branded stock

2N4156	1.40	2N3390	0.37	2N5295	0.40	AF186	0.50	BC2598	0.18	BF194	0.12	14D1L	0.41	SN7603N	2.36
2N456A	1.54	2N3391	0.29	2N5296	0.36	AF200	0.70	BC261A	0.21	BF195	0.11	LM7805P	1.99	SN76013N	1.50
2N457A	1.70	2N3391A	0.34	2N5298	0.36	AF239	0.74	BC262B	0.19	BF196	0.13	LM7812P	1.99	SN76023N	1.95
2N490	4.60	2N3392	0.14	2N5457	0.29	AF240	0.90	BC263C	0.31	BF197	0.14	LM7815P	1.99	SN760250	2.50
2N491	5.10	2N3393	0.15	2N5458	0.29	AF279	0.80	BC300	0.45	BF198	0.15	LM7824P	1.99	ST2	0.20
2N492	5.75	2N3394	0.15	2N5459	0.29	AF280	0.85	BC301	0.45	BF200	0.29	MC1303	1.47	TAA300	2.67
2N493	5.98	2N3402	0.30	2N5492	0.42	AL102	1.50	BC303	0.60	BF225J	0.25	MC1310	1.96	AA263	1.25
2N896	0.25	2N3414	0.15	2N5494	0.45	AL103	1.50	BC307	0.20	BF244	0.35	MC1330P	0.75	TAA350	2.48
2N897	0.16	2N3415	0.17	2N5498	0.50	BC107	0.14	BC308A	0.18	BF245	0.34	MC1352P	0.87	TAA550	0.60
2N898	0.82	2N3416	0.23	2N5777	0.45	BC108	0.15	BC309C	0.25	BF246	0.75	MC1466L	3.95	TAA611C	2.25
2N899	0.55	2N3417	0.27	2N6027	0.45	BC109	0.15	BC317	0.14	BF254	0.20	MC1469R	2.80	TAA621	2.15
2N906	0.12	2N3440	0.57	3M123	0.50	BC113	0.17	BC318	0.13	BF255	0.20	ME0402	0.20	TAA681B	1.32
2N906AN	0.12	2N3441	0.78	3M139	1.45	BC115	0.19	BC337	0.19	BF257	0.27	ME0404	0.15	TAA681B	1.99
2N908	0.21	2N3442	1.20	3M140	0.85	BC116	0.19	BC338	0.21	BF258	0.49	ME0412	0.20	TAA681B	2.50
2N909	0.50	2N3638	0.16	3M141	0.85	BC117	0.22	BC354E	0.10	BF259	0.39	ME4102	0.10	TAA681B	2.90
2N911	0.55	2N3638A	0.18	3M200	2.60	BC117	0.22	BC548	0.10	BF459	0.39	MF4104	0.10	TAA681B	2.90
2N918	0.22	2N3639	0.30	3M351	0.45	BC118	0.16	BC549	0.13	BF479	0.24	ML480	1.65	TAA681B	0.30
2N918A	0.40	2N3641	0.20	3M362	0.48	BC119	0.16	BCY30	1.03	BF521A	2.60	MLJ480	1.30	TIP29A	0.50
2N920	0.69	2N3702	0.17	40363	1.00	BC121	0.45	HCY31	1.06	BF528	1.04	MLJ480	1.05	TIP30A	0.60
2N924	0.22	2N3703	0.15	40389	0.50	BC125	0.18	HCY32	1.18	BF566	0.30	MLJ490	1.55	TIP31A	0.62
2N926	0.43	2N3704	0.15	40394	1.20	BC126	0.25	HCY33	0.90	BF569	0.27	MJ2955	1.00	TIP32A	0.75
2N918	0.34	2N3705	0.15	40395	1.20	BC132	0.30	HCY34	0.98	BF579	0.36	MJ2955	1.00	TIP33A	1.00
2N929	0.25	2N3708	0.14	40405	0.70	BC134	0.30	HCY36	2.00	BFX30	0.38	MJE340	0.58	TIP33A	1.50
2N930	0.26	2N3709	0.15	40406	0.38	BC135	0.15	HCY42	0.60	BFX84	0.38	MJE370	0.68	TIP34A	1.50
2N9302	0.26	2N3709	0.14	40408	0.60	BC136	0.19	HCY58	0.55	BFX85	0.41	MJE371	0.87	TIP35A	1.70
2N1303	0.45	2N3709	0.15	40409	0.55	BC137	0.14	HCY59	0.32	BFX87	0.35	MJE520	0.65	TIP36A	8.35
2N1304	0.40	2N3710	0.14	40410	0.55	BC140	0.60	HCY70	0.25	BFX88	0.32	MJE521	0.75	TIP41A	1.32
2N1305	0.40	2N3711	0.15	40411	2.30	BC141	0.65	HCY71	0.26	BFX89	0.37	ME4955	1.25	TIP42A	0.90
2N1306	0.31	2N3712	1.20	40594	0.75	BC142	0.30	HCY72	0.24	BFX89	0.37	MJE3056	0.75	TIP29C	0.80
2N1307	0.30	2N3713	2.30	40595	0.85	BC143	0.30	BD115	1.20	BFY52	0.36	MP8112	0.40	TIP31C	0.85
2N1308	0.60	2N3714	2.45	40596	0.70	BC147	0.18	BD116	1.20	BFY53	0.34	MP8113	0.45	TIP32C	1.25
2N1309	0.60	2N3715	2.45	40602	0.50	BC148	0.10	BD121	2.00	BFY53	0.34	MPF102	0.30	TIP33C	1.70
2N1671	1.80	2N3716	2.60	40603	0.60	BC149	0.13	BD123	2.00	BFY90	1.27	MPF105	0.20	TIP34C	1.70
2N1671A	1.92	2N3721	1.60	40604	0.60	BC153	0.27	BD124	2.00	BRV39	0.50	MPSA06	0.20	TIP41C	1.00
2N1671B	2.12	2N3722	1.70	40636	1.15	BC154	0.27	BD131	0.51	BSX20	0.31	MPSA06	0.20	TIP41C	1.00
2N1711	0.27	2N3723	2.65	40673	0.73	BC157	0.12	BD132	0.54	BSX21	0.32	MPSA12	0.35	TIP42C	1.20
2N1807	5.50	2N3729	3.15	AC126	0.37	BC158	0.11	BD135	0.54	BSX21	0.32	MPSA55	0.20	TIP2955	1.00
2N2102	0.60	2N3790	2.75	AC127	0.44	BC160	0.11	BD135	0.54	BSX21	0.32	MPSA55	0.20	TIP3055	0.50
2N2147	1.40	2N3791	2.75	AC128	0.57	BC167B	0.12	BD137	0.36	CA3080A	1.10	MPSU05	0.40	1N543	0.30
2N2148	1.65	2N3792	2.90	AC151V	0.35	BC168B	0.12	BD138	0.39	CA3030A	1.80	MPSU06	0.40	ZTK300	0.15
2N2160	1.10	2N3794	0.26	AC152V	0.50	BC168C	0.12	BD139	0.42	CA3078A	0.85	MPSU06	0.45	ZTK301	0.15
2N2218A	0.47	2N3810	0.26	AC153	0.40	BC169B	0.12	BD140	0.46	CA3035	0.80	MPSU06	0.45	ZTK302	0.20
2N2219	0.42	2N3820	0.29	AC153K	0.42	BC169C	0.12	BD529	0.35	CA3057	1.62	MPSU06	0.45	ZTK302	0.20
2N2219A	0.52	2N3823	0.61	AC154	0.45	BC170A	0.16	BD530	0.38	CA3058	0.73	NF555V	1.30	ZTK501	0.15
2N2220	0.35	2N3904	0.21	AC176	0.40	BC171	0.16	BD530	0.38	CA3058	0.73	NF555V	1.30	ZTK501	0.15
2N2221	0.22	2N3906	0.22	AC176K	0.45	BC172	0.14	BDY70	1.13	CA3085E	2.00	NE561	4.48	ZTK502	0.18
2N2221A	0.25	2N4035	0.40	AC187K	0.40	BF177	0.19	BF117	0.70	CA3090Q	4.25	NE565	1.30	ZTK503	0.22
2N2222	0.25	2N4037	0.55	AC188K	0.45	BF178	0.18	BF121	0.55	LM301A	0.47	OC28	2.00		
2N2222A	0.25	2N4058	0.20	AD142	0.65	BF179	0.21	BF123	0.55	LM308N	1.32	OC35	1.50		
2N2368	0.17	2N4059	0.15	AD143	0.75	BF182	0.11	BF152	0.25	LM309K	1.80	OC42	0.50		
2N2369A	0.21	2N4060	0.20	AD149	0.74	BF183	0.11	BF153	0.25	LM380	0.98	OC45	0.75		
2N2369	0.25	2N4061	0.17	AD150	1.20	BF183	0.11	BF154	0.25	LM390N	0.55	OC71	0.45		
2N2646	0.55	2N4062	0.18	AD161	1.23	BF184	0.12	BF159	0.35	LM702C	0.75	OC72	0.45		
2N2647	1.10	2N4126	0.17	AD167	1.23	BF184	0.12	BF160	0.30	LM709T05	0.98	OC81	0.75		
2N2904	0.36	2N4289	0.30	AF106	0.45	BF184	0.12	BF161	0.60	LM711CAN	0.38	OC83	0.50		
2N2904A	0.37	2N4918	0.85	AF114	0.65	BF184	0.12	BF166	0.40	BD1L	0.35	OPR2	0.60		
2N2905	0.37	2N4920	0.90	AF115	0.65	BF207	0.10	BF167	0.33	1401L	0.40	R53	1.80		
2N2905A	0.35	2N4921	0.60	AF116	0.65	BF212	0.14	BF173	0.33	LM710	0.45	SL414A	2.35		
2N2906	0.28	2N4922	0.65	AF117	0.65	BF212L	0.14	BF177	0.38	LM390N	0.55	SL610C	2.35		
2N2906A	0.25	2N4923	0.70	AF118	0.65	BF214L	0.17	BF178	0.48	LM712	0.60	SL611C	2.35		
2N2907	0.21	2N5190	0.70	AF124	0.65	BF237	0.14	BF178	0.48	LM712099	0.40	SL612C	2.35		
2N2907A	0.22	2N5191	1.30	AF125	0.65	BF238	0.12	BF180	0.36	LM709CAN	0.48	SL620C	3.50		
2N2924	0.15	2N5192	1.00	AF126	0.65	BF239	0.15	BF181	0.36	BD1L	0.40	SL621C	3.50		
2N2926	0.13	2N5195	1.10	AF127	0.65	BF251	0.15	BF182	0.35	1401L	0.40	SL623	5.75		
2N3053	0.25	2N5245	0.35	AF139	0.69	BC253	0.22	BF183	0.35	LM747EN	0.78	SL640C	4.00		
2N3054	0.50	2N5294	0.40			BC257A	0.17	BF184	0.35	LM748	0.78	SL641C	4.00		
2N3055	0.65					BC258A	0.17	BF185	0.35	BD1L	0.44				

## NEW RANGE TOOLS — HIGH QUALITY MINIATURE ELECTRONIC PLIERS INSULATED HANDLES

Round nose box joint 4" long £2.50  
Diagonal cutters box joint 4" long £2.80  
Flat nose box joint 4" long £2.40  
Snipe nose box joint 4" long £2.40  
Desoldering tool £5.00

P.C. MARKER PEN DALO 33PC  
0.87. ZENER DIODES 400MW  
0.11, 1W, 0.17, 2.5W 0.35, 1C  
SOCKETS 8D1L, 0.14, 14D1L 0.15,  
16D1L 0.16, RESISTORS 1/4W  
0.02 (100 per value £1.30), 1/2W  
0.03 (100 per value £2.00),  
SCORPIO CAR IGNITION KIT  
£12.95, BOX £1.80 TRANS-  
FORMERS £3.75 IMF 440 VAC  
£1.50 BOARD 0.95 JUMBO  
7-SEGMENT DISPLAYS £2.00.  
LEDs RED YELLOW GREEN 2in  
dia 0.24.

## SEE MARSHALL'S FOR CMOS

CD4000	0.20	CD4018	1.01	CD4042	0.83
CD4001	0.20	CD4019	0.57	CD4043	0.91
CD4002	0.20	CD4020	1.12	CD4044	0.85
CD4006	1.16	CD4021	1.01	CD4045	1.30
CD4007	0.20	CD4022	0.97	CD4046	1.20
CD4008	0.97	CD4023	0.20	CD4047	0.95
CD4009	0.57	CD4024	0.79	CD4049	0.56
CD4010	0.57	CD4025	0.20	CD4050	0.56
CD4011	0.20	CD4027	0.56	CD451D	1.54
CD4012	0.20	CD4028	0.91	CD4511	1.70
CD4013	0.59	CD4029	1.17	CD4516	1.54
CD4014	1.01	CD4030	0.57	CD4518	1.38
CD4015	1.01	CD4031	2.26	CD4520	1.38
CD4016	0.56	CD4037	0.97	CD4553	4.07
CD4017	1.01	CD4041	0.83		

Mini ceramic capacitors  
1pF—0.015mF  
5p

# LOW Cost VDU

## Project 560

## Part 1: Construction

Components for this project are available from Watford Electronics (who supply the metal case, type WE1), Technomatic, Bywood or Catronics.

LAST MONTH WE DESCRIBED the design requirements and system description of a simple VDU; this month we will cover most aspects of construction with modifications and applications next month. The project has been designed with PCBs in order to simplify construction; there is no reason why the circuit should not be built on Veroboard as was the first prototype of the 560 VDU.

### INTERFACE TO TV

The TV set used in the prototype is a Heathkit GR-9900 set built from a kit. If you decide to use this kit set which is one of the most attractive portable sets that I have seen then it will be necessary to break the circuit in the set by removing the positive end of C18 from the PCB. On the prototype two video sockets were added at the rear of the set, one connected to the point where C18 was on the PCB (TV video out), and the other connected to the now floating end of C18 (Video in), both sockets using chassis ground. A short link of coax with a plug at each end will connect the two sockets for normal TV programs or the output from the 560 VDU can be connected to the Video in socket.

It may be possible to modify any other portable set in a similar manner but check that there is a transformer in the mains input circuit. Domestic TV sets may be modified to accept a video signal but check with manufacturer first. The alternative is to use a UHF modulator as supplied by Crofton Electronics but this must be correctly set up or else all of the verticals in each character will have a stepped or wobbly look. If a modulator is used then the 560 VDU can be used with any TV set, colour or B/W. NB: These modulators can transmit back down an aerial line even if the normal aerial line is disconnected and if the modulator output line is too near the aerial line then any other set

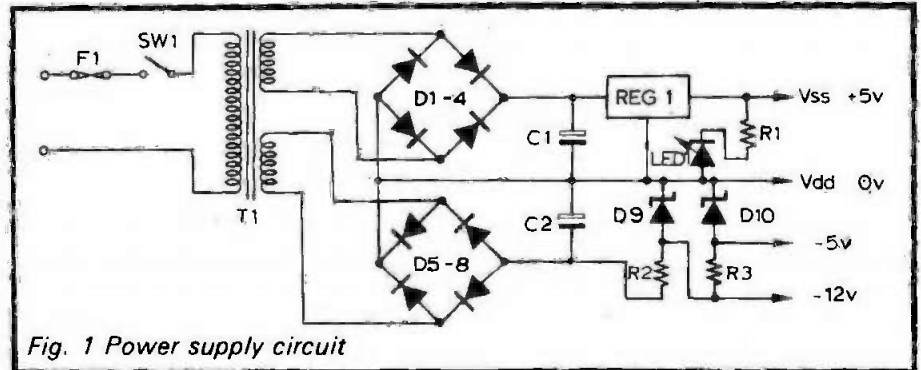


Fig. 1 Power supply circuit

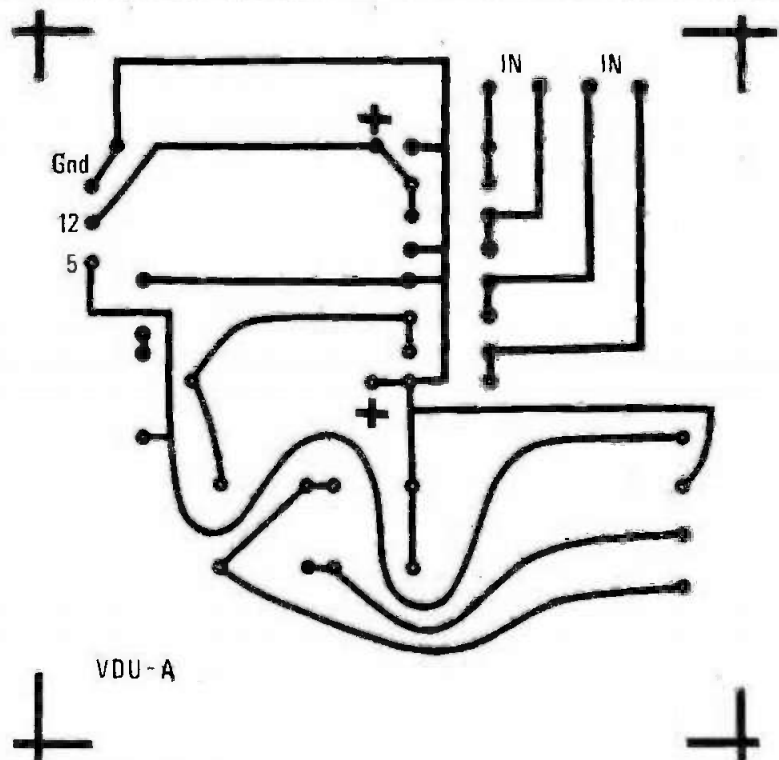


Fig. 2(a) Board A PCB

connected to that aerial may also pick up this signal. This is more likely to happen in flats, etc, where a common TV aerial is very often built-in.

### POWER SUPPLY

The TTL and MOS RAM require a stabilised 5v supply at about 1A current; this is most conveniently supplied by the well-known LM309

voltage regulator which uses the metal case as a heatsink and a groundplane. The MOS ROM (2513 character generator) requires supplies of 5v, GND, -5v and -12v, all at very low current levels; the -5 and -12v supplies are derived from a second winding on the transformer with Vdd as a common ground. The circuit diagram of the power supply shows the

two transformer windings rectified by D1-4 and D5-8 and smoothed by C1 and C2. The output from C1 is used to feed the voltage regulator REG1 which outputs a regulated 5v at up to 1Amp, LED1 and R1 are used as a panel lamp to indicate "Power On". The output from C2 will be in the area of -15v; this is limited by zener D9 to -12v and in turn this -12v is limited to -5v by zener D10. No indicators were used here but an LED could be connected across C2 (with suitable limiting resistor) to give a panel indication that both positive and negative supplies were on.

Note that the transformer must have two separate windings (12-0, 12-0); a 12-0-12 centre-tapped type will not do.

### BOARD 'B'

The block diagram of board 'B' is shown in Fig 3. Its function is to generate TV sync signals and character video information and then to mix these two signals with a blanking signal to produce a standard video signal for input to a modified TV set.

The sync generator is formed by two 555 timers in a stable mode both with a mark/space ratio of about 10:1. IC1 runs at 50Hz and IC2 at 15KHz. The outputs from these ICs consist of a short negative pulse from each which are mixed in IC5 to give a mixed sync signal. We will refer to these signals as FS (Frame Sync), LS (Line Sync) and MSYN. IC3 and IC4 are 555 timers in the monostable mode. IC3 uses FS as a trigger input and produces an output called FSD (Frame Sync Delay) which is basically FS inverted but with the length of the short pulse adjustable by VR3. The width of this pulse is used to define the distance from the top of the screen at which the output will start and the signal is used to blank the video and to reset line and row counters. IC4 produces a similar signal (LSD) which defines the distance from the left-hand side of the screen and is used to blank the video and also resets the Master Clock (MCLK) and character counters.

The Master Clock (MCLK) is generated using two gates of IC5 which will oscillate at about 6MHz whenever LSD is low. As LSD always goes low at the same "time" on each TV line MCLK always starts at the same position on each TV line; this is very important to avoid ragged edges or verticals on the characters.

### VIDEO GENERATOR

IC15 is a 7421 4-input AND gate (note not a 7420 NAND) which mixes the blanking signals RCLK, FBLK, LBLKI, and BLNK. RCLK occurs on the last two of every ten TV lines after FSD, this thus blanks at the bottom of each character row. FBLK and LBLKI are from the flip-flops IC13-14, the FBLK signal is set by FSD and reset by EOF which is generated when the text row counter exceeds the number of rows (8 at present). LBLKI is formed in a similar manner. To test board "B" connect a temporary link from LBLKO to LBLKI. BLNK signal is generated to "flash" the output character, it can be left unconnected at present. IC15 output (BVID) is mixed with the character video (CVID) from the character generator and multiplexer and then mixed with MSYN to emerge from IC16 as something close to a standard video signal. If we mix this signal reduced

by about 50% with the full scale MSYN we have a standard video signal with the large negative troughs from MSYN very apparent if seen on a scope.

If you build up board "B" with ICs 1-6 and 13-16 and associated components you should now be able to produce a video picture on the set. Set all presets to midway and turn on, adjust VR1 until picture stops "rolling" and then adjust VR2 until picture stabilises horizontally. It was found that FS and LS sometimes drifted off after warming up and thus VR1 and VR2 may need adjusting during use. You may prefer to use panel-mounted potentiometers in place of or in addition to the board-mounted presets.

Having stabilised the picture you should see a set of horizontal lines produced by RCLK, these should be thick white lines with thin spaces between; each white line will

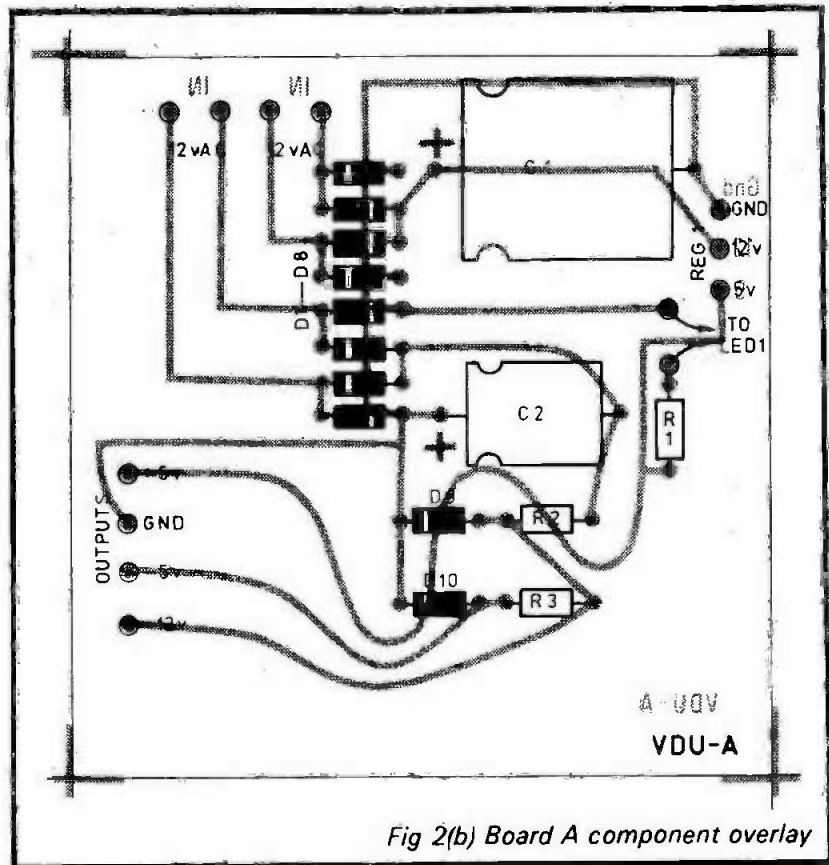


Fig 2(b) Board A component overlay

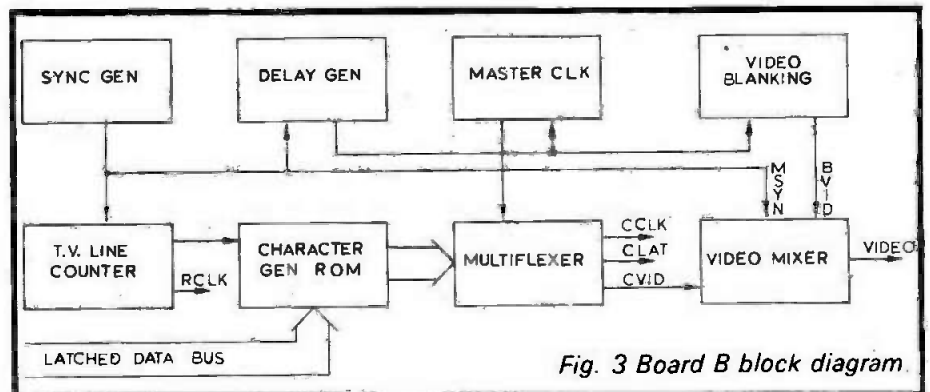


Fig. 3 Board B block diagram

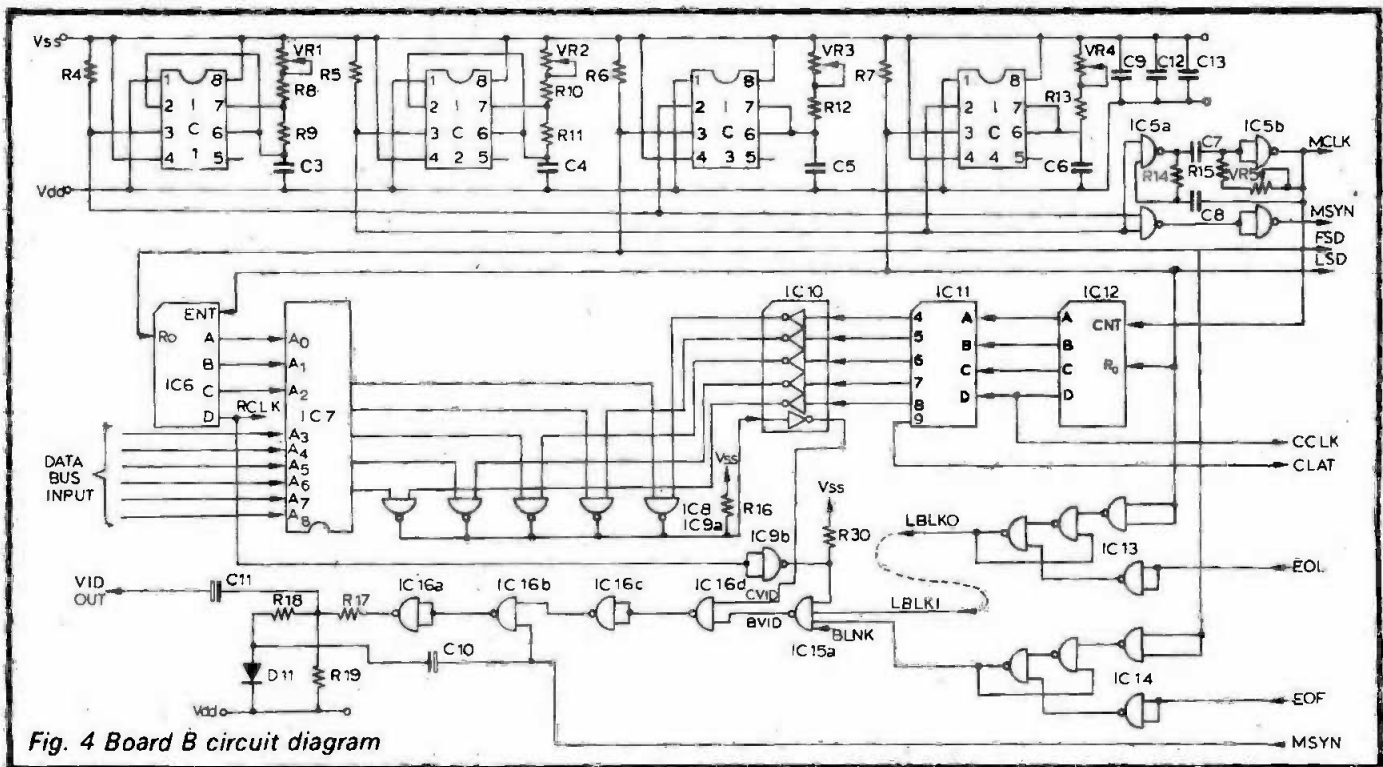


Fig. 4 Board B circuit diagram

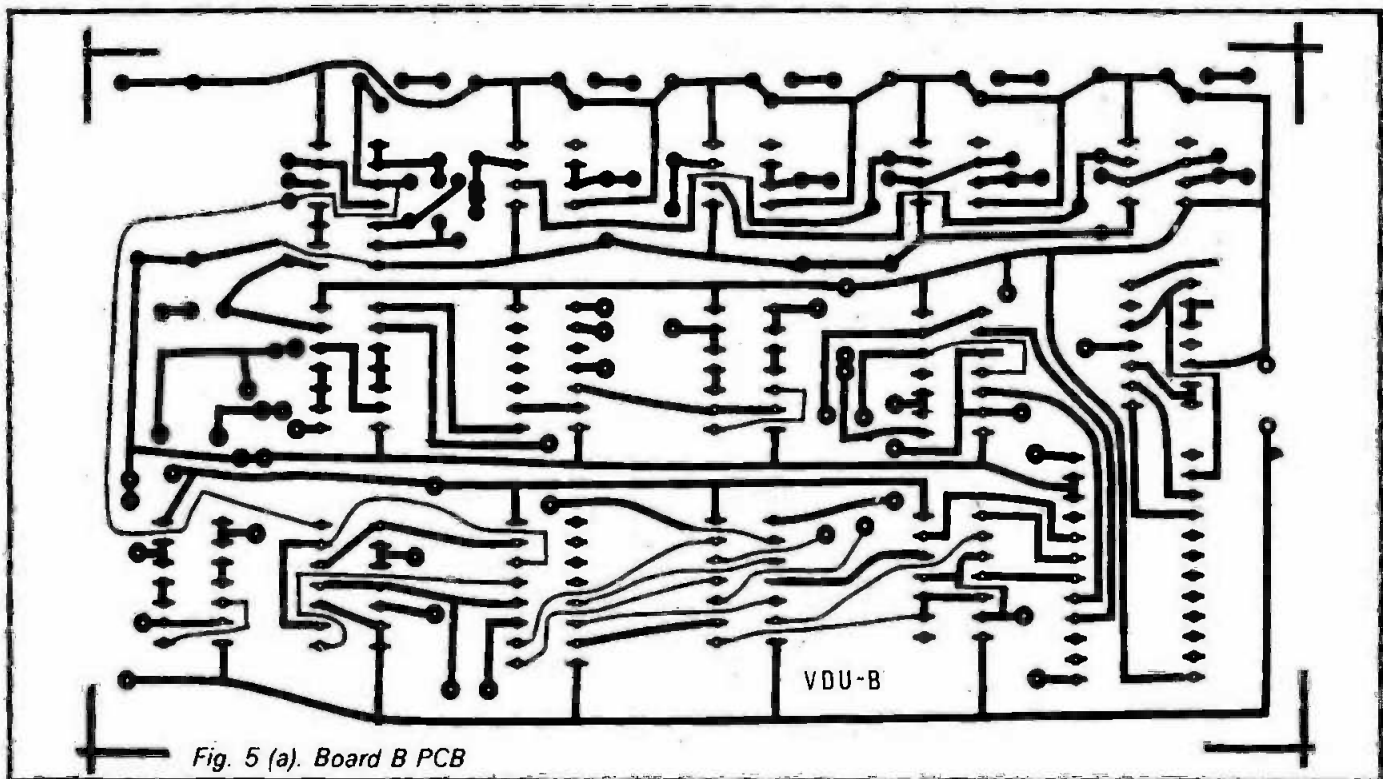


Fig. 5 (a). Board B PCB

become a character row. Adjust VR3 until the first of these rows is about two inches from the top of the screen and then adjust VR4 until the lines start about one inch from the lefthand side of the screen. If you do not have access to an oscilloscope then the TV screen can now be used to test out each part of construction. DISCONNECT POWER SUPPLY AND CONNECTION TO TV BEFORE SOLDERING EACH TIME.

ICS 8-12 can now be mounted and the supply and TV reconnected.

This should now show each white row now split up into white boxes. You may also have white vertical lines the same width as the boxes above the FSD line; do not worry about this at this stage. Count the boxes from the left and adjust VR5 until you have about 34-35 boxes across each row. When the EOL and EOF signals are connected from board "C" the boxes will be blanked after number 32 and the rows will be blanked after number 8, thus giving our display "box".

Disconnect, install IC7 with its

power supplies (note MOS handling precautions) and reconnect supply and TV. Assuming that all of the 6 data input lines to IC7 are open circuit each character box will show either an "at" sign "@" or a question mark "?" or a mix of both. The inputs may pick up stray 50Hz radiation and swap between all high ("??") and all low ("@@"). When you have become bored with watching it you can celebrate being about half-way to completion.

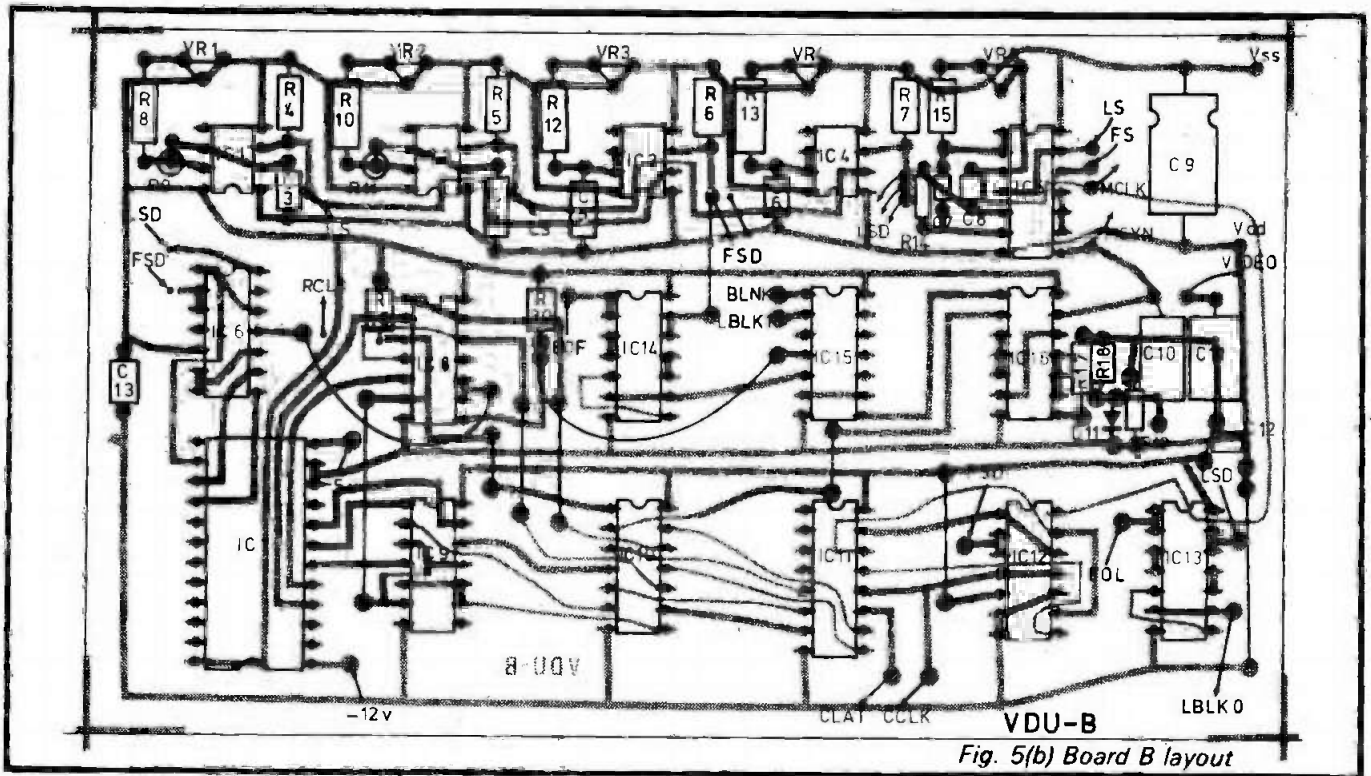


Fig. 5(b) Board B layout

### BOARD 'C'

A block diagram of board "C" is shown as Fig 6; assembly is almost as simple as it looks.

Start by inserting ICs 17-19 and connecting CCLK, RCLK, FSD and LSD from board "B" and EOF and EOL back to board "B". The results on the screen should now be that we have finished defining our display box of 32 characters wide by 8 rows high with flip-flops IC13-14 now working correctly by blanking any video generated outside our box.

### ADDRESS COMPARATOR

Any positive true logic address input from switches or other logic input to IC20-21 will be inverted by these ICs if ENABLE is connected to logic "1"; if ENABLE is at logic "0" then this will cause all 8 outputs to go high thus almost effectively disabling the address inputs. The Enable signal is not used in the basic unit and should be connected to a permanent logic "1" or via a 1K resistor to Vss. If we consider output "C" from IC19 and the inverted H input address line we can look at the expected output from the 7486 to which they are connected. A 7486 is an EXCLUSIVE NOR gate and the logic of EX-OR is a logic "1" if either *but not both* inputs are at logic "1", the output "1" is inverted to logic "0" because this is an EX-NOR gate not EX-OR. Thus we will get a logic "1" whenever either 19C is low and H is high (H low) or if 19C is high and H is low

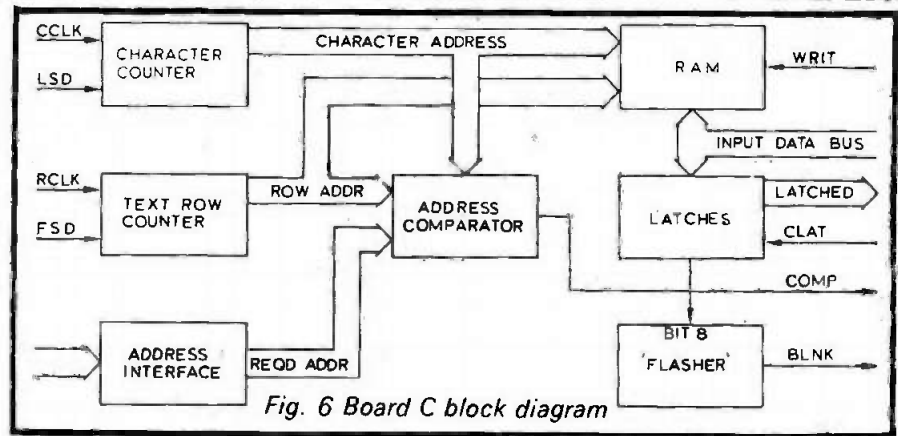


Fig. 6 Board C block diagram

(H high), or in plain language we get a logic "1" if 19C is the same logic level as input H and a "0" if they are different. Each 7486 output can be checked by leaving A-H inputs high and linking each 7486 output in turn to BLNK input to IC15. The results should be as follows: 19C-H output should be high during text rows 5-8 and low during 1-4. As a low input to BLNK will turn off the display we would expect text rows 1-4 to be turned off, 19C will be the inverse of this and thus the 19C input to the 7486 connected to BLNK will turn off rows 5-8 and the 7486 output will turn off rows 1-4. Similarly, counter output 19B will extinguish rows 3, 4, 7, 8, and 19A will turn off rows 2, 4, 6, 8. The outputs from counters 17-18 will blank columns rather than rows with 18A blanking columns 17-32, 17D blanking 9-16 and 25-32, 17C blanking groups of 4, 17B blanking groups of 2 and 17A blanking every alternate

column. The outputs from the 7486s are the inverse of the above signals and would thus cause the opposite effects.

The output from IC30 will only go low when all inputs are high and this condition only occurs when the counter outputs have the same value as the A-H address inputs, i.e. when both are addressing the same box on the screen. If the output from IC30 is temporarily connected to BLNK then only one box will be blanked off, if the address inputs are still all high then this will be the box in the bottom right corner. Check other settings of A-H input switches to ensure that the box which you think you should be addressing is the one which is then blanked.

### ADDING THE RAM

THE MM2112 is a MOS RAM containing 1024 (called 1K) bits. Each bit can be a '1' or a '0' and on turn-on will be mixed randomly; a bit can set to the desired value by

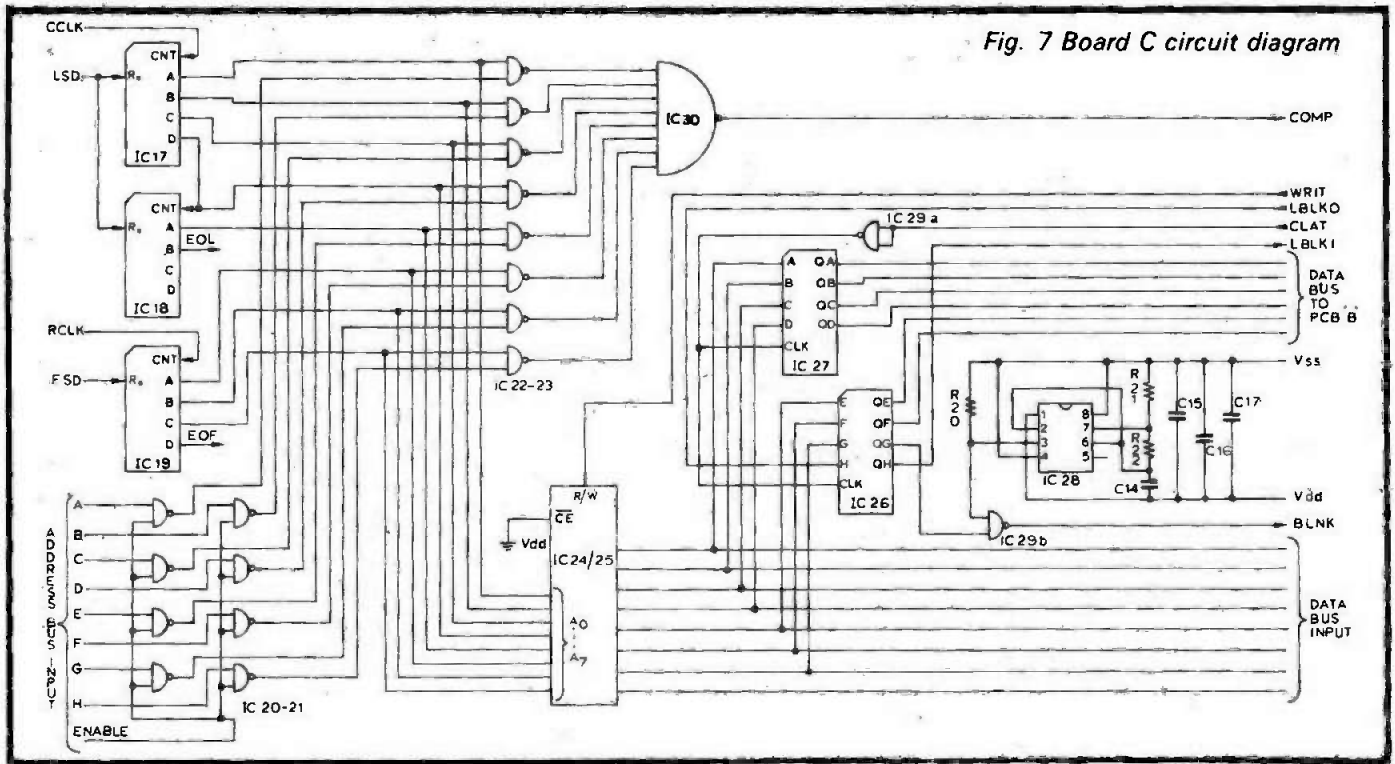


Fig. 7 Board C circuit diagram

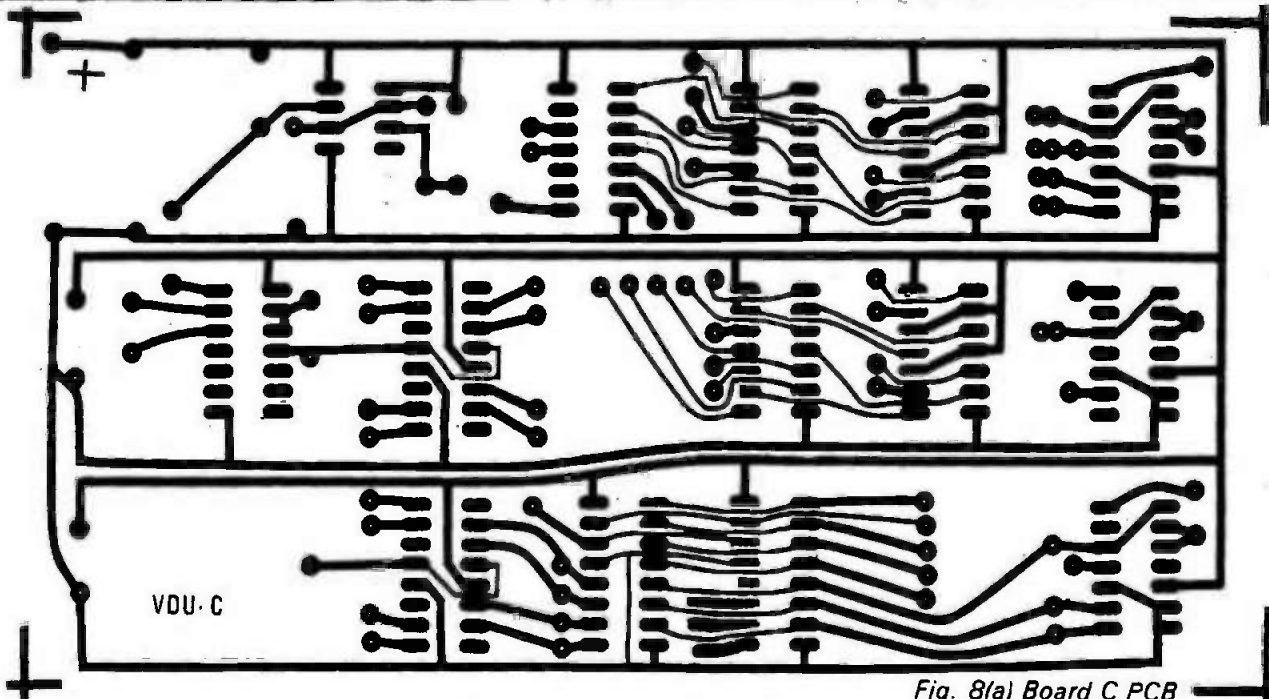


Fig. 8(a) Board C PCB

uniquely addressing that bit, setting up the required data (1 or 0) at the data I/O pin and putting a low onto the R/W pin, preferably in that sequence. Although our RAM contains 1024 bits they are organised internally as 256 words each of 4 bits in each RAM, we have two RAM chips and thus we have a choice of 512 x 4 or 256 x 8 organisation depending on a serial or parallel connection, we need words with at least 6 bits for ASC11 and thus we have chosen the 256 words of 8 bits organisation.

Ignore the concept of writing to the RAM at present and assume that the random pattern inside the RAM at switch-on is the required

display output. As each display box is addressed by ICs 17-19 so the word is also selected in the RAM and the appropriate data produced at the RAM I/O pins, six bits of this RAM word are the ASC11 code to be passed to the 2513 ROM. Now we come up against one of the problems of working with MOS devices — speed. The RAM takes at least 650nS to find the required word and present it at the I/O pins but in the meantime the data from the previously addressed word is still at the I/O pins. If we consider the reaction time of the TTL counters to be about 50nS before the data is available for that box. If we displayed the data straight from

the RAM then the character would appear to change halfway through each box. First of all we tried to fool the system by starting to display the data during the latter half of each box plus space time by using the upper 5 outputs of the 7442 rather than the lower 5. This would have given us a space 5 units wide and then a character 5 units wide. Unfortunately the RAM data appeared to change at about the 6th or 7th unit and so the first one or two units of our character box were always wrong.

If we latch the RAM outputs at a time when we know that they have settled to their new values then we can use the latched data to pass to


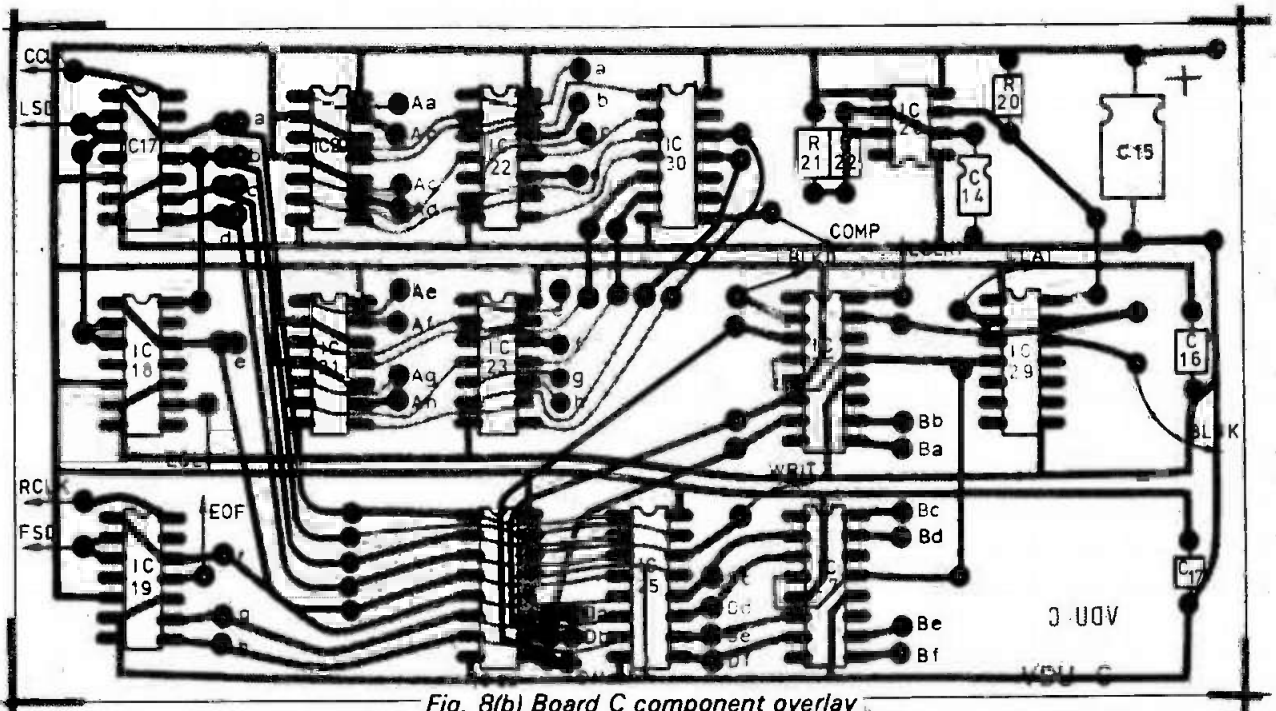
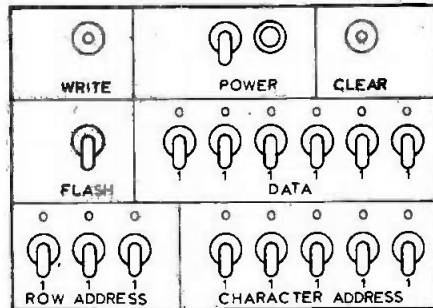


Fig. 8(b) Board C component overlay

the ROM. In our system we have decided to latch with 7442 output 9 and use 4-8 (or any other group of 5) outputs to generate our character. If we consider the first characters in each text row we can expect that box 1 will start with rubbish and then change to the desired character halfway through. At the end of box 1 the data for the first character will be latched to the ROM and thus box 2 will show the first character correctly, char 2 will be latched at the end of box 2 and displayed in box 3, etc. This means that we will have a rubbish box at the start of each row and that char 32 will be blanked because it is in box 33 and box 33 is blanked by the LSD/EOL flip-flop. If we delay the action of this flip-flop until the end of box 1 and the end of box 33 then box 1 will be enabled. We can use the same latch pulse (7442 output 9) to do this causing 9/10ths of box 1 to be blanked by LSD and the last 1/10th of box 33 to be blanked by EOL; as the last 1/10th of every box is always blank anyway (only 4-8 are used) this will have the effect of moving our complete display area about 1/4 inch to the right. As we are only using 6 or 7 of the bits we thus have a spare latch in one of the 7475's which we can use to latch the flip-flop. Disconnect the temporary link on board 'B' between LBLKO and LBLKI and connect these points to the spare input and output of IC26. We are only using 6 RAM bits and 7 latch bits at present and thus we have at least one spare. It was decided to use this bit to define that the displayed data should flash on and off to thus bring attention to any important parts of the message. A 555 timer — IC28 — is set up to

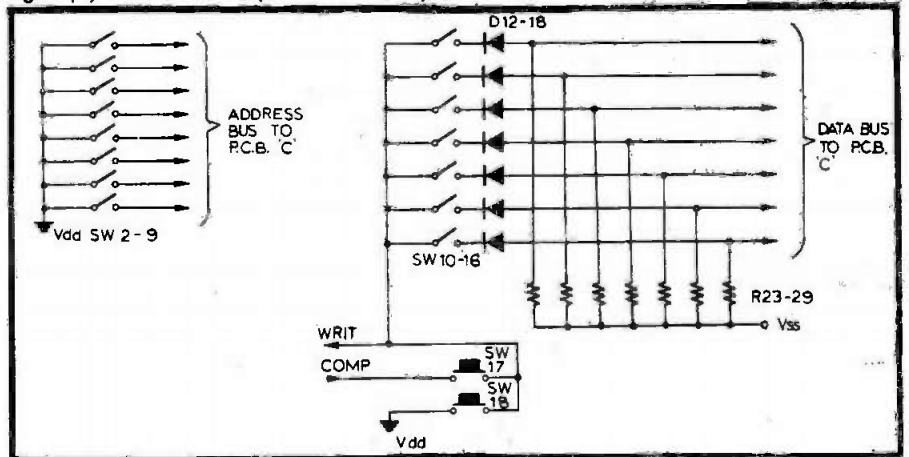

oscillate at about 1Hz, the output from this is enabled by latched bit 7 and the resulting signal passed to BLNK. If bit 7 is a logical '1' then the appropriate character will be blanked whenever the 555 output is high which is for about half a second every second; if bit 7 is low then the BLNK signal will always be high and thus the character will not flash.

### WRITING TO THE VDU

We now have a system which will display any of 128 different characters (64 steady and 64 flashing) in any of 256 possible boxes on our screen. What we need to know is how to write data into the RAM in order to get it displayed on the

screen. As we mentioned earlier a low at the R/W input of the RAMs will cause the data at the I/O pins to be placed in the memory location addressed at the same time. Thus if we set up a data word on the input data bus we can write that data into every position of the RAM by holding R/W low for a time in excess of the complete cycle time, as a complete cycle takes less than 1/50th second we can connect a push-on release-off switch between R/W and Vdd. If the data set up is ASCII '100000' our switch will load ASCII spaces into all positions of the RAM and thus the screen will be cleared of all other characters except spaces, for this reason this switch is called 'CLEAR.' Note that CLEAR will load all positions with the data set up. This data will usually be ASCII space but could be any other (all ' ' looks very pretty).

Referring to Fig 9 the CLEAR switch can be seen as SW18 connecting writ. (which goes to R/W) to Vdd. This switch also connects a low from Vdd to the common of the data switches (and

INTEGRATED CIRCUITS				RESISTORS				CAPACITORS			
IC1-4	555	IC16	7400	VR1	100k vertical preset			C1	2000µF 25V electrolytic	C7-8	150F
IC5	7400	IC17-19	7493	VR2	22k vertical preset			C2	470µF 25V electrolytic	C9-11	100F 16V electrolytic
IC6	7490	IC20-21	7400	VR3	22k vertical preset			C3	0.1µF	C12-13	0.47µF ceramic
IC7	2513	IC22-23	7486	VR4	10k vertical preset			C4	2200F	C14	4.7µF 16V electrolytic
IC8-9	7403	IC24-25	2112-2	VRF	1kΩ vertical preset			C5	0.1µF	C15	100µF 16V electrolytic
IC10	7404	IC26-27	7475			R1-3	1k	R15	490R	C16-17	0.47µF ceramic
IC11	7442	IC28	555	R4-7	4k7	R16	1k				
IC12	7490	IC29	7400	R8	220k	R17	390R				
IC13-14	7400	IC30	7430	R9	22k	R18	470R				
IC15	7421	REG1	LM309	R10	15k	R19	390R				
				R11	2k	R20	4				
				R12	33k	R21	22k				
				R13	3k3	R22	33k				
				R14	470R	R23-30	1k				

DIODES		MISCELLANY	
LED1	TIL209 or similar	PCBs	ETI 560A, 560B, 560C
D1-8	1N4001 or similar	CASE	Type WE1 (Wattford Electronics)
D9	12V Zener, 400mW	Transformer	T1 0-12v, 0-12V, 1A
D10	5V Zener, 400mW	FUSE	F1 250mA (4-holder)
D11-18	1N914 or similar.	SW1	Mains toggle switch
		SW12	Miniature toggle switch
		SW17	Miniature push-to-make

the flash switch if connected). Each switch is diode blocked from its neighbours and held high by a resistor if not connected to the common Vdd by the switch being closed, thus the data bus (6 or 7 lines) will reflect the open or closed position of the switches if the common line is low. If the common line is open circuit then each bit in the data bus will be held high by its resistor but can be pulled low against this resistor if the RAM output for that bit is low, thus the data bus from the switches is effectively Wire-Or'd to the RAM I/O pins.

If we wish to write to a particular RAM location then we have to set up that location on our address switches and the required data on our data switches. This will have the effect of causing IC30 output

(COMP) to go low whenever the comparison between the scanned address and required address shows that the scan has reached the required box. If COMP is now connected to the data switch common then this will go low causing the switch data bus to output lows wherever a switch is closed during the time that comp is low. Similarly, if COMP is connected to WRIT then the RAM will store the data bus whenever COMP is low. Thus whenever SW17 is closed COMP will cause the active data bus to be read into the RAM whenever COMP is low, as this only happens when the required box is scanned then the data for that particular box only is changed. SW17 (WRITE) must be held closed for a minimum of 1/50th second, if it is opened during the time that

comp is low then rubbish could be written into the RAM, but as this does not happen very often and it can be corrected by pressing WRITE again we have not guarded against this occurrence.

### MODIFICATIONS

FLASH. Bits 7 and 8 can be used for other purposes than flash, eg colour generation if the TV has video inputs for RGB. Remember that bit 8 will need to be latched as is bit 7. SYNC. External sync may be used if it is split into FS and LS. A switch could be installed to give internal or external sync options. MPUs. If you wish to use the 560 VDU with a microprocessor you will need a socket to connect 8 bit address, 6-8 bit data, COMP and WRIT plus a ground (Vdd) connection. Further details next month.


# CONTINUOUS DISPLAY LCD WATCHES

## UNIQUE ALTERNATING DISPLAY FEATURE

The watch continuously displays HRS. and MINS. with MONTH, DAY and SECONDS on demand. The owner selects the feature where the HRS. and MINS. or MONTH and DAY display alternatively for 2 second intervals until owner resets to normal display. During the alternating cycle seconds are still available on demand.

- \*\*Finest American MOS technology
- \*\*Quartz accuracy.
- \*\*Multi-function:  
Hrs., Mins., Month, Day, Seconds.  
Alternating display Back-light.  
Programmed 28, 30, 31 day months.  
A.M./P.M. indication for ease of date setting
- \*\*\*All important: UK factory manufacturing and servicing facilities.

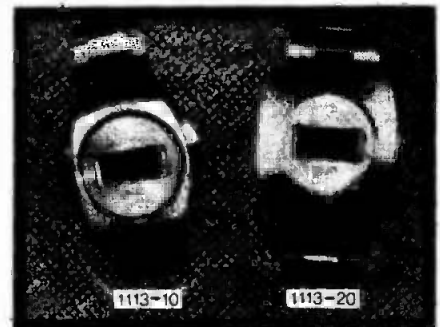Watch despatched with matching Gold plated bracelet, in presentation box with instruction booklet and guarantee. Model 1113-10 is also available in a stainless-steel bracelet.



**£34.50**

INCL. V. A. T. & P&P

**Leetronic**

Watch Division, Lee Instrumentation Ltd.  
Bedwas, Newport, Gwent NP1 8YZ  
TEL (0222) 885756-7-8. TELEX: 497084  
Reg. No. 639437. VAT Reg. No. 133 8154 80

To: Leetronic, Lee Instrumentation Ltd., Newport, Gwent NP1 8YZ  
Print — FREEPOST — no stamp required.

Please forward \_\_\_\_\_ (qty) model \_\_\_\_\_ at \_\_\_\_\_ each TOTAL: £ \_\_\_\_\_

I enclose

Name \_\_\_\_\_ cheque \_\_\_\_\_

Address \_\_\_\_\_ postal order \_\_\_\_\_

money order \_\_\_\_\_

Signed \_\_\_\_\_

Barclaycard/Access no. \_\_\_\_\_





<b>TTLS by TEXAS</b> 7400 17p 7401 18p 7402 18p 7403 18p 7404 23p 7405 25p 7406 45p 7407 38p 7408 22p 7409 22p 7410 18p 7411 26p 7412 27p 7413 36p 7414 80p 7415 34p 7417 34p 7420 18p 7421 43p 7422 24p 7423 40p 7425 33p 7427 40p 7428 39p 7430 18p 7432 30p 7437 32p 7438 32p 7440 18p 7441 78p 7442 78p 7443 118p 7444 118p 7445 80p 7446 80p 7447 81p 7448 85p 7451 18p 7453 18p 7454 18p 7460 20p 7470 32p 7472 30p 7473 34p 7474 38p 7475 45p 7476 34p 7480 84p 7481 103p 7482 78p	7483 88p 7484 103p 7485 130p 7486 32p 7489 281p 7490 43p 7491 81p 7492 48p 7493 43p 7494 81p 7495 70p 7496 84p 7497 281p 74100 118p 74104 80p 74105 60p 74107 32p 74110 55p 74118 90p 74121 32p 74122 82p 74123 73p 74126 78p 74127 81p 74136 81p 74141 80p 74145 78p 74148 175p 74150 168p 74151 77p 74153 82p 74154 164p 74155 88p 74156 88p 74180 118p 74181 118p 74182 118p 74183 118p 74164 130p 74176 131p 74177 120p 74180 120p 74181 322p 74182 88p 74185 140p 74190 168p 74191 168p 74192 130p 74193 130p 74528 130p	<b>OP. AMPS</b> 301A Ext. Comp. 8 pin DIL 40p 536T FET Op Amp TO 99 300p 708 Ext. Comp. 8/74 pin DIL 35p 741 Int. Comp. 8/14 pin DIL 28p 747 Dual 741 14 pin DIL 70p 748 Ext. Comp. 8/14 pin DIL 40p 778 Prog. Op. Amp. TO 99 180p 1458 Dual Op. Amp. 8 pin DIL 70p 3130 CMOS Op. Amp. 8 pin DIL 108p 3900 Quad Op. Amp. 14 pin DIL 60p	<b>LINEAR I.C.s</b> CA3028A DM. Cascade Amp TO99 112p CA3046 5 Transistor Array 14 pin DIL 75p CA3049 4 Lo Noise Amp 16 pin DIL 280p CA3053 DM. Cascade Amp. TO5/DIL 80p CA3089E FM IF System 16 pin DIL 250p CA3D90AQ FM Stereo Decoder OIL 500p ICL8038CC VCO Fun. Gen. 16 pin DIL 370p LM3800 2 W Audio Amp. 14 pin DIL 115p LM381N Stereo Pre Amp. 14 pin DIL 175p LM52 Rhythm Generator 16 pin DIL 1000p MC13510P FM Stereo Decoder 14 pin DIL 175p MC1351P Lum/Det. Aud. Pre amp 104p MFC4000B 1W Audio Amp. PCB 75p MFC6040 Electronic Attenuator 180p NE540L Aud. Pwr. Driver TO5 140p NE555V Timer 8 pin DIL 40p NE556 Dual 555 14 pin DIL 98p NE5618 PLL with AM Demod. 390p NE562B PLL with VCO 16 pin DIL 390p NE585 PLL 14 pin DIL 200p NE566V PLL Fun. Gen. 8 pin DIL 200p NE567V PLL Tone Decoder 8 pin DIL 200p 2567 Dual 567 16 pin DIL 400p SN72710 Diff. Comparator 14 pin DIL 54p SN72733 Video Amp. 14 pin DIL 150p SN76003N Aud. Pwr. Amp. with int. HS 175p SN76013N Aud. Pwr. Amp. with int. HS 175p SN76023N Aud. Pwr. Amp. with int. HS 175p SN76033N Aud. Pwr. Amp. with int. HS 275p TAA521A Aud. Amp. for TV 225p TAA561B FM/IF Amp. Lim/Det OIL 150p TBA641B Audio Amp. OIL 100p TBA800 5W Audio Amp. OIL 100p TBA810 7W Audio Amp. OIL 125p TBA820 20W Audio Amp. OIL 100p TDA2020 20W Audio Amp. OIL 375p XR2240 Prog. Timer/Counter 400p ZN414 TRF Radio Receiver 140p	<b>TRANSIS-TORS</b> AC125 20p AC126 18p AC127 18p AC128 16p AC176 18p AC187 18p AC187K 25p AC188 18p AC188K 25p AD149 48p AD161 38p AD162 38p AF115 18p AF116 18p AF117 18p AF199 43p AF239 48p BC107/B 10p BC108/B 10p BC109/C 11p BC147 9p BC148 9p BC149 10p BC157 11p BC158 13p BC159 13p BC169C 15p BC171 12p BC172 12p BC173 13p BC177 20p BC178 17p BC179 20p BC182 12p BC183 12p BC184 14p BC187 32p BC212 14p BC213 12p BC214 17p BC478 32p BC547 12p BC557 12p BCY70 20p BCY71 24p BD124 80p BD131 39p BD132 43p BD135 84p BD136 80p BD139 79p BD140 87p BF115 24p BF157 25p BF173 27p	BF178 30p BF194 13p BF195 11p BF196 17p BF197 19p BF200 40p BF257 34p BF258 38p BF839 37p BF840 37p BF879 37p BF880 37p BF888 37p BFX30 32p BFX84 30p BFX85 30p BFX86 30p BFX87 30p BFX88 30p BFY50 18p BFY51 16p BFY52 18p BRV39 45p BSX19 20p BSX20 20p BU105 175p BU108 312p MJE340 48p MJ2955 120p MJ2955 120p MJE171 12p MJE3055 70p MPSA06 40p MPSA12 62p MPSU06 78p MPSU56 88p OC2B 75p OC35 75p OC71 25p TIP29A 50p TIP29C 62p TIP30A 62p TIP30C 72p TIP31A 56p TIP31C 88p TIP32A 62p TIPK 88p TIP33A 97p TIP33C 120p TIP34A 124p TIP34C 180p TIP35A 243p TIP35C 290p TIP36A 287p TIP36C 360p TIP41A 70p TIP41C 81p TIP42A 78p	TIP42C 88p TIP2955 76p TIP3055 80p TIS93 30p ZTX108 11p ZTX300 18p ZTX500 18p ZTX504 60p ZNE697 22p ZNE698 32p ZNE706 22p ZNE708 22p ZNE918 43p ZNE930 19p ZNE1131 20p ZNE1132 20p ZNE1304 38p ZNE1305 38p ZNE1306 43p ZNE1613 27p ZNE1711 27p ZNE1893 32p ZNE2219 22p ZNE2222 22p ZNE2369 16p ZNE2484 32p ZNE2804A 22p ZNE2905A 22p ZNE2906 22p ZNE2026R 9p ZNE2826G 11p ZNE3053 19p ZNE3054 54p ZNE3055 84p ZNE3442 181p ZNE3702 14p ZNE3703 14p ZNE3705 14p ZNE3706 12p ZNE3708 12p ZNE3709 12p ZNE3707 14p ZNE3773 270p ZNE3866 90p ZNE3904 22p ZNE3905 25p ZNE3906 25p ZNE3907 22p ZNE4058 19p ZNE4060 19p ZNE4123 22p ZNE4124 22p ZNE4125 22p ZNE4126 22p ZNE4371 142p ZNE4348 173p ZNE4401 34p	<b>RECTIFIER</b> BY100 31p BY127 15p BY127 15p IN4001 8p IN4002 8p IN4004 7p IN4005 7p IN4007 8p	<b>BRIDGE RECTIFIERS</b> 1A 50V 25p 1A 100V 27p 1A 400V 31p 1A 600V 37p 2A 50V 37p 2A 100V 44p 2A 400V 58p 4A 100V 78p 6A 50V 78p 6A 100V 78p 6A 200V 84p 6A 400V 90p	<b>ZENER</b> 2.7 to 33V 400mW 11p 1W 22p	<b>TUNNEL</b> AEY11 78p	<b>TRIACS</b> Amp Volts 3 400 130p 6 400 182p 6 500 184p 10 400 200p 10 500 270p 15 400 310p 15 500 340p 40430 108p 40669 108p	<b>DIAC</b> BR100 25p	<b>FETs</b> BF244 45p MPF102 40p MPF103 40p MPF104 40p MPF105 40p 2N3819 27p 2N3820 20p 2N3823 54p 2N5457 40p 2N5458 40p 2N5459 40p 2N2026R 9p 3N140 82p 3N141 80p 40B03 63p 40B73 63p	<b>SCR THYRISTORS</b> 1A 50V T05 43p 1A 100V T05 45p 1A 400V T05 80p 3A 400V STUD 81p 7A 400V T05 + HS 87p 8A 50V Plastic 142p 12A 400V Plastic 173p 16A 100V Plastic 180p 16A 400V Plastic 188p 16A 600V Plastic 238p	<b>DIODES</b> 8p 10p 15p 18p 75p 8p 9p 9p 9p 9p 10p 11p 11p	<b>BJT</b> BT104 1A 700V STUD 130p C108D 4A 400V Plastic 83p MCR101 1/2A 15V T02 27p 2N3825 5A 400V T066 87p 2N4444 8A 800V Plastic 200p 2N8060 0.8A 30V T092 36p 2N8062 0.8A 100V T092 40p 2N8064 0.8A 200V T092 43p
---	--	---	---	---	---	---	--	---	---	----------------------------	--	--------------------------	--	--	--	---

VAT INCLUSIVE PRICES. Add 20p P&P — no other extras  
MAIL ORDER ONLY. Minimum Order £2  
**TECHNOMATIC LTD**  
54 Sandhurst Road, London NW9

# BINDERS

In reply to the question "Do you keep your copies of ETI for more than three months?" a staggering 98% of readers replied "Yes." This is also borne out by the enormous sales of ETI Binders since they were introduced in December . . . our original order for a year's estimated sales were sold out by February!

Our binders are a real top-quality product finished in black leather-look plastic with gold lettering and designed to hold 12 issues. Cost is £2.50 each including VAT and postage.

**ETI BINDERS,  
ETI MAGAZINE,  
36 EBURY STREET,  
LONDON SW1W 0LW.**

# TAKE AN S-DeC

## No 15 Electronic Coin Tosser

David Gibson

This device generates a random sequence of binary digits. It has the advantage over tossing a coin in that there is no possibility of cheating.

When the battery is connected the lamp will glow at half its full brightness. To electronically "toss" a coin, connect a lead between sockets 19 and 51 on your S-DeC when the state of the lamp, ON or OFF, will represent a HEAD or a TAIL.

The n-p-n/p-n-p pair (the two transistors on the right) is connected as a Unijunction transistor which oscillates at a frequency determined by the  $1\mu\text{F}$  capacitor and the resistor between sockets 48 and 53 on the S-DeC.

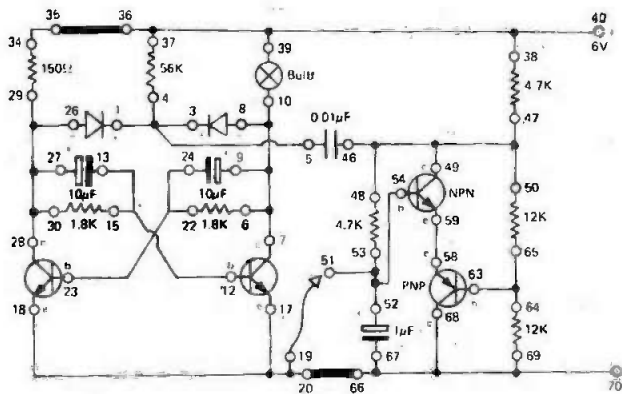


Fig. 1 Circuit diagram of Electronic Coin Tosser showing relevant hole numbers of S-DeC.

The output signal from the oscillator is made to switch a binary multivibrator, the two-transistor circuit on the left, and this in turn switches the bulb on and off. When S-DeC sockets 51 and 19 are connected, the oscillator stops and the binary freezes in the state it had immediately before stopping the oscillation.

Building circuits like this is simple if you use an S-DeC (see photograph). Component leads are plugged into the relevant numbered holes (see circuit diagram) and are automatically connected into circuit.

Beneath the holes are special sockets connected together in a pattern which is shown on the upper surface of the S-DeC. When you have finished building the Electronic Coin Tosser, simply unplug your components and use them again.

If you want to keep a circuit permanently wired, then for only a few pence you can buy a Super Solder Board. These printed circuit boards have holes and copper tracks which exactly match those on the S-DeC. To preserve your circuit, simply transfer the components from the S-DeC to exactly the same matching holes on the Super Solder Board and solder a permanent circuit. Holes on both S-DeC and Super Solder Board have the same letter/number marking. Making mistakes is almost impossible.

When you have built your Electronic Coin Tosser you can build other exciting projects on your S-DeC. Many of the circuits featured in the popular electronics construction journals can be built on your S-DeC. In addition, P.B. Electronics has written a special projects handbook for the S-DeC experimenter. The book contains 48 different projects to build. These include record player amplifiers, emotion meter, radio jammer, electronic tug-of-war, strength meter, radio microphone and dozens of others – and you can build every one on your S-DeC.


The S-DeC costs only £1.98 plus 37p post, packing and VAT. It also includes a booklet giving 9 S-DeC circuits you can build.



Please rush me ..... S-DeC's at £1.98 plus 37p p. & p. and VAT each.  
I enclose a postal order/cheque for .....

Name .....

Address .....

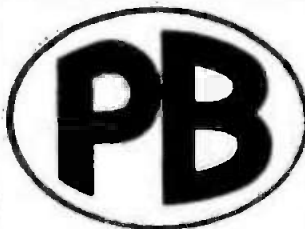


**P.B. ELECTRONICS (SCOTLAND) LTD.**

57 HIGH STREET • SAFFRON WALDEN • ESSEX CB10 1AA • ENGLAND
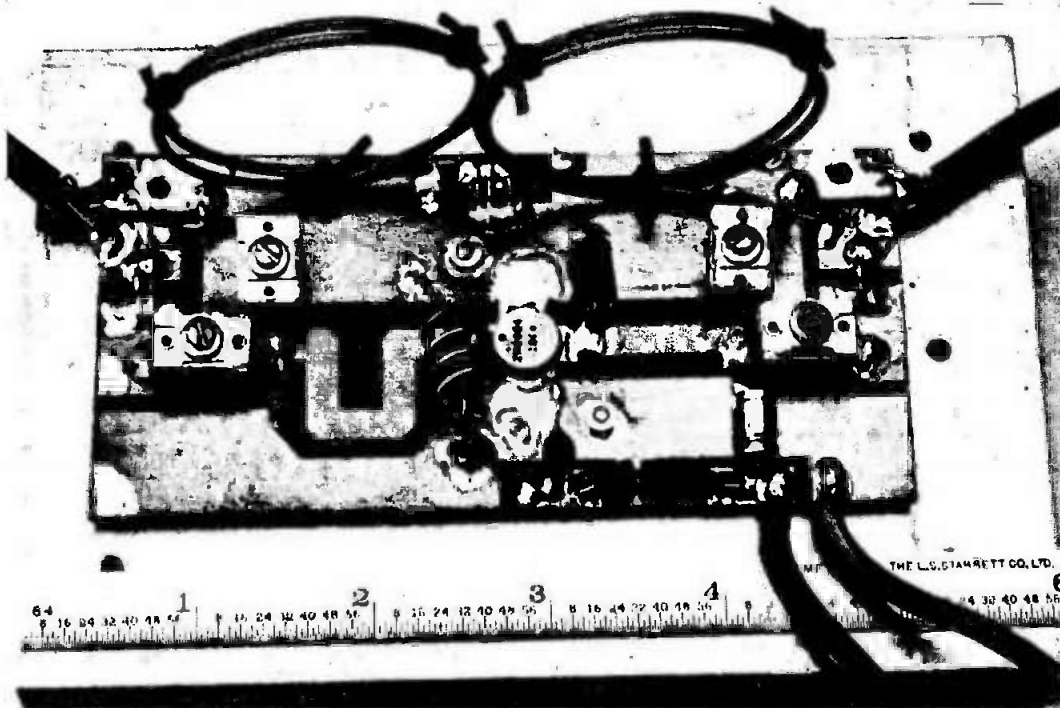
# 2m POWER AMP

Most mobile two metre transceivers are limited to about ten watts output. This RF power amplifier boosts output to 45 watts



**Project**  
**710**

Fig. 1. The 45W, two metre RF power amplifier. The 2N6084 transistor is visible in the centre of the p.c. board. The mica compression trimmers located on the right hand side are for tuning the input, those on the left for tuning the output. The printed inductances are readily visible. The two quarter wave coax lines are visible at the top. They may be coiled up as shown or conveniently arranged in some other way. Note that the components are soldered on the copper side of the printed circuit board.

ONE OF THE MOST POPULAR amateur radio activities these days is FM mobile operation on the two-metre band. The use of FM, particularly mobile, has a number of advantages. It reduces the effects of impulse noise interference, mostly generated by car ignition systems and provides clear, largely noise-free communications. But mobile operation has its problems such as flutter caused by surrounding buildings and terrain, and the relatively low gain of mobile antenna systems.



The majority of mobile transceivers, such as those made by Icom, Yaesu, Trio etc, produce about 10W output power. They also have pretty 'hot' receivers, which means that output power and receiver sensitivity are not 'matched' and you can hear higher power stations or repeaters over much greater distances than they can copy you. Simple solution: an RF power amplifier to boost your output power.

When considering the pocket, or how much a suitable power amplifier would cost, a good rule of thumb is 'less than 70p per watt'. Thus, one needs to consider a single transistor. This must have adequate gain and be able to accept an input power in the range of 8 to 12 watts. There are a number of suitable transistors that commence at this level and will produce output powers in the range of 25 to 50 watts or more from a power supply rail of 12V. Those transistors producing output powers over 50 watts from the 10 to 12 watt price level become more expensive on a per-watt basis than those transistors producing output powers below 50 watts. The higher power transistors require a substantially larger heat-sink also — increasing size and cost considerations. As most of the popularly used commercial transceivers — and many homebrew ones, are quite small physically, the size of the power amplifier is also a consideration.

Apart from cost, availability of suitable transistors and other components is a necessary consideration. The 2N6084 transistor fits all our requirements very well. The data sheet on this transistor indicates a power input of between 8 watts and 12 watts at a supply voltage of 12.6 volts. The manufacturers claim that the transistor will withstand severe mismatch under operating conditions. A graph of power output versus power input (i.e.: drive power) is given in Fig 2 along with a table of typical performance and base input — collector output impedances.

Having chosen the device, an appropriate circuit, suitable for a kit or simple home construction was necessary. The current ARRL VHF Handbook describes a circuit that works very well, but has a number of drawbacks, local availability of some of the components in particular. It was also felt that the design could be simplified with a consequent reduction in components and

# 2m POWER AMP

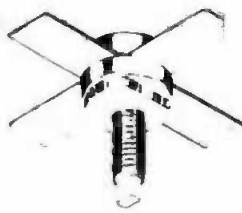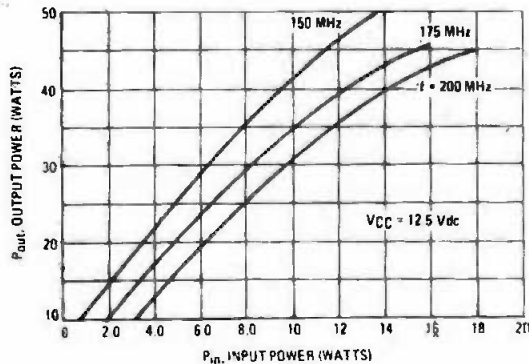

Physical construction of 2N6084

$f_o = 175 \text{ MHz}, V_{CC} = 12.5 \text{ VOLTS}$			
$P_{IN}$ WATTS	$P_{OUT}$ WATTS	INPUT OHMS	OUTPUT OHMS
4	21.7	$0.8 - j 1.1$	$2.2 - j 0.3$
8	37.1	$0.8 - j 1.3$	$1.7 - j 0.5$
10	40	$0.8 - j 1.45$	$1.65 - j 0.4$
12	46.5	$0.8 - j 1.6$	$1.6 - j 0.3$

Fig. 2. Power output Vs power input for 2N6084.

Fig. 2(b). Input and output impedances vs power for 2N6084.

cost. Another drawback was the problem of an antenna changeover relay. To cope with this level of power and have adequate isolation between the transmitter output and receiver input contacts a coaxial changeover relay is necessary. These items are not on everybody's shelf and generally cost in excess of £10 over the counter. Very off-putting.

## DIODE AND COAXIAL LINE SWITCHING

Quarter wave coaxial lines and diodes are now being successfully used for this purpose however — and several articles describing the technique have recently been published in amateur radio publications. The method is simple, cheap and very effective. The circuit is shown in Fig 4 and works as follows:

During the receive condition, all the diodes are non-conducting and thus present a high resistance to the signal coming from the antenna. Thus, no signal is dissipated in the amplifier input or output circuits. The two diodes from the centre point present a high impedance across the coax line and thus have no effect on incoming signals from the antenna. Thus the signals travel through the two quarter-wave coax lines to the antenna input of the receiver without loss. When the transmitter is operated, all diodes conduct. The diodes at the centre point will conduct and since a quarter-wave line shorted at one end presents an open circuit at the other end, each quarter wave line will present a high impedance at the input and output terminals respectively. The diodes between the input terminal and the power amplifier stage input will conduct and pass

the driving power. The diodes between the power amplifier and the output terminal will likewise conduct, passing the output of the amplifier to the output terminal. The output power cannot return to the input as the two diodes from the centre point of the coax lines will conduct, shorting the quarter-wave line and presenting a high impedance at the output terminal. Happily, the impedance of the quarter-wave coax lines is immaterial and anything suitable may be used. However, their lengths must be an accurate quarter wavelength electrically taking into account the velocity factor of the cable. In developing this project, some trouble was experienced in this respect — so make sure you have the right length. It appears that the velocity factor of ordinary, run-of-the-mill, garden variety RG58/U coax, obtainable from most suppliers varies considerably in its velocity factor, even over relatively short lengths. You can use this type of coax but a lot of pruning and turning will be required. If a cable

manufactured to tighter tolerances in velocity factor is used, this problem disappears. It is suggested that cables such as RG59B/U (or C/U) or RG223/U, which are nominally 5 mm diameter be used. Alternatively, a 2.5 mm diameter cable such as RG174/U may be used. All these cables have a velocity factor of 0.665 and have been found to be consistent in practice. They must, however, be accurately cut to the lengths specified, as detailed later.

Some trouble was also experienced with a commonly available 2.5mm diameter cable of unknown type number, so be wary.

## THE POWER AMPLIFIER CIRCUIT

The circuit is illustrated in Fig 4. Inductances L1 and L2 are actually rectangular, 5.5 mm wide strips, on the printed circuit board. They are not microstripline sections which would require a double-sided printed circuit board so single-sided p.c. board is used in this project.

Turning capacitors, C4, C5, C6, C7 are all mica compression trim-

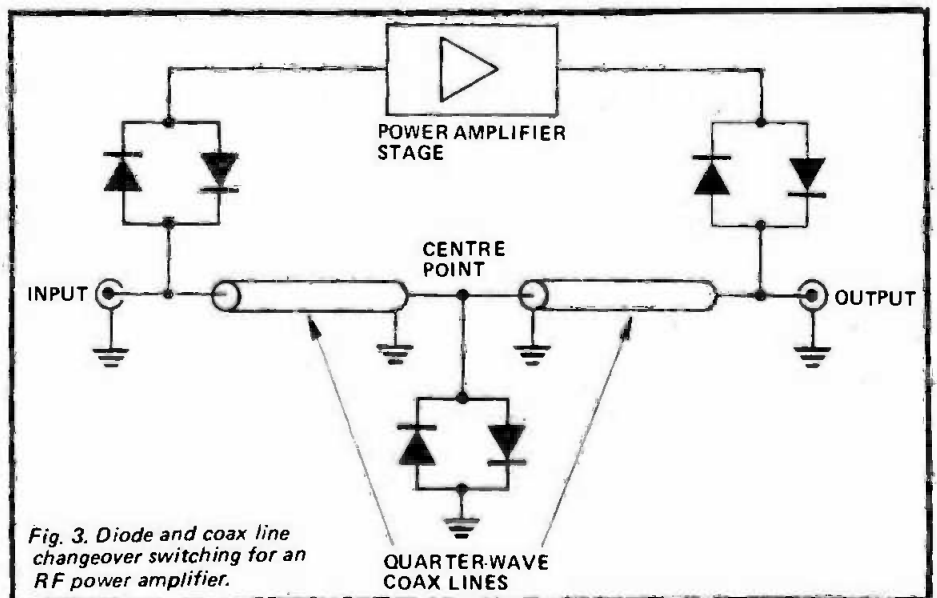


Fig. 3. Diode and coax line changeover switching for an RF power amplifier.

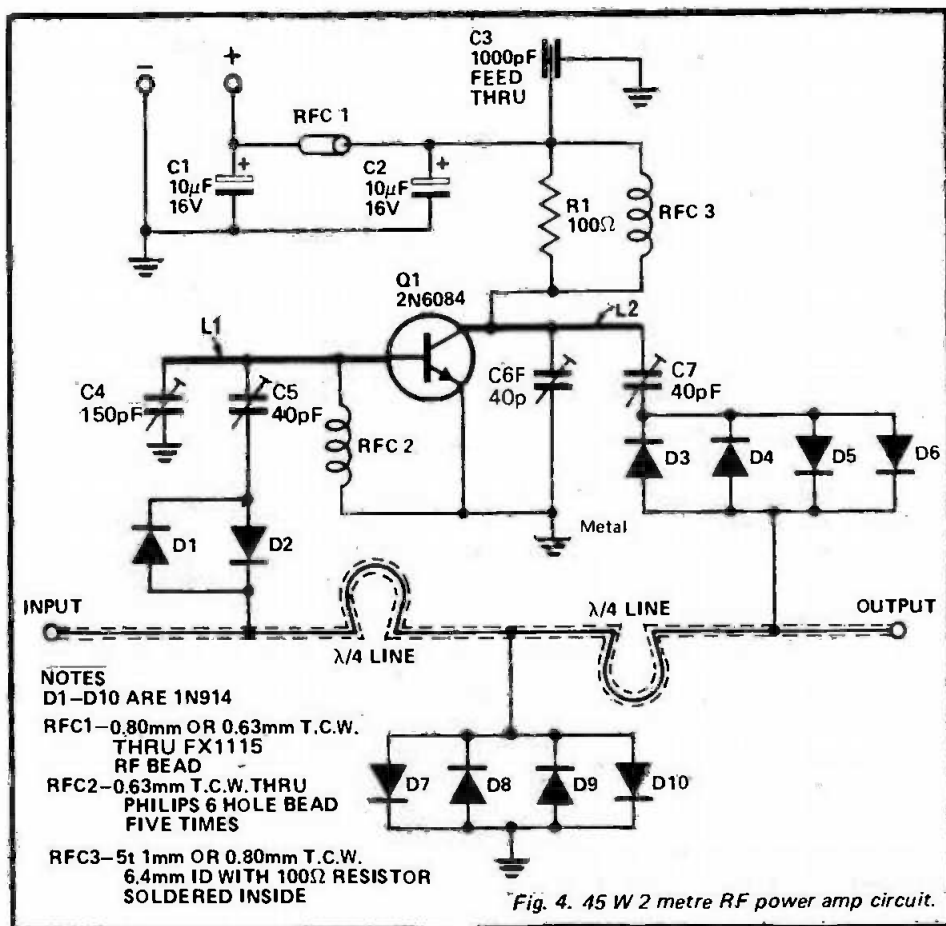


Fig. 4. 45 W 2 metre RF power amp circuit.

mers mounted on a ceramic base and are readily seen in Fig 1.

The dc return for the transistor base circuit is via an RF choke, RFC2, visible just to the right of the transistor in Fig 1. This consists of a number of turns of tinned or enamelled copper wire passed through the holes of a six-hole ferrite bead. This makes a low resistance, high inductance RF choke. Some published circuits specify the use of a low value resistor, or two resistors in parallel, in place of an RF choke in this part of the circuit. However, this is not recommended as the available power output is considerably reduced.

The transistor collector is shunt fed from the supply via RFC3. This is simply five turns of tinned or enamelled copper wire of a suitable heavy gauge, anything between 20SWG and 26SWG is adequate, with a low value resistor mounted inside to dampen it and lower the Q. A resistor value between 47 ohms and 180 ohms is quite satisfactory. The supply end of RFC3 is decoupled for RF by a 1000 pF feedthrough capacitor used as a standoff and tie point.

As the low frequency gain of the 2N6084 is quite high, the supply is also decoupled by several large value electrolytic capacitors, C1 and C2. The latter is a 10uF/35 V

tantalum. The supply input is decoupled by C1 and RFC1. C1 is a 10uF electrolytic. RFC1 is an FX1115 ferrite bead, slipped over a 22 mm length of tinned copper wire. The gauge of wire is largely immaterial. Anything between 22SWG and 26SWG is quite satisfactory.

The diode switching requires a total of ten diodes. These may be 1N914 (1N418) or 1N916 types, although these were found to be only barely adequate for the job. They do get quite hot to the touch after only a few minutes operation. More suitable types would be the Philips type BAX13, or even better still — BAV10. These latter ones are recommended. Despite the heating problem, no failures have been experienced with 1N914 diodes. However, if you have a predilection for holding long 'overs', then use the recommended types for added safety. Absolute minimum lead length possible must be used when soldering them into position.

The input and output tuned circuits, consisting of L1-C4-C5 and L2-C6-C7 respectively, are designed to match the transistor base input and collector output impedances, at the required input and output power levels, to about 50 ohms. C5-C4 and C7-C6 form capacitive dividers. From the table included with Fig 1, it is

obvious that the transistor impedances vary with power level. Thus the amplifier should be tuned up at the power level at which it is intended to be used. There is sufficient range in the tuning capacitors to accommodate a range of input power levels.

The 2N6084 is encased in the MT-72 stripline package, having two emitter leads. The collector lead has one corner removed — see the illustration of the package in Fig 2. The collector lead is also marked by a dot on the header as can be seen in Fig 1 & 6. The threaded stud is electrically isolated from the transistor leads. This sort of package construction reduces lead inductance and allows the stud to be bolted directly in contact with a heatsink for maximum heat transfer. The 2N6084 is manufactured by both Motorola and Solid State Scientific (SSS).

## HEATSINK REQUIREMENTS

A heatsink is required to dissipate at least 45 watts of heat with a low temperature rise. As operation is of an intermittent nature, with relatively long intervals between on periods, heatsink requirements can be relaxed somewhat. A 150 mm length of 100 mm wide heatsink having fins on one side only (fins about 25 mm deep) as can be seen in Fig 1, was found to be quite adequate. A diecast box having dimensions somewhat larger than the pc board could be used but its heatsinking properties would be barely adequate and amplifier on times would have to be kept short. A proper heatsink is recommended. The heatsink illustrated was obtained un-anodised. A black anodised heatsink would certainly do a better job. However, it is good practice to sand off the anodising in the immediate vicinity of the transistor stud, where it contacts the heatsinks.

## CONSTRUCTION

The amplifier is constructed on a single-sided printed circuit board, 120 mm long by 58 mm wide, the board layout being given in Fig. 5. The component layout is illustrated in Fig. 6, and one can get a good idea of the component layout also from Fig. 4. Note that all the components are mounted on the copper side of the board, contrary to common practice adopted with most other circuits constructed on pc board.

If you have facilities for making your own pc board, construction

# 2m POWER AMP

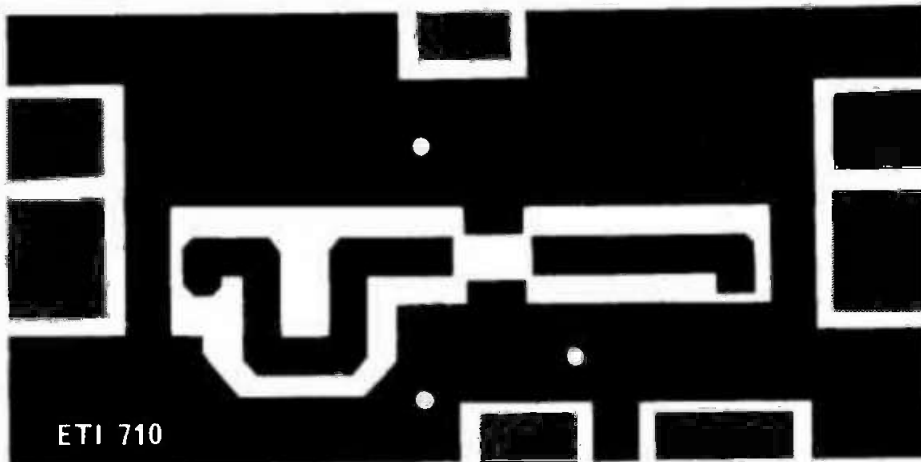


Fig. 5. Printed circuit board layout, copper side.

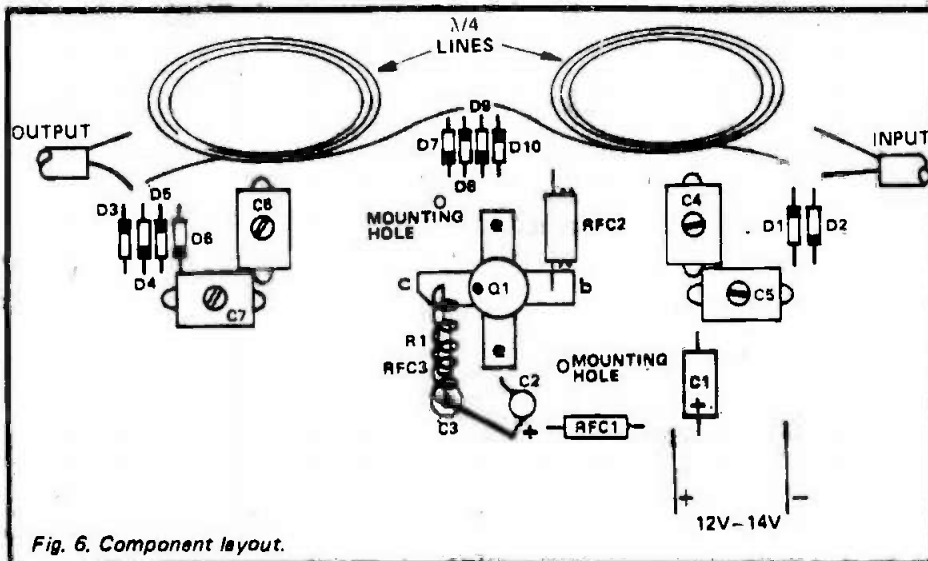


Fig. 6. Component layout.

should commence by first making the board. Although the board is of very simple design, it should preferably be made by one of the etching processes. Do not attempt to make the pc board by cutting away the unrequired copper. This usually results in: (a) a board that looks grotty and (b) a project that either does not work at all or does not work satisfactorily.

Commence by drilling the transistor mounting hole in the pc board using a 9.5 mm (3/8in) drill. File it out slightly with a small round file so that the transistor header is a loose fit through the board. Next drill the two mounting holes, which are positioned diagonally opposite each other either side of the transistor, and the 100pF feedthrough capacitor mounting hole. Use a 3.2 mm (1/8in) diameter drill. A clearance hole of about 4.5 mm to 5 mm diameter (3/16in) will need to be drilled in the heatsink

beneath the position of this capacitor.

Now place the pc board centrally over the heatsink to be used and mark the positions of the transistor mounting hole, the feedthrough capacitor clearance hole, and the two mounting holes. Drill the heatsink using a 4.5 mm drill (3/16in) as this is a good

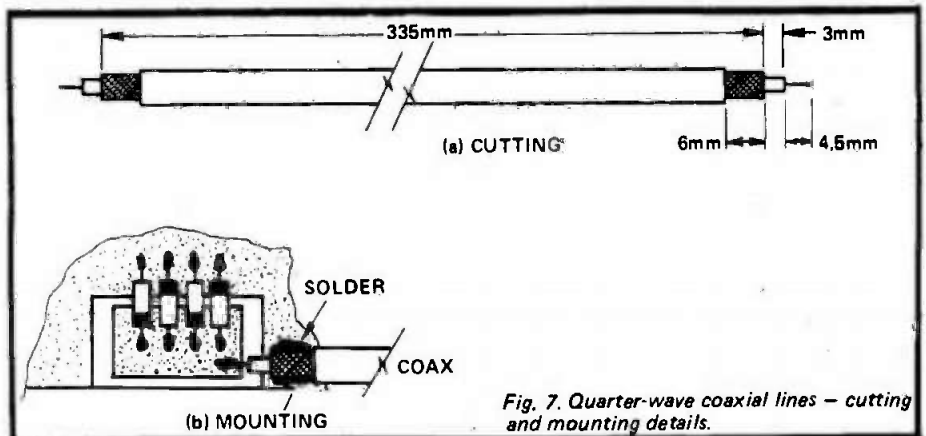


Fig. 7. Quarter-wave coaxial lines - cutting and mounting details.

clearance size for the American 4-40 threaded stud on the 2N6084. Then drill clearance holes in the heatsink for the mounting bolts and the feedthrough capacitor.

Once the pc board and heatsink have been drilled and the hole positions checked to see that everything fits correctly without strain, the pc board may be wired.

Commence by mounting the mica compression trimmers, C4, C5, C6, C7. Refer to the layout in Fig. 6. The trimmer capacitors are constructed with large lugs, formed of the capacitor plates, that project more or less straight down from the ceramic body of the component. Carefully bend the end of each lug out at right angles before soldering the capacitor in place. Use a hot soldering iron with a large tip and solder rapidly, making sure that the solder is adequately melted to ensure proper wetting of the joint. It is advantageous to lightly tin the lugs before soldering. A temperature-controlled iron, such as the Weller, with an appropriate tip, is recommended.

Next slip a 22 mm or 25 mm length of 24 or 26SWG tinned copper wire through the Neosid type 159 x 059 x 375/F8 RF bead, making RFC1, and solder it into place as shown in Fig. 6. Now mount C1, C2 and C3. Cut the lead of the feedthrough capacitor (C3) flush with the body of the component on the back (heatsink) side of the board, as shown in Fig. 7.

When mounting C1 and C2 ensure that the proper polarity is observed. If C2 is connected to reverse it goes up in flames when the power is applied. It may damage C1 as well.

Mount all the switching diodes using an absolute minimum of lead length. Check that they are correctly oriented.

Before mounting the 2N6084, cut the base and collector leads to about 6 mm (1/4") length. This should be done with care so as not to damage the rather soft leads. A

Fig. 8a. Mounting feedback capacitor C3.


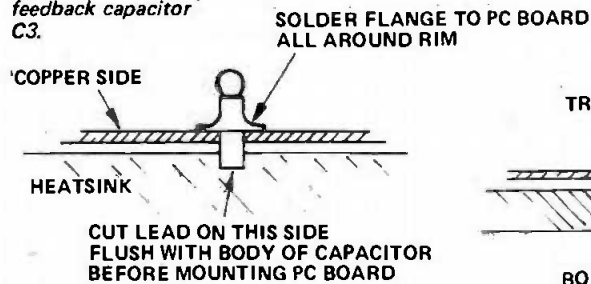


Fig. 8b. How the 2N6084 is mounted.

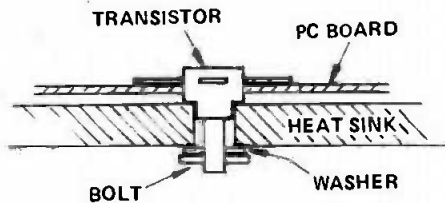

pair of sharp, ordinary household scissors is a good tool for the job. On the premises that what people don't know won't hurt them, turn your back when you do this little job or else do it at some suitable hour in the dead of night so that the prime user/owner of the scissors doesn't see what you are doing. It avoids complications such as black eyes and minor stab wounds. Reasoned arguments such as the softness of the metal tend to go unheeded.

Straighten the leads carefully if necessary, so that they run straight out from the transistor header without any kinks. Place the transistor on the board and see that the leads sit flush on the board right up to the transistor header. Orient the transistor as shown in Fig 6. Carefully solder it into position, flowing the solder near to the 2N6084 case. Use a hot iron and ensure that proper wetting of the joints occurs.

Next wind RFC2 and RFC3. RFC2 requires a length of 26 SWG tinned copper wire about 100 mm long. Thread it through the six-hole Philips ferrite head five times. Solder it into position from the base of the transistor to the ground plane as shown in Fig 6. Keep the leads short. RFC3 requires a 100 mm length of 18 or 20 gauge B & S tinned copper (enamelled copper wire is also suitable). Wind five turns around the shank of a 6 mm (1/4") diameter drill or other suitable former and then slip it off. Cut the leads to a suitable length, 5 mm to 7 mm is adequate, and then stretch the coil to a length of about 12 mm. Solder one end to the collector of the 2N6084 and the other end to the top terminal of the feedthrough capacitor, C3. Solder a short link of hookup wire from this terminal to the rectangular pad nearest C3, see Fig 8.

The pc board may now be mounted into position on the heatsink. Apply a little silicone grease or heatconducting compound to the transistor stud where it contacts the heatsink. Bolt the transistor down first. Carefully orient the mounting holes before-

hand. Now slip a suitable-sized nut or fibre washer under the pc board mounting holes. Either should be a close fit between the pc board and the heatsink so that no upward or downward strain is placed on the transistor leads. Any upward strain may cause the cap to pop off — an inconvenience rather than a disaster, as it can be glued back on with a quick-setting glue without any apparent ill effect. Extreme care must be exercised in doing this though. Not a recommended procedure, but possible. Any downward strain can cause the transistor leads to 'tear' at the header. This sort of damage is very difficult to repair.

The quarter-wave coax lines may now be installed. Cut two lengths to the dimensions shown in Fig 7. Solder the lines into position as illustrated, being careful not to damage the centre conductor or insulation. Use a hot iron and solder quickly. The braid at each end is best tinned beforehand. Alternatively, wrap it with a length of light gauge (say 265 WG) tinned copper wire and tin the lot before attaching the line to the pc board.

The coax lines may be coiled and tied up as shown in Fig 1 or they may be wrapped conveniently in any position around the inside of any cabinet or case the amplifier may be mounted inside.

Finally, the input and output connections can be made via short lengths of coax to convenient coax sockets. As individual constructors will have different requirements in this regard, it is best left as an individual decision. Sockets that are compatible with the existing installation are best used.

The power supply leads will need to be rated to carry currents up to six amps. Any connectors will need to be adequately rated to carry these currents. As the amplifier is completely stable with no drive, and does not draw any current, it is not necessary to switch the 12 volt supply rail, except perhaps as a precaution, and this may be routed via a complete installation supply switch.

A COMPLETE KIT OF COMPONENTS for the 2m power amp is available from **Catronics Ltd, Communications House, 20 Wallington Square, Wallington, Surrey**, for £23.10 inc VAT and 20p p&p. They are also able to supply individual components e.g. 2N6084 at £19.40, special coax at 25p/metre, BAV10 diodes at 11p each and the PCB at £1.23, all including VAT and with a standard postage and packing charge of 20p.

## TUNE UP

Tune up is quite simple. You will need a dummy load of adequate rating and either an in-line power meter of reasonable accuracy or some power output indicating device. A power supply that can deliver up to six amps at 14 volts (maximum) is necessary. An ammeter that can read up to at least six amps would be handy also.

After carefully checking the construction, apply a supply voltage of between 12 and 14 volts. Check that no current is drawn by the amplifier.

With the dummy load connected and the driving transceiver or transmitter, apply a drive of between 5 W and 12 W, preferably the lower power. Tune the input trimmers for a peak in the output power indication. Do not hold the drive on too long with the amplifier in this condition. Next, apply drive again and tune the two output trimmers for a maximum in output indication.

Now, with the maximum drive power to be used, touch up all the trimmers for maximum power output.


Maximum collector dissipation should be kept under 80 watts. Also see that the maximum continuous collector current of six amps is not exceeded.

## PERFORMANCE

At a supply voltage of close to 13 volts and a drive level of between 7 to 8 watts, a power output of 42 watts was obtained from the prototype. This is a gain of around 7 dB. The manufacturers of the 2N6084 specify a minimum gain of 4.5 dB at 175MHz. However, one could expect a somewhat higher minimum gain at 146 MHz. An efficiency in excess of 55% is readily obtainable.

# ambit international

## WIRELESS SPECIALISTS

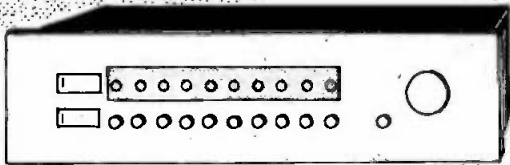

### fm tuner number two

The New FM Tuner from Ambit.

1.2uV for 30dB SN, adjustable output voltage, ultrasonic suppression better than 70dB. 6 presets, geared manual drive. Double IC stabilizers. Supplied with prealigned Larsholt RF/IF and decoder module. Complete with black woodgrain cabinet, and solid aluminium front panel. Kit £63.00 (70.87 inc. VAT)

Built and tested £79.75 (£89.71 inc. VAT)  
(Carriage £3.00 extra)

### modules for rf, if, mpx: (12v) audio and general components

NEW	7020	Dual ceramic filters, 2 stage preamp into the improved CA3089E (HA1137W), with mute, AFC to suit ANY varactor tunerhead, meter output and edge terminations. kit £5.25 built £6.55
NEW	92310	The MC1310 mpx decoder, with twin audio preamps, and BLR3107 ultrasonic block filter, kit £5.35 built £6.65
NEW	71197	A new varicap tuner for MW/LW, with ceramic filter, 80dB AGC, low noise and distortion. kit with ferrite rod £9.65 built £11.35
NEW	5800	The state of the art in FM tunerheads. 6 double varicap tuned circuits, 2 MOSFET AGC controllable RF stages, double tuned IF output stage. kit £11.35 built £14.00
	TDA2020 kit	A stereo power amp, with the TDA2020 15W RMS 0.1% THD IC from SGS. £7.85. (Special extruded heatsinks 75p each).

LINEAR ICs	(* at 8%)	DISCRETE DEVICES
CA3089E 1.94	LS8038 3.10*	ZTX107/8/9n 0.14
CA3090AQ 3.75	NE560 2.50	ZTX212/3/4p 0.16
MC1310 2.20	NE561 2.50	ZTX551/451pn 0.18
SN76660 0.75	NE562 2.50	BF256 0.34
TBA120AS 1.00	NE565 2.50	40673/MEM616 0.50
TBA651 1.81	NE566 2.55*	40822/MEM615 0.38
uA720 1.40	7805UC 1.55*	BD535n(60v - 50w) 0.52
LM380 1.00	TDA1412 0.95*	BD536p(60v - 50w) 0.53
LM381 1.81	78M20UC 1.20*	BD609n(80v - 90w) 0.70
TBA810 1.09	uA723 0.80*	BD610p(80v - 90w) 1.20
TCA940 1.80	NE550 0.80*	n = NPN type
TDA2020 2.99	NE567 2.50*	p = PNP type

VARIABLES	FOIL TRIMMERS	POTS
MVAM2 1.05	3-12pF 0.18	100k+100k LIN 0.60
MV104/BB104 0.45	4-30pF 0.23	100k+100k with..... 0.65
BA102 0.30	6-45pF 0.26	50% tap 0.65
BA121 0.30	(7.5 diameter types)	20 turn 100k..... 0.35
		diode law

### TOKO COILS, FILTERS, TUNERS FOR AM/FM AND MPX.

Full details of standard types in lists:

10mm IFTs for 455-470kHz	30p	Linear Phase filter for 10.7MHz	2.25
10mm IFTs for 10.7MHz	33p	MFH41/71T mechanicals for 455	1.65
Ceramic filters for 10.7MHz	50p	SFD470 new Murata ceramic block	0.75
Ceramic filters for 6.0MHz	80p	BLR3107 19/38kHz notch (stereo)	1.75
Ceramic 455kHz type CFX104	1.50	Variable chokes 11, 23 & 36mH	.30
CFT455B/C, CFT470C ceramic	60p	EC3302 low cost varicap FM tuner	5.50
CFU050D 470kHz ceramic	65p	EF5600 5 stage varicap FM head	12.50

Send an SAE for a free price list and stock list. There is a new Larsholt Signalmaster FM tuner and more details on our range of wireless products. PP 22p per order, VAT is generally at 12% - and the min. CWO charge is £1. Min. invoice £7.50, Catalogue 40p. (\* 8% VAT).

37 HIGH STREET,  
BRENTWOOD, ESSEX.  
CMI4 4RH tel 216029

# Learn to understand electronics for your hobbies

## 1. Lerna-Kit course

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- (1) BUILD AN OSCILLOSCOPE.
- (2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS.
- (3) CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK.

## 2. Become a Radio-Amateur

Learn how to become a radio-amateur in contact with the wide world. We give skilled preparation for the G.P.O. licence.

**FREE!**

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**

P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

**BLOCK CAPS**  
PLEASE ETA 9/6

# PRACTICAL SOLID STATE DC SUPPLIES

This book covers in, practical detail the design and construction of a wide range of DC power supplies, which form an integral part of every piece of modern electronic equipment.

The book is an up-to-date coverage of DC supplies, from simple batteries through to the most highly stabilised.

The particular selection of circuits and designs owes much to the author's practical industrial experience.



Students might find that the book becomes a constant reference source. Its high number of circuits makes it a valuable bench manual for any electronics workshop, where the making up of power supplies is one of the daily chores. Price £5.50.



Orders to:  
ETI Book Services,  
25 Court Close,  
Bray, Maidenhead, Berks.



# GET HUNG UP!

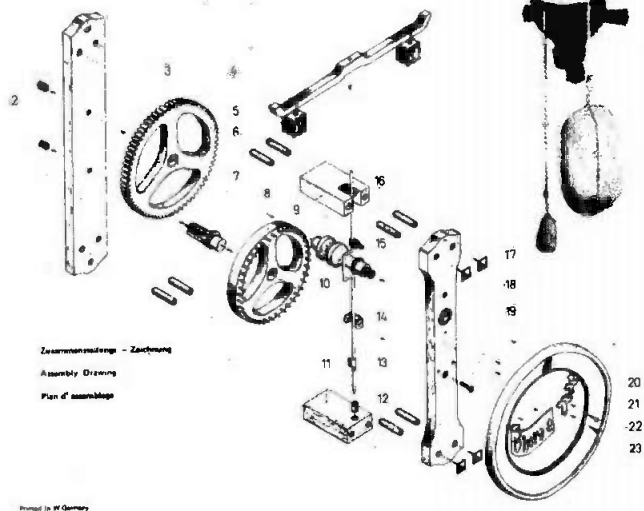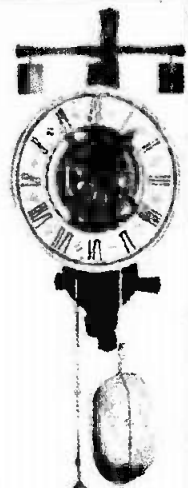

Our new range of clock kits is based on designs hundreds of years old. These clock kits use wood, stone and iron to reproduce authentic "olde worlde" wall clocks in full detail. The kits contain all you need including glue, screws, etc., and very comprehensive instructions. This range complements our fully electronic clock kits.

PRICES (All inclusive)	KIT	BUILT
Gothic Clock Kit—Diam. 6½"	£23.95	£36.50
Rotating Dial Kit—Diam. 6"	£19.95	£32.50
Wrought-Iron Kit—Diam. 5½"	£46.35	£69.50
Wooden Wheel Kit—Diam. 6½"	£31.50	£45.25
Knight Clock Kit—Diam. 7½"	£39.50	£62.45
Oak Foliot Kit—Diam. 14"	£89.50	£125.00

(As illustrated)

For coloured Brochure please send 15p stamps.  
Completed clocks can be seen at our offices  
★ Use special offer coupon in August ETI to save 15%

**560 VDU  
MICRO  
PROCESSORS**

**MM2112 RAM  
2513 ROM  
SC/MP Introkit**

**£4.30 ea  
£9.00 each  
£54.50 ea**

## PRICE LIST

ALL PRICES EXCLUDE VAT AT 8%

### MHI DISPLAY KITS

MHI-707/4 (digit) 0.3"	6.60	MHI-727/6 0.5"	12.00
MHI-707/6 0.3"	9.50	MHI-747/4 0.6"	9.80
MHI-727/4 0.5"	8.50	MHI-747/6 0.6"	14.70

### MHI CLOCK KITS

(Chip, Socket, PCB + Driver IC)

MHI-5309 reset zero	1.9
MHI-5311 BCD	7.35
MHI-5314 clock	7.35
MHI-5318 external digit select	6.60
MHI-5378 car (crystal + trimmers incl)	7.35
MHI-50250 alarm	15.10
MHI-50397 counter series	8.35
MHI-7001 alarm, calendar	19.50
	10.00

### CLOCK CHIPS

NATIONAL	
MM5309 7 seg + BCD with reset	1.9
MM5311 7 seg + BCD	5.69
MM5312 7 seg + BCD. 4 digit only	5.69
MM5313 7 seg + BCD	4.88
MM5314 7 segment	5.69
MM5315 7 seg + BCD with reset	4.88
MM5316 Non-mpx alarm clock	5.69
MM5318 7 seg + BCD (external digit select)	10.17
MM5371 Alarm clock 50Hz	3.36
MM5377 Car clock, crystal controlled, LCD	8.14
MM5378 Car clock, crystal controlled, LED	7.21
MM5379 Car clock, crystal controlled. Gas discharge	6.73
	6.73

### MOSTEK

MK50250 Alarm clock (12Hr+60Hz/24Hr+50Hz)	5.60
MK50253 Alarm clock (12Hr+50Hz/24Hr+50Hz)	5.60
MK50395 UP/DOWN Counter—6 Decade	14.50
MK50396 UP/DOWN Counter—HHMMSS	14.50
MK50397 UP/DOWN Counter—MMSS.99	14.50

### CALTEX

CT7001 Alarm/calender 7 segment	7.30
CT7002 Alarm/calender BCD	7.30
CT7003 Alarm/calender 7 seg Gas discharge	7.30
CT7004 Alarm/calender 7 seg	7.30

### GENERAL INSTRUMENTS

AX5-1202 4 digit 7 seg	4.76
AY5-1230 on-off -- alarm. 7 seg	5.25

### DISPLAYS

1-9	
LITRONIX	
DL707, 704, 701	1.48
DL727, 72B, 721	3.75
DL747, 746, 750	2.45
FUTABA PHOSPHOR DIODES	
5LTO1 4 digit MPXD	5.80
5LTO2 4 digit static	5.80
5LTO3 5 digit MPXD	5.80

### LITRONIX CLASS II PRODUCTS

1-9	25.99
DL707E, 704E, 701E	0.70
DL727E, 728E, 721E (2 digit pack)	1.80
DL747E, 746E, 750E	1.50
	1.00

### CASES

VERO A 8" x 5.5" x 3"	}	£2.95 + 25p P & P
VERO B 6" x 3¼" x 2¼"		

### SOCKETS

18 pin	0.60	24, 28 or 40 pin	1.00	Soldercon strip sockets 0.30
--------	------	------------------	------	------------------------------

### MODULES

MA1002F 12HR 50Hz or MA1002H 24Hr 50Hz—Alarm	£7.97
Suitable Transformer MTX1001	0.90
★MODULE + TRANSFORMER + VERO CASE	£12.50 incl.
	(VAT + P & P INCL)

### PAYMENT TERMS

Cash with order, Access, Barclaycard (simply quote your number and sign)  
Credit facilities to accredited account holders. Pro-forma invoices can be issued.  
Please send 20p for post and packing.

ALL PRICES EXCLUDE VAT AT 8%  
(EXCEPT MECHANICAL CLOCKS AS ABOVE)

# BYWOOD

BYWOOD ELECTRONICS  
68 Liberos Road  
Hemel Hempstead  
Herts HP3 9QR  
Tel 0442 62757

# Opto-Electronics

**With the advent of precision-moulded optical systems the way to practical opto-electronic devices has really opened up.**

FOR SOME time now there has been an increasing trend towards integration between optics and electronics. For this there are two main reasons: visible light may well become the carrier medium for the next generation of communications systems, and the greater need for accurate information in all fields has led to a great expansion in the demand for visual displays.

Before visible light can be employed for data transmission, a whole range of components will have to be developed as the optical equivalents of electrical plugs and sockets, jacks, switches and relays, amplifiers, attenuators, filters, tuners and similar units.

Miniaturisation resulting from solid-state technology has drastically reduced the size of electronic equipment. Meters, indicators and display screens, however, cannot be similarly reduced in size, because no one could read them. An important

sector of opto-electronics therefore concerns itself with providing legible data from systems of the smallest possible size. The most common example is probably the light-emitting diode (LED) display.

The layout and arrangement of printed circuit boards and the interchangeable plug-in modules (which presuppose the absence of permanent wiring to the outer case), often create problems of conveying indication from the point most convenient to the circuit designer to the point most convenient to the user. Again, optical components in the form of mirrors, prisms, light guides and lenses (or any combination of them) can solve such problems.

## ADVANTAGES OF PLASTICS LENSES

Several clear polymers, such as acrylics, polystyrene, polycarbonate, ABS, cellulose, vinyl, polyester and others, can be used instead of glass to make optical components. The most important technical advantages of plastics optics are freedom of design, greatly reduced assembly costs, greatly reduced weight, and elimination of shattering.


On average, optical plastics are about 55-65% lighter than glass. In practical terms the weight saving is usually much greater because most of the metal mounting and retaining parts essential for glass lenses can be dispensed with, since plastics lenses can be moulded with integral spacers and retaining lugs.

The most interesting aspect of plastics lenses is the freedom of optical form conferred by the nature of the material. With moulded plastics optics, human skill is concentrated on the manufacture of the moulds, from which any required number of lenses of uniform quality can be produced, aspheric (non-spherical) lenses can readily be made.


Aspheric lenses are important because they permit aberrational correction of a system without affecting its focal length and magnification. Certain shortcomings of spheric lenses can therefore be eliminated or minimised by 'aspherising' one or several lens surfaces in an optical system. A given amount of correction can be achieved by fewer components if one or more of them are made aspheric. In both cases significant savings result.

The advantage of aspherics is well

*Fig.1. The aspheric lens (top) gives an undistorted view of at least 20 squares, while the spherical glass lens (below), of the same diameter and power, only shows four reasonably undistorted squares.*

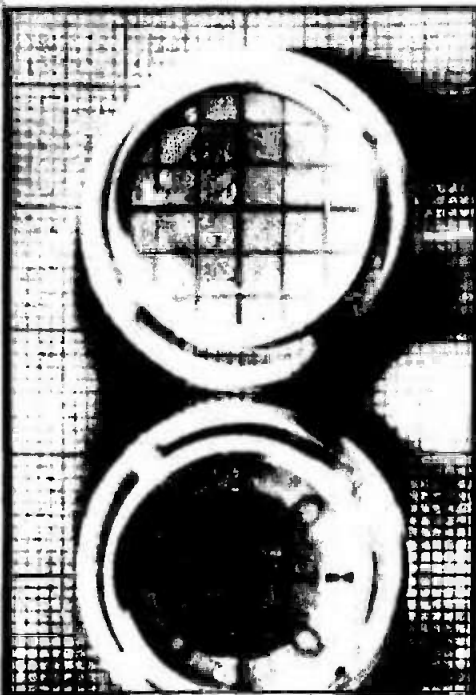

*Fig.2. Integral array of nine miniature aspheric lenses with a magnification of 3x for an electronic pocket calculator.*

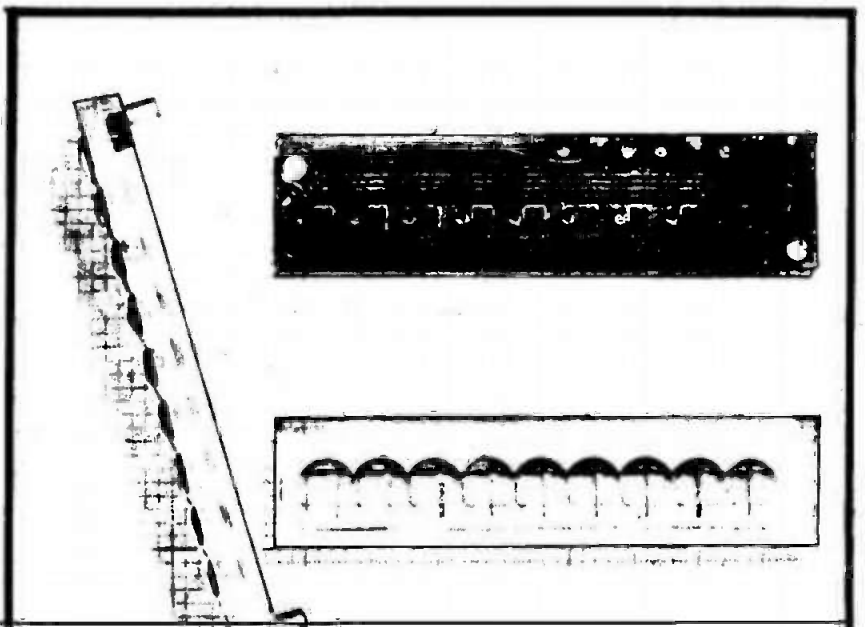



*Fig. 3. This combined mini-computer, moving map and electronic display unit (Comed) for aircraft navigation uses a moulded plastics lens of complex aspheric design to give an undistorted, brilliant image of the map.*



*Fig. 4. This one-piece light guide splits the light from a single bulb into six beams to scan six rows of holes in a punched card for an automatic telephone dialling unit.*

shown in Fig.1. Both magnifiers have the same size and magnification, but while the aspheric moulded plastics lens in the top unit has a distortion-free field of view of 20 squares, the spherical glass lens of the lower unit has an effective field of view of only four squares. Yet the glass lens is heavier and more expensive.

Aspherics can be also produced at apertures greater than  $f/1$ . They are already widely used in portable devices involving high magnification, such as reading aids for sub-normal vision. Aspheric lenses from 3 mm to 180 mm diameter are readily available, while lenses up to 630 mm diameter have been made. In ophthalmics, magnifications of 8x are frequently used.

### INTEGRAL PLASTICS OPTICS

The freedom of shape conferred by moulding frees designers from the limitations imposed by glass — he can create systems which are functionally superior. Plastics lenses can be moulded with integral lugs, bosses,

rims, pivots and similar mounting, swivelling, adjusting and actuating members, in a wide range of shapes, sizes or configurations, as shown for instance in Fig.4. This means that in a well-designed product, the optical system parts snap or slide into the housing without any further assembly operations and, with precision-moulded housings, no subsequent setting or adjustment should be necessary.

### TYPICAL APPLICATIONS

A multiple aspheric lens array moulded integrally with its mounting plate is shown in Fig. 2, with the associated nine-digit seven-bar circuit board for pocket calculators. The moulding has two pins on the underside which locate through the two holes in the board in two further holes in the calculator casing. Two ledges on the underside of the moulding ensure that it is held at the correct focal distance above the board. Assembly is therefore very simple and the need for any adjustment is eliminated. The lenses have a

magnification of 3x and provide a distortion-free image.

A much larger moulded lens is used on the Ferranti Comed (combined map and electronic display) for aircraft, shown in Fig.3. In addition to alpha-numeric readouts of latitude, longitude, range, bearing and other navigational data, the unit has a screen on to which a moving map or radar picture can be projected from the rear. The lens is a bivet type, the flatter surface having a special form known as a Schmidt corrector plate. This complex aspheric surface is essential to ensure an undistorted image from any position, despite movements of the pilot's head, and a brilliant image even in strong daylight.

Light guides can be of many different basic types, depending on the function they are required to perform. A good example is the Card Callmaker, a compact unit which can automatically dial a telephone number with up to 16 digits when the appropriate punched card is inserted into it. The light guide (see Fig.4), which is moulded accurate to  $\pm 0.012$  mm in all dimensions, has six 'fingers', which split the light from a single lamp into six beams. Each finger incorporates a lens at its tip, which focuses the light on to a photocell. The inserted card blocks the light, except where holes are punched in any of the six rows available. This automatic dialling unit could, of course, also work with six lamps and conventional glass lenses, but then failure of any one lamp out of six would result in a wrong number. If the single lamp in the Card Callmaker fails, the unit will simply not operate. This moulded unit is much cheaper than a light guide made up from bundles of glass fibres.

In addition to lenses, prisms, light guides and similar components, mirrors and reflecting surfaces of almost any shape can also be produced. Aluminium, gold and thorium are most commonly used for coating the reflective surface, which may be the front or rear surface of the component.

Integrally moulded optics will undoubtedly play an increasing part in opto-electronics, including such equipment as self-scanning arrays, low light level vision aids (both active and passive), cathode-ray tubes (for combined optical digitisers), rear-ported cathode-ray tubes (for combined optical and electronic projection), photometers and densitometers, video recording systems, optical character readers, holographic and thermal imaging equipment, laser equipment of all kinds and many others. ●

# FIXED CAPACITORS

## PART 2 This section in our electronic component series is a definitive guide to the many various systems commonly in use.

THE CHARACTERISTICS AND value of a capacitor may be indicated on the body of the component in one of three ways:—

- (a) The value, tolerance, working voltage and any other characteristic may be stamped or printed on the body of the component. This is usually used on physically large components such as paper capacitors, electrolytics etc. However, it is being increasingly used on smaller capacitors, particularly plastic film types. Figure 1 shows representative markings.
- (b) A sequence of coloured bands or dots is painted on the component body. This is deciphered according to the standard colour code table for the value and tolerance. Additional bands may indicate other characteristics according to a specified table.

- (c) The value and other characteristics may be indicated by a 'typographic' code; a sequence of numbers and letters stamped or printed on the component body. There is a variety of these codes. These will be elaborated upon shortly.

The particular marking code used depends largely on the style and type of capacitor, i.e: paper, mica, button mica, plastic film, ceramic, etc, and the code preferred by the manufacturer.

The temperature coefficient of a capacitor may be expressed directly in parts per million per centigrade degree (ppm/°C) or simply the significant figures preceded by the letter N for a negative coefficient or P for a positive coefficient. Examples are given below:—

P100	= +100 ppm/°C
P30 or P030	= +30 ppm/°C
NP0	= 0 ppm/°C (negative/ positive zero)
N30 or N030	= -30 ppm/°C

N033	= -30 ppm/°C
N075 or N080	= -75 ppm/°C
N470	= -470 ppm/°C
N2200	= -2200 ppm/°C

Wound foil and metallized capacitors may have a black line marking one end of the component body, as illustrated in Figure 2. This indicates that the *outermost* foil is connected to the lead at that end of the body. This is useful in bypassing applications or where the 'hot' terminal may be sensitive to the surrounding environment. This lead is connected to the circuit common, or the 'low' portion of the circuit and shields the 'hot' electrode of the capacitor, reducing stray coupling to or from the external circuit.

Remember that the capacitors are non-polar so that the black line does not indicate polarity or the negative terminal.

**Mica Capacitors:** The most common method of marking moulded mica capacitors is by an arrangement of coloured dots. The widely used British and American systems are illustrated in Figs 3 and 4. The value and tolerance may be found by referring to Table 1. The other characteristics may be obtained from Table 2.

Three, four, five and alternative six-dot codes have been employed from time to time. These are illustrated in Fig 5. The capacitor's value and other characteristics can be obtained from Table 1. The alternative six-dot code is for high-tolerance, high stability capacitors.

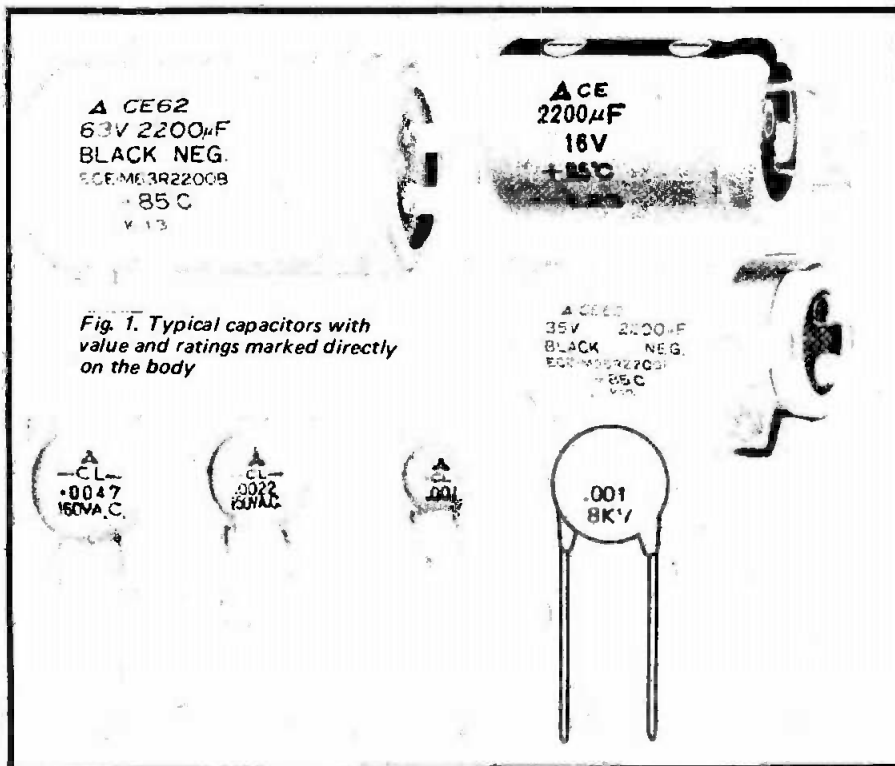


Fig. 1. Typical capacitors with value and ratings marked directly on the body

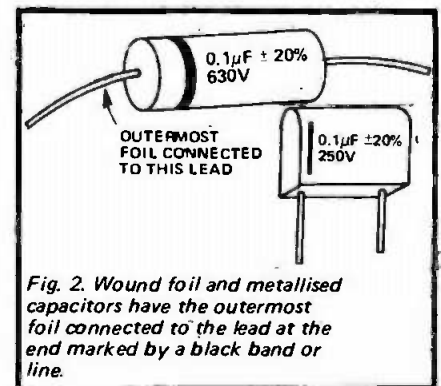


Fig. 2. Wound foil and metallised capacitors have the outermost foil connected to the lead at the end marked by a black band or line.

**TABLE 1**  
**MICA CAPACITOR COLOUR CODE**

Colour	1st & 2nd Digits	Multiplier	Tolerance	Voltage Rating	Characteristic	
					Temp. Coeff. (ppm/°C)	Capacitance Drift
Black	0	1	±20%**	350	± 1000	±5% + 1 pF
Brown	1	10	± 1%		± 500	±3% + 1 pF
Red	2	10 <sup>2</sup>	± 2%		± 200	±0.5%
Orange	3	10 <sup>3</sup>	± 5%	750	± 100	±0.3%
Yellow	4	10 <sup>4</sup>			- 20 to + 100	±0.1% + 0.1 pF
Green	5	—			0 to + 70	±0.05% + 0.1 pF
Blue	6	—	±10%	2000	-50 to + 150	±0.3% + 0.2 pF
Violet	7	—			-50 to + 100	±0.2% + 0.2 pF
Grey	8	—				
White	9	—				
Gold	—	0.1				
Silver	—	0.01				

Note: Value indicated in pF. \*\* no-colour also used in lieu of black.

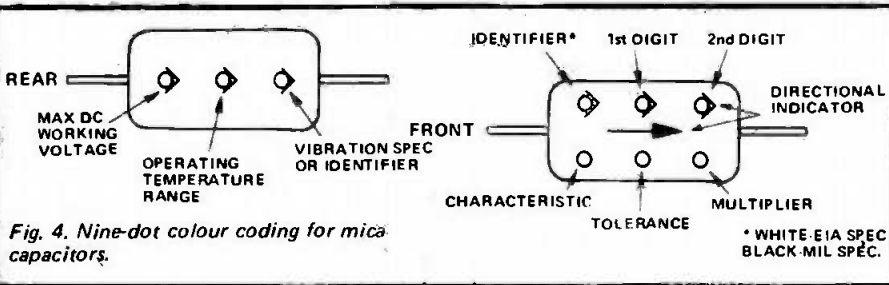


Fig. 4. Nine-dot colour coding for mica capacitors.

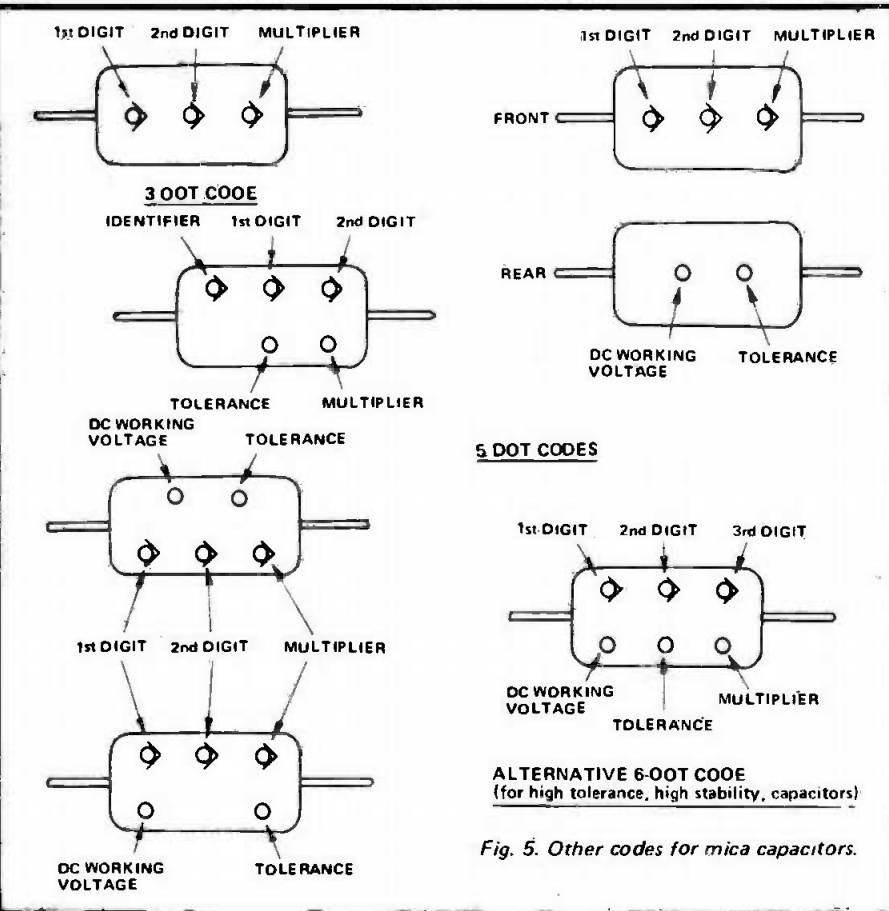


Fig. 5. Other codes for mica capacitors.

**Button Mica Capacitors:** The characteristics of button mica capacitors are indicated by a system of three, five or six dots on the rim of the component. These are illustrated in Fig 6. The value and characteristics are obtained from Table 1.

Note that there are three six-dot codes. Numbers 1 and 2 are for standard tolerance capacitors but number 3 in Fig 6 is for close tolerance, high stability types where the capacitance is specified to three significant figures.

**Ceramic Capacitors:** A variety of

**TABLE 2**

Colour	Voltage Rating	Operating Temp. Range
Black	100	-55 to +70°C
Brown		-55 to +85°C
Red		-55 to +125°C
Orange	300	-55 to +150°C
Yellow		
Green		
Blue	500	-55 to +150°C
Violet		
Grey		
White	1000	
Gold		
Silver		

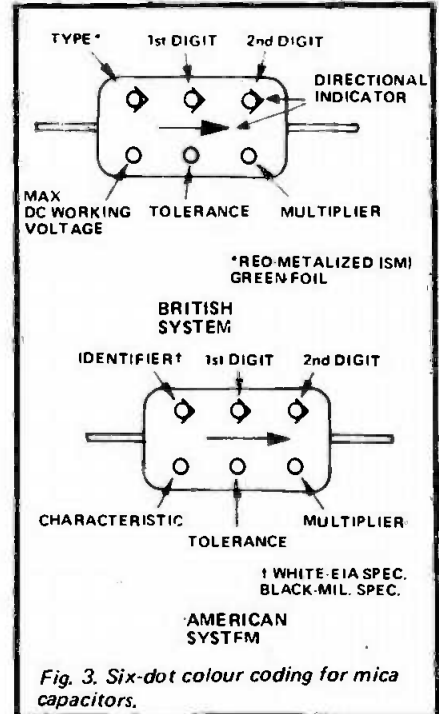


Fig. 3. Six-dot colour coding for mica capacitors.

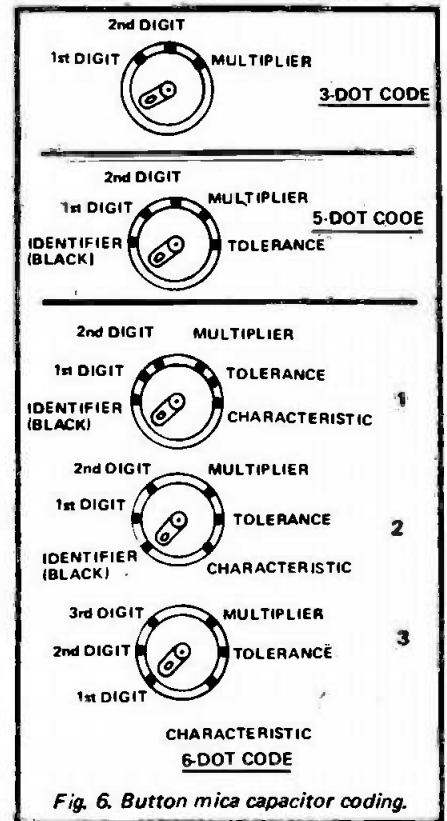


Fig. 6. Button mica capacitor coding.

# FIXED CAPACITORS

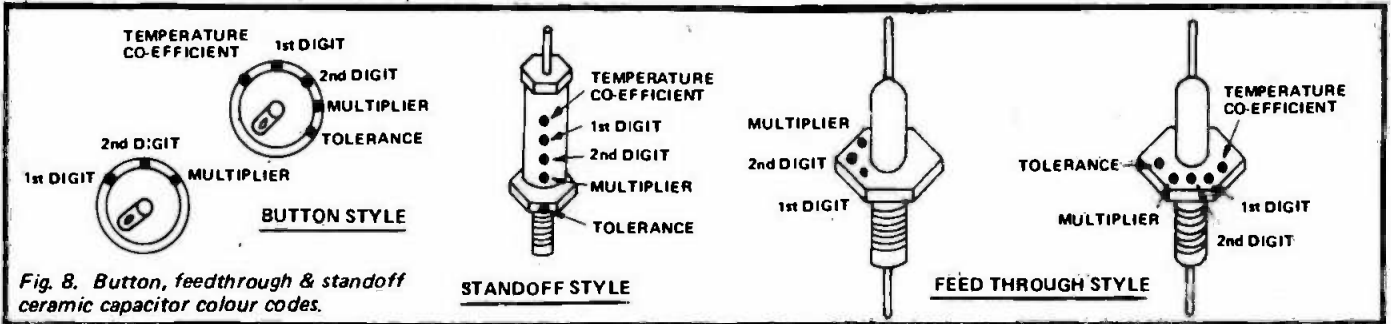


Fig. 8. Button, feedthrough & standoff ceramic capacitor colour codes.

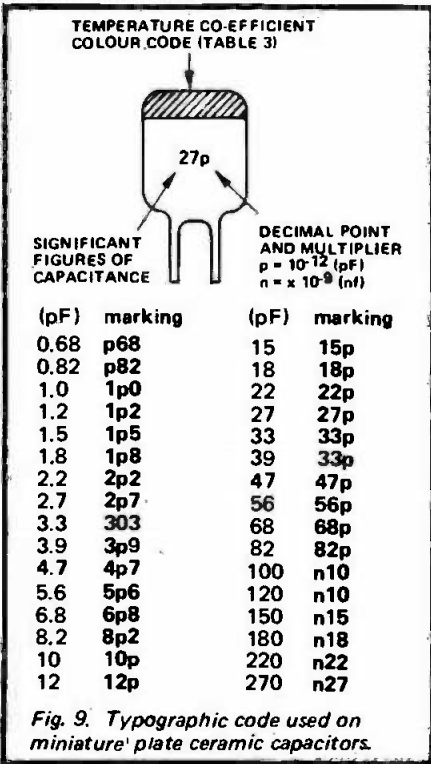


Fig. 9. Typographic code used on miniature plate ceramic capacitors.

typographic and colour codes is used for ceramic capacitors, largely depending on style of construction and the preference of the manufacturer. The codes used for various construction styles are illustrated and explained.

Colour code systems for the common styles of ceramic capacitor are illustrated in Fig 7. Note that in the five and six colour systems, the first band or dot is always larger than the others. For the axial lead style, this distinguishes them from resistors. In the six-colour system, the first two bands indicate the temperature coefficient. The value and other characteristics of these capacitors may be obtained from Table 3. Figure 8 illustrates colour codes for button, feedthrough and standoff style capacitors.

The typographic codes used on ceramic capacitors are illustrated in Figs 9, 10 and 11.

The code used on miniature plate ceramic capacitors, typical of the type manufactured by Philips, is illustrated in Fig 9. The value is indicated in farads, the letters p and n being used as a multiplier and to indicate the decimal point. If the multiplier is omitted, the value is indicated directly in pF. The temperature coefficient is indicated by a

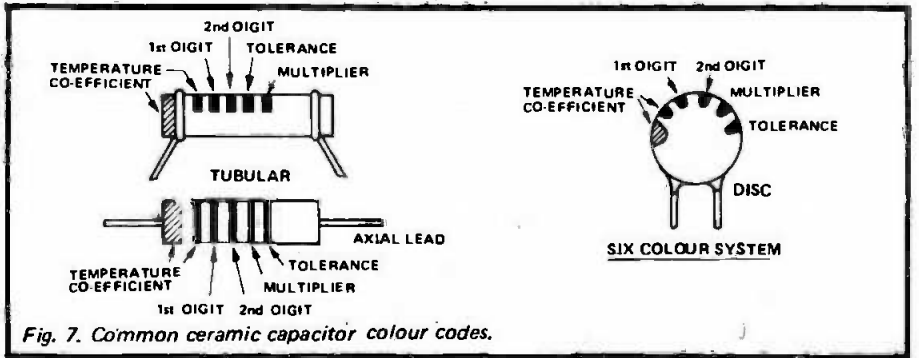
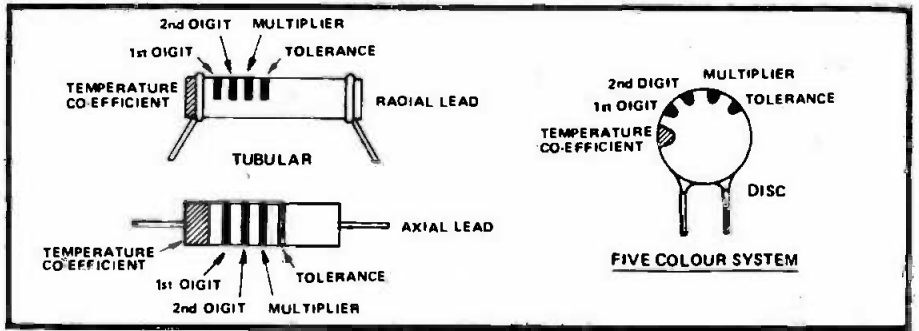
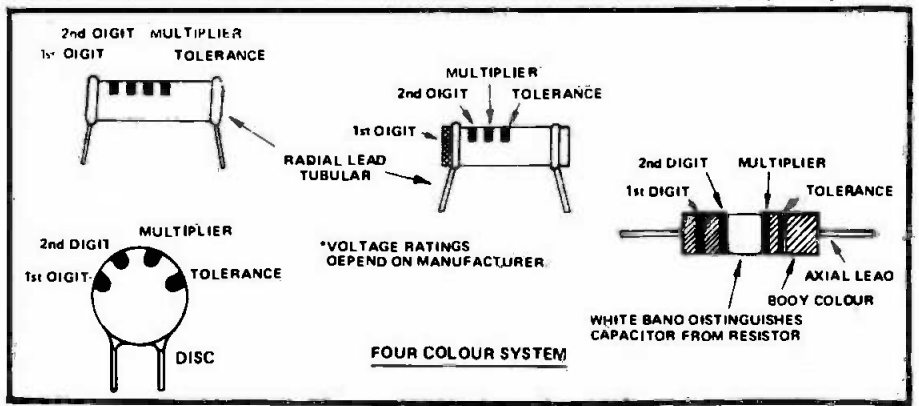
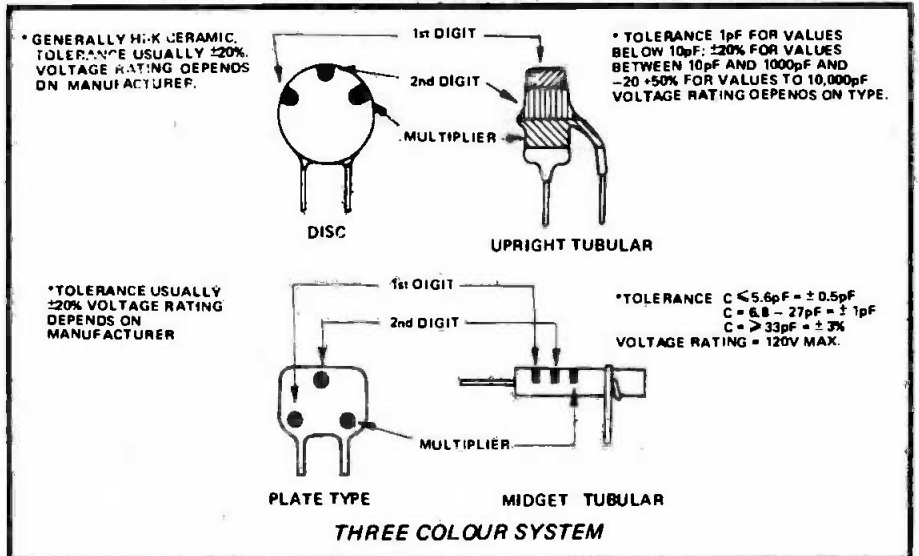
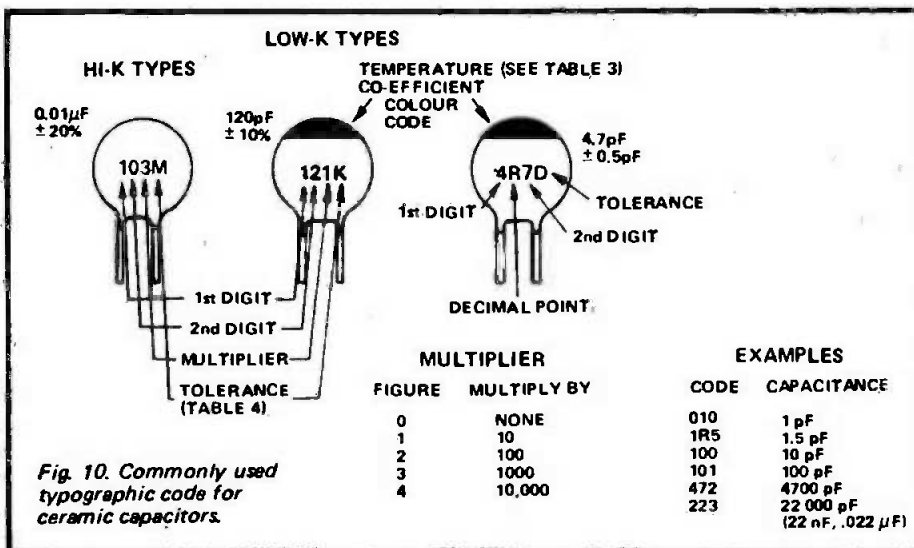


Fig. 7. Common ceramic capacitor colour codes.

**TABLE 3**  
**CERAMIC CAPACITOR**  
**COLOUR CODE**

COLOUR	1st & 2nd digits	Multiplier	Tolerance		Temperature Coefficient	6-COLOUR SYSTEM TEMPERATURE COEFFICIENT	
			C < 10pF (pF)	C > 10pF (%)		Integer	Multiplier
Black	0	1	±2pF	±20	NPO	±0	1
Brown	1	10	±0.1	±1	N030/N033	-3	10
Red	2	10 <sup>2</sup>	±0.25	±2	N075/N080	-8	10 <sup>2</sup>
Orange	3	10 <sup>3</sup>	±0.25	±2.5 (or 3)	N 150	-1.5	10 <sup>3</sup>
Yellow	4	10 <sup>4</sup>			N 220	-2.2	10 <sup>4</sup>
Green	5		±0.5	±5	N 330	-3.3	
Blue	6				N 470	-4.7	
Violet	7				N 750	-7.5	
Grey	8	10 <sup>-2</sup> (0.01)	±0.25			+3	
White	9	10 <sup>-1</sup> (0.1)	±1.0	±10	P 100	+1	
Red and Violet	—	—	—	—	P 100	—	—

NOTE: Value indicated in pF

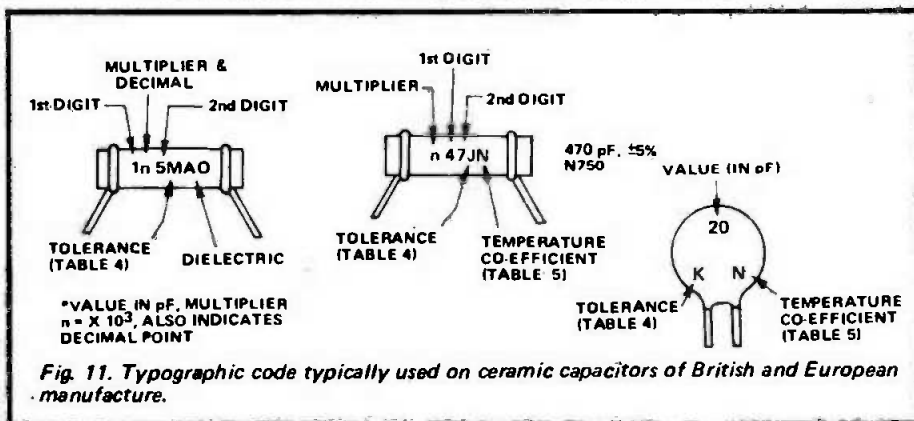


**TABLE 4**  
**Typographic Tolerance Code**

Letter	Tolerance	
	≤ 10 pF	≥ 10 pF
B	±0.1 pF	
C	±0.25 pF	
D	±0.5 pF	
E	—	±25%
F	±1 pF	±1%
G	—	±2%
H	—	±2.5%
J	—	±5%
K	—	±10%
M	—	±20%
P	—	-0 + 100%
S	—	-20 + 50%
W	—	-0 + 200%
X	—	-20 + 40%
Z	—	-20 + 80%

**TABLE 5**  
**Typographic T.C. code**

Letter	Temp. Coeff.
A	P100
C	NPO
D	N033/N030
E	N047/N050
F	N075/N080
G	N150
H	N220
J	N330
K	N470
N	N750
P	N1500
R	N2200
S	N3300
T	N4200
U	N4700
V	N5600



coloured band on top of the capacitor, the characteristic can be obtained from Table 3. Values below 100 pF (In) are generally Low-K, temperature compensating (TC) types. Hi-K types will not have the coloured band. Typical markings and corresponding values for low value capacitors are shown in the table on the right of Fig 9.

Another widely used code is illustrated in Fig 10. Generally, this involves a group of three numbers with a following letter. The first two numbers are the significant figures of capacitance, the third digit denoting the number of following zeros. The value is indicated


in pF. For values below 10 pF which require a decimal point, the letter R is interposed between the two significant figures of capacitance. The value is followed by a single letter indicating the tolerance. The tolerance can be obtained from Table 4. If the tolerance code is not included, assume a tolerance of ±20%. Low-K types will have a colour-coded band on top similar to the miniature plate ceramics, and Table 3 will indicate the value.

A typographic system used commonly on capacitors of British and European manufacture, particular tubular, radial-lead types, is illustrated in Fig 11.

Values below 100 pF are indicated directly in pF. Values between 100 pF and 1000 pF are indicated in pF using the multiplier n (= x10<sup>3</sup>). The position of the multiplier may indicate the decimal point. For example, a 470 pF capacitor will be marked n47 for the value, whereas a 1500 pF capacitor will be marked In5. Values above 10000 pF are generally marked in µF.

A system of two or three letters following the value are used to indicate the tolerance and temperature coefficient or dielectric characteristics of the capacitor in this system. The first letter indicates tolerance, the value

# FIXED CAPACITORS

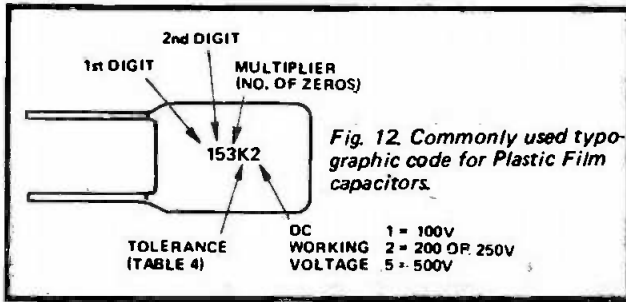

being obtainable from Table 4. A single letter following the tolerance code indicates that the capacitor is a Low-K TC type, the value of the temperature coefficient can be found from Table 5. If the tolerance code is followed by two letters, this indicates an H-K type and the manufacturer's data should be consulted if the dielectric characteristics are needed.

Some ceramic capacitors of Japanese manufacture may have a voltage rating code, consisting of a number and a letter, or two letters, also stamped on the component. It may precede the value and tolerance code or be placed separately. This code is given in Table 6.


A range of Hi-K disc ceramic capacitors are manufactured that have the value printed on the body and a red band painted at the end opposite the leads. They are commonly known as 'redcaps', the red band indicating a Hi-K capacitor with a 25 Vdc working rating. They should not be confused with a range of epoxy-encapsulated ceramic capacitors manufactured by Erie, which have a red coating all over and are also known as redcaps.

**Plastic Film Capacitors:** By and large, plastic film capacitors have their value, tolerance and voltage rating marked on them directly. Small, low-value polystyrene capacitors are marked thus:— 47/100. The first figure is the value in pF, the latter figure the dc working voltage. Thus, a capacitor marked that way would be 47 pF, 100 Vdc working. Polystyrene capacitors have the lead connected to the outer foil marked by a black band at the end of the body as illustrated in Fig 2.

Often, the tolerance rating is not marked on plastic film capacitors. Except for polystyrene and mylar capacitors, a tolerance of  $\pm 20\%$  can be assumed.

Typographic codes used on plastic film capacitors are very similar to that used on Hi-K disc ceramics as illustrated in Fig 10. For example, a capacitor may be marked 102K, which indicates a 1000 pF,  $\pm 10\%$  capacitor. In addition, a single digit following the tolerance code may be added. This indicates the voltage rating and represents volts x 100. For example, a capacitor marked 272K1 is a 2700 pF,  $\pm 10\%$  100 V capacitor.

The common typographic code used

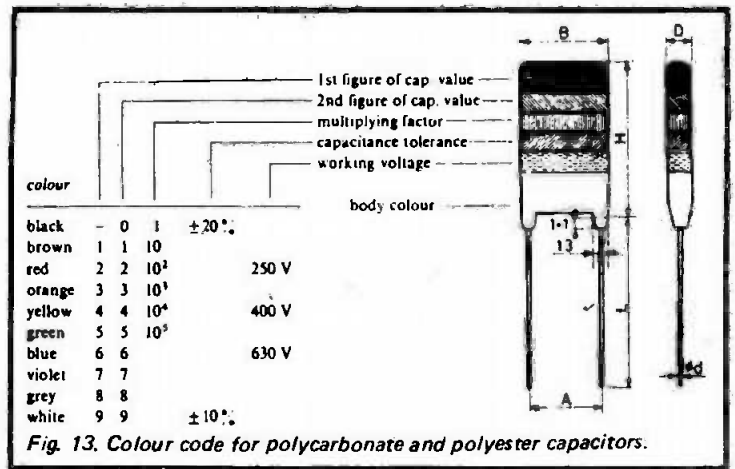

on plastic film capacitors is shown in Fig 12.

Polycarbonate and polyester capacitors are marked with coloured bands around their body indicating their value and characteristics — illustrated in Fig 13. The table gives the values of the bands. The capacitance is indicated in pF. The body colour is usually a light tan.

**Paper Capacitors:** Paper capacitors are large enough to have the value, tolerance and rating printed directly on them. The flat moulded style, largely superseded, now uses a code of four coloured dots, similar to that used on flat moulded mica capacitors. Figure 14(A) illustrates the code for flat moulded paper capacitors. Note that the body will be dark brown or black in contrast to the light tan bodies used on flat moulded mica capacitors. The capacitance and voltage rating may be obtained from Table 1.


Moulded tubular paper capacitors are sometimes marked with a colour code as illustrated in Fig 14(B). The capacitance and tolerance may be obtained from Table 1. The voltage rating is indicated by one or two coloured bands at the end opposite the value. Add two zeros to the significant figures. A single band

indicates a rating under 1000 volts. A gold band indicates a rating of 1000 volts. The value is indicated in pF. Example:—

Value      1st band = brown  
              2nd band = red      120000 pF  
              3rd band = yellow       $\pm 20\%$   
              4th band = black  
Voltage    1st band = brown  
              2nd band = green      1500 volts

**Electrolytic Capacitors:** Most wet electrolytic capacitors have the capacitance, voltage rating and tolerance rating marked on them. Miniature, low voltage types use a kind of shorthand as follows:— 25/25 means 25  $\mu$ F, 25 V working. The tolerance is not usually marked on them but it may be assumed to be at least  $-20\%$ ,  $+80\%$ . The positive terminal will be marked with a + symbol or perhaps a red end cap or red dot. The negative terminal may be marked with a - symbol or a black stripe. One terminal may not be marked. In this case it is usually the negative terminal that is not marked. Most electrolytics have the can connected to the negative terminal. Some high voltage electrolytics have the can insulated and the electrodes brought out to separate terminals.

**Tantalum Capacitors:** These may have the value marked on them or the value

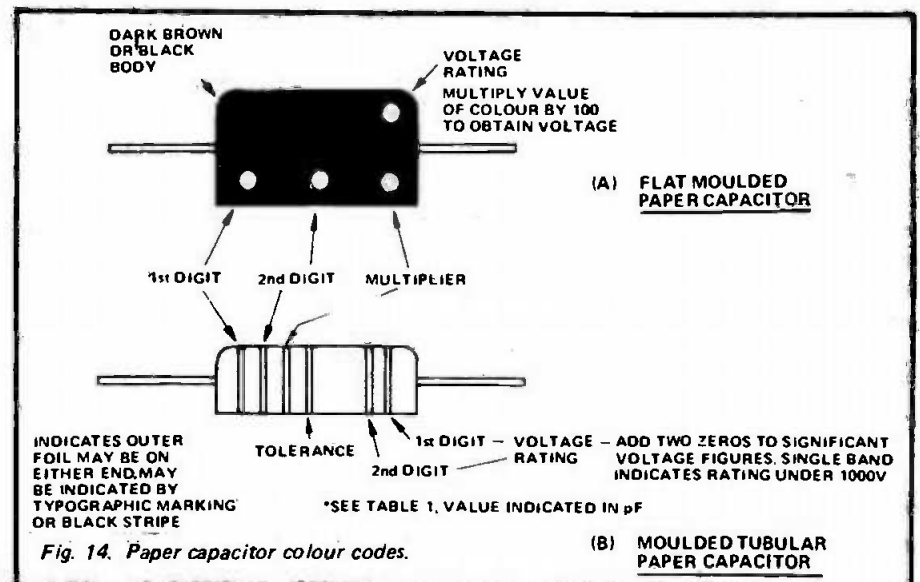



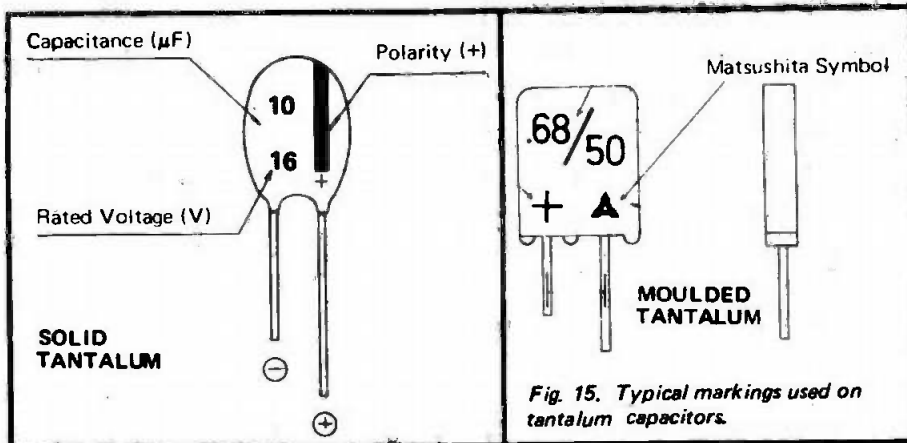


Fig. 15. Typical markings used on tantalum capacitors.


TABLE 7  
COLOUR CODE  
FOR TANTALUM CAPACITORS

Colour	Voltage	Tens & Units	Multiplier
Brown	—	1	x 10
Red	—	2	x 100
Orange	35 V	3	—
Yellow	6.3 V	4	—
Green	16 V	5	—
Blue	20 V	6	—
Violet	—	7	—
Grey	25 V	8	x 0.01
White	3 V	9	x 0.1
Black	10 V	0	x 1
Pink	35 V	—	—

TABLE 6  
Voltage rating code  
for Japanese ceramic  
capacitors

Code	Rating	
1E	25	Vdc
1H	50	"
2H	500	"
3A	1 kV	"
3D	2 kV	"
3F	3 kV	"
3G	4 kV	"
3H	5 kV	"
3J	6 kV	"
3M	7 kV	"
3K	8 kV	"
4A	10 kV	"
4B	12 kV	"
4C	15 kV	"
AL	1500	Vac
CL		
DS	2500	Vac

SOLID TANTALUM TYPES

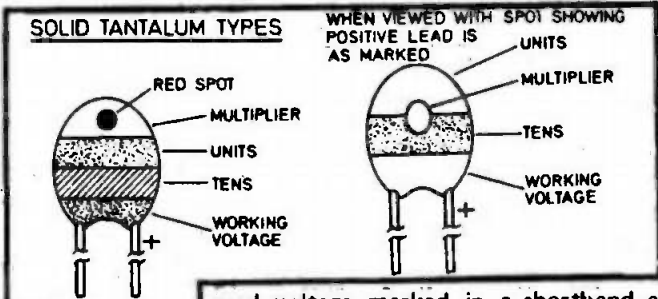

Example  
Units = Blue = 6  
Tens = Grey = 8  
Mult. = White =  
x 0.1 µF  
Body = Grey = 25V  
6.8 µF / 25V

Fig. 16. Common colour code for tantalum capacitors.

and voltage marked in a shorthand as explained previously. The positive terminal is usually marked with a black stripe and/or a + symbol. The negative terminal is usually not marked. Markings on a solid tantalum and a moulded tantalum are shown in Fig 15. The solid tantalum type has the positive lead longer than the negative lead — the opposite with moulded tantalum.

TABLE 8

Working Voltage	Surge Voltage
3.15 volts	4 volts
6.3	8
10	13
16	20
20	25
25	32
35	44
50	63

Solid tantalum ('Tag') capacitors are also marked with a colour code. There are two systems in use, illustrated in Fig. 16. Table 7 gives the values and ratings for the colours.

Tantalum capacitors can withstand a surge voltage about 20-30% greater than their rated working voltage. Table 8 below lists the maximum surge voltage of a capacitor having the rated working voltage shown.

# SPECIALS

## FROM ETI

To: ETI Specials, ETI Magazine, 36 Ebury Street, London SW1W 0LW.  
POSTAGE AND PACKING is 15p for the first, 10p for subsequent (overseas, 20p and 15p).

LOW STEREO AMP. TEMPERATURE ALARM. LM380 INTERCOM AND RECORD PLAYER. RU-MABLE FILTER. BATTERY CHARGER. TAPE/SLIDE SYNCHRONISER. METER FAMILY.

**ETI TOP PROJECTS No 2**  
electronics 75p  
today international

... PERRY. LINEAR IC TESTER. IGNITION TIMING LIGHT. SPRING LINE REVERBERATION UNIT. ADD-ON QUAD UNIT. NI-CAD BATTERY CHARGER. DIGITAL STOPWATCH. HI-POWER STROBE. TRAFFICATOR CANCELLOR. AUDIO WATTMETER. FET 4-INPUT MIXER. PRINTER. AUTOMATIC CAR THEFT ALARM. IC POWER SUPPLY. OVER-LED. AERIAL MATCHER. LOGIC PROB. PLUS MANY MORE...

**ETI TOP PROJECTS No 3**  
£1

**ELECTRONICS TODAY**

4600 Synthesiser complete reprint of our superb, synthesiser design produced by Maplin  
£1.50 + 15p p&p.

**electronics it's easy**  
Volume 1

electronics - It's Easy the first thirteen parts of our popular introductory series  
£1.20 + 15p p&p.

**electronics it's easy**  
Volume 2

electronics - It's Easy Volume 2 - the next thirteen parts of our series.  
£1.20 + 15p p&p.

Projects Book Two - contains 26 popular projects from the pages of ETI, first published July 1975  
75p + 15p p&p.

Project Book Three - contains 27 popular projects from the pages of ETI, first published March 1976  
£1.00 + 15p p&p.

4600 Synthesiser complete reprint of our superb, synthesiser design produced by Maplin  
£1.50 + 15p p&p.

electronics - It's Easy the first thirteen parts of our popular introductory series  
£1.20 + 15p p&p.

electronics - It's Easy Volume 2 - the next thirteen parts of our series.  
£1.20 + 15p p&p.

# TECHNICAL BOOKS FROM ETI

## CALCULATORS

- 99 WAYS TO KNOW AND USE YOUR ELECTRONIC CALCULATOR**  
L. Frenzel £4.50
- SCIENTIFIC ANALYSIS ON YOUR POCKET CALCULATOR**  
Smith £8.25

## COMPUTERS AND MICROPROCESSORS

- BEGINNER'S GUIDE TO COMPUTER LOGIC**  
G. Stapleton £1.95  
Grasp quickly computer codes, digital logic ops and switching circuits
- COMPUTER CIRCUITS AND HOW THEY WORK**  
B. Wells £1.80  
Become acquainted with the various parts of a computer and its technology
- COMPUTER TECHNICIANS HANDBOOK**  
B. Ward £3.25  
This giant volume compares to a 1,000 hour course on computer mechanics
- CONTROL ENGINEERING**  
N. M. Morris £3.70  
This is the 2nd edition of a highly successful book, keeping fully abreast of developments in control engineering
- DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS**  
N. M. Morris £2.60  
The ideal book for the enthusiast confused by logic and digital techniques
- MICROPROCESSORS** £10.80  
L. Altman  
Gives a general overview of the technology, design, ideas and practical application
- MICROPROCESSORS** £8.00  
D. C. McGlynn  
Technology, Architecture and Applications. This introduction provides a clear explanation of this important new device
- MICROPROCESSORS AND MICROCOMPUTERS** £15.90  
B. Soucek  
Describes the application programming and interfacing techniques common to all microprocessors

## ELECTRONICS

- ACTIVE FILTER COOKBOOK**  
D. Lancaster £9.75  
Everything you need to know to build and use active filters
- ELECTRONIC ENGINEERS REFERENCE BOOK — 4th EDITION**  
L. W. Turner £25.60  
A completely new and up-to-date reference book for all engineers and students
- BASIC MATHS COURSE FOR ELECTRONICS**  
M. Jacobowitz £1.75  
Quick short cut way to learn the language of maths as applied to electronics
- BEGINNERS GUIDE TO ELECTRONICS**  
T. L. Squires £2.55  
Short cut for those wishing to obtain a quick acquaintance with modern electronics
- BEGINNERS GUIDE TO TRANSISTORS**  
J. A. Reddihough £2.55  
Covers the basic theory and practice of modern transistors
- DESIGNING WITH TTL INTEGRATED CIRCUITS**  
Texas Instruments £7.65  
Covers the entire family of TTL and practical applications of circuits in digital systems
- ELECTRONIC MEASUREMENTS SIMPLIFIED**  
C. Hallmark £2.10  
Covers just about every conceivable test or measurement you will need
- ELECTRONICS POCKET BOOK**  
P. McGoldrick £4.15
- ELECTRONICS AND PHOTOGRAPHY**  
R. Brown £2.20  
Practical circuit projects devoted to photography
- ELECTRONICS SELF TAUGHT** £2.20  
J. Ashe  
Covers basic principles of electronics, includes a large number of simple circuits.
- ESSENTIAL FORMULAE FOR ELECTRICAL AND ELECTRONIC ENGINEERS**  
N. M. Morris £1.20  
Handy reference book, includes a section on S.I. units, resistor colour codes and preferred values.
- HOW TO BUILD ELECTRONIC KITS**  
V. Capel £2.10  
Instructs the kit builder on how to check components, how to assemble and how to cure faults
- FIRE AND THEFT SECURITY SYSTEMS**  
B. Wells £1.90  
Selection and installation, home maintenance and business security devices
- HANDBOOK OF IC CIRCUIT PROJECTS**  
J. Ashe £1.75  
From half circuits to complete digital counters in a single package
- HOW TO READ ELECTRONIC CIRCUIT DIAGRAMS**  
B. Brown £1.85  
Everything you need to know from basic circuit components to integrated circuits

- HOW TO BUILD PROXIMITY DETECTORS AND METAL LOCATORS**  
J. Shields £3.25  
A practical do-it-yourself book

- HOW TO USE IC CIRCUIT LOGIC ELEMENTS**  
J. Searlet £3.25  
Helps those unfamiliar with digital logic circuits

- INTEGRATED ELECTRONICS**  
J. Millman £7.16  
Using an IC approach the text leads the reader step by step from semiconductor physics to devices, models, circuits and systems

- IC OP-AMP COOKBOOK**  
W. Jung £8.25  
Covers the basic theory of IC op amps in great detail, also includes 250 practical circuit applications

- INDEXED GUIDE TO MODERN ELECTRONIC CIRCUITS**  
R. Goodman £2.23  
Practical Schematics with concise theory and troubleshooting information

- INTRODUCING ELECTRONIC SYSTEMS**  
I. R. Sinclair £1.75  
Provides a basic insight into what makes electronics 'tick'

- INSTALLING AND SERVICING ELECTRONIC PROTECTIVE SYSTEMS**  
H. Swearer £2.10  
Covers installation and servicing of all electronic security systems

- LINEAR ELECTRONIC CIRCUITS AND SYSTEMS**  
G. Birtop £2.55  
Illustrates the use of the op amp in many different applications

- LINEAR INTEGRATED CIRCUIT APPLICATIONS**  
G. Clayton £4.90  
A practical approach is emphasised throughout, encouraging the reader to try out devices himself.

- LINEAR IC PRINCIPLES EXPERIMENTS AND PROJECTS**  
E. M. Noll £5.80  
An introduction to one of electronics most exciting devices

- 110 OPERATIONAL AMPLIFIER PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85  
Outlines the essential characteristics of op amps and presents useful projects.

- 110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85  
Introduces the reader to P.E.T.s, SCR's and IC's with full construction details of many useful circuits

- 110 COSMOS DIGITAL IC PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £3.10

- 110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR**  
R. M. Marston £2.85  
All the projects have been devised, built and fully evaluated by the author

- 110 THYRISTOR PROJECTS USING SCR's**  
R. M. Marston £2.85  
A companion to the author's previous books

- MOS DIGITAL IC'S**  
G. Flynn £4.50  
This book contains information about MOS and CMOS from basic construction to circuit application

- OPERATIONAL AMPLIFIERS DESIGN AND APPLICATIONS (Buff Brown)**  
G. Tobay £5.00  
Covers the entire field of operational amplifiers

- PIN POINT TRANSISTOR TROUBLES IN 12 MINUTES**  
L. Garner £2.85  
Complete information on circuit operations, troubleshooting charts and service procedures

- PRACTICAL TRIAC/SCR PROJECTS FOR THE EXPERIMENTER**  
R. Fox £2.15  
Thyristor theory and practical circuits with low cost SCR TRIACs and DIACs

- PRINCIPLES OF TRANSISTOR CIRCUITS**  
S. Amos £4.40  
Generally accepted as being a standard textbook on fundamental principles underlying the design of circuits and using transistors

- RAPID SERVICING OF TRANSISTOR EQUIPMENT**  
G. King £2.85  
A systematic guide to the servicing of transistor radio, television tape and hi-fi equipment

- SEMICONDUCTOR CIRCUIT ELEMENTS**  
T. D. Towers £6.00  
Gives readers an account of all semiconductor devices commercially available, for each device it covers a general description, circuit diagram symbols and working principles

- SOLID STATE CIRCUIT GUIDE BOOK**  
B. Ward £2.15  
Step by step instructions to design circuits to your own specifications

- TRANSISTOR CIRCUIT DESIGN**  
Texas £7.90

- TTL COOK BOOK**  
D. Lancaster £6.00  
Complete and detailed guide to TTL, how it works, how to use it and practical applications

- UNDERSTANDING ELECTRONIC CIRCUITS**  
R. Sinclair £4.00  
Describes various circuits encountered today with a strong emphasis on fault finding and servicing procedures.

- UNDERSTANDING ELECTRONIC COMPONENTS**  
R. Sinclair £4.00  
Explains about components and bridges the gap between elementary textbooks and unapproachable advanced treatments

- UNDERSTANDING CMOS INTEGRATED CIRCUITS**  
R. Melan £3.50  
Begins with basic digital IC's, covers semiconductor physics, CMOS fabrication technology and design

- UNDERSTANDING SOLID STATE CIRCUITS**  
N. Crowhurst £1.90  
Written to service the interests of anyone at sub-engineering level

## ELECTRONIC ORGAN BOOKS

- TRANSISTOR ELECTRONIC ORGANS FOR THE AMATEUR**  
A. Douglas £4.90  
Written in a simple style, this gives a complete explanation of everything to do with transistorized organs and is profusely illustrated with clear diagrams

- THE ELECTRONIC MUSICAL INSTRUMENT MANUAL**  
A. Douglas £8.00  
A comprehensive guide to the theory and design of electronic musical instruments

- ELECTRONIC MUSIC PRODUCTION**  
A. Douglas £3.10  
A practical guide to the production of electronic music

- SEMICONDUCTOR DATA**

- INTERNATIONAL TRANSISTOR SELECTOR**  
T. D. Towers £3.75  
If it takes you longer than one minute to find out all about transistors, then you need a copy of this book.

- POPULAR VALVE/TRANSISTOR SUBSTITUTION GUIDE** £2.15  
Substitution data for both valves and transistors in one new volume

- RADIO VALVE AND SEMICONDUCTOR DATA**  
A. M. Bell £2.50  
Characteristics of 1,000 valves, cathode ray tubes, transistors, diodes, rectifiers and optical semi-conductors. This new edition (1975) is right up to date and over 450,000 copies have been sold

## RADIO AND TELEVISION

- FOUNDATIONS OF WIRELESS AND ELECTRONICS**  
M. G. Scroggie £4.35  
(New 1975 edition) Covers the whole basic theory, no previous technical knowledge is assumed

- SERVICING TRANSISTOR RADIOS**  
L. D'Auro £2.30  
Complete guide giving theory analysis and servicing techniques

- WORLD RADIO TV HANDBOOK—1976** £5.00  
Complete Directory of international radio and television and this year contains: How to listen to the world

## TEST EQUIPMENT AND OSCILLOSCOPES

- BASIC ELECTRONIC TEST PROCEDURES**  
I. M. Gottlieb £2.35  
Shows how to get accurate measurement with VOM's meters and oscilloscopes

- THE OSCILLOSCOPE**  
G. Zwick £2.10  
Starts from the first principles and takes the reader to an advanced level

- PRACTICAL TEST EQUIPMENT YOU CAN BUILD**  
W. Green £2.15  
For technicians, radio/TV service operators and serious experimenters

- RADIO, TV AND AUDIO TEST EQUIPMENT**  
G. King £4.95  
A practical guide to test instruments and applications, concerned largely with the oscilloscope

- TEST INSTRUMENTS FOR ELECTRONICS**  
M. Clifford £1.65  
Easy modifications to your VOM, VTVM and scope with the aid of this book

- WORKING WITH THE OSCILLOSCOPE**  
A. Saunders £1.85  
Includes workshop test projects with large size drawings

- SERVICING WITH THE OSCILLOSCOPE**  
G. King £5.00  
Includes a unique series of photographs showing oscilloscope traces to be found in normal and faulty equipment, stereo radio, colour TV. Circuits servicing is dealt with

### HOW TO ORDER

All prices are correct at the time of going to press but are subject to alteration without notice. All prices include postage. Please print your name and address clearly and list each title and price separately. Cheques and postal orders should be made payable to ETI Book Service. Books are sent on seven days approval against a full cash remittance plus postage. Book stock is not held at ETI's London offices and orders should be sent to ETI BOOK SERVICE, P.O. BOX 179, MAIDENHEAD, BERKS SL6 2EG.

# SEND PCB KIT £5.95

**HOW IT WORKS**



1. First rub down the board.




2. Punch through the component positions.



3. Lay down the transfer pads.



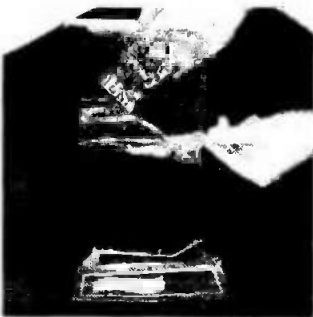4. Now use the Dalo pen to join up the circuit.



5. Into the bag, and unclip the liquid.



6. Agitate the etchant over the board.



7. When complete, reseal and wash off.



8. Rub off the transfers, and that's it!

The GS System is a complete PCB etching kit for the amateur normally selling at around £9.00. It contains, as shown below, Dalo etch-resist pen, two Polifix blocks for rubbing down and polishing boards, five sheets of etch-resist 'pads' for a neat finish, and of course the 'etching-bag' which is the heart of the system. You need never come into contact with the liquid, the entire process takes place within the thick-walled polythene bag. When the liquid loses its power, (after 10 'Euro-boards',) simply mix in the powder supplied and throw the whole thing in the bin! Simplicity itself.

Take the board-dom out of PCB's with this month's offer, and at a price which won't etch out your bank balance!



**CUT**

P.C.B. KIT OFFER  
 ETI MAGAZINE  
 36 Ebury Street, London SW1W 0LW.

Enclose cheque/P.O. for £5.95 (payable to ETI) for a P.C.B. Kit

NAME: .....

ADDRESS: .....

.....

.....

# electronics today

international


What to look for in the October issue: on sale Sept 3rd



## Build yourself a personal computer

System 68 is a powerful microcomputer which will operate without an expensive teletype or VDU. You can write, debug and run programs simply, using the system keyboard and display, and the ETI 560 VDU can be added to enhance the system I/O capability. Based on the Motorola M6800 microprocessor, System 68 is modular and can be adapted and expanded to suit your requirements and peripherals. Play computer games, solve scientific problems, control your central heating, write computer music — here's a whole new world of electronics.

## Digital Multimeter

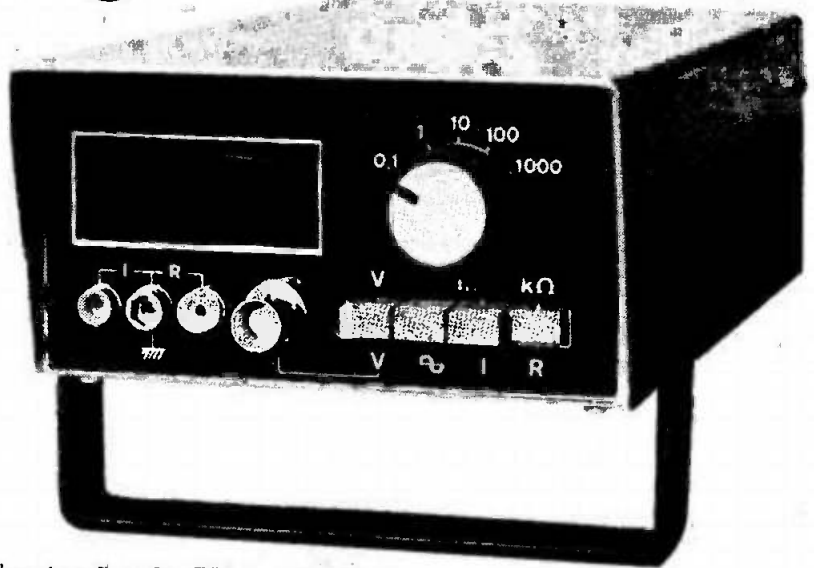


Another first for ETI — not just a DVM but a DMM with excellent spec. A 3½ digit display takes the AC/DC voltage ranges from 0.1 to 1000V plus AC/DC current from 0.1µA to 2A plus resistance readings from 0.1Ω to 2MΩ. Accuracy varies with range from 0.2% to 1%: it can be either mains or battery

operated.

The spec only should whet your appetite but the constructional design is also superb — so much so that we expect our DMM to become one of the 'standard' circuits for the amateur constructor.

## Electronics in Printing

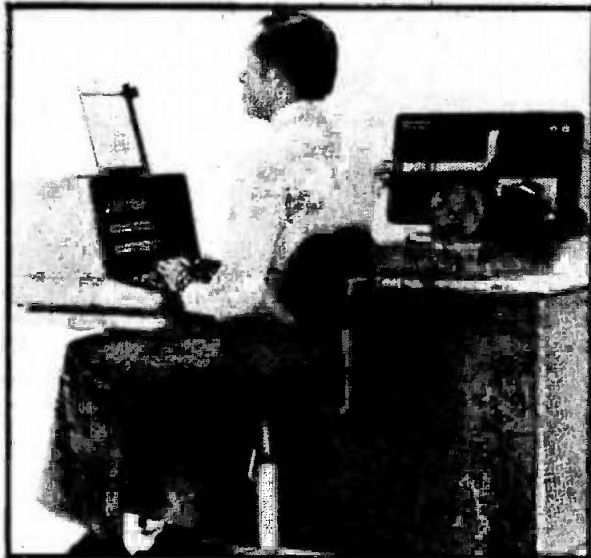

Electronics in general, and the computer in particular, is playing an ever-greater part in the production of newspapers and magazines. The newsman's world is fast becoming a world of colour VDUs, optical character recognition, microprocessing typesetters and other high technology products and processes. Read about the computer-controlled ink jet press which will soon be printing your morning paper — in next month's ETI.

## POCKET 1-2 HOUR TIMER

Many applications suggest themselves for this but the obvious one is to avoid being caught out with an expensive parking ticket. It's truly pocket-sized and operates from a PP3 battery.

## X-HATCH GENERATOR

The winning entry for last year's Doram design competition was a cross-hatch generator. We hope to give you constructional details in next month's issue.

# Modifications to the ETI CLOCK



The ETI Digital Alarm Clock now being re-offered in ETI after its successful introduction last year is a very attractive clock, but a useful additional feature would be facility to turn on a radio, instead of the buzzer, at the alarm time. (This is a more gentle way of being awakened!

Two matters which must be considered are (1) the alarm output from the CK 3000 clock chip is a pulsed audio tone, and (2), more importantly, the Pulsar uses a transformerless circuit, (Fig. 1) so that any switching output must be totally isolated from the clock circuitry.

As space inside the Pulsar case is limited, a further transformerless circuit has been designed, which offers two operating modes, (a) buzzer alarm, and (b) turn-on with buzzer silenced.

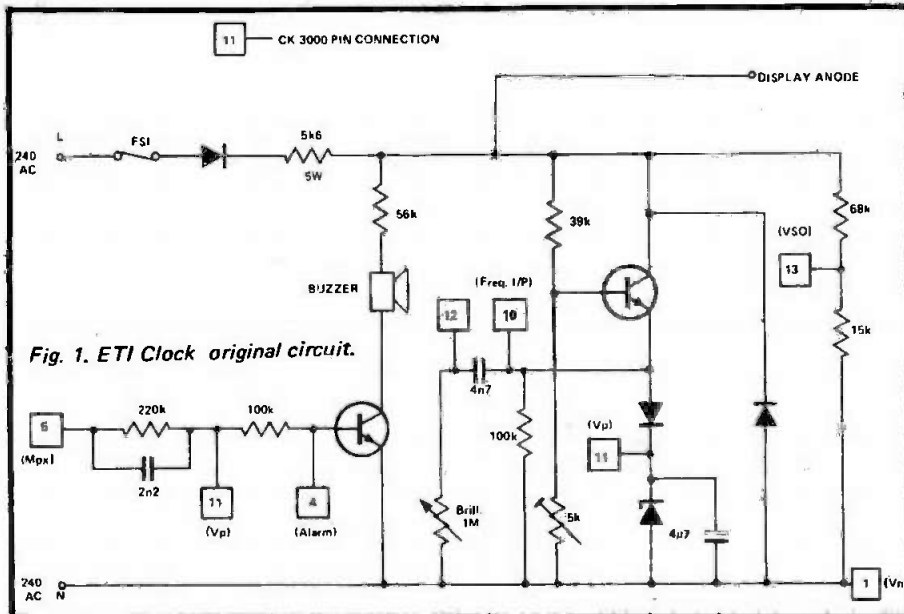


Fig. 1. ETI Clock original circuit.

## RADIO ALARM CIRCUIT

This consists of three sections, (1) a reed relay and its driver TR4, (2) a flip-flop (bistable) TR2 and TR3, and (3) a trigger transistor TR1. When TR2 is 'off', the high voltage at its collector turns TR4 'on', thus energising the reed relay. In the pre-alarm period, TR2 is 'on' whilst TR3 is 'off'. This state is set by temporarily closing S1a, which grounds TR3 base, turning TR3 off. The bistable is changed over by an AC signal from the buzzer switching transistor collector turning TR1 on momentarily, which grounds TR2's base. The blocking capacitor C1 ensures that the DC conditions of the clock chip are not disturbed.

Switch S1b is used to connect the buzzer to its driver transistor (the wire connecting the buzzer to the clock board must be cut to insert the switch). When S1 is in the 'radio' position, the buzzer is disconnected, and the flip-flop is free to toggle when the alarm output from the clock chip is energised. When S1 is in the 'alarm' position, the flip-flop is anchored in one state, and the buzzer can then operate.

Sufficient power is available from the clock chip power supply (pin 11) to operate the bistable, but not enough to energise the relay. If the relay is driven directly from the clock

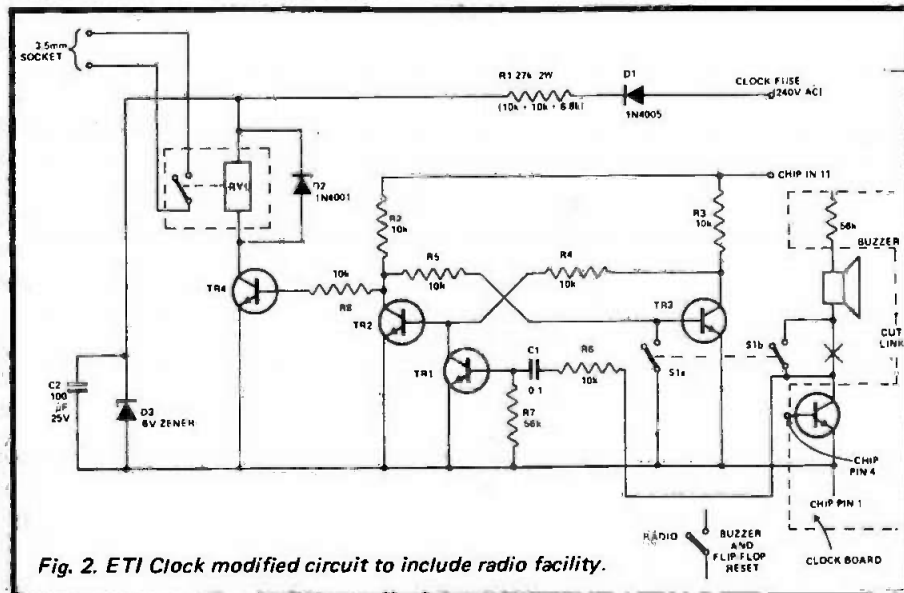


Fig. 2. ETI Clock modified circuit to include radio facility.

power supply, the ensuring voltage drop turns the clock off!

## CONSTRUCTION

A separate transformerless supply D1, R1 stabilised at 6V with D2, C2 is used for the relay. To reduce the heat dissipation, the dropper resistance R1 was selected to pass 5mA, which is sufficient to hold the relay on. Power to energise the relay is obtained from the storage capacitor C2.

The circuit was fabricated on a piece of 0.1" pitch Veroboard 3" x 1 1/2".

"We have previously sold this Digital Clock under the name Pulsar. At the time that this name was chosen by us we were unaware that the name Pulsar had been previously registered, but it has been drawn to our attention that this is the case. We have been asked to point out that our Digital Clock is not associated with Pulsar Watches, Time Computer Inc. or Pulsar S.A."

# George Hanslip shows how to interface

THE ADVANTAGES OF CMOS, namely low power consumption, high noise immunity, tolerance of wide power supply voltage variations, and the relatively higher level of integration, i.e. circuit functions per package, make it the obvious choice of logic to use in not only battery powered designs but also mains operated equipment. This is particularly so if power for the circuit is to be derived from the a.c. mains by means of a mains dropper resistor — a much cheaper solution than a mains transformer. With CMOS the total current consumption of the logic will probably be below 5mA as opposed to about 100mA for a comparable TTL design and, therefore, a low power mains dropper resistor will suffice.

Problems will, however, arise when the logic circuit has to interface with a high power a.c. load such as a mains lamp or motor. Here, two solutions are possible: a relay or a triac. The first device, a relay, uses a lot of power and currents of the order of tens of mA are required to keep the relay energised, which defeats the original object and prevents the use of a power mains dropper resistor.

## TRIAC TRIGGERING

To investigate the possibilities of using CMOS to drive triacs it would be helpful to state the triggering requirements of these devices. Triacs may be triggered into conduction on both positive and negative mains half cycles, with either polarity of gate current. They are, however, more sensitive (i.e. require less gate current) to negative gate current. Triac triggering requirements are, in fact, normally specified for gate current polarities which are in phase with the main terminal voltage, i.e. main terminal voltage positive with positive gate current and main terminal voltage negative with negative gate current. These and the gate sensitivity for the case of main terminal voltage positive with a negative gate current are equal. Triacs are generally much less sensitive to positive gate current on negative mains half cycles (i.e. main terminal voltage negative) and need to be selected for applications which require this mode of triggering. The gate current may be d.c. or a pulse since the triac will remain on once it has been triggered, until the end of the mains half cycle.

The current required to trigger a

triac will depend on the type of device used as well as the temperature. Higher power devices of 25A or greater rating may require up to 100mA to trigger while low power devices, 4A and less, may need only 10mA or less. Manufacturers generally state the maximum current required to trigger. Thus a triac type TAG250-400, for example, has a maximum gate current of 50mA and this is guaranteed to trigger all devices of this type. There will, of course, be many TAG250 devices which require a good deal less but unless the constructor has many

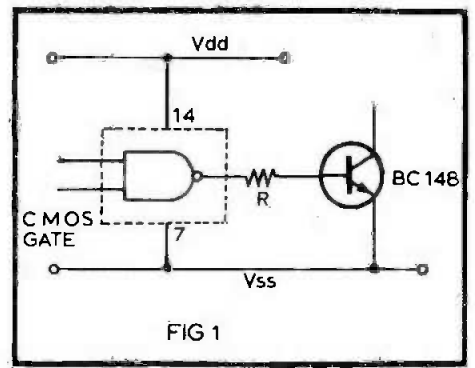


FIG 1  
The maximum current which can be supplied by CMOS devices is 10mA. Exceeding this limit will probably

# CMOS..

such devices and can choose those with lower gate current, for good reliability he should aim to provide a current of 50mA.

Before gate current can flow, a certain voltage, the gate trigger voltage must be exceeded. This for the TAG250-400 is 2.5V maximum. Thus for a worst case device, the trigger circuit must provide a voltage of at least 2.5V plus the voltage required to drive 50mA through any resistance in series with the gate.

## CMOS GATES AS DRIVERS

Unfortunately, CMOS gates, such as the 4001 or 4011, cannot provide anything like 50mA output current.

destroy the device. With a 5V supply, the output of a CMOS gate may drive a transistor base directly as the device will limit its output current to below 10mA, but above about 8V a current limiting resistor R will be required (see Figure 1).

If the output of the gate is required to maintain a recognisable logic state when supplying output current, to drive another gate for example, then the current must be limited to below 1mA. Figure 2 shows a circuit for a bistable a.c. switch.

If input "a" is momentarily connected to logic 0 (negative supply rail) the transistor will turn on

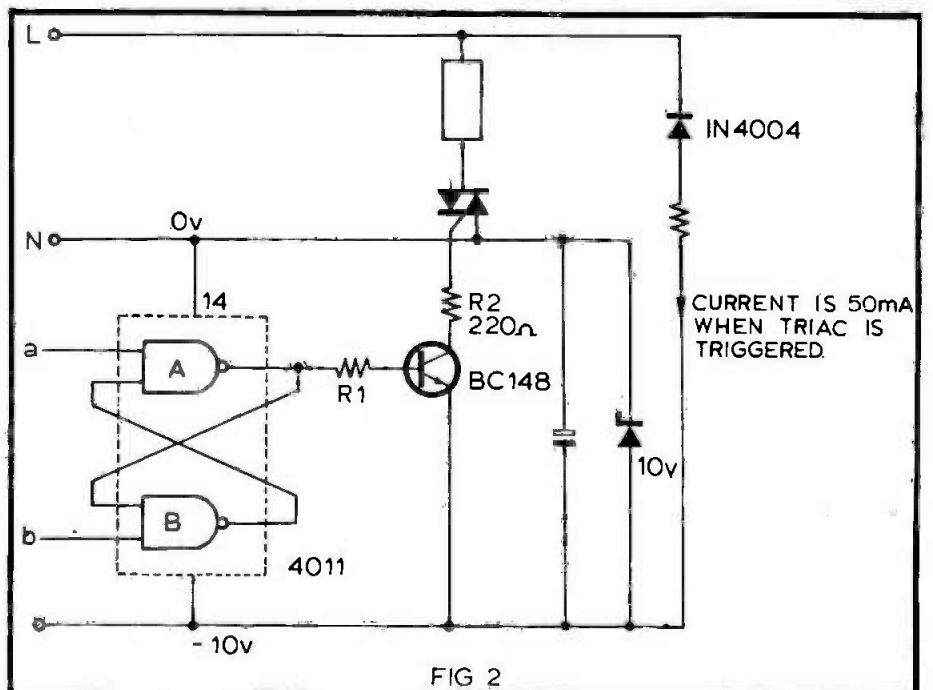



FIG 2

and trigger the triac, which will remain on until input "b" is connected to logic 0. Note that a negative supply is used to provide negative gate current for the triac. R2 is chosen to give the required 50mA gate current and R1 to give the required base current. Since gate A must drive both the transistor and present a defined logic level to gate B, the output current of gate A must be less than 1 mA giving R1 a minimum value of 10Kohm with a 10V supply. If the gain of the transistor is greater than 50, R1 may be increased in value, thus reducing further the current taken from the output of gate A.

This type of circuit, however, still draws a large current from the supply when the transistor and hence the triac is on. This current, about 50mA must, of course, come through the mains dropper and defeats the object of low current consumption. We get round this by
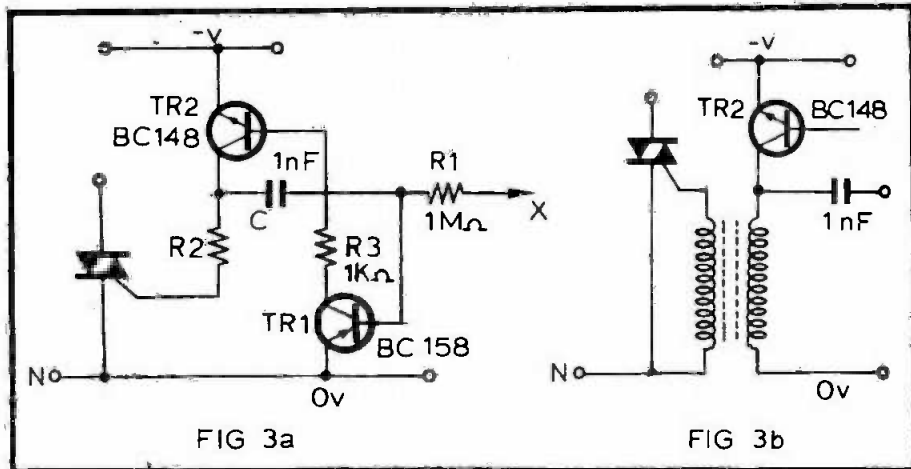
### PULSE TRIGGERING THE TRIAC

Use can be made of the fact that the triac will latch once it has been



When the circuit is not oscillating it draws very little current, and so stand-by power will be minimal.

In a circuit like this it is desirable that the frequency of the oscillator be at least 5KHz. This ensures that the triac is triggered as early as possible in each half cycle, minimising radio interference.

If isolation of the trigger circuit from the mains is required, then resistor R2 may be replaced by a transformer. This may be wound on a 3/8" diameter x 1 1/4" ferrite rod and

The negative d.c. supply for the circuit is derived from the a.c. mains supply via diode D1 and resistor R4. The zener and capacitor stabilise and smooth the supply. The zener and capacitor stabilise and smooth the supply. The zener may have a breakdown voltage of anywhere between 5V and 15V. Since the current drawn by the circuit is only 1.5mA, R4 need only be a 1/4 watt component.

If resistor R2 is replaced by a pulse transformer, then the current drawn by the circuit rises to about 2.5mA and resistor R4 may need to be reduced to 74Kohm.

### APPLICATIONS OF THE CIRCUIT

The circuit of Figure 3 forms a low power trigger circuit for triacs and is, therefore, ideal for interfacing between these devices and CMOS digital integrated circuits. The cost of the extra transistor compared to that of Figure 2 is far outweighed by the reduced cost of the mains dropper. The difficulty of synchronising the circuit with the mains makes its use in phase control circuits (such as lamp dimmers) unattractive compared to programmable unijunction transistor (P.U.T.) trigger circuits, but in ON-OFF type switching applications it is superior.

By removing the push buttons and the 100Kohm resistors from the circuit of Figure 4, the load current may be switched on by a negative pulse to the input of gate A and off by a negative going pulse to the input of gate B. By suitably decoding the outputs of a digital clock and

# ...TO MAINS

triggered. Thus the trigger current of 50mA pulses of short duration, the duty cycle of which may be such that the average current is only a few mA. The supply smoothing capacitor thus supplies the 50mA peak current while the mains dropper replaces the charge over a longer period and, therefore, needs to carry a current of only a few mA.

This is the principle behind the circuit shown in Figure 3. Transistors TR1 and TR2 form a circuit which oscillates at a frequency determined by C and R1 when point X is connected to the negative supply line. This can be done by a CMOS gate. The loading on the gate is minimal; about 10μA, but the circuit can supply 50mA pulses to the triac gate while keeping the total current consumption below 5mA.

The circuit has been used on a range of supplies from 3 to 15V with success, although, of course, less trigger current will be available with the lower supply voltages. It is, therefore advisable to use a supply voltage of at least 5V. The frequency of oscillation is also slightly dependent on the supply voltage but this is of little consequence.

consists of 10 turns of 28 swg wire for the primary and 10 turns for the secondary, insulated by a layer of PVC insulating tape.

Table 1 lists the supply current (Is) the gate current (I<sub>g</sub>) and the frequency oscillation (F) for the circuit of Figure 3 supply as measured on a prototype when the supply voltage was varied between -3V and -15V, and no voltage applied to the triac. The two cases are R2=100 ohms and 47 ohms.

The circuit together with the CMOS gates thus forms a useful a.c. power switch as shown in Figure 4. When the ON button is pushed, the triac is turned on a supplies power to the load. Since the circuit latches, the triac will remain on until the OFF button is pushed.

TABLE 1	KHz	Vs Volts	Is MA	I <sub>g</sub> MA	Frequency
R2=100Ω	3	0.15	20	5	
	6	0.32	50	5	
	9	0.45	70	5	
	12	0.6	100	5.2	
	15	0.85	120	6.25	
R2=47Ω	3	0.25	35	5.3	
	6	0.45	80	5.3	
	9	0.6	140	5.3	
	12	0.75	180	5.3	
	15	1.0	200	6.0	

# CMOS...TO MAINS

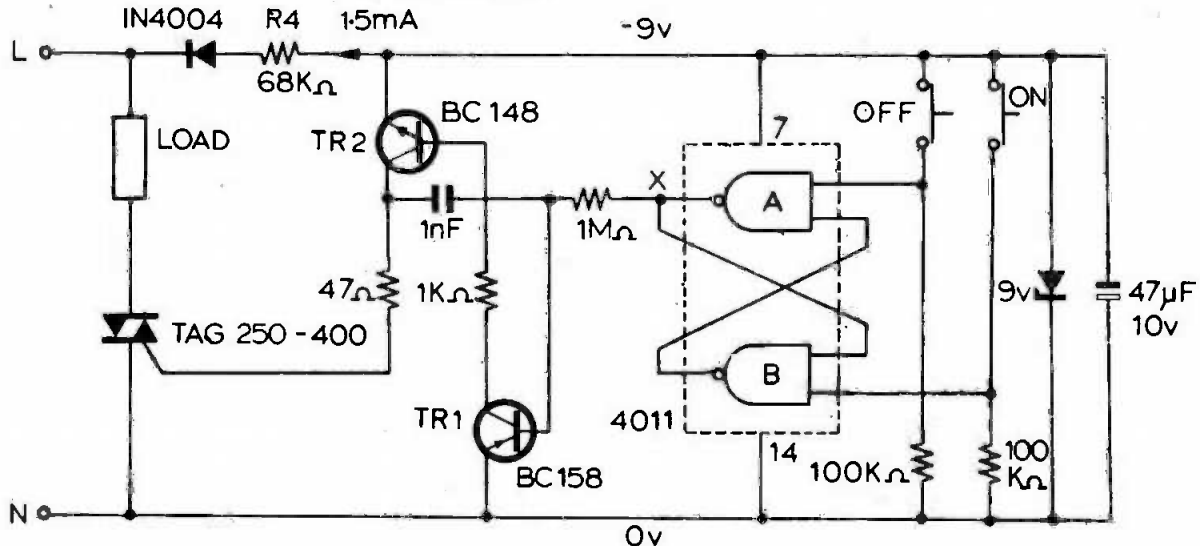


FIG 4

connecting these to gate A and B, the circuit could be used to switch mains and driven equipment such as lamps, tape recorders or central heating systems on and off at certain times. Power for the circuit could be obtained from the clock power supply line, as this would almost certainly be able to supply the small

extra current required. The use of a pulse transformer (as shown in Figure 3b) would isolate the clock and decoding circuitry from mains.

Referring to figure 3, by making TR1 a BC148 (NPN) and TR2 a BC158 (PNP) and connecting the positive supply to the emitter of TR2 and negative to TR1 emitter, the

circuit would produce positive going trigger pulses when X is connected to the positive line. The pulses applied to the triac gate could be made negative by correct phasing of the transformer windings. In this way the circuit may be used with a positive or a negative supply depending on which is available.

## LYNX ELECTRONICS (LONDON) LTD

Transistors		Diodes		ICs		Resistors		Capacitors	
BC183	10p	BF337	32p	CRS1-10	25p	2N697	12p		
AC126	15p	BC183L	10p	CRS1-20	35p	2N706	10p		
AC127	16p	BC184	11p	CRS1-40	40p	2N829	14p		
AC128	13p	BC184L	11p	CRS1-60	65p	2N930	14p		
AC128K	25p	BC207B	12p	CRS3-05	34p	2N1131	15p		
AC141	18p	BC215	11p	CRS3-10	45p	2N1132	16p		
AC141K	28p	BC212L	11p	CRS3-20	50p	2N1304	20p		
AC142	18p	BC213	12p	CRS3-40	80p	2N1305	20p		
AC142K	28p	BC213L	12p	CRS3-60	85p	2N1711	18p		
AC176	18p	BC214	14p	MJ480	80p	2N2102	44p		
AC176K	25p	BC214L	14p	MJ481	81.05	2N2369	14p		
AC187	18p	BC237	16p	MJ490	90p	2N2369A	14p		
AC187K	25p	BC238	16p	BR100	20p	2N2484	18p		
AC188	18p	BC300	34p	BRY39	40p	2N2646	50p		
AC188K	25p	BC301	34p	BSX19	16p	2N2905	18p		
AD140	50p	BC323	60p	BSX20	18p	2N2905A	22p		
AD142	50p	BC327	18p	BSX21	20p	2N2926R	10p		
AD143	48p	BC328	18p	BSY95A	12p	OA5	55p		
AD149	45p	BC337	17p	BT106	£1.00	OA90	8p		
AD161	35p	BC338	17p	BT107	£1.60	OA91	8p		
AD162	35p	BCV70	12p	BT108	£1.60	OC41	15p		
AL102	95p	BCY71	18p	BT109	£1.00	OC42	15p		
AL103	93p	BCY72	12p	BT116	£1.00	OC44	12p		
AF114	20p	BD115	55p	BU105	£1.80	OC45	10p		
AF115	20p	BD131	36p	BU105/		OC70	10p		
AF116	20p	BD132	40p		£1.90	OC71	10p		
AF117	20p	BD135	36p	BU126	£1.00	OC72	22p		
AF118	50p	BD136	38p	BY206	15p	DC84	14p		
AF139	33p	BD137	48p	BY207	20p	SC40A	73p		
AF239	37p	BD138	48p	BYX36-300		SC40B	81p		
BC107	14p	BD139	8p	BYX36-500	12p	SC40D	90p		
BC107B	16p	BD181	86p	BYX36-900	15p	SC40F	65p		
BC108	13p	BD182	82p	BYX36-900	15p	SC41A	65p		
BC109	14p	BD183	87p	BD232	60p	SC41B	70p		
BC109C	16p	BD232	60p	BD233	48p	SC41D	85p		
BC117	19p	BD237	85p	BD238	48p	SC41F	60p		
BC125	18p	BD238	85p	BYX38-		ST2	20p		
BC126	26p	BD238	80p	300	30p	TIP29A	44p		
BC141	26p	BD184	£1.20	BYX38-		TIP30A	32p		
BC142	23p	BDY20	80p	600	55p	TIP31A	54p		
BC143	23p	BDY38	80p	BYX38-		TIP32A	64p		
BC144	30p	BDY60	60p	900	80p	TIP34	£1.05		
BC147	9p	BDY61	65p	BYX38-		TIP41A	60p		
BC148	9p	BDY62	58p	1200	65p	TIP42A	72p		
BC149	9p	BF178	28p	BZX61	series	IN2069	14p		
BC152	25p	BF179	30p	zeners	20p	IN2070	16p		
BC153	18p	BF194	10p	BZX83	or	IN4001	4p		
BC157	9p	BF195	10p	BZX88	series	IN4002	5p		
BC158	9p	BF196	12p	zeners	11p	IN4003	6p		
BC159	9p	BF197	12p	C106A	40p	IN4004	7p		
BC160	32p	BF224J	18p	C106B	45p	IN4005	8p		
BC161	38p	BF244	17p	C106D	30p	IN4006	9p		
BC168B	9p	BF257	30p	C106F	35p	IN4007	16p		
BC182	11p	BF258	35p	CRS1-05	25p	2N696	14p		
BC182L	11p					2N5496	65p		

### DIGITAL DISPLAYS & LED'S

DL704	99p	DL747	1-75	2 RED LED ONLY	13p
DL707	99p	DL750	1-75	GREEN CLEAR	15p

### THYRISTORS

	8A (TO92)	1A (TO5)	3A (C106 type)	6A (TO220)	8A (TO220)	10A (TO220)
50	20	25	35	41	42	47
100	25	25	40	47	48	54
200	27	35	45	50	60	68
400	30	40	50	67	88	98
600		65	70	1-09	1-19	1-25

### TRIACS (PLASTIC TO-220 PKGE, ISOLATED TAB)

	4A		6-5A		8-5A		10A		15A	
	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)	(a)	(b)
100 V	0-60	0-60	0-70	0-70	0-70	0-70	0-83	0-83	1-01	1-01
200 V	0-84	0-84	0-75	0-75	0-87	0-87	0-87	0-87	1-17	1-17
400 V	0-77	0-78	0-80	0-83	0-87	0-87	1-13	1-13	1-70	1-74
600 V	0-96	0-99	0-87	1-01	1-21	1-20	1-42	1-50	2-11	2-17

N.B. Triacs without internal trigger diac are priced under column (a). Triacs with internal trigger diac are priced under column (b). When ordering please indicate clearly the type required.

### 74 TTL mixed prices

	1-24	25-99	100+		1-24	25-99	100+		1-24	25-99	100+
7400	14p	12p	10p	7445	85p	71p	57p	7492	87p	48p	36p
7401	14p	12p	10p	7447	81p	75p	65p	7493	45p	40p	32p
7402	14p	12p	10p	7448	75p	62p	50p	7495	87p	85p	85p
7403	15p	12p	10p	7447A	95p	83p	67p	74100	£1-00	89p	72p
7404	16p	13p	11p	7470	39p	25p	20p	74107	35p	28p	22p
7405	16p	13p	11p	7472	25p	21p	17p	74121	34p	28p	23p
7409	16p	13p	11p	7473	39p	25p	20p	74122	47p	39p	31p
7410	18p	13p	11p	7474	32p	26p	21p	74141	78p	63p	53p
7413	28p	24p	20p	7475	47p	39p	31p	74145	65p	60p	48p
7417	27p	22p	20p	7476	32p	26p	21p	74154	£1-02	£1-48	88p
7420	16p	13p	11p	7482	75p	62p	50p	74174	£1-00	83p	87p
7427	27p	22p	18p	7485	£1-30	£1-00	87p	74180	£1-06	80p	71p
7430	16p	13p	11p	7486	32p	26p	21p	74181	£3-20	£2-50	£1-89
7432	27p	22p	18p	7489	£2-92	£2-88	£2-10	74192	£1-36	£1-14	90p
7437	27p	22p	18p	7490	49p	40p	32p	74193	£1-35	£1-14	90p
7441	75p	62p	50p	7491	65p	55p	45p	74196	£1-64	£1-34	80p
7442	15p	55p	43p								

### LINEAR IC'S

301A 8 pin DIL	35p	3900 14 pin DIL	70p	565 14 pin DIL	£2-00
307	55p	709 8/14 pin DIL	35p	566 8 pin DIL	£1-90
309K	1-00	741 8/14 pin DIL	28p	567 8 pin DIL	£2-00
380 14 pin DIL	90p	748 8 pin DIL	35p		
381 14 pin DIL	1-60	555 8 pin DIL	45p	CA3046 14 pin DIL	50p

Matching clock 20p per pair. P & P 20p—Overseas 80p. CA3045 85p.

### NATIONAL CLOCK CHIPS

MM5314	£3.75	MM 5316	£5.25
--------	-------	---------	-------

(Basic clock chip giving 6 digit display) (Sophisticated device including alarm, similar to CT 7001)

HIGHAM MEAD, CHESHAM, BUCKS. Tel. (02405) 75151

VAT—Please add 8% except items marked \* which are 25%





*"We're makin' you  
an offer you can't  
refuse"*

WRP

**TAKE OUT A SUBSCRIPTION BEFORE SEPTEMBER 30th  
AND YOU CAN HAVE ANY TWO OF THESE SPECIALS FOR**



**JUST**



ETI Subs, Electronics Today,  
36 Ebury Street, London SW1W  
0LW.

Please start with the  
..... issue.

Please tick if this is a renewal

TOP PROJECTS BOOK TWO. ....

TOP PROJECTS BOOK THREE .....

ELECTRONICS - IT'S EASY 1. ....

ELECTRONICS IT'S EASY 2. ....


I enclose £5 (overseas £5.50), plus 60p for the two specials indicated,  
for the next twelve issues of ETI. Payment in Sterling only, please.

Please send me the issues indicated above; I enclose. .... which includes postage

NAME .....

ADDRESS .....

# 100W STEREO DISCO PART ONE

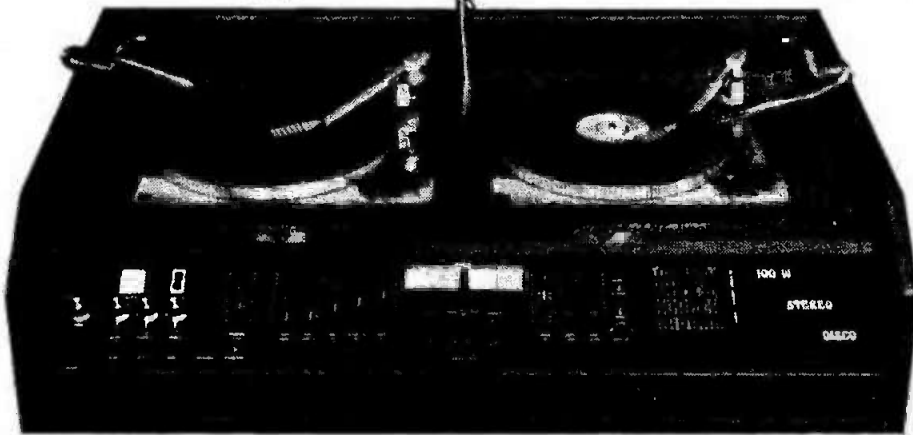

**A COMPREHENSIVE  
UNIT WITH  
BUILT IN  
LIGHT SHOW**

THE DISCO UNIT to be described here reaches professional standards at a very moderate price, only about £130 for the electronics, plus whatever decks, cartridges, etc, you should choose to add. It is designed for the home constructor, and gives many of the features found on professional equipment.

## DESIGN CONSIDERATIONS

It was decided to work as closely as possible to the following basic design parameters: the disco must be robust and simple to operate giving the deejay as much freedom as possible, whilst at the same time retaining full control. It should reach generally accepted high fidelity standards and be capable of stereophonic reproduction, to take advantage of the excellence and

range of modern recording techniques.

The unit should be capable of producing continuous high sound levels to the loudspeakers, without distress to the power amplifiers. 100W per channel should be more than sufficient in any hall in which a portable disco is likely to be used, and thus meets this condition.

Designs of good quality 100W power amplifiers are infrequently found, but rather than start from scratch it was decided to use a tried and tested design. Our own design (originally published in February 1973) was employed, but the recommended power supply was modified slightly so that the amplifiers could deliver 100W continuous rms power with both channels driven simultaneously.

**ETI PROJECT 458**

## VOICE-OVER

In order to allow the deejay his freedom it was considered that an automatic voice operated fader was essential. The deejay does not have to be continually adjusting the microphone level, and provided that a uni-directional microphone is used he will only have to set up the microphone level at the beginning of the evening. The mic will only pick up sounds made within a few inches of it, and when the deejay speaks the volume of music from any other source will be automatically reduced to an adjustable preset level. As soon as the announcement is completed the music level is automatically restored to its previous level.

The microphone should be a uni-directional (cardioid) type in order to minimise acoustic feedback, it should be hard-wearing, resistant to damage and distortion when shouted at, whilst capable of faithfully reproducing soft sounds. After careful consideration it was decided that the microphone which best met these conditions (at a reasonable price) was the electret microphone. The input on the disco was specifically designed with this type of microphone in mind therefore.

## DECISIONS DECISIONS

A decision had to be made over whether to design the disc inputs for magnetic or ceramic cartridges. After considering the advantages and limitations of both types it was

### ETI 458 DISCO: PROTOTYPE SPECIFICATION

<b>Output power:</b>	<b>4Ω load both channels driven</b>	<b>100W RMS</b>
<b>Frequency response:</b>	<b>+0.25dB—1dB</b> <b>+0.25dB—3dB</b>	<b>30Hz to 20kHz</b> <b>15Hz to 37kHz</b>
<b>Total harmonic distortion at 100W:</b>		<b>&lt;0.2% at 1kHz</b>
<b>Stereo separation:</b>		<b>50dB</b>
<b>Damping factor:</b>		<b>80</b>
<b>Sensitivity: (ref: 100W into 4Ω)</b>		
	<b>Ceramic PU</b>	<b>:88mV (&gt;2MΩ)</b>
	<b>Tape</b>	<b>100mV (50K)</b>
	<b>Aux</b>	<b>100mV (50K)</b>
	<b>Mic</b>	<b>75mV (50K)</b>
<b>Pickup overload threshold:</b>		<b>1.3V</b>
<b>Outputs:</b>		<b>Tape: 1.7v into 10K</b> <b>Pre-amp: 1V</b>
<b>Tone controls:</b>		<b>Bass ±19dB at 65Hz</b> <b>Treble ±20dB at 10kHz</b>

A complete kit of parts for this project is available from Maplin Electronic Supplies (see their ad. on the back cover).

decided to design for ceramic cartridges since for the purposes of a disco they have several advantages over their rivals and their limitations can be largely overcome by careful design of the preamplifier.

Heavy stamping on the floor near the disco could cause light tracking cartridges to join in the fun and dance across the disc whilst the heavier tracking type will remain (hopefully) in the groove. The ceramic cartridge is more robust and replacement styli for them are considerably cheaper than magnetic, with the result that they are more likely to be regularly changed leading to less significant record wear despite the heavier tracking weight.

Many ceramic cartridge inputs on amplifiers do not provide the correct loading, resulting in woolly-sounding bass and coarse hissy treble. After experimenting with various types of equalisation an input using a field effect transistor was eventually adopted. The FET gives an input impedance in excess of  $2M\Omega$  and the difference this pre-amp made was spectacular. Listening tests, comparing the sound with that of magnetic cartridges and pre-amps showed that the ceramic cartridge coupled with its FET input sounded at least as good to the designer as many medium priced magnetic pickups and better than a lot of cheap ones. The bass is firm and tight and the treble clean and extended.

#### PARTS LIST FOR POWER SUPPLY

- |   |  |
|---|--|
| R <sub>1</sub>  | 150R   |
| R <sub>2</sub>  | 150R   |
| R <sub>3</sub>  | 22K  |
| All "STD RES" 1/2W carbon film                                    |  |
| C <sub>1</sub> , C <sub>2</sub> , C <sub>3</sub>                  | 1,000 $\mu$ F @ 25V axial electrolytic                             |
| C <sub>4</sub> , C <sub>5</sub>                                   | 150 $\mu$ F @ 25V axial electrolytic                               |
| C <sub>6</sub> , C <sub>7</sub>                                   | 10,000 $\mu$ F @ 100V can type elect                               |
| VR <sub>1</sub>   | Horizontal subminiature preset 22K                                 |
| D <sub>1</sub> , D <sub>2</sub> , D <sub>3</sub> , D <sub>4</sub> | IN4002   |
| D <sub>5</sub> , D <sub>6</sub>                                   | 3A 50 PIV rectifier  |
| BR <sub>1</sub>   | Bridge 10A 200 PIV   |
| ZD <sub>1</sub> , ZD <sub>2</sub>                                 | BZX61.C. 15V   |
| T <sub>1</sub>  | 32-0-32 volts at 6 1/2 amps plus<br>12-0-12 volts 1 1/2 amps       |
| FS <sub>1</sub>   | Fuse 20 mm 3A  |
| FS <sub>2,3,4,5</sub>   | Fuse 20 mm 3A with<br>20 mm chassis holder                         |
| LP1   | Square neon  |
| SW1   | DPDT rocker switch   |
| PCB   | Disco power supply p.c.b.<br>Mains Skt SA1862<br>Mains plug SA2190 |
- (5A 3 pin mains connectors)

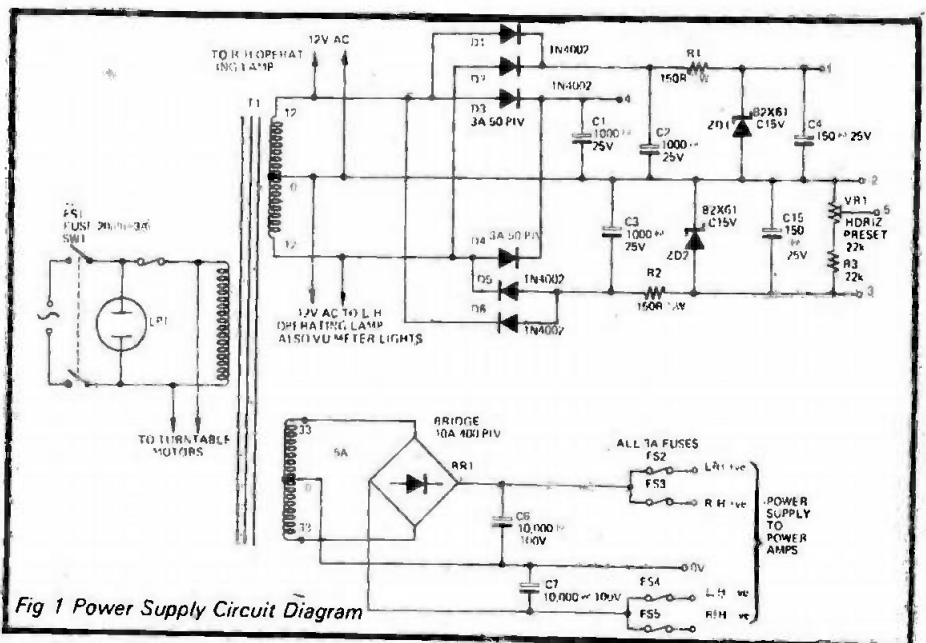


Fig 1 Power Supply Circuit Diagram

#### How it works

The power supply for the power amps is a simple, unregulated, circuit which provides all that is required — a more sophisticated circuit would make no appreciable difference to the overall result due to the symmetrical nature of the power amp output stages.

The lower voltage supply is rectified by the bridge formed by D1, 2, 5 and 6 and stabilised by ZD1 and 2 to

give the +15V and -15V supplies required by the pre-amps, monitor circuits and fader. A special negative supply for the FET's in the fader is derived from VR1 and R3. The power to the headphone amp is derived from a separate pair of rectifiers D3 and 4 in order to isolate the effect of its widely varying current requirements from the circuits requiring a stabilised supply.

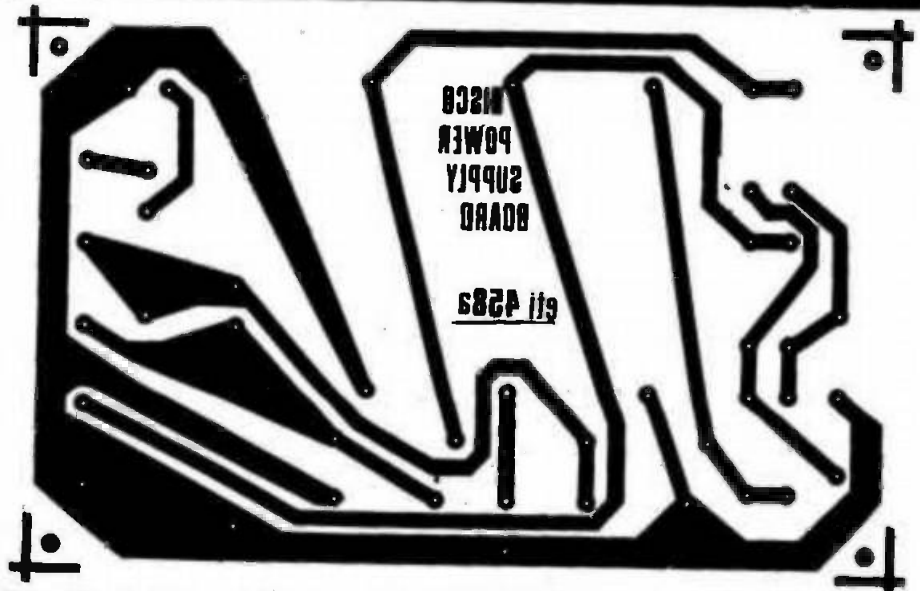


Fig 2 The P.S.U. mounted in the case

# 100W STEREO DISCO

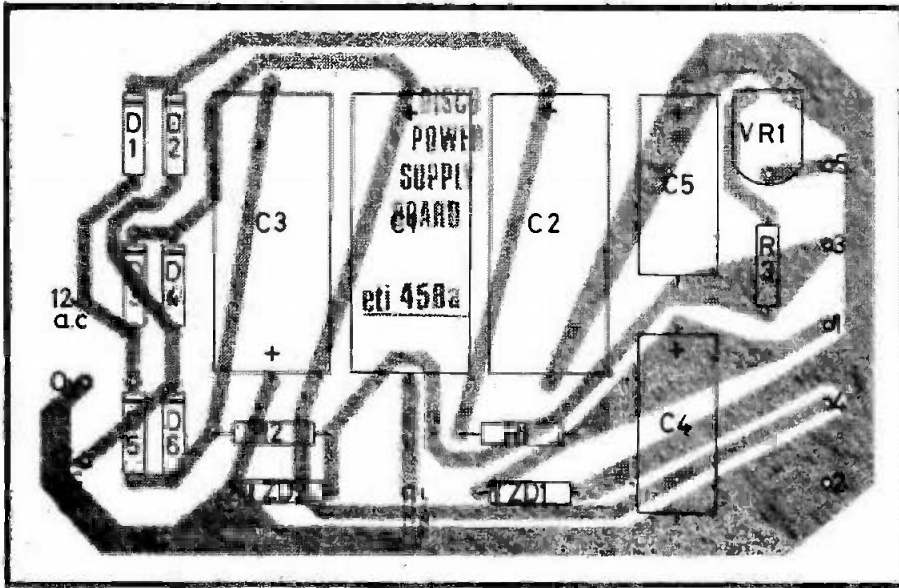


Fig 3 Component Overlay for power supply

## CUE FOR A SONG

In order to give a really professional show, the deejay must have available ways of cueing the records accurately. The monitor facilities on this disco are quite extensive, providing a headphone output which may be switched between either turntable and peak reading VU meters which can monitor the signal on the input level controls of either deck or the signal level present at the input to the power amp. Thus the level controls and master volume control can easily be set for optimum performance.

The output of the pre-amplifier can also be monitored by the headphones so that an impression of what the music sounds like in front of the speakers can be obtained by the deejay for more accurate setting of the stereo balance and tone controls.

There are various ways of cueing records — the simplest being to lower the cartridge onto the record on one deck when the record already playing on the other deck is just about to end. With the VU meters switched to show the level from the new disc, when the pick-up reaches the start of the music the meters will be deflected and the cross-fade control can be pushed over. It is a rather hit and miss method, but any overlaps or gaps in the music when crossfading could be covered up by simply speaking into the microphone when the music will automatically be faded into the background.

A better method of cueing

records with dramatic beginnings is to place the pick-up on the record being cued and revolve the turntable until the music starts (as heard on the headphones or seen on the VU meters). Turn the turntable back until the sound ceases, and then back a further one revolution. When the music on the other turntable ends push over the cross-fade and make any necessary announcement. About two seconds before you stop speaking flick on the power to the turntable motor which will pick up speed in the blank groove until reaching virtually full speed before the music begins. Switches for the turntable motors can be fitted at each end of the cross-fade control so that starting the new record can be accompanied with one hand.

## TAPE MEASURES

The deejay may wish to use a jingle machine and/or tape recordings of hard-to-get discs so the disco is equipped with tape and auxilliary inputs. These are full stereo inputs (i.e. a mono signal applied to any one input will not reduce the stereo separation of the signal on any other input). Each has its own level control and feeds into an input mixer where the various inputs are combined.

Slider controls are used on the disco mainly for the reason that they can be adjusted accurately without looking at them. With rotary controls the deejay has to be continually looking down, and quickly loses the audience's attention.

An output socket is provided so that the deejay could tape record the evening's performance if he wished. It is unaffected by the settings of the master volume or tone controls.

## Light work

Most professional discothèques employ a light show and it was decided to include a light show with this unit. A three channel circuit is used, each driving one 100W bulb in the rear of the console. The unit itself is capable of driving over 1.2kW (or 750W with spot bulbs) on each channel, but in this event it must be fed from a separate mains supply. It is not recommended that it be used to drive more than 250W per channel (including the 100W bulbs in the disco) if its mains is fed through the recommended plug and socket on the disco front panel, since this load added to the requirements of the amplifiers approaches the maximum current carrying capability of the plug and socket.

It is designed so that one channel lights when the music contains very low frequency signals, that is the light flashes in unison with the bass drum or bass guitar, one channel operates in the voice range and flashes in unison with the singer whilst the third channel flashes with the high frequencies — violins, etc. Sensitivity controls are provided on the front panel so that the on and off time of the lights can be adjusted. Three LED's are provided on the front panel and they flash in unison with the lamps so that the deejay can see immediately whether the sensitivity controls need adjustment.

## Work light

When the music slows down and the lights get low, light will be needed so that the operator can still see what he's doing. Two lights on goosenecks are provided which can be swung round as required. They have adjustable hoods so that a narrow or wide area can be illuminated. (The VU meter faces are also illuminated.)

## TURNING POINT

The choice of a turntable was governed by the consideration that it should be cheap, since two are required but should have some form of simple cueing facility with reasonable rumble and wow and flutter. With this in mind the BSR McDonald BDS80 was chosen as being the all round best buy.

## Construction of Power Amps

The circuit of one channel is shown in Fig. 6. Fit the components to the pcb as shown in Fig. 4. Note that clip-on heatsinks are required for Q3, 4 and 5 and a special heatsink is required for Q6 and 7.

Note that Q6, 7, 8, 9, 10 and 11 must be mounted using mica washers and silicone grease. The pcb is fixed to the heatsink using three 19mm stand-offs. These slot neatly into the vanes of the heatsink so that it is not necessary to drill the heatsink to fit the board. The connections to the collectors of Q8, 10 and 9 and 11, are made by means of solder tags mounted under the nuts. The solder tags are then linked in pairs and the two wires taken through the 8mm hole in the centre of the transistors. The connections between the output transistors and the pcb should be as short as possible and use 32/02 wire. By mounting the pcb as shown in the photographs the wires can be kept very short.

The heatsink should be bent to fit the board and screwed down. A type 6W-1 heatsink is required for the four output transistors

### HOW IT WORKS

The amplifier is of conventional design using a quasi-complementary symmetry output stage and a differential input stage.

Output transistors are paralleled for greater output capacity — and transistors Q6 and Q7 connected in a Darlington configuration provide current gain.

Q3 is a current regulator supplying approximately 10 mA. This controlled current passes through Q4, thus setting the bias for the output stage, and Q5. The voltage at the collector of Q5 is set by its own base-emitter voltage. Since this transistor is working with an almost constant current in its collector it has a very high voltage gain. This gain is attenuated at high frequencies by C7.

Transistor Q5 is controlled by the differential pair Q1 and Q2. Due to the negative feedback via R7 & R9, the action of Q1 and Q2 is that of an error amplifier. Thus it tries to keep the voltage at its two inputs (the bases of Q1 and Q2) constant. Because of this action, the output voltage is held equal to the input voltage multiplied by  $(R9 + R7)/R7$ . This gives the amplifier a voltage gain of approximately 2.2. This gain may be changed by varying the value of R7. An appropriate change must then also be made to C6 as R7/C6 determine the lower 3dB point. The value of R9 should not be altered.

The output bias current — which is necessary to prevent cross-over distortion — is set by RV1.

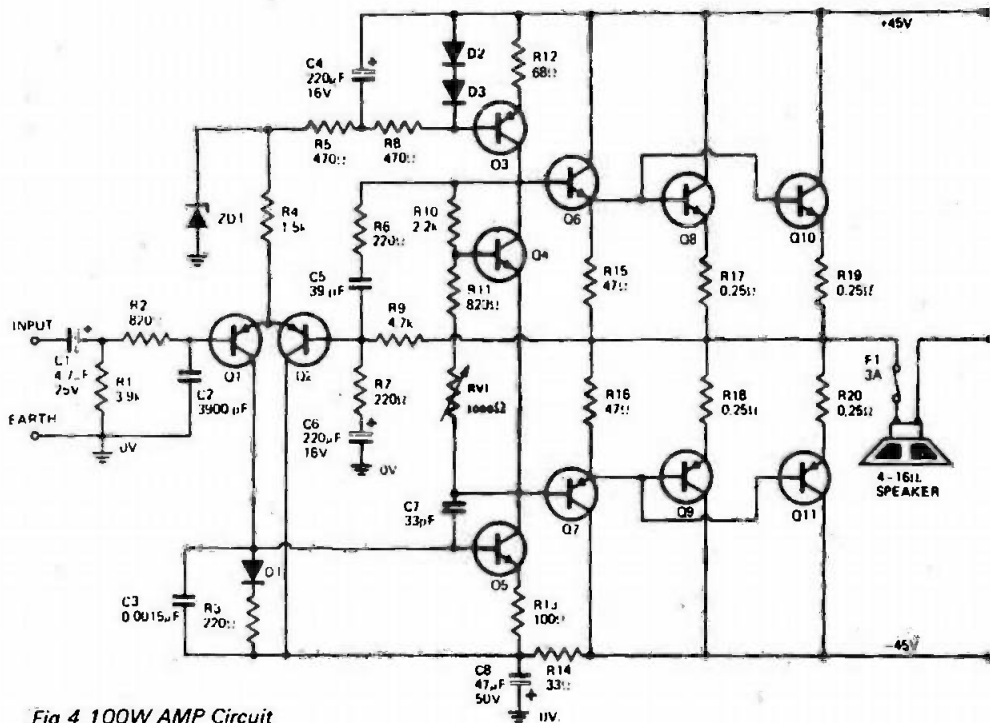


Fig 4 100W AMP Circuit

### PARTS LIST FOR 100W amp

R <sub>1</sub>	3K9	C <sub>8</sub>	47μF 50V printed circuit
R <sub>2,11</sub>	820R	C <sub>9,10</sub>	0.1μF Polyester
R <sub>3,8,7</sub>	220R	D <sub>1,2,3</sub>	IN4005
R <sub>4</sub>	1K5	ZD <sub>1</sub>	BZx61 C15V
R <sub>5</sub>	470R	Q <sub>1,2,3</sub>	BFX30
R <sub>6</sub>	4K7	Q <sub>4,5</sub>	BFY 50
R <sub>10</sub>	2K2	Q <sub>6,7</sub>	BD139
R <sub>12</sub>	68R	Q <sub>8,10</sub>	BD140
R <sub>13</sub>	100R	Q <sub>9,11</sub>	2N3055
R <sub>14</sub>	33R		
R <sub>15,16</sub>	47R		

### MISC.

All "STD res" 1/2W carbon film resistors  
R<sub>17,18,19,20</sub> 0.27R wirewound miniature 3W

RV1 Horizontal subminiature preset 470R

C<sub>1</sub> 4.7μF @63V printed circuit electrolytic  
C<sub>2</sub> 3900pF ceramic

C<sub>3</sub> 1500pF Polystyrene (ceramic)

C<sub>4,5</sub> 220μF 16V printed circuit electrolytic

C<sub>5</sub> 39pF miniature ceramic  
C<sub>7</sub> 33pF miniature ceramic

Some Veropins type 2141  
P.C. board 100W amplifier p.c.b.  
1x Jack SKT mono (plastic moulded)  
Fuse 20 mm 3A

Chassis fuse holder 20 mm  
3 "stand offs" 19 mm  
3 "heat sink clip on" for TO5 case  
1 heatsink 6W-1  
1 heat sink type DR2 (see drawing)  
4 mounting kits TO3  
some heat conducting grease  
2 mounting kits P Plas  
Double all quantities for stereo pair

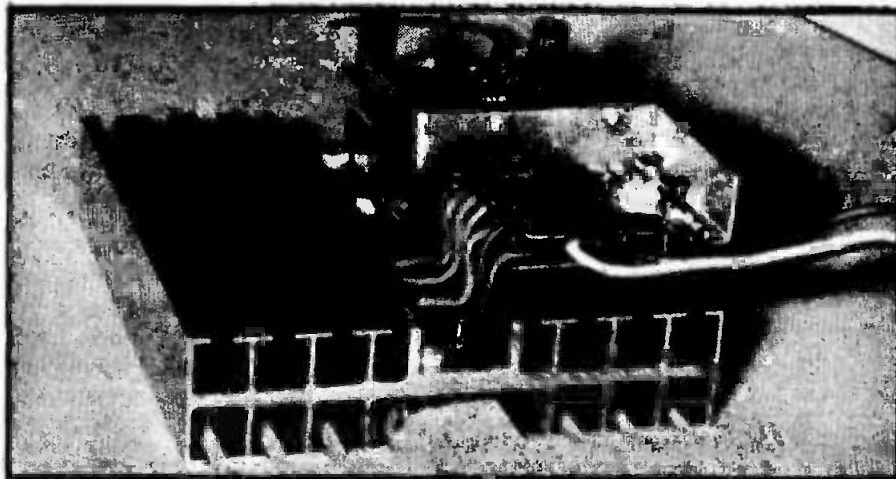


Fig 5 100W Amplifier complete and mounted

# 100W STEREO DISCO

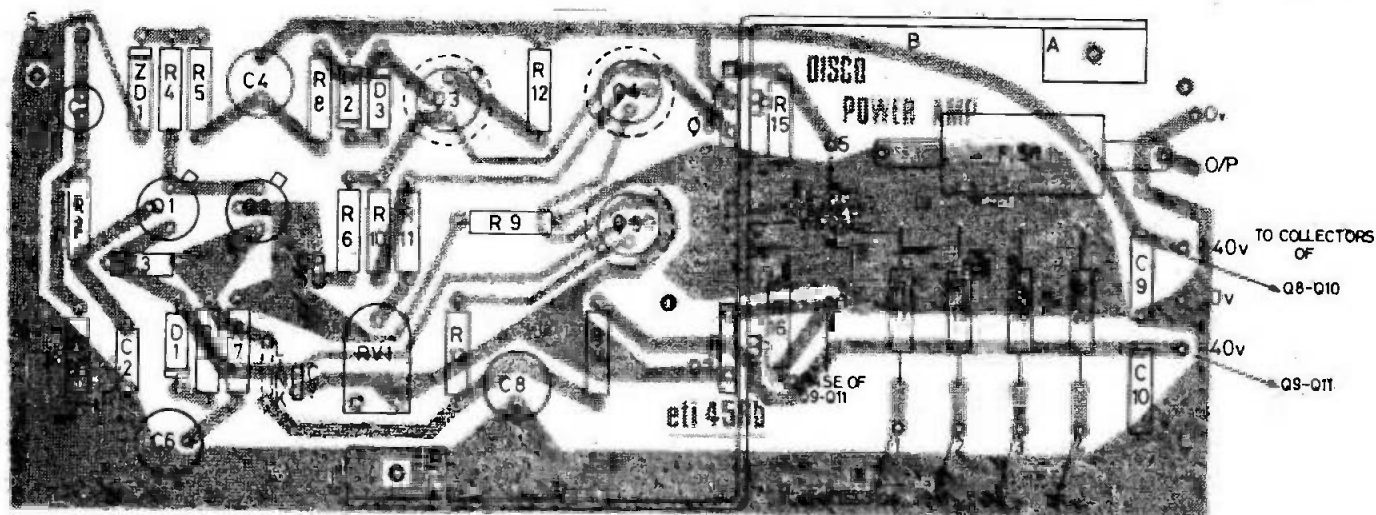
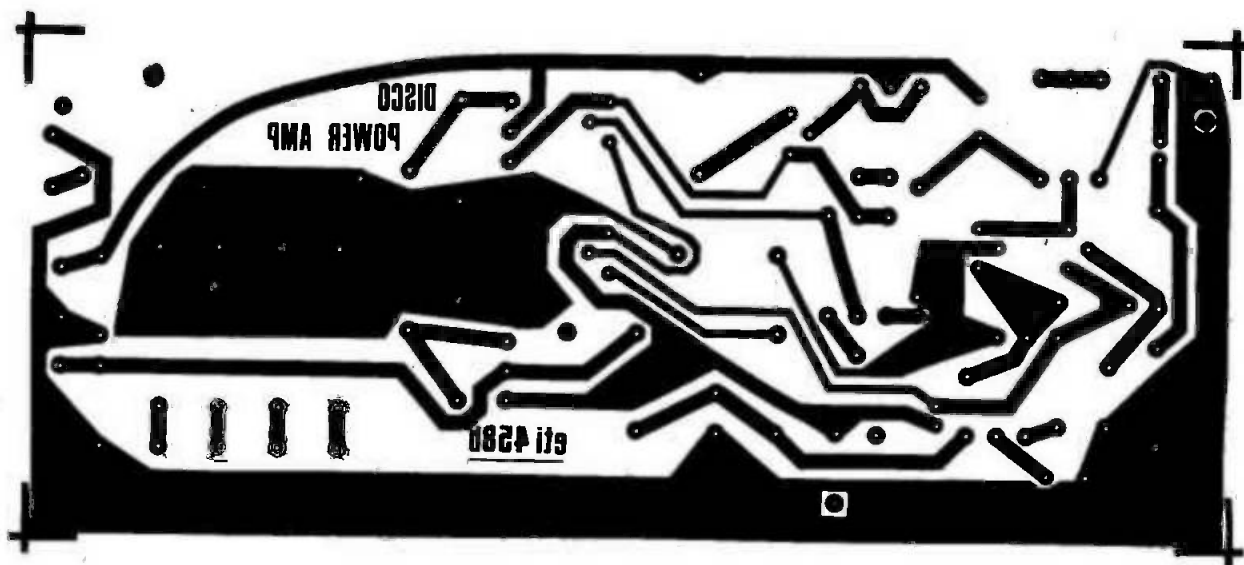


Fig 7 Component overlay for 100W Amplifier

## Setting up the Power Amps

Remove the fuse FS2 (FS3 on other channel) and connect a milliammeter in its place. Adjust RV1 so that the wiper is nearest C7 (i.e. maximum resistance). Switch the unit on and adjust RV1 until a reading of 65mA is obtained. Allow the amplifier to warm up for about five minutes and then readjust the output current for between 70 and 80mA. (Note — the current will increase as the unit warms up.) Switch the unit off and re-insert FS2 (FS3). Switch the multimeter to the volts range and check the voltage between the outputs and 0V. It should be within 200mV of zero (either polarity). If both measurements are correct the power amplifiers are working correctly.

## Construction of Power Supply

The mains transformer which must be capable of delivering a full 32-0-32 volts at 6½ amps should be bolted to the base of the console using two plates to spread the load. The circuit of the power supply is shown in Fig. 5. Fit the components to the pcb as shown in Fig. 6. Although there are two points marked 0V on the transformer these points must NOT be connected together in the power supply. The centre of C6 and C7 is the main 0V earth point for the power amps and five wires are connected here. They should all be 32/02 wire except the transformer wire. The centre tap of the 32-0-32 tapping is connected here (regarded as one wire), a wire to each power amp 0V and the

return from each loudspeaker is returned to this point **NOT** to the power amp.

Fuseholders for fuses F2, 3, 4 and 5 are fixed to the baseboard close to the power supply pcb. These are separate fuses, one for each supply of each power amp. The power for the operating lights and VU meter lights is taken directly from the 12V AC supply on the transformer.

Before connecting the power supply to the power amps check the output voltages as follows.

The voltage at

pin 1	should be +15V DC
pin 3	—15V DC
pin 4	+17 to +19V

*Continued next month with pre-amp and light show...*

# The easy way to a PCB...

...the Seno 33 system!

**33PC**

**The Dalo Pen!**  
The original fine-line etch resist marker. Simply draw the planned tracks onto the copper-clad board — new Quick-Dri inks ready for etching in minutes. Valve controlled ink dispensing for longer life. £1.50 for 1, £5.00 for 6, £9.40 for 12.

**Polifix**

**Polifix** — a unique bonded abrasive block for the clean, simple, totally effective cleaning and polishing of copper laminated boards. Degreases, removes tarnish, and 'keys' the copper surface perfectly to accept etch resist. Pack of 2 blocks £1.50, 6 £4.20, 12 £7.70.

**Seno Transfer Symbols**

**Seno etch resist transfer symbols for a truly professional finish!**  
Sharply defined, adhesive-backed symbols in easy-to-use strip form, adhere direct to copper laminate and offer total etch resistance. Presented in packs of 10 strips, each of different symbol. £2.00 per pack, £17.50 per 10 packs.

**Seno GS Etching System**


**A revolutionary solution to the problems of etching PCBs!** Unique sealed system minimises the risk, inconvenience, storage and disposal problems associated with the use of acid etchants — a complete kit designed to etch up to eight boards rapidly, visibly, effectively and SAFELY! £4.00 for a complete kit, £3.45 per kit in packs of 6.

## Seno 33 — The Laboratory in a box

From your usual component supplier or direct from:

DECON LABORATORIES LTD.  
Ellen Street, Portslade,  
Brighton BN4 1EQ  
Telephone: (0273) 414371  
Telex: IDACON BRIGHTON 87443

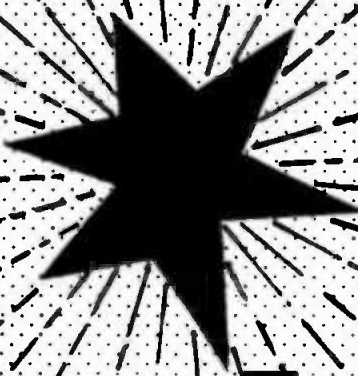All prices post & VAT inclusive. Data sheets free of charge




a star is born..

# ROTEX

## Emmen Holland

**ask for our catalogue!**

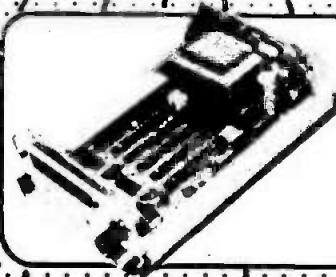

**FREQ. COUNTERS**  
RFC 30  
RFC 250

**DIGITAL  
MULTIMETERS**



**2 MTR. RECEIVERS**

**DIN-NORM**



**STEREO MIXERS 6 MODELS**



**2 M.FM  
CONVERTER**

and a large variety  
of other  
electronic modules

**LIGHTDIMMER  
700 WATT**



### sales only via wholesale dealers

## ROTEX EMMEN HOLLAND

P.O. BOX 260, TELEF. 01031\_5910\_16810 , TELEX 53910



# ETI CLOCK: £13.95

THE LONG-RUNNING OFFER ON A DIGITAL ALARM CLOCK HAS BEEN ONE OF OUR MOST SUCCESSFUL EVER! OUR PRICE INCLUDES VAT AND POST & PACKING

Our clock shows the time on 7 in bright Planar Gas Discharge displays (there is a brightness control on the back). The dot on the left of the display shows AM/PM, and the flashing (1Hz) colon shows that the alarm and clock are working.

A bleeper alarm sounds until the clock is tipped forwards. Then the 'snooze' facility can give you 5 minutes sleep before the alarm sounds again, and then another 5 minutes, etc, until you switch the alarm off. The clock also features a mains-failure indicator, and is 12hr — the alarm being 24 hour.

We have a large number of units in stock for this offer but please allow 25 days for delivery.

**CLOCK OFFER  
ETI MAGAZINE  
36 Ebury Street.**

I enclose cheque/P.O. for £13.95 (payable to ETI) for an Alarm Clock. Please write your name and address on the back of your cheque to speed processing of your order.

Those not wishing to cut their magazine may order on their own notepaper.

Follow us on across the

We have previously sold this Digital Clock under the name Pulsar. As you may know that this name was chosen by us for our watches that the name Pulsar had been previously registered, but it has been drawn to our attention that this is the case. We have been asked to point out that our Digital Clock is not associated with Pulsar Watches. Time Computers Inc. or Pulsar S.A.



# ETI WATCH OFFER £18.95

A five function digital watch for under £19 is our new offer to readers. A gold plated, LED display 5 function watch at the VERY special price of £18.95 inclusive of VAT, postage and packing (normal price £23.75).

As well as hours/minutes (with AM/PM indicator), day/date and seconds, you also get a guarantee which in this case is no small addition!

- Two years cover — repairer replacement on any watch developing a fault within two years of purchase.
- Free calibration check at the end of each of the first 3 years.

**WATCH OFFER  
ETI MAGAZINE**

36 Ebury Street, London SW1W 0LW.

I enclose cheque/P.O. for £18.95 (payable to ETI) for a Digital Watch.

NAME .....


ADDRESS .....

Those not wishing to cut their magazine may order on their own notepaper.

# TOSHIBA ST-910

**MEASURED PERFORMANCE OF TOSHIBA ST-910 FM TUNER**  
S/N 52530001

Sensitivity (IHF Method)	1.5 $\mu$ V
Distortion Factor (500 Hz & 100% Modulation)	> 0.3%
Signal Noise Ratio	> 60 dB
Frequency Response	$\pm 0.5$ dB 20 Hz - 15 kHz
Selectivity	> 80 dB
Image Rejection Ratio	> 80 dB
IF Rejection Ratio	> 80 dB
Capture Ratio	> 1.5 dB
FM Stereo Separation	> 30 dB
Dimensions	450 mm x 136 mm x 340 mm
Weight	8 kg

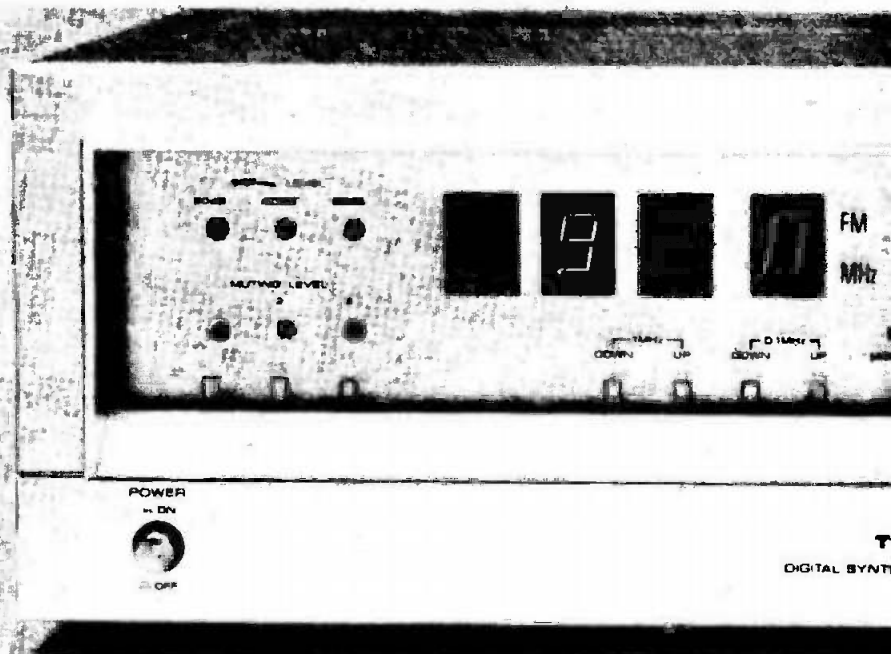

The Toshiba ST910 is quite unlike any other piece of hi-fi equipment that we have previously seen. To start with there's not a single visible control apart from an ON/OFF switch. All other control functions are effected via capacitive touch switches, the positions for which are marked on the rear of the front glass panel forming most of the unit's front face.

The glass panel itself is divided into six sections which are from left to right; a signal level-indicating section consisting of six LED's, the top three being red LED's indicating signal level at +20 dB, +40 dB and +60 dB re 1  $\mu$ V; whilst the lower three LED's (which are green in colour) indicate

the muting level that has been selected as the threshold level for the receiver to respond to. These are activated by touching the capacitive switches indicated below them. To the right of this section is a four digit display of FM frequency. This uses 7-segment LED displays for showing the frequency to which the receiver is tuned. The first three digits indicate the frequency in MHz, whilst the last digit indicates the frequency in 100 kHz increments.

Immediately below the digital display are two capacitive touch switches which enable the frequency to be increased up or down by 1 MHz steps. Two further capacitive touch

switches allow the frequency to be increased up or down by 0.1 MHz steps. Immediately to the right of these is a memory switch which allows subsequently required stations to be preset by a series of IC devices. When this switch is touched, the green indicator lamp is turned on. It is also necessary to touch one of the adjacent sensor panel capacitive switches, whose indicating LED is turned on by the process. Thereafter, all that is necessary to recall the memorised frequency is to touch one of the seven selected sensor channels switches. We found however that the memory would only 'hold' preselected stations for about two days.

To the right of the sensor channel switch positions is the auto-tuning section. This has a down-start capacitive selector switch, an up-start capacitive selector switch, and stereo-only capacitive selector switch.

## DOWN START

The down-start starts the receiver searching down in frequency till it finds a signal the level of which is above the muting level (or sensitivity level) which has been pre-set. The up-start button does the same, but in the reverse direction. The stereo-only selector accepts only those stations having a 38 kHz or 19 kHz sub-carrier signal in their format.

At the extreme right hand end of the escutcheon is the stereo/monophonic indicator. When the capacitive touch switch is activated the green, monophonic light comes on, the red stereo light is extinguished and the


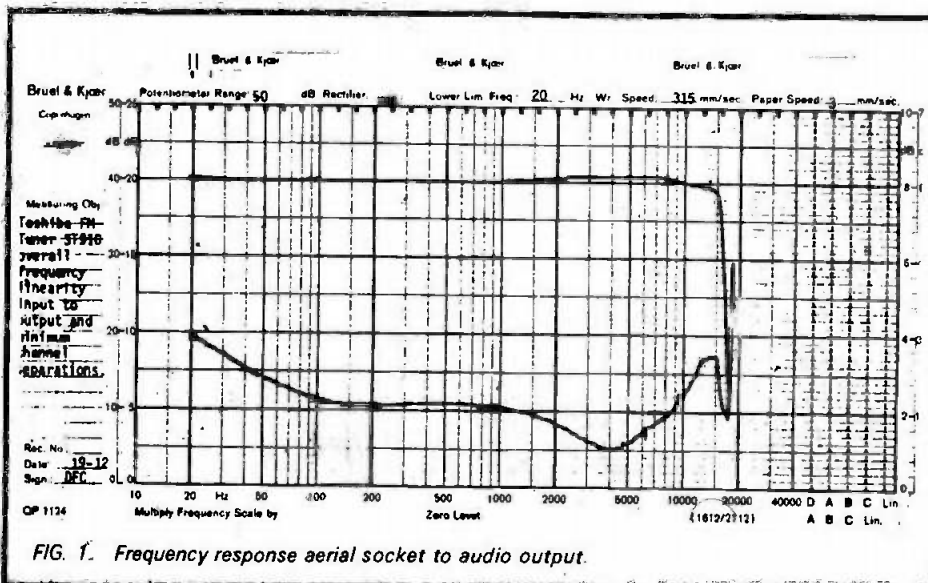


FIG. 1. Frequency response aerial socket to audio output.

# DIGITAL TUNER

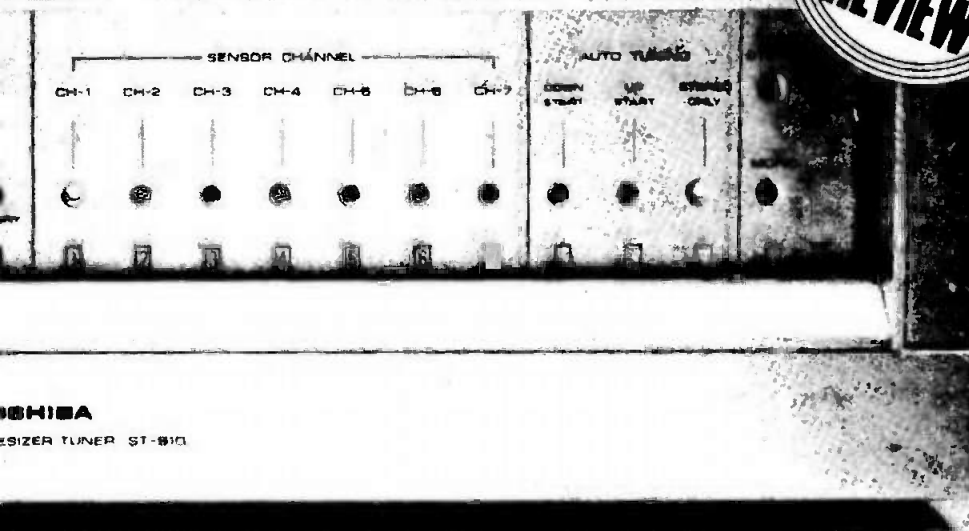

## Toshibas £535 super-tuner under the microscope

tuner looks for monophonic stations only.

The back panel is a little different from other FM receivers in that as well as input terminals for either 300  $\Omega$  feeder cable or 75  $\Omega$  co-axial cable, it provides output terminals for left and right channels; a multiplex output terminal to facilitate four channel reception in the unlikely event that somebody proposes introducing it; a remote control DIN plug to facilitate the use of special remote control offered as an optional extra; an output level control which allows the setting of the audio line output levels; and a scanning speed control knob which allows the automatic tuning operation to vary between approximately 0.05 MHz/sec. to approximately 3 MHz/sec. scanning rate.

Another most interesting facility are two terminals which can be respectively connected to the horizontal and vertical axes of an oscilloscope to measure and minimise multi-path reception and thereby optimise signal quality. The handbook describes very simply yet practically, how this should be carried out.

### DIGITAL FREQUENCY SYNTHESIZER

The heart of the ST910 is a digital frequency synthesizer based on a quartz crystal oscillator. This provides accurate and stable frequencies, replacing the normal variable frequency oscillator, to provide extremely accurate signal tuning. When used in conjunction with the phase locked loop, this provides an extremely precise and stable frequency tuning section. The great advantage of such a combined system is that the tuner receive frequency is extremely accurate (without the need for automatic frequency control) and nearly equal to the precision provided by the quartz crystal oscillator used in the original transmitting station.

Frequency stability claimed for the synthesizer section is better than 50 parts per 1,000,000 — subject to the period of operation and thermal conditions in which the receiver is used.

The inside of the receiver is more reminiscent of communication receiver construction and design than a piece

of consumer electronics. Firstly, it makes use of a 300 mm x 240 mm mother card which is connected by plug-in sockets to the front circuit board on which are located the digital frequency display, the LED's and the capacitive touch switches. On the main section of the mother board are additional vertically mounted plug-in cards comprising the power supply, the digital memory sections, the frequency synthesizer and its crystal ovens and three cards on which are mounted the very high quality FM receiver.

An input pre-filter reduces the effect of unwanted high level AM signals on the following electronic circuitry.

### PERFORMANCE CREDITS

Toshiba claim a frequency response of 20 Hz to 15 kHz  $\pm$  0.5 dB. And that is exactly what we found in our testing.

Image rejection ratios and IF rejection ratios of 100 dB are also claimed, we couldn't confirm that these were 100 dB but they were certainly better than 80 dB. Toshiba claim a capture ratio of 1.5 dB, we found it to be slightly better than this. They also claim a FM stereo separation of 40 dB in the range of 100 Hz to 8 kHz — we certainly measured better than 30 dB, and if allowance is made for the performance of our signal generator the claim of 40 dB separation would be very near the mark.

The calibrated sensitivity signal level LED's which are supposedly 20 dB, 40 dB and 60 dB re 1  $\mu$ V are spot on at the 20 dB and 40 dB levels, and 57 dB for the 50 dB indicator. The major sensitivity on monophonic signals was 1.5  $\mu$ V which is better than the manufacturers' claim. Total harmonic distortion was (delightfully) less than 0.3% which is as good as one could ask for.

After all this one might well ask how does the unit perform. Its listening performance is Grade A. We could in no way fault it, except for the minor possible criticisms that with digital frequencies set at 0.1 MHz intervals, one could possibly find oneself in a situation where the receiver was not tuned *exactly* to the station one was looking for and that on our review unit at least the preset tuning was effective for only a day or so before it needed to be reset.

We listened to all the available programme content we could find, the performance was in all respects almost perfect.

Is it really worth £535? This is for you to decide — but you'll buy nothing approaching it for less. ●

# BREAKDOWN BEACON

AN ESSENTIAL DEVICE FOR ANY  
CAR OWNER.....

THE BREAKDOWN BEACON IS A dual purpose device. It can be used atop a disabled motor vehicle as a flashing warning to other traffic — a highly desirable safety device. Alternatively it can be used as a non-flashing trouble light for finding and fixing faults at night. Its three rubber-sucker feet will hold it to the roof of a car, to the underside of a bonnet, or to any other convenient flat surface.

The circuit operates from the vehicle's battery and, as all electrical parts are isolated from the metal case, the same circuit can be used for cars with either negative or positive earth wiring systems. The beacon is fed from a plug pushed into the cigarette lighter socket — however as this plug is polarised, a beacon with a plug for negative earth cannot be used in a car with opposite polarity unless the plug connections are reversed. Alternatively it could be powered from the car battery.

## CONSTRUCTION

The nicest thing about the construction of this project is that first you have to eat half a pound of jam, in order to get the empty glass jar for the lamp housing. Other jars about 70mm dia. and 70mm high with a twist off cap would do. You'll need also a round tobacco tin about 75–80mm dia. and 30mm high with a twist off cap. These two parts make up the case.

First solder the lids of the jar and the tin together, concentrically — outside to outside. Then before fitting the batten lamp holder fit the lamp to it and check that it will fit inside the jar when the jar is screwed into its lid. If it will, then mount the lamp holder by three bolts through both lids. Two of these bolts should be longer than the third as they will carry a piece of Veroboard. If the jar is slightly too short to accept the lamp holder and lamp — as was the case in the proto-


type — then cut a hole for the lamp holder through both lids, and fit the lamp holder so that its flange finishes up inside the tobacco tin. Spacing washers may be added if necessary. Again the lamp holder is secured to the lids with one short and two long bolts.

The electronic part of the beacon is constructed on 0.1 inch matrix Veroboard 45mm x 36mm. Only one break needs to be cut in the copper strips — between the two leads of capacitor C. Only the outer legs of RV1, are passed through the Veroboard. The centre leg is connected to either outer leg above the board and the excess cut off. Note that all resistors except R5 are vertically

mounted. The upper end of R4 is soldered straight on to the base terminal of Q2, and the upper end of R3 is soldered straight on to the collector. A wire is also run from the collector terminal of Q2 through the board to the strip below it. Another wire is run from the emitter terminal of Q2 to the negative rail which is the copper strip just below.


The Veroboard is mounted into the case below the lamp holder, using two of the lamp holder mounting bolts.

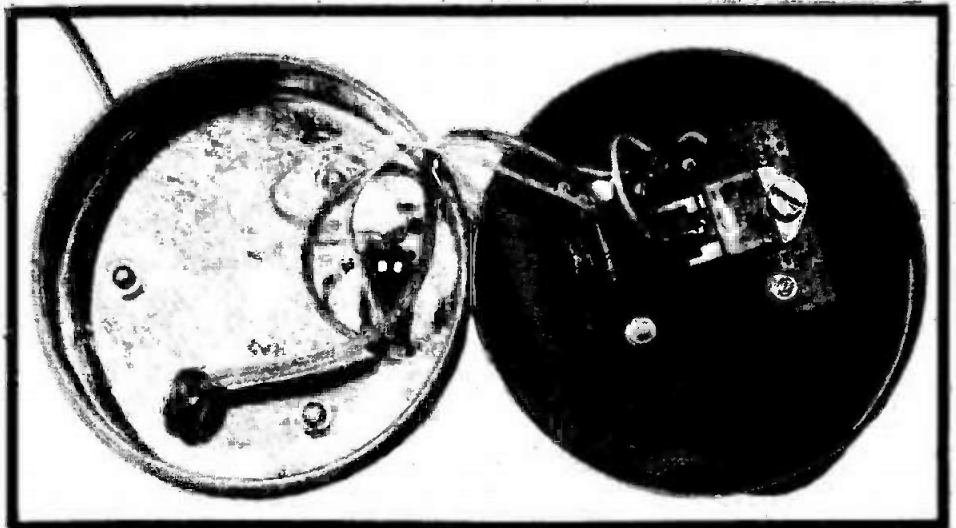The switch SW1 is mounted on the bottom of the tobacco tin where it is out of the weather. The switch must be positioned such that it does not clash with the components on the Veroboard when the tobacco tin is screwed



Inside view of the completed unit. Note the plastic disc used to replace the normal airtight seal of the jar.

**Project**  
**239**

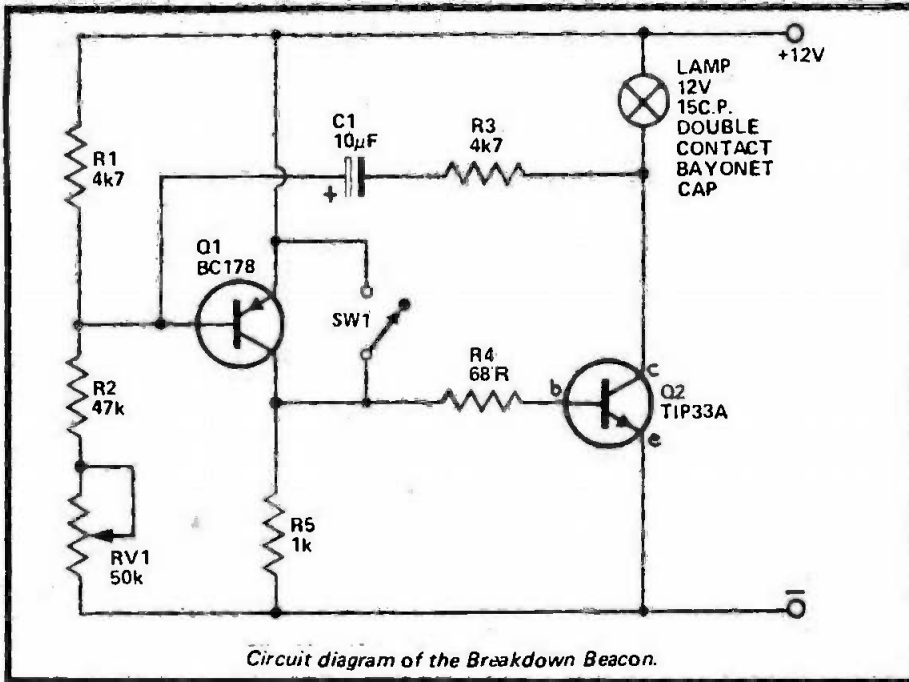

### PARTS LIST - ETI 239

R1	Resistor	4k7	¼ watt	Lamp	12 volt automotive lamp 15 candlepower double contact cap.
R2	"	47k	"	Lampholder	to suit lamp, batten mounting, double contact bayonet catch type. (This is an electricians line not an automotive line. They are used for pilot lamps).
R3	"	4k7	"	Tobacco tin, jam jar, or similar.	Nuts and bolts, hook up wire.
R4	"	68R	"	Lead to battery	— 7 m speaker extension lead.
R5	"	1k	"	Cigarette-lighter plug.	
RV1	Preset pot	50k			
C	Electrolytic capacitor	10 µF	at least 15 volts		
Q1	Transistor PNP	BC 178	or similar		
Q2	Transistor NPN	TI P33A	or similar		
SW1	small on/off slider switch,	single pole			

### HOW IT WORKS

The circuit is an oscillator of a not very common type. It is *not* a multivibrator as both transistors conduct at the same time, rather than alternately as in a multivibrator. Most explanations of this type of circuit state that the circuit oscillates by a regenerative action from Q2 to Q1. This doesn't really explain how it works, so perhaps the following is a little clearer.


The setting of the pot RV1 is such that when power is first applied Q1 is turned on slightly. By varying RV1 the circuit can be made to 'lock' with the lamp on or off. In between these extremes the circuit oscillates. The setting of RV1 is not critical.

As said above, when power is applied Q1 turns on slightly. Current through Q1 feeds into the base of Q2 and turns it on. Capacitor C charges, through R1, R3 and Q2. This increases the current through R1 and so lowers the voltage at the base of Q1 thus turning it on harder — hard enough to turn Q2 full on and light the lamp.

As C charges, the voltage at the base of Q1 rises and so tends to turn Q1 off, thus reducing the base current in Q2 and hence the current through the lamp. This increases the voltage across Q2 quite rapidly. As the voltage across the capacitor cannot be changed rapidly, the increase of voltage across Q2, i.e. the voltage charge at the collector of Q2, is transferred through the capacitor to the base of Q1 — so turning it off. This turns Q2 hard off. The voltage at the collector of Q2 then rises rapidly to 12 volts, so the voltage at the base of Q1 is forced up through capacitor C, turning Q1 hard off.

Capacitor C then discharges round R1, the lamp, and R3 until, when fully discharged, Q1 turns on slightly and the cycle is repeated.

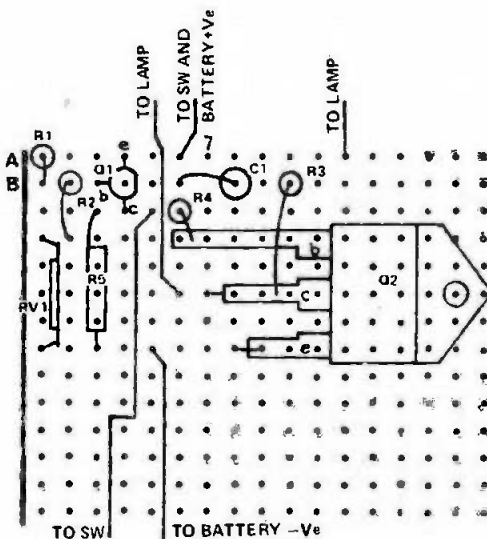The switch SW1 (connected across Q1) is used to disable Q1 and so give a steady light when SW1 is closed.



Veroboard layout for the beacon circuit. The copper strips run from left to right across the board. Only one break is required, and this is at B7.

It is likely that the operation of soldering the two lids together will have destroyed the air-tight seals in the jar and tin; they should be replaced with a disc in the tin and a ring in the jar cut from fairly heavy plastic sheeting.

### TESTING

Before connecting up make sure that switch SW1 is open — otherwise the unit will not flash.

Connect the unit to the battery by inserting the plug into the cigarette lighter socket. It may now be found that RV1 needs some adjustment to

make the circuit operate correctly, so don't be disappointed if the lamp does not light at first or alternatively, stays on all the time. The flashing rate may be altered by changing either C or R3 if thought necessary. About 70 to 100 flashes per minute is right.

The value of R4 shown in the circuit was selected to suit the transistor Q2 used in our prototype. If the lamp lights at less than full brilliance then R4 may be reduced until Q2 saturates and the lamp is turned on fully.

### USE

The illustration shows the prototype with a clear glass 'lens'. This is ideal when the beacon is used as a trouble light — turned permanently on. However, if it is thought desirable to have an amber or red colour when the beacon is flashing, then it is a simple matter to make a sleeve of suitable coloured material to be dropped inside the jar. ●

# DORAM

A PROFESSIONAL DEAL  
FOR AMATEURS


Over 50,000 customers  
REGULARLY SERVICED

**NEW**  
**CATALOGUE**  
Edition 3

DORAM'S NEW CATALOGUE HAS BEEN SPECIFICALLY DESIGNED FOR THE AMATEUR RADIO, ELECTRONICS & HI-FI ENTHUSIAST.

DORAM'S SERVICE ALSO INCLUDES -

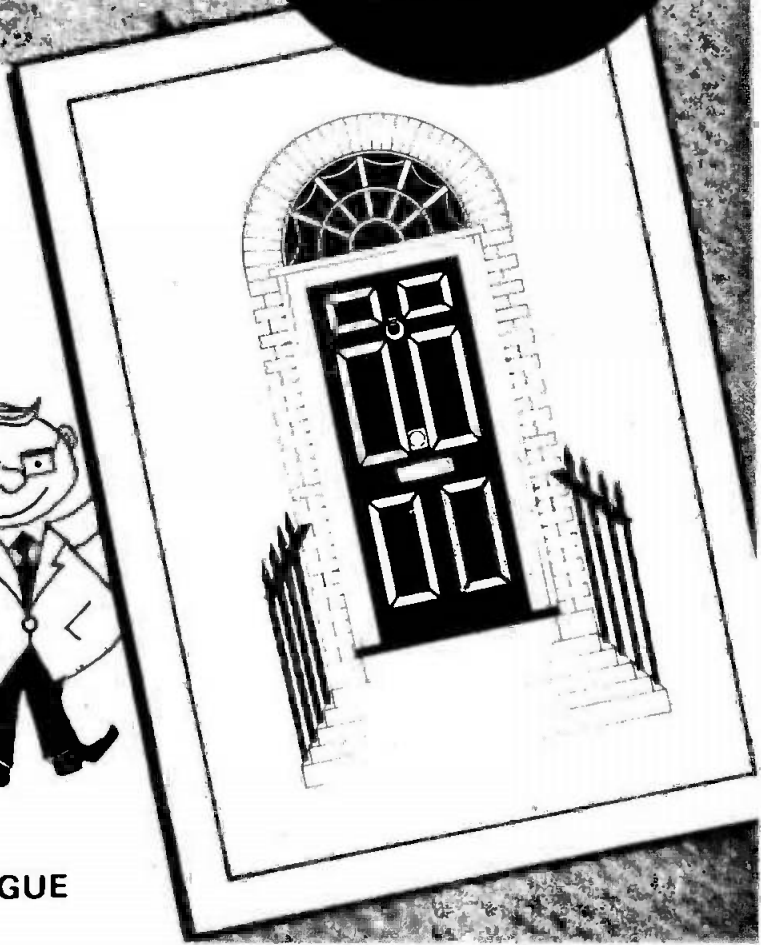- ★ MANY PRICE REDUCTIONS - QUANTITY DISCOUNTS ON CAPACITOR, RESISTOR OR SEMI-CONDUCTOR ORDERS
- ★ **FREE** - UP-DATE PRODUCT INFORMATION SERVICE DURING LIFE SPAN OF CATALOGUE
- ★ ALL ORDERS SENT BY RETURN-OF-POST
- ★ NO-QUIBBLE REPLACEMENT PART SERVICE
- ★ **POST & PACKING FREE FOR ORDERS OVER £1** (Only applies for Great Britain N.Ireland and B.F.P.O. Nos.- Overseas orders F.O.B.)



**SEND FOR YOUR NEW CATALOGUE AND/OR KIT BROCHURE NOW!**

If catalogue ordered (priced 60p) you will receive a refund voucher of 25p.

If catalogue and kit brochure ordered together, price 70p plus 2 x 25p refund vouchers.

DORAM ELECTRONICS LTD.  
P.O. Box TR8,  
Leeds, LS12 2UF.

I enclose ..... Please send me by return my new catalogue and/or kit brochure. (Over seas orders except for N.Ireland please add 30p for post and packing surface only.

ETI - 9/76

PLEASE PRINT BLOCK CAPITALS

NAME: .....

ADDRESS: .....

..... POST CODE.....

An Electrocomponents Group Company

# ETI DATA SHEET

## LM 3909 IC OSCILLATOR/FLASHER


NATIONAL

Most linear integrated circuits are designed to operate with power supplies of 4.5 to 40 V. Practically no battery/portable equipment is provided with indicator lights due to unacceptable power drain. Even LEDs (solid state lamps) won't light from a 1.5 V battery, and drain the common 9 V radio battery in a few hours.

The LM3909 changes all this. Obtaining long life from a single 1.5 V cell, it opens a whole new area of applications for linear integrated circuits. Sufficient voltage for flashing a light emitting diode is generated with cell voltage down to 1.1 V. In such low duty cycle applications batteries will last for months to years of continuous operation. Such flasher circuits then become practical for marking location of flashlights, emergency equipment, and boat mooring floats in the dark.

With 1.5 V supplies, certain problems can occur to stop oscillation or flashing. Due to the way gain is achieved and the type of feedback, too heavy a load may stop an LM3909 from oscillating. 20  $\Omega$  of pure resistive load will sometimes do it. Strangely enough, lamp filaments, probably because of some inductance, don't seem to follow this rule. Also in flasher circuits, an LED with leakage or conductivity between 0.9 and 1.2 V will stop the LM3909. Maybe 1% of LEDs will have this defect because they are not often tested for it.

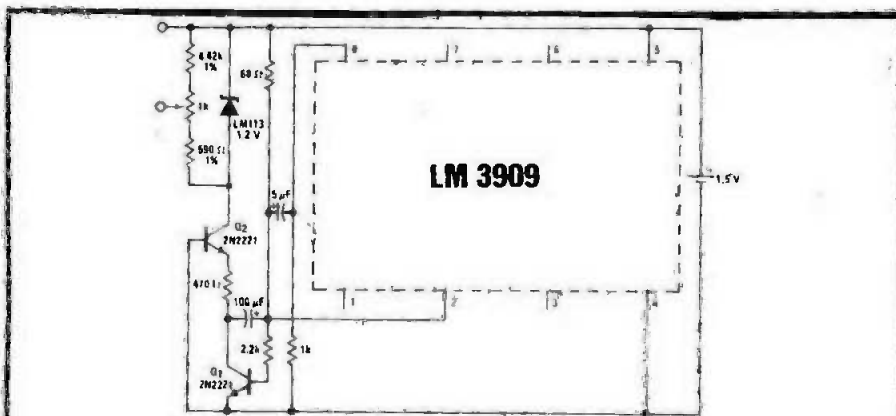Great frequency stability was not one of the design aims of the LM3909. In LED flasher circuits it is better than might be expected because the negative temperature coefficient of the LED partially compensates the IC.



Scope Calibrator


A useful electronic lab device is a precision square wave generator/calibrator. If the output is held at a few tenths percent of 1 V, peak-to-peak, it is useful in calibrating oscilloscopes and adjusting 'scope probes. Many lower cost or battery-portable oscilloscopes do not have this feature built in. Also it is useful in checking gain and transient response of various amplifiers including "hi-fi" power amplifiers.

Output is a clean rectangular wave which can be adjusted to exactly a 1 V amplitude. A


rectangular wave of approximately 1.5 ms "on" and 5.5 ms "off" was chosen for circuit simplicity and low battery drain. Waveform clipping is virtually flat due to complete turnoff of the current switch Q<sub>2</sub> and the typical "on" impedance of 0.2  $\Omega$  provided by the LM113. The 0.01% temperature coefficient of the LM113 at room temperature allows negligible drift of the waveform amplitude under laboratory conditions. Loading by a 'scope probe will also be insignificant.

National Semicon.  
Larkfield Industrial  
Estate, Greenock  
Scotland

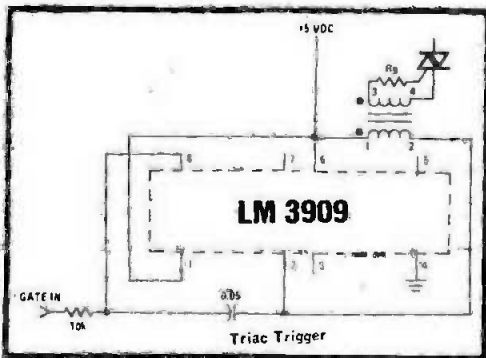Available from  
Marshall's Ltd  
42 Cricklewood  
Broadway London  
NW2 3ET at a special  
offer price of 80p inc  
of V.A.T. and p&p




Triac Trigger

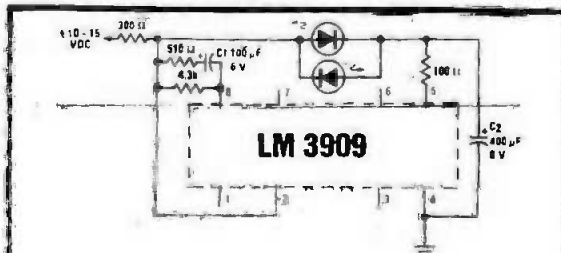

Alternating Flasher

The circuit above is a relaxation type oscillator flashing 2 LEDs sequentially. With a 12 VDC supply, repetition rate is 2.5 Hz. C<sub>2</sub> the timing and storage capacitor.

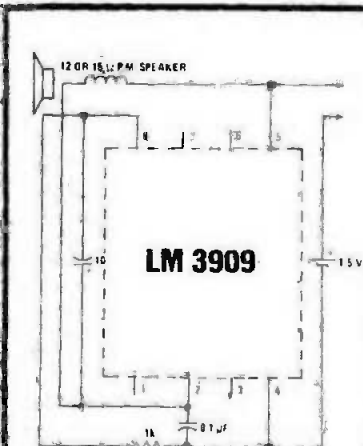
If a red/green flasher is desired, the green LED should have its anode or plus lead toward pin 5 (like the lower LED).



"Buzz Box" Continuity and Coil Checker

short, up to about 100  $\Omega$ , across the test probes provides enough power for audible oscillation. By probing 2 values in quick succession, small differences such as between a short and 5  $\Omega$  can be detected by differences in tone.

A novel use of this circuit is found in setting the timing of certain types of motorcycles. This is due to the difference in tone that can be heard from the tester depending whether there is a short or not across the low resistance primary of the cycle's ignition coil. In other words, the difference between a 1  $\Omega$  resistor and a 1  $\Omega$  inductor can be heard. Quick checks for shorts and opens in transformers and motors can therefore be made.

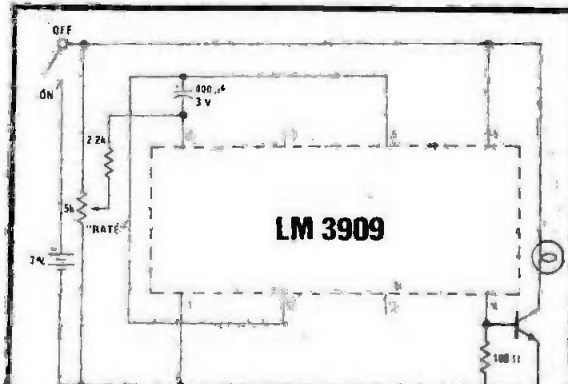

"Mini-Strobe" Variable Flasher

The 3 V "mini-strobe" may be used as a variable rate warning light or for advertising or special effects. The rate control is so wide range that it adjusts from no flashes at all to continuously on.


# MK 50075 MK 50103 MK 50104 EXPANDABLE SCIENTIFIC CALCULATOR CHIP SET

The MK 50075, ALU circuit, combined with the MK 50103, 50104 ROM circuits forms a powerful twelve digit scientific calculator. The display format can be fixed point (user programmed) or floating point in either business or scientific notation. The calculator has four rotatable stack registers plus nine addressable memory registers. All entries use the reverse polish notation.

Effective combination of key functions on this calculator make it possible to offer fifty-five functions with thirty keys. Multifunction keys are accomplished by utilising the SHFT/DSP, INV/STO, and HYP/RCL control keys. SHFT (Function) enables the upper case key function while INV (Function) enables the inverse of a function. The HYP key is used in conjunction with hyperbolic functions while COS, SIN, and TAN have hyperbolic, upper case, and inverse functions. The order in which the control keys are entered will have no effect on the function. For example, both the key sequence SFHT, INV, C → F and INV, SHFT, C → F will convert degrees Fahrenheit into degrees Celsius.




The calculator can work trigonometric functions in either degrees, grads, or radians. When in the radian mode an indicator is turned on. Switching between grads and degrees is achieved by a slide switch while switching from grads to radians or degrees to radians is a key function. The calculator can do the following transcendental functions:  $\sin x$ ,  $\arcsin x$ ,  $\cos x$ ,  $\arccos x$ ,  $\tan x$ ,  $\arctan x$ ,  $\sinh x$ ,  $\operatorname{arcsinh} x$ ,  $\cosh x$ ,  $\operatorname{arccosh} x$ ,  $\tanh x$ ,  $\operatorname{arctanh} x$ ,  $e^x$ ,  $\ln x$ ,  $10^x$ , and  $\log x$ .

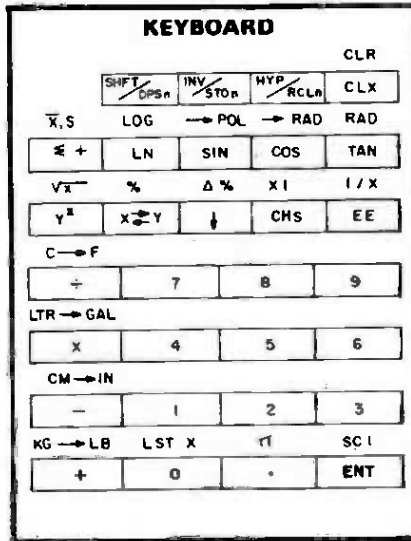Besides transcendentals, it calculates the single variable functions of  $X!$ ,  $1/X$ ,  $\sqrt{X}$ , and  $x^2$  and the two variable functions of  $y^x$ ,  $\sqrt{y}$ ,  $\%$ , and  $\Delta\%$ . It has ten preprogrammed conversions which automatically change the contents of the display register into the desired unit calculates mean and standard deviation using the unbiased method.




**The chip set is available from Mostek U.K. Ltd, 240 Upper Street, London N.1. The price, inclusive of V.A.T. and p&p is £27.**

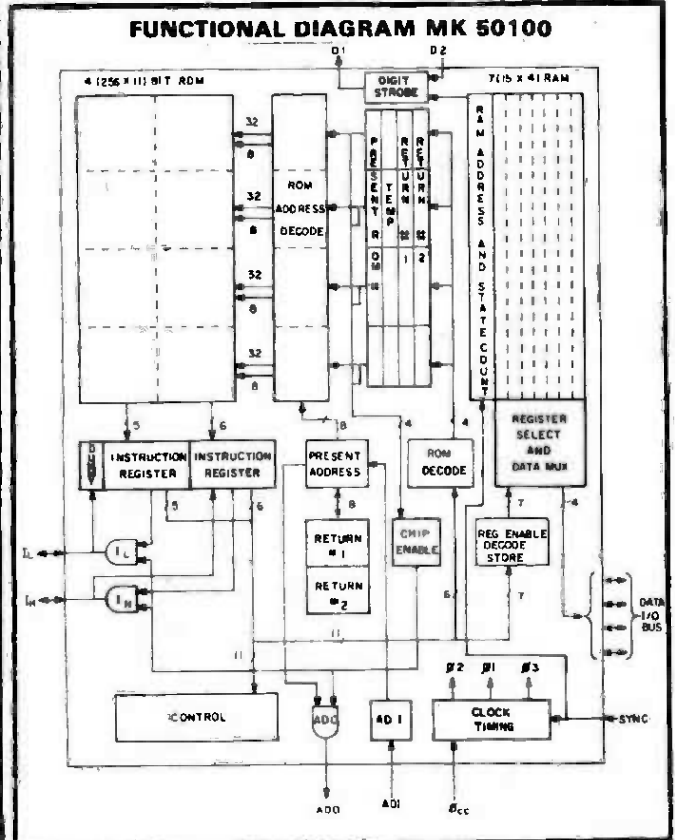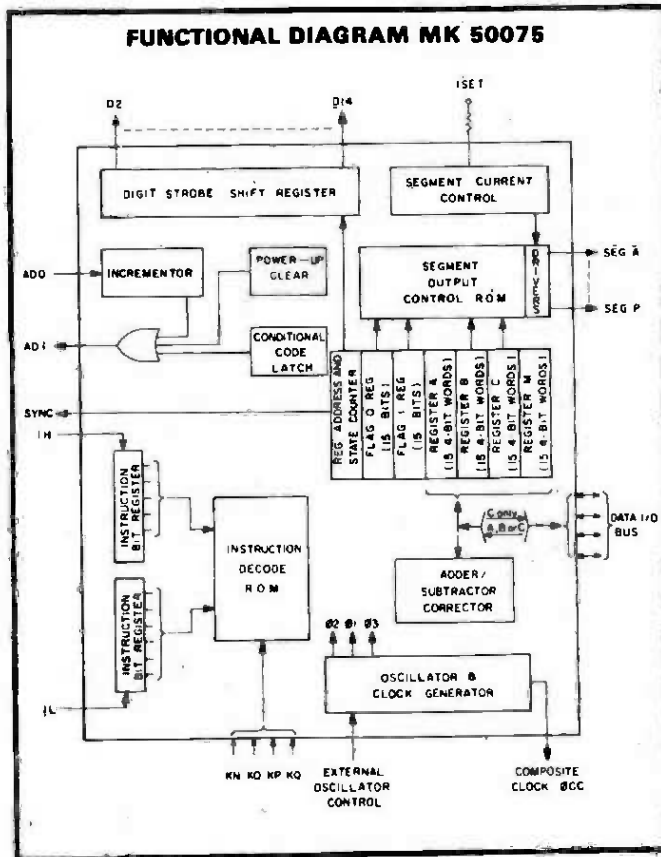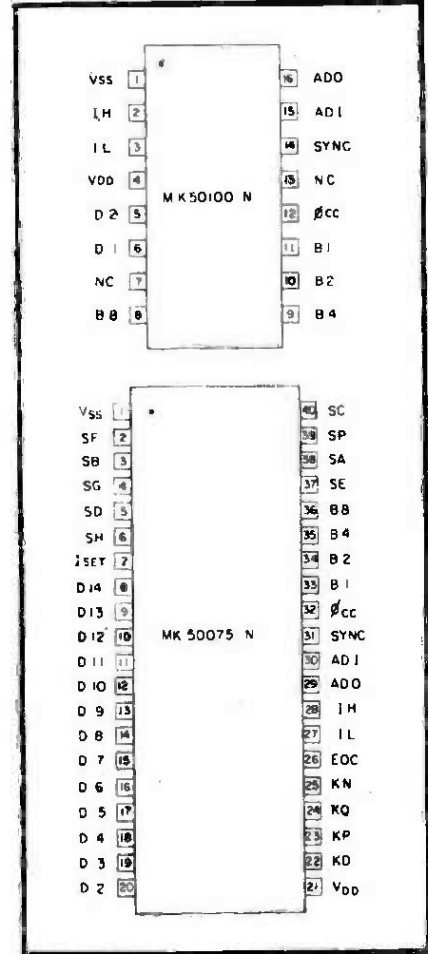**A comprehensive data booklet is included with each set.**






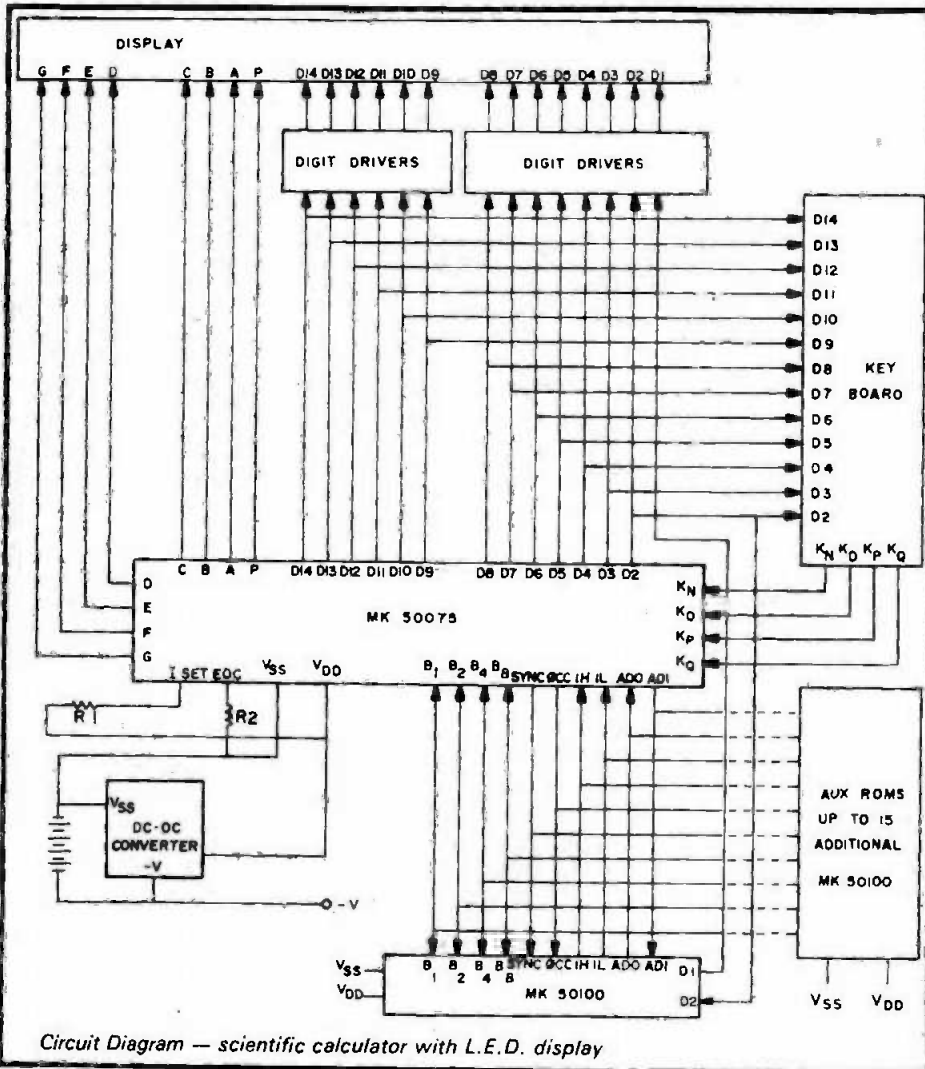

**RECOMMENDED OPERATING CONDITIONS**

PARAMETER	MAX	
	MK 50075	MK 50100
V <sub>DD</sub> Supply Voltage	-18.0	-18.0
V <sub>IH</sub> Input Voltage, Logic "1"	V <sub>SS</sub>	V <sub>SS</sub>
V <sub>IL</sub> Input Voltage, Logic "0"	V <sub>SS</sub> - 6	V <sub>SS</sub> - 6
φ <sub>CC</sub> Clock Period	10	10

**KEY MATRIX**

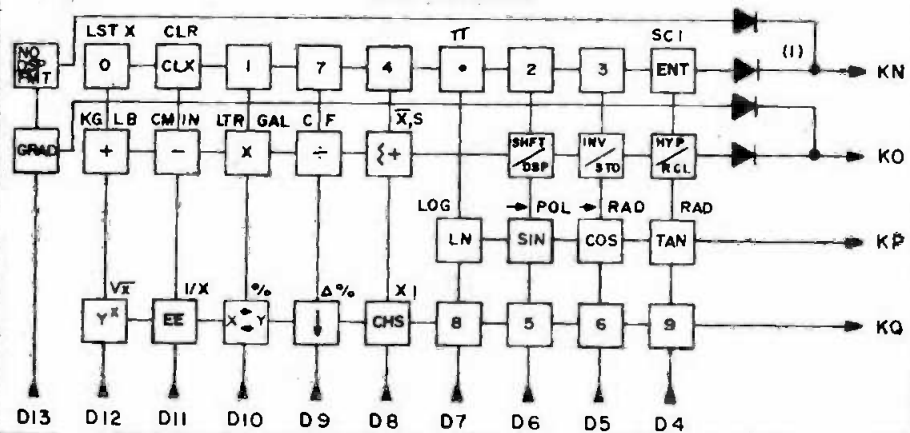

**Functions available:**

- Clear
  - Clear display
  - Add, subtract, multiply, divide
  - Scientific display format:
    - 10-digit mantissa,
    - 2-digit exponent,
    - floating decimal
  - Mode set to radians
  - Fix decimal point (0-9) in display
  - Sine
  - Cosine
  - Tangent
  - Hyperbolic sine
  - Hyperbolic cosine
  - Hyperbolic tangent
  - Memory store, 9 registers
  - Memory recall, 9 registers
  - Memory exchange, 9 registers
  - X ↔ Y exchange
  - Common Log
  - Natural log
  - 4-stack register
  - Rotate stack
  - Recall last X
  - Business display format: 12-digits, floating decimal point
  - Arc sine
  - Arc cosine
  - Arc tangent
  - Arc hyperbolic sine
  - Arc hyperbolic cosine
  - Arc hyperbolic tangent
  - Xth root of Y
  - Gross profit margin percentage
  - Summation minus for vector subtraction
  - Y to the X power
  - Reciprocal for all values exponent range from +99 through - 100
  - PI
  - Change sign
  - Square root
  - Factorials
- 
- Summation plus (adds X and Y to memory for vector addition, recalls sum of X and sum of Y)
  - Percentage
  - Percentage difference (Δ%)
  - Mean
  - Standard deviation
  - Centigrade to fahrenheit
  - Litres to gallons
  - Centimeters to inches
  - Kilograms to pounds
  - Degrees to radians
  - Set radian mode for trigonometric functions
  - Trigonometric rectangular to polar
  - Hyperbolic rectangular to polar
  - Anti log, natural (e<sup>x</sup>) for all values from x = +230 through - 230
  - Anti log, common (10<sup>x</sup>), for all values from x = +99.9 through -99.9
  - Trigonometric polar to rectangular
  - Hyperbolic polar to rectangular
  - Set degree mode for trigonometric functions
  - X<sup>2</sup>
  - Fahrenheit to centigrade
  - Gallons to litres
  - Inches to centimetres
  - Pounds to kilograms.

# Part 7 Bits & Bats

A MONTH OF VARIETY, this month as we take the opportunity to cover one or two subjects and fill in a few gaps. Firstly

## I/O HARDWARE


On the input side, keyboards such as the Clare Pendar types are available from firms like *Computer Sales and Services, 49-53 Pancras Road, London, NW1 2QB*. These keyboards usually have a ROM mounted on them to generate a parallel ASCII output, but some use a diode matrix for code generation. This can be an advantage, since diodes are more robust electrically than MOS devices and additionally offer you the facility of changing the coding if you wish. These keyboards are ideal for connection to one half of a PIA to make a simple interface, or can be used with a UART chip for serial I/O.

On the other half of the PIA you could hang a Burroughs Self-Scan display as shown in fig. 1. This is an alphanumeric gas discharge display available in 16, 32, and 80 character sizes and will display a single line of text. Further details from *Walmore Electronics Ltd., 11-16 Betterton St., Drury Lane, London WC2*.

A cheaper alternative to display up to 8 lines of 32 characters is to build yourself the ETI 560 VDU. A suggested interface is given in this month's article, but M6800 users (and perhaps users of other micros) will probably find that the simplest interface for their system is to use a PIA with one half outputting the address on the screen of the character and the other half handling the data. In use this is fairly simple from both the hardware and software points of view. You simply output data to the PIA 'B' half and then increment the 'A' side so that it is ready for another character. Handshaking can be done automatically by the PIA control lines.

If you require hard copy output from a serial interface, you could do worse than the Teletype 35RO available from *Chiltmead* who advertise in the mag. This is a heavy duty machine which should operate reliably if noisily. If you have a serial interface, but want blissful silence, then a VDU

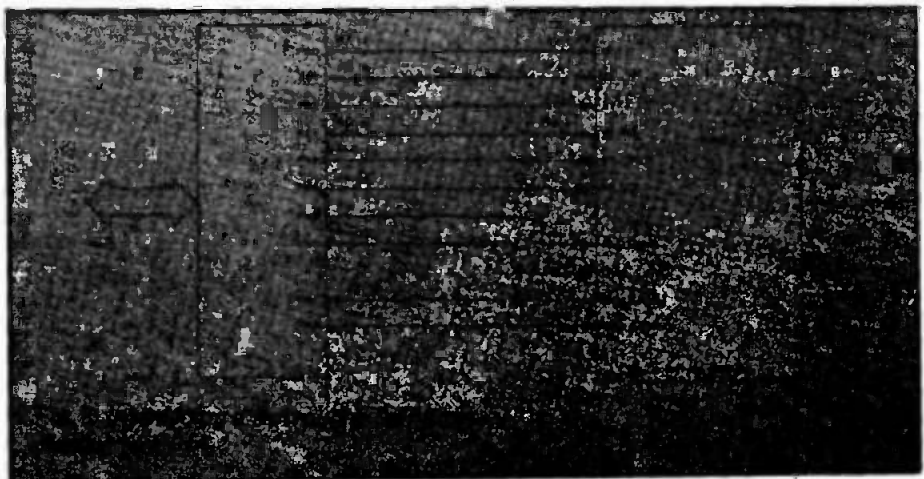such as Computer Workshop's CT1024 is a good bet. Their address (which we forgot in the last issue!) is *174 Ifield Road, London, SW10 9AG*. Alternatively, you could stick the other side of that UART (Universal Asynchronous Receiver Transmitter) chip we mentioned earlier onto your 560 VDU.



As we have said, there are lower cost approaches to I/O such as hex keyboards and displays, or even switches and LEDs. The great advantage of this approach is that you can cheaply have a development system up and running, and then purchase or otherwise obtain whatever peripherals become available to you, since you can easily write the routines to run them.

## THE ACIA

Although we have very briefly looked at the MC6820 PIA, we have only mentioned the ACIA (Asynchronous Communications Interface Adapter). This is another example of the move by manufacturers towards 'intelligent' peripheral adaptors/controllers, and in all probability, this chip is very nearly as complex as the MPU chip itself.

The ACIA (MC6850) is a very smart chip indeed, and can perform an amazing repertoire of functions. Its primary function is the conversion of parallel data addressed to it into serial data, but in addition it can generate a parity bit, either even or odd, for error detection and can also control the most sophisticated

peripherals and modems through 3 control lines. On receive, it will perform the required serial to parallel conversion, and in addition, can check the parity bit of each byte, and flag an error if the parity is wrong, or if there is an overrun or framing error.

Since this chip is intended for asynchronous communication, it

sticks a start bit, '0', in front of the byte it is outputting, and tags on 1 or 2 ones as stop bits at the rear. The ACIA can operate at any speed up to 500 kbps, so it is plenty fast enough to drive a teletype!

## CASSETTE TAPE

Interesting application number 1 for the ACIA is to do with cassette tape. If you can't see the link, here it is.

If you are using a system based on switches and LEDs, or a hex keyboard — in fact no matter what you are using to get your program into the micro's memory, you will soon find it tedious loading programs by hand. You now have a choice of leaving your program permanently in memory with the power on (like the HP25C), or outputting it onto punched paper tape or magnetic tape or even onto a magnetic card (like the HP67). Which is where cassette tape comes in. Almost everyone has a cassette tape recorder these days, and you can put it to better use than recording Top of the Pops by using it to record, and later, reload the programs you have written on your micro. This is done by the (simple?) expedient of converting the digital data to audio tones which can

be directly recorded. In fact, a new standard has now been largely agreed between the computer manufacturers in the States for this low-cost method of data recording.

Known as CUTS (Computer Users Tape Standard) the system works by converting a digital '0' to 1200Hz and a '1' to 2400Hz, and recording these tones at 300 bits/second. However, as this is an asynchronous system, i.e. it does not require synchronisation with the micro system clock, it records the start bit and two stop bits, as shown in fig.2.

This, obviously, is where the ACIA comes in, as it can do this job almost entirely on its own. One neat trick lies in the fact that the chip which normally generates the ACIA's clock frequency, the MC14411 bit rate generator, is really just a crystal oscillator and a divider chain. Now two of the frequencies which are produced by this chain are: yes, you've guessed it, 1200 and 2400Hz. It doesn't take much thought to come up then with the set-up shown in fig.3. As can be seen the two signals are simply gated, rounded off by the LPF, and fed to the mic. input of your cassette recorder. To get the signals out again, possibly the easiest technique is to use a phase locked loop. This would feed straight into the Received Data input of the ACIA.

Whilst this circuit is not tried and tested, we can't see why it shouldn't be persuaded to work, and we intend to have a bash at it.

### MORE MICROS

Whilst we have used Motorola's M6800 microprocessor as an example thus far in order to make the series consistent (and it may also have something to do with the fact that we're using 6800 in our own System 68!) we feel that it would be rather unfair not to wander off at some point and see what else is about in the microcosm(?).

Firstly, there's the company who really started it all, *Intel*. They produce a range of 4 and 8 bit MPUs, as well as the 3000 series bit slices, which are like TTL fast chunks of MPU. The 3002 is a 2-bit slice, so if you stick 8 of them in parallel with some other parts you get a 16-bit processor. But the best known of Intel's products is the 8080, which is an 8-bit MPU similar to 6800, and is the other 'industry standard'. The 8080 is comparable to 6800, it has, perhaps, some 'nicer' instructions, but some of its pins carry multiplexed signals, and so it requires a handful of external logic to make it go. You pay your money and you take your choice.

Also of interest is the 8008, the fore-runner of the 8080, which is slower

and has only a subset of the 8080's instruction set, but is cheaper.

*Fairchild*, and their second source, *Mostek*, are going strong with their F-8 chip set, which is an 8 bit MPU, in two sections, the 3850 CPU and the 3851 Program Storage Unit, which carries the Program Counter, two 8 bit I/O ports, and 1k of ROM. Sounds great, but the snag is the ROM is mask programmed, which rules it out for the home constructor. But you will hear more of this device, as it forms the basis of Fairchild's new TV games, and has also been built into an electronic chess set.

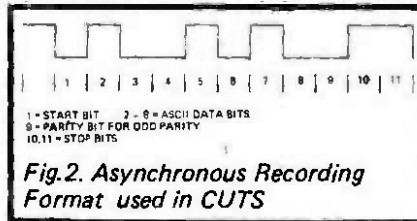


Fig.2. Asynchronous Recording Format used in CUTS

A device which will almost certainly appear in educational environments is *Intersil's* IM6100. This chip is of interest on two counts; firstly it is a CMOS chip, and secondly, it obeys the instruction set of the well known, if not ubiquitous, PDP-8/E minicomputer, so that programs written for the PDP-8/E will run on the IM6100. This means that there is a vast library of software available for this MPU, which makes it very attractive indeed. Like the 8/E, it has a 12-bit word length.

*National Semiconductor* are responsible for SC/MP, which they claim is 'enough to make any machine think'. A stroke of brilliance on the part of NS, who when other semiconductor manufacturers were falling over themselves to produce a really 'smart' MPU, came up with what most people really wanted: a stupid but cheap one. Don't be fooled, it's slow and it's got a small instruction set, but it can do things.

Also from NS is PACE, which is a


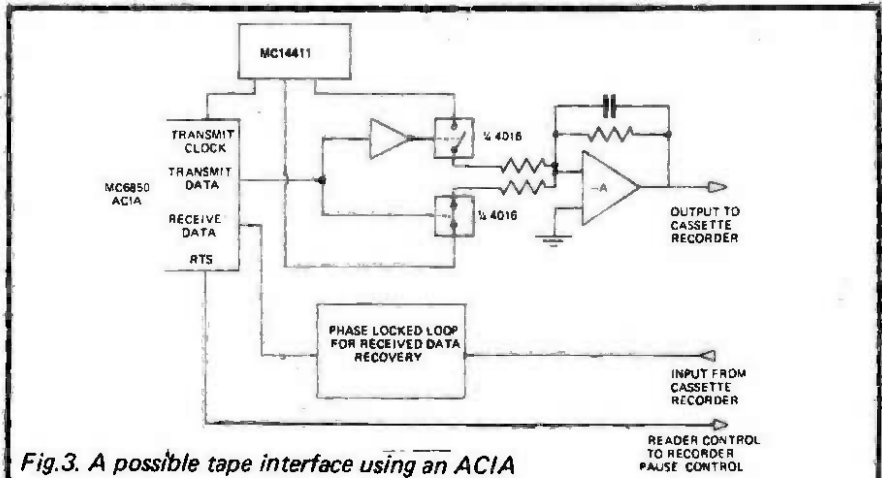


Fig.3. A possible tape interface using an ACIA

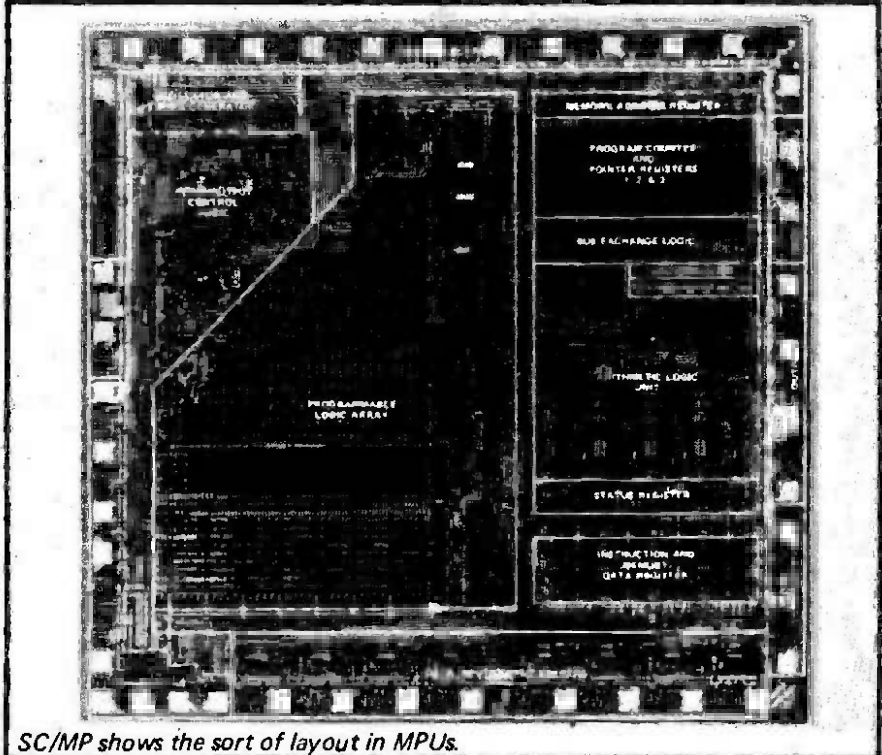

SC/MP shows the sort of layout in MPUs.

# microfile

16-bit device with some nice features such as 4 levels of interrupt. It has it's nasties like every other MPU, e.g. the address and data busses are common, and the address has to be latched externally.

RCA are offering their CDP 1802 device which is a CMOS 8 bit micro. Despite RCA's attempts at the mating game, Synertek have been a bit coy, leaving Hughes holding the baby as sole second-source. Quite a nice device, this though a bit weak on decimal arithmetic, but nice from the point of view of power supply and clock requirements.

The PPS-8 from Rockwell has special I/O chips for just about every kind of peripheral. The power supply is a bit odd, being a single -17V, and the stack pointer is only 5 bits allowing for only 32 values on the stack. But without having used it, it's impossible to say what its good and bad points are.

That well known little company in Bedford, Texas Instruments, have a couple of nice products. The first is the SBP0400, which is a 4-bit bipolar bit slice built using IIL.

This is an interesting device that one doesn't hear too much of; somebody somewhere must be using, or planning to use, the SBP0400, but they're not saying anything. Not really suitable for the amateur, unless you want to get involved in microprogramming!


TI's other front-line device is the TMS9900, which is a 16-bit n-MOS machine with a very nice architecture and a big plus in the form of hardware multiply and divide. If the price comes down sufficiently this could be a very nice device for the amateur - but wait and see.

Finally, a device which a lot of people have been waiting with baited breath - the Zilog Z-80. This is basically a super 8080 in concept, with a much improved instruction set, and an extra turn of speed. Not yet readily available in this country, but when it is....
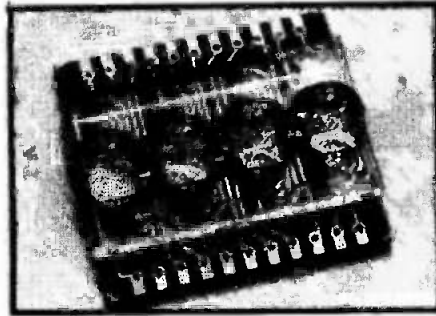
## MICRO DATA

Getting hold of manufacturer's data sheets on MPUs isn't very easy for the home constructor who only wants to buy 1 micro, but fortunately many readers of this column will already have the data sheets on 6800. The trouble is that MPUs are complex devices and the data sheets are only the beginning of the story. If you want to 'read' further you have two options; you can play about with System 68 (next months ETI), or if you are in a hurry, buy the 3 $\frac{1}{2}$ lb 'M6800 Appli-

cations Manual' which gives complete design details of a number of systems, including an absurdly complex Point of Sale terminal. A boring book to read, but good meaty stuff. It is available from *The Modern Book Company, 19-21 Praed Street, LONDON W2 1NP*, or from *Cramer Electronics, 16 Uxbridge Road, Ealing, LONDON W5 2BP*, who charge £7.50 + 50p p&p.



## MICRO NEWS

### ALPHA LED DISPLAY

Litronix have introduced a new low-cost alphanumeric display which contains four 16-segment LED characters. The DL-416 common-cathode display has integral magnifying lenses mounted on an edge-connected, end stackable PCB. Intended for use in portable and hand-held equipment, the DL-416 offers high contrast daylight viewing and high legibility at distances up to 5ft. Typical operating characteristics are a forward voltage of 1.65V at 10mA, reverse current of 100uA at 3.5V, and a luminous intensity of 0.5mcd at 10mA. This looks like a pretty useful device for the MPU builder.

### MORE ALTAIR IN UK

Altair's UK agents have released further details of their 680b micro-computer kit. This machine is based on the M6800 and comes complete with 1k of RAM, 1k of ROM (256 bytes pre-programmed with a monitor and loader), as well as an ACIA for teletype or VDU interface. The 680b with turnkey front panel (i.e. without the switches and lamps often found on more conventional minicomputers) is priced at £290. Also available is a 16k memory card, priced at £496. Free with this card is a copy of Altair's new BASIC compiler for the 680b. In addition, the system will run an assembler and text editor for 6800 Assembly Language.

Altair's other microcomputer system is the 8800, which is based on the Intel 8080. A very wide range of software is available for this system, including business and scientific programs, as well as games programs and even routines to play music. Also available is a wide range of peripherals, including a floppy disc memory

system and a line printer.

*Compelec Electronics, Ltd., 310 Kilburn High Road, LONDON NW6.*

## SERT SYMPOSIUM

The Society of Electronic and Radio Technicians are holding a residential symposium at Sussex University on 26th to 29th September on the subject of 'Microprocessors at Work'. The technical programme will consist of 25 contributions spread over 5 sessions which will cover: Devices; Evaluation, Testing and Diagnosis; Programming and Software; and two sessions on Applications. Each contribution will be followed by a discussion period.

The registration fee is £98 per delegate, unless you are an SERT member, in which case it is only(?) £82. This includes full board and conference documentation, as well as participation in all extra-curricular activities.

Associated with this symposium is a competition to find a working application of an MPU by a home constructor which is simple, economic, original, and useful or entertaining.

Further details on both these items are available from *The Microprocessor Secretary, SERT, Faraday House, 8-10 Charing Cross Road, LONDON WC2H 0HP*. First prize of the competition is £150, but you'll have to be quick, as the closing date is 19th September.

## HP ADVANCE

Since many Microfile Readers are interested in, or own, programmable calculators, here is some news of the latest developments in this field from Hewlett Packard. HP have released 3 new machines, the HP25C, the HP67, and the HP97. The 25C is simply an HP25 which retains both program and data stored in it, even while switched off, thus saving the repeated entry of often-used programs. The HP67, however, represents a considerable advance on the HP65, in that it has around 3 times the program storage and 3 times the data storage. In addition, it has 20 user definable functions, 3 levels of subroutines, label, indirect and relative addressing, and 14 conditional execution functions. One important key is the Write Data key, which outputs the data register contents onto a magnetic card. The card reader is 'smart' in being able to detect whether a card carries program or data. If there is information remaining on the other side of the card to be read, it will prompt the user by displaying 'CRD'. Also included are pause and automatic register review instructions. The HP97 is a printing portable version of the hand-held HP67. Prices: HP25C; £155, HP67; £349, HP97; £590. The price of the HP21 has been reduced to £56.

# KITS - CMOS - DISPLAYS - MEMORIES - BOOKS - MODULES

Components from leading manufacturers only

## KITS



### ATTRACTIVE 6-DIGIT ALARM CLOCK KIT

With optional CRYSTAL CONTROL for high accuracy and battery back-up (see below). Complete kit including attractive slim case with deep red panel for 6-digit alarm clock with beep alarm, snooze, automatic intensity control and high brightness display driving. Uses MK50253 IC and Jumbo 0.5" red LEDs. 12 or 24-hour format (easy to add a switch to switch between them). Optional "touch switch" for snooze (extra). Order as "ACK" **£26.80**

Complete kit as above, plus CRYSTAL CONTROL and BATTERY BACK-UP. If mains power is disconnected (through a power cut, accidental switching off or moving clock) the clock will keep perfect time. Accuracy to within a few seconds a month. The extra components, with two PP3 batteries, all fit in the same case. While on back-up, the displays are off to conserve battery life but the alarm remains fully operational. Order as "ACK + XTK + BBK" **£33.56**

### SLIM GREEN CLOCK



Complete kit for this attractive 4-digit Mantlepiece Clock with bright 0.5" GREEN display. While constructing, select 12 or 24 hour format, flashing or fixed colon. Kit includes miniature transformer. Housed in a new all-white slim case with green perspex front panel. Easy to build. Order as "GCK" **£12.90**  
Kit as above, but less case and perspex. Order as "GMK" **£11.14**

CRYSTAL CONTROL and BATTERY BACK-UP can be incorporated in this clock too. No need to reset your clock each time power is disconnected. For the complete kit including this feature, order as "GCK + XTK + GBBK" **£18.65**

### Crystal Controlled 6-Digit CAR CLOCK Kit With Independent Journey Timer

Runs off 12V (car) battery — protected against low voltage drop-out — display comes on with ignition — internal battery back-up allows temporary disconnection. 6 digit timer times journeys up to 24 hours in hours, minutes and seconds — automatic intensity control (essential for car use) — uses 0.5" red LED digits. Same external appearance as our ACK but with 8 push-buttons for setting time, starting, stopping and resetting timer, selecting display to show "time" or "journey time" — all control buttons functional irrespective of display mode selected. Complete kit including case. Order as "CCK" **£39.50**

## CMOS

CMOS from the top manufacturers — nearly all RCA and Motorola

CD4000	0.15	CD4033	1.21	CD4066	0.61	CD4520	1.08
CD4001	0.15	CD4034	1.65	CD4067	3.12	CD4527	1.37
CD4002	0.15	CD4035	1.02	CD4068	0.18	CD4532	1.25
CD4006	1.02	CD4036	2.23	CD4069	0.18	CD4555	0.78
CD4007	0.16	CD4037	0.83	CD4070	0.48	CD4556	0.78
CD4008	0.83	CD4038	0.83	CD4071	0.18	MC14528	1.01
CD4009	0.48	CD4039	2.23	CD4072	0.18	MC14553	4.07
CD4010	0.48	CD4040	0.92	CD4073	0.18	MC14566	1.21
CD4011	0.16	CD4041	0.73	CD4075	0.18	MC14552	8.05
CD4012	0.16	CD4042	0.73	CD4076	1.34		
CD4013	0.48	CD4043	0.87	CD4077	0.48	Clock Chips	
CD4014	0.87	CD4044	0.81	CD4078	0.18	AY51202	2.89
CD4015	0.87	CD4045	1.22	CD4081	0.18	AY51224	3.50
CD4016	0.48	CD4046	1.16	CD4082	0.18	MK50250	5.00
CD4017	0.87	CD4047	0.78	CD4085	0.62	MK50253	5.60
CD4018	0.87	CD4048	0.48	CD4086	0.62	MM5314	4.44
CD4019	0.48	CD4049	0.48	CD4089	1.34		
CD4020	0.97	CD4050	0.48	CD4093	0.69	Flat Cable	
CD4021	0.87	CD4051	0.81	CD4094	1.62	20-w Im.	1.00
CD4022	0.83	CD4052	0.81	CD4095	0.91	10m. for	8.00
CD4023	0.16	CD4053	0.81	CD4096	0.91		
CD4024	0.67	CD4054	1.01	CD4097	3.12	Other ICs	
CD4025	0.18	CD4055	1.14	CD4099	1.59	CA3130	0.88
CD4026	1.50	CD4056	1.14	CD4502	1.07	75491	0.96
CD4027	0.48	CD4057	21.56	CD4510	1.18	75492	1.22
CD4028	0.78	CD4059	4.77	CD4511	1.36	3CA741	
CD4029	0.99	CD4060	0.97	CD4514	2.72	Mini-DIP	
CD4030	0.48	CD4061	18.92	CD4515	2.72	4 io	1.16
CD4031	1.92	CD4062	7.77	CD4516	1.18		
CD4032	0.92	CD4063	0.95	CD4518	1.08		



**50Hz CRYSTAL TIMEBASE KIT:** provides an extremely stable output of one pulse every 20ms. Uses. May be added to all types of digital clocks to improve accuracy to within a few seconds a month. If used with battery back-up also makes clocks power-out or switch-off. Replacing 50 Hz signal on battery-powered equipment. Providing firm synchronisation. Monitoring or improving turntable speed. Complete kit. Orders as "XTK" **£8.28**

## STOPWATCH KIT

Complete kit for stopwatch (as in Dec. ETI): choose 6 digit range from tens of hours to milliseconds. Uses 6 x MAN3M displays. All necessary parts, including case and Manganese batteries **£31.80**  
**STOPWATCH WITH ONE LATCH:** As above, but kit also includes facility to repeatedly freeze the displays with count continuing **£43.23**

## FAST SERVICE

We guarantee that telephone orders, for goods in stock, received by 4.30 p.m. (Mon-Fri) will be despatched the same day. First Class Post — and our stocking is good. Telephone orders: Private customers, quote Access or Barclaycard card no. (min. tel. order £5). Official orders, no minimum.

32.768 kHz Min. Watch Quartz Crystal	£4.50	5.12 MHz Crystal	£3.80
8-way BOSS Switch: 8 ultra-min. toggle switches in 16-pin DIL			£2.60
Miniature Transformers (Both fit in all Verocases below)			
Clock transformer, 6.0-6/300mA. Order as "LED-TRF"			£1.80
For 5LT01, 12-0/12/100mA, 1.5-0.1/5/50mA. Order as "5LT-TRF"			£1.80
VEROCASES. Heat cases with PCB guides, etc. front and rear aluminum panels. We have pre-cut perspex for some cases, making them ideal for clocks or instruments. For 751247J, PX-RJ-12 (Red) 28p, PX-GJ-12 (Green) 28p. For 751410J, PX-RJ-14 (Red) 30p, PX-GJ-14 (Green) 30p. For 751411D, PX-R-D-14 (Red) 40p. The cases are as used in our ACK & GCK. Dimensions are in mm.			
751410J (205x140x40)	£2.64	751237J (116x85x40)	£1.72
751411D (205x140x75)	£3.04	751238D (154x85x60)	£2.15


We have many other Verocases and Vero products in stock — see our Price List.

<b>BOOKS and Datasheets (do not add any VAT)</b>	
New 1976 RCA CMOS and Linear IC Combined Databook	£4.95
New 1976 RCA "Power and Microwave" Databook	£4.95
1976 National Semiconductor 7400 series TTL Databook, c. 200 pages	£3.46
TTL Pin-Out Card Index. Set of cards with pin-outs (top and bottom views) of TTL range and many other TTL ICs	£2.95
Intel Memory Design Handbook, c. 280 pages	£4.75
Intel 8080 Microcomputer Systems Users' Manual, c. 220 pages	£4.85
Motorola MC/MOS Databook (Vol. 5, Series A) c. 500 pages	£2.77
Motorola M6800 Microcomputer Applications Manual, c. 650 pages	£12.45
Motorola M6800 Programming Manual, c. 200 pages	£6.85
Motorola Booklet introducing Microprocessors	£1.50
DATA SHEETS on Microprocessors: RCA 1802 8-bit CMOS	£0.75
National SCAMP 8-bit	£0.75
Intel 6100 12-bit CMOS	£0.75

## PULSE GENERATOR MODULES

New Crystal Timebase Modules, built, tested and with output to within 2.5ppm. High stability, low current consumption (3 mA typical).  
50 Hz Module: Many uses (see by 50 Hz Kit). Order as "671-50" **£9.80**  
100 Hz Module: For any system counting in 1/100th sec. Order as "821-100" **£12.70**  
Other Crystal Timebase modules are available with the following outputs:  
10 Hz, 1 Hz, 1 pulse/min. 1 pulse/hr. Order nos. and prices on application.

<b>MEMORY ICs</b>	
Intel P2102A-6 (new version of 2102-2) 16 pin IC, TTL compatible, single +5V supply, 650msc, 1024 x 1 bit Static NMOS RAM	£3.35
Intel P2112-2 650msc, 256 x 4 bit Static NMOS RAM	£4.76
Intel-IM6508CPE CMOS 1024 x 1 bit Static RAM	£8.05

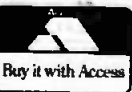


ADD VAT at 8%. 25p P&P on all orders. Price List sent with orders or free on request. Access and Barclaycard welcome, by post or phone. Export orders very welcome. No VAT but add 10% (Europe), 15% (Overseas for Air Mail P&P. (For export postage rates on books, contact us first.)



**SINTEL** 53a Aston Street, Oxford  
Tel. 0865 49791
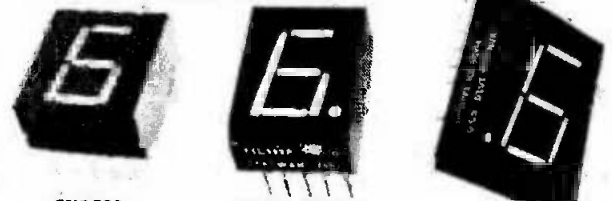
## DISPLAYS

These Jumbo LED displays take no more current than 0.3" types. All our Common Cathode (C.C.) digits can be used in place of any other C.C. display (0L704, B1750, MAN3640, etc.) as they are all electrically identical (but may have different pin-outs). Similarly our Common Anode digits may be used in place of any other C.A. types (DL707, DL747, RS/Doram 586/699, etc.).



Part No.	Manufacturer	Colour	Type	Size	Price
FND500	Fairchild	Red	Common Cathode LED	0.5"	£1.02
TIL 321	Texas Instr.	Red	Common Anode LED	0.5"	£1.30
TIL322	Texas Instr.	Red	Common Cathode LED	0.5"	£1.20
XAN652	Xciton	Green	Common Anode LED	0.6"	£1.78
XAN654	Xciton	Green	Common Cathode LED	0.6"	£1.78
MAN3M	Monsanto	Red	Common Cathode LED	0.13"	48p
5LT01	Futaba	Green	Phosphor Diode	0.5"	£5.80

Display PCBs (each fits neatly into Verocase 751410J). All are for multiplexed arrays. All are suitable for FND500, TIL321, TIL322  
D500-4 (for 4 digit clock) 90p; D500-6 (for 6 digit clock) **£1.35**  
D500-8 (for counter, up to 8 digits) **£1.36**

Display-holding PCBs are available for multiplexed arrays using our LED digits. PCBs also available for displays with TTL and CMOS Count/Latch/Decoder drivers. See our catalogue for more details (free on request — send SAE).


USING DISPLAYS WITH CMOS OR TTL? Send SAE, asking for free application note "SN1" which gives simple circuits with component values.

## LOW COST IC SOCKETS

Soldercon Pins are the ideal low cost method of providing sockets for TTL, CMOS, Displays, ICs. Simply cut off the lengths you need, solder into board and snap off the connecting carrier. A single purchase of Soldercon Pins gives you any socket you may need, and at low prices: 8 pin for 4p, 14 pin for 7p, cheaper in quantity. 50p per strip of 100 pins. 1,000 for £4, 3,000 for £10.50.
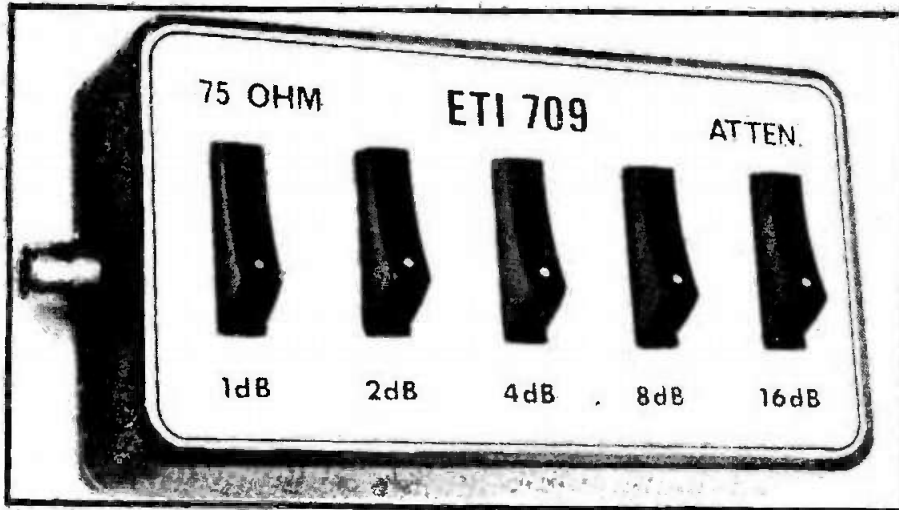
# RF ATTENUATOR

0 to 31 dB attenuation in 32 steps of 1 dB — useable to more than 200 MHz.



EVERYONE experimenting with RF circuitry will sooner or later need an RF attenuator. Some of the typical uses of such attenuators are listed below.

- Checking intermodulation on HF, FM, and TV receivers.
- Checking if incoming signals are high enough to allow splitting — to feed more than one receiver.
- Changing signal levels when checking the performance of receivers.
- Evaluation of filters, RF amplifiers, and other electronic devices.
- To find the loss in coaxial cable by the substitution method (as well as the gain of amplifiers). This method is convenient as a calibrated detector is not required: merely one that will give the same reading for two successive inputs of the same level.

## DESIGN FEATURES

An RF attenuator should have a useable frequency range of dc to 200 MHz. It is also necessary for the attenuator to be adequately shielded so that signals may only enter or leave via the coaxial connectors. For this latter reason a diecast box has been used to house the attenuator.

To obtain the wide frequency response required it is necessary to use resistors that have low inductance and capacitance — ¼ to ½ watt carbon types are the most suitable. If higher power handling is required one or two watt carbon types may be used but with these accuracy will start to fall off at around 100 MHz.

The switches should also have low inductance and capacitance but specially designed switches are prohibitively expensive. Many Japanese slide switches were evaluated and initially gave good results. However the ingress of dust and dirt was found to cause faulty operation after a time.

## CONSTRUCTION

Construction is simple and straightforward but to obtain optimum results we suggest that you follow our method as closely as possible.

Examine the photographs carefully, the method of construction may readily be seen from them. The unit is housed in an Eddystone diecast box having dimensions of 110 by 62 by 31 mm. The switches are mounted flush onto the bottom of the box. Those at either end of the box are mounted so that the centre pin of the

## HOW IT WORKS — ETI 709

The ETI 709 attenuator works by switching into the signal path a selected network or group of networks that reduces the signal strength by known amounts. The networks are specially designed so that they do not disturb the characteristic impedance of the line. That is, they appear to both the source and the load as a single parallel resistor equal in value to the respective source or load impedance. In our case the networks have been calculated to provide matching to 75 ohm impedance.

As can be seen from the circuit diagram each section of the attenuator has a characteristic shape that has led to the use of the name 'pi network' for this attenuator section.

The steps of attenuation are expressed in decibels. The voltage attenuation in decibels is equal to

$$20 \log \frac{V_1}{V_2}$$

Where  $V_1$  equals the

input voltage and  $V_2$  equals the output voltage. Thus if the output is

$$\frac{V_2}{V_1} \text{ equals}$$

0.5 and  $20 \log 0.5$  equals  $-6.02$  dB. (the minus sign indicating attenuation).

The use of decibels is very convenient as it allows the combined value of two or more attenuators to be found by simply adding their separate values rather than by multiplying the separate attenuation ratios.

Each succeeding attenuator is chosen to be twice that of the one previous. This binary form allows us to obtain a range of 0 to 31 dB in 32 steps with only five switches. Thus for example if we require 5 dB we depress SW1 and SW3 to give us  $1+4=5$  dB.

switch is in contact with the centre pin of the socket. This allows the connection to be made without the


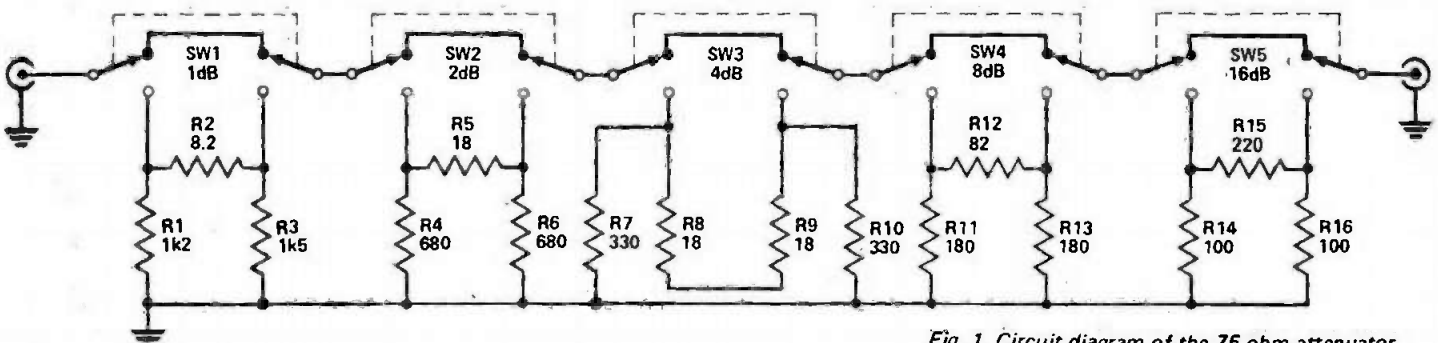


Fig. 1. Circuit diagram of the 75 ohm attenuator.

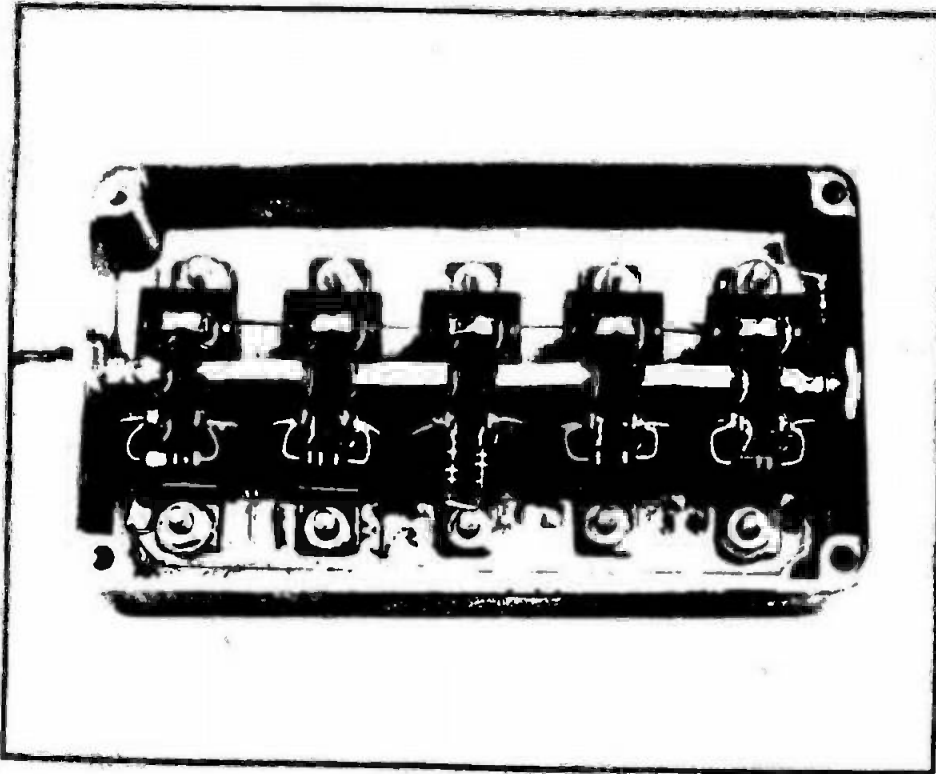

**PARTS LIST ETI 709**

R2	Resistor	8.2Ω	1/4W	5%
R5,8,9	"	18	"	"
R12	"	82	"	"
R14,16	"	100	"	"
R11,13	"	180	"	"
R15	"	220	"	"
R7,10	"	330	"	"
R4,6	"	680	"	"
R1	"	1k2	"	"
R3	"	1k5	"	"

SW1-5 Slide Switch min DTDP

2 RCA Phono Sockets (see text)  
Die cast box Eddy stone 7134P  
110mm x 60mm x 30mm

**TABLE 1**

ATTENUATION	R*	ACCURATE VALUES 75 OHM	ACCURATE VALUES 50 OHM	CLOSEST PREFERRED VALUE 50 OHM
1 dB	R1	1304	889.5	820
	R2	8.8	5.8	5.6
	R3	1304	889.5	820
2 dB	R4	864	436	470
	R5	17.4	11.6	12
	R6	864	436	470
4 dB	R7	331.6	221	220
	R8	38.8	23.9	12 + 12
	R9	0	0	0
6 dB	R11	174.2	118	120
	R12	79.3	62.8	27 + 27
	R13	174.2	118	120
18 dB	R14	103.2	88.8	88
	R15	230.7	184	180
	R16	103.2	88.8	88

\* All values in ohms

use of hookup wire. Evenly space the remaining three switches between the two outer ones. Note that a thin strip of tin plate is run the full length of the box and is held in place by the lugs and screws at one end of each switch. To this strip are soldered the ends of the resistors which go to ground. The


resistors are held in such a position by their leads that the metal body of the switch acts as a shield between the resistors mounted on either side of it.

The centre poles of the switches are interconnected by first bending the centre lugs of the switch outward towards the next switch and then by

soldering lengths of 3 mm wide tinplate between them as shown in the photos.

# Catronics


## 2 METER POWER AMPLIFIER

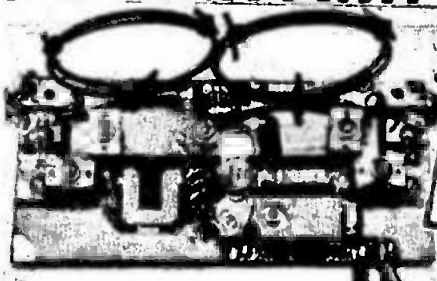

**AS DESCRIBED IN THIS ISSUE!**

Complete Kit to build this 40 watt power amplifier  
Price Only £23.10. Components also available separately.

## AMATEUR RADIO BULK BUYING GROUP

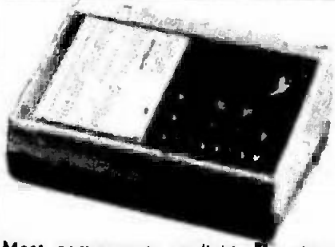

### LOW COST V.D.U.

Most components available for this project, including 2613 character generator, £9.82. Send s.a.e. for detailed price list.

Many other components specified for ETI projects are also available from stock.

### UNIVERSAL TIMER

2 digit Thumbwheel switch £3.70

CMOS i.c.s. 4011, 19p; 4017, 89p; 4023, 19p; 4516, £2.12; IN4001, 7p; IN914, 7p; TIL209, 29p.

**ALPHABET DECODER, DIGITAL FREQUENCY METER, AMATEUR RADIO AERIALS ALSO AVAILABLE**

(See inside last month's cover for details)

Send S.A.E. for full price list 30p plus large 11p s.a.e. for your copy of our Data Catalogue. All prices include VAT at current rates. Please note our minimum U.K. post and packing charge, except where indicated, is 20p. Export orders welcomed — write for export price list.

**PLEASE NOTE NEW ADDRESS:**

DEPT. 659

COMMUNICATIONS HOUSE,  
**20 WALLINGTON SQUARE,**  
WALLINGTON, SURREY SM6 8RG

Tel: 01-669 6700 (9 a.m. to 6 p.m., 1 p.m. Sat.)

# ELECTRONICS

## —it's easy!

# PART 31

## Concluding counting and D/A conversion

### BLANKING

In normal writing practice we do not write the '0's that appear at either end of a number, for example, 0001357.0 as could be held in an eight digit display, is better presented as 1357 or as 1357.0. A facility is sometimes provided in display-counter systems that blanks unnecessary zeros. Leading zero suppression is performed within the decoder stages of Fairchild seven-segment decoders by connection of the ripple blank output RBO (ripple because each stage connects to the next) of the decoder stage to the ripple blank input RBI of the next lower decoder stage. Blanking of least-significant zeros is not usually included. The actual arrangement for blanking control varies from maker to maker. Fig. 1 shows a method using ripple blanking.

The blanking facility can also serve other purposes. It can, in certain applications, be used to blank-out illegal display values resulting from incorrect codes. The RBO output also provides a detection output indicating when the decoder stage is at the BCD zero state.

### INTENSITY CONTROL

Displays are usually manufactured to supply one value of output brightness.

When brightness is to be tailored to particular ambient light conditions an appropriate kind of display can be selected that provides the desired luminance level. This however, does not always lead to a satisfactory choice when other considerations are taken into account.

Intensity of any display, however, can be controlled in a digital manner (that most desirable in digital systems) by turning the display on and off with an appropriate duty cycle (ratio on to off period). This is called pulse-duration intensity modulation. Provided the repetition rate exceeds 100 Hz the eye cannot detect that the radiation source is being modulated. Modulation may be achieved with any of the blanking methods given above. The schematic of Fig. 1 includes an intensity modulation facility.

With LED displays, intensity modulation can actually increase the apparent brightness. The human eye has a characteristic response to radiation that has greater sensitivity to the peak value of modulated light, rather the average or rms power. LEDs can be pulsed at high frequency with high peak currents because of their nanosecond response time. The net result is apparently higher brightness for a given amount of power.

### STROBING OR SCANNING

Displays which generate characters in the 7 x 5 dot matrix or seven-segment formats require decoding logic which energises the correct dots or segments. If each character has its own decoder we would need 7 lines for each digit of a seven-segment display. And 35 lines for each digit of a 7 x 5 dot-matrix display!

Obviously a method is needed to reduce the number of lines and circuitry required for multi-digit displays.

One such method is called strobing where lines of dots or segments are illuminated sequentially. The 7 x 5 array can be either strobed as lines horizontally or as rows vertically as illustrated in Fig. 2. Each row is selected one by one in sequence and the appropriate diodes in the row energised. Provided each row is returned to at no greater than 10 ms intervals the characters will be flicker free.

A diagrammatic illustration of how specific diodes are selected in a row is given in Fig. 3. The row switches are scanned in turn to cause a vertical scan. Simultaneous excitation of the other switch sets decides which diodes in the row are to be illuminated.

A strobing system requires a



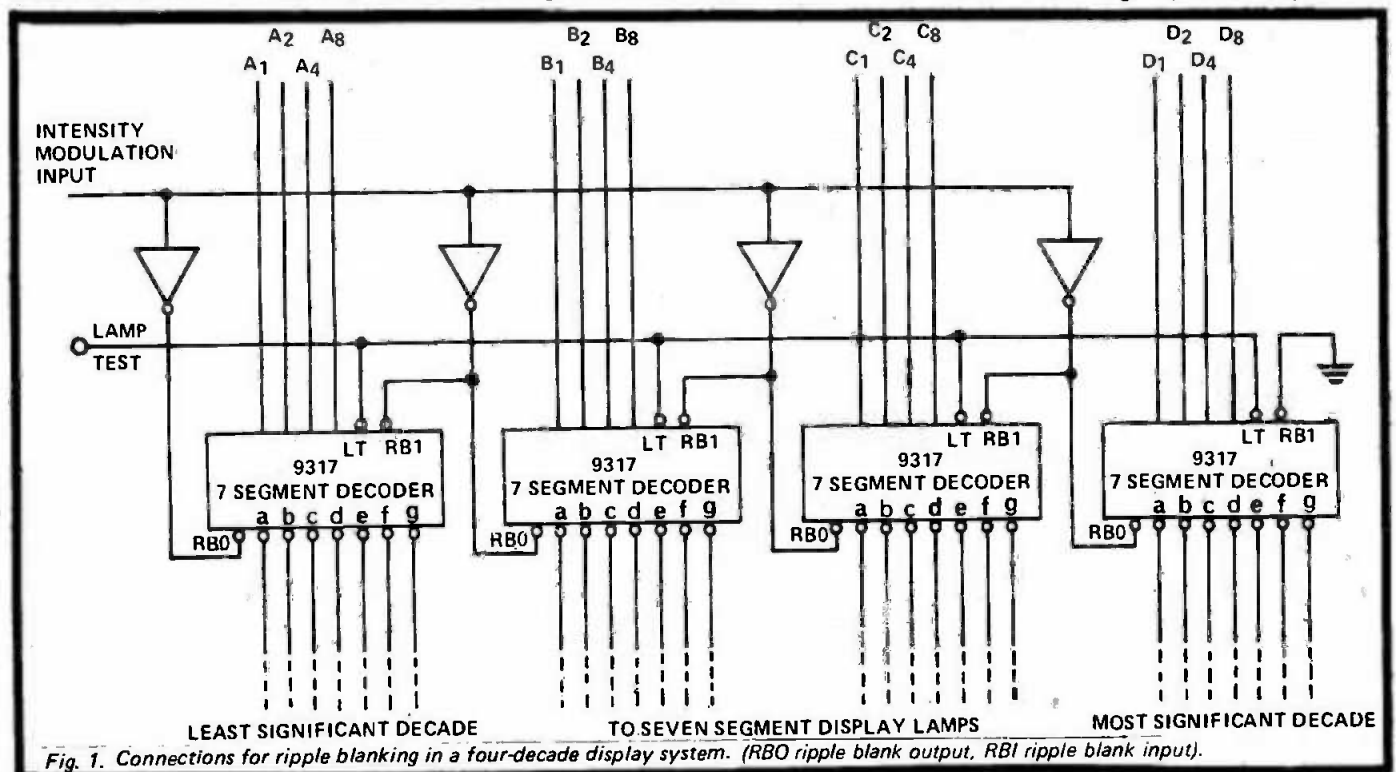
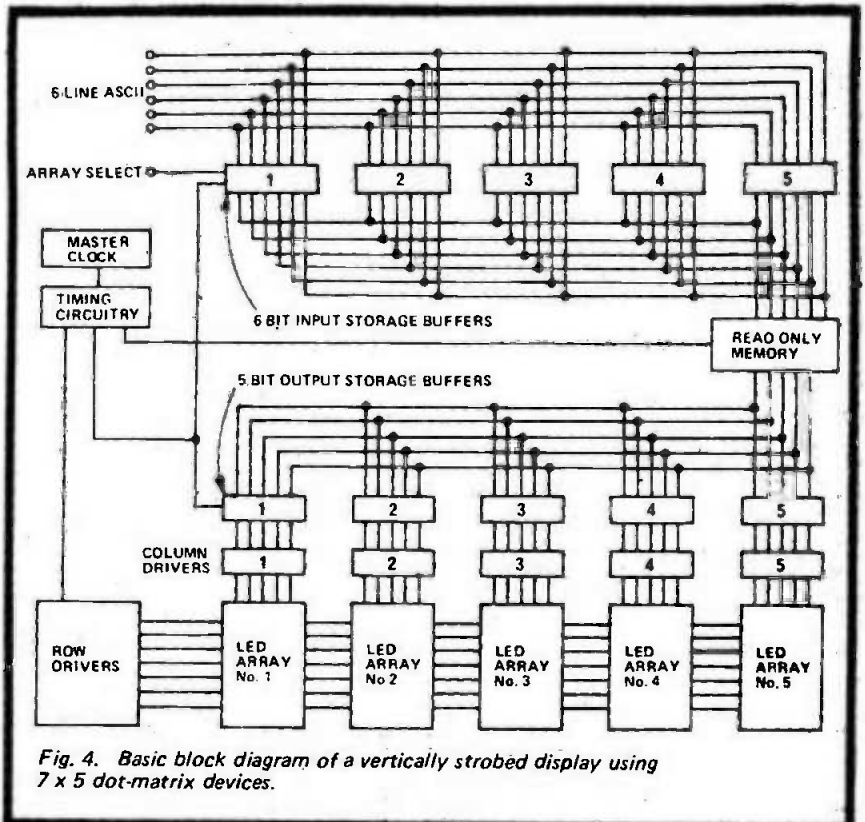


Fig. 1. Connections for ripple blanking in a four-decade display system. (RBO ripple blank output, RBI ripple blank input).

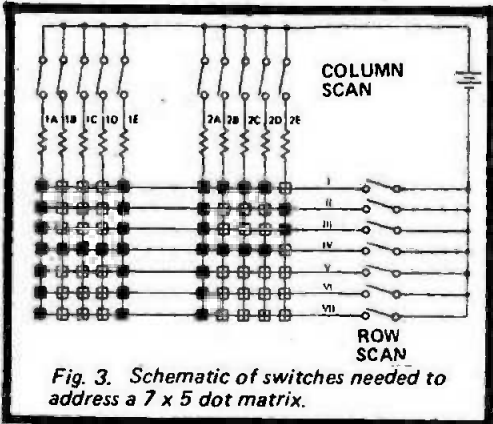

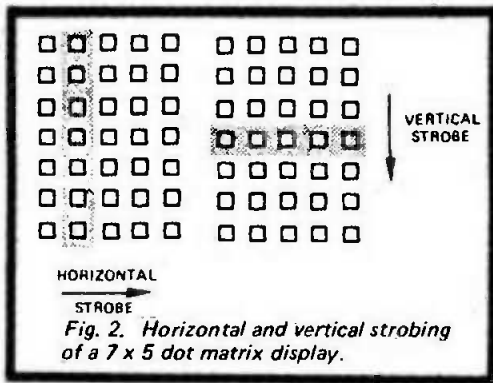

procedure to sequence the scanning action and a method of setting the selection switches that corresponds to the characters needed. The whole is controlled by a clock and timing generator. Storage buffers are also required to store the sequentially generated information. The task of creating the appropriate character timing codes is performed by a read-only-memory ROM. Clearly this method adds up to a complex system... really beyond this course's purpose. A schematic block diagram of a vertically-strobed five-digit LED display is given in Fig. 4. Although of apparently great complication this method is less expensive to employ than direct actuation through fixed gates. (Considerably more detail is to be found in the suggested reading list).

Another scanning method scans the matrix as a raster — across a row, one by one, and then to the next row. Strobing obtains its advantages by time-sharing common elements in a time-multiplexed manner.

### MULTIPLEXING

When the input data to be displayed appears in serial form or when large numbers of displays (over four digits) are involved, multiplexing (selection of complete digits sequentially) becomes advantageous for driving seven segment and one-of-ten displays. The basic multiplexing system requires the main system units shown in Fig. 5. An upper limit to the number of digits is around 12 and higher for LEDs. There are disadvantages; namely, a higher voltage is required in the

display to achieve the same brightness (LEDs are not so critical as other forms of display); the scan frequency must be at least 100 Hz to prevent flicker; transients must be carefully decoupled; and a clock failure (which stops the scan) may produce partial display failure because of excessive dissipation brought about by the increased voltage applied. (It is usual to include a failsafe protection circuit).

Again, the complexity appears great but in practice the multiplexed system is simpler to build. For example, a multiplexed, seven-segment display, with storage for eight digits, involves around 10 dual-in-line packages and a few discretes which compares with about 16 ICs for a non-time shared system.


To further reduce the connections that must be made upon assembly, manufacturers offer multi-digit displays in which the anodes and cathodes of the LEDs are internally

connected ready for multiplexed operation.
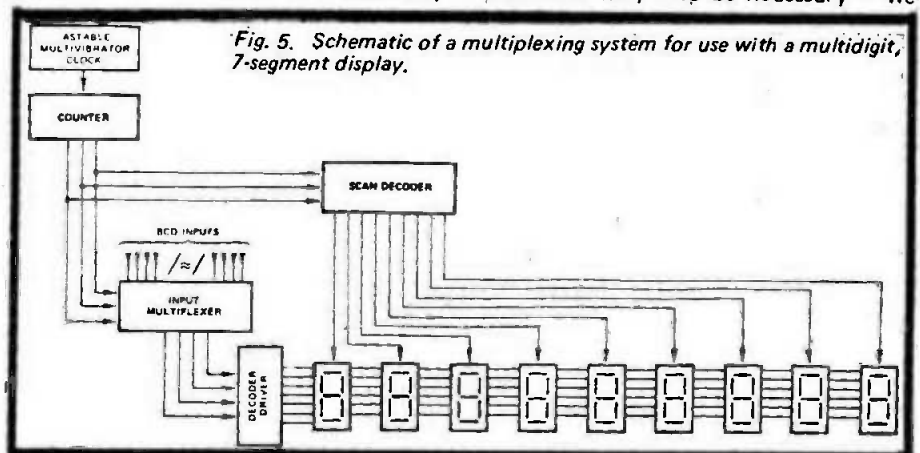
### OTHER CONVERTERS

Apart from digital-code converters, other converters are required in instrumentation: for example, when interfacing different systems of logic, eg TTL to CMOS, it is necessary to alter the dc levels of signals so that the output of one system provides the logic levels required by that following. This may require amplification or attenuation or shifting of a level.

However specific ICs are marketed to suit various interfacing requirements. Other converters are needed for sending digital signals through standard transmission lines in communication links, for receiving signals from lines, for increasing the logic level differences to increase noise immunity (again for transmission), and units that drive peripheral devices such as relays and indicators. Signal inversion may also be necessary — we



# ELECTRONICS — it's easy!

have already dealt with the inverter block earlier in the course.

Another class of converter is needed for converting digital signals to analogue voltages (D to A) and analogue voltages (and currents) into digital form (A to D). Such converters will be dealt with in the next section.

## D TO A AND A TO D

In order to control or modify the physical world around us we must first measure what is happening. The measurement data is almost always in analogue form, as is the actuation required for control. Between measurement and control some kind of electronic system is needed to amplify and shape the data.

We have seen that electronic systems may be of either analogue or digital form and it would seem best to use an analogue system between inputs and outputs that are both of analogue form. But not necessarily so — analogue systems are plagued with problems such as noise, dynamic range limitations, accuracy and linearity. Digital systems, as well as offering improved performance in the above areas, offer more economical processing of data, the ability to store data as long as needed, and more readable displays of data held within the system.

Thus there is much to be said for converting primary analogue signals into equivalent digital forms that are processed and stored etc until conversion back to analogue form becomes a necessity. Electronic sub-systems that perform these conversions are called Digital-to-Analogue Converters (DAC's or D/A converters) and Analogue-to-Digital Converters (A/D converters).

We will see that these are quite complicated systems in themselves — their design a skilled task. Nevertheless, many such sub systems are now marketed as single, largish circuit blocks that are wired into the total system in the same way as other complicated system building-blocks we have already encountered. It is, however, important to understand the basic techniques used if not so much the refinement of actual practice.

By use of certain input combinations DAC's can also be used as multiplier/dividers of two signals and as summing/subtraction units. It is also

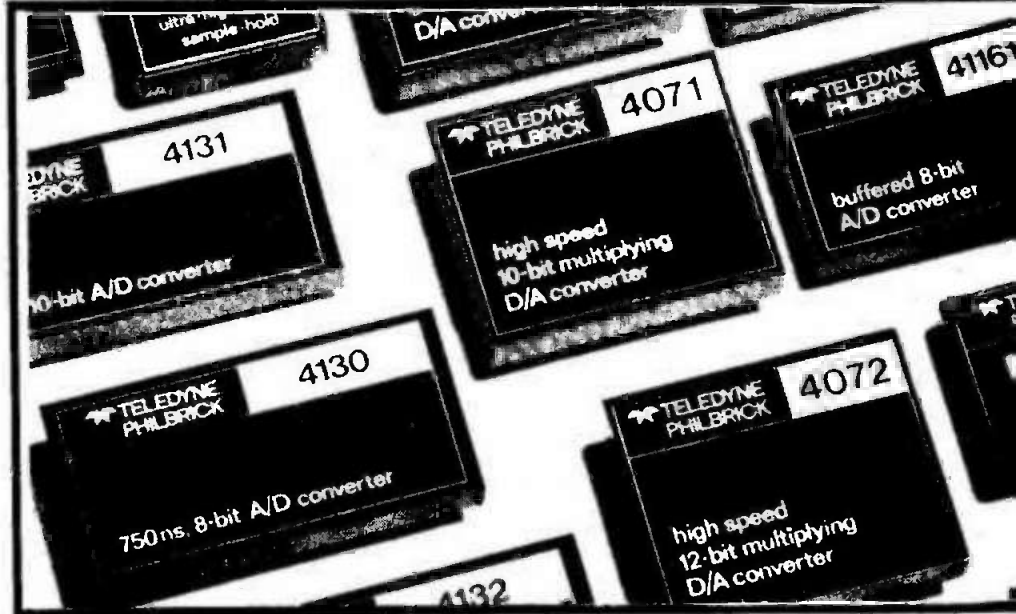


Fig. 6. Typical A/D converters.

relevant in this part to deal with multiplexers in a little more detail and with the so-called sample-and-hold circuit. These are often used in conjunction with DAC's.

Figure 7 illustrates the basic requirements of a typical data-acquisition system in which a number of physical variables are measured and processed to provide digital signals for storage. It uses multiplexer, sample-and-hold, and A/D converter sub-systems to form the whole.

Also pertinent, because similar techniques are involved, is the method for converting an analogue voltage to a signal of proportional frequency (which is a form of digital signal) — the Voltage-to-Frequency or VF converter.

The uses for A/D and D/A converters are limitless. Their application is ever-increasing as the unit cost falls to undreamed-of prices. Extreme complication using digital techniques often costs far less than simpler but less accurate analogue alternatives. Hence D/A and A/D converters will be found in digital panel meters, digital multimeters and data acquisition systems. They are also found in industrial plant; in process control of chemical and other manufacturing plant; in telemetry systems and other data transmission applications; in the interfaces (units matching the output signal requirements of one system with

the input requirements of another) found between sensors and computing units; between stages of hybrid computers; and the like. Although highly accurate DAC's may cost as much as £1000 the great universal demand has resulted in lower performance units being available for as little as £5.

## DIGITAL-TO-ANALOGUE CONVERSION

We begin with Digital-to-Analogue converters because they are the simplest in concept and use only one basic technique.

You will remember that each digit position of a binary number (held in a register, counter or other form of storage) has a weighting factor, eg 1:2:4:8 etc. An analogue signal equivalent to the binary number can be obtained by using each digital digit position to switch an amount of current (proportional to the position weighting) to a common summing junction. This system concept is shown in Fig. 8. When voltage output is needed the currents feed an op-amp. The detail of a precision ladder network is shown in Fig. 9 — it is set to convert the input digital number 11010001 by appropriate positioning of the digit position switches. When at 0 input the inputs to the summing op-amp are held to ground; when at 1 to an appropriate stabilized voltage.

The simplest form of ladder is used in the circuit of Fig. 9. It arises from the use of a binary weighted resistor sequence shown in Fig. 10. The actual values of resistors are selected to obtain adequately sized lowest and largest values, for at either end the op-amp loses accuracy due to imperfections of resistance ratios. It can be seen from the circuit of Fig. 9


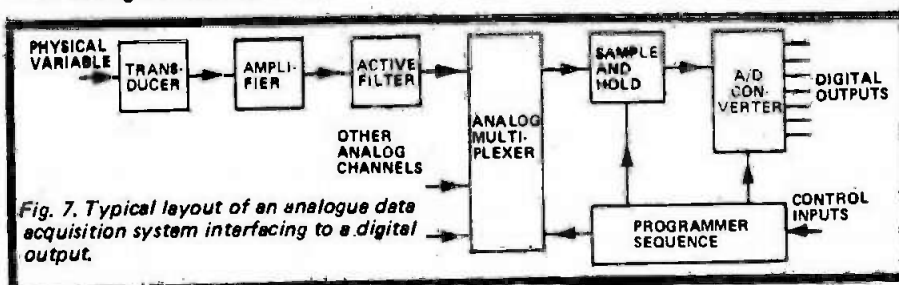
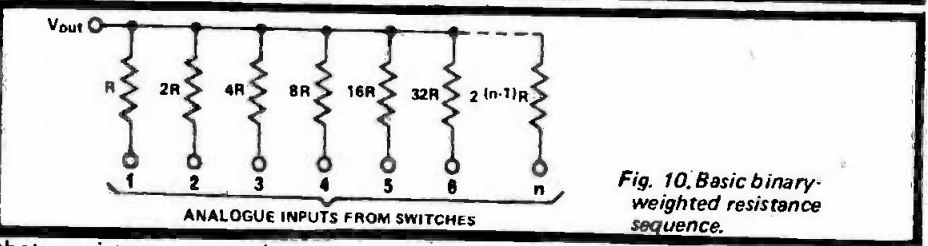
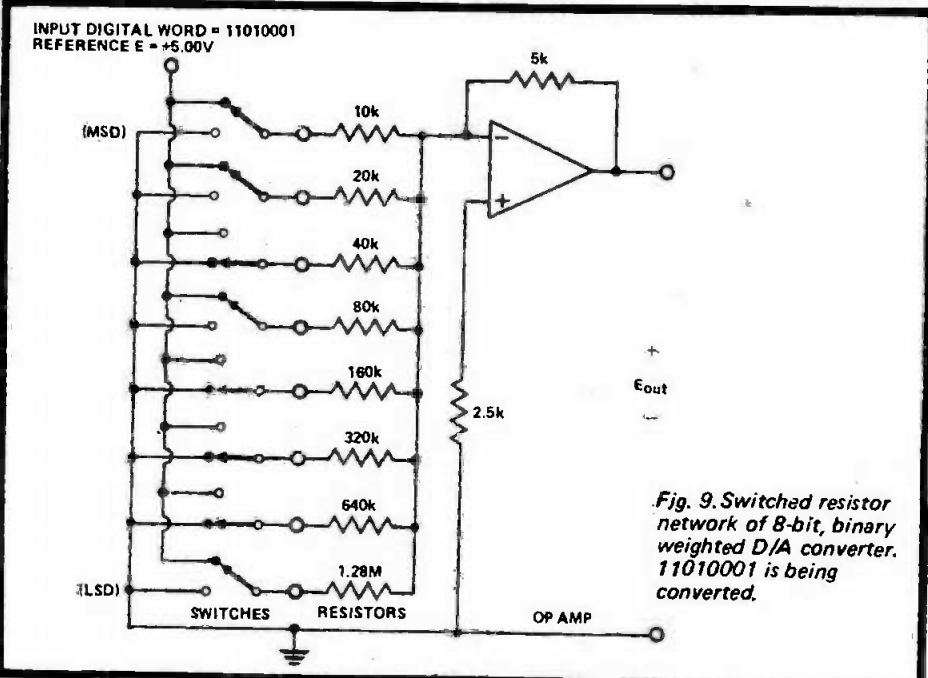


Fig. 7. Typical layout of an analogue data acquisition system interfacing to a digital output.

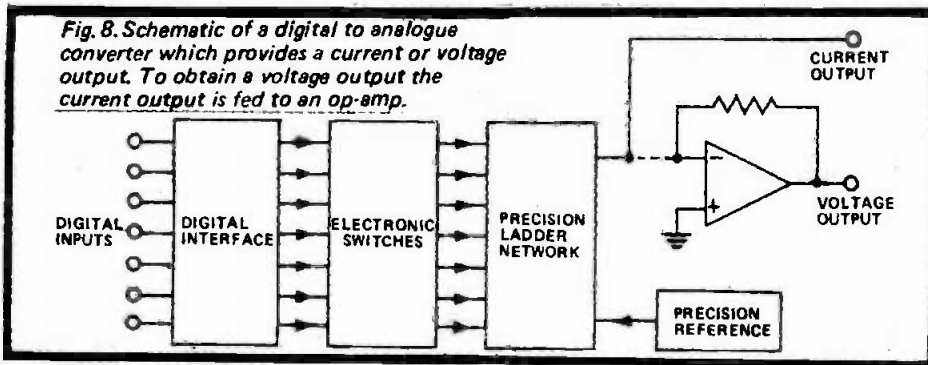


that resistors, even in a smallest capacity 8 bit converter, can extend to extreme values. The least significant bit must be clearly resolved when its switch operates, implying that all other resistors must have precision of absolute value and constancy with time that rises very rapidly with the number of bits required.

In practice this simple form of ladder is not used beyond about 8 bits conversion due to the cost of the precision resistors required.

The disadvantages of the simple ladder method are mostly overcome by the use of the R-2R ladder network shown in Fig.10. The through leg of the chain is permanently grounded, each spur is switched as needed to a reference stabilised voltage level. The features of this method are that only two values of resistors are needed (an easier practical problem) and that the absolute range seen by the op-amp varies much less than the above method for a similar bit capacity - it presents a virtually constant

impedance regardless of the binary code sequence switched in. With the R-2R ladder it is routine to provide 12 bit conversion.

It is probably obvious that other forms of digital-coding conversion can be handled by the use of appropriate resistor weightings. For example it is often necessary to chart-plot the output of a digital instrument. Thus a BCD to analogue converter is required for such applications. Figure 12 shows the weighting sequences for the simple and the R-2R ladder DAC's needed to convert BCD inputs to an analogue

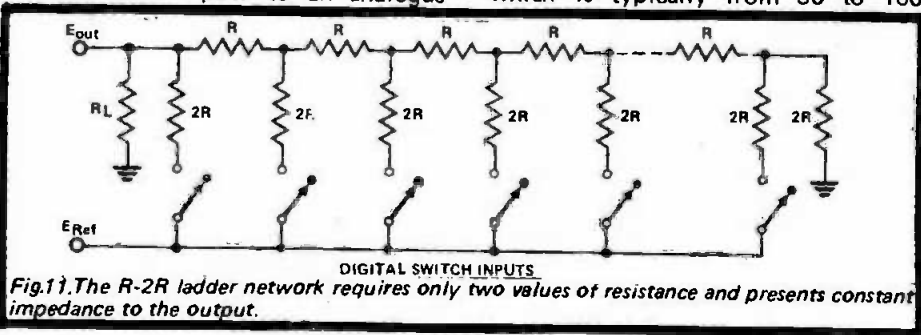

output.

Resolution and accuracy - DAC's rarely go beyond 12 binary bits (or 3 digit BCD) because the output analogue signal for greater bit-ranges must be of high stability. A 16 binary bit (or a 4 digit BCD) unit could provide  $\pm 0.005\%$  full scale linearity and accuracy, a performance requirement that is best avoided where possible because of the high cost of the DAC. By contrast 8 bit DAC's can be obtained with accuracies ranging from  $\pm 0.2\%$  full scale to  $\pm 0.01\%$  full scale. It is important, however, to realise that whereas analogue resolution, see Fig. 13, is a function of the number of bits that are equivalent to full scale, the accuracy and linearity of DAC's depend upon the tolerances and stability of resistors used in the conversion networks, for these decide the value of the slope and straightness of the slope - Figs. 14a, 14b. It is, therefore, possible to have a highly accurate converter that has quite coarse resolution - in which case the resultant analogue output signal will consist of very large step changes. This step form of signal defect is called quantum or quantization noise. In practice resolution and accuracy are tied together keeping quantum noise to an acceptable level.

Conversion and settling times - As both D/A and A/D conversion are dynamic processes, a finite amount of time is required for each conversion point to reach its final value. In DAC's the switching and settling times of the op-amp largely dictate the time for a bit change to finally appear as a steady-state analogue signal level. Early DAC systems using mechanical switches were slow indeed - today output settling times range from a slow  $25\mu s$  for very-low power consumption units to ultra-fast 25ns units.

Temperature coefficient - Each subsystem of a DAC has a temperature coefficient; resistances alter with temperature and the op-amp characteristics deviate. Both the overall conversion gain and the dc zero will be affected.

Gain will be affected due to the temperature coefficient of resistors which is typically from 50 to 100

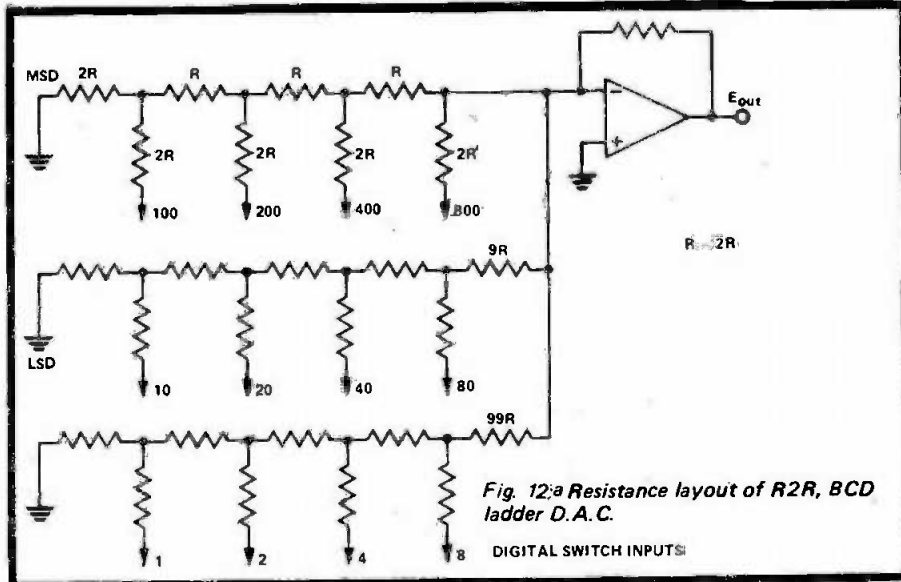


Fig. 12a Resistance layout of R2R, BCD ladder D.A.C.

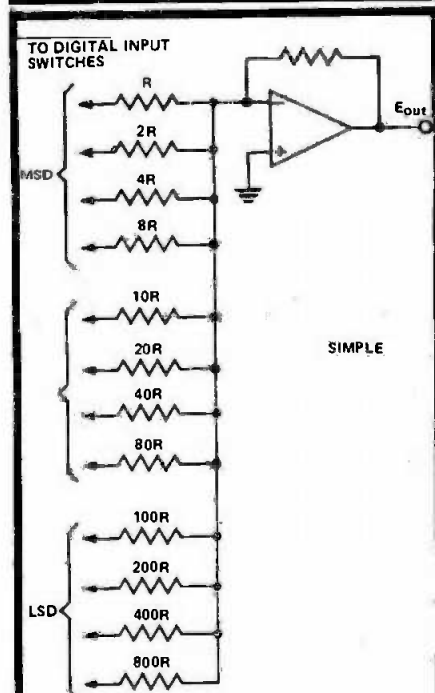


Fig. 12 Resistance layout for simple BCD-weighted DAC.

PPM/°C (100 parts per million, PPM, is equivalent to 0.001% change per degree Celsius). The main op-amp characteristic which affects performance is offset-voltage drift — typically 30 microvolts per degree Celsius.

For each particular type of DAC it is necessary to consult the makers' specification sheets, for no general rules apply for these parameters.

DAC's are available as either current or voltage output systems. Typical outputs deliver around 3 mA and 10-20 V swings.

Further explanation of terms used is to be found in the articles listed in the further reading section.

Glitches — Certain digital input states, whilst in a transient state, can cause the output to produce noticeable transients to the smooth, stepwise analogue — signal progression. These are known as glitches; examples are shown in Fig. 15. If the output is only to be observed after the system has settled, these matter little. In

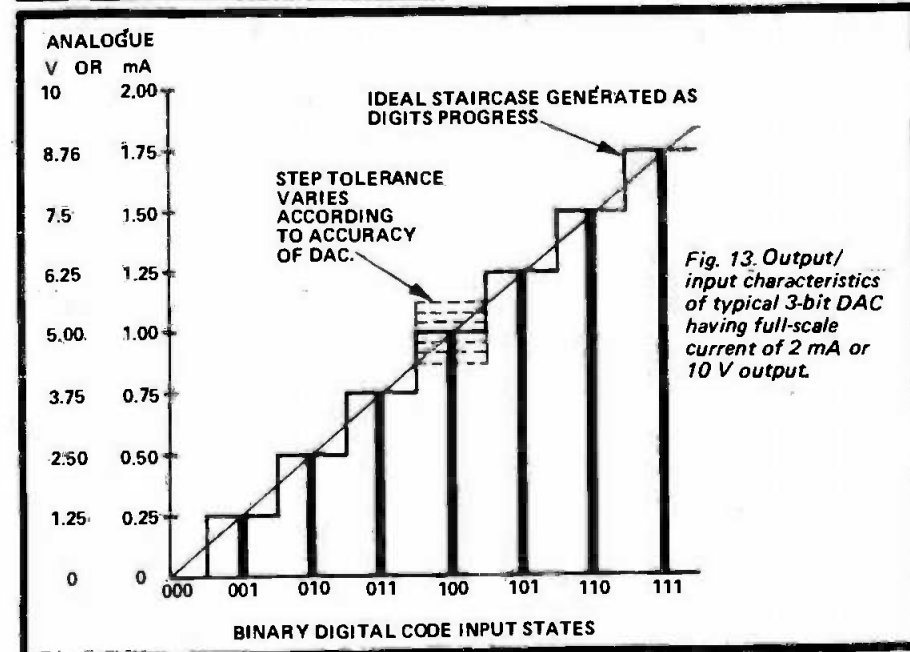


Fig. 13 Output/input characteristics of typical 3-bit DAC having full-scale current of 2 mA or 10 V output.

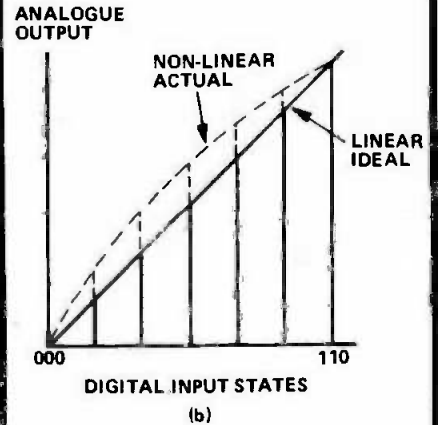
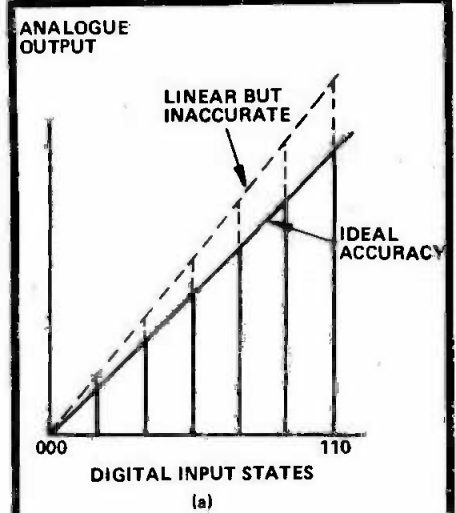


Fig. 14 Output/input definitions for DAC's (a) deviation of accuracy. (b) deviation of linearity.

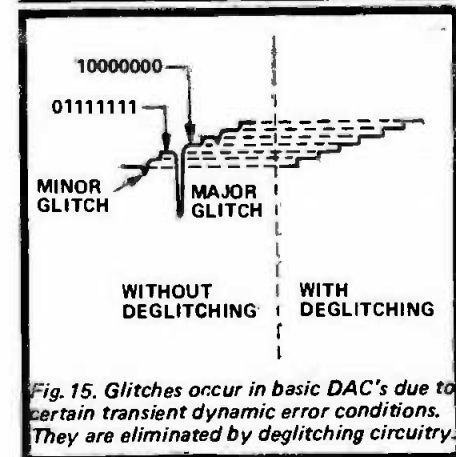


Fig. 15 Glitches occur in basic DAC's due to certain transient dynamic error conditions. They are eliminated by deglitching circuitry.

dynamic use of DAC's however, they may well excite unwanted behaviour in the system they are driving.

Deglitching in DAC's is not feasible with a low-pass filter on the output, for glitches vary widely in nature. The best solution is to use adequately fast and matched switching coupled with special deglitching, (sample-and-hold) circuits, that hold the output fixed during unwanted switching — transient conditions. Glitching states are, however, known states and are quite unlike random noise which defies prediction.

# Can anyone beat the Altair System?



## We doubt it.

When it comes to microcomputers, Altair from MITS is the leader in the field.

The Altair 8800 is now backed by a complete selection of plug-in compatible boards. Included are a variety of the most advanced memory and interface boards, PROM board, vector interrupt, real time clock, and prototype board.

Altair 8800 peripherals include a revolutionary, low-cost floppy disk system, Teletype™ line printer, and soon-to-be-announced CRT terminal.

Software for the Altair 8800 includes an assembler, text editor, monitor, debug, BASIC, Extended BASIC, and a Disk Operating System. And this software is not just icing on the cake—it has received industry wide acclaim for its efficiency and revolutionary features.

But MITS hasn't stopped with the Altair 8800. There is also the Altair 680—complete with memory and selectable interface—built around the new 6800 microprocessor chip. And soon-to-be-announced are the Altair 8800a and the Altair 8800b.

MITS doesn't stop with just supplying hardware and software, either. Every Altair owner is automatically a member of the Altair Users Group through which he has access to the substantial Altair software library. Every Altair owner is informed of up-to-date developments via a free subscription to Computer Notes. Every Altair owner is assured that he is dealing with a company that stands firmly behind its products.

WE HAVE EXPLAINED THE 8800 SYSTEM. TO OBTAIN INFORMATION ON THE 8800 KIT PLEASE SEND 50p

NAME .....

ADDRESS .....

### Compelec Electronics Ltd

310 Kilburn High Road, London NW6. Tel:01-328 1124

# ELECTRONICS TOMORROW

by John Miller-Kirkpatrick

LAST MONTH I, very foolishly, announced that the SC/MP Introkkit was priced at £50 (which it isn't!). It is REALLY £54.50 plus 8%. The WORST thing that I did was to mention the pseudo-TTY unit called the Telekit which was also supposed to be about £50. It isn't. The prices being quoted for it are in the range £160-£200 and you can build your own for less than that!

One of the main problems with all of the instant MPU kits on the market is that they all require a TTY teletype in order to communicate with the KITBUG or BUGBUG program supplied with the kit. These programs are supplied in PROM form and thus it is rather difficult for the average user to reprogram the kit, especially as you have not been able to practise programming because you cannot communicate with the MPU (except through a TTY which costs nearly £1,000). National Semiconductor came up with an answer to this problem for their own use, teaching people to use SC/MP in their educational courses.

As each course might have 50-100 people, the cost in normal teletypes would be enormous and so the brains at NS in Germany modified a calculator to a very simple TTY compatible unit to talk to the Introkkit. Apparently they made about 25 of these units, considered production, then (in the USA) pulled the calculator which they had used out of production. Disheartened, it seems that they gave up for the time being as nobody can quote a delivery date or price for the unit although NS distributors have taken orders for it.

## SECRET REVEALED

Now we tell you the secret -- you can make one for yourself! If SC/MP is intelligent enough to be able to talk to a TTY then conversely

SC/MP is intelligent enough to BE a TTY. So you buy two Introkkits and reprogram one of them to be a very simple TTY device. I know I mentioned earlier that it was difficult to program when you have not been able to practise, but the point is that NS already have a TELEKIT program and if they want to sell SC/MP units they MIGHT make this program available.

It only needs one person to have a suitable program, and anybody else can have a copy of the PROM with the program in it.

N.B. If you send PROMs through the post, especially abroad, put a big notice on the outside of the packet about X-raying as this can be a good cheap way to clear U-V erasable PROMs.

## KIT INTROS

Fig 1 shows the components used in addition to an Introkkit, Flag 0 and Sense B are used for the I/O, buffered through a pair of opto-isolators. The PROM is programmed to put one "1" and seven "0's" out on the SOUT line and to shift the one bit across the keyboard matrix using another Flag as a clock. Any key pressed will connect the bit in the DM8546 shift register to an input on the 74C175 register.

This register is eventually read back into the CPU chip, and can be used to decode which of the keys was pressed. The code generated by the key is used to look up a table in the PROM to decode it into an alpha-numeric character displayed on the seven segment calculator display (NS have worked out a 40 character set which can be displayed using 7-seg plus a DP). This character is now output to the character register which will eventually direct it onto the display.

## PROGRAMME TIMERS

The other half of the program

accepts any keyboard entry and outputs it with all stop bits etc. to FLAG 0, and eventually to the pseudo-TTY output pins. Similarly, any input at the TTY pins is detected by SENSE B, decoded and checked internally then output to the display.

The 9 digit output is enough for most programming applications, but is not so good for normal I/O requirements. However, if you are using SC/MP for a complex timer, such as a traffic light controller or similar, this does not need to communicate with people via the alphabet, and thus Telekit is great for programming this application.

So off you go to buy two Introkkits and reprogram one of the PROMs -- can't afford two plus a calculator, etc? Well, how about programming into RAM instead of PROM? Introkkit comes complete with a KITBUG PROM and very thoughtfully a listing of KITBUG, the listing can be used to study programming by working out what the KITBUG program is doing. The PROM comes complete with socket so it can be removed and replaced with RAM chips in a PROM simulator.

## SIMULATOR PLUG



This can be simple to build and requires four MM2112 256x4 RAMS plus a MM74C00 (CMOS 7400) to replace the 512x8 bit PROM plus about 20 switches and buttons and some LED lamps. The Simulator is made to plug into the 24-pin socket normally used by the PROM and looks like a PROM to the CPU chip.

The difference is that this 'PROM' can be programmed by 9 address toggle switches, 8 data switches and a 'program' button connected to the R/W pins. Power for the unit is derived from the socket, but it may be an idea to include a large storage capacitor to allow for temporary disconnection without loss of memory.

If you really want low power you can use some of the new CMOS RAMs available which will store the memory for several days from a small battery or for a couple of hours from a large capacitor. Cost of such a simulator would be about £20 for MOS 2112 RAMs, or £50 for CMOS RAMs. This plus an Introkkit allows you to program your own MPU for less than £100.
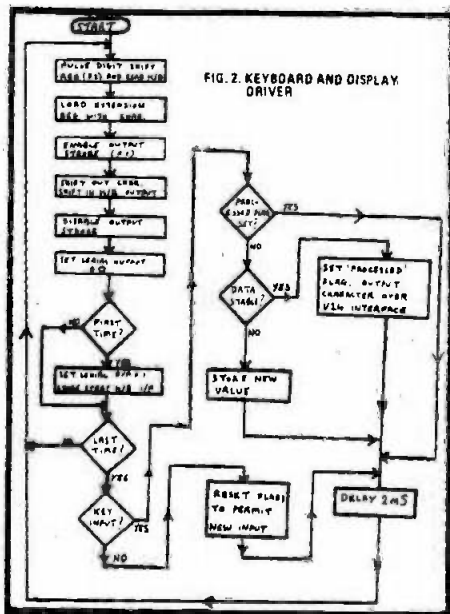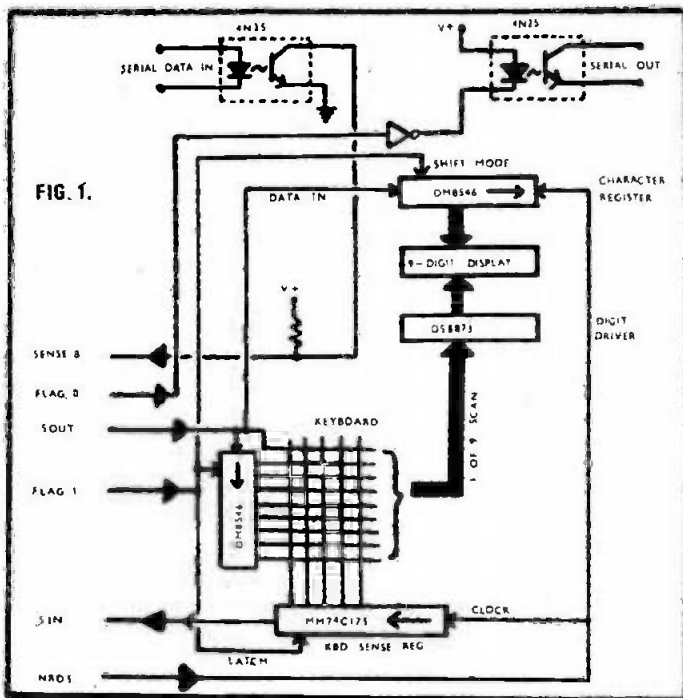
## DO IT WITH YOUR MPU!

We now have an MPU kit which can be programmed to your own



requirements (you could even copy most of the KITBUG program if you so wished) so now what can you do with it?

How about using the ETI 560 VDU to enable you to play games on your own TV set? Total cost is in the area of £150 we know, but for this you have a unit MUCH more sophisticated than any other TV game. You could play Draughts, Nim, Scrabble, Chess, Go, Backgammon, Monopoly etc with the CPU generating the dice.

Invent NEW MPU games -- after all **you** are the programmer.

If you come up with any programs, or with a TELEKIT program for SC/MP or 6800 let us know at ETI -- then we can pass this information onto other readers, in MICROFILE perhaps. ●

# Sparkrite mk2

Capacitive discharge  
electronic ignition kits

VOTED BEST  
OF 8 SYSTEMS  
TESTED BY  
'POPULAR  
MOTORING'  
MAGAZINE



- \* Smoother running
- \* Instant all-weather starting
- \* Continual peak performance
- \* Longer coil/battery/plug life
- \* Improved acceleration/top speeds
- \* Up to 20% better fuel consumption

Sparkrite MK. 2 is a high performance, high quality capacitive discharge, electronic ignition system in kit form. Tried, tested, proven, reliable and complete. It can be assembled in two or three hours and fitted in 15/30 mins.

Because of the superb design of the Sparkrite circuit it completely eliminates problems of the contact breaker. There is no misfire due to contact breaker bounce which is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high R.P.M. Contact breaker burn is eliminated by reducing the current to about 1/50th of the norm. It will perform equally well with new, old, or even badly pitted points and is not dependent upon the dwell time of the contact breakers for recharging the system. Sparkrite incorporates a short circuit protected inverter which eliminates the problems of SCR lock on and, therefore, eliminates the possibility of blowing the transistors or the SCR. (Most capacitive discharge ignitions are not completely foolproof in this respect). All kits fit vehicles with coil/distributor ignition up to 8 cylinders.

#### THE KIT COMPRISES EVERYTHING NEEDED

Ready drilled pressed steel case coated in matt black epoxy resin, ready drilled base and heat-sink, top quality 5 year guaranteed transformer and components, cables, coil connectors, printed circuit board, nuts, bolts, silicon grease, full instructions to make the kit negative or positive earth, and 10 page installation instructions.

#### OPTIONAL EXTRAS

Electronic/conventional ignition switch. Gives instant changeover from "Sparkrite" Ignition to conventional ignition for performance comparisons, static timing etc., and will also switch the ignition off completely as a security device, includes: switch connectors, mounting bracket and instructions. Cables excluded. Also available RPM limiting control for dashboard mounting (fitted in case on ready built unit).

**CALLERS WELCOME.** For Crypton tuning and fitting service -- phone (0922) 33008.

**PRICES INCLUDE VAT, POST AND PACKING.**

Improve performance & economy NOW

**POST TODAY!**

**Quick installation**  
No engine modification  
required

Electronics Design Associates, Dept. ET19  
82 Bath Street, Walsall, WS1 3DE. Phone: (0922) 33652


Name .....  
Address .....

Mk. 2 DIY Ass. Kit @ £11.80	QUANTITY REQD.	I enclose cheque/PO's for £
Mk. 2 Ready Built Negative Earth @ £14.97		
Mk. 2 Ready Built Positive Earth @ £14.97		
Ignition Changeover switches @ £4.30		
R.P.M. Limit systems in above units @ £2.42		Cheque No. ....

Send SAE if brochure only required.

# tech-tips

## Self adjusting AM noise limiter

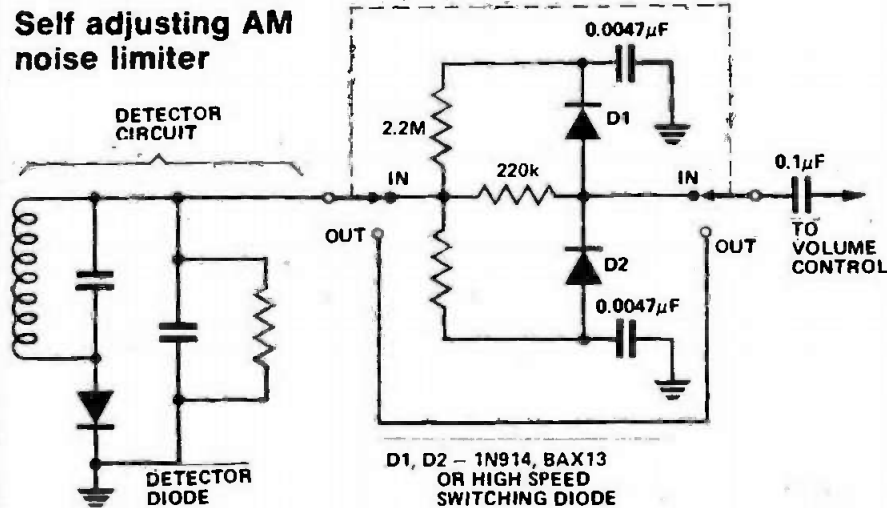

This is a very effective self-adjusting positive and negative peak noise limiter. The detector diode is part of the usual detector arrangement in a receiver and provides a negative bias which varies with the average signal strength (bias provided by D1 and D2). When a noise spike appears on the positive swing of the demodulated audio wave form, D1 conducts flattening out the spike. Similarly when a noise spike appears on negative swing of the audio, D2 conducts flattening out the spike.


The circuit causes considerable reduction in audio output when in circuit and cuts the high frequency response.

## VOLTAGE CONTROLLED CURRENT SOURCE

The voltage follower IC1, buffered by TR1 provides a current at the collector proportional to the input voltage due to R1. This current is applied to R2 which means that the voltage across it will be  $V_{in} \frac{R2}{R1}$ .

IC2 forces the voltage across R3 to equal that across R2. The zener prevents IC2's inputs from operating at the supply rail.

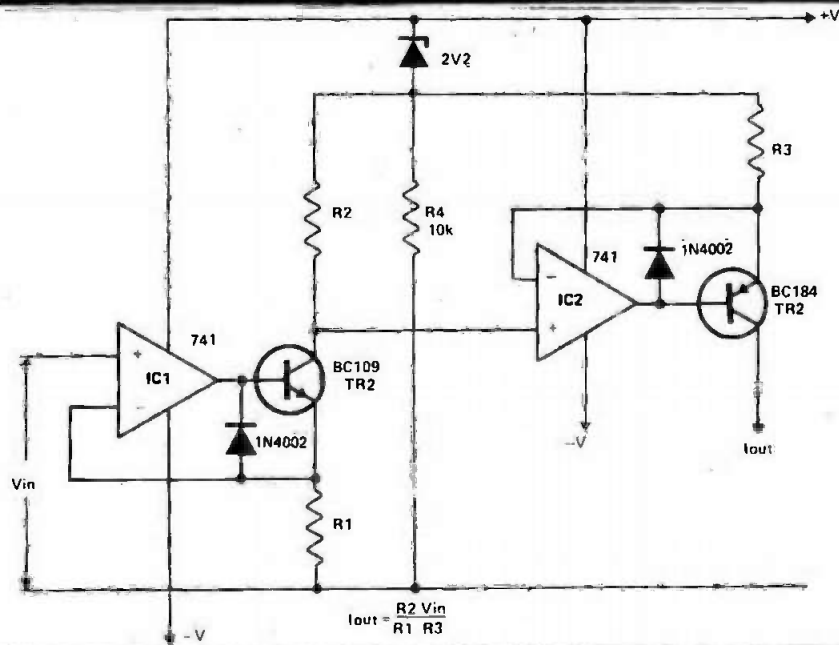In this circuit the input voltage is generated relative to the 0V rail. For maximum output voltage capability the voltage across R2 and R3 at the maximum proposed output current should be kept small. However offsets in the IC's have more effect on the linearity as the max resistance of VR2 becomes smaller - these should be nulled out.




## CHEAPO VCF!

Readers intending to build the dynamic noise limiter may be interested in the following circuit.

The circuit consists of two RC low pass filters connected by a unity gain buffer (inverting).

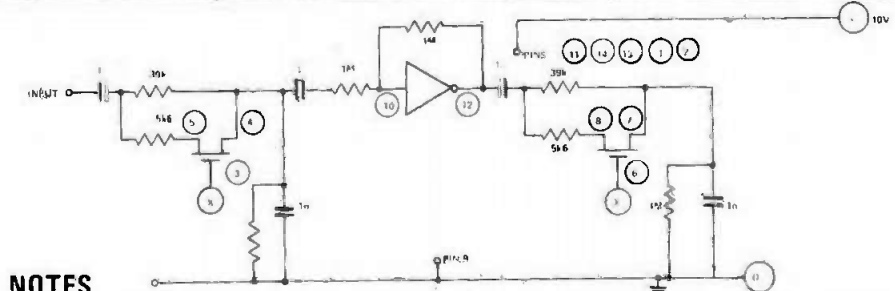The n-channel MOSFETs are used as voltage controlled resistors to vary the cut-off frequency of the two filters which are controlled by a voltage entered at points X - The additional resistors limit the variation to limits of 5 and 50kHz.



### NOTES

1. The control voltage should be positive-going, not negative-going as in the original.
2. Signal input should be restricted to 50mV, when distortion will be low.
3. The cut-off is less sharp than the

DNF VCF so less trouble can be expected from changes in bandwidth, as such changes will be less obvious.

4. A high impedance buffer is required at the output.




### SELF-CLEAR

The network consists of two resistors R2 and VR1 arranged as a potential divider, the latter being shunted with a non linear load Q1 whose value depends on the voltage developed across R1. This is related to the charge of the capacitor C1. The resistor VR1 was made variable to make the design less critical.

As soon as S is closed, C1 starts charging; at the same time the base-emitter junction is being forward biased and Q1 conducts, bypassing VR1. Voltage at point A is "low" and a set pulse is produced, therefore.

When the charge on C1 reaches a given value, Q1 stops conducting and voltage at point A rises to a stabilized value which is approx.  $4.5 VR1 / (R2 + VR1)$ .

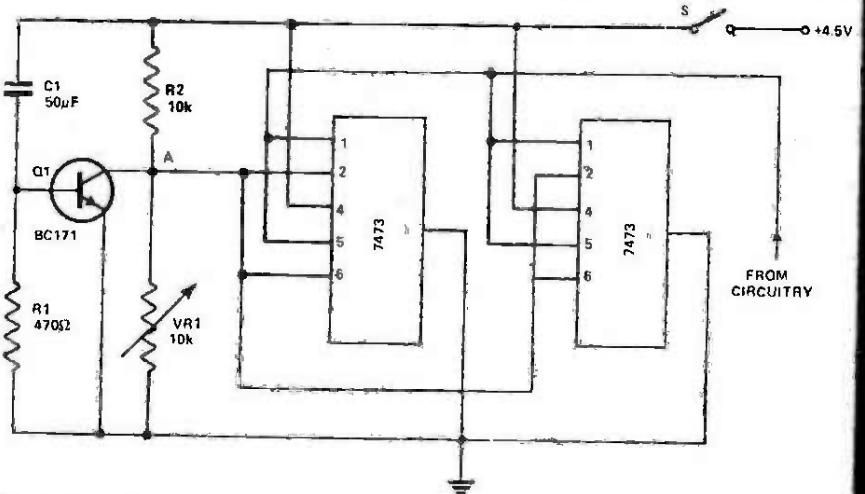Component values are not critical although R1 and R2 must be close to




the indicated values.

Any NPN silicon transistor will work the prototype being assembled with the BC171.

VR1 adjustment depends, amongst other things, on the number of flip-flops and must be adjusted in each particular case to give best results.
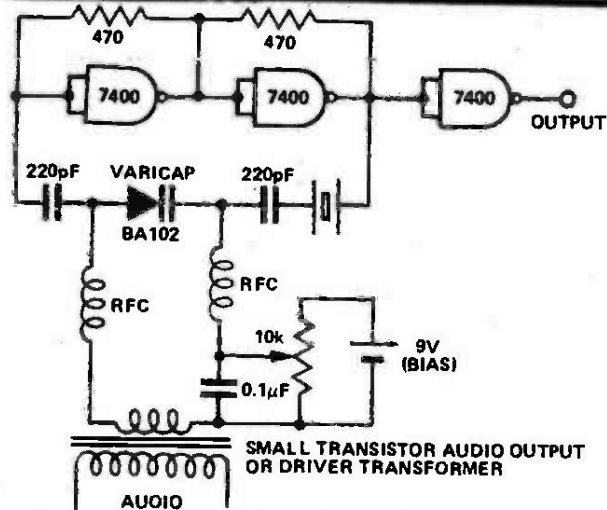
### FM modulated TTL crystal oscillator


This TTL crystal oscillator is useful for checking FM receivers or to drive multipliers-amplifiers for an FM transmitter. It will accept crystals between 1 and 18 MHz. Output level is quite high and rich in harmonics. Audio can be provided at a low level from an audio oscillator or a microphone amplifier.


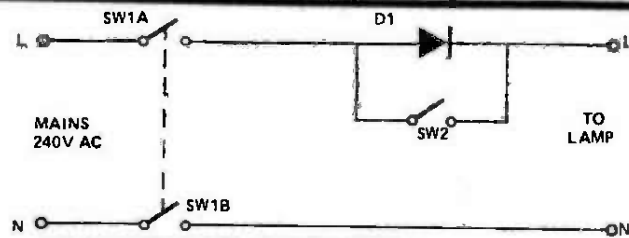
### SIMPLE AND CHEAP LIGHT DIMMER

More than one lamp may be "dimmed", but the total wattage ratings should not be exceeded. The current ratings in the table are minimum values.

With SW1, the normal mains switch, "On" and SW2 closed, the lamp operates normally. But with SW1 "On" and SW2 "open", only half the mains waveform is allowed to energise the lamp, the other half being blocked by D1. This is the "Half-on" mode. Orientation of D1 does not matter.



\* D1 VOLTAGE RATING: AT LEAST 400 PIV

D1 ..... BY126, BY127, ETC. (see table) SW2 ..... SPST MAINS SWITCH (see table for current rating)

LAMP WATTAGE: UP TO:-	100W	250W	500W	1kW
D1 & SW2 CURRENT RATING:	½A	1½A	2½A	5A

Being small, the unit could be mounted in a normal double wall-switch, utilising both switches as SW1 and SW2, or inside a table lamp.

# tech-tips



## MULTIPURPOSE AUDIO TESTER

The instrument is designed primarily to provide a cheap and reliable method of testing for wiring faults in projects. As a secondary use it may be used as a capacitor checker. Additionally the apparatus may be used as a ready made siren. The output from this instrument may also be fed to an external source, such as an amplifier.

Each circuit can be made to oscillate at audio frequencies using simply a capacitor connected from input to ground and a resistor connected between input and output. The output is detected using a crystal earpiece. Thus, simply completing the resistive arm of the circuit via the "R" sockets, causes oscillation to commence, at a frequency governed by the resistance between the sockets. Similarly, by completing the other circuit by means of connecting a suitable capacitor across the "C" sockets, the other circuit is set into operation at a frequency dependent on the unknown capacitance. Thus we have an instrument which provides a "go/no go" indication of a circuit or a component. In addition a rough order of value of the component may be obtained from the frequency of oscillation.

For use as a continuity tester, probes are simply inserted into the "R" sockets and the instrument used as a conventional "ohmmeter". The maximum detectable resistance would be of the order of 1k. Similarly, these sockets may be used to check diodes and transistors.

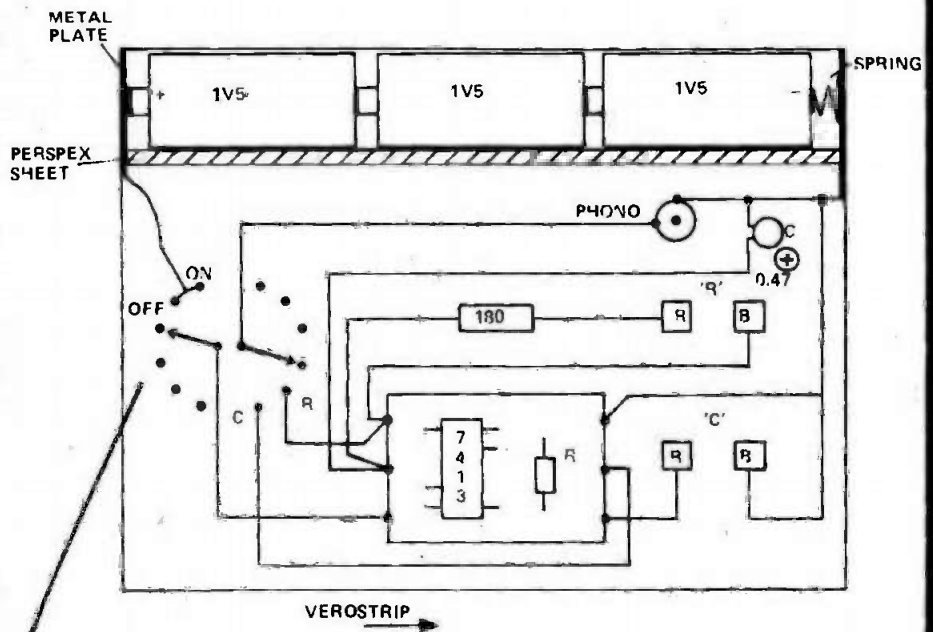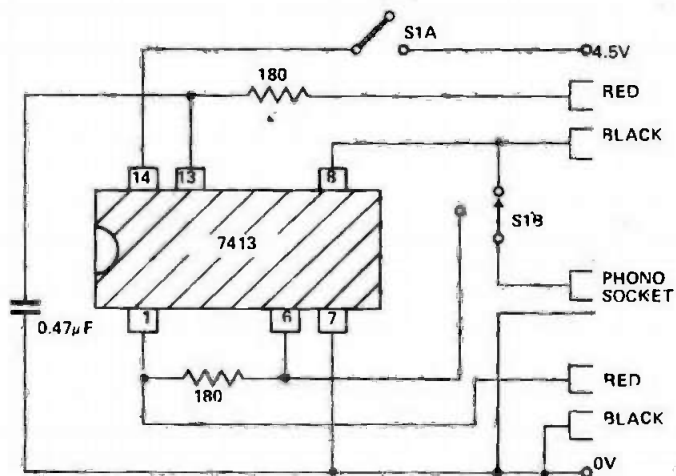Using the "C" sockets for checking capacitors, observe polarity when using electrolytics. The range of checkable capacitors is large varying from  $.22\mu\text{F}$  to  $5000\mu\text{F}$ .




## DANCING LIGHTS

This device will produce a shifting light display in time to the signal from a loudspeaker. Setting will vary according to the volume at which the

music is played. When VR1 is at maximum the lights remain lit most of the time. At minimum the lights may not come on at all. A suitable position can be established in between these two

extremes.

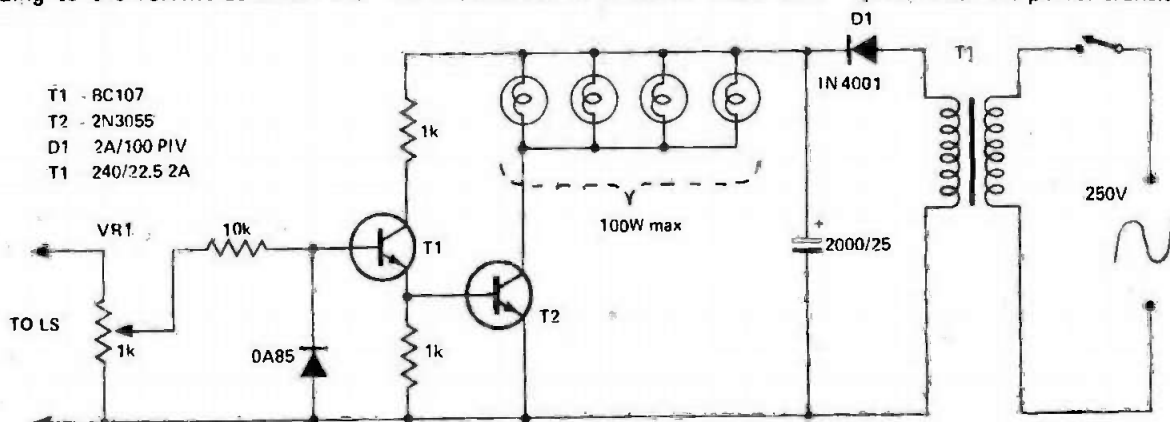The bulbs used can be any number at 25V each and the total should not be more than 100W. A heatsink should be used for the power transistor.



**complete** DIGITAL CLOCK KITS  
**TEAK CASES**  
prompt order despatch



NON ALARM **£9.60** + VAT  
£0.76

ALARM **£11.95** + £0.96

**"DELTA"**

GENUINE TEAK OR PERSPEX CASE

**DELTA DATA:** 4 Radiant Red 1/2 inch high LEDs. 12 hr display with AM/PM indication. Beautiful Burma Teak Case or Pretty Perspex in White, Black, Blue, Red, Green. Power failure is indicated by flashing display.

**MODULES:** Kits can be bought without case Non Alarm £8.00  
Alarm £10.50 incl.

**READY BUILT:** Buy a working tested module and fit your own case.  
Non Alarm £8.50. Alarm £11.00. Or put it with our case parts @  
£3.78 and save on complete clock price.  
Complete Clock ready built. 2 yr. guarantee. Non Alarm £14.00  
Alarm £16.50

**ALARM FEATURES:** Pulsed tone. Tilt operated 10 minute 'Snooze'  
period. Single switch setting. Optional extra mercury switch (45p)  
allows Alarm reset by tilting clock. Digit brightness is  
automatically controlled to suit lighting level.


**6 DIGIT:** "Comet" Non Alarm with 6 red 0.6" high digits. Complete  
kit £17.00. Case style as Delta.

**NOVUS** 650 **£5.40** 4510 **£18.20**  
**CALCULATORS:** 850 **£8.75** 6030 **£21.60**  
Send payment with order. S.a.s for complete range of clocks, calculators &  
components



**PULSE ELECTRONICS**  
**LTD.**

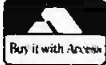DEPT. E3, 202 SHEFFORD ROAD  
CLIFTON, SHEFFORD, BEDS.  
Telephone: Hitchin (0462) 814477



# ELECTROVALUE

*the good components service  
with a still more up-to-date catalogue*

In relatively few years, Electrovalue has risen to a position of pre-eminence as mail-order (and industrial) suppliers of semi-conductors, components, accessories, etc. There are wide ranges and large stocks to choose from as well as many worthwhile advantages to enjoy when you order from Electrovalue

**CATALOGUE 8 ISSUE 2**

Second printing now ready, revised and up-dated on prices, etc., 144 pages. New items. Opto-electronics. Diagrams of components, applications, I.C. circuits. Post free 40p, including voucher for 40p for spending on order over £5 list value.

**DISCOUNTS**

On all C.W.O. mail orders, except for some items marked NETT.

**5%** on orders list value £10 or more      **10%** on orders list value £15 or more

**FREE POST & PACKING**

On all C.W.O. mail orders in U.K. over £2 list value, if under, add 15p handling charge.

**PRICE STABILIZATION POLICY**

Prices are held and then reviewed over minimum periods of 3 months, next review due April 1st.

**QUALITY GUARANTEE**

On everything in our Catalogue -- No manufacturer's rejects, seconds or sub-standards merchandise.

**ELECTROVALUE LTD**

All communications to: Section 5/4, 28 ST. JUDE'S ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Telephone Egham 3603. Telex 284475. Shop hours 9.5-3.30 daily, 9-1 p.m. Sats.

NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone (061) 432 4945. Shop hours daily 9.5-3.30 p.m.; 9-1 p.m. Sats.

**ENGINEERS**

**FREE**



**YOURSELF FOR A BETTER JOB WITH MORE PAY!**

Do you want promotion, a better job, higher pay? "New opportunities" shows you how to get them through a low-cost, Home Study Course. There are no books to buy and you can pay as you learn.

This easy to follow **GUIDE TO SUCCESS** should be read by every ambitious engineer. Send for this helpful 44-page free book **NOW!** No obligation, nobody will call on you. It could be the best thing you ever did.

**CHOOSE A BRAND NEW FUTURE HERE**

**CUT OUT THIS COUPON**

Tick or state subject of interest. Post to address below.

**ELECTRICAL & ELECTRONICS**

Practical Radio & Electronics (with Kit)

Electronic Engineering Certificate

General Elect. Eng. Certificate

C & G Elect Installations

Elect. Install. & Work

C & G Elect. Technicians

**RADIO AND TELE-COMMUNICATIONS**

Colour TV Servicing

C & G Telecoms. Technician's Cert.

C & G Radio, TV & Electronics Mech. Certificate

Radio & TV Engineering Course

Radio, Servicing & Repairs

Radio Amateur's Exam.

**AUTO & AERO**

Motor Mechanics

C & G Motor V Mechnirs

General Auto Engineering

A.M.I.M.I.

Air Registration Board Certs.

MAA/IMI Dip.

**MECHANICAL**

A.M.S.E. (Mech.)

General Mech. Eng.

Inst. Engineers & Technicians

Maintenance Engineering

Welding

**MANAGEMENT & PRODUCTION**

Computer Programming

Inst. of Cost & Management Accts.

**CONSTRUCTIONAL**

Heating Ventilating & Air Conditioning

Architectural Draughtmanship & Design

L.I.O.B.

Carpenry & Joinery

Plumbing Technology

General Building

Painting & Decorating

**DRAUGHTSMANSHIP & DESIGN**

General Draughtmanship

A.M.I.E.D.

Electrical Draughtmanship



**G.C.E.**

-58 'O' & 'A' Level Subjects  
-over 10,000 Group Passes!

**Aldermaston College**

Dept. TET 18, Reading RG7 4PF

also at our London Advisory Office, 4 Fore Street Avenue, Moorgate, London EC2Y 5EJ. Tel. 01-628 2721.

NAME (Block Capitals) \_\_\_\_\_

ADDRESS \_\_\_\_\_

Postcode \_\_\_\_\_

Other subjects of interest \_\_\_\_\_

Age \_\_\_\_\_

Accredited by C.A.C.C.

Member of A.B.C.C

**HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

# New Course in Digital Design

Understand the latest developments in calculators, computers, watches, telephones,

television, automotive instrumentation . . . .


Each of the 6 volumes of this self-instruction course measures 11¼" x 8¼" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

After completing this course you will have broadened your career prospects and considerably increased your fundamental understanding of the changing technological world around you.
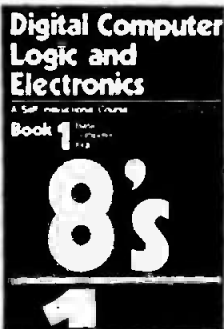
## Design of Digital Systems

A Self-Instruction Course in 6 Volumes

- 1 Computer Arithmetic
- 2 Boolean Logic
- 3 Arithmetic Circuits
- 4 Memories & Counters
- 5 Calculator Design
- 6 Computer Architecture



Also available — a more elementary course assuming no prior knowledge except simple arithmetic.


In 4 volumes:

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flip flops and Registers

£4.20 plus 80p p&p

**Offer.** Order this together with Design of Digital Systems for the bargain price of £9.70, plus 80p p&p.

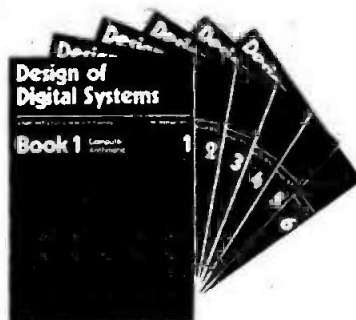Design of Digital Systems contains over twice as much information in each volume as the simpler course, Digital Computer Logic and Electronics. All the information in the simpler course is covered as part of the first volumes of Design of Digital Systems which, as you can see from its contents, also covers many more advanced topics.



£6.20

plus 80p packing and surface post anywhere in the world (VAT zero rated). Payments may be made in foreign currencies. Quantity discounts are available on request.

Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self-instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

### Guarantee — no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To: Cambridge Learning Enterprises, Dept. Dig., FREEPOST, St. Ives, Huntingdon, Cambs PE17 4BR

\*Please send me . . . . set(s) of Design of Digital Systems at £7.00 each, p&p included

\*or . . . . set(s) of Digital Computer Logic and Electronics at £5.00 each, p&p included

\*or . . . . combined set(s) at £10.50 each, p&p included

Name . . . . .

Address . . . . .

. . . . .

\*delete as applicable. ETI 9  
No need to use a stamp — just print FREEPOST on the envelope.

# New to the UK from PRONTO


Battery operated LCD read out  
**CALENDAR CLOCK KIT** - crystal accuracy  
 Bold Digits - runs on two Penlight Cells.



- Now is the time for the hobbyist to move into Advanced Technology with Pronto!
- PRONTO MODEL 301** - The first completely portable liquid crystal display, digital CALENDAR CLOCK KIT offered in the United Kingdom.
- \* Battery operation - two small alkaline cells give a minimum life of 12 months.
  - \* Superb accuracy through crystal control - of 3 minutes a year
  - \* Wide angle display with 1/2" digits
  - \* Push Buttons give choice of 3 display modes - hours minutes on 12 hour display with flashing colon, or seconds, or date.
  - \* PRONTO 301 comes complete with easy to follow

Instructions AT **£29-50** including V.A.T. You save Pounds off the recommended retail price of a comparable made up clock.

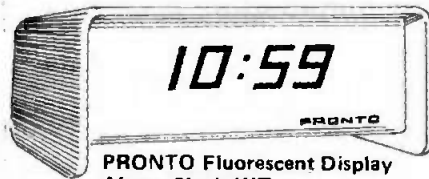**TERMS:** Cash with order - make cheque and/or postal order payable to PRONTO ELECTRONIC SYSTEMS LIMITED. (P & P - U.K. £0.45 Overseas £1.50)



**PRONTO Fluorescent Display Alarm Clock KIT**

- Wake up to the electronic age with the new PRONTO 304 Alarm Clock
- \* Large Bright Green Display
  - \* Alarm with 10 minute 'snooze' feature
  - \* AM/PM indication and simple setting
  - \* Automatic brightness control on digits governed by room lighting

- \* Ingenious gravity alarm - time setting mode switch
- \* Full assembly instructions

AT **£15-50** including V.A.T. With all PRONTO products - enquiries from the Trade, as well as the Hobbyist, are welcome, and you can also buy individual components!

**PRONTO CONSTRUCTOR'S CLUB**  
 When you buy your first Pronto kit you're automatically a Member of the PRONTO CONSTRUCTOR'S CLUB. It will not only keep you in the picture on new ideas and kits... but gives you **FREE a £2 Voucher** against the purchase of your next kit!  
 Isn't it time you joined the Club?

Please send me -

- PRONTO 301 KIT/S AT £29.50 EACH (Plus P & P)
- PRONTO 304 KIT/S AT £15.50 EACH (Plus P & P)

My cheque/P.O. for \_\_\_\_\_ is enclosed

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

Pronto Electronic Systems Ltd.  
 645/647 High Rd., Seven Kings,  
 Essex IG3 8RA. 01-599 3041


## ETI PCB'S

TITLE	PROJECT NO.	BOARD NO.	TOTAL	TITLE	PROJECT NO.	BOARD NO.	TOTAL
Int. 25W Stereo Amp.	105	014	£3.00	Magic Synthesizer	601	601A	£2.30
Dist. Power Supply	125	014	£1.48			601B	£2.30
Wide Range Voltmeter	105	022	£1.39			601C	£1.48
L.C. Power Supply	111	111	£1.43			601D	£0.9
Thermocouple Meter	113	113	£1.57			601E	£3.36
Dist. Beam Adapter	114	114	£1.00			601F	£1.11
Impedance Meter	116	116	£1.01			601G	£1.58
Digital Voltmeter	117	117A	60p			601H	£2.14
		117B	60p			601J	£2.30
Simple Frq. Counter	118	118	60p			601K	97p
The Oscilloscope	213	213	60p			601L	60p
Brake Light Warning	303	007	60p			601M	£2.75
Auto. Car Theft Alarm	305	019	90p			601P	£1.40
Int. Military Charger	309	309	90p			601N	£1.51
Tacho Timing Light	311	311	80p	Radar Int. Alarm	702	702	£1.13
Dist. Ign. Oil/Tach	312	312	£1.72	Int. P.M. Tester	751	751	£2.49
Car Alarm	313	313	67p	Light Detector			60p
Auto Amp.	314	314	65p	Print Tester			60p
Four Input Mixer	401	005A	67p	Inter. Com.			60p
Super Stereo	410	025	£1.37	Intruder Alarm			94p
100W Guitar Amp.	413	413	£1.73	Digital Alarm Clock	Zirconic	5017	£1.24
Meter Mixer	414	414A	£1.14	Ultrasonic			£1.68
		414B	£1.52	Bicycle Speedometer			60p
		414C	£1.52				
		414D	£1.05				
Diagn. Mixer	414	414E	£1.70				
		414F	60p				
The Over L.E.D.	417	417	60p				
Mixer Pre-Amp.	419	419	83p				
Int. 420 Four C/Amp.	420	420A	70p				
		420B	97p				
		420C	£1.10				
		420D	£1.10				
		420E	£1.54				
		422	£2.69				
		423	63p				
		424	£1.62				
		426	70p				
		427	£1.79				
		428	£2.19				
		429	70p				
		436	70p				
Fluorescent Lamp Dimmer	506	011	70p				
Holographic Filter	512	023	70p				
Temp. Alarm	513	026	70p				
Digital Stop Watch	520	520A	£2.05				
		520B	40p				
		524	£1.30				
		527	90p				
		529	£2.32				
		529B	£2.32				
		530	60p				
		532	87p				
		533A	£1.60				
		533B	60p				
		533C	60p				
		533D	60p				
		533E	60p				
		533F	60p				
		533G	60p				
		533H	60p				
		533I	60p				
		533J	60p				
		533K	60p				
		533L	60p				
		533M	60p				
		533N	60p				
		533O	60p				
		533P	60p				
		533Q	60p				
		533R	60p				
		533S	60p				
		533T	60p				
		533U	60p				
		533V	60p				
		533W	60p				
		533X	60p				
		533Y	60p				
		533Z	60p				

Orders of less than £5.00 Postal Orders only. Delivery time approximately 3 weeks. Large quantity orders - discount by negotiation. All P.C.B.'s prices include P&P and VAT. Majority of orders despatched within a week.
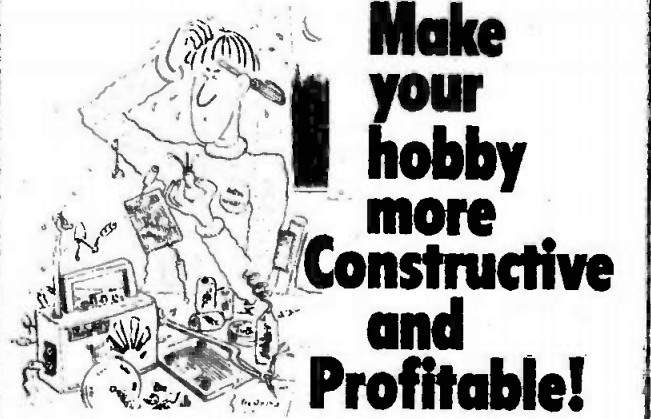
### CROFTON ELECTRONICS LTD.

35 Grosvenor Road, Twickenham, Middlesex Tel. 01-891 1923



## Make your hobby more Constructive and Profitable!

Make your interest in electronics pay, with relevant qualification

At the Polytechnic of North London you can study either full and part-time, day and evening courses from technician engineer to post-graduate level.

**The Courses offers are:**

- B.Sc. in Electronics and Communications Engineering** (If you have Maths and Physics 'A'-levels).
- Technician Engineers Course in Electronic and Communications Engineering.** (For which you need 3 'O' levels including English Language).

And a variety of other short courses.

Write to: Department of Electronics and Communications Engineering, The Polytechnic of North London, Holloway N7 8DB (01-607 6767).

The Polytechnic of North London

# TELETYPE 35R0 ASC11 CODE HEAVY DUTY CONTINUOUS OPERATION

With 240 Volt Power Supply and Paper Feed. Circuits, Diagrams. Information supplied with all purchases.

**A MUST AT £50 each**

To all purchasers of the Teletype 35R0 a **REBUILDABLE** Keyboard can be purchased for £10 only. Attractive cast alloy front panel, vertical mount, size 16 1/2 x 15 x 5 1/2" containing 72 push buttons with manual or electrical reset (28V) with provision for labelling with your code; 65 illuminated symbols or functions (complete with 28V lamps) which again you can change; 15 bit front panel microswitch assembly to enable your coded cards to be read (sample supplied) and host of other electronic parts. Complete with circuit diagrams. Now only £10 each.

## ROYAL INVERTERS

Manufactured USA. 28V DC input. Output 115V AC 400HZ up to 2KVA. Brand new. Crated.

## THE LATE MODEL MARCONI OSCILLATOR TF855A/1

in superb condition covering 25HZ to 12MHZ sine wave in 3 ranges and 50HZ to 150KHZ square wave. High output 31.6V. Meter scaled in volts and dBs.

## SOLARTRON AC MILLIVOLT METER VF252

1.5MV to 150V full-scale in 10 ranges. 6" meter ±1%. Good condition.

## AVO RF SIGNAL GENERATOR

AM Modulation. Freq range 2 to 250MHZ. 240V operation. Suitcase style. Size approx. 15" wide x 10" high x 6" deep.

ALL ITEMS **£22.50** each  
SPECIAL OFFER — pick 3 different items of the 5 for

**£60**

Carriage £2.50 each or £5 for 3

## AVO VALVE TESTED CT160

"The Suitcase". Size approx. 15" wide x 10" high x 11" deep.

### TRANSFORMERS — All 240V 50HZ

Type A 17.0-17V 250 MA; 7.50-7.5V; 250MA 0-20V 5Amps; 0.4V 5 Amps; 0-1.1.5V 5 Amps. £2 ea. P&P £1.25.  
Type B 17.0-17V 250MA; 8.0-8V 250 MA; 0-12.5-13.5V 5 Amps; 0-1.5-2V 5 Amps; £1.50 ea. P&P £1.  
Type C 19.0-19V 250MA; 8.0-8V 250MA; 0-7.5V 5 Amps; 0-1.4V 5 Amps. £1.25 ea. P&P £1.25.  
Type D 34V 4 Amps; 19V 4 Amps; 17V 4 Amps; £3 ea. P&P £1.25.  
Type E 3V 1 Amp. 25p ea. P&P 50p.  
Type F 17V 1 Amp. 85p ea. P&P 50p.  
Type G 20.0-20V 200 MA; 0-6V 100MA; 75p ea. P&P 75p. Atlantic series.  
All Brand New. (APT surplus types A, B, C & D; Honeywell surplus type E; Recordacall surplus type F; Parmeko Atlantic series type G).

Type GEC 924F 3 1/2" dia. (Replacement for Telequipment D33 & Solartron 1016 scopes) £30 ea. P&P £1.50.

SEMICONDUCTORS — All at 8p ea. P&P extra. Guaranteed all full spec. devices. Manufacturer's markings.  
BC147; BC158; 2N3707; BC107; BF197; BC327; 2N4403; BC172B; BC261B; BC251B; BC348B; BC171A/B.  
2N3055RCA 50p ea. P&P 8p.  
2N5B79 with 2N5881 Motorola 150 Watt Comp. pair £2 pr. P&P 15p.  
\*Linear amp 709 25p ea. P&P 8p

VARIACS 240V input 0-270V output.  
8 Amp £18 ea. 20 Amp £30 ea. Carr. extra.

BNC Plug to BNC Plug lead, assembled ready to use 75p ea. P&P 20p.  
Ex-eq. BNC Socket 15p. BNC Plug 20p. BNC Plug & Socket 30p pair. P&P 15p.

Type GEC 924E 3 1/2" dia. (Replacement for Solartron 1015 scope) £20 ea. P&P £1.50.  
Magnetic Deflection  
120P7 12" round. Blue with yellow afterglow. £1 ea.  
And for the VDU BUILDERS  
M3B-111GH Rectangular 30 x 20cm Green Trace. Superb value £12 ea.  
or Economy type CME1220 24 x 18cm. White Trace. £9 ea.

CRYSTALS. High quality B7G. etc.  
2MHZ £2.20 ea.  
1MHZ £2.75 ea.  
100KHZ £2.50 ea.  
50KHZ £3 ea.  
20KHZ £4.50 ea.  
P&P all 50p.  
\*4.43MHZ CB Crystal at 25p ea. P&P 15p

\*SPECIAL OFFER  
Guaranteed full spec. devices. Manufacturer's markings.  
BC 204 & BC 207A 4p ea. P&P extra.

\*TELEPHONES  
Post Office Style 746. Black or two-tone Grey £8.50 ea.  
Modern Style 706 Black or two-tone Grey £4.50 ea.  
Modern Standard Style in Grey or Black with a place to put your fingers like the 746. £3 ea. As above but discoloured Grey only £2 ea. All telephones complete with standard dial and bells. P&P all styles 75p ea. Handsets, complete with 2 inserts and lead £1.75 ea. P&P 65p.

NEW — UPGRADED CONTENTS — FOR LESS MONEY  
\*31b Electronic Goodies £1.60 post paid  
\*High Value Printed Board Pack — hundred of components, transistors, etc. — no flat to the board transistors £1.85 post paid

VERY SPECIAL PRICES  
\*1000f Feed thru Capacitors 10 for 30p. P&P 15p.

\*BEEHIVE TRIMMERS 3/30pf. BRAND NEW.  
10 Off 40p, P&P 15p. 100 off £3.50, P&P 75p. 500 off £15, P&P £1.25; 1,000 off £25, P&P £1.50.

HIVAC Miniature NEONS  
App 60v Brand New. 10 off 20p. P&P extra.

LARGE RANGE ELECTROSTATIC VOLT-METERS. from 0-300V 2" £3; to 250KV Max.  
General guide 5KV 3 1/2" £5; thereafter £1 per KV P&P 75p.

MARCONI TF1101 Audio Oscillator. 20c/s to 200kc/s. Low distortion. 80db step attenuator. £65 each.

MUFFIN Fans. 115Volt. Size 5 x 5 x 1 1/2". Superbly quiet and reliable. Ex-eq. but tested. £1.50 ea. P&P 75p.  
IBM CLOCKS — SLAVES. 1 1/2". £3 ea. P&P £1; 1 7/8" £5 ea. Plus Carr.; 2 3/8" £7 ea. Plus Carr.; ITR CLOCKS SLAVES 7 1/2" £5 ea. P&P 75p.  
\*Meter PACKS — 3 different meters £2, P&P £1.

DON'T FORGET YOUR MANUALS. S.A.E. with requirements.  
GRATICULES 12 x 14 cm high quality plastic 15p ea. P&P 10p.  
\*CAPACITOR Pack. 50 Brand New components. only 50p. P&P 48p  
\*TRIMMER PACK. All Brand New. 2 Twin 50/200pf ceramic; 2 Twin 10/60pf ceramic; 2 min. strips with 4 preset 5/20pf on each; 3 air spaced preset 30/100pf on ceramic base 25p the lot, P&P 15p.  
RESETTABLE COUNTERS: 4 digit by Stonebridge/Sodeco 1000ohm coil £2 ea. P&P 35p

\*POTENTIOMETERS — All 5p each. P&P extra. Metal bodied AB Linear. PCB mount. Brand new. 10K single; 100K Ganged; 250K Ganged; 100K Ganged concentric shafts.

FIBREGLASS BOARD PACK. More board — less money. Large pieces Not less than 2.5 sq. ft. for 95p, P&P 65p.  
Double or single sided cut to any size. New Lower Price 1p per sq. in. P&P extra.

### 20HZ to 200KHZ SINE AND SQUARE WAVE GENERATOR

In four ranges. Wien bridge oscillator thermistor stabilised. Separate independent sine and square wave amplitude controls. 3V max sine, 6V max square outputs. Completely assembled P.C. Board, ready to use. 9 to 12V supply required. £8.85 each. P&P 35p. Sine Wave only £6.85 each. P&P 35p.

### WIDE RANGE WOBBLULATOR

5MHZ to 150MHZ (useful harmonics up to 1.5GHZ) up to 15MHZ sweep width. Only 3 controls preset RF level sweep width and frequency. Ideal for 10.7 or TV IF alignment filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6.3V AC and use within minutes of receiving. All this for only £6.75. P&P 35p (Not cased, not calibrated).

Minimum Mail Order £2. Excess postage refunded

Unless stated — please add £2.50 carriage to all units

VALUE ADDED TAX not included in prices — Goods marked with \* 12 1/2 % VAT, otherwise 8 %  
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order

Open 9 a.m. to 5.30 p.m., Mon. to Sat.



# CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel. Reading 582605

# For Toshiba say Erie



If you're looking for ex-stock, competitively priced solid-state devices, look no further! Because at Erie, we are offering the comprehensive Toshiba range. It includes signal and power transistors, FETs, diodes, ICs, and LEDs (single and 7-segment).

Here's a selection of Toshiba devices, with prices for quantities from 1 to 24 inclusive.

15% discount applies to all orders for quantities of 25 to 99. If you want 100 or more of any one item, special prices apply—send for price list direct from Erie, or complete the reader service card.

Data sheets for devices ordered are supplied free on request, but if you want data sheets only, please send top for each set of device data, to cover costs.

P & P of 30p is applicable on all orders up to 100 devices (any mix of types).

VAT Please add 12½% for VAT to all prices, except those marked with an asterisk (\*) which are rated at 8% VAT.

## TRANSISTORS

### Small Signal (2-5B)

2SA 561 PNP	13p
2SA 562 ..	12p
2SA 493 ..	17p
2SA 495 ..	12p
2SC 372 NPN	9.5p
2SC 373 ..	9.5p
2SC 382 ..	26p
2SC 383 ..	24.5p
2SC 388A ..	22.5p
2SC 733 ..	6p
2SC 734 ..	11.5p
2SC 735 ..	11p
2SC 1000 ..	16p
2SC 1681 ..	16p
(TO-92)	
BC 451 NPN	11p
BC 452 ..	11p
BC 453 ..	11p
BC 454 PNP	11.5p
BC 455 ..	11.5p
BC 456 ..	11.5p

### Plastic Power (2-7)

S1234 NPN	33.5p
(TO-126)	
BD 135 NPN	33.5p
BD 137 ..	36.5p
BD 138 PNP	40p

BD 139 NPN	40p
BD 140 PNP	44p
(TO-220AB)	
*2SA 473 PNP	40p
*2SA 489 ..	75p
*2SC 790 NPN	50.5p
2SC 1173 ..	35.5p
*2SC 1447 ..	50.5p
*2N 5296 ..	59p
Metal Power (TO-66)	
2SC 515A NPN	48.5p
2SC 782 ..	£1.08
(TO-3)	
*2SC 643A ..	£2.05
2SC 1434 ..	£14.30
*2SC 1576 ..	£2.43
2SC 1617 ..	£1.29
*2N 3055 ..	£0.86
*S 2530A ..	£3.48
S 1299 ..	£4.09
Integrated Circuits	
TA 7093P	£1.49
TA 7109AP	£1.57
TA 7117P	£2.36
TA 7205P	£1.55
F.E.T.	
(2-5J)	
*2SK12	£1.04
2SK30A	27p
*3SK35	£1.45

## DIODES

Zener	
05Z5.6	14p
05Z6.2	12p
05Z6.8	13p
05Z7.5	13p
05Z8.5	13p
05Z9.1	13p
05Z10	13p
05Z11	13p
05Z12	13p
05Z13	13p
05Z15	13p
General Purpose	
S5089A	7.5p
(IN4001)	
S5089B	8p
(IN4002)	
S5089F	11p
(IN4006)	

Vari Cap	
1S1658	25p
Switching	
1S1554	4p
Pulse Rectifier	
1S2756	23.5p
Diac	
1S2093	25p
Thyristors	
SF0R 2B41	52.5p
Triac	
*SM6G14	£1.61
Uni Junction	
*2SH21	57p

Light Emitting Diodes	
TLR 102	21.5p
TLR 103	21.5p
TLR 104	21.5p
TLR 105	21.5p
TLR 106	21.5p
TLR 114	30p
TLG 102	36.5p
TLG 103	35.5p
TLG 105	35.5p
Seven Segments	
TLR 301	£1.08
TLR 302	£2.22
TLR 306	£3.08
TLR 307	£3.08

**ERIE ELECTRONICS LIMITED**  
South Denes, Great Yarmouth, Norfolk.  
Tel: 0493 56122 Telex: 97421

Components **ITT**

# Metac Digital Watches



## TLC4 LIQUID CRYSTAL ELECTRONIC WATCH

Continuous display with backlighting, 6 function watch. Hours/minutes/seconds/date/a.m./p.m. setting. Available in 18ct. Gold/Rhodium plated. Slimline Case.

£29.95 + £2.40 VAT  
2 year Guarantee



## TLE5EA QUARTZ CRYSTAL ELECTRONIC WATCH

8 separate functions, Hours/minutes/day/date/a.m./p.m. indicators/Auto-Fade. Available in 18ct. Gold/Rhodium plated. Slimline Case.

£21.95 + £1.80 V.A.T.  
2 year Guarantee



## DIGITAL MAINS CLOCK

Bright Planar Gas digit display. A.M./P.M. Indicator and flashing second indicator, 24 hour bleeper alarm, 5 minute repeater. Mains failure indicator. 5" across x 3½" deep. Attractive White Case. Hundreds sold.

£13.95 Incl. V.A.T.



## MISTRAL DIGITAL CLOCK

In kit or built form. Large 4 digit display. Push button setting. 12-24 hour read out. Pleasing green display. Pulsating second indicator. Build in 1 hour.

Complete kit £11.07 Incl. V.A.T.  
Built Clock £14.95 Incl. V.A.T.

REMEMBER with every WATCH you get METAC SUPER COVER. Full 2 years guarantee. Two year replace or repair if faulty. Free Calibration check 1st, 2nd & 3rd year. Free Technical advice.

To METAC INTERNATIONAL, Cross Lane, Braunston, Northants. Tel: Rugby 890672

Please supply the following:—

Name .....

Address .....

I enclose cheque/Postal Order/Money Order

I wish to pay by Barclay Card/Access and my number is

Signature .....

Mail Order Customers. Please add 58 pence per order to cover postage and insurance.

# MINI-ADS

FOR DETAILS ON ADVERTISING IN  
MINIADS, OR ELSEWHERE IN ETI,  
CONTACT: BOB EVANS, 01-730 8282

## CMOS WITH DISCOUNTS!

Any Qty	10%	25%	100%	333%	1000+
4000/4000	0.20	4000/	1.24	14174/	1.00
4001/4001	0.20	4001/	22.86	14174/	1.04
4002/4002	0.20	4002/	10.18	14194/	1.17
4008/4008	1.31	4063/	1.22	14501/	0.20
4007/4007	0.20	4006/4006	0.60	14502/4502	1.39
4008/4008	1.87	4067/	4.13	14503/	9.75
4009/4009	0.80	4008/4008	0.24	14506/	4.38
4010/4010	0.80	4009/4009	0.24	14508/	0.57
4011/4011	0.20	4010/4010	0.24	14507/4030	0.80
4012/4012	0.20	4011/4011	0.24	14508/4500	3.00
4013/4013	0.08	4012/4012	0.24	14510/4510	1.31
4014/4014	1.12	4013/4013	0.24	14511/4511	1.74
4015/4015	1.12	4014/4014	0.24	14512/	1.03
4016/4016	0.80	4015/4015	1.71	14514/4514	3.47
4017/4017	1.12	4016/4016	0.85	14515/4515	3.47
4018/4018	1.12	4017/4017	0.24	14518/4518	1.51
4019/4019	0.80	4018/4018	0.24	14517/	4.02
4020/4020	1.24	4019/4019	0.24	14518/4518	1.39
4021/4021	1.12	4020/	0.80	14519/4018	0.37
4022/4022	1.87	4020/	0.80	14519/4520	1.38
4023/4023	0.20	4020/	1.74	14521/	2.77
4024/4024	0.87	4023/4023	0.89	14522/	2.15
4025/4025	0.20	4024/	2.08	14524/	N/3
4026/	1.92	4025/	1.10	14526/	2.15
4027/4027	0.80	4026/	1.18	14527/4527	1.78
4028/4028	1.80	4027/	0.88	14528/4098	1.22
4029/	1.27	4028/	1.22	14529/	1.72
4030/4030	0.80	4029/	2.03	14530/	0.95
4031/	2.46	4030/	1.78	14531/	1.74
4032/4032	1.19	4031/	2.10	14532/4532	1.39
4033/	1.55	4032/	2.16	14534/	8.15
4034/4034	2.11	4033/	2.28	14536/	4.08
4035/4035	1.31	4034/	0.88	14537/	13.17
4036/	3.09	4035/	0.18	14538/	1.24
4037/	1.88	4036/	2.21	14541/	1.52
4038/4038	1.20	4037/	4.30	14543/	1.82
4039/	3.08	4038/	1.73	14549/	4.18
4040/4040	1.18	4039/	2.26	14552/	10.50
4041/	0.80	4040/	2.38	14553/	4.88
4042/4042	0.83	4041/	1.18	14554/	1.67
4043/4043	1.12	4042/	4.25	14555/4555	1.81
4044/4044	1.04	4043/	5.78	14556/4556	1.81
4045/	1.58	4044/	9.54	14557/	4.55
4046/4046	1.48	4045/	17.07	14558/	1.25
4047/	1.01	4046/	7.35	14559/	4.18
4048/	0.80	4047/	2.87	14560/	2.17
4049/4049	0.80	4048/	4.98	14561/	0.70
4050/4050	0.80	4049/	7.83	14562/	9.98
4051/4051	1.04	4050/	11.58	14566/	1.87
4052/4052	1.04	4050/	2.87	14568/	3.15
4053/4053	1.04	4051/	2.87	14569/	3.72
4054/	1.29	4052/	0.51	14572/	0.72
4055/	1.48	4053/	1.18	14580/4018	8.35
4056/	1.48	4054/	1.18	14581/4018	4.30
4057/	20.81	4055/	1.18	14582/4018	1.64
4058/	0.20	4056/	1.18	14602/	0.84
			14605/		1.18

Free on request: Data on AT-5-1274 and NE5253 clock chips, 4 and 8 digit status clock, monostable circuit, 4000 (270) timer, and L.E.D. displays if you can send us S.A.E. in envelope 10c stamp for each.

CLOCK CHIPS AT-5-1274 & 4 digit basic clock CS.50. MK 50253 4/6 digit economy red LED displays (Class II quality, but guaranteed by us, fully returnable if not satisfied).

DL-7276/OL-7282 12mm (0.5") Double Digit ETI. DL-7476/OL-7482 16mm (0.6") ETI.50.

DR-AMP CA 3130 FET-Mixer-CMOS ETI.50. CA 3140 FET-Digital 85p. 741 Monthly 25p.

Turns: C.W.R. Add VAT to all prices of 8%. Post etc. UK 25p per order, export £2.00 (no VAT). All orders processed on day of receipt.

**GREENBANK ELECTRONICS (Dept. 19c)**  
94 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG, England. Tel: 051-645 3391

## PRINTED CIRCUITS and HARDWARE

Readily available supplies of Constructors' hardware, Aluminium sheet and sections, Printed circuit boards, top quality for individual designs.

Full range of E.T.I. boards always in stock. Prompt service.

Send 15p for catalogue.

**RAMAR CONSTRUCTOR SERVICES**  
MASONS ROAD  
STRATFORD-ON-AVON  
WARWICKS. Tel. 4879

## This Month MORE SPECIAL OFFERS, while stocks last, of BRAND NEW DEVICES

- These are not accessory layouts
- 4 off PRO 500 0.5" Cam. Cath. 7-seg. LED Display ..... £3.95
  - 4 off PRO 357 0.375" Cam. Cath. 7-seg. LED Display ..... £3.15
  - 5 off RV 117 0.2" Red LED with Clip ..... 90p
  - Power Pack No. 1: Contains 2 off TIP2955, 2 ON TP3055 + 90p Mts ..... £2.10
  - Power Pack No. 2: Contains 5 off 1N4002, 5 off 1N4003, 5 off 1N4004 ..... 50p
  - Power Pack No. 3: Contains 2 off 1A/400V Bridges, 2 On 2A/600V Bridges ..... £1.00
  - AUDIO PACK No. 1: Contains 8 Transistors + circuit for 10W 8 ohm Amplifier ..... £2.50
  - AUDIO PACK No. 2: Contains 8 Transistors + circuit for 20W 8 ohm Amplifier ..... £2.25
  - Project Pack No. 1: Contains 2 off of each BC107/8/9, BF750/51/52, 2N3085 (14 Devices total) ..... £2.40
  - Digit Pack No. 1: Contains 1 off each red, green, yellow, orange, 0.125" LED with Clips ..... 80p
  - 1,000, YES, ONE THOUSAND 10W/12V Axial Lead Capacitors (16mm x 7mm Dia.) ..... £8.50
- VAT INCL ALL ORDERS, 20p P&P
- AUDIO-OPTICS, 19 MIDLEWAY CHINNOR, OXON. Tel. 0844 52683**

## PRECISION POLYCARBONATE CAPACITORS

440V AC  
All High Stability - Extremely Low Leakage

RANGE VALUE (pF)	DIMENSIONS (mm)	PRICE EACH	5% DC Range	±1%	±2%	±5%
0.1µF	27 12.7	85p	0.47µF	11.32	7.7	31p
0.22µF	33 16	95p	1.0µF	11.38	9.1p	60p
0.25µF	33 16	92p	2.2µF	12.94	11.32	75p
0.47µF	33 19	£1.10	4.7µF	12.92	11.32	1.23
0.5µF	33 19	£1.16	6.8µF	13.44	12.52	1.47
0.68µF	50.8 19	£1.25	10µF	13.98	13.32	1.81
1.0µF	50.8 19	£1.37	15µF	17.14	14.78	2.28
2.0µF	50.8 25.4	£1.95	22µF	19.86	16.14	£3.90

TANTALUM HEAD CAPACITORS - Values available: 0.1, 0.22, 0.47, 1.0, 2.2, 4.8, 8.0µF at 15V/25V or 35V; 10µF at 18V/20V or 25V; 22.0µF at 6V or 16V; 33.0µF at 6V or 10V; 47.0µF at 3V or 6V; 100.0µF at 3V. ALL at 12p each, 10 for £1.10, 50 for £5.00, 100 for £9.00.

TRANSISTOR & IC'S

Part No.	IC No.	Price	Part No.	Price	
AC128	11p	BC287	12p	OC74-IC45	20p
AC176	18p	BC547/53KA	12p	OC71-72	20p
AD149	40p	BCY72	13p	2N2926G	12p
AF178	48p	BD131/132	39p	2N2928G	11p
AF239	38p	BF115/167	24p	2N3054	50p
BC107-R/9	9p	BF173	22p	2N3055	38p
BC114	12p	BF178	22p	2N3702	52p
BC147-R/9	10p	BF184	22p	3744	11p
BC153	18p	BF194/195	12p	TIP30A	32p
BC157-R/9	12p	BF196/197	13p	NPN10A	35p
BC177	18p	BF200	27p	TIP32A	64p
BC182/182L	11p	BF262/263	60p	TIP3055	65p
BC183/183L	11p	BFY30-51-52	20p	NPN10A	49p
BC184/184L	12p	BFY84/86/88	20p	NE555	61p
BC212/212L	12p	BFY85	25p	741 N pin	32p
BC213/213L	11p	BR101	41p	2N414	£1.15
BC214/214L	11p	CE172	33p	SN76613ND	£1.39

POPULAR DIODES—1N914 6p. 8 for 45p. 16 for 80p. 1N916 6p. 6 for 35p. 14 for 90p. 1N44 5p. 11 for 50p. 25 for 110p. 1N4148 5p. 6 for 27p. 22 for 10p. 1N4001 34p. 002 8p. 003 6p. 004 7p. 006 8p. 007 8p.

LOW PRICE ZENER DIODES—400mw. Tol. ±5% at 5mA. Values available: 3V, 3.3V, 3.6V, 4.7V, 5.1V, 5.6V, 6.2V, 6.8V, 7.5V, 8.2V, 9.1V, 10V, 11V, 12V, 15V, 13.5V, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V. All at 12p each; 5 for 33p; 10 for 65p. SPECIAL OFFER: 100 Zeners for £6.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 80°C. 1/4W at 70°C. E12 series only—10mm 2.2 to 3.2MΩ. ALL at 12p each, 5p for 10 of any one value; 70p for 100 of any one value.

SPECIAL PACK, 10 of each value: 2.2 to 2.2MΩ (740 resistors) 65. SILICON PLASTIC RECTIFIERS—1.5 amp, brand new wire ended DO18; 100 P.I.V. 7p (4 for 26p), 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2.5 amp, 200V 40p, 350V 50p, 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1V only, ALL at 5p each; 502 100Ω, 220Ω, 470Ω, 680Ω, 1kΩ, 2.2kΩ, 4.7kΩ, 6.8kΩ, 10kΩ, 15kΩ, 20kΩ, 47kΩ, 68kΩ, 100kΩ, 250kΩ, 600kΩ, 1MΩ, 2.5MΩ, 5MΩ.

PLEASE ADD 30p POST AND PACKING ON ALL ORDERS. ALL EXPORT ORDERS PLEASE ADD COST OF SEA AIR MAIL. PLEASE ADD N. VAT to all items except those marked with which are 12%.

Send S.A.E. for lists of additional extra stock items. Wholesale price lists available to bona fide companies.

**MARCO TRADING**  
(Dept. P3)  
The Old School, Edstaston, Wem, Shropshire  
Tel. Whixall (Shropshire) (STD 094872) 464/5  
(Proprs: Minicos Trading Ltd.)

## Same Day Despatch Glass-Fibre P.C.B.s

G.P. Power Supply	ETI 131	90p
Sweet Sixteen Amp	ETI 457	180p
Woo Woo Unit	ETI 455	240p
Touch Switch	ETI 539	75p
Audio Level Meter	ETI 438	85p
Logic Tester	ETI 122	150p
INT. 2.5 Stereo Amp		375p

OTHER PROJECTS AVAILABLE Ex STOCK

ETI 022	15p	ETI 309	100p	ETI 441	50p
ETI 116	85p	ETI 312	170p	ETI 529A	225p
ETI 117A & B	90p	ETI 413	140p	ETI 529B	225p
ETI 120	80p	ETI 422	270p	ETI 533A&B	100p
ETI 121	60p	ETI 424	140p	ETI 534	50p
ETI 122	150p	ETI 433A	90p	ETI 751	225p
ETI 128	175p	ETI 433B	90p	ETI 951	30p

RESISTORS H.S. Carbon Film 1/4w 5% E12 Series 1p  
Mixed Values 50 45p 100 80p

ELECTROLYTICS 10µF 12v 10 25 50 330µF 25v 6p  
TANTALUM BEAD 2.2 & 4.7µF only 7p

THIS MONTHS SNIPS

CA 3046	40p	uA 741	25p	7474	25p
NE 555	40p	7470	7p	7493	40p

Miniature Glass Reed Switches. 10 for 50p  
Toggle Switches by Arrow. DPST. 240v. 3A. 17p  
Slide Switches. SPST. 240v. 3A. 8p

STOP PRESS FRONT PANEL for ETI 122. 200p

All prices include VAT. Add 20p P & P. List 10p.

**R.F. EQUIPMENT SPARES Ltd**  
3 LACY CLOSE WIMBORNE DORSET

## GLASS FIBRE P.C.B.'s

Send 1:1 master and 7p per square inch tinned or 10p per square inch drilled and tinned PLUS 40p per board. Discount for quantity.

E.T.I. boards glass fibre drilled and tinned.

100w guitar amplifier E.T.I. 413 £1.40  
Mixer pre amplifier E.T.I. 419 60p  
Audio 1 level meter E.T.I. 438 75p  
G.P. Power Supply ETI 131 96p  
Sweet Sixteen Amp ETI 457 £1.92  
High Power Beacon ETI 240 52p  
Sound Light Flash Trigger ETI 514B 49p

**PROTO DESIGN**  
4 Highcliffe Way, Wickford, Essex  
SS11 8LA

## P.C.B.s FOR E.T.I. PROJECTS

G.P. Power Supply	ETI 131	94p
Sweet Sixteen Amp	ETI 457	£1.94
Woo-Woo	ETI 455	£2.65
Touch Switch	ETI 539	58p
Marker Generator	ETI 706	50p
Audio Expander-Compressor	ETI 443	£3.00
Temperature Meter	ETI 130	50p
Calculator Stopwatch	ETI 534	42p
Audio Noise Generator	ETI 441	41p
Audio Millivoltmeter	ETI 128	£1.85
Audio Level Meter	ETI 438	75p
Active Crossover	ETI 433A	86p
Active Crossover	ETI 433B	86p
Logic Probe	ETI 120	35p
Logic Pulsar	ETI 121	35p
Logic Tester	ETI 122	£1.85
Tone Burst Generator	ETI 124	83p
Graphic Equalizer	ETI 427	£1.96
International 25 Amplifier		£4.22
F.M. Tuner	ETI 751	£2.23
Line Amplifier	ETI 430	35p
Electronic Ignition	ETI 312	£1.86
Impedance Meter	ETI 116	88p
Digital Display	ETI 533a	42p
Digital Display	ETI 533b	35p
Digital Voltmeter	ETI 117a	35p
Digital Voltmeter	ETI 117b	35p

New projects and others in TOP PROJECTS BOOK 3 available at 1.25p per sq. cm. for single sided or 1.5p per sq. cm. for double sided (min. 35p). NOTE: All boards are fibre-glass and price inc. DRILLING AND TINKING.

Send S.A.E. for list of boards and components available including cases, panels and hardware etc.

Mail orders, please, to: D.B.M. PRODUCTS  
Unit 14 Southern Road, Aylesbury, Bucks.



## TRANSISTORS + ICs

AC127	16p	LM301A TD99	52p
AC28	16p	LM709 T999	41p
AD161	44p	LM710 1401L	49p
AD162	44p	LM740 14 DII	82p
9C107/8	11p	7400 TTL	16p
BC109	12p	7401	16p
BC182/182	12p	7402	16p
BC183/183L	12p	7404	19p
BC184/184L	13p	7410	16p
8FY50	21p	7413	35p
8FY51	20p	7420	16p
8FY52	20p	7430	16p
8D131	43p	7440	16p
8D132	44p	7441	85p
8RY39	48p	7447	95p
TIP29A	48p	7474	36p
TIP32A	52p	7475	50p
2N1711	25p	7490	45p
2N3053	25p	74121	37p
2N3054	67p	7141	85p
2N3055	55p	C106D SCR	70p
2N3702	12p	S-DEC	
OC44	22p	Broadboard	£2.15
OC45	22p	T-DEC	
OC71	22p	Broadboard	£3.93
741 Op. Amp.	29p		

Prices VAT inclusive + 20p P&P  
1,500 types of Diodes, Transistors, + ICs, SCRs, Triacs, in stock plus; Full range of passive components.  
List 10p + SAE

### AITKEN BROS. & CO.

38 HIGH BRIDGE NEWCASTLE-ON-TYNE NE1 1EW  
Your Electronic Component Centre for North East.  
Callers welcome

SHOP FROM HOME with our catalogue. Fully illustrated and covering over 3,000 components, audio and disco accessories, tools and test meters. Reviewed as one of the best catalogues available. Send 30p now for your copy (issue No 5). Access, Giro, Barclaycard, Government and educational orders accepted. (Giro No 331-7056).

**B. H. COMPONENT FACTORS LTD.**  
Leighton Electronics Centre  
59 North St., Leighton Buzzard, Beds  
Tel: 2316 (0286) Shop hours: 9-12.30, 1.30-5 p.m. Closed Wednesday

TURN YOUR SURPLUS capacitors, transistors, etc., into cash. Contact COLES-HARDING & CO., P.O. Box 5, Frome, Somerset. Immediate settlement.

**MM5316** sophisticated alarm clock chip, £4.99.

**5-LT-02** matched full alarm clock display, £5.60.

**10% off** over £10. Post 25p.  
Pinewood Electronics  
57 Monmouth Road, Dorchester  
Dorset

MOTOROLA M6800

## MICROPROCESSORS

DO YOU NEED ASSISTANCE?  
HARDWARE AND SOFTWARE EXPERTISE IS AVAILABLE

MEK kits & components supplied.  
Send SAE to:  
**FRASER-MANNING LTD.**  
26 Hervey Street, Ipswich, Suffolk



*Mist Curler*

Manufacturer:  
**PACIFIC ELECTRIC**

Export:  
**Pacific Trading Company**  
77A Waterloo Road, Kowloon, Hongkong  
Telex: 84672 VRHGT HX  
Cable: PACIFICTRA

## OVER 2,000 ELECTRONIC COMPONENTS IN A

# BIG NEW FREE



**TANDY**  
100 PAGE CATALOGUE

**TANDY**  
Nationwide supermarket of sound!

Please send me the 100 page Tandy catalogue

Name: \_\_\_\_\_

Address: \_\_\_\_\_

BLOCK CAPITALS PLEASE

Tandy Corporation (Branch UK), Bilton Road  
Wednesbury, W. Midlands, WS10 7JN. ET

### Treasure Locator Kits by

## DETECTOR PRODUCTS

Suppliers to the UK & Abroad

Circuits & Instructions ..... £2  
Complete Kit ..... £12  
Total £14 incl. VAT p&p

Solid aluminium frame with an efficient Faraday screen. For enquiries please send s.a.e. to:

**DETECTOR PRODUCTS**  
58a King Street, Blackburn, Lancs  
Tel. 62561 or 54105

**WANTED:** ETI Jan, Feb, Nov 1973. Jan, March, Sept., Nov 1974. Jan, June, Aug, Sept 1975. — St Leonards House, Ashtree Close, Worlingham, Suffolk.

## MTV

### Best choice for used TV

Worldwide exporters of colour and mono TV. Unlimited supplies.

Midland TV Trade & Retail Services,  
Worcester Road, Kidderminster, England.  
Tel: Kidderminster 61907 or 67390.

**100 POLYESTER CAPACITORS £2.15**

100 fully guaranteed electrically tested polyester capacitors. No floor sweepings. An famous makes: ITT, MULLARD, ERIE, etc

Mixed pack or YOUR CHOICE from the following values — mainly 250 V. Prompt despatch

01MF	047 MF	22 MF
015	068	33
022	.1	.47
033	15	Mail Order Only

£2.25 includes P&P  
MALLOY, W.G.M. ELECTRONICS (E.T.I.)  
66 Woodvale Avenue, Belfast BT13 3EX, N. Ireland

## INDEX TO ADVERTISERS

Ambit	p24	Island Devices	Miniads
B.H. Components	Miniads	Lee Instruments	p18
B.I.E.T.	p75	Lynx Electronics	p40
Bi-Pak	p4 & 5	Maplin	p84
Bi-Pre-Pak	p83	Marco Trading	Miniads
B.N.R.S.	p24	Marshalls	p9
Bywood	p25	Metc	p79
Cambridge Learning	p78	Minkits	p82
Catronics	p83	P.B. Electronics	p18
Chitmead	p78	Polytechnic of N. London	p77
Compolec	p69	Pronto Electronics	p77
Crofton	p77	Pulse Electronics	p75
Decon	p47	Radio Rotor	p48
Doram	p54	Ramar	Miniads
Electronic Design Associates	p71	R.F. Equipment Spares	Miniads
Electrovalue	p75	Sintel	p81
Erie Electronics	p78	Tandy Corporation	Miniads
Greenbank Electronics	Miniads	Technomatic	p17
I.L.P.	p2	Wilmslow Audio	p82

LED	0.125	0.2	INFRA RED	
	RED	15p	18p	550nm
	G/Y	27p	33p	Actual lead 48p
OR	27p	33p	8nmV £1.68	
panel clip 1p			OPTO DIODE	
			ORP 12 15p	

OPTO-ISOLATORS		SCRs	50V	100V	400V	Disc
TIL111	1.5AV 150kHz	E1	T06 1A	27p	48p	BR100
4350	2.5AV 5MHz	£2.28	T068 3A	27p	36p	21p

AVDEL BOARD	2gm.	85p	400V TRIACS	2A	60p	10A	£1.65
-------------	------	-----	-------------	----	-----	-----	-------

AC126/6/7/8	18p	2N3063	45p	VOLTAGE REGS	
AD181/162	40p	2N3064	18p	5V 7805 PHEM	
AF117	20p	2N3065	45p	12V 7812 1 Amp	
AF124/5/6/7	20p	2N3702/3/4	12p	15V 7815 all	
BC107/8/9	8p	2N3903/4/5/6/10p	20p	18V 7818 £1.80	
BC108C	12p	2N2646	20p	723 DIP 14	60p
BC147/8/9	10p	MPF102	40p		
BC157/8/9	11p	2N3819	20p	BRIDGE RECTS.	
BC167/8/9	11p	2N3823	30p	2A 50V	30p
BC169C	12p	8A100	8p	2A 100V	36p
BC177/8/9	17p			2A 200V	41p
BC182/3/4L	11p	IN914	2p	2A 400V	48p
BC186/7	30p	IN4001	2p		
BC12/3/4L	12p	IN4002/3	5p	ZENERS 2.7-33V	
BCY70/71/72	13p	IN4004/5	7p	82Y88 or sim.	8p
BF154/5	12p	IN4006/7	7p		
BF198/7	14p	IN4148	4p	555 Timer	80p
BFY50/51	18p	8A100	8p	558 2x555	£1.10
BFQ29	30p	0A47	8p	LM380	£1.00
BFX84	24p	0A70 0A79	8p	2N414	£1.10
BSX19/20	16p	0A81 0A90	7p	7400	18p
OC71	10p	0A91 0A95	6p		
2N706	10p	0A200	7p	D.I.L. SOCKETS	
2N1711	20p	0A202	7p	8-pin	12p
2N2219	20p			14-pin	13p
2N2904/5/6/7/10p	20p	OP. AMPS		18-pin	14p
2N2904/5/6A	15p	709 all	28p	Micro + touch	
2N2928B	7p	741 8-pin	28p	TO3 TO98	8p
2N2928C	12p	748 D.I.L.	34p	Dial Pan	70p

PRICES INCLUSIVE + 15p P&P (1st class)

**ISLAND DEVICES, P.O. Box 11, Margate, Kent**

## VALVES

Radio-TV Industrial Transmitting

2200 Types. 1930 to 1975, many obsolete. List 20p. S.A.E. for quotation. Postal export service. We wish to purchase all types of new and boxed valves. Wholesaler's Dealer's, etc., stocks purchased.

**COX RADIO (SUSSEX) LTD., The Parade, East Wittering, Sussex, West Wittering 2923**

## LED WATCH

(Hour, min., sec., date, day, month)  
£20.00 each including postage & VAT

Campbell Gyroplanes Ltd.  
High Street Farm  
Boxford  
Newbury, Berkshire



## H.M. ELECTRONICS (ET1)

275a FULWOOD ROAD, BROOMHILL  
SHEFFIELD S10 3BD

BEC CABINETS (illus'd)  
with wooden end cheeks  
Also  
METAL CASES  
DRY TRANSFER LETTERING

Send 15p for leaflets (Refundable)  
Trade enquiries invited



RF Sig. Gen. TF 144G — £15; Home-Built Score, dual trace — £20; Avro 7 — £10; Sinclair Scientific — £6. — Phone Maiden Newton 525 (Dorset).

# Wilmslow Audio

**THE firm  
for  
speakers!**



Baker Group 25, 3, 8, or 15 ohm	£9.00
Baker Group 35, 3, 8 or 15 ohm	£10.75
Baker Deluxe, 8 or 15 ohm	£12.38
Baker Major, 3, 8 or 15 ohm	£10.69
Baker Regent, 8 or 15 ohm	£9.00
Baker Superb, 8 or 15 ohm	£16.31
Celestion MH 1000 horn, 8 or 15 ohm	£13.50
EMI 14" x 9" bass 14A/700 B ohm	£11.92
EMI B x 5, 10 watt, d/c, roll/s 8 ohm	£3.58
Elac 59RM 109 15 ohm, 59RM114 8 ohm	£3.38
Elac 6 1/2" d/c roll/s 8 ohm	£3.83
Elac 10" 10RM239 8 ohm	£3.83
Fane Pop 15 watt 12"	£5.50
Fane Pop 55, 12" 60 watt	£15.50
Fane Pop 60 watt, 15"	£17.95
Fane Pop 70 watt 15"	£18.75
Fane Pop 100 watt, 18"	£27.96
Fane Crescendo 12A or B, 8 or 15 ohm	£37.96
Fane Crescendo 15, 8 or 15 ohm	£49.95
Fane Crescendo 18, 8 or 15 ohm	£67.95
Fane 801T 8" d/c roll/s 8 ohm	£8.96
Goodmans 8P 8 or 15 ohm	£8.20
Goodmans 10P 8 or 15 ohm	£6.50
Goodmans 12P 8 or 15 ohm	£14.95
Goodmans 12P-D 8 or 15 ohms	£16.95
Goodmans 12P-G 8 or 15 ohms	£16.50
Goodmans Audiom 200 8 ohm	£13.48
Goodmans Axent 100 8 ohm	£7.80
Goodmans Axiom 402 8 or 15 ohm	£19.80
Goodmans Twinaxiom 8" 8 or 15 ohm	£9.80
Goodmans Twinaxiom 10" 8 or 15 ohm	£8.78
Kef T27	£8.18
Kef T15	£8.25
Kef B110	£6.78
Kef B200	£7.85
Kef B139	£18.08
Kef DNB	£2.08
Kef DN12	£8.38
Kef DN13	£4.05
Richard Allan CG8T 8" d/c roll/s	£7.85
STC 400 1 G super tweeter	£5.80
STC 4001 K super tweeter	£5.90
Baker Major Module, each	£13.28
Goodmans Mezzo Twinkit, pair	£48.80
Goodmans DIN 2D, 4 ohm, each	£13.28
Helma XLK30, pair	£21.95
Helma XLK35, pair	£28.78
Helma XLK40, pair	£38.50
Kefkit I, pair	£51.00
Kefkit III, each	£46.00
Peerless 20-5D, pair	£38.80
Peerless 20-6D, pair	£53.00
Richard Allan Twinkit, each	£13.48
Richard Allan Triple B, each	£20.28
Richard Allan Triple, each	£28.18
Richard Allan Super Triple, each	£28.28
Wharfedale Linton 2 kit, pair	£21.80
Wharfedale Glendale 3 XP kit, pair	£47.80
Wharfedale Dove Dale 3 kit, pair	£59.40
Wharfedale Super 1ORS/DD	£13.80
Castle Super B RS/DD	£8.26
Jordan Watts Module 4, 8 or 15 ohm	£16.38
Tannoy 10" Monitor HPD	£78.00
Tannoy 12" Monitor HPD	£88.00
Tannoy 15" Monitor HPD	£98.88

Prices correct at 19.7.76

### ALL PRICES INCLUDE VAT

Cabinets, wadding, Vynair, crossovers etc.

Send stamp for free booklet "Choosing a Speaker"

**FREE with all orders over £10 — "HiFi Loudspeaker Enclosures" Book**

All units are guaranteed new and perfect

Prompt despatch

Carriage: Speakers 55p each, 12" and up 85p each, tweeters and crossovers 33p each, kits £1 each (£2 pair).

## WILMSLOW AUDIO

Dept. ETI

Swan Works, Bank Square, Wilmslow, Cheshire SK9 1HF. Tel. Wilmslow 28598 (Discount HiFi, PA and Radio at 10 Swan Street, Wilmslow)

# BUILD THE TREASURE TRACER MK III

METAL  
LOCATOR



AS SEEN  
ON BBC-1  
& BBC-2  
TV

- Genuine 5 silicon transistor circuit, does not need a transistor radio to operate.
- Incorporates unique varicap tuning, for extra stability.
- Search head fitted with Faraday screen to eliminate capacitive effects.
- Loudspeaker or earphone operation, (both supplied).
- Britain's best selling metal locator; kit, 4,000 already sold.
- Kit can be built in two hours using only soldering iron, screwdriver, pliers and side-cutters.
- Excellent sensitivity and stability.
- Kit absolutely complete including: drilled, tinned, fibreglass p.c. board with components sited printed on.
- Complete after sales service.
- Weighs only 22oz; handle knocks down to 17" for transport.

Send stamped, self-addressed envelope for literature.

Complete kit  
with pre-built  
search coil

**£12.50**

Plus 85p P & P  
Plus £1.00 VAT (8%)

Built, tested  
and Guaranteed

**£17.50**

Plus 85p P & P  
Plus £1.40 VAT (8%)

MINIKITS ELECTRONICS,  
6d Cleveland Road, South Woodford,  
LONDON E18 2AN  
(Mail order only)

# electronics today

## reader services

### BACK ISSUES

These cost 40p each. Postage and packing costs 15p for the first, and 10p for each subsequent issue. Orders to ETI BACK ISSUES Dept. please. We CANNOT supply the following issues: All 1972: January, February and November 1973: January, March, September, October, November and December 1974: January, June, July, August, September, November and December 1975: January, March 1976: April, August, October 1973.

### SUBSCRIPTIONS

The annual subscription to ETI for UK readers is £5.00. The current rate for readers overseas is £5.50. Send orders to ETI SUBS Dept. PAYMENT IN STERLING ONLY PLEASE.

### BINDERS

Binders, for up to 13 issues, are available for £2.50 including VAT and carriage. Send orders to ETI BINDERS DEPT. . . .

### EDITORIAL QUERIES

Written queries can only be answered when accompanied by an SAE, and the reply can take up to three weeks. These must relate to recent articles and not involve ETI staff in any research. Mark your letter ETI QUERY . . . Telephone queries can only be answered when technical staff are free, and never before 4 pm.

### MINI-ADS & CLASSIFIEDS

This is a pre-payment service — rates on application to ADVERTISING.

### SPECIAL ISSUES

Presently we produce five specials — Top Project 2 and 3, Electronics It's Easy (parts 1-13 and Parts 14-24) and 4800 Synthesiser (published by Maplin). Prices are 75p, £1, £1.20 and £1.50 respectively. Post and packing 15p per copy. Orders to ETI SPECIALS Dept. please.

### BOOKS

ETI Book Service sells books to our readers by mail order. The prices advertised in the magazine include postage and packing. Send orders to ETI Book Service, P.O. Box 79, Maldenhead, Berks.

### NON-FUNCTIONING PROJECTS

We cannot solve the problems faced by individual readers building our projects unless they are concerning interpretation of our articles. When we know of any error we print a correction as soon as possible at the end of News Digest. Any useful addenda to a project will be similarly dealt with. We cannot advise readers on modifications to our projects.

### PCBs

PCBs are available for our projects from companies advertising in the magazine, such as Ramar and Crofton, who do an excellent service.

### T-SHIRTS

ETI T-shirts are available in Large, Medium, or Small sizes. They are yellow cotton with black printing and cost £1.80 each. Send orders to ETI T-SHIRTS Dept. . . .

ADDRESS FOR ETI DEPARTMENTS—  
36 EBURY ST, LONDON SW1W 0LW

PLEASE MARK REVERSE OF EACH CHEQUE  
WITH NAME & ADDRESS AND ITEMS  
REQUIRED.

ALLOW 10 TO 14 DAYS FOR DELIVERY




# Stirling Sound Products

FROM BI-PRE-PAK
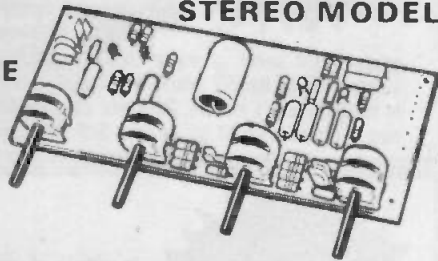
## UNIT 1 PRE-AMP/CONTROL STEREO MODEL

**SUPERB VALUE AT £7.80**  
with active tone control circuitry



UNIT 1 latest addition in the Stirling Sound range of realistically priced constructional modules is going to assure many many more constructors of obtaining quality where price has prevented it before.

UNIT 1 offers full stereo facilities is guaranteed and easy to connect up

- Input sensitivity — 50 mV, adjustable.
- Output — 200 mV for 50 mV in
- Bass control — 15 dB at 30 KHz
- Treble control — 15 dB at 10 KHz
- Balance control, volume control, 1/2" spindles
- Operating voltage — 10 to 16V

## MORE POWER — LESS SPACE



### SS.140 Mk. 3 POWER AMP

Built for hard work  
Now with built-in output capacitor

40 watts R.M.S. into 4Ω

**£3.95**  
+ 8% V.A.T.

Resulting from research and development the Mk 3 version of this most popular power amp now includes built in output capacitor with improved stability under severe working conditions. Greatly used for P.A. disco and similar work. SS 140 offers fantastic value for the price.

## SUPER SPARK MK. 5 C.D.I. UNIT

Thousands are in use saving motorists time and money. Very easy to install. Incorporates switch for instant change to conventional ignition. Easy to set for pos. or neg. earth. anti-burglar immobilising switch. pre-set rev limit control. neon light. The unit is in p.c.b. housed in strong enclosed metal box. With instructions and leads. Size 7 1/2" x 4 1/2" x 2 1/2" (193 x 117 x 54MM) (P/P add 50p)

K11 **£7.95**\*\* BUILT & TESTED **£10.50**\*\*

## X-44 CROSS-HATCH GENERATOR

Operates at R.F. level

For colour and mono TV. Plugs into aerial socket of set. Operates without need for transmissions. 4 push-button operation. Runs on a self-contained penlite type batteries. Will fit easily into a large pocket. Strong plastic case.

BUILT **£27.50**\*\* (less batts)

## A USEFUL CATALOGUE — FREE

Send us a large SAE with 10p stamp and we will send you the latest Bi-Pre Pack catalogue free by return. Packed with useful lines it's a real money saver. **Semi-conductors, components, accessories, surprise bargains.**

## MORE STIRLING SOUND MODULES

SS.201	FM Front End with geared tuning and A.F.C. facility 88-108MHz	£5.00
SS.202	1 F amp. A meter and/or A.F.C. can be connected (size 3" x 2") For use with SS 201	£2.65
SS.203	Stereo decoder For use with Stirling Sound modules, or with any other good mono F.M. tuning section. A LED beacon can be added (Price 18p) to indicate when a stereo signal is tuned in (3" x 2")	£3.85

## POWER AMPS

SS.103	Basic 3 watt r.m.s. I.C. power amp	£1.75
SS.103.3	Stereo version of above	£3.25
SS.105	5 watt amplifier to run from 12V (3 1/2" x 2" x 1/4")	£2.25
SS.110 Mk. 3	Similar to SS 105 but more powerful giving 10W into 4ohms using 24 volts	£2.75
SS.120 Mk. 3	20 watt module when used with 34 volts into 4	£3.25
SS.125	De-luxe 25 watt R.M.S. power amp having 0.04% distortion at all levels. Operates from 50V to give 25w.r.m.s. into 8 ohms	£5.00

## CONTROL

SS.100	Active tone control stereo, ± 15dB cut and boost with suitable network	£1.60
SS.101	Pre-amp for ceramic p.u. radio & tape with passive tone control details	£1.60
SS.102	Stereo pre-amp with R.I.A.A. equalisation mag. p.u. tape and radio in	£2.25

## VOLTAGE STABILISER

SS.300	Power Supply Stabiliser. Add this to your unregulated supply to obtain a steady working voltage from 12 to 50V for your audio system, workbench, etc. Money saving and very reliable	£3.25*
--------	--	--------

## NEW SHOWROOM

You are invited to our new equipment showroom forming part of our newly extended premises.

## TERMS OF BUSINESS:

VAT at 12 1/2% must be added to total value of order except for items marked \* or (8%), when VAT IS TO BE ADDED AT 8%. No VAT on overseas orders. POST & PACKING add 30p for UK orders unless marked otherwise. Minimum mail order acceptable — £1. Overseas orders, add £1 for postage. Any difference will be credited or charged. PRICES subject to alteration without notice. AVAILABILITY All items available at time of going to press when every effort is made to ensure correctness of information.


Order your Stirling Sound products from **BI-PRE-PAK LTD**

Co Reg No 820919  
222 224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 90F.  
TELEPHONE: SOUTHEND (0702) 46344

FACTORY — SHOEBOURNESS, ESSEX

## Stirling Sound

### POWER PACKS

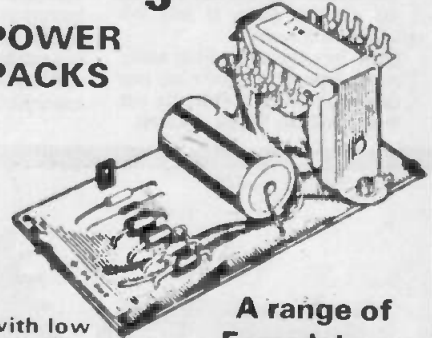

with low voltage take off point

A range of 5 models to choose from

Not only do these excellent power packs stand up unflinchingly to hard work, inclusion of a take-off point at around 13.15 V adds to their usefulness and once again price value is outstanding. Generously rated for reliability.

SS 312	12V/1A	£3.75*
SS 318	18V/1A	£4.15*
SS 324	24V/1A	£4.60*
SS 334	34V/2A	£5.20*
SS 345	45V/4A	£6.25*

Please add 50p for P/P either model

TO STIRLING SOUND (BI-PRE-PAK) LTD 222 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SSO 0DF

Please send

for which I enclose £

Inc. V.A.T.

NAME


ADDRESS

(ETI.9)

# Make it with MAPLIN!


**ELECTRONIC COMPONENTS**  
WIDE RANGE • HIGH QUALITY • FAST SERVICE

## The 4600 SYNTHESISER

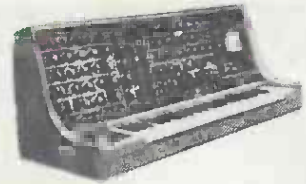

We stock all the parts for this brilliantly designed synthesiser, including all the PCB's, metalwork and a drilled and printed front panel, giving a superb professional finish. Opinions of authority agree the ETI International Synthesiser is technically superior to most of today's models. Complete construction details in our booklet now available price £1.50, or send SAE for specification.

## ELECTRONIC ORGAN

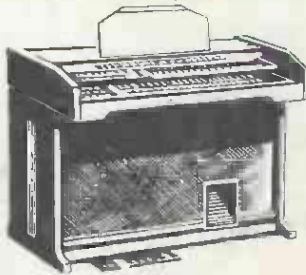


### BUILD IT YOURSELF... IN STAGES

Get started with a 49 note instrument — features tremulant and reverberation. Ideal to learn on, Leaflet MES 51. Price 15p gives full details to build this complete instrument. Extend the range of MES 51 by adding another keyboard and several new tone colours. Leaflet MES 52. Price 15p also shows how to use 61 note keyboards.

Fully controllable attack and delay controls (normally found only on the most expensive organs), up to seven footages on each keyboard, up to 70 controls including drawbars, and a 13 note pedalboard, make up the additions described in the step-by-step 32 page instruction leaflet MES 53. Price 35p.


## GRAPHIC EQUALIZER

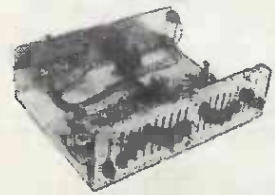

A really superior high quality stereo graphic equalizer featuring 9 octaves per channel. We stock all the parts (except woodwork) including the metalwork drilled and printed. 15p brings you a reprint of the article.

## DIGITAL CLOCK KITS

ONLY **£8.60** INC. VAT  
E P I P

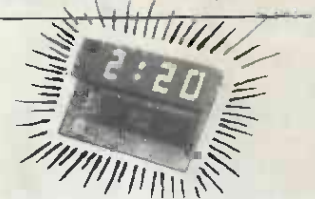


This is a fully constructed and tested electronic clock module as illustrated. Data sheet supplied. Simple to connect to alarm and your battery/mains radio. Smart case available shortly. Data sheet available separately. Please send SAE.

- ★ Bright 4 Digit 0.5" Display
- ★ Flashing Colon (1Hz)
- ★ Switch for Display Seconds
- ★ Alarm Set Indicator
- ★ P.M. Indicator
- ★ Power Failure Indicator

- ★ Sleep Timer
- ★ Snooze Timer
- ★ Time can be set accurately to within one second
- ★ Leading Zero Blanking

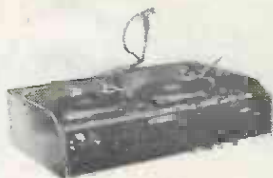SIMPLE ALARM KIT — £9.38      ALARM CLOCK KIT — £10.99  
ALARM CLOCK & RADIO CONTROLLER KIT — £11.51  
SMART PLASTIC CASE with fully punched chassis — £2.49  
Please send SAE for our Clock data sheet



## 100 W PER CHANNEL STEREO DISCO

- ★ Automatic voice operated fader.
- ★ Belt drive turntables
- ★ Monitor facilities (Headphones and VU meter)
- ★ Sound operated light show — plus many other advantages.

Full details in Sept./Oct. editions of this magazine

Send for our leaflet MES 41, giving full details for construction. Price 20p. Soon you'll be the DeeJay everyone wants at their party!

## Get our FABULOUS NEW 1977/78 CATALOGUE

PUBLICATION DATE OCT. 28, 1976 ON APPROVAL

All new ● Completely re-written ● Hundreds of new lines.  
Lots of exciting new projects to build — PRICE 50p  
SEND NO MONEY NOW Overseas send 8 International reply coupons.

### JOIN OUR MAILING LIST NOW!

Published every two months our Newsletter gives full details of our latest guaranteed prices.

Send just 30p towards cost of postage and we'll send you the next six issues as they are published. (A 5p voucher is sent with each newsletter which may be used on purchases.)

- ★ SAVE ££'s ON SPECIAL OFFERS!
- ★ DETAILS OF NEW PROJECTS AND NEW LINES

Please rush me a copy of your brand new 1977/78 catalogue the instant it is printed (Oct. 28th, 1976). Only if I am completely satisfied that it is worth every penny will I send 50p within 14 days of receipt. If I am not satisfied I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it.

NAME .....

ADDRESS .....

ETI



MAPLIN ELECTRONIC SUPPLIES  
All mail to: P.O. Box 3, Rayleigh, Essex S56 6LR  
Shop: 284 London Road, Westcliff-on-Sea, Essex  
(Closed on Monday). Tel: Southend (0702) 441 01

If you do not wish to cut magazine, write your request for catalogue on separate sheet 1975/76 GREEN COVER CATALOGUE STILL AVAILABLE. PRICE 40p