

# electronics today

ISSN 0142-7229

INTERNATIONAL

AUGUST 1982 75p

## ETI MOBILE—To Be Built By Humans Run By Computer ETI MICROTUTOR—Teach yourself To Handle Machine Code!

**Configurations—a new “building block”  
approach to circuit design**

**Build our new game project—  
novel design concept**

**Playmate project  
for aspiring  
guitarists!**



**Major New Series!  
Designing Micro Systems—  
Computer Circuitry Made Easy**

AUDIO... COMPUTING... MICRO...

...ROBOTICS...

Powertran's black boxes are packed with punch. Not only are they superb kits to buy and build they really do the job! Imaginative and ingenious design goes hand in hand with top quality materials and outstanding performance capability. With their smart black styling the kits harmonise visually as well as musically.

Your can built each unit independantly for its set task and then gradually increase your array until you have a complete bank of formidable controllable power.



Complete Kit — £49.90 + VAT

**MPA 200** is a low price, high power 100W amplifier. Its smart styling, professional appearance and performance, make it one of our most popular designs. With adaptable inputs the mixer accepts a variety of sources yet straightforward construction makes it ideal for the first-time builder.



Complete Kit — £49.50 + VAT

**CHROMATHEQUE 5000** — a 5-channel lighting system powerful enough for professional discos yet controllable for home-effects. Sound to light, strobe to music level, random or sequential effects — each channel can handle up to 500W yet minimal wiring is needed with our unique single-board design.



Complete Kit — £175.00 + VAT

**ETI VOCODER** — 14 channels, each with independent level control, for maximum versatility and intelligibility; Two input amplifiers — for speech/excitation — each with level control and tone control. The Vocoder is a powerful yet flexible machine that is interesting to build and thanks to our easy to follow construction manual, is within the capability of most enthusiasts.




Complete Kit — £64.90 + VAT

**SP2 200** twice the power with two of the reliable, durable and economic amps from the MPA200; fed by separate power supplies from a common toroidal transformer. Superb finish and quality components throughout — up to (even over!) the standard of high priced factory-built units.



**DJ90 Stereo Mixer** — this is a really versatile new mixer that enables the constructor DJ to produce a professional performance every time. There are two stereo inputs for magnetic cartridges, a stereo auxiliary input and mike input. Other 'plus' features are auto-panning for fast or slow, slider controls, multi-mixing, ducking, interrupt, input modulation, in short everything... the whole works — AND — under £100 complete! (We have illustrated the DJ90 teamed in our own console with the Chromatheque and an SP2 200 and speakers.

Complete Kit — £97.50 + VAT

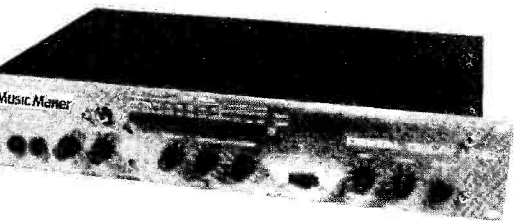

**Digital Delay Line** — our latest kit! With its ability to give delay times from 1.6 mSecs to up to 1.6 secs. Many powerful effects including phasing, flanging, A.D.T., chorus, echo & vibrato are obtained. The basic kit is extended in 400 mS steps up to 1.6 secs. Simply by adding more parts to the PCB. Compare with units costing over £1,000! Complete kit (400 mS delay) **£130** + VAT. Parts for extra 400 mS delay £9.50p.

*Quite simply the best way to make music*



#### WORLD LEADERS IN ELECTRONIC KITS

- **Money Back Guarantee** — If you are not completely satisfied with your Powertran Kit return it in original condition within 10 days for full refund.
- **Free Soldering Practice Kit** — To assist the beginner we will supply, on request with your first kit order, a free soldering practice kit with useful tips and illustrations.
- **Component Packs** — Most kits are available as separate packs (e.g. PCB component sets, hardware sets etc). Prices in our FREE catalogue.
- **Ordering** — Full ordering details, delivery service, and sales counter opening — inside back of this issue.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM. (0264) 64455.

# electronics today


INTERNATIONAL AUGUST 1982 VOL 11 NO 8



**Ron Harris B.Sc** : Editor  
**Peter Green** : Assistant Editor  
**Kathryn McFarland** : Editorial Assistant  
**Rory Holmes** : Project Editors  
**Phil Walker** : Project Editors  
**Alan Griffiths** : Divisional Advertisement Manager  
**T.J. Connell** : Managing Director

**PUBLISHED BY:**  
 Argus Specialist Publications Ltd.,  
 145 Charing Cross Road, London WC2H 0EE.  
**DISTRIBUTED BY:**  
 Argus Press Sales & Distribution Ltd.,  
 12-18 Paul Street, London EC2A 4JS  
 (British Isles)  
**PRINTED BY:**  
 QB Limited, Colchester.  
**COVERS PRINTED BY:**  
 Alabaster Passmore.

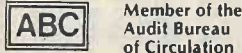**OVERSEAS EDITIONS and their EDITORS**  
 AUSTRALIA — Roger Harrison  
 CANADA — Halvor Moorshead  
 GERMANY — Udo Wittig  
 HOLLAND — Anton Kriegsmann



Electronics Today is normally published on the first Friday in the month preceding cover date. □ The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. ©1982 Argus Specialist Publications Ltd □ All reasonable care is taken in the preparation of the magazine contents; but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

□ Subscription Rates. UK £11.95 including postage. Airmail and other rates upon application to ETI Subscriptions Department, 513 London Road, Thornton Heath, Surrey CR4 6AR.


## EDITORIAL AND ADVERTISEMENT OFFICE

145 Charing Cross Road, London WC2H 0EE. Telephone 01-437 1002/3/4/5. Telex 8811896.
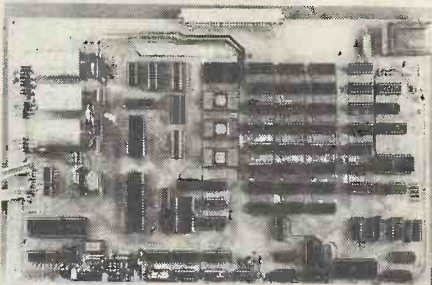
## FEATURES

**DIGEST** ..... 10  
 Some humour and some hard facts about the electronics scene.

**DESIGNING MICRO SYSTEMS** ... 19  
 Everything you ever wanted to know about microcomputing hardware (but didn't know who to ask).



**TECH TIPS** ..... 34  
 Three pages of circuit designs submitted by our inventive readership.


**CONFIGURATIONS** ..... 45  
 Ian Sinclair has done us proud on this one. This new series examines some of the basic transistor building blocks and gives all the design data you need to use them yourself. One to cut out and keep.

**READ/WRITE** ..... 58  
 This month's page of readers' correspondence deals with such diverse topics as lucid dreams, car control and crossword puzzles.

**DESIGNER'S NOTEBOOK** ..... 66  
 The device under scrutiny this month is the versatile DPM200, an excellent little DVM module.

**DATA SHEET** ..... 78  
 You wanted it back and here it is! Our monthly glimpse at the manufacturers' info begins with a fast buffer amplifier.

## PROJECTS

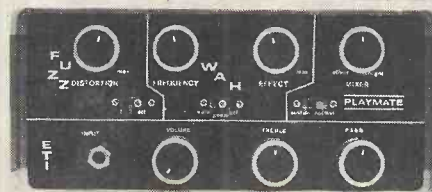

**THE PLAYMATE** ..... 28  
 No, not *that* sort of Playmate — this one's a guitar amplifier with built-in fuzz and wah-wah effects. It's portable, too.

**KITCHEN SCALES PART 2** ..... 39  
 We conclude this novel project with the full constructional details and the calibration procedure.

**MICROTUTOR** ..... 50  
 Get to grips with 6502 machine code; this very cheap teaching tool allows you to get hands-on experience with the language of the microprocessor.

**RUGBY CLOCK** ..... 60  
 How would you like a clock/calendar you never have to put right? Here it is, with a whole lot more to offer besides.

**SOUND TRACK** ..... 72  
 We were bored with the usual sort of hand-held DIY electronic game, so we came up with this audio version of the shoot-'em-down type.

**MOBILE 2** ..... 82  
 We've enough modules designed now to make something of them — and it's time you got involved, too.

**FOIL PATTERNS** ..... 87



## INFORMATION

**NEXT MONTH'S ETI** ..... 17  
**BREADBOARD '82** ..... 26  
**BINDERS** ..... 43

**PCB SERVICE** ..... 69  
**BOOK SERVICE** ..... 71  
**SUBSCRIPTIONS** ..... 77



**SWITCHES**

TOGGLE: 2A, 250V  
 SPST 33p  
 DPDT 44p

**SUB-MIN TOGGLE**  
 SPST on/off 54p  
 SPDT 1/cover 60p  
 SPDT centre both ways 105p  
 DPDT 6 biased 75p  
 DPDT centre off 88p  
 DPDT biased both ways 145p  
 DPDT 3 positions on/off 185p  
 3-pole 2 way 205p

**SLIDE 250V:**  
 DPDT 1A 14p  
 DPDT 1A c/off 15p  
 DPDT 12A 13p

**PUSHBUTTON 6A**  
 with 10mm Button  
 SPDT latching 99p  
 DPDT latching 145p  
 SPDT moment 99p  
 DPDT moment 145p

Mini Non Locking Push to Make 15p  
 Push to Break 25p

**DIL SWITCHES**

(SPST) 4 way 70p; 6 way 85p;  
 8 way 90p; 10 way 145p.  
 (SPDT) 4 way 190p.

**ROTARY SWITCHES:**  
 (Adjustable Stop type)  
 1 pole/2 to 12 way, 2/2 to 6 way;  
 3 pole/2 to 4 way; 4P/2 to 3 way 45p

**ROTARY:** Mains DP 250V 4 Amp on/off 56p

**ROTARY:** (Mak-a-switch)  
 Make a multiway switch. Shafting assembly has adjustable stop. Accommodates up to 6 wafers (max 6 pole/12 way - DP switch) Mechanism only 90p

**WAFERS:** (make before break) to fit the above switch mechanism.  
 1 pole/12 way, 2 pole/6 way, 3 pole/4 way, 4 pole/3 way, 6p/2 way 56p  
 Mains DP 4A Switch to fit Spacers 4p. Screen 6p 45p

**ROCKER:** 5A/250V SPST 28p  
 ROCKER: 10A/250V SPDT 38p  
 ROCKER: 10A/250V DP c/off 95p  
 ROCKER: 10A/250V DPST with neon 85p

**VEROBOARD 0.1in**

2 1/2 x 3 1/4	73p	52p
2 1/2 x 5	83p	
3 3/4 x 3 3/4	83p	
3 3/4 x 5	95p	79p
3 3/4 x 17	425p	211p
4 3/4 x 17	425p	211p
Pkt. of 100 pins	50p	
Spot face cutter	118p	
Pin insertion tool	162p	

**VERO WIRING**  
 PEN - Sprock 310p  
 Spare Spool 75p  
 Combs 6p

**FERRIC CHLORIDE**  
 1 lb bag Anhydrous 195p  
 50p P&P

**COPPER CLAD BOARDS**  
 Fibre Single 5 R B P  
 glass sided 110p  
 6 x 6 90p  
 6 x 12 150p

**VERO BOARD 0.1in**

VQ Board 175  
 DIP Board 385  
 Vero Strip 144

**PROTO DECS**  
 Veroblock 375p  
 S-Dec 350p  
 Eurobreadboard 520p  
 Bimboard 1 575p  
 Superstrip SS2 1350p

**DALO ETCH RESIST PEN**  
 - Spare tip 90p

**ULTRASONIC TRANSDUCER**  
 40kHz 325 pr

**ICD CONNECTORS**

PCB Plugs with Header Socket	PCB Pins	Angle	Price
2 x 5 way	90p	85p	65p
2 x 8 way	130p	150p	110p
2 x 10 way	145p	165p	125p
2 x 13 way	175p	200p	150p
2 x 17 way	205p	235p	165p
2 x 20 way	220p	250p	180p
2 x 25 way	235p	270p	175p
2 x 30 way	-	-	230p

**EURO CONNECTORS**

DIN	Socket Strt	Socket Angle	Plug Strt	Plug Angle	Price
41617-31	200p	-	-	150p	-
41612	-	-	-	-	-
A+B	-	-	-	-	-
2 x 32 way	340p	345p	295p	325p	-
41612	-	-	-	-	-
A+C	-	-	-	-	-
2 x 32 way	360p	355p	300p	350p	-
41612	-	-	-	-	-
A+B+C	-	-	-	-	-
3 x 32 way	420p	425p	370p	400p	-

**RIBBON CABLE**  
 12cr Grey Cable 10 way 12p 22p  
 16 way 18p 32p  
 20 way 25p 40p  
 24 way 30p 50p  
 34 way 48p 60p  
 40 way 55p 75p  
 50 way 65p 90p  
 64 way 85p 110p

**DIL PLUG HEADERS**  
 14 pin 4p 99p  
 16 pin 4p 105p  
 24 pin 8p 178p  
 40 pin 25p 255p

**ZIF DIL SOCKETS**  
 24 pin 575p  
 28 pin 620p  
 40 pin 975p

**PANEL METERS**

**FSD**  
 60 x 46 x 35mm  
 0-500µA 200p  
 0-100µA 200p  
 0-500µA 200p  
 0-1mA 100p  
 0-5mA 100p  
 0-10mA 100p  
 0-50mA 100p  
 0-100mA 100p  
 0-1A 100p  
 0-2A 100p  
 0-25V 100p  
 0-50V AC 100p  
 0-300V AC 100p

'VU' 495p each

**RELAYS**

Miniature, enclosed, PCB mount Our RL5 series.  
 S.P.C.O.  
 RL6-91 170i coil, 7V5 to 12V DC; 380V/6A AC, 1300VA/50W 210p  
 D.P.C.O.  
 431i coil, 4V2-7V DC; 250V AC, 5A; 1100VA/150W 215p  
 RL5-111 170i coil, 8V-14V; 250V AC, 5A 220p  
 RL6-114 740i coil, 17V5-29V 250V AC, 5A 222p

**'WEMON' WATFORD'S Ultimate Monitor IC**

A 4K Monitor chip specially designed to produce the best from your Superboard Series I & II, Enhanced Superboard & UK101. As reviewed by Dr. A. Berk in Practical Electronics, June 1981.  
 Price only £12 + 50p P&P

**CRYSTALS**

32.768kHz	100
100kHz	350
455kHz	295
1MHz	375
1.008MHz	275
1.28MHz	302
1.6MHz	395
1.8MHz	395
2.0MHz	220
2.4576MHz	225
3.278MHz	150
3.5794MHz	98
3.6854MHz	300
4.0MHz	150
4.032MHz	290
4.80MHz	200
4.194304MHz	200
4.433619MHz	120
5.0MHz	160
5.185MHz	300
5.24288MHz	225
6.144MHz	320
6.5536MHz	225
7.168MHz	250
7.68MHz	200
8.0MHz	220
8.86723MHz	175
9.00MHz	175
10.0MHz	150
10.24MHz	200
10.7MHz	200
12.0MHz	200
14.31814MHz	170
16.0MHz	270
18.0MHz	180
18.432MHz	180
19.968MHz	240
24.0MHz	150
26.189MHz	150
27.648MHz	170
27.145MHz	190
38.66667MHz	175
48.0MHz	170
100.0MHz	250
116.0MHz	250

**PIEZO TRANSDUCERS**

Type PB-2720 75p

**BUZZERS**, miniature, solid-state

6V, 9V & 12V 70p

**LOUDSPEAKERS**

Miniature, 0.3W, 8Ω, 2in, 3 1/2in, 2 1/2in, 3in 2 1/2in 40i, 64i or 80i 80p

**ASTEC UHF MODULATORS**

Standard 6MHz 280p  
 Wideband 8MHz 425p

**BBC MICRO UPGRADE**

(Our BBC Micro Upgrade Kits will save you £ s s s...)  
 16K Memory (8 x 4186AP) £18  
 Printer User I/O Port Kit £8.20  
 Expansion Bus Kit £2  
 Complete Printer Cable 36" £13  
 SK9 with 36" Cable £41  
 Disc Interface Kit £3  
 Analogue I/O Kit £6.75  
 Serial I/O Kit £7.50  
 Expansion Bus Kit £6.50  
 SK11 with Cable 36" £3  
 SK12 with Cable 36" £3.75  
 5 pin DIN Socket £0.40

**ETI PROJECTS**

We stock most of the parts



**JUMPER LEADS** (Ribbon Cable Assembly)

Length	14 pin	16 pin	24 pin	40 pin
24 inches	145p	165p	240p	380p
6 inches	185p	205p	300p	485p
12 inches	185p	215p	315p	490p
24 inches	215p	235p	345p	540p
36 inches	230p	250p	375p	585p

**AMPHENOL PLUGS**

IEEE (24 way) 675p  
 Centronic parallel (36 way) 650p

**DIL SOCKETS (TEXAS)**

Low	Wire	Price
8pin	8p	25p
14pin	10p	35p
16pin	10p	42p
18pin	16p	52p
20pin	22p	60p
22pin	25p	70p
24pin	25p	70p
28pin	28p	80p
40pin	30p	99p

**ANTEX SOLDERING IRON**

C-15W 450p CX17W 475p  
 CCN-15W 495p CX25W 500p

Spare tips, assorted sizes 65p  
 Spare Elements 210p  
 Iron stand with sponge 165p

**D CONNECTORS: Miniature**

9 way 15way 25way 37way

Plugs	18way	160p	250p
Solder	160p	210p	250p
Angle	160p	210p	250p
Pins	120p	130p	195p
Sockets	110p	160p	210p
Angle	165p	215p	290p
Pins	150p	180p	240p
Covers	100p	95p	100p

**25 way 'D' CONNECTOR**

Jumper Lead Cable Assembly 560p  
 18" long, Single end, Male 570p  
 18" long, Single end, Female 570p  
 36" long, Double Ended, M/M 1025p  
 36" long, Double Ended, F/F 1050p  
 36" long, Double Ended, M/F 995p

**ZX81 16K RAM PACK**

Fully built & tested. Plugs straight into ZX81 Micro Only  
 £17.35 + p&p 50p

**TRANSFORMERS:**

Prim 240V  
 6-0-6V; 9-0-9V; 12-0-12V 100mA 98p

pcb mounting, Miniature, Split Bobbin  
 3VA; 2x6V-0.25A; 2x9V-0.15A; 2x12V-0.12A; 2x15V-0.1A 200p  
 6VA; 2x6V-0.5A; 2x9V-0.3A; 2x12V-0.25A 270p  
 2x15V-0.2A 270p  
 Standard Split Bobbin type:  
 6VA; 2x6V-0.5A; 2x9V-0.4A; 2x12V-0.3A; 2x15V-0.25A 220p  
 12VA; 2x6V-1.3A; 2x6V-1A; 2x9V-0.6A; 2x12V-0.5A; 2x15V-0.4A; 2x20V-0.3A 295p (35p p&p)  
 24VA; 2x6V-1.5A; 2x9V-1.2A; 2x12V-1A; 2x15V-0.8A; 2x20V-0.6A 330p (60p p&p)  
 50VA; 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-1A; 2x30V-0.8A 440p (80p p&p)  
 100VA; 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x25V-2A; 2x30V-1.5A; 2x50V-1A 920p (75p p&p charge to be added over and above our normal postal charge).

**VOLTAGE REGULATORS**

P.V.	Price
1A TO3 Metal case -ve	
5V 7805 145p	7905 220p
12V 7812 145p	7912 220p
15V 7815 145p	7915 220p
18V 7818 145p	
1A TO220 Plastic casing	
5V 7805 40p	7905 45p
12V 7812 40p	7908 60p
15V 7815 40p	7912 45p
18V 7818 40p	7915 45p
24V 7824 40p	7924 60p
100mA TO92 Plastic casing	
5V 78L05 30p	79L05 60p
12V 78L12 30p	79L12 60p
8V 78L08 30p	79L08 60p
12V 78L12 30p	79L12 60p
15V 78L15 30p	79L15 60p

**CA3085**

LM3008	95p
LM3004	170p
LM3004H	170p
LM305H	140p
LM305K	135p
LM317K	350p
LM317KP	89p
LM317H	280p
LM323K	500p
LM325N	240p
LM326N	240p
LM337	175p
LM723	350p
LM723	135p
TBA625B	75p
DA1412	150p
78H05 + 5V/5A	550p
5H5 + 5V to +25V	595p
79HC-2.5V to 24V 5A	785p

**CMOS**

4000	10	4075	15	4539	110
4001	10	4576	48	4543	150
4002	12	4077	18	4544	150
4006	50	4081	16	4549	375
4007	15	4082	16	4553	245
4008	48	4085	50	4555	35
4009	24	4086	52	4556	35
4010	24	4089	125	4557	320
4011	11	4093	26	4557	320
4012	16	4094	120	4558	320
4013	25	4095	75	4561	10
4014	50	4096	70	4562	495
4015	50	4097	250	4563	180
4016	20	4098	75	4566	165
4017	38	4099	110	4568	250
4018	45	4100	95	4572	20
4019	25	4101	99	4570	85p
4020	50	4102	99	4581	250
4021	50	4103	99	4582	99
4022	50	4104	99	4582	99
4023	16	4105	105	4583	99
4024	32	4106	105	4585	99
4025	16	4408	790	4597	330
4026	90	4409	790	4598	290
4027	24	4410	725	4599	290
4028	50	4411	675	4599	290
4029	60	4412	675	40085	45
4030	30	4415	480	BARGRAPH, Red 10 segments	225
4031	125	4422	280	40100	215
4032	90	4433	770	40101	130
4033	125	4433	770	40102	140
4034	140	4437	770	40103	175
4035	65	4435	850	40104	95
4036	275	4440	999	40105	110
4037	110	4450	350	40106	46
4038	110	4450	350	40107	60
4039	290	4490	350	40108	450
4040	50	4500	675	40109	100
4041	60	4501	28	40110	300
4042	45	4502	60	40111	240
4043	50	4503	40	40112	300
4044	50	4504	75	40113	50
4045	105	4506	35	40114	65
4046	650	4507	35	40115	75
4047	50	4508	130	40116	220
4048	40	4510	46	40117	180
4049	25	4511	46	40118	220
4050	25	4512	50	40119	220
4051	45	4513	199	40120	30
4052	60	4514	115	40121	88
4053	50	4515	115	40122	90
4054	85	4517	275	40123	72
4055	85	4518			



# COMPUTER WAREHOUSE

**NOW OPEN**  
MONDAY-SATURDAY  
9.30-5.30

## BULK BUY SPECIALS

### RAM SCOOP

4116 200 NS 8 for £12.95  
4164 200 NS £8.50 each  
2102-650 NS 8 for £5.50  
INC VAT

### 25 WAY "D" CONNECTORS

50+ 100+  
25p 1.70 1.10 0.95  
25S 1.90 1.20 1.00  
ALL + VAT

### WIRE WRAP SKTS.


24 Pin Vero 28p  
14 Pin Gold 22p  
16 Pin Gold 24p  
100 PCS Min Ord.

**C10**  
DATA CASSETTES  
10 for £5.75  
Inc. VAT

### RF CONNECTORS

50Ω BNC PLG 50p  
75Ω BNC PLG 50p  
PL269 PLG 40p  
SO239 SKT 35p  
100 PCS MIN ORD.

## TELETYPE ASR33 I/O TERMINALS

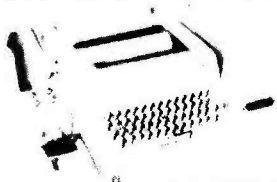


From £195 + CAR + VAT

Fully fledged industry standard ASR33 data terminal. Many features including ASCII keyboard and printer for data I/O, auto data detect circuitry, RS232 serial interface, 110 baud, 8 bit paper tape punch and reader for off line data preparation and ridiculously cheap and reliable data storage. Supplied in good condition and in working order. Options: Floor stand £12.50 + VAT

KSR33 With 20ma loop interface £125.00 + VAT.  
Sound proof enclosure £25.00 + VAT

## "OLIVETTI TE300" PRINTER/TERMINALS

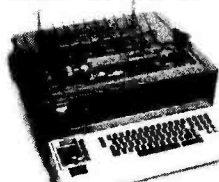

A complete I/O terminal with integral 8 hole paper tape punch and reader, full ASCII keyboard, 120 column printer, and control unit. The printer is capable of 150 baud with a serial TTL or balanced input-output sold in good overall condition but untested. Complete with circuit unguaranteed. Connect direct to your micro at ONLY £99.00 + £11.50 carr + vat.

## MPU EXPERIMENTATORS +5v, 12v, 12v+24v POWER SUPPLY

Once again we are very pleased to offer this superb Power Supply Unit, and hope to satisfy most of our previous customers who were disappointed when we sold out due to demand last time they were advertised!!! These units may just have well been made for your lab., they consist of a semi-enclosed chassis measuring 180mm x 120mm x 350mm containing all silicon electronics to give the following fully regulated and short circuit proof outputs of:  
+5v @ 2 amps DC +12v @ 800 ma DC  
-12v @ 800 ma DC +24v @ 350 ma DC  
and if that's not enough a fully floating 5v output @ 50 ma DC which may be sensed to give a host of other voltages. All outputs are brought out to the front panel via miniature jack sockets and are also duplicated at the rear on short flying leads. Units accept standard 240v mains input. They are ex GPO and may have minor scratches on the front panels, they are sold untested but in good internal condition. £16.50 each + £2.50 p+p complete with circuit and component list. Transformer guaranteed. HURRY WHILE STOCKS LAST!!

## HIGH SPEED DATA MODEMS

A superb piece of engineering made by SE Labs Ltd. to a "no cost spared" spec for the GPO, the Modem 12 is a synchronous Modem for use on DATEL 2412 services, or other data links. Many features include switchable V26 modulation, 2400 baud full duplex 600/1200 standby, auto answer, 4 wire or 2 wire operation. Self test, LED status indication, CMOS technology, modular construction, original cost over £700 each. Believed brand new, supplied complete with PSU etc. £185.00 + £9.50 carriage + VAT.  
\*Permission may be required for connection to PD lines

## DISTEL ©

"Dial our Database!"  
Get information on 1000's of stock items and order via your computer. 300 baud on 01-689 6800  
18.30 to 09.00 6 days a week and all day Sundays. **IT'S FREE!**

## DIABLO S30 DISK DRIVES

Another shipment allows us to offer you even greater savings on this superb 2.5 MB (formatted) hard disk drive. Two types are available both fully refurbished and electronically identical, the only difference is the convenience of changing the disk packs.

S30 front loader, pack change via front door £350 + vat  
S30 fixed, pack change via removal of top cover £295 + vat

+ & - 15v PSU for 2 drives £125 + vat  
Carriage & insurance on drives £15.00 + vat fully DEC RK05, NOVA, TEXAS compatible further info on controllers etc on request.

## MAINS FILTERS

Professional type mains filters as used by "Main Frame Manufacturers" ideal for curing those annoying hang ups and data glitches. Fit one now and cure your problems! Suppression Devices SDS A10 5 amp £6.95  
Corcom Inc F1900 30 amp £13.95 + pp £1.00

## DC SYSTEM SUPPLY

Professional fully cased fan cooled system supply. Standard 240V ac input with the following DC outputs 5V @ 11 amps +15-17v @ 4 amps, -15-17v @ 8 amps and +24v @ 4 amps. All outputs are fully crowbar protected and the 5 volt output is fully regulated. Sold tested and in a new or little used condition complete with circuit £55.00 + carr £8.50 + vat DIM 15.5" x 9" x 6"

## NATIONAL MA1012 LED CLOCK MODULE

- ★ 12 HOUR
- ★ ALARM
- ★ 50/60 HZ



The same module as used in most ALARM/CLOCK radios today, the only difference is our price! All electronics are mounted on a PCB measuring only 3" x 1 1/2" and by addition of a few switches and 5/16 volts AC you have a multi function alarm clock at a fraction of cost. Other features include snooze timer, am pm, alarm set, power fail indicator, flashing seconds cursor, modulated alarm output etc. Supplied brand new with full data only. Suitable transformer £1.75. **£5.25**

ELECTRONIC COMPONENTS & EQUIPMENT


**66%**  
DISCOUNT

Due to our massive bulk purchasing programme which enables us to bring you the best possible bargains, we have thousands of I.C.'s, Transistors, Relays, Cap's., P.C.B.'s., Sub-assemblies, Switches, etc. etc. surplus to our requirements. Because we don't have sufficient stocks of any one item to include in our ads., we are packing all these items into the "BARGAIN PARCEL OF A LIFETIME". Thousands of components at giveaway prices! Guaranteed to be worth at least 3 times what you pay plus we always include something from our ads. for unbeatable value!! Sold by weight

2.5kds £ 4.75 + pp £1.25    5kds £ 6.75 + pp £1.80  
10kds £11.75 + pp £2.25    20kds £19.99 + pp £4.75

SAVE OVER £1000
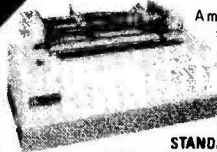
## THE PRINTER SCOOP OF THE YEAR THE LOGABAX Z80 MICROPROCESSOR CONTROLLED LX180L MATRIX PRINTER



A massive bulk purchase enables us to offer you this superb professional printer at a fraction of its recent cost of over £2000. Utilising the very latest in microprocessor technology, it features a host of facilities with all electronics on one plug in P.C.B. Just study the specification and you will instantly realise it meets all the requirements of the most exacting professional or hobbyist user.

STANDARD FUNCTIONS: Full ASCII character set ★ Standard ink ribbon ★ RS232/V24 serial interface - 7 xtal controlled baud rates up to 9600 ★ 194 characters per line ★ Parallel interface ★ Handshakes on serial and parallel ports ★ 4 Type fonts, italic script, double width, italic large, standard ★ Internal buffer ★ Internal self test ★ 170 CPS ★ Variable paper tractor up to 17.5" wide ★ Solid steel construction ★ All software in 2708 eeproms easily reconfigured for custom fonts etc. All this and more, not refurbished but BRAND NEW At Only **£525 +VAT**

OPTIONAL EXTRAS: lower case option £25.00 \* 16k buffer £30.00 \* Second tractor for simultaneous dual forms £85.00 \* Floor stand £45.00 \* specialist carriage £19.00 All items plus VAT data sheet on request.

## 8" FLOPPY DISK DRIVES

Unbelievable value the DRE 7100 & 7200 8" disk drives utilise the finest technology to give you 100% bus compatibility with most drives available today, the only difference being our PRICE and the superb manufacturing quality. The 7100 single sided & 7200 double sided drive accept hard or soft sectoring. (IBM or ANSI standard giving a massive 0.8 MB (7100) & 1.6 MB (7200) of storage. Absolutely SHUGART, BASF, SIEMENS etc compatible. Supplied BRAND NEW with user manual and 90 day warranty.



7100 single sided £225.00 + 9.50 carr + vat  
7200 double sided £295.00 + 9.50 carr + vat  
full technical manual £20.00 alone £9.00 with drive. refund of difference on purchase of drive. Data sheet on request.  
SPECIAL new, KODE PSU, drives 2 DRE drives £39.99 + carr + vat.  
8" single sided, single or double density diskettes £1.80 each £15.00 for 10 inc. lib case + vat.

## COOLING FAN SPECIAL

Keep your equipment cool and reliable with our range of professional fans.  
ETRI 99XU01 Miniature equipment fan 240 vac working DIM 92 x 92 x 25 mm BRAND NEW complete with finger guard. Makes price £18 our price £10.25  
BUHLER 89.11.22 micro miniature 8-16 vDC reversible fan. Measures only 62 x 62 x 22 mm. Uses a brushless DC servo motor, almost silent running ideal portable equipment, life in excess of 10,000 hours. BRAND NEW manufacturers price £32.00 our price £13.95  
MUFFIN/CENTAUR cooling fans, tested ex equipment 240v £6.50, 115v £5.50 + p+p £1.90  
KOOL TRONICS Powerful snail type blower gives massive air movement with centrifugal rotor DIM as a cube 8" x 8" x 6" air aperture 2.5" x 2.5" with flange fixing. BRAND NEW 110v 50Hz ac working ONLY £9.95 + £1.90 p+p

## SOFTY 1 & 2 EPROM BLOWER

Software development system invaluable tool for designers, hobbyists, etc. Enables open heart surgery on 2716, 2708 etc. Blows, copies, reads EPROMS or emulates EPROM/ROM/RAM in situ whilst displaying contents on domestic TV receiver. Many other features. £115 + carr. + VAT. Optional 2716, 2716 Function Card £40 + VAT. PSU £20 + £1.50 carr. + VAT.  
Softy 2 for 2716/2732 £169 + VAT  
Write of phone for more details.

## 9" VIDEO MONITORS

Ex-equipment 9" Motorola Video Monitors 75Ω composite input, tested but unguaranteed. £39.99 + £7.50 carriage + VAT. Complete with circuit.

## SEMICONDUCTOR 'GRAB BAGS'

Mixed Semic amazing value contents include transistors, digital, linear, I.C.'s, triacs, diodes, bridge rect., etc. etc. All devices guaranteed brand new full spec. with manufacturer's markings, fully guaranteed. 50+ bag £2.86 100+ bag £5.15 TTL 74 Series.  
A gigantic purchase of an "across the board" range of 74 TTL series I.C.'s enables us to offer 100+ mixed "mostly TTL" grab bags at a price which two or three chips in the bag would normally cost to buy. Fully guaranteed at I.C.'s full spec. 100+ £8.90 200+ £12.30 300+ £18.60

## RCA FULLY CASSED ASCII CODED KEYBOARDS



IDEAL - TANGERINE, OHIO ETC.

Straight from the U.S.A. made by the world famous R.C.A. Co., the VP600 Series of cased freestanding keyboards meet all requirements of the most exacting user, right down to the price! Utilising the latest in switch technology. Guaranteed in excess of 5 million operations. The keyboard has a host of other features including full ASCII 128 character set, user definable keys, upper/lower case, rollover protection, single 5V rail, keyboard impervious to liquids and dust, TTL or CMOS outputs, even an on-board tone generator for keypress feedback, and a 1 year full R.C.A. backed guarantee.

VP601 7 bit fully coded output with delayed strobe, etc. **£43.95**  
VP611 Same as VP601 with numeric pad. **£54.95**  
VP606 Serial, RS232, 20MA and TTL output, with 6 selectable Baud Rates. **£64.26**  
VP616 Same as VP606, with numeric pad, Plug and cable for VP601, VP611 £2.25 **£84.34**  
Plug for VP606, VP616 **£2.10**

Post, Packing and Insurance. **£1.95**  
ORDER NOW OR SEND FOR DETAILS.

## 5v D.C. POWER SUPPLIES

Following the recent "SELL OUT" demand for our 5v 3 amp P.S.U. we have managed to secure a large quantity of ex-computer systems P.S.U.'s with the following spec.: 240 or 110v A.C. input. Outputs of 5v @ 3-4 amps, 7.2v @ 3 amps and 6.5v @ 1 amp. The 5v and 7.2v outputs are fully regulated and adjustable with variable current limiting on the 5v supply. Unit is self contained on a P.C.B. measuring only 12" x 5" x 3". The 7.2v output is ideal for feeding "on board" regulators or a further 3 amp LM323K regulator to give an effective 5v @ 7 amp supply. Supplied complete with circuit at only £10.95 + £1.75 pp. Believed working but untested, unguaranteed.

# ELECTRONICS

Dept. E.T.I., 64-66 Melfort Rd., Thornton Heath, Croydon, Surrey, Tel: 01-689 7702 or 01-689 8800  
MAIL ORDER INFORMATION  
Unless otherwise stated all prices inclusive of V.A.T. Cash with order. Minimum order value £2.00 Prices and Postage quoted for UK only. Where post and packing not indicated please add 60p per order. Bona Fide account orders minimum £20.00. Export and trade enquiries welcome. Orders despatched same day where possible. 3% surcharge on Access and Barclaycard orders.

# SALE ELECTRONIC GAMES



**NOW £40 OFF**

## ATARI T.V. GAME

THE GAME WITH 50 CARTRIDGES  
R.R.P. £129.95 (inc. VAT)

**OUR PRICE**  
**£78.22 + VAT**  
(= £89.95 inc. VAT)

The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

### ATARI CARTRIDGES

We now have several special offers on Atari cartridges including several at half price. We also have all of the new cartridge releases including Pac-Man and Haunted House.

Free Atari 32 page catalogue  
We have just released the Silica Shop 32 page Atari catalogue covering the complete range of cartridges currently available for the Atari video game. For a free copy telephone 01 301 1111

**ATARI OWNERS CLUB** — Why not join our **FREE** Silica Atari Owners Club and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.

## MATTEL INTELLIVISION



**NOW £70 OFF**

THE ULTIMATE T.V. GAME  
R.R.P. £229.95 (inc. VAT)

**OUR PRICE**  
**£129.95 + VAT**  
(£149.44 inc. VAT)

6 NEW CARTRIDGES JUST RELEASED:  
**ASTROSMASH \* SNAFU \* BOWLING  
SPACE ARMADA \* BOXING  
TRIPLE ACTION**

All 19 current cartridges + the six new ones above now retail at £119.95 — Silica special offer price **£17.95 inc. VAT**

The Mattel Intellivision is the most advanced T.V. game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision + free soccer cartridge is £229.95 but our special offer price is £149.44 inc. VAT saving you £70.00.

**MATTEL OWNERS CLUB** — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.


**FREE 16 PAGE CARTRIDGE CATALOGUE** — If you are interested in owning a Mattel, we now have available a 16 page colour catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.

## T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: **ATARI \* MATTEL \* ACETRONIC \* PHILIPS \* DATABASE \* ROWTRON \* INTERTON \* TELENG**. Let us know if you own any of these games and we will let you have details of the range of cartridges available.

Attention INTERTON & ACETRONIC owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

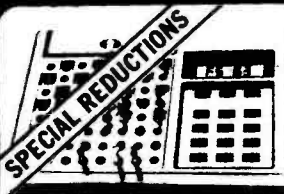We also have a number of secondhand games and cartridges.



**SPECIAL REDUCTIONS**

### ELECTRONIC CHESS

Liquid crystal battery chess computer with 100-200 hrs battery life and two levels of play. Comes with separate chess board and pieces.

**NOW £5 OFF**  
R.R.P. £24.95  
**SALE PRICE**  
**£19.95**

### GRADUATE CHESS

A de luxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.

(inc. VAT)  
**NOW**  
**£29.95**  
INC. VAT

### FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board. Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are planned for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE WAS £54.50 **NOW £49.95 INC. VAT**

Silica Shop are one of the country's leading specialists in Chess Computers and now stock a range of more than 20 Chess Computers, including Challenger 7/10/Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machine, Voice Champion, and the new Scicys Mark V

**LESS THAN 1/2 PRICE**

**COLOUR CARTRIDGE T.V. GAME**  
4 cartridges  
mains transformer  
**NOW £43.50 OFF**  
R.R.P. £73  
**SALE PRICE £29.50 inc. VAT**

**SCOOP PURCHASE NOW**

**BACKGAMMON COMPUTER**  
Silica stock a wide range of Backgammon computers from £29.95 upwards. Special offers now available on Gammonmaster.

**NOW £48.95 inc. VAT**

**CALL — THE AFFORDABLE ANSWER**  
The Post Office certified telephone answering machine

"Sorry darling, I will be late home — Love John"  
The Call Jotter 1 brings the affordable answer at the amazing price of £69 (or £99 for the Call Jotter 2 with built-in remote recall facilities). These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.

Call Jotter 3 illustrated **NOW £69.00 inc. VAT**  
By NTAPE 1139

**NOW £80 OFF**


**AYR TELETEXT**  
Plug the adaptor into the serial socket of your colour TV and receive the CEEFAX and ORACLE television information services.

**ADD-ON ADAPTOR**  
WAS £199 inc. VAT  
**SALE PRICE £159 inc. VAT**

THIS NEW MODEL INCORPORATES "Double height character facility" True PAL Colour "Meets latest BBC & IBA broadcast specifications"

THIS UNIT HAS A REMOTE CONTROL

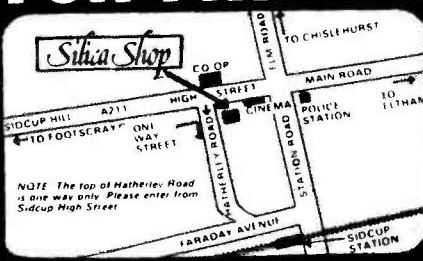
**FOR FREE BROCHURES — TEL: 01-301 1111**



For free illustrated brochure and reviews on our range of electronic games, please telephone 01-301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS/BARGAINCARD number, and leave the rest to us. Post and packing free of Charge. Express 48 hour delivery service available.

- **CALLERS WELCOME** Demonstrations daily at our Sidcup shop open from 9am-6pm Monday-Saturday (Early Closing Thursday 1pm) Late Opening Friday 8pm.
- **2 YEAR GUARANTEE** All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica Shop 2 year Guarantee.
- **MONEY BACK UNDERTAKING** If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.
- **AFTER SALES SERVICE** Available on all machines out of guarantee.
- **COMPETITIVE PRICES** We are never knowingly undersold.
- **HELPFUL ADVICE** Available on the suitability of each machine.
- **CREDIT FACILITIES** Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.
- **PART EXCHANGE SCHEME** Available on second hand machines.
- **CREDIT CARDS WELCOME** Access, Barclaycard, Diners Club, American Express.

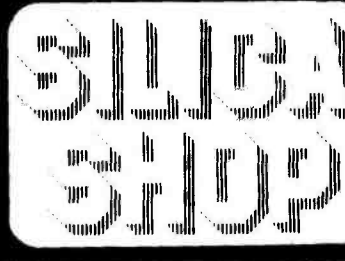**SILICA SHOP LIMITED ET10882**  
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111







# GET A GOOD DEAL FROM CRICKLEWOOD: OVER 300 PRICE CUTS NOW EFFECTED

Cricklewood is the shop in London with the largest variety of brand new, full-spec, guaranteed electronic components. Just look at our range and that's only part of it! Items not covered on this list include soldering equipment, tools, meters, tri-colour LEDs, D-connectors, fuses, knobs switches, plugs and sockets, transformers cases etc. etc., all at competitive prices, all under one roof. We have a 95% stock situation with all in stock items posted the same day. OFFICIAL ORDERS FROM SCHOOLS, GOVT. DEPTS, ACCEPTED. OVERSEAS ORDERS WELCOME (CWO) PLUS ADEQUATE POSTAGE. QUANTITY DISCOUNTS BY NEGOTIATION.

★ THE LAZY WAY Phone your order through on Access, Barclaycard, Visa or American Express for immediate service; no extra charge, no minimum order.  
 ★ THE TRADITIONAL WAY Send cheque, PO or credit card number. Cash not encouraged but accepted (no coins please). All in stock items shipped same day.  
 ★ THE IDEAL WAY Call in and collect. We are on the main Edgware Rd (A5) just 1 1/2 miles from Staples Corner and approx 3 miles from Marble Arch.  
 VAT Please add VAT at the current rate to all orders except books. VAT not chargeable abroad.  
 POST, PACKING & INSURANCE Standard small order charge is 70p (more for heavier goods). Export orders minimum £1.50.

TELEXY NO 914977 CRKEL G.


<p><b>DIACS</b>                  BR100 40p                  ST2 29p</p> <p><b>THYRISTORS</b>                  Sensitive Gate                  Small Signal                  2N5600 30p                  2N5601 32p                  2N5602 35p                  2N5603 37p                  2N5604 40p                  2N5605 42p                  2N5606 45p                  2N5607 48p                  2N5608 50p                  2N5609 52p                  2N5610 55p                  2N5611 58p                  2N5612 60p                  2N5613 62p                  2N5614 65p                  2N5615 68p                  2N5616 70p                  2N5617 72p                  2N5618 75p                  2N5619 1808p                  2N6312 1810p                  2N6313 1812p                  2N6314 1815p                  2N6315 1818p                  2N6316 182</p>
--

# DIGEST
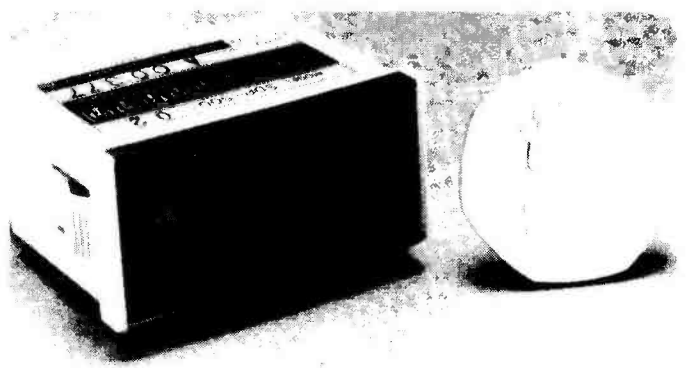
## Beeb's Loss of Memory

If you're stuck in the waiting list for a BBC Microcomputer, we've done some simple arithmetic that may persuade you to cancel your order and choose an alternative. One of the major selling points of the Beeb machine has always been the high resolution graphics, but it isn't until you let high-res loose on your memory that you find out the snag. For example, the Model A is advertised as being a 16K machine. In fact it's only 16K if it's turned off. As soon as you switch on, the operating system automatically reserves 3328 bytes as its workspace, and a further 1K goes to the memory-mapped screen if you're in mode 7 (40 x 25 teletext).


In any other graphics mode you lose a whopping 8-10K, so a '16K' machine actually has a maximum of 11.75K of user memory for programs, and a minimum of 2.75K! In the '32K' Model B, the screen can steal up to 20K in highest-res graphics mode, giving 27.75K maximum, 8.75K minimum. These figures have been available since the specs were published over a year ago, but how many people have actually put two and two together and come up with 2.75? Not many, we suspect. The most charitable comment we can make is that there could be a lot of disappointed customers when deliveries are finally made. On the other hand, you do get one of the best BASIC interpreters around—but stick to mode 7 if you want enough memory to use it properly.


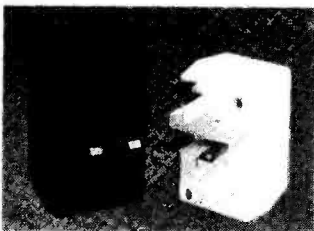
## SDP Shrinks Drastically

Hot on the heels of the BICC-Verro Speedwire prototyping system, reviewed exclusively in the June ETL, comes the SDP-500 range of digital panel meters. The SDP range (do we detect political overtones?) is, into miniaturisation in a big way, if that's not a contradiction — they measure only 48 x 24 x 48 mm. Packed into this tiny case we have the latest

LSI dual-integration A-to-D technology for high stability and excellent noise rejection (40dB at 50 Hz), bright 9.2 mm LED display with anti-glare filter, externally programmable decimal points and external hold. The eight models cover DC voltage or current measurement from  $\pm 199.9$  mV to  $\pm 199.9$  V and  $\pm 199.9$   $\mu$ A to  $\pm 199.9$  mA. The supply is 5 V at 100 mA maximum. For a comprehensive application guide contact Verospeed, Stansted Road, Boyatt Wood, Eastleigh, Hants SO5 4ZY.






## Plug-in Power

These smart cases have been added to the West Hyde range and are designed to house power supplies for low-voltage equipment such as calculators, radios and TV games. Two sizes are available, both able to accommodate PSU components including the transformer, and the case may be plugged directly into a 13 A socket. You can have any colour so long as it's black or white, and the case is moulded in impact-resistant ABS. More details from West Hyde Developments Ltd, Unit 9, Park Street Industrial Estate, Aylesbury, Bucks, HP20 1ET.
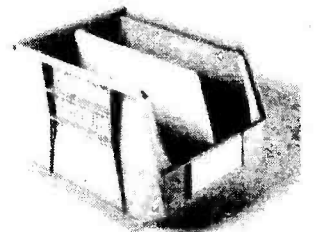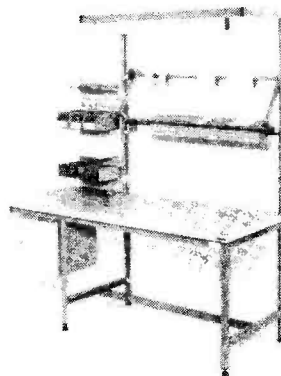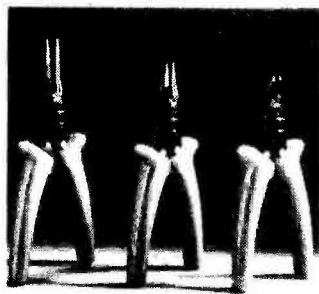
## Cut With Comfort

Now hands that do cutting can feel soft as your face...with these self-opening, cushion-grip hand tools. The three tools each weigh about 80 grams and comprise an angle side cutter, short fine nosed and long fine nosed pliers. Each tool costs £2.90 plus 45p P&P and VAT, and is available by mail order from Electronic Hobbies Ltd, 17 Roxwell Road, Chelmsford, Essex, CM1 2LY.



## That's Entertainment?

It seems there's at least one jolly wag at Linvar Ltd; they've sent us details of the ASAD Work Centre. ASAD? — well, that stands for All Singing All Dancing, to signify the fact that it's somewhat versatile. When

assembled the Work Centre is 5' by 2'6", but it can be packed up into its tailor-made carton for storage. The total cost is £89.90. Drawers, cupboards, shelves and a host of other accessories are available, including a paper cutting unit. This features in the Linvar Packing Bench, built from ASAD components. This more specialised work centre is designed to be the basis of a cost-effective packing department. Another aspect of Linvar's involvement in small parts storage is the 'Linbin' range of polypropylene containers, one of which is shown in the second photo. Linvar can be contacted at Barkby Road, Leicester, LE4 7LL.

## Flock Of Eagles

Eagle International, the industrial electronics company, have introduced three new professional public address mixer/amplifiers. These are the TPM 40, TPM 80 and TPM 120 models which offer — surprise, surprise — 40, 80 and 120 W RMS output power. All three are suitable for both four-eight ohm or 100 V line speaker systems. General spec is 30 Hz-15 kHz frequency response, priority paging over background music, master volume controls

etc, and two year guarantee. Individually, the TPM 40 has battery backup for mains failure, three mike and two auxiliary inputs, plus a tone control; the TPM 80 is mains-only with a tone control, four mike, one record deck and two auxiliary inputs; and the TPM 120 has the same inputs as the 80 but with independent bass and treble controls and more versatile input controls. Further information from Eagle International, Precision Centre, Heather Park Drive, Wembley, Middlesex HA0 1SU.



# Rapid Electronics

Tel: 0206 36412  
Hill Farm Industrial Estate  
Boxted, Colchester  
Essex CO4 5RD



## HARDWARE

PP3 battery clips	6p
Red or black crocodile clips	6p
Black pointer control knob	15p
Pi Ultrasonic transducers	350p
*6V Electronic buzzer	60p
*12V Electronic buzzer	65p
*PB2720 Piezo transducer	70p
*64mm 8 ohm speaker	75p
*64mm 8 ohm speaker	75p
20mm panel fuseholder	70p

## CABLES

20 metre pack single core connecting cable ten different colours	65p
Speaker cable	10p/m
Standard screened	16p/m
Twin screened	24p/m
2.5A 3 core mains	23p/m
10 way rainbow ribbon	66p/m
20 way rainbow ribbon	120p/m

## PANEL METERS

Size 60 x 46 x 35mm	
0-500mA	0-500mA
0-100uA	0-1A
0-500uA	0-50V AC
0-1mA	VU
0-10mA	0-300V AC
0-50mA	0-25V
0-100mA	0-30V DC
495p each	

## TRANSISTORS

AC125	35	BC157	10	BC548	10	BF880	25	TI29C	60	ZTX300	14	*N23702	6
AC126	25	BC158	10	BC549	10	BF829	25	TI30A	45	ZTX301	16	*N23703	9
AC127	25	BC159	8	BC550	10	BF828	25	TI30B	50	ZTX302	15	*N23704	6
*AC128	20	BC160	45	BCY72	18	BF882	25	TI30C	60	ZTX304	17	*N23705	9
AC176	25	BC168C	10	BCY72	18	BF887	25	TI31A	45	ZTX341	20	*N23707	10
AC187	22	BC169C	10	BD015	80	BF888	25	TI32A	45	ZTX501	15	*N23708	10
AC188	22	BC170	8	BD132	35	BFY51	23	TI32C	60	ZTX502	15	*N23709	10
AD142	120	BC171	10	BD133	50	BFY52	23	TI33C	75	ZTX504	25	*N23773	210
AD149	80	BC172	8	BD135	50	BFY53	32	TI34A	60	ZN697	20	*N23819	18
AD181	40	BC177	18	BD136	30	BFY56	32	TI34C	85	ZN698	40	*N23820	40
AD182	40	BC178	18	BD137	30	BFY56	32	TI35A	160	ZN706A	20	*N23823	65
AF124	60	BC179	18	BD138	30	BRV39	40	TI35C	180	ZN708	20	*N23866	90
AF126	50	BC182	10	BD139	35	BSX20	20	TI36A	170	ZN918	35	*N23903	10
AF139	40	*BC182L	8	BD140	35	BSX29	35	TI36C	195	ZN1132	22	*N23904	10
AF186	70	BC183	10	BD024	110	BSY95A	25	TI41A	60	ZN1613	30	*N23905	6
AF229	75	BC183L	10	BD026	110	BUD06	110	TI42A	60	ZN2218A	45	*N23906	10
BC107	10	BC184	10	BD022	85	BUD06	200	TI20	100	ZN2219A	25	*N24037	10
*BC107B	12	*BC184L	7	BF180	35	BUD08	170	TI21	100	ZN2221A	25	*N24038	10
*BC108	9	BC212	10	BF182	35	MJ2955	99	TI22	90	ZN2222A	20	*N24060	10
BC108B	12	BC212L	10	BF184	25	MJ2955	50	TI141	120	ZN2368	25	*N24061	10
BC108C	12	BC213	10	BF185	25	MJ2955	65	TI142	120	ZN2369	18	*N24062	10
*BC109	9	BC213L	10	BF186	15	MJ2955	65	TI147	120	ZN2370A	15	*N24063	10
BC109C	12	BC214	10	BF192	12	MJ2955	65	TI147	120	ZN2370A	15	*N24063	10
BC114	22	*BC214L	8	BF196	12	MPF102	40	TI3055	55	ZN2904	20	*N24539	30
BC115	22	BC237	8	BF197	12	MPF104	40	TI340	45	ZN2904A	20	*N24539	30
BC117	22	BC238	14	BF198	10	MPA505	22	TI44	45	ZN2905	22	*N24577	45
BC1119	35	BC308	15	BF199	18	MPA506	25	TI45	45	ZN2906A	22	*N24607	30
BC137	40	BC327	14	BF200	30	MPA512	30	TI50	30	ZN2906	25	*N24608	40
BC139	40	BC328	14	BF201	30	*BF244B	22	TI51	30	ZN2906A	25	*N24609	40
BC140	30	BC337	14	BF245	30	MPA550	30	TI59	30	ZN2906A	25	*N24610	40
BC141	30	BC338	14	BF256B	45	MPA505	55	VN464F	75	ZN2907	25	*N24611	40
BC142	25	BC477	30	BF257	32	MPA506	55	VN66AF	85	ZN2926	9	*N24612	40
BC143	25	BC478	30	BF258	25	MPA505	65	VN66AF	95	ZN3053	23	*N24613	40
BC147	8	BC479	30	BF259	35	MPA556	60	*VTX107	40	ZN3054	25	*N24614	40
BC148	8	BC479	30	BF259	35	MPA556	60	*VTX108	8	ZN3055	20	*N24615	40
BC149	9	BC547	7	BF240	23	TI29B	45	ZTX109	12	ZN3442	120		

## FREE TRANSISTORS!

Yes that's right! It's transistor month at Rapid! On all orders over £15 received we give you 10 BC184L general purpose transistors (value £10) absolutely free of charge. Offer expires 31st August 82. Please mention this magazine.

## POTENTIOMETERS

Rotary Carbon track Log or Lin 1K-2M2  
Single 32p; Stereo 85p; Single switched 80p;  
Slide 60mm travel single Log or Lin 5K-500K 63p each  
Preset. Submin. hor. 100 ohms-1M 7p each  
Cernmet precision multiturn, 0.75W 1/4in 100 ohms to 100K 85p each

## CONNECTORS

DIN	Plug	Skt	Jack	Plug	Skt
2 pin	9p	9p	2.5mm	10p	10p
3 pin	12	10p	3.5mm	9p	8p
5 pin	13p	11p	Standard	16p	20p
Phono	10p	12p	Stereo	24p	25p
1mm	12p	13p	4mm	18p	17p

## BRIDGE RECTIFIERS

1A 50V	22
1A 400V	35
2A 200V	40
2A 400V	45
6A 100V	80
6A 400V	95
VM18 DIL	
0.9A 200V	50

## CAPACITORS

Polyester. Radial leads. 250V. C280 type  
0.01, 0.015, 0.022, 0.033 6p; 0.047, 0.068, 0.1  
7p; 0.15, 0.22 9p; 0.33, 0.47 13p; 0.58, 20p; 1u  
23p  
Electrolytic. Radial or axial leads.  
0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V  
7p; 22/25V, 47/25V 8p; 100/25V 9p; 220/25V  
14p; 470/25V 22p; 1000/25V 30p; 2200/25V  
50p  
Tag end Power Supply Electrolytics.  
2200/40V 110p; 4700/40V 160p; 2200/63V  
140p; 4700/63V 230p  
Polyester. Miniature Siemens PCB  
1n, 2n2, 3n3, 4n7, 6m6, 10n, 15n 7p; 22n, 33n,  
47n, 68n 8p; 100n 9p; 150n 11p; 220n 13p; 330n  
20p; 470n 26p; 680n 29p; 1u 33p; 2u 80p  
Tantalum bead  
0.1, 0.22, 0.33, 0.47, 1.0 @ 35V 12p; 2.2, 4.7,  
10 @ 25V 20p; 15/16V 30p; 22/16V 27p;  
33/16V 45p; 47/16V 27p; 47/16V 70p; 68/6V  
40p; 100/10V 30p  
Ceramic disc. 22p 0.01u 50V 3p each  
Multilayer miniature ceramic plate  
1.8p to 100pF 6p each  
Polystyrene. 5% tolerance  
10p-1000p 6p; 1500-4700p 8p; 6800-0.012u  
10p  
Trimmers. Mullard 808 Series  
2-10pF 22p; 2-22pF 30p; 5.5-65pF 35p

## UHF (CB) Connectors

PL259 Plug 40p Reducer 14p	38p
SO239 square chassis socket 38p	38p
SO239S round chassis socket 40p	38p
IEC 3 pin 250V/6A	38p
Plug chassis mounting	80p
Socket free hanging	80p
Socket with 2m lead	120p

## Simply phone 0206 36412 with your order

## DIODES

BY127	12	*1N4001	3
OA47	10	1N4002	5
OA90	8	1N4006	7
OA91	7	1N4007	7
OA200	8	1N5401	15
OA202	8	1N5404	16
1N814	4	1N5406	17
*1N4148	2	4000M/Zen 6	
BZK61 Series	zeners	1.3W	
4V7-39V		15p each	

## BARCLAYCARD VISA

## SOLDERING IRONS

Antex CS 17W Soldering iron	450p
2, 3 and 4.7mm bits to suit	65p
CS 17W element	210p
Antex XS 25W Soldering iron	480p
3.3mm and 4.7mm bits to suit	65p
Solder pump desoldering tool	480p
Solder nozzle for above	70p
10 metres 22awg solder	100p
Soldering iron stand for above	190p

## REGULATORS

78L05	25	79L05	65
78L12	25	79L12	65
78L15	25	79L15	65
7805	40	7905	45
7812	40	7912	45
7815	40	7915	45

## SWITCHES

Submin toggle	
SPST 56p SPDT 60p *DPDT	
50p	
Mixtute toggle	
SPDT 80p SPDT centre off 90p	
DPDT 90p DPDT centre off	
100p	
Standard toggle	
SPST 35p DPDT 48p	
*Miniature DPDT slide 12p	
*Push to make 12p Push to	
break 22p	
Rotary type adjustable stop	
1P12V 2P2V 3P4V all 55p	
DIL switches	
4 SPST 80p 6 SPST 80p 8	
SPST 100p	

## SOCKETS

*8 pin	7p	Wire-wrap	25p
*14 pin	9p	25p	35p
*16 pin	10p	42p	42p
18 pin	15p	52p	52p
20 pin	18p	60p	60p
22 pin	20p	70p	70p
24 pin	22p	70p	70p
28 pin	28p	80p	80p
40 pin	32p	98p	98p
Soldercon pins	60p/100		

## RESISTORS

1W 5% Carbon film E12 series 4.7-10M 3p each	
1W 5% Carbon film E12 series 4.7-10M 2p each	
1W 1% Metal film E24 series 100-1M 6p each	

## TRANSFORMERS

Please add carriage charges to our normal post charges  
Miniature mains  
60V, 90V, 120V all @ 100mA 100p each  
PCB mounting. Miniature  
6VA 0.6, 0.6 @ 0.25A; 0.9-0.9 @ 0.15A;  
0.12, 0.12 @ 0.12A 200p each (plus 60p carriage)  
6VA 0.6, 0.6 @ 0.5A; 0.9, 0.9 @ 0.4A; 0.12, 0.12 @ 0.25A 270p each  
High quality. Split bobbin construction  
6VA 0.6, 0.6 @ 0.25A; 0.9, 0.9 @ 0.4A; 0.12, 0.12 @ 0.3A 220p each  
12VA 0.6, 0.6 @ 0.1A; 0.9, 0.9 @ 0.4A, 0.12, 0.12 @ 0.5A; 0.15, 0.15 @ 0.4A 295p (plus 40p carriage)  
25VA 0.6, 0.6 @ 1.5A; 0.9 @ 1.2A; 0.12 0.12 @ 1A; 0.15, 0.15 @ 0.8A 330p each (plus 60p carriage)  
50VA 0.12, 0.12 @ 2A, 0.15, 0.15 @ 1.5A 440p each (plus 75p carriage)

## VERO

* Verobloc 350p	
Size 0.1 matrix	
2.5 x 1	22p
2.5 x 3.75	75p
2.5 x 5	85p
3.75 x 5	95p
VO board	160p
Verobins per 100	
Single sided	50p
Double sided	75p
Spot face cutter	105p
Pin insertion tool	162p

## OPTO

*3mm red	8	*5mm red	8
*3mm green	12	*5mm green	12
*3mm yellow	12	*5mm yellow	12
Clips to suit 3p each			
*red	TL132		
*green	TL178		
*yellow	TL111		
TL138	40	ORP12	85
2N5777	45	TTL colour	90

## COMPONENT KITS

An ideal opportunity for the beginner or the experienced constructor to obtain a wide range of components at greatly reduced prices. 1W 5% Resistor kit. Contains 10 of each value from 4.7 to 1M (650 resistors) 480p  
Ceramic Capacitor Kit. Contains 5 of each value from 22p to 0.01u (135 caps) 370p  
Polyester Capacitor Kit. Contains 5 of each value from 0.01 to 1uF (86 caps) 575p each  
Preset Kit. Contains 5 of each value from 100 ohms to 1M (total 65 presets) 425p each  
Nut and Bolt Kit. Total 300 items 180p  
50 68A 1/2" bolts  
50 68A 1/4" bolts  
50 68A washers  
25 68A 1/2" bolts  
25 68A 1/4" bolts  
50 68A nuts  
50 68A washers

## VERO WIRING PEN

Pen + spool 310p	
Pin Insertion Tool	162p
Combs	75p

## ORDERING INFO

All prices exclude VAT. Please add to total order.  
Please add 50p carriage to all orders under £10 in value. Send cheque/PO or Access/Visa number with your order. Please note new address. Callers most welcome - we are just 10 minutes from the centre of Colchester. Telephone orders welcome with Access and Visa. Official orders welcome from colleges and schools etc. Export orders no VAT but please add carriage. All components brand new and full spec.

## LINEAR

ICL7106	90	LM358	50	LM3914	200	NE567	100	TL064	96	
ICL7611	95	LM377	150	LM3915	220	NE570	100	TL071	90	
*555CMOS 80	ICL7621	180	*LM380	65	LM1360	120	NE571	400	TL074	96
*555CMOS 150	ICL7622	180	LM381	120	MC1310	150	*RC4136	68	*TL081	26
709	25	ICL8038	200	LM3						

## Shorts

- A lot of hot air from Hellermann Electric of Plymouth; their new heat-guns, the GHM Mite and GHW-Triac are ideal for use with the "Helashrink" range of heatshrink sleeving.
- The ZN435 from Ferranti is a new multifunction eight-bit data converter. The standard 18-pin DIL IC contains a fast DAC, an up/down counter, a precision voltage reference and a clock generator. Uses include ramp-and-compare and tracking ADCs, low-frequency waveform generators, fader controls and radio channel selectors.
- Thorn EMI and JVC have postponed the launch of the VHD videodisc system in Japan for economic and marketing reasons. The same decision was recently taken in the USA. To achieve a co-ordinated launch, VHD won't now appear in the UK until 1983.
- Gulf Oil have donated an out-of-date IBM computer to the Science Museum in London. The machine was originally bought in 1978 for a quarter of a million pounds; the Science Museum hope

to have it in running order eventually.

- The first edition of the Electroware catalogue is now available and contains too much to list here; we'll just say it's good, it's free (30p P&P, though) and it's available from Electroware, Dutton Lane, Eastleigh, Hants, SO5 4AA.
- Stuck when it comes to metric conversion sums? The LC950 from Casio can switch from one system of weights and measures to another and has a split level display showing both sets of figures. RRP is £18.95.
- It seems there are people in the electronics industry who can think up even worse puns than us (is this possible, you gasp). MC Computers Ltd, of Newbury has launched a repackaged version of the Apple II personal computer, so naturally they've called it the Apple Pi.
- The 1982 edition of the IC Master (which contains details of more than 55,000 ICs) is now available in two hardback volumes from Paterson, Steadman and Partners of Saffron Walden. Price is £59.00 inclusive, which is one tenth of a penny per IC.



## Fax You Should Know

For a special three-month evaluation period, ITT Business Systems will allow customers to rent a Telefax facsimile unit at virtually half-price. At the end of the three months, they have the option to buy the unit or return it.

Facsimile transmission, as if you didn't know, is an electronic method of sending test, pictures, or graphics: the document is scanned, coded and sent down a telephone line to be printed out as hard copy on a receiver anywhere in the world — all very clever, although the young lady looks quite bored by it all. If you're interested, ITT Business Systems live at Diversey House, Chalk Lane, Cockfosters, Barnet, Herts EN4 0BU.

## Lithium Cell Clicks

Kodak's new disc camera is revolutionary in more ways than one — it will be using a high performance lithium battery from Matsushita. The disc camera does not use conventional film — pictures are taken on a flat disc of film and the camera includes automatic film advance exposure control and electronic flash. The lithium battery was chosen to power all this lot because of its high-rate pulse discharge capability (greater than 1 A), wide operating temperature range,



10-year shelf life and high reliability and safety. The lithium cell is expected to find increasing use in consumer products including cameras, flashguns, radios, transceivers, and telephone pocket pagers, as well as security and emergency equipment.

## Orient On Air

Here's a novel story — Pye Telecommunications have won an order to supply mobile radio equipment for Chinese transport vehicles. It would have been nice to report that the rickshaw in the picture was being fitted with the equipment, but not

such luck; it's the Kew Kwan Motor Road Co. buses that are getting the two-way treatment. It'll be the first time that China has had radio-controlled vehicles, and Kee Kwan, who hold the exclusive bus tour franchise for Macau, expect that the system will improve route supervision, efficiency and safety.



## More For Less

Zemco's latest car computer, the CompuCruise, has several new features but costs £20 less than the previous model. For £130 you get on-line fuel consumption; clock with stopwatch facility, cruising speed control, distance/time/fuel-to-arrive calculations, battery voltage indicators, inside and outside temperatures and about 15 other functions. The car freak who has everything (except a computer) can contact Zemco at 66 Earlsdon Street, Coventry, CV5 6EJ.

## Candid Cameras



Could this be a prototype TV of the future, once satellite TV brings us a bewildering choice of channels? Nope — it's JUPITER, a CCTV control system from Photo-Scan Ltd for multi-camera configurations. The microprocessor-based system allows cameras to be incorporated in multiples of 32, with up to 10 monitors, video recorders, remote camera controls, controls for up to four alarms per camera, and a lot of other stuff for security with a vengeance. Because the system is software-based the surveillance system can be modified to meet the needs of any customer. Photo-Scan are at Dolphin Estate, Windmill Road, Sunbury-on-Thames, TW16 7HG, if you want to know more — what we want to know is, why we never see security guards that look like this.



Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.
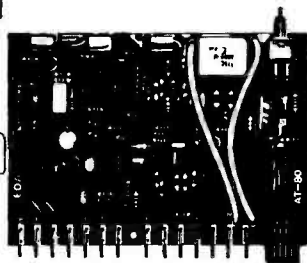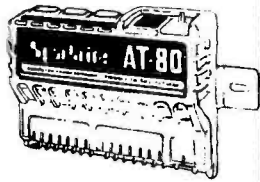
# Sparkrite

BRANDEADING ELECTRONICS  
NOW AVAILABLE IN KIT FORM




## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble

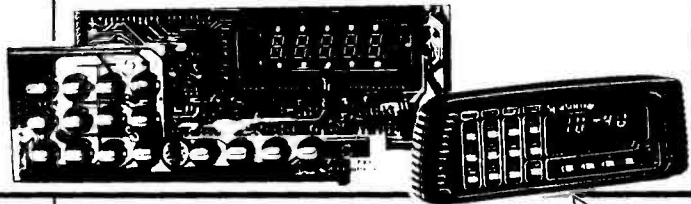
## VOYAGER Car Drive Computer

- A most sophisticated accessory
  - Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd.
  - Affords 12 functions centred on Fuel, Speed, Distance and Time.
  - Visual and Audible alarms, warning of Excess Speed, Frost/Ice, Lights-left-on.
  - Facility to operate LOG and TRIP functions independently or synchronously.
  - Large 10mm high 400ft-L fluorescent display with auto intensity.
  - Unique speed and fuel transducers giving a programmed accuracy of + or - 1%.
  - Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours
  - Full Imperial and Metric calibrations.
  - Over 300 components to assemble
- A real challenge for the electronics enthusiast!



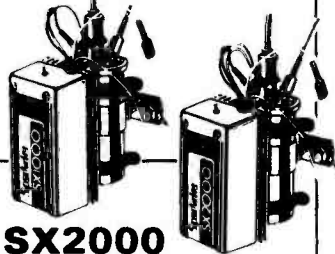
## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




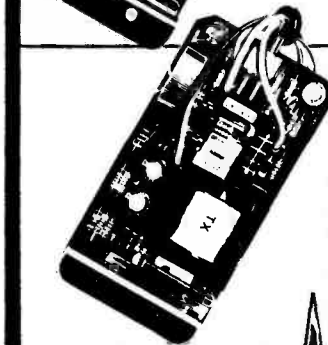
## TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble.


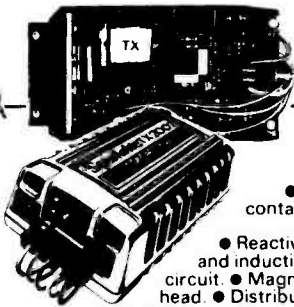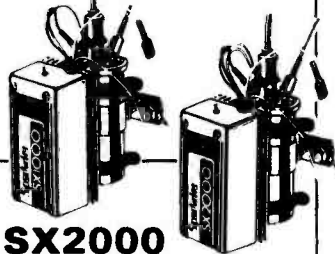
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




## TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive.
- Extended coil energy storage circuit.
- Magnetic contactless distributor triggerhead.
- Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers
- Die cast weatherproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

All EDA SPARKRITE products and designs are fully covered by one or more World Patents
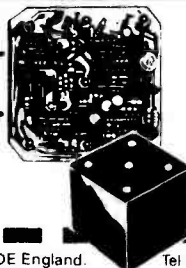
## SPECIAL OFFER

"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England.

Tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
TX 1002	£22.95	£45.90
AT 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

NAME \_\_\_\_\_ ETI

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO \_\_\_\_\_

24 hr. Answerphone

PHONE YOUR ORDER WITH ACCESS/ BARCLAYCARD


SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDEADING BRITISH ELECTRONICS


CUT OUT THE COUPON NOW!
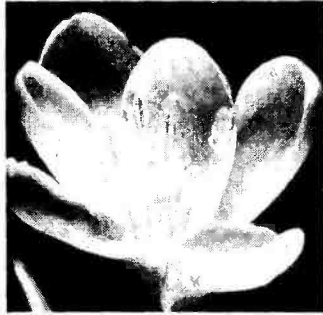
## The Light Fantastic

This bizarre pic arrived at the office with an announcement that General Instrument Lamps of Bury St. Edmunds will be marketing Tokyo Minilite Ltd products in Europe. Assuming they haven't cheated with a fake flower, then Minilite definitely lives up to its name. For further information contact General Instrument Lamps Ltd, Beetons Way, Bury St. Edmunds, Suffolk IP32 6RA. Note to ad agencies: it's ingenious pix like



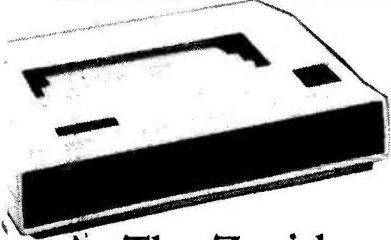this one that make it worthwhile ploughing through the hundreds of boring press releases we get each week.




## At The Zenith

Regular readers of the mag will know the high regard we have for Heath Electronics and the quality of their kits, so a new printer from Zenith Data Systems (a Heath division) has to be good news. The Z-25 is a bi-directional printer with quad tractor feed which provides accurate forms

registration, and a 9 x 9 dot matrix head for high quality print. The character set includes all 95 ASCII characters (upper and lower case) as well as 33 graphics characters. The high print rate (greater than 150 characters per second) results in a print speed of about 300 lines per minute for 10 column lines, and 65 lines per minute for 132 column lines. The operator can select from 10, 12, 13.2 or 16.5 characters per inch, while the completely enclosed cabinet results in quiet operation. The printer interfaces to microcomputers via an RS-232C serial interface or 20 mA current loop. The printer (and other Zenith products) are marketed in the UK through Zenith Data Systems outlets.
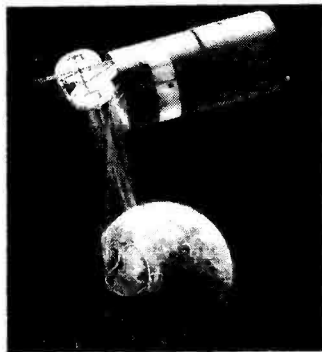
## AUSSAT — Owzat?


Hughes Aircraft Company have signed an agreement to build Australia's first communication satellite system. The three satellites, to be known as AUSSAT, will provide a variety of communication services including the first TV transmissions to many of the communities and homesteads in the remote outback regions. Other services include digital data transmissions, telephony, air traffic control and maritime radio coverage. The first of the satellites



will be launched in mid-1985, and each satellite is warranted for seven years; one hell of a trip for the service engineer, though!
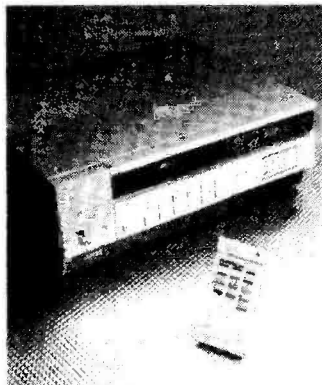
## Stereo VHS

Sound quality continues to improve in the video recorder field; the new top-of-the-line HR7650 EK from JVC features stereo sound amongst a host of other goodies. This means that the increasingly frequent simultaneous broadcasts on TV and FM radio can be recorded, as well as allowing playback of the fast-growing number of pre-recorded stereo video tapes. Sound quality is further improved by the inclusion of a Dolby noise reduction system. There are some pretty good extras on the video side too, such as insert and assemble editing, a special effects playback for fast or slow picture search, double speed play, still



frame and frame advance. A full function IR remote control unit is also provided. Please can I have one for my birthday?

## Change Of Key


This is a gorgeous young lady and that's her hotel key in her hand. Well, no-one would dispute the first statement, but the second probably requires a bit of explanation. The card is part of a new programmable electronic door lock system developed by the Yale Security Group for better hotel security; the system is known as Yaletronics. Each lock uses a Yale mortice lock and a microprocessor synchronised to the central computer — the locks are each battery-powered to avoid any costly hard-wiring. The present "credit-card" keys are presently made from plastic, but anything could be used; they have the advantage of being small, light and able to have the hotel's logo, room number and other information printed on them.

Each successive guest at the hotel is assigned a different code combination from the millions stored in the computer on a floppy disc with a 5000-room capacity. The system has a printer to record such information as who made each key, the security level and the date. There are six security levels, from guest keys through maid's keys to master keys and emergency keys. The receptionist uses the system to punch a new key for a guest when he checks in, the microprocessor in the lock



cancelling the previous card. Hotel owners with security problems can obtain further information from Yale Security Products Ltd, Wood Street, Willenhall, East Midlands, W13 1EA.

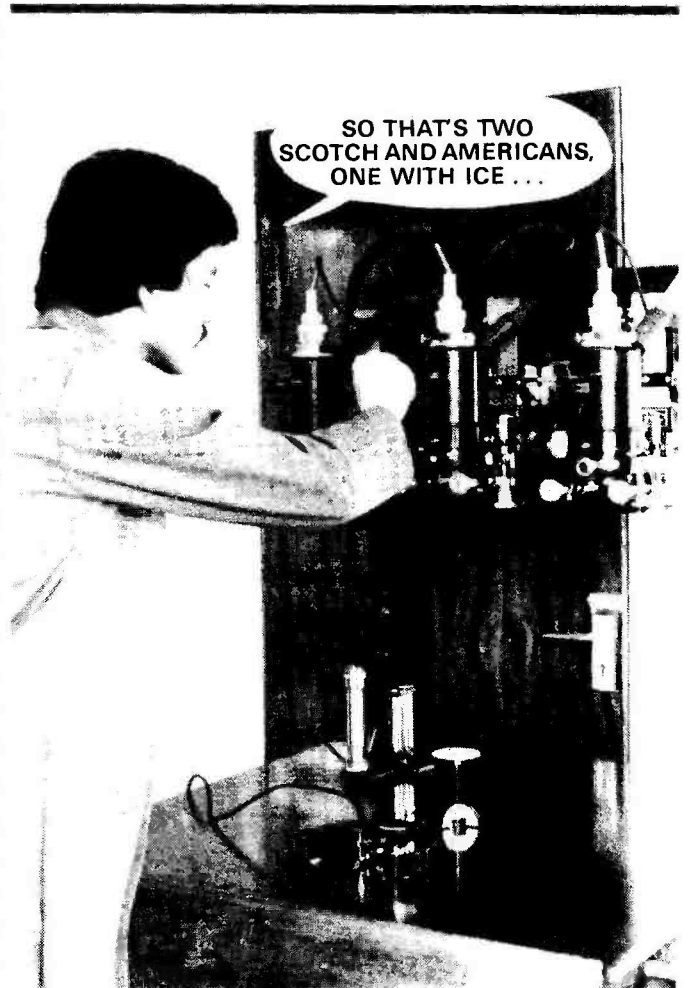Of course, it was only a matter of time before a security company caught up with the private detectives on TV, who've been opening doors with credit cards for years...




## THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

### FEATURES INCLUDE:-

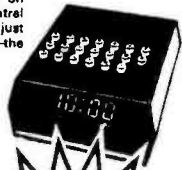- 0.5" LED 12 hour display.
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs.
- 50/60Hz mains operation.
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied).
- Display blanking during power failure to conserve battery power.
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set.
- Useful "sleep" function—turns on output for one hour.
- Direct switch control enabling output to be turned on immediately or after a specified time interval.
- 20 function keypad for programme entry.
- Programme verification at the touch of a button.

(Kit includes all components, PCB, assembly and programming instructions).




**NOW ONLY £39 WITH SO MANY EXTRA FEATURES. OPTIONAL BLACK PLASTIC CASE. READY DRILLED £2.50**
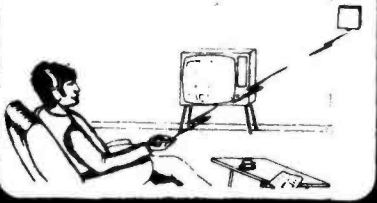
## HOME LIGHTING KITS

These kits contain all necessary components and full instructions & are designed to replace a standard wall switch and control up to 300w. of lighting.

- TDR300K Remote Control Dimmer **£14.30**
- MK6 Transmitter for above **£4.20**
- TD300K Touchdimmer **£7.00**
- TDE/K Extension kit for 2-way switching for TD300K **£2.00**
- LD300K Rotary Controlled Dimmer **£3.50**



## MINI KITS

- MK1 TEMPERATURE CONTROLLER/THERMOSTAT**  
Uses LM3911 IC to sense temperature (80°C max.) and triac to switch heater. 1KW **£4.00**
- MK2 Solid State Relay**  
Ideal for switching motors, lights, heaters, etc from logic. Opto-isolated with zero voltage switching. Supplied without triac **£2.50**
- MK3 BAR/DOT DISPLAY**  
Displays an analogue voltage on a linear 10 element LED display as a bar or single dot. Ideal for thermometers, level indicators, etc. May be stacked to obtain 20 to 100 element displays. Requires 5-20V supply. **£4.50**
- MK4 PROPORTIONAL TEMPERATURE CONTROLLER**  
Based on the SL441 zero voltage switch, this kit may be wired to form a "burst fire" power controller, enabling the temperature of an enclosure to be maintained to within 0.5°C. Max. load 3KW **£5.55**
- MK5 MAINS TIMER**  
Based on the ML1034E Timer IC this kit will switch a mains load on (or off) for a preset time from 20 mins. to 36 hrs. Longer or shorter periods may be realised by minor component changes. Max. load 1KW. **£4.50**

## 3-NOTE DOOR CHIME

Based on the SAB0600 IC the kit is supplied with all components, including loudspeaker, printed circuit board, a pre-drilled box (95 x 71 x 35mm) and full instructions. Requires only a PP3 9V battery and push-switch to complete. AN IDEAL PROJECT FOR BEGINNERS.  
Order as XK102. **£5.00**

For a detailed booklet on remote control - send us 30p & SAE today.

## "OPEN-SESAME"

The XK103 is a general purpose infra-red transmitter/receiver with one momentary (normally open) relay contact and two latched transistor output. Designed primarily for controlling motorised garage doors and two auxiliary outputs for drive/garage lights at a range of up to 40 ft. The unit also has numerous applications in the home for switching lights, TV, closing curtains, etc. Ideal for aged or disabled persons.

The kit comprises a mains powered receiver, a four button transmitter, complete with pre-drilled box, requiring a 9V battery and one opto-isolated solid state switch kit for interfacing the receiver to mains appliances. As with all our kits, full instructions are supplied.

Only **£23.75**

Extra Solid State Switch Kits (XK104) and transmitters (XK105) can be supplied.

**XK104 £2.40    XK105 £10.50**

## THE HOME CONTROL CENTRE

This New Remote Control Kit enables you to control up to 16 different appliances anywhere in the house from the comfort of your armchair. The transmitter injects coded pulses into the mains wiring which are received by receiver modules connected to the same mains supply and used to switch on the appliance addressed. Receivers are addressed by means of a 16-way keyboard, followed by an on or off command. Since pushing buttons can become rather boring, the transmitter also includes a computer interface so you can heating, electric blanket, make your coffee in the morning, etc. without rewiring your house. **JUST THINK OF THE POSSIBILITIES.** The KIT includes all PCBs and components for one transmitter and two receivers plus a pre-drilled box for the transmitter.

Order as XK112 **£42.00**

**ALL PRICES EXCLUDE VAT**

## DISCO LIGHTING KITS

**DL 1000K**  
This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **Only £14.60**



A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DLA1 Allowing audio ("beat") light response. **60p**

## DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. **£15.50**



## REMOTE CONTROL KITS

- MK6 SIMPLE INFRA RED TRANSMITTER**  
Pulsed infra red source complete with hand-held plastic box. Requires a 9V battery. **£4.20**
- MK7 INFRA RED RECEIVER**  
Single channel, range approx. 20ft. Mains powered with a triac output to switch loads up to 500W at 240V ac. **£3.00** (RC500K—Special Price for MK6 and MK7 together **£12.50**)
- MK8 CODED INFRA RED TRANSMITTER**  
Based on the SL490, the kit includes all components to make a coded transmitter and only requires a 9V (PP3) battery and keyboard. 8 x 2 x 1.3cms **£5.90**
- MK18 16-WAY KEYBOARD**  
For use with MK8 and MK18 to generate 16 different codes for decoding by the ML928 or ML926 receiver (MK12) kit. **£5.40**
- MK11 10-Channel + 3 Analogue o/p IR Receiver**  
Based on ML922 decoder IC. Functions include on/standby output, toggle, control of volume, tone and lamp brightness. Includes its own mains supply. **£12.00**
- MK12 16-CHANNEL IR RECEIVER**  
For use with MK8 kit with 16 on/off outputs, which with further interface circuitry, such as relays or triacs, will switch up to 16 items of equipment on or off remotely. Latched or momentary outputs—please specify when ordering. Includes its own mains supply. **£11.95**
- MK13 11-WAY KEYBOARD** For use with MK8, MK18 and MK11 kits. **£4.35**
- MK16 Mains Powered IR Transmitter**  
Mains powered for continuous operation—single channel, for applications such as burglar alarms, automatic door openers, etc. Range approx. 6 ft. **£2.50**
- MK17 12V d.c. IR RECEIVER**  
For use with MK6 or MK16. Relay output with DP 3 Amp change-over contacts, may be used as latched, momentary or "break beam" receiver. Operates from 6-13V d.c. **£9.50**
- MK18 HIGH POWER IR TRANSMITTER**  
Similar to MK8 but with range of approx. 60ft. **£6.20**
- Auxiliary Kits: MK2 Solid State Relay**  
Opto-isolated with zero voltage switching. No. triac supplied. **£2.60**
- MK15 DUAL LATCHED SOLID STATE RELAY**  
Comprises 2 solid state relays and latch for use with momentary version of the MK12. 2 output triacs required (not supplied). **£4.50**

We have the **SOFTY 2 EPROM programmer** in stock at **£169**

## THE KEY TO YOUR SECURITY IS IN OUR LOCK

If the thought of car thieves, house breakers or people tampering with your electrical and electronic equipment upsets you, we have just the kit for you. Our **ELECTRONIC LOCK KIT** includes 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is prewired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7x6x3 cms. Power Consumption is 40uA at 5V to 15V d.c.

At only **£10.50 + VAT**, it will make a smaller hole in your pocket than a bunch of keys!

Electric Lock Mechanism **£13.50**  
Suitable for use with existing door locks and above electronic lock kit.

## 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

- CT1000K Basic Kit **£14.90**
- CT1000K with white box (56/131 x 71mm) **£17.40**
- (Ready Built) **£22.50**

Add 50p postage & packing +15% VAT to total.

Overseas Customers: Add £1.50 (Europe), £4.00 (elsewhere) for p&p. Send S.A.E. for further STOCK DETAILS. Goods by return subject to availability.

**OPEN** 9am to 5pm (Mon to Fri) 10am to 4pm (Sat)

**FREE SHORT FORM CATALOGUE** - send SAE (6" x 9"). We also stock Vero, Books, Resistors, Capacitors, Semi-Conductors etc.

## FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to—

# ELECTRONICS ETI

11 Boston Road London W7 3SJ



TEL: 01-567 8910 ORDERS 01-579 2842 TECHNICAL AFTER 3PM

ENQUIRIES 01 579 9794

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!

This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.



## New Job? New Career? New Hobby? Get into **Electronics Now!**

**FREE!**  
COLOUR BROCHURE

Please send your brochure without any obligation to

I am interested in:

ETI/8/821



NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE



OTHER SUBJECTS \_\_\_\_\_

POST NOW TO:

BLOCK CAPS PLEASE

**British National Radio & Electronics School** Reading, Berks. RG1 7BR

# New Products

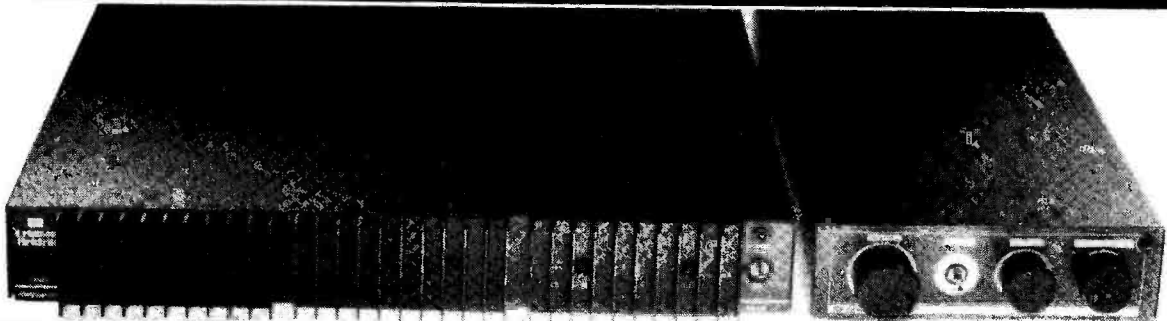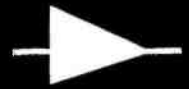

### HIFI STEREO AMPLIFIER KITS

From one of Britain's leading esoteric amplifier manufacturers comes an exciting new package of stereo amplifier kits, designed to offer all the advantages of true high fidelity but without the usual price penalty.

These new kits offer the choice of moving magnet or moving coil inputs, 40 to 100 watts per channel, in fact, everything that made the previous models so popular is included but with added style, easier construction and a full two year warranty.

The new range consists of The CK 1010 Stereo Pre Amplifier, The CK 1040 WPC Power Amplifier, The CK 1100 WPC Power Amplifier.

#### CK 1010

This kit contains all the necessary parts to build a complete pre-amp. The main PCB is ready assembled and tested therefore construction is simply a matter of point to point wiring and mechanical assembly of the connections and controls to the pre punched chassis.

The CK 1010 takes its DC supply from the CK 1040, 1100 or, if using a different power amplifier a PSK power supply kit. Inputs for disc, tuner and tape are provided and an optional add-on moving coil input can be fitted to extend its versatility. (MC2K)

#### CK 1040

This is a nominal 40 watt per channel power amplifier kit which features our dual power supply and the DC output for the CK 1010. All components such as heatsinks, wire and connectors are included and protection is provided from short circuit outputs.

#### CK 1100

Similar to the CK 1040 this model provides a nominal 100 watts per channel with extra heatsinking and thermal cutouts are provided as standard. When correctly assembled these kits are guaranteed for two years.

"It would seem then that Crimson have maintained their position at the top of the commercial kit-build field. There is no oriental amplifier I know of that can better the sound of this combination overall at any price and only a few - such as the KA-1000 (£500+) - are of comparable standard. . . . I can say no more than that for £250 it (CK 1010/MC2K/1100) is a bargain and one that becomes the reference point for kit amplifiers from now on."

**PRICES** CK 1010 - RRP £90.00; CK 1040 - RRP £119.00; CK 1100 - RRP £149.00; MC2K - RRP £25.000; PSK - RRP £20.00

Barclaycard or Access accepted, otherwise send C.W.O. C.O.D. £1.00 extra. All prices include P&P to anywhere in the U.K. Export: Write for pro-forma

**SEND FOR FULL DETAILS ON OUR HIFI KIT PRODUCTS BY WRITING TO FREEPOST ADDRESS BELOW**

**CE** **Crimson Elektrik**

**FREEPOST, 9 CLAYMILL ROAD  
LEICESTER LE4 5ZD. ENGLAND  
TEL. 0533 761920, TLX 34694**



# electronics today

INTERNATIONAL

NEXT  
MONTH

## ACTIVE SPEAKER

A long time ago in a magazine far, far away (well, ETI December '75 to be exact), we published a design for an active crossover. The idea was to avoid the need for bulky, high current coils along with all the problems involved in high-power crossover design, and perform the filtering on the low-level signal. Each audio band was then fed to its driver via its own power amp, removing the need for any conventional crossover altogether. For some time now we've been planning to go one better by presenting a complete active speaker system, with the electronics built right into the speaker cabinet. When we tell you it's a joint design with the speakers by Badger Sound Systems and the power amplifiers by Crimson Elektrik, you'll appreciate how good it is. Don't miss the September issue of ETI if you know what's good for your ears.

## AUTO VOLUME CONTROL




We had hoped to bring you this project in the issue you're holding but lack of space at the last moment meant it had to be held over. The best laid plans of mice and men etc (you can decide for yourself which category editorial staff are part of . . .). Anyway, it's well worth waiting for, because with only a four transistor circuit on a small PCB you can replace your manual volume control with a completely automatic version. Note that this is true volume control, affecting loud and soft sounds equally; not a compressor which reduces the dynamic range of the signal. It's the ideal upgrade for the mike inputs on your public address system.

## SIGNAL MEASUREMENT

Tim Orr, our man of many parts (most of them integrated circuits), is usually to be found within the pages of ETI expounding on the subject of electronic music in one form or another. Next month we have something a little different from him — an article about audio from the point of view of test gear. This is an in-depth feature about several aspects of electronic measurement techniques, including true RMS conversion, noise measurement, and an explanation of the decibel, a unit many people find a trifle confusing. Naturally there's also the usual helpful tables and circuits you've come to expect from us.
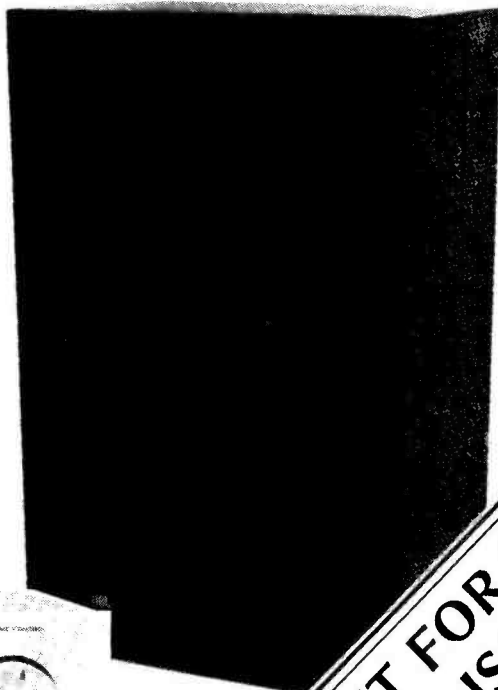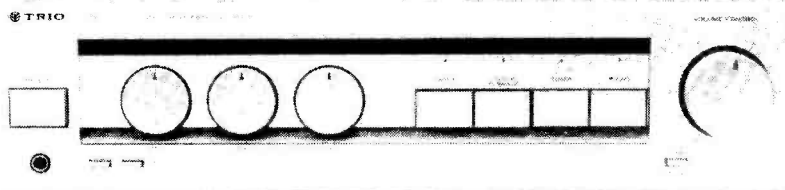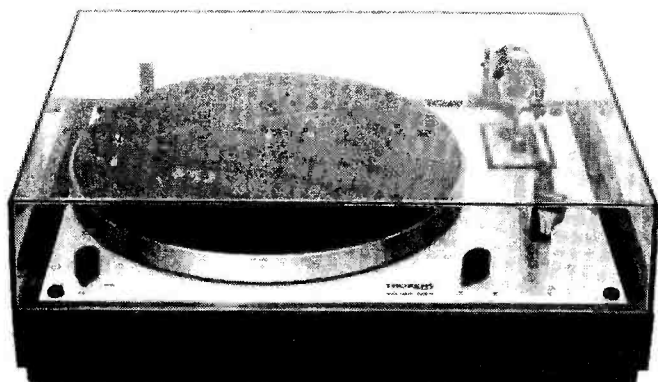
## AUDIOPHILE

Something for the (relatively) hard of wallet is the subject of our (relatively) tame hi-fi expert. The September Audiophile will contain a review of the system shown here, which will provide you with excellent sound quality for an outlay of £500. Deck by Thorens, amplifier by Trio, loudspeakers by JBL — we're not sure if it's built by robots too, but it certainly delivers as far as performance is concerned.



Articles described here are in an advanced state of preparation. However, circumstances may dictate changes to the final contents.


LOOK OUT FOR THE  
SEPTEMBER ISSUE ON  
SALE AUGUST 6th



### MULLARD SPEAKER KIT

40 watt R.M.S. 8ohm DESIGNED BY MULLARD SPECIALIST TEAM IN BELGIUM comprising a Mullard 8" woofer with foam rolled surround, Mullard 3" high power dome tweeter and a cleverly designed B.K. Electronics crossover combining spring loaded loud-speaker terminals and recessed mounting panel. Supplied complete with assembly and cabinet details. Recommended cabinet size 240 x 216 x 445mm.

PRICE £13.90 + £1.50 P&P per kit

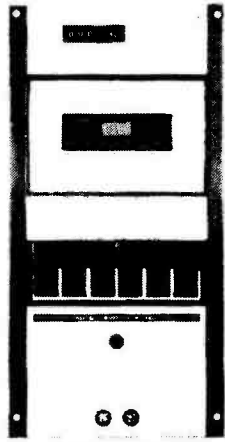

6 piano type keys

### STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels. **Output Impedance:** 10K. **Signal to noise ratio:** 45dB. **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

**Price £26.70 + £2.50 postage and packing.** Supplementary parts for 18V D.C. power supply (transformer, bridge rectifier and smoothing capacitor) £3.50.

**NEW RANGE QUALITY POWER LOUD-SPEAKERS** (15", 12" and 8"). These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. Specification and Price.


**15" 100 watt R.M.S.** Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB. **Price £32 each.** £2.50 Packing and Carriage each.

**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz magnet, 2" aluminium voice coil. Resonant Frequency 25Hz. Frequency Response to 4KHz. Sensitivity 95dB. **Price £23.70 each.** £2.50 Packing and Carriage each.

**8" 50 watt R.M.S.** Impedance 8 ohms, 20 oz. 1 1/2" aluminium voice coil, Resonant Frequency 40Hz. Frequency Response to 6KHz. Sensitivity 92dB. Also available with black cone fitted with black metal protective grill. **Price: White cone £8.90 each. Black cone/grill £9.50 each.** P & P £1.25 each.
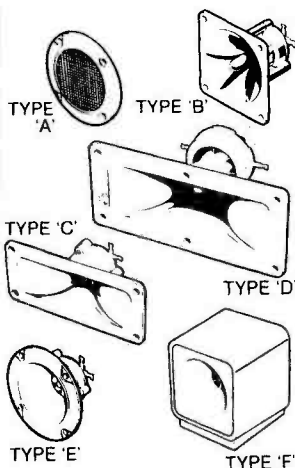
### PIEZO ELECTRIC TWEETERS MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**



**TYPE 'A' (KSN2036A)** 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. **Price £3.45 each.**

**TYPE 'B' (KSN1005A)** 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. **Price £4.35 each.**

**TYPE 'C' (KSN6016A)** 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. **Price £5.45 each.**

**TYPE 'D' (KSN1025A)** 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. **Price £6.90 each.**

**TYPE 'E' (KSN1038A)** 3 1/4" horn tweeter with attractive silver finish trim. Suitable for Hi fi monitor systems etc. **Price £4.35 each.**

**TYPE 'F' (KSN1057A)** Cased version of type 'E'. Free standing satellite tweeter. Perfect add on tweeter for conventional loudspeaker systems. **Price £10.75 each.** U.K. post free (or SAE for Piezo leaflets).



### 1000 MONO DISCO MIXER

A superb fully built and tested mixer/pre-amp with integral power supply. 4 Inputs 2 turntables (ceramic cartridge). Aux. for tape deck etc., plus Mic. with override switch, all with individual level controls. Two sets of active tone controls (bass and treble) for Mic. and main inputs. Master volume control. Monitor output with select switch and volume control. **Outputs** Main 750 mV Monitor 500 mV into 8 ohms **Supply** 220/240V AC50/60Hz **Size** 22 1/2" x 4 1/4" x 2 1/4" **zprice** £39.99 + £2.50 P&P

### 1K.WATT SLIDE DIMMER



- Controls loads up to 1KW
- Compact size 4 3/4" x 1 3/8" x 2 1/2"
- Easy snap in fixing through panel/cabinet cut out
- Insulated plastic case
- Full wave control using 8amp triac
- Conforms to BS800
- Suitable for both resistance and inductive loads

Innumerable applications in industry, the home, and discos/theatres etc.

**Price: £11.70 each + 50p P&P** (Any quantity)

### BSR P256 TURNTABLE

P256 turntable chassis • S shaped tone arm • Belt driven • Aluminium platter • Precision calibrated counter balance • Anti-skate (bias device) • Damped cueing lever • 240 volt AC operation (Hz) • Cut-out template supplied • Completely manual arm. This deck has a completely manual arm and is designed primarily for disco and studio use where all the advantages of a manual arm are required.


**Price: £28.50 + £2.50 P&P**



### POWER AMPLIFIER MODULES



Vu Meter

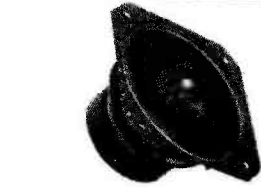


### GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems etc.

- Rolled fabric surround • Twin cone • 8ohm impedance • 15 watt RMS • 1" voice coil
- 13oz magnet • Frequency range 50/15000Hz

**Price: £6.90 each + 75p P&P**

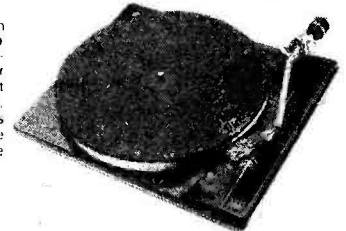

### 100 WATT R.M.S. AND 300 WATT R.M.S. MODULES

Power Amplifier Modules with integral toroidal transformer power supply, and heat sink. Supplied as one complete built and tested unit. Can be fitted in an L.E.D. Vu meter available as an optional extra.

#### SPECIFICATION:

**Max Output Power:** 110 watts R.M.S. (OMP 100) 310 watts R.M.S. (OMP 300)  
**Loads:** Open and short circuit proof. 4-16 ohms.  
**Frequency Response:** 20Hz - 25KHz ±3dB.  
**Sensitivity for Max. Output:** 500mV at 10K (OMP 100) 1V at 10K (OMP 300)  
**T.H.D.:** Less than 0.1%  
**Supply:** 240V 50Hz  
**Sizes:** OMP 100 360 x 115 x 72mm  
 OMP 300 480 x 153 x 66mm  
**Prices:** OMP 100 £29.99 each + £2.00 P&P  
 OMP 300 £89.00 each + £3.00 P&P  
 Vu Meter £6.50 each + 50p P&P

### Matching 3-way loudspeakers and crossover

Build a quality 60watt RMS system 8ohms


Build a quality 60 watt R.M.S. system

- ★ 10" Woofer 35Hz-4.5KHz
- ★ 3" Tweeter 2.5KHz-19KHz
- ★ 5" Mid Range 600Hz-8KHz
- ★ 3-way crossover 6dB/oct 1.3 and 6KHz

Recommended Cab-size 26" x 13" x 13"  
 Fitted with attractive cast aluminium fixing escutcheons and mesh protective grills which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.  
**Price £22.00 per kit + £2.50 postage and packing.** Available separately, prices on request
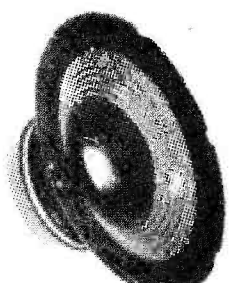
### 12" 80 watt R.M.S. loudspeaker.

A superb general purpose twin cone loudspeaker. 50 oz magnet, 2" aluminium voice coil, Rolled surround. Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.  
**Price £17.99 each + £2.50 P&P**



# B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



# DESIGNING MICRO SYSTEMS

When the chips are down, ETI delivers the goods. In this major new series, Owen Bishop takes the lid off computers and the ICs that go into them. This is the definitive treatise on hardware.

This series is aimed at those readers who already know something about electronics, but who would like to know how electronics is being used today in perhaps its most important application of all — the computer. The series will be concerned with only one of the two types of electronic computer, the digital computer. The other type, the analogue computer, has several important applications but in the main its work has been taken over by digital computers.

We still owe something to the analogue computer, for our trusty work-horse, the op-amp, was originally designed as its building block. Whereas the analogue computer operates with precisely determined voltages which are allowed to vary continuously over their range and are analogues of continuous physical quantities, the digital computer operates with only two discrete voltage levels. The analogue computer depends on the high precision of its op-amps, and needs an op-amp for every step in its computations.

As we shall see, the electronic requirements for the digital computer are much simpler, allowing designers to concentrate on obtaining high speeds of action. The units of the circuit are simple logic gates, thousands of which can be manufactured on a single slice of silicon, already connected to form the complex logic circuits of the computer. This allows the digital computer to have great computing power combined with flexibility of function. It also allows the computer to be mass-produced cheaply so that, today, anyone with a few tens of pounds to spend can buy one.

## The Heart Of The Matter

Figure 1 shows the heart of the computer to be its central processing unit (CPU). It is connected to a number of other devices — the peripheral devices. Input devices usually include a keyboard, so that the operator can send information to the CPU. Information may consist of instructions and data. Input devices might include sensors (eg circuits to measure


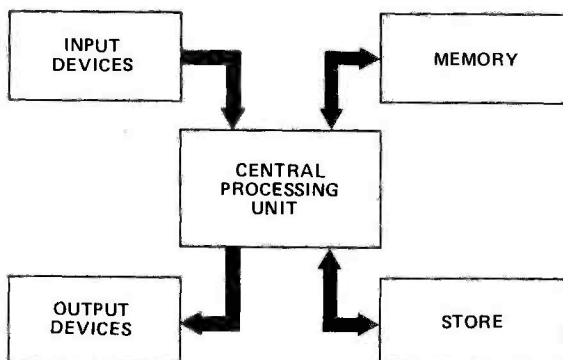


Fig. 1 Block diagram of a computer.

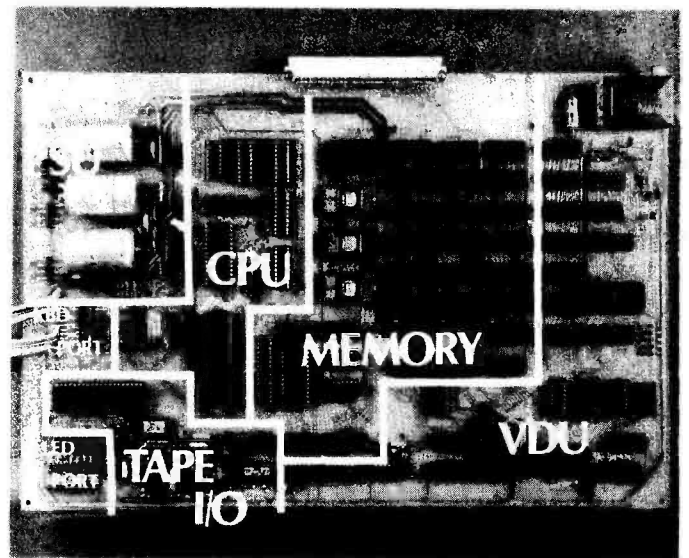

temperature) so that the CPU can obtain its data directly without need for intervention by a human operator. One essential part of this would be an analogue-to-digital converter sub-circuit, to convert the analogue quantity (in this case temperature), to its digital coded equivalent.

Output devices allow the CPU to communicate the results of its computations to the world outside. There is usually a monitor screen on which messages and the results of calculations are displayed. There may also be a printer or a chart plotter. Alternatively there may be direct control of a robot arm or similar device.

The memory is one place where information is stored. The instructions tell the CPU what to do (its program), and it is provided with data to work on. The computer is able to use part of the memory for storing other data which arises from its computations. Information can be transferred between CPU and memory very rapidly and in either direction. Memory is where the currently-used information is held. The store is for information that is not required urgently. The store may consist of a tape deck or disk drive, by means of which information is stored in magnetic form. Blocks of information can be transferred between CPU and store in either direction, but only relatively slowly. The amount of information which can be held in store is much greater than the amount held in memory.

## The CPU

This has the job of receiving instructions and data, either from input, memory or store, processing the data according

to the instructions, and then sending the results of its computation to an output device, memory, store, or possibly to more than one of these. In a main-frame computer, the CPU occupies several circuit boards, but in the personal computer the whole CPU is replaced by a single integrated circuit, the **microprocessor**. This article and the remainder of the series will concentrate on the personal computer, or microcomputer, using a microprocessor as its CPU.

We have been able to use very large scale integration (VLSI) to put all the logical parts of the CPU on to one slice of silicon. The CPU must include an oscillator, or clock, by means of which all its actions and the actions of other peripheral devices are synchronised. It is not possible to reduce the physical size of the components required for this, in particular the quartz crystal, so a least part of the clock circuit is external to the microprocessor. The clock circuit and microprocessor (MPU) together constitute the CPU of the microcomputer.

### We Want Information

Before we look at what goes on inside the MPU we must consider the concept of information in more detail. The unit of information is the bit. The term 'bit' is a shortened version of 'binary digit'. A bit can have one of two values, '0' or '1' but not any other value. This binary concept is widespread in thought, in logic and also in electronics. Table 1 shows pairs of opposite and mutually exclusive states. A binary digit is '0' or '1'; it cannot be anything else. A statement is true or false; truth is by definition the *whole* truth, for half-truth is meaningless. A switch is either on or it is off; it cannot be partly on. If the circuits are made so that only two voltages (low and high) produce definite results and so that intermediate voltages give indeterminate results, then voltages are either high or low. Transistors are either fully off, or fully on (saturated). Given these binary states, the state of any one pair in Table 1 can be used to represent the state of any other pair. For example, we can stipulate that the digit '0' is represented in a computer circuit by a low voltage, and the digit '1' is represented by a high voltage; falsity by '0' or a low voltage, truth by '1'. Here we have a system which allows numerical values and logical statements to be represented in terms of electrical signals. This is the basis of the digital computer.

TABLE 1

0	1
No	Yes
False	True
Absent	Present
Switch off	Switch on
Transistor off	Transistor on
Open circuit	Closed circuit
Low voltage	High voltage

### Grab A Byte

In this system, the bit is the minimum quantity of information to be dealt with. Normally a computer deals with far more information than this. Bits are usually handled in groups. Some of the earlier MPUs handled bits in groups of four, but the majority of micros handle them in groups of eight. A group of eight digits is called a **byte**. In the computer, a byte is represented by a set of eight lines (eg tracks on the PCB), each at high (= 1) or low (= 0) voltage. Or it might be represented by a set of eight flip-flops or bistables, each one either set (= 1) or reset (= 0). According to the interpretation placed on it, the byte could represent:

- A binary value, ranging from 0000 0000 (= 0 decimal) to 1111 1111 (= 255 decimal)
- The truth or falsity of eight different logical statements.
- A coded instruction to the computer.

There is more to be said on this subject next month, but for the moment we will rest with the fact that the computer has to handle binary information represented in electronic form.

### On The Level

For most MPUs the low and high voltages are standardised at 0 V and +5 V respectively. These are the same levels as are used in the 7400 TTL series of ICs. These values are nominal; a Z80 MPU, for example, interprets any voltage between — 0V3 and 0V8 as 'low'. Any voltage between 2 V and 5 V is interpreted as 'high'. Voltages between 0V8 and 2 V produce indeterminate results and must not be allowed to occur. The lack of insistence on precise voltage levels allows computer circuits to remain relatively simple in electronic terms, yet be highly reliable in action.

### Those Important Little Places

If the CPU is the heart of the computer, the heart of the CPU is its **arithmetic logic unit**. The ALU is where data is manipulated according to the instructions stored in memory; we shall describe some of its operations next month. The ALU is able to operate on all eight bits of a byte in a single operation. We say that the **word length** is eight bits, or one byte. Some MPUs, such as the Texas 9980A, have a 16-bit word, but the general principles of its operation are the same as described below.

As an example of a well-known MPU we shall first consider the 6502 (Fig. 2). This successful but relatively simple MPU is used in the Apple, the PET, the BBC Microcomputer, and several other popular microcomputers. The ALU operates in close conjunction with the **Accumulator**. This is a set of eight flip-flops which temporarily hold a byte which is to be operated on by the ALU, or is the result of an operation performed by the ALU. The two registers known as X and Y may also be used to store one byte of data each. Data can be transferred between these registers and the Accumulator in either direction. These registers are therefore useful for storing values obtained in one stage of a calculation, ready for use at a later stage. They are also used as index registers, in which the values held in X or Y are the base addresses of selected blocks of memory. This makes it simpler to access blocks of memory; when storing a table of data, for example.

Since data has to be transferred from one register to another, or from a register to the ALU, it speeds the operation of the MPU if a whole byte is transferred in one operation, rather than bit-by-bit. This requires a set of eight lines connecting all the registers and the ALU. This is called the **data bus**. To distinguish it from a similar set of lines which connect the MPU with the peripheral devices, it is more precisely known as the **internal data bus**.

### It's Under Control

The **control bus** consists of several lines along which signals are sent to coordinate the actions of the various parts of the MPU. For example, if the data held in register X is to be sent to the ALU, a signal must be sent along a control line to register X, making it place the data on the data bus. Register X makes the lines go 'high' or 'low' according to the pattern of 0s and 1s held in its eight flip-flops. At the same time a signal must be sent along another control line to the ALU, making it accept the data now present on the data bus. The control lines emanate from a special part of the MPU called the **Control**.

Despite its impressive name, the Control is no more than a slave. It knows how to carry out the tasks it is allotted, but does not remember what it has just done, and does not know

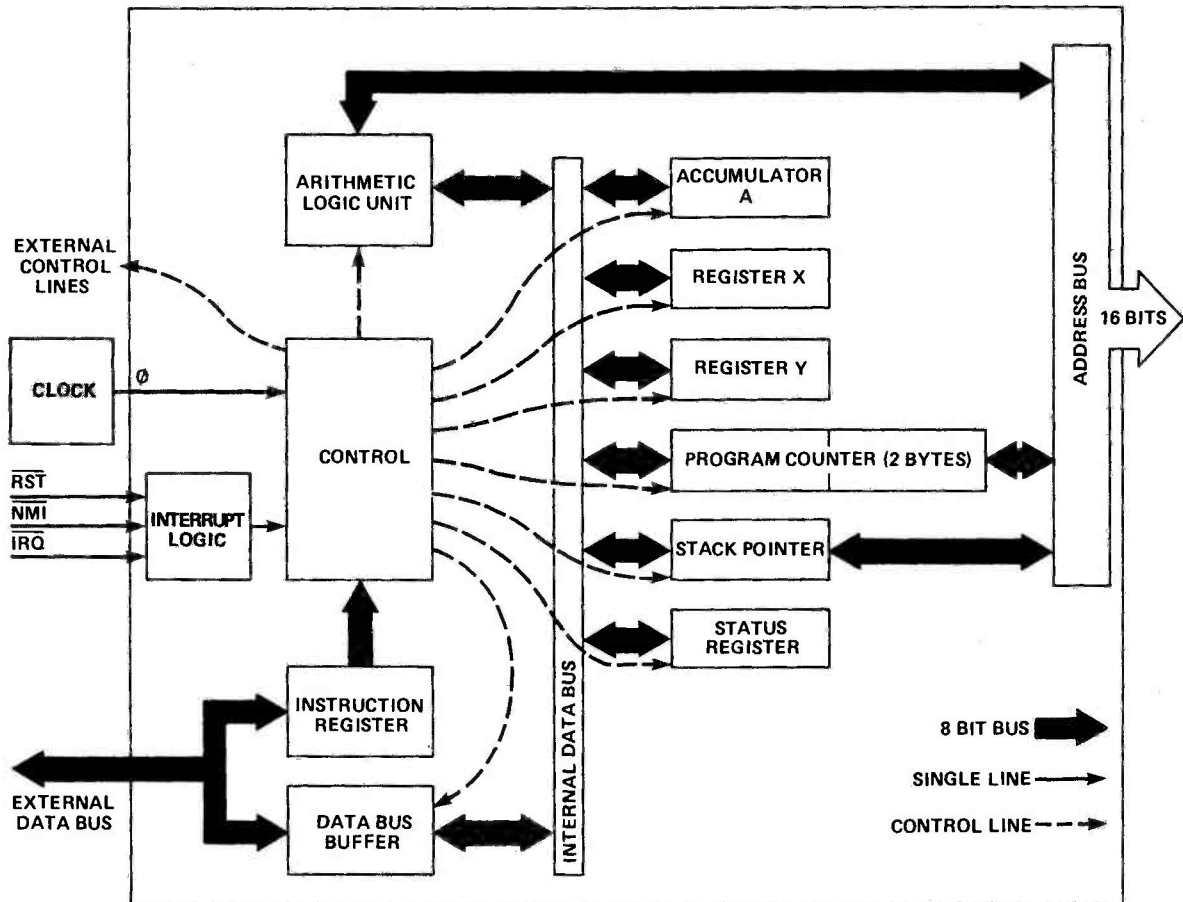


Fig. 2 The internal structure of the popular 6502 microprocessor.

what task it must perform next. The list of tasks (the program) is stored in memory at a sequence of locations. The control simply fetches these instructions from memory, a byte at a time, and acts on each immediately it is received. For this purpose it needs the **Program Counter**, a register in which it records how far it has reached in the program — a sort of 'bookmark'. Since a single byte cannot store numbers greater than 255 (decimal), and since most programs have far more bytes than this, the Program Counter is a double-byte register. Its 16 bits allow any number up to 1111 1111 1111 1111 (binary) to be stored, equivalent to 65535 (decimal).

During its calculations, the MPU often has to store data in the **Stack**, a special section of memory set aside for this purpose. As data is added to or removed from the Stack, the position in memory of the first item in the Stack (the Top of Stack) changes. The **Stack Pointer** register records the current position of Top of Stack, so that the MPU knows where to go to retrieve the stacked data.

### Status Symbols

The **status register** should be considered as eight individual bits, arranged together for convenience as a byte. Each bit is set (made equal to 1), or reset (made equal to 0) individually as the result of a particular operation. For example, bit 7 is set whenever the result of an operation results in a negative value. Bit 1 is set when the result of an operation is zero. These bits, which indicate whether a particular event has occurred or not, are often known as **flags**. Bit 0 holds the 'carry' digit from additions or subtractions in the accumulator.

The remaining sections of the MPU are concerned with communicating with the peripheral circuitry. There is the **data bus buffer** which detects voltage levels on the external data bus and copies these on to the internal data bus. Or it

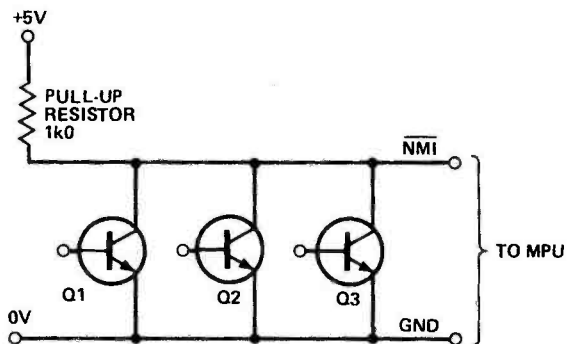


Fig. 3 Switching on any of the transistors generates an  $\overline{\text{NMI}}$

can operate in the reverse direction. If the data bus is carrying an instruction, this is accepted by the **instruction register**. From there it goes to the control which decodes it and then acts upon it. The **address bus** receives outputs from certain registers putting voltage levels on the 16 address lines, a subject which will be dealt with later.

### Dealing With Interruptions

The **interrupt logic** receives signals along any of three lines. All three lines are normally held high by pull-up resistors. The lines are thus described as 'active-low'. In other words, it requires a low level on the line to make the MPU respond. Most control lines in the computer are active-low. This makes it simple for any number of devices to bring the line to its low state. If the line is connected to open-collector transistors, for example (Fig. 3) this is equivalent to a wired-OR

configuration. Then if any one of these transistors is turned on, the voltage level on the line is made low. If a line is active-low, this fact is indicated by a line above its abbreviation (eg  $\overline{RST}$  for active-low 'reset').

The reset line is used to initialize the MPU, either when the computer is first switched on or if it gets into a 'latched-up' condition, in which normal methods of controlling it do not work. There is generally a pull-up resistor holding the voltage high, with a 'Reset' press-button hidden in a fairly inaccessible place at the rear of the computer. Pressing this button temporarily grounds the reset line.

When the computer is first switched on, resetting is usually done automatically, by having a large-value capacitor to hold the line low for a short period while the rest of the system reaches its full voltage levels (Fig. 4). There is no reset button in the Sinclair ZX-81. To reset, you simply turn off the power, wait a moment or two and then reapply power. Resetting the MPU resets the program counter to zero, so that it returns to the beginning of the program stored in memory and starts again.

On receiving a low signal on one of the interrupt lines (NMI or  $\overline{IRQ}$ ) the MPU finishes whatever operation it is engaged in, then stores away (on the stack) any data relating to that operation. This takes only a few microseconds, after

which the program counter is sent to the address in memory of a special interrupt service program. It performs whatever this program requires, then returns to its original program, recovers the data from the stack and continues with the original program as if nothing had happened. Interrupts are used by peripheral devices to gain the attention of the MPU when it is urgently required. The non-maskable interrupt (NMI) takes priority. It cannot be ignored by the MPU, and, while the MPU is performing the NMI task, it cannot be interrupted again. The Interrupt Request ( $\overline{IRQ}$ ) has second priority. The MPU can be pre-programmed to ignore an  $\overline{IRQ}$  altogether. In the 6502, this is done by setting digit 2 of the Status Register to '1'. An  $\overline{IRQ}$  task can be interrupted by an NMI. After completing the NMI task, the MPU continues with the interrupted  $\overline{IRQ}$  task. When this is completed (assuming there is no further NMI) it returns to its original program.

### Z80 Anatomy

Most MPUs have the same kind of organization, or architecture, as the 6502. The Z80 MPU, which is the processor for a wide range of computers including the TRS-80 Models I and II, the Research Machines 380Z, and the Sinclair ZX-81, has a rather more elaborate set of registers. The main set comprises the accumulator (A), the flag register (F, corresponding to the status register of the 6502), and registers B, C, D, E, H, and L, which are general-purpose registers. There is also an alternate set of registers, A', F', B', C', D', E', H', and L'. The MPU normally begins operations by using the main set, but can be switched over to use the alternate set instead, leaving the main set unaffected. It can be switched back to the main set again later.

In addition there are two index registers (IX, IY corresponding to X and Y in the 6502), a stack pointer, and a program counter. In the Z80, IX, IY, SP and PC are double-byte registers (16 bits). Finally there's the interrupt vector register (I) in which instructions for a complex series of vectored interrupts can be stored, and the memory refresh register (R) which is used in connection with refreshing the dynamic memory of the system. This topic will be dealt with in a later article.


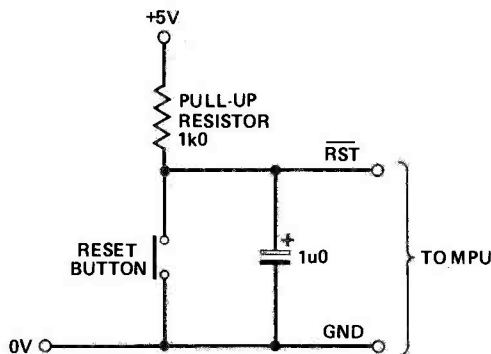


Fig. 4 A suitable circuit for generating a power-on reset pulse. A manual reset button is also provided.

Fig. 5 Pinout of the Z80 microprocessor, with a suitable clock circuit.

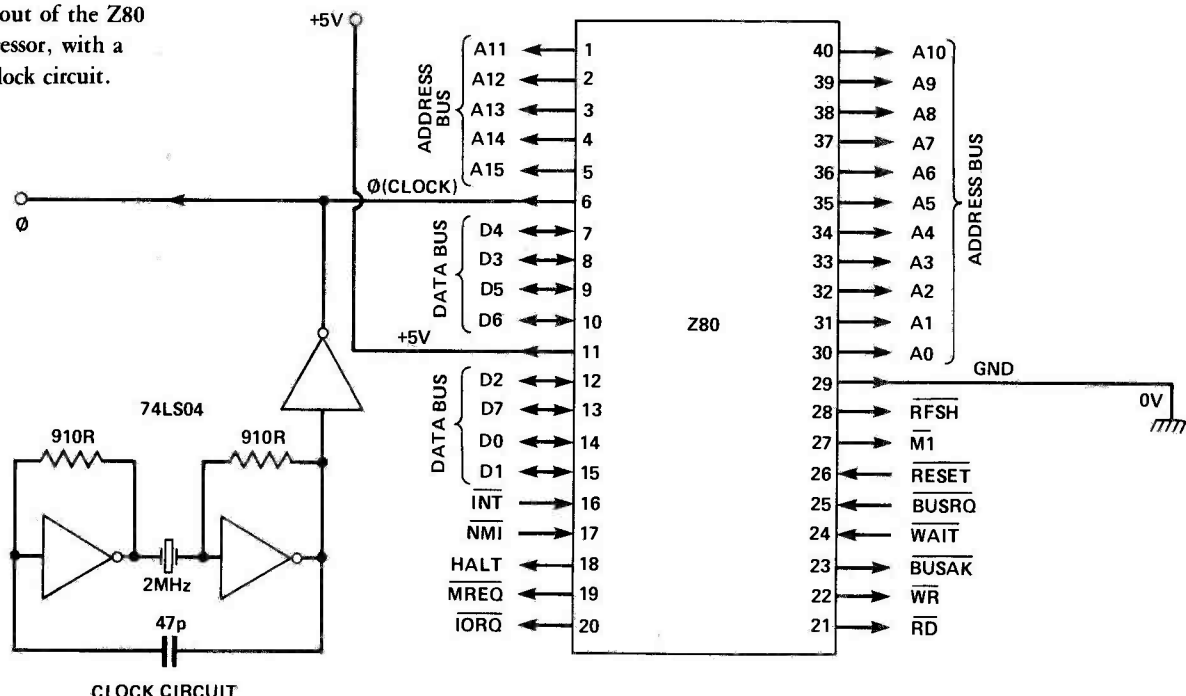

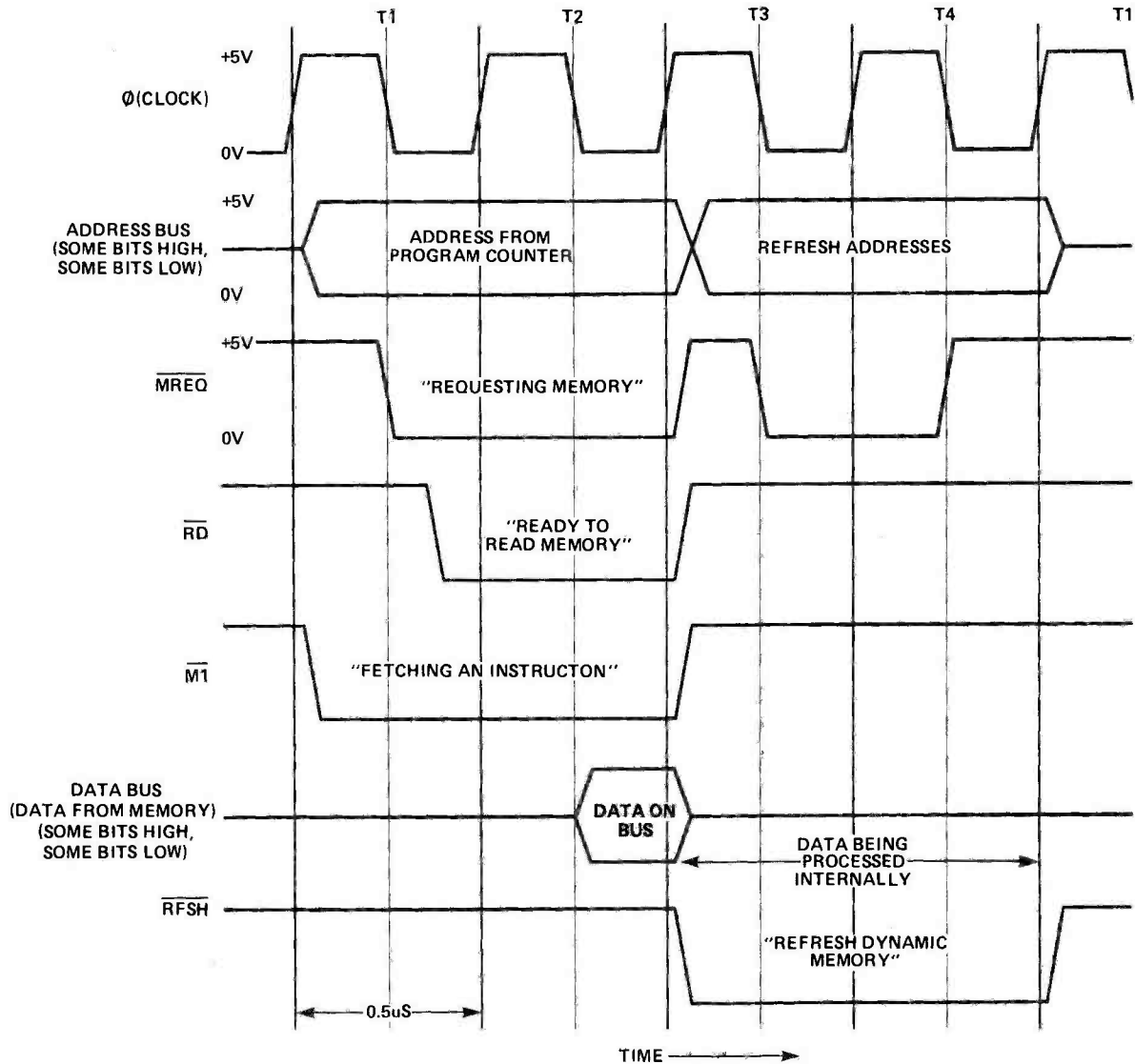


Fig. 6 The clock and control signals for the Z80.

## Making The Connection

The typical MPU is contained in a 40-pin DIL package as shown in Fig. 5, which uses the Z80 as an example. It requires a regulated 5 V DC supply, which is applied between pins 29 (system ground) and 11 (+5 V). The clock circuit supplies pulses at 2 MHz in the case of the original Z80 MPU. The newer Z80A can operate with a clock rate up to 4 MHz. The clock signal may also be taken to peripherals; for example, the circuits which control the monitor.

The eight data lines, D0 to D7, come direct from the data buffer (Fig. 2). These may act as inputs or outputs, though not in both capacities at the same time. The data bus is taken to the peripherals, to allow for transfer of data between these and the MPU. In order that the peripherals will know which one (and *only* one) of them is to receive or transmit data, each peripheral is also connected to the address bus. This is a set of 16 lines, A0 to A15. Address lines are outputs from the MPU. By putting various combinations of highs and lows on these lines the MPU can indicate which peripheral it is addressing. The peripheral may be a printer or a relay on a control board. It may be a single location in memory. Since there are 16 lines, there are 65536 possible combinations of highs and lows, this being the maximum number of locations which can be directly addressed. This figure is usually written in its shorter form, 64K, where one 'K' is not 1000, but 1024 ( $= 2^{10}$ ).

## Peripheral Procedures

The remaining pins of the IC are connected to control lines which connect the MPU to certain of the peripherals. We will consider the input control lines first. The functions of  $\overline{RST}$ ,  $\overline{NMI}$  and  $\overline{INT}$  (=  $\overline{IRQ}$ ) have already been dealt with. A low level on  $\overline{WAIT}$  causes the MPU to halt its operations. It may have asked a peripheral to send data to it but the peripheral is not ready to put the data on the bus. Instead the peripheral sends the  $\overline{WAIT}$  signal, and the MPU suspends action until the peripheral has had time to put the required data on the bus and let the  $\overline{WAIT}$  line go high again. The bus request signal ( $\overline{BUSRQ}$ ) is used by certain peripherals to force the MPU to hand over control of the address bus, the data bus and certain control lines. This is used during an operation known as **Direct Memory Access (DMA)** in which blocks of data are transferred between memory and other peripheral devices without the intervention of the MPU. This is not usually implemented on the smaller microcomputers.

There are eight outputs in the control bus of which we shall mention only three now, dealing with the rest later as part of specific examples. The Machine Cycle One output ( $\overline{M1}$ , pin 27) indicates when the MPU is fetching an instruction from memory. Two outputs of special importance are read ( $\overline{RD}$ ) and write ( $\overline{WR}$ ). When the MPU is to receive data from a peripheral it puts the address of the peripheral on the address bus and make the  $\overline{RD}$  line low. This indicates to

the peripheral, which is also wired to the  $\overline{RD}$  line, that it is to transmit data and not to receive it. When the MPU wants to transmit data to a peripheral, it puts the address on the address bus and makes the  $\overline{WR}$  line low.

## Clocking On

With so many signals being passed in several directions, and with the data bus being required for transmissions into or out of the MPU, it is essential that all these activities take place to a clearly defined schedule. Although micros and their peripherals act at fantastic speeds, these are only fast according to our human scale of appreciation. To an MPU a memory which responds in a microsecond is not particularly speedy. The MPU even has to wait a while to give it time to put the data on the bus, and for the voltages to settle to their intended levels. To keep all sections of the system operating in an orderly way, and to allow the circuits a finite (even if infinitesimal) time to react, the clock is of major importance.

As an example of the way the various parts of the system interact, let us consider what happens when the MPU goes to memory to find the instruction which it is to execute next. Figure 6 shows the voltage levels on the lines concerned. The top curve shows the regular pulsing of the system clock at, say, 2 MHz. At this frequency, each of the periods  $T_1$  to  $T_4$  is 0.5 microseconds (uS). The MPU begins by making  $\overline{M1}$  low, indicating that it is about to fetch an instruction from memory. At the same time it puts on the address bus the address of the memory location in which this instruction is stored. It has obtained this address from its program counter, which has just been incremented following the execution of the previous instruction. The addressed location does not

know at this stage whether it is to be read or written to.

On the next low-going edge of clock, the Memory Request line ( $\overline{MREQ}$ ) indicates that this is an operation involving memory (as opposed to a printer, or monitor peripheral, for example). Immediately after this, the  $\overline{RD}$  line is taken low by the MPU, indicating that this is a read operation. The  $\overline{MREQ}$  signal is used to enable (or 'turn on') the memory IC so that it is ready to put its data on the bus. Since many such ICs are permanently wired to the bus and since only one can be allowed to put data on to any line at any one time, memories have tri-state outputs. These can be high, low or 'high impedance'. The high impedance state means that the output is virtually isolated from the bus and not able to communicate with it. Outputs are in this state until a  $\overline{RD}$  signal is received by the IC. The  $\overline{RD}$  signal can be fed to the memory IC so as to make its outputs change to low impedance and take the lines of the bus to high or low states.

As soon as the data has appeared on the bus the CPU reads it into its instruction register. It has until the next rising edge of the clock to do this. Then  $\overline{M1}$ ,  $\overline{MREQ}$  and  $\overline{RD}$  are made high, indicating that the operation has been completed. The total time for the whole operation is 1 uS. During the next 1 uS the CPU passes the data along its internal bus to its control, where the data is decoded as an instruction and then acted upon. While this is happening there is no need to take in further data and, since the instruction is still being decoded, the time for acting upon it has not yet arrived. In the Z80, this period is used for refreshing dynamic memories, as will be explained in a future issue.

ETI

INFRA RED IMAGE CONVERTOR type 9606 (CV144) 1 1/2" dia. Requires single low current 3KV to 6KV supply. Individually boxed. With data. £12.50 ea. 10 off £100.

INFRA RED QUARTZ LAMPS. 230V 620 Watts Size 1 1/2" x 1/2" dia. £1.50 ea. 10 off £10. 240V 1650 Watts Size 2 1/4" x 1/2" dia. £3 ea. 10 off £25.

FANS 115V 13 Watt Size 3 1/2" x 3 1/2" x 1 1/2". Secondhand £2.50 ea.

CENTAUR FANS 115V Size 4 1/2" x 4 1/2" x 1 1/2". New £4.50 ea.

Secondhand £2.50 ea.

DELAY LINES 50 nanosecs. Ground-in-out. Size 2 x 7/16 x 5/16".

New 25p ea. 10 off £2.

PULSE TRANSFORMERS. Sub min Size 1/2 x 5/16 x 1/4". Secondary centre tapped. New. Suitable for Thyristor triggering. 20p ea. 10 off £1.80.

100 off £15.

MOTORS 12V DC with pulley & semiconductor speed control. New £1 ea.

10 off £8.

DIAMOND H CONTROLS ROTARY SWITCH Single pole 10 way. Printed circuit mount. New 10p ea. 100 off £7. 1000 off £50.

STEPPING MOTORS - 200 Steps 20 oz/in torque. 12/24V input. 5 wire. £12 ea.

STEPPING MOTORS - 5 Volt 3.3 Amp operation 2 Wire. PPS 0-220. RMP 0-250. Used £16 ea.

STEPPING MOTORS - 6/12 position can be used as a tach. 12/24V will work on 5V £1.50 ea. 5 for £8.

SINGLE PLY TELEPRINTER PAPER. Size 8 1/2" x 37 1/8". 1.25 each or 12 rolls for £12 P&P £3.50.

BLACK RIBBONS FOR TELEPRINTERS 75p each or 8 for £4.

MIN KEYBOARD Push contacts, marked 0-9 & A-F & 3 optional. £1.75 ea.

10 for £15.

KEYBOARD PAD Size 3 x 2 1/2 x 2" high with 12 Alma Reed Switches. Blue keys marked in green. 0-9 & star with one blank. £4 ea. 5 off £15. P&P £2.50.

DON'T TAKE CHANCES Use the proper EHT Cable 10p metre. £7.50 100 metres P&P £2.

RAPID DISCHARGE CAPACITORS 8 mfd 4KV £5 each. P&P £2.

HUNTS CAPACITOR 0.1 mfd 3KV DC Wkg. Size 1 1/2" dia x 3". £1.25 ea.

10 for £10.

E.H.T. CAPACITOR 500 pf 8KV 20p each.

DECOUPLING CAPS 0.05mfd 10V; 0.01mfd; 0.047 250V; 330pf. 100 off one type £1.50.

CAPACITORS all at 5p each. 3300pf; 220nf 250V; 0.01mfd 160V; 0.1 uf 400V.

REMO TV Type MULTIPLIER. Two high voltage outputs & focus £1 each.

10 for £8.

RANCO 250V 18A THERMOSTATS with Control Knob calibrated 50-200°C. £2.50 each.

MICROPHONE/EARPIECE INSERTS. Ex. Min. Brand New wrapped. 75p ea.

10 off £8.

TRANSFORMERS - All Brand New.

Auto 240V Input 115V 1 Amp output £1.25 ea.

240V Input Sec 6V 1.86A. Size 2 1/2" x 2 x 2". Good quality £1.50 ea.

240V Input Sec 12V 100MA. Size 60 x 40 x 42mm 80p ea.

240V Input Sec 12-0-12V 50MA. Size 63 x 45 x 40mm £1 ea.

115V Input Sec 5V 250MA Size 1 1/16 x 1 1/2 x 1 1/4". 2 for 50p.

240V Input Sec 2 windings 12V and 24V 1 Amp. Size 2 1/2" x 2 x 2". £2 ea.

Sub-Min 0-120-240V Input Sec 12-0-12V rated 4VA. 75p ea. 10 off £8.

100 off £45.

TOROIDAL 0-115-230V Input. Output 13.5-0-13.5V rated 8VA. £1.70 ea. 10 off £15.

TOROIDAL 0-120-240V Input. Output 0-12V; 10VA per winding. Encapsulated Identical to R.S. Components at £9.40. OUR PRICE £5 ea.

TELEPHONES - P&P £1.50 ea. 5-10 units £6. Over by arrangements. 706 style Black, Grey, Blue, Green £5.50 ea. 10 off £45. Discoloured £4 ea. 10 off £27.50.

746 style Black or Grey £7.50 ea. Older Black style £2.50 ea.

SOME EHT TRANSFORMERS & CAPACITORS always available - please enquire.

VARIACS - 2 Amp. Ex-equipment. Good condition. £12 ea. P&P £3.

TRANSISTOR INVERTOR. 115V AC 1.7 Amp input. Switching at 20KHZ. Output windings from Pot Core. Can be rewound or broken for components. Circuit Supplied. £1.25 ea. P&P £2. 10 off £10 Carriage £8.

Convert this unit to a SUPER BATTERY CHARGER. Attractive green

ministry quality case - removable top/bottom plates - heavy duty power

switches - high power resistors to control current - centre mounted

amp meter - wing nut terminals on front panel for connecting leads.

£3.50 ea. P&P £5 FOUR UNITS £12 Carriage £8.

Miniature VARIAC 0.6 amp in Blue Case size 10 1/4 x 6 1/4 x 6 1/4" with 20

coloured screw style 4mm sockets giving multiple voltage & current

outputs. As new £12 P/P £4.

AMPLIFIER BOARD complete with Heat Sink & two output Transistors

type 2N5293 Circuit supplied £1.50 ea.

CABLE TIES Black 13cm long or White 9cm. 50 for 50p.

TOGGLE SWITCH. Centre off. 20p each 10 for £1.80

4 CORE CURLY WIRE extending to 2 metres. 20p ea. 10 off £1.80; 100 off £15

Min Potentiometers - Erie. 1K Lin; 3.3K Lin; 4.7K Lin. All 15p each.

100 off £12.

WIRE WOUND RESISTORS 4 WATTS - all at 10p ea; 10 off 85p; 100 off £7

Values - 1R0; 2R2; 2R4; 750R; 22K - 1R5; 82R; 100R; 150R; 820R; 9K1; 15K.

MULTICORE CABLE. 18 Way. Multi colour. 75p per metre. 100 metre drum

£66. Carr £8.

GEC 4 Button UHF TUNER £1.50 ea. 10 off £12.

GEC 6 Button UHF/VHF TUNER. £2 ea. 10 off £15.

SOLID STATE UHF TUNER 38MHz £1 ea. 10 off £8.

PHOTOMULTIPLIERS - All with information - P&P all tubes £1.50 ea.

British 2" window £2 ea; American 2" £3 ea; RCA type 2020 £4 ea. Special

American by RCA £8 ea; MULLARD 150AVP Useful dia 32mm £4 ea.

HONEYWELL STRIP CHART PAPER 122ft rolls. Ref no 378528-0100

EVEN 12/68. 50p per roll. 10 rolls £4 P&P £3.50.

BLUE THERMAL PAPER 430ft roll 8 1/4" wide £1.50 per roll P&P £2. 6

rolls £8. Carr. £8.

FOR FULL COMPONENT & TEST EQUIPMENT LIST WRITE OR PHONE

MARCONI AM/FM SIGNAL GENERATOR type TF1066B/6S. 10-470MHz in 5 bands. £275 each. Carriage £6.

WAYNE KERR COMPONENT BRIDGE type B521 (CT375). Resistance 10mOhm-1000 Meg Ohm; Capacitance 5000uF-1pF; Inductance 1uH-500kH. With copy of manual. ONLY £40 each. Carriage £6.

AVO VALVE TESTER type CT160 (22 valve bases) with copy of manual. £20 each. Carriage £6.

AVO TRANSISTOR ANALYSER type CT446 with copy of manual £20 each. Carriage £6.

AVO SIGNAL GENERATOR No 2 AM/FM. AM 0.45-225MHz; FM 20-100MHz. With copy of manual £75 each. Carriage £6.

MARCONI COUNTER/FREQUENCY METER TF1417/2 with Converter type TF2400/TM7265 - 500MHz. £35 each. Carriage £6.

TELETYPE PRINTERS KSR33-ASC11 Keyboard £50. ASR33 - as above with 8 bit punch and reader £75. Carriage £6 each unit.

MULTIMETER Russian type 4324 AC/DC volts, AC/DC current; ohms etc. Brand new, boxed £12.50 each P&P £2.50

SINE & SQUARE WAVE AUDIO GENERATOR Type TE22 20Hz-200KHz. Portable. As new ONLY £35 each P&P £4

SCOPE STYLE CASE size 7 1/2" x 7 1/8" x 13 1/4" deep with attractive blue covers & strap handle. As is a TACHITOSCOPE but ideal for the home constructor for parts. £4.50 each P&P £2.50.

PLEASE NOTE - WE WILL BE CLOSED TO CALLERS MONDAY AUGUST 9th UNTIL SATURDAY AUGUST 21st INCLUSIVE

MINIMUM ORDER OF GOODS £3. MINIMUM PACKAGING & POSTAGE £1.50. VAT at 15% MUST be added to TOTAL of GOODS & PACKAGING, BUT PLEASE ensure sufficient monies is sent to cover PACKAGING and Postage to avoid delays in us dispatching your order. CALLERS VERY WELCOME STRICTLY BETWEEN 9am-1pm and 2-5pm Monday to Saturday inc. BARCLAYCARD (VISA) and ACCESS taken. Official orders welcome.

# CHILTMELD LTD

NORWOOD ROAD, READING


TELEPHONE NO. READING 669656

(2nd turning left past Reading Technical College in King's Road then first right - look on right for door with "Spoked Wheel")



# MEMOTECH Explores the Excellence of your ZX81

THIS MONTH -  
**2 NEW  
PAKS!**

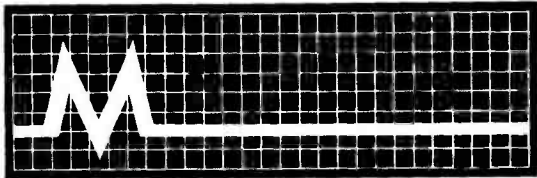

**MEMOPAK 32K RAM**  
Operates in tandem with Sinclair 16K Ram to give a full 48K!

## Memotech's Memopak Range

All five of the currently available Memopaks are housed in elegant black anodised aluminium cases, and are styled to fit wobble-free onto the back of the ZX81, allowing more add-ons (from Memotech or Sinclair) to be connected.

<p>£ <b>68</b><sup>70</sup> plus VAT</p>	<p><b>MEMOPAK 64K MEMORY EXTENSION</b> The 64K Memopak extends the memory of the ZX81 by 56K, and with the ZX81 gives 64K, which is neither switched nor paged and is directly addressable. The unit is user transparent and accepts commands such as 10 DIM A(9000). Breakdown of memory areas...0-8K-Sinclair ROM. 8-16K-This area can be used to hold machine code for communication between programmes or peripherals. 16-64K-A straight 48K for normal Basic use.</p>
<p>£ <b>43</b><sup>43</sup> / £ <b>26</b><sup>00</sup> plus VAT</p>	<p><b>MEMOPAK 32K and 16K MEMORY EXTENSIONS</b> These two packs extend and complete the Memotech RAM range (for the time being!) A notable feature of the 32K pack is that it will run in tandem with the Sinclair 16K memory extension to give 48K RAM total.</p>
<p>£ <b>52</b><sup>00</sup> plus VAT</p>	<p><b>MEMOPAK HIGH RES GRAPHICS PACK</b> HRG Main Features — • Fully programmable Hi-Res (192 x 248 pixels) • Video page is both memory and bit mapped and can be located anywhere in RAM. • Number of Video pages is limited only by RAM size (each takes about 6.5K RAM) • Instant inverse video on/off gives flashing characters • Video pages can be superimposed • Video page access is similar to Basic plot/unplot commands • Contains 2K EPROM monitor with full range of graphics subroutines controlled by machine code or USR function</p>
<p>£ <b>34</b><sup>70</sup> plus VAT</p>	<p><b>MEMOPAK CENTRONICS TYPE PARALLEL PRINTER INTERFACE</b> Main Features — • Interfaces ZX81 and parallel printers of the Centronics type • Enables use of a range of dot matrix and daisy wheel printers with ZX81 • Compatible with ZX81 Basic, prints from LLIST, LPRINT and COPY • Contains firmware to convert ZX81 characters to ASCII code • Gives lower-case characters from ZX81 inverse character set</p>

**Coming Soon...**

MEMOPAK RAM  
HI-RES GRAPHICS  
CENTRONICS I/F

ZX81

A complete range of ZX81 plug-in peripherals  
Digitising Tablet    RS232 Interface

We regret we are as yet unable to accept orders or enquiries concerning the above products, but we'll let you know as soon as they become available.

Access Barclaycard holders  
Please tel. Oxford  
(0865) 722102  
(24 hrs)

Please make cheques payable to MEMOTECH Ltd.

Please Debit my Access/Barclaycard\* account number

\*Please delete whichever does not apply

Please send me	Price	No	Total
64K RAM	£68.70 + £10.30 VAT	£79.00	
32K RAM	£43.43 + £6.52 VAT	£49.95	
16K RAM	£26.00 + £3.90 VAT	£29.90	
HRG	£52.00 + £7.80 VAT	£59.80	
CENTRONICS I/F	£34.70 + £5.20 VAT	£39.90	
Packaging & Postage	£2.00 per unit		
<b>TOTAL ENC</b>			



SIGNATURE \_\_\_\_\_ DATE \_\_\_\_\_

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_



TELEPHONE \_\_\_\_\_

We want to be sure you are satisfied with your Memopak – so we offer a 14-day money back Guarantee on all our products.  
Memotech Limited, 3 Collins Street, Oxford OX4 1XL, England Tel: Oxford (0865) 722102 Telex: 837220 Orchid G

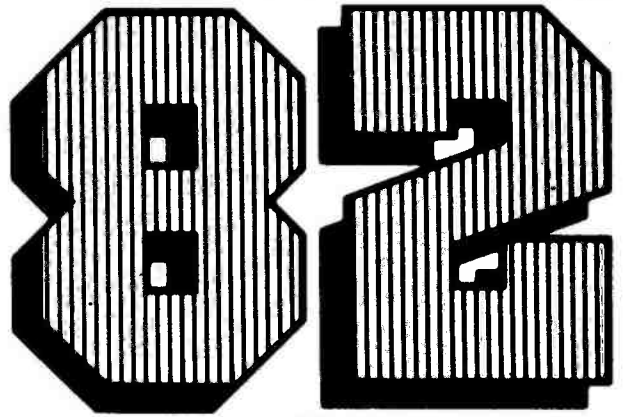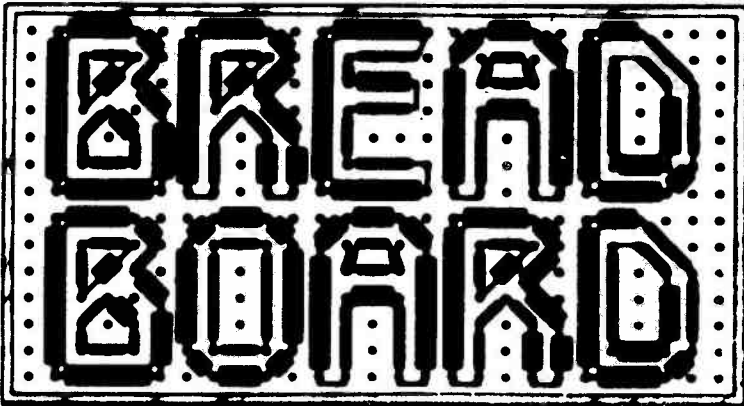BRITAIN'S LEADING EXHIBITION FOR ELECTRONICS ENTHUSIASTS



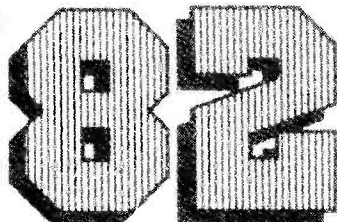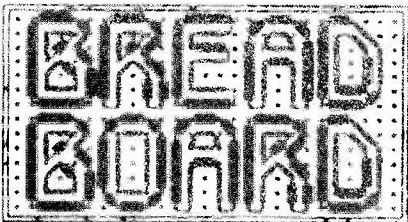**10-14 NOVEMBER 1982 at:**  
**ROYAL HORTICULTURAL SOCIETY'S NEW HALL**  
**GREYCOAT ST, WESTMINSTER, LONDON SW1.**



**MORE  
COMPREHENSIVE  
THAN EVER BEFORE:**

- ★ COMPUTERS
- ★ LOGIC
- ★ KITS
- ★ AUDIO
- ★ TEST GEAR
- ★ COMPONENTS
- ★ RADIO
- ★ C.B.
- ★ DEMONSTRATIONS
- ★ MUSIC
- ★ GAMES
- ★ LECTURES
- ★ MAGAZINES
- ★ BOOKS
- ★ SPECIAL OFFERS

# SPECIAL TICKET OFFER

For the fifth consecutive year BREADBOARD is back with even more to offer electronics enthusiasts.

This is the best opportunity to update yourself on all the latest equipment, ideas and developments.

**COME AND SEE THEM IN ACTION.**

Book your tickets now at this special low rate.

# 50<sup>p</sup> OFF

**BOOK NOW**  
(OFFER ENDS SEPTEMBER 30th)

**SPECIAL ADVANCE BOOKING PRICE**  
ADULTS £1.50 – STUDENTS/SENIOR CITIZENS £1.

PLEASE SEND ..... tickets @£1.50 and ..... tickets @£1.  
I enclose cheque/P.O. for .....


NAME .....

ADDRESS .....

.....

.....

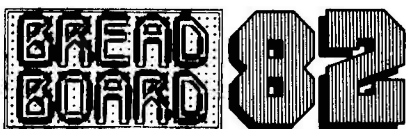Send to: BB 82, Argus Specialist Publications Ltd,  
145 CHARING CROSS ROAD, LONDON WC2H 0EE.



**THE EXHIBITION YOU CAN'T AFFORD TO MISS**

**NEW CASIO WATCHES**

**100 METRE WATER RESISTANT**

W-100  
Resin  
case/strap  
£16.95



W-450  
Stainless  
steel  
£24.95

Time and auto calendar. Alarm and hourly chimes. Count-down alarm timer with repeat memory function. Professional 1/100 second stopwatch. Time is always on display, regardless of display mode. Amazing 5 year lithium battery life. 12 or 24 hour display.

50M W/R

100M, W/R

200M W/R




W-35  
£19.95

W-450C  
£21.95

DW-1000  
£39.95

W-35, W-450C and DW-1000 Divers watch. Identical functions to the W-450 above. They are all stainless steel (W-450C, resin strap).

**50 METRE WATER RESISTANT**

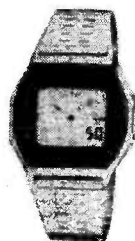

AA-92W  
Analog/  
digital.  
Stainless  
steel  
£25.95

W-20  
(Right)  
Resin  
£12.95

AA-92W. LCD analog time, or digital time and calendar display (dual time). Countdown Alarm Timer and alarm have amazing moving graphics. Chimes and professional stopwatch. Night Light. W-20. Alarm, chimes, pro stopwatch. 12/24 hour.

WS-70 (left)  
Stainless  
steel  
£22.95



SA-50  
Chrome  
Not W/R  
£14.95

WS-70. Compact and ultra slim, only 5.7mm thick. Countdown alarm, professional stopwatch, alarm, hourly time signal, calendar, dual time (24 hour). SA-50. Non water resistant version, 4.6mm thick. SA-50G. Gold plated version of the SA-50 £19.95

**NEW LOWER PRICES**

**ANALOG/DIGITAL  
AX-5 ONLY £19.95**

Black resin version of the AX-250, below  
The World's most versatile watches?

AX-250 ONLY £24.95

- Analog LCD hours/minutes  
Digital display
- Local time, 12 or 24 hour
  - 62 day calendar display
  - Dual time, 12 or 24 hour
  - Alarm time display
  - Countdown alarm timer with memory function
  - Professional stopwatch
  - Optional hourly time signal
- Daily alarm: electronic buzzer or 3 optional melodies



AQ-11  
True analog  
Chrome  
£39.95

AQ-101  
True analog  
Chrome  
£39.95

Classical analog with digital hours, minutes, seconds; Auto calendar; Alarm and hourly time signal; Professional stopwatch; Date memory.

**MULTI ALARMS**

MM-400  
6 Melodies  
Chrome  
£29.95



CA-95 (right)  
2 Melodies  
Calculator  
Resin  
£19.95



Both have 12 or 24 hour time and calendar display; Professional stopwatch; Hourly time signal; Daily alarm with pre-alarm; Daily alarm with post-alarm; Weekly alarm/extra daily alarm.  
MM-400. Time is always on display. Dual time, 12 or 24 hour. Monthly alarm/extra daily alarm.  
CA-95 Calculator. CA-951 Metal version £29.95

**OTHER WATCHES**

- J-100 Jogging pacer/computer; calculator; alarm; stopwatch. Elsewhere £18.95. Pricebeater £19.95
- GM-30 Battleships/Submarines version £14.95
- A656A. Alarm; Dual time; stopwatch. Chrome £9.95

**NEW KEYBOARDS NEW**

**CT-1000P DIGITALIZED  
SYNTHESIZER**




**ONLY £325** Interest free credit available

10 pre-set instruments, 1,000 switchable sounds, with a protected memory for your ten favourites. 5-octave, split keyboard, programmable arpeggio or real time sequencer, transposition between -1 and +0.5 octaves. Integral amp/speaker, Output and Headphones jacks. Details on request.

**PORTABLE COMPUTERS**

SHARP PC-1500 Colour Computer

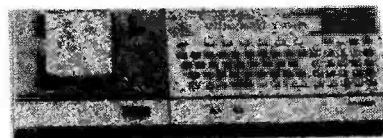


**PRICEBEATERS**

- PC-1500 Computer (elsewhere £158.95) £157.50
- CE-150 Printer/Interface (£139.95) £137.50
- CE-151 4K RAM expansion module (£47.95) £46.95
- CE-155 8K RAM expansion module (£77.95) £76.50
- CE-15A 14 application programs on tape £14.95
- 16K ROM extended BASIC, 3.5K RAM (expandable). 7 x 156 dot matrix display. With clock, calendar, alarm and around 30 scientific functions on board.

Colour brochure on request  
MICROL 1500 SOFTWARE - DETAILS ON REQUEST

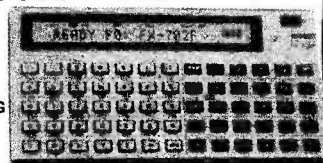**CASIO POCKET COMPUTER**

FX-702P  
Usual Price  
£99.95  
Elsewhere  
£97.95  
PRICE-BEATING  
£95.95



FX-702P PLUS MICROL Professional Programming Pack (worth £9.95) ONLY £99.95

- BASIC programming. Up to 1,680 program steps, up to 226 memories. 55 scientific functions.
- MICROL PROCOS Visualc type software on tape £24.95
- FP-10 Printer for 702/602/601/502/501. Usually £44.95 Price elsewhere £43.95 PRICEBEATING £42.95
- FA-2 Cassette interface for 702/602/1/502/1 £19.95

**PROGRAMMABLES**

FX-602  
Usual price £74.95  
Price elsewhere £71.95  
PRICEBEATING £69.95  
OR with MICROL Professional Programming Pack worth £9.95  
ONLY £74.95  
Up to 512 steps, up to 88 memories. 50 scientific functions.



**CALCULATORS**

- Scientifics
- FX-950 50 functions, 10 digits. SOLAR POWER £22.95
  - FX-900 8 digit version with less functions £19.95
  - FX-550 50f, 10d, Lithium battery. Wallet size £15.95
  - FX-8100 Clock, calendar, alarms, stopwatch £19.95
  - FX-82 £11.95, FX-100 £14.95, FX-7 £9.95, FX-5 £7.95
- Calculating alarm clocks
- FT-7 Fortune Teller £16.95; BG-15 Boxing game £16.95; ML-75 Card size, 12 melody alarms £12.95; BQ-1100 Biorhythm £16.95; UC-365 Wallet £19.95; UC-360 Card size £19.95
- Basic
- LC-950 Metric conversions. Double display. £16.95
  - SL-801 SOLAR £8.95; MG-777 3 games, clock £14.95; MG-880 £10.95; MG-885 £10.95

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

**TEMPUS**

LEADING CASIO SPECIALISTS  
Dept HE  
38 Burleigh Street, Cambridge CB1 1DG  
Telephone: 0223 312866

DELIVERY  
NORMALLY  
BY RETURN

# PLAYMATE GUITAR EFFECTS/AMP

The sounds of the superstar in your own room — or in the middle of a field! The PLAYMATE will help you on your way. Design and development by Phil Walker

The Playmate is a small practice amplifier for use with a guitar giving a few watts output for easy listening while also providing some of the basic effects used by many musicians. It is ideally suited to those who do not carry all the various effects units around in their guitar case but would like to be able to practice at odd moments or in out-of-the-way places.

In addition to the amplifier and standard tone controls etc, various distortion and wah-wah effects are possible. As a by-product of the circuitry a sustain effect is also possible.

The sound output is provided by a small internal loudspeaker and the whole module is powered from a small mains unit or batteries. An

external foot pedal could be used with the wah effect if required. This consists of a variable resistor and a couple of other resistors to provide the necessary control current. The internal control is still active at this time and can be used to set an operating range.

## The Circuit

The circuit is in general straightforward. It consists of an input buffer with a gain of about 50 followed by a signal compression stage which reduces the dynamic range greatly in order to feed the effects circuitry at a constant level. The effects consist of a distortion-inducing stage for fuzz and a variable band-pass filter for the wah wah. After the effects stages, the

dynamic range of the signal is restored to normal before being fed to the mixer, tone controls and power output stages.


The input buffer consists of a single 3140 CMOS op-amp whose gain is set at 48 by R2, R3. The following dynamic range compressor consists of one part of a LM13600 dual transconductance amplifier. The gain of this device is a function of the amplifier bias current, the input diode current and the load resistor. The output buffer of the device is used here as a peak detecting rectifier which charges a capacitor (C3) to the peak value of the output signal less two base-emitter drops (about 1V4). If this voltage is greater than about 0V7 the resulting current flowing through the input linearising diodes causes the effective stage gain to decrease and keep the output level constant.

## Distorting The Facts

Distortion effects in this project are of two types. The first is mainly even harmonic generated by half-wave-rectifying the input, inverting it and then mixing it with the original signal to get from no distortion to complete frequency doubling. In addition to this, overload type distortion is provided by a high gain clipping amplifier using non-linear feedback (IC3a,3b).

Wah wah sound effects are produced by a current-controlled state variable filter. The control current determines the centre frequency of the pass band while a two-gang variable resistor sets the bandwidth and compensates for inevitable gain changes.

Tone controls are of a standard type and use frequency-selective feedback networks around an op-amp. The following power amplifier has been designed to have a low quiescent

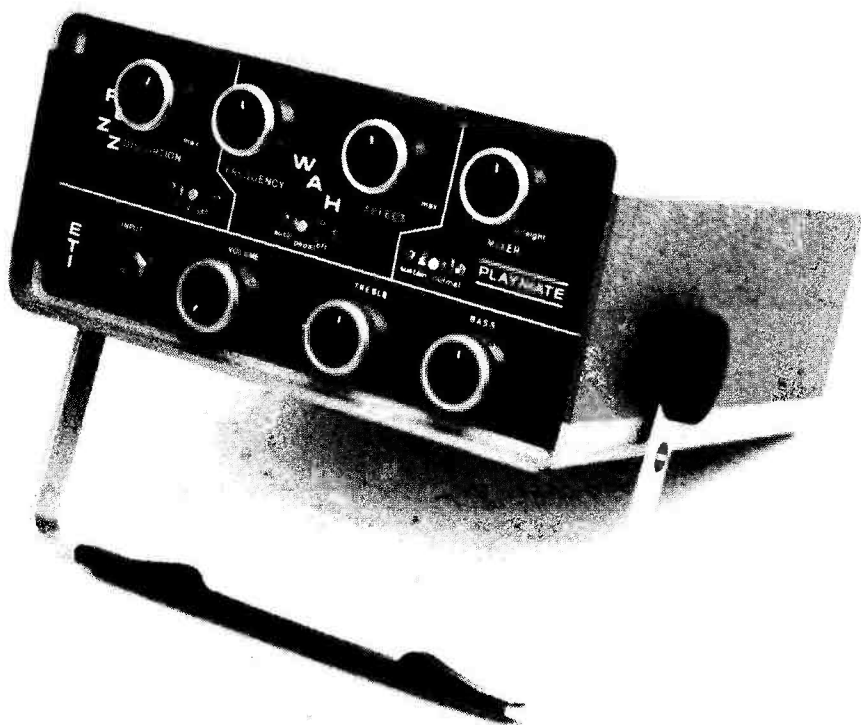

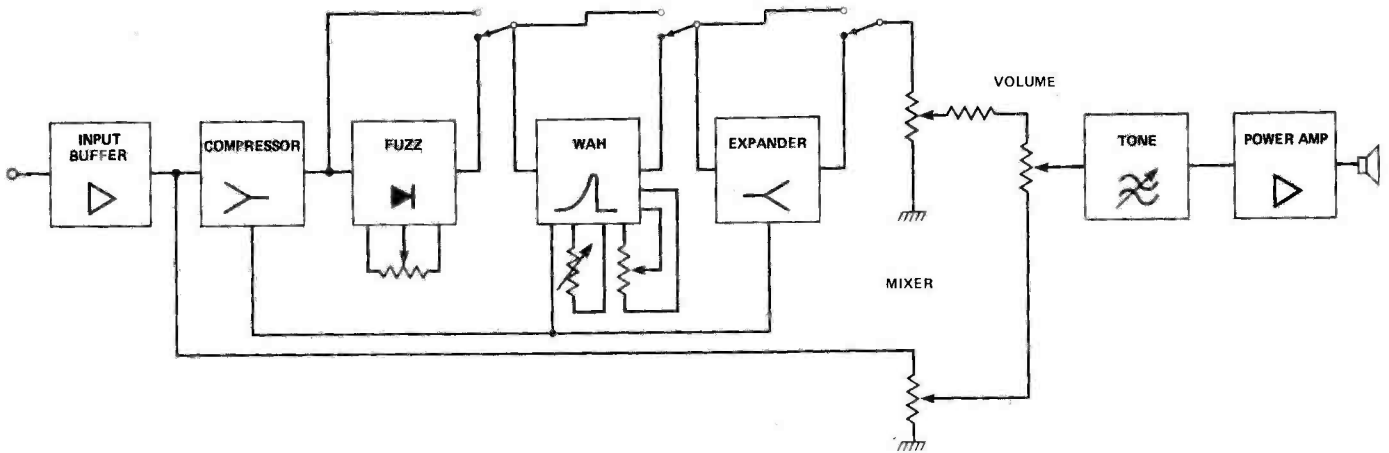


Fig. 1 Block diagram of the Playmate.

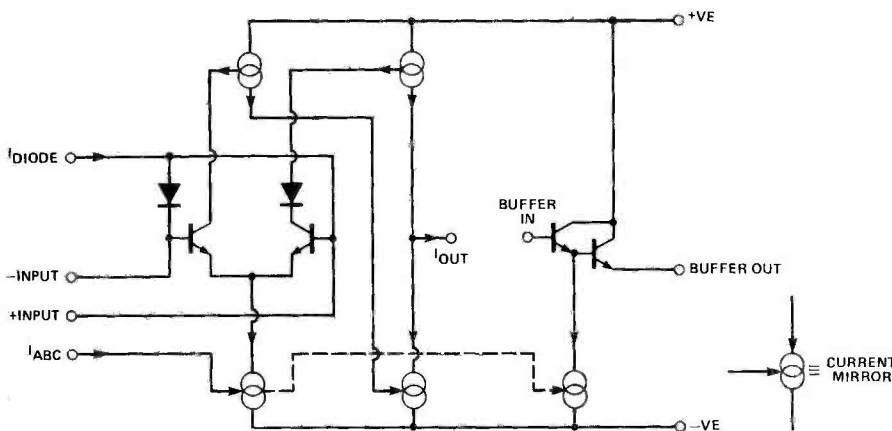


Fig. 2 Internal circuitry of the LM13600 — an operational transconductance amplifier!

$$I_{out} = \frac{I_{abc} \times q \times V_{in}}{2KT} \times V_{ir}$$

$$26 \times 10^{-3}$$

If the diode current is not zero and the signal current is less than  $I_{D/2}$  then the transfer function is:—

$$I_{out} = 2 \times I_{abc} \times \frac{I_s}{I_D}$$

where

- $I_s$  = signal current
- $I_{abc}$  = amp. bias current
- $I_D$  = lin. diode current
- $I_{out}$  = output current

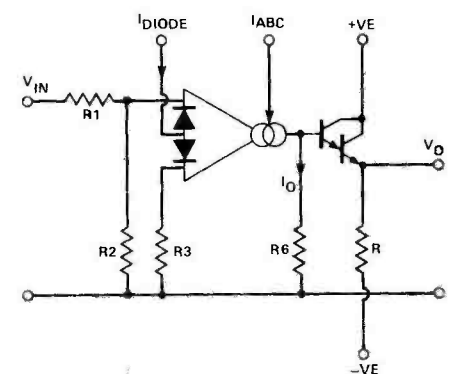


Fig. 3 Basic voltage amplifier circuit.

current. This is important if batteries are to be used as many amps of the IC variety take 30 mA or more, or are designed for single rail working.

### The LM13600


This device is used for two functions in this project. One of these is the compressor/expander while the other is the wah wah. In both of these, use is made of the fact that the

gain of the device is dependent on the amplifier bias current and the linearising diode current (provided that the input current is less than half the diode current). In fact the output resistor also determines the gain but is not so easily varied.

If the diode current is zero then the manufacturers' data sheet shows that the transfer function of the device is:—

If we use resistors for input and output, it can be seen that the voltage gain of a stage using this device can be controlled easily by use of the bias and linearising diode currents.

Figure 3 shows the basic circuit for a voltage amplifier and from it we can show that the output voltage  $V_o$  is dependent on the bias and diode currents.

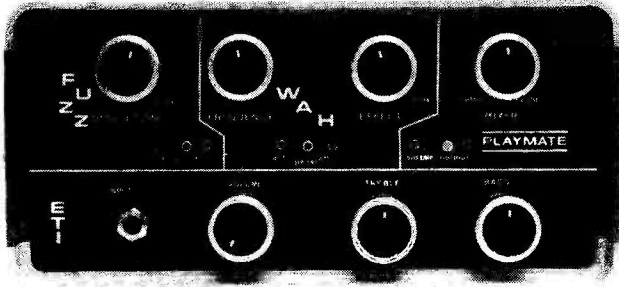

## HOW IT WORKS

The gain of the input buffer IC1 is set by R2 and R3 at 48. R1 determines the input impedance while C1 provides DC blocking. The output from this device goes to the dynamic range compressor IC2a and its buffer IC3a. This part of the circuit also provides control signals for the expander circuit and, if required, for the wah wah effect. The buffered output from the compressor then goes via C4 to the first part of the fuzz effect circuitry constructed around around IC3b. Here an inverted half-wave-rectified version of the input signal is produced by the action of D1 and D2 in the feedback network of IC3b. This is applied to RV1 from which a portion is selected and mixed with a little of the original signal. As the half-wave-rectified signal at this point of the circuit is twice as great as the straight-through signal, by varying the setting of RV1, amounts of distortion varying from none to virtual frequency doubling can be selected.

The mixture of signals obtained above is now applied to IC3c where they are amplified. The amount of amplification is determined by the setting of SW1. In position 3 minimum gain is provided and in fact the whole fuzz section is bypassed. Position 2 gives the same gain, allowing the first distortion stage to be effective. The final position connects D3 and D4 via C5 and R19 into the feedback circuit of IC3c instead of R18. This has the effect of greatly increasing the small signal gain but causing the output to limit sharply, thus clipping and squaring the output. This facility is available on whatever output is coming from IC3b.

The output from the fuzz stages now passes to the wah wah. This effect is produced by the current controlled state variable filter used in a band-pass mode. The filter is realised by using a LM13600 device with a controlled bias current providing the variable centre frequency. The 'Q' factor is controlled by a dual gang potentiometer, half of which is used to control the 'Q' factor while the other half compensates for the effective gain change as this is altered. In this type of circuit the frequency range is determined by the values of C7, C8, R24 and R26, while the actual centre frequency is controlled by the amplifier bias current. If the bias current is allowed to become too small it is sometimes found that a thump is heard at the output; in order to prevent this R34, R35, D5 and R33 are used in the control circuitry to keep the current above this threshold.

SW2 selects between the control options for the wah wah circuit. The 'off' position bypasses the circuit altogether, the 'pedal' position makes access to an external foot pedal if fitted, while the 'auto' position connects to an output from the compressor stage. This control signal is a current which is proportional to the amount of signal compression being

applied to the input signal. The magnitude of this current increases as the input signal increases. The result of this is that when the input signal is loud, the wah wah centre frequency is high and as the input decays, the wah wah frequency decreases with it. The effect of this is to make a wah sound automatically whenever a string or chord is played.

The output from this section is buffered and adjusted in level by IC3d. After this the signal passes to the signal expansion stage built around IC2b. C23 provides DC isolation and R36 converts the input voltage to a suitable drive current for the IC. For this application the linearising diode current is held constant while the amplifier bias current is varied. Q1 in the compressor circuit provides the control current for this stage allowing a good match in the attenuation/gain characteristics of the two stages. SW3 selects either the output from the expander or bypasses it as required to give normal or sustain on the effects channel.

A dual gang potentiometer RV4 allows mixing between the original signal and the effect-modified signal. This is followed by a volume control RV5 to set the output sound level.

After the volume control, IC5a buffers the signal before applying it to the tone control circuit around IC5b. The configuration used here is a very common type of feedback arrangement. As an approximation, the gain of an op-amp with feedback is taken as  $-(\text{feedback resistor value})/(\text{input resistor value})$ . If we replace the feedback and input resistors with variable impedances, we find that when the feedback impedance is greater than the input impedance then the overall gain is greater than unity, and vice versa. As impedances vary with frequency, the gain at each frequency will tend to be different. The only time the gain does not vary is when the input and feedback impedances are equal whatever their magnitude. This is the general principle on which the tone control networks operate.

The final section to be considered is the power amplifier stage. Voltage amplification is provided by IC6 and the output from it drives two complementary compound Darlington pairs, Q4/Q6 and Q5/Q7. Quiescent current through the output devices is set by RV8 in conjunction with Q3, R54 and C19. R59 and R60 aid in maintaining bias stability and provide some protection to the output transistors in the event of a fault. R61 and C20 compensate for load impedance variations at high frequency and C18 reduces the high frequency gain of the power amplifier to reduce the possibility of RF oscillation. The large capacitors C21-25 are to reduce the effects of aging batteries and prevent low frequency oscillation or intermodulation distortion.

$$V_o = \frac{V_{in} \times 2 \times I_{abc} \times R_L}{R1 \times I_D}$$

$$I_{in} = V_{in}/R_{in} \text{ Therefore}$$

$$\text{and the gain } \frac{V_o}{V_{in}} = 2 \times \frac{I_{abc}}{I_D} \times \frac{R_L}{R1}$$

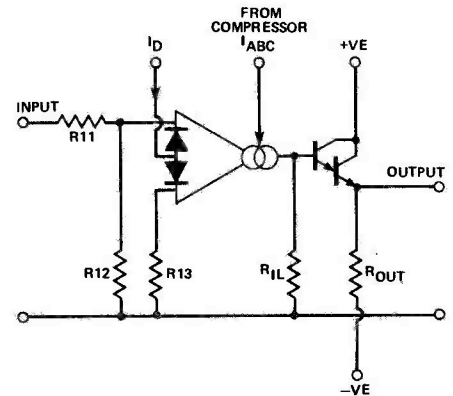


Fig. 4 The LM13600 as an expander.

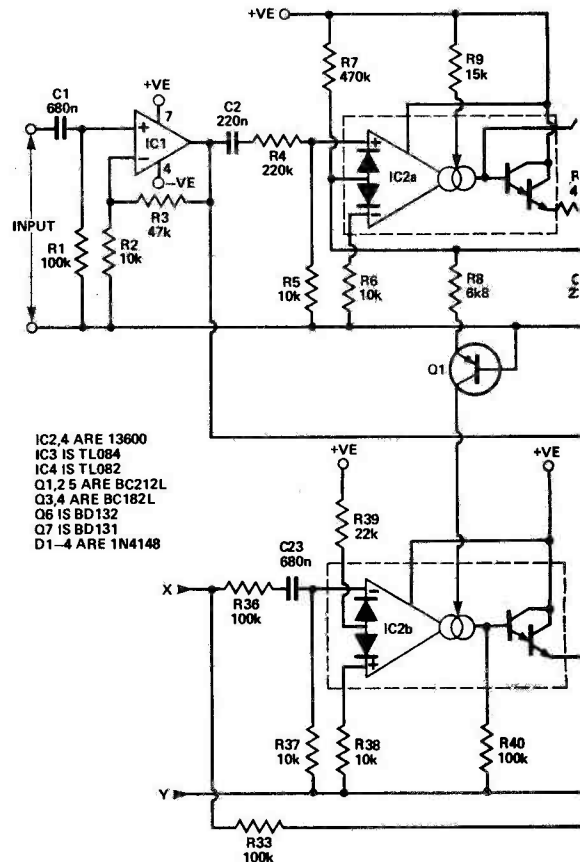


Fig. 6 Circuit diagram for the Playmate.

## Compressing With The LM13600

Figure 5 shows the circuit used in this project to compress the dynamic range of the signal input. For very small signals  $I_D$  is virtually zero and the amplifier operates with a very high gain. As the signal increases, the output peak voltage will reach a level sufficient to charge the capacitor C to about one diode drop. If the input

signal tries to increase further the resulting current into the input diodes will cause their impedance to fall, thus increasing the attenuation of the input and maintaining a constant output level.

At any time the current flowing into the diodes is:—

$$I_D = \frac{2 \times (V_o - 3 \times 0.7)}{R_2}$$

The  $3 \times 0.7$  represents the voltage drops associated with the base-emitter junctions of the output buffer transistors and the voltage drop of the linearising diodes. This voltage does vary with temperature and current so since another control current is required for the expander function, this is derived by using a resistor and common base transistor. The configuration gives a current output which tracks the compressor control current very closely as it has the same number of junctions in series.


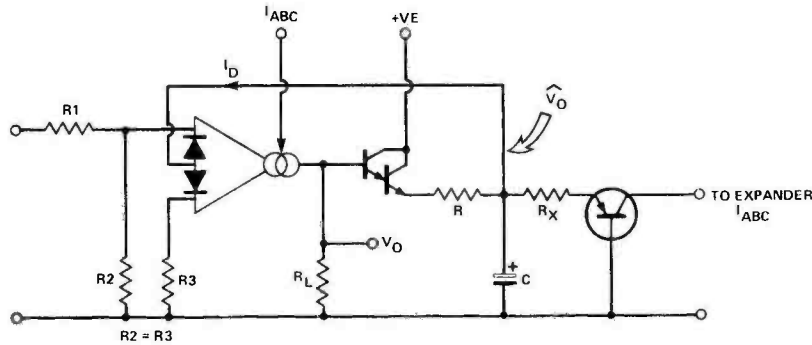


Fig. 5 Here the LM13600 is configured as a compressor.
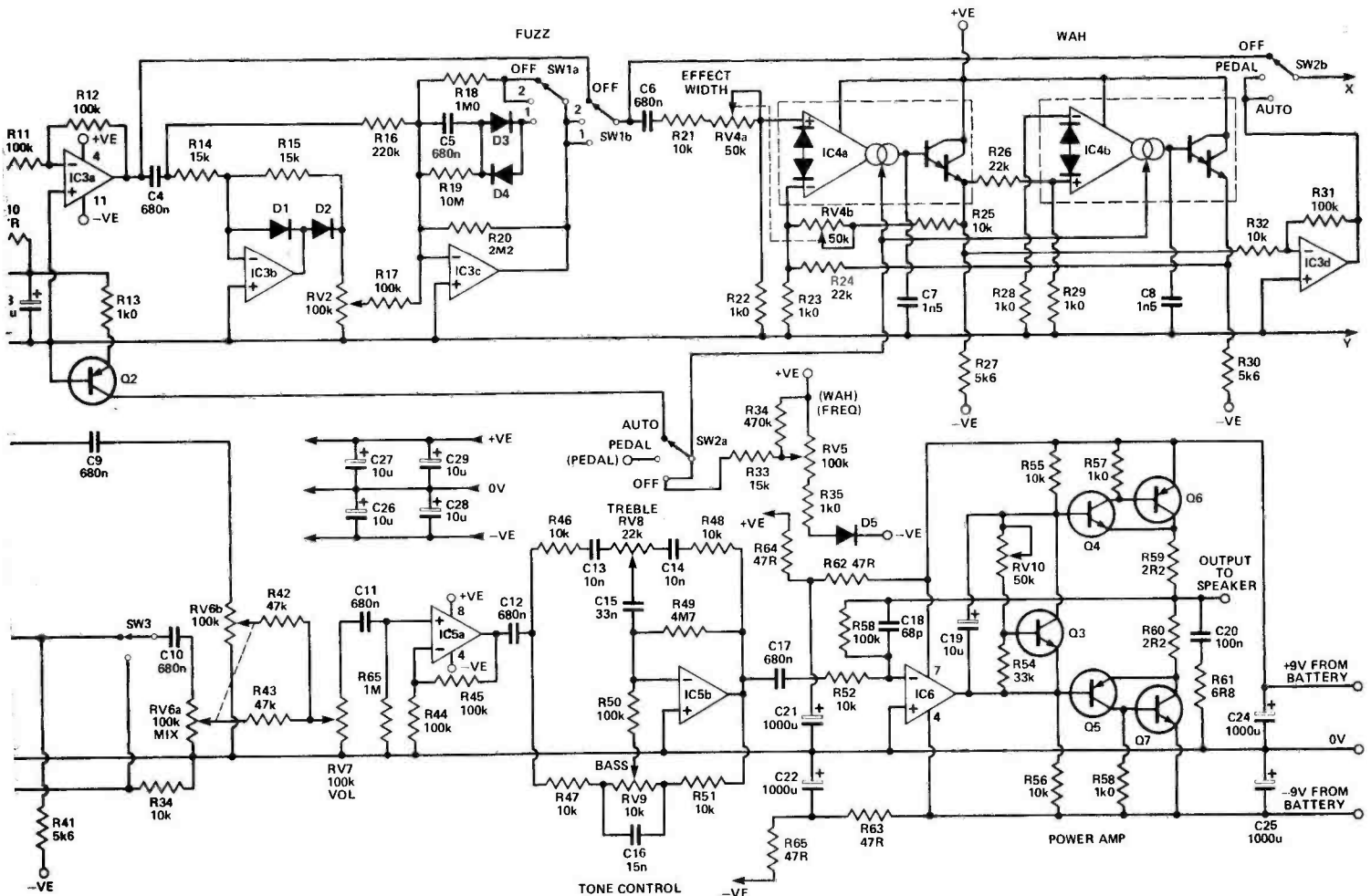
## The LM13600 As An Expander

If the current produced by the above circuit is fed into the bias current input of a virtually identical stage while the diode current is held a constant then the voltage gain equation above shows that the gain of the circuit will be increased as the current increases. Moreover the product of the two gains will be constant giving an invariant overall signal transfer function.



The construction details, parts list and overlays will appear next month. ET

# TOROIDALS

The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.



Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
30 VA 70 x 30mm 0.45kg Regulation 18%	1x010	6+6	2.50	<b>£5.12</b> +DP1 04 +VAT 10.92 TOTAL £7.08
	1x011	9+9	1.66	
	1x012	12+12	1.25	
	1x013	15+15	1.00	
	1x014	18+18	0.83	
	1x015	22+22	0.68	
	1x016	25+25	0.60	
50 VA 80 x 35mm 0.9 kg Regulation 13%	2x010	6+6	4.16	<b>£5.70</b> +DP1 30 +VAT 11.05 TOTAL £6.85
	2x011	9+9	2.77	
	2x012	12+12	2.08	
	2x013	15+15	1.66	
	2x014	18+18	1.38	
	2x015	22+22	1.13	
	2x016	25+25	1.00	
80 VA 90 x 40mm 1 kg Regulation 12%	3x010	6+6	6.64	<b>£6.08</b> +DP1 57 +VAT 11.91 TOTAL £8.09
	3x011	9+9	4.44	
	3x012	12+12	3.33	
	3x013	15+15	2.66	
	3x014	18+18	2.22	
	3x015	22+22	1.81	
	3x016	25+25	1.60	
120 VA 90 x 40mm 1.2 kg Regulation 11%	4x010	6+6	10.00	<b>£6.90</b> +DP1 57 +VAT 11.26 TOTAL £8.16
	4x011	9+9	6.66	
	4x012	12+12	5.00	
	4x013	15+15	4.00	
	4x014	18+18	3.33	
	4x015	22+22	2.72	
	4x016	25+25	2.40	
160 VA 110 x 40mm 1.8 kg Regulation 8%	5x011	9+9	8.89	<b>£7.91</b> +DP1 57 +VAT 11.44 TOTAL £9.35
	5x012	12+12	6.66	
	5x013	15+15	5.33	
	5x014	18+18	4.44	
	5x015	22+22	3.63	
	5x016	25+25	3.20	
	5x017	30+30	2.66	

- ★ 294 TYPES TO CHOOSE FROM!
- ★ ORDERS DESPATCHED WITHIN 7 DAYS OF RECEIPT FOR SINGLE OR SMALL QUANTITY ORDERS
- ★ 5 YEAR NO QUIBBLE GUARANTEE

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE
225 VA 110 x 45mm 2.2 kg Regulation 7%	6x012	12+12	9.38	<b>£9.20</b> +DP1 57 +VAT 11.66 TOTAL £12.86
	6x013	15+15	7.50	
	6x014	18+18	6.25	
	6x015	22+22	5.11	
	6x016	25+25	4.50	
	6x017	30+30	3.75	
	6x018	35+35	3.21	
300 VA 140 x 50mm 2.6 kg Regulation 6%	7x012	12+12	10.00	<b>£10.17</b> +DP1 57 +VAT 11.83 TOTAL £14.00
	7x014	18+18	8.33	
	7x015	22+22	6.82	
	7x016	25+25	6.00	
	7x017	30+30	5.00	
	7x018	35+35	4.28	
	7x026	40+40	3.75	
500 VA 140 x 60mm 4 kg Regulation 4%	8x016	25+25	10.00	<b>£13.53</b> +DP1 57 +VAT 12.38 TOTAL £16.26
	8x017	30+30	8.33	
	8x018	35+35	7.14	
	8x026	40+40	6.25	
	8x025	45+45	5.55	
	8x033	50+50	5.00	
	8x042	55+55	4.54	
625 VA 140 x 75mm 5 kg Regulation 4%	9x017	30+30	10.41	<b>£16.13</b> +DP1 57 +VAT 12.42 TOTAL £18.95
	9x018	35+35	8.92	
	9x026	40+40	7.81	
	9x025	45+45	6.94	
	9x033	50+50	6.25	
	9x042	55+55	5.68	
	9x029	220	2.84	

**IMPORTANT:** Regulation - All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

### The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

### How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders.

Also available at Electrovalue, Maplin and Technomatic.

Please send \_\_\_\_\_

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order


Debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

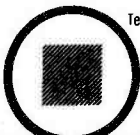Post to: ILP Electronics Ltd, Freepost, 4 Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.  
Telephone Sales (0227) 54778. Technical (0227) 64723. Telex 965780.



**ILP TRANSFORMERS**  
(a division of ILP Electronics Ltd)

TECHNOMATIC TECHNOMATIC TECHNOMATIC

## ★ SPECIAL OFFER ★

2114L-200nS	1-24	25-99
2114L-450nS	100p	90p
2716 (+5v)	90p	85p
2532	250p	225p
2732	400p	375p
6116P-3	400p	375p
	500p	475p

### CONNECTOR SYSTEMS

I.D. CONNECTORS (Spendlock Type)				D CONNECTORS 9 way 15way 25way 37way				DIP PLUGS (Grey)		FLAT CABLE (Grey)	
No. of Wires	Header Plug	Receptacle	Edge Conn.	Solder Tackle	90p	160p	250p	Solder Type	10C	14 way	80p
10	90p	90p	200p	Angled	180p	230p	285p	40p	14C	18 way	90p
20	145p	125p	240p					50p	100p	20 way	105p
26	175p	150p	300p					100p	175p	26 way	140p
34	200p	160p	360p					200p	225p	34 way	220p
40	220p	180p	550p							40 way	285p
50	235p	200p	800p							50 way	300p
										64 way	370p

### JUMPER LEADS

24" Cable with DIP Headers		14 pin 16 pin 24 pin 40 pin	
1 End	145p	165p	240p
2 Ends	210p	230p	345p
			540p
			Cable with Sockets
No. of Ways	20	26	34
1 End	160p	210p	270p
			300p
			Cable with D Connectors
			24" Single End Male £5.50 Female £8
			36" Double End Male £11 Female £11.50
			36" Male/Female £11.00

### EDGE CONNECTORS

0.1" 0.156"	
2 x 18 way	140p
2 x 22 way	200p
2 x 23 way	210p
2 x 25 way	225p
2 x 43 way	280p
2 x 43 way	395p
1 x 77 way	700p
	S-100 £5.00

### EURO CONNECTORS

DIN41612 2 x 32		2 x 32 Angled	
Plug	220p	Socket	280p
			230p
			330p
			250p
			475p
			180p
			170p

## ● ACORN ATOM ●

Built 8K + 2K £135 5K + Coloured Card £175 12K + 12K £180  
(p & p £3/unit)

Atom PSU £7 (p & p 70p) 3A 5V Regulated PSU £24 (p & p £1.50)  
F.P. ROM £20 1K RAM (2 x 2114L) £2 Tool Box Room £25  
NEW COLOUR ENCODER CARD £39.00

Ask for our ATOM list for details on Sound Board and Atom Vision

## PRINTERS

SEIKOSHA GP100A dot matrix printer, full graphics double width characters, up to 10" wide paper, self testing parallel interface  
£189 + Carriage £6

EPSON MX80 Friction and Tractor, 9 x 9 matrix 80 CPS bi-directional with logic seeking, variety of charac.

MX80 F/T 1 £350 + £6 carr. MX 80 F/T 2 with High Res Graphics £360 + £6

BMC 12" Green Screen Monitor £100 + £6 carr.

## BBC COMPUTER UPGRADE

### MEMORY

IC61-68 16K RAM 100nS AP3 £25.60

### PRINTER & USER PORTS

IC69, 70, PL9, 10 £8.50 SK10 with 36" Cable £2.20

36" Printer Connector Lead Complete £13.50

SK9 with 36" Cable £3.30

### ANALOGUE PORT

IC73, SK6 £6.80 PL6 £1.60 PL6 + Hood with 36" Cable £5.00

### F.D. PORT

IC77-87 + PL8 £44 SK8 with 36" Cable £3.50

### BUS PORT

IC71-72 + PL11 £3.30 SK11 with 36" Cable £3.50

### TUBE PORT

PL12 £3.00 SK12 with 36" Cable £3.90

## SOFTY II EPROM PROGRAMMER

The complete microprocessor development system for both Engineers and Hobbyists. You can develop programs, debug, verify and commit them to EPROMs. Will accept most +5V EPROMs. Can also be used as a ROMULATOR. Full review in September '81 P.E. Built unit complete with PSU and TV lead  
£169

## MENTA

New Z80 Development System. Plugs into TV and cassette recorder. 40 key direct ASSEMBLER/EDITOR, 24 bits of I/O. Ideal for study, micro control and robotics. PSU & TV lead incl.  
£115


TECHNOMATIC TECHNOMATIC TECHNOMATIC



74 SERIES		74LS279		4042		45p	
7400	11p	74259	150p	74LS280	180p	4043	50p
7401	11p	74273	140p	74LS283	40p	4044	50p
7402	12p	74276	110p	74LS284	105p	4045	50p
7403	12p	74278	100p	74LS293	40p	4046	50p
7404	12p	74283	150p	74LS295	90p	4047	50p
7405	15p	74284	175p	74LS297	25	4048	50p
7406	15p	74285	150p	74LS298	90p	4049	24p
7407	20p	74290	175p	74LS299	270p	4050	24p
7408	14p	74291	100p	74LS300	150p	4051	45p
7410	14p	74292	100p	74LS301	150p	4052	80p
7411	18p	74293	100p	74LS302	100p	4053	50p
7412	18p	74294	100p	74LS303	100p	4054	90p
7413	18p	74295	100p	74LS304	150p	4055	90p
7414	28p	74296	100p	74LS305	100p	4056	90p
7416	20p	74297	100p	74LS306	100p	4057	90p
7417	20p	74298	100p	74LS307	100p	4058	90p
7420	15p	74299	100p	74LS308	100p	4059	90p
7421	20p	74300	100p	74LS309	100p	4060	90p
7422	20p	74301	100p	74LS310	100p	4061	90p
7425	24p	74302	100p	74LS311	100p	4062	90p
7426	24p	74303	100p	74LS312	100p	4063	90p
7427	22p	74304	100p	74LS313	100p	4064	90p
7428	22p	74305	100p	74LS314	100p	4065	90p
7429	22p	74306	100p	74LS315	100p	4066	90p
7500	22p	74377	100p	74LS386	100p	4137	90p

LINEAR ICs		CPU's		Z80PIO		81LS98	
ADC0808	900p	LM358P	80p	Z80PIO	280p	81LS98	90p
AN103	200p	LM377	175p	Z80PIO	300p	960	220p
AY10212	600p	LM380	75p	Z80CTC	280p	9637AP	160p
AY11313	680p	LM381AN	180p	Z80DART	300p	ZN425E-8	360p
AY11320	320p	LM382	120p	Z80OACTC	300p	ZN425E-8	360p
AY11500	140p	LM386	90p	Z80ADMA	300p	ZN427E-8	850p
AY31270	825p	LM387	120p	Z80ADMA	300p	ZN428E-8	850p
AY31350	40p	LM389	90p	Z80SIO 0/1/2	300p	CR76545	950p
AY38910	550p	LM391	150p	8802	350p	CR76547	180p
AY39122	650p	LM392N	80p	8809	850p	CR76549	180p
AY5-3600	60p	LM393	100p	8809B	140p	CR76573	180p
AY5-4007D	520p	LM394CH	300p	8809E	150p	CR76575	180p
CA3028	120p	LM747	70p	8809F	150p	CR76577	180p
CA3019	80p	LM711	70p	8809G	150p	CR76579	180p
CA3046	70p	LM725	40p	8809H	150p	CR76581	180p
CA3048	225p	LM733	70p	8809J	150p	CR76583	180p
CA3059	300p	LM741	18p	8809K	150p	CR76585	180p
CA3060	350p	LM747	70p	8809L	150p	CR76587	180p
CA3080E	72p	LM748	35p	8809M	150p	CR76589	180p
CA3086	48p	LM754	70p	8809N	150p	CR76591	180p
CA3089E	200p	LM1014	150p	8809P	150p	CR76593	180p
CA3090A0375p	150p	LM1801	300p	8809Q	150p	CR76595	180p
CA3130E	90p	LM1820	250p	8809R	150p	CR76597	180p
CA3130T	130p	LM1871	450p	8809S	150p	CR76599	180p
CA3131E	90p	LM1872	450p	8809T	150p	CR76601	180p
CA3160E	100p	LM1886	70p	8809U	150p	CR76603	180p
CA3161E	175p	LM1889	350p	8809V	150p	CR76605	180p
CA3162E	450p	LM2917	200p	8809W	150p	CR76607	180p
CA3189E	300p	LM3302	90p	8809X	150p	CR76609	180p
CA3240E	120p	LM3900	50p	8809Y	150p	CR76611	180p
CA3280G	250p	LM3901	50p	8809Z	150p	CR76613	180p
D7002	480p	LM3911	130p	8809AA	150p	CR76615	180p
DA1408.8	200p	LM3914	225p	8809AB	150p	CR76617	180p
HA1366	195p	LM3916	225p	8809AC	150p	CR76619	180p
HA1368	270p	LM3917	225p	8809AD	150p	CR76621	180p
HA1369	270p	LM3918	225p	8809AE	150p	CR76623	180p
ICL7660	200p	LM3919	225p	8809AF	150p	CR76625	180p
ICL8038	300p	LM3920	225p	8809AG	150p	CR76627	180p
ICM7216B	160p	LM3921	225p	8809AH	150p	CR76629	180p
ICM7217	750p	LM3922	225p	8809AJ	150p	CR76631	180p
ICM7555	70p	LM3923	225p	8809AK	150p	CR76633	180p
ICL7611	90p	LM3924	225p	8809AL	150p	CR76635	180p
LC7120	325p	LM3925	225p	8809AM	150p	CR76637	180p
LC7130	325p	LM3926	225p	8809AN	150p	CR76639	180p
LF347	160p	LM3927	225p	8809AO	150p	CR76641	180p
LF351	48p	LM3928	225p	8809AP	150p	CR76643	180p
LF343	100p	LM3929	225p	8809AQ	150p	CR76645	180p
LF356P	90p	LM3930	225p	8809AR	150p	CR76647	180p
LF357	120p	LM3931	225p	8809AS	150p	CR76649	180p
LM13331	50p	LM3932	225p	8809AT	150p	CR76651	180p
LM103	425p	LM3933	225p	8809AU	150p	CR76653	180p
LM301A	27p	LM3934	225p	8809AV	150p	CR76655	180p
LM310	120p	LM3935	225p	8809AW	150p	CR76657	180p
LM311	75p						

# TECH TIPS

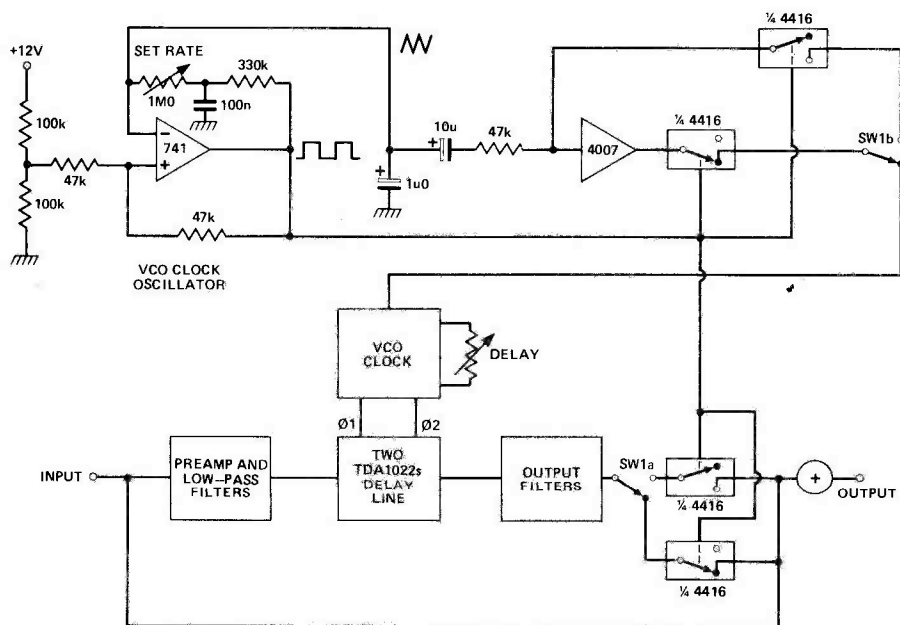

## CMOS Phaser

S.P. Giles, Edmonton

This is an extension of the usual op-amp phaser, which uses CMOS inverters instead. IC1a amplifies the input signal to compensate for some of the loss in gain through the four-stage allpass network formed by IC1b-1f and IC2a-2c. The resistance of the four resistors marked  $R_x$  is altered by the enhancement FETs in IC3 and the changing voltage applied to their gates by slow oscillator IC2d,e as in the ETI audio phaser.

To set up, adjust RV2 for approximately the same level as at X, then adjust PR2 until the familiar phasing sound is heard with a smooth sweep. RV2 can then be adjusted for the best effect. These adjustments should be made with RV1 at a minimum; this is a feedback control which gives a deeper phasing effect. PR1 should be adjusted so that with RV1 full on, the feedback whistle just disappears.

## Guitar Harmoniser

S.P. Giles, Edmonton

This is one for guitarists who cannot afford commercial units which cost at least £1000 at the moment. Constructors who have built the CCD phaser will be familiar with the pitch-changing effect when it is set up in the vibrato mode, and must have noticed that the longer the delay, the greater the pitch change above and below the frequency of the input.

All that this circuit does is to silence the output for one half of the clock modulation oscillator's cycle. This is achieved using a 4416 quad CMOS switch, which is controlled by the square wave output of the clock modulation oscillator. This IC differs from the 4016 in that two switches will be on and two will be off even when the same control signal is applied to each switch. Depending on which way SW1 is connected, either the raised or the lowered frequency of the input will appear at the output, which can be

adjusted by the rate control or by altering the delay of the TDA1022s.

There are many circuits available for TDA1022 clocks and filters so I have not bothered to include them here. Constructors must remember that there will be a slight tremulant effect as the signal in harmony with the input will only be present for the time that the clock modulation oscillator is high or low.

## Mains Remote Speaker


G.M. Perry, West Kilbride


I have used the idea you recently published as the 'Ear-stretcher' com-

munication system to produce an extension speaker. The receiver unit (slightly modified) has been built into a small speaker/cabinet unit, while the transmitter is connected to the hi-fi via a 20 dB amp and mixer. (This combines the stereo channels into a mono signal). The result is a portable speaker

which can be plugged into any mains socket in the neighbourhood and produce an acceptable audio quality from the hi-fi system. In three weeks I've been asked to build four units!

The modifications are as follows. The receiver is built as in the Ear-stretcher except for the following; the mains input is switched and RV1 is a 220k log pot (not a switched pot); the 'mute' is wired off; C13, 14 are 100n; C15 is omitted; C19 is 3n3. In the transmitter, C6, 7, IC3 and RV1 are not used and the circuit shown here is used to provide the signal input (instead of the microphone unit). This is a mixer with a high impedance input followed by a 20 dB amp. It is important to connect the positive supply of the mixer amp to the regulated side of the transmitter power supply. Screened cable has been used for all audio connections and an operating frequency of 250 kHz was chosen to minimise mains-borne RFI on Radio 4.

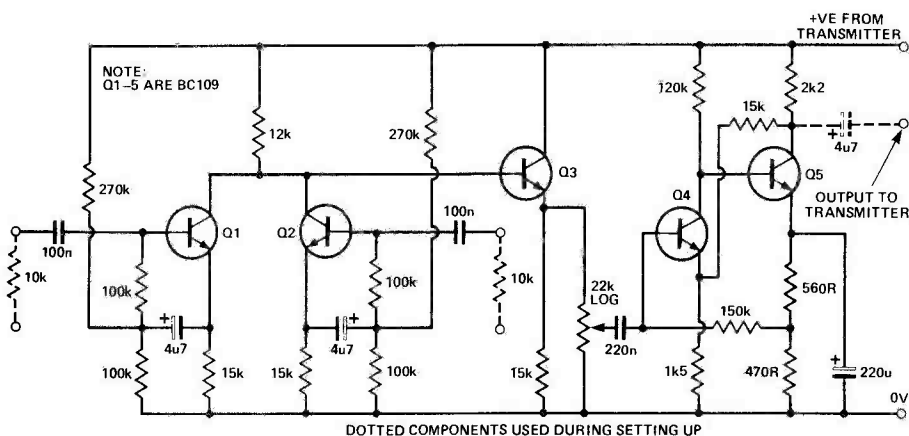

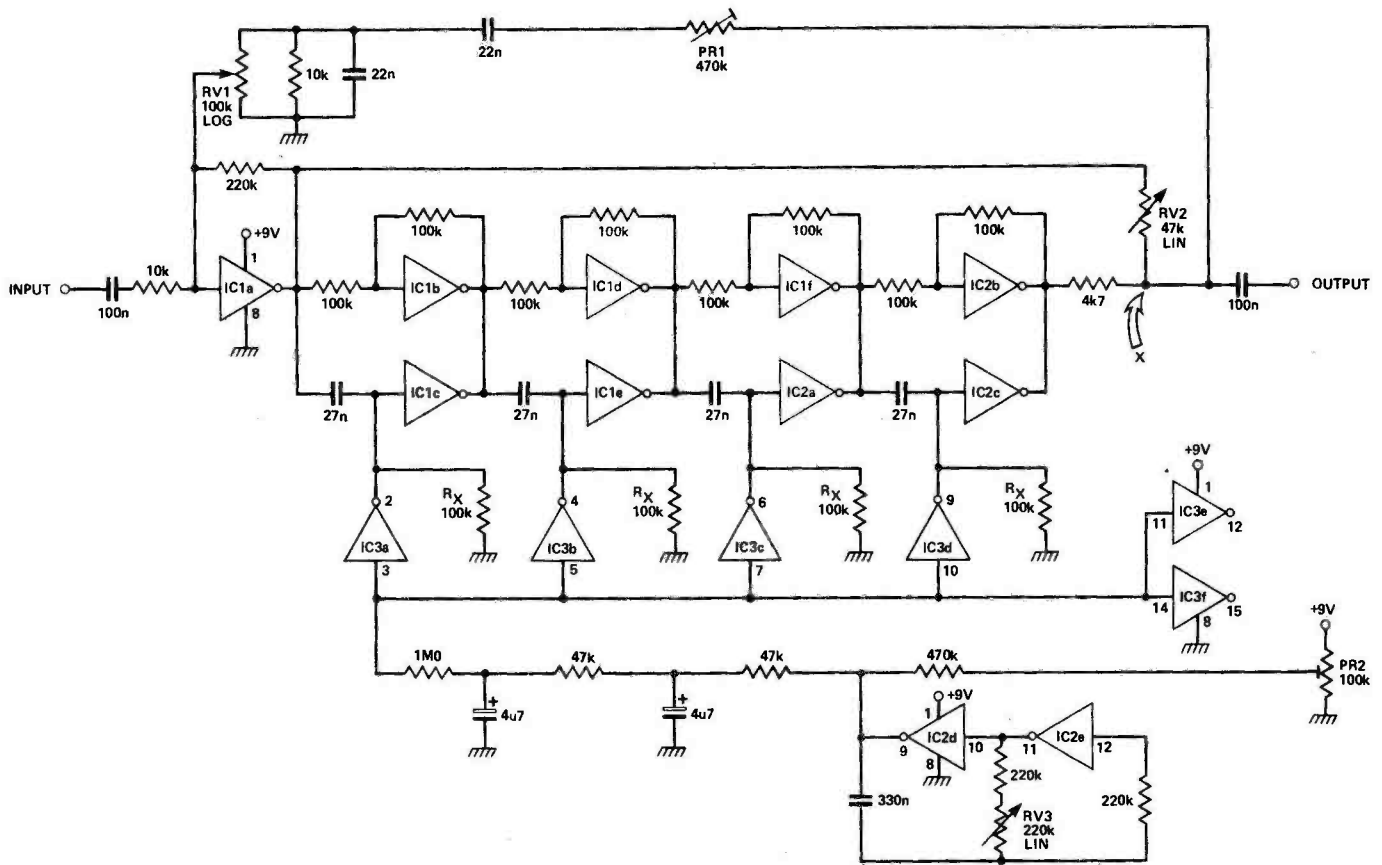

## Number-guessing On The FX-501P

David Kenyon, Knaresborough

I wrote this program for the Casio FX-501P and FX-502P, but it could easily be adapted for other programmables. The object is to guess a three-digit number generated by the calculator. To start the game, press INV P8. The display will show the number 15, which is the number of attempts you have. To make a guess, enter the number followed by EXE. One of two numbers will come up on the display; -1 means the guess was too low, while 2 means the guess was too high. If you succeed in guessing the number the number of attempts you made will be displayed. The numbers in the program marked with an asterisk may be changed to give a different number of attempts.

CODE	LOC	
INV P9		MR 0
INV RAN	1	=
x	2	MIN 3

1	HLT	22
0	LBL 2	23
0	2	24
0	=	25
=	INV PAUSE	26
AC	INV DSZ	27
INV P8	GOTO 5	28
GSB INV P9	LBL 1	29
1*	1	30
5*	+ / -	31
MIN 0	=	32
LBL 5	INV PAUSE	33
HLT	INV DSZ	34
INV X ≥ F	GOTO 5	35
GOTO 3	TOTAL IS 44	
INV X F		
GOTO 2		
GOTO 1		
LBL 3		
0		
=		
INV DSZ		
1*		
5*		
—		
MR 0		
=		
MIN 3		



Tech-Tips is an ideas forum and is not aimed at the beginner. We regret we cannot answer queries on these items. ETI is prepared to consider circuits or ideas submitted by readers for this page. All items used will be paid for at a competitive rate.

Drawings should be as clear as possible and the text should be typed. Text and drawings must be on separate sheets. Circuits must not be subject to copyright. Items for consideration should be sent to ETI TECH-TIPS, Electronics Today International,

145 Charing Cross Road, London WC2H 0EE.

## Intelligent Alarm Switch


S. S. Norman, Sunbury-On-Thames

This simple circuit is built around a TCA965 window discriminator. It is a device which is given a predefined "voltage window" set by RV1 (lower limit) and RV2 (upper limit). The four outputs, which are normally high, indicate whether the input voltage (pin 8) is inside, outside, above or below the "window". Figures 1 and 2 show two possible circuits for normally open or normally closed switches.

The resistors marked \* are mounted inside or fixed with epoxy to the switch to be "defended". RV1 and RV2 are set to form a window around the voltage at point Z. Once set, any attempt to cut the wires to the switch or short the switch out in an attempt to bypass it will pull the voltage at point Z out past the window and the output to the alarm will go high. Needless to say the switch will also activate the alarm in the normal way.

The smaller the window about point Z the more sensitive the circuit becomes. To set up the circuit, measure

Fig. 1

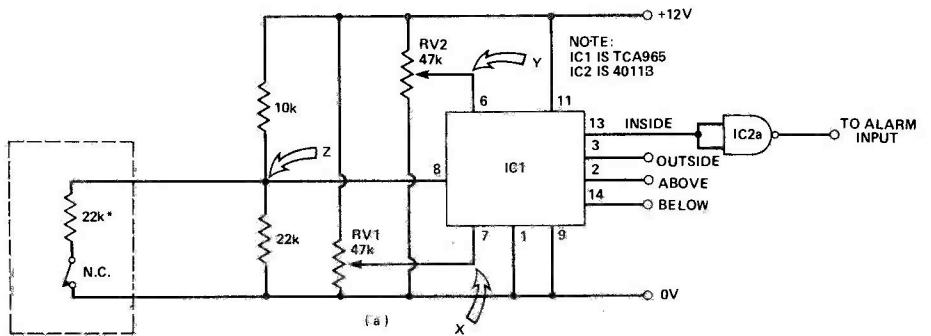

REMOTELY LOCATED ALARM SWITCHES

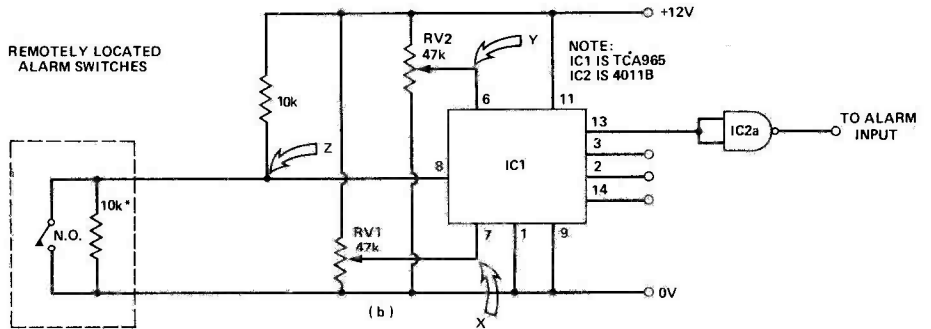


Fig. 2

the voltage at point Z (with the circuit in its standby condition). Then adjust RV1 to set the voltage at point X to be

0V5 lower than point Z. Now adjust RV2 to set voltage at point Y to be 0V5 higher than point Z.


## Current Saving Modifications For The Musical Doorbell

William Leung, Harlow

In the original Musical Doorbell circuit (ETI December '80) IC1 and IC2 can



be replaced by a single CMOS IC. This chip has four NAND Schmitt triggers. The bistable formed around IC1a,b is different from that of the original, in that it requires a negative trigger pulse. This explains why R1 and PB1 are transposed, the presence of IC1c as an inverter, and R4 being connected to the output of IC1a rather than IC1b. Next comes the astable; this is only gated into operation when IC1 pin 8 goes high.

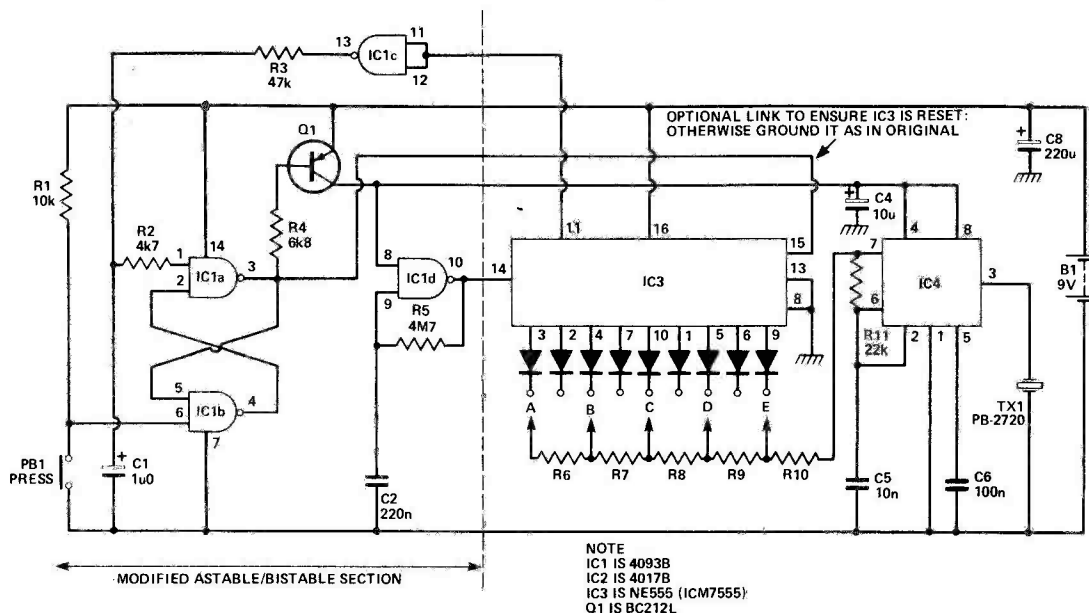One further current-saving modification which I have yet to try out is to replace C7, R13 and the speaker with a piezo-electric transducer (the PB-2720). To go even further, IC4 can be an ICM7555 when using TX1, although it must be stressed that TX1 only has a range between 1 kHz and 7 kHz, so R6-R10 will need some adjustment ie they should be reduced.



NOTE  
IC1 IS 4093B  
IC2 IS 4017B  
IC3 IS NE555 (ICM7555)  
Q1 IS BC212L

# THE CASE FOR

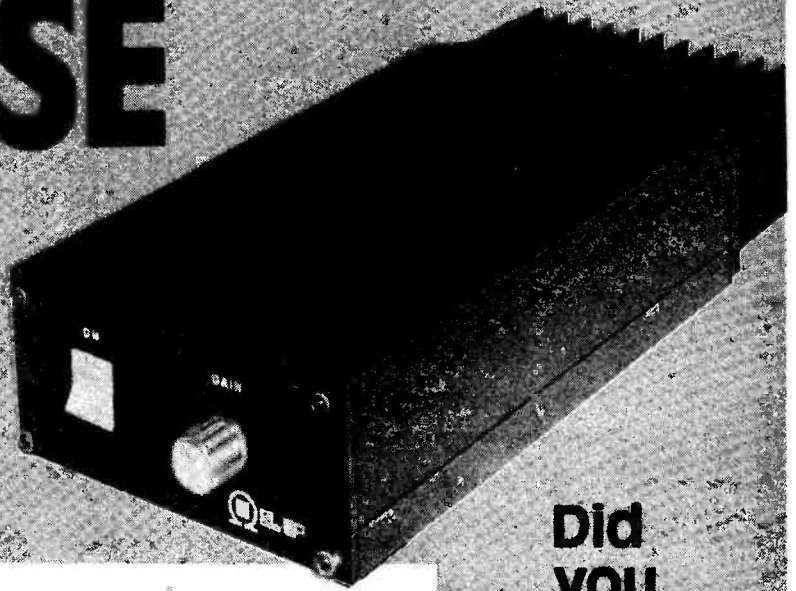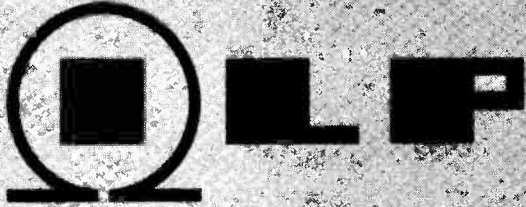

It's the chance  
every constructor wants

Did  
you  
know

I.L.P. are the world's  
largest designers and  
manufacturers of hi-fi audio  
modules?


I.L.P. pioneered encapsulated  
power amps and pre-amps for  
enhanced thermal stability,  
mechanical protection and  
durability?

There are TWENTY power  
amplifiers from 15 to 240 watts  
RMS including the very  
latest super-quality Mosfets to  
choose from?

TWENTY pre-amp modules  
allow you to incorporate  
exciting professional  
applications to your equipment,  
never before available to  
constructors and  
experimenters?

I.L.P. are suppliers to  
the B.B.C., I.B.A., N.A.S.A.,  
British Aerospace, Marconi,  
Racal, Ferranti, G.E.C., Rolls  
Royce etc?

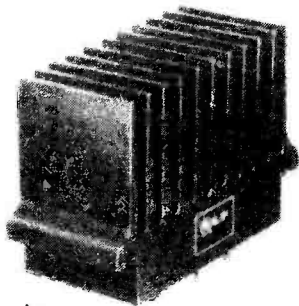Goods are despatched within 7  
days of your order reaching us and  
covered by our 5 year no-quibble  
guarantee?



POWER AMPS

It's something you have always wanted...something to build your equipment into that's smart, modern, strong, adaptable to requirement and not expensive. The 'UniCase' is yet another triumph of I.L.P. design policy. It presents totally professional appearance and finish, ensuring easier and better assembly to make it equal to the most expensive cased equipment. The all-metal 'UniCase' is enhanced by precision aluminium extruded panels engineered for speedy and perfect aligned assembly within a mere five minutes. Designed in the first case to accommodate I.L.P. power amps with P.S.U.'s, the range will shortly be extended to house any other modular projects.

## WHAT WE DO FOR CONSTRUCTORS

Our product range is now so vast we cannot possibly hope to show it all in our advertisements without overcrowding or abridging information to the point of uselessness. So we have devised a solution which we invite you to take advantage of without delay. ALL YOU NEED DO IS FILL IN AND FORWARD THE COUPON BELOW TO RECEIVE OUR NEWEST COMPREHENSIVE I.L.P. CATALOGUE POST FREE BY RETURN. It gives full details of all current I.L.P. products for the constructor together with prices, full technical and assembly details, wiring and circuit diagrams etc. and it's yours, FREE. You don't even have to stamp the envelope if you address it the way we tell you.



P.S.U.'s



PRE-AMP  
MODULES



**FREEPOST 4**  
GRAHAM BELL HOUSE, ROPER CLOSE, CANTERBURY CT2 7EP  
Telephone Sales (0227) 54778 Technical Only (0227) 64723 Telex 965780

**FREEPOST**  
Mark your envelope clearly **FREEPOST 4** and post it **WITHOUT** a stamp to I.L.P. at address above. We pay postage when your letter reaches us.

**SEND COUPON**  
(NO STAMP NECESSARY)  
**FOR YOUR FREE  
I.L.P. CATALOGUE  
AND OPEN UP  
TO A  
NEW WORLD OF  
QUALITY & VALUE**

To: I.L.P. ELECTRONICS LTD.  
PLEASE SEND ME I.L.P. CATALOGUE,  
POST PAID BY RETURN

I HAVE/HAVE NOT PREVIOUSLY  
BUILT WITH I.L.P. MODULES

Name: \_\_\_\_\_  
Address: \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I.L.P. products are available also from Henry's, Marshall's, Technomatic & Watford.

# SECOND GENERATION POWERFET AMPLIFIERS

## NEW DESIGNS

With the introduction of two new boards PANTECHNIC have pushed forward the performance and reliability of their powerfet amplifiers. Four key improvements have been incorporated in these second generation modules —


- 1.) The use of H-PAK powerfets, resulting in improved thermal efficiency and consequently enhanced power output capabilities.
- 2.) Low  $C_{OB}$  drivers now in power transistor packages, maintaining the superb HF performance and improving driver reliability.
- 3.) Separate driver and input supply rails allowing a 10% increase in available output power by increasing output stage efficiency.
- 4.) Bridge mode input pin allowing instant bridging between any two amplifiers without the need for extra circuitry.

## PFA100 Specification


Bandwidth 10Hz-100KHz  $\pm 1dB$   
 Output Power into 8 $\Omega$  100W (Vs =  $\pm 55V$ )  
 THD (20Hz-20KHz) <0.006%  
 THD (1KHz at 100W) 0.004% typ.  
 SNR 120dB  
 Slew rate >30 V/ $\mu$ S  
 Gain  $\times 23$   
 Rin 30K  
 Vs max  $\pm 70V$

Price £18.45

Distortion figures worst case

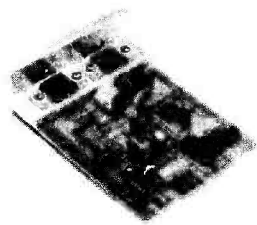

PFA100 120W into 8 $\Omega$

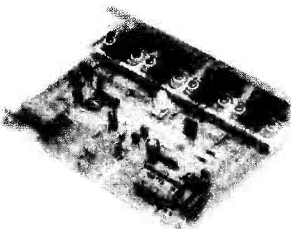

## PFA200 Specification

Bandwidth 10Hz-100KHz  $\pm 1dB$   
 Output power into 8 $\Omega$  150W (Vs =  $\pm 60V$ )  
 THD (20Hz-20KHz) <0.006%  
 THD (1KHz at 150W) 0.002% typ.  
 SNR 120dB  
 Slew rate >30 V/ $\mu$ S  
 Gain  $\times 23$   
 Rin 30K  
 Vs max  $\pm 70V$

Price £25.95

Distortion figures worst case

PFA200 180W into 8 $\Omega$   
 300W into 4 $\Omega$

## POWER SUPPLY COMPONENTS

Toroidal Mains Transformers

Voltage	160VA	225 VA	300 VA	500 VA	625 VA
40-0-40	11-51	13-75	15-59	—	—
45-0-45	—	13-75	15-59	20-45	—
50-0-50	—	—	—	20-45	27-53

Special low flux windings. Carriage + VAT included

25A 400PIV Bridge rectifier	£2.50
10,000 $\mu$ F 80V Electrolytics	4.75
30,000 $\mu$ F 75V Electrolytics	£11.50

Phone or write for advice on selecting the right components for your particular application.

All prices VAT inc. Carriage 75p. Trade lists available.

Ask about our preamps, protection boards and lower and higher power amp modules.

THE POWERFET SPECIALISTS  
**pantechnic**  
 (incorporating J.W. Rimmer)

Mail order only to:  
 Dept ET1/8, 148 Quarry Street, Liverpool L25 6HQ

Telephone: 051 428 8485

Technical enquiries.

367 Green Lanes, London N4 1DY. Tel: 01 800 6667

# ACTIVE COMPONENTS MAIL ORDER SPECIALISTS

Lowest Prices

Fastest Delivery

<b>Device</b>	<b>Price</b>	<b>Device</b>	<b>Price</b>	<b>Device</b>	<b>Price</b>	<b>DIL SOCKETS LOW PROFILE</b>	<b>Price</b>
<b>MEMORIES</b>		280A CPU	3.90	4933	0.38		
2114 Low Power	2.90	280 CTC	2.90	4508	1.90	TIN	—
200ns	0.80	280A CTA	3.10	4512	0.89	8 Pin	0.07
2708 450ns	2.79	280A DART	5.70	4518	0.40	14 Pin	0.09
2718 450ns	2.29	280A DMA	11.95	4520	0.89	16 Pin	0.09
4 + 5V	2.29	280 P10	2.85	4526	0.70	18 Pin	0.13
2716 350ns (+5V)	3.59	280A P10	3.15	4528	0.70	20 Pin	0.14
		280A S10-0	11.99	4541	0.99	22 Pin	0.17
2718 (3 rail)		280A S10-1	11.99	4543	0.99	24 Pin	0.19
450na	5.95	280A S10-2	11.99	4549	0.99	28 Pin	0.25
2732 450ns	3.90	MK3886-4	14.47	<b>74LS SERIES</b>		40 Pin	0.29
2732 350ns	4.40			74LS00	0.10		
2532 450ns	3.90	<b>8000 FAMILY</b>		74LS01	0.11		
4116 200ns	0.70	6800	2.99	74LS02	0.12	<b>LOW PROFILE - GOLD</b>	
4118 150ns	0.94	6802	3.99	74LS03	0.12	8 Pin	0.22
4118 200ns	3.35	6803C	12.10	74LS05	0.12	14 Pin	0.29
4164 200ns	4.05	6809	9.99	74LS09	0.12	16 Pin	0.31
4516/4816 100ns	3.25	6810	1.12	74LS10	0.12	18 Pin	0.33
5516 200ns	8.38	6821	1.25	74LS11	0.12	20 Pin	0.36
6118 200ns	5.18	6840	4.20	74LS12	0.12	22 Pin	0.40
6116 LP 200/150ns	7.81	6845	9.50	74LS13	0.22	24 Pin	0.42
				74LS14	0.37	28 Pin	0.54
				74LS15	0.12	40 Pin	0.81
				74LS16	0.12		
				74LS17	0.12		
				74LS18	0.12		
				74LS148	0.12		

# KITCHEN SCALES PART 2

The final part of this out-of-the-ordinary, state-of-the-art, nifty little gadget describes the construction and calibration procedures. Design and development by Rory Holmes.

Assemble the PCB in the usual fashion, noting the IC orientation, and the polarity of ZD1 and the tantalum capacitors. Also check the BC184L pinouts; these often cause confusion. Twelve Veropins should be inserted at the points marked for external connections. Another point to watch is the hole marked beneath preset PR1; this should be drilled out to 3 mm diameter before mounting the preset, thus allowing its adjustment from either side of the board. Likewise, a 3 mm hole drilled on the other centre allows a secure 6BA mounting bolt for the board.

When complete, the board may be initially tested by inserting all the ICs into their sockets and connecting a 9 V PP7 battery to the supply terminals as indicated. If a scope is available, the

digital sine wave approximation should be observed at the junction of R14 and C6; it could also be checked with a crystal earpiece, when a high pitched tone of 10 kHz should be heard. The reference supply voltage can be measured with a multi-meter across the wire link and a 0 V terminal. It should be in the region of 5 V if all is well, the exact value being unimportant. At this stage the transducer should be built and wired up before further testing of the PCB.

## Winding You Up

The LVDT is wound using 32 swg enamelled copper wire on a piece of 20 mm diameter plastic tubing of the type used for electrical conduit, and available from DIY shops. Any similar piece of tubing will suffice since the dimensions are not critical. Figure 1 shows the winding arrangements. Two separate secondaries are wound either side of the central primary winding. All the windings consist of 100 turns wound in the same direction in flat layers; four layers of 25 turns for each secondary, and two layers for the primary. The accuracy and linearity of the LVDT transducer depends upon the two secondaries being as similar as possible and symmetrically positioned about the primary winding. Care should thus be taken to ensure the layers are evenly wound and tightly packed. Super-glue may be used to retain each layer as it is wound. After completing the windings and finishing with a liberal coat of glue the two secondaries are then wired in series opposition to form one coil by connecting together the end of each winding.

The LVDT should now be wired up to the PCB using screened leads as illustrated on the overlay diagram. On



our prototype assembly we used a four way 'Molex' PCB plug and socket for this connection since the transducer assembly could then be conveniently plugged in.

Figure 2 shows how the LVDT is mounted to measure displacement. As described last month the mechanics of an ordinary pointer scale are utilised to provide the linear displacement with weight via the in-built spring and pivot.

For our prototype we used a small low cost Salter scale which incorporated a ball-race slide mechanism to support the weighing pan. Practically any type of scales could be converted to a digital readout, provided there is room to mount the LVDT and its associated driver electronics.

## Scaling The Heights

Obviously, the more precise the mechanics of the original scale, the greater the degree of accuracy that can finally be achieved with the electronic transducer. The principle is to attach the main coil to a fixed part of the scale while the ferrite core is attached via some rigid element to the weighing pan movement, such that as weight is put on the scale the core moves linearly along its axis into the coil former.

In our prototype the two steel plates of the slide were used to support the transducer as represented in the diagram. Two pieces of PCB material fixed with epoxy act as brackets for the coil former and ferrite core.

The mounting arrangement is not too critical but the following points should be observed. The coil must not be too close to steel or other magnetic material and likewise the ferrite core mounting should be non-magnetic and non-conductive. Remember to allow sufficient leeway on the ferrite mounting

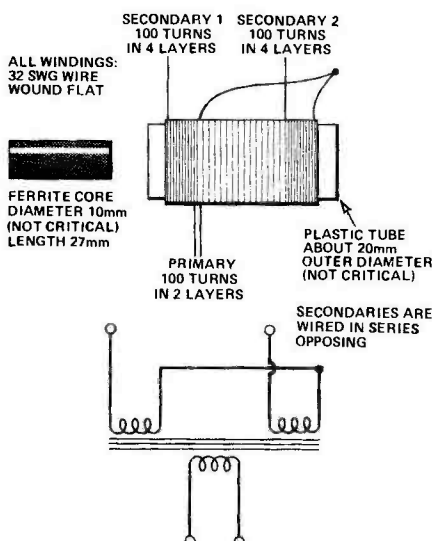


Fig. 1 Coil winding details.


## BUYLINES

The bandgap reference diode ZN423 is available from most semiconductor suppliers as are all the other more familiar semiconductors. Ferrite rods and copper wire can be supplied by Watford Electronics and 10 turn wirewound potentiometers are available from Henry's Radio.

The most expensive item in this project is the very neat LCD panel meter, a state-of-the-art CMOS module available from Verospeed Ltd (known as the DPM200, order ref. 89-25453C).

Suitable mechanical scales are available from most large department stores from about £5 upwards. The type used on our prototype conversion was a small Salter scale with a ball-race slide mechanism (around £6). The PCB Service advert is on page 69.

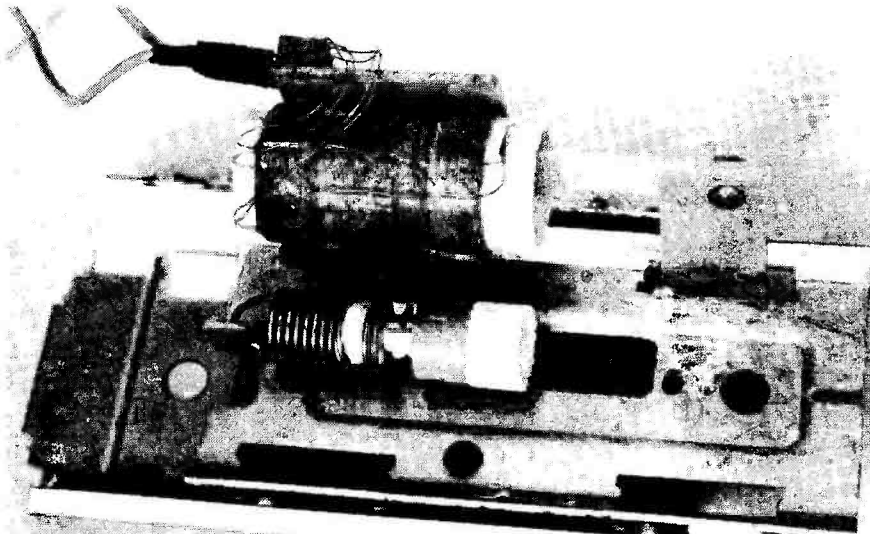Alternatively, for the mechanically ingenious with a bent to experiment, a large selection of springs can be obtained from Proops of Tottenham Court Road for about £1!



The scale mechanics with the LVDT added. Compare with Fig. 2.

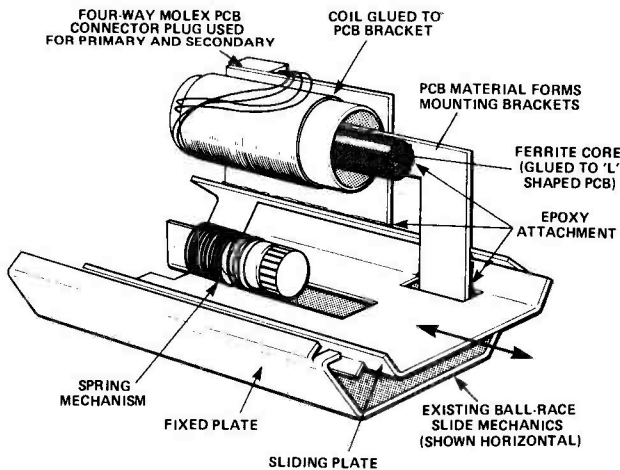


Fig. 2 An artist's impression of the sensor to help with construction.

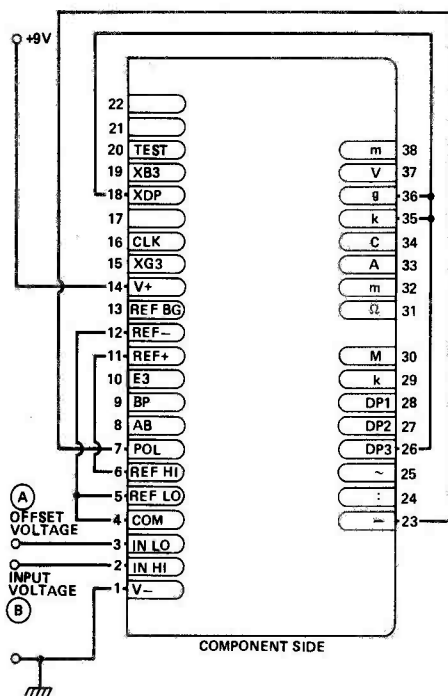


Fig. 3 The (corrected) wiring diagram.

for the full displacement (about 1 cm). The ferrite core must be central in the tube, with the axis of both coil and core parallel to the direction of weight displacement. Sufficient rigidity can be achieved using epoxy glue on the transducer, but initially the ferrite core should only be secured to its bracket with tight rubber bands until the calibration procedure.

Having completed the transducer the entire unit can now be tested by wiring up to the LCD meter-module. Wire up the module according to the connections shown in Fig 3 (this has been reprinted due to an error in last month's diagram).

The input voltage at point B should then be connected to the corresponding point on the PCB; point A temporarily connects to the 2V5 reference terminal. After connecting the DVM supply rails to the 9 V terminals on the PCB, power can be switched on. When the ferrite core is near the middle of the coil the meter should be close to 0 V and will indicate + or - readings as the core is

moved to either side of the null position. The 100 mV sine wave across the primary coil can be observed on a scope along with the other waveforms illustrated last month. If all is well, the electronics can be assembled inside the scale. Figure 5 shows how we arranged the various components to fit into the existing scale box. The back of the case has now become the front to allow room for the LCD display! The 10 turn potentiometer, RV1, should also be connected up at this stage, along with the on/off switch, so completing the interwiring.

## Calibration

Once you are satisfied with your mechanical arrangement for mounting the transducer and associated electronics, the scale should be calibrated using standard or known weights. First, the offset voltage input to the DVM module, marked 'A' on the wiring diagram, should be temporarily connected to the 2V5 reference terminal shown on the PCB overlay. The preset PR1 should be set at roughly half travel, and the scale loaded up with about 1 kg. After switching on the supply, the ferrite core should be adjusted relative to the coil until it's approximately in the middle at the null output position (this corresponds to half scale deflection). As the null position is approached the DVM will accordingly decrease to zero reading. The ferrite core should now be fixed permanently to its mounting plate using epoxy and allowed to set. When set, the DVM reading must be brought exactly to zero by the addition of small increments of weight, sugar or salt being ideal. The known weight, which can be anywhere between 1/2 and 1 kg, should be added to the scale pan, and PR1 adjusted until this weight is shown on the LCD display




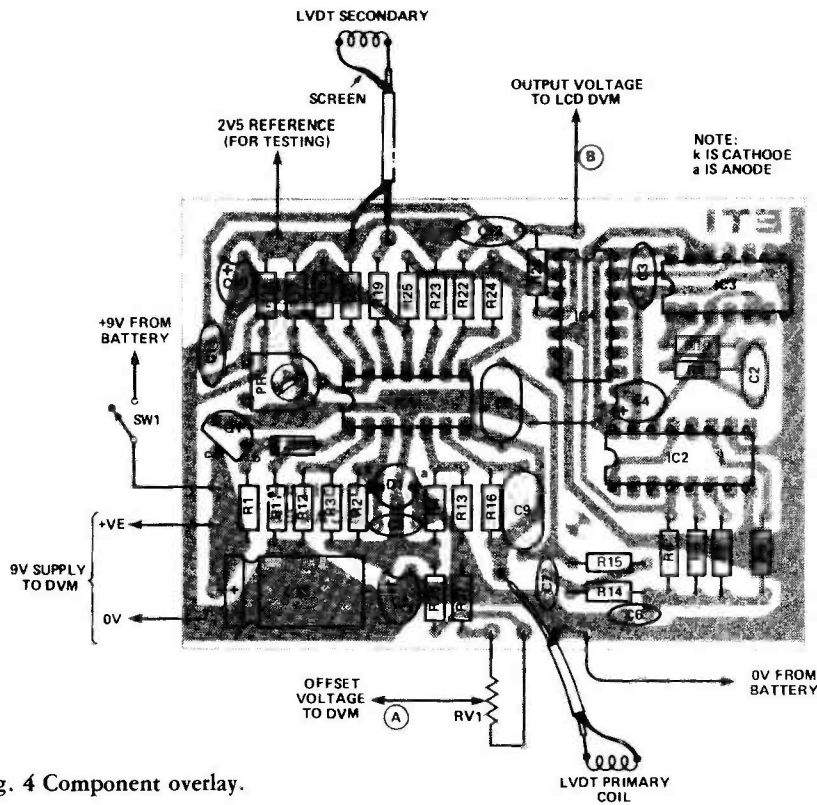


Fig. 4 Component overlay.

(turning PR1 clockwise increases the reading).

Now remove the weight to check that the reading returns to zero, and adjust PR1 accordingly (a few adjustments to PR1 may be necessary to set the correct reading for the known weight).

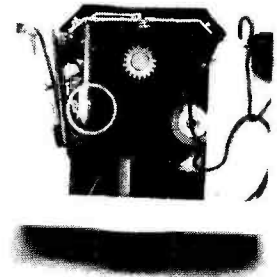Finally, the offset input 'A' can be disconnected from the 2V5 reference and wired to the slider of RV1. Rotating RV1 will alter the reading and the meter can now be easily zeroed for any weight measured, including the empty scale pan. You may now proceed to calibrate the larder.



The mechanics, seen from above.

## PARTS LIST

### Resistors (all 1/4W, 5%)

R1, 11, 13	1k0
R2	2k7
R3	27k
R4,28	100k
R5,8	33k
R6,7,16	22k
R9,12,17,18,19,20,22,24	10k
R10	220k
R14	68k
R15	5k6
R21,25	1k5
R23	4k7
R26,27	270k

### Potentiometers

RV1	47k 10 turn wirewound potentiometer
PR1	470k miniature horizontal preset

### Capacitors


C1,4,10	22u 16V tantalum
C2	220p polystyrene
C3,7	10n ceramic
C5	68n ceramic
C6	2n2 ceramic
C8,9	1n5 polystyrene
C11,12	100n polycarbonate
C13	220u 16V electrolytic

### Semiconductors

IC1	LM324
IC2	4018B
IC3	4093B
IC4	4066B
Q1	BC184L
D1	ZN423
ZD1	2V7 400 mW zener diode
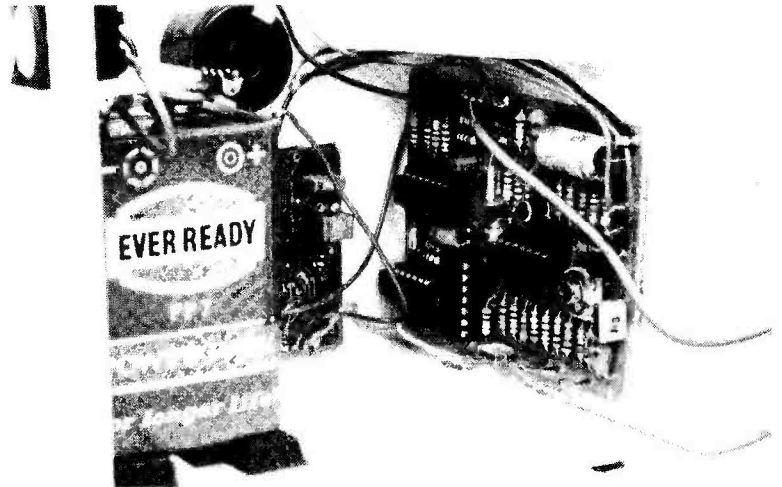
### Miscellaneous

LVDT (see text); PCB (see Buylines); scales (see Buylines); 3 1/2 digit LCD panel meter type DPM 200 (see Buylines)



An internal view showing the arrangement of the boards.

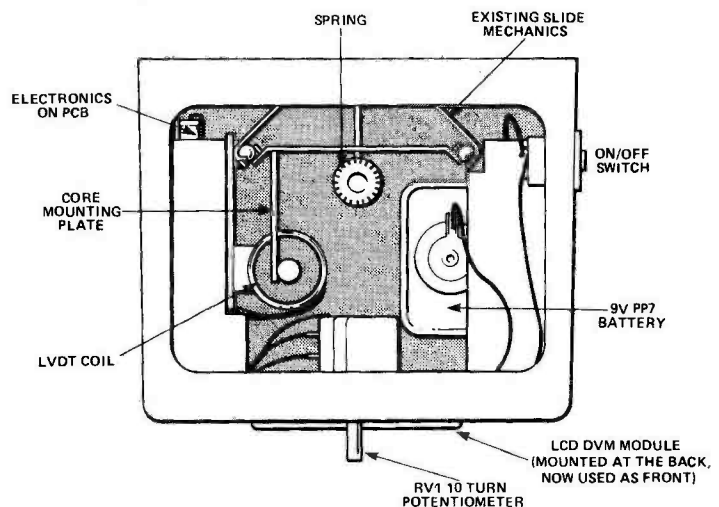


Fig. 5 Artist's impression of the 'view from the top'.

# Greenbank

Greenbank Electronics  
(Dept. T8E) 92 New Chester Rd., New Ferry,  
Wirral, Merseyside L62 5AG  
(Tel. 051 645 3391)



**TERMS, VAT, D.W.O.** Cheques etc payable to Greenbank Electronics and Crossed. **Add VAT to all prices at 15% except where stated otherwise.** Post etc: UK 50p (+8p VAT/58p) per order. Export: NO VAT but add 50p (Eire), £1 (Europe) and £3.50 elsewhere. Access: BarclayCard, Visa, telephoned orders accepted. [Polys, universities, gov't depts, etc can telephone their orders for immediate despatch on account.]

## FREE LEAFLETS

Please write or telephone for leaflets, price lists or quantity prices. A large SAE is not essential but helps us.

# INTERAK 1 COMPUTER SYSTEM

**INTERAK 1 Computer System:** International Size Cards, Rack mounting, 4 MHz Z80, 16K RAM expandable to 48K. Single card VDU suits standard 625 line television sets (VDU special cards "no snow", "no wait" states; character set held in EPROM permits user-defined graphics characters etc - effective resolution 256 x 240 dots). 2K ZYMON 1 monitor in 2716 EPROM £14.95, includes manual with listing. Easy to interface with international size cards from various manufacturers, e.g. "Kermit" EPROM Programmer cards, Dual RS 232 Interface. Relay output (optoisolated). Cards plug into 13 slot ISBUS motherboard (any card in any slot), cost £11.50, suits 19" x 3U rack. Typical bare-board prices: MZB-3 CPU Card £11.50, MKD 2 16K Dynamic RAM card £11.50, VDU/K single board VDU £15.95.

INTERAK 1 is also available in industrial environments e.g. programs can be developed on the complete system, then the "target" system can be constructed on a few cheap cards, using e.g. ROM and RAM cards (mixed 2716 and 2114 devices). In the event of more work being needed on the "target" system, the cards can be brought back to the main INTERAK 1 system and simply plugged into the standard ISBUS.

Note: INTERAK 1 uses no ULA or other "funny" chips; the majority of components used are simple 74LS series gates, buffers, etc., and all popular (i.e. low cost) memories such as 4116, 2114, 2716, etc. Moreover any ASCII encoded keyboard is suitable for input. Programs and data (Kansas City standard) are stored on your unmodified domestic tape cassette recorder; a special feature of ZYMON 1 is that check-sums are embedded throughout the data stream for increased data confidence. We have already sold several thousand boards from this range, which has been established since prehistoric times (1978), i.e. pre-Sinclair, pre-Com, pre-Tangerine etc.

Come to us if you want a system which is sold by people who know and care about the system they offer, rather than by advertising and media-marketing men. We are small, and we hope, friendly company (established 12 years), and we would be happy to tell you more if you were to telephone or arrange to call and see us, or if you prefer, you can write in for a free descriptive leaflet, which includes a price list.

## FEATURED CARD THIS MONTH - VDUK

- \* International Size Card (114 x 204mm)
- \* Fast Z80A CPU runs at full 4MHz
- \* Quartz crystal controlled.
- \* Address and data lines fully buffered (four buffer chips).
- \* Power on reset, and manual reset.
- \* Reset line pulsed to maintain Dynamic RAM data when reset is active.
- \* Z80A Refreshed Dynamic RAMs transparently.
- \* On-board 4-bit address latch included for easy interface to Dynamic RAMs.
- \* On-board "boot" EPROM socket, addressable at any 4K boundary.
- \* Boot EPROM can be disabled under software control.
- \* Power & I/O mp circuit to any 4K boundary.
- \* Epoxy-glass PCB.
- \* Double-sided board, tinned copper tracks.
- \* Gold-plated edge connector on A side.
- \* Needs only single 5V rail (if 5V on-board EPROM is used!)

**DESCRIPTION**  
The MZB-3 is a "Kermit" card which has been selected for use in the INTERAK 1 computer, as it is ideally suited for this purpose.

**Bus Allocations**  
The "Kermit" allocation for the NWAAT line on the card is position A30, and this needs re-routing to position A34 to suit ISBUS-A and INTERAK 1. The CPU card is the heart of a computer system (or perhaps more correctly the "brains"). The Z80A is an ideal choice since it is rapidly becoming the standard 8-bit microprocessor. (This is proved by observing that many 6502 based computers now provide "add-on" Z80A adapters; you never see an add-on 6502 for a Z80A based computer.)

**Crystal Controlled**  
The Z80A is a specially selected fast version of the standard Z80, it is used on this card at its full 4 MHz operating speed. No "Wait" states are included to slow the CPU down, but the NWAAT line on the bus is available for use with slow memories. Note that the

VDU-K and the MKD-2 Dynamic RAM cards do not require any wait states, and so the CPU card in an INTERAK 1 system can operate at its full speed. The "Clock" signal required for the Z80A is not a normal LSTTL level, but is required to swing right up to +5V. At full speed an "active pull-up" is needed to meet this requirement, and is included on the MZB-3 card. A separate clock of the same frequency is output to the bus for those cards which require it.

**Reset**  
A power-on reset circuit is included as standard, so that the system starts to operate in an orderly manner. A push-button switch is provided so that the user can reset the system at any time, without the need to sacrifice the contents of memory by switching the computer off. The reset signal is taken to the bus, so that any other cards which require resetting can be reset at the same time.

**Dynamic RAM**  
As the user can reset the CPU at any time special circuitry is needed, and is included on the card, to ensure that the reset pulse does not occur in the middle of a Dynamic RAM access, and so corrupt any data stored. As Dynamic RAM needs "refreshing" several hundred times a second, and this is carried out by the CPU, it is important that the reset pulse is not maintained for too long a time. The reset circuitry on the MZB-3 card ensures that this requirement is met also.

Although the Z80A has been chosen primarily because it is the best and most well-known microprocessor, a very useful built in feature it possesses, which is not available to the users of say the 6502, is its ability to refresh Dynamic RAM "transparently". More will be said on the subject of refreshing, why it is needed and so on, on the MKD-2 card data sheet, but there are several aspects which are most conveniently covered here.

The built in Z80A refresh is described as "transparent" because it is carried out at a time when the Z80A is not using the bus, and so does not slow the Z80A down in any way. The particular time

used is available after each "op code fetch"; this is when the next instruction of the program has been fetched and is being decoded by the Z80A. Special hardware within the Z80A chip outputs the necessary refresh signal at this time, without the rest of the CPU being involved at all.

A special 4-bit latch has to be added to the CPU circuit, to feed the top four address lines when Dynamic RAMs are being used, and of course this is included on the standard MZB-3 card.

**Buffers**  
Buffers are needed in a computer system to allow each card to drive the bus with sufficient power so that neither computer or data will be damaged to expensive integrated circuits will occur. It becomes doubly important when the CPU is being run at top speed, so that the signals can reach their full voltage levels in the short times available.

Beware of systems where the buffering is omitted simply to give a low price "starter kit", or to cram too much circuitry on the introductory card in the system.

**Power on Jump**  
An important feature of INTERAK 1 is that it has RAM starting at location zero. This is for many technical reasons why this apparent complexity is a good thing, and these are discussed in the various INTERAK 1 leaflets. Suffice it to say that the technique of having RAM at zero solves more problems than it causes. There is in fact very little benefit in starting the minimum address, but an expandable system like INTERAK 1 should have as few limits as possible placed on the future needs of the more advanced user (for example note that the well known disk operating system CP/M will not work correctly if RAM is present from zero upwards).

At power on the RAM at zero will not usually contain any useful program, and it is necessary to force the Z80A to "jump" to get its first instructions from some other address (usually one at which an EPROM is to be found). This address can be set by wire links to any 4K boundary, and the INTERAK 1 system it has been chosen to be E000 (hexadecimal). One of the first tasks of the program at E000 is to disable the power-on jump circuitry.

74LS			
74LS00	11	74LS78	18
74LS01	11	74LS79	18
74LS02	11	74LS80	18
74LS03	12	74LS81	18
74LS04	12	74LS82	18
74LS05	13	74LS83	18
74LS06	12	74LS84	18
74LS07	12	74LS85	18
74LS08	12	74LS86	18
74LS09	12	74LS87	18
74LS10	13	74LS88	18
74LS11	13	74LS89	18
74LS12	13	74LS90	18
74LS13	21	74LS91	18
74LS14	38	74LS92	18
74LS15	13	74LS93	18
74LS16	13	74LS94	18
74LS17	13	74LS95	18
74LS18	13	74LS96	18
74LS19	13	74LS97	18
74LS20	13	74LS98	18
74LS21	13	74LS99	18
74LS22	13	74LS100	18
74LS23	14	74LS101	18
74LS24	14	74LS102	18
74LS25	14	74LS103	18
74LS26	14	74LS104	18
74LS27	13	74LS105	18
74LS28	14	74LS106	18
74LS29	14	74LS107	18
74LS30	13	74LS108	18
74LS31	13	74LS109	18
74LS32	13	74LS110	18
74LS33	15	74LS111	18
74LS34	15	74LS112	18
74LS35	15	74LS113	18
74LS36	15	74LS114	18
74LS37	15	74LS115	18
74LS38	15	74LS116	18
74LS39	15	74LS117	18
74LS40	13	74LS118	18
74LS41	13	74LS119	18
74LS42	32	74LS120	18
74LS43	38	74LS121	18
74LS44	38	74LS122	18
74LS45	40	74LS123	18
74LS46	14	74LS124	18
74LS47	14	74LS125	18
74LS48	14	74LS126	18
74LS219	14	74LS297	18
74LS220</			

# Road Runner®

## WIRING SYSTEM

**SPECIAL INTRODUCTORY OFFER!**



**PROJECT KIT - ONLY £5.40**  
**MORE THAN 25% OFF**  
 Normal Price £7.26

Consists - High density hobby board, wiring pencil, 5 x 6" Glue Strips, 4 coloured enamelled wire bobbins, 1 tinned copper wire bobbin.

**ROADRUNNER IRON**  
**- ONLY £5.00**

**MORE THAN 15% OFF**  
 Normal Price £5.99

Spec - 240V 17W High Temp Iron suitable for soldering enamelled wire.



### ROADRUNNER PRODUCTS IDEAL FOR

- WIRING SIMPLE LOGIC CIRCUITS
- WIRING MICROS & MEMORIES
- WIRING DISCRETE CIRCUITRY
- REPAIRING & MODIFYING PCB's
- USE AS A TRAINING AID

WIRING SYSTEM	£	LOW PROFILE IC SOCKETS	ONE-PIECE GUIDE BLOCKS
EURO INTERKIT	15.99	TINNED CONTACTS	08 CARD FITCH
PROJECT KIT	7.26	8 WAY 9p 14 WAY 12p 16 WAY 14p	JU A 6U/84HP 2 per pack
MINI KIT A	6.58	16 WAY 16p 20 WAY 18p	JU 40HP
MINI KIT B	6.21	22 WAY 21p 24 WAY 22p	JU 20HP
PCB REPAIR KIT	5.41	28 WAY 25p 40 WAY 35p	INDIVIDUAL RAILS
TRAINING KIT	8.95	CARD CONTACTS	DIN 41612 Conn. fang
GEN. GLUE STRIPS 20 PKT	3.10	8 WAY 17p 14 WAY 18p	screws
H.D. GLUE STRIPS 20 PKT	3.29	16 WAY 20p 18 WAY 24p	0.36/20
PHESS STRIPS 20 PKT	2.71	20 WAY 27p 22 WAY 28p	Other accessories available
USE PENCIL	2.99	24 WAY 31p 28 WAY 40p	<b>ROADRUNNER IRONS</b>
TOW PLUGS	2.94	40 WAY 50p	High temp. Iron
EURO BOBBINS 4 PKT	2.12	<b>DIN 41612 CONNECTORS</b>	General Purp. Iron
COPPER COLOUR	2.12	32 way B type Plug	Iron Stand
GREEN COLOUR	2.12	32 way Socket WW Pins	Solder Iron bits, etc.
PINK COLOUR	2.12	32 way Socket Solder tag	Weller iron bits, etc.
MIXED PACK (UP 3)	2.20	64 way C type Plug	Desolder braid etc.
TOW BOBBINS 2 PKT	0.98	64 way Socket WW Pins	Microweavers
HOBBY BOARD S SIDE	1.75	64 way Socket Solder tag	Knife
PROJECT 1 EUROCARD	3.80	96 way also available	Tweezers
S SIDE	4.50	<b>EUROCARD SUBRACKS</b>	Spifface cutter
D SIDE	4.50	Kits of 2 end plates, 2 front & rear	Pin Insertor
DOUBLE EUROCARD	8.60	pins, 4mm screws, and integral hanger	Solder Pins 1100
D SIDE		for DIN 41612 Connectors	22 SWG Xkerson 1kg
<b>HOBBY BOARD CONNECTOR</b>		JU/84HP 19 wide frame	Glue strip adhesive
28 WAY MODULAR TYPE	1.95	JU/84HP 10 wide frame	
WV PINS	1.95	JU/20HP 6 wide frame	
SOLDERTAGS	1.95	JU/84HP 19 wide frame	



## For the man who has everything else...

there is the ETI binder. Spend your nights enjoying the finer things in life, secure in the knowledge that the finer magazines of life are safe and sound. Order one now, and let the Joneses keep up with you.

ETI Binders cost **£4.25 each** for UK residents, including postage, packing and VAT. For overseas orders add 30p. Send the completed coupon together with your remittance to:

**ETI Binders, Argus Specialist Publications Ltd,**  
 513 London Rd., Thornton Heath, Surrey CR4 6AR.  
 Please allow three-four weeks for fulfillment of order.

### USE ROADRUNNER PRODUCTS FOR VERSATILITY, ECONOMY AND PROFESSIONAL RESULTS

TAKE ADVANTAGE OF THIS INTRODUCTORY OFFER TO THE ROADRUNNER WIRING SYSTEM & ORDER NOW

**WHEN ORDERING ASK FOR THE NEW ROADRUNNER CATALOGUE FREE!**

#### GOOD VALUE FROM ROADRUNNER

19" Eurocard Subrack complete **£17.86**  
**ONLY £19.86**  
 Full range of accessories available.

ADD 5% TO NET ORDER VALUE TO COVER CARRIAGE AND PACKAGING. THEN ADD 15% VAT. Please supply requested items.

I enclose cheque/P.O. for £ .....  
 or debit my Barclay Card/Access No. ....

Signature .....

Name (Please print) .....

Address .....

Orders to **ROADRUNNER ELEC. PRODS, 116 BLACKDOWN RURAL INDUSTRIES, HASTE HILL, HASLEMERE, SURREY GU27 3AY (0428 53850)**

#### ORDER FORM

Please send me ..... ETI Binders. I enclose cheque postal order for £ .....

I wish to pay by Access Barclaycard. Please debit my account

5 2 2 4 .....  
 4 9 2 9 .....

Signed

Name

Address

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

RETAIL-MAIL ORDER-EXPORT INDUSTRIAL-EDUCATIONAL

TEST EQUIPMENT CENTRES


CALL IN AND SEE FOR YOURSELF OPEN SIX DAYS A WEEK ALL MODELS ON DISPLAY

## DIGITAL MULTIMETERS

- All models complete with leads and batteries
- Hand Held Models** 3 1/2 digit LCD (UK C/P 65p)
- 601 26 range push button 2A AC/DC Basic 0.5% **£36.50**
  - 2033A Similar to above by Sabtronics **£39.95**
  - 703 As 601 but 0.2% basic **£54.00**
  - 188m/6011A 15 range + Hie tester push button 10A DC **£43.50**
  - 189m 30 range plus Hie tester. Rotary switch 10A AC/DC **£69.95**
  - 2035A 28 range 0.1% basic 2A AC/DC push button (Sabtronics) **£71.00**
  - 2037A As 2035A plus 2-temp. ranges **£77.00**
  - 129 25 range 0.8% basic 10A AC/DC rotary switches (Keithley) **£79.35**
  - 130 As model 129 but 0.5% basic **£102.35**
- Bench Models** 3 1/2 digit LCD unless stated (UK C/P 90p)
- 2010A LED 31 range. 10A AC/DC basic 0.1% (Sabtronics) **£81.50**
  - TM353 LCD 27 range 2A AC/DC basic 0.1% (Sinclair) **£86.25**
  - 2015A LCD 31 range 10A AC/DC basic 0.1% (Sabtronics) **£89.50**
  - TM351 LCD 29 range 10A AC/DC basic 0.1% (Sinclair) **£113.85**
  - 2001 LCD 28 range plus 5 range capacitance meter 10A AC/DC Basic 0.1% (Pantec) **£108.00**
  - 1503A 4 1/2 digit LCD 30 ranges 10A AC/DC 4 MHz counter. 4 KHz osc. 0.05% basic (Thurby) **£171.00**
  - 1503HA As above but 25A and 0.03% basic **£189.75**
- ACCESSORIES**
- AC Adaptors (2010A & 2015A only) **£5.69**
  - Cases TM351/353 **£6.84**
  - 2001 **£7.50** 1503 **£20.45** Touch and hold probe THP20 **£14.95**
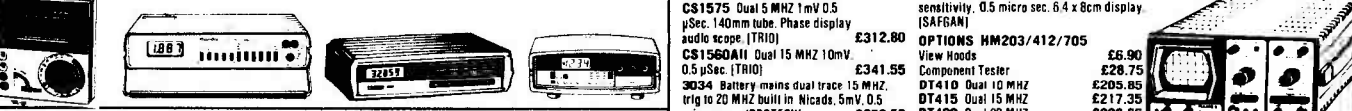
## OSCILLOSCOPES

- (UK C/P Single track £3 ea. Safgan £3 ea. Dual track £4 ea. SC110 £1.00)
- TR10 CS1566A 20 x 20 MHz dual trace triggered sweep 5mV/0.5 **£402.50** (Optional case £21.85)
- HM412-5 Dual 20 MHz delayed sweep trig to 40 MHz. 5mV/0.1 micro sec 8 x 10cm display (HAMEG) **£402.50**
- SC110A New Model 10 MHz battery portable. 10mV/0.1 pSec. 2 trace All facilities (THANDAR) **£171.00** (Options: Carry case **£6.84**, AC Adaptor **£5.69**, Nicads **£8.63**)
- CS1820 Dual 20 MHz 2.5mV/0.1 pSec. Delay sweep. 140mm tube (TRIO) **£483.00**
- CS1577A Dual 35 MHz. 2mV/0.1 pSec. Single sweep facility. 140mm tube (TRIO) **£523.25**
- CS1830H Dual 30 MHz. 2mV/0.2 pSec. (Hited delay line). Delay sweep. 140mm tube (TRIO) **£626.75**
- HM705 Dual 70 MHz delayed sweep. Single sweep. Delay line. Trig to 70 MHz. 2mV/0.1 micro sec. 8 x 10cm display (HAMEG) **£667.00**
- Range of low cost Dual Trace Scopes mains operated. Made in UK to exciting standards. Available as 10 MHz, 15 MHz, or 20 MHz. All feature 5mV sensitivity. 0.5 micro sec. 6.4 x 8cm display. (SAFGAN)
- OPTIONS HM203/412/705**
- View Hoods **£6.90**
  - Component Tester **£28.75**
  - DT410 Dual 10 MHz **£205.85**
  - DT415 Dual 15 MHz **£217.35**
  - DT420 Dual 20 MHz **£228.85**
- Scope probes all models - see below.



## GENERATORS

- R-C Pulse RF Function Audio (UK C/P £1)
- All models 220/240 V AC AUDIO (20 Hz - 200 KHz 4 band. Sine/SQ 0/P) TE220 Max distortion 1% **£69.95**
- LAG27 Max distortion 0.5% (LEADER) new model **£86.25**
- AG202A Max distortion 0.5% (TRIO) **£78.20**
- LAG120A 5 band 10 Hz - 1 MHz. Sine/SQ 0.05-0.8% dist. **£146.00**
- LAG125 As LAG120A but 0.02% dist. (LEADER) **£273.00**
- AG203 10 Hz - 1 MHz 5 band 0.1% Sine/SQ (TRIO) **£126.50**
- RF (All with Int/Ext mod. variable output) TE200 100 KHz - 100 MHz 6 band (300 MHz harm) **£59.95**
- LSG17 As above made by LEADER - new model **£71.30**
- SG402 100 KHz - 30 MHz 6 band (TRIO) **£68.00**
- FUNCTION (All sine/SQ/Triangle/TTL etc.)
- 5020A 1 Hz - 200 KHz (SABTRONICS) **£90.00**
- TS100 1 Hz - 100 KHz (THANDAR) **£90.00**
- TI102 0.2 Hz - 2 MHz (THANDAR) **£166.75**
- PULSE TB105 5 Hz - 5 MHz Various outputs (THANDAR) **£97.75**

## INSULATION AND CLAMP METERS

- Multi-range clamps all with resistance range. Carry case and leads. Also digital and DC clamp in stock. (UK C/P 75p)
- ST300 300A, 6000V AC. 9 ranges. **£25.95**
  - K2606 300A, 6000V AC. 8 ranges. (Optional probe £13.80) **£49.50**
  - K2903 900A, 750V AC. 9 ranges. **£77.50**
- Battery operated complete with carry case. (UK C/P £1)
- YF501L 500V/100 Meg. Plus 0-100 ohm **£65.00**
  - K3103 600V/100 Meg. Plus 0-2.6K ohm **£109.00**
  - K3106 500V & 1000V. 1000 & 2000 Meg. **£119.00**
  - K4110 Earth resistance tester **£149.00**
  - M500 Hand cranked insulation tester 500V/100 Meg. **£79.50**
  - K8031 110V/600V phase tester **£23.50**

## ELECTRONIC INSULATION TESTERS

- Multi-range clamps all with resistance range. Carry case and leads. Also digital and DC clamp in stock. (UK C/P 75p)
- ST300 300A, 6000V AC. 9 ranges. **£25.95**
  - K2606 300A, 6000V AC. 8 ranges. (Optional probe £13.80) **£49.50**
  - K2903 900A, 750V AC. 9 ranges. **£77.50**

## AMATEUR RADIO AND CB TESTING

- (Full lists send S.A.E.)
- KDM6 1.5 to 250 MHz 6 range DIP meter (illus) **£47.95**
  - RC1000 0/10/100/1000 watts SWR etc. 150 MHz max. (illus) **£45.00**
  - CB20 SWR/Power twin meter to 30 MHz. 1KW (illus) **£8.95**
  - HM20 20K/Volt multirange multimeter. Plus SWR/Power meter 150 MHz **£22.95**
  - LPM880 RF Power meter 5/20/120W 1.8 - 500 MHz **£84.00**
  - LPM885 SWR/Power. 20/200/1000W. 1.8 - 54 MHz (illus) **£54.00**

## HAVE A BANANA!

- Low cost reliable meters (All supplied with batts/leads) (UK C/P 55p)
- BANANA 15 range pocket 20K/Volt plus cont. buzzer (illus) **£20.64**
  - KRT101 10 range pocket 1K/Volt **£4.85**
  - T10L 12 range 1K/Volt + overload **£5.75**
  - NH55 10 range pocket 2K/Volt **£6.50**
  - ST5 11 range pocket 4K/Volt **£7.50**
  - NH56R 22 range pocket 20K/Volt **£11.50**
- YN360TR 19 range plus Hie test 20K/Volt **£14.95**
- KRT5001 16 range 10 amp OC range double 50K/Volt **£17.95**
- ST303TR 21 range plus Hie Test 20K/Volt **£18.95**
- TMK500 23 range plus 12A DC plus cont. buzzer 30K/Volt **£24.50**
- 168m 36 range large scale 10A AC/DC 50K/Volt **£28.50**
- 360TR 23 range large scale 10A AC/DC Hie test 50 meg ohm. 1KV AC/DC 100 K/Volt **£39.95**
- Choose from UK's largest range

## TOP QUALITY ANALOGUE MULTIMETERS

- (UK C/P £1.20)
- All featuring AC/DC Volts/Current and Ohms ranges.
- MAJOR 20K 29 range 20K/V. 2 1/2 DC. 12 1/2 AC (PANTEC) **£33.90**
  - MAJOR 50K 29 range 50K/V. 2 1/2 AC. 12 1/2 AC (PANTEC) **£40.25**
  - M1200 30 range 100K/V. 15A AC/DC. 200 Meg. (ROBIN) **£49.95**
  - PAN3001 34 range 40K/V. 5A AC/DC. 50 Meg. (PANTEC) **£59.80**
- Also 500KHz - 500 MHz signal injector and 3 range cap. meter.
- PAN3003 42 range 1 Meg/V. 5A AC/DC. 1 uA. F50 **£66.70**
- (NOTE 3001 & 3003 Electronic Protection Mirror Scales)
- K1400 28 range large scale 20K/Volt. 10A AC/DC. 20 Meg ohm. 5KV AC/DC **£95.00**
  - K200 30 range 10 Meg. ohm input. 25 Hz - 1 MHz **£105.00**

## VARIABLE POWER SUPPLIES

- Mains input - Volts/Amps meter (UK C/P £1)
- PP241 0/12 12/24 Volt. 0/1 amp **£35.00**
  - PP243 0/12 12/24 Volt. 0/3 amp **£59.95**

## 'SCOPE ADD ON UNITS

- LTC905 Semiconductor curve tracer (illus) (LEADER) **£95.45**
- 1 uA. F50 (UK C/P 85p) **£27.95**
- HZ65 Component tester (HAMEG) (UK C/P 85p) **£27.95**

## DIRECT READ HV PROBE

- (UK C/P 65p) 0/40 KV. 20K/Volt **£18.40**

## OSCILLOSCOPE PROBE KITS

- (UK C/P 50p per 1 to 3) BNC plug
- X10 **£7.95**
  - X10 - X10 **£9.45**
  - X100 **£10.50**
  - X100 **£16.95**

## DECADE BOXES

- RSB2 32 value Resr. box. 1 ohm to 4 Meg. **£18.50**
- CSB20 20 Value Cap. box. 470 pF to 1 uF. **£21.00**

## PORTABLE TV COLOUR GENERATOR

- MC101 8 patterns/dots/lines etc. Built in nicads. Pat B UNF only. Complete with charger, case and leads. **£162.50**

## DIRECT READ TEMPERATURE

- TH301 -50 C to -750 C. LCD readout. Complete with battery and thermocouple. **£68.43**

## LOGIC PROBES/MONITOR

- Sabtronics LP10 10 MHz probe **£26.50**
- GSLP2 15 MHz probe **£19.95**
- LEADER LOP076 50 MHz (with case) **£56.90**
- GSLC1M1 monitor (8 to 16 pin IC's) **£33.00**
- GSC DPI Digital pulser. Single/100 pps **£58.50**

# AUDIO ELECTRONICS CUBEGATE LIMITED

301 EDGWARE ROAD, LONDON, W2 1BN, ENGLAND. TEL 01-724 3564 ALSO AT HENRYS RADIO, 404/406 EDGWARE ROAD, LONDON W2

WE ARE OPEN 6 DAYS A WEEK - CALL IN AND SEE FOR YOURSELF!

Order by Post with CHEQUES/ACCESS/VISA or Telephone your order

Allow up to 10 days for delivery (unless advised)

ALL PRICES INCLUDE VAT


FREE CATALOGUE

Send large SAE (20p UK) Schools, Companies, etc. Please write in.
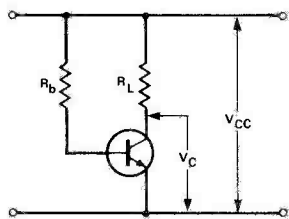
# CONFIGURATIONS

Not ETT's answer to James Burke but a new series aimed at the designer. Ian Sinclair will be looking at some of the basic workaday circuits that often get eclipsed by the more glamorous ICs, showing you how and why they work and how and why to use them. We kick off this month with common-emitter transistor bias.

Configurations is a new series which aims to provide you with fundamental circuit design data for a number of the most commonly used circuit blocks. A very large amount of circuit work concerns these standard arrangements, so that by gathering your pages of Configurations each month, you will be able to build up a complete designer's handbook of circuits and their design data. We're starting this month with the most fundamental of all — biasing and calculating gain and bandwidth of the single-stage common-emitter amplifier, using a silicon transistor with a resistive load.



(a) TO FIND A VALUE FOR  $R_b$ , GIVEN A DESIRED VALUE OF  $V_c$ :

$$R_b = \frac{R_L h_{fe} (V_{CC} - 0.6)}{V_{CC} - V_c}$$

$R_L$  AND  $R_b$  IN KILOHMS

(b) TO FIND WHAT VALUE OF  $V_c$  WILL BE CAUSED BY A GIVEN BIAS RESISTOR:

$$V_c = \frac{V_{CC} R_b - R_L h_{fe} (V_{CC} - 0.6)}{R_b}$$


$R_L$  AND  $R_b$  IN KILOHMS

Fig. 1 Simple single-resistor bias circuit. The value of resistance depends critically on the value of  $h_{fe}$  for the transistor.

The simplest bias circuit, of course, is that of Fig. 1, using a single bias resistor connected between the base and the supply positive. We're not going to spend much time on this one, because it's not a very good bias method from any point of view. The reason is that the resistor value has to be spot on for this method to work, and you have to know the current gain ( $h_{fe}$ ) value for that particular transistor (not just the average for the type) to a fair degree of accuracy. If you need to use that method and have a box of 1% tolerance resistors handy, then the design data is illustrated in Fig. 1. One of the few things that can be said for the circuit is that a high input resistance is attainable, but more on that subject later.
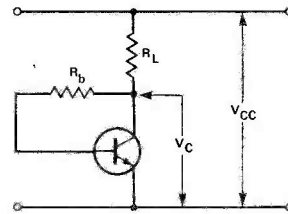
## A Favourable Bias

A much more practical bias method is illustrated in Fig. 2. This makes use of DC shunt feedback between the collector and the base of the transistor, and is less likely to be upset by the changes that occur in the characteristics of the transistor as it heats up. You still have to know the  $h_{fe}$  value for the transistor, but the collector voltage won't be so far out if you just use an average value for the type and it happens that the one you're using is at one end of the range of values. The formula, like the previous one, assumes that the base-to-emitter voltage when the transistor is conducting will be 0V6 and since this is the quantity that changes most as a silicon transistor heats up, it's worth while taking a look at how this bias method is affected.



(a) TO FIND A VALUE FOR  $R_b$ , GIVEN A DESIRED VALUE OF  $V_c$ :

$$R_b = \frac{R_L h_{fe} (V_{CC} - 0.6)}{V_{CC} - V_c}$$

$R_L$  AND  $R_b$  IN KILOHMS

EXAMPLE: IF  $R_L = 2k2$ ,  $h_{fe} = 100$ ,  $V_{CC} = 9V$ ,  $V_c = 3V$ , THEN

$$R_b = \frac{2.2 \times 100 \times 2.4}{6} = 88k$$

(b) TO FIND A VALUE FOR  $V_c$ , GIVEN  $R_b$ :

$$V_c = \frac{R_b V_{CC} + 0.6 R_L h_{fe}}{R_b + R_L h_{fe}}$$

Fig. 2 Shunt-feedback bias. The value of collector voltage is less dependent on the  $h_{fe}$  value. Note the units, with all resistances in kilohms.

Figure 3 shows two calculations of collector voltage, both assuming a supply voltage ( $V_{cc}$ ) of + 9 V, load resistor of 2k2,  $h_{fe}$  value of 100, and bias resistor  $R_b$  of 88k. However, one uses 0V6 as the  $V_{be}$  figure and the other uses 0V5. The difference in the collector voltage is negligible, which points to this method of bias as being a very useful one when you are worried about the effect of temperature changes on the performance of the transistor.

<p>ASSUME IN BOTH CASES THAT <math>R_b = 88k</math>, <math>h_{fe} = 100</math>, <math>V_{CC} = 9V</math>, <math>R_L = 2k2</math>.</p> <p>WHEN <math>V_{be} = 0V6</math>, <math>V_c = \frac{88 \times 9 + 0.6 \times 2.2 \times 100}{88 + 2.2 \times 100} = 3V</math></p> <p>WHEN <math>V_{be} = 0V5</math>, <math>V_c = \frac{88 \times 9 + 0.5 \times 2.2 \times 100}{88 + 2.2 \times 100} = 2V93</math></p> <p>DIFFERENCE IN <math>V_c = 70</math> mV</p>
---

Fig. 3 Effect of temperature. The  $V_{be}$  (assumed 0V6 for a silicon transistor) decreases as the temperature rises. The calculations show that the collector voltage value is hardly affected.

The circuit uses feedback, of course, and unless something is done to remove the feedback of AC, the gain of the stage and its input resistance will be reduced. The reduction in gain isn't serious for most circuits, but the input resistance problem can be more serious — it's detailed later in this article. Both can be tackled if AC is removed from the feedback path by splitting the bias resistor into two parts and decoupling it, as shown in Fig. 4.


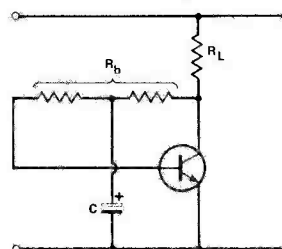


Fig. 4 Removing AC feedback by splitting the bias resistor into two sections and decoupling.
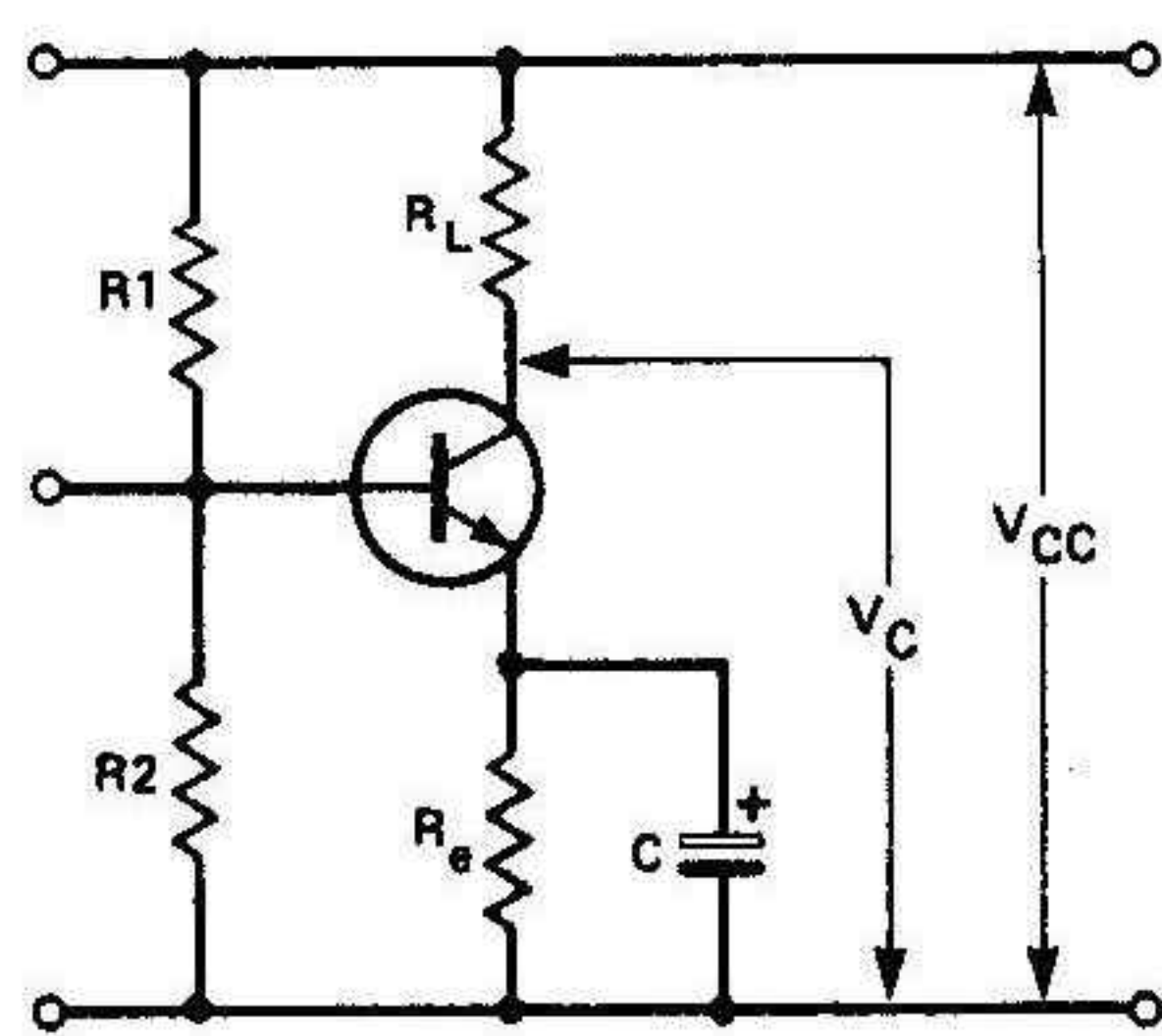
## An Arrangement With Potential

The most-extensively used of all bias methods is our old friend in Fig. 5, which uses a potential divider to provide a constant voltage (we hope) at the base of the transistor, and DC feedback (series feedback this time) through the emitter resistor to stabilise the bias. The notable thing about the formula is that  $h_{fe}$  doesn't appear anywhere in it, so that the bias should not be affected by the value of  $h_{fe}$ . This means that the circuit is very tolerant of wide ranges of  $h_{fe}$  values, providing the base current of the transistor is not so large that it disturbs the base bias voltage set by the potential divider. As a rule of thumb, if the current flowing through R1 and R2 (equal to  $V_{CC}/(R1 + R2)$ ) is something like 100 times the base current of the transistor, then the circuit will work exactly as per design, and any transistor whose base current is within limits can be used with the same bias components. If the base current of the transistor is far from negligible then complications arise, and it's easier just to use lower values of R1 and R2 — but for the effect on input resistance, see later. For voltage amplifier stages where the collector current is only about 1 mA, values like 6k8 and 1k5 on a 9 V supply will suit the circuit very nicely.



(a) TO FIND  $R_e$  FOR A DESIRED  $V_C$ :

$$R_e = \frac{R_L \left( \frac{V_{CC} R_2}{R_1 + R_2} \right) - 0.6}{V_{CC} - V_C}$$

(b) TO FIND  $V_C$  FOR A GIVEN  $R_e$ :

$$V_C = V_{CC} - \frac{R_L \left( \frac{V_{CC} R_2}{R_1 + R_2} \right) - 0.6}{R_e}$$

Fig. 5 The potential-divider bias method. This is particularly useful for mass-produced circuits, because bias does not depend on  $h_{fe}$  values.

## Decoupling Is De Problem

One disadvantage of the circuit is that there's an emitter DC voltage so that the available voltage swing at the collector is correspondingly reduced. The other point, which is important where space is limited, is that decoupling of the emitter resistor is essential. Without decoupling the gain is low; it's given by  $R_L/R_e$  and will be around two to six times for the kind of values you are likely to end up with in a practical circuit. The decoupling capacitor operates at low voltage, so that a 3 V or 6 V type is normally adequate, but its value has to be large to avoid a noticeable loss of gain at low frequencies. It certainly isn't enough to have the reactance of the capacitor equal to the resistance value of  $R_e$  at the lowest frequency for which the amplifier is intended to be used, because if you make this assumption for each coupling and decoupling time constant, you'll end up with practically no gain at that frequency. Aim for a capacitor reactance of about one fifth of the emitter resistance value at the lowest frequency you intend to use and the results will be more acceptable. With C in microfarads and  $R_e$  in kilohms, this means a value given by the equation

$$C = \frac{5000}{2\pi f R_e}$$

and for a 390 ohm emitter resistor, this indicates a capacitor value of around 50uF for a 40 Hz breakpoint. Even at 3 V working, this is going to be a component that will be larger than the resistors or the transistor.

IF  $h_{ie}$  = INPUT RESISTANCE IN KILOHMS,  $I_C$  = STEADY COLLECTOR CURRENT IN MILLIAMPS, AND  $h_{fe}$  = VALUE OF CURRENT GAIN, THEN

$$h_{ie} = \frac{h_{fe}}{40 I_C}$$


EXAMPLE: IF  $h_{fe} = 400$  AND  $I_C = 1\text{mA}$ , THEN  $h_{ie} = \frac{400}{40 \times 1} = 10\text{k}$

Fig. 6 Transistor input resistance,  $h_{ie}$ . Note this is for the transistor only, and assumes zero-signal conditions.
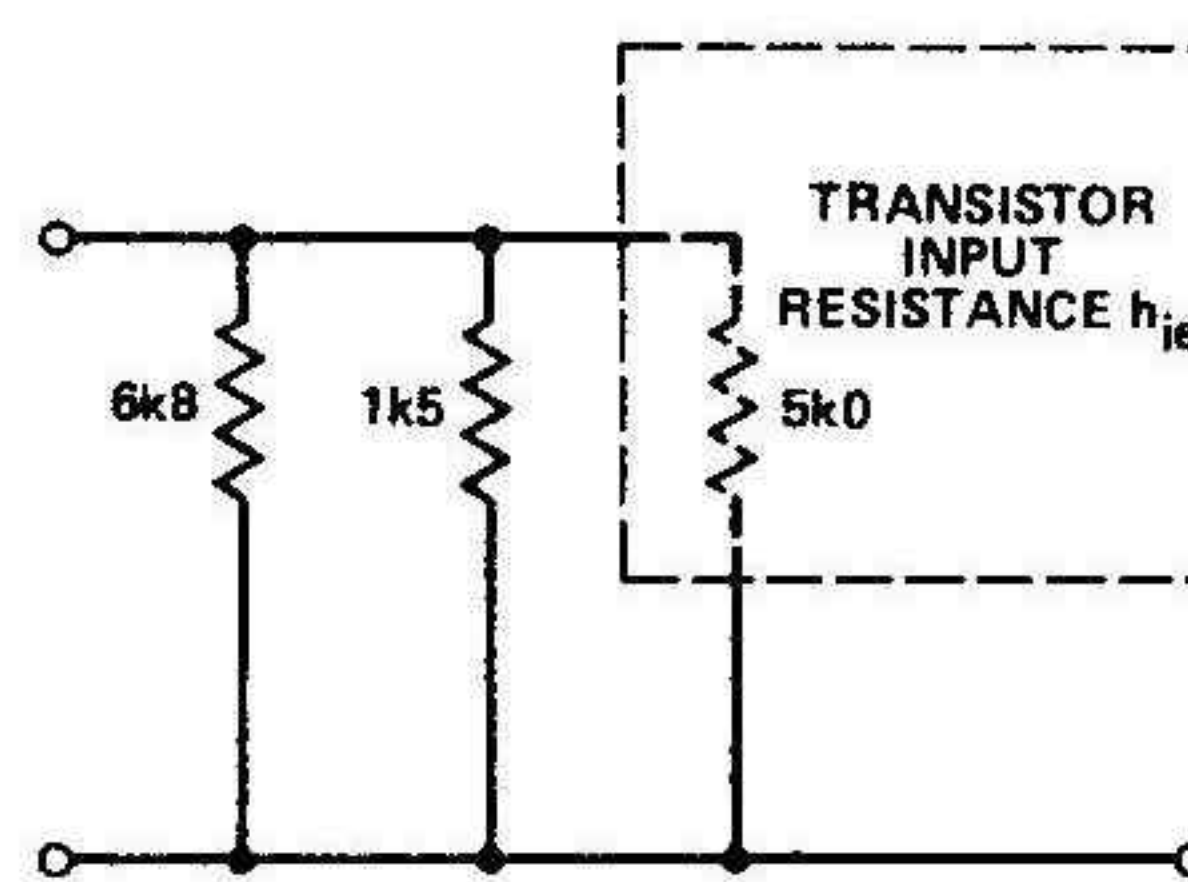
## You Know My Resistance Is Low

The input resistance of an amplifying stage is, as the name suggests, the ratio of input voltage to input current for an AC signal at a frequency in the middle of the bandwidth. The input resistance of a transistor is not constant, but if we take the value which it has at the setting of the bias current, with no signal, then this is a reasonable average to take for small signal inputs — small meaning millivolts. The value is calculated as shown in Fig. 6, and it depends on the  $h_{fe}$  value and the bias current. In general, using transistors with high  $h_{fe}$  values operated at low collector currents will give the highest input resistance values for the transistor, but you can usually assume values in the region of 1k0 to 10k.

These are just input resistance figures for the transistor itself, however, and the total input resistance will be affected by the bias components. When we use the potential divider bias circuit, for example, both R1 and R2 (in Fig. 5) are connected between the base and a line which is at 0 V (AC). How so, you ask? Well, as far as AC voltage is concerned, the supply positive line is as much of an earth as the genuine earth line, since they are connected to each other by a whopping great electrolytic in the power supply circuit. Hence all of these bias resistors are in parallel across the base-to-earth path, considerably lowering the input resistance (Fig. 7). If you think that the shunt feedback circuit of Fig. 2 is better then think again, because the collector end of the bias resistor is connected to a voltage which is in antiphase to (and of much greater amplitude than) the base voltage, so it behaves as if its value were  $R_b/G$  connected to earth. G is the voltage gain of the stage, so that if  $R_b = 88\text{k}$  and  $G = 50$ , then the bias resistor is effectively 1k76 in parallel with the input resistance of the transistor itself.



$1/R_{IN} = 1/5 + 1/1.5 + 1/6.8$  (ALL RESISTANCES IN KILOHMS), SO  $R_{IN} = 0.986\text{k} = 986\Omega$  WHERE  $R_{IN}$  IS TOTAL INPUT RESISTANCE

Fig. 7 The effect of bias components and  $h_{ie}$  on total input resistance.

## Gainful Employment

The output resistance of a single transistor amplifier consists of the output resistance of the transistor itself, usually around 30k, in parallel with the load resistor. Since load resistor values are usually of the order of 1k0 to 10k, this in practice means that we can use the load resistor value as the value for output resistance when we are dealing with resistor-capacitor coupled stages.

The crunch comes when we want to find what the gain of an amplifying stage will be. For a silicon transistor which has enough  $h_{fe}$  to class it as being in the land of the living, the maximum voltage gain is given by  $40 \times V_{RL}$ , where  $V_{RL}$  is the voltage across the load resistor when no signal is applied — the bias voltage in other words across  $R_L$ . For example, if you are using a transistor with 4V5 across the load resistor, then the maximum gain is  $40 \times 4.5$ , which is 180 times (we showed how to derive this figure in 'Gm Revisited', April 79), and that's the value which can be

# FEATURE : Configurations

measured if you use a low impedance signal generator, a very small signal amplitude, and a high-impedance oscilloscope to measure the output.

Practical circuits, however, use higher-resistance devices as signal sources and lower resistance devices as signal loads, so that the gain when we take into account the potential-dividing effect of all these loss-makers is a lot less. For example, if we imagine our transistor stage to be fed with a signal from another stage with an output resistance of 2k2 and feeding into a stage with input resistance of 1k0 (and with these same values itself) then its gain (Fig. 8) will be a miserable 17.5 times. It's not the gain of the transistor which has fallen, notice; it's the attenuation caused by the potential dividers which is dissipating the signal. The moral is that input and output resistances are important when you are aiming for maximum gain, and that everything you can do to raise input resistance and reduce output resistance can be useful.

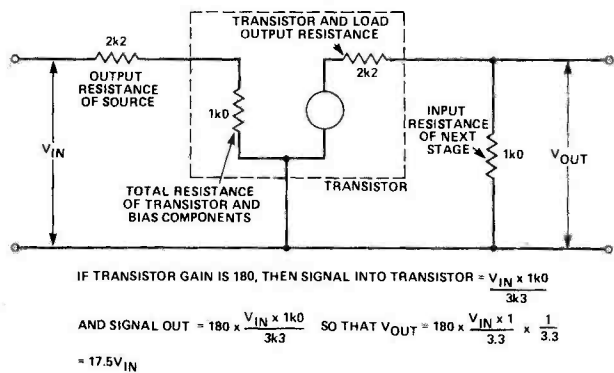


Fig. 8 The effect of input and output resistances in forming potential divider circuits with the internal resistances of source and load.

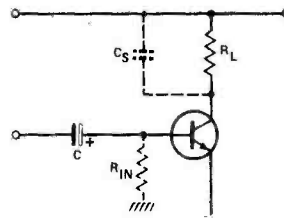


Fig. 9 The time constants which affect bandwidth for a single stage. Note the different units for the two equations.

LOW-FREQUENCY GAIN IS 3dB DOWN ON MIDBAND GAIN WHEN

$$\frac{1000}{2\pi f C_S} = R_{IN} \quad (C_S \text{ IN MICROFARADS, } R_{IN} \text{ IN KILOHMS})$$

OR  $f = \frac{1000}{2\pi C_S R_{IN}} \quad (f \text{ IN HERTZ})$

HIGH-FREQUENCY GAIN IS 3dB DOWN ON MIDBAND GAIN WHEN

$$f = \frac{1000}{2\pi R_L C_S} \quad (C_S \text{ IN PICOFARADS, } R_L \text{ IN KILOHMS, } f \text{ IN MEGAHERTZ})$$

## Strike Up The Bandwidth

The bandwidth of an amplifier stage is defined as the range of frequencies over which the gain does not drop 3 dB below its mid-band value. For a simple amplifier stage, the limits of bandwidth are set by the time constants of the coupling and emitter-decoupling capacitors at the low frequencies, and by the effects of stray capacitance at the high frequencies — Fig. 9 shows the details. Most modern transistors have good high-frequency gain and since stray capacitance can be made small with modern circuit layouts, frequencies into the many megahertz range can be expected. This is much more than is necessary (or desirable) in many cases, and it's a wise precaution to trim the bandwidth for the purpose you need. This can be done by introducing a time constant into the feedback network of a simple filter.

All of which brings us inexorably to the subject of feedback, and that's where we'll start next month, when we'll be looking at feedback pair circuits, their biasing and their gain. **ETI**

# ENFIELD ELECTRONICS

## SPECIAL MONTHLY OFFER No 1

Hand held Micro Cassette Tape Recorder. Compact and handy, this memory device records at two speeds providing up to one hour of recording. Comes complete with mini cassette earphone and carrying pouch.



ONLY £20.70 + 50p p&p

## SPECIAL MONTHLY OFFER No 2

Illustrated is one of a wide range of SWR meters in stock. Other examples are — Model 171 only £16.95 SWR/40A — just £12.95



ONLY £8.95 + 50p p&p

## BELOW IS JUST A SHORT LIST OF OUR TRANSISTORS, 74 SERIES & CMOS 4000 SERIES

TRANSISTORS				74 SERIES				CMOS 4000 SERIES			
AC107 27	BC137 32	BC212B10	BCY71 15	BD233 45	7400 2u	7480 80	7163 90	4000 22	4089 30		
AC122 27	BC138 32	BC213 10	BCY72 15	BD234 45	7401 20	7481 175	7164 100	4001 20	4070 30		
AC125 27	BC139 32	BC213A10	BCX31 17	BD235 45	7402 20	7482 70	7166 100	4002 22	4071 27		
AC126 27	BC140 32	BC213B10	BD106 65	BD236 45	7403 20	7483 68	7167 100	4006 30	4072 27		
AC127 27	BC141 32	BC213C10	BD115 64	BD237 45	7404 20	7484 295	7170 195	4007 26	4075 25		
AC128 27	BC142 32	BC214 10	BD116 82	BD238 45	7405 20	7485 95	7173 120	4008 36	4076 90		
AC141 28	BC143 32	BC214B10	BD121 80	BD239 45	7406 28	7486 28	7174 90	4009 36	4077 40		
AC142 28	BC144 32	BC214C10	BD123 240	BD240 55	7407 48	7487 198	7175 80	4010 45	4078 30		
AC176 28	BC145 12	BC214L10	BD131 45	BD240A55	7408 20	7488 38	7176 85	4011 24	4081 28		
AC187 28	BC149 12	BC237 18	BD132 45	BD241 55	7409 20	7489 75	7177 85	4012 28	4082 30		
AC188 28	BC153 12	BC238B30	BD133 45	BD437 47	7410 28	7492 30	7180 90	4013 40	4085 92		
ACY18 70	BC154 12	BC239C30	BD135 45	BD438 47	7411 25	7493 50	7181 200	4014 92	4093 52		
ACV19 70	BC157 12	BC251 12	BD136 45	BD506 55	7412 22	7494 75	7182 200	4015 96	4099 155		
ACV21 90	BC158 32	BC258B30	BD137 55	BD519 47	7413 40	7495 65	7184 200	4016 39	4100 140		
ACV132 90	BC159 32	BC301 30	BD138 45	BD520 55	7414 80	7496 85	7185 200	4017 82	4106 140		
AD130 100	BC160 32	BC303 30	BD139 45	BD589 100	7416 28	7497 80	7188 500	4018 87	4107 115		
AD143 95	BC161 32	BC307 30	BD140 45	BD648 100	7417 28	7100 310	7190 100	4019 81	40174 95		
AD140 95	BC167B32	BC308 30	BD155 55	BD711 48	7420 20	7104 150	7191 190	4020 96	4160 83		
AD149 105	BC168 12	BC309 10	BD175 75	BD712 48	7425 28	7105 150	7192 95	4021 72	4161 83		
AD161 50	BC169 12	BC317 10	BD178 52	BF115 28	7426 30	7107 48	7193 100	4022 82	4162 83		
AD162 50	BC170 12	BC318 10	BD177 87	BF117L28	7427 25	7109 27	7194 90	4023 25	4163 83		
AF106 50	BC171 12	BC327 10	BD178 68	BF119 100	7428 54	7110 25	7195 90	4024 30	4175 83		
AF114 65	BC172 12	BC328 10	BD179 80	BF121 55	7430 20	7111 60	7196 95	4025 23	4402 83		
AF115 50	BC173 12	BC337 12	BD180 80	BF123 60	7432 28	7116 170	7197 85	4026 152	4412 83		
AF116 65	BC174 12	BC338 12	BD185 75	BF125 55	7433 36	7118 95	7198 145	4027 50	4419 83		
AF126 55	BC177 12	BC384L30	BD186 75	BF127 60	7437 30	7119 340	7199 145	4028 102	4445 83		
AF127 50	BC178 12	BC440 40	BD187 75	BF152 32	7438 30	7121 36	7221 200	4029 140	4446 83		
AF139 52	BC179 12	BC441 32	BD188 75	BF154 15	7440 25	7122 48	7278 95	4038 117	4449 83		
BC107 12	BC181 12	BC461 30	BD189 80	BF153 32	7441 60	7123 60	7428 95	4040 97	4501 83		
BC107B12	BC182L12	BC477 20	BD190 80	BF155 50	7442 80	7126 80	7428 95	4041 115	4502 83		
BC107C12	BC183 10	BC478 20	BD195 80	BF156 40	7443 100	7135 50	7436 64	4042 80	4503 83		
BC108 12	BC183A10	BC479 20	BD196 80	BF157 35	7444 100	7141 60	7439 375	4043 90	4510 90		
BC108A12	BC183B10	BC517 12	BD197 90	BF158 35	7445 90	7143 550	7439 195	4044 95	4511 125		
BC108B12	BC183C10	BC527 12	BD198 90	BF159 35	7446 90	7144 250	75107 120	4045 90	4512 85		
BC108C12	BC184 10	BC537 12	BD199 95	BF160 35	7447 65	7145 65	75108 130	4046 152	4514 205		
BC109 12	BC184B10	BC547 12	BD200 95	BF162 32	7448 65	7147 125	75110 240	4047 112	4515 215		
BC109B12	BC184C10	BC548 12	BD201 85	BF163 32	7449 25	7148 85	75140 180	4048 67	4516 72		
BC109C12	BC184L10	BC549 12	BD202 85	BF165 30	7451 25	7150 120	75141 95	4049 80	4518 95		
BC113 18	BC186 12	BC550 12	BD203 78	BF166 60	7453 50	7151 75	75150 200	4050 47	4526 115		
BC114 18	BC187 20	BC556 12	BD204 90	BF167 60	7454 25	7153 65	75154 186	4051 80	4528 80		
BC115 18	BC204 20	BC557 12	BD205 85	BF173 32	7460 25	7154 100	75182 150	4052 85	4538 85		
BC116 18	BC205 20	BC558 12	BD206 85	BF177 35	7470 32	7155 60	75451 45	4053 75	4539 85		
BC117 18	BC207 20	BC559 12	BD207 95	BF178 32	7472 28	7156 80	75452 45	4054 150	4541 110		
BC118 18	BC208 10	BCY30110	BD208 95	BF179 32	7473 32	7157 70	75453 45	4055 135	4555 68		
BC125 18	BC209 10	BCY31120	BD222 45	BF180 35	7474 30	7160 90	75454 95	4056 145	4561 68		
BC126 32	BC212 10	BCY32120	BD225 45	BF181 35	7475 44	7161 90	75494 110	4066 80	4568 85		
BC136 32	BC212A10	BCY70 15	BD232 45	BF182 35	7476 35	7162 90	76003 220	4068 30	4569 85		

WE ARE OPEN 9 AM - 6 PM MONDAY TO SATURDAY

208 Baker Street · Enfield · Middlesex · 01-366 1873



# QUALITY DOES NOT HAVE TO COST VERY MUCH!

ALL PRICES INCLUDE VAT

## AUDAX HI-FI - SPECIAL PURCHASES

- HD20825H4C 8" Bass mid range Bextrene cone 40/60 watt systems £9.95
- HD24S452C 10" high performance Bass Foam suspension 60/80 watt systems £12.95
- HD13825H4C 5 1/2" bass mid range Bextrene cone 40/60 watt systems Heavy magnet £6.95
- HD13825J Smaller magnet version £5.95
- HIF20JSMC 8" bass mid range foam surround square silver front 30/50 watt system £8.95
- HIF20ESM 8" bass mid range For 30/50 watt systems roll surround treated cone 4 ohm £6.95 8 ohm £7.95
- HIF878SMQ 4" closed back mid range for 30/50 watt systems £5.50
- HD100825HR 1" dome tweeter 4" frame for 60/80 watt systems £5.95

All models for 8 ohms unless stated. (UK Post etc. Speakers 70p, tweeters and mid range 50p)

## TV SOUND FROM YOUR HI-FI (Mk III)


High quality TV sound converter, plugs into aerial socket of your FM tuner 9 volt battery operated (battery not supplied). Nothing to look at... but just listen! Covers all U.K. UHF Channels.

\*Fitted slow-motion drive (Mk III) £11.50

Four button push-button version £14.50 c/p 65p. (UK Post etc 65p) On Demonstration for callers to 301 Edgware Road.
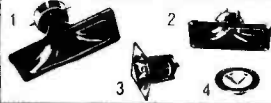
## PIEZO TWEETERS

Clean sound. Very low distortion tweeters. No crossover required. Suitable up to 100 watts - more in series.



- 1 Mid-range horn for hi-fi disc groups
- 2 Tweeter horn for hi-fi disc groups
- 3 Popular hi-fi and disco
- 4 Flat type hi-fi
- 5 Round version of No 3
- 6 Bored free standing hi-fi piezo

- 1025A £6.90
- 1016A £5.45
- 1005A £4.35
- 1026A £3.45
- 1028A £4.25
- 1067A £8.95

On Demonstration to callers

ORDER BY POST (OR PHONE) OR CALL IN

ALL PRICES INCLUDE VAT



Cubegate Limited


# AUDIO ELECTRONICS

301 Edgware Rd. London W2 1BN  
Tel: 01-724 3564

Also at Henrys Radio 404 Edgware Rd. W2

FREE Catalogue send large 20p SAE

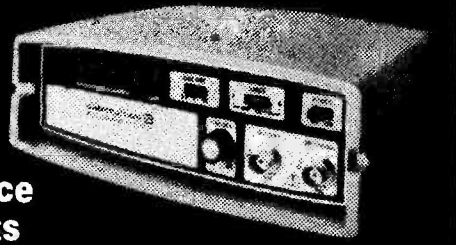An entire range of low-cost high-performance instruments



# sabtronics

'Making Performance Affordable'

- \*2010A 3 1/2-Digit L.E.D. Bench DMM
- \*2015A 3 1/2-Digit L.C.D. Bench DMM
- 2020 3 1/2-Digit L.E.D. Bench DMM with Microcomputer Interface
- 2033 3 1/2-Digit L.C.D. Hand DMM
- \*2035A 3 1/2-Digit L.C.D. Hand DMM
- \*2037A 3 1/2-Digit L.C.D. Hand DMM with Temp.
- LP-10 10MHz Logic Probe
- 5020A 1Hz-200KHz Function Generator
- \*8110A 100MHz 8-Digit Frequency Meter
- \*8610A 600MHz 8-Digit Frequency Meter
- \*8610B 600MHz 9-Digit Frequency Meter
- 8000B 1GHz 9-Digit Frequency Meter
- 8700 10MHz Universal Frequency Counter/Timer
- PSC-65 600MHz Prescaler
- 9005 5MHz Single Trace Oscilloscope

\* Also available in kit form.

Test our low priced test equipment. It measures up to the best. Compare our specs and our prices - no-one can beat our price/performance ratio.

Full colour illustrated brochure and price list from: **BLACK STAR LTD.**, 9a Crown Street, St. Ives, Cambs. PE17 4EB  
Tel: (0480) 62440. Telex 32339



# CLEF ELECTRONIC MUSIC

## ELECTRONIC PIANOS

SPECIALISTS SINCE 1972

Clef Pianos adopt the most advanced form of Touch Sensitive action which simulates piano. Key inertia using a patented electronic technique.

**7 1/2 OCTAVE DOMESTIC MODEL COMPONENT KIT £244 COMPLETE KIT £399.90 MANUFACTURED £675**

Two Domestic Models are available including the 88 note full size version. Four interchangeable Voice Controls may be used to obtain a wide variation of Piano tone, including Harpsichord. Both Soft and Sustain Pedals are incorporated in the Design and internal Effects are provided in the form of Tremolo, Honky Chorus, and Phase Flange.

A power amplifier integrates into the Piano top which may be removed from the Base for easy transportation.

**SIX OCTAVE DOMESTIC MODEL COMPONENT KIT £217 MANUFACTURED £595**

Component Kits include Keyboard, Key switch hardware, and all electronic components and may be purchased in four stages at no extra cost.

Complete Kits further contain Cabinets, wiring harness, Pedals, and in the case of Domestic Models both Power Amplifier and Speaker.

The Six Octave Stage Piano has the same range of Voices and Effects and is designed for use with an External Amplifier and Speaker.

**SIX OCTAVE STAGE MODEL COMPONENT KIT £217 MANUFACTURED £530**




COMPLETE KIT £363.90



COMPLETE KIT £349

## MICROSYNTH

THE COMPACT MUSIC SYNTHESIZER

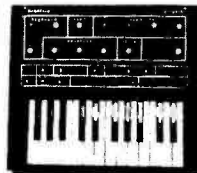

COMPLETE KIT WITH CABINET

- 2 1/2 OCTAVES
- TWO OSCILLATORS
- 2 SUB OCTAVES
- SWITCH ROUTING
- THUMBWHEEL

£118.50

### STRING ENSEMBLE

(As Published in conjunction with 'Practical Electronics')

A very popular Keyboard Synthesizer Kit, for Group or Home use, with a four octave compass and split Keyboard facility.

COMPLETE KIT £179.00

### ROTOR-CHORUS

Comprehensive two speed organ rotor simulator plus a three phase chorus generator.

COMPLETE KIT £89.00

### KEYBOARDS

Our Square Front Keyboards

- 88 NOTE (A-C) £57.00
- 73 NOTE (F-F) £47.00
- FIVE OCTAVE £38.00
- FOUR OCTAVE £28.75

Since 1972 Clef Products have consistently produced leading designs in the field of Electronic Musical Instruments, many of which have been published in technical magazines. With musical quality of paramount importance, new techniques have been evolved and the latest musically valid technology has been incorporated into projects which have been successfully completed by constructors over a wide range of technical capability. Back up TELEPHONE advice is available to all our customers.


PRICES INCLUDE VAT, UK CARRIAGE & INSURANCE (CARRIAGE EXTRA ON MPD PIANOS). Please send S.A.E. for our complete lists, or use our telephone VSA/ACCESS Service. Competitive quotations can be given for EXPORT orders - in Australia please contact JAYCAR in Sydney.

CLEF PRODUCTS (ELECTRONICS) LIMITED  
(Dept ET1) 44A Bramhall Lane South, Bramhall, Stockport, Cheshire SK7 1AH 061 439 3297

## "THE COMPUTER BAND-BOX"

(As Published in conjunction with 'Practical Electronics')

COMPLETE KIT £289 £399 MANFD.

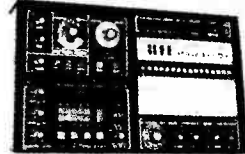

PRICES INCLUDE MASTER RHYTHM

A revolution in the field of Computer Music Generation!

A MUSICIANS INSTRUMENT FOR: SOLOISTS - SINGERS - RECORDING - PRACTICE - LIVE PERFORMANCE - COMPOSITION

The BAND BOX provides an Electronic Backing Trio consisting of Drums, Bass, and a Chord Instrument (one of 16 Waveform Envelope combinations), with the capacity to store over 3,000 User Programmable Chord Changes on more than 120 different Chords. Using advanced Microprocessor technology, Playback of 50,100 Scores can be executed in any Key and at chosen Tempo. Complete Master Pad is electronically indexed and stored on secondary battery back up. Facility exists for composition of Intro, Repeat Chorus, and Coda sections including Multiple Score Sequences. Sockets are provided for Volume Pedal and Footswitch plus separate and mixed instrument Outputs. Total size 19" x 11" x 4 1/2" incorporating Master Rhythm.

## THE Programmable DRUM MACHINE

(As Published in conjunction with 'Practical Electronics')

EIGHT TRACK PROGRAMMING TWENTY-FOUR PATTERNS/TWELVE INSTRUMENTS SEQUENCE OPERATION COMPLETE KIT £79.00 MANFD. £119.00




The Clef Master Rhythm is capable of storing 24 selectable rhythmic drum patterns, invented, modified, and entered by the Operator on to Eight Instrumentation tracks. A three position Instrumentation control expands the number of instruments available to twelve, grouped into sounds typical of playing with Drumsticks, Brushes, or Latin American Bongos and Claves. Sequence operation allows two rhythm sections to be coupled with the second (B) section appearing at four, eight or sixteen bar repetition. All drums can be adjusted for level and resonance on internal controls to suit individual taste, thus producing good musical sounds in a battery driven unit 8 1/2" x 5" x 2 1/2".



# ELECTRONIC IGNITION

Makes a good car better

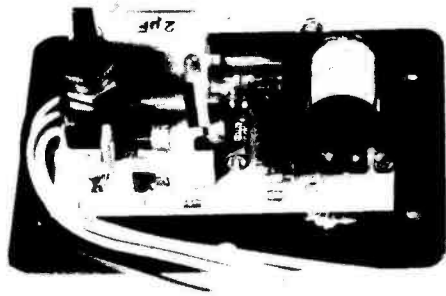

As a  
KIT  
or  
READY  
BUILT

**TOTAL ENERGY DISCHARGE** electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** — no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

## AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue  
and EVERYDAY ELECTRONICS December '81 Issue

**FITS ALL NEGATIVE EARTH VEHICLES,**  
6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**  
Some older current impulse types (Smiths pre '74) require an adaptor —  
PRICE £2.95

**STANDARD CAR KIT £14.85**  
**Assembled and Tested £24.95**

**TWIN OUTPUT KIT £22.95**  
For MOTOR CYCLES and CARS with twin ignition systems  
**Assembled and Tested £34.70**

PLUS  
£1.00  
U.K.  
P. & P.  
Prices  
Include  
VAT.

**DIMENSIONS:** Length 12.5 cm  
Width 8.9 cm  
Height 4.3 cm  
Lead length 100.0 cm

## TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

**SUPER POWER DISCHARGE CIRCUIT** A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

**HIGH EFFICIENCY INVERTER** A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

**PRECISION SPARK TIMING CIRCUIT** This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

## TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ 135 mJ	10 mJ 65 mJ
SPARK DURATION	500 µs	160 µs
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µs	30 µs

TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

## ELECTRONIZE DESIGN



Dept. E, Magnus Road, Wilnecote  
Tamworth, B77 5BY  
Phone: (0827) 281000



# MICROTUTOR PART 1

BASIC, Pascal and the like are OK but if you want to get the most out of your micro then machine code is where it's at. This machine code tutor will help you throw off your chains; you have nothing to lose but your SYNTAX ERRORS. Design and development by Tangerine Computer Systems.

**R**eal computing was able to escape from the lofty realms of the mainframe and into the hands of the layman because of two major developments. The first was when large-scale integration techniques enabled the production of small, versatile microprocessor chips which were adapted into small, relatively low-cost microcomputers. (The microprocessor was originally conceived for use in industrial machine control.) The second was the invention of the BASIC computing language, which allowed the complete beginner to write working computer programs easily and without any knowledge of the system hardware he was working on.

Unfortunately such ease of use can only be obtained by means of a compromise, and the major drawback of the average microcomputer is speed — or rather lack of it. BASIC is painfully slow when compared to the speed of operation of the microprocessor, because each BASIC statement requires a series of machine code subroutines to be executed. Obviously better use can be made of the system hardware if programs are written directly in the language of the microprocessor — machine code. Direct access to the processor means access to swift, versatile and efficient programming.

## All Systems Go

Consequently some of the most popular

micro systems haven't had BASIC as a language at all! Typical products include KIM, SYM, the late lamented MK14 and the AIM 65, still a well-known 6502 machine code development system. And now there's the ET1 Microtutor, a project we're hoping will coax more of our readers away from the security of BASIC and into machine code, the real stuff of microcomputing.

The Microtutor has been designed for us by Tangerine Computer Systems, who were responsible for the highly popular Space Invasion game we published in November 1980. The monitor program for the system is based on TANBUG, as used in the Microtan 65 computer from the same company; this is a remarkably powerful monitor with many useful programming commands available to make machine code easier to manipulate. The hardware is designed around the 6503, a member of the 6502 family with the same instruction set but an address range of only 4K as opposed to the more usual 64K. Thus the microprocessor is more compact

(only 28 pins instead of 40), but any software written for it will also run on the Microtan 65. Furthermore, once you're familiar with the instruction set of the 6500 family you should be able to write machine code programs for home computers based on the 6502 such as the PET, Acorn System 1, Acorn Atom, Superboard, UK101, Apple, VIC and the BBC machine, which should give you plenty of scope! (Indeed, the PET is designed so that the entire system can be reconfigured from software, but you'll have to become pretty good to attempt that!)

## Give Us The Tool

The Microtutor is a very sophisticated and professional-looking piece of equipment. The hex keypad is mounted directly on the PCB, as are the power supply regulator, cassette interface, and a VDU with UHF output on channel 36 for direct connection to a domestic TV set (one up on the AIM 65!). The PCB is incredibly compact and a masterpiece of design, as you can see from the photographs.

The only external equipment required is a battery charger type power supply (supplied with the kit from Tangerine), and a domestic TV and cassette recorder for storing your programs (not supplied with the kit!). In the interests of economy of design and cost, the Microtutor has no




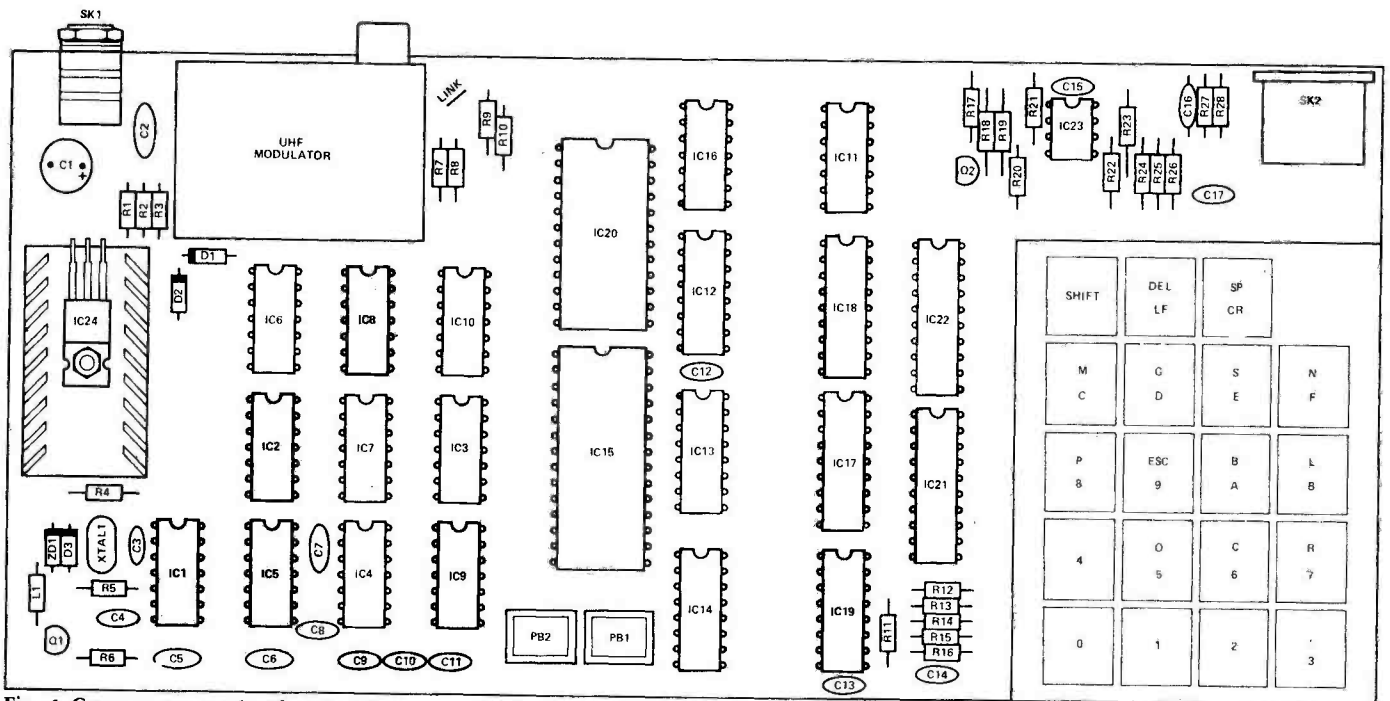


Fig. 1 Component overlay for the Microtutor. Note that all the ICs have pin 1 pointing upwards.

graphics and the ASCII set repeats through the entire range of 256 character codes. Only upper case is available (see Table 1).

Apart from a teaching aid for machine code programming, the Microtutor is also intended to be used for I/O experiments; thus all the bus lines and control signals are brought out to pads on the PCB so that external circuitry can be connected.

The only thing to remember about machine code is that it is very unforgiving of errors. Unlike BASIC, a programming blunder won't produce a polite message on the screen and a chance to try again; more often than not your program and data may be corrupted, or the thing gets locked into an endless loop until it disappears up its own data bus. When developing software for a home computer there is often little choice at this point but to switch off the machine to cure things, causing loss of program and laborious re-entry. We've had some nasty experiences in the office with the PET this way! On the Microtutor things are more civilised; two buttons are

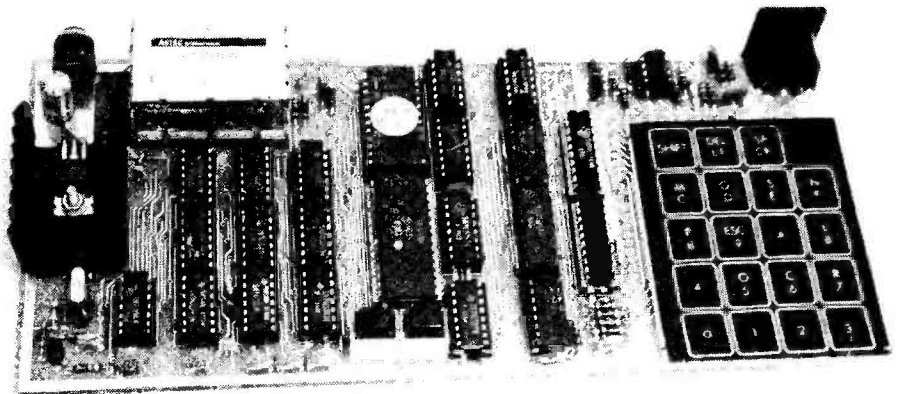

The PCB is very compact and uses thin tracks, so a fine bit is essential on your soldering iron.

## SPECIFICATION

CPU:	6503 (addresses 4K)
ROM:	2K containing monitor program. EPROM is 2716 (5 V version)
RAM:	1K. Used for user program and memory-mapped VDU
I/O:	1K space available
Display:	16 rows by 32 characters, upper case only
UHF Output:	Channel 36

## PARTS LIST

Resistor (all  $\frac{1}{4}$ W, 5%)

R1	75R
R2	470R
R3	220R
R4-17 22 27	1k0
R18, 24	10k
R19, 23	120k
R20, 21	2k2
R25, 26, 28	22k

Capacitors

C1	100u 10 V PCB electrolytic
C2, 5, 6, 9-17	100n ceramic
C3, 8	10n ceramic
C4, 7	100p ceramic

Semiconductors

IC1, 8	74LS04
IC2	74LS73
IC3, 9	74LS393
IC4	74LS21
IC5, 16	74LS74
IC6	74LS08
IC7	74LS11
IC10	74LS00

IC11	74LS32
IC12-14	74LS157
IC15	6503
IC17, 18	2114
IC19	86S64BWF
IC20	2716
IC21	74LS374
IC22	74LS244
IC 23	LM358
IC24	7805
Q1, 2	BC184L
D1-3	1N4148
ZD1	6V8 400mW zener

Miscellaneous

XTAL1	6 MHz crystal
L1	100uH choke
SK1	miniature charger socket (PCB-mounting)
SK2	5-pin DIN socket (PCB-mounting)
PB1, 2	push-buttons (PCB-mounting)
PCB	(see Buylines); hex keypad; UHF modulator type UM1111E36; IC sockets; PCB-mounting heatsink for regulator.

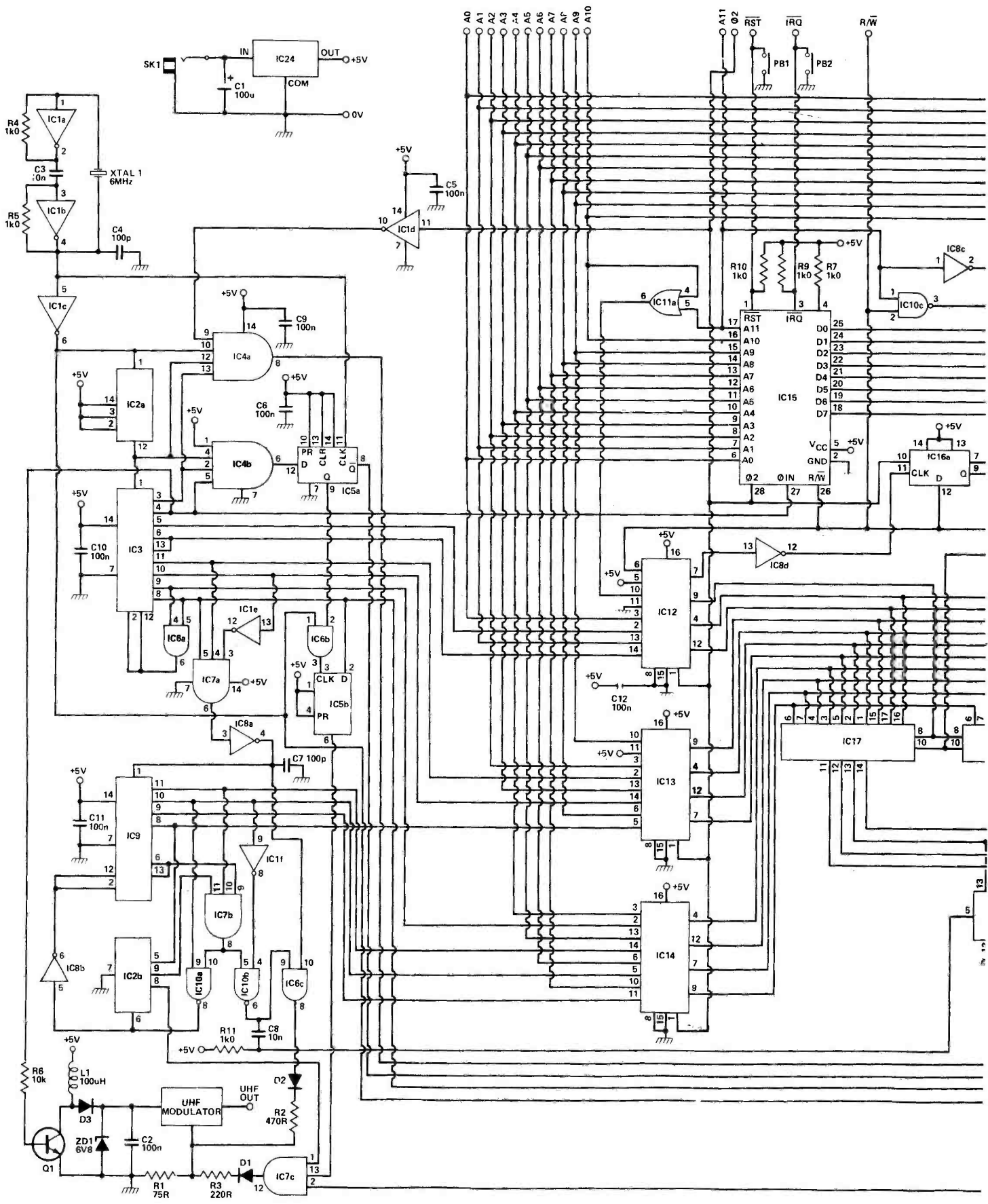


Fig. 2 Complete circuit diagram for the Microtutor.

## BUYLINES

A complete kit of parts for this project, including the power supply, is available from Tangerine Computer Systems, The Science Park, Milton Road, Cambridge CB4 4BH.

## HOW IT WORKS

The CPU (IC15) and the video display share the same memory. Access to the memory is switched at the processor's  $\phi 2$  clock rate (as on the Microtan 65), using the address selector IC12-14. This alternately connects the CPU and CRT address onto the RAM chips IC17, IC18. IC16a is a R/W synchroniser to ensure the RAM chips get proper set-up and hold times on the R/W line after it passes through the address selector IC12.


The master clock oscillator is built around three of the inverters in IC1; XTAL1 sets the operating frequency at 6 MHz. The clock signal enters the counter chain down the left of the circuit diagram at pin 1 of IC2a. IC3 generates all the character addresses along the video line for CRT refresh, with IC4a and IC4b/IC5a generating two of the timing signals required by the character generator IC19. The count length of IC3 is determined by the AND gate IC6a. IC7a generates the line sync pulses while IC5b/IC6b produce the line blanking. The line sync pulses also clock counter IC9, which together with IC2b generates all the line addresses. IC2b, IC7b and the associated logic controls the count length of the line counter and produces the frame sync. IC2b also produces the frame blanking directly.

IC19 is the character generator which receives data from the memory chips IC17, 18 during the time interval that the CRT refresh address is switched through. Data is latched and the character pattern is clocked out under the control of the various input signals to this chip. The character data is mixed with the line and frame blanking in IC7c, while the line sync and frame sync pulses are mixed in the AND gate IC6c to give a composite sync. The output of IC7c is mixed with the composite sync in the diode circuit (D1, D2 and associated resistors) to give an analogue video signal which is fed to the UHF modulator.

The modulator requires a supply of about 6V5. To avoid the need for a separate PSU, this is derived using the DC-DC converter based on L1 and Q1, which is driven via R6 from the CRT counter chain.

IC20 is the 2K EPROM containing the monitor program. For the EPROM to be enabled, A11 must be high and R/W in the read mode; these lines drive NAND gate IC10c which provides the chip select signal to pins 18 and 20 of the EPROM. Gates IC8c, IC6d, IC10d, IC8e and IC11b,c enable the I/O port, controlling the hex keypad and the cassette interface. Any location between 400 and 7FF (Hex) will address the port provided the I/O control line has not been pulled low externally. When reading, IC22 is enabled; when writing, IC21 is enabled. IC23 and associated components form the input amplifier for the cassette interface.

The only expansion the Microtutor has is for I/O experiments; the address bus, data bus, R/W,  $\phi 2$  and I/O control lines all come out to pads on the PCB. If the user builds an external I/O circuit then that circuit must operate the I/O control, which is active low, to disable the keypad circuits, otherwise bus contention will result. The monitor program assumes that they keypad is located at 7FF. Any location in the I/O address space will activate the keypad port if I/O control is not pulled low, however. For further I/O experiments, all eight bits from IC21, 22 are brought out to pads. This means that users can experiment with bigger keypads or utilise the unused bits. RST and IRQ also come out to pads on the PCB.

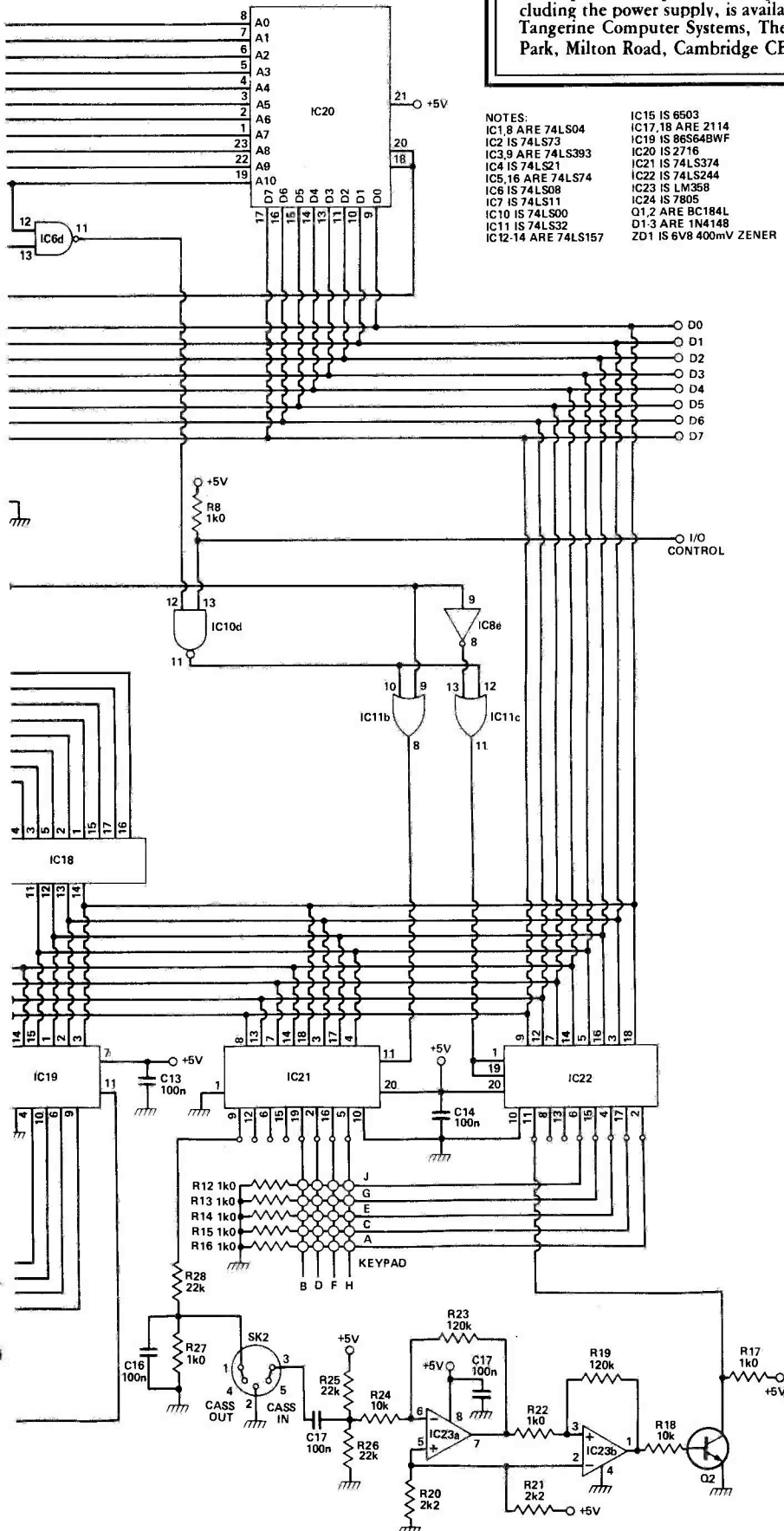

- NOTES:
- |                     |                        |
|---------------------|------------------------|
| IC1,8 ARE 74LS04    | IC15 IS 6503           |
| IC2 IS 74LS73       | IC17,18 ARE 2114       |
| IC3,9 ARE 74LS393   | IC19 IS 86S64BWF       |
| IC4 IS 74LS21       | IC20 IS 2716           |
| IC5,16 ARE 74LS74   | IC21 IS 74LS374        |
| IC6 IS 74LS08       | IC22 IS 74LS244        |
| IC7 IS 74LS11       | IC23 IS LM358          |
| IC10 IS 74LS00      | IC24 IS 7805           |
| IC11 IS 74LS32      | Q1,2 ARE BC184L        |
| IC12-14 ARE 74LS157 | D1-3 ARE 1N4148        |
|                     | ZD1 IS 6V8 400mV ZENER |

provided, reset and interrupt. Both will get you back into the monitor from a faulty program if it gets out of hand, without clearing the memory; interrupt will do so without losing any breakpoints you may have set (breakpoints are explained fully later).

### Construction

The PCB is double-sided but through-hole plated, so components only have to be soldered on the underside. Fit all the low profile components first, ie the link, resistors, diodes and choke, then the keypad. This is stuck to the component side of the board with double-sided sticky pads; insert the connecting wires through the holes in the PCB first, secure the keypad in position with the pads and then solder the connections.

Now you can fit all the IC sockets and capacitors but don't insert the ICs until later. Solder the choke, crystal and transistors in place, then the UHF modulator. The voltage and its heatsink are bolted to the PCB and no insulating washers are required.

Finally mount the two sockets (power and cassette) and the large push-buttons, then insert all of the ICs paying great attention to the device type.

### Ready To Go

Once you've double-checked everything, you're ready to connect the power supply and TV set. The modulator is connected to the TV using UHF coaxial cable with a phono plug at one end and the usual coax plug at the TV end. Switch on the set and tune the TV until you get a steady black-and-white picture — at this point the screen will contain garbage. Press the RESET button and the screen should announce TANBUG. You may now use the keypad, as described below, to enter the wonderful world of machine code.

As an example of the sort of power you've got at your fingertips, here's a direct comparison. Some time ago it was necessary for someone in the office to check all four-digit numbers for certain combinations of digits. A BASIC program on the PET took about five minutes to write and about 15 minutes to run. The same problem, when solved by the Microtutor, took somewhat longer to write the program, but checked through all 10000 numbers in three seconds!

### All About TANBUG

The TANBUG monitor program is located in 2K bytes of read only memory (ROM) at the top of the address space ie pages 8-15. It

contains facilities to enter, modify, run and debug programs. TANBUG will only operate in the memory map of the Microtan system, it is not a general purpose 6502 software package and has been specifically written for Microtan/Microtutor.

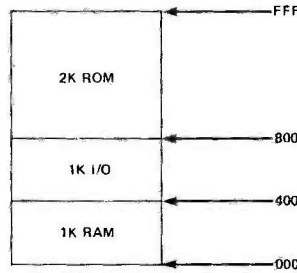


Fig. 3 Memory map.

Locations 200-3FF (pages 2 and 3) are the visual display memory — TANBUG writes to these locations whenever a command is typed to the monitor. Locations in pages 4 to 7 are the addresses of the peripheral attachments, eg keyboard. Locations 100-1FF (page 1) are used as the stack by the microprocessor. Since the stack is of the push-down variety it follows that the whole of this will not be used as stack storage in the majority of programs. TANBUG requires to use locations 1F0-1FF as stack storage (only 16 locations). The rest of this area is free for user programs. Locations 40-FF are also available as user RAM, the preceding locations 0-3F being reserved for use by TANBUG. User programs which do

not use the stack may therefore be loaded anywhere in the area 40-1FF. For user programs which do use the stack, the user must calculate how many stack locations are required and reduce the upper limit accordingly.

The keypad is used as follows, its layout being shown in Fig. 1. TANBUG interrogates the keypad for a depressed key, then translates the matrix encoded signal into an ASCII character which it puts up on the visual display. Because of the limited number of keys it has been necessary to incorporate a shift function on the keypad. So, to obtain the character P for example, the user presses and releases SHIFT, then depresses and releases P. The SHIFT key contains a self-cancelling facility — if the user presses SHIFT twice in succession the pending shift operation is cancelled. So as an example, using the two keys SHIFT and 8 the operations SHIFT P yields P on the display. SHIFT SHIFT P yields 8 on the display. DEL deletes the last character typed. Repeated deletes erase characters back to the beginning of the line.

Having described some of the background to TANBUG it is now possible to describe the commands and syntax of TANBUG, ie how to use it. An example is shown later on. All numerical values of address, data and monitor command arguments are in hexadecimal. The symbol <CR> means on depression of the carriage return key, <SP> the space key, and <LF> line feed. In all examples, text to be typed by the user will be in bold type, while TANBUG responses will not. ■ indicates the cursor.

<ADDR> means a hexadecimal address, <ARG> means hexadecimal data and <TERM> means one of the terminators <CR>, <SP>, or <LF>.

All commands are of the form <COMMAND><TERM>

or <COMMAND><ARG> <TERM> or <COMMAND><ARG>, <ARG><TERM> or <COMMAND><ARG>, <ARG>, <ARG><TERM>

where <COMMAND> is one of the mnemonic commands and <ARG> is a hexadecimal argument applicable to the command. It should be noted at an early stage that the longest argument will contain four hexadecimal characters. If more are typed all but the last four are ignored. As an example consider the memory modify command M12340078 <CR>. In this case location 0078 will be modified or examined as all but the last four characters are ignored.

TABLE 1

Hex	Character	Hex	Character
20	Space	40	@
21	!	41	A
22	"	42	B
23	#	43	C
24	\$	44	D
25	%	45	E
26	&	46	F
27	'	47	G
28	(	48	H
29	)	49	I
2A	*	4A	J
2B	+	4B	K
2C	,	4C	L
2D	-	4D	M
2E	.	4E	N
2F	/	4F	O
30	0	50	P
31	1	51	Q
32	2	52	R
33	3	53	S
34	4	54	T
35	5	55	U
36	6	56	V
37	7	57	W
38	8	58	X
39	9	59	Y
3A	:	5A	Z
3B	;	5B	[
3C	<	5C	\
3D	=	5D	]
3E	>	5E	^
3F	?	5F	_

<TERM> is one of the terminating characters <CR>, <SP>, <LF> or <ESC>. In fact TANBUG accepts any of the "control" characters (HEX code 0-20) as terminator. TANBUG will reply with a ? if an illegal command is encountered.

## Starting The Monitor

Press the reset button on the Microtutor. TANBUG will scroll the display and respond with TANBUG

Note that on initial power-up the top part of the display will be filled with spurious characters. These will disappear as new commands are entered and the display scrolls up. On subsequent resets the previous operations remain displayed to facilitate debugging.

## Memory modify/examine command M

The M command allows the user to enter and modify programs by changing the RAM locations to the desired values. The command also allows the user to inspect ROM locations, modify registers and so on. To open a location type the following

M <ADDR> <TERM>  
TANBUG then replies with the current contents of that location. For example, to examine the contents of RAM location 100 type M100<CR> TANBUG then responds on the display with

M100,0E,■

assuming the current contents of the location were 0E.

There are now several options open to the user. If any terminator is typed the location is closed and not altered and the cursor moves to the next line scrolling up the display by one row. If however, a value is typed followed by one of the terminators <CR>, <LF> or <ESC> the location is modified and then closed. For example, using <CR>

M100,0E,FF

location 100 will now contain FF. If however <SP> is typed, the location is re-opened and unmodified.

M100,0E,FF

M0100,0E,■

This facility is useful if an erroneous value has been typed. The terminators <LF> and <ESC> modify the current location being examined, then open the next and previous locations respectively ie using <LF>

M100,0E,FF

M0101,AB,■

and using <ESC>

M100,0E,

M00FF,56,■

Using <LF> makes for very easy program entry, it only being necessary to type the initial address of the program followed by its data and <LF>, then responding to the cursor prompt for subsequent data words.

Note that locations 1FE and 1FF should not be modified. These are the stack locations which contain the monitor return addresses. If they are corrupted TANBUG will almost certainly "crash" and it will be necessary to issue a reset in order to recover.

## List command L

The list command allows the user to list out sections of memory onto the display. It is possible to display the contents of a maximum of 120 consecutive memory locations simultaneously. To list a series of locations type

L <ADDR>, <NUMBER>  
<TERM>

where <ADDR> is the address of the first location to be printed and <NUMBER> is the number of lines of eight consecutive locations to be printed. TANBUG pauses briefly between each line to allow the user to scan them. For example, to list the first 16 locations of TANBUG (which resides at C00-FFF) type LC00,2<CR>.

The display will then be

LC00,2

C00 A2 FF 9A E8 86 17 20 B7

C08 FF 8D F3 BF A2 0E BD DF

If zero lines are requested (ie <NUMBER> = 0) then 256 lines will be given.

## Go command G

Having entered a program using the M command and verified it using the L command, the user can use the G command to start running his own program. The command is of the format G <ADDR> <TERM>. For example, to start a program whose first instruction is at location 100 type G100<CR>. When the user program is started the cursor disappears. On a return to the monitor it re-appears.

The G command automatically sets up two of the microprocessor's internal registers:

- The program counter (PC) is set to the start address given in the G command.
- The stack pointer (SP) is set to location 1FF.

The contents of the other four internal registers, namely the status word (PSW), index X (IX), index Y (IY) and accumulator (A), are taken from the monitor pseudo registers

(described next). Thus the user can either set up the pseudo registers before typing the G command, or use instructions within his/her program to manipulate them directly.

## Register modify/examine command R

Locations 15 to 1B within the RAM reserved for TANBUG are the user pseudo registers. The user can set these locations prior to issuing a G command; the values are then transferred to the microprocessor's internal registers immediately before the user program is started. The pseudo register locations are also used by the monitor to save the user internal register values when a breakpoint is encountered. These values are then transferred back into the microprocessor when a P command is issued, so that all intents and purposes the user program appears to be uninterrupted.

The R command allows the user to modify these registers in conjunction with the M command. To modify/examine registers, type R <CR> and the following display will appear (location 15 containing 00 say).

TABLE 2

15	Low order byte of program counter (PCL)
16	High order byte of program counter (PCH)
17	Processor status word (PSW)
18	Stack pointer (SP)
19	Index X (IX)
1A	Index Y (IY)
1B	Accumulator (A)

## R

M0015,00,■

Now proceed as for the M command.

Naturally the M command could be used to modify/examine location 15 without using the R command — the R command merely saves the user the need to remember and type in the start location of the pseudo registers. Pseudo register locations are shown in Table 2. Two typical instances of the use of the R command are:—

- Setting up PSW, IX, IY and A before starting a user program.
- Modifying registers after a breakpoint but before proceeding with program execution (using the P command) for debugging purposes.

Note that when modifying registers in case (b) care must be taken if PCL, PCH or SP are modified, since the proceed command P uses these to determine the address of the next instructions to be executed (PCL, PCH) and the user stack pointer (SP). ET

# BI-PAK

## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty	Description	Price
SK10	400	Mixed "All Type" Resistors	£1
SK11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SK12	200	1/4 watt Carbon Resistors	£1
SK13	200	1/4 watt Carbon Resistors	£1
SK14	150	1/2 watt Resistors 22 ohm 2m2 Mixed	£1
SK15	100	1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SK12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.

\*Quantities approximate, count by weight

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty	Description	Price
SK16	250	Capacitors Mixed Types	£1
SK17	200	Ceramic Capacitors Miniature Mixed	£1
SK18	100	Mixed Ceramics Tol. 5% pf	£1
SK19	100	Mixed Ceramics 680pf 0.5m	£1
SK20	100	Assorted Polyester/Polystyrene Capacitors	£1
SK21	60	Mixed C820 type capacitors metal foil	£1
SK22	100	Electrolytics all sorts	£1
SK23	50	Quality Electrolytics 50 1000mf	£1
SK24	20	Tantalum Beads mixed	£1

\*Quantities approximate, count by weight

## AUDIO PLUGS, SOCKETS AND ACCESSORIES

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180°, 240°, In-line 3-6 Pin Speakers, Phono, Jack Stereo and Mono, etc. Valued at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SK26	3 Pcs of 6 pin 240° DIN Plugs and Chassis Sockets	50p
SK27	1 x Right Angle Stereo Jack Plug 6.3mm plus matching metal chassis mounting socket	30p
SK28	4 Phono plugs and 2 dual phono connectors	30p
SK29	1 x 2.5mm Plug to 3.5mm Socket adaptor	20p
SK30	1 x 3.5mm Plug to 2.5mm Socket adaptor	20p
SK31	1 x 3.5mm Plug to Phono Socket adaptor	20p

## 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncodded — you select for V.L.T.S. ALL perfect devices — NO duds Min 50v 50 for £1.00 — worth double ORDER NO. SX76

Silicon General Purpose NPN Transistors TO-18 Case Lock fit leads — coded CV7644. Similar to BC147 — BC107 — ZT89 ALL NEW! VCE 70v IC500mA Hfe 75-250 50 off 100 off 500 off 1000 off

PRICE £2.00 £3.80 £17.50 £30.00  
Order as CV7644

## BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises:  
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit.  
1 Sheet PCB Transfers. 210mm x 150mm  
1 Etch Resist Pen.  
1 1/2 lb pack FERRIC CHLORIDE crystals.  
3 sheets copper clad board.  
2 sheets Fibreglass copper clad board.  
Full instructions for making your own PCB boards.

Retail Value over £15.00  
OUR BI-PAK SPECIAL KIT PRICE £9.75  
ORDER NO. SX81

## Silicon NPN 'L' Type Transistors

TO-92 Plastic centre collector  
Like BC182L — 183L — 184L  
VC80 45 VCE 30 IC200mA Hfe 100-400

ALL perfect devices — uncodded ORDER AS SX183L  
50 off 100 off 500 off 1000 off

PRICE £1.50 £2.50 £10.00 £17.00

## PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line  
VCE 40 VCE 35 Ic 300mA Hfe 50-400  
Brand New — Uncodded — Perfect Devices  
50 off 100 off 500 off 1000 off

PRICE £2.00 £3.50 £15.00 £25.00  
Order as ZTXPNP

## BI-PAK SOLDER-DESOLDER KIT

Kit comprises ORDER NO. SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit  
1 Quality Desoldering pump High Suction with automatic ejection. Knurled anti-corrosive casing and tetion nozzle.  
1 5 metres of De-soldering braid on plastic dispenser  
2 yds (1.83m) Resin Cored Solder on Card  
1 Heat Shunt tool tweezers Type  
Total Retail Value over £12.00  
OUR SPECIAL KIT PRICE £8.95

## BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require, plus some very interesting ones you will soon be using and of course, the largest range of semiconductors for the Amateur and Professional you could hope to find.

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts: i.e. price, description and individual features of what we have available. But remember, Bi Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK.

To receive your copy send **75p** plus 25p p&p

Send your orders to Dept ET18  
BI-PAK PO BOX 6 WARE HERTS.  
SHOP AT 3 BALDOCK ST.  
WARE HERTS.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order.  
Total Postage add 75p per Total order.

## USED EQUIPMENT

Ex-P.O. Multimeters in leather case. AC/DC Volts, DC current, ohms. Absolute Bargain  
Leads not included.  
£6 + £1.50 p&p

## 500V MEGGER

Transistorised Insulation Tester and four decade resistance bridge with four ranges. Invaluable piece of test gear. In case with carrying handle. Uses one PP9 batt. £15.00 + £2 P&P

Recent Style P.O. Telephones  
£4.75 + £1.80 P&P  
2 for £9 + £2.50. 5 for £20 + £5

COMPACT TELEPHONE  
With wall-mount bell £6.50  
Older style black telephones, £3. p&p as above. Our leaflet explains how to use G.P.O. phones in home intercom systems.

5 Digit Counters 48V coil. Non resettable 75p

UNISELECTORS. 50v, 4 Bank + Homing Bank, 25 way £3.50

D CONNECTOR SOCKETS with cover. 50 way £2

60V 8A TRANSFORMER. Ideal for high power supply unit or amplifier £12 inc. p&p. BEAT THAT!

FREE on request — Leaflet "D.I.Y. Telephone Systems and Automatic Exchange Design".




L.E.M. SERVICES  
239 RUGBY ROAD  
LEAMINGTON SPA CV32 6DY  
WARWICKSHIRE

TEL: 0926 30622 FOR QUANTITY DISCOUNTS ETC.  
ALL ITEMS — MONEY BACK IF NOT DELIGHTED.

ADD 50p P&P  
ORDERS OVER  
£7.50 POST FREE  
unless stated otherwise

## LOW-COST, RUGGED TEMPERATURE CONTROL

HIGH QUALITY

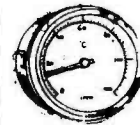

TEMP. GAUGE 0° - 120°C  
Remote sensor on 38" capillary, panel mounting, dial 55mm. dia.

ONLY £2.50

## 16A 240V RANCO THERMOSTAT

Wide control range (low room temp. to over boiling point) Sensor on 22" capillary. £2.30, including control knob

## RANCO THERMAL CUT-OUT 100°C

15A 240V. Sensing coil on 41in. capillary panel mounting with reset button £1.20

BUY ONE EACH OF ABOVE FOR £5.50

LIGHT DEPENDENT RESISTORS in plastic housing with window, heavy-duty lead. Similar to ORP 61. You normally pay well over double for resistor alone. Only 30p or £2.35 for 10.

GEARED Synchronous motor, 8 r.p.m., 240V A.C. 3 Watt £2.

SOLENOID GAS VALVE. 240V A.C. 5 P.S.I. suitable for non-corrosive fluids. £2.20

BULGIN 3 pin free plug & panel socket, 2A 240V 50p


AUTOMATIC DIAL UNIT. (mains powered). These units connect into a telephone and dial a number when a punch-card is inserted. Card & instructions supplied. Cards readily available. Many uses. Only £8 + £1 p&p

## SINCLAIR COMPUTERS

We are the leading world-wide Sinclair expert specialist including Norway, Sweden, Finland and Denmark. Write for our surprisingly low prices.
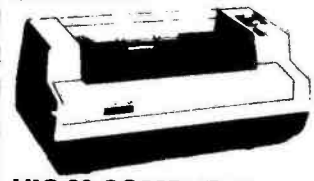
## PRINTERS

Buy any of the below and get a free interface kit and word processor program for UK101 or Superboard. Seikosa GP100A £205. OKI Microline 80 £275. OKI Microline 82A £399. Epson MX707 £289. Epson MX807/3 £319. Epson MX807/3 £349. Epson MX100/3 £429.



## VIC 20 COMPUTER

Two special offers: If it is bought with the Vic 20 we can supply the cassette recorder for £30.43. Alternatively, we will supply a free kit with each Vic 20 to allow the use of an ordinary cassette recorder. Vic 20 £165. Ordinary cassette conversion kit £8. Vic 20 cassette recorder £36.50. High resolution cartridge £27.95. Machine code monitor £27.95. Vic printer £189. Floppy disc drive £309. Ram cartridges: 3K £24, 8K £36, 16K £5. Game cartridges: Superlander, Alien or Avenger £15 each. Joystick £6.52. Intro to Basic Pat 1 £13. New low cost memory board, no need for a mother-board, comes with 3K ram on board + socket for a rom + sockets for another 24K of low current Nmos ram (Just plug in chips to expand memory) £49. 27K version £109. Extra memory chips £6 per 2K.



## UK101 AND SUPERBOARD

32 x 48 display expansion kits UK101 £9. Series 1 Superboard £14. Guard band kit for Superboard

## SWANLEY ELECTRONICS

DEPT ET1, 32 GOLDSL RD., SWANLEY, KENT BR8 8EZ  
Tel Swanley (0322) 64861

only £10. The below accessories suit both the UK101 and Superboard: Extra ram £2.10 per K. Cegrom £22.50. Wemon £14.95. Word processor program £10. Centronics interface kit £10. 610 expansion board £179. Cassid minifloppy disc drives with DOS single £275, dual £415.

## NEW GENI 1 £299

EG3014 Expansion box with 16K/32K ram £199/£213. We are Gamma disc drive specialists for the Gene. Single sided disc drives: 40 track £205, dual 40 track £345, 80 track £268, dual 80 track £468. Double-sided disc drives: 80 track £395, dual track £699. Double density converter £72. Parallel printer interface £36.



## BATTERY ELIMINATORS\*

3-way type 6/7.5/9V 300ma £3.50. Stabilized model 3/6/7.5/9V 400ma £7.95. 100ma radio types with press studs 9V £4.95, 9V + 9V £6.25. Car converter 12V input, output 3/4.5/6/7.5/9V 800ma £3.04.

## BATTERY ELIMINATOR KITS\*

100ma radio types with press-studs 9V £1.75, 9 + 9V £2.50. Stabilized 8 way types 3/4.5/6/7.5/9/12/15/18V 100ma £3.12, 1A £8.50. Stabilized power kits 2-18V 100ma £3.12, 1-30V 1A £8.50, 1-30V 2A £15.30. TTL and computer supplies 5V stabilized 1.5A £9, 3A £14, 6A £23. 12V car converters 1A £1.82.

## TV GAMES\*

AY-3 8550 + kit £9.26.

## BI-PAK AUDIO MODULES\*

PS12 £1.75. T538 £2.90. AL60 £5.62. BMT80 £6.36. Stereo 30 £19. AL80 £8.56.

Postage £3.50 on computers, £4.50 on printers and 50p on other orders. Please add VAT to all prices except those sections marked with a \*. Overseas and official credit orders welcome.



**POWER SUPPLY PCB:** (5" x 3")  
To build stabilised PSU for TTL CMOS  
5 micro 1A5 @ 5V 12 V 15 Full  
components and construction details  
supplied ..... 80p  
Components less transformer..... 250p

**MAINS TRANSFORMER:** compact,  
well constructed by AIR LINK 0.9V 2A  
DIL 3 way SPST ..... 35p

**HEAT SINK:** TO 220 10°C/W ..... 45p

**CERAMIC CAPACITOR (50V)**  
33pF to 50nF ..... 2p

**POLYSTYRENE CAPACITORS (50V)**  
100pF to 1000pF ..... 3p

**POLYESTER CAPACITORS (100V)**  
1nf to 680nF 6p 1uF 1u5 8p

**ELECTROLYTIC CAP (uF/V)**  
1/25 to 150/25 6p 160/25 640/16 3p  
220/25 470/25 10p 470/40min 12p  
1500/40 22p 2000/18 14p ..... 15p

**DIOLYTR 2A/250V DPST..... 20p**

**RCT 3 way SPST..... 30p**

**RESISTORS (1W 5% carbon film)**  
10 ohms to 10 Mohms E12..... 1p

**PRESETS** (miniature horizontal) ..... 4p  
100 ohms to 1 Mohms..... 4p

**POTENTIOMETERS LIN 4K7 10K 22K**  
100K 1M LOG 47K 22K 47K 100K  
220K  
470K 1M 2M2 ..... 25p

**ZENER DIODE**  
3V3 to 27V 5p  
1A/200V 17p  
1A/400V 20p  
1A/600V 17p  
1A/100V 16p  
2A/100V 20p  
8A/400V 32p  
3A/600V 35p

**THYRISTORS**  
1A/400V 20p  
1A/600V 17p  
1A/100V 16p  
2A/100V 20p  
8A/400V 32p  
3A/600V 35p

**OPTO ELECTRONICS**  
DL703 70p  
DL707 70p  
OR172 65p  
5 mm clip 3p  
3mm & 5mm  
Red LED 9p  
Green 9p  
Yellow 9p  
Rect Green 9p

**DIL SOCKETS**  
8 pin 7p  
16 pin 11p  
18 pin 16p  
5 mm clip 3p  
3mm & 5mm  
24 pin 16p  
28 pin 16p  
40 pin 16p

**DIODES**  
DA91 7p  
DA200/2 4p  
1N916 4p  
1N4148 4p  
1N4005 4p  
1N5400 11p  
1N5402 13p  
1N5404 14p

**VOLTAGE REGULATORS**  
500mA: 1N4148 4p  
1N4005 4p  
1N5400 11p  
1N5402 13p  
1N5404 14p  
79M12 20p  
79M24 20p  
1 Amp: 1N5402 13p  
7805 50p  
7812/15 50p  
7818 50p  
7905 60p  
7912/15 80p  
7918/24 60p  
1A5 70p  
7805 70p

**BRIDGE RECTIFIERS**  
W02M 16p  
W06M 17p

**AY-5:**  
4007D 450p  
CA2018H 50p  
CA2019 50p  
CA2028A 40p  
CA2048 245p  
CA2054 40p  
CA2080 65p  
CA2090A 40p  
CA2090A 40p  
CA2130E 70p  
CA2160E 100p  
LF351N 32p  
LF356N 60p  
LM10C 80p  
LM301AN 14  
LM308N 8  
LM318H 80p  
LM318N 100p  
LM339N 40p  
LM380N 55p  
LM381N 90p  
LM382N 70p  
LM4158N 35p  
LM4180 170p  
LM4390N 40p  
LM4391N 200p  
LM13600 100p  
LM1310N 50p  
MC1495L 400p  
MC1496P 50p  
MC15098 600p  
ML922 450p  
NE555 22p  
NE562 40p  
NE567 140p  
NS76115AN 125p  
TAA621 290p  
TBA641BX11 125p  
TB A651 100p  
TB A800 65p  
TB A820 80p  
TDA1004 35p  
TDA1008 35p  
UA1A170 40p  
ZNA24E 150p

**CMOS**  
13p  
4001B 14p  
4002 13p  
4006B 45p  
4007 11p  
4008 56p  
4010B 33p  
4011B 14p  
4012 15p  
4013B 28p  
4014 40p  
4015B 60p  
4016 20p

**33p**  
4020B 65p  
4021 6p  
4022 37p  
4023 15p  
4025 14p  
4027 30p  
4028 45p  
4029 65p  
4030 18p  
4035 92p  
4041 75p  
4042 55p  
4043 60p  
4044 40p  
4047 90p  
4048 45p  
4049 28p  
4050B 29p  
4068 18p  
4069 14p  
4070B 17p  
4071 20p  
4072 23p  
4073 23p  
4081 14p  
4082 22p  
4086 66p  
4087 80p  
4088 40p  
4089 75p

**35p**  
7448 11p  
7451 6p  
7453 13p  
7454 13p  
7460 7p  
7470 22p  
7472 22p  
7473 14p  
7474 16p  
7475 23p  
7476 18p  
7480 25p  
7482 55p  
7483 45p  
7489 110p  
7490 22p  
7491 38p  
7492 30p  
7494 35p  
7495 35p  
7496 35p  
7497 166p  
7498 166p  
7499 166p  
7500 166p  
7501 166p  
7502 166p  
7503 166p  
7504 166p  
7505 166p  
7506 166p  
7507 166p  
7508 166p  
7509 166p  
7510 166p  
7511 166p  
7512 166p  
7513 166p  
7514 166p  
7515 166p  
7516 166p  
7517 166p  
7518 166p  
7519 166p  
7520 166p  
7521 166p  
7522 166p  
7523 166p  
7524 166p  
7525 166p  
7526 166p  
7527 166p  
7528 166p  
7529 166p  
7530 166p  
7531 166p  
7532 166p  
7533 166p  
7534 166p  
7535 166p  
7536 166p  
7537 166p  
7538 166p  
7539 166p  
7540 166p  
7541 166p  
7542 166p  
7543 166p  
7544 166p  
7545 166p  
7546 166p  
7547 166p  
7548 166p  
7549 166p  
7550 166p


**TTL "LS"**  
LS00 12p  
LS01/2 12p  
LS03 12p  
LS04 13p  
LS08 14p  
LS10 14p  
LS11 15p  
LS12 15p  
LS13 24p  
LS14 36p  
LS20 15p  
LS21 15p  
LS27 15p  
LS30 14p  
LS32 36p  
LS42 17p  
LS47 42p  
LS48 45p  
LS73 20p  
LS74 18p  
LS75 25p  
LS76 25p  
LS78 22p  
LS86 18p  
LS90 38p  
LS93 28p  
LS95 46p  
LS109 23p  
LS122 25p  
LS123 40p  
LS157 36p  
LS163 42p  
LS221 52p  
LS251 50p  
LS253 50p  
LS279 30p

**TRANSISTOR**  
AC127 20p  
AC128 22p  
AC181 15p  
AC142 15p  
AC153 20p  
AC176 20p  
AC187 13p  
AC188 20p  
AD149 37p  
AF118 30p  
AF124 40p  
AF125 40p  
AF139 35p  
AF186 40p  
AS54 18p  
AS55 18p  
BC107 8p  
BC108 8p  
BC109 8p  
BC113 6p  
BC117 10p  
BC119 10p  
BC142 23p  
BC143 23p  
BC147 6p  
BC148 6p  
BC149 7p  
BC158 9p  
BC169 9p

**50p**  
7455 13p  
7456 13p  
7457 13p  
7549 13p  
7550 13p

**50p**  
7551 13p  
7552 13p  
7553 13p  
7649 13p  
7650 13p

# MEMORY TELEPHONE

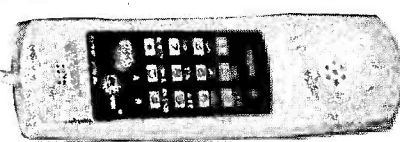

One piece phone with 11 or 22 number memory. These numbers can be changed at will. Last number dialled or any memory number can be automatically redialled. Plays a melody to the called party when muted. Requires no external power or batteries. Distortion free sound. Electronic bell can be switched off. Easy to connect. 12 foot cord. 12 months warranty. **11 no mem: £55. 22 no mem: £65.**

## STOP THIEF!

This miniature self-contained battery operated volumetric burglar alarm has won the Electronic Industries coveted Tottie Award for 1981 and has been chosen for London Design Centre for its outstanding performance. Unlike other home alarms this is controlled by Motorola custom built micro and has self diagnostic features. It works like a submarine sonar. It has independent range and sensitivity controls and can differentiate between a fly and an intruder over the whole range of 27 ft. The memory checks 4 times before sounding 100 db cut wrenching alarm that makes coherent thinking impossible. All these features combine to reduce false trigger, a major drawback with most alarms to absolute minimum. Comes complete with wired remote key operated control with test and personal attack button. **£150.00**

BFX29	25p	IP33C	36p	2N698	20p	3N3711	8p
BFX84	23p	TIP34A	40p	2N706	9p	2N3823	52p
BFX86	18p	TIP38A	127p	2N914	14p	2N3866	40p
BFX87	23p	TIP2955	54p	2N918	16p	2N3903	11p
BFX88	22p	TIP3055	48p	2N1131	11p	2N4037	35p
BFY50	20p	2N2217	18p	2N1132	13p	2N4058	10p
BFY52	18p	2N2219	15p	2N1304	23p	2N4061	6p
BFY53	10p	ZTX107	10p	2N1306	23p	2N5458	40p
BSX20	10p	ZTX108	10p	2N1308	30p	2N5459	35p
BZ205	105p	ZTX109	10p	2N2222A	15p	2N6027	15p
BU208	11p	ZTX300	9p	2N2369	14p	3N128	20p
MJ2955	90p	ZTX301	9p	2N2484	18p		
MPF104	40p	ZTX303	10p	2N2646	40p		
MPF105	40p	ZTX311	16p	2N2904	17p		
MPF106	40p	ZTX341	16p	2N2906/7	17p		
OC28	50p	ZTX500	11p	2N2926G	10p		
TIP29	25p	ZTX501	11p	2N3053	20p		
TIP28B	28p	ZTX502	16p	2N3055	40p		
TIP30	25p	ZTX503	14p	2N3702	to		
TIP30B	28p	ZN697	20p				

**MAIL ORDER ONLY**  
**DELTA TECH & CO.**  
62 NAYLOR ROAD, LONDON, N20 0HN  
Tel: 01-445 8224  
Prices include VAT, Add 50p P&P

Minimum ACCESS order £5. All items branded full spec and guaranteed. Our Sale offer: Buy 5 and get 1 free. This means almost a 20% discount!

**"SALE SALE"**

**D.I.Y. MINIATURE ON-OFF SWITCHES**  
Gold plated contacts  
Sealed base. Ideal for programming & position at less than half manufacturer's price  
**ONLY 75p**  
Will fit into 14 pin di socket. Ten at 65p ea. per 100 55p ea.

**U.H.F. MODULATORS**  
Latest type adjustable  
Ideal for computers  
with data circuit  
Size 1/2" x 1/2" x 1/2"  
No brand name  
Only £3.50

**MINIATURE EDGE**  
Ideal for computers  
with data circuit  
Size 1/2" x 1/2" x 1/2"  
No brand name  
Only £1.85

**MONSANTO**  
Half-inch  
1 Display  
High Intensity  
£1 each  
set of £3.50  
Common anode  
14 Pin DIL Package

**BRIDGE RECTIFIER**  
800 PIV 35 amps  
1/2x1/2x1/2" £3.50

**NATIONAL**  
FERRITA Chips  
£2.15  
£1.75

**1N148 Diodes**  
Full spec, but no polarity band  
Per 1,000 £10

**MINIATURE M.P.C. POTENTIOMETERS, Model M2**  
High quality, 5% tolerance, 2-watt, with lin spindles. All values, 47 ohms-47k only 80p each per 10. 50p each per 100. 40p each

**QUANTITY DISCOUNTS ON ALL items (unless stated), 15% per 10, 20% per 50, 25% per 100. All items BRAND NEW (unless otherwise stated).**  
**DELIVERY** from stock - add post 35p per order, incl. VAT.

**HONEYWELL PROXIMITY DETECTOR**  
Integral amplifier 8V D.C. ea.  
**PHOTO CONDUCTIVE CELL** £1.25 High-power CdS cell 600MW for control circuits  
Resistance 800 ohm to 4K Max volts 240 Size 1/2" x 1/2" x 1/2"

**RIBBON MICROPHONE**  
with pre amp on chassis  
£1.75

**LM380 Amplifier** ..... 85p  
**LM318N Hi-Slew Op. Amp** ..... £1.50  
**LM323K, 5v, 3 amp reg.** ..... £2.50  
**LM310N Volt. follower** ..... £1.20  
**LM311H High Perf. Volt. Comparator** ..... £1.90  
**LM339AN, 5-watt Amp** ..... £1.20  
**LM339N Dual Com.** ..... 50p  
**7905 Reg. Dv.** ..... 75p

**STEREO CASSETTE TAPE HEADS.**  
Quality replacement for most recorders, with mounting plate Record/Replay. £2.80

**MARRIOTT TAPE HEADS**  
Quarter track  
Type  
XRPS18 Record/Replay (each) ..... £2.00  
XRPS36 Record/Replay (each) ..... £3.00  
XES11 Erase (each) ..... £1.00

**RECHARGEABLE BATTERIES**  
VARTA 36 volts DEAC M AH 225 ..... £1.50  
DRYFIT 6-volt 4.5 amp ..... £1.50

**XTAL FILTER 10 Mcs, 12.50B separation, 1/2x1/4x1 inch £7.00**  
100KC/S + 1 meg 3.00

**MULLARD MODULES**  
LP1171 LP1175  
If Strip AM, FM Front end Pair £5.75  
Complete with Data LP1186 LP1185  
varicap Med & Long Tuner  
£5.00 £2.50

**CRYSTALS COLOUR TV**  
4.33x3.19 mcs £1.25  
Miniature type sealed

**QUALITY FANS**  
"Whisper Model" by Roton  
Low power consumption (less than 10 watts)  
Silent running 115v (two in series for 230v 50/60Hz)  
Size 4" x 4" x 1/2"  
Only £5.50 inc. VAT  
**BRAND NEW**  
50% less than manufacturer's price

**HEWLETT-PACKARD DISPLAYS**  
5082-7650  
HIGH EFFICIENCY AND VERY BRIGHT  
Only £1.00 each  
Set of 6 for £5  
Half-inch red common anode will replace DL707, 14-pin DIL.

**"CHERRY" ADD-ON KEYPAD**  
LIST PRICE £22.00  
**OUR PRICE ONLY £7.50 INC. VAT**  
A compact 12-button keypad suitable for use with Cherry Keyboard to extend its functions plus four extra keys  
Supplied brand new with data  
A 3 x 4 non encoded single mode keyboard

**EXPORT enquiries invited.**  
**TELEX 262284 Transonics Mono 1400**

**HENRY'S**  
01-723 1008/9  
Callers to: 404 EDGWARE ROAD, LONDON W2 1ED  
All mail orders/export enquiries, 11/12 Paddington Green, London W2

# ELECTROVALUE

**A SPECIAL SUMMER PROMOTION**

**FREE VOUCHERS TO SAVE YOU UP TO £2.10**

**ELECTROVALUE CATALOGUE 82**

**70p**

**Hardware Components Semi-conductors Computing**

**THREE 70p REFUND VOUCHERS FREE** for spending singly at any time on any one C.W.O. (U.K.) order minimum list value £10. This can quickly save you up to £2.10 in addition to the other benefits you enjoy by buying from Electrovalue. Send 70p for Catalogue 82 + 3 free vouchers by return now

**+ USUAL DISCOUNTS + FREE POSTAGE**

**DISCOUNTS**  
5% on orders over £23 (inc. V.A.T.)  
10% on orders over £57.50 (inc. V.A.T.)  
on most catalogue items, but not on payments by credit cards.

**POSTAGE**  
Not charged on U.K. orders over £5.75 inc. V.A.T. if under, add 40p handling charge.

**SEMI-CONDUCTORS/ICs/OPTOs**  
**COMPUTERS/SOFTWARE etc.**  
**CAPACITORS/RESISTORS**  
**CONNECTORS/SWITCHES/KNOBS**  
**POTS/FERRITES/METERS**  
**BOOKS/SOLDER TOLDS**  
**AND MORE AND MORE AND MORE**

**ELECTROVALUE LTD.** 28E St. Junes Road, Englefield Green Egham, Surrey TW20 0HB  
Phone: Egham 33603 (STD 0784; London 67). Telex: 284475  
Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1MA. Phone: (061) 42 4945

**ETI AUGUST 1982**

**57**

# READ/WRITE

Letters for this page should be addressed to Read/Write at 145 Charing Cross Road, London WC2H 0EE.

Dear Sir,

I am writing to enquire if your magazine or any of your readers have heard about or tested an electronic device for inducing dream consciousness (lucid dreams).

This bedside machine monitors the breathing rate of a sleeper by means of a sensitive thermistor attached to the nose. During a dream period, the breathing rate increases above normal; this is used to trigger a mild electric signal to the wrist of the dreamer telling him that he is dreaming and should become conscious in his dream.

Lucid dreams, being far more vivid than normal, are in full colour and three dimensional. The dreamer also has full control over his dream environment and can manipulate it at will. He can dream consciously about anything he chooses and total dream recall is normal.

This equipment was designed and developed by a Dr. Keith M. T. Hearne of Hull University and I believe manufactured and marketed by Campden Instruments (Incam Ltd) of London. But despite persistent enquiry, I have seen no test or reports on this equipment in electronic magazines. Have you or any of your readers seen anything?

I would be very grateful for any information you may have come across on this interesting device!

Yours faithfully,  
Mark Botham,  
Northumberland

Sorry, never heard of it. Sounds like it makes video games look a bit sick though. Control your dreams at will, eh? Interesting...very interesting...

Dear Mr. Harris,

I am enclosing my entry for your Prize Crossword No. 3. However, I am sorry to say that I do not find this feature up to the usual standards of the rest of the magazine.

May I draw your attention to Crossword No. 1 in the January issue. Clue 24 Down was "Radiation particles are certainly not passive." At first I chose "Active" as the answer. However, on reflection, a radiation particle may be an ion, so I changed the answer to "Action."

You can imagine my surprise when you published the answer as "Active." The problem really lay in the fact that

the only letter crossed with this puzzle was the letter 'C', common to both possible answers.

Now, five months later, in Crossword No. 3, the same difficulty arises. Clue 22 Across is "Timely happening." The only letter crossed with is the second letter, which I make an 'E'. Hence the possible answers (all having some connection with time) are as follows: Decay, Death, Delay, Hence, Hertz, Leave, Merge, Peaky, Recur, Relay, Relic and Telex.

Many of these are also technical terms and therefore likely to be the correct answer. May I remind your Crossword compiler that the rule is: "If a clue is to be made wholly or partly vague, the answer must have sufficient letter crosses to enable it to be verified as the sole answer." The puzzle to be solved should involve ingenuity in word manipulation, not guesswork or thought transfer!

Yours sincerely,  
Paul M. Richardson,  
Tavistock

Comments received. Passed on to our compiler, who will no doubt have a few cross words to say in reply.

Dear Sir,

I was happy to read the article in your April Birthday supplement entitled, "Steering Wheel? - Wot Steering Wheel?". Enclosed is a copy of a letter I sent to the Prime Minister in February this year.

Robert W. Teasdale,  
Newcastle-Upon-Tyne

Letter to Prime Minister,  
February 1982

On giving some thought to future cars, I thought it would be a good idea if they had some form of electronic control.

The system of flashing lights on the motorways was a good idea, but motorists tend to ignore this system, and I thought that futuristic systems could be devised to electronically control the speed of cars (to prevent them going too fast under certain conditions, eg fog), with a built-in safety device for the driver to ignore these signals in an emergency: electronically controlled to respond to certain speed limits; controlled to stop or slow at traffic lights (being able to override this signal if

conditions desired it); controlled to slow at pedestrian crossings, crossroads and junctions; controlled to keep a safe distance from the car in front (with an override to overtake for a short period if necessary and an exterior signal to indicate when on override); controlled to slow at obstructions, again with an override.

Fast cars are dangerous and use a lot of energy. What is required is a safe, controlled car with power to get up hills and through adverse conditions.

I'm sure it would be better to have a safe, controlled system rather than fast dangerous cars, thus cutting down on accidents, death, disablements, and the work of all the services involved in accidents. I hope these suggestions can be put to future scientists and car manufacturers.

Dear Sir,

As so many of us are now using electronically operated quartz crystal controlled watches, may I suggest that an article giving a detailed description of their operation would be of considerable interest.

I am, yours sincerely,  
H. Vernon Kirby (Regular Reader),  
Hayling Island

Couldn't agree more. You wanna write it?

Dear Sir,

I know that you are busy men, but looking through recent ETIs, I came across two speaker systems - the ETI V3 (Oct 1981) and the Wharfedale E70 kit (April 1982). I would be interested in knowing your views on them.

Do you feel that it would be of interest to ETI's readership if you reviewed all the hi-fi projects and compared them to corresponding commercial units?

Yours faithfully,  
M. G. Hill,  
Harrow

The V3 and E70 are designed to meet different criteria. The V3 is an 'all-rounder' primarily intended for use with a wide range of music at 'normal' (if there is such a thing) volume levels. It is designed to be as neutral as possible in its portrayal of the signal.

The E70 is a high-efficiency speaker with an exciting 'lively' sound balance. It is most at home with the type of music best suited to this method of replay.

As to reviewing ETI projects, could you believe anything anyone says about their own product? Our objectivity would have to be suspect.

ETI

# LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts. i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder and hook-up wire. Self assembly simulated wood cabinet — only £4.50 + £1.50 p&p.

Featured in April issue of P.E. Reprint 50p. Free with kit.

## ELECTRONICS ONLY!

Ideal for updating your existing cassette. Includes pcb diagram, all semiconductors, IC's, Capacitors, resistors. +£1.40p&p

**£18-95**

**£32<sup>95</sup>**

+ £2.75 p&p.

# HI-FI STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.O.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES



## 125W HIGH POWER AMP MODULE

KIT: **£10-50** BUILT: **£14-25**  
+ £1.15 p&p + £1.15 p&p

The power amp kit is a module for high power applications — disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is pre-formed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Suitable mains power supply kit with transformer. £7.50 plus £3.15 p&p.

### SPECIFICATIONS:

Max. output power (RMS): 125W. Operating voltage (DC): 50-80 max. Loads: 4-16 ohms. Frequency response measured @ 100 watts: 25Hz - 20KHz. Sensitivity for 100 watts: 400 mV @ 47K. Typical T.H.D. @ 50 watts, 4 ohms: 0.1%. Dimensions: 205x90 and 190x36mm.



Reprint 50p — FREE with kit!

## TV SOUND TUNER KIT

As featured in E.T.I. Dec. '81. Kit of parts including PCB, UHF tuner and selector switch with all components exc. case.

**£11-45** + £1.50 p&p

• Transformer £1.50 + £1.50 p&p free on transformer if ordered with kit. • Ready built LP1183 Module for simulated stereo. £1.95 + 75p p&p.

## P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with P.E. (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. FEATURES: VHF, MW, LW bands, interstation muting and AFC on VHF. Tuning meter. Two back printed pcb's. Ready made chassis and scale. Aerial: AM — ferrite rod, FM — 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" app. Complete with diagram and instructions. Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/2" x 8 1/2" x 3 3/4". **£3.50** Plus **£1.50** p&p. Reprint 50p — FREE with kit.



**£17-95** + £2.50 p&p.

SPECIAL OFFER! TUNER KIT PLUS:  
• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pickup and aux. inputs.  
• Matching power supply kit with transformer. • Matching set of 4 slider controls for bass, treble + vols. **£21.95** + **£3.80** p&p.

All mail to: 21E HIGH STREET, ACTON, W3 6NG. Note: Goods despatched to U.K. postal addresses only. All items subject to availability. Prices correct at 30/6/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch. RTVC Limited reserve the right to update their products without notice. Send S.A.E. for full list of products. Telephone or mail orders by ACCESS are welcomed.

ALL CALLERS TO: 323 Edgware Rd, London W2. Tel: 01-723 8432, 9.30 - 5.30, closed all day Thurs. ALL PRICES INCLUDE VAT AT 15%.



## 19" RACK MOUNTING CABINET.

Front Panel 480 x 150mm Rear Case 425 x 250 x 140mm

**£23-95**

**£19-50**

Or Free Standing



Brushed Ali Front with CHROME HANDLES

This is a professional rack mounting cabinet that will allow you to get your equipment off the bench. Rack mounting provides security for your equipment and easy access for maintenance. This Precision rack mounting cabinet has all the features you would expect from a professional unit.

• Top, bottom and rear cover removable for access • Plates have heavy duty grey paint finish • Front panel is heavy gauge 3mm aluminium • Strong screwed construction throughout — screws included • Heavy gauge chassis mounting plate is pre drilled and has four mounting positions to choose from • Front panel is of brushed aluminium finish enhanced with heavily chromed handles.

Many sold to TANGERINE users & INDUSTRY.

ADD V.A.T. AT STD RATE & ORDERS UNDER £5.00. P & P 50p. ABOVE ITEM £2 P & P

## metal cabinets

These are beautifully manufactured cabinets with an aluminium base and 18 gauge steel covers. They come fitted with rubber feet (to please the wife!), louvred for ventilation and finished in an attractive two tone finish. They make excellent cabinets for power supplies, remote control units and many more projects.

- a — 102(d) x 56(h) x 83(w)mm **£1-70**
- b — 150(d) x 61(h) x 103(w)mm **£2-55**
- c — 180(d) x 78(h) x 134(w)mm **£3-04**
- d — 184(d) x 70(h) x 160(w)mm **£4-08**


Ask for our FREE Catalogue.



TRADE PRICES ON QTY ORDERS
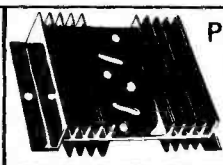
## Slide Switches

- 1P 2t 10p
- 2P 2t 12p
- 2P 3t 19p
- 4P 2t pcb 28p
- 6P 3t .. 35p
- 6P 3t .. 42p
- 1P 4t .. 26p
- 4P 4t .. 45p



## POWERSINK £1-35p

Flag mounting type with fins top and bottom. Available either undrilled or drilled to accept two power transistors of most types including TO-3, TO-18, TO-220, TO-66. Size 75(h) x 102(w) x 25(d)mm. Thermal resistance mounting surface to ambient — 1°C/Watt (2.0W/sec air velocity). Mounting surface temperature rise above ambient 60°C @ 30W heat dissipation.

RELAY-A-QUIP We EXPORT ✓

Moat Lodge, Stock Chase, MALDON, Essex, U.K.

Tel 0621-57242 10am - 8pm. Mon-Sat



## CENTRONICS 306



Superb professional quality fast compact line-printer 80 columns 120 char/sec. Parallel i/f. Beautiful quality at a silly price. Vertical format unit. To include copy of operations manual. ONLY **£149.00** Cabbage (England) **£17.50**. Tech manual (230 pages) **£10.00**.

TEKTRONIX 545B/543 Oscilloscopes from ONLY **£249.00** DISPLAY OSCILLOSCOPE. Neat unit but no data hence ONLY **£56.00** + **£10.00**

ADVANCE LF oscillator type SG66. Sn/sq 10HZ-100KHZ. ONLY **£37.50** + **£10.00**.

MARCONI RC oscillator type TF1101 20HZ-200KHZ. ONLY **£65.00** plus **£6.00**.

DATA RECORDING EQUIPMENT 4000A (258 - 9901) hard disc drives, 5 mbyte exchangeable, BRAND NEW boxed, only **£600.00** plus carriage and insurance.

PLESSEY Static Inverters 375VA 50Hz mains output from 48/56v DC input. ONLY **£110.00**

POWER SUPPLY. Modern multirail unit giving 5v at 4amp, 12v twice at 2.5 amp and 350mA Toroidal transformer. Protection features. Ideal for micro applications. ONLY **£17.50** + **£1.80**

5 volt 5 amp reg module. The perfect basis for your custom power supply ONLY **£2.50** plus 50p carriage.

DATA DYNAMICS R0390 printer 110 baud ascii 20mA/RS232. ONLY **£75.00** + **£17.50**

## MAWSON ASSOCIATES

124 Lennard Rd, Beckenham, Kent BR3 1QP

01-778 3600

WE ALSO BUY SELECTED COMPUTERS AND COMPUTER PERIPHERALS

## COMPUTER COMPONENTS


Part	1-9	10-49	50+	Low profile	
2101	1.16	1.04	0.95	DIL	Sockets
2114 200ns	1.05	0.95	0.85	Double	side wipe
4116 250ns	0.80	0.70	0.60	08 pin	0.07
4118 250ns	3.10	2.80	2.65	14 pin	0.09
4816 100ns					
BBC Micro	3.00	2.75	2.62	16 pin	0.10
6116 Rams	4.50	4.10	3.70	18 pin	0.12
6502	3.98	3.70	3.35	20 pin	0.14
2716 5 volt	2.20	2.10	2.00	24 pin	0.17
2716 3 rail	5.90	5.45	4.70	28 pin	0.20
2732	4.00	3.70	3.35	40 pin	0.30
2532	4.00	3.70	3.35		

Transformers & PSU's, Prices on Application  
Mail Order, please add 45p p&p and VAT at 15%  
Credit Card available soon

## WOODFIELD SYSTEMS

1 Coedcae Road, Abertridwr, Caerphilly, S. Wales  
Tel: 0222 830934 24 hour answering service

# RUGBY CLOCK

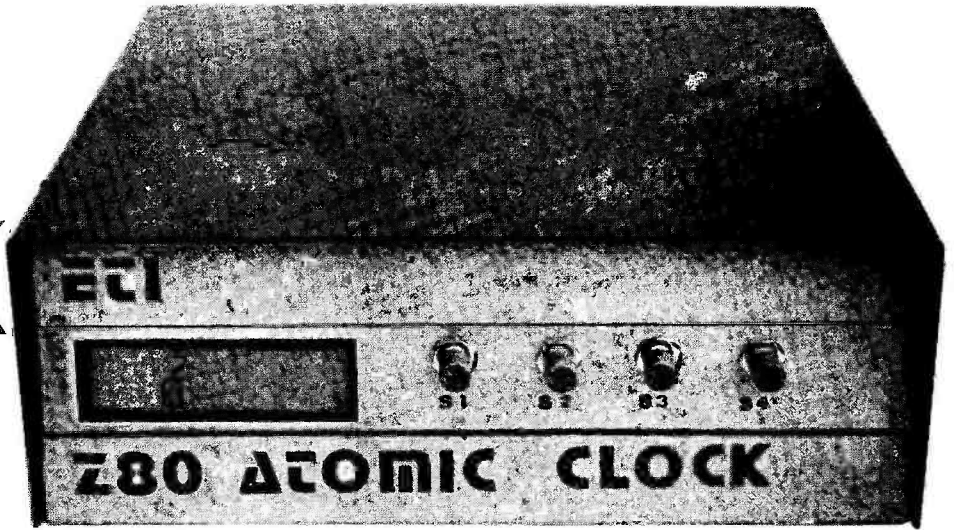

If you want to know the time, ask MSF Rugby. This accurate and versatile clock/calendar is packed with facilities and never needs resetting. Design and development by Stephen Makumbi.

Clock designs appear fairly regularly in hobbyist magazines, but they usually fall into one of two basic types. The first type derives clock pulses from the 50 Hz mains, and while these provide a highly accurate long-term performance, mains frequency variations in the short term can cause errors of several seconds in either direction. The second type relies on a built-in oscillator, usually crystal-controlled which gives excellent short-term precision but a steadily accumulating long-term error.

If only you could build your own atomic clock! This is a project slightly

outside the scope of the magazine, but fortunately it isn't necessary to go quite that far. We can all get to share the atomic clock at the National Physical Laboratory because it's used to send coded time data, 24 hours a day, on a 60 kHz radio carrier from a transmitter at Rugby. The signal is transmitted at around 50 kW RF power and can be received over most of Western Europe. Of course, a specialised receiver is required to demodulate and decode the time signals, and *that's* the project we're offering; a clock that displays the correct time of day, date, day of week, and plenty more besides, with no need to ever

correct it. Even when the signal completely disappears the clock senses this and automatically switches on to its own crystal timebase back-up clock.

All the information is checked thoroughly for parity and validity. As an example, February 29th 1983 will be rejected and dashes put into the display in place of the date.

We've included a comprehensive alarm system comprising no less than eight independent alarms. For each alarm setting there is a choice of a melody (author's 12 bar rock), altering the state of eight TTL-compatible lines, or both! The eight lines could, of course, be used

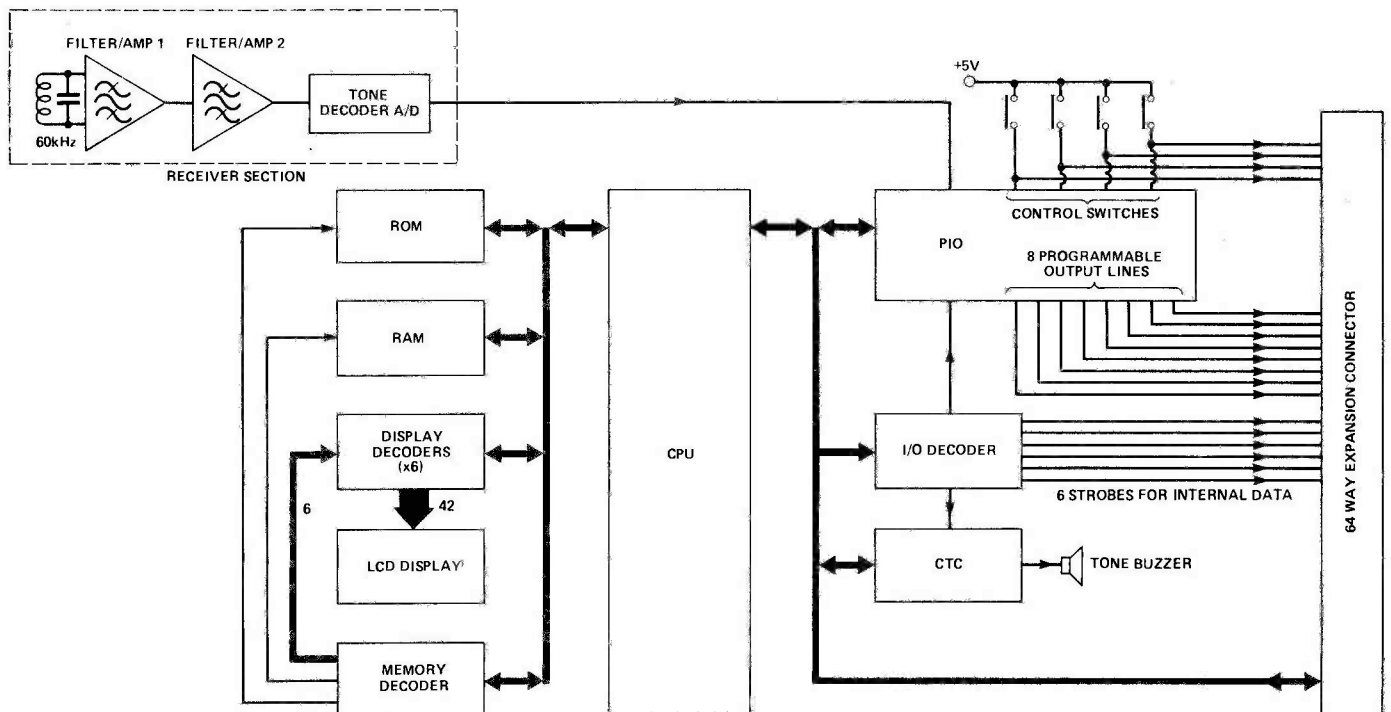


Fig. 1 Block diagram of the Rugby Clock.



Typical time display. Display format is set to 12 hour clock.



Mode 2, phase 1; the hours have been set at 12 for alarm number 2.



Mode 2, phase 2; alarm number 1 has been set for buzzer and port to function.



Mode 2, phase 3; bit 1 of alarm 6 will switch high when the alarm goes off.

to turn on and off eight different electrical appliances (through relays).

There is also a separate timer with a unique mode of operation capable of recording up to 240 lap times without interrupting the count! All this makes is simply the best clock available for home use — or anywhere!

## General Description

There are three basic modes of operation designated 1, 2 and 3; clock, alarm, and timer respectively. On reset the clock automatically enters mode 1. Another switch would enter mode 2. In order to enter mode 3 (timer) you have to press reset while pressing one of the switches.

The emphasis in this system is ease of expansion and interfacing. To this end, all the important CPU lines are brought out to a dual 32-way connector. Also, all the information that is transmitted is output to six decoded port selects (including the timer). We intend to publish useful add-on units in the future. The entire unit can be controlled by an external computer, instead of by the push-buttons.

## The Circuit

At the heart of the system is a Z80 microprocessor. Several other processors were considered including the RCA CPD 1802 for its low power consumption, Intel 8039 for its 'all-in-one' design, plus good BCD handling, and the Intel 8088 for its speed and overall superior processing power.

The Z80 was chosen because a good interrupt structure was of paramount importance in this application. IC4 decodes the lower 32K of the 64K address space into eight blocks each 4K long. These eight blocks are allocated to the PROM, RAM and six LCD displays. It might appear a waste for each digit in the display to take up an entire 4K of addressing space, but this simplifies

decoding logic and reduces chip count. Furthermore, there is 32K of memory still free!

As you may have gathered from the above text, the displays are 'memory mapped'; whenever the CPU wants to read or write to memory (in the lower 32K) pin 3 of IC6c goes high,  $\overline{MREQ}$  goes low, and A15 is low, indicating to IC4 that a memory read or write is about to take place. If at this time the address bus contains 2XXX to 7XXX hex (X = don't care) then one of the six LCD displays will be selected. Similarly IC19 is used to decode the input/output section. This IC is active when A7,  $\overline{IORQ}$  and one of  $\overline{RD}$  or  $\overline{WR}$  are low; the port selected depends on the binary value that is present on A2 to A4. This effectively divides the lower 128 port addresses (out of a possible 256) into eight separate ports each four addresses long and repeating 16 times.

The CPU clock signal is generated by XTAL1, IC5a, R1, C1, CV1. This is fed to IC5b and IC5c which are connected in parallel to provide a higher drive and isolation.

IC5d and IC5e together with R2, R3, R4, C2, SW5 form the manual and automatic power-on reset. The RESET signal is ANDed with M1 by IC6a, IC6b to form a hardware reset for the PIO (Zilog ran out of pins and omitted a proper reset pin). Incidentally although Zilog don't mention it, it's possible to reset the PIO by software. This method is used in this application, but the hardware alternative is there in case another application using the board requires it. (Anyway, we had a couple of NAND gates spare!)

IC9 to 14 are LCD display latch-decoders. Information available at the

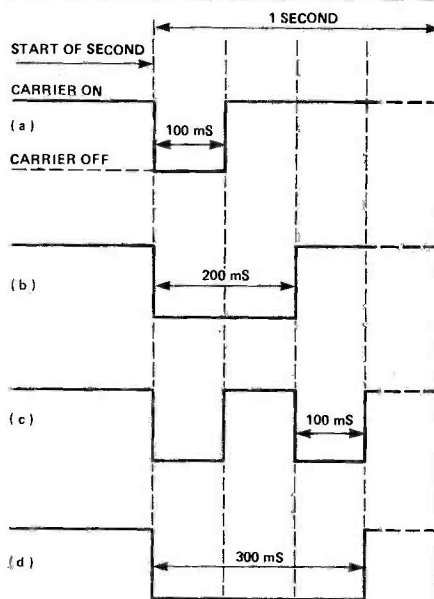


Fig. 2 (Above) Coding data into one second. (a) a 0; (b) a 1; (c) time difference; (d) a second containing odd parity.

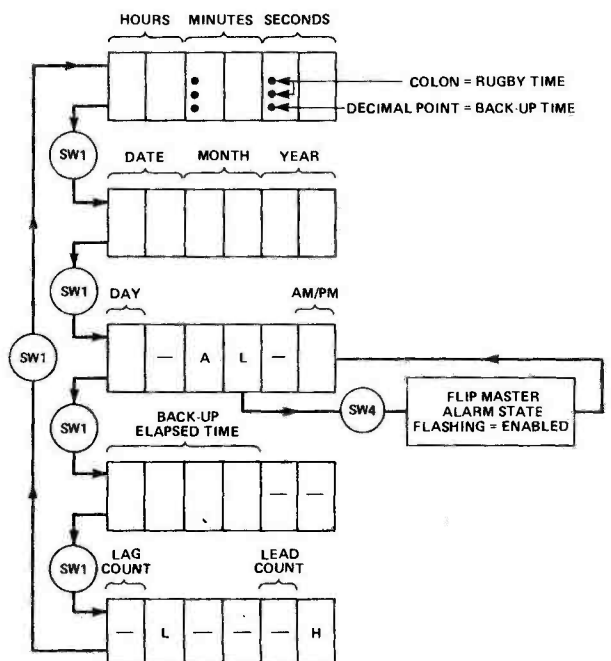


Fig. 3 (Right) The five clock faces available in Mode 1. From top to bottom they are time of day; date; day of week and master alarm indicator; time since clock switched to back-up; and BST/GMT time difference.

data pins (2-5) is latched internally when the latch input (pin 1) receives a positive-going pulse. Since this is of opposite polarity to the signals coming from IC4, a hex inverter is used.

LCD displays require a square wave drive signal on the segments in antiphase to that on the backplane. IC8c and IC8d provide such a signal with a frequency of approximately 50 Hz.

This is fed to the backplane input of the display and also to each display driver (IC9-14). These ICs perform the phase reversal, but unfortunately they don't have decimal point and colon outputs so these have to be generated externally using PIO A0 and A1. IC8a and IC8b perform the phase reversal on these.

IC15 performs several functions; serial input port (SIO), timer, tone generation for radio data, internal timing, user timer (mode 3) and alarm tune.

IC17 also performs several functions, including inputting the state of the switches SW1-SW4, inputting radio data, controlling the display decimal point and colon, inputting the default hour format (12/24); it's also a programmable output

port in conjunction with mode 2!

The receiver follows an unusual design. For a start there are no cumbersome coils; instead the entire tuning section comprises two state variable filters in series (IC20, 21). They also provide the necessary gain to couple to IC22 via FET buffer Q1. The two filters provide very good selectivity which is required at these low frequencies due to interference, especially from TV timebase circuitry. When properly tuned by PR1-4 it is possible to have the receiver closer to a TV set than is possible with many current designs. IC22 is a tone decoder whose output pin goes low when a signal within its passband is present at its input (pin 3). Q2 inverts this signal to high for 'carrier on'. There are some spare inverters on the main board which could have been used instead, but the aim was to have a self-contained receiver.

### Rugby Transmissions

The incoming radio carrier is switched off and on throughout the entire minute to convey the time information in

binary-coded form. The carrier is switched off at the beginning of every second, and the point within the first half of the second that it comes on again determines whether the bit sent within that second is a logic 1 or 0, ie, if it switches on after 100 mS, then the bit is a 0. Otherwise it will switch on after 200 mS in which case the bit is a 1. Figure 2 should make this clear.

As each second transmits only one bit of a binary coded number more than one second may be needed to transmit a whole number. Each unit is allocated the minimum number of bits which will represent the maximum value of that unit; for instance, 'Day of Week' takes up three seconds (three bits) since these will contain binary combinations 0-8 (8 not used).

Seconds 7-16 contain information about the time difference between BST and GMT. An extra pulse (break in carrier) will indicate 1/100th second difference.

The total number of pulses within seconds 1-8 represent the number of hundredths of a second that BST lags behind GMT. Otherwise, those which occur in seconds 9-16 indicate BST leading GMT by their total multiplied by 10 milliseconds.

Seconds 17-51 contain the time, date, day of week, month and year. Seconds 51-59 contain a unique binary code which is used by detecting systems to synchronise; although the clock presented here uses a different system for synchronisation.

Seconds 52-58 also contain a parity checking code on the information that was received between seconds 17-51. That is to say a pulse 300 mS long indicates that the unit in question should have an odd number of 1 bits. A pulse of 200 mS indicates an even number of 1s.

The first second (0th) contains a fast serial code which also specifies the time, date and month.

Just before this code is a very short negative-going pulse (carrier off). It is the only pulse shorter than 3 mS in the entire minute. For this reason it is detected by its unique size and used for synchronisation. The fast code is then read immediately. Synchronizing on this code as opposed to the six second ident makes it possible to make another attempt within 10 mS of the previous attempt if the previous one was false. In the other case it would take at least six seconds to find out if the ident is valid or not before the subsequent trial is attempted.

### More On Modes

As mentioned earlier, there are three basic modes which the clock could be in. In order to economise on front panel switches, SW1-4 are all multi-function and the function of each switch

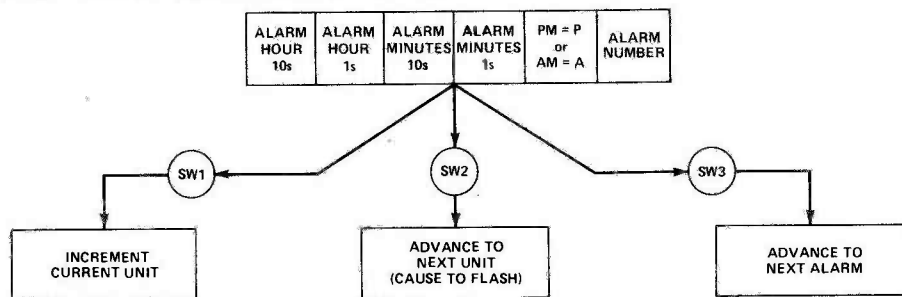


Fig. 4 Switch functions for Mode 2, phase 1.

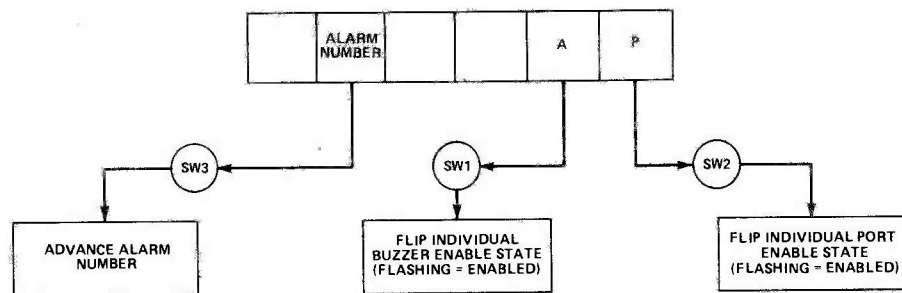


Fig. 5 Switch functions for Mode 2, phase 2.


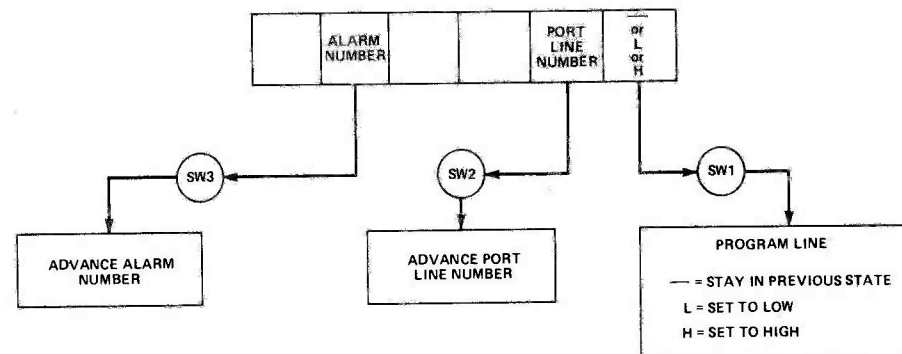


Fig. 6 Switch functions for Mode 2, phase 3.

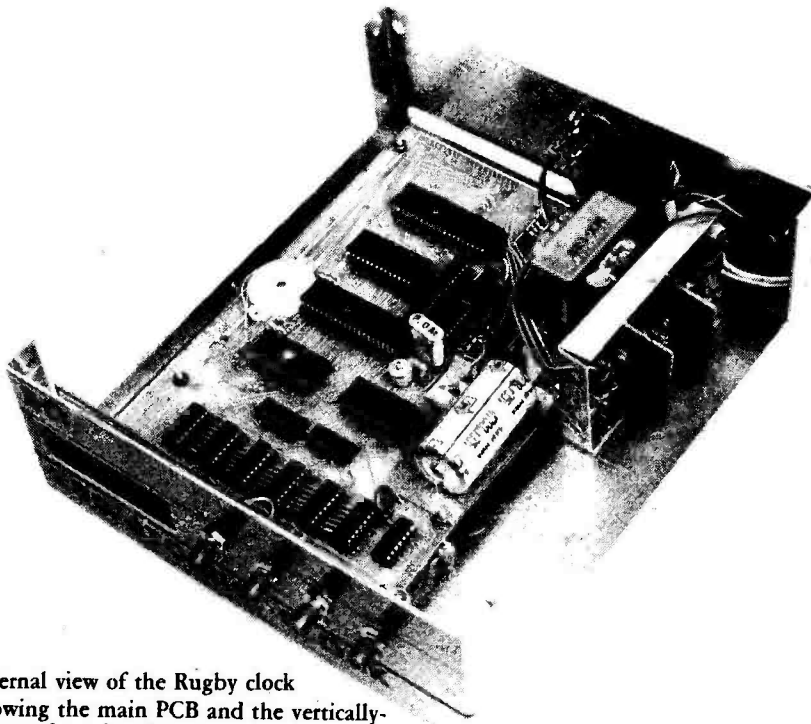

Internal view of the Rugby clock showing the main PCB and the vertically-mounted receiver board.

depends on which mode, face or phase one is in.

## Mode 1

Mode 1 is the default mode on power-on and displays the current time and related information. When the unit is first switched on a blip should be heard from the buzzer in sympathy with the incoming signal. This is useful for tuning purposes, as the receiver can be tuned until a clean blip (generally one a second) is heard.

After some time the blip will stop and the display will change from dashes to the correct time. The date information will take a further minute to appear. Now, assuming that you have waited this further minute, then pressing SW1 causes the display to change to date, month, and year. Press SW1 again and the day of week will appear on the left hand digit while the right hand digit will be either 'A' or 'P' (AM or PM). The middle two digits will contain letters 'AL'. This is the master buzzer enable/disable indicator. If while on this third face you press SW4 the letters 'AL' will begin to flash, indicating that the master alarm is enabled, ie any of the eight alarm settings will sound the buzzer of the preset time. With the master alarm disabled, none of the alarm settings will ever activate. Repeatedly pressing SW4 will toggle the master alarm between 'enabled' and 'disabled'.

Pressing SW1 once more will move on to face 4 which shows the amount of time in hours and minutes since the clock has switched to automatic back-up time. Normally this face will show

“00.00--” meaning that the clock is running on Rugby Time.

Pressing SW1 once more will move on to face 5 which shows the BST/GMT time difference information. L indicates 'lagging' while 'H' indicates 'leading'

Finally, pressing SW1 again will wrap round to face 1 to display the time. It is possible to do a quick return to face 1 from any face except face 3 by pressing SW4 twice. Pressing SW2 while face 1 is displayed will change from 12 to 24 hour display and vice-versa.

## Mode 2

In Mode 2 any one of eight alarms may be set to sound the buzzer and/or configure the state of the eight lines on port B. Each individual alarm can be enabled/disabled to sound the buzzer or alter the settings of the eight port lines.

From Mode 1, press SW4. The display will show 'AL', indicating the alarm mode. From here you can branch in any one of three directions depending on what you want to do. Let's call this point X. If you want to set an alarm time, from point X press SW3. The display will show a 1 on the right hand side indicating that the current alarm is alarm 1. The rest of the display will contain dashes, and the hour position will be flashing meaning that the hours will be the next unit to be set (like a digital watch). Pressing SW1 will advance the hours. Pressing SW2 will cause the minute 'tens' to flash. Similarly pressing SW1 will alter the minute tens. Pressing SW2 once more will advance to minute 'ones', and then wrap round to hours. SW3 will advance through the alarm

numbers and is effective from whichever state the 'setting' procedure is in.

To exit 'alarm set' mode at any time press SW4 which will turn the display back to time display. Press SW4 again to go back to point X. This time we want to enable the alarm we have just set to sound, so press SW1 and then press SW3 to the desired alarm number. Now press SW1; the 'A' will start to flash. If you also want to enable the alarm to alter the port lines, press SW2; 'P' will start flashing. Press SW4 to go to mode 1.

For the third branch from point X, press SW4 again and this time follow it by SW2. Press SW3 to advance to the desired alarm number, then press SW2 to advance to the required bit number. Pressing SW1 will cycle through -, H, L; refer to Fig. 3 for the significance of these letters. Once, again, to exit, press SW4.

When any of the set alarm times come up the buzzer should play a tune and the port lines will take up the state that was programmed. Anyone who dislikes the tune can get it changed for one of their choice by sending a good quality tape or a manuscript to the designer via Technomatic. Details of the charge for this service will be available from Technomatic.

When the tune starts playing, pressing SW4 will stop it. Pressing SW3 will start a 10 minute snooze delay after which the tune will play again. When the tune is playing SW4 and SW3 will perform these two functions no matter what mode, phase or face you happen to be in; the current meaning of those switches will be postponed for one key depression.

## Mode 3

This is the timer mode. It is entered by pressing SW5 (reset) and SW4 simultaneously, then releasing reset followed by SW4. The display will show both the colon and the decimal point. Pressing SW4 will start the count; pressing SW4 again will stop it. Pressing SW2 during the count will latch the current display. Repeated pressing of SW2 will latch (and store) up to 240 laps. Pressing SW1 will view the laps in store even while counting is in progress. Pressing SW3 will display the current count, if you happen to be viewing laps or have just latched a lap.

## Expansion

The board was built with expansion in mind, hence the 64-way connector which carries all important signals. We hope to publish useful add-ons in the future.

Next month we continue this project with the circuit diagrams and How It Works.

# HEMMINGS

16 BRAND ST.,  
HITCHIN,  
HERTS.  
SG5 1JE

# ELECTRONICS AND MICROCOMPUTERS

Tel: (0462) 33031  
Shop open Mon-Fri 9am-5.30pm  
Closed all day Wednesday  
24hr Ansaphone service



Professional quality components, brand new and fully guaranteed. Mail order by return of post. Cash/Cheque/P.O.s or Banker's Draft with order, payable to HEMMINGS ELECTRONICS LTD. Official orders from Schools, Colleges and Universities welcome. Trade and export enquiries welcome. P&P add 60p to all orders under £10. VAT — All prices are exclusive of VAT. Please add 15% to total cost including P&P. No VAT on export orders or books.

## ANTEX SOLDERING IRONS

CS230	480p
CS-8P	545p
SK5-BP	710p
X5-BP	555p
C240	480p
CN240	555p
Spare bits	85p
Element	200p
ST4 Stand	150p
1144 Sponge	20p

## DIL SOCKETS

Pins	Low Profile	Wire Wrap
8pin	10p	30p
14 pin	12p	38p
16 pin	12p	46p
18 pin	18p	—
20 pin	24p	60p
22 pin	25p	—
24 pin	25p	70p
28 pin	28p	95p
40 pin	30p	120p

## LED's

TIL209 Red	13p
LD37C Green	17p
0.2" Red	10p
0.2" Green, Yellow	18p
Panel Clips	4p
0.2" Square Red, Green, Yellow	30p
Red Flashing LED: 5V 3Hz	50p
Tri-Colour LED	85p

## EUROCARD CONNECTORS

DIN 41612 2 x 32 way	—
Socket	345p
Plug (Solder)	230p
Plug (W/Wrap)	325p

## TRANSFORMERS

2 x 15V @ 1A	395p
2 x 12V @ 1A	395p
2 x 30V @ 0.5A	395p
2 x 15V @ 0.5A	350p
2 x 6V @ 500mA	275p
2 x 12V @ 250mA	275p
2 x 20V @ 150mA	275p
2 x 6V @ 250mA	155p
2 x 12V @ 125mA	155p
2 x 15V @ 100mA	155p
2 x 20V @ 67mA	155p

## MEMORIES

2114-200ns	90p
2114-450ns	90p
2716-450ns	210p
2732-200ns	440p
4116-200ns	85p
4164-200ns	590p
6116-150ns	550p

## IC TEST CLIPS

14 pin	344p
16 pin	363p
20 pin	882p
24 pin	1080p
28 pin	1163p
40 pin	1804p

WE ALSO STOCK: Fuses, Cable, Meters, Resistors, Capacitors, Switches, Pots, Tools, Control knobs, Transistors, Many Vero and OK Tool products, Connectors, Boxes, Solder, Diodes, Wire Wrap equipment etc. Please phone for details or send S.A.E. for our current price list.

## NEW NEC PC8023B Dot Matrix Printer

100cps bidirectional logic seeking printer. Print types — condensed, enlarged, pica, elite, enhanced, proportional spacing, high res. and block graphics, true descenders. Centronics parallel interface.

**SPECIAL PRICE £385.00**

## EPSON MX80F/T PRINTER

TYPE I	£360.00
TYPE II	£380.00

## PRINCE 12" MONITOR

24MHz. Green or B/W display

**£98.50**

## C12 CASSETTES

300p/10	44p
---------	-----

## VIC-20 MICROCOMPUTER

VIC-20 CPU	£173.90
C2N Cassette Unit	£38.08
Printer	£200.00
Single Drive Floppy	£344.35
RS232C I/F Cartridge	£30.39
IEEE-488 I/F Cartridge	£47.39
3K Ram Cartridge	£25.04
8K Ram Cartridge	£30.09
16K Ram Cartridge	£65.17
Programmers Aid	£30.39
High Res. Cartridge	£30.39
Machine Code Monitor	£30.39
Joystick	£8.52
Paddles (1 pair)	£11.74
VIC Revealed	£10.00
VIC Reference Manual	£9.95
VIC Computing Magazine	£9.95
Games Cartridges	£17.35
Introduction to Basic (Part 1)	£14.95

## FLOPPY DISCS

Soft Sector 5 1/4"	£19.50/10
SSSD	£25.50/10
DSDD	£25.50/10

BBC MICROCOMPUTER. Please phone for details of RAM expansion, printer and monitor interface cables etc.

74LS TTL	LS133	LS352	4023	16p	4508	240p
LS000	LS137	LS353	4023U	16p	4510	75p
LS01	LS138	LS365A	4024	55p	4511	75p
LS02	LS139	LS366A	4025	18p	4512	75p
LS03	LS140	LS367A	4026	37p	4513	180p
LS04	LS141	LS368A	4027	37p	4514	180p
LS05	LS142	LS372	4028	48p	4515	180p
LS08	LS143	LS374	4029	60p	4516	90p
LS09	LS144	LS375	4030	120p	4517	290p
LS10	LS145	LS377	4031	165p	4518	56p
LS11	LS146	LS378	4032	120p	4519	35p
LS12	LS147	LS379	4033	90p	4520	80p
LS13	LS148	LS385	4040	58p	4521	195p
LS14	LS149	LS386	4042	62p	4522	110p
LS15	LS150	LS390	4043	70p	4523	110p
LS20	LS151	LS393	4044	70p	4524	110p
LS21	LS152	LS395	4046	65p	4528	90p
LS22	LS153	LS398	4049U	28p	4529	120p
LS26	LS154	LS399	4050	28p	4530	90p
LS27	LS155	LS400	4051	72p	4531	90p
LS28	LS156	LS401	4052	72p	4532	120p
LS30	LS157	LS402	4053	480p	4534	480p
LS32	LS158	LS403	4060	90p	4536	290p
LS33	LS159	LS404	4066	105p	4538	105p
LS39	LS160	LS405	4068	18p	4539	105p
LS38	LS161	LS406	4069U	18p	4541	110p
LS40	LS162	LS407	4070	20p	4543	120p
LS42	LS163	LS408	4071	20p	4544	175p
LS47	LS164	LS409	4072	20p	4547	130p
LS48	LS165	LS410	4073	20p	4549	380p
LS49	LS166	LS411	4074	20p	4551	105p
LS51	LS167	LS412	4075	20p	4553	295p
LS54	LS168	LS413	4076	20p	4554	165p
LS55	LS169	LS414	4077	20p	4555	70p
LS56	LS170	LS415	4078	20p	4556	75p
LS57A	LS171	LS416	4081	20p	4557	260p
LS74A	LS172	LS417	4082	20p	4558	125p
LS75	LS173	LS418	4093	40p	4559	410p
LS76A	LS174	LS419	4094	120p	4560	180p
LS77	LS175	LS420	4099	180p	4561	100p
LS78A	LS176	LS421	4100	14p	4562	385p
LS83A	LS177	LS422	4101U	14p	4566	165p
LS84	LS178	LS423	4102	14p	4568	280p
LS85	LS179	LS424	4103	80p	4569	170p
LS86	LS180	LS425	4104	80p	4570	38p
LS89	LS181	LS426	4105	100p	4572U	38p
LS91	LS182	LS427	4106	480p	4580	395p
LS92	LS183	LS428	4107	480p	4581	240p
LS93	LS184	LS429	4108	39p	4582	65p
LS95B	LS185	LS430	4109	39p	4583	105p
LS107A	LS186	LS431	4110	16p	4447	390p
LS109A	LS187	LS432	4111	33p	4493	320p
LS112A	LS188	LS433	4112	33p	4494	320p
LS113A	LS189	LS434	4113	33p	4495	320p
LS114A	LS190	LS435	4114	33p	4496	320p
LS122	LS191	LS436	4115	33p	4497	320p
LS123	LS192	LS437	4116	33p	4498	320p
LS125A	LS193	LS438	4117	33p	4499	320p
LS126A	LS194	LS439	4118	33p	4501	320p
LS132	LS195	LS440	4119	33p	4502	320p
		LS441	4120	33p	4503	60p
		LS442	4121	33p	4504	100p
		LS443	4122	33p	4506	680p

## COMPUTER

6800	450p
6801	450p
6802	395p
6809	955p
6809E	1495p
6809E	1295p
6810	150p
6821	160p
6829	1335p
6840	410p
6840	620p
6844	1295p
6845	75p
6850	165p
6852	250p
6854	795p
6875	490p
8726A	140p
8795	105p
8796	105p
8797	105p
8798	105p
8799	105p
8728	140p
8080A	360p
8085A	595p
8154	1000p
8155	880p
8205	242p
8259	170p
8216	70p
8224	200p
8226	275p
8228	250p
8243	495p
8250	320p
8251	320p
8253	300p
8255	300p
8257	800p
8259	800p
8279	950p
MC1408	295p
MC1488	60p
MC1489	60p
MC3459	285p
75491	80p
75492	80p
280ACPU	440p
280APIO	340p
280ACTC	340p
280ADART	750p
2N4444	125p

## LINEAR ICs

709	35p
709	35p

## NEW

TL061	40p
TL062	60p
TL064	98p
TL071	30p
TL072	50p
TL074	100p
TL075	25p
TL082	45p
TL084	95p
TL084	95p

## SCR

BT106	150p
BT116	175p
C106D	45p
TIC44	30p
TIC45	30p
2N5062	30p
2N5064	30p
2N4444	125p

## Triacs

TIC205D	55p
T2800D	95p

# HAPPY MEMORIES

Part type	1 off	25-29	100 up
4116 200ns	0.83	0.72	0.66
4116 250ns	0.75	0.65	0.60
4816 100ns For BBC comp	2.95	2.70	2.50
4164 200ns	6.15	5.25	4.65
2114 200ns Low power	1.15	1.00	0.90
2114 450ns Low power	0.95	0.85	0.80
4118 250ns	3.25	2.85	2.65
6116 150ns CMOS	4.25	3.65	3.35
2708 450ns	2.60	2.25	2.10
2716 450ns 5 volt	2.60	2.25	2.10
2716 450ns three rail	5.75	5.00	4.65
2732 450ns Intel type	3.95	3.45	3.25
2532 450ns Texas type	3.95	3.45	3.25

Z80A-CPU £4.35 Z80A-PIO £3.25 Z80A-CTC £3.25  
6522 PIA £3.98 7805 res 0.50 7812 res 0.50

Low profile IC sockets:  
Pins 8 14 16 18 20 22 24 28 40  
Pence 9 10 11 14 15 18 19 25 33

Soft-sectored floppy discs per 10 in plastic library case: 5 inch SSSD £17.00; 5 inch SSDD £19.25; 5 inch DSDD £21.00; 8 inch SSSD £19.25; 8 inch SSDD £23.65; 8 inch DSDD £25.50

74LS series TTL, large stocks at low prices with DIY discounts starting at a mix of just 25 pieces. Write or phone for list.


Please add 30p post & packing to orders under £15 and VAT to total. Access & Barclaycard welcome. 24 hour service on (054 422) 618. Government & Educational orders welcome, £15 minimum. Trade accounts operated, phone or write for details.

# HAPPY MEMORIES (ETI)

Gladestry, Kinston, Herefordshire HR5 3NY  
Telephone: (054 422) 618 or 628

# Constructor Series Speakers

IT'S SO EASY

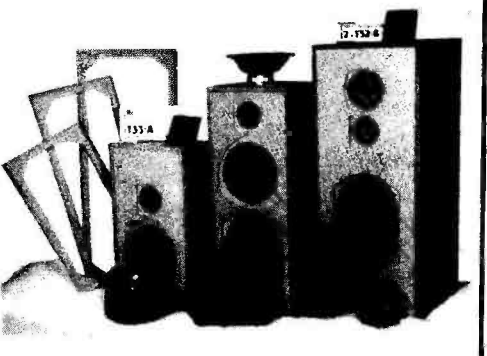

Have fun, save money, building a Kef design with a Wilmslow Audio CS Total kit. No electronic or woodworking knowledge necessary and the end result is a proven top-quality design that you'll be proud of.

Each kit contains all cabinet components, accurately machined for easy assembly, speaker drive units, crossovers, wadding, grille fabric, terminals, nuts, bolts, etc. The cabinets can be painted or stained or finished with iron-on veneer or self adhesive woodgrain vinyl. Easy foolproof assembly instructions supplied. Set of constructor leaflets sent free on receipt of large S.A.E.

Prices: CS1 (B110B/T27A)	£110 pr. inc. VAT, plus carr./ins. £ 5
CS1A (B110A/T27A)	£103 pr. inc. VAT, plus carr./ins. £ 5
CS3 (B200G/T33A)	£129 pr. inc. VAT, plus carr./ins. £10
CS5 (B200G/BD139B/T33A)	£192 pr. inc. VAT, plus carr./ins. £15
CS7 (B139B/B110B/T33A)	£250 pr. inc. VAT, plus carr./ins. £15






# NICADS : UK's LOWEST PRICES

AMBIT'S NEW CONCISE COMPONENT CATALOGUE IS OUT NOW -

Price on the page

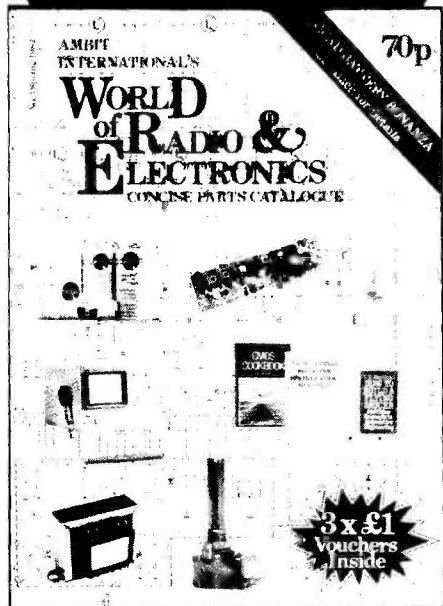

Ambit's new style catalogue continues to lead the market with low prices, new items, info, 3 x £1 discount vouchers. Here's a few examples of some super low prices:

- 78XX 1A 37p
- BC237/8/9 8p
- 3SK51 54p
- 10MHz XTALS £2
- 8 Pole 10.7MHz XTAL filters £14.50
- 2GHz coax relay 150W £10.95

+ all the usual stuff at rock bottom prices + Toko coils, crystal and ceramic filters, micrometals toroids, Fairite ferrites, Alps switches, OKI LSI, Piezo sounders, RF, IF Modules + Kits etc.

Available at your newsagent or direct, for 70p inc.

RECHARGE UP TO 300 TIMES PER CELL!

CAPACITY	TYPE	1-9	10-49
500 mAh	AA	80	74
2200 mAh	C	2.35	1.99
1200 mAh	D	2.14	2.06
4000 mAh	D	3.05	2.85
110 mAh	PP3	3.70	3.50

Prices shown EXCLUDE VAT. Access/Barclaycard may be used with written or telephone orders, official MA details on application. E & EO.  
**POSTAGE and PACKING** 50p per order

**AMBIT international** TELEPHONE STD 0277 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG  
200 North Service Road, Brentwood, Essex


## HENRY'S COMPUTER KIT DIVISION

404 EDGWARE RD, LONDON W2 1ED TEL: 01-402 6822

• TANGERINE • TANGERINE • TANGERINE
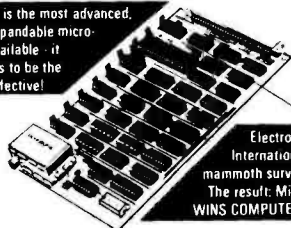
### MICROTAN 65

Microtan 65 is the most advanced, powerful, expandable micro-computer available - it also happens to be the most cost effective!



Electronic Today International held a mammoth survey of kits. The result: Microtan 65 WINS COMPUTER CLASS!

#### MICROTAN 65 CONTENTS

High quality plated thru hole printed circuit board, solder resist and silk screened component identification 8502 microprocessor 1K monitor TANBUG Now with 'V' Bug 1K RAM for user programme, stack and display memory, VDU alphanumeric display of 16 rows by 32 characters, MICROTAN 65 system file binder 136 page, bound, users hardware/software manual with constructional details and sample programmes. Logic and discrete components to fully expand MICROTAN 65.

The MICROTAN 65 kit has won widespread acclaim for its superb presentation. We pay attention to detail -

Kit Form **£69.00** + £10.35 VAT, total £79.35

MICROTAN 65 assembled and tested. Specification as above, but assembled and fully bench tested by ourselves **£79.00** + £11.85 VAT, total £90.85

YOU MAY DEDUCT **£10** FROM MICROTAN 65 KITS AND ASSEMBLED UNITS LISTED HERE ONLY FROM US DELIVERY EX-STOCK POST PAID

Limited Quantity Available

## WRONG TIME?

**MSF CLOCK** is ALWAYS CORRECT - never gains or loses, SELF SETTING at switch-on, 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, can expand to Years, Months, Weekdays and Milliseconds, also STOPCLOCK and parallel BCD output for computer or alarm, receives Rugby 60KHz atomic time signals, built-in antenna, 1000Km range, GET the RIGHT TIME, £69-60.  
**60KHZ RUGBY RECEIVER**, as in MSF Clock, serial data output, decoding details and ZX81 listing for local, GMT and SIDEREAL time, £22-20.

Each fun-to-build kit includes all parts, printed circuit, case, postage etc, instructions, money back guarantee so GET yours NOW.

### CAMBRIDGE KITS

45 (TH) Old School Lane, Milton, Cambridge

#### PARNDON ELECTRONICS LTD.

Dept. No. 23, 44 Paddock Mead, Harlow, Essex CM18 7RR. Tel. 0279 32700

**RESISTORS:** 1/4 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/coloured and colour coded  
**£1.00** per hundred mixed (Min 10 per value)  
**£8.50** per thousand mixed (Min 50 per value)  
Special stock pack 60 values 10 off each **£5.50**


**DIODES:** **1N4148** 3p each. Min order quantity 15 items  
**£1.60** per hundred

**DIL SWITCHES:** Gold plated contact in fully sealed case - solve those programming problems  
4 Way **86p** each 6 Way **£1.00** each 8 Way **£1.20** each

**DIL SOCKETS:** High quality, low profile sockets  
8 pin - 10p. 14 pin - 11p. 16 pin - 12p. 18 pin - 19p. 20 pin - 21p.  
22 pin - 23p. 24 pin - 25p. 28 pin - 27p. 40 pin - 42p.

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE



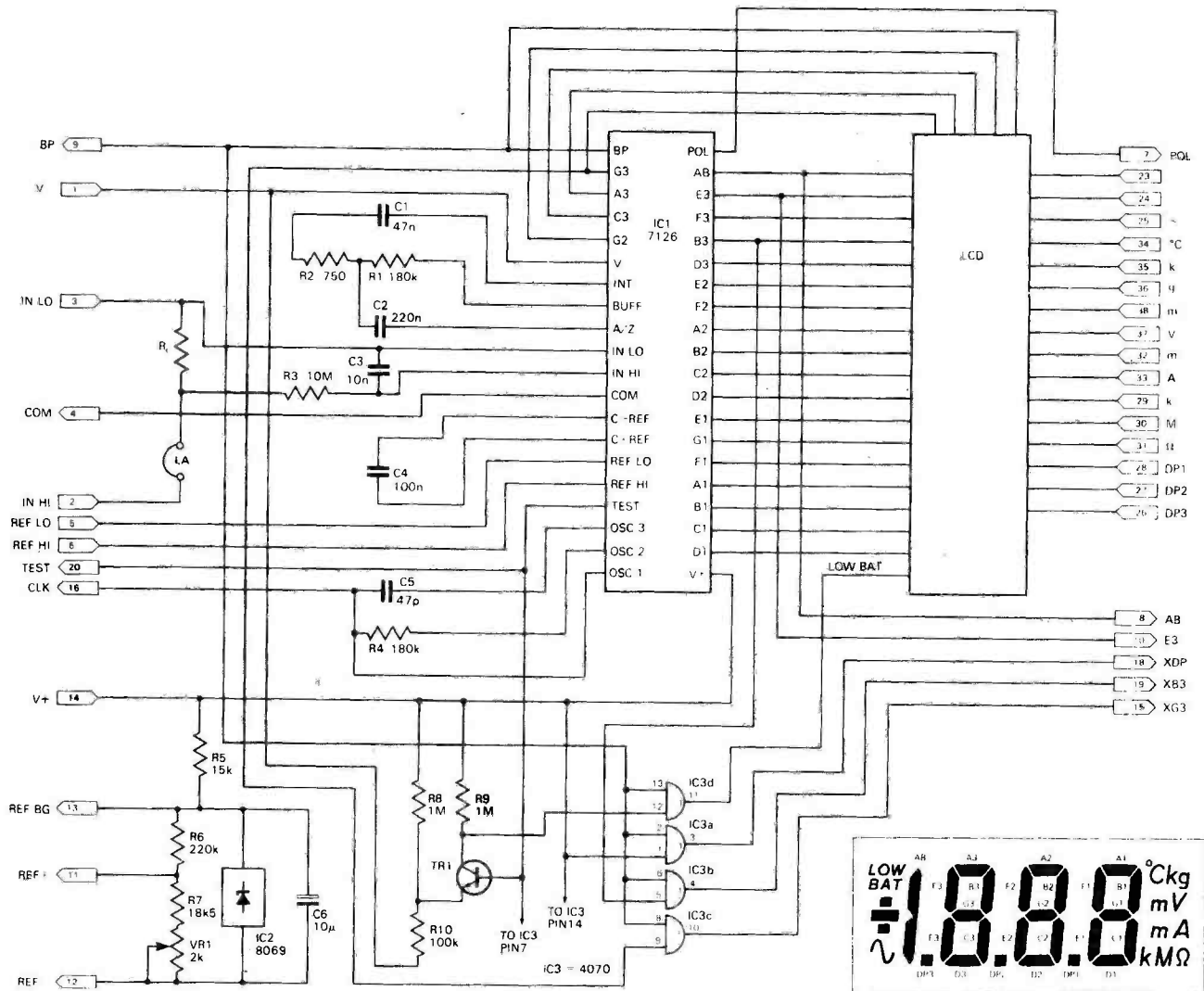

**Fig. 3** Circuit diagram of the module. R1, R2 and C1 determine the integrator time constant and C2 reduces the susceptibility to noise of the auto-zero circuitry. The display is guaranteed to read zero when the analogue input is 0 V. An input filter formed by R3 and C3 assists with overload protection for the 7126 IC. The input voltage may exceed the

supply voltage provided the input current does not exceed 100  $\mu$ A. The frequency of the internal oscillator is determined by R4 and C5 and provides three samples per second typically. The module is calibrated by means of VR1 for a full scale reading of 200 mV with link LA in circuit and resistor R<sub>c</sub> omitted.

number of unexpected bonuses for the designer. A square wave clock signal, an extra negative supply rail, a bandgap precision voltage reference, a common rail for op-amp references, plus four logic signals for autoranging meter circuits — all these signals are available for use in external circuits. Table 1 charts the pin numbers in numerical order with their symbols and basic functions.

## Supply Rails

The module can be operated from a single supply between 5 V and 15 V across pins 1 and 14, at a current of 100  $\mu$ A, using the bandgap reference. However, the internal reference can be used instead, reducing the current to 50  $\mu$ A with a minimum voltage of 7 V. A low battery warning indicator is set to come on at 6V4, determined by the R8/R10 potential divider. R10 can be altered if required; 220k gives a 7V2 warning.

## Legends/Annunciators

The symbols can be enabled very easily by directly connecting the XDP output on pin 18 (an inverted backplane

signal) to the required segment. This may also be done via logic or switches for automatic selection of the decimal points.

## Inputs

Pins 2 and 3 are the non-inverting and inverting inputs respectively; these analogue inputs are truly differential and may be operated to within 0V5 below the positive supply and 1 V above the negative supply. Common mode rejection ratio within this range is typically 86 dB.

## Voltage References

The Analogue Common pin is included primarily to set the common mode voltage for battery operation or for any system where the input signals are floating with respect to the power supply. The common pin sets a voltage that is approximately 2V8 more negative than the positive supply. This is selected to give a minimum end-of-life battery voltage of about 6 V. However, the analogue common has some of the attributes of a reference voltage. When the total supply voltage is large enough to cause the zener to regulate (greater than 7 V) the common voltage will

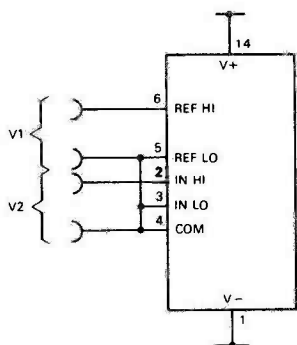


Fig. 4 Measuring the ratio of two voltages. The maximum input voltage is  $\pm 2$  V with a 9 V supply.

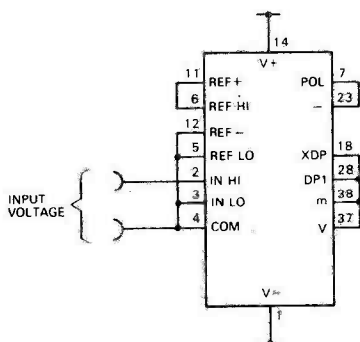


Fig. 5 Measuring a floating voltage source with 200 mV full scale. Autopolarity indication is implemented, together with the decimal point and mV annunciation.

TABLE 2			
	REQUIRED FSD	LA	$R_c$
IN HI	2 V	10M	1M0
	20 V	10M	100k
IN LO	200 V	10M	10k
	2000 V	10M	1k0
IN HI	200 $\mu$ A	LINK	1k0
	2 mA	LINK	100R
	20 mA	LINK	10R
	200 mA	LINK	1R

have a low voltage coefficient (0.001%), low output impedance (about 15R), and a temperature coefficient typically less than 800 ppm/ $^{\circ}$ C.

The analogue-to-digital converter of the IC operates in a ratiometric mode, such that the digital display is  $1000 V_2/V_1$ , as shown in the diagram of Fig. 4. Here, the inverting inputs of the reference and voltage inputs are both connected to common (REF LO and IN LO). REF HI is normally connected to the 100 mV bandgap reference from REF + as shown in Fig. 5, thus giving the 200 mV full-scale deflection. Output REF + is 100 mV with respect to REF - when the latter is correctly terminated. REF BG is 1V2 with respect to REF -. REF - should normally connect to the COM terminal as the diagram indicates.

To alter the full-scale reading of the DVM module, the link LA and resistor  $R_c$  shown in the circuit of Fig. 3 should be altered. Table 2 shows the values required for several ranges of current and voltage.

## Outputs

The polarity output on pin 7 is a square wave in-phase with the backplane signal when the analogue input has positive polarity and in anti-phase when the input has negative polarity. It can be connected directly to the “-” symbol (pin 23) for normal

polarity indication. The clock on pin 16 may be used for systems timing or as an input to override the internal oscillator and control the sample rate. If CLK is connected to V - the display may be held at a particular value but this should not be connected for extended periods as the steady DC potential applied to the LCD may cause the segments to “burn”.

The oscillator frequency is divided by four before it clocks the decade counters. It is then further divided to form the three convert-cycle phases. These are signal integrate (1000 counts), reference de-integrate (0 to 2000 counts) and auto-zero (1000 to 3000 counts). For signals less than full scale, auto-zero gets the unused portion of reference de-integrate. This makes a complete measure cycle of 4000 (16000 clock pulses) independent of input voltage.

An oscillator frequency of 48 kHz is used for three readings per second.

## Test

The test pin serves two functions. It is coupled to the internally generated digital ground through a 500R resistor (digital ground is set at approximately 5 V below +V). Thus when operated from a single battery supply, TEST can be used as the 0 V rail for externally generated segment drivers, such as decimal points (or any other presentation the user may want to include on the LCD display), or it may be used as a common mode reference level to ensure compatibility with most op-amps.

If TEST is connected to V + the LCD segments will be turned on and the display will read as shown in Fig. 6 (This mode should not be used for extended periods, to avoid damage to the LCD).



Fig. 6 The display when in the “TEST” condition.

SPECIFICATION	
Input impedance:	>100M
Full scale reading:	199.9 mV
Accuracy:	0.05% of reading $\pm 1$ digit
Power supply:	5 - 15V DC
Power consumption:	50 $\mu$ A (in low power mode), typically 8,000 hours PP3 life
Sample rate:	3 readings per second
Auto-zero:	No necessity to adjust for offsets
Auto-polarity:	Automatic polarity indication eliminates the need to reverse input leads to obtain correct reading.
Overrange warning:	1 in leading digit with other digits suppressed
Bandgap reference (50 ppm/ $^{\circ}$ C typ.)	incorporated for excellent stability of reading
Digit height:	15 mm (0.6") can be read at distances up to 10 metres
Low battery warning:	direct display, voltage threshold easily adjusted
Operating temperature:	0 $^{\circ}$ C to 50 $^{\circ}$ C
Overall dimensions:	72 x 36 x 12 mm
Panel cut-out:	68 x 33 mm
Display annunciators:	many useful legends are built into the custom LCD which may be activated as required
Auto-zero	With the inputs shorted, the display should read zero, the negative sign being displayed about 50% of the time
Overrange:	Inputs greater than full scale will cause suppression of the three least significant digits, i.e. only 1 or -1 will be displayed
Polarity	The absence of a polarity sign indicates a positive input reading. A negative input is indicated by a negative sign.

# ETI PCB SERVICE

Up until now PCBs were always the hardest component to obtain for a project. Of course you could make your own, but why bother anymore?

Now you can buy your boards straight from the designers — us! As of this issue all (non-copyright) PCBs will be available automatically from the ETI PCB Service. Each board is produced from the same master used to build our prototypes, so you can be sure it's accurate, and will be finished to the high standard you would expect from ETI.

In addition to the PCBs for this month's projects, we are making available some of the more popular designs from our recent past. See the list below for details. Please note that **NO OTHER BOARDS ARE AVAILABLE**. If it's not listed, we don't have it!

<b>APRIL 79</b>	<input type="checkbox"/> Guitar Effects Unit	£2.64	<b>APRIL 81</b>	<input type="checkbox"/> Musical Box	£2.64	<b>FEBRUARY 82</b>	<input type="checkbox"/> Ripple Monitor	£2.08
	<input type="checkbox"/> Click Eliminator	£6.64		<input type="checkbox"/> Drum Machine (two boards)	£5.60		<input type="checkbox"/> Pest Monitor	£1.85
<b>JUNE 79</b>	<input type="checkbox"/> Accentuated Beat Metronome	£3.60		<input type="checkbox"/> Guitar Note Expander	£3.20		<input type="checkbox"/> I Ching Computer (two boards)	£5.31
<b>FEBRUARY 80</b>	<input type="checkbox"/> Tuning Fork	£2.64	<b>JUNE 81</b>	<input type="checkbox"/> Mini-drill Speed Controller	£2.93		<input type="checkbox"/> Moving-magnet stage	£3.80
<b>MARCH 80</b>	<input type="checkbox"/> Signal Tracer	£2.27		<input type="checkbox"/> Antenna Extender	£3.20		<input type="checkbox"/> Moving-coil stage	£3.80
<b>AUGUST 80</b>	<input type="checkbox"/> CMOS Logic Tester	£2.64		<input type="checkbox"/> Alien Attack	£2.64	<b>APRIL 82</b>	<input type="checkbox"/> Contrast Meter	£2.83
	<input type="checkbox"/> Capacitance Meter	£2.93		<input type="checkbox"/> LED Jewellery: Cross	£1.47		<input type="checkbox"/> Sound Effects board	£2.40
	<input type="checkbox"/> Ultrasonic Burglar Alarm	£2.87		<input type="checkbox"/> Spiral (two boards)	£2.64		<input type="checkbox"/> High Impedance Probe	£1.97
<b>OCTOBER 80</b>	<input type="checkbox"/> Cassette Interface	£2.93		<input type="checkbox"/> Star (two boards)	£2.65		<input type="checkbox"/> Guitar Practice Amp	£7.57
	<input type="checkbox"/> Fuzz/Sustain Box	£3.27		<input type="checkbox"/> Waa-phase	£1.53		<input type="checkbox"/> Accurate Voltage Monitor	£2.05
<b>NOVEMBER 80</b>	<input type="checkbox"/> Touch Buzzer	£1.93	<b>JULY 80</b>	<input type="checkbox"/> System A A-MM/A-MC	£2.65	<b>MAY 82</b>	<input type="checkbox"/> DV Meg	£2.92
	<input type="checkbox"/> Light Switch	£1.93		<input type="checkbox"/> System A A-PR	£5.17		<input type="checkbox"/> Analogue PWM	£3.37
	<input type="checkbox"/> Metronome	£1.93		<input type="checkbox"/> Smart Battery Charger	£1.97		<input type="checkbox"/> Slot Car Controller	£4.96
	<input type="checkbox"/> 2W Power Amp	£1.93	<b>AUGUST 81</b>	<input type="checkbox"/> System A Power Amp (A-PA)	£4.77		<input type="checkbox"/> Wattmiser	£4.53
	<input type="checkbox"/> RIAA Pre-amplifier	£1.93		<input type="checkbox"/> Flash Sequencer	£3.44		<input type="checkbox"/> Sound Effects Board	£2.40
	<input type="checkbox"/> Audio Test Oscillator	£3.13		<input type="checkbox"/> Hand-clap Synthesiser	£3.97	<b>June 82</b>	<input type="checkbox"/> Ion Generator (two boards)	£6.22
<b>DECEMBER 80</b>	<input type="checkbox"/> Musical Doorbell	£2.80		<input type="checkbox"/> Heartbeat Monitor	£1.83		<input type="checkbox"/> Ion 'Blinker'	£2.60
	<input type="checkbox"/> Bench Amplifier	£2.53		<input type="checkbox"/> Watchdog Home Security (two boards)	£5.31		<input type="checkbox"/> MOSFET Amp Module	£6.99
	<input type="checkbox"/> Four Input Mixer	£2.64	<b>SEPTEMBER 81</b>	<input type="checkbox"/> Laboratory PSU	£4.53		<input type="checkbox"/> Logic Lock	£3.41
<b>JANUARY 81</b>	<input type="checkbox"/> LED Tacho	£4.13		<input type="checkbox"/> Mains Audio Link (three boards)	£7.35		<input type="checkbox"/> Digital PWM	£3.84
	<input type="checkbox"/> Multi-Option Siren	£3.20		<input type="checkbox"/> Enlarger Timer	£3.40		<input type="checkbox"/> Optical Sensor	£1.98
	<input type="checkbox"/> Universal Timer	£3.31	<b>OCTOBER 81</b>	<input type="checkbox"/> Sound Bender	£2.65		<input type="checkbox"/> Stylus Timer	£2.98
<b>FEBRUARY 81</b>	<input type="checkbox"/> Infra-red Alarm (four boards)	£6.64		<input type="checkbox"/> Thermal Alarm	£2.63		<input type="checkbox"/> Oscilloscope (four boards)	£13.19
	<input type="checkbox"/> Pulse Generator	£3.57		<input type="checkbox"/> Micropower Pendulum	£2.21	<b>JULY 82</b>	<input type="checkbox"/> Mike Switching Unit	£2.04
<b>MARCH 81</b>	<input type="checkbox"/> Engineer's Stethoscope	£2.65	<b>NOVEMBER 81</b>	<input type="checkbox"/> Music Processor	£7.35		<input type="checkbox"/> TV Bargraph (main board)	£4.85
				<input type="checkbox"/> Voice-Over Unit	£3.97		<input type="checkbox"/> TV Bargraph (channel card)	£2.44
				<input type="checkbox"/> Car Alarm	£2.81		<input type="checkbox"/> Hotwire	£2.99
				<input type="checkbox"/> Phone Bell Shifter	£2.96		<input type="checkbox"/> Bridging Adaptor	£2.74
						<b>AUGUST 82</b>	<input type="checkbox"/> Playmate (three boards)	£7.92
							<input type="checkbox"/> Kitchen Scales	£2.70
							<input type="checkbox"/> Sound Track	£4.38

**How to order:** indicate the boards required by ticking the boxes and send this page, together with your payment, to: ETI PCB Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2H 0EE. Make cheques payable to ETI PCB Service. Payment in sterling only please. Prices may be subject to change without notice.

Total for boards: £ . . . . .  
 Add 45p p&p                    0.45  
 Total enclosed                   £ . . . . .

I wish to pay by Access/Barclaycard. Please debit my account

BARCLAYCARD

VISA

5	2	2	4																
4	9	2	9																

Signed . . . . .  
 Name . . . . .  
 Address . . . . .



## POWER DIMMER MODULES

A range of electronic modular dimmers designed to suit your custom channel and facility requirement

- Considerable saving over commercial equipment
- All the commercial facilities and more
- Compatible special effects
- Preset/remote/master
- Easily installed and wired

SPC — Simple but effective 1000W controller.....	£15.70
SPU — Used in conjunction with RS units for Remote desks in 1000 and 2000W versions.....	£23.90 (2K)
MC — Master dimmer for SPC/RS units.....	£7.90
RS — Remote controller for SPU/SPC Units.....	£9.40
SUP/REF — Supply/signals for up to 50 modules.....	£20.00
Discounts on above only (order £100 to £199 15% £200 to £299 20% £300+ 25%)	
<b>EFFECTS ACCESSORIES</b>	
MXSL — Four channel sound to light.....	£36.90
MXLS — Four Channel Sequencer.....	£23.70
MXLC-S Four channel sound chaser.....	£26.70
PSU — Supply for MX.....	£7.20

### 3 CHANNEL SOUND/LIGHT CHASER £35.70 LB31000SLC



A high performance sound to light providing bass, mid and treble separation, employing active filters. Automatic switching to chase in the absence of a music signal 1000W/chan

### 4 CHANNEL SEQUENCER LB41000LS

£19.20

A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

### 3 CHANNEL SOUND/LIGHT LB31000SL



£22.70

All the advantages of the SLC without chase. Controls: bass/mid/treble/master sensitivity.

#### BLUE FASCIAS (White letters)

Type	Knobs	Leds	Sw	Price
MULTI	5	4	1	9.70
41000SLC	2	4	1	9.20
31000SLC	5	—	1	8.70
31000SL	4	—	1	7.70

Don't hesitate to write or phone for immediate information. All prices include VAT. Please include 75p post except power dimmer (£1.75). Cheques/PO/C.O.D./

Access all welcome  
TEL: 01-889 4138 (Mon to Fri 9-5)

L & B ELECTRONIC 45 Wortley Road, W. Croydon, Surrey CR0 3EB


OPEN FRAME MONITORS AVAILABLE FOR OEM'S

## The 'PRINCE' of Monitors

offers better Monitoring.

24MHz Bandwidth—ensures a clear crisp display.

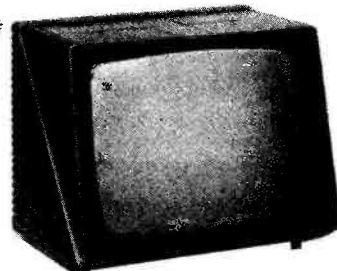Available with P4 White P31 Green AND L1 ORANGE




Scan: 625 lines/50 Hz. Deflection: 110°. Active raster: 240 x 172mm. Bandwidth (3dB): 10 Hz-24 MHz (at 3dB points). Character display: 80 characters x 24 lines. Horizontal frequency: 15625 Hz ± 0.5 KHz. Vertical frequency: 50 Hz. Horizontal linearity: ± 3%. Vertical linearity: ± 2%. Geometric distortion: ± 1.5%. EHT (at zero beam current): 13kV ± 0.5kV. Power drain: 30 Watt approx. Voltage supply: 110V A.C. 50 Hz/220V A.C. — 50 Hz/240V A.C. 50Hz/ ± 10% upon request. Video Input: 2 x BNC — or CINC — or PL 259. (Composite video) negative sync. input 0.5-4V p.p. across 75 Ohms. X Ray radiation: conforms to I.E.C. Spec. No. 65. Overall dimensions: 320 x 270 x 265 mm. Weight: 7 Kg. approx. Ambient temperature: 0-45°C.

OTHER CROFTON PRODUCTS INCLUDE: Computer peripheral equipment, Frame grabber, Floppy disk drives, Floppy disks, Computer power supplies, C.C.T.V. monitors, Uncased monitors, Monitor P.C.B.'s, Cathode ray tubes, VHF/UHF modulators, Video switchers, Video distribution amplifiers, Camera housings, Pan and tilt units, Camera lens, Camera tubes, Printed circuit board service.


### CROFTON ELECTRONICS LTD

35, Grosvenor Road, Twickenham, Middx, TW1 4AD.  
Telephone: 01-891 1923/1513 Telex: 295093 CROFTN G

## SC110 FULLY PORTABLE OSCILLOSCOPE

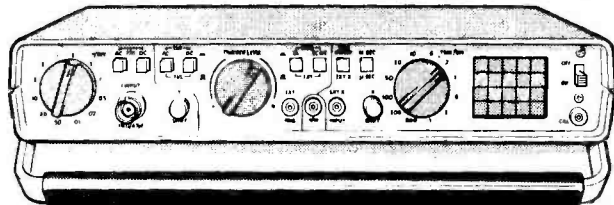

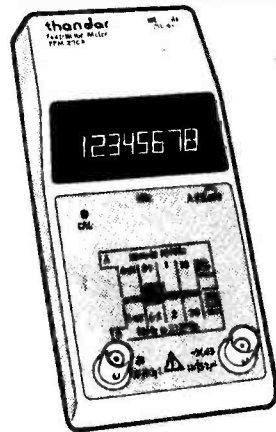The new THANDAR SC110 represents a break through in Oscilloscope development. The SC110 is only 2" thick and weighs under 2 lbs yet it retains the standard features of a bench oscilloscope.



#### FULL-SIZED PERFORMANCE

- 10MHz band width
  - 10mV per div. sensitivity
  - Full trigger facilities are provided including bright line and auto, with T.V. line and frame filtering
  - RUNS ON ORDINARY HP11 (four) batteries or rechargeables
  - Basic price — £159 UK Post free
- Optional extras —  
AC Adaptor £5.69; Rechargeable batteries £8.63; X1 Probe £8.05; X10 Probe £9.20; X1/X10 Switched Probe £10.90; Carry Case £8.86.

#### PFM200A FREQUENCY METER

- Pocket size ● 8-Digit LED display ● Frequency range 20Hz-200MHz ● Resolution 0.1Hz ● Sensitivity typically 10mV rms
  - Timebase accuracy 2ppm ● Battery life 10 hours ● Frequency: 2 ranges, 4 gate times
  - Price £67.50 UK Post free
- Optional extras — AC Adaptor £5.69

LARGE 25p S.A.E. Brings details of: Oscilloscopes, Frequency Meters, Signal Generators, Function Generators, Pulse Generators, Analogue and Digital Multimeters, Digital Thermometer, C.R.T. Tester, Logic Analyser etc.

All prices include VAT. Official orders welcome. Mail order only, or callers by prior appointment. Barclaycard/Access welcome. Cash/cheque, etc., with order. Government and Educational Establishments official orders welcome.

### B.K. ELECTRONICS

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY  
Tel: Southend 527572



# ALARMS

## DIY KITS 'N' BITS

PROFESSIONAL EQUIPMENT AT DISCOUNT PRICES!

- KITS £32, £50, £75, £85 including full instructions ● CONTROL PANELS £18, £23, £29, £37 ● BELL BOXES £6.25, £7.50 ● PRESSURE PADS £1.06, £1.45, £2.45 ● 4 CORE CABLE (100m) £8 ● SIRENS £7.50 ● CONTACTS 72p, 74p, 76p ● ULTRASONIC £34.50 ● DOOR PHONES £49.42 ●

### BUY A KIT OR DESIGN YOUR OWN SYSTEM

SEND SAE OR PHONE NOW FOR FREE FULLY ILLUSTRATED CATALOGUE. IT TELLS YOU ALL YOU NEED TO KNOW!

Carriage Included. VAT Extra 15%

A. D. Electronics, Dept ET1 7, 217 Warbrick Moor, Aintree, Liverpool L9 0HV 051 523 8440

Trade Enquiries Welcome

## AMARAL Limited

26 HIGHFIELDS, EARLEY, READING RG6 2RZ, ENGLAND

Tel: National 0734 864745; International + 44 734 864745

Access or Barclaycard Add VAT 15% 50p p&p, Mail Orders / Tel orders only

Send SAE for complete list

- CMOS — 4001 15p; 4002 15p; 4006 52p; 4011 15p; 4012 15p; 4013 25p; 4016 26p; 4017 45p; 4020 53p; 4022 47p; 4023 15p; 4024 40p; 4025 15p; 4027 25p; 4028 60p; 4029 60p; 4040 50p; 4046 47p; 4046 67p; 4049 25p; 4050 25p; 4051 52p; 4052 52p; 4053 47p; 4060 76p; 4066 31p; 4068 15p; 4069 15p; 4070 15p; 4076 56p; 4081 15p; 4082 15p; 4085 39p; 4086 39p; 4511 57p; 4518 59p; 4520 57p; 4543 87p; 4555 43p; 40106 17p.
- 74LS — 00 12p; 02 13p; 04 14p; 08 14p; 10 13p; 11 14p; 14 47p; 20 13p; 21 15p; 27 15p; 28 18p; 30 13p; 32 13p; 40 13p; 42 40p; 73 24p; 74 22p; 76 24p; 85 71p; 86 17p; 90 39p; 93 44p; 112 23p; 123 60p; 126 31p; 132 40p; 138 38p; 139 36p; 153 47p; 155 47p; 157 37p; 164 55p; 166 116p; 173 53p; 174 37p; 175 37p; 193 63p; 221 60p; 240 83p; 241 83p; 244 73p; 245 90p; 251 46p; 253 51p; 257 44p; 279 39p; 283 46p; 366 39p; 367 39p; 373 81p; 374 79p; 393 60p.
- MICROS ETC — Z80CPU 345p; Z80ACPU 395p; Z80CTC 295p; Z80ACTC 295p; Z80P10 340p; Z80AP10 370p; 8085 375p; 8085A 525p; MC1488 58p; MC1489 58p.
- CRYSTALS — 3.6864 125p; 4.0000 125p; 6.144 125p.
- SPECIAL OFFER — Buy a Micro from us and get a crystal for 75p.
- IC SOCKETS — 14 pin 8p; 16 pin 8p; 18 pin 12p; 24 pin 18p; 28 pin 24p; 40 pin 28p.
- REGULATORS — T.O. 220 Type - 7805 38p; 7812 38p; 7815 38p.

# electronics today international BOOK SERVICE

How to order: indicate the books required by ticking the boxes and send this page, together with your payment, to: ETI Book Service, Argus Specialist Publications Ltd, 145 Charing Cross Road, London WC2 0EE. Make cheques payable to ETI Book Service. Payment in sterling only please. All prices include P & P. Prices may be subject to change without notice.

## BEGINNERS

- Beginners Guide to Electronics** Squires £4.50
- Beginners Guide to Transistors** Reddihough £4.50
- Beginners Guide to Integrated Circuits** Sinclair £4.50
- Beginners Guide to Radio** King £4.50
- Beginners Guide to Audio** Sinclair £4.50
- Introducing Amateur Electronics** Sinclair £4.50
- Introducing Microprocessors** £5.20
- Understanding Electronic Circuits** Sinclair £5.30
- Understanding Electronic Components** Sinclair £5.30

## APPLICATIONS COOKBOOKS

- TV Typewriters Cookbook** £9.35
  - CMOS Cookbook** £9.85
  - Active Filter Cookbook** £11.30
  - IC Timer Cookbook** £8.65
  - IC Op-Amp Cookbook** £12.20
  - ITL Cookbook** £9.15
  - MC 6809 Cookbook** Carl D. Warren £5.30
  - PLL Synthesiser Cookbook** Kinley £5.85
  - 8085A Cookbook** Titus £10.75
- 
- How To Build Electronic Kits** Chapel £3.45
  - 110 Electronic Alarm Projects** Marston £5.25
  - 110 Semiconductor Projects for the Home Constructor** Marston £5.25
  - 110 Integrated Circuit Projects for the Home Constructor** Marston £5.25
  - 110 Thyristor Projects Using SCRs** Marston £5.25
  - 110 Waveform Generator Projects** Marston £5.25
  - 99 Practical Electronic Projects** Friedman £4.20

## COMPUTING & MICROPROCESSORS

- What is a Microprocessor?** 2 cassette tapes plus a 72-page book £10.00
- Beginners Guide to Computers and Microprocessors** with projects £6.05
- Basic Computer Games** Ahl £6.05
- Basic for Home Computers** Albrecht £6.60
- Illustrating Basic** Alcock £4.25
- Troubleshooting Microprocessors and Digital Logic** Goodman £6.10
- Z-80 Microcomputer Handbook** £9.35
- Microprocessors in Instruments and Control** Bibbero £15.30
- Basic Basic** Coan £9.95
- Advanced Basic** Coan £9.95
- 1001 Things to do with your Personal Computer** Sawusch £6.00
- Microcomputers, Microprocessors, Hardware, Software and Applications** Hilburn £17.40
- Microprocessor Systems Design** Klingman £21.95
- Introduction to Microprocessors** Leventhal £11.25
- Microprocessor Technology, Architecture and Applications** £11.30
- Basic with Style** Nagin £6.30
- Microcomputer Design** Ogdin £9.25
- Hands on Basic with a PET** Peckham £11.95
- 6800 Software Gourmet Guide and Cookbook** Scelbi £9.30
- 8080 Software Gourmet Guide and Cookbook** £9.30
- The 8080A Bugbook** Rony £10.05
- 8080/8085 Software Design** Titus £10.05
- How to Design, Build and Program your own Working Computer System** £7.10
- Your Own Computer** Waite £2.25
- Microcomputer Interfacing Handbook A/D & D/A** £6.35
- Crash Course in Microcomputers** Frenzel £14.95
- Musical Applications of Microprocessors** Chamberlain £20.95
- The Pascal Handbook** Tiberghien £12.45
- 50 Basic Exercises** Lamotier £11.10
- Learning Basic with the Sinclair ZX80** £4.95
- Microprocessors for Hobbyists** Coles £4.25
- Introduction to Microcomputer Programming** Sanderson £5.25

- Microprocessors and Microcomputers for Engineering Students and Technicians** Woolland £5.95
- Using CP/M – Self Teaching Guide** Ashley Fernandez £6.95
- Digital Counter Handbook** Frenzel £8.65
- 33 Challenging Computer Games for TRS80-Apple-Pet** Chance £5.75
- How to Build Your Own Working Robot Pet** Dalesta £5.75
- Microprocessor and Digital Computer Technology** £16.00
- Guidebook to Small Computers** Barden £4.20
- How to Debug Your Personal Computer** Huffman £6.30
- How to Troubleshoot and Repair Microcomputers** Leuk £6.30
- 6809 Microcomputer Programmes and Interfacing with Experiments** Staugaard £11.45
- Wordprocessors Programmed. Training Guide with Practical Application** £
- Digital Circuits and Microcomputers** Johnson £9.75
- Experiments in Artificial Intelligence for Small Computers** £7.25

## TEST

- The Oscilloscope In Use** Sinclair NEW EDITION 1982
- How to Get More Out of Low-cost Electronic Test Equipment** Tobery £5.50

## THEORY

- Digital Signal Processing. Theory and Applications** Rabiner £26.40
- Electronic Communication Systems** Kennedy £8.95
- Principles of Communication Systems** Taub £8.40
- Introduction to Digital Filtering** Bognor £13.30
- Transistor Circuit Design** Texas Instruments £10.95
- Electronic Circuit Design Handbook** Design of active filters, with experiments: Berlin £6.80

## REFERENCE

- Electronic Engineers Reference Book** Turner £42.00
- Electronic Components** Colwell £4.00
- Electronic Diagrams** Colwell £4.00
- International Transistor Selector** Towers New £10.70
- International FET Selector** Towers £4.60
- International Op-Amp Linear IC Selector** Towers £8.00
- International Microprocessor Selector** Towers £16.00
- Dictionary of Audio – Radio and Video** Roberts £16.00
- Dictionary of Electronics** Amos £16.00
- Dictionary of Electrical Engineering** Amos £16.00
- Dictionary of Telecommunications** Amos £16.00
- Giant Book of Electronic Circuits** Collins £12.75
- World Radio/TV Handbook Vol. 35 1981** £10.50
- How to Build Electronic Projects** Malcolm £6.45
- Modern Electronic Circuit Reference Manual** Marcus £33.50

Please send me the books indicated. I enclose cheque/postal order for £.....

I wish to pay by Access/Barclaycard. Please debit my account.

5	2	2	4																	
4	9	2	9																	

Signed .....

Name .....

Address .....

# SOUND TRACK

Play it again (and again, and again), SAM!  
When you feel like working off your aggressions, try to zap the nasties as they fly past. Design and development by Phil Walker.

The ETI Sound Track is an 'arcade' game you can carry in your pocket. It requires no special displays as all the cues are sounds. The object of the game is to intercept all 15 of the attackers with your own armament. In order to do this you have to judge the best moment to fire from the simulated sound of the attacker. It is made more realistic by the fact that both volume and frequency changes due to Doppler shift are included. As the game progresses the speed of the attack increases to prevent you getting too used to one pace. Also there are three levels of skill which determine how difficult it is to hit the attackers at all.

At the end of the game, if enough of the attackers have been intercepted, an LED will light up to

give an assessment of your performance. As an option, an aiming control can be fitted, if space permits, which will allow multiple shots if you are quick enough. To start the game, press the reset button and wait for the first attack. Now it's up to you. Bear in mind that your shots are effective only at the end of the shooting noise and while the target light is on.

## The Circuit



The circuit for this project uses standard op-amps, CMOS counters and gates and a special sound effects IC. This allows us to make fairly realistic sounds to simulate an object flying past, some sort of weapon being fired and an explosion if a successful interception has been

made. In order to make the completed project hand-held, the PCB is fairly crowded but quite a lot has been put onto it.

The heart of the system is a voltage controlled oscillator operating at a frequency of less than 0.2 Hz. This provides two outputs; one is an asymmetrical triangle wave which controls the attack sound effect and simulates the position of the target while the other output is a logic signal to drive the score counters. The VCO frequency is modified by the attack counter such that the attacks proceed more rapidly as the game progresses.

The fire control section of the circuit produces two signals. The first of these is a long pulse which causes the shooting sound to be made by the sound generator. The second, immediately after, is a short pulse which enables the hit detector. If at the same time the ramp from the VCO is within the limits of the window discriminator in the hit detector, then a HIT will be registered and the HIT counter updated. At the same time the sound generator will be switched to provide an explosion effect.

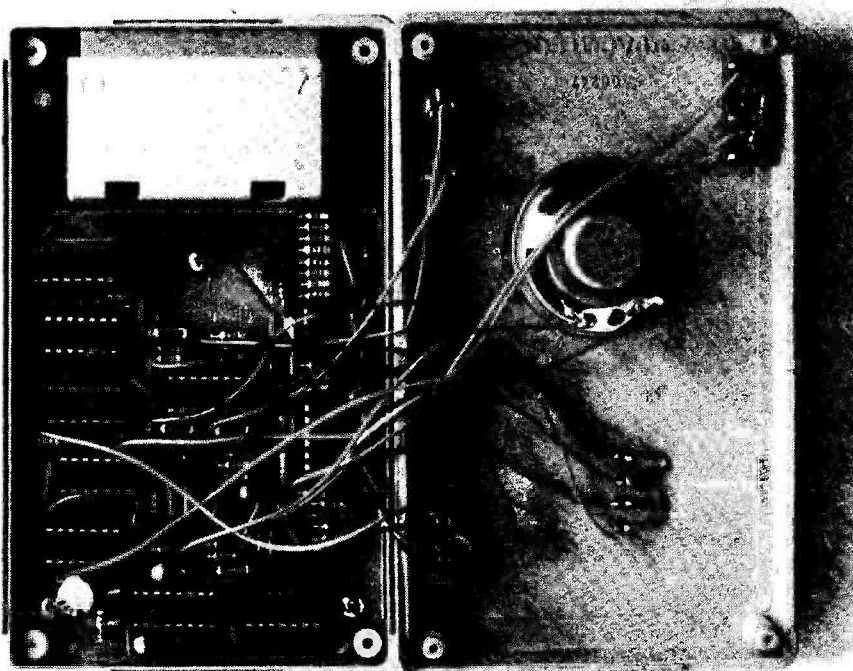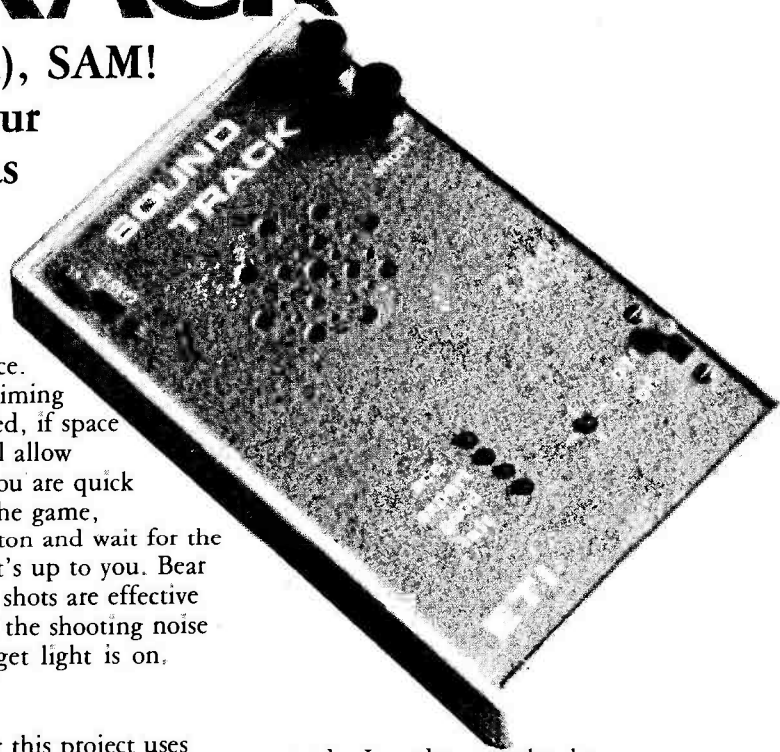The sound select logic and analogue control switching (in the absence of any other demand) will





assume an attack sequence and configure the sound generator to give a mixture of white noise and a tone. As the ramp voltage from the VCO falls, simulating an attack, the volume will increase to a maximum and then decrease again. Simultaneously, as the volume reaches its peak, the pitch of the tone will decrease rapidly and stabilise at a lower level to simulate Doppler shift. While the ramp voltage returns to its starting level the sound generator is inhibited.

If either shooting or explosion effects are demanded, these will take precedence over the attack sound. The explosion is produced by envelope-shaping the white noise source in the chip while the shooting sound is given by an audio frequency VCO, frequency-modulated by a much lower frequency triangle wave.

The display given by the LEDs is to give some indication of the number of successful interceptions made in a game. The first LED will light when eight out of the 15 attacks have been stopped. The next will light at 12, then 14, and finally 15. There is one other LED which flashes each time a HIT is possible, but note that the shoot button usually has to be pressed before it lights.

## Construction

No major problems should be encountered in making this project; care must be taken when soldering the board as there are many places where tracks run between IC pins. Make sure that all the links are in

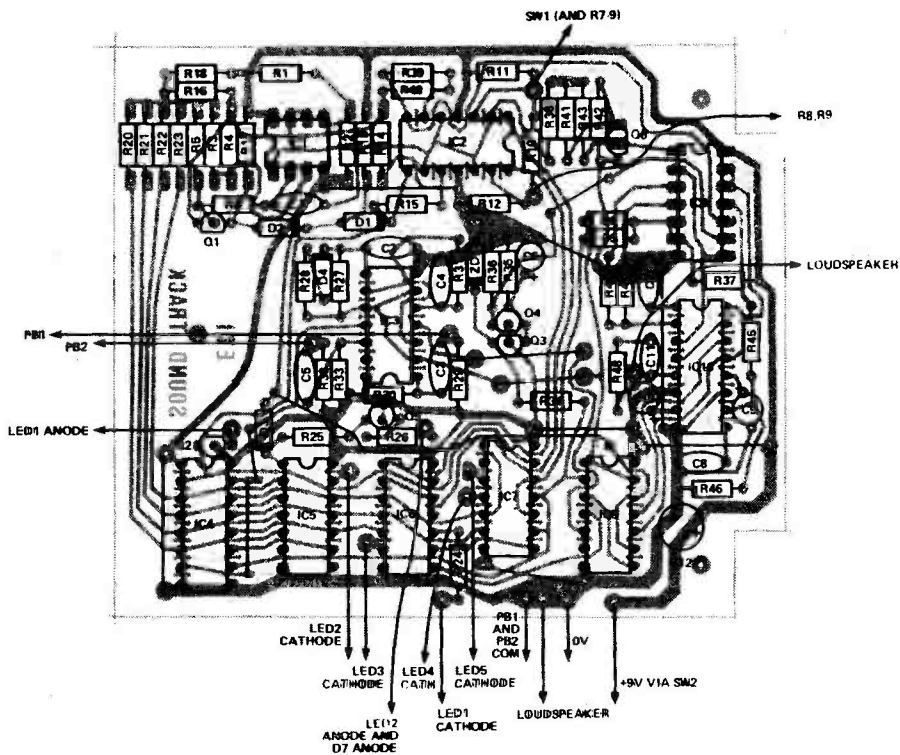


Fig. 1 Component overlay for the Sound track hand-held 'arcade' game. Note that some components are mounted off-board; see the photographs.

place and that diodes, ICs and polarised capacitors are the right way round. Low profile IC sockets may be used but the case we used may then be a little tight.

SW1, R6 and R7 were mounted so that they fitted beside the battery compartment on one side while PB1 and PB2 went the other side. The LEDs are mounted on the front of the box so that they poke through the panel; use a little glue to hold them in place. Some interconnection work

and components have to be put on to these (D7-10) and this should be kept as close to the panel as possible. If there is room, fit RV1 and R7 but this will only be possible if a very small potentiometer is available or a different box is used.

All interwiring should be carried out using thin flexible wire and kept as short as practicable. When fixing the loudspeaker check first that it will fit in the desired position and adjust fixing pillars etc. to ensure this. It is

## PARTS LIST

### Resistors (all 1/4W, 5%)

R1,2,4,12,39	100k
R3,5,6,22,29,30	
R31,32,33,35	1M0
R7,15	220k
R8,46	6k8
R9,10,42	15k
R11,41	82k
R21,27	2M2
R14,23	470k
R16	180k
R17,19,37	27k
R18	150k
R20	4M7
R25	47k
R24,26,38	1k0
R28,48	10k
R34,36	22k
R40	3k3
R43	4k7

R44	1k5
R45	68k
R47	12k
R13	is not used
Potentiometer	
RV1	100k linear
Capacitors	
C1,8	100n polycarbonate
C2	220n polycarbonate
C3,5	4n7 ceramic
C4,11	1n0 ceramic
C6	2u2 16 V tantalum
C7	10n ceramic
C8	68n polycarbonate
C9,10	10u 10 V PCB electrolytic
C12	100u 10 V PCB electrolytic

### Semiconductors

IC1	TL082
IC2	TL084
IC3	4093B
IC4	4520B

IC5	4012B
IC6	4023B
IC7,8	4011B
IC9	4066B
IC10	SN76495 (see Buylines)
Q1,2,3,4,6	BC182L
Q5	BC212L
D1-10	1N4148
ZD1	5V6 400 mW zener
LED1,3,4,5	Green miniature LED
LED2	Red miniature LED
Miscellaneous	
SW1	miniature 3-position slide switch
PB1,2	miniature push-to-make push-button
SW2	miniature slide switch (on/off)

Case (Pac-tec type HP); PP3 battery and connector; knob for pot; loudspeaker (1" dia, 8 ohm) — see Buylines; PCB (see Buylines).

# PROJECT : Sound Track

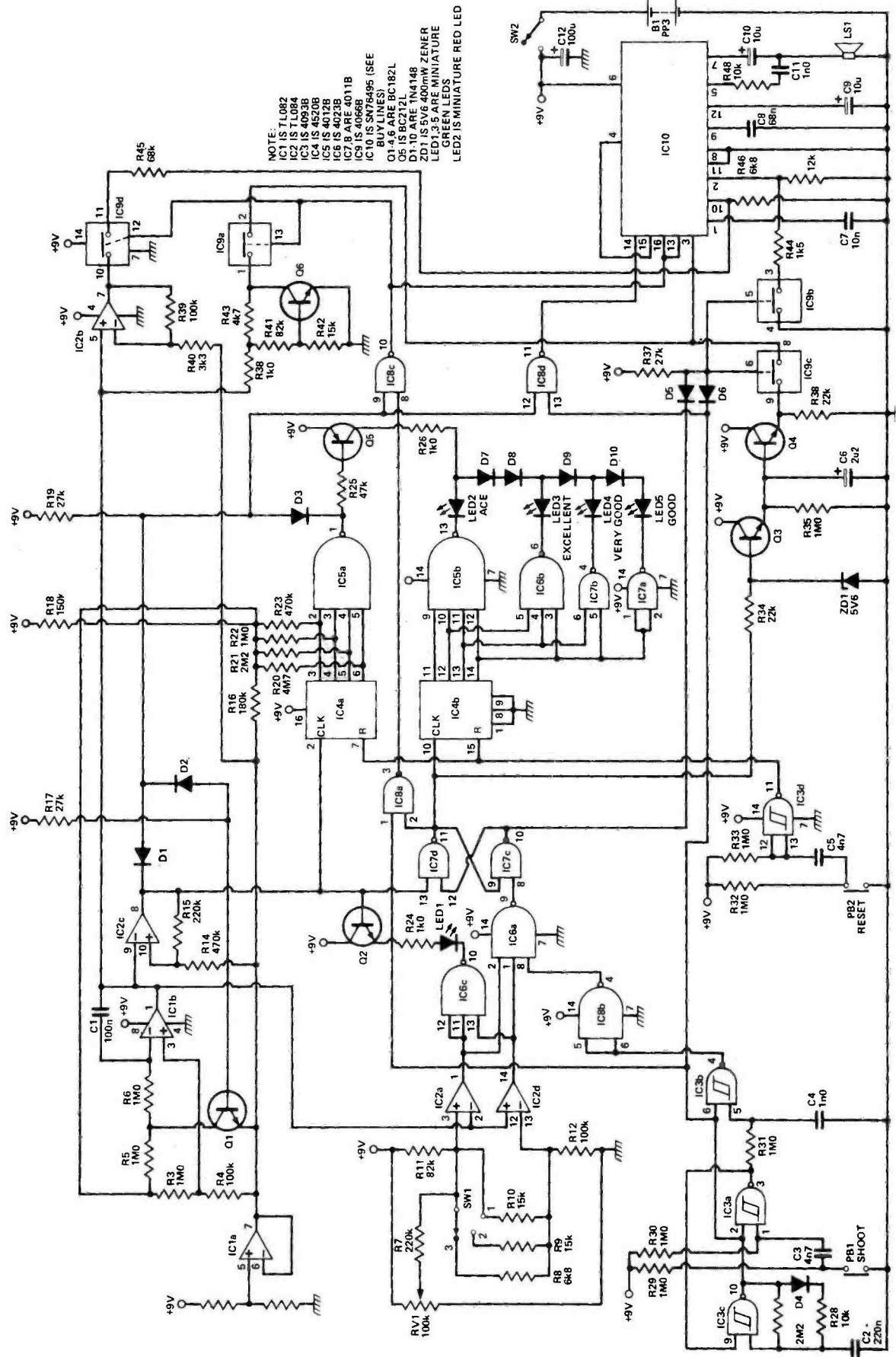


Fig. 2 Circuit diagram for the Sound Track.

## HOW IT WORKS

IC1b buffers the voltage at the junction of R1 and R2 to give a reference at half the supply. IC1a and IC2c form a very low frequency voltage controlled oscillator. R20-23 make a simple D-to-A converter which varies the VCO frequency by a small amount as the game progresses. The timing for the whole game is derived from the VCO and provision is made by D1-3 to stop the circuit oscillating when the required 15 attacks have been counted by IC5a.

IC2a and IC2d form a window comparator whose position and width can be varied by RV1 and SW1. IC3a and IC3c are connected as a monostable and are triggered by PB1 being closed. C3 ensures that the period of the monostable is not affected by further closures of PB1. When the monostable time ends, IC3b is enabled for a short time determined by R31 and C4. This signal is inverted by IC8b and is applied with the outputs from the window comparator circuit to IC6a. If all the inputs to this IC are high at the same time this signifies a "HIT" and the output of IC6a will go low. This action causes the latch formed by IC7c and IC7d to be set with IC7c output high. The resulting low on IC4b clock input increments that counter, increasing the score, while further counting on the same attack run is prevented by the latch action in IC7c/d. IC5b, 6b, 7b and 7d decode the outputs from IC4b to give a

suitable display on the LEDs when Q5 is enabled by IC5a at the end of the game. IC3d is used to debounce the reset switch PB2 and the circuit at its input ensures that only a short pulse is available at its output.

The analogue control signals for the sound generator chip IC10 are produced in three parts and switched into circuit when required by IC9. The control signals for IC9 and IC10 are derived by IC8a, 8c, 8d and an AND gate made up of D6, D5, and R37.

The analogue control signals are produced individually. The Doppler style fall in frequency as each attack progresses is produced by IC2b. This device has a fairly high gain and at the start of the attack its output is driven to the positive rail by the ramp output from the VCO. As the ramp voltage falls past the reference voltage the output of IC2b will change from positive to negative quickly (but not instantaneously). If there is no other sound required at the time this output will modulate the oscillator in IC10 via R45.


Another effect required to simulate an object passing is that the noise produced by it will first increase and then decrease. This is accomplished by the circuit around Q6. At high voltages Q6 will be fully on and the output is low. At low voltages Q6 will be off but the output will again be low. As the voltage applied to the circuit increases, until the voltage on the base of Q6 is sufficient

to make it conduct) the output voltage will be the same as the input. When, however, Q6 starts to conduct, the junction of R38, R41, and R43 will stay at a constant potential. The reason for this is that as the input voltage rises, more current will flow into the circuit via R38. A small amount of this will go through R41 to drive Q6 further into conduction, drawing the rest out via R43. This action will continue until the voltage across Q6 is virtually zero again. The output from Q6 drives the volume control pin of IC10 via IC9a.

The last effect is of a decaying explosion. While IC10 will produce the noise of the explosion, the decay envelope has to be generated by Q3 and Q4. Most of the time the base of Q3 is held at 5V6 by the output of IC7d (part of the "HIT" latch). In the event of a "HIT" being registered, the base of Q3 will now be driven low. C6, which previously was held at about 5V by Q3, will start to discharge via R35. The voltage on C6 is buffered by Q4 and fed to IC10 by IC9c. Also for the explosion effect, R44 is connected into circuit by IC9b. This changes the noise slightly to give a more realistic sound. C11 and R48 are included in the amplifier circuit feedback to give more prominence to the mid-frequencies and cut down on the hiss effect of the digital generation of the various noises.

intended that it fits with part of the cone overlapping the battery compartment so a little shaving with a sharp knife may be required. When the speaker position is known, drill a series of holes in the panel and glue it into position.

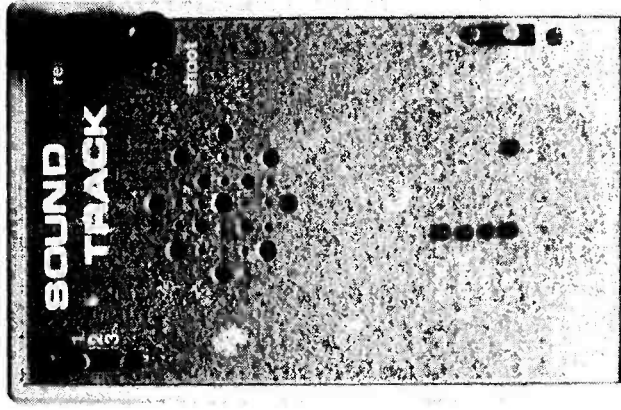The wiring may now be completed and the box assembled to finish the project. Fit a PP3 battery to the connectors and it should be ready.



The on-off switch, SW2, is mounted on the front panel at the bottom right-hand side such that it will be over R38, 41-43.

## BUYLINES

Not too much here that's hard to find. The sound generator chip is one of the latest ones from the Texas Instruments range, so it should be available from TI stockists such as Technomatic and Watford Electronics. The Pac-tec case is available from Watford or direct from OK Machine and Tool Ltd, 22 Dutton Lane, Eastleigh, Hants. The speaker is type R3812 from Henry's Radio, while the PCB is available from us via our PCB Service (see page 69).

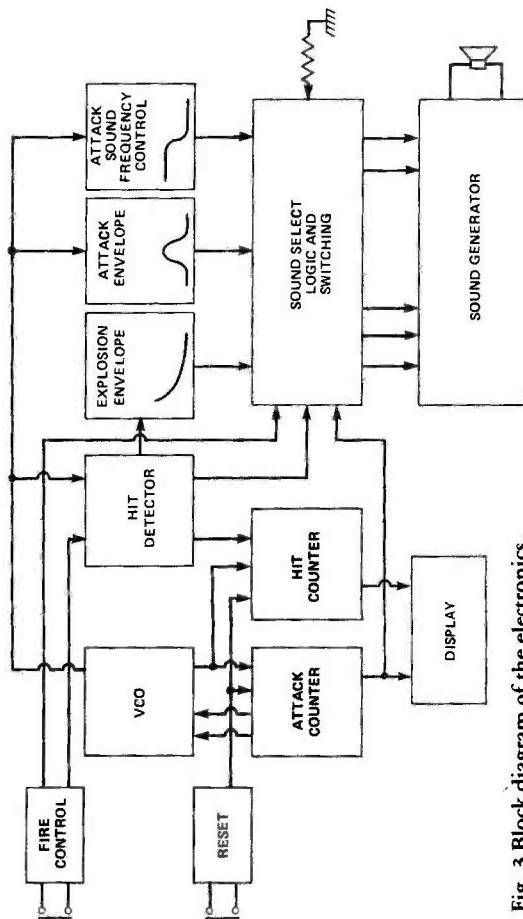


Fig. 3 Block diagram of the electronics.

MAKE IT WITH  
BRADLEY

# Marshall's

OF LONDON

SPECIALIST ELECTRONIC COMPONENT DISTRIBUTORS  
Tel: 723-4242

**PROBABLY THE LARGEST STOCK OF ICs & TRANSISTORS IN THE SOUTH TRY US FIRST**

**LARGE RANGE OF ACCESSORIES**

Plugs  
Sockets  
Audio Connectors  
Veroboard  
IC Sockets  
Soldering equipment  
Screw drivers  
(BAHCO)  
Sifam Knobs  
etc.

**LARGE RANGE OF ICs**

Transistors  
Capacitors  
Diodes  
Triacs  
Thyristors  
Opto  
Resistors  
Potentiometers  
Fuses  
Bridges

Please send S.A.E. for list.

**SPECIAL OFFER**  
STEINAL  
MULTICHECK  
£7.50  
+ VAT  
Normal price £10.26

**BUY WITH ACCESS BARCLAYCARD A/EXPRESS DINERS**

Just phone we do the rest

**MAIL ORDER FASTER SERVICE PHONE**  
723-4242

**40 WAY RIBBON CABLE £2.20 metre**  
Header plugs 14 way,  
16 way, 40 way

**BAHCO TOOLS SIDE CUTTERS**

2132 £7.10  
2112 £9.00

**END CUTTERS**  
2211 £10.43

**PLIERS**

2411 £6.75  
2415 £6.78

**ICE MULTIMETERS**

Microtest 80 £16.60  
Supertest 680 R £32.00  
Supertest 680E £24.50

**EXPERIMENTER BREADBOARD'S**

EXP 325 EXP 600  
EXP 350 EXP 650  
EXP 300 EXP 4B

**LOGIC PROBES**

LP1 £31.00  
LP2 £18.00

**EXPERIMENTER KITS**

PB6 £9.20  
PB100 £11.80

PLEASE REMEMBER  
To ADD 15% VAT

325 EGWARE ROAD LONDON W2 1BN

BARCLAYCARD \* ACCESS \* DINERS \* A/EXPRESS

## HOME CONSTRUCTOR TURNTABLE KITS

from

## INPUT DESIGN LTD

THE LEADING MANUFACTURERS OF  
TURNTABLES IN KIT FORM

NORMAL RETAIL PRICE £49.50

**SPECIAL INTRODUCTORY OFFER TO READERS OF ETI**

**£44**

inc VAT  
(P & P £1.95)

This kit includes AC Synchronous motor (as used on £350 decks), Pulley, Belt, Drive Hub, Spindle, Bearing, Glass Platter, Felt Mat, Switch, Electronics, Cable and full instructions together with blueprint for plinth assembly.

Any other parts (ie Lid) available as optional extras.

**5 YEAR GUARANTEE - MONEY BACK IF NOT SATISFIED**

Pay by Barclaycard, Access or CWO. Export: Write for Pro-forma.



**INPUT DESIGN LTD**

Victoria House, Shortmead Street,

Biggleswade, Beds. SG18 0AP

Telephone: Biggleswade (0767) 316655 Telex: S26671



*Bigger and Better for 1982*  
the colourful Wilmslow Audio brochure  
- the definitive loudspeaker catalogue!

Everything for the speaker constructor - kits, drive units, components for HiFi and PA.

50 DIY HiFi speaker designs including the exciting new dB Total Concept speaker kits, the Kef Constructor range, Wharfedale Speakercraft, etc.

Flatpack cabinet kits for Kef, Wharfedale and many others.

★ Lowest prices — Largest stocks ★

★ Expert staff — Sound advice ★

★ Choose your DIY HiFi Speakers in the comfort of our ★  
two listening lounges

(Customer operated demonstration facilities)

★ Ample parking ★

Send £1.50 for catalogue  
(cheque, M.O. or stamps - or phone with your credit card number)

★ Access - Visa - American Express accepted ★  
also HiFi Markets Budget Card.



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders!



## SUMMERTIME SALE! DEDUCT 20% OFF ALL ORDERS OVER £10 FROM THIS ADVERTISEMENT

All prices include VAT at 15% - just add 50p post

1982/3 CATALOGUE

ELECTRO-DIAL

- Bigger! Better! Buy one!!  
Only 75p inc. post - Look what you get!!
- Vouchers worth 60p
  - 1st class reply paid envelope
  - Wholesale list for bulk buyers
  - Bargain List with hundreds of surplus lines
  - Huge range of components
  - Low, low prices

Sent free to schools, colleges etc.

**SOLENOIDS AND RELAYS**

W921 Solenoid rated 48V at 25% duty cycle, but work well on 24V (700gm pull, 10mm travel) push or pull 27 x 18 x 15mm 65p.

W922 Mains 240V ac solenoid, 10% duty cycle, push or pull, 16mm travel. 50 x 20 x 16mm. Only £1.50

W895 9V DC relay 500R SPCO 28 x 24 x 19.50 50p

W733 11 pin plug in relay, 240V ac, 3PCO 5A contacts £2.50. Base £36p

W838 700R 24V 4PCD "continental" relay 35 x 30 x 18, only 84p; 10/£7.00

W847 37R 5-10V relay, SP 3A contact, PCB mntg 11 x 33 x 20. 95p; 10/£7.50

W893 Omron LY4 mains relay, 4PCO 5A contacts. £2.50

W896 24V ac coil, but works well on 6V DC. 2 x 10A c/o contacts. Ex-equip, only 60p

**PACKS PACKS PACKS**

K517 Transistor Pack. 50 assorted full spec marked plastic devices PNP NPN RF AF. Type numbers include BC114, 117, 172, 182, 183, 198, 239, 251, 214, 255, 320, BF198, 255, 394, 2N3904 etc. Retail cost £7+. Special low price 275p

K520 Switch Pack. 20 different assorted switches - rocker, slide, push, rotary, toggle, micro etc. Amazing value at only 200p

K522 Copper clad board. All pieces too small for our etching kits. Mostly double sided fibreglass. 250g (approx 110 sq ins) for 100p

Vero outfits. This has been restricted for some time, but we have now built up a reasonable stock and can once again offer 100 sq ins of vero copper clad outfits, average size 4 x 3". Offered at around 1/2 the price of a new board 320p



Electrical combination lock for maximum security, absolutely pick-proof!! One million combinations!! Dial is turned to the right to one number, left to a second number, then right again to a third number. Only when this has been completed in the correct sequence will the electrical contacts close. These can be used to operate a relay or solenoid etc. Overall dia 65mm x 60mm deep. Finished in bright chrome. With combination the price is £9.95. Also available without combination, but instructions are provided on how to find it. Takes about 20mins £2.95

**'COMPUTER BATTLESHIPS'**

Probably one of the most popular electronic games on the market. Unfortunately the design makes it impractical to test the PCB as a working model, although it may well function perfectly. Instead we have tested the sound chip, and sell the board for its component value only (PCB may be chipped or cracked): SN76477 sound IC; TMS1000 u processor; batt clips, R's, C's etc. Size 160 x 140mm. Only £1.50. Instruction book and circuit 30p extra.

**10W AMP PANEL**

Neat board 115 x 62mm with Class B output. Uses 2 x 2N5293, 2 x BFY50 BFX29. Supply can be either 36V or 18-0-18V

Input sensitivity 1V for 10W output. Small H/S on board. £2.95. Suitable transformer, bridge rect, smoothing and o/p capacitor: size 4 x 3". Offered at around 1/2 the price of a new board 320p

## GREENWELD

443A Millbrook Road Southampton SO1 0HX



# DATA SHEET

The HOS-100 high speed, bipolar, voltage follower/buffer amplifier is designed to provide high current drive at frequencies from D.C. to 125MHz. Featuring a slew rate of 1400V/ $\mu$ s, output drive of  $\pm 10$ mA into 1K $\Omega$  loads, excellent phase linearity ( $2^\circ$ ) and low distortion (<0.1%).

Ideal for wide range for buffer applications including high impedance input buffers for fast A to D convertors and comparators, coaxial cable drivers, yoke drivers in high resolution CRT displays etc.

## Features

- Wide Bandwidth - d.c. to 125MHz
- High Slew Rate - 1400V/ $\mu$ s
- Operating Temperature Range  $-25^\circ\text{C}$  to  $+85^\circ\text{C}$
- High Output Drive -  $\pm 10$ V with 100 $\Omega$  Load

## Applications


- Current Boosters
- High Speed A/D Input Buffers
- Coaxial Cable Drive
- High Speed Line Drivers
- Video Impedance Transformation

## Absolute Maximum Ratings

Supply Voltage (V+ to V-)	40V
Maximum Power Dissipation	1.5W
Input voltage	Equal to supply Voltage
Maximum Continuous Output Current	$\pm 100$ mA
Maximum Peak Output Current	$\pm 250$ mA
Operating Temperature Range (Case)	$-25^\circ\text{C}$ to $+85^\circ\text{C}$
Storage Temperature	$-65^\circ\text{C}$ to $+150^\circ\text{C}$
Lead Temperature (Soldering 10 sec)	$+300^\circ\text{C}$
Maximum Junction Temperature	$+175^\circ\text{C}$
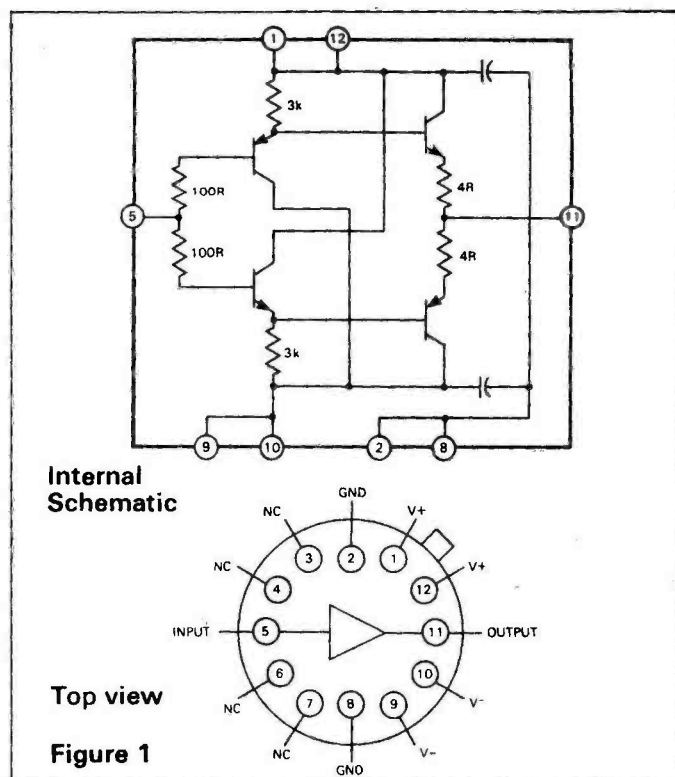
## Electrical Characteristics




( $V_S = \pm 15$ V,  $R_L = 1$ k $\Omega$ ,  $T_C = 25^\circ\text{C}$ )



Parameters	Conditions	Min	Typ	Max	Units
Input Bias Current			5	25	$\mu$ A
Input Impedance	$V_{IN} = 1$ V rms, $f = 1$ kHz	100	200		k $\Omega$
Voltage Gain	$V_{IN} = 1$ V rms, $f = 1$ kHz	0.94	0.96	1.0	V/V
Output Offset Voltage	$R_S = 50\Omega$		10	25	mV
Output Offset Voltage $T_C$	$R_S = 50\Omega$		25	75*	$\mu$ V/ $^\circ\text{C}$
Output Impedance	$V_{IN} = 1$ V rms, $f = 1$ kHz, $R_S = 500\Omega$		8	12*	$\Omega$
Output Voltage Swing	$R_S = 50\Omega$ , $V_S = \pm 5$ V	$\pm 12^*$	$\pm 13$ 6		V
Supply Current	$V_{IN} = 0$ V, $V_S = \pm 15$ , $V_S = \pm 5$		15 10	20	mA mA
Power Consumption	$V_{IN} = 0$ V		450	600	mW
Slew Rate	$V_{IN} = \pm 10$ V, $R_S = 50\Omega$	1000	1400		V/ $\mu$ s
Bandwidth	$V_{IN} = 1$ V rms, $R_S = 50\Omega$	100	125		MHz
Rise Time	$\Delta V_{IN} = 0.5$ V, $R_S = 50\Omega$		2		ns
Propagation Delay	$\Delta V_{IN} = 0.5$ V, $R_S = 50\Omega$		1.5		ns
Phase Nonlinearity	BW = 1 to 20MHz, $R_S = 50\Omega$		2		Degrees
Harmonic Distortion	$f > 1$ kHz, $R_S = 50\Omega$		<0.1		%

\*Applies over full temperature range  $-25^\circ\text{C}$  to  $+85^\circ\text{C}$

## Typical Performance Curves

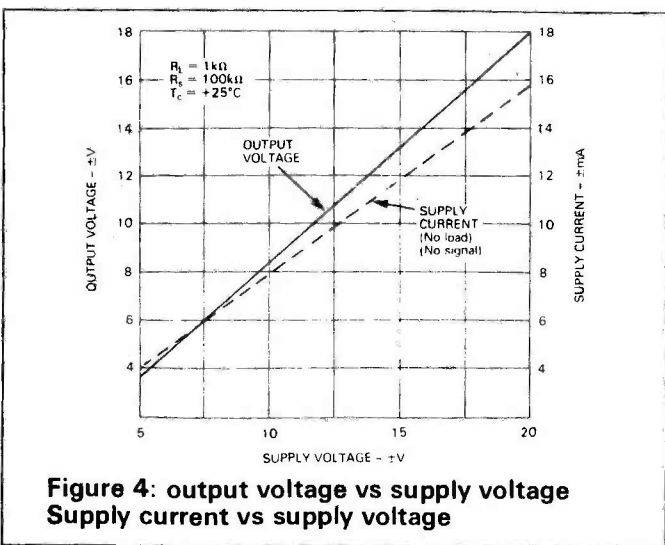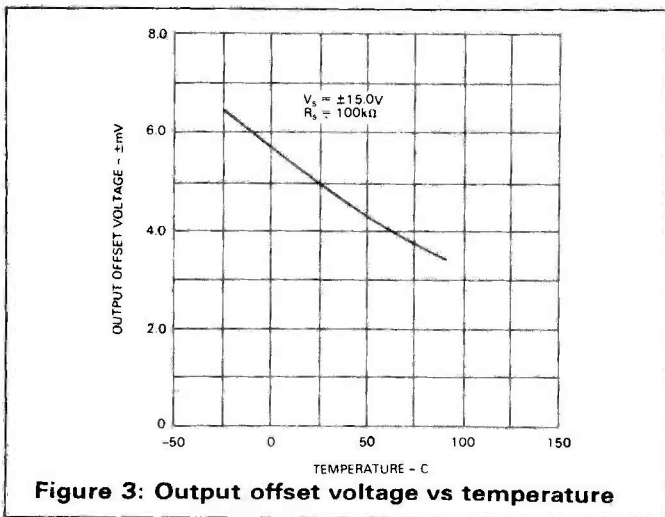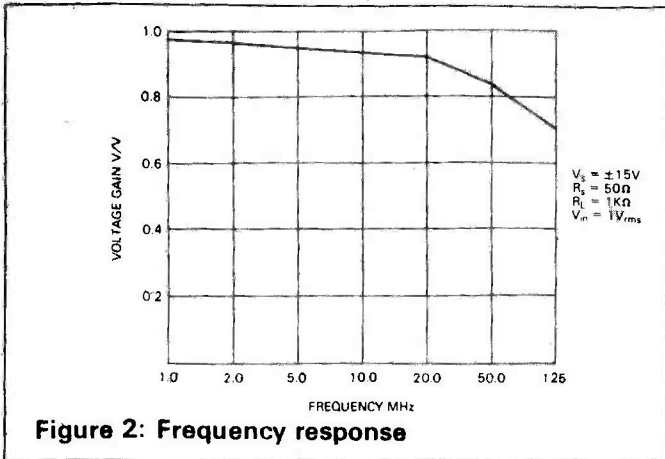

## Applications

### Layout Considerations

As is the case with any high-speed design, proper layout is critical to avoid the introduction of unnecessary errors due to high-frequency coupling, stray capacitance, and the like.




Large ground planes should be used whenever possible to provide a low resistance, low inductance circuit path, as well as shielding the effects of high-frequency coupling. Sockets should be avoided, as the increased inter-lead capacitance can degrade bandwidth. Input and output connections should be kept as short as practical.

### Capacitive Loading

The HOS-100 has been designed to drive capacitive loads of several thousand picofarads (such as coaxial cable) without oscillation. In these applications, peak current resulting from  $(C \times dv/dt)$  should be limited below the absolute maximum peak current rating of  $\pm 250\text{mA}$ .

Also, power dissipation due to driving capacitive loads plus standby power should be kept below the total power rating of 1.5W.

### Typical Applications

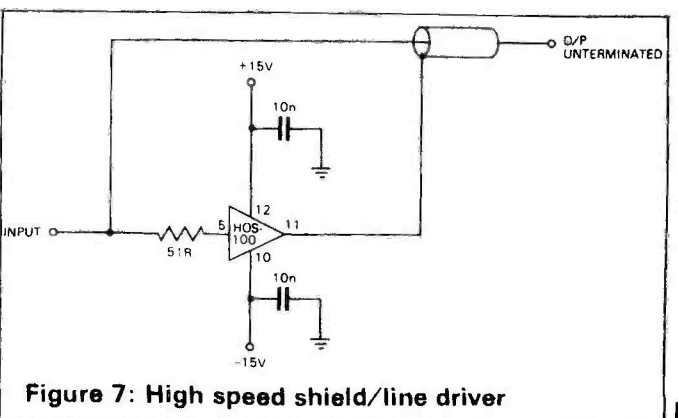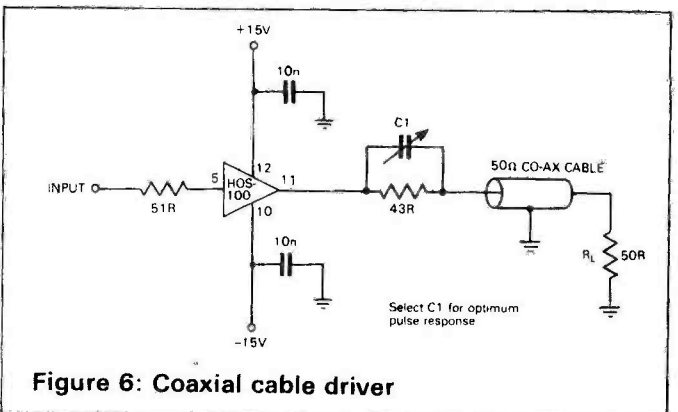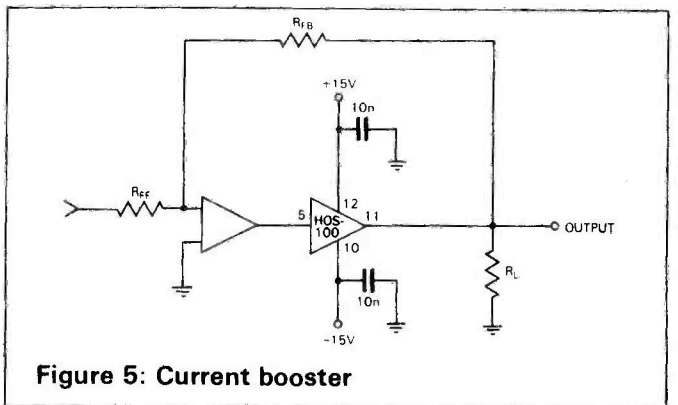


## RESISTOR KITS

¼W 10R to 82K (FL12 RANGR) 10 FLACK VALUR — 600 Resil £5 + VAT  
 ½W 2R2 to 2M2 (FL12 RANGR) 10 FLACK VALUR — 730 Resil £5.50 + VAT

# FAST RESPONSE STRIP CHART RECORDERS

Made in USSR

## Series H3020

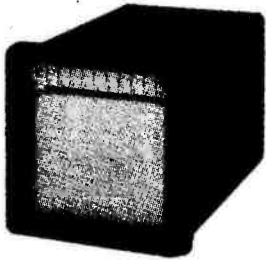

Basic error: 2.5%  
 Sensitivity: 8mA F.S.D.  
 Response: 0.2 sec.  
 Width of each channel:  
 Single and three-pen  
 recorders: 80mm  
 Five-pen recorders: 50mm

Chart speeds, selected by push buttons: 0.1 0.2 0.5-1.0-2.5-5.0-12.5-25 mm/sec.

Chart drive: 200-250V 50Hz

Recording: Syphon pen directly attached to moving coil frames. Curvilinear co-ordinates.

Equipment: Marker pen, timer pen, paper footage indicator, 5 rolls of paper, connectors, ink etc.

H3020-3 (Three pen): 475mm wide × 384mm deep × 165mm high inc VAT ..... **PRICE £69**

H3020-5 (Five pen): 475mm wide × 384mm deep × 185mm high inc VAT ..... **PRICE £105**

All recorders supplied complete in a sturdy custom built wooden carrying case. Carriage: £10.00 per recorder

## SPECIAL OFFER

## MULTI-RANGE UNIVERSAL PORTABLE AC/DC RECORDING VOLTAMMETER H390

(SUPPLIED WITH 5 CHART ROLLS)

Measurements ranges, AC/DC: 5-15-150-250-500mA, 1.5-5 Amps  
 5-15-150-250-500V


Accuracy: 1.5% DC, 2.5% AC

Chart width: 100mm

Chart drive: 220-250V AC mains

Chart Speed: 20-60-180-600-1800-5400 mm/hour

Carriage £6.00

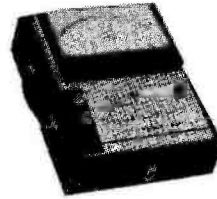

PRICE: £70.00

### TRANSFORMERS

British made transformers at very attractive prices

Primary	Secondary	Current	1+	10-	100+
240v:	4.5 0-4.5v	400m/a	50p	45p	35p
240v:	6-0-6v	100m/a	58p	52p	43p
240v:	6-0-6v:	500m/a	65p	60p	48p
240v:	9-0-9v:	200m/a	75p	70p	58p

Manufacturers note: We can supply FROM STOCK 1000+ quantities of the above transformers and adaptors below.

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.

REF	D.C. Voltage	Current	1+	10-	100+
EOB	4.5V	200m/a	50p	45p	32p
EM3	6V	200m/a	£1.00	80p	55p
EO3	6V	400m/a	£1.50	£1.25	85p
ET4	9V	150m/a	£1.50	£1.25	85p

Send your orders to:

**MARCO TRADING, (Dept. ETI)**  
 The Old School, Edstaston,  
 WEM, Shropshire SY4 5RJ  
 Tel: Whixall (094872) 464

Send for list of other reduced equipment and component lists. Official orders welcome. Wholesale prices upon request. Callers at our office welcome

## MULTIMETER — TYPE U4324 — 20,000 O.P.V.



D.C. Current: 0.06-0.6-60-600mA-3A  
 A.C. Current: 0.3-3-30-300mA-3A  
 D.C. Voltage: 0.6-1.2-3-12-30-60-120-600-1200V  
 A.C. Voltage: 3-6-15-60-150-300-600-900V  
 Resistance: 500Ω-5-50-500kΩ  
 Accuracy: d.C. 2.5%: A.C. 4% (of F.S.D.)

PRICE complete with test leads and fibreboard storage case  
 £10.50 inc of VAT Packing and postage £2.00

# MAGENTA ELECTRONICS LTD.

## E.T.I. KITS

Full kits include printed circuit boards, components, hardware, I.C. sockets, cases etc. unless stated (Not batteries). If you do not have the issue of E.T.I. which includes the project — you will need to order the instruction reprint at an extra 45p each. Reprints available separately 45p each + p&p 45p.

INSULATION TESTER May 82	£15.98	HANDCLAP SYNTHESISER Aug 81	£28.98
AUTORANGING CAPACITANCE METER Mar/April 82	£71.99	WAH PHASE June 81. Less pedal	£13.44
ACCURATE-VOLTAGE MONITOR Apr 82	£13.63	LED JEWELLERY June 81. Cross	£2.47
AUTOMATIC CONTRAST METER Apr 82	£26.77	Star £9.41. Spiral £7.20.	
less extrusion	£26.77	ALIEN ATTACK Jan 81	£19.76
HIGH QUALITY PHONO AMPLIFIERS Feb 82. Less case	£17.96	GUITAR NOTE EXPANDER April 81	£16.47
MOVING COIL STAGE	£17.68	DRUM MACHINE April 81	£59.98
MOVING MAGNET STAGE	£6.77	ENGINEERS STETHOSCOPE Mar 81	£19.19
PEST CONTROL Feb 82	£28.98	SOUND PRESSURE LEVEL METER Feb 81	£39.96
GUITAR TUNER Jan 82	£7.98	INFRA RED ALARM Feb 81	£54.98
COMPONENT TESTER Dec 81	£17.98	4 INPUT MIXER Dec 80	£19.77
CAR ALARM Nov 81	£26.59	MUSICAL DOORBELL Dec 80	£11.61
ENLARGER TIMER Oct 81	£20.76	METRONOME Nov 80	£5.98
SOUND BENDER Oct 81	£43.33	ULTRASONIC BURGLAR ALARM Aug 80	£26.82
WATCHDOG SECURITY ALARM Aug 81	£19.96	CAPACITANCE METER Aug 80	£20.26
RECHARGEABLE BATTERY extra		CMOS LOGIC TESTER Aug 80	£10.97
		CLICK ELIMINATOR April 79. £61.55. Or less case £46.57.	

## NEW! SOUND TO LIGHT LADDER

10 channel drive to line of lights — very effective. 0-300 watts per channel. Total 3000 watts. Select bar or dot display mode. Also includes 10 channel strobe and chase effects. Switch selectable frequency — low — middle — high. Mono or stereo input either by direct wire or internal microphone. LED panel monitoring of status. Kit includes all parts and instructions. Lights not included. Output via 2 P652 sockets. Plugs extra £2.24 each.

SOUND TO LIGHT LADDER — GREAT NEW KIT  
 £49.98 inc. VAT and Postage (Less lights)

## MAGENTA ELECTRONICS LTD

EZ15, 135 HUNTER ST., BURTON-ON-TRENT, STAFFS  
 DE14 2ST. 0283 65435. MON-FRI 9-5. MAIL ORDER ONLY  
 ADD 45p P&P TO ALL ORDERS

PRICES INC VAT P&P 45p



OFFICIAL ORDERS WELCOME.  
 IRISH REPUBLIC & B.F.P.O. EUROPE:  
 Deduct 10% from prices shown Payment  
 must be in Sterling.  
 ACCESS and BARCLAYCARD (VISA)  
 ORDERS ACCEPTED BY PHONE OR  
 POST.  
 SAE ALL ENQUIRES.

Please  
 mention  
**E.T.I.**  
 when replying  
 to all  
 adverts



# ELECTROMART

**MONTHLY IN  
ELECTRONICS TODAY —  
YOUR OWN 'WHERE TO  
BUY IT' GUIDE**

## AVON

### ANNLEY ELECTRO

190 Bedminster Down Road  
Bedminster Down, Bristol  
Tel: 0272 832622  
Open: Mon-Sat 9am-6.30 pm Wed 9am-2pm

## BEDFORDSHIRE

### BROADWAY ELECTRONICS

1 The Broadway, Bedford,  
Tel: 0234 213639

Open: 6 days 9.5.30 - ½ day Thur.  
lunch 1.30-2.30.  
Specialists in electronic components and  
Acorn computers

## DORSET

### D.J. ELECTRONICS

64 Ensbury Park Road,  
Bournemouth.

Tel: (0202) 515073.

Open: Mon-Sat 9am-6pm.

## HAMPSHIRE

### GAINES ELECTRONICS

3, West Street, Fareham.  
Tel: (0329) 234891

Open: 6 days 9am-5.30pm.  
RS component stockist. Wide range of components for  
the enthusiast.

## HERTFORDSHIRE

### GODDARDS COMPONENTS

110 London Road, St. Albans.  
Tel: St. Albans 64162

Open: Mon-Sat 9.30am-5.30pm  
(½ day Thur)

**LOOKING FOR  
COMPONENTS! HARDWARE!  
CASES! TRY YOUR LOCAL  
LISTED STOCKIST**

## S. IRELAND

**peats**  
the world of electronics

25 Parnell St, Dublin 1.  
Tel: Dublin 740662

Open: 6 days 9am-5.30pm  
Components. Computers. Video games.

## LANCASHIRE

### ETESON ELECTRONICS

15B Lower Green,  
Poulton-le-Fylde, Blackpool  
Tel: (0253) 885107

Open: 9.30am-12.30 1.30-5.30 Closed Wed & Sun.  
Electronic Component Specialists.

## LONDON

### SAMSONS ELECTRONICS LTD

9/10 Chapel St. 21/23 Bell St. NW1.  
Tel: 01-262-5125, 01-723-7851.

Open: 10am-6pm. (Sat 11am-5pm).  
Vast selection of components at ridiculous  
prices.

## W. MIDLANDS

### PATH ELECTRONIC SERVICES

369 Alum Rock Road, B'ham.  
Tel: 021 327 2339.

Open: 10am-6pm weekdays.  
Sat 9.30am-5pm. Contact Peter A.  
Thomas. Wholesale and retail supplies.

## NOTTINGHAMSHIRE

### DAMON electronics

99 Carrington St. Nottingham.  
Tel: 53880 (mail order available)

Open: 6 days 9.30am-5.30pm.  
Specialists in T.V. F.M. aerials.

**FOR YOUR BUSINESS TO  
BE INCLUDED, CALL  
ELECTROMART ON  
01-437-1002.**

## TYNE AND WEAR

### AITKEN BROS & CO

35 High Bridge  
Newcastle Upon Tyne.  
Tel: 326729

Open: 9am-5.30pm (Sat 5pm) closed Wed.  
Retail and Wholesale supplied.

## S. WALES

### CARDIGAN ELECTRONICS

Chancery Lane, Cardigan,  
Tel: Cardigan (0239) 614483

Open: Mon-Sat 10am-5pm. Closed Wed.  
Electronic components &  
Acorn computer stockist.

## WILTSHIRE

### camlab electronics

27 Faringdon Rd. Swindon  
Tel: (0793) 34917

Open: 6 days 9am-5.30pm  
Specialists in loud speakers. Wide selection: 1¼"-18"

## YORKSHIRE

### ACE MAILTRONIX LTD.

3A Commercial Street,  
Batley. Tel: (0924) 441129

Open: Mon-Fri 9am-5.30pm. (Sat 1pm)  
Retail and wholesale.

**PLEASE MENTION  
ELECTRONICS TODAY  
WHEN USING THESE  
SHOPS!**

Please include my business details in the next available issue of Electronics Today International:

Business Name: .....

Address: .....


.....

Tel. No.: ..... Open Hrs: .....

Contact (Office Use Only): .....

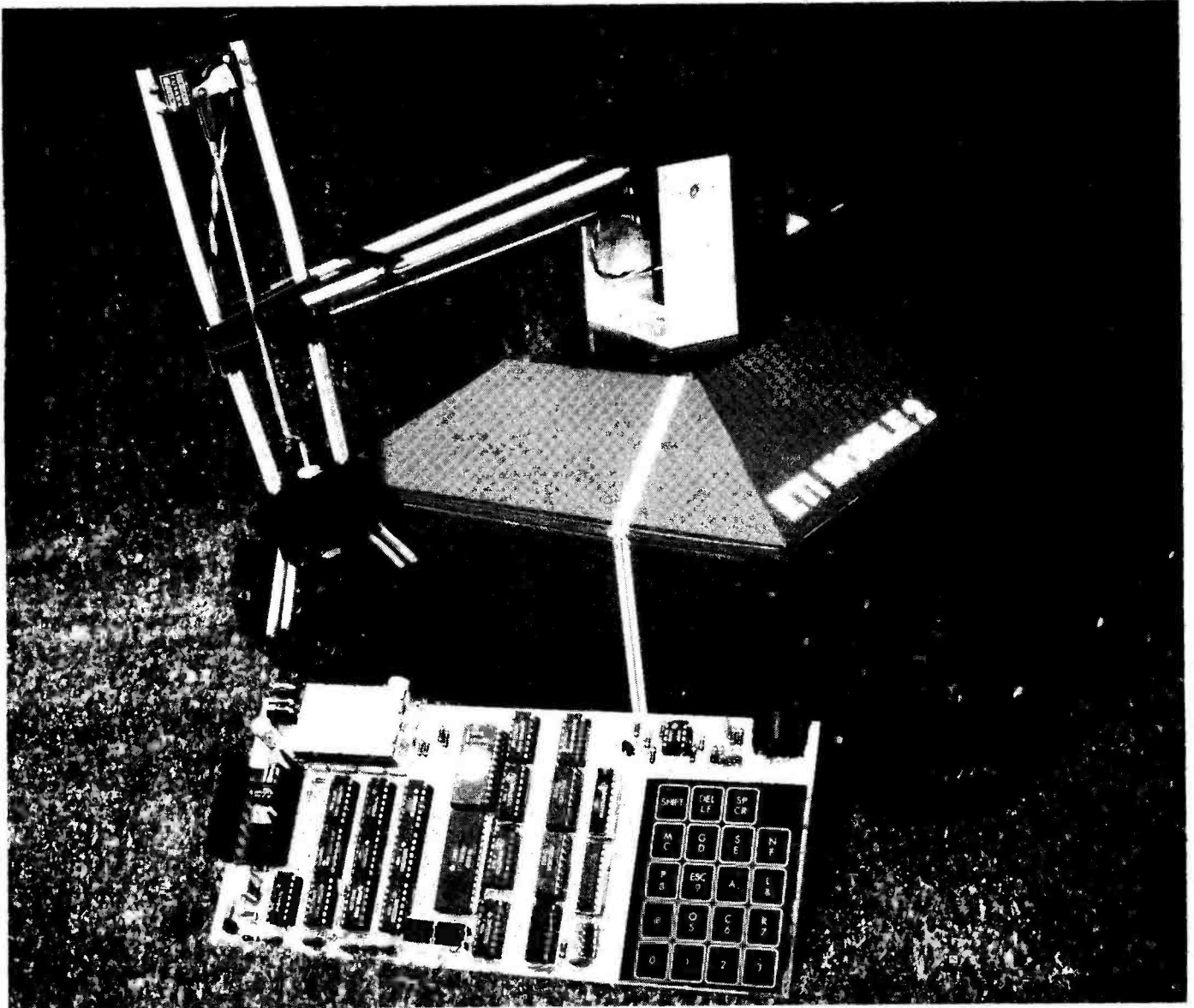Post To: Electronics Today, 145 Charing Cross Rd., London WC2H 0EE.





# ETI MOBILE 2

Regular readers will have followed our Motor Control series with (we hope!) a curious interest. It may have crossed your mind to wonder exactly what ETI is up to *now*. All this talk of Robot Control and no robot!

Way back in our April issue we showed the base of our Mobile 2, and since then have been steadily mounting modules into it, building up the basis of an advanced robotics project.

This month it's time to lay out the complete series and to involve the future participants and designers in the project – you! We have developed a complete mobile, with arm and

computer link which we will be presenting over the next few months. After that it's up to you, our readers. We hope to be able to continue the series with projects and features based upon your designs and programs for the Mobile 2.

## Too Mobile?

The complete ETI Mobile comprises a tracked base with servo driven arm – for which a low-cost metalwork kit is available – infra-red proximity detectors, on-board interface and control circuitry, wireless link to a home computer port and an experimental positional detection system.

Enough of this 'you and us' attitude – it's time for some reader involvement. We've been publishing robot modules thick and fast, but now it's your turn to be inventive; together we can make beautiful robots.

The home computer acts as the "brain" and can be thus programmed to make decisions upon the information returned to it by the Mobile. The latter's motor drive system is linked via an eight-bit port arrangement to the control board, placing the tracks directly under computer control.

This means that a set of pre-arranged instructions can be sent to the mobile, causing it to follow a path around obstacles and obstructions, thus functioning in any environment. As the computer carries all the software, decisions upon "what to do if..." can be modified and expanded at the touch of a cursor!


Similarly, the arm is ported onto the bi-directional data link and can be software controlled from the computer. Alternatively the arm may be used as a 'stand-alone' design, for which the interface has also been configured.

### Some Arm In it

The servo-driven manipulator we are proud of! Produced in conjunction with Remcon Electronics, it overcomes many of the complex mechanical hang-ups which beset earlier constructs.


It is ideal for teaching purposes, being controllable by any of:

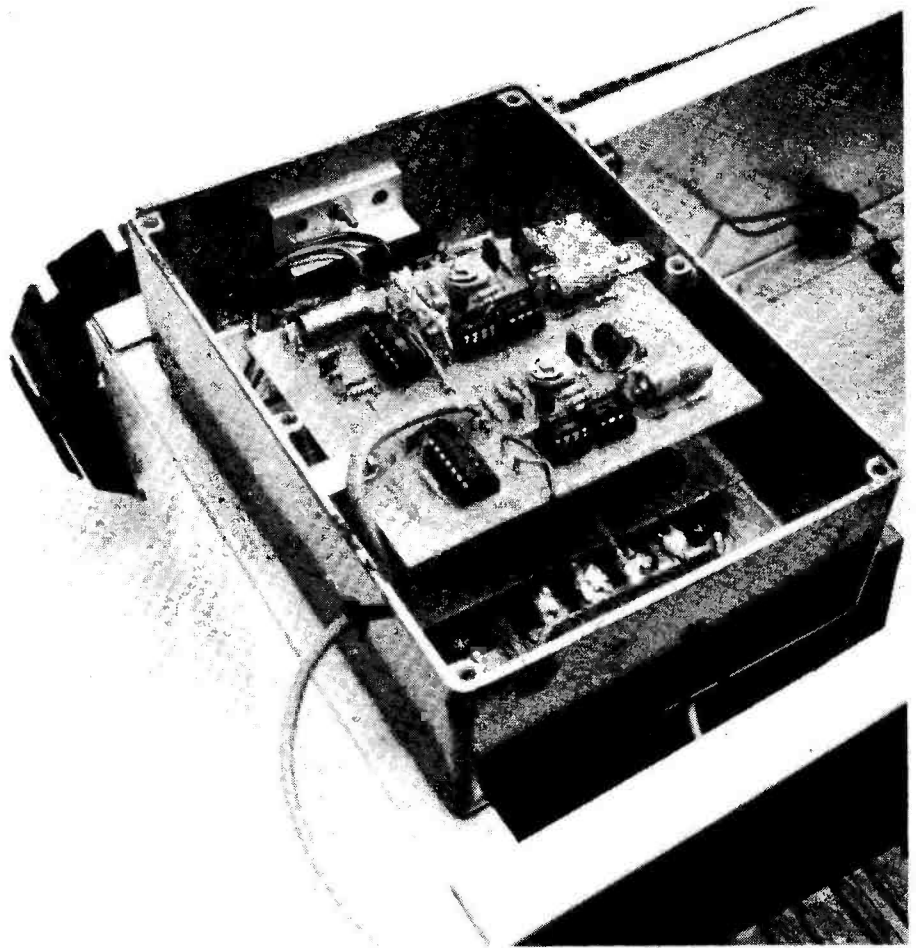
- (i) a standard radio control system, such as employed in model aircraft, etc.
- (ii) a 'tele-operator' which allows direct instruction of the arm – and the pupil operating it.
- (iii) a microcomputer, using our interface.



Above: The analogue PWM control board and motor driver board for the Mobile 2.

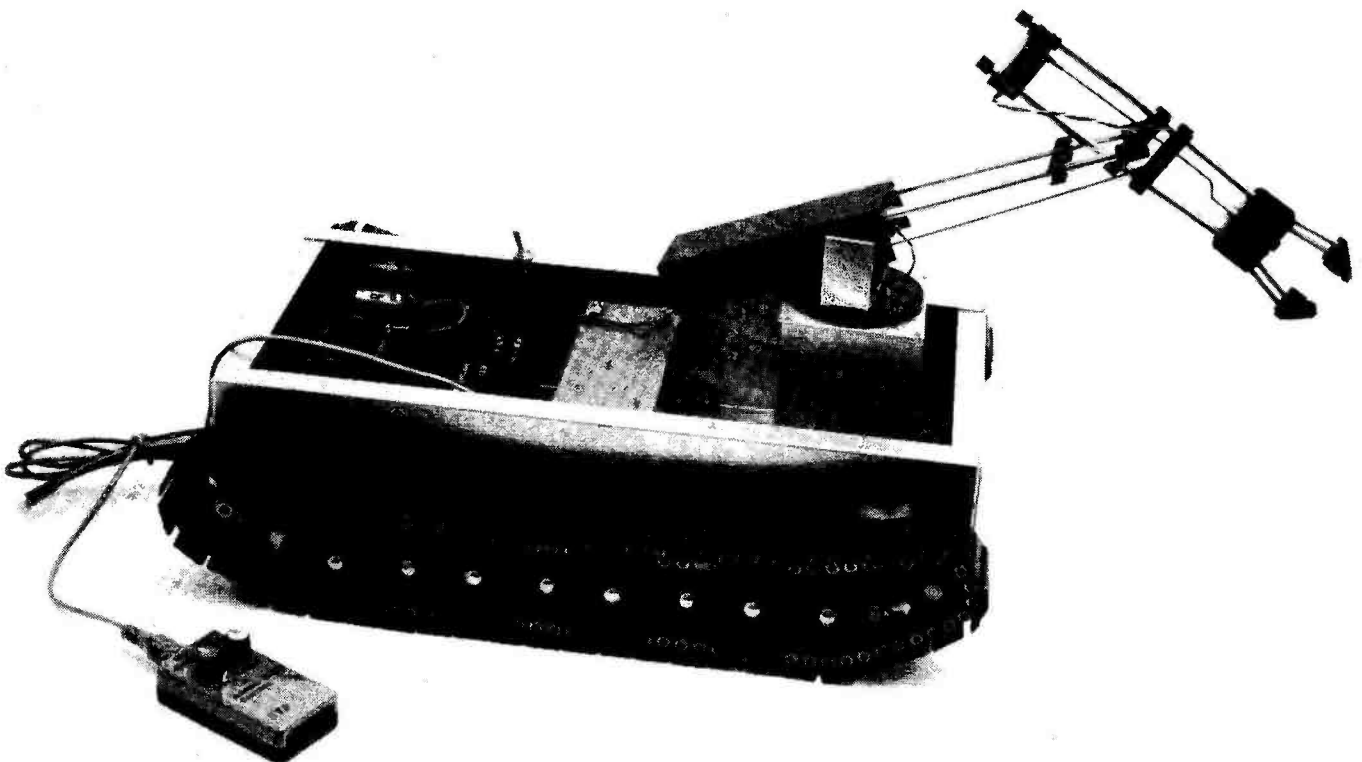Below: The Mobile 2 with hand controller and servo manipulator.



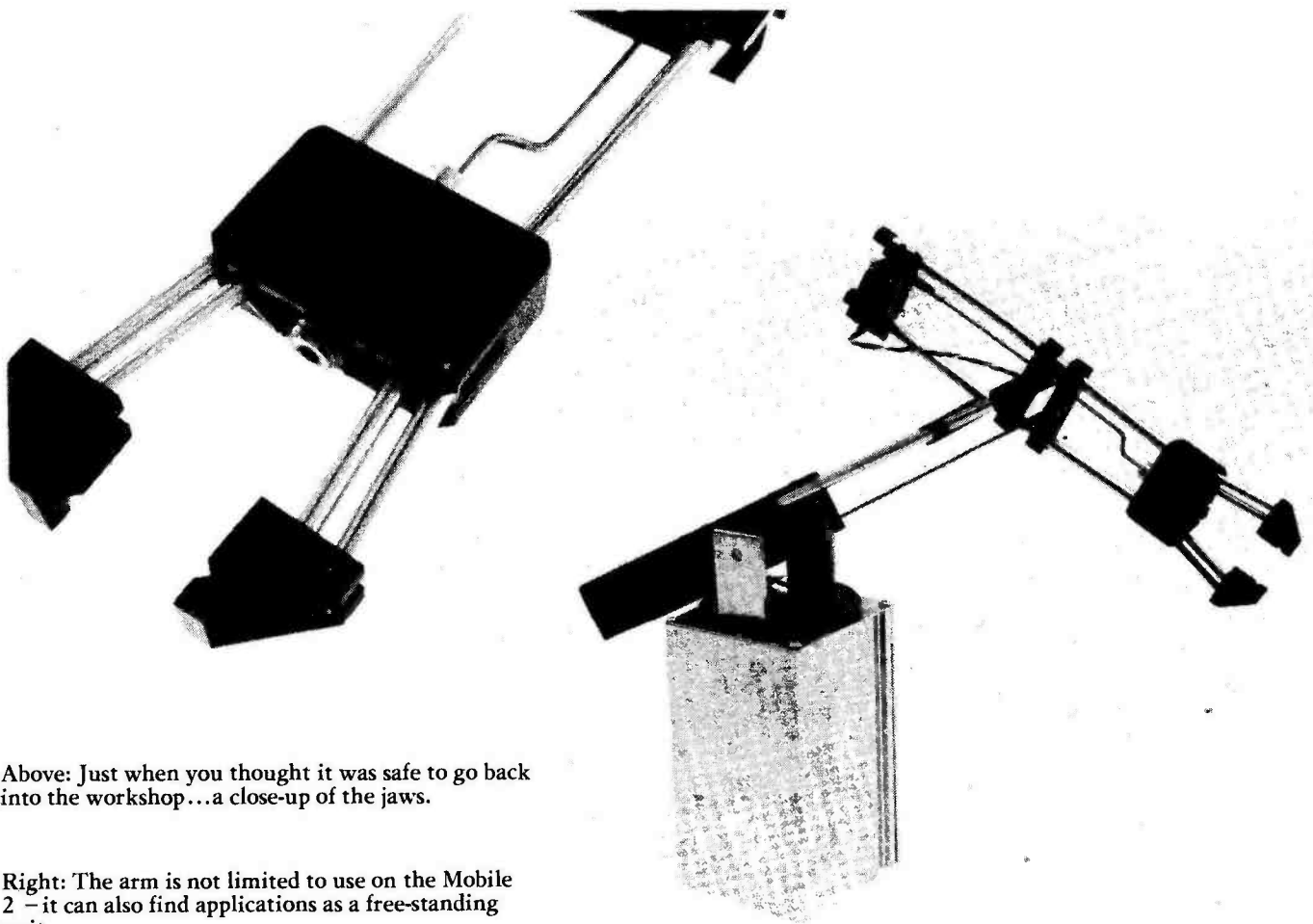

Above: Just when you thought it was safe to go back into the workshop... a close-up of the jaws.

Right: The arm is not limited to use on the Mobile 2 - it can also find applications as a free-standing unit.

## MOBILE 2 - MECHANICAL SPECIFICATION

### TRACTOR UNIT

Dimensions:	19 3/4" x 13 1/2" x 5 1/2" high (unloaded)
Ground Clearance:	1 1/4" unladen
Operational Payload:	11 lbs.
Will climb a 3" stepped obstruction with full payload.	
Ratio of drive units:	60:1 (variable, see Buylines).
Drive Voltage:	7V2
Starting Current:	9 A
Running current:	3A5
Operational Velocity:	2.5 feet per second.
Smooth Incline Capability:	30°

By varying the type of servo employed, the function and power of the arm can be selected to suit the application required.

To reduce the load placed on the servos, the arm is designed to be self-balancing, whatever servos are used. On the standard manipulator, high resolution types are employed to improve accuracy as much as possible

while under computer control.

The mechanical set-up of these arms is critical for best performance, and for that reason we have arranged that they be supplied built and tested, as part of the mobile metalwork, or as a separate item if you prefer. Buylines has the details.

### Base Comments

The heart of the whole system is the tractor unit upon which the Mobile is constructed. The final design, although very simple in appearance, has only been arrived at after much debate and experimentation.

Tracks were used for their superior abilities with regard to climbing obstacles and coping with varying surfaces, ie. carpet, concrete, vinyl, etc. Infra-red rotation counters are fitted to both the motordrive shafts, to enable accurate control to be exercised over both the base speed and direction.

A brief spec of the capabilities of the base are given elsewhere in this article. All the metalwork is purpose built, and pre-drilled for our range of modules. After having tried out various commercial options - model tank mechanics, for example - we came to

the conclusion that not only is it the superior to have custom metalwork made - it is actually cheaper! Initially we had ruled it out purely on grounds of expected price level.

### How Close Encounters?

Mobile 2 is a fairly large beast to let loose around your living room (19 x 13 x 5" approx. not including arm and cover!) and so it is important that it be prevented from colliding with obstacles. Remember that so far as *it* is concerned anything in the way, be it your prize drinks cabinet, hi-fi speaker or granny, is simply an obstruction.

In our June 82 edition we published our 'Proximity Detector' module, of which Mobile 2 has four. They are mounted above each track corner and may be angled, such that even glancing contact is prevented. They provide adequate protection.

The control board logic is so configured that the IR detectors provide an override which halts operation of any program, so long as an obstacle is present. Unless programmed to do anything else, the mobile will halt at any obstruction large enough to register on two detectors, ie a wall.

## Well Developed Robot

Our Mobile 2 is presented as an open-ended project. We want our readers to carry it on and develop it as far as they can. The modules to come from us will be:

- 1) Arm Interface and control circuitry, to allow stand-alone control, or porting to main PCB of Mobile 2.
- 2) Main Control PCB – mounted within the mobile and will accept up to four eight-bit peripherals, with appropriate strobing, and operate in conjunction with the link.
- 3) Computer Link – a bi-directional data transfer system which has as a receiver a home computer system to which it connects via a standard interface.
- 4) Experimental Positional System – to allow the Mobile to 'map' its environment and thus function more precisely.

One future use for the Mobile – which we are still working on – is that of office messenger. It would be 'called' to a particular room or desk, loaded with papers, etc, and dispatched to another location, programmed at point of departure. It will have to avoid doors, people and cats whilst doing so! That one may be a while coming if left to us,

but we'll get there! It would use the same metalwork and basic electronics.

"If left to us" is the key phrase there – what about that vast reservoir of design talent and ingenuity that goes under the name of ETI's readership? It's about time *you* got into robotics, too!

Once we complete the basics of this project, then it's up to you to carry it on. Even now, if you have any ideas or strong feeling as to how the Mobile should grow, let's hear them. We will publish what correspondence we can on the subject and implement any ideas which are practical!

Next month, we commence construction of the Mobile with the base, motors and speed control. Past modules which will be used in the Robot were published in:-

- 1) ETI March 82 p. 61-63
- 2) ETI April 82 p. 94-97
- 3) ETI May 82 p. 34-36
- 4) ETI June 82 p. 66-70

Photocopies are available from our offices if you've been foolish enough to lose your back issues! (Enclose £1.25 – inclusive of p&p – for each article. Address your request to: Xerox Department, ETI, 145 Charing Cross Road, London, WC2H 0EE)


## BUYLINES

The metalwork for this project is all available from Remcon Electronics Ltd, 1 Church Road, Bexleyheath, Kent (Tel. 01-304 2055)

They supply the tractor unit as a complete kit with full assembly instructions. All injection moulded components for track and suspension system are included – as is an assembly spanner! The aluminium chassis is ready punched and drilled with all required fixings. Motors and gearboxes are supplied as assembled and coupled to the

output shafts. The final ratio of the gearboxes may be varied between 300:1 and 3:1 to obtain different performances from the mobile. The price complete, including VAT and p+p, is £125. Drive units are available separately at either £21.25 without shafts, or £26.75 with. Prices are inclusive.

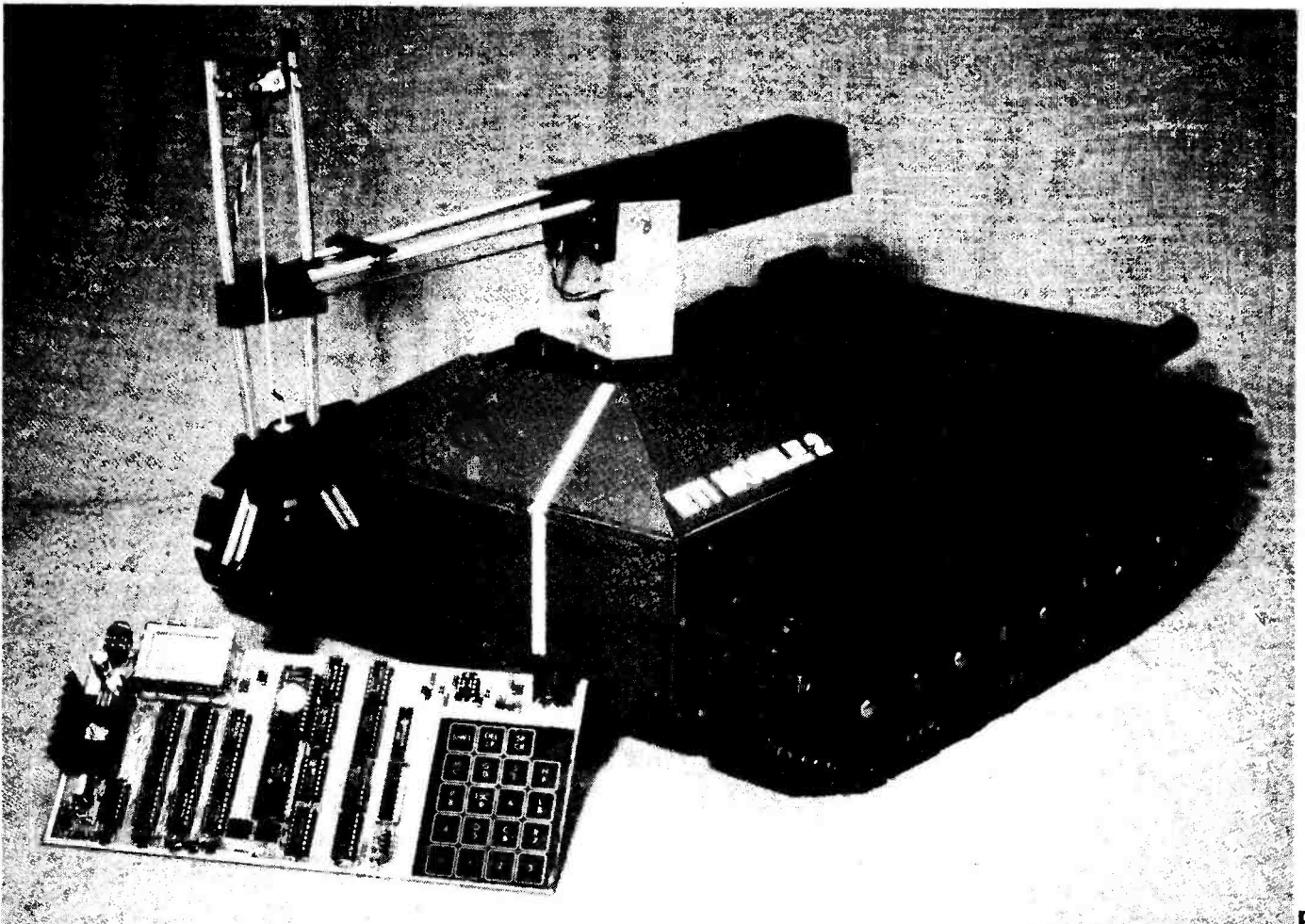The manipulator, supplied built and tested and ready wired, will be described more fully in a forthcoming article, but is available now, with high precision servos, for £175 all inclusive.



**CLASSIFIED**

THE PATH TO  
SUCCESSFUL SALES!

01-437 1002

Ext 211

## ADVERTISEMENT RATES

**Semi-Display** (min 2 cms)  
1-3 insertions **£6.00** per cm  
4-11 insertions **£5.50** per cm  
12+ insertions **£5.00** per cm

Lineage 21p per word (min 15 words)  
Box Nos. **£2.00**

**Closing date 2nd Friday of the month  
preceding publication date.**

All advertisements in this section must be prepaid. Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)

Send your requirements and cheque/P.O. to:

**HOBBY ELECTRONICS CLASSIFIED**  
ADVERTISING, 145, CHARING CROSS RD,  
LONDON WC2H 0EE.

**MICROMINATURE** medium wave matchbox radio kit, astound your friends, £5. Ion Electric, 72, Willow Drive, Solihull, B90 4HW.

**ANY SINGLE SERVICE SHEET** £1/L.S.A.E. Largest stockists Service/Repair manuals. Named T.V. Repair data £6.50 (with circuits £8.50). S.A.E. pricelists, free publications, quotations. Auseti, 76 Churches Larkhall, Lanarkshire.

**CLOSE ENCOUNTERS GROUP** Personal introductions and social events. Meet interesting, attractive people. Local, 051-931 2844 (24 hours).

**PRINTED CIRCUITS.** Make your own simply, cheaply and quickly! Golden Fotolac light-sensitive lacquer - now greatly improved and very much faster. Aerosol cans with full instructions, £2.25. Developer 35p. Ferric Chloride 55p. Clear acetate sheet for master 14p. Copper-clad fibreglass board, approx. 1mm thick £1.75 sq. ft. Post/packing 75p. White House Electronics, Castle Drive, Praa Sands, Penzance, Cornwall.

## ASSISTANT FILM RECORDISTS (OR TRAINEES) Manchester

To work in sound transfer and dubbing areas operating sound recording and reproduction equipment for a wide range of programmes. Some mobile film recording work involved. Candidates must have professional experience and practical knowledge in this field, current driving licence and normal hearing. Salary £6384 - £7929 according to qualifications and experience. Relocation expenses considered.

Candidates not possessing all the qualifications may be considered as Trainees on a lower salary scale, requiring attendance at the BBC's Training Department at Evesham. For appointment as a Trainee, 'O' level standard of education or equivalent, preferably including Physics and/or Maths and a basic knowledge of electronics, plus a practical interest in sound recording, would be required.

Contact us immediately for application form (quote ref. 1396/ET and enclose s.a.e.): **BBC Appointments, London W1A 1AA.** Tel. 01-580 4468 Ext. 4619.

We are an Equal Opportunities employer

**BBC tv**

## COMPUTER CONTROLLED SOUND IS HERE!

This unique device receives serial data from any computer, baud rate up to 4800, responds only to its own address code (preset by on-board d.i.l. switch) and is capable of attenuating any audio signal in 1.5db steps from 0db to infinity. Once the device has been enabled, all other devices will ignore the commands until a new address has been transmitted. These devices can be built into amplifiers, mixers etc, or anywhere computer control of audio signals is required. The kit comes complete with all parts, sockets etc, and is supplied with instructions for use. A 5V power supply is required. Up to 127 devices can be individually addressed on one loop. Order ref: MED01.

Price **£69.50 + VAT P&P £1.50**

Cheques, postal orders crossed and payable to:

### MEDIATRONICS

3 Alnwick Drive, Hollins, Bury, Lancs  
**061-796 6410**

**CENTURION BURGLAR ALARM EQUIPMENT** Send SAE for **free** list or a **cheque/PO for £5.95** for our **special offer** of a **full sized decoy bell cover**. To **Centurion Dept ET1265, Wakefield Rd., Huddersfield W. Yorkshire.** **Access & Barclaycard** Telephone orders on 0484-35527.

**CIRCUIT DESIGN,** Prototype construction, analogue or Digital, Single Circuits or Complete Instruments/Systems. Write A. J. ATTWOOD, C.Eng., MIERE, Heathercote, Heatherton Park, Taunton, Somerset, TA4 1ET, or Phone Bradford-on-Tone (082-346) 536.

### TOP QUALITY - UNBEATABLE PRICES




We specialise in top quality equipment for groups, disco and HiFi. High power amplifiers up to 600W, lighting units, consoles, power supplies, etc.


Send for catalogue **60p** from:

### SILVERQUEST LTD

21 Belmont Road, Luton LU1 1LL,  
Bedfordshire  
Tel: (0582) 37226

# PCB FOIL PATTERNS

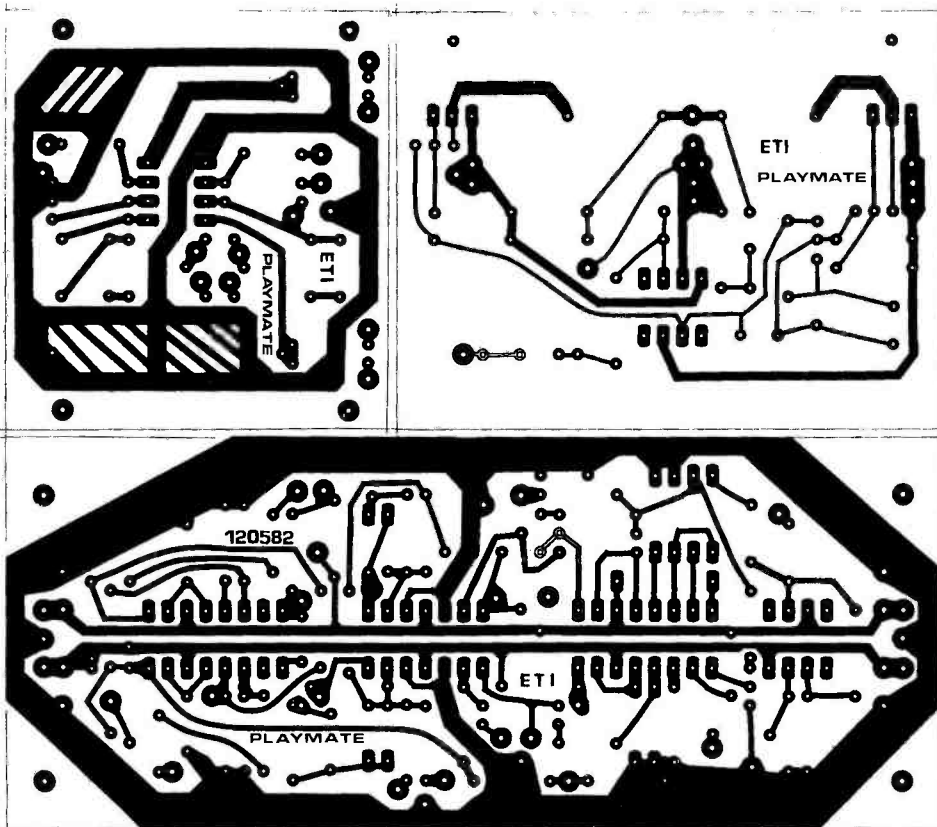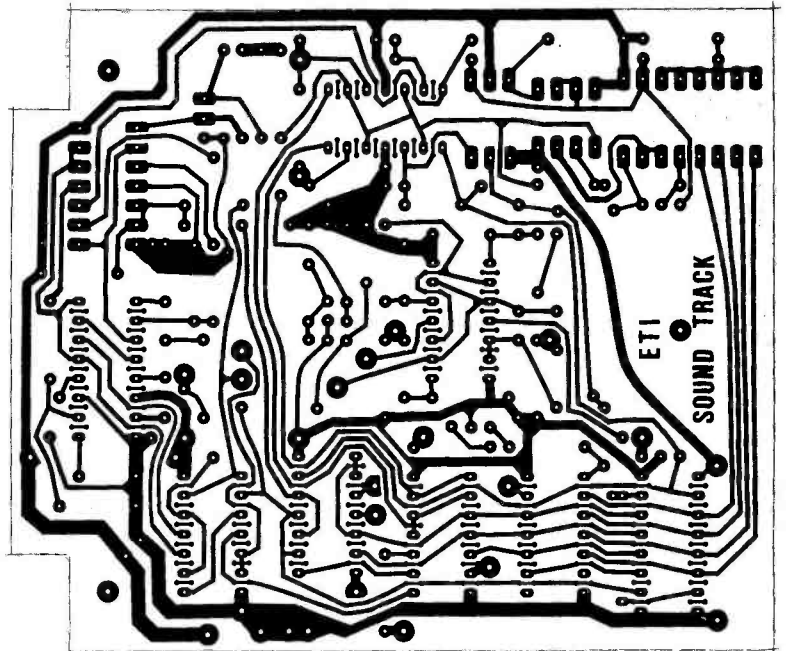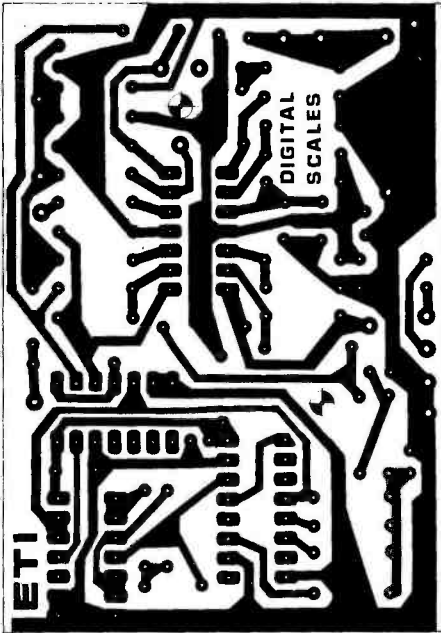

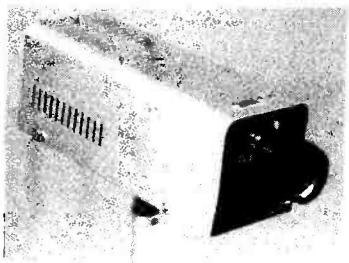

A really compact high performance CCTV camera for only £130.00 plus VAT plus P/P, Total £152.95. Size 3"x3"x9". 240v operation. 1v p-p output. Lens extra.

**CROFTON ELECTRONICS LIMITED**

35 GROSVENOR ROAD, TWICKENHAM, MIDDLESEX TW1 4AD  
Telephone 01 891 1923 01 891 1513  
Telex 295093 CROFTNG

125 WATT firebrenglass poweramps toz heat-sink + instructions £10.85p. A Law 8 Cunliffe Road, (over Incatle) Ilkley LS29 9DZ — Return ad — Free Pak — Quality. Capacitors

**CABINET FITTINGS**

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers

**ADAM HALL SUPPLIES LTD.**

Send 30p cheque/PO for illustrated catalogue. Adam Hall (ET Supplies), Unit B, Carlton Court, Grainger Road, Southend-on-Sea.

TRITON L5.1 1u.5K RAM, 8K Eprom board in single enclosure, remote keyboard, fully documented, £125 o.n.o. 0438 2366, extension 917, office hours.

**GUITAR/P.A. MUSIC AMPLIFIERS**

100 watt superb treble/bass overdrive, 12 months' guarantee. Unbeatable at £50, 60 watt £44, 200 watt £68, 100 watt twin channel, sep. treble/bass per channel £65, 60 watt £52, 200 watt £78, 100 watt four channel, sep. treble/bass per channel, £75, 200 watt £98, slaves 100 watt £37, 200 watt £60, 250 watt £70, 500 watt £140, fuzz boxes, great sound £12, bass fuzz £12.90, overdrive, fuzz with treble and bass boosters £28, 100 watt combo, superb sound, overdrive, sturdy construction, castors, unbeatable, £100; twin channel £115, bass combo £118, speakers 15in, 100 watt £38, 12in, 100 watt £24, 60 watt £18, microphone Shure Umdyn B £28.

Send cheque/P.O. to: WILLIAMSON AMPLIFICATION, 62 Thorncliffe Avenue, Dukinfield, Cheshire. Tel: 061-308 2064.

BURGLAR alarm equipment. Ring Bradford (0274) 308920 for our catalogue, or call at our large showrooms opposite Odsal Stadium, C.W.A.S. Ltd.

COPPER CLAD BOARD double sided fibre glass, 20 sheets, 12x8" £6.00. 5 sheets 12"x8" £4.00. Including P&P. Davron, 1 Bankside, off New Street, Chelmsford.

STOCK CLEARANCE. Mixed Resistor Packs: 1/3w, pre-formed, un-used. 1-1lb pack (2500-plus) £2.50.50; 2lb pack £4.60; Exceeding 2lbs £2.00 per lb. 2A Mains Filters RS 238-435, £3.50 each. 16-pin Headers (without covers) 6 for £1. 8-pin i/c holders 12 for £1. 20mm Chassis Fuseholders 4 for £1. General Purpose Diodes 25v 50ma, 75 for £1. TTL Sale: 7412, 10 for £1; 7485, 2 for £1; 7491 4 for £1; 74122, 5 for £1; 74123, 5 for £1, 74188, £2 each. 2N 3055 (full spec.) 2 for £1, Bridge Rect 26m B10A, 25A/100v, 11/10" sq., £2.50 each. All prices include VAT/P&P. Linway Electronics, 843 Uxbridge Road, HAyes End, Middx UB4 8HZ.

PROXIMITY SENSORS infra red, 6 inch range 5 to 15v supply. Miniature design 6.5 x 5 x 2cm. Only £16.50. Leaflet. Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent, Staffs.

OSCILLOSCOPE £12. Easy built unit plugs into T.V. aerial socket and converts it to large screen oscilloscope. Costs approx. £12 to make. Circuit and plans £3. J. Bobker, 29 Chadderton Drive, Unsworth, Bury, Lancs.

T. & J. ELECTRONICS COMPONENTS — Quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

ELECTRONICS component shop in MAIDSTONE, KENT! Thyronics Control Systems, 8 Sandling Road, Maidstone, Kent. Maidstone 675354.

**600 RESISTORS**

High quality Carbon Film 1/4W 5% E12 series 60 values 10 per value

£5 INCLUDING VAT P&P

**COVE COMPONENTS**

58 Southwood Rd., Cove, Farnborough, Hants GU14 0JJ  
Mail Order only

AERIAL AMPLIFIERS Improve weak television reception. Price £6.70, S.A.E. for leaflets. Electronic Mailorder, Ramsbottom, Lancashire BL0 9AGH.

WANTED: ELECTRONIC COMPONENTS and Test Equipment. Factories cleared. Good prices given. Q Services, 29 Lawford Crescent, Yateley, Camberley, Surrey. 0252 871048.

**RADIATION DETECTORS**

BE PREPARED

VIEW THRU LENS



- THIS DOSIMETER WILL AUTOMATICALLY DETECT GAMMA AND X-RAYS
- UNIT IS SIZE OF FOUNTAIN PEN & CLIPS ONTO TOP POCKET
- PRECISION INSTRUMENT METAL CASED WEIGHT 20Z
- MANUFACTURERS CURRENT PRICE OF A SIMILAR MODEL OVER £25 EACH

British design & manufacture. Tested & fully guaranteed Ex-stock delivery

£6-95 inc VAT Post & Pack 60p

Ideal for the experimenter COMPLETE WITH DATA

**HENRY'S**

404 EDGWARE ROAD LONDON W2 1ED



**MOS-FET AUDIO MODULES**

Hitachi devices, Hitachi spec., glass boards, extruded heatsinks, tested, guaranteed 24 months.

120 watts/8 ohms, 120v/2A supply; £13.95.  
240 watts/4 ohms; 120v/4A supply; £19.95.  
400 watts/2 ohms; 120v/7A supply; £29.95.

Power supplies/pre-amps available. Post/packing 80p. Stamp for details. Quantity discount.

Audio-Tech., 8 Parsons Close, Church Crookham, Aldershot, Hants GU13 0HL. Tel: 02514 22303.

Please mention E.T.I. when replying to all adverts



**DO YOU WISH TO LEGALLY TRANSMIT AUDIO SIGNALS  
OVER BRITISH TELECOM CIRCUITS?**

We manufacture approved Interface Equipment for NARROW or WIDE BAND PRIVATE WIRE and PUBLIC SWITCHED TELEPHONE NETWORK circuits. also TELECOM LINE CIRCUIT SAFETY BARRIERS

**PARTRIDGE  
ELECTRONICS**

The Mixer People

..56 Fleet Road, Benfleet,  
Essex, SS7 5JN, England  
(Telephone 03745 3256)

**DIGITAL WATCH REPLACEMENT** parts batteries, displays, backlights etc. Also reports publications, charts. S.a.e. for full list Profords Conersdrive, Holmergreen, Bucks, HP15 6SGD

**B.C.N.U. AT THE SUSSEX MOBILE RALLY** 10.30 to 5.0pm on Sunday 18th July 1982, Brighton Race Ground, Racehill, Brighton. It's the winner for radio amateurs. Free car parking and many attractions for the whole family. Usual trade stands. All under cover.

**A LASER FOR £120.** Complete in cabinet with power supply. Send 50p for details, plus information regarding other Lasers, Holograms, available new and ex-exhibit. DHS Developments, 18 Eldred Road, Workington, Cumbria.

**MORSE TUTOR KIT,** generators, text or letter/number groups, speed, fully adjustable. P.C.B. components, case £21.71 + £3.28 V.A.T., s.a.e. details. Whitehythe Electronics Limited, Ockham Works, Ewhurst Green, Robertsbridge, E. Sussex TN325RD

**FIND-A-FRIEND** through **FIND-A-FRIEND'S** new confidential, inexpensive service. Your ideal friendship/relationship — all ages — countrywide. SAE/Telephone: **FIND-A-FRIEND (ETI)**, Temple House, 43-48 New Street, Birmingham, B2 4LH. 021-429-6346.

**AMAZING ELECTRONICS PLANS.** Lasers, Super-powered Cutting Rifle, Pistol, Light Show, Ultrasonic Force Fields, Pocket Defence Weaponry, Giant Tesla, Satellite TV Pyrotechnics, 150 more projects. Catalogue 95p — From Placentre, 16 Mill Grove, Bilbrook, Codsall, Wolverhampton.

**LYNX (Audio Processors)** — The Great New Name in Electro-Music. Revers £29.95; Fuzz/sustains £19.95; Drum synthesizers £21.95; Autowahs, phasers and custom-built multi-music processors. S.a.e. for brochure: to: Lynx (Audio Processors) 26 Aldingbourne Close, Ifield, Sussex.

**BRYPSTEPELECTRONICS**

10 Camphill Industrial Estate  
West Byfleet, Surrey KT14 6EW  
Tel: Byfleet (09323) 51676

**CMOS**

- 4001 £0.10
- 4007 £0.16
- 4008 £0.47
- 4011 £0.11
- 4012 £0.16
- 4013 £0.24
- 4015 £0.50
- 4016 £0.19
- 4017 £0.40
- 4018 £0.46
- 4021 £0.48
- 4022 £0.48
- 4023 £0.16
- 4024 £0.32
- 4025 £0.16
- 4028 £0.48
- 4040 £0.48
- 4042 £0.48
- 4047 £0.58
- 4049 £0.24
- 4050 £0.24
- 4055 £0.29
- 4056 £0.29
- 4069 £0.15
- 4070 £0.15
- 4076 £0.16
- 4081 £0.14
- 4093 £0.28
- 4503 £0.38
- 4506 £1.44
- 4510 £0.48
- 4511 £0.46
- 4512 £0.50
- 4514 £1.19
- 4515 £1.20
- 4516 £0.59
- 4518 £0.36
- 4520 £0.59
- 4525 £0.84
- 4529 £0.70
- 4531 £0.65
- 4534 £3.98
- 4541 £0.88
- 4585 £0.90

Many, many other items held in stock. S.A.E. for full stock and price list. Also separate list of items which are ex-Surplus/Liquidator stock, at bargain price. We fully guarantee your money back in FULL if any item fails, whether old or new, provided it is returned within 28 days of receipt. We have never had to return money yet.

**D Connectors (Cannon Type)**

9 Way	£0.80	£0.95	£0.90
15 Way	£1.10	1.50	£0.92
25 Way	£1.50	£2.00	£0.92
37 Way	£2.20	£3.25	£1.28

**Rt Angle P.C.B. Mtg**

9 Way	£1.17	£1.80
15 Way	£1.53	£2.32
25 Way	£2.20	£2.20
37 Way	£2.97	£4.20

**Volt Regulators**

7805	£0.39	1N4002	£0.05
7815	£0.38	1N4148	£0.03
LM309K	£1.30	1N5401	£0.15
LM323K	£4.88	1N5406	£0.16

**FREE** With every order: 1 BDX42 (INPN Darlington)

Surly: MAIL ORDER ONLY  
Please add £0.30 p&p and V.A.T. @ 15%

**SPECIAL OFFER FOR THIS ISSUE**  
4011 £0.06 4017 £0.30 4534 £3.20

**COPPER CLAD BOARD** s/s, 5p sq ins, 50p sq ft up to 6" x 6" pr 4' x 3" d/s 7p sq ins, 80p sq ft inc p&p. 29 Andrews Way, Hatt, Cornwall PL12 6PE.  
**DIGISOUND** Modular synthesiser, three vco's, two filters, reverb, etc, 49 keyboard, cased, £240. Tel 0438 72093

**USE ELECTRONICS TODAY INTERNATIONAL'S CLASSIFIED**

(35p per word, minimum 15 words. Box Nos. £2.50 extra or £10.00 per single column centimetre — all prepaid).

Just write the details on the form below and send it with your cheque, made payable to **A.S.P. Ltd, to Electronics Today International Classified, 145 Charing Cross Road, London WC2 0EE**

1.	2.	3.	4.	5.
6.	7.	8.	9.	10.
11.	12.	13.	14.	15.

Please place my ad in the next available issue of E.T.I.:

Name .....

Address .....

Tel. No. ....

I enclose my cheque/P.O. for the value of £ .....

# TRAIN FOR SUCCESS

in Television, Radio & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry. ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

## City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C&G/ICS)  
Radio Amateurs

## Certificate Courses

TV & Audio Servicing  
TV, Radio and Audio Engineering  
Radio & Amplifier Construction  
Electronic Engineering\*  
Computer Electronics\*  
Industrial Electronics\*  
Radio Frequency Electronics\*  
Introduction to Microprocessing\*  
Electrical Engineering\*  
Electrical Contracting & Installation

\*Qualify for IET Associate Membership

Approved by CACC

ICS

Established 1961



Member of ABC

POST OR PHONE TODAY FOR FREE BOOKLET

FREE BOOK

Please send your FREE School of Electronics Prospectus

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

ICS

Dept 265X  
ICS School of Electronics  
160 Stewarts Road,  
London SW8 4UJ



01 622 9911  
(all hours)

## ADVERTISEMENT INDEX

Active Component .....	88
A.D. Electronics .....	70
Ambit International .....	65
Amral .....	70
Audio Electronics .....	44 & 48
Bi-Pak.....	56
BK Electronics .....	18 & 70
Black Star .....	48
BNRS .....	16
Bradley Marshall.....	76
Cambridge Kits .....	65
Chiltmead .....	24
Clef Products .....	48
Cricklewood Electronics .....	8 & 9
Crimson Electrik .....	16
Crofton Electronics .....	70
Delta Tech.....	57
Electronize Design .....	49
Electrovalue .....	57
Enfield Electronics .....	47
Greenbank Electronics .....	42
Greenweld .....	76
Happy Memories .....	64
Hemmings Electronics .....	64
Henrys Radio .....	57 & 65
ILP .....	32 & 37
L & B Electronics.....	70
L.E.M.....	56
Magenta Electronics .....	80
Maplin .....	92
Marco Trading .....	80
Mawson Ass .....	59
Memotech .....	25
Pantechnic .....	38
Powertran .....	2 & 91
Parndon.....	65
Rapid Electronics .....	11
Relay-A-Quip .....	59
T.J. Brine.....	42
RTVC .....	59
Tempus .....	27
Swanley Electronics.....	56
Technomatic.....	32 & 33
TK Electronics .....	15
Watford Electronics .....	4 & 5
Wilmslow Audio .....	64 & 76
Woodfields Systems .....	59

# PRECISION - by POWERTRAN

THE FIRST WORDS AND THE LAST WORD IN ELECTRONIC KITS

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same — we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance — capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range — many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout — months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging... even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

**TRANSCENDENT POLYSYNTH** — A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.  
Complete kit **£275.00** plus VAT (single voice).  
Extra voice (up to three more) **42.00** plus VAT.

**EXPANDER** — A new matching 4 voice expander to team up with your polysynth for even a greater range and capability.  
Complete kit **£249.00** plus VAT.

**TRANSCENDENT DPX** — Offers a five octave keyboard with power to match. Two audio outputs (can be used simultaneously) to give harpsichord and piano/honkytonk or reed with strings/brass and both are fully polyphonic. Other features include switchable touch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly laid out instruction manual.  
Complete kit **£295.00** plus VAT.

**TRANSCENDENT 2000** — Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder — buy it, build it... play it! You will know you have made the right choice.  
Complete kit **£165.00** plus VAT.

**1024 COMPOSER** — Come right up to the minute with this new design. It will control your synthesiser with a sequence of up to 1024 notes — or an equal selection of shorter sequences. The Composer is mains powered with automatically charged battery to preserve your programme after switch-off.  
Complete kit **£85.00** plus VAT.

**DEMONSTRATION TAPE** — Demonstration tape now available of all three kits (30 minutes).  
**£2.00**



**T20 + 20** — Originally designed by Texas Engineers. This is a 20 watt amplifier with true Hi-Fi performance at a minimal cost. New features include true Toroidal transformer, new wiring, single circuit board and improved presentation. An ideal beginners project. Complete kit **£29.50** plus VAT. Also T30 + 30 - 30 watt version complete kit **£34.50** plus VAT.

**LINSLEY HOOD 75 DE LUXE** — A 75 watt amplifier originally published in Hi-Fi News. Superb performance characteristics with less than .01% distortion. Modular construction with 14 interconnecting boards — virtually no wiring so assembly is easy as is subsequent checking and maintenance. Complete kit **£75.00** plus VAT.

... Quite simply the best way to make music





## WORLD LEADERS IN ELECTRONIC KITS.

**PRICE STABILITY:** Order with confidence irrespective of any price changes we will honour all prices in this advertisement until the end of the month following the month of publication of this issue. (Errors and VAT rate changes excluded).  
**EXPORT ORDERS:** No VAT. Postage charged at actual cost plus £1 handling and documentation.  
**U.K. ORDERS:** Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Access, Barclaycard accepted.  
**SECURICOR DELIVERY:** For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.  
**SALES COUNTER:** If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m.-12 noon, 1-4.30p.m. Monday-Friday

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3NM (0264) 64455.

Order by phone **(0264) 64455**   
Simply telephone us with your order and quote your Access or Barclaycard number.  
40 page catalogue free — contains full details of all our kits.

# Make it with MAPLIN

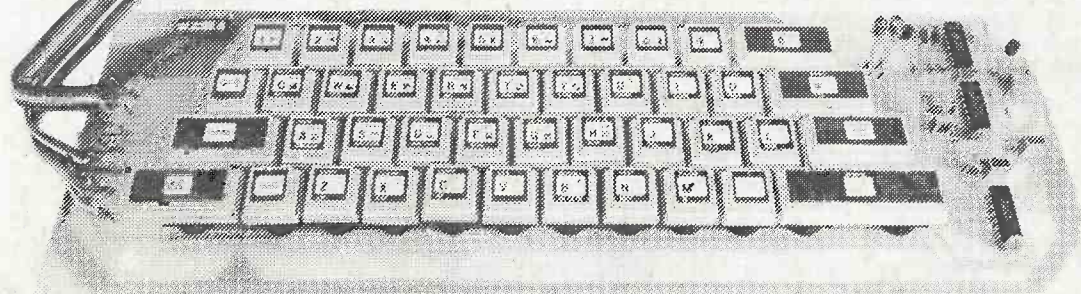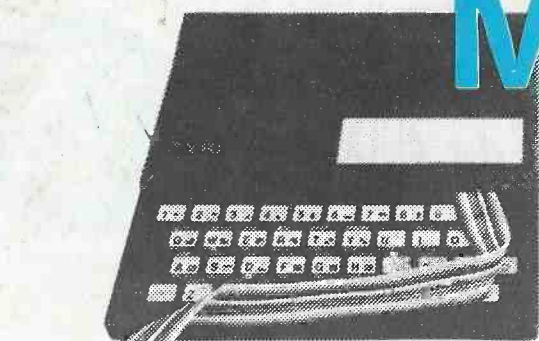


## KEYBOARD WITH ELECTRONICS FOR ZX81

- \* A full size, full travel 43-key keyboard that's simple to add to your ZX81 (no soldering in ZX81).
- \* Complete with the electronics to make "Shift Lock", "Function" and "Graphics 2" single key selections making entry far easier.
- \* Powered from ZX81's own standard power supply - with special adaptor supplied.
- \* Two-colour print for key caps.
- \* Amazing low price.

Full details in our projects book. Price 60p.  
Order As XA03D

Complete kit for only £19.95 incl. VAT and carriage.  
Order As LW72P

## 25W STEREO MOSFET AMPLIFIER

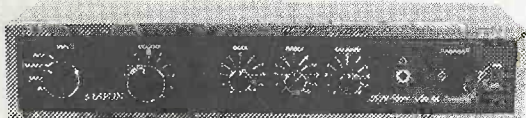

A superb new amplifier at a remarkably low price.

- \* Over 26W per channel into 8Ω at 1kHz both channels driven.
- \* Frequency response 20Hz to 40kHz ± 1dB.
- \* Low distortion, low noise and high reliability power MOSFET output stage.
- \* Extremely easy to build. Almost everything fits on main pcb, cutting interwiring to just 7 wires (plus toroidal transformer and mains lead terminations).
- \* Complete kit contains everything you need including pre-drilled and printed chassis and wooden cabinet.

Full details in our projects book. Price 60p.

Order As XA03D

Complete kit for only £49.95 incl. VAT and carriage.  
Order As LW71N

## MATINÉE ORGAN

Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50.

Order As XH55K.

Complete kits available:

Electronics - £299.95.

Cabinet - £99.50 (carriage extra).

Demo cassette price £1.99. Order As XX43W.



## HOME SECURITY SYSTEM



Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability. Full details in our projects book. Price 60p.  
Order As XA02C.

## MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.

Complete kits available.

Full details in our projects book.


Price 60p.

Order As XA02C.


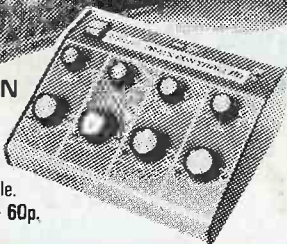
## DIGITAL MULTI-TRAIN CONTROLLER

Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available. Full details in our projects book. Price 60p.  
Order As XA02C.



Don't miss out - get a copy of our catalogue now! Over 140,000 copies sold already!

On sale now in all branches of WHSMITH price £1.

320 big pages packed with data and pictures of over 5,500 items.



## Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&pt). If I am not completely satisfied I may return the catalogue to you and have my money refunded.

If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name \_\_\_\_\_

Address \_\_\_\_\_

ET1882

# MAPLIN

ELECTRONIC SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR

Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000

Note: Shops closed Mondays