

electronics today

INTERNATIONAL

JULY 1987

£1.30

NUCLEAR STRATEGY

Electronic simulator to build

PLUS:

SURFACE MOUNTING

PROGRAMMABLE LOGIC

DEVICES

TRANSMISSION LINE

SPEAKERS

TELEPHONE ALARM



...AUDIO....COMPUTING....MUSIC....RADIO....ROBOTICS...

OMP POWER AMPLIFIER MODULES


* PRICES INCLUDE V.A.T. * PROMPT DELIVERIES * FRIENDLY SERVICE * LARGE S.A.E. 28p STAMP FOR CURRENT LIST

OMP POWER AMPLIFIER MODULES


Now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models available to suit the needs of the professional and hobby market, i.e., Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE all models include Toroidal power supply, Integral heat sink, Glass fibre P.C.B., and Drive circuits to power compatible Vu meter. Open and short circuit proof. **Supplied ready built and tested.**



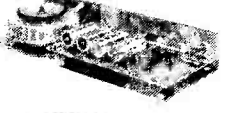OMP100 Mk II Bi-Polar Output power 110 watts R.M.S. into 4 ohms, Frequency Response 15Hz - 30KHz -3dB, T.H.D. 0.01%, S.N.R. -118dB, Sens for Max. output 500mV at 10K, Size 355 x 115 x 65mm. **PRICE £33.99 + £3.00 P&P.**



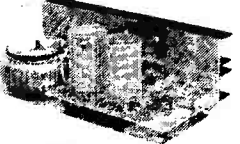OMP/MF100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 80, Slew Rate 45V/uS, T.H.D. Typical 0.002%, Input Sensitivity 500mV, S.N.R. -125dB, Size 300 x 123 x 60mm. **PRICE £39.99 + £3.00 P&P.**



OMP/MF200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 250, Slew Rate 50V/uS, T.H.D. Typical 0.001%, Input Sensitivity 500mV, S.N.R. -130dB, Size 300 x 150 x 100mm. **PRICE £62.99 + £3.50 P&P.**



OMP/MF300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, Frequency Response 1Hz - 100KHz -3dB, Damping Factor 350, Slew Rate 60V/uS, T.H.D. Typical 0.0008%, Input Sensitivity 500mV, S.N.R. -130dB, Size 330 x 147 x 102mm. **PRICE £79.99 + £4.50 P&P.**

NOTE: Mos-Fets are supplied as standard (100KHz bandwidth & Input Sensitivity 500mV). If required, P.A. version (50KHz bandwidth & Input Sensitivity 775mV) Order - Standard or P.A.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.F.D. diodes (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control circuits for very fast rise and decay times. Tough moulded plastic case, with tinted acrylic front. Size 84 x 27 x 45mm. **PRICE £8.50 + 50p P&P.**

LOUDSPEAKERS 5" to 15" up to 400 WATTS R.M.S. Cabinet Fixing in stock. Huge selection of McKenzie Loudspeakers available including Cabinet Plans. Large S.A.E. (28p) for free details.



POWER RANGE
8" 50 WATT R.M.S. Hi-Fi/Disco.
20 oz magnet 1" ally voice coil. Ground ally fixing escutcheon Res. Freq. 40Hz Freq. Resp. to 6KHz Sens. 92dB PRICE £10.99 Available with black grille £11.99 P&P £1.50 ea
12" 100 WATT R.M.S. Hi-Fi/Disco
50 oz magnet 2" ally voice coil. Ground ally fixing escutcheon Die cast chassis White cone Res. Freq. 25Hz Freq. Resp. to 4KHz Sens. 95dB PRICE £28.60 + £3.00 P&P ea

McKENZIE
12" 85 WATT R.M.S. C1285GP Lead Guitar/keyboard/Disco
2" ally voice coil Ally centre dome Res. Freq. 45Hz Freq. Resp. to 6.5KHz Sens. 98dB PRICE £29.99 + £3.00 P&P ea.
12" 85 WATT R.M.S. C1285TC P.A./Disco 2" ally voice coil. Twin cone.
Res. Freq. 45Hz Freq. Resp. to 14KHz PRICE £31.49 + £3.00 P&P ea
15" 150 WATT R.M.S. C15 Bass Guitar/Disco.
3" ally voice coil Die-cast chassis Res. Freq. 40Hz Freq. Resp. to 4KHz PRICE £57.87 + £4.00 P&P ea
10" 60 WATT R.M.S. 1060GP Gen. Purpose/Lead Guitar/Keyboard/Mid. P.A.
2" voice coil. Res. Freq. 75Hz Freq. Resp. to 7.5KHz Sens. 99dB. PRICE £19.99 + £2.00 P&P
10" 200 WATT R.M.S. C10200GP Guitar, Keyboard, Disco.
2" voice coil. Res. Freq. 45Hz Freq. Resp. to 7KHz Sens. 101dB PRICE £44.76 + £3.00 P&P
15" 200 WATT R.M.S. C15200 High Power Bass.
Res. Freq. 40Hz Freq. Resp. to 5KHz Sens. 101dB. PRICE £62.41 + £4.00 P&P
15" 400 WATT R.M.S. C15400 High Power Bass.
Res. Freq. 40Hz Freq. Resp. to 4KHz Sens. 102dB PRICE £89.52 + £4.00 P&P.

WEM
5" 70 WATT R.M.S. Multiple Array Disco etc.
1" voice coil Res. Freq. 52Hz Freq. Resp. to 5KHz Sens. 89dB PRICE £22.00 + £1.50 P&P ea
8" 150 WATT R.M.S. Multiple Array Disco etc.
1" voice coil. Res. Freq. 46Hz Freq. Resp. to 5KHz Sens. 92dB PRICE £32.00 + £1.50 P&P ea.
10" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 92dB PRICE £36.00 + £2.00 P&P ea.
12" 300 WATT R.M.S. Disco/Sound re-enforcement etc.
1 1/2" voice coil Res. Freq. 35Hz Freq. Resp. to 4KHz Sens. 94dB PRICE £47.00 + £3.00 P&P ea

SOUNDLAB (Full Range Twin Cone)
5" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil Res. Freq. 63Hz Freq. Resp. to 20KHz Sens. 86dB PRICE £9.99 + £1.00 P&P ea
6" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1" voice coil Res. Freq. 56Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £10.99 + £1.50 P&P ea
8" 60 WATT R.M.S. Hi-Fi/Multiple Array Disco etc.
1 1/2" voice coil Res. Freq. 38Hz Freq. Resp. to 20KHz Sens. 89dB PRICE £12.99 + £1.50 P&P ea
10" 60 WATT R.M.S. Hi-Fi/Disco etc.
1 1/2" voice coil Res. Freq. 35Hz Freq. Resp. to 15KHz Sens. 89dB PRICE £16.49 + £2.00 P&P

PANTEC HOBBY KITS. Proven designs including glass fibre printed circuit board and high quality components complete with instructions.

FM MICROTRANSMITTER (BUG) 90/105MHz with very sensitive microphone. Range 100/300 metres. 57 x 46 x 14mm (9 volt). Price: £8.62 + 75p P&P.

3 WATT FM TRANSMITTER 3 WATT 85/115MHz varicap controlled professional performance. Range up to 3 miles 35 x 84 x 12mm (12 volt) Price: £14.49 + 75p P&P.

SINGLE CHANNEL RADIO CONTROLLED TRANSMITTER/RECEIVER 27MHz. Range up to 500 metres. Double coded modulation. Receiver output operates relay with 2amp/240 volt contacts. Ideal for many applications. Receiver 90 x 70 x 22mm (9/12 volt). Price: £17.82 Transmitter 80 x 50 x 15mm (9/12 volt). Price: £11.29 P&P + 75p each. S.A.E. for complete list.



3 watt FM Transmitter

BURGLAR ALARM

Better to be 'Alarmed' than terrified. **Thandar's famous 'Minder' Burglar Alarm System.** Superior microwave principle. Supplied as three units, complete with interconnection cable **FULLY GUARANTEED.**

Control Unit - Houses microwave radar unit, range up to 15 metres adjustable by sensitivity control. Three position, key operated fascia switch - off - test - armed. 30 second exit and entry delay.

Indoor alarm - Electronic swept freq. siren 104dB output.


Outdoor Alarm - Electronic swept freq. siren 98dB output. Housed in a tamper-proof heavy duty metal case.

Both the control unit and outdoor alarm contain rechargeable batteries which provide full protection during mains failure. Power requirement 200/260 Volt AC 50/60Hz. Expandable with door sensors, panic buttons etc. Complete with instructions.

SAVE £138.00 Usual Price £228.85
BKE's PRICE £89.99 + £4.00 P&P

Why buy a collection of self assembly boards!

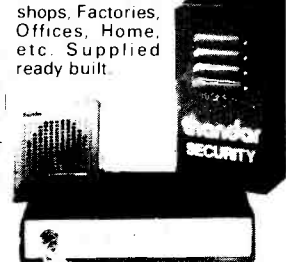
IDEAL for Work-shops, Factories, Offices, Home, etc. Supplied ready built.



OMP LINNET LOUDSPEAKERS

The very best in quality and value. Made specially to suit today's need for compactness with high sound output levels. Finished in hard wearing black vinyl with protective corners, grille and carry handle. All models 8 ohms Full range 45Hz - 20KHz Size 20" x 15" x 12" Watts R.M.S. per cabinet Sensitivity 1W 1mtr dB

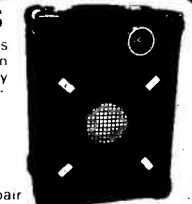OMP 12-100 Watts 100dB. Price £149.99 per pair.
OMP 12-200 Watts 102dB. Price £199.99 per pair. Delivery Securicor £8.00 per pair



OMP 19" STEREO RACK AMPS



Professional 19" cased Mos-Fet stereo amps. Used the World over in clubs, pubs, discos etc. With twin Vu meters, twin toroidal power supplies. XLR connections. MF600 Fan cooled. **Three models (Ratings R.M.S. into 4 ohms). Input Sensitivity 775mV.**
MF200 (100 + 100)W. £169.00 Securicor
MF400 (200 + 200)W. £228.85 Delivery
MF600 (300 + 300)W. £322.00 £10.00

1 K-WATT SLIDE DIMMER

* Control loads up to 1Kw
* Compact Size 4 1/2" x 1" x 2 1/2"
* Easy snap in fixing through panel cabinet cut out
* Insulated plastic case
* Full wave control using 8 amp triac
* Conforms to BS800

* Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's, theatres etc.
PRICE £13.99 - 75p P&P



BSR P295 ELECTRONIC TURNTABLE

* Electronic speed control 45 & 33 r.p.m. * Plus Minus variable pitch control * Belt driven * Aluminium platter with strobed rim * Cue lever * Anti-skate (bias device) * Adjustable counter balance * Manual arm * Standard 1 1/2" cartridge fixings * Supplied complete with cut out template * D.C. Operation 9-14V D.C. 65mA
Price £36.99 £3.00 P&P




ADC Q4 mag. cartridge for above. Price £4.99 ea. P&P 50p

PIEZO ELECTRIC TWEETERS - MOTOROLA


Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series) **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**

TYPE 'A' (KSN2036A) 3" round with protective wire mesh, ideal for bookshelf and medium sized Hi-fi speakers. Price £4.90 each + 40p P&P.
TYPE 'B' (KSN1005A) 3 1/2" super horn. For general purpose speakers, disco and P.A. systems etc. Price £5.99 each + 40p P&P.
TYPE 'C' (KSN6016A) 2" x 5" wide dispersion horn. For quality Hi-fi systems and quality discos etc. Price £6.99 each + 40p P&P.
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid range (2KHz). Suitable for high quality Hi-fi systems and quality discos. Price £9.99 each + 40p P&P.
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-fi monitor systems etc. Price £5.99 each + 40p P&P.
LEVEL CONTROL Combines on a recessed mounting plate, level control and cabinet input jack socket. 85 x 85 mm. Price £3.99 + 40p P&P.

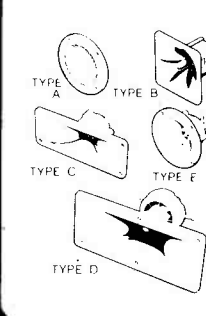

STEREO DISCO MIXER

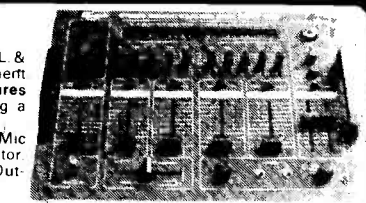STEREO DISCO MIXER with 2 x 5 band L & R graphic equalisers and twin 10 segment L.E.D. Vu Meters. Many outstanding features. 5 Inputs with individual faders providing a useful combination of the following:-
3 Turntables (Mag), 3 Mics, 4 Line plus Mic with talk over switch. Headphone Monitor. Pan Pot. L & R Master Output controls. Output 775mV. Size 360 x 280 x 90mm.
Price £134.99 - £3.00 P&P




B. K. ELECTRONICS DEPT ETI
UNIT 5, COMET WAY, SOUTHEND-ON-SEA,
ESSEX, SS2 6TR. TEL: 0702-527572

POSTAL CHARGES PER ORDER £1.00 minimum. OFFICIAL ORDERS WELCOME. SCHOOLS, COLLEGES, GOVERNMENT BODIES, ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER VISA/ACCESS/C.O.D. ACCEPTED.



electronics today

INTERNATIONAL JULY 1987 VOL 16 No. 7

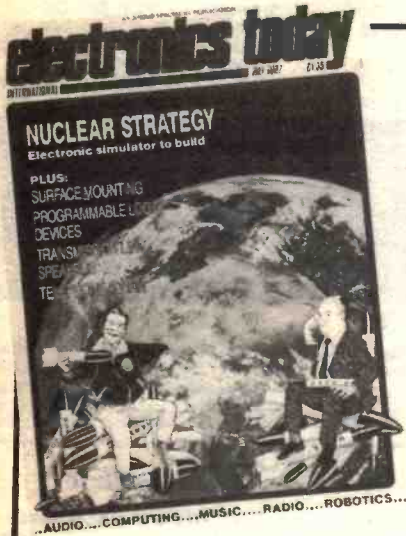

Cover photograph courtesy
ESA/Meteosat

Geoff Bains: Editor
Ian Pitt: Deputy Editor
Paul Chappell: Projects Editor
Jerry Fowler: Technical Illustrator
Angela Farrell: Ad Manager
Nicola Baty:
Classified Sales Executive
Andrew Selwood: Copy Control
Dave Bradshaw:
Group Editor — Electronics

PUBLISHED BY:
Argus Specialist Publications Ltd.,
1 Golden Square, London W1R 3AB.

DISTRIBUTED BY:
Argus Press Sales & Distribution Ltd.,
12-18 Paul Street, London EC2A 4JS.
(British Isles).

TYPESET BY:
Project Three.

PRINTED BY:
Adlard & Son Ltd, The Garden City Press.

COVERS PRINTED BY:
Loxley Brothers Ltd.

ISSN
0142-7229



Member of the
Audit Bureau
of Circulation

Electronics Today is normally published on the first Friday in the month preceding cover date. The contents of this publication including all articles, designs, plans, drawings and programs and all copyright and other intellectual property rights therein belong to Argus Specialist Publications Limited. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Argus Specialist Publications Limited and any reproduction requires the prior written consent of the Company. © 1987 Argus Specialist Publications Ltd. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

■ Subscription Rates. UK: £18.10, Overseas: £22.50. USA: \$29.50, Airmail: £49.50.

EDITORIAL AND ADVERTISEMENT OFFICE

1 Golden Square, London W1R 3AB. Telephone 01-437 0626.
Telex 8811896.

FEATURES

ALL ABOVE BOARD13
Is small really beautiful? Mike Bedford certainly thinks so and he's been looking into the increasingly popular use of tiny surface mounting components.

CIRCUIT THEORY18
Paul Chappell continues to fathom Fourier and finds it's all not as tricky as it first appears.

HARDWARE DESIGN CONCEPTS.....21
Top breeders recommend PAL. Who is Mike Barwise to argue with that?

He's found PALs are no use for strong bones and a healthy coat but wonderful for saving space and money.

RED CURRY26
Helen Armstrong talks to Sinclair's main rival in the 'Founding father of British home computing' stakes.

PROJECT INDEX 1972-1987Centre Pages
The final pull-out part of the indispensable guide to all of ETI's long history of projects.

PROJECTS

NUCLEAR STRATEGY SIMULATOR28
David Guinness has found détente is not all it's cracked up to be. His simulator lets you prove the point for yourself.

THE ETI KAPELMEISTERS.....33
Vivian Capell's novel transmission line loudspeakers are cheap to build, small and sound wonderful. What more could you ask for?

MIDI MASTER KEYBOARD40
John Yau's keyboard is really shaping up now with the final circuit board and details of the cabinet construction.

TELEPHONE ALARM44
Barry Taylor has come up with an ingenious way of keeping tabs on his house. Intruders beware!

TECH TIPS52
Some more circuit ideas hot off the backs of readers' envelopes.

REGULARS

NEWS6
NEXT MONTH8
DIARY9
READ/WRITE11
SPECIAL OFFER38
PHOTOCOPIES54
BACKNUMBERS54
PLAYBACK48
BOOK LOOK48

KEYNOTES49
OPEN CHANNEL49
PCB SERVICE50
READERS' FREE ADS53
PCB FOILS56
VELLEMAN KITS OFFER58

CLASSIFIED ADS60
AD INDEX62

BBC Micro Computer System

BBC Master Series
 AMB15 BBC MASTER includes one free ROM cartridge £385 (a)
 AMB12 BBC MASTER Econet computer £315 (a)
 AMC06 Turbo (65C102) Expansion Module £99 (b)
 ADF14 Rom Cartridge £13 (d)
 ADF10 Econet Module £41 (c)
 ADJ22 Ref. Manual Part I £14 (c)
 ADJ23 Ref. Manual Part II £14 (c)
 ADJ24 Advanced Ref Manual £19.50 (c)
ACORN ADD-ON PRODUCTS
 Universal 2nd Processor £75 (b)
 TORCH ZEP 100 £229 (a)
 Multifom Z80 2nd Processor £289 (b)
 Acorn Teletext Adaptor £95 (b)
 Acorn IEEE Interface £265 (a)
BBC Master Compact
SYSTEM 1
 128K, Single 640K Drive & bundled software £385 (a)
SYSTEM 2
 System 1 with a 12" Med Res RGB Monitor £469 (a)
SYSTEM 3
 System 1 with a 14" Med Res RGB Monitor £599 (a)

Second Drive Kit £99 (c)
UPGRADE KITS
 1770 DFS Upgrade for Model B £43.50 (d)
 Basic II ROM £22.50 (d)
 1.2 OS ROM £15 (d)
 DNFS ROM £17.50 (d)
 DNFS Rom (for B with 1770 DFS & B Plus) £26 (d)

ECONET ACCESSORIES
 Econet Starter kit £85 (d)
 Econet Socket Set £29 (c)
 Econet Bridge £174 (b)
 File Server Level II £75 (d)
 Printer Server Rom £41 (d)
 10 Station Lead set £26 (c)
 Adv. Econet User Guide £10 (d)

COMMUNICATIONS ROMS
 Termlator £25 (d)
 Communicator £49 (d)
 Commstar £28 (d)
DATABEEB £24 (d)

BBC FIRMWARE & SOFTWARE
 Database Management Systems, Word Processors, Languages, Spreadsheets, Utilities
 For full details on the wide range of above packages please write to us.

ACCESSORIES

EPSON
 FX plus sheet feeder £129.00 (b)
 LX80 Sheet feeder £49.00 (b)
 Paper Roll Holder £17.00 (d)
Interfaces: 8143 RS232 £28.00 (c)
 8132 Apple II £86.00 (c)
 8165 IEEE + cable £85.00 (c)
 8177P NLQ (FX80+FX100) £99 (d)
Serial & Parallel Interfaces with larger buffers available.
Ribbons: RX/FX 100/100+ £9.00 (d)
 RX/FX 80/80+ £4.00 (d)
 LX80 £4.50 (d)
Spare pens for H180 £8.25/set (d)
 FX80 Tractor Attachment (c)

RS232 Interface + 2K Buffer £63 (c)
 Ribbon KP810/910/815/915 £6.00 (d)
JUKI:
 RS232 Interface £65 (c)
 Spare Daisy Wheel £14.00 (d)
 Ribbon £12.00 (d)
 Sheet Feeder £182 (a)
 Tractor Feed Attachment £149 (a)

Sheet Feeder £239 (a)
 Tractor Feeder £116 (a)
 Ribbons Carbon or Nylon £3.00 (d)
 Red Correction Ribbon £2.00 (d)
BBC Printer Lead:
 Parallel (1.2m) £6.00 (d)
 Serial (1.2m) £7.00 (d)
 Printer Leads can be supplied to any length.

EPSON
 LX86NLQ (80 col) £199 (a)
 EX800 £409 (a)
 EX1000 £579 (a)
 EX1000 £579 (a)
 LQ800 (80 col) £439 (a)
 LQ1000 (136 col) £589 (a)
 JX80 4 colour £229 (a)
 FX800 £329 (a)
 FX100 £499 (a)
TAXAN KP815 (80 col) NLQ £269 (a)
TAXAN KP915 (156 col) £369 (a)

NATIONAL PANASONIC
 KXP1081 (80 col) £169 (a)

NATIONAL PANASONIC
 KXP 3131 £249 (a)

STAR NL10 (IBM Interface) £209 (a)

JUKI 6100 Daisy Wheel £259 (a)

BROTHER HR20 £329 (a)

INTEGREX Multicolour £525 (a)

HITACHI 672 A3 Plotter £459 (a)

Paper:
 2000 Sheets Fanfold:
 9.5" x 11" £13 (b)
 14.5" x 11" £18.50 (b)
Labels: (per 1000)
 3.5" x 17/16" Single row £5.25 (d)
 27/16" x 17/16" Triple row £5.00 (d)

MODEMS

— All modems listed below are BT approved

MIRACLE 3000:
 MIRACLE WS2000 V21/23 Manual £95 (b)
 MIRACLE WS4000 V21/23. (Hayes Compatible, Intelligent, Auto Dial/Auto Answer) £149 (b)
 MIRACLE WS3000 V21/V23 As SW4000 and with BELL standards and battery pack up for memory £295 (b)
 MIRACLE WS3000 V22 As WS3000 V21/V23 but with 1200 baud full duplex £495 (b)
 MIRACLE WS3000 V22 bis As V22 and 2400 baud full duplex £650 (b)
 The price of WS4000 & WS 3000 Modems includes a Commstar II ROM and BBC Data Cable.

DATATALK Comms Package if purchased with any of the above modems* £79 (c)
PACE: Nightingale Modem V21/V23 Manual £75 (b)

Serial Test Cable
 Serial Cable switchable at both ends allowing pin options to be re-routed or linked at either end using a 10 way switch making it possible to produce almost any cable configuration on site.
 Available as M/M or M/F £24.75 (d)

DISC DRIVES
 These are fully cased and wired drives with slim line high quality mechanisms. Drives supplied with cables manuals and formatting disc suitable for the BBC computer. All 80 track drives are supplied with 40/80 track switching as standard. All drives can operate in single or dual density format. All floppy drives carry a two year warranty.

PD800P (2 x 400K/2 x 640K 40/80T DS) with built in monitor stand £249 (a)
 PD800 (2 x 400K/2 x 640K 40/80T DS) £229 (a)
 TD800 (as PD800 but without psu) £199 (a)
 TS400 1 x 400K/1 x 640K 40/80T DS £114 (b)
 PS400 with psu 1 x 400K/1 x 640K 40/80T DS £129 (b)
3.5" DRIVES
 1 x 400K/1 x 640K 80T DS £75 (b)
 TS35 1 £119 (b)
 2 x 400K/1 x 640K 80T DS £135 (b)
 TD35 2 £187 (b)
 PD35 2 with psu £187 (b)

3M FLOPPY DISCS

High quality discs that offer a reliable error free performance for life. Each disc is individually tested and guaranteed for life. Ten discs are supplied in a sturdy cardboard box.

5 1/4" DISCS
 40T SS DD £10.00 (d) 40T DS DD £12.00 (d) 80T SS DD £20.00 (d)
 80T SS DD £14.50 (d) 80T DS DD £15.50 (d) 80T DS DD £25.00 (d)

DISC ACCESSORIES

FLOPPICLENE Disc Head Cleaning Kit with 20 disposable cleaning discs ensures continued optimum performance of the drives: 3 1/2" £16 (d), 5 1/4" £14.50 (d)
 Single Disc Cable £6 (d) Dual Disc Cable £8.50 (d)
 10 Disc Library Case £1.00 (c) 30 Disc Case £6 (c)
 40 Disc Lockable Box £8.50 (c) 100 Disc Lockable Box £13 (c)

MONITORS

All 14" monitors now available in plastic or metal cases, please specify.

MICROVITEC: 14" RGB
 1431 Std Res £179 (a) 1431 AP Std Res £199 (a)
 1451 med Res £225 (a) 1451 AP Med Res £259 (a)
 1441 Hi Res £365 (a)
 Swivel Base for Plastic 14" Microvitecs £20 (c)

20" RGB with PAL & Audio
 2030CS Std Res £380 (a) 2040CS Hi Res £885 (a)
TAXAN SUPERVISION 620 12" High Resolution £279 (a)
TAXAN SUPERVISION 625 with amber/green option, BBC & IBM £329 (a)
MITSUBISHI XC1404 14" RGB Med Res IBM & BBC Compatible £219 (a)

TAXAN KX 1201G Hi Res 12" Etched Green Screen £85 (a)
TAXAN KX1202G Hi Res 12" Long Persistence (P39) £95 (a)
TAXAN KX 1203A Hi Res 12" Etched Amber Screen £95 (a)
PHILIPS BM7502 12" Hi Res Green Screen £75 (a)
PHILIPS BM7522 12" Hi Res Amber Screen £75 (a)

Swivel Base for Taxan Monochrome fitted with Digital Clock £21 (c)

SPECIAL OFFER
 2764-25 £2.50
 27128-25 £2.75
 6264LP-15 £2.80

ATTENTION
 All prices in this double page advertisement are subject to change without notice.
ALL PRICES EXCLUDE VAT
 Please add carriage 50p unless indicated as follows:
 (a) £8 (b) £2.50 (c) £1.50 (d) £1.00

Serial Mini Patch Box
 Allows an easy method to reconfigure pin functions without rewiring the cable assembly. Jumpers can be used and reused. £22 (d)

Serial Mini Test
 Monitors RS232C and CITT V24 Transmissions, indicating status with dual colour LEDs on 7 most significant lines. Connects in Line. £22.50 (d)

CONNECTOR SYSTEMS

I.D. CONNECTORS	EDGE CONNECTORS	AMPHENOL CONNECTORS	RIBBON																																																																																																														
<p>(Speedblock Type)</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>No of ways</th> <th>Header Plug</th> <th>Receptacle</th> <th>Edge Conn.</th> </tr> <tr> <td>10</td> <td>90p</td> <td>85p</td> <td>120p</td> </tr> <tr> <td>20</td> <td>145p</td> <td>125p</td> <td>195p</td> </tr> <tr> <td>26</td> <td>175p</td> <td>150p</td> <td>240p</td> </tr> <tr> <td>34</td> <td>200p</td> <td>180p</td> <td>320p</td> </tr> <tr> <td>40</td> <td>220p</td> <td>190p</td> <td>340p</td> </tr> <tr> <td>50</td> <td>235p</td> <td>200p</td> <td>390p</td> </tr> </table>	No of ways	Header Plug	Receptacle	Edge Conn.	10	90p	85p	120p	20	145p	125p	195p	26	175p	150p	240p	34	200p	180p	320p	40	220p	190p	340p	50	235p	200p	390p	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>2 x 6-way (commodore)</th> <th>0.1"</th> <th>0.156"</th> </tr> <tr> <td>2 x 10-way</td> <td>150p</td> <td>300p</td> </tr> <tr> <td>2 x 12-way (vic 20)</td> <td>—</td> <td>350p</td> </tr> <tr> <td>2 x 18-way</td> <td>—</td> <td>140p</td> </tr> <tr> <td>2 x 23-way (ZX81)</td> <td>175p</td> <td>220p</td> </tr> <tr> <td>2 x 25-way</td> <td>225p</td> <td>220p</td> </tr> <tr> <td>2 x 28-way (Spectrum)</td> <td>200p</td> <td>—</td> </tr> <tr> <td>2 x 36-way</td> <td>250p</td> <td>—</td> </tr> <tr> <td>1 x 43-way</td> <td>260p</td> <td>—</td> </tr> <tr> <td>2 x 22-way</td> <td>190p</td> <td>—</td> </tr> <tr> <td>2 x 43-way</td> <td>395p</td> <td>—</td> </tr> <tr> <td>1 x 77-way</td> <td>400p</td> <td>500p</td> </tr> <tr> <td>2 x 50-way (S100conn)</td> <td>600p</td> <td>—</td> </tr> </table>	2 x 6-way (commodore)	0.1"	0.156"	2 x 10-way	150p	300p	2 x 12-way (vic 20)	—	350p	2 x 18-way	—	140p	2 x 23-way (ZX81)	175p	220p	2 x 25-way	225p	220p	2 x 28-way (Spectrum)	200p	—	2 x 36-way	250p	—	1 x 43-way	260p	—	2 x 22-way	190p	—	2 x 43-way	395p	—	1 x 77-way	400p	500p	2 x 50-way (S100conn)	600p	—	<table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th colspan="2">Solder</th> <th>ZDC</th> </tr> <tr> <td>36 way plug</td> <td>500p</td> <td>475p</td> </tr> <tr> <td>36 way skt</td> <td>550p</td> <td>500p</td> </tr> <tr> <td>24 way plug</td> <td>—</td> <td>—</td> </tr> <tr> <td>IEEE</td> <td>475p</td> <td>475p</td> </tr> <tr> <td>24 way skt</td> <td>—</td> <td>—</td> </tr> <tr> <td>IEEE</td> <td>500p</td> <td>500p</td> </tr> <tr> <td>PCB Mtg Skt Ang Pin</td> <td>—</td> <td>—</td> </tr> <tr> <td>24 way 700p</td> <td>—</td> <td>36way 750p</td> </tr> </table>	Solder		ZDC	36 way plug	500p	475p	36 way skt	550p	500p	24 way plug	—	—	IEEE	475p	475p	24 way skt	—	—	IEEE	500p	500p	PCB Mtg Skt Ang Pin	—	—	24 way 700p	—	36way 750p	<p>(grey/metre)</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>10-way</td> <td>40p</td> <td>34-way</td> <td>160p</td> </tr> <tr> <td>16-way</td> <td>60p</td> <td>40-way</td> <td>180p</td> </tr> <tr> <td>20-way</td> <td>85p</td> <td>50-way</td> <td>200p</td> </tr> <tr> <td>26-way</td> <td>120p</td> <td>64-way</td> <td>280p</td> </tr> </table>	10-way	40p	34-way	160p	16-way	60p	40-way	180p	20-way	85p	50-way	200p	26-way	120p	64-way	280p
No of ways	Header Plug	Receptacle	Edge Conn.																																																																																																														
10	90p	85p	120p																																																																																																														
20	145p	125p	195p																																																																																																														
26	175p	150p	240p																																																																																																														
34	200p	180p	320p																																																																																																														
40	220p	190p	340p																																																																																																														
50	235p	200p	390p																																																																																																														
2 x 6-way (commodore)	0.1"	0.156"																																																																																																															
2 x 10-way	150p	300p																																																																																																															
2 x 12-way (vic 20)	—	350p																																																																																																															
2 x 18-way	—	140p																																																																																																															
2 x 23-way (ZX81)	175p	220p																																																																																																															
2 x 25-way	225p	220p																																																																																																															
2 x 28-way (Spectrum)	200p	—																																																																																																															
2 x 36-way	250p	—																																																																																																															
1 x 43-way	260p	—																																																																																																															
2 x 22-way	190p	—																																																																																																															
2 x 43-way	395p	—																																																																																																															
1 x 77-way	400p	500p																																																																																																															
2 x 50-way (S100conn)	600p	—																																																																																																															
Solder		ZDC																																																																																																															
36 way plug	500p	475p																																																																																																															
36 way skt	550p	500p																																																																																																															
24 way plug	—	—																																																																																																															
IEEE	475p	475p																																																																																																															
24 way skt	—	—																																																																																																															
IEEE	500p	500p																																																																																																															
PCB Mtg Skt Ang Pin	—	—																																																																																																															
24 way 700p	—	36way 750p																																																																																																															
10-way	40p	34-way	160p																																																																																																														
16-way	60p	40-way	180p																																																																																																														
20-way	85p	50-way	200p																																																																																																														
26-way	120p	64-way	280p																																																																																																														
<p>D CONNECTORS</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>No of Ways</th> <th>9</th> <th>15</th> <th>25</th> <th>37</th> </tr> </table> <p>MALE: Ang. Pins 120 180 230 350 Solder 60 85 125 170 IDC 175 275 325</p> <p>FEMALE: St Pin 100 140 210 380 Ang. pins 160 210 275 440 Solder 90 130 195 290 IDC 195 325 375 St Hood 90 95 100 120 Screw 130 150 175</p>	No of Ways	9	15	25	37	<p>EURO CONNECTORS</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>DIN 41612</th> <th>Plug</th> <th>Socket</th> </tr> <tr> <td>2 x 32 way St Pin</td> <td>230p</td> <td>275p</td> </tr> <tr> <td>2 x 32 way Ang Pin</td> <td>275p</td> <td>320p</td> </tr> <tr> <td>3 x 32 way St Pin</td> <td>260p</td> <td>300p</td> </tr> <tr> <td>3 x 32 way Ang Pin</td> <td>375p</td> <td>400p</td> </tr> <tr> <td>IDC Skt A + B</td> <td>—</td> <td>400p</td> </tr> <tr> <td>IDC Skt A + C</td> <td>—</td> <td>400p</td> </tr> </table> <p>For 2 x 32 way please specify spacing (A + B, A + C).</p>	DIN 41612	Plug	Socket	2 x 32 way St Pin	230p	275p	2 x 32 way Ang Pin	275p	320p	3 x 32 way St Pin	260p	300p	3 x 32 way Ang Pin	375p	400p	IDC Skt A + B	—	400p	IDC Skt A + C	—	400p	<p>GENDER CHANGERS 25 way D type</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>Male to Male</td> <td>£10</td> </tr> <tr> <td>Male to Female</td> <td>£10</td> </tr> <tr> <td>Female to Female</td> <td>£10</td> </tr> </table> <p>RS 232 JUMPERS:</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <td>(25 way D)</td> <td>£5.00</td> </tr> <tr> <td>24" Single end Male</td> <td>£5.25</td> </tr> <tr> <td>24" Single end Female</td> <td>£5.25</td> </tr> <tr> <td>24" Female Female</td> <td>£10.00</td> </tr> <tr> <td>24" Male Male</td> <td>£9.50</td> </tr> <tr> <td>24" Male Female</td> <td>£9.50</td> </tr> </table>	Male to Male	£10	Male to Female	£10	Female to Female	£10	(25 way D)	£5.00	24" Single end Male	£5.25	24" Single end Female	£5.25	24" Female Female	£10.00	24" Male Male	£9.50	24" Male Female	£9.50	<p>DIL HEADERS</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>Solder</th> <th>IDC</th> </tr> <tr> <td>14 pin</td> <td>40p</td> </tr> <tr> <td>16 pin</td> <td>50p</td> </tr> <tr> <td>18 pin</td> <td>60p</td> </tr> <tr> <td>20 pin</td> <td>75p</td> </tr> <tr> <td>24 pin</td> <td>100p</td> </tr> <tr> <td>28 pin</td> <td>180p</td> </tr> <tr> <td>40 pin</td> <td>200p</td> </tr> <tr> <td></td> <td>225p</td> </tr> </table>	Solder	IDC	14 pin	40p	16 pin	50p	18 pin	60p	20 pin	75p	24 pin	100p	28 pin	180p	40 pin	200p		225p																																																
No of Ways	9	15	25	37																																																																																																													
DIN 41612	Plug	Socket																																																																																																															
2 x 32 way St Pin	230p	275p																																																																																																															
2 x 32 way Ang Pin	275p	320p																																																																																																															
3 x 32 way St Pin	260p	300p																																																																																																															
3 x 32 way Ang Pin	375p	400p																																																																																																															
IDC Skt A + B	—	400p																																																																																																															
IDC Skt A + C	—	400p																																																																																																															
Male to Male	£10																																																																																																																
Male to Female	£10																																																																																																																
Female to Female	£10																																																																																																																
(25 way D)	£5.00																																																																																																																
24" Single end Male	£5.25																																																																																																																
24" Single end Female	£5.25																																																																																																																
24" Female Female	£10.00																																																																																																																
24" Male Male	£9.50																																																																																																																
24" Male Female	£9.50																																																																																																																
Solder	IDC																																																																																																																
14 pin	40p																																																																																																																
16 pin	50p																																																																																																																
18 pin	60p																																																																																																																
20 pin	75p																																																																																																																
24 pin	100p																																																																																																																
28 pin	180p																																																																																																																
40 pin	200p																																																																																																																
	225p																																																																																																																
<p>SOFTY II This low cost intelligent eprom programmer can program 2716, 2516, 2532, 2732, and with an adaptor, 2564 and 2764. Displays 512 byte page on TV — has a serial and parallel I/O routines. Can be used as an emulator, cassette interface. Softy II £195 (b) Adaptor for 2764/2564. £25.00 (c)</p>	<p>TEXTOL ZIF</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <tr> <th>SOCKETS</th> <th>24-pin</th> <th>40-pin</th> </tr> <tr> <td></td> <td>£7.50</td> <td>£12</td> </tr> <tr> <td></td> <td>28-pin</td> <td>£9.00</td> </tr> </table>	SOCKETS	24-pin	40-pin		£7.50	£12		28-pin	£9.00	<p>UV ERASERS All erasers with built in safety switch and mains indicator. UV1 B erases up to 6 eproms at a time. £47 (c) UV1 T as above but with a timer £59 (c) UV140 erases up to 14 eproms at a time. £88 (b) UV141 as above but with a timer. £88 (b)</p>	<p>TECHNOLINE VIEWDATA SYSTEM Using 'Prestel' type protocols for information and orders phone 01-450 9764. 24 hour service, 7 days a week.</p>																																																																																																					
SOCKETS	24-pin	40-pin																																																																																																															
	£7.50	£12																																																																																																															
	28-pin	£9.00																																																																																																															


- Greenweld is planning to celebrate summer by having a clear out of all its old 'Bargain List' stock. From June 15th there will be big price reductions on many items with some on sale for half price. Those who already have a Greenweld catalogue can obtain a sale price list free-of-charge while new customers will have to pay £1.00 for the catalogue and price list. Greenweld Electronics Ltd, 443 Millbrook Road, Southampton SO1 0HX. Tel: (0703) 772 501.

- Test equipment specialist Alpha Electronics has issued its Spring 1987 catalogue. Its six pages list a selection of analogue and digital multimeters plus attenuators, leads, pocket electrical testers and probes measuring temperature and rotational speed. The catalogue is free from Alpha Electronics Ltd, Unit 5, Linstock Trading Estate, Wigan Road, Atherton M29 0QA. Tel: (0942) 873 434.

- The City & Guilds of London Institute is an examining body which offers qualifications in a wide range of craft and technical subjects, most of which can be taken on day release as well as on full-time courses. A new pamphlet from the Institute lists the qualifications available in subjects such as electronics, electrical installation and computing and explains how these are recognised by industry and professional bodies. A helpful graph shows how students progress through the various levels of qualification and there are some brief case histories of people who are taking or have taken CGLI courses. The City & Guilds of London Institute, 76 Portland Place, London W1N 4AA.

- We often tell you about companies publishing guides to their product lines but here's one publishing a guide to the guides. Axiom distribute Motorola products and they have put together a complete guide to the literature available on Motorola devices. For details contact Axiom Electronics Ltd, Turnpike Road, Cressle Industrial Estate, High Wycombe, Buckinghamshire HP12 3NR. Tel: (0494) 442 181.

- The range of control knobs and accessories manufactured by Sifam Ltd is described in a 16-page A4 colour catalogue recently issued by the company. Collet, push-on and slide potentiometer knobs are among the types covered and the catalogue also lists knob caps, dials, pointers, assembly tools and push-button switch caps. Contact Sifam Ltd, Accessories Division, Woodland Road, Torquay, Devon TQ2 7AY. Tel: (0803) 63822.

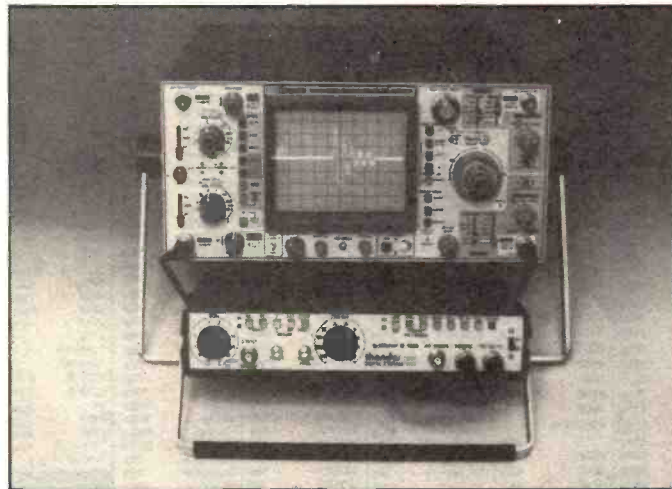

Digital Storage Scope Add-On


Thandar Electronics has introduced a portable, low-power digital storage unit which allows waveforms to be captured and stored on an ordinary real-time oscilloscope.

At its minimum sampling rate the unit can capture slowly-changing waveforms lasting more than an hour whilst the maximum rate of 200kHz allows it to capture fast transients and similar events. The operating modes available are real-time, refresh, roll and single-shot and the trigger facilities allow the unit either to start sampling when a trigger signal is received

or to sample continuously and use the trigger pulse to define the mid-point or end of the sampling period.

The unit has variable input sensitivity down to 5mV and uses a 1K memory to store data. Operation is from batteries or from the mains via an AC adaptor and data stored in the memory can be retained for up to four years when batteries are fitted.

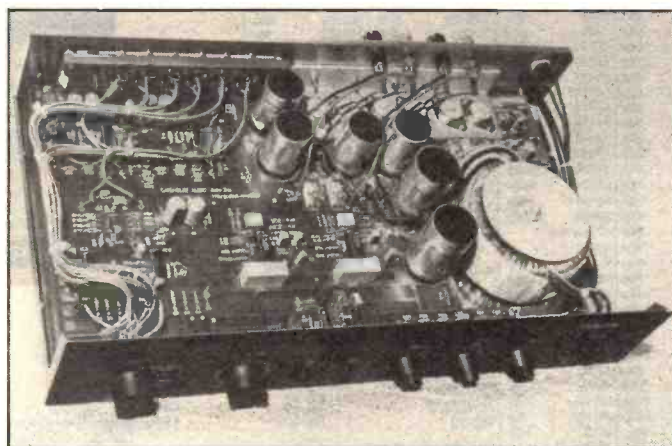The TD201 costs £195 plus VAT and is available from Thandar Electronics Ltd, London Road, St. Ives, Huntingdon, Cambridgeshire PE17 4HJ. Tel: (0480) 64646.



Hi-Fi Kit Claims High Performance

Gatehouse Audio says its new Gate One amplifier is no ordinary kit design.

Selling for £161, the amplifier is said to provide a sound quality equal to that of amplifiers in the £300-£400 class while sacrificing nothing in terms of facilities or appearance.

The Gate One provides 40 watts per channel into 8R (80 watts into 4R) and accepts inputs from moving-coil cartridges and CD players as well as from moving magnet cartridges, tuners and tape recorders. Features include a tone cancel switch which removes the

treble and bass controls from circuit when not required, a subsonic filter to remove noise on discs and a bass boost facility for use with loudspeakers which have a poor bass response.

Full instructions are included and the PCB is screen printed with component numbers and locations to simplify assembly. The amplifier is also available ready-built for £201.25. Prices include carriage and VAT.

Gatehouse Audio, 105 High Street, Evesham, Worcestershire WR11 4EB. Tel: (0386) 48873.

IC Firms Fight Health Scare

Electronics companies in America's Silicon Valley are fighting to retain their non-union working policies following the publication of a report which highlights increasing health problems among female workers.

The report was drawn up by researchers at the University of Massachusetts and catalogues the health problems of female production workers at a DEC semiconductor plant. Labour and womens' rights groups have seized on the findings and used them to challenge the safety of semiconductor manufacturing plants around the world.

Worried by the bad publicity, some companies have refused to employ women on production tasks. Women's rights groups insist this is discrimination and say the companies should concentrate on finding the cause of the problems.

A coalition of concerned groups wrote to the heads of 15 major semiconductor manufacturers and invited them to meet and discuss the report. Many refused, believing that to respond to the letter would confer recognition on the groups as workers' representatives and so open up the way to unionisation. This would remove the manufacturers' ability to cut costs rapidly when necessary simply by sacking thousands of workers.

Instead, the industry has responded with an attempt to discredit the report, describing it as 'too small to make it applicable to the industry as a whole'. An internal report is being planned by the Semiconductor Industry Association (SIA) to determine how best to mount a health study. However, many people are critical of the SIA's decision not to accept an offer of help from the University of California, widely recognised as a centre of excellence in occupational health matters.

TV Sound In The Balance

The BBC and the IBA are planning to conduct a series of tests to investigate the intelligibility of dialogue in television programmes.

The initiative follows complaints from people with hearing difficulties who say they cannot follow dialogue easily when it is accompanied by background music, sound effects or audience noises. A working party set up by the two organisations will assess the intelligibility of dialogue both for people with hearing difficulties and those with normal hearing.

Z80 Features, Sixteen Bits

Following the success of the 8-bit Z80 microprocessor, Zilog has introduced a CMOS 16-bit version which offers full compatibility and improved performance.

The Z280 can operate in 8 or 16-bit mode, allowing it to use all existing Z80 applications software and to be interfaced easily with Z80 peripherals. In 16-bit mode it can be used with Zilog's family of Z-BUS peripherals.

Improved features include clock speeds from 10 to 25MHz, a 16M byte on-chip memory management unit and a 256 byte instruction and data cache which can be used in conjunction with the burst mode access facility on modern DRAMs. A number of functions which would previously have been carried out by peripheral devices have been built-in to the Z280 including three 16-bit counter/timers, a full duplex UART and four channels of DMA.

Zilog claims to have captured over 35% of the 8-bit market with the Z80 and says the library of software available for the device is the most extensive in the world. The Z280 will allow companies to preserve the value of their investment in Z80 hardware and software while gaining the benefits of improved performance, higher levels of integration and low power consumption.

The Z280 is available now and costs about \$27 in quantities of a thousand.

Zilog, 1315 Dell Avenue, Campbell, California 95008, United States of America.


A Job — If You're Quick Enough

Students who don't start job hunting until they have finished their studies are taking an unnecessary risk according to a new report from PA Personnel Services.

Competition for graduates has been building up for several years, and employers now start recruiting as early as October in the final year in order to secure the best students.

Those studying shortage subjects such as electronic engineering or computer sciences may still be able to find jobs once the exams are over, but in general employers are only taking the best and those who show real initiative. Late entry into the employment market is inadvisable in today's climate of high unemployment, the report says.

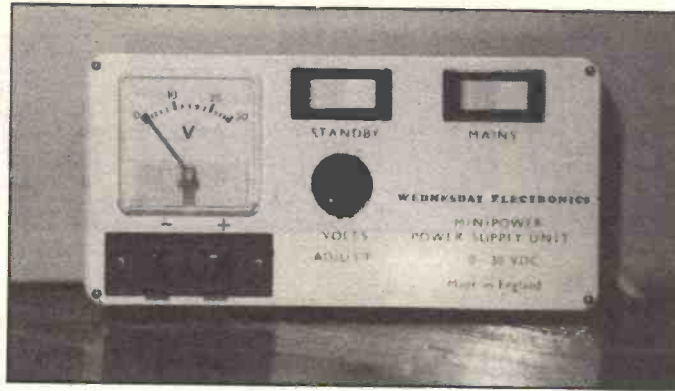The Pay Research Unit, PA Personnel Services, Hyde Park House, 60A Knightsbridge, London SW1X 7LE. Tel: 01-235 6060.



Small PSU For Small Budgets


The Minipower PSU is a single-rail bench power supply which has been designed to offer good performance at a low price.

At just over £30 inclusive, the Minipower is expected to prove popular with schools and colleges, hobbyists, model-makers and any individual or organisation operating on a tight budget.

The Minipower provides a regulated DC voltage which is continuously variable between 0 and 30V (35V absolute maximum)

at currents up to 1.5A. An automatic current limiting circuit protects the supply from overload. The output voltage remains constant to within 0.01% from zero to full load, line regulation is to within 0.3% and the total output noise level is 150uV.

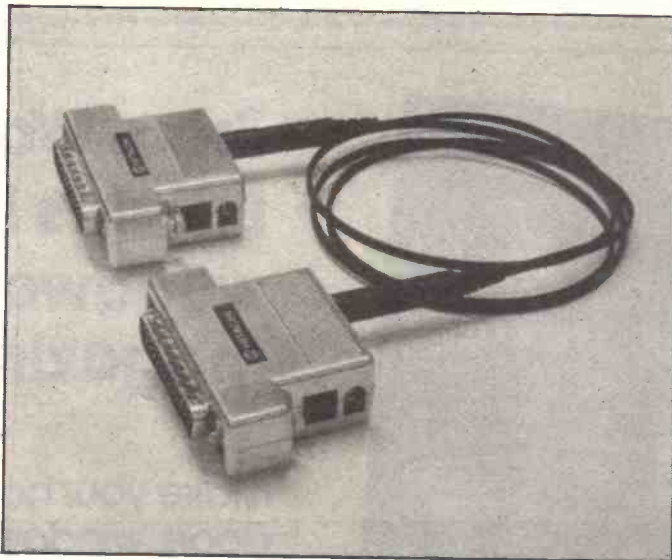The Minipower PSU costs £31.70 including VAT and postage and is available from Wednesday Electronics, 4 Church Street, Offenham, Worcestershire WR11 5RW. Tel: (0386) 40314.



Optical Communications The Easy Way

A new data communication link from Hitachi offers all the advantages of fibre optic cable but is as easy to use as an ordinary digital serial interface.

The HAC105 cable has two fibre optic cores to allow full duplex operation and has all the necessary transmit and receive circuitry built into the moulded plugs at each end. A simple PCB-mounting socket allows the cable to be connected directly to logic circuit boards while an active adaptor is available to enable the cable to be used with RS232 links.

The cable is available in standard lengths of 5, 10 and 20 metres with other lengths available to order in suitable quantities. Power for the

cable circuitry is derived from the board circuitry where a PCB socket is used or from a mains power unit when the RS232 adaptor is being used.

The cable and adaptors are only available in large quantities at present but Hitachi hope to arrange dealerships which will make them available in smaller quantities. A one-off price of around £30 is anticipated for the cable with the ADPRSI RS232 adaptors costing around £65.

A brochure giving full technical details of the system is available from Hitachi Electronic Components (UK) Ltd, 21 Upton Road, Watford, Hertfordshire WD1 7TP. Tel: (0923) 46488.

- The latest edition of Ferranti's MOSFET handbook contains over 340 pages of data on the company's range of enhancement mode N and P channel devices. Surface mounting types are now included along with the more traditional TO-92, TO-39 and TO-220 packages and the handbook also features a comprehensive cross reference list of industry part numbers. Copies are available free-of-charge from Ferranti Electronics Ltd, Fields New Road, Chadderton, Oldham, Lancashire OL9 8NP. Tel: 061-624 0515.

- A new 44-page colour brochure from PKS-Digiplan Ltd contains a wealth of information on motion control techniques as well as describing the company's range of motor drive and control modules. The topics covered include open and closed loop control of DC and stepper motors, motor and drive selection criteria, torque calculation and inertia matching. There are also worked examples for a variety of different applications. PKS-Digiplan Ltd, 21-22 Balena Close, Creekmoor, Poole, Dorset BH17 7DX. Tel: (0202) 690 911.

- Omni Electronics is a recently established, family-run company which supplies electronic components, kits, tools and accessories. Everything listed in their catalogue is normally available by return of post and the company will also try to obtain 'difficult' components to order. The catalogue costs 38p inclusive from Omni Electronics, 174 Dalkeith Road, Edinburgh EH16 5DX. Tel: 031-667 2611.

- A potentially serious bug has been found in the 32-bit multiplier logic of Intel's 80386 microprocessor. About 100,000 of the devices have already been sold but most have been used in 16-bit DOS applications where the bug is not apparent. However, Intel believes that many companies are now planning to use the 80386 in more critical applications and reckons it has about nine months to correct the fault. The cost of field-replacement for faulty devices could run as high as \$30 million, a heavy blow for the company which has just returned to profitability after a period of heavy losses.

- Yes, we know, the supposed safety problem with Amstrad's PC1512 IBM clone was the absence of a mains earth, not the absence of a mains lead as we reported last month. A suitable revenge awaits our news writer should we ever find him again, but just at the moment he seems to have gone to ground.

**NEXT
MONTH**

AN ARGUS SPECIALIST PUBLICATION

electronics today

INTERNATIONAL

CARS CARS CARS

The August issue of ETI contains a whole bundle of stuff for the motorist and the DVLC has graciously decided to bring out a new registration number prefix (E for ETI) in August in our honour.

Keith Brindley has been taking a look at the world of auto electronics. Although high technology has been comparatively slow to filter through to the conservative car industry it looks like things are changing at last.


There's several short and easy projects for the DIY motorist in the August issue too — everything from a car alarm to a very novel rev counter.

PLUS

For readers reliant on public transport, next month's ETI has all the old favourites which go to make up Britain's best loved magazine for the electronics enthusiast. There's projects, features, news, diary, Tech Tips, ads, special offers, letters and so much more.

**THE AUGUST ISSUE OF ETI — OUT 3rd JULY
MISS IT AT YOUR PERIL!**

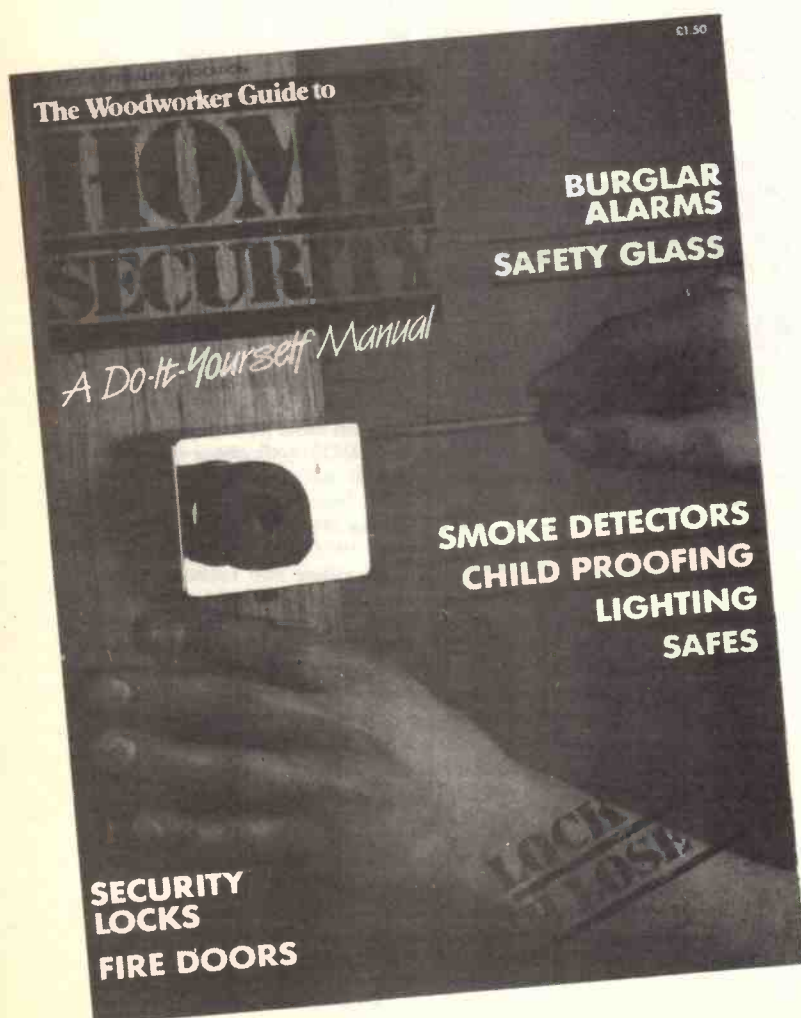All the articles listed are in an advanced state of preparation but circumstances beyond our control may prevent publication.



**From Woodworker,
Britain's leading
woodworking
magazine ...**

make your home more secure:
doors, windows, alarms, fire
precautions and child proofing—
it's all in this invaluable do-it-
yourself manual.

At your newsagent **NOW!**
or order direct for **£1.50 + 50p**
p&p from *Infonet*, 10-13 Times
House, 179 The Marlowes, Hemel
Hempstead, Herts. HP1 1BB.

The Italian Collection

West Hyde has extended its range of instrument cases with the introduction of several new low-cost designs from Teko of Italy.

They come in free-standing and wall-mounting varieties, in a range of colours and can be specified with lacquered aluminium front panels, internal PCB mounting slots and many other features. Contact West Hyde Developments Ltd, 9-10 Park Street, Aylesbury, Buckinghamshire HP20 1ET. Tel: (0296) 20441.



● 'Nuclear Power In The UK' is the latest in a series of energy factsheets produced by the Public Affairs Board of the IEE. It aims to provide basic technical information at a level suitable for the intelligent layman and covers such topics as the history of nuclear power in this country, the physical principles underlying reactor operation, the question of safety and the economics of nuclear energy. Copies may be obtained free-of-charge from the PAB Secretariat, IEE, Savoy Place, London WC2R 0BL. Tel: 01-240 1871.

● If you hadn't heard of Clare Instruments until you saw the ST300 Clamp Tester in last month's News Digest (you did see it, didn't you?) now is your chance to find out more. The company has issued a catalogue covering its complete range of ELCB testers, high voltage flash testers, 500V megohmmeters and other specialised safety equipment plus more general items such as watt-meters, resistance bridges and milliohmmeters and of course, clamp ammeters. Contact Clare Instruments Ltd, Woodsway, Goring-by-Sea, Worthing, West Sussex BN12 4QY. Tel: (0903) 502 551.

Changing Attitudes To Information Technology

Britain is in a good position to take advantage of information technology and meet the challenges of the 21st century, according to a new report from the National Economical Development Office.

However, if we are to take up the challenge we need to pay far more attention to education and training and we need to change many of our attitudes.

The report considers the

changes likely to result from the application of information technology in Britain in the period up to the year 2010. As well as taking such a long-term view it takes account of values.

To bring about positive changes we need to overhaul our educational system. The report describes education as 'massively under-resourced' and calls for expansion coupled with a shift of emphasis from theory to practical

application. The present policy of providing science and engineering places at the expense of arts places is rejected by the authors who feel our society will need more of both types of student in the future.

The report is entitled IT Futures ... IT Can Work and costs £20 inclusive from NEDO Books, Millbank Tower, Millbank, London SW1P 4QX. Tel: 01-211 5989.

DIARY: DIARY: DIARY: DIARY: DIARY: DIARY: DIARY: DIARY:

UK Telecommunications Networks: Present & Future — June 2-3rd
IEE, London. Conference. Contact the IEE at the address below.

CableSat '87 — June 2-4th
Metropole Hotel, Brighton. Exhibition and conference. Contact Online at the address below.

International ISDN Conference — June 15-18th
London. Conference on the Integrated Services Digital Network. Contact Online at the address below.

Networks '87 — June 16-18th
London. For details contact Online at the address below.

Scottish Technology Week — June 16-18th
Scottish Exhibition Centre, Glasgow. Single event combining the Scottish Electronic Technology Show & Conference, the Scottish Factory Efficiency Show & Conference and OEM Scotland. Contact Cahners at the address below.

Radio Frequency Techniques — July 19-24th
University of Bradford. Vacation school organised by the IEE. Contact them at the address below.

Condition Monitoring For Safety — June 25th
Regent Crest Hotel, London. Seminar and Exhibition. Contact ERA Technology on (0372) 374 151.

Satellite Communication Systems — July 26-31st
University of Surrey. Vacation school organised by the IEE. Contact them at the address below.

Designing For Electromagnetic Compatibility — September 13-18th
University of Sussex. Vacation school organised by the IEE. See address below.

7th International Display Research Conference — September 15-17th
The IEE, London. Conference covering all aspects of electronic display research. Jointly organised by a number of professional bodies. Contact the Institute of Physics on 01-235 6111.

Design Engineering Show — September 15-18th
NEC, Birmingham. Exhibition and conference covering all areas of engineering including electronics and CAD/CAM. Contact Cahners on 01-891 5051.

IDEX '87 — September 21-23rd
Metropole Exhibition Halls, Brighton. See April '87 ETI or contact Nutwood Exhibitions on (04848) 25891.

Semiconductor International — September
NEC, Birmingham. Covers materials, design assembly and testing of semiconductors. Contact Cahners at the address below.

Internecon — October 6-8th
Metropole Convention Centre, Brighton. Exhibition and conference covering wire, cables, power supplies, components and racks/cases. Contact Cahners at the address below.

Automotive Electronics — October 12-15th
The IEE, London. International conference organised by the IEE in conjunction with many other professional bodies. Contact them at the address below.

Conference For Young Engineers — October 16-18th
Strand Palace Hotel, London. Weekend conference on commercial awareness and business skills for young engineers (under 30) of all disciplines. Events include an engineering company simulation game which tests the ideas under discussion. Contact the IEE at the address below.

Radar '87 — October 19-21st
Kensington & Chelsea Town Hall, London. International conference on civil and military systems organised by the IEE and the American IEEE. Contact the IEE at the address below.

International Video & Communications Exhibitions — October 18-21st
Metropole Exhibition Centre, Brighton. Exhibition with seminar programme covering video equipment, services, programme production, etc. Contact Peter Peregrinus Ltd at the IEE address below.

Testmex '87 — October 20-22nd
Business Design Centre, London. Exhibition covering all areas of electronic test and measurement. Contact Network Events on (0280) 815 226.

Addresses:
Cahners Exhibitions Ltd, Chatsworth House, 59 London Road, Twickenham TW1 3SZ. Tel: 01-891 5051.

Institute of Electrical Engineers, Savoy Place, London WC2 0BL. Tel: 01-240 1871.

Online Conferences Ltd, Pinner Green House, Ash Hill Drive, Pinner, Middlesex HA5 2AE. Tel: 01-868 4466.



BIO-FEEDBACK ACCESSORIES

A METER MOVEMENT which can be built into your bio-feedback monitor to make it a completely self-contained instrument. Don't worry if you've already drilled the terminal holes - the meter will cover them up!

SENSITIVE METER MOVEMENT ONLY £1.90!

SPARE ELECTRODES AND GEL

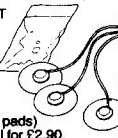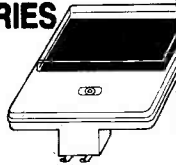5 sets of electrodes (10 electrode pads) and a sachet of conductive gel, all for £2.90.




LEDs

RECTANGULAR LEDs

Green rectangular LEDs for bar-graph displays.
50 for £3.50 100 for £6 500 for £25
1000 for £45

DIGITAL AND AUDIO EQUIPMENT LEDs

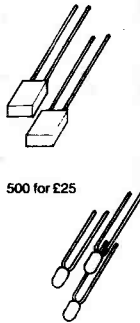Assorted 3mm LEDs: red, green, yellow and orange. 25 of each (100 LEDs) for £6.80



PROJECT BOX WITH BATTERY COMPARTMENT

As used in our tachometer and bio-feedback kits. This attractive/and versatile case can be used to house the experimenter kit projects, or your own battery operated projects.

PROJECT CASE WITH PP3 BATTERY COMPARTMENT ONLY £2.60!



LEDSCOPE

FEATURED IN ETI JANUARY 1987

Tony Ellis's famous LED oscilloscope. The most important bench instrument for any electronics enthusiast must be a 'scope, and at this price anybody can afford one! The Ledscope also acts as a voltmeter and ohm-meter. It's got everything!

The complete parts set includes a smart brushed aluminium case, PCB, all components, pots, knobs, switches, and full instructions.

LEDSCOPE PARTS SET, WITH CASE ONLY £59.95!

SUITABLE PROBE SET £7.95

BIO-FEEDBACK

FEATURED IN ETI DECEMBER 1986

A complete parts set for the ETI bio-feedback monitor. Previously offered at £14.55, the last few sets to clear at £9.99! We will also supply a free meter movement for the monitor. The complete parts set includes case, PCB, all components, meter and full instructions.

YOUR LAST CHANCE

BIO-FEEDBACK PARTS SET ONLY £9.99!

£14.55 **£9.99**
ONLY UNTIL APRIL 30th
WITH FREE METER!





HI-FI POWER METER

FEATURED IN ETI MAY 1987

Measure the output power of your hi-fi with the ETI power meter. The meters can be back-lit for effect - the scale and 'power' legend will glow green to contrast with the red pointer. Two switched ranges give readings of 0-10W and 0-100W.

The parts set consists of meter movement, PCB, all components, range switch and full instructions.

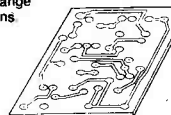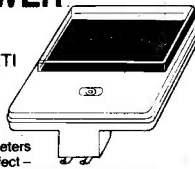MONO POWER METER PARTS SET £3.90
STEREO POWER METER PARTS SET £7.20
SUITABLE CASE £7.50



TACHOMETER AND DWELL METER

FEATURED IN ETI JANUARY 1987

MOTORISTS QUIZ
You are driving along the road one day when the sound of a horn makes you look behind. The driver of a milk float is cursing you for driving so slowly. A while later, an invalid carriage overtakes you, and just as you turn into your drive you hear a tractor driver mutter: 'At last I can get out of first gear!'

- Do you:
- Fit a £500 Pie-in-ear in-car stereo with digital flexi-woofers and 24-band ramification?
 - Buy a set of fluffy dice and sticker saying 'My other car is a Macaroni'?
 - Give your car in part exchange for a milk float/ invalid carriage/ tractor?
 - Tune your engine.

The combined tachometer and dwell meter parts set contains: case with battery compartments; printed circuit board; all components; switches; plug, socket and test leads; battery connector; full instructions. The answer to the quiz, by the way, is: e) Buy a bright red Lotus Esprit.

TACHOMETER AND DWELL METER PARTS SET
£12.90 (with terminals for external meter)
£16.40 (with self contained meter)



MATCHBOX AMPLIFIER


FEATURED IN ETI, APRIL 1986

No ordinary amplifiers, these. When our first customers took an interest, it was for the diminutive size (both modules will fit in a matchbox!), the total disregard for power supplies and speaker impedances, and the impressive power output from these little amplifiers. When they re-ordered, it was for the sound quality.

Two amplifier modules were described, both based on the powerful L165V IC. The single IC version will deliver over 20 Watts with a suitable speaker and power supply. The bridge version can provide up to 50W! Although the specified supply voltage and speaker impedance must be used to achieve maximum power, both modules are quite happy to work from any voltage between 12V and 32V, and will accommodate any type of speaker. The bridge version is ideal for giving a boost to car Hi-Fi systems, driving two 4 Ohm speakers in parallel on each channel for best effect.

Both designer-approved parts sets consist of a roller tinned printed circuit board and all components. The L165V ICs are also available individually, with a free mini data sheet giving specifications and suggested circuits.

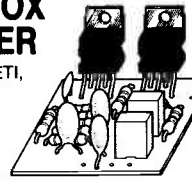SINGLE IC MATCHBOX BRIDGE AMPLIFIER SET (20W into 4 Ohms) £6.50
L165V IC, with data, £3.90



Complete Parts Sets for ETI Projects

MAINS CONDITIONER

FEATURED IN ETI, SEPTEMBER 1986


It is astonishing how many people buy or build top-flight hi-fi equipment, and then connect it to a noisy, spiky mains supply. Rather like buying a Ferrari and trying to run it on paraffin, you might think. Expecting crystal clear sound, the poor music enthusiast ends up with a muddy, confused mush, and feels that he has somehow been cheated. 'Is this hi-fi? My music centre sounded just as good!'

The domestic mains supply is riddled with RF interference, noise, transient spikes, and goodness knows what else. Computers crash, radios pop and crackle, tape recordings are spoiled and hi-fi sounds 'not quite right'. Why put up with it when the solution is so simple? The ETI mains conditioner is the lowest cost upgrade you will ever buy, and probably the most effective!

Our approved parts set consists of PCB, all components, toroid*, enamelled wire, fixing ties, fast response VDR*, and full instructions.

ETI MAINS CONDITIONER PARTS SET ONLY £4.60!

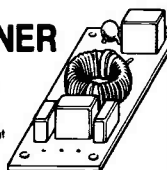*Note: the toroid and VDR supplied are superior to the types specified in the article.



CREDIT CARD CASINO

FEATURED IN ETI, MARCH 1987

This wicked little pocket gambling machine measures only 3"x2"x1/2". It will play all kinds of casino games, including:

- Roulette
- Craps
- Pontoon

Our approved parts set comes complete with case; self-adhesive fascia; tinned and drilled printed circuit board; all components; hardware; full instructions and three different games to play!

CASINO PARTS SET ONLY £5.90!



SPECIAL OFFER
Five extra games FREE with all orders March - April 30th

MAINS CONTROLLER

FEATURED IN ETI, JANUARY 1987

Have you ever wondered what people do with all those computer interfaces? Put your computer in control, say the ads. 'The Spectrabee has eight TTL outputs. What on earth can you control with a TTL output? A torch bulb?'

The ETI Mains Controller is a logic to mains interface which allows you to control loads of up to 500W from your computer or logic circuits. An opto-coupler gives isolation of at least 2,500V, so the controller can be connected to experimental circuits, computers and control projects in complete safety. Follow your computer interface with a mains controller and you're ready in business with automatic control!

The mains controller connects directly to most TTL families without external components, and can be driven by CMOS with the addition of a transistor and two resistors (supplied).

Your mains controller parts set contains: high quality roller tinned PCB; MOC3021 opto-coupler; power trace with heatsink, mounting hardware and heatsink compound; all components, including snubber components for switching inductive loads; transistor and resistors for CMOS interface, full instructions.

MAINS CONTROLLER PARTS SET £6.20



POWERFUL AIR IONISER

FEATURED IN ETI, JULY 1986

Ions have been described as 'vitamins of the air' by the health magazines, and have been credited with everything from curing hay fever and asthma to improving concentration and putting an end to insomnia. Although some of the claims may be exaggerated, there is no doubt that ionised air is much cleaner and purer, and seems much more invigorating than 'dead' air.

The DIRECT ION ioniser caused a great deal of excitement when it appeared as a constructional project in ETI. At last, an ioniser that was comparable with (better than?) commercial products, was reliable, good to build... and fun! Apart from the serious applications, some of the suggested experiments were outrageous!

We can supply a matched set of parts, fully approved by the designer, to build this unique project. The set includes a roller tinned printed circuit board, 66 components, case, mains lead, and even the parts for the tester. According to one customer, the set costs about a third of the price of the individual components. What more can we say?

DIRECT ION PARTS SET £9.50

Instructions are included



MATCH BOX AMPLIFIERS

20W Single IC parts set £6.50

50W Bridge Amplifier parts set £8.90

L165V Power Amplifier IC, with data, £3.90

LM2917 EXPERIMENTER SET

Consists of LM2917 IC, special printed circuit board and detailed instructions with data and circuits for eight different projects to build. Can be used to experiment with the circuits in the 'Next Great Little IC' feature (ETI, December 1986).

LM2917 Experimenter Set £5.80

RUGGED PLASTIC CASE,

suitable for mains conditioner and mains controller.

ONLY £1.65



SPECIAL OFFER

Our best selling ioniser kit is now available with an elegant white case.

WHITE IONISER PARTS SET ONLY £9.80!

Orders should be sent to Specialist Semiconductors at the address below including 50p towards postage and packing. Please allow up to 14 days for delivery. There is no telephone service at the moment, but all letters or requests for lists will be answered (at top speed if you send SAE!)

Specialist

FOUNDERS HOUSE REDBROOK MONMOUTH GWENT

READ/WRITE

Missing MIDI

I am considering building the MIDI Master Keyboard from the May issue and I have had difficulty in contacting Clef Products for the keyboard mechanism.

It seems that this company is no longer trading. Is there another suitable source for the key switches?

Jonathan Templar
Richmond, Surrey.

Clef Products do seem to have ceased trading but suitable keyboard mechanisms are available elsewhere. Maplin can supply the keyboard mechanics and the individual contact springs and bus bars. Unfortunately the mechanics are only available in 49 and 61 note versions but a 72 note keyboard could easily be constructed from two of these cut down (wasteful but a good source of spares!).

WEM (Tel: 01-761 6568) can provide two octave keyboard mechanics (which can be joined end to end), complete with bus bars. These may require a little modification but cost only £8 a time.

Radio Activity

My hobby has always been constructing and experimenting with VHF broadcast transmitters (88-108MHz). I have built and quite often use a stereo FM transmitter with 120W output from solid state devices. The response from listeners over 40 miles away is fascinating.

Perhaps this subject is a bit taboo but I would be pleased to hear from others who tinker with broadcasting equipment.

Paul Smith
(Address supplied).

The Department of Trade and Industry would be most pleased to hear from likeminded people too! This activity is not at all taboo, it's just downright illegal.

Although low power transmitters are legal in some other European countries and plans for similar legislation here have been made (and shelved) it is still against the law to transmit in this way without a licence (which will not be granted for this kind of use).

If you get caught (which should not be difficult for the DTI as you must stick out like the radio equivalent of a sore thumb) the DTI will come down on you like the proverbial ton (or even tonne) of bricks with a hefty fine or a spell at Her Majesty's pleasure and confiscate all your gear.

If any other readers still want to get in touch with Mr. Smith they can write to him care of ETI (enclose a stamped envelope) but don't say we didn't warn you!

Decline And Fall

With less children today interested in an electronics career and talent scouts with cheque books from the States awaiting our graduates, I had hoped the recent budget would have done more for our homebased science and technology.

Are we going to see a repeat of the hospitals where a nurse finds a more lucrative career serving in a shop nine to five?

The new Silicon Glen in Scotland is very impressive but when you tour this country and see the wilderness of the forgotten heroes, listen to their despair in Durham, Sheffield and Lincoln, you realise every city needs a Silicon Valley of new industries.

Incidentally, I very much enjoyed Anna Paczuska's contribution on 'Bad Health in Electronics' back in the August 1986 ETI. More please! With man pushing the frontiers of Electronics Technology to unknown limits for space travel and defence it is extremely interesting to read the problems behind the science of

man's capabilities.

However, the limits of the science were clearly realised recently when a friend accidentally wired a 10µ 63V capacitor the wrong way across a 50V power supply. He nearly lost an eye and the metal top of the radial lodged in the ceiling tiles nine feet up. He now leaves the room before switching on!

Keith Lawrence
Ilkley, West Yorkshire.

We couldn't agree more. Interest in electronics as a hobby has certainly declined over the last few years and government funding for research and development and for investment in industry seems set to do its best to kill off what is left of the British electronics manufacturing base.

Any millionaire ETI readers should find a local electronics firm to invest in immediately.

Shock, Horror, Probes


What a surprise you would get if you held the ends of the probes from a resistance meter and got the reading I did. Please explain this one.

C. Ford

Easy one this, for any regular reader of ETI. If you're not a regular reader go and stand in the corner immediately. If you are a regular reader but didn't read the pieces on biofeedback and galvanic skin response back in the November and December 1986 issues, go and stand in two corners (at once).

Skin has a fairly low resistance — anything from about 5kΩ to 1MΩ. The variations in resistance tell you all sorts of interesting things about your body and state of mind. In the ETI office we go around the whole time with probes sticking into bits of our anatomy just to see if we're still awake!

CORK

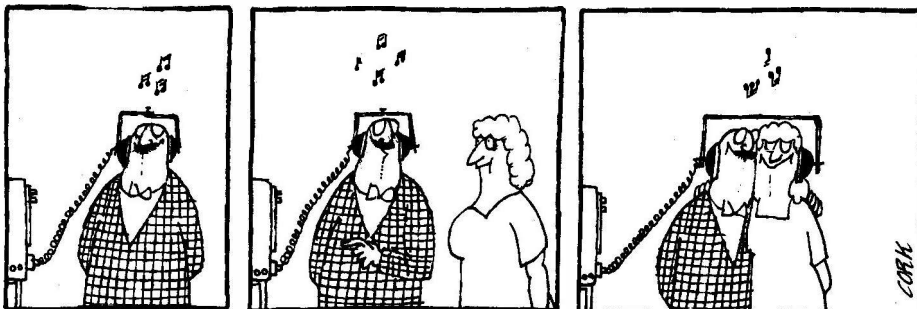

The ETI post room staff are planning to walk around China at the end of the year in aid of the campaign to save the South Yorkshire Mongoose and so they need plenty of training lugging heavy mail sacks. All ETI readers are formally requested to send in one interesting letter each for this page. Write to:

Electronics Today International
1 Golden Square
London W1R 3AB.

ETI

For KITS & COMPONENTS
Choose the easy way - with

TK

Send **50p & SAE** for **CATALOGUE** (refundable with first order)
ORDERS: RING (01) 567 8910 - 24 HRS

POWER STROBE KIT

Designed to produce a high intensity light pulse at a variable frequency of 1 to 15Hz this kit also includes circuitry to trigger the light from an external voltage source (eg. a loudspeaker) via an opto isolator. Instructions are also supplied on modifying the unit for manual triggering, as a slave flash in photographic applications or as a warning beacon in security applications. The kit includes a high quality pcb, components, connectors, 5W strobe tube and full assembly instructions. Supply: 240V ac. Size: 75x50x45
KK124 STROBOSCOPE KIT £12.50

HIGH SECURITY LOCK KIT

Designed for use with our lock mechanism (701 150) this kit will operate from a 9V to 15V supply drawing a standby current of only 50uA. There are over 5000 possible 4-digit combinations and the sequence can be easily changed. To make things even more difficult for an unauthorised user an alarm can be sounded after 3 to 9 incorrect entries - selectable by means of a link. The alarm can sound for a few seconds to over 3 minutes during which time the keyboard is disabled preventing further entries. A latched or momentary output is available making the unit ideal for door locks, burglar alarms, car immobilisers, etc. A membrane keyboard or pushbutton switches may be used and a beep sounds when a key is depressed. Kit includes high quality PCB, all components, connectors, high power piezo buzzer and full assembly and user instructions.
KK121 LOCK KIT £15.95
350 118 Set of Keyboard Switches £4.00
KB12S 12-Way Membrane Keyboard £9.98
701 150 Electric Lock Mechanism £16.50

VERSATILE REMOTE CONTROL KIT

This kit includes all components (+ transformer) to make a sensitive IR receiver with 16 logic outputs (0-15V) which with suitable interface circuitry (relays, triacs, etc - details supplied) can be used to switch up to 16 items of equipment on or off remotely. The outputs may be latched (to the last received code) or momentary (on during transmission) by specifying the decoder IC and a 15V stabilised supply is available to power external circuits.
 Supply: 240V AC or 15-24V DC at 10mA.
 Size (excluding transformer) 9 x 4 x 2 cms.
 The companion transmitter is the MK18 which operates from a 9V PP3 battery and gives a range of up to 60ft. Two keyboards are available MK9 (4-way) and MK10 (16-way), depending on the number of outputs to be used.
MK12 IR Receiver (incl. transformer) £14.85
MK18 Transmitter £7.50
MK9 4-Way Keyboard £2.00
MK10 16-Way Keyboard £5.95
601 133 Box for Transmitter £2.60

PROPORTIONAL TEMPERATURE CONTROLLER KIT

Uses "burst fire" technique to maintain temperature to within 0.5°C. Ideal for photography, incubators, wine-making, etc. Max load 3kw (240V ac) Temp. range up to 90°C.
 Size: 7x4x2.5cms.
MK4 £7.10

DISCO LIGHTING KITS

DL1000K This value-for-money 4-way chaser features by-directional sequence and dimming. 1kW per channel. **£17.50**
DLZ1000K - A lower cost uni-directional version of the above. Zero switching to reduce interference. **£9.85**
 Optional opto input allowing audio 'beat/light' response (DLA/1) **70p**
DL3000K - 3-channel sound to light kit features zero voltage switching, automatic level control and built-in microphone. 1kW per channel. **£14.25**
DL8000

The **DL8000K** is an 8-way sequencer kit with built in opto-isolated sound to light input which comes complete with a pre-programmed EPROM containing EIGHTY - YES 80 different sequences including standard flashing and chase routines. The KIT includes full instructions and all components (even the PCB connectors), and requires only a box and a control knob to complete. Other features include manual sequence speed adjustment, zero voltage switching, LED mimic lamps and sound to light, LED and a 300W output per channel. And the best thing about it is the price: **ONLY £28.50.**

ELECTRONIC GUARD DOG KIT

One of the best deterrents to a burglar is a guard dog and this new kit provides the barking without the bite! The kit when assembled can be connected to a doorbell, pressure mat or any other intruder detector and will produce a random series of threatening barks making the would be intruder think again and try his luck elsewhere. The kit is supplied complete with high quality PCB, transformer, all components and instructions. All you need is a mains supply, intruder detector and a little time. The kit even includes a horn speaker which is essential to produce the loud sound required. The "dog" can be adjusted to produce barks ranging from a Terrier to an Alsatian and contains circuitry to produce a random series of barks giving a more realistic effect.
KK105 Complete kit of parts £21.95

HOME LIGHTING KITS

These kits contain all necessary components and full instructions and are designed to replace a standard wall switch and control up to 300w of lighting.
TD300K Remote Control Dimmer **£16.45**
MK6 Transmitter for above **£4.95**
TD300K Touchdimmer **£9.50**
TS300K Touchswitch **£8.50**
TDE/K Extension kit for 2-way switching for TD300K **£2.70**
LD 300K Light Dimmer **£4.35**

TK

ELECTRONICS
13 BOSTON RD
LONDON W7 2SJ
Tel: 01:567 8910

SEND 9x6" S.A.E. AND 50p FOR CATALOGUE OR CALL AT SHOP MON-FRI 9-5 pm SATURDAY 10-4 pm

ORDERING INFORMATION:
ALL PRICES EXCLUDE VAT

FREE P&P on orders over £20 (UK only), otherwise add 75p + VAT. Overseas P&P. Europe £2.75. Elsewhere £6.50. Send cheque/PO/Barclaycard/Access No. with order. Giro No. 5293 14002.

LOCAL AUTHORITY AND EXPORT ORDERS WELCOME
 GOODS BY RETURN SUBJECT TO AVAILABILITY

TRANSFORMERS EX-STOCK

MAINS ISOLATORS				30/15V or 15.0-15V				24/12V or 12-0-12V			
Pri/Sec 120V-2 OR 240 to 415/440V (60-1000VA Tap Secs)				2-15V TAP SECS				2-12V TAP SECS			
VA	£	P&P		30V	15V	£	P&P	12V	24V	£	P&P
20	7.60	2.16		0.5	1	3.88	1.41	0.3	0.15	2.92	1.10
60	11.51	2.31		1	2	5.24	1.70	0.5	0.25	3.08	1.60
100	13.43	2.59		2	4	8.47	1.92	1 A	0.5	3.70	1.60
200	18.03	3.10		3	6	9.82	2.10	2 M	1	5.15	1.70
250	23.01	3.24		4 A	8	11.72	2.20	4 P	2	5.94	1.90
500	35.45	3.66		5 IM	10	14.49	2.31	6 S	3	9.31	2.05
1000	64.28	4.62		6 P	12	16.40	2.55	8	4	10.89	2.10
1500	82.92	5.95		8 IS	16	21.95	2.60	12	6	13.20	2.25
2000	98.76	6.36		12	24	28.07	2.95	16	8	15.73	2.60
3000	139.89	6.36		15	20	31.66	3.51	30	15	26.31	3.10
6000	298.89	6.36		20	40	43.22	5.95	40	20	37.56	3.75
								60	30	53.92	4.90
								83	41	62.09	5.65

50/25V or 25-0-25V 2-25V TAP SECS
 50V 25V £ P&P
 0.5 A 1 5.01 1.76
 1 M 2 6.09 1.90
 2 P 4 10.84 2.20
 3 S 6 12.54 2.25
 4 8 17.16 2.58
 6 12 21.84 2.79
 8 16 30.89 3.15
 10 20 38.66 3.60
 12 24 43.87 3.80

60/30V or 30-0-30V 2-30V TAP SECS
 60V 30V £ P&P
 0.5 1 5.69 1.85
 1 A 2 8.67 1.91
 2 M 4 11.15 2.20
 3 P 6 16.12 2.34
 4 8 18.38 2.55
 5 10 23.23 2.78
 6 12 26.50 3.02
 8 16 37.25 3.62
 10 20 43.17 3.99
 12 24 49.98 4.65

PLEASE ADD 15% VAT TO ALL ITEMS AFTER P&P

WINDING SERVICES 3VA TO 15KVA INVERTERS 12/24V DC to 240V AC 100W to 4kW CONSTANT VOLTAGE TRANSFORMERS FOR Spike-free stable mains ALSO VALVE MAINS OUTPUT & MATCHING TRANSFORMERS

Stock items by return

AUTOS
 105, 115, 220, 230, 240V
 For step-up or down
 VA £ P&P
 80 5.86 1.70
 150 8.49 1.85
 250 10.34 1.98
 500 16.12 2.68
 1000 28.79 3.25
 1500 34.17 3.68
 2000 51.09 4.62
 3000 86.88 5.72
 4000 112.78 6.04
 5000 131.33 6.04
 7500 202.71 6.04
 10KVA 239.53 6.04

CASED AUTOS
 240V Cable Input
 115V USA Socket Outlets
 VA £ P&P
 20 6.34 1.76
 80 11.33 1.87
 150 14.67 2.20
 250 17.87 3.02
 500 29.32 3.19
 1000 40.29 4.34
 2000 73.33 5.28

TOROIDALS
 Wound to order

Unit 211, Stratford Workshops, Burford Road, London E15 2SP
BARRIE ELECTRONICS LTD
 Tel: 01-555 0228 (3 lines)

PROFESSIONAL QUALITY MODULES AT REALISTIC PRICES!!

THESE AMAZING QUALITY AUDIO MODULES represent real value, each one comes with full wiring & application details together with a **3 YEAR GUARANTEE! YOU CAN'T GO WRONG!!**

HA20 HEADPHONE AMP

- Gain + 20dB nominal
- Frequency response of 20Hz - 20KHz
- Distortion - 0.0014%
- Noise - 105dBu

ONLY £29.95 + P&P
 Only £29.95 + P&P

EBU 28 BALANCED OUTPUT

- Gain + 6 dB
- Frequency response 20Hz - 20KHz
- Distortion 0.0025%
- Noise - 105 dBu
- Headroom + 21dBu I/P + 26 dBu Balanced O/P

Only £9.95 + P&P

PMA 30 RIAA PRE-AMP

- Designed to exacting RIAA specification.
- Contact us for full details

Only £144.95 + P&P

Microphone Amp **£19.95+P&P**, Hi-Power Headphone Amp **£34.95+P&P**, "PEAK" LED Indicator **£4.99+P&P**, Reverb Control **£34.95+P&P**..... Call now for more details and specifications.

NEMPRO•CORNWALLIS HOUSE•HOWARD CHASE• BASILDON•ESSEX•SS16 3BB•0268 286668•TLX:995092• Allow £1.50 P&P

MAKE YOUR INTERESTS PAY!

More than 8 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 90 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for your **FREE INFORMATION PACK** on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	Radio, Audio and TV Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Radio Amateur Licence Exam (City & Guilds)	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCE over 40 'O' and 'A' level subjects <input type="checkbox"/>			

ICS Name _____ P. Code _____
 Address _____
 International Correspondence Schools, 312/314 High St., Sutton, Surrey SM1 1PR. Tel: 01-643 9568 or 041-221 2926 (24hrs) Dept EBS77

ALL ABOVE BOARD

Mike Bedford takes a look at surface mounting components and techniques — the miniature future of electronics.

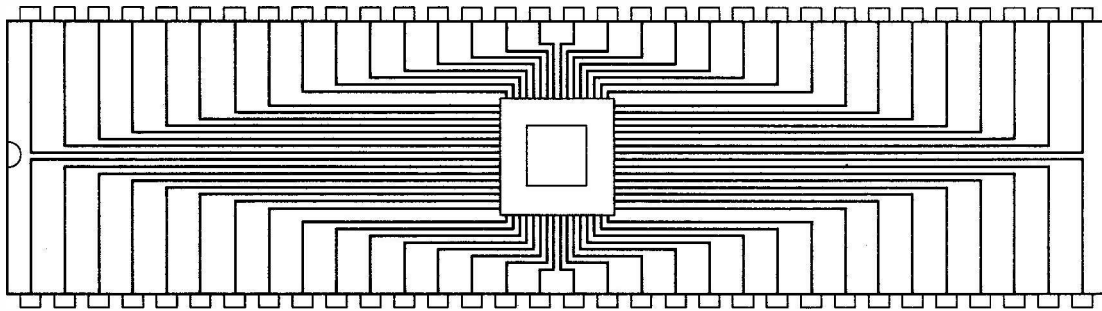


Fig. 1 Poor space utilisation on a typical 64 pin DIL device.

Throughout the realm of electronics and especially in digital applications, one type of component has become increasingly predominant over the past 15 years or so — the 'chip' or integrated circuit housed in one of the various DIL packages.

Of course it is a misnomer to refer to a DIL package as a chip. The actual chip is a small square of silicon embedded inside. The plastic or ceramic housing is provided for purely mechanical reasons. An unpackaged chip could be difficult to handle, prone to damage by environmental factors and impossible to make connections to by conventional manufacturing methods.

Although in the early days the space overhead of DIL packaging was not very significant (most devices requiring only 14 or 16 external connections) this can no longer be said for today's VLSI devices requiring 40 or 64 pins. Figure 1 shows how in a typical 64 pin DIL package, there is a very high area ratio of packaging to silicon.

Clearly this is inefficient in PCB space and recent moves in IC packaging are providing much greater economy of space. The new ICs also require a departure from conventional PCB assembly methods.

Traditionally, components are mounted through holes in the board making solder connections to the copper tracks on the opposite side to the components. Newer packaging methods are intended for surface mounting which, as the name suggests, means the components are mounted on the surface of the PCB and the solder contact is made on the same side of the board as the components. Figure 2 illustrates the two mounting methods.


Advantages

The most notable advantage of surface mounting is the space saving achieved. This is a result of two factors. Surface mounting packages take up less room than their DIL counterparts. This is not an inherent advantage of surface mounting but results from the fact that a need for efficient board utilisation was a major consideration when the new packages were designed.

Surface mounting devices can also be fitted to both sides of a board.

SIL and DIL Modules

When is a surface mounting package not a surface mounting package? When it is a SIL or DIL module. These forms of packaging provide a means of taking some advantage of the space saving achieved by using surface mounting without the initial capital outlay required to convert to true surface mounting assembly. A SIL module is a small PCB with PLCC packages already mounted on it by the semiconductor manufacturer and pins spaced at 0.1in along its edge. This board can be through mounted on a conventional PCB as a single component. Dynamic RAMs are currently available in this format, a typical SIL pack containing, say, eight 64K × 1 devices giving a capacity of 64K × 8. A DIL module on the other hand is a ceramic substrate with pins along two edges allowing it to match the standard DIL footprint. LCCC packages are mounted on the ceramic substrate and this format is often used for static RAMs.

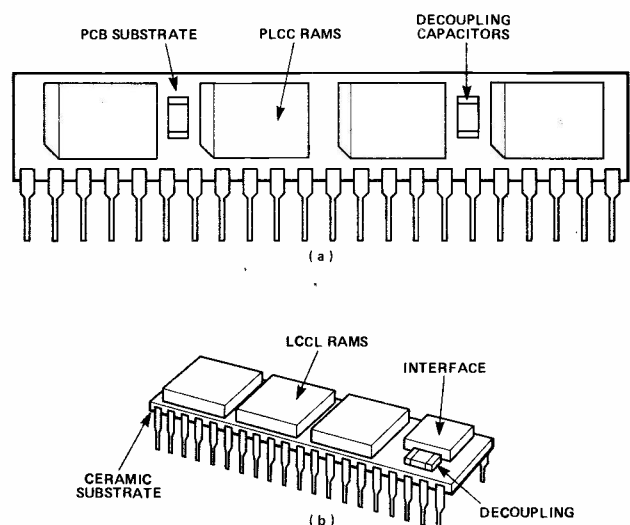

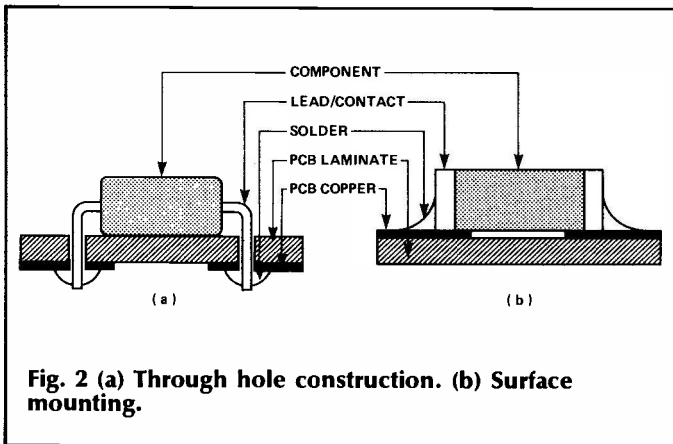


Fig. 2 (a) Through hole construction. (b) Surface mounting.

To the home constructor, a slightly larger PCB is not usually a problem but in a commercial environment PCB 'real estate' is a very valuable commodity. Quite apart from the extra cost of a larger board, there is the possibility the required circuitry will not fit onto a single board. If two boards have to be used in place of the one, costs really escalate as expensive and potentially troublesome interconnections have to be made. If the increased size results in the need for a larger case, space saving becomes even more significant.

As well as allowing smaller printed circuit boards, surface mounting also results in PCBs which are less expensive than expected from the size comparison alone. This is because the manufacturing cost of PCBs depends on a number of factors, a major one being the number of holes to be drilled. PCBs for surface mounting are not devoid of holes since there is still a requirement for through plated holes to connect between the two sides of a double sided board but there will clearly be a marked reduction in their number.

The assembly of boards may be slightly more difficult when surface mounting components by hand (a much smaller soldering iron bit and a steady hand are required) but when automated PCB assembly is considered there are significant gains of speed and costs to be achieved. Although the actual copper pads on the PCB are smaller

for surface mounted components, the need for accurately placing leads through small holes is obviated. A moderate degree of inaccuracy in terms of position and rotation of components can be tolerated. A further consideration is that pre-forming passive component leads prior to fitting into holes is no longer required.

Conventional assembly equipment is no longer applicable and so there is a capital outlay requirement on first adopting the technology. However, a long term saving is still achieved.


Surface mounting also claims the advantages of increased reliability (especially where the circuit board is subject to vibration), improved frequency response and decreased immunity to electromagnetic radiation. Of course these later two points are directly attributable to the smaller package size which allows shorter track lengths both within the IC package and on the PCB.

Surface mounting has necessitated improved methods of PCB printing and etching to be developed to cope with the narrower tracks and decreased gaps. Current technology has reduced track widths and spacings to 0.15mm and the through holes to 0.3mm which is sufficient for current surface mounting packages but a further reduction to 0.075mm and 0.1mm respectively will be required for some proposed new packages. Heat dissipation is also a potential problem and is exaggerated by the reduced surface area of the new packages. Some manufacturers have attempted to reduce this problem by incorporating fins onto the packages but the general consensus is that overheating is better avoided than cured. Accordingly many manufacturers are converting to CMOS for the new devices.

Packaging

For well over a decade there has been a high degree of standardisation as far as IC packaging is concerned. ICs for through hole mounting will usually be standard DIL packages.

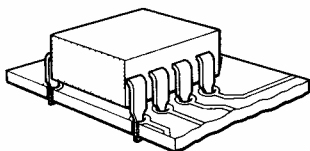
Surface mounting components are available in a bewildering array of different packages. Clearly there is a need for standardisation in this area and for one or two package types to be accepted as the standard in the same way as the DIL package has been for many years.



DIL Package

The DIL package is currently the standard IC package for through hole PCB assembly. All packages have straight pins spaced at 0.1in in two rows. The row spacing is dependent on the total number of pins in the package. Devices with up to 20 pins use a 0.3in row spacing. For 22 pins the spacing is 0.4in, for 24-40 pins it's 0.6in and for larger devices the row spacing is 0.8in.

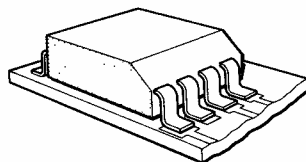
New packages (such as the 'skinny DIP' with a row spacing of 0.3in for all ICs, the shrink DIP with pin spacing reduced to 0.07in and the pin grid array used for high pin count ICs with a grid of pins on 0.1in centres) all represent attempts to reduce PCB space but are less effective than surface mounting techniques.



SOP or SOIC

The Small Outline Package (SOP) or Small Outline Integrated Circuit (SOIC) tend to be used for pin counts up to 24 — the range in which they are most efficient in terms of board space occupied. SOICs have the same pin arrangement as DIPs but on a smaller scale, pins being separated by 0.05in and the two rows by 0.15in for 8-16 pins and 0.3in for larger pin counts.

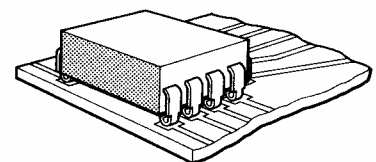Standard TTL and CMOS logic families are now available in SOP and since these packages have a clear similarity to DIPs, the pin outs are identical. Some analogue devices are also available in this format. In order to allow them to be surface mounted, SOICs have so called 'gull wing' pins.




PLCC

The Plastic Leaded Chip Carrier (PLCC) is a greater departure from DIL packaging having leads on all four sides of a square or rectangle. Like SOICs, the leads are spaced at 0.05in, half the distance of DIPs, but unlike SOICs, the leads are bent under the plastic package in what is referred to as a J-bend.

Pin counts available in PLCC are 18, 20, 28, 44, 68 and 84. Currently, logic families, memories, microprocessors, peripherals, gate arrays and analogue devices are available in PLCC format.

FEATURE: Surface Mounting

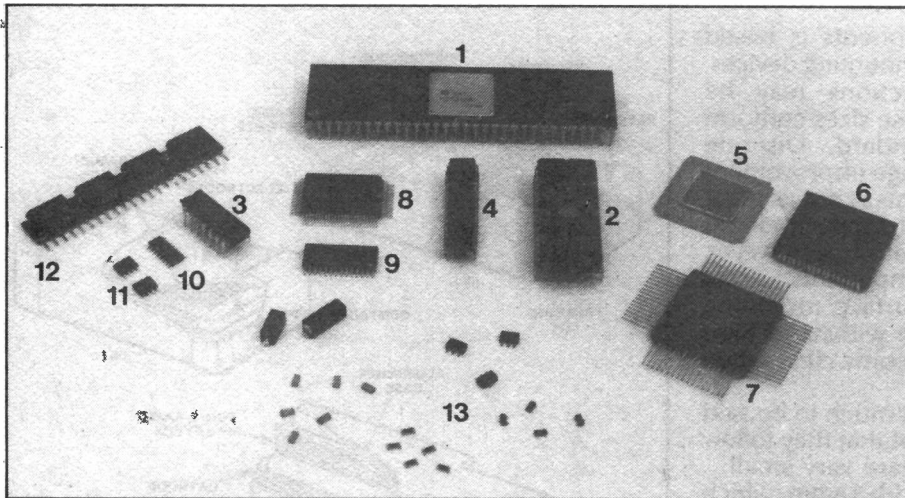

- 1) 64 pin DIL
- 2) 28 pin DIL
- 3) 14 pin DIL
- 4) 24 pin skinny DIL
- 5) 68 pin LCCC
- 6) 68 pin PLCC
- 7) 68 pin flat pack
- 8) 80 pin FPP
- 9) 28 pin SOIC
- 10) 16 pin SOIC
- 11) 8 pin SOIC
- 12) SIL module
- 13) Discrete components

Size Considerations

Surface mounting components are significantly smaller than their DIL counterparts. Figure 3 illustrates this more quantitatively, comparing the surface area of DIL, SOIC, FPP and chip carrier (PLCC or LCCC) packages. (See the box for explanations). Although this graph shows how a very significant saving in board area is achieved, it should be borne in mind that whereas the surface area increases with the square of the linear dimensions, the volume and hence the weight increase with the cube. In other words, the saving in weight will be even more significant so long as we compare similar packaging materials (both plastic or both ceramic).

Discrete Components

As the advantages to be gained by surface mounting integrated circuits would be considerably reduced if discrete components still had to be through mounted, most discrete components are either already available in surface mounting packages or under development. Resistors, capacitors, inductors, diodes and transistors may now be obtained in the surface mounting format from a number of suppliers. Connectors and variable components, on the other hand, are yet to make their


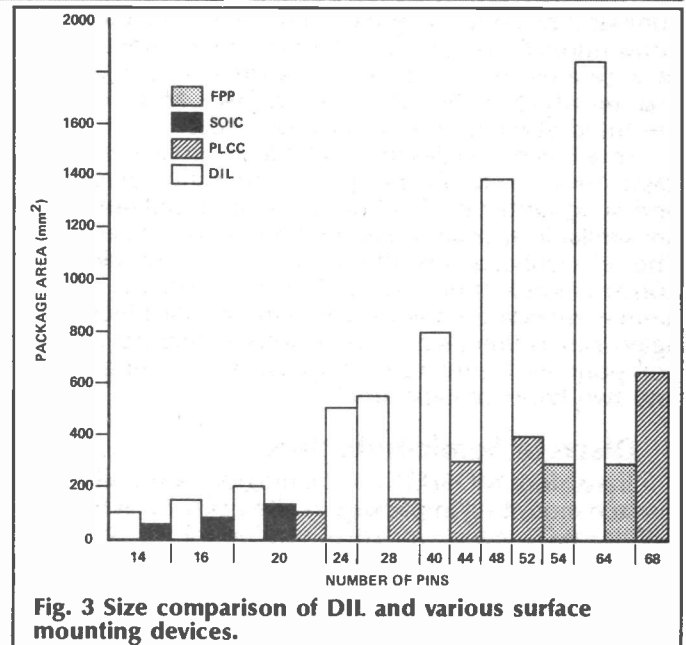



Fig. 3 Size comparison of DIL and various surface mounting devices.

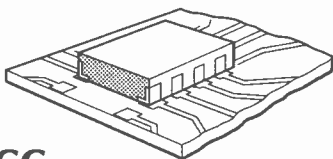

LCCC

The Leadless Ceramic Chip Carrier (LCCC) is similar to the PLCC but has no leads at all, the J-bend leads of the PLCC being replaced by metal contacts moulded into the ceramic body. As LCCCs are thinner than corresponding PLCCs and they lack leads protruding from the package, they are more robust and easily handled by automatic placement equipment. However, they are the most expensive surface mounting package and tend to be used primarily for military applications.

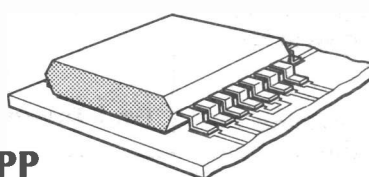Non military uses are mostly microprocessors and EPROMs where a quartz window is required. There are a number of different variants of the LCCC package to accommodate chips of different shapes. For example, there is both a square and a rectangular version of the 28 pin LCCC.



FPP

The Flat Plastic Package (FPP) has probably achieved less overall acceptance than the other three packages but nevertheless is used quite extensively by some manufacturers. Having gull wing leads on all four sides, spaced at even smaller gaps than SOIC, PLCC and LCCC packages, the FPP is well suited for large pin counts.

Currently, FPPs are available with up to 100 pins and the 200 pin package is under development. FPPs have various different pin spacings: 1.0mm, 0.8mm and 0.65mm versus being available and a move to a 0.55mm (0.02in) spacing looking likely.

As the pin spacing decreases as the pin count increases, packages up to 100 pins are all the same size. Clearly a major application of FPPs will be in semi-custom chips, gate arrays, etc — an area in which pin out has traditionally been a major limitation.



Other Packages

Further types of surface mounting package abound and include leaded ceramic chip carriers (which are not a ceramic version of the PLCC), PLCC variants (in which the pin count is increased by having two rows of pins in a castellated arrangement) and flat packs which can have leads protruding directly out of the sides of the pack. They can, however, have their leads pre-formed for either through hole or surface mounting assembly.

A further packaging strategy developed by British Telecom uses neither plastic nor ceramic but, in an attempt to overcome problems of thermal mismatch and strain between board and component, it uses epoxy glass PCB laminates as the chip carrier. Essentially, this is a surface mounting version of the pin grid array.

appearance in large numbers.

My information on discrete components is based mainly on the Mullard range of surface mounting devices. Although different internal constructions may be adopted by other manufacturers, the case sizes conform to an internationally accepted standard. Discrete components are small but the percentage improvement over through hole mounting components is not as great as with integrated circuits. Since most modern circuit boards are predominantly populated with ICs, however, size is not as critical with discrete components.

One important characteristic of surface mounting discrete components is their ability to withstand high temperatures. The need for this will become clear when we consider assembly.

From a user point of view, there isn't much to be said about a surface mounting resistor except that they follow the accepted E24 range of values and are very small.

The length is only 3.2mm and the width 1.6mm, which compares to a body length of 5mm for a comparable 1/4W conventional resistor. The internal construction consists of a ceramic block on which is deposited a resistive coating which is then trimmed by laser. Metal contacts are fitted at each end in place of leads.

Three technologies are available in surface mounting capacitors — ceramic multilayer, aluminium electrolytic and solid tantalum. The multilayer and tantalum types are similar in appearance to the resistors described above. The electrolytics on the other hand are closer in construction to their through hole counterparts with the aluminium cylinder then encased in a plastic block. Once again small dimensions are a notable feature of these components. Figure 4 shows a surface mounting resistor and two types of capacitor.

Discrete Semiconductors

Transistors, MOSFETs and Darlingtons are available for surface mounting in packages called SOT-23, SOT-89 and SOT-143 (SOT stands for small outline transistor). These SOT packages are very similar in appearance to a diminutive SOIC package with 3 or 4 pins. The SOT-23 and SOT-43 packages are only 3.5mm x 2.7mm and the SOT-89 is a little larger as it tends to be used for Darlington transistors which require a greater heat dissipation. The package used for diodes is the SOD-80. Some typical discrete semiconductors are shown in Fig. 5.

Assembly Methods

Conventional assembly involves first inserting the components through holes in the board either by hand

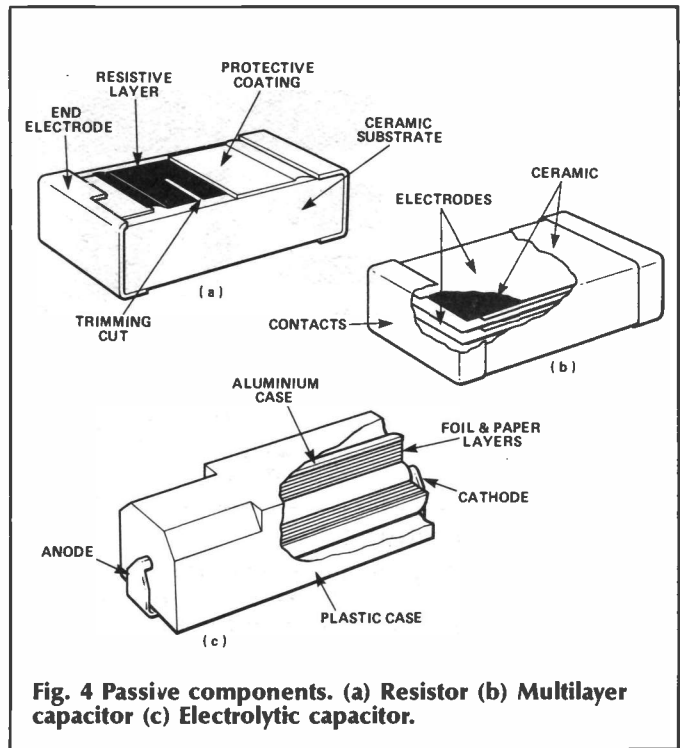


Fig. 4 Passive components. (a) Resistor (b) Multilayer capacitor (c) Electrolytic capacitor.


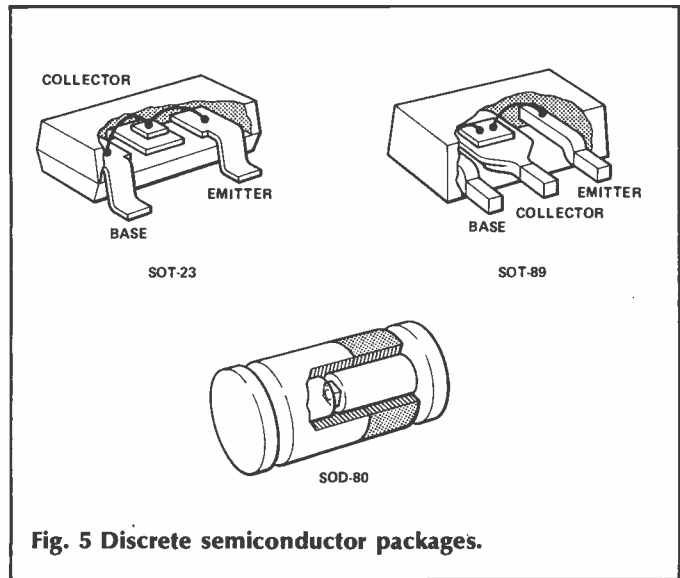


Fig. 5 Discrete semiconductor packages.

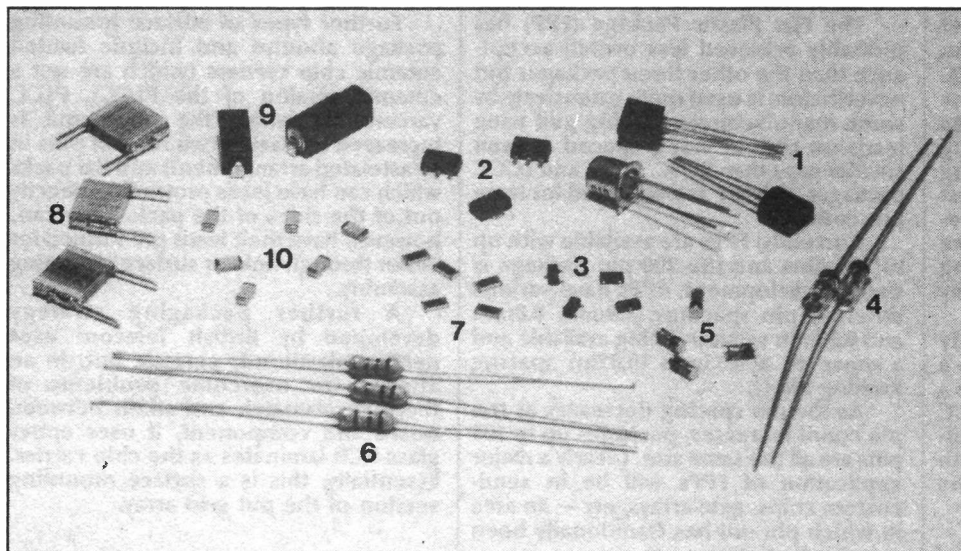

- 1) Conventional transistors
- 2) SOT-89 transistors
- 3) SOT-23 transistors
- 4) Conventional diodes
- 5) SOD-80 diodes
- 6) Conventional resistors
- 7) Surface mounting resistors
- 8) Conventional capacitors
- 9) Electrolytic SM capacitors
- 10) Ceramic SM capacitors

FEATURE: Surface Mounting

or by automatic insertion equipment and then passing the PCB through a wave soldering machine.

As the component leads pass through holes in the board the components are held in place while soldering is taking place. This would clearly not be the case with surface mounting components. In this case, some form of adhesive has to be used to secure the components until they are finally soldered. The adhesives used for this purpose fall into two categories — inert adhesive and solder paste.

Ordinary adhesive is used simply to fix the package to the board and is obviously applied to an area of the component well away from its electrodes (for example in the centre of a LCCC package). This type of adhesive is used with wave soldering, but an obvious difference between this and the wave soldering used with through-mounting components is that the solder wave is applied to the component side of the board. This explains why surface mounting packages are designed to withstand high temperatures. Figure 6 illustrates the solder wave method of PCB assembly.

The other type of adhesive (solder paste) is used with a family of assembly methods known as reflow methods. Solder paste is a form of adhesive which actually contains a high proportion of solder powder. This paste is applied to the copper pads of the PCB and the component is fixed to the board by its electrical contacts. The board is then heated to about 260°C at which temperature the solder in the paste melts and forms a solder joint between PCB and component.

Various methods are used for this reflowing. The most widely accepted is vapour phase. In this, the board is placed in the vapour of a boiling inert liquid, usually a fluorinated hydrocarbon. The advantage of vapour phase over other reflow methods is that it enables the reflowing to be carried out at a comparatively low temperature. A constant temperature is achieved without the need for complex control circuitry and the use of an inert atmosphere eliminates the possibility of oxidation. Figure 7 shows a typical arrangement for vapour phase reflow soldering.

Other methods used for reflow heating are infrared, convection, hot air jets, laser and pulse heated solder tools. Of these only infrared and possibly convection offer a viable large scale alternative to vapour phase, the other methods being used for small volume production or repair.

It will be obvious that both board and components are raised to a high temperature during soldering and subsequently both return to room temperature. If the materials used for the PCB and the components have different co-efficients of expansion, there is a very real possibility of stress being placed on the assembly.

In the case of the LCCC and most passive components, this is exaggerated due to the lack of leads which would allow some degree of flexibility. For this reason, a great deal of research has been carried out to find new and more suitable materials for the PCB. New materials used for PCBs for the surface mounting of ceramic chip carriers and which have similar co-efficients of expansion include ceramics and insulated aluminium or copper.

The Future

There is no doubt that surface mounting is the way ahead in the electronics industry, the only questions are *How much?* and *How soon?*. Today a relatively small percentage of applications have gone to surface mounting due mostly to a resistance to change, the capital outlay required and the higher cost of surface mounting components.

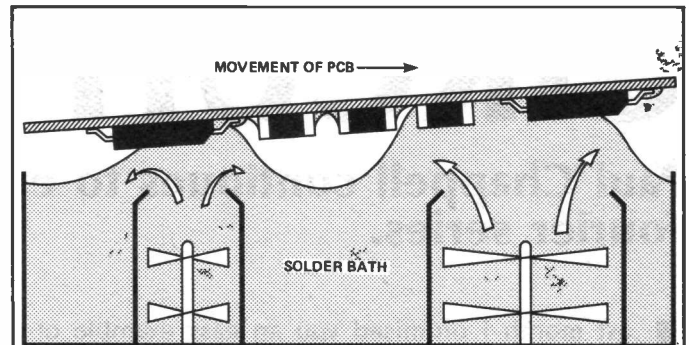


Fig. 6 Dual wave soldering.

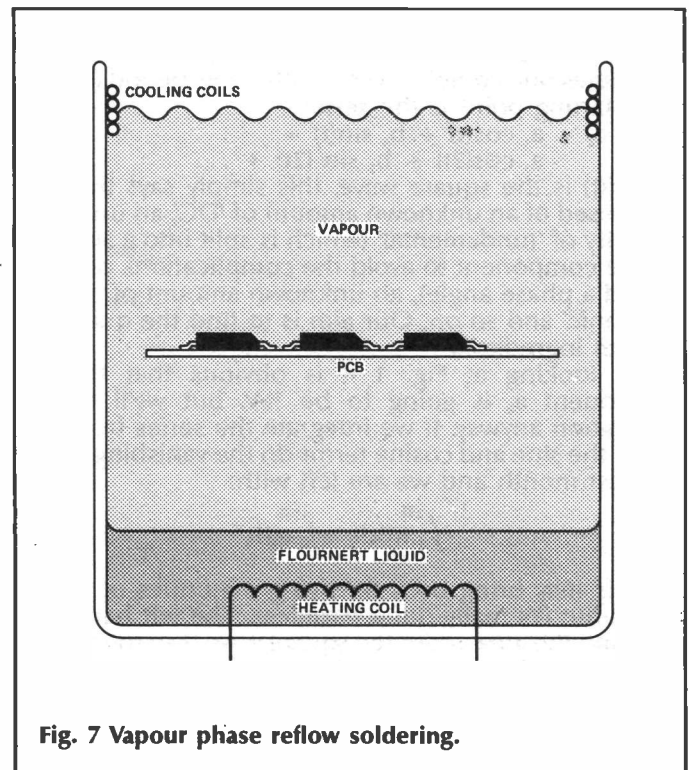


Fig. 7 Vapour phase reflow soldering.

It is generally considered that this price premium is only a short term situation and that by the end of the decade it will be the DIL components which are the more expensive. It is also significant that even now some of the new microprocessor peripherals coming onto the market are only available in PLCC or LCCC packages. Despite these factors, however, the move to surface mounting is perhaps not taking place quite as rapidly as predicted only a couple of years ago.

Japan is the current world leader in this technology, being the first country to use it on a large scale in cameras and other consumer goods where space saving is important. About 30% of electronics manufacturing used surface mounting during 1985 in Japan and it is suggested that this will rise to about 50% by 1990.

On the other hand, it looks as if Europe will be using only 35% by the end of the decade. Indications are that it is in the area of active components that the changeover will be most apparent.

Already the world usage of passive components is about 25% surface mounting but the vast majority of transistors used are still leaded. By 1990 it is predicted that the figure for transistors will be approaching 75%.

Certainly time will tell but in the meantime it could be worthwhile getting in some practice with a very small soldering iron and a very steady hand!

ETI

CIRCUIT THEORY

Paul Chappell continues to explore the labyrinth of the Fourier series.

Last month I promised you an easy example of a Fourier Series. In all good textbooks (and bad ones for that matter) it is *de rigueur* to begin with a square wave. Since the calculations are easy, I'll do the same!

In the calculations of the Fourier coefficients, the integrations are carried out over the interval 0 to 2π , so to make things really easy let's have a square wave which completes one complete cycle within this period (Fig. 1a). Our starting point is the series:

$$f(t) = a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t) + b_2 \sin(2t) + \dots$$

If $f(t)$ is the square wave, this simply says that it is composed of an unknown amount of 'DC', an unknown quantity of 'fundamental' (which is split into a sine and cosine component to avoid the complications of trying to find a phase angle), an unknown amount of 'second harmonic' and so on. Our aim is to find the quantities of each ingredient.

By looking at Fig. 1 it is obvious that the DC component a_0 is going to be $\frac{1}{2}V$, but we'll do the calculation anyway. If we integrate the series from 0 to 2π all the sine and cosine terms do the vanishing act we saw last month and we are left with:

$$\int_0^{2\pi} f(t) dt = \int_0^{2\pi} a_0 dt$$

This may bring back terrifying memories of school maths but it's really quite harmless. The left hand side says 'find the area under the square wave over the interval 0 to 2π '. Looking at Fig. 1, this is going to be $1 \times \pi$.

The right hand side says 'find the area under a straight line of 'height' a_0 over the interval 0 to 2π '. From Fig. 1b, it's going to be $a_0 \times 2\pi$. The 'equals' sign in the middle says 'make the two areas the same'. Once again, it's obvious that the value of a_0 which will make the two areas the same is $\frac{1}{2}$.

Although it's obvious what the result will be, we'll press on regardless. Replacing $f(t)$ with the square wave it represents, the result is:

$$\int_0^{\pi} (1) dt + \int_{\pi}^{2\pi} (0) dt = \int_0^{2\pi} a_0 dt$$

What has happened now is that the area under the square wave has been replaced by the area under it when it's equal to 1 (over the first half of the interval from 0 to π) plus the area under it when it's equal to zero (over the second half of the interval from π to 2π), which I'm sure you'll agree is the same thing.

Now we do the integrations and end up with:

$$\pi + 0 = a_0 \times 2\pi \Rightarrow a_0 = \frac{\pi}{2\pi} = \frac{1}{2}$$

We knew it all along, but doesn't it boost your confidence to see the maths trot out the same answer? No? Well, can't please everyone I suppose!

Finding the other coefficient is just as easy. Take b_1 as an example. Again, start with the series:

$$f(t) = a_0 + a_1 \cos(t) + b_1 \sin(t) + a_2 \cos(2t) + b_2 \sin(2t) + \dots$$

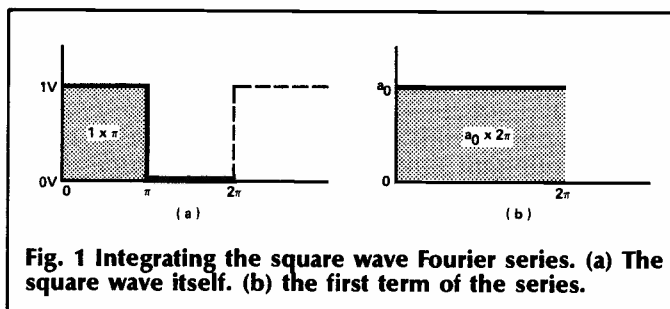


Fig. 1 Integrating the square wave Fourier series. (a) The square wave itself. (b) the first term of the series.

Now, somehow we have to get rid of all the terms in the series (Fig. 2a) except for the one involving b_1 (the coefficient we're concentrating on for the moment). If the series is multiplied throughout by $\sin(t)$, the result is shown graphically in Fig. 2b. It results in all the components having equal areas above and below the axis except for the $\sin^2(t)$ part. If we now integrate over one period, the areas above and below the axis cancel out, so all the terms disappear except for the one we're interested in. So, first we multiply through by $\sin(t)$: $f(t) \sin(t) = a_0 \sin(t) + a_1 \cos(t) \sin(t) + b_1 \sin^2(t) + a_2 \cos(2t) \sin(t) + b_2 \sin(2t) \sin(t) + \dots$

Now we integrate from 0 to 2π (Fig. 2c):

$$\int_0^{2\pi} f(t) \sin(t) dt = \int_0^{2\pi} a_0 \sin(t) dt + \int_0^{2\pi} a_1 \cos(t) \sin(t) dt + \int_0^{2\pi} b_1 \sin^2(t) dt + \dots$$

Since all the terms except the one involving b_1 are zero (Fig. 2d) this leaves:

$$\int_0^{2\pi} f(t) \sin(t) dt = \int_0^{2\pi} b_1 \sin^2(t) dt$$

Finally, replacing $f(t)$ by the square wave it represents, the left hand side follows $\sin(t)$ for half a cycle, then becomes zero for the rest:

$$\int_0^{\pi} \sin(t) dt = \int_0^{2\pi} b_1 \sin^2(t) dt$$

Now, the left hand side of this equation says 'find the area under one cycle of a half-wave rectified sine', the right hand side says 'find the area under $b_1 \sin^2(t)$ (the two mountain peaks, or whatever else your imagination may make of them, in Fig. 2d). The 'equals' sign says 'make the two areas equal'. This time it's not obvious what value of b_1 is needed to make the two areas equal, so we'll have to continue with the maths.

There's no need to 'do' the integration on the right hand side — from the orthogonality properties of sines we already know that $\int_0^{\pi} \sin^2(t) dt = \frac{\pi}{2}$. The result is:

$$\int_0^{\pi} \sin(t) dt = b_1 \frac{\pi}{2} \Rightarrow 2 = b_1 \frac{\pi}{2} \Rightarrow b_1 = \frac{2}{\pi}$$

The other coefficients are calculated in exactly the same way, so there's nothing to be gained by going through another in detail (but do try one for yourself). To save time, I'll do all the rest at once:

$$\int_0^{\pi} \sin(nt) dt = b_n \int_0^{2\pi} \sin^2(nt) dt$$

The left hand side is the result of multiplying the square wave by $\sin(nt)$. It's equal to $\sin(nt)$ over the first half of the interval (0 to π) and zero thereafter. The right hand side is the remaining term after all except the one involving b_n have vanished.

$$\left[-\frac{1}{n} \cos nt \right]_0^\pi = b_n \pi \Rightarrow b_n = \begin{cases} 0 & \text{for } n \text{ even} \\ \frac{2}{n\pi} & \text{for } n \text{ odd} \end{cases}$$

A similar calculation for the cosine coefficients shows that every single one of them is zero, so the Fourier expansion of a 0.5Hz, 1V square wave is:


$$f(t) = \frac{1}{2} + \frac{2}{\pi} \left(\sin t + \frac{1}{3} \sin 3t + \frac{1}{5} \sin 5t + \dots \right)$$

So, a square wave has a DC component and a series of sine components which diminish with frequency. There are no even harmonics at all.

What happens if we want to find the spectrum of a higher frequency square wave? Or a higher amplitude one? Or one centred on 0V instead of above it? Do we need to do the calculations all over again?

You'll be relieved to hear that having found the spectrum for one square wave, we've found them all. Because integration is a linear operation (double the amplitude of a wave and you double the area under it, for instance) all we need to do is scale the coefficients. The time axis can also be scaled for different frequencies. I said earlier that the 0 to 2π interval represents 2 π seconds, but I could equally well have said 2 π milliseconds, or any other scale I happened to choose.

When calculating a Fourier series it is usual to choose the easiest possible values to work with, which generally means an angular frequency of 1 radian per second and a peak value of 1V. The use of *normalised* values (easy values which can be scaled afterwards to suit your purposes) is very common in linear circuit theory. (It doesn't work with non-linear maths or circuits because the values can't be scaled!)

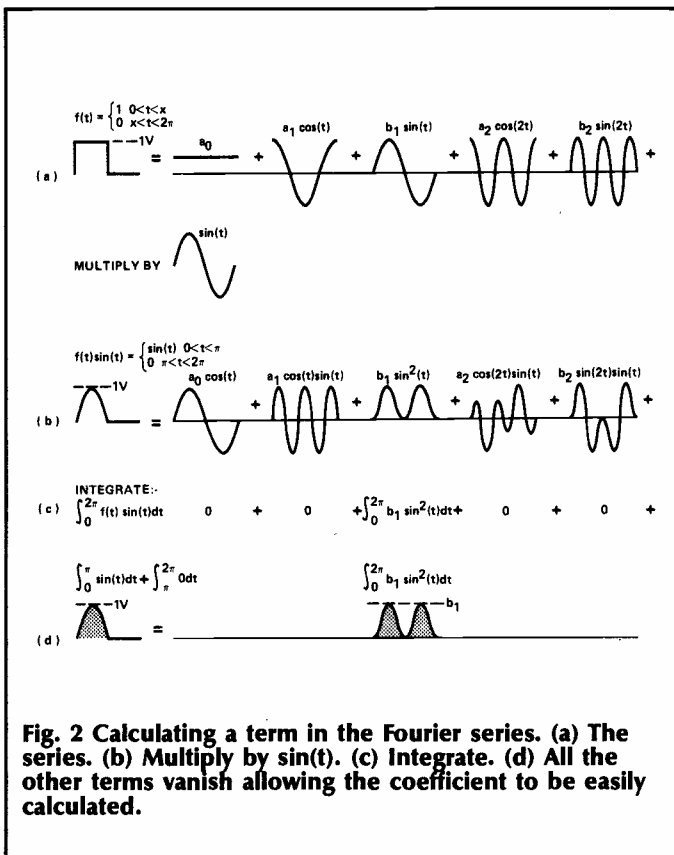

As an example, to find the Fourier expansion of an 8V peak-to-peak square wave at 1kHz, varying between $-2V$ and $+6V$, first multiply the coefficients by 8: $f(t) = 4 + \frac{16}{\pi} \left(\sin t + \frac{1}{3} \sin 3t + \dots \right)$ (this wave is of frequency 0.5 Hz, 0 to 8V). Scale up the frequency from 0.5Hz to 1,000Hz (increase frequency by a factor of 2000π)

$f(t) = 4 + \frac{16}{\pi} \left(\sin(1000\pi t) + \frac{1}{3} \sin(3000\pi t) + \dots \right)$ (this is 1kHz wave, 0 to 8V). Finally, adjust the DC level — the whole wave is shifted 'downwards' by 2V, so the mean level will also be 2V lower: $f(t) = 2 + \frac{16}{\pi} \left(\sin(1000\pi t) + \frac{1}{3} \sin(3000\pi t) + \dots \right)$ (this is 1kHz wave, $-2V$ to $+6V$).

A question I raised last month, but left unanswered, was the range of functions which can be expanded as a Fourier series. In the broadest sense of the question it seems clear that since all the harmonic components repeat after each interval of 2π the series is only appropriate to continuous, repetitive waveforms. Euler (who derived the 'Fourier series' before Fourier did) would have agreed. Fourier himself, with his cavalier attitude to the niceties of maths had no difficulty in accepting that if he could make the series fit over the length of his iron bar, what it did elsewhere was irrelevant.

It's a notion we feel comfortable with today, but to the mathematicians of Fourier's time it was a huge conceptual stumbling block. If we *do* care what the series does beyond the interval of interest, it's a job for the Fourier integral, which is a story for another day.

On another level, what guarantee do we have that the Fourier series actually matches the initial waveform? Last month I showed graphically how adding extra sines in the correct proportions brought the *partial sum* (the sum of the harmonic components 'so far') closer and closer to a square wave — for the first three at least. Could there be a series in which adding extra sines takes the waveform further and further from the original?

The process of getting a better approximation as more terms are added is called *convergence*. If the approximation gets worse as more terms are added, the series is said to *diverge*. The notions of 'better' and 'worse' are too loose to work with but think about this for a moment.

Suppose I choose some point along the time axis ($\pi/2$, say) for the square wave of Fig. 1, and note the value at that point (it will be 1). Now I'll take the Fourier series for the square wave and calculate the first few partial sums at that point. Taking only the first term, the DC component, it's $1/2$. 50% out! Not too good so far. Add in the next term, which is $2/\pi \sin t$. At $\pi/2$ this will have a value of roughly $2/3$. Adding to this the first term gives $1/2 + 2/3 = 5/6$, $1/6$ too high. The next term has a value of roughly $-2/9$ at $\pi/2$; adding this in gives $17/18$. The value is low again, but only $1/18$ out.

With each successive term, the partial sum oscillates about the required value, but the general trend is to get closer to it quite rapidly. From a 50% error to a little over 5% in three terms is not too bad! If this happens for every single point on the square wave and the partial sums remain within any arbitrarily small distance from the true value if enough terms are taken, the series can certainly be said to converge.

The notion of a series converging at every single point is called (naturally enough) *pointwise convergence*. This aspect of the Fourier series was investigated in detail by Dirichlet (1805-1859). He concluded that a Fourier series will match any continuous waveform with a finite number of turning points. (It can have a million billion of them, a googolplex of them, a moser of them, as many as you like as long as it's finite). If the waveform also has a finite number of discontinuities, it will have a Fourier series which matches it everywhere *except* at the discon-

tinuities, where it will have a value half way between the points on either side.

An example of a waveform with discontinuities is the square wave. We are used to seeing square wave approximations displayed on 'scopes, where they have 'vertical sides' from a finite rise and fall time, but really a square wave should be drawn as in Fig. 3a. A true square wave leaps instantaneously from one value to another — this is known mathematically as a discontinuity. Dirichlet's claim is that the Fourier series for the square wave actually adds in spurious points as in Fig. 3b!

It's easy to see that the series will indeed add in these points. Think about the point $t = \pi$ where Fig. 1 drops from 1 to 0. Here, every single sine term will have a value 0, so all that remains is the constant term of $\frac{1}{2}$, which puts in a point smack in the middle of the two square wave values!

What's going on here! For practical purposes the appearance of a single extra point at each transition makes no difference. After all, a single point lasts for exactly no time at all, so no circuit will ever notice it. But it's still rather disconcerting to find that the maths is wrong. Thanks to Dirichlet it's predictably wrong, but wrong all the same.

This is by no means the end of the story. Take the wave in Fig. 3c, for example. It is a square wave except for a few odd points which have gone astray. The Fourier series for this is exactly the same as for a perfect square wave! The common sense reason is that since the Fourier coefficients are calculated by integration, the points have no area beneath them and are therefore 'invisible' to the process.

It's interesting to see how far this notion can be pushed. Clearly, any finite number of points (a million billion, a googolplex, a moser — you name it) will be invisible to the integration. If one point has no area beneath it, a million points will have no area beneath them. There are even some infinite sets of points which will do the trick. If the square wave goes astray on every point in the interval which can be expressed as a rational number (a 'fraction') the Fourier coefficients will still turn out with the same values. To see how outrageous this is,

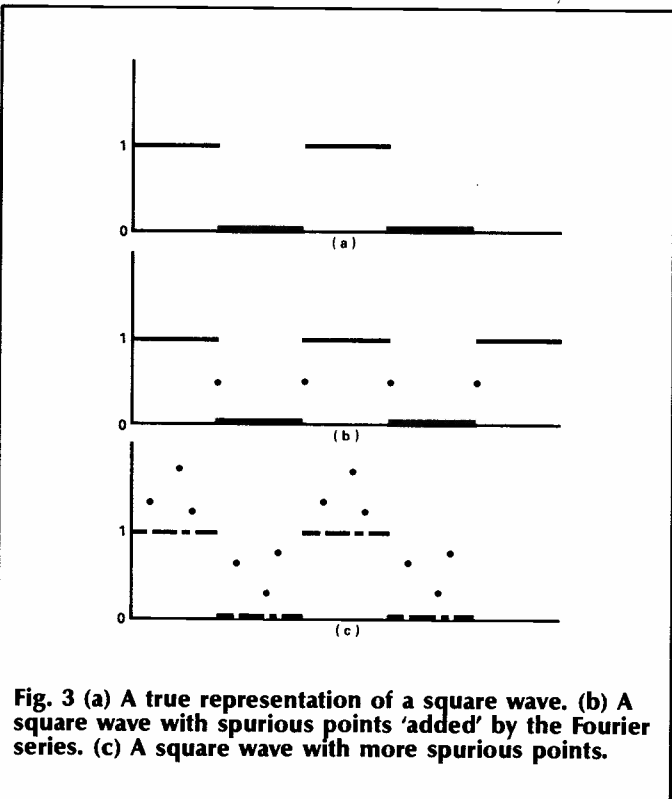


Fig. 3 (a) A true representation of a square wave. (b) A square wave with spurious points 'added' by the Fourier series. (c) A square wave with more spurious points.



Joseph Fourier
1786-1830

Fourier would probably have thought of himself as a politician rather than a physicist (although he should not be confused with Charles Fourier, the utopian socialist, who was born and died within a few years of J. Fourier). Today he is remembered almost exclusively for his *Theorie Analytique de la Chaleur* (Analytic Theory of Heat) published in 1822.

Fourier's study of heat conduction led him to believe, by physical rather than mathematical reasoning, that the temperature distribution in a rectangular bar could be expressed as a series of sines and cosines.

He then set off on a most bizarre calculation which involved a Taylor series expansion of functions which didn't actually have one and division by (in effect) infinity. He ignored everything that didn't correspond to his preconceived idea of what the answer ought to be!

Fourier was not the first person to propose sine wave expansions or even to calculate what we now call the Fourier coefficients (Euler had done it some 45 years previously). His outstanding contribution was to recognise the full extent of the validity of the expansion. It had previously been supposed to apply to only a very limited range of functions.

For this insight, Fourier was awarded the Grand Prize of the Academy without having proved a single correct result about the series that bears his name!

consider that any interval, however small, has a rational number in it. There is not the tiniest portion of the modified square wave where its Fourier series matched it at every point!

At this stage there are two options. You can say 'Enough of this nonsense!' and refuse to admit that square waves with points scattered here and there have a Fourier series at all. Alternatively, you can shift the goal posts — devise a new definition of convergence which allows for the fact that it seems to be possible to derive a Fourier series for some very bizarre functions.

Mathematicians, needless to say, have taken the latter course. Research into Fourier series is still a fertile area to this day and a definitive answer to the question of which functions do and do not have a Fourier expansion is still not in sight.

ETI

HARDWARE DESIGN CONCEPTS

Mike Barwise takes a look at programmable logic devices and finds they are not exclusively the province of commercial designs.

Programmable logic devices (PLDs) are frequently considered a great mystery. There is a myth that they are very difficult to use, possibly due to their requirement for programming equipment beyond the pocket of most amateurs.

Designing with PLDs is in fact extremely easy and several suppliers of these devices now run programming services at quite moderate cost (a £25 setup charge is typical) and so the use of PLDs in logic design no longer has to be solely the domain of manufacturing industry.

PLDs come in three basic official categories, PAL, PLE and PLA. It is, however, seldom pointed out that the now familiar EPROM is also a programmable logic device. The assumption that EPROMs only store PROGRAMS is a very limited view of their potential.

I have been asked to mention at this point that PAL and PLE are trademarks of Monolithic Memories, who arguably invented the PAL concept.

Conventional Logic

I do not intend to go into the theory of Boolean algebra here, as there are many good textbooks available. The fundamental concept behind PLDs is worth stating though. The concept is: *Any logic function can be reduced to a sum-of-products expression.* A sum-of-products expression is a formula equating an output with a set of inputs via the operators AND, OR and NOT. For example the EXCLUSIVE-OR function can be expressed as:

$$Y = A \cdot \bar{B} + \bar{A} \cdot B$$

where A and B are two inputs, Y is the output, * means AND, + means OR, the bar means NOT (invert) and = means equals! This relationship is shown as logic gates in Fig. 1.



This axiom holds true for both combinatorial (gates only) and sequential (clocked logic), the only difference being that race conditions establish the timing of combinatorial networks, whereas the outputs of sequential circuits are synchronised by the clock. The conventional symbol for *equals* in sequential logic equations is := (colon-equals) which is interpreted as *results in after clock*.

PAL, PLE, PLA: The Differences

Assuming that a finished logic network is constructed according to the axiom given above, there will be considerable variation in the interconnection density at the different levels according to the nature of the logic function implemented. Some functions may need lots of inputs to each AND gate while others need few inputs per AND term but lots of OR inputs from a large AND array. To accommodate these differing requirements, the three types of device have been produced — PAL, PLE and PLA. See Fig. 2.

PAL consists of a programmable AND array with true and inverting inputs to each AND gate, coupled to one fixed OR array per output (Fig. 3). PAL is the most useful

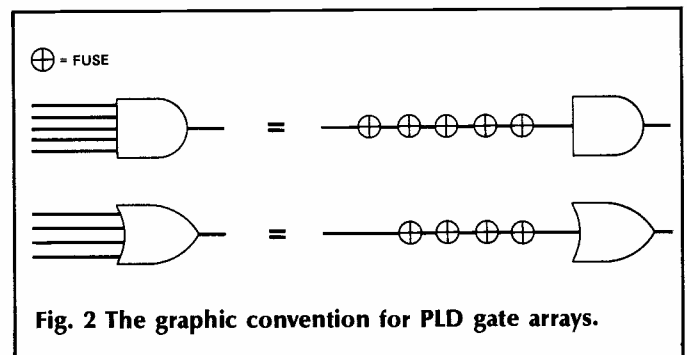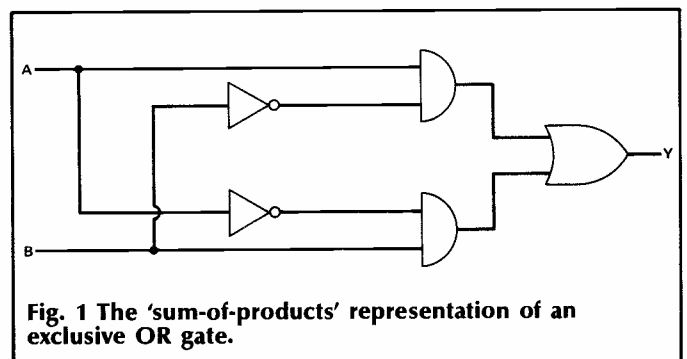when you are designing AND intensive circuits like counters and shift registers. The range of alternative matrix configurations is greater than that of PLE (this is necessary as there is a limited number of AND terms



allocated to each OR/output term due to pinout and programming constraints), and many parts have additional 'higher level' functions built in, such as registers with feedback into the AND array, or exclusive-OR networks at the inputs to provide additional terms to the array.

PLE is the logic designers' definition of the familiar PROM. It has a fixed, exhaustively decoded AND array (all possible combinations of all inputs available and no 'don't care' inputs) and a programmable OR array. This is beneficial when you want a complex random logic sequence, or for random block decoders, in fact anywhere your number of alternative output states is the measure of complexity.

Some PLE devices are available with output registers, allowing safe feedback into the PLE or its own outputs. If you can handle the brain strain, this is a method of generating surprisingly complex logic sequences and is the basis of microcontroller design. It is quite possible to cause fed back inputs to conditionally modify the output sequence by gating them externally with real world stimuli.

The PLA is the most complex of the three to work with, but arguably the ultimate in versatility. It has both programmable AND and programmable OR arrays, and

is the next best thing to a fully custom chip layout (Fig. 5). However, design tools for PLA tend to be expensive and flashy (in the £1000-plus bracket) so we won't give these devices much further attention at the moment.

Designing Your Logic'

Let us take a very simple problem to start with. Suppose we want to create our own 1-of-8 decoder equivalent to the TTL 74LS138. It can be implemented in a PROM (PLE, EPROM) very easily. There are two common routes to the solution. One is to write out an exhaustive truth table (the whole size of your PROM!) of the data for all addresses (including those not actually required) and then key the PROM output data into a programming file.

The other method is to express the problem as a set of Boolean equations (one for each of the eight PROM outputs) and let a PLE assembler generate the actual programming data. In fact, the limited number of states required (nine) suggests that the latter is the only sensible approach.

The first task is to define the input and output requirements. We must:

- Recognise eight unique input patterns of three bits but only if all enable signals are active.
- Provide a standard null output for all other input patterns.
- Provide eight unique outputs which correspond to the literal binary values of 0-7 in accordance with the relevant inputs.

Supposing we want a direct replication of the 74LS138, we have two low enables and one high enable. However, let us make a small improvement and add another high enable. This gives us three address inputs and four enable inputs (a total of seven) which dictates a PROM size of 128 bytes. We also need eight outputs, so the minimum device is a 128x8 PROM. The sensible EPROM

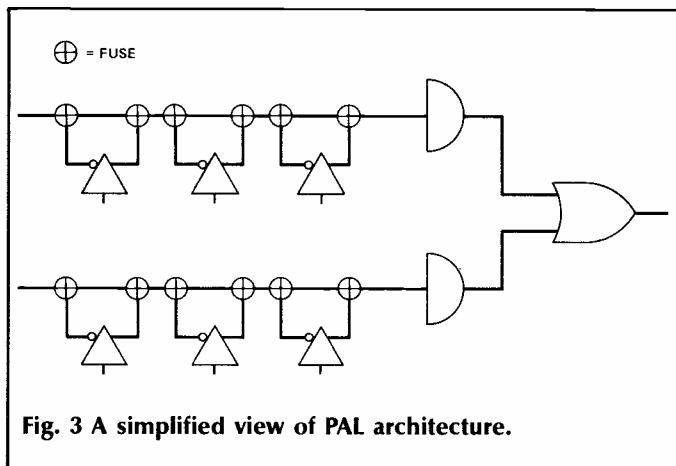


Fig. 3 A simplified view of PAL architecture.

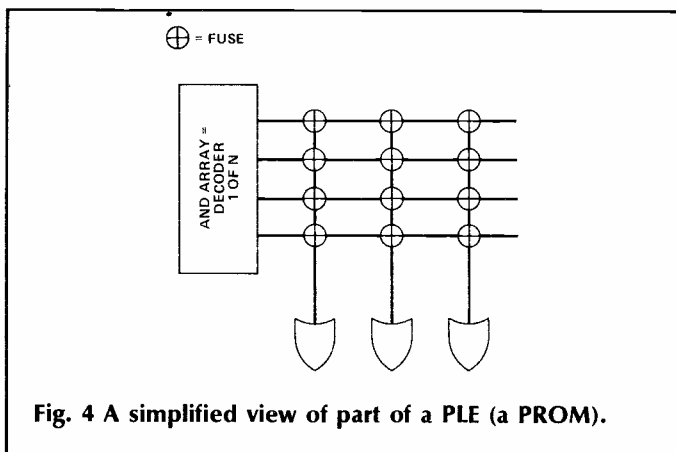


Fig. 4 A simplified view of part of a PLE (a PROM).

solution is a 2716 (2Kx8) with the three high address lines grounded.

If we design our decoder in EPROM by the truth table method, it is necessary to consider the best choice of address pin for each input. If, for example, the enables were allocated to low address lines (A0, A1, A2, A3) the active data in the EPROM would be widely distributed throughout its memory map (consecutive control bytes 16 addresses apart) which would make data entry very tricky.

The alternative (selection of inputs to simplify the generation of the PROM table) could make the resultant device less easy to connect up in use. A PLE assembly tool such as MMI's Pleasm would automatically handle this problem. As there are no design tools for EPROM, however, we must be our own PLE assembler and we must find a short cut if we want to minimise the possibility of errors and optimise the resultant device. Any short cut will become obvious as soon as the equations for our decoder have been generated, so let's do that next.

The Boolean Solution

The description of the 1-of-8 decoder in sum-of-products form is really very simple. We consider each output in isolation. First we must declare our input and output signals (the constants and variables in our equations).

Let us call our inputs HE1, HE2 (the active high enables), LE1, LE2 (the active low enables), A0, A1, A2 (the three address inputs), and our outputs M0-M7 (memory chip selects).

The universal condition for operation is that all enables are active. So there is a common term to all eight output equations, which is:

$$ACT = HE1 * HE2 * \overline{LE1} * \overline{LE2}$$

where ACT is a macro name (a shorthand reference) for the right hand expression. This can be used to reduce the typing burden and improve readability in the remaining equations. The active low enables have been negated to demonstrate their active low status.

Whenever ACT is TRUE (HE1 and HE2 are high and LE1 and LE2 are low) the decoder will generate one of the selectable outputs. ACT is only a theoretical term (the full right hand expression will always be substituted for it eventually) so it can be considered as active high (the default) for convenience.

The equation for M0 (the lowest addressed output) is thus:

$$\overline{M0} = ACT * \overline{A2} * \overline{A1} * \overline{A0}$$

so M0 will go LOW when all enables are active and all three addresses are LOW).

The remaining equations are:

$$\overline{M1} = ACT * \overline{A2} * A1 * \overline{A0}$$

$$\overline{M2} = ACT * \overline{A2} * \overline{A1} * A0$$

$$\overline{M3} = ACT * \overline{A2} * A1 * A0$$

$$\overline{M4} = ACT * \overline{A2} * \overline{A1} * \overline{A0}$$

$$\overline{M5} = ACT * \overline{A2} * \overline{A1} * A0$$

$$\overline{M6} = ACT * \overline{A2} * A1 * \overline{A0}$$

$$\overline{M7} = ACT * \overline{A2} * A1 * A0$$

Note that the outputs are labelled with the NOT symbol to indicate that they are active LOW. All the equations are interpreted in a similar manner to the first.

When this set of equations (which exhaustively describes the 1-of-8 decoder) is fed into a PLE (PROM) assembler, all the internal mapping and address correlation is automatically taken care of and the user only has to specify which device pins he has chosen to perform each function. Similarly, the EPROM user has to decide which pins are which but instead of working out and then keying the whole table into an EPROM programmer, we use our short cut. This consists of

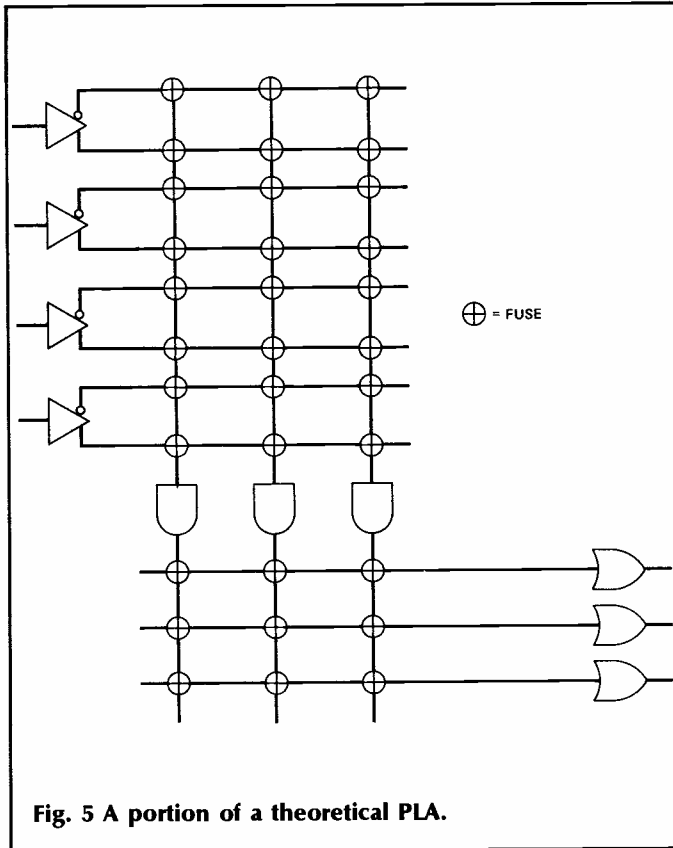


Fig. 5 A portion of a theoretical PLA.

referencing the chosen inputs and outputs to their theoretical binary weight.

Mapping Into The EPROM

First you choose a convenient input pin for each device input in terms of the physical layout of the final device. You might, for example, want all your enables together at the top left of the chip, and your address inputs below them. At this point you must also decide which inputs are to be used. Note that any EPROM enables must be considered as unused, as these tri-state the device, which we don't want. We are concerned here with *address inputs* and *data outputs* only.

Having defined the function of all inputs, you proceed similarly with the outputs. A table of the result of this process demonstrates that each active pin has been assigned a 'binary weight' resulting from its conventional EPROM AD or D values (Table 1). By substitution of these binary weights into both sides of each equation in turn, you arrive at a data byte expected at each of eight unique input addresses (Fig. 6).

Poking these bytes into a table the full size of your EPROM (2K) will produce the desired result (Fig. 6). The large number of 'non-active' states (when the enable term ACT is not true) can be handled by pre-writing the whole EPROM table with FFh. This equates in logic terms to 'all outputs high'.

Any truly 'don't care' inputs (spare address lines) can be hard wired to ground to minimise the size of the required table, otherwise the equations you create must include them as phantom terms. If, for example, eight address lines were present and you have chosen to use the low seven (A0-A6) the table you generate must be duplicated in both the upper and lower halves of the EPROM (selected by A7) unless A7 is assumed hard wired to ground, when only the lower table is needed.

Do not expect much performance from the EPROM decoder. It is really a demonstration rather than a viable option. However the same process applied to a 128x8 or 256x8 bipolar PROM yields a perfectly useable device.

PLE or PAL?

While the 128x8 PROM (PLE) version of the decoder is quite adequate, the number of used terms (in particular the lack of OR terms) makes this decoder a prime candidate for implementation in a PAL.

A PAL is chosen for a given implementation, after the Boolean equations have been written, according to the following criteria:

- How many input pins do you need?
- How many outputs pins do you need?
- How many OR terms per output? If this varies from output to output, is the distribution of OR terms in a given PAL adequate?

This looks surprisingly like the decision set for choice of PLE (PROM), doesn't it! The major difference is the third item. The number of OR terms per output in PAL is fixed so the OR terms matter. Next month we will look in more depth at PAL implementation and consider some more complex examples where PAL scores heavily in terms of neatness and ease of use.

Function	EPROM pin	Binary Weight (hex)	Function	EPROM pin	Binary Weight (hex)
HE1	1 AD7	I 80	Vcc	24 Vcc	Vcc
HE2	2 AD6	I 40	GND	23 AD8	I 100
LE1	3 AD5	I 20	GND	22 AD9	I 200
LE2	4 AD4	I 10	Vcc	21 Vpp	Vcc
A2	5 AD3	I 8	GND	20 OE	GND
A1	6 AD2	I 4	GND	19 AD10	I 400
A0	7 AD1	I 2	GND	18 CS	GND
GND	8 AD0	I 1	M7	17 D7	Q 80
M0	9 D0	Q 1	M6	16 D6	Q 40
M1	10 D1	Q 2	M5	15 D5	Q 20
M2	11 D2	Q 4	M4	14 D4	Q 10
GND	12 GND	GND	M3	13 D3	Q 8

Table 1 Binary Weight Table for 1-of-8 decoder in 2716 EPROM. I = input, Q = output, GND = NOT for weighted terms.

Boolean equation:

$$\overline{M0} = HE1 * HE2 * LE1 * LE2 * A2 * A1 * A0$$

Assume all inputs/outputs default high:

Input pins AD7-AD0

Output pins D7-D0

Any included GND = NOT

Expand the equation:

$$M7 * M6 * \overline{M5} * \overline{M4} * \overline{M3} * \overline{M2} * \overline{M1} * \overline{M0} = HE1 * HE2 * LE1 * LE2 * A2 * A1 * A0 * \overline{GND}$$

Substitute EPROM pin names:

$$D7 * D6 * D5 * D4 * D3 * D2 * D1 * \overline{D0} = AD7 * AD6 * AD5 * AD4 * AD3 * AD2 * AD1 * \overline{AD0}$$

Sum the binary weights:

$$FE \text{ (hex)} = CO \text{ (hex)}$$

In other words, program EPROM byte CO (hex) with data FE (hex)

Fig. 6 Manual function mapping. An example substitution for M0.

FINDING LOVE

through **Dateline**

When you join Dateline you meet so many people that if you choose to stay on your own, you know it's not through lack of opportunity. The problem is, of course, that faced with that special person you've always hoped to meet, the joys of the single life fade fast.

Dateline arranges over half a million introductions each year — people of all ages, all walks of life, and from all over the country join Dateline and are matched specifically to the type of person they want to meet in the area they choose.

WHY DATELINE?

●Dateline has operated a computer dating service in this country since 1966, many years longer than any other company, and is now the largest and **MOST SUCCESSFUL** computer dating service in the world.

●Our experience over more than **20 YEARS** has created a **professional, reliable and confidential** service which we are proud to offer our clients.

●We want Dateline to be successful for you so take great **CARE** that your requirements are met.

●Dateline is the only national computer dating company to allow you to choose the area you would like your dates to come from.

●Dateline provides the **BEST VALUE FOR MONEY** service, with more people to meet than any other agency.

●Despite having the **LARGEST** membership, Dateline is not just a box number service. You can call at our offices to discuss your membership and to read the thousands of letters from happily matched Dateline members; or telephone us on 01-938 1011. We are always happy to help.

Dateline is a member of the Association of British Introduction Agencies
29 Manchester St., London W1.



Over the years Dateline has been featured many times by press, radio and television and has been acclaimed by many thousands of clients who have found happiness through our services. If you are interested in learning what Britain's largest, longest-established and most successful computer dating service can do for you, complete this coupon and post it today to: Dateline, 23 Abingdon Rd., London W8 6AH.



John Scott and Anne Coburn, Wiltshire — engaged.

Anne found there were scarcely enough nights in the week once she joined Dateline, and just ten weeks later she met John — but she was John's first date. John felt slightly shellshocked when he realised his first date was the one for him. 'Life now is so enjoyable' says Anne. All their friends are very impressed and Anne's sister has now joined Dateline too!

Dateline works — so joining makes sense.



Cindy and Tony Smith — fourteen years on

Cindy and Tony met through Dateline way back in 1970 and have now celebrated fourteen years of 'computer matched marriage'. Cindy at the time was a 28 year old PA with a small son. She was fed up with 'getting involved with men I shouldn't'. Tony was a 33 year old electronics engineer. When they met through Dateline they found they had so much in common. For Cindy and Tony joining Dateline was a recipe for lasting love.

●All couples featured in Dateline advertising are genuine Dateline members who have met through the Dateline service.

FREE

Computer Test to Find Your Ideal Partner

1 START HERE Do you consider yourself:

- | | |
|--|---------------------------------------|
| <input type="checkbox"/> Shy | <input type="checkbox"/> Generous |
| <input type="checkbox"/> Extrovert | <input type="checkbox"/> Outdoor type |
| <input type="checkbox"/> Adventurous | <input type="checkbox"/> Creative |
| <input type="checkbox"/> Family type | <input type="checkbox"/> Practical |
| <input type="checkbox"/> Clothes-conscious | <input type="checkbox"/> Intellectual |

2 Indicate which activities and interests you enjoy by placing a '1' (one) in the appropriate box. If you dislike a particular activity, write a '0' (nought) in the appropriate box. If you have no preference, leave the column blank.

- | | |
|-------------------------------------|--|
| <input type="checkbox"/> Pop music | <input type="checkbox"/> Politics |
| <input type="checkbox"/> Fashion | <input type="checkbox"/> Classical music |
| <input type="checkbox"/> Pubs | <input type="checkbox"/> Art/Literature |
| <input type="checkbox"/> Sport | <input type="checkbox"/> 'Live' theatre |
| <input type="checkbox"/> Pets | <input type="checkbox"/> Science or technology |
| <input type="checkbox"/> Folk music | <input type="checkbox"/> Creative writing/painting |
| <input type="checkbox"/> Jazz | <input type="checkbox"/> Poetry |
| <input type="checkbox"/> Travelling | <input type="checkbox"/> Philosophy/Psychology/Sociology |
| <input type="checkbox"/> Cinema | <input type="checkbox"/> History/Archaeology |
| <input type="checkbox"/> Good food | <input type="checkbox"/> Conversation |

I am over seventeen and would like you to send me completely free and without obligation a description of my ideal partner. Plus a free full colour brochure and lots more information about Dateline. I enclose two first class stamps.

3 Your sexput M or F Your Height ft ins

Your Age yrs. Age you would like to meet Min. Max

Christian Name

Surname

Address

Nationality Religion

Occupation

Send today to:
Dateline, Dept EDT
23/25 Abingdon Rd
London W.8.
01-938 1011

Dateline

CONFIDENTIAL

OSCILLOSCOPES	SPECIAL OFFERS
TELEQUIPMENT D63 Dual Trace 50MHz. Delay Sweep. Large Tube £375	COSSOR OSCILLOSCOPE CDU150. Dual Trace 35MHz Delay Sweep. Solid State Portable 8x10cm Display With Manual NOW ONLY £180ea
TELEQUIPMENT D75 Dual Trace 50MHz. Delay Sweep. With Manual £325	Optional Front Protection Cover Containing 2 Probes & Viewing Hood £10
S.E. LABS SM111 Dual Trace 18MHz Solid State. Portable AC or External DC operation 8x10cm display with Manual £165	SOLARTRON OSCILLOSCOPE CD1400 Dual Beam 15MHz With Manual ONLY £95ea
SCOPEX 4D10A Dual Trace 10MHz. Solid State with Manual £160	AVO VALVE TESTER CT160 Suitcase style. 22 Bases ONLY £25ea (p&p £7)
TELEQUIPMENT D61 Dual Trace 10MHz. With Manual £150	DISK DRIVE PSU 240V 1N. 5V 1.6A & 12V 1.5A out. Size W125mm H75mm. D180mm. Cased Un-used. ONLY £10 (p&p £2)
TELEQUIPMENT D43 Dual Trace 15MHz. With Manual £100	SWITCHED KEYBOARD (as in LYNX MICRO). Push to make Cased. ONLY £/ea (p&p £2)
TELEQUIPMENT S54A Single Trace 10MHz. Solid State With Manual £110	QUERTY MODE PSU +/- 12V 0.25A. 5V 15A etc. £30ea (p&p £3)
PHILIPS PM3200 Single Trace 10MHz £80	DATRON 3000 PROM COPIER (copies up to 10) £150ea (p&p £7)
MULTIMETERS	COMMUNICATION RECEIVERS
AVO 9 Mk4 (Identical to AVO 8 Mk4 but scaled differently) Complete with Batteries & Leads £55	Racal RA17L 500KHz-30MHz ... ONLY £140 each with manual
AVO 8 Mk2 Complete with Batteries & Leads £45	Eddystone 730/4 480KHz-30MHz only £110 each , with manual.
Above items in GOOD WORKING ORDER - appearance not at A1 hence the price.	AVO TRANSISTOR TESTER TT169
VAO TEST SET No 1 (Military version of AVO 8) Complete with Batteries, Leads & Carrying Case £65	Handled. GO/NO GO for in-situ Testing. With batteries, leads & instructions. (p&p £3) NOW ONLY £12
TEST LEADS suitable for AVO METERS Red & Black with 2 croc-clips & 2 prods (p&p £2) £5	ISOLATING TRANSFORMERS 240V INPUT
AVO Model 7x. Complete with Batteries, Leads & carrying case £40	240V Out 500VA £15(p&p £5) 100VA £6(p&p £2)
AVO Model 72 Pocket Multimeter (Analogue) 30 ranges. With Batteries & Leads £10	24V Out 500VA £6(p&p £5) 200VA £4(p&p £4)
ANALOGUE POCKET MULTIMETERS. Philips/Taylor etc. With Batteries & Leads from £10	B + K Precision CRT Restorer/Analyser Model 467. Supplied with 2 bases and Manual. (P&P £7) ONLY £125 each
ADVANCE/BOULD DVMS	LARGEAR Colour Bar Generator KG1. 8 Test Patterns. (P&P £4) ONLY £40 each
Auto ranging; max reading 20,000 AC/DC volts - resistance only £50 p&p £5	BLACK STAR FREQUENCY COUNTERS P&P £4
GENERATORS	Meteor 100 - 100MHz £99
MARCONI TF1066B AM/FM 10-470 MHz £350	Meteor 600 - 600MHz £125
MARCONI TF995A/5 1.5-220 MHz Narrow Deviation £250	Meteor 100 - 1GHz £175
FARNELL SINE/SQUARE type LFM2 1Hz-1MHz Compact £80	BLACK STAR JUPITOR 500 FUNCTION GENERATOR Sine/Square/Triangle. 0.1Hz - 500KHz. P&P £4 £110
ADVANCE SG62B AM 150KHz-220MHz £45	BLACK STAR ORION. PAL TV/VIDEO COLOUR PATTERN GENERATOR £199
Many others available	HUNG CHANG DMM 7030. 3 1/2 digit. Hand held 28 ranges including 10 Amp AC/DC 0.1%. Complete with Battery and Leads P&P £4 £39.50
STEPPING MOTORS	As above DMM6010 0.25% £33.50
Type 1 200 Steps per rev. 4 Phase (5 wire) 12 24V Torque 25oz inch will run on 5V with reduced torque. £15 ea	OSCILLOSCOPES PROBES. Switched x1: x10. P&P £2 £11
Type 2 6/12 Steps per rev. 3 Phase. 12/24V (will work on 5V) £2 ea 5 off £7.50	
Type 3 NORTH AMERICAN PHILIPS 24 Steps per rev. 4 wire 5V 3Amps 0.250rpm £6 ea	
Used equipment - with 30 days guarantee. Manuals supplied if possible.	
This is a VERY SMALL SAMPLE OF STOCK. SAE or Telephone for Lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to Total of Goods & Carriage.	
STEWART OF READING	
110 WYKEHAM ROAD, READING, BERKS RG6 1PL	
Telephone: 0734 68041 Callers welcome 9 am - 5.30 pm Mon.-Fri. (until 8 pm Thurs.)	

NEW! from **Cirkit**

SUMMER 1987 ELECTRONIC CONSTRUCTORS CATALOGUE





6
MULTIMETERS
TO BE WON

- Many new lines
- Extended range of test equipment

PRICE ONLY **£1.20**

- £11 worth of discount vouchers
- 6 Multimeters to be won in easy to enter competition.
- Available at your local newsagent or direct from address below.




(0992) 444111

Cirkit Distribution Ltd Park Lane, Broxbourne, Herts EN10 7NQ
Telephone: (0992) 444111 Telex: 22478

Zenith Electronics. ©

Kits - Modules - Hardware

YOU KNOW US FOR OUR TRANSMITTER KITS—NOW
TAKE A LOOK AT OUR GROWING RANGE OF
QUALITY KITS AND READY-BUILT PROJECTS:
MODULES AND ELECTRONIC HARDWARE

The following are examples of our proven product designs in kit form:

- ★ Miniature FM Transmitter; 60-145MHz. Kit £6.95; R/Built £8.95.
- ★ 3 Watt FM Transmitter, 80-108MHz. Kit £13.99; R/Built £18.99.
- ★ 10 Channel Variable Speed Running Light; Drives LEDs or mains lamps. Kit £14.97.
- ★ 3 Note Electronic Door Chime unit; 9 volt operation, 3 melodious tones; variable frequency. Kit £9.83.
- ★ 300 Watt Light Dimmer unit for 240 volt mains lights. Kit £6.95
- ★ 5 Code Digital Code unit plus Key Pad—select own code; 9 volt. Kit £14.21.
- ★ 5-100 Watt Electronic Loudspeaker Overload Protector, adjustable. Kit £11.11.
- ★ VU Meter 10 LED indicator; -5 to +12dB range. Kit £12.59.
- ★ Automatic light controller; automatically turns on and off lights at pre-set times and triggered by darkness. Kit £25.08.
- ★ Mains Wiring and Metal Detector; complete with case. £11.00
- ★ Digital Clock module; 12-24 hour timing; LED type—£17.49, or LCD type—£22.80.
- ★ Amplifier Power Meter; 10 LED indicator from 0-25-100 Watt Input—9 volt operation. Kit £9.52.
- ★ Light sensitive relay unit; variable sensitivity trigger control; senses light or dark—selectable. Kit £8.45.

ALL KITS CONTAIN FULL INSTRUCTIONS. P.C.B.s AND COMPONENTS.

ALL PRICES INCLUDE VAT AND POSTAGE & PACKING.


OVERSEAS ORDERS—ADD 10% TO ABOVE PRICES.

PLEASE SEND CHEQUE OR POSTAL ORDERS WITH ORDER.

S.A.E. For
FREE
Data Pack

Zenith Electronics, 14 Cortlandt Business Centre,
Hailsham, E. Sussex, U.K. BN27 1AE.
Tel: 0323 847973 Dept 2.

AUDIOKITS PRECISION COMPONENTS




The ETI VIRTUOSO PREAMP
(featured ETI July-Sept & Nov 86)

THE TRUE ENTHUSIASTS PREAMP

- ★ Superlative sonic performance
- ★ Versatile case with space for mods, other circuit designs etc.
- ★ MC stage, upgraded, uses transistors of lowest noise currently available.
- ★ Two stage MM circuit with passive RIAA equalisation.
- ★ High performance optional tone stage.
- ★ Circuits and pcbs can easily be adapted for other audio uses, low noise mic preamps, active crossovers, filters, balanced/unbalanced amps, mixers etc.
- ★ High performance power supply board with up to 4 positive and 4 negative regulated outputs - ideal for many other audio projects.
- ★ All components incl. case & pcbs available separately.
- ★ Complete kits cost a fraction of similar quality ready built preamps, saving hundreds of pounds.

For details, please send 9" x 4" SAE (overseas 3 IRCs) to:

AUDIOKITS
6, Mill Close, Borrowash, Derby DE7 3GU
Tel: 0332-674929



RED CURRY

Helen Armstrong finds Chris Curry striving to get back in control.

Chris Curry was in the boardroom of General Information Systems wielding what looked like a twig covered in withered leaves. I remarked the plant did not look well. "On the contrary," Curry announced. "It's getting a chance to procreate". He shook a peppering of seeds from the dried pods into a used envelope, and handed the packet to an assistant with instructions to file it. Chris Curry, former Sinclair collaborator and leading light of Acorn, is still planting for the future.

When Acorn was losing money like a leaky sieve in the race for the cut price micro market and was bought out by Olivetti, co-founder Curry was free to try out a different line of enquiry which had attracted him even before the development of Acorn. He formed General Information Systems (GIS) and with a team of about a dozen people, many former Acorn colleagues, set out to develop and market microprocessor-controlled devices whose application was specific and practical.

Early Days

"When I was first selling microcomputer systems," says Curry, "it was before the micro boom and we were selling to people like ETI readers who already had an interest in technology. I was always asked 'what can I do with it?' This is the most difficult question in the world to answer. If I'd relied on market research, for instance, it would have shown there was no point trying to sell computers because there was no market! Fortunately, we don't all work by market research.

"Today the answer to that question is 'control, timing, energy management, word processing and desk diary'. Interactive control in the home was always talked about but never really achieved except by a few enthusiastic amateurs."

Curry's latest offspring are Red Boxes. Apart from their fire engine colour, Red Boxes could be a cryptic breed of distribution board. They plug into and operate down standard mains wiring and some of them double as mains outlets, but their real task is control.

The first generation of Red Boxes are marketed as add-ons for already popular home micros (BBC micro, Spectrum and Commodore 64) in the form of a £133 starter pack with a control module, a 13A switched outlet and a heat-sensitive movement detector. These are known respectively as Red Leader, Red One and Red Two. "Second World War RAF flying jargon," explains Curry.

Red Leader contains its own 6502 processor, ROM, RAM and modem. "The unit itself detects which computer it is connected to and downloads an appropriate terminal program to the micro. Once programmed, it is no longer dependent on the outside computer, which can be disconnected.

"Anybody with a home computer already has an advantage," says Curry. They are familiar with keyboard interfaces. There are three million micros out there — mostly Sinclairs, some BBCs and

Commodores — which are mostly not being used. A machine which makes them useful again is good in a number of ways. Seeing a computer doing something practical, like switching, has great appeal and putting a discarded machine back into use is highly satisfying."

In The Future

That assumes centralised microprocessor control will be commonplace in the future. Few people have a clear idea of what they want from it in the home. The old question is still being asked: what do we do with it? "At the moment," maintains Curry, "the answers are energy management, security alarms, or simply automating — like an intelligent timer, but without fiddling with the mains wiring. It's interesting to notice home security systems are being installed at a rate of knots but they are inflexible. A floodlight is a good deterrent, but only at night. During the day something different (such as a siren) could automatically replace it on the same sensing and timing information. A system which expects different things at different times of the day or year would be even more useful." A siren (inevitably christened Red Alert) is on the way.

"The next really important step will be a modem which allows you to phone in and bleep the system to alter settings down the line. It will work both ways. It'll also phone you and indicate if it has received certain readings. No, it won't speak — we aren't using voice synthesisers yet! This is particularly important, because people like to be able to change the system remotely."

With the general extension of remote control into all areas of domestic and business life, the inviolability of these personalised systems has been an important consideration.

Interference

Potential problems of interference between two systems working on the same ring main, and the more sinister threat of accidental or deliberate data trespass by outside mischief-makers has been forestalled by allocating an incredibly complex address code to each box.

"Anyone trying to break in would have a devil of a time. The data is encrypted in a number of ways. First, there is the large address. Secondly, when the data is sent out it is jumbled with an encryption with a key which is unique to that package of data. Even if they recorded the signal and tried to read it with an oscilloscope, it would remain jumbled. This is unique among mains borne comms systems."

As they stand, Red Boxes are aimed at micro owners. Programming experience is not required, but it helps. "The system has high programmability at the moment. Red Basic is a bit like BBC Basic with extensions and there is a complete guide to Red Basic in the Basic manual for those who want to get to know the system inside out."

Eventually there will be a Red Box which is not connected to a computer, with a simple single-line

display, a few buttons, and limited programming possibilities. Even so, will homes be a flourishing market for computer-based hardware in the immediate future? Curry's attitude is that although it is early days, his boxes have other outlets.

"You could divide Red Boxes into two concepts. On the one hand it is a mains modem, which actually allows you to send digital information along the mains wiring. On the other hand, it is quite a sophisticated communications protocol for point to point serial transmission of data, with a quite powerful control language to go with it. If you put the two things together there are some interesting industrial applications. I don't have any concrete examples to offer you because the product is too new but at exhibitions a lot of energy management engineers have been showing interest. Security people too. Even in a house, it costs from £500 to £1,000 to have a fairly simple system wired in."

"These are devices which people can build applications around, enabling devices for all kinds of purposes. People have the opportunity to use their imaginations.

Communication

General Information Services, says Curry, was set up to develop the processing of information and the use of computers in information technology. "Computers will be used more frequently for communications than anything else but the information to be carried is not yet available in the quality and quantity needed for the market."

With their other main project, the Communicator, GIS is looking at ways of introducing a desktop computer which is essentially a remote database terminal with local data manipulation facilities, built in modem and automatic telephony. It can receive Teletext and, with a small modification, Datacast, and can be built into a local area network. "This Communicator was developed by Acorn and they are still marketing it. It's only available to OEMs at the moment. GIS has the rights to it and we are still working on creating the necessary information base to launch our version. It is a long process, providing a systems house role if you like. We are presenting the hardware with the software, not just the systems software but material people are actually in need of, the raw information.

"We are hoping to appeal to the top end of the consumer market, in which case the software must be available as part of the machine. When the Communicator is ready, it must be absolutely straightforward to extract information. You should be able to feed a demand into the computer, and it will search for the database and do the rest. It must be capable of reprocessing the data, of extracting the exact details or figures you want and giving a printout that you don't have to analyse further. It has half a megabyte of storage — it's not just a dumb terminal."

So what is it that appeals to him personally? Developing new ideas, or developing the company as a whole?

"Success. Whether it's a successful product or a successful company. Both, preferably. The pleasure of seeing something well received, and the added pleasure of seeing it make a profit for the company. I think the two go together. In a small company, which GIS is, if you're not very close to the conceptual development of a product then you are not close to the company. I'm also very close to the corporate development and strategy of the company. I make no claims to be close to the technical development of



the products — there are people much better than me to look after that. But no matter how clever the technology is, if the concept is wrong, the product fails, and vice versa, of course."

"There are lots of really clever products that have failed because they weren't marketed properly. The development of a company is an expensive gamble. If you don't get the market and the product right, you will lose a lot of money.

"Having said that, there are a lot of independent commercial organisations these days where people with an idea can go to get support, without laying out a lot of money. They can get a bit of market research done, or management advice on how best to produce and market the product. That type of support didn't exist a few years ago. People ought to take full advantage of it, while being careful not to be taken advantage of. Some provide venture capital as well, but I think one should try to separate venture capital from management services. Some sources of capital are offshoots of banks, who probably know less about the management problems of a small company than the inventor of the idea!

"But if you are looking for ongoing management support, it is very important to remember that you must have a good, personal working relationship with any partners. People with ideas don't like being interfered with. Unfortunately, there are no set rules. You can't separate being the boffin from running the business in a small company.

"I'm a great believer in working back from the market's needs. You have to try and imagine what the customer will want and work back to the product without detracting from the craft. As the developer of a product, you are leading the customers. If you ask them what they want, they won't know. It's only when they see it they can make a decision. We have to use our imaginations to show people the possibilities open to them. But if the product isn't right, they won't have it however clever it is."

NUCLEAR STRATEGY SIMULATOR

Deterrence is dead, the victim of precisely-targetted Cruise and Trident missiles. So says David Guinness and he sets out to prove it with the aid of a map and a little logic.

Most of us have got used to thinking of nuclear weapons as a simple deterrent: if they launch theirs against us, we'll launch ours back at them. That way, everyone loses so it is in both our interests not to fire first.

This concept of Mutually Assured Destruction (MAD) is out of date in the view of many people. It relied on the fact that missiles were not terribly accurate and a large number would have to be launched against an enemy to ensure complete destruction of important targets. Such an attack could be detected with relative ease long before any missiles arrived, giving the enemy plenty of time to launch their own missiles in response.

Now we have highly accurate weapons such as Cruise and Trident, many of which can fly at low altitude so that they are very difficult to detect until shortly before they hit their target. With this sort of accuracy, missiles can be directed at enemy missile silos and have a good chance of destroying them before the missiles can be launched in return.

The result is a complete reversal of deterrence theory. When it is possible to destroy enemy missiles with little risk to oneself, the best means of defence is to fire first. You may not get enough warning to fire second.

This view is inevitably controversial. Governments don't want to give away a possible advantage so they certainly won't announce that they have a first strike capability in these terms. Indeed, most refuse to concede

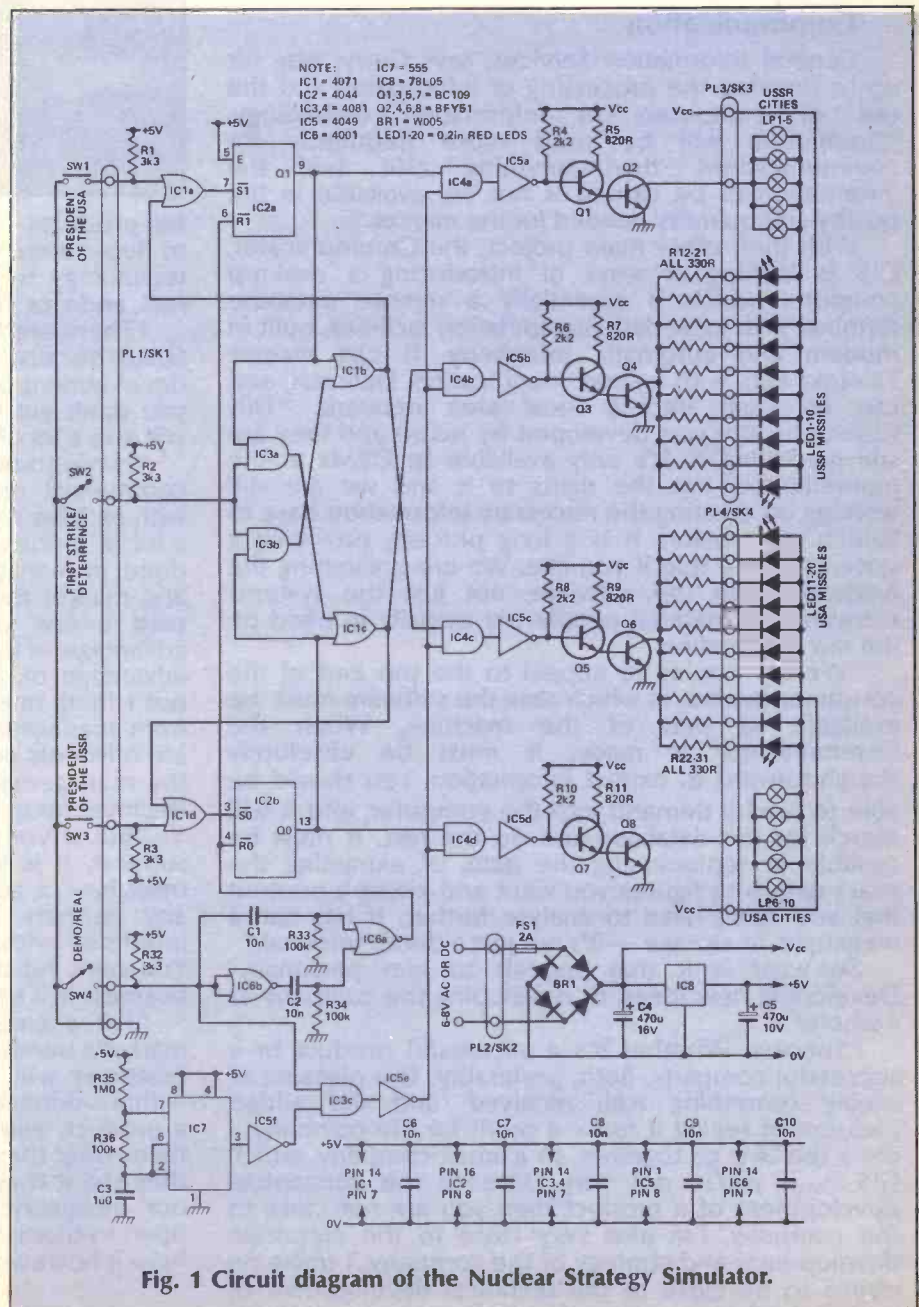


Fig. 1 Circuit diagram of the Nuclear Strategy Simulator.

HOW IT WORKS

With SW2 closed and SW4 open, the Nuclear Strategy Simulator is set to the DEMO and DETERRENCE modes. One input of IC1a and IC1d will be held high and a logic high will appear on the inputs to the two latches (IC2a and b). These inputs are active low so outputs Q₁ and Q₂ will not latch.

When SW1 is pressed the previously high input to IC1a is pulled low and a low output level is passed to pin 7 of IC2. The output from pin 9 will go high and remain latched in this state when SW1 is released.

The high level output from the latch is combined in AND gate IC4a with the signal from IC7 and its associated circuitry. IC7 is a 555 timer which generates a low-frequency (roughly 1Hz) square wave. This output is passed via IC3c and IC5e to IC4a and produces a square wave output which drives Q1/Q2 and causes LP1-5 to flash steadily on and off. These lamps represent USSR cities.

The high level on IC2 pin 9 is also passed to IC1b whose output in turn feeds IC4c. The other input of IC4c receives the square wave output from the oscillator circuitry so the output of this gate will also be a square wave. This is passed via IC5d to Q5/Q6 and causes LEDs 11-20 to flash. These LEDs represent USA missiles.

When SW4 is set to the REAL position, IC3c receives a low on one of its inputs. This stops the oscillator output being passed to the rest of the circuitry. Instead, the output of IC3c goes low and is inverted by IC5e so as to provide a high level on the inputs of the four AND gates, IC4a-d. Pressing SW1 or SW3 now causes one output of IC2 to latch as before and produces a high level on the other input of two AND gates. The resulting high output level is inverted by the buffers IC5a and c or IC5b and d to provide a low level into the transistor pairs. Pressing one of the buttons in the REAL mode therefore

causes one set of missile lights and the opposite set of city lights to go out completely.

Moving SW4 from DEMO to REAL also puts a low level on the input of IC6b and a short high level pulse emerges from the differentiating network, C2/R34. This is inverted by IC6a to form a short, low-level pulse into the active-low reset inputs of IC2. Moving SW4 back to DEMO sends a high level to the other differentiating network, C1/R33, producing a short high level pulse which is again inverted by IC6a. In this way the two latches are reset every time SW4 is operated.

Opening SW2 transfers the simulator from DETERRENCE to FIRST STRIKE mode. R2 pulls up one input on each of the two AND gates, IC3a and b. If SW1 is pressed now, the resulting high on the output of latch IC2a will take the other input of IC3a high and place a high level on one input of the OR gate, IC1c, causing its output to go high as well.

The output of IC1c feeds one input of OR gate IC1d which drives the input of latch IC2b. This high level will prevent the active-low input of IC2b being triggered. In this way, pressing SW1 first prevents SW3 being used and vice versa.

The output of IC1c also feeds the AND gate IC4b, the other input of which receives the square wave output from the oscillator circuitry. This signal will be passed to inverter IC5b and the transistor pair Q2/Q3, causing LEDs 1-10 to flash. These LEDs represent USSR missiles.

LEDs 11-20 (representing USA missiles) and LP1-5 (representing USSR cities) will also flash, having been enabled in the normal way by the high output on latch IC2a. The difference between DETERRENCE and FIRST STRIKE modes is in the addition of the extra set of flashing LEDs.

Just as in the DETERRENCE mode, moving from DEMO to REAL in the FIRST STRIKE mode removes the flashing oscillator from the circuit.

The missile lights go out once the missiles have been fired and the city lights go out when the cities have been destroyed.

In the second mode (FIRST STRIKE) the missiles on each side are assumed to be accurate enough to destroy enemy missile sites as well as cities. Firing either set of missiles now causes all the lights on the opposite side to go out and prevents the enemy mounting a return attack.

A DEMO mode allows missiles which have been fired and cities which have been destroyed to flash rather than go out. This is helpful while the rules are being explained to players.

Construction

All the main circuitry is carried on one printed circuit board which mounts on the back of the map board. The lamps, LEDs and switches are mounted directly through the map board and wired with ribbon cable to three sockets on the PCB.

The only item not mounted on the back of the board is the transformer which will be required for mains operation. This is housed in a separate earthed metal box and only the low-voltage output taken to the Simulator.

The board as it stands is designed to operate from a 6-8V supply, AC or DC. If preferred, the values of the LED series resistors (R12-31) can be altered to allow the Simulator to run from a 12V AC or DC supply such as a car battery. The filament lamps would also need to be changed from 6V to 12V for this. Decide before proceeding which voltage you want the Simulator to run from and select the appropriate resistor values (330R for 6-8V operation, 510R for 12V operation).

The PCB component layout is shown in Fig. 2. Begin assembly by installing the connectors, the fuseholder and the IC sockets (if you plan to use them). The fuseholder has a screw-cap on one end and should be positioned so that this overhangs the side of the board. Insert the resistors and capacitors next and then the transistors. Last of all, solder the ICs into place or install them in their sockets.

The board can be tested by connecting it to a 6V battery or a suitable power supply (you won't need a large battery at this stage because the board draws very little current without the lamps and LEDs). Connect the supply to


that such a scenario is militarily feasible and continue to talk in terms of nuclear deterrence.

Because of this, we have no firm idea just when either of the superpowers is likely to achieve full first strike capability. Estimates for the USA range from 1992 (put forward by Robert Alridge in his book *First Strike*) to as close as 1988 (according to the book *Death Of Deterrence*). Even the most optimistic independent sources expect the change to take place before 1995. There are fewer estimates regarding progress in the USSR because less information is available but given their oft-stated intention to match US capabilities it is unlikely they will be more than a few years behind.

The Nuclear Strategy Simulator

described here is a simple demonstration unit which allows the concepts of deterrence and first strike to be explored in the form of a game. One player (or a group of players) takes the part of America while the other is Russia. Both have cities to protect (represented by white lamps on a large map) and both have missiles they can fire at the enemy (represented by red LEDs on the map).

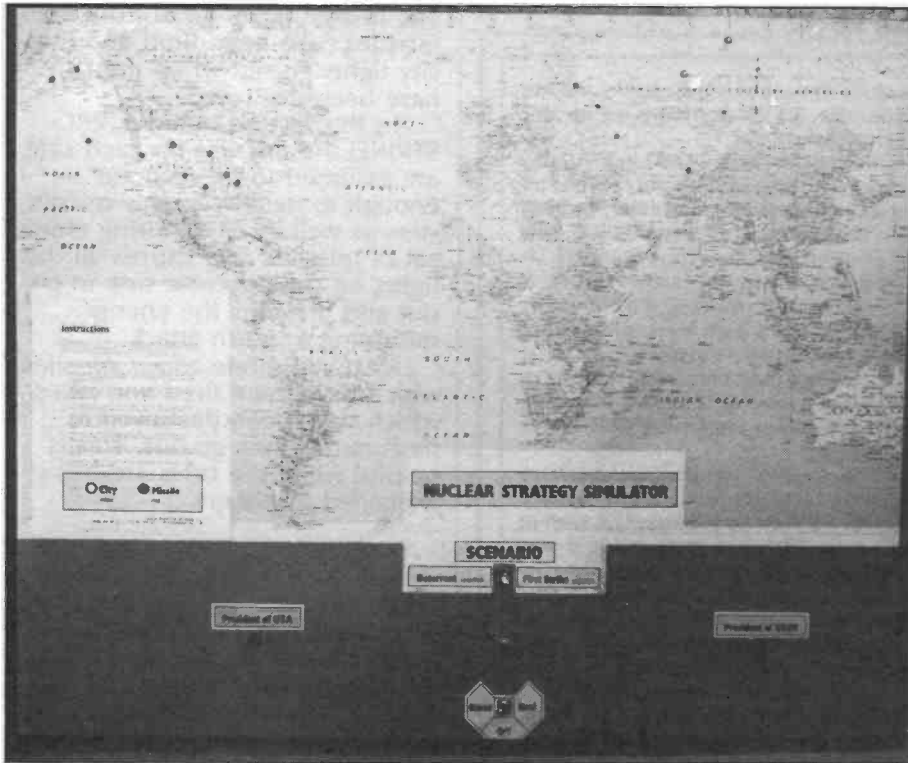The Simulator has two very simple modes of operation. In DETERRENCE mode, the missiles are assumed to be fairly inaccurate on both sides and therefore threaten only the enemies' cities. Firing one set of missiles destroys the opponents' cities but leaves them with missiles which they can fire back.



SK2 and leave plugs PL1, 3 and 4 empty. Assuming nothing nasty happens at switch on, connect one of the 6V bulbs between V_{cc} and the collectors of Q2, Q4, Q6 and Q8 in turn. The bulb should light in each case.

If all seems well, take a piece of wire and briefly short it between 0V and the 'TO SW1' connection of PL1. Go back and check the collectors of the four output transistors again. You should find that the bulb lights up when connected to Q8 but flashes when connected to Q2, 4 or 6.

The next stage is to stick the map firmly to its backing board. When complete, it is a good idea to protect the edges of the map and board with tape or edging strip.

Refer to Fig. 3 and drill the holes for the LEDs and filament lamps. Drill the holes from the front of the board and take care not to rip the map.

Drill a further set of holes for the switches, one directly above the other in the lower middle part of the board and one at each side directly below America and the USSR.

The PCB is attached to the back of the board using wood-screws and spacers and the LEDs, lamps and switches are wired using ribbon cable. The LEDs and lamps representing American missiles and cities are wired to one piece of 12-way cable, the LEDs and lamps on the USSR side

are wired to another 12-way cable and the four switches are wired to a 6-way ribbon cable.

The wiring of the lights and switches should be obvious from the circuit diagram and component overlay. Each LED has its own resistor on the PCB so ten of the twelve ways on each of the larger connectors are for the LEDs. The remaining connections are a common 0V lead for the five lamps and a common V_{cc} connection for both the lamps and the LEDs. The only point to watch is that the LEDs must, of course, be wired the right way round.

If you intend using the Simulator from a mains supply, a transformer unit will be needed. This should consist of a metal box with a suitable transformer firmly fixed inside it. The box should be earthed and all the usual care must be taken with the mains input lead and wiring. Use a strain relief bush and include a fuse in the mains circuit.

In Use

The Simulator can be used by any number of people from two upwards. Provided clear instructions are printed in a prominent position, it can be left unattended

PARTS LIST

RESISTORS (all 1/4W)			
R1, 2, 3, 32	3k3		
R4, 6, 8, 10	2k2		
R5, 7, 9, 11	802R		
R12-31	330R (or 510R — see text)		
R33, 34, 36	100k		
R35	1M0		
CAPACITORS			
C1, 2, 6	10n		
C3	1u0 35V tantalum		
C4	470u 16V axial electrolytic		
C5	470u 10V axial electrolytic		
SEMICONDUCTORS			
IC1	4071		
IC2	4044		
IC3, 4	4081		
IC5	4049		
IC6	4001		
IC7	555		
IC8	78L05		
Q1, 3, 5, 7	BC109		
Q2, 4, 6, 8	BFY51		
LED1-20	0.2" red LEDs, preferably high intensity types		
BR1	S005 bridge rectifier		
MISCELLANEOUS			
FS1	2A 20mm fuse and PCB-mounting holder (fully enclosed type with screw-on end cap — see Buylines)		
LP1-10	6V 60mA wire-ended filament lamps (or 12V 60mA — see text)		
PL1	6-way 0.1" PCB plug		
PL2	2.1mm DC power plug		
PL3, 4	12-way 0.1" PCB plug		
SK1	6-way 0.1" insulation displacement connector		
SK2	2.1mm DC power socket, PCB-mounting		
SK3, 4	12-way 0.1" insulation displacement connector		
SW1, 3	non-latching, push-to-make switch		
SW2,4	SPST toggle switch with long shank		
	PCB; world map; backing board; wood-screws and spacers to mount PCB; ribbon cable, 5-way and 12-way; IC sockets (optional), 1 x 8 pin, 4 x 14 pin, 2 x 16 pin; connecting wire; tape, glue, etc.		
	Optional mains transformer unit: chassis-mounting mains transformer with 6-8V output rated at 2A or more (eg., RS/Electromail 207-504 giving 6V at 3.3A); metal case; fuseholder and 1A fuse; cable strain-relief bushes; 3-core mains cable and 2-core low voltage cable; nuts, bolts, etc for transformer mounting.		

and people approaching it will work out for themselves what to do. This makes it ideal for use in libraries, in the foyer at conference centres or in any other position where people are passing by.

Where larger groups are expected it is helpful if someone is around to demonstrate the Simulator and explain its significance. In this case, the people present should be divided into two groups ('Russians' and 'Americans'), each of which selects a 'President' to operate the button.

Start with the Simulator set to DEMO and DETERRENCE so that all the lights are on. Explain to the players that the red lights represent missiles and the white lights represent cities. Get one of them to press their button so that one set of missiles and the opposite set of cities start flashing. This represents one superpower using its missiles to threaten the cities on the other side.

Now tell the other side to press their button and show that they can return the threat, causing their missiles and their opponents' cities to flash. Thus either side can launch an attack

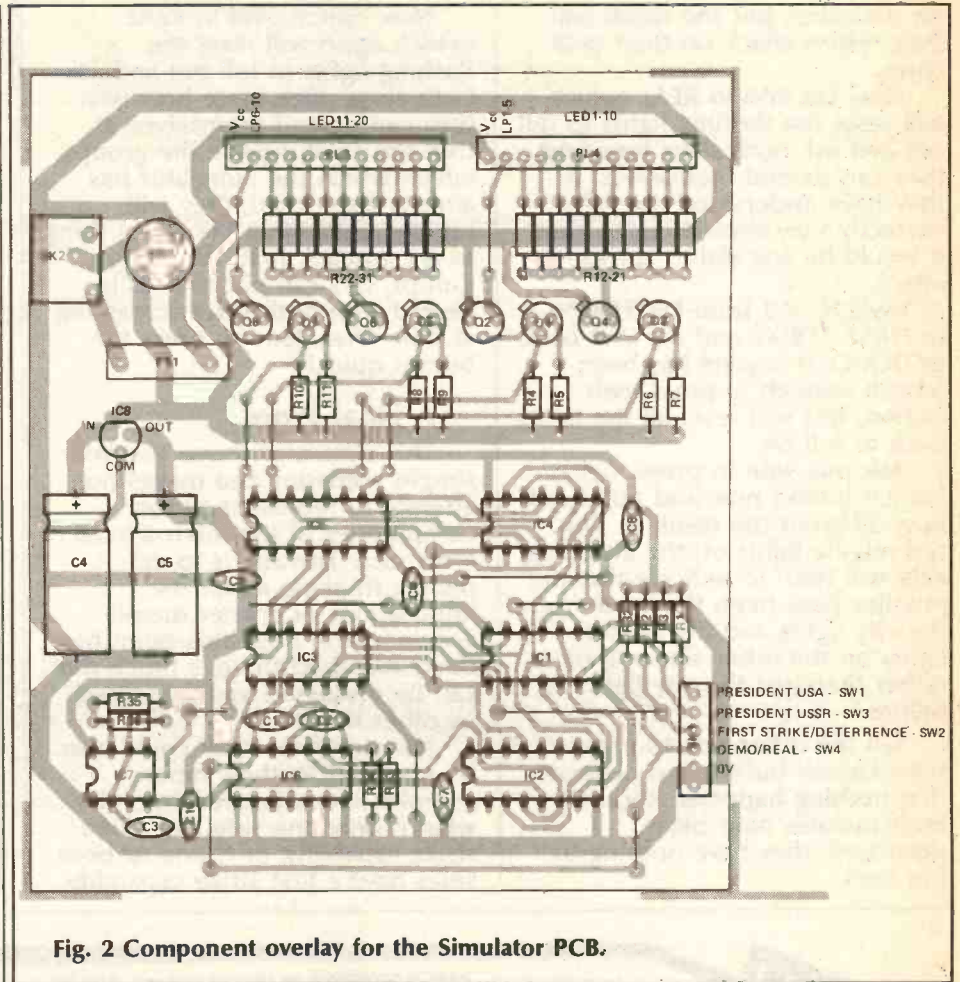


Fig. 2 Component overlay for the Simulator PCB.

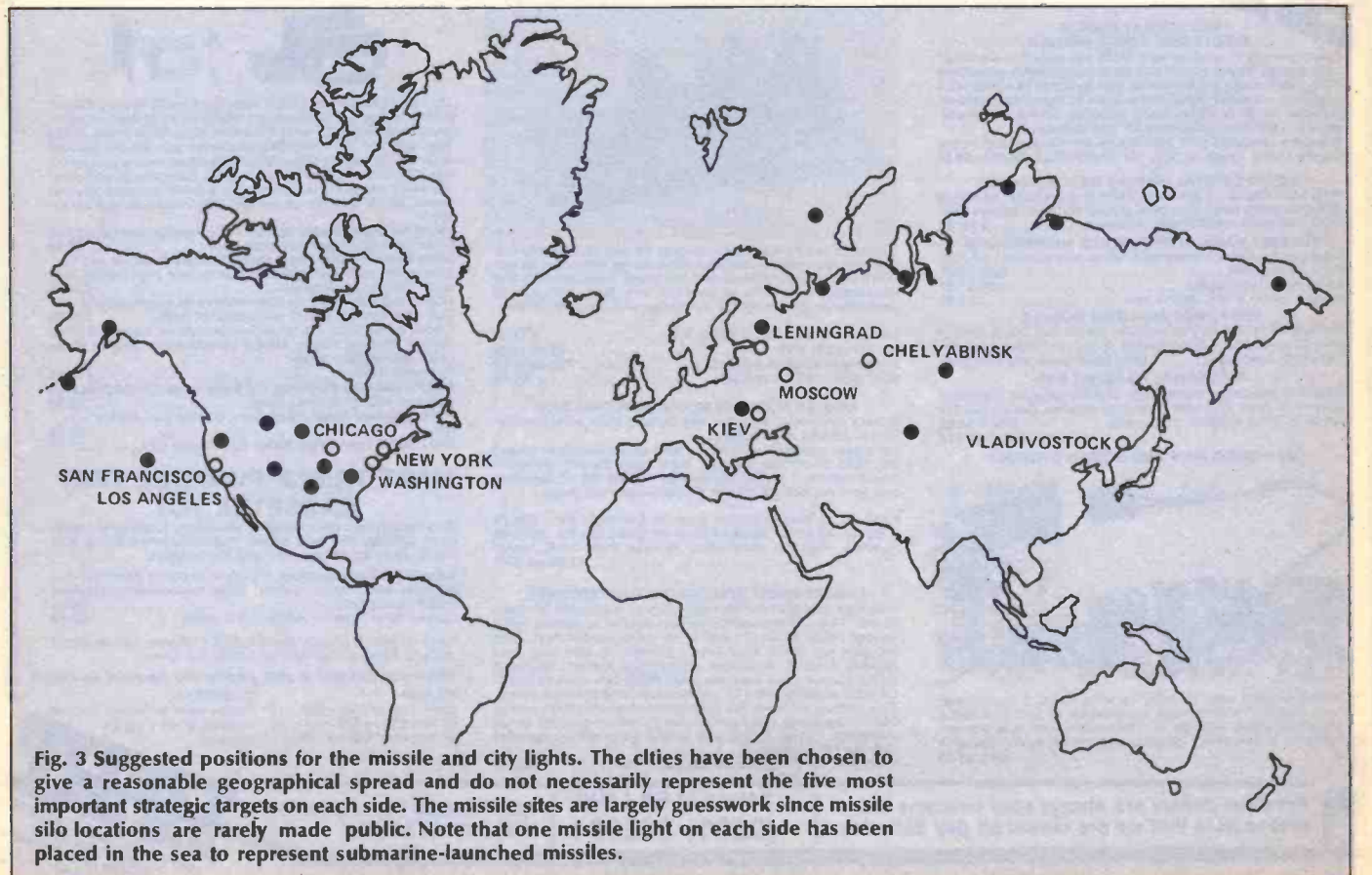


Fig. 3 Suggested positions for the missile and city lights. The cities have been chosen to give a reasonable geographical spread and do not necessarily represent the five most important strategic targets on each side. The missile sites are largely guesswork since missile silo locations are rarely made public. Note that one missile light on each side has been placed in the sea to represent submarine-launched missiles.

on the other, but the result will be a return attack on their own cities.

Now set SW4 to REAL (which will reset the flashing lights to full on) and ask both sides how best they can defend themselves. If they have understood the rules correctly they should realise that it would be suicidal to launch an attack.

Switch SW2 from DETERRENCE to FIRST STRIKE and set SW4 back to DEMO. If anyone has been foolish enough to press their button, this will reset all the lights back to full on.

Ask one side to press their launch button now and point out how different the result is. The red missile lights on the attacking side will flash to indicate that the missiles have been fired, but both the city lights and the missile lights on the other side will flash rather than just the city lights as before.

Tell the other side to press their launch button and observe that nothing happens. Because their missiles have been destroyed, they have nothing to fire back.

Now switch SW4 to REAL (which again will reset the flashing lights to full on) and ask both sides once more how best they can defend themselves. If they are anything like the groups which the Simulator has already been tried, they will rapidly realise that the safest thing to do is attack first. With large groups, this can become quite heated with both sides screaming at their 'President' to press the button quickly.

A Final Word

This simulator shows two very simple scenarios and makes no attempt to represent all the complexities of the international arms race. The aim is to get people thinking about the implications of greater missile accuracy, and once this point has been absorbed there is much that can be discussed and presented by other means.

The simulator itself could also be modified to show more complex scenarios. For example, what if only one side has a first strike capability, or if one or both sides have a first strike capability


which does not destroy all of their opponents' missiles? What if Star-Wars technology is added to the equation on one or both sides, allowing any missiles not destroyed by a first strike to be wiped out before reaching their targets? This makes a first strike even, more tempting.

ETI

BUYLINES

Most of the components for this project are readily available from the usual mail-order suppliers. The 6V wire ended-lamps and the fuseholder came from RS/Electromail (order codes 587-069 and 413-147) and the six and twelve-way PCB connectors came from Maplin. The S005 rectifier was also obtained from Maplin but other 2A, 50V bridge rectifiers should do just as well. Push-button switches with long shanks for SW1 and SW3 are easy enough to obtain but you may have more difficulty with long-shank toggle switches. The ones used on the prototype came from a surplus store.

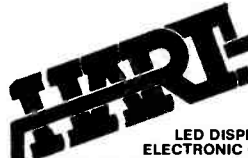World maps can be purchased from local booksellers or stationery stores. The one used on the prototype was a 48 x 26in 'Pioneer' map from the London Map Centre, Caxton Street, London SW1.



LED DISPLAY DIGITAL ELECTRONIC CLOCK MODULE

Electronic clock module with MOS LSI circuit, 4-digit 0.5" LED display, power supply and other components on a single PCB. Only needs a transformer and switches to construct a complete pretested digital clock/timer for many applications. Suitable for 50 or 60 Hz mains supplies. Direct (non-multiplexed) LED drive eliminates RF interference. Supplied complete with 240v mains transformer and wiring diagram/data. Order as SOL 144 Alarm Clock Module £6.85

LIQUID CRYSTAL DISPLAY WATCH MODULE

With LCD display, 2 pieces of Polarising material, backlight diffuser, micro lamp, precision crystal, trimmer, battery contacts and open microcircuit. Untested 5 for £1

PLESSEY MAINS INTERFERENCE SUPPRESSORS

Filter unit for mains borne interference. Max current 1.5A. Our Price, brand new only £2.27
Same item, store soiled only £1.61
Similar Unit but 10A. Brand new £3.49


10W POWER AMPLIFIER MODULE

Mullard LP1173 Amplifier module. Needs 24v DC Supply to give 10 watts into 4 ohm speaker. Size 112x70x29mm. Complete with heat sink Only £2.40 complete with Data

ALPS FF317U FM FRONT END

Beautiful precision made High Quality variable capacitor tuned FM Front End with Dual-gate MosFet. Covers full FM range of 87 to 109MHz. 12v supply ONLY £8.90
Circuit if required 35p


CAR RADIO FM IF AND STEREO DECODER

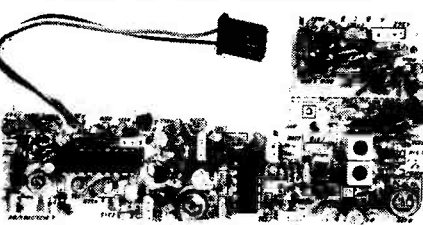

Miniature PCB with 10.7MHz ceramic filters, 2-transformer ratio detector, AX010 noise suppression IC and TCA4500A advanced stereo decoder IC. Only needs front end to make FM tuner or car radio. Complete with circuit. Incredible value at Only £1.99

HART ELECTRONICS are specialist producers of kits for designs by JOHN LINSLEY-HOOD. All kits are APPROVED by the designer.

LINSLEY-HOOD CASSETTE RECORDER CIRCUITS

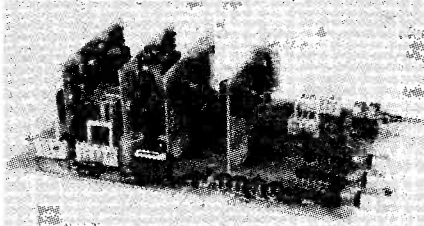

Complete record and replay circuits for very high quality low noise stereo cassette recorder. Circuits are optimised for our HS16 Super Quality Sendust Alloy Head. Switched bias and equalisation to cater for chrome and ferric tapes. Very easy to assemble on plug-in PCBs. Complete with full instructions.

Complete Stereo Record/Play Kit £33.70
VU Meters to suit £2.30 each
Reprints of original Articles 75p no VAT
860X Stereo Mic Amplifier £8.70

LINSLEY HOOD 300 SERIES AMPLIFIER KITS

Superb integrated amplifier kits derived from John Linsley-Hoods articles in 'Hi-Fi News'. Ultra easy assembly and set-up with sound quality to please the most discerning listener. Ideal basis for any domestic sound system if quality matters to you. Buy the kit complete and save pounds off the individual component price.

K300-35. 35 Watt Discount price for Complete Kit £98.79
K300-45. 45 Watt. Discount price for Complete Kit £102.36
RLH4&5. Reprints of Original Articles from 'Hi-Fi News' £1.05 no VAT

LINSLEY-HOOD SYNCHRODYNE AM RECEIVER

Very high quality kit for this recent design featured in 'Wireless World'. This unit represents the first attempt to make a much needed HIGH QUALITY AM Tuner since pre-FM days. This will give you Radio 4, or even 1 in better quality than your Eastern 'Tranny'. Advanced construction system, approved by the Author, uses 3 double sided PCBs in a stacked layout for total stability, ease of construction and minimal wiring. This module will form the AM section of an ultra high quality AM/FM switched bandwidth tuner to match our 300 series amplifiers. Power supply and tuning gang will be included with the FM section.
K450 JHL Synchrodyne Kit Special Price £59.95

HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do your tapes lack treble? A worn head could be the problem. Fitting one of our replacement heads could restore performance to better than new! Standard mountings make fitting easy and our TC1 Test Cassette helps you set the azimuth spot-on. We are the actual importers which means you get the benefit of lower prices for prime parts. Compare us with other suppliers and see! The following is a list of our most popular heads, all are suitable for use on Dolby machines and are ex-stock.

HC20 Permalloy Stereo Head. This is the standard head fitted as original equipment on most decks £7.66
HS16 Sendust Alloy Super Head. The best head we can find. Longer life than Permalloy, higher output than Ferrite. Fantastic frequency response £14.86
HQ551 4-Track Head for auto-reverse or quadrophonic use. Full specification record and playback head £14.60
Please consult our list for technical data on these and other Special Purpose Heads. MA481 Latest version Double Mono (2/2) Record/Play head £13.35
Replaces R484 £13.35
SM166 Standard Mounting 2/2 Erase head. Compatible with above or HQ551 4-Track Head £8.85
H524 Standard Erase Head. Semi double gap, high efficiency £2.25
H561 Metal Tape Erase Head. Full double gap £7.35

HART TRIPLE-PURPOSE TEST CASSETTE TC1

One inexpensive test cassette enables you to set up VU level, head azimuth and tape speed. Invaluable when fitting new heads. Only £4.66 plus VAT and 50p postage

Tape Head De-magnetiser. Handy size mains operated unit prevents build up of residual head magnetisation causing noise on playback £4.54
Curved Pole Type for inaccessible heads £4.85

Send for your free copy of our LISTS. Overseas please send 2 IRCs to cover surface Post or 5 IRCs for Airmail.

Please add part cost of post, packing and insurance as follows:

INLAND
Orders up to £10 - 50p
Orders £10 to £49 - £1
Orders over £50 - £1.50

OVERSEAS
Please send sufficient to cover Surface or Air Post as required.



Personal callers are always very welcome but please note that we are closed all day Saturday

24hr SALES LINE
(0691) 652894

ALL PRICES EXCLUDE VAT UNLESS STATED

ROBOTICS

Robot arm	part 1	Sep 1981	50
	part 2	Oct 1981	43
Robot motor controller	part 1	Mar 1982	61
	part 2	Apr 1982	94
	part 3	May 1982	34
Servo arm interface	part 1	Oct 1982	69
	part 2	Dec 1982	77

SECURITY

Alarm alarm		Jul 1977	29
Alarm extender		Nov 1983	39
Alarm module		Mar 1983	63
	Errata	Aug 1983	70
Alarm, ZX-based		Dec 1983	31
Anti-theft auto alarm		Jan 1974	16
Automatic car-theft alarm		Aug 1972	50
Automatic light switch		May 1984	19
Automatic porch light		Jul 1980	77
Banshee siren unit		Sep 1984	35
Burglar alarm system		Apr 1977	57
	Errata	Jun 1977	9
Burglar proof your home		Jul 1974	30
Car alarm		Mar 1975	24
	Errata	Jul 1975	68
Car alarm		Dec 1978	16
Car alarm		Oct 1983	66
	Errata	Nov 1983	96
Car security device		Apr 1980	50
CMOS burglar alarm		Apr 1975	51
CMOS house alarm		Jan 1978	16
Combination lock		Mar 1981	74
Ecolight		Jul 1984	55
Electronic combination lock		Mar 1975	46
Home security system		Aug 1981	18
Infant guard		Jan 1982	80
Infra-red intruder alarm		Jul 1972	54
Infra-red intruder alarm		Feb 1981	62
Infra-red Intruder Alarm	part 1	Jul 1984	61
	part 2	Aug 1984	59
	Errata	Jul 1986	56
Logic lock	part 1	Jun 1982	79
	part 2	Jul 1982	39
	Errata	Nov 1982	75
Porch light		Feb 1978	28
Proximity switch		Oct 1978	75
Radar intruder alarm		Aug 1975	21
Second line of defence, the — simple house alarm		Nov 1985	60
Ultrasonic burglar alarm		Aug 1980	86
Warlock alarm system		Jul 1984	35
Watchdog home security system		Aug 1981	18
ZX-based alarm		Dec 1983	31

TELEVISION AND VIDEO

CCTV camera		Dec 1977	46
Colour board for the Ace microcomputer		Apr 1984	41
	Errata	May 1984	69
Digital framestore	part 1	Dec 1984	61
	part 2	Jan 1985	44
	part 3	Feb 1985	55
	part 4	Mar 1985	59
	part 5	Apr 1985	48
Low-cost framestore	part 1	Sep 1986	36
	part 2	Oct 1986	48

Low-cost VDU interface	part 3	Nov 1986	43
	part 1	Aug 1976	56
	part 2	Sep 1976	10
	part 3	Oct 1976	30
	Errata	Oct 1976	30
RGB-composite converter		Jan 1987	32
Teletext decoder	part 1	Jul 1979	20
	part 2	Aug 1979	41
TV chess game	part 1	Oct 1978	48
	part 2	Nov 1978	44
TV games unit		May 1977	12
TV sound tuner		Sep 1980	73
TV sound tuner		Dec 1981	37
UHF aerial preamplifier		Aug 1973	34
VDU interface (System 68)	part 1	Jun 1977	33
	part 2	Jul 1977	54
Vector graphic display		Jan 1984	19
Videograph — TV audio display		Apr 1979	27
Video Vandal		Nov 1984	50
	Errata	Jul 1985	27

TEMPERATURE MEASUREMENT AND CONTROL

Differential temperature switch Module		Mar 1981	49
Digital thermometer		Oct 1977	20
Economical heater controller		May 1982	22
	Errata	Jul 1982	35
Freezer alarm		Dec 1977	30
Heater controller		Mar 1980	67
Heat/light controller (Free PCB project)		Oct 1982	25
Heat pen — temperature probe for DVMs		Jun 1985	48
	Errata	Mar 1986	60
Immersible heater		Jun 1983	65
Micropower thermal alarm		Oct 1981	68
Seven-input thermocouple meter		Dec 1973	23
Temperature alarm		Nov 1974	25
Temperature alarm		Mar 1977	53
Temperature alarm (free PCB project)		Apr 1986	44
Temperature controller		Nov 1984	63
Temperature controllers, three		Mar 1975	18
Temperature meter		Aug 1974	30
Temperature meter		Jul 1978	21
Temperature meter add-on for voltmeters		May 1976	49
Thermometer — max/min memory thermometer		Apr 1983	70
	Errata	Jul 1983	20
Under temperature switch module		Mar 1981	51
Wine temperature meter		Dec 1978	31

TEST EQUIPMENT

1kHz function generator		Mar 1977	55
All purpose power supply, 30V, 1A		Aug 1978	75
Amplifier, bench (Short Circuit)		Feb 1977	52
Amplifier, bench		Aug 1979	67
Amplifier, bench		Dec 1980	74
Analogue/digital probe (ETI Modular Test Equipment)		Apr 1986	36
Attenuator, audio		May 1973	53
Attenuator, RF		Sep 1976	62
Audio Analyser		Oct 1986	43

Project	Mth	Yr	Pg	Project	Mth	Yr	Pg
Audio frequency meter	Jul	1973	66	part 2	Nov	1986	29
Audio millivoltmeter, 'A' weighted	Apr	1976	26	Frequency meter, audio	Jul	1973	66
Audio noise generator	Apr	1976	22	Frequency meter, digital, 0-150 MHz	Jan	1980	56
Audio oscillator	Nov	1980	27	Frequency meter, digital (Short Circuit)	Jun	1977	19
Audio oscillator with LCD DFM	Nov	1978	71	Errata	Aug	1977	8
Audio power meter	Jun	1976	29	Frequency meter, linear 100 Hz-100 kHz	Jul	1980	99
Audio power meter	Mar	1979	67	Frequency meter module for DVMs (free PCB Project)	Apr	1986	46
Audio spectrum analyser	Mar	1978	27	Function generator, 1kHz (Short Circuit)	Mar	1977	55
Audio wattmeter	Oct	1973	46	Function generator, 1Hz-100kHz	Dec	1979	20
Autoranging capacitance meter	part 1 part 2 Errata	Mar Apr Jul	1982 1982 1982	Grid dip oscillator	Aug	1975	34
Basic power supply, 4.5A-12V, 0.4A	Oct	1974	53	High impedance instrument probe	Apr	1982	57
Bench amplifier	Errata	Nov	1974	IC power supply	Jan	1973	34
Bench amplifier	Aug	1979	67	IF strip tester (Free PCB project)	Oct	1982	26
Bench amplifier (Short Circuit)	Dec	1980	74	Impedance meter, direct reading	Jun	1975	17
Bench PSU, 20V/2.5A or 40V/1.25A	Feb	1977	52	Instrument probe, high-impedance	Apr	1982	57
Bench PSU, 3-8V/2.5A and ±8-16/0.5A	Jul	1976	18	Insulation tester, 500V	May	1982	73
Bench PSU, 25V/1.5A (Short Circuit)	Feb	1984	41	Laboratory PSU, 0-30V, 1,2A	Sep	1981	87
Cable tester	Apr	1977	47	LCD digital multimeter	Aug	1978	23
Capacitance meter, 10pF-10uF	Oct	1979	23	Errata	Oct	1978	13
Capacitance meter, autoranging	Aug	1980	93	LEDline logic analyser	Feb	1987	50
Capacitance meter, autoranging	part 1 part 2 Errata	Mar Apr Jul	1982 1982 1982	LEDscope AF flat-screen oscilloscope	Jan	1987	57
Capacitance meter, direct-reading	Nov	1984	41	Linear frequency meter, 100Hz-100kHz	Jul	1980	99
Capacitance meter (ETI Capacitometer)	Mar	1987	45	Linear IC tester	Nov	1974	30
Capacitance meter, large value (ETI Millifaradometer)	Nov	1985	44	Linear ohmmeter, 1k-1M FSD	Jun	1980	34
Capacitance meter module for DVMs (Free PCB project)	Mar	1986	30	Logic/analogue probe (ETI Modular Test Equipment)	Apr	1986	36
Circuit probe, analogue/digital (ETI Modular Test Equipment)	Apr	1986	36	Logic analyser (ETI LEDline)	Feb	1987	50
CMOS IC tester	Aug	1984	64	Logic clip, 16 point, TTL/CMOS	Nov	1983	91
Errata	Sep	1984	68	Logic IC tester, TTL/CMOS	Jan	1976	19
CMOS IC tester, simple	Feb	1976	19	Logic probe	Sep	1972	32
Component bridge (RCL bridge)	Aug	1985	30	Logic probe	Dec	1975	32
Component tester (for semiconductors)	Dec	1981	69	Logic probe, CMOS, single point	Mar	1983	73
Continuity tester, audible (ETI Loudspeaker Squeaker)	Nov	1984	17	Logic probe, dual	Sep	1982	68
Continuity tester (Short Circuit)	Sep	1977	38	Logic probe, TTL/CMOS	Dec	1979	101
Counter/timer module (ETI Modular Test Equipment)	Jan	1986	54	Logic Pulser	Dec	1975	37
Cross hatch generator	Sep	1978	33	Logic tester, CMOS	Aug	1980	73
Crystal calibrator	Mar	1981	39	Logic-trigger for oscilloscopes	Mar	1979	39
Curve tracer	Dec	1978	73	Loudspeaker squeaker	Nov	1984	17
Decade resistance box	Dec	1972	38	Low-ohm meter, 0.1-100R FSD	Apr	1981	40
Digital frequency meter (Short Circuit)	Jun	1977	19	Marker generator	May	1976	25
Errata	Aug	1977	8	Memory 'scope display	Nov	1985	28
Digital frequency meter, 0-150MHz	Jan	1980	56	Meter mount (multimeter stand)	Jan	1973	43
Digital multimeter	Oct	1976	42	Millifaradometer — large-value capacitance meter	Nov	1985	44
Errata	Nov	1976	8	Millivoltmeter, audio, 'A' weighted	Apr	1976	26
Digital multimeter	Aug	1978	23	Modular test equipment	part 1 part 2 part 3 part 4 part 5 Errata	Oct Nov Dec Jan Apr Jun	1985 1985 1985 1986 1986 1986 1986
Digital oscilloscope trigger	Sep	1983	51	Multimeter (DMM/DFM)	Errata	Apr	1981
Digital test meter (DMM/DFM)	Sep	1980	79	Multimeter, digital	Errata	Oct	1976
Digital voltmeter	Mar	1977	35	Multimeter, LCD digital	Errata	Nov	1976
Errata	Jun	1977	9	Errata	Aug	1978	23
Digital voltmeter module	Oct	1975	18	Ohm-meter, linear, 1k-1M FSD	Errata	Oct	1978
Direct-reading capacitance meter	Nov	1984	41	Oscillator, audio	Jun	1980	34
Distortion Meter	part 1 part 2 part 3	Jan Feb Mar	1985 1985 1985	Oscillator, audio, with LCD DFM	Nov	1980	27
Dual logic probe	Sep	1982	68	Oscillator, sweep	Nov	1978	71
Dual power supply	Apr	1972	50	Oscillator, wide range	Aug	1977	10
Dual trace adaptor	Oct	1974	18	Oscilloscope, 10 MHz	Jun	1978	90
Dual trace adaptor (Design Competition)	Feb	1983	72	part 1	May	1982	53
Dual trace adaptors (Readers' Designs)	Jul	1981	27	part 2	Jun	1982	30
Dummy load for audio testing	Jan	1982	71	part 3	Jul	1982	63
FET DC voltmeter	Dec	1972	36	Errata	Feb	1983	41
Frequency counter module, 1 MHz	Nov	1975	11	Oscilloscope calibrator	Apr	1972	12
Frequency counter module (ETI Modular Test Equipment)	Jan	1986	54	Oscilloscope, flat-screen AF (ETI LEDscope)	Jan	1987	57
Frequency counter, PLL	part 1	Oct	1986	Oscilloscope logic trigger	Mar	1979	39
				Oscilloscope memory display	Nov	1985	28
				Oscilloscope probe, high-impedance	Apr	1982	57

Oscilloscope, television	part 1	Jul	1983	21
	part 2	Aug	1983	30
	Errata	Sep	1983	46
Oscilloscope, television (Videograph)		Apr	1979	27
Oscilloscope trigger, digital		Sep	1983	51
PLL frequency counter	part 1	Oct	1986	28
	part 2	Nov	1986	29
Power meter, audio		Jun	1976	29
Power meter, audio		Mar	1979	67
Power meter, RF		Oct	1978	30
Power meter, stereo		Mar	1984	35
Power supply, 0-30V/1.2A		Sep	1981	87
Power supply, 4.5-12V/0.4A		Oct	1974	53
	Errata	Nov	1974	71
Power supply, 3-8V/2.5A and $\pm 8-16V/0.5A$		Feb	1984	41
Power supply, 10V/1A or 15V/0.5A		Jan	1973	34
Power supply, 25V/1.5A (Short Circuit)		Apr	1977	47
Power supply, 30V/1A		Aug	1978	75
Power supply, 20V/2.5A or 40V/1.2A		Jul	1976	18
Power supply board (ETI Modular Test Equipment)		Oct	1985	38
Power supply, dual, 0-20V/1.8A		Apr	1972	50
Power supply, programmable		Jan	1983	83
Pulse generator board (ETI Modular Test Equipment)		Dec	1985	37
Pulse generator, precision		Nov	1982	39
Pulse generator, single/delayed		Feb	1981	46
RCL bridge		Aug	1985	30
Resistance box, decade		Dec	1972	38
RF attenuator		Sep	1976	62
RF power meter		Oct	1978	30
SCR tester (Short Circuit)		Jan	1977	36
Semiconductor tester		Dec	1981	69
Signal injector/tracer (Short Circuit)		May	1977	37
Signal generator (ETI Modular Test Equipment)		Nov	1985	36
	Errata	Jun	1986	55
Signal tracer		Mar	1980	26
Simple CMOS IC tester		Aug	1984	64
	Errata	Sep	1984	68
Simple frequency counter		Nov	1975	11
Sound pressure level meter		Feb	1981	74
Spectrum analyser, audio		Jun	1978	27
Spectrum analyst		Nov	1982	52
	Errata	Dec	1982	83
Stereo power meter		Mar	1984	35
Stereo test amplifier (Short Circuit)		Jul	1977	30
Sweep oscillator		Aug	1977	10
Telescope (television oscilloscope)	part 1	Jul	1983	21
	part 2	Aug	1983	30
	Errata	Sep	1983	46
THD meter	part 1	Jan	1985	55
	part 2	Feb	1985	37
	part 3	Mar	1985	43
Tone burst generator	part 1	Feb	1976	25
	part 2	Mar	1976	57
Transistor tester		Jul	1974	63
True RMS voltmeter		Mar	1978	13
TTL supertester		May	1975	30
TV bargraph		Jul	1982	50
TV pattern generator		Nov	1976	31
TV storage 'scope	part 1	Jul	1983	21
	part 2	Aug	1983	30
	Errata	Sep	1983	46
Videograph TV oscilloscope		Apr	1979	27
Versatile grid dip oscillator		Aug	1975	34
Voltmeter, digital		Mar	1977	35
	Errata	Jun	1977	9
Voltmeter, FET DC		Dec	1972	36
Voltmeter module, digital		Oct	1975	18
Voltmeter, true RMS		Mar	1978	13
Voltmeter, wide range		Apr	1972	36
	Errata	Feb	1973	58
Wattmeter, audio		Oct	1973	46
Wide range oscillator		Jun	1978	90
Wide range voltmeter		Apr	1972	36

A number of errors have come to light since the publication of the first part of this index in the April 1987 issue. The correct entries are given below in the sequence in which they appear.

Under the heading AUDIO (page I of the index):-

2040 II active loudspeaker, September 1982 page 46: a correction concerning this article was published on page 75 of the November 1982 issue;

Balanced line preamplifier: this article appears on page 38 of the May 1983 issue, not page 63 as stated;

FM tuner with digital frequency display: this article appears on page 21 of the September 1978 issue, not page 71 as stated;

Headphone adaptor; this article appears on page 53 of the March 1976 issue, not page 52 as stated;

Moving coil preamplifier, Audiophile: the first errata for this article appears on page 17 of the February 1980 issue, not page 29 as stated;

Preamplifier, RIAA: this article appears on page 98 of the September 1980 issue, not page 73;

Under the heading CLOCKS and TIMERS (page III of the index):-

STAC timer: this article appears in the September 1978 issue, not the September 1981 issue.


It's easy to complain about advertisements. But which ones?

Every week millions of advertisements appear in print, on posters or in the cinema. Most of them comply with the rules contained in the British Code of Advertising Practice.

But some of them break the rules and warrant your complaints. If you're not sure about which ones they are, however, drop us a line and we'll send you an abridged copy of the Advertising Code. Then, if an advertisement bothers you, you'll be justified in bothering us.

The Advertising Standards Authority.
If an advertisement is wrong, we're here to put it right.
 ASA Ltd, Dept 2 Brook House, Torrington Place, London WC1E 7HN

This space is donated in the interests of high standards of advertising.



BINDERS

FOR YOUR VALUABLE COLLECTION OF ELECTRONICS TODAY INTERNATIONAL MAGAZINES

- SMART • EASY TO USE • TOP QUALITY

To ASP Readers Services, PO Box 35, Wolsey House, Wolsey Road, Hemel Hempstead, Herts HP2 4SS (0442-41221)

Please supply.....Electronics Today International Binders @ £5.20 inc. P&P

Total £ (Please make cheques payable to ASP Ltd.)


Years Required — 198.....198.....198.....198.....

Name

Address

Please allow 21 days for delivery

£5.20 inc P&P



TRANSISTORS

BC107	15
BC107A	15
BC107B	15
BC108	15
BC108A	18
BC108B	15
BC108C	15
BC109	18
BC109B	18
BC109C	18
BC182	12
BC182B	12
BC183	12
BC183B	12
BC184	12
BC212	12
BC212B	12
BC213	12
BC213B	12
BC214	12
BC327	16
BC337	16
BC548	12
BCY70	22
BCY71	22
BD131	60
BD132	60
BD135	34
BD136	35
BD239-A	60
BF258	60
BFX85	40
BFX88	40
BFY50	37
BFY51	37
BFY52	39
TIP31	42
TIP31A	48
TIP31B	56
TIP31C	54
TIP32A	42
TIP32C	42
TIP33A	100
TIP41A	63
TIP42A	55
TIP3055	76
TIP2955	76
ZTX300	17
ZTX500	17
2N3053	60
2N3054	160
2N3707	12
2N3703	12
2N3705	12
2N3771	140
2N3904	15
2N3906	15

DIODES

IN4001	5
IN4003	6
IN4004	6
IN4007	8
IN4008	6
IN4148	6

CAPACITORS

Electrolytic	Tantalum	Ceramic
47uF 25V 10	.1uF 35V 10	220pF 500V 6
100uF 25V 12	.22uF 35V 10	470pF 500V 6
470uF 25V 28	.47uF 35V 10	1000pF 100V 6
1000uF 25V 36	1uF 35V 10	2200pF 100V 6
10uF 25V 08	2.2uF 35V 15	4700pF 100V 6
220uF 25V 15	4.7uF 35V 20	

VERO BOARD

0.1" matrix copperclad 37 strip wide at 4p per hole, 41 strips by 40 holes + 4 mounting holes £2.20. spot face cutters £1.99.

SWITCHES:— ABS Boxes ribbon. Cable. Potentiometers, soldering irons, solder & desolder pumps. **P.O.A.**

OPTO ISOLATORS

TILTIL 111 transistor	110
TIL 113	
Darlington o/p 3021	120
Triac driver	150

ZENER DIODES

BZY88C 500m W	
4V7	10
10V	10
12V	10
BZX55C 500m W	
24V	10
BZX85C 1.3 Watt	
4V7	20
10V	20
12V	20
24V	20

BRIDGE RECTIFIERS

W004 1.5A	50
6005 6A	90

VOLTAGE REGULATORS

LM317T +1.2V to 37V	150
LM341P +5V	60
LM7905 -5V	70

IC SOCKETS, Low Profile

8pin	7
14pin	12
16pin	13
24pin	20
40pin	30

RESISTORS

Metal Film 5% 1/3 Watt
100R 680R 1K 1K2 2K2 4K7
5K6 6K8 10K 12K 15K 22K 27K
33K 39K 47K 56K 68K 82K
100K 120K 150K 180K 220K
270K 330K 390K 470K 560K
680K 820K 1M 2p

SKELETON PRESETS

Horizontal	19
Vertical	19

LEDs

T1 3/4 5mm	
Red	18
Yellow	18
Green	18
Super bright	
t1 3/4 5mm	
Red	35

LINEAR ICs

741	18	NE5532	120	LM308	70
555	30	NE5534	80	TL081	50
556	65	ZN414	90		
LM301	28	ZN416	160		

TRIACS

3 Amp 400V	75	8 Amp 400V	90
------------	----	------------	----

B.T. APPROVED TELEPHONES

B.T. Statesman with Stone last number redial	31.26	B.T. Viscount with Beige last number redial	26.04
Brown	31.26	Ice Grey	26.04
Maroon	31.26	Red	26.04
Grey	31.26	White	26.04

B.T. cordless Freeway 700ft range security coded, last number redial with base paging, Ivory **85.00** Telephone accessories and sockets **P.O.A.**
Carriage on telephones and telephone accessories **£1.50**
Add 15% VAT to total. Allow ten days for delivery.

DPDT centre off slide switches, 8ohm earpieces, 2KHz buzzers, price lists **P.O.A.**

Super Alpha Guarantee

All components brand new and by top manufacturers to full specification.

ORDERING: Cash, Postal-Order, or Visa, orders despatched same day by first class post. Add **50p** p&p to order then add 15% VAT. Telephone orders welcome with Visa, orders accepted by answer service outside office hours. Overseas orders add **£2.00** no VAT. Prices subject to alteration.

THE ETI KAPELLMEISTERS

Vivian Capel has been hard at work in the garden shed and now emerges to show off his high quality but novel loudspeaker design.

The perfect loudspeaker which exactly reproduces the sound field obtaining at the original performance does not, of course, exist. So many of the requirements are incompatible when applied to practical loudspeaker design. If we want one feature we must sacrifice another.

The designer usually tries to effect a compromise, giving us some of both as far as that is possible. One designer may favour one characteristic and so slant his design in that direction, while another may consider the other to be of greater importance.


The Kapellmeister speaker was designed to fulfil a particular pattern of priorities. Some unorthodox methods were used to achieve them and constructing the prototypes though not difficult, was time-consuming. However, the results obtained more than justified the time and effort expended.

Requirements

The overriding consideration was that of size. In many homes, so much has to be accommodated in a modest living space there just isn't room for two large speaker boxes. However, most of the furniture stands around the walls so it is cabinet width that is the most critical dimension. Depth is of less importance and (within reason) height is no problem at all.

I found that eight inches was the maximum width I could allow for each speaker. This didn't seem very hopeful for a hi-fi unit!

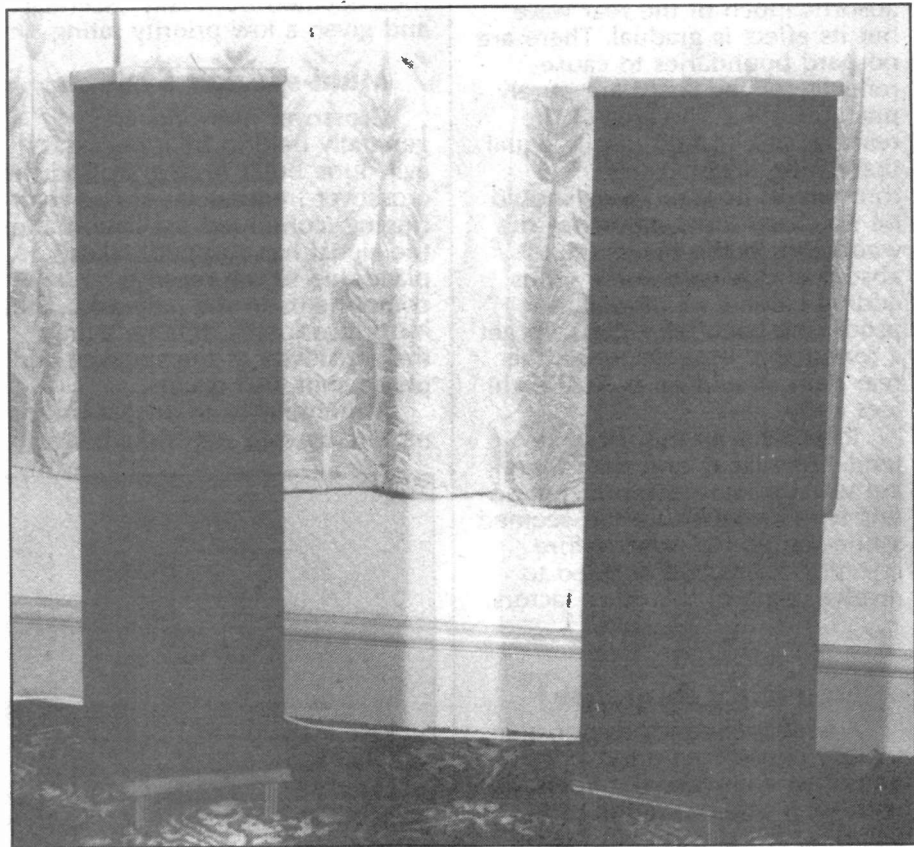For small size, the infinite baffle seemed the obvious choice, yet I wasn't too happy with the prospect. Pressure acting on the back of the cone is non-linear because it increases as the cone



moves back. As the cone can only move in accord with *all* forces acting on it, its movement is thus not in exact proportion to the applied electrical signal.

The effect is more pronounced at lower frequencies. Indeed, the measured distortion of infinite baffle enclosures is high in the bass region. Internal reflections lead to standing waves and hangover, while high internal pressures produce panel resonances in the cabinet which require rigid construction, careful selection of materials and various forms of damping.

Bass resonance can be tamed only by critical adjustment of

cabinet volume in conjunction with the driver parameters. Many designers adjust the cabinet Q to give moderate bass resonance to enhance the bass response.

However, in my priorities, low distortion and lack of coloration came higher than a pronounced bass response. Infinite baffles, especially small ones, need a lot of amplifier power which I did not have, so the infinite baffle enclosure was out.

Reflex enclosures suffer from similar drawbacks although there are some very good ones. These also were rejected.

The rear-loaded folded horn is

A particular problem is phasing. As the cones of tweeters, mid-range units and bass drivers are of different depths, they are at different distances from the listener when mounted normally.

The resulting phase differences vary with frequency and the total wavefront pattern from all units is quite different from that of the original sounds. These phase anomalies are compounded by those arising from the crossover networks.

Phasing is particularly important in the reproduction of the stereo signal because stereo information is largely conveyed by subtle phase differences between the channels, as well as by amplitude variations. Some commercial speakers have stepped front baffles so that all the cones are in line (and in phase). This is an improvement on the conventional arrangement but only one listener right on axis will gain any benefit. Those off axis still have to suffer phase differences. Others have the tweeter reverse-connected to minimise phase shifts in their crossover networks, but all these are really palliatives.

All this casts grave doubts on the desirability of multi-speaker units. The problems can so easily be resolved by using a single full-range speaker if some limitation of the frequency range is accepted. The question is, how much?

Investigation into available drive units revealed a full-range elliptical 8-inch by 5-inch with centre HF cone that had a frequency response of 45Hz to 16,000Hz — just the frequency range I had decided on!

Power rating seemed rather low at eight watts RMS, but without the inherent loss of the infinite baffle enclosure and those of the crossover networks a high efficiency could be anticipated, giving ample sound output.

Freedom from the clutter of extra drivers could well make a transmission line possible too.

A single driver also approaches the ideal point source, something achieved with considerable complication and expense in the prestigious Quad ELS-63 electrostatic. Coupled with the narrow eight inch cabinet width, this should produce outstanding stereo imaging.

Is there any disadvantage with using a single driver apart from restricting the frequency response? Doppler effect is one sometimes mentioned. High frequencies are modulated by the

forward and backward cone movement made when reproducing bass at the same time. However, with an acoustically efficient system, cone movement due to bass is limited so the effect is small.

Even so, a point sometimes overlooked, is that the microphone diaphragm itself originally experienced doppler effect by responding to some high and low frequencies at the same time, although its bass movements are much smaller than those of a speaker cone. The motion of a single-speaker cone is therefore closer to that of the microphone diaphragm than those of the cones of a multiple-speaker system.

Design Considerations

The transmission line type of enclosure is top of the league for pure uncoloured reproduction — providing good design principles are observed. These are not easy to achieve in practice, and usually mean considerable bulk.

The Kapellmeister speakers use some novel and highly successful methods of overcoming the problems, while occupying only 8x11in of floorspace.

One of the requirements is for the area of the transmission line to equal that of the driver cone throughout its length. Any variations result in sound pressure differences, back pressure and other complex effects which upset the smooth passage of sound along the line.

This ideal is frequently compromised in practical designs because of another rule that there should be no sharp bends. These can cause reflections, absorption and release of energy from wooden baffles angled to deflect the sound around the corners. All of this results in coloration.

Conventional designs usually house all the drivers in a cubicle which extends to the back of the cabinet. From this the path, considerably reduced in area, descends to follow its course through horizontal and vertical sections. At the back of the cubicle there is usually a deflection back to the drivers.

For reasons already mentioned, we use only one driver and this simplifies matters because we can dispense with the cubicle. The driver is thereby mounted at one end of the line which does not vary in area throughout its length, so totally fulfilling one of the

main requirements.

The path followed is shown in Fig. 1. It is in three sections; the sound travels downwards, then up through the centre section, and finally down again through the rear one to exit at the bottom.

This arrangement appears to violate the other main rule regarding bends and deflectors. However, that rule does not apply if deflectors could reflect the sound perfectly along the required path without back reflection and without adding coloration.

Wood does not fulfil that requirement but other materials can do. One excellent one is ceramic tile with concrete backing. (Note how sound bounces around in a tiled swimming bath). So, the deflectors are glazed ceramic tiles set on concrete corner blocks. These might seem to be a nuisance when considering construction, but they are easily formed in situ, and are the real secret of the quality obtainable from these speakers.

The tiles are set at an angle of 45° to reflect the sound accurately around the bends. It will be noticed that there is also a tile at the top just above the driver. The purpose of this is to reflect sound generated by the top part of the cone downward.

The wave-front radiated by the back of a loudspeaker cone travels outward along an axis that is perpendicular to the surface of the cone. If the cone is at an angle of 22° the tile should be set at an angle of 56°. If the speaker has a different angle from this, the difference for the angle of the tile should be halved, so a 20° cone should have a tile angle of 55°. Most loudspeakers of this size have cone angles in this region, but the angle varies slightly with cone curvature anyway, so the above figure can be used in most cases and is not too critical.

As the sound pressure on either side of the baffles is almost the same they are not excited into vibration to produce coloration, and this is true also of the back. The top and bottom pieces are of stout timber lined on their insides with the concrete and tiles, so they too are prevented from vibrating.

Only the front panel has a sound pressure differential between its faces but this is much lower than with a totally enclosed cabinet. Also its narrow width makes for high rigidity which inhibits vibration. The material of

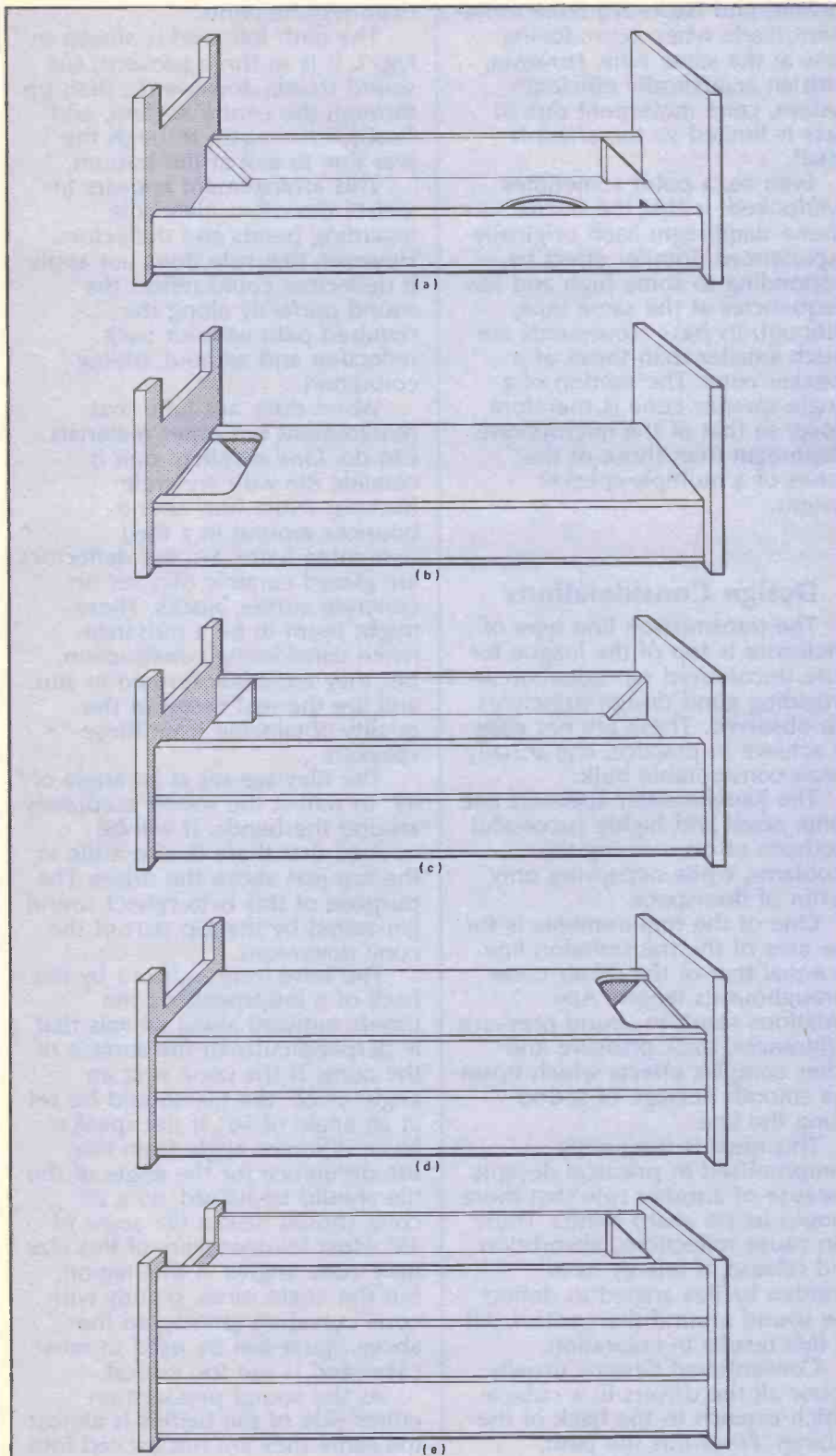


Fig. 3 (a) First stage in construction. The front is glued to top and bottom cheeks using $\frac{1}{4}$ in supports to lift front into correct position. First pair of side pieces fitted and triangular blocks (small ones at the top) in position. Apply concrete, fit tiles and lay wadding. (b) Fix first baffle, glueing and pinning down to ensure close fit. (c) Fit second pair of side pieces and four triangular blocks (all blocks from now on are regular size). Apply tiles, concrete, and wadding. Tuck two extra lengths of wadding through aperture into first channel. (d) Fit second baffle glueing and pinning. Aperture goes at the top. (e) Glue in third pair of sides and last pair of blocks. Fit tile and concrete, lay wadding and fit back. Double an extra length of wadding around the ends of the full lengths. Sand down, fill crevices, finish top and bottom cheeks, fit fabric and fix legs.

the enclosure thereby adds very little to the sound.

Closed Pipe

The transmission line is in effect a pipe that is closed at one end but open at the other. As such it inhibits a fundamental resonance plus odd harmonics. There are no even harmonics. The fundamental resonance occurs where the total length equals a quarter wavelength of the frequency. Here, the length is just over eight feet, so the resonance is at 35Hz, which is below the lower limit of the driver at 45Hz. However, being broadened by the dampening material in the pipe, it can influence the range of the speaker, usefully extending it by a few Hertz.

The antinodes (points of maximum air motion) at the third harmonic occur at the third and two-thirds positions, that is at the bends. Extra wadding at these points serve to suppress this harmonic. Extending the extra wadding up the first channel and also at the exit dampens out two of the three antinodes of the fifth harmonic. Above the fifth, the harmonics are smaller and the normal wadding fitted throughout the length of the pipe tames them.

The speaker unit is an 8in x 5in elliptical unit which, allowing for the frame and surround, has 7in x 4in cone. Thus the approximate area is 21in². Area of the channels is a 7in x 3in rectangular, which is the same as the cone.

Parameters of the driver are not too critical, so if the specified one is not available any similar unit will do. The size is important and this includes the front to back measurement which should be about 2½ inches. It should be a full-range speaker with a response from 45Hz to 15kHz or better. Generally you will find that an extension at one end is at the expense of the other.

High power is not essential because of the good acoustic and electrical efficiency, but eight watts RMS minimum is recommended. General good quality construction with a magnet of not less than 9,000 gauss should be looked for.

Construction

Although quite a lot of wood-working is needed, none of it is difficult and it consists mostly of cutting straight edges. These *must*

be straight though, so if your saw cuts tend to wander, get the timber yard to cut them for you. The measurements are uniform with many pieces being the same, which helps.

Use standard 8in x 4in ceramic tiles, cut down to 7in x 4in. That is just one straight cut per tile. The exception is the top tile over the speaker which because of its different angle must be 7in x 3½in.

Triangular blocks are used to support the tiles as shown in Fig. 1. These are made by first cutting four 3in squares, then sawing diagonally to give eight triangles. The two blocks for the over-speaker are made by halving a 3in x 2in rectangle. A standard 3:1 mix of sand and cement is used to fill the space behind the tiles. In some cases the cement is applied first between the blocks and the cement applied at the back afterwards.

In all cases screw two or three stout screws at random angles into the wood where the cement is to be laid leaving about an inch out of the wood, so that they will be buried in the cement. These will then secure the concrete block in place when it is dry. Thoroughly wet the back of the tile before applying it to the cement. In some cases the front of the tile may need to be held in place while the cement sets, with panel pins knocked into the wooden sides. It does little harm to leave them in place afterward.

All jointing is done by a strong wood glue. Evostik wood glue was used for the prototypes which is very strong and convenient to apply. If not available, a substitute can be used but make sure it is a wood glue and not a general purpose adhesive.

Construction must proceed in numerous stages (Fig. 3) to allow the glue and concrete to set before continuing with the next, so some patience must be exercised. Make both speakers at the same time so that each stage can be completed on both and some time saved.

Stages

Having cut all the pieces, we start with the front panel. Lay it face downward supported on some scrap ¼in ply or hardboard. Glue the top and bottom edges and fit the top and bottom boards. The front edges of these should *not* rest on the ply supports but directly on the work

surface. They will then protrude a quarter of an inch beyond the panel. They should also be positioned to give an equal overlap at either side. The idea is for the top and bottom cheeks to overhang the front, sides and back. Weights should be applied to the free sides of the cheeks to hold them against the panel while drying.

Measure the distance between the rear edges of the top and bottom cheeks to ensure that it is exactly 33in and therefore the top and bottom are parallel. Wait for the glue to set and harden.

Next, fit the first pair of side pieces, glueing the ends and the edge contacting the back of the front panel. Ensure the pieces are flush with the edge of the front panel. Measure across the upper edges to make sure they are 7¾in and so are true. Now glue the triangular blocks in place at the bottom and top as shown in Fig. 3. The top ones are the special sized ones. Glue the edges as well as the face that contacts the sides, but be careful in pressing them into place that you do not move the sides. Leave it to set.

Now fit the speaker, screwing it in place over the aperture, and solder a pair of wires which are run down the panel to a hole drilled in the bottom. Leave a few inches free, and make sure both speakers are connected the same way to colour-coded wire. It is prudent to cover the front of the speaker with a piece of card secured by drawing pins to protect the cone during subsequent operations.

Fit supporting screws to the base and top, then fill the space between the bottom blocks with cement (not too wet) and bed the tile. Fit the top narrow tile on the blocks and fill in behind it with cement. Allow time to harden. If desired, a quick-drying additive can be used to speed matters up.

Saw suitable lengths of quadrant and glue into the corners between the front panel and the sides. If they are warped they should be held in place with panel pins. Glue two further strips of quadrant at the top inside edge of the sides and pin to secure.

Cut three lengths of BAF wadding to size and lay them in the cabinet so that two start at the bottom of the speaker and the third lies over it to the top of the case. Fill the space above the speaker with a rolled up piece of

wadding. Make the lengths a few inches longer than the channel so they bend up at the bottom over the tile. The three layers will fill the channel without compression.

Now fit the first baffle with the cut-out at the bottom, glueing to the top edge of both sides and the upper quadrant surface. Also glue to the top and bottom cheeks. Secure with panel pins to ensure a close fit. Next, fit the second pair of side pieces and two pairs of blocks top and bottom. Fit quadrant to the corners, as with the first channel, and to the top edges of the sides. Wait for all the glue to dry.

Fit the tiles and cement as with the first pair, but this time the top one will be bedded and the bottom one rear-filled. Wait for the concrete to set.

Cut two pieces of wadding about 18in long and push half the length of each up the lower channel through the cut-out, and lay the other half length back along the top channel. Now lay three full length strips over these along the complete upper channel. This gives the extra density at the first bend needed to dampen the third harmonic antinode.

Next comes the second baffle which is glued and pinned as the first but with the cut-out at the top. Fit the third and final pair of sides, also the last pair of blocks plus the quadrant in the corners and top edges. Allow the glue to harden.

Now for the last tile. Don't forget the screws in the top to secure the concrete block inside. Mount the tile on the blocks using panel pins to keep it in place; this will be easier if the enclosure is stood vertically upside down. Return to the horizontal, and fill in rear with cement. Wait until set.

Lay three strips of wadding in the channel making sure the bend is filled. Put some extra here if necessary to fill completely. Cut another strip about 24in long and tuck half the length under the other three at the outlet, and bring it over the top so that it covers the rough ends.

Lastly glue and pin the back in place. Now for the finishing. Sand down any ridges in the sides, but do not be too fussy, for they will be completely covered with fabric. Check carefully for any cracks or crevices in the jointing and fill

PROJECT: Kapellmeisters

with wood glue. Sand, then stain or varnish the top cheek and the edges of the bottom one. There is no need to do the underneath. Paint the body with matt black.

This is not strictly necessary, but if it isn't done, bare wood can show through the fabric. Take care not to get any paint on the loud-speaker cone as this would affect its flexibility.

Cut the fabric to the exact size to cover the body between the cheek overhangs, but leave a 4in flap 8in wide, at the start. Secure the vertical starting edge at one edge of the back of the enclosure with tacks so that the flap overhangs the bottom. Then pull it around, keeping it taut overlapping the start and securing it with a wooden strip (previously painted) down the middle of the back. Trim the flap to fit between the prongs of the bottom and fix it across the exit port with gimp pins.

Fit some 2in high legs. The rear ones should be inclined backward to give greater stability as in Fig. 1. Pack filler around the hole in the bottom through which

the speaker wire passes to make it airtight, and fit a connecting block underneath.

Performance

Well, was it all worth it? That's what I wondered when the prototypes were complete. It took very few listening sessions to provide the answer. Ambience and sense of presence was perhaps the first noticeable effect. Woodwind was clear, easily identifiable and rounded in tone. Brass was brilliant yet mellow, stacatto passages really were stacatto, not slurred as they sometimes sound.

A recording of harpsichord was remarkable, revealing tones and subtleties never heard before. A solo violin sounded natural with no moments of discomfort in the higher passages. One passage in an orchestral work which I always thought was performed by the cellos playing pizzicato, could be clearly identified as played on the lower registers of a harp. I am now really hearing many of my recordings for the first time.

Stereo broadcast drama is quite dramatic, with positive

locational identification even in crowd scenes. Sensitivity of the speakers enabled a 4+4 watt amplifier used for initial tests to provide ample undistorted volume. This opens up the possibility of using low-powered class A amps for even higher fidelity. Just one drawback though, I now find I cannot listen to other speakers with enjoyment (especially infinite baffle systems) so be warned!

ETI

BUYLINES

The speaker used is the ALTAI 8553DU, a full range 8in x 5in elliptical with centre HF cone. Frequency response: 45-16,000Hz, 8W RMS power. Any similar unit can be used, but it must be no more than 2½in deep.

Maplin can supply the Altai model (part number WY13P) or Wilmslow Audio (Tel: (0625) 529599) can supply an equivalent (part number EMI99140EB).

Back Again! ONYX PORTASOL Portable Gas Soldering Iron

AVAILABLE FROM
ETI READERS'
SERVICES

FINELY CONTROLLED SOLDERING
ANYWHERE! COMPLETELY SELF-CONTAINED
GAS POWERED SOLDERING IRON

FEATURES

- Totally portable
- Powered by ordinary lighter fuel
- Up to 60 minutes continuous use
- Adjustable temperature equivalent to 10-60 watts
- Top temperatures to max. of 400°C
- Refill in seconds
- High performance — small size 175mm x 19mm
- Meets all safety standards

To ETI READERS SERVICES, 9 Hall Road, Maylands Wood Estate, Hemel Hempstead, Herts, HP2 7BH

PLEASE SUPPLY THE FOLLOWING:

ORDER CODE..... Price.....
..... Price.....
..... Price.....
Postage.....



I enclose my cheque payable to ASP for
Please debit my Access/Barclaycard No.....
Name.....
Address.....


OFFER PRICE
— ONLY £15.35
+ 40p P&P

ORDER CODE ROSL 1


ALSO AVAILABLE AT SPECIAL PRICES TO ETI READERS

ROSL 2 Oryx 15 — Electronic assembly iron	£6.95 + 60p P&P
ROSL 3 Oryx 30 — General purpose iron	£7.55 + 60p P&P
YMR 45 Oryx TC 82 — 45 watt iron	£17.50 + £1 P&P
YMR 100 Oryx TC 100 — 100 watt iron	£26.50 + £1 P&P
ROSL 4 Soldering iron stand	£4.95 + 50p P&P

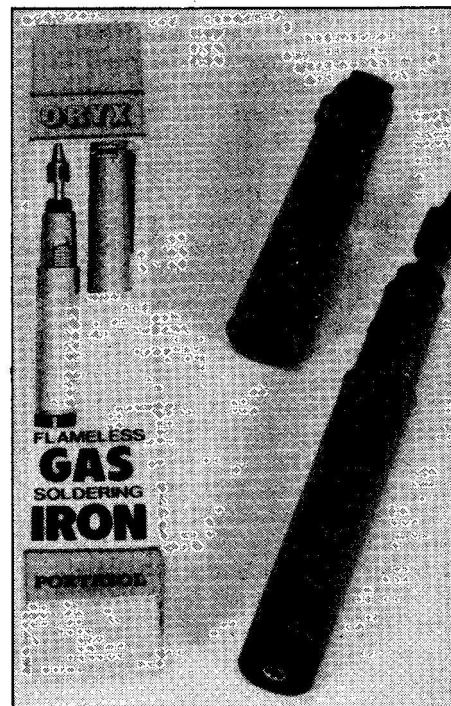ETI Readers Services, 9 Hall Road, Maylands Wood Estate, Hemel Hempstead, Herts, HP2 7BH.



FROM JAYTEE

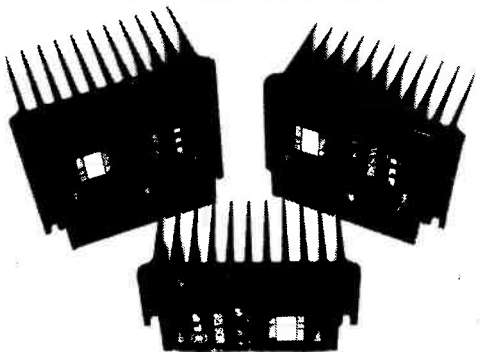

THE SPECIAL DISTRIBUTOR FOR SPECIAL AMPLIFIERS

ILP have long been recognised as manufacturers of top quality amplifiers.

All ILP products are built to extremely high specification for the ultimate in hi-fi performance. They're unique in being completely encapsulated with integral heatsinks, and can bolt straight onto the chassis. They're also extremely robust, ensuring high levels of reliability as well as performance.

ILP Amplifiers are now available through Jaytee. The UK Distributor with the availability and service to match the quality of the amplifiers.

POWER BOOSTER AMPLIFIERS

The C15 and C1515 are power booster amplifiers designed to increase the output of your existing car radio or cassette player to 15 watt rms.

C15 15 watts **£10.65**
 C1515 15 + 15 watts **£19.78**

ILP LOUDSPEAKER

power 350 watt rms
 size 12 inches
 impedance 8 ohms
 range 20 Hz to 5 KHz

NEW £78.61

FOR FREE DATA PACK PLEASE
 WRITE TO OUR SALES DEPT.

PREAMPLIFIER MODULES

All modules are supplied with in line connectors but require potentiometers, switches, etc. If used with our power amps they are powered from the appropriate Power Supply.

Type	Application	Functions	Price
HY6	Mono Pre-Amp	Full Hi Fi facilities	£8.95
HY66	Stereo Pre-Amp	Full Hi Fi facilities	£14.55
HY73	Guitar Pre-Amp	Two Guitars plus Microphone	£14.95
HY78	Stereo Pre-Amp	As HY66 less tone controls	£14.25

NEW! HY83 Guitar and Special Effects Pre-Amp as HY 73 Plus Overdrive and Reverb **£18.95**

MOUNTING BOARDS: For ease of construction we recommend the B6 for HY6 **£0.95**. B66 for HY66-83 **£1.45**.

MOSFET MODULES

Ideal for Disc's, public address and applications with complex loads (line transformers etc.). Integral Heatsink

Type	Output Power Watts (rms)	Load Impedance Ω	Price
MOS128	60	4-8	£35.95
MOS248	120	4-8	£42.25
MOS364	180	4	£67.45

BIPOLAR MODULES

Ideal for Hi Fi, Full load protection integral Heatsink, slew rate 15v/μs

Type	Output Power Watts (rms)	Load Impedance Ω	Price
HY30	15	4-8	£10.95
HY60	30	4-8	£10.95
HY6060	30 + 30	4-8	£22.95
HY124	60	4	£17.95
HY128	60	8	£17.95
HY244	120	4	£23.45
HY248	120	8	£23.45
HY364	180	4	£34.95
HY368	180	8	£36.45

Distortion less than 0.01%

POWER SUPPLY UNIT

Type	For Use With	Price
PSU30	PRE AMP	£9.45
PSU212	1 or 2 HY30	£17.20
PSU412	1 or 2 HY60, 1 HY6060, 1 HY124	£19.35
PSU422	1 HY128	£21.35
PSU432	1 MOS128	£22.35
PSU512	2 HY128, 1 HY244	£23.70
PSU522	2 HY124	£23.70
PSU532	2 MOS128	£24.65
PSU542	1 HY248	£24.65
PSU552	1 MOS248	£26.65
PSU712	2 HY244	£28.35
PSU722	2 HY248	£29.30
PSU732	1 HY364	£29.30
PSU742	1 HY368	£31.25
PSU752	2 MOS248, MOS364	£31.25

All the above are for 240v operation



Jaytee Electronic Services, 143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL Telephone: (0227) 375254
 All Prices include VAT, Post & Packing

CRICKLEWOOD ELECTRONICS LTD



FREE!
catalogue

SUMMER EDITION
 HUNDREDS OF LOWER PRICES
 HUNDREDS OF NEW DEVICES

It's no secret...

...that there is a real difference at Cricklewood Electronics. That's why you should never be without the FREE CRICKLEWOOD ELECTRONICS COMPONENTS CATALOGUE, for sheer variety, competitive prices and service from the U.K.'s number one 100% component shop. No gimmicks, no gadgets or computers, just components, millions of them, all easily available by mail order, calling or credit card telephone orders. Just pick up the phone (or a pen) to get your FREE copy now (no SAE required). You have nothing to lose.

CRICKLEWOOD ELECTRONICS LIMITED
 40 Cricklewood Broadway, London NW2 3ET
 Tel: 01-450 0995/01-452 0161
 Telex: 91 4977




ETI

Interak 1

AN EXPANDABLE DISK-BASED Z80A DEVELOPMENT SYSTEM YOU CAN BUILD YOURSELF!

Universities, Colleges, Industry, Enthusiasts:

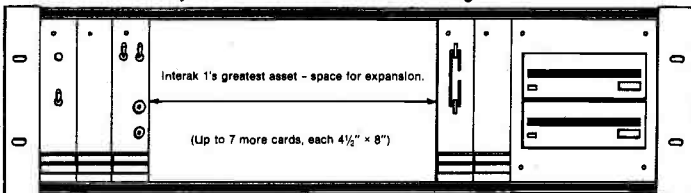Unlike home computers, development systems have entirely "open" architectures, use standard TTL etc. chips (ie no ULA's!), and are built in a proper engineering fashion. Usually these superior products carry a correspondingly superior price tag, but you can build Interak yourself board by board and thus afford a system which would normally be out of your reach and/or understanding.



The initial development system has 64K of RAM, a 4 MHz Z80A CPU, parallel ASCII keyboard interface, VDU interface (TV set or monitor), and a floppy disk drive interface for up to 4 drives. Any size (including 8" double density) can be used, but our 1 Megabyte 3.5" drives are proving very popular because they can fit into the system rack, (and they only cost £94.00 each + VAT). CP/M Plus is available, giving access to thousands of "public domain" programs.

The system can be described as "future proof" because it uses plug in 4.5" x 8" cards in an industrial quality 19" 3U rack. We have been established since 1970, and this system was first made in 1977 so (unlike almost all other computers) it has stood the test of time.

Send two second class stamps, or telephone for a detailed descriptive leaflet, specification, prices, etc.

Greenbank

Greenbank Electronics (Dept T7E), 460 New Chester Road, Rock Ferry, Birkenhead Merseyside L42 2AE. Tel: 051-645 3391

MIDI MASTER KEYBOARD

John Yau continues his musical masterpiece with a description of building the power supply and wiring the whole system together.

There is just one more PCB to make to complete the electronics of the MIDI Master Keyboard. This is the power supply board.

This month we shall also look at the construction of the keyboard cabinet and show how to wire up all the boards already constructed (the three keyswitch boards, the front panel and the CPU board) to make up the complete keyboard hardware.

The power supply is of a very ordinary design using three 78 series regulator ICs to provide the +5V supply required by all the other boards and $\pm 5V$ for the analogue to digital converter section of the CPU board.

Construction

Building the power supply PCB is straightforward. Ensure correct orientation of the bridge rectifier BR1 and all the electrolytic

HOW IT WORKS

The power supply is constructed on a single PCB and supplies all the necessary power rails for the other boards. The main +5V power rail derived from IC37 is used by the front panel PCB, keyswitch PCBs and most of the main CPU board. A separate, lower power, +5V supply rail derived from IC36, along with the -5V rail from IC38 is used to power the joystick section of the CPU board.

The three regulator circuits are extremely standard and require little in the way of explanation.

Independent supply lines for the analogue joystick circuitry ensure maximum stability and noise immunity from the digital circuitry elsewhere.

External components in the power supply circuitry are the mains transformer, fuse and the 7805 +5V voltage regulator (IC37). IC37 is bolted to the aluminium cabinet lid, which acts as an effective heatsink. Current consumption from the main +5V power rail is around 600mA, whilst the other rails draw substantially less power.

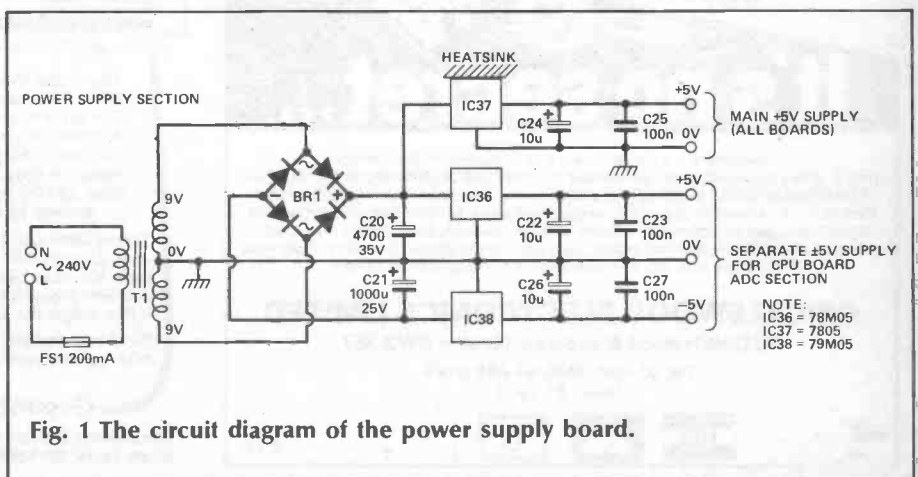


Fig. 1 The circuit diagram of the power supply board.

capacitors (especially the big ones!) as shown in Fig. 2. Mount C20 and C21 using the hole spacings on the PCB which are most suitable for the capacitors' sizes.

Solder regulators IC36 and IC38 directly onto the PCB and add a clip-on heatsink to IC36. IC37, the main 5V regulator, is to be mounted remotely to a large heatsink. In the prototype the aluminium lid of the keyboard cabinet was used for this.

Finish off the power supply PCB by adding veropins for the wire terminal points.

Cabinet Construction

Figure 3 shows the details of the cabinet used by the author in the prototype. The base is made of 1cm plywood whilst the end blocks and struts are of hardwood.

Start construction by joining the front trim to the plywood base, using a combination of wood screws and glue. Next prepare the keyboard chassis strut by cutting a recess large enough for the wiring harness to thread through on its way to the CPU board.

Position the strut on the plywood base so that the plastic notes lie just flush along the wooden front trim. Mark and join

PARTS LIST

CAPACITORS

C20	4700 μ 35V axial electrolytic
C21	1000 μ 25V axial electrolytic
C22,24,26	10 μ 16V axial electrolytic
C23,25,27	100n polyester

SEMICONDUCTORS

IC36	78M05
IC37	7805
IC38	79M05
BR1	W01 bridge rectifier

MISCELLANEOUS

FS1	200mA fuse and fuseholder
T1	9-0-9V mains transformer
PCB; mains rocker switch; clip-on heatsink for IC36; wire and cable.	

BUYLINES

None of the components used for the power supply board should provide any problems. The PCB will be available from the ETI PCB Service in due course. Details at the back of this issue.

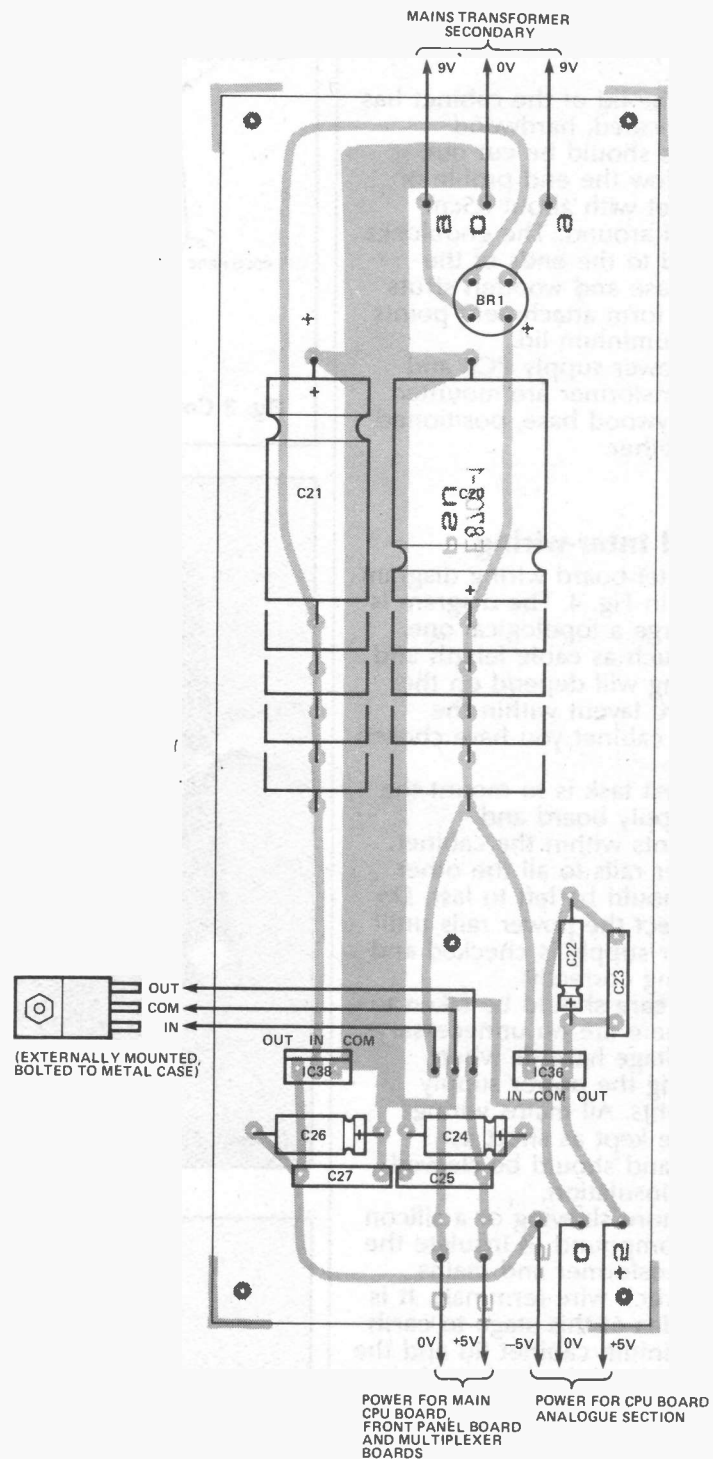


Fig. 2 The component overlay for the power supply board.

it to the base using glue and wood screws from the underside. Glue additional strutting along the join for extra strength.

After the glue has dried, fix the keyboard to the cabinet by attaching the long brass hinge along the length of the keyboard to the mounting strut. The keyboard chassis should then be

able to pivot freely about the hinge.

The lid for the prototype cabinet was made out of sheet aluminium, folded and machined to provide all the necessary holes and recesses. Both the front panel and CPU boards are mounted on the underside of the lid. The whole lid is hinged along the

edge of the plywood base using small brass hinges.

This method of mounting allows easy access to the circuit boards.

After the lid of the cabinet has been fabricated, hardwood endblocks should be cut out. These follow the end profile of the cabinet with about 0.5cm margin all around. The endblocks are joined to the ends of the cabinet base and wooden struts added to form attachment points for the aluminium lid.

The power supply PCB and mains transformer are mounted on the plywood base, positioned close together.

Board Inter-wiring

The inter-board wiring diagram is shown in Fig. 4. The diagram is by and large a topological one. Matters such as cable length and positioning will depend on the final board layout within the keyboard cabinet you have chosen or made.

The first task is to mount the power supply board and components within the cabinet. The power rails to all the other boards should be left to last. *Do not connect* the power rails until the power supply is checked and functioning correctly.

Great care should be taken to ensure there are no unnecessary mains voltage hazards when assembling the power supply components. All mains wiring should be kept as short as possible and should be sleeved for extra insulation.

Use more sleeving or a silicon rubber compound to insulate the mains transformer and mains power switch wire terminals. It is a good idea at this stage to earth the aluminium cabinet lid and the steel chassis of the keyboard.

Wire up the MIDI OUT DIN sockets to the CPU board and the footswitch sockets to the front panel PCB as shown in Fig. 4, before bolting them onto the aluminium lid. The board clearance of the Front Panel PCB should be such that the push button bank protrudes with the key caps flush with the lid.

Before finally bolting the front panel board into place, make sure the LEDs are all properly slotted into position.

Bolt the two joysticks onto the front panel and make up the wiring harness as shown in Fig. 5. Earth the two potentiometer cases as shown and use screened cable



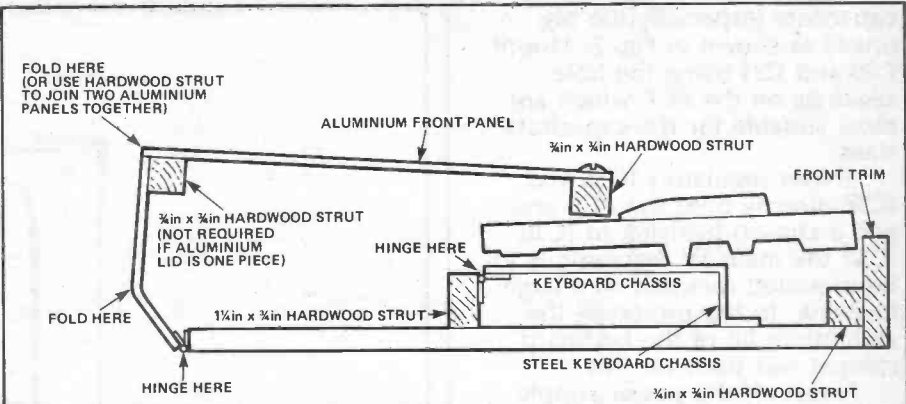


Fig. 3 Constructing the keyboard cabinet.

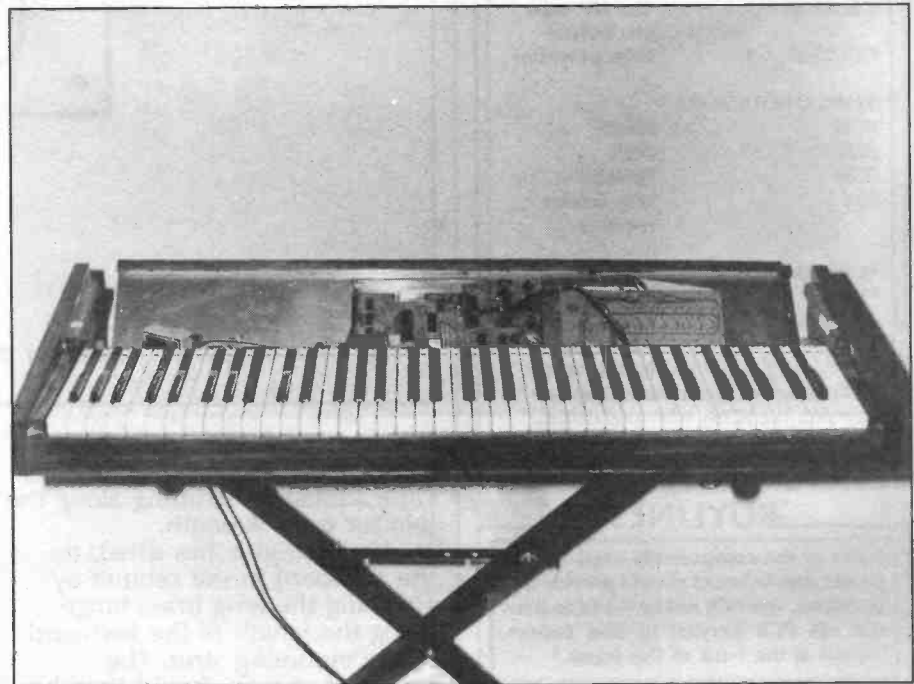

PROJECT: MIDI Keyboard

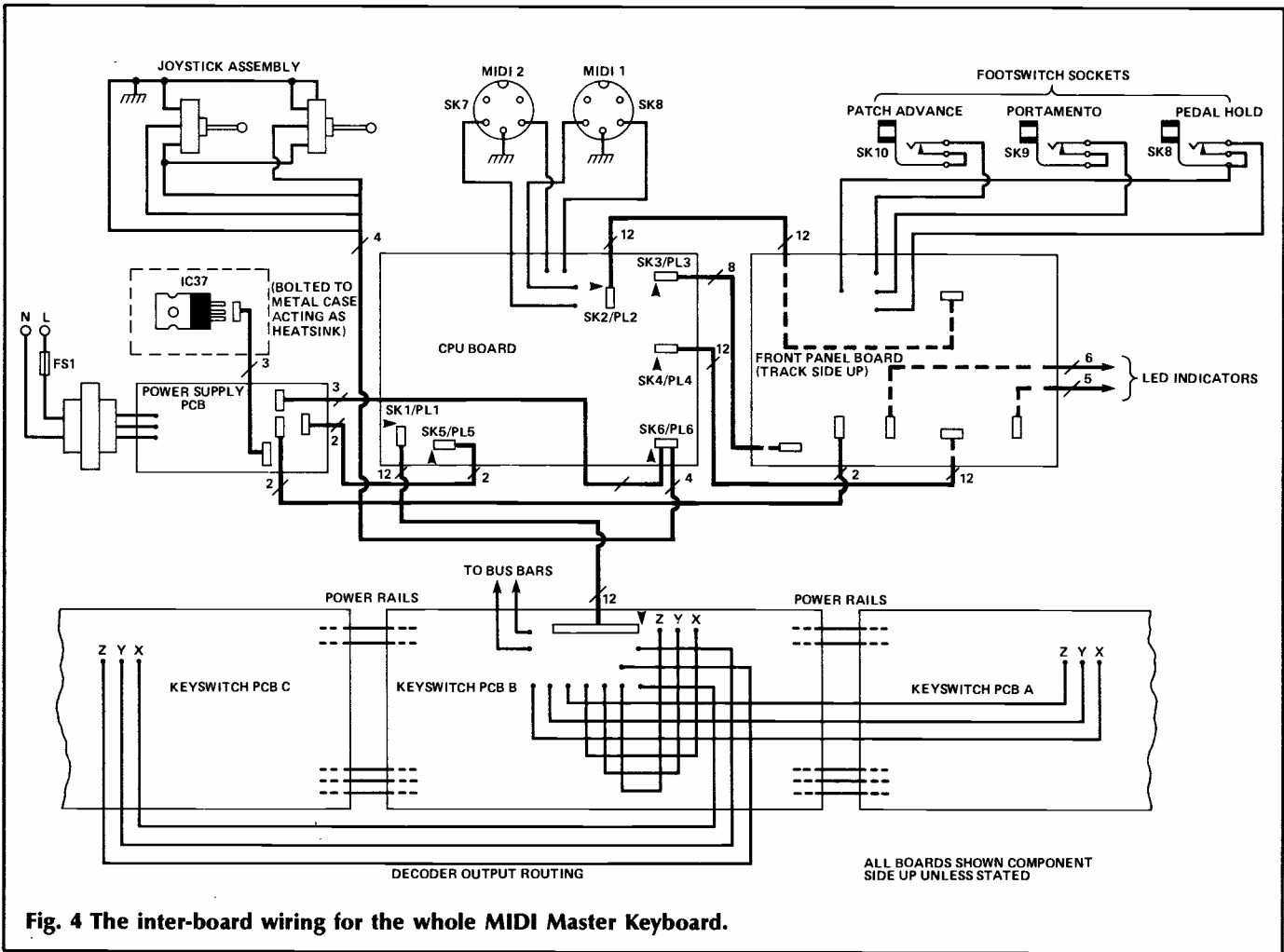


for the connections to the potentiometer wiper terminals.

Adjust the modulation joystick potentiometer so as to make the wiper voltage register 0V when the joystick lever is at its lowest point of travel. The potentiometer setting for the pitch bend joystick needs to be set so that the wiper is near the centre of the track when the joystick lever is in its neutral position. The precise position is attained later when adjusting in conjunction with the CPU board powered and operating.

All that remains is to plug all the wiring harness multi-way plugs into their respective destinations — the connectors which jump between the front panel board and CPU board and the one which links the keyswitch PCBs to the CPU board. Prepare the wiring for the power supply rails, but do not finally connect the PSU board until it has been verified that the power supply rails are functioning correctly.

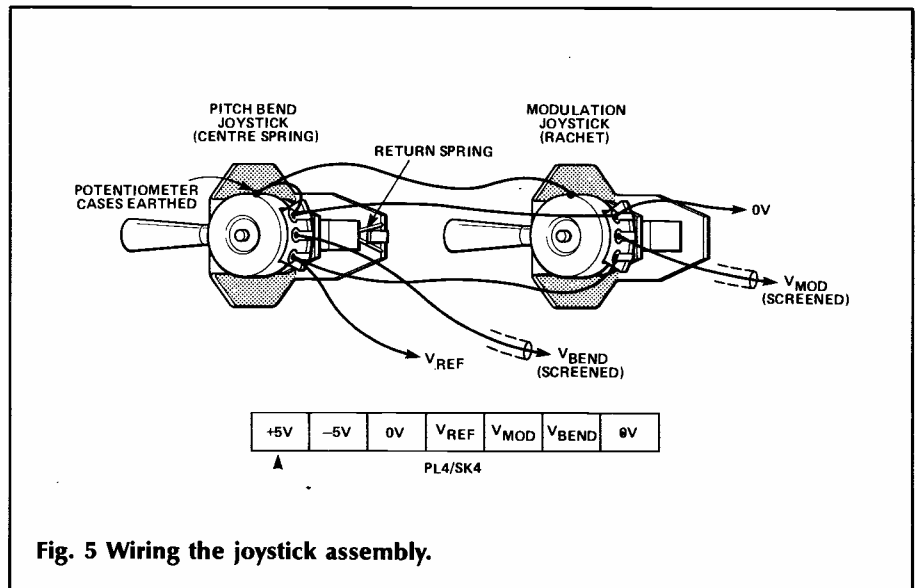Give the whole assembly a double check for correct inter-board wiring, paying particular attention to the power rail connections. Incorrectly



connected power rails are catastrophic as far as the integrated circuits are concerned!

Getting the power supply working should be fairly straight forward as very little can go wrong provided all the components are correctly orientated on the PCB. Power on the mains and check the output voltages. If they are incorrect,

switch off immediately and check everything over again. If the power supply regulators are operating properly, switch off and disconnect the mains supply before wiring the power rails to all the other boards.

Next month we shall look at the software to drive the MIDI Master Keyboard and the final setting up and testing.

TELEPHONE ALARM

Anyone breaking into Barry Taylor's house had better watch out. This unit will phone him up and tell him just what's going on.

WARNING

The Telephone Alarm was originally designed by the author for commercial manufacture and sale. However, this circuit does not have approval from the British Approvals Board for Telecommunications (BABT) and as such should not be connected to a BT line.

Nevertheless, the Telephone Alarm can legally be used with any private exchange equipment and can form the basis of a submission to BABT for approval.

Even the most sophisticated alarm has a major drawback — it is dependent on the response of passers-by to an alarm bell or siren. Many commercial premises are in self-contained industrial estates with few or no (authorised) visitors walking around after dark. Rural homes and farms can be well isolated and far from any potential help when a break-in occurs.

Moreover, given the frequency of false alarms from all systems and in all premises it is not surprising that few passers-by who do hear an alarm bell starting up in their street do more than curse.

There is clearly a need for an alternative form of alarm. Several companies offer central station monitoring systems to enable alarms to be relayed over the telephone network to a computerised control centre. However, this and the option of systems offering a direct line to the police are well beyond the scope of most pockets.

It's For You-hoo

A cheaper alternative is a unit which would dial up a pre-programmed number and give an audible warning over the telephone that it had been triggered. That is exactly what this project offers.

The Telephone Alarm will automatically dial a pre-programmed number of up to 16

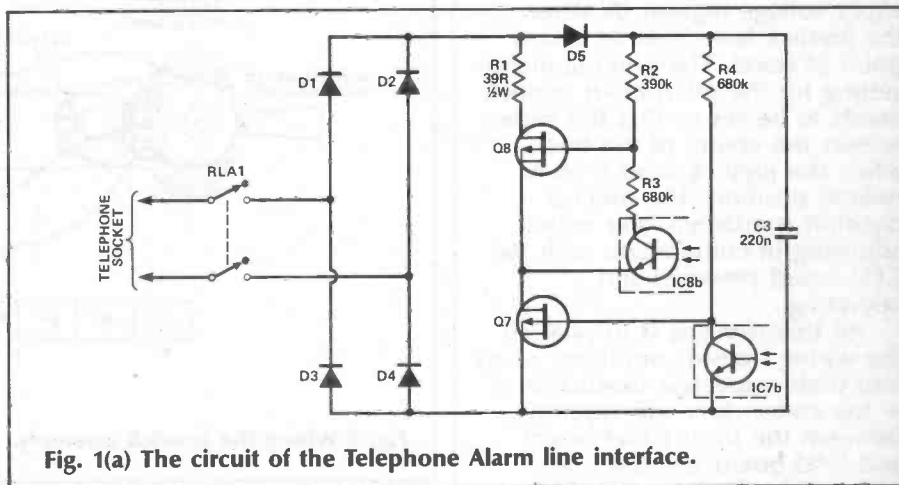
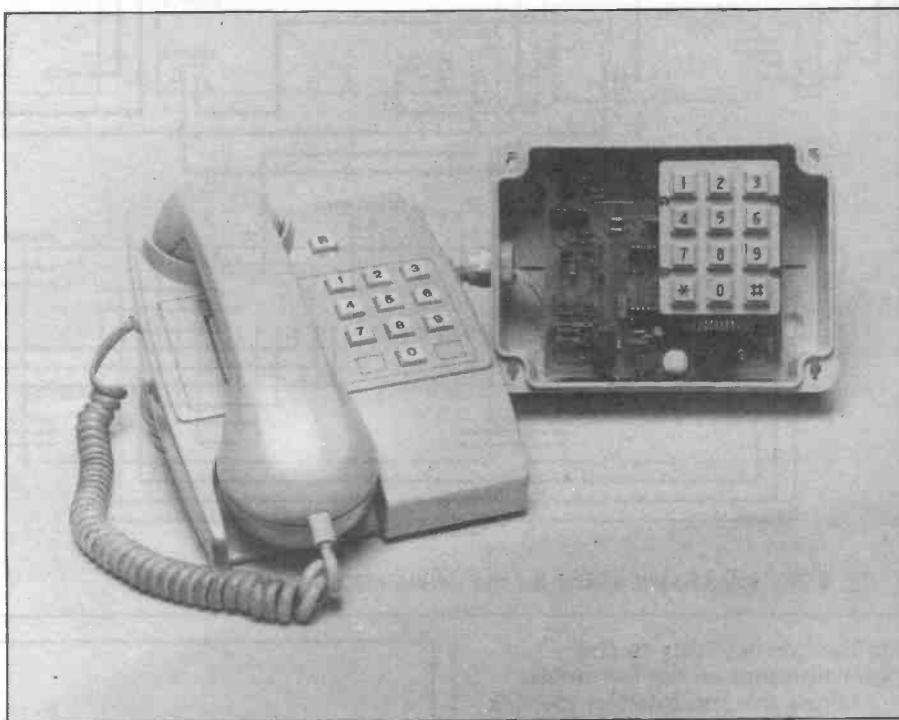


Fig. 1(a) The circuit of the Telephone Alarm line interface.

digits on activation of a set of external contacts. It will then transmit an alarm tone for about three minutes before hanging up. The unit is then automatically reset to dial again should another alarm occur.

Naturally, you may be so far away as to not be able to take useful direct action yourself. However, you can call the police

(or a neighbour) and rest assured that the alarm has been well and truly raised.

The Telephone Alarm is not only suitable for telling you if your home or business is being burgled. Other uses, less criminal but just as vital to your piece of mind are also possible:

- fire alarm (combined with smoke and heat detectors)

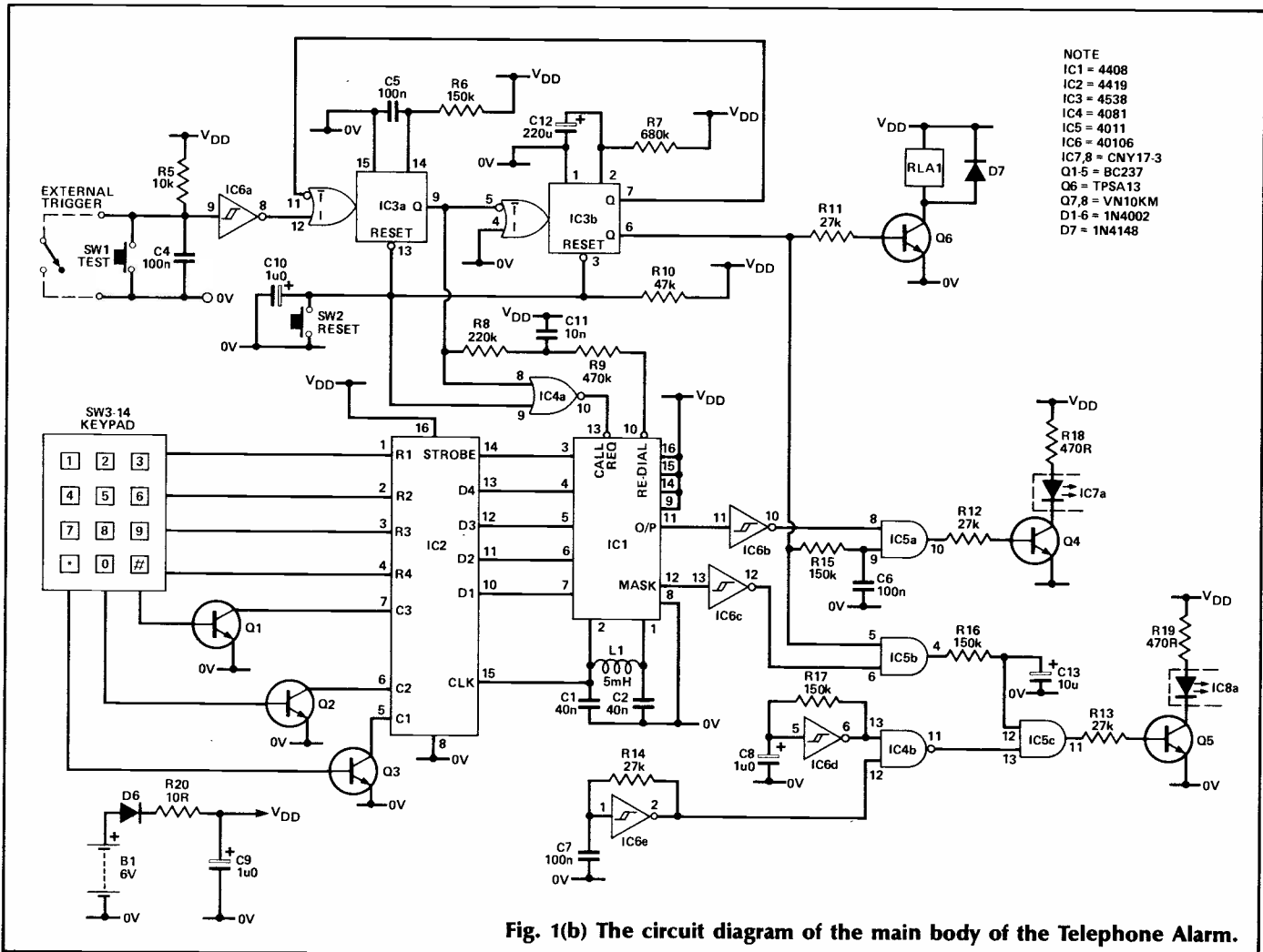


Fig. 1(b) The circuit diagram of the main body of the Telephone Alarm.

HOW IT WORKS

The full circuit of the Telephone Alarm is shown in Fig. 1. The line interface uses VMOS FETs (Q7,8) to make and break the telephone line loop to dial the number and to produce the alarm tone.

The diode bridge (D1-4) ensures that the correct polarity is observed across the FETs. When RLA1 operates the unit is connected to the telephone line and 50V from the line appears across the bridge. This turns on both FETs and completes the loop circuit.

Q7 is turned off and on via optoisolator IC7 to dial the number. Q8 is pulsed on and off via IC8 to produce the audio tone.

At the heart of the main body of the circuit is IC1. This is a MC14408 phone pulse converter. This IC was chosen because it can be made to re-dial simply by taking pin 10 low.

Pins 14 and 15 are permanently tied high to configure the IC for the UK standard of 33% mark-to-space ratio for the dialling pulses and an interdigit time of 800ms. The on-board oscillator is set for 16kHz by L1, C1 and C3 to enable a pulse rate of ten per second.

When a valid key is pressed, the keypad encoder (IC2) outputs a strobe

signal on pin 14 followed by the BCD value of the key number on pins 10 to 13. IC1 then pulses out this number on pin 11 (with ten pulses output for key zero) and stores the value in memory. IC5 prevents the number being simultaneously dialled when the unit is being programmed.

When the trigger input is closed it causes pin 8 of schmitt inverter IC6 to go high triggering the monostable IC3a. Pin 13 of IC1 (call request) is then momentarily taken low followed by a low on IC1 pin 10 (re-dial).

The monostable IC3b turns on relay RLA1 for three minutes to connect the unit to the phone line and enables the dial and tone pulses through to the optoisolators via IC5a and IC5b. IC3b also prevents further triggering of the unit by disabling IC3a pin 11.

The two schmitt trigger oscillators formed around IC6d and IC6e make up the alarm tone generation circuitry. This is inhibited by IC5b and IC5c from reaching the optoisolator IC8 by the mask output from IC1 while dialling is in progress. The alarm tone is then transmitted to the line via IC8 and Q8.

- freezer alarm (to warn of the imminent loss of the Sunday roast)
- flood alarm (for burst pipes and faulty tank ballcocks)

All the applications of the Telephone Alarm require some extra circuitry. In the case of the burglar alarm, simple detectors (window switches, pressure mats and so on) can be directly connected to the unit.

Many other commercial detector devices can be connected to the unit if they have a switched output and of course your own triggering devices can be designed and used with the Telephone Alarm. However, note that no voltage should be presented to the trigger input.

The Phone

Two wires are provided from the telephone exchange to each house or subscriber. These are used for carrying the audio tones, the ringing tone and dialling signals to the exchange.

The exchange is informed that the subscriber wishes to dial by completing the circuit between the two wires. The loop circuit is then broken in a series of short

pulses to signal the number being dialed.

When the exchange has then connected the call to the intended destination, the line appears as a 600ohm balanced line for the audio signals.

The Telephone Alarm circuit is in two sections — the line interface and the main body of

the circuit. These are electrically isolated from one another by opto-isolators. The main body of the circuit is powered by a battery supply although a simple mains power supply could be added to the circuit. The line interface derives its power from the telephone line.

When triggered, the main

body of the Telephone Alarm circuitry produces the correct sequence of making and breaking the telephone line loop to dial the number and then produces an audio tone to signal down the line that the unit has been triggered.

PARTS LIST

RESISTORS (all 1/4W, 5% unless specified)

R1	39R 1/2W
R2	390k
R3,4,7	680k
R5	10k
R6,15-17	150k
R8	220k
R9	470k
R10	47k
R11-14	27k
R18,19	470R
R20	10R

CAPACITORS

C1,2	40n polyester
C3	220n 100V polyester
C4-7	100n polyester
C8-10	1µ 63V axial electrolytic
C11	10n ceramic
C12	220µ 63V axial electrolytic
C13	10µ 63V axial electrolytic

SEMICONDUCTORS

IC1	4408 or MC14408
IC2	4419 or MC14419
IC3	4538
IC4	4081
IC5	4011
IC6	40106
IC7,8	CNY17-3 opto-isolator
Q1-5	BC237 or BC337
Q6	TPSA13 or MPSA13
Q7,8	VN10KM or VN10LM
D1-6	1N4002
D7	1N4148

MISCELLANEOUS

B1	6V (4 x 1.5V) battery
L1	5mH coil
PL1	7 way 0.1in PCB connector (male)
RLA1	DPDT, 5V coil DIL relay
SK1	7 way 0.1in ribbon cable connector (female)
SW1,2	SPST push button switch
SW3-14	12 switch keypad 4x3 matrix type
PCB; 2-way and 4-way terminal blocks; telephone lead type 431A; case.	

BUYLINES

The keypad matrix of 4x3 keys used in the prototype is available from MS Components as part number 7331. MS can also supply the relay as part number 8041. MS Components is at Zephyr House, Waring Street, West Norwood, SE27 9LH. Tel: 01-670 4466.

The opto-isolators (IC7,8) used were CNY17-3 types but any six pin opto-isolator which can withstand a Vce of 50V or more should be adequate.

IC1 and IC2 are available from Watford Electronics (Tel: (0923) 377774).

The case used for the prototype was from Legrand although any suitably sized metal or plastic case will do. None of the other components should be difficult to find.

The PCB will be available from the ETI PCB service in due course.

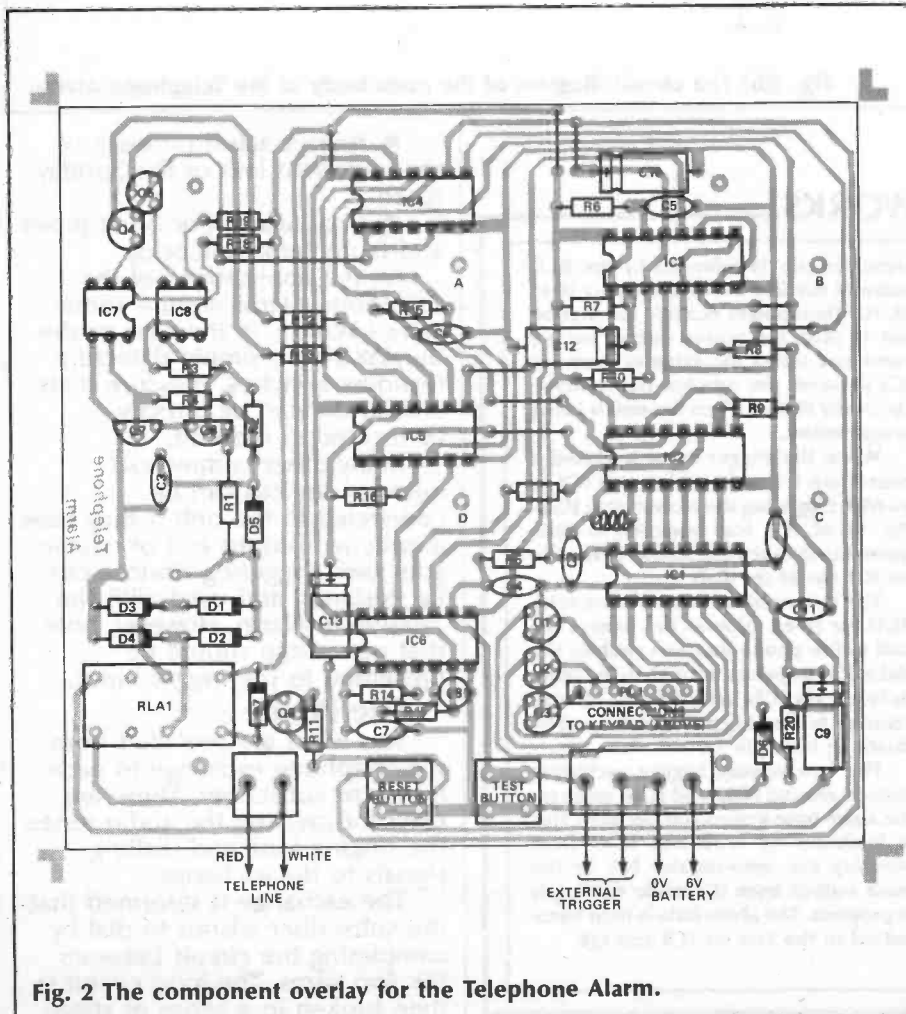
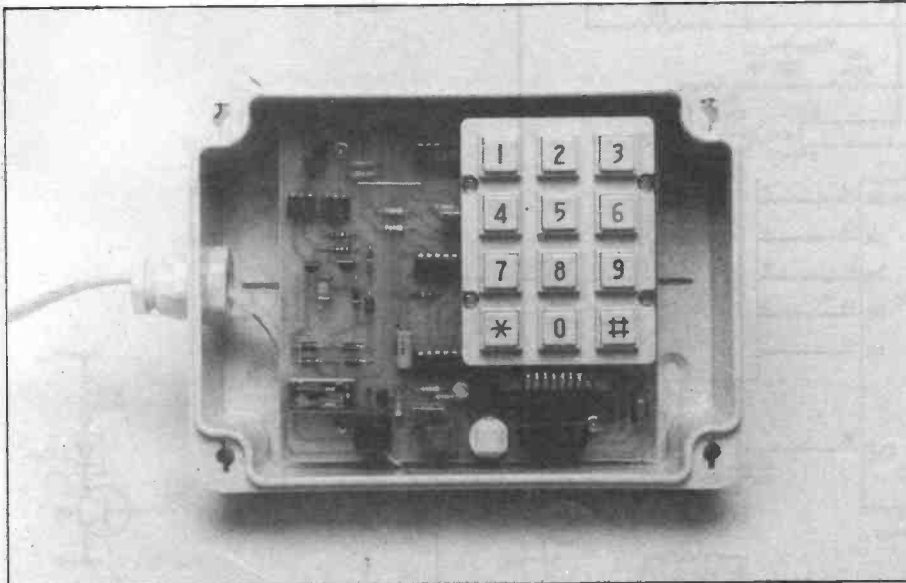


Fig. 2 The component overlay for the Telephone Alarm.

PROJECT: Telephone Alarm

Construction

Figure 2 shows the component overlay for the Telephone Alarm PCB. All the ICs used are CMOS types and should be treated with the normal respect reserved for these static-sensitive devices. The usual care should also be taken to ensure the diodes and electrolytic capacitors are inserted the correct way around.

It is recommended that terminal blocks are used to connect the trigger input, the battery and the phone line itself (see Fig. 3).

The keypad should be connected last of all the components. The keypad used for the prototype (see the parts list) is mounted above the PCB on spacers secured to the PCB through the holes, A,B,C and D. The ribbon cable from the keypad is terminated with a seven way connector which is plugged onto the connector on the main PCB.

The keypad can also be mounted in the lid of the case for easy alteration of the programmed number.

You can make up your own keypad as shown in Fig. 4 on a piece of stripboard. The switches used can be any single pole, push to make buttons such as keyboard switches.

Only the switches for the numbers 0 to 9 are actually required for the Telephone Alarm. Many commercial keypads also

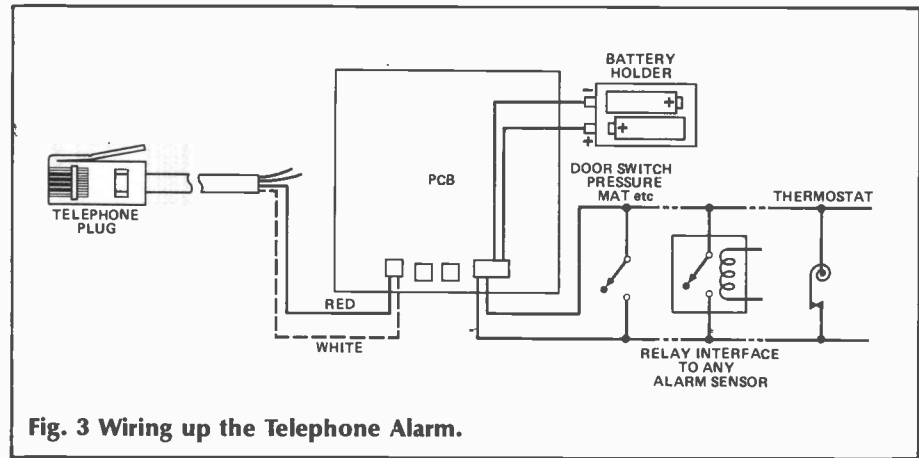


Fig. 3 Wiring up the Telephone Alarm.


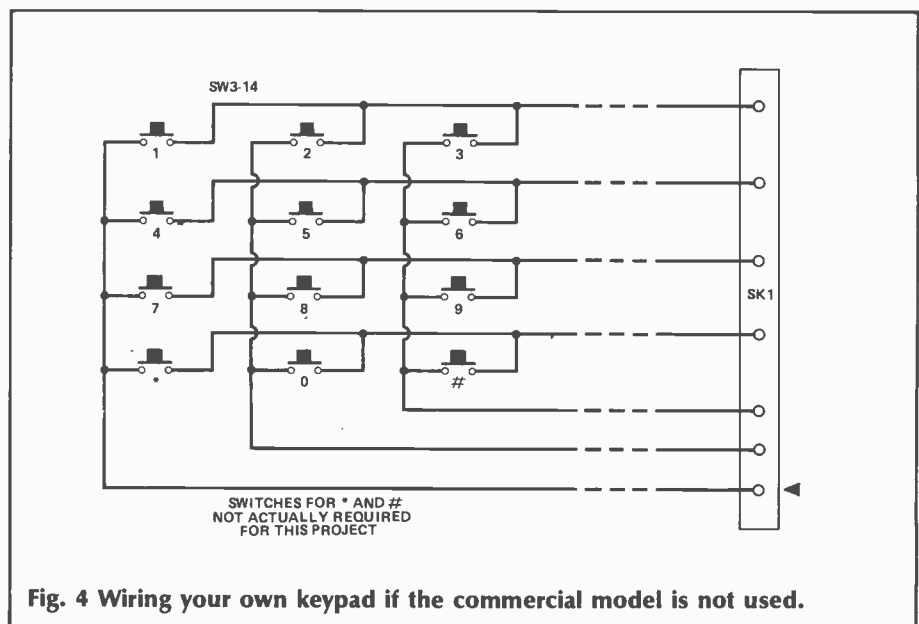


Fig. 4 Wiring your own keypad if the commercial model is not used.

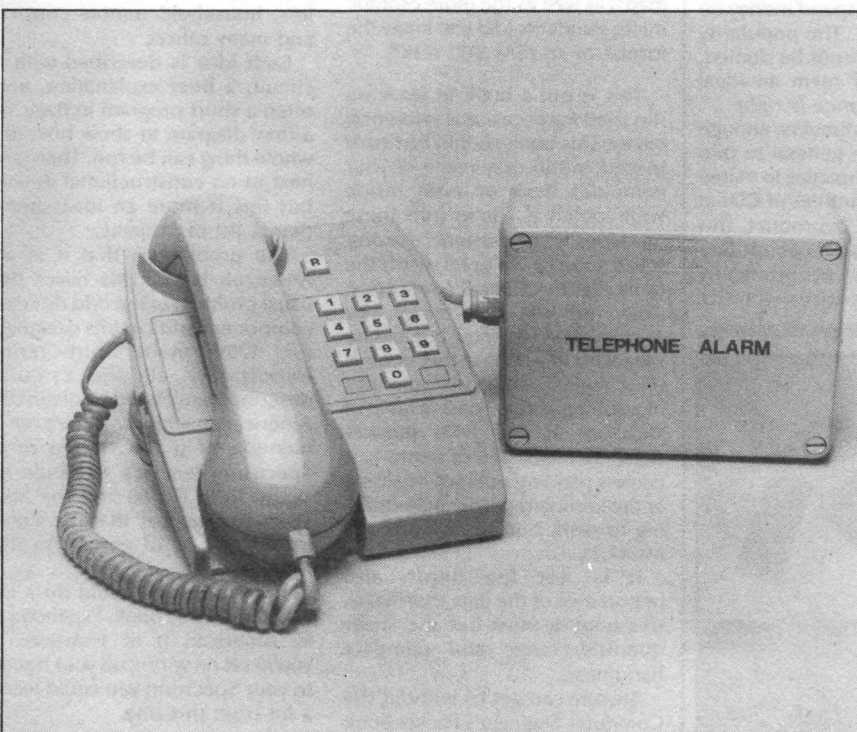





have the * and # keys found on most push button telephone keypads. The Reset and Test buttons could occupy these positions on a keypad of your own making.

Operation

The Telephone Alarm is very simple to use. The number to be dialled when the unit is triggered is programmed using the keypad and the Reset button. After the Reset button is pressed the number to be dialled (up to 16 digits) is then keyed on the keypad.

If either the Test button is now pressed or the trigger input circuit is closed the unit will dial the programmed number and sound a tone down the telephone line for approximately three minutes before hanging up and resetting the whole system.

PLAYBACK

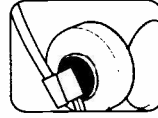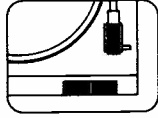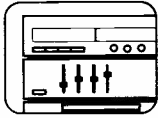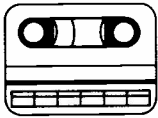

After loudspeakers, I reckon that room acoustics have the greatest effect on the sound of good quality systems. Graphic equalisers can correct some room acoustic problems but I suspect most people use them to provide their own particular idea of what the sound colour should be.

It can be difficult to detect and null out room resonances but when you do remove a serious resonance there is less 'listener fatigue' even though the difference may not be easy to pin down at first.

All this leads me to speculate on some possible future developments. Some CD recorders nowadays have digital outputs, for connection to an external DAC (digital to analogue converter) to reduce the already minuscule noise and distortion on the original.

As microprocessing speed increases, this opens the door to the possibility of having a programmable digital room equaliser, running a high order digital filtering algorithm in up to 32 bits.

Such a microprocessor equaliser could automatically run white noise tests on the system and compute an accurate correction function. By sending many and varied test signals to each channel in turn, it could even provide a digital correction for some system non-linearities, effectively determining what distorted signal has to be fed to the loudspeakers to produce a sound equivalent to the original signal source. The amplifier may occasionally be called on to perform crazy contortions but that is no problem.

If the microprocessor equaliser was actually a computer with a colour monitor, the user could superimpose his own chosen tone correction on to the equaliser characteristic by sketching it on the screen using a mouse or lightpen. A menu of different corrections could be stored and accessed at the touch of a key.

Sound And Vision

You may wonder why I specified a colour monitor. Well, those clever chaps at Phillips are extending the CD medium to include a development of their old Laserdisc system. This was always technically excellent but it was not what the market had in mind at the time. Their new development will enable five minutes of sound and video plus twenty minutes of

sound alone to be encoded on a CDV (CD Video) the same size as a conventional CD. In addition there will be 8in extended play and 12in long play discs, and combination players will be available to play all sizes. Surely a colour computer monitor could also display the CDV pictures and form an integral part of a future audio/video system.

On the 5in CDVs (which look like ordinary CDs except for the gold dye in the plastic) the video information is coded on the outer area where the scanning speed is greatest. A linear speed of between 9.2 and 10.2 m/s is used for PAL video, with NTSC requiring slightly higher rates. To keep the scanning rate correct as the scanned diameter varies, the rotational speed varies from 1512 to 2250RPM.

Audio compact discs have worldwide compatibility but not so the video ones. There is no worldwide video compatibility, you see. They have, however, retained compatibility with the old Laserdiscs, so that they will play on the new players. Laserdiscs used an analogue FM sound system, but the new CDVs use (of course) digital sound.





Whether CDV will catch on remains to be seen. I think it is more likely to suit the market than Laservision ever was and maybe more people will spend money on this than on DAT. The popularity of pop videos cannot be denied, and CDV would seem an ideal medium, if the price is right.

CDV may also stimulate enough interest in CD in general to persuade record companies to manufacture larger quantities of CDs at lower cost. As a byproduct, this may calm the hysteria about DAT making it less economically attractive in comparison with CD.

Andrew Armstrong



BOOK LOOK

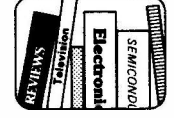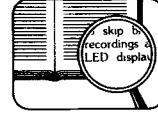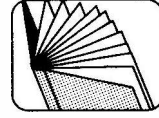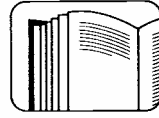

Newnes Computer Engineer's Pocket Book by Michael Tooley (Heinemann) £8.95

Computer Peripherals That You Can Build by Gordon W Wolfe (John Wiley & Son) £15.30

At last Newnes (now part of William Heinemann publishers) has produced a version of the run-for-ever Electronic Engineer's Pocket Book exclusively for the computer enthusiast or professional.

This is the first edition of this computer version but it looks like there will be many more. This one will (as they say) run and run.

The pocket book is basically a reference work. No enrapturing bedtime reading here. What there is, is just about everything you could want to know about computer hardware. Within these pages is condensed data on most of the common processors and support chips, interface standards, operating systems, typical video waveforms, and so on (and on and on).

The pocket book is in the usual Newnes format of a long thin hardback about 8in by 3½in and around 200 pages long. Into these pages is crammed masses of information. The contents page has over 80 headings!

The information ranges over a wide area. The most basic electronics is covered (items such as TTL pin-outs and Karnaugh maps) as well as the more esoteric micro standards (did you know the format of an IBM 3740 disk?).

This is not a book to leave on the shelf for occasional reference, either. This book should be firmly placed within easy reach of your computer desk or even inside your toolkit if you're into these machines for professional reasons. It will soon prove to be worth the (only slightly inflated) cover price.

It's not just the 'things you always wanted to know but had no idea who to ask' that this book is filled with. There is vast quantities of seemingly trivial data (a table of 'divisors of 256 with remainders'...). Much of this seems just useless padding until you're sitting at the keyboard desperately straining to work out just what is 256 MOD 21.

It is not the depth and importance of the data that makes this book a must but the sheer quantity, range and compact handiness.

Anyone can get by without the Computer Engineer's Pocket Book but why take the hard way out?

Not a cheap one this, mainly because it comes all the way from the USA. This one's a big book, too — around 280 pages.

The biggest problem facing anyone with a home computer (after they have finished playing the games and 'learning about computers') is what the hell to do with it. It's depressing but true that most micros don't spend time doing anything useful at all.

The *raison d'être* often quoted is control, automation, and the like. Now it is probable that few if any of the proponents of these claims actually do anything about them themselves. Nevertheless, they leave lots of folk out there wanting to connect up their machines to anything and everything available.

Having got that off my chest, I must say that even if the idea is a little dubious, this book approaches the whole matter in a logical and instructive way. Not a lot of knowledge is assumed at the start but the book covers an amazing amount of ground.

It starts by describing exactly what a computer is and 200 pages later it's showing how to make a flatbed plotter. In between there's paper tape readers, servo controllers, household remote control, and many others.



Each idea is described with a circuit, a brief explanation, and often a short program in Basic or a flow diagram to show how the whole thing can be run. There are next to no constructional details but this is more an ideas book than a list of projects.

The problem is that it is an American book. This raises the usual problem of the odd difficult component and circuits designed for 120V mains but more importantly all the circuits described are aimed at distinctly American machines. There's not a mention of a BBC micro or a Spectrum here. It's all Apple II, Tandy 1000, TRS-80 and the like. The good news is that the Commodore 64 is, of course, to the fore.

That aside, you could do a lot worse than this book. Expensive it is. American it is. However, if you're set on wiring up your house to your Spectrum you could learn a lot from this one.

Malcolm Brown

KEYNOTES

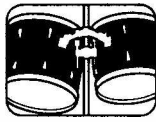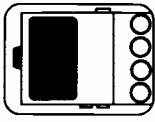

So far, 1987 has proved to be a dull year with regard to innovations in music technology. In fact, it is difficult to pinpoint any real innovations and, although the year is only half gone, we shall probably be forced to wait until the next NAMM and Frankfurt trade shows (in January and February respectively) to see anything original emerge.

The question is will the story be the same in 1988 too? Some people are already speculating that the electromusical instrument market may be flattening out from its previously high rate of growth or, in plainer terms, plunging into a recession not unlike the one that began hitting the semiconductor industry several years ago. The symptoms are exactly the same — prices stay fixed and new developments get shelved due to the high cost of R&D.

The cause might be put down to an increasing saturation of a finite market with cheap keyboards designed to make MIDI, not music. The result may ultimately be for such machines to paint themselves into the dark and sullen corner of obsolescence with the disgraceful lack of standardisation of the MIDI protocol as their suicidal paintbrush.

Signs of middle-aged flatulence are already in evidence and it is intriguing to compare the so-called new developments of 1987 with the music trends of our time. Old machines are being repackaged in new boxes at the same rate with which club remixes are remixed and cover versions are recovered. Furthermore, manufacturers are currently stealing ideas off each other to a degree that puts the 'sample before you get sampled' ethic of Hip-Hop to shame.

Take Sequential Circuits' Vector Synthesis technique, in which four sounds derived from digital wave-tables are mixed under the control of a joystick with X-axis position controlling balance between two sounds and Y-axis position controlling balance between the other two. To be fair, this is a very useful and ergonomic feature, beautiful in its simplicity, but by the same token scarcely deserving of a name as convoluted as Vector Synthesis. With respect to originality, the technique was possible on many modular analogue synths, not unknown on DJ's mixing desks and not very dissimilar to the soundfield control joysticks found on quadrophonic equipment.

Sequential knew their re-discovery would be nicked in due course and trade-marked Vector Synthesis (no doubt patented it also) in order to make the villain's life more difficult.

Undeterred, stray dog Roland went rummaging in the dustbins and came out with a bone — Linear Arithmetic Synthesis, whereby only two sounds are mixed by means of a joystick. Boffins with lightbulbs over their heads will immediately realise at this point that joystick technology could even be extended to the control of a single sound. Maybe I shouldn't be giving Roland ideas!

FM Rules OK!





The greatest disappointment of the year is undoubtedly Yamaha's long awaited sequel to the DX7. The original DX7 made such an impact on the music world that we might reasonably have expected a follow-up to be the last nails in the coffins of their competitors but that would be overlooking the obvious. The philosophy behind the DX7 II is that if a machine is selling well then there is no point in changing it — just add a few embellishments and increase the price!

Korg has fixed up a corporate deal with Yamaha which apparently allows them to reap the benefits of Yamaha R&D. The first visible result of this deal is Korg's new DS8, a DX7 clone with an original feature: on power-up, the LCD greets you with 'Welcome to Synthworld!'

Casio's Phase Distortion is essentially identical to Yamaha's FM (which is actually phase modulation and not FM at all), except the waveforms which do the modulating or get themselves modulated are not necessarily sine waves (as on the DX7). This was a dodge for getting around patent legislation and, predictably enough, Yamaha has in its turn torn a page out of Casio's book with the introduction of the TX81Z expander — a keyboardless synth designed to be controlled by MIDI, usually housed in a 19in rack-mount case. This machine replaces their marginally popular and somewhat limited FB01 (production of which has ceased) and simultaneously provides Yamaha with the opportunity of incorporating a choice of eight operator waveforms. All one can say is that honour among thieves is a thing of the past.

Bruno Hewitt

OPEN CHANNEL

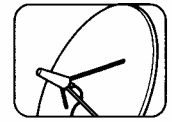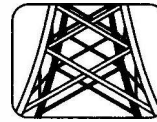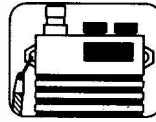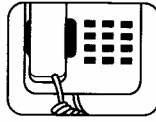

Today, I took delivery of my new Mercury telephone. I ordered it less than a week ago from Mercury Communications Ltd, having made a few rough calculations based on the use of my telephone.

I will be able to use this telephone to connect me to the Mercury 2200 telephone network which now has some 59 access areas. The latest expansion incorporates my address.

Eventually, of course, the whole country will be covered but meanwhile it's worth checking with Mercury (the customer assistance number is 0800 424 194 and no charge is made by BT for your call, incidentally) to see if you live in one of the current access areas.

The savings in telephone charges by using Mercury 2200 can make the enquiry well worthwhile. For example, a standard rate trunk call via BT can cost around 12p per minute, whereas the same call via Mercury 2200 is less than 9p per minute.

Alternatives

Mercury's alternative telephone network to British Telecom's is, unlike BT's, only a trunk network. In other words, you can't use the Mercury network to dial a local call. (In fact, this not *strictly* true — it is possible to use the Mercury 2200 network to make local calls by routing them out of the local area onto the trunk network then back into the local area but then it costs more than a BT local call anyway, so it's not worth the bother). So, to make a local call you must still be connected via a local line to the BT network.

However, any calls made which are longer distance and must be connected via a trunk network, can now be made via BT or Mercury. I have a choice of telephone networks for the very first time! At least, I *will* have a choice of network, when BT finally gives me a new socket.

Apart from a choice of network on trunk calls, I have a choice of prices. Needless to say Mercury's prices generally undercut BT's somewhat. As most of my calls are long distance, I calculate I will make savings of at least £70 per year by making all my trunk calls using my Mercury telephone.

I applied to BT to have their engineers call and fit me a new socket some seven weeks' ago. At the time, I was told that a date *eleven weeks after that* was the earliest possible appointment to

do the simple job — and telecommunications in Britain are supposed to be liberated?

Do you think BT will pay up if I send them a bill for £14.80 (which is 11/52 x £70), to make up for the lost savings in telephone charges which their slow service has caused me?

Looking At A Problem

Users of, potential users of or even just parties interested in, optical fibre communications would do well to get a copy of a new booklet published by BICC Electronic Cables Ltd called 'UFO's Explained'.

The UFO's in question are 'unidentified fibre optics'. The booklet is a well thought out, well written, and well put together tome (no, I had nothing to do with it!) which starts at the beginning and ends at the end of the topic (shouldn't they all?). Somewhere in the middle is also a pretty fair description of optical fibre technology, in a non-technical yet thorough manner.

BICC has obviously seen that one problem in getting Joe Public to use optical fibres is the sheer reluctance to get to grips with the technology. Most people believe it to be too expensive and too technical for general cabling purposes. 'UFO's Explained' goes a long way to sorting this problem out.

A free copy of the booklet can be had from BICC Electronic Cables, Optical Fibre Technology Unit, Helsby Works, Helsby, Warrington, WA6 6BR. Tel: (09282) 2700.

TDF's DBS

French broadcasting body, Tele-diffusion de France, intends to launch the country's first direct broadcasting satellite (DBS) later this year. Problems have arisen in the satellite's launch, not because the satellite was not ready but because the launch rocket (Ariane) has been grounded following its failure some time ago.

However, now Ariane's technical problems appear to have been overcome and launch dates are currently being tentatively mooted.

Meanwhile, it has been reported that Germany's DBS satellite launch, although agreed to have been via Ariane, will instead go ahead on a Chinese or Russian rocket if further problems with Ariane occur.

Keith Brindley

ETI PCB SERVICE

Build your projects in style with a properly designed PCB.

Use the form below (or a photocopy) for your order. Please fill in all parts of the form.

The board reference number tells you when the PCB foil was published. The first two numbers are the year and the next two the month. The number after the dash indicates the particular project in that issue.

The terms are strictly cash with order. Make cheques payable to ASP Ltd. We cannot accept official orders but we can supply a pro-forma invoice if required. Such an order will not be processed until payment is received.

Orders can also be made by telephone on (0442) 211 882 for Access and Visa card holders.

Please allow 28 days for delivery.

Price Code	Price (inc VAT) £
C	1.80
D	2.50
E	3.23
F	4.00
G	4.75
H	5.50
J	6.62
K	7.20
L	8.80
M	10.60
N	13.10
O	15.80
P	17.90
Q	21.80
R	23.90
S	25.90
T	29.00
U	32.20
V	35.80
W	37.90
X	40.70

TO: ETI READERS' SERVICES DEPARTMENT
Argus Specialist Publications Ltd,
9 Hall Road, Hemel Hempstead,
Herts HP2 7BH

Please supply:

No. required per type	Board reference number	Price letter	Price each £	Total for board type £
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p
	E	-	£ . p	£ . p

POSTAGE & PACKING £ 0.75p

TOTAL ENCLOSED £ . p

ORDER TO BE SENT TO: (BLOCK CAPS PLEASE)

Name

Address

Postcode


(Make cheques payable to ASP Ltd)

ACCESS and VISA credit card orders can be taken on (0442) 211 882 (office hours only).

- E8107-1 System A Disc Input bd MC-MM..... F
- E8107-2 System A Preamplifier Main ... K
- E8108-1 System A Power Amp L
- E8109-2 System A PSU F
- E8201-2 Infant Guard C
- E8202-5 MM Stage Disc Preamp (Tilsbrook) G
- E8206-5 Logic Lock F
- E8208-1 Playmate Practice Amp 3bds SA1 K
- E8212-1 ELCB F
- E8301-2 Analogue to digital conv (ZX81/Spectrum) E
- E8305-3 Dual Audio Power Supply, Linsley Hood G
- E8305-5 Balanced Input Preamplifier F
- E8307-2 Flash Trigger-sound or FR F
- E8308-1 Graphic Equaliser 1/2 Oct/Chnl M
- E8308-2 Servo Fail-safe C
- E8309-1 NICAD Charger/Regenerator F
- E8310-3 Typewriter Interface - EX42 ... F
- E8311-1 Mini Drum Synth F
- E8311-8 Moving Coil Pre-Preamp F
- E8312-3 Light Chaser EPROM Controlled (2 Boards) K
- E8402-1 Speech Board M
- E8402-2 Modular Pre-amp Disc Input Mono F
- E8402-3 Modular Pre-amp Stereo Output F
- E8402-4 Modular Pre-amp Relay, PSU F
- E8402-5 Modular Pre-amp Tone Main Mono F
- E8402-6 Modular Pre-amp Tone Filter, Stereo F
- E8402-7 Modular Pre-amp Balanced Output F
- E8402-8 Modular Pre-amp Headphone Amp F
- E8404-2 Mains Remote control Receiver F
- E8405-1 Auto Light Switch F
- E8405-2 ZX81 EPROM Programmer... N
- E8405-3 Mains Remote Control Transmitter H
- E8405-4 Centronics Interface F
- E8405-6 Drum Synth F
- E8406-1 Oric EPROM Board O
- E8406-2 Spectrum Joystick E
- E8406-3 Audio Design RIAA Stage G
- E8406-4 AD Buffer/Filter/Tone H
- E8406-5 AD Headphone Amp F
- E8406-6 AD Preamp PSU K
- E8406-7 AD Power Amp H
- E8406-8 AD Power Amp PSU J
- E8406-9 AD Stereo Power Meter F
- E8406-10 AD Input Clamp C
- E8407-1 Warlock Alarm M
- E8408-2 EPROM Emulator N
- E8408-3 Infrared Alarm Transmitter ... E
- E8408-4 Infrared Alarm Receiver F
- E8409-1 EX42 Keyboard Interface F
- E8409-2 Banshee Siren Unit F
- E8410-1 Echo Unit F

E8410-2 Digital Cassette Deck N
E8410-3 Disco Party Strobe H
E8411-5 Video Vandal (3 boards) N
E8411-6 Temperature Controller D
E8411-7 Mains Failure Alarm D
E8411-8 Knite Light D
E8411-9 Stage Lighting Interface F
E8411-10 Perpetual Pendulum E
E8412-1 Spectrum Centronics Interface
..... F
E8412-4 Active - 8 Protection Unit F
E8412-5 Active - 8 Crossover F
E8412-6 Active - 8 LF EQ F
E8412-7 Active - 8 Equaliser F
E8501-3 Digital Delay (2 boards) T
E8502-1 Digital Delay Expander N
E8502-2 Data Logger J
E8503-1 Combo Preamplifier F
E8503-2 THD Meter mV & oscillator
bds (2 boards) K
E8503-3 THD Meter Mains PSU F
E8504-1 Framestore Memory M
E8504-3 Framestore Control N
E8504-4 Buzby Meter E
E8504-5 CCD Delay F
E8505-5 Stereo Simulator F
E8506-1 Audio Mixer Main J
E8506-2 Audio Mixer PSU F
E8506-3 Audio Mixer RIAA D
E8506-4 Audio Mixer Tone Control ... D
E8506-5 EPROM Prog MKII O
E8508-1 RCL Bridge N
E8508-2 EX42/BBC Interface E
E8508-3 EPROM Emulator L
E8509-1 Spectrum F
E8509-2 Direct Injection Box E
E8510-9 Sunrise Light Brightener K
E8511-1 MTE Waveform Generator ... H
E8511-2 Millifaradometer H
E8511-3 Cymbal Synth J
E8511-5 Chorus Effect H
E8511-7 Enlarger Exposure Meter F
E8511-8 Switching Regulator E
E8511-9 Second Line of Defence M
E8512-1 Specdrum connector F
E8512-2 MTE Pulse Generator H
E8511-3 Specdrum L
E8601-2 Walkmate L
E8601-3 MTE Counter-timer M
E8602-1 Digibaro O
E8603-2 Programmable Logic Evaluation
Board H
E8603-3 Sound Sampler Analogue
Board R
E8604-1 JLLH PA PSU H
E8604-2 Matchbox Amplifier C
E8604-3 Matchbox Amp Bridging
Version C
E8604-4 MTE Analogue/Digital
Probe M
E8605-1 Microlight Intercom E
E8605-2 Baud Rate Converter M
E8605-3 Baud Rate Converter
PSU Board G
E8605-4 Portable PA H
E8606-1 Midi-CV Converter Board H
E8606-2 Midi-CV Converter PSU D
E8606-3 Troglgraph F
E8606-4 80m Receiver H

E8606-5 Sound Sampler R
E8607-1 Direction E
E8607-2 Upgradeable Amp, MC stage
(Stereo) G
E8607-3 BBC Motor Controller F
E8608-1 Digital Panel Meter G
E8608-2 Upgradeable Amp, MM stage
(mono) H
E8609-1 Mains Conditioner E
E8609-2 Experimental preamp F
E8609-3 Upgradeable amp, Tone board
(mono) H
E8609-4 Upgradeable amp, Output
board (mono) F
E8610-1 Audio Analyser Filter
Board L
E8610-2 Audio Analyser Display
Driver K
E8610-3 Audio Analyser Display H
E8610-4 Audio Analyser Power
Supply F
E8611-1 Audio Switcher (2 bds) H
E8611-2 PLL Frequency meter (4 bds)... Q
E8611-3 Upgradeable Amp PSU J
E8611-4 Call meter, main bd. O
E8611-5 Call meter, interface bd. N
E8612-1 Bongo Box J
E8612-2 Biofeedback monitor
(Free PCB) E
E8701-1 RGB Converter F
E8701-2 Mains Controller D
E8701-3 Flanger H
E8701-4 Audio Selector main board ... M
E8701-5 Audio Selector PSU H
E8701-6 Tacho-Dwell F
E8702-1 Ratemeter main board K
E8702-2 Ratemeter ranging board F
E8702-3 Photo Process Controller
(3bds) O
E8702-4 LEDline display board
(2 off) K
E8702-5 LEDline PSU and controller
(2 bds) G
E8703-1 Capacitometer F
E8703-2 Geiger Counter L
E8703-3 Credit Card Casino E
E8704-1 BBC micro MIDI interface ... L
E8704-2 ETIFaker patch box H
E8704-3 24Hr. Sundial E
E8705-3 MIDI Keyboard keyswitch
boards (3 boards) W
E8705-4 Batlite C
E8705-5 Budget Power Meter E
E8706-1 Hi-fi Power Meter N
E8706-2 MIDI Keyboard CPU U
E8706-3 MIDI Keyboard Front Panel ... O
E8706-4 Flame Simulator G
E8707-1 MIDI Keyboard PSU H
E8707-2 Telephone Alarm J
E8707-3 Nuclear Strategy Simulator J

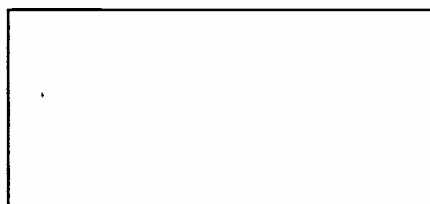

Biofeedback Monitor (December 1986)

The capacitor C4 is shown the wrong way around in the component overlay diagram (Fig. 4).

The Intelligent Call Meter (December 1986)

The hex dump listing of the ROM for this project (Table 3) was badly printed. The byte at location BF should read 7F.

The Better Flanger (January 1987)

In the circuit diagram (Fig. 2) D1 is not labelled. This is connected to Q1. In the component overlay (Fig. 5) several components are missing. A link should connect the two pads to the left of C1. Q1 is situated next to D1 and connection point P4 is situated between R16 and R33. In addition, the positions of R16 and C11 should be swapped.

Photo Process Controller (February 1987)

In the circuit diagram (Fig. 2) the cathodes of diodes D3,5 are shown connected to 0V. They should connect to the junction of R16,17,18. In the overlay diagrams (Figs. 3 and 5) the flying leads are numbered incorrectly. Leads 7, 8, 9 and 10 at the top of Fig. 3 should be numbered 16-19. In Fig. 5 leads 6 and 8 from the top of R13 should be numbered 16 and 17. Numbers 9 and 10 from Q1 and Q2 should be 18 and 19. In addition the leads 11 and 'A' should be swapped.

Capacitometer (March 1987)

The circuit diagram (Fig. 1) should show pin 1 of IC1 connected to 0V. The zener diode (ZD1) should be connected between the junction of R10/R11 and 0V. The PCB foil is correct.

BBC Micro MIDI Interface (April 1987)

IC7 and IC8 (the 6N139 opto-isolator ICs) are missing from the parts list. In the Buylines section it is incorrectly said that these are available from Electromail as part 302-126. The isolator is available from Maplin as part number RA59P. Resistors R8,9 are missing from the overlay diagram (Fig. 4). These are located in the two pairs of pads below IC6. There should also be no 0V connection to the MIDI IN sockets, only to the OUT sockets (pin 2) so as to prevent earth loops.

Power Meter (May 1987)

The foil for the budget power meter was given 50% full size on the foil pages. The correct size foil appeared in the June issue.

MIDI Master Keyboard (June 1987)

The foils for the CPU board were given 64% full size on the foil pages. Photocopies of the correct size foils can be obtained by sending a SAE to the Editorial address.

TECH TIPS

3-in-1 Reset


A.J. Holme
York

This circuit was designed for a 6502 controller board. It provides power-on reset, a TTL compatible input for externally generated resets, and a push button for manual reset.

A PNP output stage is used to prevent $\overline{\text{RES}}$ briefly going high at power-up, before the supply stabilizes at +5V. It is not strictly necessary and may be replaced by a NAND inverter if preferred.

The state of the EXT $\overline{\text{RES}}$ input is echoed at the $\overline{\text{RES}}$ output while the one-shot generator is in its stable state. There are two possible uses for this:

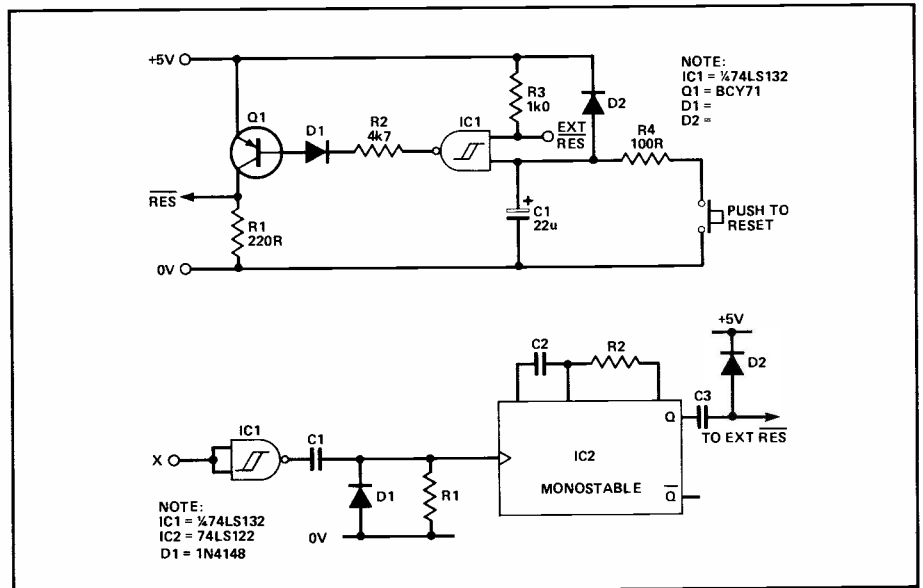- Driving EXT $\overline{\text{RES}}$ with a clock causes the processor to continuously repeat its power-on reset sequence. Provided suitable triggering can be arranged, this enables the processor buses to be viewed on an oscilloscope as steady, logic-analyser style traces.
- With the addition of the lower circuit shown a restart from crash facility may be added. Point X is



connected to a signal which regularly changes during normal processor activity. The network on the output of the NAND inverter produces positive pulses which clock the monostable at every falling edge of X. This ensures that the mono is permanently in its triggered state. Should the processor crash (for example from mains-borne inter-

ference) these pulses will cease, causing the mono to reset. The resulting negative edge at Q is capacitively coupled to the EXT $\overline{\text{RES}}$ input and this generates a processor reset which recovers execution.

Some simple software support for this circuitry will be required to enable the processor to distinguish between warm and cold starts.

Simple Audio Limiter


R.J. Eggleton
St Ives

Audio limiters are useful in many applications such as recording, transmitting or public address systems where over-modulation would cause unwanted distortion.

This circuit has the virtues of simplicity, fairly low distortion and no need for adjustment.

Input voltages below the limit level are amplified by the op-amp eleven times to the output ($(R7+R8)/R7$). When the output level rises to the limit level of 775mV RMS the diodes conduct to the two limiting transistors and limit the level. Since the transistor limiters are inside the feedback loop of the op-amp, distortion is reduced significantly.

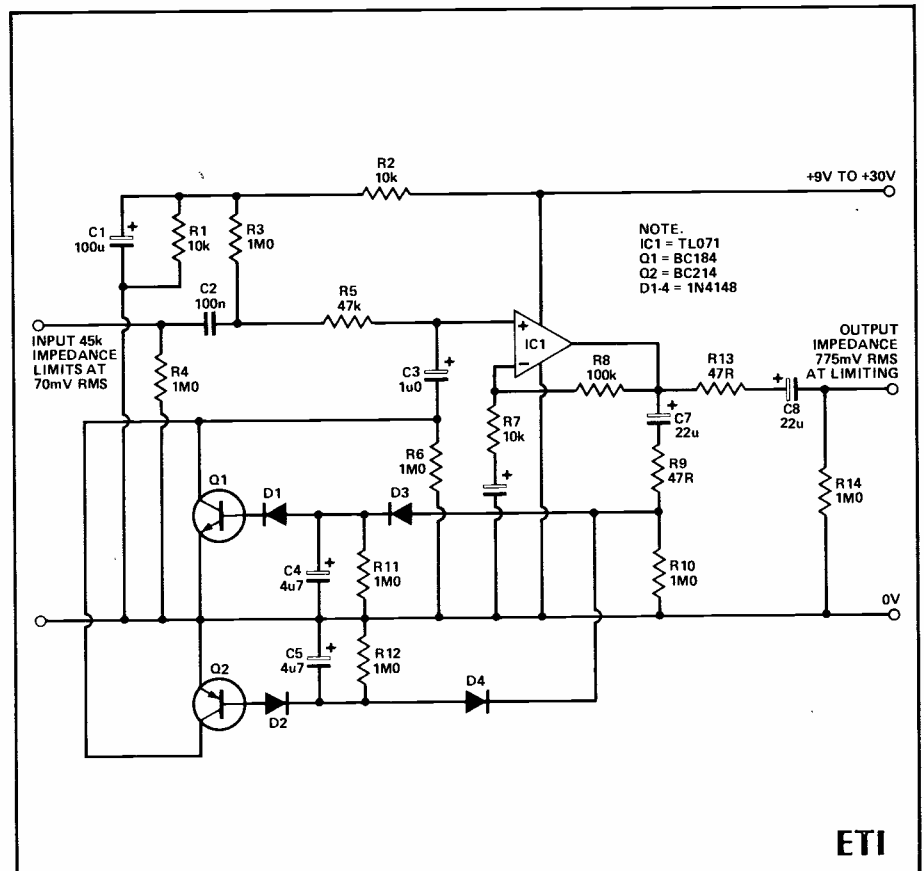As the input is immediately limited before entering the op-amp, the circuit can withstand considerable overload. However distortion will rise above 40dB of limiting (approx 7 volts RMS input).



ETI

FREE READERS' ADS

Buy, sell or exchange through our free service to readers

HELP! Does your intelligent callmeter work? If so, contact Jeff, Bristol 303030 Ext. 3294.

WANTED SCIENCE OF CAMBRIDGE MK14 COMPUTER and manual. Preferably working. Shaun, 46 Grosvenor House, A-U-L, Lancs OL7 0SB. 061-344 1054.

TAYLOR signal generator. 100kHz-45MHz. Also Cossor sweep generator 7-70MHz. Both mains valve types. £10 each. Windsor (0753) 860889.

WANTED parts for **ACORN ATOM**: EPROM, disk interface, wordproc software. Reasonable prices. Tel: 01-841 0486 evenings.

TEKTRONIX 545B scope £75. Great Yarmouth. Tel: (0493) 667689.

WANTED: secondhand strobe light. Contact: B. Clark, 73 Greenlaw Crescent, Glenrothes, Fife.

MODULAR 19 INCH RACK units, power supplies, fans, CMDs, optos, panel controls, etc. Cheap. (0725) 22684 evenings.

REVOX A77, 3¾/7½, built-in Revox amps plus 100hrs tapes. £450. Tel: Nik 01-253 0661 daytime.

WANTED. Technical service manual, circuit diagram, details of expansion ROMs for Acorn Atom. Tel: (0422) 70270.

USED COMPONENTS for sale. Send SAE for list to 23 Dickens Court, Newthorpe, Nottingham, NG16 3RG. Soon!

WANTED valve power amp circuit and board layout. Mr. J. Smith, 93 Breda Road, Belfast, BT8 4BW.

VARIAC type variable auto transformer. 5 amp rating. Enclosed. £20. Tel: Windsor (0753) 860889.

TWO DIABLO SERIES 30 front loading hard disc drives. Discs required. £100 each. 091-482 4307.

SOLID STATE MULTIBAND TRS-30 receiver. Coverage 540kHz-12MHz, 30-50MHz, 88-173MHz. Details: Write to Victor McKaig, 15 Islandranny Road, Bushmills, Co. Antrim, N. Ireland, BT57 8YE.

WANTED Grundig Satellite 1400 professional or similar multiband communications receiver. Write to Victor McKaig, 15 Islandranny Road, Bushmills, Co. Antrim, N. Ireland, BT57 8YE.

HELP. Does any reader have a copy of instructions for Quicksilva sound board? Tel: Jim Branston 01-200 7165. **CCT100-EXCELLENT** terminal (DEC VT100 compatible). Very good condition. A great buy at £200. Tel: (0273) 203682.

MULTICORE light duty cable. Mostly 5-core, 100m reels. £5 a reel. Approx 20 reels available. Tel: 01-690 3131.

VOCODER WANTED. ETI Powertran or similar. Working or part assembled (not knackered!) Tel: Jake. (0227) 730410 evenings.

SEIKOSHA GP-100A graphics, 80 column, dot-matrix printer. £65 ONO. Tel: Alan 01-866 4579.

CRIMSON 520 40W stereo power amp. £40. F. Richardson, 20 Callerton Close, Ashington, Northumberland, NE63 9QT.

FOR SALE: Pioneer cassette deck model CT-4. £55. Tel: 051-928 8011 evenings. Possibly deliver.

WANTED any info on DBS satellite TV, plans, circuits, leaflets, etc. Postage refunded. Smith, 12 Shelley Rd., Taunton, Somerset.

200+ OLD RADIO VALVES. 1929/48 mains and battery. Offers. Tel: 051-677 3341. F. Brown, 5 Snowden Rd., Moreton, Wirral, L46 6BH.

100W/CHAN MOSFET POWER AMPLIFIER. Very hi-fi. Ideal power amp for the ETI pre-amp. £100. Tel: 01-558 6129.

WANTED: TELEQUIPMENT D43 OSCILLOSCOPE. Modules and/or complete unit. Also manuals, circuit diagrams wanted. R. Neale, 2 Salmond Avenue, Stafford, ST16 3QP.

WANTED: GEIGER RATEMETER and counter, urgently. Nico Taylor, PO Box 1377, Durban 4000, South Africa. tel: 031-846994.

CONDITIONS

- These ads are only for readers not engaged in buying or selling the same equipment or services on a commercial basis.
- Ads will be inserted as and when space is available. Insertion in a particular issue cannot be guaranteed.
- Ads should be of 20 words or less and in block capitals or typed. Words to appear in bold should be underlined.
- Advertisers should fill in their name, address, and telephone number and sign the form to indicate acceptance of these conditions. Adverts can be on the printed form or a photocopy of it but they must be accompanied by the token at the top of this page.
- ETI reserves the right to refuse or to alter submitted ads wherever this is judged necessary.
- Ads are accepted in good faith. Neither the magazine nor its publishers can be held responsible for any errors in the reproduction of an ad, nor for untruths or misrepresentations, nor for the activities of advertisers or respondents. By acceptance of these conditions the advertisers undertake to indemnify the publisher against any legal action arising from publication of their advertisement.

Enter your advertisement below

Name

Address

Telephone

I accept the conditions set out here.

Signed

Send this form to:

**Free Readers' Ads
Electronics Today International
1 Golden Square
London W1R 3AB.**

BACK NUMBERS

- Missed part one of your favourite project?
- Lost that all-important article on circuit design?
- Desperately need that Tech Tip to get your latest masterpiece going?
- Pining for that one issue to complete your valuable collection?

ETI Backnumbers Department to the rescue!

Please note that backnumbers are only held for 12 months. Articles published previous to this must be obtained through our photocopy service.

Please supply the following backnumbers of ETI. Note: Backnumbers are held for 12 months only (complete in block capitals)

Month Year Month Year

Month Year Month Year

Month Year Month Year

Month Year Month Year

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.80 per issue ordered.

Total remittance £ Date

Name

Address

.....

..... Postcode

Send the completed form and your remittance to:

ETI Backnumbers Department
Infonet Ltd.
Times House
179 The Marlowes
Hemel Hempstead HP1 1BB



PHOTO-COPIES

ETI has been published for over 15 years and in this time a great many interesting and valuable projects and features have graced its pages. Although backnumbers are available for only the past 12 months issues we can supply photocopies of any individual article ever published in ETI.

Photocopies cost £1.50 per article regardless of their length. Please note that projects published over several issues must be ordered as a series of individual articles, each for £1.50.

PCB foil patterns and any errata are included with all photocopies, as applicable.

Please supply photocopies of the following articles from ETI (complete in block capitals):

Month Year Page (if known)

Title

Month Year Page (if known)

Title

Month Year Page (if known)

Title

I enclose a cheque/postal order made out to ASP Ltd. to the value of £1.50 per photocopy ordered.

Total remittance £ Date

Name

Address

.....

..... Postcode

Send the completed form and your remittance to:

ETI Photocopy Service
Argus Specialist Publications
1 Golden Square
London W1R 3AB



HY - TEK ELECTRONICS...

HY - TEK ELECTRONICS...

PROFESSIONAL POWER AMPS. CROSS-OVERS & GRAPHIC EQUALIZERS

1000 WATT STERO POWER AMP	£429.98	10 BAND STERO GRAPHIC	£129.98
600 WATT STERO POWER AMP	£329.98	15 BAND STERO GRAPHIC	£167.98
300 WATT STERO POWER AMP	£249.98	27 BAND MONO GRAPHIC	£164.98
150 WATT MONO POWER AMP	£169.98	3 WAY ELECTRONIC CROSS-OVER	£99.98
150 WATT POWER AMP WITH EQ	£184.98	2 WAY ELECTRONIC CROSS-OVER	£74.98



All the above units are 19" rack mount & are designed to be reliable under the most rigorous & testing sound system, disco & PA situations.

- * Pitch Control
- * Illuminated strobe
- * 12V DC Operation
- * Fits standard BSR cut out (only slight mod required)
- * High quality ceramic cartridge supplied.
- * Ideal replacement for disc's etc.

CITRONIC BELT DRIVE TURNTABLE.



£29.97 (p&p £3.00) * Magnetic cartridge £9.99




TOSHIBA KT 4046K
Personal Cassette Radio
* FM Stereo + MW + Radio
* 3 Band Graphic Equalizer
* Dolby 'B' + Metal Facility
* Complete with Belt Clip
(Note: Both above items are fully guaranteed mail order returns)

Normal price £69.96
SAVE £20.00 our price
£49.97 + P&P £3.00



PERSONAL HI-FI price breakthrough
SANYO MGP600
PERSONAL CASSETTE PLAYER
* 4 Band Graphic Equalizer
* Auto Reverse * Dolby 'B'
* Metal Tape

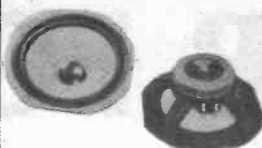Normal price £49.96
SAVE £15.00 our price
£34.96 + P&P £3.00



16" CHASSIS
CELESTION 1000 WATT £199.97
CELESTION 400 WATT £134.97
CELESTION 200 WATT £99.97
GOODMANS 230 WATT £97.97
TITIAN 200 WATT £69.97

CHASSIS SPEAKERS

HY-TEK stock a vast range of chassis speakers, midranges, tweeters, X overs, cabinet fittings & piezo drive units. Below is a short list please phone and ask for a full list if you don't see what you require.

15" CHASSIS
CELESTION 600 WATT £164.97
CELESTION 250 WATT £99.97
CELESTION 200 WATT £74.97
GOODMANS 250 WATT £69.97
TITIAN 100 WATT £39.97

HIGH QUALITY TEST EQUIPMENT.

3" single beam oscilloscope.
* High sensitivity 10mV/division
* Frequency range DC to 5MHz * Ideal for lab, school and service use.
* Sweep range 10Hz to 100KHz in 4 steps and H.EXT
£169.97 p&p £5.00

AUDIO GENERATOR
* 20Hz to 200KHz in 4 ranges. (sine wave)
* 20Hz to 20KHz. (square wave)
* Variable output 5V sine wave & 10V square wave p.p.
* Suitable for testing all types of audio units. * Power 240V AC. £84.97 p&p £5.00

ANALOGUE MULTIMETERS.

MODEL NO KRT5001
* 35 ranges (using range doubler switch)
* Carrying handle/stand
* Measures AC & DC VOLTS, DC CURRENT, RESISTANCE & DECIBELS
* Complete with test leads, batteries & instruction book
£24.97 p&p £2.00

DIGITAL METERS.

MODEL NO KD508
* 3 1/2 Digit multimeter
* Slide switches for single handed use
* 15 ranges
* Measures AC & DC VOLTS, DC CURRENT & RESISTANCE
* Complete with battery leads & instruction manual
£22.93 p&p £2.00



PHONIC MRT60

- * 10 Band Graphic * 3 Deck Inputs
- * 2 Tape Inputs * Cross Fade Mixer
- * Microphone Override
- * Plus Many More Features.

£129.97 p&p £3.00

THE NEW 1987 HY-TEK CATALOG NOW AVAILABLE!!
100s OF SPEAKERS, MIXERS, TOOLS, SPECIAL EFFECTS EQUIPMENT. PLUS MUCH MORE JUST SEND £1.50 FOR RETURN OF POST SERVICE.



PHONIC MX 7700 DISCO MIXER

This unit offers many features only found on mixers costing much more. Like a cross-fade between the turntable inputs, 5 band graphic equalizer, full headphone monitoring plus much more. Many other models available in this range from only £29.98

MX 7700
£119.98

JAMO HI-POWER HI-FI SPEAKERS

JAMO D5E
£199.98

JAMO D5E - The top of the dynamic range of speakers from JAMO. With a host of features that include an impressive 300 watt peak power handling, a massive 12" bass driver plus twin tweeters and a high efficiency midrange driver. All fitted in tastefully styled cabinet complete with castors. Also available JAMO D4 speakers (3way 170 watts) £119.98 & JAMO D3 speakers (3 way 130 watts) £99.98

DIGITAL DELAYS, SAMPLES & ECHO UNITS

JSH DX77 DIGITAL DELAY 512ms & HOLD	£149.97
VESTA FIRE DIG 420 sampler 1024ms SAMPLE	£249.98
VESTA FIRE DIG 411 DELAY 1024ms & HOLD	£259.98
VESTA FIRE DIG 412 programmable DELAY	£499.98
ALTAI EC 500 BBD 250ms echo	£99.98
ALTAI VG1 BBD 200ms ECHO	£79.98
ALTAI EEM 612 ECHO microphone	£39.98



INSTRUMENTS FROM STOCK UK'S LARGEST IN-STOCK RANGE


DIGITAL MULTIMETERS

105 14 Range 2A DC. 2 Mohm	£24.75
528 14 Range 0.2A DC. 2 Mohm Hfe test	£29.95
615 19 Range 10A DC. 20 Mohm Hfe West	£34.95
6010 28 Range 10A AC/DC 20 Mohm (0.2MA AC/DC)	£38.53
578 20 Range 10A AC/DC 2M. Buzzer Display Hold Auto Range Memory (20MA AC/DC)	£39.68
5010 28 Range 10A AC/DC 20 Mohm (20mA AC/DC)	£41.98
5010EC 34 Range 10A AC/DC 20 Mohm Hfe test Capacitance test. Conductance	£59.95
MES40 Auto/manual 10A AC/DC 20M	£48.30
6013 Digital Capacitance meter 8 ranges 200pf-2000 MFD	£63.25



ANALOGUE MULTIMETERS

1015 15 Range Pocket 10K/V	£8.63
1035 19 Range Pocket 20K/V 10A DC 10 Mohm	£11.95
1038Z 19 Range 20K/V 10A DC Hfe Buzz 10 Mohm	£14.50
201 19 Range 20K/V 12A AC/DC 10 Mohm	£17.95
2010 20 Range 30K/V 10A DC 20 Mohm	£21.95
3010BZ 24 Range 30K/V 10A DC Buzz Mohm	£23.95
830A 26 Range 30K/V 10A AC/DC 10 Mohm	£28.95
8060E 41 Range 20MEG FET 12A AC/DC 1000 MEG	£32.95

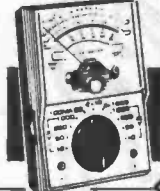

POWER SUPPLIES


001c 13.6v 3A DC	£14.95	154 5/15v	£38.25
243 D/24v D/3A DC	£49.75	0/4A DC	£38.25
D.30V 1.5A DC	£34.44		

OSCILLOSCOPES

UK FREE DELIVERY
HAMEG Dual trace with component testers 8 x 10cm screen:-
203/8 Dual 20MHz with probes £361.10
204 with a sweep delay £480.70
CROTECH with component tester single trace:
3031 5 1/4 x 8 1/2cm Display £228.85
3036 8 x 10cm Display £253.00
HUNG CHANG
620 Dual 20MHz + component test £339.25
635 Dual 30MHz Sweep delay £458.85
615 Dual 15MHz bat/Mains £458.85

LOGIC PROBE

07 20MHz Logic Probe
TTL CMOS etc £10.95

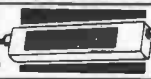

LCR METER

TC200 Digital LCD Handheld Tester £97.75

STOCKISTS FOR

Frequency Counters * Generators * Power Supplies * Tools * Computer Equipment * TV/Video Accessories * Nicads * Communications and Security Equipment * Public Address & Audio (See catalogue)


ALL PRICES INCLUDE VAT

ORDER BY POST OR PHONE. OPEN 6 DAYS A WEEK FOR CALLERS

HENRY'S AUDIO ELECTRONICS
301 Edgware Road, London W2 1BN. 01-724 3564
404 Edgware Road, London W2 1ED. 01-724 0323
EDUCATION/TRAINING & EXPORT SUPPLIED

FREE CATALOGUE
Ref TG/E
Send s.a.e. (min 12" x 9") with £1 stamp UK Callers/export £1.00

LIGHTING!

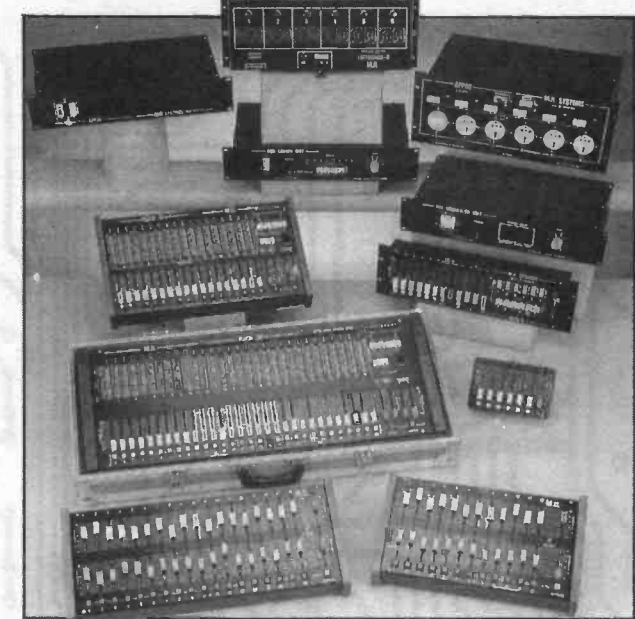


ITS GREAT NEWS AT MJL. WE CAN NOW SELL DIRECT TO THE PUBLIC IN THE UK AT TRADE PRICE - SO MR. TRADE CUSTOMER WHAT ARE YOU READING THIS FOR. ASK FOR YOUR FREE COLOUR BROCHURE AND SAVE YOURSELF A FORTUNE!


MJL (INTERNATIONAL) LTD
01/689/4138

45 WORTLEY RD. W. CROYDON. SURREY CR0 3EB, UK


PCB FOIL PATTERNS

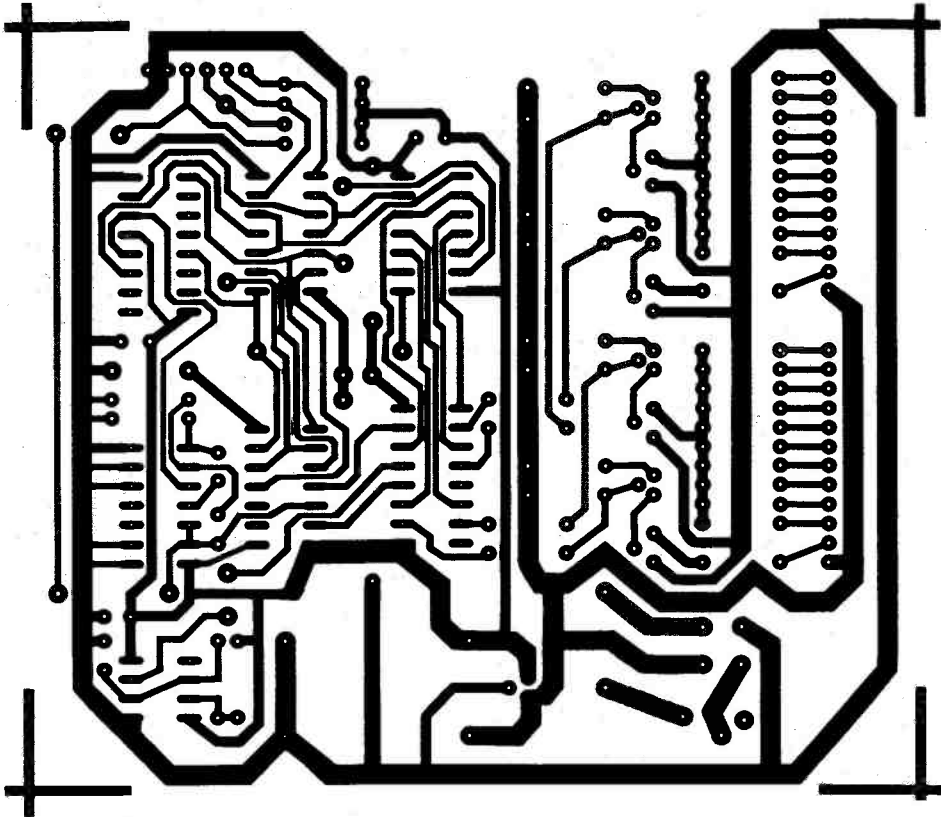

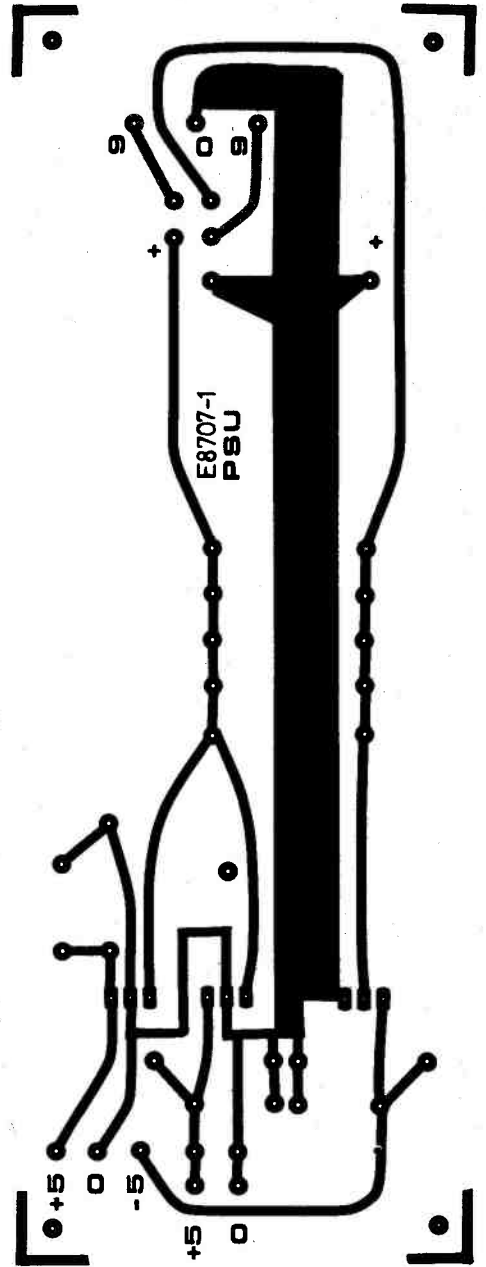The foil for the Nuclear Strategy Simulator.




The MIDI Master Keyboard PSU foil.

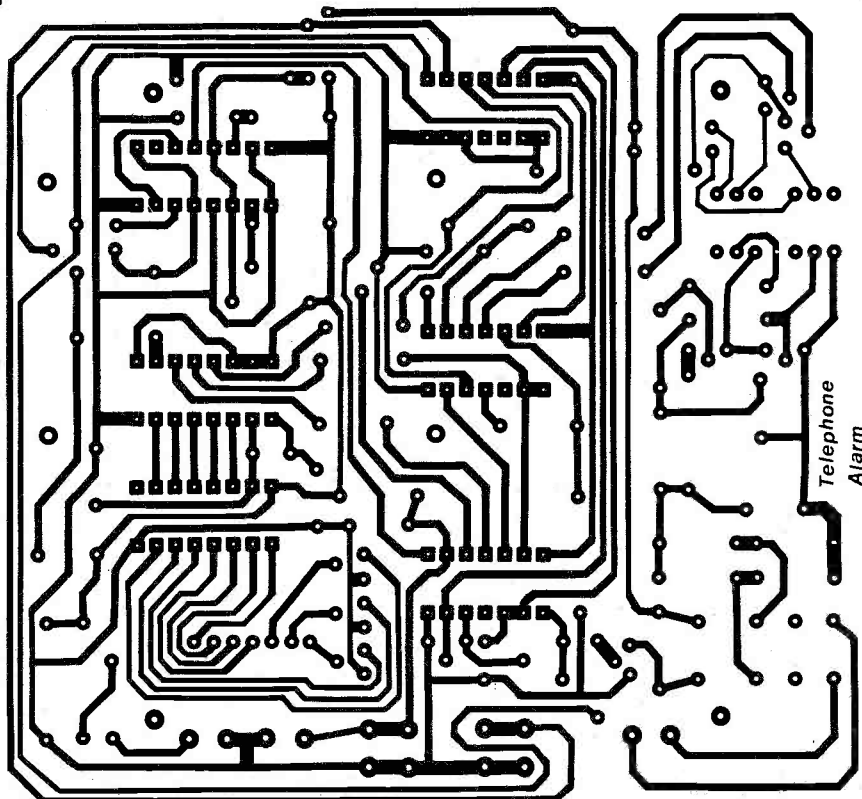


The Telephone Alarm PCB foil.

PCB FOIL PATTERNS

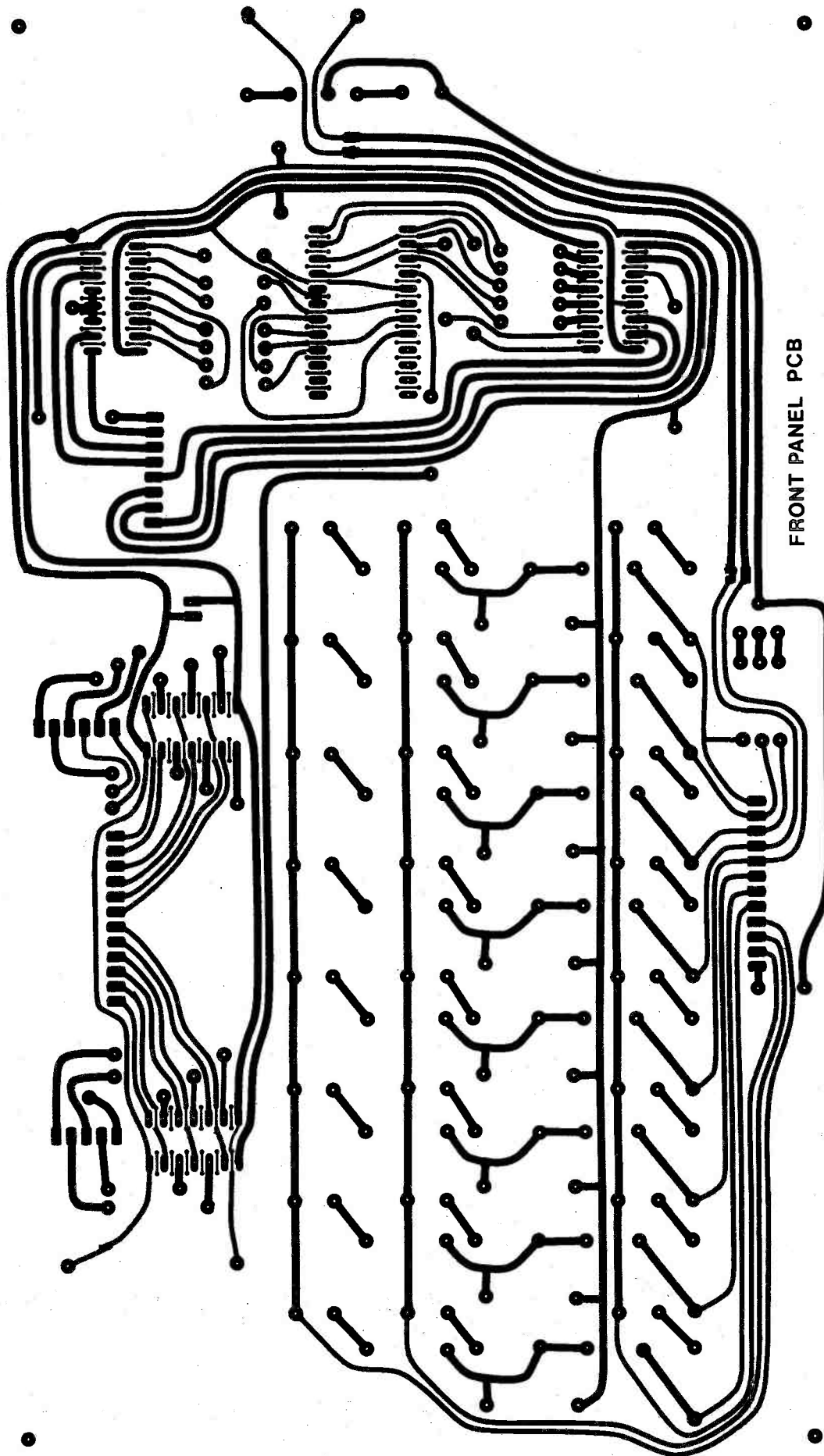Please note: The MIDI Master Keyboard CPU foils given last month were shown 64% full size. Photocopies of the full size foils can be supplied on receipt of an SAE. Please send in to ETI MIDI Keyboard Foils, 1 Golden Square, London W1R 3AB.




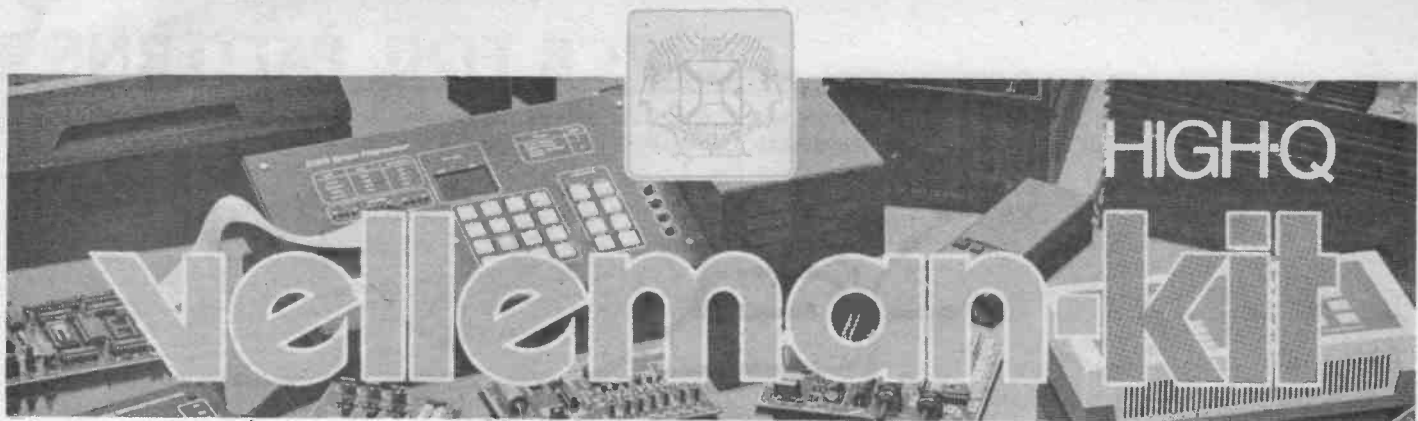The MIDI Master Keyboard front panel board foil held over from last month.



NOW AVAILABLE FROM ETI READERS SERVICES, 9 HALL ROAD
MAYLANDS WOOD ESTATE, HEMEL HEMPSTEAD. HP2 7BH.

POWER CRAZY

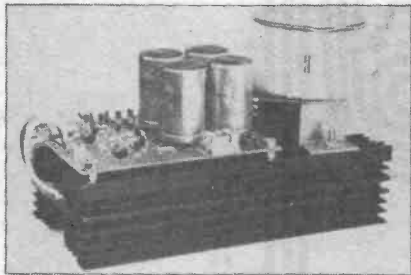

240W HIFI AUDIO POWER AMPLIFIER KIT NR. K2587

The introduction of MOSFET transistors in power amplifiers opened a new area in this field. Wide power bandwidth, low driving power, high output power and an almost ideal transient response are only a few of the advantages. This kit is based on this technology. Apart from the power-amplifier, it also includes the power supply, heatsink and transformer. Once assembled, its ready for use and can easily be housed. Only 2 final adjustments are required and only needs a multimeter.

- Some applications: Discobars and discotheques - Orchestra or theatre - DC coupled power controls.
- Power supply (including transformer) 2x45 VDC/5A
 - 240w music power at 4 Ohm.
 - Distortion (1kHz): 0.0%
 - Intermodulation distortion: 0.0%
 - Input impedance: 33K.


Price £184.80 + p&p

AUDIO LABORATORY DIY TEST GEAR COMPUTERS TOP QUALITY KITS FOR HOME CONSTRUCTION



velleman-kit

YOU CAN'T MISS IT

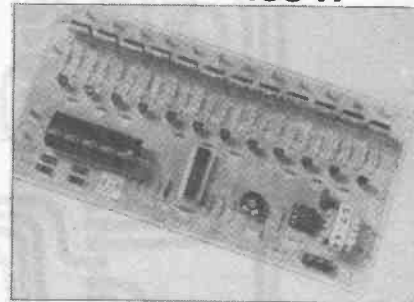

GIANT VU METER KIT NR. K2620

Several circuits providing different light effects, from the simple lightorgan to real 'lightcomputers', have already appeared on the market.

This kit is something new... a giant VU meter with 240V bulbs. The 12 bulbs are mounted as a lightcolumn which varies according to the sound level.

The input is galvanically separated and the sensitivity is adjustable, so there is no danger when connected to a pre-amplifier or to a power amplifier.


- 12 triac outputs: 400W each (non-cooled).
- Input impedance: ca. 20 Kohm.
- Input sensitivity: adjustable from ca. 100mV to 3V at full scale.
- Power supply: 9 VAC/0.5A.

Price £36.85 + p&p

K610	VU-LED MONO (JAA 180) USING LED'S	13.74
K611	7W LF AMPLIFIER	7.13
K612	DIMMER 1000 WATTS	7.93
K613	DIMMER DEPARASITE 9 (NOISE SUPPRESSED)	12.60
K1771	FM OSCILLATOR	7.48
K1803	PRE-AMPLIFIER UNIVERSAL MONO	5.22
K1804	60 WATT LF AMPLIFIER	23.84
K1823	1 AMP POWER SUPPLY WITH LM317 IC	9.18
K1861	POWER SUPPLY FOR 60 WATT STERO (K1804)	24.67
K1874	RUNNING LIGHT (4 CHANNEL)	23.70
K2032	LOW COST DIGITAL PANEL METER	26.82
K2532	ADAPTOR SOCKET FOR TMS2532 TO	39.45
K2543	ELECTRONIC TRANSISTOR IGNITION	13.13
K2545	UNIVERSAL CRYSTAL 50HZ TIMEBASE	18.66

K2557	DIGITAL PRECISION THERMOMETER	37.68
K2568	20 CM DISPLAY (CATHODE)	31.93
K2569	3 TONE CHIME (DOOR CHIME)	11.23
K2570	POWER SUPPLY 5-14 DC 1AMP	9.18
K2572	STEREO PRE-AMPLIFIER	9.13
K2573	STEREO RIAA CORRECTION AMPLIFIER	10.33
K2574	UNIVERSAL 4 DIGIT UP & DOWN COUNTER WITH COMPARATOR	65.50
K2575	MICRO PROCESSOR DOORBELL (25 TUNES PLUS 1 CHIME)	23.12
K2576	40WATT AUDIO AMPLIFIER	17.10
K2578	MICRO PROCESSOR CONTROLLED EPROM PROGRAMMER	316.81
K2579	UNIVERSAL START & STOP TIMER	10.93
K2580	POWER SWITCH DIMMER (600 WATT UNCOOLED)	13.69
K2581	DC CONTROLLED STEREO TONE CONTROL	21.00
K2582	STEREO AUDIO INPUT SELECTOR	16.50
K2588	3 CHANNEL SOUND TO LIGHT WITH PRE-AMPLIFIER	29.70
K2590	LIGHTCOMPUTER WITH EPROM	31.30
K2592	20 WATT LF AMPLIFIER KIT	13.45
K2594	ZERO CROSS PROGRAMMABLE TIMER	15.25
K2598	CAR BOOSTER 15-30 WATT	18.15
K2578M	EPROM PROGRAMMER (BUILT AND TESTED)	374.23
K2600	2A DIMMER	10.12
K2601	STROBOSCOPE	14.78
K2602	4 CHANNEL RUNNING LIGHT WITH MODULATOR	32.25
K2603	MICROPROCESSOR YEAR TIMER	152.15
K2604	KOJAK POLICE SIREN	9.90
K2606	LED AUDIO POWER METER	16.75
K2607	THERMOMETER ADAPTOR	16.00
K2622	AM & FM AERIAL AMPLIFIER	10.40
K2623	LAB POWER SUPPLY 0-24V 3 AMP	38.41
K2625	DIGITAL RPM METER	31.00
K2626	27640/27128 ADAPTOR KIT FOR K 2578	38.30
K2632	HARDWARE EXTENSION KIT FOR K 2603	22.08
K2636	AC MOTOR CONTROL	20.30
K2637	2.5 WATT AUDIO AMPLIFIER	8.23
K2638	CAR ALARM	19.32
K2639	LIQUID LEVEL CONTROL	21.50
K2644	FROST INDICATOR	11.15
K2646	MEDICAL-PILL TIMER	18.86
K2645	GEIGER MUELLER COUNTER	71.53

LIGHT UP THE SKY

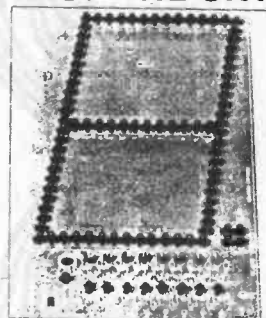

20CM DISPLAY 'COMMON ANODE' KIT NR. K2567

This kit contains a 7-segment display consisting of 12 leds per segment and 4 leds for the decimal point. With the aid of a supplementary power supply, it is possible to connect this kit to any existing circuit equipped with common anode displays of any brand and any dimension.

If the digit and segment drivers of the circuit can supply sufficient current, it will be possible to connect in parallel two or more displays, or even, leave the small display of the circuit in place and connect the 20cm display in parallel. This latter will not effect the brightness of the 20cm display due to the special concept of the driver circuit.

- Common anode.
- Power supply: 22 to 26VDC non-stabilized.
- Minimum anode input voltage (on): 2V.
- Maximum anode input voltage (off): 1.2V.
- Segments input impedance: 10K.
- Segment current: static (R6=00): +40mA multiplex (R6=220hm): +75mA.
- Total current consumption in static mode: maximum 400mA.
- Maximum power (U=22V): 8.8Watt.

Price £30.26 + p&p

20CM DISPLAY 'COMMON CATHODE' KIT NR. K2568

This kit is in terms of appearance and application identical to K2567 'COMMON ANODE'. As far as specifications are concerned; read cathode for anode.

Price £31.93 + p&p

VELLEMAN KIT PACKS FOR SCHOOLS

5 quality-components packs and (undrilled) printed circuit boards in one package. Includes Construction manual, data sheet and special instruction for educational experiments.

K 1823	1A POWER SUPPLY or	35.90
K 2637	2.5 AUDIO AMPLIFIER or	30.60
K 2644	FROST INDICATOR	41.05

NEW PRODUCTS

K 2649	THERMOSTAT WITH LCD DISPLAY	53.95
K 2650	TELEPHONE CALL CONTROLLED SWITCH	26.25
K 2651	DIGITAL VOLTAGE METER LCD DISPLAY	31.95
K 2652	TOUCH CONTROLLED DIMMER	14.50

K2549	INFRA-RED DETECTOR TRANSMITTER (ALARM)	17.88
K2550	INFRA-RED DETECTOR RECEIVER (ALARM)	21.37
K2551	CENTRAL ALARM UNIT	25.26
K2553	STEREO DECODER WITH 19KC FILTER	16.26
K2554	HIGH QUALITY FM TUNER	30.30

A FULLY ILLUSTRATED CATALOGUE IS AVAILABLE WHICH GIVES COMPLETE DETAILS OF KITS.

MICROPROCESSOR UNIVERSAL TIMER KIT NR. K1682




This unique timer is in principle a 24-hour clock provided with 4 relay-switched outputs and a programming period of 1 week. 20 switching programs can be memorized and via the membrane keyboard be programmed. Outputs or timing periods can be selected at random. All program steps are indicated by leds. A printed alu frontplate is included in the kit, making building-in of this timer a simple affair. This microprocessor timer was primarily designed for industrial and labo purposes, but the amateur can use it in dozens of applications as well.

- 20 daily- or weekly programmable timerfunctions.
- Memory display of programmed timer functions per output or per day.
- 4 independent relay outputs (1 relay included).
- Display of: day of week - AM/PM - output - clock.
- ON/OFF - sleep.
- The timer is based on the TMS 1122 microprocessor.
- Transformer 12VAC/1A (not included).

Price £75.85 + p&p

TAPE/SLIDE SYNCHRONIZER KIT NR. K2565

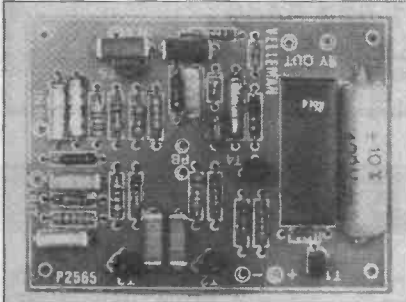


Actually, a lot of tape/slide synchronizers are available on the market. The price of these devices varies from expensive to very expensive. Those owning a tape- or cassette recorder can with this simple and inexpensive device, record synchronizing pulses and use these pulses to control automatic slide projectors. The circuit is small in size and can easily be housed.

- Power supply: 9 to 13VDC.
- Current consumption: 40mA.
- Output frequency (tone): +1.5KHz.
- Output amplitude: +250mV.
- Input sensitivity A: minimum 1.5V peak to peak.
- Input sensitivity B: minimum 100mV.
- Oscillator: AMV type.
- Input impedance (B): 1 KOhm.
- Output impedance: 15 KOhm.

Price £12.75 + p&p

SCREEN WIPER ROBOT KIT NR. 2599

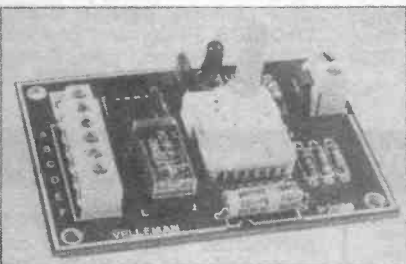

Three different time intervals may be selected by using a multiple rotary switch. With small component changes, the intervals may be varied. Some applications: windscreen wiper delay - diaprojector control - hazard warning via the brakelights of the car. In the manual you will find a complete description how to build this kit in a car, with wiring instructions to connect it to the existing wiper installation.

- Power supply: 12-15V DC.
- Intervals: 5-10-15-seconds.
- Relay output: 240V/2x3A.
- Relay output with two change-over contacts.
- Current consumption:
- Output 'OFF': 25mA.
- Output 'ON': 100mA.
- Dimensions: 82x56x41mm.

Price £14.84 + p&p



NEW DIMENSIONS IN COMPUTER INTERFACES

The Velleman Interface System starts your computer to measure, convert and control signals. This universal interface links your computer with everyday devices such as light and heat sources, audio amps, pumps, waterheaters, etc...

AUTOMATION, CONTROLLING, MASTERING ROBOTICS

Even the smallest computer can afford powerful applications you wouldn't dare to imagine. Today we have 10 function cards in our system but tomorrow there might be more. And while using this system you keep all communication means originally provided on your computer.

VELLEMAN INTERFACE SYSTEM - KITS

K2609 OC OUTPUT BOARD INTERFACE FOR HOME COMPUTER	22.60	K2631 EXTENSION BOARD FOR K2640 OR K2641	21.22
K2610 A/D CONVERTER INTERFACE FOR HOME COMPUTER	35.55	K2633 RELAY CARD	15.25
K2611 OPTO INPUT BOARD INTERFACE FOR HOME COMPUTER	26.30	K2634 QUAD TRIAC SWITCH CARD	16.33
K2613 BREADBOARD INTERFACE	32.43	K2635 8 TO 1 ANALOG MULTIPLEXER INTERFACE	27.60
K2614 ZX 81 SPECTRUM CENTRONICS INTERFACE	39.56	K2640 INTERFACE MOTHERBOARD FOR AMSTRAD	48.70
K2615 INTERFACE MOTHERBOARD (SPECTRUM)	40.02	K2641 INTERFACE MOTHER-BOARD KIT FOR MSX STANDARD	48.70
K2618 D/A CONVERTER INTERFACE FOR HOME COMPUTER	32.80	K2642 MOTHERBOARD KIT FOR B.B.C. AND MASTER COMPUTERS	53.13
K2628 INTERFACE MOTHERBOARD (COMMODORE)	51.65	K2643 MOTHERBOARD KIT FOR AMSTRAD CPC6128 COMPUTERS	55.32
K2629 REAL TIME CLOCK INTERFACE FOR HOME COMPUTER	41.35	K2612 RS232 MOTHERBOARD (I.B.M. COMPATIBLE)	123.34

VELLEMAN INTERFACE SYSTEM - BUILT AND TESTED

M2615 INTERFACE MOTHERBOARD SOECTRUM	63.85	M2618 D/A CONVERTER INTERFACE FOR HOME COMPUTER	36.86
M2616 INTERFACE MOTHERBOARD ZX 81	63.60	M2629S REAL TIME CLOCK INTERFACE (SPECTRUM)	58.60
M2628 INTERFACE MOTHERBOARD COMMODORE 64	80.40	M2629U REAL TIME CLOCK INTERFACE (UNIVERSAL)	58.48
M2609 OC OUTPUT BOARD FOR HOME COMPUTERS	29.96	M2633 RELAY CARD	22.31
M2610 A/D CONVERTER INTERFACE FOR HOME COMPUTER	41.92	M2634 QUAD TRIAC SWITCH CARD	22.21
M2611 OPTO INPUT INTERFACE FOR HOME COMPUTER	40.13	M2635 8 TO 1 ANALOG MULTIPLEXER INTERFACE	38.64
M2614 ZX 81 SPECTRUM CENTRONICS INTERFACE	45.60		



Schneider

MSX



Sinclair

COMMODORE 64 K

EURO CARDS

ECL 160x100 MM	4.07	ECS3 160x100 MM	4.07
ECS 160x100 MM	4.07	ECL 1/2 80x100 MM	2.24
ECL 160x100 MM	4.07	ECS 1/2 80x100 MM	2.24

ECL, ECS3 AND ECC CARDS ARE COMPATIBLE WITH EURO DIN CONNECTORS DIN 41617 AND DIN 41612
ALL CARDS ARE MADE OF BLUE (TINNED) MULTILAYER EPOXY PRE DRILLED.



TOROIDAL TRANSFORMER - KITS

TR2623 TOROIDAL TRANSFORMER KIT (2x16V/2x7.5V-130VA) FOR K2623	44.39	TR2603 TRANSFORMER FOR K2603	9.66
--	-------	------------------------------	------

MEMBRANE KEYBOARDS

KN12 MEMBRANE KEYBOARD 12 KEYS WITHOUT SYMBOLS	11.48	KB16S MEMBRANE KEYBOARD 16 KEYS WITH SYMBOLS	11.48
KB12S MEMBRANE KEYBOARD 12 KEYS WITH SYMBOLS	11.48	DF1R DISPLAY FILTER	1.61
KB16 MEMBRANE KEYBOARD 16 KEYS WITHOUT SYMBOLS	11.48		

TO ETI READERS SERVICES, 9 HALL ROAD, MAYLANDS WOOD ESTATE, HEMEL HEMPSTEAD, HP2 7BH.

Kit number	QTY	DESCRIPTION	Unit Price	TOTAL
Postage & packing: UK - 75p per kit			Overseas - £1.50 per kit, surface mail	
			(Airmail charged at cost)	
Please send me (tick as required):				
<input type="checkbox"/> VELLEMAN KITS CATALOGUE (VK1)				
<input type="checkbox"/> INTERFACE SYSTEM CATALOGUE (VK2)				
Cost per catalogue (inc. P&P): UK - 75p, Overseas - £1.50 (NO VAT)				
Please make cheques/postal orders payable to ARGUS SPECIALIST PUBLICATIONS			IF INVOICE IS REQUIRED PLEASE TICK HERE <input type="checkbox"/>	
Payment by ACCESS - see below				
			P&P	£
			Sub Total	£
			TOTAL	£

NAME
ADDRESS

Please debit my ACCESS account with the amount of (ACCESS orders must go to cardholder's address)
Signed
ACCESS account no.

Lineage:
48p (VAT incl) per word (minimum 15 words)
Semi Display: (minimum 2 cms)
£11.60 per single column centimetre
 Ring for information on series bookings/discounts
 All advertisements in this section must be prepaid.
 Advertisements are accepted subject to the terms and conditions printed on the advertisement rate card (available on request)



01-437 0699 Ext 292

Send your requirements to:
Nicola Baty
ETI Class. Dept.,
ASP Ltd.,
1 Golden Square,
London W1.

COURSES

Start training now for the following courses. Send for our brochure — without obligation or Telephone us on **06267 79398**

REF: ETI/6

NAME _____ **City & Guilds Exam**
 _____ **Radio Amateur Licence**
 _____ **Micro-processor**
 _____ **Introduction to Television**

Radio & Telecommunications Correspondence School,
 12, Moor View Drive, Teignmouth, Devon. TQ14 9UN.

ALARMS

ALARMS

FREE BOOKLET
 on
BURGLAR ALARMS
 with
LOWEST U.K. DIY PUBLISHED PRICES
 PHONE OR WRITE FOR YOUR COPY
051-523 8440
AD ELECTRONICS
 217 WARBRECK MOOR
 AINTREE, LIVERPOOL L9 0HU

01-437 0699
= RESULTS

ELECTRONICS TECHNICIANS
 Updating Courses
 London Electronics College,
 (Dept ETI), 20 Penywern Road,
 London SW5 9SU. 01-373 8721.

ENGINEERING

DESIGNERS

Making Your Own Software/Hardware?
 Need special Standoffs, Riv Brushes,
 Boxes or Panels?
 For FREE estimate contact
ANDREWS ENGINEERING
 Unit 42, Middlefield Industrial Est.,
 Sandy, Bedford.

SUPPLIES

QUALITY WALKIE TALKIES 49 MHz, long range satisfaction or refund. £24.99/pair (normally £31.49), 48 hrs delivery, Xenon (dept ET 19) 24 Wharnccliffe Street, Barnsley, Yorkshire.

SCOPES

MENDASCOPE LTD.

REPAIR & RECALIBRATE
 OSCILLOSCOPES.
 ALL MAKES ALL MODELS.
 NATIONWIDE COLLECTION &
 DELIVERY
FREE ESTIMATES
Phone 069-172-597

FOR SALE

CORTEX COMPUTER - Complete with two SSD Disc Drives, with CDOS, RS232 Port, E-BUS implemented, Centronics Printer Port, RGB Display adaptor. Closest offer to £150 secures. Tel:0480-860821.

KITS AND READY BUILT

ETI VALVE PREAMP, complete kit £59.95. Bass unit kit, Jan.85, including drivers, £59.95. Supplied by the designer. Fully inclusive prices, D.I.Y. Valve amps. List SAE, Dept ETI, Bewbush Audio, 47b Elmer Road, Bognor Regis PO22 6DZ.

LINSLEY HOOD Designs. Send S.A.E. for details to Teleradio Electronics, 325 Fore Street London N9 OPE.

ETI KITS assembled and tested* by electronic trainees under supervision within a purpose built electronic workshop for as little as £10* (* depending on type of kit and complexity). Contact:- A.J. Smith, Dept K.A. Electronics Workshop, Lincoln I.T.E.C. Dean Road, Lincoln LN2 4JZ. Tel. 0522 43532.

FM TRANSMITTERS Same day despatch **MINIATURE MODEL** frequency 60-145 Mhz, range 1 mile. Glass fibre P.C.B. All components. Full instructions 9-12V operation, broadcast reception. Super sensitive microphone. Pick up on **FM/VHF** radio. £6.95 inc or ready built £8.95. Size 57 x 19 x 12mm. **HIGH POWER MODEL**. 3 watts 80-108 MHz. Professional broadcast performance. Low drift varicap controlled. Range up to 7 miles. 12V operation. Any input audio/microphone. All components P.C.B. diagrams and instructions. Size 103 x 39 x 29mm. Kit 13.99 inc or ready built £18.99 inc. Send S.A.E. for our DataPack on other products. **ZENITH ELECTRONICS**. 14 Cortlandt Business Centre, Hailsham, East Sussex BN27 1AE. Tel: **0323 847973**.

SPECIAL OFFERS

FREE MEMBERSHIP to a new **NATIONAL ELECTRONICS CLUB**. For details and a free gift of components worth over £10 send only £1.00 p&p to **Woodside, Dowsett Lane, Ramsden Heath, Essex CM11 1JL.**

SWITCHES

VOICE/SOUND ACTIVATED SWITCHES easy to follow diagrams and uses only £1.00. Components and P.C.B's available: **Herrington, 63 Home Farm Rd, Hanwell, London W7 1NL.**

BOOKS

PARAPHYSICS Journal (Russian Translation); Psychotronics; Kirlianography, Heliphonic Music, Telekinetics. Computer Software. S.A.E. 4 x 9", Paralab, Downton, Wiltshire.



LOUGHBOROUGH UNIVERSITY OF TECHNOLOGY

DEPARTMENT OF ENGINEERING PRODUCTION

MSc in Computer Integrated Manufacture

* One year full time course starting in October 1987. Including specialist treatment of **ROBOTICS, FMS, CAD, CAD/CAM, COMPUTER NETWORKS** and **ARTIFICIAL INTELLIGENCE** with considerable emphasis being placed on the role of computers in the organisation, design and control of manufacture. Applicants should normally have a good honours degree in Engineering or Science or fulfil the academic requirements for CEng, MSC retraining grants and SERC advance-course studentship are available for suitable applicants. Industrial sponsorships are also available from major companies such as ICI, Ford, Baker Perkins, Rolls Royce, British Aerospace, GEC etc who collaborate closely with the Department in CIM research. The Department also has a limited number of SERC grants for applicants wishing to pursue PhD research in CIM. Application forms and further details from: Professor R H Weston (please quote: Ref RW6). Department of Engineering Production

Loughborough Leicester

ETI 3TU

COMPONENTS

PROMs - EPROMs - PALs ANY PROGRAMMABLE IC SUPPLIED OR BLOWN

PRICES (Including Programming)

2716	£3.45	2732	£3.60
2764	£2.85	27128	£3.20 etc.

BIPOLAR PROMs from £1.35

e.g. 82S123, 18S030, 74S288

PALs, PLDs etc. from £3.26

e.g. 82S153, 16L8, EP300

Full design and prototyping service

Any quantity programmed - SAE or

phone for details

P.L.S., 16 Wordsworth Drive,

Cheam, Surrey, SM3 8HF

Phone 01-644 8095

DISKS

3"CP2 Amsoft branded disks £2.20

3.5" DS unbranded disks £1.26

5.25" 96 tpi DS, unbranded, labels etc £0.43

RIBBONS

Cannon PW1080A Citizen 120D £3.50

Epson LQ800 £2.90

Citizen MSP10 Epson LX 80/86 £2.50

Epson MX/RX/FX80 Kaga Taxan £2.69

Epson MX/RX/FX100 £3.10

All prices inc. P&P. Please add VAT @ 15%

T-systems Ltd Tel: 0689 22196

The Signal Cabin, 61 High Street

Orpington, Kent BR6 0JF

I.G.S. COMPONENTS, NO 18 QUEENSWAY, SHELLEY, ONGAR, ESSEX. CM5 0BN.

Resistors 1/4W 5% carbon film E12 1+2p, 25+1.5p, 100+1p 4R7 to 10M anymix. 10off each above=770 resistors £4.40. 5mm LEDs red 1+8p, 25+6p, 100+5p, green or yellow 1+11p, 25+9p, 100+8p. IDC Ribbon Cable Grey 0.05in pitch, 10way, 12p/ft, 16way 18p/ft, 20way 23p/ft, 26way 30p/ft, 34way 34p/ft, 40way 46p/ft. IDC connectors also available full list free on request. All prices inc VAT. Orders under £10.00 50p extra.

LOUDSPEAKERS

UK MADE HIGH QUALITY LOUDSPEAKERS AVAILABLE.

Dome Tweeters, Dome Mid-Range, Woofers and Sub-Woofers. **UNIQUELY ENGINEERED. ALUMINIUM VOICE COILS.**

For further information please phone: **0473-719212**

SERVICES

DESIGN SERVICES, microprocessor, special interfaces, analogue, digital, signalling, alarm systems, PCB design and artwork. Prototype and small batch production. **ALAB ELECTRONICS,** Grantham (0476) 860089.

LOW COST PCB'S. At last a totally affordable design and manufacture service aimed at the person with low quantity in mind. From Designers to Home Hobbyists send your details for a quote to: Gardner Printed Circuits, 55 Withermoor Road, Winton, Bournemouth, Dorset BH9 2NU.

EQUIPMENT

McKENZIE LOUDSPEAKERS; compare our prices! C1285 GP £26 + £3 p&p, C15150 BS £54 + £4 p&p, C10200GP £40 + £3 p&p, C15400 BS £80 + £4 p&p. Projek Sound and Lighting, Unit 1 St. Andrews Street, Greenock, Scotland, (0475) 43089.

WANTED

WANTED

Test equipment, receivers, valves, transmitters, components, cable and electronic scrap and quantity. Prompt service and cash.

M & B RADIO

**86 Bishopgate Street
Leeds LS1 4BB
0532 435649**

**We purchase for cash or immediate settlement surplus stocks of I.C's, Memories, Transistors, etc. Please contact P.C.S. (Marketing) LTD
FAX:0767 318200
TEL:0767 317388
TELEX NO:825616**

Turn your surplus transistors, IC's etc., into cash. Immediate settlement. We also welcome the opportunity to quote for complete factory clearance. Contact:

**Coles Harding & Co.
103 South Brink
Wisbech, Cambs.**

**ESTABLISHED OVER 10 YRS
Tel: 0945 584188**

PLANS & DESIGNS



Design and build your own electronic dashboard. Plans, instructions, circuits, parts lists £4.95 inc p&p

**BURLINGTON MOTOR CO. LTD.,
(G5) ARCH 39M, BATH PLACE,
LEAMINGTON SPA. CV3 3AQ.**

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage teslas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, String Works, Bye St., Ledbury HR8 2AA.

REPAIRS

INSTRUMENT REPAIRS oscilloscopes, generators, multimeters and more. Viking Electronics, Potkins Lane, Orford, Suffolk IP12 2SS (0394) 450006.

MISCELLANEOUS

HEATHKIT U.K. Spares and service centre. Cedar Electronics, Unit 12, Station Drive, Bredon, Tewkesbury, Glos. Tel. 0684 73127.

EDINBURGH

OMNI ELECTRONICS

stock a wide range of electronic components at

**174 Dalkeith Road
Edinburgh EH16 5DX
Tel: 031 667 2611**

situated midway between
Commonwealth Pool and Cameron Toll

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street Tel: 051 236 0154

47 Whitechapel. Tel: 051 236 5489

Liverpool 2

'THE ELECTRONICS SPECIALISTS'


Open: Tues-Sat 9.30-5.30

LONDON

**Fill the gap Ring
Nicola Baty on
01-437 0699**

TYNE AND WEAR

ELECTRONIC COMPONENTS AND KITS

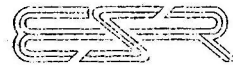

STATION ROAD, CULLERGOATS,
NORTH SHIELDS, TYNE & WEAR NE30
4PQ. 091 251 4363.

MON-SAT 9.30 to 5.30
CLOSED THURS.

electronics today

CLASSIFIED ADVERTISING COUPON

Post to: **ETI, 1 Golden Square, London W1A 3RB**
Rates:- 48p per word (min. charge £7.20 (VAT incl)). Semi display (min. 2cms) £11.60 (+ VAT) per single column centimetre.

Please debit my Access/Barclaycard No.  

Expiry date.....

£.....for.....insertions.

Or I enclose my cheque/PO for £.....for.....insertions.

Please use **BLOCK CAPITALS** and include post codes.

Classification.....

Name (Mr/Mrs/Miss/Ms).....

(delete accordingly)

Address.....

Signature.....


Date.....

Daytime Tel. No.

ELECTRONICS CAD

IBM PC (and compatibles) R.M. NIMBUS, BBC MODEL B, B+ and MASTER
AMSTRAD CPC and SPECTRUM 48K.

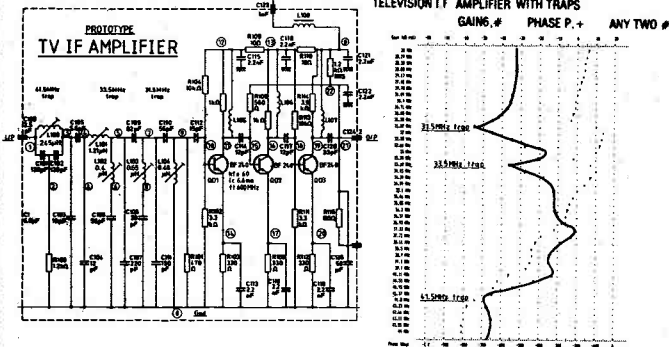Number One Systems Limited
Linear Circuit Analysis Program ANALYSER II
Circuit Name: IFAMP3 30th September 1986



ANALYSER I and II compute the A.C. FREQUENCY RESPONSE of linear (analogue) circuits. GAIN and PHASE, INPUT IMPEDANCE, OUTPUT IMPEDANCE and GROUP DELAY (except Spectrum version) are calculated over any frequency range required. The programs are in use regularly for frequencies between 0.1Hz to 1.2GHz. The effects on performance of MODIFICATIONS to both circuit and component values can be speedily evaluated.

Circuits containing any combination of RESISTORS, CAPACITORS, INDUCTORS, TRANSFORMERS, BIPOLAR AND FIELD EFFECT TRANSISTORS and OPERATIONAL AMPLIFIERS can be simulated - up to 60 nodes and 180 components (IBM version).

Ideal for the analysis of ACTIVE and PASSIVE FILTER CIRCUITS, AUDIO AMPLIFIERS, LOUDSPEAKER CROSS-OVER NETWORKS, WIDE-BAND AMPLIFIERS, TUNED R.F. AMPLIFIERS, AERIAL MATCHING NETWORKS, TV I.F. and CHROMA FILTER CIRCUITS, LINEAR INTEGRATED CIRCUITS, etc.

STABILITY CRITERIA AND OSCILLATOR CIRCUITS can be evaluated by "breaking the loop". Tabular output on ANALYSER I. Full graphical output, increased circuit size and active component library facilities on ANALYSER II.

Check out your new designs in minutes rather than days.

ANALYSER can greatly reduce or even eliminate the need to breadboard new designs. Full AFTER SALES SERVICE with TELEPHONE QUERY HOT LINE and FREE update service. Used by INDUSTRIAL, GOVERNMENT and UNIVERSITY R & D DEPARTMENTS worldwide. IDEAL FOR TRAINING COURSES, VERY EASY TO USE. Prices from £20-£195.

For further details and example computation or for details on our draughting program, please write or phone:

NUMBER ONE SYSTEMS LTD,
Ref. ETI, Crown Street, St Ives, Huntingdon, Cambs. PE17 4EB.
Tel: (0480) 61778

PERFORM IN-CIRCUIT EMULATION CHEAPER WITH THE NEW ICE-KING. SINGLE STEP OR BREAK POINT PROGRAMS — TEST RESULTS IMMEDIATELY! SYSTEM CONSISTS OF POD WITH FLAT CABLE CONNECTORS, PLUS A 2764 EPROM TO PLUG INTO ROM (SIDEWAYS) SOCKET. IDEAL FOR SMALL SYSTEM DEVELOPMENT, EDUCATION, TRAINING, ROBOTICISTS, ETC.


COMPLETE SYSTEM £250 + VAT
S.A.E. FOR FURTHER DETAILS:
ICE-KING, LANCASTER
CONSULTANTS,
PO BOX 65,
LANCASTER
LA1 1PG

ICE KING
THE IN-CIRCUIT EMULATOR
TURN YOUR BBC INTO A COMPLETE DEVELOPER TARGET FOR 8088-BASED COMPUTERS

RACK STYLE CABINET

* Suitable for instruments, high quality amplifiers and many other purposes * Top, side and rear covers removable for access * Black anodised aluminium front panel * Separate front mounting plate * Heavy gauge front panel is of brushed aluminium finish enhanced with two professional handles * With ventilation slits and plastic feet * Rear box manufactured from steel painted in black. Rack mounting or free standing. Comes in quick assembly flat package

Order Code	Panel Size W H (inch)	Rear Box W H D	Price £
NME19101	19 x 1.75	17 x 1.5 x 10	23.50
NME19103	19 x 3.5	17 x 3.0 x 10	24.50
NME19105	19 x 3.25	17 x 5.0 x 10	26.50
NME19123	19 x 3.5	17 x 3.0 x 12	25.50
NME19125	19 x 5.25	17 x 5.0 x 12	27.50
NME19127	19 x 7.0	17 x 6.5 x 12	29.95

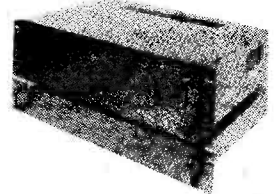


Please add £3.00 P&P for the first item and £1.50 for each additional item. To order send cheque/postal order - please allow up to 7 days despatch for cheque clearance. Quantity discount available. Customers who require further information please send S.A.E. Mail order only. Overseas orders welcome.

T.J.A. DEVELOPMENTS
Dept. ETI, 53 Hartington Road,
London E17 8AS.

ADVERTISER'S INDEX

Audiokits	25
BK Electronics	IFC
Barrie Electronics	12
Cirkit Distribution	25
Cricklewood Electronics	39
Crofton Electronics	62
Dateline	24
Display Electronics	IBC
Greenbank Electronics	39
Hart Electronics	32
Henrys Audio Electronics	55
HYTEK Electronics	55
ICE King	62
ICS	12
Jaytee Electronics	39
Maplin Electronic Supplies	OBC
MJL Systems	55
Nemesis	12
No 1 Systems	62
Specialist Semiconductor Devices	10
Stewarts of Reading	25
Super Alpha Electronics	33
Technomatic	4,5
TJA Development	62
TK Electronics	12
Velleman Kits	58,59
Zenith Electronics	25

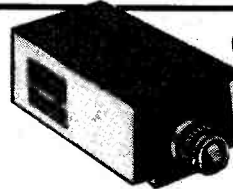

CCTV CAMERAS
FROM ONLY
£69.50 EACH!
PLUS CARRIAGE & VAT

Crofton Electronics are now able to offer C.C.T.V. cameras from as little as £69.50 + VAT & carriage. These cameras have been refurbished to a high standard. The output is 1 volt p-p and will work with most video equipment. These cameras are powered from 240volt mains, and have a vidicon rack giving a focusing range from an inch or two to infinity. A standard 16mm lens is also supplied. The sensitivity is in the order of 10 lux which allows their use in the domestic environment. Pictures can be produced with only 2.5 lux but with a worse signal to noise ratio. Low light versions are available having sensitivities of 0.1 lux (half moonlight) at #350 + VAT and carriage. Many other lens are available from stock. A mounting bush is standard. Many other cameras are available from stock both reconditioned and new. ie brand new mini 12volt camera at only £80 plus VAT and carriage. lens extra. Many other items of CCTV equipment such as monitors (both new and refurbished) switchers, panning units, housings, time and date generators are available from stock). We also supply camera and monitor tubes, as well as scanning yokes for a wide range of equipment.

SPECIAL SPECIAL SPECIAL SPECIAL

Currently on offer is a professional drive board and tube to make a superb 12" professional green panelled tube monitor at £23.50 inclusive. Would normally cost well over £200 +. Buy 10 off and they will only cost you £180.00 inclusive. Be sure to ask us to quote for any of your camera/monitor requirements we will never be beaten on price.

HURRY HURRY HURRY

(Not many left. First come first served.)

Brand New Time Date generators at a fraction of their original price. Only £132 inclusive. Normal price £477. These generators are mains driven and accept normal composite video in. The produce video out with time/date/day/month/year added to the signal in normal or reverse video. Adjustable positioning anywhere on screen. Switchable character size also provided. A REAL MUST FOR SECURITY APPLICATIONS WHEN RECORDING. We also have a host of used items such as cooling fans power supplies at give away prices, so why not ask for a list?

Send a 40p SAE for our complete range of catalogues.

MOST MAJOR CREDIT CARDS ACCEPTED

CROFTON ELECTRONICS

☎ 05448 557

'KINGSHILL', NEXTEND, LYONSHALL, HEREFORDSHIRE HR5 3HZ

COMPUTER WAREHOUSE

1000's OF BARGAINS FOR CALLERS

THE "ALLADINS" CAVE OF COMPUTER AND ELECTRONIC EQUIPMENT

HOT LINE DATA BASE

DISTEL

The ORIGINAL FREE OF CHARGE dial up data base. Buy, browse or place YOUR OWN AD for goods or services to sell. 1000's of stock items, spares and one off bargains. Updated daily. ON LINE NOW. CCITT, 8 bit word, no parity. For 300 baud modems call 01-679 1888. For 1200-75 baud modems call 01-679 6183

FREE

Your monitor from its computer! For only £29.95 it becomes a SUPERB HIGH QUALITY * COLOUR * TV SET

The fabulous TELEBOX, an INVALUABLE MUST for the owner of ANY video monitor with a composite input, colour or monochrome. Made by a major UK Co. as a TOP QUALITY, stand alone UHF tuner and costing OVER £75 to manufacture, this opportunity to give your monitor a DUAL FUNCTION must not be missed! The TELEBOX consists of a compact, stylish two tone charcoal moulded case, containing ALL electronics tuner, power supply etc to simply plug in and convert your previously dedicated computer monitor into a HIGH QUALITY COLOUR TV SET, giving a real benefit to ALL the family! Don't worry if your monitor doesn't have sound - THE TELEBOX even has an integral 4 watt audio amplifier for driving an external speaker, PLUS an auxiliary output for superb quality television sound via your headphones or HI FI system etc. Other features include: Compact dimensions of only 15.75" w x 7.5" d x 3.5" h, latest technology, BRITISH manufacture, fully tuneable 7 channel push button tuner, Auto AGC circuit, SAW filter, LED status indicator, fully isolated 240v AC power supply for total safety, Mains ON-OFF switch etc. Many other uses.

LIMITED QUANTITY - DON'T MISS THIS OFFER!!!

ONLY £29.95 OR £24.94 if purchased with ANY of our video monitors. Supplied BRAND NEW with full instructions and 2 YEAR warranty. Post and packing £3.50 *When used with colour crt

COLOUR & MONOCHROME MONITOR SPECIALS

'SYSTEM ALPHA' 14" COLOUR MULTI INPUT MONITOR

Made by the famous REDIFFUSION Co. for their own professional computer system this monitor has all the features to suit your immediate and future requirements. Two video inputs: RGB and PAL Composite Video, allow direct connection to BBC/IBM and most other makes of micro computers or VCR's, including our very own TELEBOX. An internal speaker and audio amp may be connected to computer or VCR for superior sound quality. Many other features: PIL tube, Matching BBC case colour, Major controls on front panel. Separate Contrast and Brightness - even in RGB mode. Separate Colour and audio controls for Composite Video input, BNC plug for composite input, 15 way 'D' plug for RGB input, modular construction etc.

THE MUST BE ONE OF THE YEAR'S BEST BUYS. PC USER

Supplied BRAND NEW and BOXED with DATA and 90 day guarantee. ONLY £159.00 as above OR IBM PC Version £165.00 15 Day 'D' sct £1.00, BNC sct 75p BNC interface cable £5.50

DECCA 80 16" COLOUR monitor. RGB Input.

Little or hardly used manufacturer's surplus enables us to offer this special converted DECCA RGB Colour Video TV Monitor at a super low price of only £99.00, a price for a colour monitor as yet unheard of! Our own interface, safety modification and special 16" high definition PIL tube, coupled with the DECCA 80 series TV chassis give 80 column definition and quality found only on monitors costing 3 TIMES OUR PRICE. The quality for the price has to be seen to be believed! Supplied complete and ready to plug direct to a BBC MICRO computer or any other system with a TTL RGB output. Other features are: internal speaker, modular construction, auto degaussing circuit, attractive TEAK CASE, compact dimensions only 52cm W x 34 H x 24 D, 90 day guarantee. Although used, units are supplied in EXCELLENT condition. ONLY £99.00 + Carriage.

DECCA 80 18" COLOUR monitor. Composite video input. Same as above model but fitted with Composite Video input and audio amp for COMPUTER, VCR or AUDIO VISUAL use. ONLY £99.00 + Carr.

REDIFFUSION MARK 3, 20" COLOUR monitor. Fitted with standard 75 ohm composite video input and sound amp. This large screen colour display is ideal for SCHOOLS, SHOPS, DISCOS, CLUBS and other AUDIO VISUAL applications. Supplied in AS NEW or little used condition. ONLY £145.00 + Carr.

BUDGET RANGE EX EQUIPMENT MONOCHROME video monitors.

All units are fully tested and set for 240v standard working with composite video inputs. Units are pre tested and set up for up to 80 column use. Even when MINOR screen burns exist - normal data displays are unaffected 30 day guarantee.

12" KGM 320-1 B/W bandwidth input, will display up to 132 x 25 lines. £32.95

12" GREEN SCREEN version of KGM 320-1. Only £39.95

9" KGM 324 GREEN SCREEN fully cased very compact unit. Only £49.00

Carriage and insurance on all monitors £10.00

DC POWER SUPPLY SPECIALS

GOULD OF443 enclosed, compact switch mode supply with DC regulated outputs of +5v @ 5.5a, +12v @ 0.5a, -12v @ 0.1a and -23v @ 0.02a. Dim 18 x 11 x 6 cm. 110 or 240v input. BRAND NEW only £16.95

GOULD G6-40A 5v 40 amp switch mode supply NEW £130.00

AC-DC Linear PSU for DISK drive and SYSTEM applications. Constructed on a rugged ALLY chassis to continuously supply fully regulated DC outputs of +5v @ 3 amps, -5v @ 0.8 amps and +24v @ 2.5 amps. Short circuit and overvoltage protected. 100 or 240v AC input. Dim 28 x 12.5 x 7 cm NEW £49.94

Carriage on all PSUs £3.00

KEYBOARDS

Manufacturer's BRAND NEW surplus

DEC L434 Uncoded keyboard with 67 quality gold plated switches on X-Y matrix - ideal micro conversions etc £24.95

AMKEY MPNK114 Superb word processor chassis keyboard on single PCB with 118 keys. Many features such as On board Micro, Single 5v rail, full ASCII coded character set with 31 function keys, numeric keypad, cursor pad and 9600 baud SERIAL TTL ASCII OUTPUT! Less than half price. Only £69.00 with data. Carriage on Keyboards £3.50



DON'T MISS THE CPM Deal OF the CENTURY

The FABULOUS CPM TATUNG PC2000 Professional Business System

A cancelled export order and months of negotiation enables us to offer this professional PC, CPM system, recently on sale at OVER £1400, at a SCOOP price just over the cost of the two internal disk drives!! Or less than the price of a dumb terminal!!

Not a toy, the BIG BROTHER of the EINSTIEN computer, the DUAL PROCESSOR PC2000 comprises a modern stylish three piece system with ALL the necessities for the SMALL BUSINESS, INDUSTRIAL, EDUCATIONAL or HOBBYIST USER. Used with the THOUSANDS of proven, tested and available CPM software packages such as WORDSTAR, FAST, DBASE2 etc, the PC2000 specification, at our prices, CANNOT BE BEATEN!!

The central processor plinth contains the 64K, Z80A processor, DUAL TEAC 55F 5 1/4" Double sided 40/80 track disk drives (1Mb per drive), PSU, 4K of memory mapped screen RAM, disk controller, RS232, CENTRONICS and system expansion ports, and if that's not enough a ready to plug into STANDARD 8" DRIVE port for up to FOUR 8" disk drives, either in double density or IBM format. The ultra slim 92 key, detachable keyboard features 32 user definable keys, numeric keypad and text editing keys, even its own integral microprocessor which allows the main Z80A to devote ALL its time to USER programs, eliminating "lost character" problems found on other machines. The attractive, detachable 12" monitor combines a green, anti-glare etched screen, with full swivel and tilt movement for maximum user comfort. Supplied BRAND NEW with CPM 2.2, user manuals and full 90 day guarantee. Full data sheet and info on request.

PC2000 System with CPM etc. COST OVER £1400

PC2000 Business System with CPM and 'Ready to Run' FAST Sales and Purchase ledger, supports up to 9000 Accounts, VAT etc. COST OVER £1700

PC2000 Wordprocessor System with CPM and TEC FP25 daisywheel printer

NOW only £399

NOW only £499
Carriage & Insurance £1200

NOW only £799

MODEMS

Join the communications revolution with our super range of DATA MODEMS, prices and specifications to suit all applications and budgets.... BRAND NEW State of the art products.

DACOM DSL2123 Multi standard 300-300, 1200-75 Auto answer etc. £268.00
DACOM DSL2123AQ Auto dial, smart modem with multi standard AUTO SPEED detect, and data buffer with flow control etc. £365.00
DACOM DSL2123GT The CREAM of the intelligent modems, auto dial, auto call, index, buffer etc. £498.00
Stebeck SB1212 V22 1200 baud FULL DUPLEX sync or async optional auto dial. £465.00
TRANSDATA 307A Acoustic coupler 300 baud full duplex, originate only, RS232 interface. £49.00

Ex BRITISH TELECOM full spec, CCITT, ruggedised, bargain offers. Sold TESTED with data. Will work on any MICRO or system with RS232 interface. MODEM 1200-300 baud unit, only 2" high fits under phone. CALL mode only. £45.00
MODEM 20-1, 75-1200 baud. Compact unit for use as subscriber end to PRESTEL, TELECOM GOLD, MICRONET etc. £39.95 + pp £6.50
MODEM 20-2 1200-75 baud. Same as 20-1 but for computer end. £65.00 + pp £6.50
DATEL 2412. Made by SE Labs for BT this two part unit is for synchronous data links at 1200 or 2400 baud using 2780/3780 protocol etc. Many features include 2 or 4 wire working, self test, auto answer etc. COST OVER £800. Our price ONLY £199 + pp £8.00
DATEL 4800, RACAL MFS4800 baud modem, EX BT good working order. ONLY £295.00 + pp £8.00

SPECIAL OFFER

MODEM TG2393. Ex BT, up to 1200 baud, full duplex 4 wire or half duplex over 2 wire line. ONLY £85.00 PER PAIR + pp £10.00

For more information contact our Sales Office.

MATRIX PRINTERS

SPECIAL BULK PURCHASE of these compact, high speed matrix printers. Built in Japan for the Hazeltine Corporation this unit features quality construction giving 100cps bidirectional, full pin addressable graphics, 12 type fonts, up to 95" single sheet or tractor paper handling, RS232 and CENTRONICS parallel interface. Many other features. BRAND NEW and BOXED. COST £240. Our price ONLY £199.00

RECHARGEABLE BATTERIES

Dry Fit MAINTENANCE FREE by Sonnenschein & Yuasa.

A300 07191315 12v 3Ah NEW £13.95

A300 07191312 6v 3Ah NEW £9.95

A300 07191202 6-0-6v 1.8Ah TESTED Ex Equip £5.99

VDU TERMINALS

Standard VDU data entry terminals

at give away prices!!
QUME QVT108. Current product, state of the art terminal with detachable keyboard, 12" Green screen, 2 page RAM, TVI 925, Hazeltine, ADMSA emulations, software support, 25 x 80, Clock, Swivel and tilt base, Printer port, Function keys etc. BRAND NEW and BOXED AT ALMOST HALF PRICE Only £425.00
AJ510 - EX RENTAL, Z80 controlled, 15" green screen 24 x 80 display, graphics, cursor addressing, printer port etc. Very good condition TESTED complete with manual only £225.00
ADS £20 - dumb terminal, used, 12" b/w screen RS232 interface and printer port TESTED. ONLY £125.00. Carriage on terminals £10.00
100's of other terminals in stock. CALL for more details.

SURPLUS SPECIALS ON PRESTEL - VIEWDATA - TELEX

PLESSEY VUTEL, ultra compact unit, slightly larger than telephone features A STANDARD DTMF TELEPHONE (tone dial) with 5" CRT monitor and integral modem etc for direct connection to PRESTEL VIEWDATA etc. Designed to sell to the EXECUTIVE at over £800!! Our price BRAND NEW AND BOXED at only £99.00

DECCAFAX VP1 complete Professional PRESTEL system in slimline desk top unit containing Modern, Numeric keypad, CPU, PSU etc. Connects direct to standard RGB colour monitor. Many other features include: Printer output, Full keyboard input, Cassette port etc. BRAND NEW with DATA. A FRACTION OF COST only £55.00

ALPHANTELE. Very compact unit with integral FULL ALPHA NUMERIC keyboard. Just add a domestic TV receiver and you have a superb PRESTEL system and via PRESTEL the cheapest TELEX service to be found! Many features: CENTRONICS Printer output, Memory dialling etc. Supplied complete with data and DIY mod for RGB or Composite video outputs. AS NEW only £125.00

Post and packing on all PRESTEL units £8.50

EX-STOCK INTEGRATED CIRCUITS

4164 200 ns D RAMS 9 for £11 4116 ns £1.50 2112 £10.00 2114 £2.50 2102 £2.00 6116 £2.50 EPROMS 2716 £4.50 2732 £3.00 2764 £4.95 27128 £5.50 6800 £2.50 6821 £1 68A09 £8 68B09 £10 8085A £5.50 8086 £15 8088 £8 NEC765 £8 WD2793 £28 8202A £22 8251 £7 8748 £15 Z80A £ART £6.50 Z80A CPU £2.00. Thousands of IC's EX STOCK send SAE for list.

DISK DRIVES

Japanese 5 1/4" half height, 80 track double sided disk drives by TEAC, CANON, TOSHIBA etc. Sold as NEW with 90 day guarantee ONLY £85.00
TEC FB-503 Double sided HH 40 TRK NEW £75.00
SUGART SA400 SS FH 35 TRK £55.00
SIEMENS FDD100 SS FH 40 TRK £85.00

carriage on 5 1/4" drives £5.50
Brand New metal 5 1/4" DISK CASES with internal PSU.
DSK1 for 2 HH or 1 FH drive £29.95 + pp £4.00
DSK2 for 1 HH drive £22.95 + pp £3.50
DSK3 3 As DSK1 LESS PSU £12.95 + pp £2.50
DSK4 3 As DSK2 LESS PSU £10.95 + pp £2.00
8" IBM format TESTED EX EQUIPMENT.
SHUGART 800/801 SS £175.00 + pp £8.50
SHUGART 851 DS £250.00 + pp £8.50
TWIN SHUGART 851*2 2 Mb total capacity in smart case, complete with PSU etc. £595.00
MITSUBISHI M2894-83 8" DS1 1 Mb equiv. to SHUGART S480R. BRAND NEW at £275.00 + pp £8.50
DY'SAN 8" Alignment disk £29.00 + pp £1.00
Various disk drive PSU's Ex Stock SEE PSU section.

HARD DISK DRIVES
DRE/DIABLO Series 30 2.5 Mb front load £525.00
Exchangeable version £295.00. ME3029 PSU £95.00
DIABLO 44/DRE4000A, B 5+5 Mb from £750.00
CDC HAWK 5+5 Mb £795.00. CDC 9762 80 MbrMO3 etc. £2500.00
PERTEC D3422 5+5 Mb £495.00
RODIME 5 1/4" Winchester ex-stock from £150 CALL
Clearance items - Sold as seen - No guarantee.
ICL 2314 BRAND NEW 14" Mb. Removable pack hard disk drive, cost over £2000 with data. ONLY £99.00
BASF 8172 8" 23Mb Winchester £199.00
Unless stated all drives are refurbished with 90 day guarantee. Many other drives and spares in stock - call sales office for details.

All prices quoted are for U.K. Mainland, paid cash with order in Pounds Sterling PLUS VAT. Minimum order value £2.00. Minimum Credit Card order £10.00. Minimum BONA FIDE account orders from Government Depts, Schools, Universities and established companies £20.00. Where post and packing not indicated please ADD £1.00 + VAT. Warehouse open Mon-Fri 9.30-5.30, Sat 10.30-5.30. We reserve the right to change prices and specifications without notice. Trade, Bulk and Export

32 Biggin Way, Upper Norwood, London SE19 3XF
Telephone 01-679 4414 Telex 894502 Data 01-679 1888

DEFINITE ELECTRONICS

Go Racing this Summer with the Super Apache Scale Model Car!



The Apache

A superb ready-built scale-model off-road racer complete with a 2-CHANNEL DIGITAL PROPORTIONAL RADIO CONTROL SYSTEM – for the price of the RC system alone!
 All this is included in the price:
 Ready-built 1/4 scale model car (overall size 325 x 186 x 130mm, 12.8 x 7.3 x 5.1in.).
 Front and rear low-profile semi-pneumatic rubber tyres.
 Front wheel independent suspension.
 High or low gear selection.
 Sealed box with differential gearing.
 Powerful motor gives scale speeds up to 140 mph.
 Front and rear coil-spring shock absorbers.
 2-channel digital proportional radio control transmitter (and receiver). (Standard 27MHz AM – no licence required in UK).
 Servo-controlled proportional steering.
 Proportional motor speed control in forward and reverse.

EVEN MORE SUPER SUMMER SAVERS!!

If you are already a Maplin customer, soon you will be receiving (if you haven't already) a bumper bundle of smashing Summertime specials, plus the chance to win a beautiful, sleek, Ford XR3i (if you register in the prize draw before 1st July 1987).

If you are not a Maplin customer, but would love to know more about the special offers and have a chance to win the car, fill in the coupon below with your personal details, tick the appropriate box, and post it now.

*Batteries and ni-cad charger not included. Car requires 8 AA cells (ni-cad recommended YG00A £1.35 each). Transmitter requires 6 AA cells. (alkaline SX69A 55p each or ni-cad as above). NB – and if you have a collision at 100mph or more, you'll be pleased to hear that spare parts are available.

I'LL BE RACING THIS SUMMER WITH MY SUPERB APACHE CAR!

Please rush me my Apache model racer, with 2 channel digital proportional radio control system. I wish to receive:

	Code	Qty	Price
Apache model racer	SX08J		
AA ni-cad battery	YG00A		
AA alkaline battery	SX69A		
		Total	

All prices include VAT. Please add 50p towards postage.
 If order below £5.00, please add 50p handling.

I enclose cheque/postal order made payable to Maplin Electronic Supplies Ltd. or see credit card details.

Here are my personal details:

Customer Number
 Name
 Address
 Post Code

I have never been a Maplin Customer, but I would be pleased to receive details of the super Summertime special offers.

Tick box.

If you have already received the Summertime special offers, please use the Order Coupon supplied with that.

Please register me in the prize draw.

Tick box.

I authorise you to debit my Credit Card account for the cost of goods despatched.

Credit Card Number

Access/American Express Mapcard Visa/
 Delete as required

Note: Goods will be despatched only if the address given is the cardholder's address.
 If ordering by Credit Card please sign:

Signature: Expiry Date

Maplin

Send to:
 Maplin Electronic Supplies Ltd.
 P.O. Box 3, Rayleigh, Essex, SS6 8LR.

Telephone, Credit Card Sales (0702) 554161 Enquiries (0702) 552911

Shops at: Lynton Square, Perry Barr, Birmingham. Tel. 021-356 7292. 159-161 King Street, Hammersmith, London W6. Tel. 01-748 0926. 8 Oxford Rd., Manchester. Tel. 061-236 0281. 46-48 Bevois Valley Rd., Southampton. Tel. 0703 25831. 282-284 London Rd., Westcliff-on-sea, Essex. Tel. 0702-554000.

ETI 7/87