



**ELECTRONICS
TODAY INTERNATIONAL**

TOMORROW'S TECHNOLOGY TODAY

Shape changing robots

**science fiction
or reality?**


**Noise masker
for a quieter
life**

**Switching off
on time for safety**

**Stop thief
cycle alarm**

Plus

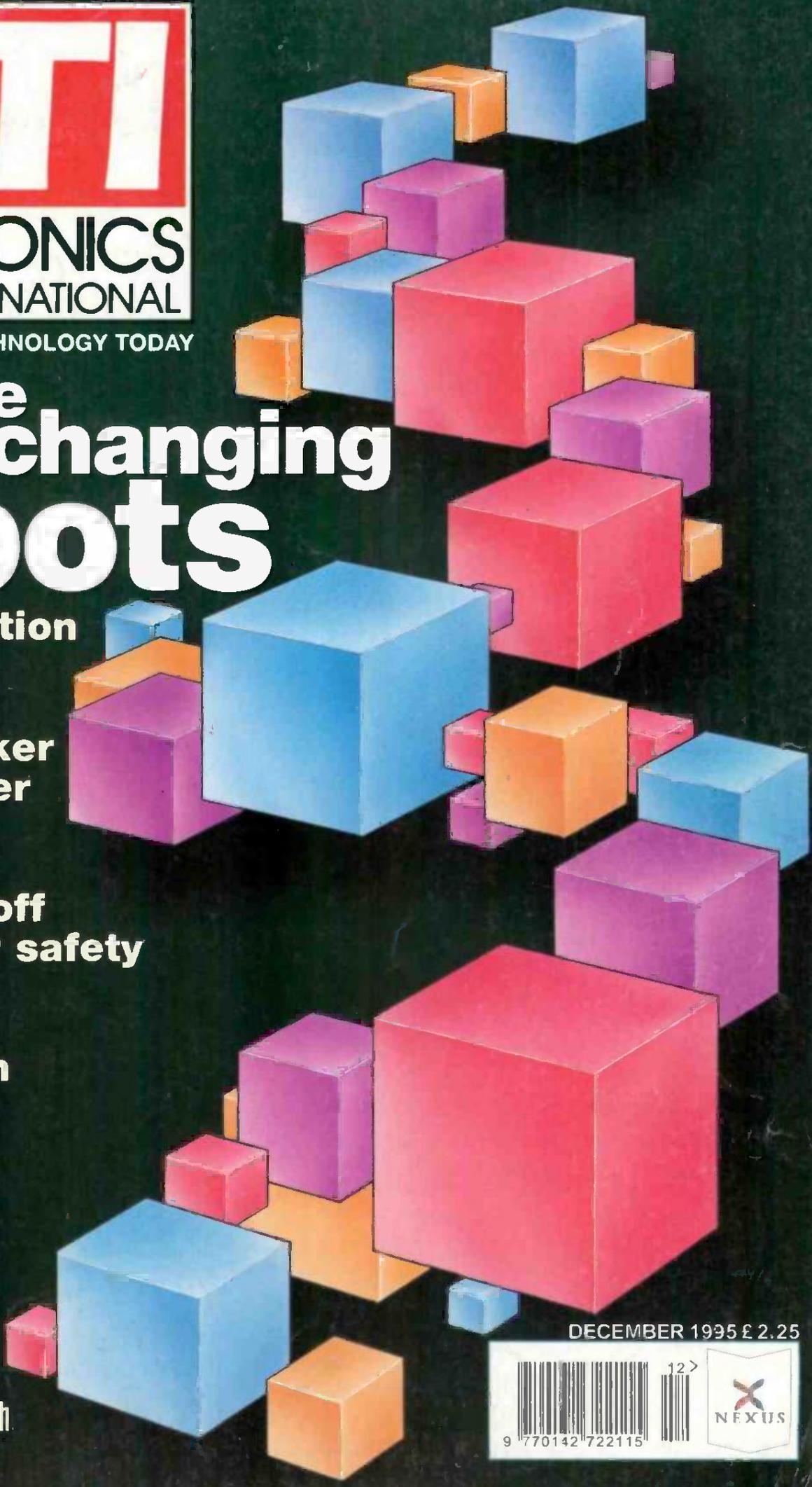- The ETI Basic microcontroller
- The PIC tutorial
- Electronics Workbench a review




DECEMBER 1995 £ 2.25

9 770142 722115 12>

NEW

quickroute 3.5

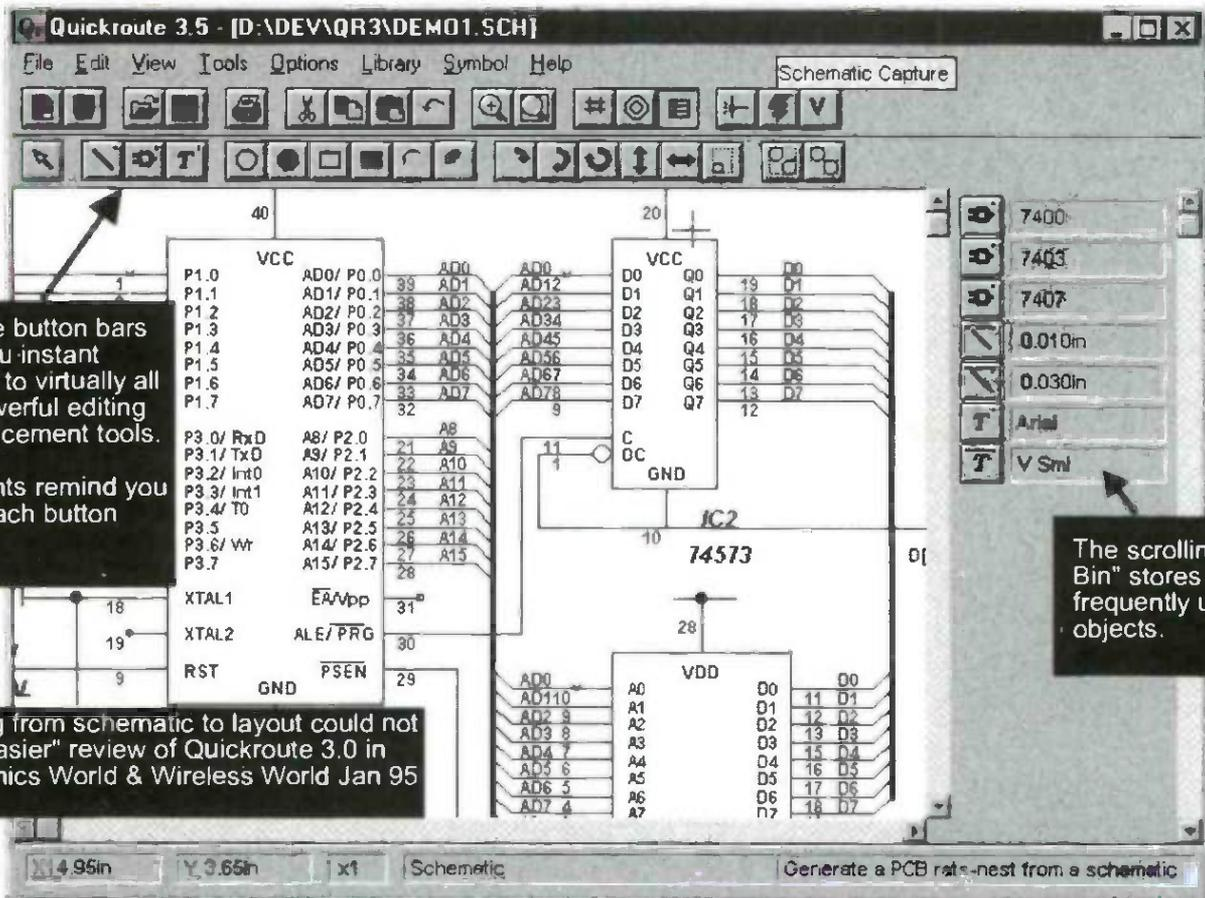


Multiple button bars give you instant access to virtually all the powerful editing and placement tools.

Tool hints remind you what each button does.

"moving from schematic to layout could not be easier" review of Quickroute 3.0 in Electronics World & Wireless World Jan 95

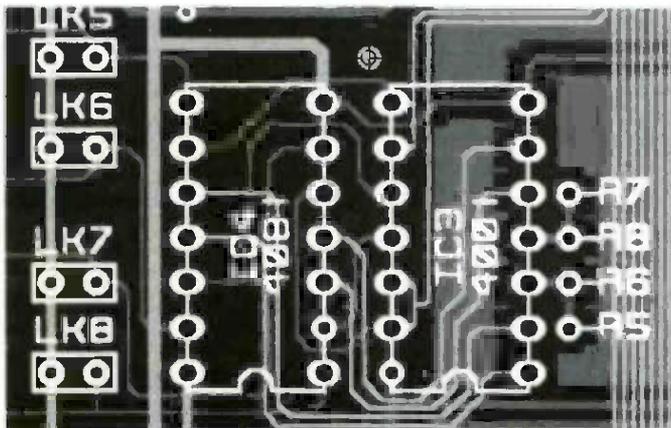The scrolling "Parts Bin" stores frequently used objects.



Contact Quickroute Systems for a free demonstration pack & brochure. Prices quoted exclude post & packing, and V.A.T.

quickroute SYSTEMS Limited
14 Ley Lane, Marple Bridge, Stockport, SK6 5DD. UK.
Tel/Fax 0161 449 7101
email info@quicksys.demon.co.uk

Personal

£68

The Personal Edition gets you started with schematic & PCB drafting for just £68.00. The full set of editing & placement tools are included, with support for 2 copper layers & 1 silk screen layer. You can also create your own custom symbols. Note that the manual is provided on disk.

Designer

£149

The Designer Edition of QR 3.5 includes schematic capture & automatic generation of a PCB 'rats-nest'. Routes can then be manually routed, and checked against the schematic. The full manual is also included.

PRO

£249

The PRO Edition is our base professional product with support for 8 copper layers. It includes schematic capture, automatic PCB rats-nest generation, an auto-router and support for a range of CAD-CAM outputs. Also included is our extended library pack (CMOS, Surface mount PCB symbols, etc).

PRO+

£399

PRO+ is our full professional product. It supports advanced schematic capture (global nets), copper fill, enhanced auto-routing, and a range of export and import capabilities including GERBER import, and SPICE & SpiceAge support.

Contents



Volume 24 No.12



& Features Projects

Shape changing robots 10

A look at the potentially revolutionary work of a British inventor which could have an enormous impact on the lives of all of us

Bar-code reader 18

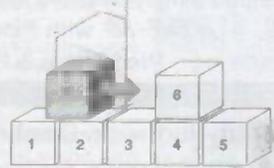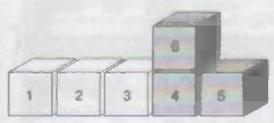Dr Pei An has developed a system which allows a PC to read any bar-code, even the one on the front cover of ETI!



The Electronics Engineer's PC

In this new series, Paul Stenning takes a look at Electronics Workbench, an electronic circuit simulation package

Noise Masker

Robert Penfold devises an electronic solution to the increasingly pervasive problem of noise pollution

Electronic Cycle Alarm

Worried about having your bike stolen? Then Simon Brown's cycle alarm may be the solution to your worries




Timed Isolator

A useful device which will automatically switch off mains equipment after a specified period

28 The ETI Basic microcontroller 52

In part 3 of this premier project, Robin Abbott looks at some other versions of the ETI PIC based controller module, which offer the user a range of additional options

34

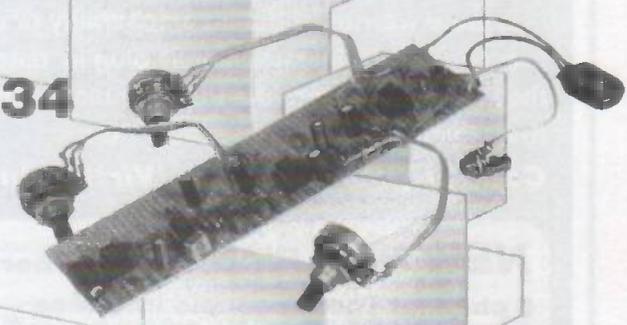

40 Designing a PIC microcontroller based project 56

In Part 6 of this short tutorial series, Bart Tropek concludes his look at the circuit and design of a PIC based alarm clock

Regulars

- News 6
- PCB foils 68
- Roundup 74

Subscribe & Save

Phone the hotline and take advantage of our special offer detailed on page 66

SUBSCRIPTIONS & BACK ISSUES HOTLINES:
01858 435344


ORDERS: ENQUIRES:
01858 435322

Lines Open 9am - 6:30pm

Pico Releases PC Potential

Pico's Virtual Instrumentation enable you to use your computer as a variety of useful test and measurement instruments or as an advanced data logger.

PicoScope
'Virtual instrument' software.

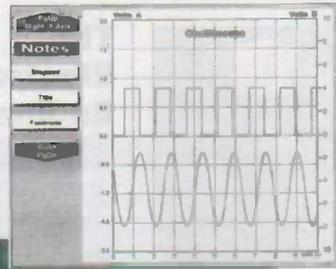

Hardware and software are supplied together as a package - no more worries about incompatibility or complex set-up procedures. Unlike traditional 'plug in' data acquisition cards, they simply plug into the PC's parallel or serial port, making them ideal for use with portable PC's.

PicoLog
Advanced data logging software.

Call for your Guide on 'Virtual Instrumentation'.

NEW from Pico TC-08 Thermocouple to PC Converter

8 channel Thermocouple Interface

- Connects to your serial port - no power supply required.
- Supplied with PicoLog datalogging software for advanced temperature processing, min/max detection and alarm.
- 8 Thermocouple inputs (B,E,J,K,N,R,S and T types)
- Resolution and accuracy dependant on thermocouple type. For type K the resolution is better than 0.1°C.

TC-08 £ 199

TC-08 + Calibration Certificate £ 224

complete with PicoLog, software drivers and connecting cable. A range of thermocouple probes is available.



SLA-16 & SLA-32 Logic Analysers

Pocket sized 16/32 channel Logic Analysers

- Connects to PC serial port.
- Up to 50MHz sampling.
- Internal and external clock modes.
- 8K Trace Buffer.

SLA-16 £ 219
SLA-32 £ 349
with software, power supply and cables



ADC-100 Virtual Instrument

Dual Channel 12 bit resolution

- Digital Storage Scope
- Spectrum Analyser
- Frequency Meter
- Chart Recorder
- Data Logger
- Voltmeter

The ADC-100 offers both a high sampling rate (100kHz) and a high resolution. It is ideal as a general purpose test instrument either in the lab or in the field. Flexible input ranges ($\pm 200\text{mV}$ to $\pm 20\text{V}$) allows the unit to connect directly to a wide variety of signals.

ADC-100 with PicoScope £199
with PicoScope & PicoLog £219



ADC-10 1 Channel 8 bit

- Lowest cost in the Pico range
- Up to 22kHz sampling
- 0 -5V input range

The ADC-10 gives your computer a single channel of analog input. Simply plug into the parallel port.

ADC-10 with PicoScope £49
PicoScope & PicoLog £59



Carriage UK free, Overseas £9 Oscilloscope Probes (x1; x10) £10

PICO TECHNOLOGY



Pico Technology Ltd. Broadway House, 149-151 St Neots Rd, Hardwick, Cambridge. CB3 7QJ
Tel: (0)1954 - 211716 Fax: (0)1954 - 211880 E-mail: 100073.2365 @compuserve.com



Phone or FAX for sales, ordering information, data sheets, technical support. All prices exclusive of VAT

PORTABLE X RAY MACHINE PLANS Easy to construct plans on a simple and cheap way to build a home X-ray machine! Effective device, X-ray sealed assemblies, can be used for experimental purposes. Not a toy or for minors! £65/set. Ref FXP1.

TELEKINETIC ENHANCER PLANS Mystify and amaze your friends by creating motion with no known apparent means or cause. Uses no electrical or mechanical connections, no special gimmicks yet produces positive motion and effect. Excellent for science projects, magic shows, party demonstrations or serious research & development of this strange and amazing psychic phenomenon. £45/set Ref FTKK1.

ELECTRONIC HYPNOSIS PLANS & DATA This data shows several ways to put subjects under your control. Included is a full volume reference text and several construction plans that when assembled can produce highly effective stimuli. This material must be used cautiously. It is for use as entertainment at parties etc only, by those experienced in its use. £15/set. Ref FEH2.

GRAVITY GENERATOR PLANS This unique plan demonstrates a simple electrical phenomena that produces an anti-gravity effect. You can actually build a small mock spaceship out of simple materials and without any visible means - cause it to levitate. £10/set Ref FGRA1.

WORLDS SMALLEST TESLA COIL/LIGHTENING DISPLAY GLOBE PLANS Produces up to 750,000 volts of discharge, experiment with extraordinary HV effects, "Plasma in a jar", St Elmo's fire, Corona, excellent science project or conversation piece. £55/set Ref FBTCILG5.

COPPER VAPOUR LASER PLANS Produces 100mw of visible green light. High coherency and spectral quality similar to Argon laser but easier and less costly to build yet far more efficient. This particular design was developed at the Atomic Energy Commission of NEGEV in Israel. £105/set Ref FCVU1.

VOICE SCRAMBLER PLANS Miniature solid state system turns speech sound into indecipherable noise that cannot be understood without a second matching unit. Use on telephone to prevent third party listening and bugging. £65/set Ref FVSS9.

PULSED TV JOKER PLANS Little hand held device utilises pulse techniques that will completely disrupt TV picture and sound works on FM too! DISCRETION ADVISED. £85/set Ref FBTJ5.

BODYHEAT TELESCOPE PLANS Highly directional long range device uses recent technology to detect the presence of living bodies, warm and hot spots, heat leaks etc. Intended for security, law enforcement, research and development, etc. Excellent security device or very interesting science project. £85/set Ref FBHT1.

BURNING, CUTTING CO2 LASER PLANS Projects an invisible beam of heat capable of burning and melting materials over a considerable distance. This laser is one of the most efficient, converting 10% input power into useful output. Not only is this device a workhorse in welding, cutting and heat processing materials but it is also a likely candidate as an effective directed energy beam weapon against missiles, aircraft, ground-to-ground, etc. Particle beams may very well utilize a laser of this type to blast a channel in the atmosphere for a high energy stream of neutrons or other particles. The device is easily applicable to burning and etching wood, cutting, plastics, textiles etc. £125/set Ref FLC7.

MYSTERY ANTI GRAVITY DEVICE PLANS Uses simple concept. Objects float in air and move to the touch. Defies gravity, amazing gift, conversation piece, magic trick or science project. £67 set Ref FANTIK.

ULTRASONIC BLASTER PLANS Laboratory source of sonic shock waves. Blow holes in metal, produce 'cold' steam, atomize liquids. Many cleaning uses for PC boards, jewellery, coins, small parts etc. £65/set Ref FULB1.

ULTRA HIGH GAIN AMP/STETHOSCOPIC MIKE/SOUND AND VIBRATION DETECTOR PLANS Ultrasensitive device enables one to hear a whole new world of sounds. Listen through walls, windows, floors etc. Many applications shown, from law enforcement, nature listening, medical heartbeat, to mechanical devices. £65/set Ref FHGA7.

ANTI DOG FORCE FIELD PLANS Highly effective circuit produces time variable pulses of acoustical energy that dogs cannot tolerate. £65/set Ref F/DOG2.

LASER BOUNCE LISTENER SYSTEM PLANS Allows you to hear sounds from a premises without gaining access. £125/set Ref F/LLIST1.

CRAWLING INSECT ROASTER PLANS Harmless high frequency energy pulses destroy pests as they crawl into the energy field! £45/set Ref F/RCR1.

LASER LIGHT SHOW PLANS Do it yourself plans show three methods. £6 Ref F/LLS1.

PHASOR BLAST WAVE PISTOL SERIES PLANS Handheld, has large transducer and battery capacity with external controls. £65/set Ref F/PSP4.

INFINITY TRANSMITTER PLANS Telephone line grabber/room monitor. The ultimate in home/office security and safety! simple to use! Call your home or office phone, push a secret tone on your telephone to access either: A) On premises sound and voices or B) Existing conversation with break-in capability for emergency messages. £7 Ref F/TELEGRAB.

BUG DETECTOR PLANS Is that someone getting the goods on you? Easy to construct device locates any hidden source of radio energy! Sniffs out and finds bugs and other sources of bothersome interference. Detects low, high and UHF frequencies. £55/set Ref F/BD1.

ELECTROMAGNETIC COIL GUN PLANS Projects a metal object a considerable distance - requires adult.

ELECTRIC MAN PLANS. SHOCK PEOPLE WITH THE TOUCH OF YOUR HAND! £55/set Ref F/EMA1.

PARABOLIC DISH MICROPHONE PLANS Listen to distant sounds and voices, open windows, sound sources in 'hard to get' or hostile premises. Uses satellite technology to gather distant sounds and focus them to our ultra sensitive electronics. Plans also show an optional wireless link system. £85/set Ref F/PM5.

2 FOR 1 MULTIFUNCTIONAL HIGH FREQUENCY AND HIGH DC VOLTAGE, SOLID STATE TESLA COIL AND VARIABLE 100,000 VDC OUTPUT GENERATOR PLANS Operates on 9-12vdc, many possible experiments. £10 Ref F/HVM7/TCL4.

WOLVERHAMPTON BRANCH NOW OPEN AT WORCESTER ST W'HAMPTON TEL 01902 22039

MINI FM TRANSMITTER KIT Very high gain preamp, supplied complete with FET electret microphone. Designed to cover 88-108 MHz but easily changed to cover 63-130 MHz. Works with a common 9v (PP3) battery. 0.2W RF. £7 Ref 1001.

ELECTRONIC SIREN KIT Impressive 5 watt power output. Ideal for car/bike alarm etc. 6-12v dc max current 1A, 1.2kHz £6 Ref 1003.

3-30V POWER SUPPLY KIT Variable, stabilized power supply for lab use. Short circuit protected, suitable for professional or amateur use 24v 3A transformer is needed to complete the kit. £14 Ref 1007.

1 WATT FM TRANSMITTER KIT Supplied with piezo electric microphone 8-30vdc. At 25-30v you will get nearly 2 watts! £12 ref 1009.

FM/AM SCANNER KIT Well not quite, you have to turn the knob yourself but you will hear things on this radio that you would not hear on an ordinary radio (even TV). Covers 50-160mhz on both AM and FM. Built in 5 watt amplifier, inc speaker. £15 ref 1013.

MOSQUITO REPELLER KIT Modern way to keep midges at bay! Runs for about a month on one 1.5v battery. £7 Ref 1015.

3 CHANNEL SOUND TO LIGHT KIT Wireless system, mains operated, separate sensitivity adjustment for each channel, 1,200 w power handling, microphone included. £14 Ref 1014.

MOTORBIKE/CYCLE TREMBLER ALARM KIT Adjustable sensitivity, preset alarm time, auto reset. Could be connected to horn etc. £12 Ref 1011.

0-5 MINUTE TIMER KIT adjustable, will switch up to 2A mains. Perfect for alarms, photography, etc. £7 Ref 1020.

4 WATT FM TRANSMITTER KIT Small but powerful FM transmitter, 3 RF stages, microphone and audio preamp included. £20 Ref 1028.

STROBE LIGHT KIT Adjustable from 1-60 Hz (a lot faster than conventional strobes). Mains operated. £16 Ref 1037.

ULTRASONIC RADAR KIT Ideal as a movement detector with a range of about 10 metres, automate your cat flap! 12v dc, £15 Ref 1049.

LIQUID LEVEL DETECTOR KIT Useful for tanks, ponds, baths, rain alarm, leak detector etc. Will switch 2A mains. £5 Ref 1081.

COMBINATION LOCK KIT 9 key, programmable, complete with keypad, will switch 2A mains. 9v dc operation. £10 ref 1114.

PHONE BUG DETECTOR KIT This device will warn you if somebody is eavesdropping on your line. £6 ref 1130.

ROBOT VOICE KIT Interesting circuit that distorts your voice! adjustable, answer the phone with a different voice! 12vdc £9 ref 1131.

TELEPHONE BUG KIT Small bug powered by the phone line, starts transmitting as soon as the phone is picked up! £8 Ref 1135.

FUNCTION GENERATOR KIT Produces sinusoidal, saw tooth and square waves from 20-20kHz, separate level controls for each shape. Will produce all 3 together. 24vac. £16 ref 1008.

3 CHANNEL LIGHT CHASER KIT 800 watts per channel, speed and direction controls supplied with 12 LEDs (you can fit triacs instead to make kit mains, not supplied) 9-12vdc £17 ref 1026.

12V FLOUORESCENT LAMP DRIVER KIT Light up 4 foot tubes from your car battery! 9v 2a transformer also required. £8 ref 1069.

VOX SWITCH KIT Sound activated switch ideal for making bugging tape recorders etc. adjustable sensitivity. £8 ref 1073.

INCAR SOUND TO LIGHT KIT Puts some atmosphere in your car with this mini 3 channel sound to light. Each channel has 6 leds. £10 ref 1086.

7W HI FI AMPLIFIER KIT Useful, powerful, ideal for audio systems, intercoms etc. 12-18vdc £7 ref 1025.

PHONE CALL RELAY KIT Useful device that operates a relay whenever the phone rings. Switches mains at 2A. £10 ref 1122.

LEAD ACID CHARGER KIT Two automatic charging rates, visual indication of battery state, ideal for alarm systems etc, 100mA 12vdc £12 ref 1095.

CAR ALARM KIT Works on voltage drop and vibration, entry/exit delays, adjustable alarm duration. Ideal caravans etc. £12 ref 1019.

PORTABLE ALARM KIT Based on mercury switch, alarm continues to sound until reset by owner. Buzzer inc. £11 ref 1150.

PREAMP MIXER KIT 3 input mono mixer, sep bass and treble controls plus individual level controls, 18vdc, input sens 100mA. £15 ref 1052.

METAL DETECTOR KIT Range 15-20cm, complete with case, 9vdc. £8 ref 1022.

SINGLE CHANNEL SOUND TO LIGHT KIT Mains operated, add rhythm to your party for only £8 ref 1006.

SOUND EFFECTS GENERATOR KIT Produces sounds ranging from bird chips to sirens. Complete with speaker, add sound effects to your projects for just £9 ref 1045.

GUITAR PREAMP KIT Complete with tone controls, small enough to fit in any guitar, based on TL082 IC, 9-12vdc £8 Ref 1091.

16 WATT FM TRANSMITTER (BUILT) 4 stage high power, preamp required 12-18vdc, can use ground plane, yagi or open dipole. £69 ref 1021.

TELEPHONE AMPLIFIER KIT Very sensitive amplifier which uses a pickup coil (supplied) will let you follow a conversation with out holding the phone. £11 ref 1059.

*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

BULL ELECTRICAL

250 PORTLAND ROAD, HOVE, SUSSEX.

BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE

WITH ORDER PLUS £3 POST PLUS VAT.

PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS

WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500

FAX 01273 323077

HUMIDITY METER KIT Builds into a precision LCD humidity meter, 9 ic design, pcb, lcd display and all components included. £49

PC TIMER KIT Four channel output controlled by your PC, will switch high current mains with relays (supplied). Software supplied so you can program the channels to do what you want whenever you want. Minimum system configuration is 286, VGA, 4.1, 640k, serial port, hard drive with min 100k free. £24.99

DIVING RODS Expensive technology cannot challenge the fool proof art of water diving, passed down from generation to generation. Seeing is believing. Use in the home, garden, countryside or desert, it's divinely simple! £4.99 a pair ref E3.

HUGE BUBBLE MAKING KIT You'll be amazed at the size of the bubbles you can achieve with this bubble making kit. Once you have got the knack it's possible to make bubbles of up to 40 feet long. £11.99 ref E9.

FM CORDLESS MICROPHONE This unit an FM broadcasting station in miniature, 3 transistor transmitter with electret condenser mic + fet amp design result in maximum sensitivity and broad frequency response. 90-105mhz, 50-1500hz, 500 foot range in open country! PP3 battery required. £15.00 ref 15P42A.

MAGNETIC MARBLES They have been around for a number of years but still give rise to curiosity and amazement. A pack of 12 is just £3.99 ref G1R20.

STETHOSCOPES A fully functioning stethoscope for all those intricate projects. Enables you to listen to motors, pipes, heartbeats, walls, insects etc. £6 ref MAR6P6.

NICKEL PLATING KIT Professional electroplating kit that will transform rusting parts into showpieces in 3 hours! Will plate onto steel, iron, bronze, gunmetal, copper, welded, silver soldered or brazed joints. Kit includes enough to plate 1,000 sq inches. You will also need a 12v supply, a container and 2 12v light bulbs. £39.99 ref NIK39.

SHOP WOBBLERS! Small assemblies designed to take D size batteries and 'wobble' signs about in shops! £3.99 Ref SEP4P2.

OMRON ELECTRONIC INTERVAL TIMERS.

*****NEW LOW PRICES TO CLEAR!*****

Miniature adjustable timers, 4 pole o/o output 3A 240v, HY1230S, 12vDC adjustable from 0-30 secs. £4.99

HY1210M, 12vDC adjustable from 0-10 mins. £4.99

HY1260M, 12vDC adjustable from 0-60 mins. £4.99

HY2460M, 24vAC adjustable from 0-60 mins. £2.99

HY243H, 24vAC adjustable from 0-3 hours. £2.99

HY2401S, 240v adjustable from 0-1 secs. £4.99

HY2405S, 240v adjustable from 0-5 secs. £4.99

HY24060m, 240v adjustable from 0-60 mins. £6.99

DRINKING BIRD Remember these? Hook onto wine glass (supplied) and they drink, stand up, drink, stand up. ETC! £4 each Ref E1

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

BUGGING TAPE RECORDER Small voice activated recorder, uses micro cassette complete with headphones. £28.99 ref MAR25P1.

PLUG IN ACORN PSU 19v AC 14w, £2.99 REF MAG3P10

POWER SUPPLY fully cased with mains and o/p leads 17v DC 900mA output, Bargain price £5.99 ref MAG6P9

9v DC POWER SUPPLY Standard plug in type 150mA 9v DC with lead and DC power plug, price for two is £2.99 ref AUG3P4

13.8V 1.9A psu cased with leads. Just £9.99 REF MAG10P3

INFRA RED REMOTE CONTROLLERS Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

MAINSCABLE Precut black 2 core 2 metre lengths ideal for repairs, projects etc. 50 metres for £1.99 ref AUG2P7.

COMPOSITE VIDEO KIT, Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

UNIVERSAL PC POWER SUPPLY complete with flyleads, switch, fan etc. 200w at £20 REF: MAG20P3 (265x155x125mm).

GYROSCOPE About 3" high and an excellent educational toy for all ages! Price with instruction booklet £6 Ref E15.

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector, 150watt, 12v fan, iec inlet and on/off switch. £12 Ref EF6.

VENUS FLYTRAP KIT Grow your own carnivorous plant with this simple kit £3 ref EF34.

TWEETERS 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

6"X12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. Bargain price just £5.99 ea REF MAG6P12.

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG5P13 ideal for experimenters! 30 m for £12.99 ref MAG13P1

ROCK LIGHTS Unusual things these, two pieces of rock that glow when rubbed together believed to cause rain! £3 a pair Ref EF29.

3" by 1" AMORPHOUS SOLAR PANELS 14.5v, 700mA 10 watts, aluminium frame, screw terminals. £44.95 ref MAG45.

ELECTRONIC ACCUPUNCTURE KIT Builds into an electronic version instead of needles! good to experiment with. £7 ref 7P30

SHOCKING COIL KIT Build this little battery operated device into all sorts of things, also gets worms out of the ground! £7 ref 7P36.

FLYING PARROTS Easily assembled kit that builds a parrot that actually flaps its wings and flies 50 m range £6 ref EF2

HIGH POWER CATAPULTS Hinged arm brace for stability, tempered steel yoke, super strength latex power bands. Departure speed of ammunition is in excess of 200 metres per hour! Range of over 200 metres! £7.99 ref R/9.

BALLON MANUFACTURING KIT British made, small blob blows into a large, long lasting balloon, hours of fun! £3.99 ref G1E9P9R

WE BUY SURPLUS STOCK FOR CASH

FREE CATALOGUE


1995 100 PAGE CATALOGUE NOW AVAILABLE, 45P STAMP OR FREE ON REQUEST WITH ORDER.

Halfsize Industrial Single Board PC

The AMC-350A comes equipped with a 80386SX-40 or 80486SLC-33 CPU. Also included are two serial RS-232 ports, a bi-directional parallel port, an IDE hard disk drive interface (which controls up to two hard disk drives), and a watchdog timer. The watchdog timer ensures that the CPU will be reset if it stops due to a program or EMI problem, allowing the AMC-350A to be used in stand-alone systems or unmanned environments. With its industrial grade reliability, the AMC-350A can operate continuously at up to 140°F (60°C) temperatures.

The AMC-350A is specifically designed as a compact all-in-one CPU card which incorporates a PC/104 connector into its design, making non-passive backplane applications possible. The 4-layer CPU card turns any system into a 16-bit 386 compatible computer. Its highly compact form and numerous features make it an ideal cost/performance solution for high-end commercial and industrial applications where CPU speed and mean-time-to-repair are critical. In addition, its all-in-one configuration frees up valuable expansion slots. Built using CMOS technology, the AMC-350A consumes very little power.

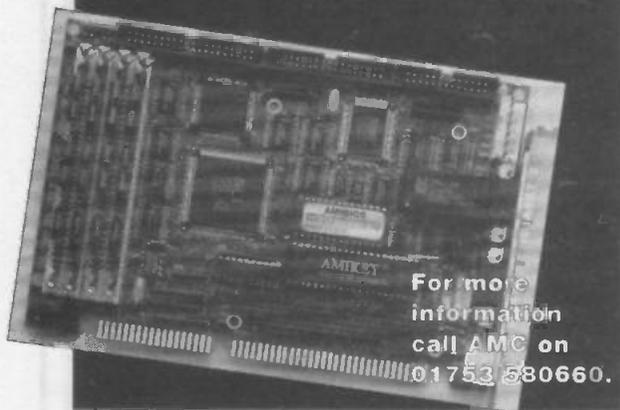The AMC-350A provides 4 SIMM (Single In-Line Memory Module) sockets for its on-board system DRAM. Each socket accepts one 256KB 1MB or 4MB SIMM. Total on-board memory can be configured from 1MB up to 16MB.



For more
information
call AMC on
01753 580660.

Car Battery Booster Charger

The latest in car products from Maplin Electronics is the Car Battery Booster/Charger. Costing £39.99, it is a high quality, powerful battery charger which supplies a useful 15A charge and is also capable of providing a short boost charge or even starting a car.

The compact charger will prove a useful tool to anyone who uses machinery, such as the building and farming industries, or the motor trade. It will also prove valuable to most car owners in winter when engines and batteries are cold and indifferent towards starting - thanks to its ability to supply a healthy 12V 100A boost for up to 5 seconds.

The charger is housed in a robust case with a built-in handle and can be wall-mounted. Two sturdy leads, terminating in heavy-duty crocodile clips, carry the charge to the battery. Built-in overload protection is provided and reset with a push switch.

For further information,
telephone (01702) 552911.



Gang Programming for Microcontrollers & SIMM Modules

MQP Electronics has announced support for many more devices in their range of production devices programming equipment.


Support is now available for the full range of microcontrollers from several leading manufacturers. The microcontrollers can typically be programmed 8 at a time, at very high speeds. Manufacturers supported include Motorola with their 68HC705 and 68HC711 series and NEC with the popular 75P and 78P series. A gang module is also available for the SGS-Thomson ST6 family.

This year, for the first time, MQP also offers gang programming of FLASH SIMM modules, up to 128Mbit and beyond, as well as in the PCMCIA format.

Another recent addition to the S2000 gang programming system is a single site universal programming module. This makes the system arguably the most versatile production programming system available.

MQP Electronics provides programming solutions for both development and high volume production. All MQP programmers offer comprehensive PC software support, with batch controlled modes to automatically deal with the

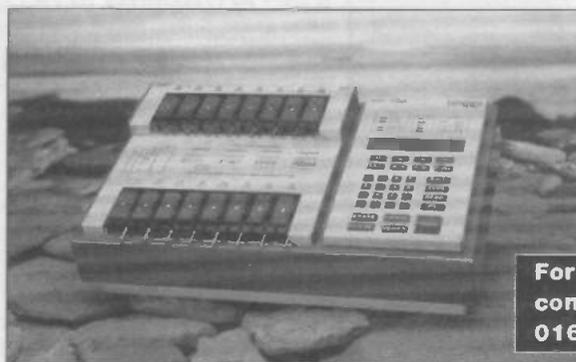special programming options required by users and converters are available to deal with all package variants.



For further details,
contact MQP on
01666 825146.

BULL CLEAROUT SALE

WIRELESS VIDEO BUG KIT Transmits video and audio signals from a miniature CCTV camera (included) to any standard television! All the components including a PP3 battery will fit into a cigarette packet with the lens requiring a hole about 3mm diameter. Supplied with telescopic aerial but a piece of wire about 4' long will still give a range of up to 100 metres. A single PP3 will probably give less than 1 hours operating time. E98 REF EP79. (probably not licensable!)

GOT AN EXPENSIVE BIKE? You need one of our bottle alarms, they look like a standard water bottle, but open the top, insert a key to activate a motion sensor alarm built inside. Fits all standard bottle carriers, supplied with two keys. SALE PRICE £7.99 REF SA32.

GOT AN EXPENSIVE ANYTHING? You need one of our cased vibration alarms, keyswitch operated, fully cased just fit it to anything from videos to caravans, provides a years protection from 1 PP3 battery, UK made. SALE PRICE £4.99 REF SA33.

DAMAGED ANSWER PHONES These are probably beyond repair so they are just £4.99 each. Mainly response 200 machines. REF SA30.

COMMODORE GAMES CONSOLES Just a few of these left to dear at £5 ref SA31. Condition unknown.

COMPUTER DISC CLEAROUT We are left with a lot of software packages that need clearing so we are selling at disc value only 50 discs for £4, that's just 8p each!! (four choice of discs) SALE PRICE £4 ref EP66

IBM PS2 MODEL 160Z CASE AND POWER SUPPLY Complete with fan etc and 200 watt power supply. SALE PRICE £8.95 ref EP67

DELL PC POWER SUPPLIES 145 watt, +5, -5, +12, -12, 150x150x85mm complete with switch, flyleads and IEC socket. SALE PRICE £9.99 ref EP65

1.44 DISC DRIVES Standard PC 3.5" drives but returns so they will need attention SALE PRICE £4.99 ref EP68

1.2 DISC DRIVES Standard 5.25" drives but returns so they will need attention SALE PRICE £4.99 ref EP69

PP3 NICADS New and unused but some storage marks. SALE PRICE £4.99 ref EP52

SOLAR PANELS 3v output with two flyleads, 100x60 mm pack of 10 SALE PRICE £6.99 ref EP56

DELL PC POWER SUPPLIES (Customer returns) Standard PC psu's complete with fly leads, case and fan, pack of two psu's SALE PRICE £5 FOR TWO!! ref EP61

GAS HOBBS AND OVENS Brand new gas appliances, perfect for small flats etc. Basic 3 burner hob SALE PRICE £24.99 ref EP72. Basic small built in oven SALE PRICE £79 ref EP73

BITS AND BOBS We have a quantity of cased modems, multiplexers etc different specs but ideal strippers. SALE PRICE £4 each ref EP63

RED EYE SECURITY PROTECTOR 1,000 watt outdoor PIR switch SALE PRICE £9.99 ref EP57

ENERGY BANK KIT 100 6"x6" 6v 100mA panels, 100 diodes, connection details etc. £69.95 ref EP112

CCTV CAMERA MODULES 46x70x29mm, 30 grams, 12v 100mA, auto electronic shutter, 3.6mm F2 lens, GCIR, 512x492 pixels, video output is 1v p-p (75 ohm). Works directly into a scart or video input on a tv or video. IR sensitive. £79.95 ref EP137.

IR LAMP KIT Suitable for the above camera enables the camera to be used in total darkness! £5.99 ref EP138.

PASTEL ACCOUNTS SOFTWARE, does everything for all sizes of businesses, includes wordprocessor, report writer, windowing, networkable up to 10 stations, multiple cash books etc. 200 page comprehensive manual. 90 days free technical support (0345-326009 try before you buy) Current retail price is £128, SALE PRICE £9.95 ref SA12, SAVE £120!!

MINI MICRO FANS 12v 1.5" sq SALE PRICE £2. Ref SA13.

REUSEABLE HEAT PACKS. Ideal for fishermen, outdoor enthusiasts elderly or infirm, warming food, drinks etc, defrosting pipes etc reusable up to 10 times, lasts for up to 8 hours per go, 2,000wh energy, gets up to 90 degC. SALE PRICE £9.95 REF SA29

12V 2AMP LAPTOP psu's 110x55x40mm (includes standard IEC socket) and 2m lead with plug. 100-240v IP. SALE PRICE £8.99 REF SA15.

PC CONTROLLED 4 CHANNEL TIMER Control (on/off times etc) up to 4 items (8A 240v each) with this kit. Complete with Software, relays, PCB etc. £25.99 REF 9526

COMPLETE PC 300 WATT UPS SYSTEM Top of the range UPS system providing protection for your computer system and valuable software against mains power fluctuations and cuts. New and boxed, UK made. Provides up to 5 mins running time in the event of complete power failure to allow you to run your system down correctly. SALE PRICE just £89.00.

SOLAR PATH LIGHTS Low energy walklights powered by the sun! built in PIR so they work when you walk past. Includes solar panel & rechargeable bat. SALE PRICE £19.99 REF EP62

BIG BROTHER PSU Cased PSU, 6v 2A output, 2m alp lead, 1.5m input lead, UK made, 220v. SALE PRICE £4.99 REF EP7

WANT TO MAKE SOME MONEY? STUCK FOR AN IDEA? We have collated 140 business manuals that give you information on setting up different businesses, you peruse these at your leisure using the text editor on your PC. Also included is a certificate enabling you to reproduce the manuals as much as you like! SALE PRICE £14 REF EP74

RACAL MODEM BONANZA! 1 Racal MPS1223 1200/75 modem, telephone lead, mains lead, manual and comms software. the cheapest way onto the net! all this for just £13 ref DEC13.

New LASER POINTER. Supplied in kit form, complete with power adjuster, 1.5mw, and beam divergence adjuster. Runs on 2 AAA batteries. Produces thin red beam ideal for levels, gun sights, experiments etc. Cheapest in the UK! just £39.95 ref DEC18. TRADE PRICE £28 MIN 10 PIECES.

RADIO PAGERs Brand new, UK made pocket pagers clearance price is just £4.99 each 100x40x15mm packed with bits! REF SEP5.

BULL TENS UNIT Fully built and tested TENS (Transcutaneous Electrical Nerve Stimulation) unit, complete with electrodes and full instructions. TENS is used for the relief of pain etc in up to 70% of sufferers. Drug free pain relief, safe and easy to use, can be used in conjunction with analgesics etc. £49 REF TEN1

COMPUTER RS232 TERMINALS. (LIBERTY) Excellent quality modern units, (like wise 50, s) 2xRS232, 20 function keys, 50 thro to 38,400 baud, menu driven port, screen, cursor, and keyboard setup menus (18 menu's) £29 REF NOVA.

PC PAL VGA TO TV CONVERTER Converts a colour TV into a basic VGA screen. Complete with built in psu, lead and swave. Ideal for laptops or a cheap upgrade. Supplied in kit form for home assembly. SALE PRICE £25 REF SA34

EMERGENCY LIGHTING UNIT Complete unit with 2 double bulb floodlights, built in charger and auto switch. Fully cased. 6v 8AH lead acid req'd. (secondhand) £4 ref MAGAP11.

SWINGFIRE GUIDED MISSILE WIRE, 4,200 metre reel of ultra thin 4 core insulated cable, 28lbs breaking strain, less than 1mm thick! Ideal alarms, intercoms, fishing, dolls house's etc. SALE PRICE £13.99 ref EP51

ELECTRIC CAR WINDOW DE-ICERS Complete with cable, plug etc SALE PRICE JUST £4.99 REF SA28

ASTEC SWITCHED MODE PSU BM41012 Gives +5 @ 3.75A, +12 @ 1.5A, -12 @ 4A, 230V/110, cased, BM41012, £5.99 ref AUG6P3.

AUTO SUNCHARGER 155x300mm solar panel with diode and 3 metre lead fitted with a cigar plug. 12v 2watt. SALE PRICE £8.99 REF SA25.

TOP QUALITY CENTRIFUGAL MAINS MOTORS SALE PRICE £2 FOR JUST £2.60 REF SA38

ECLATRON FLASH TUBE As used in police car flashing lights etc, full spec supplied, 60-100 flashes a min. SALE PRICE £6.99 REF SA15.

24v AC 96WATT Cased power supply. New. SALE PRICE JUST £9.99 REF SA40

MILITARY SPECGEIGER COUNTERS Unused an straight from Her Majesty's forces. SALE PRICE £44 REF SA16

MICRODRIVE STRIPPERS Small cased tape drives ideal for stripping, lots of useful goodies including a smart case, and lots of components. SALE PRICE JUST £4.99 FOR FIVE REF SA26

SOLAR POWER LAB SPECIAL You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit! SALE PRICE JUST £4.99 REF SA27

RGB/CGA/EGA/TTL COLOUR MONITORS 12" in good condition. Back modded metal case. SALE PRICE £49 REF SA16

SWITCHED MODE PSU ex equip. 60w +5v @5A, -5v @5A, +12v @2A, 12v @5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF MAG7P1

PLUG IN ACORN PSU 19v AC 14w. £2.99 REF MAG3P10

POWER SUPPLY fully cased with mains and alp leads 17v DC 900mA output. Bargain price £5.99 ref MAG6P9

ACORN ARCHMEDES PSU +5v @ 4.4A, on/off sw uncased, selectable mains input, 145x100x45mm SALE PRICE £4.99 REF SA1

13.8V 1.9A psu cased with leads. Just £9.99 REF MAG10P3

PPC MODERN CARDS. These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

200 WATT INVERTER Converts 10-15v DC into either 110v or 240v AC. Fully cased 115x36x156mm, complete with heavy duty power lead, cigar plug, AC outlet socket. Auto overload shutdown, auto short circuit shut down, auto input over voltage shutdown, auto input under voltage shut down (with audible alarm), auto temp control, unit shuts down if overheated and sounds audible alarm. Fused reversed polarity protected. output frequency within 2%, voltage within 10%. A well built unit at an keen price. Just £64.99 ref AUG65.

UNIVERSAL SPEED CONTROLLER KIT Designed by us for the CS motor but ok for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

COMPUTER COMMUNICATIONS PACK kit contains 100m of 6 core cable, 100 cable clips, 2 line drivers with RS232 interfaces and all connectors etc. Ideal low cost method of communicating between PC's over a long distance. Complete kit £5.99.

ELECTRIC MOTOR KIT Comprehensive educational kit includes all you need to build an electric motor. £9.99 ref MAR10P4.

VIEWDATA SYSTEMS made by Phillips, complete with Internal 1200/75 modem, keyboard, psu etc. RGB and composite outputs, menu driven, autodialler etc. SALE PRICE £12.99 REF SA18

AIR RIFLES .22As used by the Chinese army for training purposes, so there is a lot about! £39.95 Ref EF78. 500 pellets £4.50 ref EF80.

PLUG IN POWER SUPPLY SALE FROM £1.60 Plugs in to 13A socket with output lead. Three types available. 9vdc 150mA £1.50 ref SA19, 9vdc 200mA £2.00 ref SA20, 6.5vdc 500mA £2 ref SA21.

VIDEO SENDER UNIT. Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range! (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

***SOME OF OUR PRODUCTS MAY BE UNLICENSABLE IN THE UK**

BULL ELECTRICAL
250 PORTLAND ROAD, HOVE, SUSSEX.
BN3 5QT. (ESTABLISHED 50 YEARS).

MAIL ORDER TERMS: CASH, PO OR CHEQUE
WITH ORDER PLUS £3 POST PLUS VAT.
PLEASE ALLOW 7-10 DAYS FOR DELIVERY PHONE ORDERS
WELCOME (ACCESS, VISA, SWITCH, AMERICAN EXPRESS)

TEL: 01273 203500
FAX 01273 323077

***FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

***MINIATURE RADIO TRANSEIVERS** A pair of walkie talkies with a range up to 2km in open country. Units measure 22x52x155mm. Including cases and earpieces. 2xPP3 req'd. £30.00 pr. REF: MAG30

FUTURE PC POWER SUPPLIES These are 295x135x60mm, 4 drive connectors 1 mother board connector 150Watt, 12v fan, IEC Inlet and on/off switch. SALE PRICE £7.99 REF SA 22

***FM TRANSMITTER KIT** housed in a standard working 13A adapter! the bug runs directly off the mains so lasts forever why pay £700? or price is £15 REF: EF62 Transmits to any FM radio. (this is in kit form with full instructions.)

***FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

TALKING COINBOX STRIPPER COMPLETE WITH COIN SLOT MECHANISMS originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? SALE PRICE JUST £2.50 REF SA23

GAT AIR PISTOL PACK Complete with pistol, darts and pellets £12.95 Ref EF82 extra pellets (500) £4.50 ref EF80

6"x12" AMORPHOUS SOLAR PANEL 12v 155x310mm 130mA. SALE PRICE £4.99 REF SA24

FIBRE OPTIC CABLE BUMPER PACK 10 metres for £4.99 ref MAG6P13 ideal for experimental 30 m for £12.99 ref MAG13P1

MIXED GOODIES PACK. BOX OF MIXED COMPONENTS WEIGHING 2 KILOS YOURS FOR JUST £2.00

SIDE LEVER .177 AIR RIFLE Superb, low priced general purpose rifle, 18" tapered, filled barrel, fully adjustable open sights, wooden stock, very accurate with low recoil, 41". £39.95 ref R/3

4X28 TELESCOPIC SIGHTS Suitable for all air rifles, ground lenses, good light gathering properties. £19.95 ref R/7.

RATTLE BACKS Interesting things these, small piece of solid perspex like material that if you try to spin it on the desk it only spins one way in fact if you spin it the wrong way it stops of its own accord and goes back the other way! £1.99 ref GUJ01.

GYROSCOPES Remember these? well we have found a company that still manufactures these popular scientific toys, perfect gift or for educational use etc. £6 ref EP70

EDIBLE LONG LIFE CANDLES Made from Oleo Beef Steann so you can eat them in an emergency alternatively, you could just light them! Each candle burns for approx 10 hours. 2 for £2.99 ref ON326

HYPOTHERMIA SPACE BLANKET 215x150cm aluminium foil blanket, reflects more than 90% of body heat. Also suitable for the construction of two way mirrors! £3.99 each ref OL04.1

LENSTATIC RANGER COMPASS Oil filled capsule, strong metal case, large luminous points. Sight line with magnifying viewer. 50mm dia, 86gm. £10.99 ref OK604.

RECHARGE ORDINARY BATTERIES UP TO 10 TIMES! With the Battery Wizard! Uses the latest pulse wave charge system to charge all popular brands of ordinary batteries AAA, AA, C, D, four at a time! Led system shows when batteries are charged, automatically rejects unsuitable cells, complete with mains adaptor. BS approved. Price is £21.95 ref EP31.

TALKING WATCH Yes, it actually tells you the time at the press of a button. Also features a voice alarm that wakes you up and tells you what the time is! Lithium cell included. £7.99 ref EP26.

PHOTOGRAPHIC RADAR TRAPS CAN COST YOU YOUR LICENCE! The new multiband 2000 radar detector can prevent even the most responsible of drivers from losing their licence! Adjustable audible alarm with 8 flashing leds gives instant warning of radar zones. Detects X, K, and Ka bands, 3 mile range, 'over the hill' 'around bends' and 'rear trap' facilities, micro size! just 4.25"x2.5"x.75". Can pay for itself in just one day! £79.95 ref EP3.

SNOREBUSTER! A small wristwatch style device that detects the noise of snoring and instantly produces a stimulation to the wrist of the snorer without waking them. The bio feedback effectively prevents future bouts of snoring, thus reducing Snorebuster to only occasional use. 10 of 1,000's sold. £24.99 ref LA15999.

WORLDS SMALLEST TAPLESS MEMO PEN! Not only is the smart pen but will record 20 seconds of memos etc. No more scratching about for scraps of paper! £39.99 ref AA21381.

ELECTRIC TYRE INFLATOR High power micro air compressor inflates tyres, airbeds footballs etc. Includes pressure gauge. £14.99 ref J8231.

MAMOD STEAM ENGINE SP2 Powerful compact model steam engine complete with fuel etc. £39.95 ref SP2.

SANYO NICAD PACKS 120mmx14mm 4.8v 270 mAh suitable for cordless phones etc. Pack of 2 just £5 ref EP78.

WE BUY SURPLUS STOCK FOR CASH FREE CATALOGUE

1995 100 PAGE CATALOGUE NOW AVAILABLE, 45P STAMP OR FREE WITH ORDER.

PORTABLE RADIATION DETECTOR WITH NEW COMPUTER INTERFACE £59

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. ref NOV18

AN5521	1.35	STK73410/2	5.95	TDA5660P	2.50
AN5732	1.40	STK73605	4.50	TDA7072	3.99
AN6327	9.85	STR441	14.75	TDA8370	14.00
AN6577	8.50	STR451	25.00	TDA8405	8.00
BA5114	1.55	STR3125	5.50	TDA8732	5.95
BA6218	1.85	STR4211	5.50	TEA2018A	1.50
BA6219	1.20	STR4090	11.15	TEA2026C	4.50
HA11423	1.65	STR20005	5.00	TEA5170	1.40
HA13119	2.50	STR40090	4.00	TJA2000-4	4.25
KA6210	4.99	STR50103A	3.85	U884B	2.35
LA3220	0.60	STR54041	3.75	U4606B	5.50
LA4183	1.35	STR58041	3.75	UAA1008	3.00
LA4445	1.90	STR80001	6.00	UPC1178	1.05
LA4495	1.40	STR1706	4.75	UPC1182H	5.15
LA4588	2.55	STRD1806	4.50	UPC1278H	2.20
LA7835	2.35	STRD8008	10.00	UPC1420	4.50
LB1416	2.25	TA7227	1.85	UPD1937	3.00
LM301	0.25	TA7271	2.50	25A814	0.71
LM317T	1.50	TA7280	2.25	25A839	1.40
M491BBI	4.75	TA7281	2.20	25A1062	1.00
M494BBI	6.75	TA7698	5.00		
M51393	5.95	TA8200	3.50		
M58655	3.30	TA8210	3.00		
MB3730	1.70	TA8214	3.00		
MB3756	8.00	TA8215	3.00		
STK078	6.00	TA8205	3.95		
STK435	4.00	TA8659	13.00		
STK461	6.00	TA75339	**		
STK2250	7.45	TDA1908A	2.00		
STK4121/2	7.00	TDA2170	3.00		
STK4141/2	5.50	TDA2270	2.50		
STK4142/2	6.50	TDA3500	4.99		
STK4162/2	6.25	TDA3562A-TFK	3.25		
STK4171/2	8.10	TDA3562A-PAILL	3.25		
STK4191/2	8.50	TDA3562A-SSSG	3.00		
STK4352	6.20	TDA3645	8.00		
STK4372	5.65	TDA3650	8.99		
STK4803	7.05	TDA3850	18.99		
STK4843	7.05	TDA4400	1.75		
STK5315	5.85	TDA4500	3.50		
STK5332	1.80	TDA4505A	4.10		
STK5338	3.25	TDA4505B	4.10		
STK5361	4.15	TDA4505M	5.25		
STK5372	2.85	TDA4505K	6.15		
STK5372H	4.15	TDA4660	4.50		
STK5412	3.75	TDA4950	1.40		
STK5471	3.85				
STK5490	4.95				
STK6732	14.00				
STK7226	7.50				
STK7308	4.05				
STK7308	4.05				
STK7348	4.05				
STK7356	4.75				
STK7004	6.50				
STK73410	5.15				

Please phone us for the types not listed. Please add 60p post & packing and then add 17.5% VAT to the total. Callers by appointment only.

J.J. COMPONENTS
63 THE CHASE, EDGEWARE,
MDDX. HA8 5DN, ENGLAND
Hotlines No 081 381 1700 081 952 4641
Free Fax Order Line only: 0800 318498
General Fax 081 381 1700

ATTENTION ALL NORTH AMERICAN READERS!

Did you know that you can order an annual subscription to this magazine direct from our official U.S. subscription representative?

For more information and rates contact:
Wise Owl Worldwide Publications,
4314 West 238th Street,
Torrance, CA 90505 4509
Tel: (310) 375 6258

COMPUTER KNOWLEDGE CALL NOW ON: 0891 515 066

MODEM DOWNLOAD SERVICE V21 UP TO V42bis & V.FC.
* Over 330 file areas to download from *

The latest Shareware, updates & Additions via daily file links to Europe & USA for the PC, Amiga & Atari

Areas of specialisation include DOS, OS/2, Windows/Windows NT, DESQview, Novel, Virus Protection, Dbase/Clipper, Engineering/Electronics & recently DOOM + Much More.

Recreational * Multi User Games Available *
Calls cost 39p per minute cheap rate & 49p per minute at all other times.
MODEM PARAMS: -8 Data Bits, No Parity, 1 Stop Bit.
Computer Knowledge, 3 Station Cottages, Cheddington, LU7 0SQ

WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 7000 SERIES OSCILLOSCOPES
Available from £200 - PLUG-INS SOLD SEPARATELY

TEKTRONIX TA8745 4Ch 100MHz Delay Cursors	£1300
TEKTRONIX TA8455 Dual Trace 60MHz Delay Cursors	£580
TEKTRONIX 2465 4 Channel 30MHz Delay Cursors	£1750
TEKTRONIX 2245A 4 Channel 100MHz Cursor Voltmeter etc	£1800
TEKTRONIX 2235 Dual trace 100MHz Delay	£780
TEKTRONIX 485 Dual Trace 300MHz Delay Sweep	£750
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£500
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£480
TEKTRONIX SC504 Dual Trace 80MHz In 1/1000	£400
TEKTRONIX 2215 Dual Trace 50MHz Delay Sweep	£680
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep	£400
PHILIPS PM2017 Dual Trace 50MHz Delay Sweep	£400
HITACHI V223 Dual Trace 20MHz Delay Sweep	£280
BECKMAN 9025 Dual Trace 20MHz Delay Sweep	£240
HAMEG 412 Dual Trace 20MHz Delay Sweep	£225
GOULD OS 1100 Dual Trace 30MHz Delay Sweep	£280
GOULD OS1100S1 Dual trace 30MHz	£380
KIKUSUI 5530A Dual Trace 35MHz	£220
GOULD OS300 Dual Trace 20MHz (No Handle)	£180
GOULD 4020 Dual Trace 20MHz Digital Storage Cursors	£190
GOULD OS400 Dual Trace 10MHz Digital Storage	£250
GOULD OS4000 Dual Trace 10MHz Digital Storage	£200
H.P. 1714 Dual Trace 100MHz Analogue Storage	£480

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

EATONALTECH 300K11 Syn Sig Gen 1-2000MHz with PK6022 AM/FM Phase Mod	£90A
MARCONI 2019 Syn AM/FM Sig Gen 800kHz-10400kHz	£2000
MARCONI 2048 Syn AM/FM Sig Gen 800kHz-5200kHz	£1800
H.P. 8620C Sweep Osc 5.9-12 MHz or 0.1-2.4GHz	£380
H.P. 8620C Sweep Oscillator Main Frame only	£200
RACAL 9081 Syn AM/FM Sig Gen 5-320MHz	£480
MARCONI TF2937 Automatic Distortion Meter	£200
MARCONI TF2231A Distortion Factor Meter 20Hz-200kHz 0.05% unatt	£280
MARCONI TF8036 Audio Power Meter 50Watt	£380
MARCONI TF2183 Attenuator DC-1GHz	£180
H.P. 8495B Attenuator DC-100kHz 0-1dB in 10dB Steps	£380
TEKTRONIX TDR1102	£1800
R & S Video Noise Meter UPSF2 with UPSF2E2	£1500
H.P. 6160A Programmable Prec Pulse Gen 50MHz	£90A

BRUEL & KJOER EQUIPMENT AVAILABLE
PLEASE ENQUIRE

SPECTRUM ANALYSERS

TEKTRONIX 2710 10kHz - 1.8GHz	£90A
IFR A7500 Synthesised 1 GHz	£4000
H.P. 8585A 0.01-22GHz	£4000
POLARAD 811-1 100kHz-18GHz	£1000
H.P. 142 with 8554B 100kHz-3500MHz	from £1500
H.P. 141T with 8554A & 8552B 100kHz - 18GHz	£780
H.P. 141T with 8554B & 8552B 500kHz - 1250MHz	£600
H.P. 141T with 8553B & 8552A 10kHz - 110MHz	£380
H.P. 141T Main Frame & ONLY GOOD TUBES	£280
MARCONI TF2370 30MHz - 110MHz	£1000
TEKTRONIX 7L5 with Main Frame 70MHz - 5MHz	£1000
H.P. 3585A 20Hz - 40MHz	£20A
H.P. 3580A 5Hz-500Hz	£1000

Used Equipment - Guaranteed. Manuals supplied if possible.
This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of Goods and Carriage.

STEWART OF READING
110 WYKEHAM ROAD, READING, BERKS RG6 1PL
Tel: 01734 268041 Fax: 01734 351696

£30 WORTH OF VOUCHERS

CATALOGUE WAS £2.50 NOW FREE
Only the cost of a stamp

THINK COMPONENTS - THINK CRICKLEWOOD

- TELEVISION & VIDEO SPARES • RESISTORS & CAPACITORS • HI-FI GADGETS & SPEAKERS
- TRANSISTORS & I.C.'s • AUDIOPHILE CAPACITORS
- IN CAR AUDIO • COMPUTER BOARDS • TOOLS & TEST EQUIPMENT • PLUGS SOCKETS & LEADS

NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay	£247
HAMEG OSCILLOSCOPE HME50A (Dual Trace 60MHz Delay Sweep	£353
HAMEG OSCILLOSCOPE HME303 Dual Trace 30MHz Comp. Inst.	£422
HAMEG OSCILLOSCOPE HME305-3 Dual Trace 20MHz Digital Storage	£883

All other models available at all oscilloscopes supplied with 2 probes.

BLACK STAR EQUIPMENT (P&P all units £5)

APOLLO 10 100MHz Counter Timer Ratio/Period/Time File etc	£223
APOLLO 100 100MHz (as above with more functions)	£325
METRO 100 FREQUENCY COUNTER 100MHz	£119
METRO 600 FREQUENCY COUNTER 600kHz	£100
METRO 1000 FREQUENCY COUNTER 10kHz	£300
AURTON 500 FUNCTION GEN 0.1Hz-500kHz Sine/Sqr/Tri	£125
ORION COLOUR BAR GENERATOR Pal/TV/Video	£243

All other Black Star equipment available

MANY OTHER POWER SUPPLIES AVAILABLE


CRICKLEWOOD ELECTRONICS

PLEASE SEND ME A COPY OF THE 1995 CRICKLEWOOD CATALOGUE.

Name: _____
Address: _____
_____ETI

Cricklewood Electronics Ltd, 40-42 Cricklewood Broadway, London NW2 3ET. Tel: 0181-450 0995 Fax: 0181-208 1441

8 BIT, 250 MSPS A/D Card

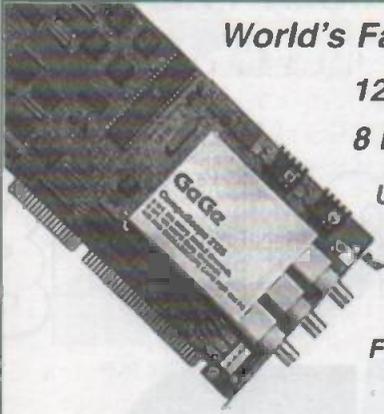

World's Fastest A/D Cards

12 bit, 60 MSPS A/D
8 bit, 250 MSPS A/D

Up to 16 meg memory
Up to 32 inputs
Low Noise
LabVIEW Driver
C & BASIC Drivers
Free Software Support
New PCI Version.

Ultra-Fast D/A Cards
Also Available

Scope Emulation
Software Included!!

CSLITE	8 bit/40 MSPS/16k	£495
CS250	8 bit/100 MSPS/32K	£2500
CS2125	8 bit/250 MSPS/256K	£3600
CS1012	12 bit/20 MSPS/512K	£4995
CS6012	12 bit/60 MSPS/512K	£6400
CS6012/PCI	12 bit/60 MSPS/512K	£6400


**STRATEGIC
TEST**

Tel: 01734 795950
Fax: 01734 795951

Turn Your PC into a Powerful Real-Time Spectrum Analyzer

Features

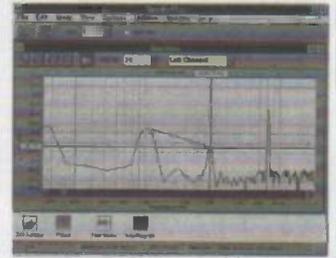- Dual channel FFT Analyzer
- Narrowband and 1/3 Octave
- Real-Time, Record, Playback, or Post Process
- Time Series, Spectrum, Phase, 256 Color Spectrogram and 3-D Surface plots
- FFT sizes through 16,384 pts
- Digital Filtering
- Signal Generation
- Decimation and Triggering
- Overlap Processing



Applications

- Acoustic Research
- Distortion Measurements
- Noise Analysis
- Frequency Response Testing
- Vibration Measurements
- Transfer Function Measurements

System Requirements

- 386/486/Pentium and Windows 3.1
- Windows compatible sound card
- 4 MB RAM minimum
- Mouse and Math coprocessor
- 256 Color VGA (for spectrogram)

Software only £295

Software plus pro quality* sound card £595

*DC-19kHz flat to 0.2 dB, THD <0.005%, S/N - 90 dB

2 channel, 16 bit, 44.1 kHz sampling.

PCMCIA sound cards also available

Call now for Free Demo Disk!


**STRATEGIC
TEST**

Tel: 01734 795950
Fax: 01734 795951

DEVELOPMENT AND PRODUCTION SOLUTIONS

- Gang Programmers
- Development Programmers
- Universal Cross Assembler
- Package Converters
- Development Tools
- Emulator Pods + Adapters

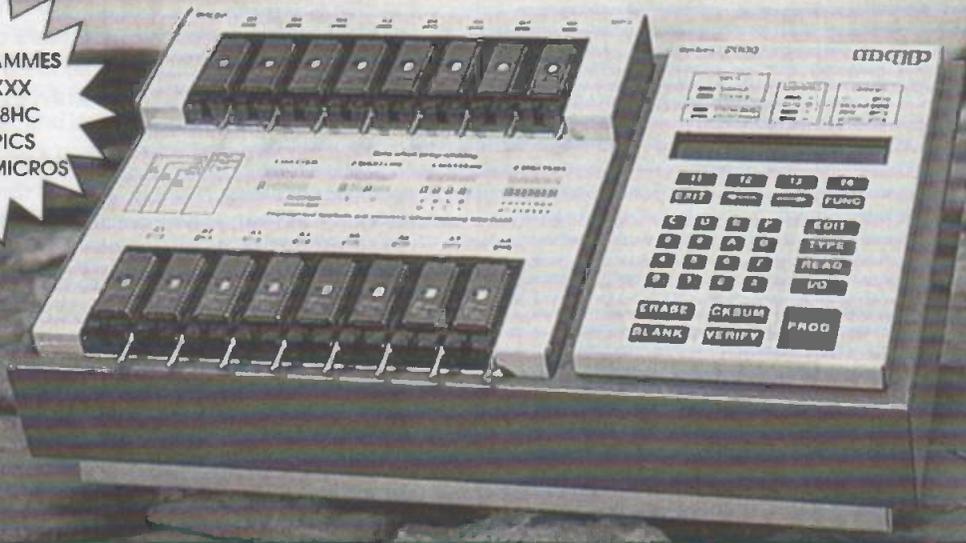GANG PROGRAMMES
NEC 78/75PXXX
MOTOROLA 68HC
HITACHI H8, PICS
SGS AND INTEL MICROS



WQP


ELECTRONICS Ltd

Park Road Centre, Malmesbury, Wiltshire SN11 0BX UK

Tel: 01 666 825146 Fax: 01 666 825141

e/mail 100447_1124@compuserve.com




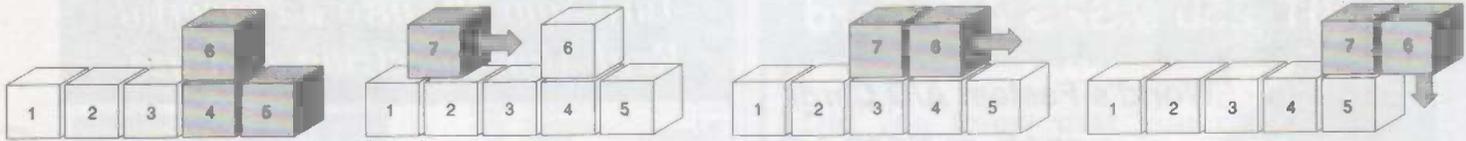
IRELAND 1-2800995
GERMANY 089/4602071
NORWAY 0702-17890
ITALY 02 92 10 35 54
FRANCE 1 69 30 13 79
SWEDEN 08 590 32 185
Also born ELECTROSPED



Shape Changing

RO

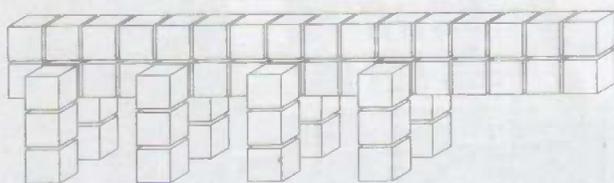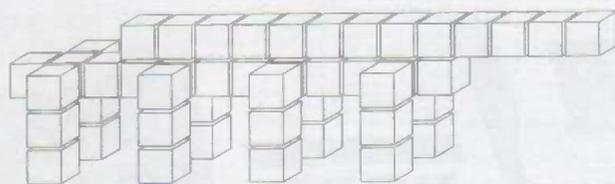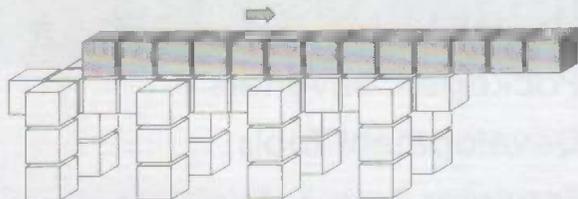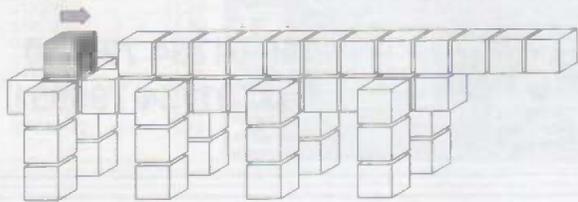A look into the future as envisioned by a British inventor, a future filled with robots ranging in size from smaller than a grain of sand to as big as a skyscraper, yet all created using a single simple cubic unit.




Walking mechanism with legs

For the past 17 years, a North London electrical engineer and computer programmer, Joe Michael, has had a dream - a dream which started when he was still a student, a dream to design and build the world's first shape-changing robot.


The shape-changing robot idea was initially conceived as some way of moving atoms and molecules to create new types of matter, but as a student of biochemistry he quickly realised that such a technique was either impossible or, at best, extremely difficult to implement. It was then that he hit on the idea of using a fractal-like system of small interlocking cubes that can slide over each other and, in so doing, form any desired shape.

In pursuit of this idea, he studied electrical engineering and computing, spending most of his time and money working on the idea and developing it to a stage where he could demonstrate its practicality. After years of work, and the expenditure of over £35,000 in securing world-wide patents, his dream will become a reality when the first prototype units are completed in early 1996.

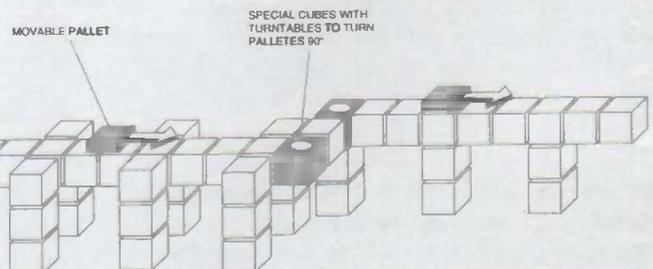The concept developed by Joe Michael is already attracting considerable interest from a variety of disciplines from all around the world. Indeed, at a recent nuclear industry exhibition in Lyons, France, his modest stand was visited by over 150 leading engineers, most of whom were highly impressed, and now eagerly await the first practical demonstration.



Pallet transportation system

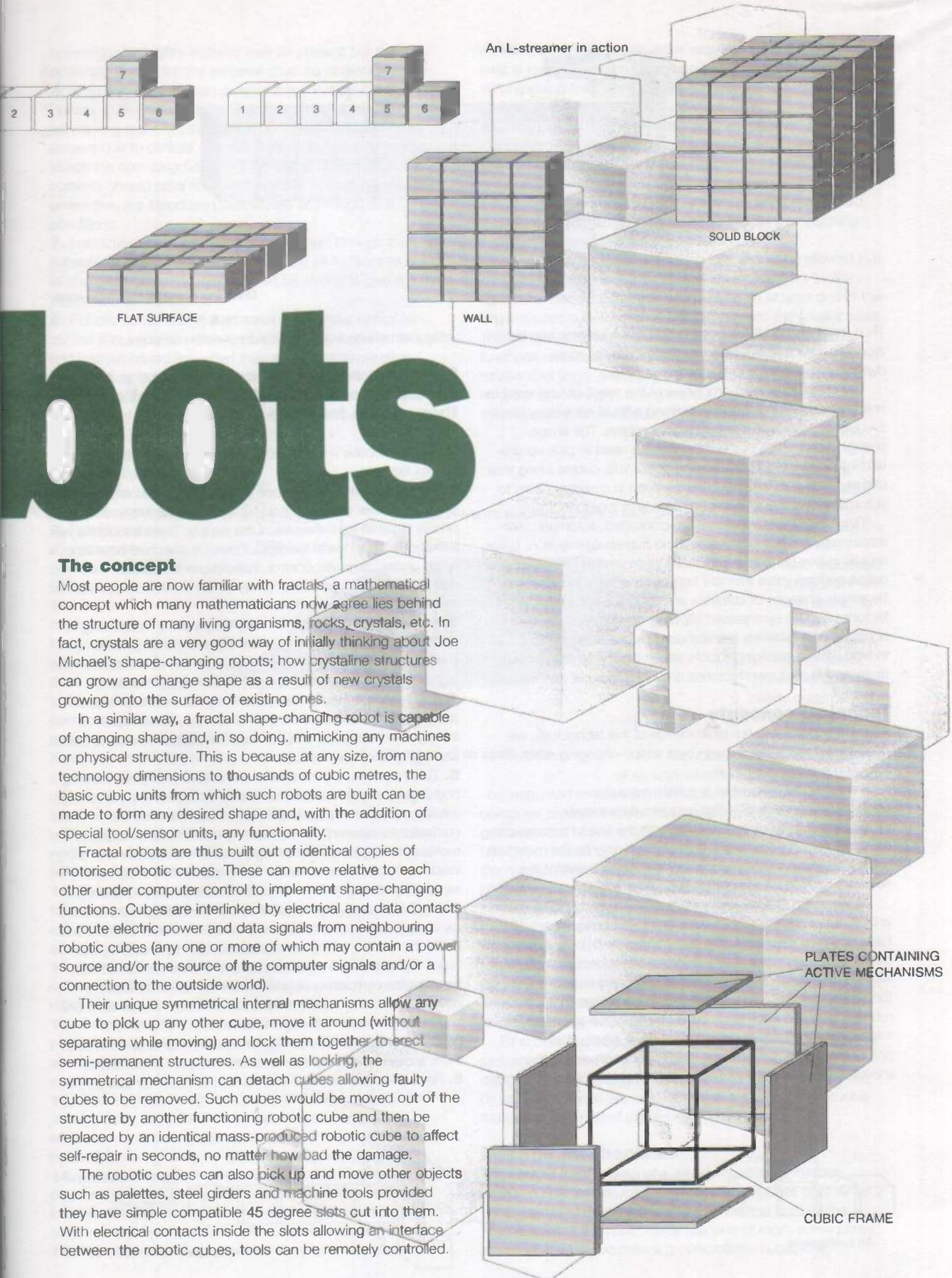

bots

The concept


Most people are now familiar with fractals, a mathematical concept which many mathematicians now agree lies behind the structure of many living organisms, rocks, crystals, etc. In fact, crystals are a very good way of initially thinking about Joe Michael's shape-changing robots; how crystalline structures can grow and change shape as a result of new crystals growing onto the surface of existing ones.

In a similar way, a fractal shape-changing robot is capable of changing shape and, in so doing, mimicking any machines or physical structure. This is because at any size, from nano technology dimensions to thousands of cubic metres, the basic cubic units from which such robots are built can be made to form any desired shape and, with the addition of special tool/sensor units, any functionality.

Fractal robots are thus built out of identical copies of motorised robotic cubes. These can move relative to each other under computer control to implement shape-changing functions. Cubes are interlinked by electrical and data contacts to route electric power and data signals from neighbouring robotic cubes (any one or more of which may contain a power source and/or the source of the computer signals and/or a connection to the outside world).

Their unique symmetrical internal mechanisms allow any cube to pick up any other cube, move it around (without separating while moving) and lock them together to erect semi-permanent structures. As well as locking, the symmetrical mechanism can detach cubes allowing faulty cubes to be removed. Such cubes would be moved out of the structure by another functioning robotic cube and then be replaced by an identical mass-produced robotic cube to affect self-repair in seconds, no matter how bad the damage.

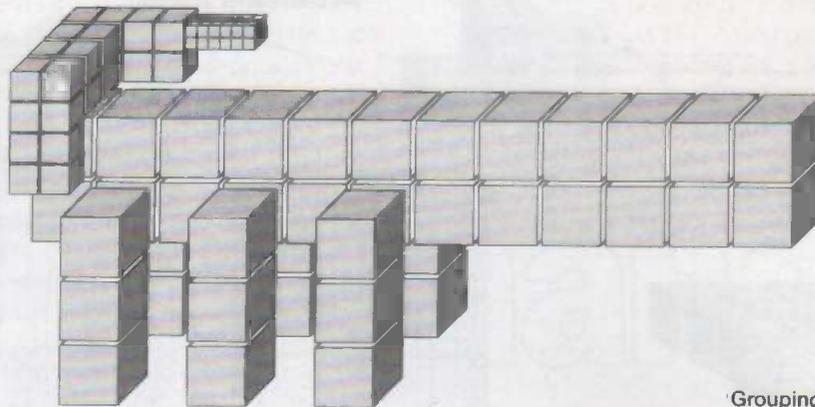The robotic cubes can also pick up and move other objects such as palletes, steel girders and machine tools provided they have simple compatible 45 degree slots cut into them. With electrical contacts inside the slots allowing an interface between the robotic cubes, tools can be remotely controlled.



Grouping using fractal cube sizes

Thus, not only can the robotic cubes move objects and tools around a structure but also use them locally to make dynamically re-configuring robotic machines.

The shape-changing properties of the robot can be used to erect new structures in minutes along with all necessary heavy production tools and interconnecting cables. The shape-changing properties of the robot can be used to pick up pre-terminated electric, hydraulic and pneumatic cables along their mid sections and transport them around in complex paths to automatically connect two or more points together.

This type of system allows pre-packaged, automatic, self-repairing factories to be built with no human intervention. Large robotic cubes perform heavy tasks while smaller cm-sized cubes perform more intricate tasks with greater local access. By simple changes of software and production tools, different factories can be synthesised allowing huge diversity to be achieved with relatively few standard pieces of equipment. Indeed, shape-changing robots are, in theory, flexible enough to assemble their own factories and build more of themselves

Technical concepts

As a starting point in our examination of this technology, we need to define what we mean by a shape-changing robot. The following is a brief definition:



A shape-changing robot is a finite resolution electromechanical device that acquires dynamically programmed geometric shapes through the use of a computer or computers, these shapes being limited only by the minimum resolution of the electromechanical mechanism and/or the software running on the computer(s).

As we have already seen, Michael's shape-changing robot is built out of a collection of cube-shaped robotic cubes. These have electromechanical locks that connect with neighbouring cubes and also enable them to slide with respect to each other without detaching. The locks carry power and data between the robotic cubes. There are electronic controllers in each robotic cube and each such cube has a unique address. The robotic cubes attach or detach from each other under computer control. Computers located internally inside the robotic cubes issue control instructions to the controllers, or

relay instructions from an external control computer.

From this outline we can produce a set of specifications for a standard robotic cube; they are as follows:-

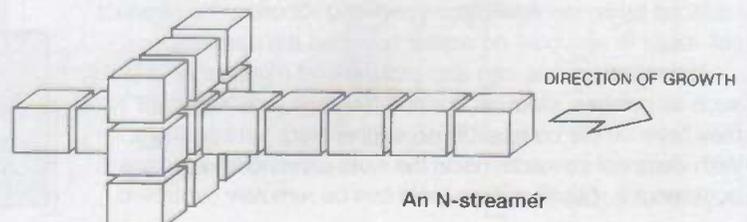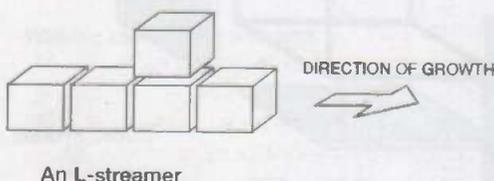1. A robotic cube must be able to receive power from any of the six faces.
2. Power received on one face can be directed to any number of faces. Power drains caused by short circuits are limited and/or isolated from the rest of the supply. There should be no leakage (such as earth leakage). Power is switched between faces under computer control. Instructions for power management are calculated locally within a cube or received externally through the network.
3. Robotic cubes talk to their neighbours using networking ports. The networking port can be either serial or parallel. Parallel methods allow greater bandwidth but cost more in terms of wiring and hence serial methods are preferred.
4. The robotic cubes route network signals from one face to another under computer control. Short circuits and earth leakages are detected and the network cables isolated to avoid damaging electronic devices.
5. There must be a minimum of one master computer holding and issuing control messages to robotic cubes. The remaining robotic cubes are slaves implemented using a minimal controller for receiving and executing movement instructions received through the networking ports. The computer can sit inside a robotic cube or reside externally and be linked with wires or by telemetry. The computer should be able to interrogate the status of each robotic cube's controller. Multiple computers can be present in a structure and these should co-operate and share the loading of the computational task by localising sub tasks. Tasks that are inherently parallel should be carried out by separate computing centres within the same structure. A collection of autonomous robotic cubes must have at least one computer with sufficient capabilities to turn into a control centre for local control and task execution. For large structures there should be many such computers to take local control.
6. Robotic cubes with less than six active faces for power,



networking and other features may be present but the operating system for the software must be notified of these facts so that software can cater to these special conditions. Robotic cubes with less than six active faces for power, networking and any other conditions described below may be present due to defects or other reasons but so long as they inform the operating system of the status of each face, the software should cater for a vast number of such special cases where they are introduced deliberately or through fault conditions.

7. Instructions calculated locally or received through the network allow a robotic cube to lock any of its faces to any of its six neighbours. The locks should be strong to give rigidity to the structures erected.

8. Robotic cubes sliding past each other under computer control should do so without rubbing harshly between faces and without separating when they are sliding (separation should take place only if requested by the controlling computer). Robotic cubes should be able to travel upside down as well as scale walls made of other cubes. The sliding mechanism should be of a low friction type in the direction of the slide. However, it should not be slack to avoid vibrations and wobble when being moved.

9. Robotic cubes should not be powered whilst being moved. This avoids having to use batteries within the cubes to move them and/or having to use sliding electrical contacts that supply power to move the cubes. The configuration details prior to power off should be retained with non-volatile memory or by the operating system. The controllers on board each robotic cube (if fitted) should power up into on-line status within milliseconds after power is applied. The robotic cube electronics should be resilient to frequent loss of power and surges on the power line.

10. Robotic cubes should sense other cubes attached to its face and interrogate it using the networking system. Fault conditions detected are communicated through interrogation and networking.

11. It should be possible to move a deeply buried robotic cube within a structure without having to move the remaining robotic cubes.

12. Robotic cubes should be switched off in the locked position if their sole function is to give structural strength whether temporary or permanent to save power and avoid over heating.

13. Robotic cube computers and other related equipment should ideally run cool. That is, they should not require extensive ventilation. (Facilities to erect ventilator ducts should be available in software for large and complex structures.)

14. Robotic cube electronics and electrical circuits must not be prone to moisture damage, vibration and radio frequency interference. Electrical connector pads should be designed to mate in a gas tight joint to minimise corrosion defect rates.

15. Robotic cubes should be able to synchronise their

activities using a single electrical wire that can be networked (that is routed from one cube face to another). This routeable synchronising line is vital for large collections of robotic cubes to synchronise their collective activities


16. The locking mechanism locks cubes together. The locking mechanism should also be able to lock to dead cubes and to robotic cubes which have tools attached or to objects that have only the minimum of necessary grooves cut into it.

17. Robotic cube controllers and/or their computers should audit their recent movements so as to enable the operating system to recover from simple faults.

18. Large and small robotic cubes should be allowed in a structure to form fractal mechanical structures. This facility should be made available as an interface on at least one of the larger robotic cubes which is compatible with the smaller scale. The computer software should make no distinctions in the functions and facilities available and the transition between the smaller and larger excepting the physical characteristics such as dimension, weight, strength etc.

19. Robotic cubes should be able to pick up tools with a minimal interface between itself and the tool.

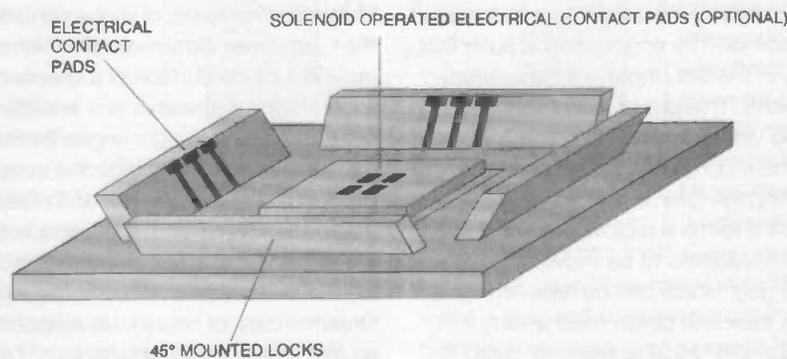20. Tool manufacturers should be able to write driver software to control the tool under full automation and integrate it with the operating systems running the robotic cubes using an open and clearly documented set of interfaces.



Structure of an active plate

The robotic cubes can be thought of as optimal space filling atoms that can be instructed to move from one place to another under computer control. It is the total computer control of shape and geometry that allows shape-changing robots to be built. The two basic mechanisms for changing geometry are known as the normal streamer and the L-streamer and these provide the necessary movements to synthesise all known shapes.

All the cubes can be identical, in other words uni-cellular, thus making the manufacturing operation relatively straightforward and cheap. Symmetrical uni-cellular cubes with the above listed desirable properties, together with the two algorithms for moving cubes around, present the smallest possible set of atomic concepts that allows a fully functional shape-changing robot to be built.

Of course there have been several kinds of cellular robotics systems proposed over the years, including hexagonal designs, cellular linkage robots and multi-cellular designs but, by and large, these are inefficient systems, since they involve more than one kind of cellular robotic component.

Internal mechanisms

The internal mechanisms of a robotic cube are extremely simple in both construction and operation. Cubes start life as a cubic frame to which plates are attached that contain the mechanisms. If the cubic frame has one or more active plates attached, then it becomes a proper robotic cube. The

remaining faces do not have to be fitted with anything.

The robotic cube can be hollow and in some respects the need for a frame is unnecessary if a sufficient number of the plates can be bolted together without reducing mechanical integrity. Frames can also be fitted with passive plates which have no mechanisms. Or they can be fitted with plates that have tools attached and, by fitting plates to just five sides, one can make it into a hollow bucket to carry materials such as parts in a robotic assembly line.

Each active plate has electromechanical mechanisms to push out wedges at a 45 degree angle from its surface. The wedges are always operated in opposing pairs using an electric motor. Thus the left and right pair of wedges extend and retract by the same amount at all times. There are electrical contact pads on the wedges for connecting electrical signals between one face plate and another. The wedges also act as the locking mechanism if all four wedges are inserted simultaneously.

A pair of wedges can insert itself into the face of a neighbouring robotic cube for which a perfectly fitting slot has been machined at a 45 degree angle. This neighbouring cube, with its totally symmetrical and identical mechanism, must have its wedge pair retracted in order for this to be possible. The slot is machined with a taper to allow the wedges to enter without jamming. The slot is carefully machined so that it has a ledge on which the wedge can sit. The engineering is such that when the wedges are sitting in the slot, there is a separation distance between the two faces. This prevents the faces from rubbing when they are sliding under computer control.

To slide a robotic cube under computer control, the wedges have serrated edges which engage gear wheels in the neighbouring robotic cube. This forms a rack and pinion mechanism which allows heavy objects to be moved. To increase lifting capability, the gear wheel can be replaced by a helical screw to give a better rack and pinion mechanism.

The serrated edges engage the helical screw and, with each turn, move the neighbouring robotic cube by one thread length which gives enormous power amplification. Furthermore, since the serrations rest on the length of the helical screw, a very good weight distribution is achieved across the length of the screw. The centre of a robotic cube is mostly empty and that could be used to house a very powerful motor for heavy lifting. Note that the cube that is being moved does not need any power, it is the opposing cube that is moving it through its rack and pinion mechanism.

A robotic cube on the move has only one pair of wedges in contact with the helical screw. This means that all four helical screws can be connected together to turn at the same time using a single motor. This means that, in theory, only three motors would be needed per face, of which only one has to be powerful enough to operate the helical screws. This is referred to as the primary motor.

Motor count could be cut by installing clutch mechanisms etc. and by making the robotic cubes with multiple faces into a more compact single mechanism - but that approach would only increase engineering complexity and increase field reliability problems. The preferred motors for use in these robotic cubes are stepper motors or, failing that, brushless motors. This increases field reliability as it reduces the possibility of brush components failing in use.

Apart from micro switches to detect positioning, there are no other mechanisms in a robotic cube. This means that the mechanical construction of a single robotic cube is far simpler than any conventional robot.

The only other component is a printed circuit board with a micro controller with about 1K RAM and 10K ROM; the main function of this is to listen to the data signals coming down the contacts on the wedges. The power also comes from the wedge and so there are power conditioning circuits in the printed circuit board.

Instructions that the robotic cube receives are very simple. In a minimal instance, the messages can be 'are you there?' which then responds with its unique hard coded address, 'operate wedges', 'operate primary motor' and 'route power and data wires from one face to another'. (By default, power and data are not routed from one face to another to avoid short circuits dissipating the power and signals and to minimise environmental leaks. If leakage is detected, then power is shut down straight away from a face, regardless.)

Of course, a microprocessor could be used with much larger RAM, ROM and other computing functionality. This would be an overkill for most applications, but it does raise the possibility of using a shape-changing robot to create a self-repairing, auto-configuring, and potentially very powerful parallel computer - given, of course, an operating system which could handle such a dynamic parallel architecture.

Robotic cube movement

There are two forms of movement, the normal streamer and the L-streamer. Streamers are thin rods similar to tentacles that grow out of the surface of a shape-changing robot body.

The normal streamer is a rod-like protrusion which can grow out of a surface at right angles to that surface; it is Normal to the surface. It is extended, one cube at a time, by attaching a cube at the rear of the rod and pushing it out. The L-streamers derive their name from the L shape that characterises the tip of the streamer. It grows by attaching cubes, one at a time, to the front of the streamer. The steps for growing both types of streamer can, of course, be reversed to shrink a streamer with as much ease as to grow it.

L-streamers can be grown in any direction and the direction of growth can be changed. Once a streamer is erected, the rest of the shape-changing robot can travel over this streamer with little or no difficulty to re-assemble itself at the other end. This is how the shape-changing robot can squeeze through narrow entrances to re-assemble itself at the other end.

Instead of moving individual robotic cubes, groups of robotic cubes can be clumped together and use the same algorithms to achieve the same desired effect. Grouping is an important software tool in minimising the flow of instructions in a structure. Grouping simply involves, of course, the use of fractally larger robotic cubes.

Normal streamers are used to erect pylons. However, any movement in one direction which may get supplemented with a filling operation at the base is classified as a normal streamer. Reversing the steps will reverse the growth of the streamer. These mechanisms can also work with integer multiple collections and fractally larger robotic cubes.

Streaming is a very important attribute of shape-changing robots since it essentially allows the robot 'body' to move by flowing like a liquid. This means that like a liquid it can be made to flow through small apertures the size of which is limited only by the dimensions of individual cubes. This would, for example, allow large shape-changing robots to be put in a dangerous environment, such as a nuclear reactor containment vessel, with only a minimal opening into that dangerous environment.

Robotic pick-up mechanisms

By using L-streamers and N-streamers, any structure can be erected in an orderly manner with the aid of multiple collections and fractally larger robotic cubes. However, that in itself is not enough to create large structures or machines. Such structures also need the means to move objects which are not robotic cubes, as well as having the means to interact with the world with the aid of tools sensors etc.

The robotic cubes can be used to move other objects around if they had protruding wedges, as illustrated for a pallet system. Such wedges are at times difficult to manufacture into a product and in those instances we can go a stage further by reversing the condition and require the work piece to have slots cut into so that a robotic cube can insert its wedges into it to pick it up.

Using these techniques, a shape-changing robot could install an environmental shield around itself using plates that have been cut with slots. Or a system of girders with slots cut into them that act as structural supports when erecting large and complex structures. These girders can be used as supports when travelling up and down structures without stressing the structure.

An important type of special handling tool is the turntable, used to re-orient cubes in different directions. This is important because, using normal movements, a robot cube cannot change its relative orientation with respect to another robotic cube without the aid of a turntable to rotate it. In an ideal situation, there are three separate turntables available to turn the robotic cube in any of the three rotational axis.

Rotation can also be used to switch in different tools attached to different faces of a robotic cube. Tools and sensors for special purpose applications are fitted with electrical contacts identical in specification to that of the wedges so that they are compatible with the robotic cubes and their controlling software.

A shape-changing robot can grip a cable all along its mid sections and carry it through complex contours by deforming around the obstacles. This cable could be hydraulic, pneumatic, electrical or fibre optic. If the cables are pre-terminated, or if there are terminating tools available then potentially all machinery to be found in a factory floor can be rearranged and re-cabled using shape-changing robots.

Shape-changing robots can also cope with situations where cables have to run into a progressively narrowing pipe, or the pipe divides into two. Since they are fractal in nature, the shape-changing robot simply switches to using smaller cubes, or divides into multiple robots using streamers and, if necessary, into totally detached walking/crawling machines connected by telemetry.

We have just stated how shape-changing robots can be used to move tools around to make a factory. The shape-changing robots can also be used to take tools to the work in situations where conventional robots cannot possibly operate. For example, conventional robots when assembling cars can only get so far within the car before they are impeded by the doors, the engine etc. But shape-changing robots can switch to smaller cubes and enter the work piece using a streamer to, for example, tighten up nuts and bolts, tuck in carpeting, connect up wiring, test vibrations etc.

Manufacturing

Robotic cubes measuring one to three centimetres are adequate for the vast majority of operations requiring high dexterity to be found in manufacturing. Bearing in mind that shape-changing robots are self-repairing, these robotic assembly lines would work day and night without stopping, producing indisputably high quality products.

Another advantage of shape-changing robots in production assembly work is that they require far less energy to operate. Instead of moving a large robotic arm and its entire mass, for small movements perhaps only one robotic cube and the attached work piece to needs to be moved. For more delicate work, even less power is required since smaller fractal robots with smaller mass and power consumption can be used.

Of course the most intriguing attribute of the shape-changing

robot is that it is capable of making copies of itself in a factory made up of itself. In other words it could become self-replicating. Alternatively, shape-changing robots can take the next step in their own evolution by using smaller fractal cubes.

The smallest components of sub millimetre sized robotic cubes could be manufactured using the photo lithographic techniques that are being employed at the moment to build micro mechanical structures such as electric motors that are smaller than a pin head. It is then possible that the shape-changing robots can build/maintain and repair these very same photo lithography machines

(which are large in comparison to the small robotic cubes) to make a truly self-sustaining machine system that can manufacture, repair and renew all its components including itself. This process could be applied even to the electronics - after all, they too are produced using photo lithography; all that is needed is a source of raw materials.


The shape-changing robot acts as the glue between all the different kinds of tools to be found on the factory floor. The configuration of any machine is thus defined by software rather than by hardware; this means that increasing production, changing the product being made or to making a copy of the machine tool or factory, becomes a matter of giving the system the correct sequence of commands.

In the future, not only will the factories that produce shape-changing robots and other goods be fully automated, but the factory to produce factories of all descriptions would also be automated.

Fault recovery

In large complex structures, it is not always possible to ensure that all cubes are functioning. However, unlike normal machines, cubes can repair themselves from almost any kind of isolated fault. Any cube that becomes faulty is simply picked up by a functioning cube and deposited elsewhere in the structure, or ejected altogether.

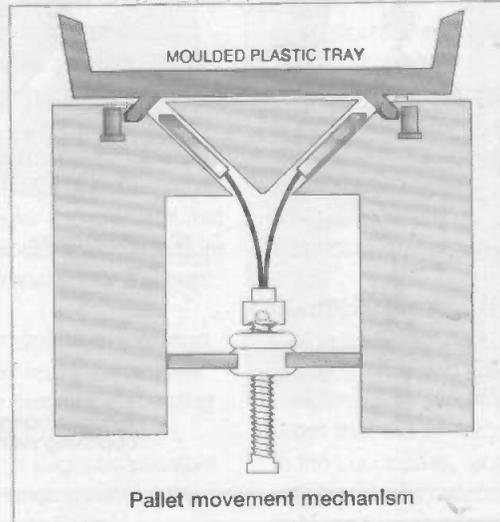When more than one cube becomes faulty in a clump, the functioning cubes that are attached to these clumps can detach from the faulty part of the structure or, if the clump is small enough, move them elsewhere in the structure as before. Because cubes are clones, repairs are effected by substituting other cubes from a reservoir of spare cubes held elsewhere in



the structure.

This means that to critically damage or destroy a shape-changing robot one would have to damage a very high percentage of the cubes and/or destroy all the central computers and power sources connected to the robotic cubes. Since multiple copies of the computers and power sources can be carried in a large structure, the possibility of destroying such a machine in one blow is therefore remote.

Applications

The potential applications for shape-changing robot technology, especially for robots with a very small fractal dimension, is enormous. Indeed, it would be fair to say that there is not a single area of human activity which would not be affected by the use of such systems. In the rest of this article we will look at just a few of the potential applications which have already attracted considerable interest.

One area that has already attracted a lot of interest is the use of shape-changing robots to both contain, limit and then clear up accidents involving nuclear material, such as the disaster at Chernobyl. Intense radiation from a nuclear accident can prevent any kind of repair work which involves human operators from being undertaken. This means that the machinery involved in such operations has to be operated remotely, but the problem here is that standard remote control equipment, such as robotic rovers, either cannot operate in high radiation environments (due to the effect of radiation on electronic equipment and signal transmission), in confined spaces or on undefined terrain. Shape-changing robots, on the other hand, could in theory be built to overcome all these difficulties.

In a typical nuclear installation, the reactor is never directly accessible for servicing or repairs because it is contained in a concrete containment dome. This, in turn, is surrounded by installation specific buildings that can make access difficult after an accident. Indeed, access constraints pose one of the main problems in clearing up catastrophic reactor failures, a factor which can make it impossible to use conventional systems.

In the case of a chemical and/or a pressure explosion that rips the dome off the reactor and destroys other parts of the installation, not only is the reactor damaged but so are buildings within the installation. There is debris everywhere and the general terrain of the installation remains undefined at all times during the emergency. A remotely operated robot has to negotiate this terrain, a legged robot could become trapped in the debris, and small robots with caterpillar tracks would be of little use. Furthermore large robots would not be able to enter the building and, even if they did, could cause further damage.


However, if the installation is fitted with shape-changing robots, they can start working seconds after an accident and because any system built using robotic cubes is self-repairing it will work even if some are damaged by the accident. It is envisaged that there would normally be shape-changing robots

inside the reactor complex which could be moved into danger areas under operator control to very quickly erect protective walls and seal off radioactive areas.

Shape-changing robots can help in a number of ways inside a damaged installation. For example, they could squeeze through small holes as streamers and take with them cameras, lighting and any other special equipment that can be squeezed through the hole. Under operator control, the shape-changing robots then install the lighting and cameras for initial monitoring of the accident. The robotic cubes can then be used as structural

supports to prevent further collapse.

Conventional equipment can malfunction in a highly radioactive environment if sensitive electronic components are used. That possibility can be avoided with lead shielding. However, specialised robotic cubes could be constructed that have no electronics and instead have a mechanical or fluidic computer inside it, in many ways not dissimilar to an old fashioned washing machine controller. This is possible because the instruction set for the robotic cube is very simple. Shape-changing robots could also be utilised to minimise the effect of other potentially

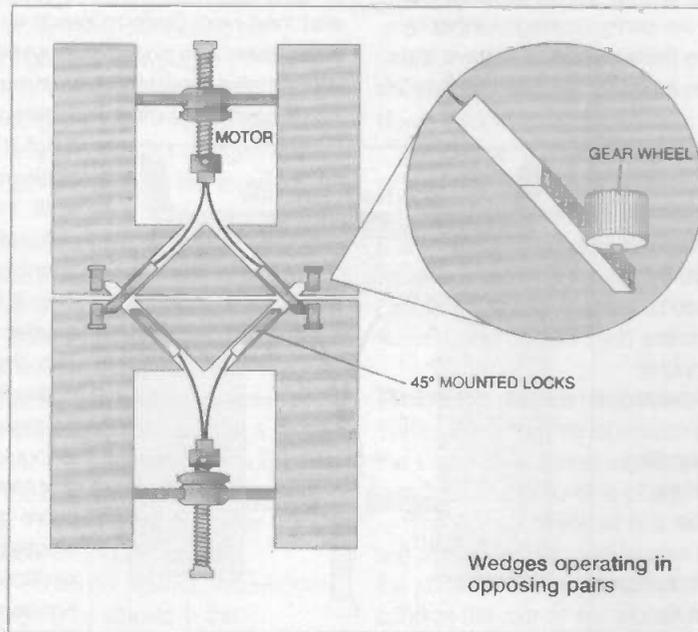

disasterous accidents. Even in this modern day and age, there are no safety systems for ocean-going liners, ferries, supertankers, aircraft carriers and nuclear-powered ships that can prevent a ship from sinking once it starts to take in water. Suppose a nuclear power pack is damaged in a nuclear powered ship. To contain leaks, it is vital that some kinds of systems are still in operation that is, to its best abilities, self-repairing and able to contain the leaks regardless of the damage. Shape-changing robots are just that - technology that can erect new walls, floors, supports and shielding while actively repairing itself against damage as an incident develops.

A similar kind of situation applies when an oil tanker spills its load due to ship damage or running aground. The shape-changing robots are far cheaper than the repair bill of around a billion dollars for a catastrophic oil spill. Shape-changing robots with inflatable buoyancy bags can be deployed to encircle the oil that has leaked and, significantly, hold it back from drifting so that it can be dealt with by emergency measures. This, of course, would only happen if the oil leak in the first place could not be plugged in time by the shape-changing robots fitted to such super tankers.

Space applications

Space offers perhaps the biggest range of potential application for shape-changing robots. The ability to change shape and synthesise physical structures reliably, cheaply with self-repair and without human intervention is the most important demand made by space-related applications. It is that hurdle which holds up a vast majority of projects. Shape-changing robots for space is the most significant development that will push space research into the next century. To see how all this will come about we can look at existing problems and see how shape-

changing robots will overcome these.

Space structures built with shape-changing robots can be sent from earth in the form of loose cubes and then be made to deform into the desired structures when delivered to their desired orbit or planetary location. The launch phase to deploy a shape-changing robotic vehicle follows normal procedure. Shape-changing robots are packed into every available nook and cranny to deliver the maximum payload into space. On deployment of the payload, the initial phase of changing shape is the erection of the solar panels to supply the necessary energy.

Shape-changing robot applications go beyond simple satellite technology. Exploration probes and landers can be built. Complex satellites can be assembled in space using simpler docking mechanisms built of more shape-changing robots. They can be used in the construction of space stations without taking expensive space walks. Absence of gravity allows complex and exotic structures to be built very quickly. Each shuttle payload can be self-unloaded and left in docking orbits and then all the shape-changing robots can be brought together to quickly make the desired structure.

Such robots can make space travel much safer by repairing damaged and faulty systems on the way. They could be programmed to crawl about all sorts of nooks and crannies that even on a manned mission are not easily accessible and ensure that any damaged and faulty systems are repaired for the best possible mission outcome.

Shape-changing robots are ideal for sending to moons and planets where their reconfigurability and self-repair capabilities would be particularly useful. Indeed, if their first task on landing was to form an automatic assembly system to make more cubes using locally available materials then it might be possible for a base to be built prior to any manned landing without the necessity of sending very heavy payloads from Earth.

Making the cubes smaller

Further miniaturisation using photolithography could conceivably shrink the robotic cubes to micron or even sub-micron dimensions. At this size they would still function in an identical manner to their larger equivalents, but by being so small would open up a whole range of new applications.

These micron scale cubes would still use the same computer software as the larger scales because each cube has a minimal controller that obeys the basic instructions to move left, right, forward, backward, up, down, attach, detach and return "what's your address"? Anything else that it does not understand is ignored or passed on to any tools that may be attached.

One of the potential applications for such ultra-small shape-changing robots would be in medicine. Using cubes of 1 mm size and below would allow them to be directly injected into the patient and then under control of an external computer perform otherwise complicated surgery to remove cancers, cysts, blood clots etc.

Surgical shape-changing robots could squeeze through tiny holes no bigger than the largest cube and spread out once it has reached the other side which means that it can be used to perform pinhole surgery where the robot cuts its way into the patient and spreads out inside the body to perform the required operation around the affected area.

Another application area would be in the construction of wafer scale electronics where, instead of splitting a silicon wafer into large numbers of individual components, they could all be left on the same wafer and a miniature shape-changing robot employed to configure or reconfigure the interconnection between all the components.


Ultra-small dimension shape-changing robots could also be used to build smart materials that could repair themselves in case of damage, react in different ways to the external environment, change colour, texture, or shape on demand. Indeed, as with most aspects of shape-changing robot technology the potential range of applications seems limitless.

Conclusion

Without a doubt, Joe Michael's development of the concept of a shape-changing robot based upon fractal mechanics is both intriguing and potentially very useful. However, despite the years that the inventor has spent upon the project it is still only in the conceptual, wooden block and computer modelling stage and, like most engineering projects, there are doubtless an enormous number of problems still to be ironed out.

Many of these problems will doubtless come to light when the inventor has completed construction of the first working prototype cubes in the next few months. Hopefully, he will then be able to give practical demonstrations of how the system will work, and now that he has secured world-wide patents, use these demonstrations to gain further funding for continued development.

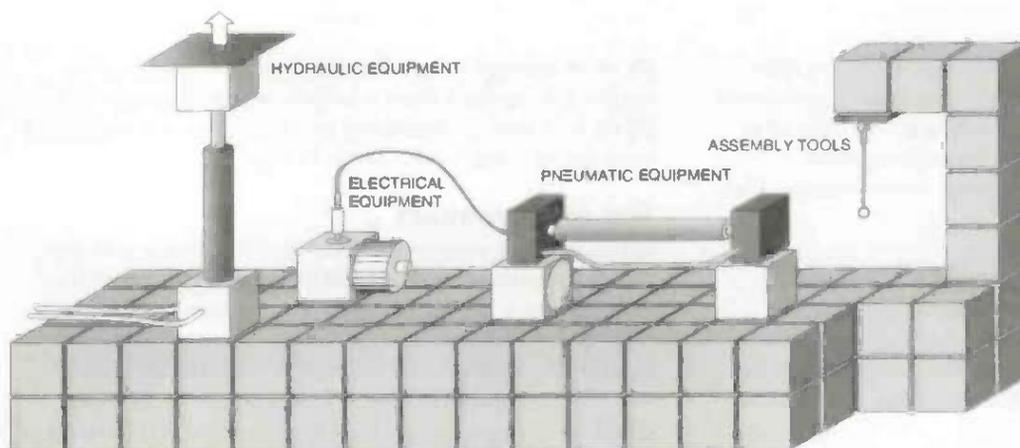We at ETI think that this is a great idea and wish Joe Michael good luck in his pursuit of a dream that could easily change the way that we do a great many things. We look forward to seeing the prototype and even more eagerly await the arrival of the first commercial shape-changing robots. Let's hope we will not have to wait too long!



Robotic cube based assembly system.

Anyone wanting more information about shape changing robots can contact the inventor, Mr. Joseph MICHAEL, at: E.C.C. Ltd
23 Portland Rise
London N4 2PT.
United Kingdom.
Tel: +44 181 800 9914
Fax: +44 181 800 9915
Internet E-mail: joe@stellar.demon.co.uk

Experimenting with bar code readers

Bar codes are in use everywhere, even on the cover of ETI. Here Dr Pei An presents a project which, when attached to a computer, will allow users to read any printed bar code

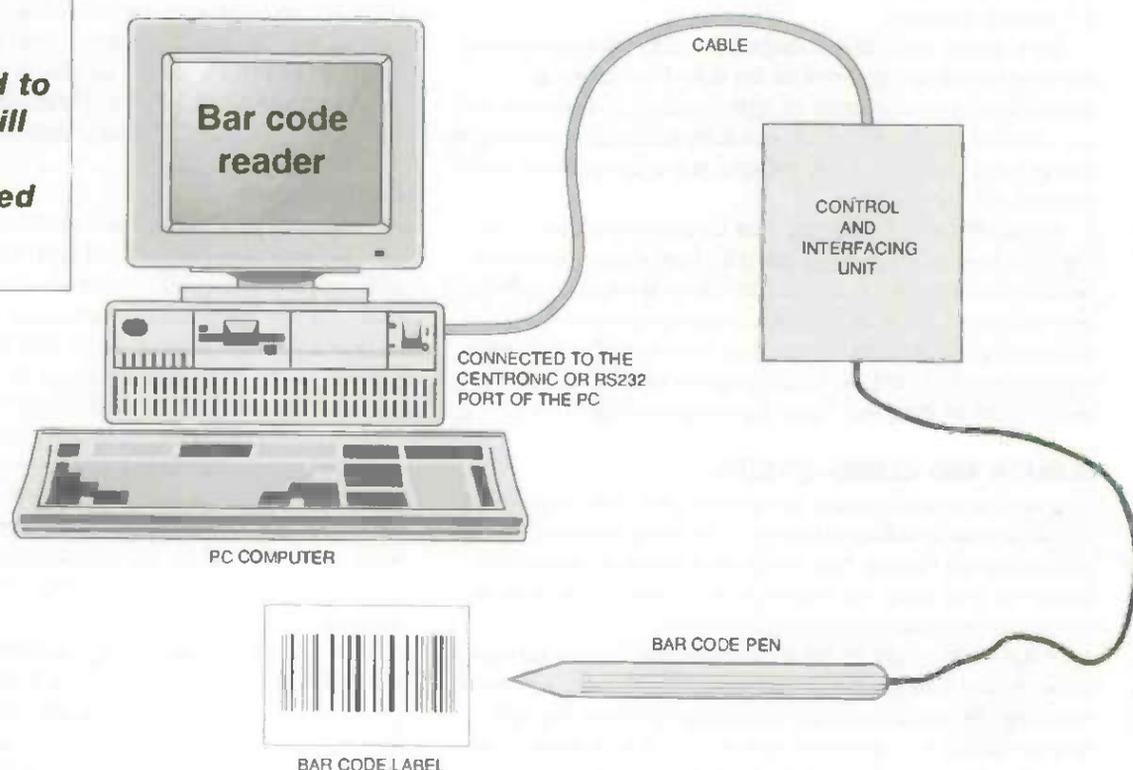


Fig.1. Complete bar code reader (pen-type) system

Bar coding was first developed for use in retail application to assist with automatic supermarket checkout. Nowadays it is used for many other applications, such as the card key entry, automatic library checkout, stock logging, video recorder settings etc.

A practical bar code reading system consists of four elements:

- (1) It is, of course, no good having a bar code reader without a suitable bar code label to read; this consists of white and dark bars.
- (2) An optical bar code reader converts the printed bar code pattern into electronic signals.

- (3) An amplification/decoding circuit which interprets the signals into numbers (from 0 to 9) or characters (from A to Z).
- (4) An I/O circuit for interfacing to a computer. A complete bar code reader system is illustrated in Figure 1.

Bar code readers

Bar code readers we see in everyday life have many shapes. The most common ones are the hand-held bar code pens (also referred to as 'the wand'), the hand-held bar code guns and bar code readers built inside the counter. Although their shapes vary, their working principle is the same for most of them. Bar code optical readers emit a beam of light which creates a tiny light spot on the bar code label. The diameter of the spot is smaller than the thinnest bars on the bar code (Figure 2). The light reflected from the bar code is detected by

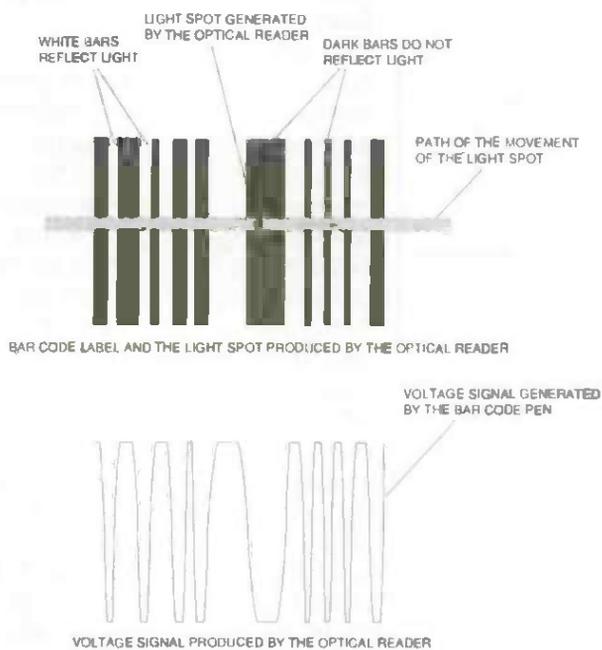


Fig.2. Principles of bar code reader

a photo detector. Because light reflected from a white area is different in intensity than that from a dark area, the photo detector will respond differently. Therefore, as the bar code reader scans across the bar code label, a signal in sympathy with the pattern of the bar code is produced (Figure 2). The relative movement between the bar code label and the light spot is produced either by keeping the bar code label stationary while moving the light spot, or by keeping the spot stationary while moving the bar code label.

The bar code pen

The pen is held by hand and the tip of the pen runs over the surface of the bar code label. The optics of this type of reader

varies slightly from one design to another. Figure 3 shows the structures of three types. The light emitted by LEDs (Figures 3a and 3b) or light emitted from an optic fibre (Figure 3c) is focused on the bar code label by a small sapphire sphere mounted at the tip of the pen. Light on the bar code label is reflected back through the sphere into the pen and received by a photo detector. The signal generated by the photo detector is amplified and decoded into numerical or alphabetical digits by electronic circuits.

Bar code gun

There are two types of bar code guns. The first one utilises a laser light source and a rotating mirror system while the other uses a charge coupled device (CCD) light sensor. In the first case, a narrow laser beam is intercepted by a rotating mirror, which causes the laser beam to scan across the bar code label. The light reflected by the bar code is detected by photo detectors (Figure 4a). The other type utilises a CCD device. The bar code is illuminated by a LED array. The image of the bar code is focused on to the CCD sensor by a lens. The CCD device contains several hundred light sensitive cells in a small area (or in a row). The voltage output from a single CCD cell depends on the intensity of light on it. Therefore, the pattern of voltage level from the CCD sensors indicates the pattern of the bar code label (Figure 4b).

Bar code reader built in the counter

There are two types of bar code readers. The first one has a fixed light beam and the other has a scanning beam. For the first type, the light beam emitted by a laser source travels through a transparent window to the bar code label. The label has to be moved over the window to allow the light beam to scan the bar code (see Figure 5a). The light reflected back from the label is detected by photo detectors. The other type incorporates a rotating mirror system to make the laser beam to scan across the window in a fraction of a second. As a result, it does not matter whether the bar code label moves or not. The moving beam scans so rapidly that the label appears to be standing still even through it is being moved (Figure 5b).


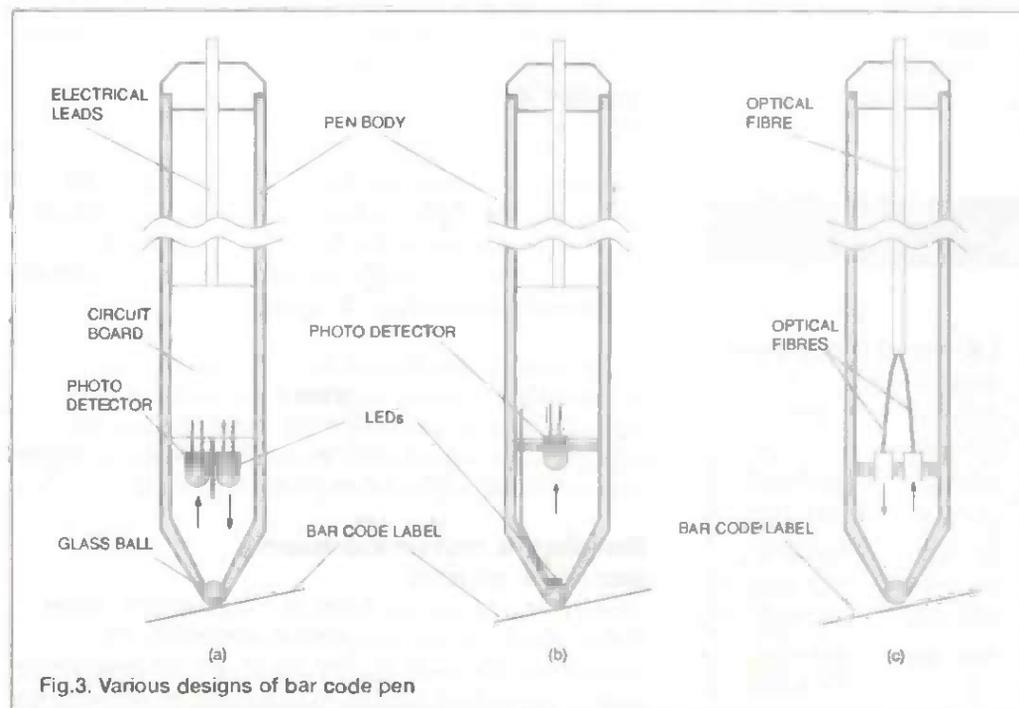


Fig.3. Various designs of bar code pen

The bar code

Several bar code standards are available nowadays. They are based on an encoded pattern of wide and narrow dark/white bars to represent alphabetical or numeric characters. The Universal Product Coding (UPC) was created in the United States of America in 1973. In this scheme, a unique number is allocated to a particular manufacturer who can then add a number that is specific to a product. In 1977 European Article Number (EAN) standard came into being. Most bar code labels on articles in supermarkets, books or newsstand magazines in the UK have an EAN code on it.

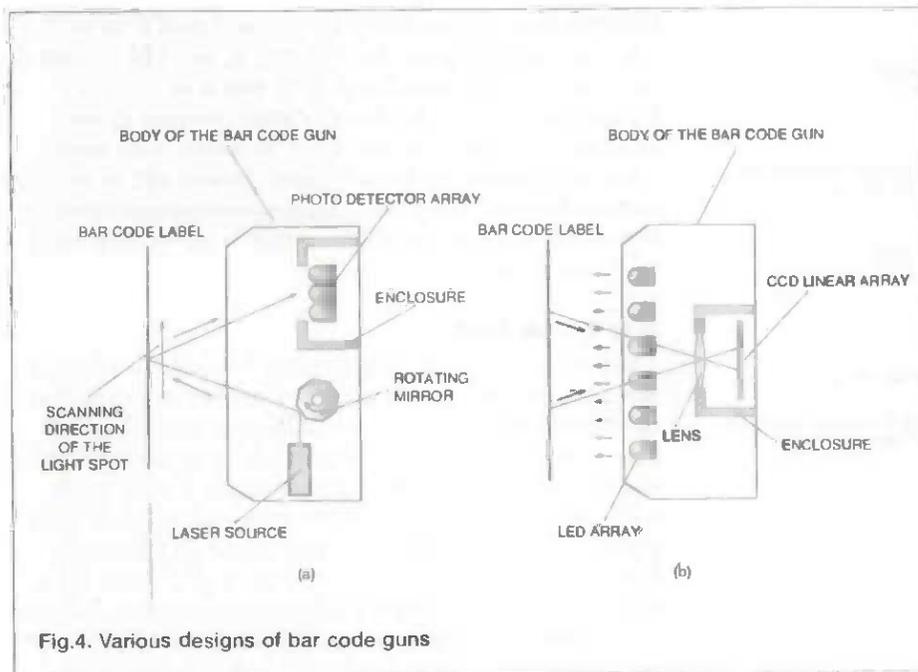

Encoding of digits using bars

Each digit in the EAN code is expressed by a combination of seven dark or white bars of a fixed width as illustrated in Figure 6a. A dark bar corresponds to 1 and a white bar corresponds to 0. Multiple dark bars adjacent to each other appear as a wide dark bar. In theory, there are 128 (2⁷) possible combinations of bars. Digits 0 to 9 on the left hand side of the code are coded differently from those on the right hand side to indicate whether the code is read from left to right or from right to left. The right hand codes have an even parity, i.e. even number of 1's. Left hand digits are encoded using a mixture of 'Left Hand A', with odd parity, and 'Left Hand B', with even parity. Thus, 30 bar encodings are used in the EAN

The format of the EAN bar code

Have a look of the bar code label printed on the front page of this magazine. The section on the left is a standard EAN label. The small one on the right has nothing to do with the EAN, so we can ignore it. The EAN label has two areas with one area above the other. The upper area consists of bar strips and the lower consists of 13 numerical digits, arranged into three sections. The first section contains only one digit, '9'. The second section (the left hand section) contains 6 digits '770142' and the third one (the right hand section) contains 6 digits '722092'. These sections are separated by two thin bars, which are known as the guard. Another guard also appears at the end of the bar code.

These 13 digits are split into four functional parts, a prefix, a manufacturer number, an item reference number and a check digit. The prefix has 2 digits; the manufacturer number has 5 digits; the item reference has 5 digits and the check digit has 1 digit. The bar code for ETI magazine is '9770142722092'. '97' is the prefix; '70142' is the manufacturer; '722092' is the product number. In fact, the prefix '97' indicates a publication. The number '7' indicates a magazine. '014272209' is the ISSN number and '2' is the check digit.

Table 2

Encoding of the first digit Number	Prefix 2	Data 1	Data 2	Data 3	Data 4	Data 5
0	A	A	A	A	A	A
1	A	A	B	A	B	B
2	A	A	B	B	A	B
3	A	A	B	B	B	A
4	A	B	A	A	B	B
5	A	B	B	A	A	B
6	A	B	B	B	A	A
7	A	B	A	B	A	B
8	A	B	A	B	B	A
9	A	B	B	A	B	A

coding. Table 1 lists the bar encoding for digits 0 to 9. Figure 6b shows samples of the bar codes. Not again that '0' represents a white bar and '1' represent a dark bar

Table 1


EAN bar encoding set Number	Left Hand A	Left Hand B	Right Hand
0	0001101	0100111	1110010
1	0011001	0110011	1100110
2	0010011	0011011	1101100
3	0111101	0100001	1000010
4	0100011	0011101	1011100
5	0110001	0111001	1001110
6	0101111	0000101	1010000
7	0111011	0010001	1000100
8	0110111	0001001	1001000
9	0001011	0010111	1110100

The use of Left Hand A and B in the left hand side codes enables the 13th digits (the first digit) to be encoded. This is why there are no bars for the first digit in the label! The relationship between the digit and the pattern of the usage of Left Hand A and B is shown in table 2.

In application, a calculation using the first 12 digits is performed after each bar code reading to generate a checksum value for detecting errors occurred during the reading. On the basis of what has been explained, can readers work out the bar code label on ETI magazine now?

Building a computer-based bar code reader

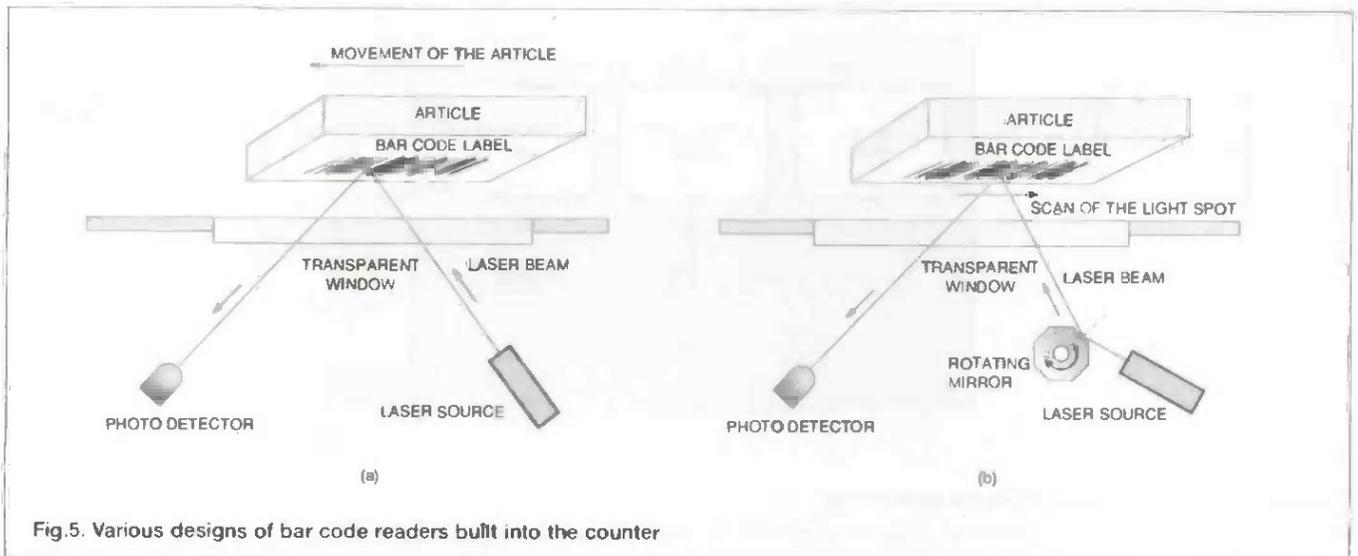Using commonly available materials, it is possible to design and construct a simple pen-type bar code reader. It is connected to the Centronic port of a pc and the computer can read the bar code and display the waveform generated by the



bar code reader on the screen. The software of the system is not in the ready-to-use state. Its main purpose is to show readers how the bar code system works and encourage readers to develop their own software.

This bar code system consists of a bar code reader pen and a box which contains the amplification and interfacing circuits. The complete system is shown in Figure 1.

The electronics of the bar code reader

Figure 7 gives the circuit block diagram of the bar code reader. It consists of 6 units, namely, the optical reader unit, the input stage, the amplification unit, the A/D converter unit, the pc interfacing unit and the power supply unit. The optical reader unit generates the voltage patterns when it travels over the bar code label. The input stage is used to interface with the photo diode.

The signal from this is amplified by the amplification unit and is then converted into digital form by the A/D conversion unit. The interface unit enables the computer to read the digitized signals via the printer port. The circuit diagram is shown in Figure 8.

The optical reader unit and the input stage

The photo detector is a BPW34 which is a 7 mm² planar silicon PIN photodiode and is highly sensitivity to red light. It is housed in a two pin epoxy package. The signal from the photodiode is amplified by a FET op-amp which is configured as a standard differential amplifier. The capacitors around the op-amp are used for reducing ripples from AC lighting and controlling the response time.


The amplification unit

The signal from the input stage is amplified further by an op-amp which is configured as a standard non-inverting amplifier. The gain of the amplifier is set by R6 and R7 and is calculated by $1+R6/R7$. R6 is 200K and R7 1K. This gives an amplification of about 200. Resistors R4 and R5 are used to set the quiescent voltage to about 0.012V. The output from the amplifier is a signal with an amplitude between 0V and 2.5V.

The A/D converter unit

The A/D converter is a ADC0804 CMOS successive-approximation A/D converter. Only a timing resistor (connected between Pins 19 and 4) and a capacitor are used for generating the clock signal and an external band-gap voltage reference is used to set the voltage reference for the converter. The power supply is 5V with a typical current consumption of about 13 mA. The maximum data conversion rate is about 8700 Hz. In most cases, the analogue ground (Pin 8), the digital ground (Pin 10) and Vin(-) (Pin 7) are connected together as a single ground.

-CS (Pin 1) is the chip select. To enable the converter, this pin must be held low. At the low-going edge of the -WR (Pin 3), the A/D converter starts the A/D conversion. During a conversion, -INTR (Pin 5) is at logic high. When a conversion is completed, -INTR goes low. When -RD (Pin 2) is taken low, the converted data will appear on the output lines DB0 to DB7 (Pins 18 through to 11); otherwise these lines are in high impedance state. In the present circuit, the converter is configured in a free-running mode by connecting the -INTR and -WR together and the -RD input is held low all the time.

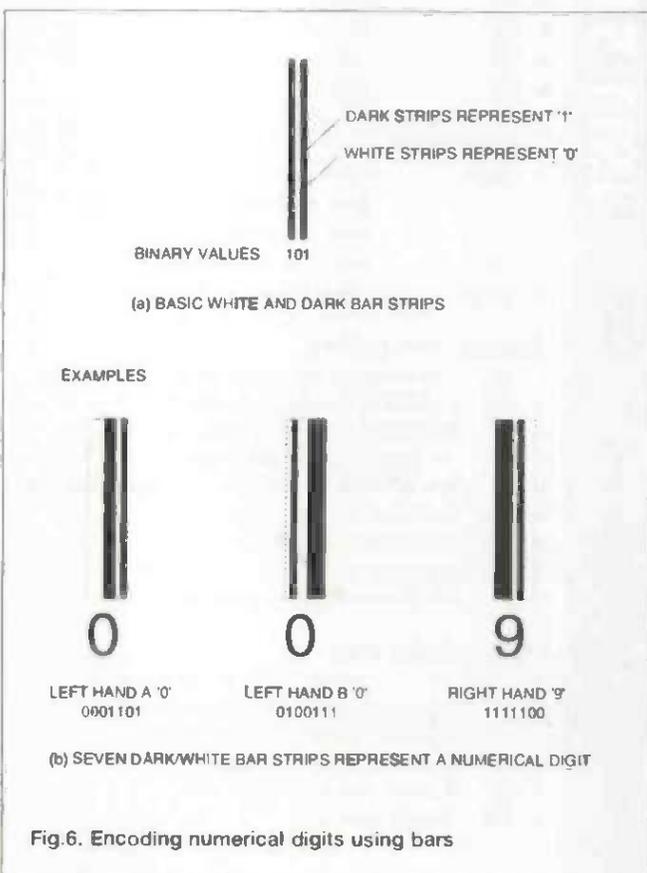

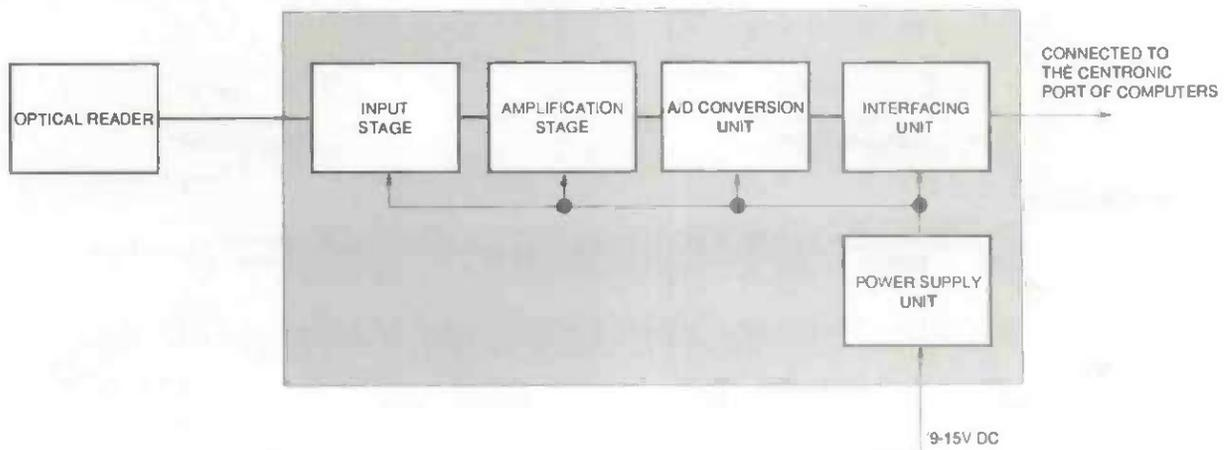


Fig.7. Circuit block diagram of the bar code reader

The PC interfacing unit and the Centronic port

The Centronic port of pcs consists of three separate I/O ports; the Data port, the Control port and the Status port. The Data port is an 8-bit output port, which sends data to the printer. The Control port is a 4-bit output port, which issues commands to the printer. The Status port is a five-bit input port which reads the information from the printer into the pc. For the LPT1 Centronic port, which is allocated on the mother board of the computer (not on the expansion card), these ports correspond to three I/O addresses: 888, 890 and 889, respectively. Because the Centronic port only has 5 input lines, in order to read an 8-bit data generated by the A/D converter a suitable Interface has to be used.

A 74LS241 tri-state octal buffer IC is used in the interfacing unit. It has two sets of tri-state buffers, each containing four buffers. Each set has an enable input, Pin 1 for the first set and Pin 19 for the second. When Pin 1 is taken low, the first set of buffers works (i.e. the outputs will follow the status of the inputs). When pin 19 goes high, the second set of buffers works. Pin 1 and 19 are connected together to form a Data Selection Line (DSL). By putting the line low and then high, the computer can read the 4 bits connected to the first set of buffers (DB0, DB1, DB2 and DB3) and the other 4 bits connected to the other set of buffers (DB4, DB5, DB6 and DB7) in turns. Operating in such a manner, the 8-bit data from the A/D converter can be read into the computer in two halves. By manipulating the bits of the two readings, an 8-bit data can be formed.

The power supply unit

The power supply unit incorporates a 7805 5V voltage regulator for supplying the 5V DC to the circuit. A 9-15V DC external power supply is required.

Construction

The electronics are mounted on a single-sided PCB board (see section at end of magazine). The component layout is shown in Figure 10. The circuit board is mounted in a plastic box. A suggested arrangement is illustrated in Figure 12 and shown in the photos.

Figure 11 shows the detail of the construction of the bar code pen. The optics of the pen are similar to the one shown in Figure 2(1). An LED and a photo detector are mounted side

by side on a small piece of strip board with their active areas facing in the same direction. The board is fixed inside a tiny plastic box. A hole was drilled on the side wall of the box and a plastic tube glued over the hole. The inside of the tube is painted black. A conical plastic tube was mounted on the other end of the tube with a tiny glass bead (2-3 mm in diameter) installed on the tip. The bar code pen is connected to the control box by two pairs of wires. The first pair supply the power to the LED and the other transfers the signal

PARTS LIST

Resistors (0.25 W, 1% metal film resistors)

- 2,R3 10M
- R4,R6 200K
- R5 500R
- R7 1K
- R8 10K
- R9 270R

Capacitors

- C1,C2 1000pF ceramic disc
- C3 33pF ceramic disc
- C4 10uF electrolytic
- C5 150pF ceramic disc
- C6,C7 100nF ceramic disc

Semiconductors

- IC1 CA3140 operational amplifier
- IC2 NE5230 operational amplifier
- IC3 ADC0804 8-bit A/D converter
- IC4 74LS241 tri-state octal buffer
- IC5 TLE2425C 2.5V precision voltage reference
- IC6 7805 +5V voltage regulator
- LED13 mm super bright LEDs
- LED25 mm standard LEDs
- D1 BPW34(no filter) photodiode

Miscellaneous

- J1,J2,J3 2-way PCB connector pairs
- J4 36-way Centronic female connector
- J5 6-way PCB connector pair
- J6 5-pin DIN connector pair
- SK 2.5 mm power socket
- SW Toggle switch

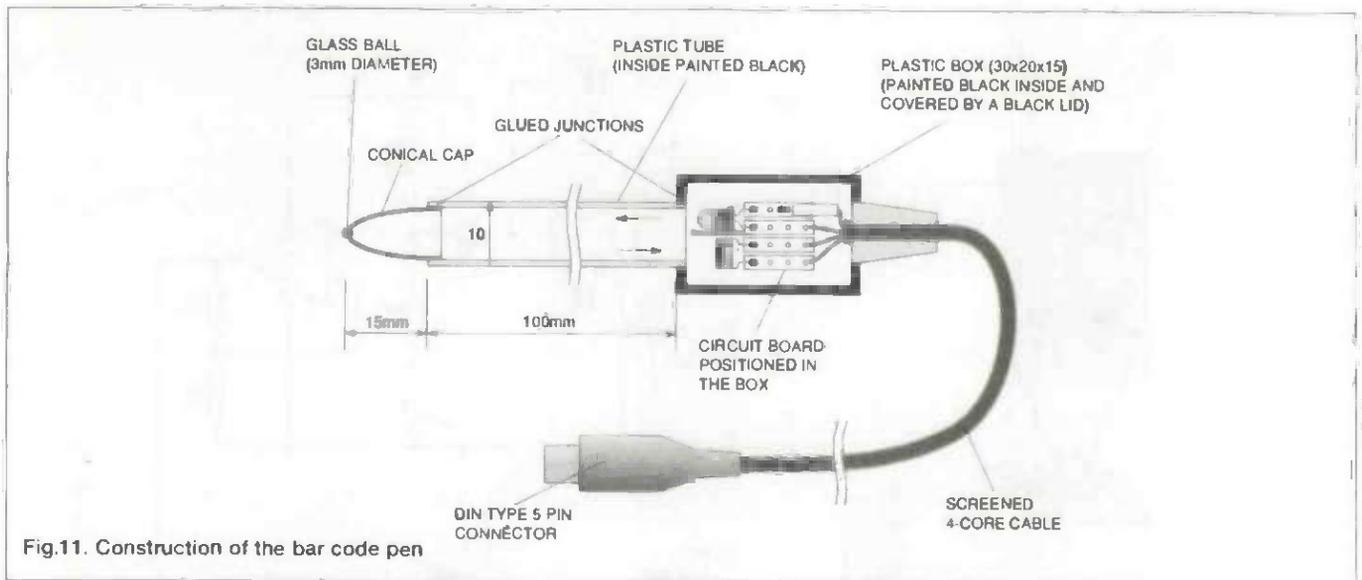


Fig.11. Construction of the bar code pen

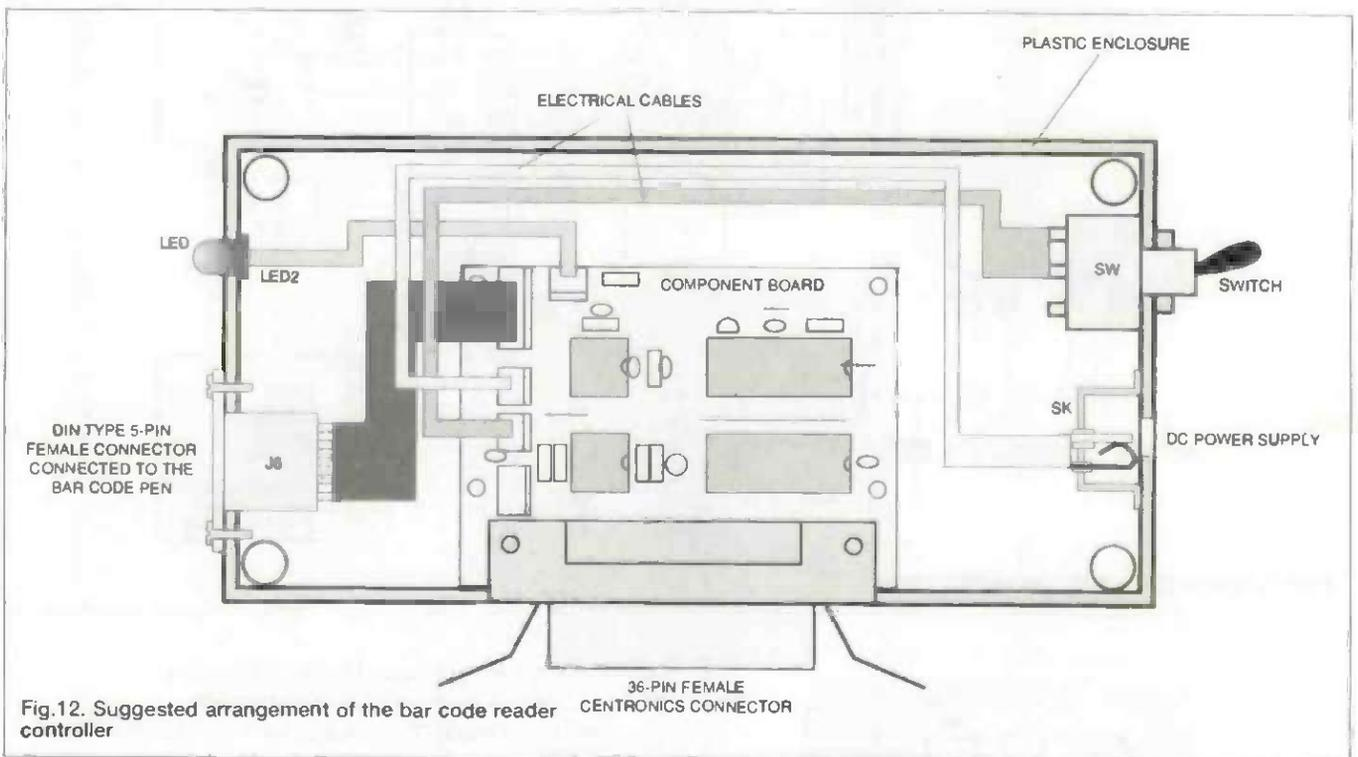


Fig.12. Suggested arrangement of the bar code reader controller

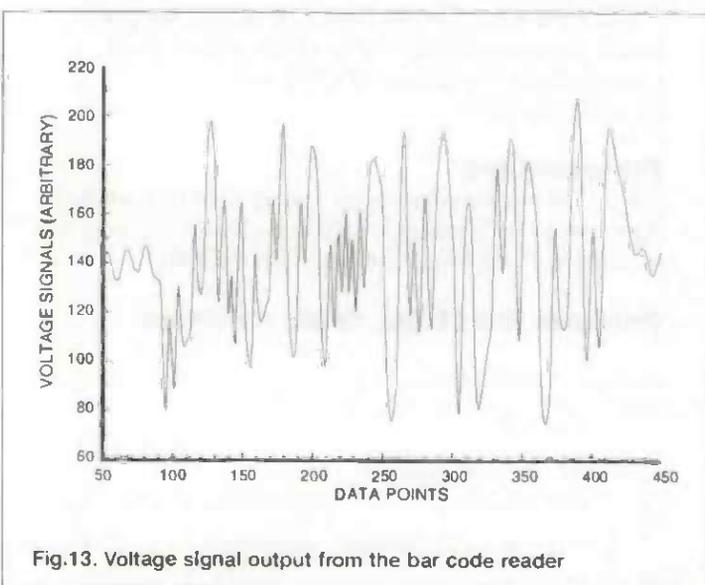


Fig.13. Voltage signal output from the bar code reader

```
integer;
sum, average: real;
datafile:text;

(Variables: byte1=4 high bits, byte2=4
low bits, truebyte=8 bit byte from the
A/D converter)

Procedure initial_bit;
{Initialize binary bitweight and bit}
begin
  for i:=1 to 8 do begin bitweight[i]:=1;
bit[i]:=0; end;
  for j:=1 to 8 do begin
    for i:=1 to j-1 do
      bitweight[j]:=bitweight[j]*2;
    end;
  end;
end;

Procedure Input_printer_address;
{Input the address of the printer}
begin
  writeln('Configure the address of the
```



```
printer port');
  writeln('LPT1 on motherboard is 888');
  writeln('LPT1 on I/O card, check the address
of your computer, 956 for example');
  write ('Input the address of the printer
port: ');
  readln(P_address);
end;
```

```
Function voltage:real;
(Logging data into pc)
var
  sum:real;
  ii:integer;
```

```
begin
  initial_bit;
  port[P_address+2]:=0;
(CONVERT=0, DSL=1)
repeat
  byte1:=port[P_address+1];      (read
1st byte, check BUSY line and wait it to become
high)
until byte16666128;             (note: BUSY
line is inverted in the PC)
  byte1:=port[P_address+1];      (DSL=1,
read the high 4 bits)
  port[P_address+2]: 2;          (DSL=0)
  byte2:=port[P_address+1];      (read
the 4 low bits)
                                     (binary format)
of byte1 and byte2
...hhhh0 (high 4 bits)             byte1:
...llll0 (low 4 bits)             byte2:
```

```
care, h,l=data)
  byte1:=byte1 and 120;          (00011110 and
...hhhh0 = 000hhhh0)
  byte1:=byte1 shl 1;           (shift 1 bit
left, byte1 = 0000hhhh)
  byte2:=byte2 and 120;          (00011110 and
...llll0 = 00011110)
  byte2:=byte2 shr 3;           (shift 3 bits
right, byte2 = 11110000)
  truebyte:=byte1 or byte2;      (byte1 or byte2 =
11110000 or 0000hhhh = 1111hhhh)
  Voltage:=(truebyte);
end;
```

```
Procedure delaytime;
var kk:integer;
begin
  for kk:=1 to 300 do dummy:=10;
end;
```

```
Procedure read_barcode;
begin
  for k:=1 to 500 do begin
V[k]:=round(voltage);delaytime; end;
end;
```

```
Procedure print_barcode;
begin
  for k:=1 to 500 do writeln(V[i]:5);
end;
```

```
Procedure save_data;
begin
  readln;
  assign(datafile,'c:barcode.dat');
  rewrite(datafile);
  for i:=1 to 500 do writeln(datafile,i,
',V[i]);
  close(datafile);
end;
```

```
Procedure crtinitialization;
(show initial data on the screen)
begin
  writeln;
  writeln('*****
*** *****');
  writeln('          IBMPC 8 input 8 bit
          analogue to digital
          converter program');
```

```
writeln('*****
*** *****');
  writeln;
  writeln;
end;
```

```
procedure display_results;
begin
  gotoxy(40,7);write(Voltage:7:3); (show
results on crt)
end;
```

```
Procedure Plot_barcode;
var
  Gd, Gm : Integer;
begin
  Gd := Detect; InitGraph(Gd, Gm, '');
  if GraphResult 66669999 grOk then Halt(1);
  OutText('Voltage from barcode reader');
  moveto(1,V[1]);
  for k:=2 to 800 do begin lineto(k,300
V[k]);end
  readln;
  CloseGraph;
end;
```

```
Procedure Scan;
(barcode scan procedure)
begin
  repeat
    writeln('Please use your barcode reader pen');
    {repeat
      sum:=0;
      for k:=1 to 50 do sum:=sum+voltage;
      average:=sum/50;
      until (voltage6666round(average6));}
```

```
    writeln('Start reading barcode');
    read_barcode;
    plot_barcode;
    save_data;
    writeln('Finish reading barcode');
    readln;
  until keypressed;
end;
```

```
Procedure Analysis_barcode;
begin
end;
```


```
{=====main program=====}
begin
  clrscr;
  input_printer_address;
  crtinitialization;
  scan;
  gotoxy(10,19);write('Thank you for running
this program');
  readln;
end.
```

Decoding the bar code

Figure 13 shows the voltage signal of a bar code sample read into the computer. To write a software to decode the bar code signal into numerical digit is certainly a challenge. It is also a difficult task.

EASY-PC, Schematic and PCB CAD

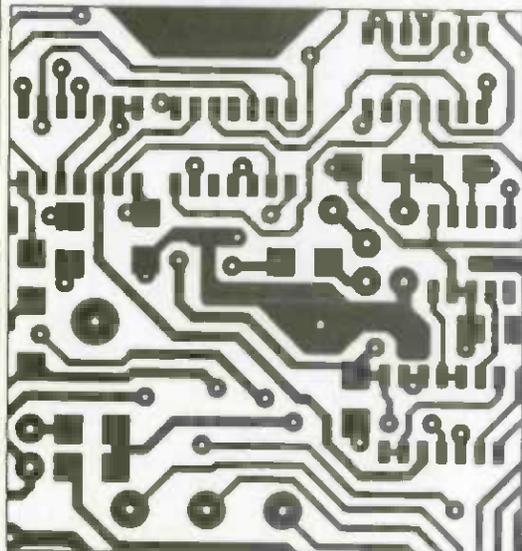Over 19,000 Installations
in 80 Countries World-wide!




- Runs on:- PC/XT/AT/286/386/486 with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design:- Single sided, Double sided and Multi-layer (8) boards.
- Provides full Surface Mount support.
- Standard output includes Dot Matrix / Laser / Ink-jet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Tech Support - free.
- Superbly easy to use.

Still
Only
£98.00!

Plus P&P+VAT


**BRITISH
DESIGN
AWARD
1989**

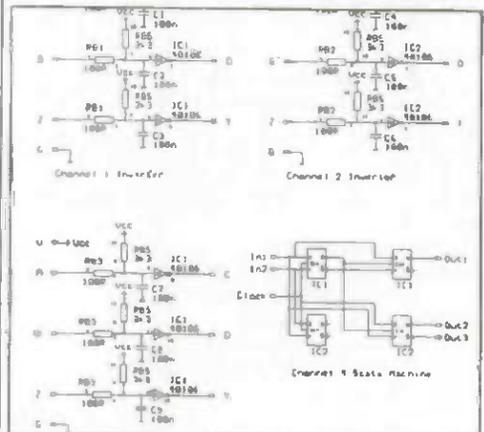

Options:-500 piece Surface Mount Symbol Library £48,
1000 piece Symbol Library £38, Gerber Import facility £98.

Electronic Designs Right First Time?


Integrated Electronics CAD

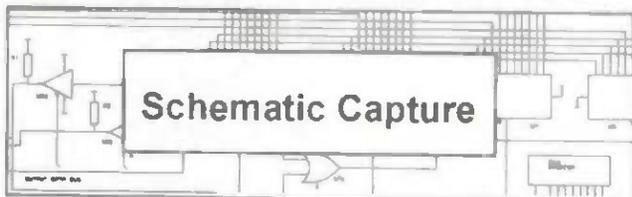

Schematic Capture



Analogue
& Digital
Simulation

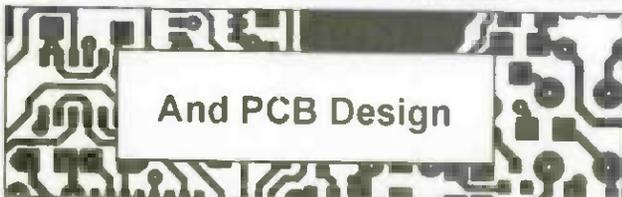

And PCB Design

Prices from UK£195 / US\$375

Affordable Electronics CAD

LAYAN: New Electro-Magnetic layout Simulator. Include board parasitics in your Analogue simulations. Links with and requires EASY-PC Professional XM and ANALYSER III Professional	\$950	£495
EASY-PC Professional: Schematic Capture and PCB CAD. Links directly to ANALYSER III, LAYAN and PULSAR.	From \$375	£195
PULSAR: Digital Circuit Simulator	From \$195	£98
ANALYSER III: Analogue Linear Circuit Simulator	From \$195	£98
FILTECH: Active and Passive Filter Design program	From \$275	£145
STOCKIT: New comprehensive Stock control program for the small or medium sized business	\$275	£145
EASY-PC: Entry level PCB and Schematic CAD.	\$195	£98
Z-MATCH for Windows: Windows based Smith-Chart program for RF Engineers.	\$475	£245

We operate a no penalty upgrade policy.
US\$ prices include Post and Packing
Sterling Prices exclude P&P and VAT.

For full information, please write, phone or fax:-

Number One Systems

UK/EEC: Ref: ETI, HARDING WAY, ST.IVES, CAMBS., ENGLAND, PE17 4WR.

Telephone UK: 01480 461778 (7 lines) Fax: 01480 494042

USA: Ref: ETI, 126 Smith Creek Drive, Los Gatos, CA 95030

Telephone/Fax: (408) 395-0249

- TECHNICAL SUPPORT FREE FOR LIFE
- PROGRAMS NOT COPY PROTECTED.
- SPECIAL PRICES FOR EDUCATION.

Email: sales@numberone.com
International +44 1480 461778





**8 CAVANS WAY,
BINLEY INDUSTRIAL ESTATE,
COVENTRY CV3 2SF**
Tel: 01203 650702
Fax: 01203 650773
Mobile: 0860 400683

(Premises situated close to Eastern-by-pass in Coventry with easy access to M1, M6, M40, M42, M45 and M69)

OSCILLOSCOPES

Gould OS3000/ADVANCE 3000 - 30MHz Dual ch.	£200
Gould 5110 - 100MHz Intelligent oscilloscope	£850
Hewlett Packard 1740A, 1741A, 1774A, 100MHz dual ch.	from £350
Hewlett Packard 1707A, 1707B - 75MHz 2ch	from £275
Hewlett Packard 1980B - 100MHz, 2 Channel, HPIB Progble.	£750
Hewlett Packard 54201A - 300MHz Digitizing	£1750
Hewlett Packard 54501A - 100MHz - Digitizing 4 channel	£1950
Hewlett Packard 54100D - 1GHz Digitizing	£4500
Iwatsu TS 8129 - 100 MHz - D. Storage	£850
Kikusui COS 6100 - 100MHz, 5 Channel, 12 Trace	£475
Lecroy 140 - 100MHz - D.S.O.	£3250
Nicolet 3091 - LF D.S.O.	£1100
Phillips PM 3315 - 60MHz - D.S.O.	£750
Phillips 3211, 3217, 3240, 3243, 3244, 3261, 3262 (2ch + 4ch)	from £125 to £350
Phillips PM 3295A - 400MHz Dual Channel	£1950
Phillips PM 3295 - 350MHz Dual Channel	£1500
Tektronix 468 - 100MHz - D.S.O.	£800
Tektronix 2213 - 60MHz Dual Channel	£425
Tektronix 2215 60MHz dual trace	£450
Tektronix 2235 Dual trace 100MHz (portable)	£800
Tektronix 2335 Dual trace 100MHz (portable)	£750
Tektronix 2225 - 50MHz dual ch	£450
Tektronix 2465A - 350 Mhz 4 channel	£2950
Tektronix 464/466 - 100MHz An storage.	from £350
Tektronix 465/465B - 100MHz dual ch.	from £350
Tektronix 475 - 200MHz Dual Channel	£475
Tektronix 7313, 7603, 7613, 7623, 7633, 100MHz 4 ch	from £300
Tektronix 7704 - 250MHz 4 ch	from £650
Tektronix 7904 - 500MHz	from £850
Tequipment D68 - 50MHz Dual Channel	£200

Other scopes available too

SPECTRUM ANALYSERS

Advantest 4133B - 100KHz - 20 GHz (60 GHz with ext. mixers)	£8995
Alltech 727 - Spec. Analyser 2.4 GHz with	} £2000
Alltech 70727 - Tracking Generator (10KHz - 12.4 GHz)	
Anritsu MS2610A - 10KHz - 2.2GHz	£5250
Advantest 4133B - 10KHz - 20GHz (60GHz with ext. mixers)	£8995
Eaton/Alltech 757 - 10KHz - 22 GHz	£2750
Hewlett Packard 3580A - .5Hz-50KHz	£995
Hewlett Packard 3709B - Constellation Analyser with 15709A High Impedance Interface (As New)	£6750
Hewlett Packard 182T with 8559A (10MHz - 21GHz)	£3750
HP 3582A - 25KHz Analyser, dual channel	£2500
Hewlett Packard 35601A - Spectrum Analyser Interface	£1000
Hewlett Packard 8754A - Network Analyser 4 - 1300MHz	£3250
Hewlett Packard 853A with 8558A - (0.1 - 1500 MHz)	£3500
Hewlett Packard 853A with 8559A - (0.01 - 21GHz)	£4250
Hewlett Packard 8565A - (0.01 - 22GHz)	£4000
Hewlett Packard 141T + 8552B + 8555A - (10MHz - 18GHz)	£1600
Hewlett Packard 8756A - Scalar Network AN (10MHz - 18GHz)	£2250
Hewlett Packard 8505A - Network Analyser (500KHz - 1.3GHz)	£4000
Hewlett Packard 3562A Dual Channel Dynamic Sig. Analyser	£7500
Hewlett Packard 8590A 15 10KHz-1.5 GHz	£4350
Marconi 2370 - 110MHz	£995
Marconi 2371 - 30KHz - 200MHz	£1250
Poird 641-1 - 10MHz - 18GHz	£1500
Rohde & Schwarz - SWOB 5 Polysok 0.1 - 1300MHz	£2500
Schlumberger 1250 - Frequency Response Analyser	£2500
Tektronix 7L14 with 7603 mainframe (1.8GHz)	£2000
Tektronix 2710 9 KHz - 1.8 GHz	£4250
Tektronix 496P - 9KHz - 1.8GHz (Programmable)	£4500
Texscan AL51A (4MHz - 1GHz)	£850

MISCELLANEOUS

ANRITSU ME 462B DF/3 Transmission Analyser	£3000
Anritsu MG642A Pulse Pattern Generator	£1500
Databal DL 1080 Programmable Transient Recorder	£350
Datron 1061 - Precision Multimeter	£650
Dyanpert TP20 Intellipace - Tape peel Tester - Immaculate condition	£1950
E.I.P. 548A - Frequency counter (26.5 GHz)	£3500
EIP 331 - Frequency counter 18GHz	£700
Farnell SSG-520 Signal Generator (520 MHz)	£400
Farnell TTS 520 Transmitter Test Set	£400
Farnell TSV 70 MkII Power Supply (70V-5A or 35V-10A)	£200
Ferroglyph RTS-2 Audio Test Set with ATU 1	£500
Heiden 1107 - 30V-10A Programmable Power Supply (IEEE)	£650
Hewlett Packard 4953A - Protocol Analyser	£2995
Hewlett Packard 3437A System voltmeter	£350
Hewlett Packard 3456A Digital voltmeter	£850
Hewlett Packard 5420A Digital Signal Analyser	£350
Hewlett Packard 8011A Pulse gen. 0.1Hz-20MHz	£500
Hewlett Packard 8620C Sweep oscillator mainframe	£400
Hewlett Packard 8750A Storage normaliser	£375
Hewlett Packard 8684A 5.4GHz to 12.5GHz Sig-Gen.	£3500
Hewlett Packard 8640B - AM/FM Signal Gen (512MHz)	£850
Hewlett Packard 5340A - 18GHz Frequency Counter	£900
Hewlett Packard 5356A - 18GHz Frequency Converter head	£450
Hewlett Packard 432A - Power Meter (with 478A Sensor)	£275
Hewlett Packard 435A or B Power Meter (with 8481A/8484A)	from £750
Hewlett Packard 3438A Digital multimeter	£200
Hewlett Packard 6181C D.C. current source	£150
Hewlett Packard 3711A/3712A/3791B/3793B Microwave Link Analyser	£3500
Hewlett Packard 5385A Frequency Counter - 1GHz - (HP1B) with OPTS 001/003/004/005	£995
Hewlett Packard 6623A Triple output system power supply	£1950

Hewlett Packard 3586A Selective level meter	£1750
Hewlett Packard 3325A - 21MHz Synthesiser/Function Gen	£1500
Hewlett Packard 8152A - Optical Average Power Meter	£1250
Hewlett Packard 8158B - Optical Attenuator (OPTS 002 + 011)	£1100
Hewlett Packard 3488A - HP - 1B Switch control unit (various Plug-Ins available)	£650
Hewlett Packard 3581C - Selective Voltmeter	£900
Hewlett Packard 3708A - Noise & Interference Test Set	£850
Hewlett Packard 4192A - L.F. Impedance Analyser (5Hz - 12MHz)	£8000
Hewlett Packard 4261A - L.C.R. Meter (Digital)	£500
Hewlett Packard 4271B - L.C.R. Meter (Digital)	£900

HEWLETT PACKARD 6261B Power Supply 20v-50A £500 Discount for Quantities


Hewlett Packard 4342A - 'Q' Meter	£995
Hewlett Packard 4954A - Protocol Analyser	£3500
Hewlett Packard 8116A - Pulse/Function Generator (1MHz - 50MHz)	£2750
Hewlett Packard 8349B - Microwave Broadband Amplifier (as new) 2 - 20GHz	£4700
Hewlett Packard 8350B - Sweep Oscillator Mainframe (various Plug-Ins available) extra	£2650
Hewlett Packard 8656A - Synthesised Signal Gen (100KHz - 990MHz)	£1750
Hewlett Packard 8683A - Microwave Signal Gen (2.3 - 6.5GHz)	£3500
Hewlett Packard 8901B - Modulation Analyser (150KHz - 1300MHz)	£4250
Hewlett Packard 8903A - Audio Analyser (20Hz - 10CKHz)	£2600
Hewlett Packard 8903B - Analyser (20Hz - 100KHz)	£3250
Hewlett Packard 3455A 61/2 Digit M/Meter (Autocal)	£750
Hewlett Packard 3326A - Two Channel Synthesiser	£3750
Hewlett Packard 4948A - (TIMS) Transmission Impairment M/Set	£2000
Hewlett Packard 8601A - Generator/Sweeper (110 MHz)	£300
Hewlett Packard 8660C - Synth Signal Gen. (1300 MHz)	£1750
Hewlett Packard 3575A Gain/Phase Meter (1Hz - 13 MHz)	£500
Hewlett Packard 8165A - 50 MHz Programmable Signal Source	£1650
Hewlett Packard 3746 A - Selective Level Measuring Set	£1750
Hewlett Packard 6002A - Autoranging P.S.U. 50V - 10A	£650
Hewlett Packard 8403A - Modulator	£500
Hewlett Packard 334A - Distortion Analyser	£300
Hewlett Packard 339A - Distortion Measuring Set	£1500
Hewlett Packard 5314A (NEW) 100MHz Universal Counter	£250
Hewlett Packard 5350B (NEW) 20GHz - Microwave Freq. Counter	£2500
Hewlett Packard 8901B - Modulation Analyser	£4250
Hewlett Packard 8903A - Audio Analyser	£2600
Hewlett Packard 8903B - Audio Analyser	£3250
Hewlett Packard 8116A - Pulse/Funct. Gen (1MHz - 50 MHz)	£2750
Hewlett Packard 8349B - Microwave Broadband Amp (as new)	£4700
Hewlett Packard 8350B - Sweep Oscillator Mainframe (Various Plug-ins)	£2650
Hewlett Packard 8683A - Microwave Sig. Gen. (2.3 - 6.5 GHz)	£3500
Hewlett Packard 8656A - Synthesised Sig. Gen (100KHz - 990 MHz)	£1750
Hewlett Packard 4954A - Protocol Analyser	£3500
Hewlett Packard 4192A - L.F. Impedance Analyser (5Hz-13MHz)	£8000
Hewlett Packard 4261A - LCR Meter (digital)	£500
Hewlett Packard 4271B - LCR Meter (Digital)	£900
Hewlett Packard 4342A - 'Q' Meter	£995
Hewlett Packard 3708A Noise + Interference Test Set	£8500
Hewlett Packard 6623A - Triple Output system P.S.U.	£1950
Hewlett Packard 3581C Selective Voltmeter	£900
Krohn-Hite 2200 Lin/Log Sweep Generator	£995
Krohn-Hite 4204A Oscillator	£250
Krohn-Hite 6500 Phase Meter	£250
Marconi 2432A 500MHz digital freq. meter	£200
Marconi 2337A Automatic dist. meter	£150
Marconi - 2019A - 80KHz - 1040MHz - Synthesised Signal Generator	£1950
Marconi 2305 Modulation Meter	£200
Marconi 2871 Delta Comms Analyser	£200
Marconi 6500 Automatic Amplitude Analyser	£1750
Phillips PM 5167 10MHz function gen.	£400
Phillips PM 5565 - Waveform Monitor	£200
Phillips PM 5567 - Vectorscope	£500
Phillips PM 8226 - 6 Way Pen Recorder	£350
Phillips 5190 L.F. Synthesiser (G.P.I.B.)	£800
Phillips 5390 Programmable R/F Signal Gen (1020 MHz)	£1250
Phoenix 5500A - Telecomms Analyser with various Interface Options	£2500
Powersense - Power Line Analyser	£1950
Racal Dana 9242D Programmable PSU 25V-2A	£300
Racal Dana 9246S Programmable PSU 25V-10A	£400
Racal Dana 3100 40-130MHz synthesiser	£750
Racal 1992 - 1.3GHz Frequency Counter	£850
Racal Dana 9081 Synth. sig. gen. 520MHz	£550
Racal Dana 9084 Synth. sig. gen. 104MHz	£450
Racal Dana 9303 True RMS/R/F level meter	£650
Racal Dana 9917 UHF frequency meter 560MHz	£175
Racal Dana 9302A R/F millivoltmeter (new version)	£375
Racal Dana 9082 Synthesised am/fm sig gen (520MHz)	£500
Racal 9301A - True RMS R/F Millivoltmeter	£300
Racal 9921 - 3GHz Frequency Counter	£450
Rohde & Schwarz - Scud Radio Code Test Set	£995
Rohde & Schwarz SUF 2 Noise Generator	£300
Schlumberger S.I. 4040 Stablock - High accuracy 1GHz Radio Test Set	£5950
Schlumberger 4923 Radio Code Test Set	£1500
Schlumberger 2720 1250 MHz Frequency Counter	£500
Syston Donner 1702 Synthesised Sig. Gen 1GHz	£990
Syston Donner 6054B or D 18GHz or 24GHz Freq. Counter	from £800
Tequipment CT71 Curve Tracer	£250
Tektronix TM5003 + AFG 5101 Arbitrary Function Gen.	£1750
Tektronix 1240 Logic Analyser	£750
Tektronix 1480 Waveform Monitor	£POA
Tektronix 651 HR Monitor	£POA
Tektronix DAS9100 - Series Logic Analyser	£500
Tektronix - Plug-ins - many available such as SG504, SW503, SG502, PG508, FG504, FG503, TG501, TR503 + many more	£POA
Tektronix 576 - Curve Tracer (with Test Fixture)	£1250
Tektronix AM503 + TM501 + P6302 - Current Probe Amplifier	£995
Tektronix PG506 + TG501 + SG503 + TM503 - Oscilloscope Calibrator	£1995
Tektronix CG5001 - Programmable Oscilloscope Calibrator Generator	£7500
Time 9811 Programmable Resistance	£800
Time 9814 Voltage Calibrator	£750
Wayne Kerr B905 - Precision L.C.R. Meter	£850
Wiltron 560 Scalar Network Analyser	£800

**MANY MORE ITEMS AVAILABLE - SEND LARGE S.A.E. FOR LIST OF EQUIPMENT
ALL EQUIPMENT IS USED - WITH 30 DAYS GUARANTEE.
PLEASE CHECK FOR AVAILABILITY BEFORE ORDERING - CARRIAGE & VAT TO BE ADDED TO ALL GOODS**

Electronics Workbench

Version

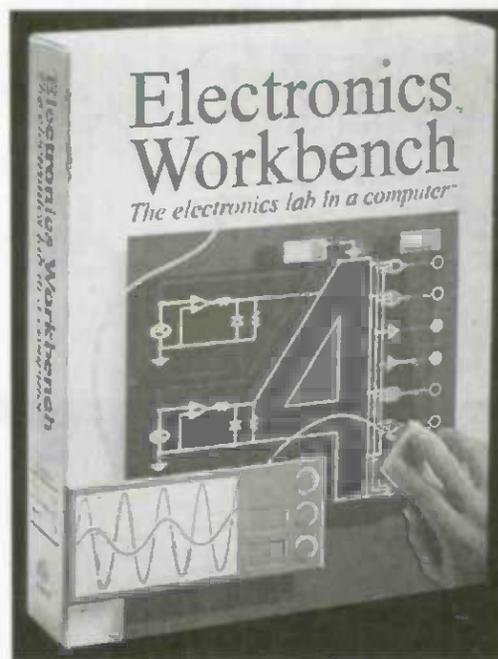Paul Stenning takes a look at a software package which lets you design circuits on your PC



I tend to regard myself as a practical electronics engineer. Most of my designs are based on experiment and I do not normally calculate much if I can avoid it. I studied electronics at college some years ago and have a reasonable understanding of the theory. However, I normally find that designing circuits by calculation takes longer than hooking together a few components and making some measurements.

I have tried conventional analysis (SPICE) software in the past, but I normally found this to be difficult to use. This usually involves manually creating a netlist from the circuit and keying it in - a time-consuming and error-prone procedure. In theory, it should have been possible to create netlists from schematic capture software, but I had little success getting this to work properly. The numerical results were often difficult to interpret - which made me wonder if it was worth all the effort!

Electronics Workbench

"Electronics Workbench" offers a different and much more logical approach to circuit simulation. The circuit diagram is first drawn on the screen, using components supplied. Test Instruments are then connected, and the setup is 'switched on'. The results are displayed on the instruments in a similar manner to real instruments.

Previous versions of Electronics Workbench have had separate programs for analogue and digital circuits, with no

facilities to readily mix the two. Version 4 is a true mixed-mode simulator, allowing analogue and digital circuitry to be combined in one design.

So we have the ability to analyse analogue, digital and mixed signal circuits, in what appears to be close to real-life situations, for just £199 + VAT. But how does it stand up in practice?

Installation

Electronics Workbench Version 4 is available in versions for Microsoft Windows, MS-DOS and the Apple Macintosh. I reviewed the Windows version on a 486SX computer with 4MB of RAM, running MS-DOS 5.00 and Windows for Workgroups 3.11.

The software is supplied on two 720K 3.5" disks. When installed, it takes up about 3.5MB of hard disk.

Installation was uneventful, except for one question about whether I wished to use North American ANSI or European DIN component symbols. There is no mention of this in the installation guide or the other manuals. Both variants are shown in the Quick Reference Card, but I didn't find this until after installation!

I chose the default ANSI standard because it is the one I am most familiar with and the one used in this magazine. In the DIN standard, logic gates and many other components are represented by rectangles containing characters - most confusing!

Copy protection

From reading the Installation Card, I was initially worried that I was about to encounter some horrendous disk-based copy protection system that would not allow normal backup operations (I have lost software in the past due to this, when a hard drive failed). I understand that some previous versions of Electronics Workbench had this affliction, but this current version seems to be more polite. I was able to copy the original disks for safety and then install the software from the copies.


During installation, the product serial number and the user's name is requested and written to the floppy disk. When the software is started for the first time only, it requests the entry of a specified word in the User's Manual - a simple and effective scheme that makes pirate copies useless! The first time I tried this, it did not work, probably due to a minor discrepancy between the software and the manual, but the second time it was fine.

A single Hidden System file is written to the hard disk and the software will not work if this is missing. Having successfully installed the software, I deleted it manually from the hard disk and then tried to install it again. This was also successful, confirming that the copy protection is not too restrictive and that an accidentally lost installation can be replaced.

Screen layout

The screen layout is tidy and uncluttered. The top section contains the usual windows title and menu bars and, below this, are the buttons to select different component libraries and the test equipment icons. The contents of the current library is displayed in the 'Parts Bin' down the left side of the screen, leaving a large area (referred to as 'The Workbench') for drawing the circuit.

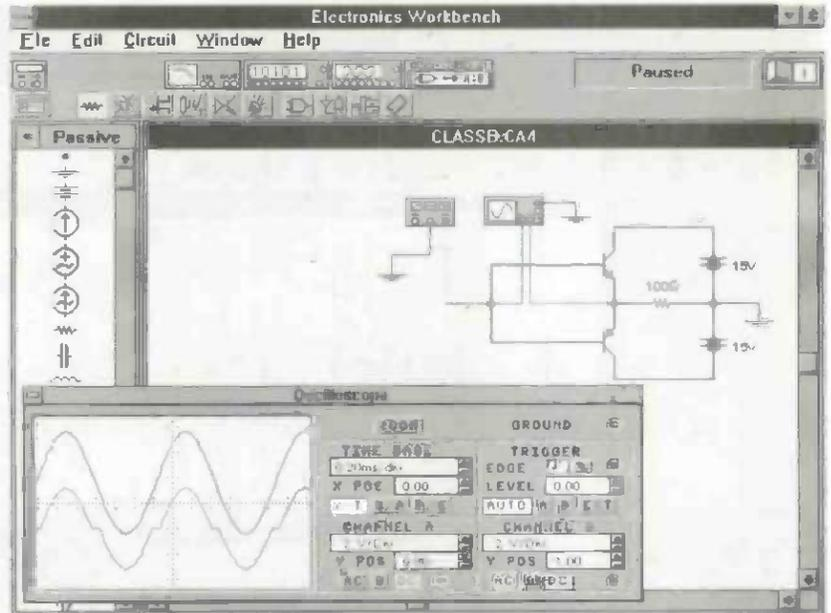I started by working my way through the Getting Started and Tutorial sections in the User's Guide. This is clearly written and guides new users gently through the software. It obviously



does not try to teach the user about electronics, but the circuits used to illustrate the tutorial are straightforward and probably readily understood by most people with at least a little electronics knowledge.

Components

A good selection of common components are included with the software; however, there is an American bias to the devices offered. For example, the Zener diodes all have 1N type numbers, rather than the BZX79 style numbers commonly used in the UK. Also, the AC voltage source defaults to 120V 60Hz. Additional components can be created and the defaults modified, but this requires some understanding of SPICE models. Perhaps the UK distributors might consider including an additional disk of European components within the price of the software.

I found a couple of minor errors in the component models. For example, the forward voltage drop of the LEDs was set at 0.75V, whereas in reality it should have been about 2V. This is easy enough to correct, but how could a silly error like this


remain, in a standard component, in Version 4 of the software?


Approximately 350 different components are included with the software as standard. An additional 2100 are available in four add-on libraries which are available at extra cost.

As well as actual components, "ideal" components are included. These are useful for comparing the performance of real components with ideal parts and for proving whether a non-working circuit is due to the peculiarities of a specific component.

Connections

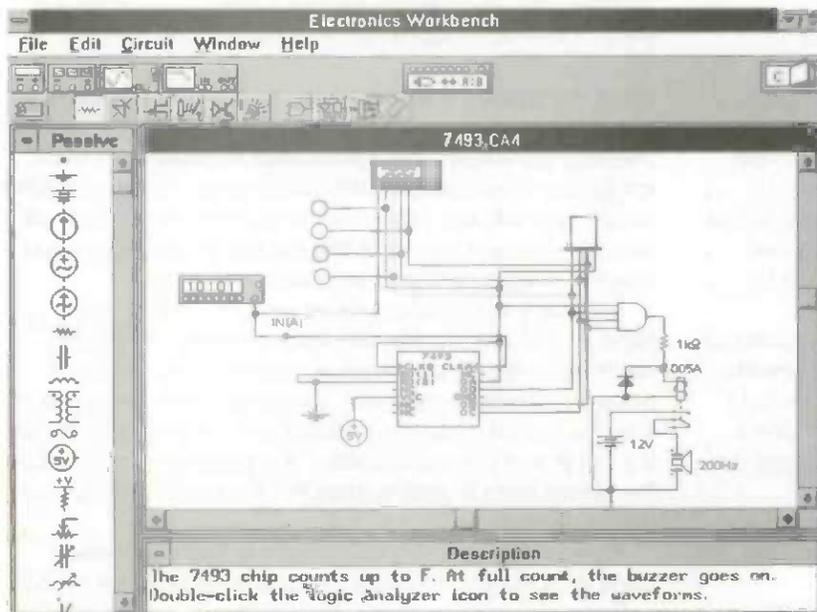Connections are made by simply dragging a wire from one component terminal to another - the wires being routed tidily automatically. Wires can also be connected from components to other wires, whereupon connector dots will



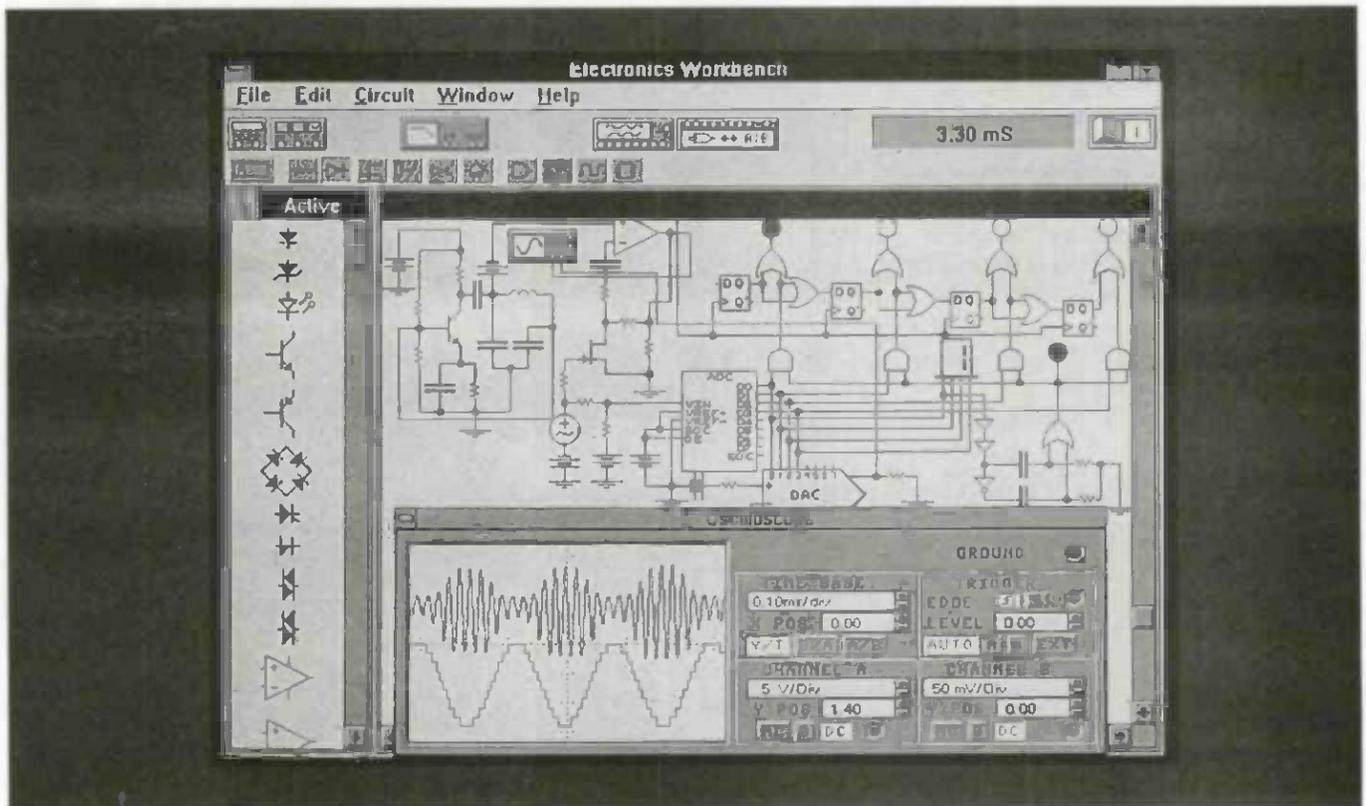

appear automatically.

I sometimes wished for a method of routing the connections manually, as things can get somewhat untidy if one is not careful. However, the purpose of the schematic drawing is for entering circuits for analysis; the software is not really intended for circuit diagram illustration.

A PCB export package is available as an optional add-on module, for those who want to use Electronics Workbench as a schematic capture front-end. I personally wouldn't bother with this sort of thing though. I find trying to get two unrelated programs to communicate successfully is a superb way of wasting time! It is much easier and more productive to use a PCB design package that includes schematic editing and capture as standard.

Test Equipment

Having drawn the circuit, the next stage is to add the appropriate test equipment. A selection of instruments are included, including a Multimeter, Logic Analyser and Function Generator.

The Oscilloscope has just two channels, in common with most bench units. I would have preferred a couple of extra channels. I sometimes wanted to monitor the input and output of a circuit, as well as a couple of intermediate points. Two channels can be limiting at times and I think four would be more realistic.

A Bode Plotter allows frequency responses to be measured and displayed. The Word Generator and the Logic Converter allow digital circuits to be tested and analysed. One feature I appreciate is the ability of the Logic Converter to produce a logic circuit from a truth table. I have spent hours working this sort of thing out on paper in the past!

Only one of each of these instruments can be used in a circuit. The instruments can be displayed by double-clicking on them and can then be set up as required.

Ammeters and Voltmeters are included in the Parts Bin, and

can be used in any quantity. On AC, these read in RMS terms. The manual does not state whether they will read on a fluctuating DC signal - it appears to be some sort of average value.

Circuit analysis

Once everything is connected up, the analysis is started by clicking on the On switch at the top right corner of the screen. The software will analyse the behaviour of the circuit from the switch-on time until a steady state is reached. The displays on the test equipment update as the analysis continues and can normally be adjusted as necessary without restarting the analysis.

The time taken for analysis obviously depends on the complexity of the circuit, the analysis settings and the speed of the computer. The software will use a maths co-processor if one is fitted and I imagine this would make a significant difference. The process can seem slow if you are watching it but, if you consider the level of calculations involved, it is quite impressive.

The software does not take into account the maximum current, voltage and power ratings of the components. The fuse and lamp components will blow if over-run, but the other components just continue working. I appreciate that this sort of calculation would slow the analysis, so it could be a selectable option.

For example, I created a circuit where a 1N4001 diode (rated at 50V and 1A) was half wave rectifying a 1000V AC supply and carrying a continuous current of over 5A! A real diode would never survive this. The diode model does have an entry for reverse breakdown voltage (set in this case to 49.9V) but this seems to have little effect. It is possible to work around the current limits by adding fuses but this sort of thing should not be necessary.

It would also be useful (sometimes) to know the power being dissipated by a resistor. This can be established by the insertion of suitable ammeters and voltmeters, and multiplying

the readings manually but I would have expected to be able to get the results automatically.

I feel that the interface between the analogue and digital circuits may need some more work in places. For example, the input protection diodes on logic gates are not simulated and diodes would have to be added externally if a logic input was presented with an analogue input.

Other Circuits

I have entered some of my own experimental circuits, which I know from experience had various problems. I was impressed to see that the software reproduced most of these - including an amplifier that worked fine with sine waves but was prone to ringing with square waves. This sort of thing can be difficult to prove in practice, even with the appropriate test equipment.

I could not simulate a triac circuit that was prone to erratic behavior. This is probably due to the lamp model being purely resistive and not having the low cold resistance (and high initial current) that real lamps have.

Obviously the software cannot allow for layout problems and external noise, so some circuits will still need to be proved on the bench. Indeed, it would be foolish to commit to a design without proving it in practice but, with most of the design work already carried out using Electronics Workbench, the time involved in proving the circuit can be considerably reduced.

Documentation

Electronics Workbench is supplied with two main manuals. The User's Guide contains the tutorial, menu reference and general information needed for running the software. I would recommend reading most of this manual and working through the examples to appreciate the power and flexibility of the software. The Technical Reference manual contains useful detailed information on the test equipment and components and also describes the SPICE models used. Both manuals are clearly written and produced to a very high standard. I liked the idea of spreading the documentation over two manageable manuals, rather than having one bulky publication.

System Requirements

MS-DOS version

386 or higher processor, 4MB of RAM, 5MB hard disk space, VGA display, Microsoft or compatible mouse and installed driver, MS-DOS 3.0 or greater. Supports math co-processor if available (recommended).

Windows version

As MS-DOS version above, with Microsoft Windows version 3.1 or greater.

Macintosh version

Apple Mac with 68020 processor or higher, 4MB RAM (2MB available), System 6.0.5 or System 7. Does not support Macintosh Plus, SE, Classic, and PowerBook 100.

The same manuals are provided with the DOS and Windows versions of the software. There are some sections for DOS users only, but the emphasis is definitely towards Windows users, which may give DOS users the impression that they have been left behind.

Conclusion

Overall, I am very impressed with Electronics Workbench. I will certainly be using my copy for many of my future designs - the software has convinced me of the value of circuit analysis! I particularly like the way the software gives the feel of real components and instruments, rather than abstract netlists and charts of results. As a 'practical' engineer, it suits my way of thinking and working.

Supplier Details

Product Title - Electronics Workbench version 4
Publisher - Interactive Image Technologies Ltd,
111 Peter St., Suite 801,
Toronto, Ontario, Canada,
M5V 2H1. Tel (from UK)
001 416 977 5550. Fax
001 416 977 1818.
UK Distributor - Robinson
Marshall (Europe) Plc,
Nadella Building, Progress
Close, Leofric Business
Park, Coventry,
Warwickshire, CV3 2TF.
Tel 01203 233216. Fax
01203 233210.
Price - £199, plus £5.99
postage, plus VAT (total
£240.86). 30 day money-
back guarantee.
Four additional
component libraries are
available, price £29.95
each or £99.00 for set of
four. PCB Export add-on
module £49.95. All prices
are subject to postage
and VAT and are correct
at the time of writing.

Mega Download Internet

Bulletin Board
0891 516 126

No Subscriptions

Full Download Access
on your First Call

All Speeds to 28,800

Zmodem, Ymodem,
Xmodem, Kermit,
Sealink & others

New Files Daily

0891 516 126

Over 13,000 files
for immediate
download

Thousands
of GIF files

Your own Internet
email address for
contact with the
rest of the world

Science &
Technical
Programs

Super, Full Colour
ANSI Graphics

Mega Download
0891 516 126

Megadownload. POBox 3463, London SE19 1DB
Calls charged per minute
39p cheap rate, 49p all other times

Applications:

- Remote control systems
- Data transfer and networks
- Wire free PC-PC modems
- Wire free security alarms

Our 173.225MHz, 173.250MHz and 418MHz modules are DTI Type Approved and Licence Exempt within the UK.




TXM-418 or 433-A

WANTED

we urgently require sales representatives in countries outside the EEC

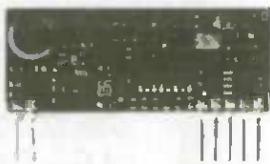Generous Quantity Discounts Available. We will beat any published price !



SILRX-418 or 433-A

Transmitters :

PART No	MPT	Freq MHz	Data Rate	ERP mW	Power (Vs)	Price 1 +
TXM-418-A	1340	418	10000	0.25	6 - 9	£14.00
TXM-418-F	1340	418	20000	0.25	2.7-3.6	£14.75
TXM-433-A	N/A	433.92	10000	0.25	6 - 9	£14.75
TXM-433-F	N/A	433.92	20000	0.25	2.7-3.6	£14.75
TXM-4689-UK-00	1328 1344	173.250 173.225	1000	1.0	3.0	£22.48
TXM-4689-UK-03	1328 1344	173.250 173.225	1000	10.0	5.0	£24.50

Key: MPT = DTI Type Approval Specification. ERP = Output Power into 50Ω Load.

Receivers :

PART No	Freq MHz	RSSI	CD	Data Rate	Power (V)	Price 1+
RXM-418-A	418	✓	✓	10000	5.0	29.05
RXM-433-A	433.92	✓	✓	10000	5.0	29.95
SILRX-418-A	418	x	✓	5000	4.5 - 9	22.50
SILRX-433-A	433.92	x	✓	5000	4.5 - 9	23.95
RXM-4666-60	173.225 173.250	✓	✓	1000	5.0	31.62

Key: RSSI = Received Signal strength Output. CD = Carrier Detect Output

The BIM High Speed Transceiver :

Part No	MPT	Freq MHz	Data Rate	Power (V)	ERP mW	Price 1 +
BIM-418-F	1340	418	40000	5.0	0.25	49.95
BIM-433-F	ETS	433.92	40000	5.0	1.0	49.95



BIM-418 or 433-F

The BIM Engineering Kit.

To assist new customers unfamiliar with the BIM, we are offering an engineering kit comprising: Two PCB's each containing a BIM-418 or 433 transceiver, status LED's, bit error rate LED bar graph, PIC microcontroller with test firmware, antenna and batteries. Using the kit you will be able to simulate data transfer at up to 40000bps, conduct range tests, evaluate various data protocols and finally transmit your own data. BIM-418-DEV.

Only £ 149.95

The BIM Remote Packet Controller Board

Cut your development timescales by half ! You can avoid developing your own RF protocol for the BIM. The RPC makes the BIM as simple to use as an IC. Just load in a parallel nibble/s and receive it the other end! The RPC board comes complete with a BIM on 418 or 433MHz, a PIC micro with user E²PROM, 4 - bit parallel interface with control lines and antenna.

Only £ 79.95

Delivery: Most items are available from stock. Antenna & Screening cans now available.

Orders: Prices exclude carriage and VAT. Radio - Tech Limited, Overbridge House, 41 Weald Hall Lane, Thornwood Common, Epping, CM16 6NB. Telephone and credit card orders welcome.

Tel: Sales 0181-368-8277 Fax 0181-361-3434, Admin 01992 - 576107 Fax 01992 -561994



SEETRAX CAE RANGER PCB DESIGN

WITH COOPER & CHYAN AUTOROUTER

RANGER3 - DOS £2500
- Windows\NT £2900

Hierarchical or flat schematic linked to artwork.
 Unlimited design size, 1 micron resolution
 Any shaped pad, definable outline library
 Pin, gate & outline swapping - auto back annotation
 Split power planes, switchable on - line DRC

COOPER & CHYAN SPECCTRA
 autorouter (SP2)

Inputs: OrCAD, Cadstar,
 PCAD, AutoCAD DXF

Outputs: Postscript, Windows bit map

R2 & R3 Outputs: 8/9 & 24 pin printers, HP
 Desk & Laser Jet, Cannon Bubble Jet,
 HP-GL, Gerber,
 NC Drill, AutoCAD DXF

RANGER2 £150

Upto 8 pages of schematic linked to artwork
 Gate & pin swapping - automatic back annotation
 Copper flood fill, Power planes, Track necking,
 Curved tracks, Clearance checking,
 Simultaneous multi-layer auto-router

RANGER2 UTILITIES £250

COOPER & CHYAN SPECCTRA auto-router (SP1)
 Gerber-in viewer, AutoCAD DXF in & out

UPGRADE YOUR PCB PACKAGE
TO RANGER2 £60

TRADE IN YOUR EXISTING PACKAGE TODAY

Seetrax CAE, Hinton Daubnay House, Broadway Lane, Lovedean, Hants, PO8 OSG
 Call 01705 591037 or Fax 01705 599036 + VAT & P.P All Trademarks Acknowledged

FIELD ELECTRIC LTD
 TEL: 01438 353781 FAX: 01438 359397
 MOBILE: 0836 640328
 UNIT 2, WILLOWS LINK, STEVENAGE, HERTS SG2 8AB

102 KEY IBM COMPATIBLE KEYBOARD TERMINATED TO 6 PIN MINI DIN TYPE PS2 PLUG	8.00 c/p 3.75
YUASA NP10-6 6v 10ah SEALED LEAD ACID BATT NEW	7.95 c/p 4.00
PC PSU NEW 200 WATT SQUARE TYPE STANDARD PLUG	15.00 c/p 5.00
SONY 9" COLOUR RGB TRINITRON VDU (rgb connection supplied)	50.00
NEC CMV 123ne 12" COLOUR VGA/SVGA 800 x 600 VDU	5.00 c/p 14.00
NEC CMV 103 9" COLOUR VGA/SVGA 800 x 600 VDU	60.00 c/p 12.00
CCD BARCODE READER READS HIGH & LOW DENSITY CODES	60.00 c/p 6.00
ASTECA SA 301306 +5 @2A +15 @1.8A -15 @3A NEW BOXED	8.00 c/p 2.00
240v to 110v 80w AUTO TOROIDAL TRANSFORMER NEW	7.00 c/p 3.00
CALCOMP 2200 DIGITIZER (SLIGHT CASE DAMAGE)	100.00 c/p 15.00
LASER DRIVE INC.134 HE-NE GAS LASER NEW INPUT 10-14V OUTPUT DC 1250V	100.00 c/p 12.00
FLAN FOR COPIER/PROGRAMMER EPROM PROM EDITING & INTERFACE NEW BOXED	325.00 c/p 18.00
HP 7470A PLOTTER IEEE INC.INTERFACE CABLE	95.00 c/p 17.00
HP 1727A 275-MHz STORAGE OSCILLOSCOPE	490.00 c/p 24.00

WE STOCK FANS/MOTORS/PSU/TRANSFORMERS/COMPUTER HARDWARE/TEST EQUIP/TELEPHONE EQUIP/
 PLEASE RING.

PLEASE ADD 17.5% VAT TO ORDER. RING FOR C/P PRICES NOT SHOWN.
 OFFICIAL ORDERS AND OVERSEAS ENQUIRIES WELCOME.

★★ FOR SALE ★★

DEFENCE & AEROSPACE INDUSTRY
 ELECTRONIC EQUIPMENT & COMPONENTS ALL HIGH QUALITY SURPLUS
 MANY SPECIALS. WE STOCK 1000 +
 ITEMS & IF WE DON'T STOCK IT WE MAY
 BE ABLE TO GET IT FOR YOU
 PLEASE WRITE OR PHONE FOR LISTS
 OR REQUIREMENTS

MAYFLOWER ELECTRONICS
 48 BRENDON ROAD,
 WATCHET, SOMERSET, TA23 0HT
 TEL (01984) 631825 FAX 634245

Create your own **Mobile Robot v2**
 CONTROLLED BY COMPUTERS VIA PRINTER PORT
 EXPENDABLE TO RADIO CONTROLS

33.00 pounds +£2 P&P


A complete Kit including hard/software for you to build
 A Catalogue Full of PC interfacing ideas and plans

Innovative Interfacing Enterprise

Other PC Interfacing kits are available!
 Centronic and RS232 Explorer kits, Centronic and RS232 24-line programmable I/O cards
 Data logging systems, triple stepper motor boards, Radio controllers. see our catalogue!

Add £2 P&P in UK (£3.5 abroad) and make cheque payable to 'Innovative Interfacing Enterprises'
 58 Lamport Court, Lamport Close, Manchester M1 7EG, U.K. Tel/Fax +44-(0)161 272-8279

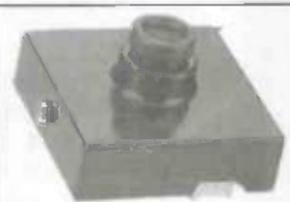HIGH QUALITY LOW COST C.C.T.V. CAMERA
 EXTREMELY LOW LIGHT LEVEL
 AUTO ELECTRONIC SHUTTER.
 COMPOSITE VIDEO OUT VIA BNC PLUG.
 SMALL DISCRETE SIZE.
 CAN BE USED WITH PC DIGITISER.




This super quality CCD camera can be connected into your existing TV or video using the AV channel and can be used for discrete surveillance or observing your property externally using a suitable weatherproof housing. Can accommodate lighting levels ranging from daylight to street lighting using its built-in electronic shutter. Excellent when using with an infra red source. Built-in wide angle fixed focus lens, the camera has a resolution of 380 TVL. Can be housed inside an empty floodlight case. (extra). Camera size only 45mm x 45mm.

Special offer price of only: **£79.95 plus VAT (P&P £3.00)**
 For full range of CCTV products send SAE to:
**DIRECT CCTV LTD., DEPT ETI, UNIT 6,
 CARRICK COURT, FORREST GROVE BUSINESS
 PARK, MIDDLESBROUGH TS2 1QE**

noise masker

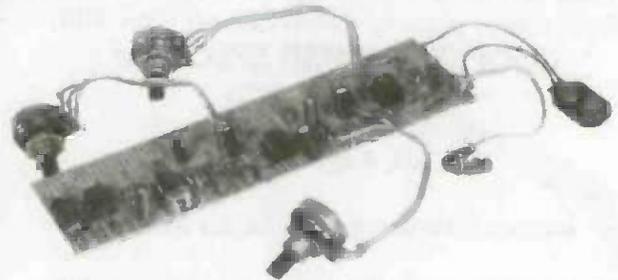Robert Penfold devises an electronic solution to the increasingly pervasive problem of noise pollution



The problem of noise pollution is one that seems to have steadily grown over the past twenty years or so. The generally accepted reason for this escalation is an increase in the range of electrical and electronic gadgets that can generate high enough sound level to cause annoyance to others. The average

home is now equipped with hi-fi equipment, power tools, "ghetto blasters" etc and it is virtually certain that one of these devices will cause annoyance to someone before too long. A certain amount of noise pollution is probably something that has to be accepted as a fact of modern life, but are there ways of counteracting the noise if you find yourself at the

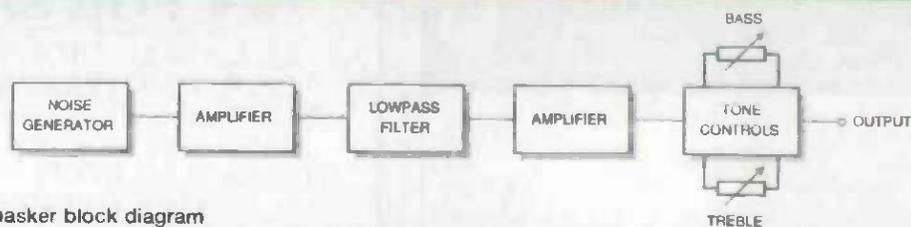


Fig.1. The sound masker block diagram


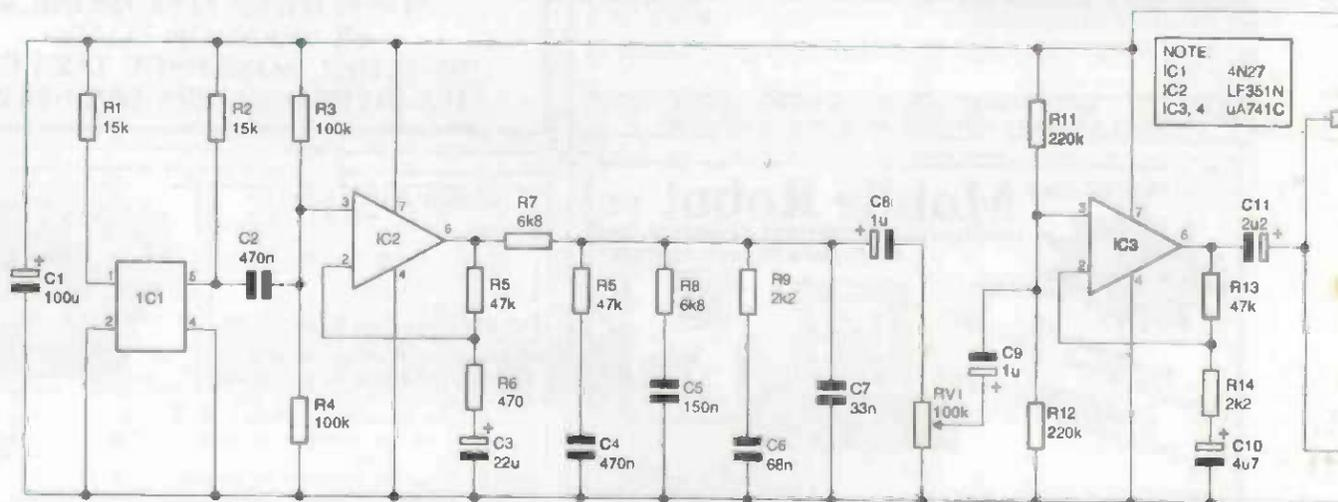



Fig.2. Full circuit diagram for the sound masker

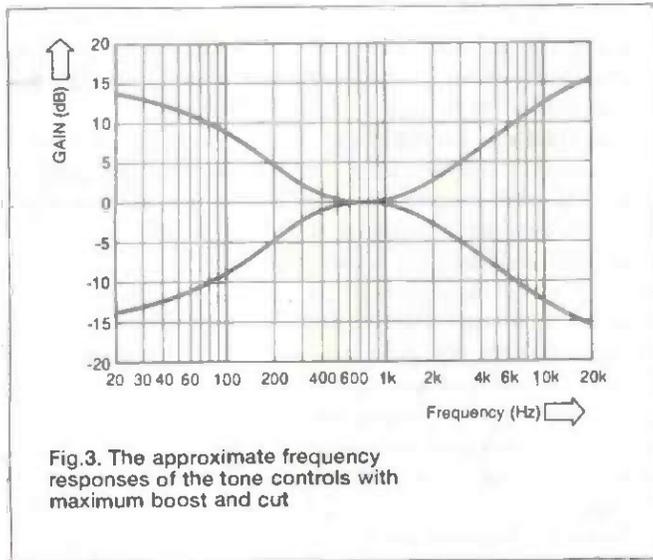

receiving end rather too often? There are actually several mechanical and electronic means of counteracting noise. Probably the most effective method (and the least comfortable) is to use ear defenders or earplugs. The RS/Electromail catalogue lists a fair range of devices to block sounds, such as the "Tracer Earplug" (662-485). With my ears, at any rate, earplugs such as these are very effective at combatting the "thump-thump-thump" from neighbours' hi-fi systems etc. The problem with devices such as these is that they tend to give you a sort of "shut off from the rest of the world" feeling that many people find unacceptable. Wearing them can also become a little uncomfortable after an hour or so.

Masking


There are a few electronic means of counteracting noise. The most simple method, but one that can be quite effective, is to use electronically generated sounds to mask the offending noise. At its most basic, this just entails using your own hi-fi system, television set or whatever to produce sounds that cover up the noise from your neighbours. In practice, this basic method tends to be unsatisfactory. One reason for this is that you may simply want to "put your brain into neutral" and relax without any background music or other distractions. Another

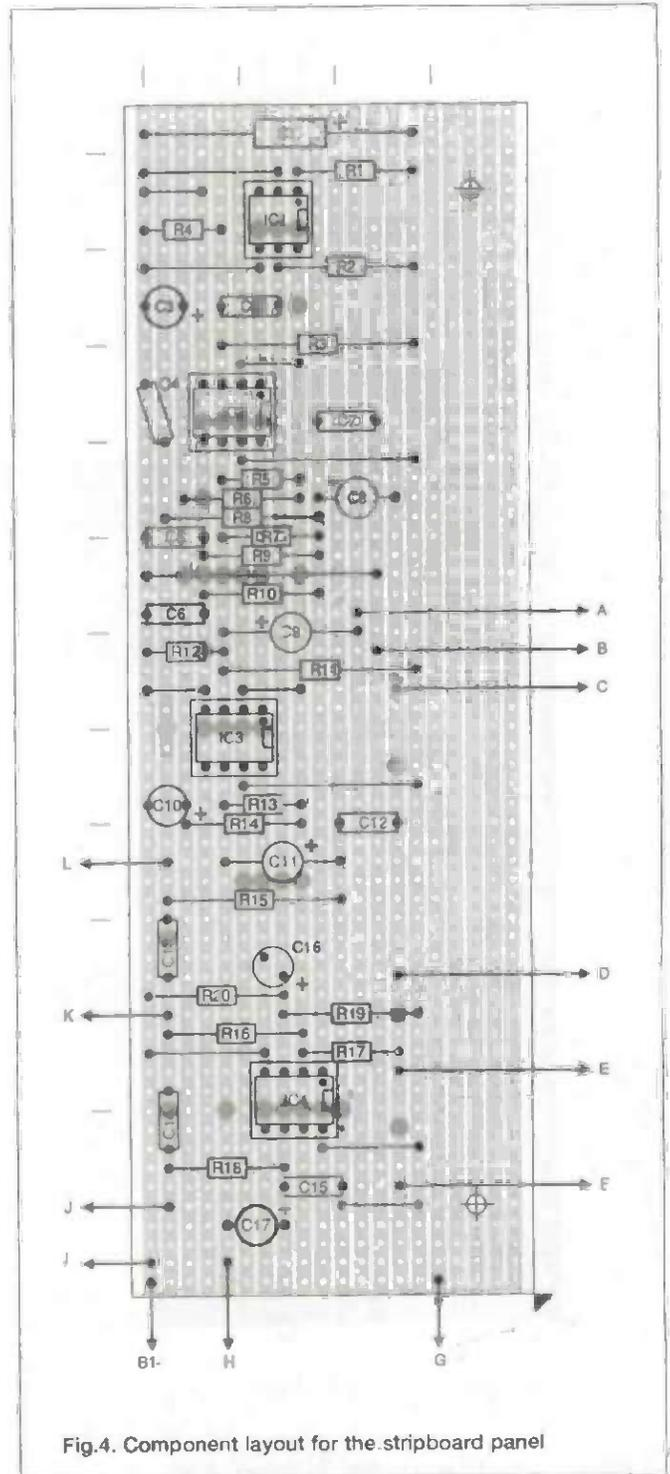

problem is that most programme sources are intermittent in nature and the noise from your neighbours during the quiet bits can be more irritating than continuous noise.

There is a third problem, which is simply that your sounds might not be good at masking the noise from your neighbours: Sounds tend to mask similar sounds very well, but are ineffective at blocking disparate sounds. It seems to be the frequency content that is of prime importance here. For instance, low frequency sounds are good at masking other low frequency sounds, but middle and high frequency sounds tend to stand out clearly above them.

There is an electronic solution to these problems in the form of a noise generator. "Hiss" type noise covers the full audio range and is therefore reasonably effective at masking any noise, regardless of its frequency content. It is continuous, with

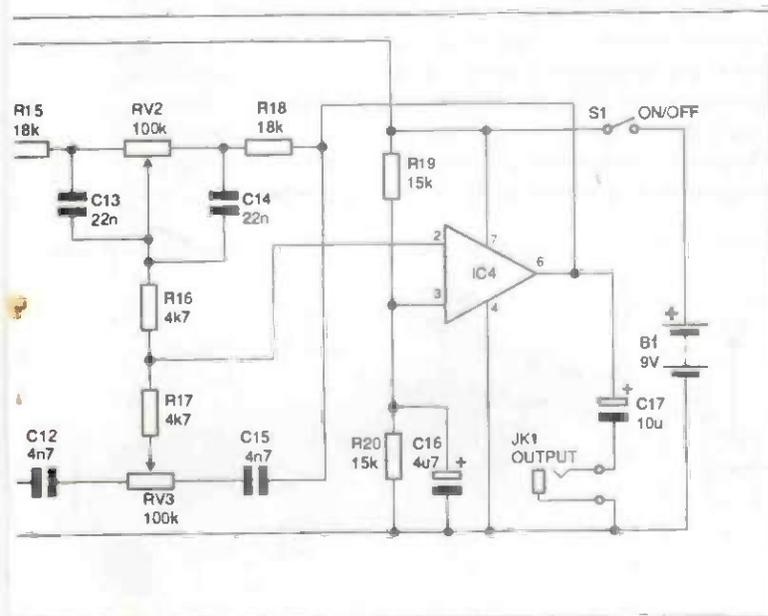

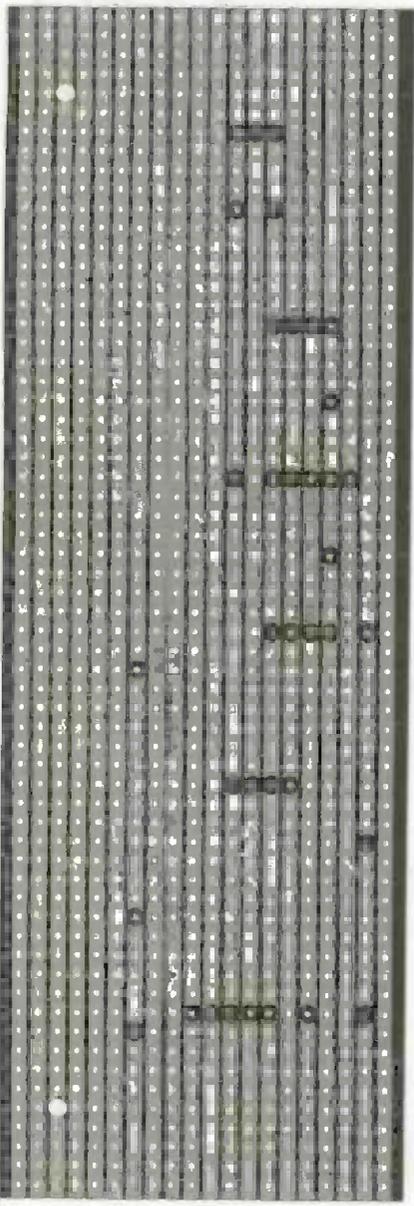


Fig.5. Underside view of the stripboard panel

no gaps for the neighbours' noise to sneak through. Most people do not find "hiss" type noise too distracting. In fact, it can be quite relaxing, particularly if a normal "white" noise source is filtered to provide so-called "pink" noise.

"Pink" noise gives what is still a "hiss" type sound, but with greatly reduced high frequency content. The sound of "pink" noise is generally perceived as being less aggressive than that of "white" noise and it is often likened to the sound of gentle rainfall. This is possibly the reason that many people find the sound of "pink" noise quite relaxing. Compared to "white" noise, the "pink" variety is less effective at masking high frequency sounds, due to its lower high frequency content. This is not normally of any major importance, since low frequency sounds travel better through walls and windows than high frequency sounds. In fact, it means that "pink" noise will usually be well matched to the noises that you are trying to mask.

The device featured here is a "pink" noise generator that has built-in tone controls which provide the usually bass and treble boost and cut. This enables the sound to be adjusted to give what is deemed to be the most relaxing effect and also enables, say, extra bass content to be produced if the offending noise is predominantly at low frequencies. The noise generator can directly drive earphones or headphones, or its output can be connected to a hi-fi system if loudspeaker operation is required.

How It Works

The block diagram of Fig.1 shows the general make-up of the noise masker. The first stage is the basic noise generator circuit, which produces a normal "white" noise signal. Generating electrical noise is not difficult, since it is produced by all electronic components. The problem in this case is generating a strong signal using components that are designed to produce as little noise as possible. Noise can be produced digitally, or using noise analogue components. After a few experiments with various noise sources, an opto-isolator was used as the basis of the noise generator in this circuit. This method is inexpensive and seems to provide consistently high noise levels. The noise output is still somewhat weaker than we require in this application, but a modest amount of amplification is all that is needed in order to bring the noise signal to a satisfactory level.

"White" noise contains all frequencies at equal levels. "Pink" noise also contains all frequencies, but there is the same signal level in any single octave band. For example, the noise is at the same level from 20Hz to 40Hz as it is from 20kHz to 40kHz. Clearly there is a much wider frequency span from 20kHz to 40kHz than there is from 20Hz to 40Hz, but there is only the same signal level in each band. In order to convert "white"


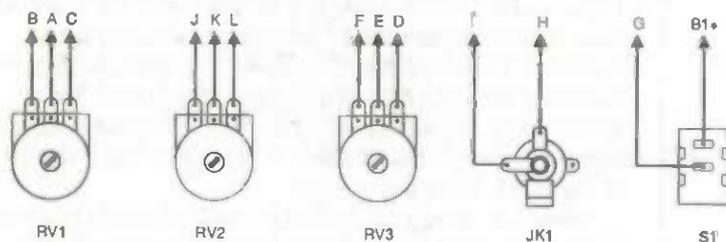


Fig.6. Details of the hard wiring

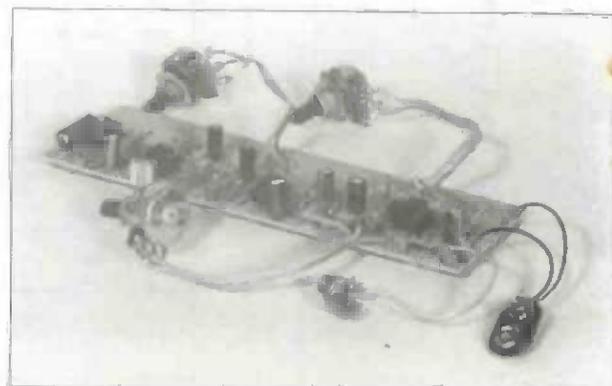

Resistors

- (0.25 watt 5% carbon film)
- R1,R2,R19,R20 15k (4 off)
- R3,R4 100k (2 off)
- R5,R13 47k (2 off)
- R6 470R
- R7,R8 6k8 (2 off)
- R9,R14 2k2 (2 off)
- R10 680R
- R11,R12 220k (2 off)
- R15,R18 18k (2 off)
- R16,R17 4k7 (2 off)

Potentiometers

- VR1 100k log carbon
- VR2,VR3 100k lin carbon (2 off)

Capacitors

- C1 100u 10V axial elect
- C2,C4 470n polyester (2 off)
- C3 22u 25V radial elect
- C5 150n polyester
- C6 68n polyester
- C7 33n polyester
- C8,C9 1u 50V radial elect (2 off)
- C10,C16 4u7 50V radial elect (2 off)
- C11 2u2 50V radial elect
- C12,C15 4n7 polyester (2 off)
- C13,C14 22n polyester (2 off)
- C17 10u 25V radial elect

Semiconductors

- IC1 4N27 or similar
- IC2 LF351N
- IC3,IC4 uA741C (2 off)

Miscellaneous

- S1 s.p.s.t. min toggle
- B1 9 volt (PP3 size)
- JK1 3.5mm jack socket

0.1 inch pitch stripboard having 62 holes by 20 copper strips, control knob (3 off), 6-pin DIL IC holder, 8-pin DIL IC holder (3 off), battery connector, case, wire, solder etc.

noise to "pink" noise it is merely necessary to use some low-pass filtering to provide a 3dB per octave roll-off right across the audio range. In this case, the lowpass filter is a passive type and it is therefore followed by an amplifier which compensates for the overall signal loss through the filter.

The "pink" noise signal is then processed by a standard bass and treble tone control circuit which, if necessary, enables the sound of the noise to be contoured. For example, if the noise to be masked is predominantly at low frequencies, some bass boost should enable it to be masked effectively without having to resort to very high volume levels. The tone control circuit is only needed if the noise generator will be used as a stand-alone unit driving earphones or headphones. If the unit is used in conjunction with a hi-fi amplifier, the tone control circuit is not really necessary, because the hi-fi system will presumably have either built-in tone controls or a graphic equaliser.

Fig.2 shows the full circuit diagram for the noise masker. IC1 is the opto-isolator used in the "white" noise generator. On the input side, R1 is used to provide a small current to the LED. On the output side, R2 acts as the collector load resistor for the transistor. No connection is made to the base terminal of the transistor (pin 6), but a collector current flows due to the leakage induced by the infra-red "light" from the LED. Although there is no obvious reason why this arrangement should provide a relatively high noise level, it is a fact that a normal opto-isolator is quite noisy and does produce plenty of noise when used in this way.

On the prototype, a 4N27 is used for IC1, but any "bog standard" opto-isolator (TIL111 etc) seems to provide similar results. However, the opto-isolator must be a type which has the standard 6 pin DIL encapsulation and pinout arrangement and it must also be a type which has a transistor at the output (not a Darlington pair, photo-diode plus a transistor, etc). High speed or otherwise "improved" devices might not work as well and would be more expensive, so it is better to use a low cost type.

IC2 is used as the basis of the first amplifier stage and this is a conventional non-inverting mode circuit. R5 and R6 are the negative feedback circuit and they set the closed-loop voltage gain of the circuit at about 100 times (40dB). R3 and R4 bias the non-inverting input of IC2 and set the input impedance of the amplifier at 50k.

The output of IC2 is direct coupled to the passive lowpass filter. The required roll-off rate of 3dB per octave is an awkward one, since the ultimate roll-off rate of a single pole C - R filter is double this at 6dB per octave. An approximation of a 3dB per octave roll-off is obtained by using a four stage filter with a resistor in series with all but one of the filter capacitors. The basic idea is that as the attenuation provided by one of the capacitors starts to go above 3dB per octave, its series resistor limits its effect and prevents the full 6dB per octave rate from being achieved.

Above a certain frequency, the series resistor prevents its capacitor from having any further effect, but the next resistor and capacitor in the filter then take over and continue to provide a roll-off at approximately 3dB per octave. C7 has no series resistor, but the fact that the attenuation rate reaches 6dB per octave at the frequencies above the audio range is of no practical significance. The filter only provides an approximation of a 3dB per octave roll-off, but its accuracy is perfectly adequate for the present application and quite a good "pink" noise sound is obtained.

The output from the lowpass filter is coupled to volume control VR1 and then to the second amplifier stage. This is another non-inverting circuit, this time based on IC3. R13 and R14 form the negative feedback network and they set the closed loop voltage gain of IC3 at about 22 times (22dB). The value of VR1 and the input impedance of the amplifier (110k) are made relatively high so that they do not place excessive loading on the lowpass filter.

IC4 is used as the basis of the active tone control circuit, which is a conventional inverting mode type. VR3 is the treble control and it operates in conjunction with C12 and C15 as a negative feedback network. The basic principle of operation is very straightforward and is dependent on the fact that C12 and C15 have a relatively low impedance at high audio frequencies. The closed loop voltage gain of the circuit is therefore largely controlled by the setting of VR3. With its wiper towards the C15 end of its track, the amount of negative feedback is large, and the voltage gain is less than unity. Taking the wiper to the

C12 end of the track gives a small amount of feedback and considerably more than unity gain. At middle and low frequencies, the impedance of C12 and C15 is large in relation to the value of VR3, effectively swamping it and giving approximately unity voltage gain at any setting. VR3 therefore controls the gain of IC4, but only at treble frequencies.

VR2 is the bass control and its operation is also dependent on the fact that two capacitors have a relatively low impedance at high audio frequencies. In this case, the capacitors are C13 and C14 and, at high audio frequencies, they effectively short circuit VR2, making its setting irrelevant. R15 and R18 form the negative feedback network and set the voltage gain of the circuit at unity. At bass frequencies, the impedance of C13 and C14 is high in relation to the track resistance of VR2 and VR2 can then exercise considerable control over the closed-loop gain of IC4. Taking VR2's wiper to the R15 end of the track gives increased gain - taking it to the R18 end of the track produces lower gain. R16 and R17 form a simple mixer which integrates the two tone controls and ensures minimal interaction between them.

The tone controls provide up to about 15dB of boost and cut at the extremes of the audio range, or around 12dB at most frequencies within their respective frequency bands. Fig.3 shows the approximate frequency responses of the tone controls in the prototype noise masker. The upper response is with both controls set for maximum boost and the lower response is with them both set for maximum cut.

The current consumption of the circuit is about 4 milliamps and the unit can therefore be powered from a small (PP3 size) 9 volt battery. However, if it is likely to be used for long periods of time, it would be more economical to use a higher capacity battery, such as six HP7 size cells in a holder.

Construction

Figs.4 and 5 respectively show the component layout and underside view of the stripboard component panel. This has 62 holes by 20 strips and it can conveniently be a piece cut from a standard 160 x 100mm board. Start by drilling the two 3.3mm diameter mounting holes and then make the 37 breaks in the copper strips. These can be made using the special tool or a hand-held twist drill bit of about 4.5 to 5mm in diameter. Make sure that all the breaks cover the full width of the board, but do not cut so deeply into the board that it becomes seriously weakened.

Next, the components are added, working methodically across the board. Although none of the integrated circuits are MOS types, it is still a good idea to fit them in holders. A six-pin holder for IC1 might be difficult to obtain, but they are available from some component retailers. Alternatively, it is not difficult to trim an eight-pin holder down to size. The non-electrolytic capacitors will fit neatly into this component layout provided they are miniature printed circuit mounting types having 7.5mm (0.3 inch) lead spacing. Fitting other types of capacitor into this layout would almost certainly be problematic.

Do not overlook any of the link wires (there are a dozen in all). These are made from 22 or 24 swg tinned copper wire. At this stage, only fit single-sided solder pins to the board at the places where connections to the potentiometers etc will eventually be made. Tin the tops of the pins with a liberal amount of solder.

Practically any medium sized plastic or metal case should accommodate this project. The circuit is fairly sensitive to stray pick up of electrical noise, particularly mains "hum" when a large amount of bass boost is used. This gives some advantage in using an all-metal case earthed to the negative supply rail, as this will help to screen to circuit against sources of interference. The general layout of the unit is not critical, but avoid having long connecting wires from the circuit board to the potentiometers and the output socket. The board is bolted in place using 6BA or metric M3 fixings, including spacers to hold the underside of the board a little way off the base panel of the case.


The hard wiring is shown in Fig.6, which should be used in conjunction with Fig.4. This wiring is very straightforward and should present no difficulties. JK1 is a 3.5mm jack socket on the prototype, but this can obviously be changed for a standard jack, phono socket, or any other type of socket that suits your particular setup.

In use

The output level from JK1 is typically about one volt peak-to-peak, which should be ample to drive most hi-fi amplifiers. Simply connect JK1 of the noise generator to a spare high level input of the amplifier via a screened lead. Quite good results are obtained if the output of the unit is used to drive a pair of crystal earphones. These seem to provide an earplug action, giving two lines of defence against the offending noise. Another 3.5mm jack socket must be added in parallel with JK1 in order to accommodate two earphones.

Headphones of the type sold as replacements for use with personal stereo units also work well but, due to their relatively low impedance, C17 must be replaced with a 220u 10 volt capacitor. Otherwise, there will be a very noticeable lack of low frequency output from the headphones. JK1 must be replaced with a stereo 3.5mm jack socket and it should be wired so that the two phones are connected in series (ignore the earth tag and connect the other two tags to the circuit board). The output of the unit is inadequate to drive most other types of headphone or low impedance dynamic earphones properly.

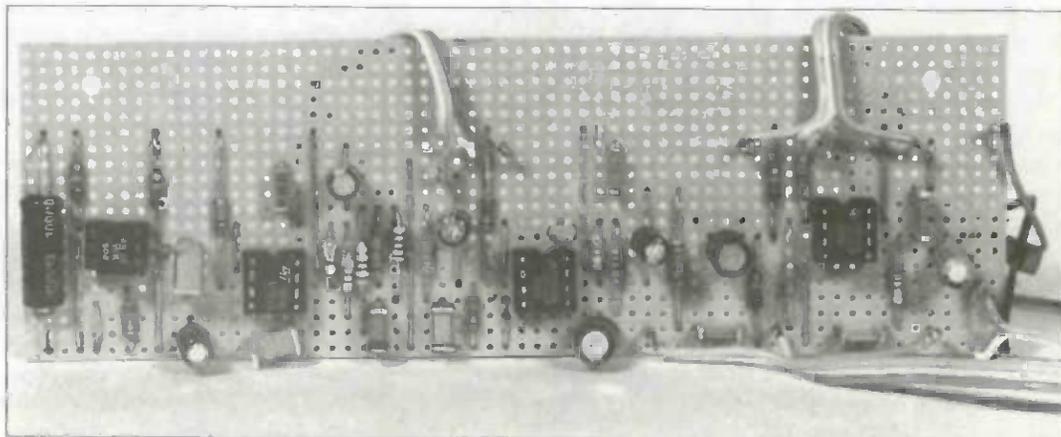Noise masking is not a viable way of tackling high noise levels, but it seems very effective at rendering unwanted background noise innocuous. It also seems to work well with a wide range of sounds, including hi-fi systems and burglar alarms.



POWER AMPLIFIER MODULES-TURNABLES-DIMMERS-LOUDSPEAKERS-19 INCH STEREO RACK AMPLIFIERS

19 INCH STEREO RACK AMPLIFIERS • PROMPT DELIVERIES • FRIENDLY SERVICE • LARGE (A4) S.A.E. 80p STAMPED FOR CATALOGUE

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS
FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)
MXF600 (300W + 300W) MXF900 (450W + 450W)
ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: ★Independent power supplies with two toroidal transformers ★ Twin L.E.D. Vu meters ★ Level controls ★ illuminated on/off switch ★ XLR connectors ★ Standard 775mV inputs ★ Open and short circuit proof ★ Latest Mos-Fets for stress free power delivery into virtually any load ★ High slew rate ★ Very low distortion ★ Aluminium cases ★ MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"
 MXF400 W19" x H5 1/4" (3U) x D12"
 MXF600 W19" x H5 1/4" (3U) x D13"
 MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85
 MXF600 £329.00 MXF900 £449.15
 SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER



Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1,8/3.5/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV Input/Output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE ★ ECHO & SOUND EFFECTS★

STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED Vu meters. **MANY OUTSTANDING FEATURES:-** Including Echo with repeat & speed control, DJ Mic with talk-over switch, 8 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mic, 5 Line for CD, Tape, Video etc.



SIZE: 482 x 240 x 120mm

Price £144.99 + £5.00 P&P

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piero revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). **FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.**

- TYPE 'A'** (K5N1038A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.
 - TYPE 'B'** (K5N1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.
 - TYPE 'C'** (K5N1016A) 2"x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.
 - TYPE 'D'** (K5N1025A) 2"x6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.
 - TYPE 'E'** (K5N1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.
- LEVEL CONTROL** Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminum loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminum corner protection and steel ball corners, complemented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.



POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz

IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR
IBI FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR

OPTIONAL STANDS PRICE PER PAIR £49.00
 Delivery £5.00 per pair

IN-CAR STEREO BOOSTER AMPS




PRICES: 150W £49.99 250W £99.99
400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS
 150 WATTS (75 + 75) Stereo, 150W Bridged Mono
 250 WATTS (125 + 125) Stereo, 250W Bridged Mono
 400 WATTS (200 + 200) Stereo, 400W Bridged Mono
ALL POWERS INTO 4 OHMS
Features:
 ★ Stereo, bridgable mono ★ Choice of high & low level inputs ★ L & R level controls ★ Remote on-off ★ Speaker & thermal protection

OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

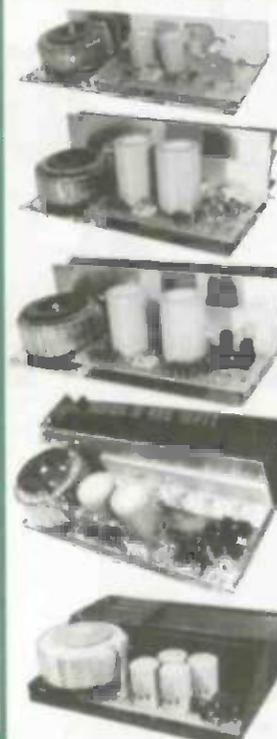THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts
 R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
 -3dB, Damping Factor >300, Slew Rate 45V/uS,
 T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R.
 -110 dB. Size 300 x 123 x 60mm.
PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts
 R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
 -3dB, Damping Factor >300, Slew Rate 50V/uS,
 T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
 -110 dB. Size 300 x 155 x 100mm.
PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts
 R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
 -3dB, Damping Factor >300, Slew Rate 60V/uS,
 T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
 -110 dB. Size 330 x 175 x 100mm.
PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts
 R.M.S. into 4 ohms, frequency response 1Hz - 100KHz
 -3dB, Damping Factor >300, Slew Rate 75V/uS,
 T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R.
 -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2
 Second Anti-Thump Delay. Size 385 x 210 x 105mm.
PRICE £132.85 + £6.00 P&P

OMP/MF 1000 Mos-Fet Output power 1000 watts
 R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms,
 frequency response 1Hz - 100KHz -3dB, Damping
 Factor >300, Slew Rate 75V/uS, T.H.D. typical
 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan
 Cooled, D.C. Loudspeaker Protection, 2 Second
 Anti-Thump Delay. Size 422 x 300 x 125mm.
PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS:
 STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz.
 PE2 (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS
 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PE2.

LOUDSPEAKERS



LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.

McKenzie and Fane Loudspeakers are also available.

EMINENCE:- INSTRUMENTS, P.A., DISCO, ETC

- ALL EMINENCE UNITS 8 OHMS IMPEDANCE**
- 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P
 - RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, SENS 97dB.
 - 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P
 - RES. FREQ. 71Hz, FREQ. RESP. TO 7KHz, SENS 97dB.
 - 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYBD, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P
 - RES. FREQ. 65Hz, FREQ. RESP. TO 3.5KHz, SENS 99dB.
 - 12" 100 WATT R.M.S. ME12-100LE GEN. PURPOSE, LEAD GUITAR, DISCO, STAGE MONITOR. PRICE £35.84 + £3.50 P&P
 - RES. FREQ. 49Hz, FREQ. RESP. TO 6KHz, SENS 100dB.
 - 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £36.87 + £3.50 P&P
 - 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £48.71 + £3.50 P&P
 - RES. FREQ. 58Hz, FREQ. RESP. TO 4KHz, SENS 99dB.
 - 12" 300 WATT R.M.S. ME12-300GF HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £70.19 + £3.50 P&P
 - 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P
 - RES. FREQ. 46Hz, FREQ. RESP. TO 3KHz, SENS 99dB.
 - 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P
 - RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

- ALL EARBENDER UNITS 8 OHMS (Except EB150 & EB100 which are dual impedance tapped @ 4 & 8 ohms)**
- BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 8" 50watt EB8-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.
 - 10" 50WATT EB10-50 DUAL IMPEDANCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.
 - 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.
 - 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P
 - RES. FREQ. 26Hz, FREQ. RESP. TO 3KHz, SENS 93dB.
 - FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND**
 5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P
 - RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.
 - 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P
 - RES. FREQ. 36Hz, FREQ. RESP. TO 20KHz, SENS 94dB.
 - 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P
 - RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 93dB.
 - 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P
 - RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 2 1/2 x 123mm SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 106-108MHz VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC. RANGE 100-100m, SIZE 56 x 46mm SUPPLY 9V BATTERY. PRICE £8.99 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA,

ESSEX, SS2 6TR


Tel. 01702 - 527572 Fax: 01702-420243

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.

bicycle ALARM

Worried about having your bike stolen? Then Simon Brown's cycle alarm may be the solution to your worries.

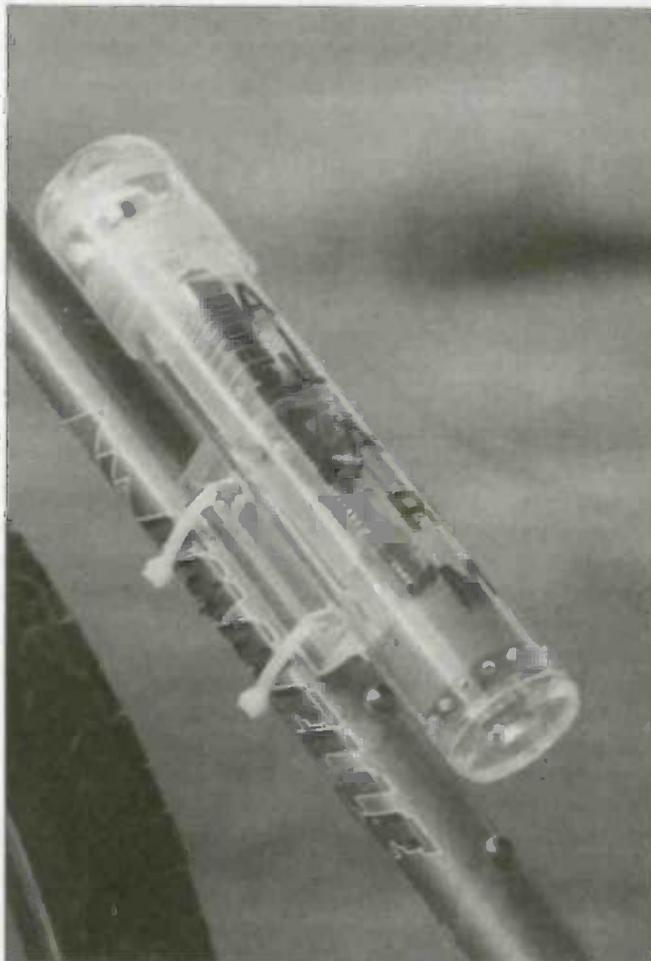It is a sad fact of life that crime is on the increase, in particular theft. The cycle alarm is an elegant electronic solution that helps protect your cycle from theft. This easily constructed alarm can also protect other items that attract casual theft, unattended suit-cases for example.



The alarm works by recording the position of any item to which it is attached and monitoring it for change. Should change be detected, then a piezo sounder will emit an ear-piercing sound. This principle was designed to protect cycles that are often parked in various positions, from horizontal to vertical. The position is recorded by the electronic alarm as the normal position and then distinguished from any other position that would indicate unwanted attention. This is achieved by the use of four mercury tilt switches configured into what I believe to be a unique electronic solution to movement detection. The four tilt switches are mounted at different angles so whatever position the cycle is left, some switches will be closed and some will be open, or all the switches closed or all the switches open.

The state of each individual switch is recorded in an electronic memory circuit and then constantly monitored for a change of state which would indicate that the cycle was receiving unwanted attention. Any change of state in the switch pattern will result in the alarm being sounded. In this way, the cycle could be parked at any desired angle prior to setting the alarm and locking the switch pattern into memory. Once the alarm has been set, any change in the switch pattern will result in the alarm being activated. Setting is achieved by a simple key switch operation and a flashing LED indicates that the unit is armed.

Electronic circuitry

At the heart of the electronic system is an array of mercury tilt switches. These consist of two contacts which are mounted in a sealed tube along with a small quantity of mercury. If the tube is held vertically, the mercury will run to the bottom and bridge the gap between the contacts, thus completing an electrical circuit. If the tube is inverted, or even laid horizontally, the mercury will run away from the contacts and open the electrical circuit.

To make the alarm sensitive, four of these switches were used and mounted at different angles. No matter how the bicycle is parked, either all the switches will be open circuit, all closed circuit or a mixture of some open circuit and some closed circuit. This pattern needs to be memorised when the alarm is activated, and then monitored; should it change the


alarm needs to be sounded.

The circuitry is constructed from CMOS logic. CMOS was chosen because it works over a very wide range of supply voltages and uses zero power when the signal inputs are not changing and very little when they are, making it ideal for battery operation. The four mercury tilt switches are connected between the D input and ground of four D type latches (IC2). The D input is also pulled up to Vcc via a 6k8 resistor. In this way, if the switch is closed, a logic 0 is presented to the D input and, if the Switch is open, a logic 1 is presented to the D input. This logic state is stored by the latch when commanded by the (clock) input.


This input is activated by a transition of a logic 0 changing to a logic 1 (pulse). This pulse is generated at switch on by the reset generator.

The reset generator is constructed from two logic gates - a single capacitor and a resistor. When the alarm is switched on, the capacitor is in a discharged state and soon charges via the resistor (electrolytic capacitors are very poor at holding a charge in the absence of power). The values shown take about one second for the capacitor to charge - the resulting waveform can best be described as a ramp. This ramp is converted into a pulse and inverted by the first logic gate (inverter) and further sharpened by the second logic gate and inverted back to the same direction as the ramp only with sharp edges. The CMOS inverters will ignore the ramp until it reaches half the supply rail and then they will change state very quickly. Thus, the reset command is generated about one second after the alarm is switched on and the tilt switch states are then locked into the D latches.

The latched logic and the logic produced by the tilt switches is then monitored for change in IC3 (magnitude comparator). This chip has eight inputs arranged as four A inputs and four B inputs. It can compare them and detect if they are equal or not. The chip is designed to compare two four bit binary numbers and indicate if A is greater than B, if B is greater than A or if they are equal; hence its name, magnitude comparator. The A greater than B and B greater than A outputs are not used in this design. The A=B output connects pin 3 A=B input to A=B output when A=B. This should always be the state if

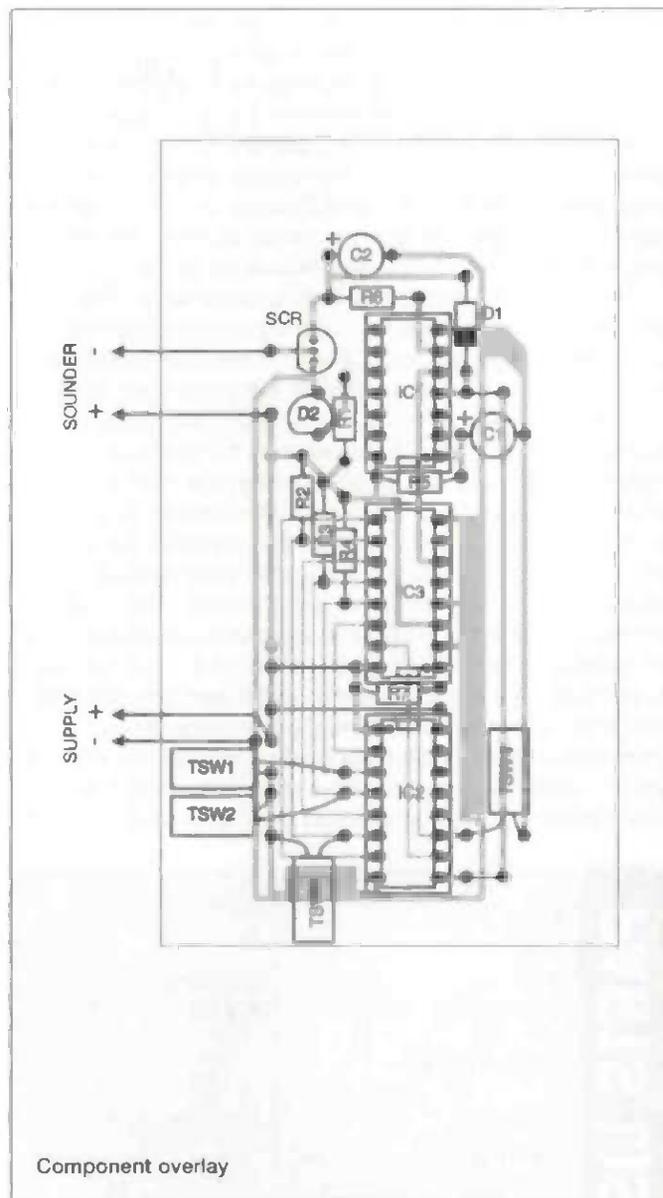

Component overlay

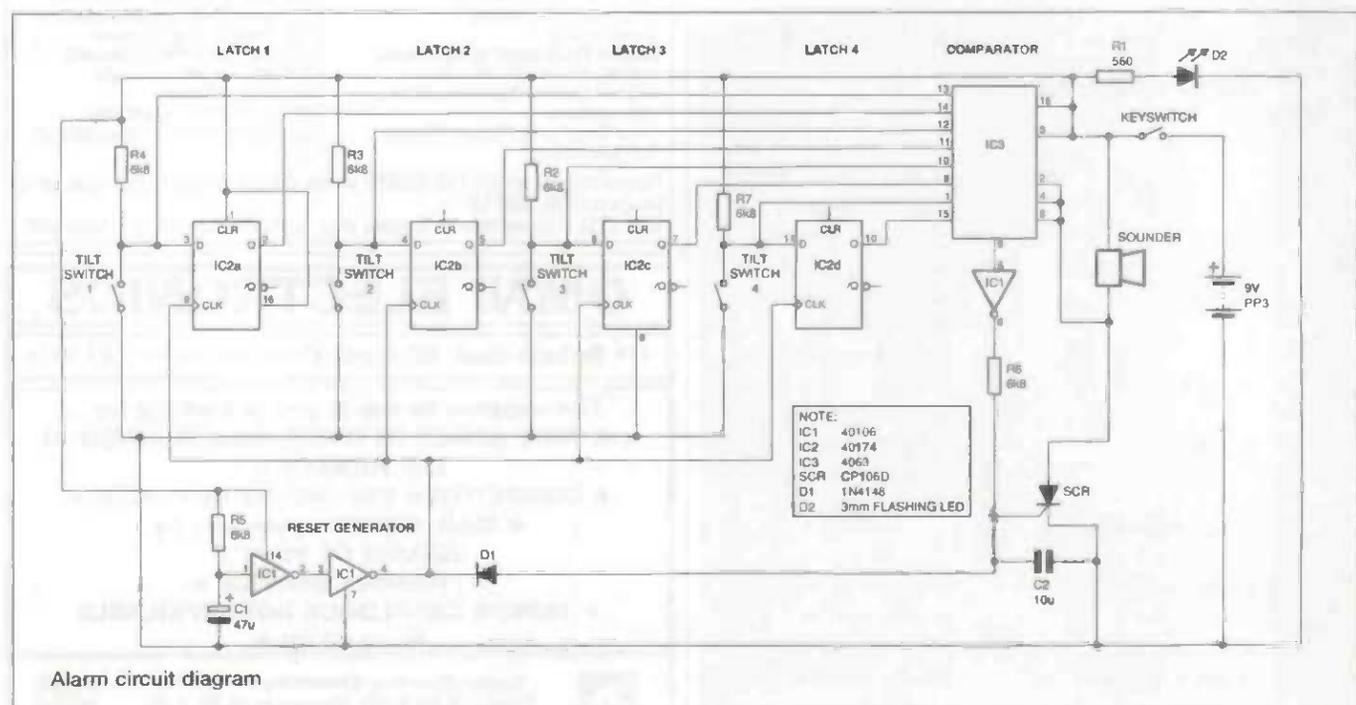

Alarm circuit diagram

the alarm has been set, the latches loaded with the switch pattern and the bicycle not moved. If the bicycle is moved, then the switch pattern will change and not equal the pattern latched in the D types. A will not equal B on the magnitude comparator and a logic 0 will be presented for our circuit configuration i.e. pin 3 at Vcc. This logic is inverted by the Logic gate and will turn on the SCR which will sink current and develop a potential difference across the sounder. This will produce a high pitched 103 dB (decibels) of sound.

The SCR was necessary so as to latch the alarm. The alternative would have been a switching transistor, but this would enable the alarm to be silenced if the cycle was moved to such a position that the original switch pattern was restored. Once the SCR is switched on by the logic, it will function as a transistor and sound the alarm, but it will not switch off, no matter what logic state is presented to its gate, even if the original switch pattern is restored. D1 is necessary to stop the SCR from being activated when the alarm is switched on, because the switch pattern is not latched until the reset pulse. During this time, the D types are set to random states that may or may not match the switches so the alarm would sound until C1 charges and latches the switch pattern. D1 stops the input to the SCR going to Logic 1 until the reset pulse has occurred. This is because it conducts when the reset generator is producing a logic 0, and therefore stops the SCR gate going to logic 1, when the reset generator is producing a logic 1 (i.e. after the latches have been loaded D1 is biased to open circuit).

C2 delays this pulse because the D latches and the magnitude comparator response is not instant. This is called propagation delay and is very small and is measured in nanoseconds

Construction

The ICs were installed using sockets but this is not necessary. The switches are wire-mounted devices that can be bent into their final position. It is important that all the positions are different to get the best performance out of the alarm - some experimenting with the final positions is inevitable. Any flux left on the PCB after soldering in the components should be cleaned off with flux remover as CMOS logic works at very high impedances and can easily be upset by any residue on the PCB. The on/off switch was the key operated kind for obvious reasons as the alarm would be less than useless if an ordinary toggle switch was used, enabling the thief to disarm the alarm

Battery life

This depends upon a number of things; in particular, how often the alarm is sounded and the quality of battery used. If long periods of duty are required, use an Alkaline battery. The battery life can be extended by omitting the LED. Further battery economies can also be made by increasing the value of the tilt switch pullup resistors R2, R3, R4, and R7. Values approaching 100k should still provide a logic 1 when the tilt switch is open

Case

The case is down to individual choice. The prototype was housed in transparent acrylic tube with a pair of suitable engineered end caps. The unit was then fixed to the cycle with tie wraps. But there are numerous other solutions.

PARTS LIST

Resistors

- R1 560ohms
- R2 TO R7 6K8 ohms

Capacitors

- C1 47Mfd radial electrolytic (MAPLIN FF083)
- C2 10 Mfd radial electrolytic (MAPLIN FFO4E)

Semiconductors

- IC1 40106 HEX INVERTER WITH SCHMITT INPUT (MAPLIN QW46U)
- IC2 40174 HEX D LATCH (MAPLIN QW46U)
- IC3 4063 MAGNITUDE COMPARATOR (MAPLIN QW41U)
- SCR CP106D (MAPLIN UM74R)
- L.E.D. FLASHING 3mm (MAPLIN UK33L)

Miscellaneous

- SW1 to SW4 miniature tilt switches (Maplin FE11N)
- Battery clip to suit PP3 (Maplin HF28F)
- Piezo sounder (Maplin UM47R)
- Key switch (Maplin FE44X)

EQT LTD STEVENAGE

Professional Sub-Contract Manufacturing & Suppliers to the Electronics Industry

Do you have a requirement for any of the following services:

- | | |
|---|--------------------------------------|
| PCB Assembly (Conventional and Surface Mount) | Product Design/Consultation |
| Wave & Hand Soldering | Full Procurement Service |
| Complete Equipment Manufacture | PCB Test & "Burn in" Facilities |
| Device Programming from hand written sheets or PC 3 1/2" disc | Enclosure Design & Manufacture |
| Cable Harness Assembly/loom Manufacture | PCB Artwork Manufacture |
| Card Cage and Module Wiring | Circuits Drawn Professionally |
| Full Inspection | Kit Procurement & Supply |
| | Component Sales |
| | Refurbishment a speciality |
| | Top Quality Work at Reasonable Rates |

Phone Angela on (01438) 360406 or fax details of your requirements to us on (01438) 352742

EQT LTD, Cromer House, Caxton way, STEVENAGE, HERTS, SG1 2DF

OMNI ELECTRONICS

174 Dalkeith Road, Edinburgh EH16 5DX • 0131 667 2611

The supplier to use if you're looking for -
★ A WIDE RANGE OF COMPONENTS AIMED AT THE HOBBYIST ★

★ COMPETITIVE VAT INCLUSIVE PRICES ★

★ MAIL ORDER - generally by RETURN OF POST ★

★ FRIENDLY SERVICE ★

★ 1995/96 CATALOGUE NOW AVAILABLE

Price £2.00 ★



Open: Monday-Thursday 9.15-6.00
Friday 9.15-5.00 Saturday 9.30-5.00



Surplus always wanted for cash!

THE ORIGINAL SURPLUS WONDERLAND!

THIS MONTH'S SELECTION FROM OUR VAST EVER CHANGING STOCKS

Surplus always wanted for cash!

LOW COST PC's - ALL EXPANDABLE - ALL PC COMPATIBLE

SPECIAL BUY

AT 286

40Mb HD + 3Mb Ram



LIMITED QUANTITY only of these 12MHz HI GRADE 286 systems Made in the USA to an industrial specification, the system was designed for total reliability. The compact case houses the motherboard, PSU and EGA video card with single 5 1/4" 1.2 Mb floppy disk drive & Integral 40Mb hard disk drive to the front. Real time clock with battery backup is provided as standard. Supplied in good used condition complete with enhanced keyboard, 640k x 2Mb RAM, DOS 4.01 and 90 DAY Full Guarantee. Ready to Run!

ONLY £149.00 (E)

CALL FOR QTY DISCOUNTS

Optional Fitted extras: VGA graphics card	£29.00
1.4Mb 3 1/4" floppy disk drive (instead of 1.2 Mb)	£24.95
NE2000 Ethernet (thick, thin or twisted) network card	£49.00

PC SCOOP COMPLETE COLOUR SYSTEM ONLY £99.00



A massive bulk purchase enables us to bring you a COMPLETE ready to run colour PC system at an unheard of price! The Display Electronics PC99 system comprises of fully compatible and expandable XT PC with 256k of RAM, 5 1/4" 360k floppy disk drive, 12" CGA colour monitor, standard 84 key keyboard, MS DOS and all connecting cables - just plug in and go! Ideal students, schools or anybody wishing to learn the world of PC's on an ultra low budget. Don't miss this opportunity. Fully guaranteed for 90 Days.

Order as PC99COL £99.00 (E)

Optional Fitted extras: 640k RAM	£29.00
2nd floppy drive, specify 5 1/4" 360k or 3 1/2" 720k	£29.95
Above prices for PC99 offer ONLY.	

19" RACK CABINETS

Superb quality 6 foot 40U Virtually New, Ultra Smart Less than Half Price!



Top quality 19" rack cabinets made in UK by Optima Enclosures Ltd. Units feature designer, smoked acrylic lockable front door, full height lockable half louvered back door and removable side panels. Fully adjustable internal fixing struts, ready punched for any configuration of equipment mounting plus ready mounted integral 12 way 13 amp socket switched mains distribution strip make these racks some of the most versatile we have

over sold. Racks may be stacked side by side and therefore require only two side panels to stand singly or in bays.

Overall dimensions are: 77 1/2" H x 32 1/2" D x 22" W. Order as:
OPT Rack 1 Complete with removable side panels. £335.00 (G)
OPT Rack 2 Rack, Less side panels £225.00 (G)

32U - High Quality - All steel cabinet

Made by Eurocraft Enclosures Ltd to the highest possible spec, rack features all steel construction with removable side, front and back doors. Front and back doors are hinged for easy access and all are lockable with five secure 5 lever barrel locks. The front door is constructed of double walled steel with a 'designer styre' smoked acrylic front panel to enable status indicators to be seen through the panel yet remain unobtrusive. Internally the rack features fully slotted reinforced vertical fixing members to take the heaviest of 19" rack equipment. The two movable vertical fixing struts (extras available) are pre-punched for standard 'cage-nuts'. A mains distribution panel internally mounted to the bottom rear, provides 9 IEC 3 pin Euro sockets and 1 x 13 amp 3 pin switched utility socket. Overall ventilation is provided by fully louvered back door and double skinned top section with top and side louvres. The top panel may be removed for fitting of integral fans to the sub plate etc. Other features include: fitted castors and floor levelers, pre-punched utility panel at lower rear for cable / connector access etc. Supplied in excellent, slightly used condition with keys. Colour Royal blue. External dimensions 64" H x 25" D x 23 3/4" W.



Sold at LESS than a third of makers price !!

A superb buy at only £195.00 (G)
Over 1000 racks in all sizes 19" 22" & 24" 3 to 44 U. Available from stock !!
Call with your requirements.

FLOPPY DISK DRIVES 3 1/2" - 8"

5 1/4" from £22.95 - 3 1/2" from £24.95

Massive purchases of standard 5 1/4" and 3 1/2" drives enables us to present prime product at industry beating low prices! All units (unless stated) are BRAND NEW or removed from often brand new equipment and are fully tested, aligned and shipped to you with a 90 day guarantee and operate from standard voltages and are of standard size. All are IBM-PC compatible (1 3/4" supported on your PC).

3 1/2" Panasonic JU363/4 720K or equivalent	£24.95(B)
3 1/2" Mitsubishi MF355C-L 1.4 Meg. Laptops only*	£36.95(B)
3 1/2" Mitsubishi MF355C-D 1.4 Meg. Non laptop	£29.95(B)
5 1/4" Teac FD-55GR 1.2 Meg	£29.95(B)
5 1/4" BRAND NEW Mitsubishi MF501B 360K	£22.95(B)

* Data cable included in price	
Shugart 800/801 B" SS refurbished & tested	£195.00(E)
Shugart 851 B" double sided refurbished & tested	£250.00(E)
Mitsubishi M2894-63 B" double sided NEW	£275.00(E)
Mitsubishi M2896-63 02U B" DS slimline NEW	£285.00(E)

Dual 8" drives with 2 mbyte capacity housed in a smart case with built in power supply. Ideal as exterior drives! £499.00(F)

HARD DISK DRIVES

End of line purchase scoop! Brand new NEC D2246 8" 85 Mbyte of hard disk storage! Full Industry standard SMD interface. Ultra hi speed data transfer and access time, replaces Fujitsu equivalent model. Complete with manual. Only £299.00(E)

3 1/2" FUJII FK-309-26 20mb MFH I/F RFE	£59.95(C)
3 1/2" CONNER CP3024 20 mb IDE I/F (or equiv.) RFE	£69.95(C)
3 1/2" CONNER CP3044 40mb IDE I/F (or equiv.) RFE	£89.00(C)
3 1/2" RODIME RQ3057S 45mb SCSI I/F (Mac & Acorn)	£99.00(C)
5 1/4" MINISCRIBE 3425 20mb MFH I/F (or equiv.) RFE	£49.95(C)
5 1/4" SEAGATE ST-238R 30 mb MH I/F Refurb	£69.95(C)
5 1/4" CDC 94205-51 40mb HB RFL I/F RFE tested	£69.95(C)
8" FUJITSU M2322K 160Mb SMD I/F RFE tested	£195.00(E)

Hard disc controllers for MFH, IDE, SCSI, RLL etc. from £16.95

THE AMAZING TELEBOX

Converts your colour monitor into a QUALITY COLOUR TV!!

TV SOUND & VIDEO TUNER!

The TELEBOX consists of an attractive fully cased mains powered unit, containing all electronics ready to plug into a host of video monitors made by makers such as MICROVITEC, ATARI, SANYO, SONY, COMMODORE, PHILIPS, TATUNG, AMSTRAD etc. The composite video output will also plug directly into most video recorders, allowing reception of TV channels not normally receivable on most television receivers* (TELEBOX MB). Push button controls on the front panel allow reception of 8 fully tuneable 'off air' UHF colour television channels. TELEBOX MB covers virtually all television frequencies VHF and UHF including the HYPERBAND as used by most cable TV operators. A composite video output is located on the rear panel for direct connection to most makes of monitor or desktop video systems. For complete compatibility - even for monitors without sound - an integral 4 watt audio amplifier and low level Hi FI audio output are provided as standard.

TELEBOX ST for composite video input type monitors	£34.95
TELEBOX STL as ST but with integral speaker	£37.50
TELEBOX MB Multiband VHF-UHF-Cable. Hyperband tuner	£69.95

*For overseas PAL versions state 5, 6 or 6mhz sound specification, *For cable / hyperband reception Telebox MB should be connected to cable type service. Shipping code on all Teleboxes is (B)

FANS & BLOWERS

MITSUBISHI MMF-D612DL 60 x 25 mm 12v DC	£4.95 10 / £42
MITSUBISHI MMF-09B12DH 92 x 25 mm 12v DC	£5.95 10 / £53
PANCAKE 12-3.5 92 x 18 mm 12v DC	£7.95 10 / £69
EX-EQUIP 120 x 38mm AC fans - tested specifiy 110 or 240 v	£6.95
EX-EQUIP 80 x 38mm AC fans - tested specifiy 110 or 240 v	£5.95
VERO rack mount 1U x 19" fan tray specifiy 110 or 240v	£45.95
IMHOF B26 1900 rack mnt 3U x 19" Blower 110/240v NEW	£79.95

Shipping on all fans (A). Blowers (B). 50,000 Fans Ex Stock CALL

IC's - TRANSISTORS - DIODES

OBsolete - SHORT SUPPLY - BULK

5,000,000 items EX STOCK

For MAJOR SAVINGS - SAE or CALL FOR LATEST LIST

VIDEO MONITOR SPECIALS

One of the highest specification monitors you will ever see - At this price - Don't miss it!!

Mitsubishi FA3415ETKL 14" SVGA Multisync monitor with fine 0.28 dot pitch tube and guaranteed resolution of 1024 x 768. A variety of inputs allows connection to a host of computers including IBM PC's in CGA, EGA, VGA & SVGA modes, BBC, COMMODORE (including Amiga 1200), ARCHIMEDES and APPLE. Many features: Etched faceplate, text switching and LOW RADIATION MPH specification. Full 90 day warranty.

Supplied in EXCELLENT like used condition. Only £139 (E)

Order as MITS-SVGA £139 (E)
Tilt & Swivel Base £8.00 Leads for IBM PC £8.95 (A)
External Cables for other computers £ CALL

PHILIPS HCS35 (same style as CM8833) attractively styled 14" colour monitor with both RGB and standard composite 15.625 KHz video inputs via SCART socket and separate phono jacks. Integral audio power amp and speaker for all audio visual uses. Will connect direct to Amiga and Atari BBC computers. Ideal for all monitoring / security applications with direct connection to most colour cameras. High quality with many features such as front concealed fan controls, VCR correction button etc. Good used condition - fully tested with a 90 day guarantee. Dimensions: W14" x H12 1/4" x 15 1/2" D. Only £99 (E)

Special Offer save £16.95 - Order TELEBOX ST & HCS35 together - giving you a quality colour TV & AV system for Only £122.50 (E)

KME 10" high definition colour monitors. Nice light 0.28" dot pitch for superb clarity and modern styling. Operates from any 15.625 KHz sync RGB video source, with RGB analog and composite sync such as Atari, Commodore Amiga, Acorn Archimedes & BBC. Measures only 13 1/2" x 12" x 11". Only £125 (E). Good used condition, 90 day guarantee. KME 10" as above for PC EGA standard £145.00 (E)

PHILIPS HCS31 Ultra compact 9" colour video monitor with standard composite 15.625 KHz video input via SCART socket. Ideal for all monitoring / security applications. High quality, ex-equipment fully tested with a 90 day guarantee (possible minor screen burns). In attractive square black plastic case measuring W10" x H10" x 13 1/2" D. Mains powered. Limited Quantity - Only £79.00 (D)

20" 22" and 26" AV SPECIALS

Superbly made UK manufacture. PIL all solid state colour monitors, complete with composite video & optional sound inputs. Attractive leak style case. Perfect for Schools, Shops, Disco, Clubs, etc. In EXCELLENT like used condition with full 90 day guarantee.

20"....£135 22"....£155 26"....£185(F)

DC POWER SUPPLIES

Virtually every type of power supply you can imagine. Over 10,000 Power Supplies Ex Stock Call for info / list.

SPECIAL INTEREST

Zeta 3220-05 A0 4 pen HPGL R5232 (ast drum plotter	£1950
3M VDA - Video Distribution Amps. 1 in 32 out	£375
Trio 0-18 vdc bench PSU. 30.0amps New	£470
Fujitsu M3041 600 LPM band printer	£1950
VG Electronics 1035 TELETEXT Decoding Margin Meter	£3750
Andrews LARGE 3.1 m Satellite Dish + mount (For Voyager)	£950
RED TOP IR Heat seeking missile (not armed !!)	POA
KNS EMC / Line Interference tester NEW	£1200
Thurley LA 180B logic analyser	£375
INTEL 58C 486/1335E Multibus 486 system 8Mb Ram	£1200
GEC 15kw 115v 60hz power source	£950
Brush 2Kw 400 Hz 3 phase frequency converter	£850
Anton Piller 75 Kw 400 Hz 3 phase frequency converter	POA
Newton Derby 70 KW 400 Hz 3 phase frequency converter	POA
COMPONEDER X1000 Portable TELEX tester NEW	£250
Sekonic SD 150H 18 channel digital Hybrid chan recorder	£1995
HP 7580A A1 8 pen HPGL high speed drum plotter	£1850
Computer MCA1613APC 16mm auto iris lenses C mount	£125
Seaward PAT2000 dual voltage computerised PAT tester	£585
Densel MJD 0185AH 1KVA UPS system with balls NEW	£575

LOW COST RAM & CPU'S

INTEL 'ABOVE' Memory Expansion Board. Full length PC-XT and PC-AT compatible card with 2 Mbytes of memory on board. Card is fully selectable for Expanded or Extended (286 processor and above) memory. Full data and driver disk supplied. In good used condition fully tested and guaranteed. Windows compatible. Order as: ABOVE CARD £59.95(A1)
Half length 8 bit memory upgrade cards for PC AT XT expands memory either 256k or 512k in 64k steps. May also be used to fill in RAM above 640k DOS limit. Complete with data. Order as: XT RAM 400, 256k, £32.95 or 512k £38.95 (A1)

SIMM OFFERS

1 MB x 9 SIMM 9 chip 120ns only	£19.50 (A1)
1 MB x 9 SIMM 3 chip 80 ns	£23.50 70ns
1 MB x 9 SIMM 9 chip 80 ns	£22.50 70ns
4 MB 70ns 72 pin SIMM module only	£125.00 (A1)
SPECIAL INTEL 486-DX3 CPU	£79.99 (A1)

NO BREAK UNINTERRUPTIBLE P.S.U'S

EMERSON ACCUCARD UPS, brand new 8 Bit half length PC compatible card for all IBM XT/AT compatibles. Card provides DC power to all internal system components in the event of power supply failure. The Accusaver software provided uses only 6k of base RAM and automatically copies all system, expanded and video memory to the hard disk in the event of loss of power. When power is returned the machine is returned to the exact status when the power failed!! The unit features full self diagnostics on boot and is supplied brand new, with full, easy fitting instructions and manual. Normally £189.00 NOW! £69.00 or 2 for £120 (B)

Issue 13 of Display News now available - send large SAE - PACKED with bargains!

Display Electronics - ESTABLISHED 25 YEARS

LONDON SHOP
Open Mon - Sat 9:00 - 5:30
215 Whitehorse Lane
South Norwood
On 68A Bus Route
N. Thornton Heath &
Seahurst Park SR Rail Stations

ALL MAIL & OFFICES
Open Mon-Fri 9.00-5.30
Dept Ent. 32 Bgllyn Way
Upper Norwood
LONDON SE19 3XF

DISTEL © The Original
FREE On Line Database
Info on 1000's of items
V21,V22, V22 BIS
0181 679 1888

ALL ENQUIRIES
0181 679 4414
FAX 0181 679 1927

All prices for UK Mainland. UK customers add 17.5% VAT to TOTAL order amount. Minimum order £10. Bank File account orders accepted from Government, Schools, Universities and Local Authorities - minimum account order £50. Cheques over £100 are subject to 10 working days clearance. Carriage charges (A)-£3.00, (A1)-£4.00, (B)-£5.50, (C)-£8.50, (D)-£12.00, (E)-£15.00, (F)-£18.00, (G)-CALL. Allow approx 6 days for shipping - faster CALL. All goods supplied to our Standard Conditions of Sale and unless stated guaranteed for 90 days. All guarantees on a return to base basis. All rights reserved to change prices / specifications without prior notice. Orders subject to stock. Discounts for volume. Top CASH prices paid for surplus goods. All trademarks etc acknowledged. © Display Electronics 1995 E & O.E. 45




In my own case, I have a tumble dryer in my garage to which my two year old son can, on occasion, get access. Although the switched socket outlet feeding it is too high for him to reach, it is often left plugged in and switched on - therefore my son could operate the dryer. Before now he has managed to put one of our cats in the machine but thankfully has not then switched it on!



We also have a washing machine in the kitchen where similar risks are apparent. Electrical isolation rendering the appliance inoperative would mean (in our case) the door could not even be opened.

A secondary risk is that garages (particularly wooden ones such as mine) and similar outbuildings can suffer from leaks, flooding floors, and other sources of moisture.

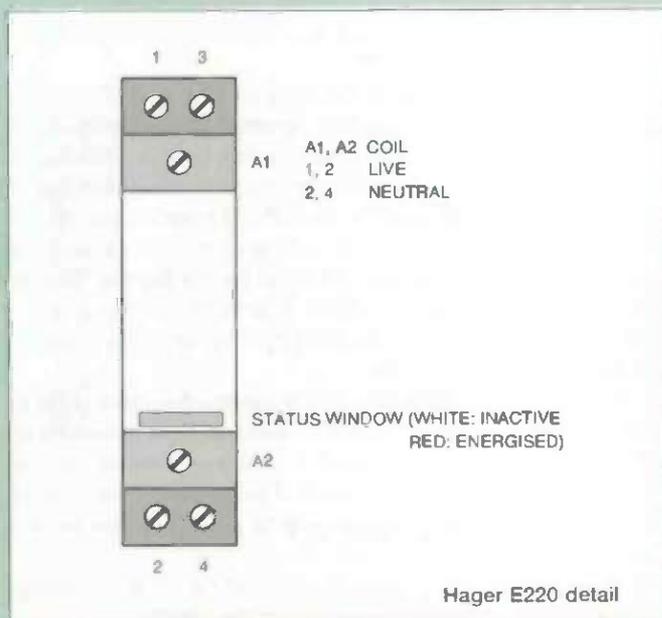The purpose of the design outlined here is to provide power to the appliance for just the necessary amount of time. Isolation is double-pole, i.e. both live and neutral. Maximum loads with the standard design are limited by the relay, around 5A resistive. Use of a contactor extends capability to a full 13A



Hager E220 detail

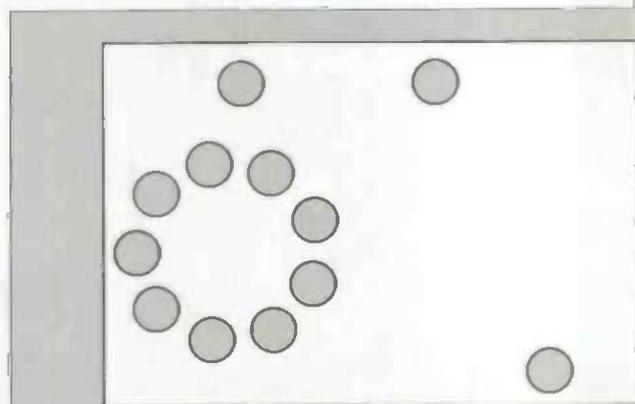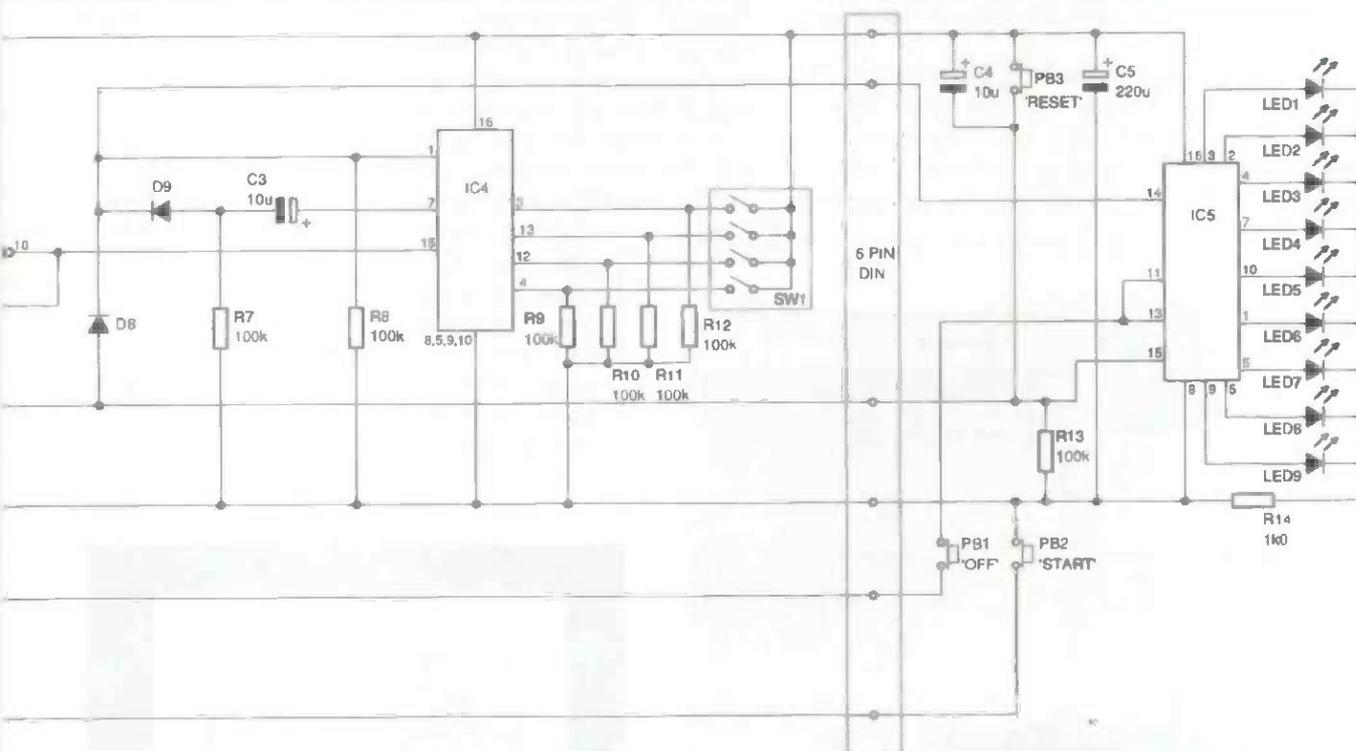

Remote unit panel layout

load with an inductive content, e.g. the aforementioned tumble dryer, or a washing machine.

An added benefit is that the three controlling pushbuttons are also isolated from the mains, operating at low voltage (12v). An advantage is to allow another use in a kitchen where, for example, a dishwasher or washing machine is installed next to the sink. The IEE Regulations state that it must be impossible to both have a hand in the sink area and on a socket outlet at the same time. The isolator unit could be mounted under the sink with the ring main outlet and a remote control box or panel with the pushbuttons and optional countdown LEDs mounted in any convenient position.

Continuing the theme of isolation, in the quiescent state the transformer primary is double-pole isolated from the mains by a relay. An alkaline battery is used to provide power for the "ON" pushbutton and the relay coil while the transformer is isolated, thereby allowing the timing cycle to be initiated. However, a double-pole mains-rated (override) pushbutton can also be provided on the main unit to short circuit the isolator, thereby starting the timer if necessary without the battery.

This article shows the timed isolator made up as two units, the main unit and the remote control. There is no reason why these cannot be combined; the LEDs are optional as are the "Reset" and "Off" controls.

Delay is set by a DIL switch on the PCB, in multiples of 15 minutes or 30 minutes depending on the wiring of the PCB, giving maximum delays of 4 or 8 hours. The delay period is determined by counting mains cycles and is therefore quite accurate and predictable, helping to eliminate the risk of power

being removed until, for example, the washing machine has completed its cycle.

Changing the delay time means opening the case and changing the DIL switch setting to a calculated value or consulting a reference table (given later). This feature is quite deliberate and improves the tamperproof qualities of the system. However, there is no reason why four small toggle switches or similar could not be used, if desired.

The project also presents an opportunity to provide MCB (Miniature Circuit Breaker) or better still RCD (Residual Current Device) protection to the appliance, more on which later.



How It Works

In the quiescent state, relay contacts RLAI isolate the mains transformer and the load from the supply. Pressing pushbutton PB2 connects battery B1 to the relay coil via D5. The relay contacts then energise T1 and the load. D5 is included to prevent reverse current through B1, a potentially explosive situation in the case of an alkaline battery.

C4 and R13 provide a reset pulse to IC2 and IC5, and a preset enable pulse to IC4 to load data from SW1. Mains waveform pulses are fed to TR1 via potential divider R1, R2 and diode D2. TR1 is wired as a collector follower with R3, forming a high gain amplifier. The effect is to limit both polarity and amplitude to within the bounds of the power supply. IC1, C1, and C2 form a 12v regulated supply.

Pulses from TR1 of either 50Hz or 100Hz are counted by IC2. The 100Hz frequency is produced by BR1 full wave rectifying the 50Hz sinewave from T1. On reaching a count of 10000, IC2 is reset by the AND-gate network built around IC3. Diode OR-gate D6, D7, R6 is necessary as the reset pin is shared by the "on-reset" configuration C4, R13.

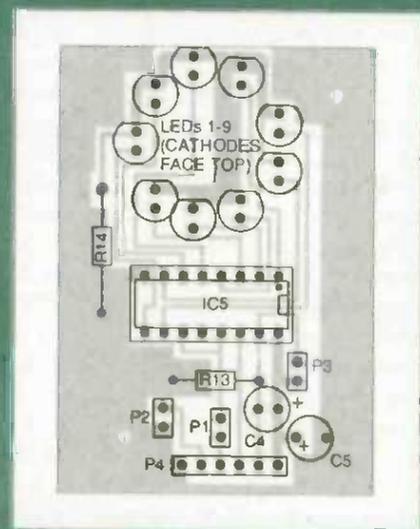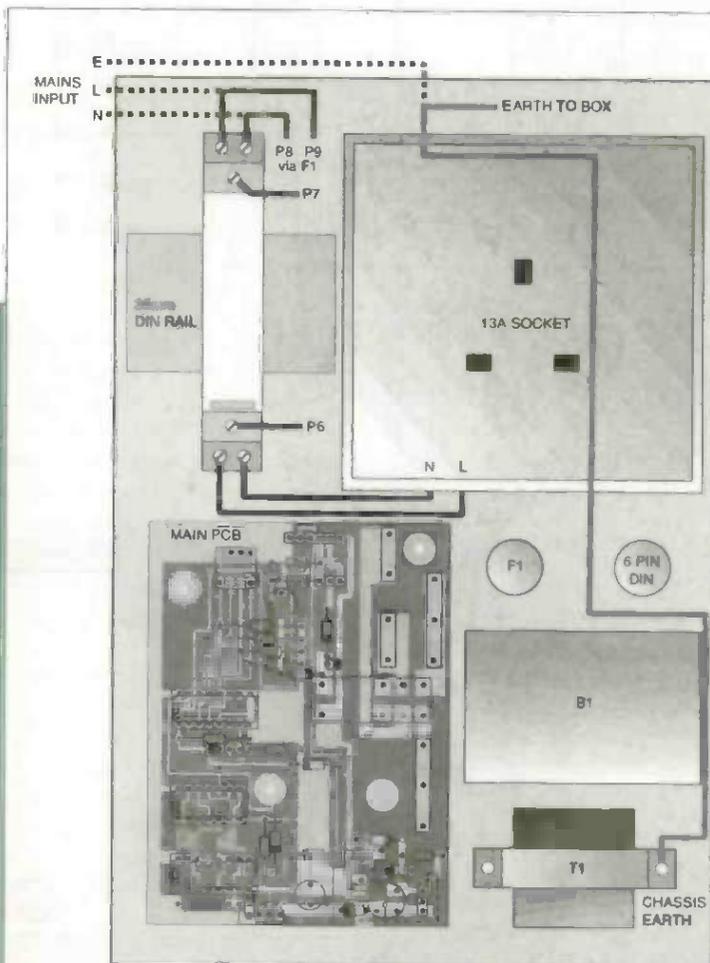This reset pulse on 10000 is also fed to IC4, which is wired as a down counter. IC4 therefore counts down on every 10000 pulses from TR1 until reaching zero, having been preset to "n" (set by SW1) on power-up. At this point R8, C3,



Above: Component overlay LED display board

Left: Main unit internal unit with optional contractor

R7, D9 produces a pulse from the "CARRY-OUT" pin of IC4, presetting IC4 to repeat the cycle and clocking IC5. In this way IC4 is connected as a modulo-n divider depending on the binary number set up on SW1.

IC5 counts from 0 to 9; outputs 0 to 8 are connected to an LED moving-dot display formed from LED1 to LED9. When the "9" output goes high, it takes the clock inhibit pin of IC5 high to prevent further counting. TR2 has been kept turned hard on by the path to ground via R5 and IC5. When IC5 pin 11 goes high at the count of "9", TR2 turns off, releasing the relay contacts. Power is therefore withdrawn from the circuit. As smoothing capacitors C1 and C5 discharge, the fact that the clock inhibit pin of IC5 is kept high by the "9" output as the supply voltage falls helps prevent any nuisance retriggering of the circuit.

At any time during the counting cycle, pressing PB3 pulls the reset/preset line high by shorting C4. The count on all chips therefore starts again and a new timing cycle is initiated. Pressing PB1 interrupts the ground path from TR2's base via R5, ending circuit operation immediately. R4 is included to stop TR2's base floating.

TR2 is a small signal, high gain transistor which would not normally be used to switch such a large load as RLA1. However, it is always hard on or completely off, and therefore power dissipation is minimised. D1, D4, and D5 are specified as 1N4001 where the current requirement is approaching the 75mA maximum of the 1N4148.


B1 should last quite some time as only a brief pulse is required on each occasion the unit is activated. An alkaline battery is recommended as they tend to be leak-resistant and capable of maintaining p.d. and current capability for some years.

Output devices

The relay used in the prototypes were from Maplin, who state the contacts are rated at 5A resistive. Some of this capability is used by T1, a very small although inductive load. A 5A limit would restrict use of this project to small loads, e.g. my computer printer which I have a habit of leaving switched on. A number of the electrical accessory manufacturers have made available larger relays (contactors) designed to fit into modern consumer units. They are available from specialist electrical outlets and electrical wholesalers, and are made by such names as Mk, Merlin Gerin, Hager, Crabtree, etc. This type tends to be DIN-rail mounting, and so to use them you need to obtain some DIN rail. RS/Electromail can supply, but it might be worth asking your source of contactor if they can supply the rail as well, if only to save the postage! Alternatively, some contactors made for industrial use are screw mounting, but tend to be rather larger and more expensive. The prototype used the DIN-rail mount Hager E220 which, with a 20A rating, is perfect for controlling large appliances. Figure 2 shows the six connections to the Hager device, looking at the front of the unit.

Industrial contactors may provide more facilities which may be of use under special circumstances. For example, normally closed contacts would mean the timer could interrupt supply for a given period of time. This could be achieved using the spare Normally Closed contacts on RLA1, but would mean the contactor coil remaining energised for most of the time. Auxiliary contact blocks can often also be fitted in combinations of Normally Open (N.O.) and Normally Closed (N.C.).

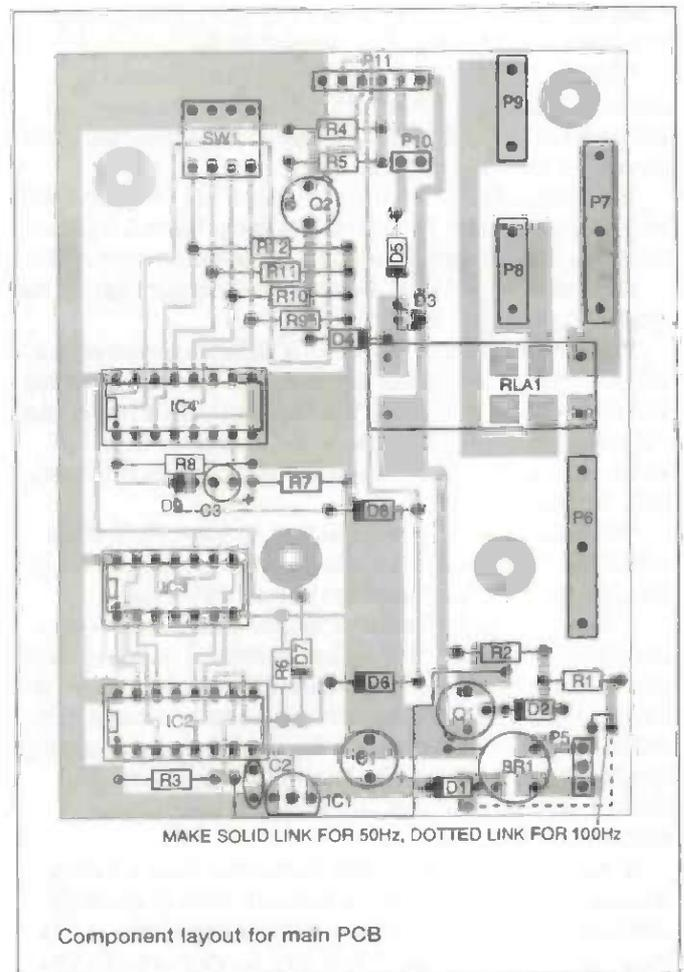If you use DIN-rail, you have the opportunity to include a Miniature Circuit Breaker (MCB), which is effectively a very fast



overcurrent protection device. The 5916s (16A), 5910s (10A), or even 5906s (6A) could be included here depending on your application.

Alternatively, you could install a Residual Current Device (RCD), which monitors current flow in both Live and Neutral supply lines. A difference (a RESIDUAL of (Live Current - Neutral Current)) indicates a current to earth, the only other path available. A fault condition is likely to exist under these circumstances, and therefore the RCD will trip, isolating the supply. There are various types, some combining over-current with residual current protection, often known as an "RCBO". These only break the live side of the supply, and therefore do not provide full isolation. A double-pole type, with a sensitivity of 30mA or better still, 10mA, is recommended. Examples are the Mk 6316s and Mk 5716s. My preference for double-pole isolation is based upon the possibility that Live and Neutral connections can be reversed. This could be due to an error by the constructor or whoever installed the house wiring. How many of us have checked?

You are recommended to consult a qualified electrician if you have the slightest doubt.

Construction

There are two PCBs which are very straightforward to construct, following the usual rules of orientation, etc. I tend to use PCB connectors (as listed in the Parts List) as they make for a very neat job and easy removal of the PCB if necessary. However, when constructing the remote PCB, P1, P2, and P3 are best connected to pushbuttons directly with flexible wire due to lack of space.

Remember that D1, D4, D5, BR1 and RLA1 require larger

holes than most components, as do all of the PCB connectors. It is much easier to drill out an "empty" PCB.

Start by soldering the IC sockets in place, followed by resistors, capacitors (except C1), connectors and then semiconductors. Fit C1 and RL1 last as they make the board unwieldy if installed at an early stage.

Don't forget the link from R1 to either T1 or BR1 depending on your chosen clock frequency/time delay. There is only one other link in the project, connecting to the "south" side of R3.

Beware of P4 and P11; although they connect together the order of connections is mirror image.

If you mount the remote PCB in a separate enclosure, use a six-pin DIN plug and socket with some six-core "signal" cable to make the interconnection. The following table is based upon the colours in the Maplin cable as per the components list. References for P4 and P11 are counting from 1 to 6, starting from the top.

The DIN socket is not numbered at the back. Pin 6 is the centre pin. If you look at the socket with the chassis connection nearest, count anticlockwise from bottom right as pin 1.

The project can be used in a number of different ways so the choice of case and final layout will depend on the intended use. I have not included a fuse (other than F1 to protect T1 and RL1) as it is anticipated that the unit will be connected to the mains supply via a fused plug. If this is not the case, you must include a fuse to suit the total load at the mains input. My layout is shown in Figure 5, and allows for the optional contactor.

If you follow my example and purchase a 9 x 6 x 3 black enamel "Adaptable Box" for the main unit from an electrical wholesaler you will find you have a box of remarkable quality for a relatively small outlay. Prices vary, so shop around. The size I have used is the smallest that is realistically suitable but it is not the most common, you will more easily get 9 x 9 x 3 or 12 x 12 x 3. Note that a larger case will be required if adding MCB or RCD protection as described earlier. The boxes are steel and highly suitable for mounting in the back of cupboards, under workbenches etc. I mounted all of the

Table 1
References for P4 and P11

Signal	Colour	P11	6-pin DIN	P4
Ov	Black	6	Pin 6 (centre)	1
Start	Blue	5	Pin 1	2
Out	Green	4	Pin 2	3
Clock	White	3	Pin 3	4
Reset	Yellow	2	Pin 4	5
+ve	Red	1	Pin 5	6

electronics on the reverse of the lid, bringing only the incoming supply through the box itself. This makes it easier to mount the box on a wall, but please remember to earth the box and lid. Another advantage of this method is that it is a lot easier to assemble the project and inter-wire on a fairly flat steel sheet than in a box 3" deep!

The range of adaptable boxes come in galvanised or black enamel finishes, the latter being cheaper. They are also available "plain" or "knockouts". I use the knockout type as they have 20mm holes available all round, and are the same price. When buying your box ask for a Pirelli 251 cable gland, or an equivalent "stuffing gland", and make sure you get a locknut or locking for it. You can then press out one of the knockouts using a blunt tool in the centre of the knockout and a hammer, install your gland through it, and secure your incoming flex cable very neatly.

The remote unit, if built in the specified case, is an exercise in small, neat construction! The PCB as been designed to just fit. With the height of the LED's there is no need to secure the board in the case. There are knockouts in the side of the case where the lid can trap the cable once fitted. Two holes are provided in the base for screw fixing, but remember to stick some insulating tape or other material over the screw heads to prevent a short circuit with the bottom of the PCB. You will

Table 2
100Hz clock (dotted link on Overlay)

DIL Switch Setting Minutes	Total Delay (Hrs:Min)	LED count every Seconds	(Min:Sec)
0 (0000)	15	(0:15)	100 (1:40)
1 (0001)	30	(0:30)	200 (3:20)
2 (0010)	45	(0:45)	300 (5:00)
3 (0011)	60	(1:00)	400 (6:40)
4 (0100)	75	(1:15)	500 (8:20)
5 (0101)	90	(1:30)	600 (10:00)
6 (0110)	105	(1:45)	700 (11:40)
7 (0111)	120	(2:00)	800 (13:20)
8 (1000)	135	(2:15)	900 (15:00)
9 (1001)	150	(2:30)	1000 (16:40)
10 (1010)	165	(2:45)	1100 (18:20)
11 (1011)	180	(3:00)	1200 (20:00)
12 (1100)	195	(3:15)	1300 (21:40)
13 (1101)	210	(3:30)	1400 (23:20)
14 (1110)	225	(3:45)	1500 (25:00)
15 (1111)	240	(4:00)	1600 (26:40)

Table 3
50Hz clock (solid link on Overlay)

DIL Switch Setting	Total Delay Minutes	LED count every (Hrs:Min)	Seconds	(Min:Sec)	
0	(0000)	30	(0:30)	200	(3:20)
1	(0001)	60	(1:00)	400	(6:40)
2	(0010)	90	(1:30)	600	(10:00)
3	(0011)	120	(2:00)	800	(13:20)
4	(0100)	150	(2:30)	1000	(16:40)
5	(0101)	180	(3:00)	1200	(20:00)
6	(0110)	210	(3:30)	1400	(23:20)
7	(0111)	240	(4:00)	1600	(26:40)
8	(1000)	270	(4:30)	1800	(30:00)
9	(1001)	300	(5:00)	2000	(33:20)
10	(1010)	330	(5:30)	2200	(36:40)
11	(1011)	360	(6:00)	2400	(40:00)
12	(1100)	390	(6:30)	2600	(43:20)
13	(1101)	420	(7:00)	2800	(46:40)
14	(1110)	450	(7:30)	3000	(50:00)
15	(1111)	480	(8:00)	3200	(53:20)

need to bend the connections to the pushbuttons at right angles to the body to make them fit. The location of the controls on the lid is only critical in as much as taking care not to foul components on the PCB. Figure 4 provides a scale template for the relative position of holes for the prototypes. Take a photocopy if you want to avoid damaging this magazine, but please check it matches with your PCB, etc, before using it! It should be possible to replace the "on" and "reset" pushbuttons with a subminiature toggle switch, DPDT, centre off, momentary action. I have not tested this idea but it would save space.

Pressing the START button PB2 will close the relay contacts, energising the load or contactor if used. The first LED will light (About the 11 o'clock position with the remote

board upright). The LEDs will count anticlockwise, at the end of the count the unit and load will turn off.

Setting the delay depends on the clock frequency chosen at time of construction and the number set on DIL switch SW1. The table below gives the various combinations. Pressing PBI at any time will turn the load and the unit off prematurely. Pressing PB3 resets the count for a fresh time delay without interrupting the supply to the appliance.

Note that if you turn the unit off with PBI and wish to turn it on again almost immediately, press PB3 (Reset) and then PB2 (Start) as C3 and C5 take 30 seconds or so to discharge.

My cat now sleeps soundly in the knowledge he will not wake to see the world revolving at an alarming rate on what appears to be a very warm day

PARTS LIST

Resistors

● R1	220K	(A220K)
● R2,6,7,8,9,10,11,12,13	100K	(A100K)
● R3	1K8	(A1K8)
● R4	47K	(A47K)
● R5	10K	(A10K)
● R14	1K0	(A1K0)

Capacitors

● C1	1000u 35v Electrolytic	(F18U)
● C2	10n Disc Ceramic	(WX77J)
● C3,4	10u 50v Electrolytic	(FF04E)

PARTS LIST

● C5	220u 35v Electrolytic	(JL22Y)
------	-----------------------	---------

Semiconductors

● IC1	78L12ACZ Voltage Regulator	(WQ77J)
● C2	4020 14 stage binary counter	(QX11M)
● IC3	4081 Quad 2-Input AND-gat	(QW48C)
● IC4	4516 Binary Presettable Counter	(QW87U)
● C5	4017 Decoded Decade Counter	(QX09K)
● TR1	BC109C NPN Bipolar Transistor	(QB33L)
● TR2	BC179 PNP Bipolar Transistor	(QB54L)


PARTS LIST

- D1,4,5 1N4001 Rectifier Diode (QL73Q)
- D2,3,6,7,8,9 1N4148 Signal Diode (QL80B)
- BR1 W005 Bridge Rectifier (QL37S)
- LED1 - 9 Red 5mm LED (WL27E/AQ12N)

Miscellaneous

- T1 6v-0-6v or 0-12v 100mA Sec (WBO0A)
- RLA1 0-240v Pri Mains Transformer
12v 200 ohm coil
240v 5A DPDT Relay (YX98G)
- PB1 Push to break pushbutton (FH60Q)
- PB2,3 Push to make pushbutton (FH59P)
- BI Alkaline "PP3" (ZB52G)
- SW1 4 way SPST DIL switch (JH081)
- CT1 Hager E220 Contactor (Optional)
16 pin DIL sockets x 3 (BL19V)
14 pin DIL socket x 1 (BL18U)
- P4, P11 6way PCB Connectors as Maplin BH65V/YW12N/YW25C
- P5 3 way PCB Connector as Maplin BX97F/BX96E/YW25C
- P6,P7 3 way Mains Connectors as Maplin JY95D
- P8,P9 2 way Mains Connectors as Maplin JY93B
- P10 2 way PCB Connector as Maplin HB59P/RK65V/YW25C
- FI Panel Mounted fuseholder (DA59P) & suitable fuse (up to 5A) - see text.
- Insulated Spacers, 20mm. (FS38R)
- 35mm "Top Hat" DIN rail (see text).
- MK 2757WHI single 13A socket or equivalent (note the unswitched type also suitable), MK2200 mounting frame.
- 6 pin DIN chassis socket (HH36P)
- 6 pin DIN plug. (HH29G)
- 6 Core cable. (XS54J)
- 3 Core Mains Flex (XR10L)
13A Plug (see text)
- Cable Gland (see text)
- PP3 connector (HF28F)
- Battery Holder 9" x6 "x 3"
- adaptable box (see text) for main unit.
- Maplin case Box 321 (FK31Q)
- Cable Ties, Nuts, Bolts, etc.

WINTER 1995/6 CATALOGUE

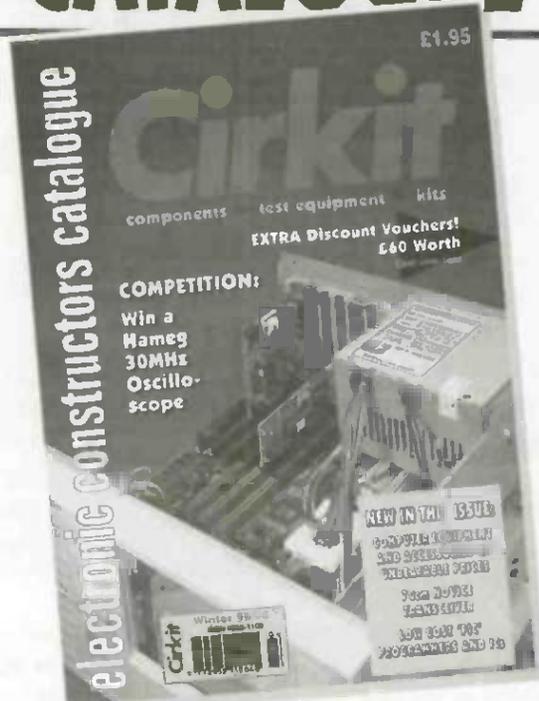

The new winter '95/96 edition has 280 pages packed with over 4000 products.

- ▶ New editions to our computer section further extending our range of PC components and accessories at unbeatable prices
- ▶ Free competition with a chance of winning a Hameg 30MHz oscilloscope
- ▶ 100's of new products including; Books, Component Packs, Connectors, Switches, Test Equipment and Tools.
- ▶ New range of oscilloscopes from Hameg and extended range of mobile phone batteries and accessories
- ▶ Latest PIC Microcontroller IC's and programmer
- ▶ New 70cms mobile transceiver for the novice radio amateur enthusiast
- ▶ 280 pages, 26 sections and over 4000 products from some of the worlds finest suppliers
- ▶ Available at most newsagents or direct from Cirket
- ▶ Out 26th October 1995
- ▶ Send for your copy today!

£1.95
+ 30p p&p

Cirket



Cirket Distribution Ltd

Park Lane · Broxbourne · Hertfordshire · EN10 7NQ
Telephone: 01992 448899 · Fax: 01992 471314

BASIC

for the

PIC microcontroller

PART 3

The developer of this unique project, Robin Abbott, looks at some other versions of the ETI PIC based controller module. These offer the user a range of additional options which make them ideal for specific applications

This month we will look at the versions of PIC Controller BASIC which operate on the 16C5x series of processors. In the original article, it was stated that there would be a version of PIC Controller BASIC which would operate on the 16C56. However, it has very little RAM and the extra program requirements of the paged memory system used on the 16C5x series meant that the version which was eventually produced was too limited in capability for serious use.

The 16C57 and 16C58 processors, however, have the advantage of 70 bytes of RAM each and 2K of EPROM. This means that versions of PIC Controller BASIC for these processors allow extensions to the BASIC language which are described in this article. The 16C57 is provided in a 28-pin package which supports three I/O ports and so, for the BASIC application (which uses 4 bits of port A), there are 16 I/O pins and one input for the real time counter. The 16C58 is provided in an 18-pin package, and uses the same circuit and board layout as that shown in last month's article for the 16C84 device.

The 16C57 and 16C58 processors are a better processor than the 16C84 for the BASIC project in every respect with the exception of interrupt support and upgrading. Although it is possible to upgrade the 16C84 device to the latest version of PIC Controller BASIC, it is only possible to do this with the '57 and '58 versions by using the more expensive erasable devices. However, One Time Programmable (OTP) versions of the '57 and '58 are available at a very reasonable cost.

Circuit description

Figure 1 shows the circuit diagram for the 16C57 version of PIC Controller BASIC. The essential circuit is identical to the

18-pin version shown in the October issue of ETI. The serial port is a low-cost interface which relies on the voltage on the incoming data line to provide the negative supply on the outgoing data line. The oscillator can be a crystal or ceramic resonator. I/O on this module type is provided on a 20-way IDC connector which allows connection to application circuits through 20-way cable. The voltage regulator is optional, the circuit will work up to 6V but, if greater voltages than this are to be used, then a regulator must be provided. For application circuits which will use less than 90mA then a 78L05 may be used; for greater current consumption, use a 78M05 (500mA) or 7805(1A) device.

IC2 is the EEPROM device; either 24LC16 or 24LC65 devices may be used. However, a different program is used in the PIC for each device.

The brown out protection circuit is based around TR1 which ensures that the PIC is reset if the power supply falls below 4V. Interestingly, Microchip has recognised that brown out protection should be provided on the chip and the latest devices (the 16C2X series) all have a brown out protection circuit and an enable bit in the configuration fuses.


The 16C58 version uses the circuit shown in the October issue of ETI. However, the component references are identical to those shown in Fig. 1 and it is possible to build the circuit from Fig. 1. The I/O connector for 18 pin versions of BASIC is a 16-pin DIL IC socket.

Versions of the '57 and '58 devices are available for 4MHz, 10MHz and 20MHz clock frequencies. The clock frequency is hard programmed in to the code to save on program space.

Construction and testing

Construction is straightforward. Use sockets for IC1 and IC2. The circuit board overlay is shown in Fig. 2 for the 16C57 version and the overlay for the 16C58 is shown again in Fig. 3; this is the board which was given away with the October issue of ETI. The 16C57 version has three wire links. Use thin single core hook up wire as the links must not interfere with PL3. Insert wire links and IC sockets first, then resistors, capacitors, voltage regulator and transistors. Finally, insert PL1 and PL2.

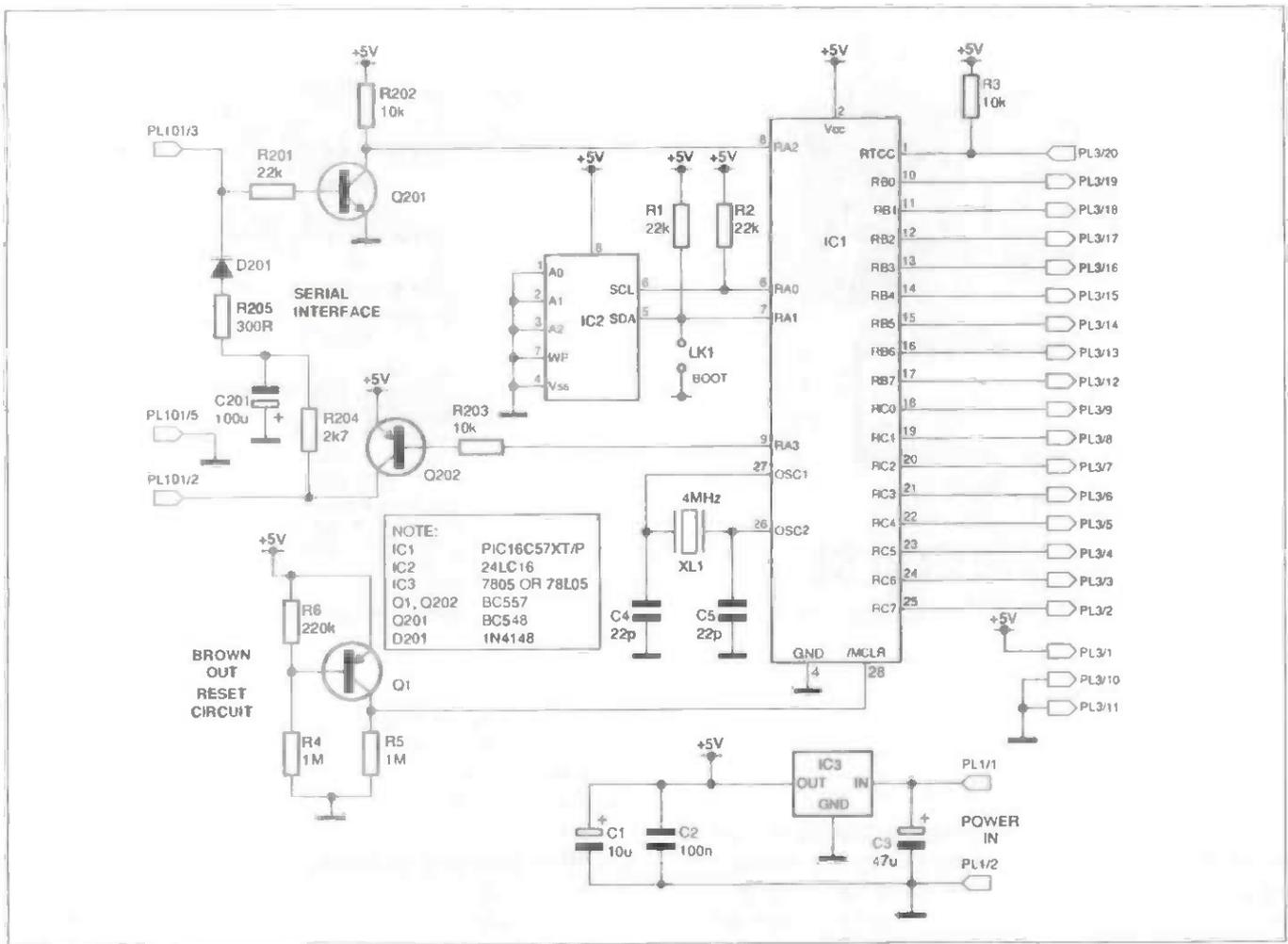Testing is very straightforward. Without IC1 or IC2 in circuit, connect the power supply and check that the socket for IC1



has +5 between pins 2 and 4. Power down, insert IC1 and IC2 and connect to the host PC. Start the PICBASDE program and check that the module is detected. There are a number of test programs provided with PICBASDE. Provided that they don't use interrupts, any of these may be downloaded to the module to test it. It is recommended that a program which uses no external devices is used.

The use of PICBASDE is fully explained in the November issue of ETI.

Extended BASIC

The BASIC language provided for the '57 and '58 is extended to level 1. This provides new program constructs and various commands to drive external hardware.

The new commands and facilities in level 1 PIC Controller BASIC are as follows:

- LED driving. A new command provides for the M4540 device which allows 4 digit, 7 segment LED displays, or up to 36 external devices to be driven from 2 output pins on the BASIC module.
- LCD driving. New commands provide a simple 4 bit interface to those LCD modules (the majority) which use the Hitachi chip set.
- Infra red transmission and reception is supported to send 8 bit numbers between two PIC BASIC modules, which may be separated by up to 10m.
- A fast data protocol is provided to send information on a clocked data line between two PIC BASIC modules.

- The width command measures pulse width of either polarity on an input pin.
- The clocks command sends any number of clocks of either polarity on an output pin.
- The wait command pauses program execution for any time between 1mS and 30S.
- Shift left and shift right operators provide fast multiplication and division by 2.

Some of these new commands and constructs are detailed in the rest of this article.

Parameter passing to functions and local variables



The extended RAM which is available in the '57 and '58 devices allows PIC Controller BASIC to make use of the stack to provide parameters in functions, recursive functions and local variables in functions.

Function parameters allow numbers to be passed to functions and subroutines. These are set up in the same way as normal functions and subroutines using the TYPESUB and TYPEFUNC keywords. For example, the following program calculates the Centigrade equivalent of Fahrenheit temperatures from 0 to 100 in 10 Fahrenheit steps and puts them in the array temps, which can be read in the debugging window on the host PC.

```

typefunc ftoc(temp)
dim temps[11].8
for i=0 to 100 step 10
temps[i/10]=ftoc(i)

```

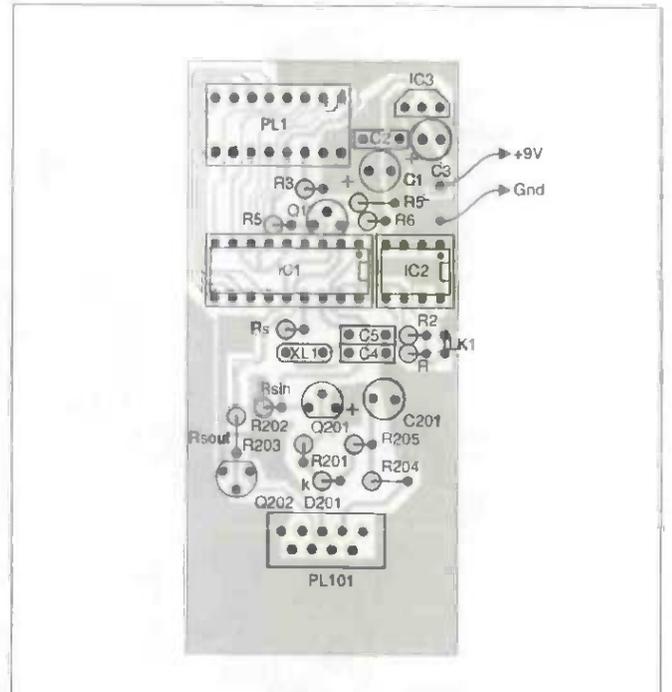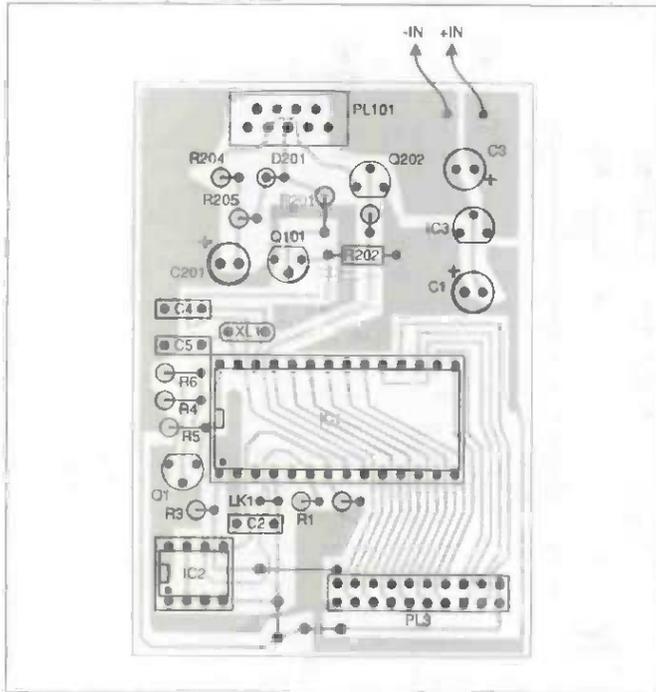

```

next
monitor()
func ftoc(x)
return ((x-32)*5)/9
end

```

Local variables are variables which are declared in a function or subroutine. They may then only be used in that function. If the same variable is declared in the main program and in a function or subroutine, then the local variable takes precedence in the function or subroutine, but is invisible outside it. Local variables may only be of 8 or 16 bits in length and should be declared using the DIM statement. Local variables must be declared at the top of the function or subroutine.

For example, the following version of the function ftoc works exactly the same as that shown above, but uses a local variable. It is less efficient of RAM usage and is only shown here as an example. Local variables do not appear in the debugging window.

```

func ftoc(x)
dim i.8
i=((x-32)*5)/9
return i
end

```

The final advantage that local variables and parameter passing gives is that recursive functions may be used. To consider a typical use for recursive functions, consider the factorial function. The factorial of a number X is defined as $X*(X-1)*(X-2)...(1)$. Thus, the factorial of 4 is $4*3*2*1$ which is 24. The alternative definition of factorial of X is to say that factorial(1) is 1, and if x is greater than 1 then factorial(x) is $x*(factorial(x-1))$. This latter definition is used in the recursive function factorial shown below:

```

typefunc factorial(x)
; program here
func factorial(x)
if (x=1) then return 1
return factorial(x-1)
end

```

Recursive functions can often be a very neat method of calculating results, or performing complex operations. However, they consume stack memory very rapidly and a

simple test program based on the factorial function shown only worked up to factorial(8) (which exceeds the range of 16 bit numbers), factorial(9) caused the stack to overwrite the system variables and BASIC crashed.

Device driving commands

Most of the commands in the following sections allow the user to define any pin on the I/O ports of the PIC to be used for peripheral device connections. These pins are defined using the port definition form. This is the form used for the serout, seroutstring and serin commands which were shown in the November issue of ETI. Consider the width command. The width command looks at the current state of an input pin, looks for a pulse of the opposite state and measures its width. Thus, if the pin is high, then the width command waits until the pin becomes low, then measures the time before it goes high again. The width command needs one parameter which is the pin on which a pulse is to be measured. The pin is defined as the address of the port+16*bit number. Thus, bit number 4 on port A is defined as $ADDPORTA+16*4$. The following example program shows how to measure the width of a pulse on port B, bit 5; the result can be read in the debugging window.

```

const portpin=ADDPORTB+16*5

dim x.16
x=width(portpin)
monitor()

```

The result returned depends on the processor frequency. For example, with a 4MHz clock, the result is in units of 10uS; with a 20MHz clock the result will be in units of 2uS. Thus, the above program will measure a 1KHz square wave as $x=100$ with a 4MHz clock, and $x=500$ with a 20MHz clock.

Next Month...

Next month we'll take a look at the 16C64 version of PIC BASIC, which offers further extensions to the language.



**NEWS FROM THE NEXUS
PHOTOSTAT SERVICE.
EFFECTIVE FROM 1ST
NOVEMBER 1995**

NEXUS

The Nexus Photocopying Service can provide you with all those interesting

features and valuable projects that have been published in your favourite magazine. The new costs of our photocopying service are as follows:-

First article: £2.75 inc of VAT. Please note that projects published over several issues must be ordered as a series of individual articles, each for £2.00.

A £2.75 search fee is required if full information is not supplied. Please note delivery could be up to 28 working days.

Please supply photo-copies of the following articles from
(Complete in BLOCK CAPITALS)

Month Year Page (if known)

TITLE

Month Year Page (if known)

TITLE

Month Year Page (if known)

TITLE

I enclose a cheque/postal order made out to Nexus Special Interests to the value of:

£ P&P £1.00 (UK only) 20% Overseas

Total remittance £

Name:

Address:

Post Code:

Send the completed form and remittance to:
Photocopy Service, Nexus Special Interests, Nexus House, Boundary Way,
Hemel Hempstead, Hertfordshire. HP2 7ST


BASIC Stamp

-Stamp sized Computer runs BASIC

The Basic Stamp by PARALLAX measures only 40x60mm yet is a true microcomputer that runs BASIC programmes written on your PC. Its size, ease of use and extensive I/O features make it an ideal tool for both educational and industrial applications as well as for the serious hobbyist.

Writing programmes for the Stamp is easy. A 3-pin cable connects the Stamp to your PC printer port. One piece of software is used to enter, debug and download your programme. Features include 8 I/O lines, non-volatile memory, serial comms, pulse measurement and PWM; all achieved with a minimum of external components.


Typical Application

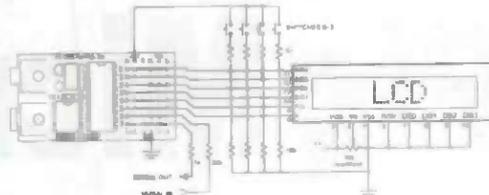

The BASIC Stamp Development Kit at £99 includes: 1 BASIC Stamp, instruction manual, PC cable, software and extensive application notes. Further Stamps are available from £29.

Muscle Wires

-wires that contract when heated!

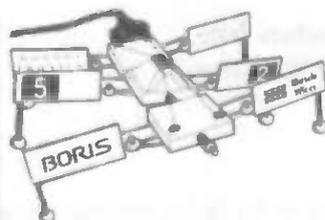

Fascinating, highly processed Shape Memory Alloy wires that actually contract when electrically heated producing a useful amount of force.

Low cost linear actuators at last!

Their light-weight makes them excellent for use in models, robots and many other types of project. Low voltage and power allows simple control by computer or electronics (eg The BASIC Stamp).

Detailed Data and Project Book (128 pages) plus Muscle Wire kit suitable for 13 projects including BORIS the walking, six-legged robot; only £44.95.

All prices excl VAT and £3 postage per order. For further details of the Stamp, Muscle Wires and other products please call for our NEW colour catalogue.


MILFORD INSTRUMENTS

24hr Answerphone - 01977 683665, Fax 01977 681465
Milford House, 120 High Street, South Milford LEEDS LS25 5AQ

PCB Designer

For Windows 3.1

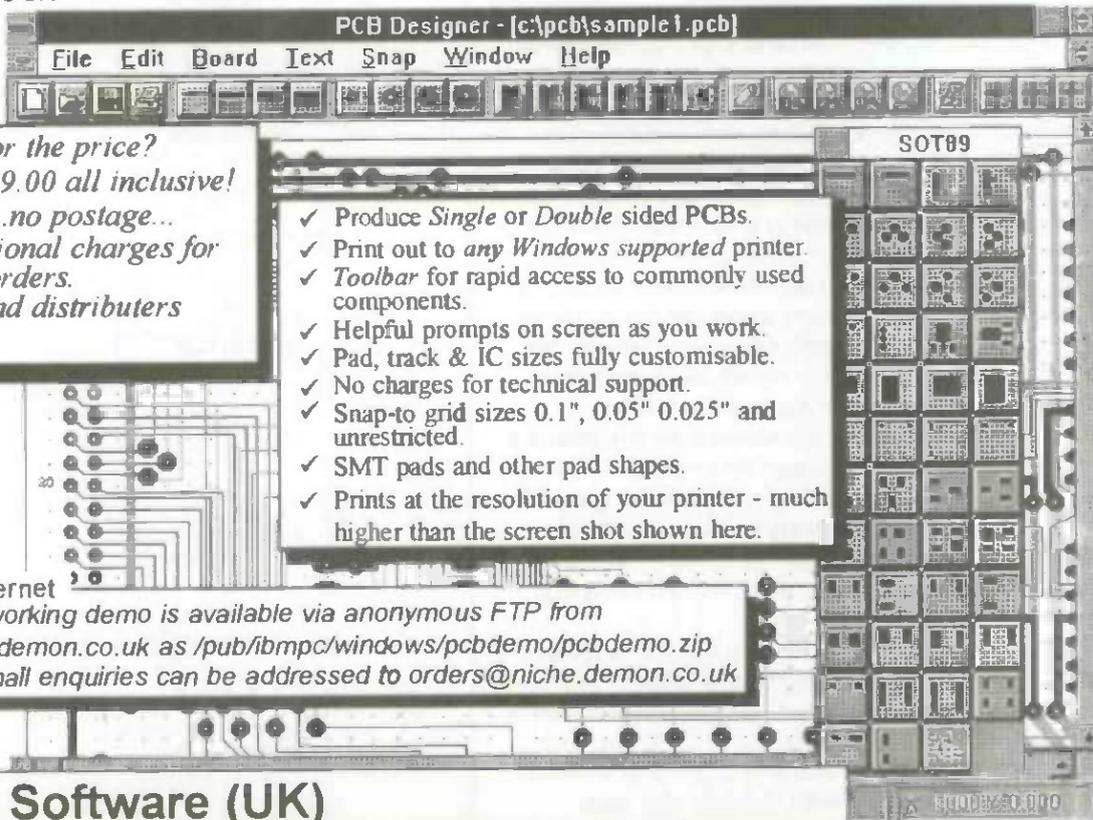Runs on any PC running Windows 3.1 in standard or enhanced mode with 2MB RAM
Will work with any Windows supported printer and monitor



Looking for the price?
It's just £49.00 all inclusive!
...no VAT...no postage...
...no additional charges for
overseas orders.
Dealers and distributors
wanted.

- ✓ Produce Single or Double sided PCBs.
- ✓ Print out to any Windows supported printer.
- ✓ Toolbar for rapid access to commonly used components.
- ✓ Helpful prompts on screen as you work.
- ✓ Pad, track & IC sizes fully customisable.
- ✓ No charges for technical support.
- ✓ Snap-to grid sizes 0.1", 0.05" 0.025" and unrestricted.
- ✓ SMT pads and other pad shapes.
- ✓ Prints at the resolution of your printer - much higher than the screen shot shown here.

Internet
A working demo is available via anonymous FTP from
[ftp://demon.co.uk](ftp://demon.co.uk/pub/ibmpc/windows/pcbdemo/pcbdemo.zip) as /pub/ibmpc/windows/pcbdemo/pcbdemo.zip
e-mail enquiries can be addressed to orders@niche.demon.co.uk

Niche Software (UK)

22 Tavistock Drive, Belmont, Hereford, HR2 7XN.

Phone (01432) 355 414

Designing a PIC Micro controller based project

Bart Trepak concludes his construction of a PIC based alarm clock

PART 6

As discussed earlier in this series, five switches will be required to set our clock (plus the pressure mat) and these have been connected as a 6x1 matrix as shown in Fig 5. During the KEYBD routine, the digit drives are switched off and port line B6 is redefined as an input while the rest of port B remains programmed as outputs. Each output port is then switched high in turn using the BSF instruction and the line B6 read using the BTFSS instruction.

The PRESSURE MAT input is a bit of a problem because, unlike the other keys, it does not have a momentary action and could be on for long periods of time (if you are in bed) and especially during periods when the other keys may have to be read. You may, for example, want to set the alarm time when you are already in bed and the mat "switch" is closed and you will almost certainly want to operate the snooze button next morning when this is the case. During the time that the other keys were being scanned, the output B5 would be at 0 Volts which would have the effect of placing a 1k resistor in parallel with the 10k pull down resistor if the mat switch were closed. This would prevent the voltage at B6, resulting from a possible closure of another switch, from rising above half the supply rail which may not be enough to register as a switch closure. The solution to this is to programme the line B5 as an input (high impedance) during the time when the mat status is not required. This means that even if it is closed it will not affect the voltage at B6 and will not interfere with the operation of the rest of keyboard. Because the reverse would also be true, with operation of other switches preventing the mat status to be read, the lines B0-B4 will also be defined as inputs during the period when the mat switch is read which occurs only during the alarm routine.

The Key scanning flowchart is shown in Fig. 21a and like the CONVRT routine it returns with a number in the W register which depends on the key pressed. If no key is pressed, the routine returns with 00h in the W register. This is written as a subroutine called KEYBD in the final programme and is called from the main routine after the DISPLY routine. The value returned is further processed in the routine marked KEY

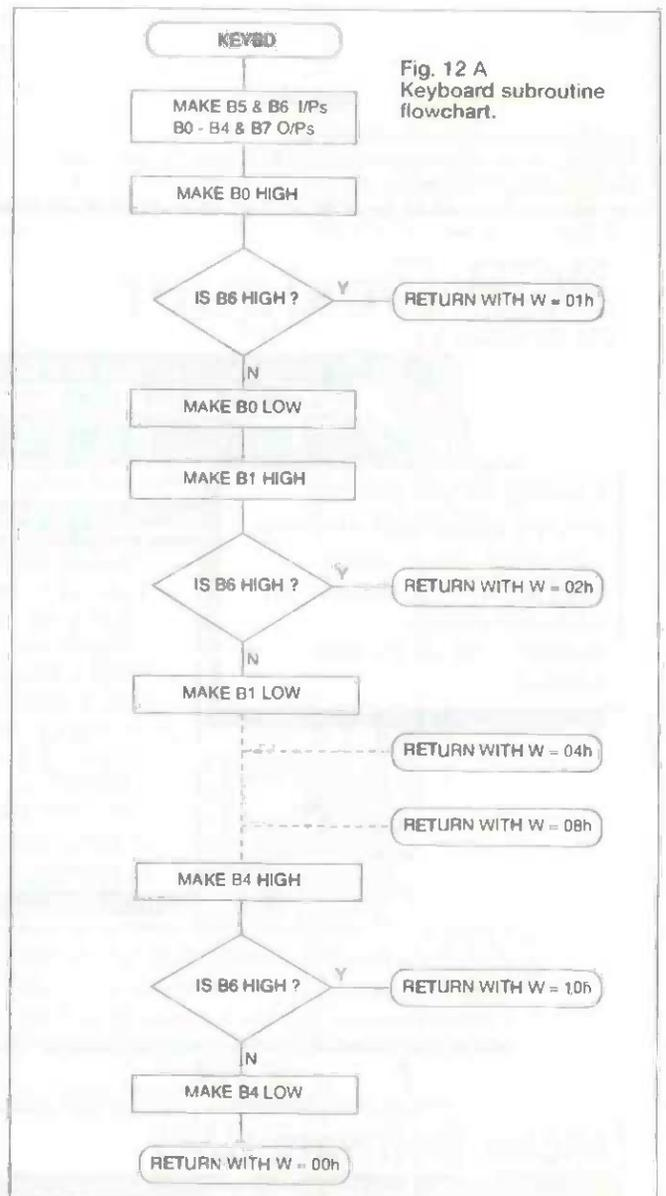


Fig. 12 A
Keyboard subroutine
flowchart.

(FIG.21), where it is compared with the LKP register (Last Key Pressed register defined as 14h) and if it is different, the new value is stored in LKP and the programme goes back to the beginning to display digits and continue counting which takes 10mS and forms the keyboard debounce delay.

If the key currently pressed matches that already stored in the LKP register from the previous scan, bit 0 in a FLAG register (defined as 13h and shown in FIG. 21b) is tested and if it is clear, it is set to one and the function of the key is performed. The next time the subroutine is called, the chances are that the same key will still be pressed so that the LKP register will match the number returned by the KEYBD routine. This time however, bit 0 of the FLAG register will already be set so that the function of the key will be ignored. Only when a 00h is returned when the key is released will bit 0 be cleared enabling a new function (or the same one) to be performed when a key is pressed.

Each key will therefore operate only the first time that it is pressed so that to set 11:15 PM from a display of 12:00 AM, the mode button will have to be pressed until the SET TIME mode is reached (i.e. colon on but not flashing) and the SET HOURS button pressed and released 23 times and the SET MINUTES button 15 times. Although this may seem very time-consuming, it does not take that long and is perhaps not as annoying as the fast set button on some clocks which runs the clock at a faster rate. Here the required setting is invariably missed and the procedure of going through the whole 24 hour sequence has to be repeated. For those interested, the setting method could be converted to this by altering the value loaded into the HSREG and/or TBREG to make the clock count faster and the key processing routine changed to continuously increment the hours or minutes as long as the relevant key were held down. It would make an interesting exercise to gain experience in programming the PIC micro-controller.

The function of each key and the order in which they are scanned is determined by the programme and this could easily be changed to make the controls more (?) logical or easier to lay out on the front panel. Here the switches are numbered S1 to S5 reading from top to bottom of the printed circuit board and the functions assigned to them are SNOOZE, ALARM ON/OFF, MODE SELECT, SET HOURS and SET MINUTES respectively. Initially the programme can be developed with only one function implemented, say SET MINUTES to check that the KEYBD routine is working correctly before the logic for the other switches is worked out.

The switch functions are perhaps best understood with the aid of the flowcharts shown in Fig. 22. The corresponding code for this can again be found in the final programme listing under labels S1 to S5. The set hours and set minutes (S4 and S5) are not shown because they consist simply of calling the subroutines INCRH and INCR and since the appropriate register for the current mode will already have been loaded into the FSR, the correct register for that mode will be incremented. The MODE SELECT function (S3) is shown and is basically also an increment instruction operating on MDREG, but since there are only three modes this register must be reset to zero if a count of three is reached so that only modes 0, 1 and 2 (corresponding to RUN, SET ALARM TIME and SET TIME) are possible. This could easily be changed so that a fourth, fifth or greater mode were possible for setting alternate alarm times or switch off times if required. Note that it is most important that this register is cleared to zero during the initial power-up routine otherwise it could start with an initial value greater than three which would be most confusing - not only to the

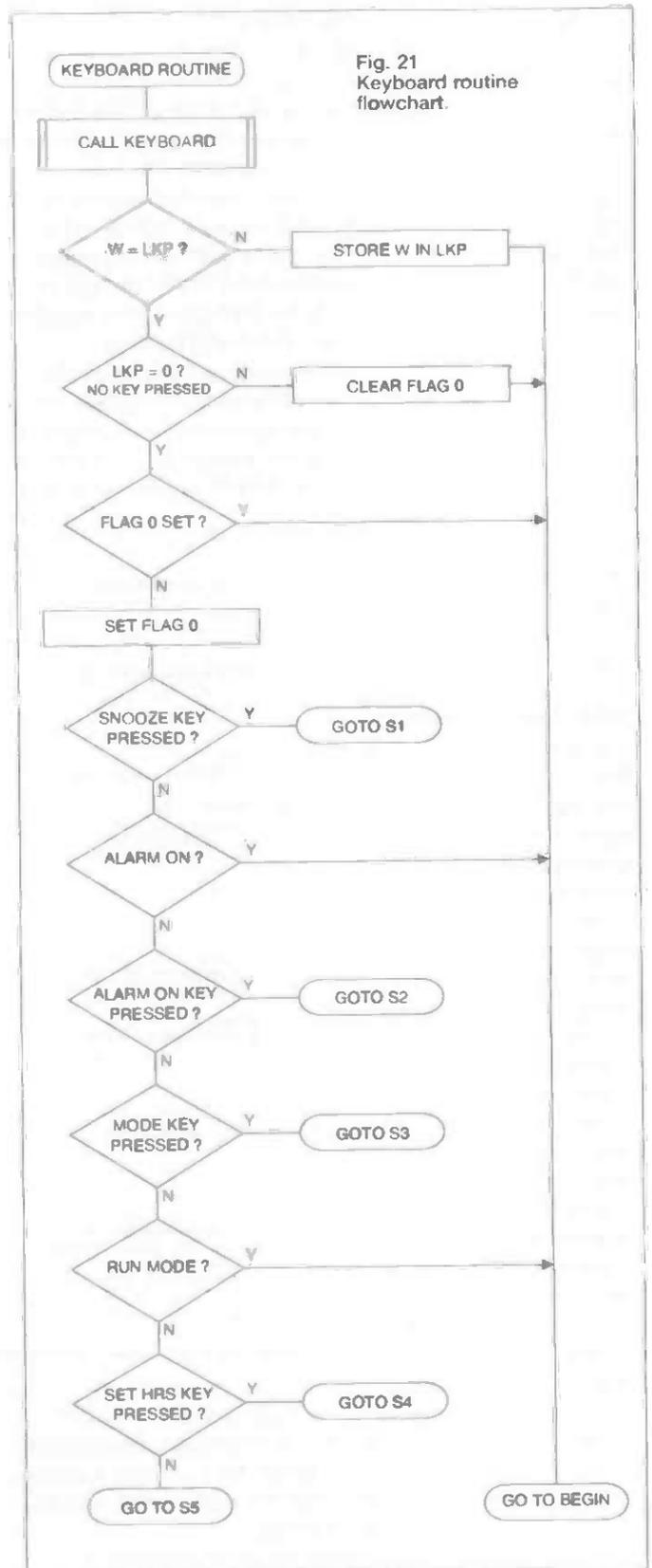


Fig. 21 Keyboard routine flowchart.

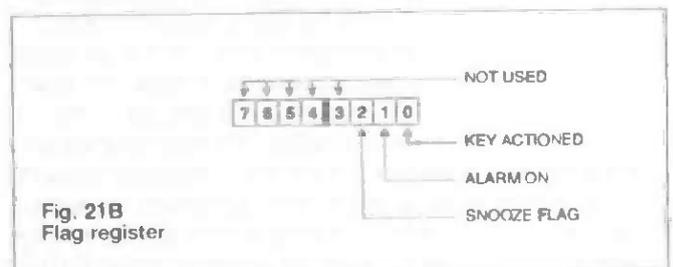


Fig. 21B Flag register

programme but also to the programmer.

The ALARM ON/OFF switch (S2) should only be allowed to operate if the alarm is not already on to prevent the alarm being switched off by pressing this once it has sounded. The alarm output (PORT B7) cannot be used to check this because the alarm may not actually be sounding when the clock is in the alarm mode as it could have been cancelled temporarily by the snooze button or indeed by the occupant getting out of bed. Instead, bit 1 of the FLAG register is set when the alarm time is reached and this is tested instead. Only if this test is passed is the alarm LED (bit 2 in the INDFLG register) toggled. The logic for the SNOOZE switch (S1) is slightly more complicated because it is only allowed to operate once after the alarm has sounded. Another bit in the FLAG register (bit 2) is used to remember if the snooze switch has been pressed by setting it if it is. The effect of pressing the SNOOZE button is to increase the number stored in the TMTMR register by ten but to understand the logic behind this it is first necessary to consider the alarm sounding routine. The flowchart for this function is shown in Fig. 23.

Don't be alarmed

The software development for the clock is now nearing its end and it only remains to design the logic required to actually sound the alarm when required. This is done in the ALRM subroutine, but before we develop the flowchart, it would be best to recap on what is required.

The first step to take before deciding if the alarm is to be sounded is, of course, to see if the current time (as stored in the HRCTR and MINCTR) has reached that stored in the alarm time registers and, indeed, if the alarm has been set in the first place. This can be easily done using the XOR function as discussed before - not only on the hours and minutes counters but also on the INDFLG register which contains AM/PM and alarm ON/OFF information. Because the alarm is to be maintained, if necessary, for more than a minute, a successful initial comparison should be noted after which the registers need no longer be compared.

Since the alarm is to remain active for ten minutes, a separate counter (TMTMR or Ten Minute TiMeR designated 15h and loaded with .10 when the above registers match) is decremented at the same time as the MINCTR is incremented, and this is used to time the alarm interval. This has not been shown on the flowchart as it belongs more properly to the INCR (increment counters) subroutine. The code for this has been added to the beginning of the INCR subroutine shown in Fig. 24. Operating the SNOOZE switch postpones the alarm for a period of ten minutes by adding another ten to the above counter when this switch is pressed using the "addwf TMTMR"

instruction. The alarm is then potentially activated only if the count remaining in this timer is less than ten minutes, but made inactive if it is greater than this which would be the case if the SNOOZE button had been pressed. Since only one operation of the SNOOZE button is allowed during each alarm period, more than ten cannot be added by repeatedly pressing this switch.

Assuming that the time remaining in the TMTMR register is less than ten minutes, the alarm would still only be required if the occupant were still in bed so the mat switch would need to be tested at this point. The alarm would only be cancelled when the count in the TMTMR reached zero which would take ten minutes so that before this happened, any return to bed would immediately restart the alarm. By this time, it is hoped, the owner would be well and truly awake.

Finally, because a pulsed alarm is more effective than a continuous tone at waking people from their slumbers, the

output is switched on only if the colon is on resulting in the alarm being switched on and off every half a second.

The flowchart for this is shown in Fig. 23 and it should now be quite easy to code using the mnemonics given in Fig. 3. The only new technique required is how to determine if the contents of the TMTMR register are less than ten. The simplest way to do this is to load ten into the W register and subtract it from TMTMR using the "subwf TMTMR,w" instruction, having first set the carry bit in the STATUS register. If TMTMR contains a value of ten or less, the carry bit in the STATUS register (bit 0) will be cleared indicating that a "borrow" has occurred, while, if the value is greater it will remain set.

Although not used here, by loading W with the contents of another register, this technique could be used by extension to compare two registers to decide which of the two was greater or smaller or by testing the zero bit

(bit 2) if they were equal. The SUBWF instruction could therefore also be used to test equality instead of the XOR instruction used earlier.

The listing for this part of the programme is shown at the label ALRM in Fig. 24 which is the complete listing for the alarm clock. Note the additions to the list of "equ" statements at the beginning of the programme and the changes in the INILTLSE routine which now contains the initial conditions required in all the relevant registers to ensure that at switch on, the initial time stored is 12:00 AM with the clock in the RUN mode and the alarm time set to 12:00 AM but disabled.

Because the ALRM routine drives port B7 which has to be on continuously while the alarm is to sound, the DISPLY routine which also shares the rest of the port B lines must be altered to make sure that B7 is not reset when the LED displays are switched on and off. In the original listing for this routine (Fig.

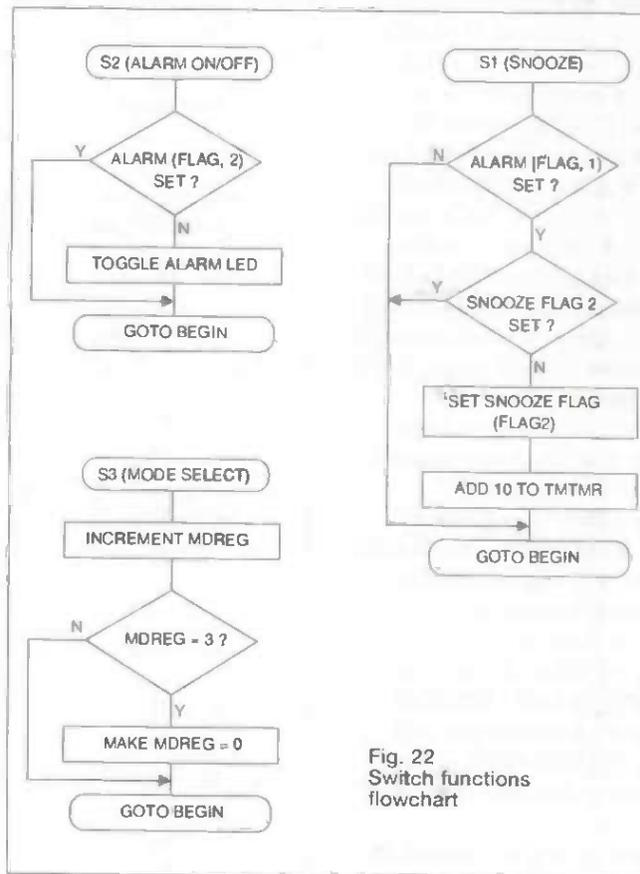


Fig. 22
Switch functions
flowchart

13) the value returned from the CONVRT routine was simply re-written to port B to switch the appropriate display segments on. Since bit 7 in the CONVRT table is always zero as it does not drive any segment, it would be reset as soon as the DISPLY routine was called. One way around this would be to have two look-up tables with one having bit 7 set and the other cleared. Then choose which table to use depending on whether the alarm was to sound or not. The solution adopted here is to "inclusive or" the data from the look-up table with port B using the IORWF PORTB, same instruction which loads the seven segment data into the port while leaving B7 unchanged, instead of the original MOVWF instruction. For this to work, however, the other bits in port B must first be reset; otherwise, data from the last digit displayed would be mixed with the new data. All outputs except B7 are therefore cleared using an ANDLW instruction before the digit is displayed which accounts for the slightly longer DISPLY routine in the final version of the programme compared with that originally shown.

Around and around


This ends our series as far as the "Digital Clock for the Unemployed" is concerned and it only remains to programme a chip and plug it into the socket on the board to complete it. The software has been fully described and many other techniques mentioned so it should be an easy matter to modify the design to, say, take week-ends and even public holidays into account or to allow two (or more?) snooze operations before the alarm sounds constantly. Many of the routines could be used as they are or slightly modified for other projects where, say, a keyboard and/or a display is required. In some cases, even the printed circuit board may remain the same!

Perhaps the only major instructions listed in Fig. 3 not used in this series are the "Rotate Left Through Carry" and "Rotate Right Through Carry" instructions (RLF f,d and RRF f,d). The operation of both of these is similar and quite simple to

understand although their uses may not be so obvious. The RLF f,d instruction, for example, takes the value of the most significant bit in the register "f" and places it into the carry bit in the STATUS register while the value of the carry bit is pushed into the least significant position and all the other bits are also shifted one place to the left. This is shown in Fig. 25, along with the corresponding situation for the RRF f,d instruction, which depicts the contents of a register before and after these instructions have been executed.

One application of these instructions is to shift information serially out of an I/O pin in, say, a remote control transmitter application. After every shift operation, the carry bit in the STATUS register (bit 0) could be tested and the relevant I/O port bit set or cleared using the "BSF f,b" or "BCF f,b" as required. A similar routine could then read an input pin and set or clear the carry bit and shift this into a register to reproduce the transmitted word at the receiver. A separate output on the transmitter could be used to synchronise the shift operation at the receiver to keep the two in step or the received signal sampled at precise time intervals provided that the clocks in the transmitter and receiver were stable enough for the application. This is not the only use of these instructions, however. Just as with normal decimal numbers, where shifting the position of the digits one place to the left is equivalent of multiplying the number by ten while shifting them one place to the right effectively divides it by ten, with binary numbers the effect is similar except that the value is not increased or decreased by a factor of ten but two. The RLF instruction can therefore be used as a convenient way to multiply a number stored in a register by two (provided that the carry bit is first cleared) while the RRF can be used to divide it by two. Care must be taken to ensure that the carry bit is taken into account if necessary. Successive shifts will multiply or divide the original number by 4, 8 and so on provided an overflow (or underflow) does not occur.

Fig. 23 Alarm subroutine flowchart

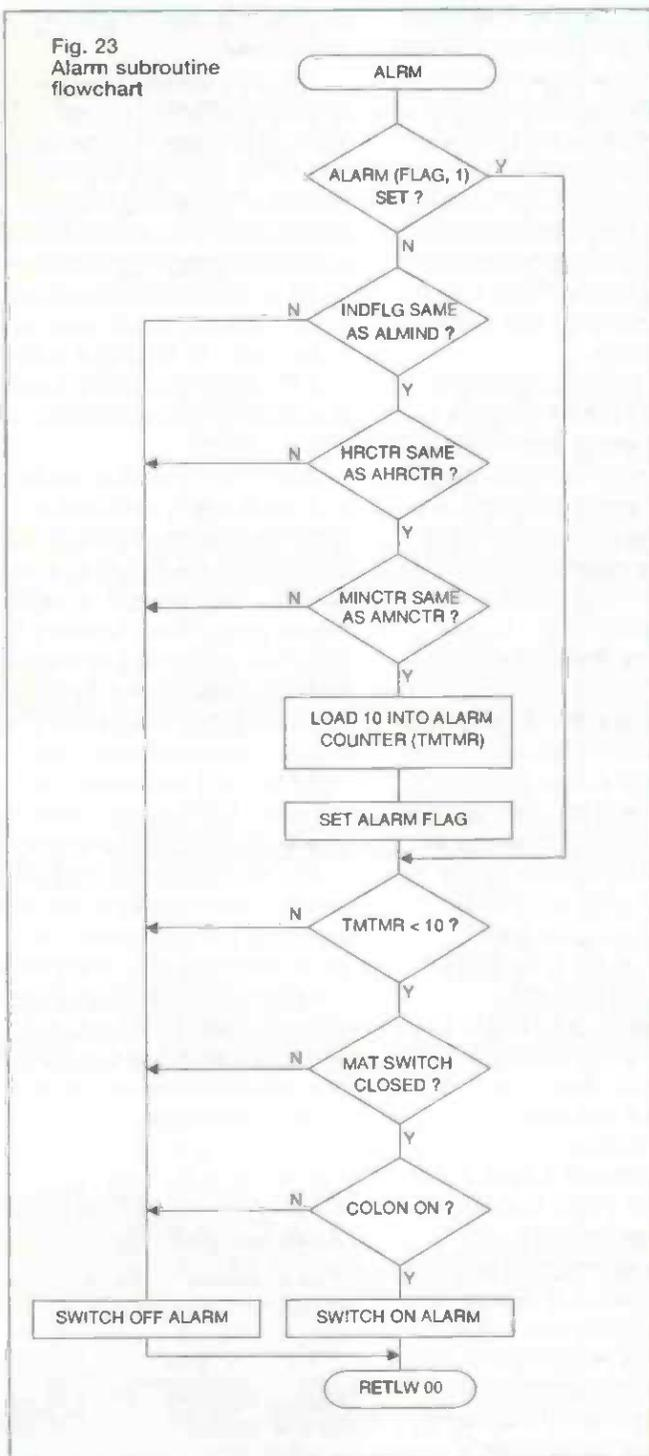

PIC and mix

This series of articles has only scratched the surface of the possibilities opened up by designing with micro-controllers. The PIC16C5X series has many other features which have not been used in the clock project but which can be useful in other applications.

All the devices in the series have, for example, a Watch Dog Timer (WDT) which runs independently of the main clock and will reset the processor every 18mS or so. This time can be extended by assigning the prescaler to the WDT, although not if it is already being used by the RTCC register. In use, the CLRWDT (Clear Watch Dog Timer) instruction is inserted into the programme so that this instruction will normally be executed before the WDT times out, ensuring that the processor is not reset. If due to noise, or other malfunction, the contents of a memory location get corrupted or for some other reason the programme crashes, the WDT will time out because the CLRWDT instruction will no longer be executed regularly or at all and the processor will be reset allowing it to restart the programme correctly. By reading certain bits in the STATUS register, the programme can differentiate between a reset caused by the WDT and the reset which occurs when power is first applied. This means that overwriting any previously stored conditions by the normal initialisation routine can be avoided. This feature is useful in electrically noisy environments such as cars or applications where a programme malfunction could have bad or even dangerous consequences.

If this function is not used, the WDT must be disabled by suitably programming the Configuration EPROM. This is not part of the main EPROM used for programme storage and consists of four bits. Two are used to select the clock type (i.e. RC, crystal etc.) one disables the WDT when set to zero while the fourth bit, when set to zero, prevents the contents of the programme memory being read out in a meaningful way - thus preventing someone from copying your design. To help with identifying programmed and code protected chips, there is also another 16 bit EPROM which can be programmed with a user identification code.

Another useful feature is the ability to put the circuit to sleep by executing the SLEEP instruction. This switches off the clock and shuts down the circuit so that current consumption falls to only a few micro-amps making it very useful in battery powered applications and eliminating the need for an on/off switch. In this condition, the output pins remain in their previously set conditions as inputs or outputs driving high or low and the WDT (if it is enabled) keeps running. The circuit may be awakened by a WDT time out or a reset pulse to the MCLR pin. Again, bits in the STATUS register can be read to determine what caused the device to wake up and the programme executed accordingly. This feature can be used in remote control transmitters for example where the circuit needs to be switched on when a key is pressed and switch off automatically when the transmission is finished.

Perhaps the best thing about the PIC series is the fact that the EPROM versions are also available at greatly reduced prices in a plastic package without the window. This, of course, means that the device can only be programmed once (One Time Programmable or OTP) and cannot be erased so it is not suitable for developing new programmes but is ideal for use in a finished project enabling the EPROM part to be used again to develop a new application. The only limitation is that the oscillator type is not programmable in the OTP device so that the required type must be purchased but even this is about to change.

We should at least mention two other members of the PIC16CXX family which share all of the features of the PIC16C5X. These include virtually the same instruction set but also have more advanced features such as interrupts and a deeper stack enabling more subroutines to be nested i.e. called from within subroutines. They also have some hardware

features which will make them useful in more advanced applications.

The first of these is the PIC16C71 which has a built in A/D converter and a four way input multiplexer. This could be used, for example, to measure and display temperature at four different locations. The obvious application which springs to mind is to measure and display the house temperature and use this to control the heating while the other channels could measure the freezer, greenhouse and hot water temperatures and sound an alarm if the temperature moves outside the preset levels.

The other device is the PIC16C84 which has an EEPROM programme memory instead of the EPROM of the 16C5X series. This enables the device to be reprogrammed electrically without first erasing it with UV light which can make the whole process of developing programmes a lot faster. As well as this, the PIC16C84 has a small EEPROM memory which can be written to during programme execution. This enables the device to retain data even when the circuit is switched off. This can be extremely useful in some applications (e.g. milometers, digital locks - or keeping a running total of grass cut to date in that all-singing, all-dancing lawnmower perhaps?) and removes the need for back-up batteries when non-volatile storage of data is required.

Both of these devices are available in 18 pin DIL packages and use the same mnemonics (and to a large extent the same architecture) as the PIC16C54 micro-controller described together with one or two new instructions to support the new functions. This makes it very easy to "upgrade" to these or convert programmes from one device to another. The PICSTART programmer and software can also be used to develop programmes and programme these devices, despite the fact that they have a 14-bit wide programme memory instead of the 12-bit one of the earlier device making the PICSTART-16B even better value for money. The down side is, of course, that they cost more but still not as much as an equivalent CMOS design would cost - even if you could build it.

The trouble with technology is that it always seems to create as many problems as it solves. With all these micro-controllers at my disposal, I find that far from not being able to get up in the morning, I now cannot get to sleep thinking about my next project! The Alarm Clock has fallen into disuse (by me, at any rate) and as for watching soap operas, I find myself still looking at a screen all day but the programmes on mine are rather different compared to those on the other screen in the corner of the lounge.

FIG 24 - COMPLETE PROGRAMME FOR ALARM CLOCK

```

;
;*****
;*****
;
MDREG equ 08h          ; MoDe REGister -
RUN=0, SET ALARM=1, SET TIME=2
MINCTR equ 09h        ; MINute DiSPlay
HRCTR equ 0Ah         ; HouR DiSPlay
INDFLG equ 0Bh        ; INDicator FLAg holds
status of AM/PM, COLON & ALARM
DYCTR1 equ 0Ch        ; DelaY CounTer 1
DYCTR2 equ 0Dh        ; DelaY CounTer 2
HSCTR equ 0Eh         ; Half Second CounTer
TBCTR equ 0Fh         ; Time Base CounTer -
counts 120 half seconds
AMNREG equ 10h        ; Alarm MiNute REGister
AHRREG equ 11h        ; Alarm HouR REGister
AINDFG equ 12h        ; Alarm INDicator FlaG

```

```

; FLAG equ 13h ; FLAG register 0=KEY
; DTIONED
; KP equ 14h ; Last Key
; pressed register
; TMTMR equ 15h ; Ten Minute TiMER -
; counts alarm and snooze time
;
; LIST P=16C54 ; f=inhx16
; INCLUDE "PIC.H"
; *****
; *****
; goto START
; *****
; *****
; DISPLY movlw 00h
; tris PORTA
;
; make port A o/p
; tris PORTB
;
; make port B o/p
; clrf PORTA
;
; switch off digit drives
; movlw 80h
;
; ie 1000 0000
; andwf PORTB,same
;
; clear PORTB except B7
; *****LED DISPLAY SUBROUTINE*****
;
; swapf 0,w
;
; load tens of mins into w
; andlw 0Fh
;
; mask MSDs by ANDing with 0000 1111
; call CONVRT
;
; no - decode segments
; iorwf PORTB
;
; switch on segment drive
; bsf PORTA,0
;
; switch on digit drive
; call DLY
;
; delay for
; bcf PORTA,0
;
; switch off digit drive
; movlw 80h
;
; ie 1000 0000
; andwf PORTB,same
;
; clear PORTB except B7
;
; movf 0,w
;
; load units of mins into w
; andlw 0Fh
;
; select units of mins for display
; call CONVRT
;
; decode segments
; iorwf PORTB
;
; switch on segment drive
; bsf PORTA,1
;
; switch on digit drive
; call DLY
;
; delay for
; bcf PORTA,1
;
; switch off digit drive
; movlw 80h
;
; ie 1000 0000
; andwf PORTB,same
;
; clear PORTB except B7
;
;
; incf FSR,same
;
; increment FSR to point to
; Hours
;
; swapf 0,w
;
; Swap counter pointed to by FSR(10's HRS)
; andlw 0Fh
;
; mask MSDs by ANDing with 0000 1111
; btfss STATUS,2
;
; is digit zero? ie STATUS,2 is set
; call CONVRT
;
; no - decode segments(skipped if digit=0)
;
;
; incf FSR,same
;
; point to indicator flag
; register

```

```

; iorwf 0,w
; add colon (to be modified later)
; decf FSR,same
;
; reset pointer
;
; iorwf PORTB
;
; switch on segment drive
; bsf PORTA,3
;
; switch on digit drive
; call DLY
;
; delay for
; bcf PORTA,3
;
; switch off digit drive
; movlw 80h
;
; ie 1000 0000
; andwf PORTB,same
;
; clear PORTB except B7
;
;
; movf 0,w
;
; load counter pointed to by FSR
; andlw 0Fh
;
; select units of hours for display
; call CONVRT
;
; decode segments
; iorwf PORTB
;
; switch on segment drive
; bsf PORTA,2
;
; switch on digit drive
; call DLY
;
; delay for
; bcf PORTA,2
;
; switch off digit drive
; movlw 80h
;
; ie 1000 0000
; andwf PORTB,same
;
; clear PORTB except B7
;
;
; decf FSR,same
;
; reset pointer
; retlw 00
;
; RETURN FROM SUBROUTINE
; *****
; *****
; CONVRT addwf PC,same
; *****BCD-7SEG CONVERSION SUBROUTINE*****
;
; retlw 3Fh
;
; segment drives for 0
; retlw 12h
;
; segment drives for 1
; retlw 4Fh
;
; segment drives for 2
; retlw 57h
;
; segment drives for 3
; retlw 72h
;
; segment drives for 4
; retlw 75h
;
; segment drives for 5
; retlw 7Dh
;
; segment drives for 6
; retlw 13h
;
; segment drives for 7
; retlw 7Fh
;
; segment drives for 8
; retlw 77h
;
; segment drives for 9
; *****
; *****
;
; DLY movlw .4
; *****DELAY ROUTINE*****
;
; movwf DYCTR1
;
; load DYCTR1 with 4 decimal
; D1 movlw .100
; movwf DYCTR2
;
; load DYCTR2 with 100 decimal
; D2 decfsz DYCTR2,same
;
; decrement and skip if zero
; goto D2
;
; if not zero
;
; decfsz DYCTR1
;
; decrement DYCTR1 if DYCTR2 is zero
; goto D1
;
; reload DYCTR2 if DYCTR1 is not zero

```

```

                retlw 00
; RETURN FROM SUBROUTINE if DYCTR1 is zero
;*****
;*****
;
INCR            nop
;*****INCREMENT COUNTERS SUBROUTINE*****
                movf TMTMR,same
                btfsc STATUS,2
; is TMTMR =0 ?
                goto INCR1
; TMTMR is zero - cancel alarm
                decf TMTMR,same
; not zero - decrement
                goto INCRM
;
INCR1           bcf FLAG,1
;
; clear Alarm time reached
flag
                bcf FLAG,2
; clear SNOOZE key pressed flag
;
INCRM           incf 0,same
; INCREMENT MINUTES - POINTED TO BY FSR
                movf 0,w
                andlw 0Fh
; and with 0000 1111 to mask MS bits
                xorlw 0Ah
; compare with Ah (10 decimal)
                btfss STATUS,2
                retlw 00
; not = 10
                movlw 06h
; equal to 10
                addwf 0,same
; add 6 to file pointed to by FSR
                movf 0,w
; place in W register
                xorlw 60h
                btfss STATUS,2
; equals 60?
                retlw 00
; no
                clrf 0
; set to zero
;
                movf MDREG,same
                btfss STATUS,2
; RUN mode? bit will be set if it is
                retlw 00
; no - do not change hours
;
INCRH           incf FSR,same
; change pointer to hour
register
                incf 0,same
; INCREMENT HOURS
                movf 0,w
                andlw 0Fh
; mask MS bits
                xorlw 0Ah
; compare with Ah (10 decimal)
                btfss STATUS,2
                goto CHECK1
; not = 10 - check if counter = 12
                movlw 06h
; equal to 10
                addwf 0,same
; add 6 to file pointed to by FSR
;
CHECK1          movf 0,w
; COUNTER EQUALS 12?
                xorlw 12h
                btfss STATUS,2
; equals 12?
                goto CHECK2
; no - check if counter = 13
                incf FSR,same
; change pointer to
indicator register
                movlw 40h
; ie 0100 0000
                xorwf 0,same

```

```

                toggle AM/PM flag
                retlw 00
;
CHECK2          movf 0,w
; COUNTER EQUALS 13?
                xorlw 13h
                btfss STATUS,2
                retlw 00
; no
                movlw 01h
; yes
                movlf 0
; set hours register to 01
                retlw 00
;
;*****
;*****
KEYBD           movlw 60h
;*****KEY READIND ROUTINE*****
                tris PORTB
; make B0-B4 & B7 o/ps and B5 & B6 inputs
                movlw 80h
; ie 1000 0000
                andwf PORTB,same
; clear bits 0-6 B7 does not change
;
                bsf PORTB,0
; set B0 high
                nop
                btfsc PORTB,6
; B6 high?
                retlw 01h
; S1 pressed
                bcf PORTB,0
; no - clear B0
;
                bsf PORTB,1
; set B1 high
                nop
                btfsc PORTB,6
; B6 high?
                retlw 02h
; S2 pressed
                bcf PORTB,1
; no - clear B1
;
                bsf PORTB,2
; set B2 high
                nop
                btfsc PORTB,6
; B6 high?
                retlw 04h
; S3 pressed
                bcf PORTB,2
; no - clear B2
;
                bsf PORTB,3
; set B3 high
                nop
                btfsc PORTB,6
; B6 high?
                retlw 08h
; S4 pressed
                bcf PORTB,3
; no - clear B3
;
                bsf PORTB,4
; set B4 high
                nop
                btfsc PORTB,6
; B6 high?
                retlw 10h
; S5 pressed
                bcf PORTB,4
; no - clear B4
;
                retlw 00
; no keys pressed
;
;*****
;*****

```

```

ALRM          nop
;*****ALARM SUBROUTINE*****
;   has alarm time been reached?
;           btfsc FLAG,1
;           goto CHKTMR
yes - check if TMTMR is zero
;           movf AINDFG,w
;           no
;           xorwf INDFLG,w
;           compare INDFLG with AINDFG
;           btfss STATUS,2
;           goto NOALRM
not the same - switch off alarm
;           movf HRCTR,w
;           xorwf AHRREG,w
;           compare hours
;           btfss STATUS,2
;           goto NOALRM
not the same - no alarm
;           movf MINCTR,w
;           same
;           xorwf AMNREG,w
;           compare minutes
;           btfss STATUS,2
;           goto NOALRM
not the same - no alarm
;           movlw .10
;           same - alarm time reached
;           movwf TMTMR
load Ten minute timer with 10
;           bsf FLAG,1
;           set ALARM TIME flag
;
CHKTMR        bsf STATUS,0
set carry bit
;           movlw .10
;           check if TMTMR is less than 10
;           subwf TMTMR,w
;           btfsc STATUS,0
;           is carry bit reset? ie. result negative
;           goto NOALRM
no - time > 10 mins - SNOOZE
;           movlw 5fh
;           yes - snooze is over - check mat
;           tris PORTB
;           make B5 and B7 o/p all others i/p
;           bsf PORTB,5
;           make B5 high
;           nop
;           test B6
;           btfss PORTB,6
;           goto NOALRM
mat not closed - no alarm
;           btfss INDFLG,0
;           is colon on?
;           goto NOALRM
no - makes alarm switch off for 0.5sec
;           bsf PORTB,7
;           switch on alarm
;           retlw 00
;
NOALRM        bcf PORTB,7
;           switch off alarm (B7)
;           retlw 00
;
;*****
;
START         nop
;
;*****INITIALISE ROUTINE*****
INTLSE        movlw 00h
;           ie 0000 0000
;           tris PORTA
;           make PORTA o/p
;           movwf PORTA
;           make PORTA 0000
;           tris PORTB
;           make PORTB i/p except B4
;           movlw 07h
;           ie 0000 0111
;           OPTION

```

```

;   int signal, L to H, presclr 256 to RTCC
;           movlw .224
;           move 244 decimal into
;           movwf RTCC
;           RTCC - gives 10ms with 3.2768Mhz xtal
;
;           movlw 12h
;           movwf HRCTR
;           load HRCTR with 12
;           movwf AHRREG
;           movlw 04h
;           movwf MINCTR
;           load MINCTR with 00
;           movwf AMNREG
;           movlw 04h
;           movwf AINDFG
;           set AINDFG to AM, colon off and alarm on
;           clrf MDREG
;           set MDREG to 0 ie. run mode
;           movlw .50
;           movwf HSCTR
;           load HSCTR with 50 dec to count halfsecs
;           movlw .120
;           load TBCTR with 2 (temporary) so that
;           movwf TBCTR
;           clock runs faster (change to 120 later)
;           clrf INDFLG
;           INDFLG = am, colon and alarm off
;           clrf FLAG
;           clrf TMTMR
;
BEGIN         movf RTCC,w
;           btfss STATUS,2
;           test if w (RTCC) = 0
;           goto BEGIN
;           w (RTCC) not zero
;
;           movlw .224
;           if RTCC=0 move
;           movwf RTCC
;           224 dec. into RTCC
;
MODE         movf MDREG,w
places MDREG into w
;           btfsc STATUS,2
;           test if MDREG=0
;           goto RUN
;           yes
;           xorlw 01h
;           no - XOR MDREG (w) with 01h
;           btfsc STATUS,2
;           test if MDREG=1 = Z bit will be set if
;           it is
;           goto SETARM
;           yes
;
SETTIM        movlw 09h
;           no - set time routine
;           movwf FSR
;           set pointer to time registers
;           bsf INDFLG,0
;           switch colon on
;           goto PROG
;
SETARM        movlw 10h
;           set alarm routine
;           movwf FSR
;           set pointer to Alarm registers
;           goto PROG
;
RUN           movlw 09h
;           RUN ROUTINE
;           movwf FSR
;           load address of MINCTR into FSR
;
;           decfsz HSCTR,same
;           goto RUNEND
;           if HSCTR not zero go to RUNEND
;           movlw .50
;           movwf HSCTR
;           if zero - reload with 50 dec
;           movlw 01h

```

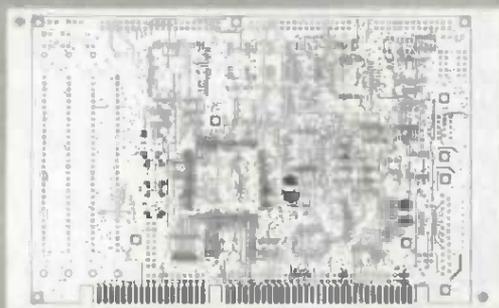
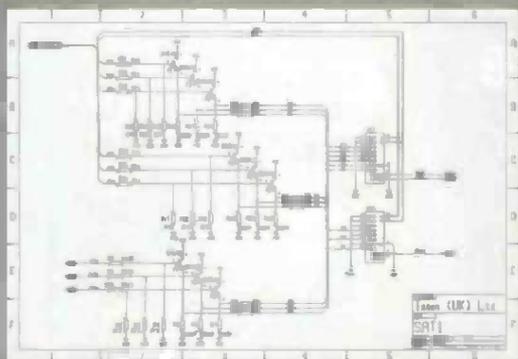

Is your PCB design package not quite as "professional" as you thought? Substantial trade-in discounts still available.

Board Capture

Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single-sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2

£395



BoardMaker

BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

£95

BoardMaker2 - Advanced level

- All the features of BoardMaker1
- Full netlist support- BoardCapture, OrCad, Schema, Tango, CadStar
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator- Database ASCII, BOM
- Thermal power plane support with full DRC

£395

Board Router

Gridless re-entrant autorouter


- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing

£200


Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

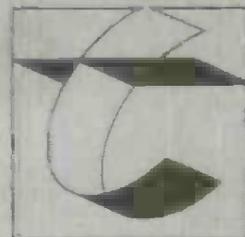For further information contact
Tsien (UK) Limited
 Aylesby House
 Wenny Road, Chatteris
 Cambridge, PE16 6UT
 Tel 01354 695959
 Fax 01354 695957
 E-mail Sales@tsien.demon.co.uk



tsien

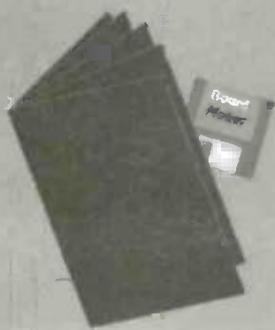

Seasonal Savings

Subscribe today and take your pick from Britain's favourite hobby magazines.

This may be the toughest decision you will make this Christmas... Should you ensure your special friends don't miss out on super subscriptions to their favourite magazines? OR spoil yourself with a gift you deserve at a price that won't bite? With these irresistible offers plus price frozen rates you can probably afford to do both.



The more you spend the more you save!!!



It's Your Choice Super savings.

Save Once
Subscribe now and receive up to 5 extra issues free!

Save Twice
What's more, subscribe to more than one magazine and we'll give you a fantastic free binder! What could be better?



FREE



WORTH
£6.95

BINDER

Save Three Times!
In addition, for this offer only, we've kept the Summer 1995 prices so you'll beat any future price rises until 1998 with a two year subscription.


The Best Gets Better!
The Perfect Gift For Everyone, Including You!!

Our binders hold up to 12 issues of your favourite magazine and keep them looking fresh and tidy. Now you'll know just where to look for a new idea or project.

Don't Delay, Fill out our priority order form on the next page TODAY

Order now - From the comfort of your armchair

Five Simple Steps to a Good Read....

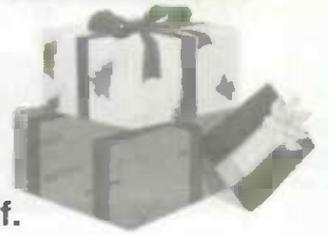

- Just tick ✓ the relevant box for a 1 or 2 year subscription.
- Then tick ✓ the magazines you wish to subscribe to.
- Remember to tick ✓ the box for a gift subscription or for yourself.
- If you have ordered more than one subscription don't forget to tell us which binder you require.
- Fill in the coupon with all your details and send this page with your payment to the address below. Then sit back and look forward to a good read.



Your Exclusive Christmas Subscription Order Form

ONE YEAR

One year subscription tick here <input type="checkbox"/>		U.K.	Europe & Eire	Sterling O/Seas	U.S.\$	Extra issues	Saving per issue on today's cover price
Gift Subscription	Your Subscription						
<input type="checkbox"/> AW15	<input type="checkbox"/> Archimedes World	£45.00	£56.00	£58.00	\$104.00	12 + 2 extra issues	54p
<input type="checkbox"/> ET12	<input type="checkbox"/> Electronics Today Int.	£25.80	£34.70	£36.20	\$54.00	12 + 2 extra issues	41p
<input type="checkbox"/> HR13	<input type="checkbox"/> Ham Radio Today	£21.60	£28.40	£29.60	\$53.00	12 + 2 extra issues	46p
<input type="checkbox"/> CB13	<input type="checkbox"/> Citizens' Band	£21.60	£25.80	£26.50	\$48.00	12 + 2 extra issues	41p

TWO YEARS

Two year subscription tick here <input type="checkbox"/>		U.K.	Europe & Eire	Sterling O/Seas	U.S.\$	Extra issues	Saving per issue on today's cover price
Gift Subscription	Your Subscription						
<input type="checkbox"/> AW16	<input type="checkbox"/> Archimedes World	£90.00	£112.00	£116.00	\$208.00	24 + 5 extra issues	65p
<input type="checkbox"/> ET13	<input type="checkbox"/> Electronics Today Int.	£51.60	£69.40	£72.40	\$108.00	24 + 5 extra issues	45p
<input type="checkbox"/> HR14	<input type="checkbox"/> Ham Radio Today	£43.20	£56.80	£59.20	\$106.00	24 + 5 extra issues	52p
<input type="checkbox"/> CB14	<input type="checkbox"/> Citizens' Band	£43.20	£51.60	£53.00	\$96.00	24 + 5 extra issues	47p

Claim for your free binder here. ONLY if you have subscribed to more than one magazine.
 Please state which binder you would prefer 027 Archimedes World 028 Electronics Today Int.
 029 Ham Radio Today 030 Citizens' Band

Please commence my subscription(s) from the next available issue.

If renewing/extending please quote subscription number.....

I enclose my Cheque/P.O. for £ made payable to Nexus

or please debit my Access/Visa account:

**ORDER
HOTLINE**
01858 435344

Expiry Signature

Name: Mr/Mrs/Miss Initial Surname

Address:

Post Code

Gift Subscription Name: Mr/Mrs/Miss Initial Surname

Address:

Post Code

Photocopies of this page are acceptable. Not to be used in conjunction with any other offer.

This offer is open to all readers - until 1st February 1996.


Please post this coupon to: Nexus Subscription Services, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire LE16 9EF.

Please tick this box if you would prefer not to receive mail from other companies which may be of interest to you


ETI

ELECTRONICS
TODAY INTERNATIONAL


FOILS FOR THIS ISSUE

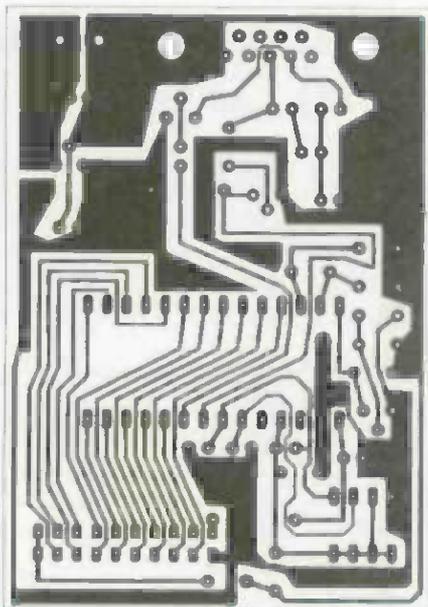


Basic for the pic
microcontroller

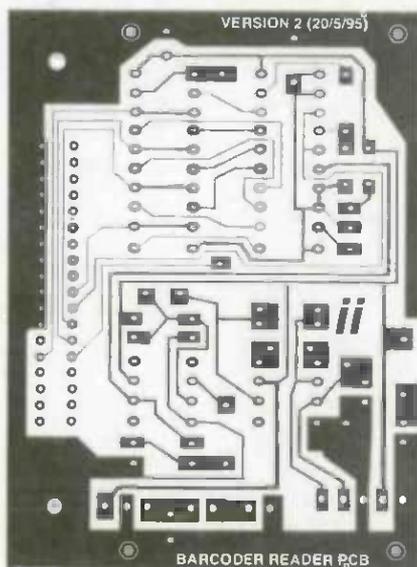


Bar code reader

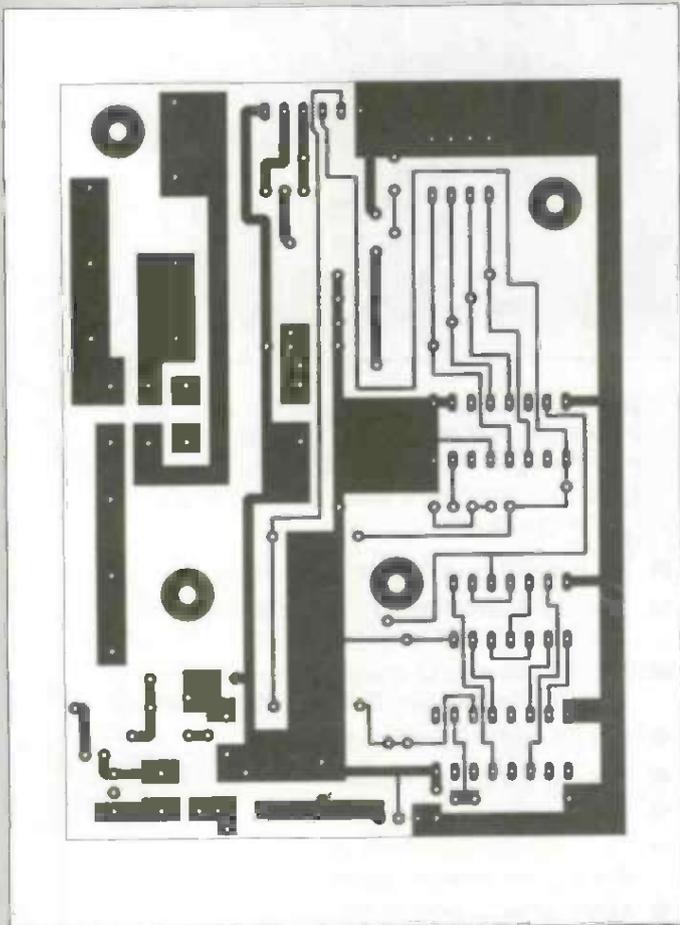

Timed isolator

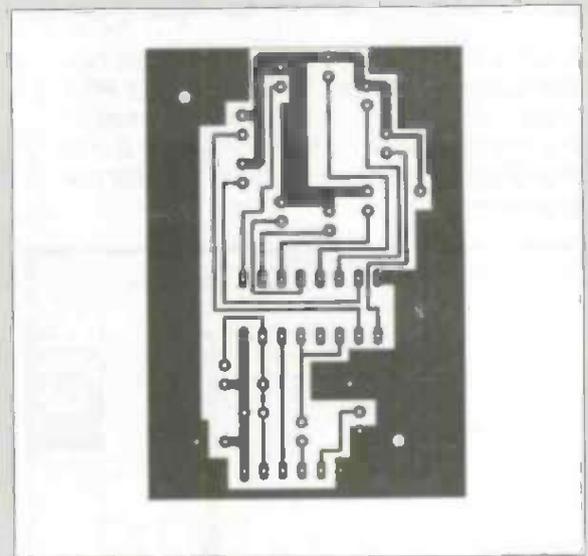


Timed isolator

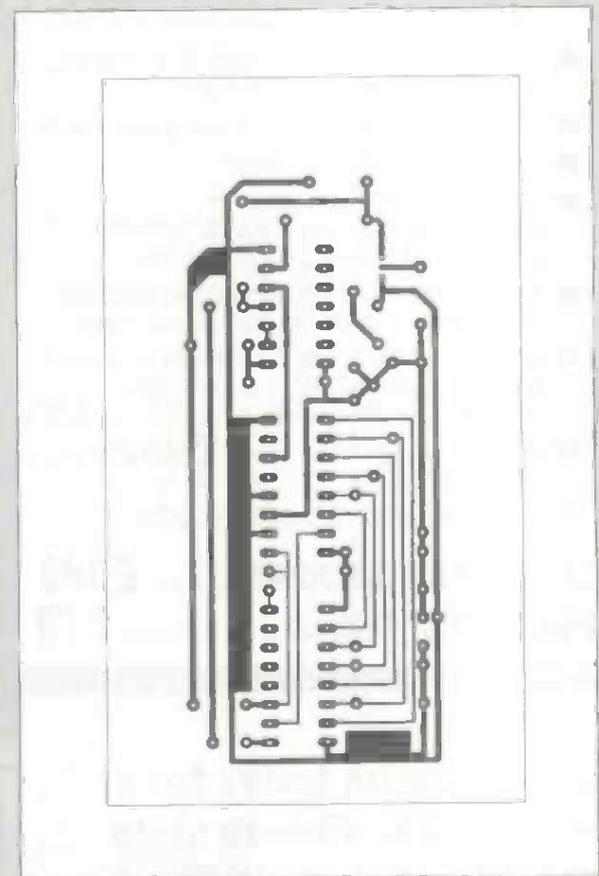

Bicycle alarm

CADPAK for Windows

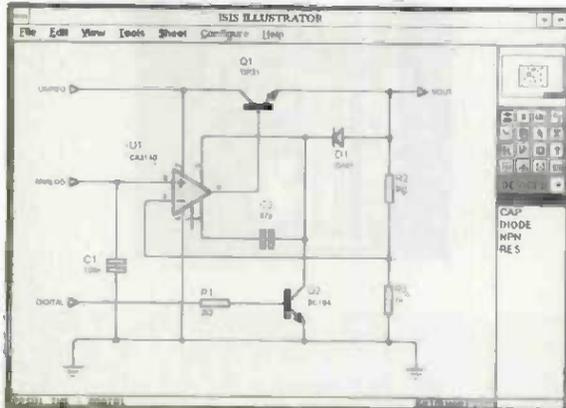CADPAK is especially suited to educational, hobby and small scale schematic and PCB design. CADPAK includes both schematic drawing and 32-bit PCB drafting tools but as an entry level product, there is no netlist link between them.



The schematic drawing module of CADPAK, ISIS ILLUSTRATOR, enables you to create circuit diagrams like the ones in the magazines.


- Runs under Windows 3.1 making full use of Windows features such as on-line help.
- Full control of appearance including line widths, fill styles, fonts, colours.
- Automatic wire routing & dot placement.
- Fully automatic annotator.
- Complete with device and comprehensive package libraries for both through hole and SMT parts.
- Advanced route editing allows deletion or modification of any section of track.
- Gerber, Excellon and DXF outputs as well as output via Windows drivers. Also includes Gerber viewer.
- Exports diagrams to other applications via the clipboard.
- CADPAK is also available for DOS.

CADPAK FOR WINDOWS £ 149

CADPAK FOR DOS £ 79

PROPAK for Windows

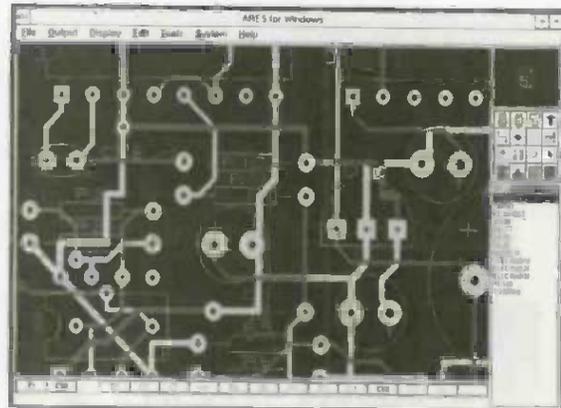PROPAK has all of the features in CADPAK plus netlist based integration, automatic power plane generation and a powerful auto-router. PROPAK includes enough schematic capture and PCB design functionality for all but the most demanding applications.



PROPAK's schematic drawing editor ISIS ILLUSTRATOR+ includes even more features than ISIS ILLUSTRATOR. PROPAK's 32-bit PCB design tool, ARES for Windows, is our most powerful and easy to use yet.

- Multi-sheet and hierarchical designs.
- Netlist link between modules guarantees consistency between schematic and PCB.
- Netlists are also compatible with SPICE-AGE and most other electronics CAD packages.
- Generates a full bill of materials.
- ASCII data import facility.
- Electrical rules and connectivity checkers.
- Ratsnest display with automatic update during placement and routing.
- Multi-strategy autorouter gives high completion rates.
- Power plane generator creates ground planes with ease.
- PROPAK is also available for DOS.

PROPAK FOR WINDOWS £ 495

PROPAK FOR DOS £ 395

Call or fax us today for a demo pack. Please state whether you would like a DOS or Windows pack.

Prices exclude postage (£5 for UK) and VAT. ISIS ILLUSTRATOR and ARES for Windows are also available separately. All manufacturers trademarks acknowledged.

labcenter


E l e c t r o n i c s

53-55 Main St. Grassington, N. Yorks. BD23 5AA

Tel: 01756 753440 Fax: 01756 752857

ETI Book of Electronics

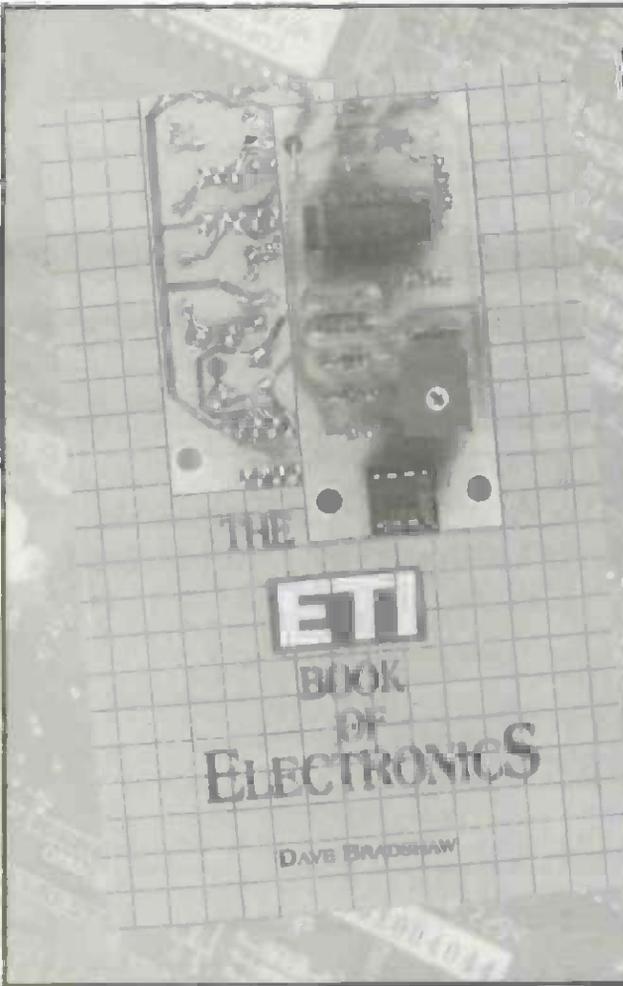An introduction to electronics that clearly explains the theory and principles involved. Each chapter includes a project to make. Projects include a loudspeaker divider, continuity tester, mini-amplifier, a burglar alarm and more!



ETI Book of Electronics 0 85242 928 2 £10.95
 P&P + 10% MINIMUM £1 (UK only) Overseas + 20%
 Telephone orders (01797) 366905
 I enclose my remittance of £.....
 Please make cheque payable to Bailey Distribution
 and send to the address below:
 Please charge my Mastercard/Visa

 Expiry Date..... Signature.....
 Name.....
 Address.....
 Post code.....
 Complete details and return to Bailey Distribution,
 Learoyd Road, Mountfield Road Ind. Estate, New Romney,
 Kent, TN28 8XU.
 Please tick this box if you do not wish to receive information
 from any other carefully vetted companies

High quality stepping motor kits (all including stepping motors) Complete independent control of 2 stepping motors by PC (Via the parallel port) with 2 motors and software
 Kit £67.00 ready built £99.00
 Software support and 4 digital inputs kit £27.00
 Power interface AA kit £36.00
 power interface BA kit £46.00
 Stepper kit 4 (manual control) Includes 200 step stepping motor and control circuit £23.00
 We are now stocking a range of stepping motors and kits to drive them please ask for the stepping motor data sheet for full information.
 Inverter toroidal transformers 225VA 10.5-0-10.5 primary 0.260-285 secondary £29.95
 LEDs 3mm or 5mm red or green 7p each yellow 11p each
 cable ties 1p each £5.95 per 1000
 £9.50 per 10,000
 High quality photo resist copper clad epoxy glass boards

Dimensions	single sided	double sided
3x4 inches	£1.09	£1.25
4x8 inches	£2.75	£2.99
6x12 inches	£6.20	-
12x12 inches	£12.25	-

Rechargeable Batteries
 AA (HP7) £0.99
 AA 700mAh £1.75
 C 2AH w/ri solder tags £3.60
 D 4AH with solder tags £4.95
 1/2AA with solder tags £1.55
 AAA (HP16) 180mAh £1.75
 AA 500mAh with solder tags £1.55
 C (HP11) 1.8AH £2.20
 D (HP2) 1.2AH £2.60
 PP3 8.4V 110mAh £4.95
 Sub C with solder tags £2.50
 1/3 AA with tags (philips CTV) £1.95
 Standard charger charges 4 AA cells in 5 hours or 4Cs or 4Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time) £5.95
 High power charger as above but charges the Cs and Ds in 5 hours AAAs Cs and Ds must be charged in 2s or 4s £10.95
 Nickel Metal Hydride AA cells high capacity with no memory, if charged at 100ma and discharged at 250ma or less 1100mAh capacity (lower capacity for high discharge rates) £3.75
 Special offers please check for availability
 stick of 4 - 42 x 16mm nicad batteries 171mms 16mm dia with red & black leads 4.8v £8.95
 Computer grade capacitors with screw terminals 5800uf 60v £4.95
 115v ac 80v dc motor 4mm x 22mm shaft 50mm dia x 60 long body (excluding the shaft) it has replaceable thermal fuse and brushes £4.95 each £3.95 100+ 7 segment common anode led display 12mm £0.45
 LM337A TO3 case variable regulator £1.95
 £1.44 100+
 GaAs FET low leakage current S8873 £12.95 each £9.95 10+ £7.95 100+
 BS250 P channel mosfet £0.45, BC559 transistor £3.95 per 100
 74LS05 hex inverter £10.00 per 100, used 8748 Microcontroller £3.50
 SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet £1.95
 AM27S02 £1.25 each 90p 100+, CD4007UB 10p 100+, 6p 1000+

Sinclair light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50hz flickering light with output wave form chart £3.95
 DC-DC converter Reliability model V12P5 12v In 5v 200ma out 300v input to output isolation with data £4.95 each or pack of 10 £39.50
 Hour counter used 7 digit 240v ac 50Hz £1.45
 QWERTY keyboard 58 key good quality switches new £5.00
 Arpac A82903-C large stepping motor 14v 7.5' step 27ohm 68mm dia body 6.3mm shaft £8.95 or £200.00 for a box of 30
 Polyester capacitors box type 22.5mm lead pitch
 0.9uf 250vdc 18p each 14p 100+, 9p 1000+
 1uf 250vdc 30p each, 20p 100+, 10p 1000+
 3.3uf 100vdc 30p each, 20p 100+, 15p 1000+
 1uf 50v bipolar electrolytic axial leads 15p each, 7.5p 1000+
 0.22uf 250v polyester axial leads 15p each, 7.5p 1000+ Polypropylene 1uf 400vdc (Wima MKP10) 27.5mm pitch
 32x28x17mm case 75p each 60p 100+
 Philips 123 series solid aluminium axial leads
 33uf 10v & 2.2uf 40p each, 25p 100+
 Philips 108 series long life 22uf 63v axial 30p each 15p 1000+
 Multilayer AVX ceramic capacitors all 5mm pitch 100v 100p, 150p, 220p, 10,000p (10n) 10p each, 5p 100+, 3.5p 1000+
 500pF compression trimmer .50p
 40 uf 370vac motor start capacitor (dielectric type containing no pch) £5.95 or £49.50 for 10
 Solid carbon resistors very low inductance ideal for RF circuits
 27pwm 2W, 68ohm 2W 25p each 15p each 100+ we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list
 P.C. 400W PSU (Intel part 201035-001) with standard motherboard and 5 disk drive connectors, fan and mains inlet/outlet connectors on back and switch on the side (top for lower case) dims
 212x49x140mm excluding switch £26.50 each
 £138.00 for 8
 MX150 Digital multimeter 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 15v battery test £12.95
 AMD 27256-3 Eproms £2.00 each, £1.25 100+
 DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each 40p 100+
 Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm £7.95 or £49.50 for 10
 Hand held ultrasonic remote control £3.95
 CV2486 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light 20p each or £7.50 per 100
 All products advertised as new and unused unless otherwise stated. Wide range of CAVOS TTL 74HC 74F Linear Transistors kits rechargeable batteries capacitors tools etc. always in stock.
 Please add £1.95 towards P&P val included in all prices

JPG ELECTRONICS
 ETI 276 276 Chatsworth Road,
 Chesterfield S40 2BH
 Access Visa Orders (01246) 211202
 Callers Welcome

ADVERTISERS INDEX

BK Electronics	39
Bull Electrical	5, 7
Chelmer Valve	51
Circuit Distribution	50
Classified Section	72, 73
Cricklewood Electronics	16
Direct CCTV	33
Display Electronics	43
EQT	42
Field Electric	33
Innovative Interfaces	33
JJ Components	16
JPG Electronics	71
Komputer Knowledge	16
Labcentre Electronics	70
MadLab	64
Maplins	OBC
Mayflower Electronics	33
Megadownload	31
Milford Instruments	55
MQP Electronics	17
Niche Software	55
Number One Systems	26
Omni Electronics	42
Pico Technology	4
Quick Route Systems (powerware)	IFC
Radio Tech	32
Robinson Marshall	IBC
Seetrex CAE	33
Starts of Reading	16
Strategic Tests	17
Telnet	27
Tsien (UK)	65

Classified



James Gale
01442 66551

Send your requirements to:
ETI Classified Department, Nexus, Nexus House,
Boundary Way, Hemel Hempstead, HP2 7ST
Lineage: 75p per word (+ VAT) (minimum 15 words)
Semi display: (minimum 2.5cms)
£10.50 + VAT per single column centimetre



Ring for information on series bookings/discounts.
All advertisements in this section must be pre-paid.
Advertisements are accepted subject to the terms and conditions
printed on the advertisement rate card (available on request).

FOR SALE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60
OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£31.90	£6.00
	(£44.53 inc VAT)	
1KVA 5 amp max	£41.15	£7.00
	(£56.58 inc VAT)	
2KVA 10 amp max	£59.40	£9.50
	(£79.78 inc VAT)	
3KVA 15 amp max	£78.65	£9.50
	(£102.40 inc VAT)	
5KVA 25 amp max	£139.15	

(Plus Carriage)
Buy direct from the Importers. Keenest prices in the country

COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO
(110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

WIDE RANGE OF XENON FLASH TUBES

Write/Phone your enquiries

ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES

4ft 0" watt £14.00 (callers only)	(£16.45 inc VAT)
2ft 20 watt £9.00 (callers only)	(£10.58 inc VAT)
12in 8 watt £6.80 + 75p p&p	(£6.52 inc VAT)
9in 8 watt £3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt £3.96 + 50p p&p	(£5.24 inc VAT)

220V AC BALLAST KIT

For either 6in, 8in or 12in tubes £6.05 + £1.40 p&p (£8.75 inc VAT)

The above Tubes are suitable for Forged Bank Note detection, security marking etc
Other Wave Lengths of U.V. TUBE available please telephone your enquiries

400 WATT UV LAMP

Only £38.00 + £4.00 p&p (£48.28 inc VAT)

160 WATT SELF BALLASTED BLACK LIGHT MERCURY BULB

Available with BC or ES fitting. Price inc VAT & p&p and VAT £25.55



12V D.C. BILGE PUMPS

500 GPH 1 1/2" head 3 amp £19.98
1750 GPH 1 1/2" head 8 amp £34.55
Also now available 24V D.C. 1750 GPH 1 1/2" head 5 amp £36.55 All designed to be used submerged. PRICES INCLUDE P&P & VAT

SUPER HY-LIGHT STROBE KIT

Designed for Diaco, Theatrical uses etc.
Approx 16 joules. Adjustable speed £30.00 + £3.00 p&p (£2.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (£31.73 inc VAT)
SAE for further details including Hy-Light and Industrial Strobe Kits.



SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

FAX 0181-995 0549 0181-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10



Ample Parking Space

SMART CARD PRODUCTS

Smartcards, Readers/Writers, OEM couplers, Evaluation kits and more.

EPSILON ELECTRONICS
Brynsengvn, 1A, 0667 Oslo,
Norway TEL/FAX
+4722640810

L.F. HANNEY
Your Electronic
Component Specialist for
Avon, Wilts & Somerset.
**77 Lower Bristol
Road, Bath, Avon.**
Tel: 01225 424811

"BOFFINS SPECIAL"- UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (fetter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends. Audible warning.
These are sold for the dismantling of the exceptional quality components, regret no Circuits available. Ridiculously low price: £20.00 + £8.00 p&p (£28.20 incl VAT)

5KVA ISOLATION TRANSFORMER

As New Equipment fully shrouded Line Noise Suppression, Ultra Isolation Transformer with terminal covers and knock-out cable entries. Primary 120/240V Secondary 120/240V 50/60 Hz .005 pF Capacitance. Size L37 x W18 x H16cm Weight 47 Kilos
PRICE £120.00 + VAT

240V AC CENTRIFUGAL BLOWER

New Manuf. Surplus Skeleton Blower suitable for mounting inside an enclosure to cool equipment. Overall size 130x110x85mm. Outlet 80x35mm. Impeller 60mm dia x 60mm long. £14.10 incl P&P & VAT

SEWING MACHINE MOTOR

Brand new 220/240V AC-DC SEW-TRIC 2 lead Brush Motor. Size L. 100mm x H. 70mm x W.55mm. Spindle. 1/4in. dia x 1in. long. £14.10 incl. P&P & VAT

GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £27.73

SOLID STATE UNIT

Input 230/240V AC. Output approx 15KV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (£12.81 inc VAT) NMS

EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Argon Tube Ballast unit, pair of 8-pin leads, neon indicator, on/off switch, safety microswitch and circuit £15.00 + £2.00 p&p (£19.98 inc VAT)

WASHING MACHINE WATER PUMP

Brand new 240V AC. fan cooled. Can be used for a variety of purposes. Inlet 1 1/2" outlet 1 in. dia. Price includes p&p & VAT. £11.20 each or 2 for £20.50 inclusive.

MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171. Brand new price \$ for £7.05 inc VAT & p&p

COOKE INTERNATIONAL

SUPPLIER OF QUALITY USED TEST INSTRUMENTS.

ANALYSERS, BRIDGES, CALIBRATORS, VOLTMETERS,
GENERATORS, OSCILLOSCOPES, POWER METERS. ETC
ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE
COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND U.K. ENQUIRIES WELCOME
SEND FOR LIST OF EQUIPMENT AND MANUALS
ALL PRICES EXCLUDE VAT AND CARRIAGE
DISCOUNT FOR BULK ORDERS SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM - 5PM

COOKE INTERNATIONAL
ELECTRONIC TEST & MEASURING INSTRUMENTS
Unit Four, Fordingbridge Site, Main Road, Barnham, Bognor Regis,
West Sussex, PO22 0EB Tel (+44) 01243 545111/2 Fax (+44) 01243 542457
WANTED TEST EQUIPMENT & MANUALS TO PURCHASE

LIVERPOOL

PROGRESSIVE RADIO

87/93 Dale Street
Tel: 051 236 0982 051 236 6154

47 Whitechapel
Tel: 051 236 5489
Liverpool 2

'THE ELECTRONICS SPECIALISTS'
Open: Tues-Sat 9.30-5.30

SWC SCIENTIFIC
WIRE COMPANY

ENAMELLED COPPER WIRE
TINNED WIRE SILVER
PLATED COPPER WIRE
SOLDER EUREKA WIRE
NICKEL CHROME WIRE
BRASS WIRE LI TZ WIRE
BIFILAR WIRE MANGANIN
WIRE TEFZEL WIRE NICKEL
SAE BEINGS LIST 18 RAVEN
RD LONDON E18 1HW
FAX 081 559 1114

PLANS

ELECTRONIC PLANS, laser designs, solar and wind generators, high voltage lesas, surveillance devices, pyrotechnics and computer graphics tablet. 150 projects. For catalogue, SAE to Plancentre Publications, Unit 7, Old Wharf Industrial Estate, Dymock Road, Ledbury, Herefordshire, HR8 2HS.

Black and White
Monitors 5" screen

Accept composite video signal operate on 12 volt D.C. Pre-owned but tested and working Only £85 inc. postage & packing

Alsco Trading,
Astley House, Johnson Street,
Tyldesley Manchester M29
8AB. Tel 01942 893573

DIY PLANS!! Windgenerators, petrol generators, inverters, portable welding generators, engine crane, electric bike, solar projects, boats and the famous Homebuilt Dynamo. Plus books on sterling engines, mechanical wonders, the writings of Thomas Tesla, electromagnets etc. Hundreds of exciting projects. 2 x 1st stamps for descriptive catalogue. Jemmett Engineering 8 Hallam Gardens Pinner Middlesex HA5 4PR

COMPONENTS

EPROMS PLDs + MICRO CONTROLLERS copied or programmed. We supply devices/convert discrete logic to PLDs. PCB for ETI PIC project card supplied at £10. PO Box 1561, Bath 01225 444467.

TO ADVERTISE IN ETI
PHONE JIM ON 01442 66551

Roundup

Nick Hampshire takes a look at the technology of tomorrow

Three-dimensional imaging systems have been a constant theme in science fiction films - images hovering in the air in front of the actors as if the subjects of the image were really there. As is very often the case, science fiction has a habit of becoming fact and, in this instance, for the last couple of months, shoppers in New York's Union Square have been astounded to see completely life-like images of products floating above the pavement in front of Bradlees, a well known department store.

The technology which produces these three-dimensional floating images is causing considerable excitement in the advertising and entertainment industries. It was invented by Dimensional Media Associates of the US and is now being further developed in conjunction with CRL of Hayes in Middlesex, the former research division of Thom EMI.

Surprisingly, the technology is not based on holography but on a complex system of polarisers, lenses and filters which build up the image, focused in free space, from multiple image sources. The technique is capable of generating true three-dimensional volumetric displays that look almost solid.

The big advantage it has over holographic systems lies in the fact that for the first time it is possible to generate full motion, high resolution images which can not only be seen by viewers without the aid of special glasses but can also be generated virtually in real time.

It is understood that advertising companies are queuing up to buy systems as soon as they become commercially available. In the meantime the world's second demonstration system is being installed in London and should be projecting three-dimensional images outside the Knightsbridge store of Emporio Armani in time for Christmas.

There has been quite a lot of work done

on 3-D imaging systems, primarily using holography or flexing/rotating mirrors. Much of this work has been funded by the US Dept of Defence whose main interest it seems is the construction of battlefield display systems which will show the exact location of aircraft, both friend and foe, within the battle zone. However, virtual reality systems seem to have put some of this work onto the back burner.

The development of 3-D imaging systems has also attracted the interest of civilian air traffic controllers for whom it would offer an excellent way of looking at, and control of, aircraft movements. But judging by recent announcements from America's Federal Aviation Authority, the whole concept of air traffic control is about to change, thanks to another bit of military technology - the satellite-based global positioning system (GPS).

It is being proposed that all aircraft are fitted with GPS systems which can accurately determine the aircraft's position and height to within a few metres. This data would then be relayed by satellite to a system of ground-based computers that would maintain a safety zone around each aircraft and automatically order a shift in course if the safety zones of two aircraft overlapped.

This essentially means the end of the human air traffic controller, but because there is no longer any need to stick to predefined air corridors it should be possible to increase considerably the number of aircraft in the air at any one time and theoretically improve punctuality with flights being up to 20% shorter.

In Britain, the CAA are also examining this so-called 'free flight' technology but, understandably, severe reservations are being expressed by both existing air traffic controllers and by many pilots. The pilots are particularly concerned about how failsafe the system actually is, a legitimate concern since there will be no human backup.



EDITORIAL

Editor **Nick Hampshire**
Sub Editor **Eamonn Percival**
Editorial Assistant **Lynn Bugden**

CREATIVE

Designer **Nadia Ahdout**
Technical Illustration **John Puczynski**
Photography **Manny Cefai**

ADVERTISEMENT SALES

Display Sales
Alison Wetherill
Advertisement Copy Control
Marie Quilter
Classified Sales
Jim Gale
Group Advertising Manager
Diane Farnham

MANAGEMENT

Divisional Director
Terry Pattison
Production Administrator
Theresa Davis
Business Manager
Claire Jenkinson
Marketing Manager
Jason Doran
Copy Sales Manager
David Pagendam



ETI is normally published on the first Friday in the month preceding the cover date. The contents of this publication including all articles, plans, drawings and programs and all copyright and all other intellectual property rights therein belong to Nexus Special Interests. All rights conferred by the Law of Copyright and other intellectual property rights and by virtue of international copyright conventions are specifically reserved to Nexus Special Interests and reproduction requires the prior written consent of the company ©1990 Nexus Special Interests. All reasonable care is taken in the preparation of the magazine contents, but the publishers cannot be held legally responsible for errors. Where mistakes do occur, a correction will normally be published as soon as possible afterwards. All prices and data contained in advertisements are accepted by us in good faith as correct at the time of going to press. Neither the advertisers nor the publishers can be held responsible, however, for any variations affecting price or availability which may occur after the publication has closed for press.

Subscription rates-UK £26.80 Europe £34.70 Sterling Overseas £36.20 US Dollars Overseas \$54.00

Published by Nexus Special Interests, Nexus House, Boundary Way, Hemel Hempstead HP2 7ST, Telephone (01442) 66551. UK newspaper distribution by SM Distribution Ltd, 6 Lougham Court Road, London SW18 2PG, Telephone 0181-667 8111. Overseas and non-newspaper sales by Magazine Sales Department, Argus House, Boundary Way, Hemel Hempstead, HP2 7ST, Telephone (01442) 66551. Subscriptions by Nexus Subscription Dept, Tower House, Sovereign Park, Lathkill Street, Market Harborough, Leicestershire, LE16 9EF.

US subscriptions by Wise Owl Worldwide Publications, 4314 West 238th Street, Torrance, CA 90505 USA. For Visa/Mastercard orders in USA - Telephone (310) 375 6758 Fax (310) 375 0548. Pacific Time: 9am-5pm Weekdays, 10am-6pm Weekends. Typesetting and origination by Ebony, Liskeard, Cornwall. Printed by Wiltshire Ltd, Bristol.



Nexus House, Boundary Way,
Hemel Hempstead HP2 7ST
Telephone (01442) 66551
Fax (01442) 66998

Next Month...

In the January 1996 issue of Electronics Today International we will be continuing our premier autumn project, the ETI Basic Programmable micro controller.

Dr Pei An shows how to build a heartbeat monitor and, from Terry Balbirnie, there is an electronic guard dog project which will bark at any unwelcome visitors. Meanwhile, if you blow a fuse and are plunged into the dark Bob Noye's torch pad will allow you to find the torch that will help you mend the fuse. There is a 16-channel MIDI-controlled audio mixer project from Tom Scarff and Bart Trepak concludes his practical look at designing a project around the PIC micro controller.

The main feature article will be looking at the Ulysses solar mission and we will also be reviewing some more PC software of interest to readers.

MIXED-MODE SIMULATION. THE POWER OF VERSION 4.


**New
Version 4**

Analog, Digital & Mixed Circuits

Electronics Workbench® Version 4 is a fully integrated schematic capture, simulator and graphical waveform generator. It is simple to mix analog and digital parts in any combination.

Design and Verify Circuits... Fast!

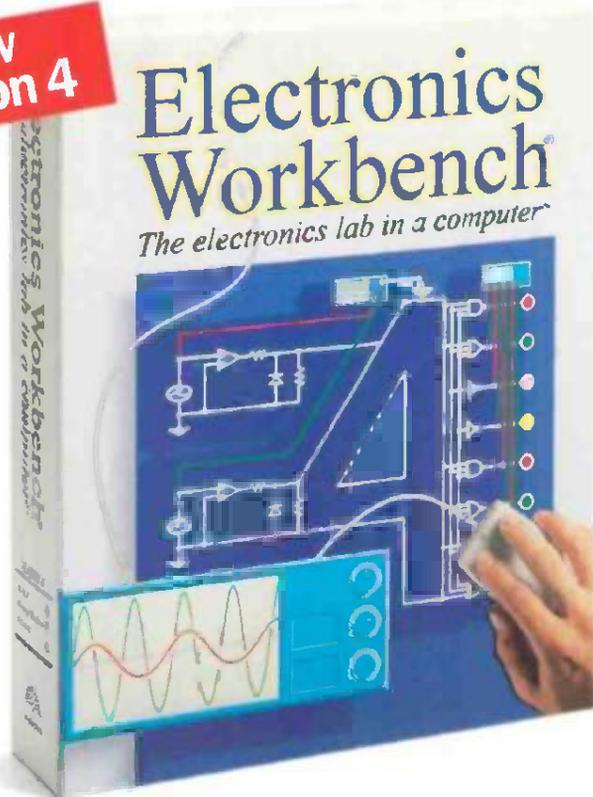Electronics Workbench's simple, direct interface helps you build circuits in a fraction of the time. Try what if scenarios and fine tune your designs painlessly.



More Power

Simulate bigger and more complex circuits. Faster. On average, Electronics Workbench Version 4 is more than 5 times faster than Version 3.

More Parts

Multiple parts bins contain over twice the components of Version 3.


More Models

Over 350 real world analog and digital models are included free with Electronics Workbench. And, if you need more, an additional 2,000 models are available.

Incredibly Powerful. Incredibly Affordable.

If you need mixed-mode power at a price you can afford, take a look at this simulator and graphical waveform generator that mixes analog and digital with ease.

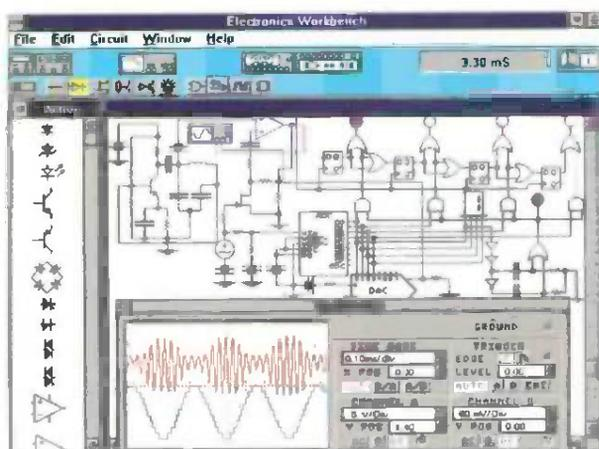With over 20,000 users world-wide, Electronics Workbench has already been tried, tested and accepted as an invaluable tool to design and verify analog and digital circuits. With Version 4 true mixed-mode simulation is now a reality with incredible simplicity.



True mixed-mode simulation: Simultaneous AM transmission, digitization and pulse-code modulation of a signal.

**BETTS '96
STAND No 284**

Electronics Workbench™
The electronics lab in a computer™

Order Now! Just £199*

44-(0)1203-233-216

RM Robinson Marshall (Europe) Plc

Nadella Building, Progress Close,
Leofric Business Park,
Coventry, Warwickshire CV3 2TF
Fax: 44 (0)1203 233-210

E-mail: rme@cityscape.co.uk

Shipping charges UK £5.99. All prices are plus VAT.
All trade marks are the property of their respective owners.
Electronics Workbench is a trademark of Interactive Image
Technologies Ltd., Toronto, Canada.
* 30 Day money-back guarantee.



Australia: 2-519-3933 • Brazil: 11-453-5588 • Cyprus: 2-62-1068 • Denmark: 33-25-0109 • Finland: 0-297-5033 • France: 14-908-9000 • Germany: 711-62-7740 • Greece: 1-524-9981
Hungary: 1-215-0082 • India: 11-5441343 • Israel: 3-647-5613 • Italy: 11-437-5549 • Japan: 3-3382-3136 • Malaysia: 603-7778945 • Mexico: 5-396-3075 • Netherlands: 18-031-7666
New Zealand: 9-267-1756 • Norway: 22-16-70-45 • Portugal: 1-814-6609 • Singapore: 462-0006 • Slovenia: 61-317-830 • South Africa: 351-68309 • South Korea: 2-2-222-3431
Spain: 1-553-3234 • Sri Lanka: 1-86-5970 • Sweden: 8-740-5500 • Thailand: 66-2-398-6952 • United Kingdom: 203-23-3216



With over 14,000 products the new Maplin Catalogue is now bigger than ever



THE EIFFEL TOWER

Built in 1889 by Alexandre Gustave Eiffel, the Eiffel Tower is 984 feet high and gives an unrivalled view of the whole of Paris.



THE NEW MAPLIN CATALOGUE

Built for 1996 by Maplin, the new catalogue is almost 1,200 pages long and gives an unrivalled view of the whole world of electronics.
Now Only £2.95

PCB Etching Tray
£3.49

COMPLETE RANGE OF PCB MAKING EQUIPMENT

COMPREHENSIVE RANGES OF TEST EQUIPMENT

20MHz Oscilloscope with Function Generator £349.99

Weller Temperature Controlled Soldering Iron £44.07

OVER 60 PAGES OF TOOLS AND SOLDERING ACCESSORIES

RANGE OF SATELLITE RECEIVERS AND ACCESSORIES

Astra 1D Satellite Frequency Extender £25.99

Video Doorphone
£199.99

WIDE RANGE OF SECURITY DEVICES AND ALARMS

OVER 300 KITS FOR YOU TO BUILD FROM £5 TO £599

Shortwave Receiver Kit £9.99

50 Watt Mobile 2m Transceiver
£389.95

FULL RANGE OF TRANSCEIVERS, RECEIVERS AND SCANNERS

'BIG NAME' HI-FI SEPARATES AND ACCESSORIES

Dolby Pro-Logic Surround Sound Processor £229.99



Get your copy now from **WH SMITH, John Menzies and Maplin stores nationwide**
Or order direct NOW on 01702 554161

Catalogue Mail order Price £3.45 (inc p&p). Prices refer to the 1996 Maplin Catalogue and are inclusive of VAT.
All items are subject to availability. E&OE. Maplin Electronics, P.O. Box 3, Rayleigh, Essex, England SS6 8LR.