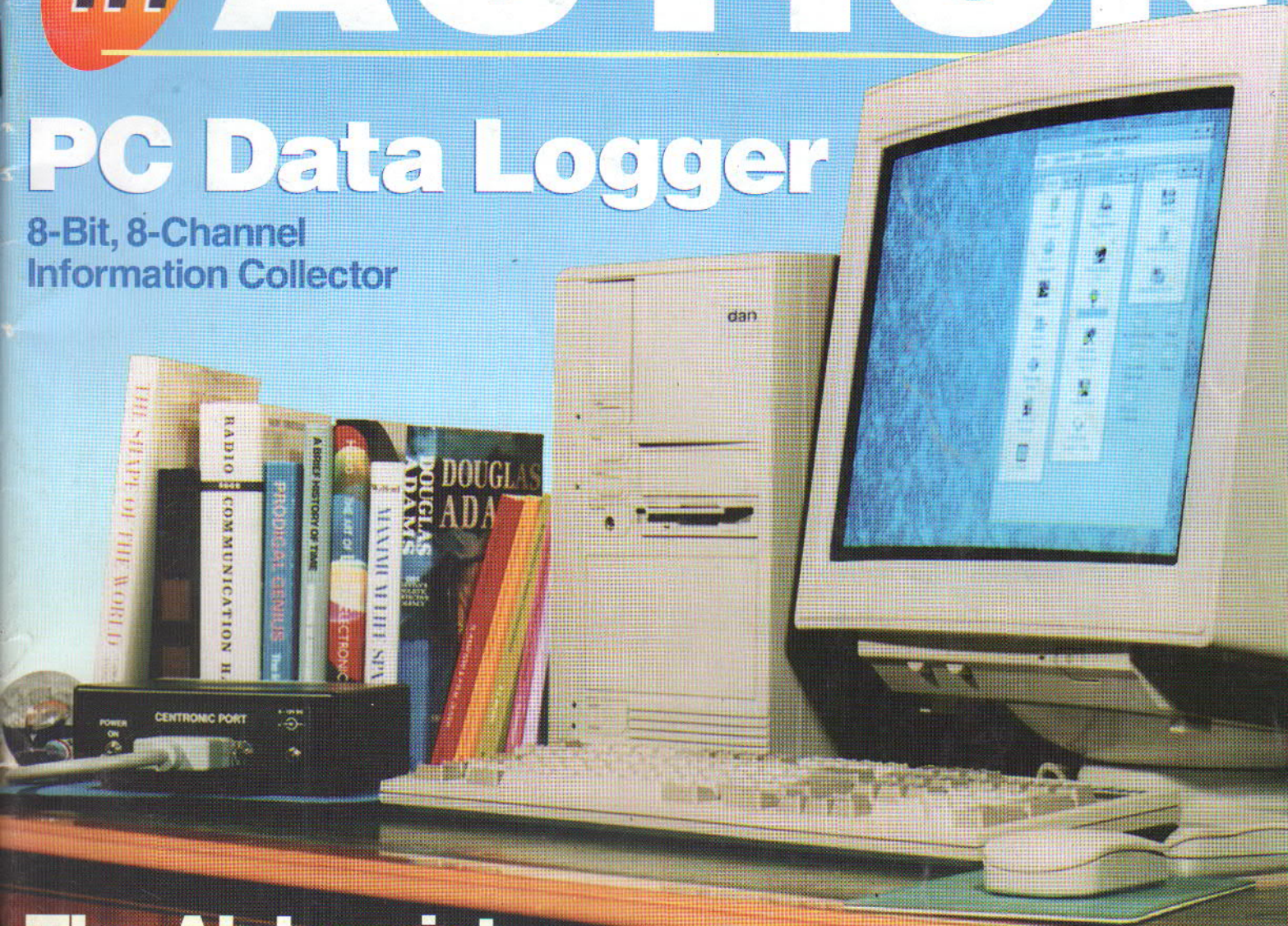


SECURITY-Special offer from **Cirkit** -see page 61

# ELECTRONICS *in* ACTION

## PC Data Logger

8-Bit, 8-Channel  
Information Collector



## The Alchemist

Hi-Fi Preamp for vinyl connoisseurs

## Guitar Amp A/B Switchbox

No more channel hopping blues



## Audio for Video

Cleaning up in the  
Home Movie sound  
department

April 1994  
£2.25





# Take your PC into a new dimension

*...with an Ultra high quality digital sound sampler.  
Just one of the excellent projects in NEXT MONTHS*

**ELECTRONICS**  
**in ACTION**

ON SALE THURSDAY 21<sup>st</sup> APRIL

### EDITOR

*Paul Freeman-Sear*

### NEWS EDITOR

*Geoff Martin*

### DESIGN

and **TECHNICAL  
ILLUSTRATION**

*Iain Houston*

### CONTRIBUTORS

*Dr. Pei An*

*Edward Barrow*

*Douglas Clarkson*

*Daniel Coggins*

*John Linsley-Hood*

*Mike Meechan*

*John Mitchell*

*Brian Padgett*

*Mark Price*

*Paul Stenning*

### ADVERTISING SALES

*Gilly Martin*

☎ 0442 842069



Page 52



PO BOX 600, BERKHAMSTED  
HERTS. HP4 1NL  
TELEPHONE 0442 842069  
FAX 0442 842279

## **4 Here is the news...**

What's going on in the technology world  
A news view from all points of the compass.

## **8 Research World**

Technical advances from around the globe.

## **10 Mission Control**

In his first project, Dr. Pei An shows us how to build an 8 Bit,  
8 Channel Data Logger that utilises the Centronic port on your PC.

## **18 Intercommunications**

An intercom is the answer if you're missing out on vital cups of  
tea or important calls whilst hiding in your workshop. By Mark Price.

## **22 5 Band Graphic Equaliser**

Clean up the sound track of your latest movie with this audio  
project from Paul Stenning.

## **26 Signal to Noise**

Another batch of correspondence from the post bag.

## **29 The Evolution of Audio Amplifier Design Part 3**

More transistor designs from the 50s, 60s and the 1970s by  
John Linsley Hood.

## **36 At the Waters Edge**

This is no ordinary water level detector, for it senses water that  
has no ions. A piece of sensitive detection by Edward Barrow.

## **42 The Alchemist**

The start of a moving coil preamplifier project from Mike Meechan.

## **48 The Eyes Have It**

Douglas Clarkson takes a look at Ophthalmic Excimer Lasers.

## **52 At the Channel Hop**

If you have those, can't get enough of those, amplifier channel  
switching blues, Daniel Coggins has the low noise medicine.

## **56 Ideas Forum**

Where innovative ideas turn into inventions.

## **57 At Your Service**

The one stop shop for PCBs past and present.

## **60 Technoshop**

More offers and exchanges in our monthly team-up with The  
Technology Exchange.


## **64 Future View**

Has the computer keyboard a future or will all operations be  
made by voice command? John Mitchell explains.

# Operate - you stupid machine!

The idea of using voice commands to operate machines or computers has been around for many years now, but it has only been within our grasp technically in the last decade. It has surely been a typists dream to speak a letter into the computer making verbal corrections on the way rather than to set fingers tapping on that awkward thing called a Qwerty keyboard. The new technology will clearly benefit those who cannot for a variety of reasons, operate a keyboard by hand. However, a more seemingly bizarre outcome to this voice responsive technology has already been observed in trials and it is this. People have a tendency to shout abuse at machines if things don't go the way they should. A natural tendency you may think, but should it be? And further still, just as some UK residents think that by shouting at our European cousins in English will make them understand our language, a parallel has been observed with the voice-operated machine. I suppose it's our way of establishing a dominance over a dumb machine. Would we even want the machine to utter a clever reply even it could? There may be a market for voice actuated machines but I don't somehow feel we are quite ready for the machine that can pull a fast one over its operator.

**Paul Freeman-Sear**

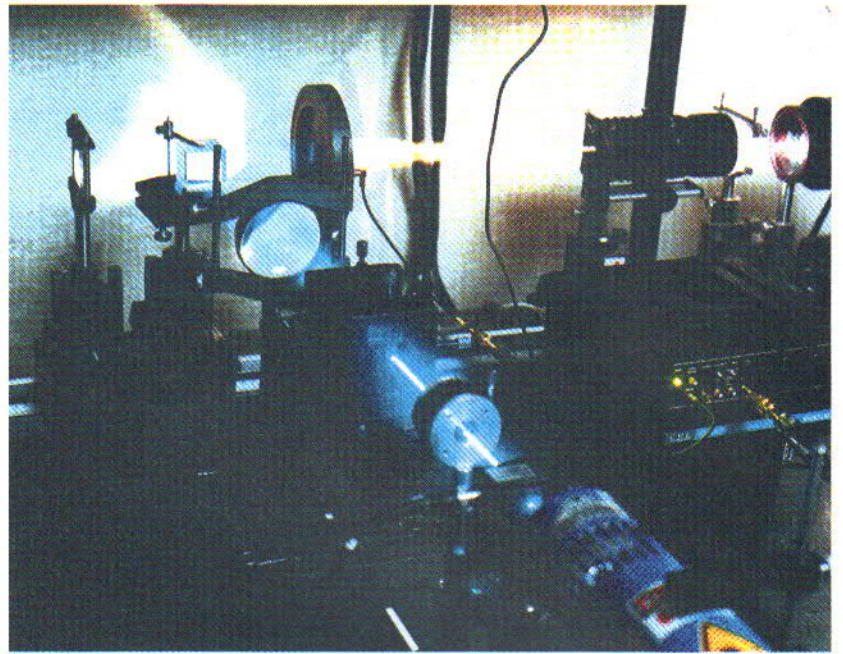


## A new method of display

CRL (Central Research Laboratories Ltd.), a subsidiary of THORN EMI, located in Hayes, has launched the highest resolution Ferroelectric Liquid Crystal Spatial Light Modulator (SLM) yet available. This is a 320 x 320 resolution device.

Manipulating optical information in real time is now a viable, low cost alternative to electronic processing for a variety of operations. Examples are comparing and recognising images, beam steering in communications systems, and programmable masking. These are all made possible using high resolution spatial light modulators.

SLMs are devices which act like high speed electronic transparencies taking images from computer memory to modulate light beams. This enables information to be manipulated optically in two dimensions.

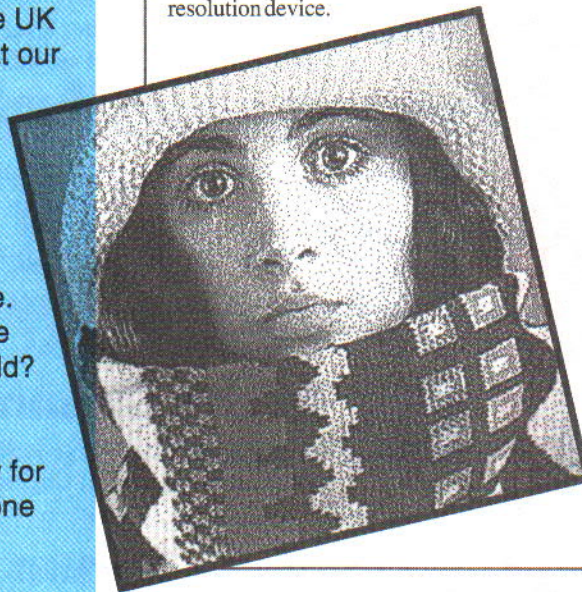In one major application, known as correlation, a stored image is compared optically with a real scene. The system indicates if the stored image



## Even Lower Cost Colour Printer



Every care is taken when compiling the magazine. However, the publishers cannot be held legally responsible for errors in the magazine or from loss arising from those errors. Any errors discovered will be published in the next available edition of the magazine.

Electronics in Action is published on the third Thursday of the month preceding the cover date. The magazine contents remain the copyright of Quantum House Publications Ltd. Any reproduction requires written consent of Quantum House Publications Ltd. All prices contained in the magazine are correct at time of going to press. The publishers or the advertisers cannot be held responsible for any variations in price or availability after the magazine has gone to press.

Published by Quantum House Publications Ltd., PO Box 600, Berkhamsted, Herts. HP4 1NL. Newstrade distribution by Seymour, Windsor House, 1270 London Rd., Norbury, London SW16 4DH Tel: 081 679 1899. Reproduction by Island Graphics, Chesham, Bucks. Tel: 0494 773082. Printed by Wiltshire (Bristol) Ltd., Philip St., Bedminster, Bristol BS3 4DS. Tel: 0272 760076

is present in the scene, and if so where it is. CRL is working in collaboration with a group including a car manufacturer to apply this comparing technique in road vehicles, principally to enhance road safety.

In this case, road signs will be recognised by comparing those seen through the windscreen with a library of stored images of signs. The driver can then be given a warning as appropriate; for instance, if the vehicle is approaching a bend too quickly. The new CRL SLM offers the ability to perform these comparisons optically at much higher speeds and lower costs than can be achieved electronically. This technique can already be used in quality inspection on production lines.

A second application is for product marking. Laser marking systems (used for example, for writing "Best Before" dates onto food products and batch codes onto pharmaceutical products) work either by mechanically scanning a

eliminate the need for mechanical scanning of the laser beam in the first type of system. This will have an impact on the maintenance costs of systems by removing complex moving parts. The fixed or mechanically changed metal masks of the second type can also be replaced by an SLM. In this case the SLM acts as an electronically 'programmable mask', allowing fast and frequent changing of the marking code to be made.

The CRL SLMs can also be used to manipulate the phase of the light beam passing through them. This means that the SLM can produce 'real-time' holograms. These holograms can be used to steer beams of light between optical fibres, correct telescopic images, or replicate images accurately, all under direct software control. The fact that these holograms are programmable clearly gives advantages over fixed holographic elements made by traditional chemical methods of production.

The 2DX320 SLM is supplied as a development unit with a compact optical head, and a control unit which can rapidly scan through images stored in the device memory. The control unit interfaces to a PC compatible host computer via a custom 8-bit expansion card, and is supplied with Microsoft Windows 3.1 compatible software. The control unit contains an embedded

80386 processor, so the system can also operate in a stand alone mode. The SLM may be configured to match a customer's specific requirement. ●

provides a high quality, low cost total printing solution for the Windows environment at a cost of a low priced ink jet printer. Cost/copy is around 50 pence for colour A4 paper prints and around £1.20 for overhead transparencies.

Notably the new package provides the added advantage of higher throughput, much faster output and superior quality print, with better saturated colours, at a far lower cost/copy compared

to ink jet printers, especially when producing OHP transparencies with


colour backgrounds.

Features include one colour plane memory for maximum performance. The G370-S produces high quality, A4 colour prints in 60s and is capable of up to 256,000 colours. Outputs can be on paper or transparency from an automatic, 100 sheet cassette and using special size A4 media, the printer provides full A4 imaging.

The rugged printer is quality designed and built for quality performance. Features include a rugged cast alloy chassis compared to alternatives on the market which use fragile plastic designs.

The SuperPrint Windows driver software provides high quality PostScript comparable printing and comes with 34 fonts plus the capability of speed printing on host PC fonts including Adobe, BitStream, Compugraphic and TrueType. The intelligent software even allows typefaces from different companies to be mixed and matched.

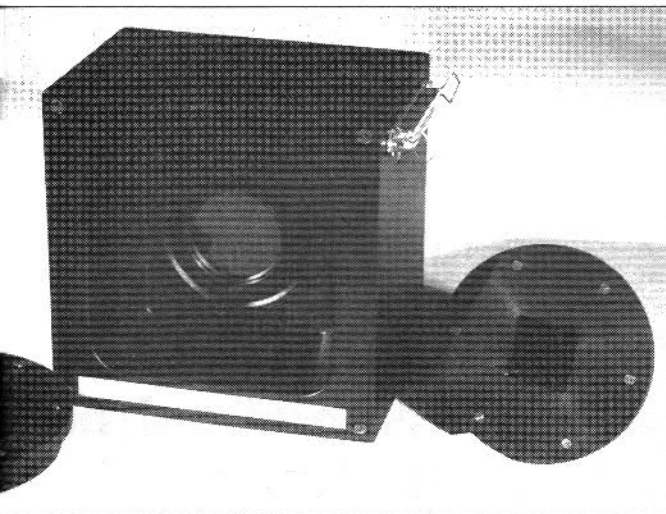The package provides true WYSIWYG screen fonts and outputs, via a software RIP imaging technology, complex graphics and bitmaps as well as virtually any font on the PC system. Dithering and fine tuning facilities are also provided to improve graphics imaging and to increase colour capabilities. ●



laser beam to form the required pattern, or by passing a larger diameter laser beam through a metal stencil to define the marking pattern. The use of an SLM within a laser marking system can

**Mitsubishi** has announced the introduction of its new, cost effective thermal transfer PostScript comparable colour printer for Windows applications. The G370-S high performance, high resolution A4 printer comes complete with a SuperPrint software Windows driver, free consumables starter pack and twelve months on-site warranty for £1395.

The new 300dpi resolution printer package represents a major cost reduction compared to other printers on the market. It makes colour thermal transfer printing more affordable and

### Miniature FM radio, smaller than a 50p

**Maplin Electronics** has introduced a mini radio into its catalogue. The auto-tuning, FM radio receiver produces a quality of reception that is normally only expected from radios many times its size. The little radio is provided with an on/off switch, a seek button and a 'reset' button and a pair of earphones, attached to 800mm of cord, that also doubles as the aerial. To operate, the 'reset' button is pressed once for each station that is automatically tuned in to, until the desired station is found. However, if the user has a favourite station, then tuning is not required every time the radio is switched on, as the last station selected is always remembered when the power is switched off. Ideal for commuters, cyclists and outdoor pursuits.

## Half Size Contactless IC Cards



A new contactless IC card has been introduced at the SmartCard '94 exhibition and was designed specifically to be fast and convenient to the user. It would provide reliable access control to mass user systems ranging from ticketing to automatic warehousing and production control, providing authorisation and even proof of payment.

At half the size and double the thickness of Mitsubishi's existing credit card sized version, the new contact less MelCard provides a handy alternative and gives the user a choice of styles. It measures 43x54mm and at 5mm thick provides a robustness and durability to withstand daily wear and tear. It is easily converted, for example into a key fob and thus kept

safe by the user.

Mitsubishi's contactless IC cards operate using a read/write device linked to a computer network for data I/O, read and write operations. When the card is presented near to the reader/writer head it automatically transmits data at up to 455kHz. Exact frequencies can be customised to specific applications, allowing the card to operate a ticket barrier for example or read part recognition data in factory automation and CIM.

The card operates at distances of up to 800mm and a typical operation takes less than 0.2s. The mini card has a single chip microcontroller inside and communicates with the reader/writer via half duplex amplitude shift keying transmission. The 8-bit microcontroller could be used in security applications and consumes little power. The SRAM memory provides high speed read and write operations at very low current consumption.

Radio frequency transmission avoids any electrical connections and possible transmission failure.

Under extensive testing, the contactless IC card has proved highly reliable, withstanding extensive bending and torsion tests in temperatures down to -200°C. All electrical and data retention characteristics withstand temperature cycling between -20 and +600°C and is waterproof.


## Hand-held digital IC tester

Polar Instruments has introduced a portable IC tester capable of functionally testing the vast majority of logic devices in general purpose use, as well as numerous common memory devices. Designated the Polar D320, the tester costs £180 and comes in a hand-held package weighing 285g, powered by a 9V PP3 cell.

A comprehensive built-in library of over 350 popular standard devices allows test engineers to test suspect digital ICs.

D320 tests digital components with up to 20 pins, and has a built-in library of truth table tests for 74/74LS/74HC TTL and 4000 series CMOS logic, plus checks for 41/44-series dynamic RAMs. If the component being tested does not have markings, or has a manufacturer's coding, the D320 can be switched to search and compare its logic function against the library to identify the generic type.

ICs are tested out of circuit, by placing them in a ZIF (zero insertion force) socket. Using the tester's six control keys and one-line LCD, the user can select a standard test by scrolling through the library, or switch the instrument into search mode. Although the primary application of D320 is in equipment service, in the field or at repair depots, most electronics companies will find the instrument a useful aid in both manufacturing test and goods-in inspection environments.

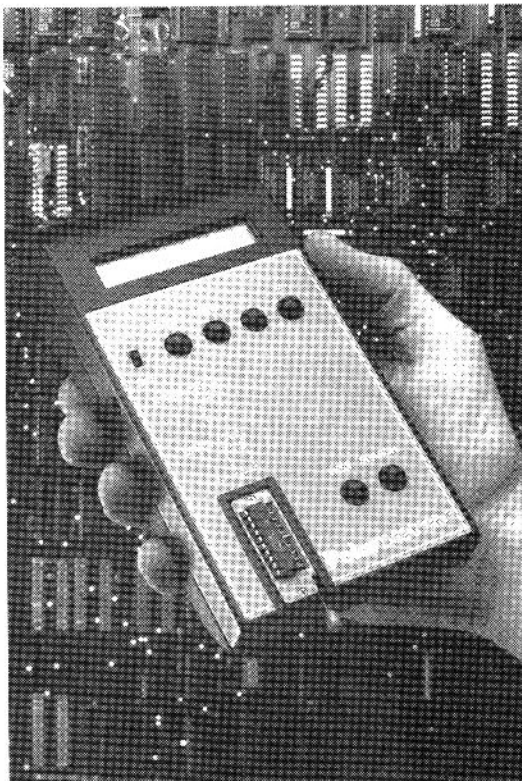

## RemoteControl Car Alarm

A simple, portable car alarm, suitable for any car or van is now available from Maplin. The unit takes power from the cigarette lighter socket via a coiled lead. It also contains its own back-up battery which will keep sounding the built-in alarm siren if it is disconnected. A green LED indicates battery state, while a red LED shows that the main supply is present and doubles as an armed state indicator.

The unit is armed and disarmed by a remote keyring transmitter, using a UHF radio link instead of the infrared method. The transmitted code is unique, and a processor in the main unit interprets the code upon arming, and then expects to receive the same code for disarming, so another keyring transmitter, even of the same type, cannot disarm it. The price is £39.95 (to incl. vat)

# Remote control on information superhighway

Echelon Corporation and Oracle Corporation demonstrated how their technologies will use the information superhighway to support the home automation and energy management market.

By connecting millions of homes and businesses to the superhighway, utility companies like gas and electricity, can reduce the need for new power plants by offering their customers simple and unintrusive ways to reduce their energy bills.

In the demonstration, Oracle's Media Server software sent billing, energy usage, peak load and pricing data from the local utility to homes and businesses. Echelon's Lonworks control network technology acted upon the information to control thermostats, water heaters, dryers, dishwashers and other energy consuming appliances. The two-way communication link between utilities and their customers demonstrated today is expected to accelerate the implementation of DSM programs by the utility companies worldwide.

With high capacity data networks now beginning to reach residential neighbourhoods, Oracle's Media Server could provide homeowners with countless services," said Larry Ellison, President and CEO of Oracle Corp., the world's largest information management software company.

"The Media Server isn't Jules Verne science fiction. Oracle's technical expertise and creative implementation have produced a product that can be a catalyst in implementing the data superhighway. When combined with LONWORKS technology, Oracle's Media Server gives utilities what they need to provide energy efficiency and savings to millions of homes and offices around the world," said M. Kenneth Oshman, President and CEO of Echelon. The delivery of voice, data and video services will have a major impact on the home automation market as well. As utilities provide real-time pricing data over the highway and begin billing customers based on time-of-use, customers and industry will seek ways to reduce their energy bills.

# Supersensitive nose on a chip

IBM scientists have developed the world's most sensitive heat-measuring instrument. Called a calorimeter, it is a thousand times more sensitive than any similar instrument available today: it can measure the heat generated in chemical reactions with a sensitivity to temperature changes as small as a hundred-thousandth of a degree.

The calorimeter was microfabricated with integrated-circuit technology and is relatively inexpensive. It should prove useful in a large variety of chemical observation, detection, measurement, and analysis applications such as drug design, forensics, and catalysis. When specially configured, the calorimeter can function as a supersensitive 'nose on a chip,' capable of 'smelling' extremely minute quantities of a wide range of substances.

Developed at the IBM Research Division's Zurich Research Laboratory, the technique employs a micromechanical silicon lever that is coated with aluminium. When heated, the lever bends because the two materials expand by different amounts. The amount of bending directly indicates how much heat has been absorbed by the lever. The effect is similar to what happens in an ordinary thermometer. When it absorbs heat, the liquid mercury expands. Whereas markings on the thermometer show how much the mercury expands, the IBM researchers use a laser to measure how much the lever bends; and they can measure bends as small as one hundredth of the diameter of an atom.

In a particular demonstration, a thin layer of platinum was applied to the aluminium-coated silicon lever. In the presence of a mixture of oxygen and hydrogen, the platinum functioned as a catalyst that promoted the combining of oxygen and hydrogen to form ordinary water. In the process, the platinum layer generated heat that was then absorbed by

the lever, causing it to bend. By carefully monitoring and measuring that bend, the researchers were able to show that the hydrogen and oxygen do not combine at a uniform rate. The rate actually oscillates with time, a phenomenon previously known to occur but never before sensed with a calorimeter.

The lever in this new calorimeter has a thickness only about a fiftieth of the diameter of a human hair - actually 1.5 microns - and a length of 400 microns. (A micron is one millionth of a metre). An array of hundreds or even thousands of such levers could be integrated on a chip. If each lever were coated and thereby sensitised for the detection of a specific chemical, the resulting combination would function as a 'supernose.' Even coatings such as reaction-specific enzymes and bacteria could be used, and because the calorimeter is so sensitive, chemical reactions involving only a few molecules could be detected.

A typical person can discern several hundred odours, and a trained expert might be able to identify several thousand. While computers have been given the ability to see, hear and touch, they are as yet unable to emulate the olfactory organ - they can't smell. This may soon change. The IBM scientists believe that the apparatus for this technique could be incorporated into a portable package, with the 'nose on a chip' and a laptop computer, to provide an instrument capable of detecting gases and pollutants such as ozone and carbon monoxide and even odours such as that of fish.

The researchers believe that through the use of micromechanics and nanotechnology, their calorimeter, already the most sensitive in the world, can be made many thousands of times even more sensitive. They are already working on that!

Utilities, in turn, will provide new tools and services for customers by installing energy management systems.

Consumers, for example, will set energy rates and program energy consuming devices, such as water heaters, clothes dryers, dishwashers to operate when rates are low. Then consumers will add control of lighting, security, sprinklers and other components to make a complete home automation system.

LONWORKS technology was

introduced by Echelon in December 1990. Today, Echelon Corporation provides over 700 customers with a full range of hardware and software products to support development, installation, and management of control networks. It is a privately-held company headquartered in Palo Alto, California with subsidiaries in London, Paris, Munich and Tokyo.

# Research World

## Technical Advances from around the Globe

### Magneto optical recording material

**N**ippon Steel Corp. has developed, with the support of Science & Technical Research Laboratories, a magneto-optical recording material capable of raising current memory capacity by about ten times. The material is a garnet-based one that can be formed as a film on a substrate. It responds to a green light source with a shorter wavelength and is thus suitable for larger-capacity recording and reproduction.

The technical breakthrough has been achieved by controlling the noise resulting from the large diameter of component particles of recording material.

For raising the recording capacity of M0 discs it is believed appropriate to utilize a light source with a shorter wavelength such as green for recording and playing back. The new material can respond specifically to a green semiconductor laser beam for reproduction.

The Japanese steel maker has succeeded in forming a uniform film of the new material on a 130mm-disc substrate and recording the reproducing data in far larger amounts. Combined with the new material, the new recording method and the optical parts still to be improved, the 130mm M0 disc will have a memory capacity of 3 gigabites - ten times that of conventional M0 discs.

### Pulse-driven vibrator

**T**oshiba Corp. engineers have improved a conventional ultrasonic LCD cleaning unit by use of a pulsed-wave power supply. The unit is a slit-shower type cleaner that combines a flow of ultrapure water with ultrasonic vibration at 1.4MHz.

It is expected that the cleaning unit will decrease the number of final defects by nearly 20%.

In such cleaning systems, sonic pressure - and therefore washing

capability - increases as power increases. A conventional power supply produces a continuous wave that vibrators cannot stand up to very long at peak power. By using a pulsed-wave supply, peak power can be doubled without raising either power consumption or the load on the vibrators.

Substrates with 70 particles per square centimetre were cleaned with the new system, leaving an average of 0.7

particles/cm<sup>2</sup>; the conventional unit left an average of seven.

Cleaning an LCD substrate measuring 400 x 500mm takes 45 seconds - about one-fifth the time required by previous cleaning methods. The same principles can be applied to semiconductor manufacturing, especially to replace the brushing and washing stage before photoresist coating.

### New PC performance monitoring technique

**A** U.S. motherboard has developed a new PC-performance-monitoring technique, called Power-Shift, that puts hardware and software to work to improve desktop power management.

PowerShift is said to reduce PC power consumption below the EPA established Energy Star limit of 30W for systems based on Intel 486DX2/66 class.

Elitegroup Computer Systems of Fremont, California, has put the technology in a 2 x 4in plug-in module with associated software that it will use in its own motherboards as well as sell to other OEMs. In the future, the module may be shrunk, in cooperation with a chip-set vendor, to a single ASIC.

The PowerShift scheme monitors temperature and various PC operations in real-time to reduce power consumption and limit CPU temperature to 70C. Using the same scheme, a user can monitor temperature increases to determine how much to increase PC performance for specific applications.

PowerShift hardware initially will be built into IBM and IBM-compatible ISA, EISA, Micro Channel, VESA local bus and Peripheral Component Interconnect motherboards that use Intel 486 and Pentium microprocessors. The company has also tested the technology with Alpha-based systems and will make a version for Alpha under an agreement with Digital Equipment Corp.

The Power-Shift circuit board plugs into an 82-pin connector built into each Elitegroup-manufactured motherboard. The module packs an 80C51SL microcontroller, some ROMs with PowerShift's specialized power-saving and performance-boosting algorithms, and converter circuitry for translating temperature and performance measurements into digital form. Via the connector PowerShift can access sensors and various components throughout the motherboard to collect information.

A closed-loop circuitry scheme, linked to the controller on the module, monitors the motherboard, disk drives and power supply. When those components are not active, PowerShift slows them down without putting systems into the 'sleep' state used in other energy-conservation solutions.

Power-Shift can shut down inactive display monitors and printers if those devices are designed to respond to PowerShift software commands or if Elitegroup writes the appropriate commands. Sensors incorporated into the architecture monitor PC-component temperature as well as environmental conditions. The technology can detect a problem, such as fan or heat-sink failure, in real-time or use a special software algorithm that can predict an increase in temperature and then cool down or turn off the PC before the CPU is damaged.





# Electronics in Action... Don't leave home without it!

In fact don't leave home to get it either... Just subscribe and wait for it to leap through your letterbox (post free\*) once a month. 66 pages of top projects, in-depth articles and all the latest news, views and happenings from the science technology and electronics world. To make sure you make the best use of your armchair (or your project building workshop) just fill in the coupon and send it to us with either **£27** if you live in the UK or **£42** if you live overseas.



**MAKE SURE  
YOU'RE NOT  
MISSING OUT**

## ELECTRONICS in ACTION

### SUBSCRIPTIONS

Please start my 12 month subscription to **Electronics in Action** from the ..... issue

Please print your name and address in **BLOCK CAPITALS**

Name .....

Address .....

..... Postcode .....

I enclose a cheque/postal order (payable to Electronics in Action) for £ .....

Please send this form to: **Electronics in Action, PO Box 600,  
Berkhamsted, Herts. HP4 1NL**

\*In the UK only

# Mission Co

Computerized data acquisition systems are widely used within industry and scientific research for the purpose of automatically monitoring physical quantities of a system. These quantities may be temperature, pressure, light intensity and sound level.

The present data acquisition system is an 8-bit analogue to digital converter system with an 8-channel analogue multiplexer and a conversion time of 10 $\mu$ s (in other words, 100000 conversions per second). The specification of the data logger is given in Table 1 and the block diagram of the complete system is shown in Figure 1.

An unique feature of this data logger is that it is directly connected to an IBM-PC via the Centronic port. This has several obvious advantages. Firstly no extra input/output card is required. Secondly there is no need to open the computer case for installing I/O cards and thirdly the data logger enables laptop computers to be used for data acquisition applications. In addition, this device is easy to build and costs less than £20 which is much cheaper than the commercial data logging system available on the market.



## Centronic Port

The Centronic port of an IBM-PC, which is also referred to as the printer port or parallel port, is an industrial standard input/output port provided by PCs and is dedicated to interface with printers. A PC at least has one such a port and it is normally labelled as LPT1. Two more printer ports namely LPT2 and LPT3 can be added to the computer by using extra I/O cards. Although the

ports were designed for interfacing with printers, they can also be used to interface with other devices, provided a special electronic circuit is incorporated.

Let us have a look of the Centronic port. One can quickly find that the Centronic port connectors on the computer and on the printer are different. The former is a 25-pin female D-type connector (Figure 2(a)) and the latter a 36-pin female Centronix-type


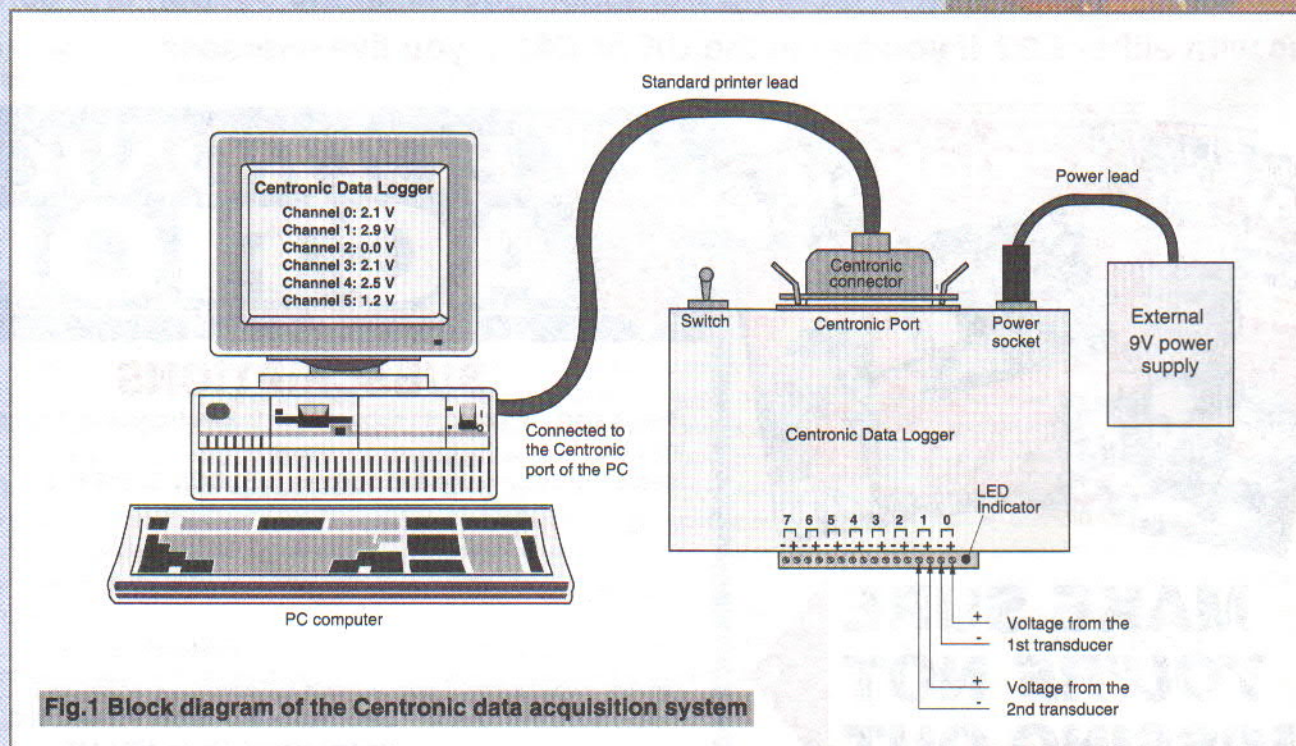


Fig.1 Block diagram of the Centronic data acquisition system

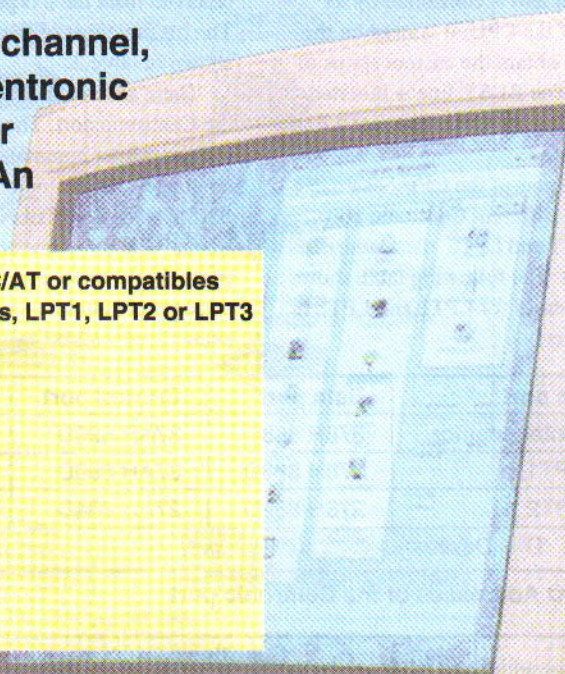
## An 8 bit, 8 channel, IBM-PC Centronic data logger by Dr Pei An




Computer requirement	IBM-PC/XT, PC/AT or compatibles
Interface requirement	Centronic ports, LPT1, LPT2 or LPT3
Supply voltage [V]	9 - 12 DC
supply current [mA]	<100
On-board voltage reference [V]	2.55
Number of input analogue channels	8
Analogue input range [V]	0 - 2.55
Resolution [V]	0.01
Input impedance [MΩ]	>2
Sample time [μs]	10
Size (Length × Width × Height) [mm]	180 × 150 × 60
Weight excluding DC power [Kg]	<0.2

Table 1 Specifications of the data acquisition system

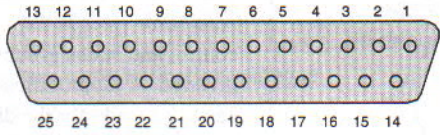Pin functions of the Centronic port connectors



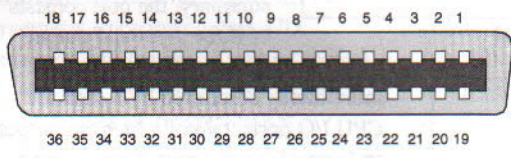(a) Pin-out of the Centronic connector on PC computers - 25 pin female D-type connector



(b) Pin-out of the Centronic connector on printers - 36 pin female Centronic-type connector

Connectors on		Direction	Name	Explanation
computer	printers			
1	1	C to P	STROBE	Strobe data
2	2	C to P	DB0	Data bit 0
3	3	C to P	DB1	Data bit 1
4	4	C to P	DB2	Data bit 2
5	5	C to P	DB3	Data bit 3
6	6	C to P	DB4	Data bit 4
7	7	C to P	DB5	Data bit 5
8	8	C to P	DB6	Data bit 6
9	9	C to P	DB7	Data bit 7
10	10	P to C	ACK	Indicating data received
11	11	P to C	BUSY	Indicating printer busy
12	12	P to C	PE	Indicating paper empty
13	13	P to C	SLCT	Indicating printer on line
14	14	C to P	LF/CR	Auto linefeed after carriage return
15	32	P to C	ERROR	Indicating printer error
16	31	C to P	INITIALIZE	Initialize printer
17	36	C to P	SLIN	Select/deselect printer
18-25	19-30 and 33		GND	Twisted-pair return Ground
	18,34		Unused	
	16		Logic GND	Logic ground
	17		Chasis GND	Chasis ground

'C' = Computer 'P' = Printer

Fig.2 Pin-out of the Centronic port connectors on computers and printers

connector (Figure 2(b)). To link the computer and the printer, a specially designed cable, known as the printer lead, is used. Although the two connector are different in shape, their functions are exactly the same. The pin-out of the two connectors and their pin functions are summarized in Figure 2. Basically the Centronic port consists of 3 input/output groups with each controlled by an I/O ports of the CPU of the computer. These 3 groups are named

the data group, control group and status group and the corresponding ports are the data port, control port and status port (see Figure 3). The functions of these three groups are explained below:  
**Data group:** It has 8 latched output lines (DB0-DB7) which are directed from the computer to the printer and is controlled by an output port of the CPU. In operation, it sends data from the computer to the printer.  
**Control group:** The group has 4

latched output lines (-STROBE, -LF/CR, -SLIN and -INITIALIZE) which are directed from the computer to the printer and is controlled by an output port on the CPU. It transfers commands from the computer to the printer for controlling printer operations. It is noted that the -STROBE, -LF/CR and -SLIN lines are the inverted output of the CPU port. The -INITIALIZE line is not inverted.  
**Status group:** It has 5 input lines (-ERROR, SLCT, PE, -ACK and BUSY)

which are directed from the printer to the computer and is controlled by an input port of the CPU. It is used by the computer to obtain the current status of the printer. The BUSY line is inverted before entering the CPU. The rest 4 lines are not inverted.

Each I/O port of the CPU has an I/O address. For different Centronic ports such as LPT1 and LPT2, these addresses are different. The following table shows the I/O addresses for LPT1 and LPT2 of PC computers:

Centronic port	Data port	Control port	Status port
PC/XT printer adaptor,	378H 888D	37AH 890D	379H 889D
PC/AT, LPT1	378H 888D	37AH 890D	379H 889D
PC/AT, LPT2	278H 632D	27AH 634D	279H 633D

'H' = Hex, 'D' = Decimal

**Table 2 I/O Addresses of the Centronic port**

Bit	Name	Functions
data port bit 0-7	DB0 - DB7	Functions data from bit 0 to bit 7
control port bit 0	-STROBE	LOW=normal; HIGH=Output of data
bit 1	-LF/CR	LOW=normal; HIGH=auto line feed after
bit 2	-INITIALIZE	LOW=initialize printer; HIGH=normal
bit 3	SLIN	LOW=deselect printer; HIGH=Select printer
bit 4		LOW=printer interrupt disabled; HIGH=enabled
bit 5-7		Unused
<b>Status port</b>		<b>Functions</b>
bit 0-2	UNUSED	Unused
bit 3	-ERROR	LOW=printer error; HIGH=no error
bit 4	SLCT	LOW=printer not on-line; HIGH=printer on-line
bit 5	PE	LOW=printer has paper; HIGH=out of paper
bit 6	-ACK	LOW=printer acknowledges data sent; HIGH=normal
bit 7	BUSY	LOW=printer busy;

**Table 3 Bit functions of the input/output ports of the Centronic port**

Inside the computer, data sent to or received from the I/O ports are 8-bit. The bit functions of these ports are shown in table 3.

There are two methods of controlling the Centronic port. The first one is to use the printer commands in computer languages, for example, 'PRINT' in BASIC and 'Writeln(LST)' in Turbo Pascal. The other one is to use direct I/O port access commands to control the three ports individually. Let us take an example of controlling the LPT1 port.

For this port, the address of the data, control and status ports are 888, 890 and 889 decimal, respectively. To send data to the data and control group lines, the following commands can be used:

```
OUT 888, X
OUT 890, X (in BASIC)
```

and

```
PORT[888] := X
PORT[890] := X (in Turbo Pascal)
```

In which X is the decimal value of the binary bit pattern. To read data from the status group, the following commands can be used:

```
Y = INP[889] (in BASIC)
Y := PORT[889] (in Turbo Pascal)
```

The value Y is the decimal value of the input binary bit pattern present at the status group lines. It should be noted

that when writing data to the control group, the 4 output lines corresponds to bits 0 to 3 of port 890 decimal and when reading data from the status group, the 5 input lines correspond to bits 3 to 7 of the port 889 decimal. Also some lines in the control and status groups are inverted. A bit modification has to be made for the data to be sent to the control group and that received from the status port.


So far we have discussed the fundamentals of the Centronic port. As a summary, the port consists of three input and output groups which are

individually controlled by 3 separate CPU I/O ports, two of which are output and one of which input. The first port has 8 output lines, the second has 4 and the third port has 5 input lines.


### The Works

As shown in Figure 4 the data acquisition system can be divided into four units, namely, the input analogue channel switching unit, A/D conversion unit, interfacing unit and power regulating unit. The complete circuit diagram of the system is shown in Figure 5.

The analogue switching unit incorporates a 4051 analogue switch (IC3) which is a low cost 8-to-1 COMS analogue switch. 8 analogue input lines from channels 0 to 7 are connected to pins 13, 14, 15, 12, 1, 5, 2, 4 of the IC3. One of these inputs will be switched to the output (pin 3) by putting an address at pins 11 (bit 0), 10(bit 1) and 9(bit 2),

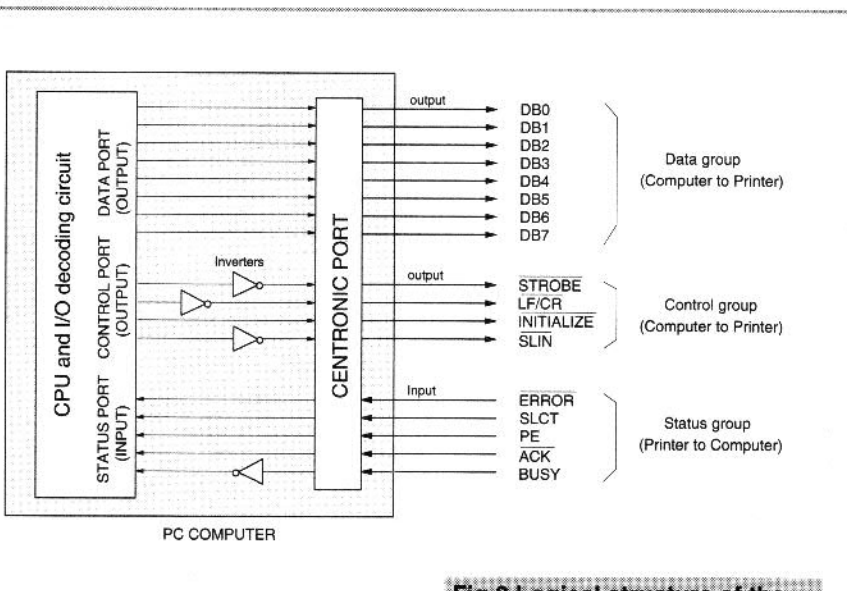

**Fig.3 Logical structure of the Centronic port on the computer**

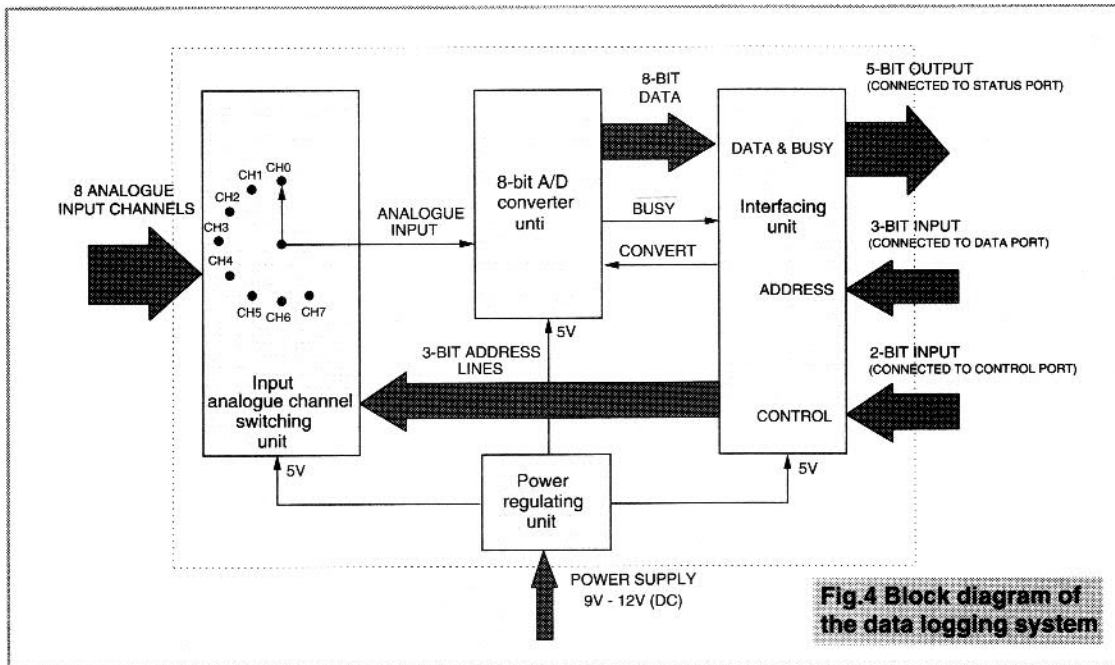

**Fig.4 Block diagram of the data logging system**

which is supplied by the data group lines of the Centronic port via buffers. The voltages to be measured are connected directly to the terminal blocks (J5) on the data logger (see Figure 5).

The A/D conversion unit uses a ZN448 A/D converter IC (IC1), manufactured by Ferranti, which is an 8-bit successive approximation analogue to digital converter with a guaranteed accuracy of 0.5 LSB and minimum conversion time of 9µs. A clock generator and a bandgap voltage reference are included on the chip. The pin-out of the ZN448 is shown in Figure 6(a). When the -CONVERT input (pin 4) receives a low-going signal, the A/D converter is triggered to start A/D conversion and the BUSY output (pin 1) becomes low. The -BUSY output will go high at the end of the conversion

indicating that the conversion is completed. The -RD input (pin 2) is the data enable line which is taken low to enable the data on the output lines (pins 18 to 11) which otherwise are in impedance state. Refer to the circuit diagram (Figure 5), the -CONVERT output (pin 4) is connected to the control group lines of the Centronic port via a buffer. To start a conversion, the computer will send a high-to-low-then-high signal to the -CONVERT line, then it reads the -BUSY output line and check whether it goes high. When high state is detected, the PC reads data from the A/D converter. A clock capacitor (C2) of a value of 100p is connected across pin 3 and the ground (pin 10) which enables the on-board clock generator to operate at about 800KHz. For other clock frequencies C2


has to be chosen according to the manufacture's data sheet. A negative power supply ranging from -3V to -30V should be supplied to pin 5 (-V) via a tail resistor R3, the value of which has to be chosen according to the input voltages. Table 4 shows the required resistance value in relation for various

Voltage(V)	Tall resistor (KΩ)
-3	47
-5	82
-10	150
-12	220
-20	330

**Table 4 Required resistance values of the tall resistor**

voltages:

In the present circuit, the negative voltage is generated by a diode pump circuit driven from the -BUSY output. The principle is that whilst the -BUSY output is high capacitor C3 is charged to about 4 - 4.5 volts. During a conversion, the BUSY output goes low and the upper end of C3 is also pulled low. The low end of C3 therefore applies about -4V to R3. The time constant of R3 and C3 is chosen according to the clock frequency so that the drop of capacitor voltage is not significant during a conversion. Pin 8 of the IC is the output of the 2.55V on-board reference  $V_{ref.out}$ . To use this reference, a resistor R1 and a decoupling capacitor C1 are required and  $V_{ref.out}$  (pin 8) is connected to  $V_{ref.in}$  (pin 7). The input voltage to be measured,

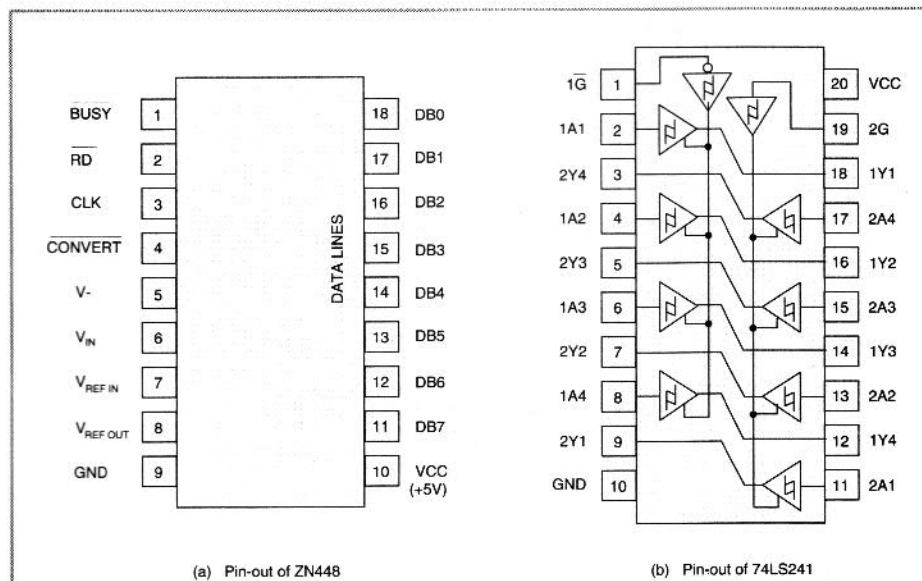

**Fig.6 Pin out and pin function of ZN448 A/D converter and 74LS241 buffer ICs**

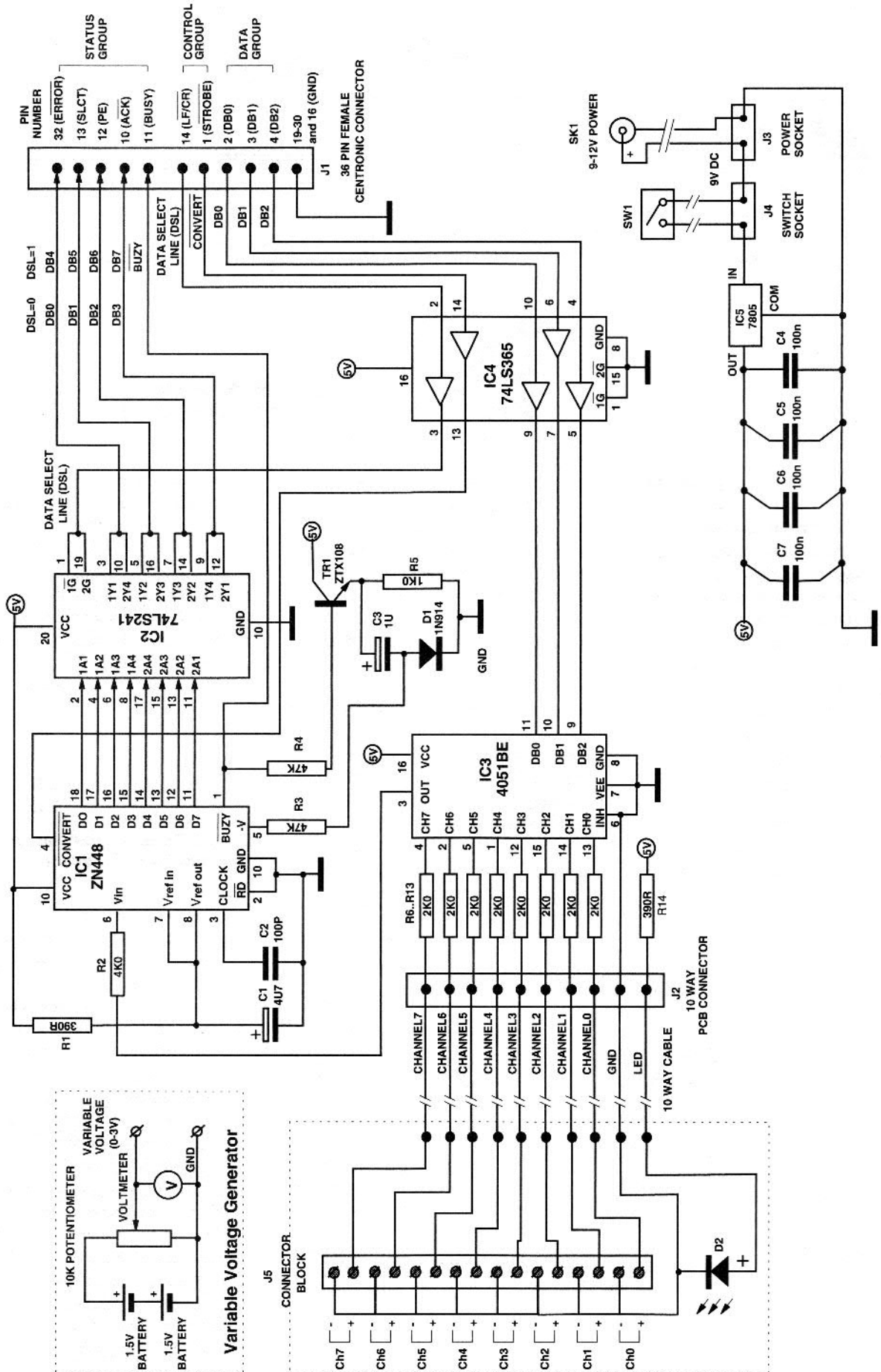


Fig.5 Circuit diagram of the Centronic data logging system

which should be between 0 to +2.55V, is fed to  $V_{in}$  (pin 6) via a resistor R2. A 2.55V input voltage will produce a byte of 255 decimal (FF Hex) at the data lines of the A/D converter. The decimal values for other input voltages are calculated using the following equation:

$$\text{Decimal Value} = \frac{\text{Input voltage}}{2.55 \times 255}$$

The interfacing unit consists of two chips, a 74LS365 IC (IC4) and 74LS241 IC (IC2), and a 36-pin female Centronix-type connector. 74LS365 is a Hex buffer IC which is used to buffer the output lines from the Centronic port. Since the port only have 5 input lines and one of them has already been used for monitoring the -BUSY output of the ZN448, only 4 lines are left for reading the data. To read an 8-bit byte, the 74LS241 IC, the 3 state octal buffer, is used. The pin-out of the 74LS241 is showing in Figure 6(b). We can see that when pin 1 (the 1st enable input) is taken low, the 4 left hand side buffers works (i.e. the outputs will follow the status of the inputs). When pin 19 (the 2nd enable input) goes high the 4 right hand side buffers will work. If pin 1 and pin 19 are connected together to form a Data Selection Line (DSL), by putting

the line low and then high, we can read 4 bits connected to the left hand buffers and the other 4 bits connected to the right hand buffers in turns. Operating in such a manner, the 8-bit data from the A/D converter can be read into the computer (see Figure 5)

The power regulating unit incorporates a 7805 5V voltage regulator for supplying 5V DC to the circuit. A 9-12V DC external power supply is required.

### Programming

The control program of the data logging system is written in Turbo Pascal 6. The flow chart of the program is shown in Figure 7. The program is based on the LPT1 port. Firstly, an initialization procedure is performed which sets the -CONVERT input high. Secondly, a 3-bit address is sent to the data logger to select an analogue channel. It is followed by sending a short high-to-low-then-high pulse to the -CONVERT input. After this the computer starts to read the -BUSY output line continuously until the line becomes high. Then the computer sets the Data Selection Line high and reads the 4 high bits from the converter. Next the Data

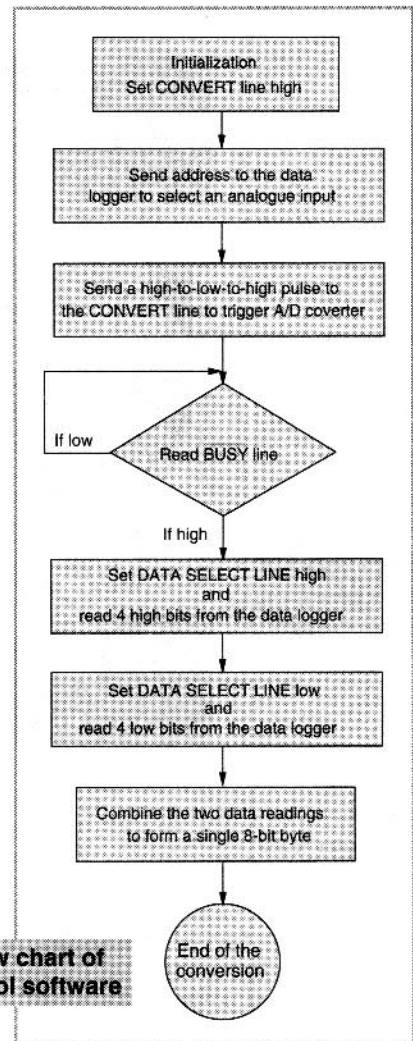


Fig.7 Flow chart of the control software


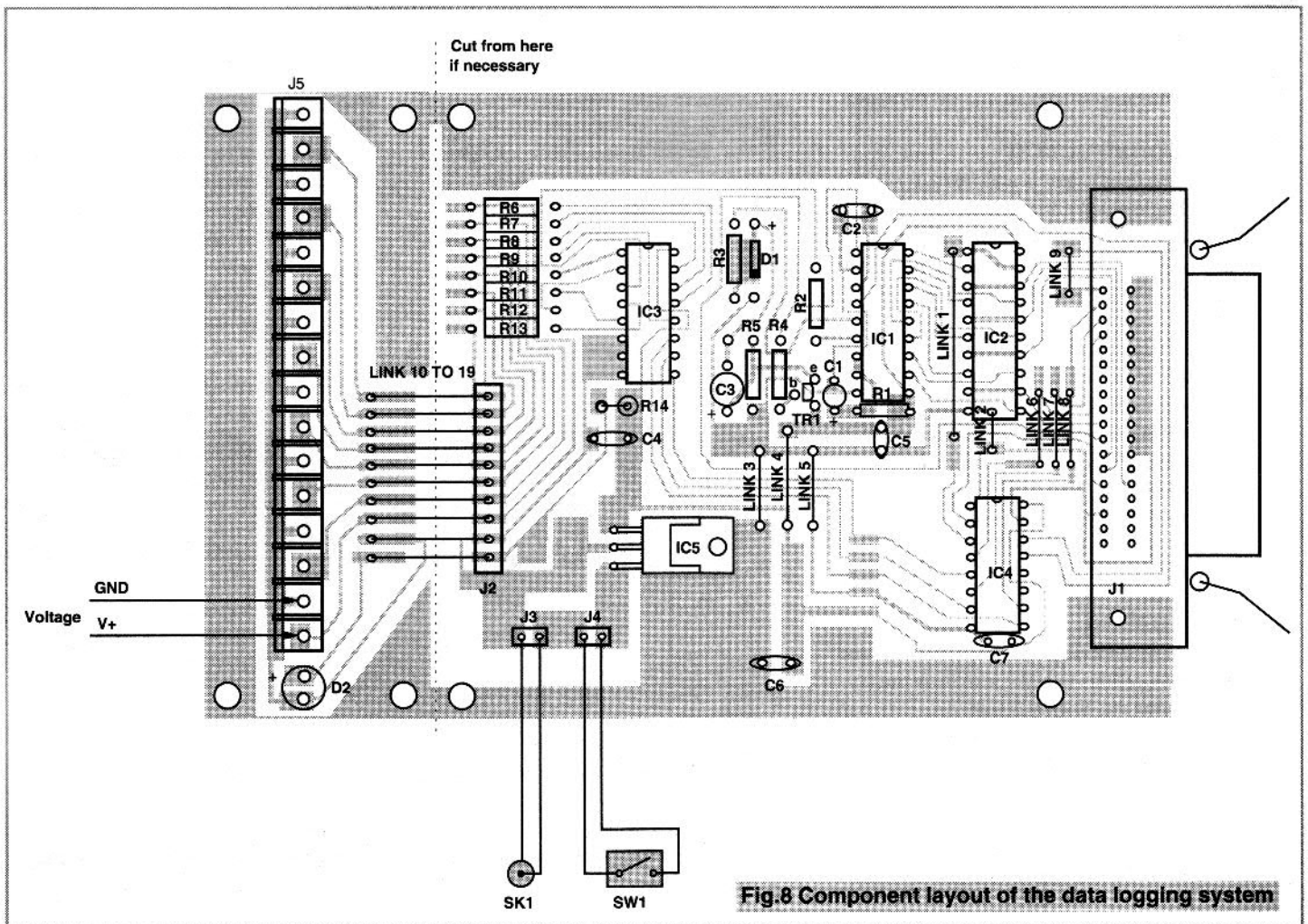


Fig.8 Component layout of the data logging system

Fig.9 Copper foil pattern of the data logging system

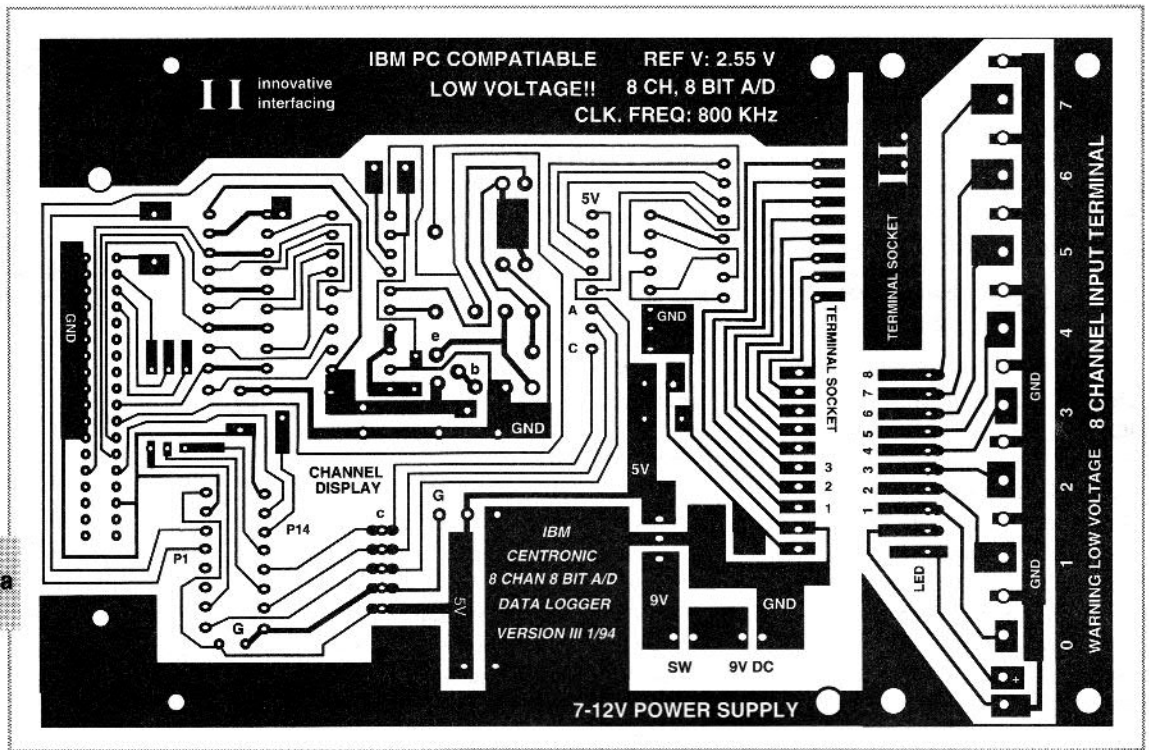

Selection Line is taken low and the computer reads the 4 low bits. The two readings are then rearranged and combined to form a single 8-bit byte which is the byte appeared on the data lines of the A/D converter.

The complete program list is shown on the right. Readers can either type the program into the computer or contact the author for the software written on floppy disks. It is noted that the messages in {} are the explanations and can be omitted when inputting them into the computer.

## Construction

This data logger is constructed on a single-sided printed circuit board. The full size foil pattern and component layout are shown in Figure 8 and 9. The PCB is available from the EIA PCB service on page 57.

Components may be mounted on the board in the following order: links, resistors, diodes, DIL IC sockets, capacitors, electrolytic capacitors, PCB connectors, voltage regulators, Centronix female connector and finally the ICs. It is suggested that the DIL IC sockets are used for IC1 and IC3. IC2 and IC4 can be soldered on the board directly.

## Testing

After soldering, check all the joints and connections to make sure there are no shorts due to excess solder.

Only when you make sure that the board is properly constructed, can you connect the power supply to the data logger! An oscilloscope can be used to check the waveform at pin 3 (CLOCK) of the ZN448. It should be a 800KHz

square wave. A logic probe can also be used for doing this. To connect the data logger to the computer, first of all, switch off the computer and the data logger, then connect the data logger to the printer lead. Next switch on the data logger and the computer. If the computer does not boot up properly turn off the computer, unplug the device and check the board again. If every thing is okay, you can now run the driver program. If the whole system is working properly, the voltages at the analogue inputs should be printed on the computer screen. To test an input channel, connect an 1.5V battery to one of the inputs (Be careful of the polarity!) and use a voltmeter to measure the voltage, that voltage value should appear on the corresponding channel on the screen. A variable voltage generator can also be used to check the system. A simple voltage generator using only two 1.5V

batteries, a potentiometer and a voltmeter can be constructed easily. The circuit diagram is shown in Figure 5.

## Application Note

There are various applications for this data acquisition system. With some simple transducers, it can be used to measure various quantities such as temperature and pressure, etc. There are many dedicated books and papers on the measurement techniques. Readers are encouraged to read some books and explore the possibilities of using the data logging system for various applications. The author would be delighted to hear any suggestions and ideas on this project.

A copy of the program for the data logger is available from the author at a cost of £3-50, including postage and packing. Please send cheques payable to Dr. P An and send them to the EIA office.

EIA

Resistors  
(0.25W, Metal film 1%)

R1,14 390R  
R2 4K0  
R3,4 47K  
R5 1K0  
R6-13 2K0

Semiconductors

IC1 ZN448 A/D converter IC  
IC2 74LS241 octal buffer IC  
IC3 4051BE 8-to-1 analogue switch IC  
IC4 74LS365 hex buffer IC  
IC5 7805 5V voltage regulator IC  
TR1 ZTX108C  
D1 1N914  
D2 Red 5mm LED

## Parts

Capacitors

C1 4µ7/10V electrolytics  
C2 100p Ceramic disc  
C3 1µ/10V electrolytics  
C4-7 100n Ceramic disc

Additional items

J1 36 pin female  
Centronix-type connector  
J2 10 way PCB connector  
J3,4 2 way PCB connector  
J5 16 way connector blocks  
SK1 Power socket  
SW1 Toggle switch  
LINK1-LINK9 Tined copper wire  
24swg  
LINK10-LINK19 Multi-core wires  
PCB (see page 57)



## List of the control program

```
Program Centronic_A_D_Converter;
{This program is written to drive the IBM-PC 8-line 8-bit data logger. The follow program is based on LPT1 Centronic port}
{This program is written in Turbo Pascal 6. The basic version of the program is available from the author}
{Author: P. An 1/1/94}
uses
  crt;
var
  byte1,byte2,truebyte   :byte;
  bitweight,bit         : array [1..8] of byte;
  i,j,CN                : integer;
  V                      : real;
  {byte1 = 4 high bits, byte2=4 low bits,      truebyte = 8 bit byte from the A/D converter}
  { CN = channel number,                      V =Voltage in volts}

Procedure initial_bit;
{Initialize binary bitweight and bit}
begin
  for i:=1 to 8 do begin bitweight[i]:=1; bit[i]:=0; end;
  for j:=1 to 8 do begin
    for i:=1 to j-1 do bitweight[j]:=bitweight[j]*2
                      end;
  end;
end;{of initial_bit}

Procedure initialization;
{initialize the data logging system}
begin
  port[888]:=0;      {Address=0};
  port[890]:=0;     {CONVERT=1, DSL=1};
end;{of initialization}

Function voltage(channel_number,average_number:integer):real;
{Logging data from a specified channel and averaging the value
 channel_number: channels from 0 to 7
 average_number: number to average the measured voltage}
var
  sum:real;
  ii:integer;
begin
  port[888]:=channel_number;      {output the selected channel address to port 888}
  delay(10);      {delay 10 mS}
  sum:=0;
  for ii:=1 to average_number do begin
    initial_bit;
    port[890]:=1;      {CONVERT=0, DSL=1}
    port[890]:=0;     {CONVERT=1, DSL=1}
    repeat
      byte1:=port[889]; {read 1st byte, check BUSY line and wait it to become high}
    until byte1<128; {note: BUSY line is inverted in the PC}
    byte1:=port[889]; {DSL=1. read the high 4 bits}
    port[890]:=2;     {DSL=0}
    byte2:=port[889]; {read the 4 low bits}
    {binary format of byte1 and byte2
     byte1: xxxhhhh0 (high 4 bits)
     byte2: xxx11110 (low 4 bits)
     note: x=do not care, h,1=data}
    byte1:=byte1 and 120; {00011110 and xxxhhhh0 = 000hhhh0}
    byte1:=byte1 shl 1;  {shift 1 bit left, byte1 = 0000hhhh}
    byte2:=byte2 and 120; {00011110 and xxx11110 = 00011110}
    byte2:=byte2 shr 3;  {shift 3 bits right, byte2 = 11110000}

    truebyte:=byte1 or byte2; {byte1 or byte2 = 11110000 or 0000hhhh = 1111hhhh}
    sum:=sum + truebyte/255*2.55; {convert the binary value into a voltage, Reference voltage=2.55V}
    end;



  voltage:=sum/average_number;
end;{of voltage function}

Procedure crtinitialization;
{show initial data on the screen}
begin
  writeln;
  writeln('*****');
  writeln('          IBM-PC 8 input 8 bit analogue to digital converter program');
  writeln('*****');
  writeln;
  writeln;
  for cn:=0 to 7 do
    writeln('          Channel ',cn:3,' Voltage = ');
  gotoxy(10,20);write('Press any key to stop scanning');
end;{of crtinitialization}

procedure display_results;
begin
  gotoxy(40,7+cn);write(V:7:3); {show results on crt}
end;{of display_results}

{=====main program=====}
begin
  repeat
    clrscr;
    crtinitialization;
    initialization;
    for cn:=0 to 7 do begin
      V:=voltage(CN,2); {logging channel CN, average number=2}
      display_results;
      end;
    delay(400); {delay for 400 mS}
  until keypressed;
  gotoxy(10,19);write('Thank you for running this program');
  readln;
end;{of main program}
```

# Intercommun

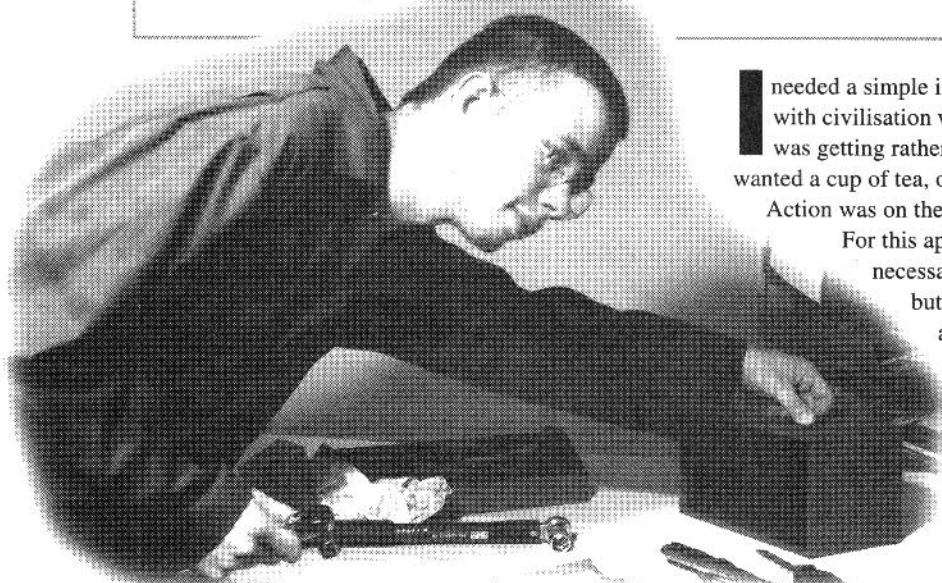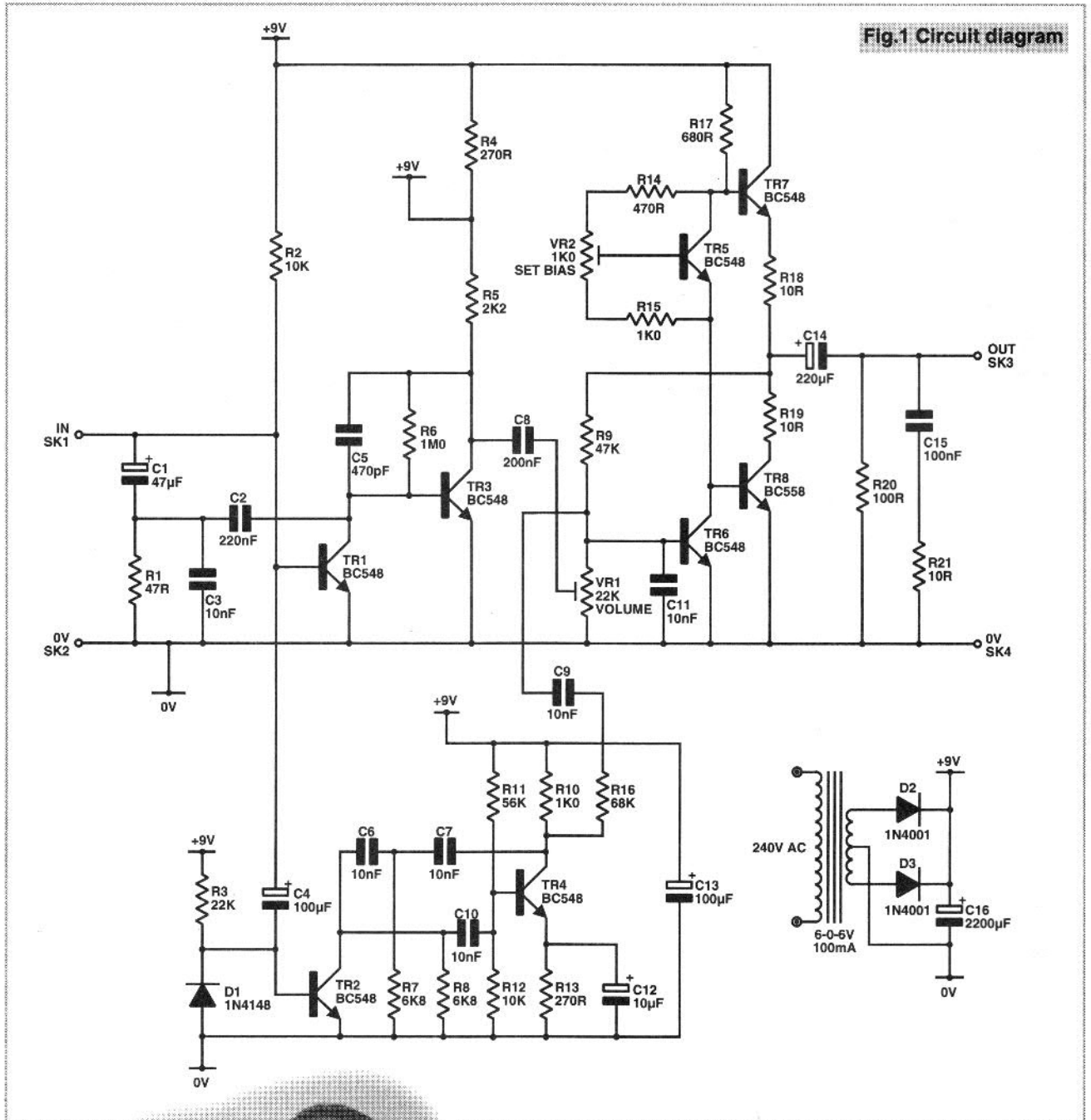

I needed a simple intercom system, so that I could keep in touch with civilisation when I was hiding in my workshop! My partner was getting rather fed up of making journeys just to ask me if I wanted a cup of tea, or to tell me that the editor of Electronics in Action was on the phone!

For this application a separate "call" function is not necessary. Instead I opted for a short tone when the talk button was pressed. This is to get the other person's attention, rather like the "bing" sound on the announcement systems in public places. I was originally hoping for a "peep" sound, although it ended up more like a "pweee"!

There is a talk button at each end, so it's impossible to eavesdrop on the other party -

# ications

## Mark Price keeps in touch with a simple 2 wire intercom.

unlike some cheap commercial systems. However if the remote talk button is replaced with a normal switch, it can be left on so that the system may be used as a baby monitor.

I already had a twelve-core cable between the workshop and the living room, carrying audio from the hi-fi, serial computer data and a telephone extension. There were just two cores left, hence this design for a two-wire system. Any convenient two core cable can be used.

### What - No Chips!

I built this unit using bits from the "Junk Box", and assumed others might like to do the same. If you don't have the right chips, there's no option but to buy them. If you don't have the right transistors, you can usually find something similar, and the same applies with most of the other components. Since the circuit doesn't have to do anything exacting, a simple transistor design is ideal.

There is sufficient gain in the system that a person can be heard clearly when talking at a normal volume, about two feet from the unit. Since the person speaking would be pressing the talk button, this is the maximum distance necessary.

### Construction

The circuit is assembled on a single sided PCB, available from Electronics in Action (page 57). The component overlay and track layout is shown in Figure 3.

Assembly is straightforward and should present no difficulties. None of the component values are critical, there should be no problems using the value above or below if the correct part is not available. If you are using different transistors, ensure that TR7 and TR8 have a maximum collector current rating of at least 100mA.

Ceramic disk capacitors can be microphonic and are not recommended for C2, C3 and C5. The oscillator phase shift capacitors, C6, C7 and C10, should have a good Q rating or the circuit may fail to oscillate. Disk and dipped polyester

### The Works

Figure 1 is the main circuit diagram, and shows the components mounted on the PCB. Figure 2 is the interwiring diagram, which shows the switching arrangement and loudspeakers.

The requirement for a talk switch at each end on a two-wire system complicated the design slightly. Capacitor C17 is connected in series with the remote speaker, and is short-circuited when the talk switch is pressed (R22 limits the discharge current). The electronics at the local end detects the DC path when the switch is pressed.

TR3 and the associated components form the first audio amplifier stage. When a low resistance DC path is present between SK1 and SK2, TR1 will switch off, allowing TR3 to be biased by R6. The audio signal is coupled to the base of TR3 by C1 and C2.

R1 reduces the input impedance to reduce the chance of noise pickup along the long connecting lead. C3 and C5 remove any RF interference that may be present and limit the top end of the frequency response to about 4KHz. The low values of C2 and C8 limit the lower end of the frequency range to about 200Hz. This frequency response is adequate for speech, and allows a high gain to be achieved with minimal problems

types are fine, but the small resistor sized tubular devices are not suitable.

The PCB should be mounted in a suitable enclosure, together with a loudspeaker. A similar box will be

due to hum and noise.


Since TR3 is biased off when the unit is not in use, the gain is low and no hum or noise can be heard.

TR5 to TR8 and surrounding components form a basic class B audio output stage, with a power output of about 200mW RMS into 8Ω. VR2 is adjusted to give a quiescent current of 2mA, to minimise crossover distortion. Preset VR1 sets the audio gain. In use this will probably be set to maximum, although it is useful to be able to reduce this when testing to avoid feedback.

TR4 and surrounding components form a standard RC phase shift oscillator. The output of this is fed into the power amplifier via R16 and C9. TR2 has been added to short out the signal at one of the phase shift points, disabling the oscillator. This transistor is normally held on by R3, however when one of the talk buttons is pressed it is turned off for about half a second. This time is set by the values of R3 and C4. Thus the oscillator produces a brief tone when a talk button is pressed.

The circuit is mains powered using a small six volt transformer. Since the current requirement when the unit is silent is minimal, a 100mA transformer is adequate. The supply to TR3 and TR4 is additionally decoupled by R4 and C13.

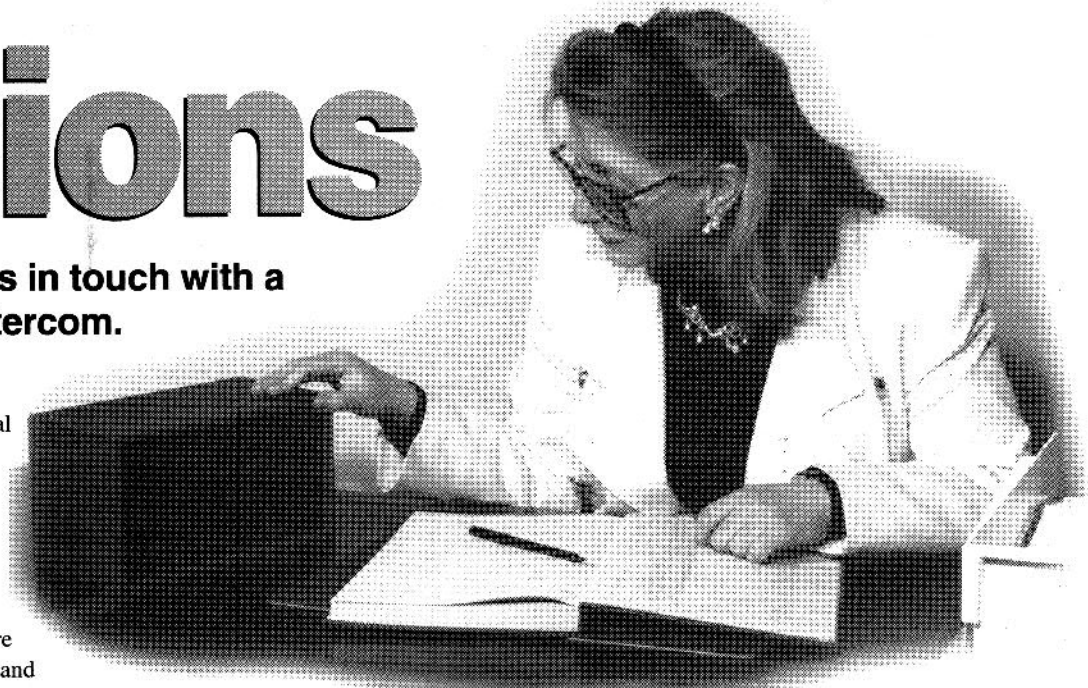needed for the remote unit. The prototype system was built into a pair of small stereo loudspeaker cases, containing 16Ω oval speakers. These are readily available at car boot sales for a



few pounds, complete with a matching defunct stereo record player!

Suitable holes should be made on the top surfaces of both case, for the push button switches. The PCB and transformer can be mounted in any convenient position, in one unit. A suitable connector should be fitted on the rear of each unit for the interconnection cable. If the installation will be reasonably permanent, electrical chock-block connectors will suffice.


The units should then be wired up as shown in Figure 4. If the interconnection cable does not have polarity markings there is a 50% chance that C17 will be the wrong way round! In this case fit two 220µF capacitors in series but opposite ways round as shown.

## Testing

Initially set VR1 to the centre position and VR2 fully anticlockwise. Connect the two units together and connect the master unit to the mains. Connect a voltmeter across R18 or R19 and adjust VR2 to obtain a reading of 20mV. This gives a quiescent current of 2mA, which is sufficient to eliminate crossover distortion with 16R speakers. With 8R speakers it may be necessary to increase this to 3 or 4mA (30 or 40mV), this should only be done if distortion is noticeable.

Both speakers should now be silent. Press the talk button on the remote unit. A brief tone should be heard from the local unit, and you should then be able to hear yourself speaking through the system. Check this the other way too. VR1 should be set so that speech is loud enough to be clear without being deafening. This setting can only be finalised once the units are installed, since feedback will be a problem with both units in the same room.

**Fig.2 Component positioning and foil pattern**

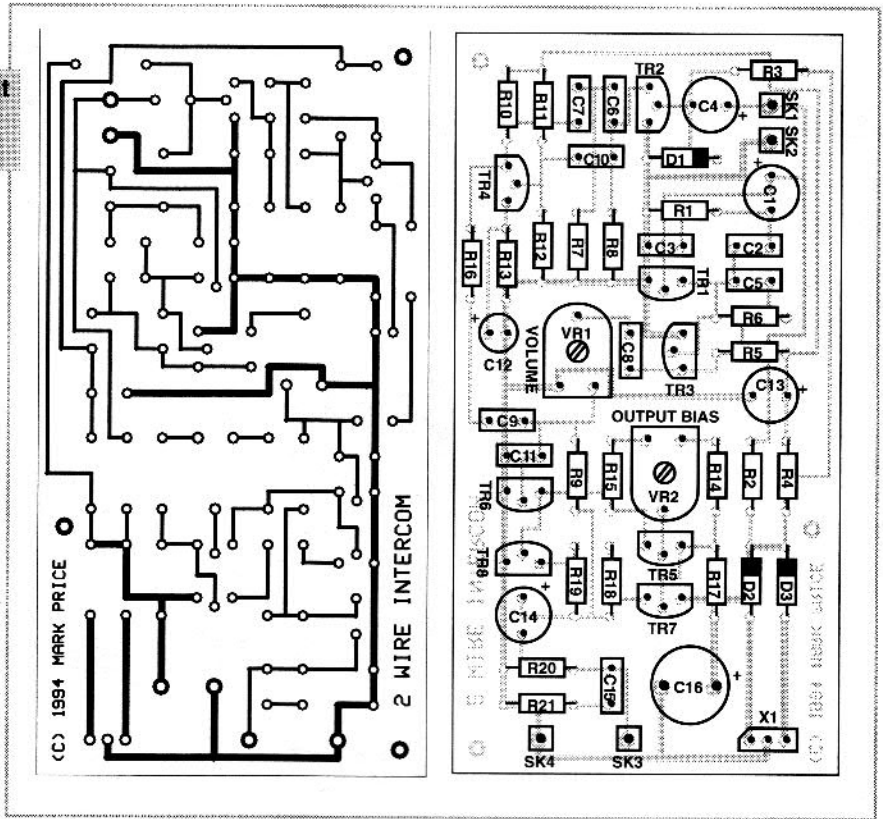

If the volume of the bleep is too loud (unlikely), it can be reduced by increasing the value of R16

## In Use

Push the button to talk and release to listen. If both buttons are pressed simultaneously, the master unit will dominate.

The units will pop as the buttons are pressed and released, this is due to the varying bias on TR3. It is useful to hear when the other party has released the button.

You can now keep in touch with your loved one, and enjoy your hobby. However, there is one problem with such a useful communication system installed - it is much easier for your partner to nag you about how much time you spend in the workshop! Make sure you have the master unit, then you can always "accidentally" unplug it!

## Parts

Resistors (0.25W 5% or better)

R1	47R
R2,12	10K
R3	22K
R4,13	270R
R5	2K2
R6	1M0
R7,8	6K8
R9	47K
R10,15	1K0
R11	56K
R14	470R
R16	68K
R17	680R
R18,19,21,22	10R
R20	100R
VR1	22K Horiz Preset
VR2	1K0 Horiz Preset

Capacitors


C1	47µ 10V
C2,8	220n
C3,6,7,9,10,11	10n
C4,13	100µ 10V
C5	470p
C12	10µ 10V
C14,17	220µ 10V
C15	100n
C16	2200µ 10V

Semiconductors

TR1,2,3,4,5,6,7	BC548
TR8	BC558
D1	1N4148
D2,3	1N4001

Mechanicals

X1	6-0-6V 100mA Transformer
SW1,2	DPDT Push Switch
PCB	Two Loudspeakers (8 or 16R), Two Cases, Two Connectors and Thin 2 Core Flex for Interconnection, Mains Flex.

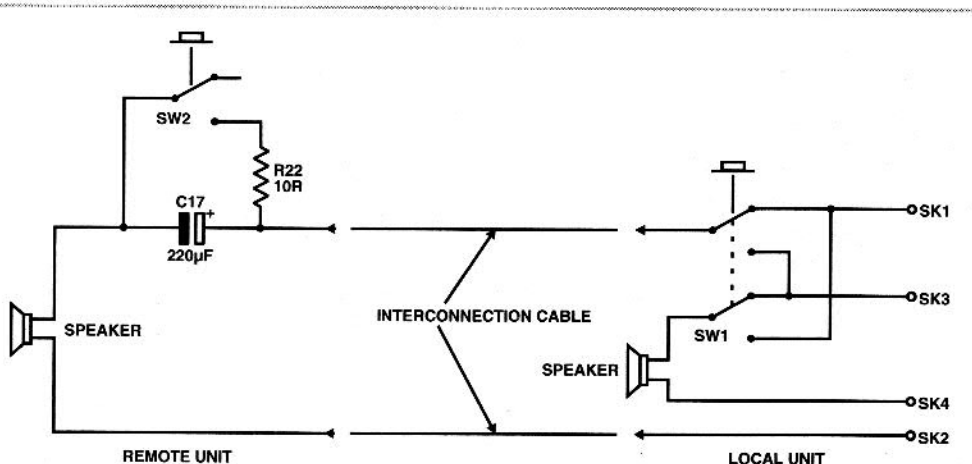


If the polarity of interconnection cable is unknown, replace C17 with two capacitors connected as shown left.

**Fig.3 Interwiring**

OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

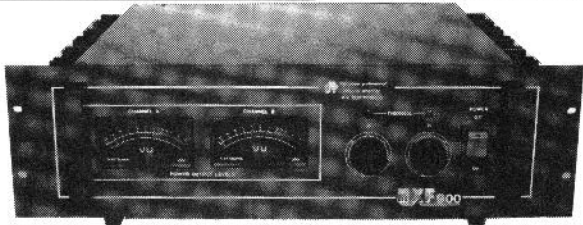THOUSANDS PURCHASED BY PROFESSIONAL USERS



THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W) MXF600 (300W + 300W) MXF900 (450W + 450W) ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: \*Independent power supplies with two toroidal transformers \* Twin L.E.D. VU meters \* Level controls \* illuminated on/off switch \* XLR connectors \* Standard 775mV inputs \* Open and short circuit proof \* Latest Mos-Fets for stress free power delivery into virtually any load \* High slew rate \* Very low distortion \* Aluminium cases \* MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19"xH3 1/2" (2U)xD11" MXF400 W19"xH5 1/4" (3U)xD12" MXF600 W19"xH5 1/4" (3U)xD13" MXF900 W19"xH5 1/4" (3U)xD14 3/4"

PRICES:- MXF200 £175.00 MXF400 £233.85 MXF600 £329.00 MXF900 £449.15 SPECIALIST CARRIER DEL. £12.50 EACH

OMP X03 STEREO 3-WAY ACTIVE CROSS-OVER




Advanced 3-Way Stereo Active Cross-Over, housed in a 19" x 1U case. Each channel has three level controls: bass, mid & top. The removable front fascia allows access to the programmable DIL switches to adjust the cross-over frequency: Bass-Mid 250/500/800Hz, Mid-Top 1.8/3/5KHz, all at 24dB per octave. Bass invert switches on each bass channel. Nominal 775mV input/output. Fully compatible with OMP rack amplifier and modules.

Price £117.44 + £5.00 P&P

STEREO DISCO MIXER SDJ3400SE \* ECHO & SOUND EFFECTS \*

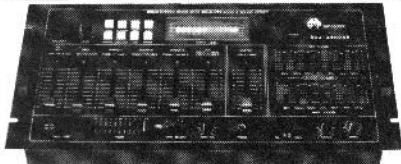STEREO DISCO MIXER with 2 x 7 band L & R graphic equalisers with bar graph LED VU meters. MANY OUTSTANDING FEATURES:- including Echo with repeat & speed control, DJ Mic with talk-over switch, 6 Channels with individual faders plus cross fade, Cue Headphone Monitor, 8 Sound Effects. Useful combination of the following inputs:- 3 turntables (mag), 3 mics, 5 Line for CD, Tape, Video etc.



Price £144.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.


- TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P. TYPE 'B' (KSN1005A) 3 1/4" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P. TYPE 'C' (KSN1016A) 2"x5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P. TYPE 'D' (KSN1025A) 2"x6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P. TYPE 'E' (KSN1038A) 3 3/4" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P. LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.




IBI FLIGHT CASED LOUDSPEAKERS

A new range of quality loudspeakers, designed to take advantage of the latest speaker technology and enclosure designs. Both models utilize studio quality 12" cast aluminium loudspeakers with factory fitted grilles, wide dispersion constant directivity horns, extruded aluminium corner protection and steel ball corners, complimented with heavy duty black covering. The enclosures are fitted as standard with top hats for optional loudspeaker stands.

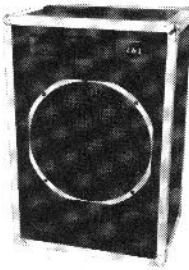POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET FREQUENCY RESPONSE FULL RANGE 45Hz - 20KHz IBI FC 12-100WATTS (100dB) PRICE £159.00 PER PAIR IBI FC 12-200WATTS (100dB) PRICE £175.00 PER PAIR SPECIALIST CARRIER DEL. £12.50 PER PAIR OPTIONAL STANDS PRICE PER PAIR £49.00 Delivery £6.00 per pair



IN-CAR STEREO BOOSTER AMPS

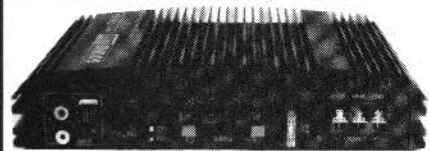

PRICES: 150W £49.99 250W £99.99 400W £109.95 P&P £2.00 EACH

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS 150 WATTS (75 + 75) Stereo, 150W Bridged Mono 250 WATTS (125 + 125) Stereo, 250W Bridged Mono 400 WATTS (200 + 200) Stereo, 400W Bridged Mono ALL POWERS INTO 4 OHMS Features: \* Stereo, bridgable mono \* Choice of high & low level inputs \* L & R level controls \* Remote on-off \* Speaker & thermal protection.



POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLCs ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.



OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible VU meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 300 x 123 x 60mm. PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 50V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 300 x 155 x 100mm. PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Size 330 x 175 x 100mm. PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm. PRICE £132.85 + £5.00 P&P

OMP/MF 1000 Mos-Fet Output power 1000 watts R.M.S. into 2 ohms, 725 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 422 x 300 x 125mm. PRICE £259.00 + £12.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.

LOUDSPEAKERS LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (60p STAMPED) FOR COMPLETE LIST.



McKenzie and Fane Loudspeakers are also available.

EMINENCE- INSTRUMENTS, P.A., DISCO, ETC


- ALL EMINENCE UNITS 8 OHMS IMPEDANCE 8" 100 WATT R.M.S. ME8-100 GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £32.71 + £2.00 P&P RES. FREQ. 72Hz, FREQ. RESP. TO 4KHz, VOCAL, 97dB. EXCELLENT MID. PRICE £33.74 + £2.50 P&P 10" 100 WATT R.M.S. ME10-100 GUITAR, VOCAL, KEYBOARD, DISCO, EXCELLENT MID. PRICE £33.74 + £2.50 P&P 10" 200 WATT R.M.S. ME10-200 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT HIGH POWER MID. PRICE £43.47 + £2.50 P&P RES. FREQ. 65Hz, FREQ. RESP. TO 6KHz, SENS 99dB. PRICE £35.64 + £3.50 P&P 12" 100 WATT R.M.S. ME12-100 GUITAR, KEYB'D, DISCO, VOCAL, EXCELLENT MONITOR. PRICE £36.67 + £3.50 P&P RES. FREQ. 49Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £46.71 + £3.50 P&P 12" 100 WATT R.M.S. ME12-100LT (TWIN CONE) WIDE RESPONSE, P.A., VOCAL, STAGE MONITOR. PRICE £36.67 + £3.50 P&P RES. FREQ. 42Hz, FREQ. RESP. TO 10KHz, SENS 98dB. PRICE £50.72 + £4.00 P&P 12" 200 WATT R.M.S. ME12-200 GEN. PURPOSE, GUITAR, DISCO, VOCAL, EXCELLENT MID. PRICE £46.71 + £3.50 P&P RES. FREQ. 58Hz, FREQ. RESP. TO 6KHz, SENS 98dB. PRICE £70.19 + £3.50 P&P 12" 300 WATT R.M.S. ME12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARD, DISCO ETC. PRICE £50.72 + £4.00 P&P RES. FREQ. 47Hz, FREQ. RESP. TO 5KHz, SENS 103dB. PRICE £50.72 + £4.00 P&P 15" 200 WATT R.M.S. ME15-200 GEN. PURPOSE BASS, INCLUDING BASS GUITAR. PRICE £50.72 + £4.00 P&P RES. FREQ. 46Hz, FREQ. RESP. TO 5KHz, SENS 99dB. PRICE £73.34 + £4.00 P&P 15" 300 WATT R.M.S. ME15-300 HIGH POWER BASS, INCLUDING BASS GUITAR. PRICE £73.34 + £4.00 P&P RES. FREQ. 39Hz, FREQ. RESP. TO 3KHz, SENS 103dB.

EARBENDERS- HI-FI, STUDIO, IN-CAR, ETC


- ALL EARBENDER UNITS 8 OHMS (Except EB8-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm) BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND PRICE £8.90 + £2.00 P&P 8" 50WATT EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB. PRICE £30.39 + £3.50 P&P 10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £42.12 + £3.50 P&P RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB. PRICE £42.12 + £3.50 P&P 10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £46.71 + £3.50 P&P RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB. PRICE £46.71 + £3.50 P&P 12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £46.71 + £3.50 P&P RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB. FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND 5 1/4" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB. PRICE £10.99 + £1.50 P&P 6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB. PRICE £12.99 + £1.50 P&P 8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB. PRICE £16.49 + £2.00 P&P 10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS 3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £9.89 + £1.00 P&P

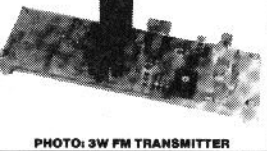


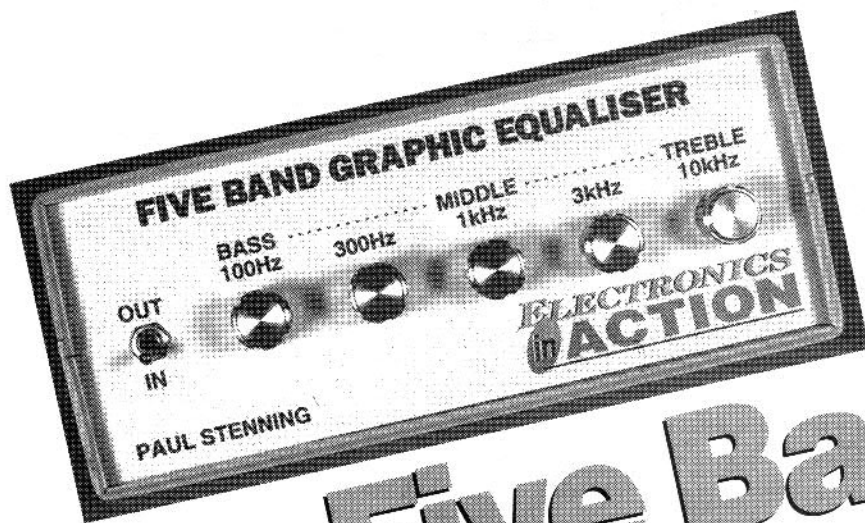B.K. ELECTRONICS UNITS 1 & 5 COMET WAY, SOUTHEND-ON-SEA, ESSEX, SS2 6TR. Tel.: 0702-527572 Fax.: 0702-420243



# Five Band Graphic Equaliser

by Paul Stenning

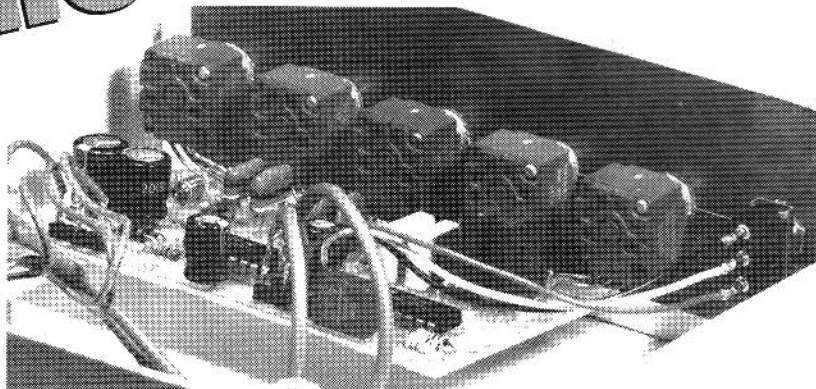

**R**egular readers of this magazine will be aware of my interest in video editing. A Video Effects Unit has already been published, and other video processing projects are planned.

A problem I frequently encounter when copying video tapes is the deterioration in the sound quality. The five band graphic equaliser described here was designed to connect between two video recorders, so that the frequency response can be corrected somewhat. Its use is by no means limited to video recording however, it is a general purpose design that will prove useful for many audio applications.

The five controls each have a range of  $\pm 10$ dB at centre frequencies of 100Hz, 300Hz, 1KHz, 3KHz and 10KHz. The 3dB points on each band are at half and twice the centre frequencies. Thus, the 3dB points on the 100Hz control are at 50Hz and 200Hz. With all controls at maximum the unit has a total gain of 15dB. The unit will

accept an input of up to about 1V RMS (3V pk-pk) before distortion occurs with all controls at maximum.

I do not possess suitable test equipment to measure noise and distortion, although none was apparent on the oscilloscope trace. I would describe the unit as suitable for good quality stereo equipment, but perhaps

## The Works

The complete circuit diagram is shown in Figure 1. This basic circuit principle has been used in several graphic equaliser designs, so I am making no great claims about its originality!

The input is buffered by the first section of IC1, which has unity gain and a consistent output impedance. If any overall gain or attenuation is required, it may be achieved by altering the values of R1 to R4.

To make the explanation of the second stage clearer, assume that all five frequency selective sections have disappeared, as well as four of the control pots. The wiper of the

remaining pot is connected to ground via a 1K $\Omega$  resistor.

If the pot is in the upper position (fully clockwise), the 1K $\Omega$  resistor appears between the inverting input of the op-amp and ground, giving the stage a gain of ten. If the pot track resistance is 10K (five 50K pots in parallel), the signal at the non-inverting input is halved, giving a total gain of five.


With the pot in the lower position (anticlockwise), the input to the non-inverting input is reduced to a tenth, and the gain of the op-amp circuit is two, giving a total gain of a fifth.

With the pot in the centre the gain

of the whole stage is unity, since the attenuation of the input signal is cancelled by the gain of the op-amp. If our imaginary 1K $\Omega$  resistor is replaced with a tuned circuit, the effects described above will only occur around its centre frequency. In this circuit we have five tuned circuits giving the five bands.

Traditionally the tuned circuits would consist of a capacitor and inductor in series. Due to the lack of availability of suitable inductors, modern designs use a gyrator circuit to simulate an inductor. This uses an op-amp to reverse the phase relationship of a capacitor, to make it

**Fig.1 Complete circuit of Graphic equaliser**

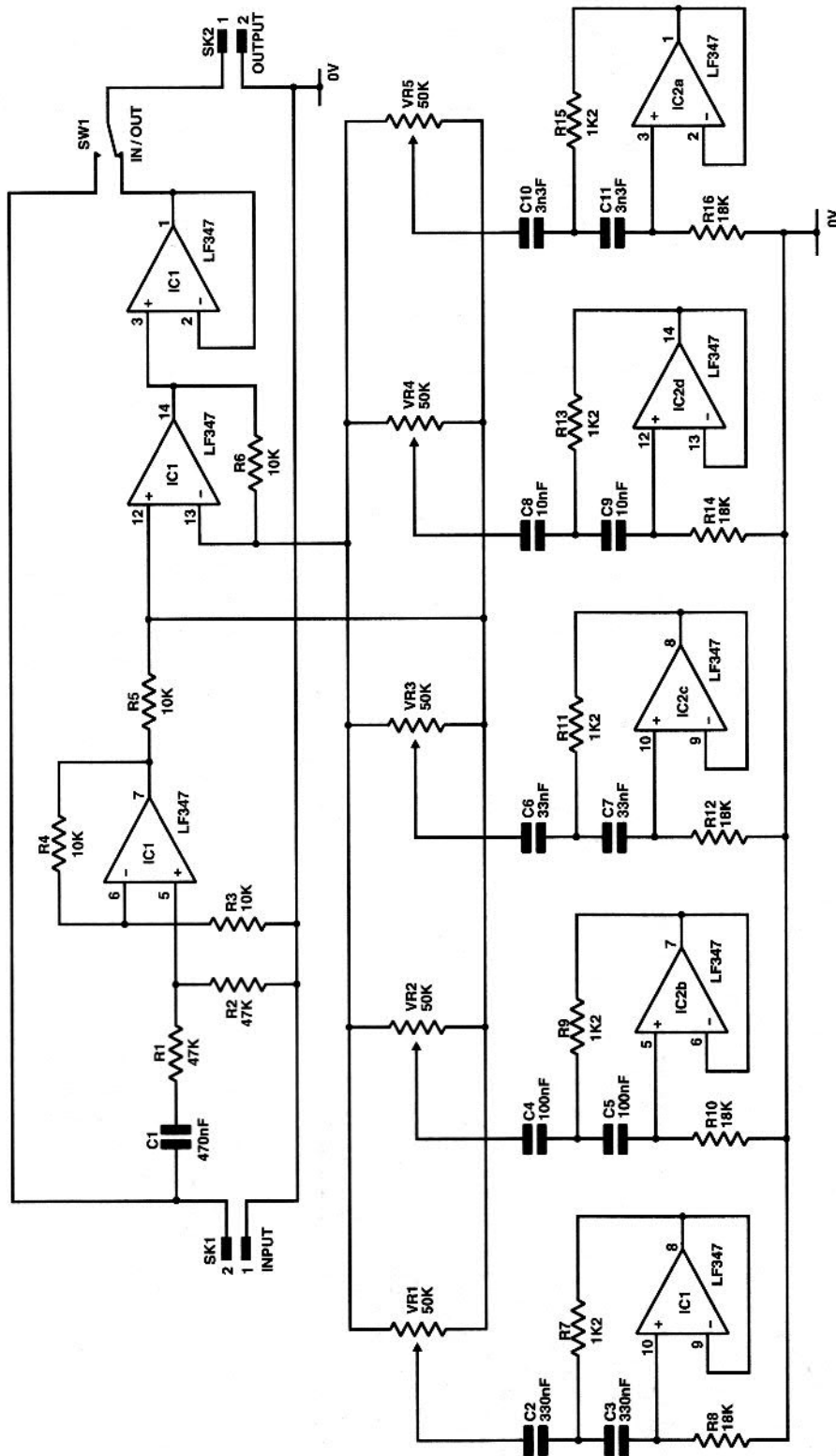

appear like an inductor.

Taking the first stage, C4 is the real capacitor and the op-amp and remaining components form the gyrator. The R7 controls the reactance of our "inductor", and therefore the Q of the tuned circuit. In this case we do not want a particularly sharp response so the Q is fairly low. R7, R8 and C3

all affect the "inductance", and I have yet to find the correct formula for calculating this!

The final output of the circuit is buffered by a unity gain op-amp stage. SW1 selects whether the equaliser is in the audio path.

The circuit requires a supply of +/- 12 to 15V, at less than 10mA. This

does not need to be regulated but must be smooth and have minimal ripple. The output of a 9-0-9 transformer is full wave rectified and smoothed giving approximately +/-13V across the 220µF capacitors. About a volt is dropped by the 100R decoupling resistors, leaving around 12V to power the circuit.

not true hi-fi.

Although the design is mono, a stereo version could be built using two PCBs and stereo pots. More details on this are given later.


## Construction

All the components, except the transformer and pots, are mounted on a single sided PCB. This is 113mm \* 51mm, and is available from the EIA PCB service. The component overlay is shown in Figure 2.

There are two wire links that should be fitted first, along with the resistors and diodes. The remaining components may then be fitted. Sockets may be used for the ICs, but this is not really necessary providing they are fitted last and soldered carefully.

The non-polarised capacitors should be reasonable quality types, dipped polyester or mylar types are suitable. Try to avoid the cheap ceramic disk types, for this project. The PCB holes for these components are on a 0.4" pitch, which is suitable for the suggested types.

Fig.1b Power supply

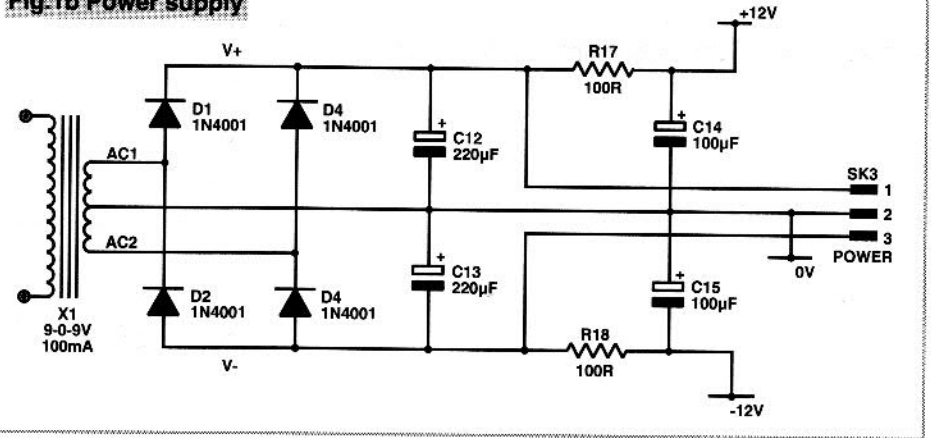

layout, with slider controls and an instrument or desk case.

Whatever case is used, the PCB's should be mounted as close as possible to the control pots. Use short lengths of wire to connect the pot tags directly to the PCB pads. On the PCB, the left pad for each pot is the minimum or anticlockwise end of the track, the centre pad is the wiper, and the right pad is the maximum or clockwise end.

Connect the input socket to the SK1 pads, and the output socket to SK2. In

a stereo unit, connect the transformer to the PCB with the diodes fitted, and link the SK3 pads on the two boards together. The mains input flex may be joined to the transformer primary wires with a choc-block connector or similar.

## Testing and Operation

There is nothing to set up on this unit, it will either work or fail depending on how well it was put together! These few checks with a test meter will confirm that everything is reasonably OK, before connecting the unit to your audio equipment.

First set the test meter to the 20V range, and check the supplies on one of the ICs. There should be about +12V on pin 4 and -12V on pin 13. Now connect the meter to the output (pin 1 of IC1), the voltage should be 0V or thereabouts. Turn each of the five pots to both ends, and check the output remains at almost 0V. If the output is not at 0V (+/- 0.1V) something is wrong, which should be investigated. Now connect the unit to your audio equipment, cross your fingers, and try it.

If the output of this unit is connected to a video recorder or some other piece of equipment with an automatic level control, you may find that the sound level drops if the 100Hz or 300Hz controls are turned up too far. Most automatic level circuits respond more to the bass frequencies.

Bearing this in mind, faint and grotty recordings can sometimes be avoided by turning the 100Hz and 300Hz bands down a bit to reduce the effect of the level control. Turn the 1KHz and 3KHz up a bit to improve the clarity, and turn the 10KHz down to get rid of any hiss. The result may sound a bit thin, but it is better than a quiet muffled sound with tape hiss.

There's not much else I can say about using this unit. Most people know what a graphic equaliser does, and a little trial and error will show the effect of each frequency band.

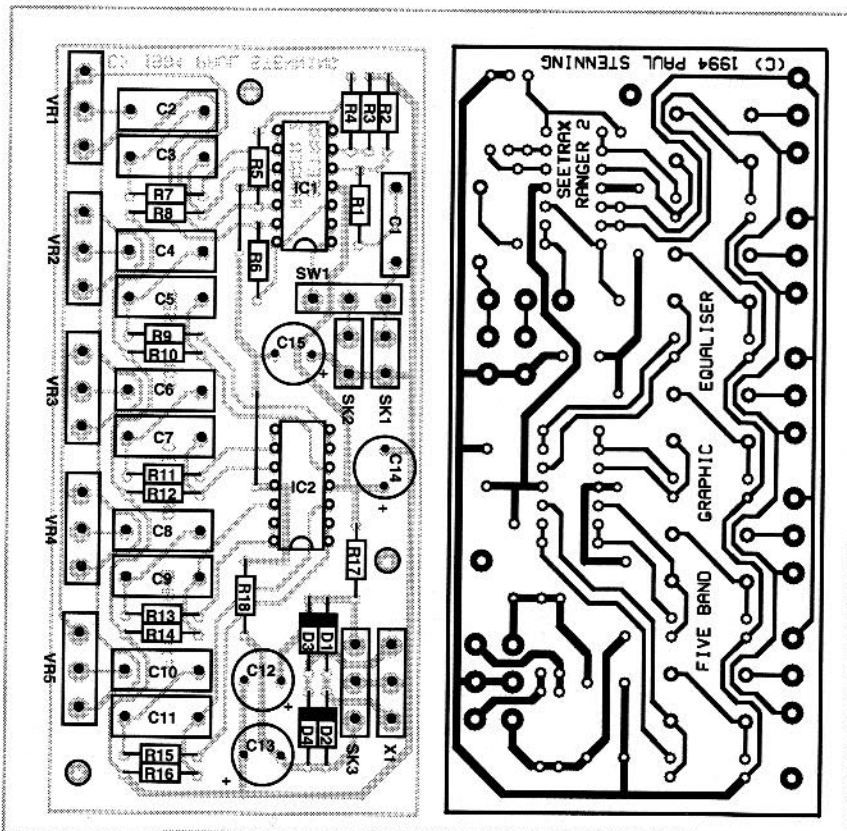


Fig.2 Component positioning and foil pattern

Two PCBs are required for a stereo unit. Do not fit D1-D4, C12 and C13, on one PCB.

The prototype had rotary pots, and was constructed in a plastic case that matched my other projects. Many constructors may prefer a more orthodox

both cases the centre core of the screened cable goes to the left pin. The IN/OUT switch connects to the SW1 pads, with the wiper to the centre pad.

The transformer may now be connected to the X1 pads on the PCB, with the centre tap to the middle pad. For



# Parts

(0.25W 5% or better)

R1,2 47K  
 R3,4,5,6 10K  
 R7,9,11,13,15 1K2  
 R8,10,12,14,16 18K  
 R17,18 100R  
 VR1,2,3,4,5 50K Pot


C1 470n  
 C2,3 330n  
 C4,5 100n  
 C6,7 33n  
 C8,9 10n  
 C10,11 3n3  
 C12,13 220µ/16V  
 C14,15 100µ/16V

9-0-9V 100mA Transformer  
 PCB (see page 57)  
 Case  
 Knobs  
 SPDT Switch  
 Two Phono Sockets  
 Screened Cable  
 Wire  
 Mains Flex

IC1,2 LF347  
 D1,2,3,4 1N4001



## FIVE BAND GRAPHIC EQUALISER

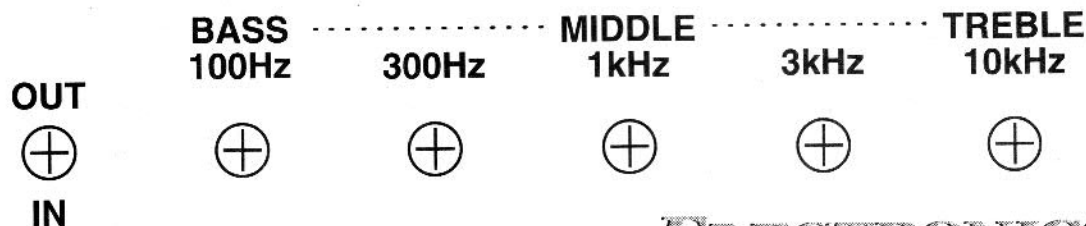

PAUL STENNING

*ELECTRONICS*  
 in ACTION

Fig.3 Front panel design (shown full size)



**DELICIA**  
 THE TRANSMITTER PEOPLE

**4 WATT PPO FM BROADCAST (Built) TRANSMITTER:** with Low Pass Filter  
 Modulation .....75KHz Wide Band  
 Range ..... up to 4-2 miles  
 Supply ..... 10-16 Volts AC/DC  
 Current ..... 250mA  
 Audio Input ..... 100mV (ADJ)  
 Frequency range ..... 88-108MHz FM  
 Stability ..... ± 20KHz  
 Size ..... W. 70mm, D. 90mm, H. 50mm.  
**MANY USER CONTROLS ..... Price: £23.50**

**7 WATT PPO FM BROADCAST (Built) TRANSMITTER:** Higher Watt  
 Version of above Transmitter  
 (Range 7 miles)..... **Price: £52.50**

**KIT: 3 WATT TRANSMITTER 80-108MHz**  
 Coil Tank Controlled up to 3 miles range.  
 Supply 12V dc at 0.5 amps..... **Price: £12.50**

ALL PRICES INCLUDE VAT  
 PLEASE ADD £1 P&P PAYMENT WITH  
 ORDERS TO:

DELICIA ELECTRONICS,  
 14 ST. MERYL PARK, GLEN ROAD,  
 BELFAST, BT11 8FY. Tel: (0232) 611995  
 Please send Two 1st class stamps for our catalogue.



## Cooke International SUPPLIER OF QUALITY USED TEST INSTRUMENTS

ANALYSERS, BRIDGES, CALIBRATORS,  
 VOLTMETERS, GENERATORS, OSCILLOSCOPES,  
 POWER METERS, ETC.  
 ALWAYS AVAILABLE

ORIGINAL SERVICE MANUALS FOR SALE  
 COPY SERVICE ALSO AVAILABLE

EXPORT, TRADE AND UK ENQUIRIES WELCOME  
 SEND SAE FOR LISTS OF EQUIPMENT AND  
 MANUALS

REPAIRS & CALIBRATION UNDERTAKEN  
 ENQUIRE FOR DETAILS

ALL PRICES EXCLUDE VAT AND CARRIAGE  
 DISCOUNT FOR BULK ORDERS. SHIPPING ARRANGED

OPEN MONDAY TO FRIDAY 9AM-5PM

**COOKE INTERNATIONAL  
 ELECTRONIC TEST & MEASURING INSTRUMENTS**

Unit Four, Fordingbridge Site, Main Rd, Barnham,  
 Bognor Regis, West Sussex PO22 0EB  
 Tel: (+44) 0243 545111/2 Fax: (+44) 0243 542457

•HIGH END TEST & COMMUNICATIONS EQUIPMENT PURCHASED •

# Signal to NOISE

The Editor  
Electronics in Action

PO Box 600, Berkhamsted Herts. HP4 1NL

## Pro-quality components problem

Firstly congratulations on the continuing high quality of the publication - apart from minor errors it is really very good. Like your correspondent J R Evans (Feb 94) my own sphere of interest is studio quality analogue audio - preferably balanced - and I hope that you will continue to feature circuits of this nature.

Again like Mr Evans I also favour practical designers like Mike Meechan and Ben Duncan who do not pay lip service to much of the hi-fi hype but whose designs deliver the goods both technically and sonically.

For my own part, I suppose I do not undertake a great deal of actual construction mainly for reasons of financial constraints but when I do the biggest problem that I encounter is actually sourcing pro quality components in small quantities, especially precision capacitors and resistors.

Most component manufacturers are happy to supply literature - although some never bother to reply but I suppose this is indicative of the state of British enterprise.

However, for components a little out of the ordinary I have found that distributors are only interested in orders of 100s. This has recently happened to me in respect of really good quality PSU reservoir capacitors for my present brainchild, an audio power amp, where I wanted audio quality elcos that would fit vertically within a 2U case - easy to find, difficult to buy! (And I'm still looking).

The main reason for the above story is to ask if anyone is aware of any distributors who handle pro components and who would be prepared to deal in small quantities - it would be worth paying a slight premium to ensure component quality.

Finally I look forward to Mike's audio projects in the near future.

**A G Crane**  
King Lynn  
Norfolk


I am writing to you to say thanks for the Photo CD player that I won in your December competition.. I have only recently been able to set it up and I have found the quality amazing.


Once again many thanks as this is the first time I have won a competition. Having enjoyed reading Electronics in Action and am looking forward to each issue in the future.

**F R Stephens**  
Worthing  
Sussex

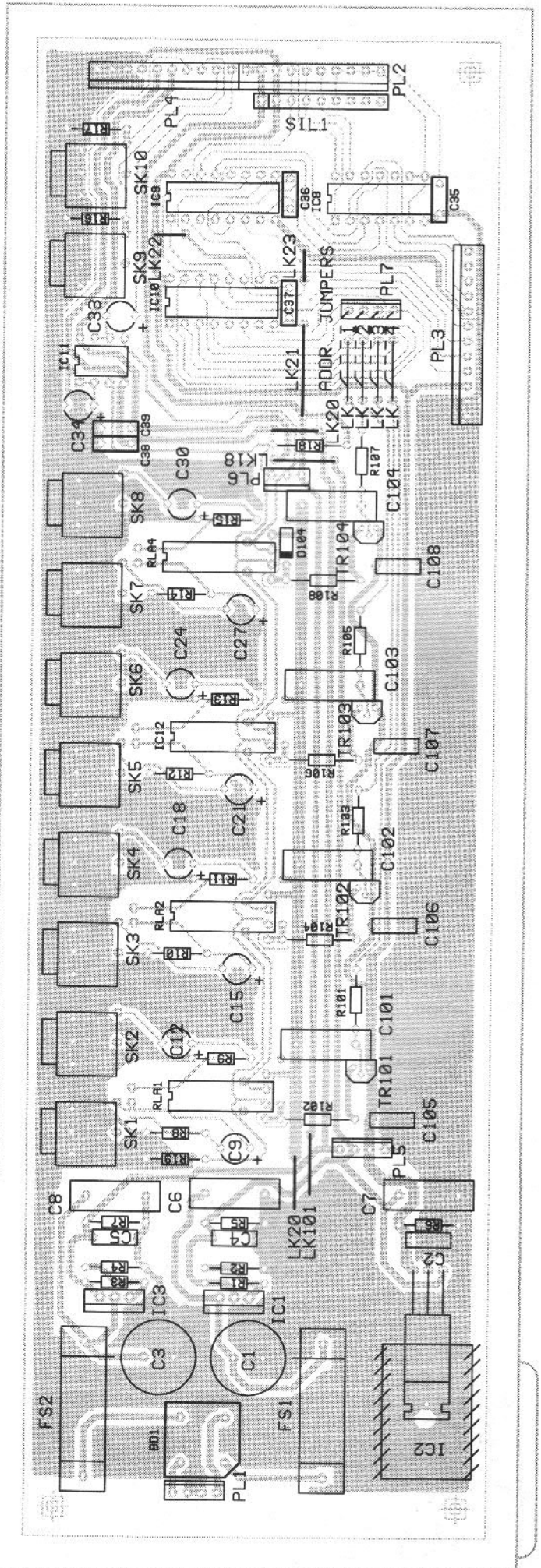
# Clang

Owing to a shortage of space last month we were unable to print the component positioning diagram of The Switcher relay board. We reproduce it here.



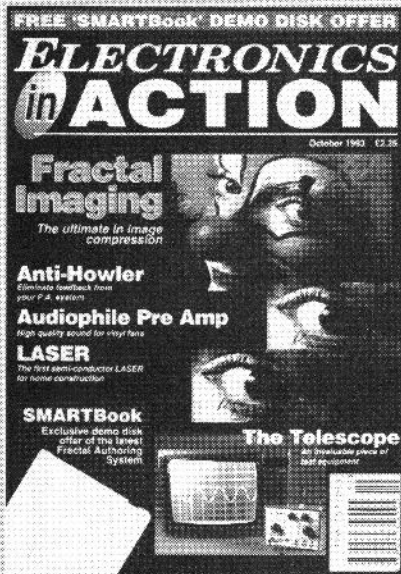

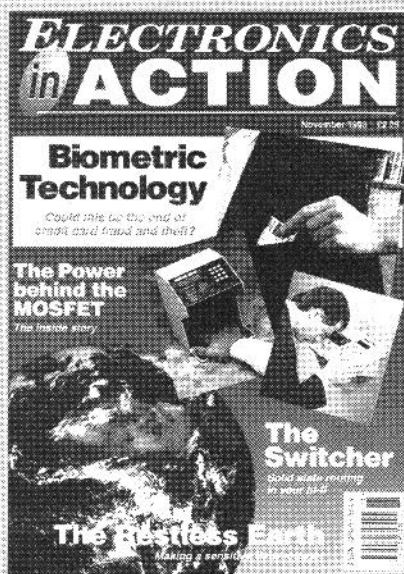
**October 93** ●Fractal Imaging ●The Telescope Pt1 ●Anti-Howler ●Audiophile Pre-amp ●Sine wave generator




**November 93** ●Biometric Technology ●The Switcher Pt1 ●Selsmometer Project ●The Telescope Pt2
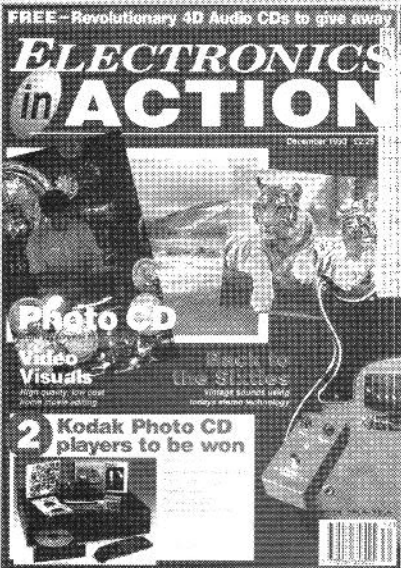
# HAVE YOU MISSED A FEW?


Fear not, our Back Numbers Dept. should be able to furnish you with almost any issue (our January issue was simply too popular). Just fill in the coupon below and post it to us with a cheque or postal order for the correct amount.



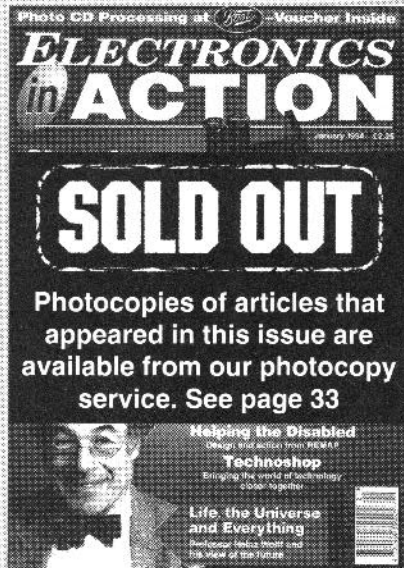
**December 93** ●Photo CD ●4D Recording ●Video editing unit ●Stereo tremolo unit ●The Switcher Pt2



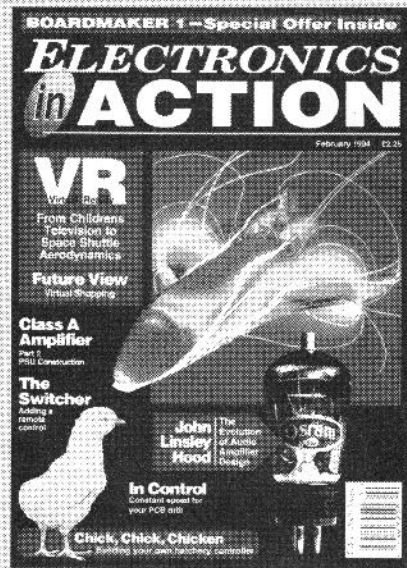**January 94** ●Class A power amp ●The Harmoniser ●Remote control extender ●The Switcher Pt3



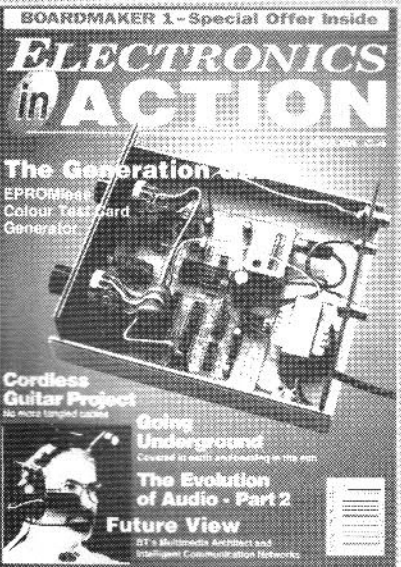**February 94** ●Virtual Reality ●Class A amp Pt2 ●Hatchery Controller ●The Switcher Pt4



**March 94** ●Colour test card generator ●Cordless guitar project ●Plug-in mains wiring tester ●Intelligent Communication Networks ●The Switcher Pt5

## BACKNUMBERS

Print your name in **BLOCK CAPITALS**

Name .....

Address .....

..... Postcode .....

Please send me ..... issue(s) of the October '93 edition

Please send me ..... issue(s) of the November '93 edition

Please send me ..... issue(s) of the December '93 edition

Please send me ..... issue(s) of the February '94 edition

Please send me ..... issue(s) of the March '94 edition

Each copy (including postage & packing) costs £2.50

I enclose a cheque/postal order for .....

Please send to: **Electronics in Action, PO Box 600 Berkhamsted, Herts. HP4 1NL**



# HART

## HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI


HART KITS give you the opportunity to build the very best engineered hifi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase. Our list will give you fuller details of all our Audio Kits, components and special offers.
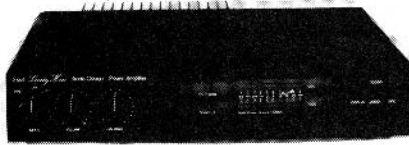
### AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hifi system. This kit is your way to get £K performance for a few tenths of the cost! Featured on the front cover of 'Electronics Today International' this complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- "The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout." Options include a stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monobloc' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heatsink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component ident side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH11 Reprints of latest articles.....£1.80  
K1100CM HART Construction Manual.....£5.50

### LINSLEY HOOD 1400 SERIES ULTRA HIGH-QUALITY PREAMP

Joining our magnificent 80 Watt power amplifier now is the most advanced preamplifier ever offered on the kit, or indeed made-up marketplace. Facilities include separate tape signal selection to enable you to listen to one programme while recording another, up to 7 inputs, cross recording facilities, class A headphone amplifier, cancellable 3-level tone controls and many other useful functions, all selected by high quality relays. For full details see our list.

Send or 'phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write or telephone your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:-INLAND Orders up to £20 - £1.50,

Orders over £20 - £3.50. Express Courier, next working day £10.  
OVERSEAS - Please see the ordering information with our lists.

### LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIERS



Modern, ultimate sound systems are evolving towards built-in preamplifiers within or near the turntable unit. This keeps noise pickup and treble loss to a minimum. We now offer two units, both having the sonically preferred shunt feedback configuration to give an accurate and musical sound, and both having the ability to use both moving magnet and moving coil cartridges.

Kit K1500 uses modern integrated circuits to achieve outstanding sound quality at minimal cost. The very low power requirements enable this unit to be operated from dry batteries and the kit comes with very detailed instructions making it ideal for the beginner. K1500 Complete kit with all components, printed circuit board, full instructions and fully finished case.....£67.99  
Instructions only.....£2.80

Kit K1450 is a fully discrete component implementation of the shunt feedback concept and used with the right cartridge offers the discerning user the ultimate in sound quality from vinyl disks. Can be fitted inside our 1400 Preamp, used externally or as a standalone unit. It has a higher power requirement and needs to be powered from our 1400 Series preamplifier or its own dedicated power supply. K1450 Complete Discrete Component RIAA Phono Preamp.....£109.58  
Factory Assembled and Tested.....£159.58  
K1565 Matching Audio Grade Power Supply with potted toroidal transformer and limited shift earthing system.....£79.42  
Factory Assembled and Tested.....£118.42  
U1115 Power Interconnect Cable.....£7.29

### SPECIAL OFFER PRECISION Triple Purpose TEST CASSETTE TC1DD.

Are you sure your tape recorder is set up to give its best? Our latest triple purpose test cassette checks the three most important tape parameters without test equipment. Ideal when fitting new heads.

A professional quality, digitally mastered test tape at a price anyone can afford.

Test Cassette TC1DD.....Our price only £10.99.

### DISK-COUNT Classical CDs.

Top Quality, Full Digital (DDD) Compact Disks of the great classical favourites.

Like everyone else we didn't like the idea of paying silly prices for CDs. After a long search we have now located a source of top quality classical recordings at prices that make you suspect the quality - until you try them! Send for our list of titles.

### CDROMs

Like music CDs these have overpriced for some time but with low prices of CD ROM drives the multimedia revolution is with us now. Send for our list of titles. Most popular up to now have been "Too Many Typefonts" with 514 TrueType fonts along with 393 ATM and lots of others.

"Shareware Overload" with over 6100 programs extending to 550MB and "Kodak Photo CD Access". The first two are only £12.95, the Kodak only £24.

### TECHNICAL BOOKSHELF

Modern Books. Selected to represent the state of the art today.

#### "THE ART OF LINEAR ELECTRONICS."

J.L. Linsley Hood.

Just Out! Hot off the Press, the definitive electronics and audio book by the renowned John Linsley Hood.

This 300+ page book will give you an unparalleled insight into the workings of all the types of audio circuits. Learn how to read circuit diagrams and understand amplifiers and how they are designed to give the best sound. The virtues and vices of passive and active components are examined and there are separate sections covering power supplies and the sources of noise and hum. As one would expect from this writer the history and derivation of audio amplifier circuitry have an entire chapter, as does test and measurement equipment.

Copiously illustrated this book is incredible value for the amount of information it contains on the much neglected field of linear, as opposed to digital, electronics. Indeed it must be destined to become the standard reference for all who work, or are interested in this field.

#### SPECIAL OFFER.

With each book purchased you may request a FREE extended index, written by the author, exclusively from HART. 0-7806-0868-4.....£16.95

Don't forget most of our kits have reprints of articles by John Linsley Hood that you can purchase separately.

#### "THE ART OF SOLDERING"

R Brewster.

Absolutely essential reading for anyone who ever picks up a soldering iron. Written from knowledge gained in a lifetime in the field, this is the first book ever solely devoted to this essential and neglected skill for all electronic enthusiasts. Covers everything from the correct choice of soldering iron and solder to the correct procedures to follow with many illustrations and practical exercises.

0-85935-324-3.....£3.95

#### "AUDIO" F.A. Wilson.

320 pages. 178 x 111. Publ. 1985

BP111 "AUDIO" by F.A. Wilson.....£3.95

#### "AN INTRODUCTION TO LOUDSPEAKERS & ENCLOSURE DESIGN" V Capel.

160 pages. 178 x 111. Publ. 1988

BP256.....£2.95

#### "LOUDSPEAKERS FOR MUSICIANS" V Capel.

176 pages. 178 x 111. Publ. 1991.

BP297.....£3.95

#### "HOW TO USE OSCILLOSCOPES & OTHER TEST EQUIPMENT" R. A. Penfold.

112 pages. 178 x 111. Publ. 1989

BP267.....£3.50

#### Classics from the "Golden Age"

#### "THE WILLIAMSON AMPLIFIER."

D.T.N. Williamson.

In April 1947, Williamson's power amplifier, using excellent quality push-pull output valves, a special output transformer, and a highly filtered power supply, became an overnight success. The author takes the reader deep into his design considerations, offering practical advice on how to build the units plus concise instructions on setting up the new amp. A cult classic.

1947, Reprinted 1990. 40 pages.

0-9624-1918-4.....£4.95

#### LOUDSPEAKERS; THE WHY AND HOW OF GOOD REPRODUCTION.

G.A. Briggs

This easy-to-read classic, last revised in 1949, introduces the reader to concepts such as impedance, phons and decibels, frequency response, response curves, volume and watts, resonance and vibration, cabinets and baffles, horns, room acoustics, transients, crossovers, negative feedback, Doppler and phase effects, and much more. A provocative survey of the right questions about sound reproduction.

1949 reprinted 1990. 88 Pages. 215 x 140

0-9624-1913-3.....£6.95

#### COMPUTER TITLES.

#### "A CONCISE ADVANCED USERS GUIDE TO MS DOS"

N. Kantaris.

144 pages. 198 x 130. Publ. 1992

BP264.....£3.95

#### "A CONCISE USERS GUIDE TO MS DOS 5"

N. Kantaris.

144 pages. 198 x 130. Publ. 1992.

BP318.....£4.95

#### "MAKING MS DOS WORK FOR YOU"

N. Kantaris & P.R.M. Oliver

160 pages. 198 x 130. Publ. 1993.

BP325.....£4.95

#### "A CONCISE USERS GUIDE TO WINDOWS 3.1"

N. Kantaris.

160 pages. 198 x 130. Publ. 1992.

BP325.....£4.95

QUALITY AUDIO KITS

24 hr. SALES LINE (0691) 652894

ALL PRICES INCLUDE UK/EC VAT

HART ELECTRONIC KITS LTD  
3 PENYLAN MILL  
OSWESTRY, SHROPSHIRE  
SY10 9AF



In this part, John Linsley Hood introduces transistor 'Hi-Fi' and the great quasi-complementary swindle.

In the last part of this article I looked at the designs used in early attempts to design audio amplifiers based on transistors. The need at that time was to use inter-stage coupling transformers but this made it difficult to apply enough overall negative feedback to increase the bandwidth and reduce the harmonic distortion to levels which would be acceptable in a hi-fi system.

A solution to this difficulty was proposed in 1956 by H. C. Lin, an ingenious electronics engineer from the USA. His answer was to use a high gain, small signal amplifier stage to provide the necessary voltage gain, and then to reduce its output impedance to a low enough level to drive a loudspeaker load by the use of a push-pull pair of output emitter followers, as I have shown in Figure 1.

At the time of the Lin circuit, the only transistors available in any quantity, at sensible prices, were Germanium diffused junction types, made on what was virtually a one-off basis, and their use led to a lot of snags. To start with, since the transistors were made by a one at a time process, they would probably vary considerably from one to another, and any circuit using them would need individual setting up on test, a procedure which might need to be repeated from time to time during use.

Also, the amount of power which could be dissipated in the output transistors was pretty limited, and some form of temperature compensation, usually a thermistor, would need to be included in the circuit to avoid the possibility of 'thermal run-away' in the output transistors at high room temperatures, or if the amplifier got a bit over warm in use.

Clearly, this did not yet amount to a system which could be sold as a reliable design to the hi-fi buying public, although Lin had proposed an output emitter-follower circuit arrangement, based on the use of one PNP/PNP and one NPN/PNP output emitter follower layout, which would get around the difficulty that fully symmetrical (PNP/NPN) power transistor types were not yet commercially available. (This layout is shown, in its +ve rail version, in

# The Evolution of Audio Amplifier Design

Part 3

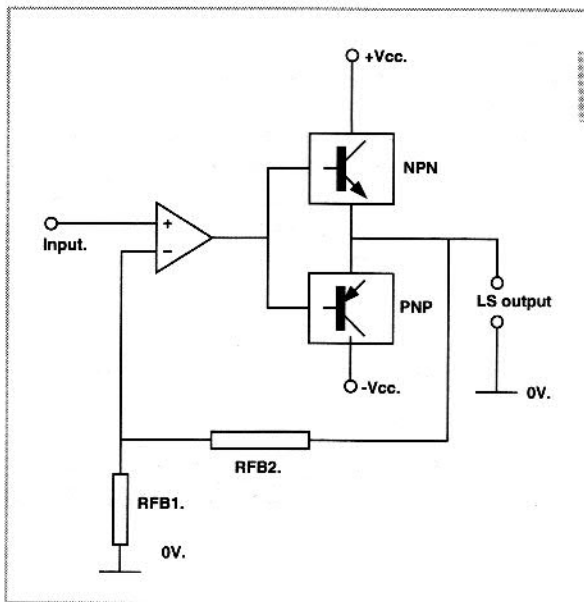


Fig.1 Lin circuit schematic


Figure 2, and became known as the 'quasi-complementary' configuration.)

When, in the early to mid 1960s, good quality silicon power transistors became available, made by versions of the 'planar' process, audio design engineers began to put together power amplifiers, using high gain silicon planar transistors, with typical designs of the kind shown in Figure 3, based on the use of Lin-type 'quasi-complementary' output pairs, which appeared to meet the technical requirements for a marketable piece of audio hardware.

With designs of this type, 30 watt power amplifiers, with output harmonic

distortion levels of less than 0.1% at full power, and bandwidths of 10Hz - 100KHz or greater, were easily obtainable, and their triumphant designers - and their employers advertising agencies - proudly, but prematurely, proclaimed the arrival of true transistor operated hi-fi.

The truth was, sadly, that these amplifiers really sounded quite nasty, in spite of their superb claimed specifications. This led to a regrettable loss of confidence, by a sizeable proportion of the buying market, in the engineers and all their doings.

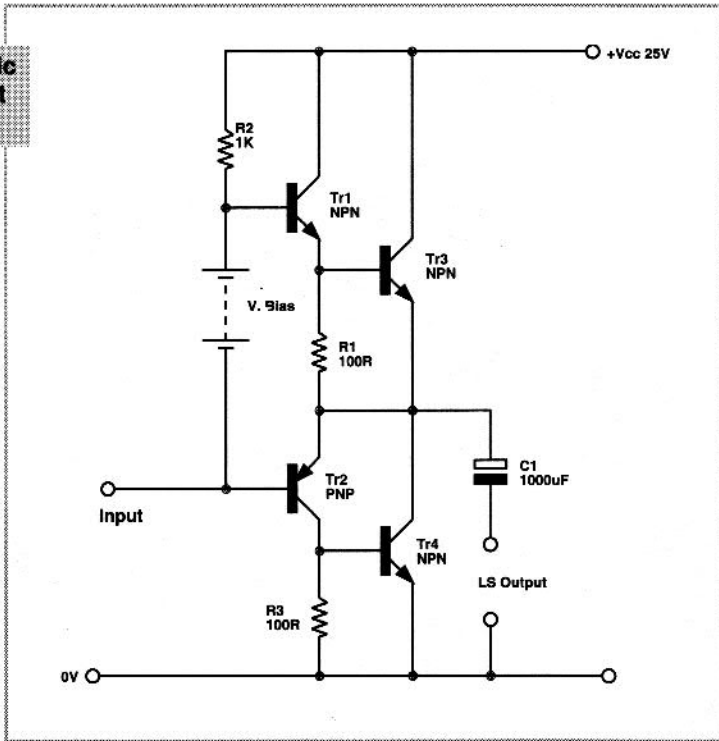**Fig.2 Basic  
Lin output  
circuit**

### 'Listener fatigue' and 'transistor sound'

Criticism of the sound quality of transistor amplifier designs started to appear, diffidently at first, but then more vociferously, and terms like 'transistor sound' and 'listener fatigue', were coined to describe the users objections. There were, in reality, quite a lot of problems with these new amplifier designs, and the process of remedying them took at least a decade, and some

might say that the process is not yet finished. I have listed the more conspicuous of these 'nasties', below, under their various headings.

#### 1 'Crossover distortion'


In any push-pull output system, of the kind shown in Figure 1, there is always the possibility of distortion in the region of the input/output transfer characteristic, where one half of the output push-pull pair hands over to the other. The only

certain way of avoiding this is to ensure that both halves of the output pair are working in a straight line part of their characteristics, at a current level which is adequate for them to handle the demands of the signal voltage swing.


This situation would always be the case for the push-pull output stages of valve amplifiers, but would never (or almost never) be true for transistor output systems. In fact, in many cases, the designers deliberately sought to avoid the problems of keeping the bias of the output transistors at the correct level, by setting it to zero, and then relying on the use of massive amounts of negative feedback (NFB) to try to straighten out the residual kinks in the curve... an attempt which was doomed to failure.

This difficulty in push-pull output stages is made much worse by the nature of the 'quasi-complementary symmetry' type of layout shown in Figure 3, in that the transfer slopes of the two halves - the NPN/NPN half and the PNP/NPN half - are very different, as shown in Figure 4a, so even if the output devices are biased so that the two curves join, there will always be a conspicuous kink in overall output curve, as shown in Figure 4b.

This results in the amplifier distortion getting worse as the output power is reduced, so even if the total harmonic distortion (THD) is as low as, say, 0.05% at full output, it may well be 5-10% or more at typical quiet listening

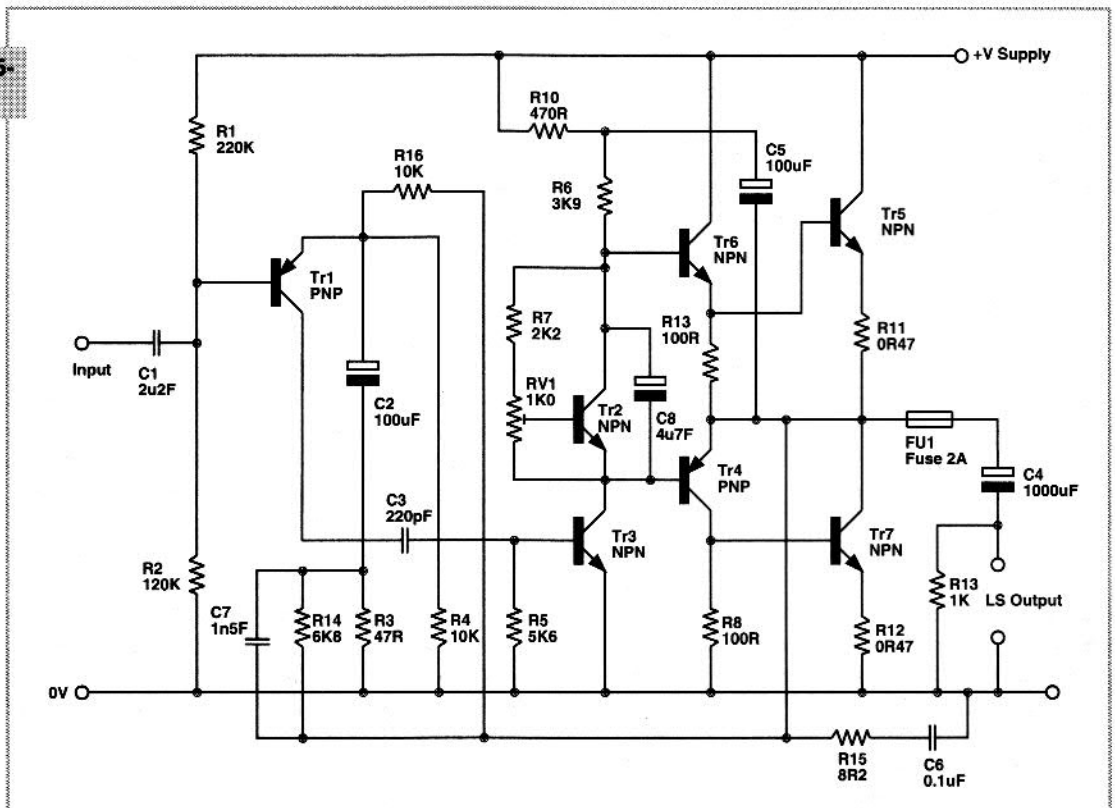**Fig.3 Typical 1965-  
70 audio amp**

**Fig.4 Quasi complementary pair characteristics**

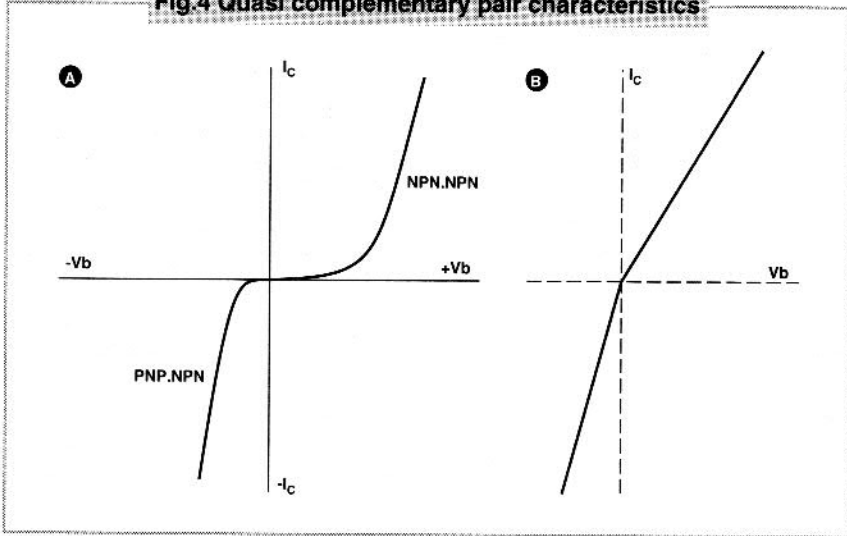

**2 'Transient intermodulation distortion'**

In order to improve the performance of these new 'transformerless' transistor amplifiers, the designers used lots of overall NFB. Much more in fact, than would have been possible with their valve based predecessors, and this had the predictable effect that, left to itself, the whole circuit would oscillate at some high frequency, and measures were therefore needed to prevent this.

The almost invariable method for stabilising such a feedback amplifier, used at that time and since (!), is what is known as 'dominant lag' stabilisation, in which a capacitor, (C3), is typically connected between the collector and the base of the second stage amplifier transistor, (Tr3), as shown in Figure 3. If a sudden voltage transient appears at the input of the amplifier, as part of the input signal, the effect of the negative feedback loop applied to Tr2 base will be to cause Tr1 to be driven into cut-off until C3 is able to charge or discharge to its proper equilibrium level.


The transient paralysis of amplifiers using this type of feedback loop stabilisation was first publicised by Professor Otala, who called it 'Transient Intermodulation Distortion', or 'TID'. It can be avoided by the use of a different type of loop stabilisation, and minimised by an input C-R HF roll-off circuit in those instances where the designers either know or care enough to try to do something about it.

**3 Poor stability margins**

A further problem with the use of a lot of overall NFB is that it reduces what is known as the amplifier's 'stability margin', and this can cause the amplifier to suffer sudden bursts of oscillation - usually in the MHz region - at parts of the signal output voltage swing, particularly when the loudspeaker has an awkward load characteristic. Usually, amplifiers with good stability margins sound more 'restful' to listen to than those where NFB has been used to excess, and the resulting loop stability margin is inadequate.

It is usually possible to do a quick check on freedom from this type of fault, if one has access to a signal generator and an oscilloscope, by driving the amplifier into clipping, while it is operating into various


**Fig.5 Comparative distortion characteristics of early transistor amp vs. valve amplifier**

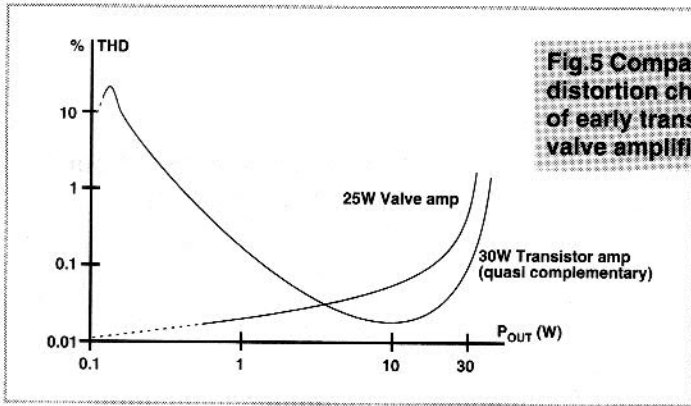

levels and what is worse, this distortion would be of the sonically unpleasant high-order odd-harmonic type. I have shown this effect in Figure 5, where I have contrasted the output power vs.

THD of a typical 1960s transistor audio amplifier with that of a typical 1950s valve amplifier. No wonder the valve amplifier sounded better, but that wasn't the only reason.

**Fig.6 The JLH 10watt class A**

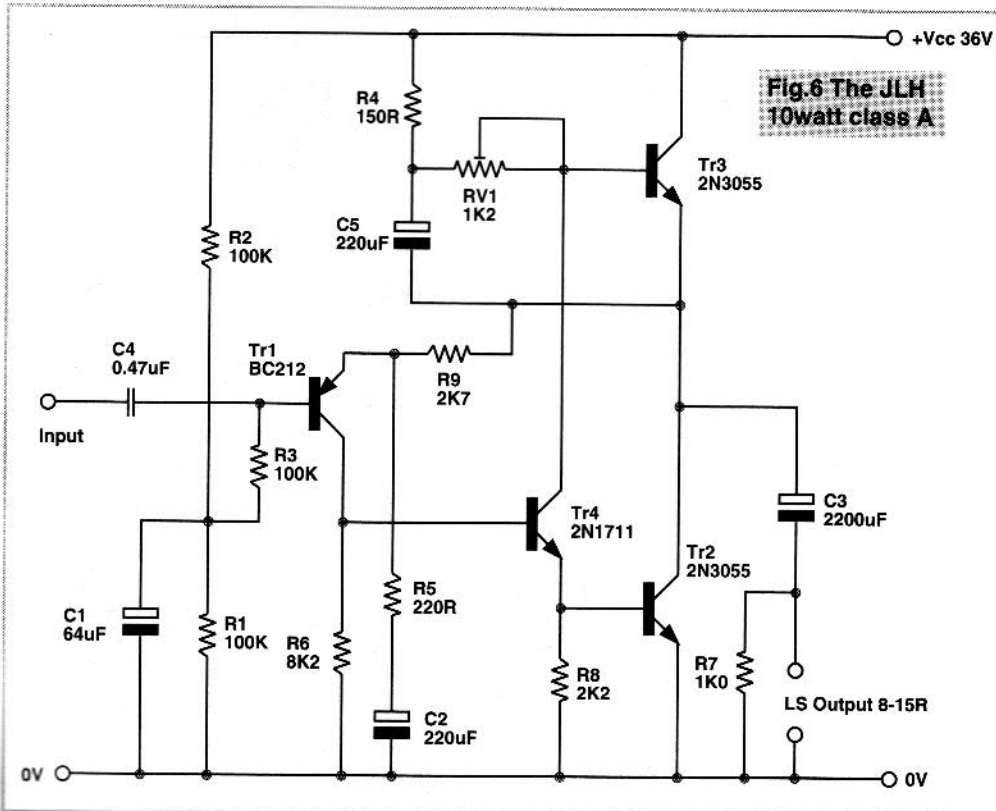

types of dummy load. Usually a resistor of the 4-8 ohm range in parallel with a range of capacitors in the range 0.01 $\mu$ F - 2 $\mu$ F, will serve as a load. While one is doing this, one can also check for 'hang-up' following clipping - which usually indicates transient output transistor malfunction. All of these faults spoil the sound quality of the system, without necessarily being shown up in the THD figures.

### Class 'A' operation.

Until the mid-1960s my domestic audio system consisted of a 'Williamson' power amplifier, driven by various transistor operated pre amplifier stages; the result of a recent JLH 'anti-hum' modernisation programme. This part of my system updating had been trouble free to put together, since it is easy to design small-signal amplifier stages without running into the raft of problems which beset the design of solid state power amps. However, this was still a 'mono' setup, and I wanted to take advantage of the new 'stereo' LP records which were replacing the older 'mono' discs. I also wanted, if possible, to avoid the need to build another large and expensive 'Williamson' power amp.

Since I had at home an adequately equipped electronics workshop, which I had set up in an upstairs box room, I put together four or five transistor operated


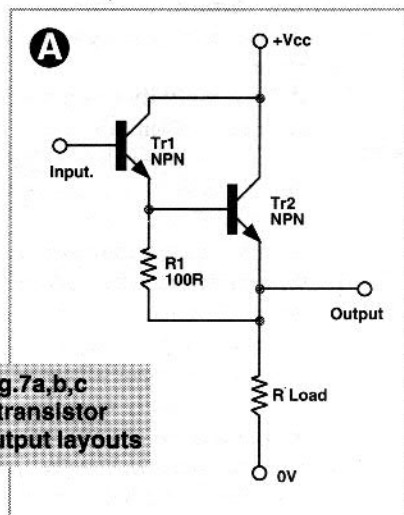


Fig. 7a, b, c  
2 transistor  
output layouts

audio power amplifiers; built to various published circuits, for which high performance was claimed; and I sat down to do a thorough listening trial comparing the performance of these with the Williamson. Well, that was my original intention. In reality, it took only a few seconds listening to each to conclude that none of these designs was in the same league in terms of sound quality, as my old valve amplifier. Since I had spent some time in constructing

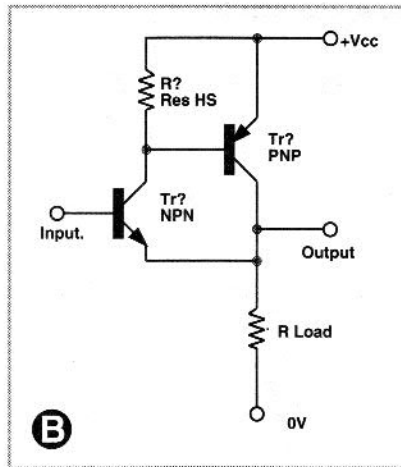

these comparative transistor operated designs I felt exceedingly let-down by this whole exercise, and was at a loss to know what next to try.

However, some months previously, I had built a transistor operated class 'A' power amplifier, mainly as a technical exercise to see how simple such a circuit could be. This was very much a pin-board hook-up, but it worked and would deliver some 10 watts into a 15 ohm load. So, having been disappointed with the performance of the other transistor power amplifiers I had tried, I went to my junk box, retrieved my hook-up class 'A' circuit, and tried this out as well.

To my astonishment and pleasure, this sounded as good as the Williamson - perhaps, I thought, it was even just a little bit more transparent - and provided a simple answer to my wish to go stereo, since the circuit, which I have shown in Figure 6, was a very easy one to make. I therefore spent the next month or so in constructing a complete stereo system, with a tidy two-channel class 'A' power amplifier to fit in place of the 'Williamson'.

### The 10W class 'A' amp.

The basic advantage of this circuit design was that it was not a push-pull system, in the normal sense of the term. It could be thought of either as Tr3 acting as an output emitter follower, with Tr4 acting as an 'active' emitter load, or with Tr4 acting as an amplifier, using Tr3 as an 'active' collector load. Since it wasn't a push-pull system it couldn't suffer from crossover distortion, and since both output transistors (which were, conveniently, identical NPN types) were operating in a linear part of their characteristics, it didn't need much overall NFB to reduce the distortion to my target value of 0.05%, so it didn't need any TID introducing stabilisation networks.


I was lucky to have avoided by

accident, the various problems that I didn't even know existed at that time, and after a couple of years of use, offered the circuit design to one of our more prestigious technical journals, where it was published. As a design, it worked well, and didn't need adjustments after initial setting up, but I was a bit unhappy about the need to pre-set the operating currents of the output transistors, and, since it wasn't a push-pull system, it was wasteful of current, and ran fairly hot.

One of my fellow designers, at the time, reproached me, in print, for 'sweeping the design problems of class 'B' (low quiescent current) amplifiers under the carpet, rather than attempting to solve them'. This was perfectly true, but the required solutions for push-pull operation were quite some time in coming, and even then were not complete.
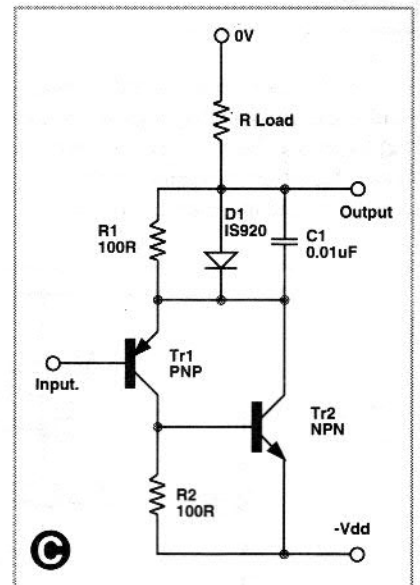
### Improved low quiescent current push-pull amplifier designs.

It is taken for granted these days, unless you happen to be a 'hot glass' buff, that the domestic hi-fi set up will run cool,



so that it can sit unobtrusively, in a shelf on ones equipment rack. The basis for this expectation was the increasing availability during the 1970s, of better power transistors, and the use of improved output transistor circuit layouts, using either PNP-PNP/NPN-NPN complementary arrangements, as shown in Figure 7a and 7b, or improved 'quasi-complementary' circuits of the kind shown in Figure 7c, which I used in a popular DIY 75 watt amplifier. A version of this output layout was also used commercially, at a later date, in a



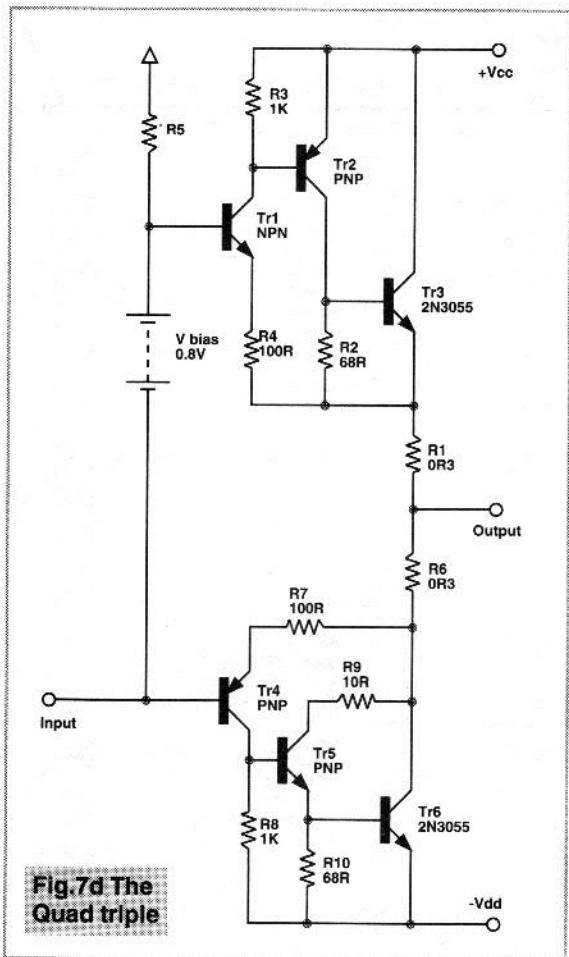


Fig.7d The Quad triple


very successful 'audiophile' power amplifier design.

'Quad' used an alternative three transistor output stage layout in their 'Quad 303' power amplifier, shown in Figure 7d, a power amplifier which has proved very successful in commercial practice, though modern practice mostly favours one or other of the fully complementary circuit layouts shown in Figure 7a or 7b.

In general, the majority of the better commercial solid-state hi-fi systems now are quite satisfactory in terms of listening quality, but there were still a few snags which needed ironing out, and, since 'specmanship' is now the name of the hi-fi advertisers game, much design effort has been expended on getting more '0's behind the decimal point in the THD specification. EIA

**NEXT MONTH**  
**John Linsley-Hood probes into:**  
***The so-called 'better' specifications***

# PHOTOCOPY SERVICE

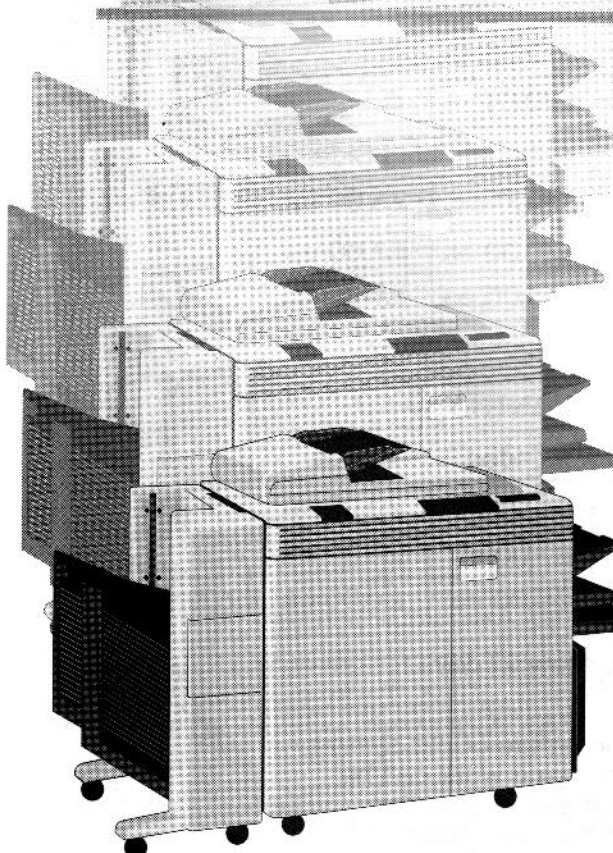

As our January issue was so popular and is now sold out, we have introduced a new service to enable you to obtain any articles that you may be missing. Each article copy costs £2.00 (including P&P).

**PHOTOCOPIES**

Please Photocopy me the following articles:

Month	Title of article	
.....	.....	@ £2.00
.....	.....	@ £2.00
.....	.....	@ £2.00
.....	.....	@ £2.00

Please print your name and address in **BLOCK CAPITALS**

Name .....

Address .....

..... Postcode .....

I enclose a cheque/postal order (payable to Electronics in Action) for £.....

Please send this form to: **Electronics in Action, PO Box 600, Berkhamsted, Herts. HP4 1NL**

**WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY**

TEKTRONIX 7000 SERIES OSCILLOSCOPES AVAILABLE FROM £200 PLUG-INS SOLD SEPARATELY

TEKTRONIX 2235B Dual trace 100MHz Delay Sweep	£800
PHILIPS 3065 2-1 channels 100MHz Dual TB Delay Sweep	£700
TEKTRONIX 475 Dual trace 200MHz Delay Sweep	£550
TEKTRONIX 465B Dual trace 100MHz Delay Sweep	£550
TEKTRONIX 465 Dual trace 100MHz Delay Sweep	£450
TEKTRONIX 2215 Dual Trace 60MHz Delay Sweep	£450
TEKTRONIX 455 Dual Trace 50MHz Delay Sweep	£400
HITACHI V550F Dual Trace 60MHz Delay Sweep	£375
HAMEG 605 Dual Trace 60MHz Delay Sweep	£400
PHILIPS PM3217 Dual Trace 50MHz Delay Sweep	£400
WATSUJ 555702 Dual Trace 20MHz	£225
GOULD OS300 Dual Trace 20MHz	£200
GOULD OS250B Dual Trace 15MHz	£125
HITACHI V209 Dual Trace 20MHz Mains Battery	£400
TELEQUIPMENT D32 Dual Trace 10MHz Mains Battery	£200
TEKTRONIX 2400 Dual Trace 150MHz Digital Storage	£2000
TEKTRONIX 466 Dual trace 100MHz Delay sweep Storage	£450
HP 1741A Dual Trace 100MHz Delay Sweep Analog storage	£450

THIS IS JUST A SAMPLE, MANY OTHERS AVAILABLE

PHILIPS PM 5139 Programmable synthesizer/Function Generator 0.1MHz-50MHz IEEE-488 as new	£1500
MARCONI 2019 Synthesized AM/FM Sig Gen 80KHz-1040MHz	£2000
RACAL 9081 Synthesized Sig Gen 1.5-620MHz	£800
EIP/DANA 3510 Microwave Frequency counter 20Hz-18GHz	£950
RACAL 9921 Frequency Counter 3GHz	£300
RACAL/DANA 1991 Nanosecond Universal counter	£800
RACAL 9302 Millivoltmeter True RMS 10KHz-1.5GHz	£450
RACAL 9301A RF Millivoltmeter True RMS 10KHz-1.5GHz	£300
RACAL 9009 Auto Mod. Meter 10MHz-1.5GHz Wide deviation	£250
LYONS PG73N Pulse Gen. PRF 1Hz-20MHz	£150
GOULD Birmalox K5000 Logic Analyser	£500
FARNELL P5G520H Synthesized Sig Gen AM/FM 100KHz-520MHz	£800
PHILIPS FM6309 Distortion Meter 0.01%	£300

BRUEL & KJOER Vibration Exciter System Consisting of Exciter Control 1047; Power amp 2708 in exciter body 4802 (up to 1750W - 4001st) Other B & K equipment available

**SPECTRUM ANALYSERS**

HP 141T with 855A & IF Plug-In 10MHz-18GHz	£2000
HP 141T with 854B & 8552B 500KHz-1250MHz	£1900
HP 140T with 8554L & 8552A 500KHz-1250MHz	£1000
HP 141T with 8556A & 8552B 20Hz-300KHz	£1000
HP 140T with 8553L & 8552A 1KHz-110MHz	£1000
MARCONI TF2370 30Hz-110MHz	£1500
HP 1820 with 8558B 100KHz-1500MHz	£2000
HP 3562A 0.02Hz-25.5KHz	£2000

**Used Equipment - GUARANTEED. Manuals supplied if possible**

This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £16. VAT to be added to total of Goods and Carriage

**STEWART OF READING**  
110 WYKEHAM ROAD, READING, BERKS RG6 1PL  
TELEPHONE (0734)268041 Fax: (0734)351696  
Callers Welcome 9am-5.30pm Monday to Friday (until 8pm Thursday)

DATRON 1061A - 6 1/2 digit true RMS AC/Current	£1250
DATRON 1066 Multimeter 5 1/2 digit AC/DC Ohms IEEE	£600
HEWLETT PACKARD 3480A Bench Multimeter 5 1/2 digit AC/DC Ohms	£200
PHILIPS PM2534 Multifunction DMM 5 1/2 digit 3 1/2 digit IEEE	£450
MARCONI Digital Frequency Meter 2430A 10Hz-60MHz	£125
MARCONI Digital Frequency Meter 2431A 10Hz-200MHz	£150
MARCONI Universal Counter Timer 2432 DC - 200MHz	£175
MARCONI Universal Counter Timer 2438 DC - 500MHz	£225
HP 3311A Function Generator 0.1Hz - 1MHz Sine/Square/Triangle	£125
BLACK STAR Juptor 500 Sine/Sq/Tri 0.1Hz - 500KHz	£70
FEEDBACK FG600 Sine/Sq/Tri 0.1Hz - 100KHz	£60
MULTIMETERS Hand-Held M2355-32 ranges AC DC 10A Diode Transistor Tester, Freq counter	£32.50

ISOLATORS/SCHLUMBERGER 1250 Frequency response analyser	£3500
HP 8690 Sweep Osc with 86974 Plug-in 26.5-40GHz	£300
RACAL/DANA RF Power Meter 9104	£400
RACAL/DANA 9341 Databridge. Automatic LCR & Q	£350
WAYNE KERR 8905 Automatic Precision bridge 0.05%	£900
WAYNE KERR 8905 Automatic Component bridge 0.1%	£350
WAYNE KERR 8424 Digital Component Meter L.C.R.	£125
FARNELL PSU TV570MK2 70V 5A/30V10A	£300
FARNELL PSU HQ425 0-50V 0-5A Metered	£400
FARNELL 83020 0-30V 20A	£250
FARNELL 83010 0-30V 10A	£200
HP 8208B 0-320V DC 1A Metered	£125
BRANDENBURG 472R PSU +/- 2KV	£200
MARCONI TF2700 Universal LCR Bridge. Battery from	£150
AVO Characteristic Meter VCM163	£300
FARNELL LAS20 RF Power Amp. 1.5-520MHz 300mW	£175
RACAL 9100 Absorption Wattmeter 1MHz-1GHz SW	£100

FARNELL Isolating Transformers GU500, 240V 500VA, unused...£50

**NEW EQUIPMENT**

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase	£547
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay sweep	£553
HAMEG OSCILLOSCOPE HM203.7 Dual Trace 20MHz Component Tester	£563
HAMEG OSCILLOSCOPE HM203.8 Dual Trace 20MHz Digital Storage	£563

At other models available - all oscilloscopes supplied with two probes

BLACK STAR EQUIPMENT (PAP all units £5)

APOLLO 10 - 100MHz Counter timer Ratio/Period/Time interval etc	£222
APOLLO 100 - 100MHz (As above with more functions)	£325
METOR 100 FREQUENCY COUNTER 100MHz	£119
METOR 800 FREQUENCY COUNTER 600MHz	£145
METOR 1000 FREQUENCY COUNTER 1GHz	£189
JUPITOR 500 FUNCTION GEN 0.1Hz - 500KHz Sine/Square/Tri	£119
ORION COLOUR BAR GENERATOR PartV/Video	£229

At other Black Star Equipment Available

OSCILLOSCOPE PROBES Switchable x1 x10(PAP £3)	£12
---	-----



**Chelmer Valve Company for High Grade Audio Valves**

Major Brands e.g Mullard, Brimar, Philips, GE (UK), GE(USA), etc.

A2900 GEC	£12.00	GZ34 Mullard	£10.00
E80F Philips	£10.00	GZ37 Mullard	£7.00
ECC81/CV4024 Mullard	£6.00	6CA7/EL34 GE	£9.50
ECC82/CV4003 Mullard	£6.00	6L6GA Sylvania	£7.00
ECC88 Mullard	£6.00	6SN7GT Brimar	£4.50
E88CC Mullard	£8.50	6V6GT Brimar	£4.00
EF86/CV4085 Mullard/GEC	£8.50	12AT7WC Sylvania	£6.00
EL84 Mullard	£6.00	6146B GE	£15.00
EL84 GE (USA)	£5.00	6550A GE	£17.50
GZ32 Mullard	£8.00	7581 GE	£12.00
GZ33 Mullard	£8.00		

**CVC PREMIUM:** Our own BRAND from selected worldwide sources, processed in our special facility to provide low noise/hum/microphony Pre-Amp valves and Power Valves burnt-in for improved stability and reliability.

**PRE-AMP VALVES**

ECC81/12A17	£5.00
ECC82/12A17	£4.00
ECC83/12AX7	£5.00
ECC85	£4.00
ECC88	£5.00
EF86	£4.00
E81CC (GOLD PIN)	£6.00
E82CC (GOLD PIN)	£6.00
E83CC (GOLD PIN)	£6.00
E88CC (GOLD PIN)	£7.00
E80F	£9.00
E83E	£5.50
6SL7GT	£4.00
6SN7GT	£4.20

**POWER VALVES - contd.**

E84L/7189A	£15.00
KT66	£9.20
KT88	£12.50
KT88 (GOLD Q)	£18.50
6L6GC	£6.50
6L6WGC/5881	£8.00
6V6GT	£5.00
6146B	£10.20
6336A	£40.00
6550A	£11.00

**RECTIFIERS**

GZ33	£4.50
GZ34/5AR4	£5.00
5U4G	£5.00

**POWER VALVES**

2A3 (OCTAL) or (4pin)	£14.00
211	£22.00
300B	£9.50
811A	£9.50
845	£29.90
EL34/6CA7	£7.50
EL84/6BQ5	£4.00

**SOCKETS**

5Y3GT	£3.20
5Z4GT	£3.50
B9A (PCB)	£1.60
B9A (CHASSIS)	£1.60
OCTAL (CHASSIS)	£1.75
4PIN (UX4)	£3.00
4PIN (for 211 & 845)	£11.00

Add £1.00 per valve for matching if required. Plus Post & Packing £3.00 + VAT at 17.5% for UK/Europe.

Send Fax order with cheque or credit card details to: Chelmer Valve Co., 130 New London Rd, Chelmsford, Essex CM2 0RG Tel: (0245) 265865 Fax: (0245) 490064

**Printed Circuit Boards**

**HIGH QUALITY PRINTED CIRCUIT BOARDS BY MAIL ORDER!**

Our unique Mail Order system allows us to provide you with High Quality Circuit Boards made to BS Spec. at a fraction of the cost available commercially. Simply send your order stating the type and quantity required, along with either Artwork or Gerber Cad Data.

Spec: 16mm fibreglass, 1 oz Copper, Non plated holes, Roller-Tinned finish.

REMEMBER TO ADD:

PHOTOPLOTTING	£10.00
POST & PACKING	£5.00

Send a Cheque or Postal Order along with your order to :

**MAIL ORDER CIRCUITS,**  
Meridian Centre, King Street,  
Oldham, OL8 1EZ

QUANTITY 1-8		
Sq In	2 Sides	1 Side
0-20	£8.00 ea	£5.00 ea
21-40	£10.00 ea	£7.00 ea
40-90	£15.00 ea	£11.00 ea

QUANTITY 9-20		
Sq In	2 Sides	1 Side
0-20	£5.00 ea	£3.00 ea
21-40	£7.00 ea	£4.00 ea
40-90	£9.00 ea	£6.00 ea

Please allow 21 days for delivery.

Due to the nature of our system, only Prototyping work can be carried out. For information on other commercial orders, please phone AO Electronics on 0203 612341

**MAIL ORDER**

**VIEWDATA RETURNS** £6 made by Tandata, includes 1200.75 modem, k/bd, RGB and comp o/p, printer port. No PSU. £6 MAG6P7

**IBM PC CASE AND PSU** Ideal base for building your own PC. Ex equipment but OK. £14.00 each REF: MAG14P2

**SOLAR POWER LAB SPECIAL** You get TWO 6"x6" 6v 130mA solar cells, 4 LED's, wire, buzzer, switch plus 1 relay or motor. Superb value kit just £5.99 REF: MAG6P8

**SOLID STATE RELAYS** Will switch 25A mains. Input 3.5-26v DC 57x43x21mm with terminal screws £3.99 REF: MAG4P10

**300DPI A4 DTP MONITOR** Brand new, TTL/ECL inputs, 15" landscape, 1200x1664 pixel complete with circuit diag to help you interface with your projects. JUST £24.99 REF: MAG25P1

**ULTRAMINI BUG MIC** 6mmx3.5mm made by AKG, .5-12v electret condenser. Cost £12 ea, Our? four for £9.99 REF: MAG10P2

**RGB/CGA/EGA/TTL COLOUR MONITORS** 12" in good condition. Back anodised metal case. £99 each REF: MAG99P1

**GX4000 GAMES MACHINES** returns so ok for spares or repair £9 each (no games). REF: MAG9P1

**C64 COMPUTERS** Returns, so ok for spares etc £9 ref: MAG9P2

**FUSELAGE LIGHTS** 3 foot by 4" panel 17" thick with 3 panels that glow green when a voltage is applied. Good for night lights, front panels, signs, disco etc. 50-100v per strip. £25 ref: MAG25P2

**ANSWER PHONES** Returns with 2 faults, we give you the bits for 1 fault, you have to find the other yourself. BT Response 200's £18 ea REF: MAG18P1, BT Response 400's £25 ea REF: MAG25P3 Suitable power supply £5 REF: MAG5P12

**SWITCHED MODE PSU** ex equip. 60w +5v @5A, -5v @.5A, +12v @2A, -12v @.5A 120/220v cased 245x88x55mm IEC input socket £6.99 REF: MAG7P1

**PLUG IN PSU 9V** 200mA DC £2.99 each REF: MAG3P9

**PLUG IN ACORN PSU** 19v AC 14w, £2.99 each REF: MAG3P10

**POWER SUPPLY** fully cased with mains and o/p leads 17v DC 900mA output. Bargain price £5.99 ref: MAG6P9

**ACORN ARCHMEDES PSU** +5v @ 4.4A. on/off sw uncased, selectable mains input. 145x100x45mm £7 REF: MAG7P2

**GEIGER COUNTER KIT** Low cost professional twin tube, complete with PCB and components. £29 REF: MAG29P1

**SINCLAIR C6 13"** wheels complete with tube, tyre and cycle style bearing £8 ea REF: MAG6P10

**AA NICAD PACK** encapsulated pack of 8 AA nicad batteries (tagged) ex equip. 55x32x32mm. £3 a pack. REF: MAG3P11

**13.8V 1.9A** psu cased with leads. Just £9.99 REF: MAG10P3

**360K 5.25"** brand new half height floppy drives IBM compatible industry standard. Just £6.99 REF: MAG7P3

**PPC MODEM CARDS.** These are high spec plug in cards made for the Amstrad laptop computers. 2400 baud dial up unit complete with leads. Clearance price is £5 REF: MAG5P1

**INFRA RED REMOTE CONTROLLERS** Originally made for hi spec satellite equipment but perfect for all sorts of remote control projects. Our clearance price is just £2 REF: MAG2

**TOWERS INTERNATIONAL TRANSISTOR GUIDE.** A very useful book for finding equivalent transistors, leadouts, specs etc. £20 REF: MAG20P1

**SINCLAIR C6 MOTORS** We have a few left without gearboxes. These are 12v DC 3,300 rpm 6"x4", 1/4" OP shaft. £25 REF: MAG25

**UNIVERSAL SPEED CONTROLLER KIT** Designed by us for the above motor but suitable for any 12v motor up to 30A. Complete with PCB etc. A heat sink may be required. £17.00 REF: MAG17

**VIDEO SENDER UNIT.** Transmits both audio and video signals from either a video camera, video recorder, TV or Computer etc to any standard TV set in a 100' range (tune TV to a spare channel) 12v DC op. Price is £15 REF: MAG15 12v psu is £5 extra REF: MAG5P2

**\*FM CORDLESS MICROPHONE** Small hand held unit with a 500' range! 2 transmit power levels. Reqs PP3 9v battery. Tuneable to any FM receiver. Price is £15 REF: MAG15P1

**LOW COST WALKIE TALKIES** Pair of battery operated units with a range of about 200'. Ideal for garden use or as an educational toy. Price is £8 a pair REF: MAG8P1 2 x PP3 req'd.

**\*MINIATURE RADIO TRANSCEIVERS** A pair of walkie talkies with a range of up to 2 kilometres in open country. Units measure 22x52x155mm. Complete with cases and earpieces. 2xPP3 req'd. £30.00 pair REF: MAG30.

**COMPOSITE VIDEO KIT.** Converts composite video into separate H sync, V sync, and video. 12v DC. £8.00 REF: MAG8P2.

**LQ3600 PRINTER ASSEMBLIES** Made by Amstrad they are entire mechanical printer assemblies including printhead, stepper motors etc etc In fact everything bar the case and electronics, a good stunner £5 REF: MAG5P3 or 2 for £8 REF: MAG8P3

**SPEAKER WIRE** Brown 2 core 100 foot hank £2 REF: MAG2P1

**LED PACK** of 100 standard red 5m leds £5 REF: MAG5P4

**JUG KETTLE ELEMENT** good general purpose heating element (about 2kw) ideal for heating projects. 2 for £3 REF: MAG3

**UNIVERSAL PC POWER SUPPLY** complete with flyleads, switch, fan etc. Two types available 150w at £15 REF: MAG15P2 (23x23x23mm) and 200w at £20 REF: MAG20P3 (23x23x23mm)

**\*FM TRANSMITTER** housed in a standard working 13A adapter!! the bug runs directly off the mains so lasts forever why pay £700? or price is £26 REF: MAG26 Transmits to any FM radio.

**\*FM BUG KIT** New design with PCB embedded coil for extra stability. Works to any FM radio. 9v battery req'd. £5 REF: MAG5P5

**\*FM BUG BUILT AND TESTED** superior design to kit. Supplied to detective agencies. 9v battery req'd. £14 REF: MAG14

**TALKING COINBOX STRIPPER** originally made to retail at £79 each, these units are designed to convert an ordinary phone into a payphone. The units have the locks missing and sometimes broken hinges. However they can be adapted for their original use or used for something else?? Price is just £3 REF: MAG3P1

**100 WATT MOSFET PAIR** Same specs as 2SK343 and 2SJ413 (8A, 140v, 100w) 1 N channel, 1 P channel, £3 a pair REF: MAG3P2

**VELCRO** 1 metre length of each side 20mm wide (quick way of fixing for temporary jobs etc) £2 REF: MAG2P3

**MAGNETIC AGITATORS** Consisting of a cased mains motor with lead. The motor has two magnets fixed to a rotor that spin round inside. There are also 2 plastic covered magnets supplied. Made for remotely stirring liquids! you may have a use? £3 each REF: MAG3P3

## BULL'S BULLETIN BOARD

**100MHZ DUAL TRACE OSCILLOSCOPES JUST £259 RING FOR DETAILS**

**MASSIVE WAREHOUSE CLEARANCE FANTASTIC £20.00 REDUCTION REFURBISHED PC BASE UNITS COMPLETE WITH KEYBOARD**

**FROM ONLY £29.00 AMSTRAD 1512 BASE UNITS GUARANTEED PERFECT WORKING ORDER.**

A LOW COST INTRODUCTION TO THE HOME COMPUTER MARKET.

**AMSTRAD 1512SD**  
1512 BASE UNIT, 5.25" FLOPPY DRIVE AND KEYBOARD. ALL YOU NEED IS A MONITOR AND POWER SUPPLY. WAS £49.00  
NOW ONLY £29.00  
REF: MAG29

**AMSTRAD 1512DD**  
1512 BASE UNIT AND KEYBOARD AND TWO 5.25" 360K DRIVES. ALL YOU NEED IS A MONITOR AND POWER SUPPLY WAS £59.00  
NOW ONLY £39.00  
REF: MAG39

## SOLAR POWER PANELS

**3FT X 1FT 10WATT GLASS PANELS 14.5v/700mA NOW AVAILABLE BY MAIL ORDER £33.95**

(PLUS £2.00 SPECIAL PACKAGING CHARGE)

TOP QUALITY AMORPHOUS SILICON CELLS HAVE ALMOST A TIMELESS LIFESPAN WITH AN INFINITE NUMBER OF POSSIBLE APPLICATIONS, SOME OF WHICH MAY BE CAR BATTERY CHARGING, FOR USE ON BOATS OR CARAVANS, OR ANYWHERE A PORTABLE 12V SUPPLY IS REQUIRED. REF: MAG34

## FREE SOFTWARE!

Brand new, UNUSED top quality Famous brand licensed software discs. Available in 5.25" DSD or 5.25" HD only. You buy the disk and it comes with free BRAND NEW UNUSED SOFTWARE. We are actually selling you the floppy disc for your own "MEGA CHEAP" storage facilities, if you happen to get software that you want/need/like etc well..... you get a "MEGA BARGAIN" too!  
DSD PKT10 £2.99 REF: MAG3P7 PKT100 £16.00 REF: MAG16

\*\*\*\*\*WE BUY SURPLUS STOCK\*\*\*\*\*  
TURN YOUR SURPLUS STOCK INTO CASH.  
IMMEDIATE SETTLEMENT. WE WILL ALSO QUOTE FOR COMPLETE FACTORY CLEARANCE.

## 1994 CATALOGUE.

PLEASE SEND 45P, A4 SIZED SAE FOR YOUR FREE COPY. MINIMUM GOODS ORDER £5.00 TRADE ORDERS FROM GOVERNMENT, SCHOOLS, UNIVERSITIES, & LOCAL AUTHORITIES WELCOME. ALL GOODS SUPPLIED SUBJECT TO OUR CONDITIONS OF SALE AND UNLESS OTHERWISE STATED GUARANTEED FOR 30 DAYS. RIGHTS RESERVED TO CHANGE PRICES & SPECIFICATIONS WITHOUT PRIOR NOTICE. ORDERS SUBJECT TO STOCK. QUOTATIONS WILL ONLY GIVEN FOR QUANTITIES HIGHER THAN THOSE STATED.

\*SOME OF OUR PRODUCTS MAY BE UNLICENSEABLE IN THE UK

**BULL ELECTRICAL**  
250 PORTLAND ROAD HOVE SUSSEX BN3 5QT

MAIL ORDER TERMS: CASH PO OR CHEQUE WITH ORDER PLUS £3.00 POST PLUS VAT.

PLEASE ALLOW 7 - 10 DAYS FOR DELIVERY

TELEPHONE ORDERS WELCOME

TEL: 0273 203500

FAX: 0273 323077



**TOP QUALITY SPEAKERS** Made for HI FI televisions these are 10 watt 4R Jap made 4" round with large shielded magnets. Good quality general purpose speaker. £2 each REF: MAG2P4 or 4 for £6 REF: MAG6P2

**TWEETERS** 2" diameter good quality tweeter 140R (ok with the above speaker) 2 for £2 REF: MAG2P5 or 4 for £3 REF: MAG3P4

**AT KEYBOARDS** Made by Apricot these quality keyboards need just a small modification to run on any AT, they work perfectly but you will have to put up with 1 or 2 foreign keycaps! Price £6 REF: MAG6P3

**XT KEYBOARDS** Mixed types, some returns, some good, some foreign etc but all good for spares! Price is £2 each REF: MAG2P6 or 4 for £6 REF: MAG6P4

**PC CASES** Again mixed types so you take a chance next one off the pile £12 REF: MAG12 or two the same for £20 REF: MAG20P4

**COMMODORE MICRODRIVE SYSTEM** mini storage device for C64's 4 times faster than disc drives, 10 times faster than tapes. Complete unit just £12 REF: MAG12P1

**SCHOOL STRIPPERS** We have quite a few of the above units which are 'returns' as they are quite comprehensive units they could be used for other projects etc. Let us know how many you need at just 50p a unit (minimum 10).

**HEADPHONES 16P** These are ex Virgin Atlantic. You can have 8 pairs for £2 REF: MAG2P8

**PROXIMITY SENSORS** These are small PCB's with what look like a source and sensor LED on one end and lots of components on the rest of the PCB. Complete with fly leads. Pack of 5 £3 REF: MAG: 3P5 or 20 for £8 REF: MAG8P4

**SNOOPERS EAR?** Original made to clip over the earpiece of telephone to amplify the sound-it also works quite well on the cable running along the wall! Price is £5 REF: MAG5P7

**DOS PACKS** Microsoft version 3.3 or higher complete with all manuals or price just £5 REF: MAG5P8 Worth it just for the very comprehensive manual! 5.25" only.

**DOS PACK** Microsoft version 5.0 original software but no manuals include only £3 REF: MAG3P6 5.25" only.

**FOREIGN DOS** 3, 3-German, French, Italian etc £2 a pack with manual. 5.25" only. REF: MAG2P9

**CTM644 COLOUR MONITOR.** Made to work with the CPC464 home computer. Standard RGB input so will work with other machines. Refurbished £59.00 REF: MAG59

**PIR DETECTOR** Made by famous UK alarm manufacturer these are hi spec, long range internal units. 12v operation. Slight marks on case and unboxed (although brand new) £8 REF: MAG8P5

**WINDOW SOLAR POWERED RADIO** AM/FM radio complete with hand charger and solar panel £14 REF: MAG14P1

**COMMODORE 64 TAPE DRIVES** Customer returns at £4 REF: MAG4P9 Fully tested and working units are £12 REF: MAG12P5

**COMPUTER TERMINALS** complete with screen, keyboard and RS232 input/output. Ex equipment. Price is £27 REF: MAG27

**MAINS CABLES** These are 2 core standard black 2 metre mains cables fitted with a 13A plug on one end, cable the other. Ideal for projects, low cost manufacturing etc. Pack of 10 for £3 REF: MAG3P8 Pack of 100 £20 REF: MAG20P5

**SURFACEMOUNT STRIPPER** Originally made as some form of high frequency amplifier (main chip is a TSA5511T 1.3GHz synthesiser) but good stripper value, an excellent way to play with surface mount components £1.00 REF: MAG1P1

**MICROWAVE TIMER** Electronic timer with relay output suitable to make enlarger timer etc £4 REF: MAG4P4

**MOBILE CAR PHONE £5.99** Well almost! complete in car phone excluding the box of electronics normally hidden under seat. Can be made to illuminate with 12v also has built in light sensor so display only illuminates when dark. Totally convincing! REF: MAG6P6

**ALARM BEACONS** Zenon strobe made to mount on an external bell box but could be used for caravans etc. 12v operation. Just connect up and it flashes regularly! £5 REF: MAG5P11

**FIRE ALARM CONTROL PANEL** High quality metal cased alarm panel 350x165x80mm. With key. Comes with electronics but no information. sale price 7.99 REF: MAG8P6

**SUPER SIZE HEATSINK** Superb quality aluminium heatsink. 365 x 183 x 61mm, 15 fins enable high heat dissipation. No holes! sale price £5.99 REF: MAG6P11

**REMOTE CONTROL PCB** These are receiver boards for garage door opening systems. You may have another use? £4 ea REF: MAG4P5

**6"X12" AMORPHOUS SOLAR PANEL** 12v 155x310mm 130mA. Bargain price just £5.99 ea REF: MAG6P12

**FIBRE OPTIC CABLE BUMPER PACK** 10 metres for £4.99 ref: MAG5P13 Ideal for experimenters! 30 m for £12.99 ref: MAG13P1

**LOPTX** Line output transformers believed to be for hi res colour monitors but useful for getting high voltages from low ones! £2 each REF: MAG2P12 bumper pack of 10 for £12 REF: MAG12P3.

**SHOP OPEN 9-5.30 SIX DAYS A WEEK**


## PORTABLE RADIATION DETECTOR

**£49.99**

A Hand held personal Gamma and X Ray detector. This unit contains two Geiger Tubes, has a 4 digit LCD display with a Piezo speaker, giving an audio visual indication. The unit detects high energy electromagnetic quanta with an energy from 30K eV to over 1.2M eV and a measuring range of 5-9999 UR/h or 10-99990 Nr/h. Supplied complete with handbook.

REF: MAG50

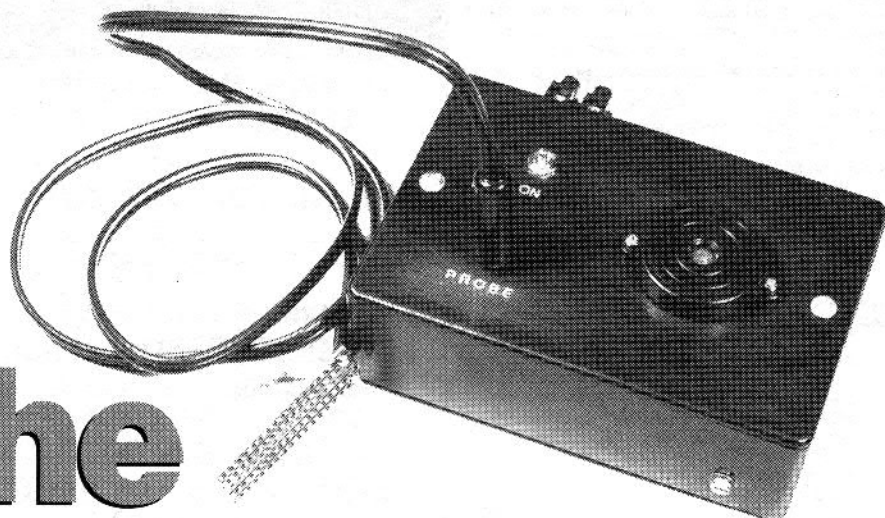A de-ionised water level detector by Edward Barrow



# At the waters edge

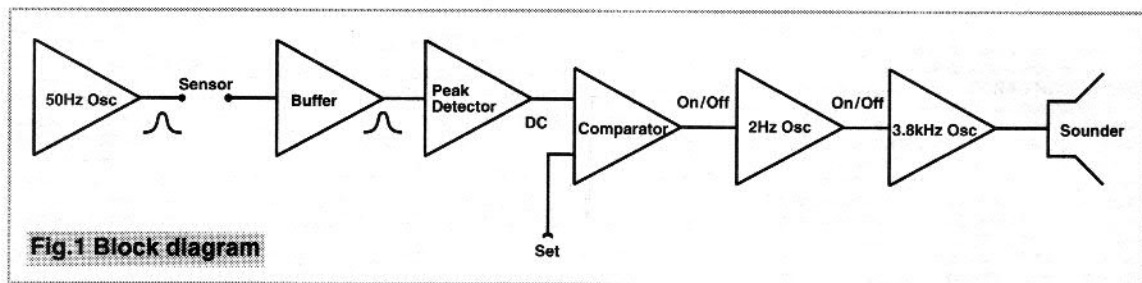


Fig.1 Block diagram

This project started its life over dinner with my potential father-in-law who is a chemist. Being an absent minded chemist in the classical vane he was having problems when his 'water de-ioniser' overflowed due to lack of attention. So he asked me if I could

To understand the working of this circuit it is best to glance at the block diagram in Figure 1. As this project was designed for use with de-ionised water certain problems had to be overcome, the main one being its high resistance. This arises because the process of de-ionising by its nature involves the removal of the very charged particles which are responsible for its conducting properties. A second problem is that the currents passing through the solution must not create new ions and thus re-ionise the water.

This latter problem can be remedied by using an AC current to sense as it produces no resulting current. The high resistance of the water is countered by using a high input impedance buffer on the returning signal. This minimises the current drawn by the sensor

in sensing. So some pull down impedance is needed. Another unexpected problem can be caused by pick up from across the two wires that are used to connect the circuit to the sensors. This I found out when I used screened wire for connecting the sensor to the board. Unfortunately this has a capacitance of about 320pF per meter and so relays the signal from output to input even when there is no liquid to act as a conductor. This is especially true for the edges of a nice clean square wave, as it contains higher harmonics. It does not need a fertile imagination to see that this will play havoc with any AC detection system further on. To counter these tendencies the sharp edges (the higher harmonics) are firstly removed by lowpass filtering. Also to calm down the input impedance with respect to AC some capacitance has been included, this helps mitigate the effects of stray capacitance and mains pick-up.

Detection of the AC signal is done by means of an active peak detection system. This is basically built around a diode which feeds a capacitor (memory). Here the diode only conducts when the input signal is higher than the previous one, so

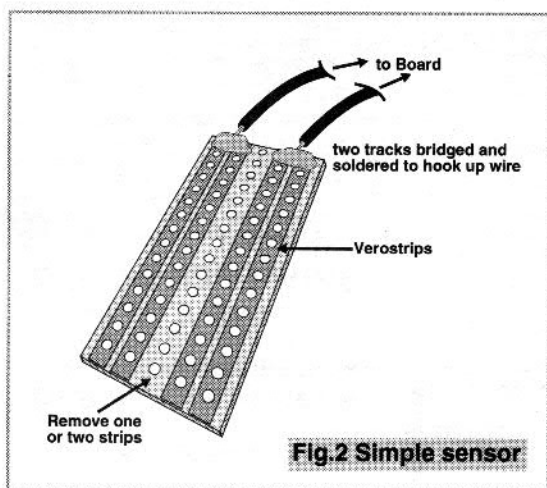


Fig.2 Simple sensor

come up with a potential solution to his problem, modern form of 'dowry' I suppose. This I felt obligated to do not for the sake of his daughter's hand but rather because he was footing the bill!

through the liquid. On the other hand however using AC as your medium does mean that the resulting detector is prone to mains 50Hz pick-up. This problem is made worse by the high impedance used


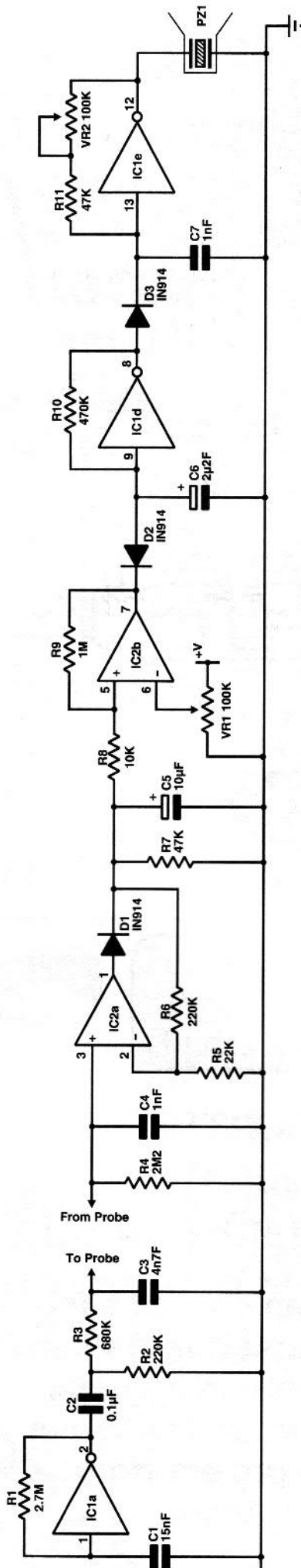


Fig.3 Main circuit

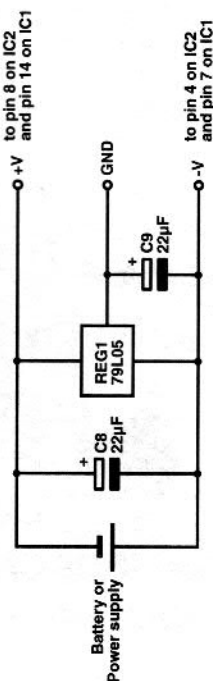

the highest one is retained by a capacitor which acts as a memory. If the input is less than the previous one then the diode does not conduct and the value across the capacitor remains the same. A resistor to ground is used to reset the capacitor. The prefix "active" only implies that an op-amp is used to cure the problems caused by the 0.7 volt diode drop.

A comparator is used to compare this DC output with that of a set voltage, and its output is used to trigger the sounding part of the circuit. So when the AC signal rises above a certain set level the alarm sounds.

The noise in this circuit is generated by using 2 oscillators feeding into each other. The first generates a 2Hz square wave and this is used to turn on and off a second oscillator which oscillates at 3800Hz. The latter feeds the piezo sounder.

### Construction

This circuit can be powered by a PP3 9V battery or an equivalent DC source. A 79L05 has been used to generate a

### The Works

The oscillators used to generate all signals in this circuit are of a simple relaxation type built around a Schmitt trigger inverter. Wired up in a feedback loop which is delayed by a simple RC network, an inverter becomes an oscillator. For example, say its output is high, after a fixed time, set by the RC time constant, the input goes high thus forcing the output low, the process is repeated on and on... Some hysteresis is needed, i.e. there must be some differential between the switching levels to allow a delay to be manufactured.

In this circuit output frequency is given by:

$$F_{out} = 4/RC$$

The first of these oscillators generates the reference signal of 60Hz. This is AC coupled and filtered at 60Hz by a simple RC filter to remove annoying higher components.

One of the TL082's op-amps are used to build a high input impedance active peak rectifier (its input resistance being 1 trillion ohms!). A gain of about 10 is given to restore what can be a weak signal. The "memory capacitor" is set with a time constant of about 5s, which means while it is set quickly, it only resets slowly, thus making its output appear as a clean DC source. The comparator has been wired up with some positive feedback to ensure clean switching about the level set by VR1.

Switching the oscillators on and off is done by using diodes to gate the inputs. So when the comparator is in the off state (i.e.; no alarm needed), the diode D2 is forward biased thus forcing the input of the inverter IC1d low. Now this means its output is now high, similarly the diode D3 is forward biased and so holds the input of inverter IC1e high, and so in turn its output low.

However when the comparator is triggered by some form of conduction, i.e. some alarm is needed, the diode D2 is now reverse biased and so does not conduct. Thus the oscillator (IC1d) is free to do what it does best and oscillate. This output alternately turns the diode D3 on and off and the oscillator (IC1e). Thus the audible tone turns on and off. The frequency of the tone is set in the 3800Hz range and can be adjusted by VR2. Note that piezo sounders do have an optimum frequency as they are really low frequency crystal oscillators. So VR2 allows either the loudest or the most annoying tone, or both, to be set.

ground line roughly at the midpoint. A negative regulator was used as it sinks current better than a positive one which is an important criterion for insuring stability. A piece of veroboard was used to make the sensor (see Figure.2). I removed the central track to make it more immune to dirt forming a bridge and the problem of surface tension causing a film of water to stick over the tracks even after the level of the water has receded. Some silicone repellent can also be smeared between the tracks as an added protection against this.

Separate the copper tracks where required firstly. Then solder in the link wires, diodes and resistors. After this the IC sockets, capacitors, presets and the regulator. Make sure the capacitor polarities are the right way round. Also be sure to tie the unused CMOS inputs to ground to prevent problems. ICs can then be plugged in and the circuit tested.

**Testing and Setting up**

The oscillators can be tested easily with a 'scope and the 2Hz one with a meter. To test the peak detector short out the sensor and observe its output which should go from low to high. By the way the alarm should also sound at the same time. If not check the polarity of the diodes are correct.

Only two presets need to be adjusted. The first VR1 adjusts the triggering level of the alarm so it is quite easy to set. Place the sensor in the liquid in question and set it so the alarm just sounds, then turn it a little further to be sure of consistent operation. Remove the sensor, dry if necessary, and the alarm should go off. The second preset has been explained before and adjusts the alarm frequency.

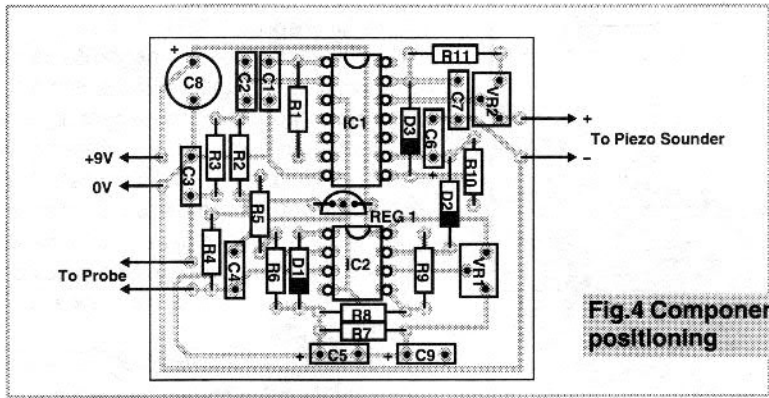


Fig.4 Component positioning

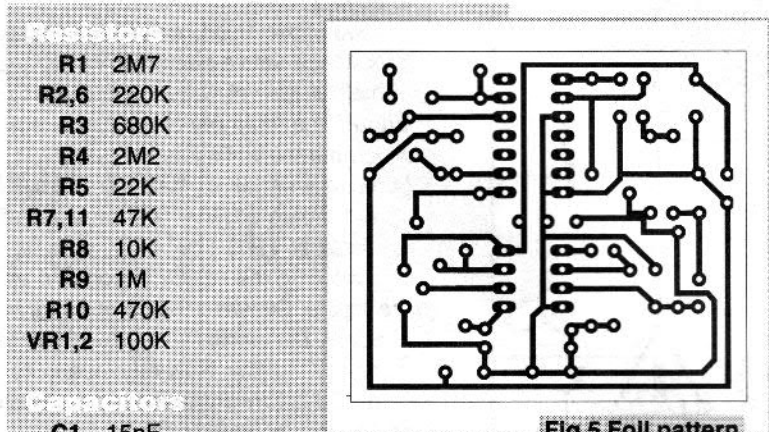


Fig.5 Foil pattern

- Resistors**  
 R1 2M7  
 R2,6 220K  
 R3 680K  
 R4 2M2  
 R5 22K  
 R7,11 47K  
 R8 10K  
 R9 1M  
 R10 470K  
 VR1,2 100K
- Capacitors**  
 C1 15nF  
 C2 100nF poly  
 C3 4n7F poly  
 C4,7 1nF poly  
 C5 10µF tant 16V  
 C6 2µ2F tant 16V  
 C8,9 22µF tant 16V

- Semiconductors**  
 IC1 40106 hex Schmitt trigger inverter  
 IC2 TL082 dual FET input op-amp  
 D1-3 1N914  
 REG1 79L05

- Additional Components**  
 PZ1 Piezo sounder  
 PCB (see page 57)  
 9V battery  
 case

**Parts**

**'WE'RE WORKING ON GOOD REVERBERATIONS'**

**NEXT MONTH**

Keep on repeating yourself with Paul Stenning's Digital Echo Unit. Another superb project from Electronics in Action

**ON SALE 21st APRIL**

# HARD DISC DRIVE PARAMETERS

This new volume covers a vast range of Hard Disc Drives, mainly IDE types, thus enabling you to easily set up the BIOS on your machine when you install a replacement drive. Listed by Make and Model, it gives the parameters for the Type, Capacity, Cylinders, Heads, Sectors per Track etc. If you need to know the parameters of a drive then this book is for you.



**Just £5.95 inclusive. Order Code MP-247.**

*The above is just one of hundreds of Technical and Repair books we publish. From Valve Data to Video Recorders with everything else in between. We also have what is probably the largest range of Service Manuals available anywhere, for practically any Make, Model, Type or Age of equipment.*



For your FREE catalogue detailing our full range of Technical Books and Repair Guides complete the coupon below.



**MAURITRON TECHNICAL SERVICES (EA247),**

47A High Street, Chinnor, Oxon, OX9 4DJ.

*Tel:- 0844-351694. Fax:- 0844 352554.*

Please forward your latest catalogue for which I enclose 2 x 1st Class Stamps.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

POSTCODE \_\_\_\_\_


**At last, a fully functional upgradeable PCB CAD system to suit any budget. Substantial trade-in discounts are available against other "professional" PCB design packages ...**

**... call now for details.**

## Board Capture
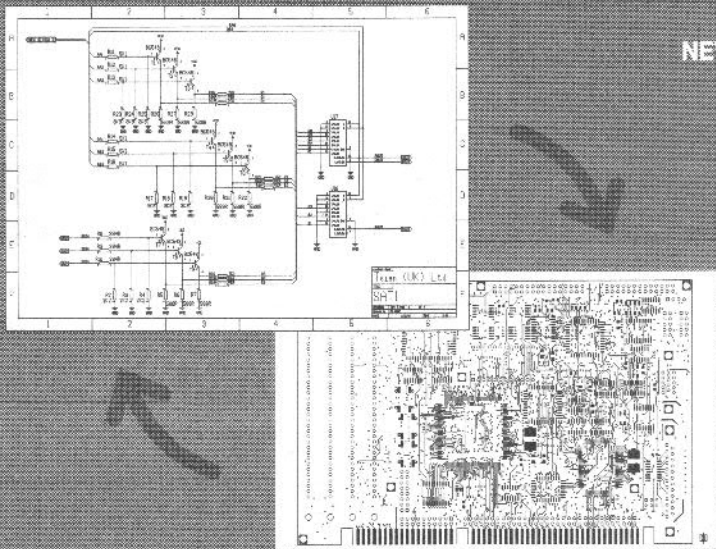
### Schematic Capture Design Tool

- Direct netlist link to BoardMaker2
- Forward annotation with part values
- Full undo/redo facility (50 operations)
- Single sheet, multi-paged and hierarchical designs
- Smooth scrolling
- Intelligent wires (automatic junctions)
- Dynamic connectivity information
- Automatic on-line annotation
- Integrated on-the-fly library editor
- Context sensitive editing
- Extensive component-based power control
- Back annotation from BoardMaker2



## Board Maker

### BoardMaker1 - Entry level

- PCB and schematic drafting
- Easy and intuitive to use
- Surface mount and metric support
- 90, 45 and curved track corners
- Ground plane fill
- Copper highlight and clearance checking

### BoardMaker2 - Advanced level

- All the features of BoardMaker1 +
- Full netlist support - BoardCapture, OrCad, Schema, Tango, CadStar and others
- Full Design Rule Checking both mechanical and electrical
- Top down modification from the schematic
- Component renumber with back annotation
- Report generator - Database ASCII, BOM
- Thermal power plane support with full DRG

NEW

## Board Router


### Gridless re-entrant autorouter

- Simultaneous multi-layer routing
- SMD and analogue support
- Full interrupt, resume, pan and zoom while routing
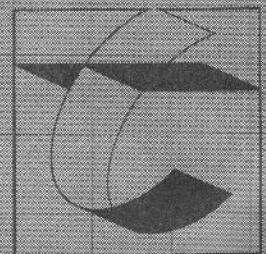
### Output drivers - Included as standard

- Printers - 9 & 24 pin Dot matrix, HPLaserjet and PostScript
- Penplotters - HP, Graphtec & Houston
- Photoplotters - All Gerber 3X00 and 4X00
- Excellon NC Drill and Annotated drill drawings (BM2)

Call, write or fax for more information  
or a full evaluation kit  
Tsien (UK) Limited  
Aylesby House  
Wenny Road, Chatteris  
Cambridge  
PE16 6UT  
Tel (0354) 695959  
Fax (0354) 695957



**tsien**



# EUROPEAN COMPUTER MARKETING (U.K.)

ROWAN HOUSE, WOODLANDS ROAD, RILLINGTON, MALTON, YO17 8LD, N YORKSHIRE

SALES AND INFORMATION HOTLINE

**0944 - 758989**

**FAX: 0944 - 758989**

All prices are exclusive of V.A.T @ 17.5% and UK mainland delivery. Export orders are welcome. Please call for carriage to country of destination. Payment by cheque, bankers draft, cash or postal orders.

Subject to availability despatch is normally effected within 2 days from receipt of cleared payment. Please allow 7 working days for cheque clearance. All orders will be fulfilled within 28 days unless otherwise notified.

E & O.E All prices subject to change without notice. Please call before ordering. Goods are not supplied on a trial basis.

## TOP QUALITY DEALS!!

		120MB HDD	170MD HDD	210MB HDD
386 SX-40MHZ	MONO VGA	:£620.00	:£635.00	:£650.00
	COLOUR SVGA	:£696.00	:£711.00	:£726.00
386DX-40MHZ	MONO VGA	:£635.00	:£650.00	:£665.00
	COLOUR SVGA	:£717.00	:£726.00	:£745.00
486SX-25MHZ	MONO VGA	:£695.00	:£710.00	:£725.00
	COLOUR SVGA	:£775.00	:£786.00	:£805.00
486DX-33MHZ	MONO VGA	:£832.00	:£847.00	:£862.00
	COLOUR SVGA	:£912.00	:£923.00	:£942.00
486DX-50MHZ	MONO VGA	:£934.00	:£949.00	:£964.00
	COLOUR SVGA	:£1014.00	:£1024.00	:£1044.00
486DLC-40MHZ	MONO VGA	:£734.00	:£749.99	:£764.00
	COLOUR SVGA	:£814.00	:£824.00	:£844.00



STANDARD FEATURES INCLUDE: MINI TOWER OR DESK TOP CASE WITH DIGITAL SPEED DISPLAY, 3.5" FLOPPY DRIVE (1.44MB), 5.25" (1.2MB) FLOPPY DISK DRIVE, 2 SERIAL/2 PARALLEL/1 GAMES PORT, 102 KEY UK KEYBOARD, MICROSOFT COMP MOUSE, \* 3 YEAR WARRANTY, M5 DOS 5, MS WINDOWS 3.1. ALL SYSTEMS ARE SOAK TESTED FOR 48 HRS.

### MOTHERBOARDS

ECM100 386SX-40MHZ	£62.00
ECM101 386DX40MHZ128K CACHE	£92.00
ECM102 486SX25MHZ VLB 256K CACHE	£147.00
ECM103 486SX33MHZ VLB 256K CACHE	£160.00
ECM104 486DX33MHZ VLB 256K CACHE	£278.00
ECM105 486DX40MHZ VLB 256K CACHE	£290.00
ECM106 486DX50MHZ VLB 256K CACHE	£379.00
ECM107 486DLC40MHZ VLB & CO-PRO	£162.00

### HARD DISK DRIVES

ECM108 120MB IDE CONNER	£153.00
ECM109 170MB IDE CONNER	£169.00
ECM110 210MB IDE CONNER	£173.00
ECM111 250MB IDE CONNER	£178.00
ECM112 330MB IDE CONNER	£210.00
ECM113 1GB FAST SCSI-2 FUJITSU	£640.00

### MEMORY

ECM114 256K SIMMS MODULE	£CALL
ECM115 1MB SIMMS MODULE 70NS	£CALL
ECM116 4MB SIMMS MODULE 80NS	£CALL

### LATEST DESIGN CASES

ECM117 DELUXE DESKTOP	£45.00
ECM118 DELUXE SLIMLINE CASE	£52.00
ECM119 DELUXE MINITOWER	£48.00
ECM120 DELUXE FULLTOWER	£80.00
ECM121 DELUXE MULTIMEDIA	£87.00

### KEYBOARDS

ECM122 102 KEY UK KEYBOARD	£14.00
ECM123 HIGH QUALITY (CORPORATE) KEYBOARD	£23.00
ECM124 CHERRY KEYBOARD	£26.00

### ADD-ON CARDS

ECM131 I/O CARD 2S/1P/1G	£11.00
ECM132 IDE CARD 2HD/2FD WITH CABLES	£11.00
ECM133 IDE & I/O CARD 2HD/2FD/2S/1P/1G WITH CABLES	£14.00
ECM134 IDE CACHE CONTROLLER 2HD/2FD	£62.00
ECM135 ADEPTIC 1542C SCSI HIGH PERFORMANCE KIT	£192.00

### COMMS PRODUCTS

ECM136 FAX/MODEM 9600/4800 WITH BITFAX FOR DOS	£49.00
ECM137 FAX/MODEM 9600/2400 WITH BITFAX FOR DOS/WINDOWS	£57.00
ECM138 POCKET FAX/MODEM 9600/2400	£57.00

### MONITORS

ECM154 MONO VGA 14" MONITOR	£85.00
ECM155 COLOUR SVGA 14" MONITOR	£169.00
ECM156 COLOUR SVGA 14" NON INTERLACED	£182.00
ECM157 COLOUR SVGA 15" NON INTERLACED	£CALL
ECM158 COLOUR SVGA 17" NON INTERLACED	£560.00

### SOFTWARE

ECM163 MS DOS V5.0	£25.00
ECM164 MS DOS V6.0	£37.00
ECM165 MS WINDOWS V3.1	£33.00
ECM175 MS DOS V3.3 (FOREIGN) GERMAN 5.25" ONLY	£22.00
ECM176 MS DOS V3.3 (FOREIGN) FRENCH 5.25" ONLY	£22.00
ECM177 MS DOS V3.3 (FOREIGN) ITALIAN 5.25" ONLY	£22.00

### CD TITLES

ECM150 WORLD ATLAS CD	£25.00
ECM151 GUINNESS DISC OF RECORDS 1993 CD	£25.00
ECM152 WORLD VIEW WITH VIDEO FOR WINDOWS	£25.00
ECM153 KODAK PHOTO CD ACCESS SOFTWARE	£20.00
ECM166 AA HOTELS & RESTAURANTS	£20.00
ECM167 SHAREWARE OVERLOAD	£15.00
ECM168 PUBLISHERS DREAMS	£35.00
ECM169 WIN PLATINUM	£25.00
ECM170 WORLD FACT BOOK '93	£25.00
ECM171 WINDOWS MASTER	£22.00
ECM172 BUSINESS MASTER 2ND EDITION	£22.00
ECM173 VIDEO MOVIE GUIDE '93	£35.00
ECM174 TOOLWORKS REFERENCE LIBRARY	£25.00

### DISPLAY CARDS

ECM139 MONO CARD WITH PRINTER PORT	£16.00
ECM140 VGA CARD 256K	£36.00
ECM141 16 BIT SVGA CARD 512K	£39.00
ECM142 TRIDENT 8900CL 16 BIT SVGA 1MB	£52.00
ECM143 TSENG LAB ET4000 1MB 16.7MB COLOURS	£64.00

### PRINTERS

ECM125 HP DESKJET 510	£239.00
ECM126 HP DESKJET 550	£419.00
ECM127 HP LASERJET 4L	£492.00
ECM128 PANASONIC KXP1123 24 PIN DOT MATRIX	£139.00
ECM129 CANON BJ10SX BUBBLE JET	£184.00
ECM130 PARALLEL PRINTER CABLE	£2.90

### MULTI MEDIA

ECM144 MITSUMI CD ROM & INTERFACE CARD	£125.00
ECM145 PANASONIC 582 DUAL SPEED CD ROM COMPLETE KIT	£159.00
ECM146 SOUNDBLASTER V2 COMPATIBLE WITH SPEAKERS	£45.00
ECM147 SOUNDBLASTER PRO WITH CD INTERFACE	£82.00
ECM148 AMPLIFIED POWER SPEAKERS	£24.00
ECM149 VIDEO CAPTURE CARD AND VIDEO FOR WINDOWS	£215.00
ECM178 MICROSOFT COMPATIBLE MOUSE	£14.00
ECM179 ANALOG JOYSTICK (REQUIRES GAMES PORT)	£22.00

### FLOPPY DRIVES

ECM160 3.5" 1.44MB FLOPPY DISK DRIVE	£32.00
ECM161 5.25" 1.2MB FLOPPY DISK DRIVE	£40.00
ECM162 FLOPPY DRIVE MOUNTING KIT	£7.00

### TELECOM PRODUCTS

UNFORTUNATELY WE ARE UNABLE TO LIST OUR FULL LINE OF TELECOM PRODUCTS AS IT IS SO LARGE. BELOW IS A LISTING OF CATEGORIES, FULL LISTS ARE AVAILABLE BY TELEPHONE/FAX.

STANDARD AND FEATURE PHONES  
SPECIAL APPLICATION PHONES  
OPERATOR HEADSETS  
SPECIAL ENVIRONMENT TELEPHONES  
NOVELTY & CLOCK RADIO TELEPHONES  
DECORATIVE TELEPHONES  
ANSWERING MACHINES  
ANSWERING MACHINE TAPES & ACCESSORIES  
CORDLESS TELEPHONES  
CORDLESS ACCESSORIES BATTERIES & AERIALS  
CT2 DIGITAL CORDLESS TELEPHONES  
FULL RANGE OF CELLULAR TELEPHONES  
RADIO PAGING SYSTEMS (WIDE AREA)  
RADIO PAGING SYSTEMS (LOCAL AREA)  
PAYPHONES  
PAYPHONE ACCESSORIES  
FACSIMILE MACHINES  
FAX SWITCHES & MODEMS  
BUSINESS TELEPHONE SYSTEMS  
CALL BARRING DEVICES  
AUDIO & VISUAL INDICATORS  
VOICE MAIL SYSTEMS  
FAX-ON-DEMAND SYSTEMS  
FULL LINE OF OFFICE PRODUCTS (COPIERS ETC)  
SECURITY PRODUCTS

COMING SOON:  
VIDEOCONFERENCING SYSTEM  
CALL METERING DEVICE (TELAMETA)  
CALLER IDENTIFICATION (SUBJECT TO APPROVAL)

EUROPEAN COMPUTER MARKETING OFFERS  
YOUR ULTIMATE LINE OF SUPPLY!!!  
THE ULTIMATE SERVICE!!!  
VERY COMPETITIVE PRICES!!!  
AND THE HIGHEST QUALITY PRODUCTS !!!


SALES & INFORMATION HOTLINE 24 Hrs  
ALSO PRODUCT DETAILS & LATEST PRICES  
AVAILABLE BY FAX-ON-DEMAND CALL FROM  
A FAX MACHINE AND PRESS START WHEN  
REQUESTED 0944 - 758989

**TRADE & CORPORATE ENQUIRIES WELCOME**

# The Alchemist

## Moving Coil Head Amp

Fig.1 Stylus mounting with damping control

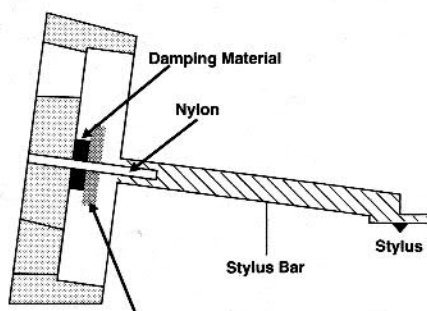

Mike Meechan gets to grips with another pre-amp design for the hi-fi enthusiast.

### Part 1

The cartridge.

**R**eaders *au fait* with the Audiophile RIAA project of the first issue of EIA (October 1993) are probably wondering why I omitted a moving coil stage from said preamp. There are two reasons. Firstly, I'm a firm believer in the *minimalist* approach to engineering. Being a Scot, money - and the saving thereof - is a subject very dear to my heart. It follows that any project that I'm involved in is engineered with cost uppermost in mind - this isn't to say that I abandon all performance considerations because they depend, ultimately, on cost. Rather, I'll look for ways to achieve a certain level of performance in a given field, whilst keeping the bank manager happy about my approach to the more fiscal aspects of everyday life. It could be summed up in one rather naff, advertising copywriters phrase - performance for peanuts...Furthermore, I chose not to include a front end stage suitable for moving coil cartridge preamplification because it would have cost more and would - I then thought - have minimal appeal. Readers of magazines such as this are susceptible to the same pressures and temptations as everybody else. To use the vernacular, "Where am I coming from?" Read on.

We've already mentioned the major technological upheaval that the sound recording industry has undergone in the few years since the birth of digital optical storage and retrieval systems for audio. Despite all of the excellent attributes of CD, and there are indeed many, analogue recordings using vinyl


discs and mechanical recording/retrieving systems have been around for over one hundred years, and much of the music of famous composers, orchestras, bands, and the sounds of historical events have only been captured in the intricate excursions of the analogue record groove. The format persists in the countless millions of discs hoarded in

audiophile archives, music libraries and radio stations, as well as in the homes of personal devotees.

The contents of such discs can never totally be re-recorded using modern-day digital techniques, so it remains of vital importance that the art of preserving, restoring and reproducing such material remains both in the present, and in years to come. Aficionados of the format must remain optimistic that the apparatus necessary to continue doing so remains for the foreseeable future, and beyond.

One of the unassailable attractions of the CD format must be that it is great for the AVERAGE listener. It's robust, the discs themselves will tolerate SOME abuse, there are no pops or clicks, and cuing up and playing a disc requires absolutely no manual dexterity whatsoever. So damaged tonearms and styli become a thing of the past...

But vinyl, too, has its strengths. Some audiophiles claim that they

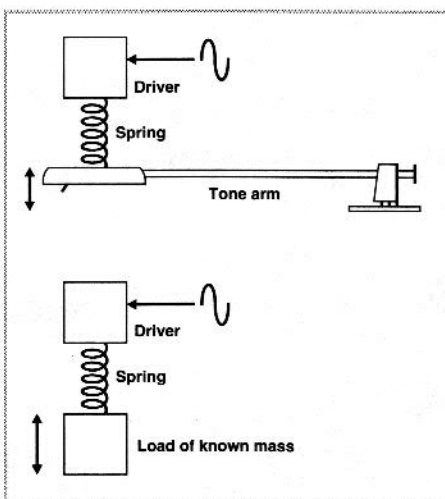

**Fig.2 Method of measuring dynamic mass of Tonearm**  
Tonearm (or cartridge vertical) resonant frequency is found by playing a special test record, with signals at specific frequencies, and recording the frequency at which the cartridge output is highest. Dynamic mass of the tonearm is calculated by suspending the complete arm/cartridge assembly from a spring (connected just above the stylus pivot), and connecting this spring to a loudspeaker-type driving force. The spring is then excited vertically at various frequencies, and the resonant frequency of the assembly noted. Next, the tonearm is freed from the spring, and precisely-valued weights attached in its place. Dynamic mass of the tonearm equates to the mass of attached weights at which the resonant frequency is the same. Once both mass and frequency are known, compliance can be readily calculated.

prefer vinyl discs to CD for one reason and one reason only - they can hear the difference. It's a very controversial subject - scientists versus subjectivists - and blind A/B listening tests have been used in an effort to prove or disprove the claim. Whatever your beliefs on the subject, it is regarded as fact that the harmonics of certain instruments - piano and violin, for instance - extend into frequencies above the accepted ceiling of the human beings ears - ie 20kHz. Proponents of analogue claim, therefore, that it is something of a backward step to stop frequencies above a certain threshold when it's taken over a hundred years for analogue technology to advance sufficiently to be able to reproduce them. It is for this reason, that the low sampling frequency of the format means that the reproduction of CD can be perceived as unnatural because all sounds above a 20kHz maximum are filtered out.

## Rebellion of the Record Lover

Because of these problems, inherent at present to some compact disc reproduction systems, there are a certain number of Luddite listeners, for want of a better phrase, who still happen to like and believe in vinyl. Put another way, these miscreants think it better that CD coexist happily with the old and quaint format known as vinyl. Not for us (yes, I count myself among them) the vast vinyl sell-off (or SELL-OUT). We believe, that it is much better to improve the component parts of the analogue system, and continue using it as a viable high fidelity alternative (or complement) to CD.

Articles in the main are either pro-vinyl and anti-CD, or unequivocally vice-versa. It is the purpose of this article to extol the virtues of vinyl and perhaps broaden the minds of some of our readers who are, perhaps, CD junkies through and through. A new generation of engineers and technologists appears every ten years or so. Perhaps some of you out there belong to this youthful fraternity and it hasn't occurred to you to give vinyl a fair crack of the whip. I hope that I can,

change your minds, but if this isn't the case, at least raise some awareness of what is presently a very topical subject.

Unfortunately the tide has now turned sufficiently that I face a somewhat uphill struggle.

It remains a sad fact of life that Compact Disc has all but displaced vinyl from the shelves of the retail outlets, and sales of CD and cassette, despite the

bizarre pricing anomaly, far outstrip those of the vinyl format. The classical labels - Nimbus initially, followed closely by Deutsche Grammophon - were the first to announce that future recordings would be available only on CD or cassette, and back catalogue on vinyl

would be available only until stocks were exhausted. More recently, this is happening with all new releases, and the only way to track down prized and treasured old vinyl is via the second-hand shop or the collectors fayres.

It is to these misguided, well-meaning miscreants of the audiophile world that this project is dedicated - if you look very closely, you'll see that my tongue is very firmly in my cheek...However, before presenting the project, it is worthwhile to look at the labour of love that is the low-noise designer's realisation of a high performance, moving-coil preamp. As a slight, but pertinent aside, the project was named The Alchemist because there seems to have been so much myth and folklore associated with the magic that is low noise design, a discipline that seems, for many audio engineering students, to have its roots more in black art than science. It is the purpose therefore, of the preliminary part of this paper to dispel some of these myths before presenting the reality in the form of a tangible audio project.

Firstly, we must look at what is involved in getting audio information, in a mechanical form, onto and ultimately from the disc in question.

## A Short History

Around the 1870's, Thomas Edison used a cylindrical phonograph and aluminium foil to reproduce sound. The "flat disc

recording", as it was called, didn't appear until 1887, and it is Emil Berliner who is accredited as being the inventor of a format which has persisted until the present day. Even the most fervent proponents would be hard-pushed not to admit that the reproduction of sound from a vinyl pressing approaches perfection. Nevertheless, where these limitations are appreciated, the attraction of the vinyl disc format, and the scope for improvement, can be seen (or heard).

## From Needle to Loudspeaker

The creation of the recording itself, the design of the apparatus required to extract this information (the cartridge), and finally, getting the information off the disc are the cause of many problems which must be surmounted if the system is to be successful and the resulting sound acceptable.

As far as electromagnetic transducers, the one found at the end of a tonearm has a much harder life than most of its family. In addition to converting the groove modulations of the record into an electrical signal, it must also support the tonearm.

The transducer can be called any one of a number of names - phono pickup, phono cartridge, or needle. The method by which the cartridge converts energy determines the classification under which it falls. Under the piezoelectric classification comes the inexpensive, low-fi and utterly avoidable crystal and ceramic types. Moving magnet (MM), moving coil (MC), and induced magnet (moving iron), on the other hand, are known as electrodynamic-type cartridges. These types use the principle that when a magnetic field intersects a wound coil, an electric current will be generated. While moving magnet cartridges have a magnet attached to the stylus tube or cantilever, and the coils are stationary, moving coil types work on the opposite principle, with the magnet fixed and the coils moving. (The moving iron type uses a magnet and coil which are fixed, and a slug of soft magnetic iron which moves instead of the magnet, and is magnetised by it). Happily, technology has advanced sufficiently that the various materials which might one day have found their way into the stylus assembly - cactus needles, whale bones, all kinds of metals, gemstones, plastics and wood, to name but a few - have all been superseded!

Because of the interaction of magnet and coil in these types of cartridges, any

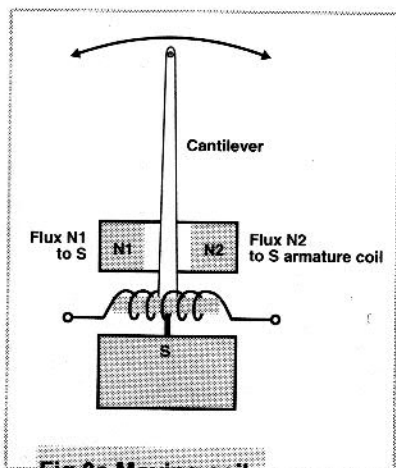


Fig.3a Moving coil cartridge

amplifier sees a decidedly non-linear source impedance at its input. With reference to Faraday's law of induction, induced voltage is proportional to the relative velocity of both the magnet and coil parts of the assembly.

The design of the cartridge must ensure that a linear relationship exists between the position of the stylus cantilever assembly and the magnetic flux (since the signal voltage generated at any instant in time is proportional to rate of change of flux with respect to time). Rate of change of stylus position with respect to time will thus be proportional to the signal voltage. However, the groove shape is proportional to the integral of the signal waveform, so the groove excursions - the waveform imprinted in the vinyl - are not directly proportional to the signal voltage.

This means that the signal voltage is proportional to the velocity of the stylus, and the signal SLOPE is proportional to the ACCELERATION of the stylus. Consequently, the cartridge cantilever assembly and associated suspension, and the magnet/coil system, must form a resonant mass-spring system if high signal slopes are to be reproduced with any degree of fidelity.

### The Appliance of Science

"Springiness" and mass determine the amount of force required to move the stylus. Using the damped mass-spring model of a magnetic cartridge, we can predict that the resonant frequency will depend upon the "springiness" of the cantilever's suspension, and on the mass of the stylus cantilever assembly. "Springiness" is given the symbol  $k$ , the spring constant, and is represented numerically.  $K$  is defined in terms of the force needed to bring about a certain compression or extension of the spring, so stiffer springs have a higher  $k$  value. Spring constants are almost unusably low numbers, so the reciprocal of the spring constant -  $1/k$  - is quoted in preference by cartridge manufacturers. This reciprocal is called compliance. Compliance of the cantilever or stylus is the ability of the assembly to react to groove modulation, and it is measured

(statically or dynamically) in  $\text{cm/dyn}$  or  $\mu\text{m/mN}$ , with a lower compliance figure equating to a stiffer suspension system. Dynamic compliance gives us the means to calculate the resonant frequency of the tonearm/cartridge assembly, and so measure the effective mass of the tonearm. Compliance is calculated as follows;

Where:


**c** is the compliance in  $\text{cm/dyne}$

**f** is the frequency in Hertz

**M** is the tonearm mass in grams

At resonance, there is no longer a linear relationship between the

frequency by lowering the  $Q$  of the system. This is done by introducing mechanical or electrical losses into the system. The most widely-used method is to introduce friction into the cantilever suspension assembly using rubber mounting blocks. Desired mechanical damping is achieved, whilst the absorption of energy (into the load resistance of the cartridge preamplifier), lowers the electrical  $Q$  of the system. See Figure 1. It would be correct to say that the reproduction of sound from a vinyl disc owes as much to complex mechanics as it does to electronics.

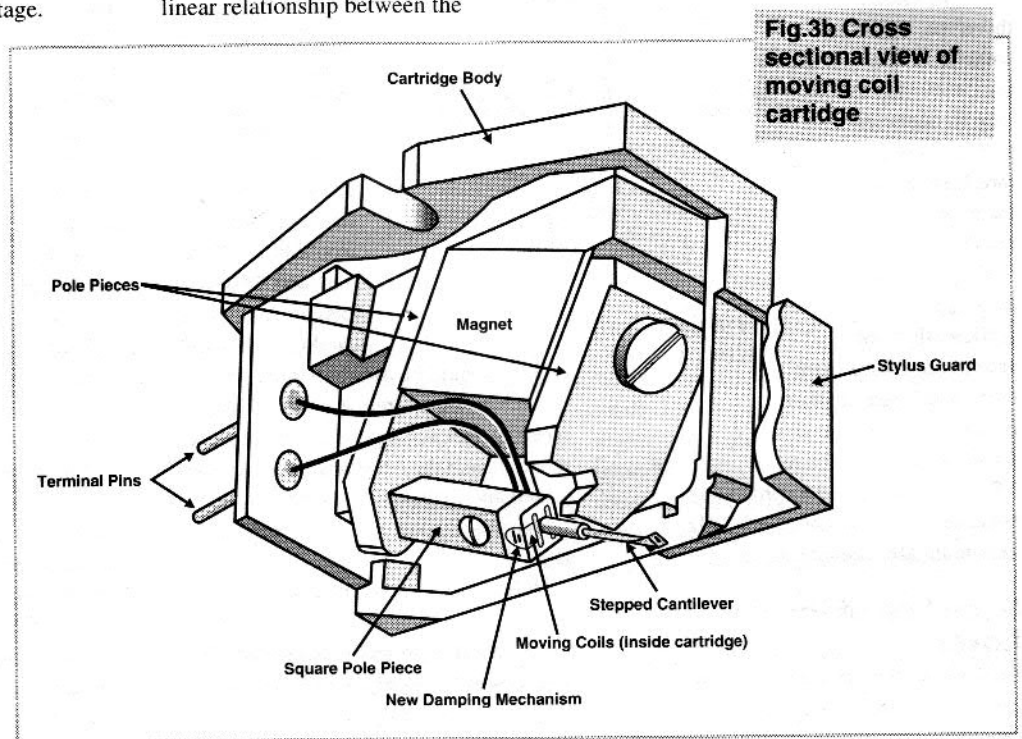

**Fig.3b Cross sectional view of moving coil cartridge**

impedance of the cartridge and the driving force on the stylus. This non-linearity results in distortion of the waveform. However, shifting the resonant frequency to a point in the spectrum which is below the lower audible limit helps to overcome this. This can be achieved either by increasing the mass or the value of the compliance (since the cartridge resonant frequency is a function both of mass, and of the compliance of the cantilever and suspension system). Lowering of the mass is the more desirable method, since the stylus is then able to respond better (more quickly) to the changes in the record groove. Compliance is thus altered until a resonant frequency which is suitable - typically below 10Hz - is then achieved. The most desirable range is between 8 and 12Hz since resonance below 8Hz will produce instability of the tonearm, and will result in poor tracking of any records with warps.

It is also possible to alter resonant

### Moving Coil Cartridges

This type were among the first to be used and employ one heavy magnet, and the cantilever assembly, (which cannot be replaced by the user). The MC cartridge is insensitive both to input load impedance, (typically in the order of 5 to 100 ohms), and to capacitive loading, so that long cables can be driven without detriment to the frequency response. Regrettably, the low impedance which creates these benefits also means low output - typically some 20-30dB below that of the moving magnet type, when referenced to an established sensitivity of  $1\text{mV/cm/s}$ . Very careful amplification of the cartridge output signal is thus required if noise performance isn't to be unduly compromised. A further downpoint of the MC type is that tracking forces are much heavier, although sound quality from the moving coil cartridge can be very good, with distortion figures typically lower than the moving magnet

type. The very fast response to transients in any musical passage (as a result of the very low impedance and inductance of the coils (much less than the 0.3 - 1H of the MM type), and a very rigid and strong cantilever (necessary to support a heavy magnet assembly) gives a flatter and more extended frequency response. Furthermore, better channel separation (some 30-40dB compared to the 20-30dB of the fixed coil type) is achieved because the stylus assembly and the coil system are in much closer proximity.

All of the above means that construction of the coil assembly is particularly critical. Flaws in this area which can lead to problems include numbers of unsupported turns, which can set up vibrations in the assembly, and generate random output at HF, and improperly-secured lead-in and lead-out wires, which can vibrate in the magnetic field, and cause colouration of the output signal. In spite of this, the moving coil, because of the extended frequency response, and excellent transient characteristics, has traditionally been favoured over other types by the true audiophile fraternity. See Figure 3.

## Moving Magnet Cartridges

This type of cartridge appeared much later than the MC, originating in Europe in the late fifties. Its durability and low relative cost when compared to the MC cartridge (no separate head amp required) have helped it to become the most popular example of the phono cartridge. It has high compliance, low dynamic tip mass, and the large number of turns in the coil assembly provide a reasonably high output voltage capability. Although the basic principle hasn't changed much since its first appearance, it has been refined to such an extent over the years that modern-day cartridges in the vanguard of the moving magnet type can produce outputs well above the audible frequency ceiling (typically 50kHz in some examples). However, the rising inductive component of the cartridge impedance, which has a typical resistive component of 200R-1k, means that the output level MUST diminish (or disappear) at frequencies higher than this. The unique electromagnetic characteristics of the moving magnet cartridge mean that any input stage

intended for use with it must have well-defined impedance at all frequencies, (and despite the worst excesses of the cartridge), if performance is not to be compromised. See Figure 4.

## Variable Reluctance (Induced Magnet)

Although their physical construction differs, performance characteristics of these are almost identical to those of the moving magnet cartridge. A small armature, in the shape of a cross, swings between four pole pins and coils, whilst a stylus bar, which has the stylus at one end, is secured to the armature at the other. 45° of motion to one side cause reverse voltage induction. This allows push-pull operation of the coils, and thus reduces harmonic distortion caused by non-linearities in the magnetic field. The coils also provide hum bucking (rejection) with crosstalk components bucked out, so channel separation is good, regardless of frequency. See Figure 5.

## Other Types

The other types of cartridges in existence (but which we won't discuss in detail) are the semiconductor cartridge and the piezoelectric (crystal or

pointless exercise - and very wasteful of design time and resources - to have an amplifier fitted with an RIAA equalisation network which is accurate to 0.1dB across the audio spectrum, but which is connected to a cartridge where has an incorrect value of shunt capacitance has been connected across it. Input capacitance, as specified by the cartridge manufacturer, is the TOTAL

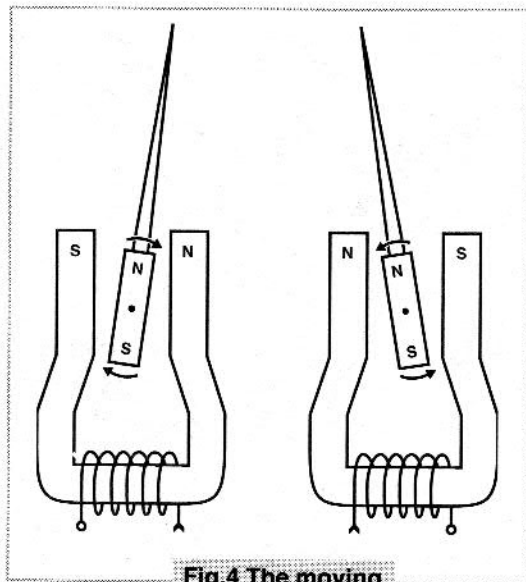


Fig.4 The moving magnet cartridge

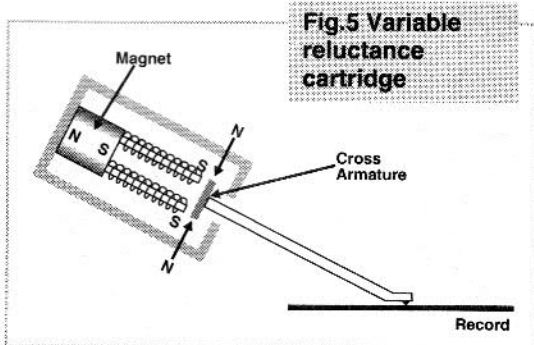


Fig.5 Variable reluctance cartridge

ceramic) type. The latter type belong to group known as constant amplitude (or pressure sensitive) cartridges, since they give an output which is proportional to the force applied to the stylus, and so produce an output voltage which is independent of frequency (no equalisation is therefore required).

## Electrical Loading

Electrical loading of the cartridge, at the amplifier input, is of paramount importance if overall frequency response isn't to be needlessly impaired. It's a


capacitance of all the conductors between the cartridge and the amplifier input. This includes cartridge connectors, tonearm wiring (both to ground and between conductors), connecting leads, preamplifier board layout, and shunt capacitance on the board. Incorrect values typically cause a peak or resonance in the circuit, somewhere between 7 and 8kHz, before the response rolls off prematurely in the upper HF part of the audible spectrum. Aside from the effect of electrical loading at high frequencies, the cartridge may also suffer because of the effective mass of the tip, since this effectively determines how close the coupling between stylus and groove wall is. Forces in effect during movement of this mass at high frequencies can actually deform the groove, which delays the acceleration of the stylus, and slurs high frequency sounds.

## Next Month

We look closely at noise - what causes it, how we can reduce its effect upon our system, real semiconductor applications - before presenting The Alchemist project.


# PROTEUS
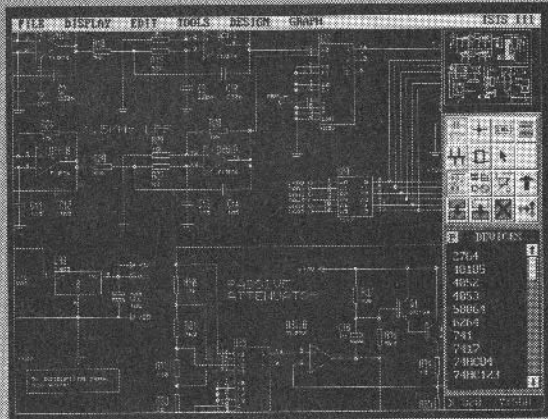
## The Complete Electronics Design System



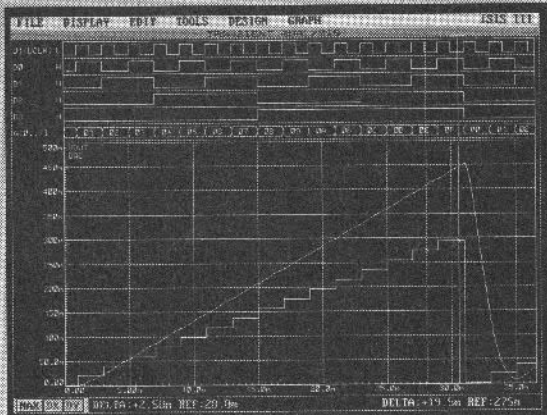
### Schematic Capture

- Easy to Use Graphical Interface.
- Netlist, Parts List & ERC reports.
- Hierarchical Design.
- Extensive component/model libraries.
- Advanced Property Management.
- Seamless integration with simulation and PCB design.


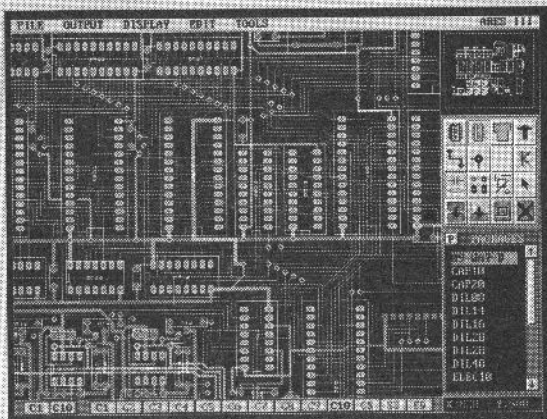
### Simulation

- Non-Linear & Linear Analogue Simulation.
- Event driven Digital Simulation with modelling language.
- Partitioned simulation of large designs with multiple analogue & digital sections.
- Graphs displayed directly on the schematic.



### PCB Design

- Multi-Layer and SMT support.
- Unlimited Design Capacity.
- Full DRC and Connectivity Checking.
- Advanced Multi-Strategy Autorouting.
- Output to printers, plotters, Postscript, Gerber, DXF and DTP bitmaps.
- Gerber View and Import capability.

**labcenter**  
**E l e c t r o n i c s**

*Write, phone or fax for your free demo disk, or ask about our full evaluation kit.*  
**Tel: 0274 542868. Fax: 0274 481078.**  
**14 Marriner's Drive, Bradford BD9 4JT.**

Proteus software is for PC 386 compatibles and runs under MS-DOS. Prices start from £475 ex VAT; full system costs £1495. Call for information about our budget, educational & Windows products. All manufacturers' trademarks acknowledged.

# EXPRESS COMPONENTS

**MAINS IONIZER KIT.** Very useful kit that increases the flow of negative ions, helps clear cigarette smoke, dust, pollen etc. Helps reduce stress and respiratory problems. £15. kit, £20 built.

**COMBINATION LOCK.** Electronic 9 key combination lock suitable for alarms, cars, houses etc, easily programmable. Includes mains 2A relay o/p. 9v operation. £10 kit, £14 built.

**VARIABLE POWER SUPPLY.** Stabilized, short circuit protected. Gives 3-30v DC at 2.5A, ideal for workshop or laboratory. £14 kit, £18 built. 24V AC required.

**LEAD ACID CHARGER.** Two automatic charging rates (fast and slow), visual indication of battery state. Ideal for alarm systems, emergency lighting, battery projects etc. £12 kit, £16 built.

**PHONE LINE RECORDER.** Device that connects to the 'phone line and activates a cassette recorder when the handset is lifted. Ideal for recording 'phone conversations etc!. £8 kit, £12 built.

**ROBOT VOICE.** Turns your voice into a robot voice! answer the phone with a different voice!. £9 kit, £13 built.

**PHONE BUG DETECTOR.** This device will warn you if somebody is eavesdropping on your 'phone line. £6 kit £9 built.

**PHONE BUG.** Small bug powered by the telephone line. Only transmits when the phone is used. Popular surveillance product. £8 kit, £12 built.

**STROBE LIGHT.** Bright strobe light with an adjustable frequency of 1-60hz. (a lot faster than conventional strobes!) £16 kit, £20 built.

**4W FM TRANSMITTER.** 3 RF stages, audio preamp. 12-18vDC. Medium powered bug £20 kit, £28 built.

**3 CHANNEL LIGHT CHASER.** 3x 800w output, speed and direction controls, can be used with 12 led's (supplied) or TRIACS for mains lights (also supplied). 9-15v DC. £17 kit, £23 built.

**25W FM TRANSMITTER.** 4 stage, a preamp will be required. (Our preamp below is suitable) £79 built. (no kits).

**SOUND EFFECTS GENERATOR.** Produces any thing from bird chips to sirens! add sounds to all sorts of things £9 kit £13 built.

**FM/AM SCANNER.** Well not quite, you have to turn the knob yourself but you will hear things on this radio (even TV) that you would not hear on an ordinary radio! A receiver that covers 50-160MHZ both AM and FM. Built in 5w amplifier. £15 kit, £20 built.

**CAR ALARM SYSTEM.** Works on vibration and/or voltage drop from door etc being opened. Entry and exit delays plus adjustable alarm duration. Low cost protection! £12 kit, £16 built.

**15W FM TRANSMITTER.** 4 stage, high power bug. You will need a preamp for this (see our preamp below which is ok) £69 built. (no kits).

**1W FM TRANSMITTER.** 2 stage including preamp and mic. Good general purpose bug. 8-30VDC. £12 kit, £16 built.

**50 I/C's for £1.50**  
Nice mix of chips at a bargain price!

**CERAMIC CAPACITOR PACK**  
Good mixed pack of 100 capacitors for just £1.00

**ELECTROLYTIC PACK 1**  
100 small mixed electrolytic capacitors just £1.00

**ELECTROLYTIC PACK 2**  
50 larger electrolytic mixed capacitors

**RESISTOR PACK NO 1**  
250 low wattage resistors, ideal for most projects etc. Just £1.00

**RESISTOR PACK NO 2**  
Hi wattage pack, good selection of mixed wattages and values 50 in all, bargain price just £1.00

**PRESET PACK**  
Nice selection of 25 mixed preset pots for just another £1!

**RELAY PACK NO 1**  
6 mixed relays for £1, that's just 17p each.

**CONNECTOR PACK**  
10 different connectors, again for £1

**FUSE PACK NO 1**  
40 mixed 20mm fuses, ideal for repairs etc, or just to stock up the spares box! Just £1.00

**FUSE PACK NO 2**  
30 mixed 1.25" fuses again ideal for spares etc. Just £1.00

**WIRE PACK**  
25 Metres of insulated wire for just £1.00, good for projects etc.

**SLEEVING PACK**  
100 assorted pieces of sleeving for connectors etc. Yours for just £1.00

**DIODE PACK**  
100 assorted diodes for just £1.00

**LED PACK**  
20 light emitting diodes for £1.00

**TRANSISTOR PACK**  
50 mixed transistors, another bargain at £1.00

**BUZZER PACK**  
10 things that make a noise for just £1.00!

**POT PACK**  
10 pots for £1, (5 different types) a snip at £1.00

**DISPLAYS**  
10 seven segment displays for £1.00

**ORDER 10 PACKS OR MORE AND CHOOSE ONE FREE PACK!!**

**FREE COMPONENT CATALOGUE WITH EVERY ORDER!!!**

99p  
Post

## BULK PACKS

**PREAMP MIXER.** 3 channel input, independent level and tone controls. Ideal for use with the hi power FM transmitters. £15 kit, £19 built.

**TREMBLER ALARM.** Designed for bikes etc, adjustable sensitivity, preset alarm time, auto reset. Could be adapted for all sorts of "borrowable" things £12 kit, £16 built.

**ULTRASONIC RADAR.** A project that can be used as a movement detector in an enclosed space. Range about 10 metres, 12vDC. Good basis for car, shed, caravan alarm etc. £14 kit, £19 built.

**PHONE CALL RELAY.** Very useful kit that incorporates a relay that operates when the phone rings. Can be used to operate more bells, signalling lights etc. Good for noisy environments or if you have your headphones on! £10 kit, £14 built.

**PORTABLE ALARM SYSTEM.** Small 9v alarm system based on a mercury switch. The alarm continues to sound until disabled by the owner. Buzzer included. £11 kit £15 built.

**800W MUSIC TO LIGHT EFFECT.** Add rhythm to your music with this simple sound to light kit. £8 kit, £12 built.

**MOSQUITO REPELLER.** Modern way to keep the midges away! Runs for

about a month on one 1.5v battery. Frequency is set to drive away mosquitos etc. £7 kit, £11 built.

**3 CHANNEL SOUND TO LIGHT.** Can be used anywhere as no connection is made to hi fi. Separate sensitivity controls for each channel, 1,200W power handling. Microphone included. £14 kit, £19 built.

**MINI METAL DETECTOR.** Detects pipes, wires etc up to 20cm deep. Useful before you drill those holes! £8 kit, £12 built.

**0-5 MINUTE TIMER.** Simple time switch adjustable from 0-5 mins, will switch 2A mains load. 12v op. Ideal for laboratory, photographic projects etc. £7 kit, £11 built.

**7 WATT HI FI AMPLIFIER.** Useful, powerful amplifier 20hz-15khz, 12-18vdc. Good for intercoms, audio systems, car etc. £7 kit £11 built.

**INCAR SOUND TO LIGHT.** Put some atmosphere in your car with this kit. Each channel has 6 led's that create a beautiful lighting effect! £10 kit, £14 built.

**VOX SWITCH.** This is a sound activated switch, ideal for use on transmitters, CB's, tape recorders etc. Adjustable sensitivity, built in delay. Mic input. £7 kit, £11 built.

## LIQUID LEVEL DETECTOR.

Useful item, can be used to detect fluid levels in watertanks, baths, ponds fishtanks etc. Could also be used as rain alarm with an easily constructed sensor. £5 kit, £9 built.

**FM TRANSMITTER.** Mini FM transmitter 2 transistor, comes with FET miniature mic and is tuneable from 63 to 130MHZ. £7 kit, £11 built.

**FUNCTION GENERATOR.** Generates sinusoidal, saw tooth and square waveforms from 20hz up to 20khz. Separate level controls for each waveform. 24vac. £15 kit, £20 built.

**5 WATT SIREN.** Powerful siren kit with an impressive 5 watts output. Ideal for alarms etc. £6 kit £10 built.

**TELEPHONE AMPLIFIER.** Very sensitive amplifier which using a 'phone pickup coil (supplied) will let you fol-

low a telephone conversation without holding the handset to your ear! £11 kit £15 built.

**SWITCH PACK**  
10 switches for just £1.00

**12v FLOURESCENT.** A useful kit that will enable you to light large flourescent tubes from your car battery etc. 9v mains transformer required. £8 kit, £12 built.

**KNOB PACK**  
10 knobs for just £1.00

**REMEMBER! YOUR FREE COPY OF OUR CUT PRICE COMPONENTS CATALOGUE SENT WITH EVERY ORDER!!!**

How to place your order.....

By phone.....0273 771156

By FAX.....0273 206875

By Post...PO box 517 Hove Sussex BN3 5QZ

Payment by ACCESS, VISA, CHEQUE OR POSTAL ORDER.

Cheques and postal orders should be payable to Express Components.

**ALL PRICES ARE SUBJECT TO 99p POST AND VAT.** Some of our products may be unlicensable for use in the UK (particularly the FM transmitters.)

# The Eyes Have It


## Ophthalmic Excimer Lasers by Douglas Clarkson

**F**rom being a scientific curiosity, excimer lasers are now becoming increasingly utilised as a means of directly modifying the focusing characteristics of the human cornea in order to rectify basic vision defects such as short sightedness. A new range of 'third generation' machines are now providing higher levels of treatment accuracy and patient benefit.

### All About the Eye

The focusing ability of the eye is described in diopters. This can be expressed in  $1/f$  where  $f$  is the effective focal length of the eye. Often it is the excess or shortfall of the eye's focusing which is referenced e.g. a short-sighted eye will have around an excess of 5 Diopters and a far sighted eye a shortfall of 5 Diopters. There are several contributions to the overall focusing undertaken by the human eye. The front surface of the cornea has a significant focusing effect due to the change in refractive index (air-cornea surface). The lens which is

**Fig.1 Basic structure of the human eye.**

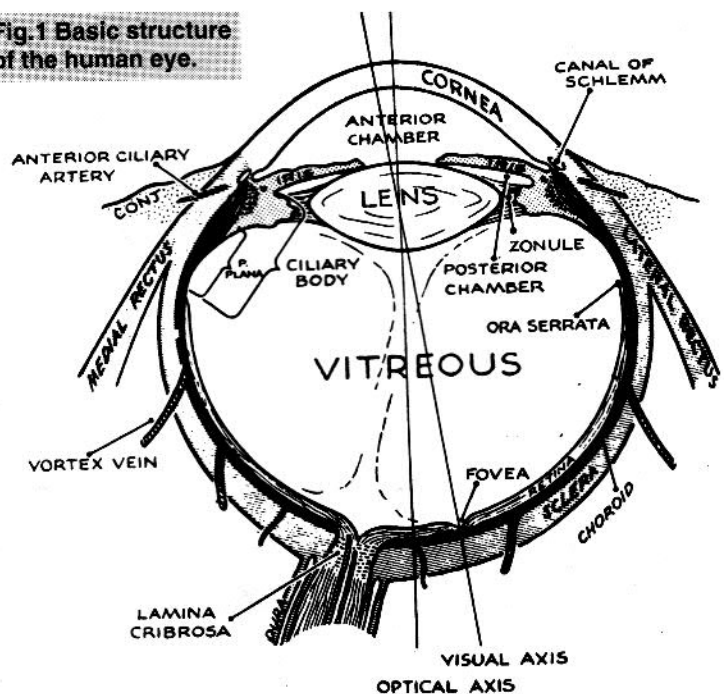

situated behind the cornea in the anterior chamber has an additional element of focusing. The lens is attached around its periphery by fine ligaments which can be drawn tighter and relaxed by muscles in the ciliary muscle. This allows 'fine' focusing on objects at varying distances from the eye. The basic structure of the eye is indicated in Figure 1.


It is quite common for the eye to develop so called short sightedness where the eye's optics tend to focus light too strongly. The net result is that the plane of the focused image is presented in front of the retina and the image on the retina is blurred.

**Fig.4 Placido image which is projected onto the eye in order to determine relative focusing ability across the cornea.**


Standard remedies to date have included the wearing of spectacles and contact lenses. Both these approaches bring benefits of correcting visual defects. About a quarter of all adults are myopic to some degree.

With age, the optical 'fitness' of the eye diminishes. The degree of accommodation provided by the ligaments attached to the lens can decrease as the lens becomes increasingly 'stiffer'. So called long-sightedness arises when the eye is not sufficiently strong to focus images on the retina. Instead images are brought to a focus beyond the retina.

The front surface of the cornea can develop asymmetry so that images cannot be focused on the plane of the retina. This is the condition known as astigmatism. Figure 2 shows the three basic types of eye conditions which result in blurred images being formed at the cornea.

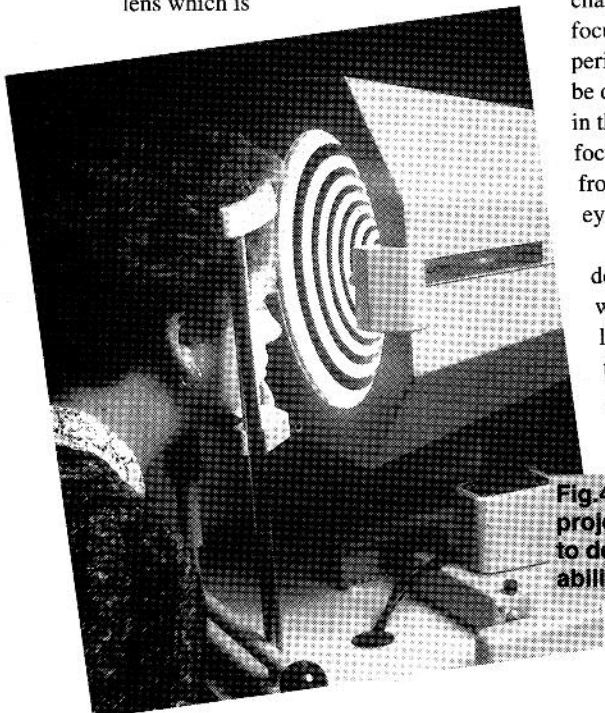



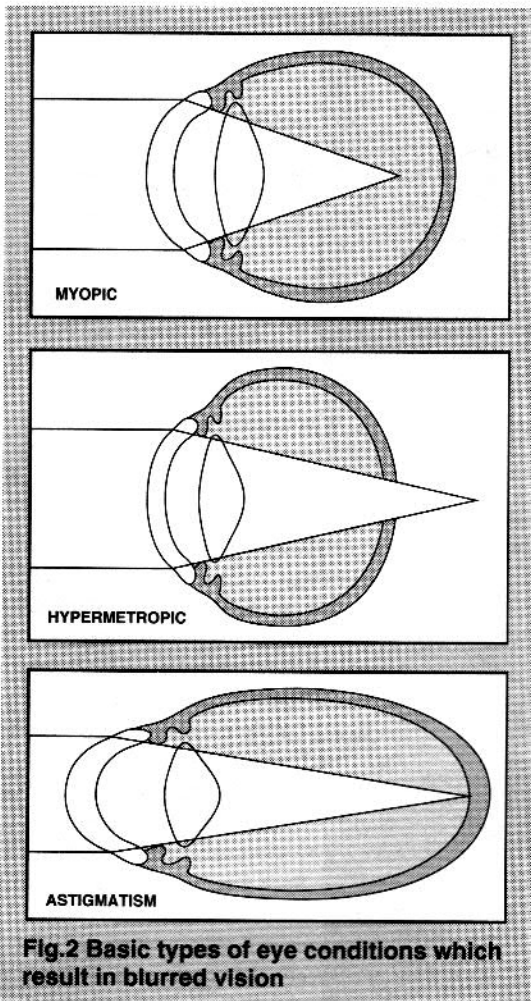

**Fig.2 Basic types of eye conditions which result in blurred vision**

## Surgical Alteration of the Cornea

During the 1980s various methods were investigated for direct surgical intervention in order to rectify some of these defects. In the radial keratotomy procedure, a series of between four and eight spoke-like incisions are made in the cornea in order to decrease its curvature and move the focal plane of images backwards. This procedure is primarily a treatment for myopia. In a trial of over 757 eyes treated in this way in the USA and completed in 1991 it was found that the procedure was more successful in older patients than younger ones and that the procedure could more readily rectify low to medium degrees of myopia - corresponding to corrections of between 1.5 to 5 diopters. The trial found that while the technique led to improvements in 'natural' focusing ability planned changes in focusing ability could not always be achieved.

## Ophthalmic Use of Excimer Lasers

During the mid 1980s interest focused on the use of lasers for direct change of the optical properties of the cornea. Excimer lasers can selectively remove

cell layers from the core of the cornea - between the outer and lower layer. Once this technique called photorefractive keratectomy had been demonstrated, the technology was developed for precise control sculpting of the cornea.

Photorefractive keratectomy (or PK) was fundamentally different from the previous surgical technique of radial keratotomy. While the surgical technique relied on wound healing to pull the cornea flatter, the laser method, by skimming off layers from the cornea does not weaken the structural integrity of the eye.

To date PK has been mainly used for the treatment of short sightedness and various types of astigmatism.

## Basic Ophthalmic Use of Excimer Lasers


Excimer lasers used for this technique operate typically at a wavelength of 193nm - in the band of UVC radiation. Energy is delivered in a series of ultra short pulses of duration between 10 and 20

treatment beam by an iris like device. This method, allows a varying thickness to be removed from the cornea in order to achieve required cornea profiles. If this method was adopted then the cornea would present a staircase profile as shown in Figure 3. This is prevented by the use of an oscillating mirror to move specific pulses over a variable area so there are no abrupt gradations.

Small plumes of smoke produced by the laser energy are visible when the cornea is being sculpted. Typically the laser will have forced air ventilation to prevent smoke contamination of laser optic elements. It is of course vital that the eye does not move during the PK procedure. An assembly can be secured to the eye under suction in order to immobilise it. Systems are also in use which incorporate 'eye tracking' where any motion of the eye is compensated for automatically.

The use of such lasers requires high accuracy. The cutting effect of the laser is after all proportional to the total delivered energy at the treatment site. Excimer lasers, however, may vary their output powers significantly during a single day of operation. This is the result of interaction of complex variables within the excimer laser system. Most systems will be calibrated before a patient undergoes treatment to ensure removal of a predetermined layer of cornea tissue. For this test a specially

**Fig.3 Staircase corneal profile which would be produced if oscillating mirror not used to 'blur' energy gradients over the cornea.**

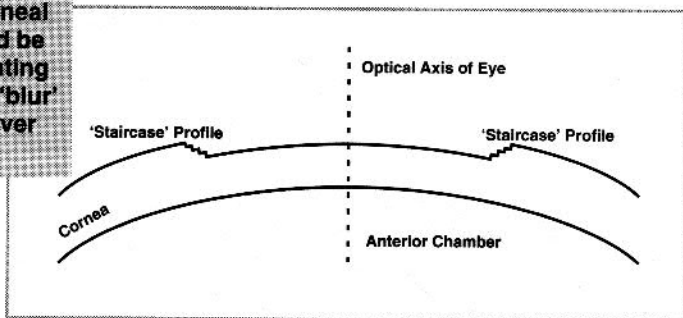

nanoseconds with maximum pulse energies typically of 0.5J. The energy density required to ablate the corneal tissue is around 120 milli-joules/cm<sup>2</sup>.


The laser energy removes a finite thin layer of cornea tissue and is typically about 0.25 micron per pulse. The interaction time is so short that there is insufficient time for heat energy to build up in the treated tissues. Prior to treatment, the thickness of the cornea is accurately measured in order to retain an adequate thickness.

While this gives a general outline, there is considerable sophistication in cornea sculpturing techniques. It is possible, to alter the size of the

fabricated target consisting of metal foil bonded onto a plastic laminate is placed at the treatment zone of the excimer laser. A specific series of laser firings are undertaken with each one removing a very thin layer of metal film from the target surface. The system will measure the number of pulses required to remove the metal film and modify the energy of each pulse fired subsequently in order to meet calibration criteria.

In assessing of patients for excimer laser sculpting, it is essential to accurately determine the refractive properties of the eye prior to and after treatment. It is important to identify eye conditions for which PK would be

**Fig.5 Basic laser resonator.** The lasing medium is contained between two mirror resonators so that photons released by stimulated emission can build up intensity as they are reflected from the end mirrors. One mirror is partially reflecting so a portion of the resonant energy can 'escape'.

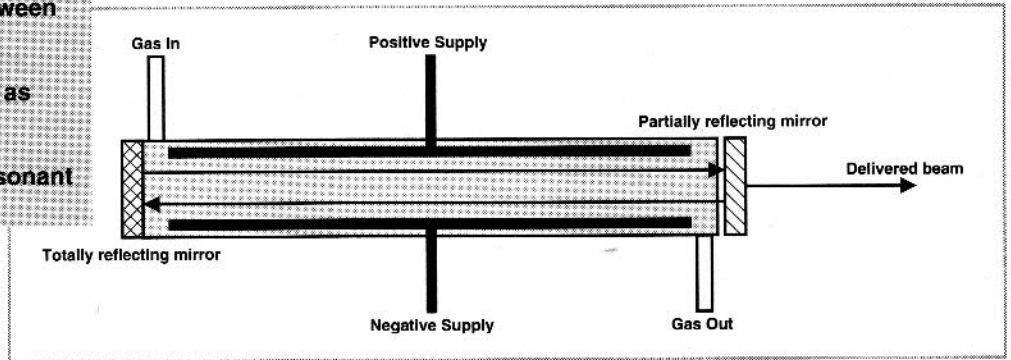

suitable. This can be rapidly undertaken using a corneal topography system. Figure 4 shows how a so called Placido image comprising 16 alternate black and white rings is projected onto the eye. Light which has passed through the eye's refractive path is then captured by a Charge Coupled Device camera comprising 6000 pixels and the image is processed by a computer to determine the relative focusing ability of the eye. Figure 5 shows the history of how the refractive properties of an eye changed with conventional radial keratotomy - where the cornea is incised with eight incisions. In this example the patient had 3D of myopia and was reduced to 0.25D.

The process of erosion of cornea thickness can usually be configured as a process of a cylindrical contour to correct for astigmatism and a circular cut to correct for myopia. It is now possible for the automated vision profile of an eye being treated to be passed from such a vision analysis unit directly to the computer in the PK system so that correction is 'tailored' for the patient.

There are also free hand modes available where the operator can move

the excimer beam over areas where non standard modes of corneal tissue removal are indicated.

Part of the preoperative test is the measurement of the thickness of the cornea. This ensures an adequate thickness of corneal tissue. Without removal of this outer cell layer, the PK procedure cannot go ahead.

It is possible also to monitor the degree of regression of the PK treatment. While in most cases there will be a minor degree of regression where the eye will lose some of its short sighted correction, it is possible for more serious regression to occur.

Figure 8 shows a relatively stable excimer PK procedure where there has been only a slight degree of regression.

## Main Features of Excimer Lasers


Excimer lasers belong to a family of lasers which use chemical reactions of stable noble gases such as Xenon and Argon with unstable Halogen atoms such as Chlorine and Fluorine. Chemical reactions do not normally tend to take place in mixtures of such gases.

It requires excitation

of a high voltage discharge across the tube or electron beam or microwave excitation for short lived chemical compounds to be generated. The short lived compounds exist for short times in raised energy levels. The unstable bound compound can break down into the free components and in so doing release energy. The excited molecules exist only for a short time - at most 20ns.

When molecule population in excited states has been established it is necessary to establish an optical resonator within which light can be released by stimulated emission of radiation. Such a resonator is shown in Figure 5. If a 'dimer' releases by spontaneous emission, a photon of light in the direction along the axis of the resonator, then this photon can induce other excited dimers to release light by stimulated emission. Photons are released with similar energy, direction and phase. A pulse of light will sweep along the resonator and be reflected from the faces of the resonator. While for many resonators it is necessary to have high values of reflectivity, low values of around 5% can be adequate for excimer lasers. One face of the resonator

**Fig.6 Key elements of the Chiron Technolas excimer laser.** Laser radiation is passed through a beam homogeniser and then through a variable aperture unit under computer control. The beam passes through various optics to reduce the beam size. A red He-Ne aiming beam provides location data along the axis of the treatment beam and a green He-Ne beam when co-incident with the red aiming beam gives accurate location in the vertical plane.

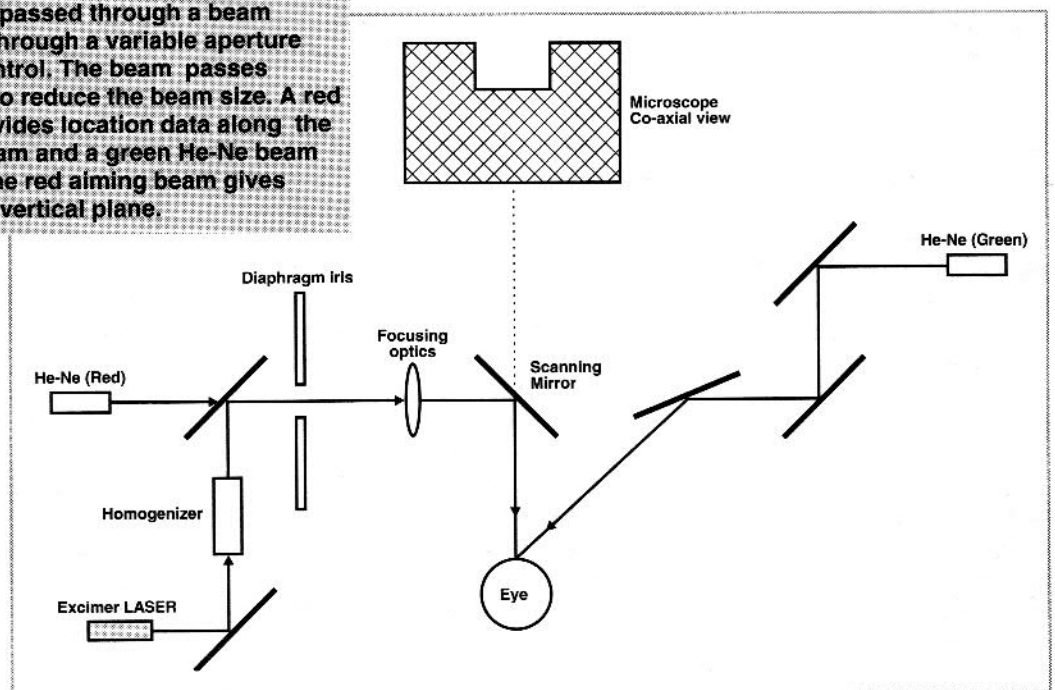


will transmit laser radiation out of the resonant cavity and into the delivery optics. Argon Fluorine gas mixtures are typically used for excimer lasers used in ophthalmology.

The gas becomes slightly depleted after each gas change. A gas cylinder will typically contain 100 gas fillings of the resonant chamber. Gas in the chamber will slowly degrade, so that if the system has not been operated for 48 hours it is advisable to renew the gas in the resonant chamber.


Key safety features can be built into the excimer gas handling procedures. A filter system can for example remove the reactive halogen (fluorine or chlorine) from the charge of used gas. The stable noble gas such as Argon or Xenon is released to air.

Figure 6 shows the key elements of a modern excimer laser such as the Chiron Technolas Keracor 116. Radiation emitted from the excimer laser is input into a homogeniser unit to produce a more even beam energy cross section. Radiation is then reflected into a variable aperture unit so that the cross section of the delivered beam can be controlled. The beam then passes into a series of focusing optics to reduce the treatment beam cross section. A scanning mirror in turn reflects the beam down onto the treatment site. This mirror can be rapidly moved in order to even out effects produced by different aperture widths and corresponding beam profiles.

A red He-Ne aiming beam (633nm wavelength) is established coaxial with

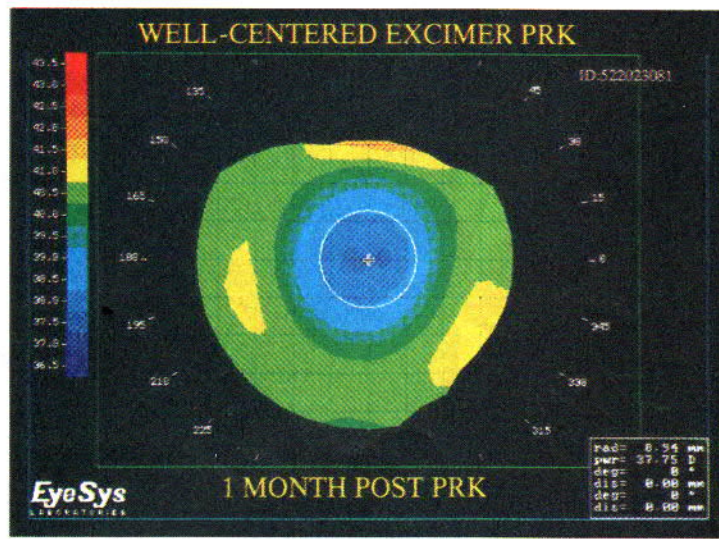

**Fig.7** Indication of how the refractive properties of an eye which underwent conventional radial keratotomy can be monitored prior to treatment and after treatment. In this case the patient had 3D of myopia which was reduced to 0.25D.

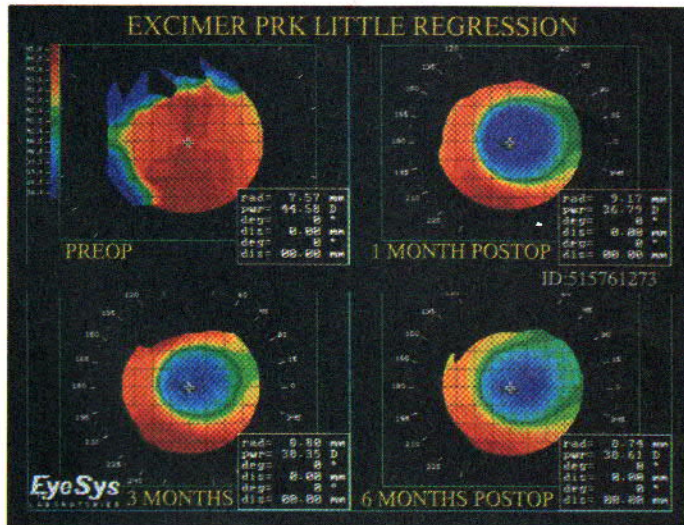

**Fig.8** Example of excimer PK procedure with relatively little regression.

the treatment beam so that the target area of the treatment beam can be identified. In addition it is important to identify the absolute height at which the excimer energy is to be delivered. This is

undertaken by the use of a separate green He-Ne laser (543 nm wavelength) set at approximately 30 degrees to the vertical axis of the treatment beam.

A 'ruggedised' PC is used as a control system for generating the laser

energy and its delivery. Special precautions are required to prevent interference from the high voltage laser system affecting the PC.

Table 1 summarises the performance details of the Chiron Technolas Keracor 116 Excimer Laser. The energy density at the treatment site can vary between different manufacturers so that different thicknesses of cornea are removed with each treatment pulse.

### Summary

Modern technology now makes possible the use of excimer lasers for the sculpting of the cornea to correct focusing defects which would normally be remedied with spectacles or contact

lenses. There is no doubt that while the excimer technology may have advanced significantly in terms of levels of control of the corrective procedure, the technique will always require clinical skills of the highest level in order to ensure that only appropriate eyes are treated and that the treatment which is undertaken is expertly done.

Thus while contact lenses can be fitted in the high street by a qualified optician, at present the skill level required is that of a consultant ophthalmologist

with broad experience of invasive ophthalmic procedures. This is both to check for abnormal eye pathology prior to treatment and to achieve a high level of skill in the delivery of the excimer laser energy.


Also, even the use of the more modern forms of contact lens has not been proved over sufficiently long periods of time to determine the relative safety of such devices. Problems encountered relate to infection, irritation and reduced oxygen levels in the cornea. So also PK and associated techniques will require a considerable time before a true perspective can be obtained on the relative safety and permanence of the treatment.

There is no doubt that the technological component of ophthalmic excimer systems is developing rapidly.

Variable	Value
Maximum power at laser site	1W
Maximum pulse energy	450mJ
Wavelength	193nm
Pulse length	18ns
Repetition Rate (max)	30Hz
Fluence test pulse count	63 +/-5
Treatment energy density	120 milli Joules/cm <sup>2</sup>
Ablation layer per pulse (cornea)	0.25 microns

**Table 1: Typical output parameters of the Chiron Technolas Keracor 116 Excimer Laser. The conversion efficiency of the laser system is low - around 0.1%.**

# at the Channel Hop

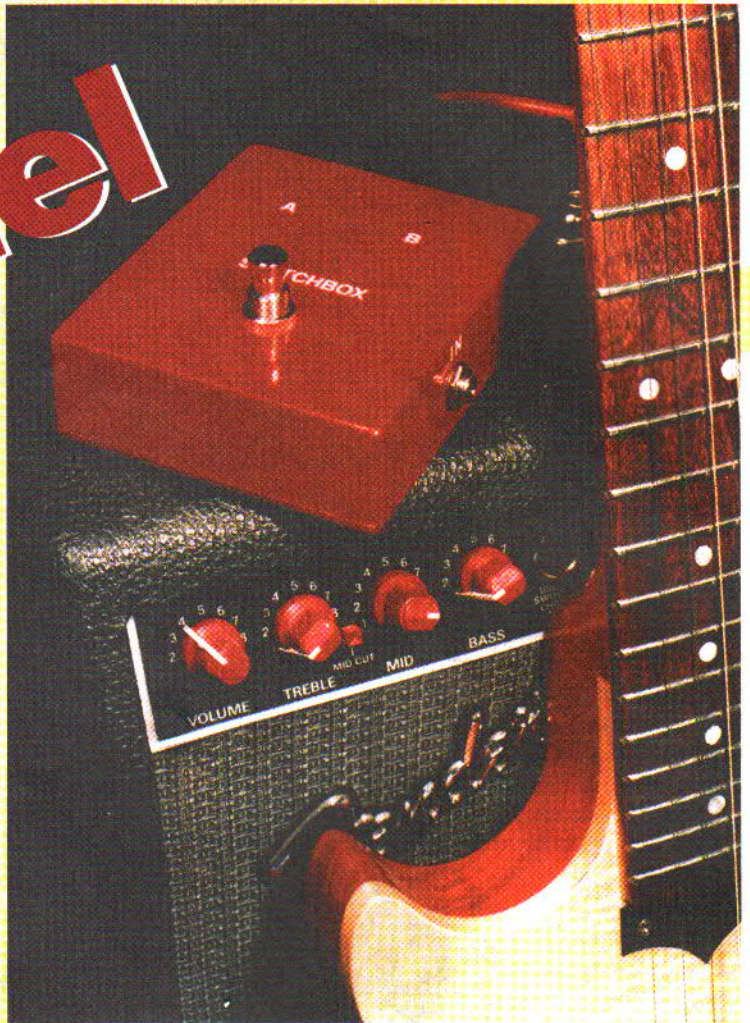

If you have those, can't get enough of those, channel switching blues! Then Daniel Coggins has the low noise medicine

**A** guitar A-B box is used to select different channels on a (basic) guitar amplifier in order to provide different sounds or volume levels, or indeed two separate

amplifiers or effects. I use it to switch channels on my old VOX AC30 - great sounding amps, but channel switching gives much more flexibility from these and other 'simple' amps. By simply

treading on a footswitch, it is possible to make the guitar louder with a different tone in an instant, which guitarists find irresistible! This design was developed out of frustration and disappointment


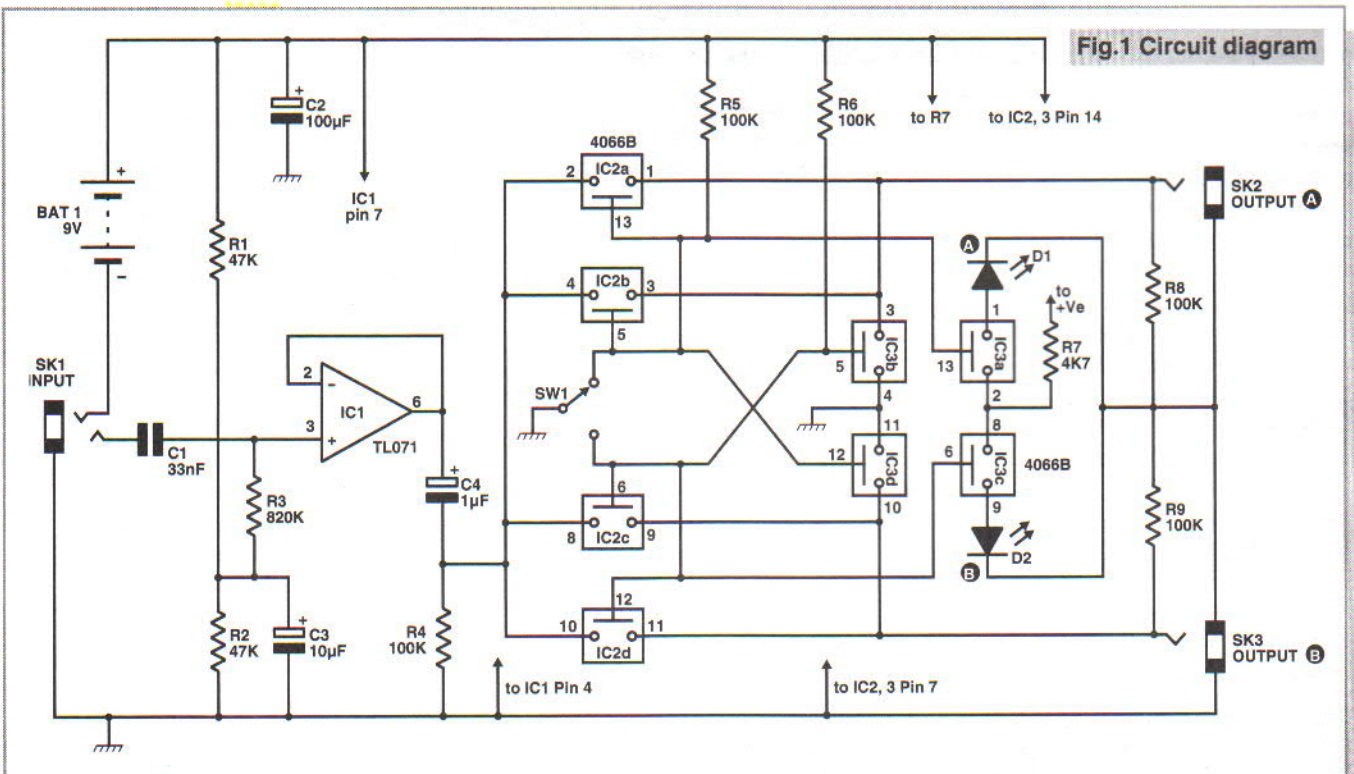


Fig.1 Circuit diagram

**Fig.2 Component positioning/interwiring and foil pattern**

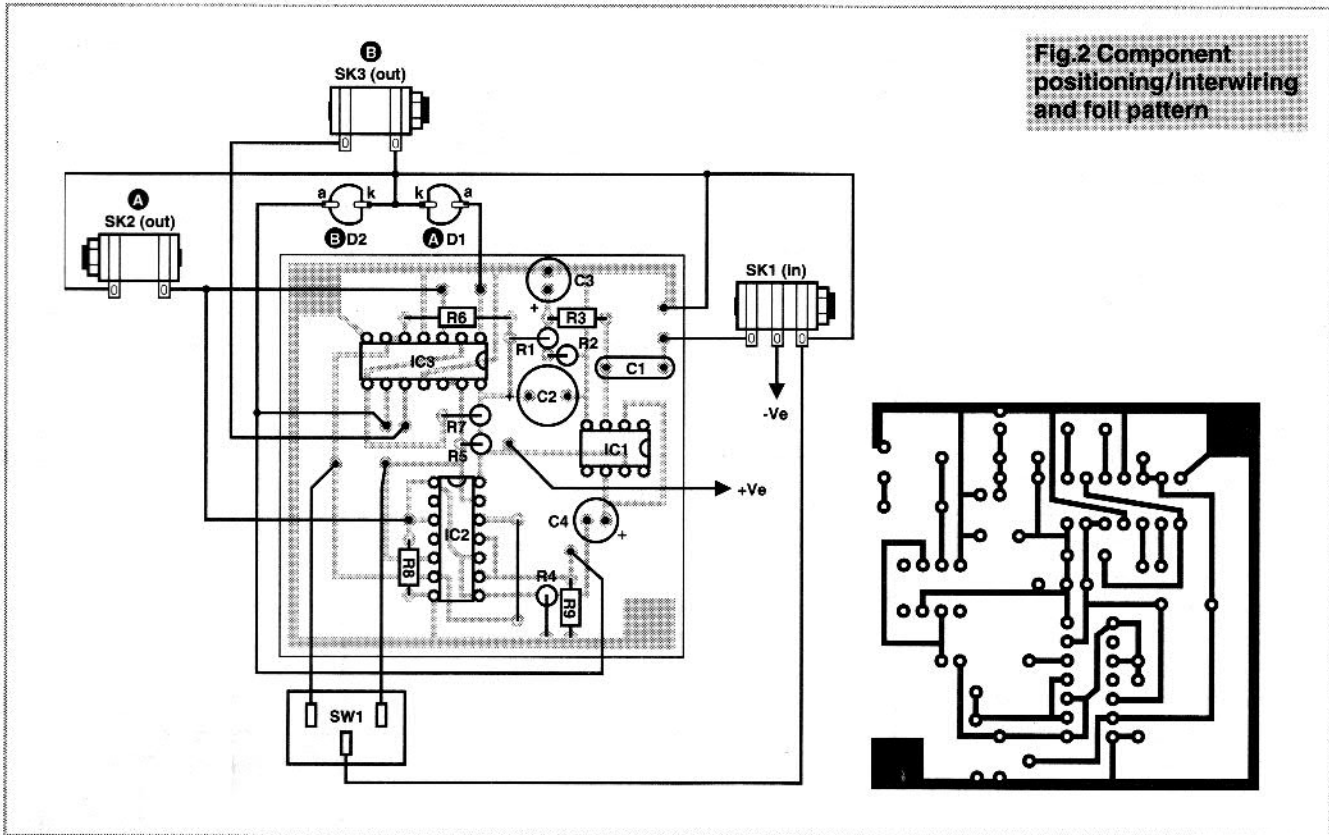

with a commercially available A-B box. Why disappointment? Well, in order to explain, the circumstances need to be examined.

Electric guitars generally produce low output signals with a high impedance that have to travel through long cables to what is effectively quite a high gain amplifier, with a high input impedance. This is an inherently inefficient system, because cable

capacitance causes significant treble loss, and even microphony (if it's really cheap). Also, hum pickup and RF breakthrough can result. But the problem that really emanates from the speaker is one of switching the signal on and off. Just unplugging a lead from an amplified guitar can result in hideous loud crackles - and a simple changeover switch will probably sound just as bad, especially as it wears.

This is normally heard as a loud, unpleasant crackle or thump and it could damage speakers, or at best result in extreme noise if followed by effects.

The unit I purchased overcame this by 'silencing' the signal as the changeover was made. This effectively masks the noise of the switch contacts, whose air gaps and resistance are made evident as noise. This method is very annoying in practice because the sound disappears

### The Works

The circuit is quite simple; on plugging in a jack to the input socket, the battery is connected to the rest of the circuit (so unplug this when not in use) and supplies the IC's and LED's. C2 decouples any glitches from the supply rail which might be heard at the outputs due to DC fluctuations.

R1 and R2 form a potential divider, to produce a half-supply rail, necessary to accommodate IC1.

IC1 is a TL071 low noise JFET op amp, ideal for this application where it is used to buffer the input signal. It is configured as a non-inverting voltage-follower, and the half-supply rail decoupled by C3 is fed to it through R3. This sets the input impedance to 820K, which will suit all guitar pickups and incur no loss of treble. C1 couples the guitar signal to IC1. C4 decouples the buffered signal, with a charging path provided by R4, to prevent any

thumps on switchover.

IC2 and IC3 are CMOS analogue switches. Their 'off' resistance is typically hundreds of megohms and with a 0-9V supply the 'on' resistance is about 120 ohms. In this design, I used the two 'spare' gates (IC2b and IC2c) to halve the 'on' resistance to 60 ohms for lower loss. The switches are turned on by putting a 'high' level (i.e. greater than half-supply voltage) on the control pin, and turned off by connecting the control pin to a low level (0V).

R5 and R6 are 'pull-up' resistors which hold all the control pins at a 'high' level, in turn switching 'on' all the switches. However, the footswitch (SW1) grounds certain control pins to pass the signal to one of two outputs and to prevent the signal going to the other socket. For instance, if we were to consider SW1 in the position illustrated in Figure 1:

Switches IC2a and IC2b are both

off, so the signal cannot pass to output 'A'. Also IC3a is 'off', so D1 will not light. IC3d is 'off', so the signal passing from C4 via IC2c and IC2d (both on - fed by R6) will reach output 'B'. This is indicated by D2, which is switched on by IC3c. Output 'A' is muted by IC3b. When SW1 is switched over, the opposite conditions exist, and the signal will emerge from output 'A'. Confused? Well, don't worry - it works, anyway.

R7's value was chosen to compromise between sufficient LED brightness and acceptable current consumption - approx. 3.7mA, which will give long life from a PP3 battery. R8 and R9 are used to prevent any excessive static charges from damaging the 4066's - should one of the output leads come into contact with some psychedelic guitarist's synthetic shirt or a Heavy Metal bassplayers spandex trousers.

completely for a second or so, and sounds to all the world like a bad tape drop-out.

Also, the offending unit had terrible hiss levels which meant that placing devices such as distortion pedals or compressors after it was out of the question. Why did I buy it in the first place, you ask? Good question, but I'm not naming the manufacturer!

## Design Considerations

So I set about designing my own A-B box. The most important thing was for it to be musically transparent; in other words, low noise and with minimal impairment of the instruments' tone. Obviously a purely mechanical switch is simple but noisy and dodgy, even. The best method is to use a mechanical footswitch to control an electronic one. There are hi-fi grade electronic switch ICs around but they are not cheap, and are probably of too high a quality for this application.

I settled for an array of CMOS analogue bilateral switches which cost pence rather than pounds, and still give good performance.

Some careful thought went into wiring these up to minimise their minor drawback of producing a small audible 'pop' as they open and close.

One low-noise op-amp is used to buffer the signal, as this eradicates further significant signal degradation from further cabling, and from the switches themselves. CMOS switches give better audio performance at lower impedances.

All this is enclosed in a sturdy low-profile die-cast box.

## The Signal Path

A signal from a musical source is fed into a buffer amplifier and subsequently directed to one of two outputs. This is achieved by controlling a series of electronic switches with a DC voltage selected by a mechanical footswitch. In either condition, the selected channel signal switch closes, along with a similar switch to power an LED.

Simultaneously, an extra switch mutes the unselected output socket to prevent noise or crosstalk escaping through it. When the footswitch is pressed again, the other channel is selected in exactly the same way.

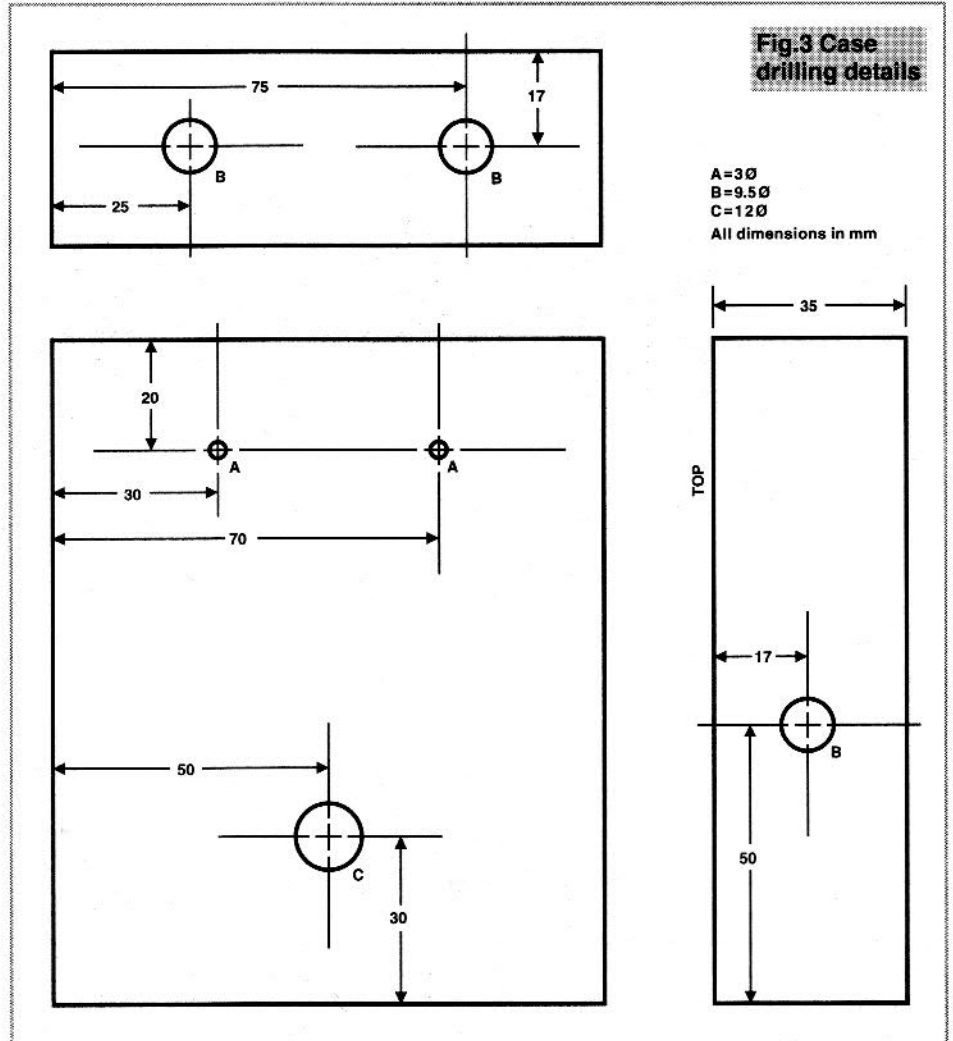


Fig.3 Case drilling details

## Construction Details

Referring to Figure 2, start with the PCB and solder in the resistors first, followed by the capacitors, making sure that you've put them in the correct way round. Take greater care with the ICs, especially the CMOS ones, that is to say, avoid charging yourself up before handling them, although 'B' suffix devices are supposedly quite robust with regard to static. If you want to be sensible, use some IC sockets - preferably the turned-pin variety, as they give a more reliable contact. Then if you are unlucky enough to destroy your chips (again, be sure to fit them correctly), it's a simple job to replace them. Be sure to fit the LED's with their correct polarity, for some reason I'm hopeless at identifying them.

Refer to Figure 3 for drilling details, making sure that all the parts fit their respective holes. The case will look more impressive if it is sprayed with some coloured car paint. Rub-down letters can then be used to label the LED's and sockets, and the unit given a name. Ever imaginative, I called mine 'A-B Switchbox'.

Fix the lettering with many coats of

clear lacquer otherwise the finish will soon deteriorate, believe me. Fit the sockets and footswitch and solder some wires to them (colour coding is invaluable here), and loom them separately, so that the footswitch doesn't interfere by means of stray capacitance. Use screened cable between the input socket and the PCB to further counteract this. Join the screen only at one end to avoid earth loops.

The LEDs can be pushed into the 3mm holes and then secured with a small blob of epoxy resin. Foam rubber is very good for supporting and insulating the PCB and preventing the battery from knocking around inside the case. I use this rather than bolts, purely for cosmetic reasons.

## Testing and use

Assuming that you have double-checked all your wiring and component orientation, the A-B BOX is ready for testing. Connect an ammeter (on mA range) between the case and the battery negative terminal. The reading should be no more than 3.7mA. If it differs greatly from this, then there is something wrong, so check things over again.

Assuming that you are luckier, and all reads well, plug your guitar/bass or keyboard into the input and press the footswitch several times to ensure that the LEDs are lighting and changing state. Select channel 'A' and connect your amplifier to output socket 'A'. The sound should emerge untainted from your amp.

Compare the sound here with that of your instrument going straight into the amp with a single, shorter lead - there should be little audible difference. Now press the footswitch - silence should result. Turn up the volume of your amp, and play some sounds - there should be no trace of it from the amp. Now turn the amp down and repeat the process for channel 'B'. If all is well, you can start to experiment with some applications of this gadget.

## In Use

Being a low noise device, the box shouldn't be too critical as to where it is placed in the signal path. But, the nearer it is to the guitar, the better the signal quality will be, because the cables, no matter how good they are, will have less loading effect on the signal, resulting in a clearer, stronger sound. However no audio processing unit is totally noise free, so try to avoid connecting it before a compressor as they tend to accentuate even the smallest amounts of noise. Why not experiment?

A great advantage of an A-B box is the fact that by splitting the signal to one of two paths you can have multiple effects pedals set differently in each path for rhythm/lead sounds. For example, channel 'A' could be designated the rhythm channel, and have an overdrive pedal connected after it with a soft tone setting, to connect to one channel of your amp.

The lead channel 'B' could have a different distortion pedal with a more

'biting' tone, followed by a digital delay line for echo. The obvious beauty of this is to reduce the complex 'tap-dancing' routine that most gadget-bound guitarists suffer from - and with an LED indicator to boot!

An obvious application would be to connect one channel to a high-powered amplifier for loud, clean sounds with the other channel connected to a lower powered valve amplifier turned up almost 'flat-out' for distorted sounds.

Another use would be to connect one output to your amp and the other to an electronic tuner, so that in performance situations the sound of a half-tuned guitar is not heard by the audience. One word of caution, though - the CMOS IC's employed in this design will start to distort (in a valve-like fashion) if the driving signal is too high. This is only likely to occur at line levels, and is one of the reasons that it is best suited to guitars, whose signal is around 30dB below line level. It is up to you to decide how critical this would be for your application.

## Food For Thought

As it stands this pedal is quite versatile, but with a little thought and application could be expanded or modified to perform many different applications, not necessarily involving guitars at all! Besides, this magazine is not a music magazine as such, but a vehicle for ideas, and I hope this article will not only be of use to the twangers, but of general technical interest.

Back to the possibilities - IC1 could introduce 6dB of gain by disconnecting pin 2 from pin 6 and connecting a 100K resistor in between, with another 100K resistor connected between pin 2 and the half-supply rail (C3 positive). The A-B Box will then substantially boost the signal. If it is too much then R8 and R9

all 1/4W 5% carbon

R1,2 47K

R3 820K

R4,5,6,8,9 100K

R7 4K7

## Parts

C1 33n Mylar

C2 100µ/16V radial electrolytic

C3 10µ/16V " "

C4 1µ/16V " "

### Semiconductors

IC1 TL071 low noise

JFET op-amp

IC2,3 4066B CMOS analogue quad bilateral switches

D1 3mm red LED

low current preferable

D2 3mm green LED

low current preferable

### Additional items

SW1 SPDT Heavy duty footswitch (Maplin)

PCB (See page 57)

IC sockets (1 x 8 PIN, 2 x 14-PIN)

PP3 9-V Battery and clip

Diecast case 120 x 100 x 35mm (RS/Electromail Cat No 225-209)

Stereo 1/4" Jack socket

Mono 1/4" Jack socket (2 OFF)


Screened lead

wire


solder

Rub-down letters

spray paint

can be replaced with 100K log pots, with the wipers connected to the output sockets, to adjust drive levels. A second op-amp, wired as a mixer/summing amplifier could combine both outputs as a single channel, resulting in a rather useful booster pedal. 

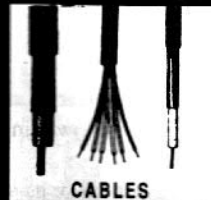**Call us now! We have the widest range of components available - At competitive prices!**



CABLES




CAPACITORS



VIDEO HEADS



SPEAKERS

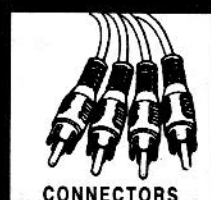

CONNECTORS



ESPECIALLY JAPANESE SEMICONDUCTORS

**CRICKLEWOOD**

ELECTRONICS

Cricklewood Electronics Ltd, 40 Cricklewood Broadway, London NW2 3ET  
Telephone: 081 452 0161 Faxsimile: 081 208 1441

All Major Credit Cards Accepted



## April

### TV Screen control

There are various ways to initiate commands using a TV screen, a mouse or roller ball are the standard ones. Not so standard, but also in use are cordless joystick controls using infrared beams and also Touch screens. This last one has excellent applications where the general public are involved and it is quick to operate but the smallest area in which to take action is typically thumbprint size. However, there could be other fast response ways to initiate more accurate commands.

Solid state LASER pencil to point and activate areas on the screen. As the spot is easily seen, it would be ideal for speedy operations in computer games and CDi. As we all tend to use our fingers for pointing at things, the unit might be portable enough to be strapped onto the back of the finger.

### A good sniff


With IBM developing the 'nose on a chip', (see news item) there must be many applications where minuscule changes in temperature could alert warnings ie. body surface temperature changes. On this basis, it could be an excellent detector for some Biofeedback techniques like controlling headaches.

### Level Detection

Most level detectors monitor rises in liquid levels and usually rely on marked changes in resistance owing to ions present. Those who rely on oil (kerosene) for heating often run out of this organic liquid at the worst possible time without warning. There must be a simple solution to this problem.
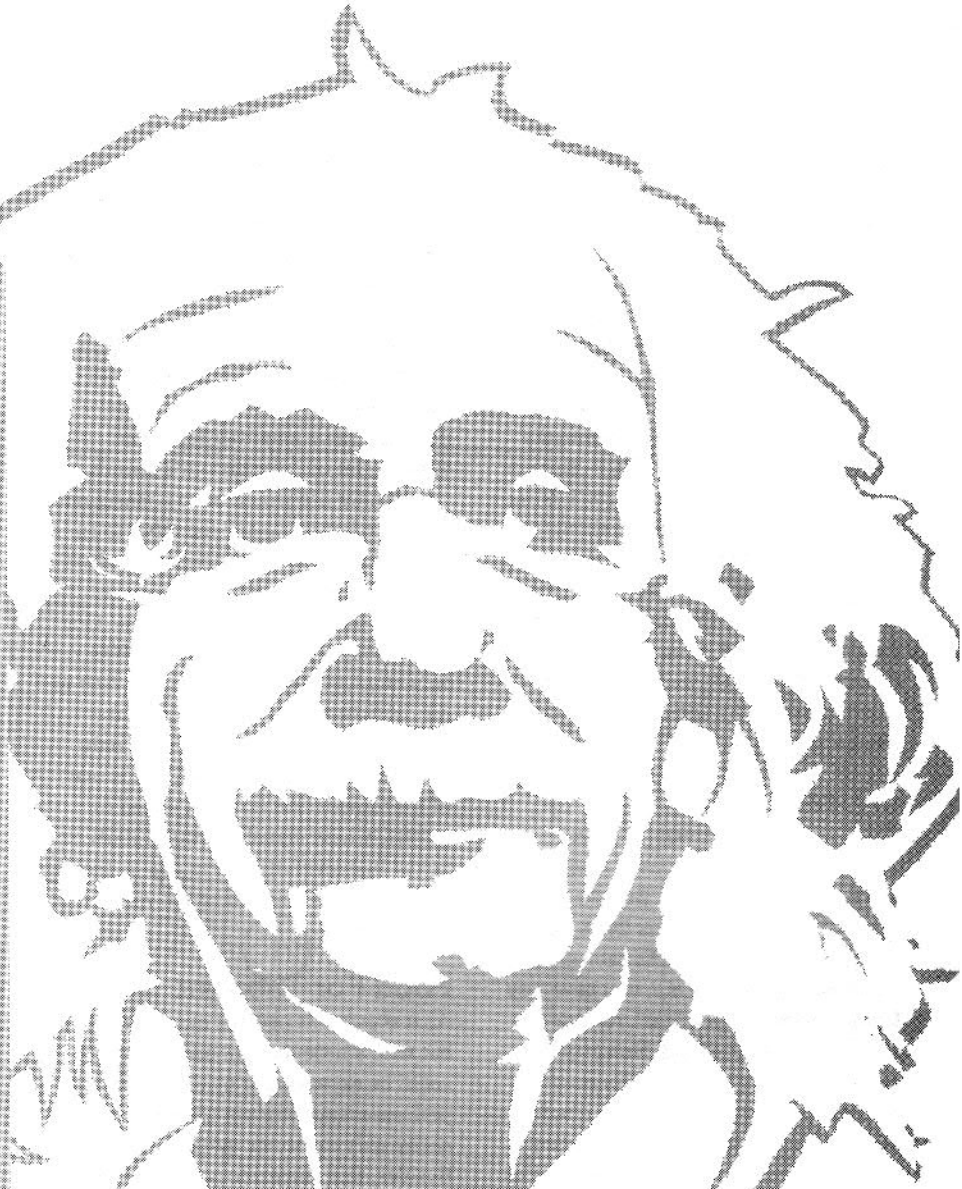
### Weather Sense

The air we breath contains positive and negative ions. The negative ones are said to make you feel good. It would be interesting to know the ion concentration and polarity at any time.



# Ideas Forum

## The page to get you thinking about what to develop next

**I**deas never come easy do they? Some say that talking to a like minded person will bring out the best in you. The more you talk, the greater the chance that an idea will come out in conversation. Also to some it depends on what the weather is like or how much sleep you have had the previous night

All great inventions start as little notions that get scribbled down and expanded upon, and that's what the Electronics in Action Ideas Forum is all

about. Now you are the inventors.

Whatever happened to the 'Beta lights' commonly used in the 60s. on the end of flick switches. Those radioactive lights were not by any means new, having previously been used to illuminate dials in aircraft cockpits during the war. Could this natural energy be converted to light, heat or any other form to save on battery power in portable equipment.

If you have any suggestions or have developed any of the ideas that have been appearing in this column we would love to hear from you, feel free to drop us a line. **Electronics in Action, PO Box 600, Berkhamsted Herts. HP4 1NL**



# At Your Service

**S**o you don't fancy messing up your best measuring jug with Ferric Chloride, but you still want to make some of our projects properly - with a PCB? This is where we step in. At Electronics in Action we can offer, at very reasonable prices, PCBs for all of our featured projects.

Just select which PCBs you require, fill in the coupon and post it to us with a cheque or postal order (for the full amount) made payable to **Electronics in Action**.

The coupon lists all the projects featured in the last four issues and anything older than that is listed below. We have left some blank spaces on the coupon should you wish to order an older PCB.

## December Issue

QH1293-1	
Guitar Tremolo .....	£5.00
QH1293-2	
Switcher main board .....	£10.00
QH1293-3	
Switcher Front panel .....	£6.00
QH1293-4	
Video Editing Unit .....	£8.00

## November Issue

QH1193-1	
Power Supply (double sided) ..	£6.00
QH1193-2	
Telescope Input board .....	£5.50
QH1193-3	
Drainpipe Seismometer .....	£5.50

## October Issue

QH1093-1	
Telescope Main Board .....	£12.00
QH1093-2	
Hi-fi Preamp .....	£4.50
QH1093-3	
Laser Zone .....	£5.00
QH1093-4	
Anti-howler (double sided) .....	£5.50
QH1093-5	
Sig Gen board .....	£4.50
QH1093-6	
Crossover unit .....	£3.00

Please print your name and address in **BLOCK CAPITALS**

Name .....

Address .....

Postcode .....

Send the completed coupon (include 80p for postage and packing) to:

**At Your Service, Electronics in Action**  
**PO Box 600, Berkhamsted, Herts. HP4 1NL**

Please enter amount required in appropriate box

<input type="checkbox"/>	QH0493-1	5-Band Graphic Equaliser .....	£5.00
<input type="checkbox"/>	QH0493-2	8-channel PC Data logger .....	£7.50
<input type="checkbox"/>	QH0493-3	Guitar A/B switchbox .....	£5.00
<input type="checkbox"/>	QH0493-4	Deionised water level detector .....	£5.00
<input type="checkbox"/>	QH0493-5	Simple Intercom .....	£5.00

## March Issue

<input type="checkbox"/>	QH0394-1	Testcard Generator .....	£7.00
<input type="checkbox"/>	QH0394-2	Guitar Transmitter (double sided) .....	£8.00
<input type="checkbox"/>	QH0394-3	Mains Checker .....	£5.00

## February Issue

<input type="checkbox"/>	QH0294-1	Hatchery Controller .....	£8.00
<input type="checkbox"/>	QH0294-2	12V drill speed controller .....	£5.00
<input type="checkbox"/>	QH0294-3	The Switcher IR transmitter .....	£5.50
<input type="checkbox"/>	QH0294-4	The Switcher IR receiver .....	£3.50
<input type="checkbox"/>	QH0294-5	The Switcher VCA board .....	£7.50

## January Issue

<input type="checkbox"/>	QH0194-1	The Harmoniser (2 boards) .....	£10.00
<input type="checkbox"/>	QH0194-2	Power Amplifier (double sided) .....	£7.00
<input type="checkbox"/>	QH0194-3	Remote Control Extender .....	£5.00

<input type="checkbox"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>
<input type="checkbox"/>	<input type="text"/>	<input type="text"/>	<input type="text"/>


Total remittance including P&P £

Allow 28 days for delivery

## ADVERTISERS' INDEX

BK Electronics .....	21	Halcyon Electronics .....	58
Baylin Publications .....	58	Hart Electronics .....	28
J & N Bull .....	35	J.D. Photo-Tools .....	34
Chelmer Valve Company .....	34	JPG Electronics .....	58
Circuit Distribution Ltd. ....	OBC	Labcenter Electronics .....	46
Cooke International .....	25	Mauritron Publications .....	39
Cricklewood Electronics Ltd. ....	55	MQP Electronics Ltd. ....	58
Delcia .....	25	Roline Systems Ltd. ....	59
European Computer Marketing (UK) ..	41	Stewart of Reading .....	34
Express Components .....	47	Tsien (UK) Ltd .....	40

# SYSTEM 200 DEVICE PROGRAMMER

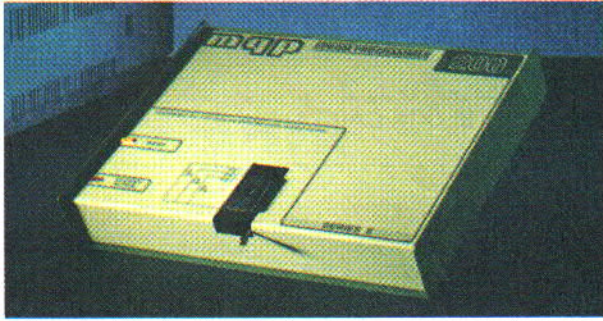

**SYSTEM:** Programs 24,28,32 pin EPROMs, EEPROMs, FLASH Memories and EPROM Emulators as standard, quickly, reliably and at low cost. Expandable to cover virtually any programmable part including serial EEPROMs, PALs, GALs, EPLDs and microcontrollers, in many different packages.

**DESIGN:** Not a plug-in card but connecting to the PC serial or parallel port; it comes complete with powerful yet easy to use software, cable and manual.

**SUPPORT:** UK design, manufacture and support. Same day dispatch, 12 month warranty. 10 day money back guarantee.

**ASK FOR FREE INFORMATION PACK**



**MQP ELECTRONICS Ltd**  
Park Road Centre  
Malmesbury, Wiltshire SN16 0BX. UK  
Tel: 0666 825146 Fax: 0666 825141

GERMANY 089/4602071  
NORWAY 0702-17890  
SWEDEN 8 590 754 04  
ITALY 02 92 10 35 54  
FRANCE 1 69 30 13 79  
Also from VEROSPEED UK

# THE DEFINITIVE 'OFF-AIR' FREQUENCY STANDARD



Still only  
**£195. +VAT**  
carriage extra

- \*Provides 10MHz, 5MHz & 1MHz
- \*Use it for calibrating equipment that relies on quartz crystals, TCXOs, VCXOs, oven crystals
- \*Phase locks to DROITWICH (rubidium controlled and traceable to NPL)
- \*For ADDED VALUE also phase locks to ALLOUIS (caesium controlled and traceable to OP - French equivalent to NPL)
- \*British designed and British manufactured
- \*Sine wave option of 10, 5 and 1MHz. Nominal 1V into 50 ohm
- \*13MHz option for G.S.M.

Output frequencies:  
10MHz, 5MHz, 1MHz  
Short term stability: better than  $1 \times 10^{-8}$  (1sec)  
Typical: =  $4 \times 10^{-8}$  (1sec)  
Long term: Tends to  $2 \times 10^{-8}$  (1000Sec)

IDEAL BEGINNERS SCOPE. SCOPEX 4S6/AQUILASCOPE 6MHz SINGLE TRACE, INT/EXT TRIG, TRACE LOCATE, BRIGHT LINE AUTO, 10mv SENSITIVITY, 1µs-ms/cm, etc. £95

AVO 8's Mk 2.5.6	FROM £55	LEADER LC6386 NTSC COL. PATT. GEN.	£393
PHILIPS PM3232 10MHz DUAL TRACE	£185	UD12026 SONAR SCANNER, SURFACE UNIT	£975
TELEQUIPMENT D67 25MHz DUAL TRACE, DEL T/B	£195	TEK 834 PROG. DATA COMMS. TESTER	£295
GOULD OS255 15MHz DUAL TRACE	£195	1" RACK, 20U, 31" DEEP	£99
TELEQUIPMENT D61A 10MHz DUAL TRACE	FROM £99	TSEG 12" x 9" DISPLAYS DIGITEX/SIGNAL EX	£15 & £10
TELEQUIPMENT S62 SINGLE TRACE 5MHz SCOPE	£95	RADIOMETER BK66 DIST. METER 20Hz-20KHz	£95
IWATSU SS5116 DUAL TRACE 10MHz	£175	RADIOMETER AFM2 MOD. METER 7MHz-16Hz	POA
TELEQUIPMENT D1011 10MHz DUAL TRACE	£165	UPS MICROPAK SX250 250W	£135
TEKTRONIX 2215 60MHz DUAL TRACE DEL T/B	£450	CITOH CX6000 6PEN A4 PLOTTER, CENT/RS232	£135
TEKTRONIX 453A 50MHz DUAL TRACE DEL T/B	£249	GENERAL RADIO 1531A XENON STROBOTAC	£79
H.P. 8405A VECTOR V-METER 1GHz	£395	BACHARACH MV2 MERCURY SNIFTERS	£89
PLESSEY TCT10 SIG GEN/ANAL 50-300 BDS	£395	FISONS FI-MONITORS LIQ LEVEL SENSORS	£85
TEK 465B 100MHz DUAL TRACE DEL T/B	£475	JAQUET TIMER 110secs RES'N 0.01s	£59
TELEQUIPMENT D67A 25MHz 2T, DEL T/B	£215	COMMODORE PETS. D/DRIVES, PRINTERS	£29 & £49
HITACHI VC 6015 10MHz DIGITAL STORAGE	£295	COMARC 2303 MV SOURCES, DUAL RANGE	£49
HP134DA X-Y DISPLAYS	£149	INTRON IF5422 FUNC. GEN. 0.1Hz-2MHz	£125
OERTLING V20 SINGLE PAN BAL. 0.1mg/200g	£69	ECG MONITOR SEM400 WITH SEM420Z	£75
ANALYTICAL BALANCES WITH WEIGHS 250g	£69	GOULD 2400 4PEN CHART RECORDER	£149
VACUUM PUMPS 1.5 & 2.8m <sup>3</sup> /hr	£125 & £149	X-Y PLOTTERS A3 & A4	FROM £35 TO £199
KINGSHILL NS1540 15V 40A PSUs CASED, AS NEW	£195	PHILIPS PM6456 FM STEREO GENERATOR	£135
ACRON 402P SYNC PULSE GENERATOR & 60SP ENCODER	£375 & £695/pr	MARCONI TF2300 FM/AM MODULATION METER	£195
MARCONI TF2304 AM/FM MOD METER PORTABLE	£249	MCKENZIE 7DAY TEMP/HUMIDITY RECORDER	£95
MARCONI TF2330 WAVE ANALYSER 20Hz-50KHz	£149	FEEDBACK S5060 1MHz SINE/SQUARE OSC	£125
H.P.5315A 1GHz F/CTR, OPTS 1.2 & 3	£595	FARNELL E350 0-350V 100mA, 2 x 6.3V	£59 TO £69
LEVELL TM68 MICRO V-METER 450MHz	£85	COMMUNICATIONS RECEIVERS, HF/LF/VHF	POA
LEVELL TM38 MICRO V-METER 3MHz	£85	LGR MARCONI TF1313 0.25% RATIO	£95
		LGR COMPONENT COMPARATOR AVO C2457/S	£95

LIST AVAILABLE BUT 1000'S OF UNLISTED BARGAINS FOR CALLERS. ALL PRICES EXC. OF P & P AND VAT QUALITY ELECTRONIC EQUIPMENT ALWAYS WANTED




**HALCYON ELECTRONICS**



423, KINGSTON ROAD, WIMBLDON CHASE, LONDON SW20 8JR  
SHOP HOURS 9-5.30 MON-SAT. TEL 081-542 6383. FAX 081-542 0340
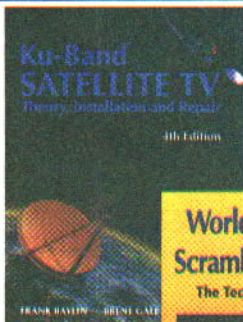
# Baylin Publications

**ALL ITEMS EX-STOCK.**  
Ku Band Satellite TV, Theory, Installation & Repair 4th Edition. Footprints, dish theory, cables, site survey, polar mount adjustment.  
**£25.**



**European Scrambling Systems, Circuits, Tactics & Techniques.** By John McCormac, digital sound, smart cards, pirate decoders, for hackers.  
**£32.**

**World Satellite TV & Scrambling Methods.** 2nd Edition, by Baylin, Madox & McCormac for the service engineer.  
**£29.**

**Home Satellite TV Installation Videotape.** Forty minutes VHS Pal. See how 3 metre dishes are installed.  
**£27.**

**Satellite Installation Guide.** 3rd Edition. By John Breeds.  
**£13.**

**The Satellite Book.** 2nd Edition. A complete guide to satellite TV. Theory and practice by John Breeds.  
**£31.**

**World Satellite Almanac.** 3rd Edition by Mark Long. 300 Footprints, Frequencies, Transponder Loading, Orbital Assignments.  
**£69.**

**World Satellite Annual.** Update by Mark Long.  
**£39.**

**TVRO System Analysis and Aiming Software.** 5.25 or 3.5 disk, (DOS 3.2). Calculates dish size and lists coordinates of all satellites in view.  
**£39.**

**Satellite Toolbox Software.** for IBM Comp. Hard Disk - 5.25 or 3.5.  
**£59.**


**Wireless, Cable & SMATV.** Microwave broadcasting & cable TV.  
**£35.**

**World Satellite Yearly** by Dr. Baylin, Loading and 200 Footprints.  
**£38.**

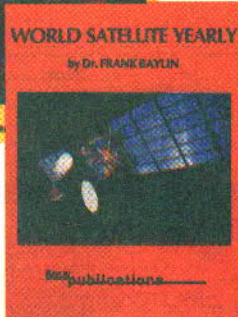**PRICES INCLUDE P. & P. UK. Airmail Europe add 10%. Outside Europe +20%.**


24 River Gardens,  
Purley, Reading.  
RG8 8BX. England.  
Tel/Fax 0734-414468  
Mobile 0836-582785

Pay by: UK £ cheque,  
Access, Mastercard,  
Visa, C.O.D.




Inverter-toroidal transformers 225VA 10.5-0-10.5 primary 0-260-285 secondary	£29.95	200mA at 300v input to output isolation with data	£4.95 each or pack of 10 £39.50
LEDs 3mm or 5mm red or green	6p each	Hour counter used 7 digit 240v ac 50 Hz	£1.45
High intensity red, green or yellow 5mm	11p each	QWERTY keyboard 58 key good quality switches new	£5.00
Cable ties 1p each	£5.95 per 1000	Airpax A82903-C large stepping motor 14x 7.5' step 270hm 68mm dia body 6.3mm shaft	£8.95 or £200.00 for a box of 30
High quality photo resist copper clad epoxy glass boards		0.9uf 250vdc 18p each 14p 100+ 9p 1000+	
Dimensions	single sided	1uf 250vdc 20p each 15p 100+ 10p 1000+	
3x4 inches	£1.09	2.2uf 250vdc (27.5mm pitch) 30p each 20p 100+ 15p 1000+	
4x8 inches	£2.75	3.3uf 100vdc 30p each 20p 100+ 15p 1000+	
6x12 inches	£6.20	1uf 50v bipolar electrolytic axial leads	15p each
12x12 inches	£12.25	7.5p 1000+	
<b>Rechargeable Batteries</b>		0.22uf 250v polyester axial leads 15p each 7.5p 100+	
AA (HP7) 500mAh	£0.99	Polypropylene 1uf 400vdc (Wilma MKP10) 27.5mm pitch 32x29x17mm case	75p each 60p 100+
AA 500mAh with solder tags	£1.55	<b>Phillips 123 series</b> solid aluminium axial leads	
AA 700mAh	£1.75	33uf 10v & 2.2uf 40v 40p each 25p 100+	
C (HP11) 1.8Ah	£2.20	<b>Phillips 108 series</b> 22uf 63v axial 30p each 15p 1000+	
C 2Ah with solder tags	£3.60	Multilayer AVX ceramic capacitors all 5mm pitch 100v	
D (HP2) 1.2Ah	£2.60	100pf, 150pf, 220pf, 10.000pf (10n) 10p each 5p 100+	
D 4Ah with solder tags	£4.95	3.5p 1000+ 500pf compression trimmer 60p	
PP3 8.4V 110mAh	£4.95	40uf 370vdc motor start capacitor (dielectric type containing no pcb) £5.95 or £49.50 for 10	
1/2A with solder tags	£1.55	<b>Welwyn W23 9W</b> 120ohm 35p each 20p 100+	
Sub C with solder tags	£2.50	680 ohm 2W metal film resistor 4p 100+ 2p 1000+	
AAA (HP16) 180mAh	£1.75	500 ohm carbon resistors very low inductance ideal for RF circuits 270hm 2W, 680hm 2W 25p each 15p each 100+	
1/3 AA with tags (phlipsCTV)	£1.95	we have a range of 0.25w 0.5w 1w and 2w solid carbon resistors please send SAE for list	
<b>Standard charger</b> charges 4 AA cells in 5 hours or 4Cs or Ds in 12-14 hours-1xPP3(1,2,3or4 cells may be charged at a time)	£5.95	<b>P.C. 400W PSU</b> (Intel part 201035-001) with standard motherboard and 5 disk drive connectors fan and mains inlet/outlet connectors on back and switch on the side (top for tower case) dims 21x214x149mm excluding switch	£26.00 each £138.00 for 6
<b>High power charger</b> as above but charges the Cs and Ds in 5 hours AAs Cs and Ds must be charged in 2s or 4s	£10.95	<b>MX180 Digital multimeter</b> 17 ranges 1000vdc 750vac 2Mohm 200mA transistor Hfe 9v and 1.5v battery test	£12.95
<b>Nickel Metal Hydride AA cells</b> high capacity with no memory. 1000mAh	£3.85	AMD 27256-3 Eproms	£2.00 each, 1.25 100-DIP switch 3PCO 12 pin (ERG SDC-3-023) 60p each
1200mAh	£4.40	40p 100+ Disk drive boxes for 5.25 disk drive with room for a power supply light grey plastic 67x268x247mm	£7.95 or £49.50 for 10
<b>Special offers please check for availability</b>		Hand held ultrasonic remote control	£3.95
F cells 32dia x 87mm	£3.95	CV2466 gas relay 30 x 10mm dia with 3 wire terminals will also work as a neon light	20p each or £7.50 per 100
F cell with solder tags 1.2v	£4.30	A23 12v battery for car alarms or lighters	75p each
42x 16mm dia 1.2v	£1.45		£50.00 per 100
Stick of 4 171mmx16mm dia with red & black leads 4.8v	£5.95	All products advertised are new and unused unless otherwise stated. Wide range of CMOS TTL 74HC 74F Linear Transistors Kits. Rechargeable batteries capacitors tools etc always in stock.	
<b>Computer grade capacitors</b> with screw terminals		Please add £1.95 towards P&P VAT included in all prices	
38000uf 20v	£2.50		
88000uf 15v	£2.95		
58000uf 60v	£4.95		
<b>Tegment</b> common anode led display 12mm	£0.45		
LM2931AT5.0 low drop out 5v regulator	£0.85		
T0220 package	£0.85		
7812 and 7912 12v 1A regulators	£26.00 per 100		
LM337K TO3 case variable regulator	£1.95		
	£1.44 100+		
GAAs FET low leakage current S8873	£12.95 each		
B5250 P channel mosfet	£0.45		
BC559 transistor	£3.95 per 100		
74LS05 hex inverter	£10.00 per 100		
used 8748 Microcontroller	£3.50		
SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet	£1.95		
AM27502	1.25 each 90p 100+		
CD4007UB	10p 100+ 6p 1000+		
Sinclair light gun terminated with a jack plug and PP3 clip gives a signal when pointed at 50Hz flickering light with output wave form chart	£ 3.95		
DC-DC converter Reliability model V12P5 12v in 5v			

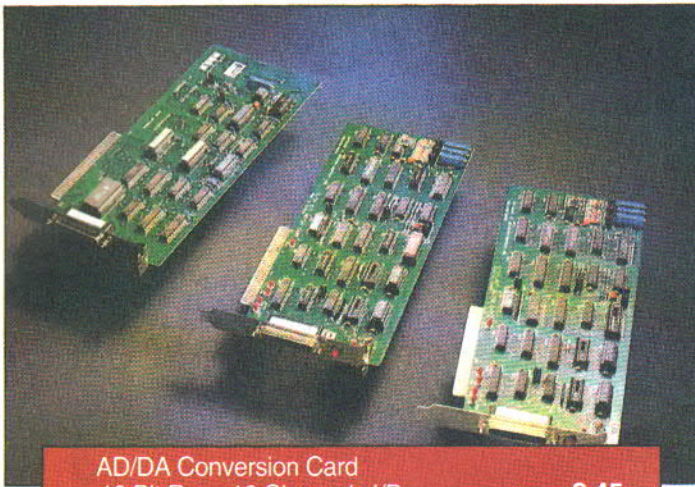**JPG ELECTRONICS**  
276-278 Chatsworth Road  
Chesterfield S40 2BH  
Access/Visa Orders  
(0246) 211202



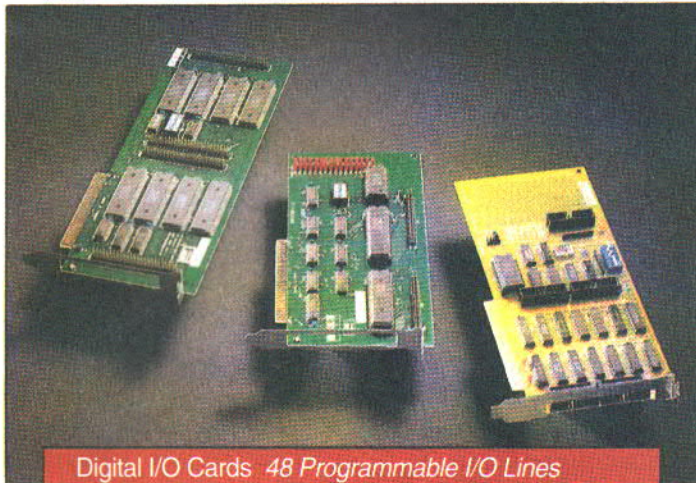
AD/DA Conversion Card  
12 Bit Res, 16 Channels I/P  
From £ 45




Digital I/O Cards 48 Programmable I/O Lines  
(3 Independent 16 Bit Counters)  
From £ 23



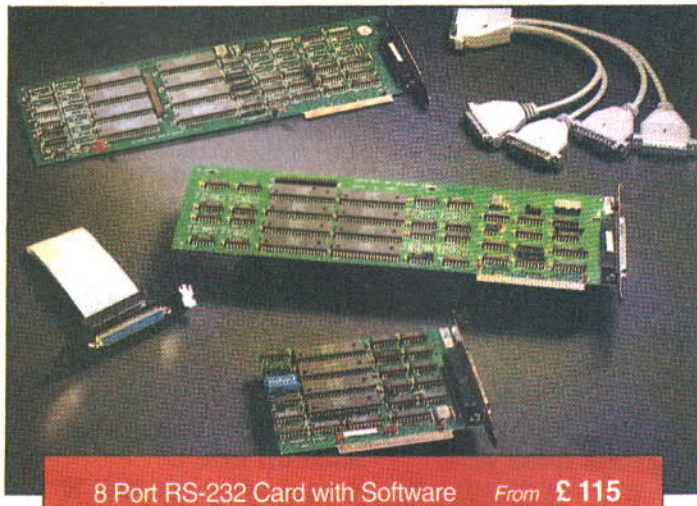Voice Communications Card  
Intelligent Telephone Card  
From £ 175



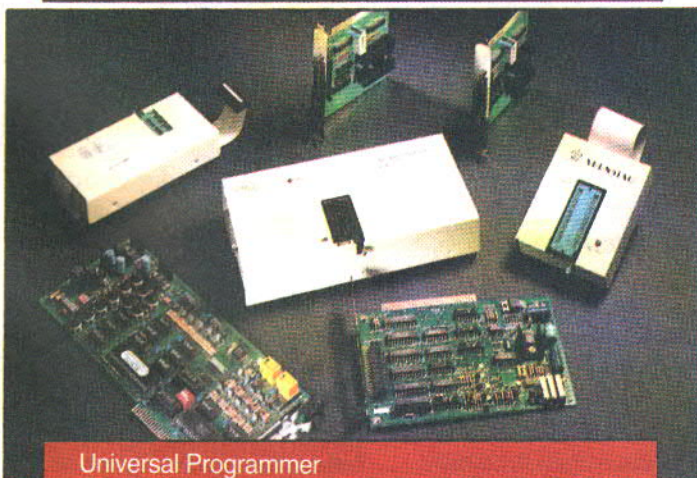8 Port RS-232 Card with Software  
From £ 115



Universal Programmer  
(A11-3A)  
From £ 395

## PC Based Industrial and Lab, Data Acquisition, Control and Measurement, Instrument Cards

- |                             |                          |
|-----------------------------|--------------------------|
| AD/DA Cards                 | Interface Converters     |
| Plus Accessories & Software | Relay Output Cards       |
| C.P.U. Boards               | RS 232 Cards             |
| Device Programmers          | Single, 2, 4, 8, 16 Port |
| Digital I/O Cards           | RS 422 Cards             |
| IEEE 488 Cards              | Single, 2, 4, 8, Port    |
| Industrial Chassis          | PC ROM Disk Cards        |
| Industrial Control Cards    | Slot Extender Cards      |

## Specialist PC & Multimedia Add-on Cards

- PC - Telecommunication Cards
- Fax Modem Cards
- Voice Recognition Cards
- Voice Digitiser Cards
- Video/TV - PC - Video/TV Cards
- Sound Cards



## Components

- |                    |                        |
|--------------------|------------------------|
| Cases              | Monitors               |
| Floppy Disk Drives | Mother Boards          |
| Hard Disk Drives   | Cache Controller Cards |
| From 40MB to 2.1GB | Network Cards          |
| Keyboards          | Tape Back Up Units     |

For further information, Product/Price List

Call Us On:

**Tel: 0902 20267 Fax: 0902 28439**

**Roline Systems Ltd, Imex House,  
Imex Business Park, Upper Villiers Street,  
Wolverhampton, West Midlands. WV2 4NU**

# Technoshop

Bringing the world closer together

**E**lectronics in Action in co-operation with The Technology Exchange Ltd., the international technology matchmaking service based in the UK, brings you each month a selection of technology partnership opportunities to which you are invited to respond.

The Technology Exchange, which was formed in 1985 as a not-for-profit technology sourcing service to industry, holds a biannual 'Technoshop' Technology Transfer Fair at Heathrow Airport and several 'Techmart' Fairs overseas for the United Nations (UNIDO).

For this issue of Electronics in Action, we are presenting a series of offers of licence, joint venture and patents rights for sale from organisations in 34 countries.

If you would like to have an introduction to any of the sources of the offers describes in these profiles, please write to The Technology Exchange quoting the reference number at the head of the entry and giving full contact details for the contact person in your own organisation and your requirements for a new product or process development.

The only cost associated with this process is a simple £10 plus VAT introduction fee for each entry to which you respond. For this we will send you full contact details for the source of the offer and invite them to send you more detailed information about their offer.

The code letters at the head of each offer indicate the stage of development, type of offer and the type of organisation making the offer as indicated in the table

Each entry is preceded by a reference number and letters indicating STATUS, OFFER and SOURCE.

Please respond directly to:

**The Technology Exchange Ltd.**  
**Wrest Park**  
**Silsoe**  
**Bedford**  
**MK45 4HS**  
**or Fax: 0525 860664**  
**Phone: 0525 860333**

The payment of £10 plus VAT (£11.75) per item should be sent with your requests.

**KEY**

Example: S O L S U

Status Offer Source

Status: indicates the stage of development.

<b>P</b> Patent or design only	<b>M</b> Laboratory model	<b>W</b> Working prototype
<b>U</b> Pre-production units available	<b>F</b> In current production	<b>C</b> Commercialised

Offer: indicates the type of agreement sought.

<b>L</b> Manufacture under licence	<b>S</b> Design and/or patent for sale	<b>J</b> Joint venture offer
------------------------------------	--	------------------------------

Source: indicates the type of organisation making the offer.

<b>C</b> Limited Company	<b>E</b> Educational Institution	<b>R</b> Independent Research Organisation
<b>G</b> Government Research	<b>P</b> Private Individual	

## 210061 M L U Metal Insulator Semiconductor - Field Effect Transistor using Germaniumnitride

the fabrication of self-aligned planar metal-insulator-semiconductor transistors on indium phosphide compound semiconductor. A new insulating material germanium nitride has been developed for use in the fabrication process of the transistor. Used for very high frequency (40-100 GHz), high power (3-6 W/mm), and high gain (5-15 dB) and high efficiency (40-50% microelectronics devices and circuits and very low noise/high power amplifiers for applications in photonics (optoelectronics).

## 708843 M S U Parametric Oscillator formed with a multiple quantum well optical wave guide

Miniature semi-conductor device with power levels comparable to laser diodes, narrow linewidth, and wavelength electrically tunable from 0.9 to 10 microns. Compact: low cost: continuous output radiation: no cooling required.

## 409812 W L U Manufacturing battery operated devices

need a variety of electronic components to function. Reducing the number of components occupying premium circuit board space is a key to manufacturing cost effective products. A device have been developed that reduces the number

of components required in battery operated products. The elimination of these components on the circuit board produces a major cost savings in the manufacturing process, while still maintaining the quality of the product.

## 508842 M S U New family Cuprate Superconductors with high TC

Critical current densities greater than  $35 \times 10^{+7}$  amp/sq cm at 132 degrees K in a 4KOe field.

## 208841 M S U High resolution wideband guided wave optical analog-to-digital convertor

Based on a new algorithm. Enhanced frequency range.

## 608968 W L C Halogen ceiling light 'SKY 10'

150 W ceiling light equipped with three low voltage 50W halogen light spots fitted with dichroic bulbs; 38 degrees adjustable spots. Ceiling light in steel - aluminium, spots of plastic material. Safety transformer. Fused. Intensive lighting.


## 708969 W L C ION implantation

For production of electronic components, clean room ion implantation service. Energy from 5KeV to 6MeV. Dose: 1E11 to 1E18 At/sq m -

Continued on page 62

Another  
Exclusive  
Reader  
offer from  
**Cirkit**

# PIR ALARM KIT

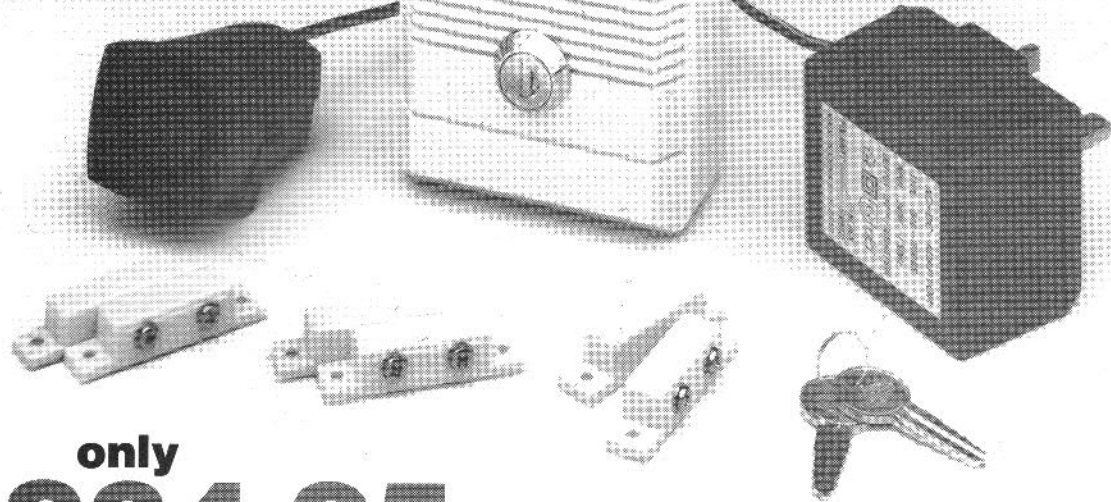

only  
**£34.95** (Usual price - £45.48)

**T**o combat the worrying trend of increasing numbers of burglaries and thefts, Cirkit have introduced a simple to install but very effective intruder alarm. It is ideal for club houses, sheds, garages, shacks or single room installations as well as caravans, trailers or boats.

The alarm combines a PIR (Passive Infra Red) detector for general coverage with magnetic switches for additional door and window protection. It is easy to use with a single key for set or reset, has a mains power supply, optional battery back-up and operates with a 2½ minute exit time and 15 second entry delay.

The kit consists the combined PIR detector and alarm box, three magnetic reed switches, compact high power siren, mains power supply, and full comprehensive instruction manual. An optional PP3 battery can be added for power failure protection.

### Specification

Power	12V DC or AC adaptor
PIR coverage	100m <sup>2</sup>
Exit delay	2.5 mins
Entry delay	15 secs
Alarm reset time	60 secs
Dimensions	140x90x56mm (PIR /alarm box)

Please print your name in **BLOCK CAPITALS**

Name .....

Please send ..... Passive Infra Red alarm Kit(s)  
at the special price of **£34.95** each  
plus **£1.40** for postage and packing.

Address .....

#### Method of payment

Cheque  Postal Order

Post Code .....

Access or BarclayCard

Telephone No .....

□□□□ □□□□ □□□□ □□□□

Please send to:

Authorised Signature .....

**Cirkit Distribution Ltd.**

Expiry Date: □□□□

**Park Lane, Broxbourne Herts. EN10 7NQ**  
**Tel. (0992)448899 Fax. (0992)471314**

types: B, As, Ph, H, He, Si, Ge, Be etc.  
 Advantages: avoids large investments.  
 Cost reduction - immediate use.  
 Applications: production of silicon and AsGa components; development of new processes.

**309415 W L/J C****Automatic vacuum cleaner**

moves under automatic control; all the sequences are piloted by a powerful electronic system. Self-monitoring to detect malfunctions by microprocessor. No programming. No understanding of electronics necessary for the user. This system improves control over worker time and guarantees thorough cleaning, including under furniture, beds etc.

**909416 W S C****Smart cards**

The card is realised by duplicate moulding in one operation including the printing of the two faces. The cost price is half of the present cost price. The investments are half of the investments at present. Phone cards, bank cards, medical cards, toll.

**509216 W L U****Canal clathrate complex**

as electronic and cationic conductor for use in solid electrolytic cells. The unique crystal structure of this novel canal clathrate complex of benzophenone and a polyiodide salt results in both electronic and cationic conductivity. This material is used either as the electrolyte or as an electrode in an electrolytic cell.

**309476 F J C****Identification systems**

A remote sensing identification system which uses low frequency electro-magnetic communication units and passive mobile tags which can be read at a distance. The communication units may be stand alone units, with own power supply or interface with IBM-PC. The tags may be either fixed code or have a readable memory and come in various forms such as credit card format, thick industrial cards or buttons. Applicable for management of automated manufacturing, material handling systems, identification of luggage, containers, vehicles or animals etc.

**909441 C M J****Pattern identification computer technique**

based on neural network artificial

intelligence. The proposed projects aim at the development of specific capabilities such as identification of cancer cells on prints produced by any medical imaging system; speaker recognition and signature verification; finger print identification; access control systems; the evaluation of polygraph tests; and the identification of explosives and other chemical substances.

**109463 F J C****Compact uninterruptable power supply**

Very compact uninterruptable power supply systems based on the innovative technology of pulse width modulation protecting sensitive equipment (eg computers) against variant power supply by providing an output voltage that is stabilised and sinusoidal. Integral self charging batteries take over instantaneously when power is interrupted and operates at the high frequency of 20,000 Hz making this a quiet system. The compact size simplifies installation.

**609508 C J C****Electro-luminescent lamp manufactured in rolls**

An advanced generation electro-luminescent (EL) lamp with high intensity is receptive to a fully continuous manufacturing process in rolls which can be cut to individual specifications. EL's are energy economical with long service life. They are suitable for various applications eg billboards, road signs, backlighting for computer screens etc.

**409365 W L U****Current steering**

CMOS logic family. Integrated digital logic circuitry that steers electrical currents and minimises switching current transients, thereby improving the operation of digital and analog circuitry on common substrates.

**408725****Magnetic antenna system**

with the characteristics of an active in-phase de-attenuation in automatic operation, designed as a combined transmitting and receiving antenna. Remote control unit designed as a blind current transfer element for resonance point adjustment. Vertical radiation angle adjustable.

**108745****Stereo sound ray loudspeaker**

The nonophonically controlled system

acoustically generates the audiophase components within the total emission required for stereo.

**708726****Magnetic antenna system**

with in-phase, automatically controlled de-attenuation amplifier. Range 1.6-500 MHz. Iron ferrocabonyl coupling for transmission and receiving operations, remote controllability, inside operation, power level on test unit 1000 Watt Hf (max). Receive/transmit switch-over not necessary.

**908647****Hologram robotic lighting**

The system consists of a centralised illumination fitted with high pressure lamps which deflect light through fibre optic light guides and balances it with the aid of optical elements. Application areas: architecture and automotive industry.

**108645****Fully automatic insertion and completion machines**

for passive electronic elements such as bases, pin and terminal strips, plugs, spring contact pins and other small parts. Precise joining processes with high place/hour capacity.

**408648****Lighting fixture with intergrated air circulation**

and cleaning device for use in rooms with poor ventilation. Space saving and inexpensive because the lighting fixture simultaneously houses the fan and filter etc.

**808419****Low voltage halogen lamps**

3 lamps (150W) with low voltage (50V), lamps can be swivelled, aluminium steel. Safety transformer, fuses. Decoration and illumination purposes.

**408761****Nesting end stage for stepping motors**

automatically calculates the path of motors (up to 600 W), dependent on inertia, friction and motor torque. Modest space requirement, low mass, self-learning function. Applications: robotics, machine tools.

**308688****Inert gas testing**

Electronic testing and measuring system with electronic gas sensors for testing and measuring inert gases.

**808732**

**Integrated switching circuits**

Method to produce integrated switching circuits and Schottky diodes. Process to apply epitaxial layers, to form oxidic insulation layers with ion implantation and precipitation of polycrystalline silicon and silicon nitride.

**408749**

**Mobile receiver aerial**

Extremely pliable rod aerial made of monocrystal alloyed material for mobile receivers, eg car radios, radiotelephonic devices. Maximum length 600 mm, diameter 1-5 mm. Aerial tested under extreme conditions during a 2 year field trial.

**808744**

**Electronic control unit for television cabinets**

Remote controlled door activation.

**508755**

**Acoustic call system**

Mains-independent acoustic call system (especially for bedridden patients). Battery operated call system foregoes the standard of conventional mains-operated devices for the sake of maximum reliability and availability.

**808747**

**Telephone call charge meter**

Telecommunication accessory: call charge meter for older telephones, for third party call charge calculation and control of own charges.

**808756**

**Silent alarm**

Alarm signal exclusively for one person. Of special importance in caring for the seriously ill, and also for shift workers.

**208754**

**Electronic foot starter for household sewing machines**

the foot starter contains an adjustable resistor which influences the control electronics to obtain speed control. The resistance characteristic of the slip ring can be adapted to the customer's requirements.

**708738**

**Electronic drive technology**

precision drives for micrometre and submicrometre range. A position controlled linear drive on the basis of a screw thread reluctance motor was created which converts the rotational motion of the rotary field directly into

linear motion. Step resolution approx 15 micrometres. Shearing force up to 80 N.

**708735**


**Chip resistor in thin film technology**

including manufacturing process. Roll by roll production under application of HT films and use of high vacuum processes. No waste products. Application in all fields of electronic equipment technology.

**8736**

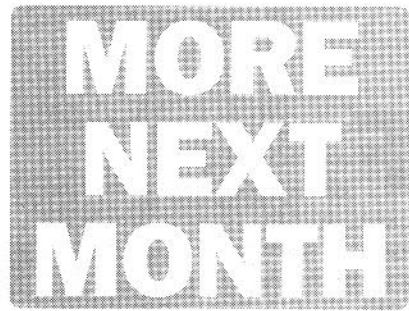**Chip capacitor including manufacturing process**

Roll by roll production under application of HT films and use of high vacuum processes. No waste products. Application in all fields of electronic equipment technology.



**Electronics in Action** is pleased to offer its readers Roy Kalawsky's fascinating book - *The Science of Virtual Reality and Virtual Environments*. This book provides a wealth of material for those who require a thorough scientific and engineering background in Virtual Reality whether they be scientist, engineer, student or layperson.

# Virtual Reading

Professor Roy Kalawsky is head of the British Aerospace Virtual Environment Laboratory

Print your name in **BLOCK CAPITALS**

Name .....


Address .....

..... Postcode .....

Please send me.....copy of *The Science of Virtual Reality and Virtual Environments* by Roy Kalawsky (Each copy costs £24.95 plus £3.00 postage and packing) I enclose a cheque/postal order for .....

Please send this form to:

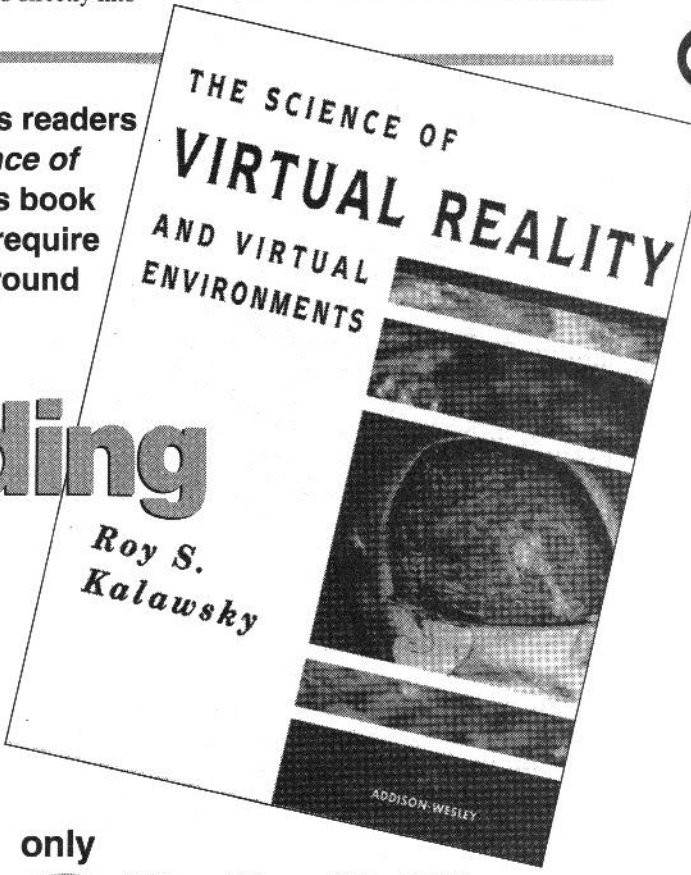**VR Book Offer, Electronics in Action**  
**PO Box 600, Berkhamsted, Herts. HP4 1NL**




only  
**£24.95**  
(+ £3.00 Postage & Packing)

# Future View

## The realities of voice recognition and its future implications

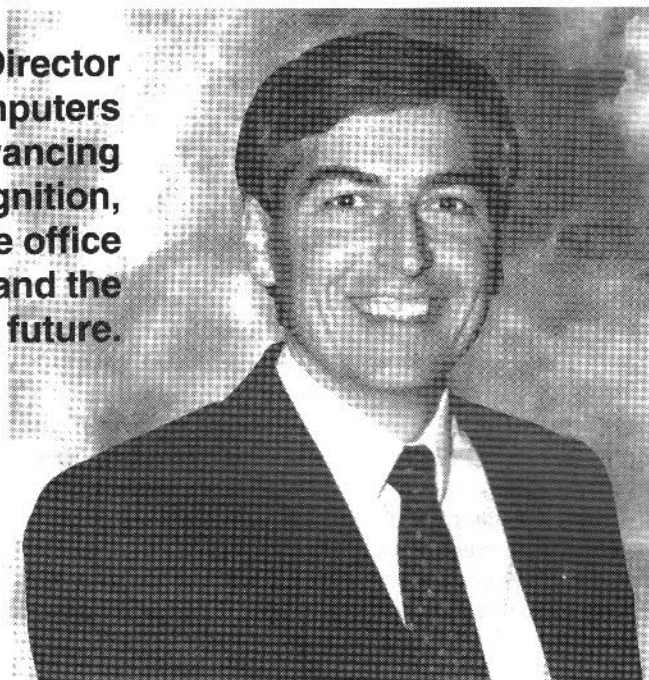**John Mitchell, Managing Director of Alltypes Business Computers discusses the rapidly advancing technology of voice recognition, its integration into the office environment and the possibilities for the future.**



For many years, the concept of controlling a computer and/or generating text by means of the spoken word has been confined to the realms of science fiction. However, since its commercial introduction in 1990 and the development of PC power, voice recognition for dictation and other large vocabulary applications is now a reality. This article discusses the implications of this radical technology, and Alltypes Business Computers are leading the way forward by integrating voice recognition for the majority of today's computer users i.e. non typists, into the office environment.

### Introduction

Excepting the introduction of certain limited vocabulary systems in the 1980s, the launch of general purpose large vocabulary systems came in 1990 from the American company, Dragon Systems. The end product was a result of extensive research and development led by Jim and Janet Baker the company founders.

DragonDictate now leads the market alongside other speech recognition products offered by companies such as IBM. It is interesting to note that until now, the speech recognition products offered by IBM were derivatives of the DragonDictate system, produced under license. Since its introduction, DragonDictate have introduced second generation products into the marketplace in 1993. The first of these products, retained the original active vocabulary of 30,000 words; however, in response to a changing market and to provide speech

recognition to a wider range of users, Alltypes launched the Dragon 5,000 word Starter Edition at the end of 1993 for less than £1000.

---

### *The DragonDictate system is a speaker dependent, large vocabulary dictation system*

---

The potential of the DragonDictate products was realised during the early stages of launch by John Mitchell, Managing Director of Alltypes Business Computers, who quickly sought to represent Dragon Systems in the UK through their trading division, AllVoice Computing. The end result, is a winning combination of the radical technological advancements provided by the Dragon speech recognition engine and Alltypes' many years expertise in word processing and office automation. Alltypes has integrated the Dragon system into a number of business applications providing voice based solutions not just word processing but to document

management, and more specialist areas such as medical and legal.

### Applications

The obvious application of large vocabulary speech recognition is in word processing. The concept of being able to produce and edit a document by means of the spoken word is by far the most exciting and obvious prospect. Performing repetitious tasks also lends itself to voice recognition and is achieved by the use of "voice macros" that command certain combinations of keystrokes. These keystrokes are usually associated with a relevant voice command or utterance such as "Print Document" to perform a printing function or "Standard Contract" to call up an entire contract document. Alltypes are the current market leaders in this area of voice recognition and provide a library of voice commands, regular phrases and even entire documents for word processing and associated applications. Leading on from this, is the integration of voice recognition with other business applications such as spreadsheets and databases.

The latter applications often go against the principles of large



vocabulary voice recognition, in that they usually only require a limited vocabulary for operation. In this situation, the "active" vocabulary is limited to accommodate this. This is an area of work that Alltypes also specialises in.

Speech recognition has already created opportunities for people with disabilities and is often solely responsible for employment rehabilitation, such as the recently publicised RSI case of Simon Crosby, a computer programmer, now working again as a result of a speech recognition system supplied by Alltypes.

potential of a computer system that you could talk to. Initial ideas were based around pattern matching, but it was quickly realized that in order for any computer type system to be able to deal with human speech, the requirement was not only that of an acoustic template, but an intelligent model that represented all the possible permutations and combinations presented by the spoken word. Combine this concept with the inconsistencies of human speech and you will be some way towards contemplating the problems facing the pioneers in this work.

The theory of this technology is far

on to work for Exxon and IBM, before forming Dragon Systems, during which time, they had rapidly built up a number of patents from their work.

It is worth mentioning one of the largest problems of speech recognition that has been overcome by various research teams all of whom profess to have arrived at the solution independently. The problem was the variation of the speed at which words are spoken. The technique that addresses this problem is called dynamic time warping. The result is an elastic word model that can be shrunk or stretched in order to accommodate a "best-fit" of the



## The Technology

The DragonDictate system is a speaker dependent, large vocabulary dictation system. Following an initial 90 minute tutorial, the user builds up a set of exclusive "voice-files" which is constantly changing according to the use of English, the environment, and even the changes in the users' voice due to a cold! In this situation, the system can be configured to revert to "normal" use following recovery or adapt back automatically as the voice changes!

In order to examine the nature of this technology, one has to consider the origins of speech recognition. In the early 1960s, AI pioneers realised the

beyond the scope of this article, suffice to say that the responsibility lies with the Russian mathematician Andrei Markov who's work that commenced at the start of the century, concentrated on the probabilities of sequences of events. His statistical methods have since been applied in many fields that have required an element of modelling. None more so than in the field of voice recognition where, in the 1980s, two research teams - one under Fred Jelinek at IBM and Jim and Janet Baker, then students at Carnegie Mellon University, Pittsburgh hit upon the idea of using Markov Statistics in speech recognition at roughly the same time. The Bakers went

word being spoken.

Current, second and third generation Dragon products, based on the principles described above, still rely on discrete speech. That is to say, the user is required to pause briefly between each word that is spoken into the system. The pause is the cue that "kickstarts" the Dragon recognition engine into action. This is not as significant a disadvantage as it may first seem. Users soon get used to the system and are quickly exceeding dictation speeds of 50 words per minute. Although some might argue that a good typist can type in excess of 100 wpm this is not the critical measurement. This comes from the consideration of

throughput. The traditional cycle of dictation, typing, proof reading and correction dramatically reduces the figure quoted above whilst the throughput speed of the speech recognition system remains.

With all potential problems seemingly addressed, later research has resulted in advanced levels of Markov modelling that takes into account, the context of the speech. This is of particular importance when dealing with words such as to, too and two where there is no audible difference in what is being said. Third generations of Dragon products will take into account what has been said in choosing phrases such as "too many" instead of "two many."

### Implementation

One might suggest that the upgrade to voice recognition is achieved by means of an installation of an expansion card and relevant software. Certainly to make a suitable PC, "voice-aware" this is the case, but this is just the beginning. We at Alltypes, are very conscientious of the importance of the implementation of voice recognition for a new installation. Current technology does not allow for a "plug-in and go" type of product. Although the strategy of newer generation computer products, is often to simply flood the market, Alltypes and Dragon recognises that this is currently not a practical or viable method.

The recommendations of Alltypes, for each and every customer investing in voice recognition technology, amount to a minimum of two days training for each new user. The resultant added-value from this training, can be equated to that of implementing voice recognition in the first place. Indeed the two are complementary.

### The Psychology of Change

Whilst Alltypes are selling systems at a dramatically increasing rate, there is still an inevitable resistance to change with technology of this kind. The very nature of this technology would, to some, suggest a means of replacement for the traditional typist or secretary. Alltypes' experience, past and current, does not provide much evidence to support this claim. In areas such as legal practice, local government and medicine, secretarial staff are often shared and are consequently over

resourced. The implementation of the AllVoice DragonDictate system in these areas, has alleviated some of the workload and has resulted in improved efficiency of document production, a point of view that is often publicly endorsed by clients.

Resistance to change is sometimes demonstrated at the other end of the company infrastructure, as senior members of staff in legal and medical areas often refuse to have a computer at their desk, regarding it as a demotion, or

---

*Society as a whole  
could well see radical  
changes as voice  
recognition is  
implemented in  
public information  
systems*

---

benefits for their organisation can be to protect their IT strategy which previously had not allowed for the possibilities of direct document production.

### The Future

With advancements in this technology over the last five years, the next five should see voice recognition on all new computers destined for the office. The inevitable advent of continuous, large vocabulary, speaker independent systems will bring about a complete change of culture in all aspects of computing. The issues discussed above will change, as certain roles in business will require different skills.

Society as a whole could well see radical changes as voice recognition is implemented in public information systems, telephone booking systems, banks, etc. the possibilities are endless and are only limited by our imagination and the associated, and often dedicated, research and development that goes in to these systems.




a task that is below them. By providing voice, as the primary means of input, Alltypes are able to offer an alternative that provides a new status to the user, often resulting in fierce competition for the use of the first system!

The other main hurdle curiously is often the IT department, who are often unaware of this technology. Their reaction rather than to see and immediately implement the astounding
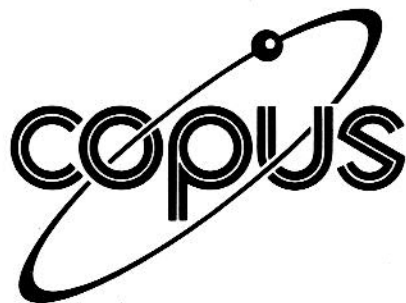
### References

- 1 Computers That Listen.** John McCrone, New Scientist 4/12/93
- 2 Using Speech Recognition for Dictation and Other Large Vocabulary Applications.** Janet M. Baker, Dragon Systems.
- 3 AllVoice Computing - the way forward.** Nicholas J. Daniel B.Eng(Hons), Voice Development, Alltypes Business Computers.



COMMITTEE ON THE PUBLIC UNDERSTANDING OF SCIENCE

ROYAL SOCIETY · ROYAL INSTITUTION · BRITISH ASSOCIATION FOR THE ADVANCEMENT OF SCIENCE

Media fellowships ★ Science book prizes

Michael Faraday Award

Lectures ★ Speaker database

Broadcasting

Grants ★ Media training courses

Research Horizons Conferences

Museums ★ Women's activities

Parliament and Government ★ Schools liaison



For further information about these and other activities contact:

COPUS, c/o THE ROYAL SOCIETY  
6 CARLTON HOUSE TERRACE  
LONDON SW1Y 5AG

Telephone: 071-839 5561, ext. 266/219

# CIRKIT ELECTRONIC CONSTRUCTORS CATALOGUE

- ◆ 240 Pages
- ◆ 26 Sections
- ◆ Over 4000 lines
- ◆ Send for your copy today!

**£1.90**  
+30p p+p



**Cirkit**

**Cirkit Distribution Ltd**

Park Lane • Broxbourne • Hertfordshire • EN10 7NQ • Tel: Sales (0992) 448899 • Fax (0992) 471314