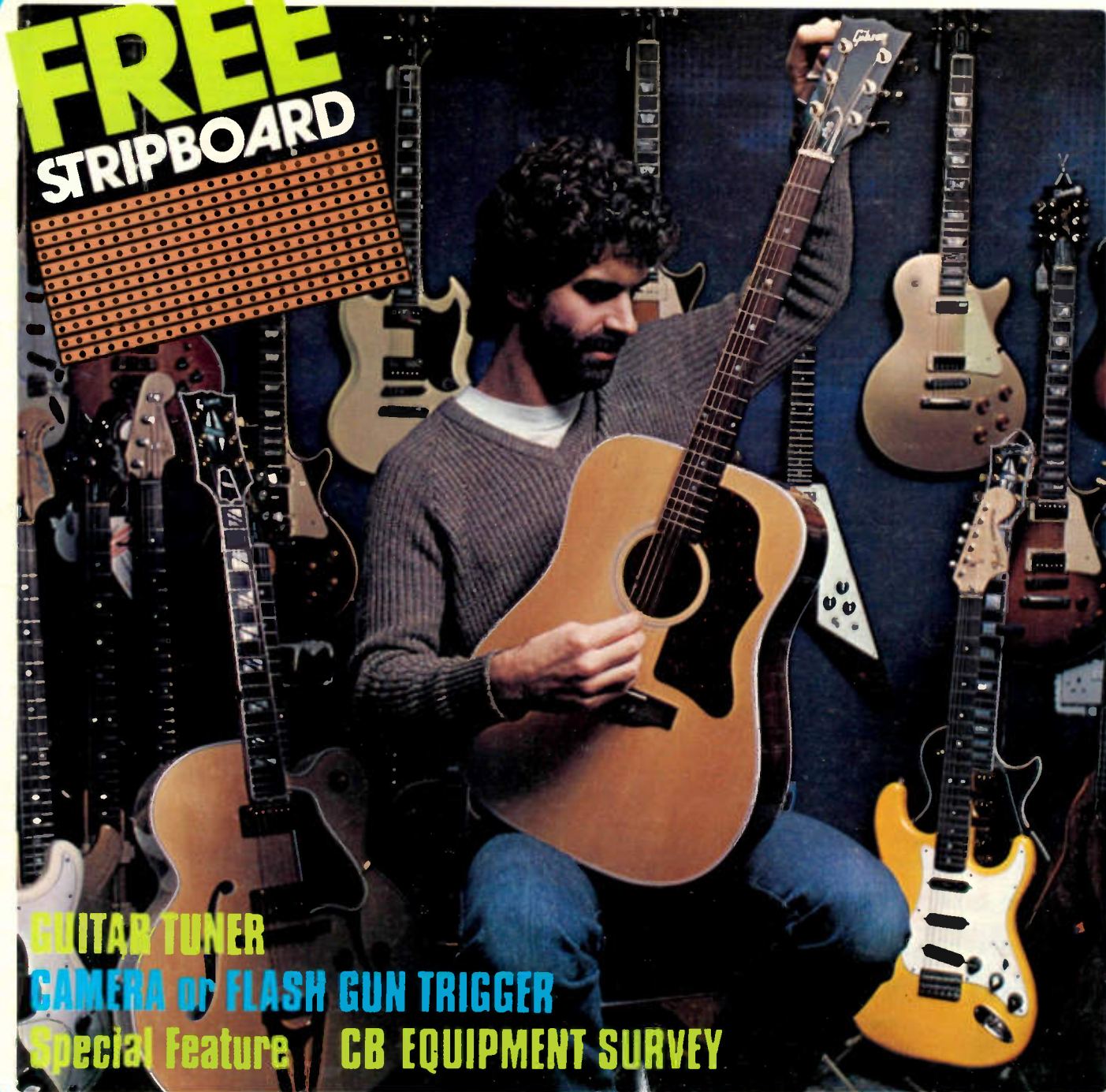


Easy to build projects for everyone

# Everyday ELECTRONICS

MARCH 82  
70p

**FREE  
STRIPBOARD**



**GUITAR TUNER**

**CAMERA OR FLASH GUN TRIGGER**

**Special Feature CB EQUIPMENT SURVEY**

# ELECTRONIC IGNITION KIT



## TOTAL ENERGY DISCHARGE

electronic ignition gives all the well known advantages of the best capacitive discharge systems.

**PEAK PERFORMANCE** — higher output voltage under all conditions.

**IMPROVED ECONOMY** —, no loss of ignition performance between services.

**FIRES FOULED SPARK PLUGS** no other system can better the capacitive discharge system's ability to fire fouled plugs.

**ACCURATE TIMING** — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

**SMOOTH PERFORMANCE** — immune to contact bounce and similar effects which can cause loss of power and roughness.

## PLUS

**SUPER POWER SPARK** — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

**OPTIMUM SPARK DURATION** 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

**BETTER STARTING** — full spark power even with low battery.

**CORRECT SPARK POLARITY** unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

**L.E.D. STATIC TIMING LIGHT** for accurate setting of the engine's most important adjustment.

**LOW RADIO INTERFERENCE** fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

**DESIGNED IN RELIABILITY** an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

## IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

**AS REVIEWED IN**  
ELECTRONICS TODAY INTERNATIONAL JUNE '81 ISSUE  
and EVERYDAY ELECTRONICS DECEMBER '81 ISSUE

**FITS ALL NEGATIVE EARTH VEHICLES,**  
6 or 12 volt, with or without ballast

**OPERATES ALL VOLTAGE IMPULSE TACHOMETERS**  
Some older current impulse types (Smiths pre '74) require an adaptor —  
PRICE £2.95

**STANDARD CAR KIT £14.85**  
**ASSEMBLED AND TESTED £24.95**

PLUS £1  
U.K. P.&P.

**TWIN OUTPUT KIT £22.94**  
For MOTOR CYCLES and CARS with twin Ignition systems  
**ASSEMBLED AND TESTED £34.70**

Prices include V.A.T.

## ELECTRONIZE DESIGN Dept. C

Magnus Road, Wilnecote,  
Tamworth. B77 5BY  
Phone 0827-281000



**DIMENSIONS:**  
Length 12.5 cm  
Width 8.9 cm  
Height 4.3 cm  
Lead length 100.0 cm

## TECHNICAL DETAILS

The basic function of a spark ignition system is often lost among claims for longer 'burn times' and other marketing fantasies. It is only necessary to consider that, even in a small engine, the burning fuel releases over 5000 times the energy of the spark, to realise that the spark is only a trigger for the combustion. Once the fuel is ignited the spark is insignificant and has no effect on the rate of combustion. The essential function of the spark is to start that combustion as quickly as possible and that requires a high power spark.

The traditional capacitive discharge system has this high power spark but, due to its very short spark duration and consequential low spark energy, is incompatible with the weak air/fuel mixtures used in modern cars. Because of this most manufacturers have abandoned capacitive discharge in favour of the cheaper inductive system with its low power but very long duration spark which guarantees that sooner or later the fuel will ignite. However, a spark lasting 2000µs at 2000 rev/min. spans 24 degrees and 'later' could mean the actual fuel ignition point is retarded by this amount.

The solution is a very high power, medium duration, spark generated by the TOTAL ENERGY DISCHARGE system. This gives ignition of the weakest mixtures with the minimum of timing delay and variation for a smooth efficient engine.

**SUPER POWER DISCHARGE CIRCUIT** A brand new technique prevents energy being reflected back to the storage capacitor, giving 3½ times the spark energy and 3 times the spark duration of ordinary C.D. systems, generating a spark powerful enough to cause rapid ignition of even the weakest fuel mixtures without the ignition delay associated with lower power 'long burn' inductive systems.

**HIGH EFFICIENCY INVERTER** A high power, regulated inverter provides a 370 volt energy source — powerful enough to store twice the energy of other designs and regulated to provide sufficient output even with a battery down to 4 volts.

**PRECISION SPARK TIMING CIRCUIT** This circuit removes all unwanted signals caused by contact volt drop, contact shuffle, contact bounce, and external transients which, in many designs, can cause timing errors or damaging un-timed sparks. Only at the correct and precise contact opening is a spark produced. Contact wear is almost eliminated by reducing the contact breaker current to a low level — just sufficient to keep the contacts clean.

## TYPICAL SPECIFICATION

	TOTAL ENERGY DISCHARGE	ORDINARY CAPACITIVE DISCHARGE
SPARK POWER (PEAK)	140 W	90 W
SPARK ENERGY (STORED ENERGY)	36 mJ	10 mJ
SPARK DURATION	135 mJ	65 mJ
	500 µS	160 µS
OUTPUT VOLTAGE (LOAD 50pF EQUIVALENT TO CLEAN PLUGS)	38 KV	26 KV
OUTPUT VOLTAGE (LOAD 50pF + 500 KΩ EQUIVALENT TO DIRTY PLUGS)	26 KV	17 KV
VOLTAGE RISE TIME TO 20 KV (Load 50pF)	25 µS	30 µS


TOTAL ENERGY DISCHARGE should not be confused with low power inductive systems or hybrid so called reactive systems.

# Everyday ELECTRONICS

VOL. 11 NO. 3

MARCH 1982

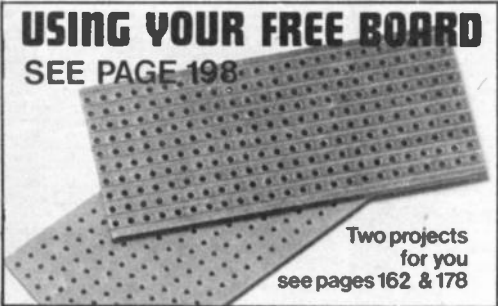PROJECTS . . . THEORY . . . NEWS . . .  
COMMENT . . . POPULAR FEATURES . . .



**USING YOUR FREE BOARD**  
SEE PAGE 198

Two projects  
for you  
see pages 162 & 178



**Guitar Tuner:**  
We are grateful to Sounds Musical Instruments of 124 Shaftesbury Avenue, London W1V 7DJ for the use of their shop and instruments featured on our front cover. The picture shows Chris Paschalides tuning a guitar.

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in **EVERYDAY ELECTRONICS** is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

## PROJECTS

- CAMERA OR FLASHGUN TRIGGER** by R. A. Penfold 156  
Infra-red beam device actuated by moving objects
- POCKET TIMER** 162  
Pre-settable from seconds to hours
- GUITAR TUNER** by A. P. Donleavy 174  
Accurate generation of the six open string notes
- ICE WARNING FOR CARS** 178  
Danger alert for the motorist
- CAR PROBE** by L. A. Privett 184  
Invaluable aid for servicing car electrics
- HOUSE REGISTER** by P. Barber 194  
For monitoring comings and goings of residents

## SERIES

- TEACH-IN 82** by O. N. Bishop 164  
Part 6: Capacitors and pulse generators
- INTRODUCTION TO LOGIC** by J. Crowther 180  
Part 11: Making other gate functions from NAND and NOR

## FEATURES

- EDITORIAL** 155  
A Matter of Interest
- PLEASE TAKE NOTE** 163  
Capacitance Meter; Cine Interval Timer & Frame Counter
- SHOP TALK** by Dave Barrington 171  
Product news and component buying
- JACK PLUG AND FAMILY** by Doug Baker 171  
Cartoon
- COUNTER INTELLIGENCE** by Paul Young 172  
A retailer comments
- BOOK REVIEWS** 172  
A selection of recent releases
- EVERYDAY NEWS** 182  
What's happening in the world of electronics
- RADIO WORLD** by Pat Hawker G3VA 186  
Gas Radio, Rechargeable Batteries, Picture Quality
- CITIZENS' BAND RADIO IN THE UK** by G. Baskerville 188  
Guide to legal rigs
- SQUARE ONE** 198  
Beginners' Page: Using Veroboard (stripboard)
- NEW PRODUCTS** 200  
Facts and photos of instruments, equipments and tools
- CIRCUIT EXCHANGE** 201  
A forum for readers' ideas

Our April issue will be published on Friday,  
March 19. See page 173 for details.

Readers Services ● Editorial and Advertisement Departments 155

# KITS, COMPONENTS, MICROS & PARTS

## DISCO LIGHTING KITS

**DL1000K.** This value-for-money kit features a bi-directional sequence, speed of sequence and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. **Only £14.80**

**DL21000K.** A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. **Only £8.00**

Optional opto input DL A1 ..... 60p  
Allowing audio ("beat")—light response.



## THE PERFECT AID FOR "LAZYITIS"

Our Lamp Dimmer Kit with **INFRA RED REMOTE CONTROL** will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, water-bed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1.3697 years or more!



This unit has considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim them to whatever brightness you require, by touch or using the hand-held infra red transmitter. When assembled, it fits into a plaster depth box to replace your conventional switch or dimmer with no rewiring.

TDR300K Dimmer Kit ..... £14.30  
MK6 Transmitter Kit ..... £4.20

We also still sell our highly popular TD300K Touch Dimmer Kit at £7.00 and the LD300K rotary controlled Dimmer Kit at **only £3.50**

All kits contain all necessary components and full instructions. You only need a soldering iron and cutters.



## REMOTE CONTROL

Published remote control systems tend to be quite complex, requiring difficult-to-get components and a well-equipped lab to get them to work. If this has put you off making your own system we have just the kits for you. Using infra-red, our KITS range from simple on/off controllers to coded transmitter/receivers with 16 on/off outputs or three analogue outputs for controlling, e.g. TV or Hi-Fi systems. The kits are easy to build and simple to set up—and they are extremely versatile, controlling anything from garage doors to room lighting just by adding the required output circuits, i.e. relays, triacs, etc. If you can design your own system we stock a wide range of remote control components at very competitive prices.

We have compiled a booklet on remote control, containing circuits, hints, data sheets and details of our remote control kits and components. So don't control yourself—SEND US 30p and a stamped addressed envelope for your copy TODAY!



## 24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains: AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

CT1000K Basic Kit ..... £14.90  
CT1000K with white box (56/131 x 71mm) (Ready Built) ..... £17.40  
..... £22.50



Add 50p postage & packing + 15% VAT to total Overseas Customers  
Add £1.50 (Europe), £4.00 (elsewhere) for p&h.  
Send S.A.E. for further STOCK DETAILS.  
Goods by return subject to availability.  
9am to 5pm (Mon to Fri)  
10am to 4pm (Sat)

**OPEN**



## TRIACS

400V Plastic Case (Texas) 3A TIC206D ..... 49p  
8A TIC226D ..... 58p  
12A TIC236D ..... 85p  
16A TIC246D ..... 96p  
25A TIC263D ..... 190p

6A with trigger O4006LT ..... 85p  
8A Isolated tab TXAL228B ..... 65p  
Diac ..... 18p  
Opto isolated triac MOC3020 0.6A/400V 110p



## DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most households.



It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1UA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions.

**IDEAL PROJECT FOR BEGINNERS—Only £5**

## DVM/ULTRA SENSITIVE THERMOMETER KIT

This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week.... Price £15.50



**FAST SERVICE - TOP QUALITY - LOW LOW PRICES**

No circuit is complete without a cail to -

**TK ELECTRONICS**  
11 Boston Road  
London W7 3SJ

Telephone: 01-579 9794/2842  
ALL PRICES EXCLUDE VAT



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits....

1000 items for the constructor.

**CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.**

- \* Lowest prices — Largest stocks \*
- \* Expert staff — Sound advice \*
- \* Choose your DIY HiFi Speakers in the comfort of our listening lounge. (Customer operated demonstration facilities)
- \* Ample parking \*
- \* Access Visa American Express accepted \*



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS

Lightning service on telephoned credit card orders!

# MUSIC KITS

ALL WITH PRINTED CIRCUIT BOARDS

128-Note Sequencer	SET76	120-45	Drum-Synthesiser	SET119	50-11
16-Note Sequencer	SET86	64-63	Enlarger Timer	SET93	30-22
3-Channel Mixer	SET107	21-50	Frequency Doubler	SET98	11-75
3-Microphone Mixer	SET108	12-99	Funny Talker	SET99	16-55
6-Channel Mixer	SET90	96-67	Guitar Effects	SET42	15-82
Analogue Reverb	SET83	45-92	Guitar Multiprocessor	SET85	70-15
Audio Effects	SET105	15-12	Guitar Overdrive	SET56	21-17
Chorusynth	SET100	125-04	Guitar Sustain	SET75	11-77
Compressor	SET120	25-05	Headphone Amplifier	SET104	21-15
Digital Reverb	SET78	75-50	Metronome	SET116	10-58
Discostrobe	SET57	30-78	Microphone Pre-amp	SET61	11-32

## 10% OFF

10% off U.K. C.W.O. orders over £20. From this advert until end of month. (5% off for credit cards). This coupon. must accompany order.

Noise Limiter	SET97	15-00	Split-Phase Tremolo	SET102	20-00
P.E. Minisonic Synth	SET30	181-50	Switched Treble Boost	SET89	12-51
Phaser	SET88	21-00	Synthesiser Interface	SET81	8-40
Phasing & Vibrato	SET70	36-25	Transient Generator	SET63	10-88
Practice Amplifier	SET106	22-15	Tremolo	SET116	13-47
Rhythm Generator	SET 103	See Lists	Tuning Fork	SET48	37-04
Signal Tracer	SET109	17-50	Voice Operated Fader	SET30	9-85
Simple Phase Unit	SET25	10-54	Voice-Scrambler	SET117	21-81
Smooth Fuzz	SET91	11-88	Wah-Wah	SET88	21-01
Speech Processor	SET110	12-18	Wind and Rain Unit	SET28	11-30

Sets include PCBs, U.K. P. & P., 15% VAT, Res., Caps., S.C.s, Pots, Knobs, SW's, Sks., Wire, Solder, Box, Photocopy of Orig. Text. Fuller details and more great kits in our Free Catalogue.

Prices correct at press, E. & O.E., subject to stock. Delivery frequently by return but please allow 14 days.

# PHONOSONICS

DEPT EE23, 22 HIGH STREET, SIDCUP, KENT, DA14 6EH  
01-302-6184

# WATFORD ELECTRONICS

35 CARDIFF ROAD, WATFORD, HERTS, ENGLAND  
MAIL ORDER, CALLERS WELCOME. Tel. Watford 40588/9

ALL DEVICES BRAND NEW, FULL SPEC. AND FULLY GUARANTEED ORDERS DESPATCHED BY RETURN OF POST. TERMS OF BUSINESS: CASH/CHEQUE/P.D.s OR BANKERS DRAFT WITH ORDER. GOVERNMENT AND EDUCATIONAL INSTITUTIONS' OFFICIAL ORDERS ACCEPTED. TRADE AND EXPORT INQUIRY WELCOME. P&P Add 50p to ALL ORDERS UNDER £10.00. OVERSEAS ORDERS POSTAGE AT COST. AIR/SURFACE. (ACCEPTS orders by telephone welcome).

**VAT** Export orders no V.A.T. Applicable to U.K. Customers only. Unless stated otherwise all prices are exclusive of V.A.T. Please add 15% to total cost including P & P.  
We stock many more items. It pays to visit us. We are situated behind Watford Football Ground. Nearest Underground/BR Stations: Watford High Street. Open Monday to Saturday 8.00 am-8.00 pm. Ample Free Car Parking space available.

**POLYESTER CAPACITORS:** Axial lead type (Values are in nF) 400V: 1nF, 1.5n, 2n, 3n, 4.7n, 6.8n 11p, 10n, 15n, 18n, 22n 12p; 33n, 47n, 68n 15p; 100n, 150n 20p; 220n 30p; 330n 42p; 470n 52p; 680n 60p; 1µF 80p; 2µF 82p; 4µF 85p.  
160V: 10nF, 12n, 100n 11p; 150n, 220n 17p; 330n, 470n 20p; 680n 30p; 1µF 42p; 1.5µ 45p; 2µ 48p; 4µ 50p.

**POLYESTER RADIAL LEAD CAPACITORS (250V)**  
10nF, 15n, 22n, 27n 6p; 33n, 47n, 68n, 100n 7p; 150n, 220n 10p; 330n, 470n 17p; 680n 19p; 1µF 23p; 1.5µ 23p; 2µ 24p.

**ELECTROLYTIC CAPACITORS:** (Values are in µF) 500V: 10 52p; 47 78p; 83V: 0.47, 1, 1.5, 2, 3, 4.7, 10, 15, 22, 33, 47, 100 15p; 15, 22, 33, 47, 100 18p; 100 70p; 100 100p; 100 150p; 100 200p; 220 240p; 470 32p; 2200 90p; 40V: 4.7, 15, 22 8p; 3300 90p; 4700 120p; 25V: 1.5, 5, 6, 8, 10, 22 8p; 33 8p; 47 8p; 100 11p; 150 12p; 330 22p; 470 25p; 680, 1000 34p; 2200 50p; 3300 70p; 4700 82p; 18V, 40, 47, 100 8p; 125 12p; 220 13p; 470 20p; 680 34p; 1000 27p; 1500 31p; 2200 36p; 3300 74p; 4700 79p.  
**TAG-END TYPE:** 70V: 4700µ 245p, 84V: 3300 180p, 2200 130p, 50V: 3300 154p, 2200 110p, 40V: 4700µ 160p, 25V: 4000 90p; 2500, 2200 90p, 1500 345p.

**TANTALUM Bead CAPACITORS**  
35V: 0.1µ, 0.22, 0.33 15p; 0.47, 0.68, 1.0, 1.5 16p; 2.2, 3.3 18p; 4.7, 6.8 22p; 10 28p, 18V: 2.2, 3.3 18p; 4.7, 6.8, 10 18p; 15 35p; 22 36p; 33, 47 40p; 100 70p; 150 72p; 220 74p; 330 76p; 470 78p; 1000 80p; 1500 82p.

**MYLAR FILM CAPACITORS**  
100V: 1nF, 2n, 4n, 4.7n, 10n 6p; 18nF, 22n, 30n, 40n, 47n 7p; 56n, 100n, 200n 8p. 470n/50V 12p.

**MINIATURE TYPE TRIMMERS**  
4-6pF, 2-10pF Z2p; 2-25pF, 5-65pF 30p; 10-85pF 35p.

**COMPRESSION TRIMMERS**  
3-40pF, 10-80pF 20p; 20-250pF 28p; 100-580pF 39p; 400-1250pF 48p.

**POLYSTYRENE CAPACITORS**  
10pF to 1nF 9p; 1-5nF to 12nF 10p.

**SILVER MICA:** 2pF, 3-3, 4-7, 6-8, 8-2, 10, 12, 15, 18, 22, 27, 33, 39, 47, 50, 56, 68, 75, 82, 85, 100, 120, 150, 180 15p; 200, 220, 250, 270, 300, 330, 360, 390, 470, 600, 800, 820 21p; 1000, 1200, 1800, 2000 30p; 3300, 4700 60p.

**CERAMIC CAPACITORS:** 50V 0-8pF to 10nF 4p; 22n to 100n 7p.

**EURO BREADBOARD £5.20.**

**VOLTAGE REGULATORS\***  
1A 7805 +ve -ve 220p  
5V 7805 145p 7905 220p  
10V 7812 145p 7912 220p  
15V 7815 145p 7915 220p  
16V 7818 145p  
1A TO220 Plastic Casing  
8V 7805 45p 7905 55p  
12V 7812 50p 7912 55p  
18V 7818 50p 7918 55p  
18V 7818 50p 7918 55p  
24V 7824 50p 7924 55p  
100mA TO92 Plastic Casing  
6V 78L05 30p 79L05 60p  
6V 78L02 30p  
6V 78L82 30p  
12V 78L12 30p 79L12 60p  
18V 78L18 30p 79L18 60p  
CA3085 95 LM326N 140  
LM300H 170 LM37N 78H05+5V/5A 595  
LM305H 140 LM723 35 78H5A +5V  
LM309K 135 TAA550 50 10+25V 550  
LM317K 350 TBA525B 75 79H5A -2.25  
LM333K 500 TDA1412 150 to -24V 785p

**POTENTIOMETERS (ROTARY)**  
Carbon Track, 0.25W Log & 0.8V Linear Value.  
500Ω, 1K & 2K (Lin. only) Single 28p  
8K-2 MΩ single gang 28p  
8K-2 MΩ single with DP switch 78p  
8K-2 MΩ double gang 88p

**SLIDER POTENTIOMETER**  
0-25W Log and linear values 60mm  
6K-0.500K Ω single gang 70p  
10K Ω-500K Ω dual gang 110p  
Self Stick Graduated Bezels 40p

**PRESET POTENTIOMETERS**  
Vertical & Horizontal  
0-1W 80Ω-5MΩ Miniature 7p  
0-25W 100Ω-3.3M Ω Horiz 10p  
0-25W 200Ω-4.7M Ω Vert 16p

**RESISTORS:** Carbon Film, High Stability, Low Noise, Miniature Tolerance 5%.  
Range Val. 1-99 100+  
1W 202-4M7 E24 2p 1p  
1W 202-4M7 E12 2p 1p  
1W 202-10M E12 5p 4p  
2% Metal Film 10Ω-1M 8p  
1% Metal Film 10Ω-1M 8p  
100+ price applies to Resistors of each value not mixed.

TGS 812 or 813 gas and smoke detector 575p. Socket for above 40p.

**SLIDE 250V:**  
1A DPDT 14p  
1A DP c/off. 16p  
1A DPDT 13p

**PUSH BUTTON**  
Latching or Momentary.  
SPST C/Over 98p  
DPDT C/Over 145p  
DPDT C/Over 145p

**SWITCHES** Miniature Non-Locking Push to Make 18p Push to Break 20p  
ROCKER: SPST on/off 10A 250V 28p  
ROCKER: Illuminated DPST Lights when on: 10A 240V 88p

**ROTARY: (ADJUSTABLE STOP) 1 pole/2-12 way 2p/2-6w, 3p/2-4w, 4p/2-3w. 45p**  
**ROTARY: 2-Mains, 250V AC, 4 Amp 595p**

**DIL SOCKETS (Low Profile - Texas)**  
8 pin 8p; 14 pin 10p; 16 pin 10p; 18 pin 10p; 20 pin 22p; 24 pin 25p; 28 pin 28p; 40 pin 30p.

**JACKSONS VARIABLE CAPACITORS**  
Dilicon 0 2 365pF with slow motion Drive 485p  
600pF 250p 90 208/178 435p  
6.1 Ball Drive with slow motion Drive 495p  
4811/DAF 185p  
Diel/Daf 4103  
6.1/38 1 775p C804-50F 10 15  
Drum 64mm 59p 28.50 pF 278p  
0.1-365pF 350p 10-3 x 310pF 725p  
0.0 2 365pF 435p 0.0-3 x 25pF 575p

**DENCO COILS RFD2 145p**  
'DP' VALVE TYPE RCT5 140p  
Range 1 to 5 Bl., RFT (19mH) 160p  
RD, YI, Whi, 122p IFC 13; 14; 18;  
6-7 B.Y.R. 110p 16; 17; 120p  
1-5 Green 150p IF 18; 18 135p  
17; 1 to 5 Bl., YI, IFC 16; 14; 152p  
RD, Whi. 150p TWC 1 125p  
B.A Valve Holder MW5FR 122p  
42p MW/LW 5FR154p

**VEROBORDS '1'** clad plain  
2x 3x 73p 52p  
2x 5x 85p — 6 x 8" 90p  
3x 5x 85p — 6 x 12" 150p  
3x 8x 95p 79p S.R.B.P.  
4x 17x 328p 211p 9.5 x 8 85p  
4x 17x 42p  
Pkt. of 100 pins 50p  
Spot Face Cutter 118p  
Pin Insertion Tool 162p

**DIODES**  
AA129 22 3A/100V 18  
BA100 15 39V 400mV  
BY126 12 Range 5V to 33V, 1.3W  
CRO33 250 15p each  
OA9 40  
OA47 12  
OA70 12  
OA78 18  
OA81 18  
OA85 18  
OA90 8  
OA95 8  
OA95 8  
OA200 8  
OA202 8  
IN914 4  
IN916 8  
IN916/2 8  
IN4003 6  
IN4004/5 8  
IN4007/7 8  
IN4148 4  
IS44 9  
IS44 9

**NOISE**  
Diode 185

**BRIDGE RECTIFIERS**  
2N5802 32 (plastic case)  
1A/50V 16  
1A/100V 28  
1A/200V 40  
1A/400V 56  
1A/600V 80  
2A/100V 16  
2A/200V 40  
2A/400V 56  
2A/600V 80  
3A/100V 18  
3A/200V 40  
3A/400V 56  
3A/600V 80  
3A/1000V 36  
6A/100V 18  
6A/200V 40

**COPPER** clad boards  
Fibreglass 3A/100V 18  
6A/100V 18  
3A/1000V 36  
6A/1000V 36  
F.R.B.P.  
9.5 x 8 85p  
Ferric Chloride 1 lb.  
Anhyd. 195p  
Dialo Pen 90p

We stock a wide selection of electronic Books and Magazines

**DPTO ELECTRONICS**  
LEDs plus clips  
TIL209 Red 3mm 13  
TIL211 Grn 3mm 18  
TIL212 Yellow 10  
2" Yellow Green 10  
Square LED 20  
OC771 120  
ORP12 80  
ORP61 48  
2N9777 48

**7 Seg Displays**  
TIL321 C An 8" 110  
TIL322 C Cth 6" 110  
DL704 C 8" 80  
DL707 C A. 8" 80  
DL747 C A. 8" 100  
FND387 or 500 180  
MAN3840 178  
3" Green C.A. 180  
TIL32 Inf. Red 82  
TIL78 Def. Red 54  
TIL100 90  
Bargraph Red.  
Ten segment 225p  
4 Digit 750p  
6 Digit 750p

**LCD DISPLAYS**  
3 1/2 Digit 550p  
4 Digit 750p  
6 Digit 750p

**SWITCHES**  
TOGGLE 2A 250V  
SPST 33p  
DPDT 44p  
SUB-MIN  
SP changeover 88p  
SPST on/off 64p  
DPDT 6 tags 73p  
DPDT C/Over 88p  
DPDT C/Over 145p

**TRANSISTORS**  
BC212L 10  
AC125 35  
AC126/7 30  
AC128 30  
AC141/2 30  
AC142 30  
AC143/17 78  
AC149/120 75  
AC151/22 75  
AC152 78  
AC153 78  
AC154 78  
AC792 78  
AC793



# Rapid Electronics

Tel: 0322 863494  
Hillcroft House  
Station Road  
Eynsford Kent DA4 0EJ



OPTO		5mm red		8p	
★ 3mm red	8p	★ 5mm green	12p	★ 5mm yellow	12p
★ 3mm green	12p				
★ 3mm yellow	12p				
Clips to suit 3p each.					
Rectangular		TIL32	40p		
★ Red	12p	TIL78	40p		
Green	17p	TIL111	60p		
Yellow	17p	ORP12	85p		
Seven Segment Displays					
Com. cathode		Com. anode			
DL704 0.3in	95p	DL707 0.3in	85p		
★ FN5000 0.5in	65p	FND507 0.5in	90p		
TIL313 0.3in	105p	TIL312 0.3in	105p		
TIL322 0.5in	115p	TIL321 0.5in	115p		

All seven segment displays are supplied with connection details.

2N5777 45p Dual colour LED 60p

## CAPACITORS

Polyester. Radial leads. 250V C280 type.  
0.01, 0.015, 0.022, 0.033, 8p, 0.047, 0.068, 0.1, 7p, 0.15, 0.22, 9p, 0.33, 13p, 0.47, 13p, 0.68, 20p, 1.0, 23p.

Electrolytic. Radial or Axial leads.

0.47/63V, 1/63V, 2.2/63V, 4.7/63V, 10/25V, 7p; 22/25V, 47/25V, 8p; 100/25V, 9p; 220/25V, 14p; 470/25V, 20p; 1000/25V, 30p.

Polyester. Siemens PCB

Ln, 2n2, 3n3, 4n7, 6n8, 10n, 15n, 7p; 22n, 33n, 47n, 68n, 8p; 100n, 9p; 150n, 11p; 220n, 13p; 330n, 20p; 470n, 26p; 680n, 29p; 1u, 3p; 2u, 50p.

Tantalum bead.

0.1, 0.22, 0.33, 0.47, 1.0 @ 35V, 12p; 2.2, 4.7, 10 @ 25V, 20p; 15/16V, 30p; 22/16V, 27p; 33/16V, 45p; 47/16V, 27p; 47/16V, 70p; 68/8V, 40p; 100/10V, 90p.

Ceramic.

22p-0.01u. 50V type. 3p each.

Polystyrene. 5% tolerance.

10p-1000p 6p. 1500p-4700p 8p. 6800p-0.012 10p.

Trimmers. Mullard 808 series.

2-10pF 22p. 2-22pF 30p. 5.5-65pF 35p.

## TRANSFORMERS

Please add carriage charges to our normal postage charge.

Miniature mains.

606V, 909V, 12012V all @ 100mA 100p each

High quality. Split bobbin construction.

6VA 0.6, 0.6 @ 0.5A; 0.9, 0.9V @ 0.4A 0.12, 0.12V @ 0.3A, 220p each

12VA 0.6, 0.6 @ 1A; 0.9, 0.9V @ 1.2A; 0.12, 0.12 @ 0.5A; 0.15, 0.15V @ 0.4A 275p each (plus 40p carriage).

24VA 0.6, 0.6V @ 1.5A; 0.9, 0.9V @ 1.2A; 0.12, 0.12V @ 1A; 0.15, 0.15V @ 0.8A; 330p each (plus 60p carriage)

50VA 0.12, 0.12V @ 2A; 0.15, 0.15V @ 1.5A; 400p each (plus 70p carriage).

100VA 0.30, 0.30V @ 1.6A 320p each (plus 80p carriage).

## SWITCHES

Submin. Toggle

SPST 55p SPDT 60p ★DPDT 50p

Miniature toggle

SPDT 80p SPDT centre off 80p

DPDT 90p DPDT centre off 100p

Standard toggle

SPST 35p DPDT 45p

★Miniature DPDT slide 12p

★Push to make 12p Push to break 22p

Rotary type adjustable stop

1P12W, 2P6W, 3P4W, 4P3W all 55p each

DIL switches

4 SPST 80p 6 SPST 80p 8 SPST 100p

## CABLES

20 metre pack single core

connecting cable, ten different

colours 85p

Speaker cable 10p/m

Standard screened 10p/m

Twisted screened 24p/m

2-5A 3 core mains 23p/m

10 way ribbon 85p/m

20 way ribbon 120p/m

## PCB MATERIALS

Alfac transfer sheets 45p

Dalco etch resist pen 100p

Fibre glass board 3.75 x 8" 78p

Ferric Chloride 250ml bottle 100p

## BOXES

Dimensions in inches. Aluminium.

3 x 2 x 1 70p 6 x 4 x 2 120p

4 x 3 x 1 85p 6 x 4 x 3 150p

4 x 3 x 2 100p 8 x 6 x 2 180p

## POTENTIOMETERS

Rotary. Carbon track Log or Lin 5K-1M

Single Slide. Stereo 85p each.

Slide. 60mm travel single

Log or Lin 5K-500K, 83p

Preset. Submin horiz. 100Ω-1M 7p

## CONNECTORS

DIN Plug Skt Jack Plug Skt

2 pin 9p 9p 2.5mm 10p 10p

3 pin 12p 10p 3.5mm ★7p ★7p

5 pin 13p 11p Standard 16p 25p

Phono 10p 12p Stereo 24p 20p

1mm 13p 13p 4mm 18p 17p

## UHF (CB) Connectors

PL259 Plug 40p Reducer 14p

S0239 Square chassis socket 38p

S0239S Round chassis socket 40p

## IEC 3 pin 250V/6A

Plug chassis mounting 38p

Socket free hanging 60p

Socket with 2m lead 120p

## REGULATORS

Negative

★78L0525p 79L05 65p

78L12 30p 79L12 65p

78L15 30p 79L15 65p

★7805 45p ★7905 45p

★7812 45p ★7912 45p

7815 60p 7915 60p

LM309K ★LM323K

★LM317T ★LM723 40p

120p

## SOCKETS

★8 pin 7p 22 pin 20p

★14 pin 9p 24 pin 22p

★16 pin 10p 28 pin 28p

18 pin 15p 40 pin 32p

20 pin 18p

Soldercon pins 60p/100.

## RESISTORS

1W 5% Carbon film E12

series. 4.7Ω-10M. 1p each

1W 5% Carbon film E24

series 4.7Ω-4M7. 2p each

1W 1% Metal film. E24

series 10Ω-1M 6p each

## PANEL METERS

Size 60 x 46 x 35mm.

0-50uA 0-500mA

0-100uA 0-1A

0-500uA 0-50V AC

0-1mA 0-50V DC

0-10mA 0-300V AC

0-50mA 0-25V

0-100mA 0-30V DC

## TRANSISTORS

BC125 35 BC157 10 BC549 10 BF x29 25

BC126 25 BC158 10 BC558 10 BFX84 25

BC127 25 BC159 8 BCY71 18 BFX85 28

★AC128 25 BC160 10 BCY72 18 BFX87 25

★AC176 25 BC168C 10 BD115 8 BFX88 25

AC187 22 BC169C 10 BD131 35 BFX50 23

AC188 22 BC170 8 BD132 35 BFX51 23

AD142 120 BC171 10 BD133 50 BFX52 23

AD149 80 BC172 8 BD135 50 BFX53 32

AD161 40 BC177 18 AD136 30 BFX55 32

AD162 40 BC178 18 AD137 10 BFX56 32

★AC179 18 BC179 18 BD138 30 BRY39 40

AF124 60 BC182 10 BD139 35 BSX20 20

AF126 60 BC182L 8 BD140 35 BSX29 35

AF139 40 BC183 10 BD204 110 BSY95A 25

AF186 70 BC183L 10 BD206 110 BU205 160

AF239 75 BC184 7 BD222 85 BV206 200

BC107 10 BC184L 7 BF120 10 BU208 170

BC107B 10 BC212 10 BF182 35 MU295 99

★BC108 8 BC212L 10 BF184 25 MU340 50

BC108B 12 BC213 10 BF185 25 MU350 50

BC108C 12 BC213L 10 BF194 12 MU521 85

★BC109 8 BC214 10 BF195 12 MU305 70

BC109C 12 BC214L 8 BF196 12 MPF102 40

BC114 22 BC237 8 BF197 12 MPF104 40

BC115 22 BC238 14 BF198 10 MPFA025 22

BC117 22 BC308 15 BF199 18 MPFA026 22

BC119 35 BC327 14 BF200 30 MPFA12 30

BC137 40 BC328 14 ★BF244B18 MPFA55 30

BC139 40 BC337 14 BF245 30 MPFA56 30

BC139C 12 BC338 14 BF256 30 MPFA55 35

BC141 30 BC477 30 BF257 32 MPFU06 55

BC142 25 BC478 30 BF258 25 MPFU55 60

BC143 25 BC479 30 BF259 35 MPFU56 60

BC147 8 BC517 40 BF337 40 TIP29 35

BC148 8 ★BC547 7 BFR40 23 TIP29A 40

BC149 9 BC548 10 BFR80 25 TIP29B 55

★4017 43 4036 285 4055 115 4082 70 4502 70 4529 150

4000 14 4018 60 4033 295 4053 480 4085 65 4507 38 4534 49

★4001 12 4020 55 4041 75 4063 90 4089 140 4508 200 4538 110

4002 14 4021 65 4042 55 4066 35 4093 33 4510 65 4543 110

4006 65 4022 70 4043 60 4067 395 4094 14 ★4511 50 4549 380

4007 17 4023 18 4044 65 ★4068 15 4095 90 4512 70 4553 295

4008 58 4024 40 4045 70 4069 18 4097 340 4514 180 4555 48

4009 30 4025 18 4046 70 4097 18 4205 65 4515 225 4557 65

4010 35 4026 98 4048 55 4071 18 4099 55 4516 75 4559 390

★4011 13 4027 30 ★4049 28 4072 18 4106 50 ★4518 45 4560 180

4012 17 4028 55 4050 28 4073 20 4109 100 4520 70 4581 45

★4013 22 4029 75 4051 60 4075 20 4163 100 4521 200 4585 99

4014 60 4030 35 4052 70 4076 63 40173 100 4526 80 4724 140

4015 60 4031 170 4053 60 4077 25 40175 100 4527 90

★4016 22 4034 179 4054 110 4081 18 40183 90 ★4528 400

## LINEAR

CA3161E 140 LM377 150 LM3900 50 NE566 150 TLO71 45

★CA3162E 450 ★LM380 100 LM3909 70 NE567 100 TLO72 75

★709 25 CA3189E 290 ★LM381 100 LM3911 120 NE571 425 ★TLO81 30

★741 14 ICL7106 790 LM382 120 ★LM3914 200 RC4136 90 TLO82 30

748 35 ICL8038 320 ★LM386 65 ★LM3915 200 SN7618 150 ★TLO84 90

AY-3-1270 840 ICM7555 80 LM387 120 LM13600 120 ★SN7817 150 ★XR2026 300

★AY-3-8910 70 ★LF351 40 LM393 100 MC1310 150 TBA800 80 ZN414 100

★AY-3-8912 LF353 85 ★LM709 25 MC3302 150 TBA810 95 ZN423 195

★743 625

CA3046 60 LM10 395 LM710 50 MC3340 135 TBA820 80 ZN424 135

★CA3080 55 ★LM301A 25 LM725 350 NE5515 270 TCA950 290 ZN425E 390

CA3089 215 LM311 70 LM733 75 NE529 225 TCA940 170 ZN426E 330

CA3090AQC LM318 85 ★LM741 14 NE531 150 TDA1004 300 ZN427E 850

★743 375 ★LM324 40 LM747 75 NE544 185 TDA1

# CAMBRIDGE LEARNING SELF-INSTRUCTION COURSES

## A PRACTICAL DIGITAL ELECTRONIC KIT FOR ★ LESS THAN £20 ★



### SUITABLE FOR BEGINNERS

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

seven LS TTL integrated circuits, breadboard, LEDs, and all the DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits.

This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

Other self-instruction courses from Cambridge Learning Ltd include:

COMPUTER PROGRAMMING IN BASIC	£10.50
DIGITAL COMPUTER LOGIC AND ELECTRONICS	£ 8.50
DESIGN OF DIGITAL SYSTEMS	£14.00

Please send for full details (see coupon below).

**GUARANTEE** No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

**CAMBRIDGE LEARNING LIMITED, UNIT 103, RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No. 313026022**

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:

.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a \*cheque/PO payable to Cambridge Learning Ltd for £..... (\*delete where applicable)

Please charge my:

\*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercharge / Trustcard

Expiry Date..... Credit Card No .....

Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, UNIT 103, Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No. 1328762).

# BI-PAK

### CB users. Home base POWER SUPPLY 3A Rugged Powerful British Made

FEATURES ★ Sale 3 Amp operation ★ 13.8V Fully regulated ★ Electronic short circuit & overload protected ★ Latest technology I.C. design ★ Attractive compact case ★ Competitively priced

SPECIFICATIONS ★ Input voltage - 240 V.a.c. 50Hz ★ Output voltage - 13.8V d.c. ±1% Maximum with mains input variation ±10% load 0-2.5A ★ Output current - 0-3Amp ★ Ripple - less than 2mV up to full load ★ Dimensions - 175g x 100w x 75h (mm)

OUR PRICE **Only £15.00** ORDER NO 3GA

CB Rigs and Accessories in stock. Send S. A. E. for full listings.

### 8 BIT MICROPROCESSOR

National INS8080AN 40 Pin DIL N. Channel Silicon GATE MOS TECHNOLOGY As used in Nationals N8080 Micro Computer Family Instruction Cycle Time 2 µs

Supplied with functional Block Diagram

BRAND NEW —

NOT seconds or reclaims

100% perfect ORDER NO. SX8080

Normal Sell price £4.50 each

Our BI-PAK Special Price

SO HURRY — LIMITED STOCKS



**only £2.00**

40 Pin IC Socket to fit SX8080 Offer price **30p** ORDER NO. 1609


### TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish all identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation

— Beat the Budget  
— Down with Depression

Price —  
**JUST £6.50.**

Order No. SX85

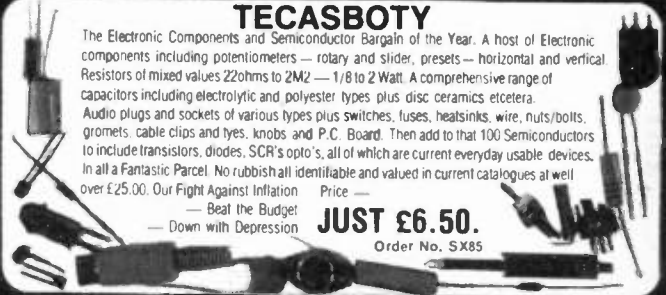

## Fantastic Audio Bargains

15 watts per channel stereo amplifier kit

Consisting of — ORDER NO STA15

2 x AL60 amplifiers

1 x PA100 pre-amplifier

1 x SPMB0 power supply

1 x 2034 transformer

2 x coupling capacitors for 8 ohms 470mfd

50v and necessary wiring diagrams

— now only

Save over £10 on this kit **£26.00**

### 5 watt (RMS) Audio Amp

High Quality audio amplifier Module. Ideal for use in record players, tape recorders, stereo amps and cassette players, etc. Full data and back-up diagrams with each module.

Specification

● Power Output 5 watts RMS ● Load Impedance 8-16 ohms ● Frequency response 50Hz to 25 KHz—3db ● Sensitivity 70 mv for full output ● Input Impedance 50k ohms ● Size 85 x 64 x 30mm ● Total Harmonic distortion less than 5%

BI-PAK'S give away price

**£2.25**

You could not Build one for this price.



### COMPLETE AUDIO CHASSIS

STEREO 30 Complete 7 watt per channel Stereo amp board — includes amps, pre-amp, power supply, front panel, knobs and Transformer

Almost ½ PRICE

**£12.50**

ORDER NO. ST30



### MONO PRE-AMPLIFIERS

MM100 suitable for disco mixer. MM100G suitable for guitar pre-amp mixer.

The MM100 and MM100G mono pre-amplifiers are compatible with the AL60, AL80, AL120 and AL250 power amplifiers and their associated power supplies.

MM100 Supply voltage 40-65v inputs. Tape Mag P.U. Microphone Max output 500mw **£12.45** MM100G Supply voltage 40-65v inputs. 2 Guitars. Microphones Max output 500mw

**each £10**



### 1 Amp SILICON RECTIFIERS

Glass Type similar IN4000 SERIES IN4001-IN4004 50 — 500v — uncodded — you select for VLTS

ALL perfect devices — NO dud's Min 50v

50 for £1.00 — worth double ORDER NO SX76

Silicon General Purpose NPN Transistors TO-18 Case

Lock fit leads — coded CV7644 Similar to BC147

— BC107 — Z789 ALL NEW! VCE 70v IC500mA

Hfe 75-250 50 off 100 off 500 off 1000 off

PRICE **£2.00 £3.80 £17.50 £30.00** Order as CV7644

Silicon General Purpose PNP Transistors TO-5 Case

Lock fit leads coded CV9507 similar ZN2905A to

BFX30 VC 60 IC 600mA Min Hfe 50 ALL NEW!

50 off 100 off 500 off 1000 off

PRICE **£2.50 £4.00 £19.00 £35.00** Order as CV9507

### Silicon NPN'L' Type Transistors

TO-92 Plastic centre collector

Like BC182L — 183L — 184L

VCBO 45 VCEO 30 IC200mA Hfe 100-400

ALL perfect devices — uncodded ORDER AS SX183L

50 off 100 off 500 off 1000 off

**£1.50 £2.50 £10.00 £17.00**

### PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line

VCEO 40 VCBO 35 Ic 300mA Hfe 50-400

Brand New — Uncodded — Perfect Devices

50 off 100 off 500 off 1000 off

**£2.00 £3.50 £15.00 £25.00**

Order as ZTXPNP

Send your orders to Dept EE 3  
BI-PAK PO BOX 6 WARE HERTS.



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail

Remember you must add VAT at 15% to your order Total. Postage add 50p per Total order



# BI-PAK BARGAINS



**5T21 SCREWDRIVER SET**  
6 precision screwdrivers in hinged plastic case Sizes — 0.8, 1.4, 2.2, 2.9 and 3.8mm **£1.75**

**5T31 NUT DRIVER SET**  
5 precision nut drivers in hinged plastic case With turning rod **£1.75**  
Sizes — 3, 3.5, 4, 4.5 and 5mm

**5T41 TOOL SET**  
5 precision instruments in hinged plastic case Crosspoint (Philips) screwdrivers — H0 and H1 Hex key wrenches — 1.5, 2 and 2.5mm **£1.75**

**5T51 WRENCH SET**  
5 precision wrenches in hinged plastic case Sizes — 4, 4.5, 5, 5.5 and 6mm **£1.75**  
BUY ALL FOUR SETS 5T21-5T51 and get HEX KEY SET FREE  
HEX KEY SET ON RING  
Sizes 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm  
Made of hardened steel  
HX/1 **£1.25**




## BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises  
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit  
1 Sheet PCB Transfers 210mm x 150mm  
1 Etch Resist Pen  
1 1/2lb pack FERRIC CHLORIDE crystals  
3 sheets copper clad board  
2 sheets Fibreglass copper clad board  
Full instructions for making your own PCB boards  
Retail Value over **£15.00**  
OUR BI-PAK SPECIAL KIT PRICE **£9.75**  
ORDER NO SX81


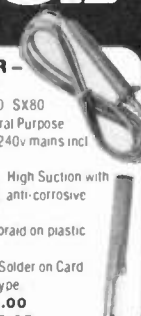
## BI-PAK SOLDER - DESOLDER KIT

Kit comprises ORDER NO SX80  
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit  
1 Quality Desoldering pump High Suction with automatic ejection Knurled anti-corrosive casing and teflon nozzle  
1 5 metres of De-soldering braid on plastic dispenser  
2 yds (1.83m) Resin Cored Solder on Card  
1 Heat Shunt tool tweezers Type  
Total Retail Value over **£12.00**  
OUR SPECIAL KIT PRICE **£8.95**



## BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m  
LCD 10 MEGOHM INPUT IMPEOANCE  
\*3 1/2 digit \*16 ranges plus NFE test facility for PNP and NPN transistors \*Auto zero, auto polarity \*Single-handed pushbutton operation \*Over range indication \*12.5mm (1/2-inch) large LCD readout \*Diode check \*Fused circuit protection \*Test leads battery and instructions included  
Max indication 1999 or — 1999  
Polarity indication Negative only  
Positive readings appear without + sign  
Input impedance 10 Megohms  
Zero adjust Automatic  
Sampling time 250 milliseconds  
Temperature range — 5°C to 50°C  
Power Supply 1 x PP3 or equivalent 9V battery  
Consumption 20mW  
Size 155 x 88 x 31mm  
RANGES  
DC Voltage 0-200mV  
DC Voltage 0-200-1000V Acc 0.8%  
AC Voltage 0-200-1000V  
Acc 1.2% DC Current 0-200uA  
0-2-20-200mA 0-10 A Acc 1.2%  
Resistance 0-2-20-200K ohms  
0-2 Megohms Acc 1%  
BI-PAK VERY LOWEST POSS PRICE **£35.00** each




## MINI VICE

This small cast iron quality made vice will clamp on to any bench or table having a max thickness of 1 1/2". The 2 1/2" jaws open to max of 1 1/2". Approx size 80 x 120 x 66mm  
Bi-Pak's Mini Vice at a Mini Price only

**£2.**

ORDER NO SX82

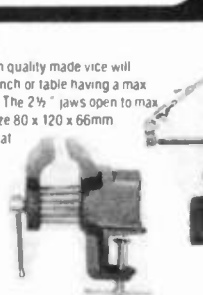

## The Third and Fourth Hand...

... you always need but have never got 'until now'  
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO T402 **£5.50**  
Without magnifier ORDER NO T400 **£4.75**

## EXPERIMENTER BOXES - ALUMINIUM - PLASTIC ALUMINIUM BOXES

Made with Bright Aluminium folded construction with deep lid and screws

SIZE	L	W	H	Order No	Price
5 1/2"	2 1/4"	1 1/2"	1 1/2"	159	<b>83p</b>
4"	2 1/4"	1 1/2"	1 1/2"	161	<b>83p</b>
4"	2 1/2"	2"	1 1/2"	163	<b>83p</b>
3"	2"	1"	1 1/2"	164	<b>57p</b>
8"	6"	3"	1 1/2"	166	<b>£1.08</b>
6"	4"	2"	1 1/2"	167	<b>£1.12</b>

All measurements for boxes are shown in inches L = Length W = Width H = Height

## Plastic Boxes

Coloured Black Close fitting  
Flanged Lid fixing screws into brass bushes

SIZE	L	W	H	Order No	Price
4"	2"	1 1/2"	1 1/2"	141	<b>£1.00</b>
4 1/2"	2 1/2"	1 1/2"	1 1/2"	143	<b>£1.30</b>
6"	3 1/2"	2"	1 1/2"	144	<b>£1.50</b>
Plastic as above but with aluminium top panel					
4"	2 1/4"	1"	1 1/2"	146	<b>£1.40</b>
Plastic sloping front					
5 1/2"	4 1/2"	2 1/2"	slope to 1 1/2"	148	<b>£2.14</b>

## MW398 NI-CAD CHARGER

Universal Ni-Cad battery charger All plastic case with lift up lid. Charge/Test switch LED indicators at each of the five charging points

Charges —	Power —
PP3 (9V)	220-240V AC
U12 (1.5V penlite)	0ms —
U11 (1.5V 'C')	210 x 100 x 50mm
U2 (1.5V 'O')	<b>£6.95</b>

**POWER SUPPLY OUR PRICE £3.25**  
Power supply fits directly into 13 amp socket Fused for safety Polarity reversing socket Voltage switch Lead with multi plug Input — 240V AC 50HZ Output — 3, 4, 5, 6, 7, 5, 9, 8, 12V DC. Rating — 300 ma MW88



## "IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty	Description	Price
SX10	400	Mixed All Type Resistors	£1
SX11	400	Pre-formed 1/4 watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/4 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects  
Quantities approximate count by weight

## "CAPABLE CAPACITOR PAKS"

Pak No.	Qty	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature Mixed	£1
SX18	100	Mixed Ceramics 1 of 5 of	£1
SX19	100	Mixed Ceramics 8 of 0.5 of	£1
SX20	100	Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal top	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50 1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

Quantities approximate count by weight

## AUDIO PLUGS, SOCKETS AND ACCESSORIES

**25** pieces of Audio Plugs, Sockets and Connectors to include DIN 180° 240° Inline 3-6 Pin Speakers, Phono Jack, Stereo and Mono etc etc Valued at well over £3 normal. Order No SX25 Our Price £1.50 per pak Guaranteed to save you money

SX26 3 Pcs of 6 pin 240° DIN Plugs and Chassis Sockets **50p**  
SX38 100 Silicon NPN Transistors—all perfect Coded mixed types with data and eqvt sheet No rejects. Real value **£2.50**  
SX39 100 Silicon PNP Transistors—all perfect Coded mixed types with data and eqvt sheet No rejects. Fantastic value **£2.50**

## TRIACS - PLASTIC

4 AMP — 400v — T0202 — TAG 136G	
1 OFF 10 OFF 50 OFF	100 OFF
40p	£3.75 £17.50 £30.00
8 AMP 400v — T0220 — TAG 425	
60p	£5.75 £27.50 £50.00

## Everyday Electronics

Teach-in '81  
Kit 1 **£15.65** (Kits 1 & 2 combined price **£23.00**)  
Kit 2 **£.94** price **£23.00**

*All prices include V.A.T. & postage.*

## IC SOCKETS

The lowest price ever.

The more you buy the cheaper they come!

Pin	10 off	50 off	100 off
8	75p	£3.00	£5
14	80p	£3.25	£5.50
16	80p	£3.25	£5.50

## VOLTAGE REGULATORS

T0220	Positive +	Negative +	(please state voltage required)
	7805 — 50p	7905 — 55p	
	7812 — 50p	7912 — 55p	
	7815 — 50p	7915 — 55p	
	7824 — 50p	7924 — 55p	

Other types LM340K — 6 volt — 18 volt — 24 volt  
T03 — 40p UA723 — 14 pin OIL — 40p



## MOTOROLA PIEZO ELECTRIC TWEETER

Maximum Ratings  
25 volts rms which is equal to 200 watts across 4 ohms  
100 watts across 8 ohms  
50 watts across 16 ohms  
BI-PAK SPECIAL OFFER PRICE **£4.65**  
ORDER NO 1907



## HOME TWEETER

Dome tweeter for systems up to 50w  
Impedance 8 ohms  
Frequency Response 2000-20,000Hz  
Dims. 98mm diam x 31mm deep  
Our Price **£2.85** OMT200

## BI-PAK'S COMPLETELY NEW CATALOGUE

Completely re-designed. Full of the type of components you require plus some very interesting ones you will soon be using and of course the largest range of semiconductors for the Amateur and Professional you could hope to find

There are no wasted pages of useless information so often included in Catalogues published nowadays. Just solid facts re price, description and individual features of what we have available. But remember Bi-Pak's policy has always been to sell quality components at competitive prices and THAT WE STILL DO.

BI-PAK'S COMPLETELY NEW CATALOGUE is now available to you. You will be amazed how much you can save when you shop for Electronic Components with a Bi-Pak Catalogue. Have one by you all the time—it pays to buy BI-PAK

To receive your copy send **75p** plus 25p p&p



# BI-PAK

Send your orders to Dept EE 3BI-PAK PO BOX 6 WARE HERTS.  
SHOP AT 3 BALDOCK ST. WARE HERTS.  
TERMS, CASH WITH ORDER, SAME DAY DESPATCH, ACCESS.  
BARCLAYCARD ALSO ACCEPTED. TEL. (0920) 3182 GPO 388 7006  
ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.  
Remember you must add VAT at 15% to your order.  
Total Postage add 50p per Total order

# Beginners' luck

**30% OFF**  
10 selected kits  
for first-time  
builders



Shortwave  
Listener's  
Receiver

With Heathkit, you're all set for a great deal. And not just big savings.

Whichever kit you choose, you'll find it easy to build. Simple, but detailed instructions take you through every stage. Everything is included. Even the solder you need is there.

Digital Clock



of. Because you built it yourself.

There are 10 great kits to start you off. An interesting choice of a digital clock to a metal locator, including a short wave listener's receiver, windspeed and direction indicator, digital readout electronic scale and five more useful kits.

All at 30% off to first-timers. Send for your catalogue right now for a start.



To Heath Electronics  
(UK) Limited, Dept (EE 3),  
Bristol Road, Gloucester GL2 6EE.

EE 3

To start me off, please send me a copy of the Heathkit catalogue. I enclose 28p in stamps.

Name \_\_\_\_\_

Address \_\_\_\_\_



HEATH **You build on our experience**

# HEATHKIT

## E.E. PROJECT KITS

Make us your No. 1 SUPPLIER OF KITS and COMPONENTS for E.E. Projects. We supply carefully selected sets of parts to enable you to construct E.E. projects. Kits include ALL THE ELECTRONICS AND HARDWARE NEEDED. Printed circuit boards (fully etched, drilled and roller tinned) or Veroboard are, of course, included as specified in the original article, we even include nuts, screws and I.C. sockets. PRICES INCLUDE CASES unless otherwise stated. BATTERIES ARE NOT INCLUDED. COMPONENT SHEET INCLUDED. If you do not have the issue of E.E. which includes the project—you will need to order the instruction reprint at an extra 45p each.

Reprints available separately 45p each + p. & p. 40p.

- SIMPLE STABILISED POWER SUPPLY. Jan. 82. £22-98
- MINI EGG TIMER. Jan. 82. £3-69
- SIREN MODULE. Jan. 81. less speaker. £5-21.
- MODEL TRAIN CHUFFER. Jan. 82. £7-73.
- PEGBOARD GAME. Dec. 81. 13aa nails. £6-34.
- SQUARE SIX. Dec. 81. £4-40.
- RACE TRACK SPEEDO. Dec. 81. £25-40.
- GUITAR ADAPTOR. Dec. 81. £3-52.
- REACTION METER. Dec. 81. £18-41.
- HEADS OR TAILS GAME. Dec. 81. £4-82.
- ELECTRONIC IGNITION. Nov. 81. £24-33.
- SIMPLE INFRA RED REMOTE CONTROL. Nov. 81. £15-99.
- LOUDHAILER. Nov. 81. less handle. £11-93.
- HORN SPEAKER. £6-75 extra.
- PRESSURE MAT TRIGGER ALARM. Nov. 81. £5-86 less mats.
- EXPERIMENTER CRYSTAL SET. Nov. 81. Less aerial. £5-60. Headphones. £2-98 extra.
- CAPACITANCE METER. Oct. 81. £21-98.
- SUSTAIN UNIT. Oct. 81. £11-93.
- 'POPULAR DESIGNS'. Oct. 81.
- SNAP INDICATOR. £3-18.
- DAMP LOCATOR. £1-51.
- TAPE NOISE LIMITOR. £4-28.
- HEADS AND TAILS GAME. £2-36.
- CONTINUITY TESTER. £3-70.
- PHOTO FLASH SLAVE. £3-24.
- FUZZ BOX. £4-82.
- OPTO ALARM. £8-34.
- SOIL MOISTURE UNIT. £5-43.
- ICE ALARM. £7-38.
- MODEL RAILWAY SPEED CONTROLLER. Sept. 81. £13-46.
- 0-12V POWER SUPPLY. Sept. 81. £16-84
- CMOS CAR SECURITY ALARM. Sept. 81. £8-49.
- CMOS DIE. Sept. 81. £7-47.
- LEO SANDGLASS. Aug. 81. £7-98.
- WHEEL OF FORTUNE. Aug. 81. less wire, panel and case. £39-98.
- CMOS METRONOME. Aug. 81. £7-70.
- COMBINATION LOCK. July 81. Less case. £18-30.
- BURGLAR ALARM SYSTEM. June 81 less bell, loop & Mic's. £38-30.
- TAPE AUTO START. June 81. £11-96.
- TREMELO. June 81 less case. £10-48.
- LOOP AERIAL CRYSTAL SET. June 81. £5-47.
- LIGHTS REMINDER AND IGNITION LOCATOR E.E. May 81. £5-29.
- SOIL MOISTURE INDICATOR E.E. May 81. £3-83.
- T.V. INTERFERENCE FILTERS E.E. May 81. LOW PASS less tinplate £2-88. HIGH PASS £1-56.
- GUITAR HEADPHONE AMPLIFIER E.E. May 81. £3-96.
- PHONE BELL REPEATER/BABY ALARM E.E. May 81. £5-29.
- DIGITAL RULE (ultrasonic) April 81. £30-20
- INTERCOM. April 81. £20-76.
- SIMPLE TRANSISTOR & DIODE TESTERS. Mar. 81. Ohmmeter version £1-89. Led version £2-56.
- MINI SIREN. Mar. 81. £7-52.
- LED DICE. Mar. 81. £7-89.
- LED FLASHER. Mar. 81. £4-01.
- MODULATED TONE DOORBELL. Mar. 81. £6-21.
- BENCH POWER SUPPLY. Mar. 81. £49-98.
- TREBLE BOOST. Mar. 81. £6-84.
- CAR ACTUATED DRIVEWAY LIGHT. Feb. 81 less socket. £23-90.
- THREE CHANNEL STEREO MIXER. Feb. 81. £17-47.
- SIGNAL TRACER. Feb. 81. £7-64 less probe.
- FOUR BAND RADIO. Feb. 81. £39-98.
- NI-Cd BATTERY CHARGER. Feb. 81. £12-72.
- ULTRASONIC INTRUDER DETECTOR. Jan. 81 less case. £49-98.
- AUTO SLIDE CHANGER. Jan. 81. £9-28.
- LOGIC PULSE GENERATOR. Jan. 81. £7-48.
- 2 NOTE DOOR CHIME. Dec. 80. £9-65.
- LIVE WIRE GAME. Dec. 80. £16-94.
- GUITAR PRACTICE AMPLIFIER. Nov. 80. £11-99 less case. Standard case £3-88. High quality case £8-33.
- SOUND TO LIGHT. Nov. 80. 3 channel. £19-95.
- TRANSISTOR TESTER. Nov. 80. £10-87 inc. test leads.
- AUDIO EFFECTS UNIT FOR WEIRD SOUNDS. Oct. 80. £12-26.
- PHONE CALL CHARGE JOGGER. Oct. 80. £6-80.
- BICYCLE ALARM. Oct. 80. £9-68 less mounting brackets.
- IRON HEAT CONTROL. Oct. 80. £5-48.
- BEDSIDE RADIO. Sept. 80. £17-57.
- TTL LOGIC PROBE. Sept. 80. £4-85.
- COURTESY LIGHT DELAY. June 80. £6-89.
- SIGNAL TRACER. June 80. £5-99.
- ZIGBAG DIODE TESTER. June 80. £8-23.
- 4 STATION RADIO. May 80. £15-33 less case.
- LIGHTS WARNING SYSTEM. May 80. £4-38.
- BATTERY VOLTAGE MONITOR. May 80. £4-63.
- CABLE & PIPE LOCATOR. Mar. 80. £3-85 less coil former.
- KITCHEN TIMER. Mar. 80. £13-70.
- STEREO HEADPHONE AMPLIFIER. Mar. 80. £18-97.
- GROU MUSIC BOX. Feb. 80. £15-20. Grey Case £3-99 extra.
- SIMPLE SHORT WAVE RECEIVER. Feb. 80. £24-17. Headphones £2-96.
- SLIDE/TAPE SYNCHRONISER. Feb. 80. £11-50.
- MORSE PRACTICE OSCILLATOR. Feb. 80. £4-32.
- SPRING LINE REVERB. UNIT. Jan. 80. £24-17.
- UNIBOARD BURGLAR ALARM. Dec. 79. £5-64.
- BABY ALARM. Nov. 79. £8-98.
- ONE ARMED BANDIT. Oct. 79. £24-60.
- HIGH IMPEDANCE VOLTMETER. Oct. 79. £17-45.
- CHASER LIGHTS. Sept. 79. £21-97.
- SIMPLE TRANSISTOR TESTER. Sept. 79. £6-88.
- ELECTRONIC TUNING FORK. Aug. 79. £9-99. Suitable microphone & plug £1-79 extra.
- DARKROOM TIMER. July 79. £2-71.
- ELECTRONIC CANARY. June 79. £4-58.
- TRANSISTOR TESTER. April 79. £4-55.
- TOUCH BLEEPER. April 79. £3-67.
- ONE TRANSISTOR RADIO. Mar. 79 less case £7-62.
- MICROCHIME DOORBELL. Feb. 79. £14-82.
- THYRISTOR TESTER. Feb. 79. £3-54.
- ADJUSTABLE PSU. Feb. 79. £31-87.
- HEADPHONE ENHANCER. Jan. 79. £2-16.
- MIC. AMP. Dec. 78. £3-08.
- AUDIBLE FLASHER. Dec. 78. £1-33.
- VEHICLE IMMOBILISER. Inc. PCB. Dec. 78. £6-31.
- FUSE CHECKER. Oct. 78. £2-10.
- TREASURE HUNTER. Oct. 78. £19-64 less handle & coil former.
- SOUND TO LIGHT. Sept. 78. £7-87.
- CAR BATTERY STATE INDICATOR. Sept. 78. Less case. £1-96.
- R.F. SIGNAL GENERATOR. Sept. 78. £24-98.
- SLAVE FLASH. Aug. 78. £3-52 less SK1.
- IN SITU TRANSISTOR TESTER. June 78. £6-33.
- POCKET TIMER. April 78. £3-27.
- WEIRD SOUND EFFECTS GENERATOR. Mar. 78. £5-28.
- AUDIO VISUAL METRONOME. Jan. 78. £5-63.
- ELECTRONIC TOUCH SWITCH. Jan. 78. £2-56 less case.
- RAPID DIODE CHECK. Jan. 78. £2-57.
- AUTOMATIC PHASE BOX. Dec. 77. £11-50 inc. p.c.b.
- PHONE/DOORBELL REPEATER. July 77. £6-98.
- ELECTRONIC DICE. Mar. 77. £5-31.

LATEST KITS: S.A.E. OR 'PHONE FOR PRICES

### GUITAR TUNER—SUPERB PROJECT

Featured by us in E.T.I. Jan. 82. Highly stable internal reference. Microprocessor generates fundamental frequencies. Special synchronous rectifier circuit compares input frequency from guitar pickup or microphone with internally generated pitch. Beat frequency is displayed on a large moving coil panel meter. Also operates with bass guitar, or acoustic instruments via a high impedance microphone.

Complete kit includes smart case, pcbs, panel meter etc. £28-00. Reprint extra 45p. Available separately 45p + 40p & p.

## TEACH IN 82

**NEW SERIES—ALL COMPONENTS IN STOCK NOW FOR FAST DELIVERY.** All top quality components as specified by Everyday Electronics. Our kit comes complete with **FREE COMPONENT IDENTIFICATION SHEET.** Follow this educational series and learn about electronics—Start today.

Send £24.98 for List 1, 2. VERO/E.E. £1.00 vouchers accepted. **WOODEN CASE KIT** also available. £11.68—wood, formica, glue, screws etc. Cut to size. **IDEAL SOLDERING EQUIPMENT FOR THE TEACH IN AND ELECTRONICS**

- |                              |                          |
|------------------------------|--------------------------|
| ANTEX X5 SOLDERING IRON      | DESOLDER BRAID 69p       |
| 25W £5.48                    | HEAT SINK TWEEZERS 29p   |
| SOLDERING IRON STAND         | DESOLDER PUMP £8.48      |
| £2.40                        | SOLDER CARTON £1.84      |
| SPARE BITS. Small standard,  | LOW COST CUTTERS £1.89   |
| large. 65p each. For X5+X25. | LOW COST LONG NOSE       |
| SOLDER. Handy size 99p.      | PLIERS £1.68             |
| HOW TO SOLDER LEAFLET        | WIRE STRIPPERS & CUTTERS |
| 12p                          | £2.69                    |

C106D 58p	2N5457 58p	BFY51 24p	LINEAR I.C.s	SN75477 £2.59
TIC48 48p	2N5484 63p	BFY52 23p	555 26p	TL064 £1.64
OA47 11p	40673 98p	BFX88 32p	556 72p	TL071 47p
OA90 9p	AC128 28p	BRY39 48p	741 22p	TL082 74p
OA202 16p	AC141 38p	MPSA65 38p	CA3130E 98p	TL083 £1.52
W005 33p	AC142 38p	RPY5A £1.18	CA3140E 52p	TL084 £1.54
W06 47p	AC178 37p	TIP31A 52p	HA1388 £3.20	TL430 95p
Z5J £2.92	BC182 11p	TIP32A 83p	ICL7611 88p	U237B £1.69
IN4001 54p	BC182L 11p	TIP33A 94p	ACM7555 99p	U267B £2.20
IN4005 6p	BC183 11p	TIP34A 99p	LF351N 56p	ULN2283 £1.57
IN4148 5p	BC184 11p	TIP121 £1.12	LF353N 99p	ZN414 98p
IN5404 11p	BC184L 11p	TIP2955 89p	LF355 £1.14	ZN419CE £2.21
IN5408 11p	BC212 11p	TIP3055 38p	LF356 £1.15	7400 22p
BF244 87p	BC212L 11p	TIS43 38p	LM301A 36p	7447 £1.14
MPF102 69p	BC213 11p	TPSA13 35p	LM317K £3.20	7490 55p
TIS88A 57p	BC214 11p	SN3053 25p	LM335Z £1.16	7495 80p
VN87AF £1.21	BC214L 11p	2N3055 59p	LM380N 82p	CMOS
2N3819 28p	BD131 48p	2N3702 11p	LM386N 99p	4001 20p
2N3820 78p	BFY50 25p	2N3704 11p	LM387N £1.10	4011 20p
			LM389N £1.10	4013 32p
			LM1830 £1.98	4017 62p
			LM3909 82p	4020 65p
			LM3914 £2.99	4024 60p
			LM3915 £3.95	4069 28p
			MC3340 £2.15	4081 20p
			NE570N £4.98	4092 38p
			NE571N £4.84	40174 £1.20
			OM335 £4.98	4522 £1.25

**±1% CARBON FILM RESISTORS**  
E12 SERIES. 1R-10M 14p each  
MIN. HORIZ. PRESETS. 100F-4M7. 12p each  
MIDGOT POTS. LINEAR. 470R-4M7 37p each  
LOG. 4K7-2M3. 39p  
SWITCHED POTS. 4K7-1M. LIN. 75p. LOG 76p

**POLYESTER (C280) CAPACITORS, 250V**  
10nF; 15nF; 22nF; 33nF; 47nF 7p each. 68nF; 100nF 11p. 150nF; 220nF 12p. 330nF 15p. 470nF 20p. 680nF 28p. 1µF 33p. 1.5µF 48p. 2.2µF 65p.

**SUB MINIATURE PLATE CERAMICS, 63V**  
Values in pF: 2.2; 3.3; 4.7; 5.6; 6.8; 8.2; 10; 15; 22; 33; 47 & 56pF 7p each. 68pF; 100pF 7p each. 150pF; 220pF; 330pF 11p each. 390pF; 470pF; 1000pF 5p each. 2200pF 8p each. 3300pF; 4700pF 7p each. 10nF 13p. 100nF 22p. 47nF 14p.

**ELECTROLYTIC CAPACITORS**  
AXIAL Leads: 1µF/16V 11p; 1µF/33V, 1µF/100V 12p; 2.2µF/63V, 3.3µF/63V, 4.7µF/63V 12p; 10µF/16V 11p; 10µF/25V, 10µF/33V 12p; 22µF/10V, 22µF/15V 12p; 22µF/63V 15p; 33µF/40V, 47µF/25V 12p; 47µF/40V 15p; 47µF/63V 18p; 100µF/16V 12p; 100µF/25V 15p; 100µF/33V 18p; 100µF/50V 29p; 220µF/10V 15p; 220µF/25V 19p; 470µF/16V 29p; 470µF/25V 34p; 470µF/40V 35p; 800µF/16V 32p; 1000µF/10V 39p; 1000µF/16V 33p; 1000µF/25V 48p; 1000µF/40V 58p; 1000µF/63V 78p; 2200µF/10V 39p; 2200µF/25V 64p; 2200µF/63V £1.10.

**SWITCHES**  
MIN. TOGGLE spst 58p; spdt 69p; dpdt 78p.  
MIN. PUSH ON. 18p. PUSH OFF. 22p.  
FOOTSWITCH & ALT. ACTION spco £1.39; dpco £1.88.

**ROTARY SWITCHES.** 1p 12 way, 2p 8w, 3p 4w, 4p 3w 42p each. 89p each. 12V 185R DPCO RELAY £2.98

**SPEAKERS.** Miniature, 8 ohm 87p  
84-75 ohm 89p  
**CRYSTAL EARPIECE** 65p  
**MONO HEADPHONES** £2.98  
**TELEPHONE PICK-UP COIL** 72p

**PP3 CLIPS** 19p  
**PANEL METERS.** 60 x 45mm, 50µA, 100µA, 1mA, 1A, 25V £4.99 each  
**VEROBOARD 9" x 1" COPPER.** 10 strips, 24 holes £1.20 per 5  
245 37H, 78p. 245 50H, 89p. 385 37H, 89p. 385 50H, 99p.  
**TERMINAL PINS** 44p/100  
**PIN INSERTION TOOL** £1.69  
**SPOT FACE CUTTER** £1.23

**PCB ETCHING KIT** £4.98  
**PLASTIC TWEEZERS** 69p  
**EUROBREADBOARD** £6.20  
**BIMBOARD 1** £6.48  
**S. DEC** £3.98  
**VEROBLOC** £3.98

**MULTIMETER TYPE 1.** 1,000 opv with probes £6.99  
**MULTIMETER TYPE 2.** 2,000 opv with transistor tester £14.79  
**CROC CLIP TEST LEAD SET.** 10 leads with 20 clips 99p  
**CONNECTING WIRE PACK.** 5 x 5yd coils 65p  
**RESISTOR COLOUR CODE CALCULATOR** 21p

**OPTO**  
BPX25 .....£2.24  
2N5777 .....60p  
ORP12 .....99p  
TIL32 .....61p  
TIL78 .....74p

**LEDS WITH CLIPS**  
3mm. Red 15p. Green 18p. Yellow 20p.  
5mm. Red 18p. Green 28p. Yellow 29p.

**FLASHING LED** 78p  
**RECTANGULAR. Red** 58p  
**MAINS PANEL. Neon** 32p

**ZENER DIODES.** 400mW.  
BZY88. Range 2V7 to 33V. 12p each.

**I.C. SOCKETS**  
8 pin. ....18p 18 pin. ....22p  
14 pin. ....17p 24 pin. ....48p  
16 pin. ....18p 28 pin. ....45p

**JACKSON**  
300pF dilecon .....£2.36  
500pF dilecon .....£2.92  
C804 Ver. Capac. 10pF £2.28  
25pF £2.48. 50pF £2.48. 100pF £2.83. 150pF £3.48.  
'01' 365pF £3.48. '02' 365pF £4.48  
'02' 208 + 176pF £3.98.

**MIN. BUZZERS.** 6V. 50p. 9V. £1.10.  
12V. 85p.  
**MAGNETIC EARPIECE** 15p  
**STEREO HEADPHONES** £4.35  
**F.M. AERIAL** 49p

### BOOKS

- |   |       |
|---|-------|
| SEMICONDUCTOR DATA BOOK. Newnes.....  | £5.80 |
| MICROPROCESSORS FOR HOBBYISTS. R. Coles.....  | £3.65 |
| PRACTICAL ELECTRONIC PROJECT BUILDING. Ainslie & Colwell.....   | £3.35 |
| CONSTRUCTOR'S PROJECT BOOKS.....  | £3.35 |
| ELECTRONIC GAME PROJECTS. Rayer.....  | £3.35 |
| ELECTRONIC PROJECTS FOR HOME SECURITY. Bishop.....  | £3.35 |
| ELECTRONIC PROJECTS IN AUDIO. Penfold.....  | £3.35 |
| ELECTRONIC PROJECTS IN MUSIC. Flind.....  | £3.35 |
| ELECTRONIC PROJECTS IN PHOTOGRAPHY. Penfold.....  | £3.35 |
| ELECTRONIC PROJECTS IN THE CAR. George.....   | £3.35 |
| PROJECTS IN AMATEUR RADIO & SHORT WAVE LISTENING. Rayer.....  | £3.35 |
| PROJECTS IN RADIO AND ELECTRONICS. Sinclair.....  | £3.35 |
| ELECTRONIC PROJECTS IN HOBBIES. Rayer.....  | £3.35 |
| ELECTRONIC PROJECTS IN THE HOME. Bishop.....  | £3.35 |
| ELECTRONIC PROJECTS IN THE WORKSHOP. Penfold.....   | £3.35 |
| ELECTRONIC TEST EQUIPMENT PROJECTS. Ainslie.....  | £3.35 |
| MORE ELECTRONIC PROJECTS IN THE HOME. Flind.....  | £3.35 |
| 110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR.....   | £3.35 |
| ELECTRONIC PROJECTS—PAPERMAC.....   | £4.35 |
| COST EFFECTIVE PROJECTS AROUND THE HOME. Watson.....  | £4.35 |
| PROJECTS FOR THE CAR AND GARAGE. Bishop.....  | £5.40 |
| AUDIO CIRCUITS AND PROJECTS. Bishop.....  | £4.35 |
| TEST GEAR PROJECTS. Dixon.....  | £1.95 |
| ELECTRONIC CIRCUITS FOR MODEL RAILWAYS. Penfold.....  | £1.30 |
| SOLID STATE SHORT WAVE RECEIVERS FOR BEGINNERS. Penfold.....  | £1.30 |
| BEGINNERS GUIDE TO BUILDING ELECTRIC PROJECTS. Penfold.....   | £1.35 |
| ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING. Berry.....  | £1.90 |
| IC555 PROJECTS. Parr.....   | £1.90 |
| BASIC ELECTRONICS—BOOKS 1-5.  |       |
| Superb set of books covering theory and practice. Educational. Suit age 14 upwards. Lots of useful projects—circuits built on an S-Dec breadboard. Sold as a set of 5 books. £11.98 |       |

## ADVENTURES WITH MICROELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering. Uses a Bimboard 1 breadboard, gives clear instructions with lots of pictures. 11 projects based on integrated circuits—includes dice, two-tone doorbell, electronic organ, MW/LW radio, reaction timer, etc. Component pack includes a Bimboard 1 breadboard and all the components for the projects. Adventures with Microelectronics £2.55. Component pack £29.84 less battery.

## ADVENTURES WITH ELECTRONICS

by Tom Duncan

An easy to follow book suitable for all ages. Ideal for beginners. No soldering, uses an S-Dec breadboard. Gives clear instructions with lots of pictures. 16 projects—including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-Dec breadboard and all the components for the projects. Adventures with Electronics £2.40. Component pack £17.98 less battery.

MAGENTA gives you FAST DELIVERY OF QUALITY COMPONENTS & KITS. All products are stock lines and are new & full specification. We give personal service & quality products to all our customers—HAVE YOU TRIED US?

## MAGENTA ELECTRONICS LTD.

EV37, 135 HUNTER ST. BURTON-ON-TRENT, STAFFS., DE14 2ST. 0283 65435. MON.-FRI. 9-5. MAIL ORDER ONLY. ADD 40p P. & P. TO ALL ORDERS. Normal despatch by return of post. OFFICIAL ORDERS WELCOME. IRISH REPUBLIC & S.F.P.O. EUROPE. Oduct 10% from prices shown Payment. must be in Sterling. ACCESS and BARCLAYCARD (VISA) ORDERS ACCEPTED BY PHONE OR POST. SEE ALL ENQUIRES.



### TRAIN SET ACCESSORIES

#### MODEL RAILWAY SPEED CONTROLLER

From E.E. Sept. Features fully variable speed control—from zero to full speed. Forward/reverse switch. Auto start and stop for realism. Brake and speed boost. Emergency stop. Use with the simple controller supplied with most train sets. Housed in an attractive 2 tone sloping front case. Built on a printed circuit board. All parts included. Kit £13.44. Reprint/instructions extra 45p.

#### TRAIN SOUNDS—from H.E.

STEAM LOCO WHISTLE Mar 81.....£12.26 inc case  
TWO TONE TRAIN HORN Feb 81.....£5.24 less case  
CHUFFER Jan 81.....£7.64 less case  
All 3 can be built into the whistle project case—or built as separate units.

### BOOK—MODEL RAILWAY PROJECTS

by Penfold £1.95. Published Sept. 81.

### MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST  
Price list included with orders or send see (9 x 4)  
CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

### 1982 ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 70p in stamps or add 70p to order.

MORE E.E. KITS PLUS H.E. and E.T.I. PROJECT KITS IN THE PRICE LIST.


Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

# Sparkrite

## BRANDEADING ELECTRONICS NOW AVAILABLE IN KIT FORM


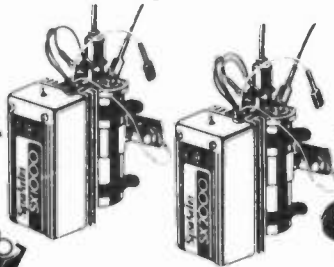
### SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




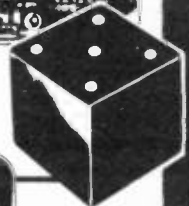
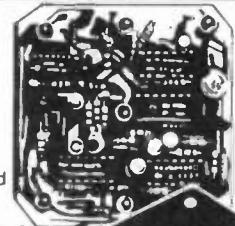
### MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble


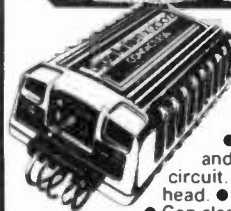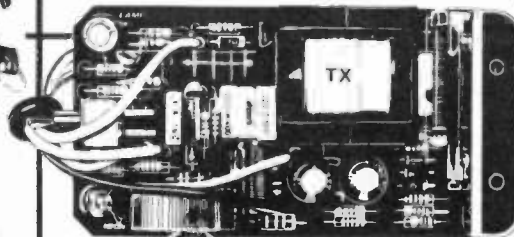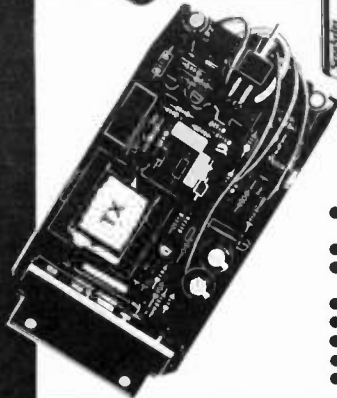
### SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




### TX2002 Electronic Ignition

- The ultimate system ● Switchable contactless. ● Three position switch with Auxiliary back-up inductive circuit.
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included.
- Can also be triggered by existing contact breakers.
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles.
- Over 150 components to assemble


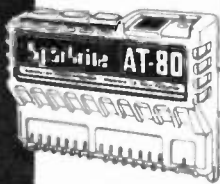
### VOYAGER Car Drive Computer

- A most sophisticated accessory. ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously.
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1%. ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble.
- A real challenge for the electronics enthusiasts!


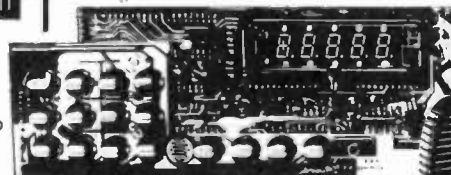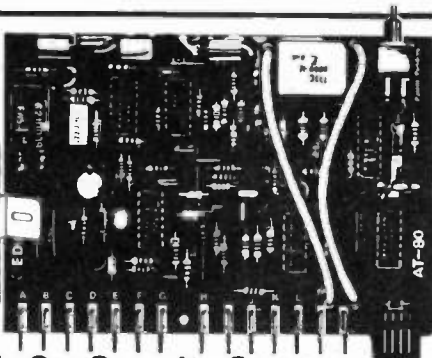
### AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble



All EDA-SPARKRITE products and designs are fully covered by one or more World Patents.

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

Please allow 28 days for delivery

NAME \_\_\_\_\_ EE3.82  
ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO. \_\_\_\_\_  
24 hr. Answerphone  
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD  
SEND ONLY SAE IF BROCHURE IS REQUIRED

	SELF ASSEM. KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

BRANDEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!

# Everyday ELECTRONICS

VOL. 11 NO. 3 MARCH 1982

**Editor**

F. E. BENNETT

**Assistant Editor**

B. W. TERRELL B.Sc.

**Production Editor**

D. G. BARRINGTON

**Technical Sub-Editor**

G. P. HODGSON

**Art Editor**

R. F. PALMER

**Assistant Art Editor**

P. A. LOATES

**Technical Illustrator**

D. J. GOODING Tech. (CEI)

**Secretary**

JACQUELINE DOIDGE

**Editorial Offices**

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

Phone: 01-261 6873

**Advertisement Manager**

R. SMITH

Phone: 01-261 6671

**Representative**

R. WILLETT

Phone: 01-261 6865

**Classified Supervisor**

B. BLAKE

Phone: 01-261 5897

**Make-Up and Copy Department**

Phone: 01-261 6615

**Advertisement Offices**

KINGS REACH TOWER

STAMFORD STREET

LONDON SE1 9LS

## A MATTER OF INTEREST

Popular interest in electronics has grown steadily over the past years. It's a true, if trite, expression—but what do we mean by *interest*? Well, there is the superficial interest arising from a general awareness that electronics is responsible somehow or another for much of the improved standard of life now enjoyed by most people. Then there is the more profound interest that extends beyond the fascia and the user controls, and involves a technical appreciation of the circuitry and components that make the whole thing tick. Finally there is the really dedicated interest that manifests itself through active participation in designing and building electronic units and equipment.

A noteworthy point is that, of the many thousands of people who come within the second and third categories just defined, the greater number will be largely self-taught in electronic matters and will have no professional involvement with this technology.

To readers of this magazine this is not likely to be a startling revelation. Yet these facts are worth advertising, especially today when hobbies assume greater importance than perhaps ever before, because of social/economic changes affecting people in all kinds of industry and business. Unwished-for leisure unfortunately is in abundance for three million fellow citizens. There are others also with time on their hands, including disabled persons and those in retirement, to consider.

It is clear that hobbies like electronics are no longer to be seen merely as pleasurable pastimes to while away spare time; they now also serve an essential and more serious purpose in keeping minds and hands occupied in the absence of full time employment. (There are gloomy predictions that the shortage of jobs will become a permanent feature of our society in the years ahead.)

Considered in this context, the attractiveness of electronics soon becomes obvious: convenient and not unduly demanding in outlay (electronic components must represent one of the best values for money these days), with an endless variety of useful projects that can be built. But most important of all for some of those victims of current economic policies will be the basic training for a new career that can be derived from a "pastime" such as this.



**Readers' Enquiries**

We cannot undertake to answer readers' letters requesting modifications, designs or information on commercial equipment or subjects not published by us. All letters requiring a personal reply should be accompanied by a stamped self-addressed envelope.

We cannot undertake to engage in discussions on the telephone.

**Component Supplies**

Readers should note that we do not supply electronic components for building the projects featured in EVERYDAY ELECTRONICS, but these requirements can be met by our advertisers.

All reasonable precautions are taken to ensure that the advice and data given to readers are reliable. We cannot however guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.

**Back Issues**

Certain back issues of EVERYDAY ELECTRONICS are available worldwide price 80p inclusive of postage and packing per copy. Enquiries with remittance should be sent to Post Sales Department, IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF. In the event of non-availability remittances will be returned.

**Binders**

Binders to hold one volume (12 issues) are available from the above address for £4.40 (home) £4.55 (overseas) inclusive of postage and packing. Please state which Volume.

**Subscriptions**

Annual subscription for delivery direct to any address in the UK: £11.00. Overseas: £12.00. Cheques should be made payable to IPC Magazines Ltd., and sent to Room 2613, Kings Reach Tower, Stamford Street, London SE1 9LS.

ON THE WING

# camera OR flash gun trigger



BY R.A. PENFOLD

WITH some types of action photography it is impossible for a human operator to act fast enough to take a satisfactory photograph. It is then necessary to use some form of automatic triggering of the camera or a flashgun in order to obtain a fast enough response time to take the photograph before the subject moves out of frame.

A sound triggered flash unit is a common example of an automatic triggering device of this type, and a number of designs have been published in the technical press in the past. This is not the only type of automatic trigger though, and sound triggered flash units are unsuitable for certain types of action photography.

For example, a sound triggered flash is unlikely to be usable for photographs of insects or birds in flight. This type of action photograph is normally taken with the aid of a broken light beam trigger unit, and a trigger of this type can also be used for other types of action photography.

## BROKEN LIGHT BEAM

The trigger unit described in this article is of the broken light beam type, and it can be used to operate either a flashgun or a camera. Of course, the camera can only be triggered by the unit if it is a type having an electro-magnetic shutter release which a suitable trigger cord is available, or if the camera is equipped with an automatic winder or motor drive which has a remote control socket.

The prototype has been tested with a Minolta XD7 (which is triggered directly) and with a Pentax LX (which is operated via the auto-winder) and worked perfectly with both of these. Automatic operation is possible with most modern S.L.R. cameras, and the unit should function properly with any that have this facility. It should also work properly with any normal electronic flashgun.

The accompanying photographs give some examples of the type of shot that can be taken with the aid of this unit.

## BLOCK DIAGRAM

Fig. 1 shows the basic arrangement of the trigger unit in block diagram form, and as can be seen from this there are actually two units in the system; the transmitter and the receiver. The unit uses a pulsed infra-red beam rather than a steady visible light beam, and the only reason for employing this system is that it gives improved reliability.

A d.c. coupled visible light system would be susceptible to spurious triggering due to changes in ambient light level and shadows falling on the sensor, even if precautions were taken against this. A steady beam with an a.c. coupled receiver seems to be just as susceptible to spurious operation as a simple d.c. circuit.

## TRANSMITTER OSCILLATOR

The system finally adopted has proved to be 100 per cent reliable, and attempts to induce spurious operation proved to be fruitless. The

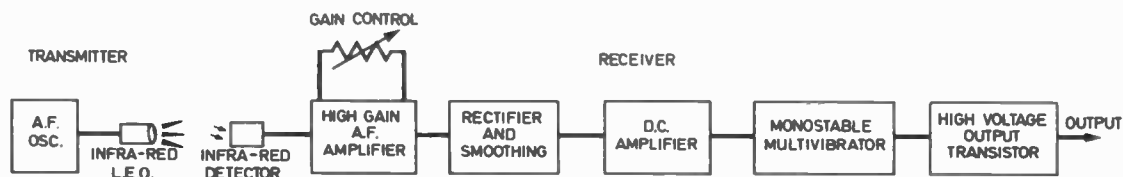


Fig. 1. Block diagram of the Camera/Flash Trigger.

transmitter is just an oscillator operating at a frequency of a few kilohertz and driving an infra-red l.e.d. so that the beam of light from the transmitter is actually a series of brief infra-red pulses.

Although of no practical significance, it should perhaps be pointed out that there is no visible light output from the l.e.d. because infra-red radiation cannot be seen by human vision, and there is no significant output from an infra-red l.e.d. at the shorter wavelengths of the visible light spectrum.

## RECEIVER

The receiver uses an infra-red photodiode to detect the infra-red pulses, and as the diode has a built-in infra-red filter it does not respond to other types of light.

The voltage pulses produced by the photodiode circuit are quite small, being probably no more than a few millivolts even if the system is used at short range. A high gain audio amplifier is therefore used to boost these pulses to a few volts peak to peak, and they are then fed to a rectifier and smoothing circuit which produces a strong d.c. signal.


This signal is used to operate a monostable multivibrator via a d.c. amplifier stage, and the monostable is normally held in the off state.

If the beam is momentarily broken a number of pulses will be prevented from reaching the receiver, causing the d.c. output of the smoothing circuit to rapidly decay and trigger the monostable. The monostable then produces an output pulse of a little over one second in duration which is used to switch on a high voltage power transistor which operates the camera or flashgun.
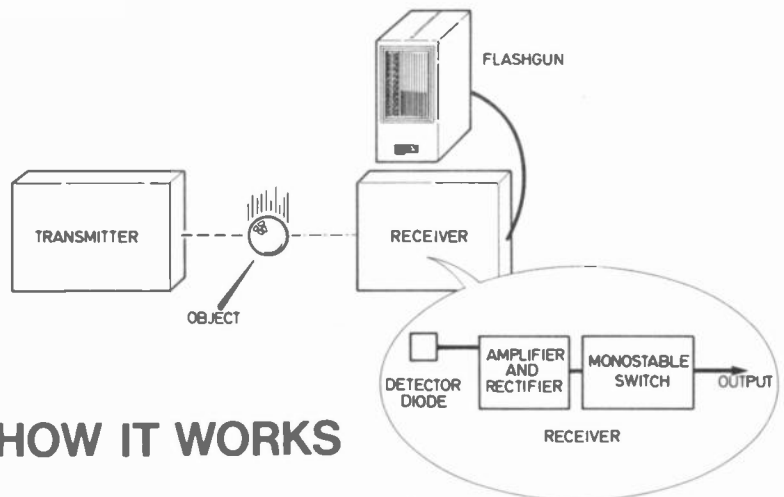
## POWER TRANSISTOR

It is necessary to use a high voltage power device at the output since the unit will need to handle a high voltage when used with an electronic flashgun, and fairly high currents when operating a camera via an auto-winder or motor drive. The output pulse of the monostable is longer than is absolutely necessary, but the relatively long output pulse length helps to avoid unwanted multiple operations of the flashgun or camera (especially when photographing insects which sometimes fly along the beam).

A gain control is fitted in the amplifier section of the receiver, and this is adjusted so that the infra-red beam produces a signal which only just prevents the unit from triggering under normal conditions. This helps to give the unit a fast response time and enables quite small and fast-moving objects to trigger the receiver.



## HOW IT WORKS

The transmitter merely consists of an oscillator driving an infra-red l.e.d. so that a rapid series of brief infra-pulses are produced. These pulses are normally picked-up by a detector diode at the receiver which converts the received infra-red pulses into minute voltage pulses. An amplifier and rectifier circuit processes this signal to produce a strong d.c. bias which normally holds a monostable circuit in the off state.

If the infra-red beam is momentarily broken (as by a passing object) the pulse signal is briefly lost, and the d.c. bias rapidly subsides so that the receiver monostable is triggered. This operates the flashgun (or camera) via a switching transistor, and automatically takes a photograph of the object which broke the beam.

## TRANSMITTER CIRCUIT

The circuit of the transmitter is shown in Fig. 2, and this part of the unit is based on the popular 555 timer device used in the astable mode. This device is ideal for this application since it has a fairly high output current capability and can provide the required rectangular pulse output waveform.


The values of R1 and R2 set the mark space ratio of the output signal at about 5.5 to one, so that infra-red l.e.d. D1 is switched off for more than 80 per cent of the time, and switched

on for less than 20 per cent of the time. This enables strong pulses of current to be applied to D1 but keeps the current consumption of the circuit down to a reasonable level.
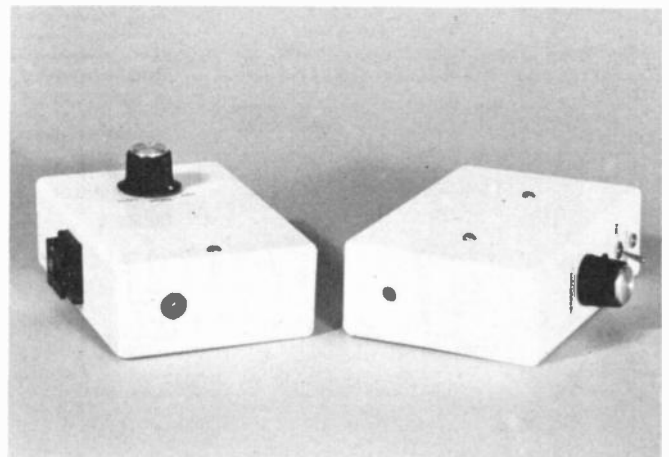
## HIGH/LOW POWER

S1 is the on/off switch, and it additionally enables two output powers to be obtained. In the "high" position R4 is switched in as the current limiting resistor for D1, and this gives an l.e.d. current of over 100mA and an average current consumption of

The completed transmitter and receiver. The mounting adaptor can be seen on the side of the transmitter.



# INFRA-RED TRANSMITTER

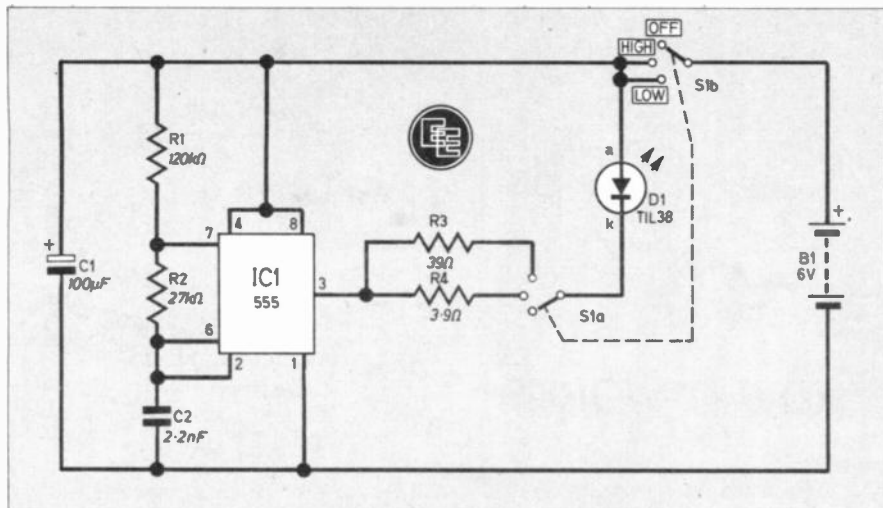


Fig. 2. Camera/Flash Trigger: transmitter circuit.

## COMPONENTS

### Resistors

- R1 120kΩ
- R2 27kΩ
- R3 39Ω
- R4 3.9Ω
- All 1/4W carbon ±5%

See  
**Shop  
Talk**  
page 171

### Capacitors

- C1 100µF 10V elect.
- C2 2.2nF ceramic plate

### Semiconductors

- IC1 555 timer i.c.
- D1 TIL38 infra-red i.e.d.

### Battery

- B1 Four AA (HP7) size batteries and plastic holder to suit PP3 type battery connector

### Switch

- S1 3-way 4-pole rotary

### Miscellaneous

- Plastic box about 114 × 76 × 38mm (type PB1 or similar); 0.1in. matrix stripboard, 13 strips × 15 holes; control knob; panel holder for D1; tripod bush; wire, solder.

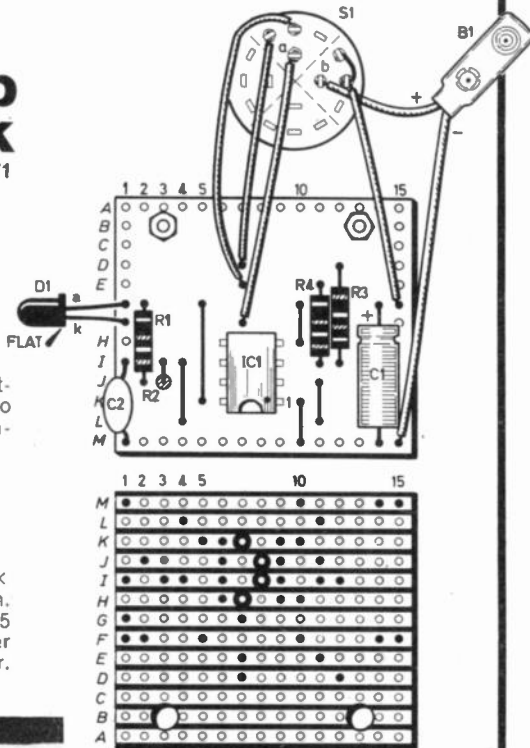
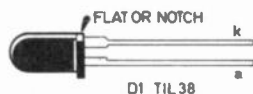


Fig. 3. Constructional details of the transmitter.

**COMPONENTS**  
approximate  
cost **£3.50**

approximately 38mA. This produces a maximum operating range of about 2 metres which is often far greater than is needed. In such cases S1 is switched to the "low" position and this gives a maximum range of a little under one metre with an i.e.d. current and average current consumption of about 11mA.

C2 sets the operating frequency of IC1 at around 5 to 6kHz, and C1 is the supply decoupling capacitor. Power is obtained from four AA (HP7) size batteries which gives a nominal 6 volt supply.

**CONSTRUCTION**  
starts here

## TRANSMITTER CONSTRUCTION

The transmitter components can be housed in a plastic box measuring about 114 × 76 × 38mm. S1 is mounted on the removable lid of the case, at one end, leaving space for the batteries and the component panel at the other end of the case.

The component panel is a 0.1in matrix stripboard which has 13 copper strips by 15 holes, and Fig. 3 provides details of this board and the wiring of the transmitter.

The board is constructed in the usual manner. Start by cutting out a board of the specified size, drill the two 6BA clearance (3.2mm diameter) mounting holes, make the four breaks in the copper strips, and finally solder in the components and link wires leaving IC1 and D1 until last.


The leadout wires of D1 are not trimmed, so that with the component board bolted to the base panel of the case D1 can be fitted into a panel holder mounted in one end panel of the case.

Complete the wiring to S1 and the battery clip before finally installing the component panel.

The battery clip is a PP3 type, and this connects to the output terminals of a plastic battery holder which is used to connect the four AA size batteries in series. The prototype is powered from NiCad cells which are almost certain to be the most economical power source in the long term, but the circuit can be powered from ordinary HP7 cells if preferred.
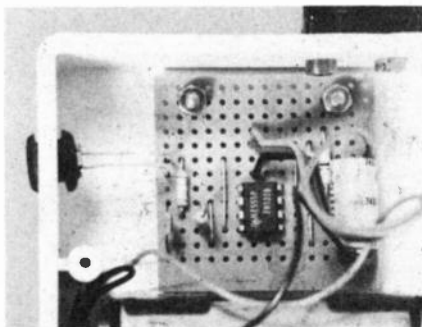
## MOUNTING BUSH

It is useful to fit the case with a tripod mounting bush, and a suitable bush can be taken from a flash





adaptor of the type used to fit a flash-gun on a tripod.

The two rivets are drilled out so that the top and bottom sections of the adaptor can be separated, and the base section is then bolted to the case by fitting the bolts through the holes which were formerly occupied by the rivets. The unit can then be mounted on an accessory shoe or on a tripod since the adaptor has an accessory foot as well as a standard  $\frac{1}{4}$ in tripod bush.

## RECEIVER CIRCUIT

The circuit diagram of the receiver is given in Fig. 4.

D1 is the photodiode and it is reverse biased by R1. The infra-red pulses from the transmitter produce an increase in the leakage current of D1, giving a series of small negative pulses at the junction of R1 and D1. These pulses are coupled by C2 to a straight forward common emitter amplifier based on TR1, and the output of TR1 is coupled by C3 to a volume control type variable attenuator, VR1.

The signal is then taken to a second common emitter amplifier TR2 by C4. C5 attenuates the high frequency response of the second common emitter stage slightly, and this is done in order to prevent instability.

C6 couples the output of TR2 to a rectifier and smoothing circuit which is comprised of D2, D3 and C7. Under normal conditions this produces a negative bias which is strong enough to bias TR3 into conduction so that its collector terminal is at virtually the positive supply potential.

## MONOSTABLE



The monostable is a conventional 555 i.c. type, and R7 plus C8 set the output pulse duration at a nominal 1.1 seconds.

In order to trigger IC1 its input at pin 2 must be taken below one third of the supply voltage, and this will happen if the input to the unit ceases even briefly as the charge on C7 will then rapidly decay and TR3 will switch off.

R8 then takes pin 2 of IC1 to the negative supply voltage, and the positive output pulse is produced at pin 3 of IC1. This switches on TR4 as it receives a heavy base current via R9; the large base current being necessary to ensure a low voltage drop across the collector-emitter terminals of TR4.

Indicator D4 is also switched on when IC1 is triggered, and this is helpful when setting the unit up ready for use.

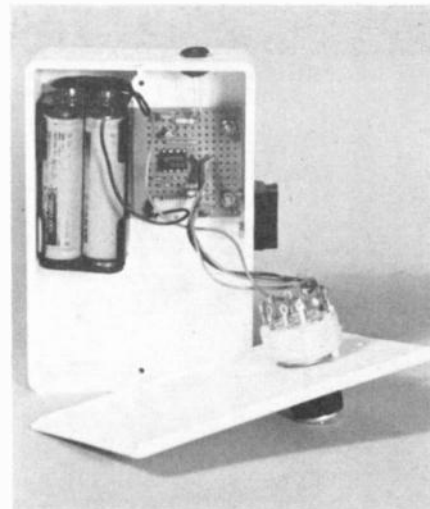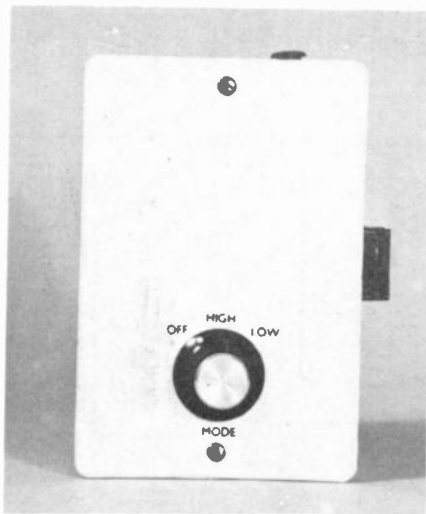The current consumption of the unit is about 9mA under stand-by conditions, and around 55mA during the



The transmitter—exterior and interior views.

output pulses from IC1. A NiCad PP3 is used to power the prototype, but an ordinary PP3 is also a suitable power source.



## RECEIVER CONSTRUCTION

The receiver uses the same type of case as the transmitter, and the general layout of the unit can be seen from the accompanying photographs. VR1, D4, S1, and SK1 are mounted on one of the 114x38mm sides of the case which then becomes



the top panel of the unit. A tripod bush is fitted on the base panel of the case.

Fig. 5 shows the component layout of the 0.1in matrix stripboard panel which accommodates the other components except the battery. The board has 15 strips by 30 holes and it is constructed using the normal techniques.

The leadouts wires of D1 are left long so that with the board mounted in the case, D1 can be positioned with its sensitive surface behind a hole about 6 or 7mm in diameter drilled in the case. The sensitive surface is the large one which does not carry the type number of the device.

Fig. 5 shows the wiring to the off-board components, and this is all perfectly straightforward apart from the connections to SK1 which must have the correct polarity if the unit is to function properly.

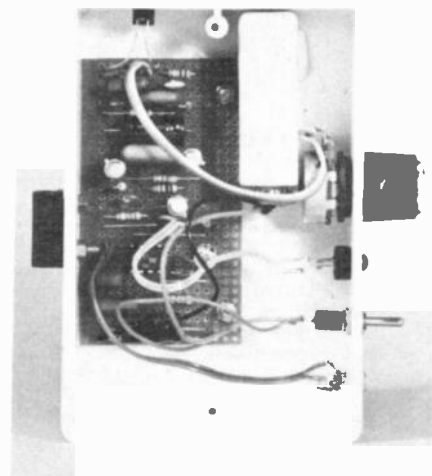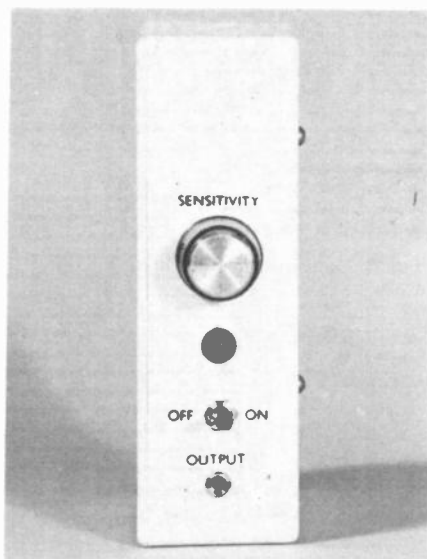The receiver—exterior and interior views.



# INFRA-RED RECEIVER

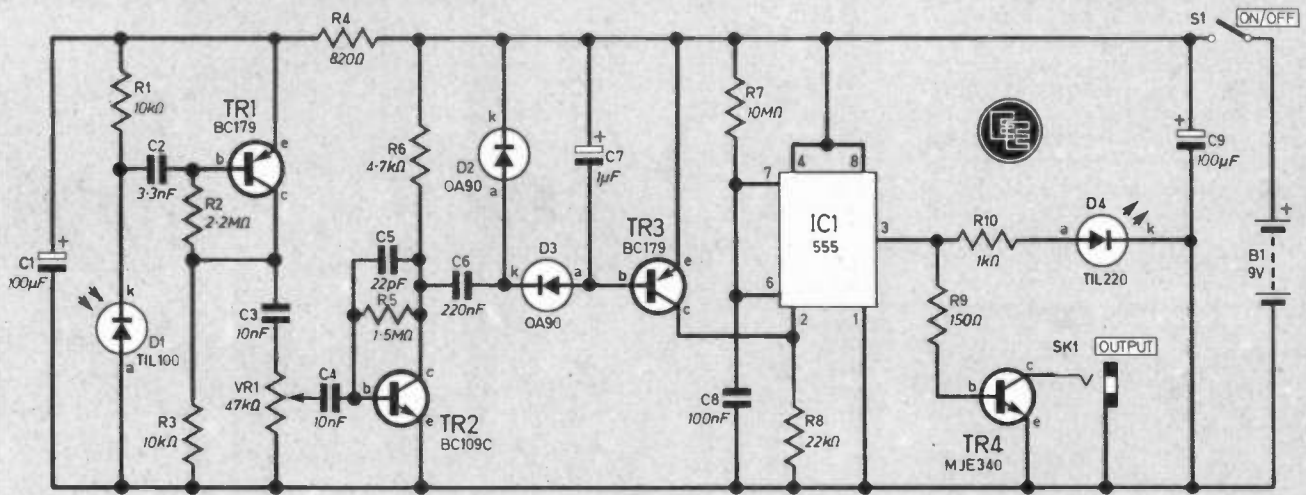


Fig. 4. Camera/Flash Trigger: receiver circuit.

## COMPONENTS

### Resistors

- R1 10k $\Omega$
  - R2 2.2M $\Omega$
  - R3 10k $\Omega$
  - R4 820 $\Omega$
  - R5 1.5M $\Omega$
  - R6 4.7k $\Omega$
  - R7 10M $\Omega$
  - R8 22k $\Omega$
  - R9 150 $\Omega$
  - R10 1k $\Omega$
- All  $\frac{1}{2}$ W carbon  $\pm 5\%$

### Potentiometer

- VR1 47k $\Omega$  log. carbon

### Capacitors

- C1 100 $\mu$ F 10V elect.
- C2 3.3nF ceramic plate
- C3 10nF polyester (C280)
- C4 10nF polyester (C280)
- C5 22pF ceramic plate
- C6 220nF polyester (C280)
- C7 1 $\mu$ F 63V elect.
- C8 100nF polyester (C280)
- C9 100 $\mu$ F 10V elect.

### Semiconductors

- IC1 555 timer i.c.
- TR1 BC179 *pnp* silicon
- TR2 BC109C *nnp* silicon
- TR3 BC179 *pnp* silicon
- TR4 MJE340 *nnp* silicon plastic power transistor
- D1 TIL100 infra-red photo-diode
- D2 OA90 germanium diode
- D3 OA90 germanium diode
- D4 TIL220 0.2in. red l.e.d.

### Battery


- B1 PP3 battery and connector to suit

### Switch


- S1 S.P.S.T. miniature toggle type
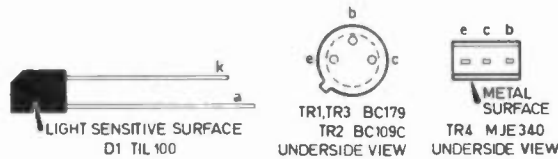
### Miscellaneous

- Plastic box about 114 x 76 x 38mm (type PB1 or similar); 0.1in. matrix stripboard, 15 strips x 30 holes; control knob; panel holder for D4; output lead; tripod bush; wire, solder; 2.5mm jack socket (SK1).



COMPONENTS  
approximate  
cost £6.50

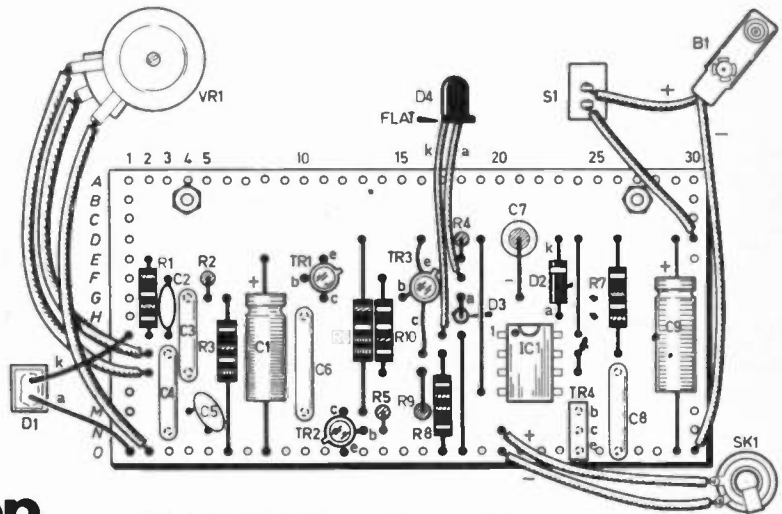

See  
**Shop  
Talk**  
page 171

**Erratum**  
Break at L9 is  
not required.


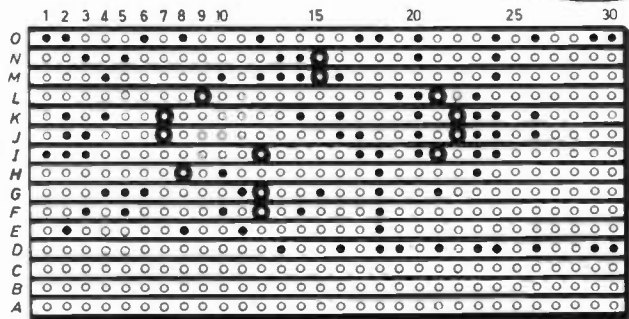


Fig. 5. Constructional details of the receiver.

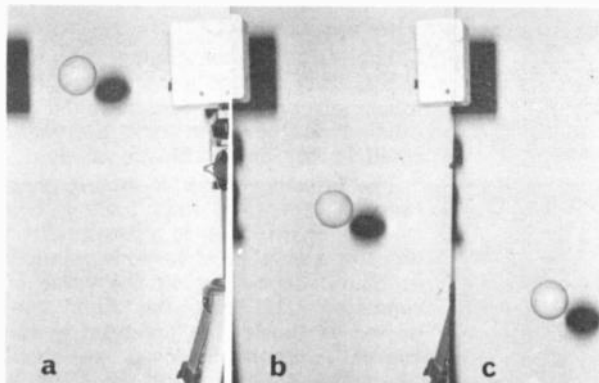

(a) The dropped ball photographed by triggering the flashgun. (b) There is a small delay if the camera is triggered and the mirror lock-up is used. (c) A longer delay is evident if the mirror lock-up is not used.



Water splash created by dropped marble.

## FLASHGUN CONNECTION

If the unit is to be used with a flashgun this can be connected to the receiver via a flash extension lead having the normal plug removed, and a 2.5mm jack plug fitted instead. With this plug connected to SK1 and the flashgun switched on, a voltmeter set to read 250 volts or more at full scale deflection can be used to check the polarity of the voltage across SK1. With the plug removed, the two leads from the component panel are connected to SK1 accordingly.

If the unit is to be used to operate a camera or winder, a remote control lead of the appropriate type can be used to make the connections to the receiver. The push-button switch is removed from the lead and replaced with a 2.5mm plug which connects with SK1. As before, a multimeter (set to the 10 volt d.c. range in this case) is used to check the polarity of the voltage across SK1 so that the leads from the component panel can be connected with the correct polarity.

An alternative method of making the connections from the camera or winder to the receiver is to use the appropriate lead for the "Kenlock Beacon" remote control device. These leads are ready-fitted with a 2.5mm jack plug.

If the unit is to be used with a flashgun and a camera or winder, make sure that all the leads are connected with the right polarity.

## USING THE SYSTEM

The exact set-up used must obviously depend upon the type of shot being taken, but the transmitter and receiver must be carefully arranged so that the object to be photographed breaks the beam at the correct point in the frame, and in the plane of perfect focus.

With many shots it is possible to simply have the beam running straight across in front of the camera with transmitter and receiver units just out of frame. In other cases it may be better to have the receiver

unit mounted on a flash bracket at the side of the camera and angled across in front of the lens, with the transmitter mounted on a tripod and sited on the other side of the camera just out of frame.

When dropping objects through the beam it is usually quite easy to ensure that they break the beam at the correct point, but with insects the standard method is to use a simple tapering flight tunnel to guide the insect to the correct point.

The beam from the transmitter should be reasonably accurately aimed towards the detector at the receiver, and S1 of the transmitter should only be set to the "high" position if inadequate range is obtained with it set to the "low" position.


The l.e.d. indicator on the receiver switches on each time the unit is triggered, and glows continuously if the two units are too far apart or VR1 of the receiver is backed-off too far. Do not be tempted to back-off VR1 to the point where the unit barely has sufficient range as this will give poor reliability by making the unit prone to spurious triggering. Advancing VR1 slightly from this point will not seriously reduce sensitivity and will give good reliability.

## FLASHGUN OPERATION


As the accompanying test shots show, the system has a virtually instant response time if it is used to trigger the flashgun. The disadvantage of this system is that it is necessary to open the shutter (using the "B" or "T" setting), activate the system, and then close the shutter. The photograph must be taken under fairly dark conditions so that the ambient light does not ruin the shot.
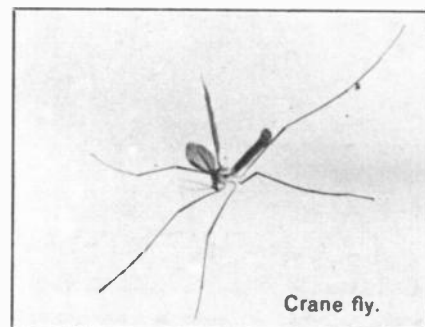
## CAMERA OPERATION

Using the unit to operate the camera or winder is more convenient since the ambient light level is no more of a problem than with normal flash photography. There is typically



Crane fly.

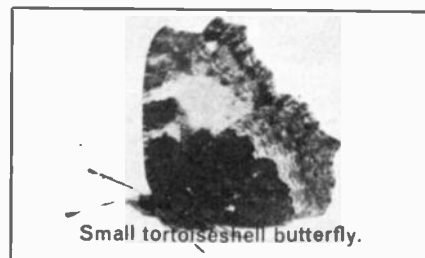


Small tortoiseshell butterfly.

a delay of about a tenth of a second before the flash fires which can sometimes be awkward, but is often of no real consequence and can even be used to advantage with some types of shot. The delay can be substantially reduced using the "mirror lock-up" on cameras that have this feature.

Most electronic flashguns give a flash duration of about 0.5 to 1 millisecond, which is short enough to "freeze" most action. Sometimes a shorter flash duration is needed, and this can be obtained using an automatic flashgun close to the subject, or using a manual flashgun having a variable power control which is set well back. This typically gives a flash duration of only about 0.05 to 0.1 milliseconds which is short enough to "freeze" virtually any action.

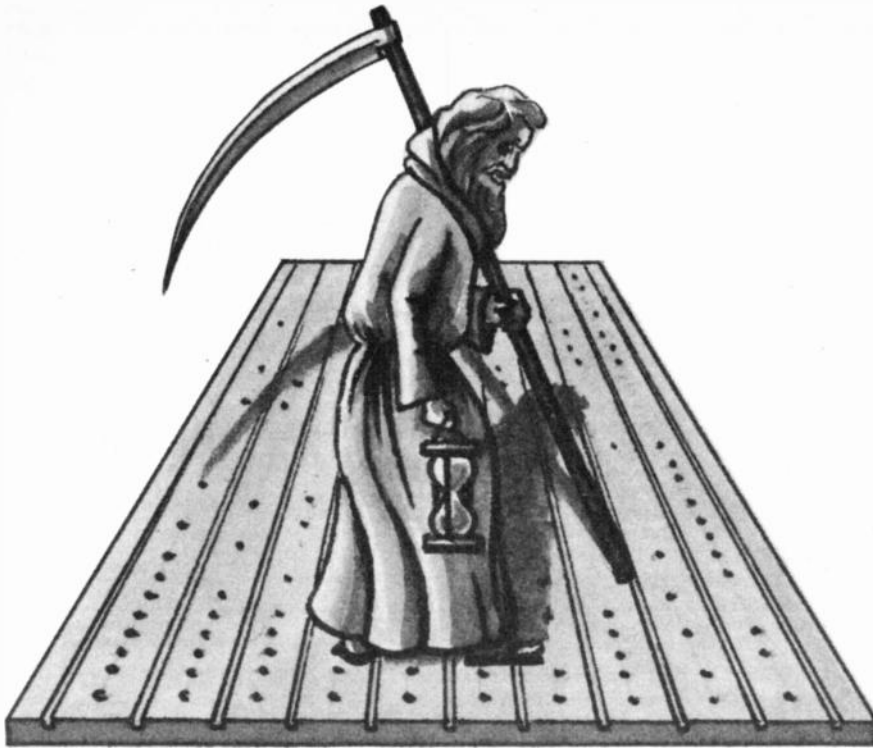One final point is that it is advisable not to connect the receiver to the camera or auto-winder (if this method is used) before switching on the receiver and transmitter as this could lead to unwanted triggering of the system. Similarly, switching off the transmitter and receiver before disconnecting the lead to the camera or auto-winder could produce an unwanted triggering. □



# POCKET TIMER

A project for your FREE piece of stripboard

THIS pocketable fixed-period timer employs only two active semiconductor devices yet, by a suitable choice of timing capacitor, can be made to cover periods ranging from a few seconds to several hours.

It has many applications such as timing moves in games, an egg timer or a parking-meter reminder.

Tucked in the top pocket of a jacket or shirt, it is inconspicuous, yet the warning lamp is easily visible in that particularly sensitive region at the edge of your field of vision.

## CIRCUIT DESCRIPTION

The circuit diagram for the Pocket Timer is shown in Fig. 1 and uses a field effect transistor, TR1, and silicon controlled switch, CSR1.

From the moment the circuit is switched on, the f.e.t. generates a slowly rising potential at its source terminal. When this potential reaches a predetermined value it triggers CSR1, which switches on the warning light, D1.

The slowly rising potential is a consequence of the slow rise of gate potential. This rises slowly because of the extremely small current that flows into the gate of an f.e.t. The smallness of the gate current also has the important consequence that we can use a timing capacitor of relatively low value.

Maximum time required	Value of C1
4 minutes	10,000pF
50 minutes	0.033μF
3 hours	0.22μF

## TIMING CAPACITOR

The value of the timing capacitor is less than 1μF, so we can use silver mica, polycarbonate, tantalum bead or other types of capacitors; these are small in size and stable in value.

The effective drain to-source resistance of the f.e.t. falls from a few kilohms at switch-on to a few hundred ohms in a number of seconds, minutes or hours, depending on the value of capacitor C1. With the f.e.t. connected as shown, the potential at the source is about 3.5V at switch-on when the resistance of the f.e.t. is somewhat greater than that of R1. As the resistance of the f.e.t. falls, the potential across it falls in proportion, giving a correspondingly greater potential-drop across resistor R1. In short, the potential of the source gradually rises from around 3.5V towards 9V. The exact values obtained depend on the characteristics of the individual f.e.t. used.

The potential at the source is too high for triggering CSR1, which needs only about 0.4V at its *gk* terminal. The variable resistor VR1 thus acts as a variable attenuator and sufficient current can be drawn from this to trigger CSR1.


By varying the setting of VR1 we can adjust the time at which triggering occurs, over a limited range, see Table 1 for C1 value.

## ASSEMBLY

The recommended layout of the components on the stripboard is shown in Fig. 2. The piece of stripboard given free with this issue will need to have two tracks cut from it to allow it to fit inside the specified case with the PP3 battery.

Drill the case end to accommodate D1 and S1. Fit the latter. The wires

Fig. 1. Circuit diagram for the Pocket Timer.

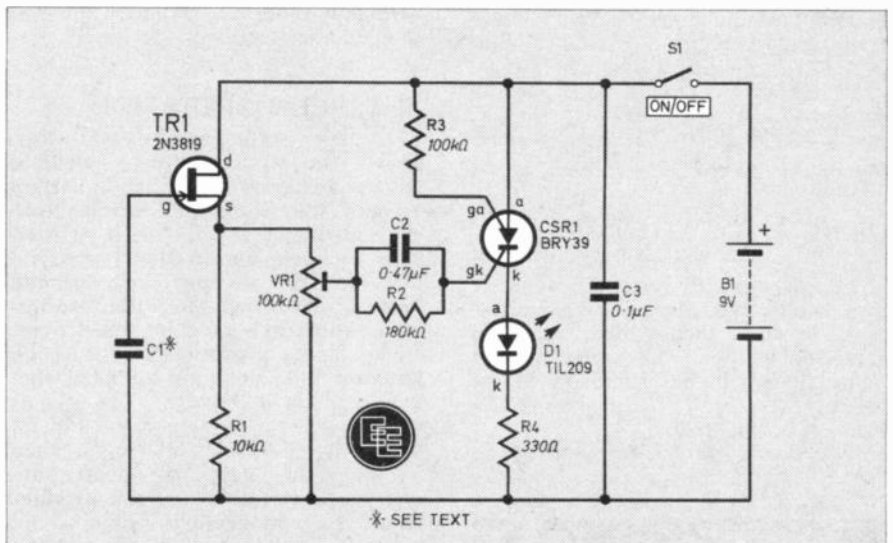

on D1 will need to be extended by soldering on about 25mm of insulated stranded wire. Use sleeving to cover the connection. Make the necessary breaks along the tracks on the underside of the board using a spot face cutter or small drill bit.

Assemble the components according to Fig. 2 leaving the semiconductors until last. Wire up the battery connector and switch. The l.e.d. can now be fitted in its clip on the case and wired to the board. A little foam sponge either side of the board in the case will hold it steady alongside the PP3 battery.

## TESTING AND ADJUSTING

Set VR1 fully anticlockwise and switch on. With *gk* of CSR1 thus grounded, the l.e.d. should not light. Switch off and set VR1 fully clockwise and switch on. With the potential at the wiper at 3.5 volts, the l.e.d. should light immediately.

Switch on and off, gradually moving the wiper of VR1 anticlockwise. After switching off after each test allow about 10 seconds before switching on again, as charge stored on the capacitors may cause unwanted and premature triggering of CSR1. This delay between switching off and on

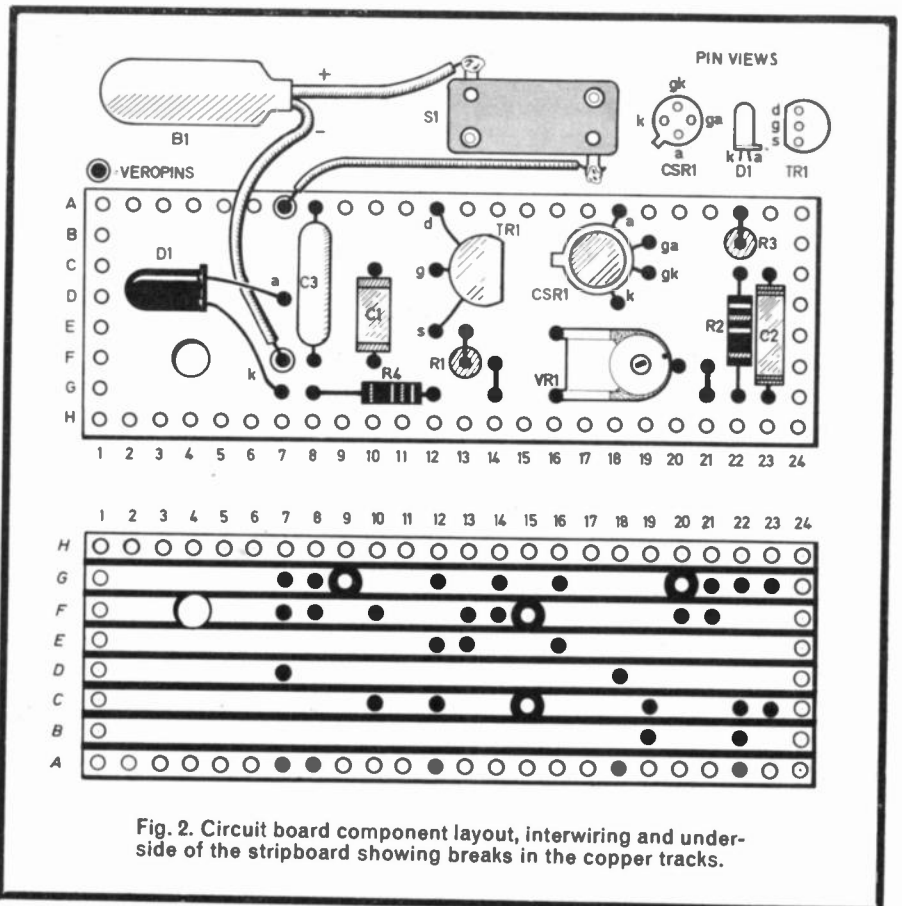


Fig. 2. Circuit board component layout, interwiring and underside of the stripboard showing breaks in the copper tracks.

## COMPONENTS

### Resistors

- R1 10k $\Omega$
- R2 180k $\Omega$
- R3 100k $\Omega$
- R4 330 $\Omega$
- All  $\frac{1}{2}$ W carbon  $\pm 10\%$

page 171

### Potentiometer

- VR1 100k $\Omega$  sub-miniature horizontal preset

### Capacitors

- C1 See Table 1
- C2 0.47 $\mu$ F polyester
- C3 0.1 $\mu$ F polyester

### Semiconductors

- TR1 2N3819 *n*-channel f.e.t.
- CSR1 BRY39 silicon controlled switch
- D1 TIL209 red light emitting diode

### Miscellaneous

- B1 9V PP3 battery
- S1 s.p.s.t. toggle switch
- Stripboard 0.1 inch matrix, 8 strips by 24 holes; battery clip; Veropins as required; Vero General Purpose plastic box type 202-21025K or similar size, 70 x 50 x 25mm; connecting wire; solder.

£2.60

See  
**Shop  
Talk**

should also be observed in use when operating the device.

You will eventually find a position at which the l.e.d. does not light at switch-on. The timer is now set for its minimum period of operation.

You may find that the l.e.d. flashes once at switch-on, due to current surges, but this can be ignored. It is best to approach a maximum setting gradually, testing and timing at each step, for if VR1 is turned too far, the potential of its wiper never reaches the triggering threshold.

## THE TIMER IN USE

Whilst running, the average current consumption of the circuit is only about 1mA, so a PP3 battery will provide many hours of use. However, once the l.e.d. has been triggered, current consumption increases to 20mA or more, so the unit should be switched off as soon as the warning has been noted.

This is not a precision timer. High precision is too much to expect from such a simple circuit. For periods within the range up to one hour, its reliability seems to be better than 5 per cent, which is more than adequate for the applications that have been mentioned.

If you are using it for periods in excess of one hour it is probably just

as well to adjust it to run for a slightly shorter time than you actually require. For a two-hour period, for example, adjust it to trigger at around 1 hour 50 minutes. This gives you time to spot the warning lamp and still get down to the parking meter in good time to avoid the wrath of the traffic warden. ☘

## PLEASE TAKE NOTE

### Capacitance Meter (October 1981)

In Fig. 2, page 692, move one end of resistor R12 from point H13 to I13 and one end of R13 from G17 to H17.

### Cine Interval Timer and Frame Counter (February 1982)

Readers using the relay remote operation circuit, Fig. 2, should insert a protection diode across the relay coil.

A suitable type is the 1N4148, the cathode (k) should connect to the +9V line and the anode (a) to the coil/collector junction.

# EE

# TEACH-IN 82

**PART 6**  
BY O.N. BISHOP



## BASIC ELECTRONIC THEORY WITH EXPERIMENTS CAPACITORS AND PULSE GENERATORS

**B**EFORE we go on to discuss this month's main topic, we shall consider the subject of capacitors.

### CAPACITORS

A capacitor consists of two plates of metal with an insulating layer (the dielectric) between them, see Fig. 6.1. Dielectrics include plastic film, mica, waxed paper and air.

In Fig. 6.2a the positive terminal of the cell attracts electrons from one plate, leaving it positively charged. The positive charge attracts electrons from the negative terminal. Currents flow until the p.d. between the plates is equal to the e.m.f. of the cell (Fig. 6.2b). The capacitor is now charged.

Note that a current flows out of one plate and an equal current flows into the other plate. *In effect*, a current has passed around the circuit even though there is a layer of insulating material in it.

The cell may now be removed from the capacitor (Fig. 6.2c). Capacitors store electrical charge. Though the charge may be conducted away slowly through the air or through the dielectric, a capacitor stores charge for several hours.

In Fig. 6.3a plate *X* is at 4.7V, *Y* is 3.3V. There is a p.d. of 1.4V between them. This circuit is perfectly stable. Suppose that for an instant point *A* is connected to the 6V line (Fig. 6.3b). The increased potential at *A* attracts electrons from *X*, giving it a potential of 6V. *X* attracts more electrons into *Y*. The capacitor maintains the 1.4V p.d. between its plates.

An increase of 1.3V at *X* brings about an increase of 1.3V at *Y*. Its potential increases to 3.3 + 1.3 = 4.6V. This attracts electrons from *B* to plate *Y*. By the time this has happened the brief pulse at *A* will probably have ended. Potential at *A* returns to 4.7V, electrons flow from *X* to *A*, potential at *Y* returns to 3.3V, electrons flow from *B* to *Y*. Everything is now as it was before.

The effect of these events is that a brief high pulse at *A* has appeared as a brief

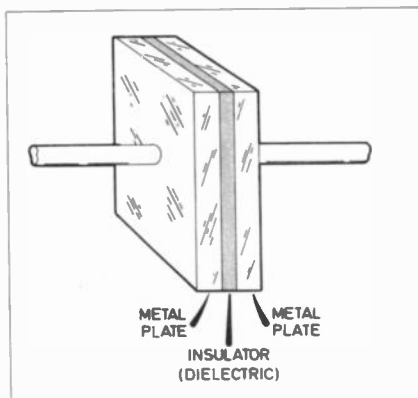


Fig. 6.1. A simple parallel plate capacitor

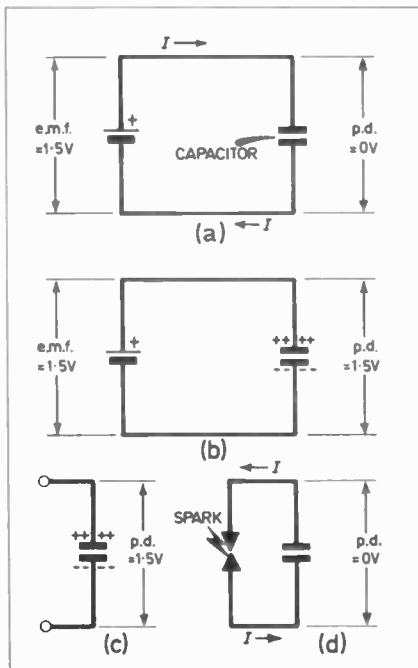


Fig. 6.2. Charging and discharging a capacitor; *I* shows direction of conventional current flow.

high pulse at *B*, just as if *A* and *B* were connected by a wire. In effect, the capacitor might just as well not be there so far as a pulse is concerned.

### COUPLING WITH CAPACITORS

In Fig. 6.4 the microphone produces an e.m.f. of only a few tens of millivolts. The potential at terminal *A* alternates between about +100mV and -100mV and its average is 0V.

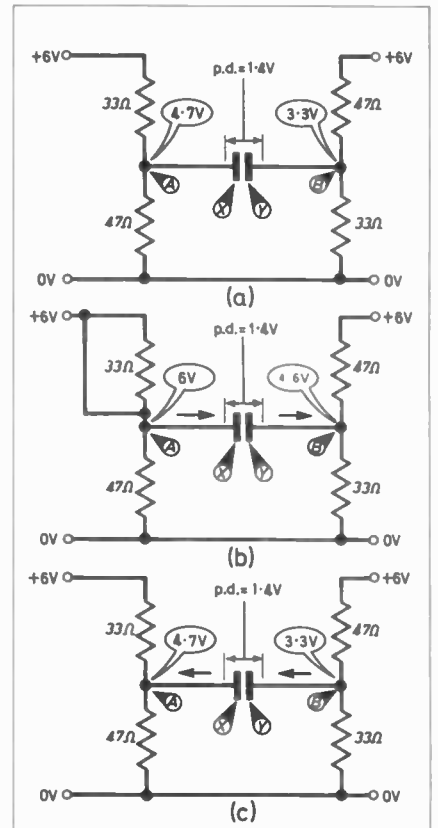


Fig. 6.3. Using a capacitor to couple two parts of a circuit: (a) steady d.c. conditions (b) pulse applied at *A* passes to *B* (c) after pulse passes. Arrows indicates direction of conventional current flow.

The transistor is biased by R4 and its base is at 0.6V, as is plate Y. With no sound there is a p.d. of 0.6V between X and Y. This is just the same as in Fig. 6.3: we have a steady p.d. across the capacitor. As before, the capacitor acts to maintain this p.d. For example, an increase of 20mV at X (from 0V to 0.02V), causes an equal increase at Y (from 0.6V to 0.62V). The capacitor is used to couple the microphone to the transistor.

It has a steady but different potential on either plate, yet transmits a varying or alternating potential from one place to the other. In other words, it does not pass d.c. potentials but readily passes a.c. potentials. The loudspeaker in Fig. 6.4 is another example of capacitive coupling.

The by-pass capacitor in last month's stabilised amplifier is used to maintain a steady potential at the emitter. Any attempt to change the p.d. between emitter and the 0V rail is resisted. Alternating voltages at the emitter are readily passed through the capacitor to the 0V line, where they are lost.

## CAPACITANCE

If a capacitor stores  $Q$  coulombs of charge when the p.d. between its plates is  $V$  volts, its **capacitance** is defined as:

$$\text{Capacitance, } C = Q/V \text{ coulombs per volt}$$

The unit for "coulombs per volt" is called the farad (symbol F). This unit is too large for practical purposes. We use its sub-multiples, such as the microfarad ( $1\mu\text{F} = 10^{-6}\text{F}$ ), the nanofarad ( $1\text{nF} = 10^{-9}\text{F}$ ) and the picofarad ( $1\text{pF} = 10^{-12}\text{F}$ ).

Capacitance depends on various factors, such as the area of the plates (larger area gives greater  $C$ ), the distance between them (closer together gives greater  $C$ ), and the

kind of material used as dielectric. Most types of capacitor have several interleaving plates, giving a large area in a compact form, see Fig. 6.5a. Some have the plates rolled with a sheet of plastic between them as shown in Fig. 6.5b.

The aluminium electrolytic capacitors, Fig. 6.5c, have relatively large capacity. They are physically larger than most other

types and have rolled plates. The surfaces of the plates are roughened to increase the surface area even more.

The plates are separated by a sheet of paper soaked in an electrolyte paste. This layer is conductive. It is not a dielectric but is effectively part of a plate. In manufacture a p.d. is applied to the plates causing a very thin layer of aluminium

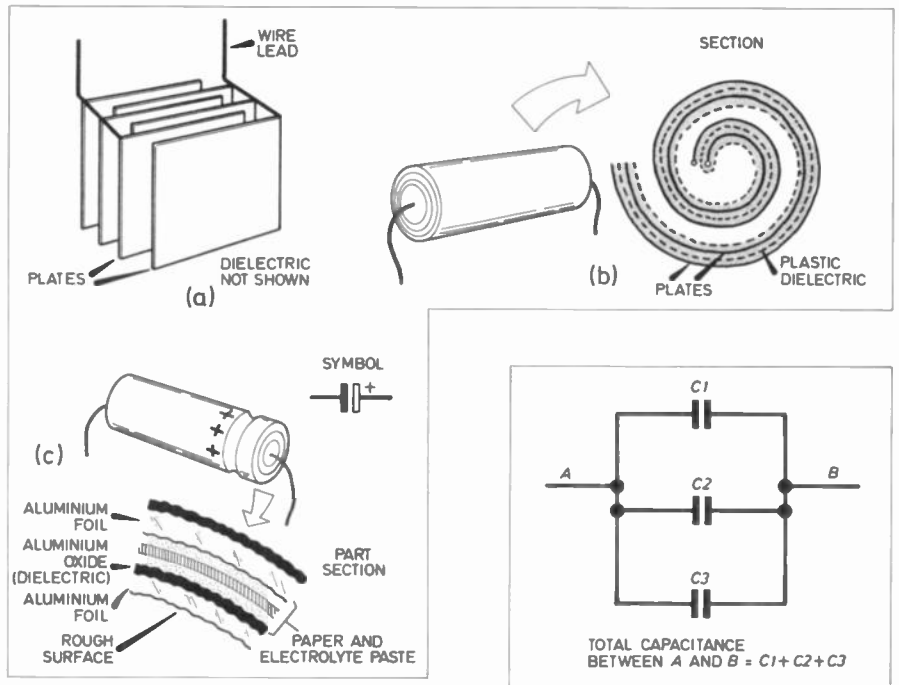


Fig. 6.5. Types of capacitor: (a) parallel plates as in polyester capacitors (b) rolled plates as in polystyrene capacitors (c) aluminium electrolytic polarised capacitor and its circuit symbol.

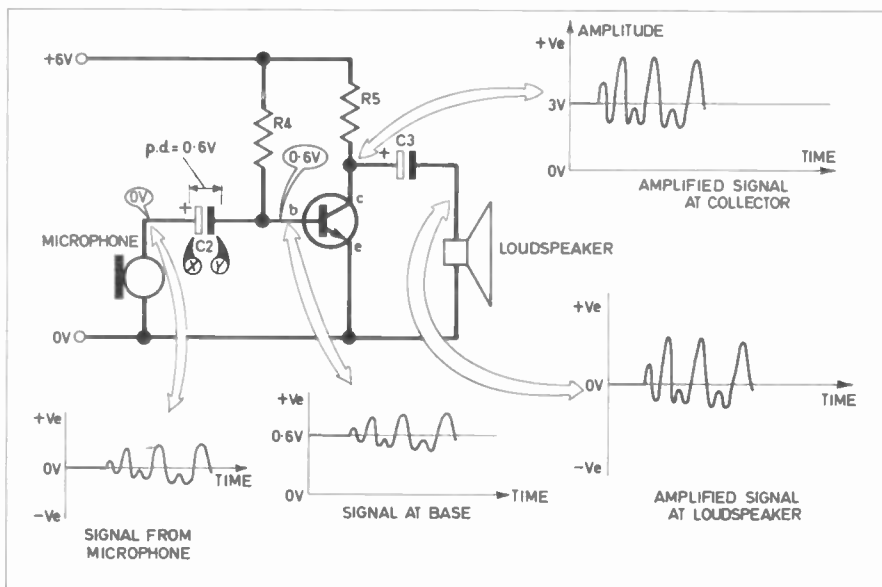


Fig. 6.4. Showing how capacitors are used to couple parts of a circuit while allowing different d.c. levels in each part.

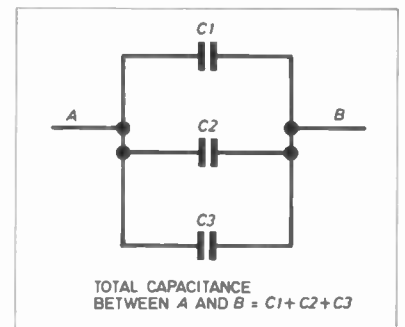


Fig. 6.6. Capacitors connected "in parallel".

oxide to be built up on one plate. This is the dielectric and being very thin it gives high capacitance.

If such capacitors are connected in a circuit in the reverse direction this layer is destroyed. This is why an electrolytic capacitor is marked to show its polarity.

Variable capacitors are used in tuning circuits of radio sets. In the rotating vane type (C1 in *Minilab*), the plates are in two alternating sets. One set can be turned so that the amount by which it overlaps the other can be varied between no overlap and full overlap. The greater the overlap the greater the capacitance.

In compression types, the plates are separated by films of plastic. The pressure on the pile of plates and plastic can be varied to alter the distance between the plates. The greater the pressure, the closer the plates and the higher the capacitance.

## CAPACITORS IN PARALLEL

When capacitors are joined in parallel, that is, connected as in Fig. 6.6, their total capacitance is the sum of their individual capacitances. This is a useful way of making up capacitance of a value which is not available in the standard range.

## PULSE GENERATORS

Last month we saw how two transistors can be cross-connected by resistors, switching each other on or off. The circuit was called a flip-flop. It is also called a bistable because it is stable in one of *two* states. What happens if we add a capacitor or two to this circuit?

### EXPERIMENT 6.1

#### Monostable circuit

In Fig. 6.7 a capacitor couples the collector of TR1 to the base of TR2. To begin with, TR1 is off, giving 6V at its collector, so D1 is out. Plate A of C2 is at 6V, plate B is at 0.6V, and TR2 is on. This gives 0.6V at the collector, so a current flows through D2, making it light.

Press S1 for an instant. This turns off TR2, so D2 goes out. The collector voltage of TR2 goes to 6V, turning TR1 on. D1 lights. Now wait. After about 2 seconds, D2 comes on again and D1 goes out.

What has happened is that when TR1 was turned on, the potential at its collector fell sharply to 0.6V. A drop at plate A of C2 means an equal drop at plate B. This holds TR2 off, even though you have stopped pressing S1. However, a current flows through R5, gradually charging plate B. Its potential rises at a rate depending on the value of R5 and the capacitance of C2. After about 3 seconds, when the potential reaches 0.6V, TR2 is turned on. Its collector potential rises and turns TR1 off.

This circuit is stable in only one of its states (TR1 off, TR2 on), so we call it a **monostable circuit**.

Put capacitors of other values in place of C2. See what effect they have on the length of time D2 stays off. Circuits such as this are useful for generating single pulses of fixed length.

### EXPERIMENT 6.2

#### Astable circuit.

Now we modify the circuit still further so that the transistors are coupled both ways by capacitors, see Fig. 6.9. Set the layout on the Verobloc according to Fig. 6.10. There is no need for you to do anything after connecting the battery. As one transistor is turned off (i.e.d. out), its collector potential rises turning on the other transistor. The falling potential at the collector of the other transistor is passed by the capacitor to the base of the first transistor, holding it off. As the capacitor charges, the potential at the base of the first transistor rises. Eventually it reaches 0.6V and the transistor is turned on again.

The process is repeated the other way about and so on, indefinitely. The transistors turn each other on and off at a regular rate. The circuit is not stable in either state—it is **astable**.

With 220 $\mu$ F capacitors the circuit changes state about eight times a second, giving four complete cycles per second, a frequency of 4Hz. Try replacing one or both of the capacitors with other values.

### EXPERIMENT 6.3

#### Using the 555 I.C.

The 555 timer i.c. is used here to build a monostable circuit. It needs far fewer components than the previous circuit, see Fig. 6.11. We begin with C2 charged to a p.d. of one-third of the supply voltage (that is charged to 2V in this instance). Current passing through R6 flows into the i.c. at pin 7, so C2 remains at one-third of the supply voltage.

A low pulse to the trigger input (S1 pushed briefly) causes pin 7 not to accept current. The current passing through R6 now increases the charge on C2. The potential at pin 6 rises until it reaches two-thirds of the supply voltage that is (4V).

Pin 6 is connected internally to a circuit which senses when this level has been reached. When reached, the capacitor is immediately discharged through pin 7 returning very rapidly to a charge of one-third of supply voltage again.

The output at pin 3 is normally 0V, but rises sharply to the supply voltage level when the i.c. is triggered.

It stays high until C2 is discharged after charging up to two-thirds supply voltage. We get a single high output pulse, the length of which is determined by the values of R6 and C2.

Wire up the Verobloc for this experiment as shown in Fig. 6.12. With the values shown, the output pulse should last about 24 seconds. Try the effect of altering the values of R6 and C2.

## EXPERIMENT 6.1

Fig. 6.7. Circuit diagram of the monostable to be investigated in Expt. 6.1. Another circuit could be coupled to this by a capacitor connected to point C.


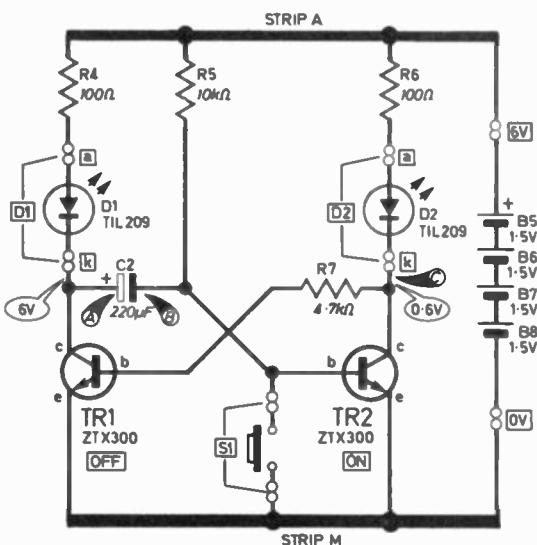


Fig. 6.8. The layout and interwiring for the circuit in Fig. 6.7.

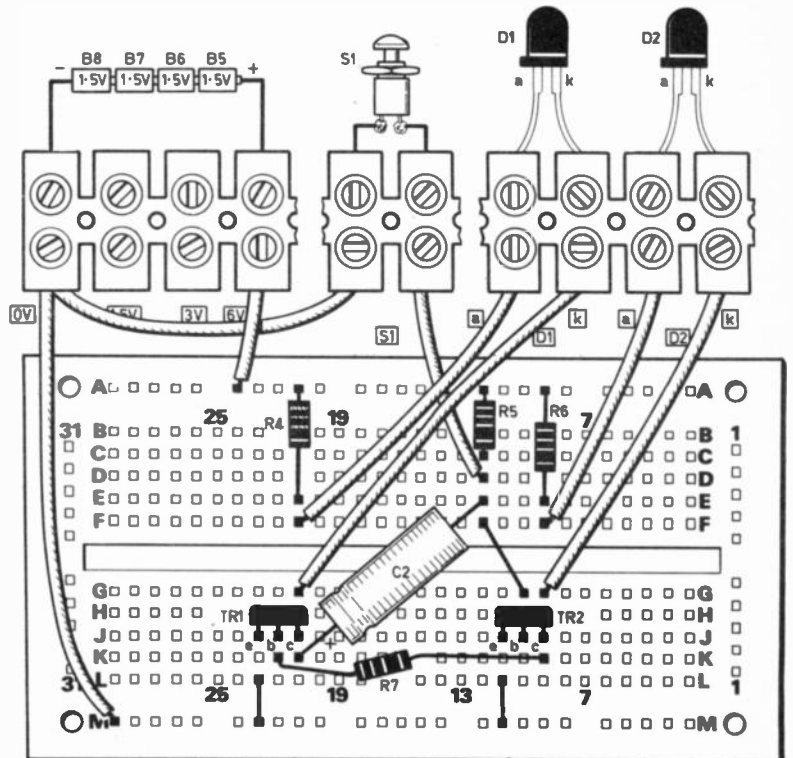



## EXPERIMENT 6.2

Fig. 6.9. The circuit of an astable multivibrator to be investigated in Expt. 6.2.


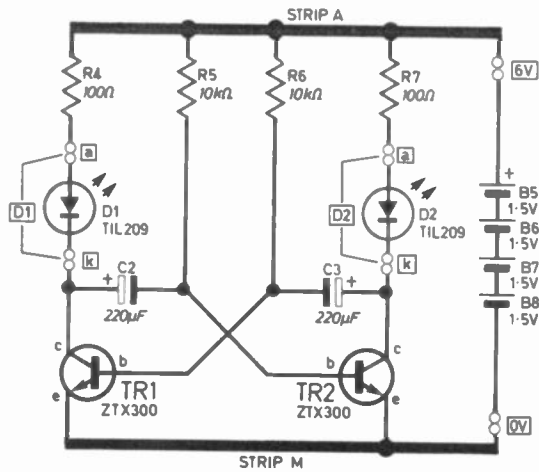


Fig. 6.10. The layout and interwiring on the Verobloc for the circuit in Fig. 6.9.

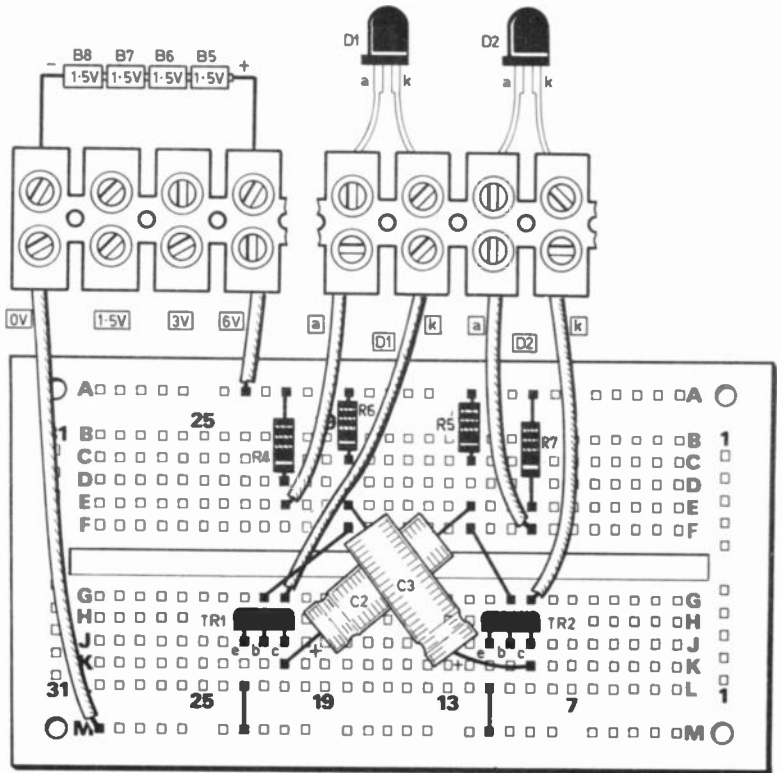

## EXPERIMENT 6.3

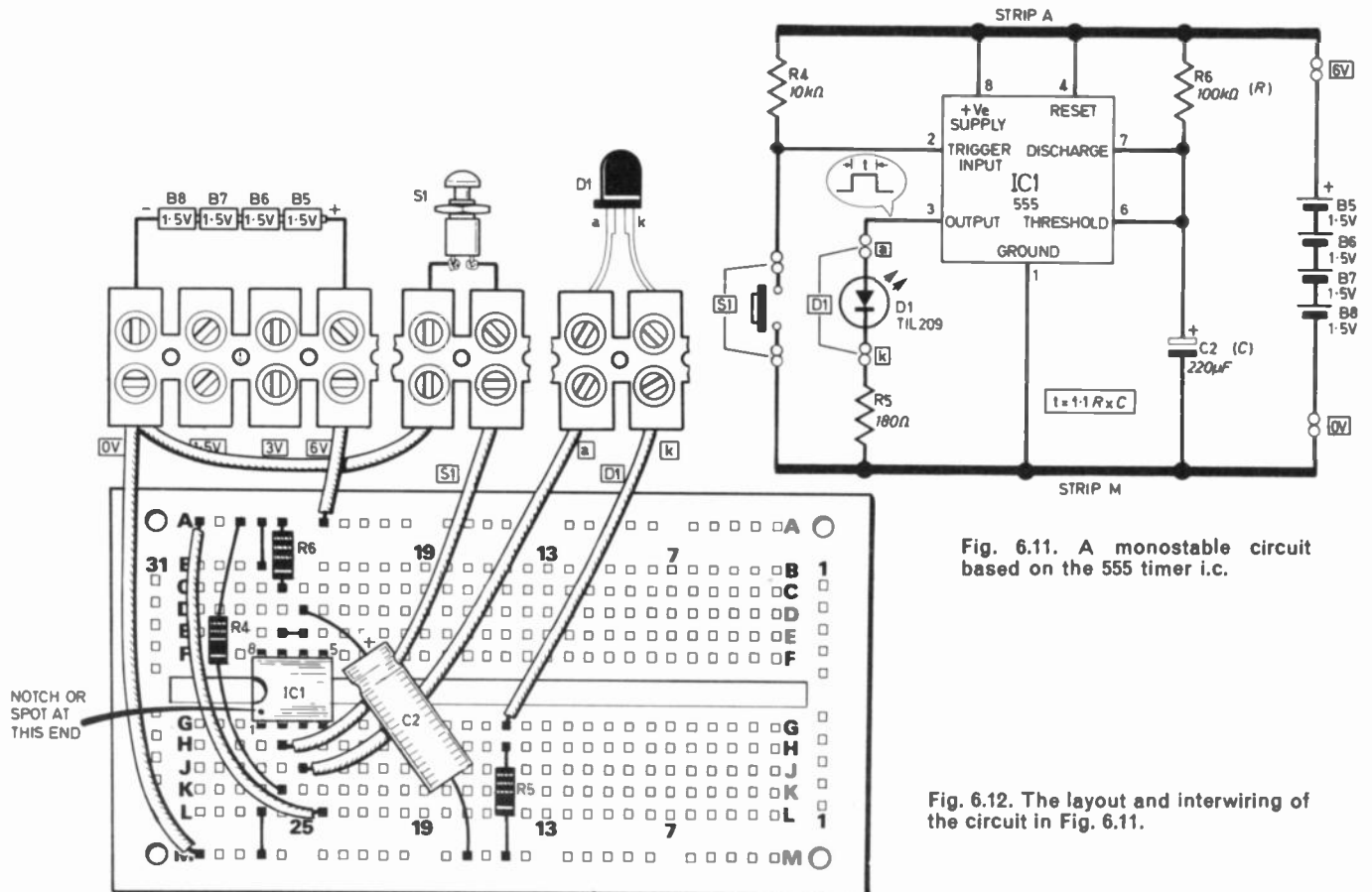



Fig. 6.11. A monostable circuit based on the 555 timer i.c.

Fig. 6.12. The layout and interwiring of the circuit in Fig. 6.11.





## TEACH-IN 82 COMPONENTS IDENTIFIED

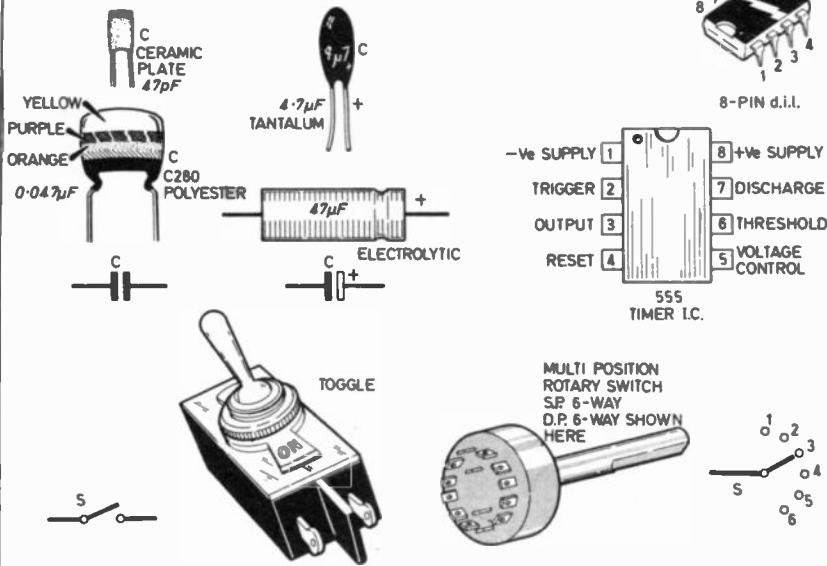

## QUESTION TIME

- A 4.7nF capacitor is wired in parallel with a 1000pF capacitor. What is their combined capacitance?
- Name some of the uses of capacitors.
- A 2.2µF capacitor is charged from 3V to 4.5V. How much extra charge becomes stored in it?
- Here is a list of materials used as dielectrics, but there is one which should not be there. Which is the odd one out? List: polystyrene, aluminium oxide, mica, carbon, waxed paper, air.
- A 555 i.c. is connected as an astable (Fig. 6.13);  $R_5=100k\Omega$ ,  $R_6=47k\Omega$ ,  $C_2=100nF$ . What is the frequency of oscillation produced?

The astable module is to be built at one end of the length of Verostrip with the amplifier module (described in Part 7) in the centre. Drill holes at each end to accept 4BA bolts.

The third module (7-segment display) is to be constructed on a small piece of Veroboard. It will in fact be the piece given free with this issue; add it to your stock of Teach-In components for use later.

Follow the layout of the components according to Fig. 6.16. Connection of flying leads to the board are made using Veropins, so the assembled board may now be screwed to the internal face of the *Minilab* rear panel.

Fit the required switches and terminal strip to the *Minilab* Control Panel. The toggle switch at the top right hand corner and its reference is S5. The rotary switch fits between C1 and VR2 and its reference is S6. The terminal block sits below S5.

Next make the interconnection between module strip and *Minilab* components. Finally replace the rear and control panels to complete the installation.

## TESTING THE MODULE

To test the module for satisfactory operation, wire up according to Fig. 6.17. with S6 set to "0.1". Switch on at S5. Clicks should be heard from the loudspeaker at a rate of approximately one per 5 seconds. Rotate S6 clockwise to hear clicks at a rate of one per half-second. The next two positions of S6 will cause a buzzing tone and a high pitched tone to be heard. If this occurs your module is functioning satisfactorily. Turn off at S5.

The remaining two unconnected positions on the rotary switch may also produce high pitched tones even though there are no capacitors actually connected. There is stray (small value) capacitance between the leads to the switch which in effect is placed across ICI pin 6 and 0V. The value may be low enough to produce an audible frequency output.

**To be continued**

## COMPONENTS required for Experiments during Parts 7 to 12. Complete kits of these (LIST 3) may be obtained from the retailers listed on page 171.

Resistors			
Quantity	Value		
1	56 ohm	1	4.7µF electrolytic 16V type preferred, radial or axial leads. Short lead types should not be supplied.
1	82 ohm		All to be suitable for working at 12V. Very large types should not be obtained.
1	150 ohm		
1	220 ohm		
2	270 ohm		
8	390 ohm		
1	1 kilohm		
1	1.5 kilohm		
1	3.3 kilohm		
2	10 kilohm		
1	12 kilohm		
1	18 kilohm		
1	56 kilohm		
4	100 kilohm		
1	330 kilohm		
1	470 kilohm		
1	820 kilohm		
2	1 megohm		
All $\frac{1}{4}W$ or $\frac{1}{2}W$ carbon $\pm 5\%$ tolerance.			
Types prepared for p.c.b.s with short preformed leads are not suitable.			
All leads on components to be between 0.5 and 0.8mm diameter to fit specified breadboard (Verobloc).			
Potentiometer		Semiconductors	
Quantity	Value	Quantity	Type
1	100 ohm horizontal mounting sub-miniature carbon preset.	1	TIL38 infra-red light emitting diode.
Must be suitable for mounting directly on 0.1 inch matrix breadboard.		2	ZTX300 silicon npn transistor.
		1	OA91 germanium diode.
		1	BZY88C5V1 5.1V 400mW Zener diode.
		1	DL704 0.3 inch common cathode 7-segment display. Litronix, RS 586-778 or other identical pin-out type.
		1	741 differential op-amp (8-pin d.i.l.).
		1	4511 CMOS b.c.d./7-segment decoder.
Capacitors		Miscellaneous	
Quantity	Value	Quantity	Description
1	6.8pF ceramic plate or disc.	2	Toggle Switch standard size s.p.s.t. (same as type obtained in LIST 2).
1	180pF silvered mica.	2	IC Sockets
2	4.7nF ceramic plate or disc.		1 off 16-pin d.i.l. low profile type.
5	0.1µF metallised polyester, Mullard C280, ITT PMT2R or similar.		1 off 14-pin d.i.l. wire wrap type.
		1	Ferrite Rod 8mm diameter, 100mm long.
		1	Filament Lamp 6V 60mA wire ended type.
		20m	Miniature Stranded Wire p.v.c. covered 10/0.1mm preferred.
		4m	Enamelled Copper Wire 28 s.w.g.



By Dave Barrington

### Catalogues Received

One of the first of this year's mail order components catalogues to be received is the Ace Mailtronix 1982 edition.

Although containing only 12 pages, they have been fairly selective and included most items that the constructor is likely to want. As they say in the catalogue "You will certainly not find every component you seek in any catalogue", but they are prepared to try and find those special items on receipt of a sae.

New additions include low leakage electrolytics, more cases and considerable expansion of the i.e.d. range to include rectangular, triangular and bargraph types. The switch range now includes keyboard switches and complete keyboards.

For those readers who like to make their own printed circuit boards they stock a full range of Alfacs etch resistant transfers.

Copies of the Ace 1982 Mail Order catalogue are available from Ace Mailtronix Ltd., Dept EE, 3a Commercial Street, Batley, West Yorks WF17 5HJ, price 30p.

### New Address

We have been informed that Tempus have moved premises and their new address is: Tempus, 38 Burleigh Street, Cambridge, CB1 1DG.

### CONSTRUCTIONAL PROJECTS

#### Camera or Flashgun Trigger

The only component problems likely to be encountered when building the *Camera* or *Flashgun Trigger* is the supply of the infra red emitter and detector devices.

The only stockist we have been able to locate for the supply of both the TIL100 and the TIL38 "matched" infra-red detector and emitter is Maplin Electronic Supplies. These are listed as stock numbers YH70M and YH71N. Some advertisers stock the TIL100 photodiode but do not seem to carry the TIL38 device.

#### Guitar Tuner

The tone generator integrated circuit used in the *Guitar Tuner* project could cause readers purchasing problems. This is the MO83 i.c. and seems to be only available from Maplin. The miniature output transformer is also stocked by them.

#### Ice Warning

The thermistor used in the original circuit for the *Ice Warning* was a THB11 type. We have been unable to locate a source for this device and have substituted it with a suitable equivalent.

This is the bead thermistor type GL16 which has a typical resistance of 1 Meg-ohm at 20°C.

The GL16 thermistor should be stocked by numerous component suppliers, but if difficulties are experienced then it is available from Maplin as the G16; stock number WH23A.

#### Pocket Timer

The silicon controlled switch type BRY-39 used in the *Pocket Timer* should be available from most suppliers. It is certainly listed by Bi-Pak, Electrovalue, Watford and Rapid Electronics.

#### Car Probe

The only unusual component in the *Car Probe* is the bi-state i.e.d. Although this is a fairly new device it seems to be stocked by several dealers. It is also available from RS Components suppliers and is listed as RS type 586-728.

The housing for the prototype *Car Probe* was an old pocket penlight and was chosen for ease of mounting the bulb and probe tip. Any similar casing, such as an old torch of solder dispenser, would suffice.

#### House Register

We have been unable to find a supply of the red, green and white miniature push-to-make release-to-break switches S1 to S9. However, any one of the many miniature push-button switches can be used and the bush-button capped with a coloured disc or "hat" for identification.


### TEACH-IN 82 KIT SUPPLIERS

Supplier	LIST 1	LIST 2	LIST 3	LISTS 1, 2 & 3
Bi-Pak (p. 151)	£15.65	£8.94	NR	NR
Electrovalue (p. 206)	£16.56	£6.32	£5.70	£27.49
Greenweld (p. 148)	£18.50	£8.10	£4.40	£29.00
Magenta Electronics (p. 152)	£16.40	£9.34	£6.48	£30.98
A. Marshall Ltd	£17.00	£12.50	NR	NR
T. Powell (p. 208)	£19.75	£10.50	£6.35	£27.50
T.K. Electronics (p. 146)	£15.52	£8.62	£5.63	£27.02
Watford Electronics (p. 147)	£18.08	£9.33	NR	NR

All prices are inclusive of VAT, postage and packing. NR = Not Received. For suppliers full address refer to page number following company name.

## JACK PLUG & FAMILY...

BY DOUG BAKER

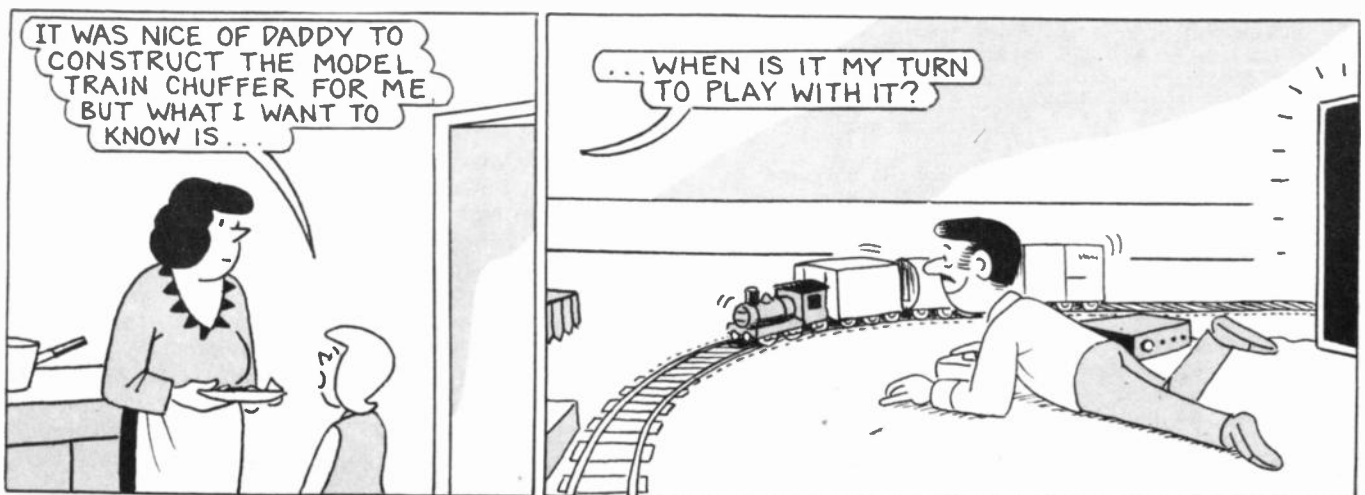



## Hot Air

The sudden cold spells always show up the weaknesses in the internal combustion engine, and I expect many readers have found themselves in the same position as I was two Sundays ago, with two cars and not a sign of life in either of them. I hate to say it, but what do we always suspect first, the electrics, and with good reason. The spark is the weakest link in the chain.

Now here's a tip for fellow motorists. Most of the trouble connected with non-starting is due to damp in the distributor cap. There are one or two firms which sell inexpensive de-frosting guns, designed to get ice off windows.

If you experience the trouble mentioned above, plug in your gun, push back the two spring clips holding the distributor cap, lift the cap clear of the rotor arm, squirt the hot air into the cap for about two minutes, and you're away. If you hold the cap over the gas as I used to, there is a danger of it melting.

## Graham Farish

Glancing quickly through the pages of "Practical Wireless", I suddenly thought I was caught up in a time warp. There on page fifty was an advert of an h.f. choke covering the Medium and Longwave band, price two shillings, and something called an "Ohmite" resistor, with the words underneath it "Better than wire-wound", price one shilling and sixpence.

Looking at the top of the page I realised it was part of an obituary notice for the late Graham Farish and the advert was a reproduction of one of his advertisements of 1932. His was a name in the components market well known to the older generation. Later he went into model railways.

## Just a word

What a difference a word can make! A customer recently wrote and asked me to quote him for a mains transformer giving an output of 12-0-12 volts because

he wanted to make a battery charger. I wrote and asked what current he wanted to draw from it and back came the answer, 4 amps.

Naturally I assumed he wanted to charge up two 12 volt car batteries. Once more I had to write and say, that if this was his intention, he would need a transformer that gave 4 amps at an off load voltage of around 17-0-17 volts.

When he replied he sent me the circuit, taken from one of the magazines. It was a circuit for a Battery Eliminator to replace a PP911

## Crystal Gazing

In spite of the myriad of the most sophisticated electronic toys imaginable, the sales of them were greatly exceeded by a non-electronic toy, the infuriating Rubrik Cube. I was also pleased to note that we sold over five hundred of the humble crystal sets. It never fails to please the youngsters and is a good stepping stone to more serious projects.

I do hope that many readers spotted the series of lectures by The Royal Institution on BBC Television. They are always first rate. This year the lecturer was Professor R. V. Jones, F.R.S., and he called his series "From Magna Carta to Micro-chips".

Some of the facts he told us were astonishing, for example, did you know that Wheatstone (the bridge man) invented the mouth organ? The good Professor not only told us about it but produced one and proceeded to play it very competently. What an all rounder!! Larry Adler had better look to his laurels!

# BOOK REVIEWS

## PUBLIC ADDRESS HANDBOOK (2nd edition)

Author Vivian Capel

Price £7.95

Size 220 × 140mm, 238 pages

Publisher Keith Dickson Publishing Ltd

ISBN 0 907266 02 9

FOR anyone involved with public address amplification, this book is a must. Written in an easy to understand style it is full of good practical information much of it only obtained after years of experience in the trade. It ranges from basic principles through microphones and amplifier systems, indoor and outdoor installations, practical problems, testing and fault finding, and special equipment. And to finish, a section on practical installations with worked examples.

A few basic circuits are described but the book mainly concentrates on the practical aspects of public address installations, for example, the correct type of microphone and/or polar diagram required for a particular installation, and loudspeakers, and their location avoiding feedback. Examples of actual systems for from about 100 people up to a stadium of 15,000 with requirements for speeches, interviews, forums as well as community singing led by taped music are given. A section on the legal aspects is also included.

The section on loudspeakers covers the 100 line system in detail with sections on matching, phasing, power tapering, frequency tapering and weatherproofing.

E.A.R.

## PRACTICAL OSCILLOSCOPE HANDBOOK

(Second edition)

Authors Howard Bierman, Paul Bierman and Rufus Drew.

Price £7.00

Size 320 × 150mm, 170 pages

Publisher John Wiley & Son Ltd

ISBN 0 8104 0851 1

THIS book should prove to be an ideal companion for all users of oscilloscopes. It covers the subject from first principles and the operation of the various types of controls found on modern scopes right through to the more advanced type of measurement. Only the minimum of calculation and theory are given where these are relevant to the practical use being described. The whole aspect of this book is on the practical and the drawings given are among the clearest this reviewer has seen for some time.

The many drawings show not only the method of connecting the oscilloscope up into practical circuits but also the types of waveform to expect. Typical control settings are also given for many of the measurements shown. In the section on audio measurements for example, there are no less than fourteen examples of square waves obtained during the testing of an amplifier showing the effects of poor frequency response, phase shift, and miscellaneous effects. Receiver alignment curves are also shown for both TV (American system) and radio and there are diagrams showing how to check transmitter modulation.

Written in plain English this book will enable the reader to understand not only how oscilloscopes work but how to put them to practical use. Anyone contemplating building or buying as well as using an oscilloscope should have a copy. Highly recommended.

E.A.R.


# APRIL FEATURES

## *A Security Problem?*

*Perhaps we have the  
answer with this*

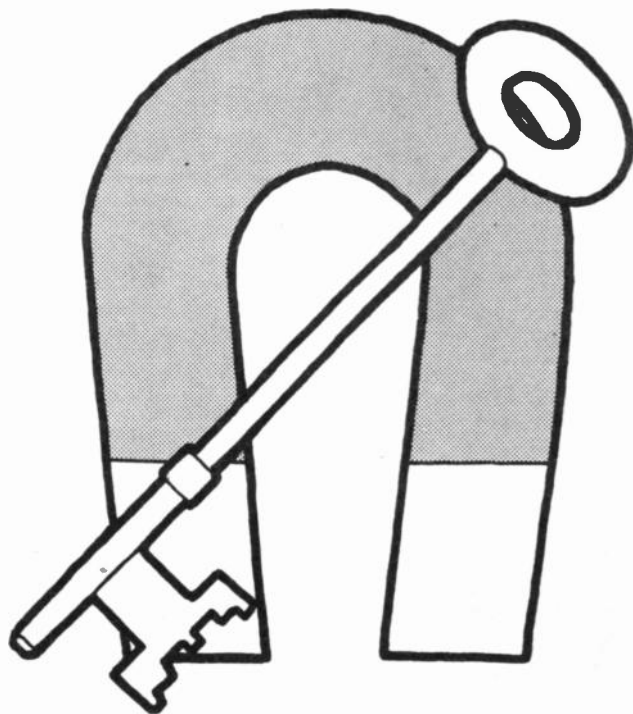
### **MAGNETIC LOCK**

Mains powered circuit incorporating four Hall Effect semiconductor devices; these can be activated only by a special magnetic key. Virtually impossible to "crack". The lock that doesn't betray its presence. Ideal for hidden compartments.


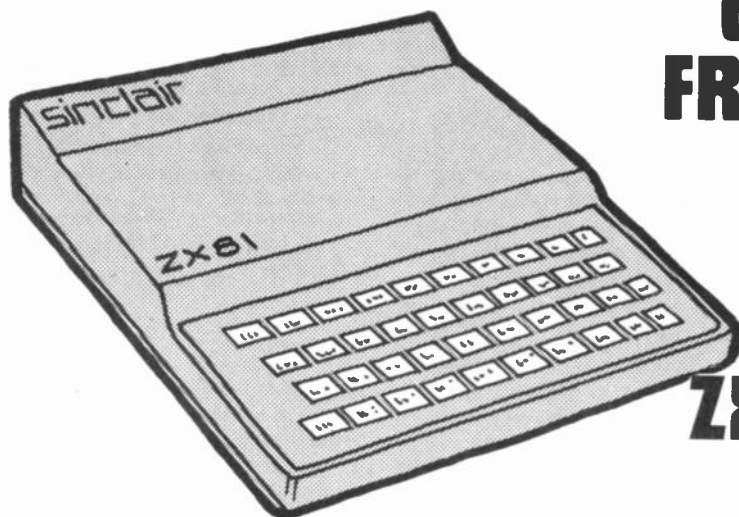
## *Music on Wheels* **IN-CAR POWER SUPPLY**

Provides 6, 7 or 9V d.c. from 12V car battery at a turn of a switch. Ideal for powering portable cassette recorders, torches, battery shavers and radios.



## *Good Measure* **CAPACITANCE & FREQUENCY METER**

Handy dual-purpose instrument for the constructor. Range: Capacitance 400pF to 10 $\mu$ F; Frequency 50Hz-1MHz. Uses calculator type digital display.

## *More Memory* **ZX81 2K RAM PACK**

Increase the data storage capacity of your ZX81 Personal Computer to 3Kbytes by plugging in this inexpensive, easy to construct module. Resides inside a cassette tape case.

APRIL 1982 ISSUE—ON SALE  
FRIDAY, MARCH 19



# GUITAR TUNER

FOR all those guitar owners who do not possess a piano, organ or the innate ability to help in the tuning of it, this instrument will be of use. All six notes of the guitar strings are reproduced by the circuit described in this project.

No precision calibration or tuning is necessary, though it can be tuned to another instrument if this is desired.

## CIRCUIT DESCRIPTION

The full circuit diagram is shown in Fig. 1. The heart of the instrument is IC2, an M083. This i.c. divides an input signal into thirteen different frequencies representing all the notes in an octave from c to c.

The six notes of the guitar strings are as follows: E (82.5Hz); A (110.0Hz); D (146.7Hz); G (195.9Hz); B (247.0Hz); E (329.8Hz). The nominal frequencies of the notes are shown in

brackets. As this range of frequencies spans two octaves, further frequency division of the output frequencies from IC2 must be done.

Dividing the frequency of a note by two, causes a drop in pitch of one octave. So, for example, as the highest E string is two octaves above the lowest E string, it has a frequency four times greater. It will be seen from Fig. 2 that a nominal clock frequency of 124994.2Hz is needed to produce the required output frequencies.

## CLOCK OSCILLATOR

This clock frequency is generated by IC1a, b, and c, three quarters of a CMOS quad 2-input NAND gate, the 4011. These three NAND gates are connected together as an oscillator, the frequency of which can be adjusted by VR1. This potentiometer, along

with R1 and C1, form the timing components of the oscillator. The signal is fed into the clock input of IC2, pin 2.

From pin 7 of IC2 comes TOP E, which on depressing S6, is fed to the audio amplifier section. Notes B, G and D come from pins 14, 10 and 5 respectively by pressing S1, S2 and S3. However, as these three notes lie in the octave below TOP E, it is necessary to divide the frequencies by two.

This is done with IC3b, half a CMOS 4013 dual D type flip-flop. By connecting the Q output to the D input, that is connecting pin 5 to pin 2, the flip-flop will divide by two.

Notes A and BOTTOM E are obtained from pins 12 and 7 respectively. However, these lie in the octave below that of notes B, G and D, and two octaves below TOP E, and hence must be divided by four. This is achieved by passing the signal through and additional flip-flop, IC3a, also connected as a divide-by-two.

## COMPONENTS

See  
**Shop  
Talk**

### Resistors

R1, 2, 3 18k $\Omega$  (3 off)  
R4, 5 68k $\Omega$  (2 off)  
R6 2.7k $\Omega$   
All  $\frac{1}{4}$ W carbon +5%

page 171

### Capacitors

C1 270pF  $\pm$ 2% polystyrene  
C2, 3, 5 680pF polystyrene (3 off)  
C4 0.022 $\mu$ F polyester

### Semiconductors

IC1 4011 CMOS quad 2-input NAND gate  
IC2 M083 MOS tone generator  
IC3 4013 CMOS dual D-type flip-flop  
TR1 BC109 silicon *npn*

### Switches

S1-6 push-to-make non-latching (6 off)  
S7 s.p.s.t. miniature toggle

### Miscellaneous

B1 9V PP3 battery  
LS1 miniature 4 $\Omega$  speaker, 57mm dia  
T1 miniature output transformer, 1.2k $\Omega$  primary, 3.2 $\Omega$  secondary  
VR1 15k $\Omega$  miniature vertical preset (see text)

Stripboard: 0.1in matrix, 25 strips  $\times$  33 holes; case, 120  $\times$  80  $\times$  35mm (Vero type 202-21390D); 16 pin d.i.l. holder; 14 pin d.i.l. holder (2 off); p.v.c. sleeved 7/0.2 equipment wire; battery clip; Veropins (12 off); epoxy resin adhesive; mounting hardware (M2.5 or 6BA); tinned copper wire (for links).



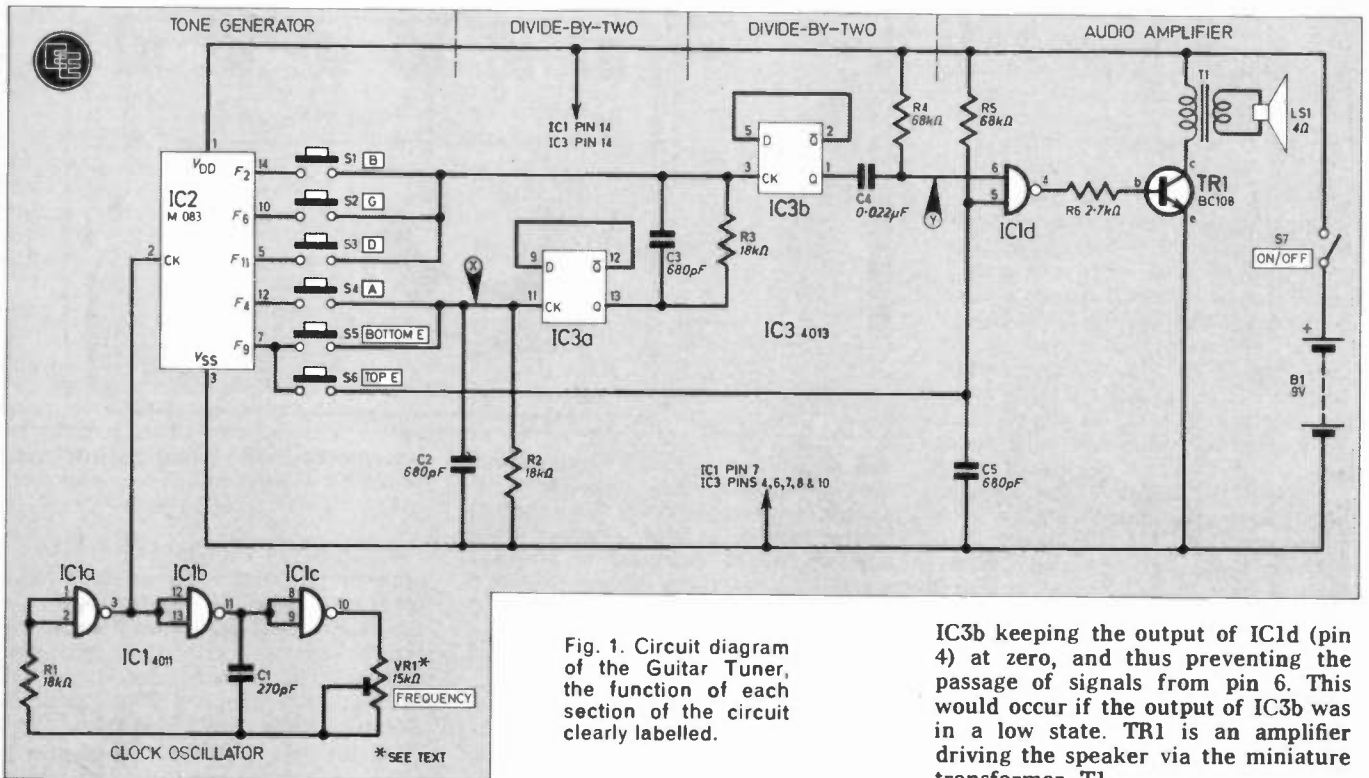


Fig. 1. Circuit diagram of the Guitar Tuner, the function of each section of the circuit clearly labelled.

IC3b keeping the output of IC1d (pin 4) at zero, and thus preventing the passage of signals from pin 6. This would occur if the output of IC3b was in a low state. TR1 is an amplifier driving the speaker via the miniature transformer, T1.

C2, C3, R2 and R3 are included to fulfil the output loading requirements of IC2 and R3 also acts as a buffer between output pins 14, 10 and 5 of

IC2 and the Q output, pin 13, of IC3. The signals are then fed into pins 5 and 6 of NAND gate IC1d as shown. C4 prevents any unwanted d.c. bias from

Although IC2 is specified to run off of 10 to 12 volts, the most convenient power source is a 9 volt PP3 battery, and the i.c. functions well at this voltage. S7 is the main ON/OFF switch.

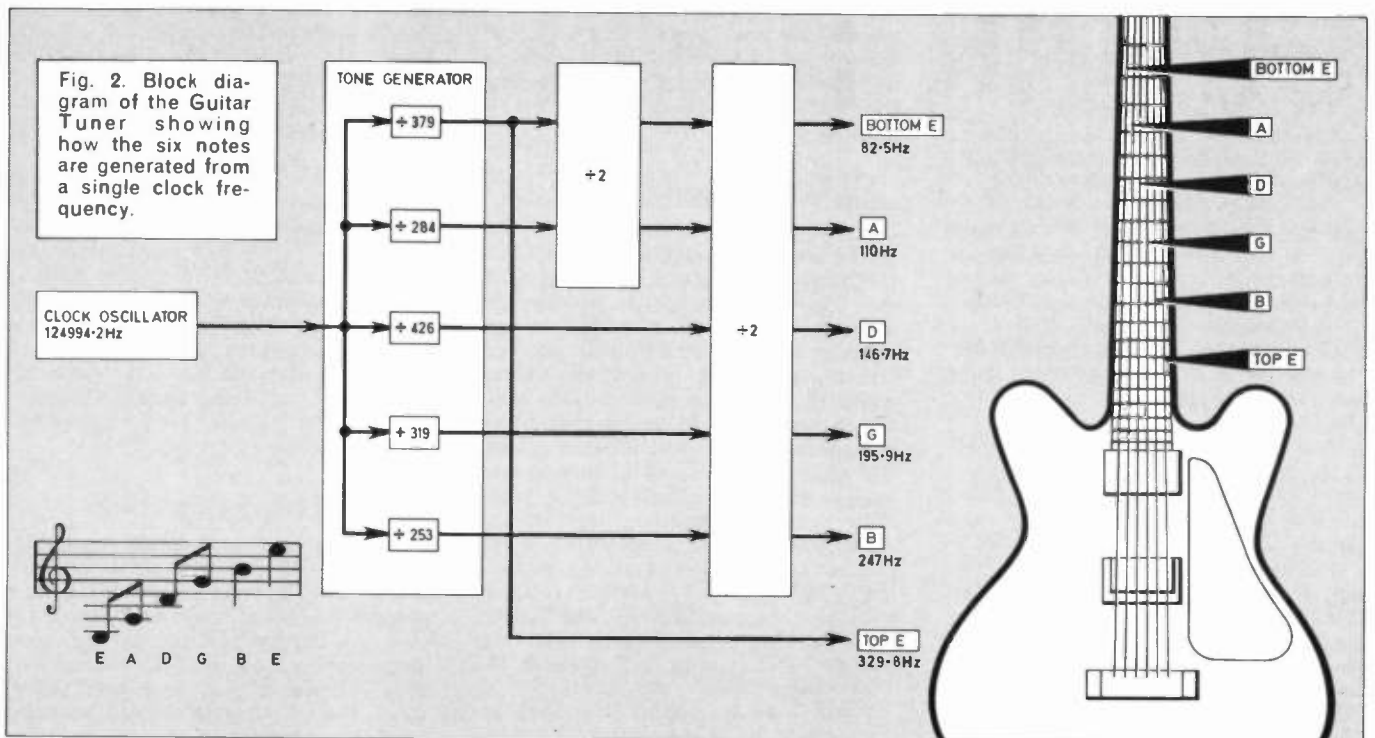


Fig. 2. Block diagram of the Guitar Tuner showing how the six notes are generated from a single clock frequency.

# CONSTRUCTION starts here

## CIRCUIT BOARD

The original prototype circuit board was built on Vero V-Q board but due to the ready availability and simplicity of use of standard stripboard, we have transferred the layout to 0.1in matrix Veroboard, 25 strips by 33 holes (shown in Fig. 3). The design requires the use of quite a large number of track breaks, 38 in all, and these must be positioned with great care.

Proceed to assemble the components onto the board, using i.c. holders for all i.c.s, especially IC2 which is quite an expensive device. None of the capacitors are polarity conscious but the orientation of TR1 and miniature output transformer, T1 must be observed.

22 wire links are required and the longer ones, spanning say four holes or more, should be sleeved or made from insulated wire to prevent them flexing and shorting out against one another. Finally all connections from the board to the switches etc, should be made to Veropins as the continuous flexing of these wires which inevitably occurs during construction often leads to wires breaking, and repairs are easier to effect when pins are used.

## CASE


The unit is built into a plastic moulded box, approximately 120 x 80 x 35mm with a removeable lid.

All seven switches are mounted into the base of the case as shown in Fig. 4. S1 to 6, the push-button switches, are equally spaced along one side of the case, fixed into 7.4mm diameter holes (for the switches we used, yours may be different) and S7 the on/off toggle switch is mounted in a 6.4mm diameter hole in the position shown.

The speaker is glued into position in the base with epoxy resin adhesive, after first drilling a pattern of holes beneath it to form a "grille" (see photo).

The circuit board is secured to the lid of the case with two M2.5 (or 6BA) screws approximately 13mm long. To space the board away from the lid, two extra nuts, one on each screw, should be screwed on first.

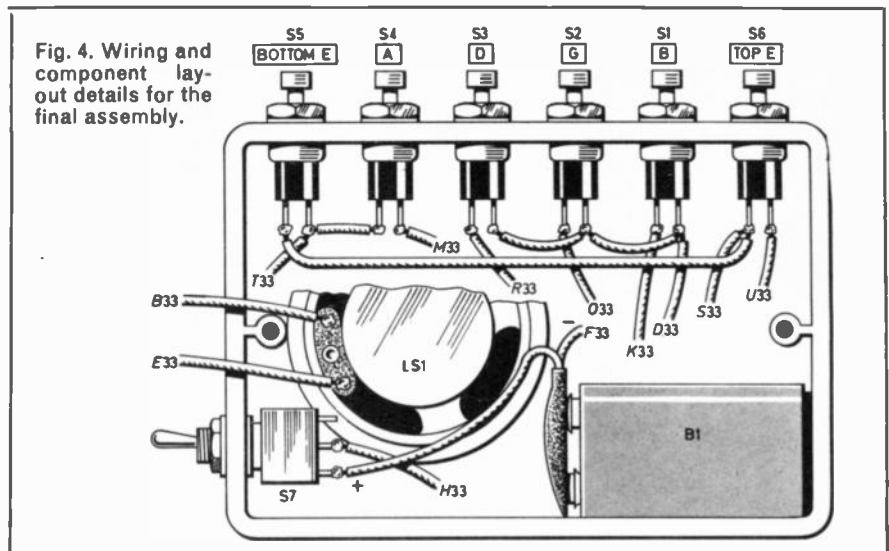When positioning the board on the lid, bear in mind the relative position of T1, the highest component, and



the magnet of LS1 and ensure they do not foul each other. It is best to do this before glueing down the speaker.

The battery is held in place with a double sided sticky tab or alternatively by using foam rubber "sponge" to fill the space.

## FINAL ASSEMBLY

Wire the board to the case mounted components with the 7/0.2 p.v.c. sleeved wire as shown in Fig. 4. Wire numbers refer to a strip/hole reference from Fig. 3, the stripboard layout diagram.

Having completed this assembly stage, it is a good idea to mark switches S5, 4, 3, 2, 1 and 6 with E, A, D, G, B, and E respectively, using dry print "rub-down" transfers. The words BOTTOM and TOP, used to differentiate between the two E's were not thought necessary, since pressing the buttons will immediately determine this!

## USING THE TUNER

As previously discussed, IC1 will divide the input frequency into all the notes of an octave, irrespective of the input frequency. So, if for example, the frequency of TOP E is not exactly 329.8Hz then this is not too critical, since the other frequencies will still be in the correct ratio relative to each other to enable the guitar to be tuned. However, adjusting VR1 will alter the oscillator frequency and enable the instrument to be calibrated against another instrument, for example, a piano. However, if no calibration source is available, replacing VR1 with a 12 kilohm resistor will give approximately the right pitch for the notes. If doing this, this resistor along with R1 should be  $\pm 2$  per cent types.

Finally, do not sound two notes at the same time, since, if for example, S1 and S2 were pressed, the output of

B would be feeding directly into that of G.

## ALTERNATIVE CALIBRATION

In the event of no musical instrument or trained ear being available to the constructor, and he still wishes to set the tuner to a reasonably accurate standard, an alternative method of calibration is to use a test transmission tone from a television set.

During test card transmissions on BBC2, a 440Hz signal (middle A) is broadcast for a period of four minutes on the hour. Although the BBC cannot guarantee this signal to be absolutely accurate, it will be sufficiently close to middle A for our purpose.

However as the A string on the guitar is at 110Hz, that is two octaves below the transmission signal, on our tuner we must take the output directly from pin 12 of IC2 into the audio amplifier section, thus by-passing the two divide-by-two stages, IC3a and b.

To achieve this, a temporary link must be made between pin 11 of IC3a and pin 6 of IC1d (point X, ref M15 and point Y, ref T12 respectively on Fig. 3) resulting in a 440Hz output from the speaker when S4 is pressed.

Now the clock oscillator can be tuned by adjusting VR1 until the output signal matches the test transmission signal. All other notes will automatically be in tune. Remove the link on completion.

## TONE GENERATOR CHIP

It may be apparent to the constructor that the full potential of the M083 has not been exploited in this project. In fact it could be adapted to give the appropriate pitches for any instrument which requires tuning. So with the aid of Fig. 5, a brief data sheet, the constructor should be able to modify the circuit to suit his own needs and musical instruments. ☞

# GUITAR TUNER


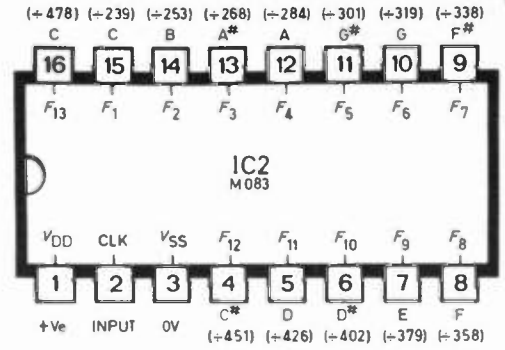
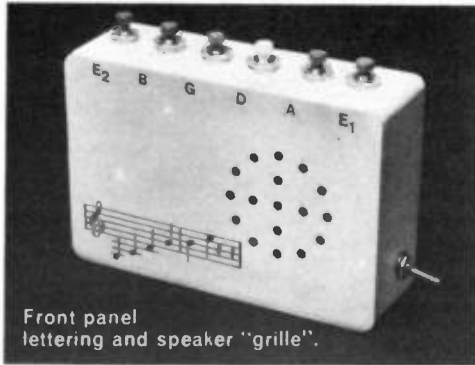
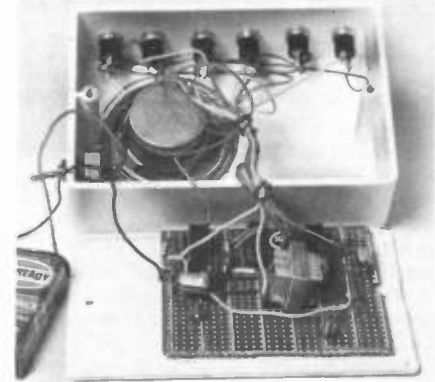


Fig. 5. Pin function diagram of the M083 tone generator i.c.

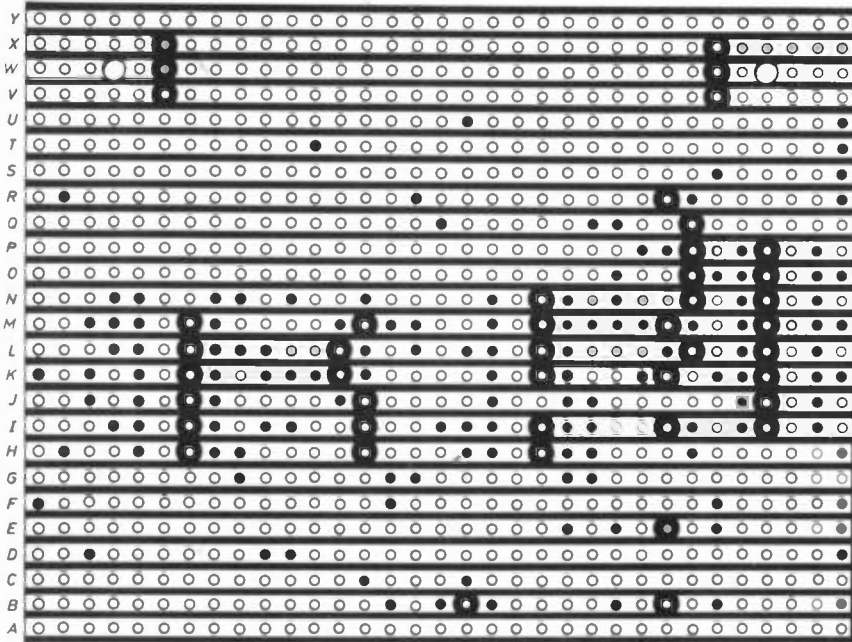

View of the unit with lid removed showing interwiring. Note that the prototype is built on Vero V-Q board and therefore differs from the layout shown in Fig. 3.


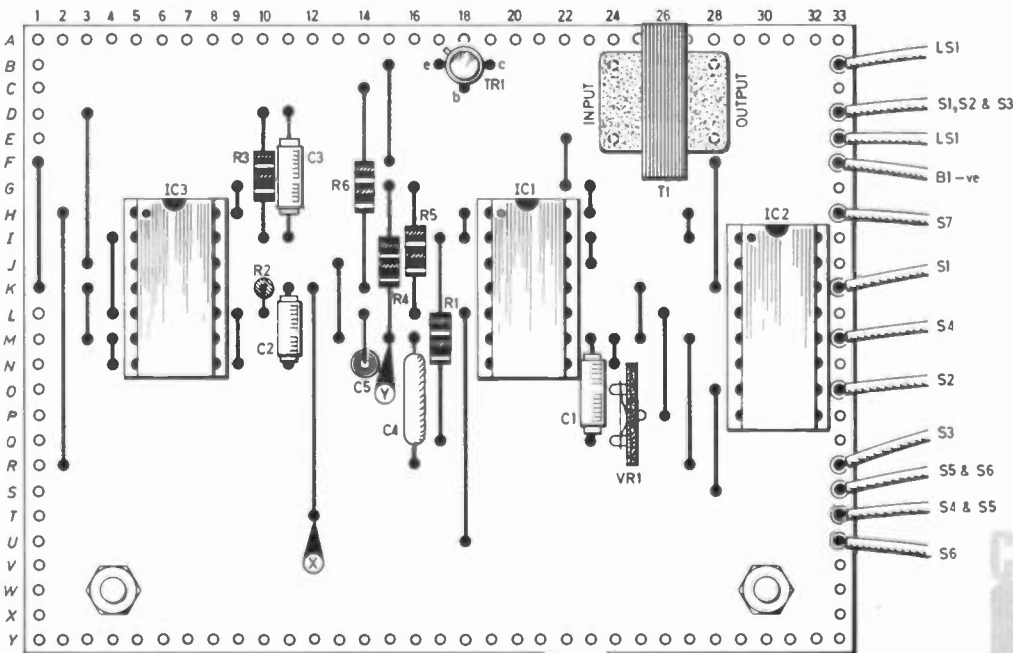


Fig. 3. Stripboard layout of the Tuner with the track view (top) showing all the necessary breaks.

**COMPONENTS**  
approximate  
cost **£15.50**

●=VEROPINS

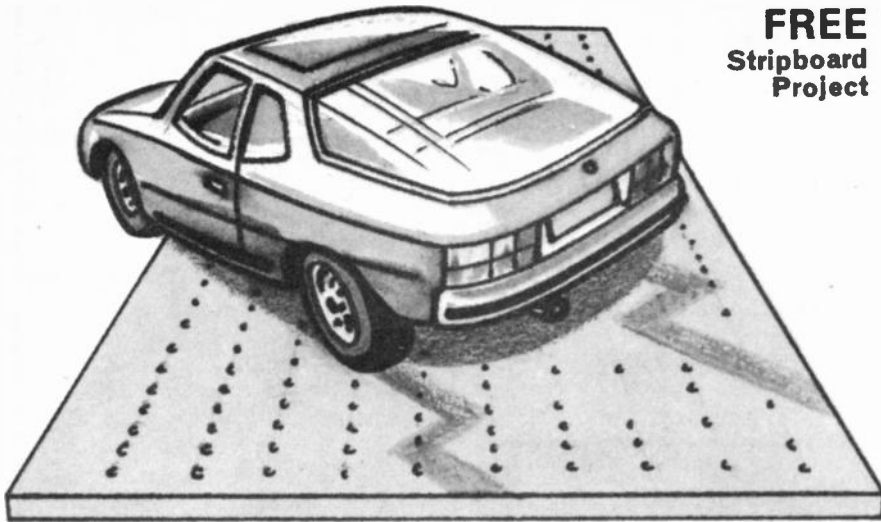

## FREE Stripboard Project

# ICE WARNING for CARS

THIS article describes how to use a thermistor as a transducer in a circuit which repeatedly flashes a lamp when the temperature of the thermistor has fallen to a preset temperature—in this case 0 degrees Celsius. Thus the circuit can be used to warn the driver of a car that icy roads are likely.

The thermistor is a glass-encapsulated negative-temperature-coefficient (n.t.c.) bead type. Its small size enables it to respond rapidly to temperature changes. Note that an n.t.c. thermistor has an electrical resistance which increases with temperature fall.

## THE CIRCUIT

The complete circuit diagram of the alarm is shown in Fig. 1. The design shown is powered by a 12V car battery, although should the circuit be used for other applications a 9V battery could be used.

The circuit consists of two distinct parts: (1) a temperature-sensitive Wheatstone bridge, the output from which is sensed by the op-amp acting as a differential amplifier and (2) a two-transistor oscillator which flashes the l.e.d. when the thermistor reaches a predetermined temperature.

## WHEATSTONE BRIDGE

The Wheatstone bridge consists of resistors R1 and R2 which set the voltage at the inverting terminal of the op-amp, IC1, at about 8V with respect to the negative line (for a 12V supply). The preset resistor VR1 and the thermistor RTH1 form the other arms of the bridge.

Since the thermistor is an n.t.c. type, as its temperature falls its resistance increases, and the voltage at pin 3 rises. When this voltage just exceeds that at pin 2, the voltage at the output of the op-amp goes from near-zero to

near +12V. The temperature at which the output goes sharply positive can be selected by adjustment of the preset resistor VR1.

The high voltage at the output of the op-amp switches on the oscillator by coupling the "high" voltage to the base of TR1 through R3. The capacitor C1 provides the positive feedback which is necessary to maintain the low-frequency oscillations.

TR2 has the l.e.d. in its collector circuit with series resistor R5 which limits the current passing through the l.e.d. to a safe value.

The frequency of the flashes of the l.e.d. are determined partly by its own resistance and C1 value.


Transistors TR1 and TR2 should be a complementary pair if the circuit is to work satisfactorily. The pairs 2N2926/2N3702 and BC182L/BC212L are suggested alternatives to the types specified in the component list.

## COMPONENT ASSEMBLY

All the components, except battery, switch and l.e.d., can be mounted on a piece of 0.1 inch stripboard size 10 strips by 24 holes as shown in Fig. 2.

Make the necessary breaks on the underside of the stripboard as shown in Fig. 2. Use a spot face cutter or a small (3mm) drill bit. Position and solder the components to the topside of the board leaving the semiconductors until last. Attach sufficient

Fig. 1. The circuit diagram of the Ice Warning alarm.

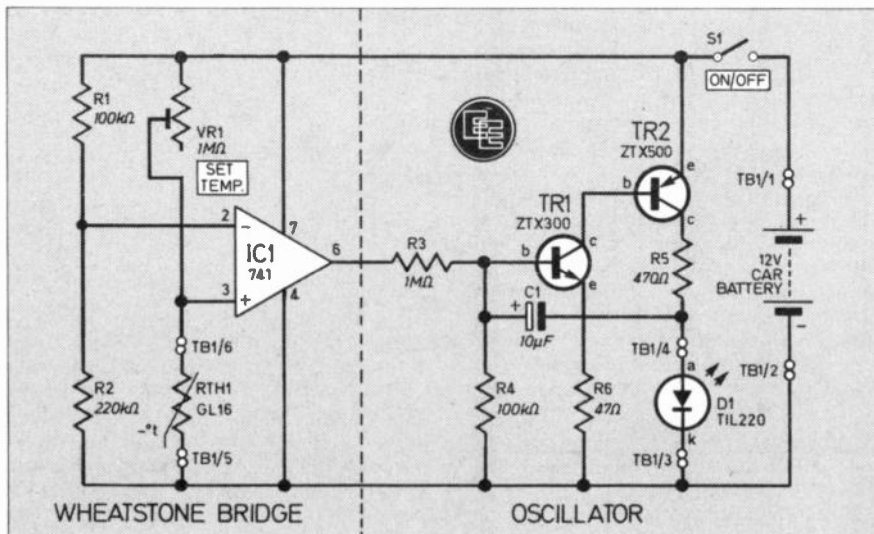

## COMPONENTS

### Resistors

R1 100kΩ  
R2 220kΩ  
R3 1MΩ  
R4 100kΩ  
R5 470Ω  
R6 47Ω

All  $\frac{1}{2}$ W  $\pm$  5% carbon

See  
**Shop  
Talk**

page 171

### Capacitor

C1 10μF elect. 15V

### Semiconductors

IC1 741 Op. amp 8-pin d.i.l.  
TR1 ZTX300, 2N2926, or  
BC182L silicon npn } See  
TR2 ZTX500, 2N3702 or } text  
BC212L silicon npn }  
D1 TIL220 red light emitting  
diode  
RTH1 GL16 glass bead  
thermistor

### Miscellaneous

S1 s.p.s.t. switch or car ignition  
switch

Stripboard 0.1 inch matrix, 10  
strips  $\times$  24 holes; insulated  
stranded connecting wire; suit-  
able small plastic case, approx.  
75  $\times$  30  $\times$  30mm—Verobox type  
202-2102K or similar; 6-way (2A  
screw) terminal strip.

Approx. cost  
Guidance only

**£4.50**

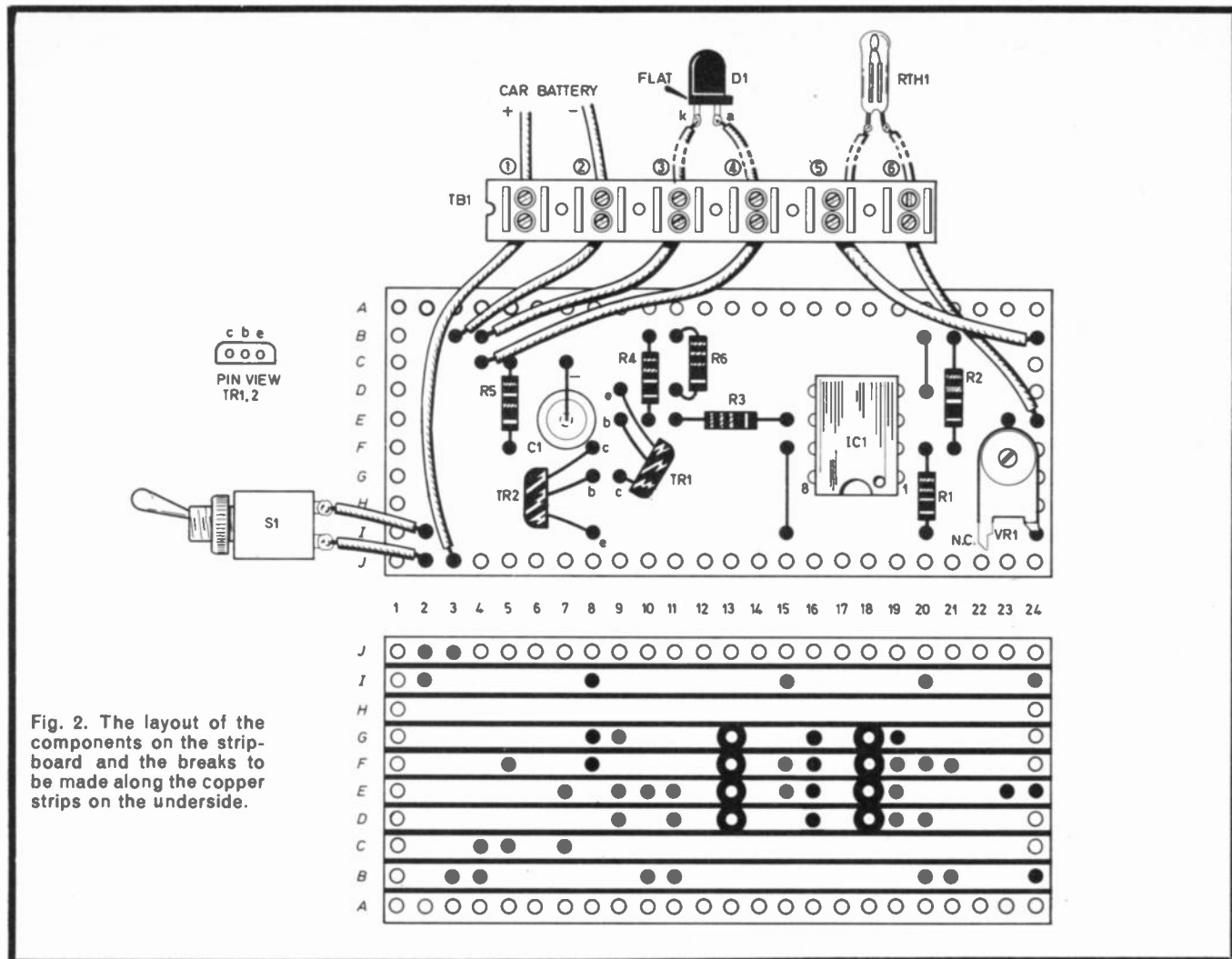


Fig. 2. The layout of the components on the strip-board and the breaks to be made along the copper strips on the underside.

lengths of flying leads to the board to reach the screw terminal block fitted on the outside of the case. The wire feed hole on the case should be fitted with a rubber grommet for protection. The board may be held in place in the case by wrapping it in foam sponge after calibration. This will dampen any vibration resulting from the running of the car. Wire up the switch and terminal block to the board and then calibrate as instructed below.

### CALIBRATION

Before fixing the unit to the car, it must be set to respond to an air temperature of 0 degree Celsius.

Crush some ice in a container until it is "slush". Ensure that the ice is melting, for then it is at 0 degree Celsius (the ice point) but check the temperature with a thermometer if you have one available. Immerse the thermistor in the melting ice and adjust the preset resistor until the l.e.d. just begins flashing. Take the thermistor out of the iced water and as it warms up the l.e.d. will cease to flash.

### THERMISTOR POSITION

The thermistor must be sited in a position where it cannot receive heat from the engine. It must be close to the ground since the conditions for ground frost, giving icy patches on roads, cannot be predicted a few feet above the ground.

The thermistor must also be protected from contact with water splashes and rain, for the cooling produced by water evaporating from the thermistor will cause it to fall to a temperature below the true air temperature. A good position for the thermistor may be behind the front bumper although the best position will be determined by the type of car it is to be used with.

Having decided on the best position for the thermistor, you will need to estimate the length of flex required between the thermistor and the circuit. Care should be exercised in soldering the flex to the thermistor since the soldered joints should be insulated with sleeving to prevent them coming into contact with water or the car body; heat-shrinkable sleeving is ideal for this purpose.

The thermistor should then be glued into the end of a short length of plastic tubing so that although air can circulate round it, it is protected from water splashes.

Any small plastics box may be used to house the circuit board which can then be mounted unobtrusively behind the dashboard of the car, in the glove compartment or even fitted to the parcel shelf using double sided foam pads. Choose a position on the dashboard where it is easy to see the flashing l.e.d.. Drill a hole to take the l.e.d. so that it can be fixed by pushing it into its plastic fixing clip. If this is unacceptable, the l.e.d. may be attached directly to the terminal strip and the assembly positioned in easy view of the driver.

### IN USE

In use it is interesting to note, as one drives along during a frosty evening, the indication given by the device. The likely conditions for ice to form on the roads is clearly indicated—under trees or other sheltered places, in hollows where cold air collects and even a change from cloudy to clear sky. □

# INTRODUCTION TO LOGIC

## PART 11 BY J. CROWTHER

### APPLICATION OF LOGIC TECHNIQUES

#### (3) The Half Adder

The purpose of a Half Adder is to add together two binary digits of a binary number.

Suppose we call the two binary digits to be added  $A$  and  $B$ , the Truth Table will be:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

From the Truth Table it can be seen that the module must have two outputs, a *sum* which goes into the register, and a *carry* which is passed on to the next column.

We only require a *carry* if  $A$  and  $B$  are 1, the Boolean Equation for this is:

$$AB = S$$

This is given by an AND gate as shown in Fig. 11.1.

If we take the case where the sum = 1, the Boolean Equation for the sum output becomes:

$$\overline{A}B + A\overline{B} = S$$

In Boolean Algebra we can add any Identity which is equal to 0, to an equation without altering its value.

Add  $A\overline{A}$  and  $B\overline{B}$  to the above equation and we get:

$$A\overline{A} + \overline{A}B + B\overline{B} + AB = S$$

$$\overline{A}(A + B) + \overline{B}(A + B) = S$$

$$(\overline{A} + \overline{B})(A + B) = S$$

$$\overline{A}\overline{B}(A + B) = S$$

This represents an AND gate fed with  $(A + B)$  and  $\overline{A}\overline{B}$  as shown in Fig. 11.2.

$(A + B)$  is obtained from an OR gate.

It will be noticed that  $\overline{A}\overline{B}$  is the inverse of the carry, and can be obtained by passing the carry through a NOT gate, so the complete module for the half adder becomes as seen in Fig. 11.3.

#### (4) The Full Adder

Since the half adder has no provision for a carry from a previous stage it can only add the first column of a binary number where there is no carry from a previous stage. To add

any other column except the first we must use a Full Adder. This consists of two half adders; the first adds the two binary digits and the second adds the carry from the previous stage to the sum from the first half adder. This arrangement would give two carries, one from each half adder, but there can only be a carry if the two inputs are 1, in which case there would be no sum, therefore there can only be a carry from the first or second stage but not from both. Because of this we can pass the two carries through an OR gate, and so obtain one carry as shown in Fig. 11.4.

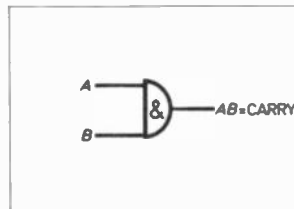


Fig. 11.1. Producing a "carry" in binary addition of  $A$  and  $B$ .

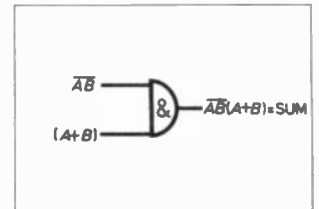


Fig. 11.2. Deriving the "sum" in binary addition of  $A$  and  $B$ .

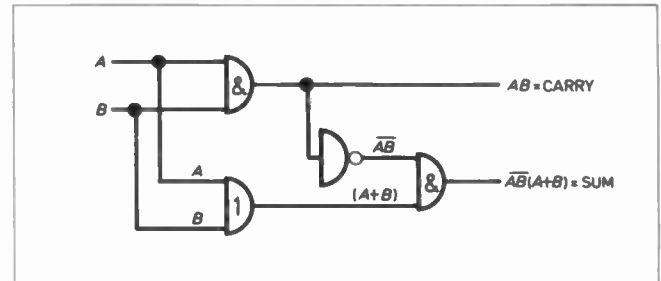


Fig. 11.3. Complete logic module for a half-adder.

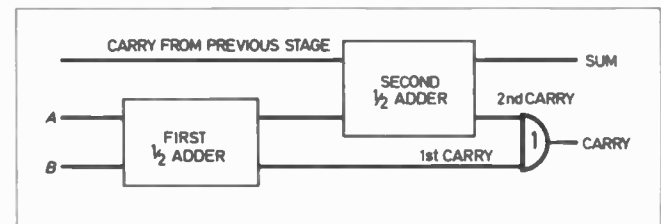


Fig. 11.4. Logic module of a full-adder.

### OTHER GATES FROM NAND GATES

#### (1) The NOT gate

Suppose the two inputs of a NAND gate were strapped together. Both inputs would be fed with  $A$ , and the output  $S$  would be given by:

$$\overline{AA} = S$$

Since  $AA = A$  (Boolean Identity 1) we get

$$\overline{AA} = \overline{A} = S$$

This is the equation for a NOT gate. Therefore we can make a NOT by strapping the inputs of a NAND gate together as shown in Fig. 11.5.

A NOT gate may also be made from a 2-input NAND gate by strapping one input to logic 1.

#### (2) The OR gate

Suppose we fed  $\overline{A}$  and  $\overline{B}$  into a NAND gate, the output  $S$  would be given by:

$$\overline{\overline{A}\overline{B}} = S$$

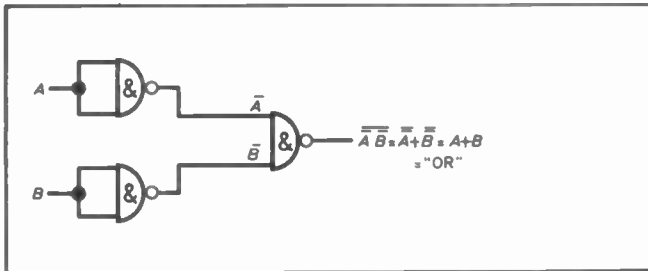


Fig. 11.6. An OR gate using NAND gates.

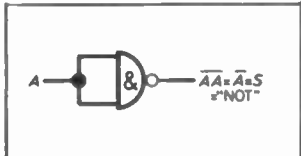


Fig. 11.5. A NOT gate using a NAND gate.

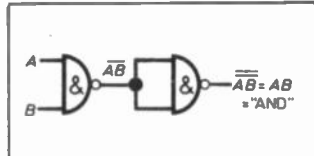


Fig. 11.7. An AND gate using NAND gates.

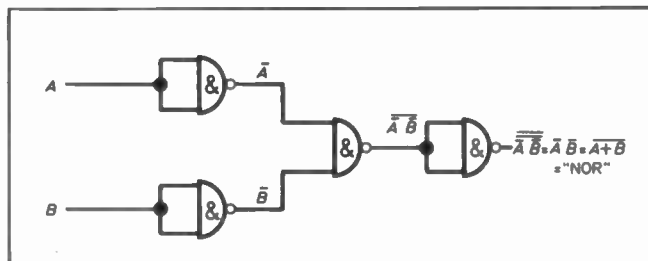


Fig. 11.8. A NOR gate using NAND gates.

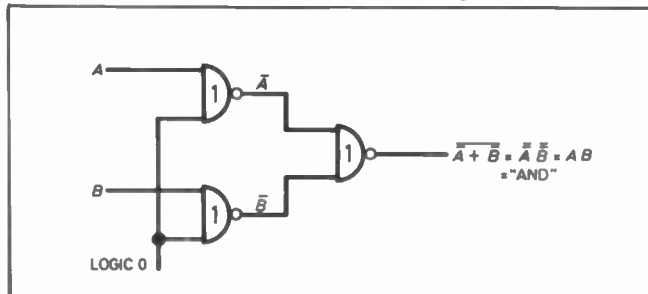


Fig. 11.10. An AND gate using NOR gates.

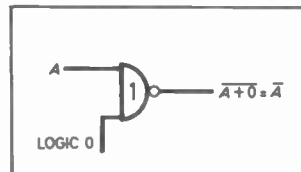


Fig. 11.9. A NOT gate using NOR gate.

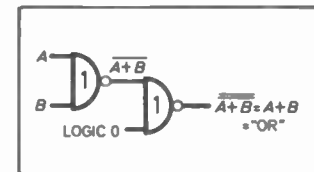


Fig. 11.11. An OR gate using NOR gates.

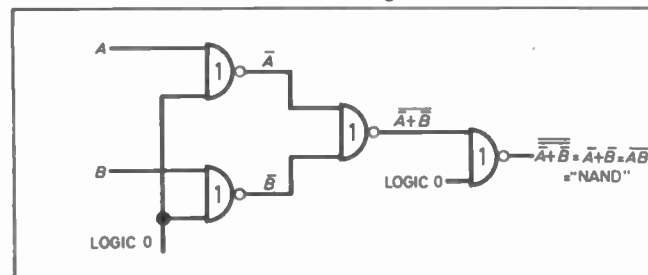


Fig. 11.12. A NAND gate using NOR gates.

If we now apply Demorgan's theorem to this equation we get:  
 $\overline{AB} = \overline{A} + \overline{B} = A + B = (A \text{ OR } B)$

$\overline{A}$  and  $\overline{B}$  can be obtained by passing  $A$  and  $B$  each through a NOT gate, and using NAND gates to form NOT gates we obtain the logic module shown in Fig. 11.6.

### (3) The AND gate

NAND means NOT AND, that is, the inverse of AND. Therefore it follows that AND is the inverse of NAND. So an AND gate is a NAND gate followed by a NOT gate. If we use a NAND gate for NOT gate we arrive at the logic module shown in Fig. 11.7.

### (4) The NOR gate

The NOR gate is the inverse of the OR gate, so if we pass the output of an OR gate through a NOT gate we get a NOR gate. By combining the OR gate in Fig. 11.6 with the NOT gate in Fig. 11.5 we get the arrangement shown in Fig. 11.8.

## OTHER GATES FROM NOR GATES

### (1) The NOT gate

Consider the NOR Truth Table shown below left.

A	B	S
0	0	1
0	1	0
1	0	0
1	1	0

Suppose that the  $B$  input was permanently connected to logic 0, then lines 2 and 4 in the truth table left would not exist. The truth table thus becomes:

A	B	S
0	0	1
1	0	0

It can be seen now that if  $A$  is 0,  $S$  is 1, and if  $A$  is 1,  $S$  is 0. So it is inverting  $A$  and acting as a NOT gate. Therefore a NOR gate connected as in Fig. 11.9 will act as a NOT gate.

A NOR gate with both inputs strapped together will also act as a NOT gate, see lines 1 and 4 in the NOR Truth Table above.

### (2) The AND gate

Suppose we fed  $\overline{A}$  and  $\overline{B}$  into a NOR gate, the output would be given by:

$$\overline{\overline{A} + \overline{B}} = S$$

If we apply Demorgan's theorem to this equation we get:

$$\overline{\overline{A} + \overline{B}} = \overline{\overline{A}} \overline{\overline{B}} = AB = (A \text{ AND } B)$$

$\overline{A}$  and  $\overline{B}$  can be obtained by passing  $A$  and  $B$  each through a NOT gate, and using NOR gates as NOT gates we obtain the logic module shown in Fig. 11.10.

### (3) The OR gate

NOR means NOT OR, that is, the inverse of OR. Therefore it follows that OR is the inverse of NOR, so an OR gate is a NOR gate followed by a NOT gate. If the latter is constructed using NOR gates, we obtain the logic module shown in Fig. 11.11.

### (4) The NAND gate

The NAND gate is the inverse of the AND gate so if we pass the output of an AND gate through a NOT gate, we get a NAND gate. By combining the AND gate of Fig. 11.10, with the NOT gate of Fig. 11.9, we get a NAND gate using NOR gates only. See Fig. 11.12.

**TO BE CONTINUED**

# Everyday News

## ≡ THE AGE OF THE TRAIN

British Rail takes on the airlines with a less than 4½ hours travelling time from London to Scotland

BR "zooms into the 80's" with the APT (*their words not ours*)

★ Speeds in excess of 125mph cut journey time by 15 to 20 per cent

★ Glasgow to London in 4 hours 15 minutes.

Amid all the ballyhoo about locked tilt mechanisms, "sea sickness" from sway and sensor malfunctions due to extreme cold, it must be remembered that the new APT high-speed tilting train, which covered the Glasgow to London run in 4 hours 14 minutes (including stops at Motherwell and Preston), is still a pre-production prototype built to evaluate the new design.

The Advanced Passenger Train is a high-performance, electric powered train with tilting coaches for passenger comfort when the train traverses curves at speed. First conceived in 1969, it was designed by BR engineers and built by British Rail Engineering Ltd to operate at speeds up to 125mph and more on existing tracks and within the present system.

### Why APT?

Nearly 50 per cent of the major rail network is on curves so average speeds and point-to-point journey times are primarily governed by permanent speed restrictions at these points.

To enable conventional trains to go round curves

faster tracks are canted, the outer rail raised above the level of the inner. Even with this arrangement only comparatively low speeds are possible.


Instead of the costly exercise of straightening out the most severe curves, BR's answer is the APT.

### How It Works

Using an entirely new suspension design it allows the train to take curves 20 to 40 per cent faster than conventional rolling stock. Tilting the coach bodies by as much as 9 degrees passenger comfort is maintained. Also, test running had

shown that a tilt failure would be rare, it was decided to fit a device to lock a coach in the upright position in the event of a failure.

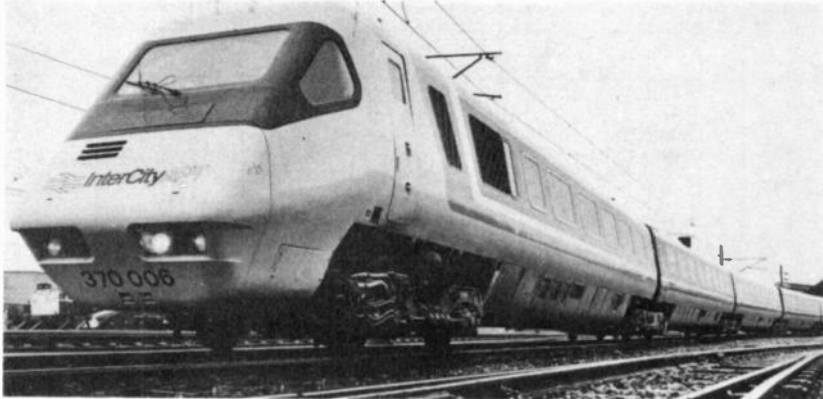
BR would not divulge all the technical details, but we understand that electronic monitoring of the various systems is used extensively.



The prototype 4000hp Power Car contains most of the monitoring equipment, power equipment and braking and tilt sensing equipment. It is hoped to fit this into a driving power car including the driving cab.

The APT instrument and control panel layout of the driving cab. Surprisingly, no tilt angle dial or indicator could be seen.

The APT taking a curve at high speed.

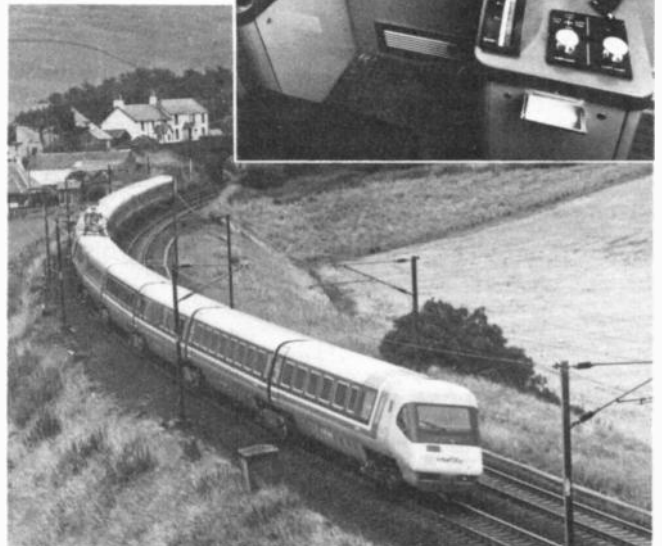

### Hot Camera

An experimental solid state infra red camera that detects small variations in heat and creates recognizable television pictures of warm objects in a room totally dark to the human eye was demonstrated by RCA researchers recently.

During the demonstration, the camera was able to discriminate veins in a human hand and detect residual thermal prints on objects that had been touched by a hand for a second or less.

The heart of the camera is a high performance imager, about the size of a "dime" or half-pence, containing over 8,000 infra red sensitive elements. While picture quality is less than commercial TV standards, present progress indicates that the technology has the potential for full-television resolution.





## ANALYSIS

### ON THE RECORD

When, one hundred and five years ago, Thomas Alva Edison made the first ever recording of sound he could hardly have foreseen what was to follow. His crude but highly original tin-foil phonograph signalled the start of a whole new industry although some fifty years were to elapse before sound recording and reproduction started to approach the levels of realism and fidelity now taken for granted.

For the real enthusiast, however, the search for perfection continues in pickups, turntables, amplifiers and speakers. Who a few years ago would have imagined that the domestic user would be offered a player unit in which the record is firmly attached to the turntable by suction, or another in which a turntable weighing 20 kg runs on a cushion of air supplied from an external pump; Or that keen types could be found willing to fork out £10,000 for a pair of speakers?

The hi-fi industry is awash with gadgets and gimmicks. One of the latest is digital time-lag to give the illusion of altering the size of your living room to suit the sound, from an intimate night club to a full-sized auditorium.

It is surprising that the classical disc record has lasted so long with its spiral groove impressed with an analogue recording track mechanically in contact with the pickup stylus. Much of the technology has been devoted to overcoming the inherent problems in such a system.

Digital recording on compact discs will dispense with the delicate mechanical intricacies of conventional pickups and the heavy engineering of turntables, both very expensive. By using laser scanning of stored digital codes on a sealed disc there is no physical contact and therefore no wear on the record or laser "pick-up", no rumbles or crackles and an hour of hi-fi can be packed into a disc smaller than today's single.

Should we therefore pause before buying "old-fashioned" records, turntables and pickups and wait, perhaps for only a year or so, for digital discs and laser scanning? Not really, says the hi-fi industry. Analogue systems, they say, are still being improved and the weakest link now in the hi-fi chain is the speaker which digital technology can not alter.

Brian G. Peck

## RADIO SURVEY

The British National Oil Corporation is conducting a survey of microwave radio reception over the North Sea with a view to pinpointing periodic deterioration of signals.

A Microdata M1600L portable data logger is being installed on a drilling platform in the Beatrice oil field. It will automatically record field strength, date, time of day and other relevant information for subsequent computer analysis on-shore.

Nearly all oil platforms in the North Sea depend for telecommunication either on line-of-sight microwave links or tropospheric scatter links for contact beyond the horizon.

The BBC has produced its first Digital SECAM to PAL transcoder, using the CCIR recommended digital sampling standard.

British Telecom's suggestions box led to a £6,000 award divided between David Atkins and Tim Walker for their idea of an automatic scanner for testing electronic telephone exchanges.

It does the work in a single night which formerly occupied a skilled engineer for a week. Known as WAM—the Walker Atkins Multitester—it is now being used at exchanges throughout the UK.

Tandy Corporation (Branch) UK have announced the signing of the world famous science writer Isaac Asimov for extensive advertising and product promotion.

## WIN £1000

British Telecom's Prestel world viewdata service is offering a £1,000 prize to the designer of the best Prestel adaptor for the Sinclair ZX81 personal computer.

The prize will be awarded to the adaptor which best combines low price, elegant design and practical robustness. The working design submitted must be capable of being modified to receive approval for attachment to the telephone network.

Closing date is March 14 and details, specification and entry forms are available from Prestel Headquarters, Telephone House, Temple Avenue, London EC4 0HL.

## BETTER VHF RADIO RECEPTION IN SOUTH-EAST

*Vertical Polarised Transmissions give improved VHF service for motorists and users of portables.*

THREE new high power VHF transmitters came operational at Wrotham, Kent, early last December. The new transmitters radiate BBC Radio 1 and 2, Radio 3, and Radio 4 including some educational programmes. This station serves nearly 13 million people in London and South East England.

A new mast has been built alongside the old one which was originally used for early experiments in VHF broadcasting thirty years ago. The new mast is 177 metres high and carries aerials specially designed to radiate both horizontal and vertical polarisations. The total power radiated has been doubled.

**Vertically polarised signals are required for good reception with portables and car radios.**


Listeners with fixed roof or loft horizontal aerials for receiving Wrotham stereo transmissions will be unaffected by the addition of the vertical radiation.

This new system should help the BBC's campaign to encourage wider use of VHF. Medium wave reception is already poor in some areas and deteriorates at night; this situation will get worse with additional European stations coming into operation. The answer, the BBC says, is VHF—which provides interference-free reception and permits higher quality and stereo transmissions.

● Wrotham is the first high-power VHF radio station in the country to radiate both horizontal and vertical polarisations.

*Improved reception for v.h.f. portables using vertical whip aerials and v.h.f. car radios is promised from the re-equipped v.h.f. sound radio transmitters at Wrotham, Kent. As well as six new 20kW Marconi transmitters the radiating elements now have vertical as well as horizontal polarisation.*

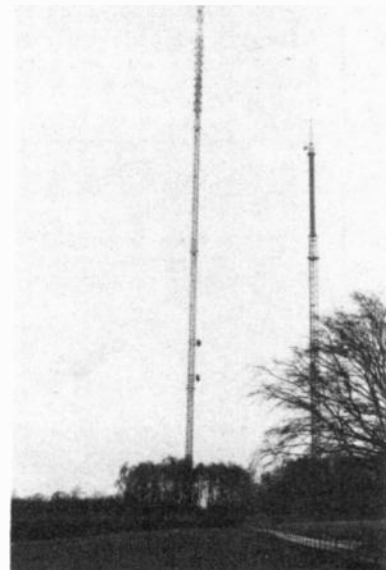*Other v.h.f. stations will have vertical polarisation added as they take their turn in the modernisation programme.*



BY L.A. PRIVETT

# Car Probe



When the probe tip is placed on a connection with a positive potential, a current (conventional) will flow through the RED half of D1, a RED/GREEN bi-colour l.e.d., then through D3, R2 being the current limiting resistor. D2 prevents any current flowing into the other branch of the circuit. See Fig. 2a.

Fig. 2b shows the direction of current flow (conventional) when the probe tip is placed on a negative or 0V connection. That is, from the +12V terminal of PL1, through D2 and current limiting resistor R1 then through the GREEN half of D1.

## A.C. VOLTAGES

Should the probe tip be placed on a connection with an alternating voltage the two halves of D1 would each turn on and off in rapid succession thus resulting in an amber colour, enabling the probe to indicate a further state, that of an a.c. signal being present.

The 12V lamp LP1 has been incorporated to indicate that the probe is connected to the car battery supply and also, perhaps more importantly, to illuminate those dark corners

WHEN testing the electrics, tracing cables or simply adding new accessories to the car, it is often desirable to know the polarity of a wire or connector at a point where it is impossible to determine this by the colour or destination of that wire.

It was for these reasons that this probe was designed to give an instant indication of the unknown polarity with the use of a bi-colour l.e.d. If it glows red, the potential is positive and green indicates 0V (chassis on negative earth cars).

## CIRCUIT OPERATION

The principle of operation of the probe is really quite simple, using only six discrete components and the circuit diagram is shown in Fig. 1.

The probe is powered from the car battery circuit via PL1, which in the authors case was an accessory plug of the type which fits the cigar lighter socket.

Finished probe with the car accessory plug, PL1, alongside it. A coloured band was added around the case to enhance the appearance.

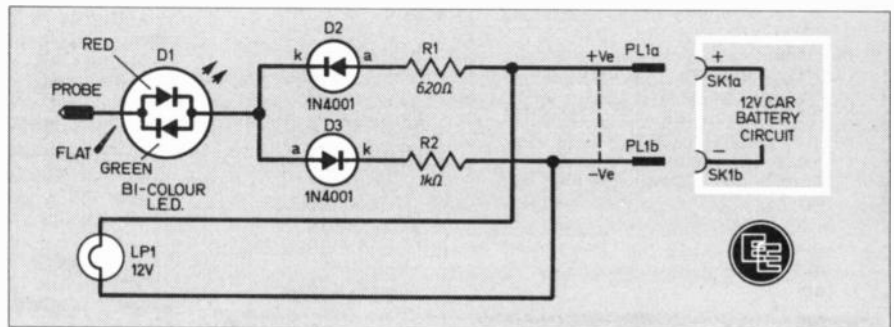
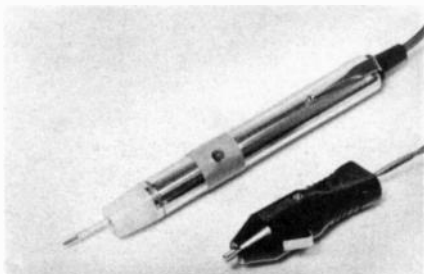


Fig. 1. Complete circuit diagram of the Car Probe. Note that SK1 is the cigar lighter socket.

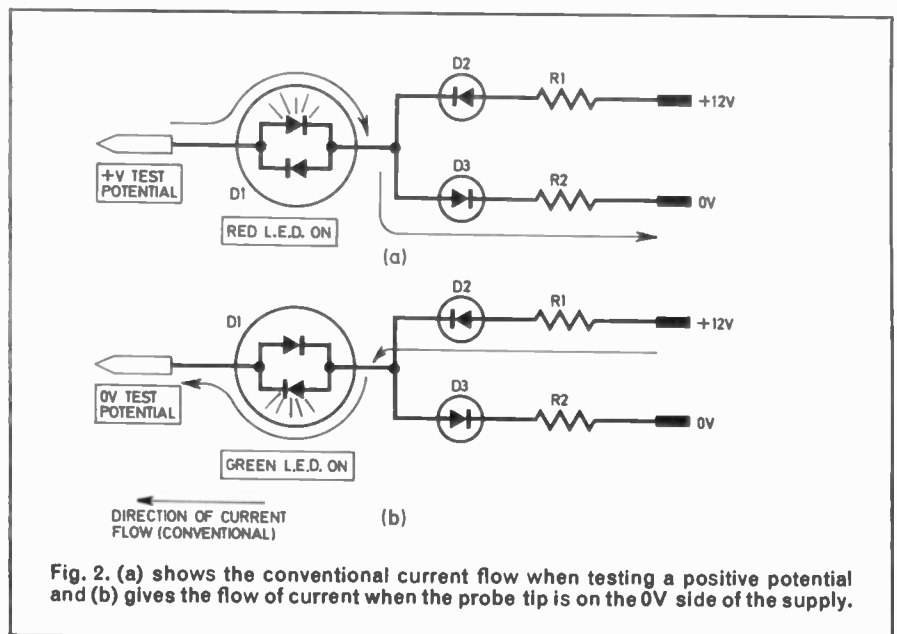


Fig. 2. (a) shows the conventional current flow when testing a positive potential and (b) gives the flow of current when the probe tip is on the 0V side of the supply.

under the bonnet and beneath the dashboard when looking for the right wire.

## PROBE ASSEMBLY

Finding a case for the probe requires careful consideration, as it has to be both hand held and fairly robust for the kind of environment in which it will be used. The prototype was built into an empty "light pen" holder which fortunately had a screw-in bezel to hold LP1 and the tip.

However, many tubular containers such as a large cigar tube or small torch housing could be adapted. A further alternative would be to build it into a hand held control box (such as the Vero 202 21026G) with the probe tip protruding from one end.

## COMPONENTS

### Resistors

R1 680Ω  
R2 1kΩ

All ½W carbon ±5%

### Semiconductors

D1 bi-colour l.e.d. red/green  
D2,3 1N4001 1A silicon or similar (2 off)

### Miscellaneous

LP1 miniature 12V bulb, L.E.S. or flange  
PL1 car accessory plug, for cigar lighter socket  
Probe case (see text); brass rod 45mm long, 1.2mm diameter (for probe); sleeved grommet; epoxy resin adhesive; p.v.c. sleeved wire; 3.5m twin cored cable; heat shrink sleeving (or electrical tape).

Approx cost £3 excluding Guidance only case

See **Shop Talk**

page 171

## WIRING

The twin-cored cable is fed into the probe housing through a sleeved grommet and soldered directly to the leads of R1 and R2. As the components are all soldered together in a "spider's web" fashion it is important to make a good mechanical joint before soldering. All joints and bare metal component leads must be insulated preferably with heat-shrink sleeving but electrical insulating tape will suffice, particularly if the probe is to be in a metal housing.

The wiring of the components is shown in Fig. 3.

The probe tip itself was made from a brass rod, approximately 1.5mm diameter and this was glued with epoxy resin adhesive into a hole drilled into the bezel. The end was fashioned into a point and a sleeve was slipped over the protruding length to prevent an accidental short circuit.

D1 was also glued into a hole in the probe body and LP1, an L.E.S. or flange type bulb was soldered directly to two wires from R1 and R2. The base of the bulb was then bound with tape to form a large enough ferrule to remain captive in the probe bezel.

## PLUG

The power for the probe is picked up via PL1 and as discussed before, this is a plug designed to fit a cigar lighter socket. This was found to be

the most convenient method for use on a car as it is fused and controlled by the ignition switch but an alternative method of connection may be used.

When wiring PL1, remember that the positive connection on *negative earth wired* vehicles will be the spring loaded tip of the plug and the chassis or negative connection is the spring on the side of PL1. These connections must be reversed for *positive earth wired* automobiles.

## IN USE

To test the probe, simply insert it into the cigar lighter and try it on connections of known polarity, the most obvious being the battery itself! The positive terminal should result in D1 glowing red and the negative terminal resulting in D1 showing green.

If these results are reversed, D1 may be soldered in incorrectly; remember that the anode (a) of the red l.e.d. within D1 is indicated by a "flat" on the body and it is this lead which is connected directly to the brass probe tip. Another possibility is the terminals of PL1 have been reversed.

The probe can also be used to examine power supply conditions on both digital and analogue circuits, provided that the probe power is taken from the board under test.

It must not, however, be used for high voltages or mains. ☞


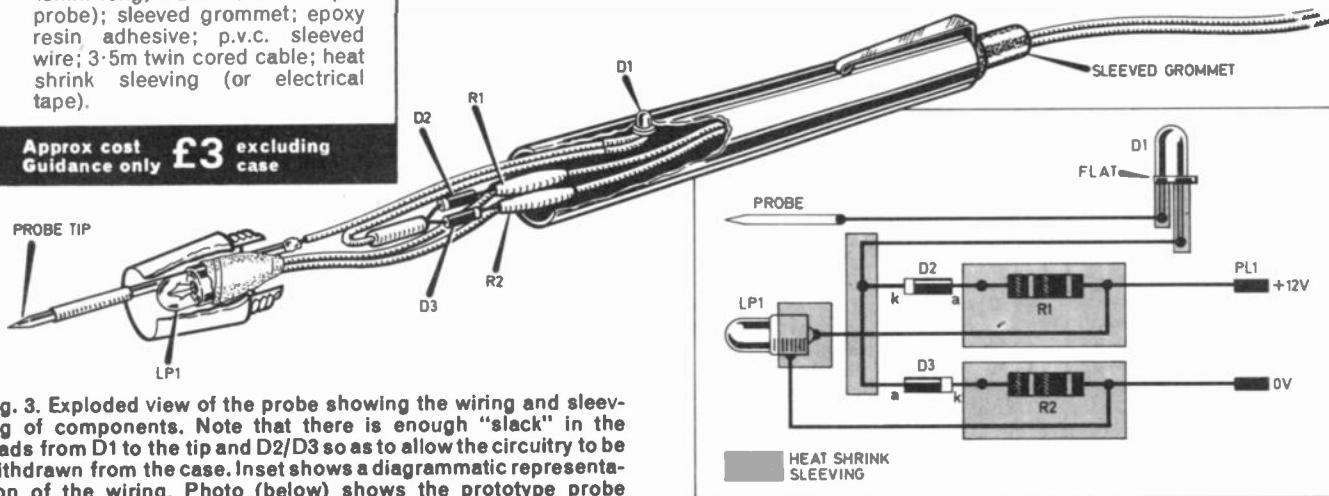


Fig. 3. Exploded view of the probe showing the wiring and sleeving of components. Note that there is enough "slack" in the leads from D1 to the tip and D2/D3 so as to allow the circuitry to be withdrawn from the case. Inset shows a diagrammatic representation of the wiring. Photo (below) shows the prototype probe with tip and bezel removed.

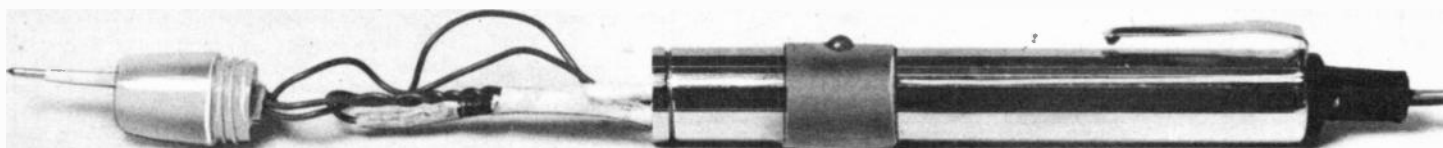

# RADIO WORLD

By Pat Hawker, G3VA

## Gas Radio

MR. W. E. CAUGHEY, G12DZG of Belfast recently drew to my attention some fascinating correspondence in *The Sunday Telegraph* about the way in which radio listeners used to run their radio sets from gas using thermoelectric techniques. It seems worth adding a little background information. Such systems, still used for some specialised purposes, make use of the fundamental principle that when the junctions between two dissimilar metals are at different temperatures a small amount of electricity is generated, the so-called Peltier effect which is, in practice, more often used for refrigeration than for electrical generation.

In the late 1920s and early 1930s the "national grid" electricity supply mains still did not reach very many homes, and of the homes that did have electricity quite a few were supplied with direct-current (it was not until after World War II that d.c. disappeared from some London districts). Most early domestic radio sets, other than crystal sets, were intended for use with "high-tension" (h.t.) batteries, which were typically 90 or 120 volts with round Leclanché cells (it was not until the 1940s that layer-type batteries came into wide use), and "low-tension" filaments were powered from 2V lead-acid rechargeable "accumulators" which when discharged were taken along to a local radio shop or garage for recharging.

Many sets also needed a 9V grid-bias battery although very little current was drawn from this. The h.t. batteries were not particularly cheap and mains-operated "battery eliminators" were popular in the late 1920s using metal rectifiers but often with poor ripple filtering.

An early gas-powered unit was the Thermataix introduced in 1927 as a substitute for the i.t. accumulators and contained thermocouples heated by small gas jets. An example can still be seen in the Science Museum in Kensington, London. Later Milnes Radio Co Ltd. of Bingley marketed a complete radio incorporating a thermo-electric generator and published a booklet "radio for the gas user".

In the 1950s, Philips of Eindhoven developed a thermo-electric generator for homes without either electricity or gas supplies. This was powered by an oil lamp and may have been the inspiration for an even later unit of Chinese manufacture that supplied 60 volts h.t. and 1.5 volts i.t. when placed on top of a hurricane lamp; an example of this device can also be seen in the Science Museum.

## Rechargeable h.t. batteries

Thermo-electricity was by no means the only technique used in the early days to lower the cost of listening. The same Bingley firm, Milnes Radio, also marketed a rechargeable h.t. unit which they recommended particularly for use with sensitive

short-wave receivers as a virtually "silent" source of energy, without mains hum. This consisted of a battery of alkaline cells with nickel-cadmium plates.

The unit had an internal switch that changed the cells from being series connected into banks of four cells in series-parallel so that the battery could then be recharged from a large 6V accumulator. Such units were available up to 200 volts though I am not sure if they were ever widely used.

It was once my experience to work for a while in a radio station where about a dozen powerful receivers, mostly the famous National HRO type, were all operated entirely from a large bank of batteries as no mains supplies were available. At the other end of the scale I remember obtaining in 1945 one of the small hand torches made by Philips that incorporated a small rotary generator that was turned by squeezing a paddle with the palm of one's hand—though mine soon stripped its gear. Perhaps it was one of the products made in the Eindhoven factory during the occupation of Holland that were deliberately made none too reliable since they were mostly destined for the "grey mice" occupation forces.

As a final note on this subject, modern thermo-electric generators run from propane gas have been quite widely used for

## Picture quality

In the latter part of 1981, the Royal Television Society held a discussion meeting that turned out to be of unusual interest. Entitled "Picture Quality—the Aesthetic and Technical Arguments" it succeeded in bringing together two very different strands of television broadcasting: famous drama producers and the engineers who are concerned with the technical quality of the transmitted pictures. It soon became clear that these two aides look at things very differently and often use the same words to mean different things.

Producers tend to like working with film because they believe it is more suitable for capturing "moods"—engineers often dislike film because of the scratches, blemishes and colour tints that can often be seen. They find it inconceivable that producers sometimes shoot a whole production with a gauze placed in front of an electronic camera when they could get the same effect (if really needed) by narrowing the depth of focus.

What really seems to be needed is for producers to discover how to use electronic systems to best advantage and for engineers to recognise, perhaps rather more, the seething resentment of producers when they find their carefully composed shots are graded "poor". Both sides seek the same thing—good television; both sides need to learn to speak the same language.

communications equipment, particularly on some American railroads: unfortunately the economics generally make them unattractive where other types of supply can be used.

## Getting on 10.1 MHz

The changing pattern of amateur radio equipment over the past decade or so has, rather regretfully, brought it casualties. One of these has been the virtual disappearance of the "junk-box" transmitter built in a couple of evenings on the kitchen table. There are a few exceptions. The very low-power (QRP) enthusiasts still tend to roll their own—and those who venture up into the microwave bands seldom have any alternative.

Then again there are still relatively simple transmitters covering a limited number of h.f. bands, or those constructed from kits or with the help of bought-in printed circuit boards (although a p.c.b. is often unsuitable for random junk-box components). But most amateurs, today, at least when first licensed, tend to buy a factory-made 144MHz or h.f. transceiver. It would indeed be irresponsible to suggest that many newcomers could hope to design or build units as complex or as compact as many of those now on the market.

But the small black boxes can be rather inflexible. The opening on January 1, 1982 of the new 10.1 to 10.15MHz band (permission for British amateurs to use the new 18 and 24MHz bands has been deferred) brought a problem to amateurs other than those who have recently bought the new "9-band" models. Fortunately some older models can be adapted quite simply by those prepared to delve inside the black boxes. The popular FT101-series, for instance, already have a 10MHz standard-frequency (WV) reception facility and it is not difficult to make the equipment transmit in the new band. The American Drake models also seem relatively easy to adapt and a friend tells me that he has successfully converted an oldish Heathkit HW101.

My own (temporary) solution was to dust off a very old home-made transmitter complete with 40-year-old 807 valve and modify this for 10.1MHz instead of 7/14-MHz. In a matter of hours the old blooper was in action on morse c.w. with about 20 watts input on the new band—for which in any case European amateurs have been asked not to use telephony in view of the limited frequency space.

Certainly in early January many hundreds of amateurs were active on the new band and finding it useful for local, medium-distance and long-distance contacts. As for the nearby 31-metre broadcast band there is every reason to believe that this will be an excellent frequency for working ("via long path") stations in Australia and New Zealand. A very valuable acquisition even though only 50kHz wide!

# MASTER ELECTRONICS NOW!

## The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

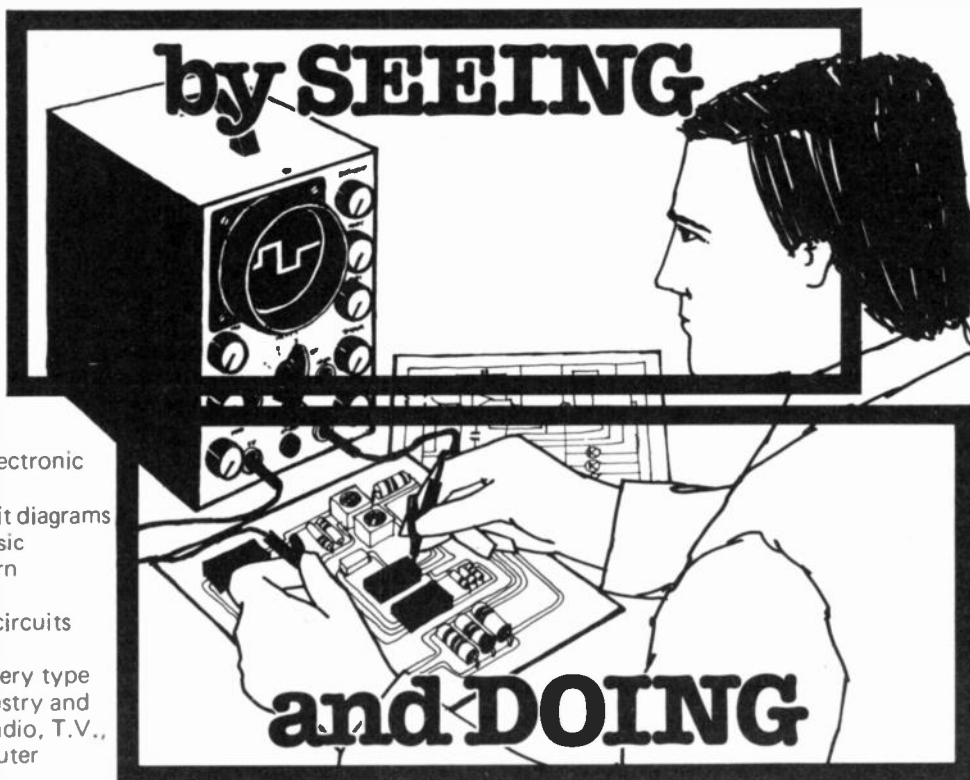

### New Job? New Career? New Hobby? Get into **Electronics** Now!

# FREE!

COLOUR BROCHURE



Please send your brochure without any obligation to

I am interested in:

NAME \_\_\_\_\_

COURSE IN ELECTRONICS as described above

ADDRESS \_\_\_\_\_

RADIO AMATEUR LICENCE

MICROPROCESSORS

LOGIC COURSE

OTHER SUBJECTS \_\_\_\_\_

POST NOW TO:

BLOCK CAPS PLEASE

EE/3/820

**British National Radio & Electronics School** Reading, Berks. RG1 1BR.

# CITIZENS' BAND RADIO IN THE UK

ACCORDING to the world's first Citizen Band user and manufacturer, one Al Gross from the East Coast of America, CB or Open Channel radio has its origins in the UK. This startling revelation came during a meeting with this revered sexagenarian on the day that CB radio became legal in this country, November 2, 1981.

Apparently Al was working for the British Government during World War 2 and was the instigator of a limited range transceiver for the use of the ground resistance forces on the continent to contact the pilots of the famous Mosquito fighter/bombers.

Be this as it may, nothing further was done in this country about this simple two-way communication idea until the oil crisis eight years ago. Not that this brought CB into use. It is just that with all the media coverage of American truckers communicating with each other to find the petrol they so badly needed to maintain their business, interest was aroused in the UK in this novel form of person to person communication.

What happened in the USA is well documented—the biggest CB boom the world has ever seen, with endless films and songs featuring this communications medium. Concurrent with this craze the governing body of the American airwaves, the Federal Communications Commission (FCC), changed the number of available channels from 23 to 40, due to the overcrowding of the air in the more densely populated areas.

Little happened in the UK during the following five years . . .

## ILLEGAL ENTRY INTO BRITAIN

The year was 1978 and large quantities of the new 40-channel AM rigs went on sale in the USA. Unfortunately with the effects of the aforementioned channel crowding the craze had by then passed and the market had all but collapsed. Over supply then led for a search of an English-speaking nation that knew all about the CB folklore, and was a willing marketplace.

So from 1978 onwards the FCC type CB equipment came into the UK in their illegal thousands. Informed

By G. Baskerville

opinion put the number of operating illegal transceivers to be almost a million at the peak of the under-the-counter trade. However illegal it was, no Government can ignore that number of voters who are willing to defy the then law of the land.

## CB BECOMES LEGAL

The government was forced into action and a Green Paper published in August 1980 outlined the basis of a British "Open Channel" service. It came to the conclusion (not, unnaturally) that there was a strong case for CB radio and favoured a much higher operating frequency around 928MHz, and seemed to favour FM modulation, along with our European cousins.

This created fairly considerable political activity from many vested interests, in the main opposed to the higher frequency. But in spite of all this the Home Office Radio Regulatory Department produced two performance specifications in April 1981. They were MPT1320 and MPT1321 and specified equipment for use on 27MHz and 934MHz respectively. The fact that the specifications were for angle modulated equipment brought uproar from the more responsible AM users who after all had lobbied for a British CB service and quite naturally had wanted their American AM FCC sets legalised.

In reality the Home Office had to choose a system that would not interfere with either broadcast or emergency service frequencies, and by making the specifications very "tight" would make for better quality.

The Home Office was able to draw on the experience gained with Private Mobile Users and knew that the better voice quality and range of FM equipment would meet all the basic requirements of a British CB system.

October 1981 saw the change to the Wireless and Telegraphy Act to allow the use of this new equipment with the appropriate licence as from November 2, 1981.

## CB EQUIPMENT

Transmitting/receiving equipment for Citizens Band divides into three main groups: mobile, handheld and base station. A variety of mobile equipments are available and as this is the type of equipment most in demand, at least initially, by newcomers to CB we have concentrated on mobile transceivers in the following introductory survey of commercial equipments.

Mobile transceivers now on the market fall broadly into two classes: the less expensive basic models costing around £70 and the more sophisticated models costing £90 and upwards. We have tried out a model from each class and hope our comments will assist those who are about to make their choice from the bewildering range of models on offer.

The accompanying table sets out the most important features of CB equipment currently available, and covers mobile, handheld and base station models. As this table shows, only a limited number of base station equipments are at present available, although several firms have indicated their intention to market models.

A similar situation exists with handheld equipments. There is potentially a large market for such "walkie-talkies", but early reports indicate that some of the cheaper handheld transceivers are disappointing in their performance. Technical improvements are to be expected in this area—and we at present withhold detailed comment on this type of instrument.

What can be said is that almost all CB equipment listed is designed and produced in the Far East. Many undoubtedly share a common circuit technique and, whatever their Brand name, will differ principally in the more superficial matters and in external details and presentation.

## MAKING A CHOICE

Assuming that you require a transceiver for mobile use what do you look for? All the legal 27MHz units are stamped with CB 27/81 on the front fascia; any unit that does not have this is either an illegal AM unit or a continental FM set that operates on totally differing frequencies.

Basic units such as the Fidelity CB1000, Amsrad CB900, Binatone Speedway and Audioline PT340 are all imported by reputable companies and sell for around £70. For this outlay you obtain the transceiver, a PTT (push to talk) microphone, wiring, and installation brackets and instructions.

As an example of this kind of basic transceiver we tested the M2 unit from CB radio specialists John Woolfe Racing. This transceiver has, in common with all units in this price sector, a rotary 40 channel selection switch with l.e.d. readout, an on/off volume

switch and squelch control, and a signal strength and power meter.

The first two controls are self explanatory, however the squelch control may be a little unfamiliar. Basically the squelch control allows the user to cut out atmospheric and weak signal noise thus only hearing the stronger and more local transmissions. Best position for this control is just past the point where the worst of the interference is blanked out.

The signal strength and power meter allow you to monitor the power you are transmitting and the strength of the incoming signal. You can find



out how much power you are transmitting by asking another CB user what the reading is on his meter. Experience will tell you whether it is adequate allowing for the range required.

## INSTALLATION

If you are installing the unit yourself then a few rules must be adhered to. First, never try and transmit with the antenna disconnected. Secondly, always match the set to the antenna.

Power source is taken directly from the car battery.

Having got power to the unit the

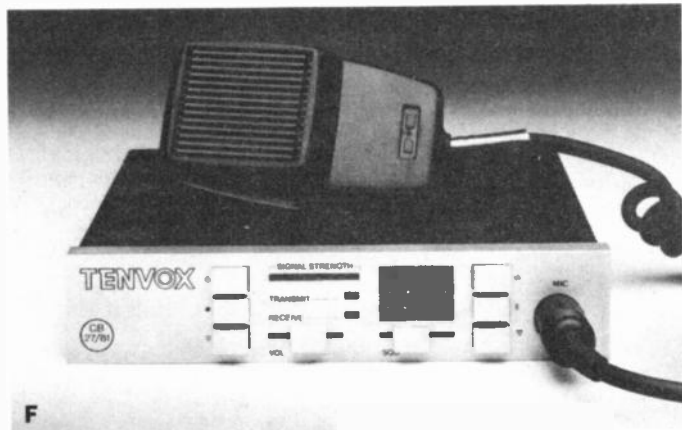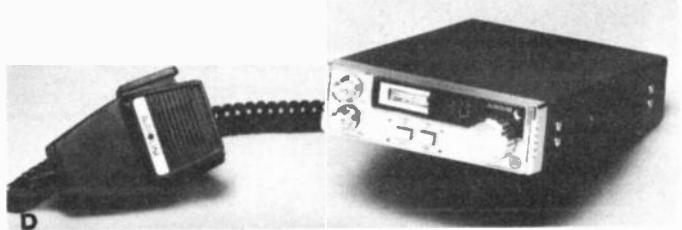

Representative selection of CB transceivers for the UK market. **A** JWR model M2 mobile. **B** JWR purpose built base station. **C** Transcom GBX4000 mobile. **D** Audioline PT340 mobile. **E** Midland 3 channel handheld. **F** British made Tenvox mobile.



next job is to match your antenna. This is simply done by using a Voltage Standing Wave Ratio meter (SWR meter for short) connected between the set and its antenna. By pressing the microphone lever you will obtain

a reading on the meter. This must be lower than 2:1 (and preferably less than 1.5:1) and is obtained by altering the length of the antenna whip following the manufacturers instructions.

If your antenna is not matched with the unit you will (a) have a poor transmission range and (b) harm the unit as power is "reflected" back into the transceiver as heat.

## LEGAL CB TRANSCEIVERS AND THEIR FEATURES

NAME (Distributor)	MODELS	MOBILE	BASE STATION HAND HELD	R.F. GAIN	MIC. GAIN	CHANNEL PRIORITY	PUBLIC ADDRESS FACILITY	TO NE CONTROL	ROGER BLEEP	TYPICAL SELLING PRICE
<b>ACADEMY</b>										
(Academy Electronics)	501	✓								£69.95
	502	✓		✓			✓			£79.95
<b>ALBA</b>										
(Alba Electronics Ltd)	CBM1	✓				✓				£74.00
	CBH 1		✓	2 Channel						£23.00
	CBH 2		✓	40 Channel		✓				£65.00
<b>AMSTRAD</b>										
(Amstrad Consumer Electronics)	CB 900	✓		✓				✓		£75.00
	CB 901	✓		✓		✓	✓		✓	£85.00
<b>AUDIOLINE</b>										
(Harry Moss International)	PT 340	✓								£90.00
	PT 341	✓		✓	✓		✓	✓		£110.00
<b>BINATONE</b>										
(Binatone International)	Speedway	✓								£79.95
	Route 66	✓					✓			£89.95
	Five Star	✓		✓	✓		✓	✓		£99.95
	Breaker-phone	✓			✓		✓	✓		£109.95
	Long Ranger 6		✓	6 Channel						£59.95
	Long Ranger 12		✓	12 Channel						£69.95
<b>COLT</b>										
(Shellpost Ltd)	295	✓								£85.00
<b>CYBERNET</b>										
(Goodmans Ltd)	BETA 1000	✓								£72.00
	BETA 2000	✓					✓	✓		£80.00
	BETA 3000	✓		✓		✓	✓	✓		£95.00
<b>DNT</b>										
(Radiotechnic Ltd)	M 40 FM	✓								£85.00
	B 40 FM		✓							£95.00
	HF 12/3 FM		✓	3 Channel						£41.35
	HF 13/40 FM		✓							£70.82
<b>FIDELITY</b>										
(Fidelity Radio Ltd)	CB 1000	✓								£69.95
	CB 2000	✓		✓	✓	✓	✓	✓		£89.95
	CB 3000		✓	✓	✓	✓	✓	✓		—
<b>GRANDSTAND</b>										
(Bee-Ware Ltd)	Buzzing Bee	✓		✓						£70.00
	Hawk	✓		✓						£80.00
	Bluebird	✓				✓				£99.00
	Gemini	✓		✓			✓			£120.00
	Base		✓	✓			✓	✓		£279.00
	Interceptor		✓	2 Channel (14 & 19)						£29.00
	Communicator		✓	40 Channel						£69.00



## OPERATING

Having correctly installed your unit, switched on and set the squelch control, what then?

Although there are 40 channels three of these have specific functions.

Channel 9 is for emergencies only, designated for use where life or property are considered to be at risk.

Channel 14 is the communication or "breaking" channel.

Channel 19 is the mobile or

"truckers" channel where motorists can obtain up to the minute traffic reports from other road users.

After selecting channel 14 what usually happens is that people become "mic shy" and literally can't

## LEGAL CB TRANSCEIVERS AND THEIR FEATURES (continued)

NAME (Distributor)	MODELS	MOBILE	BASE STATION HAND HELD	R.F. GAIN	MIC. GAIN	CHANNEL 9 PRIORITY	PUBLIC ADDRESS FACILITY	ROGER BLEEP	TYPICAL SELLING PRICE
<b>HARVARD</b>									
(Harris Overseas)	400 M	✓		✓		✓		✓	£80.00
	402 MPA	✓		✓		✓	✓		£80.00
	420 M	✓		✓		✓	✓		£100.00
	410 T		✓	✓	40 Channel				£80.00
	0-2-0		✓		2 Channel				£20.00
<b>JWR</b>									
(John Woolfe Racing)	M 1	✓					✓		£65.00
	M 2	✓					✓		£86.00
	Diplomat 40		✓	✓		✓		✓	£200.00
<b>MIDLAND</b>									
(Plustronics Ltd)	2001	✓					✓		£69.95
	3001	✓		✓			✓	✓	£79.95
	4001	✓		✓	✓		✓	✓	£89.95
	79-200		✓						£149.95
	Ready Rescue			✓		✓			£72.95
	75-720		✓		3 Channel				£59.95
<b>RADIOMOBILE</b>									
(Radiomobile Ltd)	CB 201	✓							£100.00
	CB 202	✓		✓		✓	✓	✓	£120.00
	CB 203		✓	} Details not finalised {					£149.00
	CB 204		✓	} Details not finalised {					£230.00
<b>REALISTIC</b>									
(Tandy Corporation)	TRC 2000	✓		✓	✓		✓		£99.95
	TRC 2001	✓					✓		£79.95
	TRC 1001		✓		40 Channel				£119.95
<b>ROTEL</b>									
(Rotel Hi Fi Ltd)	RVC 220	✓							£70.00
	RVC 230	✓		✓			✓	✓	£80.00
	RVC 240	✓		✓	✓	✓	✓		£90.00
<b>TENVOX</b>									
(Voxson Audio)	Tenvox CB	✓				✓			£110.00
N.B.—This is British made with Plessey components.									
<b>TRANSCOM</b>									
(Transcom International)	GBX 2000	✓							£69.95
	GBX 4000	✓		✓		✓	✓	✓	£89.95
<b>UNIDEN</b>									
(Wallace Tele- communications)	UNIACE 100	✓					✓		£99.00
	UNIACE 200	✓		✓	✓		✓	✓	£119.00
<b>YORK</b>									
(Sulkin (UK) Ltd)	JCB 861	✓						✓	£69.00
	JCB 863	✓		✓	✓	✓	✓	✓	£94.00

speak. We recommend installing the unit and listening to other CB users for a couple of days before engaging anyone in conversation. Calling up on channel 14 can be done by saying either "breaker 1-4 for a copy" or "is the channel free/anyone listening"—the preference is yours.

After making contact with another "breaker" or CB user you mutually pick another channel, say 27 and move off the breaking channel to continue your conversation.

## TEST REPORTS

Our first FM transmission using the John Woolfe M2 transceiver made us realise that the voice quality and distance of transmission were greater than expectations and we feel that no one will be disappointed by the performance of their unit. Contrary to what is said by the diehards of the illegal AM sets, FM units work better and their transmission go further. As regards the John Woolfe M2 unit we feel this is a good value-for-money transceiver and ideal for the "first time" buyer.

The second set tested was the Transcom GBX4000 which sells for around £90. This set has a pleasant brushed aluminium finish fascia which makes a change from some of the bright chrome that is featured on so many units.

As you would expect for the price the Transcom GBX4000 has several useful "extra" features, such as channel nine priority switching, and a PA switch that allows the use of an externally mounted speaker thus turning the transceiver into a mini Public Address system (not such a good idea). Rotary controls are provided for tone (rather more use with an extension speaker) and for r.f. gain control which alters the sensitivity of the receiver. This can be extremely useful when the calling channel becomes congested, as turning down the sensitivity will cut out all the weaker transmissions in the area.

The Transcom unit is also fitted with a "Roger Bleep", a noise known to thousands as the astronauts hand-over signal when talking to Mission Control. The "bleep" is emitted when the mic lever is released, thus letting everyone know that the transmission has been handed over. We have noticed that some units have a bleep override switch in case the "bleep" is not to the user's taste; however we like it as it has a definite use.

Not fitted to the Transcom unit but to be found on a lot of sets of this price is a mic gain control. This allows users to set the sensitivity of the microphone to suit their own voice level. Well that's the theory—in practise everyone turns the gain on to full and leaves it there, and our experiments have shown that when

using a CB rig people tend to speak more loudly anyway.

To sum up, if you are looking for a unit that gives you more flexibility and a better transmission, then units like the GBX4000 will suit you. As with all consumer electrical products quality is usually equated to price. Other units that are in this price range are the Fidelity CB2000, Binatone Five Star, Rotel RVC240 and the Radiomobile CB202.

Two points that are worth mentioning are the use of the attenuator switch fitted to each set by law, and the use of extension speakers.

## ATTENUATOR SWITCH

The -10dB attenuator drops the output of the transceiver from 4 to 0.4 watts, and is required if the unit is used with an antenna more than 7 metres off the ground. It can however be used to cut down your transmitting power when talking to other local CB users, say up to two miles away.

By decreasing the power you will get just as good a transmission whilst allowing the use of that channel for another user on the fringe of your transmission. This use of the attenuator saves power and makes for good RT practice.

## EXTENSION SPEAKER

As we have already said that each CB unit has an integral speaker it might seem rather strange to advise fitting a second extension speaker.

The fact is however, that the quality of sound obtained from the built-in speaker is not exactly high. An improvement can usually be obtained through the use of a special CB boxed speaker or by mounting an 8 ohm chassis speaker in the dashboard, using the manufacturers recommended position if possible. Voice quality is likely to be instantly improved: a definite benefit with FM as it has inherently a wider frequency range than the older AM sets.

## ANTENNA

Having chosen the transceiver or "rig" one further item that will dictate how well your unit will perform is the antenna. Many importers of rigs have a reasonably priced antenna that they sell along with SWR meters and extension speakers; however, many will recommend a range of antennas to suit their equipment.

In theory an antenna is best at radiating energy when its length is just one half of the wavelength of the signal fed into it. One wavelength at 27MHz measures over 36ft, so an ideal antenna length would be 18ft. As this is impracticable for mobile use a quarter wave antenna of 9ft is used.

However the Home Office specification calls for a "single element rod or wire antenna with a base mounted loading coil, overall length shall not exceed 1.5m". How then can anything like ideal performance be obtained from an antenna of 59in in length?

## LOADING COIL

Fortunately an antenna of this length can have some of its length made up of wire wound into a coil at the base, called loading a short whip. To give the full effect of a full quarter wave the whip relies on the ground plane, usually the reflected metal of the car body.

A lot of energy can be absorbed by the wire winding in the antenna so the better the design and manufacture the more power it will transmit. A cheap base load antenna with an anti-shock coil spring will cut down the effective radiated power by as much as 50 per cent. Most antenna of this type are copies of car radio-telephone antenna and are usually called "telecom type".

## ANTENNA TESTS

With our set reviews we have tried two types of antenna, the American Antenna K40 and Antenna Incorporated Persuader, both from over the Atlantic and priced between £30 and £40 depending on the type of fixing used. We chose a magnetic mount as it helped in our tests in terms of easy removal. There are usually two further fixings available: the clamp or clip-on type that can be fitted on the boot or hatchback rear door, and the wing fitting type that requires drilling of the bodywork.

Both the K40 and the Persuader antenna come from companies very experienced in producing CB and professional communications equipment and should give close to a 1.2:1 reading on a SWR meter with some small adjustment of the wire whip as per their own individual manufacturers instructions. It has been calculated these types of antenna give an effective radiated power of around 3W which is as near the theoretical limit as you can get with such a short 1.5m whip.

Two further antenna we have tested (although not as fully as the ones already mentioned) and seem to work well are the Antenna Specialists MR125 and the British Panorama CB27.

Well that covers the major points in the selection, fitting and use of CB equipment.


It just remains for us to say that using CB is both fun and informative and we have tabulated all the known legal transceivers and their features to enable prospective users to see what is available and at what price. □

**NEW**
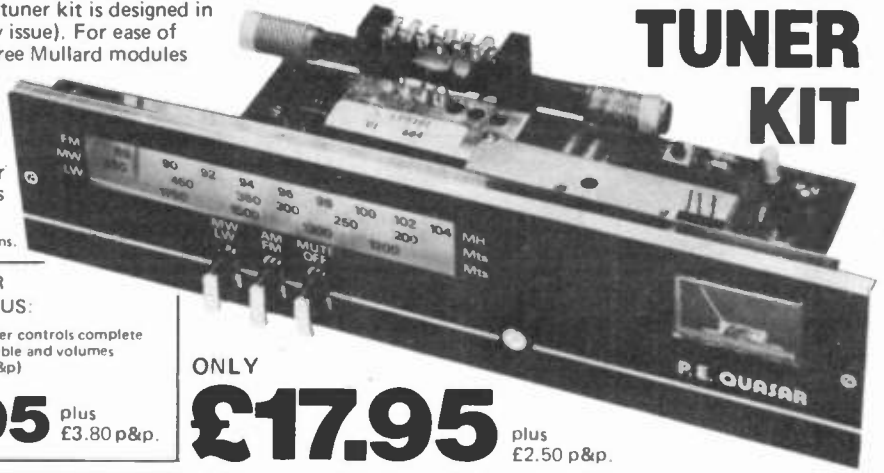
# PRACTICAL ELECTRONICS - STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF. System.

**FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size 10 1/2" x 2 1/2" approx. Complete with diagrams and instructions.



## SPECIAL OFFER!

TUNER KIT PLUS:


- Matching I.C. 10+10 Stereo Power amplifier kit (usually £3.95 + £1.15 p&p)
- Mullard LP1183 built preamp. suitable for ceramic and auxiliary inputs (usually £1.95 + 70p p&p)
- Matching power supply-kit with transformer (usually £3.00 + £1.95 p&p)

- Matching set of 4 slider controls complete with knobs for bass, treble and volumes (usually £1.70 + 80p p&p)

**£21.95** plus £3.80 p&p.

ONLY

**£17.95** plus £2.50 p&p.

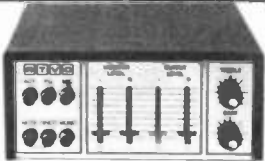

## STEREO AMPLIFIER KIT

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Pre-amplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8 1/4" x 3 3/4" (approx)
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with the kit.

**£14.95**  
Plus £2.90 p&p.

**SPECIFICATIONS:** Suitable for 4 to 8 ohm speakers.  
Frequency response 40Hz - 20KHz.  
P.U. 150mV. Aux. 200mV.  
Mic. 1.5mV.  
Bass ±12db @ 60Hz  
Treble ±12db @ 10KHz  
0.1% typically @ 8 watts  
220 - 250 volts 50Hz.

Tone controls

Distortion  
Mains supply

**STEREO MAGNETIC PRE-AMP CONVERSION KIT**  
Includes FREE Magnetic cartridge with diamond styli. All components including p.c.b. to convert your ceramic input on the 10+10 to magnetic.  
Only available with 10+10 amp. **£2.00** includes p&p.

**8" SPEAKER KIT** Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p. when purchased with amplifier. Available separately £6.75 plus £1.70 p&p.

## PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II


2 WAVE BAND  
MW - LW

- Easy to build
- 5 push button tuning
- Modern design
- 6 watt output
- Ready etched and punched PCB
- Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics March issue. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type pre-aligned and assembled, and a 8ird pre-aligned push button tuning unit.

**£10.50**  
Plus £2.00 p&p.

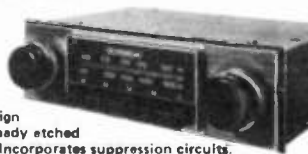Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.). available as a kit complete. **£1.95/ pack.** Plus £1.15 p&p.




## HIGH POWER AMPLIFIER MODULES

READY BUILT OR IN KIT FORM

	KIT	BUILT
125 WATT MODEL	<b>£10.50</b> Plus £1.15 p&p	<b>£14.25</b> Plus £1.15 p&p.
200 WATT MODEL	<b>£14.95</b> Plus £1.15 p&p	<b>£18.95</b> Plus £1.15 p&p.


**SPECIFICATIONS:**  
Max. output power (RMS) 125 watts  
Operating voltage (DC) 50 - 80 max.  
Loads 4 - 16 ohms  
Frequency response measured @ 100 watts 25Hz - 20KHz  
Sensitivity for 100 watts 400mV @ 47K  
Typical T.H.D. @ 50 watts, 4 ohms 0.1%  
Dimensions (both models) 205 x 90 and 190 x 36mm.  
The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of

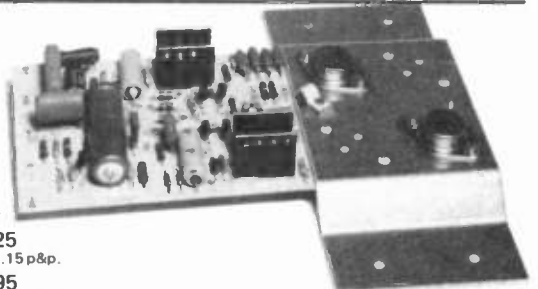

generously rated components, result, a high powered rugged unit. The PC Board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.
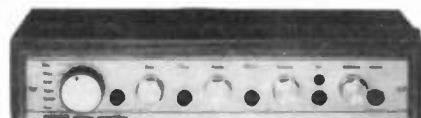
### ACCESSORIES:

- Suitable LS coupling electrolytic for 125W model **£1.00** plus 25p p&p.
- Suitable LS coupling electrolytic for 200W model **£1.25** plus 25p p&p.
- Suitable mains power supply unit for 125W model **£7.50** plus £3.15 p&p.
- Suitable Twin transformer power supply for 200W model **£13.95** plus £4.00 p&p.



## 30+30 WATT STEREO AMPLIFIER

Viscount IV unit in teak simulate cabinet, silver finished rotary controls and pushbuttons with matching fascia, mains indicator and stereo jack socket. Functions switch for mt magnetic and crystal pickups, tape and auxiliary. Rear panel features fuse holder, DIN speaker and input socket 30+30 watts RMS, 60+60 watts peak. For use with 4 to 8 ohm speakers. Size 14 1/2" x 10" approx. **£32.90** Plus £3.80 p&p.

### TV SOUND TUNER KIT

as featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner, I.C.'s, all components excluding case, and selector switch. **£11.45 + £1.50 p&p.**




• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation **£1.95 + 75p p&p.**
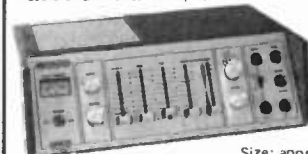
## MONO MIXER AMPLIFIERS



**50 WATT** Six individually mixed inputs for two pick ups (Cer. or Mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic and aux inputs. Size: 13 1/2" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use. **£39.95** Plus £3.70 p&p.



### 100 WATT

Brushed Aluminium fascia and rotary controls. Size: approx. 14 1/2" x 4" x 10 1/2". Five vertical slider controls, master volume, tape level, mic level, deck level, PLUS INTERDECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre fade level controls (PFL) lets YOU hear the next disc before fading it in. VU meter monitors output. 100w RMS output (200w peak). **£76.00** Plus £4.60 p&p.



### CALLERS ONLY

323 Edgware Rd, London W2. Tel: 01-723 8432.  
Open 9.30am - 5.30pm. Closed all day Thursdays.  
Persons under 16 not served without parents authorisation.

**ALL PRICES INCLUDE VAT AT 15%.**


### MAIL ORDER ONLY

21A HIGH STREET, ACTON, W3 6NG.  
Note: Goods despatched to UK postal addresses only.  
For further information send for instructions 20p plus stamped addressed envelope.  
All goods delivered within 14 days of receipt of order.

All items subject to availability. Prices correct at 1/10/80 and subject to change without notice. RTVC Limited reserve the right to update their products without notice.



BY P. BARBER

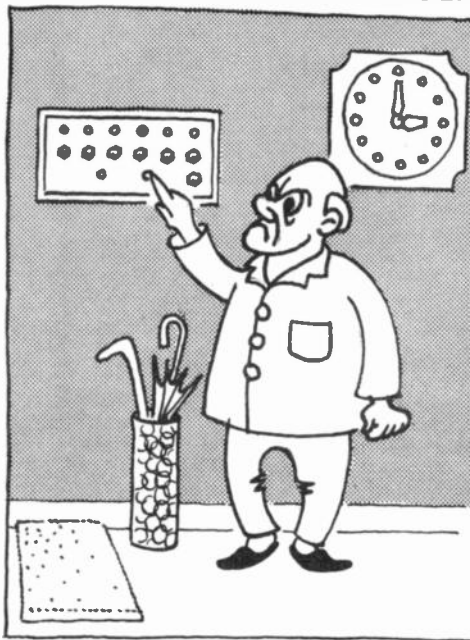

# House Register

THE idea of a "register" was originally conceived because of the problem of keeping track of people who were in the author's house at any one time. This was especially so late at night, when various members of the household found themselves locked out following trips to the pub!

At first the problem was solved by having a notice board by the back door, and people "signed" themselves in or out—the last one in at night locking the door. The circuit to be described here provides the same facilities in a smaller, neater way.

The project can be built to cater for any number of people and it is envisaged that it could be adapted for use in an office or a block of flats!

The House Register was designed using CMOS logic gates for simplicity and economy, the latter reason arising from the fact that the circuit would have to be switched on at all times, thus the low power consumption of CMOS was ideal. While the project is fairly straightforward both to build and understand, it also provides a good example of using simple binary logic.

In order to ascertain whether a person is in, his or her name switch is pressed. If the light goes on it indicates that he or she is in. It would be extremely uneconomical to allow the light to remain on at all times, hence the need to press the switch. A further feature is the master Display switch, which allows an inquiry on the complete household by switching on the lights of everyone who is in.

For this device to be effective, however, it is necessary for each person to remember to "clock in" and "clock out". This is carried out as follows: To clock in, a person presses his or her Name switch and at the same time presses the master In switch. The person's light will go on until the name switch is released. To clock out the procedure is the same, except that the master Out switch is used instead of the master In switch.

It does require some practice to get used to clocking in or out, but once it has become almost second nature this device is simple and useful.

## CIRCUIT DESCRIPTION

The circuit diagram is shown in Fig. 1. There are six "logic modules" on the prototype (as the circuit shows) and allows up to six people's comings and goings to be monitored. All modules are identical in operation and the full circuit for each is shown in the first module, labelled MIKE.

## MEMORY LOGIC

IC3b and IC3a form a binary memory (bistable latch), the state of which is controlled by gates IC1b and IC2c. The latter can switch the memory on (logic 1 at its output), and IC1b can switch it off (logic 0 at its output). Note that neither can perform the reverse function.


If S7 (the IN switch) and in this case S1 (the NAME switch) are pressed simultaneously, the output of IC2c goes high and sets the memory on (IC3b at logic high). This is the "clocking in" procedure.

If S8 (the OUT switch) and S1 are pressed together, both inputs to gate IC1b go high and therefore the output goes low and resets the memory through D1 (IC3b at logic low).

The output from the memory goes to one input of the l.e.d. enabling gate, IC1a. D4 will only turn on if the output of IC1a is low. As IC1a is a NAND gate, both inputs must be high for this to occur. D2 and D3 effectively form an OR gate to the second input of IC1a. Therefore D4 will only light if the output from the memory is high (it has been set) and either S1 or S9 (the DISPLAY ALL switch) is pressed. Resistors R2, R19 and R20 keep the inputs to gates IC1b, IC2a and IC1a normally low.

## SYSTEM DESIGN

Each person is allocated their own individual switch "Name" switch. In addition to these switches there are three further ones: "Master In", "Master Out", and "Master Display". Each person is provided with a small light beside their Name switch.

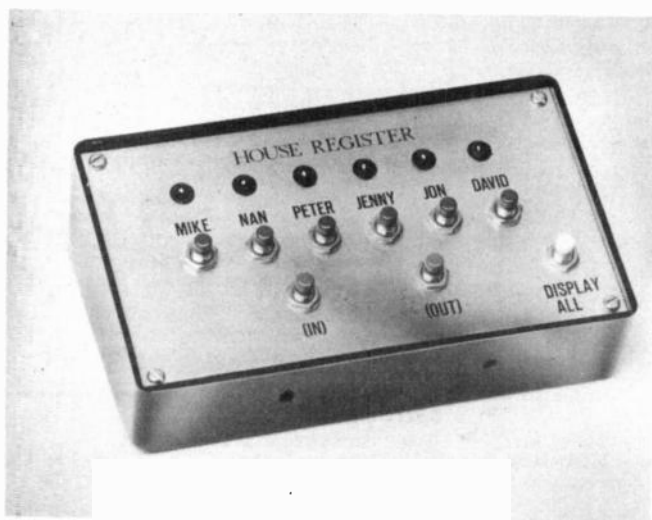

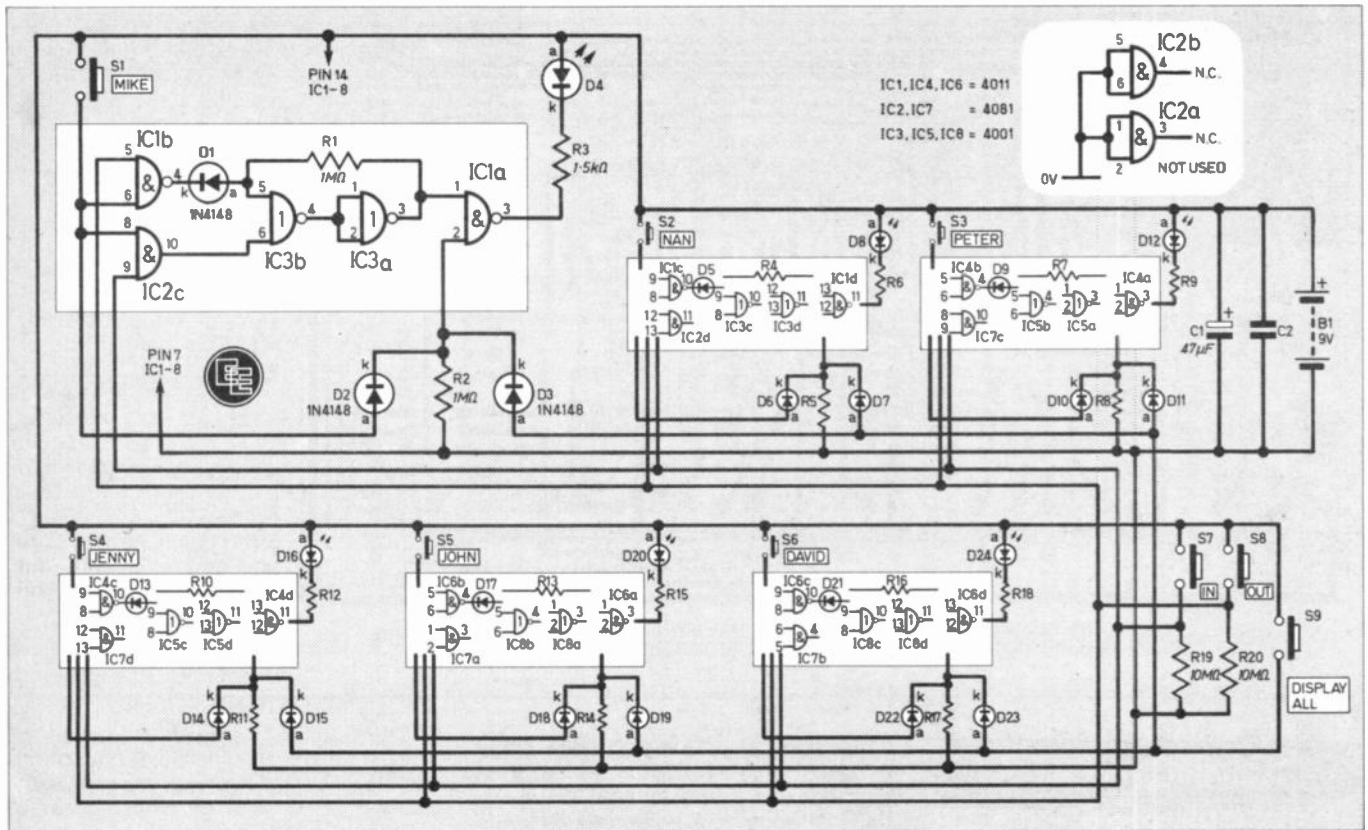


Fig. 1. The circuit diagram for the House Register. This circuit caters for six persons.

**CONSTRUCTION**  
starts here

Inside the prototype unit with the front panel hinged back. The position of a few components and the number of link wires will differ from the layout in Fig. 3. This has been carried out to aid construction.


### COMPONENT ASSEMBLY

The prototype was built on a printed circuit board size 137×75mm which fits comfortably inside the specified case. There are pillars on the base of the case which align with the fixing hole positions on the p.c.b.


The board has been designed to cater for six people, but there is no theoretical limit to the number of people who can be catered for. However, it is left to the constructor to extend the existing board or produce another for more than six people.

The full-size master of the p.c.b. pattern is shown in Fig. 2. The black areas represent the copper to remain after etching.

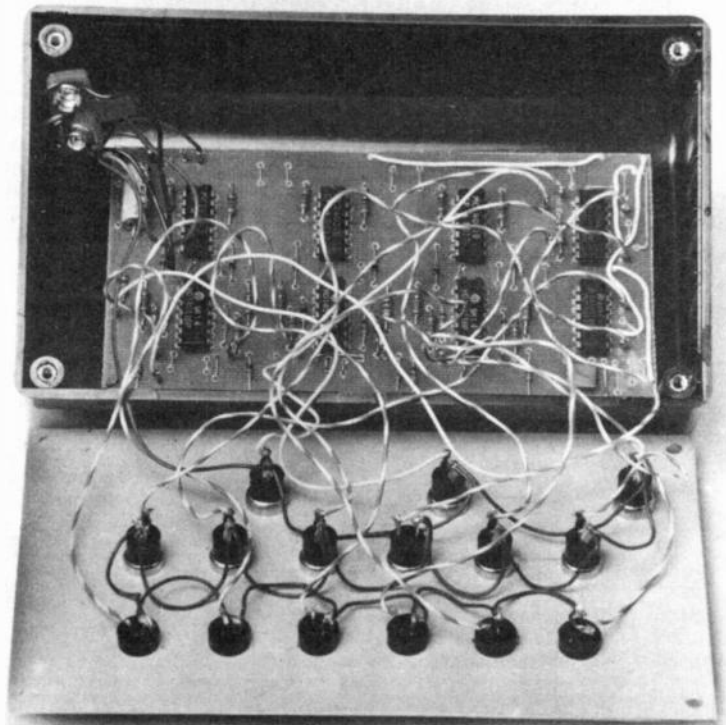The author did not use i.c. sockets for mounting the CMOS i.c.s. but we recommend that they be used as these devices are easily damaged during soldering.





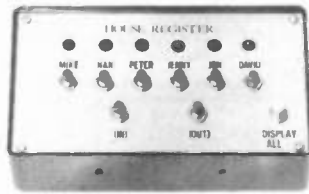

# House Register

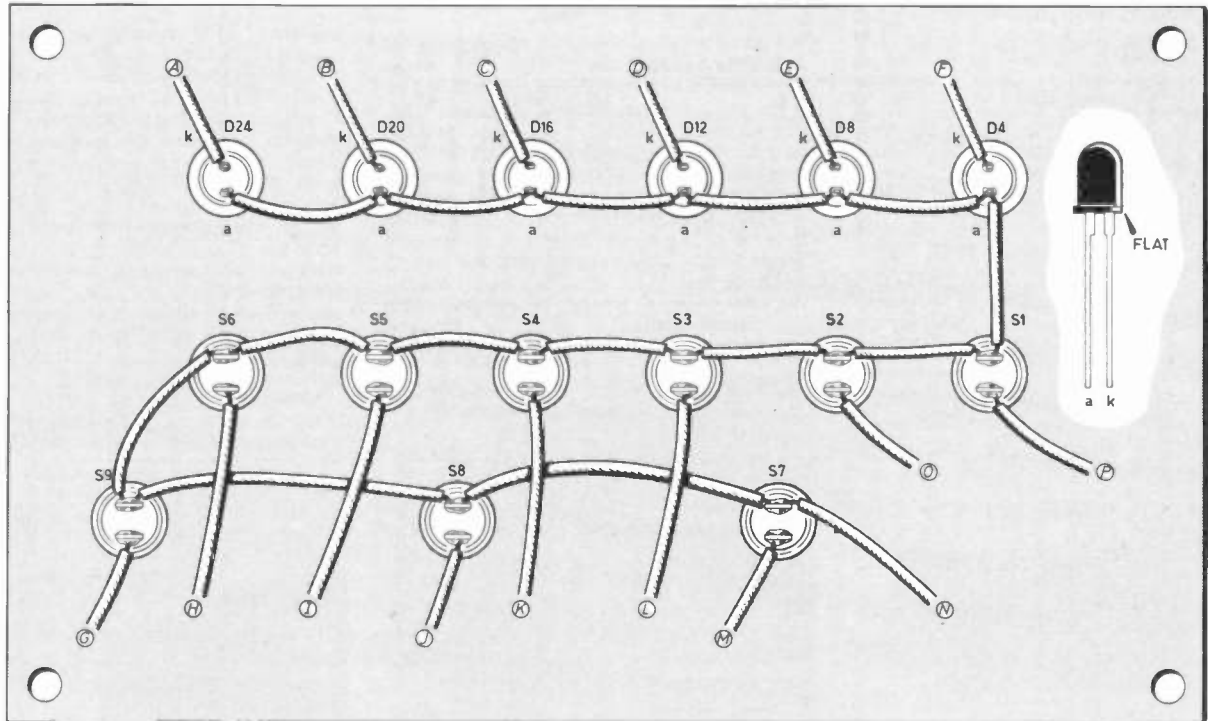


Fig. 4. The layout and interwiring of the panel mounted switches and l.e.d.s.


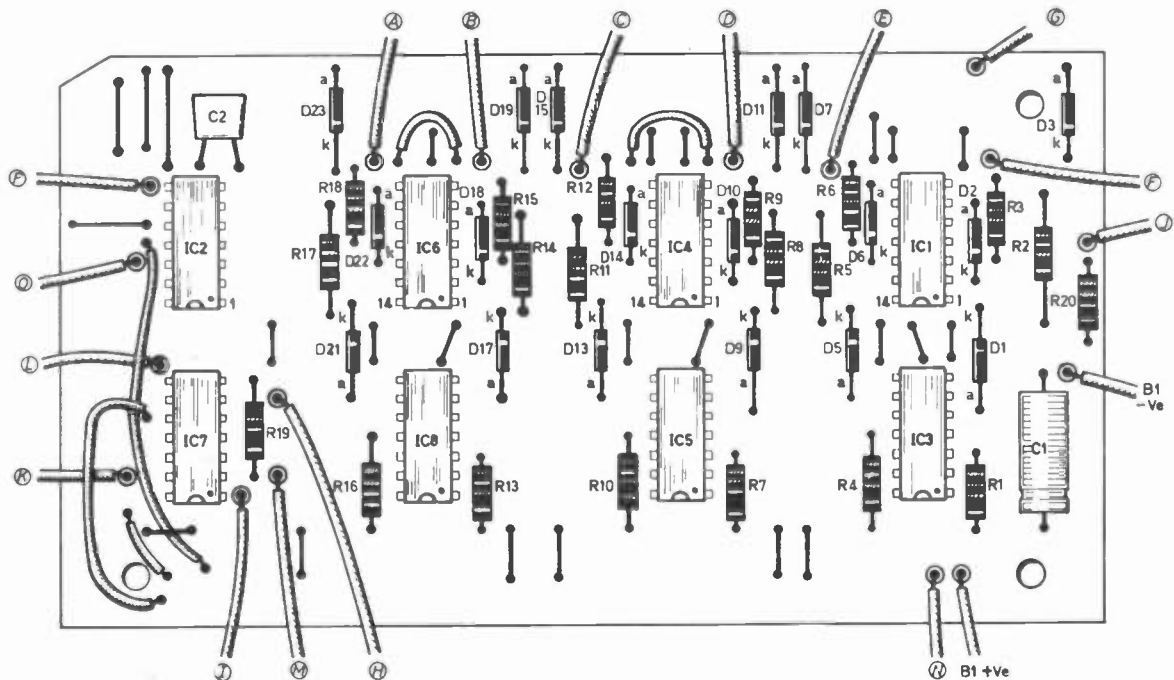



Fig. 3. The layout of the components on the topside of the p.c.b. and wiring details to the panel mounted components. Note that i.c. sockets are not shown, but their use is advised.
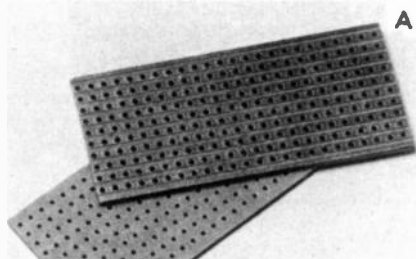
# SQUARE One FOR BEGINNERS

WHEN the newcomer to electronics builds his first circuit, it will probably be constructed on Veroboard, a unique and very versatile prototype circuit board. Presented free with this month's EVERYDAY ELECTRONICS is a piece of Veroboard (or "stripboard" as it is often referred to) 10 strips by 24 holes and to help you on your way, we have dedicated this month's *Square One* to laying down some basic guide lines as to its use.



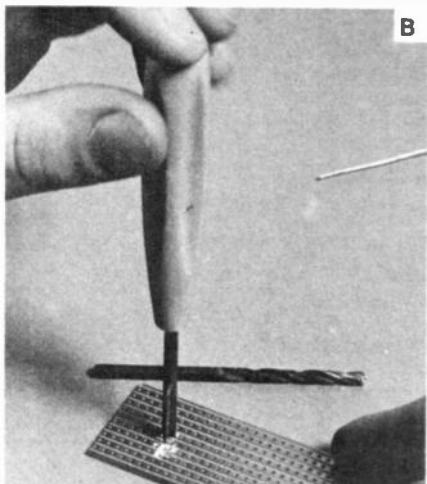
A. The board itself is made from s.r.b.p. and is drilled with a matrix of holes on a 0.1 inch (2.54mm) grid. Running horizontally along the back of the board are strips of copper linking up the rows of holes thus enabling electrical connections to be made. The 0.1 inch grid spacing of the holes permits the insertion of integrated circuits, edge connectors and other components with their leads preformed on this internationally agreed lead spacing.




B. Before constructing a circuit, carefully study the component layout and circuit

diagram of the intended project, of which incidentally, there are two, printed in this issue, and have all components to hand. You may have noticed that in EE articles, all holes are coded with a letter (the copper strip) and a number (the hole), starting from the top left hand corner. This greatly assists in locating a single point on the board. You will also have noticed that it is often necessary to make breaks in the copper strips in order to fit the circuit on the board, for example, beneath an i.c.

To make these breaks, a special tool is available but they can be just as easily made with a hand held twist drill, some 3 to 5mm in diameter gripped between the thumb and forefinger in a similar fashion to that shown in the photo. Insert the tool or drill into the hole at the correct location with the board supported on a flat surface and twist back and forth whilst at the same time applying light pressure. It is not necessary to drill very far into the board and care should be taken to prevent breaking into adjacent tracks. When the break has been made, it must be closely examined for any "whiskers" of copper.

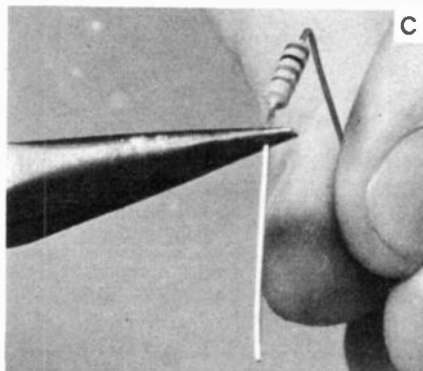


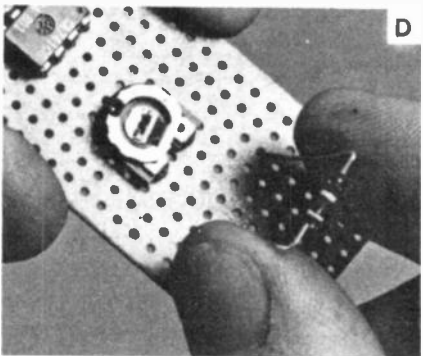C. Having made all the required breaks, the components can be inserted from the plain side and in many cases they will slot in position without modification, however axial lead components such as resistors and diodes will require their legs to be preformed. This can be done with a special gauge or simply achieved by making a neat right angled bend with a pair of long nosed pliers as shown.



D. To hold the components in place after insertion, spread their leads out at approximately 45 degrees but do not put any undue stress on the body of the component. The board can now be soldered.

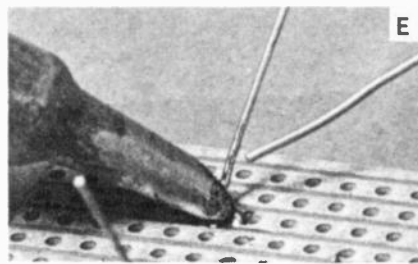
E. When it comes to soldering the components, the constructor may wish to insert all parts and then perform a single soldering operation or indeed he may prefer to solder each component as it is



inserted. This is entirely a matter of personal choice.


To make the actual joint, a small soldering iron bit must be used and it is strongly recommended that the inexperienced constructor practices on a piece of scrap board. Before each joint, wipe the "dross" from the tip of the iron with a damp sponge and liberally "wet" the bit with solder. Bring the iron to the joint and touch both the copper strip and the component lead and then two or three seconds later feed the solder to the joint. A smooth and shiny fillet of solder should form around the joint. If the solder looks dull or crystallised it is very likely to be "dry" and the joint will have to be remade.

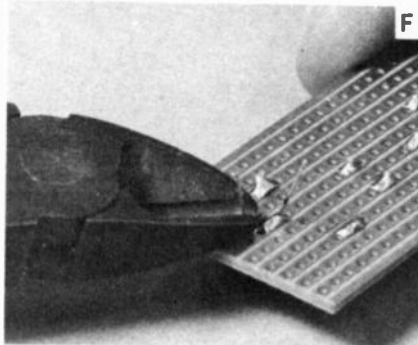Never hold an iron on the joint for more than five seconds and always use a heat-sink when soldering semiconductors.



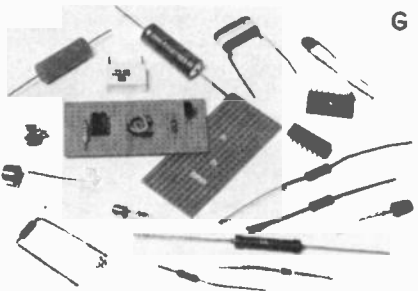F. A successful joint having been made, the excess lead must be cropped off with a pair of side cutters. It should be neatly clipped off just above the joint but take care as some cutters have a habit of firing the cropped lead away at incredible speed!

A final point. If the board layout requires wires to be soldered in to go to front panel mounted components it is advisable to attach these to Veropins as this both relieves stress on the copper strips and facilitates modification and repair.




G. This photograph shows just some of the types of components that can easily be accommodated in the Veroboard. It is always advisable to use i.c. holders for integrated circuits as this not only removes the danger of damage by soldering but also means the i.c. can readily be used in another project.



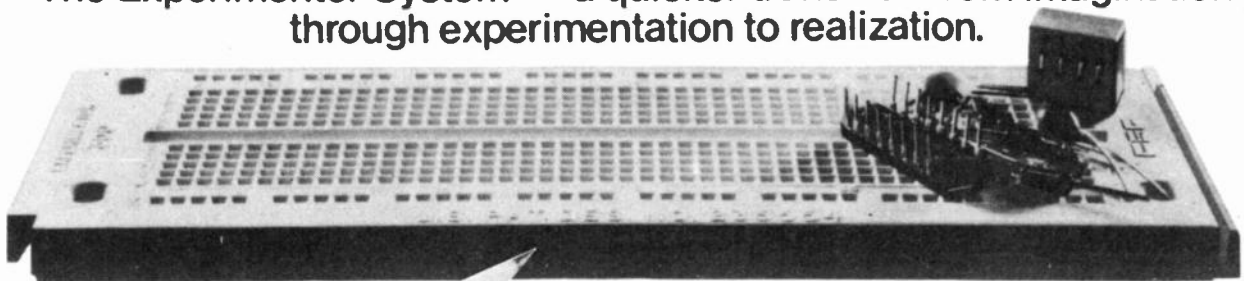
# You can't beat The System.


The Experimentor System™ — a quicker transition from imagination through experimentation to realization.



Experimentor solderless breadboard.

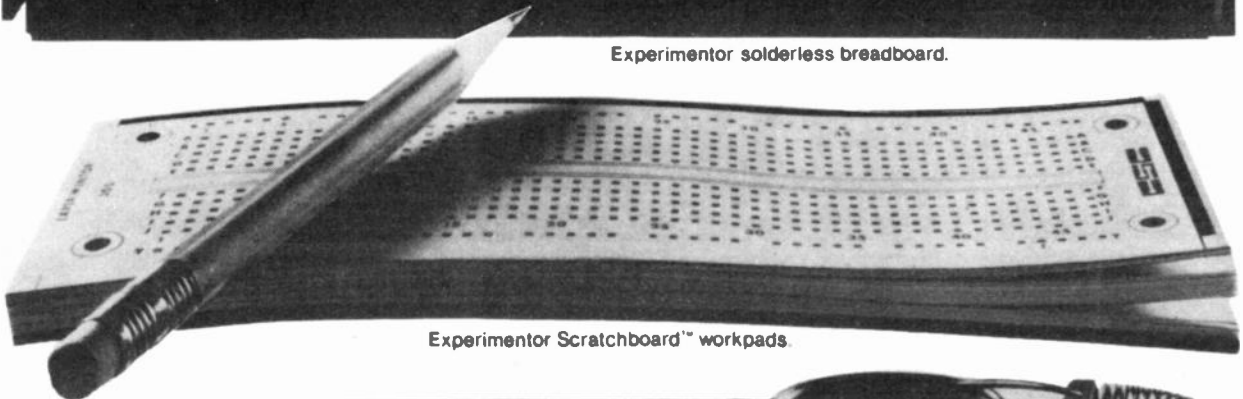

Experimentor Scratchboard™ workpads.

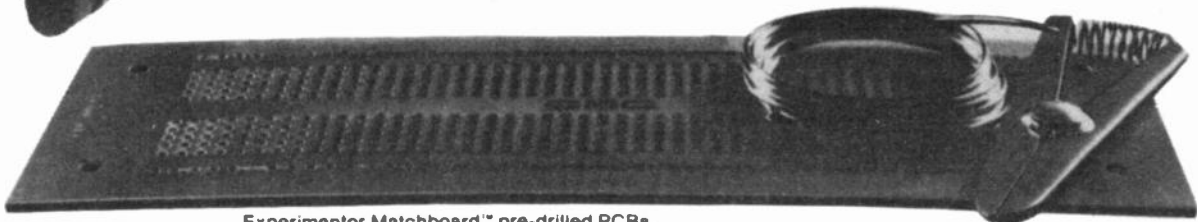

Experimentor Matchboard™ pre-drilled PCBs.

When you have a circuit idea that you want to make happen, we have a system to make it happen quicker and easier than ever before: The Experimentor System.

You already know how big a help our Experimentor solderless breadboards can be. Now we've taken our good idea two steps further.

We've added Experimentor Scratchboard workpads, with our breadboard hole-and-connection pattern printed in light blue ink. To let you sketch up a layout you already have working so you can reproduce it later.

With Experimentor Matchboard you can go from breadboard to the finished product nonstop! We've matched our breadboard pattern again, this time on a printed circuit board, finished and ready to build on. All for about £1.20

There's even a letter-and-number index for each hole, so you can move from breadboard (where they're moulded) to Scratchboard™ (where they're printed) to Matchboard™ (where they're silkscreened onto the component side) and always know where you are.

When you want to save time and energy, you can't beat The Experimentor System.

1. EXP-300PC, which includes one item. A Matchboard pre-drilled PCB £1.20	2. EXP-302, which includes three items. Three 50-sheet Scratchboard workpads £1.50	3. EXP-303, which includes three items. Two Matchboards and an EXP-300 solderless breadboard £7.60	4. EXP-304, which includes four items. Two Matchboards, an EXP-300 breadboard and a Scratchboard workpad £8.70
---	---	---	--

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited, Dept. 4W  
Unit 1, Shire Hill Industrial Estate,  
Saffron Walden, Essex. CB11 3AQ.  
Telephone: Saffron Walden (0799) 21682  
Telex: 817477

GLOBAL SPECIALTIES CORPORATION DEPT. 4W

Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex

Name \_\_\_\_\_

Address \_\_\_\_\_

Inc P&P and 15% VAT

1. EXP 300PC £2.25	Qty. Req'd	2. EXP 302 £2.58	Qty. Req'd
3. EXP 303 £9.80	Qty. Req'd	4. EXP 304 £11.15	Qty. Req'd

FREE Catalogue tick box   
I enclose cheque PO for

£ \_\_\_\_\_

Phone your order with Access, Barclaycard or American Express

Card No. \_\_\_\_\_ Expiry date \_\_\_\_\_

Goods despatched within 48 hrs.

# NEW · NEW · NEW · NEW PRODUCTS NEW · NEW · NEW · NEW

## HIGH-SPEED PROBE

The LP4 logic probe from Global Specialties Corp., is a high-speed device specifically designed to detect and indicate logic levels at the high speeds and narrow threshold differentials encountered in emitter-coupled-logic (ECL) circuitry.



The probe responds to single pulses as short as 3ns in duration and to pulse trains with repetition rates of more than 100MHz, and also incorporates a memory mode for storing pulse events and detecting spurious signals. With memory selected, a single one-shot pulse will be stored, and the pulse indicator will remain on until it is reset by the selector switch.

The LP4 is a portable, circuit-powered instrument that detects and indicates valid ECL logic levels using light emitting diode indicators for "high" (logic 1) and "low" (logic 0) levels. A third "pulse" indicator shows the presence of single pulses or pulse trains, and when this indicator is on, the other light emitting diodes indicate positive or negative pulse polarity.

Global Specialties Corporation, Dept EE, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.



## BUDGET TOROIDS

A "budget range" of toroidal transformers, rated at 30, 60, 100, 160, 230, 330 and 530VA can now be supplied by Barrie Electronics. With 110, 220 or 240V primary windings and dual secondaries ranging from 6+6 to 50+50V, they have been selected to fulfil the requirements of both the professional and amateur electronic engineer.



The toroidal transformers, from the Cotswold Electronics "budget range", will complement the 150 laminated types already held by Barrie Electronics on an off-the-shelf basis. Each transformer is supplied with a data sheet giving technical details on the operation and installation of the toroids, which are manufactured to the same materials standards as used in avionics, telecommunications and electro-medical applications.

Barrie Electronics Ltd., Dept EE, 3 The Minories, London EC3N 1BJ.

## AUTORANGING MULTIMETER

The D350 is an autoranging digital multimeter, small enough to fit into a shirt pocket, from Micro-Data Systems.

The 3½ digit liquid crystal display has both unit and function annunciators and the meter has the usual complement of functions for a.c. or d.c. current measurements to over 20A. An added feature is an audible continuity tester facility.

The multimeter is built around a single 64-pin CMOS integrated circuit. This not only performs the analogue to digital conversion and drives the display, but also contains the autorange switches, the a.c. to d.c. converter amplifier and the resistance measurement source.

The D350 measures 127mm x 64mm and is only 20mm thick. The price, including accessories, is £69 plus VAT.

Micro-Data Systems, Dept EE, Coach Mews, St Ives, Huntingdon, Cambridgeshire PE17 4BN.

## DOWN TO EARTH

An unusual but useful item from the OK range of products is the WRS-1 personal grounding strap.

Designed to safeguard work stations against static charges, the strap is attached to the user's wrist by a bead chain and to an anti-static work surface by a clip, thus protecting sensitive components from any static charge generated by the operator. A 1 megohm resistor built into the flexible wire strap protects operators from possible shocks.

OK Machine & Tool (UK) Ltd., Dept EE, Dutton Lane, Eastleigh, Hants SO5 4AA.



## BENCH POWER


With outputs from 8V 2.5A to 350V 0.2A, the 22 models in the new Kikusui PAB series d.c. bench power supplies from Telonic Berkeley UK offer a wide range of output options.

Output voltage may be varied continuously from 0V by the use of "coarse" and "fine" adjustment controls. Continuous control of current is available from 10 per cent to 100 per cent of rated value, so the units may be operated in the constant

voltage or constant current mode. Voltage and current are displayed simultaneously on separate meters. Overload protection is by constant current transfer.

Multiple units may be used in series to obtain a higher output voltage and two of the same model may be connected in parallel to double the available current.

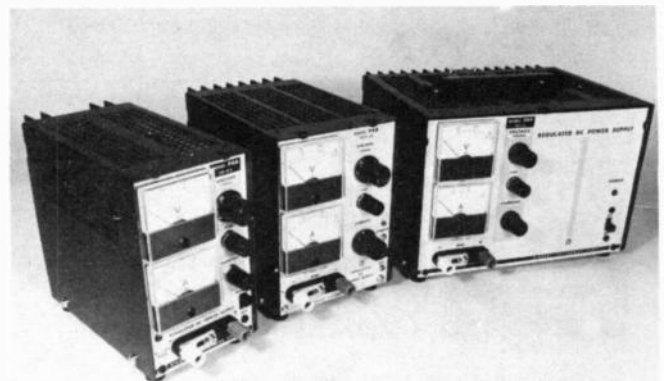Telonic Berkeley UK Ltd., Dept EE, 2 Castle Hill Terrace, Maidenhead, Berkshire.




# CIRCUIT EXCHANGE

This is the spot where readers pass on to fellow enthusiasts useful and interesting circuits they have themselves devised.

Payment is made for all circuits published in this feature.

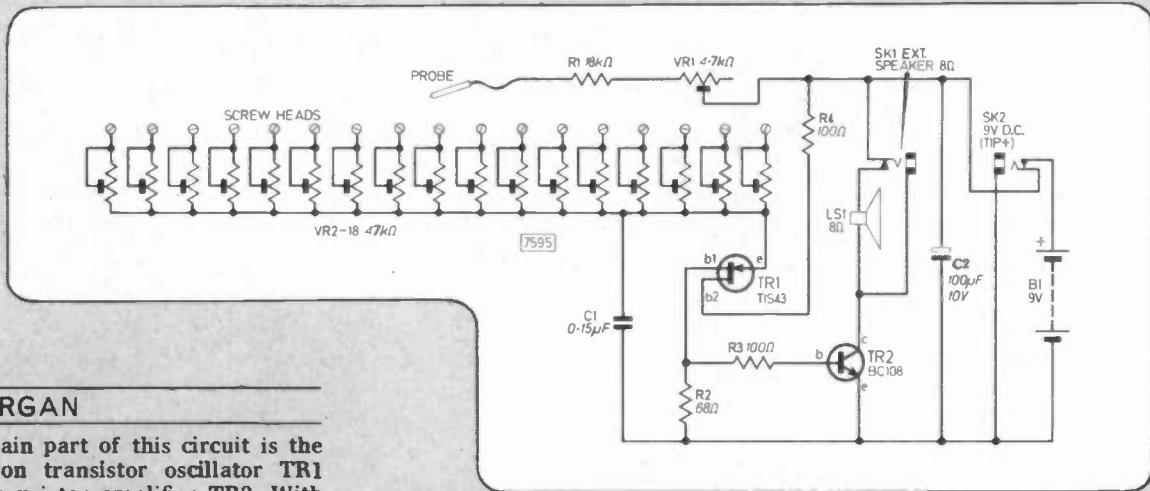Contributions should be accompanied by a letter stating that the circuit idea offered is wholly or in significant part the original work of the sender and that it has not been offered for publication elsewhere.



## MINI ORGAN

The main part of this circuit is the unijunction transistor oscillator TR1 with a transistor amplifier TR2. With the supply connected, C1 will charge up via VR1, R1, the probe and one of the presets. When the transistor switches over, C1 discharges itself into the emitter of TR1. When TR1 has switched back, C1 will charge up again. The same thing happens again and these pulses are emitted by base 1, and then amplified by TR2 and fed into LS1. C1 makes sure that the peak current requirements can be met.

The preset potentiometers are connected to wood screws fitted to the front panel of the instrument. The probe is applied to these screw heads to produce the required sounds.

An on/off switch can be mounted in the supply if required. It is advised to fit TR2 with a small heatsink. The highest note is about A before middle

C. R1 can be reduced if this is found a little low. The unit is tuned by turning the presets and comparing the output frequency with a piano or other conventional instrument.

A. Clark,  
Lichfield,  
Staffs.

## HIGH VOLTAGE PULSER

Recently I acquired an old desk top calculator in which I found some old "Nixie" display tubes. In order to

experiment with these safely, I devised the enclosed novel circuit for a high voltage pulser which may also interest your readers.


The "buzzer", made from a 4in nail and coil, supplies a broken-up d.c. voltage to a mains transformer connected the opposite way round to normal. The primary or mains input terminals forming the high voltage output or "secondary" winding.

The transformer steps up the broken d.c. and produces a series of high voltage spikes at the output terminals.

The wire for the buzzer coil was obtained from a heater winding of an old transformer. It was found that a PP9 battery provides an adequate power supply.

**Warning:** Avoid any contact with the output terminals of the transformer since it gives quite a kick.

H. Karmazyn,  
Handsworth,  
Birmingham.

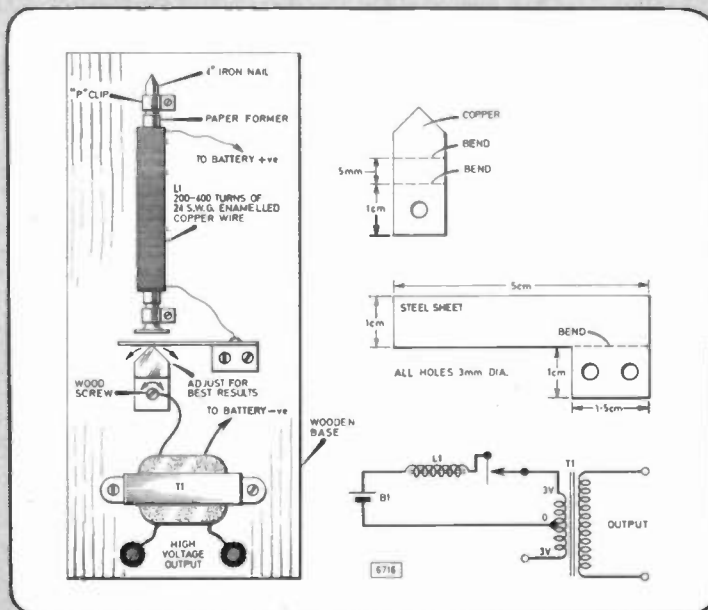

# CIRCUIT EXCHANGE

# Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!


Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

## Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

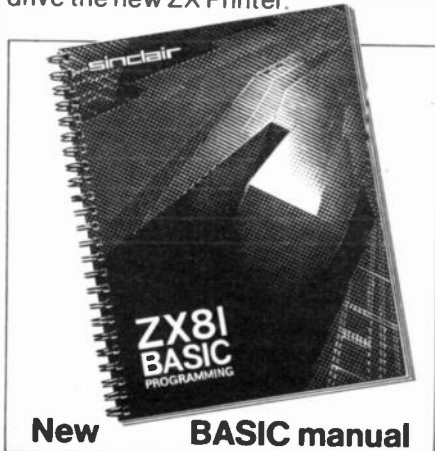And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



**New BASIC manual**

Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs.

## Kit: £49.<sup>95</sup>

### Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

### New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



## Built: £69.<sup>95</sup>

### Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



ter-



## 16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.

## Available now - the ZX Printer for only £49.<sup>95</sup>

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha- numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings – particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

### How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

# sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.  
Tel: (0276) 66104 & 21282.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.				Order
Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	<b>49.95</b>	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	<b>69.95</b>	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	<b>8.95</b>	
	16K-BYTE RAM pack.	18	<b>49.95</b>	
	Sinclair ZX Printer.	27	<b>49.95</b>	
	8K BASIC ROM to fit ZX80.	17	<b>19.95</b>	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £ \_\_\_\_\_

\*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £ \_\_\_\_\_

\*Please charge to my Access/Barclaycard/Trustcard account no. \_\_\_\_\_

\*Please delete/complete as applicable. \_\_\_\_\_

Please print.

Name: Mr/Mrs/Miss \_\_\_\_\_

Address: \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**FREEPOST – no stamp needed. Offer applies to UK only.**

EVE 03

CMOS																			
4000	0.11	4077	0.18	4705	4.24	7447N	0.62	74153N	0.55	74366N	0.85	74LS109N	0.20	74LS248N	1.35	74C00	0.20	Processors	
4001	0.11	4078	0.18	4706	4.50	7448N	0.56	74154N	0.55	74367N	0.85	74LS112N	0.20	74LS249N	1.35	74C02	0.20	8080AFC/2 (7.30	
4002	0.12	4081	0.12	4720	4.00	7450	0.14	74155N	0.55	74368N	0.85	74LS113N	0.20	74LS251N	0.35	74C04	0.20	8212	2.30
4007	0.13	4082	0.18	4723	0.95	7451N	0.14	74156N	0.55	74390N	1.85	74LS114N	0.19	74LS253N	0.35	74C08	0.20	8214	3.50
4008	0.50	4093	0.30	4724	0.95	7453N	0.14	74157N	0.55	74393N	1.85	74LS122N	0.35	74LS257N	0.40	74C10	0.20	8216	1.95
4008AE	0.80	4099	0.80	4725	2.24	7454N	0.14	74159N	0.90	74490N	1.85	74LS123N	0.35	74LS258N	0.37	74C08	0.20	8224	3.50
4009	0.25	4175	0.80	40014	0.54	7460N	0.14	74160N	0.55			74LS124N	1.80	74LS259N	0.60	74C10	0.20	8221	1.95
4010	0.30	4176	0.80	40085	0.99	7470N	0.28	74161N	0.55			74LS125N	0.24	74LS260N	0.50	74C14	0.55	8251	6.21
4011AE	0.24	4177	0.80	40096	0.54	7472N	0.27	74162N	0.55			74LS126N	0.24	74LS266N	0.22	74C20	0.20	8255	5.40
4011	0.11	4507	0.37	40106	0.69	7473N	0.28	74163N	0.55			74LS132N	0.42	74LS273N	0.70	74C30	0.20	6800/6809	
4013	0.25	4508	1.50	40160	1.05	7474N	0.28	74164N	0.55			74LS133N	0.24	74LS275N	3.20	74C32	0.20	6800P	£2.80
4015	0.50	4510	0.55	40161	1.05	7475N	0.28	74165N	0.55			74LS136N	0.20	74LS279N	0.35	74C42	0.80	68A00	4.25
4016	0.22	4511	0.45	40162	1.05	7476N	0.30	74166N	0.70			74LS138N	0.30	74LS280N	2.50	74C48	1.03	68A00	4.66
4017	0.40	4512	0.55	40163	1.05	7478N	0.26	74167N	1.25			74LS139N	0.30	74LS283N	0.42	74C74	0.50	6802	3.50
4019	0.38	4514	1.25	40174	1.05	7481N	0.20	74170N	1.25			74LS145N	1.20	74LS290N	0.50	74C76	0.48	6809	£8.75
4020	0.55	4515	1.25	40175	1.05	7482N	0.75	74173N	1.10			74LS151N	0.30	74LS293N	0.40	74C83	0.98	6810	1.25
4021	0.55	4516	0.80	40192	1.08	7485N	0.75	74174N	0.75			74LS153N	0.27	74LS296N	1.50	74C85	0.98	6810	1.85
4022	0.55	4518	0.35	40193	1.08	7486N	0.24	74175N	0.75			74LS154N	0.99	74LS298N	0.76	74C86	0.26	6810	2.04
4023	0.15	4520	0.60	40194	1.08	7489N	1.05	74176N	0.75			74LS155N	0.35	74LS305N	0.32	74C89	2.68	6820	1.95
4024	0.33	4521	1.30	40195	1.08	7490N	0.30	74177N	0.75			74LS156N	0.37	74LS306N	0.34	74C90	0.80	6821	1.25
4025	0.15	4522	0.89	<b>TTL N</b>		7491N	0.55	74178N	0.90			74LS157N	0.30	74LS307N	0.32	74C93	0.80	68A21	2.10
4026	1.05	4527	0.90	7400N	0.10	7482N	0.35	74179N	1.35			74LS158N	0.30	74LS308N	0.35	74C95	0.94	68A21	2.25
4027	0.26	4528	0.85	7401N	0.10	7483N	0.35	74180N	0.75			74LS160N	0.37	74LS313N	0.70	74C107	0.48	68A40	4.55
4028	0.50	4529	0.70	7402N	0.20	7484N	0.70	74181N	1.22			74LS161N	0.37	74LS317N	0.85	74C151	1.52	68A40	4.85
4029	0.55	4531	0.85	7403N	0.11	7485N	0.45	74182N	1.20			74LS162N	0.37	74LS319N	0.85	74C154	2.26	6850	1.50
4030	0.35	4532	0.80	7404N	0.12	7486N	0.45	74183N	1.20			74LS164N	0.30	74LS327N	0.12	74C160	0.80	6850	2.13
4035	0.67	4534	4.00	7405N	0.12	7487N	1.40	74185N	2.00			74LS165N	0.80	74LS328N	0.15	74C161	0.80	6852	2.95
4040	0.50	4536	2.50	7406N	0.22	74100	1.10	74188N	3.00			74LS166N	0.70	74LS329N	0.29	74C163	0.80	68A52	2.75
4042	0.50	4538	0.85	7407N	0.22	74104	0.62	74190N	0.55			74LS168N	0.70	74LS336N	0.68	74C164	0.80	68A52	2.95
4043	0.50	4539	0.80	7408N	0.15	74105	0.62	74191N	0.55			74LS169N	0.85	74LS338N	0.68	74C165	0.84	88488	5.25
4043AE	0.93	4543	0.80	7409N	0.15	74107	0.26	74192N	0.55			74LS170N	0.90	74LS339N	0.68	74C173	0.72	<b>Z80 series</b>	
4044	0.80	4549	3.50	7410N	0.12	74107	0.26	74193N	0.55			74LS173N	0.80	74LS340N	0.61	74C174	0.72	Z80A	£3.75
4046	0.60	4553	2.70	7411N	0.18	74110N	0.54	74194N	0.55			74LS174N	0.40	74LS341N	0.61	74C175	0.72	Z80ADRT	7.50
4047	0.68	4554	1.20	7412N	0.19	74111N	0.68	74195N	0.55			74LS175N	0.40	74LS342N	0.30	74C192	0.80	Z80APIO	3.50
4049	0.24	4555	0.35	7413N	0.27	74112N	1.70	74196N	0.55			74LS181N	1.05	74LS347N	0.35	74C193	0.80	Z80ASIO/1	11.00
4050	0.24	4556	0.40	7414N	0.51	74113N	1.98	74197N	0.55			74LS183N	1.75	74LS349N	1.99	74C195	0.80	Z80ASIO/2	11.00
4051	0.55	4557	2.30	7415N	0.27	74114N	1.20	74198N	0.85			74LS189N	1.28	74LS353N	2.30	74C200	4.52	Z80ASIO/3	9.95
4052	0.55	4558	0.80	7416N	0.27	74115N	1.98	74199N	1.00			74LS190N	1.45	74LS355N	1.99	74C201	1.06	Z80ACTC	4.00
4053	0.55	4559	3.50	7417N	0.27	74116N	1.98	74200N	1.00			74LS191N	1.45	74LS356N	1.99	74C202	1.06	Z80CTC	4.50
4054	1.30	4560	2.50	7418N	0.27	74117N	1.20	74201N	1.00			74LS192N	1.45	74LS357N	1.70	74C303	0.38	Z8001	65.00
4056	1.30	4561	1.00	7419N	0.27	74118N	1.20	74202N	1.00			74LS193N	1.45	74LS358N	1.70	74C903	0.38	<b>PR0M</b>	
4056	1.30	4562	2.50	7420N	0.13	74119N	1.20	74203N	1.00			74LS194N	1.45	74LS359N	1.70	74C905	5.64	2708	2.00
4059	5.75	4566	1.20	7421N	0.28	74120N	0.95	74204N	1.00			74LS195N	1.45	74LS360N	1.70	74C906	0.38	2716	£3.00
4060	0.75	4568	1.45	7422N	0.28	74121N	0.95	74205N	1.00			74LS196N	1.45	74LS361N	1.70	74C907	0.38	2532	0A
4063	1.15	4569	1.70	7423N	0.22	74122N	0.34	74206N	1.00			74LS197N	1.45	74LS362N	1.70	74C908	0.84	2732	£4.00
4066	0.30	4572	0.22	7424N	0.22	74123N	0.40	74207N	1.00			74LS198N	1.45	74LS363N	1.70	74C909	1.52	Prices shown	
4067	4.30	4580	3.25	7425N	0.22	74124N	0.40	74208N	1.00			74LS199N	1.45	74LS364N	1.70	74C914	0.86	exclude VAT.	
4068	0.16	4581	1.40	7426N	0.22	74125N	0.40	74209N	1.00			74LS200N	3.40	74LS365N	1.70	74C918	0.98	Postage 50p	
4068AE	0.14	4582	0.70	7427N	0.22	74126N	0.40	74210N	1.00			74LS201N	3.40	74LS366N	1.70	74C922	4.32	per order (UK).	
4070	0.16	4583	0.80	7428N	0.22	74127N	0.40	74211N	1.00			74LS202N	3.45	74LS367N	1.70	74C923	4.32		
4071	0.16	4584	0.80	7429N	0.22	74128N	0.40	74212N	1.00			74LS203N	3.45	74LS368N	1.70	74C924	4.32		
4072	0.16	4585	0.80	7430N	0.22	74129N	0.40	74213N	1.00			74LS204N	3.45	74LS369N	1.70	74C925	4.32		
4073	0.16	4586	0.80	7431N	0.22	74130N	0.40	74214N	1.00			74LS205N	3.45	74LS370N	1.70	74C926	4.32		
4077	0.16	4702	4.50	7432N	0.22	74131N	0.40	74215N	1.00			74LS206N	3.45	74LS371N	1.70	74C927	4.32		
4075	0.16	4703	4.48	7433N	0.22	74132N	0.40	74216N	1.00			74LS207N	3.45	74LS372N	1.70				
4076	0.55	4704	4.24	7434N	0.22	74133N	0.40	74217N	1.00			74LS208N	3.45	74LS373N	1.70				
				7435N	0.22	74134N	0.40	74218N	1.00			74LS209N	3.45	74LS374N	1.70				
				7436N	0.22	74135N	0.40	74219N	1.00			74LS210N	3.45	74LS375N	1.70				
				7437N	0.22	74136N	0.40	74220N	1.00			74LS211N	3.45	74LS376N	1.70				
				7438N	0.22	74137N	0.40	74221N	1.00			74LS212N	3.45	74LS377N	1.70				
				7439N	0.22	74138N	0.40	74222N	1.00			74LS213N	3.45	74LS378N	1.70				
				7440N	0.22	74139N	0.40	74223N	1.00			74LS214N	3.45	74LS379N	1.70				
				7441N	0.22	74140N	0.40	74224N	1.00			74LS215N	3.45	74LS380N	1.70				
				7442N	0.22	74141N	0.40	74225N	1.00			74LS216N	3.45	74LS381N	1.70				
				7443N	0.22	74142N	0.40	74226N	1.00			74LS217N	3.45	74LS382N	1.70				
				7444N	0.22	74143N	0.40	74227N	1.00			74LS218N	3.45	74LS383N	1.70				
				7445N	0.22	74144N	0.40	74228N	1.00			74LS219N	3.45	74LS384N	1.70				
				7446N	0.22	74145N	0.40	74229N	1.00			74LS220N	3.45	74LS385N	1.70				
						74146N	0.40	74230N	1.00										

## THIS MONTH'S NEW KITS

For the musically inclined	
Drum Synthesiser	£29.50
Mixer/Pre Amp	£16.00
Stylus Organ	£4.95
For the Service Engineer	
Micro Volt Multiplier	£3.95
Sign Wave Generator	£5.75
Linear Power Output Meter	£11.50
For the Ham or CB Enthusiast	
Aerial Director	£24.50
Aerial Direction Indicator	£5.90
For the Motorist	
Electronic Ignition Kit	£19.50
For all of you	
Electric Jigsaw Puzzle	£5.30
Blow Heater Kit	£6.45
And if you are having TV Interference Problems	
High-Pass Filter	£1.95
Low-Pass Filter	£3.45

## UNIVAC KEYBOARD BARGAIN

Ideal for use with ZX80/81. Has 50 keys and many other parts for your spares box. Probably cost in excess of £100. In very good used condition — £13.50 + £2.00 post. Diagram showing how to connect to ZX80/81 — £2.00 extra.

## COMPUTER DESK



Size approx. 4'x2'x2'6" high. These were made for hard work, the top being formica covered. Suitable for housing instruments or for use as office desks. Beautifully made, these cost over £100 each, our price only £11.50 each, however, you must arrange to collect.

## EXTRACTOR FANS

Mains operated — ex. Computer.

- 5" Woods extractor £5.75 Post £1.00.
- 6" Woods extractor £6.90 Post £1.25
- 6" Plannair extractor £7.50 Post £1.00
- 4" x 4" Muffin 115v £4.50 Post 50p.
- 4" x 4" Muffin 230v £5.75 Post 50p.



## INTERRUPTED BEAM

This kit enables you to make a switch that will trigger when a steady beam of infra red or ordinary light is broken. Main components — relay, photo transistor, resistors and caps, etc. Circuit diagram but no case. Price £2.30

## INSTRUMENT BOX WITH KEY


Very strongly made (ply-wood slides with hard board top and bottom). This is black grained effect, vinyl covered, very pleasing appearance. Internal dimensions 12½" long, 4¼" wide, 6" deep. Ideal for carrying your multi range meter and small tools and for keeping them in a safe place. £2.30. Post paid if ordered with other goods, otherwise £1.00.

## ROPE LIGHT

4 sets of coloured lamps in translucent plastic tube arranged to give the appearance of a running or travelling light. With variable speed control box, ideal for disco or shop window display. Complete, made up, ready to plug into mains. £36.00 + £2 post.
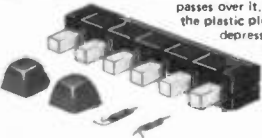
## COMPUTER KEY SWITCHES (make your own keyboard)

These are for making up on a p.c.b. and consist of a vertical mounting computer type reed switch, which makes circuit when a magnet passes over it. The magnet is located in the plastic plunger which in turn is depressed by a push rod, to which the legend top is fixed. These are made up in banks of 6, price £2.30 per bank of 6 (including tops)




**OUR CAR STARTER AND CHARGER KIT** has no doubt saved many motorists from embarrassment in an emergency you can start car off mains or bring your battery up to full charge in a couple of hours. The kit comprises: 250w mains transformer, two 10 amp bridge rectifiers, start/charge switch and full instructions. You can assemble this in the evening, box it up or leave it on the shelf in the garage, whichever suits you best. Price £11.50 + £2.50 post.

**GPO HIGH GAIN AMP/SIGNAL TRACER.** In case measuring only 5½in x 3½in x 1½in is an extremely high gain (70dB) solid state amplifier designed for use as a signal tracer on GPO cables, etc. With a radio it functions very well as a signal tracer. By connecting a simple coil to the input socket a useful mains cable tracer can be made. Runs on standard 4½v battery and has input, output sockets and on-off volume control, mounted flush on the top. Many other uses include general purpose amp, cueing amp, etc. An absolute bargain at only £1.85. Suitable 80ohm earpiece 69p.

**FREE** OUR CURRENT BARGAIN LIST WILL BE ENCLOSED WITH ALL ORDERS.

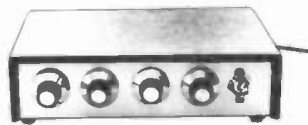
## 3 CHANNEL SOUND TO LIGHT KIT

Complete kit of parts for a three-channel sound to light unit controlling over 2000 watts of lighting. Use this at home if you wish but it is plenty rugged enough for disco work. The unit is housed in an attractive two-tone metal case and has controls for each channel, and a master on/off. The audio input and output are by ¼" sockets and three panel mounting fuse holders provide thyristor protection. A four-pin plug and socket facilitate ease of connecting lamps. Special snip price is £14.95 in kit form or £25.00 assembled and tested.


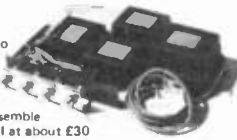
## MULLARD UNILEX

A mains operated 4 + 4 stereo system. Rated one of the finest performers in the stereo field this would make a wonderful gift for almost anyone. In easy to assemble modular form this should sell at about £30 — but due to a special bulk buy and as an incentive for you to buy this month we offer the system complete at only £16.75 including VAT and post. **FREE GIFT** — buy this month and you will receive a pair of Goodman's elliptical 8"x5" speakers to match this amplifier.



## THIS MONTH'S SNIP POCKET AUDIO COMPONENT TESTER



With it you can quickly test diodes, rectifiers, transistors, capacitors, check wiring and p.c. boards for open circuits, find the anode and cathode of a diode or rectifier and whether a transistor is PNP or NPN, which are the base collector and emitter connections. Condensers, if bad, give a continuous signal, but if good, give intermittent signals of varying length depending on their value. The test current is very low (2uA) and the voltage only 1.4v, so it is also possible to check MOS devices, as well as sensitive transistors without fear of damaging them. The unit is supplied complete with internal battery, which should last many months. Price £3.45p

## THERMOSTAT ASSORTMENT

10 different thermostats. 7 bi-metal types and 3 liquid types. There are the current stats which will open the switch to protect devices against overload, short circuits, etc., or when fitted say in front of the element of a blow heater, the heat would trip the stat if the blower fuses; appliance stats, one for high temperatures, others adjustable over a range of temperatures which could include 0 — 100°C. There is also a thermostatic pod which can be immersed, an oven stat, a calibrated boiler stat, finally an ice stat which, fitted to our waterproof heater element, up in the loft could protect your pipes from freezing. Separately, these thermostats could cost around £15.00 — however, you can have the parcel for £2.50.

## 6 WAVEBAND SHORTWAVE RADIO KIT

Bandspread covering 13.5 to 32 metres. Based on circuit which appeared in a recent issue of Radio Constructor. Complete kit includes case materials, six transistors and diodes, condensers, resistors, inductors, switches, etc. Nothing else to buy if you have an amplifier to connect it to or a pair of high resistance headphones. Price £11.95.

## MEDIUM & 2 SHORT WAVE CRYSTAL RADIO

All the parts to make up the beginner's model. Price £2.30. Crystal earpiece 65p. High resistance headphones (gives best results) £3.75. Kit includes chassis and front but not case.

## TRANSMITTER SURVEILLANCE

Tiny, easily hidden but which will enable conversation to be picked up with FM radio. Can be made in a matchbox — all electronic parts and circuit. £2.30. (Not licencible in the U.K.).

## RADIO MIKE

Ideal for discos and garden parties, allows complete freedom of movement. Play through FM radio or tuner amp. £6.90 comp. kit. (Not licencible in the U.K.).

## RADIO STETHOSCOPE

Easy to fault find — start at the aerial and work towards the speaker — when signal stops you have found the fault. Complete kit £4.95.

## MUGGER DETERRENT

A high-note bleeper, push latching switch, plastic case and battery connector. Will scare away any villain and bring help. £2.50 complete kit.

## POPULAR SNIP — STILL AVAILABLE

And it still carries a free gift of a desoldering pump, which we are currently selling at £6.35p. The snip is perhaps the most useful breakdown pump we have ever offered. It is a parcel of 50 nearly all different computer panels containing parts which must have cost at least £500. On these boards you will find over 300 IC's. Over 300 diodes, over 200 transistors and several thousand other parts, resistors, condensers, multi-turn pots, rectifiers, SCR, etc. etc. If you act promptly, you can have this parcel for only £8.50, which when you deduct the value of the desoldering pump, works out to just a little over 4p per panel. Surely this is a bargain you should not miss! When ordering please add £2.50 post and £1.27 VAT.

## BURGLAR ALARM CONTROL PANEL

Contains labelled connection block, latching relay, test switch and removable key control switch. Simplifies the whole installation, all you have to do is to take wires to pressure pads and to alarm bell. Price £7.95, with complete diagram.


## MINI MONO AMP

On p.c.b., size 4" x 2" approx. Fitted volume control and a hole for a tone control should you require it. The amplifier has three transistors and we estimate the output to be 3W rms. More technical data will be included with the amplifier. Brand new, perfect condition, offered at the very low price of £1.15 each, or 10 for £10.00.


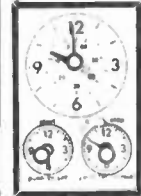
## DELAY SWITCH

Mains operated — delay can be accurately set with pointers knob for periods of up to 2½hrs. 2 contacts suitable to switch 10 amps — second contact opens a few minutes after 1st contact. £1.95.




## TIME SWITCH BARGAIN

Large clear mains frequency controlled clock, which will always show you the correct time + start and stop switches with dials. Complete with knobs. £2.50.
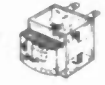
## LEVEL METER

Size approximately ¼" square, scaled signal and power but cover easily removable for rescaling. Sensitivity 200 uA. 75p.



## WATERPROOF HEATING WIRE

60 ohms per yard, this is a heating element wound on a fibre glass coil and then covered with p.v.c. Dozens of uses — around water pipes, under grow boxes in gloves and socks.

## TANGENTIAL BLOW HEATER

2.5 Kw quiet, efficient instant heating from 230/240 volt mains. Kit consists of blower as illustrated, 2.5 Kw element, control switch and data all for £4.95. post £1.60.



## 12V SUBMERSIBLE PUMP

Just join it to your car battery, drop it into the liquid to be moved and up it comes, no messing about, no priming, etc. and you get a very good head. Suitable for water, paraffin and any non-explosive non-corrosive liquid. One use if you are a camper, make your own shower. Price: £8.50.



## VENNER TIME SWITCH

Mains operated with 20 amp switch, one on and one off per 24 hrs. repeats daily automatically correcting for the lengthening or shortening day. An expensive time switch but you can have it for only £2.95. These are without case, but we can supply metal case with window £2.95.

Also available is adaptor kit to convert this into a normal 24hr. time switch but with the added advantage of up to 12 on/off per 24hrs. This makes an ideal controller for the immersion heater. Price of adaptor kit is £2.30. Post any or all items £1.

## 12V FLUORESCENT LIGHTING

For camping — car repairing — emergency lighting from a 12v battery you can't beat fluorescent lighting. It will offer plenty of well distributed light and is economical. We offer an inverter for 21" 13 watt miniature fluorescent tube. £3.45. (tube not supplied).



## FIVE UNUSUAL SWITCHES

For inventors, experimenters, service engineers, students or in fact anyone interested in making electrical gadgets. The parcel contains: — delay switch — motor driven switch — two-way and off switch — polarity changing switch — and humidity switch. Our regular price for these switches bought separately is over £10, but this month you can have the 5 for £2.50.

## SPIT MOTORS

These are powerful mains operated induction motors with gear box attached. The final shaft is a ½" rod with square hole, so you have alternative coupling methods — final speed is approx. 5 revs/min, price £5.50. — Similar motors with final speeds of 80, 100, 160 & 200r.p.m. same price.

## COMPONENT BOARD

Ref. W0998

This is a modern fibreglass board which contains a multitude of very useful parts, most important of which are: 35 assorted diodes and rectifiers including 4 3amp 400v types (made up in a bridge) 8 transistors type BC 107 and 2 type BFY 51 electrolytic condensers. SCR ref 2N 5062, 25 Ohm 100v DC and 100uf 25v DC and over 100 other parts including variable, fixed and wire wound resistors, electrolytic and other condensers. A real snip at £1.15.

# J. BULL (Electrical) Ltd.

(Dept. EE), 34 - 36 AMERICA LANE, HAYWARDS HEATH, SUSSEX RH16 3QU. **Established 30 YEARS**

**MAIL ORDER TERMS:** Cash, P.O. or cheque with order. Orders under £10.00, add 60p service charge. Monthly account orders accepted from schools and public companies. Access & Barclaycard orders phone Haywards Heath (0444) 54563. **CALLERS:** to Haywards Heath (closed Sat.), or 2, Bentham Road, Off Elm Grove, Brighton (closed Wed.). **BULK ORDERS:** Write for special quotation. Normally delivery is by return.

# ELECTROVALUE

## CATALOGUE '82

ESSENTIAL READING FOR:  
THE ELECTRONICS  
ENTHUSIAST  
THE COMPUTING FREAK  
THE EQUIPMENT  
MANUFACTURER



PACKED WITH INFORMATION  
ON MORE THAN 6,000 STOCK  
ITEMS: ACTIVE AND PASSIVE  
COMPONENTS, BOXES, CASES,  
COMPUTER HOUSINGS,  
KNOBS, POTS, SWITCHES,  
RELAYS.  
EVERYTHING FROM R's AND  
C's TO COMPUTING SYSTEMS

FOR YOUR COPY OF CATA-  
LOGUE 82 please send 70p  
(includes 70p voucher to be re-  
claimed against orders valued  
£10.00 or over).

ALL ITEMS BRAND NEW  
AND GUARANTEED  
SPEEDY MAIL ORDER  
SERVICE

No P/P charges on U.K. C.W.D.  
orders over £5.75 inc. V.A.T.  
(add 40p handling charge if  
under).

PLEASE ADD 15% V.A.T. TO  
TOTAL VALUE OF ALL  
ORDERS

FOR EV BARGAINS LIST and  
useful News Sheet send S.A.E.

4000BE SERIES	74LS00 SERIES	74LS193	90p
4000BE	74LS00	74LS193	90p
4001BE	74LS01	74LS194	87p
4002BE	74LS02	74LS196	90p
4006BE	74LS04	74LS197	85p
4007BE	74LS05	74LS253	90p
4008BE	74LS08	74LS257	75p
4009BE	74LS10	74LS259	160p
4010BE	74LS11	74LS266	31p
4011BE	74LS14	74LS273	130p
4012BE	74LS16	74LS279	76p
4013BE	74LS20	74LS299	295p
4014BE	74LS22	74LS367	56p
4015BE	74LS24	74LS368	55p
4016BE	74LS28	74LS373	150p
4017BE	74LS32	74LS374	150p
4018BE	74LS37	74LS378	84p
4019BE	74LS47	74LS393	85p
4020BE	74LS51		
4021BE	74LS52		
4022BE	74LS53		
4023BE	74LS54		
4024BE	74LS56		
4025BE	74LS58		
4026BE	74LS59		
4027BE	74LS62		
4028BE	74LS64		
4029BE	74LS66		
4030BE	74LS68		
4031BE	74LS70		
4032BE	74LS72		
4033BE	74LS74		
4034BE	74LS76		
4035BE	74LS78		
4036BE	74LS80		
4037BE	74LS82		
4038BE	74LS84		
4039BE	74LS86		
4040BE	74LS88		
4041BE	74LS90		
4042BE	74LS92		
4043BE	74LS94		
4044BE	74LS96		
4045BE	74LS98		
4046BE	74LS100		
4047BE	74LS102		
4048BE	74LS104		
4049BE	74LS106		
4050BE	74LS108		
4051BE	74LS110		
4052BE	74LS112		
4053BE	74LS114		
4054BE	74LS116		
4055BE	74LS118		
4056BE	74LS120		
4057BE	74LS122		
4058BE	74LS124		
4059BE	74LS126		
4060BE	74LS128		
4061BE	74LS130		
4062BE	74LS132		
4063BE	74LS134		
4064BE	74LS136		
4065BE	74LS138		
4066BE	74LS140		
4067BE	74LS142		
4068BE	74LS144		
4069BE	74LS146		
4070BE	74LS148		
4071BE	74LS150		
4072BE	74LS152		
4073BE	74LS154		
4074BE	74LS156		
4075BE	74LS158		
4076BE	74LS160		
4077BE	74LS162		
4078BE	74LS164		
4079BE	74LS166		
4080BE	74LS168		
4081BE	74LS170		
4082BE	74LS172		
4083BE	74LS174		
4084BE	74LS176		
4085BE	74LS178		
4086BE	74LS180		
4087BE	74LS182		
4088BE	74LS184		
4089BE	74LS186		
4090BE	74LS188		
4091BE	74LS190		
4092BE	74LS192		
4093BE	74LS194		
4094BE	74LS196		
4095BE	74LS198		
4096BE	74LS200		

**NICADS AND CHARGERS**  
by Sanyo Cadnica  
N450AA (AA size) 99p  
N1800C (C size) £2.27  
N3500D (D size) £3.76  
DN75P (PP3 size) £4.10  
**CHARGERS:**  
NC75G (PP3) £4.95  
NC450S (4 x AA) £4.95  
NC1230 (A.A. C.D) £7.60

**COMPONENT PACKS**  
Buy in quantity for best value  
CPI: 100 ceramic capacitors from 10p to 1µF  
Selection determined by relative popularity.  
Pack Price £4.20

**RESISTOR DECADE PACKS**  
±W, 5% tolerance, each pack 100 items from  
one decade. Selection determined by popu-  
larity of each value.  
RD1: 1R0-8R2; RD2: 10R-82R; RD3: 100R-  
820R RD4: 1K-82K; RD5: 10K-82K; RD6:  
100K-820K; RD7: 1M-10M, each decade pack  
£1.50

**SEMICONDUCTOR PACKS**  
LD30A-2.9mm red LED's 25 for £1.50  
L51RD-5mm red LED's 25 for £1.50  
1N4148 Diodes 25 for 88p  
1N4007-1A 1000V Diodes 25 for £1.30  
1N5402-3A 200V Diodes 25 for £2.80  
BC107/BC108/BC109 25 for £2.98  
BC182/182L/183/183L/184/184L 25 for £1.88  
BC212/212L/214/214L 25 for £1.88

**TRANSISTOR SELECTION**  
2N3053 23p  
2N3054 73p  
2N3055 70p  
BC327 11p  
BC337 11p  
BD130 45p  
BD131 77p  
BD139 30p  
BD140 32p  
BD679 53p  
BD680 55p  
BFY50 28p  
MJE2955 £1.20  
MJE3055 87p  
TIP31A 44p  
TIP32A 44p  
TIP41A 45p  
TIP42A 45p  
TIP2955 55p  
TIP3055 55p

**ANALOGUE IC SELECTION**  
741C8 18p  
748C8 35p  
7555 86p  
CA3080E 86p  
CA3130E 99p  
CA3140E 40p  
LM380N 99p  
LM381 £1.51  
LM3914N £2.68  
NE555V 23p  
NE556A 76p  
TDA2030 £1.45  
TL071CP 45p  
TL072CP 75p  
TL074CN £1.29  
UA1170 £1.52  
XR2206 £4.60  
ZN414 £1.22  
ZN425E £3.90

## SPECIAL NASCOM OFFER

Quantity purchase enables us to offer superb  
NASCOM Microcomputer system at a much  
reduced price. The system comprises:  
NASCOM 2 kit £4.95  
RAM B kit with 16k Dynamic RAM and sockets  
for a further 32k.  
3A PSU kit.  
NASSYS 3—the new NASCOM Monitor.  
Graphics ROM—block graphics.  
Programmers A10—BASIC toolkit.  
Mini-Motherboard.  
**Special price £340.00 + VAT**

## STOP PRESS


**SHARP MZ80K WITH  
HI-RES GRAPHICS  
PACKAGE  
ONLY £445.00 + VAT.**

**NEW SABTRONICS  
Frequency Meter**  
Model 8000B: 8-digit 1GHz Frequency Meter.  
Professional specification: £180.00

**OTHER SABTRONICS  
EQUIPMENT**  
£1.45 2015A Bench DMM (LCD) £83.00  
£4.50 2035A Hand-Held DMM (LCD) £82.00  
£7.50 8110A 8 digit 100MHz DFM £87.00  
£1.52 8610A 8 digit 600MHz DFM £82.00  
£4.60 5020A 1-200KHz Function Generator, Sine,  
Square, Triangle and separate TTL Square  
£1.22 wave outputs £79.00
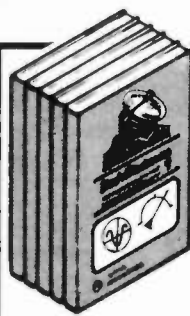
# ELECTROVALUE

Dept. EE.2, 28 St Judes Rd., Englefield Green, Egham, Surrey  
TW20 0HT. Phone Egham 35693 (STD 0874) (London 87) Telex  
244475. Northern Branch (personal shoppers only) 880 Burnage  
Lane, Burnage, Manchester M19A 1MA. Phone (061) 4324945.  
LTD



## ANNOUNCING A NEW SET OF BASIC ELECTRONICS

This 5 volume set contains over 500 pages.  
Bound in stiff linen. Cover size 8 1/2" x 5 1/2".  
Price £10.00 per set (we pay the postage).

- Book 1. Introducing Electronics
- Book 2. Resistors/Capacitors
- Book 3. Inductors/Diodes
- Book 4. Meters/Voltage-dividers
- Book 5. Transistor Project Circuitry

The manuals are unquestionably the finest and most up-to-date available  
and represent exceptional value.

This series has been written in a fascinating, absorbing and exciting  
way, providing an approach to acquiring knowledge that is a very  
enjoyable experience. Suitable for industrial trainees, City and Guilds  
students, DIY enthusiasts and readers of electronic journals.  
Each part explains electronics in an easy-to-follow way, and contains  
numerous diagrams and half tone blocks with construction details and  
circuit diagrams for making the following transistor projects: Lamp  
Flasher, Metronome, Wailer, Photographic/Monostable Timer, Metal  
Locator, Geiger Counter, Radio Receiver, Intercom., Intruder Alarm,  
Electronic Organ, Battery Eliminator, Anemometer, Sound Switch,  
Light and Water-operated Switches, Pressure-operated Switches, Light  
meter, Radio Thermometer, Ice Alarm,

Order now:  
Selray Book Company  
11, Aspen Copse,  
Bromley,  
Kent. BR1 2NZ.

### OUR 100% GUARANTEE

Should you decide to return the set after 10 days exam-  
ination, your money will be refunded by return of post.

Please allow 14 DAYS Delivery

Amount enclosed: £

Name:

Address:

EE 3

## JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron — now at a bargain price.  
Outstanding performance. Lightweight. Easy to maintain.  
Elements are enclosed in Stainless Steel shafts.  
Insulated with mica and ceramic. Non-seize  
interchangeable bits, choose from  
'copper' or 'long life'. A very special  
tool at a very special 'direct' price.  
Just £5.22 for iron fitted with 3.2mm  
copper bit. Just £2.27 for 3 spare  
copper bits (1.6: 2.4: 4.7).

A mere £4 for  
professional spring  
stand! **Or buy the  
lot for £10.34  
and save 10%.**

All prices inc. VAT P & P  
Please allow 14 Days Delivery  
Write today. Send Cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN  
or phone 01-689 0574 for Barclaycard/Access sales.



**£5.22** LITESOLD  
LIGHT SOLDERING  
DEVELOPMENTS LTD

## The ONE catalogue you MUST have!



- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing  
and insurance.

Send cheque or P.O. for £1.50.

**HOME RADIO Components Ltd**  
Dept. EE P.O. Box 92, 215 London Road,  
Mitcham, Surrey. 01-543 9659



# THE SENSATION OF THE JAPANESE MUSIC FAIR

Designed by a genius. Controlled by a computer. Programmed by a laser. Played by amateurs professionally and by professionals superbly.

## THE NEW CASIOTONE 701

"... what is going to become THE instrument of 1982... probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician... I suggest you place your orders now." (*Keyboard & Music Player*)  
 "... opens up home music making for all the family... one of the most advanced music teaching aids so far developed... this instrument is going to be one of the biggest sellers of 1982." (*Electronics & Music Maker*)




Complete Programmable Polyphonic Keyboard (RRP £555) **ONLY £495**

- ★ Input an entire piece of music, specially scored in bar code and read by a light pen attached to the instrument.
- ★ Alternatively, program your own melodies (max. 345 steps), chords (max. 201 steps) and tempo, via the keyboard, into the extensive memory, (up to 5 minutes playing or more) with full editing facilities.
- ★ 3-WAY PLAYBACK.
  1. Automatic playback of the entire piece; melody, chord, bass and rhythm with arpeggio. Follow the melody as it plays via lamps above each individual key.
  2. Manual melody playing, guided by the keyboard lamps, with automatic bass and rhythm accompaniment.
  3. ONE KEY PLAY facility, allows the melody line to be played, simply by stroking one key. Non-players can become Instant Musicians!
- ★ The 5 octave, 8-note polyphonic keyboard can be split into 2 & 3 octaves and a different voice can be selected for the accompaniment.
- ★ 20 "breathtakingly clear and bright" pre-set instruments and voices.
- ★ 3-way chord section:—Fingered, Memory and Casiochord auto accompaniment.
- ★ 16 rhythm accompaniments with "fill in" variation and two percussion effect buttons. Start/Stop, Synchro, Tempo and Balance controls. Variable Vibrato and Sustain, I/p & o/p jacks. Integral amplifier/speaker. Music book. AC only. Dims: 5 x 37 1/2 x 13-7/16". Optional extras: Foot pedals. Hard case.

**FREE** CREDIT. 0% interest, 1/3 deposit, 12 monthly repayments. (Not MT-31, MT-40, or VL-1), or reduced rates for longer period. INTEREST (0%) on ACCESS, B'CARD or VISA for first 6 months. for any keyboard purchase over £90.

## NEW PORTABLE KEYBOARDS


CASIOTONE MT-40

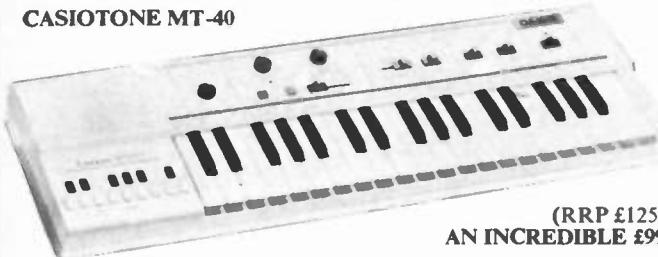

(RRP £125)  
**AN INCREDIBLE £99**

- ★ 8-note polyphonic playing of this 37 key, 3 octave keyboard.
- ★ 15 key bass keyboard with automatic synchronised bass function.
- ★ 22 lively and realistic built-in instrument sounds and voices.
- ★ 6 built-in auto rhythms, with dual "Fill-in" rhythmic interludes.
- ★ Sustain, Vibrato and Pitch controls. Line out and Headphone jacks.
- ★ Integral amplifier and speaker. Battery powered, or optional AC adaptor. Dims: 61-6 x 584 x 178mm (2-7/16 x 23 x 7"). Weight: 22kg (4-9lb).

CASIOTONE MT-31

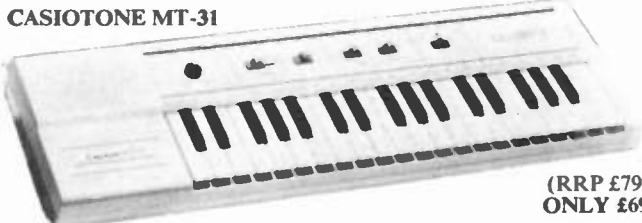

(RRP £79)  
**ONLY £69**

"... basically a revision of the MT-30 (one of my all time favourite electronic keyboards)." *Electronics & Music Maker*. Similar to the MT-40 but without the rhythm box, bass and auto functions. Dimensions: As MT-40. Weight: 2.0kg (4-4lb) including batteries.

OTHER CASIOTONES  
 CT-101 £195. CT-202 £275. CT-403 £275. VL-TONE £35-95. Lists on request.

**DELIVERY NORMALLY BY RETURN OF POST.**

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

# TEMPUS

Everyday Electronics, March 1982

## £120 COMPUTER

"Can do the job of a micro costing four times as much!"  
 Personal Computer World

## CASIO FX-702P POCKET COMPUTER



**ONLY £119.95**

Plus FREE MICROL Professional Programming Pack (RRP £9.95)  
 Or we will beat any lower advertised price by 5%.

**Eat your hearts out, H-P, Sharp and Texas!**

The Casio FX-702P features: The biggest program storage capacity (up to 1680 steps), the biggest data storage capacity (up to 226 memories), the widest range of math, science and statistics functions (55 in all, including Regression and Correlation), the most powerful English-like BASIC program-writing language and the fastest operation, for results without waiting! Subroutines: 10 levels, FOR: NEXT looping; 8 levels. Comprehensive edit, debug and trace modes. 240 hours battery life. 17 x 165 x 82mm.

FA-2. Cassette adaptor for bulk storage of programs and data, with powerful file name and remote control options. **ONLY £19.95.**

FP-10. Permanent hard copy printer: full 20 character line width, fast 40 character per second print speed. 2,600 lines per roll. (Low cost replacement rolls, £2.50 for five), 6,000 to 9,600 lines battery life. Rechargeable battery pack, NP-4M, prints 13,000 lines (£6.90). Mains adaptor, AD-4150, £5.

FP-10 Printer **ONLY £44.95.**  
 Plus FREE Pack worth £5, or we will beat any lower price by 5%.

SYSTEM PRICES—Save up to £50 on RRP	
PACK A: FX-702P + MICROL Professional Programming Pack	£119.95
PACK B: FX-702P + FA-2 cassette interface + PPP + PROCOS	£155.50
PACK C: FX-702P + FP-10 Printer + FA-2 + PPP + PROCOS	£194.50

**MICROL PROCOS for the 702P. Exclusive to TEMPUS.**  
 Now you can create powerful, reliable programs in just minutes with this advanced, integrated operating system, even if you have never programmed a computer before! "Visicalc-type" system answers "what if" questions and analyses trends. On ready-to-run cassette, with user manual. **£24.95**

**CASIO FX-602P The World's Fastest Programmable?**  
 Alpha/numeric scrolling display. From 32 program steps with 88 memories, to 512 steps with 22 memories, all non volatile. **ONLY £74.95**  
 FA-2 £19.95. FP-10 £44.94. (Also compatible with FX-501/2P, and FX-601P).

**CASIO FX-3600P low cost programmable.**  
 38 program steps, 7 memories, INTEGRALS AND REGRESSION. **£22.95**

## 50M WATER RESISTANT ANALOG/DIGITAL

Alarm chronograph with countdown alarm timer

**CASIO AA-92W**

**ONLY £25.95**

Analog. Independent hours & minutes, with sync digital seconds. Dual time ability. Digital Hours, minutes, seconds, day & date. 1/100 second stopwatch to 12 hours. Net, lap & 1st/2nd place. Start/stop & 10 min. signals. Alarm. For 30 seconds with carousel display. Countdown Alarm. Normal and net times to 1 hr. with amazing "Star Burst" flashing display. Half hourly & hourly chimes. Lithium battery. Stainless Steel W/R Case. Mineral glass face.



**CATALOGUE ON REQUEST**  
 14p stamp appreciated

ACCESS, VISA or B'CARD number to:  
**LEADING CASIO SPECIALISTS**  
 Dept. EE,  
 38 Burleigh Street, Cambridge CBI IDG  
 Telephone: 0223 312866

**DO YOU EVER NEED A FEW MORE HANDS? . . . IF SO**




# THE MINIBENCH\*

System

will add a new dimension to your hobby



	£.p	£.p
Minibench Standard model	15.95	1.75
Delux model with whisper smooth action	17.95	1.75
Delux model with rotating turn-table base on free-standing mount (as illustrated)	32.50	3.00
<b>Flexi-Arm — 12"</b>	4.75	15
— 18"	5.50	15
<b>Lens Attachment—</b>		
50mm lens	2.50	15
75mm lens	3.25	20
100mm lens	5.00	30
<b>Clip Attachment — Large</b>	2.00	—
— Small	1.25	—
<b>Light Fitting with 18" F/Arm</b>	7.50	20
<b>Transformer Unit mains to 12V 1A Complete with switch</b>	10.50	75

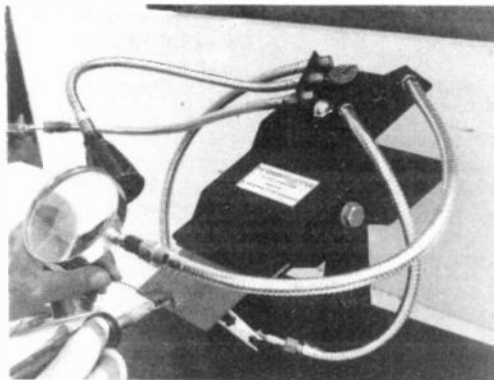

- ★ Just a squeeze to clamp or release circuit board
- ★ Adjustable minimum jaw aperture
- ★ Jaws flip over for work on either side of circuit board
- ★ Rubber lined jaws for circuit board protection & maximum grip
- ★ Single wing nut controls jaw attitude and friction setting
- ★ Crocodile clips mounted on flexi-arms hold components exactly where needed
- ★ Crocodile clip can be used as a heatshunt
- ★ Lens similarly mounted is ideal for close work and spotting those solder bridges
- ★ Flexi-arms keep station with circuit board
- ★ Built to last a lifetime!
- ★ Stove enamelled silver/grey hammer—or power coated matt orange/black finish

PLEASE ADDRESS ALL ORDERS TO:—

Pat App for

\*Trade Mark

**SALES DEPT., ABSONGLLEN LTD., PO BOX 13, HEREFORD HRI IEA**

## E.E. KITS

Model Train Chuffer	ZB175	Jan. 82	£7.25
Siren Module	ZB176	Jan. 82	£5.50
Mini Egg Timer	ZB177	Jan. 82	£3.25
Race Track Speedo	ZB173	Dec. 81	£22.50
Guitar Adaptor	ZB172	Dec. 81	£3.25
Re Action Meter	ZB171	Dec. 81	£14.50
Sustain Unit	ZB170	Oct. 81	£9.50
Audio Compression Mixer	ZB168	Sept. 81	£13.50
Model Railway Controller	ZB169	Sept. 81	£12.50
Led Sand Glass	ZB162	Aug. 81	£6.50
Cmos Metronome	ZB167	Aug. 81	£6.25
Morse Practise Oscillator	ZB163	Aug. 81	£19.95
Xenon Strobe Lamp	ZB161	July 81	£21.50
Electronic Multimeter	ZB159	July 81	£32.50
Darkroom Timer	ZB155	June 81	£4.00
Phone Bell Repeater/Baby Alarm	ZB153	May 81	£5.50
Digital Rule	ZB148	April 81	£28.00
LED Dice	ZB148	March 81	£7.50
Bench Power Supply	ZB143	March 81	£48.50
Sound to Light	ZB127	Nov. 80	£19.00
Audio Effects Unit	ZB122	Oct. 80	£12.25
Cable & Pipe Locator	ZB54	March 80	£4.00
Slide Tape Synchroniser	ZB42	Feb. 80	£11.50
Baby Alarm	ZB40	Nov. 79	£8.50
Varicap Radio	ZB1	Sept. 79	£8.50
Electronic Canary	ZB19	June 79	£5.00
Fuzz Box	ZB106	Dec. 78	£6.75
Weirs Sound Effect Generator	ZB113	March 78	£6.00

Teach-in 821 Bulk purchase of components so prices reduced List 1 and 2. Now £22.50 List 3 £6.35 list 1, 2, & 3 £27.50.

Reprints of above kits 40p + S.A.E. Teach-in Reprints 40p each from October 1981.

Mains Ioniser Kit includes parts & Drilled Case **£19.00**

Prices include Post & 15% VAT

Wide range of Japanese I.C.s & Transistors stocked.

## T. POWELL

ADVANCE WORKS,  
41 WALLACE ROAD, LONDON N1  
Tel: 01-228 1469  
HOURS: Mon-Fri 9-3.30p.m. Sat 9-4.30p.m.



Minimum Telephone Orders £5.00  
Minimum Mail Order £1.00  
Callers welcome.

## TECHNICAL TRAINING IN ELECTRONICS AND TELECOMMUNICATIONS

ICS can provide the technical knowledge that is so essential to your success; knowledge that will enable you to take advantage of the many opportunities open to you. Study in your own home, in your own time and at your own pace and if you are studying for an examination ICS guarantee coaching until you are successful.

**City and Guilds Certificates:**  
Telecommunications Technicians  
Radio, TV, Electronics Technicians  
Technical Communications  
Radio Servicing Theory  
Radio Amateurs  
Electrical Installation Work  
MPT Radio Communications Certificate

**Diploma Courses:**  
Colour TV Servicing  
Electronic Engineering and Maintenance  
Computer Engineering and Programming  
Radio, TV, Audio Engineering and Servicing  
Electrical Engineering, Installation  
and Contracting

POST OR PHONE TODAY FOR FREE BOOKLET

**ICS** To: International Correspondence Schools

Dept 2685 Intertext House, London SW8 4UJ or telephone 622 9911

Subject of Interest .....  
Name .....  
Address .....  
Tel: ..... Age: .....



# Multicore makes soldering easy fast & reliable

## Ersin Multicore

Ersin Multicore, solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required. Comes in handy dispensers and tool box reels in two different alloys 40/60 tin/lead for general purpose electrical soldering and 60/40 tin/lead ideal for small components and fine wire soldering.



Size 3 40/60 tin/lead  
£4.37 Per reel 1.6mm dia

Size 10 60/40 tin/lead  
£4.37 Per reel 0.71mm dia



Size 19A 60/40 tin/lead  
£1.15 Handy pack 1.22mm dia

Size PC115 60/40 tin/lead  
£1.38 Handy pack 0.028mm dia

## Multicore Savbit

Multicore Savbit, solder increases the life of your soldering bit by 10 times, for better soldering efficiency and economy. Comes in two handy dispensers and tool box reels.



Size 5 Savbit  
£1.15 Per pack 1.2mm dia



Size 12 Savbit  
£4.37 Per reel 1.2mm dia



Size SV130 Savbit  
£1.73 Per pack 0.048mm dia

## Multicore Alu-Sol

Multicore Alu-Sol, solder contains 4 cores of flux, suitable for most metals especially aluminium. Comes in handy dispensers on tool box reels.

Size AL150 Alu-Sol  
£2.07 Per pack 0.48mm dia



Size 4 Alu-Sol  
£7.82 Per reel 1.6mm dia



## Multicore Solder Wick

Multicore Solder Wick, absorbs solder instantly from tags and printed circuits with the use of a 40 to 50 watt soldering iron. Quick and easy to use, desolders in seconds.

Size AB10 Solder Wick  
£1.43 Per pack



## Multicore Tip Kleen

Multicore Tip Kleen, soldering iron tip wiping pad. Replaces wet sponges.



Size 2 Tip Kleen  
£0.92 Per pack

## Bib Wire strippers and cutters

Wire strippers and cutters, with precision ground and hardened steel jaws. Adjustable to most wire sizes. With handle locking-catch and easy-grip plastic covered handles.



Size 9 Wire Strippers  
£2.69 Per pair

All prices inclusive of VAT. Available from most electrical and DIYs stores. If you have difficulty in obtaining any of these products send direct with 50p for postage and packing. For free colour brochure send S.A.E.

**Bib Audio/Video Products Limited**  
(Solder Division), Kelsey House,  
Wood Lane End, Hemel Hempstead,  
Hertfordshire, HP2 4RQ.  
Telephone: (0442) 61291  
Telex: 826437

# ALCON

SPECIAL OFFER

20kΩ/V d.c.  
4kΩ/V a.c.

## mini 20

The Mini 20 is an ideal instrument for the constructor.

This special offer is a wonderful opportunity to acquire an essential piece of test gear with a saving of nearly £10 on the normal retail price.

The 28 ranges cover all likely requirements. Operation is straight-forward, just turn the selection switch to the required range position.

### RANGES

d.c. V: 100mV, 3V, 10V, 30V, 100V, 300V, 600V.

a.c. V: 15V, 50V, 150V, 500V, 1500V.


d.c. I: 50μA, 600μA, 6mA, 60mA, 600mA.

a.c. I: 30mA, 300mA, 3A.

Ohms: 2kΩ, 2MΩ.

Movement protected by internal diode and fuse.

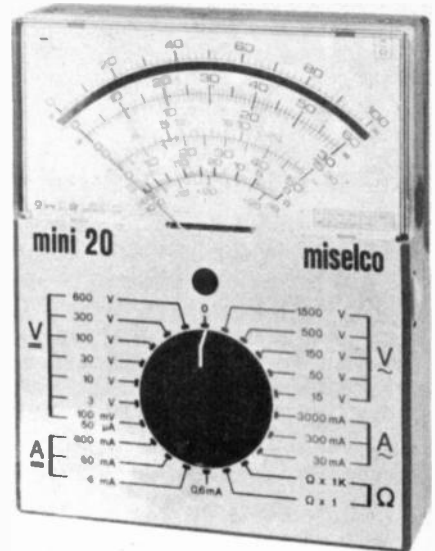For details of this and the many other exciting instruments in the Alcon range, including multimeters, component measuring and electronic instruments please write or telephone:



Supplied complete  
with case, leads and  
instructions.

**only £21.60**  
INCLUSIVE OF POST  
PACKAGE—V.A.T.

**ALCON** Instruments Ltd.

19 MULBERRY WALK · LONDON SW3 6DZ · TEL: 01-352 1897 · TELEX: 918867

Buy British—Buy Douglas Transformers  
Mail Order from TITAN Transformers &  
Components  
Central Hall Chambers, Duncombe Street,  
Grimsby, South Humberside DN32 7EG  
Prices include 15% V.A.T. Send for our  
Catalogue.



12/24V RANGE PRI 220/240V SEC (TRANSFORMER)				30/60V RANGE PRI 120/220/240V SEC (TRANSFORMER)				AUTOTRANSFORMERS 240/220—115V (TRANSFORMER)					
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P		
213	1	0.50	2.85	124	1	0.5	3.30	25	65	3.90	1.20		
71	2	1	2.77	126	2	1	6.36	64	80	4.82	1.20		
18	4	2	3.98	127	4	2	7.86	4	150	6.21	1.57		
68	3	1.5	3.46	125	6	3	11.78	69	250	7.54	1.57		
85	5	2.5	6.06	123	8	4	14.72	53	350	9.73	2.10		
70	6	3	6.87	40	10	5	17.10	67	500	11.70	2.40		
108	8	4	8.93	120	12	6	19.44	83	750	13.51	2.25		
116	12	6	9.31	121	16	8	27.70	94	1000	18.31	2.55		
17	16	8	11.46	22	20	10	32.05	95	2KVA	34.36	5.50		
187	30	15	19.23	2.50	188	24	12	37.02	5.50	73	3	64.74	5.50
232	40	20	27.81	5.00				57	5	97.85	7.00		
								101	10	178.05	10.50		

15/30V RANGE PRI 220/240V SEC (TRANSFORMER)				45/90V RANGE PRI 120/220/240V SEC (TRANSFORMER)				CASED AUTOTRANSFORMERS 240V LEAD IN 115V 2PH SOCKET OUT			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
112	1	0.50	2.84	430	1	0.5	4.69	56W	20	6.69	0.94
79	2	1	3.29	431	2	1	7.84	64W	30	8.43	1.37
3	4	2	6.18	432	4	2	12.94	4W	150	16.88	1.90
20	6	3	7.19	433	6	3	14.82	69W	250	13.17	2.10
21	8	4	8.52	434	8	4	20.04	67W	500	20.46	2.40
51	10	5	16.37	435	10	5	28.75	84W	1000	30.24	2.80
117	12	6	11.94	436	12	6	36.16	95W	2000	54.83	5.50
88	16	8	16.14	437	16	8	39.47	73W	3000	78.87	7.00
89	20	10	18.54								
90	24	12	20.57								
91	30	15	23.63								
92	40	20	33.21								

24V RANGE PRI 120/220/240V SEC (TRANSFORMER)				MILADJ ADJUSTABLE AUTOTRANSFORMERS				MILADJ ADJUSTABLE AUTOTRANSFORMERS			
TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P	TYPE	VA	PRICE	P/P
102	1	0.50	3.29	149F	60	8.40	1.90	415C	50	2.31	0.94
103	2	1	4.09	150F	100	9.71	1.90	416C	100	3.46	0.94
104	4	2	7.65	151F	200	13.84	2.25	417C	200	4.89	1.20
105	6	3	8.99	152F	250	16.69	2.40	418F	350	6.26	1.57
106	8	4	12.24	153F	350	20.77	2.80	419F	500	8.74	1.90
107	12	6	16.13	154F	500	26.03	2.90	420E	750	13.33	2.10
118	16	8	22.46	155F	750	36.78	5.50	421F	1000	11.94	2.25
119	20	10	27.05	156F	1000	47.42	6.50				
109	24	12	32.44								

Send Today 50p (Refundable with First Order) for Catalogue  
TITAN TRANSFORMERS AND COMPONENTS  
CENTRAL HALL CHAMBERS GRIMSBY DN32 7EG  
MAIL ORDER ONLY - PRICES INCLUDE 15% VAT EE 11

NOW, A PACKAGE THAT OFFERS YOU A 100uf/10V TANTALUM FOR UNDER 10p.

SPECIAL OFFER. POPULAR VALUE TANTALUM BEAD PACKAGE T1.  
3 off 0.1/35, 4 off .22/35, 6 off .33/35, 10 off 1/35, 3 off 1.5/35, 3 off 2.2/20, 3 off 3.3/15, 3 off 3.3/35, 4 off 4.7/8, 2 off 4.7/35, 3 off 6.8/25, 1 off 10/25, 2 off 22/8-3, 2 off 22/10, 2 off 22/16, 2 off 47/10, 1 off 47/16, 1 off 100/10.  
ALL THE ABOVE T1 PACKAGE NORMALLY £8-50 TO £10 SPECIAL OFFER 61 TANTS FOR £4.

TANTALUM BEAD CAPACITORS. 1 off price (10 off price).  
.1/35..10p (8p). .15/35..10p (8p). .22/35..10p (8p). .33/35..10p (8p). .47/35..10p (8p). .68/35..10p (8p). 1/35..10p (8p). 1.5/35..10p (8p). 2.2/10..12p (10p). 3.3/10..12p (10p). 3.3/35..14p (12p). 4.7/8..10p (8p). 4.7/35..10p (14p). 6.8/25..14p (12p). 6.8/35..15p (14p). 10/15..18p (15p). 10/25..18p (16p). 22/8-3..16p (14p). 22/10..25p (17p). 22/16..25p (22p). 22/25..36p (28p). 47/10..25p (22p). 47/16..40p (36p). 100/10..50p (46p). 100/16..65p (60p). 220/16..£1.20 (80p). 470/8..£1.60 (£1.40).  
OR ONE OF EACH ABOVE SPECIAL OFFER T2 FOR £7-00.  
RETAIN THIS AD. FOR ALL YOUR IMMEDIATE AND FUTURE TANTALUM REQUIREMENTS.  
SUBMINIATURE VER. MOUNTING 250V CER. DISCS Values in PF.  
2.2pf 3.3 4.7 5.6 6.8 8.2 10 15 18 22 27 33 39 47 56 68 82...3p ea. 100pf 120 150 180 200 220 270 300 330 470 560 680 820 1000 1500 1800 2000 3000 3300 4000 4700...3p ea.  
.01uf/50V .02uf/50V..4p ea. 10 off..3p ea. 5 of each value, total 200 Discs..£3-00.  
AXIAL LEAD CAPACITORS. POLYESTER. .01uf/100V..4p. 1/100..8p. 1/800..12p.  
POLYCARBONATE 4.7uf/100V..45p. VERT. MTG. 2.2uf/100V..40p. 1.5/100V..18p.  
20mm GLASS REED SWITCHES (GOLDPLATED) 10 for 50p. £28-00 per 1000.  
P & P add 50p per order. Post paid on orders over £5-00. ADD 15% V.A.T. Trade enquiries welcome. Schools etc. Send official order. Callers by appointment. Goods by return.

**C.H.J. SUPPLIES,**

4, STATION ROAD, CUFFLEY, HERTS. TEL: 01-440-8950

## NAMAL ELECTRONICS

No. 1 Claygate Road, Cambridge CB1 4JZ.

TEL: 0223 248257 Telex: 817445

2532	2732	2114	6116	4116
450 ns EPROMS	450 ns EPROMS	200 ns S/RAMS	160 ns CMOS RAM	300 ns D/RAM
£3-75	£4-10	£0-99	£5-75	£0-68

**NEW!**  
ALL PRICES SUBJECT TO  
VAT PLUS £1.00 P & P.

**INTRODUCTORY OFFER £30**  
16K Ram expansion board for ZX 81. Simply plugs into the existing expansion port of your computer to increase programme storage.

# SALE ELECTRONIC GAMES



**NOW £40 OFF**

**ATARI T.V. GAME**  
THE GAME WITH 50 CARTRIDGES  
R.R.P. £129.95 (inc. VAT)  
**OUR PRICE**  
**£78.22 + VAT**  
(= £89.95 inc. VAT)

The Atari is supplied with a free mains adaptor, a pair of paddles, a pair of joysticks and a combat cartridge and is the most popular television game on the market and has a range of over 40 different cartridges. In addition to the standard Atari range we also now stock the new Activision cartridges which are currently on special offer reduced from £18.95 to **£16.95 inc. VAT**

**ATARI CARTRIDGES**  
20% OFF R.R.P.  
Atari Soccer £29.95  
**NOW £23.95**  
Activision Dragster £18.95  
**NOW £14.95**  
Activision Boxing £18.95  
**NOW £14.95**

**ATARI OWNERS CLUB** — Why not join our **FREE Silica Atari Owners Club** and receive our bi-monthly newsletter with special offers and details of the latest new cartridge releases. Telephone us with your name and address and we will add your name to our computer mailing list.



**NOW £50 OFF**

**MATTEL INTELLIVISION**  
THE ULTIMATE T.V. GAME  
R.R.P. £229.95 (inc. VAT)  
**OUR PRICE**  
**£156.48 + VAT**  
(£179.95 inc. VAT)

6 NEW CARTRIDGES JUST RELEASED:  
ASTROSMASH \* SNAFU \* BOWLING  
SPACE ARMADA \* BOXING  
TRIPLE ACTION

All 19 current cartridges + the six new ones above now retail at £19.95 — Silica special offer price **£17.95 inc. VAT**

The Mattel Intellivision is the most advanced TV game in the world with a range of over 25 different cartridges all at our special offer price of £17.95. This game uses a 16-bit microprocessor giving 16 colours and three-part harmony sound. The picture quality is incredible with 3D effects and realistic animation. An add on keyboard will be available in the Spring 1982 to convert the Mattel into a full home computer with 16K RAM which will be fully expandable and programmable in Microsoft Basic. Other accessories will be added later in the year. The normal price of the Intellivision - free soccer cartridge is £229.95 but our special offer price is £179.95 inc. VAT saving you £50.00


**MATTEL OWNERS CLUB** — Why not join our Mattel Owners Club and receive our regular newsletters containing details of all the latest cartridge releases. Telephone us with your name and addresses and we will add your name to our computer mailing list.

**FREE 16 PAGE CARTRIDGE CATALOGUE** — If you are interested in owning a Mattel, we now have available a 16 page catalogue describing the latest six cartridges to be released, as well as a new Mattel colour leaflet with brief descriptions of all 25 cartridges. Telephone us for further details.
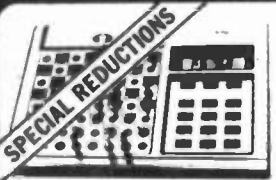
## T.V. GAME CARTRIDGES

We specialise in the whole range of T.V. games and sell cartridges for the following games: **ATARI \* MATTEL \* ACETRONIC \* PHILIPS \* DATABASE \* ROWTRON \* INTERTON \* TELEG**  
Let us know if you own any of these games and we will let you have details of the range of cartridges available.  
Attention **INTERTON & ACETRONIC** owners we have over 75 assorted used cartridges in stock all with 1 year guarantee — **SPECIAL OFFER £8.95 each**

We also have a number of secondhand games and cartridges.



**ELECTRONIC CHESS**  
Liquid crystal battery chess computer with 100-200 hrs. battery life and two levels of play. Comes with separate chess board and pieces.  
R.R.P. £24.95  
**NOW £19.95** (inc. VAT)

**GRADUATE CHESS**  
A de luxe version of the electronic chess set with integral chess board. The ideal portable chess set — see illustration.  
**NOW £29.95** (inc. VAT)

## FIDELITY MINI-SENSORY CHESS COMPUTER

The very first chess computer of its price to offer a portable computer with integral sensory board. Battery (6-8 hrs) or mains operated. This is a modular game and additional plug-in modules are planned for 1982 for advanced chess, popular openings, greatest master games, draughts and reversi.

**MINI-SENSORY COMPUTER WITH STANDARD CHESS MODULE** WAS £54.50 **NOW £49.95** (inc. VAT)

Silica Shop are one of the country's leading specialists in Chess Computers and now stock a range of more than 20 Chess Computers, including Challenger 7, 10, Voice, Sensory 8 and Sensory Voice, Diplomat, System 3, Morphy, Great Game Machines, Voice Champion, and the new Scizys Mark V.

**LESS THAN 1/2 PRICE**

**COLOUR CARTRIDGE T.V. GAME**  
Some Programmable T.V. game  
• 4 cartridges  
• mains transformer  
**NOW £63.90 OFF**  
R.R.P. £73  
**SALE PRICE £29.50** (inc. VAT)

**5000P NOW 1/2 PRICE**

**BACKGAMMON COMPUTER**  
Silica stock a wide range of Backgammon computers from £28.95 upwards. Special offers now available on Gammonmaster.  
Was £99.95  
**NOW £48.95** (inc. VAT)

## CALL JOTTER 2 — THE AFFORDABLE ANSWER

The Post Office certified telephone answering machine

"Sorry darling, I will be late home — Love John"

The Call Jotter 1 brings the affordable answer at the amazing price of £69 (or £99 for the Call Jotter 2 with built-in remote recall facilities). These amazing telephone answering machines are Post Office certified and guaranteed for one year. They make a thoughtful gift for home or business use.

**CALL JOTTER 2 ILLUSTRATED TAPE £139**  
**NOW £69.00** (inc. VAT)

## RADOFIN TELETEXT


**NOW £75 OFF**

Plug the adaptor into the aerial socket of your colour TV and receive the **CLEAR and ORACLE** television information services.

**THIS NEW MODEL INCORPORATES**  
• Double height character fonts  
• True PAL Colour  
• Memory Search REC & IBA broadcast specifications  
• Push button channel change  
• Memory channels  
• Remove the unit to easily connect to other programmes  
• Gold plated unit board for reliability

**ADD-ON ADAPTOR**  
Was £199 inc. VAT  
**SALE PRICE £124** (inc. VAT)

# FOR FREE BROCHURES — TEL: 01-301 1111

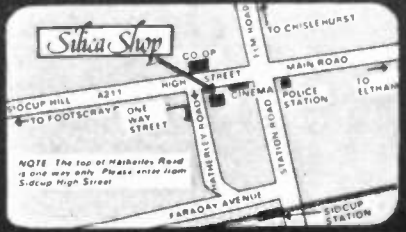

For free illustrated brochures and reviews on our range of electronic games, please telephone 01 301 1111. Free delivery service available. To order by telephone please quote your name, address and ACCESS CARD/ACCOUNT number, and leave the rest to us. Post and packing free of charge. Express 48 hour delivery service available.

**CALLERS WELCOME** — Demonstrations daily at our Sidcup shop open from 9am-6pm. Monday-Saturday 10am-Closing Thursday 10pm — Late Opening Friday 10pm.

**2 YEAR GUARANTEE** — All goods are covered by a full year's guarantee and many are further covered by our exclusive Silica 2 year Guarantee.

**MONEY BACK UNDERTAKING** — If you are unsatisfied with your purchase and return it within 7 days we will give you a full refund.

**AFTER SALES SERVICE** — Available on all machines out of guarantee.

**COMPETITIVE PRICES** — We are never knowingly under-sold.


**HELPFUL ADVICE** — Available on the suitability of each machine.

**CREDIT FACILITIES** — Full credit facilities available over 12, 24 or 36 months at competitive rates of interest.

**PART EXCHANGE SCHEME** — Available on second hand machines.

**CREDIT CARDS WELCOME** — Access: Barclaycard, Diners Club, American Express.

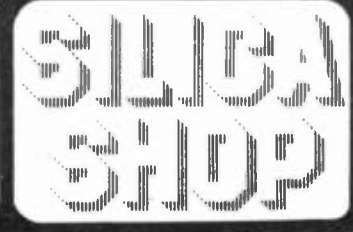**SILICA SHOP LIMITED** Dept. EE 0382  
1-4 The Mews, Hatherley Road, Sidcup, Kent DA14 4DX  
Telephone: 01-301 1111 or 01-309 1111



# ELECTRONI-KIT

## Introducing our new CHIP SHOP KITS

Each **CHIP SHOP KIT** is complete in every way and contains all the components necessary to build and operate the project described. All you need is a Soldering Iron (see Kit No. 2) and a 9v battery. Each kit includes step-by-step instructions on construction and detailed educational notes about the individual circuit, together with advice about soldering techniques.

**Kit No. 2—SOLDERING IRON**—contains a high quality British soldering iron, a 1 Amp fuse and solder together with straightforward instructions upon how to handle your soldering iron and the best techniques for its use and maintenance.

**Kit No. 3—ELECTRONICS TOOLS**—contains a selection of useful tools for anyone starting in electronics, together with instructions about the use and care of your equipment.

**SOLDER** is included with every kit.

Kit No.		Price
1(a)	Morning Call plus	£5.50
1(b)	Transistor Tester	
5	Soldering Iron	£5.50
3	Electronics Tools	£5.00
4	Electronic Organ	£4.00
5	Morse Code Trainer and Siren Oscillator	£4.50
6	Light Operated Burglar Alarm	£4.50
7	Buzzer—Aircraft	£3.50
8	Light and Sound Alarm	£3.50
9	Lie Detector	£3.50
10(a)	Lamp Flasher plus	£5.00
10(b)	Sleep Inducer	
11(a)	Cat Sound plus	£5.00
11(b)	Night Light Reminder	
12(a)	Bicycle Horn plus	£5.50
12(b)	Electronic Shocker	
13(a)	Light Sensitive Alarm plus	£5.50
13(b)	Electronic Lamp	
14	2-Transistor Radio	£4.50
15	Morning Alarm	£4.50
16	American Police Siren	£4.50
17	Flashing Dual-tone Horn	£4.00
18	Two-Way Interphone	£5.50
19	4-Transistor Radio	£5.50
20	Clicker—Helicopter Oscillator	£3.50

All kits packed individually in attractive boxes. Loudspeakers are included with each kit (except nos. 2, 3, 14 where they are not required).

Kit nos. 1, 10, 11, 12, 13 contain two separate projects.

These kits are becoming available in Hobby and Electronics Stores all over the Country—look out for the **CHIP SHOP DISPLAY** in your local store.

If you cannot locate a stockist please order direct from Electroni-Kit Ltd. Please add 50p per kit for postage and packing.

Trade and Educational Enquiries welcomed. Cheque/P.O./Access/Barclaycard (or 23p for full-colour illustrated literature) to **DEPT. EECS.**

**ELECTRONI-KIT LTD.**  
**RECTORY COURT, CHALVINGTON,**  
**E.SUSSEX, BN27 3TD (032 183 579)**

FROM A NEW COMPANY WITH NEW  
IDEAS

## SOMETHING SPECIAL

AIRWAVES ELECTRONICS INVITE YOU TO OPEN YOUR OWN PERSONAL ACCOUNT.

THERE COULDN'T BE AN EASIER WAY TO BUY COMPONENTS, ONCE YOU HAVE OPENED YOUR ACCOUNT, JUST PHONE OR WRITE YOUR ORDER THROUGH, STATING YOUR ACCOUNT NUMBER TOGETHER WITH YOUR OWN SECURITY CODE NUMBER AND GOODS WILL BE DESPATCHED SAME DAY AND YOUR ACCOUNT DEBITED WITH THE COSTS.

MAYBE, YOUR THINKING—YOU'LL HAVE TO PAY OVER THE ODDS FOR THIS, BUT YOU WILL BE WRONG, ACCOUNT CUSTOMERS WILL RECEIVE OUR PRODUCT PACKED CATALOGUE SHOWING VAT INCLUSIVE PRICES, WHICH WE BELIEVE TO BE VERY COMPETITIVE. AFTER ALL YOU'RE THE BEST JUDGE AND WE DO OFFER SOMETHING SPECIAL.

IF YOU WOULD LIKE TO OPEN YOUR ACCOUNT, THEN PLEASE CONTACT US FOR APPLICATION DETAILS ENCLOSING JUST A STAMP TO COVER POSTAGE.

CALL AND SEE US AT OUR RETAIL SHOP.

BATTERIES  
BOXES  
BOARDS  
CAPACITORS  
RESISTORS  
CONNECTORS  
CABLES  
COAX  
FLAT RIBBON  
POTS  
SWITCHES  
RELAYS  
CMOS  
TTL LS  
TTL  
MEMORIES  
SUPPORT  
CHIPS  
LINEAR  
OP AMPS  
COMPARATORS  
A-D D-A  
OPTO  
LEDS  
DISPLAYS  
LCD'S  
TRANSISTORS  
THYRISTORS  
TRIACS  
DIODES  
BRIDGES  
METERS  
ZENERS  
SOLDERING  
IRONS  
IC SOCKETS

## AIRWAVES ELECTRONICS

151 LONDON ROAD, CAMBERLEY, SURREY  
GU15 3JY. TEL. (0276) 62949

**It's easy  
to complain  
about  
advertisements.**

**The Advertising Standards Authority.** ✓  
**If an advertisement is wrong, we're here to put it right.**

A.S.A. Ltd, Brook House, Torrington Place, London WC1E 7HN.

# Vero has countless reasons to celebrate 20 years of Veroboard.

## That's how Vero began and many of you started.

Twenty years ago Vero introduced Veroboard to the designer and hobbyist market.

It was then unique in its concept and is still one of the basic boards for the electronics industry. Such is the influence that Veroboard has had, and is still having, that the very name has become part of general vocabulary. Twenty years is a long time in a new industry and Vero have been in the forefront with their standards, quality control and customer service throughout that time.

From Veroboard through Card Frames to Vero Cases, we are proud to be of service and hope that you will agree that sales of millions of Veroboards is a suitable cause to celebrate our twentieth birthday.

Please Telephone for further information about Veroboard and our other products.

Phone: Chandler's Ford

**(04215) 62829**



Vero Electronics Ltd., Retail Department,  
Industrial Estate, Chandler's Ford, Hampshire. SO5 3ZR.



# CLASSIFIED

The prepaid rate for classified advertisements is 28 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £7.24 per single column centimetre (minimum 2.5cm). All cheques, postal orders, etc., to be made payable to Everyday Electronics and crossed "Lloyds Bank Ltd." Treasury

notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Everyday Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London SE1 9LS. (Telephone 01-261 5942).

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## Receivers and Components

**300 SMALL COMPONENTS**, transistors, diodes. £1.70 7lbs assorted components £4.25 10lbs £5.75. Forty assorted 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p. Optionable insurance 20p. J. W. B. RADIO, 2 Barnfield Crescent, Sale, Cheshire M33 1NL.

**TURN YOUR SURPLUS** capacitors, transistors etc., into cash. Contact Coles Harding & Co., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

**NEW 1982 ACE COMPONENT CATALOGUE.** Let your problems be our business. Be certain; have your components delivered quickly and efficiently and get that project working. Send 30p now for the easy to use 1982 catalogue to: ACE MAILTRONIX, Dept EE, 3A Commercial Street, Batley, West Yorkshire WF17 5HJ.

## Courses

### SOUND ENGINEERS

If you're following a career in Sound Engineering or interested in learning all aspects of recording studios you should attend one of our weekend studio courses. Topics covered include:

- A. The basics of studio construction, wiring and materials used.
- B. Types of microphone uses, techniques, and limitations.
- C. Use of 2" 16 track machine, lining up, remotes, etc.
- D. Use of 24 Channel Desk and all controls.
- E. Effect equipment, ADT, reverb, Echo, etc.
- F. Ancilliary equipment.
- G. Mixing and Editing.

There are a maximum number of 8 students on each course and every one is tutored to their own level of knowledge with regard to their needs and interest. The cost is £98 for the weekend including hotel accommodation overnight. Details: please phone 01-580 4720 or 01-636 5308 during office hours.

## Service Sheets

**BELL'S TELEVISION SERVICE** for service sheets on Radio, TV etc. £1.25 plus SAE. Colour TV Service Manuals on request. SAE with enquiries to BTS, 190 King's Rd. Harrogate, N. Yorkshire. Tel: 0423 55885.

Any single service sheet £1/L.S.A.E. Thousands different Repair/Service Manuals/Sheets in stock. Repair data your named T.V. £6.50) with circuits £8.50). S.A.E. Newsletter, Price Lists. Quotations.

**AUSEL, 76 CHURCHES,  
LARKHALL, LANARKSHIRE  
(0698 883334).**

## Software

**SEVENTY ZX81 PROGRAMS.** Listings only £4.95, Barclaycard accepted. Includes many games, utility, machine code loader, home finance, maths, chequebook, etc. Includes hints 'n' tips. SUSSEX SOFTWARE, Wall-send House, Pevensey Bay, Sussex.

## Veteran & Vintage

### "SOUNDS VINTAGE"

The only magazine for all vintage sound enthusiasts, packed with articles by top writers, covering gramophones, phonographs, 78s, wireless, news, history, reviews, etc. Bi-monthly. Annual subscription £8.75 (airmail extra). Send 75p for sample copy. 28 Chestwood Close, Billericay, Essex

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Everyday Electronics for .....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Everyday Electronics)


NAME .....

ADDRESS .....

Send to: Classified Advertisement Manager

**EVERYDAY ELECTRONICS**  
Classified Advertisements Dept., Room 2612,  
King's Reach Tower, Stamford Street, London SE1 9LS  
Telephone 01-261 5942

Rate:  
28p per word, minimum 12 words. Box No. 60p extra.

Company registered in England. Registered No. 53886. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

3/82





# MIGHTY NINETY PACKS

**SUPER VALUE PACKS ALL AT 90p each  
BUY SIX PACKS AND GET A SEVENTH FREE**

Please add 15p per pack postage  
Please allow 7 days delivery.

- |   |  |
|---|--|
| MN2. 200 1/2 & 1-watt Resistors.  | MN37. 10 asstd audio connectors. Din phono etc.  |
| MN3. 100 1 & 2-watt Resistors.  | MN38. 1 PCB with triac control IC data inc.  |
| MN4. 50 Wirewound Resistors.  | MN39. 1 oscillator PCB loads of components (no data).  |
| MN5. 100 metal oxide Resistors. 1%, 2% and 5%.  | MN40. 50 Polystyrene capacitors.   |
| MN6. 12 asstd potentiometers.   | MN41. 12 BC549C (plastic BC109C) transistors.  |
| MN7. 25 asstd skeleton pre-set Resistors.   | MN42. 10BC107 Transistors.   |
| MN8. 50 asstd Electrolytic Capacitors.  | MN43. 10BC108 Transistors.   |
| MN9. 100 asstd Ceramic Capacitors Pile. disc. tub and monolithic etc.                       | MN44. 10 Screwfix S.P.C.O. min. slide switches.  |
| MN10. 100 mixed capacitors. Polyester, Polystyrene, Metallised, Radial and Axial types.     | MN45. 35 asstd diodes Zener, rect, signal, switch-ino.   |
| MN11. 20 asstd Silver Mica Capacitors.  | MN46. 15 asstd Zener diodes.   |
| MN12. 8 Tantalum Bead Capacitors (useful values).   | MN47. 3 x 68 mfd 16v tantalum bead capacitors.   |
| MN13. 20 asstd Transistors. BC, 2N Series + Power etc.                                      | MN48. 200 Items 4BA asstd length screws, nuts & washers.   |
| MN14. 40 IN4148 Diodes.   | MN49. 200 Items 6BA asstd length screws nuts & washers.  |
| MN16. 20 min. wire-ended Neons.   | MN50. 3 pieces of veroboard useful sizes, min total 35 sq inch.  |
| MN17. 2 12-volt Relays. Ex nearly new equip.  | MN51. 10 x 0 2" red LED.   |
| MN18. 3 Encapsulated Reed Relays 9-12v coil, d-pole and l-pole.                             | MN52. 10 x 0 125" red LED.   |
| MN19. 2 24-volt Relays. Ex nearly new equip.  | MN53. 20 x 0 1 mfd 25v ceramic disc caps.  |
| MN20. 1 240-110 to 12-volt, 100ma Transformer.  | MN54. 20 x 0 01 mfd 25v ceramic disc caps.   |
| MN21. 1 240-110 to 24-volt 100ma Transformer.   | MN55. 10 watt audio amp board with circuit.  |
| MN22. 8 2" Led's with clips, 4 red, 2 yellow, 2 green.                                      | MN56. 10 14 pin low profile IC ski DIL.  |
| MN23. 300 asstd screws, nuts, washers, self-tappers etc.                                    | MN57. 10 16 pin low profile IC ski DIL.  |
| MN24. 100 asstd small springs.  | MN58. 2 x CA723 Voltage Regulator.   |
| MN25. 50 asstd pop rivets.  | MN59. 1 x LM380 2 watt audio amp IC + 355 timer IC.  |
| MN26. 50 asstd insulated crimps.  | MN60. 10 asstd TTL IC's.   |
| MN27. 200 Items, grommets, spacers, cable markers, plastic screws, sleeving, tie wraps etc. | MN61. 3 x TIP 32 Transistor.   |
| MN28. 20 asstd fuses, 1" 20mm etc.  | MN62. 3 x TIP 31 Transistor.   |
| MN29. 75mts equipment, wire, asstd colours and sizes.                                       | MN63. 50 mixed polyester caps C280, Selmens etc.   |
| MN30. 3 x 2m length, 3 core, mains cable.   | MN64. 5 Press to make min switches.  |
| MN31. 12 asstd trimmer capacitors, compression film. Air-spaced etc.                        | MN65. 3 BF245 FETS.  |
| MN32. 15 30pF Beehive trimmers.   | MN66. Bank of 11 push switches 4 interlocked, 4 latch, 3 momentary.  |
| MN33. 20 coil formers, ceramic, plastic, reed relay etc.                                    | MN68. 200 asstd veropins, turret tags, PCB pins etc.   |
| MN34. 25 min glass reed switch.   | MN69. 4 min push to break switch.  |
| MN35. 10 asstd switches, toggle, slide, micro etc.  | MN70. PCB with 3 x 250v AC 4 amp push SW with attractive chrome plastic knobs 1 x BD241, 1 x BC200, 2 x BC237, 1 x BC204, 4 x IN4002, 2 x CMOS 4025, 200mm fuse holder + 22 resistors, capacitors, diodes etc. |
| MN36. 10 sub-min SP. C/D slide switch.  | MN71. IZNA14 RADIO IC.   |

## CHORDGATE LIMITED

75 FARINGDON ROAD  
SWINDON, WILTS. Tel. (0793) 33877  
Retail shop at above address

### BAKER 50 WATT AMPLIFIER

£69

Post #2



Superior quality ideal for Halls/PA systems. Disco's and Groups. Two inputs with Mixer Volume Controls. Master Bass, Treble and Gain Controls. 50 watts RMS. Three loudspeaker outlets 4, 8, 16 ohm.

AC 240V (120V available). Blue wording on black cabinet.  
**BAKER 150 Watt AMPLIFIER 4 Inputs £89**

**DRILL SPEED CONTROLLER LIGHT DIMMER KIT.** Easy to build kit. Controls up to 480 watts AC mains. Printed Circuit. £3

**DELUXE MODEL Ready Built. 800 watts. \$5**  
**STEREO PRE-AMP KIT.** All parts to build this pre-amp. 3 inputs for high, medium or low gain per channel, with volume control and P.C. Board. Can be ganged to make multi-way stereo mixers. £2-95

#### SOUND TO LIGHT CONTROL KIT MK II

Complete kit of parts, printed circuit. Mains transformer, 3 channels. Up to 1,000 watts each. Will operate from 200MV to 100 watts signal source. Suitable for home Hi-Fi. £15 and all Disco Amplifiers. Cabinet extra £4-50. Post 95p

**200 Watt Ready Selecting White Light Bulbs.** Ideal for Disco Lights. Edison Screw 75p each or 6 for £4 or 12 for £7-50.

#### MAIN TRANSFORMERS Primary 240V A.C. POST

250-0-250V 70ma. 6-5V 2A	£4-50	£2
250-0-250V 80ma. 6-3V 3-5A. 6-3V A1	£5-00	£2
350-0-350V 250ma. 6-3V 6amp C.T.	£12-00	£2
300-0-300V 120ma. 2 x 6-3V 2A C.T.; 5V 2A	£12-00	£2
220V 45ma. 6-3V 2A	£2-50	£1

#### GENERAL PURPOSE LOW VOLTAGE

Tapped outputs available		
2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V	£8-00	£2
1 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£8-00	£2
2 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10-50	£2
3 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18-50	£2
5 amp 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18-50	£2
5-8-10-16V 1a	£2-50	80p
6-12V 1a	£2-00	£1
6-0-6V 1a	£3-50	£1
9V 250ma	£1-50	80p
9V 3a	£3-50	£1
9-0-9V 50ma	£1-50	80p
10-0-10V 2a	£3-00	£1
10-30-40V 2a	£3-50	£1
12V 100ma	£1-50	80p
12V 750ma	£2-00	80p
12V 3a	£3-50	£1
12V 2a	£3-50	£1
17-0-17V 2a	£4-50	£2
35V 2a	£4-00	£1

#### TORODIAL 30-0-30V 4 Amp + 20-0-20V 1/2 Amp £10-00

#### CHARGER TRANSFORMERS-RECTIFIERS

6-12V 5a	£4-00	£1	00p
6-12V 4a	£3-50	£2	00p
6-12V 4a	£3-50	£2	00p

#### R.C.S. LOUSPEAKER BARGAINS

3 ohm. 6 x 4in. 5in., 7 x 4in. £2-50. 8 x 5in. £3-00.  
6in. £3-00. 8in. £3-50. 10in. £4-00. 12in. £6-00.  
6 ohm. 2 1/2in. £2-00. 3in. 5 x 2in., 6in. £3-50. 8in. £3-50.  
16 ohm. 6 x 4in. £1-50. 5in. £1-50. 8in. £3-50. 10 x 6in. £3-50.  
25 ohm. 3 1/2in. 35 ohm. 3in. £3-50. Many others in stock.

#### E.C.I. LOW VOLTAGE STABILISED

**POWER PACK KIT 90-100 mA** Post 75p  
All parts and instructions with Zener diode printed circuit, rectifiers and double wound mains transformer input 200-240 a.c. Output voltages available 6 or 7-5 or 9 or 12V d.c. up to 100mA. State voltage.

#### FP BATTERY ELIMINATOR. BRIFOR MADE £4.50

Mains power pack 9 volt 400 ma Post 75p  
stabilised, with overload cutout. Plastic case size 5 x 5 1/2 x 2 1/2. Suitable Radio/Cassettes.  
**DELUXE Switched Model 3-6-7V-9V 400ma. £7-50.**

#### THE "INSTANT" BULK TAPE ERASER

Suitable for cassettes and all sizes of tape reels.  
A.C. mains 200/240V. £9.50 Post 95p

#### HEAD DEMAGNETISER PROBE £5-00.

**A.C. ELECTRIC MOTORS POST 75p.**  
2 Pole, 240V, 2 Amp. Spindle—  
1-43 x 0-212in. £1-75. 2 Pole,  
240V, 15 Amp Double spindle—  
1-75 x 0-16in. Each £1-2 Pole,  
120V, .5 Amp Spindle—0-75 x  
0-2in. Two in series — 240V, 50p  
each. Brush Motor. From a Food  
Mixer 240V, .3 Amp High Speed  
and Powerful Spindle—0-5 x  
0-26in. £2-95.  
B.S.R. Motor £4. Garrard Motor £5.

#### ALUMINIUM CHASSIS 18 s.w.g. Un drilled, 4 sides, riveted

corners: 6 x 4 x 2 1/2in. £1-45; 8 x 6 x 2 1/2in. £1-80; 10 x 7 x 2 1/2in. £2-30; 14 x 8 x 2 1/2in. £3-00; 16 x 6 x 2 1/2in. £2-90; 12 x 3 x 2 1/2in. £1-80; 12 x 8 x 2 1/2in. £2-80; 16 x 10 x 2 1/2in. £3-20.  
**ALL ANGLE BRACKETS 6 x 1 x 1/2in. 25p.**  
**ALUMINIUM PANELS 18 s.w.g. 12 x 12in. £1-50; 14 x 9in. £1-45; 6 x 4in. 45p; 12 x 8in. £1-10; 10 x 7in. 90p; 8 x 6in. 72p; 14 x 3in. 72p; 12 x 6in. 72p; 16 x 10in. £1-68; 16 x 6in. £1-10; 4 x 2 1/2 x 2in. £1-00; 3 x 2 x 1in. 80p; 6 x 4 x 2in. £1-60; 8 x 6 x 2in. £2-60; 12 x 6 x 2in. £3-75; 6 x 4 x 2in. £1-80; 10 x 7 x 2in. £3.**

#### HIGH VOLTAGE ELECTROLYTICS 32+32/350V

6/800V. £1-30 50/500V. £1-30 32+32/500V. £1-30  
32/350V. £1-45 220/450V. £1-80 32+32+32/352V 75p  
32/500V. 75p 8+16/450V. 75p 16+32+32/500V £3

#### DE LUXE BSR HI-FI AUTOCHANGER

Stereo Ceramic Cartridge  
Plays 12in., 10in., or 7in.  
reels. Auto or Manual. A high  
quality unit 240V A.C.  
Size 13 1/2 x 11 1/2in.  
Above motor board 3 1/2in.  
Below motor board 2 1/2in.

BSR Single Player P207 cusing device, £20 post £2

ADC. QEM 30/3 Magnetic cartridge.

Garrard Single Player 730 SP metal turntable, £27.50 post £2

cusing device. Snake arm. Magnetic cartridge.

BSR P170 8 1/2in arm. Metal turntable. £20 post £2

Ceramic head. Cusing device. Auto stop.

B.S.R. P232. Belt drive, ceramic cartridge, snake arm. cusing device. £24 post £2.

B.S.R. Single Player. 12V D.C. motor, belt drive, magnetic cartridge. £26, post £2.

#### Radio Component Specialists

337, WHITEHORSE ROAD, CROYDON, SURREY, U.K. TEL: 01-884 1665  
Post 65p Minimum. Callers Welcome. Closed Wed. Same day despatch. Access-Barclay-Visa. Lists 25p.

# INDEX TO ADVERTISERS

Ambit .. .. .	204
Absonglen .. .. .	208
Airwaves .. .. .	212
Alcon .. .. .	210
Bib Audio .. .. .	209
Bi-Pak .. .. .	150-151
BK Electronics .. .. .	Cover iii
B.N.R.E.S. .. .. .	187
Bull J. .. .. .	205
Cambridge Learning .. .. .	150
Carlton Nicholl .. .. .	148
CHJ Supplies .. .. .	210
Chordgate .. .. .	216
Cricklewood Electronics .. .. .	148
Dzibus M. .. .. .	204
E.D.A. .. .. .	154
Electroni-Kit .. .. .	212
Electronice Design .. .. .	Cover ii
Electrovalue .. .. .	206
Global Specialist .. .. .	199
Greenweld .. .. .	148
Heath-Kit .. .. .	152
Home Radio .. .. .	206
Intertext (ICS) .. .. .	208
Litesold .. .. .	206
Magenta Electronics .. .. .	152, 153
Maplin Electronic Supplies Ltd. .. .. .	Cover iv
Namel Electronics .. .. .	210
Phonsonics .. .. .	146
Powell T. .. .. .	208
Radio Component Specialists .. .. .	216
Radio TV Components .. .. .	197
Rapid Electronics .. .. .	149
Science of Cambridge .. .. .	202-203
Selray Book .. .. .	206
Silica Shop .. .. .	211
Tempus .. .. .	207
Titan Transformers .. .. .	210
T.K. Electronics .. .. .	146
Vero Electronics .. .. .	213
Watford Electronics .. .. .	147
Wilmslow Audio .. .. .	146




APPROVED  
**thandar**  
STOCKIST

# B.K. ELECTRONICS
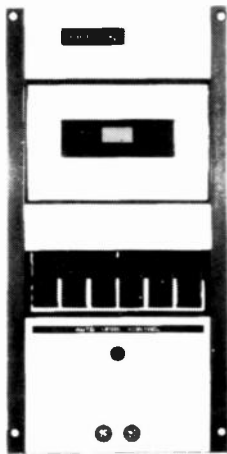
## A SOUND CHOICE

APPROVED  
**thandar**  
STOCKIST

★ PROMPT DELIVERY ★ PRICES INCLUDE V.A.T. ★ AMPLE STOCKS  
A PERSONAL SERVICE FROM A SMALL EXPANDING COMPANY



6 piano type keys

### STEREO CASSETTE TAPE DECK MODULE.

Comprising of a top panel and tape mechanism coupled to a record/play back printed board assembly. Supplied as one complete unit for horizontal installation into cabinet or console of own choice. These units are brand new, ready built and tested.

**Features:** Three digit tape counter. Auto-stop. Six piano type keys, record, rewind, fast forward, play, stop and eject. Automatic record level control. Main inputs plus secondary inputs for stereo microphones. **Input Sensitivity:** 100mV to 2V **Input Impedance:** 68K. **Output level:** 400mV to both left and right hand channels **Output Impedance:** 10K. **Signal to noise ratio:** 45dB **Wow and flutter:** 0.1%. **Power Supply requirements:** 18V DC at 300mA. **Connections:** The left and right hand stereo inputs and outputs are via individual screened leads, all terminated with phono plugs (phono sockets provided). **Dimensions:** Top panel 5 1/2" x 11 1/4". Clearance required under top panel 2 1/4". Supplied complete with circuit diagram and connecting diagram. Attractive black and silver finish.

**Price £26.70 + £2.50 postage and packing**  
Supplementary parts for 18V D.C power supply (transformer, bridge rectifier and smoothing capacitor) £3.



### 1 K-WATT SLIDE DIMMER

- ★ Controls loads up to 1KW.
  - ★ Compact Size 4 1/2" x 1 1/2" x 2 1/2".
  - ★ Easy snap in fixing through panel/cabinet cut out.
  - ★ Insulated plastic case.
  - ★ Full wave control using 8 amp triac.
  - ★ Conforms to BS800.
  - ★ Suitable for both resistance and inductive loads. Innumerable applications in industry, the home, and disco's/theatres, etc.
- Price £11.70 each + 50p P&P. (Any quantity.)**

### GENERAL PURPOSE 4 1/2" MINI SPEAKER

General purpose full range loudspeaker, ideal for mini systems, etc.

- ★ Rolled fabric surround
  - ★ Twin cone
  - ★ 8 ohm impedance
  - ★ 15 watt R.M.S.
  - ★ 1" voice coil
  - ★ 13 oz. magnet
  - ★ Frequency range 50/15,000Hz.
- Price £6.90 each + 75p P&P.**



**NEW RANGE QUALITY POWER LOUD-SPEAKERS (15", 12" and 8").** These loudspeakers are ideal for both hi-fi and disco applications. Both the 12" and 15" units have heavy duty die-cast chassis and aluminium centre domes. All three units have white speaker cones and are fitted with attractive cast aluminium (ground finish) fixing escutcheons. **Specification and Price:-**

**15" 100 watt R.M.S.** Impedance 8ohm 59 oz magnet, 2" aluminium voice coil. Resonant Frequency 20Hz. Frequency Response to 2.5KHz. Sensitivity 97dB **Price £32 each.** £2.50 Packing and Carriage each

**12" 100 watt R.M.S.** Impedance 8 ohm, 50 oz magnet 2" aluminium voice coil Resonant Frequency 25Hz. Frequency Response to 4KHz Sensitivity 95dB **Price £23.70 each.** £2.50 Packing and Carriage each.

**8" 50 watt R.M.S.** Impedance 8 ohm, 20 oz magnet 1" aluminium voice coil Resonant Frequency 40Hz. Frequency Response to 6KHz Sensitivity 92dB Also available with black cone and black protective grill **Price £8.90 each.** £1.25 Packing and Carriage each

### PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution. The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if 2 put in series). **FREE EXPLANATORY LEAFLETS SUPPLIED WITH EACH TWEETER.**


**Type 'A'** 3in round with removable wire mesh. Ideal for bookshelf hi-fi speakers. **Price (Type 'A') £3.45 each.**

**Type 'B'** 3 1/2in super horn. For general purpose speakers disco and PA systems, etc. **Price £4.35 each.**


**Type 'C'** 2in x 5in wide dispersion horn. For hi-fi systems and quality disco etc. **Price £5.45 each.**

**Type 'D'** 2in x 6in wide dispersion horn. Frequency response extending down to mid-range (2000 c/s) suitable for hi-fi systems and quality disco **Price £6.90 each.** Post and Packing, all types, 15p each (or SAE for Piezo leaflets).

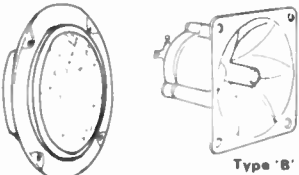**Piezo Level Control Loudspeaker Terminals.** Combines two spring loaded loudspeaker terminals wire wound potentiometer and resistor network. All mounted on a smart brushed aluminium plate. Fits neatly through a 3 x 3 cut out on rear of speaker cabinet **Price £2.99 + 20p postage and packing**




Type 'A'

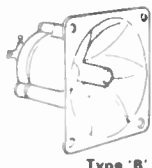


Type 'B'



Type 'C'

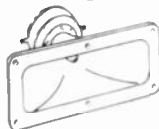

Type 'D'

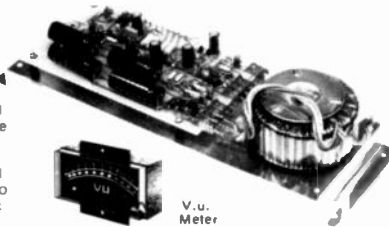

V.u. Meter

### Matching 3-way loudspeakers and crossover

Build a quality 60 watt R.M.S. system 8 ohm.

- ★ 10" Woofer
- ★ 3" Tweeter
- ★ 5" Mid Range
- ★ 3-way crossover

Fitted with attractive cast aluminium fixing es cutcheons and mesh protective grills, which are removable enabling a unique choice of cabinet styling. Can be mounted directly on to baffle with or without conventional speaker fabrics. All three units have aluminium centre domes and rolled foam surround. Crossover combines spring loaded loudspeaker terminals and recessed mounting panel.

**Price £22.00 per kit + £2.50 P&P.** Available separately, prices on request.

### 12" 80 watt R.M.S. loudspeaker.



A superb general purpose twin cone loud speaker 50 oz magnet 2" aluminium voice coil. Rolled surround Resonant frequency 25Hz. Frequency response to 13KHz. Sensitivity 95dB. Impedance 8ohm. Attractive blue cone with aluminium centre dome.

**Price £17.49 ea - £2.50 P&P.**
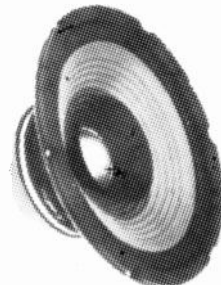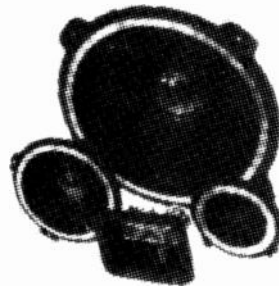
### OMP POWER AMPLIFIER MODULES

100 and 150 WATTS R.M.S. Power Amplifier Modules with integral toroidal transformer power supply and heat sink. Supplied as one complete built and tested unit. Can be fitted in minutes. Auxiliary stabilised supply and drive circuit incorporated to power an L.E.D. V.u. meter available as an optional extra.

**SPECIFICATION:**  
Max. output power 100 watts R.M.S. (OMP 100)  
150 watts R.M.S. (OMP 150)  
Loads: (Open and short circuit proof) 4-16 ohms  
Frequency Response: 20Hz-25KHz ± 3dB  
Sensitivity: for 100 watts 500mV at 10K  
150 watts 500mV at 10K  
T.H.O. 00 1%  
Size: 360 x 115 x 80mm  
Prices: OMP 100 £29.99 P & P £2.00  
OMP 250 £39.99 P & P £2.00  
V.u. Meter £6.50



# B.K. ELECTRONICS

DEPT E.E.

37 Whitehouse Meadows, Eastwood, Leigh-on-Sea, Essex SS9 5TY

★ SAE for current lists. ★ Official orders welcome. ★ All prices include VAT. ★ Mail order only. ★ All items packed (where applicable) in special energy absorbing PU foam. Callers welcome by prior appointment, please phone 0702-527572.



198

# MAPLIN the people for Atari



## 3 Consoles available:


**Atari 400 with 16K RAM (AF36P) £345**

**Atari 400 with 32K RAM (AF37S) £395**

**Atari 800 with 16K RAM (AF02C) £645**

### Lots of other hardware:

Cassette Recorder (AF28F)	£50.00	16K RAM Module (AF08J)	£64.00
Disk Drive (AF06G)	£345.00	32K RAM Module (AF44X)	£125.35
Thermal Printer (AF04E)	£265.00	32K Upgrade for 400 (AF45Y)	£75.00
Printer Interface for 400 (AF41U)	£49.95	Floppy Disk (YX87U)	£2.75
Printer Interface for 800 (AF42V)	£49.95	Le Stick (AC45Y)	£24.95
Interface Module (AF29G)	£135.00	Joystick Controllers (AC37S)	£13.95
Versawriter (AF43W)	£169.00	For full details ask for our hardware leaflet (XH54J) SAE appreciated	

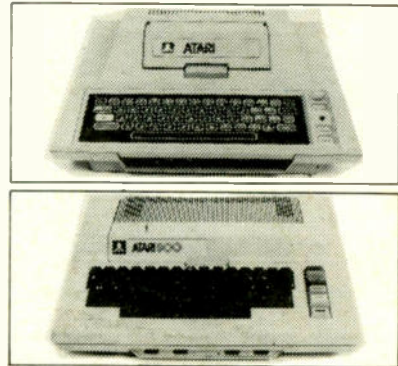

**NOW YOU CAN JOIN THE U.K. ATARI COMPUTER OWNER'S CLUB.** An independent user's group. Four issues of the club magazine for only £1.60! Address your subscription to Graham.

## THE CHOICEST GEMS OF ATARI SOFTWARE FROM MAPLIN

### Adventure Games

Star Warrior	-C-32K-(B024B)	£28.95
Rescue At Rigel	-C-32K-(B021X)	£22.45
Invasion Orion	-C-32K-(B023A)	£18.95
Dalestones of Ryn	-C-32K-(B022Y)	£14.95
Galactic Empire	-C-24K-(B014Q)	£14.95
Hi-Res Adventure // 2	-D-48K-(B025C)	£24.95
Analog Adventure	-D-32K-(B033L)	£24.95
Adventure Land	-C-24K-(B000A)	£14.95
Pirates Adventure	-C-24K-(B001B)	£14.95
Mission Impossible	-C-24K-(B002C)	£14.95
Voodoo Castle	-C-24K-(B003D)	£14.95
The Count	-C-24K-(B004E)	£14.95
Strange Odyssey	-C-24K-(B005F)	£14.95
Mystery Fun House	-C-24K-(B006G)	£14.95
Pyramid of Doom	-C-24K-(B007H)	£14.95
Ghost Town	-C-24K-(B008J)	£14.95
Savage Island I	-C-24K-(B009K)	£14.95
Savage Island II	-C-24K-(B010L)	£14.95
Golden Voyage	-C-24K-(B011M)	£14.95
Energy Czar	-C-16K-(YG53H)	£8.95
Kingdom	-C-8K-(YG55K)	£8.95

### Teach-Yourself Programs

Conversational French	-5C-16K-(YG44X)	£32.50
Conversational German	-5C-16K-(YG45Y)	£32.50
Conversational Spanish	-5C-16K-(YG46A)	£32.50
Conversational Italian	-5C-16K-(YG47B)	£32.50
Touch Typing	-2C-16K-(YG49D)	£14.95
States & Capitals	-C-24K-(YG56L)	£8.95
European Countries & Capitals	-C-16K-(YG57M)	£8.95

### Learn Programming

Initiation to Programming	-C-8K-(YG43W)	£11.95
Basics of Animation	-C-32K-(B057M)	£9.95
Basics of Animation	-D-32K-(B058N)	£10.95
Player Missile Graphics	-C-16K-(B059P)	£18.95
Player Missile Graphics	-D-24K-(B060Q)	£19.95
Display Lists	-C-16K-(B051F)	£9.95
Display Lists	-D-24K-(B052G)	£10.95
Horiz/Vertical Scroll	-C-16K-(B053H)	£9.95
Horiz/Vertical Scroll	-D-24K-(B054J)	£10.95

Page Flipping	-C-16K-(B055K)	£9.95
Page Flipping	-D-24K-(B056L)	£10.95
Master Memory Map	-Wallchart-(XH57M)	£4.00

### Business Programs

Visicalc	-D-32K-(YL39N)	£119.95
Word Processor	-D-32K-(YG42V)	£85.00
Calculator	-D-24K-(YG50E)	£16.95
Graph-1+1	-C-16K-(YG51F)	£11.95
Statistics	-C-16K-(YG52G)	£11.95

### Arcade Games

Star Raiders	-E-8K-(YG66W)	£29.95
Asteroids	-E-8K-(YG60O)	£29.95
Space Invaders	-E-8K-(YG70M)	£24.50
Missile Command	-E-8K-(YG64U)	£29.95
Super Breakout	-E-8K-(YG67X)	£29.95
Tari Trek	-C-24K-(YL36P)	£8.95
Tari Trek	-D-32K-(YL37S)	£11.95
Star Trek 3 5	-C-32K-(B015P)	£14.95
Race In Space	-C-16K-(B035D)	£14.95
Shooting Gallery	-C-16K-(B036P)	£14.95
Mountain Shoot	-C-16K-(B012N)	£10.95
Jawbreaker	-D-48K-(B026D)	£22.95
Basketball	-E-8K-(YG61R)	£29.95
Tank Trap	-C-16K-(YL34M)	£8.95
Tank Trap	-D-32K-(YL35O)	£11.95

### Home Game Programs

Scram	-C-16/24K-(YG58N)	£12.95
Cypher Bowl	-C-32K-(B020W)	£22.45
Thunder Island	-C-16K-(B037S)	£10.95
Rotating Tilt	-C-16K-(B048C)	£14.95
Lunar Lander	-C-16K-(B016S)	£10.95
Jumbo Jet Lander	-C-16K-(B046A)	£29.95
Submarine Commander	-C-16K-(B047B)	£24.50
Sunday Golf	-C-16K-(B013P)	£10.95
Darts	-C-16K-(B042V)	£19.95
Tournament Pool	-C-16K-(B045Y)	£19.95
Snooker & Billiards	-C-16K-(B044X)	£19.95
Chess	-E-8K-(YG63T)	£29.95
Microchess	-C-16K-(YL40T)	£15.95
Checker King	-C-16K-(YL41U)	£15.95
Cribbage & Dominoes	-C-16K-(B043W)	£14.95

Poker Solitaire	-C-16K-(B017T)	£10.95
Blackjack	-C-8K-(YG62S)	£8.95
Fast Gammon	-C-8K-(YL33L)	£9.95
Reversi (Dinello-type)	-C-16K-(B019V)	£14.95
Gomoko	-C-16K-(B018U)	£14.95
Hangman	-C-8K-(YG54J)	£8.95
Humpty Dumpty & Jack & Jill	-C-16K-(B038R)	£19.95
Hickory Dickyory Dock	-C-16K-(B039N)	£19.95
British Heritage	-C-16K-(B040T)	£19.95
Jig Saw Puzzles	-C-16K-(B041U)	£19.95
European Scene	-C-16K-(B049D)	£18.95
Jig Saw Puzzles	-D-16K-(B050E)	£24.95
Atari Safari (25 Programs)	-C-16K-(YL38R)	£8.95
Atari Safari (25 Programs)	-D-16K-(B050E)	£24.95
Atari Safari (25 Programs)	-C-16K-(YL38R)	£8.95

### Music Programs

Music Composer	-E-8K-(YG48C)	£32.50
Movie Themes (use with Music Composer)	-C-16K-(B034M)	£9.95

### Computer Languages

Basic A +	-D-48K-(B031J)	£52.50
Operating System A +	-D-48K-(B030H)	£52.50
Basic A + &	-D-48K-(B032K)	£99.50
Operating System A +	-D-24K-(YL29G)	£44.90
OS Forth	-D-24K-(YL29G)	£44.90
Pilot	-E&2C-8K-(YG69A)	£49.50

### Utilities

3D-Super Graphics	-D-48K-(B028F)	£29.95
3D-Super Graphics	-C-48K-(B029G)	£29.95
Atari World (Graphics)	-D-48K-(B027E)	£43.95
Assembler Editor	-E-8K-(YG68Y)	£34.50
Assembler	-C-16K-(YL32K)	£14.95
6502 Disassembler	-C-8K-(YL30H)	£8.95
6502 Disassembler	-D-8K-(YL31J)	£11.95
Character Generator	-C-16K-(YL27E)	£9.97
Character Generator	-D-16K-(YL28F)	£12.50
Teletink	-E-8K-(YG59P)	£14.95

Key C = Cassette, D = Disk E = Cartridge  
2C = 2 Cassettes etc 8K, 16K etc shows minimum memory requirement

Send sae now for our new software leaflet with details of all the above programs. Order As XH52G — Issue 2. Lots of exciting new software titles available soon. Keep in touch with Maplin!

Subscribe now to America's leading Atari-only magazine — Analog — 6 issues per year for just £9.00. Order as GG24B.



Maplin Electronic Supplies Ltd  
P.O. Box 3, Rayleigh, Essex.  
Tel: Southend (0702)  
552911/554155.

Demonstrations at our shops NOW  
See the amazing Atari's in action at  
159-161 King St., Hammersmith W6  
Tel: 01-748 0926  
or at 284 London Road,  
Westcliff-on-Sea, Essex.  
Tel: (0702) 554000

Note: Order codes shown in brackets Prices firm until 15th May, 1982 and include VAT and Postage and Packing (Errors excluded)