

**EVERYDAY**

AUGUST 1992

# **ELECTRONICS**

INCORPORATING ELECTRONICS MONTHLY

£1.60

**FREE**

**MARCO TRADING**

**32-PAGE SUMMER SALE CATALOGUE**

**NEW SERIES**

**ALTERNATIVE ENERGY**

**Developments using renewable energy sources**

**SOLAR POWERED LIGHTING UNIT**

**GAS ALARM**

**SUB WOOFER**



**THE No. 1 INDEPENDENT MAGAZINE for ELECTRONICS, TECHNOLOGY and COMPUTER PROJECTS**





# EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY



ABC  
A Division of Consumer Press

VOL. 21 No. 8 AUGUST 1992

The No. 1 Independent Magazine for Electronics,  
Technology and Computer Projects

ISSN 0262 3617

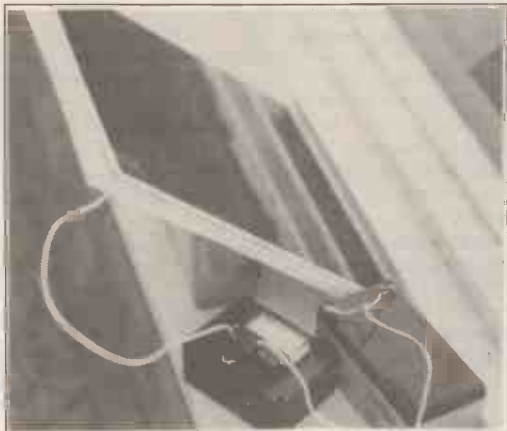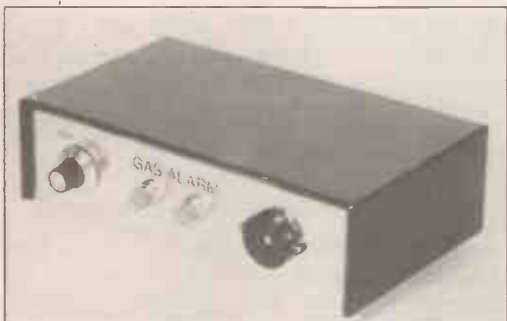PROJECTS... THEORY... NEWS...  
COMMENT... POPULAR FEATURES...



© Wimborne Publishing Ltd 1992. Copyright in all drawings, photographs and articles published in EVERYDAY ELECTRONICS is fully protected, and reproduction or imitations in whole or in part are expressly forbidden.

Our September '92 Issue will be published on Friday, 7 August 1992. See page 475 for details.

Everyday Electronics, August 1992

## Projects

- GAS ALARM** by Robert Penfold 484  
Detects gas, flammable vapours and smoke
- DUAL METRONOME** by R. M. Worthington 492  
A conventional metronome plus a "tap in" beat setter
- SOLAR POWERED LIGHTING UNIT** 510  
by T. R. de Vaux Balbirnie  
"Free" lighting for your caravan, boat, shed etc
- SUB-WOOFER** by Paul Henderson 522  
Add some real bass to your hifi setup
- ARTWORK LIGHT BOX** by Alan Winstanley 532  
Ease the production of your own p.c.b.s with this simple unit

## Series

- CIRCUIT SURGERY** by Mike Tooley 488  
Our clinic for constructors - your problems solved
- ACTUALLY DOING IT** by Robert Penfold 500  
Semiconductor leadout identification
- ALTERNATIVE ENERGY - 1** 504  
by T. R. de Vaux Balbirnie  
The use of renewable energy sources
- INFORMATION TECHNOLOGY AND THE NATIONAL CURRICULUM** by T. R. de Vaux-Balbirnie 516  
Part Ten: Computer Monitoring and Communications Systems
- INTERFACE** by Robert Penfold 528  
Bar Code Generation
- AMATEUR RADIO** by Tony Smith G4FAI 540  
Classes Re-Start; VHF Propagation; Tropo; Sporadic E; Aurora; Warm Shack in Russia

## Features

- EDITORIAL** 483
- EVERYDAY READOUT** 490  
From you to us - your news and views
- INSIDE THE MINI DISC** by Ian Graham 498  
We examine the next generation hifi medium
- SHOPTALK** with David Barrington 501  
Component buying for EE projects
- FOR YOUR ENTERTAINMENT** by Barry Fox 502  
Shock-Horror; On The Map; Sinister Aims; CDTV Disaster; Caddy Puzzle
- ELECTRONICS VIDEOS** 509  
Learn about your favourite subject with these videos
- EVERYDAY NEWS** 514  
News from the world of electronics
- DIRECT BOOK SERVICE** 535  
Selected technical books, EE books and all Babani books by mail order
- PRINTED CIRCUIT BOARD SERVICE** 538  
A special PCB SALE (while stocks last) - boards for EE projects
- ADVERTISER'S INDEX** 544

Readers Services • Editorial and Advertisement Departments 483



# SURVEILLANCE PROFESSIONAL QUALITY KITS

## No. 1 for Kits

Whether your requirement for surveillance equipment is amateur, professional or you are just fascinated by this unique area of electronics SUMA DESIGNS has a kit to fit the bill. We have been designing electronic surveillance equipment for over 12 years and you can be sure that all of our kits are very well tried, tested and proven and come complete with full instructions, circuit diagrams, assembly details and all high quality components including fibreglass PCB. Unless otherwise stated all transmitters are tuneable and can be received on an ordinary VHF FM radio.

### UTX Ultra-miniature Room Transmitter

Smallest room transmitter kit in the world! Incredible 10mm x 20mm including mic. 3-12V operation. 500m range.....£16.45

### MTX Micro-miniature Room Transmitter

Best-selling micro-miniature Room Transmitter  
Just 17mm x 17mm including mic. 3-12V operation. 1000m range.....£13.45

### STX High-performance Room Transmitter

Hi performance transmitter with a buffered output stage for greater stability and range. Measures 22mm x 22mm including mic. 6-12V operation, 1500m range.....£15.45

### VT500 High-power Room Transmitter

Powerful 250mW output providing excellent range and performance. Size 20mm x 40mm. 9-12V operation. 3000m range.....£16.45

### VXT Voice Activated Transmitter

Triggers only when sounds are detected. Very low standby current. Variable sensitivity and delay with LED indicator. Size 20mm x 67mm. 9V operation. 1000m range..£19.45

### HVX400 Mains Powered Room Transmitter

Connects directly to 240V AC supply for long-term monitoring. Size 30mm x 35mm. 500m range.....£19.45

### SCRX Subcarrier Scrambled Room Transmitter

Scrambled output from this transmitter cannot be monitored without the SCDM decoder connected to the receiver. Size 20mm x 67mm. 9V operation. 1000m range.....£22.95

### SCSX Subcarrier Telephone Transmitter

Connects to telephone line anywhere, requires no batteries. Output scrambled so requires SCDM connected to receiver. Size 32mm x 37mm. 1000m range.....£23.95

### SCDM Subcarrier Decoder Unit for SCRX

Connects to receiver earphone socket and provides decoded audio output to headphones. Size 32mm x 70mm. 9-12V operation.....£22.95

### ATR2 Micro Size Telephone Recording Interface

Connects between telephone line (anywhere) and cassette recorder. Switches tape automatically as phone is used. All conversations recorded. Size 16mm x 32mm. Powered from line.....£13.45

### UTLX Ultra-miniature Telephone Transmitter

Smallest telephone transmitter kit available. Incredible size of 10mm x 20mm! Connects to line (anywhere) and switches on and off with phone use.

All conversation transmitted. Powered from line. 500m range.....£15.95

### TLX700 Micro-miniature Telephone Transmitter

Best-selling telephone transmitter. Being 20mm x 20mm it is easier to assemble than UTLX. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. 1000m range.....£13.45

### STLX High-performance Telephone Transmitter

High performance transmitter with buffered output stage providing excellent stability and performance. Connects to line (anywhere) and switches on and off with phone use. All conversations transmitted. Powered from line. Size 22mm x 22mm.

1500m range.....£16.45

### TKX900 Signalling/Tracking Transmitter

Transmits a continuous stream of audio pulses with variable tone and rate. Ideal for signalling or tracking purposes. High power output giving range up to 3000m. Size 25mm x 63mm. 9V operation.....£22.95

### CB400 Pocket Bug Detector/Locator

LED and piezo beeper pulse slowly, rate of pulse and pitch of tone increase as you approach signal. Gain control allows pinpointing of source. Size 45mm x 54mm. 9V operation.....£30.95

### CD600 Professional Bug Detector/Locator

Multicolour readout of signal strength with variable rate beeper and variable sensitivity used to detect and locate hidden transmitters. Switch to AUDIO CONFORM mode to distinguish between localised bug transmission and normal legitimate signals such as pagers, cellular, taxis etc. Size 70mm x 100mm. 9V operation.....£50.95

### QTX180 Crystal Controlled Room Transmitter

Narrow band FM transmitter for the ultimate in privacy. Operates on 180 MHz and requires the use of a scanner receiver or our QRX180 kit (see catalogue). Size 20mm x 67mm. 9V operation. 1000m range.....£40.95

### QLX180 Crystal Colntrolled Telephone Transmitter

As per QTX180 but connects to telephone line to monitor both sides of conversations. 20mm x 67mm. 9V operation. 1000m range.....£40.95

### QSX180 Line Powered Crystal Controlled Phone Transmitter

As per QLX180 but draws power requirements from line. No batteries required. Size 32mm x 37mm. Range 500m.....£35.95

### QRX180 Crystal Controlled FM Receiver

For monitoring any of the 'Q' range transmitters. High sensitivity unit. All RF section supplied as a pre-built and aligned module ready to connect on board so no difficulty setting up. Outpt to headphones. 60mm x 75mm. 9V operation.....£60.95

### A build-up service is available on all our kits if required.

UK customers please send cheques, POs or registered cash. Please add £1.50 per order for P&P. Goods despatched ASAP allowing for cheque clearance. Overseas customers send sterling bank draft and add £5.00 per order for shipment. Credit card orders welcomed on 0827 714476.

**OUR LATEST CATALOGUE CONTAINING MANY MORE NEW SURVEILLANCE KITS NOW AVAILABLE. SEND TWO FIRST CLASS STAMPS OR OVERSEAS SEND TWO IRCS.**

## ★★★ Specials ★★★

### DLTX/DLRX Radio Control Switch

Remote control anything around your home or garden, outside lights, alarms, paging system etc. System consists of a small VHF transmitter with digital encoder and receiver unit with decoder and relay output, momentary or alternate, 8-way dit switches on both boards set your own unique security code. TX size 45mm x 45mm. RX size 35mm x 90mm. Both 9V operation. Range up to 200m.

Complete System (2 kits).....£50.95

Individual Transmitter DLTX.....£19.95

Individual Receiver DLRX.....£37.95

### BMX-1 Hi-Fi Micro Broadcaster

Not technically a surveillance device but a great idea! Connects to the headphone output of your Hi-Fi, tape or CD and transmits Hi-Fi quality to a nearby radio. Listen to your favourite music anywhere around the house, garden, in the bath or in the garage and you don't have to put up with the DJ's choice and boring waffle. Size 27mm x 60mm. 9V operation. 250m range.....£20.95

DEPT. EE

**SUMA  
DESIGNS**

THE WORKSHOPS, 95 MAIN ROAD,  
BAXTERLEY, NEAR ATHERSTONE,  
WARWICKSHIRE CV9 2LE

VISITORS STRICTLY BY APPOINTMENT ONLY



**0827 714476**

# **L.C.D. Ultrasonic Tape Measure**

*Up, down or sideways, distances of up to nine metres or 30 feet can be easily measured and displayed by this pocket-sized unit. Using twin ultrasonic transducers, a decoding counter and a 3½ digit liquid crystal display, accuracies to within one decimal place are obtainable. An unusual feature is the foreground masking circuit which enables weak distant echoes to be more readily detected.*



## **Washer Bottle Monitor**

**When the water runs out you are breaking the law!**

*A valuable accessory for the motorist. Warns when the washer fluid reservoir is nearly empty, allowing the motorist to economise in the meantime. Uses a special fluid level detector chip. Easy to build, and with full installation instructions.*

## **Quick Test**

*Testing fuses and small components for continuity can be a fiddly business, involving chasing the component around the workbench with a pair of test-prods.*

*The Quicktest described in this article is a very simple to use piece of test equipment that will perform continuity tests on various devices without the use of test leads.*

**PLUS**

**ALTERNATIVE ENERGY: INFORMATION TECHNOLOGY:  
ACTUALLY DOING IT: AMATEUR RADIO: CIRCUIT SURGERY:  
BOOKS: VIDEOS: PCBs ETC. ETC.**

# **EVERYDAY ELECTRONICS**

SEPTEMBER ISSUE ON SALE FRIDAY 7TH AUGUST 1992


EFF  
MO  
EX  
FE  
N



## 19 INCH EQUIPMENT HOUSING
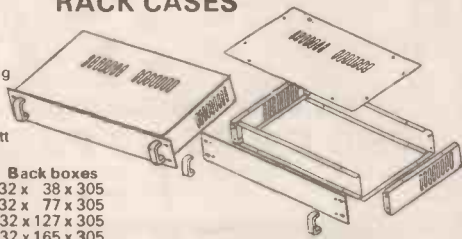
### RACK CASES


Front panels 3mm Aluminium Self Colour with removable protective plastic coating on face side.  
Back Boxes 20swg (0.9mm) Zinc plated steel. Epoxy coated, matt black.



Sizes	Front Panels	Back boxes
1U	482 x 44	432 x 38 x 305
2U	482 x 89	432 x 77 x 305
3U	482 x 133	432 x 127 x 305
4U	482 x 165	432 x 165 x 305

Supplied in flat pack for self assembly.

### "CASTLE" EQUIPMENT RACKS

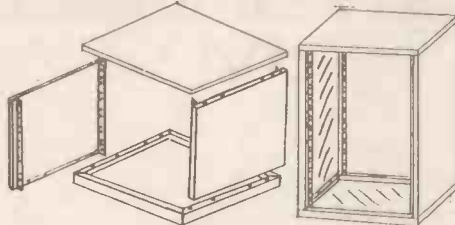

SIZES	HEIGHT
ER8	407mm
ER10	495mm
ER12	533mm
ER16	762mm
ER20	940mm

WIDTH 533mm

OVERALL DEPTH 407mm

MAX. CASE DEPTH 362mm

Manufactured of ZINTEC. Zinc plated mild steel 20swg. Epoxy coated, cream. Black to special order.

BLANK PANELS 19" fixing, 2.5mm 12g aluminium or 16g steel. Black epoxy coated.

CASTOR SET with fixings. 4 castor wheels (2 with brakes), rated 40Kg each.

#### STEEL SHELVES TO FIT RACKS



SUPPORT FOR HEAVIER EQUIPMENT

#### MAIL ORDER PRICES

CASES	RACKS	PANELS
1u - £23.50	ER 8 - £50.00	1u - 3.00
2u - £25.70	ER 10 - £53.50	2u - 4.00
3u - £30.30	ER 12 - £55.50	3u - 5.00
4u - £34.20	ER 16 - £64.50	4u - 6.00
	ER 20 - £72.00	

SHELVES	CASTOR SETS
S1 for 1u + 2u £9.00	£13.00
S2 for all others £9.00	

Please address mail orders to:  
**AIRFIELD DISTRIBUTION**  
117 The Airfield  
Little Staughton  
Bedford MK44 2BN  
Tel: 0230 62708

TRADE ENQUIRIES WELCOME  
Proprietors: Castle Engineers Ltd.

PRICES INCLUDE VAT DELIVERY ADD £4.00 PER ORDER (UK ONLY).

# PICO ADC-10


## 8-bit Analog to Digital Converter for IBM PCs & compatibles

- 10-25 kHz typical sampling speed
- 0-5 v input range

# £49

+ VAT

(including p+p)

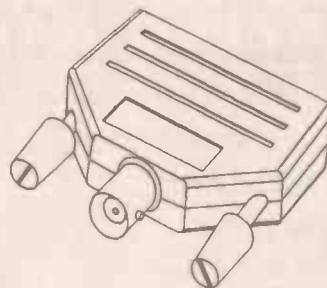

- Plugs directly into parallel printer port
- Requires no external power or expansion slots
- BNC input connector
- Supplied with software to use as a voltmeter & oscilloscope, plus Turbo C and Pascal drivers

*Pico Technology Limited*


Broadway House, 149-151 St. Neots Road,

Hardwick, Cambridge CB3 7QJ


Tel. 0954 211716 Fax. 0954 211880
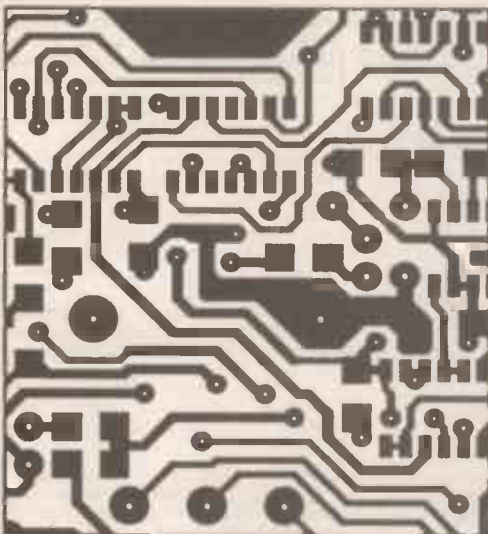
## EASY-PC PCB and Circuit Diagram CAD

Forget using tapes and lightbox! Create your Circuit Boards using CAD - like the professionals.



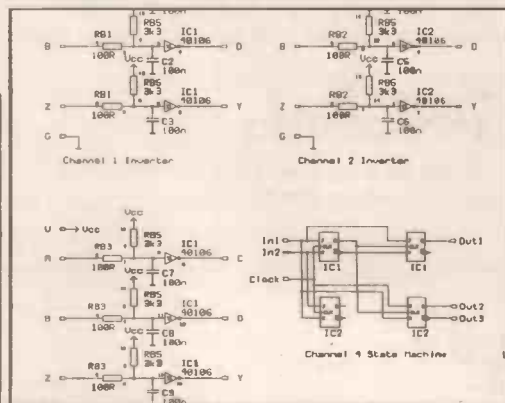- Runs on PC/XT/AT etc. with Hercules, CGA, EGA or VGA display and many DOS emulations.
- Design Schematics Single and Double sided and Multilayer boards including Surface Mount.
- Standard output includes Dot Matrix / Laser / Inkjet Printer, Pen Plotter, Photo-plotter and N.C. Drill.
- Extremely powerful.
- Very easy to use.
- Not copy protected.



## EASY-PC

Technical support is free, for life!

**Only  
£98.00!**  
Plus P&P+VAT

Over 12,000 Installations in 70 Countries Worldwide!

For full info' please Write, Phone, or Fax!

**Number One Systems Ltd.**

**The Electronics CAD Specialists.**

REF: EVD, HARDING WAY, ST. IVES, HUNTINGDON, CAMBS, PE17 4WR, ENGLAND.

Telephone: 0480 61778 (7lines) Fax: 0480 494042 ACCESS, AMEX, MASTERCARD and VISA Welcome.

# SUPER SALE NOW ON!!

# THE BIG ONE

IF YOU MISSED LAST MONTH'S EE & THE FREE 32 PAGE SALE CAT, RING/WRITE/FAX/CALL IN FOR YOUR FREE COPY NOW!!

**XTRA - XTRA - XTRA - XTRA - XTRA**  
**MORE AMAZING BARGAINS JUST ARRIVED!!**

## VHF/UHF TV RECEIVER/CONVERTER



Z8991 Amstrad  
 MP3 computer  
 modulator/converter.

A complete, fully tuneable VHF/UHF TV receiver with RGB and composite video out, and sound on the internal speaker. For use with the Amstrad CTM644-2 monitor specifically, or can be used with any colour/mono home computer monitors that have a 5.8254Hz frequency. Grey case 330x250x50mm. Controls: contrast, colour, tuning, volume and band select (VHF-L, VHF-H, UHF) RGB output on 6 pin DIN socket, and composite video. Intended for European market - needs 2 ceramic filters changing. Parts and instructions supplied. Needs stabilized 12V DC, either from monitor or separate power supply (our AL2, £8.14 is ideal).

**ONLY**  
**£14.95**

## SPECTRUM +2 LIGHT GUN

Action Pack - complete with lead, software and instruction book

**£6.95**



## Software Clearance

Z1103 Amstrad CPC464 Soft999 pack. 12 cassettes with an original retail price of £108.40 - Fast-Answer, Bridge-it, Animal Vegetable Mineral, Roland on the Ropes, Oh Mummy, Harrier Attack, Timeman One, Sultans Maze, Nanagrams, The Galactic Plague, Roland in the Caves, Fruit Machine.

**Special Price: £6.95**

## Sinclair



Z1101 Sinclair P15/G Pack. 7 cassettes (no library cases) in a boxed set with over 100 games, all with documentation.

**ONLY ONLY**  
**£4.95 £4.95**

## WIDE CARRIAGE DOT MATRIX PRINTER

HYUNDAI HDP920

**ONLY**

**£119**



BRAND NEW, FULLY GUARANTEED!

+432mm (17") Carriage  
 +Draft (12x9dot) & NLQ (24x18dot)  
 +180/34cps print speed  
 +Bi-directional printing

## TEKTRONIX MANUALS

Many scope, probe, and plug-in service manuals from £1-£25 each. E.g. 545 £20; 517A £15; 6010 £3; B,CA,D,H,L,M,W,Z plug-ins £10 each. RC815 UHF Rx/Tx £25. Ring/write/fax for list of 661

## TRANSFORMERS

Z7010 0-6, 0-6V each at 0.25A 3VA by Louth, PC mntg. Pri 0-120, 0-120. Size 38.5x32x31mm DP 3.39 Our Price £1.50 100+ 0.85

Z7011 0-6, 0-6V each at 0.5A 6VA chassis mntg. Pri 0-240. Size 45x41x37mm, individually boxed. DP 3.95 Our Price £1.50

Z7012 27V 4A Chassis mntg Pri 0-240V Size 98x83x73mm. DP around 18.00 Our Price £9.00

Z7013 40V 1.5A chassis mntg. Pri 0-240V Size 79x65x58mm. DP around 7.00 Our Price £4.00 100+ 2.50

Z7014 12V 1.5A PC or drop through mntg. Pri 0-240V Size 57x48x52mm DP around 6.00 Our Price £3.50 100+ 2.00


## HEATSINK

Z5408 Heatsink 152x50mm with 4 x TO3 devices mounted on it: 2 x 7805CK 5V 1.5A voltage regs (DP 2.00) and 2 x BUY18S, a 200V 15A NPN transistor, in our cat at 2.30. So the total value is 8.60, Our Special Price £2.50

## UHF TUNER

Z2648 UHF TV tuner - at least, the front end. Fagor SUF743 has a co-ax socket inlet into the screened case 65x50x20mm. Inside the PCB has some surface mount bits + BF966S, BF970 and BF199 transistors and a few coils. Giveaway Price 2 for £1.00

## EMERGENCY LIGHTING PARCEL

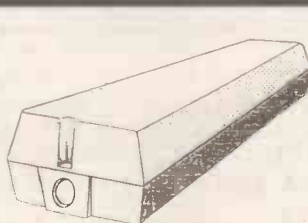

Z8986 N1615 12" fluorescent (4hr) emergency light, complete. White ABS base with translucent cover, overall 400x135x110mm. Inside the moisture proof sealed case is a 12" 8 Watt fluorescent tube & LED indicator, the charger/oscillator PCB and 3 x 4Ah 'D' size Nicads by SAFT. These are currently being sold for over £90. Standard mains input. Only £26.00

Z8987 N1613 6" version of above £18.00  
 Z2585 12" 8W fluorescent tubes £1.00  
 Z2586 6" 4W fluorescent tubes £1.00  
 Z8992 MES 1 lamp (4hr) emergency light. Tough plastic case 180mm dia x 105mm. Uses single 2.4V 1A MES lamp and 2 x 4Ah 'D' size Nicads, and has incorporated charger panel. £12.00

Z8993 N1642 MES 2 lamp (4hr) emergency light. Substantial steel case 373x126x105mm with translucent cover containing Yuasa 6V 8Ah rechargeable sealed lead acid battery and PCB with charger circuit. £18.00

## 4Ah Ni-Cads

Z7008 3.6V 4Ah 3 cell 'D' size nicad stack, by SAFT Only £7.50  
 Z7009 2.4V 4Ah 2 cell 'D' size nicad stack by SAFT Only £5.00

Z5371 Simplex rate-of-heat rise and 135°F detector, model 4255. A rise of more than 15°F per minute, or if temp reaches 135°F will close contacts. Supplied boxed with installation instructions. These normally sell for around 18.00. Our price £10.00 100+ 5.50

Z8988 Super high power siren. Standard 5" 5W 8ohm gold horn mounted on an ABS box (our V216) which contains the driver PCB. Can supply either single or swept tone and works from 6-28V DC. £8.00

## STEREO AUTO-REVERSE CASSETTE MECHS

Z5405 High quality heavy duty all metal construction stereo cassette player mechanism, probably intended for continuous background music. This is a lovely bit of kit - starts playing as soon as a cassette is inserted. Has fast forward, rewind and eject keys. It's bi-directional, and the sensing circuit automatically reverses the tape at the end. Has a Canon motor and works off 12V DC. Great value at £4.95.

## NEW POWER SUPPLIES

Z5406D High efficiency step down power regulator module by SGS. This is a GSR400 type, as listed by Farnell at £41.11 each. Output is 7V @ 4A from a DC input of 10-46V. Possible uses include battery charger, or put two together and use 24V lorry battery to power car equipment. Our special price - just £5.75 each.

Z5409 Eurocard size - 160x100mm by Protek. 115/230V input. Outputs: +5V @ 3A, +12V @ 2A, -12V @ 0.25A Price £8.95


Z5410 Skynet boxed unit 200x108mm PCB with flying leads for input (115/230V) and outputs - 5V @ 7A; 12V @ 3.5A; -12V @ 0.75A £14.95

Z5404 Stabilized power supply panel 140x85mm. AC input is rectified and smoothed and is taken via a couple of regulator transistors and a relay to a 12 way terminal block. Probably 24V. Only £2.25

## SUPER SWITCH SENSATION!!

A nice parcel of ALPS high quality push switches from DPCO to 10PCO. Available individually, or a pack of 100 assorted 4 knobs to fit £7.95. Order Code K838. Full list of types on request - prices start at 2.2p!

**DON'T DELAY - ORDER TODAY**

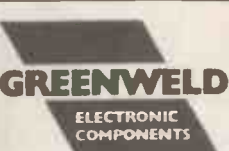

All 1 off and pack prices include VAT, qty prices do not. P&P £2.50 per order (£9 next day) Min Credit Card £12. Official orders from Education welcome; min invoice charge £15. Payment is accepted by cheque, PO, cash (inc foreign currency banknotes), book tokens, Access, Visa, Connect. Our stores have enormous stocks - we are open from 9-5.30 Mon-Sat. Come and see us!

Tel: (0703) 236363 Fax: (0703) 236307

27D PARK ROAD, SOUTHAMPTON, SO1 3TB



LEDs 3mm or 5mm red or green 5p each, yellow 11p each. High intensity red, green or yellow, 5mm 30p each  
 Cable ties 1p each. £5.95 per 1000. £49.50 per 10,000.  
 Stepping motor 4 phase 12V 7.5' step 50 ohms.....£8.95  
 SAA1027 stepping motor driver chip.....£3.60  
 FM Transmitter kit, good quality sound.....£8.60  
 High quality photo resist copper clad epoxy glass boards

Dimensions	single sided	double sided
3x4 inches	£0.95	£1.07
4x8 inches	£2.40	£2.68
6x12 inches	£5.37	£6.00
12x12 inches	£10.66	£12.00

**Rechargeable Batteries**

AA (HP7) 500mAh	£0.99
AA 700mAh	£1.95
C 2AH with solder tags	£3.60
D 4AH with solder tags	£4.95
1/2AA with solder tags	£1.55
AAA (HP16) 180mAh	£1.75
AA 500mAh with solder tags	£1.55
C (HP11) 1.8AH	£2.20
D (HP2) 1.2AH	£2.60
PP3 8.4V 110mAh	£2.45
Sub C with solder tags	£2.50
1/3 AA with tags (Philips CTV)	£1.95
Standard charger, charges 4 AA cells in 5 hours or 4 Cs or Ds in 12-14 hours + 1xPP3 (1, 2, 3 or 4 cells may be charged at a time)	£5.95
High power charger, as above but charges the Cs and Ds in 5 hours, AAs, Cs and Ds must be charged in 2s or 4s	£10.95

Special offers - please check for availability  
 F cells 32dia x 87mm.....£3.95  
 F cell with solder tags, 1.2V.....£4.30  
 42mm x 16mm dia, 1.2V.....£1.45  
 Stick of 4, 171mm x 16mm dia., with red & black leads, 4.8V.....£5.95  
 4 cell battery 94mm x 25mm dia. (1/2C cells).....£3.50  
 Computer grade capacitors with screw terminals, 39000pF 20V £2.50; 87000pF 10V £1.95; 68000pF 15V £2.95; 10000pF 16V £1.50  
 7 segment common anode led display, 12mm.....£0.45  
 LM2931AT 5.0 low drop out 5V regulator TO220 package.....£0.85  
 7812 and 7912 12V 1A regulators.....£20.00 per 100  
 LM337A TO3 case variable regulator.....£1.60 100+ £1.10  
 BS250 P channel mosfet 45p, BC559 transistor per 100 £3.95 £10.00 per 100  
 Used 8748 Microcontroller.....£3.50  
 SL952 UHF Limiting amplifier LC 16 surface mounting package with data sheet.....£1.95  
 AM27502.....£1.25 each; 90p 100+ £0.4007UB.....10p 100+; 6p 1000+  
 TV Mains switch, 4A double pole with momentary contacts for remote control, pack of 60 £19.95  
 DC-DC converter, Reliability model, V12P5, 12V in 5V 200mA out, 300V input to output, Isolation with data, £4.95 each or pack of 10 - £39.50  
 Hour counter used 7 digit 240V ac 50Hz.....£1.45  
 Resistor pack 2500 resistors 1/8-2W 50 different values.....£8.95

Resistor jumbo pack 25000, 1/4 and 1/2W resistors our choice of values and size, will be mainly in boxes or rolls of 1000, 2000 and 5000 of one type.....£25.00  
 Qwerty keyboard, 58 key good quality switches new.....£5.00  
 Qwerty keyboard with serial output, no data (used).....£6.00  
 Polyester capacitors, box type, 22.5mm lead pitch 1µf 250V dc 20p each, 15p 100+, 10p 1000+ 2.2µf 250V dc 30p each, 20p 100+, 15p 1000+ 3.3µf 100V dc 30p each, 15p 100+, 10p 1000+ 1µf 50V bipolar electrolytic axial leads, 15p each, 7.5p 1000+ 0.22µf 250V polyester axial leads, 15p each, 100+ 7.5p each  
 Philips 123 series solid aluminium axial leads, 33µf 10V & 2.2µf 40V 40p each, 25p 100+  
 Multilayer AVX ceram capacitors, all 5mm pitch, 100V 100pF, 150pF, 220pF, 10,000pF (10n) 10p each, 5p 100+, 3.5p 1000+  
 Welwyn W23 9W 120 ohm 35p each, 20p 100+ 680 ohm 2W metal film resistor, 4p 100+  
 2p 1000+  
 Solid carbon resistors, very low inductance, ideal for RF circuits, 270ohm 2W, 680ohm 2W 25p each, 15p each 100+, we have a range of 0.25W, 0.5W, 1W and 2W solid carbon resistors - please send SAE for list  
 Intelligent 4 digit alphanumeric (5x7 dot 0.145") red LED display, 12 pin 0.6 inch wide package, Siemens type DLR1414 £2.50 each, £2.00 30+, data sheets £1.00  
 AMD 27256-3 Eproms £2.00 each, £1.25 100+ DIP switch 3PC 12 pin (ERG SDC-3-023) 60p each, 40p 100+  
**MODEMS**  
 V22/V22bis IBM PC internal full length card modem, BT approved, can be set to com 1 or 2, 1200/2400 baud with software and manual, not Hayes compatible, made by Plessey.....£35.00  
 V32 9600 baud and 4800 baud GEC Plessey telecom external modem, model 9632, Hayes compatible and BT approved, with auto call, auto answer, using V25, V25bis and Hayes AT protocols and V54 remote + local diagnostics. It does not work on slower speeds, V22/V2200 baud etc and needs 1 internal dip switch to be switched on to select Hayes commands. It comes with a 100+ page comprehensive A4 size manual. An all together brilliant machine for only.....£199+ VAT = £233.83  
 All products advertised are new and unused unless otherwise stated.  
 Wide range of CMOS TTL 74HC 74F Linear Transistors kits, rechargeable batteries, capacitors, tools etc. always in stock  
 Please add 95p towards P&P VAT included in all prices

**JPG ELECTRONICS**  
 276-278 Chatsworth Road  
 Chesterfield S40 2BH  
 Access/Visa Orders:  
 (0246) 211 202  
 Callers welcome

**LASER SCIENCE**

We supply all Laser and associated optical components at low, low prices.

**SPECIAL OFFER**

High Powered  
 5mW Visible HeNe Laser Tubes.  
 £55.00 each. (inc. PSU Plans)

Easy to set up and operate.  
 These are new & direct from the factory.  
 Not to be confused with the usual lower powered devices on offer.

For Information on Lasers, Optics, Holography kits, Plans, Books etc...  
 Send S.A.E. To: Laser Science Ltd.  
 P.O. Box 79, Prestwich, Manchester M25 5AT  
 TEL: 061 773 0911. FAX: 061 773 0912

**OMNI ELECTRONICS**

174 Dalkeith Road, Edinburgh EH16 5DX 031 667 2611

**A COMPREHENSIVE RANGE WITH SERVICE SECOND TO NONE**

OUR MUCH EXPANDED, BETTER ILLUSTRATED CATALOGUE COSTS £1.50 - INCLUDES VOUCHERS TO USE AGAINST FUTURE PURCHASES. TO RECEIVE A COPY PLEASE SEND YOUR REMITTANCE WITH THE VOUCHER BELOW.



Please send me a copy of the 1990/91 OMNI catalogue. Payment of £1.50 enclosed

NAME.....  
 ADDRESS.....  
 TELEPHONE.....

Open: Mon.-Thurs. 9.15 - 6.00  
 Friday 9.15 - 5.00  
 Saturday 9.30 - 5.00



Metal detector boards with Data has tuner, mode discriminate, headphone jack, on/off volume & push button facilities.....£7.95 ea\*

Dictaphone cassette, mech/record erase playback heads, 6V solenoid, motor, hall effect switch.....£2.00 ea\*

T.V./Printer stands.....£3.95 ea\*

Bicc-Vero Easiwire construction kit.....£4.95 ea\*

TTL/CMOS short circuit snooper.....£4.95\*

Dot matrix LCD 10x2 lines.....£3.75 ea\*

Dot matrix LCD 16 x 1 lines with Data.....£4.95\*

40 characters x 1 line dot matrix LCD with data.....£15.00\*

2 digit 16 segment VF display with data.....£2.95 ea\*

4 digit intelligent dot matrix display.....£6.00\*

17 segment V.F. display with driver board and data.....£2.99 ea\*

8 digit liquid crystal display.....£1.75 ea\*

4 digit LCD with 7211 driver chip.....£3.50 ea\*

Digital clock display.....£2.50\*

11 key membrane keypad.....£1.50 ea\*

Keyboard 392mm x 180mm/100 keys on board + LCD + 74HC05/80C49 easily removable.....£4.95

19" 3U sub rack enclosures.....£8.95

12V stepper motor, 48 steps per rev, 7.3° step angle.....£3.95 ea\*

Stepper motor board with 2 slotted opto + 2 mercury tilt switches.....£3.95 ea\*

1000 mixed 1/4 watt 1% resistors.....£4.95 ea\*

250 electrolytic axial + radial caps.....£4.95 ea\*

200 off mixed polyester caps.....£7.95\*

100 Mixed trimmer caps popular values.....£4.95\*

100 off Phono plugs (red/black/grey).....£3.50\*

50 Mixed terminal blocks.....£2.95

25 off asst. buzzers & sounders.....£4.95\*

Cable box UHF modulator/video preamp/transformer/R's + C's/leads.....£6.95

1000 off mixed Multilayer Ceramic Caps.....£7.95

Solar cell modules 0.45V 700mA.....£2.95 ea\*

B.B.C. Micro to disc drive lead.....£1.50\*

Car Burglar alarm vibration auto entry/exit delay.....£5.95 ea\*

Single zone alarm panel auto entry/exit delay housed in domestic light socket.....£9.95 ea\*

P.C. P.S.U. 50 watt 115-230V input + 5V 4A + 12V 2.5A output with built in fan, IEC inlet + on off.....£9.95 ea

STC P.S.U. 240V input 5V 6A output (converts to 12V 3A details available).....£5.95 ea

240V input 5V 10A output (converts to 12V 5A no details).....£5.95 ea

600Ω line output transformers.....£1.25 ea\*

240V in 0-12V 0.75A out transformer.....£1.75\*

240V in 0-28V 62VA out transformer.....£2.75

Transformer + PCB gives 2x7.5V 32VA with skt for 5 or 12V regulator, will power floppy drive.....£3.75 ea

Ultrasonic transducers (transmit + receive).....£1.50 pair

3 to 16V Piezoelectric sounders.....50p

9VDC electromechanical sounder.....50p

24V DC electromechanical sounder.....50p

2A 250V keyswitch 3 position key removable in two positions.....£1.50\*

DIL switches PCB MT 3/4/6 way.....35p

5V SPCO SIL reed relay.....40p

5V 2PCO DIL miniature relay.....60p

12V 2PCO or 4PCO continental relay.....60p

12V 10A PCB MT (to make contact) relay.....95p\*

3 to 12V electro magnetic acoustic transducer with data.....75p\*

2.4576/8.8329/21.10 MHz crystals.....50p ea\*

Bridges 25A 200V.....£1.00

2A 100V.....50p

31b Mixed components pack.....£4.95

25 off mixed relays.....£5.95\*

40 off mixed toggle switches.....£9.95\*

50 off mixed switches, toggle, rocker, slide, micro.....£9.95

Miniature axial chokes 0.1, 0.18, 0.12, D.33, 0.39, 0.15, 1, 3.3UH.....10p ea., 100 for £7.50\*

250 off 16/22/24/40 way IC Skts.....£4.95\*

Crystal Oscillators 10/24/48 MHz.....£1 ea\*

Spider Plug Leads.....75p ea\*

**QUANTITY DISCOUNTS AVAILABLE PLEASE RING**

ALL PRICES INCLUDE V.A.T. PLEASE ADD £2.00 p&p EXCEPT ITEMS MARKED\* WHICH ARE 50P. SAE FOR BULK BUYING LIST PAYMENT WITH ORDER TO:

**Dept EE, COMPEL, 14 Constable Road St. Ives, Huntingdon, Cambs PE17 6EQ Tel/Fax: 0480 300819**





# HART AUDIO KITS - YOUR VALUE FOR MONEY ROUTE TO ULTIMATE HI-FI

HART AUDIO KITS give you the opportunity to build the very best engineered hi-fi equipment there is, designed by the leaders in their field, using the best components that are available.

Every HART KIT is not just a new equipment acquisition but a valuable investment in knowledge, giving you guided hands-on experience of modern electronic techniques.

In short HART is your 'friend in the trade' giving you, as a knowledgeable constructor, access to better equipment at lower prices than the man in the street.

You can buy the reprints and construction manual for any kit to see how easy it is to build your own equipment the HART way. The FULL cost can be credited against your subsequent kit purchase.

Our list will give you fuller details of all our Audio Kits, components and special offers.

## AUDIO DESIGN 80 WATT POWER AMPLIFIER.



This fantastic John Linsley Hood designed amplifier is the flagship of our range, and the ideal powerhouse for your ultimate hi-fi system. This kit is your way to get CK performance for a few tenths of the cost! Featured on the front cover of Electronics Today International! This complete stereo power amplifier offers World Class performance allied to the famous HART quality and ease of construction. John Linsley Hood's comments on seeing a complete unit were enthusiastic:- The external view is that of a thoroughly professional piece of audio gear, neat elegant and functional. This Impression is greatly reinforced by the internal appearance, which is redolent of quality, both in components and in layout. Options include a stereo LED power meter and a versatile passive front end giving switched inputs using ALPS precision, low-noise volume and balance controls. A new relay switched front end option also gives a tape input and output facility so that for use with tuners, tape and CD players, or indeed any other 'flat' inputs the power amplifier may be used on its own, without the need for any external signal handling stages. 'Slave' and 'monoblock' versions without the passive input stage and power meter are also available. All versions fit within our standard 420 x 260 x 75mm case to match our 400 Series Tuner range. ALL six power supply rails are fully stabilised, and the complete power supply, using a toroidal transformer, is contained within a heavy gauge aluminium chassis/heatsink fitted with IEC mains input and output sockets. All the circuitry is on professional grade printed circuit boards with roller tinned finish and green solder resist on the component input side, the power amplifiers feature an advanced double sided layout for maximum performance. All wiring in this kit is pre-terminated, ready for instant use!

RLH11 Reprints of latest articles.....£1.80  
K1100CM HART Construction Manual.....£5.50

## LINSLEY HOOD 'SHUNT FEEDBACK' R.I.A.A. MOVING COIL & MOVING MAGNET PICKUP PREAMPLIFIER



Modern, ultimate sound systems are evolving towards a built-in RIAA preamplifier within the turntable unit, keeping noise pickup to a minimum. This new circuit by John Linsley Hood uses latest generation integrated circuits in the sonically preferred shunt feedback configuration to give an accurate and musical sound, with the ability to use both moving magnet and moving coil cartridges. Power comes from two 9v PP3 size batteries or a mains power supply. This HART kit is exceptionally easy to build with detailed instructions and all the specially selected components fitting directly on to the roller tinned fibreglass printed circuit board. Even the gold plated phono sockets mount directly on the board.

This Kit now comes with latest generation low-noise front end IC and onboard power stabilisers for any DC Input voltage between 9v and 30v.

K1500 Special Discount Price for complete Kit.....£67.99

## ALPS PRECISION LOW-NOISE STEREO POTS.



To fulfil the need for higher quality controls we are now importing an exciting new range of precision audio pots in values to cover most quality amplifier applications. All in 2-gang stereo format, with 20mm long 6mm dia. steel shafts. Now you can throw out those noisy ill-matched carbon pots and replace with the real hi-fi components only used selectively in the very top flight of World class amplifiers. The improvement in track accuracy and matching really is incredible giving better tonal balance between channels and rock solid image stability. Motorised versions have 5v DC Drive motor.

2-Gang 100K Lin.....£8.67  
2-Gang 10K, 50K & 100K Log.....£9.40  
2-Gang 10K Special Balance.....£10.71  
2-Gang 20K Log MOTORISED.....£19.20  
2-Gang 10K Special Balance, MOTORISED, zero crossstalk and < 10% centre loss with near Log/Antilog Tracks.....£19.98

## HIGH QUALITY REPLACEMENT CASSETTE HEADS



Do you tapes lack treble? A worn head could be the problem. For top performance cassette recorder heads should be replaced every 1,500 hours. Fitting one of our high quality replacement heads could restore performance to better than new! Standard inductances and mountings make fitting easy on nearly all machines (Sony are special, see below) and our TC1 Test Cassette helps you set the azimuth spot on. As we are the actual importers you get prime parts at lower prices, compare our prices with other suppliers and see! All our heads are suitable for use with any Dolby system and are normally available ex stock. We also stock a wide range of special heads for home construction and industrial users.

HM120 Standard Mono R/P Head.....£3.51  
HC15 Standard Quality Stereo R/P Head.....£2.49  
HC66 High Quality Stereo R/P Head. Permalloy.....£7.98  
HS16 Sensus Alloy Stereo Head.....£21.49  
HC80 NEW RANGE High Beta Permalloy Stereo head. Modern space saver design for easy fitting and lower cost. Suitable for chrome metal and ferric tapes, truly a universal replacement head for everything from hi-fi decks to car players and at an incredible price too!.....£8.30  
HG551 4-Track RECORD & Play Permalloy Head for auto-reverse car players or quadrasonic recording £14.90  
H524 Standard Erase Head.....£1.90  
H561 Hi Field Erase Head for METAL Tapes.....£3.49  
HRP373 Downstream Monitor Stereo Combination Head.....£47.90

Many other SPECIAL cassette Heads in stock, see our LIST.

## REEL TO REEL HEADS

999R 2/4 Record/Play 110mH. Suits Stuart Tape Circuits.....£13.64  
998E 2/4 Erase Head 1mH. Universal Mount. Suits Stuart.....£11.98

## TAPE RECORDER CARE PRODUCTS

HART TC1 TEST CASSETTE Our famous triple purpose test cassette. Sets tape azimuth, VU level and tape speed.....£5.36  
DEM1 Mains Powered Tape Head Demagnetizer, prevents noise on playback due to residual head magnetisation.....£4.48  
DEM115 Electronic, Cassette Type, demagnetizer.....£8.91

## COMPUTER CORNER

The following are a selection of our new range of VERY competitively priced, High Quality, computer systems. Due to our long experience of importing we have the necessary contacts in the Far East to buy at very advantageous prices and can pass the savings on to you. All hard disk machines ordered with DOS are fully formatted and ready to use.

### HART MODEL AT-286/16WP COMPUTER

Fully fledged AT286 machine, cheap enough to use as the fastest wordprocessor in the west! Only a few years ago the AT-286 machine was the fastest standard office computer known. Now we can offer the superfast 16MHz version (earlier ones were only 10 or 12MHz) at such an incredibly low price that it can be used in any office or home. Not only that but ours comes with ultrafast memory so that the machine can run in 'zero wait state'.



Advanced features are:- Full 1MB of memory (Expandable to 4MB), 102 key UK keyboard, compact desktop case, 1.2MB 5 1/4" High Density Disk Drive and interface card for extra drive, Graphics/Printer Card, built in Hard Disk Interface.  
HART AT-286/16WP.....ONLY £277.25  
14" FST Hercules monitor, Amber.....£83  
14" Paper White Hercules Monitor. (Both have T/S Base).....£86  
Trust Writer W/P Software uses Wordstar commands.£19.50  
40MB AT-286/16UG Hard Disk Computer  
Specification as above but with 45MB 25ms hard disk, VGA Colour Graphics Card with 512K RAM, parallel printer port, 2 serial ports. 1 game port.....£523.50  
14" VGA Mono Monitor, Amber £86.70 Paper White £89

### HART 40MB AT-386/16SX EL



Entry level 386 machine for demanding applications at moderate cost. Spec as our AT286/16WP with 1MB Dram memory, Mini Tower case, 45MB 25ms hard disk drive, VGA Colour Graphics Card with 256K RAM.  
40MB AT-386/16SX EL is.....ONLY £634.30 (Ex Vat)

### HART 52MB AT-386/20SX UG



Luxury version of the above with higher processor speed and amazing 9 millisecond access time hard disk. 2MB SIMM RAM, Compact Tower Case, VGA 1024 x 768 card with 512K RAM, upgradeable to 1MB of Video memory.  
40MB AT-386/20SX UG.....ONLY £853.10

### OPTIONAL EXTRAS

HART Computers can be 'custom made' to fit your personal

requirements, at NO extra cost! Simply select the options you require. If replacing any item in the standard specification for that model then deduct the cost of the part not needed.

### SOFTWARE

MS-DOS 5 Latest Release. Full version. 3.5" or 5.25".....£59  
DR DOS 6.....£77  
Microsoft Windows Latest Version 3.1.....£67

### MONITORS

SM1421 AM TU Hercules Mono with FST Tube and Stand, Amber.....£83  
SM1421 PW TU As Above but Paper White Screen.....£86  
SM1416A VGA Mono Monitor c/w tilt and swivel stand. Amber.....£86.70  
SM1416W As Above, Paper white.....£89  
SM1485-00 Super VGA Multisync Colour Monitor, 28" dot pitch, 50MHz Bandwidth, up to 1024 x 768, c/w stand.....£235

### KEYBOARDS

K261 102 Key Enhanced UK Layout, Tactile Click, AT/XT Switchable with dual slope feet. (Standard Keyboard supplied with systems).....£31  
K106 Similar to above, single slope feet, Alps switches.....£36  
KB6153A As above but with heavy metal base.....£44

### I/O and GRAPHIC CARDS

AT Super I/O Card 2 x FDD, 1xIDE, 2 Serial, 1 Parallel, 1 Game Ports.....£21.20  
Hercules Mono Graphic & Printer card.....£11.70  
16-Bit VGA Card, 256K.....£46.50  
Trident 8900 VGA Card, 512K.....£67.30  
Trident 8900 VGA Card with 1Mb.....£86.90

### DISK DRIVES

5.25" 1.2Mb Floppy Disk Drive.....£49  
3.5" 1.44Mb Floppy Disk Drive.....£45  
Adapter to fit 3.5" drive in 5.25" slot, c/w power adapter.....£9  
45MB 25ms Hard Disk Drive.....£165  
52MB Quantum Hard Disk. Lightning Fast 9ms Access time.....£261

### CASES

WE 611P Desktop Case, Flip Top, 200W PSU.....£56.40  
WE727P Mini Tower Case, 200W PSU.....£84.70  
108MP Mini Tower Case, Compact Style.....£89  
CT107 Midi Tower Case.....£108

### MOTHERBOARDS

AT-286/16 0K.RAM.....£89  
AT-386-16SX 0K.RAM.....£195  
AT-386-20SX 0K.RAM.....£245

PLEASE NOTE THAT ALL ITEMS IN THIS SECTION ARE PRICED EX VAT.

Send or 'phone for your copy of our List (50p) of these and many other Kits & Components. Enquiries from Overseas customers are equally welcome, but PLEASE send 2 IRCs if you want a list sent surface post, or 5 for Airmail.

Ordering is easy. Just write, telephone or fax your requirements to sample the friendly and efficient HART service. Payment by cheque, cash or credit card. A telephoned or faxed order with your credit card number will get your order on its way to you THAT DAY.

Please add part cost of carriage and insurance as follows:- INLAND Orders up to £20 - £1.50  
Orders over £20 - £3.50 Express Courier, next working day. £10 (For safety all computer parts are only sent by courier) OVERSEAS - Please see the ordering information with our lists.



MANUFACTURERS OF QUALITY AUDIO KITS AND COMPUTERS

24 hr. SALES LINE (0691) 652894

AUDIO KIT PRICES are VAT INCLUSIVE. COMPUTER PRICES EXCLUDE VAT



HART ELECTRONIC KITS LTD.  
6 PENYLAN MILL  
OSWESTRY, SHROPSHIRE  
SY10 9AF



# MAGENTA ELECTRONICS LTD



MAIL ORDER AND SHOP  
EE123  
135 Hunter St  
Burton-on-Trent  
Staffs, DE14 2ST  
Tel: 0283 65435  
Fax: 0283 46932

## VERSATILE BBC INTERFACE

A comprehensive interface which allows the BBC Model B computer to be connected safely to a wide range of input and output devices. Two leads connect the interface to the User port and Printer port. Up to 16 outputs (all via single pole change-over relay contacts) and 8 inputs. All inputs are fully protected. LED indication is provided on all lines. Requires an independent 12V supply

Full Kit Ref: 844 **£51.95**

## STEPPING MOTOR DRIVER/INTERFACE

EE Jan '92

A single board, stand alone, stepping motor driver with built-in oscillator for variable low speed, high speed, and acceleration control. Suitable for all Magenta's four-phase unipolar motors and most others - up to 35V and 1.5A per phase. Half step, Full step and Wave-drive modes - switch selectable. LED mimic display and connector for computer port.

Kit includes MD35 motor  
Kit Ref: 843 **£29.95**  
Or Built **£44.95**

*Supplying Electronics  
for Education,  
Robotics, Music,  
Computing and much,  
much more*

CATALOGUE  
AVAILABLE PRICE  
**£1.00 INC. P&P**

All prices include VAT at 17.5%

Shop open 9-5 Mon.-Fri.

9-2 Saturday

Official orders welcome

Add £2


p&p to

all orders

## HAMEG HM 203-7 OSCILLOSCOPE

High quality reliable instrument made in W. Germany. Outstanding performance. Full two year parts and labour warranty. 20MHz-2 channels 1mV sensitivity. Easy to operate and high performance  
(Cheques must be cleared) **£338 + £59.15 VAT**  
Next day Delivery **£10.00**

## D.C. MOTOR GEARBOXES

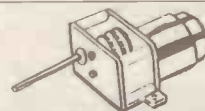

Ideal for Robots and Buggies. A miniature plastic reduction gearbox coupled with a 1.5-4.5 Volt mini motor. Variable gearbox reduction ratios are obtained by fitting from 1 to 6 gearwheels (supplied). Two types available:

**Small Unit Type MGS** **£4.77**  
Speed range 3-2200 rpm. Size: 37 x 43 x 25mm  
**Large Unit Type MGL** **£5.58**  
Speed range 2-1150 rpm. Size: 57 x 43 x 29mm

## STEPPING MOTORS

A range of top quality stepping motors suitable for driving a wide range of mechanisms under computer control using simple interfacing techniques.

**ID36 Permanent Magnet Motor** **£16.86**  
48 steps per rev  
**MD200 Hybrid Motor** **£17.10**  
200 steps per rev  
**MD35 1/4 Permanent Magnet Motor**  
48 steps per rev. **£12.98**  
**MD38 Permanent Magnet Motor** **£9.15**  
48 steps per rev.

## EVERYDAY ELECTRONICS KIT PROJECTS

ALL KITS HERE HAVE BEEN FEATURED IN EE AND ARE SUPPLIED WITH MAGAZINE ARTICLE REPRINTS. SEPARATE REPRINTS ALSO AVAILABLE PRICE 80p EACH INCLUSIVE P&P. KITS INCLUDE CASES, PCB'S HARDWARE AND ALL COMPONENTS (UNLESS STATED OTHERWISE) CASES ARE NOT DRILLED OR LABELS SUPPLIED UNLESS STATED.

Ref		Price	Ref		Price
844	VERSATILE BBC INTERFACE Mar 92	£51.95	700	ACTIVE I/R BURGLAR ALARM Mar 87	£40.74
843	STEPPING MOTOR DRIVER/INTERFACE Jan 92 or built	£29.95 £44.95	584	SPECTRUM SPEECH SYNTH (no case) Feb 87	£23.90
842	PORTABLE ULTRASONIC PEST SCARER. Aug '91	£22.56	581	VIDEO GUARD Feb 87	£9.59
841	DIGITAL LCD THERMOSTAT May 91 with punched and printed case	£29.95	569	CAR ALARM Dec 86	£14.24
840	DIGITAL COMBINATION LOCK Mar 91 with drilled case	£19.86	561	LIGHT RIDER LAPEL BADGE Oct 86	£11.65
839	ANALOGIC TEST PROBE Jan 91 (no case)	£13.23	560	LIGHT RIDER DISCO VERSION Oct 86	£22.41
838	MICROCONTROLLER LIGHT SEQUENCER Dec 90. With drilled and labelled case	£57.17	559	LIGHT RIDER 16 LED VERSION Oct 86	£15.58
835	SUPERHET BROADCAST RECEIVER Mar 90 With drilled panels and dial	£17.16	556	INFRA-RED BEAM ALARM Sep 86	£32.39
834	QUICK CAP TESTER Feb 90	£10.39	544	TILT ALARM July 86	£8.94
833	EE 4 CHANNEL LIGHT CHASER Jan 90	£32.13	542	PERSONAL RADIO June 86	£13.17
815	EE TREASURE HUNTER Aug 89	Full Kit £45.95	528	PA AMPLIFIER May 86	£30.60
814	BAT DETECTOR June 89	£21.44	523	STEREO REVERB Apr 86	£30.21
812	ULTRASONIC PET SCARER May 89	£14.81	513	BBC MIDI INTERFACE Mar 86	£31.93
800	SPECTRUM EPROM PROGRAMMER Dec 88	£30.60	512	MAINS TESTER & FUSE FINDER Mar 86	£10.07
796	SEASHELL SYNTHESISER Nov 88	£28.55	497	BBC MUSICAL DOOR BELL Jan 86	£21.41
790	EPROM ERASER Oct 88	£28.51	493	DIGITAL CAPACITANCE METER Dec 85	£49.95
769	VARIABLE 25V-2A BENCH POWER SUPPLY Feb 88	£56.82	481	SOLDERING IRON CONTROLLER Oct 85	£6.25
744	VIDEO CONTROLLER Oct 87	£33.29	464	STEPPER MOTOR INTERFACE FOR THE BBC COMPUTER less case Aug 85	£9.60
740	ACOUSTIC PROBE Nov 87	£20.01		1D35 STEPPER MOTOR EXTRA OPTIONAL POWER SUPPLY PARTS	£9.15 £5.86
739	ACCENTED BEAT METRONOME Nov 87	£23.94	461	CONTINUITY TESTER July 85	£7.08
734	AUTOMATIC PORCH LIGHT Oct 87	£19.62	455	ELECTRONIC DOORBELL June 85	£8.63
730	BURST-FIRE MAINS CONTROLLER Sep 87	£15.50	444	INSULATION TESTER Apr 85	£22.37
728	PERSONAL STEREO AMP Sep 87	£16.34	392	BBC MICRO AUDIO STORAGE SCOPE INTERFACE Nov 84	£40.82
724	SUPER SOUND ADAPTOR Aug 87	£43.86	387	MAINS CABLE DETECTOR Oct 84	£6.31
722	FERMOSTAT July 87	£13.88	386	DRILL SPEED CONTROLLER Oct 84	£9.91
719	BUCCANEER I.B. METAL DETECTOR July 87	£30.22	362	VARICAP AM RADIO May 84	£15.02
718	3-BAND 1.6-30MHz RADIO Aug 87	£30.30	337	BIOLOGICAL AMPLIFIER Jan 84	£27.59
715	MINI DISCO LIGHTS June 87	£14.39	263	BUZZ OFF Mar 83	£6.49
707	EQUALIZER (IONISER) May 87	£17.75	242	INTERCOM no case July 82	£6.50
			240	EGG TIMER June 82	£7.85
			108	IN SITU TRANSISTOR TESTER June 78	£10.76
			106	WIRED SOUND EFFECTS GEN Mar 78	£8.94
			101	ELECTRONIC DICE Mar 77	£7.15

## EDUCATIONAL BOOKS & BOOK PROJECTS

### ADVENTURES WITH ELECTRONICS

The classic Easy to Follow book suitable for all ages. ideal for beginners. No soldering, uses an S-DEC breadboard. Gives clear instructions with lots of pictures. 16 projects - including three radios, siren, metronome, organ, intercom, timer, etc. Helps you learn about electronic components and how circuits work. Component pack includes an S-DEC breadboard and all the components for the series.

**Adventures with Electronics** **£6.25**  
**Component Pack (less book)** **£22.83**

### FUN WITH ELECTRONICS

From the USBORNE Pocket Scientist series - an enjoyable introduction to electronics. Full of very clear full colour pictures accompanied by easy to follow text. Ideal for all beginners - children and adults. Only basic tools are needed. 64 full colour pages cover all aspects - soldering - fault finding - components (identification and how they work). Also full details of how to build 6 projects - burglar alarm, radio, games, etc. Requires soldering - 4 pages clearly show you how. The components supplied in our pack allows all the projects to be built and kept. The book is available separately.

**Fun with Electronics Book** **£2.95**  
**Component pack (less book)** **£17.93**

### 30 SOLDERLESS BREADBOARD PROJECTS

A book of projects by R. A. Penfold covering a wide range of interests. All projects are built on a Verobloc breadboard. Full layout drawings and component identification diagrams enable the projects to be built by beginners. Each circuit can be dismantled and rebuilt several times using the same components. The component pack allows all projects in the book to be built one at a time. Projects covered include amplifiers, light actuated switches, timers, metronome, touch switch, sound activated switch, moisture detector, MW Radio, Fuzz unit, etc.

**30 Solderless Breadboard Projects (Book 1)** **£2.95**  
**Component Pack** **£27.74**



## INSULATION TESTER

EE APRIL 85



A reliable electronic tester which checks insulation resistance of wiring appliances etc., at 500 volts. The unit is battery powered simple and safe to operate. Leakage resistance of up to 100 Megohms can be read easily. One of our own designs and extremely popular.

KIT REF 444

£22.37

## PET SCARER

EE MAY 89

Produces high power ultrasound pulses. L.E.D. flashes to indicate power output and level. Battery powered (9V-12V or via Mains Adaptor).

KIT REF 812

Mains Adaptor £2.02

£14.81

## DIGITAL COMBINATION LOCK

EE MAR '91

Digital combination lock with a 12 key keypad. 4 digit code operates 250V-16A SPCO relay. A special anti-tamper circuit allows the relay to be mounted remotely from the keypad without any loss of security. Can be operated in many modes (latching/unlatching, manual/automatic setting, continuous/momentary output, etc.). Article describes operation as Vehicle Immobilising security system. Low current drain. *Kit includes drilled case*

KIT REF 840

£19.86

## DIGITAL LCD THERMOSTAT

EE MAY '91

A versatile thermostat with LCD read out. MIN/MAX temperature recording, clock and individually settable upper and lower switching points. Covers -10 to 110 degrees Celsius, accurate to within 0.1 degrees. Submersible probe on 3 meter lead. Kit includes punched and printed case. Save on energy bills by improved control of your hot water system. Also ideal for greenhouse soil temperature and aquarium control. Complete kit includes thermostat and probe, mains power supply and relay output. PCB's and punched and printed case.

KIT REF 841

£29.95

## 3 BAND SHORT WAVE RADIO

EE AUG 87

Covers 1.6-30 MHz in 3 bands using modern miniature coils. Audio output is via a built-in loudspeaker. Advanced design gives excellent stability, sensitivity and selectivity. Simple to build.

KIT REF 718

£30.30

## PORTABLE ULTRASONIC PEST SCARER

EE AUG '91

A powerful 23kHz Ultrasonic generator in a compact hand-held case. A MOSFET output drives a weatherproof transducer at up to 300V peak to peak via a special tuned transformer. Sweeping frequency output requires no setting up or alignment. Kit includes all components, PCB, transducer and case.

KIT REF 842

£22.56

## ACOUSTIC PROBE

EE NOV '87

A very popular project which picks up vibrations by means of a contact probe and passes them on to a pair of headphones or an amplifier. Sounds from engines, watches and speech travelling through walls can be amplified and heard clearly. Useful for mechanics, instrument engineers and nosey parkers!

KIT REF 740

£20.01

## 4 CHANNEL LIGHT CHASER

EE Jan '90

A 1000W per channel chaser with zero volt switching, hard drive, inductive load capability, mic sound sensor and sophisticated 'beat' detector. Chase steps to music or auto when quiet. Variable speed and mic. sens. LED mimic on front panel. Switchable for 3 or 4 channels. P552 output. Ideal for rope lights, pin spots, disco and display lighting.

KIT REF 833

£32.13

## EE EQUALISER

EE MAY '87

A mains powered ioniser with an output of negative ions that give a refreshing feeling to the surrounding atmosphere. Negligible current consumption and all-insulated construction ensure that the unit is safe and economical in use. Easy to build on a simple PCB.

KIT REF 707

£17.75

## LIGHT RIDERS

EE OCT '86

Three projects under one title - all simulations of the Knight Rider lights from the TV series. The three are a lapel badge using six LEDs, a larger LED unit with 16 LEDs and a mains version capable of driving six main lamps totalling over 500 watts.

KIT REF 559 CHASER LIGHT £15.58

KIT REF 560 DISCO LIGHTS £22.41

KIT REF 561 LAPEL BADGE £11.65

## MICROCONTROLLER LIGHT SEQUENCER

EE DEC '90

A superb kit with pre-drilled painted and silk screen printed case for a really professional finish. This kit uses a microcontroller I.C. to generate 8-channel light sequences. Sequences are selected by keypad from over 100 stored in memory. Space for 10 user programmed sequences up to 16 steps long also available. 1000 watts per channel, zero volt switching, inductive load capability. Opto-isolated for total safety. Many other features. Complete kit includes case, PCBs, all components and hardware.

KIT REF 838

£57.17

## EPROM ERASER

EE OCT '88

Safe low-cost unit capable of erasing up to four EPROM's simultaneously in less than twenty minutes. Operates from a 12V supply. Safety interlock. Convenient and simple to build and use.

KIT REF 790

£28.51

## EE TREASURE HUNTER

EE AUG '89

A sensitive pulse induction Metal Detector. Picks up coins and rings etc., up to 20cms deep. Low "ground effect". Can be used with search-head underwater. Easy to use and build, kit includes search-head, handle, case, PCB and all parts as shown.

KIT REF 815

Including headphones

£45.95

## SUPERHET BROADCAST RECEIVER

EE MAR '90

At last, an easy to build SUPERHET A.M. radio kit. Covers Long and medium Wave bands, built in loudspeaker with 1 watt output. Excellent sensitivity and selectivity provided by ceramic I.F. filter. Simple alignment and tuning without special equipment. Kit available less case, or with pre-cut and drilled transparent plastic panels and dial for a striking see-through effect.

KIT REF 835

£17.16





# EVERYDAY ELECTRONICS

INCORPORATING ELECTRONICS MONTHLY

VOL. 21 No. 8

AUGUST '92

## SOLAR ECLIPSE

As regular readers will know we tend to use some unusual illustrations on our front cover and, as you can see, this month is no exception. The illustration by Steven Hunt is of a solar eclipse, it is particularly relevant to this month's magazine because this issue contains the first part of our *Alternative Energy* series.


When you read the series you will quickly realise the importance of the sun in relation to all forms of energy except nuclear power. Man has only very recently managed to produce controlled nuclear fusion – the process which makes the sun work. Although this “clean” method of generating power probably has the greatest potential it is still in its infancy and we are possibly 50 years away from a fusion power station, the use of which might eventually eclipse the power the sun has provided.

We all tend to use power without very much thought about how it is generated and I guess few people are aware of all the methods now used around the world for power generation. Our series will give an overview and some hints on what might develop.
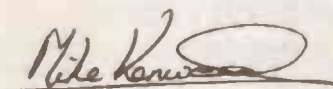
## FREE LIGHT

Perhaps the above side heading is a little misleading, as we all know there is no such thing as a “free lunch”, however our *Solar Powered Lighting Unit* will provide virtually free light once you have paid to build it. It does show in its own small way what can be achieved for a relatively small outlay.

On a larger scale the sun is being used in the U.S.A. to generate considerable amounts of power – but just one power station can contain up to 1.5 million mirrors to generate 150MW of power – not quite an EE project! By the way, it takes a 20 man team 10 days just to clean all the mirrors.



## SUBSCRIPTIONS

Annual subscriptions for delivery direct to any address in the UK: £18.50. Overseas: £23 (£40.50 airmail). Cheques or bank drafts (in £ sterling only) payable to Everyday Electronics and sent to EE Subscriptions Dept., 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: 0202 881749. Subscriptions start with the next

available issue. We accept Access (MasterCard) or Visa payments, minimum credit card order £5.

## BACK ISSUES

Certain back issues of EVERYDAY ELECTRONICS are available price £1.80 (£2.30 overseas surface mail) inclusive of postage and packing per copy – £ sterling only please, Visa and Access (MasterCard) accepted, minimum credit card order £5. Enquiries with remittance, made payable to Everyday Electronics, should be sent to Post Sales Department, Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH Tel: 0202 881749. In the event of non-availability one article can be photostatted for the same price. *Normally sent within seven days but please allow 28 days for delivery. We have sold out of Jan, Feb, Mar, Apr, June, Oct, & Dec. 88, Mar & May 89 & Mar 90.*

## BINDERS

Binders to hold one volume (12 issues) are available from the above address for £5.95 (£6.95 to European countries and £8.00 to other countries, surface mail) inclusive of post and packing. *Normally sent within seven days but please allow 28 days for delivery.*

Payment in £ sterling only please. Visa and Access (MasterCard) accepted, minimum credit card order £5. Tel: 0202 881749

## Editorial Offices:

EVERYDAY ELECTRONICS EDITORIAL,  
6 CHURCH STREET, WIMBORNE,  
DORSET BH21 1JH

Phone: Wimborne (0202) 881749

Fax: (0202) 841692. DX: Wimborne 45314.

See notes on Readers' Enquiries below – we regret that lengthy technical enquiries cannot be answered over the telephone.

## Advertisement Offices:

EVERYDAY ELECTRONICS ADVERTISEMENTS,  
HOLLAND WOOD HOUSE, CHURCH LANE,  
GREAT HOLLAND, ESSEX CO13 0JS.

Phone/Fax: (0255) 850596

Editor: MIKE KENWARD

Secretary: PAMELA BROWN

Deputy Editor: DAVID BARRINGTON

Business Manager: DAVID J. LEAVER

Editorial: WIMBORNE (0202) 881749

Advertisement Manager:

PETER J. MEW, Frinton (0255) 850596

Classified Advertisements:

Wimborne (0202) 881749

## READERS' ENQUIRIES

We are unable to offer any advice on the use, purchase, repair or modification of commercial equipment or the incorporation or modification of designs published in the magazine. We regret that we cannot provide data or answer queries on articles or projects that are more than five years old. Letters requiring a personal reply must be accompanied by a stamped self-addressed envelope or a self addressed envelope and international reply coupons.

All reasonable precautions are taken to ensure that the advice and data given to readers is reliable. We cannot however guarantee it and we cannot accept legal responsibility for it.

## COMPONENT SUPPLIES

We do not supply electronic components or kits for building the projects featured, these can be supplied by advertisers.

We advise readers to check that all parts are still available before commencing any project in a back-dated issue.

We regret that we cannot provide data or answer queries on projects that are more than five years old.

## ADVERTISEMENTS

Although the proprietors and staff of EVERYDAY ELECTRONICS take reasonable precautions to protect the interests of readers by ensuring as far as practicable that advertisements are *bona fide*, the magazine and its Publishers cannot give any undertakings in respect of statements or claims made by advertisers, whether these advertisements are printed as part of the magazine, or are in the form of inserts.

The Publishers regret that under no circumstances will the magazine accept liability for non-receipt of goods ordered, or for late delivery, or for faults in manufacture. Legal remedies are available in respect of some of these circumstances, and readers who have complaints should first address them to the advertiser.

## TRANSMITTERS/BUGS/TELEPHONE EQUIPMENT

We would like to advise readers that certain items of radio transmitting and telephone equipment which may be advertised in our pages cannot be legally used in the U.K. Readers should check the law before using any transmitting or telephone equipment as a fine, confiscation of equipment and/or imprisonment can result from illegal use. The laws vary from country to country; overseas readers should check local laws.



# GAS ALARM

ROBERT PENFOLD

*Will detect the build-up of fuel gas plus many other types of inflammable gasses and vapours. It will also detect many types of smoke*

**G**AS ALARMS are designed to detect inflammable gases and vapours before a dangerous concentration is reached. They are much used in boats and caravans, but can be utilized anywhere that is equipped with gas appliances, or where inflammable vapours could build up.

Most gas alarms, including this one, will detect all normal fuel gases, plus many other types of inflammable gas and vapour. This includes many types of smoke, and the unit will therefore operate as a fire alarm as well (but possibly less effectively than a purpose designed fire alarm). Although this device is designed to operate from the mains supply, it can be modified to operate from a 12 volt d.c. supply.

## GAS SENSOR

Smoke detectors operate using a variety of methods, including simple optical methods of detection. In this case it is not just inflammable smoke that must be detected, but fuel gases as well. These are mostly transparent, and will not be detected using simple methods such as optical detectors. Detection of fuel gases requires special sensors using quite sophisticated techniques.

Gas detectors of this type are usually based on a heating element with a special coating. With some sensors the heating element oxidises due to a reaction with

oxygen in the air, and has a high resistance. However, in the presence of inflammable gases a process known as reduction takes place, which means that the oxygen is to some extent removed from the heating element, causing its resistance to decrease.


This type of sensor has been much used in gas detectors for the home constructor in the past, but this unit uses an alternative (and now more readily available) form of sensor. This type of gas sensor has the usual heating element, but it is made from fine platinum wire coated with oxides and a catalyst.

The element normally heats to approximately 350 degrees Centigrade, but if a suitable gas is present oxidation takes place. This, together with the rise in temperature that occurs, results in a rise in resistance through the sensor.
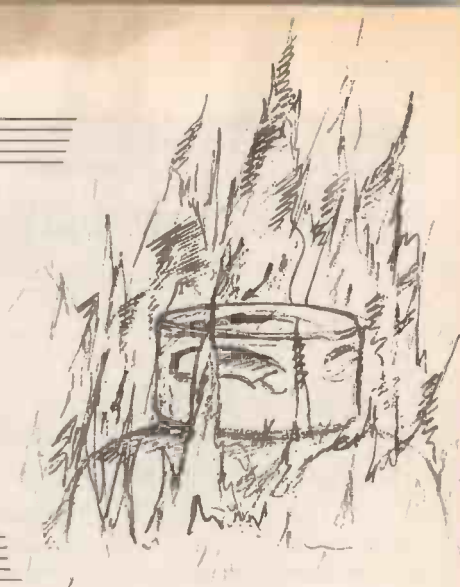
## SYSTEM OPERATION

The block diagram for the Gas Alarm project is shown in Fig. 1. The sensor is connected in a bridge circuit. One side of the bridge merely consists of a potential divider circuit which provides a "reference voltage" to one input of a voltage comparator circuit.

The other side of the bridge consists of another potential divider. This is formed by



the two resistances provided by the Sensor and a Compensating Element. The latter is very similar to the sensor, having an identical platinum wire element. The coating is different though, and it will not respond to inflammable gasses. The point of having the compensation element is that over a period of time the resistance through the sensor might change slightly due to changes in the ambient temperature, humidity, etc.

Any changes of this type should affect both the sensor and the compensation element almost equally, giving no change in the output voltage from that side of the bridge. This helps to avoid false alarms.

The use of a bridge circuit also helps to avoid spurious operation of the unit. If there should be a slight change in the supply voltage (which there will inevitably be over a period of time), it will affect both sides of the bridge circuit, and will not cause a false alarm.

Normally the output voltage from the sensor arm of the bridge is higher than that from the reference voltage side. This is detected by the voltage comparator, and its output goes to a very low voltage. When the unit is activated the sensor's resistance increases, and the output voltage from that arm of the bridge circuit falls below the reference voltage. This is detected by the voltage comparator, and its output triggers to virtually the full supply voltage.


The output of the comparator operates an electronic switch, which turns on an audible alarm circuit when the unit is activated. The alarm signal is a frequency modulated tone which is smoothly swept up and down in frequency at a rate of a little over one cycle per second.

The basic audio signal is generated by a v.c.o. (voltage controlled oscillator). The operating frequency of this circuit is controlled by a voltage which is provided by a low frequency oscillator (l.f.o.). As the output voltage from the latter rises and falls, so does the pitch of the output from the v.c.o. This gives an effective alarm signal that is not easily overlooked.

## CIRCUIT OPERATION

The full circuit diagram of the Gas Detector, including the stabilised mains power supply, is shown in Fig. 2. The circuit requires a 12V supply, and the current consumption is about 400 milliamps. This is predominantly the current consumed by the sensor and compensation element. The rest of the circuit consumes just a few milliamps.

Fig. 1. The Gas Detector block diagram. The compensation element is a sort of "dummy" sensor.

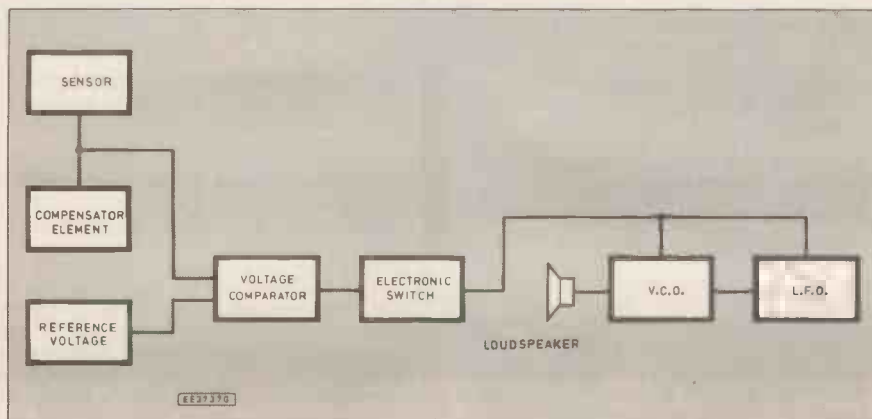



The power supply is a conventional type having full-wave bridge rectification provided by diodes D1 to D4, and smoothing supplied by capacitor C1. IC1 provides a well regulated and smoothed 12 volt output.

The sensor and compensation element require a total supply voltage of only about 2.2V. This is derived from the main 12 volt supply using a simple dropper circuit based on transistor TR1. This is just a potential divider circuit (resistors R1 to R3) and an emitter follower buffer stage to provide the fairly high currents required by the sensor and compensation elements.

Transistor TR1 is a power Darlington device which can comfortably accommodate the current and power levels involved here. Due to its very high gain it can operate properly from the low input current available from R1 to R3.

Preset potentiometer VR1 provides the reference voltage, and this is adjusted to give an output potential that is just below the level produced by the sensor circuit. IC2 is an operational amplifier which is connected to operate as a voltage comparator. Resistor R6 provides a small amount of hysteresis which helps to avoid "jitter" when the circuit is close to the trigger level. Transistor TR2 is the electronic switch, and this is an emitter follower buffer stage.

The v.c.o. is based on IC3, which is actually a "micro-power" CMOS phase locked loop (p.l.l.). In this case it is only the

It is over this frequency range that the "Siren" LS1 offers peak efficiency. Note that LS1 is a piezoelectric sounder and not a normal moving coil loudspeaker. A moving coil loudspeaker, even a high impedance type, is unsuitable for operation in this circuit.

### LOW FREQUENCY OSCILLATOR

A low power 555 timer, IC4, acts as the l.f.o. The roughly squarewave output from pin 3 of IC4 is of no use in this case as it would simply switch the v.c.o. between two frequencies. This can give quite an effective alarm signal, but the two frequencies might happen to be ones where the Piezo-sounder is not very efficient.

Sweeping the v.c.o. frequency ensures that the sounder is driven at its frequencies of peak efficiency for at least part of the time, giving a loud alarm signal. The waveform across capacitor C6 is a sort of slightly rounded triangular shape, and this gives a good sweep effect. The signal across C6 is at a high impedance, but this does not matter as the control input of IC3 has an extremely high input impedance.

### LOW VOLTAGE OPERATION

For operation on a 12V supply the mains power supply components (T1, S1, D1-D4, C1-C3, FS1, and IC1) can all be omitted. The 12V d.c. supplies in boats, caravans,

## COMPONENTS

### Resistors

R1	2k2
R2	220
R3	1k
R4, R5	1k5 (2 off)
R6	560k
R7	150k
R8	10k
R9	1M

All 0-25W 5% carbon film

### Potentiometer

VR1	4k7 sub-min horizontal preset, lin.
-----	-------------------------------------

### Capacitors

C1	470µ radial elect., 25V
C2, C3	100n ceramic (2 off)
C4	1µ radial elect., 63V
C5	10n polyester
C6	330n polyester

### Semiconductors

D1-D4	1N4002 100V 1A rect (4 off)
TR1	TIP121 npn power Darlington
TR2	BC549 npn silicon
IC1	µA7812 12V 1A reg.
IC2	CA3140E CMOS op. amp
IC3	4046BE CMOS phase locked loop
IC4	TLC555CP low power timer

See  
**SHOP  
TALK**  
Page

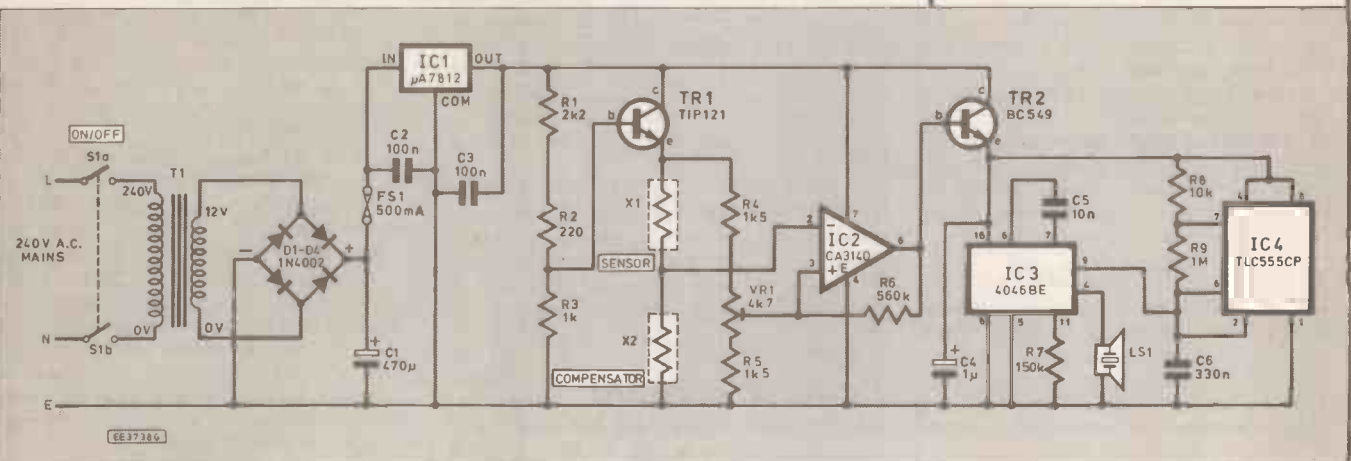


Fig. 2. The complete circuit diagram for the Gas Alarm. The detector elements are mounted on the front panel (see photograph below) together with the warning siren.

v.c.o. section that is required. The phase comparators, stabiliser circuit, etc., are simply ignored.

Resistor R7 and Capacitor C5 are the timing components. These have been chosen to give an operating frequency range that covers the middle audio range.

etc. are generally somewhat higher than their nominal 12 volt level, and often contain a lot of noise. It is therefore advisable to add a 100µ 16V electrolytic capacitor across the supply rails.

### Miscellaneous

LS1	Panel mounting piezo sounder
S1	Rotary mains switch
FS1	20mm 500mA quick-blow fuse
T1	12V 500mA secondary, mains primary
X1, X2	Matched pair of gas detector and compensator transducers

Printed circuit board, available from EE PCB Service, code EE800

Metal instrument case, size 230mm x 130mm x 65mm; 20mm p.c. mounting fuse-clips; control knob; 18s.w.g. aluminium for heatsinks; 8-pin d.i.l. socket (2 off); 16-pin d.i.l. socket; mains lead and plug; solder tag; solder pins; connecting wire; solder; etc.

Approx cost  
guidance only

**£30**



Also, a 500 milliamp fuse, a 2Ω 2W resistor, and an s.p.s.t. on/off switch should be added in series with the positive supply lead.

### CONSTRUCTION

Details of the printed circuit board component layout, full size copper foil master pattern and interwiring are shown in Fig.3. This board is available from the *EE PCB Service*, code EE800. Construction of the board is very straightforward as it is single-sided and free from link wires.

All the d.i.l. integrated circuits are CMOS types, although IC4 has built-in protection circuitry which renders the normal handling precautions unnecessary. Nevertheless, it is still recommend that holders should be used for all three d.i.l. integrated circuits.

IC4 can be any low power 555 timer (TLC555CP, ICM7555, etc.). An ordinary 555 timer might be satisfactory, but could give rather erratic results. A low power version seems to give more reliable results in this application. Note that IC4 has the opposite orientation to IC2 and IC3.

Fuse FS1 is mounted on the board via a pair of 20 millimetre fuse-clips. A 20 millimetre printed circuit mounting fuseholder should also be suitable, but might require a slightly different mounting hole arrangement.

### HOT SPOT

Components IC1 and TR1 have to dissipate about 1.5W and 3.8W respectively.

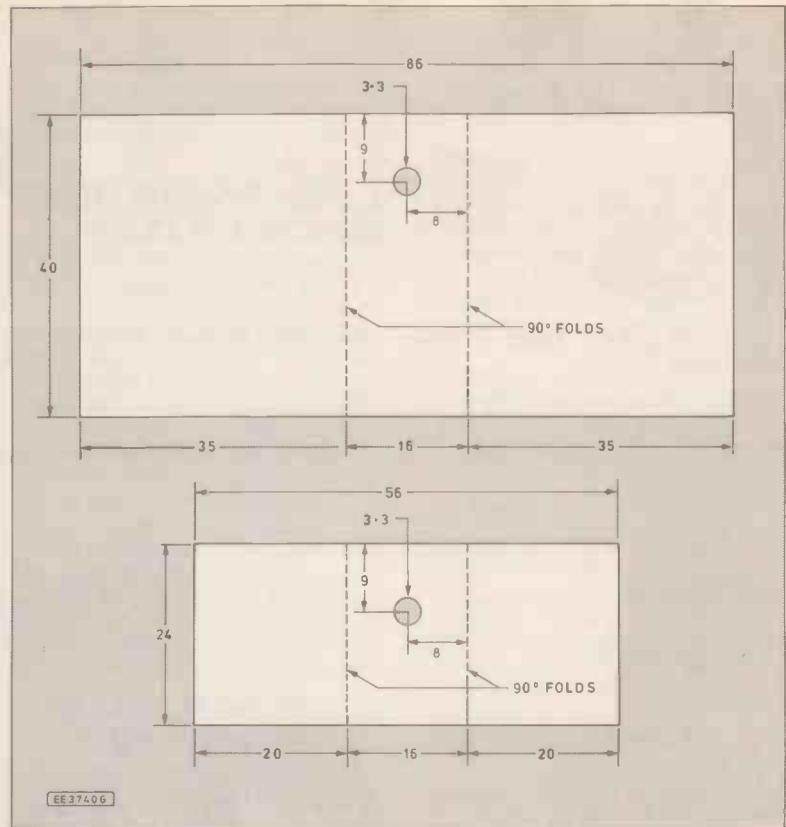


Fig. 4. Suitable heatsink designs for power Darlington transistor TR1 (top) and regulator IC1 (bottom). Dimensions in millimetres.


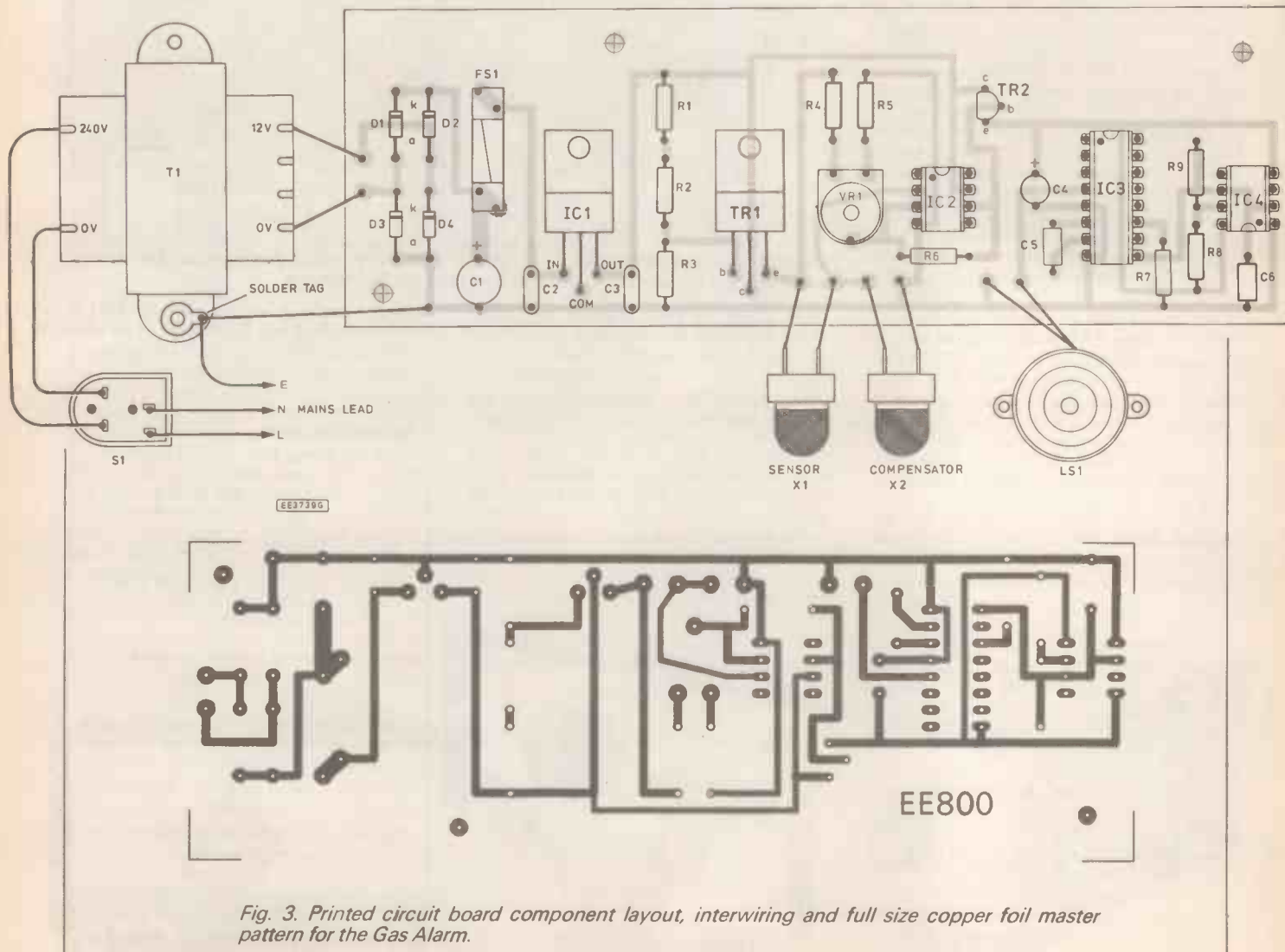


Fig. 3. Printed circuit board component layout, interwiring and full size copper foil master pattern for the Gas Alarm.

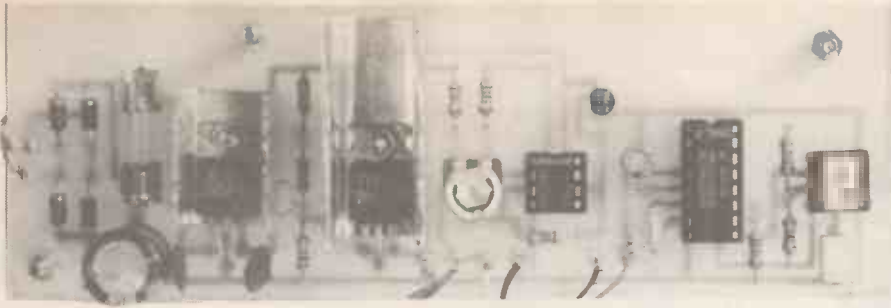



The completed circuit board showing the two heatsinks clamped to the semiconductors.

They can only do this with the aid of heatsinks. As the dissipation figures are not very high, there is no need for any large or elaborate heatsinks. The small ready made type for TO-220 and similar devices will suffice provided there is sufficient space on the board (some have bigger "footprints" than others).

Alternatively, "U" shaped heatsinks can be fabricated by the constructor from 18s.w.g. or 16s.w.g. aluminium. The thicker (16s.w.g.) grade is preferable for this type of thing, but 18 s.w.g. aluminium is much easier to work. Suitable heatsink designs are provided in Fig.4 (the larger one is for TR1).

It is advisable to use a smear of heatsink compound or a substitute to ensure that there is a good thermal contact between each heat-tab and its heatsink. Note that these heatsinks represent about the minimum that will prevent TR1 and IC1 from overheating. The heatsinks are bolted in place using M3 nuts and bolts, and it is a good idea to bolt the heatsink and transistor or integrated circuit to the board so that everything is securely held in place.

An alternative method of heatsinking is to mount TR1 and IC1 off-board, and to hard wire them to the board. They can then be mounted directly on the metal case, or on the case via a simple "L" shaped mounting bracket if preferred. This will provide them with a substantially more than adequate degree of heatsinking, but is a less neat solution.

If this method is adopted it is essential that transistor TR1 should be fitted with an insulating kit. Otherwise the +12 volt supply carried by its heat-tab will short circuit to the case which is at the 0V supply level. Use a continuity tester to make sure that the insulation is fully effective. The tab of IC1 is at the 0 volt supply level, and therefore this device does not require an insulating kit.

## CASE


A metal instrument case about 220 millimetres or more wide and 65 millimetres or more high should comfortably accommodate all the parts. The front panel layout has (from left to right) switch S1, the Sensor, the Compensating Element, and Sounder LS1 mounted in a neat line. A hole for the mains lead is drilled in the rear panel opposite S1, and this should be fitted with a grommet to protect the cable.

The sensor and the compensation element look much the same, but they have coloured dots so that you can tell which is which. The compensation element has a blue spot, while the sensor will probably have two or three spots of different colours.

There is no obvious means of panel mounting these two components, and matching panel holders do not seem to be available. Simply drill holes about three

millimetres in diameter to take their pin-type terminals, and then glue them on the panel using an epoxy adhesive. With this method you must make sure that none of the pins short circuit to the metal case.

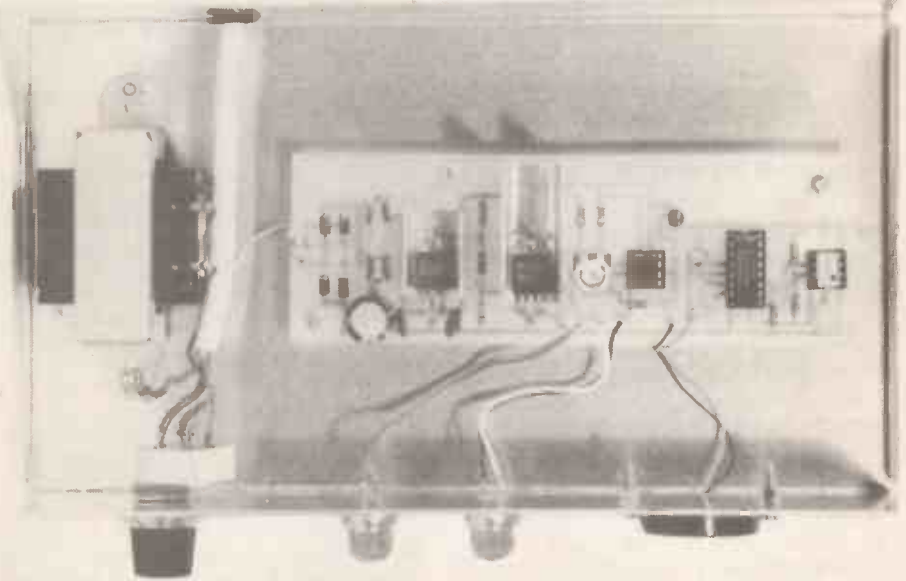The sounder LS1 is easier to deal with if it is mounted on the front surface of the



Layout of components inside the metal case. The mains transformer and switch connecting tags should be covered with insulating sleeving.

front panel. It then requires two small mounting holes for the fixing screws, and one to permit the flying leads to pass through to the interior of the case. Use LS1 as a template when marking the positions of these holes on the panel.

The mounting holes in LS1 are for very small screws (8BA or similar). It might be better to carefully enlarge the holes slightly so that bigger mounting screws (6BA or similar) can be used.

The printed circuit board is mounted on the base panel of the case well towards the right hand side, leaving plenty of space for transformer T1 to its left. A solder tag is mounted on one of T1's mounting bolts to provide an "earthing" point for the mains Earth lead. For safety reasons the case

MUST be earthed to the earth lead of the mains cable.

The small amount of point-to-point wiring is also included in Fig. 3, and this is all pretty simple. However, with any mains powered circuit you must take extra care to get everything right. Also, make sure that all the soldered joints are of good quality, and perfectly reliable.

## TESTING AND USE

To set up the Gas Alarm, start with preset VR1 and set it at a roughly the middle of its adjustment range. At switch-on the alarm generator may be activated, but do not worry if it is not. You should find that the alarm can be switched on and off by adjusting VR1 in a clockwise and a counter-clockwise direction respectively. If adjustment of VR1 does not have the desired effect, switch off immediately and recheck all the wiring.

Assuming that all is well, leave the unit for a few minutes to fully warm up and for

the d.c. levels to stabilise. Preset VR1 is then backed-off just far enough in an anti-clockwise direction to switch off the alarm. The unit is then ready for use.


The unit can be tested by subjecting it to a localised dose of inflammable gas or vapour. You should obviously take due care when doing this, but the gauze coverings on the sensor and compensation element should ensure that their heating elements cannot ignite the gas or vapour.

When the prototype was tested it even responded to fumes from a spirit based cleaning fluid, and to turpentine vapour. It will probably respond to just about anything inflammable in the atmosphere, and at concentrations below the level at which there is any risk of ignition. □



# CIRCUIT SURGERY

MIKE TOOLEY B.A.

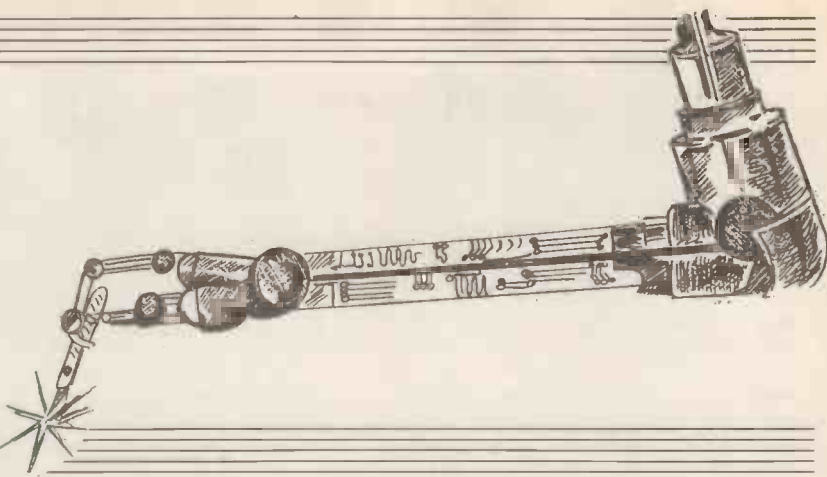

Welcome again to *Circuit Surgery*, our regular clinic for readers' problems. In this month's *Surgery* we shall be describing an improved low-battery warning indicator based on an operational amplifier. We also answer a query concerning the use of BNC coaxial connectors and illustrate the "definitive" method for terminating a standard "TV aerial connector". For good measure, we have also included a simple BASIC computer program which can be used to design astable and monostable 555 timer circuits.

## Improved Battery Warning

A number of readers have sent in comments and suggestions concerning the low-battery warning indicator which was described in the June *Surgery*. One of the principal disadvantages of this circuit is the lack of any pre-set adjustment to determine the threshold of voltage at which the unit illuminates the l.e.d.

Jim Forester, a regular EE reader, has suggested that an improved low-battery warning indicator could be based on the comparator arrangement shown Fig. 1. I have taken this idea to heart and the resulting circuit is shown in Fig. 2. This circuit provides a very much more definite switching action as the threshold voltage is reached and can provide useful indications for battery supply voltages of between 6V and 15V (by means of an appropriate setting on VR1).

A further possibility is shown in Fig. 3. This circuit uses a low-cost piezo-electric transducer to provide an audible (rather than visual) indication that the battery is about to fail. The additional transis-

tor, TR1, provides the extra current drive (up to 100mA) which may be required by certain larger transducers. Small p.c.b. mounted transducers, on the other hand, will normally require currents of no more than around 15mA to 20mA. In such cases, R4 and TR2 can both be omitted and the transducer can simply replace D2 and R3 in the circuit of Fig. 2.

## Coaxial Connectors

Alan Brown writes from Wrexham to ask for some clarification concerning the selection of coaxial connectors for r.f. and test equipment. Alan writes:

"I have a number of items of test equipment which use BNC-type connectors. These all seem to be 50 ohm types but I understand that 75 ohm BNC connectors are also available. Does this rating actually matter and could you also tell me what advantages BNC connectors offer when compared with alternative types."

Well Alan, this is an interesting question which will require a fairly lengthy answer to really do justice to it! BNC connectors seem to have become universally fitted to

most items of "quality" test equipment. Such equipment includes oscilloscopes, r.f. and pulse generators, wideband voltmeters, etc.

BNC connectors are designed to preserve a constant impedance (either 50 ohms or 75 ohms depending upon the series) within a system based on coaxial (screened) cables. The connectors are locked into place by means of a simple but effective bayonet locking action. BNC connectors are rated for operation at peak voltages of up to 500V and at frequencies up to 4GHz. This makes them ideal for wideband and r.f. applications at v.h.f. and u.h.f.

The 50 ohm BNC series is commonly used for general purpose test equipment, r.f. signal generators, and for the aerial connection to v.h.f. and u.h.f. transceivers. The 75 ohm series is invariably used with video equipment such as cameras, monitors and waveform generators.

The 50 ohm and 75 ohm series are identical save for one vitally important difference; the diameter of the terminating pins and their matching receptacles. The 50 ohm inner terminating pin is noticeably

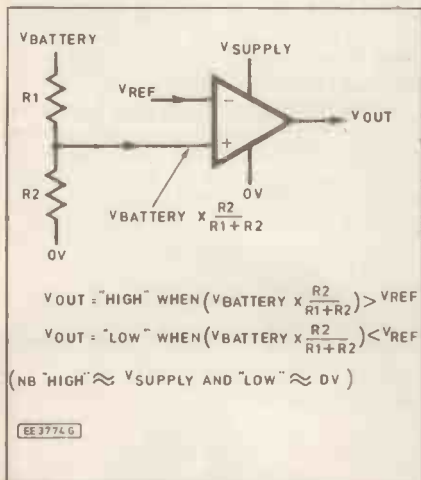


Fig. 1. Basic principle of the improved low-battery indicator.

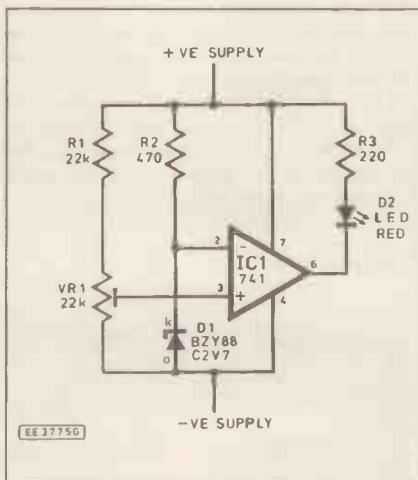


Fig. 2. Improved low-battery indicator with l.e.d. output NB: Values shown are for 6V to 9V operation. For 9V to 15V operation, R2 = 1k and R3 = 330.

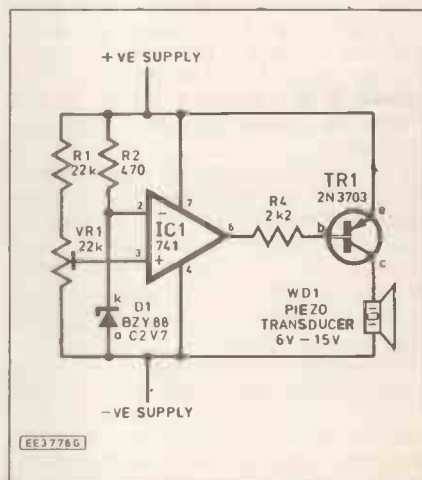


Fig. 3. Improved low-battery indicator with audible output (NB: Values shown are for 6V to 9V operation. For 9V to 15V operation, R2 = 1k).



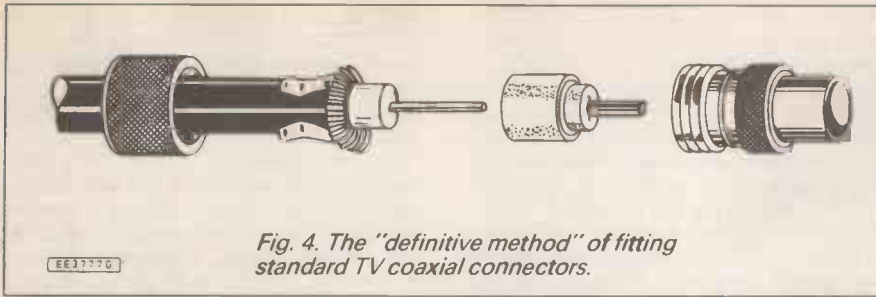


Fig. 4. The "definitive method" of fitting standard TV coaxial connectors.

larger in diameter than its 75 ohm counterpart and hence it is inadvisable to attempt to mate a 50 ohm plug with a 75 ohm socket!

Impedances (either 50 ohm or 75 ohm) are now generally marked on the outside of the body of individual BNC connectors. Alternatively, manufacturers' part numbers are invariably different for 50 ohm and 75 ohm variants of each connector type.

In conclusion, BNC connectors are an excellent choice for test equipment on both mechanical and electrical grounds. For some applications they can, however, be a little expensive and it may be worth considering alternative connector types for less critical applications. Finally, it is worth making sure that you don't "mix and match" 50 ohm and 75 ohm types!

### Low-cost Coaxial Connectors

Alan Brown's query concerning BNC connectors has prompted me to review my own use of a wide variety of different types of connector within my own workshop. After a quick tour of each item of equipment I discovered no less than nine different types of connector (including BNC, TNC, N-type, SMA, SMB, F-type and the good old "u.h.f./PL-259 series). This awesome muddle is greatly aided by a variety of "inter-series" adapters (without which inter-connection of test gear would be virtually impossible!).

Some years ago as an impecunious student I searched for a readily available coaxial connector which could be fitted to virtually any item of equipment and which would not cost an "arm and a leg". After considering several common types, I settled on the "cheap and cheerful" coaxial "TV aerial connector". This offers reasonably good performance up to 300MHz (with reduced performance to 900MHz), can reliably handle r.m.s. power levels of up to 50W, and costs very much less than any of the alternatives. Furthermore, despite the fact that this type of connector is designed for use with 75 ohm systems the consequence of mis-matching it with 50 ohm cables and terminations is usually quite negligible.

This type of connector was originated by Belling-Lee and is available from most high-street electrical and DIY stores as well as from all of the usual electronic catalogue suppliers. Provided they are of the all-metal soldered variety and are terminated correctly, they can be extremely reliable and mechanically durable.

The connectors are suitable for a wide range of applications (not just r.f.). Indeed, I must confess to having used them as a low-cost alternative to BNC connectors on a number of occasions (including some test gear and audio equipment).

Unfortunately, few people seem to know how this common type of connector should be fitted and this often gives rise to problems. Indeed, I never cease to be

amazed at the peculiar attempts that people make at fitting them. To put the record straight, Fig. 4 shows the "definitive method" (note that the outer braid is trimmed, then fanned out and effectively trapped (without soldering) between collar/cable-grip and the inner plastic insulator. After tightening, the outer braid is firmly locked and solder should be carefully run into the centre pin before trimming the inner conductor.

### The 555 Timer

Lawrence Inwood has written to point out a problem in our 1991 *Teach-In*. Regular readers will doubtless recall that this series was entitled *Design Your Own Circuits* and Part 6 was devoted to Timers. Lawrence writes:

*"I find the 555 timer to be one of the most useful of all integrated circuit devices and have used it for everything from timing an egg to generating accurate pulse waveforms. I do find the maths a bit difficult to grasp and thus very much welcomed the two nomographs which were provided in the article.*

*Unfortunately I have not been able to make much sense of the astable nomograph - the values it suggests give rise to a 2:1 error in operating frequency. Can you help?"*

Thanks for pointing this out, Lawrence. You have discovered a rather unfortunate error in the heading printed above the right hand column (the resistance axis) of Fig. 6.8. This should read: " $R = R1 + R2$ " not " $R = R1 = R2$ ". Hopefully this will put the matter right and you can now use the nomograph with some confidence!

On a related matter, Andrew Jones (a teacher of GCSE Control Technology) has asked if I can suggest a computer program for designing timer circuits. Andrew writes:

*"We have an 80386SX IBM compatible PC in the classroom and this operates with MS-DOS Version 5. We don't yet have any programming languages but we understand that Microsoft QuickBASIC would do the job. Please suggest how we might go about this as my pupils need to use the PC for their projects (which involve the use of a 555 timer i.c.)."*

Fortunately, this is an easy one! The following listing (written in Microsoft QuickBASIC) should do the job:

```

555 timer circuit designer
' Initialise
ON ERROR GOTO warning
SCREEN 0
COLOR 1, 2, 3
u$ = STRING$(31, CHR$(205))
' Display menu
DO
main:

```

```

CLS
PRINT u$
PRINT "555 TIMER I.C. CIRCUIT
DESIGNER"
PRINT u$; ""
PRINT " Select timer
configuration.."
PRINT "[M] = monostable mode"
PRINT "[A] = astable mode"
PRINT "[Q] = quit"
DO
r$ = UCASE$(INKEY$)
LOOP UNTIL r$ <> "" AND
INSTR("MAQ", r$)
IF r$ = "Q" THEN CLS : END
PRINT u$
IF r$ = "M" THEN GOSUB
monostable
IF r$ = "A" THEN GOSUB astable
LOOP

monostable:
PRINT " Monostable timer
configuration.."
INPUT " Timing period (in ms)"; t
'Recommend a value for c
crec = t / 100
c = INT(1000 * crec) / 1000
PRINT u$
PRINT " Recommended value for the"
PRINT " timing capacitor is";
PRINT USING "###.###"; crec;
PRINT " uF"
PRINT u$
r = 0
WHILE r > 1 * 103 OR r < 1
INPUT " Capacitor value (uF)"; c
r = t / (1.1 * c)
PRINT u$
PRINT " Timing resistor = ";
PRINT USING "#####.#"; r;
PRINT " kohm"
WEND
GOSUB waitkey
RETURN

astable:
PRINT " Astable timer configuration..."
INPUT " Capacitor value (uF)"; c
PRINT u$
PRINT " NB: High time MUST be
greater"
PRINT " than low time..."
PRINT u$
t1 = 0
t2 = 1
WHILE t1 < 1.05 * t2
INPUT " High output time (ms)"; t1
INPUT " Low output time (ms)"; t2
WEND
r2 = t2 / (.693 * c)
r1 = t1 / (.693 * c) - r2
f = 1.44 / ((r1 + (2 * r2)) * c)
PRINT " R1 = ";
PRINT USING "#####.#"; r1;
PRINT " kohm"
PRINT " R2 = ";
PRINT USING "#####.#"; r2;
PRINT " kohm"
PRINT " P.r.f. = ";
PRINT USING "###.###"; f;
PRINT " kHz"
GOSUB waitkey
RETURN

```

Continued overleaf

```
waitkey:
PRINT ul$
PRINT " Press any key to continue..."
DO
  r$ = INKEY$
  LOOP UNTIL r$ <> ""
RETURN
```

```
warning:
PRINT ul$
PRINT " An error has occurred!"
GOSUB waitkey
RESUME main
```

The foregoing program can very easily be adapted for other dialects of the BASIC

language. Many readers will probably be more familiar with GWBASIC than QuickBASIC (supplied with the MS-DOS 5 package) and the program can be very easily modified by simply adding line numbers to the beginning of each statement and replacing the labels (main, monostable, as-table, waitkey and warning) by line numbers followed by a REM statement.

Finally, if any reader would like a copy of the source code for the program together with a fully compiled (.EXE) version, just send a blank formatted disk (either 3½in. or 5¼in.) and a stamped addressed envelope to the address given at the end.

Next month: In next month's Surgery we

shall be attempting to unravel the mystery of the SCART connector. We also have some useful information concerning the selection of fuses for a variety of applications and include a novel circuit for testing inductors.

In the meantime, if you have any comments or suggestions for inclusion in *Circuit Surgery*, please drop me a line at: Faculty of Technology, Brooklands College, Heath Road, Weybridge, Surrey, KT13 8TT. Please note that I cannot undertake to reply to individual queries from readers however I will do my best to answer all questions from readers through the medium of this column.

# EVERYDAY READOUT

## GET CONNECTED

Dear Ed.,

One of our junior members recently built the *Low Cost Capacitance Meter* described in the article by Steve Knight in your Sept 1991 issue. He wrote to me before starting on the project and I was able to supply him with a meter and most of the components he needed. Now I don't imagine your contributor, Steve Knight, uses such a simple piece of equipment to measure capacitance; he is after all an experienced technical writer, and probably has a very well equipped workshop. As I pointed out to our young member, you simply cannot connect most modern capacitors to a pair of terminals as fitted to the meter described.

A long time ago I built the *Digital Capacitance Meter* described by Mark Stuart in EE for December 1985. The illustration of this in EE showed a pair of crocodile clips for connection to the capacitor. I'm no great lover of crocodile clips, which have a tendency to come off at an awkward moment, but they are more practical than terminals, which are also much more expensive.

Just before Christmas I got a new digital multimeter which has capacitance ranges, and this has two four-way socket strips with 0.1 inch spacing, into which you can plug most of the modern small capacitors with short leads. When I built the *EE Digital Capacitance Meter* I fitted such a socket strip to it, with short crocodile clip leads in parallel, and this caters for all types of capacitor. I have had to make an adapter for my new digital capacitance meter in the form of a plug (made from a couple of ordinary pins through a strip of s.r.b.p.) with attached crocodile clip leads to provide the same facility.

As you know, I always look critically at projects to see where one can cut costs, and I also look at them from the point of view of the user rather than the designer, who may overlook some of the practical problems of the constructor and user.

Before I took over the running of the B.A.E.C. I used to write for the Newsletter articles under the heading *Notes from an Experimenter's Workshop*, which you may have come across in the copies Cyril Bogod sent you. The idea was to pass on to beginners and others some of the practical experience gained over a lifetime of electronic experimenting; one doesn't get enough of this in any of the electronic magazines nowadays, although I know you publish articles by Robert Penfold entitled *Actually Doing It*. However, he builds most of his projects on breadboards, and I deduce from his writing (and I think he would probably agree) that his skills are stronger on the electronic than on the mechanical construction side. There is a lot of useful stuff in George Hylton's *Down to Earth* articles.

I can't help feeling that some project builders would benefit by spending less on components and more on tools, and take time to get experience in their use. But I recognise that finding workshop space in the average modern house can present problems - to put it mildly. One would hope that with the growing importance of technology as a school subject the number of people with the ability to design equipment and use tools would steadily increase.

I suppose one must recognise that ancient practitioners of the electronic art, like me, who were building projects long before

the p.c.b. and kit era, involving chassis bashing and other workshop skills, may feel that present day project builders find the hobby rather easier, but possibly less interesting and more expensive.

H. F. Howard  
Chairman, B.A.E.C.

The B.A.E.C. is a non-profit making club for everyone interested in electronics. We carry a small advertisement for the club (space donated by EE) in most issues, you can find this on the Classified Advertisement page.

## COMPUTER MALFUNCTION

Dear Ed.,

In reply to J. Conners of Cambridge, *Everyday Readout*, July, and his problem with computer malfunction. Unless he lives close to a powerful radio or radar transmitter, an airport for example, or he has an industrial site next door, I would advise him to examine his home (or neighbours) environment as almost all mains interference is generated in house so to speak.

Bearing in mind that the only items of electrical equipment which are not generators of interference are the tungsten filament light bulb, squirrel cage induction motors and static transformers, I would first of all check all my appliances for correct functioning and rectify faults or junk dicey looking items.

Thermostats, even those in good condition, are great voltage spike generators so on days he runs his computer he should send his wife home to mum to do the family ironing and switch off the immersion heater.

Portable mains filters are a good idea, three-pin plug-in types being available either in top of the range items such as supplied by Kleanpower of Oxon, or four-way filtered sockets such as are made by MK.

R. Whitaker  
Halifax

## WRITE IN

If you have a point to make or problem to air why not write to *Everyday Readout* at 6 Church Street, Wimborne, Dorset BH21 1JH




IMPORTS **EASY PC FILES**  
UPGRADE DISCOUNT AVAILABLE
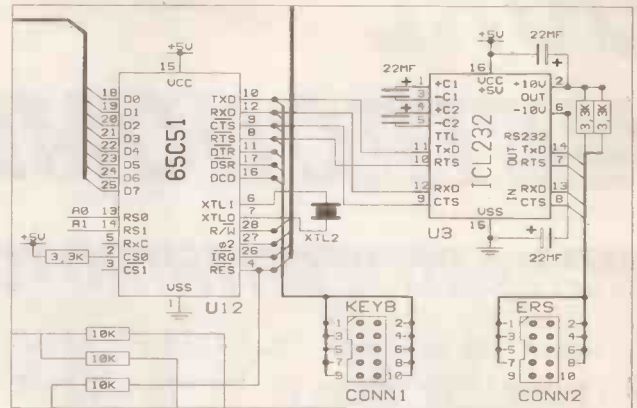
## Finally...an exceptional PCB and Schematic CAD system for every electronics engineer!

**B**oardMaker 1 is a powerful software tool which provides a convenient and professional method of drawing your schematics and designing your printed circuit boards, in one remarkably easy to use package. Engineers worldwide have discovered that it provides an unparalleled price performance advantage over other PC-based systems.

BoardMaker 1 is exceptionally easy to use - its sensible user interface allows you to use the cursor keys, mouse or direct keyboard commands to start designing a PCB or schematic within about half an hour of opening the box.



Produce clear, professional schematics for inclusion in your technical documentation.

### HIGHLIGHTS

#### Hardware:


- IBM PC, XT, AT or 100% compatible.
- MSDOS 3.x.
- 640K bytes system memory.
- HGA, CGA, MCGA, EGA or VGA display.
- Microsoft or compatible mouse recommended.

#### Capabilities :

- Integrated PCB and schematic editor.
- 8 tracking layers, 2 silk screen layers.
- Maximum board or schematic size - 17 x 17 inches.
- 2000 components per layout. Symbols can be moved, rotated, repeated and mirrored.
- User definable symbol and macro library facilities including a symbol library editor.
- Graphical library browse facility.
- Design rule checking (DRC) - checks the clearances between items on the board.
- Real-time DRC display - when placing tracks you can see a continuous graphical display of the design rules set.
- Placement grid - Separate visible and snap grid - 7 placement grids in the range 2 thou to 0.1 inch.
- Auto via - vias are automatically placed when you switch layers - layer pairs can be assigned by the user.
- Blocks - groups of tracks, pads, symbols and text can be block manipulated using repeat, move, rotate and mirroring commands. Connectivity can be maintained if required.
- SMD - full surface mount components and facilities are catered for, including the use of the same SMD library symbols on both sides of the board.
- Circles - Arcs and circles up to the maximum board size can be drawn. These can be used to generate rounded track corners.
- Ground plane support - areas of copper can be filled to provide a ground plane or large copper area. This will automatically flow around any existing tracks and pads respecting design rules.
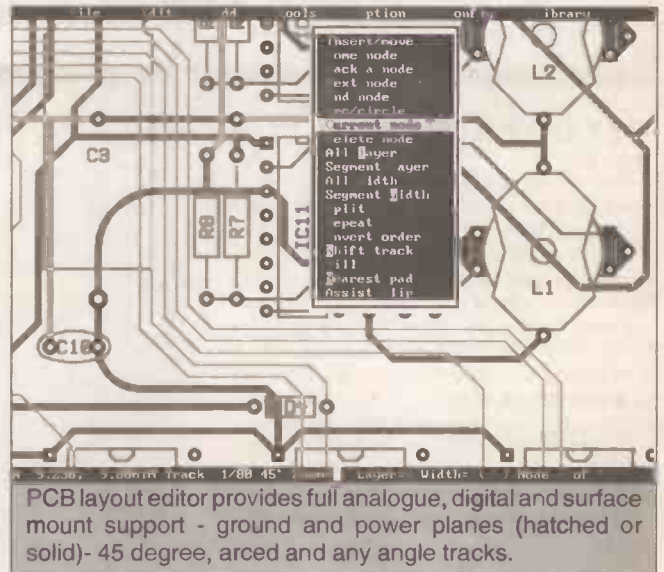
#### Output drivers :

- Dot matrix printer
- Compensated HP laser printer
- PostScript output.
- Penplotter driver (HPGL or DMPL).
- Photoplot (Gerber) output.
- NC (ASCII Excellon) drill output.



£95

Despite its quality and performance, BoardMaker 1 only costs £95.00. Combine this with the 100% buy back discount if you upgrade to BoardMaker 2 or BoardRouter and your investment in Tsien products is assured. Price excludes carriage and VAT.

**Don't take our word for it. Call us today for a FREE demonstration disk and judge for yourself.**




**tsien**

**Tsien (UK) Limited**  
Cambridge Research Laboratories  
181A Huntingdon Road  
Cambridge CB3 0DJ  
Tel 0223 277777  
Fax 0223 277747

All trade marks acknowledged

# DUAL METRONOME

**RICHARD WORTHINGTON**

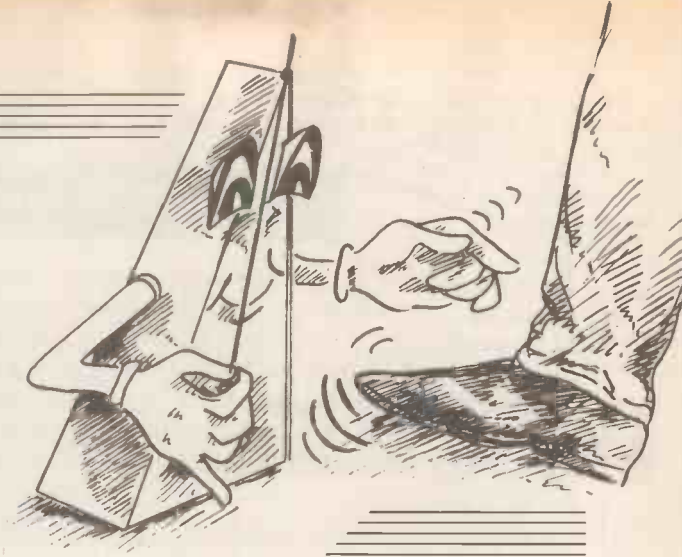

An invaluable teaching aid.  
Tap out that rhythm with this novel timekeeper and hit the high spots!

**T**HIS PROJECT describes a new type of metronome, with features which should prove both useful and convenient.

Conventional designs allow a numerical value of "beats-per-minute" to be selected, and provide a clear, audible time signal – that part remains the same in this design.

This circuit's *principal* feature, however, is that it's also activated by just tapping out the required beat (a piezo sensor detects the pressure pulse from each individual "tap"). Just two taps will define the desired speed, which the circuit measures and instantly "memorises". It then continues to beat time, out loud, at that same rate.

To name just a few examples, this new feature should prove very useful in such applications as:

- A teaching aid.
- When practising difficult music at reduced, but constant speed.
- To pick up the speed of a piece of music from a recording – for guidance when practising that piece.
- To impose a constant speed while practising at, for example, sight-reading.

A "pause" facility is also provided, using a second piezo sensor – tap once to Pause, and once again for normal operation.

## HOW IT WORKS

An outline of the circuit for the Dual Metronome is provided in the block diagram Fig. 1. The two pressure sensors – no more than ordinary, unhoused, piezo elements – each trigger one voltage comparator, thereby controlling the two flip-flops. The first of the flip-flops activates the "Pause" facility; the second directs clock pulses to either one of two 8-bit binary counters, through a 2-way CMOS switch.

One counter acts as the basis for the memory of the circuit, storing a number in the range 0-255 which corresponds to the measured time interval between the "taps". The second counter, together with the binary comparator, use this number when the circuit takes over beating time by itself.

The regular output pulses of the binary comparator briefly trigger the audio tone generator, provided that (a) the Pause facility is off, and (b) the circuit isn't still waiting for the second "tap". The audio tone generator can also be triggered by the "slow oscillator", to obtain a conventional metronome action controlled by potentiometer VR2.

## CIRCUIT DESCRIPTION

The circuit diagram for the Dual Metronome is shown in two sections for convenience, split between Fig. 2 and Fig. 3. The main diagram, Fig. 2 shows half of the total number of i.c.s involved in the circuit. These include op-amps, flip-flops, NAND gates and multiplexers. The memory circuit, illustrated in Fig. 3, makes up the rest of the i.c.s and consists of the counters and 4-bit comparators (IC5 to IC8).


To begin, X1/IC1a/IC2a detect the pressure of each tap, as mentioned earlier. The non-inverting input (pin 3) of op-amp IC1a is biased to half the supply voltage, and preset VR1 is adjusted so that the voltage change generated by tapping sensor X1 results in the op-amp changing state; i.e. it acts as a voltage comparator.

The JK flip-flop IC2a is configured as a T-(or toggle) flip-flop by connecting both the J and K inputs to battery positive. The outputs therefore change state with each incoming clock pulse (and similarly for X3/IC1b/IC2b, which is identical).

Since the SET inputs (pin 7 and pin 9) of both IC2a and IC2b are taken to battery negative (0V), the RESET pulse – generated by C7/R20 at switch-on – ensures that the Q output of each is initially high. Referring to IC2a, this means the Pause facility is switched off and l.e.d. D2 remains unlit.

Turning now to IC2b, its output Q̄ is also high at switch-on and (due to the clock pulses applied to Input 1 of the memory –

Fig. 1. Block diagram for the Dual Metronome. The "conventional" metronome action is controlled by the slow oscillator.

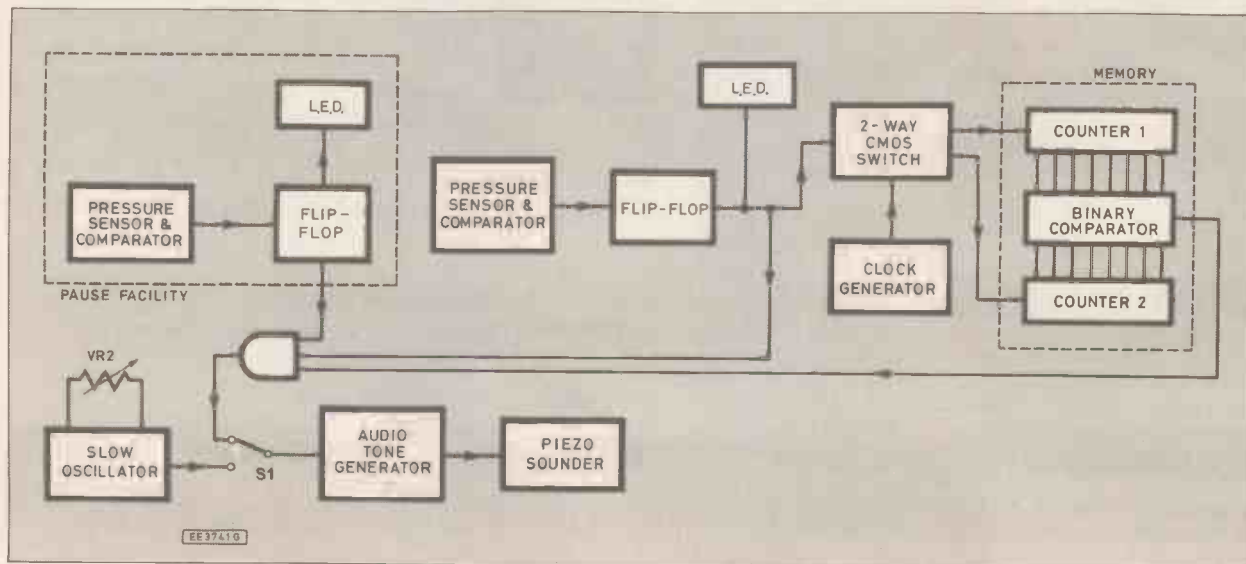



see Fig. 3) Counter 1 is continuously incrementing 0→255, 0→255 ...; initially, the circuit is just silently counting time. Output Q is low, hence i.e.d. D3 (connected to inverter IC4b) is lit, and the output of CMOS switch IC3b is held low by a pull-down resistor R14.

(Note: to minimise numbers of i.c.s, the CMOS switches IC3a and IC3b are used like 2-input AND gates – see Fig. 4a – and op-amp IC1d is used as a simple inverter. The CMOS switches are capable of passing current in both directions, and the chosen arrangement depends only on p.c.b. layout considerations).

Now, if piezo sensor X3 is tapped, flip-flop IC2b changes state as expected. Clock pulses pass instead to Counter 2 (see Fig. 3), via Input 2, and whatever value was on Counter 1 remains stored.

The third oscillator, “the conventional metronome circuit”, uses one of the op-amps of IC1 (LM324). The design is standard, but with diode D1 and resistor R5 to decrease the charge time of capacitor C1.

The voltage across the capacitor C1 is compared with that across resistor R7, produced by the potential divider R7/R8. Rotary potentiometer VR2 sets the frequency of oscillation. The resulting waveform, with a much reduced mark-to-space ratio, is used to control IC4a via switch S1, producing short “bleeps” at a rate of 40-200 beats-per-minute.

## MEMORY AND RESET

The memory section circuit, Fig. 3, of the Metronome is quite straightforward. Each

of the counters consists of two CMOS 4-bit Binary up-counters, with output Q4 of the first (pin 6) connected to the enable input (pin 10) of the second to form an 8-bit counter. The maximum reading is, therefore, binary 11111111 (decimal 255). The “clock” inputs (pins 1 and 9 of IC5 and IC8) are connected to ground (0V) so the counters are triggered on the negative-going transition.

The outputs of the counters are compared by two 4-bit binary magnitude comparators. Each comparator has outputs corresponding to  $A > B$ ,  $A = B$  and  $A < B$ , where A and B are binary numbers. However, the comparators are cascaded and just one overall output,  $A = B$ , is actually used.

The reset circuitry (see Fig. 2) consists of C3/R18/D4, C5/R17/D5 and C6/R19/D6. The first two of these are

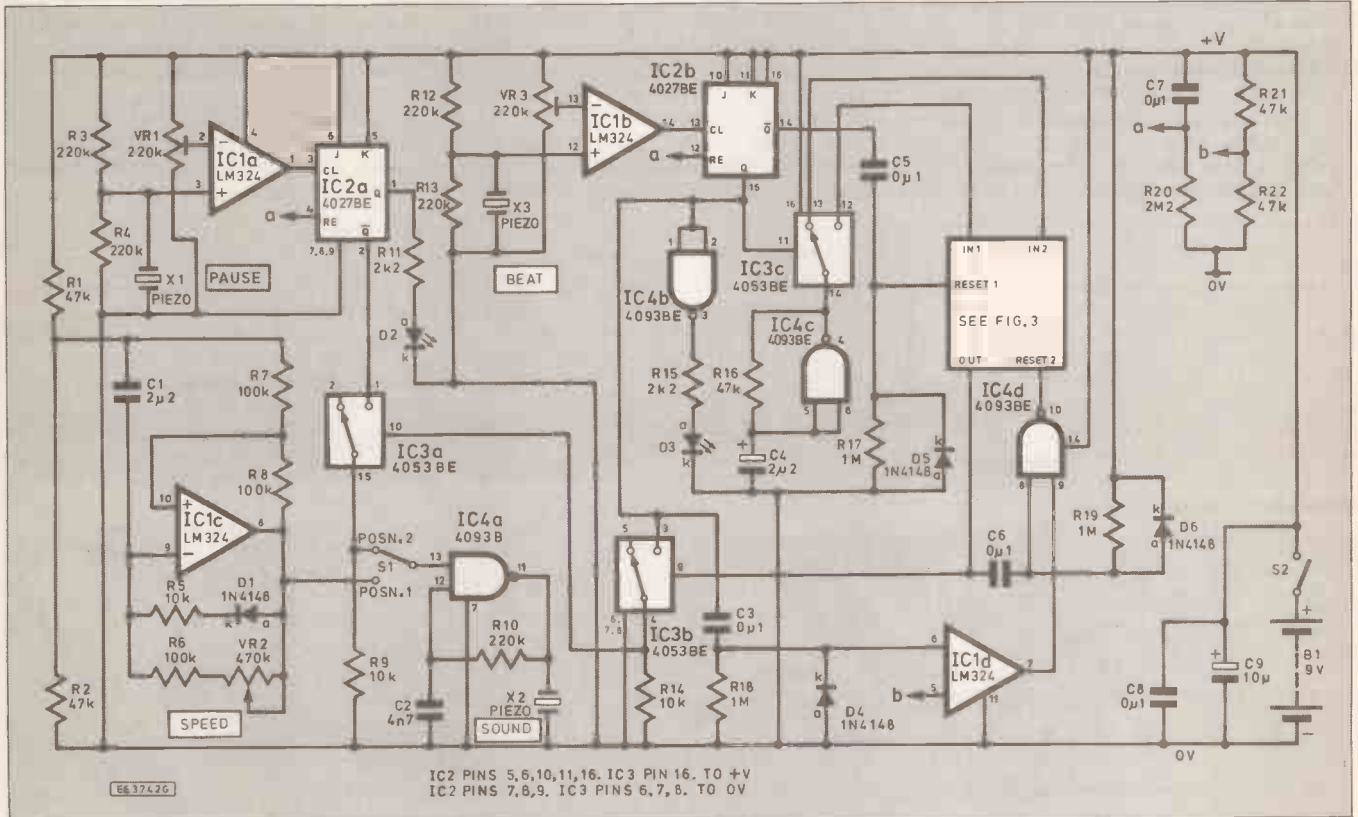


Fig. 2. Main circuit diagram for the Dual Metronome. The rate of the conventional metronome is set by VR2.

Counter 2 now counts up from zero and, whenever the values on the two counters are equal, the overall output (IC7) of the “memory” goes high. The “control” input of CMOS switch IC3a consequently goes high via IC3b and, depending of the state of flip-flop IC2a (i.e. the Pause facility), the audio tone generator IC4a sounds.

Counter 2 continues to increment, however, and the tone generator is switched off a fraction of a second later, just as Counter 2 is resetting to zero. The process repeats continually until, for example, the user taps sensor X3 once more, in order to set a new speed.

The circuit uses a total of three square-wave oscillators. The clock generator, which runs at a few tens of Hertz, is provided by IC4c/R16/C4, while the audio tone generator consists of IC4a/C2/R10. These both employ a commonplace Schmitt trigger type oscillator. Oscillation occurs because of the hysteresis of the inputs to the NAND gates (IC4a and IC4c), while the frequency depends on the time constant of the resistor and capacitor networks.

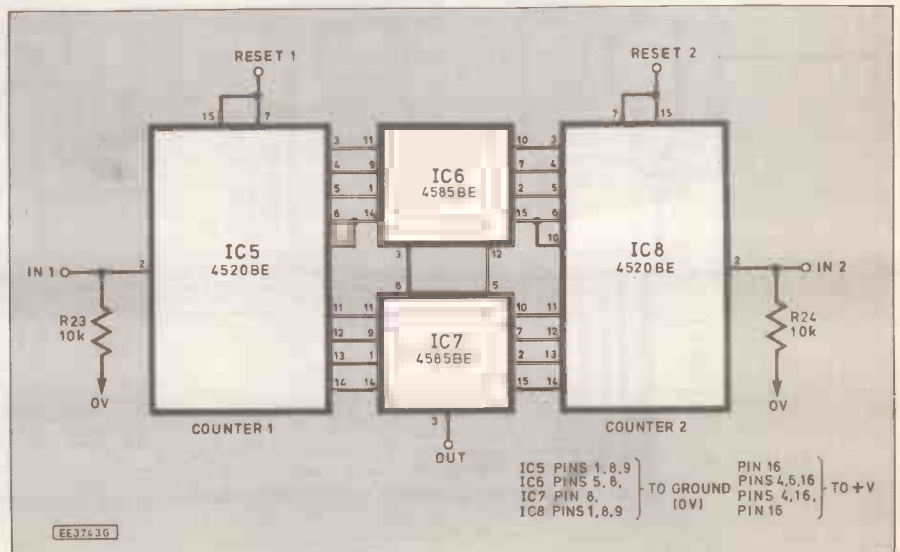


Fig. 3. Circuit diagram for the “Memory” stage of the Metronome. See Fig. 2. for its location in the main circuit.

connected to the Q and  $\bar{Q}$  outputs (pin 15 and pin 14) of the flip-flop IC2b respectively; when one of the two outputs goes high, the associated RC network produces a Reset pulse - duration  $\approx 70\text{mS}$  - while the capacitor of the other network discharges through a diode. The diodes D4-D6 prevent voltages significantly crossing the supply rails, also, the discharge time of capacitor C6 has to be shortened. (Note - D5 and D6 may, generally, be omitted on account of the built-in CMOS input protection diodes.)

Counter 2 must also reset the instant it's value exceeds that stored on Counter 1. To permit this, the falling voltage at the output of the memory (when the condition  $A = B$  is lost) generates a low pulse at one of the inputs of NAND gate IC4d. "Inverter" IC1d, connected to the other input of the NAND gate, generates a 70ms low pulse whenever output Q of flip-flop IC2b goes high.

The truth table for this combination is given in Fig. 4b. Thus, when either or both of the NAND gate's inputs go low, it's output goes high to clear Counter 2.

Finally, note that the point marked 'a' sends the reset pulse to the flip-flops at

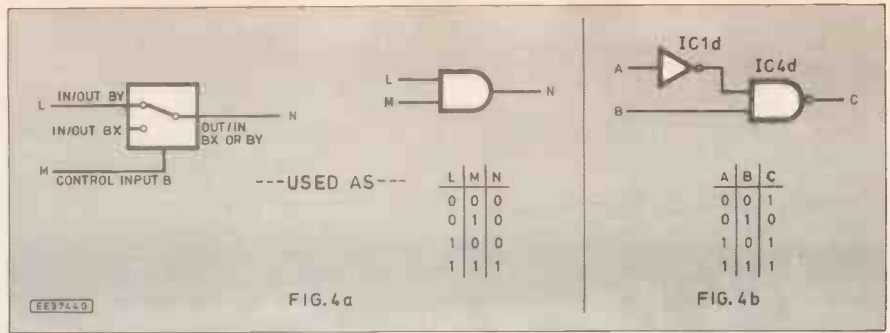


Fig. 4a. Use of IC3a and IC3b as AND gates.

Fig. 4b. Truth table for RESET logic circuit.

switch-on and 'b' sets the threshold voltage for "inverter" IC1d.

### CONSTRUCTION

The Dual Metronome is built on a single-sided printed circuit board (p.c.b.). The component layout and full size copper foil master pattern is shown in Fig.5. This board is available from the *EE PCB Service*, code EE801.

The overall dimensions are compact but, due to the scattered arrangement of the inputs on IC6 and IC7, the penalty is that a

number of wire links are required and the orientation of the i.c.s varies. The short links can be made of uninsulated wire, but the three long ones are of plastic-coated or enamelled wire; the latter sort was used in the prototype unit. Note that two links pass beneath resistor R12, which is soldered in a vertical position.

Three very short links are also fitted to the track side of the p.c.b.; Fig. 6 gives full details. This is not the neatest method, but avoids the need for a double-sided circuit board.

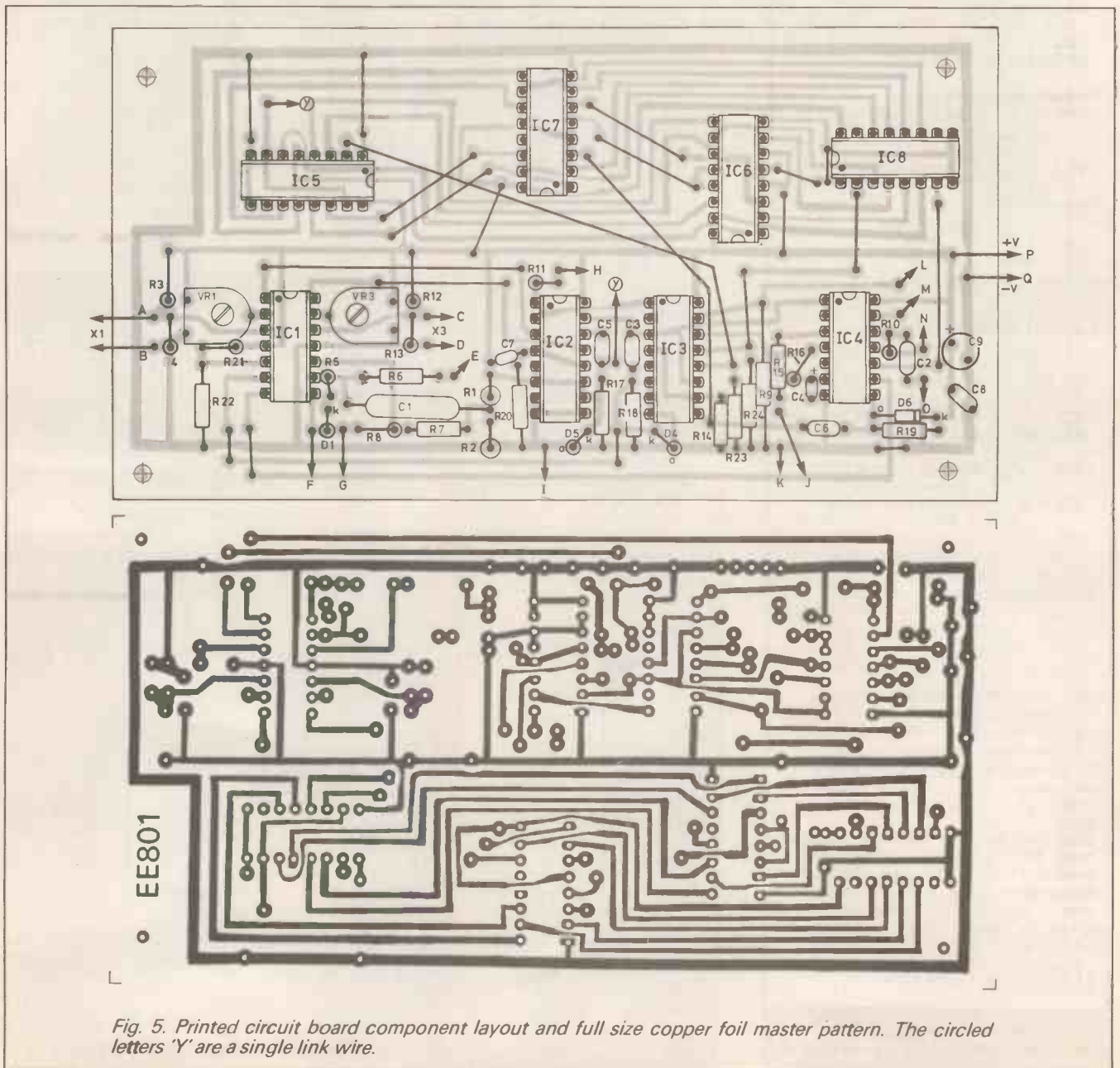


Fig. 5. Printed circuit board component layout and full size copper foil master pattern. The circled letters 'Y' are a single link wire.



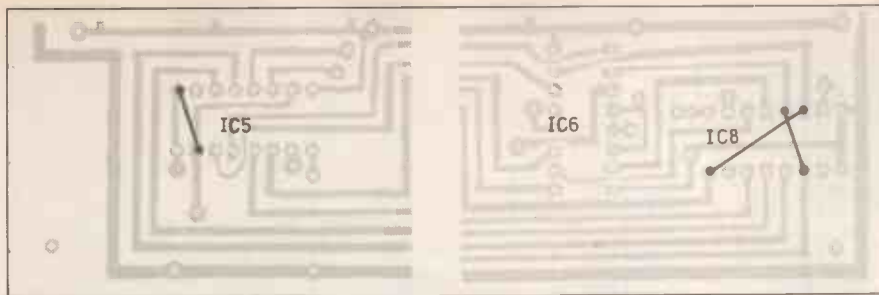


Fig. 6. Details of the underside link wires. These should be insulated leads.

## COMPONENTS

### Resistors

R1, R2, R16, R21, R22	47k (5 off)
R3, R4, R10, R12, R13	220k (5 off)
R5, R9, R14, R23, R24	10k (5 off)
R6, R7, R8	100k (3 off)
R11, R15	2k2 (2 off)
R17, R18, R19	1M (3 off)
R20	2M2
All 0.25W, 5% carbon	

### Potentiometers

VR1, VR3	220k min. enclosed preset, horizontal (2 off)
VR2	470k rotary carbon, lin.

### Capacitors

C1	2 $\mu$ 2 polyester
C2	4n7 Mylar
C3, C5 to C8	0 $\mu$ 1 ceramic (5 off)
C4	2 $\mu$ 2 tantalum, 35V
C9	10 $\mu$ F radial elect. 16V

### Semiconductors

D1, D4 to D6	1N4148 silicon diode (4 off)
D2, D3	Red 5mm l.e.d. (2 off)
IC1	LM324 quad op-amp
IC2	4027BE dual JK flip-flop
IC3	4053BE triple 2-channel multiplexer
IC4	4093BE quad NAND Schmitt trigger
IC5, IC8	4520BE dual binary counter (2 off)
IC6, IC7	4585BE 4-bit magnitude comparator (2 off)

### Miscellaneous

X1, X3	Unmounted piezoelectric transducer element, 27mm dia. (2 off)
X2	Enclosed piezoelectric sounder
S1, S2	Miniature s.p.d.t. toggle switch (2 off)
B1	9V PP3 battery

Plastic case, size approx. 165mm x 102mm x 51mm; 14-pin d.i.l. socket (2 off); 16-pin d.i.l. socket (6 off); multi-strand connecting wire; 1mm plastic sleeving; single-core plastic-coated or enamelled wire; double-sided adhesive pads; PP3 battery clip; plastic p.c.b. mounting blocks (4 off - see text); fixing screws (4 off); control knob, approx 35mm dia. for VR2; offcut of stripboard, approx. 6 strips x 4 holes; l.e.d. clips (2 off); solder pins; solder.

Printed circuit board available from the EE PCB Service, code EE801.

Approx cost  
guidance only

**£20**

The p.c.b. construction should be quite simple, with just a few points to note:

First, it's important that only the 4585B chip is used for IC6 and IC7. The functional equivalent, 4063B, has a completely different pin-out.



All the usual anti-static precautions should be taken when handling IC2 to IC8

as they are CMOS types. The pins of new, i.c.s often need to be bent slightly inwards, to fit the i.c. sockets or the holes in the p.c.b.; use an "Earthed" metal surface, and try to avoid touching the pins while doing this.

Capacitor C1 needs to be a non-polarised type e.g., polyester, while C4 (also 2 $\mu$ 2) was a tantalum bead capacitor in the prototype unit; remember that C4 is polarity conscious. The remaining capacitors will, of course, need to be selected to fit the circuit board; for example the 0.1 $\mu$ F capacitors are the miniature ceramic multilayer type, with lead spacing 5.08mm (0.2 in.).

## INTERWIRING

Details of the interwiring between the p.c.b. and panel mounted components are given in Fig. 7. All the connections should be of multistrand wire, and the type of "hook-up" wire - 7 x 0.2mm dia. copper - used in the prototype unit is ideal.

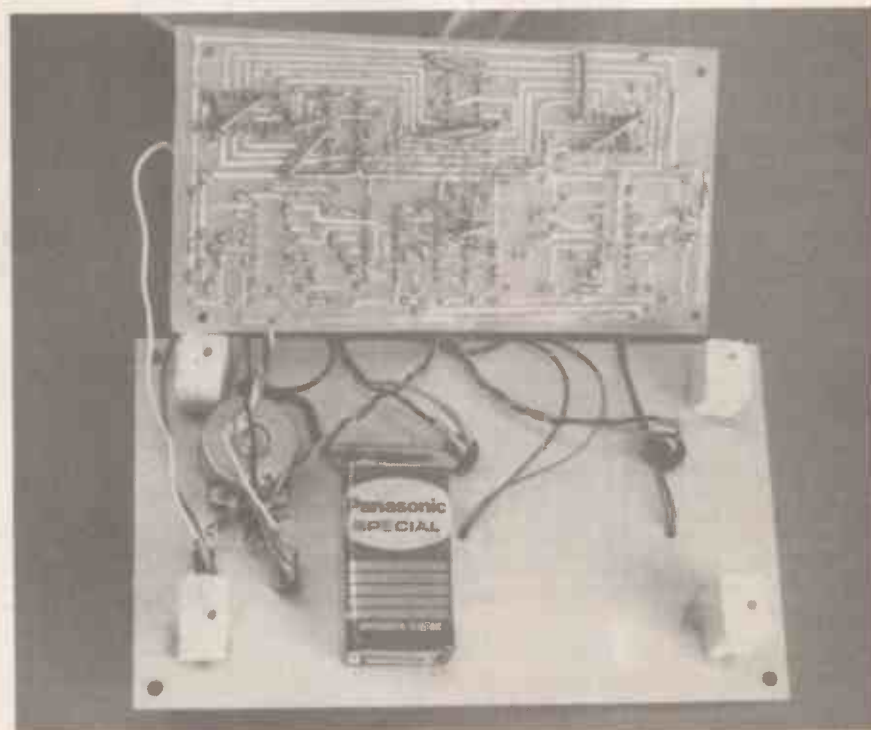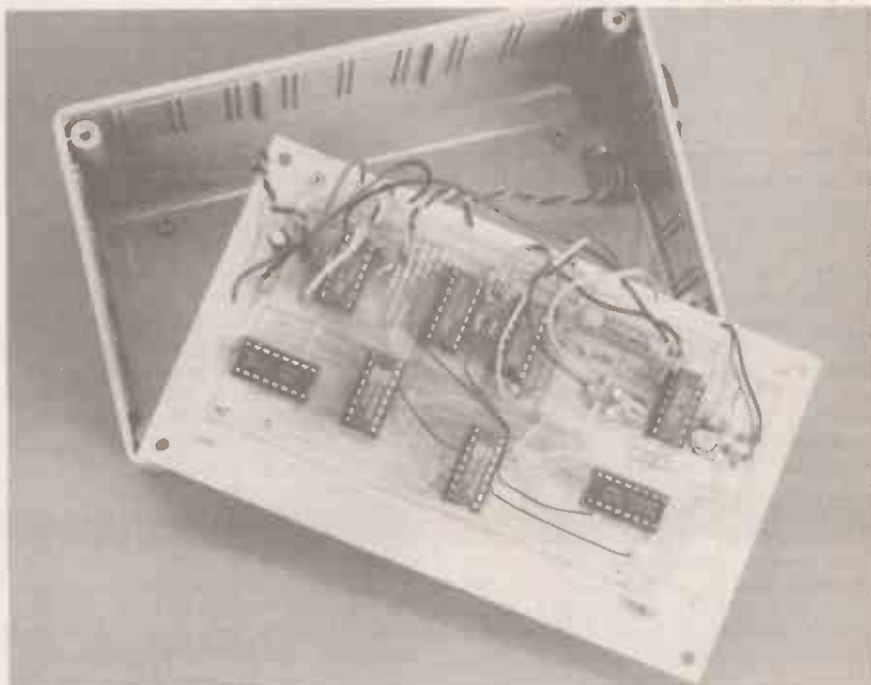

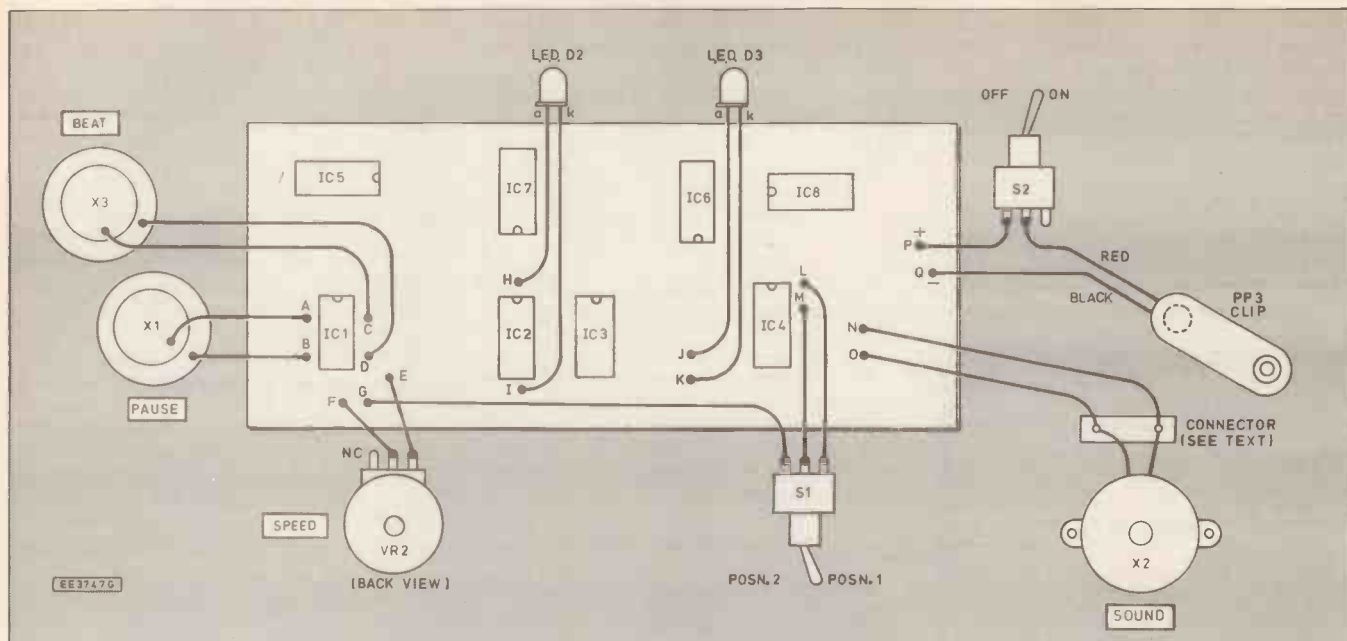


Fig. 7. Interwiring from the printed circuit board to all off-board components.

In Fig. 7, connections are shown leaving the p.c.b. in all four directions for clarity; in practice, however, all connections should pass across the same edge of the circuit board. This allows the board to be removed from its fixings and turned over for examination, without the need to unsolder connections.

The wiring-up process should not cause problems, despite the total of seventeen leads leaving the p.c.b. The wires run in groups of either two or three, and they should be twisted together or bound with cable ties to keep things tidy.

The use of p.c.b. solder pins (single-sided, 1mm diameter) is strongly recommended, and the joints are insulated and strengthened by 1mm plastic sleeving. The sleeving should be slid well back from the joints during soldering, since the p.v.c. begins to melt at a relatively low temperature, fusing to the insulation of the wire itself. All the wire/p.c.b. joints should be completed *before* starting to make the connections to the front panel mounted components.

First of all, the piezo transducers – the polarity of their connections is not significant but it is, obviously, important to match the correct transducer to each of the two l.e.d.s (i.e. D2 with X1, D3 with X3). Then, the l.e.d.s themselves must be connected the right way round; the cathode (k), indicated by a flattened side to the body of the device, and by the shorter lead, is wired directly to battery negative line in both instances.

The connections to front panel rotary potentiometer VR2 determine the direction of the scale for the Conventional Metronome circuit. The arrangement shown gives increasing “rate” with clockwise rotation of the control.

This leaves just the two s.p.d.t. toggle switches. When wiring up the function switch S1, make sure that connection “M” (see Fig. 7) goes to the central terminal of the switch. Check that none of the switch connections touch the circuit board; plastic sleeving can be used here also.

## TRANSDUCERS

The piezoelectric transducer elements X1 and X3 are mounted on the “outside” front panel of the case, silvered side down, using


double-sided adhesive pads. This has advantages over just gluing the elements in place, since the adhesive pads help to absorb the impact of each tap, reducing the risk of physical damage.

Alternatively, the elements could be mounted inside the case, fixed to the underside of the front panel. In theory, they would still pick up the “shock-wave” from each tap, whilst being protected from accidental damage; however, the reliability of this method has not been tested.

Returning to the method actually used: The elements are generally supplied with leads attached, and it may be helpful to resolder the outer lead at 90 degrees to its original position. This allows both connections to pass neatly into the case through a hole hidden beneath the piezo element (see Fig. 8). Note that the elements would almost certainly be broken by an attempt to reposition them after they’re stuck down.

The final piezo transducer, sounder X2, should be an enclosed type for maximum volume; the rigid attachment round the rim of the element produces a much higher sound output than if an unhoused element is used – despite the reduced size (approx. 20mm diameter). The sounder is glued onto the side of the case, with a small hole drilled to take its two connections.

Fig. 8. Preparation of the piezoelectric sensors X1, X3 for attachment to the front panel.

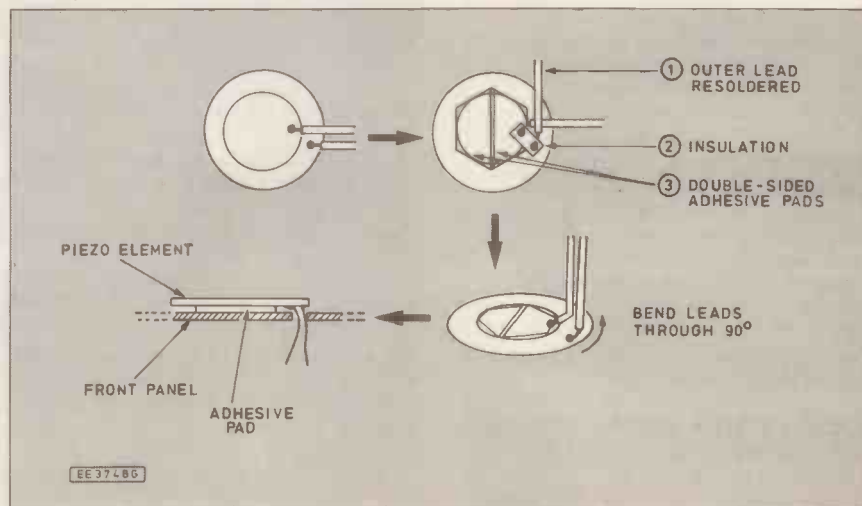

Since the leads of such piezo sounders are sometimes extremely thin, measures may be needed to reduce the risk of breakage. In the prototype unit the leads were joined to tougher multistrand wires via a piece of stripboard, about 6 strips by 4 holes, fixed to the floor of the case by a self-adhesive pad.

## CIRCUIT BOARD

When all the p.c.b. components are in place, check for the usual problems, such as broken tracks, incorrectly fitted components, solder blobs etc. In particular, examine the places where tracks pass between i.c. pads to ensure there are no short circuits or open circuits. Lastly, recheck the orientation of the i.c.s and the polarised capacitors – especially if you don’t have spares!

The completed circuit board will then need to be attached to the rear of the front panel. Space is provided on the p.c.b. for four fixing holes, but bolts are best avoided due to their effect on the external appearance of the unit. The solution used in the prototype was to securely glue four blocks of plastic (each approx. 18mm x 15mm x 10mm) in place on the panel, before mounting the p.c.b. on these using four self-tapping screws.



Finally, the battery (9V PP3) is fixed to any convenient space near the p.c.b., using a double-sided adhesive pad or Blu-tack "putty". Recheck the polarity of the battery connections before applying power, or all eight of the i.c.s may meet an untimely death!

## TESTING

Probably the simplest initial method of testing is just to briefly measure the completed circuit's overall supply current, with a 9V power source connected. The current should not exceed 5mA to 10mA and, as a further check, only diode D3 out of the two indicator l.e.d.s should be illuminated at switch-on. A large supply current might suggest an error in the direction of fitting some i.c.s.

Adjustment of the presets VR1 and VR3 across their range and back should change the state of l.e.d.s D1 and D3 respectively. With function switch S1 set to Position 1, a regular time signal should also be heard. Leave the presets at about one-third of the way along their tracks for the moment.

Now, set switch S1 to Position 2 and tap the "Beat" sensor X3 once, to switch off l.e.d. D3 (if necessary). The memory will be holding any old number at present, so tap the beat sensor X3 twice to establish the musical speed of your choice; the circuit "memories" it, hopefully continuing to beat time at that rate. The presets may still need some adjustment to increase/decrease the sensitivity of triggering; further information on this is provided later, in the section "Setting Up".

If the main circuit seems dead, though the conventional metronome circuit works, the most probable causes would include: a missing wire link or interwiring error; a non-soldered joint; a diode connected back-to-front or a flaw on the p.c.b. If a buzzing noise is heard after tapping sensor X3, the cause is multiple triggering (Counter 1 stores the number zero, hence the circuit runs at its maximum speed); readjust preset VR3.

## HEARING AID

Correct operation of counters IC5 and IC8 can be tested by connecting a crystal earpiece from the supply negative to each of the eight outputs (Pins 3, 4, 5, 6, 11, 12, 13, 14) in turn; the frequency of clicks should halve at each successive output. The state of the CMOS switch IC3c determines which one of the two counters – IC5 or IC8 – is active at any particular time, of course. Remember that the stored value on IC5 determines the maximum value reached by IC8.

The crystal earpiece can also be useful in checking whether Reset pulses are being produced; e.g. an earpiece connected to the output of "inverter" IC1d, or to the Reset 1 terminal, should click every other time the "Beat" sensor X3 is tapped. Multiple triggering, due to over-sensitive setting of comparator IC1b, can also be detected.

A further useful technique is to connect a 47µF electrolytic capacitor in parallel across capacitor C4, correct way around, using test leads. This slows down the clock pulse generator, IC4c, by a factor of about 20 and allows measurement of the changing logic levels using an ordinary analogue or even digital multimeter.

## SETTING UP

The main adjustment required is to the presets VR1 and VR3, which are wired as potential dividers. Their output voltages

may be set on either side of the reference values provided by resistors R3/R4 and R12/R13, since the piezo sensors produce both a positive and negative voltage fluctuation when pressure is momentarily applied.

The centres of the presets' tracks therefore give maximum sensitivity, and the extremes the minimum. As might be expected, triggering becomes unreliable close to the centre, and a lower sensitivity gives the best results.

A few other component values can also be fine-tuned if desired. The range of speeds from the conventional metronome circuit is determined by rotary potentiometers VR2, capacitor C1 and resistors R6-R8, working out at roughly 40-200 beats-per-minute, though component tolerances will affect the exact figures. If this is a problem, it is of course the user's decision whether it's worth changing component values slightly, to obtain the complete standard musical range.

Returning to the main circuit, the maximum interval between beats (i.e. the slowest speed) depends on the clock frequency. The specified values for resistor R16 and capacitor C4 allow for very slow speeds – as low as ≈6 beats per minute. If these are not needed, and a greater resolution is required between the higher speeds, then reduce the value of R16 to, say, 43k, 39k, 33k or even less.

It should also be checked whether the metronome exactly follows the beat which is tapped out by the user. The accuracy depends mainly on the three RC networks which provide the memory-reset pulses – each network adds the same small, constant delay (approximately 70ms) to the interval between beats, during which time one of the two counters is reset to zero.

The manufacturing tolerances of the resistors and capacitors used (5 per cent and 20 per cent respectively, in the prototype unit), together with the different input threshold levels of IC4d (Schmitt trigger) and IC5 and IC1d (ordinary inputs) may occasionally introduce detectable timing differences.

The simplest solution, if required, is to slightly increase or decrease the value of

resistor R19 as appropriate; connect a "spares-box" potentiometer or preset in parallel with, or in place of, this resistor. After careful adjustment for perfect behaviour, the potentiometer's measured resistance setting is used to obtain the best new value for R19.

The final step of setting up is to calibrate the Conventional Metronome circuit. The Speed control – potentiometer VR2 – should first be fitted with a large control knob, thereby spreading out the scale. A control of 35mm diameter, type 'K2', was used in the prototype unit.

The resulting scale isn't linear by any means, but nevertheless remains easy to use. The set of "preferred values" of musical speeds is also non-linear, the difference between the values increasing with the beat-rate; these effects go some way towards cancelling out in practice. Even with this scale, experiment showed that any speed from 40 to 200 beats-per-minute can be set with a good level of accuracy.

## IN USE

To finish off, a few points to help the use of the working unit:

1. *Battery Condition* – remember that the Beat indicator lamp (l.e.d. D3) always lights up when the circuit is first switched on. If it's weak or unlit, then the battery needs replacement.

2. *Pause Facility* – this is not available when the "conventional metronome" circuit is operating. In this case, to silence the time signal either switch off, or flip the function switch S1 then activate the Pause facility.

3. *Beat Indicator Light* – remember, the "memorised" time signal only sounds when this light is off. If it's ON, this means the circuit is awaiting another tap.

4. *Battery Life* – the circuit has very modest power requirements and the battery should have a long life, provided the unit is switched off after use. Fortunately, the likelihood of forgetting is much reduced – the circuit always has one or both its l.e.d.s lit up, on the occasions when it isn't making a noise, beating time. □



# INSIDE THE MINI DISC

IAN GRAHAM

*A new type of personal stereo is due to hit the streets later this year. We take the Mini Disc apart and look at how it works.*

ONCE upon a time record shops sold records, but now we can choose between vinyl discs, audio tape cassettes, compact discs and in many places VHS music videos. Although the CD has its detractors who criticise its clinically clean digital sound quality, it has nevertheless become by far the preferred music medium since its introduction in 1982. It dominates the market to such an extent that the days of the vinyl disc are now numbered.

Other music media are going digital too. Digital Audio Tape (DAT) is here already and the Digital Compact Cassette (DCC) will make its first appearance on the market this autumn. And Sony is to launch yet another audio format – the Mini Disc.

Including the rapidly sinking vinyl disc, by the end of 1992 there will be six different audio formats – six different ways of getting the same piece of music off a tape or disc. In reality the music buyer won't stock each title in six different formats. Tapes and CDs dominate the market at the moment. The CD will probably continue to go from strength to strength, but DCC and


the Mini Disc will threaten the existing analogue tape cassette if the price is right. Price is important. DAT hasn't made any inroads into mainstream hi-fi because of its high price.

Mini Disc and its player share a lot of technology with the CD, but it is not primarily intended to challenge the supremacy of the CD. Instead, it is aimed at the personal audio market. It is therefore a direct challenge to the tape cassette and the personal stereo.

Scheduled for introduction in late 1992, Sony claims that the Mini Disc will offer the same digital sound quality, quick random access and durability of the CD, combined with shock resistant portability and recordability. In other words, the Mini Disc has been designed to behave like a recordable CD that is also packaged to resist knocks and jolts while the listener is on the move.
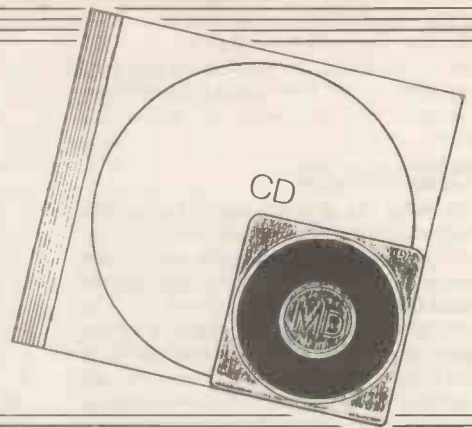
## Vital Statistics

The disc itself is 64 millimetres (2½ inch) across, almost half the size of a CD (120mm), and is housed in a protective



sleeve or "caddy". The disc and caddy together are roughly half the weight of the conventional analogue tape cassette.

The disc can store 74 minutes of music, virtually the same as a CD. Sony has achieved this by compressing the digital data onto the Mini Disc more efficiently than on a CD. Compact discs (and DAT) currently use a 16-bit linear encoding system. The analogue musical signal is sampled roughly once every fiftieth of a millisecond. Or, to put it another way, the sampling frequency is 44.1 kilohertz. Each sample is given one of 65,536 numerical values. (65,536 is  $2^{16}$ , hence "16-bit" linear encoding). So, 16 bits of data must be used for every 0.02 milliseconds of recording/playback time. Even if there is no signal present, the system carries on encoding or decoding at this rate.

## Mini Disc Recording

The encoding system used by Sony's Mini Disc, called ATRAC (Adaptive Transform Acoustic Coding) starts off with the same 16-bit data, but it analyses the signal and only encodes the elements that will be audible to the human ear. It doesn't waste time encoding data for sound that the ear won't hear. It divides the digital data into 20 millisecond chunks. Each of these is then broken down into the various sine wave components that it is composed of and each of these is assessed for amplitude (loudness).

Now for the clever bit. The ATRAC system looks at the relationship between the frequency and amplitude of the components of each 20 millisecond chunk. It's programmed to discard anything that will be inaudible to the human ear, either because it isn't loud enough or because it's masked by other sounds. The remaining data is recorded on the disc along with the usual error correction data bits.

During playback, the whole process is reversed. The various components of the signal are recombined by the ATRAC decoder into the 20 millisecond chunks, which are then combined to form a continuous digital pulse-train representing the original music. This is processed by the 16-bit DAC (Digital to Analogue Converter) in the usual way to recreate the original music. Despite discarding so much of the digital data, Sony claims that there is no significant difference in the sound quality of the source and the recording.

## Magnets and Lasers

So much for the electronics, but what is the physical process used to record new data on the disc? Sony calls it Mag-



Prototype Sony Mini Disc player.



neto-optical Overwrite (MO) technology. A magnetic head sits directly across from the laser source on the opposite side of the disc. The laser raises the temperature of a spot on the disc. This neutralises the magnetic polarity of the disc under the laser spot and effectively erases the signal that was recorded on it. As the disc spins, the temperature of the spot falls again and it takes on the polarity of the applied magnetic field. So, by feeding the magnetic head with the signal to be recorded, the track illuminated by the laser as the disc spins loses its previous recorded signal and takes on the new signal.

As Mini Disc was intended to be a highly portable medium, Sony went to great lengths to reduce its power consumption and prolong battery life. Conventional magnetic coatings used to make audio tape require a certain size of magnetic field to erase them. The field strengths needed range from 380 Oersteds for normal ferric tapes to 1,100 Oersteds for pure metal tape. The Mini Disc uses a magnetic layer composed of Terbium Ferrite Cobalt that will change polarity with a coercive force as low as 80 Oersteds. It also uses a new low power consumption magnetic head capable of reversing polarity every 100 nanoseconds – that's a ten millionth of a second.

Once a signal is recorded on the disc, it's played back by reading it off the disc using the same laser that helped to record it. This begs the question – how can a laser read *anything* on a magnetic surface? When light is reflected from any surface, it becomes polarised. The effect is used by polarising sunglasses to block the light polarised by bouncing off, say, a glass surface, and allow the rest of the unpolarised light from behind the glass to pass through the sunglasses. When the Mini Disc laser beam is reflected by the disc surface, its direction of polarisation depends on the magnetic polarity of the surface. So, as the laser tracks across the disc surface, its direction of polarisation flips to and fro in step with the signal recorded on the disc. Therefore, it's a *relatively* simple matter to convert this into an audio signal.

The system shares a lot of technology with conventional CD hardware. And it means that a Mini Disc player will be able



Prototype Sony Mini Disc recorder/player.

to play pre-recorded CD-type optical discs. The smaller disc size of the Mini Disc means that Mini Disc sized pre-recorded optical discs would have to be pressed specially for Mini Disc players. But their similarity means that existing CD pressing plants should be able to turn out pre-recorded optical Mini Discs quite easily.

### Performance

One of the practical problems that was addressed from day one was how the system could play high quality music while its user was on the move. Conventional optical pick-ups are knocked out of position very easily. Most manufacturers use an array of hardware devices – springs, buffers and servo mechanisms – to isolate the pick-up from shocks. Sony has taken a different approach. The pick-up can read data off the disc at 1.4 million bits per second, but the ATRAC decoder only needs 300,000 bits per second for real-time playback.

This difference in data rates is very useful if you know what to do with it.

Sony has used it to produce an electronic music store that can "paper over" any skips or jumps caused by sudden jolts. The pick-up sends data from a disc to a one megabyte memory chip. This is equivalent to about three seconds of music. The chip then feeds the ATRAC decoder. If the pick-up is knocked out of position, the chip can continue to feed the decoder and provide uninterrupted music for up to three seconds while the pick-up finds its place again. Then the chip fills up again. When the chip is full, the pick-up stops reading data off the disc until there is room for some more. The pick-up knows where it is and where it should be because address information is recorded on disc every 13 milliseconds. If the pick-up is jolted, it recognises that its at the wrong position and looks for the correct address before resuming playback.

The random access nature of Mini Disc means that any piece of music at any point on the disc can be found and played within one second. Try doing that with a tape cassette! □

## EVERYDAY ELECTRONICS BINDERS



Don't let your valuable issues of EE get binned, burned or bitten (by the dog). Get one of our exquisite orange hard-back binders, slip each issue into it as you get them and you will always know where they are – we hope!

Binders to hold one volume (12 issues) are available from Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH for £5.95 (£6.95 to European countries and £8.00 to other countries, surface mail) inclusive of postage and packing. **Payment in £ sterling only please.**

Binders are normally sent within seven days of receipt of your order but please allow up to 28 days for UK delivery – more overseas.



# ACTUALLY DOING IT!

by Robert Penfold

**T**HIS MONTH and in the next *Actually Doing It* article, we will consider the topic of semiconductor pinouts and leadouts. It is a subject that is rather more straightforward now than it was some years ago.

In the past you could order two transistors of the same type from different retailers, and find that you were supplied with two transistors that had totally different case styles. Worse still, you could sometimes end up with two components that looked the same, but which actually had different leadout configurations. There was usually a suffix letter at the end of the type number which indicated the leadout configuration in use, if you knew what to look for.

Integrated circuits (i.c.s) also caused problems, as some types were available in two or three different encapsulations. Again, there was usually a suffix letter tucked away somewhere at the end of the type number which showed the device's encapsulation type. Of course, it was obvious which particular type of case an integrated circuit had as soon as you examined it, but you had to be careful what you were ordering when buying components "blind" by mail order.

These days you are less likely to be troubled by semiconductors which have the wrong leadout configuration, a case of the wrong size or shape, too many pins, or whatever. It is not a possibility that can be totally discounted though. There are still a few traps for the unwary to stumble into.

Also, cheap surplus components are often "older than they used to be", and the semiconductors tend to be in obsolete and strange looking encapsulations. Some of these are actually quite usable if you know what you are doing, but for the beginner some are likely to be more trouble than they are worth.

## DIODES AND RECTIFIERS

Diodes and rectifiers are much the same, the only difference being that rectifiers can handle high currents whereas diodes are only suitable for low power applications. These components have only two leadout wires, but they must be connected the right way round if they are to give the desired result. Fig.1 shows the standard methods of polarity indication for most of the popular rectifiers and diodes.

The standard method for identifying the leadouts of diodes and rectifiers is to have a coloured band around one end of the body. This indicates the cathode (k or "active" +) end of the component.

A slightly different method is used for

some high current rectifiers. This is to have the cathode (k) end of the body thinner than the rest of the body.

Some diodes, rather unhelpfully, have a number of coloured bands, rather like those on a resistor. In fact, the bands do represent a number in something not too far removed from the standard resistor fashion, but this is the serial number in the component's 1N???? type number.

Each colour in the code represents a digit of the serial number, and this system operates in the same way as the first two digits of the standard resistor colour coding. You are most likely to encounter this system with the popular 1N4148 silicon diodes. The 4148 serial number is coded as yellow - brown - yellow - grey.

If you look carefully at a diode of this type you should find that one band is much *thicker* than the others. This one indicates the cathode end of the component.

Unfortunately, with many of these multi-band diodes the thicker band is something less than obvious. In these cases it helps to remember that the *first* band in the code is the one nearest the cathode leadout wire.

A few diodes seem to be marked with two coloured bands. These are offset towards the cathode end of the component. In effect, there is the usual band to indicate the cathode leadout, plus an extra band which is probably of little practical importance.

## ACID TEST

When you are unsure of the polarity of any rectifier or diode, remember that a

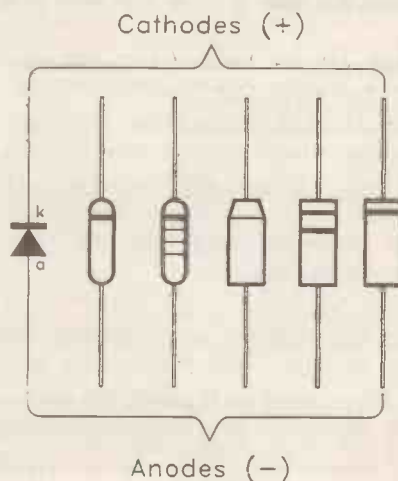


Fig. 1. Diode and rectifier polarity.

quick test using a multimeter set to a middle resistance range will soon determine its polarity.

Using a digital multimeter, there is a *low* resistance through a diode when the positive test prod is connected to the anode terminal, and the negative prod is connected to the cathode leadout. Swapping over the connections should give a high reading that will be off the scale with silicon diodes. If you do not get this high reading one way and low reading the other, then the diode or rectifier is faulty.

The same method of testing works with analogue multimeters, but they provide a test voltage of the *opposite* polarity. Thus a *low* reading should be obtained with the positive test lead connected to the cathode, and the negative prod connected to the anode. As before, reversing the connections should give an extremely high reading.

When using diodes there will probably be no major problem if you should get one or more of these components round the wrong way. The circuit will not work, but nothing is likely to be damaged as a result of the mistake.

Getting rectifiers round the wrong way is a different matter. This could produce a virtual short circuit on a mains transformer, or produce a supply having its output polarity reversed. Always be especially careful when dealing with high power circuits. In doubt, always check the polarity of a rectifier before connecting it.

## ON THE BRIDGE

Many mains powered projects use a bridge rectifier in the power supply. This is basically just a "ring" of four rectifiers which can either be made up from individual rectifiers, or bought as a single component with the rectifiers wired together internally.

The two leads which connect to the mains transformer are usually marked "A.C.", or with a wavy line (presumably intended to represent an a.c. waveform). The other two leads are marked "+" and "-", and these provide the positive and negative d.c. outputs.

There used to be quite a range of rectifier case styles in use, including the aptly named "top hat" type, and stud mounting rectifiers which could be bolted directly onto heatsinks. While I hate to recommend that any working components should be thrown away, it is probably the best course of action if you should somehow happen to obtain some of these older rectifiers.

While they might be fine electrically, they are invariably far too large to fit into the component layouts of modern equipment. At best they might be suitable for emergency repairs, and for experimental purposes.

## TRANSISTORS

Ordinary bipolar transistors are three lead devices. The three leads are called the "base", "collector", and "emitter", or just "b", "c", and "e" for short. You might very occasionally encounter transistors having a fourth lead, called the "shield". This is something that is only found on some high frequency transistors, and it simply connects to the metal case of the transistor.

Often when using transistors it is merely a matter of following the component overlay. This should clearly show



exactly where each transistor goes on the board, and which way round it fits. Provided you follow the diagrams carefully, and avoid any accidentally crossed-over leadout wires, there should be no difficulties.

Rather more care has to be exercised if you find yourself working from transistor leadout diagrams. The convention is for these to be *base* views (i.e. the device as viewed looking onto its leadout wires).

For power transistors the views are still base types, which means they are viewed looking onto the surface that fits against the heatsink. Note that this base view convention is the opposite to the one for integrated circuits (i.c.s), which are normally depicted in *top* views.

Transistor base views tend not to be too easy to work from when constructing projects, since you view transistors from above when fitting them onto a circuit board. If you have difficulty in mentally flipping-over base view diagrams, it is a good idea to sketch out top views and to then work from these.

In the past there have been different versions of the same transistor in common use. The silicon chip and the encapsulation were the same for each device; it was only the leadout configuration that was different.

A suffix letter on the type number indicated which leadout configuration a particular device actually had. The BC184L and BC184K were two transistors which sometimes caused problems, but these days the less popular "K" suffixed version

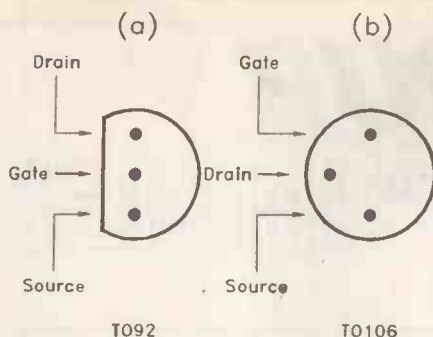


Fig. 2. F.e.t. base corrections.

seems to have disappeared from the component catalogues.

In fact, this practice now seems to have completely died out. There are some transistors which have an "A", "B", or "C" suffix, but this is concerned with gain grouping, and is nothing to do with different case or leadout styles.

There are still transistors which are available with a variety of leadout configurations and case styles, but they are sold under quite different type numbers. For example, the BC169, BC549 and BC109 are all basically the same device. This eliminates the possibility of any mix-ups over which leadout configuration a particular device happens to have.

#### EXCEPTION TO THE RULE

The only exceptions to this that I have encountered in recent times are certain

Jfet transistors. In particular, the popular BF244 and 2N3819 seem to be available in two different case styles. There seems to be no suffix letter or anything else in the type number to indicate which encapsulation one of the transistors actually has.

The base view for the original T092 cased version is shown in Fig. 2a, while Fig. 2b shows the base view for the later T0106 cased devices. The three terminals of a field effect transistor (f.e.t.) are called the *drain* (*d*), *gate* (*g*), and *source* (*s*), which roughly correspond to the collector, base, and emitter of a bipolar transistor.

Jfets having both of these case types are currently in circulation, and there is no way of telling which type will be supplied to you. This is obviously rather unhelpful. On the other hand, the two encapsulations are quite different, and there is no risk of mistaking one for the other.

As a point of interest, when the 2N3819 was first introduced, some of the base diagrams that were published had the drain and source terminals swapped-over. Devices that were connected in accordance with these incorrect diagrams often seemed to work perfectly well.

They were probably working somewhat below par, but nevertheless showed a degree of tolerance that you would not obtain from a bipolar transistor with their collector and emitter connections reversed. In fact germanium bipolar transistors are instantly destroyed by this sort of treatment.

# SHOP TALK

with David Barrington

### Solar Powered Lighting

The first question to be encountered when looking down the list of components required to build the *Solar Powered Lighting Unit* is: "where do I find the 305mm (12in.) x 305mm (12in.) solar cell panel?" The price of the solar panel seems to vary quite considerably and can be as much as £23 plus.

The answer is in two parts. The solar panel used in the prototype model was purchased from Bull Electrical (☎ 0273 203500), code 15P42R, and cost £15 plus VAT and £3 p&p. The other alternative is to use two of the 305mm (12in.) x 152mm (6in.) panels from Robert Keys (GW41ED), Dept EE, 4 Glanmoor Crescent, Newport, Gwent, NP9 8AX. These panels (£4.50 each inclusive) are rated at 12V nominal at 80mA and joining two together should meet the requirements for this simple project - although they have not been tried "in-circuit".

The panel meters used in the prototype models were purchased from Marco Trading (☎ 0939 232763) codes Pan.173 (100mA) and Pan.174 (500mA). These 51mm x 45mm panel meters are also stocked by Greenweld, Cirkitt and Cricklewood.

The five-lead L200 adjustable voltage and current regulator called for in the Current Limited version is a fairly common device and carried by most good component stockists. Electrically, the device is claimed to be virtually indestructible, but if the leadout pins do need slight bending to fit on the circuit board extreme care must be exercised when carrying out this operation.

### Sub-Woofer

Most of our component advertisers carry very good stocks of quality loudspeakers that could be used in the *Sub-Woofer* project, but, as mentioned in the article, the problem of matching two together could still prove troublesome. The latest excellent Cirkitt Constructors Catalogue lists one bass speaker which they claim can be used in pairs.

To overcome the speaker matching problem the author is offering to supply matched pairs for the sum of £39.95 plus £3 for post, packing and insurance. For further details write to: Henderson Electronics, 1 The Market Lanes, Terminus Road, Littlehampton, West Sussex BN17 5BS.

The cabinet vent tube is a piece of plastic pipe bought from a DIY store. The loudspeaker grille cloth should be available from most of our component advertisers. The equalising circuit components are standard items and should be available from your local supplier.

### Gas Alarm

The only item or items that are special to the *Gas Alarm* are the matched pair of "platinum", hot-wire, sensor and compensator transducers. These appear, after looking through our components catalogue library, to be only available from Maplin, code FM87U. Note that the compensator is marked with a blue spot, otherwise they are identical.

The power Darlington transistor and phase locked loop 4046BE i.c. are listed by most component suppliers, as is the low power CMOS timer TLC555CP or ICM7555. The Vinyl covered metal case also seems to be

readily available. Other cases can, of course, be used but they *must* be metal types.

The printed circuit board for the *Gas Alarm* is available from the *EE PCB Service*, code EE800 (see page 539).

### Dual Metronome

The piezoelectric buzzer transducers called for in the *Dual Metronome* should be widely available and are stocked in several guises. They are widely known as type PB2720 piezo sounders and the "membrane" or uncased elements are stocked by most of our advertisers.

If you are unsure about your soldering skills, then attempting the tricky task of repositioning the connecting leads should be avoided. Instead, appropriate small holes can be drilled in the front panel to take the transducer leads.

It is important that only the 4585BE 4-bit magnitude comparator be used in this circuit for IC6 and IC7. Some suppliers may offer the 4063BE instead; be warned, although functionally the same, it has a different pinout arrangement and would necessitate changing the p.c.b. layout.

The *Dual Metronome* printed circuit board is obtainable from the *EE PCB Service*, code EE801 (see page 539).

### Artwork Light Box

There should not be any problems acquiring the materials and light fitting for the *Artwork Light Box* project.

The "box" materials, including the corner blocks, may be purchased from any of the DIY Superstores. The Thorn 2D lighting fitting (2D tube plus BC adaptor) and the 45 degree BC batten mounting light socket may be purchased from any large electrical shop. When ordering the 2D fitting, quote part number: 2DA10/BC. Greenweld also stock these parts.

The opaque plastic screen could prove a problem and, if constructors cannot locate a local plastics stockist, it may, as an extreme measure, mean purchasing a clear sheet and resorting to "washing" one surface with scouring powder or pad to give the desired "Light diffuser" effect.

# FOR YOUR ENTERTAINMENT

by Barry Fox



## Shock-Horror

The press recently came up with a shock-horror item on GPS, the global positioning satellite system.

When the US Government gave the US military funds to put up a network of satellites to guide military missiles, like Cruise, it was on condition that the military would also make the system signals available for domestic use.

Each satellite continually generates a very accurate clock signal. The receiver picks up signals from four satellites simultaneously and compares their time codes. This gives it a very accurate fix on location, by longitude, latitude and altitude.

Several years ago Sony sold a GPS receiver in Japan which was used by offshore oil drilling crews to get an accurate fix on their position. Many well-heeled yachtsmen now have GPS receivers to make navigation more accurate. Sony UK now sell the first, relatively low cost (£1,000) portable receiver.

## On The Map

Car navigation systems, such as Philips' Carlin, are already under development. These will use GPS signals to control an on-board computer which reads digitised maps from a CD-ROM disc.

The main obstacle holding up the "public launch" is the cost of the maps. Organisations such as Ordnance Survey worry that once they have converted their maps into digital code and pressed the code onto a CD, the maps can be copied as easily as music from a CD.

One CD can store all the maps for a country, so the potential for piracy is enormous. Based on current map prices, a CD containing all maps for the UK would cost £4.5 million!

## Sinister aims

The popular press has now latched onto the idea that someone could connect a portable GPS receiver to the auto pilot of a light aircraft, put a bomb on board and turn it into a Cruise missile. Doubtless this could be done and would make a nice plot for an action movie. But in reality, the weapon would be a very blunt instrument.

The signals transmitted by the GPS satellites come in two types, one intended for use by the military, the other for civilians. The military time codes give accuracy sufficient to guide a Cruise missile through the front door of the Kremlin. This was the technology used in the Gulf war. But these signals are

digitally encrypted and are not available for civilian use.

The civilian signals have an accuracy of at best 30 metres and more often 100 metres. So the bomb would have to be very powerful to destroy a chosen target.

There are, unfortunately, a lot easier, lower-tech, ways for a terrorist to do damage. Think for instance of the Channel tunnel. Cars will be loaded in bulk on a trailer and carried by train through the tunnel. Each car will have petrol in its tank. One incendiary device will turn the whole train into an enormous petrol bomb.

If authorities run security checks on each car before each journey, this would put hours on the journey and make the tunnel a commercial-dead duck.

## CDTV Disaster

As Philips starts its roll-out of CD-I, with adverts and selected sales outlets in London and the South East, I wonder how long Commodore can go on pretending that its rival multimedia interactive CD format, CDTV, is a contender.

I also wonder whether Commodore's management in the US will ever be answerable to the company's shareholders for the CDTV marketing disaster. There must come a time when Commodore in the USA has to stop citing Europe as a successful market. CDTV has been such a fiasco, both in the USA and Europe, that Philips long ago stopped worrying that confusion between CDTV and CD-I might hurt CD-I sales.

Sadly, Commodore's shareholders may never know how some lone voices inside the company's UK subsidiary saw early on that the marketing pitch for CDTV was all wrong. Commodore's management has experience in the home computer and games market, but none in "brown goods" consumer electronics. And this has cost the company dearly.

More than a year after the "launch" of CDTV, it is still an invisible product with a non-existent profile. Dixons, who were supposed to stock CDTV standalone players, and demonstrate them, either keep CDTV hidden in a back room for the benefit of customers who ask, or stack them on a shelf like CD players. There is only one way to sell multimedia and interactive CD, of any format, and that is to let people get hands-on experience of what it can do.

As a quite separate issue, I happen to think that CDTV is technically a mess,

with bug-ridden hardware rushed onto the market along with mainly unappealing software.

Commodore's damage control plan was to re-launch CDTV, as a CD-ROM peripheral for the Amiga 500 using software ported from existing Amiga libraries. The launch date was given as May, but by early June there was still no further word from Commodore.

## Caddy Puzzle

The most puzzling design feature of CDTV is that the program discs must be loaded into a CD-ROM caddy before they can be used in the CDTV player. Although CD-I players do not use caddies, Commodore's justification for caddy-loading is that data discs must be protected from handling.

Commodore has also advocated the use of CDTV players for playing music CDs.

It is clearly inconvenient to have to load discs, especially music discs, in caddies before playing them. To take a disc out of its jewel box, put it in a caddy, then later take the disc out of the caddy and put it back in the jewel box, clearly involves far more handling than just popping it into the loading tray of a music or CD-I player. If I were using CDTV, then I would surely want more than the one caddy that comes with the player.

As an experiment I went shopping for CDTV caddies. Dixons in Oxford Street (the Tottenham Court Road end) said they stocked CDTV players, although none were on show. They had no spare caddies, and seemed surprised that anyone should want more than the one that comes with the player. The staff showed no interest in ordering me some.

Instead they sent me a few doors down Oxford Street to the Virgin Megastore. On the way I tried Microbyte, a games software shop, who did not stock any CDTV material.

Virgin's games department sold CDTV discs, but no caddies for them. Try Tottenham Court Road, they said.

It is the kiss of death for a product when shops are happy to send potential customers somewhere else to buy it.

I tried some shops in Tottenham Court Road, including Lasky's, but no joy. Finally I found two caddies in the Silica Shop at £7 each (which I bought for use with a CD-ROM player).

Draw your own conclusions on the impact of CDTV's year on the market, and its chances of still being around in a year's time.



# MALTECH

## ELECTRONIC COMPONENTS

### SWITCHES - RELAYS - DIL SKTS - BOXES

**PROJECT BOXES** A range of high quality boxes moulded in black high impact ABS, easily drilled or punched to produce a professional looking end product

TYPE	WIDTH	LENGTH	HEIGHT	PRICE
T2	75	56	25	£0.77
T4	111	57	22	£0.92
MB+	79	61	40	£1.35
MB2	100	76	41	£1.47
MB3	118	98	45	£1.71
MB4	216	130	85	£5.19
MB5	150	100	60	£2.35
MB6	220	150	64	£3.95
MB7	177	120	83	£3.42
MB8	150	80	50	£2.22

All sizes are in millimetres

#### SPECIAL OFFER - PROJECT BOX

As above boxes 50 x 70 x 25mm  
60p each 10 for £5.00

#### KEY SWITCH

3 Position keyswitch  
£2.35

**MICRO SWITCH** roller arm operation spdt 40p each  
**MINIATURE TOGGLE SWITCHES**

spdt	60p each	spdt 3 position c/off	70p each
dpdt	70p each	dpdt 3 position c/off	80p each
3 pdt	90p each	spdt 3 position c/off biased both ways	70p each
4pdt	£1.20 each	dpdt 3 position c/off biased one way	80p each
spdt biased	60p each		

**MINIATURE TOGGLE SWITCH** pcb mounting 3pdt 50p each 10 for £4.00

**DIL RELAYS** 5 volt dp/changeover 60p 10 for £5.00  
12 volt dp/changeover 80p 10 for £6.00

**RELAY** 10 amp contacts sp/changeover 12 volt coil £1.20 each

**CAR HORN RELAY** in metal can with fixing lug, s/pole on 10 amp contacts £1.00 each 6 for £5.00

**20 AMP RELAY** dp on 12 volt coil £1.50 each 4 for £5.00

**REED RELAY** 12 volt 50p each 10 for £4.00

**240 VOLT AC RELAY.** 3-pole c/o 10 amp contacts £1.50 each 4 for £5.00

DIL SKTS		'D' CONNECTORS		
8 pin	10 for £0.60	plug	socket	cover
14 pin	10 for £0.90	9 pin	30p	30p
16 pin	10 for £1.00	15 pin	40p	40p
18 pin	10 for £1.00	25 pin	50p	50p
20 pin	8 for £1.00			
24 pin	8 for £1.00			
28 pin	6 for £1.00			
40 pin	5 for £1.00			

**ALL COMPONENTS FULL SPECIFICATION DEVICES**

### SEMICONDUCTORS - TRANSISTORS - ICS - DIODES - REGULATORS - ETC

2N3702	10p ea 12 for £1.00	VOLTAGE REGS
BC337	10p ea 12 for £1.00	7812/7805/7912/7905
2N3904	10p ea 12 for £1.00	all 35p each, any 4 for £1.20
TIP31B	30p ea	AD592An Temperature Sensor i.c.
TIP 3055	90p ea	mounted on 1.5m screened lead complete with data and application notes £1.50 ea

**ALL PRICES INCLUDE VAT**

BC213L	10p ea 12 for £1.00
2N3055H	60p ea
2N3771	£1.20 ea
741 op-amp	25p ea 5 for £1.00
555 timer ic	30p ea 4 for £1.00
LM324 quad op-amp	30p ea 4 for £1.00
1N4007 diode	20 for £1.00
1N4001 diode	25 for £1.00
1N4148 diode	40 for £1.00
BZY88C12	6p ea 10 for 50p

LM3914/LM3915 Bargraph ics	£2.95 ea
LM317T Variable voltage regulator	mounted on a small heat sink 4 for £1.00

### OPTO DEVICES - LEDS - DISPLAYS - COUPLERS - INDICATORS - ETC

**7 SEG DISPLAY**  
MAN6610 2 digit 0.6" high com anode, amber  
60p each, 4 for £2.00  
**OPTO-ISOLATOR OP12252**  
50p each 10 for £4.00  
**SLOTTED OPTO**  
£1.00 each

#### PLASTIC BEZEL

for 5mm  
rnd leds  
10 for 40p

#### LEDS - LEDS - LEDS

5mm rnd red/yellow/green/amber 10p each 12 for £1.00 any mix  
5mm rnd high brightness red/green 20p each 6 for £1.00 any mix  
5mm rnd flashing red 60p each, yellow/green 70p each  
5mm rnd bi-colour 20p each, tri-colour 30p each  
Rectangular 6 x 6 x 2mm red stackable 10p each 12 for £1.00  
Mounted in chrome metal bezel red/yellow/green 40p each, 3 for £1, 10 for £3.00 any mix

Mounted in a black metal bezel red only 30p each, 4 for £1.00, 10 for £2.00  
20 ASSORTED FULL SPEC LEDS. Various shapes and colours £1.00

### ALARM CONTROL UNIT

Single zone alarm control unit built into a domestic light switch box. Ideal for home, caravan, boat, garage, shed etc.  
Facilities: - Normally closed loop for pir sensors, door/window contacts etc.

Normally open loop for pressure mats.  
24-hour loop for personal attack button  
Visual indication that the system is operational.

Automatic entry/exit delay.

Automatic system reset.

Alarm output cmos logic level.

#### SIREN

12 volt dc for external use  
115db £8.95

#### BELL BOX

A plastic bell box cover supplied with backplate. Red/yellow/white or blue £6.95 each

PRICE COMPLETE WITH FULL INSTRUCTIONS £8.95  
BELL/SIREN INTERFACE BOARD COMPLETE £3.95  
BELL/SIREN INTERFACE PCB ONLY £1.50

### PASSIVE INFRA-RED ALARM SENSORS

Ex installation sensors tested working.

Type 1. Measures 180 x 112 x 70mm with walk test led, relay output and tamper protection. 12 volt dc supply required £8.50 ea

Type 2. As above but a smaller unit 123 x 62 x 50mm £11.75 ea

#### DOOR/WINDOW CONTACTS

Surface or flush mounting, white £1.10 ea

#### JUNCTION BOX

white 6 way 60p

Please note: There may be variations in the size of the above passive infra red sensors depending on stock at the time of ordering. But the unit will certainly be within the stated sizes.

**DUAL TECH SENSOR** Microwave and passive infra-red combined. Separate led indication for each function. Measures 120 x 75 x 50mm. Relay output 12 volt dc tamper protection £29.95 ea

### BREADBOARDS - CAPACITORS - SOLAR CELLS - HEATSHRINK - ETC

**SOLAR CELL** 2 volt 150mA max, size 60 x 100mm £1.35 ea 5 for £6

**HEATSHRINK SLEEVING** 8mm dia x 40mm long 5 lengths for £1.00

**BNC TO BNC LEAD** 2m long £2.35 **BNC TO PL259** 2m long £2.35

**BNC SOCKETS** 50 ohm single hole fixing 50p ea 10 for £4.00

**MIN. BNC PLUGS AND SOCKETS** 2 plugs and 2 sockets £1.20

**PIEZO TRANSDUCER** 5 assorted types £1.00

#### MERCURY TILT SWITCH

£1.00 each

#### PIEZO VIBRATION SENSOR

with data sheet £1.00 each

#### BREADBOARD

173 X 65mm 840TP £5.25 each

#### TEXTPOOL ZIF SOCKET

28 pin zero insertion socket £5.95 each

#### SOLID STATE RELAY

Switch mains up to 7 amp 12 or 5 volt control voltage both types £2.95 ea

**NI-CAD BATTERY PACK** 12 volt 4Ah can be split into two 6 volt packs. High temperature fast charge type £27.95

**CAPACITOR** 10,000 mfd 25 volt with fixing clip 60p each

**CAPACITOR** 470 mfd 400 volt £1.50 each 4 for £5.00

**CAPACITOR** Tantalum bead 10 mfd 10 volt 10 for 50p

**CAPACITOR** 0.1mfd 63volt 6p each 10 for 50p

**EPROMS 27C256 - 25 27C512 - 25.** Once programmed but never used eprom. Mounted on a plastic carrier, can easily be removed from the carrier or used with a low insertion force socket.


**27C256** £1.00 each 6 for £5.00 **27C512** £1.20 each 5 for £5.00

Suitable low insertion force socket 28 pin 40p ea 3 for £1.00

**Dept EE, Mailtech  
PO Box 16 Ludlow  
Shropshire  
SY8 4NA  
Tel: 058 474475**
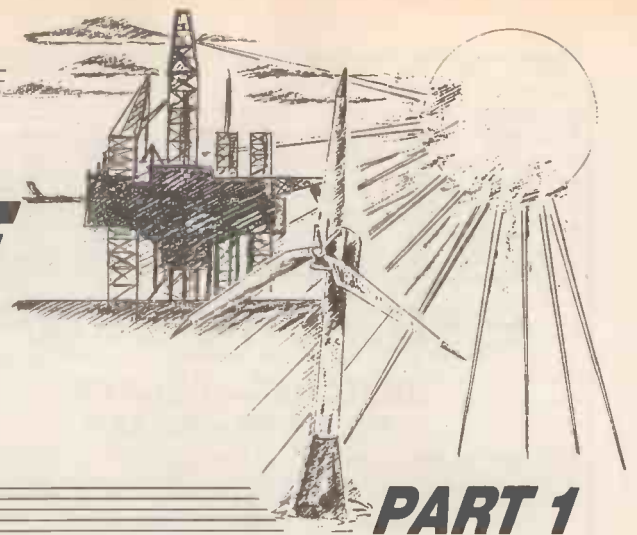
# MALTECH

All prices include VAT.  
Please add 75p carriage to all orders



# ALTERNATIVE ENERGY

T. R. de VAUX BALBIRNIE

PART 1

Developments using renewable energy sources.

**T**HIS is the first article in a short series about renewable energy – that is, sources of energy which are everlasting rather than those derived from the so-called *fossil fuels* which will eventually run out.

This month we shall take an overview of the topic and look in some detail at the *direct* use of solar power. In the following months we shall examine some particular examples of renewable energy which have the potential for large-scale exploitation in the U.K.

Wind power has particular importance already so some of next month's work will be devoted to this particular topic. The month after that will involve a trip to Denmark to examine at first hand the technology used in the design, construction and operation of modern wind turbines used to generate electricity.

## THE GLOBAL PROBLEM

At the moment, much of the world economy is based on the use of *fossil fuels* – coal, oil and natural gas – to supply our energy needs. When we use these, perhaps in



Battersea Power Station showing the main turbine hall.  
(Sinclair Stammers/Science Photo Library)

the form of petrol or diesel fuel for transport, or when coal is burnt for simple heating or to generate electricity we are actually using *solar energy* which was stored up long ago.

Coal is the remains of ancient forests – the trees grew using carbon dioxide from the air and water, together with the energy of the sun, for photosynthesis. Unfortunately, the use of fossil fuels carries with it problems of pollution and the release of carbon dioxide – a greenhouse gas which causes *global warming*. We shall look at this in detail next month.

Another problem with the fossil fuels is that they will eventually run out. Estimates of when this will be vary due to the difficulty of estimating the yield of as-yet undiscovered reserves and also in predicting future demand. However, it is said that oil supplies may be exhausted in some 35 years, gas in 50 years and coal in 200-300 years. Although not a fossil fuel, *uranium* – the raw material used for nuclear power generation – is also a finite resource.

The fossil fuels will not, of course, run out overnight. The price of oil and gas will rise as they become scarce. This will put pressure on coal and the price of this – together with uranium – will also increase. Remaining reserves of the fossil fuels will become too valuable as raw materials for the chemical industry than to be used as fuels. It is vital, therefore, that we conserve energy and seek alternative sources to fill the energy gap and assure our power supplies in the 21st century.

## ELECTRICITY

Electricity is the most convenient form of energy since it is so easy to control. We have therefore come to depend on it. In Britain, most of our electricity is generated by burning coal (and sometimes oil or gas) in power stations. This boils water and raises steam which is then used to turn a *turbine* connected to a *generator* – a so-called *turbogenerator* (see photograph).

Everyone is responsible for using electricity both directly and indirectly so we are all responsible for burning coal and the other fossil fuels. We are not particularly efficient at doing this either. Only 30 per cent of the coal's energy ever finds its way to the power socket. Most of it is simply thrown away, uselessly, in the form of heat.

Serious interest is being shown in schemes – *combined heat and power* – which utilize

this waste heat for central heating of private homes, office blocks, public buildings and the like. Unfortunately, the power stations are not necessarily close to the centres of population where the heat is most needed – they are generally sited near the source of fuel.

## THE ALTERNATIVE VIEW

Presently, the sun pours ten thousand times more energy on to the earth than we actually use. This energy is non-polluting and will be available for millions of years to come. So why do we not make use of it on a day-to-day basis rather than in the form of stored-up energy in the fossil fuels?

This is indeed possible and there are two approaches. The first is to use the solar energy *direct*. However, large-scale schemes tend to involve very expensive technology and at the moment it seems that their use will be limited to local production of power – perhaps where other methods are difficult. The other possible way forward is to use solar power *indirectly*, using such natural phenomena as waves and wind. Here, the sun's energy has already been converted into a form more suited to exploitation using familiar and cheap technology.

Some such schemes are already off the ground, some have possible longer-term potential and some are fanciful long-shots. We shall be looking at a number of these over the coming months.

## WIND POWER

Wind power promises to provide a useful contribution to Europe's energy needs in the short term – perhaps up to 10 per cent in the next ten years or so. The technology is cheap, safe and well-established.

Wind power is really a convenient way of exploiting solar energy because it is the sun which causes the differences in temperature which makes the wind blow in the first place. We shall say no more about this aspect of Alternative Energy now since some of next month's article will be devoted to it in detail.

## A SPOONFUL OF SUGAR

When we burn wood, we are again using indirect solar energy – that is, the sunlight absorbed by the green leaves over the previous few years while the trees grew. Since wood is a good fuel it may simply be used as a coal substitute. It is, however, rather dirty to burn. In some countries, this idea is taken a step further and crops are cultivated specially for their *fuel* rather than their *food* value. This is called *biomass*.



Sugar cane, a perennial grass, is a remarkable material which converts more solar energy than most other plants. Special strains have been cultivated which do even better than the old ones in this respect. In Brazil, sugar cane is grown and the sugar obtained fermented to an alcoholic brew. The liquor is then distilled to provide pure alcohol. This is a flammable liquid and a clean fuel which may be used directly to power cars or blended with a proportion of petrol for the same purpose.

It is quite possible to convert a petrol engine to burn alcohol instead. Brazil has to rely on expensive imported oil so using such alternatives saves quite a lot of money. One advantage of biomass is that there is no overall greenhouse effect. This is because the carbon dioxide released by burning the fuel matches the amount absorbed by photosynthesis as the plant grew – this will be used by the next crop and so on.

The only other product obtained by burning alcohol is water which, again, is simply the water which was absorbed during photosynthesis. The only overall effect, then, is simply to have used the sun's energy.

Using alcohol made in this way could provide a partial solution to a future world energy shortage. There is excess production capacity of sugar cane anyway since the demand for sugar has fallen over the years. Also, sugar beet has now become a major source of sugar – especially in Europe. Using alcohol as a fuel could mean that the cheap well-understood technology of the internal combustion engine could be utilized into the foreseeable future. Traditional forms of transport – including air travel – could then continue to be used.

## DIESEL TREE

On a similar theme, a tropical tree, *copaifera multijuga* produces an oil which is almost a diesel substitute. Research is going on at the moment in an effort to transfer the gene responsible for this process to a tree which can grow in cooler climates. This could rival other ways of

obtaining energy for heavy transport in the future.

Rotting plants produce methane gas. This is the same as *natural gas* obtained from the North Sea reserves and supplied to homes and industry. This method is, again, making use of the energy given by the sun to the plant during photosynthesis. On a small scale, decaying material is placed in a large vessel from which gas may be drawn as required. This is commonly used as cooking gas in some countries such as India and China.

Landfill gas is formed in this way and there are some schemes in the UK which use it to generate electricity. We shall be looking at these in a future article.

## FALLING WATER

Hydro-electric power (electrical energy gained from falling water) is yet a further indirect way of harnessing solar energy. Note that it was solar energy which evaporated the water to form water vapour which was carried to the high ground and eventually fell as rain (the water cycle). Flowing water may be used to turn special turbines and conventional generators. However, a considerable amount of flowing water and preferably a large height (head) through which it falls is needed to make this method commercially viable.

A really large hydroelectric scheme can generate 10,000MW – equivalent to the output of several large coal-fired power stations. Some countries, such as Canada, are fortunate in having immense quantities of falling water so it is not surprising that this country is a world leader in hydroelectric power technology.


Sweden produces half her electricity needs using hydroelectric schemes (the other half coming chiefly from nuclear energy) – very little coal is used for the purpose. Although scope is limited, the UK has some large-scale hydroelectric schemes – around 100MW – in operation.

We see that one way or another, almost all the energy we use has come from the sun

– either stored up long ago or that which shone on to the earth more recently. However, when people talk about using solar power they usually mean the *direct* use of sun's energy and exploiting this poses more of a problem. There are two ways used at present. One is to use the heat energy as it is and the other to convert the heat and light energy – *the solar radiation* – into electricity.



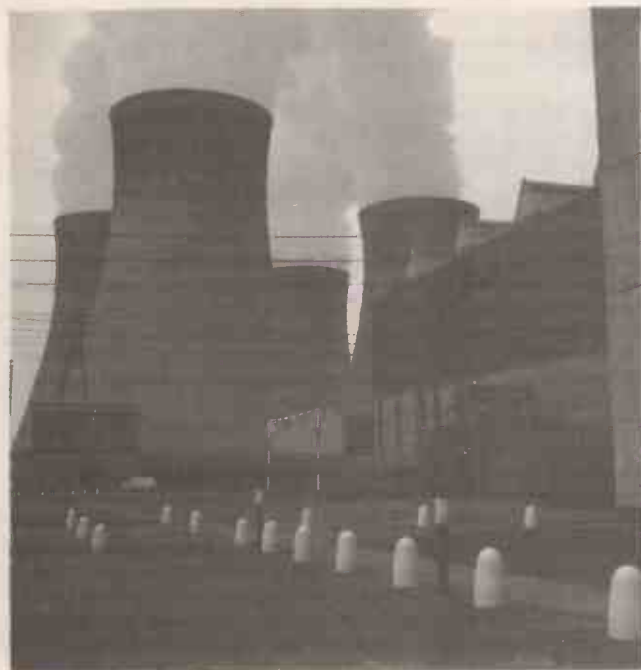Hoover Dam across the Colorado river, completed in 1936. It is 1,244 feet long and 726 feet high making it the highest dam in the USA. The hydro-electric power station has a generating capacity of 1,000MW from its 18 generators. The reservoir stores 30 million acre-feet of water in Lake Mead which extends 115 miles up the river. (Lowell Georgia/Science Photo Library)



The West Burton coal-fired power station showing the cooling towers and the generator building. (John Howard/Science Photo Library)



Pipes leading to a hydro-electric power station at the Alcan aluminium works, Fort William, Scotland. (Martin Bond/Science Photo Library)

## FACTS AND FIGURES

The unit of energy is the *joule* (J) – named after James Joule (1818-1889) a Manchester brewer. The watt (W) – named after the British engineer, James Watt (1736-1819) is the rate of *converting* energy and is equal to one joule per second. To give some idea of the size of a joule – we would need about 40,000J to boil the water needed to make a cup of tea.

The amount of solar energy which falls on the earth in one day is in the region of  $10^{22}$  joules – that is, one followed by 22 zeros! This amounts to some 700W per square metre although it varies with the latitude of the place, the time of day, the season of the year, the amount of cloud, the height above sea level and other factors. On a bright sunny day it will exceed 1kW (1000 watts) per square metre.


Several things happen to this energy. Much of it (about 30 per cent) is simply reflected back into space. Some (about 20 per cent) falls on water, causes evaporation and brings about the water cycle mentioned earlier. A little is used by green plants to perform photosynthesis. This leaves nearly half the energy simply warming the ground.

## DIRECT SOLAR POWER

Imagine a conventional coal-fired power station producing 1000MW i.e. 1,000,000,000 watts (a large power station). If the whole of the sun's energy could be collected and used, it would need about 1.5 million square metres of land area to produce the same power. This may be pictured as a square with sides rather more than 1km in length.

It seems that by using a few tens of square kilometres of land area, we could obtain all the electricity needed for Britain! However, there are some flaws here. Firstly, the energy is only available during daylight hours and then only on relatively cloud-free days – certainly not to be guaranteed in the UK. Also, no one has found a way of collecting *all* the energy – it would really need at least ten times the land area than theory suggests. This would not be a great problem but the cost of setting up the scheme would be prohibitive at the present time.

Fig. 1. Operation of a solar panel.

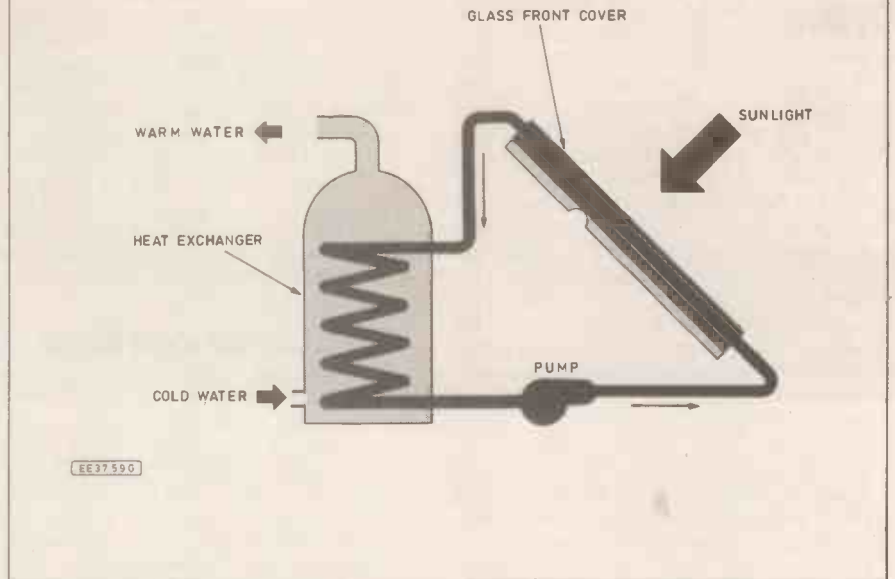

It would need cheaper technology coupled with rising prices elsewhere for this to prove commercially viable in the medium term. On the other hand, small-scale local schemes seem attractive – perhaps to provide electricity in remote places.

In hot countries it is possible to fry an egg on the pavement. Solar radiation causes significant heating of the surface on which it falls. Dark-coloured surfaces, particularly black ones, absorb the radiation much more effectively than light-coloured ones so these get hotter.

A solar panel is a simple type of passive solar energy collector which uses circulating water to carry the heat for some purpose – perhaps for household hot water or for a swimming pool. The general principle is shown in Fig. 1. Water is pumped through tubing which is laid zig-zag fashion under a glass cover. The water becomes warm and gives its heat to other water in a heat-exchanger.

The tubing and other parts inside the panel are painted black to improve absorption of the sun's energy. The glass top

surface acts like a greenhouse, traps the sun's energy and improves the overall efficiency. It is necessary to use an electric pump to circulate the water through the panel and heat exchanger so, when calculating whether or not it is worthwhile to use the solar panel, it is essential to take into account the electrical power needed by the pump.

It is a useless exercise gathering less energy from the sun in terms of warm water than the pump uses! Microprocessor-based systems using temperature sensors may be used to switch on the pump only when it is advantageous to do so.

The solar panel will work fairly well even in Britain but, of course, it works much better in hot countries with more guaranteed sunshine. Under the best conditions, the water can emerge at 70 degrees C but it will not boil. More likely, especially in Britain, it will be made warm which, nevertheless, means that less fossil fuel or nuclear energy is needed to raise it to a useful temperature.

Solar panels are often seen on house roofs (see photograph) since here they can be



Solar panels (used for domestic water heating) incorporated into the roof of a house in South East London. (Martin Bond/Science Photo Library)



The parabolic reflector at Odeillo-Font-Romeau solar power station composed of 9,500 mirrors. The furnace is capable of generating 1MW of thermal power. (Tony Craddock/Science Photo Library)





Mirrors of the Luz Solar Power Station seen in moonlight. The 1.5 million mirrors concentrate the sun's light onto narrow tubes containing synthetic oil. The oil is then fed to a heat exchanger where it boils water to provide steam for turbines, this installation can generate 150MW of power. (Roger Reismeyer, Starlight/Science Photo Library)

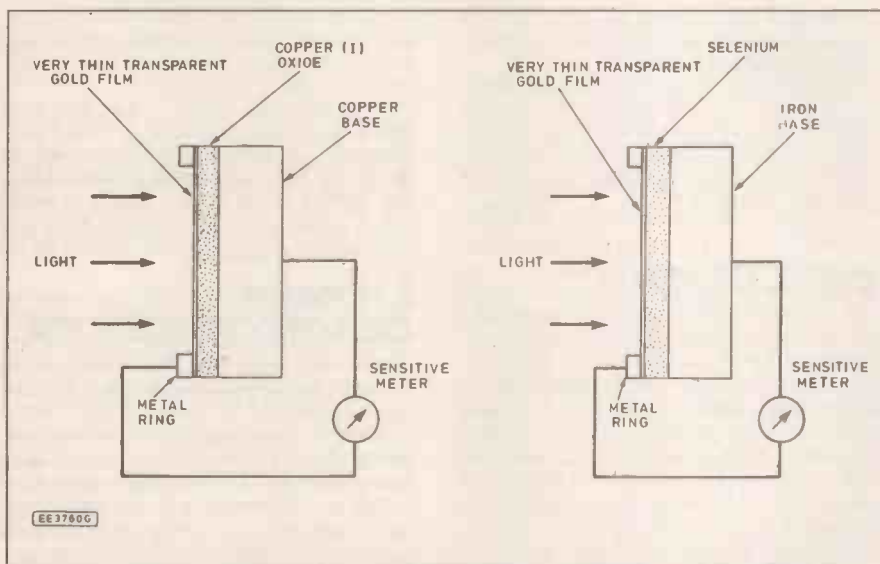


Fig. 2. Early photovoltaic cells.

angled to face the sun. Since a solar panel cannot raise the water to boiling point, it cannot generate steam. This means that it cannot be used to produce electricity using the cheap and well-developed technology of the turbo-generator. This, in practice, means that solar panels are limited to relatively small schemes for producing warm water. Even so, their contribution is worthwhile.

### SOLAR FURNACE

A solar furnace, on the other hand is designed to raise steam. Here, enormous mirrors concentrate the solar radiation to a focus. This works in a similar way to a hand lens which can focus the sun's rays and set a piece of paper alight. A boiler is placed at the focus and the water circulating through it rapidly boils. This makes steam and operates a conventional turbo-generator.

Unfortunately, the mirror needs to be of gigantic proportions – about 7000 square metres for each megawatt of electricity produced – and this is very expensive to construct. To generate 1000MW, would need a colossal mirror. Serious schemes using mirrors are used in Odeillo in the French Pyrenees (see photograph) and the United States where there is more-or-less guaranteed sunshine. At the focus of the rays, the temperature is sufficient to melt steel.

Of course, the solar furnace provides energy only during daytime. A further problem is that the sun appears to rise and set in the sky so there must be some means of tracking it and this involves even more expense. Due to high cost, large-scale use of solar furnaces for electricity generation is definitely a long-shot and it is difficult to see the method becoming economically viable in the future.

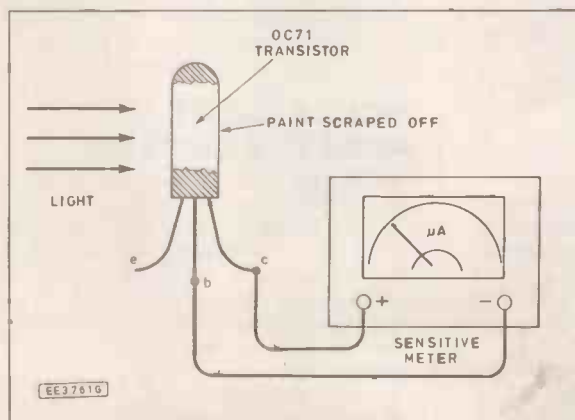


Fig. 3. The photovoltaic effect.

### SOLAR CELLS

A different approach is to use solar cells to convert the sun's energy directly into electricity without going through the steam stage. This uses a phenomenon called the photovoltaic effect. This was first observed by Antoine Becquerel in 1837 when sunlight shone on to one of his electrodes during an electrolysis experiment. The first "serious" devices, however, date from the 1870's and were based on the element selenium deposited on an iron base. More recently, a copper base coated with cuprous oxide – copper (I) oxide – was used (see Fig. 2).

In both cells, a very thin and therefore transparent gold film made a window through which the light passed. This made the front connection to the working material. The gold film was in contact with a metal ring around the periphery of the device and this formed one of the output terminals. The other connection was made to the base material at the back of the cell.

These cells develop a voltage of around 0.4V in bright light. However, they are very inefficient, converting only about one percent of the sun's energy striking the sensitive surface into electricity. They are sometimes used to measure light intensity (in, for example, some photographic exposure meters). Here, the cell output is connected to a microammeter with its scale calibrated in terms of light level instead of current.

Modern semiconductor devices are also photo-sensitive. Transistors and diodes are usually housed in opaque encapsulations to prevent light from entering. This prevents photovoltaic emission with possible unpredictable results when the device is built into a circuit. This effect may be demonstrated using an old OC71 germanium p.n.p. transistor. These are still available new from certain suppliers but are often to be found in junk boxes or in old equipment.

Such transistors are coated with black paint to prevent light from entering but this is easily scraped off to reveal the translucent encapsulation beneath. If this is done and the base wire (the centre one) is connected to the negative terminal of a 0-50µA meter (a multimeter set to its most sensitive d.c. current range) and either the collector or emitter wire touched on to the positive terminal, the photovoltaic effect may be observed. Thus, when sunlight falls on the transistor, a current of 10µA or more is registered (see Fig. 3). The working part is the junction between p and n-type germanium.


### MODERN DEVICES

More recently, purpose-made solar cells based on crystalline silicon have been developed. These also consist of junctions formed between p and n-type material. It is beyond the scope of this article to explain p and n-type semiconductor materials in terms of atomic structure – any reader interested in this topic should refer to a standard electronics or physics text book.

To understand basic operation, it must be realized that light has a dual nature. Although usually thought of as waves it may also be regarded as consisting of small particles called photons. Photons have energy and when they



A solar powered calculator.

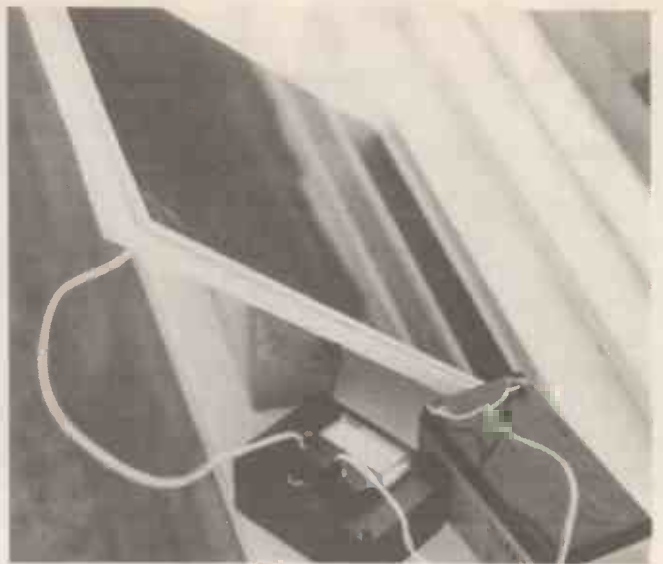

An experimental solar panel for battery charging.

strike the sensitive material they knock out electrons. When electrons are removed they leave regions of space deficient in electrons called *holes*. The electron-hole pairs can re-combine with electrons flowing in an external circuit back to the holes.

The greater the light intensity the more electron-hole pairs will be created and the greater will be the current. Unfortunately, electrons can re-combine with holes directly without going through an external circuit. Also, the electrical resistance of the material reduces the current and much of the energy is dissipated as waste heat.

Some of the radiation reflects from the surface without ever reaching the active region although making the surface black helps to minimize this effect. For this and other reasons, solar cells are not particularly efficient. Silicon solar cells can convert up to about 10 per cent of the energy striking them into electricity although a solar cell design based on *gallium arsenide* instead of silicon is said to produce 1V per cell with an efficiency of 25 per cent.

### SOLAR CELL USE

At present, probably the best use for solar cells is for small scale production of electricity. Solar-powered calculators are now commonplace but a more ambitious use is to provide the electrical energy needed for a satellite. These need electrical power to operate the electronic equipment on board – radio transmitters, receivers and so on. They can take advantage of the much more intense sunlight which exists in space.

At the earth's surface, much of the solar radiation has been absorbed by the atmosphere. In a satellite, a relatively small number of solar cells is therefore needed. In a typical installation, some 5000 cells are arranged on *solar sails* to provide a 30V supply delivering about 100W of power (see photograph in the *Information Technology* article).

One problem is that solar-powered equipment will only work when the light is strong enough. If necessary, this can be overcome by using the solar cells to charge a small battery which can then be drawn on when there is insufficient light – for example, in a solar-powered watch.

Solar-powered cars – and even solar aircraft – have been developed as experimental prototypes. Other more down-to-earth uses for solar cells include emergency telephones, marine beacons, radio

transmitters and receivers for use in remote regions, computerised information-gathering equipment and battery-chargers.

Solar cells may be used to charge batteries by day and provide electric lighting by night in regions too remote from a conventional electricity supply. They are also used to drive water irrigation pumps – it is even possible to make solar-powered refrigerators!

### CELL OUTPUT

A typical silicon solar cell provides a voltage of approximately 0.6V at a current of 15mA per square centimetre in bright sunlight. groups of cells can be connected in series to increase the voltage output (much in the same way as chemical cells are often connected in series for the same reason). They may also be connected in parallel to increase the current. A *series parallel* arrangement of solar cells is usually used to increase both the voltage and the current.

Single silicon solar cells and ready-made groups of cells (solar cell panels) may be bought quite cheaply and make an interesting basis for experiments in solar energy. For example, a typical small arrangement can produce an output of 12V at 50mA.

A more ambitious solar cell panel has a sensitive surface 30cm (1ft) square and can produce 12V at 200mA in bright sunlight (see photograph). This has a sensitive surface made from *amorphous silicon* coated thinly on a glass base. Although amorphous silicon is less efficient than the crystalline variety. It is much cheaper. Such a solar panel can operate various small pieces of electronic equipment direct or charge batteries so that the energy may be used later – in a caravan or boat, for example.

### SOLAR CELL POWER COSTS

Generating bulk electricity using solar cells, would be about ten times more expensive than by using conventional means at present prices. On the other hand, the cost of solar cells is coming down and the price of fossil fuels will rise in the medium term so this type of exercise – using land for “solar farming” – may possibly become attractive in the future.

In bright desert regions where the land is not much use for anything else, banks of solar cells could farm the sun's energy and provide large-scale electricity. It has been

estimated that 30,000 square kilometres of solar cells (an area of 100 miles square approximately) could provide the total electrical needs of the United States.

A fanciful idea is to place banks of solar cells in space to take advantage of the more powerful sunlight. The only problem would be getting the power down to earth where it is needed! Perhaps, the energy could be turned into *microwaves* and beamed down to receivers on the ground.

### LATEST DEVELOPMENTS

Now, after 20 years of research, Brian O'Regan and Michael Gratzel of the Institute of Physical Chemistry, Swiss Federal Institute of Technology in Lausanne Switzerland have developed a more advanced type of solar cell. This has an efficiency close to that of a conventional amorphous silicon cell i.e. around 7 to 12 per cent depending on conditions. Its importance is its *potentially low cost* rather than its efficiency. This is because it uses cheap and relatively impure materials in its construction.

In this cell, the working semiconductor material is a very thin layer of high surface area polycrystalline titanium dioxide. On to this surface is coated a special dye. Energy-harvesting molecules having an “antenna” arrangement absorb the sun's energy and channel it to the semiconductor surface. Advantages are to be gained by separating the jobs of energy absorption and electricity production in this way.

It is interesting to note that the natural phenomenon of photosynthesis also uses a molecular antenna system to direct solar energy to the chlorophyll. In this respect the new type of cell imitates nature.

It would seem that the direct use of solar power for large-scale generation of electricity is too expensive. Perhaps a better way forward is to exploit natural processes – wind, waves, biomass, etc. which already absorb the energy of the sun and put it into a more easily used form.

Next month: We shall examine in more detail the problems associated with using fossil fuels. We shall then look in some detail at wind energy as an example of existing alternative technology.



# NEW VIDEOS ON ELECTRONICS

Everyday Electronics is pleased to announce the availability of a range of videos designed to provide instruction on electronics theory. Each video gives a sound introduction and grounding in a specialised area of the subject. The tapes make learning both easier and more enjoyable than pure textbook or magazine study. They should prove particularly useful in schools, colleges, training departments and electronics clubs as well as to general hobbyists and those following distance learning courses etc.

The first three videos available are:

- ★ **1** *Electronics And You – Part 1: D.C. Series and parallel circuits and the use of a digital multimeter. Running time approx. 53 mins.*  
Order code VT201 **£29.95 inc. VAT**
- ★ **2** *Part 2: A.C. Coils, capacitors, transformers and other a.c. devices. Running time approx 71 mins.*  
Order code VT202 **£29.95 inc. VAT**
- ★ **3** *Part 3: Semiconductors. Basic semiconductor theory plus fifteen different semiconductor devices explained. Running time approx. 47 mins.*  
Order code VT203 **£29.95 inc. VAT**

Each video uses a mixture of animated current flow in circuits plus text, plus cartoon instruction etc., and a very full commentary to get the points across. The tapes are imported by us and originate from VCR Educational Products Co, an American supplier.

To order see our Direct Book Service "Ordering Details" – the postage for tapes is the same as for our range of books and you can order tapes and books at the same time and pay only one lot of postage.

(All videos are to the UK PAL standard on VHS tapes)

**£29.95**  
each



# SOLAR-POWERED LIGHTING UNIT

T. R. de VAUX-BALBIRNIE

"Free" power for the garden shed, boat or caravan.

## GREATER CAPACITY

Although most of the following description assumes that AA size cells are to be used as the supply, some readers will wish to use larger capacity batteries. This may be of no advantage during the winter because AA cells are sufficient to hold one day's worth of lighting energy (one hour maximum).

However, in situations where the light is not in daily use, it could be an advantage to allow the charge to accumulate over several days. Larger-capacity cells could then provide an extended period of occasional use. Note that AA cells having a slightly higher capacity – 600mAh rather than the more usual 500mAh – are available from some suppliers. It may be worthwhile using these.

By using standard (1.2Ah) C-size cells, approximately one hour's light may be expected on a three-day cycle even in the autumn. With these cells, a higher limiting

**T**HIS solar power supply was designed to provide lighting in a remote garden shed without having to rely on throw-away batteries. This may be cheaper than laying on a mains supply and is much safer. Also, being a low-voltage system, it is suitable for use by children.

A simple version will work as a trickle-charger for a 12V caravan or boat car-type battery. This will keep the battery in good condition during the out-of-season months and also allow limited use of the lights, water pump, etc. This may be found useful for the occasional visit to the caravan at night to recover odd items of crockery, the tin opener, etc.

The Solar-Powered Lighting Unit (Standard Version) will operate a small, inexpensive 12V 8W fluorescent light by charging a 12V nickel-cadmium battery pack during daylight hours. Tests carried out during late autumn on the prototype unit show that up to 20 minutes operation per day (depending on the available light) is available from an 8-watt fluorescent light. This will be found sufficient for most purposes. Even during the winter, a useful operating time will be available.

Taking account of the cost of the solar panel itself and the nickel-cadmium cells, this may be considered an expensive way of obtaining energy in the short-term even though the energy itself is free. However, it scores highly in terms of convenience since, once fitted, the installation can be forgotten and will always be ready to operate at peak efficiency. Using throw-away batteries to provide a similar light output would prove prohibitively expensive.

## USING SOLAR PANELS

The solar panel specified for the Solar-Powered Lighting Unit is 30cm (1ft) square and has a sensitive surface made from amorphous silicon. This provides a current output of 200mA in bright sunshine. In moderately bright autumn and winter weather, an output of 10mA to 20mA may be expected and 100mA is not uncommon.


These test figures were obtained with the solar panel placed behind a glass or plastic window since, in use, this will be necessary to protect it from the rain. To charge a caravan battery, the solar panel may be placed on a table near a south facing window using a wooden frame – or simply a pile of books – to point it slightly upwards to face the sun. Tests will need to be performed where windows are heavily tinted since these could reduce the efficiency.

The battery pack used in the prototype unit (standard version) consisted of ten AA size nickel-cadmium cells in a suitable holder. The maximum continuous charging current for these is 50mA approximately.

Since in bright summer sunshine this figure could be exceeded by a factor of four, it is necessary to provide some current-limiting to prevent damage. During the winter, the output current is normally less than 50mA so the limiting circuit will have little effect – it will simply reduce the charging current slightly – typically by 4mA.

A Normal/Boost switch is provided on the unit so that, in summer, the limiting circuit may be bypassed and the extra current used to "quick-charge" the battery pack. It may also be used during winter to squeeze every available milliamp out of the system. *In summer, this will need to be used with extreme care to prevent possible damage due to overcharging.*

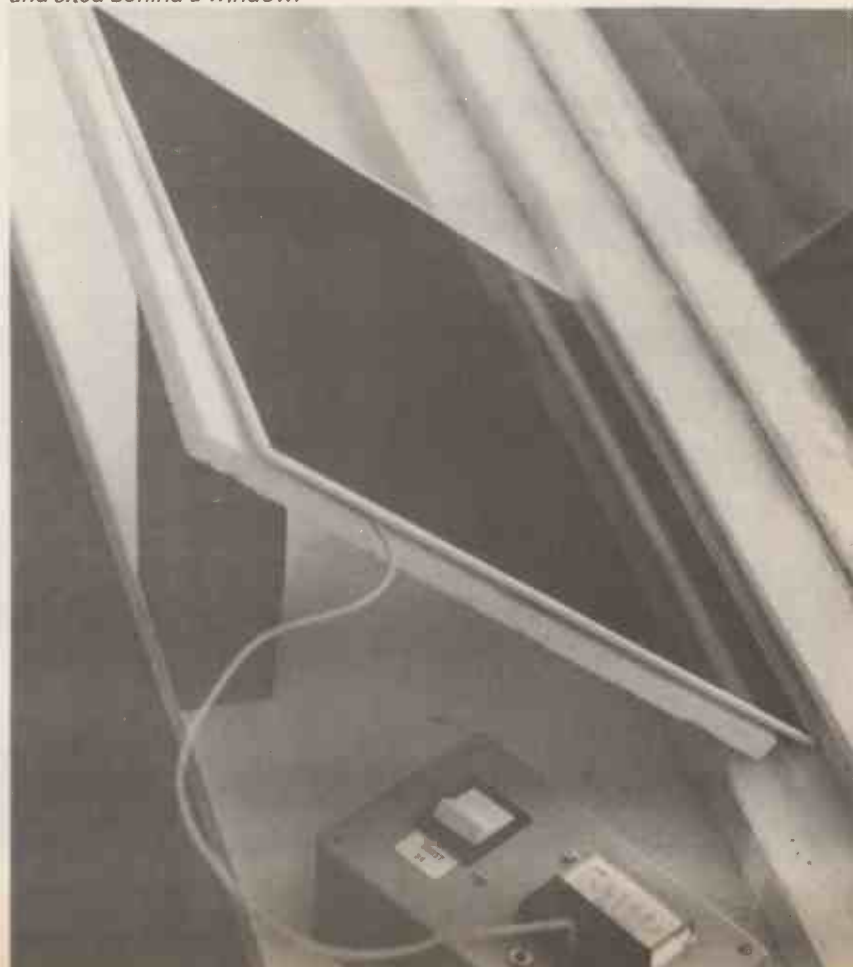*The 30cm solar panel plugged into the "Standard" prototype unit and sited behind a window.*





current – nominally 140mA – may be set to take advantage of the bright summer weather.

No current limit need be set when trickle-charging 12V car-type batteries or the smaller lead-acid batteries now available. This simplifies the circuit required and details for this are given later.

## POWER-IN

To provide a 12V supply, ten nickel-cadmium cells are needed. This is because this type of cell produces an output of only 1.2V instead of 1.5V for the conventional "throw-away" variety.

An AA size battery pack may be housed inside the main unit using the specified box (see photograph). For larger cells, a correspondingly larger box will be needed or the battery pack could, of course, be sited externally.

Plugs and sockets are used to make the external connections – a "power-in" type socket for the solar cell and a 3.5mm jack socket for the light. This ensures that these items are connected to the correct socket.

An ammeter may be mounted on the front panel (as in the prototype unit) to indicate the charging current – see photograph. This is useful for checking that the charge rate falls within specification and also to help in adjusting the mounting angle of the solar panel for best effect.

Costs could be saved by omitting the meter and connecting a multimeter to a pair of sockets on the unit instead. This would be used just for setting-up purposes then removed afterwards. When the multimeter is not in use, a link wire would simply connect the sockets together to maintain continuity. It is possible to avoid the use of a meter altogether, but the charging current would need to be taken on trust and positioning the solar panel carried out by common sense!

## LIGHTING-UP

Although a 12V 8W fluorescent light fitting is specified in the components list, it would be possible to increase the light output by using a 13W fitting. This would, of course, run down the battery pack in a correspondingly shorter time.

It may be appropriate to use the brighter lamp in some situations, especially where it is backed up by a high-capacity battery pack. However, in tests, the smaller 8W lamp was found to be perfectly adequate

for garden sheds and similar places. It is not really satisfactory to use filament lights – for a reasonable light output, these would run the battery down too quickly.

## CIRCUIT DESCRIPTION

For trickle charging lead/acid (car-type) batteries or nickel-cadmium cells which can accept a continuous charging current in excess of 200mA (industrial type C- or D-size cells – 2Ah and 4Ah respectively) refer to the circuit diagram shown in Fig. 1 (Car Battery Trickle-Charger). Here, current flows from the solar panel through diode, D1, meter ME1 and fuse FS1 hence through the battery being charged. Diode D1 prevents the battery from discharging back through the solar panel under dark conditions.

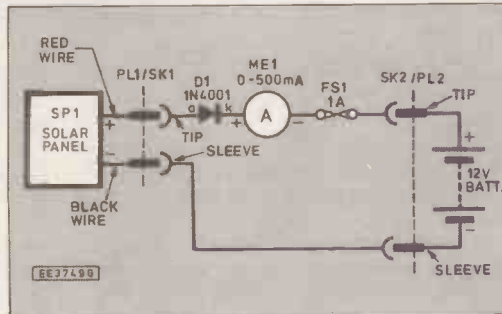



Fig. 1. Circuit diagram for the solar powered battery trickle-charger.

For charging nickel-cadmium batteries where a current limit needs to be set (50mA for AA size cells or 140mA approximately for C- or D-size commercial type cells) refer to Fig. 2 circuit diagram. Here, the main component is IC1 – an integrated circuit regulator.

Suppose the Normal/Boost switch, S1, is set to Normal for the moment. When bright light falls on solar panel, SP1, current is supplied to IC1 input, pin 1. Although IC1 is a sophisticated device providing on-chip regulation of voltage and current, in this application it is connected simply as a current limiter.

Fixed resistor, R1, connected between pin 5 and pin 2, sets the threshold current to the correct nominal level – 10 ohms for 50mA (for AA cells) or 3.3 ohms for 140mA (for commercial C-cells). If the current supplied by SP1 lies below this threshold, the regulator has little effect (it simply reduces the output current a little).

Fig. 2. Circuit diagram for the "current limited" Solar-Powered Lighting Unit.

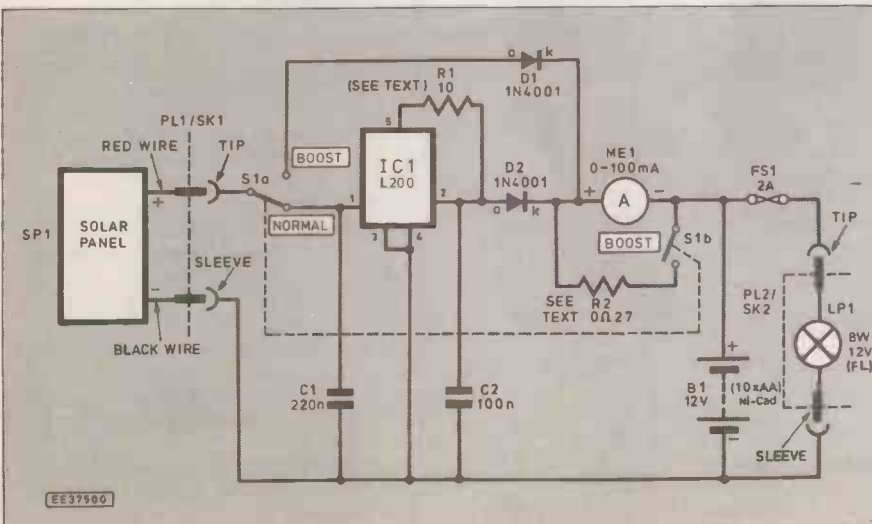

# COMPONENTS

## SIMPLE VERSION (Trickle-Charger)

### Semiconductor

D1 1N4001 50V 1A rect. diode

### Miscellaneous

SP1 30cm square amorphous silicon solar panel – output 12V at 200mA nominal

FS1 20mm chassis fuseholder, with 1A quick-blow fuse

PL1/SK1 3.5mm mono jack plug and matching chassis socket

PL2/SK2 2.1mm "power-in" plug and matching chassis socket

ME1 250mA or 500mA f.s.d. moving-coil panel meter, face size 51mm x 45mm approximately – see text

Plastic box, size 100mm x 75mm x 40mm, – see text; stranded connecting wire; nuts, bolts and washers; solder etc.

Approx cost  
guidance only

£20

## STANDARD VERSION (Current Limited)

See  
SHOP  
TALK  
Page

### Resistor

R1 10 ohms (for AA size cells)  
3.3 ohms (for commercial  
C- and D- size cells – see  
text)

R2 0.27 or 0.2 ohms (4 or 5  
off 1 ohm – see text)

All resistors 0.25W 5% metal film

### Capacitors

C1 220n ceramic

C2 100n ceramic

### Semiconductors

D1, D2 1N4001 50V 1A rectifier  
diodes (2 off)

IC1 L200CV adjustable voltage  
and current regulator in  
Pentawatt package

### Miscellaneous

SP1 30cm square amorphous  
silicon solar panel – output  
12V at 200mA nominal

B1 AA size nickel-cadmium cells  
(10 off) and holder – see  
text

S1 Miniature d.p.s.t. toggle  
or slide switch

FS1 20mm chassis fuseholder,  
with 2A quick-blow fuse

PL1/SK1 3.5mm mono jack plug and  
matching chassis socket

PL2/SK2 2.1mm "power-in" plug and  
matching chassis socket

SK3/SK4 2mm sockets – if required.  
See text. (2 off)

ME1 100mA f.s.d. moving-coil  
panel meter, face size  
51mm x 45mm

LP1 12V 8W fluorescent light  
fitting

Stripboard 0.1in matrix, size 10 strips  
x 18 holes; plastic box, size 150mm x  
90mm x 52mm approx; battery connector  
for battery holder; stranded connecting  
wire; nuts, bolts and washers, solder etc.

Approx cost  
guidance only

£25

excluding Light & Batts

When the input current rises above the threshold, a steady output current equal to the threshold is obtained from pin 2 with the excess energy being dissipated as heat. IC1 is amply-rated and the power developed will never be great enough to warrant the use of a heatsink.

The output current from IC1 charges the battery pack, B1, with current flowing through diode, D2, milliammeter, ME1, (or external meter via 2mm plugs and sockets) and fuse, FS1. Diode, D2, prevents the cells from discharging back into IC1 when the solar panel is in dim light, during the night for example.

## BOOST

When the Normal/Boost switch is set to Boost, two things happen. The switch pole of S1a disconnects the solar panel from IC1 input, pin 1, and connects it instead to the output via diode D1. This allows the maximum current provided by the solar panel to flow to the battery pack.

Meanwhile, switch S1b pole shunts fixed resistor, R2, across the meter terminals. The value of this resistor is chosen to bypass three times the meter current through itself. In practice this means that resistor R2 should have a value of one-third that of the meter. The meter scale is then effectively multiplied by four i.e. its full-scale deflection is 400mA.

Diode D1 prevents the battery pack from discharging through the solar panel under dark conditions when switch S1 is set to Boost. Capacitors, C1 and C2 are necessary to provide electrical stability to IC1.

A fluorescent light is much brighter for a given current input than a filament lamp. Note, however, that a fluorescent light designed for 12V operation *must* be used. This already contains the necessary inverter which increases the low input voltage to that needed to operate the fluorescent tube. These lights are stocked by mail-order suppliers or may be obtained from camping and caravanning shops.

Holders for ten AA cells are available from some suppliers. Otherwise, use a

holder for six and a holder for four (or some other suitable combination) connected in series. This will also be necessary where cells other than AA size are used since holders for ten of any other type do not appear to be available.

## CONSTRUCTION

If constructing the simple circuit (Car Battery Trickle-Charger - Fig. 1), i.e. having no current-limiting, this needs no circuit panel. The only active component is diode, D1, and this is suspended in the wiring.

Follow the wiring layout photograph/diagram shown in Fig. 3, noting the polarity of the meter and of diode D1. The meter should have an f.s.d. (full-scale deflection) of 250mA or 500mA.

If constructing the standard version circuit, having current-limiting, refer to Fig. 4. First calculate the value needed for resistor R2. The internal resistance of the specified type of meter is typically 0.6 to 0.8 ohms and will be found in the supplier's or manufacturer's data.

For a 0.6 ohm meter, R2 will need to have a value of 0.2 ohms and for a 0.8 ohm meter, R2 will need to be 0.27 ohms approximately. This value is not too critical since great accuracy is not required. In any case, there is a certain amount of contact resistance in the switch which can cause deviations.



It is possible to buy single resistors having these values but they will probably be of the bulky high-power type. A cheaper and more compact solution is to buy four (for 0.8 ohms internal resistance) or five (for 0.6 ohms internal resistance) one ohm resistors and connect them in parallel as shown. This will give values for 0.25 ohms and 0.2 ohms respectively.

For other meter resistances work accordingly. Fig. 4 shows four one ohm resistors in parallel on the circuit panel but there is space for a fifth one if required.

## STANDARD VERSION

Construction of the Standard Version of the Solar-Powered Lighting Unit is based on a circuit board made from a piece of 0.1 in. matrix stripboard, size 10 strips x 18 holes. Cut this to size and solder the link wire used to inter-connect IC1 pin 3 and pin 4.

The standard version stripboard component layout is shown in Fig. 4. The regulator IC1 comes in a rather curious 5-pin "Pentawatt" package. Bend its pins gently to conform with the stripboard matrix and, noting its orientation, insert them through the holes and solder the device into position using minimum heat from the soldering iron.

Follow with the other on-board components noting that diodes D1 and D2 must be connected the correct way round as indicated. Drill the two fixing holes and solder 8cm pieces of light-duty stranded connecting wire to copper strips B, C, D, E and F along the left-handed side as shown.

## CASE

Prepare the box by making holes for the regulator IC1, fuse FS1, sockets SK1 (for solar panel connection) and SK2 (for the light), for circuit panel and battery holder mounting according to type (see photograph). Make holes for the multitester sockets if needed.

Make a large hole for the meter. This may be done by drilling a circle of small holes then joining them together using a small hacksaw blade. The hole need not be particularly neat since the edge will be covered over when the meter is in position.

Mount all components. Note that everything, apart from the battery pack, is mounted on the lid of the case. This keeps the wiring short and neat and imposes less strain on it.

Referring to Fig. 5, complete the inter-wiring shortening any wires as necessary. Note the polarity of the meter. If 2mm


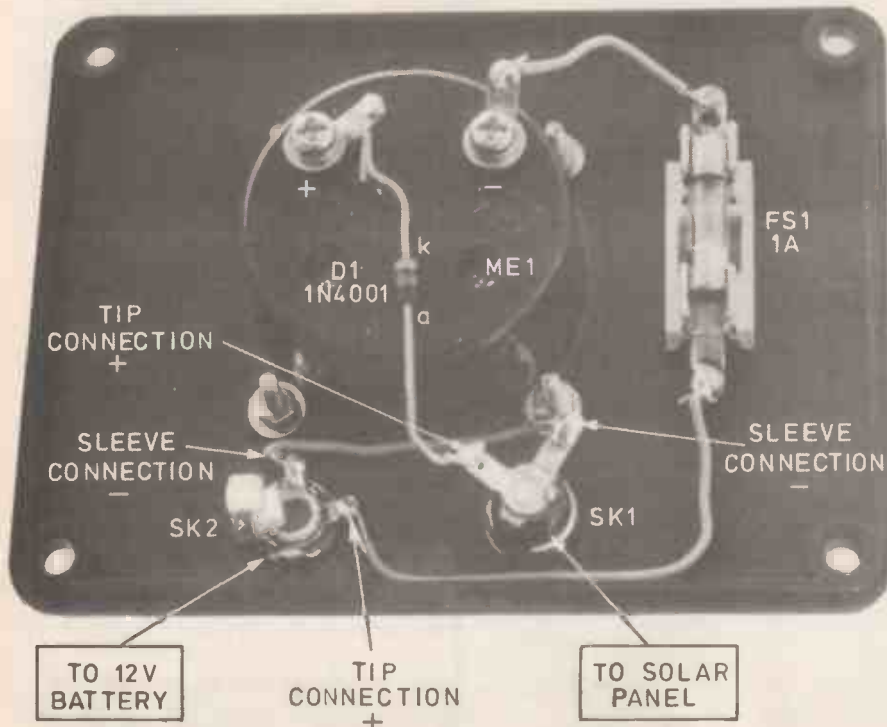


Fig. 3. Component layout and interwiring for the Simple Trickle-Charger version.

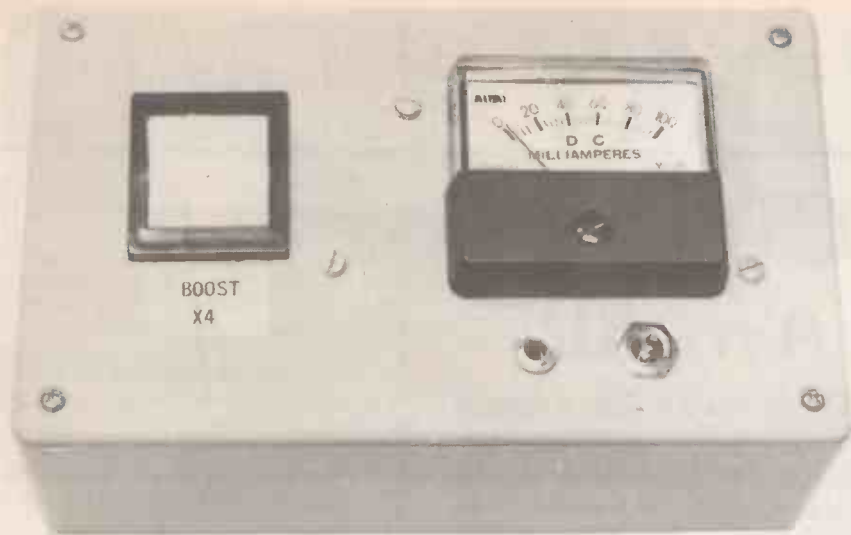



Front panel component layout of the Standard Version showing the "boost" switch position.

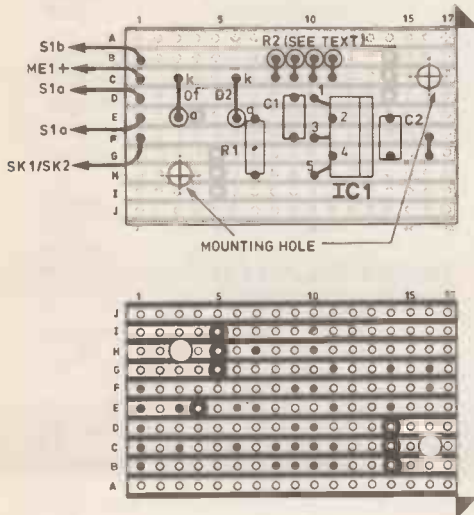


Fig. 4. Stripboard component layout and details of breaks required in the underside copper tracks.

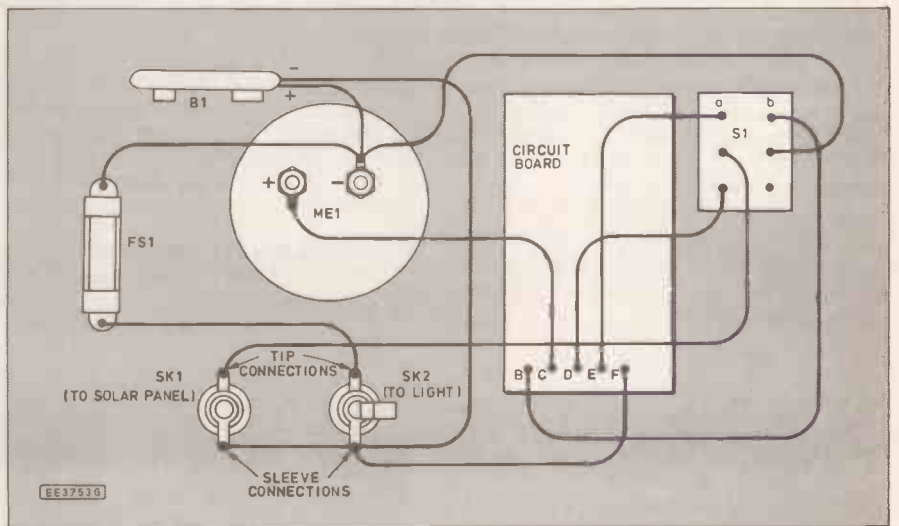


Fig. 5. Component layout and interwiring for the Standard Version. All components, except the battery holder, are mounted on the rear of the case lid.

sockets have been fitted for a multimeter to be used, make up a short lead with matching plugs on the ends so that the sockets may be linked together when the meter is disconnected. Place the cells in their holder and connect them up. Insert the fuse into its holder.

Check that the lid fits – it may be necessary to bend the switch tags slightly to give sufficient clearance. This must be done with great care since it is very easy to crack the plastic body. It is best done by gripping the tag with fine-nose pliers close to the body then bending it with a second pair of pliers.

## SETTING-UP AND TESTING

Prepare the solar panel by fitting a suitable length of flexible 2-core wire terminating in the 2.1mm power-in plug. Do not try to remove the existing wires soldered to the solar cell output since damage could easily result. Instead, shorten these wires and make soldered and sleeved connections to the new lead. Tape the wire securely to the back of the panel to provide some strain relief. Prepare the light by attaching the 3.5mm jack plug to the end of the wires taking care over the polarity.

In sunny summer conditions, testing the unit could result in overcharging the batteries – especially if AA size are used. This may be avoided by starting tests with the

Select a suitable site for the solar panel. This must not be placed in the open but behind a window to protect it from the weather. Switch S1 to "Boost" and adjust the direction of the panel for best overall effect. This may be revealed by checking the output current every so often. If no meter is used, then direct the solar panel by common sense.

Check operation of the Boost/Normal switch in the Normal position. Providing the light is bright enough, the meter should read the limit preset by resistor R1 – approximately 50mA or 140mA as appropriate. Otherwise a reading will be given depending on the amount of light falling on the panel. Note that if using the unit to charge a caravan battery, any existing charger should first be disconnected.

During the summer, boost charging at 200mA may be carried out on AA size cells


batteries in a discharged state. Switch the light on to discharge them if necessary.

They may now be safely charged at up to 250mA for two hours or so. With higher-capacity cells, greater liberties may be taken. If a built-in meter has not been used, the multimeter set to an appropriate d.c. current range should be connected to the 2mm sockets observing the polarity.

for two hours providing the cells are in a discharged state. In the winter, the switch may be set to Boost continuously providing the current remains below 50mA. This will add a few milliamps to the charging current.

It only remains to label the switch and put the Solar-Powered Lighting Unit into service. □

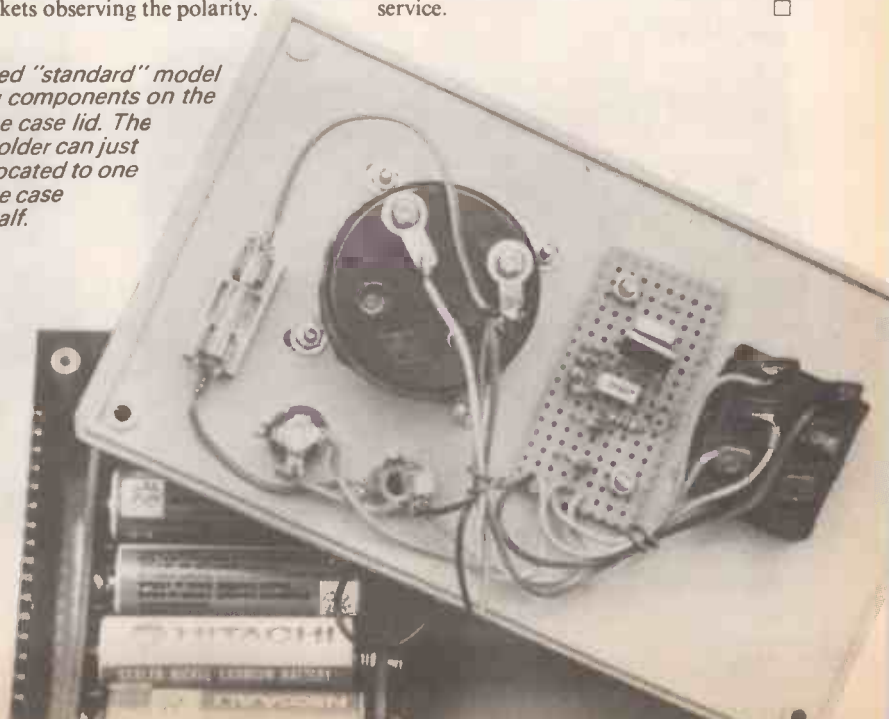Completed "standard" model showing components on the rear of the case lid. The battery holder can just be seen located to one side of the case bottom half.



# EVERYDAY NEWS

## YOUNG ELECTRONIC DESIGNER AWARD

**THE winners of the 1992 Young Electronic Designer Award (YEDA) were announced recently at the Science Museum, where HRH The Duke of York made the presentations to successful finalists. The Young Electronic Designer Awards scheme is open to students in secondary schools, colleges and universities between the ages of 12 and 25, and challenges young designers to invent and produce an electronic device that meets an everyday need.**

Presenting the awards, the Duke of York said, "Of course, electronics has a special significance to me in my career with the Royal Navy. Our aircraft and ships depend very largely on electronics in instrumentation, as well as control and communications. I was therefore particularly interested to accept this engagement to see how schools and universities are applying today's technology."

### SENIOR CATEGORY (18-25 years inclusive)

- 1st - YEDA Trophy, £1,000 and course sponsorship: Jeff Crofts (22), Royal Naval Engineering College, Plymouth - The Midi Accompanist.
- 2nd - £500: Stefan Cook (23), Cheltenham & Gloucester College of Higher Education - The Mouse Emulator.
- 3rd - £250: William James (19), Kings College, Taunton, Somerset - A fully controllable print and film driver.

### INTERMEDIATE CATEGORY (15-17 years inclusive)

- 1st - YEDA Trophy, £750: Mark Stewart (17), Cowes High School, Isle of Wight - Beam music design to encourage movement in handicapped children.

2nd - £200: Marion Hore (18), Farnborough Sixth Form College, Hampshire - A water flow meter.

3rd - £200: Benjamin Brierton (17), Mortimer Wilson School, Derby - A bike alarm.

### JUNIOR CATEGORY (Under 15 years)

1st - YEDA Trophy, £500: David Issott (15) and Tom McEwan (14), Cheltenham College - A portable monitor to evaluate the presence of carbon monoxide.

2nd - £250: Lucy Boize (14) and Claire Guerlain (14), Woldingham School - An electronic digital destination display for a bus.

3rd - £150: Jonathan Pepper (15) and Nick Davies (14), Cheltenham College - An iron for the blind, partially sighted, elderly or handicapped.

### SCHOOLS PRIZES

Joint winners of the Texas Instruments Award - £2,500 (divided) for the most commercially viable project:

Mark Stewart (17), Cowes High School, Isle of Wight - Beam music design to encourage movement in handicapped children.

BEAM MUSIC was designed for use with handicapped children, but can be used for various other applications.

Handicapped children respond well to music, and by breaking the light beams notes can be played. The computer can generate the notes internally or alternatively send them to a keyboard. This allows high quality sounds to be created and accompaniments to be added. Popular tunes can be played using this setup.

Beam Music is not limited to just music. It can be used with various computer games etc, the frame is used in a similar way to a joystick.

Jonathan Pepper (15) and Nick Davies (14), Cheltenham College - An iron for the blind, partially sighted, elderly or handicapped.

SAFE-N-EASY is a standard iron, modified in several ways to provide extra safety and to make it easier to use. Firstly, an auto-turn-off feature is included, so that the iron will turn itself off after 30 seconds if left flat, or 5 minutes if left upright.

Secondly, for ease of use, the iron sounds an audible warning as the water in the reservoir reaches the maximum level during the filling operation. A further alarm option alerts the user to the fact that the water in the reservoir requires replenishment.

A small internally mounted NiCad battery, which is recharged during normal use, provides power to the alarm circuit.

Mercury 'Planet' Award - £2,500 for the most environmentally/socially aware technology.

David Issott (15) and Tom McEwan (14), Cheltenham College - A portable monitor to evaluate the presence of carbon monoxide.

The COSMOS detects different levels of carbon monoxide concentration. It gives an accurate reading and is very concerned with safety and warning if an area is unhealthy.

The sensor uses nine l.e.d.s, one each to warn when the batteries are low, when you can start taking readings that are valid, and seven to tell you the concentration of carbon monoxide in the immediate atmosphere.



HRH the Duke of York who presented the Young Electronic Designer Awards discusses Farnborough Sixth Form College student Marion Hore's project, a Water Flow Meter.



First place in the Intermediate Category of the Young Electronic Designer Awards went to Cowes High School student Mark Stewart (17) for his project, Beam Music.



# NEW IMAGING TECHNIQUE

A NEW, safe technique for looking inside the body was demonstrated in London recently. The patient wears a belt which carries, on the inside, regularly-placed contacts which allow current (5mA at 50kHz) to flow into the skin. If the voltage is applied to one pair of contacts (1 and 2 in Fig. 1a) the pattern of current paths (dotted lines) is set up. If a sensitive voltmeter is placed at another pair (e.g. 3 and 4) a small voltage is picked up.

If the medium through which the current flows (in this case the body) is not electrically uniform but contains an insulating region such as an air pocket then the current paths are distorted (Fig. 1b). For a constructive anomaly such as a blood clot the paths are distorted in a different way. Voltages picked up by detectors at contact pairs such as 4 and 5 are now slightly different.

In the system developed by Sheffield University and the Royal Hallamshire Hospital 16 contacts are used. The driving voltage is commuted so that it is applied successively to every

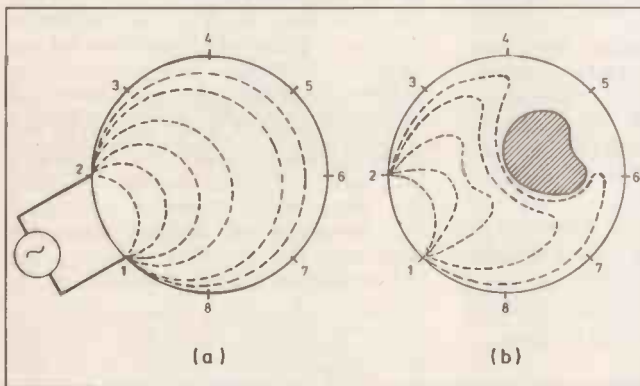


Fig. 1. Electrical Impedance Tomography. (a) Current paths through uniform object. (b) Paths distorted by an insulating region.

pair of adjacent contacts (1 and 2, 2 and 3, 3 and 4 etc) and measurements are logged automatically for every non-driven pair in succession. After computing, these yield an image of the slice of the body which is encircled by the belt.

The first, rather simple system is being used to monitor the contents of the stomach. A conducting liquid (fruit juice) drunk by the patient produces an image showing how the stomach walls move as the liquid slowly passes through. In this way abnormal stomach contractions can be identified.

A "print out" in the form of a bar graph records changes in stomach volume and is useful for diagnosis. The Sheffield team (led by Professor of Medical Physics, Brian Brown) has now developed a real-time system which should enable doctors to study blood flow and breathing. The British Technology Group is doing the marketing.

The technique has two names, Applied Potential Tomography and (preferred) Electrical Impedance Tomography. Teams in many centres are working on it. From the medical point of view its attractions are safety, comfort, portability and low cost. A simple system should cost about £15,000 and a real-time system about twice this. Comparable alternatives like magnetic resonance scanners cost £1 million or more.

Present systems display the "slice" as a circle, not as the actual shape of the body. Ways of correcting this distortion (which could be important if the image is to be used to guide surgery) are being explored. So is a possible extension to brain scanning to pinpoint the foci of epileptic seizures.

Electrical Impedance Tomography is a perfectly general technique with applications far removed from medicine. One team is using it to examine core samples drilled out during oil exploration. It might also be adapted as a geological tool to examine underlying strata or by archaeologists to detect buried buildings.

The Sheffield system is essentially a detector of changing images. An alternative, under development at the Rensselaer Polytechnic in the USA applies current simultaneously to all electrodes and generates a static image. (Successive static frames can of course be stored and played back in sequence to give a moving picture.)

## High-Speed Mass-Storage Medium of the Future

The first Sharp Palmtops and Notebooks with "flash memories" are already on the market. These new storage media could soon make conventional disk drives and hard disks with their sensitive, slow reading mechanisms obsolete. According to Dataquest, Intel, the US semiconductor giant, has over 85 per cent of the market for these new mass-storage devices. Sharp sees a wide range of potential applications for this exciting new storage technology in their products. Both companies have recently signed an agreement calling for long-term cooperation in the development and production of flash memories.

Flash memories are highly integrated storage devices that are faster and less prone to failure than conventional drives because they have no moving parts. First of all, they can be used as ROMs, which means that data remains intact without power. On the other hand, they can also be erased and rewritten, which makes them more like RAMs. However, they most resemble EEPROMs, electrically erasable read-only memories.

As the name implies, flash memories use a very fast, strong pulse of current for erasing. Both operations, erasing and writing, take place within the system and not, as is the case of conventional EEPROMs, in separate accessory devices. In addition, flash memories are designed to handle up to several hundred thousand erase-rewrite cycles. Due to the high degree of integration and the low number of components required per information unit, a single tiny chip can combine a storage capacity of 1 Mbit with an access time of under 100 ns!

## SIXTEEN BY NINE

The shape of things to come TV wise appears to be 16:9. Philips components are now producing a range of "Cineline 16:9 wide screen picture tubes" and 16:9 sets are now available. Wide screens represent a large piece of glass and well developed technology; like most forms of technology the c.r.t. is continually being improved.

The latest picture tubes from Philips have higher brightness, improved contrast and better colour, mainly due to the use of invar rather than iron for the shadowmask. This enables greater beam energies to be used producing higher brightness and allowing darker tinted glass which gives better contrast.

Shown here are three new 16:9 tubes, two of which (36 inch and 28 inch) are now available in Philips sets. The tubes are made by Philips Components at their factory in Aachen, Germany



# INFORMATION TECHNOLOGY AND THE NATIONAL CURRICULUM

T. R. de VAUX BALBIRNIE



PART 10

**T**HIS is the tenth in a 12-part series concerning Information Technology, communication systems and related matters in and around the Science National Curriculum.

This month we shall explore the use of IT devices in monitoring and controlling experiments. We shall follow with a look at the operation of modern communications devices in the transmission of large amounts of information including some economic and social implications.

## COMPUTER MONITORING

Computer monitoring no longer involves the makeshift methods which were necessary only a few years ago. There is now available a wide range of devices to suit all types of experiments in science and technology. Electrical quantities such as current, voltage and charge may be monitored as well as non-electrical ones such as temperature, humidity, sound level, magnetic field strength, position, light intensity, pH and oxygen levels.

To monitor any of these, a sensor is

plugged into the host computer – often via a connecting box – and the software provided by the manufacturer loaded from disc. The computer samples the variable being measured at specific time intervals and processes it. It may then display the results in the form of tables and graphs. It can also operate a printer to give a permanent “hard” copy of the results. Data may be saved on disc and re-loaded at a future date. It may then be compared with new results.

The BBC computer is still widely used by schools for monitoring since it is well supported by software. Also, these computers are common in schools and colleges and will be for some time to come.

## AT LOGGERHEADS

An extension to computer monitoring is *data logging*. Here, the sensor is plugged into a portable *logging box* which has its own memory. This may be carried anywhere – even where a mains supply is unavailable – because it is battery-powered. This could be particularly useful


for biology experiments carried out in the field. The data logger may be left to gather information over an extended time period if necessary.

In the case of the Unilab “Simple Logger” (illustrated) samples may be taken at any time intervals between 200 $\mu$ s and seven days. Afterwards, the logger is taken back to the laboratory and plugged into the computer. The data in the logger’s memory is then unloaded and the results processed, displayed and printed as in “straight” computer monitoring.

It is best for this type of work to be addressed at various times during the course while doing topics in technology, chemistry, physics, biology, etc. It will then crop up naturally several times during the course of a year. It would not be altogether successful to have a “data logging day” unless, of course, the equipment has to be borrowed and was only available for a short time.

Computer data-gathering techniques are readily understood by students of a wide ability range. For the more able, much more work can be covered in a given time than by using traditional methods. Also, the results can be processed in various ways, some of which would involve a great deal of work otherwise. For the less able, results are obtained without the use of mathematics and this generates enthusiasm to continue where otherwise they would lose interest. Data loggers are ideal for students who find mathematics difficult since this method frees them to see the *science* in the experiment rather than being bogged down by the maths.

On the other hand, this can be the downfall of this method if it is not used sympathetically. Traditional skills are easily abandoned and this would be a big mistake. Setting-up apparatus, using measuring instruments, gathering information, drawing tables and graphs, processing and evaluating the results are as important today as they have ever been. It is essential that new technology is used *alongside* traditional methods and not as a substitute for them.

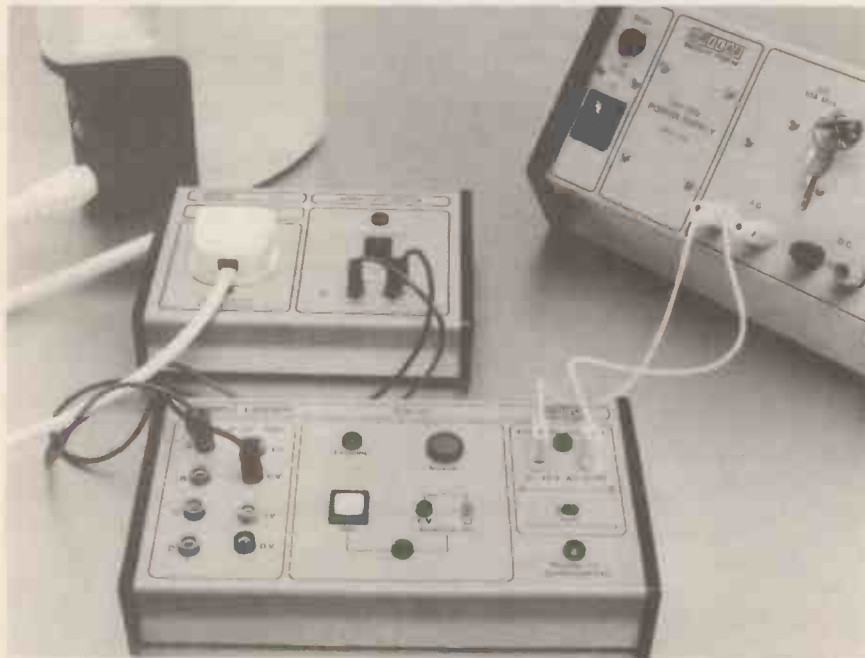

The Unilab Simple Logger in use.



## MONITORING ILLUSTRATION

To illustrate computer monitoring and data logging, let us examine a typical package – the temperature module from the Philip Harris range. For simple monitoring a temperature sensor, connecting box, a BBC computer and the software supplied on disc are needed. For data logging, in addition to the computer and sensor, you need the special data logging box and a different piece of software.

For collecting data in the laboratory, the temperature sensor is first plugged into the connecting box and this, in turn, is plugged into the analogue input socket on the computer. The software is then loaded. The appropriate sensor is selected from the main menu. The temperature range to be covered is now chosen: 0°C to 100°C, -10°C to 40°C or any 10°C span between 10°C and 40°C.

It is also necessary to calibrate the sensor against a known temperature such as a beaker of water whose temperature has been measured using a mercury thermometer. The red function keys are programmed by the software to produce various results. For example, f3 saves data on disc, f4 loads data from disc, f5 re-scales the axes and so on.

## COMPUTER CONTROL

The computer is a necessary part of modern control systems. Some knowledge of this is appropriate to various technology courses but could apply to some science topics too.

As with computer monitoring, there is now available a range of devices together with supporting software to control a system or experiment such as a robot arm, lathe or buggy. It could also operate a motor to stir a liquid at specified time intervals, switch on electrical appliances, control stage lighting or operate hydraulic or pneumatic systems. It could control gas valves to admit oxygen or carbon dioxide into a system during a biology experiment. The possibilities are endless.

## LARGE-SCALE COMMUNICATION SYSTEMS

The invention of the electric telegraph in the early part of the 19th century revolutionised communication – see Part 1 of this series (November, 1991 issue). It meant that a message could be sent hundreds of miles and a reply received within minutes. This was such a monumental advance that no one worried about its chief drawback – only one message at a time could be sent along the line. The early telephone suffered from the same disadvantage.

Today, we exchange enormous amounts of information with all parts of the world. Some of this sent by telephone (using copper wire, optical fibre or a combination of the two) – this includes private and business conversations, telex, fax (facsimile transmission) and binary

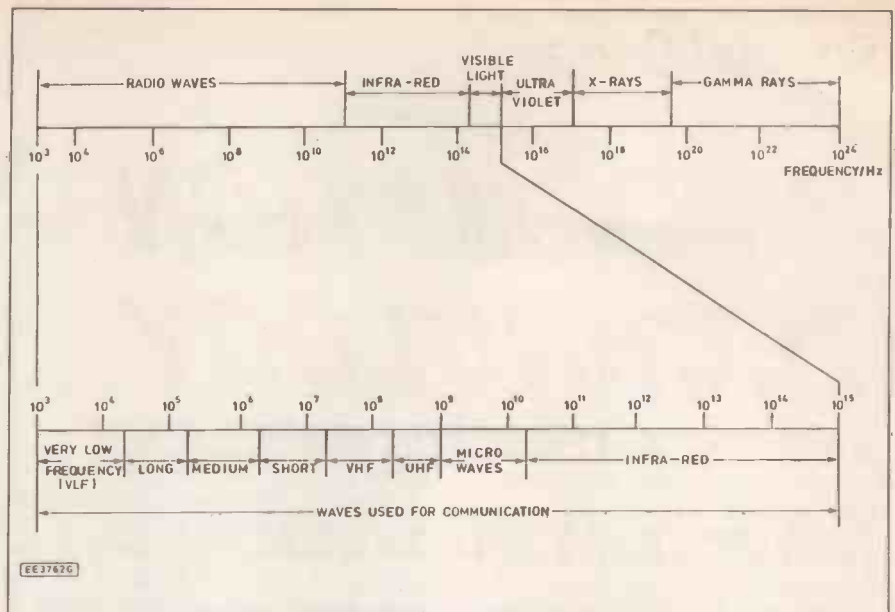


Fig. 1. The electromagnetic spectrum.

data being transferred between computers.

Some information is sent by radio using, perhaps, satellite links. This includes telephone conversations, radio and television broadcasts, use by emergency services, links with ships at sea and military communications.

All waves used for communication purposes are members of the wide family of *electromagnetic waves*. All members of this family have important properties in common. For example, they all travel at the same speed – 300,000 kilometres per second (186,000 miles per second in free space) – the so-called *speed of light*. Fig. 1 shows the entire electromagnetic spectrum and it will be noted that it covers a vast range of frequencies – that is, the number of waves per second expressed in Hertz (Hz).

The frequencies are indicated using a type of mathematical shorthand called *standard form*. This avoids writing a lot of zeros. Thus,  $10^3\text{Hz}$  means 1000Hz (that is, 1 followed by three zeros). By the same rule,  $10^{14}\text{Hz}$  means 10 followed by 14 zeros! Note also that 1kHz (kilohertz) = 1000Hz, 1MHz (megahertz) = 1000kHz and 1GHz (gigahertz) = 1000MHz.

At one end of the scale, very low frequency radio waves extend from 1kHz or so and at the other end, gamma rays (emitted by radioactive materials) have frequencies of many millions of GHz. Note how the radio wave frequencies blend into *infra-red* which then become *visible light*. It is these waves which are used for communication purposes.

## THE APPROPRIATE FREQUENCY

It is found that waves of different frequencies have subtle differences in their properties – this allows us to choose the best frequency for a particular job. Very low frequency (VLF) radio waves penetrate water reasonably well whereas the higher frequencies are absorbed very quickly. VLF waves are therefore used to communicate with submarines.

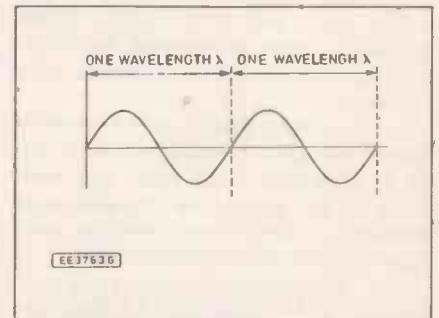


Fig. 2. Wavelength of a wave.

For much longer-range communication, waves of a low to medium frequency are used – so-called, *short*, *medium* and *long* waves. Note that the terms *short*, *medium* and *long* here refer to the *wavelength* (the size of one complete wave – see Fig. 2) rather than the frequency. We find that waves of short wavelength have a high frequency and vice-versa. Think of someone throwing pebbles. If many pebbles are thrown per second (high frequency) the space between them in flight (representing the wavelength) will be small. If fewer are thrown per second, the space between them will be larger.

Today, it is usual to refer to the *frequency* of a wave rather than its wavelength but this has not always been the case. For historical reasons, therefore, terms such as *short* (i.e. high-frequency) waves are still widely used and are often seen marked on the tuning dials of older radio receivers.

## CHARGED LAYERS

Waves of a frequency less than about 30MHz reflect from layers of charged particles (called the ionosphere) which exist some 80 to 500km above the earth (see Fig. 3). If such waves are transmitted upwards at an angle, they tend to reflect back to earth some distance from the transmitter. They may then reflect from the earth back to the ionosphere and repeatedly “skip” several times before,

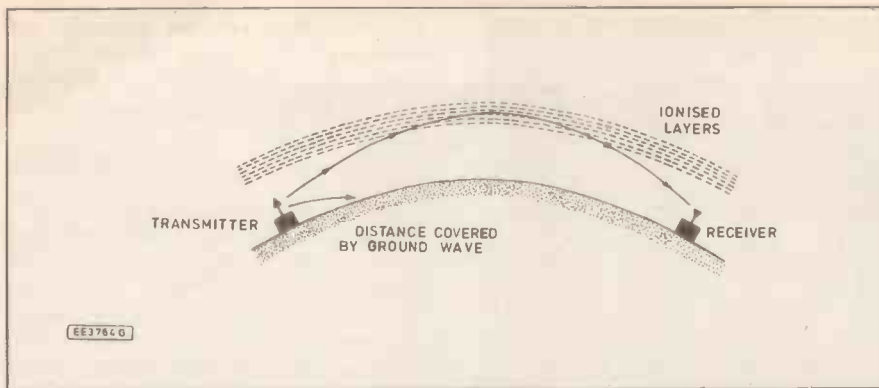


Fig. 3. Reflection of waves by ionised layers.

eventually, reaching their destination or become too weak to be intelligible.

Repeated reflection can give these radio waves a very large range when conditions are favourable. However, this is rather unreliable as it depends on the reflecting state of the ionosphere which, in turn, depends on the time of day, the 11 year sunspot cycle and other factors. Radio amateurs know how to exploit this. However, commercial systems demand reliable operation.

Long (low frequency) waves tend to spread out around the curvature of the earth so gain a large range this way. They can also pass round obstructions by diffraction making them ideal for communications in mountainous areas.

Very high frequencies (VHF) and even more so, ultra high frequencies (UHF) are close to visible light in the electromagnetic spectrum – they therefore have light-like properties. Such waves are used for regional radio and television broadcasts because they operate chiefly within line-of-sight of the transmitter. They are not picked up very well by receivers over the horizon or behind mountains. The transmitter service areas are therefore easily predicted and will not overlap with adjacent ones. The same frequencies may therefore be used for broadcasts in other areas without interference.

The highest frequency (shortest wavelength) radio waves are called microwaves. Apart from their use in cooking, they are used for radar (which includes monitoring the positions and speed of aircraft and ships, control of traffic lights, police speed detectors, etc.

Microwaves are very close to light in the electromagnetic spectrum, so in many respects, they behave like light. They reflect from certain objects very well rather than passing through them, being absorbed or going round them. This makes them ideal for the jobs just mentioned. Aerials used to transmit (and receive) microwaves are located in a dish reflector which projects them in a beam – this is rather like the reflector in a torch or car headlight and serves to emphasise the light-like properties of these waves.

Depending on the frequency of the radio waves, they may reach their destination by direct line of sight, by following the curvature of the earth or by reflection from the ionosphere. Otherwise they may pass through the ionosphere and be lost in

space or they may be absorbed by an object in their path. The foregoing is a much simplified account. Anyone seriously interested in this vast topic – for example, if they wish to study for the radio amateur exam – should consult a textbook on the subject.

### SEPARATION

It is found that information carried using one frequency of radio waves will remain separate from that using a different frequency. The receiver is simply "tuned" to the frequency required. This may suggest that any number of simultaneous signals may be sent by radio because there is an infinite number of frequencies available. This, however, is not the case.

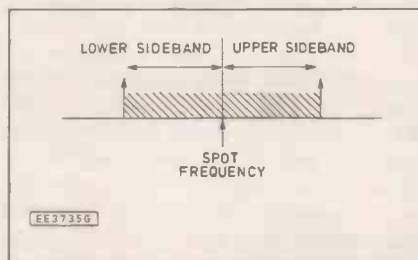


Fig. 4. Sidebands generated around the spot frequency.

When carrying information there will be a spread of frequencies on each side of the nominal or "spot" frequency called sideband (see Fig. 4). It is essential to leave enough space so that there is no overlap of the sidebands of adjacent channels. Again, this is a large topic and has only been touched on here.

Infra-red waves and visible light have an important place in modern communications systems. This is because they may be passed along optical fibres and carry digital telephone and other information. They may be used in free space but only over short distances such as in a television remote control handset. Readers who have not been following this series should note that Part 8 (June, 1992 issue) gave certain information about optical communications systems.

### COMMUNICATION SATELLITES

If you could throw a ball fast enough in a horizontal direction it would become a satellite – that is, it would go into orbit

around earth. This is because as it was falling to the ground, the ground would be falling away from it at the same rate due to the curvature of the earth. All the time gravity would be pulling the ball towards the centre of the earth so it would simply go round in a circular orbit. Remember "down" means towards the centre of the earth.

There would be several problems here. Firstly, the speed with which the ball would need to be thrown would be far too great for any normal apparatus to achieve (about 8km – or 5 miles – per second). Secondly, there would be things in the way such as tall buildings, mountains, etc. Also, friction with the air would burn it up in a very short time.

A gun can fire a shell over the horizon but it eventually strikes the ground. Isaac Newton suggested that if a sufficiently powerful cannon could be built, it could be used to launch a satellite (see Fig. 5). In practice, a rocket is used. The orbit is made

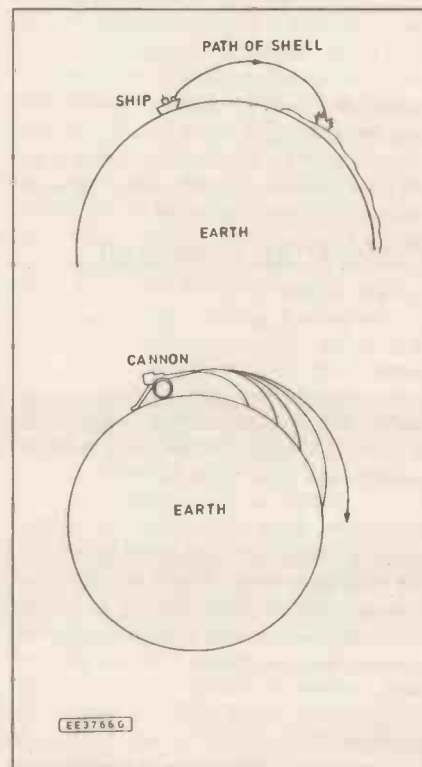



Fig. 5. Newton suggested that a powerful cannon could launch a satellite.

very high to leave most of the air behind and avoid the problems with atmospheric friction mentioned earlier. It should be said that the earth's atmosphere, although much reduced, still exists even at these great heights and all satellites gradually spiral towards the earth and burn up as they enter the denser atmosphere. The first artificial satellite was the Soviet 83kg Sputnik 1 launched on 4th October, 1957. This is believed to have stayed in orbit for almost 10 years.
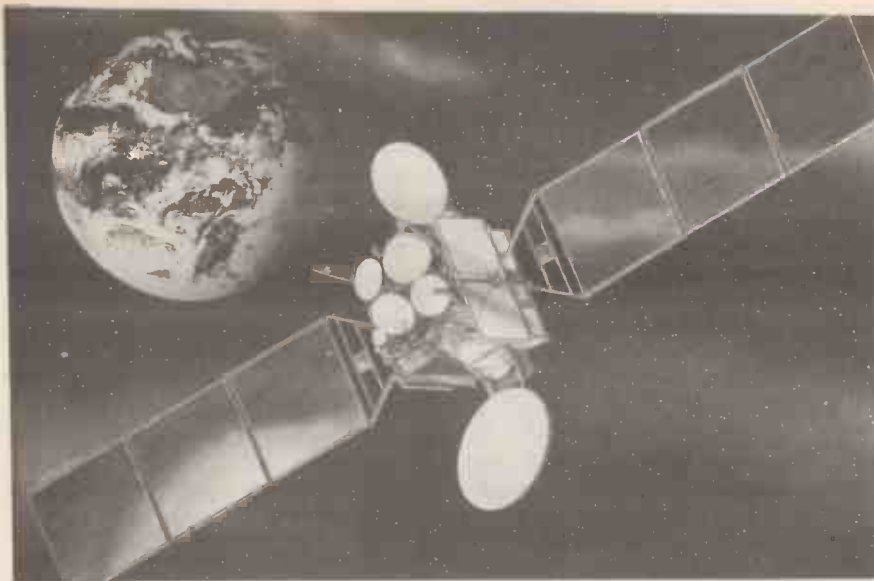
### ACTIVE SATELLITE SYSTEMS

It had been known for many years that satellites would be useful for communication purposes – long before the technical means of launching them was estab-





Artists impression of Intelsat 7 communications satellite.

lished. By using a satellite, microwaves can be sent up from a ground station whereupon the satellite can send them back to another ground station in some distant part of the world. Microwaves have a frequency too high to be reflected by the ionosphere so they pass through to the satellite.

The earliest satellites were passive – they simply reflected the waves down to earth again and much of the energy spread out and was lost before it reached the ground station. This made communications rather unreliable. Modern satellites are *active* – that is, they receive the waves from the earth station, amplify the signal and re-transmit the information using a different frequency. Obviously, for this they need a power supply to operate the on-board electronic circuits which receive, process and re-transmit the signal. Moreover, these circuits need to work reliably for many years. The usual power supply consists of *silicon solar cells* which provide enough energy to operate the equipment and charge batteries while the satellite is in sunlight. Power is then drawn from the batteries when the satellite is on the dark side of the earth.

At the working height of the satellite, the sun's rays are very powerful since they have not been reduced by the earth's atmosphere. A relatively small number of solar cells is therefore sufficient. Early satellites used *analogue* techniques but today they work *digitally* – some relevant information was given in Part 8 of this series (June, 1992 issue). A digital signal – perhaps derived from the voice or music – can undergo more than one trip to a satellite – perhaps combined with transmission along copper wires and optical fibres – and hence reach any part of the world without loss of quality.

## CATCHING THE WORM

The first satellites were placed in a low orbit where their period of rotation was

about 90 minutes. This meant that the aerial on the earth station had to "track" the satellite as it rose and set in the sky. This had to be done with great precision and was not always successful. The maximum continuous communication time was therefore 45 minutes followed by a delay of 45 minutes until the satellite appeared once again. In practice the communication channel was opened for a shorter time than this.

At such a low orbit, satellites soon spiralled back to the earth due to the considerable friction with the air. Today, satellites can be put into *geostationary* (synchronous) orbit.

Launching a synchronous satellite involves placing it at a height of 36,000km above the earth's surface and giving it sufficient horizontal velocity. At this height, the satellite orbits the earth in 24 hours – the same time as it takes the earth to spin once on its axis. Thus, to an observer on the Earth, the satellite appears stationary. This technique has two advantages. Firstly, it means that the base station can point its aerial in a fixed direction (in fact, the satellite drifts in position to some extent but this is less of a problem). Secondly, communication can be guaranteed 24 hours a day.

The first commercial geostationary communications satellite was *Early Bird* launched on 6th April, 1965. Today, everyone is familiar with satellite dishes on private houses which enable commercial TV broadcasts to be received. It is even possible to set up temporary base stations so that television and radio reporters can send back news items via a satellite link instantly.

It is necessary to use waves having a frequency of more than 30MHz for satellite communications since, otherwise, they would not penetrate the ionosphere and would be reflected back to earth instead. In practice, much higher frequencies – greater than 1GHz are used.

Communication satellites generally use microwave frequencies above 4GHz. Waves over about 100GHz are absorbed by the atmosphere and are therefore unsuitable.

## MAXIMUM USE

The cost of launching a satellite is considerable. It is necessary, therefore, that those who have provided the money get value from their investment. If a satellite could only send one piece of information at a time the cost of using it would need to be very high. However, if many pieces of information can be sent simultaneously, each may be carried cheaply. The system may then be of benefit to more people and still be commercially viable.

Imagine we wish to send telephone messages by satellite. The digital data from the national telephone network would arrive at the ground station. In one form of operation, a fixed-frequency carrier wave is used to send signals to the satellite using a parabolic dish reflector. The carrier wave is switched on (to represent a 1) and off (for a 0), according to the data being transmitted.

Instead of a continuous stream of information, the system pauses then sends a lot of data in a 2ms burst (1 millisecond = 1/1000 second). The next burst would be from another conversation and the next from yet another one and so on. Eventually it is time for a burst from the first one again. To guard against the bursts possibly overlapping there is a space of 1μs (one millionth of a second) between them. In this way, several conversations may be interleaved with one another. This technique is called Time Division Multiple Access (TDMA).

TDMA can be combined with another technique called CME (channel multiplication). This relies on the fact that most of a given telephone conversation is actually silence. Not only is there silence while the reply is received, but there are natural gaps between words, hesitations, etc. These gaps can be made use of by filling them with data from other calls. A computer constantly checks the most efficient way of filling the spaces. It all happens so rapidly that no user is aware that he or she is sharing the equipment with other people.

It is relatively difficult keeping track of which piece of information is which and re-assemble it in the correct order but where time is money, it is certainly worthwhile. Once the information has been re-assembled, each user will think that he or she has sole use of the equipment – rather like the flat in a time-share holiday.

## DELAY

One problem with sending information to and from a geostationary satellite is *propagation delay*. With the satellite at a height of some 36,000km, the waves will need to travel more than twice this distance to make a complete round trip. Since radio waves travel at the speed of light – i.e. 300 million metres (300,000km) per second – the round trip

by satellite will take 0.25 seconds approximately. This may not sound much but where more than one satellite is involved the signal may take anywhere up to one second to reach its destination. Any reply will then take the same time to be received. This could involve two seconds between questions and answers. This is noticeable in conversations but is a nuisance rather than a great disadvantage.

Satellites are now used for many purposes such as for surveillance and scientific research. These gather information using on-board cameras, digitize it and relay it to an earth station where the data is processed. Surveillance "spy in the sky" satellites photograph the ground in considerable detail. Where weather conditions obstruct the view, *infra-red* cameras may be used to penetrate the haze. It would be possible to note any military build-up which could signal that a country was preparing for war.

Satellites have other uses too. They can survey the ground and provide information for crop growing, mining, archaeology and other activities. Military communication in the field can be carried out using back-pack satellite equipment. Weather satellites collect data and allow for much more accurate weather forecasting than was possible only a few years ago.

Satellite-based scientific equipment can gather data from distant parts of the universe and help scientists piece together some of its mysteries. Navigation satellites emit radio signals which can be received by ships and aircraft to enable them to pinpoint their position very accurately. Even on the ground, navigation satellites can be used to find the exact position to begin construction work. Moreover, this is now done with relatively small and inexpensive equipment.

## SOCIAL AND ECONOMIC CONSIDERATIONS

We discussed in Part 8 of this series (June, 1992) the common features of an information transmission system. Whatever channel of communication is used, a modern system is so sophisticated

that the user is unaware of the means by which the information is carried. For example, we would be unaware if optical fibres were used or whether satellites were involved.

Speedy and efficient communication seems to make the world a smaller place. It has certainly spread understanding and tolerance between nations. It has made us more aware of the plight of others in distant countries – we see the effects of famine, war and disease on our TV screens almost as it happens. We see injustice and put pressure where required to do something about it. On a smaller scale, distant families can keep in touch relatively cheaply. With international trunk dialling, we can reach anyone with a telephone almost anywhere in the world – instantly.

Modern communications are changing our patterns of work. For example, people now find it much easier to work from home. Using a computer and telephone line with which to send information back and forth to the main computer, a printer, word-processing package, desk-top publishing, spreadsheet and, perhaps, computer-aided design (CAD) software and a fax machine it is quite easy to make a corner of a room in the house into a fully-operational office. All this equipment is now relatively inexpensive.

## MOBILE BUSINESS

It is not unknown for people to run businesses from a car or van using a portable cellular telephone. One person can attend to all the duties which were once carried out by a whole team – typist, filing clerk, office junior etc. This, of course, could increase unemployment. On the other hand these activities should – in theory at least – reduce the number of cars travelling to and from the traditional place of employment in the city so reducing pollution, conserving energy, wasting less time travelling and reducing traffic congestion.

It allows freedom for a person to choose where to live rather than being under the constraint of the company for which he or she works. It is even possible to work from a foreign country and,

perhaps, enjoy the better climate there. It could also mean that people in the future will need leisure training to help in using the extra hours of freedom which our grandparents did not enjoy.

## DIGITAL MONEY

Efficient communication of digital data means that money can be transferred almost instantly to most parts of the world. This has revolutionized banking. On a small scale, bank and building society cash dispensers are now commonplace in every town. We can even do our banking from home. By using a secret number (PIN) we can access our bank account over the telephone and check our balance, pay bills and transfer funds to other accounts instantly.

Building societies have been particularly quick to see the benefits which this new technology brings. One implication is that it is becoming less common for large sums of cash to be carried around. People are often paid electronically by transferring funds direct to their bank account. On the other hand *computer crime* is on the increase. Those with sufficient knowledge and skill, including that needed to extract secret code-words, can access accounts and withdraw funds fraudulently. The proliferation of plastic credit cards has also brought its own form of crime.

Efficient communications has made our lives less private. Without careful control and data protection laws we could have all manner of personal information banded about from one computer database to another. Even so, certain information may be legally passed on to third parties who can, in turn, send junk mail or inconvenience us with telephone calls about their products or services.

Using a personal computer, a modem and a telephone line, a *hacker* can break into computers and extract sensitive or personal information, change data or use it for illegal purposes. Note that such *hacking* is illegal and those found guilty face heavy penalties.

That's all for this month. Next time we will be chiefly concerned with problem solving and the effect of feedback in a control system.

*A modern computer the RM Nimbus PC-186 as used in many schools.*



*A Canon FAX-260E fax machine.*



# BARGAINS - 10 New Ones This Month

**SUPER MULTIMETER** Ex British Telecom, this is a 19-range 20k o.p.v. top grade instrument, covers AC & DC voltages, current and resistance, very good condition, fully working and complete with leads £9.50, leather carrying case £2 extra (batteries not included but readily available).

**MULTI-CORE CABLES** all with 8A 230V cores so suitable for disco and other special lighting effects. With earthable woven screen and thick pvc outer. 3 core, 30p per metre, 16 core, 50p per metre, 18 core, 80p per metre, 25 core, £1 metre and 36 core, £1.50 per metre.

**VARIAC** an infinitely variable unit gives any voltage from 0-230 a.c. at 1/2A. Obviously an invaluable piece of equipment which should be in every workshop and probably would be except that the usual price for this is £35 plus VAT. Now is your chance to buy one, brand new, at £15 including VAT, Order Ref. 15P42B.

**ULTRA THIN DRILLS** Actually 0.3mm. To buy these regular costs a fortune. However, these are packed in half dozens and the price to you is £1 per pack, Order Ref. 797B.

**YOU CAN STAND ON IT!** Made to house GPO telephone equipment, this box is extremely tough and would be ideal for keeping your small tools. Internal size approx. 10 1/2" x 4 1/2" x 6" high. These are complete with snap closure lip and shoulder-length carrying strap. Taken from used equipment but in good condition, price £2, Order Ref. 2P283B.

**BUILD YOUR OWN NIGHT LIGHT**, battery charger or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket. We have two cases, one 3 1/2" x 2 1/4" x 1 3/4" deep, £1 each, Order Ref. 845. The other one is 2 1/2" x 2 1/4" x 1 3/4" deep, 2 for £1, Order Ref. 565.

**SAFETY LEADS** curly coil so they contract but don't hang down. Could easily save a child from being scalded. 2 core, 5A, extends to 3m, £1, Order Ref. 846, 3 core, 13A, extends to 1m, £1 each, Order Ref. 847, 3 core, 13A, extends to 3m, £2 each, Order Ref. 2P290.

**POWER SUPPLY WITH EXTRAS** mains input is fused and filtered and the 12V dc output is voltage regulated. Intended for high class equipment, this is mounted on a PCB and, also mounted on the board but easily removed, are 2 12V relays and a Piezo sander. £3, Order Ref. 3P80B.

**5V 2.5A POWER SUPPLY UNIT** £5, Order Ref. 5P186.

**ULTRA SONIC TRANSDUCERS** 2 metal cased units, one transmits, one receives. Built to operate around 40kHz. Price £1.50 the pair, Order Ref. 1.5P14.

**100W MAINS TRANSFORMERS** normal primaries 20-0-20 at 2.5A, or 30V at 3.5A, £4, Order Ref. 4P24. 40V at 2.5A, £4, Order Ref. 4P59. 50V at 2A, £4, Order Ref. 4P60.

**PHILIPS 9" HIGH RESOLUTION MONITOR** black & white in metal frame for easy mounting, brand new still in maker's packing, offered at less than price of tube alone, only £15, Order Ref. 15P1.

**16 CHARACTER 2-LINE DISPLAY** screen size 85mm x 36mm, Alpha-numeric LCD dot matrix module with integral micro processor made by Epson, their Ref. 16027AR, £8, Order Ref. 8P48.

**INSULATION TESTER WITH MULTIMETER** internally generates voltages which enable you to read insulation directly in megohms. The multimeter has four ranges. AC/DC volts, 3 ranges DC millamps, 3 ranges resistance and 5 amp range. These instruments are ex British Telecom but in very good condition, tested and guaranteed OK, probably cost at least £50 each, yours for only £7.50, with leads, carrying case £2 extra, Order Ref. 7.5P/4.

**BRUSHLESS DC 12V FAN** tiny, only 60mm square, good air mover but causes no interference, £8, Order Ref. 8P26.

**MAINS 230V FAN** best make "PAPST" 4 1/2" square, metal blades, £8, Order Ref. 8P8.

**2MW LASER** Helium neon by Philips, full spec. £30, Order Ref. 30P1. Power supply for this in kit form with case is £15, Order Ref. 15P16, or in larger case to house tube as well £18, Order Ref. 18P2. The larger unit, made up, tested and ready to use, complete with laser tube £69, Order Ref. 69P1.

**1/3 HP 12V MOTOR - THE FAMOUS SINCLAIR C5** brand new, £15, Order Ref. 15P8.

**SOLAR CHARGER** holds 4 AA nicads and recharges these in 8 hours, in very neat plastic case, £6, Order Ref. 6P3.

**FERRITE AERIAL ROD** 8" Long x 3/8" diameter, made by Mullard. Complete with 2 coil formers. 2 for £1, Order Ref. 832B.

**AIR SPACED TRIMMER CAPS** 2-20 pf ideal for precision tuning UHF circuits, 4 for £1, Order Ref. 818B.

**FIELD TELEPHONES** just right for building sites, rallies, horse shows, etc., just join two by twin wire and you have two way calling and talking and you can join into regular phone lines if you want to. Ex British Telecom in very good condition, powered by batteries (not included) complete with shoulder slung carrying case, £9.50, Order Ref. 9.5P/2.

**MAINS ISOLATION TRANSFORMER** stops you getting "to earth" shocks. 230V in and 230V out. 150watt upright mounting, £7.50, Order Ref. 7.5P/5 and a 250W version is £10, Order Ref. 10P79.

**LIMITED SUPPLY ITEMS** are only described in our newsletter. Over 50 appear in our current issue. If you order something this month you will receive this and the next three issues posted to you free of charge.

**THIS MONTH'S SNIP**  
A £60 UNIT FOR LESS THAN  
£10 - switch mode power supply with outputs +12V at 4A, +5V at 16A and -12V at 1/2A. Enclosed in plated steel case, brand new, offered at a special price of £9.50 until July 31st, Order Ref. 9.5P1.

**MINI MONO AMP** on PCB. Size 4" x 2" with front panel holding volume control and with spare hole for switch or tone control. Output is 4 watt into 4 ohm speaker using 12V or 1 watt into 8 ohm using 9V. Brand new and perfect, only £1 each, Order Ref. 495.

**5RPM MAINS DRIVEN** This is a shaded pole motor, £5, Order Ref. 5P54.

**POWER SUPPLY UNIT** mains in, dc out, cased, 4.5V 100mA, £1, Order Ref. 104, 6V 200mA £1, Order Ref. 103, 6V 700mA, £1, Order Ref. 103A, 9V 500mA, £2, Order Ref. 2P134, 24V 200mA, £2, Order Ref. 2P4, 12V 2A, £6, Order Ref. 6P23.

**AMSTRAD POWER UNIT** 13.5V at 1.9A encased and with leads and output plug, normal mains input £6, Order Ref. 6P23.

**AMSTRAD 3.5 FLOPPY DRIVE** brand new and cased, £35, Order Ref. 35P4.

**ATARI 65XE** at 65K this is quite powerful, so suitable for home or business, unused and in perfect order but less PSU, only £19.50, Order Ref. 19.5P/5B.

**80W MAINS TRANSFORMER** two available, good quality, both with normal primaries and upright mounting, one is 20V 4A, Order Ref. 3P106 the other 40V 2A, Order Ref. 3P107, only £3 each.

**PROJECT BOX** size approx 8" x 4" x 4 1/4" metal, sprayed grey, louvred ends for ventilation otherwise undrilled. Made for GPO so best quality, only £3 each, Order Ref. 3P74.

**12V SOLENOID** has good 1/2" pull or could push if modified, size approx 1 1/2" long x 1" square, £1, Order Ref. 232.

**WATER VALVE 230V** operated with hose connections, ideal for auto plant spray or would control air or gas into tanks etc., £1 each, Order Ref. 370.

**10W ISOLATION TRANSFORMER** if you want to isolate some small piece of equipment from earth this may be what you are looking for. You can use it either with a tapped input or a tapped output. It's upright mounting and well insulated. Price £1, Order Ref. 821.

**BT POWER SUPPLY UNIT** output 9.5V AC at 600mA, in black plastic case with 13A plugs to go straight into socket and approximately 3 metres of twin output lead. Price £1.50, Order Ref. 1.5P7.

**BUILDING YOUR OWN PSU**, battery charger, night light, or any other gadget that you want to enclose in a plastic case and be able to plug into a 13A socket? We have two cases, one 3 1/2" x 2 1/4" x 1 3/4" deep, £1 each, Order Ref. 845. The other one is 2 1/2" x 2 1/4" x 1 3/4" deep, 2 for £1, Order Ref. 565.

**500V BRIDGE MEGGER** developed for GPO technicians the Ohmter 18B is the modern equivalent of the bridge megger. 9V battery operated, it incorporates a 500V generator for insulation testing and a null balance bridge for very accurate resistance measurement. Ex B.T. in quite good condition with data & tested. Yours for a fraction of original cost, £45, Order Ref. 45P2.

**EXPERIMENTING WITH VALVES** don't spend a fortune on a mains transformer, we can supply one with standard mains input and secs. of 250-0-250V at 75mA and 6.3V at 3A. £5, Order Ref. 5P167.

**15W 8 OHM 8" SPEAKER & 3" TWEETER** made for a discontinued high quality music centre, gives real hi-fi, and only £4 per pair, Order Ref. 4P57.

**FREE POWER!** Can be yours if you use our solar cells - sturdily made modules with new system bubble magnifiers to concentrate the light and so eliminate the need for actual sunshine - they work just as well in bright light. Voltage output is .45 - you join in series to get desired voltage - and in parallel for more amps.

Module A gives 100mA Price £1 Order Ref. BD631  
Module B gives 400mA Price £2 Order Ref. 2P199  
Module D gives 700mA Price £3 Order Ref. 3P42  
Module E gives 1A Price £3.50 Order Ref. 3.5P4

**3V SOLAR PANEL** price £3, Order Ref. 3P99B.

**3 GANG .0005 MFD TUNING CONDENSER** with slow motion drive. Beautifully made by Jackson Brothers and current list price is probably around £20. Yours for £5, Order Ref. 5P189.

**STEREO HEADPHONES** extra lightweight with plug, £2 each, Order Ref. 2P261.

**BT TELEPHONE LEAD** 3m long and with B.T. flat plug ideal to make extension for phone, fax, etc. 2 for £1, Order Ref. 552.

**WATER PUMP** very powerful with twin outlets, an ideal shower controller, mains operated, £10, Order Ref. 10P74.

**STUDIO 100** by Amstrad, the ultimate disco control panel, has four separately controlled and metered channels, twin cassettes, AM/FM radio, stereo audio amplifier, phono & CD inputs, etc., regular price over £400, we have a few still in maker's packing, brand new and guaranteed, yours for £99, Order Ref. 99P1.

**0-1MA FULL VISION PANEL METER** 2 1/2" square, scaled 0-100 but scale easily removed for re-writing, £1 each, Order Ref. 756.

**VU METER** illuminate this from behind becomes on/off indicator as well, 1 1/2" square, 75p each, Order Ref. 366.

**EDGE-WISE PANEL METER** ideal when short of panel space only 40 x 14mm, also have built-in led, 500µA f.s.d, scaled 0-5, £1 each, Order Ref. 131.

**PCB DRILLS** 12 assorted sizes between .75 and 1.5mm, £1 the lot, Order Ref. 128.

Prices include V.A.T. Send cheque/postal order or ring and quote credit card number. Add £3 post and packing. Orders over £25 post free.

**M & B ELECTRICAL SUPPLIES LTD**  
12 Boundary Road, Hove, Sussex BN3 4EH  
Telephone (0273) 430380  
Fax or phone (0273) 410142




**DIGITAL FREQUENCY METER.** This is a hand-held instrument with an LCD display allowing 8 digits of frequency to be read, has internal nicad batteries, and a power supply which will recharge the batteries. Ideal for field and service work as well as general and industrial applications. Has high and low BNC inputs and a plug-in antenna which enables remote tests. It covers a very wide range of frequencies: switch position 'A' covers 10Hz to 20MHz and switch position 'B' covers 20MHz to 1200MHz. Price £99, but it compares very favourably with instruments selling at over £500 by our competitors. Order Ref. 99P2.

# SUB-WOOFER

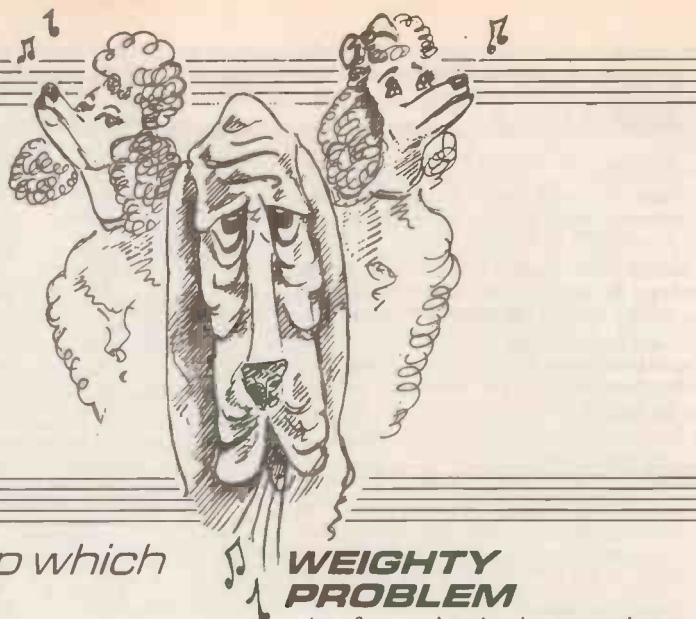**PAUL HENDERSON**

*An add-on for your hifi setup which should provide a dramatic improvement in bass.*



## WEIGHTY PROBLEM

An often used and quite apt analogy to a loudspeaker is a weight suspended on a spring. If the weight is pulled downward it will oscillate at some low frequency dependent upon the stiffness of the spring and the size of the weight. In a loudspeaker the weight is the mass of the cone and the spring is the 'speaker surround'. Both systems operate like a mechanical tuned circuit.

In free air the resonant frequency of a loudspeaker is often quite low. Some units even manage a free air resonance at 20Hz or thereabouts. Unfortunately it is not possible to operate a loudspeaker without a cabinet, at least if you want to hear any bass at all.

This is because of the nature of sound itself. Sound is a pressure wave that travels through air at a velocity of about 343m/sec. The easiest way to visualise this is to use another analogy.

If you tie a rope to a door handle and jerk it rapidly while holding it loosely you will see a wave travel along the rope. Note that the rope doesn't move itself very far but the wave can travel along at a fair rate.

If you take a loudspeaker and feed a bass signal into it you will not hear much. As the cone moves to and fro a bass sound wave is generated both from the front and the rear of the cone. As the dimensions of

IT'S A SAD fact that 90 per cent of existing speaker systems are incapable of delivering good solid bass. A recent look through a hi fi magazine's "Loudspeaker Reviews" showed only two models out of fifty tested had a -3db point below 60Hz. This state of affairs would not be tolerated in any other piece of audio equipment where a bare minimum response is required down to 20Hz, -3db.

Some audiophiles would point out that some organ music contains full power output at 16Hz. This is not all, in addition there are mysterious bass transients, even speech contains explosive sounds which are actually at sub audio frequencies.

## SACRED COW

The reasons for the shortcoming in the bass region are not hard to find. Speaker systems are designed as basically mechanical devices which follow well known physical laws. The available materials dictate that domestically acceptable speakers must either be large or be subject to some form of equalisation to operate at low frequencies.

Unfortunately, the audio industry is

fragmented. There are loudspeaker manufacturers and amplifier manufacturers. The latter have to design their equipment for a flat frequency response. The former are confined by this fact. It is quite possible to build a speaker system with an extended low frequency response but this requires that the hi fi's most sacred cow, flat frequency response from amplifiers has to be sacrificed.

While the audio punters are satisfied with the existing state of affairs nothing is likely to change. However, the recent introduction of CD with it's vastly better low frequency response than either tape or disc is beginning to force a change. In the meantime what can be done to improve matters?

One solution is to use a separate speaker system to deliver the extra bass. Such a system can be designed without regard to mid-range reproduction and can thus be optimised for it's task. This doesn't need to cost an arm and a leg either, all that is required is good design. Before getting deeply embroiled in the nuts and bolts of this project it will be as well to consider some of the basic theory behind it.

Fig. 1. The system response curves.

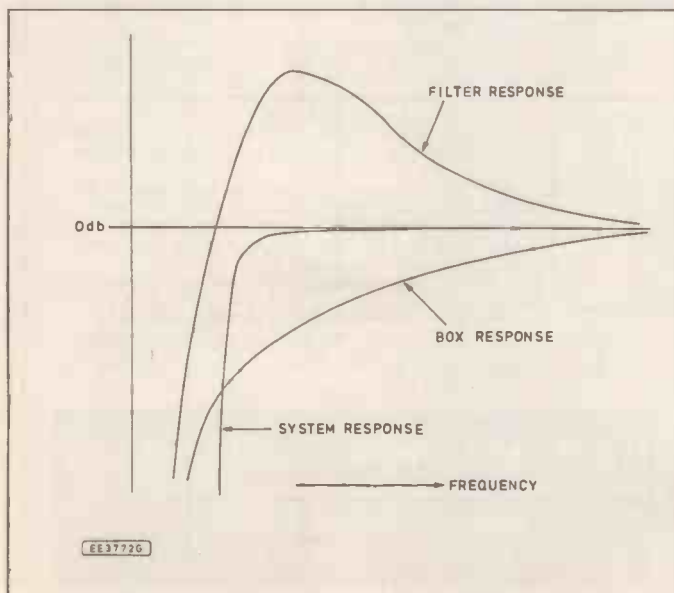


Table 1:

Bass Response of Enclosure, before top cut applied

Frequency Hz	Response db	Max Spl db	Max Power watts(W)
20	-14.49	87.65	3
30	-1.71	100.43	15.6
40	-2.04	102.14	30
50	-1.51	102.14	30
60	-0.93	102.14	30
70	-0.52	102.14	30
80	-0.27	102.14	30
90	-0.12	102.14	30
100	-0.04	102.14	30
110	0.01	102.14	30
120	0.03	102.14	30
130	0.06	102.14	30
140	0.06	102.14	30
150	0.06	102.14	30
160	0.06	102.14	30
170	0.06	102.14	30
180	0.06	102.14	30
190	0.06	102.14	30
200	0.05	102.14	30

Computer predicted response for optimum system.



the speaker are small compared to the wavelength of the sound generated the front radiation cancels that from the rear. The result, no bass!

The solution is to mount the loudspeaker in a cabinet. If this is totally enclosed the back radiation is effectively contained. However, a price has to be paid for this.

Going back to our weight on a spring analogy the enclosed air effectively stiffens the spring raising the resonant frequency. This is important because the response of a speaker below the resonant frequency rolls off rapidly. Either one must enlarge the enclosure to unreasonable dimensions or find another way of obtaining bass.

## GOOD REFLEXES

The Reflex Enclosure is one very useful solution. A duct is fitted into the cabinet and acts as a tuned acoustic circuit. Here the mass is the mass of air in the enclosure and the spring is the compliance of the air in the enclosure.

One advantage of this is that the rear cone radiation is used to excite the resonance and is thus not wasted. Properly done the response of such an enclosure extends downwards into the deep bass range.

Until recently the correct design of such cabinets was a matter of hit and miss. However, since the work of Theille and Small on 'speaker system behaviour it is now possible to design speaker enclosures with a computer program from the comfort of one's chair.

This Sub-Woofer project described here has been designed with the help of one of these programs. The computer predicted bass response, before "top cut" being applied, is given in Table 1 and the system response curves shown in Fig. 1. In practise a suitable design was evolved, built measured and then optimised.

The so called "sixth" order speaker system has been adopted, which uses electronic equalisation in conjunction with a "Reflex Enclosure" to obtain a low cut-off frequency. The design is -3db down at 30Hz, a full octave lower than most existing speaker enclosure systems. At the top end the response is rolled off with an internal filter to suit the speakers in use.

In a conventional 'speaker system a single driver (loudspeaker) is employed to cover the bass range. Here two identical 200mm diameter 'speakers are used back-to-back in a push-pull arrangement. Using this technique the necessary cabinet size is halved while even harmonic distortion from the drivers is cancelled.

## CIRCUIT DESCRIPTION

Regular readers will no doubt have noticed that I have a liking for the TLO series of j.f.e.t. input op. amp i.c.s. I make no apologies for this.

It is hard to find any devices with the same mix of good audio properties. High input impedance, low distortion, high slew rate, and which are still relatively cheap.

The "equalising" circuit for the Sub-Woofer is designed around two of these i.c.s (TLO72's) and is shown in Fig. 2. Input signals are taken from the right and left speaker outputs of your stereo-amplifier, or alternatively directly from the speaker terminals. As the signals from these points in the circuit are of very low impedance this ensures no deleterious effects on the stereo image.

The audio input signals are passively mixed by feeding them through resistor R1 and R2 to the volume control VR1. At frequencies below 100Hz there is no separation in phase between channels.

Some audio "experts" have argued that phase must be maintained to ultra low frequencies. However, I have yet to come across either a record or CD which shows any difference either in level or phase below 100Hz. Even if such information were presented to the ear it is doubtful whether we would be able to locate relative direction within a stereo sound field due to the long wavelengths involved.

## SELECTIVE FEEDBACK

The mixed signal from the slider of VR1, the Volume Control, is fed into the bass boost filter IC1a, one half of a TLO72 op.amp. As mentioned earlier the system requires bass boosting to operate correctly and this is provided by a second

# COMPONENTS

### Resistors

- R1, R2 470 (2 off)
- R3 12k
- R4 560
- R5 330k
- R6, R7, R8 15k (3 off)
- R9, R13, R14 1k (3 off)
- R10 36k
- R11 100
- R12 4k7

All 0.25W 5% carbon film.

### Potentiometers

- VR1 47 rotary carbon
- VR2 22k dual-gang rotary carbon

### Capacitors

- C1, C2, C3, C4 100n polyester, 100V (4 off)
- C5, C8, C9 100µ radial elect., 25V (3 off)
- C6, C7 4700 radial elect., 25V (2 off)

### Semiconductors

- D1, D2 1N4007 1A 1000V rec. diode (2 off)
- TR1 2N1711 npn medium power transistor
- TR2, TR4 2N3442 npn 10A power transistor (2 off)
- TR3 2N2905 pnp high speed medium power transistor
- IC1, IC2 TLO72 dual low-noise op.amp (2 off)
- REC1 W005 1.5A 50V bridge rectifier

### Miscellaneous


- LS1, LS2 Matched pair loudspeakers 200mm 8Ω (see Shoptalk)
- T1 Mains transformer, 48VA 12V-0V-12V secondary winding

Stripboard, 0.1in. matrix size 16 strips x 34 holes; cabinet, see "cutting list"; 4mm input socket (3 off); TO3 transistor mounting kit (2 off); plastic tube vent, 51mm internal diameter and 232mm long (drainpipe); heatsink 25cm length of 2.5cm "U" section aluminium; control knob (2 off); recess component mounting dish; chipboard screws; 6BA screws and nuts; speaker lead; connecting wire; solder etc.

Approx cost guidance only

**£62**

Fig. 2. Equalising circuit diagram used in the Sub-Woofer.

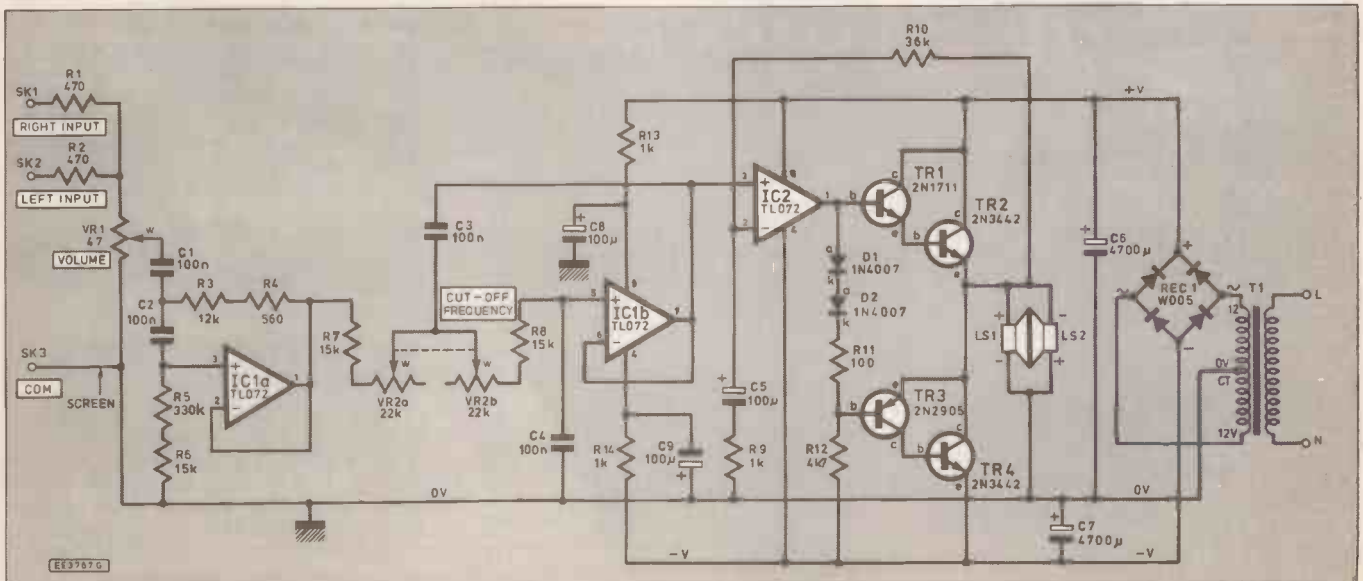



order filter. What this means is that unlike a simple RC filter which provides an ultimate attenuation of 6db/octave we require 12db/octave. This is accomplished by using an op.amp circuit with frequency selective feedback.

Resistors R3, R4, R5, R6 and capacitors C1, C2 are used to produce a standard Sallen and Key second order filter with the correct characteristics. R3 and R4 provide positive feedback to the junction of capacitors C1 and C2 simulating an inductance which is tuned by C2 and damped by R5 plus R6. By varying the ratio of these passive components a whole range of filters can be produced. Unfortunately design details are beyond the scope of this present article.

From the output of this filter, pin 1, the signal is fed, via resistor R7, into a second Sallen and Key filter. This is built around IC1b, the other half of the op.amp.

To maximise the circuit usage, we need to "roll-off" the top response to suit the particular speaker system we are using. Filter IC1b sets the upper bass roll-off to suit the characteristics of the existing speaker system. As such the cut-off frequency has to be variable and this is achieved by the dual control VR2. With the component values shown the filter operates between 50Hz-100Hz.

The output from the woofer system will now resemble a bandpass filter response accurately tailored to suit the existing speaker system. Finally to finish the description of the filter stage, resistors/capacitors R13/C8 and R14/C9 decouple the supply lines to provide power for IC1.

## INTERNAL AMPLIFIER

The internal amplifier is quite conventional. Based on the "brains/brawn" configuration, the op.amp supplies the brains whilst the brawn is taken care of by a pair of 2N3442 power output transistors. IC2 is the other op.amp which provides all the required open loop voltage gain. It drives the output stage comprising transistors TR1, TR2 and TR3, TR4.

To prevent crossover distortion from rearing it's ugly head a small bias must be provided between the bases of TR1 and TR3. Crossover distortion is produced by the fact that in a conventional power amplifier, such as this, the output stage is operated with very little quiescent current.

Positive going signals are handled by TR1/TR2 and negative going signals by

TR3/TR4. If the current is reduced sufficiently lots of distortion can be generated as one pair of transistors switches off and the other switches on. This problem can be easily avoided by applying a little current through the output stage under no signal conditions.

The required small bias voltage is produced by the voltage drop across diodes D1/D2 and resistor R11. The circuit is completed to the -V line by resistor R12.

Transistors TR1 and TR2 are configured as a Darlington pair. Connected in this fashion the two devices act as a "single" high gain npn transistor.

Transistors TR3 and TR4 are used in a complementary feedback configuration. Again, connected in this way they appear as a single high gain pnp transistor.

Overall negative feedback is applied via resistors R10 and R9. Closed loop gain being determined by the ratio between these two resistors. Capacitor C5 is included in the loop to reduce the gain at d.c. to unity, thus allowing direct connection of the speakers to the output stage.

## POWER SUPPLY

Turning now to the power supply stage of the circuit diagram Fig. 2. This is very conventional. Mains voltage is stepped down by the mains transformer, T1.

The resulting a.c. voltage is full-wave rectified by the bridge rectifier, REC 1. The raw d.c. is then smoothed by capacitors C6 and C7. Lastly, the 0V line is provided by the transformer centre tap.

## BUILDING THE ENCLOSURE

Construction can be broken into two parts, the 'speaker enclosure and the electronics. Probably it's better to build the cabinet first.

The first essential in building successful 'speaker cabinets is to go to a reliable wood merchant to get the panels accurately cut. However, a few notes on this aspect of the design wouldn't go amiss. Firstly the volume of the box is 0.8 cu. ft. As long as this volume is adhered to the box can have any appropriate dimensions.

The details and dimensions of our prototype design is shown in Fig. 3 and the project can be built to these instructions. As you can see from the Cutting List, a piece of 15mm thick shelving board is used. This is entirely adequate for this application and has the advantage that it can be purchased in a variety of finishes.

The cabinet is glued and screwed to-

gether. Use 38mm (1 1/2in.) No. 8 counter-sunk chipboard screws for this job. Leave the front panel separate and fix the sides and rear panels together initially.

Having half assembled the cabinet it's as well to seal along the joins with Polyfiller or similar. Mix up some filler into a fairly stiff paste and work it in with your finger along the panel seams. Any excess can be wiped away with a damp cloth.

Once completed the front baffle can be marked out and cut as shown in Fig. 3. Also cut out the apertures for the vent and recess speaker terminal socket dish. Make a small hole near the speaker aperture to take the speaker interwiring.

## SPEAKER UNITS

In a project such as this it is necessary to ensure that the 'speaker units acquired for use will be suitable. For this reason, arrangements have been made with the designer to supply matched speaker units of the correct specification - see *Shoptalk*. If you have the facilities to test speakers yourself you can select a suitable pair. However, you may need to purchase several to get a good match.

The loudspeakers used in this project are 200mm diameter pulp coned types, with a roll surround. They have been selected because of their large linear cone excursion and specific characteristics.

Technically there are three parameters of importance. They are: the free air resonant frequency,  $Q_{ts}$  and  $V_{as}$ . Where  $Q_{ts}$  is the "Q" of the fundamental resonance whilst  $V_{as}$  is the volume of air whose compliance, the opposite of stiffness, is equal to that of the speaker surround.

To design a speaker system correctly it's imperative that these parameters are matched between the two loudspeakers used in the enclosure and that of the design values specified. One of the attractions of the speaker unit used is that these parameters are within a few percent of the nominal values. Nevertheless matching speakers together in pairs ensures that the design functions as intended.

A complicating factor is that the speaker parameters, measured straight out of the box are misleading. After a period of use the resonant frequency lowers as the cone suspension loosens.

Fortunately, the solution to this problem is quite simple. The speakers are taken from the box and put onto a rig which feeds large signals at low frequencies into them. After a few hours the suspension compliance reaches it's final value. The measured parameters are then stable for the life of the loudspeaker.

The nominal resonant frequency is 45Hz. Matched pairs can be produced by using speakers whose resonant frequencies are equally spaced above and below this nominal value. For example a 46Hz unit matched with a 44Hz until will produce a system with the optimum response.

## LOUDSPEAKER MOUNTING

Now the 'speakers can be mounted using four, 2BA 50mm long screws and nuts. Note that the 'speakers are mounted face to face. Before mounting smooth the edges of the 'speaker mounting aperture with a file. The "drivers" (loudspeakers) must be tightened up on their mounting gaskets to ensure an airtight fit.



Wiring up the speakers comes next. Note that the external driver is connected in *reverse* phase to the internal driver or else there is no bass output from the combination. The use of twin figure-8 speaker flex or alternatively 5A mains cable is all that is required here. Leave about a 610mm (2ft) length of lead from the internal speaker to ensure easy connection to the electronics stripboard panel.

As one of the drive units protrudes



## CUTTING LIST

### MAIN CABINET

- Panel A: 305mm (12in.) × 336mm (13¼in.) - 2 off
- Panel B: 305mm (12in.) × 336mm (13¼in.) - 2 off
- Panel C: 305mm (12in.) × 273mm (10¾in.) - 2 off

All cut from a single length of veneered chipboard measuring 305mm (12in.) wide × 244cm (96in.) long × 15mm (⅝in.) thick.

### SKIRT

- Panel D: 336mm (13¼in.) × 102mm (4in.) × 15mm (⅝) - 2 off
  - Panel E: 305mm (12in.) × 102mm (4in.) × 15mm (⅝in.) - 2 off
- Length of Vynair speaker grille cloth to cover top of "skirt".



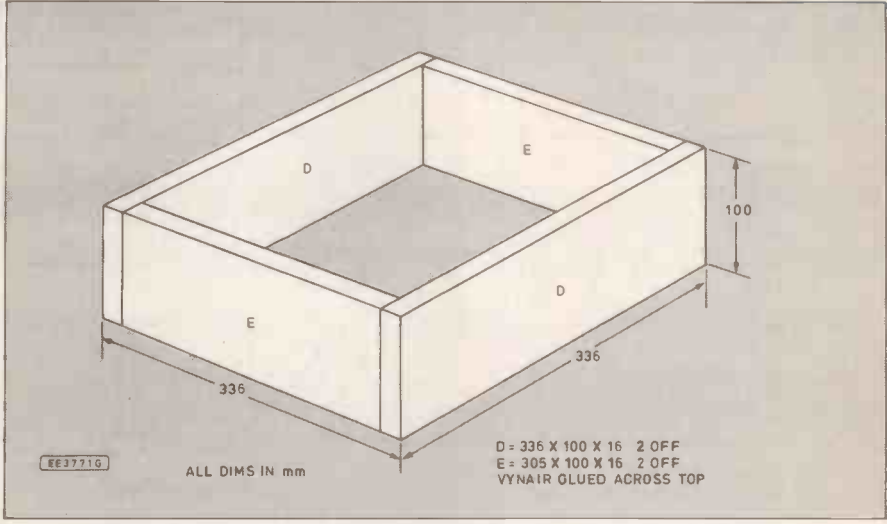


Fig. 4. Speaker surround, this is completely covered with grille cloth stretched over the top and sides.

Fig. 3. Dimensions and layout of the prototype enclosure.

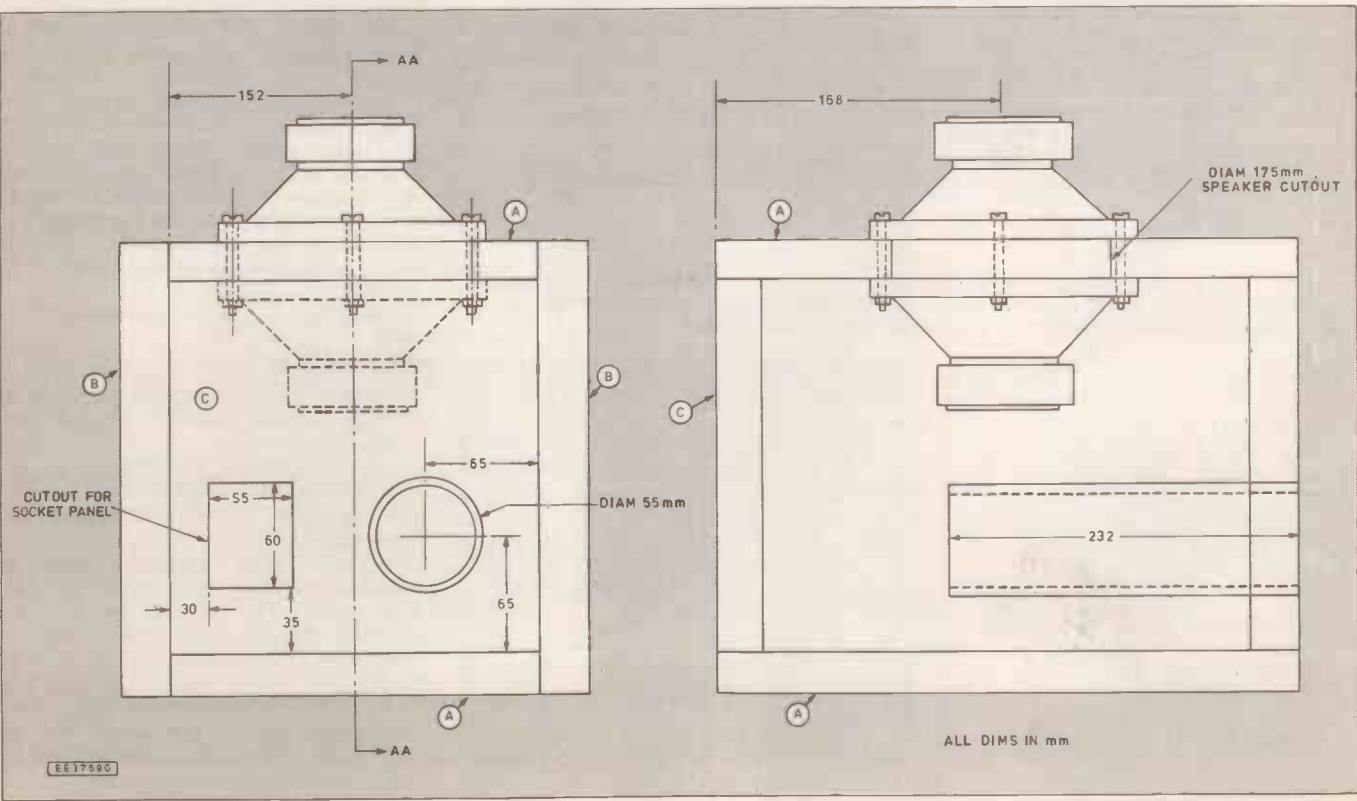

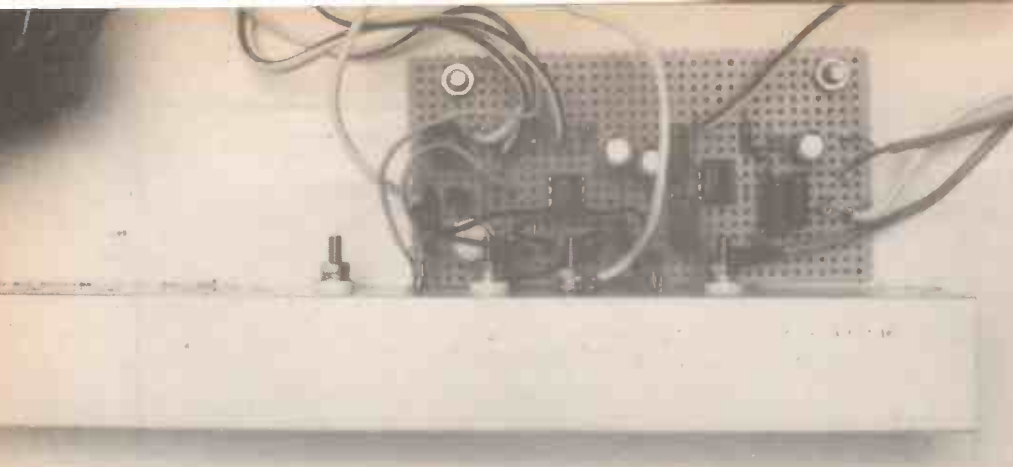

above the enclosure, some readers might like to surround this with a "skirt" and cover it with some speaker grille cloth. This can be accomplished by making a surround to cover the speaker, with grille cloth stretched across for a more cosmetic appearance, see Fig. 4. This can be fastened to the main enclosure with 6mm (1/4in.) dowels.

## EQUALISER CIRCUIT BOARD

Most of the electronic components are mounted on a piece of 0.1in. matrix stripboard, size 16 strips by 34 holes. The component layout and details of breaks required in the underside copper tracks are shown in Fig. 5.

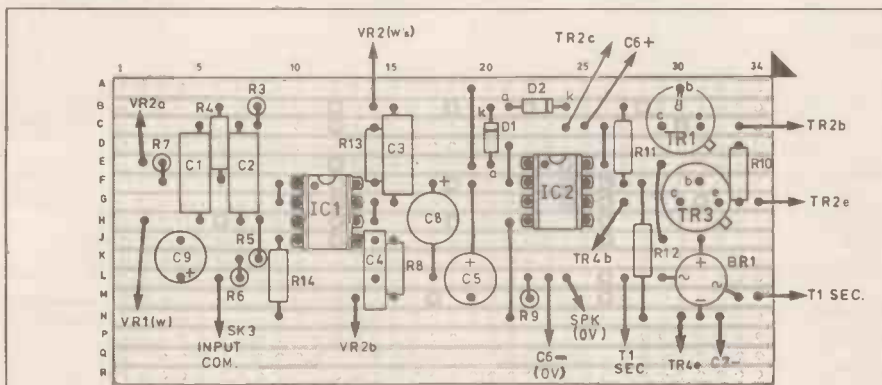


Fig. 5. Stripboard layout of the Sub-Woofer "equalising" circuit.


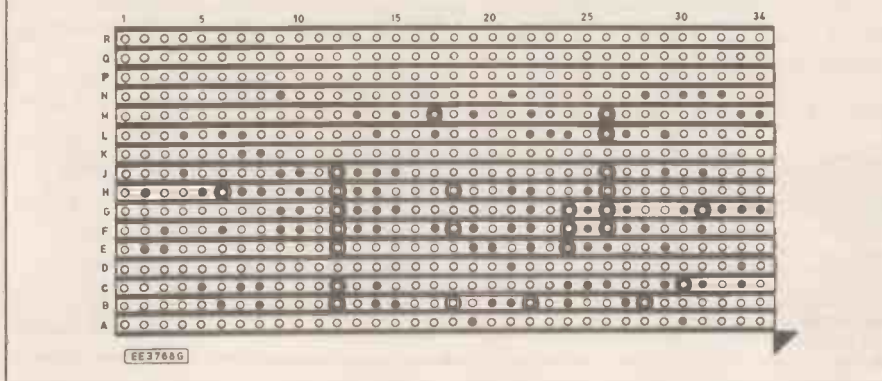


Fig. 6. Connections to the sockets, controls and off-board components. The metal casing of transistors TR2 and TR4 form the collector (c) connections and the usual insulating kit must be used when mounting them on the heatsink.

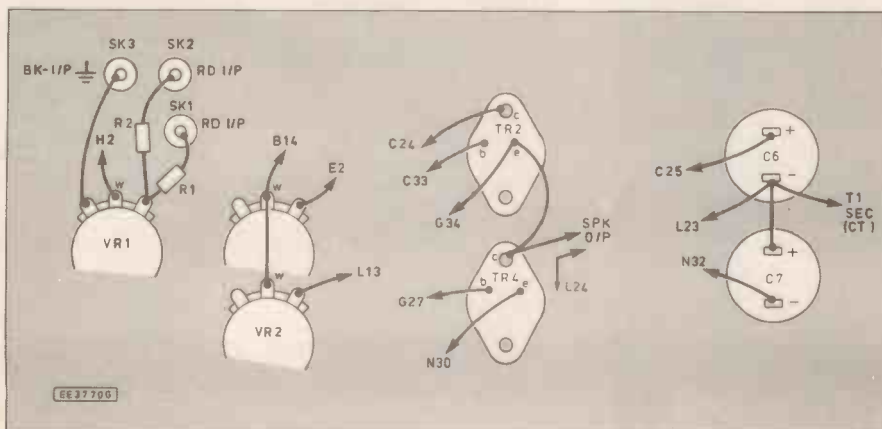

As long as the usual precautions are taken over the orientation of the transistors, capacitors and active components no problems should be experienced when making up the circuit board. In this regard special attention should be given to diodes D1 and D2.

Once you have completed the circuit board check and double-check for unwanted solder blobs and that the track breaks are complete and in the correct places. Connect flying leads to the board where indicated leaving these 305mm (12in.) long to facilitate easy interconnection.

Now mount the power transistors TR2 and TR4 on the specified heatsink. These must be insulated from the heatsink and each other in the normal manner using the washers and plastic bushes supplied. This can be checked with a multimeter switched to resistance. This should read an "open circuit".

## INTERWIRING

At this stage the circuit board, mains transformer, heatsink and the two large supply smoothing capacitors C6, C7 should be mounted in the cabinet. The other components, potentiometers and input sockets are mounted on the terminal recess dish - see photographs. Now the interwiring can be commenced.

Terminate the flying leads from the circuit board at their respective destinations. Some interwiring between off-board components will also need to be made and these can be seen in Fig. 6.

Finally, temporarily connect two 100 ohm resistors in series with the secondary leads from the transformer. This will protect your circuit in the event of an undetected error. Check your work for errors. When you are satisfied that all is well the circuit can be tried out.

## TESTING

Commence testing by gingerly switching on the power and standing back. You should be greeted with silence. If you get a loud hum or one or other of the two temporary resistors starts smoking you have a fault. Switch off immediately and rectify matters.

Assuming all is well, advance the Volume control VR1. Touching either of the input sockets SK1, SK2 should produce a buzz from the speakers. Now remove the two "protection" resistors, reconnect the transformer secondary leads and attach the front baffle to the rest of the cabinet, remembering to seal along the seams with filler.

The project is now complete.

## IN USE

All that remains is to connect the Sub-Woofer to your system and adjust the relative output levels.

The Sub-Woofer is designed to be driven from the speaker outputs of your existing speaker system. This provides the input signal.

Similarly most amplifiers have a switched auxiliary mains socket on the rear panel. The Sub-Woofer can be powered directly from this socket or alternatively connected directly to the mains.

As with any speaker system the best room placement is best found by experience. Avoid corners as this will excite the resonant modes of your room. □



# EVERYDAY ELECTRONICS

## NEWSAGENTS ORDER FORM

Please reserve/deliver a copy of  
Everyday Electronics for me each month

Signed.....

Name and Address.....  
(BLOCK CAPITALS PLEASE)

Everyday Electronics is published on the first Friday of each month and distributed by Seymour.  
Make sure of your copy of EE each month - cut out this form, fill it in and hand it to your newsagent.

### LOW COST 418MHz UHF RADIO SWITCHING

#### AS USED BY THE PROFESSIONAL SECURITY MARKET

Incorporating the latest Surface Acoustic Wave technology, the system consists of a small "zero-power", UHF transmitter with digital encoder and a UHF receiver unit with digital decoder and momentary output. Transmitter available either as fully assembled unit in its own key-lob case which is fully MPT approved (codes set by cutting tracks) or in kit form with 8-way DIL switch. Receiver also available in two kit forms, one which uses cut tracks to set code (over 13,000 codes available), the other uses an 8-way DIL switch (256 codes).

Kit Sizes:	Tx 45 x 30mm	Rx (both) 45 x 55mm
Kit Supplies:	Tx 3-15V	Rx (both) 9-15V
		Range: Up to 100m
Approved Key-lob Transmitter: TXKF.....		£25.99
Individual Kit Transmitter: TXKT.....		£15.99
Individual Kit Receiver (8-way DIL switch): RXDS.....		£19.99
Individual Kit Receiver (Cut Tracks): RXCT.....		£18.99
1 x TXKF + 1 x RXCT: SYS1.....		£39.99
1 x TXKT + 1 x RXDS: SYS2.....		£29.99

Quantity Discounts Available. Please allow 28 days for delivery  
Cheques/POs to:

### BLB Electronics

341 Darwen Road, Bromley Cross, Bolton BL7 9BY

### CAMBRIDGE COMPUTER SCIENCE LIMITED

LCD modules.....	16 char by 1: £4.00, 20 char by 2: £6.00, 40 char by 1: £8.00
5.25" Disk Drives, 80 Tk, DSDD.....	£25.00 each
5.25" Disk Drives, 80 Tk, DSDD Used, No Wty.....	£9.00 each
(The £15.00 drives are sold on a strictly "as is" basis)	
5.25" Disks, DSDD, 48tpi, boxes of 10 (free disk cleaner with 5 boxes).....	£3.00/box
Digital multimeter: 14 ranges, inc. leads & manual.....	£14.00 each
Apricot Disk drive PSU 5V w/ 2.5A, 12V w/ 2A.....	£10.00 each
5V w/ 6A PSU.....	£4.80 each
5V w/ 10A PSU.....	£6.40 each
Disk Drive Data lead BBC Micro to Disk Drives.....	Single 2.00 Dual £4.00 each
Disk Drive Power lead BBC Micro to Disk Drives.....	Single 2.00 Dual £4.00 each
8086 CPU chips.....	£2.00 each
Z80A CPU, CTC, PIO.....	£1.20 each; DMA £2.00; £4.50 all 4
27128 EPROMS (Ex equipment).....	£1.20 each or £5.00/5
256K DRAM (Ex Equipment).....	£0.40 each
1Mbit-10 DRAM (Ex Equipment).....	£1.40 each
256K Byte DRAM Modules, removed from equipment.....	£6.00 each
16, 18 & 20 pin dill low profile IC sockets 0.3" wide.....	£0.40/10; £3.00/100
22 & 24 pin dill low profile IC sockets 0.4" wide.....	£0.40/10; £3.00/100
24, 28, 32, 40 & 48 pin dill low profile IC sockets 0.6" wide.....	£0.40/10; £3.00/100
Circuit tester, finds faults in TTL & CMOS logic circuits, inc leads.....	£8.00 each
Metal project boxes drilled & painted but unused 28 x 32.5 x 9cm.....	£1.40 each
Used computer cards many useful components (large ones socketed)	£5.00 each
Floppy disk card (NEC FDC chip) £1.00, Wini controller (WD HDC chip).....	£1.00 each
CPU card (8088, Z80 & EPROMs).....	£3.00 each
Keyboards, full Qwerty, number pad and LCD.....	£8.00 each
Desktop computer case with 200W mains PSU (used).....	£30.00 each

Prices include postage. Add 50p (plus VAT) to orders below £5.00. All items new unless stated.  
Add 17.5% VAT to all prices. Send an SAE for our latest list or for more info.  
Dept EE, 374 Milton Road, Cambridge CB4 1SU  
Tel: 0223 424602, 0831 430496 or 0831 430552 (Mail order only)

### SHERWOOD ELECTRONICS

9 Lower Birchwood, Somercotes, Derbyshire DE55 4NG

#### \*\*\* SPECIAL OFFER \*\*\*

Choose any 2 packs FREE with every 10 £1 packs purchased.

SP1 15 x 5mm Red Leds	SP37 20 x 100u/35V radial caps.
SP2 15 x 5mm Green Leds	SP38 25 x 47u/25V radial caps.
SP3 12 x 5mm Yellow Leds	SP42 200 x Mixed 0.25W C.Film resistors
SP6 15 x 3mm Red Leds	SP44 12 x 5mm Leds-4 ea. Red, Grn., Yel.
SP7 12 x 3mm Green Leds	SP47 5 x Min. push button switches
SP8 10 x 3mm Yellow Leds	SP102 20 x 8 pin DIL sockets
SP10 100 x 1N4148 diodes	SP103 15 x 14 pin DIL sockets
SP11 30 x 1N4001 diodes	SP104 15 x 16 pin DIL sockets
SP12 30 x 1N4002 diodes	SP105 6 x 74LS00
SP18 20 x BC182 transistors	SP109 15 x BC557 transistors
SP20 20 x BC184 transistors	SP112 6 x Cmos 4093
SP23 20 x BC549 transistors	SP119 6 x Cmos 4072
SP25 5 x 555 timers	SP121 8 x Rect. Red Leds 5 x 2mm
SP26 5 x 741 Op-amps	SP122 8 x Rect. Green Leds 5 x 2mm
SP28 6 x Cmos 4011	SP123 5 x Rect. Yellow Leds 5 x 2mm
SP36 25 x 10u/25V radial caps.	SP125 10 x 1000u/16V radial caps

RESISTOR PACKS - 0.25W C.Film	
RP3 5 each value - total 365	£2.30
RP7 10 each value - total 730	£3.95
RP10 1000 popular values	£5.35

Catalogue - price £1  
Contains £2 vouchers redeemable  
against orders

Cheques or P.O. to **NO VAT** Please add £1 P&P to all orders  
**SHERWOOD ELECTRONICS**

### CONTROL PORT for PCs

This I/O Port follows the general approach of the 'INTERFACING to PCs' series in this mag, BUT allows user's prototype control circuitry to be set up and run OUTSIDE the PC.

The double sided pcb fits into an I/O slot, and a ribbon cable terminating in a D-25 plug allows the control of projects with little risk to the PC. On board facilities include: 8-bit A-D, 8-bit D-A, 8 inputs, 8 latched outputs, 3 strobes and 1 IRQ.

Available as:

(a) Etched double sided board with full instructions for drilling/assembly/testing using BASIC.....	£12.50
(b) Complete I/O card with ribbon cable and BASIC test programs. (Built and tested).....	£29.00

Also available: Test pod with D-25 socket providing analogue and digital test signals/outputs for the I/O card, with BASIC test programs on disc..... £17.00

All above prices include P&P. Mail Order only from:

**R. BARTLETT,**  
17, LIME TREE AVENUE, TILE HILL,  
COVENTRY CV4 9EY



# CRICKLEWOOD ELECTRONICS

CRICKLEWOOD ELECTRONICS LTD, 40 CRICKLEWOOD BROADWAY, LONDON NW2 3ET  
Tel: 081 452 0161 Fax: 081 208 1441

BOOKS	BOXES & CASES	CABLE & WIRE	CAPACITORS	CONNECTORS	KITS
RESISTORS	SEMI-CONDUCTORS	SPEAKERS	VIDEO HEADS	SWITCHES	TOOLS & BENCHWARE

SEND NOW FOR THE **CRICKLEWOOD ELECTRONICS** COMPONENT CATALOGUE  
ONE OF THE BEST RANGES AVAILABLE

Name.....  
Address.....

# INTERFACE

## Robert Penfold



**I**N LAST month's *Interface* article we considered the subject of barcodes. We continue on the same topic this month, with some ideas for a do-it-yourself barcode system. For those who missed last month's article it has to be pointed out that hardware and software featured here is not intended to be compatible with commercial barcodes. This system enables you to print out and read back your own barcodes, and it is in no way compatible with any commercial barcode systems.

### Code Writing

Clearly the first requirement of a barcode system is the ability to actually produce the barcodes. It would be possible to work out the codes and produce them using practically any computer drawing program, but this would be a slow and inconvenient way of handling things. What is needed is a program that can be fed with a decimal number, and which will then print out the corresponding barcode.

The program provided in the accompanying listing is for Microsoft QBasic or QuickBasic. It will print a barcode of any number which can be expressed in 8 binary bits, i.e. 0 to 255. The printed barcode has 10 bars, a narrow start bar, the 8 digit bars, and a broad stop bar. In the 8 bit codes broad bars are used to represent 1s, and 0s are represented by narrow bars. The decimal number symbolised by the code is printed under the barcode.

The program is suitable for either 24-pin or 9-pin Epson (or compatible) printers. Triple density is used for 24-pin printers, and quad density for 9-pin types. These high densities are necessary to ensure a reliably readable code of good contrast. For good results the printer should still be fitted with a reasonably fresh ribbon. The program defaults to the 24-pin settings, but this could be easily changed if required.

### Basic Program

The width of the barcode (not including the start and stop bars) is set by two constants declared at the beginning of the program. TD.DOTS sets the width for 24-pin printers, and QD.DOTS sets the width for 9-pin printers. The value entered here is the number of dot positions which will be printed minus 1. The values given, 175 and 239 respectively, give a width of approximately 25mm (not including stop and start bars, as mentioned above).

The 24-pin printer actually prints at 180 dots per inch, but the value given has been rounded down from 179 to 175, to give a number of positions (176) which

is exactly divisible by 8. This is important. If you want to change the width of the barcode, you just need to alter these values. All other values are derived from them.

Normally, the barcode is printed with the least significant bit represented by the left-most bar. This is not normally of any great significance, as the barcode will be machine-read. In case it offends anyone, however, provision has been included to reverse the direction of printing so the MSB is the left-most.

The program is menu-driven. Selecting the options is simply a case of pressing the highlighted initial letters. The select printer option presents a submenu which is used in the same way. Swapping the MSB acts immediately. When you select the Enter value option, you have simply to enter the value to be printed and press return. Out of range values and nonsense input are trapped. The barcode is printed immediately, so you should be sure the printer is on line and ready to print before selecting this option.

With a little ingenuity it should be possible to adapt the program to suit individual needs. It could probably be modified to print longer barcodes having more bits, to print "x" number of each barcode, etc.

### Hardware

As pointed out last month, the special high resolution sensors for use in barcode reader "pens" are very expensive, and there would seem to be no current source of supply for the home constructor anyway. My first attempts at reading barcodes used a passive sensor plus a fibre-optic cable. The cable was used as a simple means of giving a narrow angle of "view", and it seems to be possible to obtain quite good resolution in this way. The problem with the simple circuits I tried was a lack of sensitivity, and poor reliability (which probably stemmed from the poor sensitivity).

Better results were obtained using a reflective infra-red sensor. This consists basically of an infra-red l.e.d. and a photo-transistor mounted side-by-side, and "looking" in the same direction. If something fairly reflective is placed in front of and very close to the sensor, the infra-red light from the l.e.d. will be reflected back to the photo-transistor, and the latter will be switched on.

When choosing a photo-sensor of this type you are not exactly spoilt for choice. I mainly experimented with the OPB706B sold by Maplins, which would seem to be the same as the RS "miniature diffuse scan opto-switch sensor". There is also an

RS "standard" type which is somewhat larger. This seems to give quite good results despite its larger size, but as it is more expensive and less widely available, I opted to use the smaller device for the final system.

### Resolution


Looking at one of these sensors you would probably not expect the resolution to be very high, but they can read barcodes accurately provided they are not printed out using very narrow lines or spaces. With the fine lines at about 1.5 millimetres and the smallest gap between lines no smaller than this, one of these low cost reflective sensors seems to work perfectly well.

By getting everything setup just right, and using an aperture to restrict the field of view, it would probably be possible to obtain much finer resolution. However, unless you really need to use more compact barcodes, it is much easier just to settle for the natural resolution of the sensor.

In order to get good results at the natural resolution of the sensor it is still necessary for things to be setup reasonably accurately. There are two main points to watch, one of which is that the sensor is perpendicular to the barcode, and not keeled over at an angle of significantly less than 90 degrees. The second point is that the distance between the sensor and the barcode is critical. It is best to experiment a little to find the distance that gives optimum results, but the ideal gap between the barcode and the sensor is only about one to two millimetres.

In order to get good results the sensor really needs to be recessed slightly into a pen type case, so that the reader can be operated by running it over the barcode, with the case actually rubbing the barcode. Simply waving the reader above the barcode will not provide good results using one of these simple sensors.

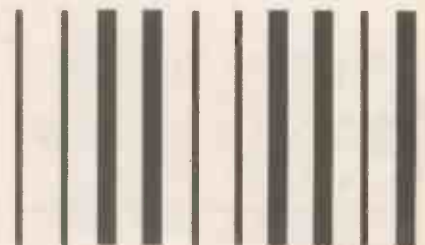Next month we will conclude this look at barcodes with a barcode reader circuit and matching software.



102 Decimal

Example of the type of barcode generated.



```

DECLARE SUB printbar (bardat$( ), all$, none$, mode%, first%,
last%, barwidth%)
DECLARE SUB selectprinter (all$, none$, mode%, printer$, first%,
last%, barwidth%, bardat$( ))
DECLARE SUB setscreen (printer$, direc$)
DECLARE SUB setdat (bardat$( ), all$, none$, num%, first%, last%,
barwidth%)

```

WIDTH LPRINT 255

'You can change the next two constants to change the width of the barcode.

'The values here give a width of 1 inch plus start and end bars.

'The value (CONST + 1) should be exactly divisible by 1,

'and the ratio TD.DOTS/QD.DOTS should be approx. 3/4.

CONST TD.DOTS = 175

CONST QD.DOTS = 239

'set defaults for Epson 24-pin, triple density.

REDIM bardat\$(0 TO TD.DOTS)

mode% = 39

all\$ = STRING\$(3, CHR\$(255))

none\$ = STRING\$(3, CHR\$(0))

printer\$ = "Epson 24 - Triple density"

direction\$(1) = "as leftmost bar"

direction\$(2) = "as rightmost bar"

first% = 0

last% = TD.DOTS

barwidth% = (TD.DOTS + 1) \ 8

SCREEN 0, 1

CLS

setscreen printer\$, direction\$(1)

DO UNTIL UCASE\$(choice\$) = "Q"

choice\$ = INKEY\$

SELECT CASE UCASE\$(choice\$)

CASE "S"

LOCATE 10, 6

COLOR 7

PRINT "elect Printer"

selectprinter all\$, none\$, mode%, printer\$, first%, last%,

barwidth%, bardat\$( )

setscreen printer\$, direction\$(1)

CASE "E"

LOCATE 12, 6

COLOR 7

PRINT "enter value and print barcode"

setdat bardat\$( ), all\$, none\$, num%, first%, last%,

barwidth%

LPRINT CHR\$(27); "3"; CHR\$(24); 'set line spacing

FOR lines = 1 TO 4

printbar bardat\$( ), all\$, none\$, mode%, first%, last%,

barwidth%

NEXT lines

LPRINT CHR\$(27); "2"; 'Reset printer line spacing

LPRINT num%

LPRINT 'Print line space

setscreen printer\$, direction\$(1)

CASE "M"

SWAP first%, last%

SWAP direction\$(1), direction\$(2)

setscreen printer\$, direction\$(1)

CASE "Q"

LOCATE 16, 6

COLOR 7

PRINT "uit"

END SELECT

LOOP

END

SUB printbar (bardat\$( ), all\$, none\$, mode%, first%, last%, barwidth%)

IF last% < first% THEN

st% = -1

limit% = first% + barwidth% + 3 \* (barwidth% \ 3)

ELSE

st% = 1

limit% = last% + barwidth% + 3 \* (barwidth% \ 3)

END IF

LPRINT CHR\$(27); CHR\$(42); CHR\$(mode%); CHR\$(limit%

MOD 256); CHR\$(limit% \ 256);

FOR dat = 1 TO barwidth% \ 3

LPRINT all\$;

NEXT dat

FOR dat = 1 TO barwidth% \ 3

LPRINT none\$;

NEXT dat

FOR dat = first% TO last% STEP st%

LPRINT bardat\$(dat);

NEXT dat

FOR dat = 1 TO barwidth% \ 3

LPRINT none\$;

NEXT dat

FOR dat = 1 TO barwidth%

LPRINT all\$;

NEXT dat

LPRINT

END SUB

SUB selectprinter (all\$, none\$, mode%, printer\$, first%, last%, barwidth%, bardat\$( ))

LOCATE 18, 5: COLOR 2: PRINT "Epson 24-pin, ";

COLOR 7: PRINT "T";: COLOR 2: PRINT "triple density"

LOCATE 20, 5: PRINT "Epson 9-pin, ";

COLOR 7: PRINT "Q";: COLOR 2: PRINT "quad density"

ERASE bardat\$

DO

choice\$ = INKEY\$

SELECT CASE UCASE\$(choice\$)

CASE "T"

mode% = 39

printer\$ = "Epson 24 - Triple density"

all\$ = STRING\$(3, CHR\$(255))

none\$ = STRING\$(3, CHR\$(0))

REDIM bardat\$(0 TO TD.DOTS)

barwidth% = (TD.DOTS + 1) \ 8

IF first% > last% THEN first% = TD.DOTS ELSE last%

= TD.DOTS

done = -1

CASE "Q"

mode% = 3

printer\$ = "Epson 9 - Quad density"

all\$ = CHR\$(255)

none\$ = CHR\$(0)

REDIM bardat\$(0 TO QD.DOTS)

barwidth% = (QD.DOTS + 1) \ 8

IF first% > last% THEN first% = QD.DOTS ELSE last%

= QD.DOTS

done = -1

CASE CHR\$(27)

EXIT SUB

END SELECT

LOOP UNTIL done

END SUB

SUB setdat (bardat\$( ), all\$, none\$, num%, first%, last%, barwidth%)

IF first% > last% THEN limit% = first% ELSE limit% = last%

getnumber:

LOCATE 18, 5

INPUT "Please enter a number 0 - 255 inclusive: ", num\$

IF num\$ = "" THEN num\$ = ""

IF (ASC(num\$) < 48) OR (ASC(num\$) > 57) THEN

num% = 256

ELSE

num% = VAL(num\$)

END IF

IF (num% < 0) OR (num% > 255) THEN

LOCATE 20, 5

PRINT CHR\$(7); "DO AS YOU ARE TOLD!"

GOTO getnumber

END IF

FOR dotpos = 0 TO limit%

IF num% AND (2 ^ (dotpos \ barwidth%)) THEN

IF dotpos MOD barwidth% < (barwidth% \* 2 \ 3) THEN

bardat\$(dotpos) = all\$

ELSE

bardat\$(dotpos) = none\$

END IF

ELSE

IF dotpos MOD barwidth% < (barwidth% \ 3) THEN

bardat\$(dotpos) = all\$

ELSE

bardat\$(dotpos) = none\$

END IF

END IF

NEXT dotpos

LOCATE 18, 5

PRINT SPACES(45)

LOCATE 20, 5

PRINT SPACES(20)

END SUB

SUB setscreen (printer\$, direc\$)

CLS

COLOR 2: LOCATE 5, 10: PRINT "Please select:"

LOCATE 10, 5: COLOR 7: PRINT "S";

COLOR 2: PRINT "elect Printer ("; printer\$; ")"

LOCATE 12, 5: COLOR 7: PRINT "E";

COLOR 2: PRINT "enter value and print barcode"

LOCATE 14, 5: COLOR 7: PRINT "M";

COLOR 2: PRINT "SB"; direc\$

LOCATE 16, 5: COLOR 7: PRINT "Q";

COLOR 2: PRINT "uit"

END SUB

## BARCODE PRINTING PROGRAMME (QBASIC)

# WHETHER ELECTRONICS IS YOUR HOBBY OR YOUR LIVELYHOOD . . . YOU NEED THE MODERN ELECTRONICS MANUAL



ORDER NOW  
ON 10 DAYS  
FREE APPROVAL

## The essential reference Work

- Easy-to-use format
- Clear and simple layout
- Regular updates
- Sturdy ring-binder
- News of latest developments
- Full components checklist
- Extensive data tables
- Detailed supply information
- Ready-to-transfer PCBs
- Comprehensive subject range
- Accurate assembly instructions
- Concise repair procedures

## EVERYTHING YOU NEED TO KNOW ABOUT ELECTRONICS!

If the fascinating and fast-changing world of electronics is your livelihood, your study subject or simply your passion, the new revised edition of **THE MODERN ELECTRONICS MANUAL** is the reference work for you to have at your side.

The base manual contains information on the following subjects:

**BASIC PRINCIPLES:** symbols, components and their characteristics, passive component circuits, power supplies, acoustics and electroacoustics, the workshop, principles of metrology, measuring instruments, digital electronics, operational amplifiers, timers, physics for electronics.

**CIRCUITS TO BUILD:** construction techniques, radio, telephony, microcomputing, measuring instruments, vehicle electronics, security, audio, power supplies, electronic music (over 25 different projects).

**REPAIRS AND MAINTENANCE:** radio, television, audio/hi-fi, telephones.

**DATA:** diodes, transistors, thyristors and triacs, digital and linear i.c.s, microprocessors.

The manual also covers **Safety, Specialist Vocabulary with Abbreviations and Suppliers.**

**OVER 1,000 pages, A4 format weighing over 3.5kg.**

**Now - at last - the most comprehensive reference work ever produced at a price you can afford, the new revised edition of **THE MODERN ELECTRONICS MANUAL** provides you with all the essential information you need.**



**Over 1,000 pages** of well-organised and clearly explained information is brought to you by an expert editorial team whose combined experience ensures the widest coverage.

**Regular supplements** to this unique publication, each around 160 pages, mean that you will always be kept abreast of the latest developments from the UK, USA and Europe as they occur

### ALL-IN-ONE AND EASY-TO-USE

A sturdy ring-binder allows you to use the manual on your workbench. The looseleaf format also means you can slot in the regular updates as they arrive – so all your information is there at a glance.

### EXTENSIVE GLOSSARY

Should you come across a technical word, phrase or abbreviation you're not familiar with – simply turn to the glossary included in the manual and you'll find a comprehensive definition in plain English.

### REGULAR UPDATES

Unlike a book or encyclopedia, the manual is a living work – continuously updated by new material. Recent or upcoming supplements include radio, superconductors, electric motors, basic electronic building blocks for beginners which can be joined together to construct elaborate circuits, filters, IBM PC and compatibles (including use of PC cards). Supplements are sent to you approximately every two months.

Each supplement contains approximately 160 pages – all for only £23.50 + £2.50 p&p. You can of course return any supplement which you feel is superfluous to your needs.

### RESPONDING TO YOUR NEEDS

We are able to provide you with the most important and popular articles in our updating supplements. Our unique updating system is based on answers from readers request questionnaires. Through this service you are able to let us know exactly what information you require in your manual. You can also contact the editor directly in writing if you have a specific technical request or query relating to the manual.

### ASSEMBLING ...

There's nothing to beat the satisfaction of creating your own project. From basic principles to circuit-building, the manual describes clearly, with appropriate diagrams, how to assemble radios, loudspeakers, amplifiers, micro-computers and measuring instruments.

The new revised edition of The Modern Electronics Manual contains practical, easy-to-follow instructions for building and programming your own computer. It shows you how to make fun gadgets such as a remote control door opener and a digital rev. counter for your car. It also tells you how to construct useful devices like test gear, security and baby alarms – plus – many more popular devices.

**Wimborne Publishing Ltd., 6 Church St, Wimborne, Dorset BH21 1JH  
Tel: 0202 881749 Fax: 0202 841692**



# THE MODERN ELECTRONICS MANUAL

**New Revised Edition of Basic Work:** Now contains over 1,000 pages of information.

**Regular Updates:** Approximately 160-page supplements of additional information which are forwarded to you immediately on publication. These are billed separately and can be discontinued at any time.

**Presentation:** Durable looseleaf system in large A4 format (197mm × 210mm)

**Price of the Basic Work:** £39.95 + £5.50 p&p (to include a recent supplement).

**YES** please send me on 10 days free approval **THE MODERN ELECTRONICS MANUAL**. If I decide to keep the manual, I shall then pay **only £39.95** plus £5.50 postage and packing at the end of the 10 days approval period. I shall also receive the appropriate Updating Supplements several times a year. These are billed separately and can be discontinued at any time.

FULL NAME .....  
(PLEASE PRINT)

ADDRESS.....

POSTCODE .....

I AM OVER 18

SIGNATURE.....

(Parent or guardian must sign if under 18)

### ORDER FORM

Simply complete and return the order form to the following address

**The Modern  
Electronics Manual  
Wimborne Publishing Ltd  
6 Church Street  
Wimborne Dorset BH21 1JH**

**OVERSEAS ORDERS:** All overseas orders must be prepaid but are supplied under a money-back guarantee of satisfaction. If you are not entirely happy with the manual return it within a month for a refund of the purchase price (you do have to pay the postage). Add the following amounts to the price of the manual to cover postage:

EIRE £10.50 (air mail only)  
EUROPE (including C.I.S.) £21.00 (air mail only)  
MIDDLE EAST/FAR EAST/INDIA } £20 surface  
AFRICA/SOUTH AFRICA } £37 air  
SOUTH AMERICA }

REST OF THE WORLD £25 surface, £31 air

Note surface mail can take around 8 weeks to some parts of the world. Each manual weighs about 4.5kg when packed.

All payments must be made in £'s Sterling payable to Wimborne Publishing Ltd. We accept Mastercard (Access) and Visa credit cards.

# ARTWORK LIGHT BOX

ALAN WINSTANLEY

Make light work of producing your own printed circuit board masters



## Construction

The general sizes of the parts used, and a cutting list is shown in Fig. 1. It should be pointed out that the prototype was partly designed to fit a piece of Perspex which happened to be available.

It should be possible for readers to obtain Perspex or polycarbonate (perhaps offcuts) from either plastics suppliers or shop sign makers, see *Yellow Pages*. Clear plastic could be used, perhaps sandpapering it down to diffuse the light.

Standard Conti-Board is 15mm (0.6in.) thick and is readily available from all D.I.Y. stores. Buy a white finish 1800mm length × 305mm wide (6ft. × 1ft. nominal) – the product is very cheap and a length can be bought for under £4.

The board can be cut to size with a handsaw or a medium-speed jigsaw. Special jigsaw blades are available to give a smooth cut and prevent the melamine coating from splintering away (e.g. Black & Decker Ref. No 5194).

When making the two sloping end pieces, cut them out and clamp them firmly in a vice. Use a Surform, for example, to file the cut edges together till smooth – both ends will then be the same size.

**T**HIS Light Box has been specially designed to be of help when originating and drafting p.c.b. (printed circuit board) artwork. It permits the constructor to view the artwork positive very clearly and he can also obtain a "see-through" view of any artwork (if it is drawn on standard translucent or transparent media), so that the designer sees both the component layout on top of the proposed artwork, plus an X-Ray view of the copper track "through" the board – see photographs.

This ability to see the copper track layout with the component layout superimposed on top can be of great assistance when drawing up artwork. It is rather like designing a transparent printed circuit board!

## Light Box

The Artwork Light Box has a sloping front panel made from white acrylic plastic (e.g. 3mm Perspex) and is illuminated from inside by a fluorescent

light. The cabinet itself is made from readily-available "Conti-Board" which has a white melamine finish. The white surface reflects light around the inside of the box and helps to diffuse it.


Rather than use miniature fluorescent tubes, which require control units, starters etc., a compact "2D"-type tube was employed on the prototype, making the light very simple to install, just like a normal light bulb. Because of the convoluted shape of the tube, this contributes to giving a relatively diffused light in the box, unlike short compact tubes (e.g. Osram types).

The tube clips onto an electronic adaptor which fits a standard BC socket. Unlike some compact fluorescent tubes, the 2D-type bulb can be replaced when it fails without having to change the whole unit, thus being cheaper to run.

It is claimed that the tube is good for some 8,000 hours, however, which is equivalent to three years usage at six hours per day. That's a lot of p.c.b. designing.



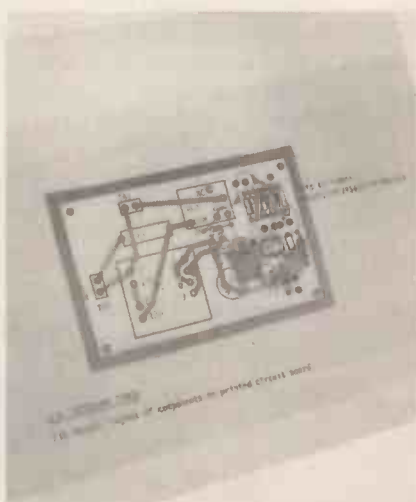The completed artwork on the light box—the precision 0.1in. matrix grid is also visible. This view is actually equivalent to seeing the copper track pattern "through" the board from the component side.




The artwork with the finalised component layout superimposed on it. This stage can be used for double-checking your copper track design for errors or omissions.




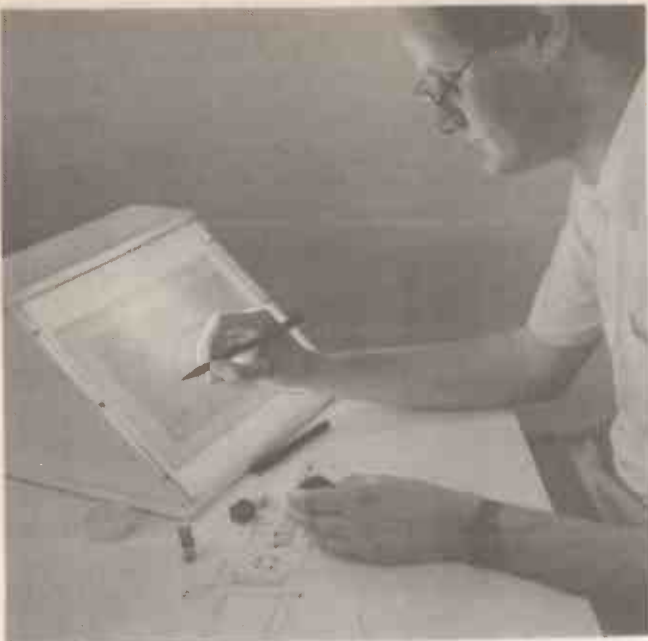The artwork is turned over and clearly labelled "Copper Track View Side" – this is your first sight of the actual copper foil pattern which will be etched into your p.c.b.!





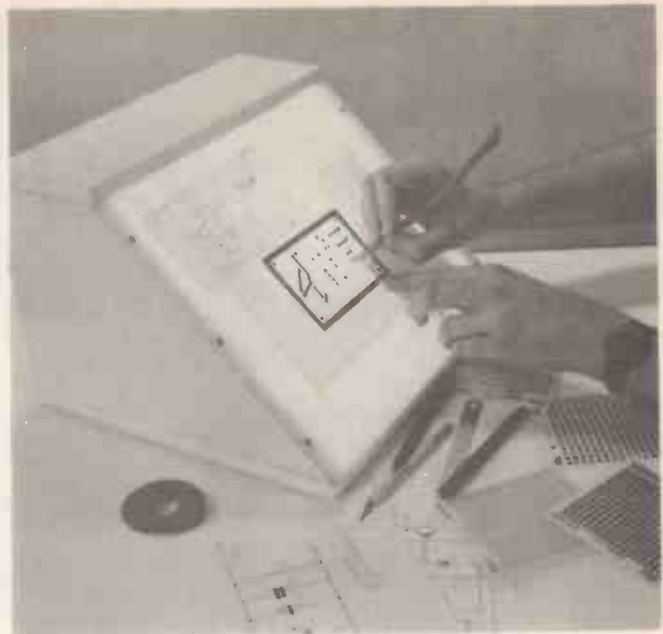Using the "light box" to draft a rough component layout diagram, referring to the circuit diagram and manufacturer's data as required.



Preparing the "master" artwork using rub-down transfers and tape. The proposed copper track layout shows through the paper so that an X-ray view is seen

# ARTWORK LIGHT BOX – CUTTING LIST

Approx cost **£20**

Base: 345mm × 305mm – Qty. 1  
 End Piece: 195mm × 305mm/105mm – Qty. 2

Rear Panel: 195mm × 315mm – Qty. 1  
 Top Ledge: 105mm × 345mm – Qty. 1

All above made from standard white Conti-Board 15mm thick. Buy a length measuring 305mm wide × 1800mm approx (available from every DIY store, £4 approx.)  
 Conti Edging Strip, white

White Perspex (acrylic): 3mm thick, 345mm × 282mm  
 Available from plastics stockists or shop sign makers (see *Yellow Pages*). A different size could be used if required, and the dimensions of the Conti-Board parts would then need amending.

## Other Parts

Chipboard Corner joint blocks (e.g. Plasplugs) – Qty. 8

No.6 × 19mm (¾in.) countersunk chipboard screws – Qty. 38


Thorn 2D Fluorescent Light Fitting (2D Tube + BC Adaptor). Part NO. 2DA10.BC

45° BC batten mounting light socket

6A twin-core mains flex, as required

p-clip, screws, 3A fused mains plug, etc

Fig. 1. Cutting details and dimensions for the Light Box. Dimensions can be altered as required, but if a 2D-tube is used the minimum depth of 305mm must be adhered to. Join like letters (A-to-A) together to realise the complete unit.

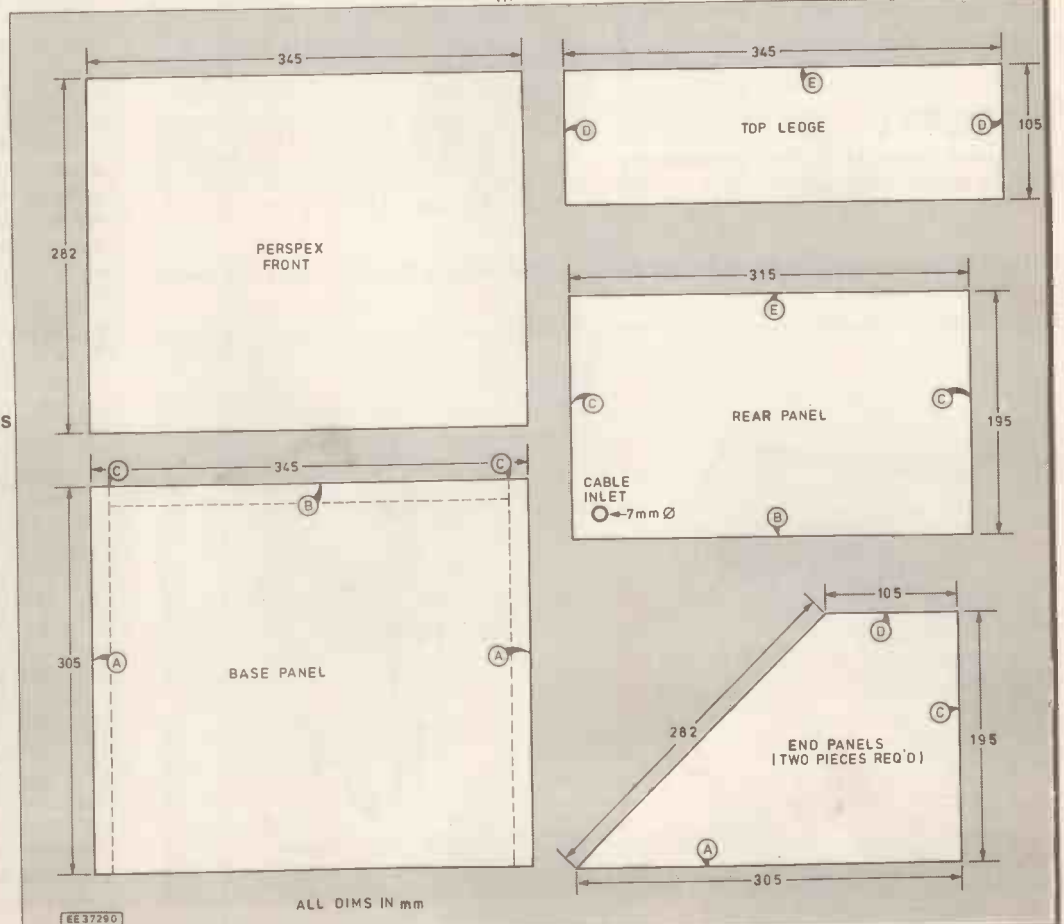

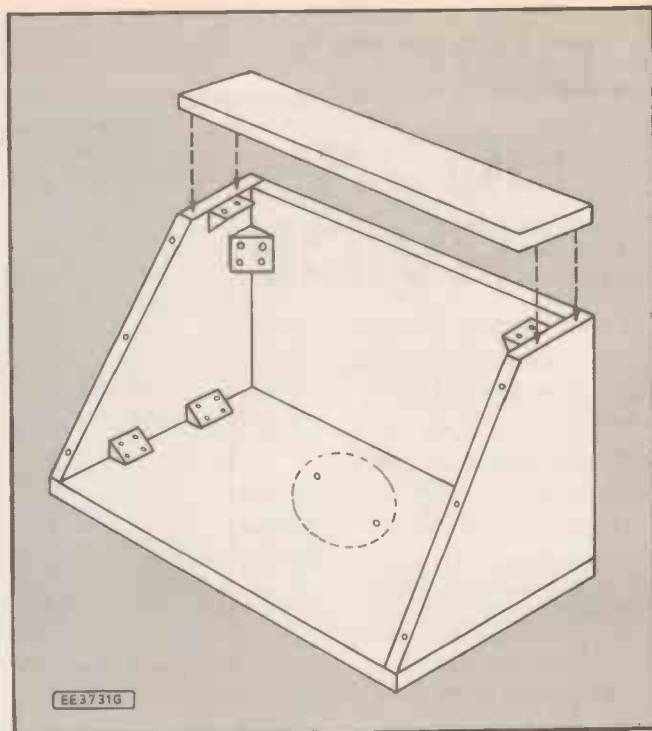
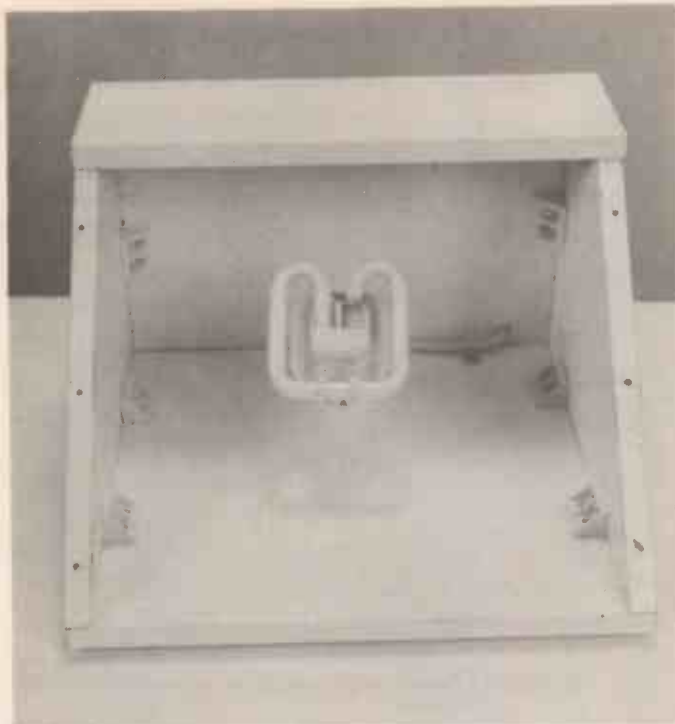


Fig. 2. (right). Three-quarter view without the Perspex front. The dotted area represents the location of the 45 degree batten bulb holder. The interior of the Light Box, with Perspex cover removed, the fluorescent 2D-type tube can be seen clearly in the photograph.

## On The Block


The Conti-Board is joined together using right-angle plastic blocks which themselves are screwed to the board, Fig. 2 and Fig. 3. Preferably use only chipboard screws for this (see Parts List).

Start off screw holes by drilling a pilot hole or use a bradawl first before driving the screws home. In fact, if ever there was a job for a rechargeable screwdriver, this is it! If necessary, do not tighten the screws until you are happy with the joint fit and alignment – it is possible to juggle the joints to a limited extent to obtain a reasonable finish before tightening the joints together for good.

The dimensions are not critical, although the cabinet must have sufficient depth to accommodate the 2D fluorescent tube. The constructor must maintain at least the same depth as per the prototype – this is very important, or the tube will not fit.

The 2D fluorescent tube is connected via a sloping batten-mounted BC socket, with the result that the tube is parallel with the Perspex front panel. It is connected via twin-core 6A flex which passes through a hole in the rear panel, and the wire is secured with a suitable p-clip inside to prevent it from pulling out. Connect the other end to a plug with a 3A fuse.

Fig. 3. End view of the Light Box showing the rough positioning of the corner blocks and sloping front opaque screen.

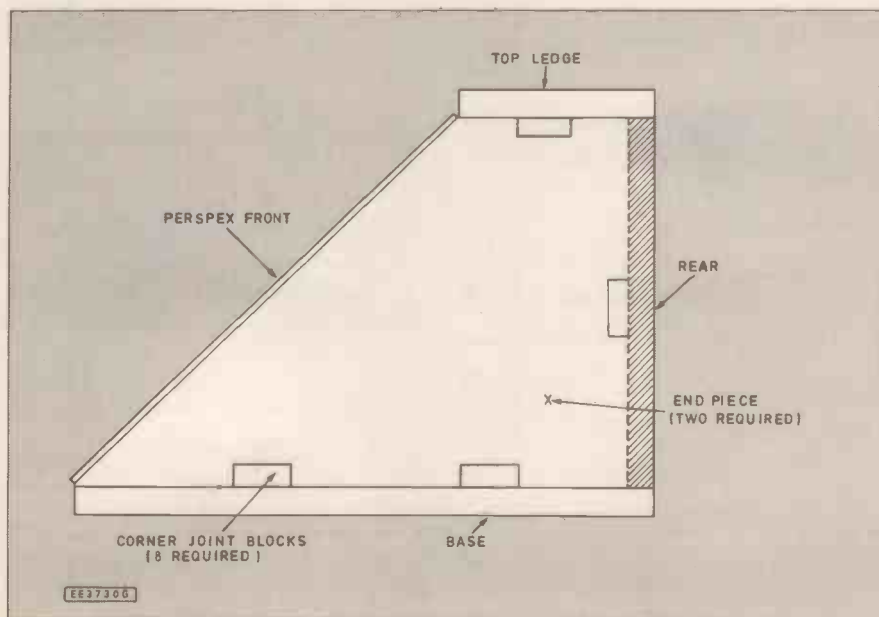

## Finishing Off

All cut edges can be finished off with iron-on edging. This is white melamine strip on a roll, with a hot-melt glue backing. A heat gun or an iron can be used to fix this down, and it can be trimmed with a knife afterwards as the strip becomes brittle after application.

After assembling all of the woodwork, plug the 2D light into the BC socket and check that it illuminates properly (it should start immediately, but will take a couple of minutes to reach full intensity). **IT CANNOT BE USED ON ANY TYPE OF DIMMER CIRCUIT.**

If the lamp operates, the final step is to screw on the perspex front panel using the same countersunk chipboard screws as before, having made countersunk recesses in the panel. Fit four adhesive cabinet feet at the bottom, and the Light Box is then ready to use.

## Light Options

One option which readers may wish to explore is the use of normal filament light bulbs in place of the fluorescent tube; this will very substantially reduce construction costs.

There is no reason why this cannot be done, but it will be best to use two sloping BC bulb holders, of the same type as used in the prototype. Employ two 15W Pygmy bulbs *only*, and this will give adequate illumination although, having used both systems, the author much prefers the fluorescent tube.

If using light bulbs, it might also be a good idea to allow a little ventilation through the box. Do this by reducing the height of the rear panel by say 13mm ( $\frac{1}{2}$ in.), so that there is a gap along the top.

You will soon find your Light Box an indispensable aid when drafting both rough layout diagrams and master artwork for p.c.b. designs. □



# DIRECT BOOK SERVICE

The books listed have been selected by Everyday Electronics editorial staff as being of special interest to everyone involved in electronics and computing. They are supplied by mail order direct to your door. Full ordering details are given on the last book page. For another selection of books see next month's issue.

## EVERYDAY ELECTRONICS DATA BOOK

**Mike Tooley BA**  
(published by EE in association with PC Publishing)  
This book is an invaluable source of information of everyday relevance in the world of electronics. It contains not only sections which deal with the essential theory of electronic circuits, but also deals with a wide range of practical electronic applications.

It is ideal for the hobbyist, student, technician and engineer. The information is presented in the form of a basic electronic recipe book with numerous examples showing how theory can be put into practice using a range of commonly available "industry standard" components and devices.

A must for everyone involved in electronics!  
256 pages **Order code DA12** £8.95

## ELECTRONICS TEACH-IN No. 3 - EXPLORING ELECTRONICS (published by Everyday Electronics)

**Owen Bishop**  
Another EE value for money publication aimed at students of electronics. The course is designed to explain the workings of electronic components and circuits by involving the reader in experimenting with them. The book does not contain masses of theory or formulae but straightforward explanations and circuits to build and experiment with.

Exploring Electronics contains more than 25 useful projects, assumes no previous knowledge of electronics and is split into 28 easily digestible sections.  
88 pages (A4 size) **Order code T13** £2.45

## COMPUTERS AND MUSIC - AN INTRODUCTION

**R. A. Penfold**  
Computers are playing an increasingly important part in the world of music, and the days when computerised music was strictly for the fanatical few are long gone. Computer-based music systems in the past have tended to be either horrendously expensive, very crude, or both. These days, prices are much more modest and the potential of the equipment is much greater. Consequently a lot of musicians are being tempted into the unfamiliar territory of computer music systems.

If you are more used to the black and white keys of a synth keyboard than the QWERTY keyboard of a computer, you may be understandably confused by the jargon and terminology bandied about by computer buffs. But fear not, setting up and using a computer-based music making system is not as difficult as you might think.

This book will help you learn the basics of computing, running applications programs, wiring up a MIDI system and using the system to good effect, in fact just about everything you need to know about hardware and the programs, with no previous knowledge of computing needed or assumed. This book will help you to choose the right components for a system to suit your personal needs, and equip you to exploit that system fully.  
174 pages **Temporarily out of print**

## A CONCISE INTRODUCTION TO MS-DOS

**N. Kantaris**  
This guide is written with the non-expert, busy person in mind and, as such, it has an underlying structure based on "what you need to know first, appears first". Nonetheless, the guide is also designed to be circular, which means that you don't have to start at the beginning and go to the end. The more experienced user can start from any section.

The guide covers versions 3.0, 3.1 and 3.2 of both PC-DOS and MS-DOS as implemented by IBM and other manufacturers of "compatible" microcomputers, including the AMSTRAD PCs. It covers both floppy disc-based systems and hard disc-based systems.  
64 pages **Order code BP232** £2.95

# Special Everyday Electronics Books

## ELECTRONICS TEACH-IN No.4 INTRODUCING DIGITAL ELECTRONICS (published by Everyday Electronics)

**Michael J. Cockcroft**  
Although this book is primarily a City & Guilds Introductory level course (726/301), approximately 80% of the information forms a very basic introduction to electronics in general, it therefore provides an excellent introductory text for beginners and a course and reference book for GCSE students.

Full details on registering for C&G assessment, details of assessment centres, components required and information on the course in general are given.

The City & Guilds introduction to module 726/301 reads: "A candidate who satisfactorily completes this module will have a competence to identify basic components and digital integrated circuits and connect them together to form simple working circuits and logic units." This provides an excellent introduction to the book.  
112 pages (A4 size) **Order code T14** £2.95

## ELECTRONIC PROJECTS - BOOK 1 (Published by Everyday Electronics in association with Magenta Electronics)

Contains twenty of the best projects from previous issues of EE each backed with a kit of components. The projects are: Seashell Sea Synthesiser, EE Treasure Hunter, Mini Strobe, Digital Capacitance Meter, Three Channel Sound to Light, BBC 16K Sideways Ram, Simple Short Wave Radio, Insulation Tester, Stepper Motor interface, Epm Eraser, 200MHz Digital Frequency Meter, Infra Red Alarm, EE Equaliser Isolator, Bat Detector, Acoustic Probe, Mains Tester and Fuse Finder, Light Rider - (Lapel Badge, Disco Lights, Chaser Light), Musical Doorbell, Function Generator, Tilt Alarm, 10W Audio Amplifier, EE Buccaneer Induction Balance Metal Detector, BBC Midi Interface, Variable Bench Power Supply, Pet Scarer, Audio Signal Generator.  
128 pages (A4 size) **Order code P1** £2.45

## ELECTRONICS TEACH-IN No.5 GUIDE TO BUILDING ELECTRONIC PROJECTS (NEW)

Published by EVERYDAY ELECTRONICS  
Due to the demand from students, teachers and hobbyists we have put together a range of articles from past issues of *Everyday Electronics* that will assist those involved with the construction of electronic projects.

The book contains the complete *Project Development for GCSE* series.

**Contents: Features -** First Steps in Project Building; Building with Vero; Project Development for GCSE; Getting your Project Working; Guide to Printed Circuit Boards; Choosing and Using Test Equipment - The Multimeter, The Oscilloscope, P.S.U.s, Logic Probes, Digital Frequency Meters, Signal Generators, etc; **Data -** Circuit Symbols; Component Codes; Resistors; Identifying Components; Capacitors; Actually Doing It - Understanding the Circuit Diagram, Component Codes, Mounting circuit boards and controls, Understanding Capacitors; **Projects -** Lie Detector; Personal Stereo Amplifier; Digital Experiments Unit; Quizmaster, Siren Effects Unit; UV Exposure Unit; Low-cost Capacitance Meter; Personal Radio.  
88 pages (A4 size) **Order code T15** £2.95

## ELECTRONICS TEACH-IN 88/89 - INTRODUCING MICROPROCESSORS (Mike Tooley BA (published by Everyday Electronics))

A complete course that can lead successful readers to the award of a City and Guilds Certificate in Introductory Microprocessors (726/303). The book contains everything you need to know including full details on registering for assessment, etc. Starting with basic terminology, integrated circuits, logic families and numbering systems the text builds in stages, with revision and assessments built in, up to programming, languages, flow charts, etc. The course is ideal for the newcomer to the subject.  
80 pages (A4 size) **Order code T1-88 89** £2.45



# Computers and Computing

## AN INTRODUCTION TO Z80 MACHINE CODE

**R. A. & J. W. Penfold**  
Takes the reader through the basics of microprocessors and machine code programming with no previous knowledge of these being assumed. The Z80 is used in many popular home computers and simple programming examples are given for Z80-based machines including the Sinclair ZX-81 and Spectrum, Memotech and the Amstrad CPC 464. Also applicable to the Amstrad CPC 664 and 6128.  
144 pages **Order code BP152** £2.76

## AN INTRODUCTION TO 68000 ASSEMBLY LANGUAGE

**R. A. & J. W. Penfold**  
Obtain a vast increase in running speed by writing programs for 68000 based micros such as the Commodore Amiga, Atari ST range or Apple Macintosh range etc., in assembly language. It is not as difficult as one might think and this book covers the fundamentals.  
112 pages **Order code BP184** £2.95

## THE ART OF PROGRAMMING THE ZX SPECTRUM

**M. James, B.Sc., M.B.C.S.**  
It is one thing to have learnt how to use all the Spectrum's commands and functions, but a very different one to be able to combine them into programs that do exactly what you want them to. This is just what this book is all about - teaching you the art of effective programming with your Spectrum.  
144 pages **Order code BP119** £2.50

## A Z80 WORKSHOP MANUAL

**E. A. Parr, B.Sc., DC.Eng., M.I.E.E.**  
This book is intended for people who wish to progress beyond the stage of BASIC programming to topics such as machine code and assembly language programming, or need hardware details of a Z80 based computer.  
192 pages **Order code BP112** £3.95

## NEWNES COMPUTER ENGINEER'S POCKETBOOK (Second Edition)

**Michael Tooley**  
An invaluable compendium of facts, figures, circuits and data, indispensable to the designer, student, service engineer and all those interested in computer and microcomputer systems. It will appeal equally to the hardware or software specialist and to the new band of "software engineers". This data is presented in a succinct and rapidly accessible form so that the book can become part of an everyday toolkit.  
205 pages (hard cover) **Order code NE01** £10.95

## UNDERSTANDING PC SPECIFICATIONS

**R. A. Penfold**  
If you require a microcomputer for business applications, or a high quality home computer, an IBM PC or compatible is often the obvious choice. They are competitively priced, and are backed up by an enormous range of applications programs, hardware add-ons, etc. The main difficulty for the uninitiated is deciding on the specification that will best suit his or her needs. PCs range from simple systems of limited capabilities up to complex systems that can happily run applications that would have been considered beyond the abilities of a microcomputer not so long ago. It would be very easy to choose a PC system that is inadequate to run your applications efficiently, or one which goes beyond your needs and consequently represents poor value for money.

This book explains PC specifications in detail, and the subjects covered include the following: Differences between types of PC (XT, AT, 80386, etc); Maths co-processors; Input devices (keyboards, mice, and digitisers); Memory, including both expanded (EMS) and extended RAM; RAM disks and disk caches; Floppy disk drive formats and compatibility; Hard disk drives (including interleave factors and access times); Display adaptors, including all standard PC types (CGA, Hercules, Super VGA, etc); Contains everything you need to know if you can't tell your EMS from your EGA!  
104 pages **Order code BP282** £3.95



# Audio and Music

## PRACTICAL MIDI HANDBOOK

R. A. Penfold

The Musical Instrument Digital Interface (MIDI) is surrounded by a great deal of misunderstanding, and many of the user manuals that accompany MIDI equipment are quite incomprehensible to the reader.

The Practical MIDI Handbook is aimed primarily at musicians, enthusiasts and technicians who want to exploit the vast capabilities of MIDI, but who have no previous knowledge of electronics or computing. The majority of the book is devoted to an explanation of what MIDI can do and how to exploit it to the full, with practical advice on connecting up a MIDI system and getting it to work, as well as deciphering the technical information in those equipment manuals.

128 pages **Order code PC10** £6.95

## PREAMPLIFIER AND FILTER CIRCUITS

R. A. Penfold

This book provides circuits and background information for a range of preamplifiers, plus tone controls, filters, mixers, etc. The use of modern low noise operational amplifiers and a specialist high performance audio preamplifier i.c. results in circuits that have excellent performance, but which are still quite simple. All the circuits featured can be built at quite low cost (just a few pounds in most cases).

The preamplifier circuits featured include:- Microphone preamplifiers (low impedance, high impedance, and

crystal). Magnetic cartridge pick-up preamplifiers with R.I.A.A. equalisation. Crystal/ceramic pick-up preamplifier. Guitar pick-up preamplifier. Tape head preamplifier (for use with compact cassette systems).

Other circuits include:- Audio limiter to prevent overloading of power amplifiers. Passive tone controls. Active tone controls. PA filters (highpass and lowpass). Scratch and rumble filters. Loudness filter. Audio mixers. Volume and balance controls

92 pages **Order code BP309** £3.95

## MUSICAL APPLICATIONS OF THE ATARI ST's

R. A. Penfold

The Atari ST's are now firmly established as *the* computers to use for electronic music applications. The range and sophistication of these applications are much greater than most people may realise, but there are still a lot of misconceptions about just what can and cannot be achieved. This book will help you sort out the fact from the fallacy and to get the most musically from the ST's.

A wide selection of topics are covered, including the internal sound chip; MIDI; applications programs such as sequencing and score writing, etc; simple but useful add-on projects and MIDI programming.

90 pages **Order code BP246** £5.95

## AN INTRODUCTION TO LOUSPEAKERS AND ENCLOSURE DESIGN

V. Capel

This book explores the various features, good points and snags of speaker designs. It examines the whys and wherefores so that the reader can understand the principles involved and so make an informed choice of design, or even design loudspeaker enclosures for him or herself. Crossover units are also explained, the various types, how they work, the distortions they produce and how to avoid them. Finally there is a step-by-step description of the construction of the *Kapellmeister* loudspeaker enclosure.

148 pages **Order code BP256** £2.95

## ACOUSTIC FEEDBACK - HOW TO AVOID IT

Feedback is the bane of all public address systems. While feedback cannot be completely eliminated, many things can be done to reduce it to a level at which it is no longer a problem.

Much of the trouble is often the hall itself, not the equipment, but there is a simple and practical way of greatly improving acoustics. Some microphones are prone to feedback while others are not. Certain loudspeaker systems are much better than others, and the way the units are positioned can produce or reduce feedback. All these matters are fully explored as well as electronic aids such as equalizers, frequency-shifters and notch filters.

The special requirements of live group concerts are considered, and also the related problem of instability that is sometimes encountered with large set-ups. We even take a look at some unsuccessful attempts to cure feedback so as to save readers wasted time and effort duplicating them.

Also included is the circuit and layout of an inexpensive but highly successful twin-notch filter, and how to operate it.

92 pages **Order code BP101** £3.95

COMPUTERS AND MUSIC. See Computers section

# Project Building

## HOW TO GET YOUR ELECTRONIC PROJECTS WORKING

R. A. Penfold

We have all built projects only to find that they did not work correctly, or at all, when first switched on. The aim of this book is to help the reader overcome just these problems by indicating how and where to start looking for many of the common faults that can occur when building up projects.


96 pages **Order code BP110** £2.50

## HOW TO DESIGN AND MAKE YOUR OWN P.C.B.s

R. A. Penfold

Deals with the simple methods of copying printed circuit board designs from magazines and books and covers all aspects of simple p.c.b. construction including photographic methods and designing your own p.c.b.s.

80 pages **Order code BP121** £2.50

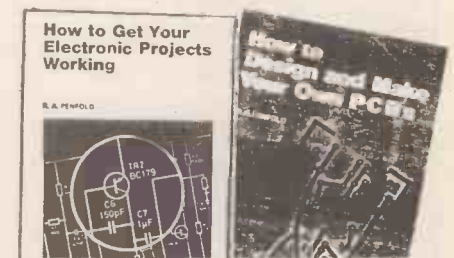

## A BEGINNERS GUIDE TO MODERN ELECTRONIC COMPONENTS

R. A. Penfold

The purpose of this book is to provide practical information to help the reader sort out the bewildering array of components currently on offer. An advanced knowledge of the theory of electronics is not needed, and this book is not intended to be a course in electronic theory. The main aim is to explain the differences between components of the same basic type (e.g. carbon, carbon film, metal film, and wire-wound resistors) so that the right component for a given application can be selected. A wide range of components are included, with the emphasis firmly on those components that are used a great deal in projects for the home constructor.

166 pages **Order code BP285** £3.95

## BEGINNER'S GUIDE TO BUILDING ELECTRONIC PROJECTS

R. A. Penfold

Shows the complete beginner how to tackle the practical side of electronics, so that he or she can confidently build the electronic projects that are regularly featured in magazines and books. Also include examples in the form of simple projects.

112 pages **Order code 227** £1.95

## ELECTRONIC SCIENCE PROJECTS

O. Bishop

These projects range in complexity from a simple colour temperature meter to an infra-red laser. There are novelties such as an electronic clock regulated by a resonating spring, and an oscilloscope with solid-state display. There are scientific measuring instruments such as a pH meter and an electro-cardiometer. All projects have a strong scientific flavour. The way they work, and how to build and use them are fully explained.

144 pages **Temporarily out of print**

## ELECTRONICS SIMPLIFIED - CRYSTAL SET CONSTRUCTION

F. A. Wilson, C.G.I.A., C.Eng., F.I.E.E., F.I.E.R.E., F.B.I.M.

Especially written for those who wish to participate in the intricacies of electronics more through practical construction than by theoretical study. It is designed for all ages upwards from the day one can read intelligently and handle simple tools.

80 pages **Order code BP92** £1.75

# Testing and Test Gear

## TRANSISTOR RADIO FAULT-FINDING CHART

C. E. Miller

Used properly, should enable the reader to trace most common faults reasonably quickly. Across the top of the chart will be found four rectangles containing brief description of these faults, viz - sound weak but undistorted, set dead, sound low or distorted and background noises. One then selects the most appropriate of these and following the arrows, carries out the suggested checks in sequence until the fault is cleared.

Chart **Order code BP70** £0.95

## HOW TO USE OSCILLOSCOPES AND OTHER TEST EQUIPMENT

R. A. Penfold

This book explains the basic function of an oscilloscope, gives a detailed explanation of all the standard controls, and provides advice on buying. A separate chapter deals with using an oscilloscope for fault finding on linear and logic circuits. Plenty of example waveforms help to illustrate the control functions and the effects of various fault conditions. The function and use of various other pieces of test equipment are also covered, including signal generators, logic probes, logic pulsers, and crystal calibrators.

104 pages **Order code BP267** £3.50

# Component Identification

## HOW TO IDENTIFY UNMARKED ICs

K. H. Recorr

Shows the reader how, with just a test-meter to go about recording the particular signature of an unmarked i.c. which should enable the i.c. to then be identified with reference to manufacturers' or other data. An i.c. signature is a specially plotted chart produced by measuring the resistances between all terminal pairs of an i.c.

Chart **Order code BP101** £0.95

## RADIO AND ELECTRONIC COLOUR CODES AND DATA CHART

B. B. Babani

Although this chart was first published in 1971 it provides basic information on many colour codes in use throughout the world, for most radio and electronic components. Includes resistors, capacitors, transformers, field coils, fuses, battery leads, speakers, etc. It is particularly useful for finding the values of old components.

Chart **Order code BP7** £0.95



# Theory and Reference

## ELECTRONIC HOBBYISTS HANDBOOK

R. A. Penfold

Provides an inexpensive single source of easily located information that the amateur electronics enthusiast is likely to need for the day-to-day pursuance of this fascinating hobby. Covers common component colour codes. Details the characteristics and pinouts of many popular semiconductor devices, including various types of logic ICs, operational amplifiers, transistors, FETs, unijunctions, diodes, rectifiers, SCRs, diacs, triacs, regulators and SMDs, etc. Illustrates many useful types of circuits, such as timers and oscillators, audio amplifiers and filters, as well as including a separate section on power supplies. Also contains a multitude of other useful data.

88 pages **Order code BP233** £4.95

## NEWNES ELECTRONICS POCKET BOOK

E. A. Parr

Newnes Electronics Pocket Book has been in print for over twenty years and has covered the development of electronics from valve to semiconductor technology and from transistors to LSI integrated circuits and microprocessors. To keep up to date with the rapidly changing world of electronics, continuous revision has been necessary. This new Fifth Edition takes account of recent changes and includes material suggested by readers of previous editions. New descriptions of op.amp. applications and the design of digital circuits have been added, along with a totally new chapter on computing, plus other revisions throughout.

315 pages (hard cover) **Order code NE62** £10.95

## ELECTRONIC MODULES AND SYSTEMS FOR BEGINNERS

Owen Bishop

This book describes over 60 modular electronic circuits - how they work, how to build them, and how to use them. The modules may be wired together to make hundreds of different electronic systems, both analogue and digital. To show the reader how to begin building systems from modules, a selection of over 25 electronic systems are described in detail, covering such widely differing applications as timing, home security, measurement, audio (including a simple radio receiver), games and remote control.

200 pages **Order code BP266** £3.95

## FROM ATOMS TO AMPERES

F. A. Wilson

Explains in crystal clear terms the absolute fundamentals behind electricity and electronics. Really helps you to discover and understand the subject, perhaps for the first time ever.

Have you ever: Wondered about the true link between electricity and magnetism? Felt you could never understand the work of Einstein, Newton, Boltzmann, Planck and other early scientists? Just accepted that an electron is like a little black ball? Got mixed up with e.m.f. and p.d.? Thought the idea of holes in semiconductors is a bit much?

Then help is at hand with this inexpensive book, in as simple a way as possible and without too much complex mathematics and formulae.

244 pages **Order code BP264** £3.50

## PRACTICAL DIGITAL ELECTRONICS HANDBOOK

Everyday Electronics

The vast majority of modern electronic systems rely heavily on the application of digital electronics, and the *Practical Digital Electronics Handbook* aims to provide readers with a practically based introduction to this subject. The book will prove invaluable to anyone involved with the design, manufacture or servicing of digital circuitry, as well as to those wishing to update their knowledge of modern digital devices and techniques. Contents: Introduction to integrated circuits; basic logic gates; monostable and bistable devices; timers; microprocessors; memories; input and output devices; interfaces; microprocessor buses. Appendix 1: Data. Appendix 2: Digital test gear projects; tools and test equipment; regulated bench power supply; logic pulser; versatile pulse generator; digital IC tester; current tracer; audio logic tracer; RS-232C breakout box; versatile digital counter/frequency meter. Appendix 3: The oscilloscope. Appendix 4: Suggested reading. Appendix 5: Further study.

208 pages **Order code BP100** £6.95

## ELECTRONICS - A "MADE SIMPLE" BOOK

G. H. Olsen

This book provides excellent background reading for our *Introducing Digital Electronics Teach-In Book* and will be of interest to everyone studying electronics. The subject is simply explained and well illustrated and the book assumes only a very basic knowledge of electricity.

330 pages **Order code NE10** £4.95



# Circuits and Design

## PRACTICAL ELECTRONIC BUILDING BLOCKS - BOOK 1

## PRACTICAL ELECTRONIC BUILDING BLOCKS - BOOK 2

**R. A. Penfold**  
These books are designed to aid electronic enthusiasts who like to experiment with circuits and produce their own projects, rather than simply following published project designs.

**BOOK 1** contains: Oscillators - sinewave, triangular, squarewave, sawtooth, and pulse waveform generators operating at audio frequencies. Timers - simple monostable circuits using i.c.s, the 555 and 7555 devices, etc. Miscellaneous-noise generators, rectifiers, comparators and triggers, etc.

**BOOK 2** contains: Amplifiers - low level discrete and op-amp circuits, voltage and buffer amplifiers including d.c. types. Also low-noise audio and voltage controller amplifiers. Filters - high-pass, low-pass, 6, 12, and 24dB per octave types. Miscellaneous - i.c. power amplifiers, mixers, voltage and current regulators, etc.

**BOOK 1** 128 pages Temporarily out of print  
**BOOK 2** 112 pages Order code BPT18 £1.95

## MODERN OPTO DEVICE PROJECTS

**R. A. Penfold**

In recent years, the range of opto devices available to the home constructor has expanded and changed radically. These devices now represent one of the more interesting areas of modern electronics for the hobbyist to experiment in, and many of these have useful practical applications as well. This book provides a number of practical designs which utilize a range of modern opto-electrical devices, including such things as fibre optics, ultra bright i.e.d.s and passive IR detectors etc.

While many of these designs are not in the "dead simple" category, they should be within the capabilities of anyone with a reasonable amount of experience in electronics construction and some of the more simple designs are suitable for beginners.

104 pages Order code BP194 £2.95

## ELECTRONIC ALARM CIRCUITS MANUAL

**R. M. Marston**

One hundred and forty useful alarm circuits, of a variety of types, are shown in this volume. The operating principle of each one is explained in concise but comprehensive terms, and brief construction notes are given where necessary.

Aimed at the practical design engineer, technician and experimenter, as well as the electronics student and amateur.

124 pages Order code NE11 £12.95

## DIGITAL LOGIC GATES AND FLIP-FLOPS

**Ian R. Sinclair**

This book, intended for enthusiasts, students and technicians, seeks to establish a firm foundation in digital electronics by treating the topics of gates and flip-flops thoroughly and from the beginning. This is not a constructor's book in the sense of presenting circuits to build and use, it is for the user who wants to design and troubleshoot digital circuitry with considerably more understanding of principles.

Topics such as Boolean algebra and Karnaugh mapping are explained, demonstrated and used extensively, and more attention is paid to the subject of synchronous counters than to the simple but less important ripple counters.

No background other than a basic knowledge of electronics is assumed, and the more theoretical topics are explained from the beginning, as also are many working practices. The book concludes with an explanation of microprocessor techniques as applied to digital logic.

200 pages Order code PC106 £8.95

## ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS

**Robert Penfold**

Robots and robotics offer one of the most interesting areas for the electronics hobbyist to experiment in. Today the mechanical side of robots is not too difficult, as there are robotics kit and a wide range of mechanical components available. The micro controller is not too much of a problem either, since the software need not be terribly complex and many inexpensive home computers are well suited to the task.

The main stumbling block for most would-be robot builders is the electronics to interface the computer to the motors, and the sensors which provide feedback from the robot to the computer. The purpose of this book is to explain and provide some relatively simple electronic circuits which bridge this gap.

92 pages Order code BP179 £2.95

## ELECTRONIC POWER SUPPLY HANDBOOK

**Ian R. Sinclair**

This book covers the often neglected topic of electronic power supplies. All types of supplies that are used for electronics purposes are covered in detail, starting with cells and batteries and extending by way of rectified supplies and linear stabilisers to modern switch-mode systems, IC switch-mode regulators, DC-DC converters and inverters.

The devices, their operating principles and typical circuits are all dealt with in detail. The action of rectifiers and the reservoir capacitor is emphasised, and the subject of stabilisation is covered. The book includes some useful formulae for assessing the likely hum level of a conventional rectifier reservoir supply.

136 pages Order code PC105 £7.95

## HOW TO USE OP-AMPS

**E. A. Parr**

This book has been written as a designer's guide covering many operational amplifiers, serving both as a source book of circuits and a reference book for design calculations. The approach has been made as non-mathematical as possible.

160 pages Order code BF18 £2.95

## MICRO INTERFACING CIRCUITS - BOOK 1

## MICRO INTERFACING CIRCUITS - BOOK 2

**R. A. Penfold**

Both books include practical circuits together with details of the circuit operation and useful background information. Any special constructional points are covered but p.c.b. layouts and other detailed constructional information are not included.

Book 1 is mainly concerned with getting signals in and out of the computer; Book 2 deals primarily with circuits for practical applications.

**BOOK 1** 112 pages Order code BP180 £2.75  
**BOOK 2** 112 pages Order code BP131 £2.75

## SENSORS AND TRANSDUCERS

**Keith Brindley**

There are a considerable number of transducers. Look through any electronic components catalogue and you'll find a wide variety of types, and each type has many versions. It's not easy to choose a transducer correctly for a particular function. In many specifications, terms and procedures are referred to which might deter you from using one that is, in fact, the best for the job. Yet, opting to use a transducer merely because it is easier to interface into the measuring system is not the answer. A greater knowledge of all types of transducers capable of doing the task is the ideal, and only then can a totally satisfactory decision be made to use one in particular.

179 pages Order code NE17 £14.95

## 50 SIMPLE LED CIRCUITS

**R. N. Soar**

Contains 50 interesting and useful circuits and applications, covering many different branches of electronics, using one of the most inexpensive and freely available components - the light-emitting diode (LED). Also includes circuits for the 707 common anode display.

64 pages Order code BP4 £1.95

**BOOK 2** 50 more i.e.d. circuits Order code BP8 £1.95

# DIRECT BOOK SERVICE

## ORDERING DETAILS

Please state the title and order code clearly, print your name and address and add the required postage to the total order.

Add 75p to your total order for postage and packing (overseas readers add £1.50 for countries in Europe, or add £2.50 for all countries outside Europe, surface mail postage) and send a PO, cheque, international money order, (£ sterling only) made payable to Direct Book Service or credit card details (including the card expiry date), Visa or Mastercard (Access) - minimum credit card order is £5 - quoting your name and address, the order code and quantities required to DIRECT BOOK SERVICE, 33 GRAVEL HILL, WIMBORNE, DORSET BH21 1RW (mail order only).

Although books are normally sent within seven days of receipt of your order, please allow a maximum of 28 days for delivery. Overseas readers allow extra time for surface mail post.

Please check price and availability (see latest issue of Everyday Electronics) before ordering from old lists.

Note - our postage charge is the same for one book or one hundred books!

## MORE BOOKS NEXT MONTH

Direct Book Service is a division of Wimborne Publishing Ltd

# Radio, TV, Satellite

## AN INTRODUCTION TO AMATEUR RADIO

**I. D. Poole**

Amateur radio is a unique and fascinating hobby which has attracted thousands of people since it began at the turn of the century.

This book gives the newcomer a comprehensive and easy to understand guide through the subject so that the reader can gain the most from the hobby. It then remains an essential reference volume to be used time and again. Topics covered include the basic aspects of the hobby, such as operating procedures, jargon and setting up a station. Technical topics covered include propagation, receivers, transmitters and aerials etc.

150 pages Order code BP25 £3.50

## SIMPLE SHORT WAVE RECEIVER CONSTRUCTION

**R. A. Penfold**

Short wave radio is a fascinating hobby, but one that seems to be regarded by many as an expensive pastime these days. In fact it is possible to pursue this hobby for a minimal monetary outlay if you are prepared to undertake a bit of d.i.y., and the receivers described in this book can all be built at low cost. All the sets are easy to construct, full wiring diagrams etc. are provided, and they are suitable for complete beginners. The receivers only require simple aerials, and do not need any complex alignment or other difficult setting up procedures.

The topics covered in this book include: The broadcast bands and their characteristics; The amateur bands and their characteristics; The propagation of radio signals; Simple aerials; Making an earth connection; Short wave crystal set; Simple t.r.f. receivers; Single sideband reception; Direct conversion receiver.

Contains everything you need to know in order to get started in this absorbing hobby.

88 pages Order code BP27 £3.95

## AN INTRODUCTION TO SATELLITE TELEVISION

**F. A. Wilson**

As a definitive introduction to the subject this book is presented on two levels. For the absolute beginner or anyone thinking about purchasing or hiring a satellite TV system, the story is told as simply as such a complex one can be in the main text.

For the professional engineer, electronics enthusiast, student or others with technical backgrounds, there are numerous appendices backing up the main text with additional technical and scientific detail formulae, calculations, tables etc. There is also plenty for the DIY enthusiast with practical advice on choosing and installing the most problematic part of the system - the dish antenna.

104 pages Order code BP19 £5.95

## AN INTRODUCTION TO AMATEUR COMMUNICATIONS SATELLITES

**A. Pickford**

Communications and broadcast satellites are normally inaccessible to individuals unless they are actively involved in their technicalities by working for organisations such as British Telecom, the various space agencies or military bodies, even those who possess a satellite television receiver system do not participate in the technical aspects of these highly technological systems.

There are a large number of amateur communications satellites in orbit around the world, traversing the globe continuously and they can be tracked and their signals received with relatively inexpensive equipment. This equipment can be connected to a home computer such as the BBC Micro or IBM compatible PCs, for the decoding of received signals.

This book describes several currently available systems, their connection to an appropriate computer and how they can be operated with suitable software.

102 pages Order code BP290 £3.95

## AERIAL PROJECTS

**R. A. Penfold**

The subject of aerials is vast but in this book the author has considered practical aerial designs, including active, loop and ferrite aerials which give good performances and are relatively simple and inexpensive to build. The complex theory and mathematics of aerial design have been avoided.

Also included are constructional details of a number of aerial accessories including a pre-selector, attenuator, filters and tuning unit.

96 pages Order code BP10 £2.50

## INTERNATIONAL RADIO STATIONS GUIDE

**P. Shore**

Provides the casual listener, amateur radio DXer and the professional radio monitor with an essential reference work designed to guide him or her around the ever more complex radio bands. This new edition has been completely revised and rewritten and incorporates much more information which is divided into the following sections:

Listening to Short Wave Radio; Choosing a Short Wave Radio Receiver; How to Use the IRSG; Abbreviations; Country Codes; Worldwide Short Wave Radio Stations; European, Middle Eastern and African Long Wave Radio Stations; European, Near and Middle Eastern and African Medium Wave Radio Stations; Canadian Medium Wave Radio Stations; USA Medium Wave Radio Stations; Broadcasts in English; Programmes for DXers and Short Wave Listeners; UK FM Radio Stations; Time Differences From GMT; Wavelength/Frequency Conversion.

226 pages Order code BP253 £5.95



# BABANI BOOKS

We now supply *all* the books published by Bernard Babani (Publishing) Ltd. We have always supplied a selected list of Babani books and you will find many of them described on the previous pages or in next months issue of *Everyday Electronics* (the books with a BP prefix to the order code are Babani books).

Many readers have asked us to also supply various other Babani books, which have a reputation for value for money. Our customers tell us they appreciate our speedy service and low postage charge and they

would like to be able to purchase all the books from us and thus keep the postage charge to an absolute minimum (**75p** for UK p&p no matter how many books you buy). We are pleased to be able to respond; with the aid of Michael Babani (M.D.) we are now able to meet all your requirements for their books. *If it's Babani and in print we can supply it.* Babani presently list over 180 different technical titles those *not* described in detail on the previous *Direct Book Service* pages or in next months issue are listed below:

Code	Title	Price	Code	Title	Price	Code	Title	Price
208	Practical Stereo & Quadrophony Handbook	£0.75	BP138	BASIC & FORTH in Parallel	£1.95	BP245	Digital Audio Projects	£2.95
214	Audio Enthusiast's Handbook	£0.85	BP143	An Introduction to Programming the Atari 600/800XL	£1.95	BP246	Musical Applications of the Atari ST's	£5.95
219	Solid State Novelty Projects	£0.85	BP144	Further Practical Electronics Calculations & Formulae	O.O.P.	BP247	More Advanced MIDI Projects	£2.95
228	A Practical Introduction to Digital ICs	£0.60	BP145	25 Simple Tropical and MW Band Aerials	£1.75	BP248	More Advanced Test Equipment Construction	£3.50
BP28	Resistor Selection Handbook	£2.95	BP148	Computer Terminology Explained	£1.95	BP250	Programming in FORTRAN 77	£4.95
BP37	50 Projects using Relays, SCRs and TRIACS	£2.95	BP149	A Concise Introduction to the Language of BBC Basic	£1.95	BP251	Computer Hobbyists Handbook	£5.95
BP39	50 (FET) Field Effect Transistor Projects	£2.95	BP153	An Introduction to Programming the Amstrad CPC 464 & 664	£2.50	BP258	Learning to Program in C	£4.95
BP44	IC 555 Projects	£2.95	BP154	An Introduction to MSX BASIC	£2.50	BP259	A Concise Introduction to UNIX	£2.95
BP45	Projects in Opto-Electronics	O.O.P.	BP156	An Introduction to QL Machine Code	£2.50	BP260	A Concise Introduction to OS/2	£2.95
BP48	Electronic Projects for Beginners	£1.95	BP157	How to Write ZX Spectrum & Spectrum+ Games Programs	£2.50	BP261	A Concise Introduction to Lotus 1-2-3 (Revised Edition)	£3.95
BP49	Popular Electronic Projects	£2.50	BP158	An Introduction to Programming the Commodore 16 & Plus 4	£2.50	BP262	A Concise Introduction to Wordperfect (Revised Edition)	£3.95
BP56	Electronic Security Devices	£2.50	BP159	How to Write Amstrad CPC464 Games Programs	£2.50	BP263	A Concise Introduction to dBASE	£3.95
BP58	50 Circuits Using 7400 Series IC's	£2.50	BP161	Into the QL Archive	£2.50	BP264	A Concise Advanced User's Guide to MS-DOS	£2.95
BP62	The Simple Electronic Circuits & Components (Elements of Electronics - Book 1)	£3.50	BP162	Counting on QL Abacus	£2.50	BP269	An Introduction to Desktop Publishing	£6.95
BP63	Alternating Current Theory (Elements of Electronics - Book 2)	£3.50	BP171	Easy Add-on Projects for Amstrad CPC 464, 664, 6128 and MSX Computers	£2.95	BP270	A Concise Introduction to Symphony	£3.95
BP64	Semiconductor Technology (Elements of Electronics - Book 3)	£3.50	BP174	More Advanced Electronic Music Projects	£2.95	BP272	Interfacing PC's & Compatibles	£3.95
BP68	Choosing and Using Your Hi-Fi	£1.65	BP175	How to Write Word Game Programs for the Amstrad CPC 464, 664 and 6128	£2.95	BP273	Practical Electronic Sensors	£4.95
BP69	Electronic Games	£1.75	BP182	MIDI Projects	£2.95	BP274	A Concise Introduction to SuperCal5	£3.95
BP74	Electronic Music Projects	£2.50	BP183	An Introduction to CPM	£2.95	BP276	Short Wave Superhet Receiver Construction	£2.95
BP76	Power Supply Projects	£2.50	BP187	A Practical Reference Guide to Word Processing on the Amstrad PCW8256 and PCW8512	£5.95	BP277	High Power Audio Amplifier Construction	£3.95
BP78	Practical Computer Experiments	£1.75	BP189	Using Your Amstrad CPC Disc Drives	£2.95	BP279	A Concise Introduction to Excel	£3.95
BP84	Digital IC Projects	£1.95	BP190	More Advanced Electronic Security Projects	£2.95	BP280	Getting the Most From Your PC's Hard Disc	£3.95
BP86	An Introduction to BASIC Programming Techniques	£1.95	BP191	Simple Application of the Amstrad CPC's for Writers	£2.95	BP283	A Concise Introduction to SmartWare II	£4.95
BP90	Audio Projects	£2.50	BP192	More Advanced Power Supply Projects	£2.95	BP284	Programming in QuickBASIC	£4.95
BP94	Electronic Projects for Cars and Boats	£1.95	BP193	LOGO for Beginners	£2.95	BP285	A Reference Guide to Basic Electronics Terms	£5.95
BP95	Model Railway Projects	£2.95	BP196	BASIC & LOGO in Parallel	£2.95	BP288	A Concise Introduction to Windows 3.0	£3.95
BP97	IC Projects for Beginners	£1.95	BP197	An Introduction to the Amstrad PC's	£2.95	BP291	A Concise Introduction to Ventura	£3.95
BP99	Mini-matrix Board Projects	£2.50	BP198	An Introduction to Antenna Theory	£2.95	BP292	Public Address Loudspeaker Systems	£3.95
BP106	Modern Op-amp Projects	£1.95	BP199	An Introduction to BASIC-2 on the Amstrad PC's	£5.95	BP293	An Introduction to Radio Wave Propagation	£3.95
BP109	The Art of Programming the 1K ZX81	£1.95	BP230	A Concise Introduction to GEM	£2.95	BP294	A Concise Introduction to Microsoft Works	£4.95
BP114	The Art of Programming the 16K ZX81	£2.50	BP243	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 1: Language	£3.95	BP298	A Concise Introduction to the Mac System & Finder	£3.95
BP122	Audio Amplifier Construction	£2.95	BP244	BBC BASIC86 on the Amstrad PC's and IBM Compatibles - Book 2: Graphics and Disk Files	£3.95	BP299	Practical Electronic Filters	£4.95
BP125	25 Simple Amateur Band Aerials	£1.95				BP302	A Concise Users Guide to Lotus 1-2-3 release 3.1	£3.95
BP126	BASIC & PASCAL in Parallel	£1.50				BP303	Understanding PC Software	£2.95
BP128	20 Programs for the ZX Spectrum & 16K ZX81	£1.95				BP304	Projects for Radio Amateurs and S.W.L.s	£3.95
BP129	An Introduction to Programming the ORIC-1	£1.95				BP307	A Concise Introduction to QuarkXPress	£4.95
BP132	25 Simple SW Broadcast Band Aerials	£1.95				BP309	Preamplifier and Filter Circuits	£3.95
BP133	An Introduction to Programming the Dragon 32	£1.95				BP312	An Introduction to Microwaves	£3.95
BP136	25 Simple Indoor and Window Aerials	£1.75				BP313	A Concise Introduction to Sage	£3.95
BP137	BASIC & FORTRAN in Parallel	£1.95				BP314	A Concise Introduction to Quattro Pro	£4.95
						BP318	A Concise User's Guide to MS-DOS 5	£4.95

IF NO PRICE IS SHOWN THE BOOK IS OUT OF PRINT (O.O.P.)  
SEE PREVIOUS PAGE FOR FULL ORDERING DETAILS

## PCB SERVICE

Printed circuit boards for certain EE constructional projects are available from the PCB Service, see list. These are fabricated in glass fibre, and are fully drilled and roller tinned. All prices include VAT and postage and packing. Add £1 per board for airmail outside of Europe. Remittances should be sent to **THE PCB SERVICE, *Everyday Electronics*, 6 Church Street, Wimborne, Dorset BH21 1JH.** Cheques should be crossed and made payable to *Everyday Electronics* (Payment in £ sterling only).

**NOTE:** While 95% of our boards are now held in stock and are dispatched within seven days of receipt of order, please allow a maximum of 28 days for delivery - overseas readers allow extra if ordered by surface mail.  
**Please check price and availability in the latest issue.**

Boards can only be supplied on a payment with order basis.

**SALE!** All p.c.b.s on this page reduced to **1/2 PRICE**

(Just send half the price shown, while stocks last.)  
**PCBS ON OPPOSITE PAGE PRICES AS SHOWN**

PROJECT TITLE	Order Code	Cost
Video Guard Alarm	FEB '87	556 £3.80
Computer Buffer/Interface	MAR '87	560 £3.32
Fridge Alarm	MAY '87	565 £3.00
Mini Disco Light	JUNE '87	567 £3.00
Fermostat	JULY '87	569 £3.34
Monomixer		571 £4.75
Noise Gate	SEP '87	577 £4.41
BBC Sideways RAM/ROM	NOV '87	585 £4.10
Pseudo Echo Unit	DEC '87	586 £4.60
Game Timer	FEB '88	583 £3.55
SOS Alert	MAR '88	595 £3.00
Pipe & Cable Locator	APR '88	598 £3.00

PROJECT TITLE	Order Code	Cost
Door Sentinel	MAY '88	605 £3.00
Multi-Chan Remote Light Dim Relay/Decoder	JUNE '88	601 £4.86
Power Supply		603 £3.00
Video Wiper	JULY '88	612 £6.75
Tea Tune Thermostat	AUG '88	609 £3.00
Time Switch		614 £4.84
Suntan Timer		610 £3.07
Car Alarm		615 £3.12
Eprom Eraser	OCT '88	620 £4.07
Doorbell Delay	NOV '88	616 £3.56
Infra-Red Object Counter (Set)		622/3/4 £9.28
Downbeat Metronome	DEC '88	629 £4.84
EPRM Programmer (On Spec)		630 £8.29
Phasor		631 £5.64
Continuity Tester	FEB '89	619 £2.67
Mini PSU		636 £3.23
Sound-to-Light Interface	MAR '89	637 £6.24
Midi Pedal		639 £7.00
Midi Merge		640 £3.00
Audio Lead Tester		641 £5.77
Light Sentinel: Main Board	APR '89	632 £9.20
Remote Interface (4 bds)		633 £4.59
4-Channel Auto-Fader Interface		642 £6.80
Electron A/D Interface	MAY '89	645 £4.84
Spectrum EPROM Programmer	JUNE '89	628 £7.87
Programmable Pocket Timer	JULY '89	648 £3.82
Electronic Spirit Level	AUG '89	609 £3.85
Distance Recorder		651 £5.23
Xenon Beacon	SEP '89	650 £4.13
Probe Pocket Treasure Finder		653 £4.12
Power Supplies: Fixed Voltage		654 £4.08
Variable Voltage		655 £4.48
Music on Hold	OCT '89	646 £3.85
Power Supplies - 25V 700mA		656 £4.35
30V 1A		657 £4.55
EE Seismograph - Control		658 £4.08
Detector		659 £4.22
Lego/Logo & Spectrum		660 £6.49



# PCB SERVICE

See opposite page for ordering details.

PROJECT TITLE	Order Code	Cost
Wash Pro <b>NOV '89</b>	643	£3.83
Biofeedback Monitor - Front End	661	£4.52
Processor	662	£4.56
Logo/Lego & Spectrum Interface	664	£5.60
EEG Electrode Impedance Meter <b>DEC '89</b>	665	£3.98
Biofeedback Signal Generator <b>JAN '90</b>	666	£4.08
Quick Cap Tester <b>FEB '90</b>	668	£3.92
Weather Stn: Anemom. - Freq./Volt Board	670	£3.94
Optional Display	669	£3.73
Wind Direction	673/674	£4.22
System Power Supply	675	£3.59
Prophet In-Car Ioniser	676	£3.18
Weather Stn: Display Driver <b>MAR '90</b>	672 & 678	£4.22
Display and Sensor	671	£4.47
Fermostat Mk2	677	£4.28
Superhet Broadcast Receiver/Tuner/Amp	679/680	£4.22
Stereo Noise Generator <b>APR '90</b>	681	£4.24
Digital Experimenter's Unit - Pulse Generator	682	£4.46
Power Supply	683	£3.66
Enlarger Timer	684	£4.28
Weather Stn: Rainfall/Sunlight Display	685	£4.27
Rainfall Sen and Sunlight Sen	686/687	£4.16
Amstrad Speech Synthesiser <b>MAY '90</b>	689	£4.68
80 Metre Direct Conversion Radio <b>JUN '90</b>	691	£4.95
Mains Appliance Remote Control <b>JUL '90</b>		
Encoder Board A	694	£6.61
Encoder Board B	695	£4.78
The Tester	696	£4.15
Mains Appliance Remote Control <b>AUG '90</b>		
Mains ON/OFF Decoder	697	£4.55
(5 or more 697's ordered together £3.25 each)		
Simple Metronome	698	£3.94
Hand Tally: Main Bd and Display Bd <b>SEP '90</b>	699, 700	£10.95
Alarm Bell Time-Out	701	£4.10
Mains Appliance Remote Control		
Temperature Controller (p.c.b. only)	702	£5.20
Ghost Waker <b>OCT '90</b>	703	£4.32
Frequency Meter	704	£5.25
Freq. Meter/Tachometer <b>NOV '90</b>	705	£3.98
EE Musketeer (TV/Video/Audio)	706	£5.78
Colour Changing Christmas Lights <b>DEC '90</b>	707	£4.39
Microcontroller Light Sequencer	708/709	£10.90
Versatile Bench Power Supply Unit	710	£4.24
Teach-In '91, Part 1 - L200 Module	711	£3.93
Dual Output Module	712	£4.13
LM723 Module	713	£4.21
Spatial Power Display <b>JAN '91</b>	714	£5.33
Amstrad PCW Sound Generator	715	£5.03
Teach-In '91, Part 2 - G.P. Transistor Amp	717	£3.77
Dual Op.Amp Module	718	£3.83
Intercom (Teach-In '91 Project 2) <b>JAN '91</b>	719	£4.41
Analogic Test Probe	720	£3.24
MARC Phone-In <b>FEB '91</b>	721	£6.87
Teach-In '91 Part 3 - TBA820M Amplifier	723	£4.05
High Quality Power Amp	724	£4.93
Bench Amplifier (Teach-In '91 Project 3)	725	£4.45
Gingernut 80m Receiver <b>FEB '91</b>		
R.F. section (726), Voltage Regulator (727)	726/7/8	£3.06
Audio Amplifier (728)	all 3 together	£8.16
Pocket Tone Dialler <b>MAR '91</b>	729	£4.36
Battery To Mains Inverter	730	£4.97
Simple Basic Alarm	731	£4.50
Car Code Lock (pair)	732a/b	£4.69
Teach-In '91 Part 4 - <b>MAR '91</b>		
Sinusoidal Oscillator	733	£4.39
8038 Oscillator	734	£4.15
Waveform Generator (Teach-In '91 Project 4)	735	£4.72
Humidity Tester <b>APR '91</b>	716	£4.97
Model Train Controller (double-sided)	736	£9.75
Electronic Die (Teach-In '91 Project 5)	737	£4.93
Teach-In '91 Part 5 - Digital Counter Module	738	£4.35
Modular Disco Lighting System <b>MAY '91</b>		
Switched Power Output Module	739	£5.91
Digital LCD Thermostat-Control Board	740	£4.05
-Power/Relay Board	741	£3.76
Pulse Generator (Teach-In '91 Project 6)	742	£4.97
Teach-In '91 Part 6- Timer Module	743	£4.62

PROJECT TITLE	Order Code	Cost
Digilogue Car Tachometer <b>JUN '91</b>	744	£5.63
Modular Disco Lights - Simple Chaser	745	£5.00
Sweeper Module	746	£5.17
Automatic Light Control - PSU Board	747	£4.88
Logic Board	748	£5.17
Radio Receiver (Teach-In '91 Project 7)	749	£4.57
Teach-In '91 Part 7 - R.F. Amplifier Module	750	£4.23
Modular Disco Lights - Masterlink <b>JULY '91</b>	752	£6.36
Ultrasonic Proximity Meter		
Display Unit (753) & Sensor Unit (754)	753/754	£7.06
Disco Lights (Teach-In '91 Project 8)		
PSU and Pre-amplifier	755	£4.54
Low, Mid, High Filter/Triac (set of 3 boards)	756	£11.00
Teach-In '91 Part 8 - Solid State Switch Module	757	£4.24
Mod. Disco Lights - Pattern Gen <b>AUG '91</b>	760	£6.79
Teach-In '91 Part 8-Light Sensitive Switch	761	£4.74
Opto-Link (Teach-In '91 Project 9) - Transmitter	762	£4.85
Receiver	763	£4.88
Portable PESt Scarer	764	£3.77
Capacitance Meter <b>SEP '91</b>	751	£5.17
Modular Disco Lights - Dimmer Interface	765	£8.17
Mod. Disco Lights <b>OCT '91</b>		
VU Sound Module (Double-sided)	767	£8.68
UV Exposure Unit	768	£4.63
PC-Scope Interface - Main Board	769	£6.95
Expansion Plug (Double-sided)	770	£5.96
Mod. Disco Lights <b>NOV '91</b>		
Superchaser (Double-sided)	771	£6.91
Supersweep (Double-sided)	772	£8.26
Bicycle Alarm	773	£5.01
Darts Scorer	774	£7.90
Knockerbox <b>DEC '91</b>	775	£5.35
Signal Generator - Main Board	776	£7.46
PSU	777	£4.73
Mind Machine - Main Board	778	£7.00
Auto Nightlight	779	£5.03
Mind Machine - Programmer Board <b>JAN '92</b>	780	£7.39
Transistor Checker	781	£4.63
Stepping Motor Driver/Interface	782	£10.39
Micro-Sense Alarm	783	£5.42
Telesound <b>FEB '92</b>	784	£4.66
Programmable Timer	785	£4.63
Auto Garage Light <b>MAR '92</b>	786	£6.10
Versatile BBC Computer Interface	787	£11.59
Economy Seven Timer	788	£5.20
Sonic Continuity Tester <b>APR '92</b>	789	£4.79
Telephone Ringer	790	£5.46
Experimental Weighing Scale <b>MAY '92</b>	792	£5.17
12V Drill Charger/PSU (both boards)	793	£5.31
Digital Servo Interface <b>JUNE '92</b>	791	£4.73
Tie Pulsar	794	£5.19
CCD Reverb Unit	795	£6.39
Switch-Mode Power Supply	796	£7.01
UV Exposure Timer <b>JULY '92</b>	797	£5.33
Cricket Game	798	£6.77
Quick Prom	799	£5.61
Gas Alarm <b>Aug '92</b>	800	£5.47
Dual Metronome	801	£6.74


**EE PRINTED CIRCUIT BOARD SERVICE**

Order Code	Project	Quantity	Price
Name.....			
Address.....			
I enclose payment of £ ..... (cheque/PO in £ sterling only to <b>Everyday Electronics</b> Access (MasterCard) or Visa No. Minimum order for credit cards £5			
Signature..... Card Ex. Date.....			
Please supply name and address of card-holder if different from the address shown			

BLOCK CAPITALS PLEASE

# REPORTING AMATEUR RADIO

**Tony Smith G4FAI**

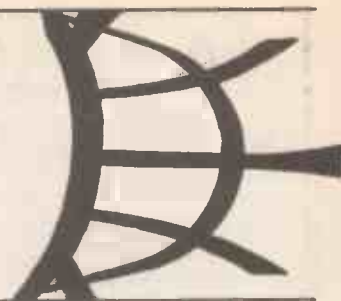

## CLASSES RE-START

A press release received from Huntingdonshire College reminds me that September sees the annual re-commencement of evening classes for the Radio Amateur's examination throughout the UK. This is the traditional means of entry into the hobby as opposed to the recently introduced more informal training arrangements for the new Novice licence.

The classes normally last for one academic year and cover basic radio and electronics theory plus radio regulations relating to the amateur transmitting licence. The classes are sometimes linked with a local radio club which provides practical examples of radio operating and an introduction into the local amateur scene. Morse courses are also available nationwide but are usually separate from the RAE courses.

Full details of examinations and courses near you can be obtained from the Radio Society of Great Britain, Lambda House, Cranborne Road, Potters Bar, Herts EN6 3JE. For the benefit of readers near Huntingdon, the College course there starts on 16th September from 1900 to 2100 hours, and is taught by Barry Street G3MSU. Ring him on 0480 52346, extension 159, for more information.

## VHF PROPAGATION

To those who might be put off by the idea of learning Morse initially, I should mention that the radio amateur "B" licence for v.h.f. and u.h.f. operation does not require a Morse test and that a wide range of activities take place on these frequencies with most not requiring a knowledge of the code.

In my March column I described these activities. I also mentioned that although v.h.f. is conventionally considered to provide "line of sight" communications, "lift" conditions enable stations many hundreds of kilometres away to be heard and worked, often with modest equipment and antennas.

Even in flat conditions v.h.f. signals do, in fact, extend well beyond line of sight due to changes in the radio refractive index of the air relative to height. The densest air, with the highest refractive index, is that nearest the ground. The v.h.f. radio waves bend towards the area of highest refractive index, thus tending to follow the curvature of the earth and to increase the range of a transmitter.

The following simplified notes describe how radio amateurs take advantage of seasonal and other phenomena to make v.h.f. operation a most interesting, and at times quite exciting, area of activity.

## TROPO

A major cause of lift conditions is tropospheric ducting, popularly known as "tropo", which occurs most frequently when atmospheric pressure is high or just beginning to fall. Warm air heated by the ground rises, leaving the air close to the ground cooler than the higher air. Cool air is denser than warm air and the refractive index near the ground becomes higher than normal resulting in increased refraction of radio signals on both the 144MHz (two metre) and 430MHz (70cms u.h.f.) bands. Contacts in these circumstances can cover up to several hundred km.

The same effect arises when a mass of warm air meets a mass of cooled air in a cold front. The warm air rises over the cold air with a defined boundary between the two but this type of temperature inversion may only last a few hours compared with the high pressure lifts which can last for several days.

## SPORADIC E

Also known as Es, sporadic E normally affects signals between 28 and 80MHz but in the summer months can extend rapidly up to 150 MHz, providing exciting conditions in the 50 (6m), 70 (4m) and 144MHz (2m) v.h.f. bands, with contacts possible on occasions up to 2000 kilometres away. This phenomenon occurs when highly ionised clouds form in the E layer of the ionosphere and signals beamed at the cloud are reflected back to earth.

As the clouds are affected by air currents in the upper atmosphere, beam headings may have to be altered and the area to which signals are reflected may change. These "openings" may last anything from a few minutes to a few hours followed by a rapid fade out. Generally speaking, sporadic E occurs on two metres from May to July, with a longer summer season on the lower frequencies.

## AURORA

Auroral propagation occurs when a solar flare releases energy from the sun and charged particles are carried to the earth by the solar wind. These ionise the E layer in the auroral zones around the poles and the aurora created act as reflecting layers for v.h.f. signals aimed at them. Apart from the radio effect, of course, this phenomena is sometimes visible in the UK as the Northern Lights or Aurora Borealis.

In the UK, amateurs aim their beams northwards to make contact with distant stations who are also beaming to the north. Those in northern locations have the greatest success but when there is a major aurora stations in the south of England, and in Europe as far south as Italy, can make exceptionally long distance contacts.

Auroral propagation follows a seasonal pattern, peaking around March and September, although it can occur at any time of the year. It offers the possibility of contacts with stations up to 2,000 km away but it does require some dedication and access to various early warning arrangements to take full advantage of this fascinating activity. Next month I will describe the even more specialised activities of moonbounce and meteor scatter to conclude this roundup of v.h.f. propagation.

## WARM SHACK PREFERRED IN RUSSIA

In a recent letter to *Morsum Magnificat*, the Morse magazine, Andy Troubachov UA3PIP, a Russian amateur, explains why there are so many radio amateurs in the former Soviet Union still using CW (Morse code) often at professional speeds.

"For a long time" he says, "the USSR was a military state. Many special schools were opened where you could be trained (absolutely free) for any technical specialty, including radio operating and Morse code, in preparation for army service.

"All young men reaching 18 years of age had to serve in the army for two years and most of the future soldiers wanted to be radio operators as they much preferred to sit in a warm shack rather than crawl in the snow with a gun! That's why there are so many high-speed CW operators in Russia with rude habits picked up in the army! Nevertheless, many Russians are very skilful on the key.

"Very few amateurs here can speak English but they do want to work foreign stations. This is easy on CW where all you have to know is just a few codes."

The "rude habits" he mentions refer of course to radio operating! He really means bad operating habits such as transmitting on a particular frequency without checking first to see if it is already in use.

In a later letter he mentions the awful quality of some Russian signals which cause interference to other stations on the bands. In the west we have often put up with this in the past, knowing that they did not always have access to decent amateur equipment or components.

This is the first time I have seen a reference to the problem from within the area, however, and interestingly the writer says to foreign stations experiencing such interference, "for goodness sake please tell the offender about it and long-suffering local hams working nearby will bless you!" He even goes on to provide a few appropriate Russian phrases to be transmitted in such circumstances. How times have changed!



# A. C. ELECTRONICS

## SURVEILLANCE? Easy-Build Kits or Built Units.

Microtransmitter, 15mm x 25mm, received on standard VHF radio; kit £5.99, built £9.99 (picks up whispers and transmits up to ½ mile). Telephone transmitter, can be hidden in handset; kit £5.99, built £9.99. "Stinger" shock circuit, can run off 9V battery, unpleasant shock, originally for electric fences etc; kit £11.99, built £19.99. Lots of locksmith tools, transmitters in calculators, plug-in adaptors, alternative technology plans, surveillance kits etc.

Send 4 x 1st class loose stamps for list - Cheque/POs to:

**A.C. ELECTRONICS, Dept. E.E.**  
53, WOODLAND WAY, BURNWOOD,  
STAFFS WS7 5UP.

CREDIT CARD ORDERS: 0543 676477 (24 hours).

MAIL ORDER ONLY.

Devices not licenceable or BT approved.

# Hesing Technology

Cromwell Chambers, 8 St. Johns Street,  
Huntingdon, Cambs. PE18 6DD

Tel: (0480) 433156  
Fax: (0480) 214488

<b>TEST EQUIPMENT</b>	<b>SYSTEM CONSULTANCY</b>
Supply	Replacement Parts
Maintenance	Supply of Service &
Commissioning	Operators Manuals
	Components

Distributors for:  
WAUGH INSTRUMENTS, RAMTEST LTD., KRENZ ELECTRONICS, PANTHER

## VARIABLE VOLTAGE TRANSFORMERS

INPUT 220/240V AC 50/60  
OUTPUT 0-260V

	Price	P&P
0.5KVA 2.5 amp max	£29.00	£4.65
	(£39.54 inc VAT)	
1KVA 5 amp max	£37.40	£6.25
	(£51.29 inc VAT)	
2KVA 10 amp max	£54.00	£7.80
	(£72.62 inc VAT)	
3KVA 15 amp max	£71.50	£7.80
	(£93.18 inc VAT)	
5KVA 25 amp max	£126.50	
	(Plus Carriage)	

Buy direct from the Importers. Keenest prices in the country

**COMPREHENSIVE RANGE OF TRANSFORMERS-LT-ISOLATION & AUTO**  
(110-240V Auto transfer either cased with American socket and mains lead or open frame type. Available for immediate delivery.

**ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES**

4ft 40 watt	£12.00 (callers only)	(£14.10 inc VAT)
2ft 20 watt	£7.44 + £1.25 p&p	(£10.21 inc VAT)
13in 10 watt	£5.80 + 75p p&p	(£7.70 inc VAT)
12in 8 watt	£4.80 + 75p p&p	(£6.82 inc VAT)
9in 6 watt	£3.96 + 50p p&p	(£5.24 inc VAT)
6in 4 watt	£3.96 + 50p p&p	(£5.24 inc VAT)

**230V AC BALLAST KIT**

For either 6in, 9in or 12in tubes £5.50 + £1.15 p&p (£7.81 inc VAT)  
For 13in tubes £6.00 + £1.35 p&p (€8.64 inc VAT)

**400 WATT UV LAMP**

Only £34.00 + £2.50 p&p £42.89 inc VAT

**175 WATT SELF BALLASTED BLACK LIGHT MERCURY LAMP**

Available with BC or ES fitting. Price inc VAT & p&p and VAT £20.86

## 12V D.C. BILGE PUMPS

Buy direct from the importers  
500 GPH 15ft head 3 amp £16.36  
1750 GPH 15ft head 9 amp £27.41  
PRICES INCLUDE P&P & VAT

## EPROM ERASURE KIT

Build your own EPROM ERASURE for a fraction of the price of a made-up unit kit of parts less case includes 12in 8 watt 2537 Angst Tube Ballast unit, pair of bi-pin leads, neon indicator, on/off switch, safety microswitch and circuit £14.00 + £2.50 p&p (€18.80 inc VAT)

## SUPER HY-LIGHT STROBE KIT

Designed for Osico, Theatrical use etc.  
Approx 18 joules. Adjustable speed £50.00 + £3.00 p&p (€62.28 inc VAT)

Case and reflector £24.00 + £3.00 p&p (€31.73 inc VAT).  
SAE for further details including Hy-Light and industrial Strobe Kits

## SERVICE TRADING CO

57 BRIDGMAN ROAD, CHISWICK, LONDON W4 5BB

081-995 1560

ACCOUNT CUSTOMERS MIN. ORDER £10

Showroom open Monday/Friday

VISA

Ample Parking Space

## "BOFFINS SPECIAL" - UNIQUE OFFER

Surplus Precision Medical Unit, internally in excellent condition. Designed primarily to eject a precise controllable amount of fluid from a medical syringe (letter not supplied). Contains the following removable components: Dual Micro Processor Boards and EPROMS, Escap Precision 12V DC Motor with 300:1 Gear Box and optical encoder coupled to a precision threaded drive mechanism. Mains supply with 6 x 1.5V Ni-Cad A.A. cells back-up. L.C.D. Digital read-out 17mm high with legends Audible warning.

These are sold for the dismantling of the exceptional quality components. Regret no Circuits available. Ridiculously low price: £16.00 + £4.00 p&p (€23.50 incl VAT).

## WIDE RANGE OF XENON FLASHTUBES

Write/Phone your enquiries

**12V D.C. GEARED MOTOR**  
12V D.C. Reversible precision-built Motor Output speeds no load approx 12V-26 rpm; 9V-20 rpm; 6V-12 rpm. Will work at lower voltages and still retain a reasonable torque. Ideal for robotics etc. Size: L 40mm, W 29 mm, H 39mm. Shaft: 3mm dia x 10mm long. Price: £8.00 + 50p p&p (€10.00 inc. VAT)

**TORIN CENTRIFUGAL BLOWER**  
230V AC, 2.800 RPM, 0.9 amp, 130mm diameter, impeller outlet 83 x 37mm, overall size 195 x 160 x 150mm long. Price £17.50 + £2.50 p&p (€23.50 inc. VAT)

## SOLID STATE RELAY

7 amp @ 240V, A.C. when mounted on suitable Heat-sink. Can be driven from T.T.L. or Computer output between 3-10V D.C. Size: 24mm x 17mm x 15mm high. Fixing centres 30mm (TO-3). Price: £3.00 + 40p p&p (€4.00 inc. VAT)

## GEARED MOTORS

71 RPM 20lb inch torque reversible 115V AC input including capacitor and transformer for 240V AC operation. Price inc VAT & p&p £23.50

## SOLID STATE EHT UNIT

Input 230/240V AC, Output approx 15kV. Producing 10mm spark. Built-in 10 sec timer. Easily modified for 20 sec, 30 sec to continuous. Designed for boiler ignition. Dozens of uses in the field of physics and electronics, eg supplying neon or argon tubes etc. Price less case £8.50 + £2.40 p&p (€12.81 inc VAT) NMS

## HEAVY DUTY MOTOR

Crouzet 115V/230V AC heavy duty 17PM motor. Anticlockwise type 82/015. Size 68mm, diameter x 55mm long. Shaft 6mm diameter x 20mm long. Price inc VAT & p&p £18.96.

## RHEOSTAT

50W 2 ohm 5 amp ceramic power rheostat. Price inc VAT & p&p £10.81

## MICROSWITCH

Pye 15 amp changeover lever microswitch, type S171. Brand new, price 5 for £7.05 inc VAT & p&p NMS = NEW MANUF SURPLUS R&T = RECONDITIONED AND TESTED

## WE HAVE THE WIDEST CHOICE OF USED OSCILLOSCOPES IN THE COUNTRY

TEKTRONIX 2445B Four Channel 150MHz	£2000
TEKTRONIX 485 Dual Trace 350MHz Delay Sweep	£800
WAITSU 555711 Four Channel 100MHz Delay Sweep	£700
TEKTRONIX 475 Dual Trace 200MHz Delay Sweep	£550
SCHLUMBERGER/ENERTEC 5218 Three Trace 200MHz Delay Sweep	£550
TEKTRONIX 2225 Dual Trace 50MHz Delay Sweep	£500
TEKTRONIX 465 Dual Trace 100MHz Delay Sweep	£450
TEKTRONIX 56217 Dual Trace 50MHz Delay Sweep	£400
GOLDO 055000 DUAL Trace 40MHz Delay Sweep	£350
TELEQUIPMENT DT75 Dual Trace 50MHz Delay Sweep (with V4 & S2A)	£200
TELEQUIPMENT V3 Differential Amplifier for above	£40
HAMEG 605 Dual Trace 60MHz Delay Sweep	£400
GOLDO 05500 Dual Trace 20MHz	£300
WAITSU 555702 Dual Trace 20MHz	£225
GOLDO 051000 Dual Trace 30MHz	£180
GOLDO 052508 Dual Trace 15MHz	£150
TEKTRONIX 422 Dual Trace 15MHz	£125
FARNELL DT12.5 Dual Trace 12MHz	£125
HITACHI V209 Dual Trace 20MHz (AC/DC Operation)	£400

THIS IS JUST A SAMPLE - MANY OTHERS AVAILABLE

### ELECTRON MICROSCOPES

A.E.I. COBOLITH 500 TRANSMISSION  
I.S.I. SUPER 111A SCANNING

MARCONI 2440 200Hz Microwave Counter	£1500
MARCONI 2510 True RMS Voltmeter	£300
FARNELL SSC1000 Sig Gen 10kHz-1GHz Synthesised	£1750
MARCONI 2019 Sig Gen 80kHz-1040MHz	£1800
MARCONI 2022A Sig Gen 10kHz-1GHz	£1500
FARNELL Synthesised Oscillator (OSC) 0.0001Hz-99.99kHz	£275
MARCONI TF2015 AM/FM 10-520kHz Sig Gen with TF2171	£400
MARCONI TF2015 without Synchroniser TF2171	£280
MARCONI TF2016 AM/FM 10kHz-120MHz with TF2173	£350
MARCONI TF2016 without Synchroniser TF2173	£175
MARCONI TF2356/2357 Level Osc/Meter 20MHz the pair	£950
MARCONI SANDERS Sig Sources Various models Covering 400kHz - 8.5GHz	From £300
RACAL 9009 Mod Meter 10MHz-1.5GHz	£300
RACAL Instrumentation Recorders Store 4D and Store 70	From £500
KETLEYE 224 Programmable Current Source	£1000
FERRORGRAPH TTSZ Recorder Test Set	From £150

FARNELL SSC520 Synthesised Sig Gen 10-520MHz £600  
FARNELL TTS520 Transmitter Test Set consisting of RF/AF counter, RF Mod Meter, RF Power Meter, AF Voltmeter, AF Distortion Meter, AF Synthesizer £600  
SOLD as a Pair for ONLY £1000

### SPECTRUM ANALYSERS

ANRITSU US68B 10kHz-4.4GHz	£4000
ANRITSU MS62B 10kHz-1.700MHz	£2000
HP 141T 8555A & IF Plug-in 10MHz-18GHz	£2500
HP 141T with 8554B & 8552B 500kHz-1250MHz	£1500
HP 140T with 8554A & 8552A 500kHz-1250MHz	£1200
HP 141T with 8556A & 8552B 20Hz-300kHz	£1250

Used Equipment - With 30 days guarantee. Manuals supplied if possible.

This is a VERY SMALL SAMPLE OF STOCK. SAE or telephone for lists. Please check availability before ordering. CARRIAGE all units £18. VAT to be added to total of goods and carriage.

**STEWART OF READING**  
110 WYKHAM ROAD, READING, BERKS RG6 1PL  
Tel: 0734 268041 Fax: 0734 351696 Callers welcome 9am to 5.30pm MON-FRI (UNTIL 8pm THURS)

PHILIPS PM2525 Multi-Function DMM 4.5-5.5 digit with GPIB/IEEE-488	Only £300
THURLBY PL320T GP Bench PSU 0-30V 2 amp twice with GPIB	Only £350
HAND HELD MULTIMETERS 3.5 digit DM105 - 14 ranges DC-2 amp	Only £18
M2355 - 32 ranges AC/DC 10 amps Diode/Transistor Tester, Freq Counter etc	Only £32.50

RACAL/DANA Syn Sig Gen 9048 0.01-104MHz	£500
RACAL/DANA RF Power Meter 9104	£800
RACAL/DANA 202 Logic State Analyser with 68000 Decoder	£500
WAYNE KERR LCR Meter 4210 Accuracy 0.1%	£600
WAYNE KERR LCR Meter 4225 Accuracy 0.25%	£500
AVO AC/DC Breakdown Leakage & Ionisation Tester RM215L2	£600

**MARCONI DIGITAL FREQUENCY METERS**  
Type 2430A 10Hz-90MHz £125  
Type 2431A 10Hz-200MHz £150

**MARCONI UNIVERSAL COUNTER TIMERS**  
Type 2437 DC-100MHz £175  
Type 2438 DC-520MHz £220

THORN PSU 0-40V 0-50 amps Metered	£300
FARNELL PSU H60175 0-60V 0-25 amps Metered	£400
FARNELL PSU L30E 0-30V 0-5 amps Metered	£80
TELEQUIPMENT CT71 Curve Tracer	£250
MARCONI TF2700 Universal LCR Bridge Battery	From £125
MARCONI TF237A Auto Distortion Meter 400Hz/1kHz 0.01%	£175
RACAL 9915 Free Counter 10kHz-520MHz Crystal Over	£150
MANNESMAN TALLY Pixy 3 XY Plotter RS232	£100

**AVO MULTIMETERS**  
Model B or 9 multimeters available: £40 each  
Test Set No.1, BK 950 from £65  
B Mk6 with Carrying Case £90  
B Mk6 with Carrying Case £120  
ALL METERS SUPPLIED WITH BATTERIES AND LEADS

### NEW EQUIPMENT

HAMEG OSCILLOSCOPE HM1005 Triple Trace 100MHz Delay Timebase	£792
HAMEG OSCILLOSCOPE HM604 Dual Trace 60MHz Delay Sweep	£670
HAMEG OSCILLOSCOPE HM205-7 Dual Trace 20MHz Component Tester	£338
HAMEG OSCILLOSCOPE HM205-3 Dual Trace 20MHz Digital Storage	£510

All other models available - all oscilloscopes supplied with 3 probes

**BLACK STAR EQUIPMENT (P&P all units £5)**

APOLLO 10-100MHz Counter Timer Ratio/Period/Time Interval etc	£222
APOLLO 100-100MHz (as above with more functions)	£325
METEOR 100 FREQUENCY COUNTER 100MHz	£280
METEOR 600 FREQUENCY COUNTER 600MHz	£380
METEOR 1000 FREQUENCY COUNTER 1GHz	£178
JUPITER 500 FUNCTION GEN 0.1Hz-500kHz Sine/Sq/Tri	£110
ORION COLOUR BAR GENERATOR PAL/TV/Video	£220


All other Black Star equipment available

OSCILLOSCOPE PROBES Switched X1 X10 P&P £51
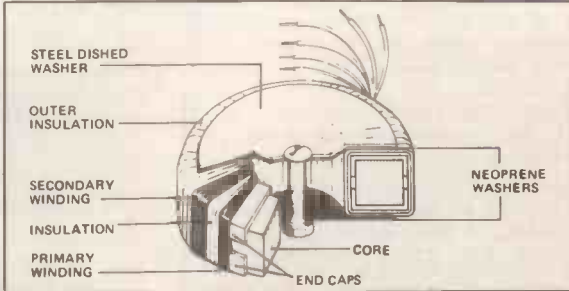
# OLP TRANSFORMERS FROM JAYTEE

The UK Distributor for Standard Toroidal Transformers

- \* 106 types available from stock
- \* Sizes from 15VA to 625VA



Write or phone for free Data Pack

Jaytee Electronic Services  
143 Reculver Road, Beltinge, Herne Bay, Kent CT6 6PL  
Telephone: (0227) 375254



EE reaches twice as many UK readers than any other independent monthly hobby electronics magazine, our audited ABC sales figures prove it. EE has been the leading independent monthly magazine in this market for the last seven years

If you want your advertisements to be seen by the largest readership at the most economical price our classified and semi-display pages offer the best value. The prepaid rate for semi-display space is £8 (+ VAT) per single column centimetre (minimum 2.5cm). The prepaid rate for classified adverts is 30p (+ VAT) per word (minimum 12 words).

All cheques, postal orders, etc., to be made payable to Everyday Electronics. VAT must be added. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Everyday Electronics, 6 Church Street, Wimborne, Dorset BH21 1JH. Tel: (0202) 881749. For rates and information on display advertisements (1/4th page and larger spaces) please contact our Advertisement Manager, Peter Mew on 0255 850596.


## SERVICE MANUALS

Available for Most Equipment  
TV, Video, Audio, Test etc  
Any Age, Make or Model

Write or Phone for Quotation
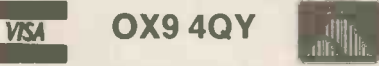
### MAURITRON (EE)

8 Cherry Tree Road  
Chinnor, Oxfordshire



Tel: (0844) 351694  
Fax: (0844) 352554

### N. R. BARDWELL LTD (EE)

200	Signal diodes 1N4148	£1.00
75	Rectifier Diodes 1N4001	£1.00
75	Rectifier Diodes 1N4003	£1.00
50	Rectifier Diodes 1N4007	£1.00
56	Rectifier Diodes 1N5401	£1.00
10	NE555 Timer i.c.s.	£1.00
5	741 Op Amp i.c.s.	£1.00
8	C106D1 400V 6 amp thyristors	£1.00
8	BFY57 Transistors	£1.00
30	BC478 Transistors	£1.00
30	MPSA82 Transistors	£1.00
25	Asstd. high brightness l.e.d.s	£1.00
50	Axial l.e.d.s (Diode package) wide angle red	£1.00
50	Rectangular red l.e.d.s	£1.00
20	Miniature axial l.e.d.s super bright red	£1.00
24	Miniature red l.e.d.s 3mm dia.	£1.00
12	Asstd. seven segment displays	£1.00
4	.43" Com. anode seven segment displays	£1.00
100	22NF 100V radial film capacitors	£1.00
100	33NF 50V radial film capacitors	£1.00
200	Asstd. disc ceramic capacitors	£1.00
80	4U7 16V Radial electrolytics	£1.00
75	4U7 63V Radial electrolytics	£1.00
80	10UF 16V Radial electrolytics	£1.00
50	10UF 50V Radial electrolytics	£1.00
80	22UF 25V Radial electrolytics	£1.00
50	33UF 16V Radial electrolytics	£1.00
60	22UF 50V Radial electrolytics	£1.00
50	47UF 50V Radial electrolytics	£1.00
60	100UF 10V Radial electrolytics	£1.00
60	220UF 16V Radial electrolytics	£1.00
60	470UF 10V Radial electrolytics	£1.00
40	1000UF 10V Radial electrolytics	£1.00
30	Asstd. IF transformers	£1.00
48	Asstd. coil formers	£1.00
100	Asstd. RF chokes	£1.00
30	Asstd. oil sockets up to 40 pin	£1.00
20	Assorted socket/conn's/edge-dill etc.	£1.00
20	1 inch Glass reed switches	£1.00
10	4P 3W MBB min. rotary switches	£1.00
20	Min SP/CO slide switches	£1.00
20	Magnetic ear pips plus lead & plug	£1.00
1	Peltier effect heat pump	£1.95
1	10 watt Stereo amplifier, 4 controls plus data	£2.95
1	10mm Flashing l.e.d. red	£0.75
1	10mm Ultra bright l.e.d. red 300 MCD	£0.60

Prices include VAT, postage £1.00. Stamp for Lists

288 Abbeydale Road, Sheffield S7 1FL  
Phone (0742) 552886. Fax (0742) 500689

### RCS VARIABLE VOLTAGE D.C. BENCH POWER SUPPLY

1 to 24 volts up to 1/2 amp, 1 to 20 volts up to 1 amp, 1 to 16 volts up to 1 1/2 amps d.c. Fully stabilised. Twin panel meters for instant voltage and current readings. Overvoltage protection.  
Fully variable. £45 inc. VAT + Post and insurance £4  
Operates from 240V a.c. Compact Unit. Size 9 x 5 1/2 x 3 in.  
NEW MODEL: Up to 36volts d.c. at 8 amps, 10 amps peak. Fully variable. Twin panel meters. Size 14 1/2 x 11 x 4 1/2 in. £98 inc VAT. Carr. £6.

### RADIO COMPONENT SPECIALISTS

337 WHITEHORSE ROAD, CROYDON  
SURREY, U.K. Tel: 081-684 1665

List. Large SAE. Delivery 7 days. Callers welcome. Closed Wednesday

### NEW VHF MICROTRANSMITTER KIT

Tuneable 80-135MHz, 500 metre range, sensitive electret microphone, high quality PCB.  
SPECIAL OFFER complete kit ONLY £5.95  
Assembled and ready to use £9.95 post free.  
Access/Visa orders telephone 021 411 1821  
Send 2x1st class stamps for Catalogue. Cheques/P.O.s payable to:  
**QUANTEK ELECTRONICS LTD**  
Kits Dept. (EE), 3 Houlday Road, West Heath,  
Birmingham B31 3HL  
SHOP NOW OPEN - CALLERS WELCOME

Looking for a home study course, in the fundamentals of electronics? Whether you are a beginner, or an old hand requiring a refresher, the  
**DIRECT PERSONAL LEARNING** course, could be right for you. Contact:  
**K. Sparrow**  
(Electronic Training Consultant)  
11 Claydon Green, Whitchurch, Bristol, Avon BS14 0NG. Tel: 0275 835669

THE BRITISH AMATEUR ELECTRONICS CLUB exists to help electronics enthusiasts by personal contact and through a quarterly Newsletter. For details, write to the Secretary  
Mr J. S. Hind, 7 Carlyle Road  
West Bridgford, Nottingham NG2 7NS  
Space donated by Everyday Electronics



### Cooke International FOR SALE

Scopes, Sig. Gens, PSU's, Power Meters, DVM's, Oscillators, Attenuators, etc.  
USED TEST EQUIPMENT  
Open Mon-Fri 9am-5pm or Phone  
Copy Service for Workshop Manuals available. Ask for details

**SATURDAYS ONLY**  
**OPEN OUR BARGAIN STORE 10am-4pm**  
**CASH ITEMS TO CLEAR. Tel 0243 545111**  
Contact: Cooke International, Units 4/5, Fordingbridge Site, Main Road, Barnham, Bognor Regis, West Sussex PO22 0EB  
Tel: 0243 545111 Fax: 0243 542457  
Wide range of items available. Send SAE for lists

### Miscellaneous

G.C.S.E. ELECTRONICS KITS at pocket money prices. S.A.E. for FREE catalogue. SIR-KIT ELECTRONICS, 70 Oxford Road, Clacton CO15 3TE.

PROTOTYPE PRINTED CIRCUIT BOARDS one offs and quantities, for details send s.a.e. to B. M. Ansbro, 38 Poynings Drive, Sussex BN3 8GR, or phone Brighton 720203.

STUDY ELECTRONICS on the BBC Micro. An interactive approach to learning. Four program titles available 'Introduction to Electronics Principles', 'Electronics Mathematics', 'Digital Techniques' and now 'Programming for Electronics'. Programs include theory, examples, self test questions, formulae, charts and circuit diagrams. User inputs and calculated outputs, £29.95 each plus £2pp. Cheque or Postal Order to E.P.T. Educational Software, Pump House, Lockram Lane, Witham, Essex CM8 2BJ. Please state BBC 'B' or Master series and disc size.

SATELLITE CHANNEL REPORT. 32 pages documenting transponder video, audio and data on every satellite within your range worldwide, updated monthly. Available as single issue or by subscription. Call: DTL 0491 681502. Fax: 0491 681944

MARCONI AM/FM sig-gen (valve TF995A/S) 1.5-220MHz, ext. modulation input (range approx. 1 mile as transmitter). Precision instrument, £150 including delivery. Tel 0254 247510.

PROBLEMS with your project? Kit assembly, problem investigations, design work undertaken. Hourly rates or fixed prices available. Contact EDS, 205 London Road, Westcliff-on-Sea, Essex. Tel 0702 464398.

**Fuselodge Ltd.** Telephone/Fax  
267 Acton Lane **081-994**  
Chiswick, London W4 5DD **6275**

We stock a large range of Electronic components, semiconductors, switches, resistors, capacitors, transformers, fans, cables, leads, boxes, tools, etc. Power supplies, test equipment. Custom made S.M. power supplies.

Mail order & Credit Cards accepted

PLEASE MENTION  
**EVERYDAY ELECTRONICS**  
WHEN REPLYING TO  
ADVERTISEMENTS

### SOLID STATE RELAYS

Switch 240V a.c. mains from low voltage circuits. Output switches 24-240V a.c. at 4A in free air up to 10A mounted on heatsink.  
Input control is 3-32V d.c. opto isolated. TTL compatible  
Zero crossing switching for noise free electrical operation. No moving parts give trouble free long life operation. 46 x 38 x 14mm. 1/2 in lag connection  
Genuine USA professional product. Also d.c. and high power versions available  
Price £7.34ea. Inc. VAT and postage. Cheque or P.O. Allow 10 days delivery  
SAE for details on this product and a wide range of systems which INTERFACE P.C.'s to drive a.c. and d.c. loads.  
**GEMINI ELECTROSYSTEMS (EE)**  
Bridgeway Business Centre, Martinefield  
Welwyn Garden City, Herts AL7 1JG  
Tel: 070 726 5936. Fax: 070 727 0877.  
Contact Eric Jones

### SUPER FM MICROTRANSMITTERS

HEAR ON ANY FM RADIO FULL INSTRUCTIONS BUILT-IN MICROPHONE LONG RANGE ENCASED EASY TO USE  
HIGHLY SENSITIVE READY TO USE FULLY TUNEABLE 74-115MHz ON/OFF SWITCH MATCHBOX SIZE GUARANTEED  
£9.50 Post free. Cheques, PO's. Tel 0205 362003  
Mr B. Hicks, 24 Brewster Rd, Boston, Lincs PE21 0DY

This 2.5cm space in  
**Everyday Electronics**  
Will ONLY cost you  
**£20 + VAT**

### BTEC ELECTRONICS TECHNICIAN FULL-TIME TRAINING

THOSE ELIGIBLE CAN APPLY FOR E.T. GRANT SUPPORT AN EQUAL OPPORTUNITIES PROGRAMME

O.N.C., O.N.D. and H.N.C.

Next course commences  
**Monday 21st September 1992**  
FULL PROSPECTUS FROM

LONDON ELECTRONICS COLLEGE  
(Dept EE) 20 PENYWERN ROAD  
EARLS COURT, LONDON SW5 9SU  
TEL: 071-373 8721

### SOLAR PANELS

Special offer 12V nom (20V o/c) 80mA. 12" x 6" pre wired Amorphous Silicon panel £4.50 includes P&P. Many other sizes, wind generators and other products.

Orders to (Cat 2 x 1st class stamps)  
**Robert Keys, 4 Glanmor Crescent**  
Newport Gwent NP9 8AX



## MAKE YOUR INTERESTS PAY!

Over the past 100 years more than 10 million students throughout the world have found it worth their while! An ICS home-study course can help you get a better job, make more money and have more fun out of life! ICS has over 100 years experience in home-study courses and is the largest correspondence school in the world. You learn at your own pace, when and where you want under the guidance of expert 'personal' tutors. Find out how we can help YOU. Post or phone today for **FREE INFORMATION** on the course of your choice. (Tick one box only!)

Electronics	<input type="checkbox"/>	TV, Video & Hi-Fi Servicing	<input type="checkbox"/>
Basic Electronic Engineering (City & Guilds)	<input type="checkbox"/>	Refrigeration & Air Conditioning	<input type="checkbox"/>
Electrical Engineering	<input type="checkbox"/>	Car Mechanics	<input type="checkbox"/>
Electrical Contracting/Installation	<input type="checkbox"/>	Computer Programming	<input type="checkbox"/>
GCSE/GCE/SCE over 40 examination subjects to choose from			

Name \_\_\_\_\_ Address \_\_\_\_\_

# ICS

International Correspondence Schools Dept ECS 82  
312/314 High Street, Sutton, Surrey SM1 1PR or 041-221 7373 (24 hours).

### Rechargeable Batteries:

Size AA Pack of 4 - £4.25      Size RX14 Pack of 2 - £4.25  
Size HP2 Pack of 2 - £4.75      Size AAA = HP16 Pack of 4 - £5.00  
Size PP3 - 1 per pack - £5.75

Universal Charger to charge all the above batteries - £5.75  
Nickel Cadmium 5 hour Battery Charger will charge: AAA, AA - 5/7 hours,  
PP3 size - 14/15 hours (cat. no. NC500P) - £6.00

Rechargeable Torch inc. mains adaptor, also charges from car battery, plug and lead included - £9.50

300 M/A Power Supply, output voltage 3, 4.5, 6, 7.5, 9, 12. Plugs into 13amp socket, suitable for calculators, small radios, etc. - £3.75

Mains Power Supply Unit DC output 300M/A regulated output, switchable for 3, 4.5, 6, 7.5, 9, 12V. - £6.25

F.M. Microphone (cordless) transmits signal on 98MHz F.M. inc. batt. - £8.50

A.M. Pocket Radio with wrist strap, inc. batteries - £3.50

Telephone Ext. Leads: 3m - £2.50, 5m - £2.80, 10m - £3.50. 15m - £4.00

Telephone Double Adaptor to run two telephones from one socket - £2.00

Master Telephone Socket - £3.00 Slave/Secondary - £2.00

Baby Night Light Auto On/Off - £4.75

All above inclusive of postage and packing.

## J. ROBINSON (ELECTRONICS)

1 WORTHINGTON DRIVE, SALFORD, MANCHESTER M7 0JE  
Tel: 061-792 2299 Fax: 061-792 2299

### Technical Information Services

76 CHURCH STREET, LARKHALL, LANARKSHIRE, ML9 1HE

Tel. (0698) 884585 Mon-Fri 8.30am - 5.00pm

Tel. (0698) 883334 Outwith business hours

FAX facility available all day on both lines

Write now with an SAE for your

**FREE QUOTE FREE VOUCHERS & FREE CATALOGUE**

Remember, not only do we have EVERY service sheet ever produced, but we also have

## THE WORLDS LARGEST COLLECTION OF SERVICE MANUALS

& WE ARE SOLE SUPPLIERS OF VARIOUS FAULT-FINDING GUIDES REPAIR MANUALS & TECHNICAL MANUALS

CTV, Video, CD, Hi-Fi, Camcorder, Satellites, Computers, Domestic Equip'...etc.

DATA REFERENCE MANUAL "... essential for the serious electrician"  
FREE updating and a 10% discount voucher only £5.95  
Incorporates Unique Model Identification and Chassis Data

### COMPONENTS

Fo: TV ★ Video  
Audio ★ Computer

WE CAN SUPPLY A VAST RANGE OF SPARES for many makes of TV, Video, Computer & Audio Equipment. WRITE (Encl. s.a.e. please) or PHONE FOR A 'PRICE & AVAILABILITY' on your requirements. **0452 526883**

VIDEO BELT KITS	
AMSTRAD VCR4600/4700/5200.....	£3.19
FISHER FVHP905/906/908.....	£3.03
JVC HR3300/3330/3660.....	£3.30
SANYO VTC6500.....	£2.23
SERVICE MANUALS	
BINATONE 019771.....	£6.99
PHILIPS KT4/K40 Chassis.....	£12.50
PHILIPS CM8833 (Mk 1).....	£3.80
SEMICONDUCTORS	
TBA530 1.74 UPC1378H.....	£2.45
TDA1001B 13.86 ZTX650.....	£0.49
OTHER ITEMS	
SHARP RGF281/4 Main belt.....	£1.40
TOSHIBA STU2 Mains transformer.....	£9.99
FIDELITY	
14"116"120" General LOPTX (+ PCB).....	£17.65
AMSTRAD VCR4500/4600 Pinch Roller Mod. Kit.....	£9.48

This is just a small sample of stock. Please send 3 x 18p stamps for our catalogue or request a free copy with first order.

Order by Post or Phone. We accept payment by VISA, ACCESS, DELTA, SWITCH, Cheque or P.O. Post & Packing is £1.20. No VAT to add on.

All items subject to availability. Prices can change without notice.



MARAPET (EEH)  
1 HORNBEAM MEWS  
GLOUCESTER GL2 0UE

### COMPUTER SPARES

AMSTRAD/SINCLAIR		ATARI	
PEG41A (PC1640).....	£30.85	CO25913 DMA (ST).....	£33.24
40010 G-Array.....	£18.86	User Manual (STFM).....	£10.00
PCW 9512 Serv. Manual.....	£14.49	PC9007/H1L3 (ST).....	£2.88
CP464 Serv. Manual.....	£8.67	ROM Basic (XE/L).....	£4.58
AY38912.....	£7.06	THERMISTOR (ST-PSU).....	£1.37
SE09420CAC.....	£14.93	CN765 (ST-PSU).....	£4.42
STK7356.....	£12.49	PC713V (STE-PSU).....	£2.94
TEA2000.....	£4.49	2SC2331 (ST-PSU).....	£1.59
TMS4532-NL4.....	£1.72	COMMODORE	
ULA6C001E.....	£17.61	17.7344MHz Xtal.....	£4.99
ULA7K010/400056.....	£16.72	C64 User Manual.....	£4.39
ZX8302(QL).....	£10.98	C64 User Manual.....	£4.25
ZX8401.....	£7.94	6510 CPU.....	£10.03
Spec. + 2 ROM.....	£16.69	6526 CIA.....	£11.11
Spec. 48K Speaker.....	£1.74	6569 VIC.....	£19.95
Spec. 48K Membrane.....	£4.73	8520 AICA.....	£11.25
+128K Membrane.....	£8.39	8565 VIC.....	£23.96
OL Membrane.....	£8.99	906114-01 PLA.....	£9.24
EPSON.....	£4.06	251641-02 PLA.....	£4.06
C78010B0031 CPU.....	£30.24	M881416-12 DRAM (C16).....	£4.99

### 19" RACK MOUNTING EQUIPMENT CASES

This range of 19" rack cases features satin black finished 16SWG (1.5mm) steel front panels (no fixing holes visible), with the rear box assembly constructed from 20SWG (.9mm) steel. The standard units are 10" (254mm) deep. 19" project cases only 4" (101mm) deep and are available in the following popular sizes:

#### PROJECT CASES

Type	Height	Price
PU1	1 1/2" (44mm)	£18.02
PU2	3 1/2" (89mm)	£20.07
PU3	5 1/2" (133mm)	£22.11
PU4	7" (178mm)	£24.16
PU6	10 1/2" (266mm)	£28.25

#### EQUIPMENT CASES

Type	Height	Price
U1	1 1/2" (44mm)	£22.33
U2	3 1/2" (89mm)	£25.85
U3	5 1/2" (133mm)	£29.38
U4	7" (178mm)	£31.72

Delivery included (UK only).  
All prices include VAT.  
BLANKING PANELS, RACKING CONSOLES and RACK CABINETS are also available.  
Please send SAE for details  
Tel: 0272 373983 for Access/Visa Sales or cheque with order to:



### RACKZ PRODUCTS

PO Box 1402 Mangotsfield, Bristol, England, BS17 3RY



## IF AN ADVERT IS WRONG, WHO PUTS IT RIGHT?

We do. The Advertising Standards Authority ensures advertisements meet with the strict Code of Advertising Practice.

So if you question an advertiser, they have to answer to us.

To find out more about the ASA, please write to Advertising Standards Authority, Department X, Brook House, Torrington Place, London WC1E 7HN.



This space is donated in the interests of high standards in advertisements.



## New for 1992

★ New MOSFET Amplifiers  
improved range of SMOS modules  
30W, 30+30W, 60W, 120W

★ 20 watt Class A Amplifier

★ Low profile PCB Transformers  
a range of encapsulated transformers  
4VA, 6VA, 10VA, 18VA, 24VA, 30VA

Write or phone for data and prices...  
which include details of standard range of toroidal transformers and audio modules.

No price increase for 1992

### Jaytee Electronic Services

143 Reclver Road, Beltinge, Herne Bay, Kent CT6 6PL  
Telephone: (0227) 375254. Fax: (0227) 365104

Carbon Film resistors 1/4W 5% E24 series 0.51 R to 10MΩ	1p
100 off per value - 75p, even hundreds per value totalling 1000	£6.00p
Metal Film resistors 1/4W 10R to 1 MΩ 5% E12 series - 2p, 1% E24 series	3p
Mixed metal/carbon film resistors 1/4W E24 series 1R0 to 10MΩ	1 1/2p
1 watt mixed metal/Carbon Film 5% E12 series 4R7 to 10 Megohms	5p
Linear Carbon pre-sets 100mW and 1/4W 100R to 4M7 E6 series	7p
<b>Miniature polyester capacitors 250V working for vertical mounting</b>	
015, 022, 033, 047, 068-4p, 01, 5p, 0.12, 0.15, 0.22 - 6p, 0.47 - 8p, 0.68 - 8p, 1.0 - 12p	
<b>Mylar (polyester) capacitors 100V working E12 series vertical mounting</b>	
1000p to 8200p - 3p, 01 to 0.68 - 4p, 0.1 - 5p, 0.12, 0.15, 0.22 - 6p, 0.47/50V - 8p	
<b>Submin ceramic plate capacitors 100V wkg vertical mountings. E12 series</b>	
2% 1.8pf to 47pf - 3p, 2% 56pf to 330pf - 4p, 10% 390p-4700p	4p
Disc/plate ceramics 50V E12 series 1P0 to 1000P, E6 Series 1500P to 47000P	2p
<b>Polystyrene capacitors 63V working E12 series long axial wres</b>	
10pf to 820pf - 5p, 1000pf to 10,000pf - 6p, 12, 0000pf	7p
741 Op Amp - 20p, 555 Timer	20p
cmos 4001 - 20p, 4011 - 22p, 4017	40p
<b>ALUMINIUM ELECTROLYTICS (Mfds/Volts)</b>	
1/50, 2.2/50, 4.7/50, 10/25, 10/50	5p
22/16, 22/25, 22/50, 33/16, 47/16, 47/25, 47/50	6p
100/16, 100/25 7p; 100/50 12p; 100/100	14p
220/16 8p; 220/25, 220/50 10p; 470/16, 470/25	11p
1000/25 25p; 1000/35, 2200/25 35p; 4700/25	70p
<b>Submin. tantalum bead electrolytics (Mfds/Volts)</b>	
0.1/35, 0.22/35, 0.47/35, 1.0/35, 3.3/16, 4.7/16	14p
2.2/35, 4.7/25, 4.7/35, 6.8/16 15p; 10/16, 22/6	20p
33/10, 47/6, 22/16 30p; 47/10 35p; 47/16 60p; 47/35	80p
<b>VOLTAGE REGULATORS</b>	
1A + or - 5V, 8V, 12V, 15V, 18V & 24V - 55p, 100mA, 5.8, 12, 15, V +	30p
<b>DIODES (piv/amps)</b>	
75/25mA 1N4148 2p, 800/1A 1N4006 4 1/2p, 400/3A 1N5404 14p, 115/15mA OA91	8p
100/1A 1N4002 3 1/2p, 1000/1A 1N4007 5p, 60/1.5A S1M1 5p, 100/1A bridge	25p
400/1A 1N4004 4p, 1250/1A BY 127 10p, 30/15A OA47	10p
Zener diodes E24 series 3V3 to 33V 400mW - 8p, 1 watt	12p
Battery snaps for PP3 - 6p for PP9	12p
L.E.D.'s 3mm, & 5mm, Red, Green, Yellow - 10p, Grommets 3mm - 2p, 5mm	2p
Red flashing L.E.D.'s require 9-12V supply only	50p
Mains indicator neons with 220k resistor	10p
20mm fuses 100mA to 5A, O. blow 6p, A/surge 10p, Holders, chassis, mounting	6p
High speed pc drill 0.8, 1.0, 1.3, 1.5, 2.0mm - 30p, Machines 12V dc	£7.00
HELPING HANDS 6 ball joints and 2 croc clips to hold awkward jobs	£3.50p
AA/HP7 Nicad rechargeable cells 90p each, Universal charger unit	£6.50p
Glass reed switches with single pole make contacts - 8p, Magnets	12p
0.1" Stripboard 2 1/2" x 1" 9 rows 25 holes - 25p, 3", x 2 1/2" 24 rows 37 holes	70p
Jack plugs 2.5 & 3.5m - 14p; Sockets Panel Mtg, 2.5 & 3.5m	10p
Ear pieces 2.5 & 3.5mm, dynamic - 20p; 3.5mm crystal	50p
<b>TRANSISTORS</b>	
BC107/8/9 - 12p, BC547/8/9 - 8p, BC557/8/9 - 8p, BC182, 182L, BC183, 183L, BC184, 184L, BC212, 212L - 10p,	
BC327, 337, 337L - 12p, BC727, 737 - 12p, BD135/6/7/8/9 - 25p, BCY70 - 18p, BFY50/51/52 - 20p,	
BFX88 - 15p, 2N3055 - 50p, TIP31, 32 - 30p, TIP41, 42 - 40p, BU208A - £1.20, BF195, 197 - 12p	
Ionisers with seven year guarantee, list price £16.95	£12.50

All prices are inclusive of VAT. Postage 30p (free over £5). Lists Free.

**THE CR SUPPLY CO**  
127 Chesterfield Rd., Sheffield S8 0RN  
Tel: 0742 557771 Return posting

## ADVERTISERS INDEX

A.C. ELECTRONICS	541	J. ROBINSON (ELEC)	543
N. R. BARDWELL	542	LASER SCIENCE	478
R. BARTLETT	527	MAGENTA	
BK ELECTRONICS	Cover (iii)	ELECTRONICS	480/481
BLB ELECTRONICS	527	MAILTECH	503
BRIAN J. REED	544	MARAPET	543
BULL ELECTRICAL	Cover (ii)	MAURITRON	542
CAMBRIDGE COMP.		M&B ELECT. SUPPLIES	521
SCIENCE	527	MODERN ELECTRONICS	
CASTLE ENGINEERS	476	MANUAL	530/531
COMPELEC	478	NUMBER ONE SYSTEMS	478
CRICKLEWOOD ELECTRONICS	527	OMNI ELECTRONICS	478
CR SUPPLY COMPANY	544	PICO TECHNOLOGY	476
ESR ELECTRONIC COMP.	482	RACKZ PRODUCTS	543
GREENWELD ELECTRONICS	477	SERVICE TRADING CO	541
HART ELECTRONIC KITS	479	SHERWOOD ELECTRONICS	527
HESING TECHNOLOGY	541	STEWART OF READING	541
ICS	543	SUMA DESIGNS	474
JAYTEE ELECTRONIC SERVICES	541 & 543	TECHNICAL INFO. SERVICES	543
JPG ELECTRONICS	478	TSIEN	491
		TYPESETTING BUREAU	544

## Millions of quality components at lowest ever prices!

Plus Tools, Watches, Fancy Goods, Toys.  
Mail order UK only.

All inclusive prices -

**NO** post, or VAT etc to add on.

Send 34p stamped self addressed label or envelope for catalogue/clearance list.

At least 2,100 offers to amaze you.

**Brian J Reed**

**6 Queensmead Avenue, East Ewell**

**Epsom, Surrey KT17 3EQ**

**Tel: 081-393 9055**

# Typefit

## THE TYPESETTING BUREAU LTD

PC page make-up software and typesetter output bureau

*"For serious document production it knocks other DTP software into the proverbial cocked hat."*

Those are the words of Jim Tyler, an independent journalist after reviewing Typefit for "Micro Computer Mart". His letter to us went on to say:

*"I spent two years editing a magazine, I have been involved in running a DTP bureau and I currently make my living writing classic car restoration manuals for a division of Reed Business International. I would choose Typefit for any of these roles."*

No we did not pay him anything - he did not even get a free copy of our software (Typefit only costs £225 + VAT anyway). And just for the sceptics he is not a personal friend, relative or shareholder in the company.

His sentiments are backed up by our customers, some of which have changed from other well-known DTP packages costing much more - they tell us Typefit is more

versatile and provides them with use of a better range of quality typefaces (230 different fonts).

With Typefit you do your own Typesetting, proof and correct your work, we provide the expensive phototypesetter and fonts to give you top quality 2000 dot per inch bromide output.

Before investing in any other DTP package and especially before spending a small fortune on a specialist typesetting computer or other equipment, please investigate Typefit.

Please send me more information on Typefit

Name.....

Address.....

Post Code.....

Tel:.....EE



# B.K. ELECTRONICS POWER AMPLIFIER MODULES - TURNTABLES - DIMMERS - LOUDSPEAKERS - 19 INCH STEREO RACK AMPLIFIERS

\* PRICES INCLUDE V.A.T. \* PROMPT DELIVERIES \* FRIENDLY SERVICE \* LARGE (A4) S.A.E. 50p STAMPED FOR CATALOGUE \*

## OMP MOS-FET POWER AMPLIFIERS HIGH POWER, TWO CHANNEL 19 INCH RACK

THOUSANDS PURCHASED BY PROFESSIONAL USERS



### THE RENOWNED MXF SERIES OF POWER AMPLIFIERS FOUR MODELS:- MXF200 (100W + 100W) MXF400 (200W + 200W)

MXF600 (300W + 300W) MXF900 (450W + 450W) ALL POWER RATINGS R.M.S. INTO 4 OHMS, BOTH CHANNELS DRIVEN

FEATURES: \* Independent power supplies with two toroidal transformers \* Twin L.E.D. Vu meters \* Level controls \* Illuminated on/off switch \* XLR connectors \* Standard 775mV inputs \* Open and short circuit proof \* Latest Mos-Fets for stress free power delivery into virtually any load \* High slew rate \* Very low distortion \* Aluminium cases \* MXF600 & MXF900 fan cooled with D.C. loudspeaker and thermal protection.

USED THE WORLD OVER IN CLUBS, PUBS, CINEMAS, DISCOS ETC.

SIZES:- MXF200 W19" x H3 1/2" (2U) x D11"  
MXF400 W19" x H5 1/4" (3U) x D12"  
MXF600 W19" x H5 1/4" (3U) x D13"  
MXF900 W19" x H5 1/4" (3U) x D14 1/2"

PRICES:- MXF200 £175.00 MXF400 £233.85  
MXF600 £329.00 MXF900 £449.15  
SPECIALIST CARRIER DEL. £12.50 EACH

## OMP VARISPEED TURNTABLE CHASSIS



\* Manual arm \* Steel chassis \* Electronic speed control 33 & 45 R.P.M. \* Vari pitch control \* High torque servo driven DC motor \* Transit screws \* 12" die cast platter \* Neon strobe \* Calibrated balance weight \* Removable head shell \* 1/2" cartridge fixings \* Cue lever \* 220/240V 50/60Hz \* 390x305mm \* Supplied with mounting cut-out template.

PRICE £61.30 + £3.70 P&P

## OPTIONAL MAGNETIC CARTRIDGES

STANTON AL500mkII GOLDRING G950  
PRICE £16.95 + 50p P&P PRICE £7.15 + 50p P&P

## STEREO DISCO MIXER DJ6500

★ WITH ECHO ★

STEREO DISCO MIXER with 2 x 7 band & R graphic equalisers with bar graph LED Vu meters. MANY OUTSTANDING FEATURES:- including Echo with repeat & speed control, DJ Mic with tone control talk-over switch, 7 Channels with individual faders plus cross fade, Cue headphone Monitor. Useful combination of the following inputs:- 3 turntables (mag), 3 decks, 5 Line for CD, Tape, Video etc.



Price £134.99 + £5.00 P&P

SIZE: 482 x 240 x 120mm

## PIEZO ELECTRIC TWEETERS - MOTOROLA

Join the Piezo revolution! The low dynamic mass (no voice coil) of a Piezo tweeter produces an improved transient response with a lower distortion level than ordinary dynamic tweeters. As a crossover is not required these units can be added to existing speaker systems of up to 100 watts (more if two are put in series). FREE EXPLANATORY LEAFLETS ARE SUPPLIED WITH EACH TWEETER.



TYPE 'A' (KSN1036A) 3" round with protective wire mesh. Ideal for bookshelf and medium sized Hi-Fi speakers. Price £4.90 + 50p P&P.  
TYPE 'B' (KSN1005A) 3 1/2" super horn for general purpose speakers, disco and P.A. systems etc. Price £5.99 + 50p P&P.  
TYPE 'C' (KSN1016A) 2" x 5" wide dispersion horn for quality Hi-Fi systems and quality discos etc. Price £6.99 + 50p P&P.  
TYPE 'D' (KSN1025A) 2" x 6" wide dispersion horn. Upper frequency response retained extending down to mid-range (2KHz). Suitable for high quality Hi-Fi systems and quality discos. Price £9.99 + 50p P&P.  
TYPE 'E' (KSN1038A) 3 1/2" horn tweeter with attractive silver finish trim. Suitable for Hi-Fi monitor systems etc. Price £5.99 + 50p P&P.  
LEVEL CONTROL Combines, on a recessed mounting plate, level control and cabinet input jack socket. 85x85mm. Price £4.10 + 50p P&P.

## OMP LINNET LOUDSPEAKERS

THE VERY BEST IN QUALITY AND VALUE

Made especially to suit today's need for compactness with high output sound levels, finished in hard wearing black vinylite with protective corners, grille and carrying handle. Each unit incorporates a 12" driver plus high frequency horn for a full frequency range of 45Hz-20KHz. Both models are 8 Ohm Impedance. Size: H20" x W15" x D12".

CHOICE OF TWO MODELS

POWER RATINGS QUOTED IN WATTS RMS FOR EACH CABINET


OMP 12-100WATTS (100dB) PRICE £163.50 PER PAIR  
OMP 12-200WATTS (200dB) PRICE £214.55 PER PAIR

SPECIALIST CARRIER DEL. £12.50 PER PAIR


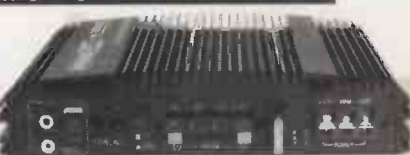
## IN-CAR STEREO BOOSTER AMPS

THREE SUPERB HIGH POWER CAR STEREO BOOSTER AMPLIFIERS



150 WATTS (75 + 75) Stereo, 150W Bridged Mono  
250 WATTS (125 + 125) Stereo, 250W Bridged Mono  
400 WATTS (200 + 200) Stereo, 400W Bridged Mono  
ALL POWERS INTO 4 OHMS  
Features:  
\* Stereo, bridgable mono \* Choice of high & low level inputs \* L & R level controls \* Remote on-off \* Speaker & thermal protection


PRICES: 150W £49.99 250W £99.99  
400W £109.95 P&P £2.00 EACH

POSTAL CHARGES PER ORDER £1.00 MINIMUM. OFFICIAL ORDERS FROM SCHOOLS, COLLEGES, GOVT. BODIES, PLS ETC. PRICES INCLUSIVE OF V.A.T. SALES COUNTER, VISA AND ACCESS ACCEPTED BY POST, PHONE OR FAX.
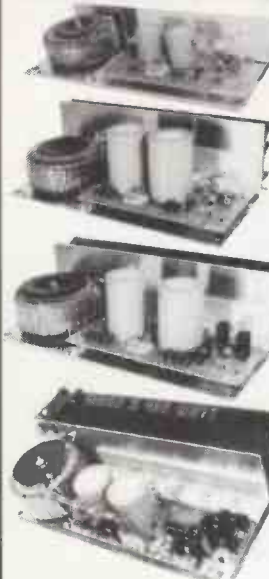
## OMP MOS-FET POWER AMPLIFIER MODULES SUPPLIED READY BUILT AND TESTED.

These modules now enjoy a world-wide reputation for quality, reliability and performance at a realistic price. Four models are available to suit the needs of the professional and hobby market i.e. Industry, Leisure, Instrumental and Hi-Fi etc. When comparing prices, NOTE that all models include toroidal power supply, integral heat sink, glass fibre P.C.B. and drive circuits to power a compatible Vu meter. All models are open and short circuit proof.

THOUSANDS OF MODULES PURCHASED BY PROFESSIONAL USERS



OMP/MF 100 Mos-Fet Output power 110 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 45V/uS, T.H.D. typical 0.002%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 123 x 60mm. PRICE £40.85 + £3.50 P&P

OMP/MF 200 Mos-Fet Output power 200 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 300 x 155 x 100mm. PRICE £64.35 + £4.00 P&P

OMP/MF 300 Mos-Fet Output power 300 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 60V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB. Size 330 x 175 x 100mm. PRICE £81.75 + £5.00 P&P

OMP/MF 450 Mos-Fet Output power 450 watts R.M.S. into 4 ohms, frequency response 1Hz - 100KHz -3dB, Damping Factor >300, Slew Rate 75V/uS, T.H.D. typical 0.001%, Input Sensitivity 500mV, S.N.R. -110 dB, Fan Cooled, D.C. Loudspeaker Protection, 2 Second Anti-Thump Delay. Size 385 x 210 x 105mm. PRICE £132.85 + £5.00 P&P

NOTE: MOS-FET MODULES ARE AVAILABLE IN TWO VERSIONS: STANDARD - INPUT SENS 500mV, BAND WIDTH 100KHz. PEC (PROFESSIONAL EQUIPMENT COMPATIBLE) - INPUT SENS 775mV, BAND WIDTH 50KHz. ORDER STANDARD OR PEC.



Vu METER Compatible with our four amplifiers detailed above. A very accurate visual display employing 11 L.E.D.s (7 green, 4 red) plus an additional on/off indicator. Sophisticated logic control for very fast rise and decay times. Tough moulded plastic case, with acrylic tinted front. Size 84 x 27 x 45mm. PRICE £8.70 + 50p P&P

## LOUDSPEAKERS

LARGE SELECTION OF SPECIALIST LOUDSPEAKERS AVAILABLE, INCLUDING CABINET FITTINGS, SPEAKER GRILLES, CROSS-OVERS AND HIGH POWER, HIGH FREQUENCY BULLETS AND HORNS, LARGE (A4) S.A.E. (50p STAMPED) FOR COMPLETE LIST.

From McKenzie Professional Series  
From McKenzie Studio Series

## McKENZIE:- INSTRUMENTS, P.A., DISCO, ETC

ALL McKENZIE UNITS 8 OHMS IMPEDANCE  
8" 100WATT C8-100GP GEN. PURPOSE, LEAD GUITAR, EXCELLENT MID, DISCO. PRICE £31.45 + £2.00 P&P  
RES. FREQ. 80Hz, FREQ. RESP. TO 7KHz, SENS 98dB.  
10" 100WATT C10-100GP GUITAR, VOICE, KEYBOARD, DISCO, EXCELLENT MID. PRICE £38.89 + £2.50 P&P  
RES. FREQ. 72Hz, FREQ. RESP. TO 6KHz, SENS 97dB.  
10" 200WATT C10-200GP GUITAR, KEYB'D, DISCO, EXCELLENT HIGH POWER MID. PRICE £53.21 + £2.50 P&P  
RES. FREQ. 69Hz, FREQ. RESP. TO 5KHz, SENS 97dB.  
12" 100WATT C12-100GP HIGH POWER GEN. PURPOSE, LEAD GUITAR, DISCO. PRICE £40.35 + £3.50 P&P  
RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 98dB.  
12" 100WATT C12-100TC (TWIN CONE) HIGH POWER, WIDE RESPONSE, P.A., VOICE, DISCO. PRICE £41.39 + £3.50 P&P  
RES. FREQ. 45Hz, FREQ. RESP. TO 12KHz, SENS 97dB.  
12" 200WATT C12-200B HIGH POWER BASS, KEYBOARDS, DISCO, P.A. PRICE £71.91 + £3.50 P&P  
RES. FREQ. 45Hz, FREQ. RESP. TO 5KHz, SENS 99dB.  
12" 300WATT C12-300GP HIGH POWER BASS, LEAD GUITAR, KEYBOARDS, DISCO ETC. PRICE £95.66 + £3.50 P&P  
RES. FREQ. 49Hz, FREQ. RESP. TO 7KHz, SENS 100dB.  
15" 100WATT C15-100BS BASS GUITAR, LOW FREQUENCY, P.A., DISCO. PRICE £59.05 + £4.00 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS 98dB.  
15" 200WATT C15-200BS VERY HIGH POWER BASS. PRICE £80.57 + £4.00 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 3KHz, SENS 98dB.  
15" 250WATT C15-250BS VERY HIGH POWER BASS. PRICE £90.23 + £4.50 P&P  
RES. FREQ. 39Hz, FREQ. RESP. TO 4KHz, SENS 99dB.  
15" 400WATT C15-400BS VERY HIGH POWER, LOW FREQUENCY BASS. PRICE £105.46 + £4.50 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 4 KHz, SENS 100dB.  
18" 500WATT C18-500BS EXTREMELY HIGH POWER, LOW FREQUENCY BASS. PRICE £174.97 + £5.00 P&P  
RES. FREQ. 27Hz, FREQ. RESP. TO 2KHz, SENS. 98dB.

## EARBENDERS:- HI-FI, STUDIO, IN-CAR, ETC

ALL EARBENDERS UNITS 8 OHMS (Except EB-50 & EB10-50 which are dual impedance tapped @ 4 & 8 ohm)  
BASS, SINGLE CONE, HIGH COMPLIANCE, ROLLED SURROUND  
8" 50watt EB8-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £8.90 + £2.00 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 7KHz SENS 97dB.  
10" 50WATT EB10-50 DUAL IMPEDENCE, TAPPED 4/8 OHM BASS, HI-FI, IN-CAR. PRICE £13.65 + £2.50 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 5KHz, SENS. 99dB.  
10" 100WATT EB10-100 BASS, HI-FI, STUDIO. PRICE £30.39 + £3.50 P&P  
RES. FREQ. 35Hz, FREQ. RESP. TO 3KHz, SENS 96dB.  
12" 100WATT EB12-100 BASS, STUDIO, HI-FI, EXCELLENT DISCO. PRICE £42.12 + £3.50 P&P  
RES. FREQ. 26Hz, FREQ. RESP. TO 3 KHz, SENS 93dB.  
FULL RANGE TWIN CONE, HIGH COMPLIANCE, ROLLED SURROUND  
5 1/2" 60WATT EB5-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £9.99 + £1.50 P&P  
RES. FREQ. 63Hz, FREQ. RESP. TO 20KHz, SENS 92dB.  
6 1/2" 60WATT EB6-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £10.99 + 1.50 P&P  
RES. FREQ. 38Hz, FREQ. RESP. TO 20KHz, SENS 94dB.  
8" 60WATT EB8-60TC (TWIN CONE) HI-FI, MULTI-ARRAY DISCO ETC. PRICE £12.99 + £1.50 P&P  
RES. FREQ. 40Hz, FREQ. RESP. TO 18KHz, SENS 99dB.  
10" 60WATT EB10-60TC (TWIN CONE) HI-FI, MULTI ARRAY DISCO ETC. PRICE £16.49 + £2.00 P&P  
RES. FREQ. 35Hz, FREQ. RESP. TO 12KHz, SENS 98dB.

## TRANSMITTER HOBBY KITS

PROVEN TRANSMITTER DESIGNS INCLUDING GLASS FIBRE PRINTED CIRCUIT BOARD AND HIGH QUALITY COMPONENTS COMPLETE WITH CIRCUIT AND INSTRUCTIONS

3W TRANSMITTER 80-108MHz, VARICAP CONTROLLED PROFESSIONAL PERFORMANCE, RANGE UP TO 3 MILES, SIZE 38 x 123mm, SUPPLY 12V @ 0.5AMP. PRICE £14.85 + £1.00 P&P

FM MICRO TRANSMITTER 100-108MHz, VARICAP TUNED, COMPLETE WITH VERY SENS FET MIC, RANGE 100-300m, SIZE 56 x 46mm, SUPPLY 9V BATTERY. PRICE £8.99 + £1.00 P&P



PHOTO: 3W FM TRANSMITTER

# B.K. ELECTRONICS

UNITS 1 & 5 COMET WAY, SOUTHERN-ON-SEA, ESSEX, SS2 6TR.

Tel.: 0702-527572 Fax.: 0702-420243



BUYER'S GUIDE TO ELECTRONIC COMPONENTS 1993

# Maplin



BS 5750  
Part 2 1987  
Level B:  
Quality Assurance  
RS12750

**Order your copy of the New MAPLIN Catalogue on sale 4th September!**  
Pick up a copy from any branch of WHSMITH or from our chain of shops for just £2.95 or  
post this coupon now to receive your copy for just £3.45 inc. p&p. If you live outside the  
U.K. send £5.50 or 14 IRC's for Airmail in Europe, surface mail outside Europe,  
or £10.65 or 27 IRC's for Airmail outside Europe.  
I enclose £3.45/£5.50/£10.65 (delete as applicable).

Name .....

Address .....

Post Code .....

Send to Maplin Electronics,  
P.O. Box 3, Rayleigh,  
Essex, England,  
SS6 8LR.  
EE93

Over 700 product packed pages with  
hundreds of brand new products.  
On sale from September 4th, only £2.95

Available from all branches of WHSMITH and  
Maplin shops nationwide. Hundreds of new  
products at super low prices!





# MARCO TRADING

1992  
SUMMER  
SALE

## SUPPLEMENT

**Free with Everyday Electronics**

(Incorporating East Cornwall Components)

## OUR FANTASTIC SUMMER OFFER

1 × Desolder Stand

1 × 200g Solder  
(60/40 18g or 22g)



WHEN YOU SPEND  
£15.00 YOU CAN  
BUY THESE TWO  
FOR ONLY **£2.99**

(Normally £5.35)


### PLUS - PLUS - PLUS - PLUS - PLUS

Our latest 132-page catalogue (normally £2.00)

**FREE** upon request when you spend £10.00

(NO MINIMUM ORDER, ALL PRICES INC. VAT. P&P £2.25)

# ANOTHER ILLUMINATING OFFER

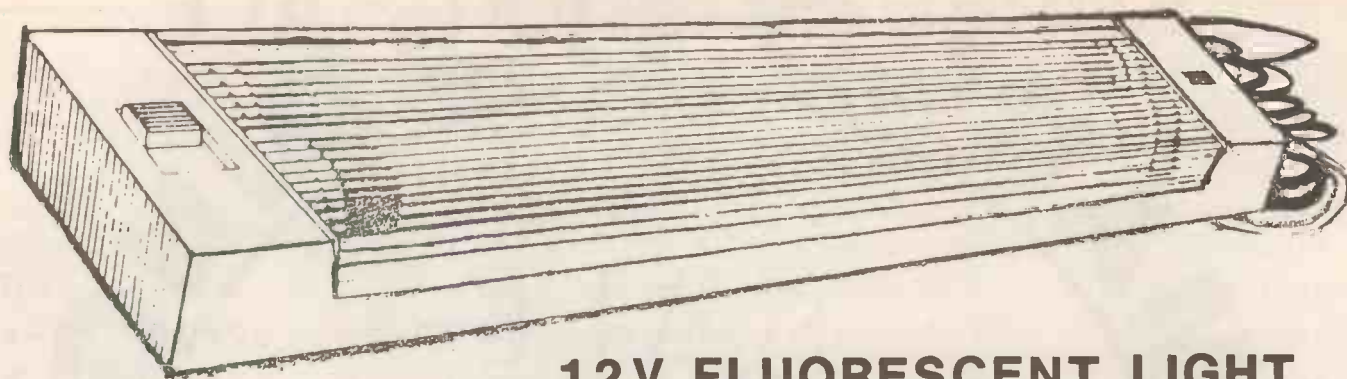

## 12V FLUORESCENT LIGHT

A very attractive **twin** tube fluorescent light complete with two 12Volt 8Watt fluorescent standard type & size tubes.

White plastic case with clear plastic ribbed diffuser and ON/OFF switch.

The light is fitted with approx. 90cms. of twin flex for connection to 12V battery or other 12V power supply. Cable is colour coded for polarity identification.

These lights are ideal for Caravans, Boats, Vans, Camping etc etc.

Overall dimensions: 370 X 65 X 41mm	1+	10+	50+	100+
ORDER CODE: OPTO/TFL12	<b>£5-99</b>	£5-50	£5-00	£4-75

### SINGLE 12Volt Fluorescent Light

Identical to the above unit but SINGLE tube fitting.

ORDER CODE: OPTO/SFL12	<b>£5-50</b>	£5-00	£4-50	£4-25
------------------------	--------------	-------	-------	-------




### SPARE TUBES

Standard 12V fluorescent tube suitable not only for our lights above but for most other makes. Tube length is approx: 300mm incl. pins.

Colour: White.

ORDER CODE: OPTO/TUBE	1+	10+	50+	100+
	<b>£1-50</b>	£1-25	£1-00	85p

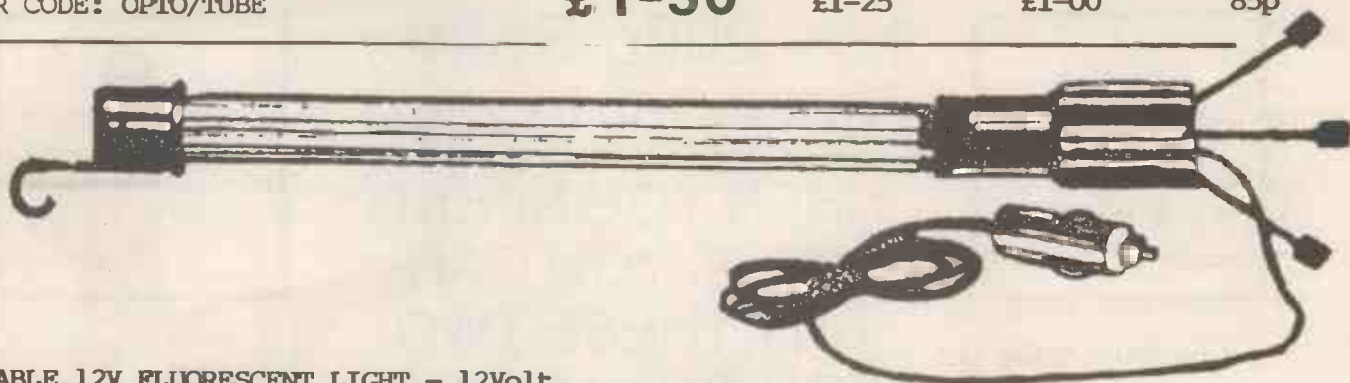

### PORTABLE 12V FLUORESCENT LIGHT - 12Volt

Free-standing or hanging (Hanging hook supplied), with approx. 5 Metres lead terminating in standard car type cigar plug. Ideal for use in Car, Boat, Caravan, Van, Camping etc.

Sealed unit therefor completely weatherproof, they even float on water!!

The fluorescent light is 12Volt & 10Watts.

Overall dimensions: 430 X 30MM dia.	1+	10+	50+	100+
ORDER CODE: OPTO/PEL12	<b>£5-99</b>	£5-50	£5-00	£4-75

**WE ARE THE IMPORTERS OF THESE ITEMS. LARGER QTY. PRICES AVAIL.**

ALL PRICES INCLUDE V.A.T.

ADD £2.25 P&P PER ORDER



# SUPER SOLDER SALE

High grade 60/40 tin/lead alloy solder available in both 18swg & 22swg, in a choice of reel sizes from 18gms to 500gms ( $\frac{1}{2}$ Kg). Manufactured to BS219. Contains 5 cores of type 362 non-corrosive flux. Melting temperature is 188°C. NOW JUST LOOK AT OUR AMAZING PRICES

18swg (1.2mm)

Reel Size	Approx. Length	ORDER CODE	1+	10+	100+
18gms	3 Metres	SOLD/18/3Y	65P	50P	40P
200gms	21 Metres	SOLD/18/200	£2-25	£2-00	£1-60
500gms ( $\frac{1}{2}$ Kg)	52 Metres	SOLD/18/500	£4-75	£4-25	£3-50
22swg (0.71mm)					
200gms	62 Metres	SOLD/22/200	£2-35	£2-10	£1-75
500gms ( $\frac{1}{2}$ Kg)	153 Metres	SOLD/22/500	£4-79	£4-30	£3-60

REMEMBER: BUY 100 REELS OF 18swg 500gms & PAY ONLY £2-98 + VAT PER REEL!

## SOLDERING IRON STAND - Heavy Duty

Suitable for use with ANTEX and most other leading makes of soldering irons. The heavy base makes it very stable. Supplied complete with sponge

ORDER CODE: SOLD/814

PRICE: £2-99



**WHOLESALE  
PRICES AND  
EX-STOCK  
NOW!!**

## EXTERNAL HALOGEN FLOODLIGHT & P.I.R.

A high power security floodlight with built-in PIR detector which reacts to body heat switching on the floodlight whenever somebody approaches within the detection zone. The PIR is adjustable for horizontal and vertical angle and contains a photo detector to prevent daylight operation.

Power: 220-240Vac.

- \* Choice of 200W, 300W or 500W lamp.
- \* Adjustable range up to 15 Metres.
- \* Adjustable 'Time On' 9 secs to 10 mins.
- \* Twilight setting is adjustable.

If you don't state a lamp wattage preference 500Watt will be sent.



**SALE PRICE £29-99 (Incl. Lamp)**

**PROTECT YOUR HOME NOW!**



ALL PRICES INCLUDE V.A.T.

1

ADD £2.25 P & P PER ORDER

# SECURITY SYSTEMS

## LOGIC 4

3 zones each with its own individual function, built in bell timer and keyswitch operation provide effective security with absolute ease of operation. Simple to install & full fitting instructions supplied. Available on its own or as complete Home Alarm Package, see below for special package price.

**ORDER CODE - SEC/LGC4 £39-99**

## OPTIMA XM

Latest updated version of the leading UK selling 'Optima' panel. Rubber keypad, fully selectable 4 digit customer code allows the system to be switched on or off, with the option of omitting zones, quick setting at night and performing simple tests.

Very simple to install supplied complete with full fitting instructions etc. Ideal for either office or home. This panel is also available below as a complete Alarm Package saving even more money.

We have sold hundreds of this truly versatile alarm panel. Our number 1 seller

**ORDER CODE: SEC/OPT/XM £49-00**

## OPTIMA PLUS

As per the Optima XM but also has two communicator outputs thus enabling connection to a British Telecom telephone line. Further technical information is available.


**ORDER CODE SEC/OPT/PLUS £75-00**

## FEATURES





- \* Keyswitch operated security control unit
- \* Selectable part guard zone
- \* Selectable PA and tamper loops.
- \* Adjustable entry-exit timers.
- \* Integral 20 minute bell timer & auto set
- \* Latching strobe output.
- \* Simple 4 terminal wiring to each zone
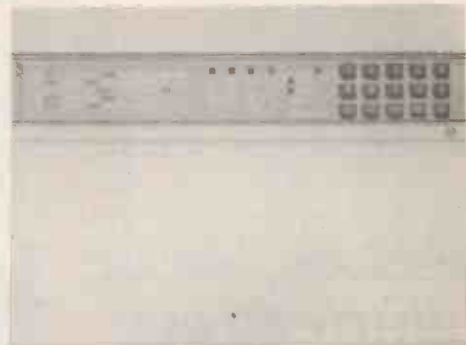
## FEATURES

- \* Keypad operated
- \* 4 zones & PA & tamper
- \* Built in internal sounder
- \* User may omit any zone.
- \* Memory recall for last alarm
- \* Programmable timers including bell cut off.
- \* Quick set feature.
- \* Intelligent auto reset and re-arm.



## PROTECT YOUR HOME NOW!

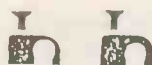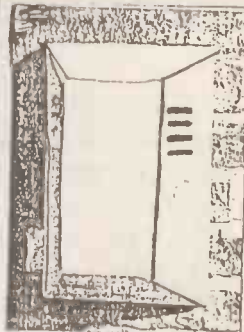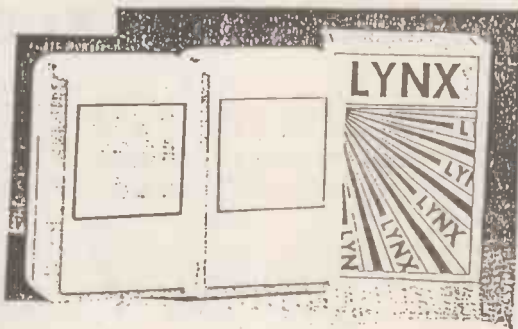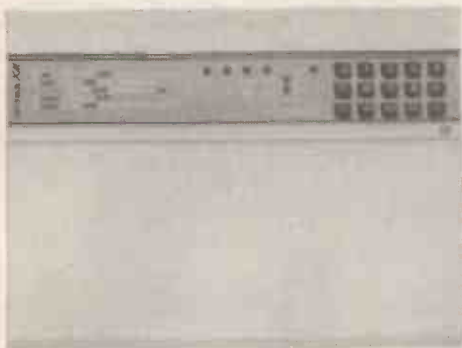

We have sold hundreds of these Home Alarm Packages. They represent truly excellent value for money. It is becoming, sadly, a necessity to protect your home and office with a security system and most important of all, one that can be relied upon! OK, and now for the contents of your package:

- |                              |                          |                        |
|------------------------------|--------------------------|------------------------|
| * OPTIMA XM or LOGIC 4 Panel | * External Bell Box      | * Siren for Bell Box   |
| * 2 X Lynx Internal P.I.R.'s | * 2 X Sets Door Contacts | * 100mts Cable & Clips |

\*\*\*\*\*FULL FITTING INSTRUCTIONS\*\*\*\*\*

**SEC/PACK/LOG £115-00**

**SEC/PACK/OPT £130-00**

\* Should you require extra P.I.R.'s for your installation they are available : ORDER CODE: SEC/LYNX PRICE: £29-00 each

**ALL PRICES INCLUDE V.A.T.**

**2**

**ADD £2.25 P & P PER ORDER**



## COMDEK HOBBY KITS

WE ARE PLEASED TO INTRODUCE A NEW RANGE OF UK DESIGNED KITS. ALL THESE KITS REQUIRE THE USE OF A SOLDERING IRON. ALL CONTAIN FULL ASSEMBLY INSTRUCTIONS AND ALL PCB'S HAVE COMPONENT LOCATION'S MARKED.

THE GOLDEN RULE FOR KIT ASSEMBLY IS SIMPLE....READ THE INSTRUCTIONS 'BEFORE' YOU START..!!!!!!

### TWIN ALTERNATE LED FLASHING UNIT

Two LED's of different colours which flash alternately at a fully adjustable rate operating on an operating voltage from 3V up to 15Volts, at approx 25mA depending on voltage.

Ideal for battery use using either AA, C, D or PP3's. Very simple to construct making it ideal for beginners.

Applications: Burglar deterrent, model construction, name badge, sign, jewellery etc.

ORDER CODE: COM/KIT/01

**£5-99**

### CABLE/METAL DETECTOR

Super device using a ferrite antenna. Detection range up to approx. 6cm. LED indicator. Operates using **2XAA (3V)** Simple to construct.

Applications: Detecting cables in walls, under floors etc.

ORDER CODE: COM/KIT/002

**£5-99**

ALL THE COM/KIT'S ARE DESIGNED IN THE UK AND ALL PCB'S ARE UK MADE & SILK-SCREENED. ALL THESE KITS ARE PACKED IN THE UK!

### FM MINI-TRANSMITTER

A super, very small mini-bug, ideal for baby alarm etc!!! Simply runs off a AA 1.5V battery, which we have had lasting a week or more! Whilst range is difficult to quote because it depends on siting conditions and the quality of the receiver, we have achieved over half a mile. Simple to construct.

ORDER CODE: COM/KIT/003

**£7-50**

(AVAILABLE READY BUILT-SEE BELOW)

ATTENTION: SCHOOLS & EDUCATIONAL ESTABLISHMENTS DISCOUNT AVAILABLE ON 10 KITS OR MORE.

ATTENTION: RETAILERS...WHOLESALE PRICES AVAILABLE WITH YOUR OWN NAME HEADER CARD..CONTACT US NOW!

### FM MINI TRANSMITTER - Made in UK - COMDEK

Very high quality Mini-bug, ideal for baby alarms etc!!

These units are well tried and tested. They may be the best on the market!


Range is difficult to quote because it depends on conditions, but we have achieved almost  $\frac{1}{2}$  a mile.

Simply remove cover, insert AA battery (not included) - and you're ready to go.

Reception can be obtained on any FM radio. Adjustable frequency.

One AA battery can last 5 days continuous!  
 Frequency range.....95-110MHz FM  
 Power.....AA 1.5V Battery  
 Dimensions.....72 x 46 x 22mm

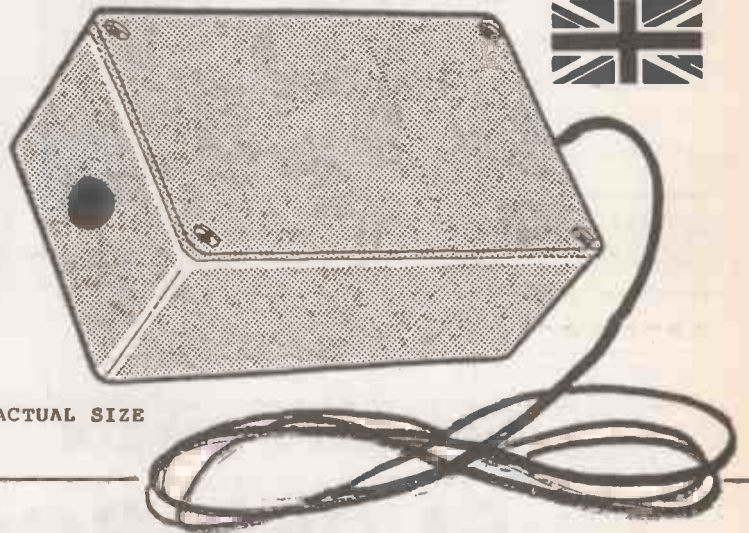ORDER CODE: SEC/FMB1 **£9-99** <sup>1+</sup> **£7-50** <sup>10+</sup>



ACTUAL SIZE

## C.C.T.V.

### C.C.T.V. CAMERA - (USED)

A steel cased, closed-circuit monochrome TV camera. Ideal for internal or outside (using the weatherproof housing) security and for industrial surveillance.

All camera's are supplied with lens fitted - normally 16MM

These units are secondhand the style and overall design may change to the illustration shown. All camera's are thoroughly tested before despatch and should give very long trouble free service. Never mount the camera facing a window or bright light as this wilburn the camera tube. Voltage generally 240V, if lower we will supply a suitable PSU

SEC/CAMERA/USED

PRICE: **£120-00**

### C.C.T.V. MONITOR - (USED)

Steel cased, good quality black & white monitors. Depending on availability we can offer sizes from 9" up to 17". State your preferred size and we will send nearest size available. Voltage: 240V

SEC/MON/USED

PRICE: **£70-00**

### C.C.T.V. CAMERA BRACKET - (NEW)

Quality, British made mounting bracket to suit not only our camera's but any standard CCTV camera.

White, plastic coated steel with standard  $\frac{1}{4}$ "-20 mount. Locking swivel allows camera to be adjusted and fixed in any position.




SEC/CB

PRICE: **£7-75**
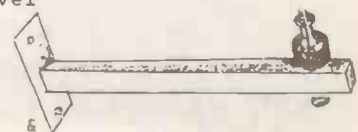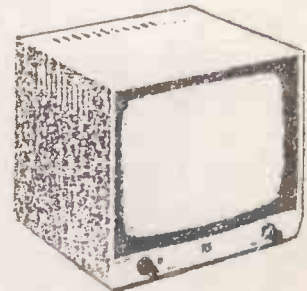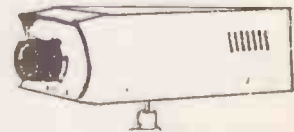
### SPECIAL OFFER

BUY THE COMPLETE PACKAGE ABOVE i.e. 1 x Camera, 1 x Monitor, & 1 x Bracket

AND PAY ONLY **£185-00** (Extra Carr. £10-00)



## BATTERIES & POWER SUPPLIES

### RECHARGEABLE BATTERIES - NI-CADS

At time of printing our Ni-Cads are **Hitachi** with the exception of the PP3. Should the Hitachi be unavailable we will supply a suitable alternative brand. We guarantee our batteries may be charges 1000 times!

Type	Volt	Ah	Order Code	1+	10+
AAA	1.2V	180mAh	BAT/AAA	£1-50	£1-30
AA	1.2V	500mAh	BAT/AA	95p	85p
C	1.2V	1.2Ah	BAT/C	£1-95	£1-80
C	1.2V	2.0Ah	BAT/CI	£3-40	£3-20
D	1.2V	1.2Ah	BAT/D	£2-00	£1-85
D	1.2V	4.0Ah	BAT/DI	£4-75	£4-50
PP3	9V	110mAh	BAT/PP3	£3-90	£3-75



P001

£19-99

PPS1205

Regulated power supply for use with CB rigs, auto equipment. High stability circuitry with high surge current capability. Overload protection. Manufactured according to the requirements of the Electrical Safety Regulations for domestic use.

Input voltage.....220/240Vac 50Hz  
 Output voltage.....13.8Vdc  
 Output current.....5A continuous, 7A max.  
 Stability.....1%  
 Ripple.....25mV  
 Connections.....4mm banana socket (screw terminals)  
 Dims.....195 x 140 x 90mm

**13.8Vdc - 5A  
Regulated output**

### NI-CAD BATTERY CHARGER

Capable of charging all the above sizes i.e.

4 X AAA, AA, C or D sizes  
 2 X PP3

White in colour, free-standing unit with LED 'charging' indicators. A built in tester is provided for 1.5V batteries.


Power: 240Vac

Dims: 180 X 85 X 50mm      1+      10+

BAT/CHARGE/UNIB      £4-99      £4-75

**JUST ARRIVED!!  
Telegquipment DM63  
50MHz Storage  
4 Trace.**

**£225-00!!!**

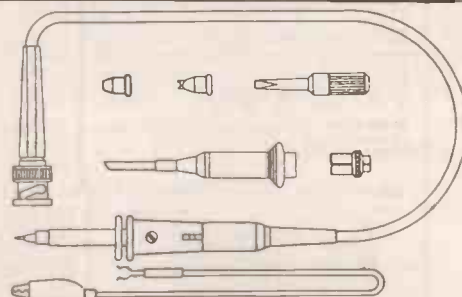

A set of very high quality 'scope probes.

Switched X1 & X10

Supplied in neat storage pack & full instructions.

TEST/BS110

PRICE - £15-50

# Hewlett Packard — 100MHZ SUPER SCOPE SALE

**HP-1740A    100MHZ DUAL TRACE  
DELAY SWEEP ..... £350**

**HP-1744A    100MHZ DUAL TRACE  
DELAY SWEEP & STORAGE,.... £399**

Supplied with full Operating Instructions & Mains leads.

Although secondhand, fully tested before despatch.

If we obtain service manuals they will also be supplied with the scopes Free of Charge.

REMEMBER: OUR PRICES INCLUDE VAT

**BUYING NEW? WHY PAY OVER £600 FOR 50MHZ**



# PROFESSIONAL - METEX DIGITAL MULTIMETERS

 <p><b>Y123HD £83 M4650</b></p> <ul style="list-style-type: none"> <li>★ 4½ digit 15mm LCD display</li> <li>★ 30 ranges including 20A ac/dc</li> <li>★ Frequency counter</li> <li>★ Capacitance ranges with zero adjust</li> <li>★ Transistor and diode test</li> <li>★ Continuity test with LED and buzzer</li> <li>★ Data hold switch</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±0.5%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.05%                  AC current ..... 0-2m-200m-20Aac ±1.0%                  DC current ..... 0-200µ-2m-200m-20Adc ±0.5%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.15%                  Capacitance ..... 0-2000pF-200m-20µF ±2.0%                  Frequency ..... 0-20k-200kHz ±2.0%                  Transistor hFE ..... 0-1000 NPN/PNP                  Dims ..... 178 x 90 x 36mm</p> <p><b>Y122HM £94 M4650B</b></p> <p>As above but with 40 point analog bargraph display</p> 	 <p><b>Y123HB £78 M4630</b></p> <ul style="list-style-type: none"> <li>★ 4½ digit 15mm LCD display</li> <li>★ 30 ranges including 20A ac/dc</li> <li>★ Capacitance ranges with zero adjust</li> <li>★ Transistor and diode test</li> <li>★ Continuity test with LED and buzzer</li> <li>★ Data hold switch</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±0.5%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.05%                  AC current ..... 0-2m-200m-20Aac ±1.0%                  DC current ..... 0-200µ-2m-200m-20Adc ±0.5%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.15%                  Capacitance ..... 0-2m-20m-200m-2µ-20µF ±2.0%                  Transistor hFE ..... 0-1000 NPN/PNP                  Dims ..... 178 x 90 x 36mm</p> <p><b>Y122HK £88 M4630B</b></p> <p>As above but with 40 point analog bargraph display</p> 	 <p><b>Y122HN £57 M818</b></p> <ul style="list-style-type: none"> <li>★ 3½ digit 17mm LCD display</li> <li>★ Autoranging voltage and resistance</li> <li>★ High and low frequency ranges</li> <li>★ True RMS AC voltage and current</li> <li>★ Diode and continuity test</li> <li>★ Data hold switch</li> </ul> <p>AC volts ..... 0-40-400-750Vac ±1.5%                  DC volts ..... 0-400m-4-40-400-1000Vdc ±0.5%                  AC current ..... 0-4m-40m-400m-2-10A ac ±1.5%                  DC current ..... 0-4m-40m-400m-2-10A dc ±1.2%                  Resistance ..... 0-4k-40k-400k-4M-20MΩ ±0.8%                  Frequency ..... 0-4k-40k-400kHz ±2%                  Dims ..... 187 x 87 x 34mm</p> <p><b>Y122HP £65 M818B</b></p> <p>As above but with 40 point analog bargraph display</p> 	 <p><b>Y123HC £56 M3650</b></p> <ul style="list-style-type: none"> <li>★ 3½ digit 17mm LCD display</li> <li>★ 30 ranges including 20A ac/dc</li> <li>★ Frequency counter</li> <li>★ Capacitance test with zero adjust</li> <li>★ Continuity test with LED and buzzer</li> <li>★ Transistor and diode test</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±0.8%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.3%                  AC current ..... 0-2m-200m-20Aac ±1.8%                  DC current ..... 0-200µ-2m-200m-20Adc ±0.5%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.5%                  Capacitance ..... 0-2000pF-200m-20µF ±2.0%                  Frequency ..... 0-20k-200kHz ±2.0%                  Transistor hFE ..... 0-1000 NPN/PNP                  Dims ..... 178 x 90 x 36mm</p> <p><b>Y123HE £66 M3650B</b></p> <p>As above but with 40 point analog bargraph display</p> 
 <p><b>Y123HA £52 M3630</b></p> <ul style="list-style-type: none"> <li>★ 3½ digit 17mm LCD display</li> <li>★ 30 ranges including 20A ac/dc</li> <li>★ Capacitance ranges with zero adjust</li> <li>★ Transistor and diode test</li> <li>★ Continuity test with LED and buzzer</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±0.8%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.3%                  AC current ..... 0-2m-200m-20Aac ±1.0%                  DC current ..... 0-200µ-2m-200m-20Adc ±1.2%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.5%                  Capacitance ..... 0-2m-20m-200m-2µ-20µF ±2.0%                  Transistor hFE ..... 0-1000 NPN/PNP                  Dims ..... 178 x 90 x 36mm</p>	 <p><b>Y122G £46 M3610</b></p> <ul style="list-style-type: none"> <li>★ 3½ digit 17mm LCD display</li> <li>★ 30 ranges including 20A ac/dc</li> <li>★ Transistor and diode test</li> <li>★ Continuity test with LED and buzzer</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±0.8%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.3%                  AC current ..... 0-200µ-2m-20m-200m-2A-20Aac ±1.8%                  DC current ..... 0-200µ-2m-20m-200m-2A-20Adc ±0.5%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.5%                  Transistor hFE ..... 0-1000 NPN/PNP                  Dims ..... 178 x 90 x 36mm</p>	 <p><b>Y131 £55 M3900TD</b></p> <ul style="list-style-type: none"> <li>★ 3½ digit 17mm LCD display</li> <li>★ 20A ac/dc ranges</li> <li>★ Dwell angle display</li> <li>★ Low and high RPM ranges</li> <li>★ Diode and continuity test</li> <li>★ Rugged yellow case</li> </ul> <p>AC volts ..... 0-200m-2-20-200-750Vac ±1.2%                  DC volts ..... 0-200m-2-20-200-1000Vdc ±0.3%                  AC current ..... 0-2-20Aac ±1.8%                  DC current ..... 0-2-20Adc ±1.2%                  Resistance ..... 0-200-2k-20k-200k-2M-20MΩ ±0.5%                  Low tach ..... 4, 5, 6, 8 cylinders - reading RPM ±2%                  High tach ..... 4, 5, 6, 8 cylinders - dwell angle ±2%                  Dims ..... 178 x 90 x 36mm</p>	 <p><b>Y123HF £57 M80</b></p> <ul style="list-style-type: none"> <li>★ Large 3½ digit 21mm LCD display</li> <li>★ Autoranging volts, ohms, amps and frequency count</li> <li>★ 20 Amp ac/dc ranges</li> <li>★ Data hold function</li> <li>★ Ruggedised, weatherproof case</li> <li>★ Diode and continuity test</li> <li>★ Auto polarity and zero</li> </ul> <p>AC volts ..... 0-400-700Vac ±1.8%                  DC volts ..... 0-400m-4-40-400Vdc ±0.5%                  AC current ..... 0-4m-40m-400m-2-20Aac ±1.8%                  DC current ..... 0-4m-40m-400m-2-20Adc ±1.2%                  Resistance ..... 0-4k-40k-400k-4MΩ ±1.2%                  Frequency ..... 0-4k-20kHz ±2.0%                  Dims ..... 182 x 85 x 34mm</p>

ALL OUR METEX METERS ARE SUPPLIED COMPLETE WITH: PP3 Battery, CARRYING CASE, SHROUDED TEST LEADS AND COMPLETE INSTRUCTION MANUAL. All METEX multimeters are built and tested to IEC348



**5 SPEED BENCH DRILL**  
 SAFETY GUARD SUPPLIED

POWER

- Drilling capacity 13mm
- 5 speed
- ¼ HP 240V motor

**£149-99**



DESOLDER TOOL  
 High quality, fitted with Teflon micro nozzle.  
 LENGTH: 190mm  
 Dia: 20mm

PRICE: £2-99


SPARE NOZZLES  
 95p each

**SOLDERING/PYROGRAPHY KIT**



- Suitable for wood, glass, plastics and craftwork
- 240V/40W Soldering Iron; various soldering tips and stand

**£14-99**

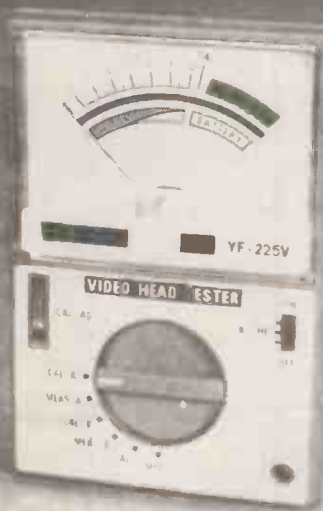

**£37-50**

**VIDEO HEAD TESTER Y139M**  
 A VHS video head tester for determining whether a video head is in good condition by detecting the wear state and displaying it on a meter. Complete with carrying case and leads.  
 Measuring frequency.....1MHz  
 Measuring system.....Bridge measuring Circuit  
 Power.....9Vdc(PP3 Battery)  
 Dims.....142 X 95 X 30mm




**Y122AA £15-75 ALT26**

- 1MΩ**
- ★ 7 ranges including 10Adc
  - ★ 3.5 digit 12mm LCD display
  - ★ Diode test
  - ★ Auto polarity and zero
  - ★ Low battery and over range indication
  - ★ Test leads with fully shrouded 4mm plugs

Battery and instruction manual included.

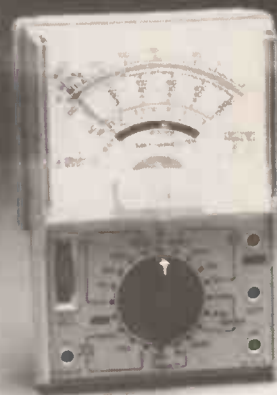AC volts 0-500-Vac ± 1.2%  
 DC volts.....0-20-200Vdc ± 0.7%  
 DC current.....0-10Adc ± 1.5%  
 Resistance.....0-2k-2MΩ ± 0.75%  
 Dims.....148 x 73 x 32mm




**Y105A £14-95 HM102BZ**

- 20kΩ/V**
- ★ 19 ranges (including 10Adc)
  - ★ Fuse and diode protection
  - ★ Battery test
  - ★ Continuity buzzer
  - ★ Audio output test
  - ★ Ohms zero
  - ★ Mirrored scale
  - ★ Leads with 4mm plugs.

Battery and instruction manual included.

AC volts.....0-10-50-250-1000V ± 5%  
 DC volts.....0-2.5-10-50-250-1000V ± 4%  
 DC current.....0-5m-50m-500m-10A ± 5%  
 Resistance.....0-10k-100k-10MΩ ± 4%  
 Battery check.....1.5V75Ω. 9V450Ω  
 Decibels.....-8 to +62dB  
 Audio power.....-8 to +22dB  
 Protection.....fuse and diodes  
 Dims.....135 x 89 x 40mm

**WHOLESALE PRICES ARE AVAILABLE**

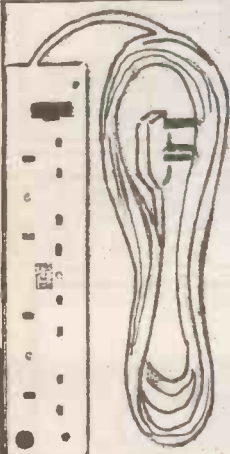

**4-WAY EXTENSION 3MTR LEAD 13A PLUG**

**£5-99**



**SALE PRICE £5-99 Y057 HELPING HANDS**

Top quality "Made in Japan" version with glass 2.5" dia. magnifier in steel frame. (Magnification x 2.5).



**SALE PRICE**

**£19-99**

**MOBILE UHF/VHF/FM ANTENNA WITH BUILT IN AMPLIFIER**

A mesh dish antenna designed primarily for use with caravans, homes, mobile homes, commercial vehicles etc. The dish can be rotated left or right to pick up the best signal which can then be boosted using the built in amplifier and gain control. The amplifier may also be used to boost the signal from an external aerial. The integral LED's indicate which aerial is in use. Supplied complete with mains adaptor enabling aerial to be used on 240Vac.

GAIN.....20dBVHF, 30dBVHF  
 GAIN CONTROL.....0-30dB  
 MAX. OUTPUT LEVEL.....100dBuV  
 POWER.....12 or 24Vdc or 240Vac  
 DIMENSIONS.....230 X 110 X 340mm(approx.)  
**SUPPLIED COMPLETE WITH ADAPTOR FOR 240Vac USE!!!!**



# WIRELESS MIC.

# SALE PRICE

## £155-00



**G200**

**WMS202**

### PROFESSIONAL WIRELESS MICROPHONE SYSTEM

A complete wireless microphone system comprising a G201 receiver with matching G202 microphone, windshield, 1.4m patch lead for connection of receiver to amp/mixer and one pair of racking brackets for the receiver. All packed in a tough vinyl case.

**Receiver:**

Receiving frequencies .....173.8MHz, 174.1MHz, 174.5MHz, 174.8MHz or 175.0MHz  
 Receiving system .....Single super heterodyne conversion FM detector  
 Intermediate frequency .....10.7MHz  
 Antenna impedance .....75Ω  
 RF sensitivity .....0.7μV  
 S/N ratio .....Better than 90dB  
 Squelch threshold .....Adjustable from 10dBμV to 40dBμV  
 Image and spurious rejection .....At least -80dB  
 De-emphasis .....75μs  
 Audio output level .....250mV at 600Ω  
 Audio harmonic distortion .....Less than 0.5%  
 Power .....220/240Vac 50Hz or 12Vdc  
 Dims .....Via external adaptor (not supplied)  
 .....190 x 54 x 200mm

Packed: BOX



**Transmitter:**

Transmitting frequencies .....173.8MHz, 174.1MHz, 174.5MHz, 174.8MHz or 175.0MHz  
 Frequency stability .....0.05%  
 Modulation system .....Crystal controlled FM  
 Harmonic and spurious output power .....Less than -45dB below carrier  
 Pre-emphasis .....50μs  
 Max frequency deviation .....±50kHz  
 Frequency response .....70Hz - 12000Hz  
 Distortion .....Less than 0.5%  
 S/N ratio .....Better than 87dB  
 Ambient temperature range .....0°C - 40°C  
 Operating voltage range .....3.8V to 4.5Vdc



**G203 £59-99 PT300**

**TIE CLIP MIC**

Tie clip wireless mic. High quality electret insert connected to transmitter pack by 1.6m lightweight screened lead. Lightweight transmitter pack (125g with batteries) with belt clip and on/off switch. Powered by 3 x AA batteries (not included). Transmitter specification same as G200 (WMS202)

**LIST PRICE SALE PRICE**

**£45-99**

**£35-99**

**G210**

**WIRELESS MICROPHONE**

2-part wireless microphone system designed for use with video cameras. The hand-held microphone has a high/low power switch to select the transmission range (up to 200ft). The receiver has a video camera mounting shoe, volume control and integral output lead to 3.5mm mono plug. The system allows for greater flexibility with the microphone than can be achieved with a conventional microphone. Complete with vinyl carrying case.

**SAVE £10-00**

Packed: BOX



**LIST PRICE £49-50**

**SALE PRICE £39-50**

**G211**

**WIRELESS MICROPHONE**

A 3-channel 2-part wireless microphone system designed for use with video cameras. The tie-clip mic has a remote belt clip transmitter with on/off switch. The receiver has a hot shoe for mounting on the video camera. The system allows greater mobility with a microphone than can be achieved with the camcorder mic.

**SAVE £10-00**

Packed: BOX



# COMPONENT PACK SALE

Due to popular demand we are pleased to introduce our new range of component packs. Only new unused components are used. Many of the components are to the highest specifications not normally available to the hobby market. The range is being introduced at SALE PRICES so hurry hurry, and take advantage of the low prices before they go up after the sale.

We are currently working on more packs, these will be introduced later this year. "Watch this Space!"

## KNOB PACK

A pack containing an assortment of knobs, both rotary and slider. Some push On and some are screw fixing.

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/018      **SALE PRICE: £4-50**

## SEVEN SEGMENT DISPLAY PACK

A most useful pack of assorted displays, may contain Red, Green, Single digit, double digit large & small. A very mixed pack.

Total Pack Qty: 20 Assorted

ORDER CODE: PACK/019      **SALE PRICE: £3-00**

## 0.5W Resistor Pack

A good assortment of good quality 0.5W Carbon Film resistors mainly 5% tolerance. Many preferred values included. A super buy.

Total Pack Qty: 1000 assorted

ORDER CODE: PACK/020      **SALE PRICE: £2-00**

## ZENER DIODE PACK

A good selection of assorted voltages, from 3.0v to 180v and wattages 250mw to 5Watt.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/024      **SALE PRICE: £2-75**

## VOLTAGE REGULATOR PACK

A most useful pack containing a good selection of assorted fixed and maybe variable regulators. Both +ve and -ve, from 100mA to 5A. Plastic and metal. Excellent value for money.

Total Pack Qty: 25 Assorted.

ORDER CODE: PACK/025      **SALE PRICE: £5-00**

## PLUG TOP MAINS FUSE PACK

A pack of assorted 1" mains fuses. Anything from 3A to 13A. Super value for money.

Total Pack Qty: 40 assorted

ORDER CODE: PACK/029      **SALE PRICE: £4-25**

## SLIDER POT PACK

A pack of metal and plastic mono and stereo sliders, Log and Lin. Values may range from 250 ohms to 1Meg

Total Pack Qty: 25pcs

ORDER CODE: PACK/030      **SALE PRICE: £2-50**

## TUBULAR CERAMIC PACK

A good mixture of capacitors, anything from 1pF up to 10,000 pF. Radial leads ideal for PCB mounting.

Total Pack Qty: 100pcs

ORDER CODE: PACK/031      **SALE PRICE: £1-50**

## TUNGSTEN DRILL BIT PACK

A mixed pack of metric solid tungsten carbide drill bits suitable for drilling glass fibre based pcb's and general hobby use.

Original price was £4-20 each bit!!

Mixed sizes, anything from 0.4mm up to 3.0mm.

Total Pack Qty: 10 pcs

ORDER CODE: PACK/033      **SALE PRICE: £3-50**

## ELECTROLYTIC PACK

A good assortment of both axial & radial capacitors. Some radial's are already pre-cropped for PCB mounting. These packs contain a good selection of voltages from 10V to 1000V and values anything from 1.0uF to 1000uF. This pack is excellent value for money.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/021      **SALE PRICE: £2-50**

## DISC CERAMIC PACK

A super selection of assorted values and voltages. Many popular values are included. Voltages, anything from 5 to 1KV, Values, anything from 1.0pF to 0.1uF. Great value for money.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/022      **SALE PRICE: £1-50**

## POLYSTYRENE PACK

A very useful range of assorted values and voltages of polystyrene capacitors. Many preferred values included. Values range from 10pF to 0.01uF, and voltages up to 400V.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/023      **SALE PRICE: £1-50**

## BRIDGE RECTIFIER PACK

A very mixed pack, excellent value for money. May contain voltages from 50 to 1000v and up to 10 Amps.

Total Pack Qty: 25pcs

ORDER CODE: PACK/026      **SALE PRICE: £5-50**

## CABLE TIE PACK

A mixed pack of assorted length cable ties and maybe black ones.

Total Pack Qty: 100pcs

ORDER CODE: PACK/027      **SALE PRICE: £2-00**

## HEATSHRINK PACK

A super pack, very high quality heatshrink sleeving. Much of it is British made.

A very good assortment of both colours and sizes.

Total Pack Qty: 10 Lengths approx 12" in length.

ORDER CODE: PACK/028      **SALE PRICE: £1-25**

## — ALL PRICES INCLUDE VAT —

## 500V SINGLE LAYER-CERAMIC PACK

A useful assorted pack of these very high quality capacitors. Very small, 8-16mm dia. Normal price over 50p each! Super value.

Total Pack Qty: 50pcs

ORDER CODE: PACK/032      **SALE PRICE: £2-00**

## CALCULATOR PACK

A mixed pack of calculators! Hand held, mains desk type, printers, non-printers, cased, uncased, damaged cases, bits missing! You name it - this pack has it! Lots of useful bits. Sold by weight. Total Pack Weight: 10Kg

ORDER CODE: PACK/034      **SALE PRICE: £5-00**



**PRE-SET PACK**

A mixed pack of various pre-sets. Miniature, standard, 0.1W, 0.25W, vertical, horizontal.

Assorted values from 100R to 1Meg.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/001 **SALE PRICE: £3-00**

**POTENTIOMETER PACK**

A mixed pack of pots single, dual, slider, convergence - in fact almost every kind of pot.

Assorted values ranging from 10R to 1Meg.

These really are super value.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/002 **SALE PRICE: £4-50**

**VOLTAGE DEPENDANT RESISTOR PACK**

A good mix of different types of V.D.R's 50-500V Super Value

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/003 **SALE PRICE: £4-00**

**WIREWOUND RESISTOR PACK**

A very mixed pack of assorted wirewound resistors. Mixed wattages and values, many popular values. A really good value pack.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/004 **SALE PRICE: £2-50**

**DIL SOCKET PACK**

A good assortment of various IC sockets which may range from 8 pin to 64 pin!

Generally low profile. May also include gold plated, turned pin, wirewrap etc.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/009 **SALE PRICE: £8-00**

**SUPADRIV. Self Tapping Pack HARDWARE**

A super pack of a mixture of No4 X  $\frac{1}{2}$  and No6 X  $\frac{1}{2}$ . All Pan head hardened steel type AB bright zinc.

Total Pack Qty: 100 assorted

ORDER CODE: PACK/010 **SALE PRICE: £1-00**

**MIXED SELF-TAPPING SCREW PACK HARDWARE**

A good mixture of various self-tapping screws of assorted types, lengths etc. All top quality. Length's 5-10mm

Total Pack Qty: 200 assorted

ORDER CODE: PACK/011 **SALE PRICE: £1-50**

**PRE-SET PACK 0.25W**

A super selection of 0.25W Pre-sets mainly Piher enclosed, AB etc.

Both vertical & horizontal and many popular values. Values may range from 100R to 10Meg!

Total Pack Qty: 100 pcs Assorted

ORDER CODE: PACK/016 **SALE PRICE: £2-50**

**POLYESTER PACK**

A good assortment of various polyester capacitors. Both Radial and Axial styles, values ranging from 0.01uF up to 2.2uF and voltages from 63V to anything up to 1000V!

This pack is very good value for money.

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/017 **SALE PRICE: £2-50**

**TANTALUM BEAD CAPACITOR PACK**

A random selection of tantalum bead capacitors of assorted voltages and values. Many popular values.

Total Pack Qty: 50 pcs

ORDER CODE: PACK/005 **SALE PRICE: £2-50**

**TRANSISTOR PACK**

A mixed pack of various transistors. many popular types including:

AC169, BC107, BC125, BC147, BC148, BC158, BC182A, BC237, BC328, BC558, BCY72, 2N2907A, TIP126, TIP141, TIS90, 2N2222A, etc etc.

Over £17-00 value at current catalogue prices!!

Total Pack Qty: 100 pcs

ORDER CODE: PACK/006 **SALE PRICE: £4-99**

**INTEGRATED CIRCUIT PACK**

A super value pack containing all types of I.C's many popular types included.

All are new and full spec.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/007 **SALE PRICE: £5-00**

**TRIMMER PACK**

A useful kit containing a selection of 'ceramic' trimmers.

Values include: 2-7pF, 4-15pF, 6-25pF, 8-30pF.

Working voltage: 250Vac

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/008 **SALE PRICE: £2-99**

**M5 & M6 Pack**

A mixed pack of steel screws, a mixture of Pan Head Supadriv and Allen type. Length's 20-30mm All super quality and a real bargain!

Total Pack Qty: 50 Assorted

ORDER CODE: PACK/012 **SALE PRICE: £1-00**

**M4 Mixed Pack**

A mixed pack of small M4 bolts - various lengths and types, pan, cross etc.

All the highest quality. Length's 5-20mm

Total Pack Qty: 100 Assorted

ORDER CODE: PACK/013 **SALE PRICE: £1-50**

**MIXED HARDWARE JUMBO PACK**

A super Jumbo pack containing all types of bolts, screws, washers. All mainly small types and high quality. Also nuts etc. Length's 10-45mm

This pack is really super value for money.

We are selling this pack by weight: 1Kg. This is up to 1000 pcs depending on sizes.

Pack Size: 1Kg

ORDER CODE: PACK/014 **SALE PRICE: £2-50**

**FUSE PACK**

A super pack containing an assortment of fuses which could include 20mm 32mm 1", fast blow, slow blow, in fact any type of fuse. Man popular sizes and values.

Total Pack Qty: 100 pcs

ORDER CODE: PACK/015 **SALE PRICE: £2-50**

— SURPLUS STOCK WANTED —

# EDDYSTONE DIECAST BOXES

WE HAVE NOW BEEN OFFICIALLY APPOINTED SOLE U.K. MAIL ORDER & RETAIL SUPPLIER.


EDDYSTONE DIECAST BOXES - Manufactured in the U.K. by Eddystone Radio - need no introduction. Respected Worldwide as the highest quality aluminium diecast enclosure available - until now only available to the professional buyers.

We have been appointed sole mail order and retail supplier of this range of boxes to the hobbyist market.

Aluminium diecast boxes with close fitting lids secured by four or six countersunk screws depending on the size of the box.

Supplied complete with screws.

ORDER CODE	EXTERNAL DIMENSIONS MM (APPROX.)				PRICE EACH	
	A	B	C	D	1+	10+
BOX/11451P	52	38	31	4	£2-05	£1-85
BOX/27969P	92	38	27	4	£2-25	£2-02
BOX/27134PSL	111	60	31	4	£2-45	£2-20
BOX/29830PSL	120	95	34	4	£3-65	£3-28
BOX/26908PSL	120	95	53	4	£4-80	£4-32
BOX/26357P	188	120	78	4	£8-40	£7-55

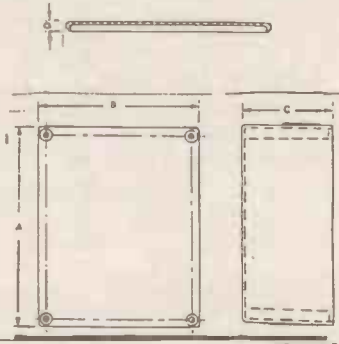

## ABS MULTIPURPOSE BOXES - STANDARD

A range of professional quality boxes, offering a high quality finish at a very realistic price.

Moulded in high impact ABS to give maximum strength, they are easily punched or drilled to produce a professional looking end-product.

Printed circuit board slots are provided on this range except for MB6.

All the lids are retained by 4 or 6BA countersunk 'posidrive' screws into brass inserts.

Colour available: Black.



INTERNAL DIMENSIONS mm			ORDER CODE	PRICE	
A	B	C		1+	10+
76	58	35	BOX/MB1	£1.25	£1.18
95	71	35	BOX/MB2	£1.35	£1.26
115	95	37	BOX/MB3	£1.58	£1.50
145	95	55	BOX/MB5	£2.20	£2.05
165	119	75	BOX/MB7	£3.20	£3.05
207	122	77	BOX/MB4	£4.96	£4.80
213	142	57	BOX/MB6	£3.78	£3.63
174	117	80	BOX/MB7	£3.20	£2.95
147	77	47	BOX/MB8	£2.15	£1.99


Dimensions B. 4.1/2" x H. 2.3/8" x W. 2.1/4"

Colour available: Black

ORDER CODE  
BOX/PSU-2

1+ 10+

PRICE - £1.26 £1.16

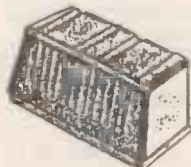

## ABS MULTIPURPOSE BOXES - MINIATURE

Colour available: Black



INTERNAL DIMENSIONS mm			WALL THICKNESS mm	ORDER CODE	PRICE	
A	B	C			1+	10+
72	46	22	1.5	BOX/T3	75p	67p
107	53	18	2.0	BOX/T4	90p	82p

## PANEL METERS

Good quality range of panel meters. Plastic with moving coil. Dims: 45x51x34mm Deep. Cut Out: 38mm Dia.



F.S.D.	INTERNAL RESISTANCE	
0.50uA	3500ohm	PANEL/164
0-100uA	3500ohm	PANEL/165
0-500uA	430ohm	PANEL/166
0-1mA	200ohm	PANEL/169
0-5mA	8ohm	PANEL/170
0-10mA	3ohm	PANEL/171
0-50mA	1.5ohm	PANEL/172
0-100mA	0.8ohm	PANEL/173
0-500mA	0.2ohm	PANEL/174
0-1A	0.1ohm	PANEL/175
0.2A	0.4ohm	PANEL/176
0-3A	0.3ohm	PANEL/176A
0-5A	0.02ohm	PANEL/177
0-10A	0.01ohm	PANEL/177A
0-25V d.c.	1000ohm/V	PANEL/178
0-30V d.c.	1000ohm/V	PANEL/179

**PRICE: £5-95**



# AMATEUR RADIO CALL BOOK AND INFORMATION DIRECTORY

1991/92 EDITION

# RSGB 1991/92 CALL BOOK (LESS THAN HALF PRICE) SUPER SALE

The Official RSGB Call Book & Information directory. This publication is a must for anybody interested in Amateur Radio. **430 PAGES!** Lists all UK & EIRE Call Signs and is packed with information including:  
Abbreviations, Awards, Band Plans, Beacons, Clubs, Contests, EMC, Licensing Info., Locators, Morse info., News, Packet nodes, Propagation, QSL, Planning permission, RAE, Raynet, Repeaters, RSGB info., Safety, Satellites, Special Event Stations Etc etc.

**CURRENT PRICE: £6-75!!**

**DIMS: 200 X 270MM**


**SALE PRICE £2-99**



**LEATHER-GRAIN P.V.C. COVERED ALUMINIUM** A very attractive range of British Made aluminium boxes covered with a leather-grain PVC. These boxes will add that finishing touch to any DIY or professional circuit.  
**THESE BOXES ARE EXTREMELY GOOD VALUE FOR MONEY.**


WIDTH	DEPTH	HEIGHT	ORDER CODE	PRICE	WIDTH	DEPTH	HEIGHT	ORDER CODE	PRICE
MILLIMETRES									
<b>NEW LINE</b>									
73	50	32	BOX/L10	£1.50	433	190	90	BOX/J46	£11.25
114	57	51	BOX/J2	£2.37	153	102	102	BOX/J10	£4.25
153	102	51	BOX/J6	£3.15	153	153	102	BOX/J15	£5.08
204	140	51	BOX/J9	£4.25	153	230	102	BOX/J22	£6.60
280	280	51	BOX/J26	£7.38	204	178	102	BOX/J23	£6.75
102	76	64	BOX/J3	£2.75	204	153	127	BOX/J24	£6.70
153	76	64	BOX/J5	£3.32	280	153	127	BOX/J33	£8.10
204	102	64	BOX/J8	£4.15	380	153	127	BOX/J45	£9.75
230	134	64	BOX/J12	£4.68	204	280	127	BOX/J44	£9.30
127	153	76	BOX/J11	£4.25	280	280	127	BOX/J60	£11.95
204	153	76	BOX/J14	£5.08	380	280	127	BOX/J83	£14.95
204	204	76	BOX/J19	£6.05	178	254	178	BOX/J49	£10.70
280	153	76	BOX/J20	£6.62	254	254	178	BOX/J70	£13.15
280	190	90	BOX/J29	£7.65	433	254	178	BOX/J119	£18.60

## BOXES

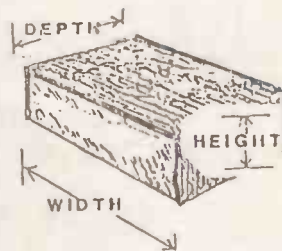

### PLAIN ALUMINIUM


WIDTH	DEPTH	HEIGHT	ORDER CODE	PRICE	WIDTH	DEPTH	HEIGHT	ORDER CODE	PRICE
51	76	26	BOX/A6	£1.16	102	102	51	BOX/A32	£2.15
51	102	26	BOX/A8	£1.32	102	153	51	BOX/A48	£2.50
51	127	26	BOX/A10	£1.55	76	127	76	BOX/A45	£2.55
76	102	26	BOX/A12	£1.60	102	153	76	BOX/A72	£3.10
51	76	38	BOX/A9	£1.45	127	178	76	BOX/A105	£3.75
76	114	38	BOX/A20	£1.78	102	254	76	BOX/A120	£4.42
76	140	38	BOX/A25	£2.10	127	171	102	BOX/A140	£4.48
51	102	51	BOX/A16	£1.65					

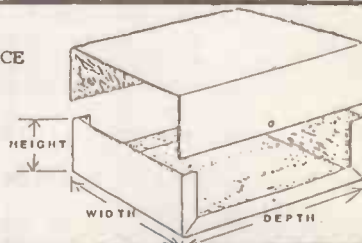

### 19" RACK CASES

7 Piece construction with 3mm aluminium front panel. Top & bottom covers are removable for easy access. Supplied in kit form for easy drilling etc.

PANEL DIMENSIONS		CASE DIMENSIONS			ORDER CODE	PRICE
WIDTH	HEIGHT	WIDTH	DEPTH	HEIGHT		
INCHES						
19.0	1.75	16.75	6.0	1.375	BOX/U106	£15.30
19.0	1.75	16.75	9.0	1.375	BOX/U109	£17.00
19.0	1.75	16.75	12.0	1.375	BOX/U112	£18.90
19.0	3.5	16.75	6.0	3.125	BOX/U206	£18.50
19.0	3.5	16.75	9.0	3.125	BOX/U209	£20.80
19.0	3.5	16.75	12.0	3.125	BOX/U212	£23.00
19.0	5.25	16.75	6.0	4.875	BOX/U306	£24.30
19.0	5.25	16.75	9.0	4.875	BOX/U309	£26.85
19.0	5.25	16.75	12.0	4.875	BOX/U312	£29.35
19.0	7.0	16.75	6.0	6.625	BOX/U406	£28.20
19.0	7.0	16.75	9.0	6.625	BOX/U409	£32.20
19.0	7.0	16.75	12.0	6.625	BOX/U412	£35.20

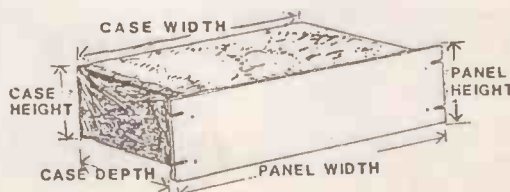

ALL PRICES INCLUDE V.A.T.

11

ADD £2.25 P & P PER ORDER

# COMPONENT KIT SALE

## Resistor Kit - 0.25W (5 off)

A pack containing 305 resistors. Values as listed below. Each value individually packed and each bag marked with the values enclosed.

Contents: 5 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M.

Order Code:

KIT/RES/25/5    ~~£3.75~~    ~~£2.25~~

**SALE PRICE £2-99**

## Resistor Kit - 0.25W (10 off)

A pack containing 610 resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 10 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M.

Order Code:

KIT/RES/25/10    ~~£5.10~~    ~~£4.60~~

**SALE PRICE £4-00**

## Resistor Kit - 0.25W POPULAR

A pack containing a total of 1,000 of 1,000 1/2W 5% carbon film resistors ranging in value from 10R to 10M.

In this pack we have included larger quantities of the more popular values.

Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
10 x	10R	10 x	82R	10 x	390R
10 x	12R	20 x	100R	30 x	470R
10 x	18R	10 x	120R	20 x	560R
10 x	22R	10 x	150R	20 x	680R
10 x	33R	10 x	180R	10 x	820R
20 x	47R	20 x	220R	40 x	1K
10 x	56R	20 x	270R	15 x	1K2
10 x	68R	20 x	330R	15 x	1K5
10 x	1K8	10 x	8K2	10 x	39K
25 x	2K2	30 x	10K	30 x	47K
20 x	2K7	15 x	12K	20 x	56K
20 x	3K3	15 x	15K	15 x	68K
15 x	3K9	15 x	18K	10 x	82K
25 x	3K7	20 x	22K	30 x	100K
20 x	5K6	15 x	27K	20 x	120K
15 x	6K8	20 x	33K	15 x	150K
15 x	180K	5 x	820K		
20 x	220K	20 x	1M		
15 x	270K	10 x	2M2		
15 x	330K	5 x	3M3		
10 x	390K	10 x	4M7		
20 x	470K	5 x	6M8		
10 x	560K	20 x	10M		
10 x	680K				

**SALE PRICE**

**£5-50**

## Resistor Kit - 0.5 POPULAR

A pack containing a total of 1,000 1/2W 5% carbon film resistors ranging in value from 2R2 to 10M.

In this pack we have included larger quantities of the more popular values. Each value individually packed.

Contents:

NO.	VALUE	NO.	VALUE	NO.	VALUE
5 x	2R2	10 x	12R	10 x	120R
5 x	2R7	10 x	18R	10 x	150R
5 x	3R3	10 x	22R	10 x	180R
5 x	3R9	10 x	33R	20 x	220R
10 x	4R7	20 x	47R	20 x	270R
5 x	5R6	10 x	56R	20 x	330R
5 x	6R8	10 x	68R	10 x	390R
5 x	8R2	10 x	82R	30 x	470R
10 x	10R	20 x	100R	20 x	560R
20 x	680R	10 x	3K9	20 x	22K
10 x	820R	25 x	4K7	10 x	27K
40 x	1K	20 x	5K6	20 x	33K
10 x	1K2	10 x	6K8	10 x	39K
10 x	1K5	10 x	8K2	30 x	47K
10 x	1K8	30 x	10K	20 x	56K
25 x	2K2	15 x	12K	10 x	68K
20 x	2K7	15 x	15K	10 x	82K
20 x	3K3	30 x	18K	30 x	100K
20 x	120K	10 x	680K		
10 x	150K	5 x	820K		
10 x	180K	20 x	1M		
20 x	220K	10 x	2M2		
15 x	270K	5 x	3M3		
15 x	330K	10 x	4M7		
10 x	390K	5 x	6M8		
20 x	470K	20 x	10M		
10 x	560K				

**SALE PRICE**

**£9-00**

Order Code:

KIT/RES/5/POP    ~~£10.75~~    ~~£9.75~~

## Resistor Kit - 0.5W (5 off)

A pack containing 365 resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

2K2, 2R7, 3R9, 4R7, 5R6, 6R8, 8R2, 10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M8, 2M2.

Order Code:

KIT/RES/5/5    ~~£5.40~~    ~~£5.00~~    **£4-50**

## Resistor Kit - 0.5W (10 Off)

A pack containing 730 Resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 10 off each value:

2R2, 2R7, 3R3, 3R9, 4R7, 5R6, 6R8, 8R2, 10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 18K, 22K, 27K, 33K, 39K, 47K, 56K, 68K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M5, 1M8, 2M2.

Order Code:

KIT/RES/5/10    ~~£8.75~~    ~~£7.75~~    **£7-00**

SALE PRICES ANY QUANTITY



# COMPONENT KIT SALE

## Resistor Kit - 1W (5 off)

A pack containing 365 1W resistors. Values as listed below. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

10R, 12R, 15R, 18R, 22R, 27R, 33R, 39R, 47R, 56R, 68R, 82R, 100R, 120R, 150R, 180R, 220R, 270R, 330R, 390R, 470R, 560R, 680R, 820R, 1K, 1K2, 1K5, 1K8, 2K2, 2K7, 3K3, 3K9, 4K7, 5K6, 6K8, 8K2, 10K, 12K, 15K, 22K, 27K, 33K, 39K, 47K, 56K, 82K, 100K, 120K, 150K, 180K, 220K, 270K, 330K, 390K, 470K, 560K, 680K, 820K, 1M, 1M2, 1M5, 1M8, 2M2, 2M7, 3M3, 3M9, 4M7, 5M6, 6M8, 8M2, 10M.

Order Code: 1+ 5+  
KIT/RES/1/5 ~~£15.25~~ ~~£14.00~~

**SALE PRICE £13-00**

## Ceramic Kit - 50V - Over £9.70 worth at catalogue prices -

A pack containing 125 50V disc and plate ceramics - ranging in value from 1pF to 10nF (0.01µF).

Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

1.0pF, 1.8pF, 2.7pF, 3.3pF, 4.7pF, 5.6pF, 6.8pF, 8.2pF, 10pF, 12pF, 22pF, 27pF, 47pF, 68pF, 82pF, 100pF, 150pF, 180pF, 270pF, 470pF, 560pF, 1000pF, 2200pF, 4700pF, 10nF.

Order Code: 1+ 5+  
KIT/CER/50V ~~3.99~~ ~~£3.50~~ **£3-00**

## Electrolytic Kit - Radial - Over £11.00 worth at catalogue prices -

A pack containing 100 miniature radial lead electrolytic capacitors. 12 different values. Each value individually packed.

Contents:

No.	VALUE	VOLTAGE	NO.	VALUE	VOLTAGE
10	1mF	63V	15	10mF	25V
10	2.2mF	63V	10	22mF	25V
10	4.7mF	63V	10	47mF	25V
15	100mF	16V	5	1000mF	16V
5	220mF	16V	2	1000mF	25V
5	470mF	16V	3	2200mF	16V

Order Code: 1+ 5+  
KIT/ELECT/RAD £8.50 £7.50

**SALE PRICE £7-00**

## Fuse Kit - 20mm Quick Blow

A pack containing 80 Quick-Blow 20mm Fuses.

Each value individually packed.

Contents:

No.	VALUE	NO.	VALUE	NO.	VALUE
5	x 100mA	10	x 500mA	10	x 3.15A
5	x 250mA	20	x 1A	5	x 5A
5	x 315mA	5	x 1.6A	5	x 6.3A
		10	x 2A		

Order Code: 1+ 5+  
KIT/FUSE/QB2 ~~£4.75~~ ~~£4.25~~ **£3-50**

## Fuse Kit - 20mm Anti-Surge

A pack containing 80 Anti-Surge 20mm Fuses.

Each value individually packed.

Contents:

No.	VALUE	NO.	VALUE	NO.	VALUE
5	x 100mA	10	x 500mA	10	x 3.15A
5	x 250mA	20	x 1A	5	x 5A
5	x 315mA	5	x 1.6A	5	x 6.3A
		10	x 2A		

Order Code: 1+ 5+  
KIT/FUSE/AS2 ~~£8.50~~ ~~£7.50~~ **£7-00**

A pack containing a total of 120 miniature horizontal mounting pre-set potentiometers. A total of 13 different values. Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
5	x 100R	5	x 2K2	10	x 47K
5	x 220R	15	x 2K7	20	x 100K
5	x 470R	20	x 10K	5	x 220K
15	x 1K	5	x 22K	5	x 470K
		5	x 1M		

Order Code: 1+ 5+  
KIT/POT/HORIZ ~~£7.75~~ ~~£7.25~~ **£6-50**

A pack containing a total of 120 miniature vertical mounting pre-set potentiometers. A total of 13 different values. Each value individually packed.

Contents:

No.	VALUE	No.	VALUE	No.	VALUE
5	x 100R	5	x 2K2	10	x 47K
5	x 220R	15	x 4K7	20	x 100K
5	x 470R	20	x 10K	5	x 220K
15	x 1K	5	x 22K	5	x 470K
		5	x 1M		

Order Code: 1+ 5+  
KIT/POT/VERT ~~£7.75~~ ~~£7.25~~ **£6-50**

## Zener Diode Kit - 400 M/W

A pack containing 55 zener diodes. 400m/w. Ranging from 3V6 to 30V. Each value individually packed and each bag marked with the value enclosed.

Contents: 5 off each value:

3V3, 4V7, 7V5, 8V2, 11V, 12V, 13V, 15V, 16V, 20V, 24V.

Order Code: 1+ 5+  
KIT/ZEN/400 ~~£3.99~~ ~~£3.50~~ **£3-00**

## Polyester Capacitor Kit

ITT PMT type 100V miniature or similar. Pack contains 110 capacitors. Each value individually packed and each bag marked with the value.

Contents: 10 off each value:

0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 0.068µF, 0.1µF, 0.15µF, 0.22µF, 0.33µF, 0.47µF.

Order Code: 1+ 5+  
KIT/POLY Price ~~£5.00~~ **£4-00**

SALE PRICES ANY QUANTITY

# KIT SALE

## 500V Ceramic Kit

Very high quality, single layer type.

These capacitors are normally very expensive and there not available to the hobbyist. We priced this kit up at current trade prices, the price manufacturers pay, and it was over £60.00!!! You really cannot afford to miss this super offer.

Physical sizes: 3.3pF to 3N3 8mm Dia.  
4.7nF to 10N 10mm Dia.  
20nF to 220N 16mm Dia.

Each Kit contains 5 off each value. Total Quantity 125 pcs.

Values: 3.3pF, 3.9pF, 10pF, 15pF, 22pF, 27pF, 33pF, 47pF, 56pF, 68pF, 82pF, 100pF, 120pF, 180pF, 220pF, 270pF, 680pF, 1N2, 1N5, 3N3, 4N7, 8N2, 10nF, 20nF, 47nF, 220nF.

Order Code: SO/HVKIT Price: £6.00

## CABLE KITS SPECIAL OFFERS

A choice of two packs of British Made equipment wire. 10/0.1mm and 7/0.2mm. We also offer this cable in 100mtr.reels. See below.

### 10/0.1mm Pack

Dia. approx 1.05mm. Max voltage RMS 1000V. Nominal current is 0.5Amps.

Each pack contains 10 Metres of each of the following colours: RED, BLACK, BLUE, BROWN, GREEN.

A total pack of 50 metres.

Order Code: SO/CBL/P1 Price: £1.50  
(Price per 100mtr reel is £1.95)

### 7/0.2mm Pack


Dia. approx. 1.2mm. Max voltage 1000volts RMS. Nominal current 1.4Amps.

Each pack contains 10 Metre of each of the following colours: RED, BLUE, GREEN, WHITE, GREEN/YELLOW.

A total pack of 60 metres.

Order Code: SO/CBL/P2 Price: £1.80  
(Price per 100Metre Reel is £2.00)
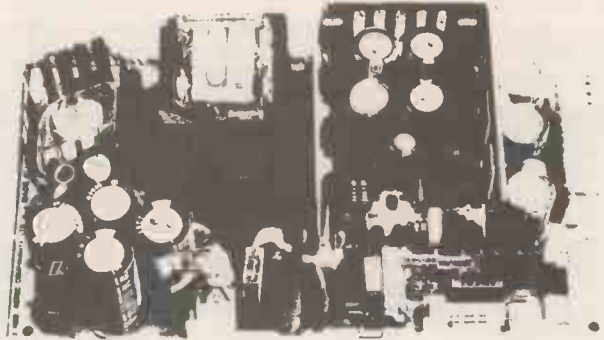
## SWITCH MODE PSU Astec AC-9355 65 WATTS



Super quality, ex-equipment but ALL tested guaranteed.

Input: 240Vac OUTPUT:

V1 +5V @ 6A V2..+12V @ 1.5A

V2 +12V @ 1.5A

V3 +12V @ 2.1A

V4 -12V @ 0.25A

DIMS: 195 X 10.5 MM

ORDER CODE: SO/ASTEC/9355

SALE PRICE: £15-00 each


## BUTANE GAS SOLDERING IRON

Uses ordinary butane 'cigarette lighter gas. Internal tank holds sufficient gas for one hours use. Ideal for: field service engineers, motor mechanics etc. supplied with 2.4mm soldering tip as standard.

Order Code:

SOLD/GT06 £ 14-50

GT36 GT48

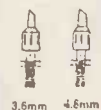

3.6mm 4.8mm



GT24 GT10



2.4mm 1.0mm

TIPS £ 4-00 EA

# PARCEL TAPE SALE

## (BUFF VINYL SEALING TAPE)

(YES, IT'S SELF ADHESIVE!)

Known by many titles, we simply call it brown parcel tape! It's the tape we have used for several years. It's the highest quality - not to be confused with the cheap & cheerful tape that's around.

We have just taken delivery of over 5,000 reels and although we use a lot we can spare a few rolls!!!

**PLEASE REMEMBER: OUR PRICES INCLUDE VAT!!**

Standard Length: 66 Metres. Standard width: 50mm  
Colour: Buff (Brown)


	1+	10+	100+
<b>SUPER SALE PRICE:</b>	<b>65P</b>	<b>55P</b>	<b>48P</b>

**HURRY HURRY, WE SOLD 200 ROLLS BEFORE WE HAD FINISHED UNLOADING OUR VAN!!**

ALL PRICES INCLUDE V.A.T.

14

ADD £2.25 P & P PER ORDER

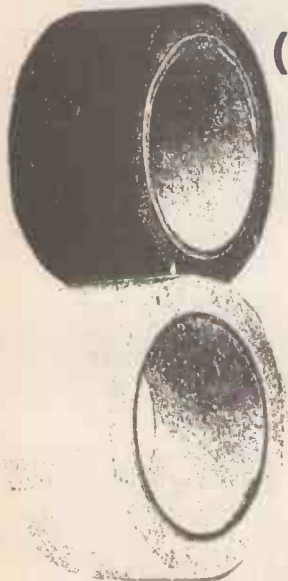




# HOBBY KITS

A range of Economy Electronic Kits for hobbyists, schools etc. Each kit contains electronic components, which must be soldered to the P.C.B. provided. The modules are ready made units and most have connections brought out to screw terminals.

Many of the kits and modules require the purchase of additional items.
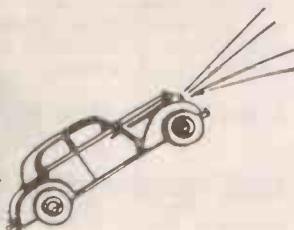
## Car Light Warning (B001)


This circuit will attract your attention by producing a noisy 'Honk' signal should you turn off the car ignition but leave the lights on, and therefore should save you the problem of a drained battery. Works off the car battery, 6-12V.



KIT/B001 £7.50
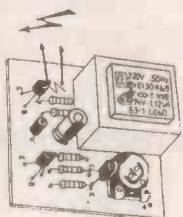
## Electrifying Apparatus (B007)

...generates a weak adjustable high tension of approx 80-300V out of 3-6V(Max 9V). May be used by anglers to catch worms. Maximum current 50-250 MA.



KIT/B007 £8.35

## Fog Horn 5W(B015)


...generates a deep, noisy sound similar to the fog-horns of ships. Operating voltage 4.5-12V wattage:Max 5W depending on the voltage. For 8Ω-loudspeakers.



KIT/B015 £5.99
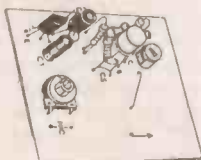
## Test Oscillator (B018)

This is a close range test only transmitter, which can be tuned between 88 and 108 MHz and used to service radio receivers by using the unmodulated carrier. This kit must not be used to transmit over any distance.



KIT/B018 £6.85

## Lighting Console (6 WAY),(B022)

Each channel is independantly adjustable. Lamps up to Max.500W. 240V can be connected per channel. High input sensitivity: Adapts to stereo or mono equipment. For discotheques, party rooms and the like.

KIT/B022 £20.50



## Telephone Amplifier (B105)


Suitable to monitor telephone conversations via the pick up coil. This kit requires a loudspeaker of 8Ω and an operating voltage of 9V.



KIT/B105 £9.95
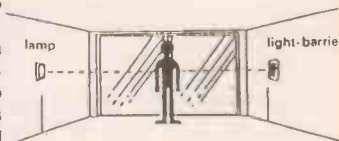
## Light Barrier 12V (B045)

A light barrier Kit which uses an LDR(Light Dependant Resistor) to trigger the relay on. Can be used to switch on an alarm, open a door or as a twilight switch etc. A light source is required which shines onto the LDR of the kit, if this light source is interrupted the relay will pull on. Max. relay current is 5A. Requires a 12V supply.



KIT/B045 £9.75

## Thermo Switch (B048)

Turns the relay on or off at a pre fixed temperature This instrument may be used as a thermostat, as an ice warning system, etc. Operating voltage: 12V. Temperatur range: approx -30 to +150 C. Relay switching capacity: 5A



KIT/B048 £9.85

## Siren Warship (B052)


'Decks clear for action' - warship siren. Creates a short swelling up sound (uiiit...uiiit...) in short intervals. Wattage 3-15W. depending on the operating voltage. For 6-12V. Loudspeaker impedance:8Ω



KIT/B052 £12.50
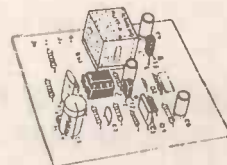
## Infra-Red Light Barrier (B062)


Light barrier with invisible infra-red light beam. Complete kit with transmitter and receiver. Range over 6M. Operating voltage: transmitter 9-12V receiver 12V. Relay contact: 3A switching capacity. Ideal for warning systems.



KIT/B062 £19.75
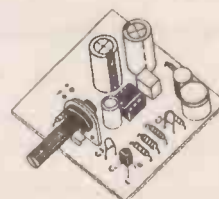
## Parabolic Microphone (B085)

Highly sensitive microphone. If mounted into a semi-circular reflector (eg half of a plastic ball), noise and voices in a distance of several hundred metres may be recorded. Ideal for animal observance, for detectives etc. For headphone connection 80. Requires 9V supply.




KIT/B085 £10.35
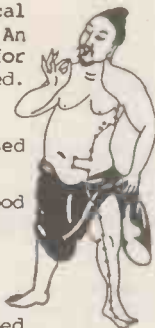
## Acupuncture Electronic (B136)

Electronical Acupuncture has an effect on many sicknesses. This kit operates in accordance with the electronical acupuncture - method. An illustrated description for the treatment is enclosed. 3-12V

- migraine, headaches caused by overstraining.
- stimulation of the blood circulation.
- neuralgia
- strained shoulders
- muscle pain like inflamed muscles and soreness
- backaches (lumbago)
- leg and arm neuralgia
- rheumatically caused articular pain
- articular pain as arthritis or sprain.




- migraine, headaches caused by overstraining
- stimulation of the blood circulation
- neuralgia
- strained shoulders
- muscle pain like inflamed muscles and soreness
- backaches (lumbago)
- leg and arm neuralgia
- rheumatically caused articular pain
- articular pain as arthritis or sprain

KIT/B136 £9.85
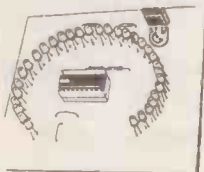
## LED VU Meter (30LEDs) (B160)


A thirty LED voltage display which uses the new U 1096B chip making it possible to construct an LED control display with 30 LEDs. The circuit can be connected directly to the loudspeaker output of an amplifier. A trimming pot allows exact setting within the required range. The display can also be used as a voltmeter etc.



KIT/B160 £19.25
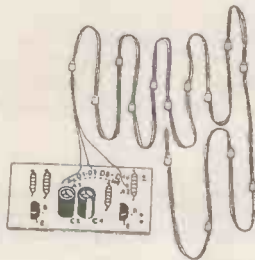
## LED Lightband (B173)


A decorative lighting band of approx. 1.5m with 14 light emitting diodes, which light up alternately to give the appearance of movement. Ideal for decorations at parties, carnivals etc. Requires 18V power supply.



KIT/B173 £9.45
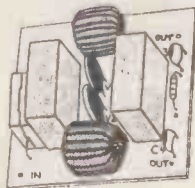
## Filter Electronic (B176)

This highly effective anti-interference device has to be connected into the mains lead of you computer, telefax, video or TV set. The kit is overvoltage protected. Max load: 750W 110-250V AC



KIT/B176 £13.25

## Dog Barking Electronics (B155)

Generates a dog barking sound. Suitable for use with 8" speaker. Operating voltage 9-12V. The barking is stored on a special speech-synthesizer IC.



KIT/b155 £19.50

## Ultrasonic Dog Whistle (B179)

The ultrasonic dog whistle emits high powered ultrasonic sounds which are widely audible for dogs, but mostly undetectable by the human ear. The output frequency is through a special piezo loudspeaker and is adjustable between 8000 and 25,000 Hz. Requires a 9V battery.



KIT/B179 £7.50



## Speed Control 12-24V (B180)

Suitable for the operation of miniature drilling machines which have DC motors. A rectifier is fitted in the kit and only requires a transformer of 12-24V secondary depending on the required voltage. Suitable for use up to 3A current input.



KIT/B180 £6.45

## Alarm Motorbike (M073)

This waterproof and shakeproof module will automatically switch on a horn or siren if the motorbike is moved, can also be used to protect other objects from theft. Additional items required: power supply (bike battery), SPST switch, horn or siren. Max current 1A.



KIT/M073 £4.50

## Ion Generator (B137)

Regenerates negatively loaded air particles (air-ions) and helps to produce a healthy climate which can reduce troubled sleep, aggressiveness, headaches and weather related dispositions etc. Input 6-18V DC. Output 2-7kV. Current limit protection < 200 A.



KIT/B137 £9.95

## Lie Detector (B087)

This lie detector will monitor changes of the skins resistance due to sweating caused by lies and fear etc., which is then indicated by an LED. Requires 4.5V



KIT/B087 £5.95

## MW Testing Transmitter (B144)

A close range test only oscillator which can be used as an unmodulated carrier to test radio receivers in the MW band. This kit must not be used to transmit over any distance.




KIT/B144 £4.99



# HOBBY KITS
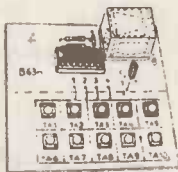
## Combination Digital Lock B(063)

After keying-in a 4-digit number, the relay switches on. The code is independently programmable and can be easily modified. Relay contact: 3A, 1xchange over. For 6V application: keyless door-lock, to switch on equipment (radio, TV-set etc.) which is not to be used by other people, for safe doors etc.



KIT/B063 £22.75

## Car Antenna Amplifier (B068)

This amplifier is connected between the antenna and the radio, using co-axial cable 60-750. Gain max: 22 dB. Frequency range: 0.5-150 MHz (Approx).



KIT/B068 £5.99

## Spy Stethoscope (B069)


Using an earpiece the spy stethoscope allows you to listen through thin walls, doors, windows etc., due to a highly sensitive pre-amplifier and microphone. Suitable for monitoring animals etc.



KIT/B069 £20.50
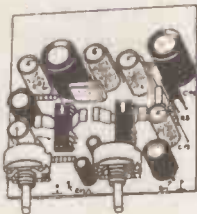
## Accoustic Water Detector (B070)

...raises a loud alarm signal on contact with water. This instrument signals broken water pipes, overflowing washing machines and bath tubs, etc. The sensor can be connected by a longer cable of up to 100m. Power supply: 9V battery.



KIT/B070 £5.99

## Microphone pre-Amp (B090)


The impedance load can be adapted for each microphone from 40 to 100kΩ. Input voltage 2-40mV. Output max. 1.8V. Adjustable gain. Frequency: approx. 20-40000Hz. Operating voltage: 6-20V approx. 1mA



KIT/B090 £6.95
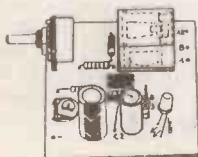
## Interval Switch (Universal) (B098)

Interval time: approx. 1-140sec. interval length: approx. 0.2-12sec. adjustable. Operating voltage: 7.5-15V. Relay capacity: max. 5A. Interval indication by LED. Application: Screen-wiper interval switch for cars, pulsator for lamps, motors etc. Delay switch for alarm systems, etc.



KIT/B098 £13.85

## Pre-Amp Universal Mono (B073)

Frequency range 10Hz-150kHz. 2-step pre-amplifier for 9-30V, output: 200mV-2V. Application: pre-amplifier for high-power amplifier, 'headphones-amplifier', etc.



KIT/B073 £4.85

## Diode Receiver MW and SW (B076)


'Detector-receiver' for Middle-wave or short wave, approx 2-9 MHz. This radio operates on the same principle as the very first radio receivers. It does not require an operating voltage. This kit is educational for beginners.



KIT/B076 £10.75
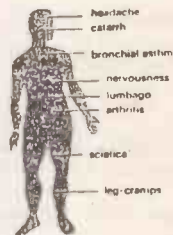
## Mesmeric Instrument (B078)


This magnetic field instrument operates on the same principle as curative instruments offered on the medical market. Alternating currents of magnetic fields are said to have a soothing effect on various kinds of sicknesses.



KIT/B078 £9.25
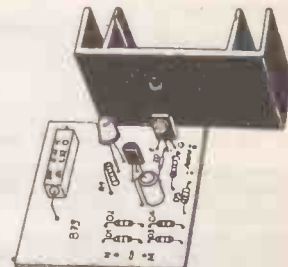
## Battery charger, Ni-Cad (Universal) (B079)

Automatic accu-charger for accumulators of 1.2-15V. The charging current will automatically adjust, to remain constant as the battery charges. Has a selection of seven settings. 5-600mA. Additional requirement: 1 transformer. Output capacity: 18-20V. 0.6 A.



KIT/B079 £9.25

## Pre-Amp Universal Stereo (B142)

2-step stereo universal pre-amplifier for operating voltages between 9-30V operating voltage. Input: 2-20mV. output: 200mV-2V: application pre-amplifier for high-power amplifier, 'Headphones-amplifier', etc.



KIT/B142 £8.45

## Robot Voice (B 107)

This kit modulates the human voice with an adjustable frequency to produce robot like sounds. This sound then requires amplification i.e. by an amplifier or a tape recorder. Requires 9-12V supply.



KIT/B107 £9.60

# 12V ACCESSORIES

## PLUG-IN FLASHING LED

A flashing LED built into a car cigar plug to act as visual warning that alarm may be fitted. Simply plug into car cigar socket. Simple but may keep your car safe!

ORDER CODE: CAR/B200Z

PRICE: £1-95



## B1188

### BROADBAND RADIO RECEIVER

A handheld broadband radio receiver with a range covering CB, FM radio, TV, Air and PB bands. Built-in telescopic aerial. Squelch, volume and tuning controls and band selector switch.

#### Frequency range:

Air 108 - 145MHz  
 PB 145 - 176MHz  
 WB 162.5MHz  
 TV 54 - 87MHz  
 FM 88 - 108MHz  
 CB 1 - 80 channels

Power.....6Vdc  
 (4x "AA" batteries, not included)  
 Dims.....93 x 198 x 50

PRICE: £17-50



## T081B

£69-99

### VIDEO LIGHT KIT

A semi-professional video light kit comprising 100W halogen lamp, remote 12Vdc 7Ah sealed lead acid battery in carrying case with shoulder strap, 220/240Vac operated battery charger and camcorder power supply adaptor.

## CAR POWER LEAD

A handy lead, Fused 3A cigar plug connected to a moulded 2.2mm DC power plug. Lead length approx. 2m.

Colour: Black


CAR/P.LEAD

1+

£1-50

10+

£1-25

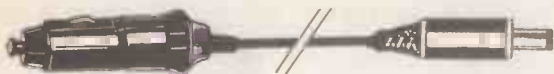

## 12VDC TRAVEL KETTLE

B049A

12Vdc kettle complete with mounting stand, cup and cup holder with self-adhesive base. Plugs directly into a car cigar lighter socket for power. A power-on light is provided at the base of the kettle. Ideal for cars, vans, campers etc.

Capacity.....0.5 pints (0.35)  
 Power.....12Vdc 9A, 14Vdc 11A  
 Dims.....143 x 125 x 112mm (approx)

£12-99 4 FOR £46-00



## QUARTZ HALOGEN SPOTLIGHT


Hand held spotlight with a 55Watt bulb, producing more than 250,000 candle power, directed by a concave, electro plated reflector. Supplied complete with hanging loop and 3.6m coiled lead with cigar plug fitted.

POWER.....12Vdc 55W  
 DIMENSIONS..125x125x140mm (Approx)

ORDER CODE: OPTO/QHS £5-75



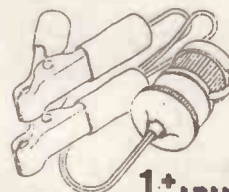A 12V car cigarette lighter socket connected to 2 x battery crocodile clips.



1+....£2-99

ORDER CODE: CAR/JL

4 FOR £10-00



# SPECIAL OFFERS


## PHOTO-TRANSISTOR Siemens Type: SFH309-5

Case: T1 (3mm)  
Sensitivity: 1.0-2.0 @ 0.5mW/cm<sup>2</sup>  
Half Angle: 32°  
Peak Response: 900nm  
Response: 10 tr(US)  
Short lead is connector.  
Lead pitch: 2.54  
We have large qty's in stock.



ORDER CODE:	1+ 38p	10+ 35p	100+ 25p	1000+ 20p
SO/601				

## SCHRACK RELAY TYPE: RP-03 10 12

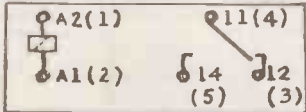

Internationally approved heavy duty PCB mounting relay in industry standard dimensions with 1 form C contact rated at 8Amps. Mounted on 0.1" grid.

Switching voltage: 380Vac max.  
8A 250Vac Dims: 28 X 25 X 11mm

Nominal V DC: 12V 270 ohm

ORDER CODE:	1+ SO/602	10+ £1-00	100+ 90p	1000+ 65p	1000+ 55p
-------------	--------------	--------------	-------------	--------------	--------------

(We still have approx 3,000 in stock!)

## EPROM LABELS 16.5mm X 5.08mm

OK INDUSTRIES TYPE CODE: 1/100A/10

A dual purpose label designed for use on Eproms or similar devices where the chip requires protection from the effects of light. These labels are also handy for marking devices or junction identification. Supplied on roll sheets which have pin-feed holes along the edge thus allowing them to be printed on a computer printer.

Total qty. per full rel: 3350 Labels (Approx)

ORDER CODE:	QTY	PRICE
SO/600	60 Labels	50p
	180 Labels	£1-40
(Full reel)	3350 Labels	£22-50


## IEC LEAD - CURLY

6A 240Vac Right Angle IEC plug fitted to 3core 0.75mm black curly cable. Stretches to approx. 2.5Metres.

ORDER CODE:	1+ SO/604	10+ £1-00	90p
-------------	--------------	--------------	-----
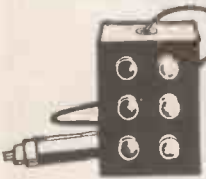
## TERMINAL BOX - 12Vdc

Terminal junction box for powering d.c. accessories. Gives three pairs of pillar screw terminals, colour coded Red & Black. 90cm lead with cigar plug fitted. Current.....3A max. Dims: 84 x 55 x 32mm



ORDER CODE:	1+ SO/158	10+ £1-50	£1-25
-------------	--------------	--------------	-------

## TOROIDAL TRANSFORMER Made in UK Manufacturer: St Ives Windings.

PRIMARY: 0-120V  
0-120V

SECONDARIES: 9V at 4Amps  
15-0-15v at 500mA

Dims: 75mm Dia 38mm Thick

Original Price in tens £24 each  
ORDER CODE: SO/268 PRICE: £9-99



## STEREO SOCKET SALE

6.35mm (1/4") Stereo chassis socket  
Metal mounting nut. Unswitched

ORDER CODE: SO/661

PRICE:	1+ 30p	10+ 26p	100+ 20p
--------	-----------	------------	-------------



## HI RES MONITOR Made in UK GREEN SCREEN

Very high quality monitor, complete apart from the case.

Resolution at Centre is 900 lines therefore ideal for computer applications.

Simply input 12V @ 1.2A.

### COMPOSITE VIDEO!


Supplied complete with full handbook and circuit diagram and full parts list.

(Manual available seperately £2-00 each)

### SPEC:

CRT Size	.....7" (178mm)
Power	.....12V/1.2A
Line Frequency	.....15-19KHz
Vertical Frequency	.....50-60Hz
Resolution at Centre	.....900 lines
Linearity	.....<2%
EHT Typical	.....12.0Kv
Line Blanking	.....12-7.5uS
Vertical Blanking	.....750uS
Video Input unterminated	.....12K terminated.....75R
Video Response	.....22MHz
Video Rise/Fall	.....17ns
Video in for 35V output	.....1Vp-p

ORDER CODE:	SO/MONITOR	PRICE: £19-99
		2 for £35-00

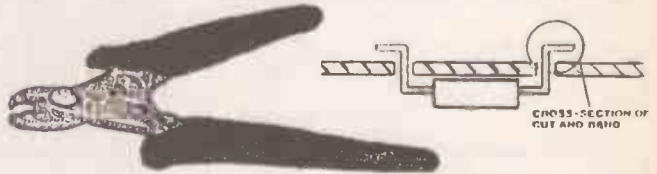

### CUT AND BEND

Cuts & bends component leads in one action (see drawing). A quick & easy method of retaining mounted components. Ideal for development work. Components can be removed & reused after desoldering at a later time. Cutting capacity 1mm dia. copper wire. Special cushion grip handles. Very high quality, manufactured in Italy.

Length: 128mm Weight: 70gms  
Normal Catalogue Price: £4-95

ORDER CODE:	TOOL/SC/TP30	SALE PRICE: £2-99
-------------	--------------	-------------------



### CUT and CLENCH

A stepped edge provides a cutting & clenching action which will cut & splay copper leads out to approx. twice the original diameter. (See drawing). Provides a permanent & secure method of retaining components, particularly useful in production. Cutting capacity 1mm dia. copper wire.

Length: 128mm Weight: 70gms

Special cushion grip handles. Made in Italy.  
Normal catalogue Price: £4-99

ORDER CODE:	TOOL/SC/TS30	SALE PRICE: £2-99
-------------	--------------	-------------------

### CAR STEREO KNOBS

A complete set of silver knobs for car stereo radio/cassette player. 4 knobs gives one each for volume, tuning, balance & tone. Serrated edges. Push On with anti-rotation spigots.

Max dia: 34mm Only a few hundred left.

ORDER CODE:	SO/606	1+ PRICE: 50p	10+ 42p
-------------	--------	------------------	------------

## SURPLUS STOCK WANTED

# SPECIAL OFFERS

## MICROPROCESSOR BOARD

A very high quality PCB manufactured by Ferranti still in its original packaging.

All Microprocessors are 'plug-in'.

2 X Z0803006PSC (40pin) 1 X Z0801604PSC (48pin)  
 1 X Z8001B1 CPU (48pin) 4 X 27256-20 (28pin)  
 1 X AM8152ADC (48pin) 1 X AM27128A (28pin)  
 1 X AM8052-5LC (68pin PLCC) Dated 1984

Over 40 assorted IC's soldered plus numerous resistors, caps., crystals etc etc.

BOARD DIMS: 220 X 225mm

ORDER CODE: SO/648

PRICE: £15-00

## SILVERED MICA 0.01uF 500V 1%

Type: RDM30FD103-F03 CDE

Super quality, good high voltage at a low price.

DIMS: Height 20mm Width 20mm Depth 7mm

Lead Pitch: 10mm (Lead length: 35mm)

The current distributor price for a 350V version is over £1-85 each plus VAT!!! Several thousand avail.

ORDER CODE: SO/649

1+	10+	100+
PRICE: 50p	45p	35p



## ANGLE SCREWDRIVER

USAG 340 Each end has flat blade 13mm tip. Very high quality, marked Vanadium USAG Extra 2 X 13.

ORDER CODE: SO/650

PRICE: £1-00 each

## POLYESTER 0.22uF 400V

ITT Made

Radial Lead. Lead Length: 15mm. Pitch: 22.5mm

Dims: H 19mm W25mm D 10mm

ORDER CODE: SO/651

1+	10+	100+
PRICE: 20p	18p	14p



## COMMUNICATIONS INTERFACE PCB - Processor Board

Sorry, no further info. but board populated with several 6800, 6116, 2764, series chips (All plug-in).

Phono sockets, resistors, caps., etc etc.

Board Size: 465mm X 195mm

ORDER CODE: SO/652

PRICE: £5-00

## IEC SOCKET - Snap Fit

10A 250V

A snap fit IEC socket providing a quick and easy installation option for IEC connector.

Chassis male.

Marked with all the approvals.

Panel Cut Out: 27 x 19.5mm

ORDER CODE: SO/653

PRICE: 50p



ORDER CODE

1+	10+	100+
SO/MAX 85p	75p	60p
SO/SKC 65p	55p	40p

## TANT BEAD SUPER SALE

We have just purchased over 150,000 tantalum bead capacitors and can offer very attractive prices while stocks last.

VALUE/Voltage	1+	10+	100+	1000+
1.0uF/35V	10p	8p	5p	3p
2.2uF/16V	11p	9p	6p	4p
4.7uF/35V	16p	12p	9p	7p
10uF/16V	20p	15p	10p	8p
10uF/35V	24p	18p	13p	10p



Lead Spacing: 5mm Approx Lead length: 5mm

## TELEFUNKEN - Selection guide Transistors & Diodes.

38 pages, packed with full specifications, drawings, pin-outs and cross-references.

Contents: BA204-2N4036

A super booklet full of useful data.

Dims: 270mm X 210mm

ORDER CODE: SO/654

PRICE: £1-00

## ANGLE SCREWDRIVER



USAG 341. Ideal where space is restricted. Two tips set at 90° to the shaft and heads for cross slot screws. Manufactured from Chrome vanadium steel, hardened, tempered and chrome plated for corrosion protection.

Blade Length: 6" (150mm)

One End: Cross Slot No. 3

Other end: Cross Slot NO. 4

ORDER CODE: SO/655

PRICE: £1-25

## REDPOINT HEATSINK

Type: 4W-4

1.2°C/W

H=32mm W=130mm D=100mm

Pre-drilled to take 2 X T03 devices.

List price £6-04 plus VAT! These really are top quality. Only a limited quantity available.

ORDER CODE: SO/260A

PRICE: £2-50



## HEATSINK Type: SW50-4

High performance heatsink, designed for plastic power transistors, including T0-220, T0-3P, T0-126 etc. Fitted with solderable pins and may be vertically mounted.

Pre-drilled, Black anodised body.

Length: 50mm Width: 34.5mm Depth: 12.5mm

Thermal Rating: 8.6°C/W (Current Price 98p!)

ORDER CODE: SO/260

PRICE: 55p

## AUDIO CASSETTES

## AUDIO CASSETTES

Used once and bulk erased. ALL FULLY GUARANTEED Over the last 12 months we have sold over 55,000 of these tapes and demand is still growing.

At time of printing we have two makes available.

MAXELL UDI-90 & SKC GX90 Ferro Position

Both tapes are supplied complete with inlay cards.

Both tapes are 90 Minutes.



# SPECIAL OFFERS



## FARNELL SWITCH MODE PSU - 240watts G Series

Model: G12 20A


They seem unused but no promises. Copy of manual available with orders upon request. These units are in the current Farnell catalogue at over £395 each!

INPUT: 115-120/240Vac

OUTPUT: 8 to 12.6V (Adjustable) 20 Amps

Dims: 88 X 160 X 194

SALE PRICE: £150-00 each

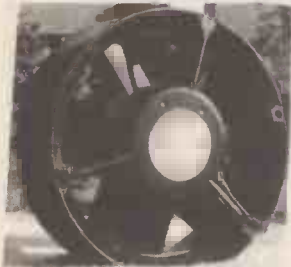

**PAPST FAN - TYPE 6124** (172 X 55mm) 206CfM  
Aluminium fan, impeller of fibreglass reinforced plastic. Electronically commutated dc motor. Counterclockwise rotation viewed from rotor, air output over struts!! OK? (Supplied with FREE guard)  
All brand new, still boxed, very high quality.  
List price is over £85-00 each!!!

ORDER CODE: SO/256A SALE PRICE: £10-00 each any qty.

**EBM FAN - Type W2G075-AE21**

80mm X 80mm (Depth 38mm)

Super quality, latest model. Run at 12Vdc. (will run on voltage between 8v and 16vdc.)

2.6watts, 3450u/min. Made in Germany.

All aluminium construction. Trade price over £30 each!

ORDER CODE: SO/257 SALE PRICE: £7-50 ea

**RAYCHEM MINIATURE CO-AX**

75 ohm Type: 7528A1317-9(100)

Commercial quality. Stranded 7/0.127mm 28awg. Dia. 2.6mm

Colour: WHITE Reel Length: 100mtrs

Current trade price: £92 per reel!!

ORDER CODE: SO/446 65p/mtr £45 per 100 mtr reel



**IEC FILTER PLUGS - Belling Lee**

Operating Voltage: 240Vac. Line Frequency: 0-400Hz.

Inductance: 3mH per line. Trade Price £9-50 each!

Two ratings available: 2Amp and 6Amp.

2A Order Code: SO/262 SALE PRICE: £3-50 each

6A Order Code: SO/262A SALE PRICE: £3-50 each



**DIL SWITCH - 10 Way - Low Profile**

Alco Type: ADF10

Very high quality. 0.1" pitch. Black with white switches. Length: 27mm. DIL package. 20 pin

At time of printing we have over 20,000 pcs in stock. 15pcs per tube.

	1+	15+	90+	900+
ORDER CODE: SO/608	50p	45p	39p	30p



**SIEMENS FILTER 0.33uF**

Type: B84150-A-A110

Stud mounting, 4 solder tags.

0.33uF(X1) + 2 X 2500pF(Y) + 680K + 2X1.8mH

250Vac 10Amp 50/60Hz

Dims: 65mm X 35mm(Dia)

ORDER CODE: SO/SIE/A110 SALE PRICE: £1-50

**SIEMENS FILTER 0.47uF**

Type: B84150-A-A115

Stud mounting, 4 solder tags.

0.47uF(X1) + 2 X 5000pF(Y) + 680K + 2 X 1mH

250Vac 10A 50/60Hz

DIMS: 75mm X 35mm(Dia)

ORDER CODE: SO/SIE/A115 SALE PRICE: £1-50



## SIMILAR TO ABOVE KEYBOARD

**KEYBOARD - Clare BRAND NEW**

Uncased Brand new keyboards manufactured by Clare General Instrument Corp.

Alphanumeric - separate numeric keypad.

107 keys with a buzzer and several IC's on the rear:

1 X 8528, 1 X 2516JL-45, 1 X ET8035N-6, 1 X 6Mhz Crystal etc etc. Plus various resistors & capacitors.

Overall dims: 480 X 160mm.

ORDER CODE: SO/472 SALE PRICE: £4-50 each

## ALLIBERT TRAYS



**Capacity 6 litres**

Ext LxWxHmm -

400x300x74

Int LxWxH -

355x255x64

**P.C.B. STORAGE TRAYS - Made by ALLIBERT**

General purpose, high quality trays. Ideal for many uses: PCB storage, component storage, desk in/out trays, seed trays etc. Very very strong & stackable.

Current price in KEYS catalogue: £3-50 ea plus VAT

Dims: 300 X 395mm Depth: 75mm

	1+	10+	100+
ORDER CODE: SO/TRAY	£1-50	£1-25	£1-00

## SHUGART 8" DRIVE



**DISK DRIVE - 8" BRAND NEW**

Shugart Model: 801

Brand new, 240Vac drives still in original packaging. These really are a bargain!

ORDER CODE: SO/DRIVE SALE PRICE: £15-00

# SPECIAL OFFERS

## SECURITY KEYSWITCH



6A 240Vac 2 tag SPST Fixing hole: 19.2mm  
 Dimensions: 40 X 20mm dia.  
 Key may be removed in 'OFF' position only.

	1+	10+	100+
ORDER CODE: SO/605	£1-50	£1-25	£1-00

SCOTCH DATA CARTRIDGE Type DC300A 3M  
 Standard length, all brand new and in original sealed packs. These really are a bargain.  
 Length: 450ft (137.2mtrs) 1600bpi/3200 ftpi  
 ORDER CODE: SO/436 SALE PRICE: £10-00!!

## MEMOGUARD LITHIUM MEMORY RETENTION BATTERY

Safe Type: 40LH220

- \* DIL Package
- \* Hermetically sealed
- \* 10 year operating life.
- \* Voltage, 3V

Dimensions: 28 X 25 X 8mm  
 Normal trade price is £2-75 plus VAT!

	1+	10+
ORDER CODE: SO/437	£1-50	£1-25




Keyswitch Cover.  
 Strong plastic cover providing protection against the weather in external applications.  
 Colour: Grey

	1+	10+
ORDER CODE: SO/607	25p	20p

PHILIPS CCTV CO-AX LEADS  
 BRAND NEW - Leads, 10Mtr long.  
 Co-Ax plug to Right Angle Co-Ax plug.  
 (Moulded Plugs)  
 Colour: GREY

	1+	10+
ORDER CODE: SO/350	£1-75	£1-50

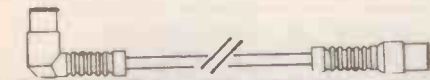

RESISTOR KIT - 1000pcs  
 Assorted values, including values that we have overstocks on. A minimum of 10 different values.  
 Absolute Bargain  
 1000 Resistors. All 0.25W Carbon 5%

ORDER CODE: SO/193 Price: £1-99

## IEC MAINS LEADS



IEC LEAD 250V 10A Right Angle  
 Made By BELDEN  
 This may be the highest quality lead available. Fully screened cable, moulded IEC socket one end with USA plug on the other.  
 To use in UK, simply cut off the USA plug and wire up a standard 13A plug.  
 At time of printing we have over 12,000 of these leads and therefore able to offer very attractive quantity prices.  
 Markings on cable: 18-3 Type SJT E-3462 LL-7874 Shielded GF  
 Colour: BLACK

	1+	10+	100+
Length: 2 Mts			
ORDER CODE: SO/307	£1-00	85p	60p

## SIEMENS



Ideal for Radio, Computer etc which require an electrical noise free supply. Each filter is constructed using toroidal chokes and a combination of safety X2 and Y capacitors configured in a delta formation.  
 Very high quality, Brand New never been used. These really are a bargain.

	1+	4+
ORDER CODE: SO/SIE/10A	£7-50	£7-00

## POWER SUPPLIES - EUROPEAN - 2 PIN

Manufactured by Commodore Business Machines (CBM) ltd. These power supplies are ideal for running radio's, cassette recorders, calculators etc etc. They fit the UK shaver adaptor (See our Electrical section). We have substantial quantities of these items and can offer attractive discounts for bulk buyers.

<p>TYPE: EOB -DC</p> <p>Input: 220/240V                  Output: 4.5V @ 200mA                  Plug: 2.5mm Jack</p> <p>SO/POW/EOB</p> <table style="width: 100%; border: none;"> <tr> <td style="width: 33%;"></td> <td style="width: 33%; text-align: center;">1+</td> <td style="width: 33%; text-align: center;">10+</td> <td style="width: 33%; text-align: center;">100+</td> </tr> <tr> <td>70p</td> <td style="text-align: center;">60p</td> <td style="text-align: center;">50p</td> <td></td> </tr> </table>		1+	10+	100+	70p	60p	50p		<p>TYPE: MM3-AC</p> <p>Input: 220/240V                  Output: 6V @ 200mA                  Plug: 3.5mm Jack</p> <p>SO/POW/MM3</p> <table style="width: 100%; border: none;"> <tr> <td style="width: 33%;"></td> <td style="width: 33%; text-align: center;">1+</td> <td style="width: 33%; text-align: center;">10+</td> <td style="width: 33%; text-align: center;">100+</td> </tr> <tr> <td>95p</td> <td style="text-align: center;">90p</td> <td style="text-align: center;">75p</td> <td></td> </tr> </table>		1+	10+	100+	95p	90p	75p	
	1+	10+	100+														
70p	60p	50p															
	1+	10+	100+														
95p	90p	75p															

JUST ARRIVED! Limited quantity....Hurry hurry...

FARNELL SWITCH MODE PSU - 240Watts G Series G12 20A  
 Seem unused, but no promises. These are in the current Farnell Electronics catalogue at over £395 each!!

INPUT: 115-120/240Vac OUTPUT: 8 to 12.6V 20A  
 Dims: 88 X 160 X 194

ORDER CODE: SO/432  
 SALE PRICE: £150-00 each!!!!!!

BULGIN FUSED TEST PROBES Red & Black  
 Made in UK, very high quality. robust moulded plastic, complete with a 1A 1 1/2" fuse fitted.

Length: 144mm Sold as a pair  
 Normal price is more than £4-00 per pair!

	1+	10+
ORDER CODE: SO/139 (per pair)	£1-20	£1-00

COMPUTER LEAD  
 A 7 pin DIN plug to 1 X 2.5mm Jack plug (Yellow)  
 1 X 3.5mm Jack Plug (Red)  
 1 X 3.5mm Jack plug (Black)

Lead length: Approx 2 metres.  
 1+ 10+

ORDER CODE: SO/194	£1-50	£1-25
--------------------	-------	-------



SPEAKER GRILL - Chrome - 12"  
 Very attractive chrome speaker grill with black rubber surround.

Robust construction made from 1.1mm thick steel.  
 Grill pitch: 11 X 11mm approx.

	1+	4+
ORDER CODE: SO/026	£3-00	£2-50

EPSON - Intelligent Printer Interface Boards.  
 Type: 8148  
 Suits Epson printer models: EX-800, EX-1000, LQ-2500 and SQ-2500 (Maybe others)  
 Integral 8kB buffer and self-test which can be used to provide either RS-232C or current loop capability.


Currently being sold in trade cats. at over £80!  
 ORDER CODE: SO/EPSON SALE PRICE: £25-00

EPROM SPECIAL - 27C256  
 Brand new, 250ns. Limited quantity, approx 800 pcs. First come first etc

	1+	10+
ORDER CODE: SO/EPROM	£3-00	£2-50

ORDER CODE: SO/EPROM £3-00 £2-50

<p>TYPE: EO9-DC</p> <p>Input: 220/240V                  Output: 6V @ 400mA                  Plug: 3.5mm Jack</p> <p>SO/POW/EO9</p> <table style="width: 100%; border: none;"> <tr> <td style="width: 33%;"></td> <td style="width: 33%; text-align: center;">1+</td> <td style="width: 33%; text-align: center;">10+</td> <td style="width: 33%; text-align: center;">100+</td> </tr> <tr> <td>£1-20</td> <td style="text-align: center;">£1-10</td> <td style="text-align: center;">90p</td> <td></td> </tr> </table>		1+	10+	100+	£1-20	£1-10	90p		
	1+	10+	100+						
£1-20	£1-10	90p							

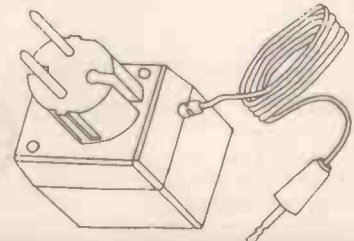




# SPECIAL OFFERS

5 1/4" Computer Disks - 3M  
 Type: 744 D-O SS DD  
 Single sided double density soft sector.  
 Limited qty, only a few hundred boxes. First come first served!  
**ORDER CODE: SO/636**      **PRICE: £2-00 per box of 10**


**MODEM LEAD**

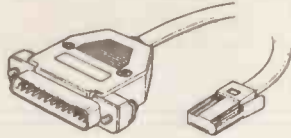

25 Way 'D' Plug connected to a BT 4 way plug.  
 Length: Approx. 3 Metres.

**ORDER CODE: SO/637**      **PRICE: £3-50**

**Adjustable Feet for Tube Fitting**

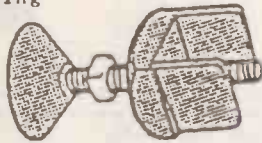

High quality feet for fitting to most makes of 25mm square tube. Each pack contains:  
 4 X Threaded Feet. 4 X Metal Cap. 4 X Tightening Nut. Current Trade price is £4-70 plus VAT per pack! Remember, all our prices include VAT.

**ORDER CODE: SO/638**      **PRICE: £3-00 per pack**

**CENTRONICS PLUG - MALE - 50 Way**  
 Amphenol Type: 226 B-50-U



50 Way plug (Without strain relief) Very high quality. Only a couple of hundred available.

	1+	10+
<b>ORDER CODE: SO/639</b>	£1-10	£1-00

**0.1uF 63V 5% Metallised Polyester Capacitor**  
 Very small capacitors, ideal where space is restricted. Overall width is only 7.5mm.  
 Lead pitch is 5mm.  
 We have a substantial quantity of these capacitors so if you use large quantities contact us now.

	1+	10+	100+	1000+
<b>ORDER CODE: SO/640</b>	5p	4p	3.5p	2.5p

**ITT- PLASTIC 25 WAY 'D' Cover with Jackscrews**  
 ITT-CANNON Type: DC77762-25



Maybe the highest quality on the market at a very low price. Current Trade Price is £1-16 plus VAT! Complete with integral Jackscrews and cable grip.  
 Colour: BLACK

	1+	10+
<b>ORDER CODE: SO/641</b>	70p	65p

**WIREWOUND POT 1watt 2K5**

AB Type: ABW1  
 Super quality,  
 Current price over £2-50 each.



**ORDER CODE: SO/642**      **PRICE: 50p each**

**Multi-channel Photodarlington Optocoupler**  
 Siemens Type: ILD32 8 pin DIL



2 input opto-coupler with darlington output  
 This device can be used to replace 4N32's or 4N33's in applications calling for several single-channel couplers on a board.

Continuous Forward Current.....80mA  
 Peak Reverse Voltage.....3V  
 Photodarlington Sensor (Load Circuit)  
 Power Dissipation @ 25°C Ambient.....150mW  
 Derate Linearly from 25°C.....2.0mW/°C  
 Collector (Load) Current.....125mA  
 Collector-Emitter Breakdown Voltage (BVceo)...30V  
 Emitter-collector Breakdown Voltage (BVeco)....5V  
 8 pin DIL package.

	1+	10+
<b>ORDER CODE: SO/643</b>	45p	40p

**INFRA-RED EMITTERS Type: OP161SLA**



T1 (3mm) Package.  
 Gallium arsenide infrared emitting diodes moulded in clear plastic, mini-axial package. The lensing effect of the package allows a radiation half angle of 8° measured from the optical axis to the half power point. Lead spacing is 0.100" (2.54mm) to allow mounting in standard sockets.

Continuous Forward Current.....50mA  
 Peak Forward Current (pulse width=lusec 300pps).....3.0A  
 Reverse Voltage.....2.0V  
 Power Dissipation.....100mW

At time of printing we have several thousand pcs of this item if you require large quantity's.

	1+	10+	100+
<b>ORDER CODE: SO/644</b>	45p	40p	25p

**PAIR - INFRA-RED EMITTER & DETECTOR**



T1 (3mm) Package.  
 No info on these pairs but we are fairly sure that the emitters are OP161SLA as detailed above with matching detector. But no promises!  
 Each pair is in a small holder.

**ORDER CODE: SO/645**      **PRICE: £1-00 per pair**


**0.01uF 2000V Wima Type FKP-1**

Tol: 5%  
 Width: 30mm    Height: 20mm    Depth: 11mm  
 Lead Pitch: 27.5mm



**ORDER CODE: SO/646**      **PRICE: 50p each**

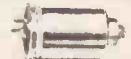**2200uF 63V Electrolytic PCB/Stud Fixing**



Dimensions: Dia. 35mm    Height. 50mm (Excluding thread)  
 Supplied complete with fixing nut and washer.

	1+	10+
<b>ORDER CODE: SO/647</b>	50p	45p

**2200uF 100V PCB Electrolytic**

Miniaturized versions ensures a saving of space in compact power supply design.. PCB snap-in terminals on a 10mm pitch for direct mounting into 2mm dia. holes. Super quality, super price!

**ORDER CODE: SO/310**  
**PRICE: £1-50 each**



We may purchase your excess stock! Contact us now.

# SPECIAL OFFERS

## MONITOR EXTENSION LEAD



15 Way 'D' Male to 15 Way 'D' Male

Length: Approx 9.5 Metres

ORDER CODE: SO/611

PRICE: £2-99

## COMPUTER LEAD



Amphenol 15 way D plug fitted to approx 1 metre of 13 way cable terminating in a 24 way 0.15" pitch double sided edge connector. (Edge connector type: TRW 50 24A-30) Edge connector can simply be cut off if not required.

ORDER CODE: SO/617

PRICE: £1-50

## MOULDED 13A PLUG & LEAD



A non-rewireable standard VOLEX 13A plug fused with 3A fuse, moulded to a 2 Metre length of 3 core 0.5mm cable. The free cable end has stripped conductors ready for fitting to your equipment.  
COLOUR: BLACK

ORDER CODE: SO/612	PRICE:	1+	10+
		£2-00	£1-75


## IEC MAINS LEAD - Right Angle - Belling Lee 6A 250V



SO/618

A non-rewireable right angle socket moulded to approx. 2 metres of 3 core 0.75mm cable terminating in prepared ends ready for wiring to your equipment.  
Length: 2 Metres      PRICE: £1-00 each      COLOUR: BLACK


## BT Type Line Cord - BT Approved

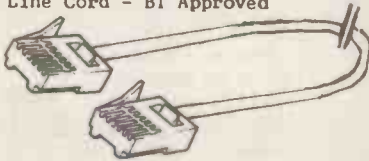

Line Cord, Plug to Plug. BT standard cord set used when modifying existing equipment. Plugs each end are 4 way.

LENGTH: 3 Metres	1+	10+	100+
SO/613	PRICE:	£1-25	£1-00
			88p

## COMPUTER LEAD

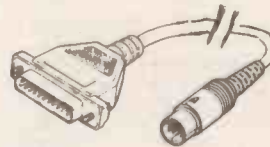


A 25 way 'D' plug fitted to approx. 1 metre of overall screened 9 way round cable with a metal 8 way DIN plug on the other end.

ORDER CODE: SO/619

PRICE: £1-00 each

## IEC MAINS LEAD Belling Lee UK 6A 250V

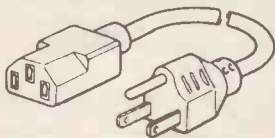

A non-rewireable IEC socket moulded to a 2M length of 3 core 0.75mm cable terminating with a USA plug. For UK use simply cut off USA plug and fit UK 13A plug.  
Rating: 10A @ 115V. 6A @ 250V. Colour: GREY

ORDER CODE: SO/614	1+	10+	25+
PRICE:	£1-50	£1-25	£1-10

## COMPUTER CURLY LEAD

A 15 way 'D' plug fitted to approx. 1 metre of black 4 core curly lead with prepared ends on the other end.  
Lead stretches to approx. 3-4 metres.

ORDER CODE: SO/620

PRICE: £1-00 each

## CAPACITOR SALE

2200uF 35Volt Ideal for power supplies. Super quality, made by Matsushita (Panasonic) in Japan. Only available while stocks last. RADIAL LEAD

Dims: Length 30mm, Dia. 16mm. Lead length approx. 30mm.


ORDER CODE: SO/621	PRICE:	1+	10+	100+
		50p	45p	35p

## L293B SGS Bridge Driver 16 pin DIL

Only a few hundred available at this once only price. 25 pcs to a tube.

ORDER CODE: SO/622	1+	25+	100+
	£1-50	£1-25	£1-00

## COMPUTER MODEM LEAD

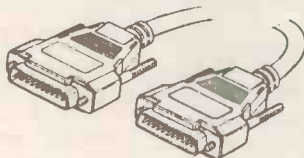

RS232 - RS232 25 way 'D' plug to 25 way 'D' plug. 9 pins connected.

Snap-fit covers allowing you to open and re-wire the pin configuration if required.

Length: 1.5 Metres (Approx)

ORDER CODE: SO/615

PRICE: £2-75

## EEPROM SALE (Yes EEPROM!)

General EEPROM characteristics include a minimum of 10,000 read/write cycles and data retention of 10 years.

NMC9346N National Semiconductor (Fairchild)

1K-Bit 1K(64 X 16) Serial NMOS EEPROM-byte erasable. 8 pin DIL. Vcc = 5V±10%

Normal trade price is £1-67 ea plus VAT!!

ORDER CODE: SO/623	1+	10+	100+
	£1-00	90p	75p



# SPECIAL OFFERS

**GOULD SWITCH MODE POWER SUPPLY 24V 1.4Amp**

Type: MMg24-1.4


No promises but most seem to be unused. Very high quality and now limited quantity left. Current list price is over £200 each.

INPUT: 110V-120V OUTPUT: 24V 1.4Amps  
220V-240V

Dimensions: 160 X 35 X 85mm



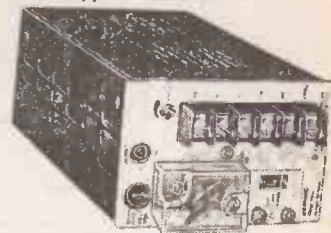**FARNELL G-Series Switch Mode Power Supply 60Watts**  
Farnell Type: G12 5S



Mostly still in sealed boxes. Unused and complete with full manual. This unit is still in production. Catalogue price over £200-00!!

Input: 240Vac

OUTPUT: 8-12.6V 5Amps

Dims: 88 X 60 X 165mm

ORDER CODE: SO/431

PRICE: £55-00

(Reduced from our Special price of £85-00!!)

Reduced from £90-00

ORDER CODE: SO/487 SPECIAL PRICE: £45-00

**WEIR SWITCH MODE POWER SUPPLY 50Watts**

MODEL: SMM 50/12 A24

Again, no promises but all these units seem unused. Still in original packaging. Complete with full spec. sheet & circuit diagram!!

(Available separately send £1 plus SAE)

INPUT: 98-132V OUTPUT: OP1: 5V  
196-264V OP2: +12V

OP3: -12V

OP4: +24V

(Fully cased)

These units just arrived and regret we have no current ratings yet.

Dimensions: 200 X 150 X 60mm

ORDER CODE: SO/WEIR/SMM PRICE: £17-50

**GREENDALE Switch Mode Type 19A-BOE-M137-TG**  
53 Watts

A partially cased unit made to commercial standard. Very high quality.

Dimensions: 195 X 125 X 60mm

Outputs are on flying leads.

INPUT: 120-240Vac OUTPUT: +5V @ 3A  
+12V @ 1A  
-12V @ 1A  
+24V @ 0.5A

ORDER CODE: SO/434 PRICE: £12-50



**CCTV MONITOR BOARD**

Weir Type: M5009/1

Custom built board by Weir UK. Board seems complete, has EHT unit fitted etc. All boards seem brand new. These really are a bargain DIMS: 200 X 160mm

ORDER CODE: SO/435

PRICE: £5-00

**BRANDENBURG Power Supply**

Type: 776AF

15KV @ 500uA

500Vdc out

Very high voltage, variable from 8.5Kv - 16Kv Made for REM & CRT application. 10 pins. SORRY, NO INFO! Hence low price. Current model over £250 each!

ORDER CODE: SO/433

PRICE: £35-00

**TRANSFORMER - 100VA**

High quality at a very affordable price. Only a 100 left, over 500 sold!

PRIMARY: 0-120v 0-120v

Secondary: 0-24v, 28v, 32v 36v, 100VA

Dims: H 120mm, D 90mm  
W 100mm

ORDER CODE: SO/470 1+ 10+  
PRICE: £5-00 £5-00

**WEIR - 120V @ 60Hz 200Watts**

Another custom built switch mode power supply manufactured by Weir UK. Again, made to the highest standard. Originally made for use in the USA hence the 120V input, however we know you have the technology to make use of these units!!!! So in return, a bargain price. Units are fitted with a 4 way molex plug - no extra charge. These units are fully cased.

INPUT: 120V OUTPUT: V1 +5V @ 4A  
V2 -5V @ 4.5A  
V3 +16V @ 3.4A  
V4 -16V @ 3.4A

The original cost of these units was over £200-00.

ORDER CODE: SO/WEIR/2 PRICE: £12-50

**ASTECSwitch Mode Power Supply 110watts**


Model: BM-41001

Once again, a commercial standard PSU. All brand new, just received another delivery, (Sorry higher price) but they still represent a REAL bargain. To date we have sold nearly 700 units!!


INPUT: 115-240vac OUTPUT: V1 +5V @ 3A  
V2 +38V @ 2.5A

Dimensions: 415 X 120mm

ORDER CODE: SO/ASTEC/BM4 PRICE: £12-00

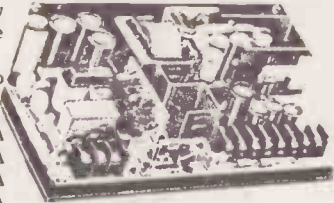

**GREENDALE**

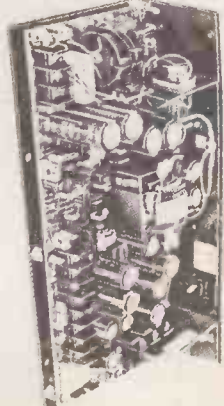

**TELECOM - Housing**  
Very smart, light tan in colour with dark brown base. Two 'quick fix' screws hold on cover. Many cut-outs both ends. Normal BT quality.

DIMS: 210 X 320 X 125mm

ORDER CODE: SO/462

PRICE: £3-50

# SPECIAL OFFERS

## SERIAL PRINTER CABLE



RS232 Ribbon cable. 25 way 'D' plug to 25 way 'D' plug.  
Length: Approx. 1.8Metres.  
ORDER CODE: SO/616 PRICE: £3-50

## SUFLEX - Lacing Cord Type R88W



These cords are specifically designed for the lacing of cable forms. The core of nylon braid ensures high tensile strength with small extensibility, and yet has sufficient elasticity under low loads to make a neat cable form. The outer PVC acts as a cushion preventing the cord from cutting the cable insulation.  
Colour: Black Reel Length: 500 Metres  
O.D. 1.1mm Working Load: 6.8Kg  
Current Trade Price: £13-11 per reel plus VAT!

ORDER CODE: SO/624 PRICE: £6-50 per reel

**BT 4 way plug to 25 way 'D' Socket Lead**  
A short lead, BT 4 way plug to 25 way 'D' socket using BT flat style cable. 4 core, pins 2,3,5 & 7 connected on the 25 way 'D'.  
Lead Length: Approx 175mm

ORDER CODE: SO/625 PRICE: 50p

## MULLARD TRIMMER CAPACITOR



Mullard type: 808 series. 2-40pF 250V  
Super quality at a very special price while stocks last!  
Mullard Code: 808-11409. Value: 2-40pF 250Vac  
Distributor price is 24p ea + VAT on 100's!!  
ORDER CODE: SO/626 

1+	10+	100+
PRICE: 25p	23p	20p

## MAINS SUPPRESSION CAPACITOR



ISKRA 0.1uF 250Vac X2  
A radial lead boxed metallised polypropylene mains suppression capacitor. Approved to VDE-0565 Class 2. Epoxy resin encapsulated in flame retardant plastic case. Iskra Type: KNB1532  
Dims: W 18mm. H 7mm. D 13mm Pitch: 15mm  
Tolerance: ±20%

ORDER CODE: SO/627 

1+	10+	100+
PRICE: 20p	18p	15p

## AVO PANEL METERS Type T60/2481



Marked 50-0-50uA  
Internal Resistance 400 ohm.  
Dims: 70 X 60mm (Approx)  
Zero adjustment on front of meter.  
As you would expect from AVO, made to the highest quality. Limited qty. available.

ORDER CODE: SO/628 PRICE: £6-50

**WANTED WANTED WANTED**  
We buy new surplus electronic components and equipment. Simply send your samples/list to our Head Office, attention The Managing Director.

## TOROIDAL TRANSFORMER 50VA Avel-Lindberg Ltd UK. Type: 40/4556



Input: 120V - 240V  
OUTPUT: 0-9v 0-15v Max. 25VA per winding.  
A PCB mounting transformer with twin primary and twin secondary windings fitted with a wound screen for safety and electrostatic screening. The transformer is encapsulated in a rugged thermoplastic case. This provides protection against mechanical damage and enables secure PCB fixing via a threaded bush moulded into the centre of the case.  
Dia: 95mm Height: 40mm. Mounting bush 2 X M4  
Weight: 893gms. The current dist. price is around £25-00 each. ALL ARE BRAND NEW STILL BOXED ETC.  
These really are a bargain. Hurry, only a couple of hundred available.

ORDER CODE: SO/629 PRICE: £12-50

## ITT PLASTIC 9 WAY 'D' Cover with Jackscrews ITT-CANNON Type: DE77762-9



Maybe the highest quality on the market at a very low price! Current Trade price is £1-05 plus VAT. Complete with integral Jackscrews and cable grip.  
Colour: BLACK 

1+	10+
ORDER CODE: SO/630	60p 55p

## MOTOR RUN CAPACITORS - 440V 5% TOL.



Stud mounting capacitors suitable for motor start/run and other similar applications. Connections via double 6.35mm tabs. Manufactured to BS5267.  
Current list price is over £6 each plus VAT!  
15uF 440V DIMS: 115mm X 45mm Dia.  
20uF 440V DIMS: 135mm X 45mm Dia.

15uF 440V ORDER CODE: SO/631 PRICE: £3-50 each  
20uF 440V ORDER CODE: SO/632 PRICE: £4-00 each

## STC 47,000uF 40V Electrolytic



Tag end STC capacitor.  
Date Code: 8512  
Dims: 115 X 65mm  
List price is over £8-50 ea plus VAT.  
ORDER CODE: SO/633 PRICE: £3-50

**8 pin DIN to 8 pin DIN Lead**  
All pins connected (Mirror Image) Plugs are Metal. Cable Colour is Black.  
Cable is overall screened.  
Length: Approx 1.5 Metre  
ORDER CODE: SO/634 PRICE: £1-00

## BULGIN Panel Mounting AA Battery Holder Takes 3 AA Batteries (Bulgin Type: B13/1)



Panel mounting battery holder. Flush fitting bayonet cap with coin slot for tightening. Mounting is from rear of panel, fixing by screws through front flange.  
ORDER CODE: SO/635 PRICE: £1-00 each









# SPECIAL OFFERS


We have a limited stock of Yuasa Sealed Lead Acid batteries which when checked at random found are not accepting a full charge. On the few that we have found to be like this we have found with patience, most eventually came up to full specification.

However, time is money as they say and so we are selling off these batteries at a very reduced price. We are selling these batteries with NO WARRANTY WHATSOEVER and therefore it is a case of taking a chance!

**NO RETURNS WILL BE ACCEPTED!**

The normal price of these batteries is approx. £16-95 each.

	1+	5+	10+
SO/656	£5-00	£4-50	£3-50

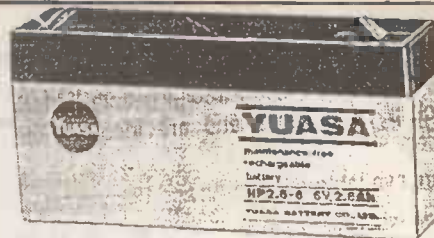

YUASA CODE: NP10-6      Dims: 101 X 151 X 50mm

Terminals: Spade Type.

Weight: 2.2Kg

6V 10Ah

### VIDEO/TV LEADS

A set of quality leads, originally manufactured for Granada.

5 pin DIN Plug to Phono Plug

BNC plug to Phono Plug.

Length: 2 Metres

ORDER CODE: SO/212

PRICE: £1-25

### VIDEO/TV Lead

Another set of quality leads.

BNC plug to Phono Plug

5 pin DIN plug to Phono Plug

ORDER CODE: SO/213

PRICE: £1-25

### 100VA Toroidal TRANSFORMER

100VA (Approx) transformer fitted into a smart metal case. Very attractive. Input is selectable.

Multiple Primary: 100V-250Vac

Secondary Voltage: 110V, 12-0-12v, 0-9v with screening

Limited quantity.

ORDER CODE: SO/657

PRICE: £9-99

### SHARP RADIO CASSETTE - Model QT-F10E

A super radio cassette Recorder offered at a fraction of the normal price.

Although some are refurbished they are all guaranteed by us for 3 months from date of purchase. In the unlikely event of any problem we would repair or exchange at our discretion.


Features include:

- \* Auto Stop
- \* Battery Operated (5 X AA) NOT Included
- \* Recording from Radio using Built-In Mic. is possible.
- \* Recording external sound is of course possible
- \* Earphone socket is fitted.
- \* FM Range: 87.6MHz - 108MHz
- \* AM Range: 526.5KHz - 1606.5KHz
- \* Some are complete with carrying case.

Limited quantity are available!

ORDER CODE: SO/658

PRICE: £12-50

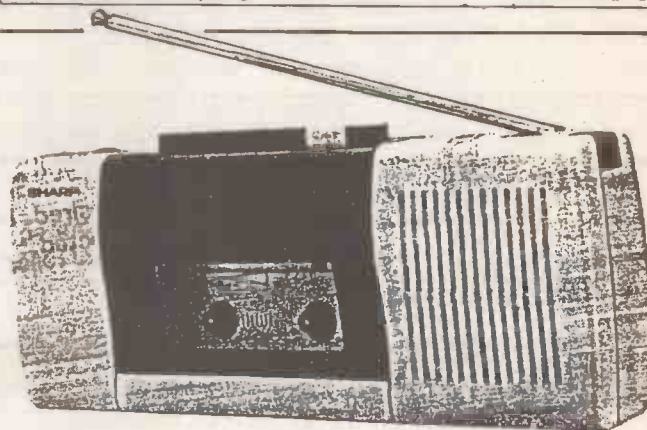

### B.T. MODEM UNIT

Brand new, still in sealed manufacturers packs. Sorry, no info but we have listed the major components on the 2 sandwich style boards.

Plug In: 1 X C875 1H-11 Intel. 40 pin  
3 X P8051AH-0121 Intel 40 pin

Soldered: 3 X LM348 1 X 74ALS74N  
1 X ULN2033A, 1 X ULN2002A, 1 X LF353  
1 X AD7528JN, 1 X AD7574KN

Assorted relays, BT Sockets, crystals switches.

Both boards are the same size: 160 X 100 X 55mm These really are made to the highest spec.

(Free prize to anyone who can supply original circuit info!)

ORDER CODE: SO/485

PRICE: £5-00 each

### GOODY BAGS

Contains a random selection of very assorted components including:

Resistors, Capacitors, Connectors, IC's, Diodes, Potentiometers, etc etc.

Sold by weight. Each bag weighs over 1Kg.

ORDER CODE: SO/660

PRICE: £1-99

### COMMODORE (CBM) Charger/Power Supply

A good quality power supply offering the electronics hobbyist/enthusiast the opportunity to purchase a quality unit that is fairly simple to alter the specification of, at a very attractive price. Plenty of room in the case to add zener's, voltage regulators etc.

Input: 220V-240V (Switchable)

Output: 7.2Vdc @ 225mA  
7.0Vac @ 45mA

DIMS: 100 X 55 X 60mm

Mains Lead: Approx. 400mm

Output Lead: Approx 2.25 Metres. Fitted with a moulded plug (Non-standard)

Several thousand of these units at time of printing.

ORDER CODE: SO/659

1+      10+      100+

PRICE: £2-99    £2-50    £1-99



ALL PRICES INCLUDE V.A.T.

ADD £2.25 P & P PER ORDER



# STOP CAR THEFT NOW!



**PROTECT YOUR CAR FOR ONLY £15-00!!**

**MADE IN UK**

## COMDEK ATL - CAR ANTI-THEFT UNIT

A brand new design, 100% designed in the Uk. A very clever device giving 100% peace of mind to the car owner and causing 100% frustration to the would be car thief! This unit may be used alongside an existing alarm or simply on its own.

Most alarms require the owner to activate them when you exit the vehicle, which can easily be overlooked or simply forgotten. The ATL circuit overcomes this by activating the moment the ignition is switched on or the vehicle is 'Hot Wired' making it impossible to forget. From the moment the ignition is first switched on the ATL circuit starts timing. When the engine has started the unit must be de-activated otherwise after a pre-set time the engine will simply cut out.

The method of de-activating the unit is set by the installer. We recommend either wiring up to one or more switches i.e. rear window de-mist, interior light, wipers etc. but you may of course wire it to a concealed switch. Therefore until the chosen switch/switches are 'switched' on/off, the ATL will **NOT** de-activate and the engine will stop after the pre-set time!

Every ATL is pre-set at approx. 21 seconds but this time may be shortened or lengthened to suit your requirements up to 130 seconds. This time governs how far your vehicle will travel before the engine cuts out.

Any car thief will then be faced with the problem of the engine cutting out and refusing to re-start. Simple. The thief will not wish to attempt to 'repair' the vehicle.

We also supply a red LED, which when installed in the car, remains lit all the time acting as a deterrent to any would be car thief.

Supplied in Kit form, full instructions etc. supplied.

ORDER CODE: CAR/COMDEK /KIT

PRICE:

1+                      10+  
£15-00              £12-00

**NOW AVAILABLE READY BUILT & TESTED**

**£24-99**

# MARCO TRADING

\*\*\*\*\* INCORPORATING \*\*\*\*\*

## EAST CORNWALL COMPONENTS

THE MALTINGS, HIGH ST. WEM, SHREWSBURY, SY4 5EN

TEL: 0939 232763

TEL: 0939 232689

FAX: 0939 233800

## BRANCHES

**SUPERTRONICS,  
65 HURST STREET,  
BIRMINGHAM. B5 4TE**

TEL: 021 666 6504

**WALTONS,  
55A WORCESTER STREET,  
WOLVERHAMPTON.  
WV2 4LL**

TEL: 0902 22039