

ELECTRONICS

December 1996 No. 108 £2.25

and Beyond

Britain's favourite monthly magazine for electronics

Heritage On a Chip



Community Radio A Christmas Cracker



Apple's PDA - A review



The Ring of Dazzling Light




Daresbury Synchrotron



FREE VOUCHER WORTH £2 Inside

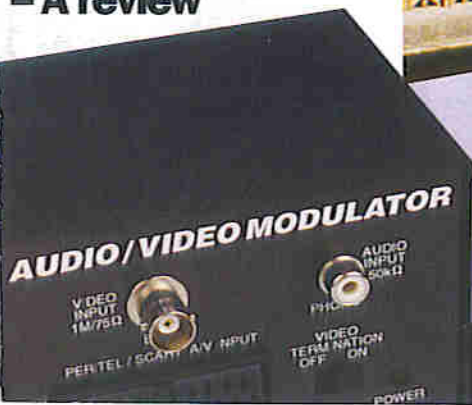24 PAGE EDUCATIONAL SUPPLEMENT
See inside for your free pull-out featuring educational circuits and products from Maplin MPS



Projects for you to make... Signal Activated Amplifier ♦ Audio/Video Modulator

Projects

- 18 Audio/Video Modulator**
A UHF modulator designed to allow a host of video equipment items with composite video/audio output signals to be made compatible with a domestic TV set tuner.
- 32 Signal Activated Amplifier**
A general-purpose amplifier that only switches on when it is needed – on application of an input signal. Incorporates a built-in trickle charger so its battery always remains ready for action.

Features

- 8 The Daresbury Synchrotron**
The Synchrotron Radiation Source (SRS) at Daresbury Laboratory near Warrington is the world's first dedicated high energy synchrotron radiation emitter – Douglas Clarkson describes its uses.
- 14 Low Cost Isolated Mains Control Interface**
Peter Bode reviews the design and operation of a general-purpose EMC mains inlet filter/power controller.
- 24 Radio Cracker**
Brian Adams introduces you to an organisation behind charity community radio stations, who aim to raise awareness of third-world issues and generate funds for relief and development work.
- 30 High Areal Density Disk Drive Technology**
Frank Booty reveals the magnetoresistive recording (MR) disk drive head technology that gave IBM a head start (!) in this competitive sector of the computing market.

- 40 Apple Notepad**
Martin Pipe reviews the original (and best?) notepad computer, the Apple Newton Personal Digital Assistant (PDA), and finds out what it's capable of.
- 46 Touch Key Technology**
In the second instalment of this series, Tony Ellis describes the construction of the Touch Key Hybrid Relay Board section of an electronic door access system.
- 49 From The Ashes of Angels Free Book Draw**
Enter our draw for your chance to win a copy of Andrew Collins' fascinating book.
- 50 The AC Power Supply**
Ray Marston explains the distribution of the domestic AC mains supply and the layout of wiring systems in homes.
- 56 Developing Applications around the PIC Architecture**
The second part of this series describes the PIC-microcontroller family and its generic characteristics.
- 64 Heritage on a Chip**
Alan Simpson describes the INFORM system, a handset that museum visitors can use to obtain a personal oratory on the artifacts seen on their tour. Plus! Enter our competition on page 66.

Regulars

- 2 News Report**
5 How to Subscribe
6 Back Issues
17 Comment
38 Air Your Views
62 What's On & Diary Dates
67 Classified Adverts
68 @Internet
71 Next Issue
72 Technology Watch



Cover pictures:
©Copyright 1996
Maplin Electronics PLC.
All rights reserved.

Editorial

Editor Robin Hall 9515, 649V
Technical Author Maurice Hunt 851C (Hons)
Editorial Assistant Lynda Hardy
News Editor Stephen Waddington 851G (Hons)
Drawing Office Ross Nisbet
Technical Illustrators Paul Evaris,
Kevin Kirwan Dico Comp.

Production

Production Controller Jason Hyatt
Design Layout Artist David Holt
Photography Co-ordinator Peter Blackmore
Photography Librarian Tracy Swann
Published by Maplin Electronics plc.,
P.O. Box 777, Rayleigh, Essex, SS6 8LU.
Tel: (01702) 554155, Fax: (01702) 554001.
Lithographic Reproduction by
Planographic Studios,
18 Sirdar Road, Brook Road Ind. Estate,
Rayleigh, Essex SS6 7UY.
Printed by St Ives (Andover) Ltd.,
West Portway, Andover SP10 3SF.

Management

Manager Paul Freeman-Sear 851C (Hons)
Marketing Services Manager Steve Drake
Product Manager Tony Bricknell.

Subscriptions

Maureen Harvey
Tel: (01702) 554155 Ext. 311.

Advertising

Advertisement Manager Paul Freeman-Sear
Tel: (01702) 554155 Ext. 288.

UK Newstrade Distribution

Seymour, Windsor House, 1270 London
Road, Norbury, London SW16 4DH.
Tel: +44 (0)181 679 1899.
Fax: +44 (0)181 679 8907.



Member of the
Audit Bureau of
Circulations.

Copyright 1996 Maplin Electronics PLC.

Copyright: All material is subject to worldwide copyright protection, and reproduction or imitation in whole or part is expressly forbidden. Permission to reproduce printed circuit board layouts, commercially or marketing of kits must be sought from the publisher.

Advertisements: Whilst every reasonable precaution is undertaken to protect the interests of readers by ensuring, as far as possible, that advertisements appearing in the current issue of Electronics and Beyond are bona fide, the publisher and staff of the magazine cannot give any undertakings in respect of statements or claims made by advertisers, whether on printed pages or on loose insert. Readers who have reasonable grounds to believe that they have been misled are advised to contact their local Trading Standards Office.

Editorial: The views of individual contributors/authors are not necessarily those of either the publisher or the editor. Where errors occur corrections will be published as soon as possible afterwards.

Publisher's Statement: Maplin Electronics PLC., take all reasonable care to prevent injury, loss or damage of any kind being caused by any matter published in Electronics and Beyond. Save insofar as prohibited by English law, liability of every kind including negligence is disclaimed as regards any person in respect thereof.

24



32



64



Inside

**Free pull-out
Educational
Supplement**

Contains details
of experimental
projects to build.

See centre pages

ELECTRONICS

THE MAPLIN MAGAZINE

and Beyond

Hello and Welcome to this month's issue of *Electronics and Beyond*! You will see that we have enclosed a 24 page editorial supplement in this issue. This will be the first of many that will contain articles for schools. We welcome any feedback from Technology Heads and pupils for possible inclusion.

This issue also includes a £2 money off voucher to save on purchases of £40 or over from Maplin Stores or on orders from mail order. Alternatively you can save it, together with last month's £5 voucher and receive a free gift when you take out a subscription to *Electronics and Beyond* (see page 5). Please note that this offer only applies to readers in the UK, and we cannot accept photocopies.

Stop Press

The Maplin Luton Catalogue Store is now open in the Arndale Shopping Centre, making it easier for enthusiasts in the area to obtain components and products.

Robin Hall, Editor



Britain's Best Magazine for the Electronics Enthusiast

NEWS

REPORT

Software makes Internet Phone Calls Easy

Software developed by Lucent Technologies is designed to give Internet callers quicker access to one another and allows them to converse via their computers as if they were on a regular speakerphone. Previous software has been half-duplex, similar to a radio channel, whereby one party must stop speaking before the other can use the line. Lucent plans to market the software to AT&T, the Bell companies and Internet service providers for distribution to their customers. By the end of the year, Lucent plans to enhance the software to enable users to video conference over the Internet.

For further details, check: <http://www.lucent.com>.
Contact: Lucent, Tel: (01344) 865900.



3DO Gets Out of the Hardware Business

Video game maker, 3DO has surprised the IT industry with its announcement that it will sell all or part of its hardware business by the end of the year, and concentrate instead on making game software for PCs and the Internet. The company has invested millions of dollars developing its Interactive Multiplayer, but was never able to compete effectively against Japanese rivals Sega and Nintendo. 3DO this month unveiled its first PC games, which can be played over the Internet and will come bundled with Netscape's Navigator Web browser.

For further details, check: <http://www.3do.com>.
Contact: 3DO, Tel: +1 (415) 261 3000.

Boom for Export Test Equipment

Orders for Racal's digital radio test equipment to the expanding GSM markets in the Far East have reached record levels. The company claims that the equipment supports both base station transceiver station (BTS) installation and the GSM infrastructure from countries throughout the region, where the growth in the number of digital cellular subscribers has increased at a rate of 105% per year since 1994.

For further details, check: <http://www.racal.com>.
Contact: Racal,
Tel: (01344) 388067.



Experimental 3D TV First

The Independent Television Commission and other members of the MIRAGE consortium have collaborated to produce what is believed to be the world's first stereoscopic 3D television program made for general viewing.

The 25-minute programme 'Eye to Eye' was made by TeleVirtual in association with AEA Technology and the ITC was shown publicly for the first time at the International Broadcasting Convention in Amsterdam on 12th September.

The programme is in the style of a documentary and was predominantly shot at the studios of Anglian Television in Norwich using digital production and a 3D studio camera. Three dimensional scenes range from Shakespeare to a shot from a rally car, using a miniature rugged 3D camera developed by the consortium.

The programme also includes scenes showing the potential for special effects, and a 3D virtual studio which looks realistic, but only exists as a model within a computer.

Nick Lodge, ITC's Head of Standards and Technology told *Electronics and Beyond*, "Digital Television will soon make it economical to deliver thousands of television channels to the home - far more than can be filled with traditional scheduled television programming. This is exciting because it will create opportunities for innovative and minority interest services, of which 3D television is just one".

"Although you need a special display, the feeling of actually being in the back of a rally car or at the exotic location in a travel log is quite an experience", added Lodge.

Contact: Independent Television Commission, Tel: (0171) 255 3000.

Long Life Blue-Green Lasers Could Double CD Capacity

A team of researchers at Sony's Research Centre at Yokohama in Japan has made a laser that could help to cram more information on to a compact disk. Several research teams are working toward the goal of semiconductor blue-green lasers, but until now, their lasers have been short lived.

In a paper in 'Electronics Letters' published by the Institution of Electrical Engineers (IEE) in the UK, Satoshi Taniguchi, Tomonori Hino, Satoshi Itoh, Kazushi Nakano, Norikazu Nakayama, Akira Ishibashi and Masao Ikeda of the Sony Corporation Research Centre report that they have made a laser that operated at room temperature for more than 100 hours. This is an improvement of about ten times on earlier lasers using the same materials.

"Requirements for higher density recording by optical disks and for thin and flat full colour displays are increasing", says Taniguchi. "Blue-green laser diodes could be the key device meeting these requirements", he adds.

Tiny lasers are used in compact-disk players and computer CD-ROM machines. Lasers detect digital information recorded as a series of pits in a reflecting surface. The amount of information that fits on a CD depends on the colour of the light used to retrieve it. Blue-green lasers can pack in at least twice as much information as the infra-red lasers in today's generation of CDs.

For further details, check: <http://www.iee.org.uk> or <http://www.sony.co.jp/CorporateCruise/News/96D-014E.html>.
Contact: IEE, Tel: (0171) 344 8403.



Motorola to Sell Mac Clones

Motorola is set to introduce a line of personal computers running Apple's Macintosh operating system, with plans to sell the machines throughout the world. The company is also introducing a new line of PowerPC-equipped computers running Microsoft's Windows NT operating system. The two product families are expected to merge into one by September 1997.

For further details, check: <http://www.motorola.com>.
Contact: Motorola,
Tel: (01753) 575555.

Fix-it Resolves Computer Conflict

Fix-it is a troubleshooting utility that automatically finds and fixes software conflicts and hardware configuration errors - the leading causes of Windows '95 problems.

On start-up, the utility from Quarterdeck automatically performs an inventory of the user's entire computer, including applications, games, utilities, Internet browsers, modems, network cards and drivers. The program looks for missing application files, conflicts between applications or hardware, improper settings and Windows system problems, such as invalid registry and system entries.

Targeted at Windows '95 users, the tool, priced at £39, compliments Quarterdeck's WinProbe '95 hardware diagnostics utility.

For further details, check: <http://www.quarterdeck.com>.
Contact: Quarterdeck,
Tel: (01245) 496699.

Network Computer Announced by IBM

IBM has announced its first network computer (NC), a sub-£400 computer platform for conducting Internet-based business. The IBM Network Station offers plug-and-play simplicity and an intuitive Windows-style graphical interface, but is managed through a server network for both Internet-related and traditional business applications. This can reduce hardware, software and management expense by 50 to 75% over traditional personal computers.

A recent Gartner Group survey said a networked personal computer (PC) costs about \$11,900 annually to own - including expenses for software upgrades and administrative services. IBM - like other manufacturers focused on building NC platforms - hopes to slash this cost.

For further details, check: <http://www.ibm.com>.
Contact: IBM,
Tel: (0171) 202 3799.

Windows Goes Palmtop

Microsoft's new Windows CE software looks and works like Windows '95, but is designed to run on limited-memory, hand-held computers. More than 40 hardware and software companies, including Hitachi, Hewlett-Packard, SkyTel, Casio Computer and Symantec have endorsed the new system, and Casio and HP have said they will use Windows CE in new hand-held devices. The machines will be able to share information with Windows-based PCs and link to the Internet using Microsoft's Internet Explorer software.

For further details, check:
<http://www.microsoft.com>

Contact: Microsoft,
Tel: (01734) 710021.

Guide to Mobile Communications

Toshiba has launched a free guide to mobile communication, called 'The Complete Guide to Mobile Data'. The guide provides an insight into how the mobile data market has developed, covers the current status of the various technologies in use and offers an insight into the way in which these technologies will continue to develop and mature.

For further details, check:
<http://www.toshiba.com>

Contact: Toshiba,
Tel: (01932) 828828.

Beat Commuter Misery

Tube and rail strike misery and the knowledge that the average commuter spends almost a working day commuting each week is enough to make many more people want to work from home.


To help those who are tempted, Telework, Telecottage and Telecentre Association (TCA) have worked together with Hewlett-Packard, Lloyds Bank, BT, insurers Tolson Messenger and the European Union to produce the first comprehensive Teleworking handbook.

This book, priced at £13.95, gives advice on every aspect of working from home - from business ideas to company teleworking. It also offers guidance on telecottage centres, where homeworkers have access to computers and hi-tech equipment plus a special section for disabled teleworkers.

According to the Department of Transport, London commuters take an average of 57 minutes to get to work - adding up to ten hours a week, which is more than a working day. Throughout the rest of the country, the average travel to work time is almost half an hour - adding up to five hours a week.

For further details, check:
<http://www.tca.org.uk>

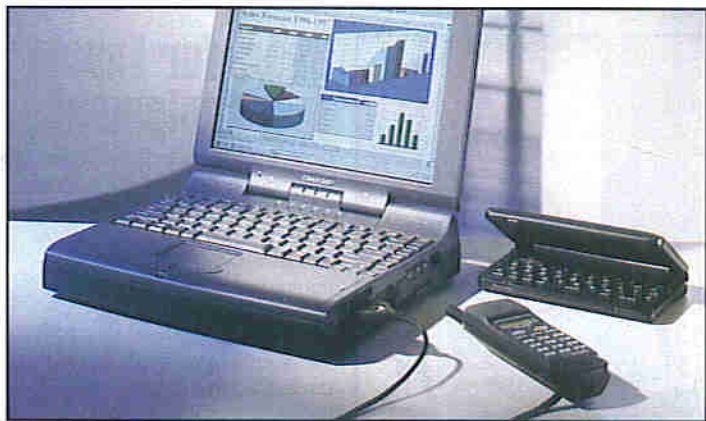Contact: Telework, Telecottage and Telecentre Association,
Tel: (0800) 616008.



Sharp Notebooks at Sharp Price

The number of people that can afford to spend £3,000 upwards on a portable PC must be fairly limited. Clearly, Sharp is more optimistic about the purchasing power of its target audience for its two new notebooks, the PC-9040 and PC-9070.

So what does £3,000 buy you? Sharp reckons to have developed the next generation portable PC.

The machines do have a neat colour display, a fast processor, CD-ROM drive and internal

sound systems, but are lacking in basics such as a fax/modem and rapid battery recharge capability, which you'd expect for this price.

But to be fair, Sharp is offering a three year return-to-workshop warranty which features helpdesk, fax, courier collection and return delivery at Sharp's cost with a five working day turnaround.

For further details, check:
<http://www.sharp-usa.com>

Contact: Sharp,
Tel: (0161) 205 2333.

BT Launches Windows Phone Disc

BT has introduced a Windows version of Phone Disc - the range of CD-ROM based telephone directory services providing access to the 17 million listed UK business and residential numbers.

Aimed at customers searching more than 20 numbers per week, the Windows Phone Disc works with Windows 3.1 and is available in either stand-alone or networked versions. The annual version is priced at £199, while the networked version costs £400 per quarter.

For further details, check:
<http://www.bt.com>


Contact: BT, Tel: (0800) 919199.

Arm Gets Speech Recognition Capability

Motorola's Lexicus Division has ported its small-memory speech recogniser to the Advanced RISC Machines (ARM) family of microprocessors. The ARM-based speech recogniser has demonstrated 99-8% accuracy in quiet, office environments. Other tests have shown it to have an average recognition rate of 96% in high noise environments, such as in a car with the stereo on and the windows open.

For further details, check:
<http://www.arm.com>

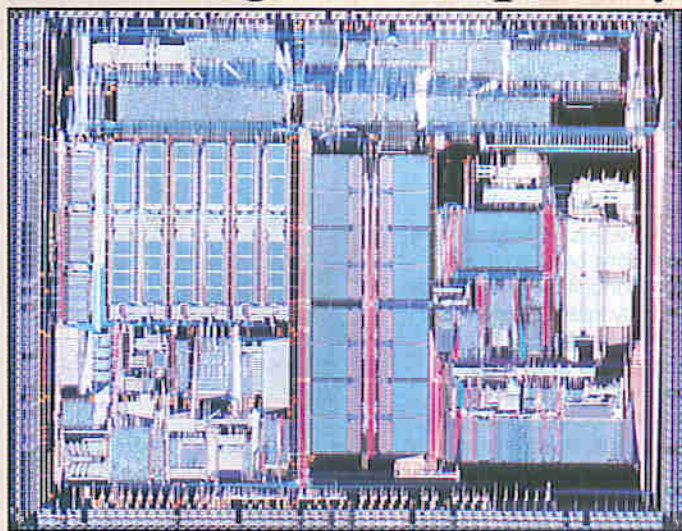Contact: Advanced RISC Machines,
Tel: (01223) 400400.



Stronger ARM

Digital has announced new versions of its StrongARM SA-110 microprocessor that take StrongARM performance beyond 250 million instructions per second (MIPS). The new versions of the StrongARM SA-110 microprocessor operate at 233MHz and 166MHz. The SA-110 233MHz processor couples the large, on-chip cache and fast bus interface of the original SA-110 with a higher-speed pipeline to deliver performance estimated at 270 Dhrystone 2.1MIPS, five to ten times that of competitively priced devices.


For further details, check: <http://www.digital.com> or <http://www.arm.com>

Contact: Digital,
Tel: (01734) 868711.

Serial DAC offers Lowest Power

Maxim, has launched a serial 14-bit digital to analogue converter which operates from a 1.5V supply, and consumes a minimal 1.5mW of power. The MAX545 handles digital data via a 3-wire interface, compatible with SPI, QSPI and Microwire standards. For bipolar operation, the device has scaling resistors which work with an external precision op-amp, such as the MAX400. On start-up, unwanted output voltages are cleared by an internal power-on reset circuit which clears the DAC output to 0V, when a voltage is first applied.

Contact: Maxim, Tel: (01734) 303338.

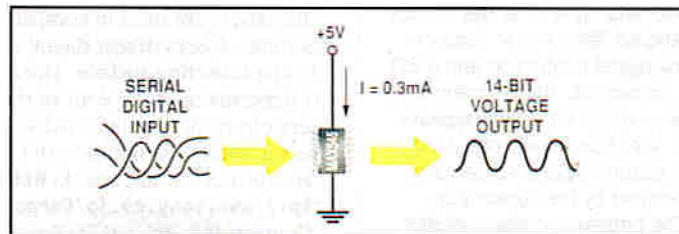

Save £2 on your next purchase from Maplin or claim this Twin Spot PIR worth £18.17 when you subscribe to

ELECTRONICS

and Beyond

Lamps not included with free gift. Code YE28F



Cut out the voucher below to use at Maplin stores or return the voucher with the claim form and the £5 voucher printed in last month's issue to claim your free gift when you subscribe to *Electronics and Beyond*.

The MICRO MODULE
A NEW LOW COST controller
that gives you customisation
for as little as **£95** one off + VAT



For users of PCs, 8051 & 68000

and that's just the half of it!..

FEATURES

- 16/32 bit 68307 CPU for fast operation
- Up to 1 Mbyte of EPROM space onboard
- Up to 512Kbyte SRAM space onboard
- 32 Kbyte SRAM fitted as standard
- RS232 serial with RS485 option
- MODBUS & other protocols supported
- Up to 22 digital I/O channels
- 2 timer/counter/match registers
- I C port or Mbus & Watch dog facilities
- Large Proto-typing area for user circuits
- Up to 5 chip selects available
- Program in C, C++, Modula-2 & Assembler
- Real Time multitasking Operating System
- OS9 or MINOS with free run time license option
- Manufacturing available even in low volumes
- A full range of other Controllers available

P.C. 'C' STARTER PACK AT ONLY £295 + VAT
The Micro Module will reduce development time for quick turnaround products/projects and with the P.C. 'C' Starter pack allow you to start coding your application immediately, all drivers and libraries are supplied as standard along with MINOS the real time operating system all ready to run from power on. The 'C' Starter pack includes: A Micro Module with 128 Kbyte SRAM, PSU, Cables, Manuals, C compiler, Debug monitor ROM, Terminal program, Downloader, a single copy of MINOS, Extensive example software, and free unlimited technical support all for £295.

CMS

Cambridge Microprocessor Systems Limited

Unit 17-18 Zone 'D', Chelmsford Rd. Ind. Est., Great Dunmow, Essex. U.K. CM5 1XG
Phone 01371 875644 Fax 01371 876077

Experimenting with PC Computers

A beginner's introduction to the design of simple electronic circuits, writing of assembly language programmes and interfacing to a PC computer.

- * 300 page book 240 by 270 mm with wire binding to open flat. Learn as you experiment, there's no boring preamble.
- * Special circuit board with 470 sockets, no soldering. Interfaces to PC using a standard printer lead.
- * Special software written to complement the book. Combined text editor, assembler & single stepper. The friendliest machine code assembler ever written.
- * Construct circuit & software for flashing LED. Experiment with resistors, capacitors & diodes. Build interface, write oscilloscope software. Display temperature graphs & audio waves.
- * Learn to programme almost without realising.

Telephone 01255 862308

For full details.

High quality 300 page book £24 (£3 pp per order)
Kit 1a, plugboard, components, BrunWord MCA £46
Kit 1b, as kit 1a + digital multimeter + tools £79

Brunning Software

138 The Street, Little Clacton, Clacton-on-sea, Essex, CO16 9LS.





Photo 1. Aerial view of the Daresbury Laboratory. The SRS is housed in the large building to the right of the main car park.

CLRC

The Ring of Dazzling Light:

THE DARESBUURY SYNCHROTRON

by Douglas C


The Synchrotron Radiation Source (SRS) at Daresbury is the world's first dedicated source of light.

Daresbury Laboratory is part of the Council for the Central Laboratory of the Research Councils and is a 'twin' with the Rutherford Appleton Laboratory at Didcot (see Issue 104).

Photo 1 shows an aerial view of the laboratory. The SRS is housed in the large building to the right of the main car park.

Since its completion in the 1970's, numerous other synchrotrons have been completed around the world. In Europe,

the 6GeV AERF facility has been completed at Grenoble in France. Several others are in the process of construction in Pacific Rim countries such as Japan. The technology of superconducting magnets has made it possible to build considerably more compact synchrotrons for specialist applications such as the SRS system developed by Oxford University with considerable input from the SRS team at Daresbury.

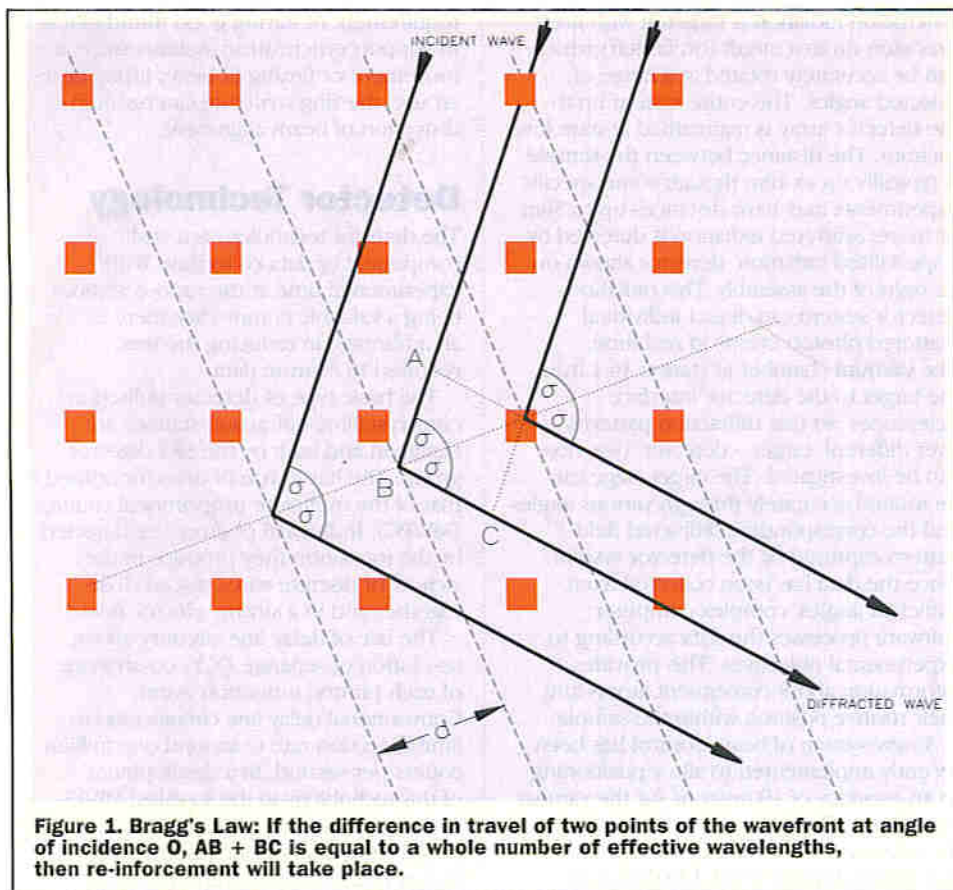

The simple Bragg equation allowed the structure of many inorganic structures to be rapidly determined. The technique of determining molecular structure based on such x-ray diffraction patterns has steadily developed from the 1920's. Complex software packages have been developed to analyse diffraction patterns by spatial arrangement and relative intensity.

The Daresbury Laboratory has been a key player in the development of a range of software packages for specific application areas in x-ray crystallography. Several software systems have developed under the wing of so called Collaborative Computational Projects (CCPs) at Daresbury.

Thus CPP4 is a collaborative group involved in protein structure analysis with over 310 installed sites around the world. Also CCP14 provides a framework for software for powder and single crystal diffraction with CCP13 being developed for analysis of polymer and fibre diffraction. Thus researchers in these fields have today access to considerable accumulated scientific expertise.

The Daresbury Synchrotron

Electrons are initially injected into the ring at a relatively low energy of 600MeV from a small storage ring which in turn is supplied from a conventional linear accelerator. The electrons may be introduced as a single 'packet' or as a series of packets distributed evenly round the ring. The choice depends on the nature of the experiment being undertaken. A total of 160 electron bunches can be injected into the SRS electron beam. The relative bunching of the electrons determines the periodicity of pulses of radiation produced at each radiation extraction point.

Electrons are normally injected into the ring at the beginning of the day and ramped up to an energy of 2GeV. Once the electrons are ramped up to this level of energy it is not possible to top the beam up since these would only be injected at 600MeV and could not be sustained in the field geometry of the 2GeV electrons. There is some residual loss of electrons due to scattering from the beam and from collision from residual gas molecules within the vacuum chamber.

When the electrons are initially introduced into the main ring, the field strength of the dipole bending magnets is sufficiently strong to maintain the beam within the ring. As radio frequency power is supplied to the various accelerating stages the velocity of the electrons increases towards the speed of light and the mass of the electrons increases also in accordance with relativistic calculations. During this process the field strength of the magnets is increased to maintain beam geometry.

electron is given up in a series of atomic collisions as the electron experiences violent de-accelerations. A component of the loss of energy of the electron at each stage is converted to photons of corresponding x-ray energy.

When an electron passes through a strong magnetic field the particle can experience a force the magnitude of which is proportional to the field strength and the electron velocity. Maximum force is experienced where the field direction is at right angles to the velocity of the electron. This component of force introduced from a magnetic field can cause a sufficiently energetic electron to radiate electromagnetic radiation.

This is the principle of the synchrotron which usually consists of a ring of elements to accelerate electrons and with bending magnets to flip the output of one accelerating stage into the axis of acceleration of another. The 'ring' is typically a regular polygon.

X-Ray Diffraction

A key property exploited extensively by the SRS at Daresbury is that of x-ray diffraction where x-rays are scattered off patterns of atoms. It was the German physicist Max Von Laue in 1912 that first

demonstrated patterns produced by diffraction of an x-ray beam through a crystal. Von Laue had anticipated such a phenomenon as analogous to the diffraction obtained with light diffraction patterns. However, Laue's group was unable to relate the patterns obtained to the geometry of the diffraction crystal. In England, Sir Lawrence Bragg was in his mid twenties and completing his studies in Physics at a time when his father was investigating the ionisation of gases by x-rays. The keen young mind of Bragg junior was able to relate the patterns obtained by Laue to reflections from planes of atoms within the crystal structure.

Figure 1 indicates photons incident at an angle θ to a crystal plane direction in a crystal. If the path difference $AB + BC$ is an integral number of wavelengths, then the diffraction radiation will re-inforce. This condition, known as Bragg's Law can be expressed as:-

$$2 d \sin \theta = n \lambda \quad n = 1, 2, 3 \dots \dots (1)$$

where d is the vertical separation of the crystal planes, and λ is the effective wavelength of the x-ray radiation.

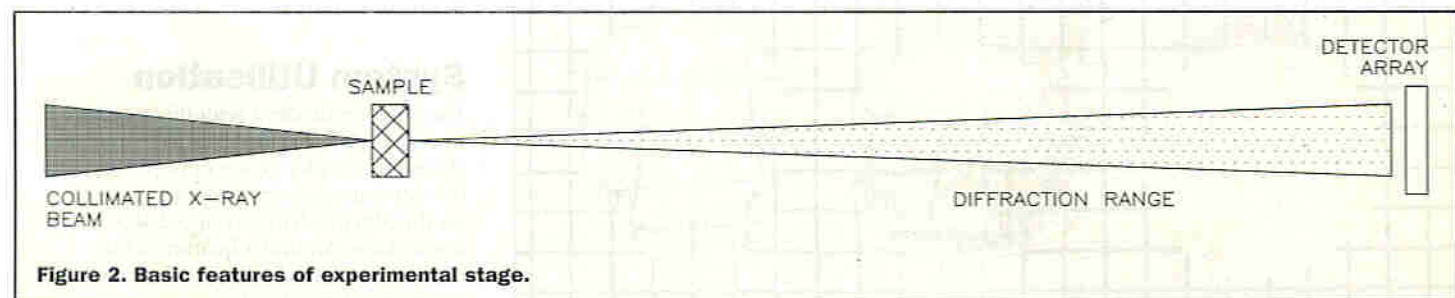


Figure 2. Basic features of experimental stage.

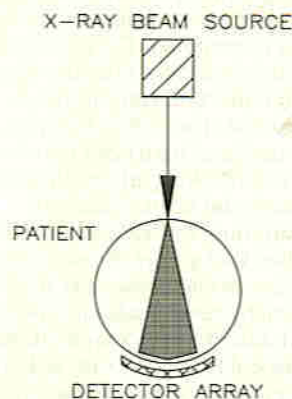


Figure 3. Basic principle of the CAT scanner.

At each of the 16 dipole points the electron beam radiates intensely over a broad range of electromagnetic wavelengths as indicated in the SRS data curves in Figure 5. Ten of these ports act as 'pick up points' for the radiation emitted by electrons bent in the magnetic field. These in turn act as inputs to around 30 experimental stations.

While the number of conventional bending dipoles is determined by the essential synchrotron geometry, it is also possible to include so called 'insertion' devices in the configuration in the straight sections between the bending dipoles. These insertion devices act to locally perturb the electron beam in order to produce additional sources of synchrotron radiation.

The so called 'undulator' magnet is essentially a stack of permanent magnets that introduces a field that produces a periodic field pattern. Such a configuration produces a narrow beam of soft x-rays. The so called 'wiggler' magnet uses superconducting technology to produce field perturbations to produce x-rays of higher energy. The system at present supports one undulator magnet and two 'wiggler' magnets (see SRS W16 curve of Figure 5).

When the SRS at Daresbury was initially designed and constructed, the technology of such insertion devices had not been anticipated. In more modern systems, the length of the straight sections has been significantly increased to facilitate the inclusion of such devices both initially and in any subsequent upgrades.

One of the stations, SRS station 16.1, supplied by x-rays from a wiggler device is shown in Photo 3. In summary, the station resembles a shooting gallery in a vacuum as indicated in Figure 2. The output from the

synchrotron radiation is targeted with great precision on to a target (on far left) which can be accurately rotated at a range of selected angles. The entire system up to the detector array is maintained at ultra low vacuum. The distance between the sample is typically up to 10m though some specific experiments may have distances up to 50m or more. Scattered radiation is detected by a specialised radiation detector shown on far right of the assembly. This radiation detector system can detect individual scattered photon events in real time. The vacuum chamber at station 16.1 from the target to the detector interface 'telescopes' so that diffraction patterns over different 'target - detector' distances can be investigated. The target stage can be rotated accurately through various angles and the corresponding diffracted field pattern captured by the detector system. Once the data has been collected from sufficient angles, complex computer software processes the data according to experimental objectives. This provides information about constituent atoms and their relative position within the sample.

A new system of beam control has been recently implemented to allow positioning to an accuracy of 10 microns for the various beam lines. This has involved increasing the accuracy of measurement of beam line position using 16 bit A/D detectors compared with previous 12 bit devices.

The drift of the beam is primarily due to thermal cycling of the SRS over the 24 hour period. There is increasingly a key

requirement of having good foundations to support synchrotron systems since any movement or flexing of heavy lifting gear around the ring structure can result in distortion of beam alignment.

Detector Technology

The detector technology is a vital component of data collection. With experimental time at the various stations being a valuable commodity, there is an advantage in reducing the time required to capture data.

The basic type of detector utilised in con-crystalline diffraction stations are designed and built by the SRS detector group. The basic type of detector utilised is that of the multiwire proportional counter (MWPC). Individual photons are detected by the ionisation they produce in the vicinity of discrete wires placed close together and in a strong electric field.

The use of delay line circuitry allows resolution of separate (X,Y) co-ordinate of each photon ionisation event. Conventional delay line circuits tend to limit detection rate to around one million counts per second. In a development of this technology in the so called MW13 system, separate instrumentation on each channel now allows an increase in speed (in theory to 200 million events per second).

An additional development is that of RAPID the fast 2-D detector system where ultra fast A/D data capture on each detector co-ordinate allows data


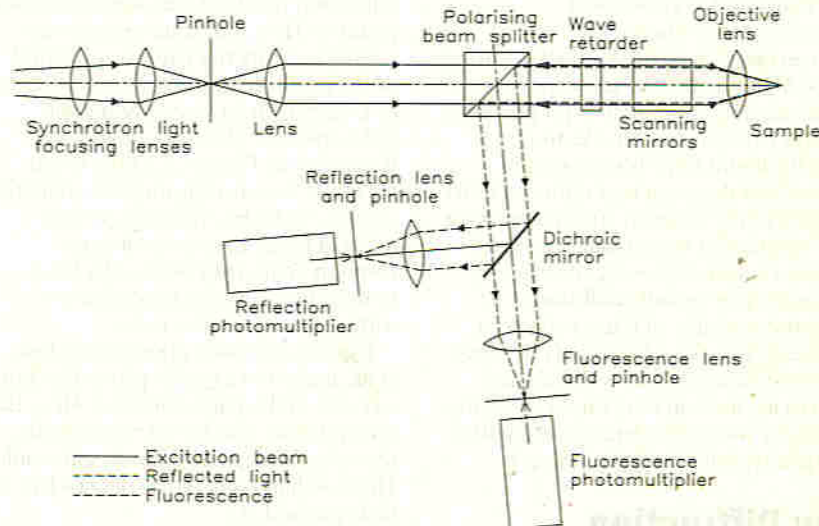


Figure 4. Operational diagram of SYCLOPS.

Photo 2. Right to left, normal, aspirin-inhibited and glycated lenses in vitro. The SRS source is used to determine how the process of glycation may be triggered by sugars or inhibited by agents such as aspirin.

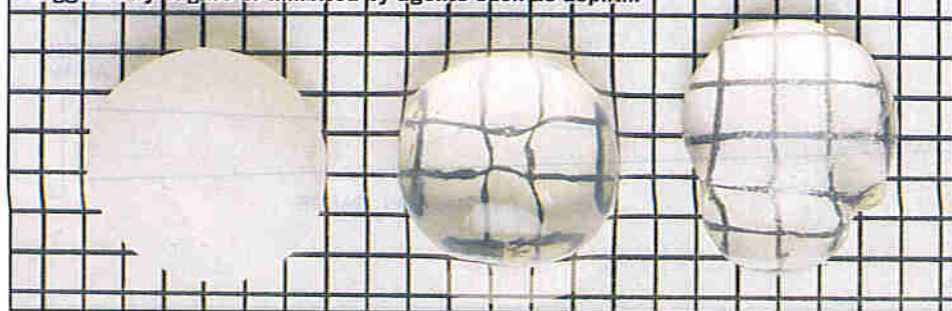

capture at rates of up to 10 million events per second and with positional spacing of 1/8th of the spacing between the wires or stripes.

System Utilisation

The trend in modern scientific research is to utilise well developed facilities that are shared by a wider group of users. Around 600 separate projects at present take time on the SRS involving around 2,400 researchers. Around a quarter of this activity originates from outside the UK as summarised in Table 1.

Country	% of Non-UK Use
Belgium	4
Germany	26
Denmark	4
Netherlands	15
Greece	1
Italy	12
France	13
Portugal	4
Spain	16
Ireland	5

Table 1. Summary of percentage of non-UK use of SRS for periods during 1994. Also, the SRS is used across a broad range of disciplines.

Utilisation of the SRS facility is relatively high with an operating efficiency of 88.4% with allowance for injection time of the beam. The facility is run for around 6,000 hours per year. Each of the experimental stations is managed by a specific local 'manager' who ensures that beam characteristics meet the specification of users of the system.

Safety Considerations

As the beam is introduced into each experimental 'hutch' for the process of data collection, the high levels of ionising radiation require all workers to withdraw behind doors and wall lined with thick layers of lead. Special attention has in particular to be paid to adequate sealing of doors to ensure that radiation does not leak out. Also, cables and controls between control rooms and 'hutches' require to be routed through special purpose conduit enclosures to prevent radiation leakage.

Unravelling Photosynthesis

One of the earliest functions developed by bacteria in the 'primeval soup' was the process of photosynthesis where photons of light from the sun are used as 'energy' to initiate chemical reactions. A group at Daresbury Laboratory in association with researchers at Glasgow University has succeeded in determining the molecular structure of the light harvesting complex of a purple photosynthetic bacterium - *Rhodospirillum rubrum*. This organism can be readily found as a purple scum on polluted waterways in North America. Studies of this most ancient of organisms, have revealed the elegant way in which incident photons of light are captured by the harvesting complex.

The reaction centre of the bacterium cannot manage photosynthesis on its own due to incident light photons. It depends on the harvesting complex to collect and distribute energy to it in sufficient amounts to enable it to achieve conversion of the chemical ATP. The 'chromophore' regions in the light harvesting complex rapidly absorb individual photons. The energy from a specific photon is in turn channelled through other chromophores until it eventually is made available at the central reaction site.

The proteins involved in the photosynthesis process reside in the actual membrane of the bacteria. The

isolation and collection of such cell membrane proteins is a notoriously difficult procedure necessitating the use of exceedingly minute samples. Use was made at Daresbury of 'wiggler' station 9.6 of the Synchrotron Radiation Source. This station is primarily used to its very high output levels of x-rays to obtain the data in the diffracted x-ray patterns.

The efficiency of the light harvesting of the bacterium approaches 95%. A total of 8 light harvesting complexes (LH2) are configured round a single LH1 complex. Light energy is captured within the peripheral centres and raise the energy at the reaction centre. Thus even a so called crude organism is actually a masterpiece of molecular engineering.

Probing the Tissues of the Eye

The transparency of the cornea and the lens are crucial for effective vision. A range of clinical disorders can render these finely balanced optical structures non-transmitting to light. With an aging population, such problems are likely to increasingly manifest. Considerable work, primarily funded by the Medical Research Council, has been undertaken to investigate how various agents may be able to block such processes of tissue degeneration.

When 'normal' clear corneal tissue is probed using the synchrotron radiation, a highly ordered pattern of bundles of collagen is observed - like logs in a log pile all aligned in the same way. An imbalance of sugars in the body, associated for example with diabetes, tends to disrupt this high level of ordering, so that while the chemical composition of the strands of collagen remains similar, the physical arrangement of the strands of collagen is more random and accordingly less transparent. In fact, the sclera, the 'white' of the eye, is chemically indistinguishable from the normally clear corneal tissue.

The process of 'glycation' has been studied extensively at Daresbury in order to determine its specific mechanisms and also to investigate how it can be prevented. Photo 2 indicates, right to left, normal, aspirin-inhibited and glycated lenses in vitro. Glycation is inhibited by paracetamol. The use of aspirin and paracetamol is relevant only in the scope of understanding the blocking mechanism that they possess in such laboratory experiments. There is no suggestion that any level of such over the counter medicines will protect against the glycation process 'in vivo'. Such basic research could one day, however, lead to the prevention or better management of such disorders.

Discipline	% SRS Allocation
Material Science	28
Engineering	1
Biology	18
Chemistry	28
Physics	25

Table 2. Typical allocation of SRS beam time between main disciplines during 1994



Photo 3. SRS station 10, which is fed by a high performance wiggler device.

The main component of the human lens consists of a range of proteins known as crystallins. The human eye contains a high proportion of gamma - crystallin. This in turn makes the lens relatively hard and less easy to distort during the process of fine focusing as the radius of curvature of the lens is changed.

The structure of delta - crystallin, the key component of the lenses of birds and which has recently been solved by workers at the SRS provides for a softer lens and one which is better adapted to rapidly changing shape to accommodate transitions between air and water environments in diving birds.

Clear corneal material is often used to effect a corneal transplant. The use of the synchrotron radiation at Daresbury has helped improve the outcome of corneal transplants. By 'reading' the axis of the direction of alignment of the collagen fibres in excised corneal transplants and matching this to the natural direction in the eyes receiving such transplants, the number of failed transplants has been significantly reduced.

Investigating Parkinson's Disease

A range of neurological disorders are thought to be associated with abnormal accumulation of various metals in brain tissue. While Alzheimer's disease tends to be linked with Aluminium, Parkinson's disease is thought to be associated with abnormally high levels of Iron. Thus while in a normal adult brain, levels of iron will typically be at a level of 50 micro grammes per gramme of tissue, in Parkinson's sufferers this figure can rise to values five times higher.

A neuroradiologist at Newcastle General Hospital and a team of researchers at Daresbury have used the synchrotron radiation source

to try to identify the molecular form of iron in Parkinson related tissue. A complex molecular structure will tend to absorb x-ray photons in a way which is characteristic of atoms present and also their relative positions. Using the technique of Extended x-ray Absorption Fine Structure (EXAFS) the profile of the absorber was obtained using absorption data from the synchrotron beam. The experimental data obtained matched that of Ferritin - a complex molecule containing up to 4,500 iron atoms. This confirms that the additional iron is held in this molecular form. Parallel work using electron microscopy was also able to identify the physical appearance and distribution of Ferritin within brain tissue samples. While not directly solving the mystery of the development of this disease, the information obtained is however significant for researchers in this field.

Looking at Catalysts

While proponents of green technology can easily describe what they would like by way of clean, non-polluting processes it is often left to the scientist to patiently research new chemical reaction processes to bring this about. This is especially true in the case of advanced catalyst design.

The SRS has been used at Daresbury to optimise the configuration and test the performance of a series of so called ALPO catalysts - a branch of the zeolite family of catalysts. Attention has in particular been directed to the formulation of CoALPO-18 and its performance in reactions such as the production of propylene and ethylene when methanol is introduced into its reactive zones. The development of catalysts using conventional 'trial and error' technology can lead to lengthy development times for such products. By using the SRS at various stages of catalyst function, it is hoped that optimised products can more

rapidly be developed. The development of such catalysts is obviously of major commercial importance to several key industries.

Microtomography

So called CAT scanners are now widely used in hospitals to image the internal composition of patients. The basic principle of the CAT scanner is indicated in Figure 3. An x-ray source delivers a narrow beam of x-ray radiation through the patient while rotating round the axis through the patient. At the same time the detector array rotates with the radiation source. The relative absorption at co-ordinates within the body is then calculated using so called back propagation algorithms. Such a technology can typically produce a resolution of the order of a mm - the characteristic of the size of features that can be distinguished.

The technique of microtomography takes advantage of superb geometry of the x-ray beam to image much smaller structures in a non-invasive way, entirely analogous to scanning a patient. Synchrotron radiation between 6keV and 30keV is typically used in this application with resolutions around 20 microns, some 50 times better than the conventional CAT systems.

A technique such as microtomography has obviously wide application. Initially the system has been used to investigate insect physiology. There is also interest in determining the structure of sandstone associated with oil deposits. This can provide valuable information regarding the scope for oil extraction from such strata.

SYCLOPS

The wide range of wavelengths of intense radiation available from the SRS has allowed development of a specialist confocal microscope system called SYCLOPS. Use is made of radiation between 200

and 700nm with appropriate interference filters being used to select a narrow band within this broad range.

The action of the confocal microscope is to image in selected planes through a sample. The SYCLOPS has been developed jointly by the Engineering Research Council (SERC) and the Netherlands Organisation for Scientific Research (NWO). The function of SYCLOPS is shown in Figure 4.

Using the confocal technique, images can be obtained from 'slices' across a specific cell. In this way, information on the spatial arrangement of components such as chromosomes within a cell can be obtained.

Using the mode of single bunching of the synchrotron, it has been possible to direct light to samples as small as individual cells in order to monitor biochemical activity. Even though laser technology has increased the range of lasers available and extended their range of wavelengths and output modes, the SRS provides a more flexible source of photons to investigate complex biological structures.

Investigating Muscle

One of the most basic of biological processes must surely be that of muscle contraction. Having such a key role in the universal scheme of things it might be assumed that all the associated processes involved had been solved years previously. Apparently, however, this is not the case. Recent work at Daresbury, however, using the high performance experimental station 16.1 has provided new insight into the process of muscle contraction.

X-ray diffraction is used to detect images from muscle in the relaxed and the contracted state. This in turn provides information on the change in ordering within the large molecules making up muscle. It is thought that muscle consists of myosin and actin filaments. The myosin possesses arm like branches which in the relaxed state are aligned about 60 degrees to the axis of the myosin filaments. When the muscle receives an electrical stimulation, the arms move forward to bind to the actin and in so doing the fibres slide past each other, causing the muscle to contract. Thus the combined strength manifested by muscle is made up of countless separate molecules/molecular interactions.

Making Plastics Attractive to Bugs

Nature, it seems, has many a solution to a range of problems of pollution. Each year at present around 100 million tons of plastic ends up on rubbish tips or dumped in landfill sites. Looking to the future, ICI is using the Daresbury SRS to investigate the properties of plastics created during a process of fermentation using sugars and specialist microbes. The plastics formed during such processes are in turn biodegradable.

The basic plastic product of this process BIOPOL is being extensively tested using the SRS source. It has been determined that the temperature at which BIOPOL is processed is a key parameter that determines its biodegradable properties.

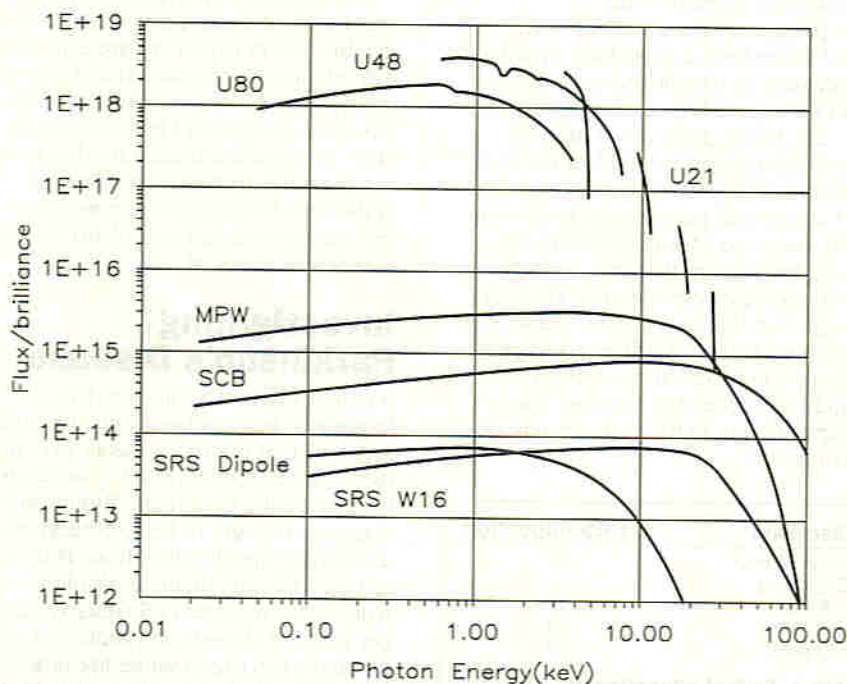


Figure 5. Estimated beam characteristics of DIAMOND compared with existing SRS system.

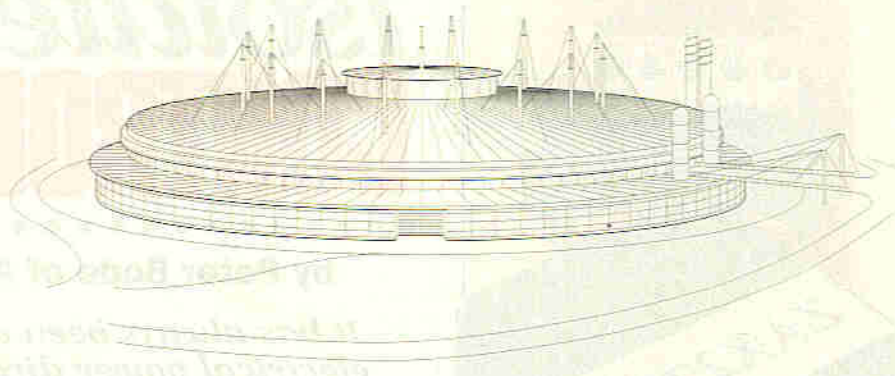
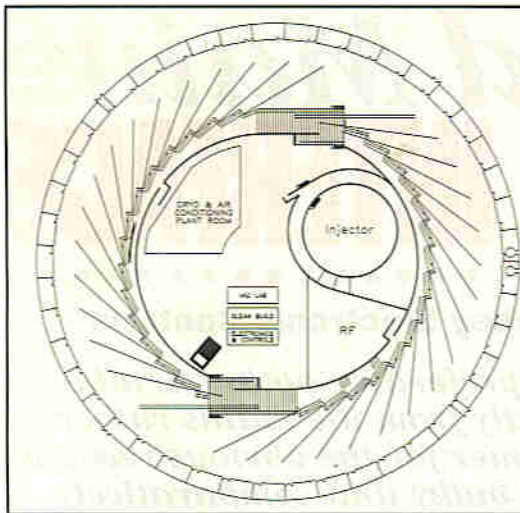


Figure 6. Anticipated design of DIAMOND.

The x-ray diffraction images obtained from samples processed at various temperatures provides a valuable indication of how molecular structures are configured with a view to optimising the manufacturing processes to develop a wide range of environmentally friendly plastics.

It should also be noted, that this specific process of plastic production involves primarily agriculture. Does this provide for another crop such as sugar beet to be grown on 'setaside' land to provide the necessary raw materials.

Crystals of Cobra Venom

Nature has provided the Cobra with an exotic cocktail of proteins in its venom, all of them poisonous. In an effort to develop new drugs to block the action of these neurotoxins, scientists at Daresbury are using the SRS to investigate the structure of one of the deadliest proteins present in cobra venom.

Using venom extracted from snakes kept at the Liverpool School of Tropical Medicine, the proteins in the venom are purified and crystallised prior to x-ray scattering investigations. This allows researchers to build up a picture of the overall protein structure with the prospect in the future of designing new drugs to block the action of the neurotoxin. The unravelling of the secrets of cobra venom developed in turn over countless millennia, will, however, take some time to unravel.

The Future's Bright – The Future's DIAMOND

The initial go ahead to build the SRS was given in 1975 and became operational on schedule during 1981. After some 15 years of high levels of utilisation, plans are being made for a new facility DIAMOND. With engineering specifications of DIAMOND now at an advanced stage, methods of funding are actively being investigated. The earliest the new facility could be completed by is estimated to be 2001, by which time the existing SRS will be over 25 years old. Figure 6 shows the present design of the DIAMOND facility and which it is hoped will be built at the existing Daresbury site.

Parameter	DIAMOND
Electron energy	3GeV
Beam current	300mA
Lifetime	20h
Circumference	338.4m
No. of cells	16
No. of bends	32
Bending field	1.4 Tesla
No. of insertion devices	12

Table 3. Key parameters of proposed DIAMOND system.

Figure 5 provides a useful comparison of the performance of the existing SRS and those proposed to use in the DIAMOND facility.

In the figure the data for SRS is that of the existing dipole magnets that bend the beam at each intersection between accelerating elements and SRS W16 is the existing performance of the superconducting wiggler (W16). The line SCB is the estimated performance of DIAMOND's superconducting bending magnets. It would be possible as part of a partial upgrade of the SRS, to use such bending magnets within the existing SRS structure. The line MPW indicates the performance of DIAMOND's multipole wigglers. The sections prefixed U indicate advanced undulatory sections of DIAMOND.

DIAMOND therefore provides considerably higher beam intensities and also extends significantly the top end of energy of delivered photons. It also provides more flexibility for addition of new insertion devices during any subsequent development.

Summary

The continual development of the beam parameters of synchrotrons and also detection systems together with sophisticated methods of numerical analysis has made such work with synchrotrons a key tool for the investigation of a broad range of physical phenomena. In particular, work in material sciences has especially benefited. It is to be hoped that the UK can maintain its eminent position in synchrotron based research and build upon its solid achievement of the past 20 years.

Further Information

Annual Report 1994 to 1995, Synchrotron Radiation Department, CLRC.
Annual Scientific Reports 1994 to 1995, Volume 1, Synchrotron Radiation Department, CLRC.
Annual Scientific Reports 1994 to 1995, Volume 2, Synchrotron Radiation Department, CLRC.

Points of Contact

Public Relations,
 Mrs. Mary Jacks, Daresbury Laboratory,
 Daresbury, Warrington, WA6 4AD.
 Tel: (01925) 603000.
 Fax: (01925) 603100.

Internet Sources

Within the high energy physics community, the Internet is hardly a new phenomenon. The research facility at CERN, Geneva, has played a key role in its development. As a first point of contact, the home page of the Daresbury Laboratory is <http://www.daresbury.ac.uk>. This is a useful point of contact for many more displayed topics.

Contacts for Specific Topics

Unravelling Photosynthesis
 Dr. M. Papiz. Tel: (01925) 603388
 e-mail: m.papiz@dl.ac.uk

System Utilisation
 Mr. P.D. Quinn. Tel: (01925) 603261
 e-mail: p.d.quinn@dl.ac.uk

Probing Tissue of the Eye
 Dr. K. Meek. Tel: (01865) 328185
 e-mail: k.meek@open.ac.uk

Parkinson's Disease
 Dr. B.R. Dobson. Tel: (01925) 603325
 e-mail: b.r.dobson@dl.ac.uk

Looking at Catalysts
 Dr. G. Sankar. Tel: (0171) 409 2992
 e-mail: sankar@ri.ac.uk

Microtomography
 Dr. B.R. Dobson. Tel: (01925) 603323
 e-mail: b.r.dobson@dl.ac.uk

SYCLOPS
 Dr. M. Tobin. Tel: (01925) 603584
 e-mail: m.tobin@dl.ac.uk

Detectors
 Dr. R. Lewis. Tel: (01925) 603544
 e-mail: r.lewis@dl.ac.uk


DIAMOND
 V.P. Suller. Tel: (01925) 603209
 e-mail: v.p.suller@dl.ac.uk

ELECTRONICS

Isolated Mains CONTROL INTERFACE

by Peter Bode of Abbey Electronic Controls

It has always been a preferable option to take electrical power directly from the mains rather than through a transformer for the obvious reasons that transformers are bulky and comparatively expensive items in electronics. In many cases where a transformer has been used it has been necessitated by either the need for low voltage isolation or the need to control a load that is unavoidably mains rated. The ZAX27™ can perform either role.

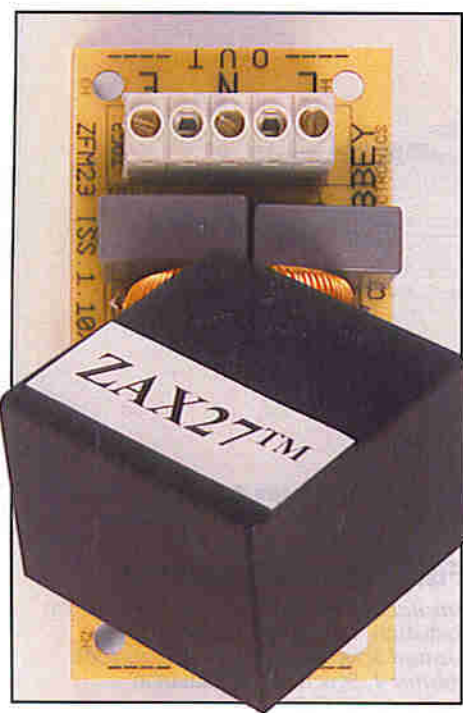

It is a fully isolated and elegant device for the accurate control of alternating current voltage of any amplitude up to 300V rms. It achieves this through a DC control voltage. The concept and principle of operation is quite simple as shown in Figure 1. Low voltage on one side of the module, high voltage and load on the other with the low voltage controlling or modulating the high voltage and providing total electrical isolation. In the simplest sense, the ZAX27™ could therefore be considered as a very compact infinitely variable isolating transformer. It is of course much complex and more versatile than that (as we shall see) and whilst the transformer is passive, the ZAX27™ is active.

The device operates in two modes, Phase Mode and Burst Mode. Which mode the device operates in is selected simply by the appropriate logic on a single MODE pin. An ingenious scheme allows certain pins to perform more than one function simply by applying different voltage levels to the pin. This has allowed the functionality of the ZAX27™ to be expanded without incurring extra I/O overhead.

Phase versus Burst Control

Both phase and burst control are well established methods for controlling alternating current voltages. Phase control is more versatile and suitable to a wider range of situations than is burst control. It however has the major disadvantage of being intrinsically very noisy. Where the electrical noise generated can not be eliminated (due to power level, for example) its use may be precluded by a suitable EMC filter such as the ZFM23/2k5 EMI Mains Inlet Filter (Stock Code CK24B).

Burst control on the other hand does not suffer from noise in the same way as phase control. It can work with full half sine wave cycles. This makes it possible to ensure the turn on point always coincide with the zero crossing point thus eliminating the main source of noise in phase control. Burst control is however inherently slower in response than phase control and is only suitable for systems with relatively fairly large inertia such as heaters, some motors, and the like. It would not for example be used in lamp dimming where there would be visible and very much unacceptable flickering.

Operation

The principle of operation is quite simple and follows the pattern that makes all well known components easy to use – predictability, precision, a well defined output for a defined input. The rms value of the AC output is a computable function of the value of the applied controlling DC voltage and the input AC voltage. The ZAX27™ maintains its output as a fixed ratio of the applied input voltage, the ratio being determined by the level of DC voltage applied to the device's control pin 5.

The DC voltage achieves this control by regulating the conduction phase (in phase mode) of the switching element of the ZAX27™ or (in burst mode) by proportionally allowing a number of half cycles of mains power to the load. Applications for the ZAX27™ include many mains operated devices which are able to work with phase or burst control. Among these are all resistive and inductive elements as well as some capacitive ones. The control of such elements directly from a microprocessor or microcontroller is now possible through the ZAX27™.

Closed Loop Application

The device has a further advantage in that it can also be used in a fully isolated closed loop design providing even better control than is possible with other controllers that work with similar principles. To aid in such applications, it has an integral, fully uncommitted, operational amplifier which can be used as an error amplifier or comparator.

Output Inhibit

In addition, the device has an in-built fully isolated load current regulation input which can be configured to limit either the peak or average load current. On the low voltage side, the ZAX27™ has an inhibit input which prevents any output from it when the pin is taken high, whatever the voltage is on the control input.

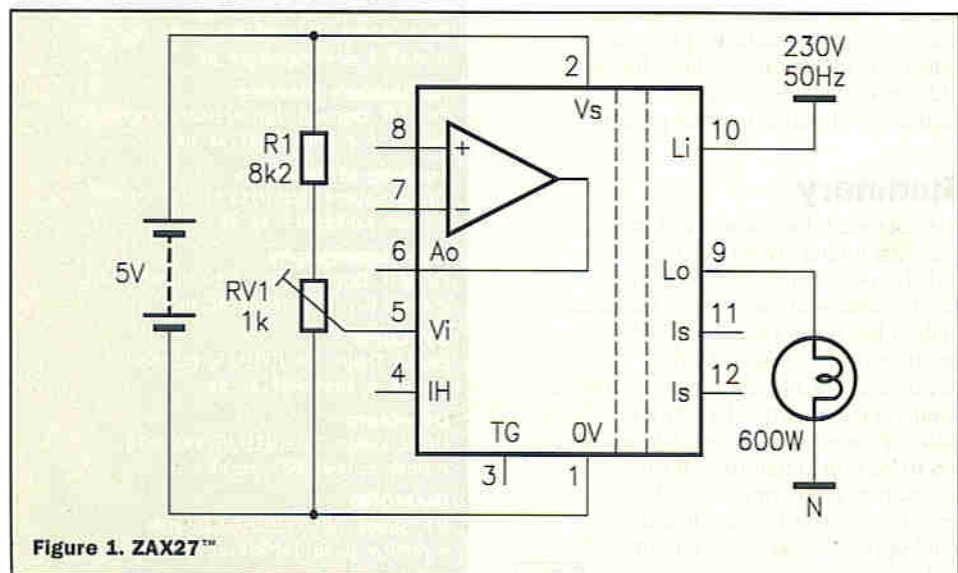


Figure 1. ZAX27™

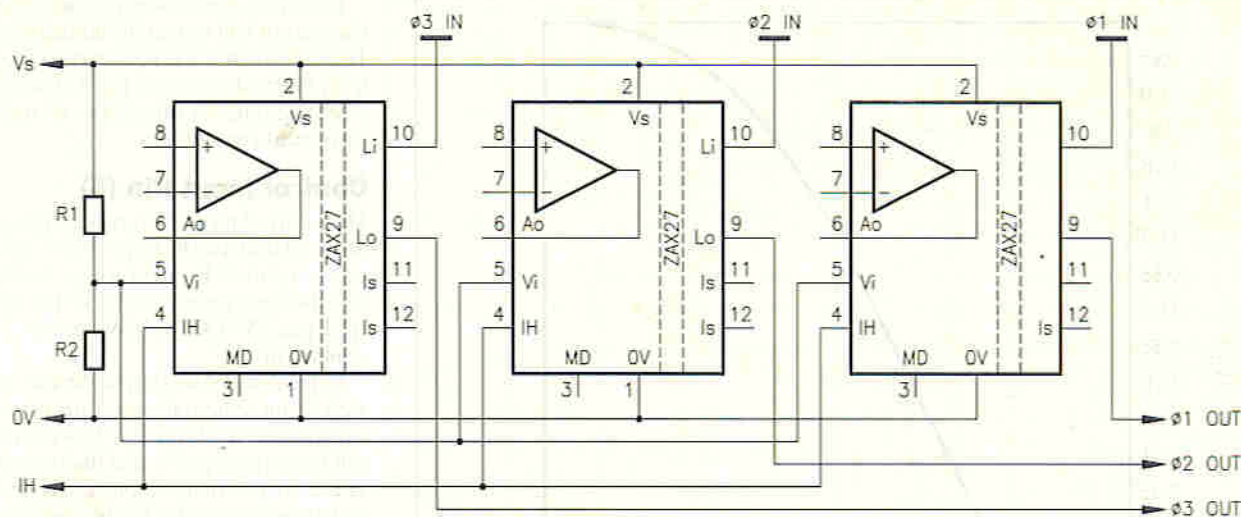


Figure 3a. Driving multiphase loads with the ZAX27A.

$$P_o = k \cdot V_i \cdot P_{max} \quad (2)$$

Where

P_o is the average power to the load, v_i is the control d.c. input which can be varied from 0 to 1V or 5V. k is a circuit constant (nominally unity), P_{max} is the maximum available power to the load.

The DC voltage achieves this control by 'burst' firing the switching element of the ZAX27™ on and off within a defined time frame or time base. Within this time base (nominally 1 second), the ZAX27™ switches its output on and off with a fixed mark/space ratio determined by the value of v_i as shown in Equation 2. The ZAX27™ is also zero-crossing switching. This means it will only switch its output on or off when the mains is passing through its natural zero. This virtually eliminates any noise that could be associated with mains switching and it is this single fact that may make the ZAX27™ a must in many applications.

The ZAX27™ only switches on and off once within a time base period. Furthermore, the minimum conduction period is determined by one half cycle of the mains which, for a 50Hz mains, is 10ms. This means the resolution of the ZAX27™, when operating with a time base of 1s, is 1% which is very good. Resolution in this case is defined as the ratio of the minimum incremental conduction period divided by the time base. On the other hand, switching on and off once every second may be too slow for some applications.

Provision is therefore made for variable time base on the ZAX27™. The minimum time base is 100ms which allows a maximum of 10 half sine waves and provides therefore a resolution of 10%.

The mode pin 3 on the device serves the dual purpose of allowing the time base to be varied thus increasing or decreasing the reaction time of the ZAX27™ but correspondingly reducing or increasing the resolution. For example, reducing the time base to half a second will increase the reaction time to half a second but this also reduces the resolution to 2% which is still good enough for most applications. If an application only needs a resolution of, say, 10%, the time base could be decreased to 100ms offering a faster reaction time.

The mode pin thus provides means for optimising the speed/resolution parameters for any given design if these matter. The time base can be varied between 100ms to 2.5s.

Figure 3a shows how the output drive capability of the ZAX27™ can be easily boosted. In this case the drive capability is limited only by the triac rating. The circuit shown for example will drive a 48kW load. Note that snubbing provision is not shown in any of the examples and some EMC suppression measure will also need to be taken depending on the load and topography of the construction.

The ZAX27™ is not restricted to driving single phase loads but can easily be configured also for multiphase loads. The illustrated example in Figure 3b is for a three phase application and it is obvious how this can be extended to other number of phases. Multiphase applications have particular advantages such as improved power delivery, frequency multiplication allowing smoother operation of machinery or lower smoothing requirements. It will be noticed in this example that there are three non-committed operational amplifiers which may be used to carry out other circuit control functions.


Figure 4 shows a typical closed loop application of the ZAX27™ (phase mode). The ZAX27™'s amplifier is used as an error amplifier to compare the reference set by R1, D5 with a sample of the output voltage. It then controls the supply to the transformer to maintain a constant output DC supply irrespective of load and mains supply variations.

As wide variations of mains supply is no problem the circuit is also suitable for automatic mains supply adjustment for appliances designed for global usage a feature only provided with expensive switch mode power supplies. Another advantage of this application is that it automatically compensates for transformer load regulation problems, an important consideration in the design of power supplies. When used as a pre-regulator at the front end of a linear supply, a very high efficiency linear supply can be realised whilst producing savings in reduced heatsink size and overall volume.

ZAX27™

The ZAX27™ is available from Maplin (Order As CK23A) £29.99 inc. VAT. EMI Filter ZFM23/2k5 (Order As CK24B) £11.99 inc. VAT.

Figure 4. Suggested circuit for regulating the output of a DC power supply.

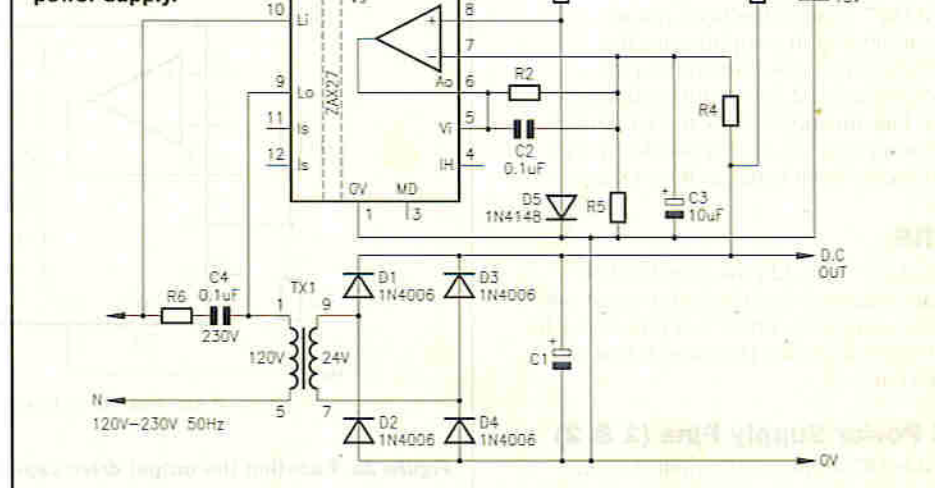

COMMENT



by Keith Brindley

Penetration of satellite broadcast television services is still increasing at a phenomenal rate throughout Europe. While it has been unusual to see more than just a handful of satellite dish aerials on houses in the average British street, if numbers of installations continues at the present rate, it's going to be the norm rather than the exception shortly, to have a dish.

In the UK, where there are some 23 million television-viewing households, nearly 4 million of these households have a satellite dish. This is an almost one in five situation. Penetration is expected to increase, of course, over the coming months in the run-up to Christmas.

In Europe, the situation is similar, although only one country beats the UK's penetration, in both numbers and percentage. Germany has nearly 38 million television-viewing households, and an almost unbelievable 10 million of them have satellite dishes.

The remainder of European countries fall a long way short of the UK and Germany in satellite penetration, but the trends are apparent, and are expected to increase rapidly over the coming years. Over all of Europe, with 162 million television-viewing homes, there are 25 million homes with satellite dishes installed.

Some European countries indirectly lend themselves to satellite dish installation more than others. Mountainous regions, for example, benefit from satellite broadcasts more so than flat regions. Flat regions, too, usually benefit from easy installation of cable television systems which can alleviate the need of satellite broadcasts altogether. Also, different governments invest different amounts in technology and its facilities. So, the picture across the continent depends on physical geography and political geography, as much as any country's desire to have satellite television.

Most current satellite broadcasts are by pretty conventional means, and the future looks rosy for them as they are. On the other hand, the launches of Astra satellites 1E and 1F in October 1995 and April of this year (as well as the future launch of Astra satellite 1G next year) bode good for future forms of satellite broadcasting too. By next year, there'll be 56 digital transponders available for use by several hundred digital television broadcast channels. The wide choice is expected to create a market surge

of customers who want satellite dish installations. Needless to say, the satellite industry is very excited over the digital prospects, and what the future holds for us all.

2001

I've looked at the problem in the past in *Electronics*, of course, but it's getting closer (the year 2000, that is) and the situation shows no sign of abating. For the few readers who aren't aware, I'm talking about what's going to happen to computers around the world which may be affected on 1st January 2000. It appears that many computers' in-built clock dates will revert back to 1900 and cause untold havoc to computer systems worldwide. To those of us with a computer built to handle the new millennium, this might all seem like a big joke, but (seriously) in fact, there is a Government sponsored agency (Taskforce 2000) which is advising UK companies on the matter.

And, as if computers themselves aren't enough, Taskforce 2000 has warned companies who manufacture goods with embedded microcontrollers in them (and let's face it, there are embedded microcontrollers in most electronically controlled appliances these days) that the new millennium could prove a difficult time for them too. Just imagine, your videocassette recorder, set to record the midnight striking of Big Ben on New Year's Eve 1999 could be the first time transporter, allowing you to record television programmes from as far back as the year 1900 – before television was even invented. Yes, I'm being facetious.

Actually, the problem is serious. It's estimated that some 80% of IT systems will be affected by the change of millennium. If yours, or your company's will be affected (you can check to see what happens to a computer simply by changing the date temporarily) and if you or your company rely on it for livelihood, then you need to do something about it. Certainly makes me glad I've an Apple Macintosh.

Surfing Blues

The public telephone network is being put under strain from Internet users who hang on the telephone line. Telephone networks were originally designed for voice calls of short duration. Typically, calls used to be of around three minutes, after which, users

would get fed up of speaking and hang up. Internet users, on the other hand, tend to be on the telephone line for much longer than this (hours, if my telephone bills are anything to go by) for regular and frequent periods. Tying up a telephone line for such long periods ties up network resources and ultimately makes it harder for other calls to get through.

While this has placed minimal pressure on telephone networks to date, the sharp increase in Internet users (particularly the mass uptake which has started to occur in home users) will put ever more increasing demands on the telephone network. With every hour of an Internet connection taking up the equivalent of 20 average voice telephone calls, it's not hard to envisage the time (in the not-too-distant future) when the networks cease to be able to cope with any reliability. (This has probably already started to occur – the last time I tried to telephone for a BT engineer to report a fault the line was busy for several hours – yes, I'm being facetious, again).

In all seriousness, it means that significant expansion of worldwide networks has to take place immediately. Without planned, rapid expansion over the next few years, the busy signal will become an all too familiar sound.

DVD

It's been a while in the pipeline, but digital video disk (DVD) is about to come to fruition – at least, the hardware is. Matsushita is about to release the world's very first DVD player in Japan, and is expected to do the same by the end of the year in North America. Germany is next in the rollout, in February of next year. The UK isn't yet featured in the company's plans for product release.

Mind you, while the players are almost released, the actual disks are a seemingly long way off yet, which leaves DVD open to question. Players without disks are like CD-ROM drives without CD-ROMs, cars without petrol, bicycles without pedals, British weather without rain, televisions without pictures, and er... yes, you get the message – I'm being facetious, yet again.

The opinions expressed by the author are not necessarily those of the publisher or the editor.

PROJECT

FEATURES

- Simple to build
- No alignment equipment required
- Colour or black and white
- SCART facility
- Pre-punched steel casing
- Test signal for receiver tuning

APPLICATIONS

- Camcorder replay
- Video editing
- Linking VCRs
- Audio/video signal testing

Audio/Video MODULATOR

Design by Chris Barlow
Text by Chris Barlow and Maurice Hunt



PROJECT RATING 2

Kit Available
Order as LU35Q
Price £34.99

This project is a substantially revised version of the Audio and Video Modulator kit (LM79L), previously featured in the February 1989 issue (No.30) of Electronics. The main reason for the update is due to the discontinuation of the originally specified UHF modulator (the UM1286), so the new circuit was designed around the recently introduced (and superior) 'Alps' modulator. This modulator features an integral 'aerial throughput' RF mixer/booster and a built-in test signal for receiver tuning, which causes a bar pattern to be displayed on a TV connected to the project, so that the picture can be adjusted for optimum results.

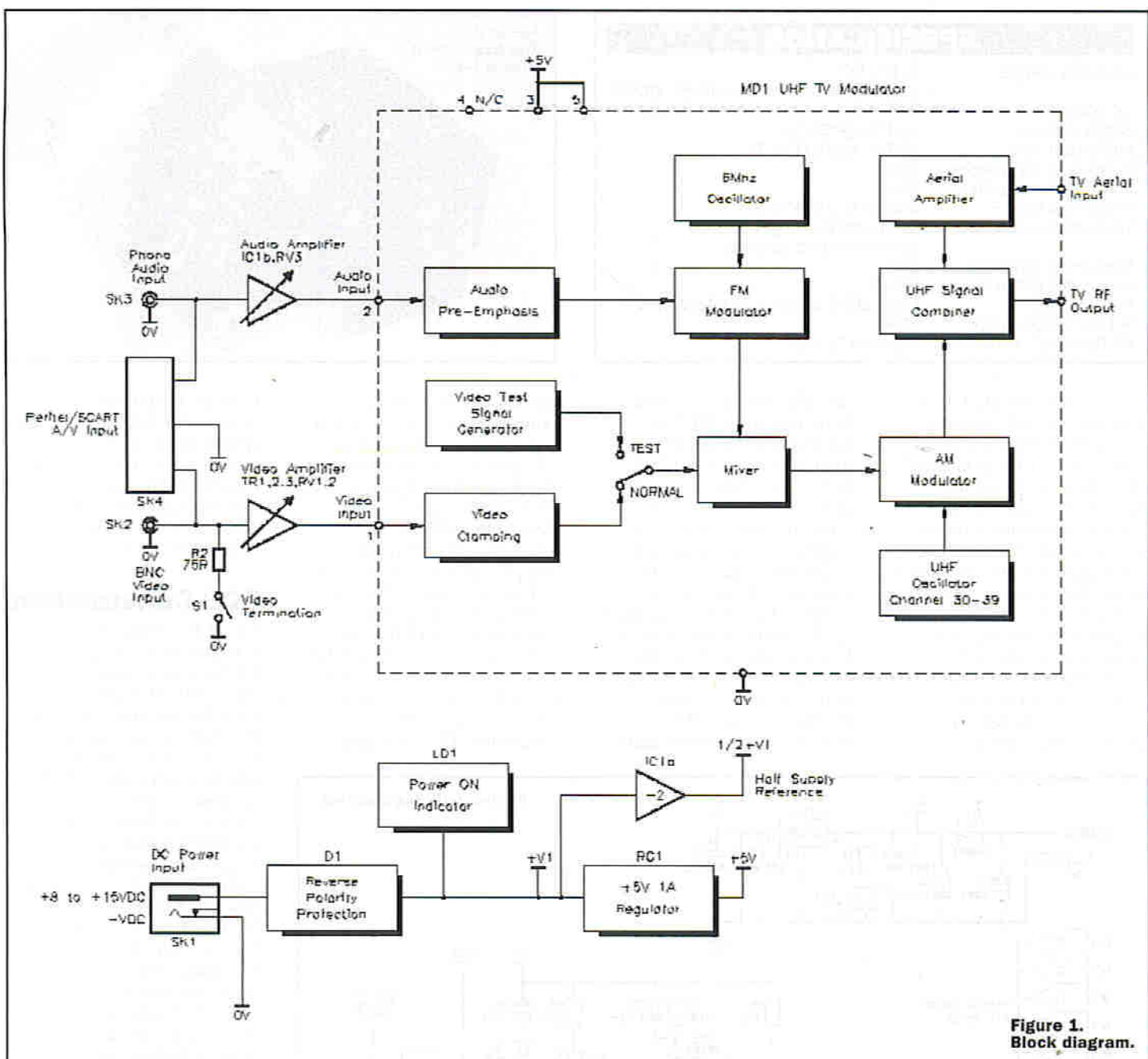


Figure 1. Block diagram.

The opportunity was taken during the redevelopment process to add a number of useful extra features to the design, including a SCART socket and provision for adjustment to cater for the imminent Channel 5 introduction, while a pre-punched steel casing makes the project easier to construct.

Circuit Description

Refer to the block and circuit diagrams, shown in Figures 1 & 2, respectively. These should be of assistance when following the description.

The DC supply from the regulated AC-DC adaptor is applied to SK1, noting that the centre-pin is positive and the outer contact negative. D1 protects against reverse polarity damage to the circuit.

Low frequency decoupling of the supply is provided by capacitors C2 and C5, while C1, C3 & C4 take care of the high frequency decoupling. LED LD1 lights to confirm when power is applied. Voltage regulator RG1 provides a steady +5V level, which is required by the UHF modulator, MD1.

For the audio circuit to function correctly, a half +V1 supply reference is necessary, which is provided by half of IC1 (IC1a). The voltage reference applied to the input of this op-amp is derived from the two resistors R14 & R15, which form a potential divider. The op-amp is configured as a unity gain voltage follower to provide a low impedance half-supply, its input being decoupled by C13-16 and its output by C11 & C17-19.


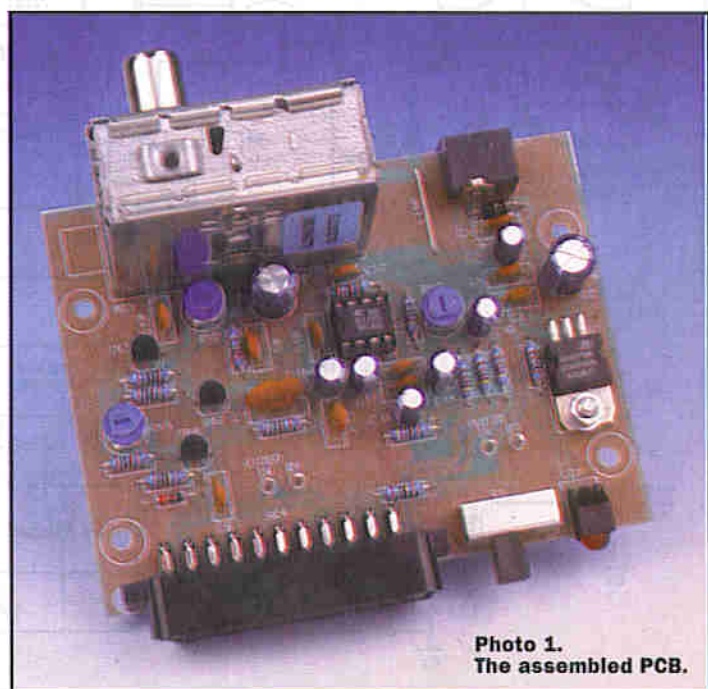


Photo 1. The assembled PCB.

SPECIFICATION

Operating voltage:	8-15V DC (e.g. 12V 300mA AC-DC adaptor, YB23A)
DC power input connector:	2.5mm power socket, centre pin positive
Supply current:	144mA @ 12V
Audio input level:	150mV to 3V Pk-to-Pk
Audio input impedance:	50k Ω
Audio input connector:	Phono
Video input level:	200mV to 3V Pk-to-Pk
Video input impedance:	1M Ω approximately, 75 Ω with termination load selected
Video input connector:	BNC
Audio/video connector:	SCART
RF TV output:	Channel 30-39 (543.25-615.25MHz)
FM sound sub-carrier:	6MHz
RF TV IN/OUT connectors:	Standard TV coax

Photo 2.
The assembled
PCB in box.

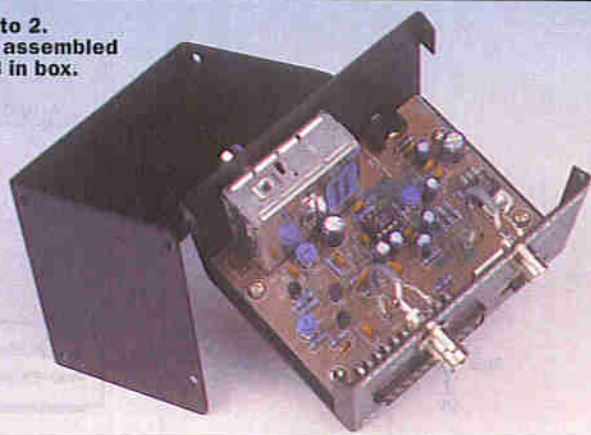

The other half of IC1 (IC1b) is used as an audio amplifier which drives the sound input (pin 2) of the UHF modulator, MD1. Resistors R12 & R13 determine the gain of the op-amp, with potentiometer RV3 setting the level of audio signal applied to the amplifier's input. The incoming signal from pins 2 & 6 of SK4, or from the phono socket SK3, is AC coupled to RV3 via C10.

The video signal is applied to pin 20 of SK4 and its ground is connected to pin 18. The input impedance of

the video amplifier, formed from transistors TR1-3, is approximately 1M Ω . However, this can be reduced to 75 Ω by closing switch S1, which places a 75 Ω resistor (R2) across the video input – this is known as a termination load.

The video signals are AC coupled via C6 into the gate of TR1, a Field Effect Transistor (FET). Diode D2 and resistor R3 are used to maintain the correct bias level. TR1 & TR2 form a broadband buffer amplifier, the gain of which is set by the value of the negative

feedback resistor, R6 and potentiometer RV1. Resistor R4 provides the source load for TR1 and preset potentiometer RV2 forms the emitter load for TR3. The DC bias for TR2 is derived from R5 and TR1. A small amount of frequency compensation is provided by C7.

The video output from the amplifier is tapped off from the wiper of RV2 and fed to the video input (pin 1) of the UHF modulator, MD1. Inside MD1, the audio signal is converted into a 6MHz frequency modulated (FM) sub-carrier.

It is then mixed with the video signal and fed to the amplitude modulated (AM) section, where the UHF carrier is combined to produce the final modulated RF output suitable for the aerial input of domestic TV sets.

PCB Construction

The PCB is a single-sided fibreglass type, with printed legend to assist assembly – refer to the PCB legend and track drawing, shown in Figure 3. The PCB has been designed for a minimum of off-board wiring, which is needed only to connect the video and audio sockets. The board is best assembled in order of ascending component size/height.

Start by fitting the four PCB pins in the position marked 'AUDIO/VIDEO' 'IN' & '0V'. Use the piece of 22swg wire supplied in the kit for the single wire link. Take care to ensure that polarised devices (electrolytic capacitors and semiconductors) are fitted the correct way round. Also, ensure that the IC socket for IC1 is fitted with its end notch aligning with the printed legend.

Fit the three preset potentiometers, and set them all to their half way positions; the circuit has been designed such that these settings should enable the unit to operate with a minimum of setting up being required.

The SCART socket (SK4) has two locating clips which are pushed through the holes in the PCB, until they lock in place, then the socket pins can be soldered. Switch S1 has tabs at each corner of its metal body, which should all be soldered in to provide support. Fit the PCB-mounting LED LD1, and the power socket SK1 flush to the board.

The voltage regulator, RG1 leads must be pre-bent at 90° and the regulator heatsink tab fitted flat onto the board

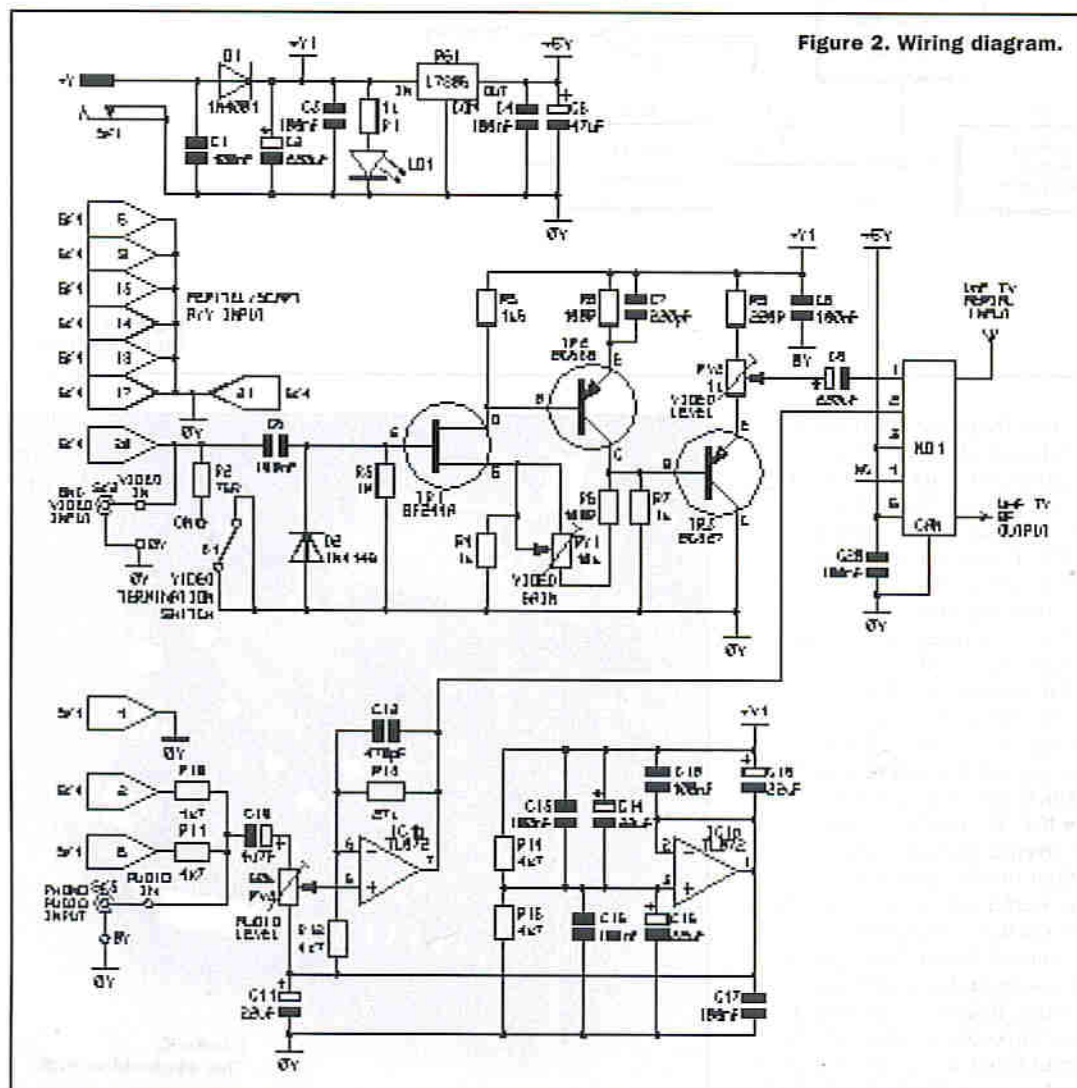


Figure 2. Wiring diagram.

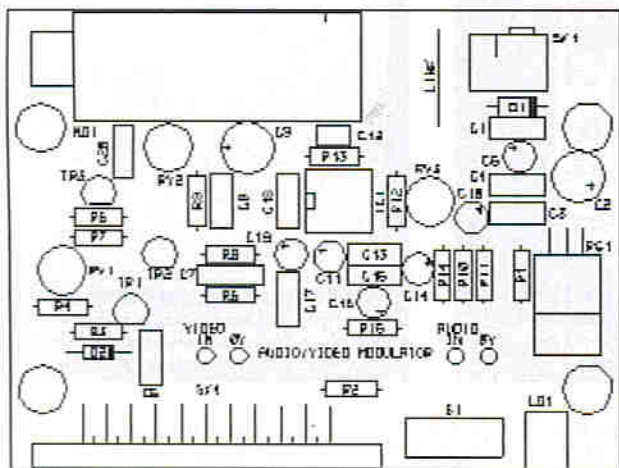


Figure 3. PCB legend and track.

using the M3 hardware supplied, as shown in Figure 4, the exploded assembly diagram.

The UHF modulator, MD1, is fitted vertically, with its corner tabs soldered in to provide support.

Install IC1 last of all, with its end notch aligning with that of the socket.

Having completed the board, check your work carefully for misplaced components, solder whiskers, bridges and dry joints, then clean off excess flux using a suitable solvent.

Testing

Testing of the completed board should be carried out prior to its installation into the casing, since faultfinding will then be easier, should it be required.

Temporary connection to the board should be made, as shown in Figure 5. At this stage, the wires can be longer than required, as they are cut to size during the final assembly.

All the tests can be made with a minimum of equipment. You will require a multimeter, a UHF TV set and an audio/video source. A regulated 12V AC-DC adaptor, with centre-pin positive, will also be required to power the unit. Carefully lay the PCB assembly onto a non-conductive surface, such as dry paper or plastic.

The first test is to measure the resistance at the DC power socket, SK1. With the multimeter set to read ohms, connect its red (+) test lead to the centre terminal and the

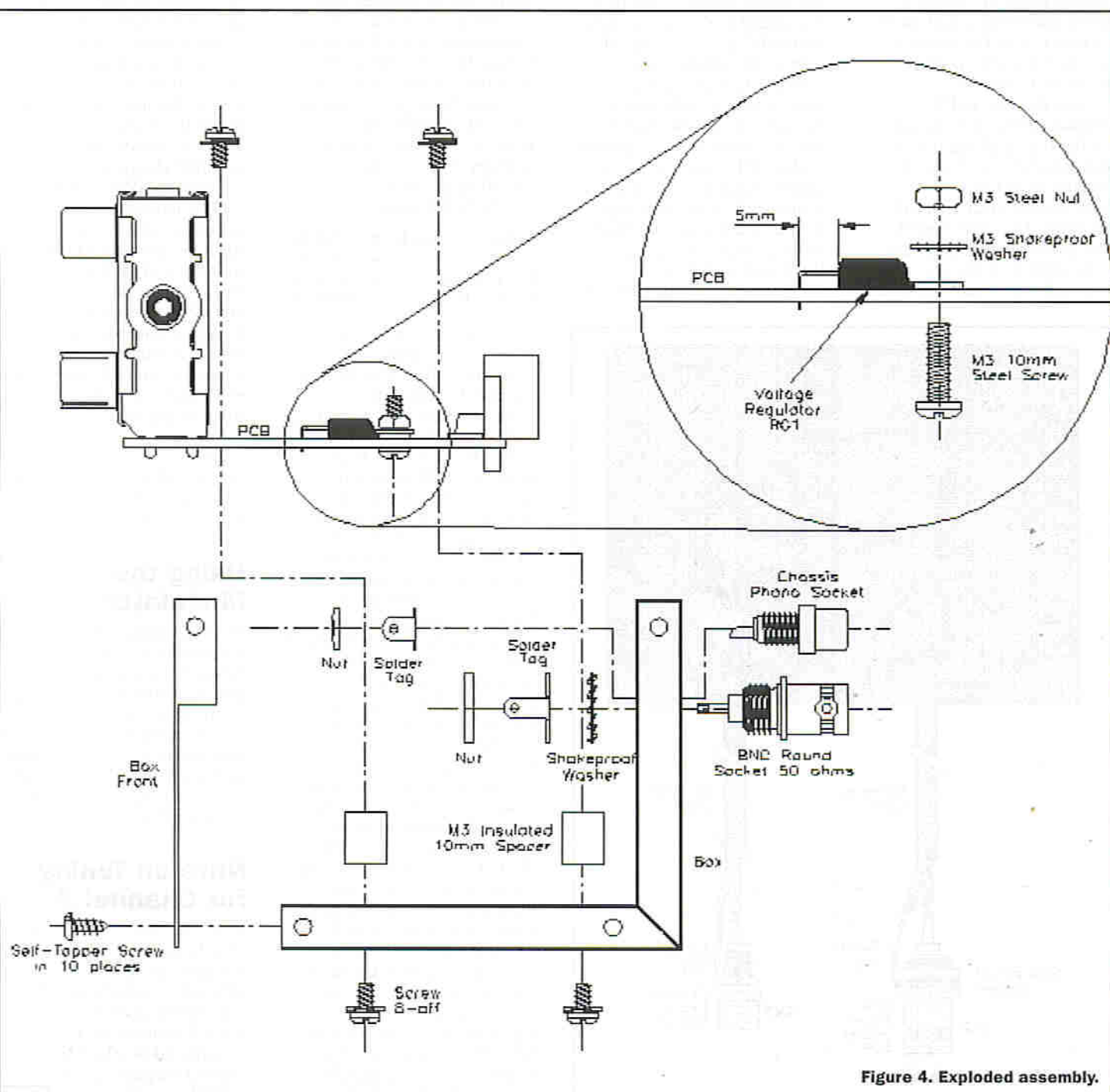


Figure 4. Exploded assembly.



Figure 3a. Video level set too low, resulting in a dark picture.



Figure 3b. Video level set correctly, giving the best picture quality.



Figure 3c. Video level set too high, resulting in saturation and flaring out of the peak whites.

black (-) test lead to the power socket's side tag or any other 0V point on the unit (such as the UHF modulator casing). You should get a reading of approximately $1.5\text{M}\Omega$ and, when the test leads are reversed, a much higher reading in excess of $20\text{M}\Omega$ should be present, due to the reverse polarity protection diode D1.

Next, the 12V AC-DC adaptor should be switched on but not yet plugged into the onboard power socket, and the multimeter set on a DC current range that will accommodate up to 300mA. The aim is to test the current consumption of the unit in its quiescent state (no signal

applied). The following process is a little fiddly in practice, and care must be taken not to short circuit the power supply.

The multimeter's red (+) test probe should be inserted into the power supply centre hole, the negative (-) test lead held on the DC power socket (SK1) centre pin, and the outer contact of the power supply plug must simultaneously be brought into contact with the tab (0V terminal) of the power socket. This can be achieved either (preferably) using a lead terminated in crocodile clips, by pressing the outer contact of the power supply plug onto the power socket tab, or onto the metal body of the UHF

modulator. The 'power on' LED, LD1 should light and a current reading of around 144mA should be obtained.

If the current consumption is satisfactory, the power supply can be plugged directly into the power socket. The multimeter should then be set to read DC volts (up to 20V). With the negative (black) test lead attached to a convenient 0V point on the board (e.g. the modulator body), voltages on the board should approximately match the following:

Cathode of diode D1	= +11.2VDC
Link	= +5V DC
Pin 1 of IC1	= +5.6V DC
Pin 7 of IC1	= +5.6V DC

This completes the DC testing of the audio/video modulator, and the multimeter can now be put aside.

Next, connect a coax lead (GW61R) from the RF output of the modulator to the aerial input of a UHF television. With the UHF modulator's test switch 'on' (upper position), tune a spare channel on the TV to approximately 36, where you should see a screen with two vertical white bars on a black background, with no sound. Connect an audio/video signal to the input (BNC/phono or SCART) of the modulator. If no other video connection is made to the unit then the termination switch (S1) must be on.

To set the audio level, adjust potentiometer RV3 until the sound level is the same as for an off air transmission (BBC, ITV, CH4/5). Next, set RV1 fully anticlockwise and RV2 to its halfway position, so that peak whites don't flare out and produce excessive buzzing on the sound channel. The final setting of the video level is down to your personal preference - see Photos 3a-c. DO NOT make any attempts to adjust any of the presets inside the UHF modulator

(MD1), as these are factory set using sophisticated test equipment.

Final Assembly

The unit is housed in a pre-punched screened metal casing for ease of construction. Fit the 10mm threaded insulated spacers to the holes in the PCB, and carefully install the PCB into the casing - see Figure 4, showing the exploded assembly diagram.

Install the BNC and phono sockets into their holes in the casing and secure them with the nuts and washers supplied with the sockets. Connect the sockets to the audio and video input PCB pins using short lengths of suitable screened cable (the outer screen connects to the 0V terminal in each case) - refer to Figure 5, showing the internal wiring required.

Finally, fit the lid onto the casing with the screws supplied, and stick on the four rubber feet on the box underside.

Using the Modulator

Refer to Figure 6, showing the general application wiring between the unit and various pieces of video equipment that can be used with it. The test switch on the modulator can be switched in to assist the tuning in of a different TV set to match the modulator if the system setup is altered.

Note on Tuning for Channel 5

When the new Channel 5 is introduced, the UHF modulator may need to be tuned for a different frequency, away from the existing channel 36 and towards channel 39. This can be achieved by adjusting the channel frequency preset control - see Figure 6. **Electronics**

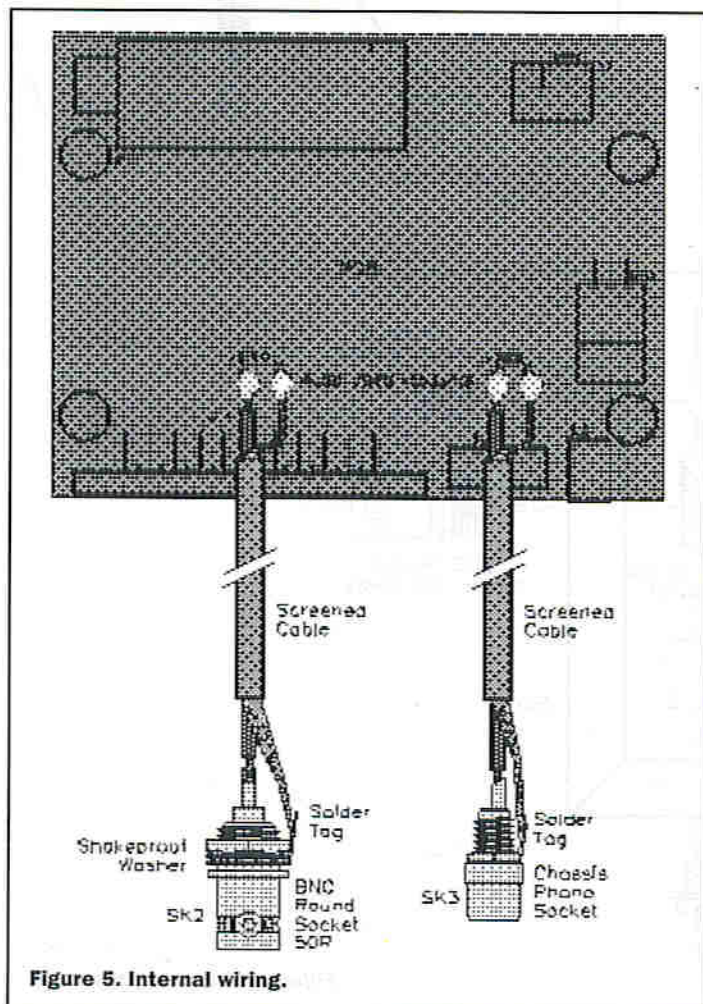


Figure 5. Internal wiring.

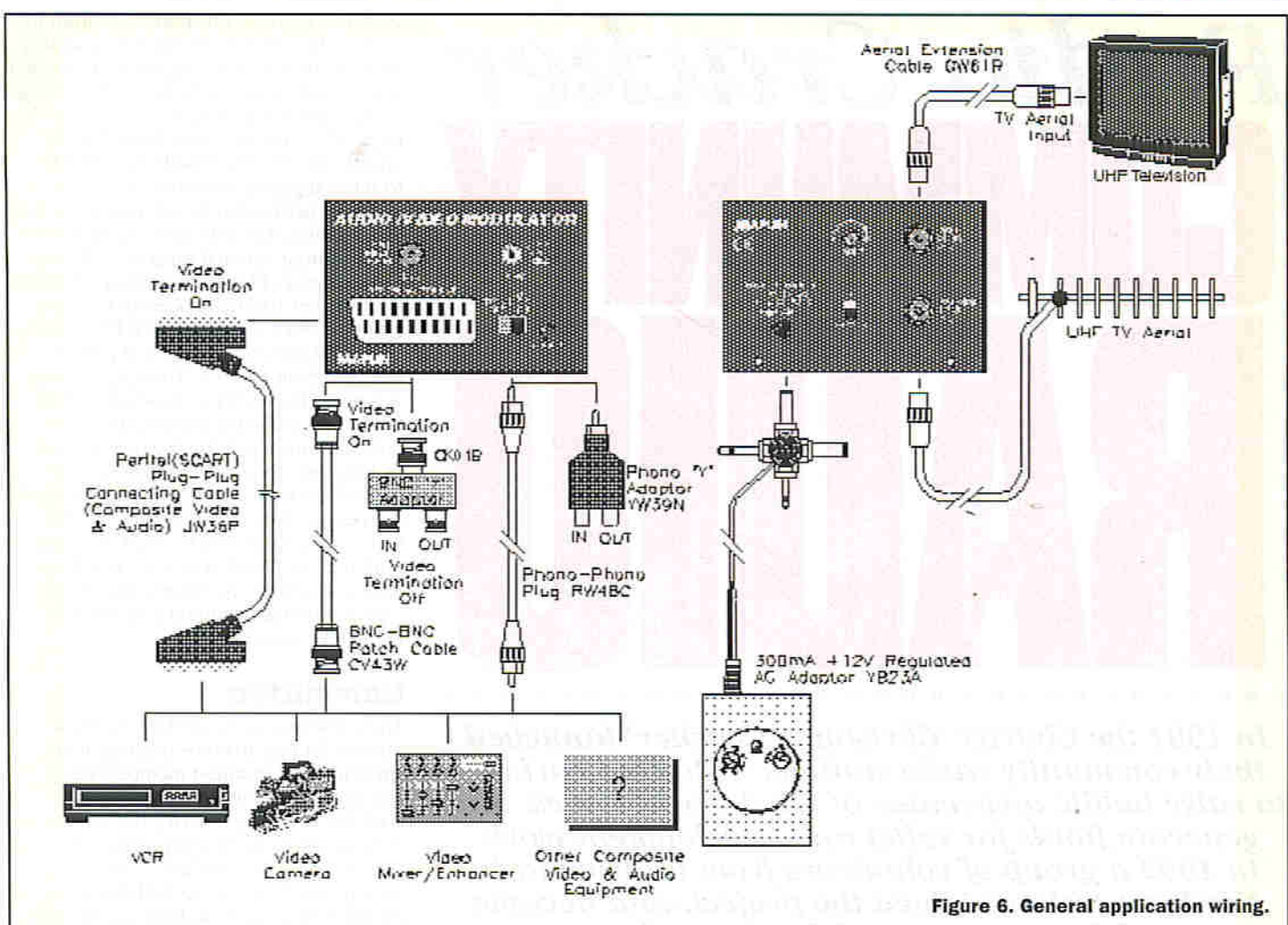


Figure 6. General application wiring.

PROJECT PARTS LIST

RESISTORS (All 0-6W 1% Metal Film, Unless Stated)

R1,4,7	1k Ω	3	(M1K)
R2	75 Ω	1	(M75R)
R3	1M Ω	1	(M1M)
R5	1k5 Ω	1	(M1K5)
R6,8	100 Ω	2	(M100R)
R9	220 Ω	1	(M220R)
R10-15	4k7 Ω	5	(M4K7)
R13	27k Ω	1	(M27K)
RV1	10k Ω Preset Potentiometer	1	(WR42V)
RV2	1k Ω Preset Potentiometer	1	(WR40T)
RV3	50k Ω Preset Potentiometer	1	(WR43W)

CAPACITORS

C1,3,4,6,8,13,15,			
17,18,20	100nF 16V Ceramic Disc	10	(YR75S)
C2,9	200 μ F 16V Radial Electrolytic	2	(AT41U)
C5	47 μ F 16V Radial Electrolytic	1	(AT39N)
C7	200pF Ceramic Disc	1	(WX60Q)
C10	4 μ 7F 63V Radial Electrolytic	1	(AT76H)
C11,14,			
16,19	22 μ F 16V Radial Electrolytic	4	(AT37S)
C12	470pF Ceramic Disc	1	(WX64U)

SEMICONDUCTORS

D1	1N4001	1	(QL73Q)
D2	1N4148	1	(QL80B)
RG1	L7805CV	1	(QL31J)
LD1	PCB-mounted Red LED	1	(QY86T)
TR1	BF244A	1	(QF16S)
TR2	BC559	1	(QQ18U)
TR3	BC327	1	(QB66W)
IC1	TL072CN	1	(RA68Y)

MISCELLANEOUS

SK1	PCB-mounted 2.5mm DC Power Socket	1	(FK06G)
SK2	BNC Round Socket 50 Ω	1	(HH18U)
SK4	Peritel Right-angled Socket (Lugless)	1	(BP65V)

SK3	Chassis-mounted Phono Socket	1	(YW06G)
S1	Right-angled SPDT Slide Switch	1	(FV01B)
MD1	6MHz UHF Modulator	1	(WC21X)
	8-pin DIL Socket	1	(BL17T)
	1mm Single-ended PCB Pin	1 Pkt	(FL24B)
	M3 10mm Insulated Spacer	1 Pkt	(FS36P)
	M3 10mm Steel Screw	1 Pkt	(JY22Y)
	M3 Steel Nut	1 Pkt	(JD61R)
	M3 Shakeproof Washer	1 Pkt	(BF44X)
	0.71mm 22swg Tinned Copper Wire	1 reel	(BL14Q)
	Miniature Coax Cable	1m	(XR88V)
	Stick-On Feet Domed	1 Pkt	(BP59N)
	Box	1	(BL98G)
	PCB	1	(GJ59P)
	Instruction Leaflet	1	(XZ10L)
	Constructors' Guide	1	(XH79L)

OPTIONAL (Not in Kit)

	300mA AC Adaptor Regulated	1	(YB23A)
	Aerial Extension Cable	1	(GW61R)
	Peritel Audio & Composite Video Plug to Plug	1	(JW36P)
	10Base2 BNC to BNC Patch Cable 2m	As Req.	(CV43W)
	BNC Y Adaptor	1	(CK01B)
	Single Phono-Phono Plug	As Req.	(RW48C)
	2-to-1 Phono Adaptor	1	(YW39N)

The Maplin 'Get-You-Working' Service is available for this project, see Constructors' Guide or current Maplin Catalogue for details. **The above items (excluding Optional) are available as a kit. Order As LU35Q (Audio/Video Modulator) Price £34.99**

Please Note: Where 'package' quantities are stated in the Parts List (e.g., packet, strip, reel, etc.), the exact quantity required to build the project will be supplied in the kit.

The following new items (which are included in the kit) are also available separately, but are not shown in the 1996/97 Maplin Catalogue. Audio/Video Modulator PCB **Order As GJ59P Price £3.49** Audio/Video Modulator Box **Order As BL98G Price £11.99**

Radio Cracker

COMMUNITY RADIO

In 1991 the Charity 'Christmas Cracker' launched their community radio stations - 'Radio Cracker' to raise public awareness of third world issues, and generate funds for relief and development work. In 1992 a group of volunteers from Ballymena in Northern Ireland joined the project, and became one of the most successful stations that year.

They were among a handful of stations who returned to the airwaves in 1993, and once again had a runaway success, raising well over £17,000 for the second year in succession. Fuelled by this success they went on in 1994 and in 1995 raised an astounding £38,000!

Brian Adams, their Technical Manager in 1993, explains how Radio Cracker Ballymena went 'On The Air'.....

Initially, a number of people who were interested in the work of Christmas Cracker arranged a public meeting, to determine

whether or not there was sufficient interest to establish a radio station. As a result of that meeting, a management committee was set up, who with the help of the national charity were to organise Radio Cracker Ballymena. National support was to include training documentation, nationally organised advertising, supply of transmission equipment, 'jingles' and station idents on CD, and a news service by satellite.

The national co-ordinating team also organised all of the official paperwork with bodies such as the radio authority, taking

away this burden of responsibility from the local bodies. In 1993 all that was to change - the Christmas Cracker organisation decided to stop radio stations, because of the danger of the charity becoming known just for radio. They had however, allowed local groups who in 1992 raised over £15,000, to retain their transmission equipment, and gave permission for any group who had already ran a station to do so again in 1993 - but without national support. Following their success in 1992, the Ballymena Committee felt that they had no choice but to return again in 1993 - no matter what the obstacles. With what experience they had gained they set about the task! Their persistence was rewarded - with no national support, and broadcasting for a shorter period of time, they managed to raise over £22,000. In 1994 they continued, raising £24,000. In 1995 the mayor of Ballymena challenged the people of the town to break the UK record for a Radio Cracker station - held until then by Wimbledon at £25,000. They were not content just to break the record - they demolished it, raising over £38,000 in the four week period!

Committee

The committee were perhaps the most unlikely lot ever to come together to do anything! The youngest members were teenagers, the oldest in their forties. With the one exception of a BBC Audio Assistant, none had any experience of radio work worth considering. There were people from various backgrounds - a social worker, a car mechanic, a computer technician, DJ's, students, salesmen, a lighting engineer - all of the wrong people for radio.

What they lacked in experience, they made up for in enthusiasm, and pure determination to make the project work. They quickly realised the importance of harnessing the local young people to work for the charity, and so established a youth committee, made up of student representatives from the local schools. The youth committee enlisted the help of friends in their schools to organise 'Cracker Events' and competitions, and later helped to staff the station.





Premises

It quickly became apparent that finding premises was top of the agenda if the station was ever to get off the ground. Because national headquarters had to collate information from many stations to pass on to the radio authority, they needed to know months in advance of broadcasting where both studios and transmitters were to be located. This created an immense problem – with high profile being important, it was felt necessary for the station to be located


in the town centre – but how do you have someone commit prime retail space to a charity for over a month, and get the commitment months in advance of needing it?

The manager of the town's new shopping centre came to the rescue. Being new, he was quite sure that he would have empty units at Christmas, and even though he could not be sure of an exact location, he could promise that space would be available somewhere in the centre. This did not only resolve the problem of an address – being within a shopping centre had many other

advantages, such as 24 hour security, and readily available services. It also promised a ready made audience of tens of thousands of shoppers passing the station premises every week!

Fund Raisers

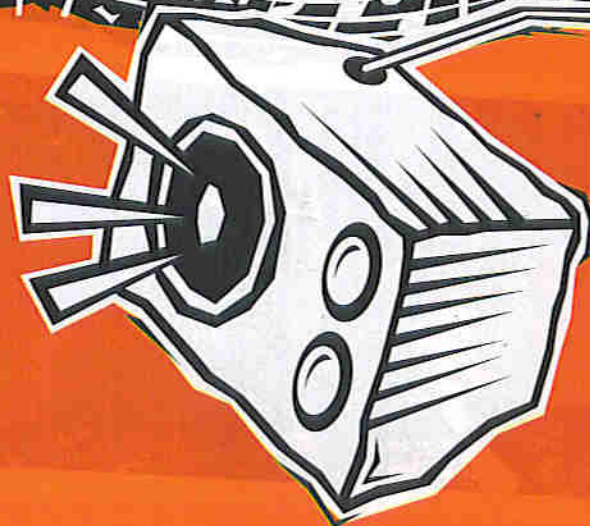Community radio stations must be licensed, just like any other radio station, and even for a low power transmitter, this can be quite expensive – the 1W FM transmitter used by Radio Cracker costs over £1,000 to license



for a month! There are fees which must be paid to other bodies, and although registered charities receive substantial discounts in many cases, there is a considerable amount of money needed before the station can go on air. In order to raise this start up money, and also to raise the public profile of the project, a number of fund raisers were organised. Some were quite common – a fashion show, and a wordsearch quiz for example. Others were a little more imaginative – a 'Shanty Town House' made of old wood and cardboard was built inside the Fairhill shopping centre, and advertised with the slogan "The alternative Ideal Home Exhibition – see how the other two thirds live!" A cake, measuring approximately five feet by three, was baked by local school pupils, and iced in the form of the radio cracker logo – it was sold in slices, as 'Crackers massive cake sale!' The fund raisers in 1992 just about met the setting up costs, and paying the fees.

Legal Obligations

Legal obligations as already highlighted, there are certain obligations to be met in establishing a radio station. The license fee is one expense, and the radio authority have strict guidelines which must be adhered to by the station organisers. These cover areas such as maximum radiated power, aerial height, broadcasting hours, and codes of conduct for material broadcast, including detailed regulations regarding advertising.

There are a number of other bodies who must be satisfied if music is to be broadcast, and in the case of Radio Cracker, music formed a major element of the station output. The Mechanical Copyright Protection Society are responsible for licensing their members work for re-recording - including the use of music to make up jingles and advertisements. Performing Rights Society govern the actual performance of their members work, whether that be in the form of live music or pre recorded material such as records and CD's. Phonographic Performance Limited look after the use of recorded works in any performance situation, including public broadcasts.

The requirements of all of these bodies must be satisfied in advance of going on air. There is also an obligation to the general public, and to that end, public liability insurance

is a necessity. Although dealing with so many authoritative bodies may seem a daunting task to the amateur, it was found that in practise, they were very helpful in advising the station of the legal requirements, and most of the paperwork involved was very straightforward, and easily filled in.

PR!

There is little point in running a radio station if the public don't know it is there! Eventually people will find it when scanning the dial for something else, but ideally, they should be waiting with a sense of expectancy for the new station to begin transmissions. The fund raising promotions certainly helped to raise public awareness, but more was necessary. Information was sent regularly to the local press, and a well known local personality – a presenter on Ulster Television – was asked to perform the official opening. Even with all of this, it was felt that the publicity in 1992 was not all that it could have been, so in 1993 some improvements were made. Instead of just sending facts to the press, complete stories were written, and these were accompanied by photographs. This means of obtaining free publicity was continued in subsequent years to great effect. A special event which gave considerable publicity, was participating in the national charity organised 'Alternative Christmas' held on the 25th of June 1993. The Radio Cracker roadshow was set up in the town centre, and DJs dressed as Santa, and various other guises, played Christmas music from a stage decorated with tinsel and a Christmas tree! Way-out events such as this were great crowd-pullers, and of course generated more of that vital press coverage.

Program Sources

It was always the intention that as much program material as possible would be locally produced. But some things are best left to the experts, and one of the prime examples of this is news. The organisers were well aware of the importance of news to the station, but knew too that they simply did not have the resources to produce it locally. In 1992, the national news was provided by satellite in a special arrangement

with Sky News. National Christmas Cracker then added their own bulletin at the end of the satellite news, and this at certain times was supplemented by local bulletins. In 1993, there was no such service available. A begging letter to BBC Radio Ulster resolved the problem – Radio Ulster gave permission to re-transmit their bulletins. The BBC helped out in more ways than one – Radio 1 FM was used as an overnight sustaining service – when Radio Cracker closed down at 11 pm at night, the presenter simply announced that Radio Cracker, by permission of the BBC, was joining Radio 1 FM. Apart from these two services, virtually all of the material originated from Radio Crackers own studio, except for a few pre-recorded programs, and interviews, which were edited off-site, and brought in on either DAT or 1/4 in. tape.

The Studio

In 1992 the shop unit used was quite large, and there was sufficient space to build two studios, as well as a control room. In practise it turned out that Studio 2, which was not as well equipped as Studio 1, was used only for recording adverts, interviews and voice overs, and the occasional news bulletin. In 1993 space was at a premium, since a Crackerteria cafe was being run alongside the radio station, so Studio 2 was dispensed with. Adverts and voice overs were recorded using the main control room desk, with the kitchen acting as a booth!

In addition to the actual studios, space was set aside for a reception area, storage, and a preparation area, with desks and facilities for staff to make tea and coffee. The walls dividing these areas were made of plywood sheeting, screwed to softwood framing, simply because the plywood sheets could be sold at the end of the project. The studio and continuity room walls were made as conventional stud walls, with a single sheet of plasterboard on each side. In 1993, two walls of Studio 1 were covered in carpet to improve the acoustics and the appearance. No multi-layer walls resting on Neoprene here – remember this is radio, where generally only one microphone is on at any point in time, the user will be very close to it, and will quite possibly be speaking over music which will at least partly mask any extraneous



noise. In practise, some noise from reception and other areas was audible on the studio mics, but not to the extent where it was very noticeable, and no real sound proofing was necessary. The materials to construct the stud walls were donated by a builders merchant in exchange for advertising on the station, and the studios for 1992 were dismantled carefully, allowing most of the timber and plasterboard to be re-used in 1993. In addition, a glazer donated glass for a double glazed window onto the shopping centre mall in 1993, because the unit used had no existing walls or windows. Another change in '93 was the acoustic treatment of the studio. The unit had a suspended ceiling, so tiles were removed and stud walls built through to the real ceiling. The walls were simply painted, but to reduce reverberation in the studio, a large screen was constructed of fibreglass wadding and cloth, and this structure strategically placed. Despite its simplicity, it made an amazing difference to the characteristic of the sound in the studio.

Disaster Looms!

In 1994 the organisers faced a prospective disaster – all of the units in the shopping centre were full! The centre management were keen to help Cracker out, and came up with a novel solution. A number of artificial bridges crossed the mall of the centre, masking some steelwork which had been installed to facilitate future first floor development. With the assistance of a number of tradesmen, a complete studio was built on one of these bridges and aptly nicknamed 'The Bridge of Hope'. A shop, and location for special broadcasts, was built near the bridge in the mall below, complete with telephone, power, and audio links between the two!

Studio Setup

The studio equipment has been basically the same for 5 years, but in 1993, the physical layout was vastly improved over that in 1992. The equipment was arranged as shown in the diagram, with the mixing desk centrally in front of the presenter, with gram decks either side, and cassette decks and CD players to left and right of centre

on an elevated section above the desk. This platform also held a cartridge player, and a third CD player for playing pre-recorded jingles etc. Opposite the presenter, there was sufficient space for two permanently set up microphones for guests or co-presenters. The desk was a Yamaha 1602 – 16 channels into stereo outputs. It was not ideal for the job, but with a little ingenuity was made to suffice. A problem which was encountered in 1992 was that presenters continuously turned up gain controls, but never turned them down, with the result that the desk output every now and then reached the point of distortion! A quick experiment revealed that this was partly a psychological problem - the idea of having gain controls fully anti-clockwise seemed to give the impression that the channel volume was too low – but for CD players, with their high output levels, this was what was needed to make them balance correctly with microphones, which even when used close up, had comparatively very little output.

The problem was resolved by placing 20dB pads in the insert points of the channels which had the CD players – this meant that for the same level as before, the gain controls were positioned at 10 – 11 o'clock on there scale. With this illusion of gain, and 'gaffa-tape' over the VU meters, the self-professed experts stopped tweaking gains, and the problem was resolved.

Technics gram decks were used in all but the last year, which with their fast startup time, and high reliability, proved more than adequate for the job. The CD players were Sony domestic models, which although not designed for studio use, worked flawlessly, and even after three weeks, were showing no signs of abuse.

Initially SM58 microphones were used throughout – mainly due to the fact that they were sure to survive three weeks of abuse and misuse by amateurs. It was found in practise though, that there was a noticeable drop in volume if the presenter moved to either side of the microphone, which occurred quite regularly if he was starting record decks. The presenters SM58 was replaced by a Beyer, fitted with a foam windshield, which gave very acceptable results.

Monitoring in the studio was accomplished using Beyer DT100 headphones supplied from the desk output via a 6 way splitter, and a Toa T150 Fashion Speaker mounted on the wall opposite the presenter, in later years being replaced by bookshelf hi-fi speakers. This was powered using a domestic Hi-Fi amp located in 'continuity'. It was fed from the right main output of the desk, the left being taken as 'Studio Output'.

The 'Studio Output' control was taped down, and tape was placed across the track of the right fader, or 'Monitor' level control. This guaranteed that even if presenters forgot to turn down the monitor speaker when microphones were turned up, at least they could not reach feedback levels.

Pre-fading was only available on headphones – quite a good idea where amateurs are involved. To listen to studio output, the presenter just pre-fade listened to the main stereo outputs. (By now you should have figured out that the station operated in mono!)

'Talkback' was achieved by bringing a line input from the continuity desk into channel sixteen of the studio desk, and permanently taping down the PFL button. This ensured that no matter what the presenter was listening to on phones, he or she could be spoken to from the control room.

The talkback circuit was also used as a clean feed of station output - everything except the studio, to enable presenters to merge smoothly with other sources, such as tape playback of adverts, or news from the tuner.

The only other equipment in the studio was a TV and video recorder, used for teletext reception (great for up to the minute news, and trivia facts!), and for playing Karaoke videos! Continuity. Although the studio was the main source of station output, it was not nearly as well equipped as the continuity room.

The technical operators in continuity were responsible for playing adverts, and other pre-recorded material, and bringing in the news and Radio 1 FM at the appropriate times. It was also possible to play in music and tapes for inexperienced presenters, and even bring up the presenters microphone remotely! Station output level was controlled by continuity, and the transmitted signal was also recorded, to comply with the license.



conditions. Sound level in the Crackerteria, and on the mall were controlled from here.

Since reel to reel tape machines were scarce, adverts were recorded through the continuity desk, using the internal phone system to cue voice over artists in the kitchen! The other functions of continuity were putting phone calls on air, and mixing live sources from the shopping centre mall. The continuity desk was a 24 channel Soundcraft 200 SR (a 16 channel Allen & Heath in 1992). Station output was taken from group fader 1, and continuity monitor from group fader 2. Group fader 3 was taken as output to one of the reel to reel machines, and group 4 and the stereo output were not used.

Since the group select buttons on the 200SR are either groups $\frac{1}{2}$ or $\frac{3}{4}$, a source could be connected either to station output, or to record output. Channel 24 on the desk was used for the talkback microphone. It was selected to groups $\frac{3}{4}$, but panned hard right, to ensure that it never went to station output, even if the group select button was accidentally pressed. Auxiliary 3 – a post fade auxiliary – was used as the talkback output, so to talk to the studio, channel 24 fader was used. (A press to talk button would have been nice, but beggars can't be choosers!)

Auxiliary 4, the other post fade auxiliary, was used as the clean feed to the telephone balance unit, which received everything except itself. Auxiliaries 1 and 2 were occasionally used to send pre fade signals to reverb and delay, both of which were returned to channels on the desk. In 1994 and 1995 continuity desks with 'Matrix' outputs were employed – which made control over the various output circuits much easier. Two CD players and a cassette deck, both domestic units, and a Sony DAT machine were located to one side of the desk, along with a Pioneer A300 Hi-fi amp, which powered the local monitors. One of these, as already mentioned, was fed from the group 2 output of the desk. The other was driven from the desk headphone output, effectively making it a cue monitor. A Sony Tuner was used to receive Radio 1, and Radio Ulster.

Two Studer $\frac{1}{2}$ in. half track machines completed the complement of signal sources. These were located directly behind the

technical operator, so that he could operate them, and still keep one hand on the desk, to operate faders. In 1995 the reel to reel machines finally were dispensed with, at least during the transmission period. Jingles and adverts were all recorded in advance, edited onto DAT, and then transferred to CD's which effectively made the reel to reel machines redundant. Other continuity equipment included two hi-fi amps, to drive the speakers on the mall and in the Crackerteria (more Toa Fashion Speakers), the telephone balance unit, two telephone extensions, and a 19in. rack housing two Panasonic Super VHS video recorders, which were used, running at half speed, as logger machines, giving six hours logging on standard VHS tapes.

Transmission

As mentioned earlier, a 1W transmitter was used. For community radio, more power is not really needed in most areas. What is much more important is aerial location. One of the conditions of the community radio license is that the top of the aerial be no more than 10m above ground level (this was increased in 1995 to 20m). Now in a built up town centre, this could easily mean being well below the tops of nearby buildings. Fortunately, the Fairhill shopping centre is located at almost the highest point in Ballymena, and is only a two story building. A local electrical company who own a hoist, erected the mast, which held the transmission aerial, the FM reception aerial, and the television aerial. The reception aerial was located as near as was possible, vertically below the transmission aerial, to minimise the effect of the relatively high power signal being radiated from it, which could easily have swamped the received signals from the distant BBC transmitters. In 1995, a new aerial joined the array – a receiving aerial for the Outside Broadcast unit.

It is certainly worth experimenting with aerial location if transmissions are not what they could be – the Radio Cracker aerial for 1993 was moved approximately 20m to a different part of the building from its site in 1992. This made a considerable difference to the coverage area. Good reception was obtained over a three mile radius, but in areas

of high ground, with a good line-of-site to the town, acceptable results were obtained five or six miles away from the transmitter. One person even picked it up on a car radio 15 miles away.

Radio Cracker broadcast from 7:00am each morning until 11:00pm each night, with Radio 1 FM filling in the overnight period. News bulletins were taken 'on the hour', which was quite convenient, since Radio Ulster's bulletins usually begin with 'pips', making the switch over quite easy for the technical operator in continuity.


Being located in the town centre ensured that shops and office premises were able to achieve good reception, and as a result there was a large audience amongst the business community.

On The Air

Generally speaking, the station operated very smoothly. The 1993 studio was completed only two days before going on air, allowing very little time for presenters to rehearse their shows and get used to the setup. Some people ended up going on air, never having been in the studio at all before their first show! The studio desk gains were initially set up so that the correct levels were obtained when the channel faders were full open. Although in recording or PA circles, it is preferred to operate at some setting below maximum, often marked on the desk as a nominal, or 0dB position, in a radio setup, full fader travel is easier to cope with.

Presenters, especially inexperienced ones, find it much easier to push a fader full open, than to move it to a specific position, especially if they are ducking music for voice overs.

Equalisation was set flat for most channels – the notable exception being those for the gram decks. The actual eq for these was far from being true RIAA, but the three band eq with semi-parametric mid allowed for sufficient adjustment to achieve reasonable results. (Most Hi-fi purists would tear their hair out, but then they are unlikely to be listening to a mono FM radio station playing chart music anyhow!) Most presenters used CD's in any case, so gram deck eq was not really a big issue.

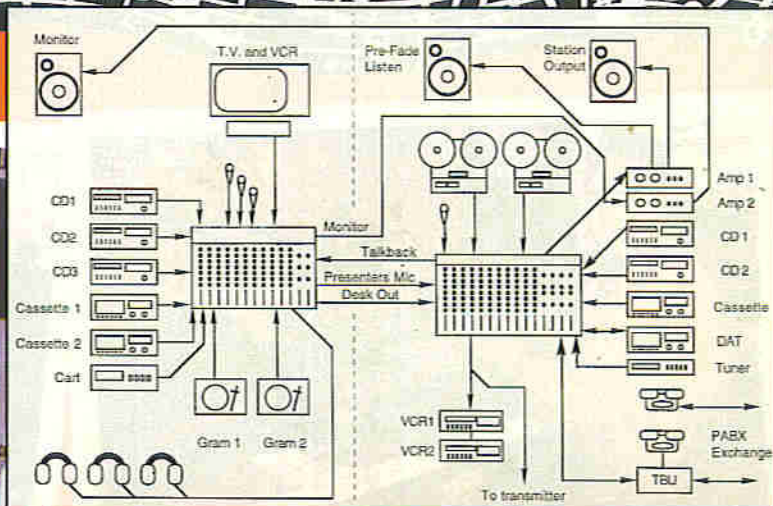

Many presenters ran 'phone in' competitions, taking the answers 'on air'. This was quite easy to achieve. An old telephone balance unit had been borrowed, and this was connected to the continuity desk as described above. When a call was directed to continuity from reception, the operator in continuity simply pressed the divert button on the balance unit, and replaced his handset.

At this point, the caller could hear station output, and the operator could speak to him or her using the talkback mic on aux 4. The caller could be pre-faded on the monitor speaker, allowing the operator and caller to converse until the presenter was ready to take the call. At that point, the phone was simply faded up on the continuity desk, allowing the presenter to hear via the talkback circuit. The continuity talkback mic was of course still active, and it was not unknown for staff in continuity to give clues to the callers, without this being heard on air!

Until 1995 and the use of CD's, adverts were kept on a single spool of 1/2 in. tape, each being separated from the next by a section of leader tape, on which was written the advert name and number. A list was available giving the advert numbers, and the time into the tape at which it could be found. It was a relatively easy task then to find a particular advert by looking up its time on the list, and spooling the tape through to this position. The Studer machines are very fast at starting, so adverts could be played almost instantly on cue. The second Studer was generally loaded with a tape containing trailers, or short pieces of information about Christmas Cracker, varying in length from about 10 to 30s. These were played between adverts to allow the operator time to cue the next advert on the reel.

Adverts were made by directing one of the CD players to groups 1/4, and mixing the music with the mic in the kitchen. The internal phone system was used as a low-grade talkback circuit to the kitchen, and the mix was monitored in continuity by pre-fade listening to group 3 output.

Station output was taken to a number of destinations, for example, the Crackerteria speakers, the transmitter, and the logging machine. This was achieved by using high quality transformer splitters connected to Group 1 output from the desk.

The studio output was compressed using an Alesis compressor, set for just over 2:1 compression, with a soft knee characteristic. The second channel of this was used as a hard knee limiter, inserted in the group 1 output, to ensure that the input to the transmitter was not overloaded.

A number of primary schools sent small groups of singers and musicians to perform live on air, and a number of other musical events in the mall were broadcast live. For this purpose, mic points had been wired on the front wall of the studio, connected back to the Soundcraft desk in continuity. Most small groups were covered using AKG 451's with either CK1 or CK8 capsules, and a mixture of SM58's and Beyer microphones.

Interviews with passers by, and other victims, were accomplished using a Sennheiser radio mic, which performed very impressively, even a long distance away from the studio. The interviewer listened to the station output on a Walkman style FM radio! A number of presenters made use of pre-recorded interviews, or short pre-recorded packages inserted into their programmes. These were generally recorded on portable DAT, and transferred to 1/2 in. tape for editing. The addition of some of these well edited packages certainly added to the air of professionalism of the station.

Cracker Hits The Road!

In 1995 the organisers felt that something new was needed to revitalise the project. Outside broadcasts were the ideal solution – taking community radio into the community!

The link to the studio was accomplished using a hired Band 1 radio link – which, like the main transmitter had to be licensed. A local sound company converted their covered trailer into a temporary outside broadcast unit, fitted with a 24 channel Soundcraft mixing desk, CD players, tuner, monitor amps, and speakers.

Using custom made adapters, their 'multicore' cable was used to link the trailer to the building which they were visiting. As well as carrying the microphone signals to the desk, this also carried back signals to the PA system amplifier, and 'Talkback' headphones. The presenters and floor

managers headphones had the 'off air' signal in one ear, and the producers 'talkback' signal in the other ear. The floor manager had a headset microphone with which he could talk back to the producer in the trailer.

With this setup, Radio Cracker went 'on the road' broadcasting lunchtime shows from local factories, and at night visiting other venues, such as the Leisure Centre, Sportsbowl, and YMCA centre.

Conclusion

The actual broadcasts from Radio Cracker were of a very high standard, despite the fact that the station was operated by amateurs with all the wrong equipment! Perhaps this will be an encouragement to anyone who is an enthusiast in any area of music or sound, who feels that they cannot possibly compete with the 'professionals' with their large budgets and top quality equipment. A little enthusiasm and determination can go a long long way!

A word of warning however, to anyone who is considering setting up a station themselves – plan carefully! Christmas Cracker Ballymena involved over 100 people from all walks of life. Many of these were involved in the Crackerteria and fund raising side of the project, but still an enormous number were involved in the radio station itself. There were 14 technical operators for continuity, and over 30 presenters, not including news and weather readers. On top of this there were readers for advertisements, advertising sales people, public relations people, and a host of others backing up the operation. Community radio most definitely requires community involvement.

A dedicated management committee who are all aware of the stations goals and ideals, and who will work well together to achieve them is a must. But with the right people working together, community radio can be successful, professional, and last but not least, enjoyable and rewarding for everyone involved.

RECORDS

Points of Contact

Mechanical Copyright Protection Society, Elgar House, 41 Streattham High Road, London SW16 1ER. Tel: (0181) 769 8792.

Performing Rights Society, 29-33 Berners Street, London W1P 4AA. Tel: (0171) 580 5544.

Phonographic Performance Limited, Ganton House, London W1V 1LB. Tel: (0171) 437 0311.

The Radio Authority, 14 Great Queen Street, Holborn, London WC2B 5DG. Tel: (0171) 430 2724.

Information

Radio Cracker Ballymena are planning to broadcast again at Christmas in 1996. They have had a float at the Mayor's Parade for the town's Summer Festival, and provided a 'roadshow' as part of the festivities. Other events have taken place, with many more planned. Some of those involved are planning a trip to India to see the GMTV/Christmas Cracker hospital, where a ward has been named after the Ballymena group, to mark their contribution to Cracker's third world work.



High Areal Density DISK DRIVE TECHNOLOGY

by Frank Booty

The figures are fascinating. IBM's \$380M infusion into its innovative hard disk drive technology – known as the magnetoresistive recording head or MR head – represents a key expansion of its OEM business. The MR head makes disk drives less costly to build and more reliable. According to Dave Ensberger, vice-president of HDD business line management at storage systems division, "OEM business represents half of our revenue today, and is expected to triple over the next three years. MR head customers are expected to include Hitachi, Fujitsu, and Seagate."

About the size of a pin head, the MR head enables the recording of ever-increasing amounts of data on the part of a hard disk known as a platter. More data can be packed onto a platter with an MR head than on a platter with an existing thin-film head. Units with MR heads are less expensive to build, more reliable, and require less power to operate because they have fewer parts and components. Earlier this year, IBM announced the world's first magnetic disk drive products to exceed one billion bits of data in a square inch of disk space (a billion bits is equivalent to 62,500 double-spaced, typewritten pages, or enough paper to make a stack 7m tall). Drives with 1.3G-bit/in.² – 1.3 billion bits/in.² – areal densities are being marketed, enabling greater capacity for end user data, and enhanced performance through higher data rates.

How's it all achieved? Through a mix of IBM-developed technologies, like MR heads, partial response/maximum likelihood (PRML) channels, and No-ID sector formatting. When IBM announced the MR head back in 1994, market research predicted the number of heads produced would double each year to reach 77.7 million heads this year. While the bean counters will have to wait until 1997 to verify this, consider the 10% growth per year for all heads (including metal-in-gap/ferrite, thin film, and MR) for the same period. IBM's Almaden Research Division near San Jose insists this vigorous demand points to the beginning of the era of magnetosensitive heads for hard disk drives.

Applications for the MR Head

The data storage industry – fast assuming a more key position in the Internet and information superhighway industry – is seizing on MR technology as an enabler in producing competitive products with "superior capacity, performance, and reliability". Back in 1991, Big Blue pioneered the use of MR heads with the introduction of a 1G-byte 3.5-in. product that had the industry's highest areal density at the time. Since then, the company has produced a number of industry leading products, including the first 1-in. high, 1G-byte disk drive.

The high areal densities attainable with MR heads have enabled IBM to produce disk drive products that permit storage capacity with a minimum number of head and disk components. The theory? Customers receive products with higher reliability for less cost. Products having fewer components also require less power to operate, an important feature for small drive applications in portable, battery operated systems and in large arrays of closely spaced drives, where heat dissipation and cooling can be factors. There has been a huge increase in areal densities for IBM disk drive products since 1980, initially due to thin film head technology. However, recent (post 1991) accelerated 60% compound growth rates have been made possible through the use of MR heads. The areal density of one billion bits of information (gigabits) per square inch of disk surface was demonstrated by IBM back in 1989.

Now the talk is of 10G-bits within the next four years. The MR head's basic design comprises separate read and write elements formed over each other and sharing common material layers. The write element is a thin film inductive head. This optimised design is easier to build than inductive heads that must perform both read and write functions, since it requires fewer copper coils, material layers, photolithographic masking operations, and head tolerance controls. Consequently, higher process yields are achieved, with the knock-on effect of reduced manufacturing and end user costs.

The Magnetic Recording Process

The read element comprises an alloy film, usually NiFe, that exhibits a change in resistance in the presence of a magnetic field – the MR effect. Shielding layers protect the MR elements from other magnetic fields. The second shield also functions as one pole of the inductive write head, giving rise to the term 'merged MR head'. In Figure 1, a merged MR head is shown flying over a rotating disk. The inductive element writes bits of information as magnetically biased regions within radially concentric areas or tracks that are subsequently read by the MR sensor.

The presence of a magnetic transition or flux reversal between bits causes the magnetisation in the MR sensor to rotate. This rotation can be detected directly as a resistance change by a precision amplifier, which produces the stronger signal that relays the information to the disk drive's electronics channel. Electricity passing through the MR sensor creates a magnetic field that interacts with the magnetisation of the underlying soft film. This transverse biasing ensures the magnetic rotation in the MR film occurs at an optimum angle with respect to the sense current, producing the preferred linear responsive MR signal. To maintain the MR sensor's stability and suppress magnetic domain noise, a longitudinal bias is also applied by an additional structure, the exchange bias, or hard bias, layer. This may be configured at and along a junction of the MR element and its electrical contacts.

Sensor element structures featuring both transverse and longitudinal biasing are used in existing disk drive products. It is expected that MR head technology will continue with a straightforward, scaled evolution to meet future areal density requirements. Advanced, high areal density heads will contain progressively thinner magnetic films and narrower MR elements. In the search for new materials that would allow MR heads to be scaled to the very small dimensions needed for areal densities greater than 1G-bit/in.² while maintaining good signal amplitude, scientists at IBM have developed films that exhibit the 'giant MR' (GMR) effect.

Spin-valve heads – based on GMR structures – produce a different signal amplitude behaviour to magnetoresistive heads as the layer thicknesses are reduced. This unique result is caused by the presence of a thin metal interlayer that maintains micro-magnetic regions within the MR film. GMR structures

PROJECT

Signal Activated AMPLIFIER

Design by Alan Williamson

Text by Alan Williamson and Maurice Hunt

This article describes a versatile general-purpose amplifier with a particularly useful feature – it automatically switches into a power saving standby mode following a preset delay if no signal is present on the input, yet switches back into action (almost) immediately if an input signal again becomes present.

The amplifier has many applications where power saving when the system is not in use is an important consideration, and/or where the amplifier is little used but

needs to be active instantly when required. This amplifier will fulfil these requirements without a time-wasting switch-on routine to go through beforehand.

In addition, the amplifier is designed to operate from either an internal battery, or an external power supply. If the optional rechargeable sealed lead-acid battery is installed, the power supply can also be used to trickle charge the battery, even when the amplifier is switched off. This enables the amplifier

to be ready for use whenever it is needed. The specified mylar loudspeaker is water resistant, therefore, operation in inclement weather (but not a downpour!) is possible.

Circuit Description

Refer to the block and circuit diagrams, shown in Figures 1 and 2, respectively. The sections are described individually for clarification of their operation.

PROJECT RATING 2

Kit Available
Order as LT93B
Price £39.99

FEATURES

Automatic power-saving function

Adjustable timeout period

Amplifier active indicator LED

Built in internal battery charger

Water-resistant loudspeaker

APPLICATIONS

Intercoms

Announcers

Telephone amplifiers



The completed unit.

Amplifier

The TDA2005M (IC1) is a stereo power amplifier IC (optimised for bridged mono; hence the 'M' designation), connected in a non-bootstrapped bridge configuration to increase output swing capability, i.e. one inverting and one non-inverting amplifier with the load (speaker) connected between the two outputs.

The input signal from JK1 is applied to the volume control RV1, then to the input of the non-inverting amplifier, the gain of which is determined by $(R1/R4)+1$. The feedback signal to the non-inverting amplifier is sniffed off by R3 and applied to the inverting amplifier input, the gain of which is determined by $R2/R3+R4$.

Connecting a capacitor (C8) to pin 3 of IC1 (the Supply Voltage Ripple Rejection input) will stabilise the IC's internal





bias network; the value of the capacitor is a compromise between 'turn on delay' and 'switch on thump' – larger values for C8 will increase the turn on delay and reduce thump, smaller values will have the opposite effect.

Trigger

The signal from the input socket (JK1) is also applied to RV2, the sensitivity control. TR1 combined with R8 & R9 form a common emitter amplifier, C11 & C13 AC couple the signal in to and out of the amplifier, blocking the DC component; diode D2 half-wave rectifies (clips off the negative half of the waveform) signal, while resistor R10 prevents the input of IC2 from floating.

IC2 is a programmable timer configured in a monostable mode which is retriggerable; when pin 6 is taken high, the output will become active low,

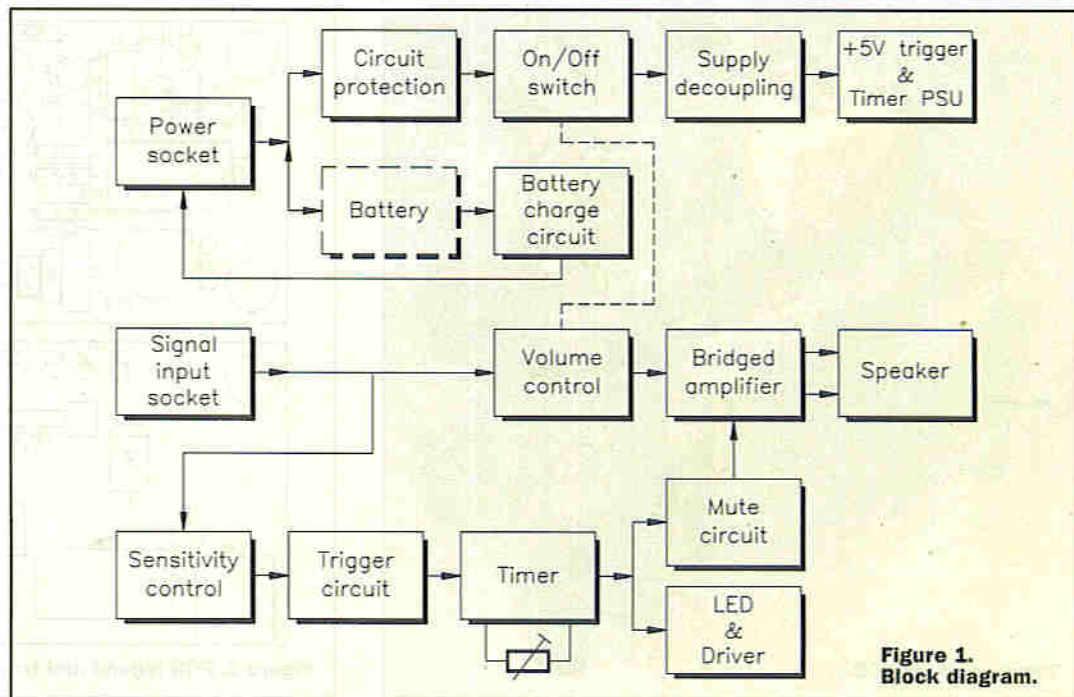


Figure 1. Block diagram.

SPECIFICATION

Operating voltage:	8-15V DC (12V nominal) external PSU or internal sealed lead-acid battery
Standby current consumption:	2.3mA @ 8V 3.7mA @ 12V 39mA @ 15V
Maximum current consumption:	1.2A (activated)
Maximum power consumption:	18W
Delay before standby state activated:	variable, between approximately 25-180 seconds (3 minutes)
Input impedance:	20kΩ
PCB dimensions:	88 × 91mm (before snapping) 88 × 45mm (each PCB when separated)

and the timeout period begins when pin 6 is returned to logic 0. Should the input become high again during the timeout period, the output will remain low but the timeout sequence will be aborted; a new timeout sequence will begin when the input returns to a low condition.

The output period 't' can be calculated from the formula:
 $t = 65,536 \times 2.3 \times (R11 + RV3) \times C14$

With the values given, the minimum timeout period is 24.87 seconds and the maximum period is 180.73 seconds (3 minutes).

Transistor TR2 is used to short circuit C8, keeping the power amp (IC1) in a standby condition until the timer (IC2) is activated. TR3 is used as a power switch for the LED (LD1), which illuminates only when the timer is active.

PSU

Power for the unit can either be derived from the power socket or the internal battery;

NOTE that when using an +15V external supply, the internal battery will be trickle charged – even when the unit is switched off. (Note: lower voltage external PSUs will not charge the internal battery.)



Construction

Refer to the PCB legend and track drawing, shown in Figure 3. Construction is fairly straightforward, but a few pointers may be helpful.

Begin with the smallest components first, working up in size to the largest. Be careful to correctly orientate the polarised devices, i.e. electrolytic capacitors, diodes, transistor, regulator and timer IC, which should be inserted into its socket (ensuring the end notches of both align with the PCB legend marking) last of all. Use the component lead offsets for the PCB links.

The four PCB pins are fitted to B+, B-, SPK+ and SPK-. Fit the clips to the fuse, then insert

Figure 2. Circuit diagram.

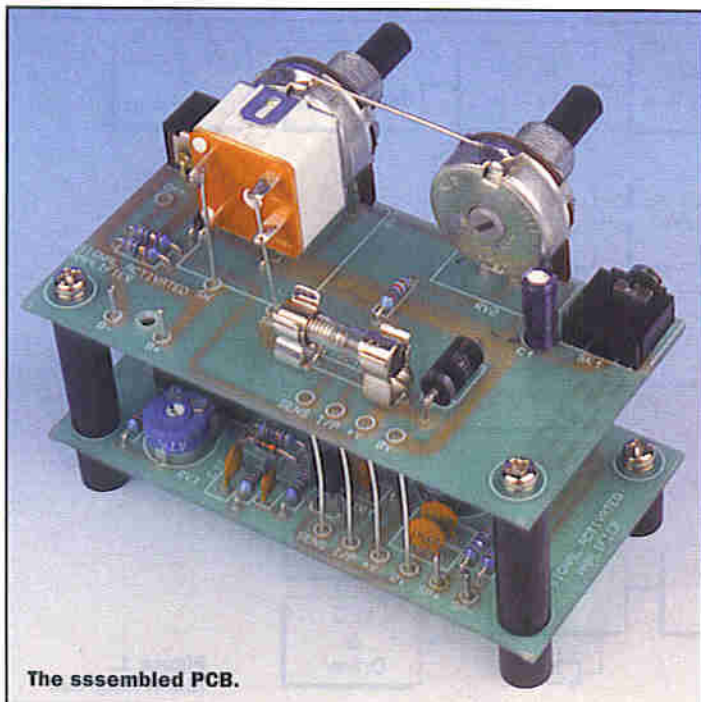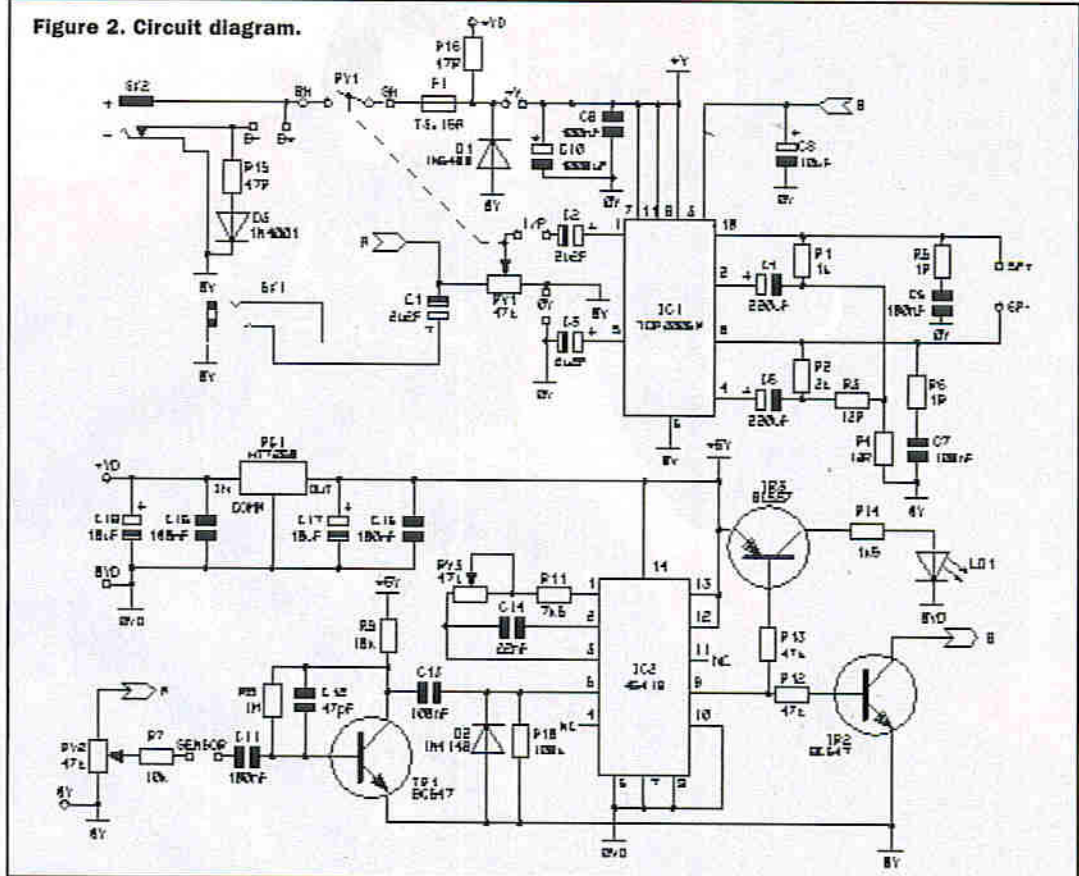

The assembled PCB.

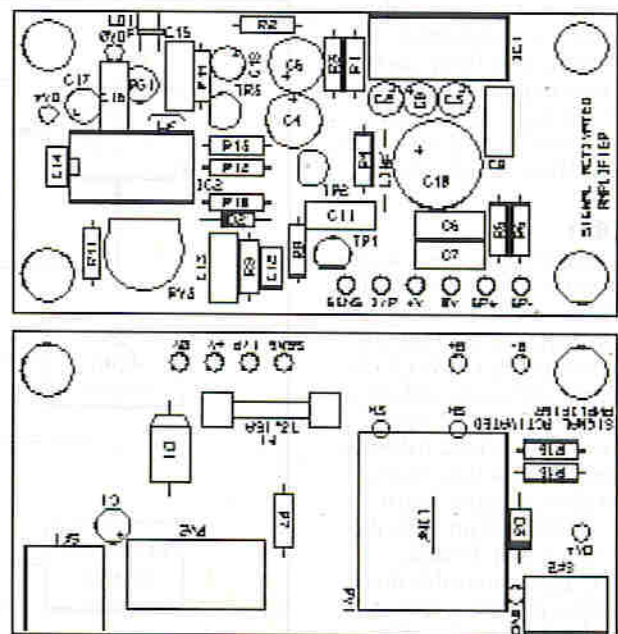


Figure 3. PCB legend and track.

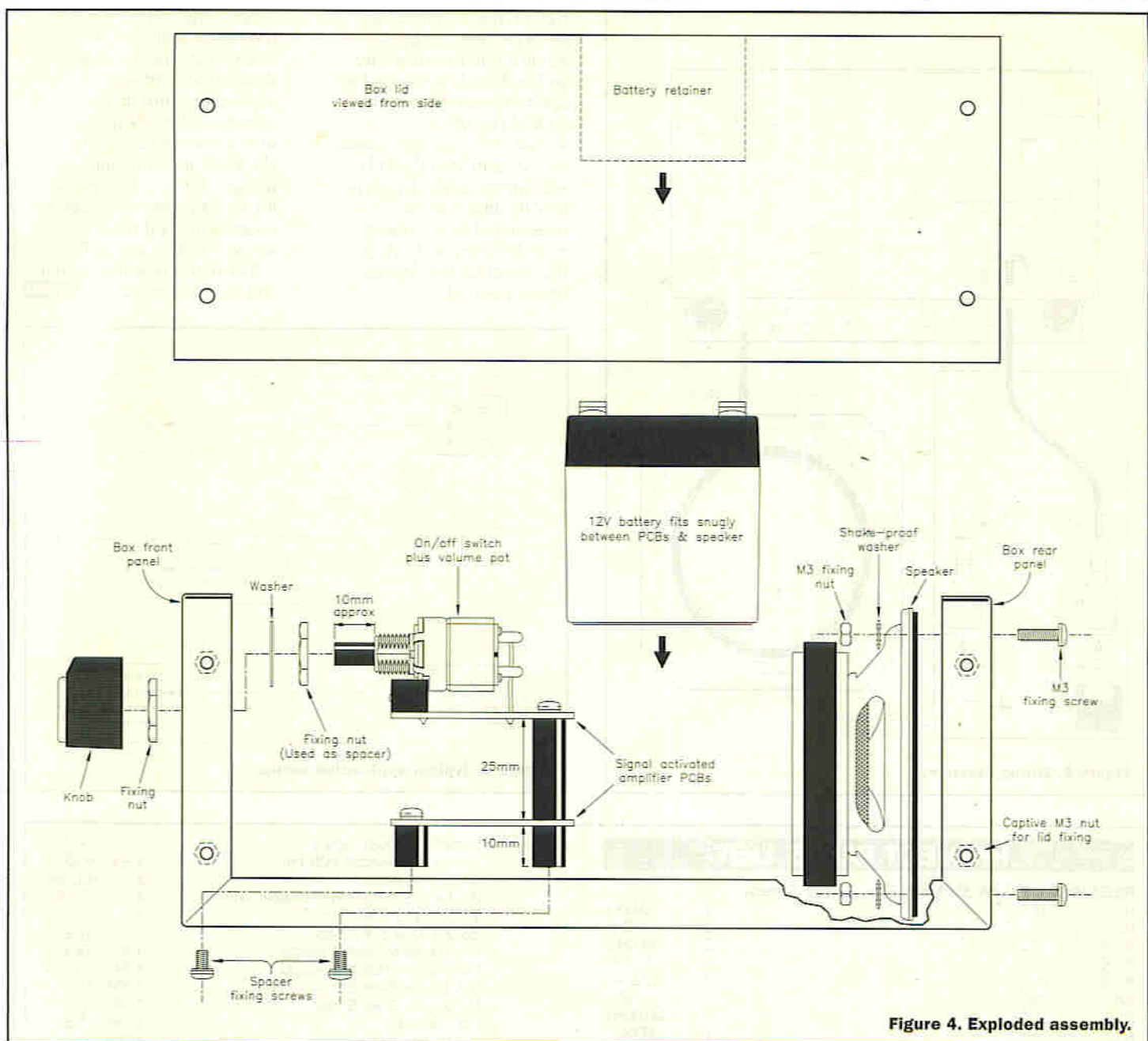


Figure 4. Exploded assembly.

into the PCB. Temporarily fit the 10mm spacers to the bottom PCB, insert the power amp (IC1) and the preformed LED into the PCB; adjust the height of the LED & IC1 to align with the holes in the enclosure, then solder in place. Trim the potentiometer shaft lengths to 10mm before installing into the PCB.

When each PCB is fully populated, thoroughly check your work for misplaced components, solder whiskers, bridges and dry joints. Finally, clean all the flux off the PCB using a suitable solvent.


Refer to Figure 4, the exploded assembly diagram. Prepare the 25mm spacers as shown, then assemble the two PCB's together. Straighten out the tinned copper wire and make the six inter-PCB connections; NOTE that the OVD connection

is also used to connect to the screening cans of the potentiometers. Fit two more links from the top PCB to the switch connections of RV1. Fit the module and speaker into the enclosure.

Referring to Figure 5, complete the wiring to the speaker and internal battery—do not forget to fit the terminal insulators. Finally, fit the knobs to the potentiometer and the rubber feet to the base of the box. Before going any further, double-check EVERYTHING!

Testing

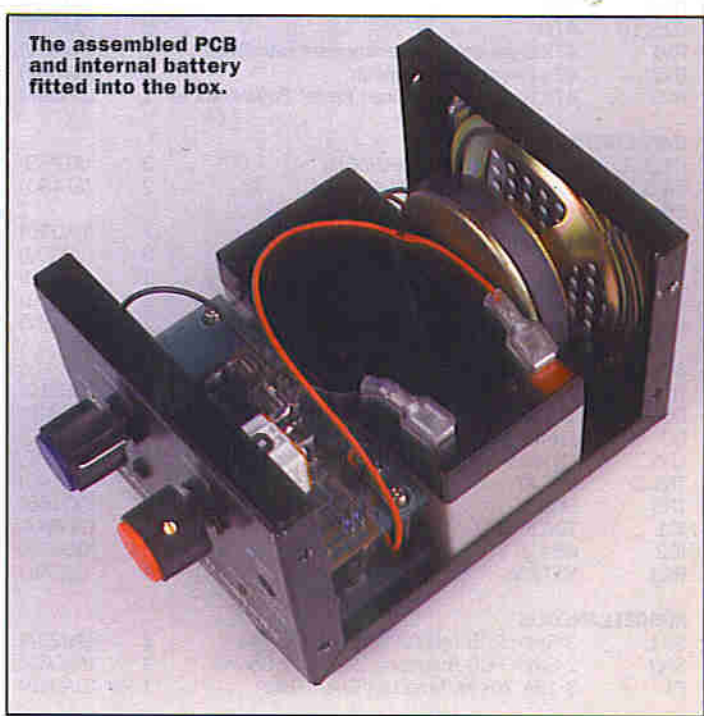Begin by setting both potentiometers to their fully anticlockwise wiper positions, then put the battery on charge (use a constant voltage charger; Ni-Cd & car battery chargers are NOT suitable for this lead-acid



The assembled PCB and internal battery fitted into the box.

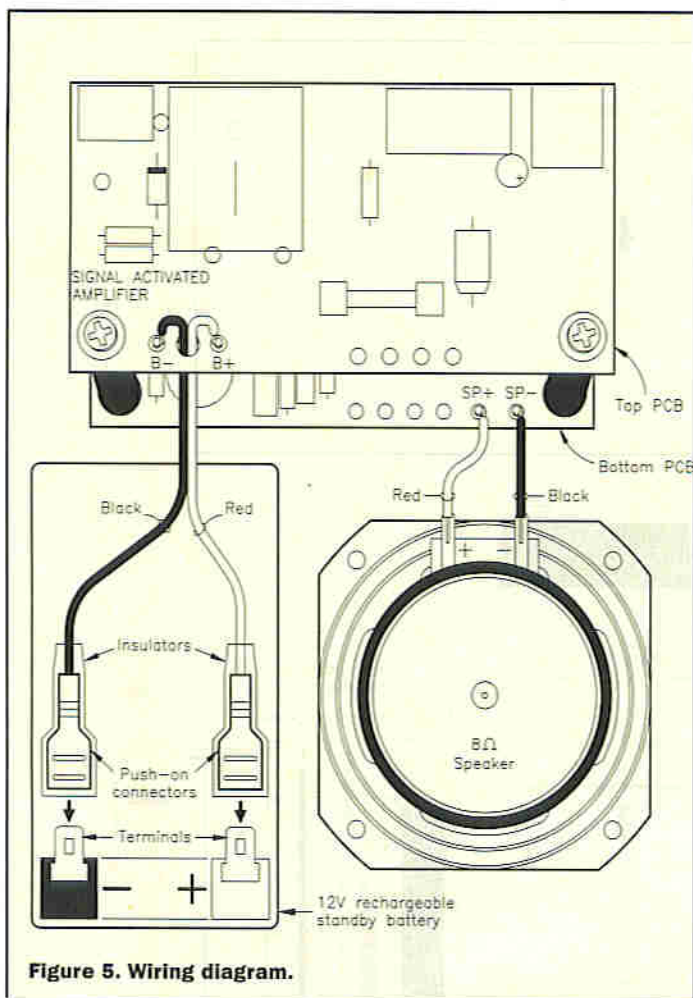


Figure 5. Wiring diagram.

type of battery). Once the battery is fully charged, install it into the enclosure and fit the lid. Switch on the unit by turning the volume control clockwise; a small click from the speaker will be heard and the LED will illuminate. The length of time the unit is active for is determined by the preset potentiometer RV3; adjust the preset for the desired timeout period.

Allow the unit to 'time out', then apply a signal to the input jack socket – refer to Figure 6, showing the wiring for a typical application. Turn up the volume slightly; then slowly turn the sensitivity control clockwise until the unit triggers; listen to the speaker for any unexpected distortions (bearing in mind that the sound quality is not Hi-Fi).

The unit is now fully tested and is ready for use.

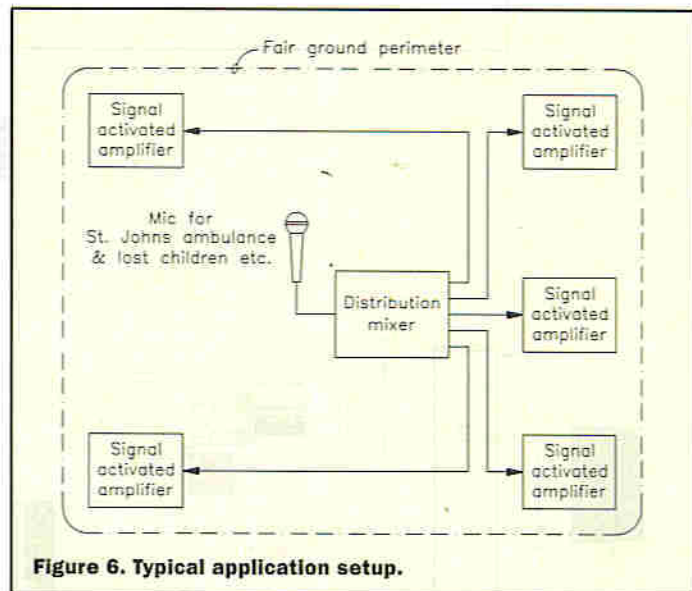


Figure 6. Typical application setup.

PROJECT PARTS LIST

RESISTORS (All 0-6W 1% Metal Film, Unless Stated)

R1	1k	1	(M1K)
R2	2k	1	(M2K)
R3,4	12Ω	2	(M12R)
R5,6	1Ω	2	(M1R)
R7,9	10k	2	(M10K)
R8	1M	1	(M1M)
R10	100k	1	(M100K)
R11	7k5	1	(M7K5)
R12,13	47k	2	(M47K)
R14	1k5	1	(M1K5)
R15,16	47Ω	2	(M47R)
RV1	47k Logarithmic Potentiometer with Switch	1	(FW65V)
RV2	47k Linear Potentiometer	1	(FW04E)
RV3	47k Horizontal Enclosed Preset Potentiometer	1	(UH05F)

CAPACITORS

C1,2,3	2μF 63V Radial Electrolytic	3	(AT75S)
C4,5	220μF 25V Radial Electrolytic	2	(AT49D)
C6,7,9,11,13,15,16	100nF 50V Ceramic Disc	7	(BX03D)
C8,17,18	10μF 63V Radial Electrolytic	3	(AT77J)
C10	1,000μF 25V Radial Electrolytic	1	(AT52G)
C12	47pF Ceramic Disc	1	(WX52G)
C14	22nF Mylar Film	1	(WW19V)

SEMICONDUCTORS

D1	1N5400	1	(QL81C)
D2	1N4148	1	(QL80B)
D3	1N4001	1	(QL73Q)
LD1	Miniature Red LED 2mA	1	(CZ28F)
TR1,2	BC547	2	(QQ14Q)
TR3	BC557	1	(QQ16S)
IC1	TDA2005M	1	(YY70M)
IC2	4541B	1	(QQ47B)
RG1	HT7250	1	(LE79L)

MISCELLANEOUS

SK1	3.5mm PCB-mounting Stereo Socket	1	(JM23A)
SK2	2.5mm PCB-mounting DC Power Socket	1	(FK06G)
F1	3.15A 20mm Time Lag Glass Fuse	1 Pkt	(DA01B)

20mm Fuse Clip Type 2	2	(KU27E)
1mm Single-ended PCB Pin	1 Pkt	(FL24B)
14-pin DIL Socket	1	(BL18U)
0.71mm 22swg Tinned Copper Wire	1	(BL14Q)
16/0.2 Wire 10m Red	1	(FA33L)
16/0.2 Wire 10m Black	1	(FA26D)
M3 10mm Insulated Spacer	1 Pkt	(FS36P)
M3 25mm Insulated Spacer	1 Pkt	(FS39N)
M3 10mm Steel Screw	1 Pkt	(JY22Y)
M3 16mm Steel Screw	1 Pkt	(JY24B)
M3 Steel Nut	1 Pkt	(JD61R)
M3 Shakeproof Washer	1 Pkt	(BF44X)
Mylar Speaker 76mm Square	1	(YN01B)
Red Knob Type RN15	1	(FE76H)
Blue Knob Type RN15	1	(FE74R)
Push-on Receptacle	1 Pkt	(HF10L)
Push-on Receptacle Covers	1 Pkt	(FE65V)
Stick-on Feet Square	1 Pkt	(FD75S)
3/4in. Hole Plug	1	(JX60Q)
PCB	1	(GJ75S)
Box	1	(BL96E)
Instruction Leaflet	1	(XZ28F)
Constructors' Guide	1	(XH79L)

OPTIONAL (Not in Kit)

12V 1.2Ah Lead-Acid Battery	1	(YJ69A)
-----------------------------	---	---------

The Maplin 'Get-you-Working' Service is available for this project, see Constructors' Guide or current Maplin Catalogue for details. **The above items (excluding Optional) are available as a kit, which offers a saving over buying the parts separately. Order As LT93B (Signal Activated Amplifier) Price £39.99**

Please Note: Where 'package' quantities are stated in the Parts List (e.g., packet, strip, reel, etc.), the exact quantity required to build the project will be supplied in the kit.

The following new items (which are included in the kit) are also available separately, but are not shown in the 1996/97 Maplin Catalogue. **Signal Activated Amplifier PCB Order As GJ75S Price £3.69**
Signal Activated Amplifier Box Order As BL96E Price £17.99

MPS

MAPLIN PROFESSIONAL

EDUCATIONAL SUPPLEMENT

December 1996



MPS

MAPLIN PROFESSIONAL

EDUCATIONAL SUPPLEMENT

Welcome to the first of a new series of Educational Supplements from Maplin MPS. We hope pupils and students will find the information presented here useful. A variety of products, those typically used in CDT or the Physics Laboratory are featured here. Many more suitable components and products also appear in the current MPS Catalogue.

Call Maplin MPS now, to order all your components.

Mini-Circuits FOR EDUCATION

Two-Tone Train Horn

This is a simple sound effects unit for model railway enthusiasts. On pressing the push-button switch, a two tone horn sound is produced of the type associated with diesel locomotives. In other words, an initial tone lasting about one second in duration, followed by a tone 50% higher in pitch, and also having a duration of about one second. If preferred, the horn can be triggered automatically at a certain point on the track (just before a level-crossing, for instance). Automatic triggering is possible using a reed switch under the track, and a magnet fitted in a piece of the rolling stock.

The circuit, shown in Figure 1, is based on three 555 timers. Two of these operate as monostables which control the timing of the tones, and the third actually generates the tone. IC3 acts as the tone generator, and it operates in a standard 555 astable mode. The output of IC3 drives a high impedance loudspeaker via a simple low-pass filter (R6 & C5). The filter provides a more realistic sound by removing the higher frequency harmonics in the output signal. Note that IC3 should be a standard 555 and not a low power type. Low power versions of the 555 are not very good at driving low impedance loads, and will not give good results in this circuit. LS1 must be a high impedance (50 Ω or greater) loudspeaker, and not an 8 Ω type.

IC1 is a standard 555 monostable which has its trigger input taken high by R2 under standby conditions. The trigger input is taken low when

S1 is operated, and an output pulse is then generated at pin 3 of IC1. R1 and C2 set the pulse duration at about 2 seconds or so. This pulse is used to control the gate input of IC3. Normally the gate input at pin 4 is held low and no oscillation is produced. During the output pulse from IC1 the gate input is taken high, and a tone is generated by the circuit.

IC2 is the second monostable, and this is triggered at the same time as IC1. It has a shorter output pulse duration which is set at just over one second by R3 and C3. The output pulse from IC2 is coupled to the modulation input of IC3 via VR1. During the initial second or so after triggering, the output of IC2 will be high, and it will pull the output frequency of IC3 lower. IC3 will remain switched on for a little over a second once the output pulse from IC2 has ceased. With IC2's output low, the tone from IC3 is pulled higher in pitch. VR1 is adjusted to give the correct difference between the pitches of the two tones.

Low power 555s are used for IC1 and IC2 in order to minimise the current consumption of the circuit. Under quiescent conditions the current consumption is about 8mA, but it increases to about 20 to 25mA when the horn is sounding. A fairly high capacity battery is needed, such as six AA (HP7) size cells in a plastic holder. Connections to the holder are made via a standard PP3 battery clip.

Construction of the unit is very straightforward. Although the lower power 555s use CMOS technology, they do not require any special handling precautions. If you require manual and automatic triggering, simply wire the reed


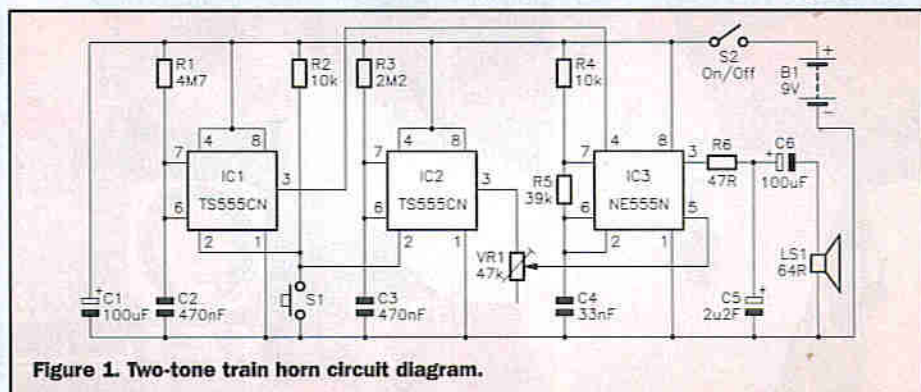


Figure 1. Two-tone train horn circuit diagram.

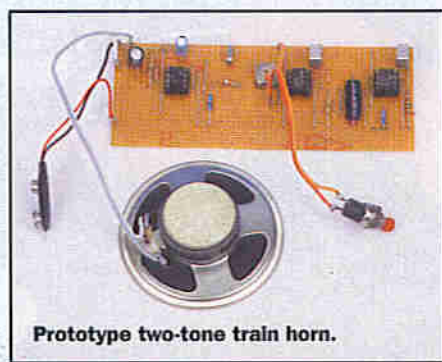

Prototype two-tone train horn.

switch and the push-button switch in parallel. In fact it is possible to trigger the circuit from several reed switches at strategic points around the track by simply wiring them all in parallel. VR1 is adjusted by trial and error to obtain what is judged to be the most realistic effect. When triggering the unit manually make sure that you only operate S1 momentarily. If it is held down for a second or more the timing of the circuit will be affected, and the correct effect will not be produced. If desired, the duration of the sound effect can be changed by altering the values of R1 and R3. The total duration of the sound is proportional to the value of R1. R3 should be maintained at about half the value of R1.

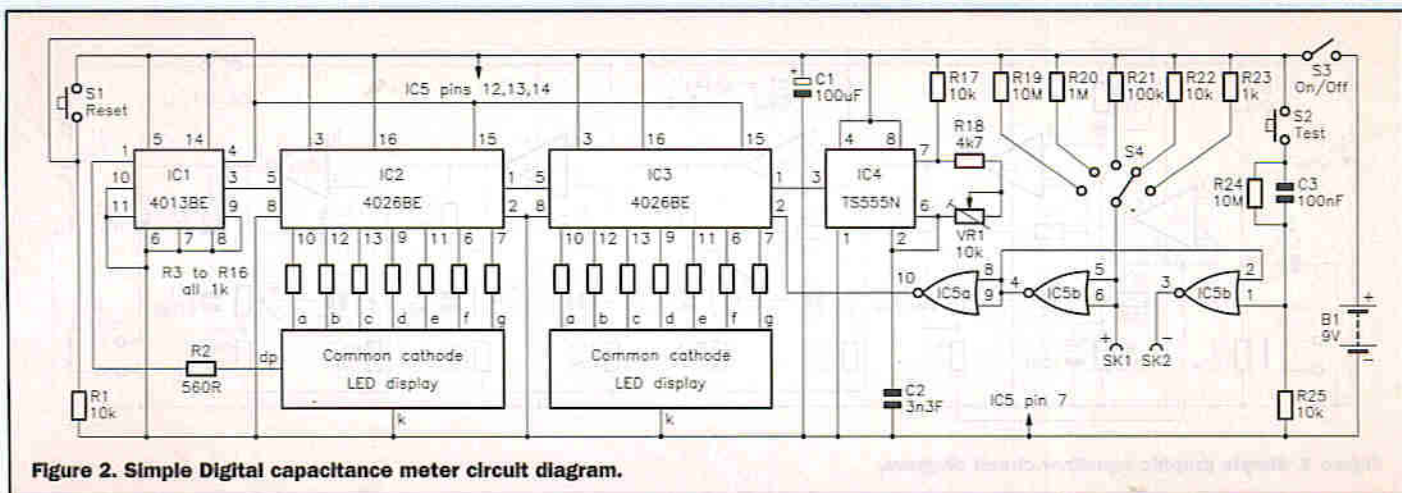


Figure 2. Simple Digital capacitance meter circuit diagram.

Simple Digital Capacitance Meter

This digital capacitance meter provides an interesting alternative to a simple analogue capacitance meter. The cost is comparable to an analogue equivalent, and the resolution and accuracy of the two digit display is at least as good as that provided by a small panel meter. The unit covers a useful spread of capacitance values in its five measuring ranges. These have full-scale values of 990pF, 9.9nF, 99nF, 990nF, and 9.9µF. An overflow indicator is included.

In order to keep the unit as simple as possible the control logic has been kept to a bare minimum. In effect, the user provides some of the control logic by pressing a push-button switch when a reading is required, and operating a second button to reset the display to zero before the next reading is taken. The circuit diagram is shown in Figure 2. Looking at the operation of the circuit in broad terms, IC5 acts as a monostable which has the test capacitance as the capacitive element of the C-R timing circuit. IC4 acts as a clock oscillator which feeds into a two digit counter based on IC2 and IC3. The output pulse from the monostable controls the gate input of the counter circuit, and the count only proceeds during an output pulse from the monostable. The higher the test capacitance, the longer the monostable pulse duration, and the higher the count. There is a linear relationship between the test capacitance and the number of clock pulses registered by the counter. In practice the clock frequency is chosen so that the counter directly indicates the test capacitance.


Looking at the circuit in a bit more detail, the monostable is based on two CMOS NOR gates (IC5b and IC5c). The low self-capacitance of this configuration ensures good accuracy with small test capacitances. IC5a acts as an inverter at the output of the monostable. This gives a better output waveform and also provides output pulses of the correct polarity for the gate input of IC3. The fourth gate in IC5 is left unused. S4 provides five switched timing resistances which give the unit its five ranges. R19 provides the 990pF range - R23 provides the 9.9µF range. S2 is used to trigger the monostable and take a reading. R24 and C3 provide 'debouncing' for S2.

The clock oscillator is a standard 555 astable. A low power 555 is used in order to keep the current drain from the battery as low as possible. VR1 enables the clock frequency to be adjusted, and this is the calibration control. The counter is a straightforward design based on two CMOS 4026BE decade counters and display drivers. The carry out output of IC2 drives the input of a 'D' type flip/flop (IC1). The 4013BE is actually a dual flip/flop, but in this circuit only one section is utilized. This acts as a sort of data latch which


switches on the overflow indicator if the count goes beyond '99'. With a two digit display and right-hand decimal points, it is not really possible to use the decimal point segments for their intended purpose. Therefore, the decimal point of one display is used as the overflow indicator, and the other one is simply left unused. It is still quite easy to convert readings into their corresponding capacitance values. S1 is used to reset both the main display and the overflow indicator. The current consumption of the circuit varies depending on the number of display segments that are switched on, but it is in the region of 50mA. This requires the use of a fairly high capacity battery, such as six AA (HP7) size cells in a holder.

When constructing this project bear in mind that, apart from IC4, the integrated circuits are CMOS types. They therefore require the standard antistatic handling precautions. The displays must be common cathode LED types. IC3 drives the units display (i.e. the right-hand display). A holder for the display is made by cutting a 20-pin DIL holder into two 10-pin SIL types, or 'Soldercon' pins can be used. SK1 and SK2 can be a couple of 1mm sockets mounted on the front panel of the unit, and many capacitors will readily connect to these. However, a couple of test leads terminated in small crocodile clips will be needed in order to make the connections to some types of capacitor. Alternatively, a pair of crocodile clip leads can simply be hard wired direct to the circuit board.

A close tolerance capacitor is needed in order to calibrate the unit. The unit can be calibrated on any range, and the value of the calibration capacitor should be at least half the full-scale value. For example, an 8.2nF capacitor could be used to calibrate the unit on the 9.9nF range (R20 switched into circuit). A series of readings would be taken, and VR1 would be adjusted by trial and error to obtain a consistent readings of '82' on the display. One final point is that capacitors should always be discharged before connecting them to any capacitance meter.

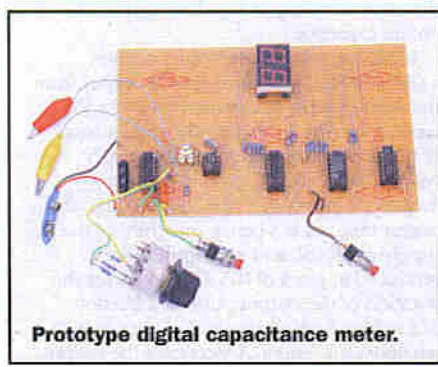

Prototype digital capacitance meter.

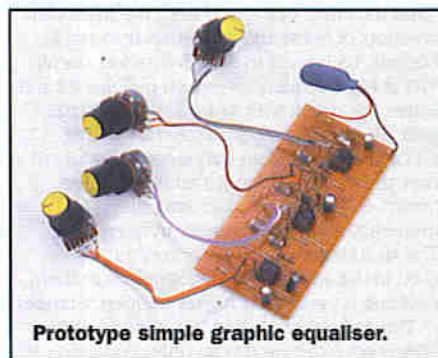

Prototype simple graphic equaliser.

Simple Graphic Equaliser

A full-blown graphic equaliser covers the entire audio range in about eight to ten bands, with each level control covering roughly one octave. These days many audio devices incorporate a sort of cut down version of graphic equaliser. These are frequently found in 'ghetto blasters', and even personal stereo units. They usually have four or five level controls with each one covering a couple of octaves or so. This obviously gives far less precise control than a full graphic equaliser, but, on the other hand, it is much better than simple bass and treble tone controls.

The circuit in Figure 3 is for a simple four band graphic equaliser. The approximate centre frequencies of the controls are 80Hz, 400Hz, 1.8kHz, and 8kHz. These respectively control the bass, lower middle, upper middle, and treble frequencies. Each control can provide a maximum of about 12dB of boost and cut at its centre frequency. The frequency response is essentially flat with all four controls centred, and the voltage gain is then approximately unity.

IC1 acts as a buffer stage at the input of the circuit, and it provides an input impedance of about 50kΩ. The buffer stage is followed by a series of four response shaping circuits, one for each band. All four stages utilize the same configuration, and this is based on an operational amplifier in the inverting mode. R4, R5 and C3 provide a half supply bias for the non-inverting inputs of all four stages.

If we consider the operation of the first stage (which is based on IC3a and covers the lowest frequency band), R3 and R6 are a negative feedback network which sets the voltage gain at unity. However, frequency selective negative feedback is provided by R7, R8, VR1, C4, and C5. If we ignore C5 for the moment, C4 significantly shunts R6 at high frequencies when the wiper of VR1 is at the top end of its track. This gives increased feedback at high frequencies, and high-frequency cut. With the wiper of VR1 at the bottom end of its track, C4 shunts R3 at high frequencies. This gives reduced negative feedback and high-frequency boost. R3 and R8

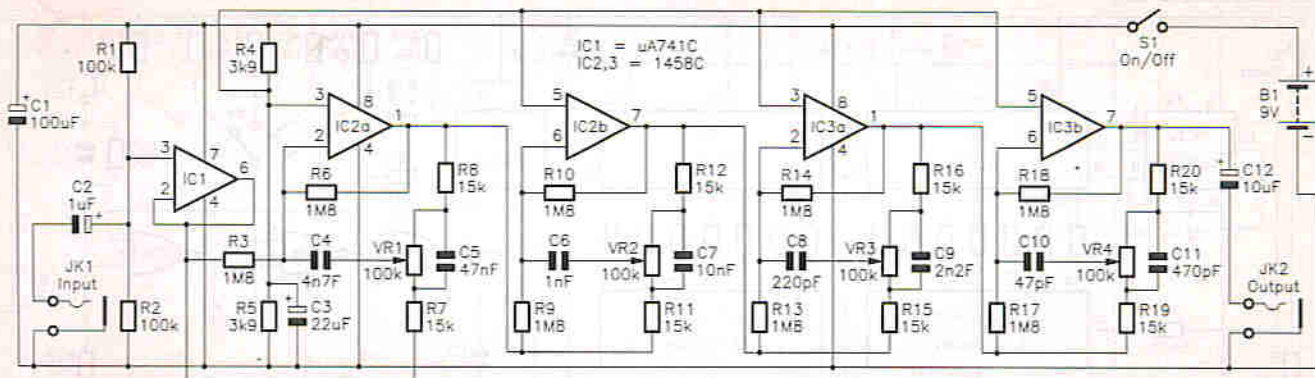



Figure 3. Simple graphic equaliser circuit diagram.

limit the effect of C4, and keep the maximum amounts of boost and cut within reasonable bounds. C5 is used to effectively short circuit VR1 at high frequencies, which nullifies C4 and leaves the circuit with its basic unity voltage gain. The circuit values are chosen so that C4 can introduce high-frequency boost or cut over the frequency range that is of interest, but C5 eliminates any doctoring of the frequency response at higher frequencies. The steadily reducing capacitance values used in the subsequent stages results in them covering progressively higher frequency ranges.

The component layout is not particularly critical since the circuit can only produce a modest amount of voltage gain. It should be borne in mind that setting a level control for 'cut' results in the relevant operational amplifier having less than unity voltage gain. This does not seem to produce any problems using 1458Cs for IC2 and IC3, but many operational amplifiers can become unstable when used at less than unity voltage gain. The LF353N for example, does not seem to work well in this circuit, with severe high-frequency instability occurring at some control settings. It is therefore advisable to use the humble 1458C for IC2 and IC3, rather than a more modern device, unless the alternative device is known to be stable when used at less than unity voltage gain. The current consumption of the circuit is only about 5mA, and a PP3 battery is therefore perfectly adequate as the power source.

Audio/Visual Metronome

The original metronomes were purely mechanical devices having clockwork mechanisms ('Maelzel's' metronomes). These are rapidly becoming collectors items, and modern metronomes are of the electronic variety. Mechanical metronomes have a swinging arm, rather like an inverted pendulum, and they produce a 'clicking' sound each time the arm reaches the limit of its swing. This gives both a visual and an audible indication of the beat rate.

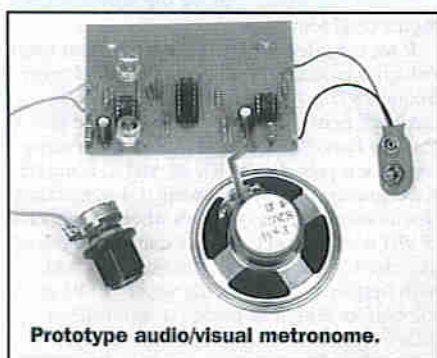

Prototype audio/visual metronome.

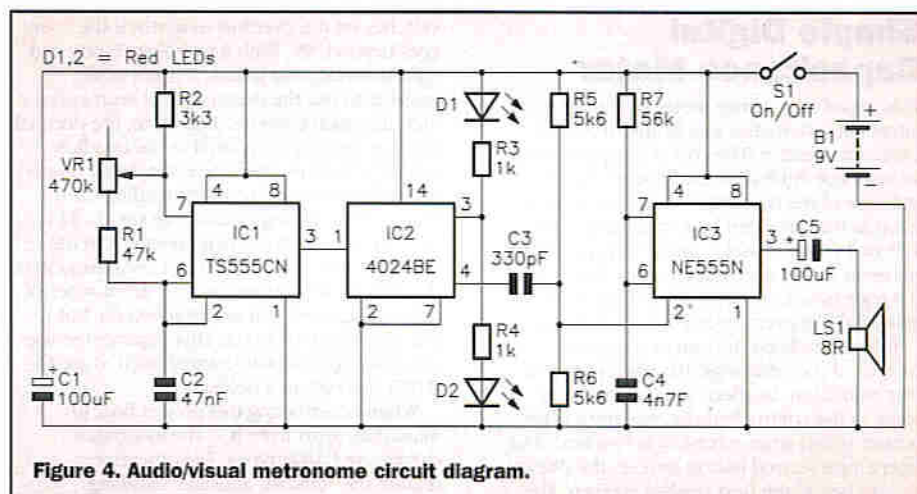


Figure 4. Audio/visual metronome circuit diagram.

This electronic metronome also produces a series of 'clicking' sounds to give an audible indication of the beat, and it provides a visual indication via two large LEDs. The LEDs are operated in anti-phase (i.e. as one switches on the other switches off), giving a form of visual indication that is roughly analogous to the swinging arm of a mechanical metronome. The beat rate can be varied from approximately 30 to 300 beats per minute.

The circuit in Figure 4 is based on two 555 timers and a CMOS 7-stage binary counter. IC1 is the clock generator, and it is a low power 555 timer used in the standard astable mode. An ordinary 555 can be used for IC1, but this will increase the current consumption of the circuit by about 8mA, with a much shorter battery life. The timing components are R1, R2, VR1, and C2. Although the 'click' rate is in the frequency range 0.5Hz to 5Hz, the clock oscillator has to operate over a much higher range of frequencies as it drives the speaker via 6 stages of the binary divider. It therefore operates at 64 times the output frequency, or in other words at around 32 to 320Hz. An advantage of this system is that it avoids the expense of a good quality, high value timing capacitor.

IC2 is the seven stage binary divider, a CMOS 4024BE. C3 couples the output from the sixth stage of IC2 to the input of a 555 based monostable circuit. The trigger input of IC3 is biased to about half the supply voltage by R5 and R6. Negative output transitions from pin 4 of IC2 briefly take the trigger input of IC3 below one third of the supply potential, and an output pulse is produced at pin 3 of IC3. R7 and C4 set the duration of the output pulse at a fraction of a millisecond, which gives a suitably high pitched 'click' sound. C5 couples the output

pulses from IC3 to a moving coil loudspeaker. I would not recommend using a low power version of the 555 timer for IC3 as many of these seem to give erratic operation when driving low impedance loads. Also, the output stages of some low power 555s cannot supply high enough output currents to give good results in this application.

The output of IC2's seventh divider stage is used to drive the two LEDs, which are connected so that they operate out-of-phase. D2 is switched on when pin 3 of IC2 goes high - D1 is switched on when it goes low. As each LED only switches on at every other 'click', the LEDs are operating at half the 'click' frequency. Hence the LEDs are driven from stage seven of IC2 while the 'click' generator is driven from stage six.

The current consumption of the circuit is about 12mA. This necessitates the use of a fairly high capacity battery, such as six HP7 size cells in a plastic holder. Construction of the unit is fairly straightforward, and the component layout is not critical. Bear in mind though, that IC2 is a CMOS device which requires the standard antistatic handling precautions. Virtually any LEDs are suitable for D1 and D2, but large high efficiency LEDs will be much more conspicuous than small low efficiency types. A scale calibrated in beats per minute must be marked around VR1's control knob. The calibration points must be found by trial and error, with the beat rate being determined by counting the number of 'clicks' in a one minute period. At high beat rates adequate accuracy should be obtained by counting the number of 'clicks' in twenty seconds, and then multiplying by three to get the beats per minute.


Model Train Signal Lights

This is a circuit for a simple three-colour signal for a model railway. It operates automatically, changing from 'green' to 'red' as the train passes the signal. After a preset time the signal changes to 'amber', and after a further period it goes back to 'green' once again. This is a sort of simplified version of the real thing, where the signals change as the train passes by sensors along the track. In this case there is only one sensor, which is positioned beside the signal. The other changes are provided by a timing circuit, which is slightly less authentic, but makes the signal much easier to install.

The circuit, shown in Figure 5, is built around IC2, which is a CMOS decade counter and one-of-ten decoder. In this case only outputs '0' to '3' of the decoder section are utilized, the other seven outputs are simply ignored.

C3, R7, and D4 supply a reset pulse to IC2 at switch-on, so that it commences with output '0' high. This switches on D1, which is the 'green' signal LED. IC1 is a 555 timer which is used here as a low-frequency clock oscillator which provides a clock pulse to IC2 every three seconds or so. The first clock pulse results in the '0' output going low, and output '1' going high. This switches off D1, and switches on D2 (the 'red' signal LED). On the next clock pulse output '1' goes low and output '2' goes high. This results in D2 switching off, and the 'amber' LED (D3) turning on. On the next clock pulse output '4' goes high, but due to the coupling through R6 this resets IC2 so that output '4' immediately returns to the low state, and output '0' goes high. This takes the circuit back to its initial state, with D1 switched on, and a 'green' signal being produced.


Some control logic is needed, so that the circuit only goes through this sequence of events when it is triggered by the passing train. The circuit must halt once it has cycled back to a 'green' signal. This control logic is provided by IC3, which is a 4013BE dual 'D' type flip/flop. In this circuit only one section of the device is used. The inputs of the unused section of IC3 are connected to the 0V supply in order to protect them against static charges and to avoid spurious operations. The other section operates really as just a simple set/reset flip/flop, with the clock and data inputs simply being wired to earth. Like IC2, IC3 is supplied with a reset pulse at switch-on. This takes the Q output low, which in turn inhibits IC1 so that no clock signal is produced. R8 ties the 'set' input of IC3 to earth, but this input is pulsed high when sensor switch S1 is activated. This takes the Q output of the flip/flop high, and activates IC3. This results in the signal changing to 'red' immediately, and to 'amber' and then 'green' after a few seconds. IC3 is reset when output '4' of IC2 pulses high, so that once the signal returns to 'green', the Q output of IC3 inhibits IC1. This holds the signal at green until S1 is activated

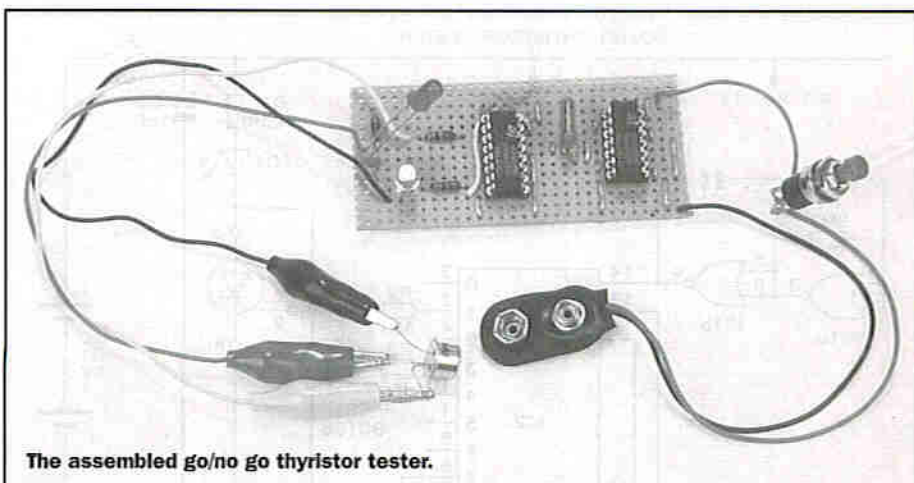

The assembled go/no go thyristor tester.

again. The sequence is then repeated, and will be repeated each time S1 is activated. The current consumption of the circuit is about 15mA, or about 7mA if a low power 555 is used for IC1.

Construction of the actual railway signal is obviously unusual. D1 to D3 must be mounted in a model signal, and it is not too difficult to improvise something reasonably convincing. Rather than controlling the LEDs directly, IC2 could be used to control them via common emitter switching transistors. This would enable a higher drive current to be used, and would also permit miniature filament bulbs to be used. S1 can be either a micro-switch or a reed type. In the case of a micro-switch, things must be arranged so that the actuator is operated by the passing train. For this application a reed switch mounted under the track is preferred. This is operated by a small bar magnet fitted in a piece of rolling stock. This method requires no direct contact with the train, which eliminates any slight risk of occasional derailments. Note that IC2 and IC3 are CMOS devices which require the usual antistatic handling precautions. The duration of the 'red' and 'amber' signals is easily altered as it is roughly proportional to the value of R2.

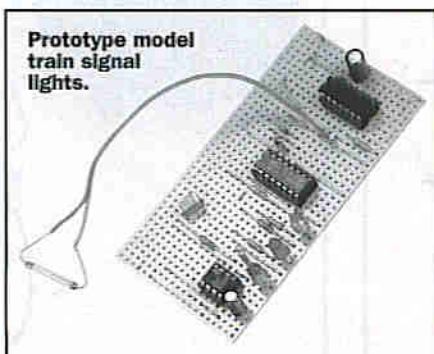

Prototype model train signal lights.

Go/No Go Thyristor Tester

This circuit (Figure 6) was designed to give a quick go/no go test of thyristors that you might find in 'bargain packs', etc. Thyristors are also known as silicon controlled rectifiers. They are like a diode, in that current can only flow one way through it. However, the thyristor has an additional terminal, known as the gate; if sufficient current is applied to the gate, then the device will stay permanently latched on. The only way to turn the device off is to either short-circuit the anode-cathode junction, or reduce the anode-cathode current below the 'holding' current, which is the minimum current necessary to keep the device on. The former method was used in this circuit. It is also possible to test thyristors using a multimeter, but this circuit has the advantage of being less 'fiddly' to use, and it also gives you an idea of how well the device under test switches from a non-conducting to conducting state.

Circuit operation is as follows: IC1a and b form a standard astable multivibrator, with a working frequency of about 2.5Hz; R1 and C1 set the frequency of the astable. Pulses from the astable are fed to the clock input of IC2, which is a '1-of-10 decoder'. As successive pulses are fed to IC2, each of its outputs will go high then low, in sequence. When the last output goes high/low, the sequence starts again. When output 1 of IC2 goes high – roughly to the supply voltage – this voltage will be fed to the gate of the device under test through R2. This turns on the thyristor, and LD1 will be illuminated. R4 is the current limiting resistor for LD1.

Now, two clock pulses later, output 3 of IC2 will go high, and this turns TR1 fully on, short-circuiting the anode-cathode junction of the device under test and, therefore, turning it off. LD1 will now be extinguished. When output 7 of IC2 goes high five clock pulses later, IC2 is reset and the whole sequence starts over again. S1 is the on/off switch, and must be pressed down long enough to see if the device under test works. C2 is a supply decoupling capacitor.

If, when testing a thyristor, LD1 is permanently on, or it does not come on at all, then the thyristor is probably suspect. When connecting a device to be tested, you can use either flying leads and clips, or sockets. Flying leads and clips were used on the prototype. A red lead and clip were used for connecting to the anode, a black lead and clip to the cathode, and a yellow lead and clip to the gate. Current consumption of the unit is about 11mA.

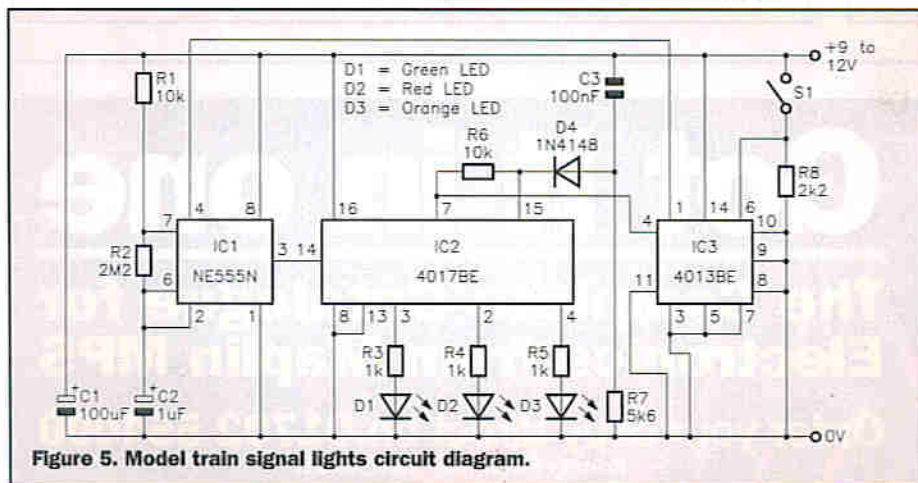


Figure 5. Model train signal lights circuit diagram.

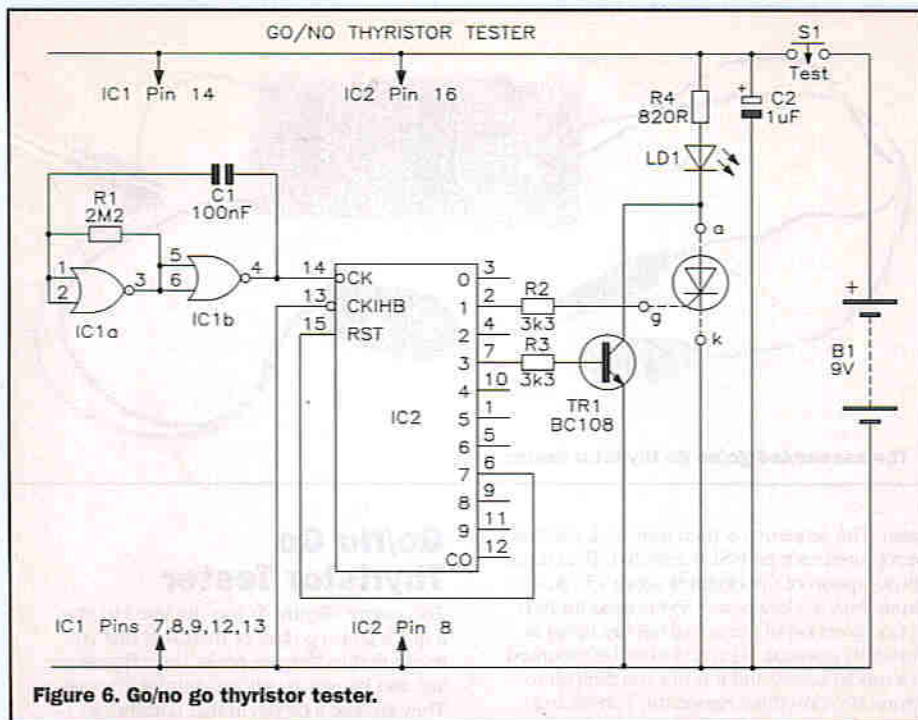


Figure 6. Go/no go thyristor tester.

The circuit is described below. It is based around a well-known square wave oscillator circuit. IC1a is an integrator, with C2 being charged and discharged through RV1, the soil resistance, and R5. IC1b forms a Schmitt trigger circuit, whose switching points are determined by R3 and R4. When the soil is wet, its resistance will be low, and therefore C2 charges and discharges faster. Therefore, the frequency of oscillation of the circuit will be higher. When the soil is dry, the resistance between the probes will be higher, and C2 will charge and discharge at a slower rate, and the frequency of oscillation of the circuit will be lower. RV1 allows the frequency of operation to be varied when the circuit is in use. The frequency of operation can be varied between about 1-3kHz for very wet soil, down to 100Hz or less for very dry soil. R1 and R2 are biasing components for IC1a and IC1b, setting the non-inverting and inverting inputs to half of the supply voltage. C1 provides AC decoupling for R2. C3 feeds the output of IC1b to LS1. It may seem unusual not to have some kind of buffer circuit between the output of IC1b and the loudspeaker, but there is enough drive from the output of IC1b to drive a high impedance speaker at a reasonable volume. The current consumption of the unit is around 9mA.

To use the circuit, place the probes into the soil to be tested, press S1 and note the tone. A low tone means that your soil is dry and should be watered. A high tone means that your soil is wet and should not be watered.

There are no special construction requirements for this circuit. The probes were made using bolts, solder tags and nuts for fixing to whatever type of case you decide to use.

Soil Moisture Tester

This circuit (Figure 7) was designed to give gardeners a quick indication of how wet or dry the soil is in their gardens or greenhouses. It can also be used to test how wet or dry the soil of house plants is. The usual way to determine the wetness or dryness of soil electronically is to measure the resistance of

the soil, and then give some kind of visual or aural indication of its value. For a visual indication, you can use circuits that drive moving coil meters or bar graph displays. However, these can be costly. It was decided to use a circuit that gave an audible indication of soil resistance because it was cheaper, and with practice you can gauge the wetness of the soil quite quickly.



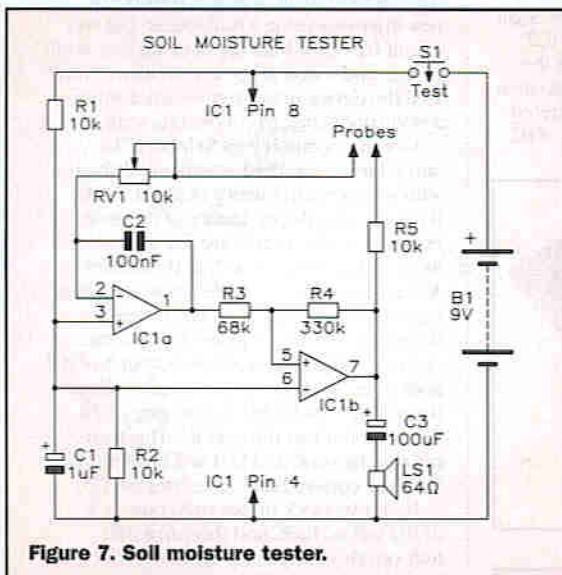


Figure 7. Soil moisture tester.

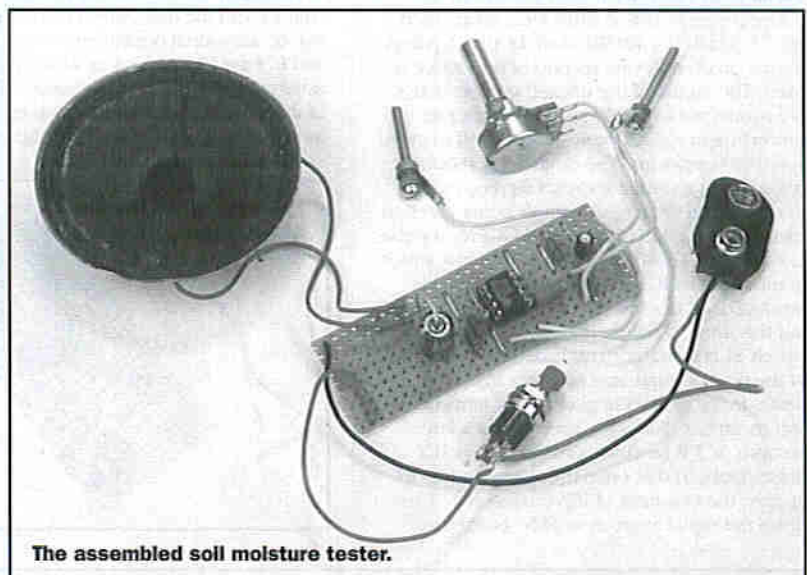

The assembled soil moisture tester.

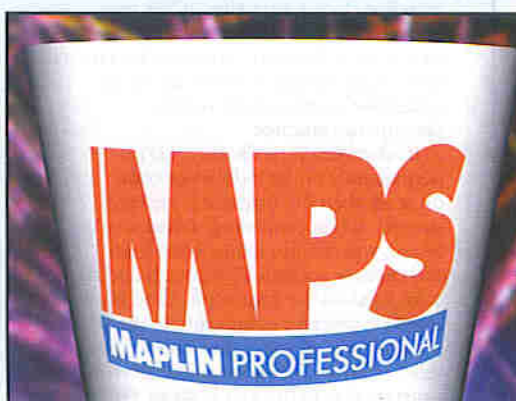


Got it in one

The Complete Catalogue for Electronics from Maplin MPS

Order your copy direct on 01702 554000

Priority reference code: MA013

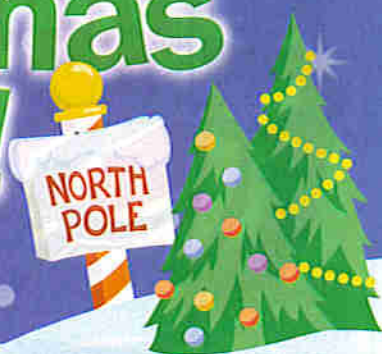Beat the festive bore with our Christmas projects galore!



Live Wire Game

See who's got the steadiest hand after the sherry trifle and a glass or two of the Christmas spirit, with this traditional game of manual dexterity! This advanced design detects even a momentary contact and incorporates a counter allowing a preset number of touches to be permitted before each person's 'life' is terminated.

PROJECT RATING 2 £27.53

Order Code 95226 (Live Wire Kit)

Project details in *Electronics* No. 78 (XA78K).



Spruce up your Christmas Tree

This fine example of arboreal high technology is decorated with 21 LEDs in three seasonal colours, which can be made to flash or twinkle at three different rates. The kit also contains a full-size template to help you make your tree.

PROJECT RATING 3 £15.29

Order Code 95224 (LED Xmas Tree)

Project details in *Electronics* No. 48 (XA48C).



Christmas Superstar

Give the fairy a rest this year and yule have the smartest tree in the street! Lift your tree's decorations onto a heavenly plane with our 19-LED, four colour, twinkling Christmas Star. The kit includes all items needed, except the star itself which you can use your own creative flair to design.

PROJECT RATING 1 £10.19

Order Code 95223 (LED Xmas Star)

Project details in *Electronics* No. 41 (XA41U).

Christmas Candle

This simple to build, electronic candle has a realistic pseudo-random flicker, but won't burn a hole in your pocket – or anything else for that matter. Ideal for decorations, nativity plays and carol singing. The kit includes constructional details of a suitable cardboard lantern for the festive season.

PROJECT RATING 1 £9.17

Order Code 95225 (Twinkling Xmas Candle)

Project details in *Electronics* No. 72 (XA72P).




Priority Quiz Buzzer

No more arguments over who answered first! The fastest finger on the button lights up that contestant's lamp and locks out all the others. Ideal for Christmas games, and quiz nights, etc. Up to eight contestants can be catered for, and the unit can be expanded to 16 or 24 by adding a second or third PCB.

PROJECT RATING 1 £13.25

Order Code 95227 (Priority Quiz Buzzer)

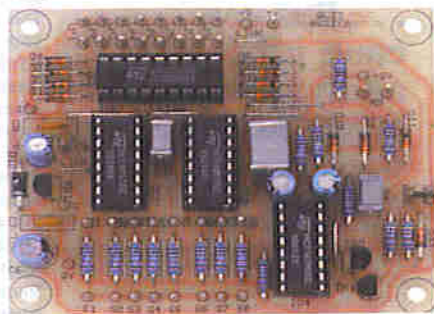Project details in *Electronics* No. 72 (XA72P).



Finish off the pud, pick up your soldering iron and make a Merry Christmas with festive projects from **MAPLIN**



E-mail your views and comments to: AYV@maplin.demon.co.uk

Write to: **Electronics and Beyond, P.O. Box 777, Rayleigh, Essex SS6 8LU**

You can please some of the people some of the time . . .

Dear Sir,

I have just finished reading your latest excellent (as always) article, on the Netscape Navigator 3.0 Browser, in my airmailed subscription copy of the September 1996 issue of *Electronics*. I've been using the 32-bit Navigator 3.0b5 for the past couple of months now and although I have not yet tried out CoolTalk, must thoroughly agree with everything else you have to say about this browser. So far, I haven't come across any discernable bugs. Fortunately, having the benefit of Netscape's CD, I didn't have to download it from their homepage. I must say, however, that I run Windows '95 on a 486DX-4 100MHz platform with 20M-byte of RAM, a 1G-byte hard drive, quad-speed CD-ROM, Pro Audio Spectrum 16 and a 28.8k-bps v34 modem, and can't imagine how anyone has the patience to get along with anything less!

dougalp@ang.sequel.net, Angeles City, The Philippines.

. . . But you can't please all the people all of the time!

Dear Editor,

I was sorry to hear that Stephen Waddington thinks he's getting a "...reduction in the cost of software..." (*Electronics* September 1996 page 73, 'Navigator 3.0 Browser'). Add up the cost of one person's time plus 'phone bills in trying to download software, retrying persistently until an error-free

copy is finally (hopefully!) obtained. Now think of the time and cost of running of an individual copy of the manual on your own printer, as distinct from the unit cost of a mass-produced version. This is NOT reduction in cost. It is the passing of a commercial organisation's costs onto the paying customer. Their profits are boosted at our expense, and Stephen Waddington has fallen for this ploy without a second thought! We hear so much about 'lean, efficient, competitive British business'. Although it sounds good, it's a myth when you start to delve more deeply. I object to the now common practice of businesses increasing their profits by making me do their work for them. If we all think about it, and apply sufficient pressure where it matters, we can stop this recent trend in its tracks.

Dr. G. L. Manning, Edgware, Middlesex.

There are many computer users/enthusiasts who are willing to spend the time downloading software from sources such as the Internet, perhaps for the reason that it represents something of a challenge, rather than simply buying a ready-packaged version - even though it may not necessarily be cost-effective in the long run. This is analogous to constructing your own electronic projects; it may be more cost-effective and sensible to purchase a ready-made product, but it's usually far more entertaining and rewarding to build your own. Additionally, with some software, a user manual is superfluous, so by downloading just the software, you would save on paying for a manual which you might not even bother reading. You would also be kinder to the environment, by avoiding the use of materials and energy that goes into making the manuals and packaging, and in transporting the end product! Sometimes, less is more.

In this issue, F. R. Morris of Peterborough wins the Star Letter Award of a Maplin £5 Gift Voucher for his suggestions on training the Watchdog.

£5 MAPLIN GIFT VOUCHER



Dear Sir,

I was very interested to read the article 'Domineye TV Watchdog' (Issue 106). The unit would appear to be ideal for further development, as if I understand correctly, it is only activated when the dedicated channel is selected on the TV remote control. This would mean that it is not affording protection during normal TV viewing, or perhaps, 95% of the time. In the applications section of the article, it is suggested that one use could be to watch over a car in the driveway, but this would only be effective when the dedicated channel is selected. This relies purely on the occupier remembering to switch over, perhaps in the middle of an interesting programme on a 'catch as catch can' basis, thus leaving time span periods without camera protection. Trusting that I have understood the unit's functions correctly, it is suitable for further development to give continuous cover, especially during darkness. This may be achieved in different ways, viz:

1. The microphone in the camera, through the modulator, could be 'audio active', thus alerting the occupiers to noises outside.
2. With a PIR sensitive floodlight installed (as suggested in the article), this could be adapted to activate an audio signal or light sensing unit to display a warning signal built into the modulator, thereby prompting the occupier to switch to the dedicated TV channel.
3. Have the camera system emit an infra-red remote control signal when movement is detected, to switch the TV to the dedicated channel automatically.

I would be interested in your views and comments into the practicalities of these options. We already have a PIR operated floodlight, and this performs satisfactorily in illuminating the driveway but does not afford any indication to us during darkness and with the curtains drawn. You will gather from my proposals

that they are intended to overcome this shortcoming by applied options.

A camera surveillance system is only effective if the people who are using it are vigilant themselves; even if a camera is monitoring a scene continuously, any action that takes place could be missed unless either someone happens to be watching the TV monitor at that instant, or a video recording is being taken (assuming the action is spotted when the video is replayed). The Domineye TV Watchdog (Order Code CD12N, £249.99) could be used in conjunction with a dedicated TV set, tuned in to show what the camera sees all the time, which would improve one's chances of noticing intruders outside, or the TV channel could be automatically switched over to the camera using the methods you mention. Your first suggestion, using the camera's built-in microphone to alert occupiers to noise outside could be problematical in noisy areas (e.g. near busy roads), with the likelihood of regular false alarms. Another possibility (a variation of your second suggestion) if you already have a PIR floodlight installed near the camera, would be to use a circuit that detects when the light switches on and passes on a signal to automatically switch the TV to the dedicated channel - or to activate a warning lamp/sounder. The Slave Flash Trigger project (Issue 98 - Order Code LP57M) could be adapted to provide this function. This would avoid having to tamper with existing mains wiring and potentially upsetting the operation of the PIR floodlight, since no direct connection to it would be necessary. Using the system to transmit an infra-red signal to automatically switch to the dedicated channel (as per your third suggestion) would be a good method, assuming you could generate the correct infra-red remote control code in the first place - perhaps a 'One-For-All' universal type remote transmitter (e.g. BV21X) could be adapted to achieve the channel switching. The Domineye system may also be used to check on callers at your door prior to you opening it, in which case, of course, you simply switch to the dedicated TV channel on hearing the doorbell or knock on the door. Alternatively, if you have dogs, you could rely on them to detect the presence of someone outside (they're remarkably effective at it!) and switch to the camera channel when you hear them barking. The dogs could then be let loose to see off any unwanted visitors.

The Generation Game

Dear Sir,

I have just read with considerable interest, C. T. F. Collett's letter on the 'gas technology of yesteryear' (Issue 107). I am referring to the extracts of the Milnes brochure for the thermoelectric generator, powered by a domestic gas supply. I am researching in the field of thermoelectrics at the NEDO Centre for Thermoelectric Engineering, University of Wales Cardiff, the largest research group of its kind in Europe, and possibly the world. Our research team have led the way forward in this field for many years, in all aspects of thermoelectricity from materials to systems. We are very interested in the information on this product, despite its age, and would appreciate it if you or the author could forward us with a copy of the brochure. This would not only be useful to our research literature, but as an interesting display item at our research centre. Perhaps you may wish to visit our research group homepage on the Internet, at <http://www.cf.ac.uk/uwcc/engin/gao/page.html>. Though still under construction, it gives an insight into this exciting field of technology.

Dr. Simon G. K. Williams,
Research Programme Co-ordinator,
NEDO Centre for Thermoelectric
Engineering, University of Wales, Cardiff.

Copies of the Milnes brochure have been passed on to Dr. Williams. Once again, thanks to C. T. F. Collett of Waterlooville, Hants, for supplying us with the brochure. Who'd have thought that a humble advertising leaflet could generate such interest after all those years?

Organised and Computerised

Dear Sir,

I read with interest, the article by Alan Simpson in the October 1996 issue of *Electronics and Beyond*. The article centred on the use of computers at 'Granada Studios Tour' at Manchester and misses completely one use of computers at Granada that links modern computer technology to the past; this is one of the aspects that the Granada Theme park is all about. The Lancastrian Theatre Organ Trust (LTOT) has, on behalf of Granada, installed the ex-Gaumont Manchester

Wurlitzer pipe organ in the Projections complex within Granada Studios Tour. To fit in with the operation of the Tours complex, the organ has been computerised and now has more computer control than any other pipe organ in Europe. The computer system used was developed as a special by Dick Wilcox, who lives in California, USA. Wilcox founded the Alpha Micro Company, and he was responsible for the design of the computer systems and software that were used in the American Space programme and were incorporated in both the US Lunar Lander and the Mars probe. The software used at Granada was all downloaded over the Internet from Dick Wilcox in 1990 before the Net became as popular as it is today. The computer hardware uses a centre core computer with a distributed telemetry system to control the 1,100 pipes in the organ. Much of this hardware was put together using the services of the Maplin shop in Manchester. Within the next few months, The Lancastrian Theatre Organ Trust will be removing the large Wurlitzer from the Free Trade Hall in Manchester to commence the task of total restoration of the organ, a part of which will be the computerisation of the organ control system. This Wurlitzer is one of the largest series of Wurlitzers built, there being only 14 in the series, and the Manchester organ was one of only two of this size and design to ever have been exported from America, its sister organ being in the State Theatre, Sydney, Australia. The sheer size of the organ presents many problems for its computerisation; the Trust is discussing the project with Dick Wilcox and his associates at the moment, in readiness for the commencement of the project early next year. The new home for the Wurlitzer will be within 1 mile of one of the newer Maplin shops, which we are looking to for supply of parts. Again, the Internet has proved invaluable in its ease of communication capabilities during the specification of the computer and will be used for software transfer as the project develops. This again will show the use of modern technology to link with the past and bring the sounds of the past to a present day audience and, we hope, to the audiences in the next Century.

Don Hyde, Vice Chairman LTOT,
Stockport, Cheshire.

Good luck with the restoration and computerisation of the Wurlitzer. Nice to hear that Maplin will play a part in the revival of this classic instrument.

Over Cooked?

Dear Editor,

It is with regret that I have decided not to continue my subscription to *Electronics and Beyond* with effect from the date of this letter. I feel it is only fair to give you my reasons, so here goes. I have in front of me the October issue. My main interest is in building things, so the projects/circuits ideas are the main reason for buying the magazine. Taking the four projects. The regulator kits I could build with my eyes closed (almost). The aerial will be of interest to those 'overhearing' other peoples conversations – not an interest of mine. The Active Transformer DI box is the only real project in my opinion. Unfortunately, I am no musician. I suggest you take a look at the magazine and ask yourself the following questions.

1. How much of the magazine is directly to do with Electronics? That is, actually electronic theory/construction and how much is consumer electronics related. Is there too much of the latter? Far too much in my view!
2. Are the projects likely to appeal to a broad range of abilities and budgets? NO. In my view, the last interesting project was your Valve Amp. No, I did not build one but reading about it was useful research as I eventually designed and built my own (I'm listening to it now).
3. Is the information in your magazine already covered by other magazines in their own fields? By this, I mean the astronomy articles. Interesting though they are, I already buy them via *Astronomy Now*.

I think if you answer these questions honestly, you will agree that the magazine has become too generalised and not really of direct appeal to the constructional enthusiast. Maybe this is what you want. It will save you time developing projects. If this is the case, I wish you every success. If this is not your aim, ditch the articles on consumer electronics,

develop some more imaginative and, if needed, complex projects. I shall still peruse the magazine in WH Smith.

J. C. Cooke, Bovingdon, Herts.

Paul Freeman-Sear, Publishing Manager replies: Thank you for your comments. You see, we do publish letters of criticism. Let us stand back and take a look at what has been happening to the business of amateur electronics. Enthusiasts and appropriate magazines for constructing radio sets have been around for a very long time, some sixty to seventy years in fact, but it was only in the early '60s that 'practical electronics' took a hold. The hobby probably peaked for the magazine business around 1980. These were boom years for the industry, with no shortage of very creative constructional projects, particularly in the audio field. However, the 1980s saw two principal events happen that would alter the hobby. Cheap, good quality, mass manufactured electronic products were being exported from Japan to satisfy the insatiable demand for high tech products. The constructor was then tempted by the ease and convenience of a complete working product and indeed, was able to buy the product cheaper than could be constructed. The second event and some say a revolution, was the effect personal computers had on our lives. Witness the number of computer titles on the shelves around now and compare with what was available in 1980. The electronics enthusiasts' attention had been attracted away and on towards a high level of involvement that computer software demanded. Another point to ponder on. There was everything, it seemed, that one could create electronically in the '60s and '70s. Now, contributors find it very difficult to come up with something new. There is also a shortage of young contributors to the business. Could this be they have been attracted elsewhere? This decline in so-called interest is across the board and has affected all magazines in the sector. We at Maplin are taking a long hard look at the hobby electronics sector. There are many new avenues for us to explore and we will certainly try to find and present new and creative ideas for constructors as soon as they become available. Maplin aim to move with the times and we are always interested in your ideas on the practical aspects. You have not been forgotten.

A merry christmas
to all our readers from
Britain's best magazine
for electronics

THE MAPLIN MAGAZINE
ELECTRONICS
and Beyond

Apple Newton PDAs PDDQ?

Reviewed by Martin Pipe BSc AMISTC

Towards the middle of 1993, the world's first Personal Digital Assistant (PDA) arrived in the UK. This was the Apple Newton, an extraordinary hand-held device that allowed its owners to take notes with a pen stylus, make sketches, organise themselves with an electronic diary, or even (with a credit card-sized PCMCIA fax/modem and a phone line) send faxes or e-mails. A menu-based GUI (Graphical User Interface) made the device easier to get to grips with, but Newton became famous mostly because of its handwriting recognition capabilities. Scribble a note on its screen with the stylus, and if the machine has been trained with your handwriting style, your words will be converted into text that can be printed, faxed or transferred to a personal computer. At the time, the Newton was revolutionary, and both product and concept certainly lived up to Apple's innovatory reputation.

Unfortunately, it was expensive (£650) and the handwriting recognition failed to live up to expectations, some called it an expensive Etch-A-Sketch for the computer age. An unsubstantiated rumour recently circulating around on a CIX on-line conference said that three hundred thousand unsold Newtons ended up in a Californian land-fill site. Other companies did start producing PDAs, including Sharp and Casio. Even Amstrad got in on the act with the 250 PenPad. Licensees of Apple's Newton Technology include Sharp, Panasonic and Motorola. Sharp's PDA, the 1993 Expert Pad, was in fact a re-styled Newton. Since 1993, things have gone rather quiet; in the years since the Newton's introduction, Apple has been its only major hardware supporter. Over 50 (mostly) American software companies have grown around the Newton, most concentrating on specialist applications such as medical data collection.

PDAs are not seen as universal replacements for notebook PCs. Notebook PCs can run universally-available and familiar Windows and DOS applications directly, and with pretty much the same functionality and speed as today's desktop machines – but with the added advantage of portability. With GSM phones and data cards, they can be used to send faxes and access the Internet, although data throughout rates are poorer.

Notebooks, however, are just not as portable as PDAs. You cannot put, at least for now, a full-spec notebook in your jacket pocket. Any such device could never have an internal floppy drive, due to limitations of size. Although hard disks are getting smaller and smaller, chances are they will be replaced by non-volatile memory cards for such uses.

For jotting down ideas on the spur of the moment, it's simply much easier and quicker to pull out a PDA, or a device like a Psion 3a; how many of us carry around notebooks with us for most of the time? The Newton's ideas jotter is called 'notepad' and will be,



for most of us, the most-used application. PDAs also provide quick access to schedulers (in the case of the Newton, the to-do list and datebook), address books, clocks and calendars. Such devices are much easier to use and more accessible than their PC equivalents. PDAs are frequently being used as data collection devices for more powerful machines, as well as personal organisers.

Newton Applications and Software

The medical field is one in which the Apple Newton is proving popular, and so far hospitals in Germany and the US have embraced it as a mobile data capture device. In the German example, a program developed by a local company is being used to capture operational or service data in the field of outpatient nursing. The hospital, in Cologne, has 50 MessagePads, which form part of a much larger system that handles areas as diverse as operations management



and accounting. The Newton's GUI-based user interface makes it easier for staff, without computing experience, to understand. Other Newton third-party software products include applications for expense tracking, personal financial management, teaching, GPS (Global Positioning by Satellite) integration, pharmacy data collection, vehicle organisation, scientific maths and sales automation.

There are even music composer and golf programs jostling for your attention – Newton software is not all spreadsheets and contact managers.

Apple also has an Internet Enabler; basically, a TCP/IP stack that supports standard transfer and 'messaging' protocols including MIME, SMTP and POP3. Some companies are already releasing basic Web browsers and e-mail packages for the Newton. On Apple's Web site <http://www.apple.com>, you can find a CompuServe access package for downloading and transferring to your Newton. It is true, that with a cellular phone and data card, Internet access has never

been so portable. You can surf the Web on the train to your heart's (and the network's) content, or at least until the cellular signal momentarily drops and the connection is lost!

Apple also produce software, for the Mac and PC platforms, known as Newton Press. This is an electronic publishing tool that creates electronic documents (similar, in principle at least, to the Adobe Acrobat format) for reading on Newtons. Such documents could include graphic files (pie charts, for example), spreadsheets and word processing files. Designed primarily for business users, Newton Press is intended to be a method of distributing travel routes, meeting agendas, reference books (such as repair guides) and phone lists among clients, suppliers and employees.

Newton Technology

But what of the Newton's inner workings? Apple's Newton Technology encompasses several areas. The first, the communications


architecture, provides a number of ways in which data can be transferred to and from the machine. Newton is certainly well-connected. There's an infrared transceiver, primarily intended for one Newton to talk to another; in business, an application of this is the exchange of electronic business cards at a meeting. Newer PC motherboards and notebooks support the connection of an infra-red transceiver that conforms to a standard developed by Hewlett Packard; unfortunately, the data format of Newton's version is incompatible.

But fear not, another option is the RS232-compliant serial port, which on other personal organiser products is normally a rather expensive option (but then again, Newtons are themselves rather expensive devices to start off with!). The serial port, which conforms to RS232 as well as Apple's LocalTalk standard, is intended for the interfacing of printers, as well as personal computers (and non-PCMCIA modems). Since this is an Apple device we are talking about here, any printer attached to Newton needs to support Adobe's PostScript standard, a legacy from the Mac. To print to a non-PostScript device, you will need to get the document into your PC first, and print from there. Finally, we have a PCMCIA Type II slot for the accommodation of memory cards and fax modems. The communications architecture has been designed to support data, fax and e-mail. Web browsing has recently been added to this list.

The second area of Newton Technology, the information architecture, is centred around an object-oriented universal database that stores any kind of information entered into the device. The Newton does not use files and filing systems in the way that conventional computers use them; instead is this common pool of data available to all of the programs that need it. Apple has created a Newton Toolkit so that programmers can work in this unfamiliar territory, and produce applications for the platform.

Programs are transferred to the machine from a personal computer via the serial lead; it is assumed that Newton users have a PC or Mac. Using a desktop machine also makes the downloading of programs and updates from the Internet, or bulletin boards, easier and safer (they are always on your hard disk, should you need to re-transfer them to the Newton). Programs could also be burnt into PCMCIA memory cards. Unless the complete program is loaded into the Newton's memory in one go (so that the card can be removed) the slot will no longer be free to accommodate a modem.

Newton Technology's third area, the recognition architecture, is the most interesting. Handwriting, whether printed, cursive (i.e. joined-up) or a mixture of the two, is recognised with the assistance of a 93,000 word vocabulary. There is also the option to define 1,000 of your own words in a custom vocabulary, which is useful for specialist applications such as medicine, science and engineering. The Newton's recognition architecture also supports various intuitive short-cuts. For example, crossing out an item of text with a four-stroke zig-zag will delete it.

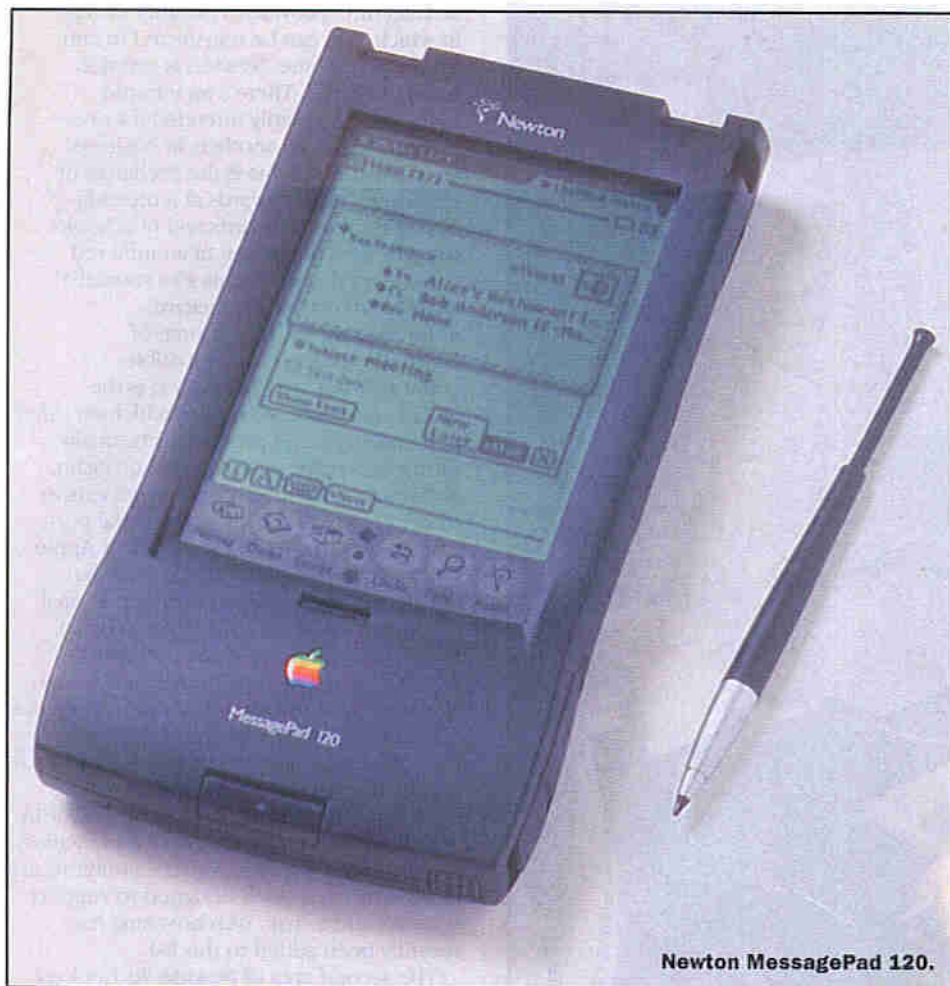

Newton MessagePad 120.

Training the Newton to recognise your handwriting style over a period of time is important, and the Newton will support a guest user as well as the main one.

Sketched drawings also benefit from Newton's recognition architecture. Lines are straightened, and circles made perfect, helping to neaten up your ideas. There is also a series of pop-up keyboards, including a typewriter. The latest release of the operating system, Newton 2.0, was released towards the end of 1995 to answer criticism of the original software's handwriting recognition capability. Interestingly enough, Newton 2.0 provides support for a full-sized keyboard that connects to the PDA via the serial port. According to Apple, this keyboard is intended to allow customers to input data quickly. Apple's research had shown that a subset of Newton customers had required keyboard input for drafting e-mails and reports, as well as typing up meeting notes.

In the area of hardware, Newton is based around powerful and efficient RISC processors developed in Cambridge by ARM (Advanced RISC Machines), an up-and-coming microprocessor designer in which Apple has a major interest. ARM is credited with producing devices with among the highest MIPS-per-watt ratings of the industry. The Newton MessagePad 120 makes use of an ARM610 processor that runs at 20MHz, as did the original model.

An ARM spokesman hinted that future Newton products could make use of the latest StrongARM, a next-generation RISC processor that would provide the power needed to speed up handwriting recognition, and maybe facilitate voice input

(dictating to your machine via a boom mike, as you currently can with IBM's VoiceType or Kurzweil's Voice, is certainly an attractive position). The processor is complemented by an Apple ASIC chip, a slice of non-volatile RAM (around 2Mb in the case of the 120, of which just over 1.3Mb is available for user applications) and a healthy 8Mb of ROM, which contains the operating system (in this case, Newton 2.0). There is also hardware support of the LCD display, serial port, infrared device and PCMCIA slot. Low power consumption is an important area (hence the choice of a RISC processor) and the Newton offers power management facilities. If nothing is pressed for a short period, a MessagePad will go into standby and conserve battery life.

The fifth and final area of Newton Technology is the assistance architecture, which Apple hopes will make operation of Newton easy and intuitive. Recent actions are correlated with items in the common database, so that it can guess the actions you might wish to take next (smart defaults). The assistance architecture is intended to help users complete repetitive tasks, including scheduling, reminding and finding, in multiple categories. It has been designed to work between, as well as in, application programs (whether from Apple or a third party).

MessagePad 120

The MessagePad 120 itself is typically Apple – sleek, comfortable, ergonomically well-designed and rather expensive (£125 + VAT). The LCD screen has a resolution of 320 × 240 pixels, and with dimensions of 9.6 by 7.2cm

is very readable. Unless you are using the device under subdued lighting conditions, that is. Apple have not included a backlight, if you want this, you will need the (£499 + VAT) MessagePad 130 which is, apart from backlight and a little extra memory – identical. The display is not colour, and will not even display greyscale – it's line-art or text only, folks. When the device is not in use, the precious screen is covered by a flip. To use, a button at the front of the machine releases the flip, which folds away behind the Newton's back.

The battery compartment is also found on the back. The Newton runs on four AA cells, which could be alkaline or NiCd types (it seems equally happy with the 4.8V of the NiCds as it is with the dry cells 6V; buried inside the unit, there seems to be some kind of inverter, which can be heard whining). A few hours of battery life is promised, and a power gauge can be selected from a menu (there is also a low-battery warning). A separate 3V lithium battery powers the Newton's RAM chips when the main batteries are dead, or the device is switched off. Power up the Newton, and the display is just as it was when last used. The backup battery needs replacing roughly on an annual basis. Apple does not supply a mains unit/charger with the Newton, which is downright annoying considering the retail price.

On one side of the MessagePad is a control for adjusting the contrast of the display, and the on-off switch. On the other side is the PCMCIA slot and, hidden under a bung, the Mac-style mini-DIN serial port and DC power/charge connector. On this side is the storage hole for the telescopic stylus; press the bit of stylus that is exposed, and it is released. Since the stylus is pressed against the display to access menu functions or write data to the device, it is important to use only the one supplied. Using a pen or sharp object may scratch the finish. The infrared Newton data-interchange window can be seen on top of the MessagePad. Inside the MessagePad is a tiny speaker that yields an audible response whenever data is entered, or a function is accessed.

Null modem cables are supplied for Mac (mini-DIN) and PC (9 and 25-way D Connectors) interconnectivity, together with Newton Back-Up software. Unfortunately, the person who had the MessagePad before me had decided to delete some of the Windows set-up files; after un-deleting them and scanning the disks for viruses, the program did not work properly when installed under Windows '95.

It defaults to COM1, which is not very sensible since this is normally the port to which your mouse is attached! Consequently, the mouse hangs, and you have to use the keyboard to select the correct port before rebooting! The replacement software worked much better, indicating that the original files had been corrupted. I can not speak for how well the Mac software functions, since I have only just acquired one of these second-hand, and am currently obtaining the rest of the items needed to get it working properly. One can only imagine that, since it originates from the same people responsible for the Mac, it should function extremely well.

Some Newton software requires more memory to run than is available on the MessagePad 120. Memory can be added in the form of PCMCIA cards (Apple sell 1Mb,

2Mb and 4Mb types) but their usage prevents other cards, such as modems, from being plugged in. This effectively prevents the MessagePad 120 from running some of the memory-intensive Internet software that is available; you may need the 130 version if you are a dedicated surfer. Perhaps future generations of Newton products might feature a Type III slot (which will accommodate two Type II cards), or two Type II slots.

I would have liked to have faxed something with the Newton. Unfortunately, it did not recognise my Portable Add-ons (Psion Dacom) v.34 PCMCIA modem – so much for 'Plug and Play' (more like Plug and Pray).

Click on card, from the extras menu, and it simply tells you that no card is inserted. It looks like Apple is once again up to its old tricks, creating its own subsets of standards. Mac users will know that the MacOS SCSI hard disk formatting tool only works with Apple drives (which are, nevertheless, normally standard models from outside world companies like Quantum, with some subtle drive firmware changes).

To get non-Apple SCSI hard drives (or for that matter, CD-ROM drives) to work with Macs, you need to spend yet more money on third-party software tools (I have recently learnt this to my cost). Apple does have a list of approved peripherals, but if you have a device that conforms to what is perceived to be a universal standard, yet is not listed or does not work, it's extremely annoying. Incidentally, the official Apple fax modem works at 2400bps data, and 9600bps fax. The low data throughput puts this device in the Dark Ages, and makes it practically useless for Internet applications. A new, faster, card should be due soon, if it is not here already.

But back to the good. The Newton operating system is very nice, neat and user-friendly. Unlike some recent versions of MacOS, it appears to be very stable too. Notes are written on the screen, which has rulings akin to lined paper. Once you get to the bottom, it scrolls downwards and gives you more space to write. A bar at the bottom has touch-sensitive function buttons that provide instant access to what Apple sees as the most-used functions (such as 'undo', 'find', 'names' and 'dates'), and two arrows that allow you to scroll up or down the text.


Entering information can be achieved in three different ways. The first is to use a miniature on-screen QWERTY keyboard, the stylus is pressed against the character that you want. While accurate, this method is very time-consuming. The second is to hand-write it onto the screen without the MessagePad trying to recognise it. This system, in which your expensive Newton hardware is being used as a 1 spiral-bound notebook, is useful if you do not have time for the device to recognise your handwriting. I can imagine that storing information in this way is rather more memory-intensive than raw (i.e. ASCII) text would be. This system can be used, however, to quickly send handwritten faxes without the intermediate paper stage (you need the PCMCIA fax modem and a telephone line, of course). As an alternative to being transmitted, the information could be stored in user-definable folders.

The third method is, of course, handwriting recognition. When you first power up the device, preferences can be set. You can define whether your handwriting is printed or cursive, and set the spacing that you normally use between characters.

A pen alignment function appears to detect whether you are left or right-handed. Finally, we have a section that puts a number of the most commonly-used shapes of each character on screen (you may see these shapes change as you use the unit more, and it becomes more familiar with your style), if your writing style is cursive. You simply inform the software as to the ones that you use most, sometimes and not at all. It certainly makes the handwriting recognition software's job easier. I would have liked a section where the Message Pad asked you to draw certain characters on screen repeatedly until it had learnt your signature. Instead, it does it on the job (provided that the 'learn my handwriting' option is switched on) which takes somewhat longer.

In this instance, the MessagePad accumulates information about your writing style; although this depends on you telling it that a word is incorrect. The correct word is selected from a word list, or a new word is defined using the on-screen QWERTY keyboard. Training is important, do not expect the MessagePad to start making sense of your handwriting immediately. It is important to keep your writing style consistent and neat. Unfortunately, mine is neither, and so myself and the MessagePad did not often see eye-to-eye (are they really selling Newton to the medical world – it must be very frustrating if you are a prescribing GP!), although I know of some people who have got on with their Newtons like a house on fire.

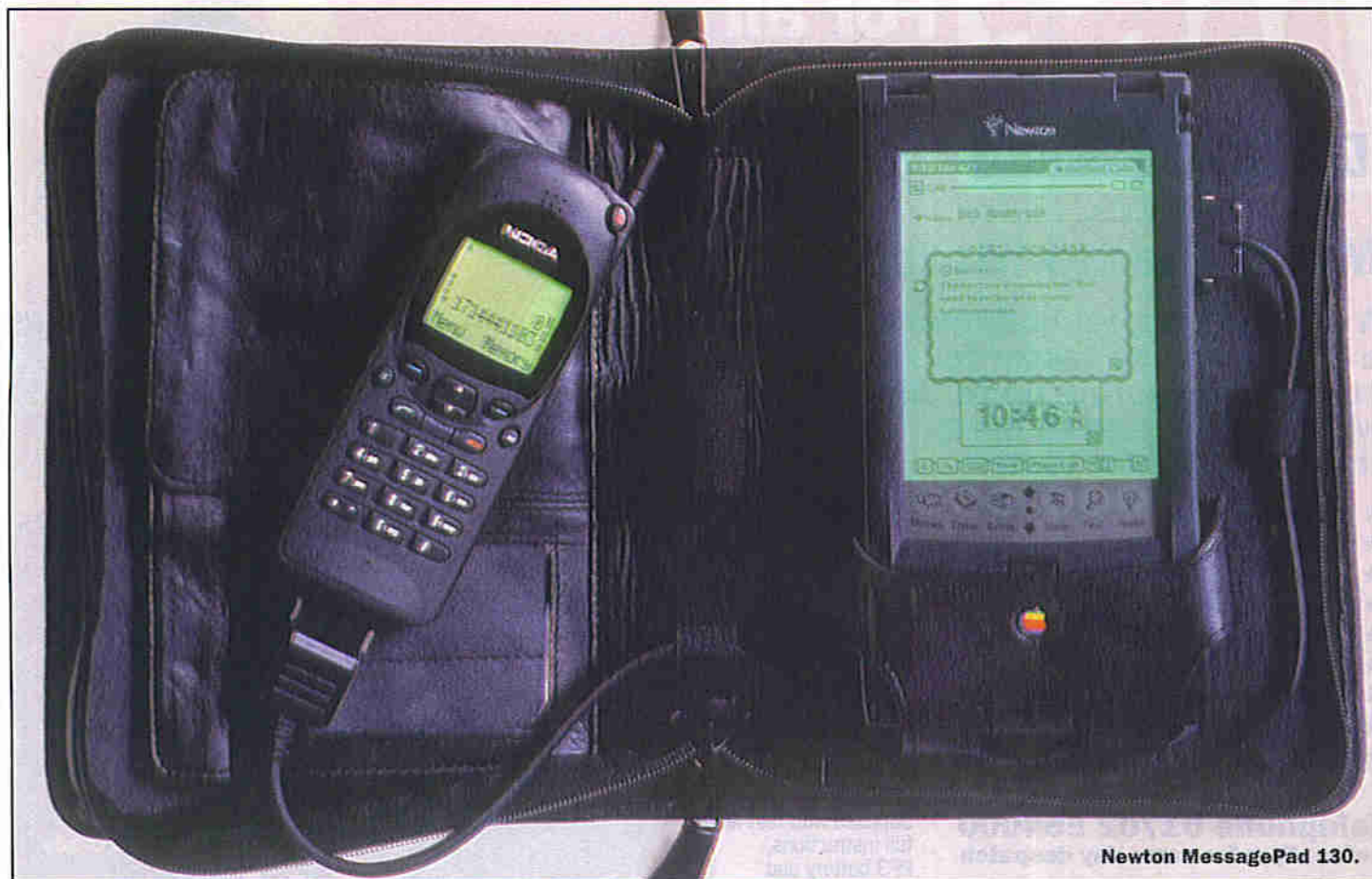Recognising a word, and particularly one that you do not often use, can take some time, that ARM610 is clearly being pushed near its limits. This delay can stop your flow of words. More powerful processors will obviously help here. Handwriting recognition



Newton MessagePad 130.

is notoriously complex, and Apple should be applauded for the fact that it works at all. But then again, the Psion 3a's tiddly keyboard looks impossible to touch-type on until you have tried it. Some companies are developing alternative handwriting recognition systems. Palm Computing's Graffiti, one of the most popular, makes use of a completely new and simple character set. Palm claim that speeds of up to 30 words per minute and 100% accuracy can be achieved using it.

The 'extras' menu on the Message Pad gives access to various other functions available. It is from here that you can initiate connection to another device, access a clock/time zones, start up a simple calculator, choose fonts and other styles, and check received or sent messages. The 'dates' menu is pretty much an exact replica of a diary page, from here, you can jot down details of meetings, lunch appointments and the like. It is augmented by an alarm facility which will warn you just before the appointed event, and a 'to-do' function that lists all future events. A card-index style function, 'names', is an address book which can also contain fax numbers and e-mail addresses for use by communications programs.

In all, the way in which Newton's capabilities dovetail is impressive. At the end of the day, though, it is rather expensive (a second-user 486 notebook can be had for less) and perhaps should only be considered if you have a real need, and an understanding

Apple dealer who will let you live with a MessagePad for a while on approval. These PDAs will definitely become more widespread once they hit the sub-£200 price point. The handwriting recognition is slow, although it is an improvement on previous Newton incarnations. Faster processors would help here, and facilitate the voice input that I see as being an important future data entry option for computer devices.

The Psion 3a is cheaper and better-supported, but for sheer innovation it's the Newton that wins.

Contact

Apple Computer, 6 Roundwood Avenue,
Stockley Park, Uxbridge UB11 1BB,
Tel: (0800) 127753 (Freephone)

NEWTON MESSAGEPAD 120 SPECIFICATIONS

Price:	£499.38, but being discounted at most Apple dealers
Processor:	ARM 610 RISC, 20MHz
ROM:	8Mb, stores Newton OS
RAM:	687k system, 1361k user (non-volatile)
Connectivity:	PCMCIA Type II slot with 325mA supply capability, serial(RS232/Apple LocalTalk), infrared.
Display:	320 x 240 pixels, not backlit
Input device:	Telescopic stylus
Weight:	0.48kg (without batteries)
Battery requirement:	4 x AA (main), DL2032 lithium (RAM back-up)
Dimensions (WHD):	101.6mm x 29mm x 203.2mm
Fax support:	Group 3 (with fax modem, not included)
Backup utility system requirements:	386DX processor, Windows 3.0 or later (PC); 68030 or later processor, System 7.1 or later (Mac)
Optional accessories:	fax modem (2400 data, 9600 fax), full-sized keyboard, GSM connection kit, replacement pen, 1Mb SRAM card, 2 and 4Mb flash memory cards, interface for parallel-port printers, power adaptor (7V, 500mA), extended-life battery pack (takes 8 AA cells), charging station, rechargeable battery packs, carrying cases

MPS
MAPLIN PROFESSIONAL

For all
**Electricians
and Contractors**

M920 Clamp Meter

A compact digital multimeter with a built-in clamp tester for AC current measuring up to 300A - without the need to break the circuit under test!

- ★ Measures AC current from 10mA to 300A
- ★ Measures AC voltage from 100mV to 750V
- ★ Measures DC voltage from 100µV to 1000V
- ★ Diode test function
- ★ Instant continuity buzzer
- ★ Display hold facility
- ★ Recessed input sockets for safety
- ★ 3½-digit LCD readout
- ★ Meets IEC 348 class II and UL 1244 standards

Telephone **01702 554000**
before 5pm for same day despatch

All orders over £30.00 inc. VAT are post FREE!

Order As
ZC61R
£34.95
inc. VAT

Special Low Price

**HURRY WHILE
STOCKS LAST**

Supplied with test leads,
full instructions,
PP3 battery and
carrying strap

We accept these Credit Cards



**NOW YOU CAN SEE
THE COMPLETE RANGE
OF MAPLIN GOODS
ALL UNDER ONE ROOF.**

Visit Maplin's biggest,
brightest, best-ever store!

MONDO

MAPLIN SUPERSTORE



**VIRTUALLY EVERY
CATALOGUE ITEM
ON DISPLAY
IN STORE!**

**3 REGENT STREET, LEEDS
TELEPHONE: (0113) 244 9200**

TECHNICAL INFORMATION SERVICES

76 Church Street, Larkhall, Lanarks, ML9 1HE
Tel: (01698) 883334 Fax: (01698) 884825
Technical Help Line (01698) 884585

We have the World's Largest
Selection of:

**SERVICE MANUALS
CIRCUIT DIAGRAMS**

We also have 100s of Titles on TVs, VCRs,
Satellites, Midi Systems, Computers, Test
Equipment, etc...

Please Phone or Send an SAE for FREE
QUOTE & CATALOGUE of Publications

ELECTRONICS and Beyond

BRITAIN'S BEST MAGAZINE FOR THE ELECTRONICS ENTHUSIAST

With features, news, reviews,
competitions, projects and lots
more besides, you won't want
to miss a single issue of your
favourite electronics magazine.
Why not ask your local newsagent
to reserve or deliver every issue
of *Electronics and Beyond*.



Subscription Orders call 01702 554000

**Reserve
your
copy
today!**

Dear Newsagent

Please reserve/deliver (delete as applicable) each issue of *Electronics and Beyond*.

Mr/Mrs/Ms

Address

Postcode

Signature

Electronics and Beyond is published monthly and is distributed through your wholesaler by:
Seymour, 1270 London Road, Norbury, London SW16 4DH. Tel: +44 (0)181 679 1899.

**BRITAIN'S BEST MAGAZINE FOR
THE ELECTRONICS ENTHUSIAST**

Published Monthly

ELECTRONICS
and Beyond

Touch Memory

THE KEY TO

THE FUTURE

PART 2

Relay Board Project

by Tony Ellis

In the first of our Touch Key Hybrid constructional projects, I describe a highly versatile circuit – The Touch Key Relay Board, which enables a multitude of existing household or commercial products to be controlled by these ultra-high security touch keys.

In the following pages, we will see how to construct an incredibly low cost, high security door access system, followed by a touch key arm/disarm module that can easily be added to existing security systems – see Figure 1, showing the system block diagram. Remember, all these projects can be accessed/controlled by the same unique ultra-high security touch key! The circuit diagram of the Relay Board is shown in Figure 2.

The first application of the hybrid relay board is an incredibly low cost electronic door access system (see Figure 3) which still retains versatility and high security associated with touch memory, but which can be built for under £85. This is quite astonishing, as you would expect to pay in excess of £300 for a commercial high security access system. The system is based around the electric door catch release also sold by Maplin (Stock Code YU89W). As this device is essentially an electronic 'keep', the user has the option to use a standard type mortice lock if they prefer to still have a mechanical key. Obviously, higher security is afforded if a non-key door latch is utilised, and these are available from most good hardware stores. Also, if required, it should be possible to produce a simple standby battery back-up system for applications where mains power failure would pose a problem. A 12V 1.5A DC power supply is required and these can be found in a reasonably small adaptor type style (but be sure to double-check the current rating).

For this application, the relay board is programmed to 'pulse output mode' via link 'P' being made. IMPORTANT for correct operation, the PA link on the hybrid board MUST BE installed.

In operation, touching a valid key on the system's receptacle fires the door release for a few seconds, enabling the door to be opened. Once the pulse is complete, the 'keep' locks again, retaining the door again when it returns to its closed position.

The second application is to integrate the touch hybrid relay board into an existing alarm control unit (see Figure 4).

One big security advantage of this configuration is that the main alarm panel can be hidden. The only part that is required to be on view (accessed) is the touch receptacle itself, which as it is effectively a 'coded link', cannot be tampered with to bypass touch key operation. In conclusion, this configuration makes for higher security and a more attractive installation.

By way of an actual practical example, we will show full details of how to connect the hybrid relay board into a typical low cost, key operated, alarm system. Referring to Figure 5, it can be seen that the modification is simplicity itself, but please note, it would be advisable to meld the 24-hour (tamper) loop into the cable serving the remote-mounted zone select switch. Of course, the receptacle/indicator and zone select switch could be installed into the same remotely mounted box.

Circuit Description

The supply voltage applied to the relay board via the double terminal block must be within the range of 10 to 14V DC, as the board's relay has a 12V coil. The touch hybrid requires a +5V stabilised supply. This voltage is obtained by using a small 100mA regulator, RG1, with capacitors C1 & C2 providing decoupling. To prevent reverse polarity damage, diode D3 is included.

The relay pulses or toggles on/off, depending on whether link J2 is installed. If C4 is shorted, then the hybrid divide-by-2 output is connected directly to the main relay driver (R2, D4 and Darlington-pair transistor TR2) giving a toggled output. If J2 is left open circuit, then an edge-triggered pulse generator circuit is formed via C4, D1, R4 and D2. Also, in pulse mode with J3 made, a pulsed link is formed via R2, TR1, C3 and R1, with the hybrid IGN line causing the passive arm function to be activated. This forces the hybrid's output line to toggle back to the hybrid's 'armed' state, after a short delay period.

PCB Assembly

Refer to Figure 6, showing the PCB legend and track whilst assembling the board. Removing a misplaced component can be tricky and may damage the component(s), so always double-check the type, value and polarity before soldering.

The sequence in which the components are placed is not critical. However, the following order is advised. Commence with the smaller, and progress through the largest. Install resistors R1 to R3, followed by D1 to D4; these have a band at one end to identify the cathode. Take care to insert the correct diodes, the 1N4148 being the smaller glass type. Next, fit the capacitors C1 to C4. The polarity for the electrolytic capacitors is indicated by a plus sign (+) on the PCB legend. However, the majority of electrolytic capacitors have their polarity designated by a negative (-), in which case, the lead nearest the symbol goes into the hole opposite to the designated hole.

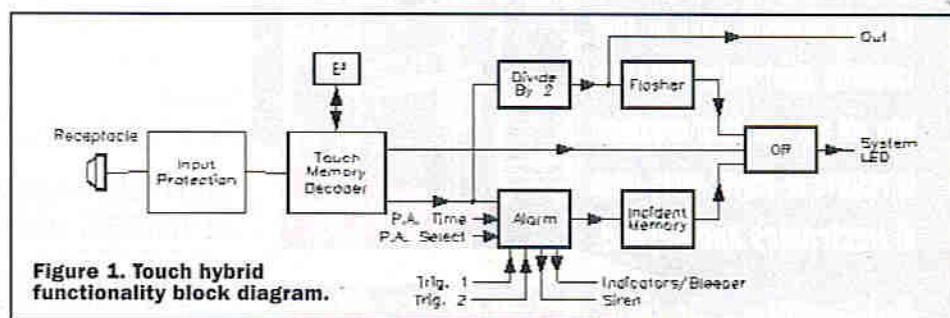


Figure 1. Touch hybrid functionality block diagram.

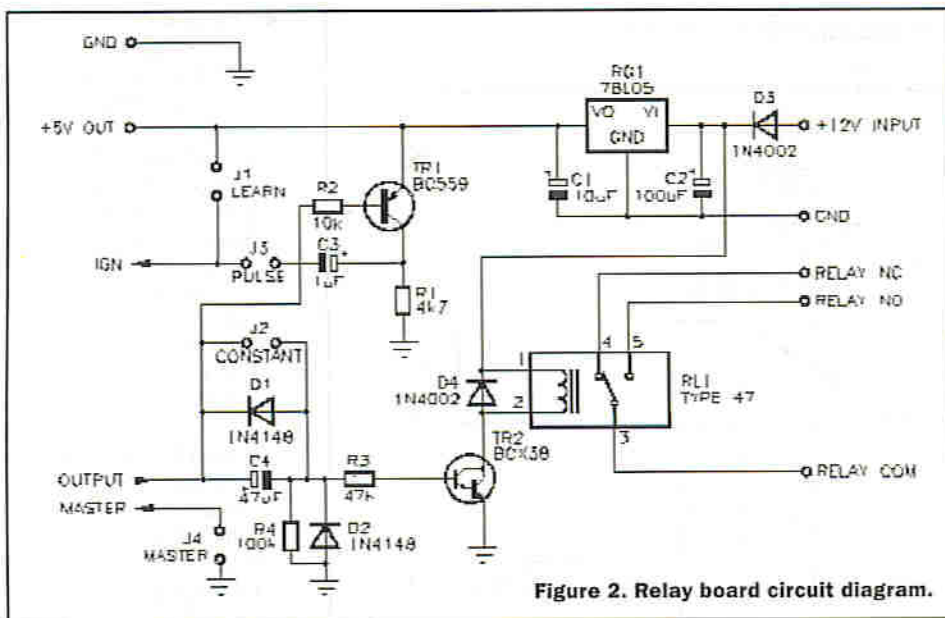


Figure 2. Relay board circuit diagram.

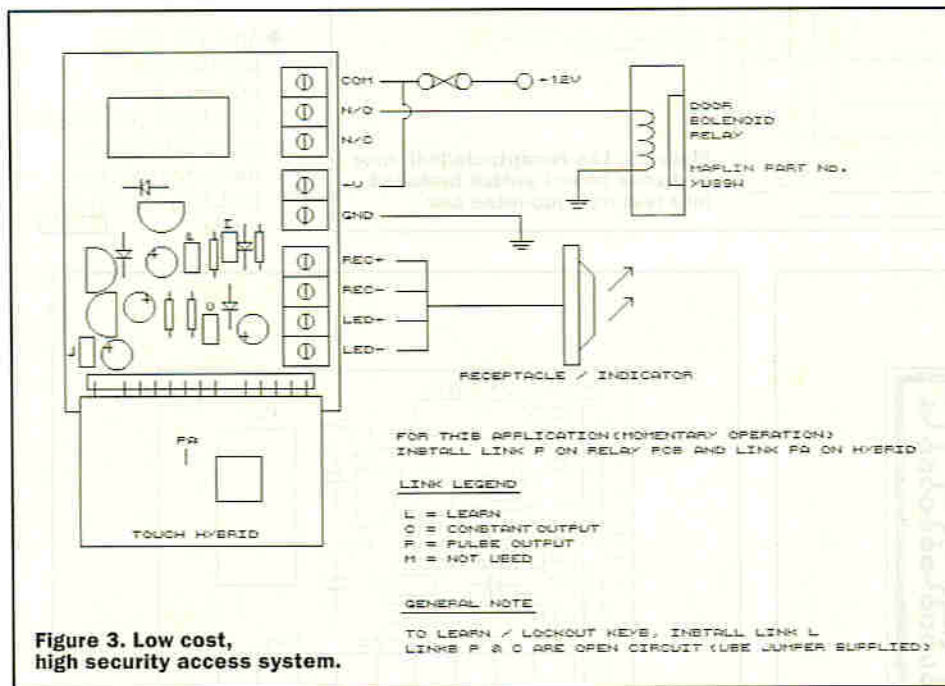


Figure 3. Low cost, high security access system.

Next, install the transistors Q1 and Q2 and voltage regulator IC1, making sure that its flat surface conforms to the package outline on the PCB legend, followed by programming link L1 to L4, followed by the screw terminal blocks (4-way, 2-way and 3-way). Finally carefully solder in the touch hybrid.

This completes the assembly of the PCB. Carefully check your assembly work, making sure that there are no misplaced components, solder bridges, or dry joints. Finally, remove any excess flux from the board using a suitable solvent.

Touch Key Learning Procedures

On powering up for the first time, the system LED goes on continuously. This means that the unit is ready to learn the Master Key. The first key presented to it is now the Master.

Learn Master Key

Not necessary with Maplin Hybrid, as Master Key is pre-learned.

Learn User Key

1. Apply power to hybrid relay board.
 2. Install learn jumper (L) J1, remove links (C) J2 and (P) J3.
 3. Touch Master key on receptacle, LED will flash at approximately 5Hz.
 4. Touch Key to be learnt on receptacle, LED will go out.
 5. Remove J1, hybrid will now switch on/off with keys.
 6. Reinststate any links removed in step 2.
- Repeat steps 2 to 4 to learn (teach) further keys.

Notes on Touch Key Technology

- ◆ There is a 4 second de-bounce period between accepting keys, i.e. after one key touch, a second will not be accepted for approximately 4 seconds. It is important to note that touch keys are meant for momentary action (i.e. touch and withdrawn); never leave the key in contact with the receptacle for more than a couple of seconds, as the output will toggle on or off or vice-versa. As a guidance, communication (to decoder) plus acceptance of an authorised touch key is generally in less than 100ms ($\frac{1}{10}$ th of a second).
- ◆ The Master Key cannot be 'learnt' as a User Key.
- ◆ The unit can learn up to four/eight keys – the system always remembers the last four/eight keys taught to it. Selection of four or eight key mode is via the key no. program pads on the rear (non-component side) of the Hybrid, e.g. open circuit is 4 key mode.*

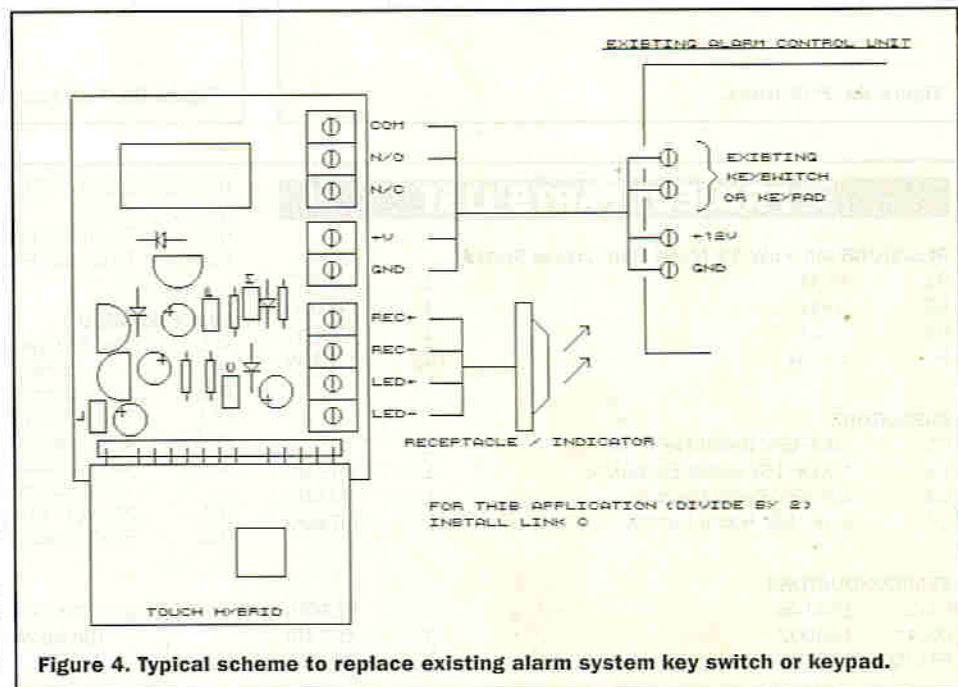


Figure 4. Typical scheme to replace existing alarm system key switch or keypad.

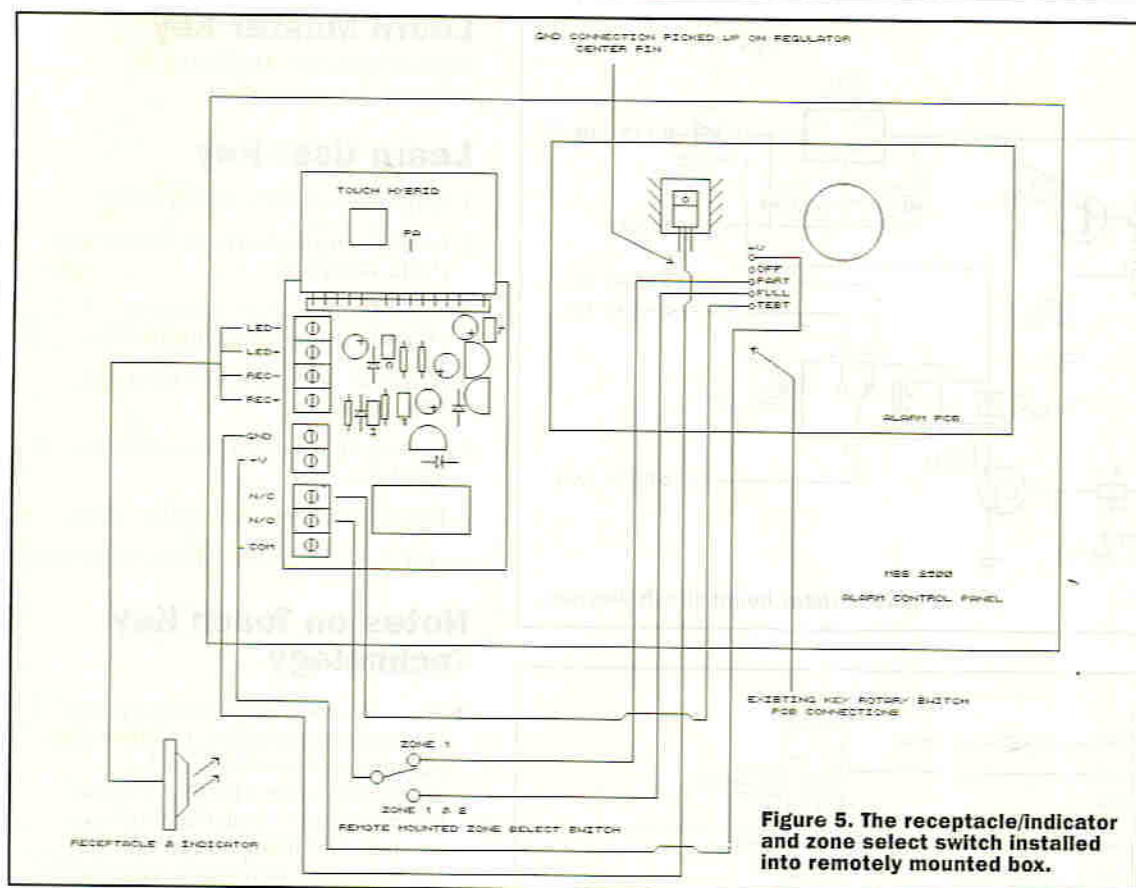


Figure 5. The receptacle/indicator and zone select switch installed into remotely mounted box.

- ◆ The same User Key can be taught to the systems more than once, this is a useful mechanism to 'lock out' lost keys. For instance, if the user wants the system to work off one key only, they can teach one key to the system four times, this will then become the only valid system key. Further, if the user wants two keys to be valid but to void a third key, then teach key one (once) and key two three times.
- ◆ After the Master Key has been presented, if no key is presented within 30 seconds, the system will revert back to its disarmed mode.

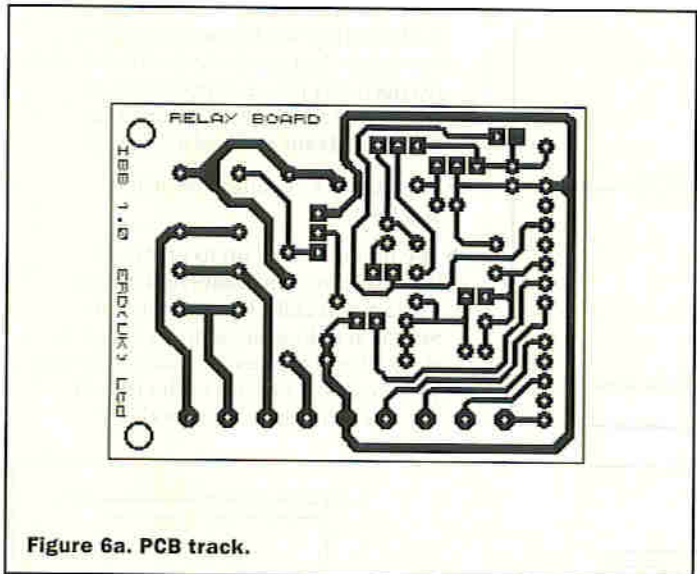


Figure 6a. PCB track.

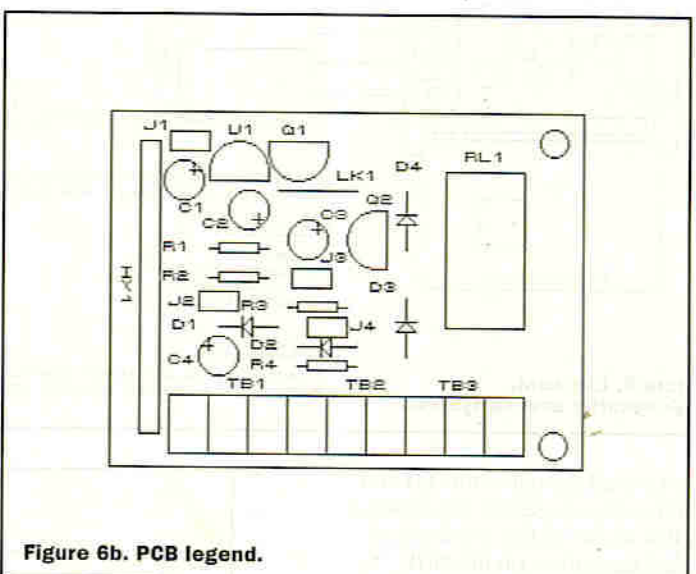



Figure 6b. PCB legend.

PROJECT PARTS LIST

RESISTORS (All 0.6W 1% Metal Film, Unless Stated)			
R1	4k7Ω	1	(M4K7)
R2	10kΩ	1	(M10K)
R3	47kΩ	1	(M47K)
R4	100kΩ	1	(M100K)
CAPACITORS			
C1	10μF 63V Radial Electrolytic	1	(AT77J)
C2	100μF 16V Radial Electrolytic	1	(AT30H)
C3	1μF 63V Radial Electrolytic	1	(AT74R)
C4	47μF 16V Radial Electrolytic	1	(AT39N)
SEMICONDUCTORS			
D1,2	1N4148	2	(QL80B)
D3,4	1N4002	2	(QL74R)
TR1 (Q1)	BC559	1	(QQ18U)

TR2 (Q2)	BCX38 NPN Darlington-pair Transistor	1	
RG1 (U1)	78L05	1	(QL26D)
HY1	Touch Key Decoder Hybrid	1	(CK41U)
REC1	Touch Key Receptacle with LED	1	(CK44X)
MISCELLANEOUS			
RL1	12V BT (Type 47) SPDT Relay	1	(DC80B)
TB1	4-way 5mm PCB-mounting Terminal Block	1	(KE55K)
TB2	2-way 5mm PCB-mounting Terminal Block	1	(FT38R)
TB3	3-way 5mm PCB-mounting Terminal Block	1	(RK72P)
J1-4	2-way Header Strip 2.54mm Pitch	1 strip	(JW59P)
K1	15-way Straight Pin Header (use part of 36-way strip, JW59P)		
LK1	22swg 0.71mm Tinned Copper Wire	1 reel	(BL14Q)
PCB	Ready made PCB (not available from Maplin)	1	

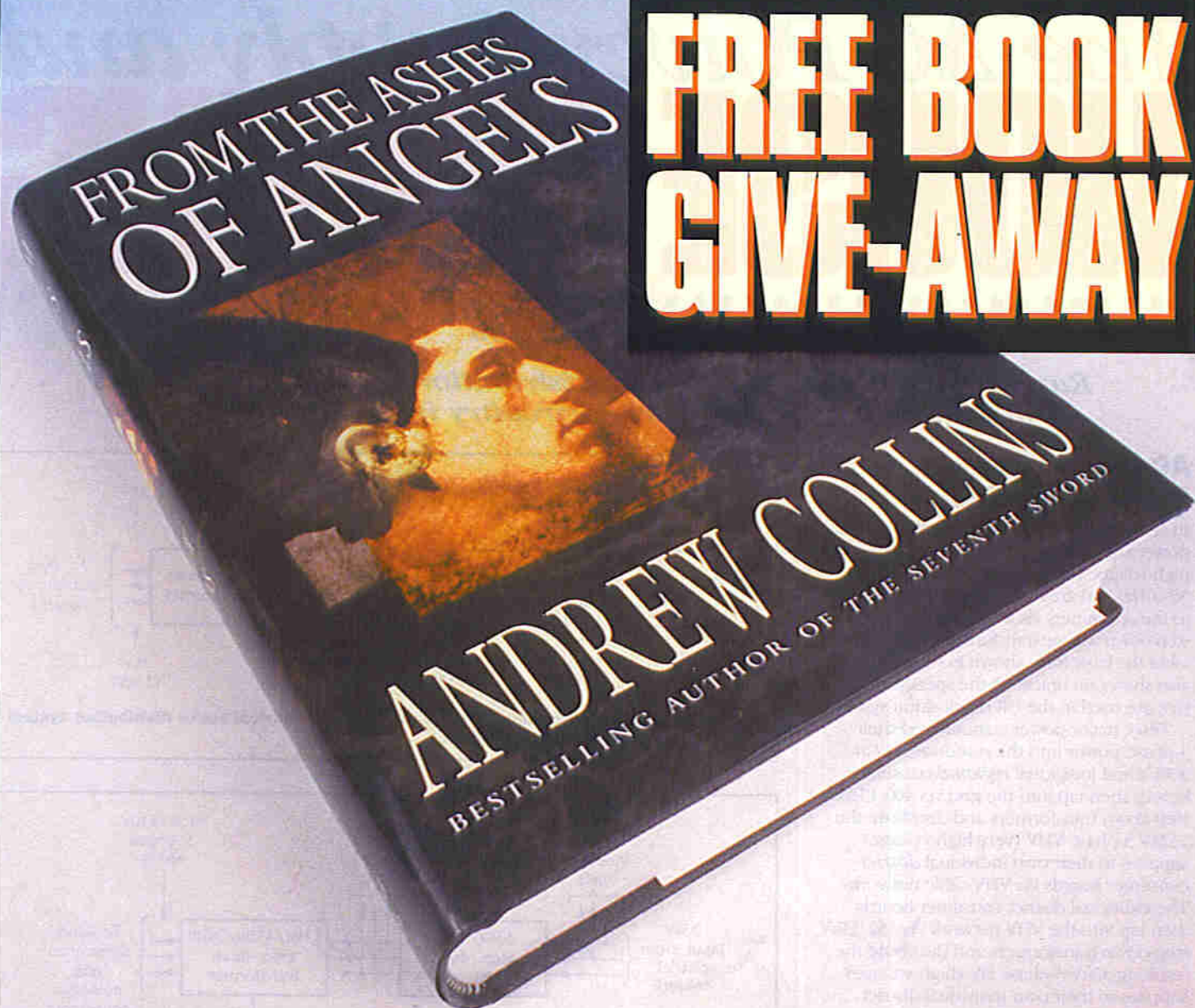The Maplin 'Get-You-Working' Service is not available for this project.
The above items are not available as a kit.



FREE BOOK GIVE-AWAY

Electronics and Beyond have six hard-cover books called *From the Ashes of Angels* by Andrew Collins to give away!

Ancient accounts speak of a time when angels and fallen angels walked freely among humanity. Where do these strange legends come from? Have they any basis in truth? And what can we learn from their existence?

Andrew Collins is the author of various books on the subject of psychic questing, a term he uses to describe his own unique brand of urban shamanism. They include his 1988 cult classic *The Black Alchemist*, *The Seventh Sword* and *The Second Coming*.

In 1991 he turned his attention to the crop circle enigma. His findings were published in a controversial, though highly successful book entitled *The Circlemakers*.

From the Ashes of Angels is the culmination of the author's ten-year project to study the archeological and historical reality of an advanced culture existing in Egypt and the Near East in prehistoric times.

"An exciting and original intellectual quest. Andrew Collins has put important new facts before the public concerning the mysterious origins of human civilisation"

Grabam Hancock, author of Fingerprints of the Gods

From the Ashes of Angels by Andrew Collins is published by Michael Joseph, priced at £16.99. Available from all good book retailers or from Penguin Direct, Tel: (0181) 899 4036 (£1.50 will be charged for postage and packing and this service is only available in the UK).

Please note that employees of Maplin Electronics PLC, associated companies and family members are not eligible to enter. In addition, multiple entries will be disqualified. The prizes will be awarded to the first six entries drawn.

FROM THE ASHES OF ANGELS

Six lucky Electronics and Beyond readers need not pay a penny for a copy of *From the Ashes of Angels*. The first six readers whose names are drawn from the Editor's hat(!) on 25th November will have a copy delivered to their home.

Name

Address

Postcode

Daytime Telephone Number

No purchase necessary. Entries on a postcard, back of a sealed-down envelope or photocopies will be accepted.

ELECTRONICS

and Beyond

Send your entry to *From the Ashes of Angels* Free Book Draw, The Editor, Electronics and Beyond, P.O. Box 777, Rayleigh, Essex SS6 8LU.

The AC Power Supply and HOUSE WIRING

by Ray Marston

Ray Marston explains AC power distribution principles and looks at practical domestic AC wiring circuitry in this special feature

AC Power Distribution Basics

In all modern countries, national electrical power supplies are generated in extremely-high-voltage (EHV) 3-phase AC form (usually 50-60Hz) and are then distributed nationwide to the consumers via a network of cables and step-down voltage transformers. The network takes the basic form shown in Figure 1, which also shows (in brackets) the specific voltages that are used in the UK distribution system.

Thus, major power stations feed their 3-phase power into the *national grid* at 400kV, and individual *regional* consumer boards then tap into the grid via 400/132kV step-down transformers and distribute the 132kV 3-phase VHV (very high voltage) supplies to their own individual *district* consumer boards via VHV cable networks. The individual district consumer boards then tap into the VHV network via 132/33kV step-down transformers and distribute the resulting 33kV 3-phase HV (high voltage) supplies to their own individual district areas. These, in turn, further reduce the voltage via 33/11kV step-down transformers before further processing the supply and distributing it to *individual consumers* such as industrial, commercial, and domestic units within those areas. Note that this system is designed to minimise current-generated distribution power losses caused by the resistance of the distribution network's supply cables. Thus, an end-consumer who draws 1A (11kW) from the local 11kV supply will impose a drain of only 27.5mA on the national grid, which may derive its power (via cable) from a generating plant that is hundreds of miles away.

Figure 2 shows the basic form of a typical *area* AC electrical distribution path, in which HV supplies are distributed to various consumer groups. Thus, the 33kV supply that feeds the input of the area's 33/11kV step-down transformer may also be fed directly to heavy industrial units that have their own step-down transformer and power distribution systems, and the 11kV output of the step-down transformer may be fed to light industrial units that have their own AC power processing systems. The 11kV 3-phase AC distribution system is also fed to local commercial and domestic consumers via local sub-stations, which employ a step-down transformer to provide a '415/240V' 3-phase 4-wire output from the 11kV 3-phase 3-wire input.

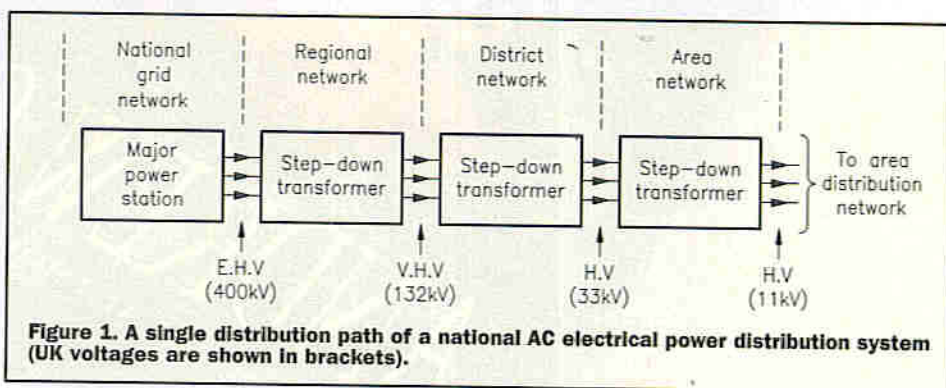


Figure 1. A single distribution path of a national AC electrical power distribution system (UK voltages are shown in brackets).

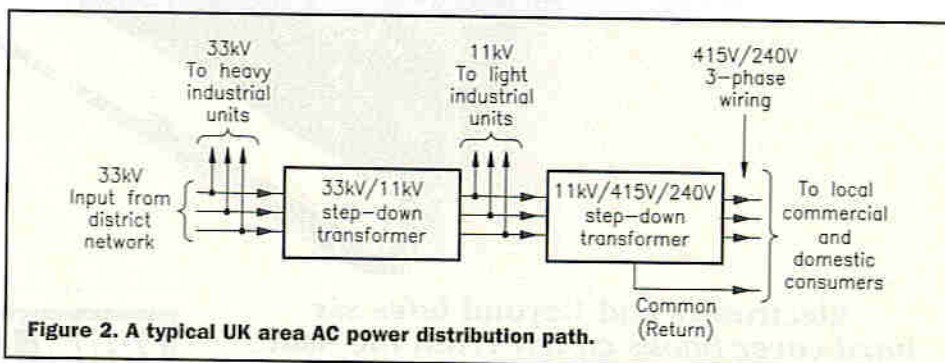


Figure 2. A typical UK area AC power distribution path.

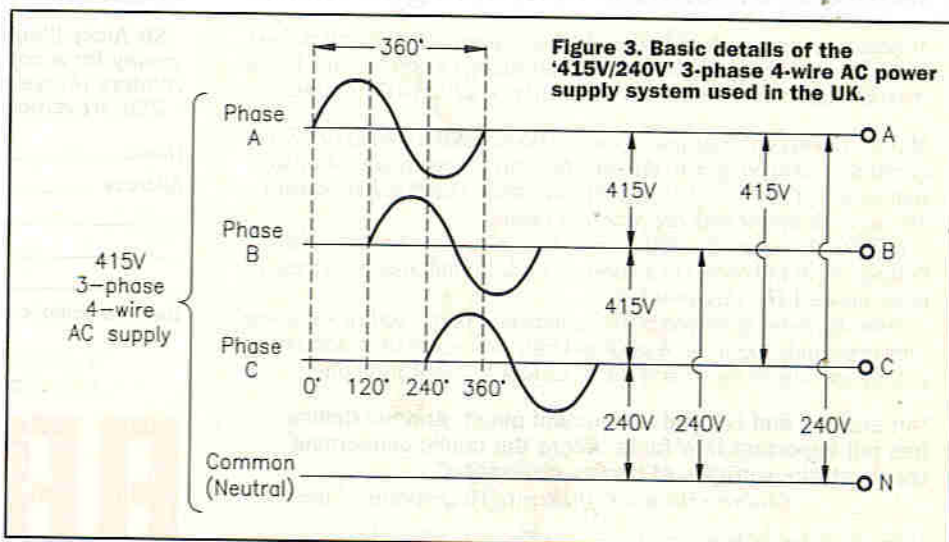


Figure 3. Basic details of the '415V/240V' 3-phase 4-wire AC power supply system used in the UK.

Figure 3 shows basic details of the above-mentioned '415/240V' 3-phase 4-wire AC power supply system. Important points to note here are that the AC voltages on the three supply lines are 120° out of phase with each other, that the rms voltage between each of the

phase lines is 415V, and that the rms voltage between each phase line and the common (neutral) line is 240V. This type of system can thus be used for driving high-power 3-phase 415V electric motors by connecting the motor to all three phase lines, or can be

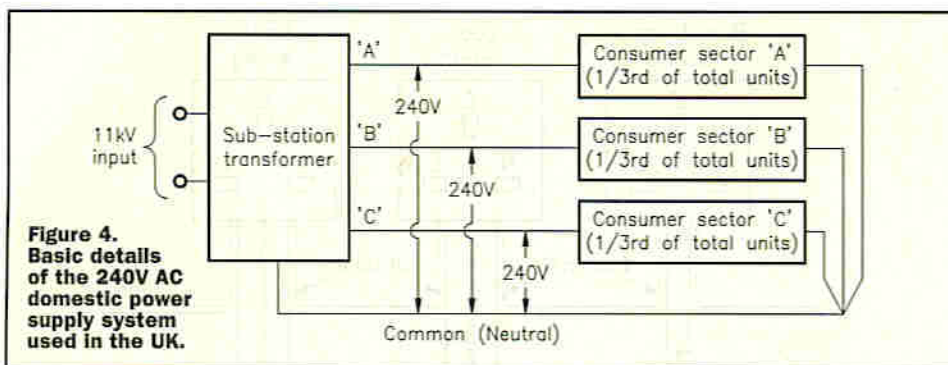


Figure 4. Basic details of the 240V AC domestic power supply system used in the UK.

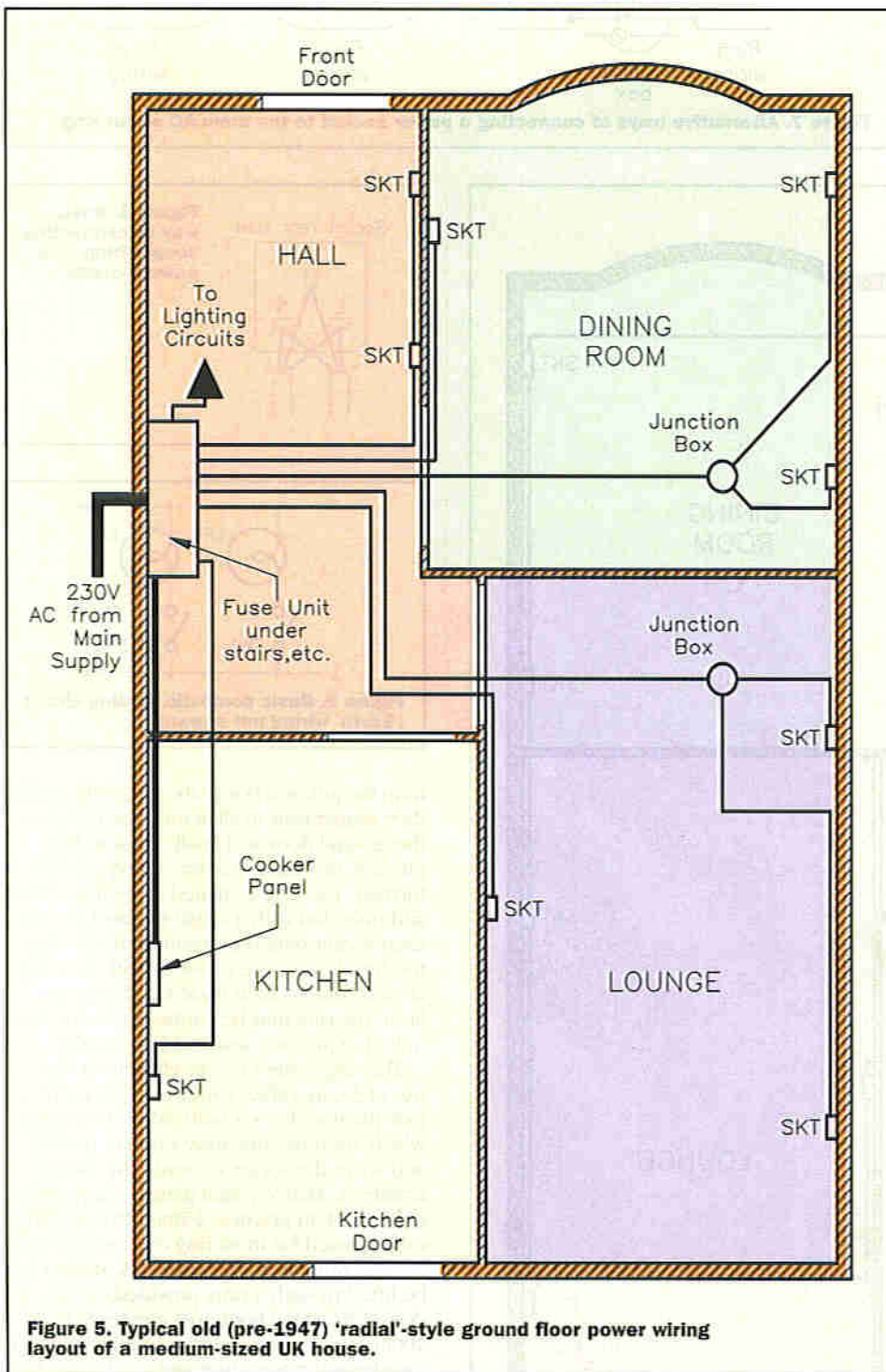


Figure 5. Typical old (pre-1947) 'radial'-style ground floor power wiring layout of a medium-sized UK house.

used to supply normal 240V AC power to domestic or commercial premises (etc.) via the common line and any one of the three phase lines.

One other important feature of the Figure 3 AC power supply system is that, because of

the 120° phase shift that exists between the three supply lines, the sum of the three instantaneous voltages that appear between common and the three phase lines always equals zero. When, for example, the 'A'-line voltage is at its peak value of +340V, the 'B'

and 'C' voltages are each at -170V, thus giving an overall sum of zero volts. Consequently, if identical loads are connected between each phase line and common, each phase line will supply an identical rms current, but zero rms current will flow in the common line. These simple facts form the basis of the normal 240V AC domestic power distribution system, which is shown in Figure 4.

In Figure 4, the area supplied by a local sub-station transformer is divided into three consumer zones or sectors, each of which consumes approximately one third of the total electrical units absorbed by the area. Each of these sectors is connected to the 240V AC supply provided by one specific phase ('A', 'B', or 'C') of the 3-phase supply, and via the sub-station's common line. Thus, if the system is perfectly balanced, the common line will always carry near-zero current, and if the system is severely disrupted (by the temporary removal of one complete sector from the system), the common line will carry a current no greater than that of the larger of the two remaining phase currents. Consequently, this basic 3-phase system allows any desired number of consumers to be supplied with a 240V AC single-phase 2-wire (plus 'earth') power supply, using only a 4-wire distribution system in which each wire requires a maximum current rating equal to one-third of the peak total current consumed by the system. This system is thus highly efficient in terms of power distribution costs.

Domestic AC Wiring Systems

Most ordinary houses are, as described above, provided with an ordinary single-phase AC power supply system. **In the UK, this is actually a 50Hz 240V supply that is regulated to within 6% of 240V (i.e., within the limits 224 to 256V), but is often called a '230V' supply to harmonise with the nominal 230V 'norm' of other European Community countries.** The supply is connected via a 3-wire 'phase, neutral and ground (earth)' distribution network. A few large domestic premises (and many industrial units) are also supplied with a 3-phase 415V supply, for operating heavy-duty electric motors (for powering lifts, etc.).

In the UK, all 'modern' house wiring is designed to conform to safety regulations that were first laid down in 1947; these regulations have since been upgraded in fine detail, but are unchanged in essence. Thus, if you live in an old house that has not been rewired since 1947, it is probable that your old wiring has now reached a point where its rubber insulation has perished to the state where a total breakdown is imminent and the whole shambles is in danger of bursting into flames, and an urgent rewire - to modern standards - is probably required.

In all domestic UK buildings, electric power is fed into the house from the external 240V AC network and applied, via the building's electricity meter, to the individual household circuits via individual fuse units or, in modern systems, via a multi-fused consumer unit. The household circuits are, for convenience, classified as three distinct types, (a) power

circuits (feeding power sockets, etc.), (b) lighting circuits and (c) accessory circuits (individual heavy-duty circuits feeding immersion heaters, cooker panels, etc.).

Old-style (pre 1947) electrical systems use a *radial* system of power circuit wiring, as shown in Figure 5. Here, each individual power socket or small group of sockets is treated as an individual circuit and is connected to the AC power line via its own specific fuse and length of 3-core cable; often, the phase ('live') and neutral lines of each circuit are individually fused. Such systems are inefficient; they require excessive amounts of cable and many fuses.

Modern (post-1947) UK systems of power wiring use a *ring* system of power-socket wiring. Figure 6 shows a typical example of such a system, in which the ring can be connected directly to the fuse box (consumer unit) or can be connected via a junction box, as shown. Here, a 3-core power cable is run

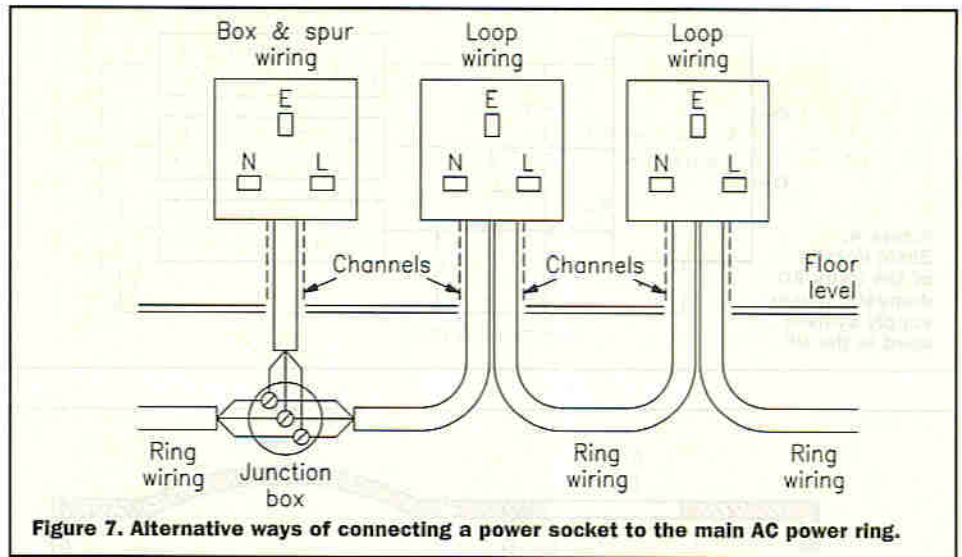


Figure 7. Alternative ways of connecting a power socket to the main AC power ring.

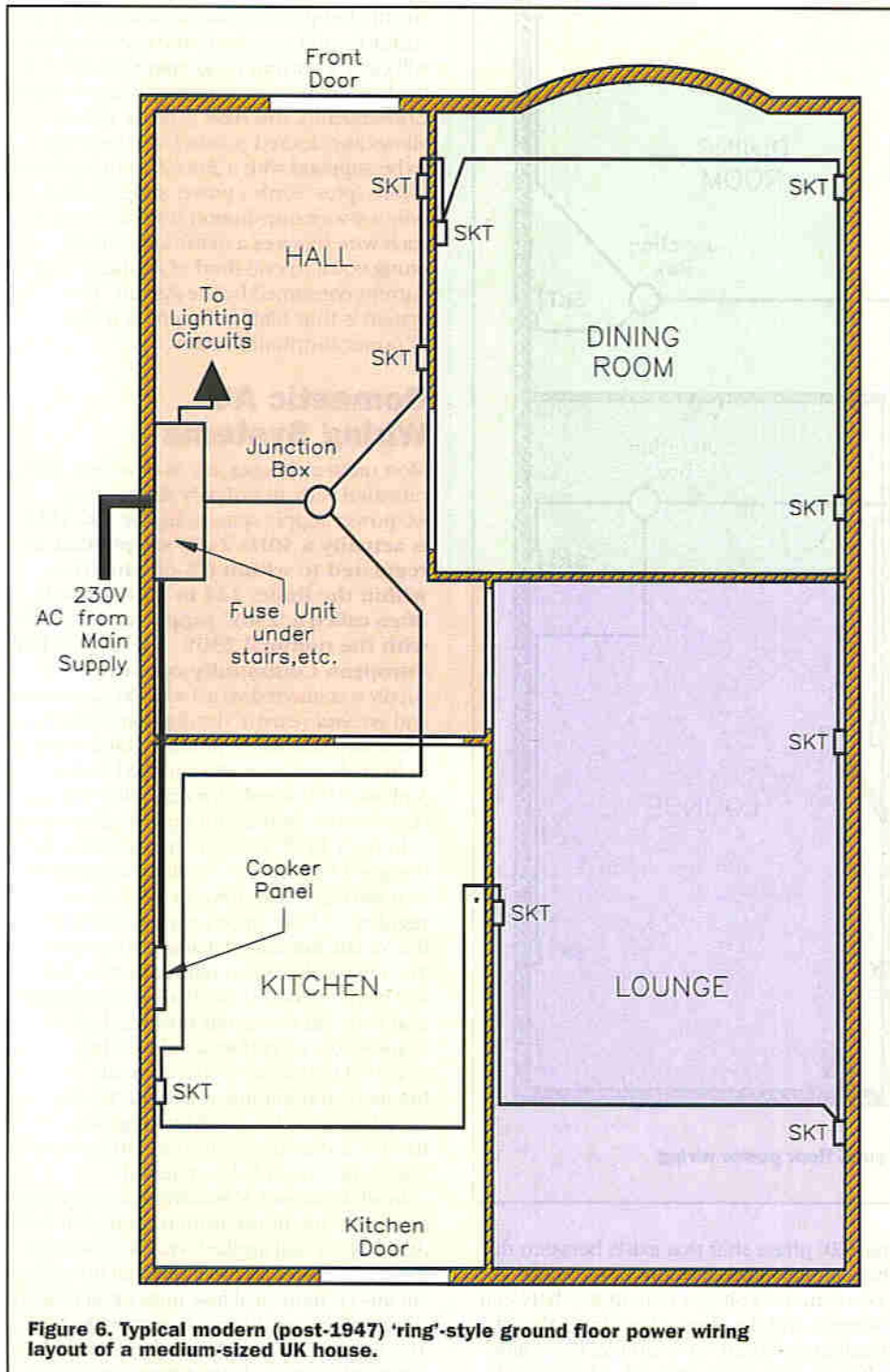


Figure 6. Typical modern (post-1947) 'ring'-style ground floor power wiring layout of a medium-sized UK house.

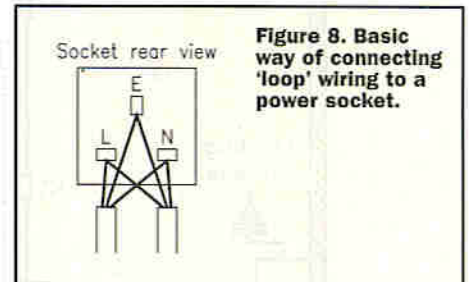


Figure 8. Basic way of connecting 'loop' wiring to a power socket.

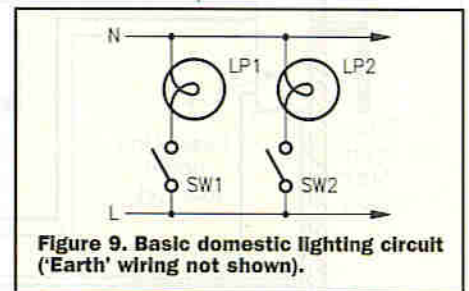


Figure 9. Basic domestic lighting circuit ('Earth' wiring not shown).

from the junction box to the first (hall) socket, then sequentially to all of the sockets on (say) the ground floor and finally, back to the junction box again, so that a 'ring' of cable is formed. The ring is treated as a single circuit and provided with a single master fuse, but each socket plug is individually fused. Most modern houses are provided with two ring circuits, one to each floor. On the upper floor, the ring may be connected to the fuse unit via a junction box and feeder cable.

The ring system is very efficient in the use of 3-core cable. Power is fed to each individual socket via both sides of the ring, which are thus effectively wired in parallel and share the socket current. This factor enables a relatively light gauge of ring cable to be used. In practice, 2.5mm² PVC sheathed cable is used for most ring circuits, and any desired number of standard 13A sockets can be fitted to such a ring, provided that it does not serve a floor area greater than 100m²; such a ring must be fitted with a 30A (maximum) master fuse and can handle up to 7.2kW. The feeder cable to such a ring (if used) must be a 4.0mm² type. Note that most 2.5mm² cable has a maximum current rating of only 20A, so if such cable is used to make a multi-socket 'spur' that is tapped into the main ring, the spur must be fitted with its own 20A (maximum) master fuse.

Modern Power Circuit Wiring

Rewiring the power circuitry of an average house to modern standards is a technically fairly simple task, but involves much dirty and hard work. Normally, the power ring is laid below the floorboards, and is connected to the individual power sockets by using either 'loop' techniques, or 'box-and-spur' techniques, as shown in Figure 7.

Before starting such a rewire, plan very carefully the precise layout of each basic wiring ring, and the desired number and positions of all of its power sockets. Flush-type sockets are fitted into special metal boxes, which must (usually) be set into a wall or plaster, in which a channel must also be cut to accommodate the socket's power wiring, which is fed upwards from the sub-floor power ring. The socket can be loop-wired into the ring by (1) making a loop in the ring's wiring, (2) feeding the loop up to the socket, then (3) cutting the loop so that two effective lengths of 3-core cable are available; finally, (4) the tips of the six 'cores' can be bared and wired to the socket as shown in Figure 8. Note that this loop technique requires two lengths of cable to be buried in the socket's wall channel; the alternative 'box-and-spur' technique (Figure 7) requires only one length of cable to be so buried, the other end of the cable being connected into the ring via a sub-floor junction box.

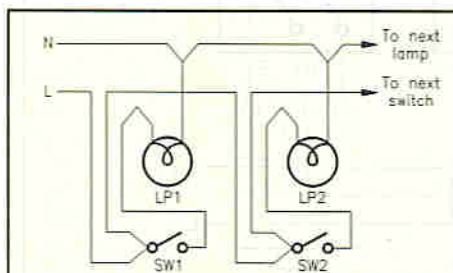


Figure 10. Old-style implementation of the lighting circuit (Earth wiring not shown), with three wires (plus Earth) running down to each switch.

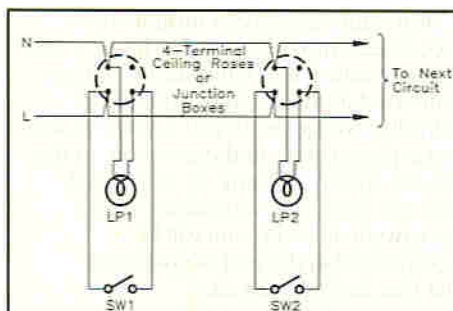


Figure 11. Modern-style implementation of the lighting circuit (Earth wiring not shown), with two wires (plus Earth) running down to each switch.

Modern Lighting Circuit Wiring

The basic AC lighting circuit of a domestic system is deceptively simple, as shown in Figure 9. Note in particular, that the light switch is used to connect the lamp to the live (L) side of the supply, thereby ensuring that an electric shock cannot be received from the lamp (when changing a bulb) when

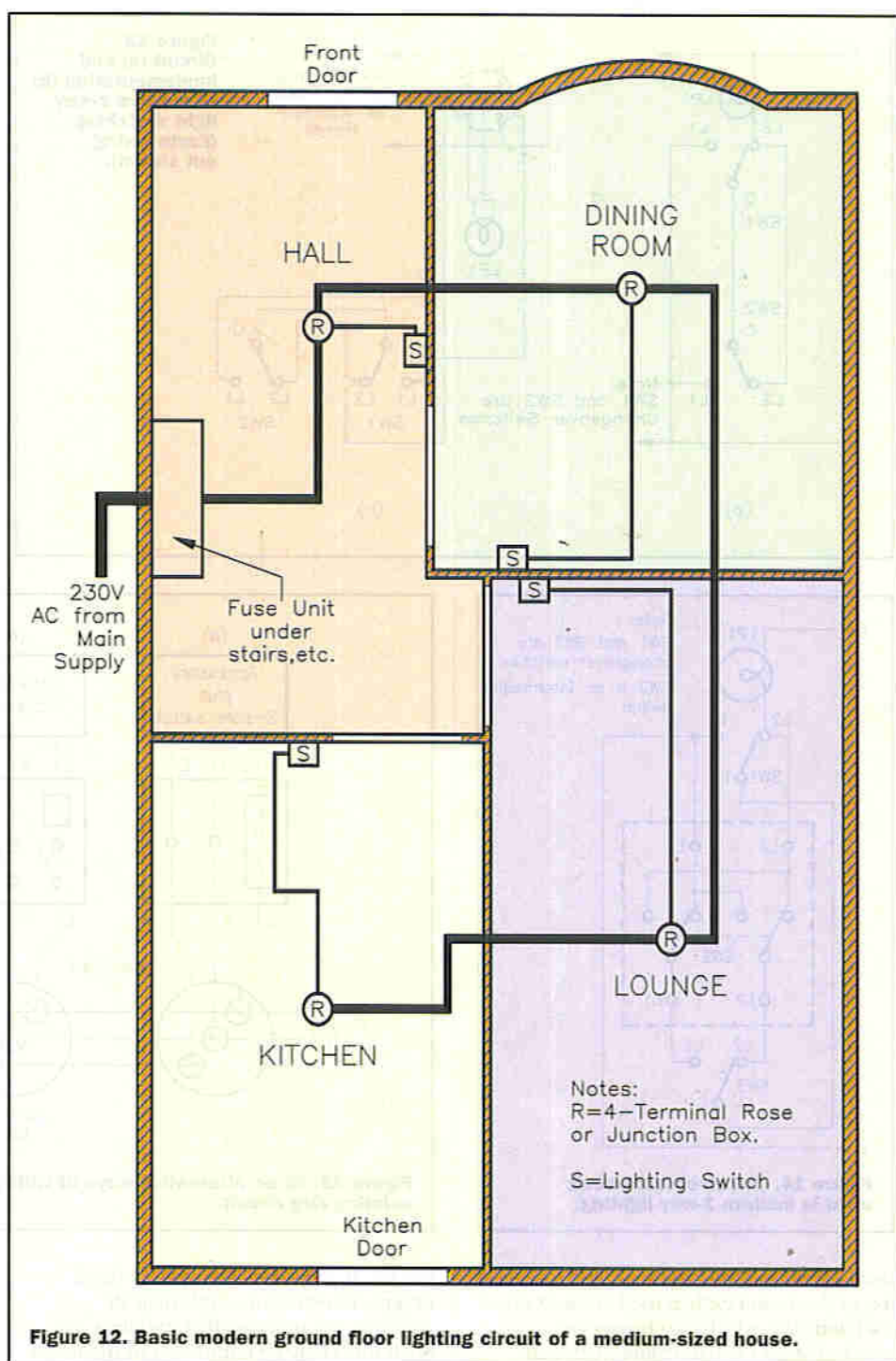


Figure 12. Basic modern ground floor lighting circuit of a medium-sized house.


the switch is open ('off'). Also note that all lamp-plus-switch circuits are wired in parallel, across the supply lines, in 'radial' form.

The physical implementation of the Figure 9 circuit is not simple. Figure 10 shows the old-style (pre-1947) method of implementation, in which Neutral (N) goes to one side of each lamp and the Live line is looped from one switch to the next. Note that this method requires three wires plus Earth (E) to be run down to each switch. In practice, the old-style wiremen often ignored the 'polarity' rules and switched the Neutral line, so that the lamp socket remained permanently (and dangerously) 'live'.

Figure 11 shows the modern wiring method, which requires only two wires (plus Earth) to be run down to each switch. The system makes extensive use of 4-terminal ceiling roses or junction boxes. In practice, 1mm² 3-core 'twin and earth' (T & E) cable is used for wiring most domestic lighting circuits.



Figure 12 shows (in simplified form) the basic modern ground-floor lighting layout of a medium-sized house. The power feed is taken from the main fuse box and runs, 'radial' style, to all the roses of the ground floor lights. Light switches are wired to the roses via additional cable. Once again, the system looks deceptively simple. In reality, the wiring to the roses runs above the ceiling; thus, the ground-floor's wiring must be laid by partially raising the carpets and floor boards on the first floor, and the wiring to the wall-mounted switches must be made by cutting suitable channels in the plaster, between the ceiling and the switches. Also, it is usual to apply multi-way switching (rather than switching from only a single point) to hall and landing lights, and this can be a very time-consuming task.

Figure 13 shows the circuit and implementation of 2-way light switching. In practice, 3-core 'twin and earth' cable is

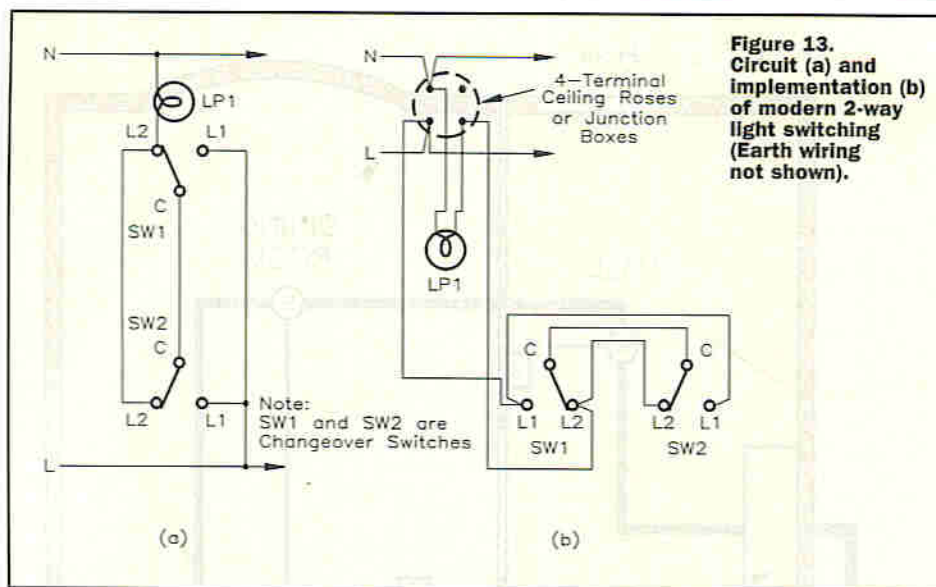

ring circuits. In the latter case, the accessory must be connected to the ring via a fused connection unit (often called a 'fused spur unit') and must be controlled via a double-pole switch, which may be incorporated in the accessory or the connection unit, or may be connected in series with the wiring.

Figure 15 shows three alternative ways of wiring fixed light-duty accessories to an existing ring circuit. In (a), the accessory incorporates a 2-pole switch and is connected to the ring via a simple fused connector unit and a junction box. In (b), the unswitched accessory is connected to the ring via a fused connector unit that incorporates a 2-pole switch and via a junction box. In (c), the unswitched accessory is connected to a switched fused connection unit that is loop-wired into the ring circuit.

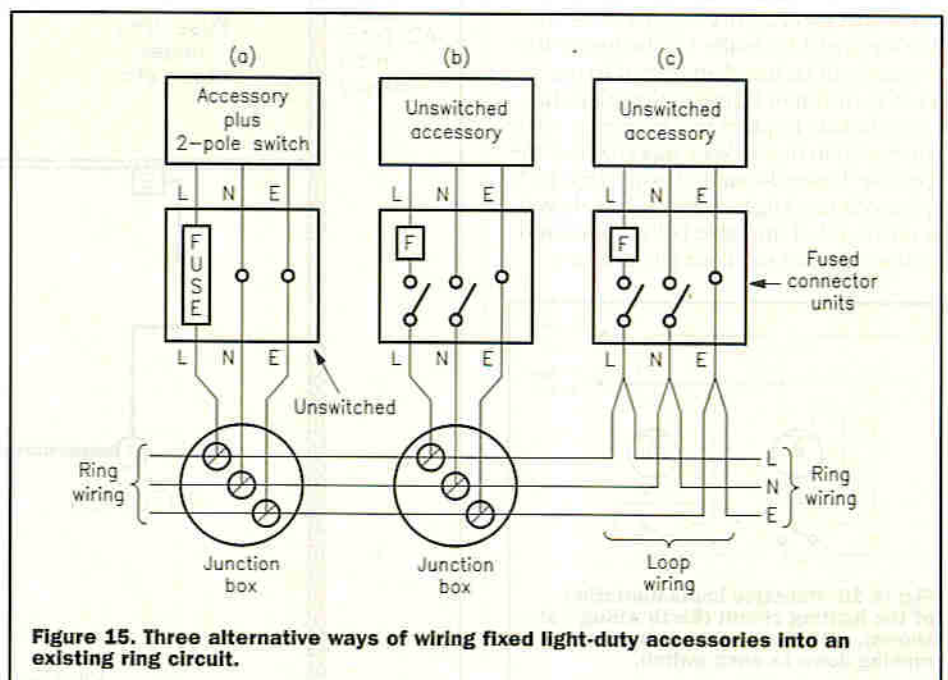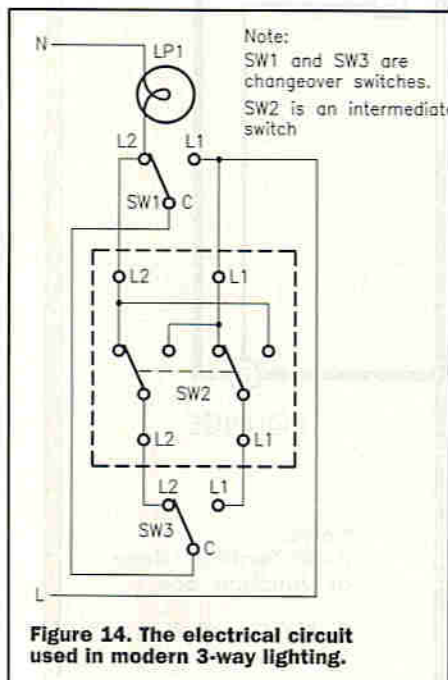

used to connect SW1 to the ceiling rose, and 4-core '3-core and earth' is used to interconnect SW1 and SW2, which are changeover switches. A lot of channelling work may be required to implement this system.


Figure 14 shows the electrical circuit involved in 3-way light switching, such as is often used in a hallway, in which the light can be controlled from either end of the hall and from an upper floor. This circuit uses two changeover switches and one standard 'intermediate' switch (available from most electrical retailers). This circuit is very time consuming to install and requires a lot of channelling.

Accessory Circuit Wiring

'Accessory' wiring is used for connecting fixed wired (non-plugged) appliances to the AC power supply, and comes in two basic types, being for either less-than-13A light-duty use, or for greater-than-3kW (= 12.5A at 240V) heavy-duty use.

Light-duty accessories include items such as electric door bells that are AC powered via step-down isolating transformers, electric clocks, small (less than 3kW) fixed

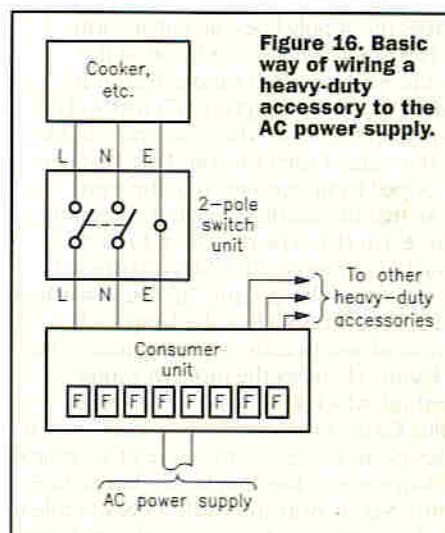electric heaters and fans, hot-air hand dryers, air extractors, and small air conditioning units or dehumidifiers, etc. Such units may be connected to the fused consumer unit via individual wiring spurs, or can be connected to one of the main



Heavy-duty accessories include items such as electric cookers, water heaters, and storage heaters, etc., which must each be connected to the consumer unit via an individual wiring circuit and a 2-pole switch that is placed close to the accessory, in the manner shown in Figure 16. The circuit does not have to be individually fused, since overload protection will be incorporated in the part of consumer unit that feeds the circuit.

Practical Rewiring Hints

Electrical rewiring is a technically simple but physically arduous, dirty and time-consuming task that can save the keen DIY enthusiast a huge amount of money. To gain access to underfloor wiring areas, you will usually have to move lots of furniture, lift large areas of carpet, and raise several floor boards in each room. You will have to crawl about beneath the floorboards, and may have to drill holes through joists and beams to facilitate wiring runs. If you are adding new flush-fitting power points or lighting switches to a house, plaster (and sometimes bricks) will have to be

Figure 17. This wiring tracer works on the magnetic-field detection principle.


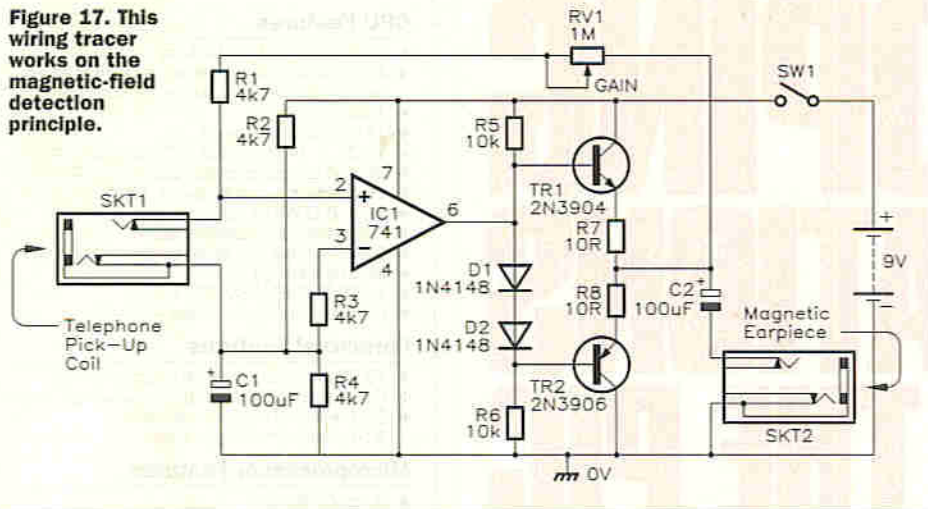


Figure 18. Circuit of a simple B.F.O.-type wiring and metal-pipe seeker; the unit is used in conjunction with a hand-held AM radio.

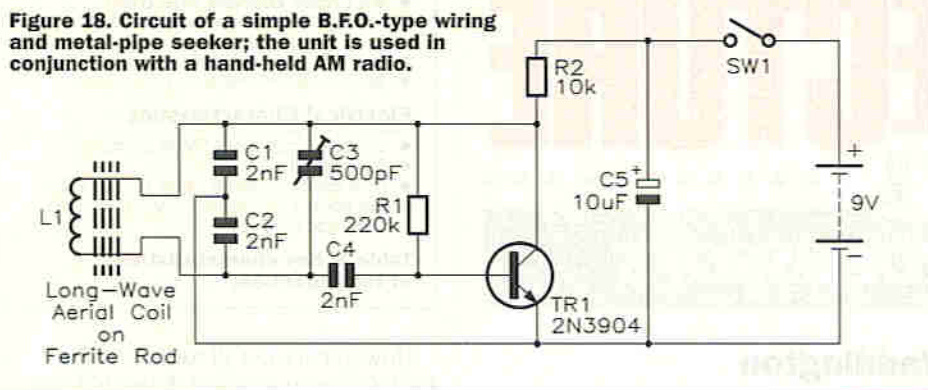

channelled to accept new cable runs and must be repaired afterwards. Essential tools for these jobs include two 2.5in. bolster chisels, a lump hammer, and a good power drill.

Before starting your first rewire, buy or borrow at least two good DIY books on the subject, and study them carefully. One highly recommended book is the Collins *Wiring & Lighting DIY Guide*, available from Maplin (Order Code WT56L), which gives step-by-step instructions on most practical aspects of house wiring. When you are ready, plan your new wiring layout with great care, giving lots of thought to the positioning of new power sockets, light switches, and ceiling roses, etc. In many

houses, most of the original switch and power-socket wiring and floor-to-floor feeder cabling, etc., is fed via metal conduit (tubing), and your rewiring task may be greatly simplified by re-using this conduit, as explained in some of your DIY books.

Figures 17 to 19 show some useful rewiring aids. The Figure 17 and 18 circuits can be used for tracing old wiring and conduit, and the Figure 19 circuit acts as a 'marker beacon' that can be used to indicate the loft or under-floor break-through positions of pilot holes drilled through ceilings when installing new feeder cable runs or when re-positioning ceiling roses, etc.

The Figure 17 wiring tracer works on the magnetic-field detection principle and is used to trace 'live' wiring that (ideally) is actually passing current to a load. The wiring is located by sweeping across its suspected path with an ordinary telephone pickup coil until its 50Hz magnetic field induces a signal in the pickup coil. This signal is amplified by op-amp IC1 and power-boostered by the Q1-Q2 (etc.) amplifier, to finally produce a distinct 'hum' sound in the magnetic earpiece.

The Figure 18 circuit acts as a simple beat-frequency oscillator (B.F.O.) metal detector that is used in conjunction with a hand-held AM (long-wave or medium-wave) radio, and can be used to locate heavy-duty wiring or metal plumbing. The circuit is simply that of an L-C oscillator, in which the inductance of L1 (and thus the frequency of oscillation) is influenced when L1 comes near most

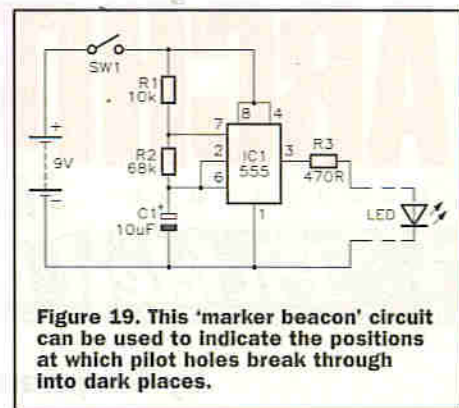


Figure 19. This 'marker beacon' circuit can be used to indicate the positions at which pilot holes break through into dark places.

common types of metal. In use, the unit and the small radio are switched on and the radio is tuned until a low 'beat' note is heard from its speaker; this 'beat' note should change when the unit's 'search head' (L1) is placed near metal. Hidden wiring (etc.) can then be located and its path traced by sweeping across its suspected route with the search head.

Finally, the Figure 19 'marker beacon' circuit consists of a simple low-frequency '555' astable multivibrator that pulses the LED on and off at a slow rate; the LED should be soldered to the end of a fairly stiff length of 2-core flex, so that it can easily be passed through small drilled (pilot) holes, etc.

MAGAZINE BINDER



The Maplin magazine binder holds twelve issues of *Electronics*. This great quality binder comes in hard-wearing laminated art board. Now you can keep all of your copies of *Electronics and Beyond* together and on hand, for when you need that extra piece of information. To order, simply fill in the Order Coupon in this issue or call the Credit Card Sales Hotline on (01702) 554000 or visit your local Maplin Store.



Order as
50913
£6.99

DEVELOPING APPLICATIONS AROUND THE PIC ARCHITECTURE

PART 2

Pickled Processors

by Stephen Waddington

Last month, we took a first look at the elements of a generic microprocessor. Here, Stephen Waddington talks through the basic characteristics of the PIC microprocessor

The PIC microprocessor family is available in three key flavours of increasing processing capability, as shown along the performance axis in Figure 1. These range from the low-end 20MHz PIC16C5X, typically with 12 I/O lines, a 12-bit instruction set and no interrupt resources, through to the 25MHz PIC17CXX with up to 33 I/O lines, a 16-bit instruction set and up to 11 interrupts.

Figure 1 also shows another type of segmentation, in terms of local memory technology ranging from conventional ROM through to EPROM (Erasable Programmable Read Only Memory) and EEPROM (Electrically Erasable Programmable Read Only Memory). Pure ROM-based devices are the least versatile, since they can only be programmed once. By contrast, EEPROM based devices can be repeatedly programmed and re-programmed with ease.

The conventional way to develop a microprocessor-based system, is to determine the scope of the application and then select a microprocessor capable of handling the job. In many ways, we decided to turn this process on its head when we opted to focus purely on PIC-based microprocessors, rather than taking a wider outlook. The bad news for purists is that we're going to go one stage further. In order to get to grips with developing PIC systems from the ground up, this article will focus on a single member of the PIC family – the PIC16C84. Table 1 shows the key characteristics of this device, while Figure 2 shows a pin-out diagram.

	ROM	EPROM	EEPROM	
PIC17CXX		17C4X		High-end 16-bit Instruction
PIC16CXX		16C6X 16C7X	16C8X	Mid-range 14-bit Instruction
PIC16C5X	16CR5X 16CR5XA	16C5X 16C5XA		Base-line 12-bit Instruction

Figure 1. PIC 16/17 microcontroller families.

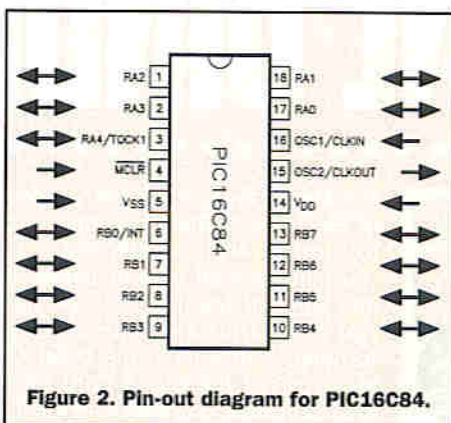


Figure 2. Pin-out diagram for PIC16C84.

CPU Features

- ◆ Only 35 instructions to learn
- ◆ All instructions are single cycle (400ns) except for program branches which are two cycle
- ◆ 10MHz clock
- ◆ 14-bit wide instructions
- ◆ 1,024 × 14 on-chip EEPROM program memory
- ◆ 36 × 8 general purpose registers (SRAM)
- ◆ 15 special function hardware registers
- ◆ 64 × 8 EEPROM data memory
- ◆ Eight level deep hardware stack
- ◆ Direct, indirect and relative addressing modes
- ◆ Multiple interrupt sources
- ◆ 1,000,000 ERASE/WRITE cycles
- ◆ Data retention greater than 40 years

Peripheral Features

- ◆ 13 I/O pins with individual direction control
- ◆ High current (25mA per pin) for direct LED drive
- ◆ 8-bit real time clock/counter with 8-bit programmable pre-scaler

Microprocessor Features

- ◆ Power-On Reset
- ◆ Power-up Timer
- ◆ Oscillator Start-up Timer
- ◆ Self clocked Watchdog Timer (WDT)
- ◆ Security EEPROM fuse for code protection
- ◆ Power saving sleep mode
- ◆ User selectable oscillator options
- ◆ Serial in-system programming capability

Electrical Characteristics

- ◆ Low power high speed CMOS technology
- ◆ Fully static design
- ◆ Wide operation voltage range (2.0 to 6.0V)
- ◆ Low power consumption: 2mA at 5V, 4MHz; 15µA typically at 2V

Table 1. Key characteristics of the PIC16C84.

However, it's not all bad news. The PIC16C84 is an excellent device to learn the basics of microprocessor and PIC development. It uses the standard PIC instruction set of 35 instructions, with two additions to address registers which are unique to the device. This means that once you've got to grips with programming the

PIC16C84, you'll be able to work with any of the other devices in the PIC family. Perhaps even more attractive is the fact that it has 1K of local EEPROM. This makes it an ideal device to learn techniques on, since it can literally be programmed and re-programmed within 20 seconds. Figure 3 shows a block diagram of the PIC16C84.

For performance details of other members of the PIC family in comparison to the PIC16C84, check the Microchip Databook – see further reading at the end of this article. In later parts of this series, we will take a look in greater detail at other members of the PIC family.


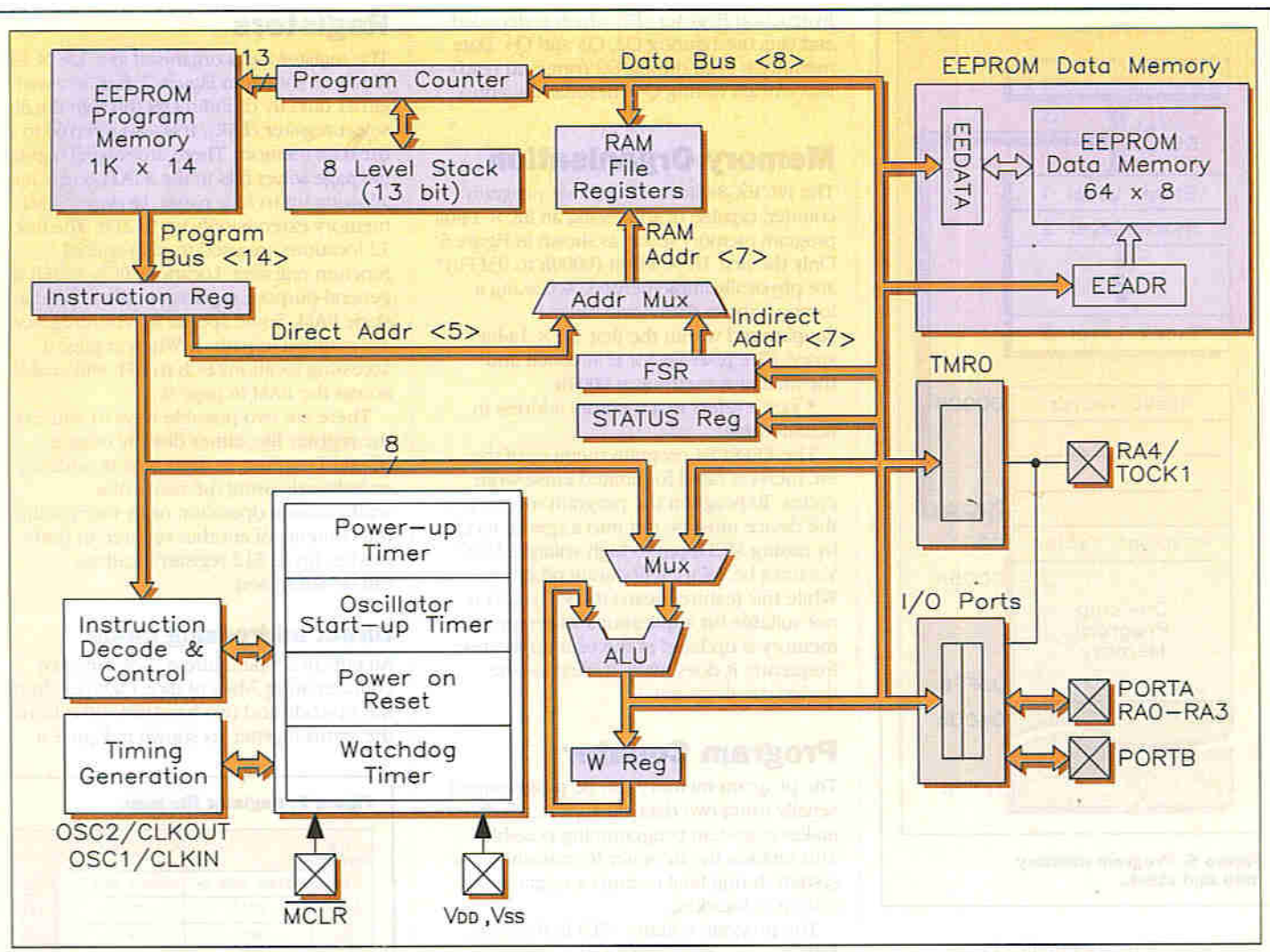


Figure 3. Block diagram of PIC16C84.

Figure 4. Clock cycle showing two stage pipeline.

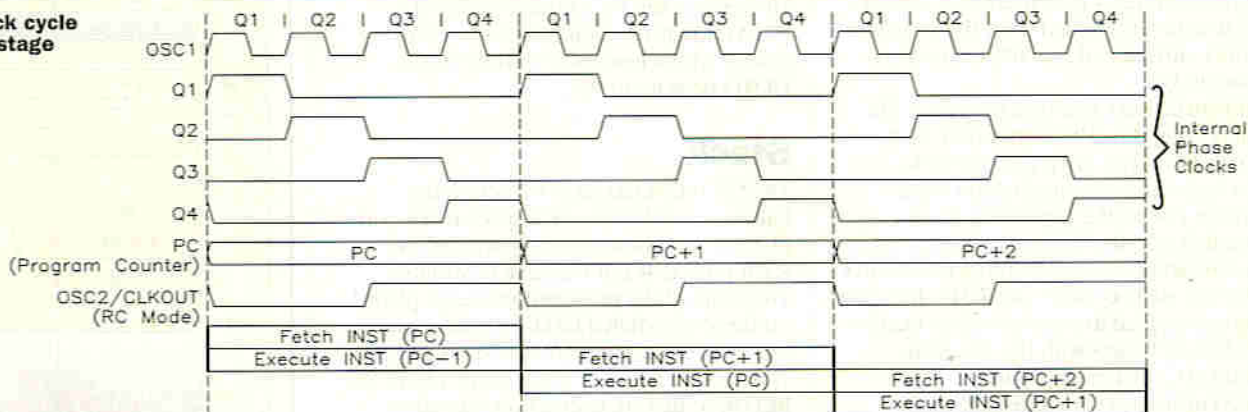

Architectural Overview

The PIC16C84 is equipped with special features such as an internal clock, sleep function, and software watchdog to reduce external components and thus cost, while enhancing system reliability and power consumption. There are four oscillator options which can be optimised by the designer for cost or power savings. The power down or SLEEP mode enables the microprocessor to be shut down when not in use, providing power savings. The user can wake up the chip from SLEEP using external interrupts or via a reset function. Meanwhile, a watchdog timer with its own on-chip RC oscillator provides protection against software malfunction.

The PIC family is based on the Harvard architecture, which means programme and data are held in separate memories. This improves the performance of the device over the Von Neuman approach, where memory is shared. It also means that the instruction length or op-code is not tied to the length of the data word. Op-codes can be greater than the 8-bit data word because they occupy their own memory.

Clock/Instruction Cycle

In the PIC16C84, all op-codes are 14-bit wide. On-chip, 1K x 14-bit is reserved for program memory. A 14-bit wide program memory

means that all instructions can be fetched in a single cycle. A two stage pipeline, as shown in Figure 4, is used to overlap the fetch, decode and execute cycle. This means that all instructions execute with a single clock cycle, with the exception of program jumps or branches.

The PIC16C84 can directly or indirectly address its 48 register files or data memory. All special function registers including the program counter are mapped in the data memory. The instruction set is fairly orthogonal, which makes it possible to carry out any operation on any register using any addressing mode. This symmetrical nature and lack of special optimal situations make programming with the PIC16C84 simplistic, yet efficient.

Indirect addressing mode

Indirect addressing is achieved by using the file address 00h (INDF). Any instruction using INDF as file register actually accesses data pointed to by the file select register (FSR). Reading INDF directly will produce 00h. Writing to indirectly results in no operation, although the status bits may be affected. An effective 9-bit address is obtained by concatenating the 8-bit FSR from the status register, as shown in Figure 8.

Event	TO	PD
Power-up	1	1
WDT time-out	0	Unchanged
SLEEP instruction	1	0
CLR WDT instruction	1	1

Table 2. Events affecting $\overline{TO}/\overline{PD}$ status bits.

Reset Event	TO	PD
WDT wake-up from sleep	0	0
WDT time-out	0	1
MCLR wake-up from sleep	Unchanged	0
Power-up	1	1
MCLR reset during normal operation	Unchanged	U

Table 3. $\overline{TO}/\overline{PD}$ status after reset.


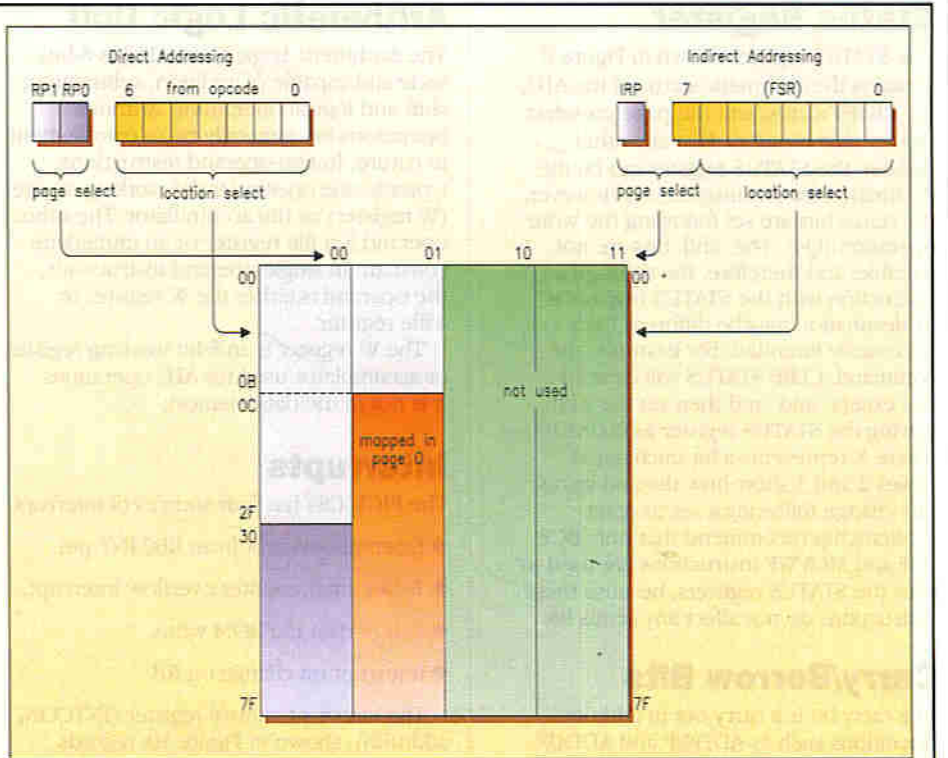


Figure 8. Direct and Indirect Addressing.

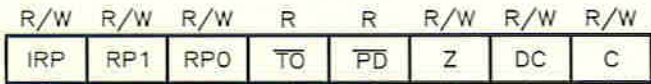

ADDRESS: 03h
RESET CONDITION: 000??XXX

CARRY/BORROW BIT:

For ADDWF, SUBWF, ADDLW and SUBLW instructions, this bit is set if there is a carry out from the most significant bit of the resultant. Note that a subtraction is executed by adding the two's complement of the second operand. For rotate (RRF, RLF) instructions, this bit is loaded with either the high or low order bit of the source register.

DIGIT CARRY/BORROW BIT:

For ADDWF, SUBWF, ADDLW and SUBLW instructions, this bit is set if there is a carry out from the 4th low order bit of the resultant.

ZERO BIT:

Set if the result of an arithmetic or logic operation is zero. Reset otherwise. Additionally, MOVF instruction will affect the Z bit.

POWER DOWN BIT:

Set to "1" during power up or by a CLRWDT command. This bit is cleared to "0" by a SLEEP instruction.

TIME-OUT BIT:

Set to "1" during power up and by the CLRWDT and SLEEP command. This bit is cleared to "0" by a watchdog timer time out.

REGISTER PAGE SELECT BITS FOR DIRECT ADDRESSING:

00 : page 0 (00h-7Fh)
01 : page 1 (80h-FFh)
10 : page 2 (100h-17Fh)
11 : page 3 (180h-1FFh)

Each page is 128 bytes.

Only RP0 is useful in PIC16C84. Bit RP1 can be used as a general purpose read/write bit. However, this may affect upward compatibility with future products.

REGISTER PAGE SELECT BITS FOR INDIRECT ADDRESSING:

IRP0 : 0 : page 0,1 (00h-FFh)
1 : page 2,3 (100h-1FFh)

This bit is effectively not used in the PIC16C84.

Figure 9. Status register.

Status Register

The STATUS register shown in Figure 9 contains the arithmetic status of the ALU, the RESET status, and the page preselect bits for data memory. Like any other register, the STATUS register can be the destination for any instruction. However, the status bits are set following the write operation (Q4). The and bits are not writable, and therefore, the result of an instruction with the STATUS register as its destination may be different than necessarily intended. For example, the command, CLRF STATUS will clear all bits except and and then set the z bit, leaving the STATUS register as 000XX100 – where X represents a bit unchanged. Tables 2 and 3 show how the and status bits change following a set or reset.

Microchip recommend that only BCF, BSF and MOVWF instructions are used to alter the STATUS registers, because these instructions do not affect any status bit.

Carry/Borrow Bits

The carry bit is a carry out in addition operations such as ADDWF and ADDLW, and a borrow out in subtract operations such as SUBWF and SUBLW. The digit carry operates in the same way as the carry bit. In this case, however, it is a borrow in subtract operations.

Arithmetic Logic Unit

The Arithmetic Logic Unit (ALU) is 8-bits wide and capable of addition, subtraction, shift and logical operations. Arithmetic operations are generally two's complement in nature. In two-operand instructions, typically, one operand is the working register (W register) or the accumulator. The other operand is a file register or an immediate constant. In single operand instructions, the operand is either the W register or a file register.

The W register is an 8-bit working register or accumulator used for ALU operations. It is not in the data memory.

Interrupts

The PIC16C84 has four sources of interrupt:

- ◆ External interrupt from RB0/INT pin.
- ◆ TMRO timer/counter overflow interrupt.
- ◆ End of data EEPROM write.
- ◆ Interrupt on change on RB.

The interrupt control register (INTCON, addr0Bh), shown in Figure 10, records individual interrupt requests in flag bits. It also has individual local and global interrupt enable bits. A global interrupt enable (GIE) bit enables – if set – all unmasked interrupts or disables – if cleared – all interrupts.

Individual interrupts can be disabled through their corresponding enable bits in the INTCON register. GIE is cleared on reset.

When an interrupt is responded to, the GIE is cleared to disable any further interrupt, the return address is pushed into the stack and the PC is loaded with 0004h. Once in the interrupt service routine, the source(s) of the interrupt can be determined by polling the interrupt flag bit(s). The interrupt flag bit(s) must be cleared in software before enabling interrupts to avoid recursive interrupts.

Next month, we'll focus on some of the special features and I/O capabilities of the PIC16C84. In Part 4 of the series, we will start building code for the PIC16C84, and begin to look at application development.

Further Reading

Data sheets containing further details of each of the PIC family are available from Maplin. Refer to the catalogue for details of individual devices.

Check the T.A.K. DesignS home page <http://www.takdesign.demon.co.uk/> for FAQ's and PIC links.

ELECTRONICS

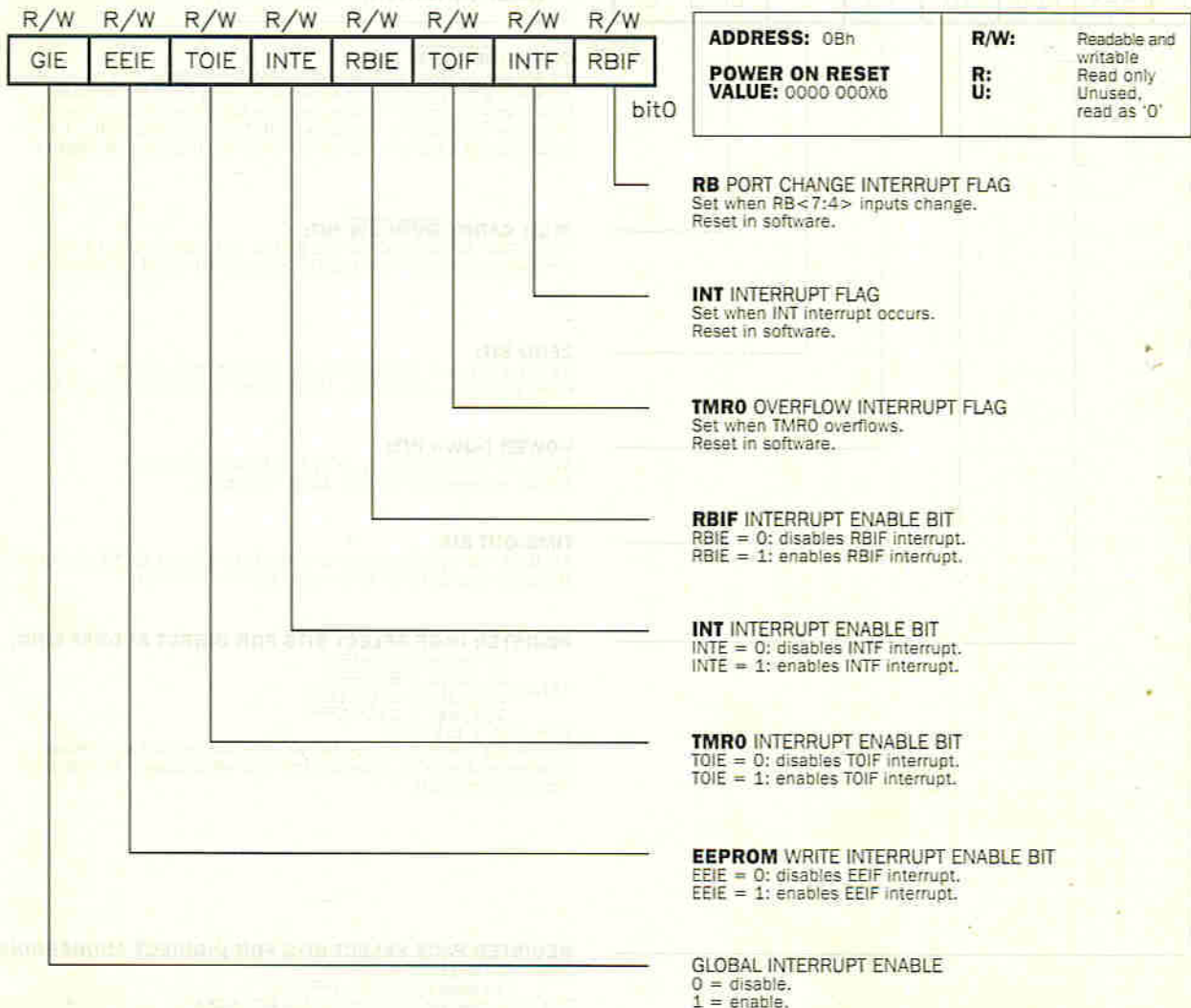



Figure 10. Interrupt control register.

ELECTRONICS PRINCIPLES 3.0


For Windows 3.1, '95 or NT.

If you are looking for a means of improving your knowledge of electronics then this is the software for you.

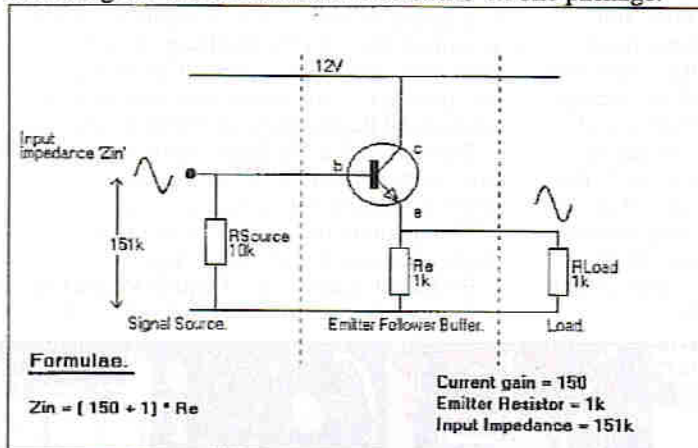Electronics Principles 3.0 now contains an extended range of fully interactive analogue and digital electronics topics, including the GCSE Electronics software in one package.



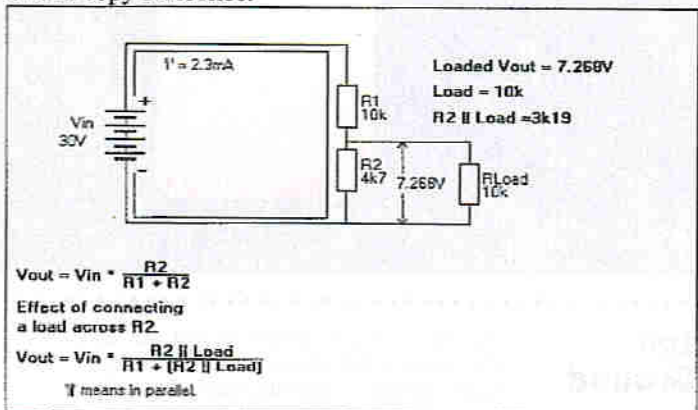
The software is completely self-contained, explanatory text and calculations are laid out in additional Windows, enabling you to see the effect of changing component values, one-at-a-time within the formulae. Graphics, text and calculations can be 'pasted', in colour into text documents for a hard copy reference.



Analogue topics, range from simple dc current flow through a conductor to complex number ac arithmetic, including bi-polar, FET transistors and Op-Amps. Digital investigation, from simple logic gates to binary arithmetic and number conversion using counters and shift registers.

Teaching Electronics & Mathematics? Our software is currently used in hundreds of UK and overseas schools & colleges to support GCSE, A level, BTEC, City & Guilds, Degree level foundation courses and a range of NVQ's and GNVQ's where students are required to have an understanding of electronics & mathematics principles.

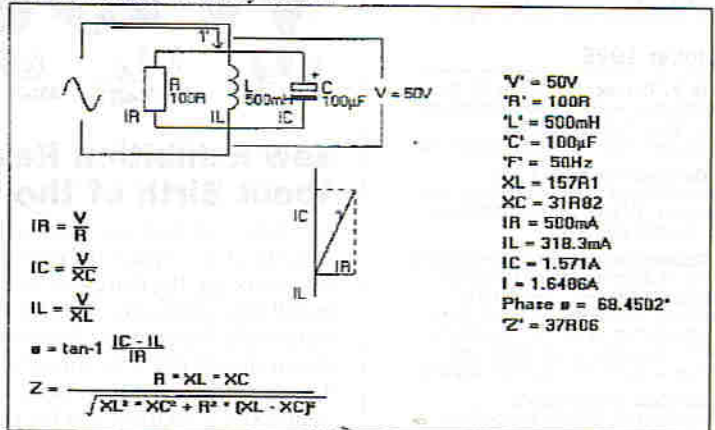'Copy to Clipboard' feature enables preparation of lecture overheads in colour, modify or expand the text to produce your own handouts or study notes.



Complete package still only £49.95


Also available as DOS version 2.1

ELECTRONICS TOOLBOX 3.0

A Windows version of the popular Toolbox Software. Presents commonly used electronics formulae and routines in a way that makes calculations easy, thus encouraging experimentation in circuit design. Just select the topic, 'pop' in your values and find the result. **Only £19.95.**

MATHEMATICS PRINCIPLES 3.0

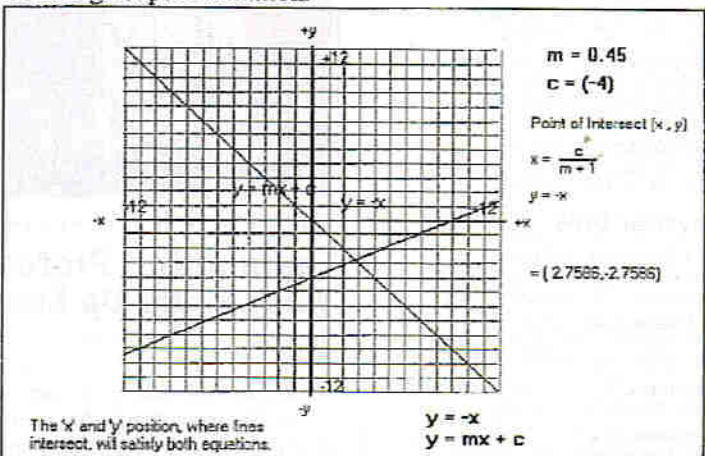An easy to use Windows package including GCSE course syllabus, enabling you to study or revise in what we believe is an interesting and enjoyable way. There are nearly two hundred mathematics topics with interactive, full colour graphics, enabling a "learning through doing" approach to encourage experimentation.



Mathematics topics, range from Number and Number Conversion, Using Numbers and Co-ordinates, Working with Fractions, Lines, Angles and Scaling, Shapes, Area and Volume, Circles, Area and Angles, Laws, Rules and Algebra, Powers, Indices, Linear Equations, Slope, Graphs and Trigonometry, Statistics, Vectors, Curves and Matrices.

As used in many schools throughout the UK. **Only £49.95.**

EPT Educational Software, Pump House, Lockram Lane, Witham, Essex, UK. CM8 2BJ. Tel/Fax: 01376 514008.

E-Mail Address, Sales@eptsoft.demon.co.uk Web pages <http://www.octacon.co.uk/ext/ept/software.htm>

For software only add £2 per order for UK post and packing. Make cheques payable to EPT Educational Software.

Switch, Visa and Mastercard orders accepted - please give card number and expiry date.

OVERSEAS ORDERS: Add £2.50 postage for countries in the EEC. Outside EEC add £3.50 for airmail postage.

Diary Dates

Every possible effort has been made to ensure that information presented here is correct prior to publication. To avoid disappointment due to late changes or amendments, please contact event organisations to confirm details.

October 1996

18 to 27 October. The Home PC Show, Autumn Ideal Home Show, International Motor Show and Connect '96, Birmingham NEC. Tel: 0121 767 4114.

20 October. Memorabilia '96. Europe's largest collectors for pop, film, SF culture, TV and comic collectables. Tel: (01462) 683965.

26 October. Computer Show, Concentrating on the 2X Spectrum and SAM Coupé. Queeby Village Hall, (outskirts of Gloucester on the B4008 Bristol Road, just off Junction 12 on the M5). Doors open to the public at 10.30am and close at 4.30pm. Tel: (01452) 412572.

28 October. Latest Kits and demonstrations. Stratford-upon-Avon & District Radio Society, Tiddington, Stratford-upon-Avon. Tel: (01789) 773286.

28 to 30 October. International Conference on Sizewell B - The First Cycle, IEE, London. Tel: (0171) 344 8432.

29 to 31 October. Electronics Commerce, Barbican Exhibition Centre, London. Tel: (0181) 332 0044.

30 October. Network Interop - Computer Networking & Interoperability, Earls Court, London. Tel: (0181) 849 6200.

November 1996

1 to 3 November. Acorn World Computer Show, Olympia, London. Tel: (01295) 788386.

6 to 9 November. Apple Expo, Olympia, London. Tel: (0171) 388 2430.

9 to 10 November. Radio Rally, Llandudno, North Wales. Tel: (01707) 659015.

11 November. System Approach to Manufacturing, IEE, Savoy Place, London. Tel: (0171) 344 5427.

11 November. Sounds of Yesteryear, Stratford-upon-Avon & District Radio Society, Tiddington, Stratford-upon-Avon. Tel: (01789) 773286.

18 November. System Approach to Manufacturing, IEE, Savoy Place, London. Tel: (0171) 344 5427.

25 November. Night on Air, Stratford-upon-Avon & District Radio Society, Tiddington, Stratford-upon-Avon. Tel: (01789) 773286.

26 November. Manufacture - Save Time, Save Money, IEE, Savoy Place, London. Tel: (0171) 344 5427.

December 1996

3 to 4 December. DSP UK - Digital Signal Processing Exhibition, Ramada Hotel, London. Tel: (0181) 547 3947.

3 to 5 December. International Online Information Exhibition, Ramada Hotel, London. Tel: (01865) 730275.

7 December. RSGB Annual Meeting, London. Tel: (01707) 659015.

8 December. SDX Cluster Support Group Eradio, Electronics & Computer Rally, Maryhill Community Centre Halls, Maryhill Road, Glasgow. Tel: (0141) 638 7670.

9 December. Quiz, Stratford-upon-Avon & District Radio Society, Tiddington, Stratford-upon-Avon. Tel: (01789) 773286.

25 December. Christmas Greetings on Air, Stratford-upon-Avon & District Radio Society, Tiddington, Stratford-upon-Avon. Tel: (01789) 773286.

January 1997

22 to 23 January. Sensors and Measurement Instrumentation, NEC, Birmingham. Tel: (01822) 614671.

Please send details of events for inclusion in 'Diary Dates' to: News Editor, Electronics and Beyond, P.O. Box 777, Rayleigh, Essex SS6 8LU or e-mail to swaddington@cix.compulink.co.uk.

What's On?



New Exhibition Reveals All About Birth of the Universe

Everything that we know of, from the tiniest particles in our bodies to space and even time itself, exists because of the Big Bang - an unimaginably hot fireball explosion some fifteen billion years ago, from which the entire Universe was born. But what is the evidence for this astonishing theory? How can today's scientists make such a convincing claim about something that happened so long ago?


By bringing together all the key evidence and latest research, an exhibition which opened on September 5th at the Science Museum, exploring fundamental questions about the origins of the Universe. Called The Big Bang - Birth of the Universe, it is the final exhibition in the Museum's highly successful Science Box series about contemporary science, sponsored by Nuclear Electric.

Highlights of The Big Bang - Birth of the Universe exhibition include a video wall featuring computer simulation of a ride back to the beginning of time, an image of deep space taken through the Hubble telescope, an interactive display which illustrates how 90% of the Universe is 'missing', and a stuffed pigeon!

A free leaflet accompanies the exhibition, containing details of some of the most compelling recent evidence for the Big Bang. Workshops, demonstrations, drama performances and trails are just some of the events that will help visitors understand the Big Bang and related subjects.

Entrance to The Big Bang - Birth of the Universe, open until 5 January 1997, is included within the Science Museum's standard admission price of £5.50 for adults and £2.90 for concessions. The Science Museum is open daily from 10.00 to 18.00hrs.

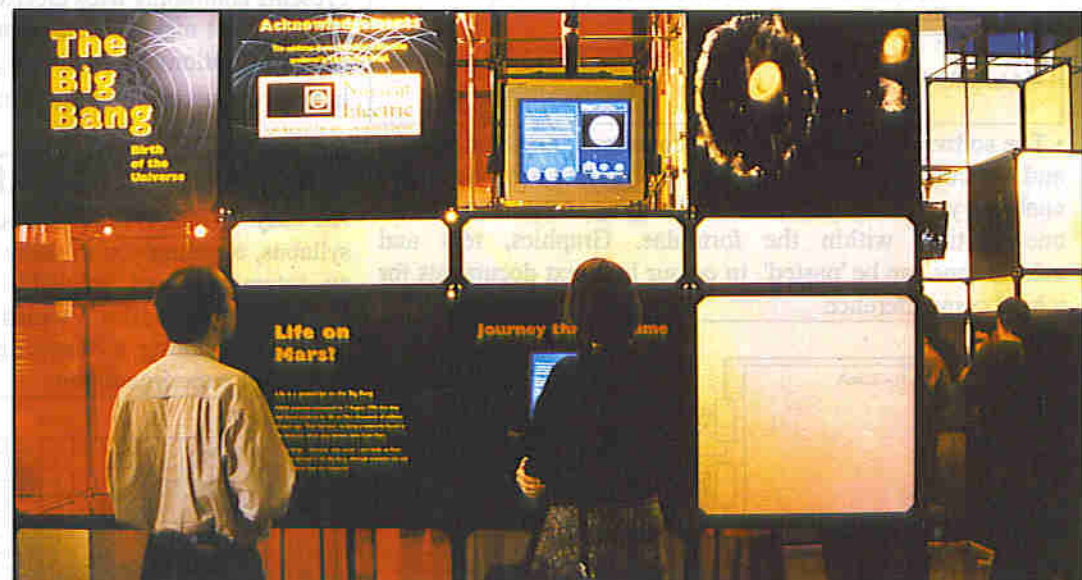For further details, check: <http://www.nmsi.ac.uk>. Contact: Science Museum, Tel: (0171) 938 8000.



Engineering Profession Must Make Up Lost Ground

The engineering profession must overcome decades of cultural complacency if it is to regain lost status and attract high-calibre recruits, said Engineering Council Chairman, Alan Rudge, speaking at the Council's annual conference in London on September 2nd.

Dr Rudge urged the profession, industry and government to work more closely together to change public perception of the profession and enable it to effectively take the initiative on issues of national debate.

"We must find ways of pooling the efforts of the whole engineering community in order to create a more credible and productive dialogue with government", said Dr Rudge, adding that the established partnership between the Engineering Council and the professional Institutions should now include closer links with industry.

"The profession needs to gain a deeper understanding of industry and this calls for a more effective ongoing dialogue than we have achieved so far", he said.

Praising the government's Action for Engineering initiative, Dr Rudge announced

that he would be discussing with Ian Taylor, the Minister for Science and Technology, how the work started by the initiative could be developed and its recommendations put into action.

Closer links between the profession and the government were also anticipated in the form of a Memorandum of Understanding between the Council and the DTI, which is currently being drafted. This, said Dr Rudge, would establish a clearer mutual recognition of what the government expects from the profession, and vice-versa.

The Conference, which addressed the key issues affecting the engineering profession and the challenges that lie ahead, is the first since the Engineering Council was restructured and relaunched as the voice of a unified profession in January this year. It also serves as a vehicle for a pre-launch event to the Year of Engineering Success (YES) - a major industry, profession and government-backed campaign aimed at raising public awareness of engineering achievement and highlighting the role of engineers in society.

Contact: Engineering Council, Tel: (0171) 240 7891.

Sega Opens Virtual Theme Park

Sega and Trocadero have teamed to open Europe's first interactive theme park in Piccadilly, London. Segaworld combines virtual reality and advanced computer graphics to create interactive entertainment instead of the movement on which traditional theme park rides rely. Sega already operates two such parks in Tokyo, and plans to open other ones in Sydney and elsewhere.

Occupying 110,000ft.², spanning four buildings of the original Trocadero building and three adjacent buildings and seven floors, Segaworld will have a capacity of about 3,000 visitors. It will provide six main high-tech interactive ride attractions. Exclusive to Sega and on the cutting edge of technology, the rides are the result of over \$1 billion worth of research and development.

Minutes after arriving in Piccadilly Circus, visitors to Segaworld will be welcomed to a totally new and incredible technological world. Transported by rocket escalator to the top of Segaworld, they will then work their way down the floors. Each floor will be uniquely themed, containing a different ride and a host of interactive experiences.

Visitors will not only travel to, for example, outer space but will become immersed in it, even looking down to see their clothes transform into space suits. During tests on Aqua Planet, the undersea ride, people actually held their breaths because they thought they were underwater.

But Segaworld's unique thrill will be when the visitor influences each ride at will and actively participates in it. With the human mind playing such an influential role, each visitor will have a totally unique experience and no two visits to the attraction will ever be the same.

In addition to the six main ride attractions, Segaworld will have six themed zones, from Sports Arena to The Carnival.

Segaworld will provide the blueprint for a roll-out to major European cities over the next few years. As with Segaworld, each indoor theme park will be themed and customised to harmonise with the culture and character of the country and with its immediate environment.

Admission Prices: Adults £12.00, Children £9.00, Groups of 15 or more - 10% discount.

For further details, check: <http://www2.segaworld.com/sega/html/home2.html>.

Contact: Segaworld, Tel: (0171) 734 2777.



RECRUITMENT ADVERTS

MONDO

MAPLIN SUPERSTORE

Maplin Electronics PLC require forward thinking, ambitious staff to help us transform the face of Electronic component retailing. Our new Superstore, based on a well established retail park in Nottingham, opens for business shortly and will need a full complement of motivated staff, trained and ready to provide the highest standards of customer care. Our success is dependant on your ability to promote the quality products and service that have established Maplin at the leading edge of Electronic component supply and we want to hear from people who have the skills and experience to support this exciting concept and can meet the criteria for the following vacancies:

TEAM LEADERS Technical

Applicants must be able to demonstrate a clear understanding of the elements that are required to manage a fast-moving, profitable specialist department. An electronics qualification, such as an HNC, or two years supervisory experience, preferably in a retail/electronics environment, coupled with good communication skills, cheerful personality and determination are essential ingredients.

There are three distinct specialist areas and your area of interest should be indicated on your application:

Sound and Vision

Specialist Electronics: Components

Computer: Accessories and Networking

TEAM LEADER Store Support

Applicants should be able to demonstrate an understanding of operating systems, gained within a retail environment, and be able to manage and administer staff training and deployment issues. Crucial to the success of this role is your ability to interpret customer needs in relation to company systems and to accept challenges in a responsible and innovative manner. Previous supervisory/health and safety experience would be an advantage.

SALES ASSISTANTS Technical/General

We also require people with an interest/qualification in electronics and/or retail experience to undertake duties consistent with the efficient running of a high turnover store. Staff will work in teams with specific areas of responsibility and your ability to satisfy customer needs and promote a welcoming atmosphere is important. Posts are available on a full-time, part-time and weekends only basis.

Applications from experienced non-technical retailers are also welcome.

Successful candidates will receive a period of basic training combined with further opportunities for personal development. We can offer an excellent reward package including staff discount on personal purchases and a uniform will be supplied.

Interested applicants should write to:

Elaine Chapman, Human Resources Department,
Maplin House, 274-288 London Road,
Hadleigh, Benfleet, Essex SS7 2DE.


Please specify the post you are applying for.

Applications should contain sufficient information about qualifications, experience, personal qualities, etc. to enable us to short list candidates for interview.

Maplin Electronics PLC is an equal opportunities employer.

Heritage ON A CHIP

by Alan Simpson

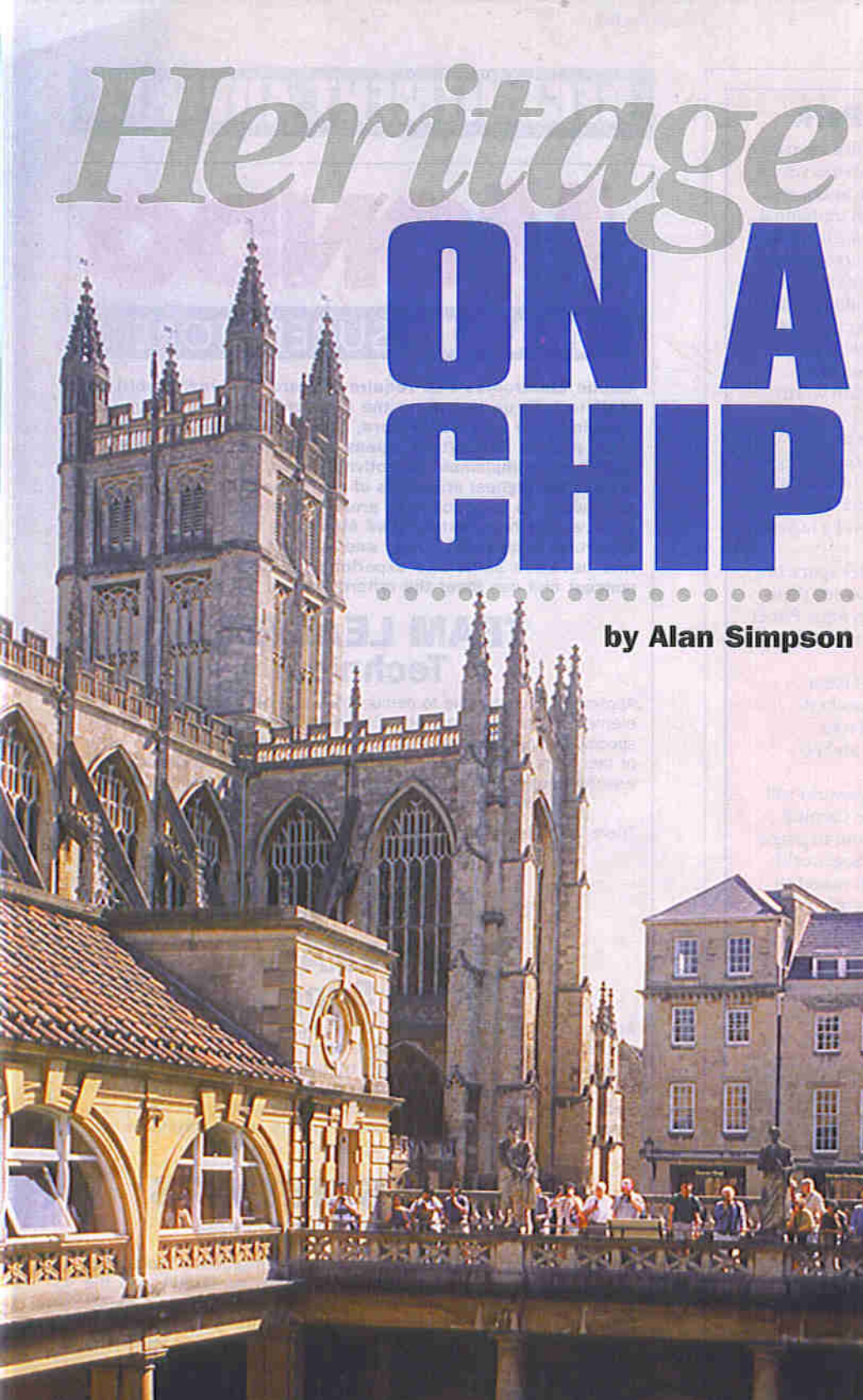

The days when you were formed into groups and led around exhibitions and museums are it seems, truly over. Instead of having to keep up with the group and push your way to the front to see and hear what was going on – only to discover that you are in the wrong group – you can now have your own personal high-tech guide to accompany you on your visit, and even more to the point, the new generation of high-tech acoustic equipment. Electronics decided to send their out and about investigative team to discover more, with first stop being Bath down in Somerset.

INFORM is a user-friendly personal audio guide which incorporates the very latest in microchip technology and is up and running at Bath's historic Roman Baths Museum as well as at the Assembly Rooms and Museum of Costume. These museums are visited by more than 1 million people each year and this installation of the INFORM system is the largest recorded tour project in the world, with each visitor receiving a handset as they enter the museums.

The system has been created by Acoustiguide, probably the world's leading record tour company, but certainly their most ambitious to date. Following the system's successful introduction to the Louvre in Paris, where the units can be hired at the entrance to all three major galleries (though what the Mona Lisa makes of it all is not known), The National Gallery of Art, Washington and at the Tate Gallery in London are also users.

See All and Hear All

Complementing the conventional guided tours, the system consists of a hand unit resembling an early generation mobile phone. The 1,300 units on site provide visitors with random access to information relating to the museum displays, allowing them to tailor their visits to individual tastes and interests. Rather than following a predetermined route through the museum, the system allows the visitor to simply key-in the relevant number, press the 'play' button and listen to an informative description of any chosen item.

Language is no barrier: more than half the visitors to the Bath museums are from overseas, so the commentaries are available in French, German, Spanish, Italian and Japanese. In addition, single earpieces adapted for visitors with impaired hearing are available. INFORM was developed specifically for use in galleries, museums and visitor attraction centres, with the unit holding considerably more information than a cassette. A further advantage is that the robust unit has no moving parts and as it can be accessed randomly, it is particularly suitable for large sites and collections.

The Tour Guide at a Touch of a Button

In terms of controls, the handset is simplicity itself. Controls include a backlit LCD display, an easy to read keypad, volume control, rewind/fast forward facility, and a pause/play button. System benefits include the ability to change the commentaries in a matter of minutes so that alterations to a gallery can be easily reflected in the audio microchip. For example, if an exhibit is removed, the tour information on the wand can be adjusted so that visitors won't wander the galleries looking for the missing item.

Flexibility is a key factor, as is the ability of museum staff to download the hand units – usually while re-charging the unit's battery is taking place – accessing such information as the most popular commentaries or the frequency that a particular item is visited. Also, such matters as how long the visitor has taken to tour the site or what sections have been skipped – invaluable data for

administrators. In winter and off-peak times, the commentary capsule can be lengthened. Statistical information can be assembled in single or multiple samples.

Rather than follow a pre-determined route through the museum, each display or section of the building has its own number. Visitors simply key in the relevant number, press the 'play' button and listen to a commentary about any chosen item. Unlike the Louvre, where the numbers attached to each object are about the size of a raffle ticket, those at Bath are clearly visible. This, of course, allows low-scale lighting to be used where appropriate and avoids the imposition of small, difficult to read labels. The labels at Bath have been designed and placed in the most conspicuous position possible, and are repeated several times around a scene or item. Positioning is particularly important in the case of children or colour blind visitors.

Acoustiguide allows museum authorities or even the artist, to speak directly to visitors at the very moment they are looking and seeing the item. However, Bath and the Louvre are not the only sites equipped with the Acoustiguide system. They have spread to the Shanghai Museum in China and the Natural Science Museum in Taiwan. Closer to home, they have been installed in Canterbury Cathedral and the Heathrow Airport Visitors Centre.

At Bath, visitors to the Roman Baths can listen to a lively narration recorded by actors bringing to life the 'caldarium' and 'frigidarium' - Roman equivalents of the Turkish bath and cold plunge. Dramatised scenes conjure up daily life at the baths in Roman times: soldiers arguing in Latin, servants scurrying about preparing their master for his daily dip and, at the nearby sacred spring, a Roman matron cursing a thief for stealing her favourite bronze pot. INFORM also highlights key exhibits such as the life-size gilded bronze head of the goddess Sulis Minerva, discovered in 1727 by workmen digging in a nearby street.



The INFORM handset's being used at the Roman Baths Museum and Museum of Costume in Bath.

Information System Makes a Splash

Increasingly, the Bath museum is incorporating technology. While touch button screens are not as yet featured, terminals do keep a close security and safety tab on what is happening within the site. Meanwhile, a virtual reality display recreates the Roman Bath complex as it was nearly 2,000 years ago. The computer graphics, incidentally, were designed by the aptly named Splash! Software Company, who worked from original drawings and documents.

Also, a degree of Roman technology has been expanded to embrace that of heat exchange. Re-using original Victorian pipes, the heat from the bubbling spring water below provides all but 5% of the energy requirements of the Museum. However, during protracted cold spells, thermostatic controls switch on conventional gas-fired boilers. (Presumably, the Romans just threw on extra towels). Not surprisingly, Bath is one of the top Local Authorities' six buildings in the country in terms of energy conservation.

The Roman Baths Museum is the most visited museum outside London, with more than 900,000 visitors every year. In Europe, Bath shares the accolade with Florence as being designated by UNESCO as World Heritage Cities. Built around the only hot springs in the UK, the museum encompasses

the remains of the Temple of Sulis Minerva, goddess of wisdom and healing, and the massive bathing complex which the Romans built next to the Temple and the spring.


Rain fell at 14.5°C, some 10,000 years ago on the nearby Mendip Hills. Driven down through carboniferous limestone cave systems by pressure from the high water table, water wells up from a depth of 3km at the rate of more than 1,100,000 litres per day. For those of a geological persuasion, the water penetrates overlying strata of impermeable Lias clay through fissures and a fault, to rise at three points in Bath. There are some 43 minerals in the water. Calcium and sulphate are the main dissolved metals, except for iron, which gives the characteristic iron staining around the baths and contributes to the water's distinctive flavour. The mineral content is 2.18g/litre.

More medical notes. In medieval times, a cure for conditions such as paralysis, colic, palsy and gout was sought from bathing in spa water. The fashion for drinking spa water arose from new medical ideas in the later 17th century. The water, it appears, was taken in the morning. For most visitors, a pint or two was sufficient, but as much as a gallon a day could be prescribed. The Roman Baths and Temple and the Grand Pump Room built above them in 1795, is a scheduled ancient monument.

All this, of course, is a far cry from the world of the microchip-driven INFORM system. But as the museum itself admits, visitors now comment on the quality of the exhibits and their enjoyment of the museum rather than the technical wizardry of the audio guides. Just what those bathing Romans would have made of the Acoustiguide is a matter for conjecture. However, for *Electronics* readers, there is a great chance to sample the system for themselves. We have no less than 10 family tickets to be won, valued at £17.60 per set. These will get you in the Roman Baths and the Museum of Costume.

So, grab your toga and get ready to pick up your Acoustiguide issued free with the ticket. And don't worry about dropping your handsets into the water. The units come fully equipped with a length of cord - to go around the neck.

ELECTRONICS

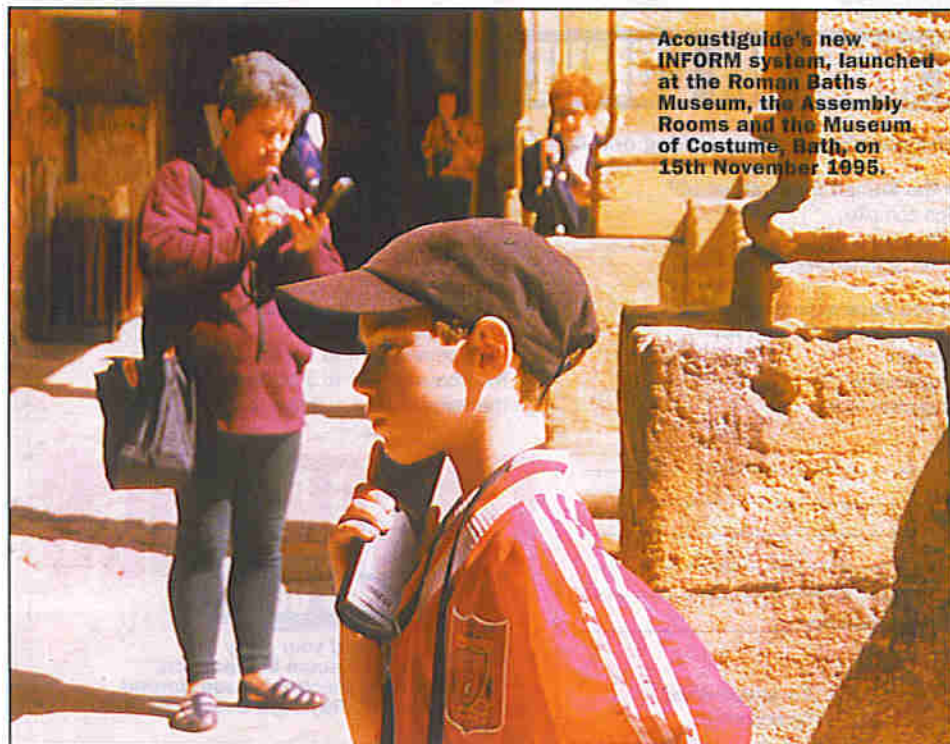


Acoustiguide's new INFORM system, launched at the Roman Baths Museum, the Assembly Rooms and the Museum of Costume, Bath, on 15th November 1995.

Bath Museum

Entrance charge for the Roman Baths Museum is £5.60 for adults and £3.30 for children. Museum of Costume admission is £3.50 for adults and £2.20 children. Combined tickets are £7.50 for adults, £4.00 for children and £17.60 for families. Open daily round the year. Tel: (01225) 477000/477785.

BATH MUSEUM

Exclusive Competition

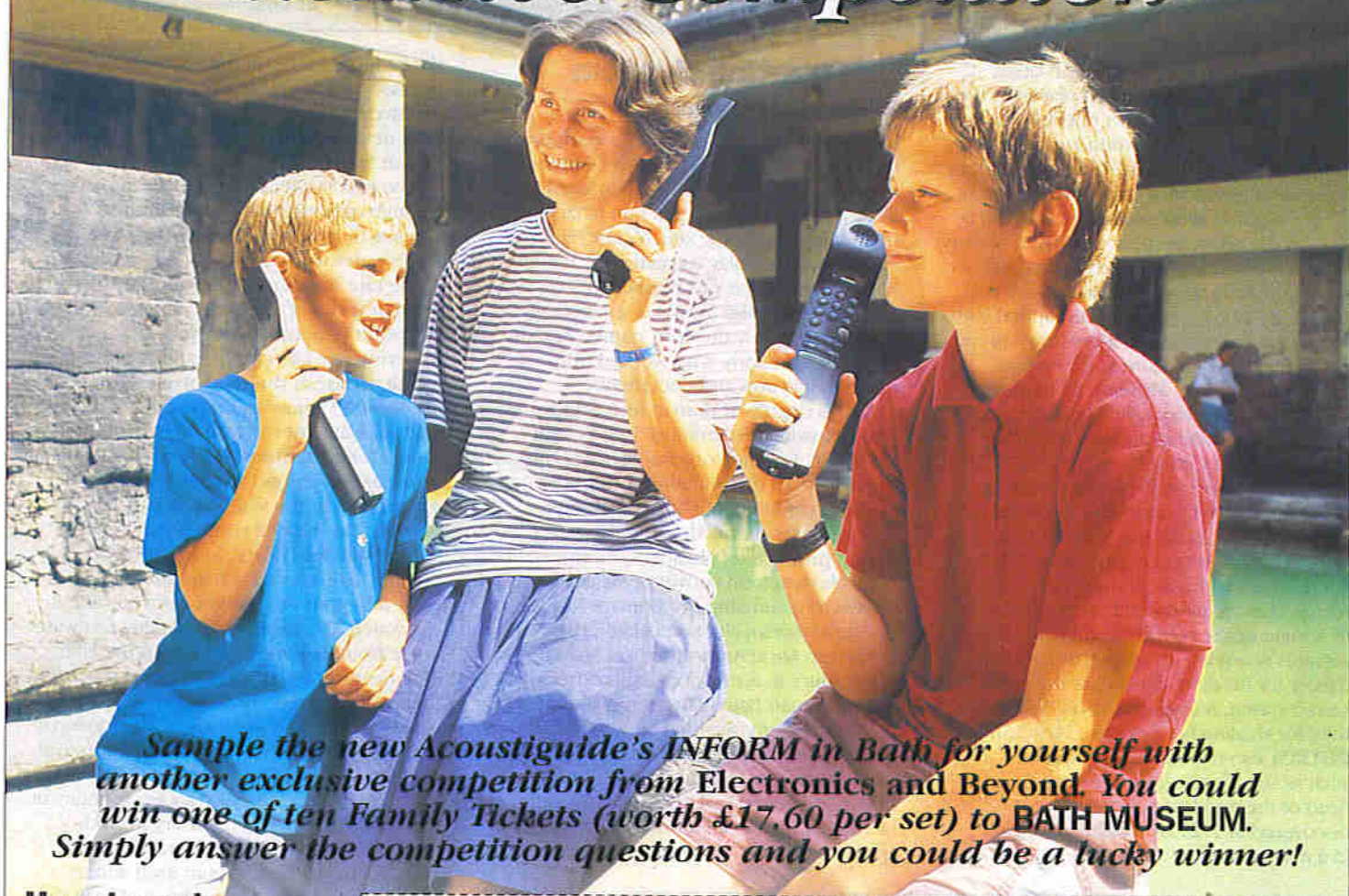

Sample the new Acoustiguide's *INFORM* in Bath for yourself with another exclusive competition from Electronics and Beyond. You could win one of ten Family Tickets (worth £17.60 per set) to BATH MUSEUM. Simply answer the competition questions and you could be a lucky winner!

How to enter

All you have to do to enter, is complete the coupon, correctly answering the four questions, or send your answers on a postcard of back of a sealed-down envelope. Don't delay - all entries must be received by 25th November 1996. Send your entry, remembering to include your name and address, and if possible, your day-time telephone number, to the address printed on the coupon.

Please note that employees of Maplin Electronics, associated companies and family members are not eligible to enter. In addition, multiple entries will be disqualified. The prizes will be awarded to the first all-correct entries drawn. The editor's decision will be final. Prizes are not exchangeable for cash. Any related travel costs will not be met by the publication or the competition sponsors.

BATH MUSEUM COMPETITION

Answer all the questions below, ticking one box for each question.

1. Where are the Roman Baths situated?

- The Bath Spa complex.
- The British Museum.
- Under the Pier, Southend-on-Sea.

2. Who would you have expected to find taking to the waters in Roman Bath?

- Pamela Anderson.
- A Roman Legionnaire.
- A Club Med snorkel class.

3. Why would anyone take to the waters?

- To alleviate a water drought.
- To cure a health problem.
- To top up the goldfish bowl.

4. Following a plunge in the Roman Baths, what happened next?

- The Romans went to a local disco.
- The Romans went to a McDonalds.
- The Romans took a steam bath.

Name _____

Address _____

Postcode _____

Daytime Telephone Number _____

No purchase necessary. Entries on a postcard, back of a sealed-down envelope or photocopies will be accepted.

ELECTRONICS

and Beyond

Send your entry to
Bath Museum Competition,
The Editor, Electronics and Beyond,
P.O. Box 777, Rayleigh, Essex SS6 8LU.

Internet Growth Heading for Red Light

According to a new study from market research house, Yankelovich Partners, the Internet is at a critical juncture. The study, Yankelovich's second annual Cybercitizen Report, reckons Internet and online usage continued to grow at 50%, from May 1995 to May 1996, but the growth from May 1994 to May 1995 was 100%.

In fact, the study predicts that growth will slow to 20% unless there's widespread movement among businesses to give employees Internet access, or unless prices for the computer equipment necessary to get online fall dramatically.

The study also reports that the average time online fell during the last 12 months from more than 16 hours a month to 12 hours a month.

"Slower growth and declining usage suggest marketers need to look beyond the faddish curiosity that has so far characterised online evolution. Marketers now need to identify compelling new reasons for people to log on and new ways of sustaining existing interests", Dr Walker Smith, Managing Partner, Yankelovich Partners told *Electronics and Beyond*.

"Consumers and marketers embraced cyberspace in 1995 without necessarily questioning why. The time has come for marketers to demonstrate a return can be made from online investments".

For further details, check: <http://www.yankelovich.com>. Contact: Yankelovich Partners, Tel: (203) 845 8288.



Save Your Screen With Internet Search

If you're bored with Starship Simulation and Flying Windows, venture out onto the Web and download yourself a new screen saver.

Organisations – both commercial and non-profit making, have been quick to follow Guinness, which last year launched a full animation screen saver with sound, based on its TV advertisement campaign.

If you try doing a search on Alta Vista at <http://www.altavista.digital.com> or one of the other Internet search engines for 'screen saver', you'll find more than 10,000 Web pages returned. Narrow the search to include 'download' and 'free' – after all, you don't want to spend any money – and you'll find around 900 Web pages returned. We've included some of best here:


- ◆ <http://www.win-uk.net/~jmoore/jon/ssaver.htm>. The Hedgehog's Bad Dream' is a screen saver with an environmental theme. It is a dynamic photo-montage, reflecting the current activities at the Newbury bypass and environmental demonstrations elsewhere around the country.
- ◆ http://ourworld.compuserve.com/homepages/silknoth/6_down1.htm. A No Smoking image and Elephant wallpaper – a variation on Microsoft's Window's wallpaper – are available for download from UK software house, Silkmoth.
- ◆ <http://www.beyondthewall.com/dlsave>. US poster company, Beyond The Wall, offers a screen saver based on 24 full screen pop-art images shown in a movie sequence to Web browsers that complete its brief questionnaire.
- ◆ <http://www.etch-a-sketch.com/etchpgs/etchss.html>. Remember Etch A Sketch? A screen saver version of the famous Etch A Sketch frame, along with five colour-animated screen savers are available here.
- ◆ <http://www.galttech.com/ssheaven.shtml>. This is reckoned to be the most comprehensive repository of screen savers available on the Internet. It's not completely exhaustive – none of the sites listed here are included – but it is packed with cool material, ranging from cartoon animation to interactive fish tanks.

Internet Config

Users of Internet Config on the Apple Macintosh should be aware that version 1.3 is released and available at several shareware sites including <ftp://ftp.tidbits.com/pub/tidbits/select/internet-config.hqx>.

Internet Config is a freeware general-purpose

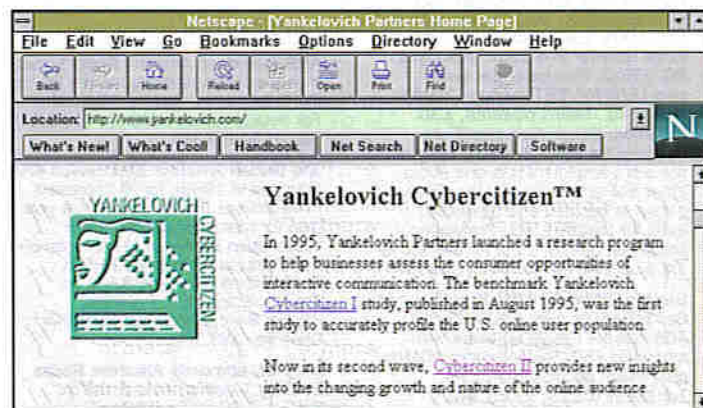Internet controlling system extension for the Mac which takes care of Internet-related topics and makes a doddle of handling multiple Internet programs on the one computer. Version 1.3 adds a few new tricks to its already impressive array. If you're not using it, you should be.



Internet Intimacy

Whatever Internet fans claim about the Internet, it remains completely impersonal. Okay, so it might be possible to 'chat' online by exchanging short messages, or send a long document to a string of people at the push of a button, but Internet communication lacks the intimacy of a handwritten note or telephone call.

Leeds Postcards claim to have solved this problem – at least, in part. Using its site at

<http://www.poptel.org.uk/leedspostcards>, you can now send a virtual postcard to anyone with an e-mail address. Enter their details; a brief message, select a postcard from one of 30 Leeds satirical postcards, and you're away.

Your recipient will receive an e-mail shortly afterwards, with details of a Web address where they can go and collect their card. As with all Leeds Postcard's material, the cards are witty, clever and well presented.






Karpov Wins Online Chess Match

In an open chess game on the Internet, Russian grandmaster, Anatoly Karpov, defeated several hundred opponents in a game that lasted 65 moves and four and a half hours. For each move, contestants had seven minutes to indicate their response, and a computer calculated the most frequently suggested response. Details of the game and forthcoming chess events can be found at: <http://www.tele.fi/karpov/gamewor1.htm>.

HTML Compiler

Oakley Data Services has launched an HTML compiler called InfoCourier for converting HTML files into executable code that can be viewed without using a Web browser. InfoCourier is available in Windows 3.1, '95 and NT flavours, priced around £120. An evaluation copy is available at <http://www.smartcode.com> or via FTP at <ftp://ftp.smartcode.com>.

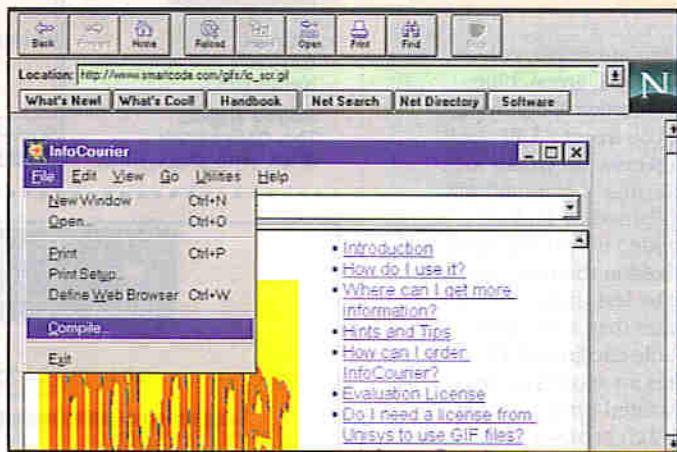Contact: Oakley Data Services, Tel: (01889) 565064.



NC-v-PC

Microsoft has finally admitted that the Network Computer (NC) concept, devised originally by Oracle, but now backed by most computer and software producers (in fact, just about all computer and software producers except Intel and Microsoft), is poised to make a significant dent in its profits. Steve Ballmer, Microsoft's second-in-command, acknowledges that unless personal computers are cheap enough to buy and maintain, a certain segment of the market (he estimates around 25% of current potential purchasers of personal computers) will buy network computers instead.

Ballmer divides the current buyers of personal computers into three definite market sectors: knowledge workers who need a powerful desktop computer, mobile workers who need efficient mobile communications (presumably currently addressed with a laptop computer), and production workers who need a computer which he calls a 'dumb terminal replacement'. This third sector is the one most vulnerable to the network computer, accounting for about 25% of personal computer sales.

The area most often touted as being the big market for network computers, on the other hand, in the home, is not even given credit by Ballmer as being of note. He cites that the cost of a Pentium computer next year will be around the same price as a network computer.

Meanwhile, other people are proposing that Microsoft is too complacent. Network computers will rely heavily on the Java language and it's Java which is seen by all (except, perhaps, notably Microsoft) as being important. Reports that Java could cut the costs of personal computing programs to 20% of their current levels are emerging. If that happens, Microsoft could be out on a limb, and the network computer on the main trunkline to success.

Shareware Web Site Creation Tool

Everyone, it seems, is having a go at building Web sites, from advertising agencies to PC vendors and from Internet service providers to graphic designers – even freelance journalists are having a go. And there's no end of tools to help novices get started. All of the major design-based software houses created Web development tools, and even companies such as Novell and Microsoft have built utilities to convert word-processor documents into HTML code.

Now, the Thompson Partnership is getting in on the action. The UK software house has launched WebExpress, a shareware application available from its Web site at <http://www.ttp.co.uk> to enable users to create a Web

site from scratch. Registration costs £58.

WebExpress is modelled on a word-processor. It allows text to be formatted and manipulated like any conventional word-processor, while graphics can be imported in GIF or JPEG formats into a text stream, either within the document or within a table cell.

WebExpress allows the user to configure background colours or images for your document and also alter the default colour for text and hypertext links.

There is nothing particularly unique or clever about WebExpress, except that it very easy to use, is low-cost, and can be downloaded from the Web. Its key limitation lies in the fact that the user is always limited by pre-defined options.

Contact: The Thompson Partnership, Tel: (01889) 564601.

Bug off

If you're using Microsoft's latest version of its Web browser Internet Explorer – version 3 – (and there are well over a million people already using it), it's worth bearing in mind that there is a bug in the program. Normally, a bug in a program's no big deal, but this one is potentially so important that you should download the official Microsoft fix for it as soon as you can. Apparently the bug means that computer hackers can access a personal computer via the Internet. All they need to do is set up a Web site and wait for a personal computer user to access the pages of the site using the Web browser. While the browser is on the hacker's site the hacker can download the computer's data, and even erase all or part of the information on the computer.

Funnily enough, the bug was found only by sheer chance, when Microsoft asked Princeton University to examine the Web browser's ability to use Java applets. While doing the work the university found the bug and notified Microsoft. The bug fix also clears up a few other (less potentially serious) known bugs.

Money give-away

Domain Name supplier, NetBenefit, is offering a rebate to all its customers who registered a UK Domain with the company during the month of August 1996. NetBenefit is the first company to respond to the decision from Nominet, the Domain Names administrative body in the UK, to give an additional 50% rebate on the registration fees for all UK Domain Names registered with Nominet in August.

Nominet charges £100 for two years registration for non-members and £60 for members. As a founder member company, NetBenefit qualifies for this discount and, unlike some other members, already pass on the entire discount by charging £60 to its customers.

Contact: NetBenefit, Tel: (0171) 336 6777.

Site Survey
The month's destinations
See page 70/71 for this month's destinations

PigMail

Macintosh Internet surfers might like to investigate a very cool e-mailing application designed for pen-friendships. It's particularly suitable for school use, where groups of students can use it as a database of worldwide pen-friends, although there's nothing to stop individuals using it too. Basically, each user has a directory of other users of PigMail worldwide. You find individual users by locating them on a world map and zooming into areas, countries, and habitats until you locate someone you'd like to get in touch with.

You can update your own database by downloading the latest update from the PigMail site, so that you can be kept up-to-date with new users and features. It's actually so good that, because it sits transparently on top of your Internet connection, you can in fact use it to manage all your e-mail, rather than using your old e-mail program. If you're lucky enough to have an Internet account with one of the many Internet service providers who provide multiple mailboxes, PigMail's best use would probably be to manage just one mailbox. That way, the kids (of whatever age) could use it alongside the main mailbox.

It's available for free download from <http://www.cyberpuppy.com/>, and is a real treat to use.

Better e-mail



The world's best e-mail program, Eudora, just got better with the release of version 3. While it does merit a full number increase from version 2 to version 3 because of its numerous new features, it's still the same basic old interface of mailboxes and filters to sort your mail, but it now includes a customisable toolbar which provides easy and quick access to your favourite functions.

Styled text to the text/enriched MIME standard is now supported, so you can stylise your e-mails now and receive stylised e-mails from other users of e-mail programs which support the standard. Styles supported in the standard include, bold, italic, underline, aligning, size (to one of five relative sizes),

margin indenting, colour (black, red, green, blue, yellow, brown), and font.


If you insert a URL, or if you receive an e-mail with a URL in, it's automatically highlighted by Eudora, provided it's prefixed and suffixed in the now-standard way by less than (<) and greater than (>) signs. Double-clicking a URL opens an accompanying associated program such as a Web browser, ftp, gopher or finger program to do what you want.

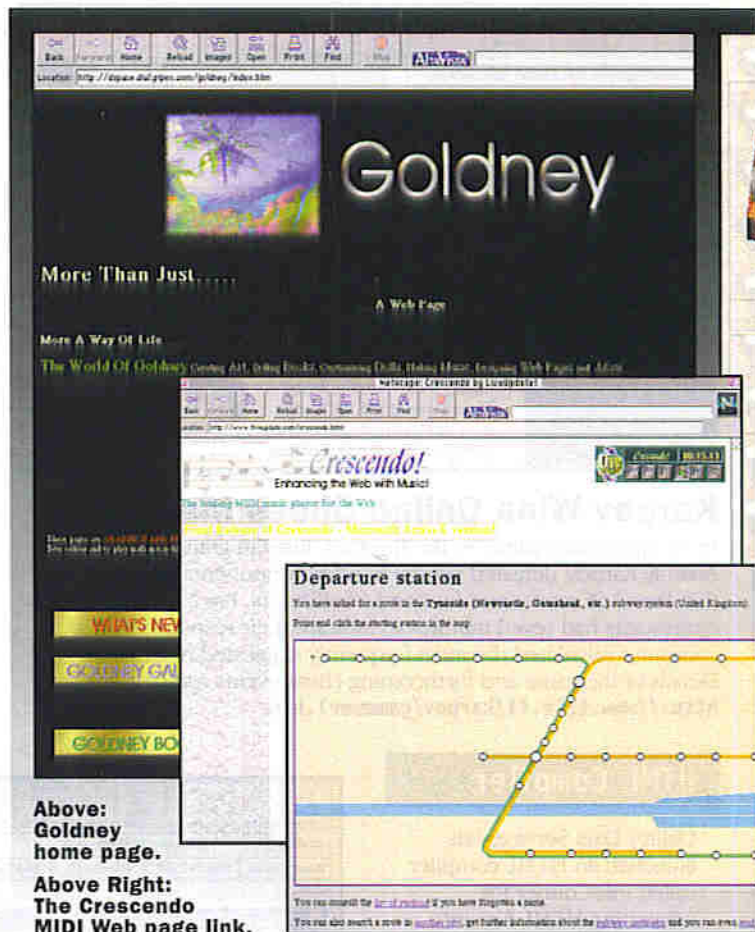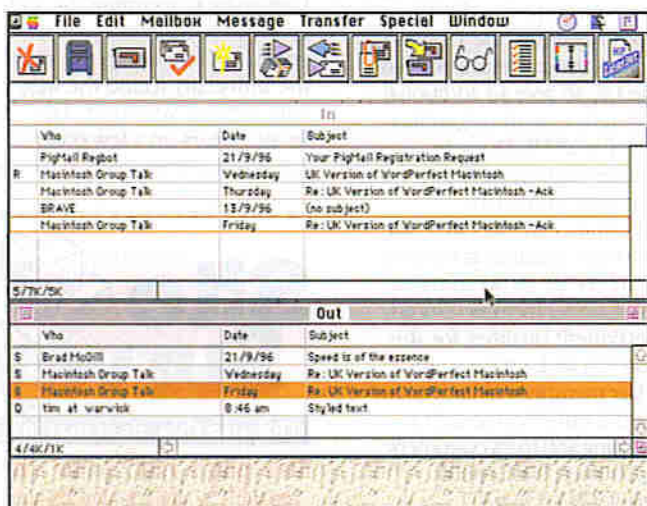Finally, the last of the new features worthy of note here are the new-found ability to drag-and-drop messages between mailboxes, and proper drag-and-drop text editing support. All-in-all, Eudora version 3 is a program you really must check out, if you haven't already.



Above: Goldney home page.

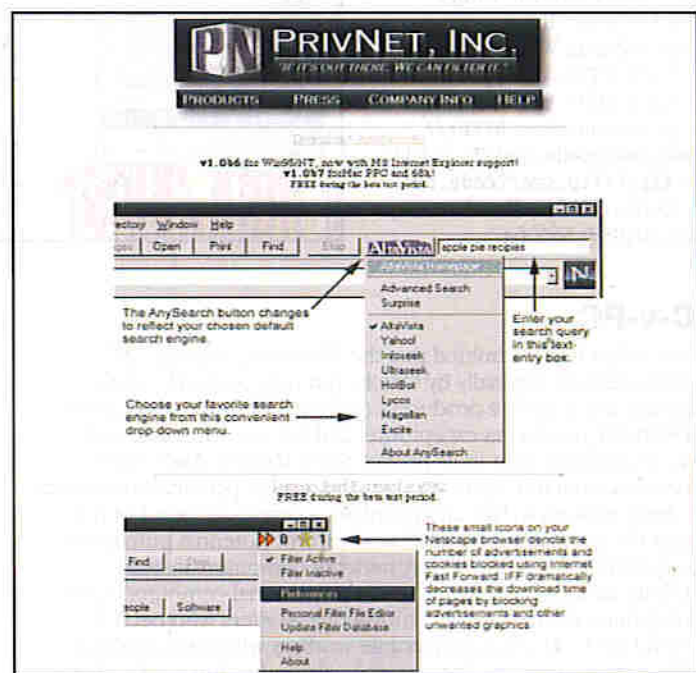Above Right: The Crescendo MIDI Web page link.



Accessing Search Engines

If you use your Web browser to access search engines on the World Wide Web, which from time-to-time most of us do, then AnySearch is of interest. AnySearch is a small add-on to Netscape Navigator which adds an extra button and text entry field so that you can instantly search your favourite search engine. Whatever text you enter into the field is used directly by the search engine, so it's easy to either type in what you want to search for, or copy and paste text from a page already displayed in the Web browser window.

AnySearch is in beta testing phase, and you can download a free copy (Mac or Windows) for installation in your Web browser from <http://www.privnet.com>. If you use search engines at all, AnySearch is a cool utility.

Site Survey



The month's destinations

The month's destinations. If you travel the world, or even to your local city, maps of underground railway networks are a boon. Check out the subway navigator at <http://metro.jussieu.fr:10001/bin/cities/english>, where you'll be able to skip to station lists and maps from subway networks around the world, and create your personalised route to your travel destination.

Download Crescendo from <http://www.liveupdate.com/crescendo.html> and install it as a plug-in to your Web browser, and you can be listening to

live MIDI created music over the Web. Crescendo allows MIDI musicians to link Web pages to MIDI files, and the plug-in lets Web browsers play the music. A cool site using Crescendo is: The Way of Goldney, at <http://dSPACE.dial.pipex.com/goldney/>, where you'll even find a musician who can create MIDI files directly for you.

Finally, for a giggle, go to LaughWEB at http://world.std.com/~joeshmoe/laughweb/tweb_ns.html. Here, you can find jokes galore. Did you hear the one about...

Above: The LaughWEB home page. Left: Subway navigator destination page.

Project Ratings

Projects presented in this issue are rated on a 1 to 5 for ease or difficulty of construction to help you decide whether it is within your construction capabilities before you undertake the project. The ratings are as follows:

- PROJECT RATING 1** Simple to build and understand and suitable for absolute beginners. Basic of tools required (e.g., soldering, side cutters, pliers, wire strippers, and screwdriver). Test gear not required and no setting-up needed.
- PROJECT RATING 2** Easy to build, but not suitable for absolute beginners. Some test gear (e.g., multimeter) may be required, and may also need setting-up or testing.
- PROJECT RATING 3** Average. Some skill in construction or more extensive setting-up required.
- PROJECT RATING 4** Advanced. Fairly high level of skill in construction, specialised test gear or setting-up may be required.
- PROJECT RATING 5** Complex. High level of skill in construction, specialised test gear may be required. Construction may involve complex wiring. Recommended for skilled constructors only.

Ordering Information

Kits, components and products stocked at Maplin can be easily obtained in a number of ways:

- 1 Visit your local Maplin store, where you will find a wide range of electronic products. If you do not know where your nearest store is, telephone (01702) 554002. To avoid disappointment when intending to purchase products from a Maplin store, customers are advised to check availability before travelling any distance;
- 2 Write your order on the form printed in this issue and send it to Maplin Electronics PLC, P.O. Box 777, Rayleigh, Essex, S56 8LU. Payment can be made using Cheque, Postal Order, or Credit Card;
- 3 Telephone your order, call the Maplin Electronics Credit Card Hotline on (01702) 554000;
- 4 If you have a personal computer equipped with a MODEM, dial up Maplin's 24-hour on-line database and ordering service, CashTel. CashTel supports 300-, 1200- and 2400-baud MODEMs using CCITT tones. The format is 8 data bits, 1 stop bit, no parity, full duplex with Xon/Xoff handshaking. All existing customers with a Maplin customer number can access the system by simply dialling (01702) 552941. If you do not have a customer number, telephone (01702) 554002 and we will happily issue you with one. Payment can be made by credit card;
- 5 If you have a tone dial (DTMF) telephone or a pocket tone dialler, you can access our computer system and place your orders directly onto the Maplin computer 24 hours a day by simply dialling (01702) 556751. You will need a Maplin customer number and a personal identification number (PIN) to access the system;
- 6 Overseas customers can place orders through Maplin Export, P.O. Box 777, Rayleigh, Essex S56 8LU, England; telephone +44 1702 554000 Ext. 376, 327 or 351; Fax +44 1702 554001. Full details of all the methods of ordering from Maplin can be found in the current Maplin Catalogue.

Internet

You can contact Maplin Electronics via e-mail at recipient@maplin.co.uk or visit the Maplin Web site at <http://www.maplin.co.uk>.

Prices

Prices of products and services available from Maplin shown in this issue, include VAT at 17.5% (except items marked NV which are rated at 0%). Prices are valid until 28th February 1997 (errors and omissions excluded). Prices shown do not include mail order postage and handling charges. Please add £2.95 to all UK orders under £30.00. Orders over £30.00 and MPS Account Holding customers are exempt from carriage charges.

Technical Enquires

If you have a technical enquiry relating to Maplin projects, components and products featured in Electronics and Beyond, the Technical Sales Dept. may be able to help. You can obtain help in several ways:

- 1 Over the phone, telephone (01702) 556001 between 9.00am and 5.30pm Monday to Friday, except public holidays;
- 2 By sending a facsimile, Fax (01702) 554001;
- 3 Or by writing to Technical Sales, Maplin Electronics PLC, P.O. Box 777, Rayleigh, Essex, S56 8LU. Don't forget to include a stamped self-addressed envelope if you want a written reply! Technical Sales are unable to answer enquiries relating to third-party products or components which are not stocked by Maplin.

Maplin 'Get You Working' Service

If you get completely stuck with your project and you are unable to get it working, take advantage of the Maplin 'Get You Working' Service. This service is available for all Maplin kits and projects with the exception of: 'Data Files'; projects not built on Maplin ready etched PCBs; projects built with the majority of components not supplied by Maplin; Circuit Maker ideas; Mini-Circuits or other similar 'building block' and 'application' circuits. To take advantage of the service return the complete kit to: Returns Department, Maplin Electronics PLC, P.O. Box 777, Rayleigh, Essex, S56 8LU. Enclose a cheque or Postal Order for the servicing cost (minimum £17) as indicated in the current Maplin Catalogue. If the fault is due to any error on our part, the project will be repaired free of charge. If the fault is due to any error on your part, you will be charged the standard servicing cost, plus parts.

ELECTRONICS and Beyond

Test Pattern Generator

Ideal for TV experimenters and repair engineers alike, this 'plug in and go' project enables the creation of a variety of patterns to be displayed on any domestic TV set.

On-Guard

Protect your valued possessions from the light-fingered brigade with this security project, which features an entry/exit delay and a loop cable which can be threaded through vulnerable contents within a room.

Educational Supplement

Another great assortment of entertaining and easy-to-make projects and essential electronics information aimed at the novice instructor.

next issue

PLUS Digital Audio Broadcasting by Ian Poole investigates the revolutionary technology set to transform radio listening into a CD-quality audio experience, with advanced station tuning for added user friendliness.

Eureka from Douglas Clarkson describes the European REcoverable Carrier, a reusable scientific space platform, from which out-of-this-world experiments can be conducted.

The opening episode of a new 4-part series, Audio Delay-line Systems by Ray Marston, explains audio delay line principles.

Touch Key Technology by Tony Ellis continues to demonstrate applications for the new ultra-high security electronic key lock systems, with circuit examples.

Synchronous Network Architecture and Internetworks from Frank Booty guides us around the most popular protocol on Wide Area Network (WAN) technology.

What's in a Name? is a new series from Greg Grant, looking at how some of the more (and less) familiar names associated with the scientific world arose.

Part 3 of PIC Programming by Stephen Waddington focuses on some of the special features and I/O capabilities of the versatile PIC16C84 microcontroller.

Issue 109 on sale Friday 6th December

BRITAIN'S BEST MAGAZINE FOR ELECTRONICS

TECHNOLOGY WATCH



with Martin Pipe

This month, I will be reflecting on computing's interconnected past, and what many see as the future. In the first computing era, there were mainframes. These colossal, highly expensive and inspirational machines, with their seemingly-endless rows of tape and disk drives, in air-conditioned rooms served hundreds of users who would run time-shared programs on terminals located in the building, or in separate facilities via modems. Mainframes, the province of sizeable multinational corporations and governments, had their heyday in the 1960s and 1970s.

In the mid-1970s, minicomputers – typically serving tens of users – became popular, and the second era commenced. Their lower price brought computing within the reach of more companies. The larger organisations would often buy minicomputers for their smaller facilities, and network them to the mainframes. The age of distributed computing had begun. Microcomputers, or personal computers, came into their own in the 1980s – the third era of computing. All users could have control of an individual machine, upon which data and programs specific to their individual requirements could be kept. PCs were cheap enough for small businesses and even members of the public to own.

In the mid-80s, companies began connecting their PCs together to form local area networks, or LANs. Although they recognised the intrinsic values of personal computing, the possibility of sharing files and programs with members of the same department was seen as useful. A LAN could, via the appropriate software, hardware and communications channels, be attached to other LANs, minicomputers and mainframes throughout the organisation. A PC LAN offered all of the advantages of the previous-era minicomputers, but users still had degrees of independence. By this time, the PCs had fallen in price by so much as to make minicomputer-based alternatives appear expensive and outdated.

In the 1960s, the Internet began as a resilient network of data communication channels. Its initial purpose was ensuring that US military computers could remain in touch with each other, even if part of the network should be destroyed by a nuclear strike. In the three decades that followed, the Internet expanded to include educational facilities and other countries. Then it became available to businesses and the public, mostly through Internet service providers. This takes us to the present era of Internet computing. Connect your PC to the Internet, and it becomes another part of this vast global network.

Computer manufacturers saw the ways in which the Internet worked, and recognised that the communication over a LAN adhered to the Internet's packetised protocols. Now companies began connecting their networks to their Internet, using a 'firewall' to prevent unwelcome intruders from gaining unauthorised access to information deemed as confidential. Companies could now send and receive e-mail from customers, suppliers and other 'Internetted' departments, be they down the road or on the next customer.

The NHS has committed itself to just such a system, known as NHSnet – other public bodies could follow suit. Just about every new software release is Internet-enabled; in other words, closely-integrated with the mechanics of Internet access, its applications and data. You could grab

bits of Web page and stuff them in your own documents, initiate dial-up, create e-mails or save a file to a hard-disk located thousands of miles away.

The LAN is now evolving into the 'intranet'. These are effectively localised and independent mini-Internets that can be run within an enterprise. The standard piece of software that is likely to be used is the good old Web browser – mainly because it is so easy to use, and modern versions support e-mail and user-specific plug-in programs to support various types of data. Established LAN hardware – such as Windows PCs, Ethernet cards and file servers – are compatible, making Intranets relatively inexpensive to set up, particularly where modern LANs exist already.

Web-type documents, authored in HTML, would be used to disseminate information around the company. The Web's multimedia potential – pictures, text, sound and video – will allow business communication to be achieved in an unprecedented way. Each corporate Intranet-surfer would normally only be granted access rights, by an administrator, to the information deemed appropriate. This preserves security, but equally importantly prevents employees from burying themselves in information.

Existing computer software, such as we know it, could disappear. Instead of loading a word processor or spreadsheet program from Windows or MacOS, you would download it from the Intranet's file server as an efficiently-coded Java applet. Java is an object-oriented programming language (like C++), and programs written in it can be downloaded and executed under the Web browser; in other words, using the same user interface. Any recent browser will run Java applets, provided that the needed virtual-machine plug-in has been installed. Some specialist programs – such as CAD and DTP – will be too complex to be ported into Java, but the results (drawings and newsletters) could certainly be placed on the Intranet.

Special computers, known as network computers or NCs, have been developed for Intranet use. A consortium, including IBM,

Oracle, Netscape, Apple and JavaSoft (a division of Sun), have been thrashing out the specifications. They are cut-down PCs, likely to be based around RISC processors (from the likes of ARM, Hitachi, etc), and will sell for a low price (around \$500). Apple and IBM, amongst others, have demonstrated prototype NCs. Since the user only needs to run downloadable Java applets, there's no need for local storage. The browser program will be stored on ROM, and appear at boot-up.

Some NCs will offer the facility to connect floppy and hard disks – some users will feel more comfortable holding off-used applets and confidential files locally. The implications of NCs for network hardware is vast. Since programs and multimedia data are flying around, the 10M-bit/s rate offered by Ethernet may be insufficient for commercial applications where time equals money. The newer Fast Ethernet (100M-bit/s) may be more suitable. What's more, the central file server, and its enormous hard disks, need to be mega-fast. Careful management of the information stored there is essential, to avoid the duplication – or indeed accidental deletion – of information. The importance of the file server harks back, ironically, to the first era of the mainframe!

The low price of NCs makes them ideal for domestic use. They won't be seen in the home, however, until the cable companies get their acts together and deliver the promised Ethernet-speed data channels – the 28.8k-bit/s (v.34 standard) currently available over a telephone line will be too slow for the frequent download of applets. Those cable data channels are several orders of magnitude faster, reducing waits to an acceptable level. They could link homes to a local server which caches often-accessed Web sites and newsgroups, as well as holding local information, and applets such as multi-user games, cable 'videotelephony' software and word-processors.

Consumer electronics manufacturers, such as Sony and Philips, will build them into TV sets. Sony has demonstrated a prototype – it was featured in the company's Live '96 extravaganza. Philips, meanwhile, already sells a networkable intelligent monitor as an interactive information display for use at airports, shops, etc. The Net in your set' could soon be with us – and with it the next computing era.

E-mail your comments or suggestions to Martin Pipe at whatnet@ix.compulink.co.uk.



Apple Pippin prototype.

ELECTRONICS

and Beyond

SUBSCRIBER'S SPECIAL OFFERS

SUBSCRIBE TODAY AND QUALIFY FOR THESE AMAZING SAVINGS!

HURRY! OFFERS END 30TH NOVEMBER 1996

Perfect Gifts for Christmas!



Code 51336

CAR CLOCK/CALENDAR

CATALOGUE PRICE £6.99

SUBSCRIBERS' PRICE £4.59

SAVE £2.40

155mm SIDE CUTTERS

CATALOGUE PRICE £3.56

SUBSCRIBERS' PRICE £2.36

SAVE £1.20

Code 51337

MULTI-PURPOSE LANTERN

CATALOGUE PRICE £6.11

SUBSCRIBERS' PRICE £3.99

SAVE £2.12

Code 51335



SUBSCRIBE TODAY
see page 5

UNIVERSAL ADAPTOR

SAVE £1

CATALOGUE PRICE £2.99

SUBSCRIBERS' PRICE £1.99

Code 51332



BABY MONITOR

CATALOGUE PRICE £18.99

SUBSCRIBERS' PRICE £12.49

SAVE £6.50


Code 51334



When ordering any of these special offers which apply only for Subscribers and new Subscribers of *Electronics and Beyond*, please quote your Subscribers' Membership number (telephone Customer Services on 01702 554002 if not sure) and the special order code number. All items are subject to availability. Prices include VAT. Catalogue prices refer to the 1996/7 Maplin MPS Catalogue. Overseas subscribers telephone +44 1702 554000 Ext. 326 for carriage charges. A £2.95 Carriage Charge will apply to all UK orders under £30.00 (MPS Account Holding Customers exempt).

As a fully paid-up subscriber you can use the special Subscriber-only order codes and save up to 34%

Got it in one!

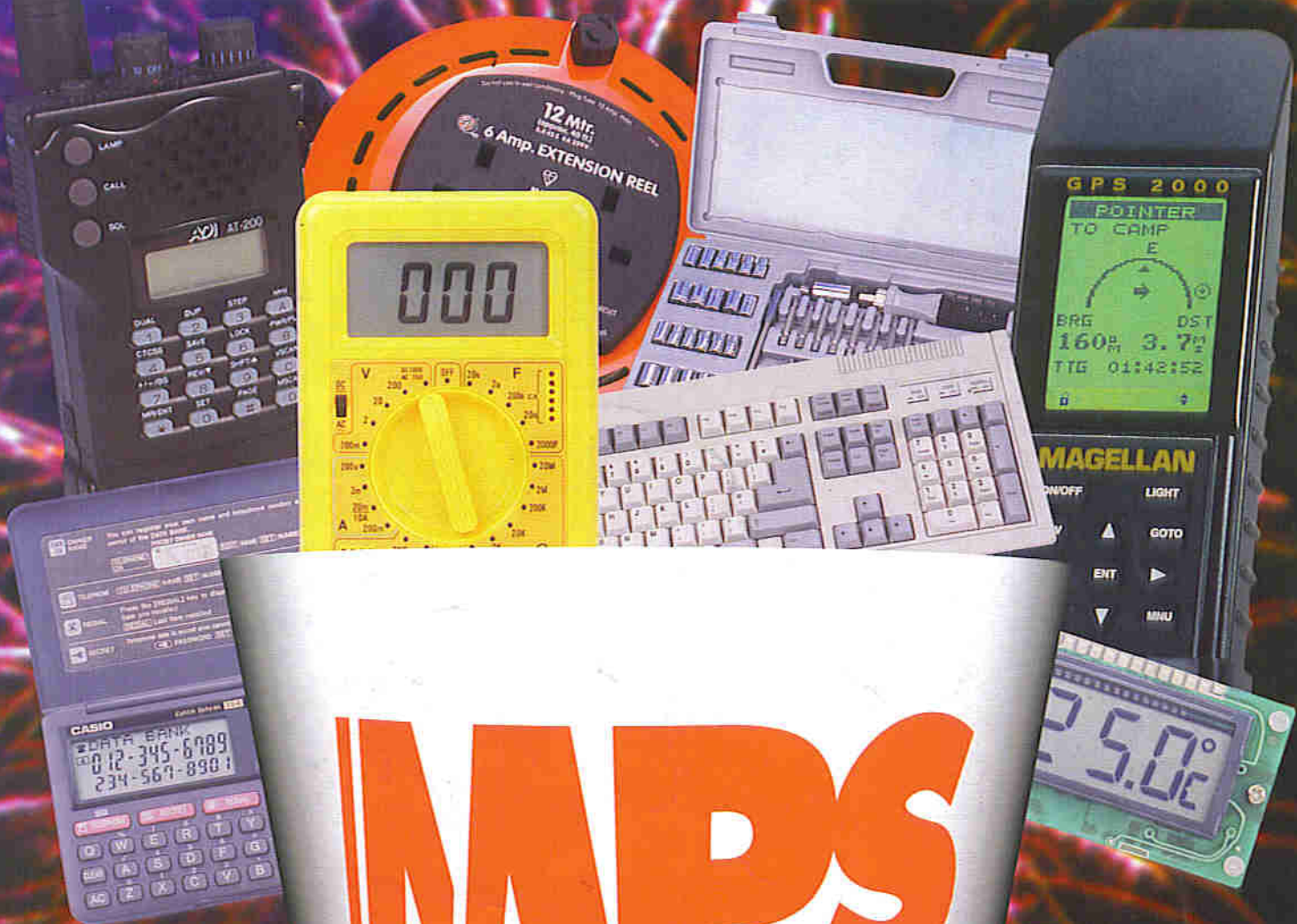

**Britain's
Best-Selling
Electronics
Catalogue**

**Free delivery
on all orders**

Applies to orders over
£30.00 (inclusive of VAT).
Free delivery also applies
on ALL orders for MPS
Business Account customers

**Call in for your
copy at WH SMITH,
John Menzies and
Maplin stores
nationwide.**

MPS

MAPLIN PROFESSIONAL

**THE COMPLETE
CATALOGUE FOR
ELECTRONICS**

1996/7

**Over
17,000
technical
products
for industry
and the
enthusiast**

**On sale now
- only £3.45!**

**Order direct
01702 554000**

Priority reference code: MA013

For overseas orders send £8.45 or
21 IRCs for Airmail in Europe or Surface mail
outside Europe; £16.00 or 37 IRCs for Airmail
outside Europe to Maplin MPS, P.O. Box 777,
Rayleigh, Essex, England SS6 8LU.