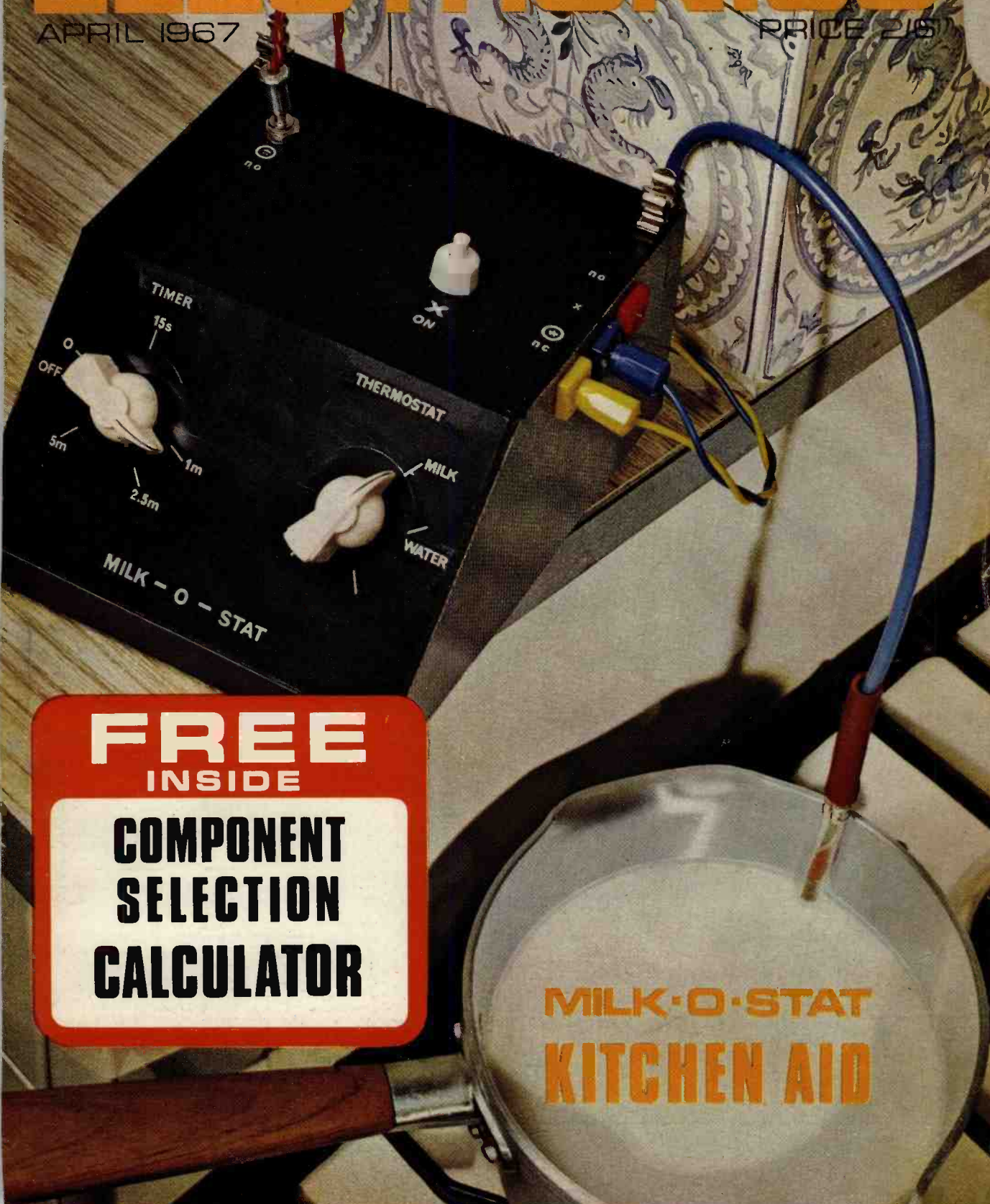


**PRACTICAL**

# **ELECTRONICS**

APRIL 1967

PRICE 21¢



**FREE**  
INSIDE

**COMPONENT  
SELECTION  
CALCULATOR**


**MILK-O-STAT  
KITCHEN AID**

# ADCOLA

PRODUCTS LIMITED  
(Regd. Trade Mark)

SOLDERING EQUIPMENT

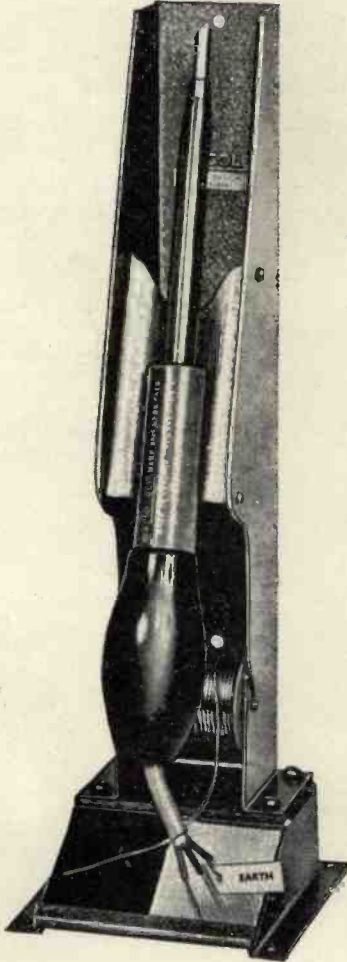for the  
**DISCRIMINATING  
ENTHUSIAST**



ILLUSTRATED:  
L64  $\frac{3}{8}$ " BIT INSTRUMENT IN  
L700 PROTECTIVE SHIELD

APPLY DIRECT TO:

SALES & SERVICE DEPT.  
ADCOLA PRODUCTS LTD.  
ADCOLA HOUSE  
GAUDEN ROAD  
LONDON, S.W.4  
TELEPHONE: MACAULAY 0291/3

# OLRUS ELECTRONICS LTD.

PADDINGTON 1515

9 NORFOLK PLACE (off Praed St.) LONDON, W.2

TRANSISTORS — DIODES — ZENER — VALVES  
FULLY GUARANTEED — FACTORY NEW. S.A.E. FOR FULL LIST.  
P.P. 2/- in £ 1/- min.

2N687 12/8	AR220 7/8	NKT228 0/-	OAZ207 9/8	OC122 15/-	GZ34 10/-
2N1304 8/8	AR231 12/8	NKT225 1/8	OAZ208 8/8	OC139 7/8	PC86 11/-
9N2906 8/8	AR233 30/-	NKT253 8/8	OAZ209 8/8	OC141 12/8	PC88 11/-
2N3819 18/-	BC107 7/8	NKT265 9/8	OAZ210 6/8	OC170 6/-	PC97 7/8
28002 10/8	BC108 5/-	NKT271 5/-	OAZ211 8/8	OC169 5/-	PC99A 6/-
28003 9/8	BC109 7/8	NKT272 5/-	OAZ212 6/8	OC170 6/-	PC99B 11/-
28004 9/8	BCY31 13/8	NKT273 4/-	OAZ213 6/8	OC171 0/-	PC189 11/-
28012 20/-	BFY17 9/8	NKT274 5/-	OAZ222 9/8	OC200 7/8	PCF80 7/-
28012A 25/-	BFY51 8/8	NKT275 5/-	OAZ224	OC201 10/-	PCF86 5/8
28013 20/-	BFY53 7/8	NKT277 5/-	10/-	OC202 13/-	PCF92 7/-
28013A 25/-	BFY10 22/8	NKT278 5/-	OAZ225	OC203 10/8	PCF93 5/8
28017 15/-	BSY27 9/8	NKT279A	10/-	OC204 15/-	PCF94 7/8
28018 17/8	BSY51 7/8	4/-	OAZ242 4/8	OC205 15/-	PCF85 9/-
28103 20/-	BSY53 7/8	NKT304 4/8	OAZ245 4/8	OC206 22/8	PCF86 8/8
28301 12/8	BSY95A	NKT352 5/-	OAZ246 4/8	OC206 22/8	PCF86 8/8
28320 9/-	5/8	NKT403	OAZ247 4/8	OC206 22/8	PCF86 8/8
28322 7/8	BY100 4/8	12/8	OAZ290 8/8	OC206 22/8	PCF86 8/8
28323 10/8	GET7 5/-	NKT404	OAZ291 8/8	OC206 22/8	PCF86 8/8
28324 12/8	GET8 8/-	12/8	OAZ292 9/8	OC206 22/8	PCF86 8/8
28512 18/8	GET16 7/8	NKT453	OC16 20/-	OC206 22/8	PCF86 8/8
28702 15/-	GET20 10/-	12/8	OC19 7/8	OC206 22/8	PCF86 8/8
AC107 10/-	GET88 5/-	NKT452	OC20 15/-	OC206 22/8	PCF86 8/8
AC126 6/8	GET102 8/-	12/8	OC22 10/-	OC206 22/8	PCF86 8/8
AC127 7/8	GET103 4/8	NKT675 8/8	OC23 12/8	OC206 22/8	PCF86 8/8
AC127E 9/8	GET106 8/8	NKT676 8/8	OC24 15/-	OC206 22/8	PCF86 8/8
AC128 8/8	GET106	NKT677 5/-	OC25 9/8	OC206 22/8	PCF86 8/8
AC176 7/8	GET113 5/-	NKT678 6/-	OC26 7/8	OC206 22/8	PCF86 8/8
ACY17 8/8	GET114 4/-	NKT713 7/8	OC28 12/8	OC206 22/8	PCF86 8/8
ACY18 5/8	GET114 4/-	NKT773 8/8	OC29 15/-	OC206 22/8	PCF86 8/8
ACY19 6/8	GET115 9/-	NKT777 8/8	OC35 12/8	OC206 22/8	PCF86 8/8
ACY20 5/-	GET116	NKT0013	OC36 12/8	OC206 22/8	PCF86 8/8
ACY21 5/-	15/-	OA5 4/-	OC31 6/-	OC206 22/8	PCF86 8/8
ACY22 3/8	GET571 5/-	OA7 4/-	OC42 5/-	OC206 22/8	PCF86 8/8
ACY28 4/8	GET872 6/-	OA10 3/-	OC43 9/-	OC206 22/8	PCF86 8/8
AD140 16/-	GET874 5/-	OA47 3/-	OC44 4/-	OC206 22/8	PCF86 8/8
AD149 18/-	GET875 6/-	OA47 3/-	OC44M 5/8	OC206 22/8	PCF86 8/8
AD161 11/-	GET880 9/-	OA73 2/8	OC45 3/8	OC206 22/8	PCF86 8/8
AD162 11/-	GET882 5/-	OA73 2/8	OC45M 4/-	OC206 22/8	PCF86 8/8
ADT140	GET883 5/-	OA79 2/8	OC46 5/8	OC206 22/8	PCF86 8/8
AF102 18/-	GET885 5/-	OA81 2/8	OC70 4/-	OC206 22/8	PCF86 8/8
AF114 8/8	NKT128 6/-	OA85 2/8	OC71 3/8	OC206 22/8	PCF86 8/8
AF115 6/-	NKT142 8/-	OA86 4/-	OC72 5/-	OC206 22/8	PCF86 8/8
AF116 6/8	NKT211 6/-	OA90 2/8	OC73 7/8	OC206 22/8	PCF86 8/8
AF117 5/-	NKT212 5/-	OA91 2/8	OC75 0/-	OC206 22/8	PCF86 8/8
AF118 10/-	NKT213 6/-	OA95 3/8	OC76 5/-	OC206 22/8	PCF86 8/8
AF124 7/8	NKT214 4/-	OA200 3/3	OC77 8/8	OC206 22/8	PCF86 8/8
AF125 6/8	NKT216 7/8	OA202 4/3	OC78 5/-	OC206 22/8	PCF86 8/8
AF126 6/-	NKT217 5/-	OA210 7/8	OC78D 5/-	OC206 22/8	PCF86 8/8
AF127 5/-	NKT218 6/-	OA211 9/8	OC81 5/-	OC206 22/8	PCF86 8/8
AF128 12/8	NKT218 6/-	OAZ200	OC81D 5/-	OC206 22/8	PCF86 8/8
AF129 12/8	NKT221 5/8	OAZ200 11/-	OC81M 5/-	OC206 22/8	PCF86 8/8
AF178 12/8	NKT222 4/-	10/-	OC81D 5/-	OC206 22/8	PCF86 8/8
AF186 17/8	NKT223 6/-	OAZ201	OC81M 5/-	OC206 22/8	PCF86 8/8
AFY19 22/8	NKT224 4/8	OAZ202 8/8	OC81Z 9/-	OC206 22/8	PCF86 8/8
AFZ11 17/-	NKT225 3/8	OAZ203 8/8	OC82 5/-	OC206 22/8	PCF86 8/8
AFZ12 12/8	NKT226	OAZ204 8/8	OC82D 5/-	OC206 22/8	PCF86 8/8
ASV26 6/8	10/-	OAZ205 8/8	OC83 5/-	OC206 22/8	PCF86 8/8
ASV28 6/8	NKT227 5/8	OAZ206 8/8	OC84 6/-	OC206 22/8	PCF86 8/8

## SCR-THYRISTORS

CRS105 1A 50PIV 7/6;	CRS110 1A 100PIV 7/6;	CRS120 1A 200PIV 12/6;	CRS130 1A 300PIV 15/-;
CRS135 1A 350PIV 16/-;	CRS140 1A 400PIV 17/6;	Unijunction 15/-;	CRS305 3A 50PIV 8/6;
CRS310 3A 100PIV 10/-;	CRS320 3A 200PIV 13/6;	CRS330 3A 300PIV 17/6;	CRS350 3A 350PIV 18/6;
CRS340 3A 400PIV 20/-;	CR74 7A 400PIV 25/-.		

## FIELD EFFECT TRANSISTOR

2N3819 18/-.	
Moulded Reed Switch	14/-
Moulded Magnet	5/-
Miniature Neon Lamp	1/3
Mains Panel Neon	3/-

## CONTIL CASES 21SWG steel.

Smart electric blue finish with white panel—outside dimensions:	
755 45/6	16127 98/6
867 47/6	161275 139/6 P.P.
975 47/6	191010 133/- inc.
1277 53/-	191010D187/-

## LIGHT SENSITIVE SWITCH

Kit 1 ORP12 Photocell-relay Transistor-circuit	27/6
Kit 2 As above—Mains operation — Transformer rectifier	47/6
Kit 3 As Kit 2+Lens+Cast Alu. box+Exciter lamp. Folded beam operation	99/6 P.P. inc.

## TUNNEL DIODES

	Imax	IP	IP/IV	VP	
JK9A	10ma	1	4	45mv	22/6
JK10A	50ma	5	4	50mv	15/-
JK10B	50ma	5	4	50mv	15/-
JK11A	150ma	15	4	55mv	12/6
JK19A	10ma	1	6	55mv	22/6
JK20A	50ma	5	6	55mv	17/6
JK21A	150ma	15	6	55mv	12/6
AEY11	50ma	5	7	55mv	19/6

## TRANSFORMERS

230v Prim. 6-10-15-18-30v 2A	32/-
230v Prim. 6-10-18v 1A	22/-
	+ P.P. 5/-

## EXPLORER KIT AM/FM VHF RECEIVER

Punched case and panel—2ADT 140 + 20C71 Transistors—2 holders	£2 19 6 P.P. inc.
---	-------------------

## SINCLAIR

Z12 int. 12w ampl. and preamp. built	89/6
PZ3 trans. mains power unit built	79/6
Micromatic built	79/6
Micromatic kit	59/6
Micro FM kit	£5 19 6
Stereo 25 preamp. and control unit built	£9 19 6 P.P. inc.

# LASKY'S RADIO

## For the Finest Value and Service to HOME CONSTRUCTORS & ELECTRONICS ENTHUSIASTS

We consider our construction parcels to be the finest value on the home constructor market. If on receipt you feel not competent to build the set, you may return it as received within 7 days, when the sum paid will be refunded less postage.

### TAPE RECORDERS

#### MAGNAVOX 363 DECKS

The very latest 8 speed model—11, 31, 71 L.P.s. available with either 1 track or 2 track head. Features include: pause control; digital counter; fast forward and rewind; new 4 pole fully screened induction motor; interlocking keys. Size of top plate: 13 1/2 x 11 x 5 1/2 in. deep below unit plate. For 200/250 v. A.C. mains, 50 c.p.s. operation. New unused and fully guaranteed.

LASKY'S PRICE 1 track model £10.10.0

LASKY'S PRICE 2 track model £13.9.6

Carriage and Packing 7/6 extra.

SPECIAL FOR OVERSEAS CUSTOMERS — the new Magnavox-Collaro 363 Deck for 110/125 v. 50 or 60 c.p.s. mains now available, prices as above. Post to any part of the world 35/-.

#### MARTIN RECORD/REPLAY TAPE AMPS.

Latest models now available from stock—for use with the Magnavox 363 Tape Deck 1/2 track model ..... LASKY'S PRICE £14.19.6

1/2 track model ..... LASKY'S PRICE £15.19.6 Carriage and Packing 4/6 extra

Optional extra: Control panel escutcheon to take deck and amplifier controls. LASKY'S PRICE 12/6. Post and Packing 2/6.

### SPECIAL INTEREST ITEMS!

#### SPECIAL PURCHASE—UHF/VHF T.V. TUNERS

Well known British makers' surplus stocks. Now available for the first time to the Home Constructor. Add 2/6 Post and Packing on each.

##### VALVE UHF MODEL (Illustrated)

In metal case size 4 x 6 x 1 1/2 in. Fully tunable—complete with PCC88 and PCC88 valves. LASKY'S PRICE 29/6. Without valves 12/6

TRANSISTORISED UHF MINIATURE MODEL 1 Shielded metal case only 3 1/2 x 1 1/2 x 3 in. Fully tunable—complete with two AF 139 transistors. LASKY'S PRICE 39/6

##### TRANSISTORISED UHF MODEL 2

Metal case size 3 1/2 (plus spindle) x 2 1/2 x 1 1/2 in. Fully tunable with slow motion drive. Comp. with two AP186 transistors and lens. LASKY'S PRICE 25/6

##### TRANSISTORISED VHF TUNER

Sub-miniature turret type fitted with 12 sets of coils and 3 Mullard AF102 transistors. In metal case size 3 x 1 1/2 x 2 1/2 in. LASKY'S PRICE 37/6

Add 2/6 Post and Packing on each.

#### MAKERS' SURPLUS TELEVISION IF AMPLIFIERS

38 Mc/s. Contains a large number of components, 1F transformers, resistors, capacitors, etc., and the following valves: 2XPCF80, 1xEB91, EF80, EF182 and EF184. Overall size 1 1/2 x 3 1/2 x 4" deep. Ideal for servicemen and experimenters. This 1F amp. when used with the Valve model UHF Tuner (above) provides a suitable conversion for B.B.C.2. Circuit supplied.

LASKY'S PRICE 29/6 Post 2/6

#### SPECIAL PACKAGE OFFER

Free standing table cabinet, size 17 1/2 x 9 x 6 1/2 in., finished in medium Mahogany. Scale marked 21 to 68 (UHF band). Designed to accept the above 1F Amplifier with space for a Valve UHF Tuner. Cabinet only 27/6 Post 3/6



Special Package Offer 1F Amplifier, UHF Tuner with valves and Table Cabinet.

PACKAGE PRICE 59/6 Post 6/-

#### WATER TEMPERATURE THERMOSTATS

British made—orig. for use in high quality washing machine, range adjustable between 114°F and 230°F. Rating 200/250 V.A.C., 20 amps (also D.C. up to 125 V.A.). Size 2 1/2 x 1 1/2 x 1 1/2 in. with 18 in. capillary tube and 6 in. bulb. Single hole fixing. 3/16 in. spindle.

LASKY'S PRICE 15/- Post 2/-

207 EDGWARE ROAD, LONDON, W.2 Tel: PAD 3271  
118 EDGWARE ROAD, LONDON, W.2 Tel: PAD 9789  
33 TOTTENHAM CT. ROAD, LONDON, W.1 Tel: MUS 2605

The above branches open all day Saturday. Early closing Thursday.


Please address all Mail Orders and Correspondence to 3-15 Cavell Street, Tower Hamlets, London, E.1. Tel.: STE 4821/2

## LASKY'S FOR SPEEDY MAIL ORDER SERVICE

### CONSTRUCTORS BARGAINS

#### THE SKYROVER

De Luxe

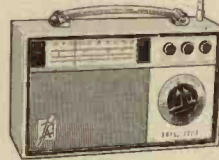


7 transistor plus 2 diode superhet, 6 waveband portable receiver covering the full Medium Waveband and Short Waveband 31-94M and also 4 separate switched bandspread ranges, 13M., 16M., 19M. and 23M., with Band Spread Tuning for accurate Station selection. The coil pack and tuning heart is factory assembled, and tested. Uses 4 U2 batteries. 6 in. Ceramic/Magnet P.M. Speaker. Telescope and Ferrite Rod Aerial. Tone Circuit, wood cabinet, size 11 1/2 x 6 1/2 x 3 in. covered with washable material, plastic trim and handle. Car aerial socket fitted.

Can be built for £8.19.6 Post H.P. Terms: 60/- deposit and 11 monthly payments of 12/9. Total H.P.P. £10.0.3. Data 2/8 extra: refunded if you purchase parcel. All parts avail. sep. Four U2 batt. 3/4 A simple additional circuit provides cover of the 1100/1950M Long Waveband. All components with construction data.

Only 10/- extra Post Free.
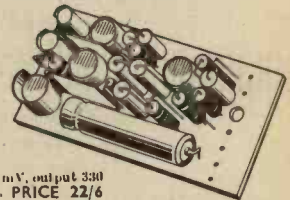
#### NEW—LASKY'S MINIATURE TRANSISTOR AMPLIFIER MODULES

Incorporating the very latest circuitry to provide high sensitivity and good quality in conjunction with extreme small size and compactness. High quality Newmarket transistors used throughout. All designed to operate on 9v. miniature battery. Add 1/- on each for post & packing



TYPE LRPC 1. 3 transistor. Input sens. 50 mV., output 150 mW. output imp. 40 Ω, size 2 1/2 x 1 1/2 in. PRICE 27/6  
TYPE LRPC 2. 5 transistor. Input sens. 1mV. output 330 mW. output imp. 15 Ω, size 2 1/2 x 1 1/2 in. PRICE 22/6  
TYPE LRPC 4. 5 transistor. Input sens. 150 mV. output 330 mV. output imp. 15 Ω, size 2 1/2 x 1 1/2 in. PRICE 22/6  
TYPE LRPC 5. 6 transistor. Input sens. 8mV. output 3W. output imp. 3 Ω, size 5 1/2 x 1 1/2 in. PRICE 59/6  
TYPE LRPC 6. Tape record/play back amp. (for use with self oscillating erase head). Output 750mW. output imp. 8 Ω. Size 4 1/2 x 2 x 1 1/2 in. LASKY'S PRICE 39/6

#### FULLY ENCAPSULATED MODULES

Special function modules — all one size 1 1/2 x 1 x 1 1/2 in. Complete with detailed function and installation instructions. Send S.A.E. for data.

TYPE PA-1. Public address amp. for use with carbon, crystal or Dynamic microphones. 3 Ω output imp. PRICE 30/-  
TYPE GR-1. Gramophone amplifier provides sufficient power to fill average room. 3 Ω output imp. PRICE 30/-  
TYPE CO-1. Morse code practice oscillator for use with morse key and 3 Ω speaker. PRICE 20/-  
TYPE MT-1. Metronome module provides audible and visual beat from 30 to 240 beats per minute (for use with 3 Ω speaker or ind. lamp) PRICE 22/6

#### SINCLAIR SUPER MINIATURE KITS

We stock the complete range. Write for details of package deals.

THE MICRO-6 miniature radio only 1 1/2 x 1 1/2 x 1 1/2 in. £2 19 6  
THE MICRO-FM. (tuner/receiver) £5 19 6  
THE X-20 20 watt P.W.M. amplifier Kit £7.19.6. Fully built £9 19 6  
STEREO 25 pre-amp control unit fully built £9 19 6  
THE Z-12 12 watt amplifier and pre-amplifier. Fully built and tested £4 9 6  
PZ-3 power pack for Z-12 £3 19 6

#### VEROBOARD — High grade laminated board with copper strips bonded to it and pierced with holes.

Boards	Accessories
42/1503 2 1/2 x 5 in. ....	3/1 Terminal pins — pkt. of 50
43/1504 2 1/2 x 3 1/2 in. ....	3/3 Spot face cutter tool
45/1507 3 1/2 x 5 in. ....	5/6 1 in. inserting tool
46/1508 3 1/2 x 3 1/2 in. ....	3/11 Post 6d. per item extra.
44/1505 3 1/2 x 17 in. ....	15/6 Orders of 10/- and over post free.

#### TRANSISTORS

ALL BRAND NEW AND GUARANTEED  
GET 81, GET 85, GET 86 2/8; 873A, 874P 3/6; OC45, OC71, OC81D 4/6; OC 44, OC 70, OC 76, OC 81 5/6; pair (10/8); AF 117, OC 200 6/8; OC 42, OC 43, OC 73, OC 82B 7/6; OC 201, OC 204 15/-; OC 205, OC 206 19/8; OC28 24/6; OC 75 8/-.

#### TRANSFILTERS By BRUSH CRYSTAL CO. Available from stock.

TO—01D 465 kc/s. ± 2 kc/s.	TO—02D 470 kc/s. ± 1 kc/s.	9/6 EACH
TO—01B 470 kc/s. ± 2 kc/s.	TF—01B 465 kc/s. ± 3 kc/s.	Post 6d.
TO—02B 465 kc/s. ± 1 kc/s.	TF—01D 470 kc/s. ± 2 kc/s.	

42 TOTTENHAM CT. ROAD, LONDON, W.1 Tel: 01-580 2573  
152/3 FLEET STREET, LONDON, E.C.4 Tel: FLE 2833

Both open all day Thursday. Early closing Saturday.

## FULLY GUARANTEED INDIVIDUALLY PACKED VALVES

AC/HL	4/6	EDC41	8/6	EL37	17/6
ACP4	5/6	EEC80	5/6	EL38	17/6
ACOPEN	5/6	EBF80	6/6	EL41	8/6
AL60	5/6	EBF83	7/6	EL42	8/6
AR8	5/6	EBF89	6/6	EL50	8/6
ARP3	3/6	EEL31	20/6	EL81	8/6
ARP12	2/6	EC52	4/6	EL83	8/6
ARP24	10/6	EC63	12/6	EL84	4/3
ATP4	2/3	EC70	4/6	EL86	7/6
ATP7	5/6	EC90	2/6	EL91	4/6
AU7	55/6	EC91	3/6	EL95	5/6
AZ1	9/6	ECR81	4/6	EM80	6/6
B6H	15/6	ECC82	5/6	EM81	7/6
BD78	40/6	ECX83	6/6	EM84	6/3
BL43	10/6	ECC84	5/6	EN31	10/6
B84	8/6	ECC85	8/6	EN174	80/6
B85	20/6	ECX81	4/6	EP208	6/6
B864	47/6	ECC180	9/6	EY51	5/6
B2134	18/6	ECC80	7/6	EY86	6/6
CC3L	2/6	ECC82	7/6	EY91	3/6
CF23	10/6	ECH42	9/6	EZ40	6/6
CL3	3/6	ECH81	5/6	EZ41	6/6
CY31	6/6	ECH83	7/6	EZ80	5/6
D1	1/6	ECL80	6/6	EZ81	4/6
D41	3/3	ECL82	6/3	F/6057	5/6
D61	6/6	ECL83	10/6	F/6061	5/6
D77	3/3	ECL86	9/6	F/6063	4/6
DA20	12/6	EK36	3/6	FW4500	8/6
DAF96	6/6	EK57A	7/6	FW4800	8/6
DD41	4/6	EF40	4/6	G12360	22/6
DF73	5/6	EF41	6/6	G50201	5/6
DF91	3/6	EF50	2/6	G4	45/6
DF92	3/6	EF52	6/6	GZ32	10/6
DF96	6/6	EF53	4/6	GZ34	10/6
DH63	5/6	EF55	8/6	HK54	22/6
DK66	5/6	EF71	7/6	HL2K	2/6
DL92	4/6	EF72	5/6	HL23	6/6
DL93	4/6	EF73	5/6	HL23DD	5/6
DL94	5/6	EF74	4/6	HL41	4/6
DL96	7/6	EF80	5/6	MVR2	9/6
DL810	8/6	EF85	4/6	K3A	30/6
DY66	7/6	EF86	6/6	KT32	8/6
E80F	23/6	EF89	5/6	KT33C	6/6
E88CC	12/6	EF91	3/6	KT44	5/6
E90CC	10/6	EF92	2/6	KT63	4/6
EA60	1/6	EF95	5/6	KT65	18/6
EA73	7/6	EF95	5/6	KT67	25/6
EAB80	5/6	EF183	6/6	KT76	8/6
EAC91	3/6	EF184	6/6	KT88	22/6
EA432	8/6	EH90	7/6	KTW61	4/6
EB34	1/6	EL32	3/6	KTW63	5/6
EB91	3/6	EL34	10/6	KTP1	6/6
EB33	6/6	EL35	5/6	KTZ63	5/6

MH4	5/6	811E12	10/6	UF89	6/6	ID8GT	8/6	3V4	5/9	6AM5	2/8	6K8M	8/6	12AU7	5/6	50CD6G	
ML0	6/6	8P2	8/6	UL41	7/6	IE7G	7/6	4C27	35/6	6AM6	4/6	6L5G	6/6	12AV6	5/6		27/8
N78	15/6	8P41	1/6	UL84	5/6	IF2	3/6	4D1	4/6	6AQ5	7/6	6L6A	7/6	12AX7	6/6	50LGGT	8/6
NE17	7/6	8P61	4/6	UU5	7/6	IIG6T	6/6	5A173G	5/6	6AQ5W	9/6	6L7G	4/6	12AY7	10/6	33A	7/6
OA2	5/9	8P210	3/6	UUP	8/6	ILA	2/8	5A174G	5/6	6AB6	4/6	6L84	3/6	12BA6	5/6	57	6/6
OB2	6/6	T41	12/6	UY21	7/6	ILA6	6/6	5B251M		6AB6W	9/6	6L8D20	5/9	12BE6	7/6	58	6/6
OB3	7/6	TY22	5/6	UY85	5/6	ILC6	7/6		40/6	6AB7G	15/6	6N7	6/6	12BH7	7/6	59	6/6
OC3	5/6	TY25	15/6	UY93	5/6	ILH	4/6	5B253M		6AT6	6/6	6N7G	5/9	12C8	3/6	75	5/6
OD1	5/6	TY27	5/6	VP23	3/6	ILH1	3/6		15/6	6B2	6/6	6P25	12/6	12CH	2/6	76	5/6
OZ4A	5/6	TT15	35/6	VR99	5/6	IN21B	6/6	5B254M		6AX4	8/6	6Q4	6/6	12C8GT	5/6	77	6/6
PC86	9/6	TT18	35/6	VR105/30		IN43	4/6			6B4G	17/6	6R7	5/6	12J7GT	6/6	78	5/6
PC88	9/6	TZ20	16/6		1R4	1R4	5/6	5B255M		6B7	6/6	6S47	7/6	12J7GT	2/6	80	5/6
PC97	7/8	U81	8/6	VR150/36		1R5	3/8		35/6	6B8G	2/6	6S47GT	6/6	12K8M	10/6	81	9/6
PC900	12/6	V12/14	8/6		1R4	1R4	5/6	3R40Y	9/6	6BA6	5/6	6K7GT	9/6	12Q7GT	3/3	82	8/6
PC94	5/6	V18	6/6		1R5	4/6	3R4	7/6		6BA7	5/6	6G87	7/6	12R47	4/6	84	8/6
PC98	10/6	V18	6/6		1R4	3/6	014G	4/6		6B6	6/6	6R5MT	5/6	12S67	3/6	85A2	8/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6B16	7/6	6R5MT	5/6	12T7GT	3/6	307A	5/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6B37	7/6	6H7	3/6	12M87	3/6	313C	25/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6BR7	9/6	6J37	5/6	12S37	5/6	350B	8/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6BW6	7/6	6J37GT	5/6	12K87	5/6	357A	70/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C4	2/6	6K7Y	6/6	12R7GT59	368A8	30/6	
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C5G	2/6	6K87	5/6	12RH7	5/6	393A	27/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6CGGT	6/6	6L7GT	5/6	12Y4	2/6	446A	3/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C9	4/6	6N7	3/6	14L7	7/6	6080	22/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C9G	3/6	6S27GT	6/6	1487	18/6	6146	25/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C9L	3/6	6S87	2/6	15D2	6/6	703A	30/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C16	4/6	6U4GT	9/6	20P4	12/6	705A	10/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C16	9/6	6V6G	5/6	21B6	7/6	715B	60/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6C4	12/6	6V6GT	7/6	25L4GT	5/6	717A	3/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6D6	3/6	6VM	6/6	25Y	6/6	724A	15/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6E4	3/6	6X4	3/6	25Z4G	6/6	757	18/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F5G	5/3	6X5G	5/3	25Z5	7/6	801	6/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F5GT	5/3	6X5GT	5/3	25Z6GT	8/6	803	22/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F6G	4/6	6Y6G	6/6	28D7	6/6	807	8/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6G7	6/6	6Z0L2	8/6	30	5/6	808	8/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6H7	5/6	6Z4	5/6	30C15	10/6	813	75/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6I7	5/6	6Z7	7/6	30C18	11/6	846A	3/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F12	4/6	7B7	7/6	30F5	8/6	829B	50/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F12	4/6	7C9	10/6	30F5	8/6	829B	50/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F13	5/6	7C8	7/6	30FL1	10/6	832	15/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F32	4/6	7C7	6/6	30FL12	19/6	832A	45/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6F33	20/6	7H7	7/6	30FL13	6/6	866A	14/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6GG6	2/6	7Q7	6/6	30FL14	13/6	884	10/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6H6	10/6	7V7	8/6	30L15	15/6	954	4/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6H7A	10/6	7Y4	8/6	30P2	8/6	954	2/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6H8	10/6	7Y4	8/6	30P19	13/6	956	2/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6I5	6/6	7Z4	4/6	30P19	13/6	956	2/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6J5G	2/6	8D2	2/6	30PL1	15/6	957	5/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6J6	3/6	8D2	2/6	30PL13	15/6	958A	4/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6J6W	6/6	9D6	2/6	35L6GT	7/6	G.R. Tubes	
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6J7G	5/6	10P9	9/6	35T	17/6	VCR87	40/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6J7W	6/6	12A6	2/6	35W4	5/6	VCR87	50/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6K6GT	5/6	12A17	5/6	35Z3	10/6	VCR87B55/6	
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6K7G	2/6	12A76	5/6	35Z4GT	6/6	VCR517C80/6	
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6K7GT	4/9	12AT7	4/6	35Z5GT	6/6	3FP7	45/6
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6K8G	3/6	12AT7WA	3/7	4/6	50P1	30/6	
PC99	10/6	V25	13/6		1R4	5/6	5A44	8/6		6K8GT	8/3	50K	38	4/6	50P7	12/6	

## TRANSISTORS

OC16	20/6	OC81D	5/6	OC201	12/6	XC411	10/6
OC22	23/6	OC81M	5/6	OC202	15/6	XC412	15/6
OC25	9/6	OC82	10/6	OC203	12/6	XC155	20/6
OC35	12/6	OC82DM	5/6	OC204	17/6	XC156	22/6
OC44	6/6	OC83	5/6	OC206	22/6	2N247	9/6
OC45	5/6	OC83B	5/6	AAZ12	6/6	2N412	7/6
OC71	4/6	OC122	5/6	AAZ18	6/6	2N502	47/6
OC72	5/6	OC122	5/6	AAZ18	7/6	2N505	10/6
OC73	6/6	OC170	6/6	BCZ11	7/6	2N1090	20/6
OC81	9/6	OC260	10/6	BY38	7/6	2N1091	29/6

V26	13/6	W91	5/6	2B26	8/6	5V44	8/6
V27	8/6	W118	5/6	2C2F	7/6	3Y3HT	

# NOW!

THE  
*World's smallest radio  
comes to you in the new  
"See for Yourself" sealed  
Kit pack*



## SINCLAIR MICROMATIC

### SIX STAGE TRANSISTOR RECEIVER

Now when you buy your Sinclair Micromatic kit, you see every component instantly in the new sealed polystyrene kit pack. Never before in the history of radio has any kit been so elegantly presented. Your Micromatic reaches you factory fresh and guaranteed. Check for yourself at once that every component is in place in the specially shaped and fitted case. The Micromatic does not cost you a penny more bought this way. Such is the appearance and performance of this brilliant new Sinclair design that you will want to build and use it immediately. There is no other set in the world as small, efficient and dependable as this. Reception both of home and overseas programmes often proves much easier than with larger conventional radios. In fact, your Micromatic will virtually play anywhere. It is also available ready built.

#### TECHNICAL DESCRIPTION

The Sinclair Micromatic is housed in a neat plastic case with aluminium front panel and spun aluminium calibrated tuning dial.

Special Sinclair transistors are used in a six-stage circuit of exceptional power and sensitivity—two stages of powerful R.F. amplification; double diode detector; a high gain three stage audio amplifier. A.G.C. counteracts fading from distant stations. The set is powered by two Mallory ZM.312 Cells from radio shops, Boots Chemists, etc., for 1/7 each. Plugging in the earpiece included switches the set on, withdrawing switches off. Complete kit in pack with instructions and solder.

#### ● READY BUILT

The Sinclair Micromatic is also available ready built, tested and guaranteed. Complete in presentation case with lightweight earpiece.

59/6

79/6

- ★ MEASURES  $1\frac{1}{5} \times 1\frac{3}{10} \times \frac{1}{2}$ "
- ★ BEAUTIFULLY STYLED CASE
- ★ AMAZING POWER, RANGE AND SENSITIVITY
- ★ NEW CIRCUITRY
- ★ TUNES OVER M.W. BAND WITH BANDSPREAD AND A.G.C.
- ★ CALIBRATED TUNING DIAL
- ★ GUARANTEED 5 YEARS

FOR MORE BRILLIANT SINCLAIR DESIGNS SEE NEXT TWO PAGES

**sinclair**

SINCLAIR RADIOLOGICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Telephone 52996 (STD Code OCA3)



# SINCLAIR STEREO 25 DE-LUXE PRE-AMP CONTROL UNIT

THE SINCLAIR STEREO 25 has been designed specially to ensure the highest possible standards of reproduction when used with two Z.12s or any other first class stereo power amplifier. Best possible components are used in the construction of this superb unit, whilst its appearance reflects the professional elegance characteristic of all Sinclair designs in hi-fi, radio and TV. The front panel of the Stereo 25 is in solid brushed and polished aluminium with beautifully styled solid aluminium control knobs. Mounting the unit is simple, and power is conveniently obtainable from the Sinclair PZ.3 which can also be used to supply two Z.12s to make a complete stereo assembly. Hi-fi enthusiasts seeking the ultimate in domestic listening will find all they want from this combination of Sinclair units. With a Micro FM for tuner, they will have an installation to compare favourably with anything costing from four to five times as much.

## FOR USE WITH ANY GOOD STEREO SYSTEM

### TECHNICAL SPECIFICATIONS

Performance figures obtained using Stereo 25, two Z.12s and a PZ.3.

- **SENSITIVITY** for 10 watts into 1.5 ohms load per channel. Mic.—2 mV into 50K ohms. Pick-up—3 mV into 50K ohms. Radio—20 mV into 4.7K ohms.
- **FREQUENCY RESPONSE** (Mic. and Radio)—25 c/s to 30 kc/s  $\pm$  1dB extending to 100 kc/s  $\pm$  3dB.
- **EQUALISATION** — Correct to within  $\pm$  1dB on RIAA curve from 50 c/s to 20 kc/s.

### TONE CONTROLS

- Treble +12dB to —10dB at 10 kc/s. Bass +15dB to —12dB at 100 c/s.
- **SIZE**—6in.x2 $\frac{1}{2}$ in.x2 $\frac{1}{2}$ in. overall, plus knobs.
- **FINISH**—Front panel sectioned in brushed and polished solid aluminium with solid aluminium knobs. Black figuring on front panel.

BUILT, TESTED AND GUARANTEED

**£9.19.6**

"Although a complete novice to radio I was able to assemble it (Micro-FM) without undue difficulty thanks to your clear and lucid instructions. I receive all B.B.C. programmes and local.....very strongly."  
H.T., Warrington, Lancs.

"The quality of reception (with Micro-FM) is 100%. I shall now purchase your Z.12 amplifier to go with it."  
N.T.S., Luton, Beds

"I consider your after sales service is excellent. I wish very much that other suppliers treated their customers in the way you do. I have tried out the Micro-FM with the Z.12 and my Quad speaker and am very pleased with the results."  
H.A., London, N.6

## SINCLAIR MICRO-FM

### COMBINED FM TUNER AND POCKET FM RECEIVER

7 TRANSISTORS

●

NO ALIGNING

●

PULSE COUNTING DISCRIMINATOR

●

A.F.C.

●

TUNES 88-108 Mc/s

●

SIZE—less than 3" x 1 $\frac{1}{2}$ " x 1"

This unique, superbly engineered FM superhet is the only set in the world which can be used both as an FM tuner and an independent FM pocket receiver just whenever you wish. Problems of alignment have been completely eliminated making the Micro-FM ready for use the moment you have built it. The pulse counting discriminator ensures best possible audio quality; sensitivity is such that the telescopic aerial included with the kit assures good reception in all but the very poorest reception areas. The Sinclair Micro-FM will give you all you want in FM reception and the satisfaction of building a unique design that will save you pounds.

Complete kit, including transistors, case, aerial, earpiece, etc.

**£5.19.6**


ANYONE CAN BUILD IT

FULL SERVICE FACILITIES AVAILABLE TO ALL SINCLAIR CUSTOMERS



SINCLAIR RADIONICS LTD., 22 Newmarket Rd., CAMBRIDGE

Telephone 52996 (STD Code OCA3)

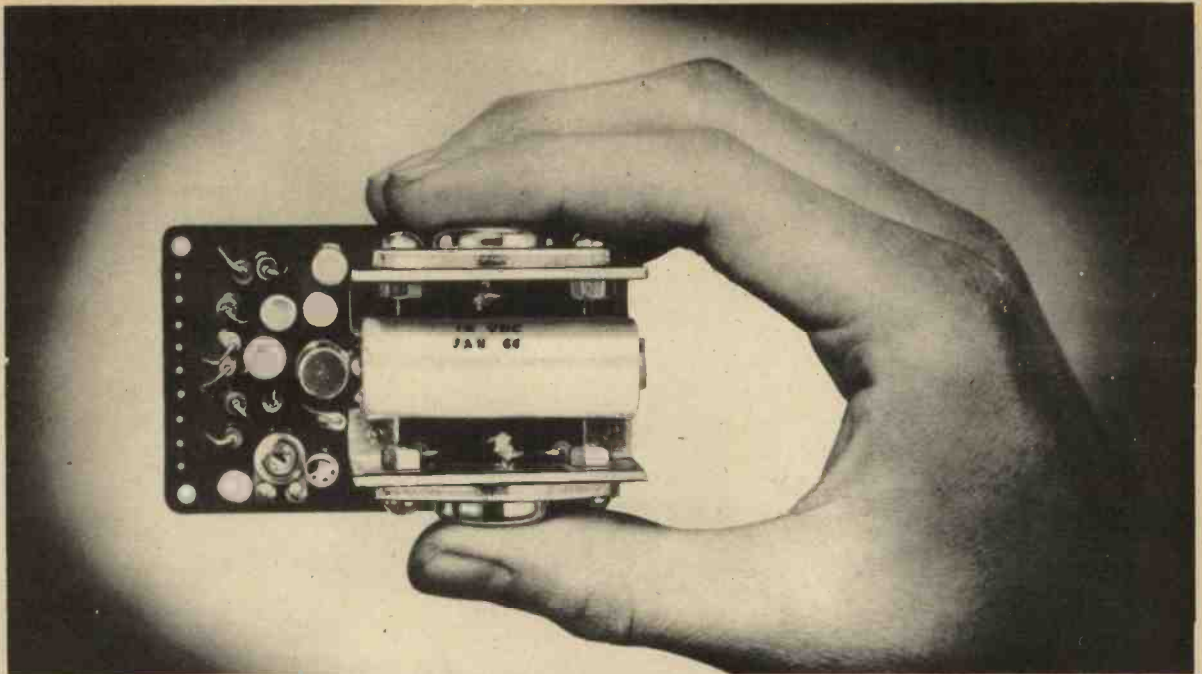


# SINCLAIR Z.12

COMBINED 12 WATT HIGH-FIDELITY AMPLIFIER AND PRE-AMP

**12 WATTS R.M.S. OUTPUT**  
CONTINUOUS SINE WAVE (24W. PEAK)

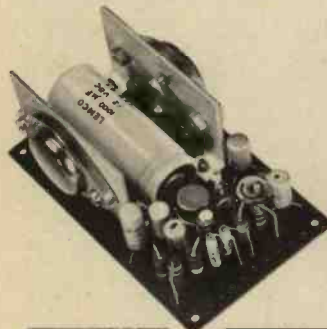**8 TRANSISTOR CIRCUIT WITH CLASS B ULTRALINEAR OUTPUT**

IDEAL FOR HI-FI (STEREO OR MONO) CAR RADIO, ELECTRIC GUITAR, P.A., INTERCOM, ETC.




The amazing adaptability and rugged construction of this very powerful and exceptionally compact amplifier make it possible to use just one type of unit with outstanding success in an unusually wide variety of applications. Eight special H.F. transistors are used in a highly original circuit to achieve the characteristics demanded of any quality amplifier irrespective of price, yet this Sinclair unit costs well under £5, including its own integrated pre-amplifier. The Z.12 accepts radio, microphone and pick-up inputs. Detailed instructions for connecting

these in mono and stereo are given in the manual supplied with every unit. A number of different control networks are also shown. The Z.12 will operate efficiently from any supply between 6 and 20 V. d.c, making it very convenient to run the amplifier from a car battery. Where it is required to run the Z.12 from mains supply, the PZ.3 is recommended. Those wishing to have a ready made pre-amp control unit can feed inputs via the Stereo 25, which, with two Z.12s will provide the finest stereophonic hi-fi possible—and the saving in cost is fantastic.
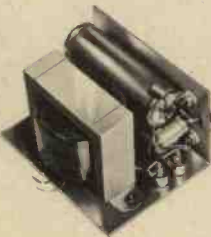
## PZ.3 MAINS POWER SUPPLY UNIT

This special power supply unit uses advanced transistorised circuitry to achieve exceptionally good smoothing. Ripple is a barely measurable 0.05 v. The PZ.3 will power two Z.12s and a Stereo 25 with ease.



**79/6**

A new Sinclair Set—see page 243

**sinclair**

SINCLAIR RADIONICS LTD.  
22 Newmarket Road, Cambridge 52996

## TECHNICAL SPECIFICATIONS

- Size 3 in. × 1½ in. × 1½ in.
- Class "B" ultralinear output
- **RESPONSE** 15-50,000 c/s ± 1 dB.
- Suitable for 3, 7.5 or 15Ω speakers. Two 3Ω speakers may be used in parallel
- **INPUT**—2mV into 2kΩ
- **OUTPUT**—12 watts R.M.S. continuous sine wave (24 w. peak); 15 watts music power (30 w. peak)
- Signal to noise ratio better than 60dB.
- Quiescent current consumption—15mA.

*Built, tested and guaranteed. Ready for immediate use. With Z.12 manual.*

**89/6**

**YOUR SINCLAIR GUARANTEE**  
If you are not completely satisfied when you receive your purchase from us, your money will be refunded at once in full and without question.

*If you prefer not to cut this page, please mention PE.467 when writing your order*

To: SINCLAIR RADIONICS LTD., 22 NEWMARKET ROAD, CAMBRIDGE

Please send items detailed below:

NAME.....

ADDRESS.....

For which I enclose cash/cheque/money order

PE.467

# COMPARE THESE PRICES

## ELECTROLYTIC CONDENSERS

64uf. . . 2.5V.	5uf. . . 6V.	30uf. . . 10V.	750uf. . . 18V.
125uf. . . 2.5V.	20uf. . . 6V.	3uf. . . 12V.	2.5uf. . . 25V.
640uf. . . 2.5V.	25uf. . . 6V.	4uf. . . 12V.	3uf. . . 25V.
0.25uf. . . 3V.	30uf. . . 6V.	25uf. . . 12V.	4uf. . . 25V.
2uf. . . 3V.	50uf. . . 6V.	200uf. . . 12V.	10uf. . . 25V.
40uf. . . 3V.	100uf. . . 6V.	2.5uf. . . 16V.	25uf. . . 25V.
4uf. . . 4V.	3.2uf. . . 6.4V.	64uf. . . 16V.	12.5uf. . . 40V.
500uf. . . 4V.	40uf. . . 6.4V.	200uf. . . 16V.	3.2uf. . . 64V.

All at 1/- each, 9/- per dozen or mixed packet (our selection) 20 for 10/-  
 150uf., 25V.; 400uf., 25V.; 2/6 each. 5,000uf., 12V., 4/- each.  
 200/100, 275V.; 200/200, 275V.; 125/300/50, 275V.; 5/- each, 3 for 10/-.

**PAPER CONDENSERS. SPECIAL CLEARANCE!**  
 0.35uf., 150V.; 0.02uf., 350V.; A.C. 0.25uf., 350V.; 0.5uf., 350V.; 0.5uf., 500 V.;  
 ALL at 15/- per 100.

Mixed packet containing 0.0001uf., 200V. to 0.5uf., 500V.  
 Very useful for service work! 50 condensers for 10/-.

## RESISTORS

1/2 watt, well assorted values, 10/- per 100, 55/- per 1,000.  
 1/4 watt to 3 watt, well assorted values, 10/- per 100, 55/- per 1,000.  
 TO CLEAR: 10 Meg. 1/6th watt resistors—to clear £1 per 1,000.

## TRANSISTORS

Untested mixed, 50 for 10/-.  
 NPN Switching transistors; Min. 200 m/c.s. 6 for 10/-.  
 PNP Switching transistors; Min. 200 m/c.s. 6 for 10/-.

## DIODES

Suitable for keying electronic organs, 20 for 10/-.  
 BY100 type rectifiers, 30/- per dozen.  
 ORP12 light cells, 9/- each.  
 TRANSISTOR BATTERY ELIMINATOR—same size as PP9, 30/-, PP6, £1.  
 BATTERY CHARGERS with meter, 4 amp, 6 or 12 V, 55/-.  
 LAPEL MICROPHONES, crystal or magnetic, 10/- each.  
 MINIATURE EARPIECES, complete with plug and lead, 5/- each.  
 SIGNAL INJECTOR, parts and circuit to make, 10/- each.  
 SIGNAL TRACER, parts and circuit to make, 10/- each.  
 MOTOR CAR REV. COUNTER, parts and circuit to make, 10/- each.  
 PORTABLE RADIOS, complete with leather case, earpiece, etc., fully  
 guaranteed, 79/6 complete.  
 ACOS PICK-UP HEADS, Mono, 10/-, Stereo, 12/6, Diamond, 17/6.  
 SAPPHIRE STYLII, TC8LP: GC2LP: GC8LP: BF40LP: GP67LP: TC8 Stereo  
 LP: Studio OLP: GP37: GP59: ALL AT 3/6 each.  
 POTENTIOMETERS—PRE-SET, 100 ohm to 680 K, ohm, 12 tor 10/- (mixed)  
 MAGNETIC RECORDING TAPE, BRITISH MADE, FULLY GUARANTEED

## STANDARD PLAY

3in., 150 ft., 3/6; 5in., 600 ft., 10/6; 5 1/2in., 900 ft., 13/6; 7in., 1,200 ft., 16/3.

## LONG PLAY

3in., 225 ft., 4/-; 5in., 900 ft., 12/9; 5 1/2in., 1,200 ft., 15/9; 7in., 1,800 ft., 21/6.

## DOUBLE PLAY

3in., 400 ft., 6/6; 5in., 1,200 ft., 20/-; 5 1/2in., 1,800 ft., 28/-; 7in., 2,400 ft., 34/-  
 2 1/2in., 300 ft., 6/9.

## TRIPLE PLAY, POLYESTER

3in., 600 ft., 12/6; 4in., 900 ft., 16/6.  
 WELLER INSTANT HEAT SOLDERING KIT, 72/6 complete.  
 WELLER DUAL-HEAT SOLDERING GUN, only 57/6 complete.  
 PISTOL GRIP SOLDERING IRON ONLY, 10/-.  
 PHILIPS/STELLA/COSSOR remote control unit, value 3 gns., our price, 10/-.  
 RUMBLE AND SCRATCH FILTER, parts and circuit to make, 30/-.  
 TRANSISTORS, COMPONENTS AND CIRCUIT to convert 1ma. meter to  
 0 to 10 Meg. ohmmeter, 10/-.

# G. F. MILWARD

17 PEEL CLOSE, DRAYTON BASSETT, NR. TAMWORTH, STAFFS.  
 TAMWORTH 2321

Due to recent heavy increase in parcel rates, please include part postage cost.

the Wyndsor Vanguard . . .  
 the most versatile  
 recorder at its price\*  
 offering so many  
 outstanding features . . .

- 4 track-3 speeds  
—7 in. spools
- Separate Record and  
replay amplifiers
- Double play
- Sound-on-Sound
- Detachable lid  
fitted 8" speaker
- Tape Monitoring  
facility



- Push button controls
- Recording meter and  
Playback indicator
- Straight through amplifier  
facility
- Bass, treble, volume  
and record gain controls
- Many other features

\* All British  
and full value  
for money at  
only 59 gns.  
inc. 1800 ft. LP  
tape and Tape  
manual. (less  
mike).

Before you buy  
an ordinary  
tape recorder  
write for full  
details of the  
Vanguard and  
other models.

WYNSOR RECORDING CO. LTD. (Dept. PE3)  
 Wyndsor Works, Bellevue Road, Friern Barnet, London, N.11. ENT. 2226

For quick, easy faultless soldering



5 CORE SOLDER

Easy to use and economical. Containing 5  
 cores of non-corrosive flux, instantly  
 cleaning heavily oxidised surfaces. No extra  
 flux required. Ersin Multicore Savbit Alloy  
 reduces wear of copper soldering iron bits.



SIZE 5  
**HANDY SOLDER  
 DISPENSER**  
 Contains 12 ft. of  
 coil 18 s.w.g.  
 Ersin Multicore  
 Savbit Alloy. Quick  
 and easy to use.  
 2/6 each



NEW SIZE 15  
 21 ft coil of 60/40  
 Alloy, 22 s.w.g. in  
 a dispenser. Ideal  
 for small compon-  
 ents, transistors,  
 diodes, etc.  
 3/- each



SIZE 12  
 Ideal for home  
 constructors.  
 Contains 102 ft.  
 of 18 s.w.g. Ersin  
 Multicore Savbit  
 Alloy on a plastic  
 reel, 15/- each  
 (Also available  
 in other sizes)



**BIB MODEL 8  
 WIRE STRIPPER  
 AND CUTTER**  
 Strips insulation  
 without nicking  
 the wire, cuts  
 wire and splits  
 plastic twin flex.  
 Plastic cushioned  
 handles. 8/6 each

From Electrical or Hardware shops. If unobtainable write to:  
**MULTICORE SOLDERS LTD., Hemel Hempstead, Herts.** M29 B



See the **HEATHKIT EXHIBITION** (Concurrent with the Audio Fair) at the **GRAND HOTEL, SOUTHAMPTON ROW, LONDON.** Admission Free  
 March 30th—April 2nd. 11 a.m.—9 p.m. (Sunday 8 p.m.). The latest models will be on view

Treat yourself to superb LW, MW entertainment with the  
**High-Performance Car Radio Kit, CR-1**



Complete your motoring pleasure with this small, compact, high-performance car radio. It can be fitted to any make of car having 12 volt positive or negative earth system. Tastefully styled in neutral grey with matching black knobs and chrome trim to harmonise with any car colour scheme.

Features include: Six-transistor, 2-diode circuit. Completely pre-assembled and aligned tuning unit. High sensitivity, combined with wide range automatic gain control (AGC), minimises fading under weak reception conditions. Easy-tune dial. Push button Long, Medium and Tone selection.

The car radio is available for your convenience, in two separate units; RF Amplifier Kit CR-1T £1.13.6 incl. P.T., IF/AF Amplifier Kit CR-1A £11.3.6.

**TOTAL PRICE KIT** (excluding Loudspeaker) £12.17.0 incl. P.T.  
 8"x5" Loudspeaker Pt. No. 401-505 £1.16.1 incl. P.T.

The Transistor Amplifier you have been looking for!



**Low-cost Stereo Amplifier Kit, TS-23**  
 Breaks the price barrier in quality  
 Transistor Amplifier cost

Incorporates all the essential features for good quality reproduction from gramophone records, radio and other sources.

Its many features include: 3 watts rms (150) each channel. Good frequency response for outstanding fidelity. Compact slim-line styling. Ganged BASS, TREBLE and VOL. controls, 6-position SELECTOR switch for programme sources. Attractive perspex two-tone front panel. 16 transistor, 4 diode circuit. Handsome fully-finished walnut veneered cabinet. Outputs for 8 or 15 ohm loudspeakers. Printed circuit boards. For free-standing or cabinet mounting. Size 3 3/4" x 13" x 8" deep.

**PRICES:** Amplifier Kit £17.15.0  
 Amplifier Kit and Cabinet £18.19.0

Walnut Veneered Cabinet  
 separate £2.0.0

Hi-Fi performance from a "Mini"  
**Speaker Kit**  
 with the  
**"AVON"  
 BOOKSHELF  
 SPEAKER  
 SYSTEM**



The challenge to our acoustic engineers was to design a speaker occupying the minimum space consistent with first class reproduction. The results of our efforts was this "AVON" compact unit of exceptional quality.

Features: Two special speakers 6 1/2" BASS, 3 1/2" HF unit and crossover network. Good frequency response. Beautiful fully-finished walnut veneered cabinet, size only 7 3/4" x 13 1/4" x 8 3/4" deep.

Supplied in two units. Can be built for a total price.

Kit £13.16.0 incl. P.T.

**A 3" Service Oscilloscope Kit with outstanding features. Model OS-2**

The attractively styled OS-2 is a compact, lightweight, portable oscilloscope that fulfills many of the general requirements in Laboratories, Service Departments and Educational Training. It is ideal for use in production line testing where otherwise expensive equipment would be tied up on ordinary routine tests. The bandwidth of the OS-2 is from 2 c/s-3 Mc/s ± 3dB, this scope can therefore be used in applications ranging through audio, ultrasonic and radio frequencies. The time base operates from 20 c/s to 200 kc/s in four ranges. Size 5" x 7 1/2" x 12" deep. Weight 9 1/2 lb.



Kit £23.18.0. Assembled £31.18.0  
 Optional extra L/Cap Probe Kit, PK-1 Kit £3.12.6

Many other models in wide range.

Prices quoted are Mail Order, Retail Prices in general 5% extra.

Full specification sheets of any model available upon request.

**FREE**

**BRITAIN'S LARGEST FREE  
 ELECTRONIC KIT CATALOGUE**

GET YOUR LATEST COPY NOW →

WHEN IN LONDON visit our

**HEATHKIT CENTRE**  
 233 Tottenham Court Road, W.1  
 Tel.: MUSEUM 7349

See a full range of British models and a selection of American Heathkit models

**HEATHKIT**

To:—  
**DAYSTROM LTD., Dept. P.E.4**  
 GLOUCESTER, ENGLAND. Tel.: Glos. 20217

Please send me model(s) .....

for which I enclose £ ..... s. .... d. post paid

Please send me FREE British Heathkit Catalogue

NAME .....

ADDRESS .....

P.E.4

**PEAK SOUND**

# Cir-kit

From stockists everywhere. In case of difficulty, direct from Peak Sound.



Think what it means to be able to have just ONE printed circuit to the design you want and you will see immediately just how wonderfully CIR-KIT more than fills that long felt need. CIR-KIT is quick—you simply lay the self-adhesive copper strip on the board, drill holes for mounting the components and you are ready to solder them in at once. CIR-KIT is clean—there are no chemicals, acids or etching processes involved. CIR-KIT is adaptable—you can amend a circuit again and

again quickly and easily. Ideal for experimenters, this. CIR-KIT is economical—No. 3 Kit contains enough material to make up about 10 circuits and components may be closely mounted if desired. You can also repair damaged conventional printed circuits; you can experiment quickly and cheaply. In fact, CIR-KIT is the most revolutionary advance in circuit techniques since the printed circuit itself was invented and is already widely used by many of the most famous houses in electronics.

**PEAK SOUND (HARROW) LTD.** 10 ASHER DRIVE, MILL RIDE, ASCOT, BERKS.

Distributors to the Radio Trade. T.S.L., 63 GOLDHAWK ROAD, W.12. (01-603 2581)

# makes better circuits quicker and cheaper

- ★ INSTANTLY APPLICABLE, INSTANTLY ADAPTABLE
- ★ NO CHEMICALS, NO ETCHING, NO HEAT
- ★ AS USED IN LABORATORIES, INDUSTRY, ETC.

CIR-KIT KIT No. 3 contains 12in. x 6in. mounting board, 4in. x 6in. CIR-KIT adhesive copper sheet for land areas and special shapes and approx. 15ft. of tin. CIR-KIT adhesive copper strip. The heat-resistant adhesive used will last indefinitely with normal use. With instructions.

# 15/-

“Cir-Kit” shows the way to economical hi-fi stereo



PEAK SOUND SA. 8-8 Kit complete with instructions £12. 19. 6  
PEAK SOUND POWER PACK 75/-

PEAK SOUND combined 16 watt stereo amplifier and pre-amp for only £12.19.6 is made possible entirely due to using “Cir-Kit”. 14 matched transistors are used in this superb hi-fi kit for crystal and ceramic pickups. Over 16 watts output into two 5-ohm speakers in stereo. 8 and 15Ω speakers may be used. This Peak Sound Kit is complete down to last piece of wire.

Phone: WINKFIELD ROW (OE47) 3217

## The safest, quick and handy connector for electrical appliances


# MAINS Keynector

Measuring only 5in. x 3in. x 1 1/2in. the MAINS KEYNECTOR is made of non-combustible urea-formaldehyde. Designed in modern style and manufactured in attractive two-tone colour. The unit eliminates the need of terminating the mains input lead of any electrical instrument or appliance with a plug. It also enables more than one instrument or appliance to be connected in parallel and used simultaneously. In the workshop, the MAINS KEYNECTOR will prove invaluable to the experimenter and handyman.

Colour: Duo-Green 32/6  
Rating: 13 amp. inc. p. & p.



British and Foreign Patents applied for

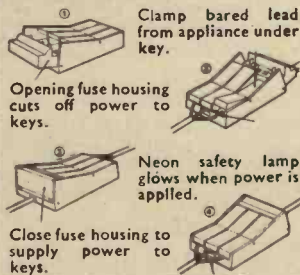

**CYBERNAUT CONTROLS LTD. (Ref. P.E.2)**  
28-30 Rivington St., London, E.C.2. Tel.: 01-739 2763

**R.S.T. VALVE MAIL ORDER**  
144-146 WELLFIELD ROAD, S.W.16  
24-HOUR EXPRESS SERVICE

AC/TRI 18/8	EC91 9/-	KT33C 6/-	PX25 18/8	354 4/9	708 6/-
AC/VP1 12/8	ECC81 3/9	KT36 22/8	PY31 6/8	3V4 5/9	727 10/-
(5 & 7 pin)	ECC82 4/9	KTW 17/8	PY22 8/8	6X4 12/8	757 19/8
AC/VP2 15/-	ECC83 5/9	KT96 20/-	PY33 8/8	5R4G 8/8	787 17/8
AC2/PEN	ECC84 5/8	KT81(7C5) 10/-	PY80 4/9	5U4G 4/-	7Y4 7/8
	ECC804 9/9		PY81 8/-	5V4G 8/-	10C1 9/-
AZ31 7/9	ECCF80 7/-	KT88 27/8	PY82 5/8	5Y3GT 5/-	10F9 9/9
B36 11/-	ECCF82 7/-	KTW61 4/3	PY83 6/-	5Z4G 8/-	10L1 10/-
C13 12/8	ECH21 19/-	KTW62 5/-	R10 15/8	5Z4GT 10/-	10P14 15/-
C1C 12/8	ECH35 11/-	KTPLA 8/-	R15 15/8	6/30L2 11/3	11E3 27/8
CR11 12/8	ECH42 9/-	MKT4 10/-	R19 7/-	6A7 15/-	12AT6 4/8
CLB11 15/-	ECH61 5/3	M14 17/8	S130 25/-	6AC7 3/-	12AT7 3/9
CHC35 21/-	ECH83 7/-	MS.PEN 10/-	S130P 25/-	6AK5 4/8	12BA6 6/-
CL4 12/8	ECL80 8/8		SP41 1/8	6AK6 6/8	12BE6 5/3
CL33 12/8	ECL82 6/8	NUI2 4/-	SP51 1/-	6AL5 3/-	12E1 19/8
CYIC 12/8	ECL86 8/9	N7 10/-	T41 9/-	6AQ5 5/8	12T7GT 7/3
DAC32 7/8	EF9 20/-	N8 15/-	U10 7/-	6B4G 10/-	12X7GT 3/-
DAP91 3/3	EF36 3/-	N329 6/6	U24 24/-	6B8G 2/-	12XKGT 6/-
DAP92 7/7	EF37A 7/8	OA 2 5/3	U25 10/8	6BA6 4/8	12Q7GT 3/-
DAP96 6/-	EF39 6/-	OB2 6/-	U28 10/8	6BE8 4/8	12SL7GT 5/-
DF91 2/8	EF42 3/9	OM4 9/-	U33 13/-	6B6G 12/8	12T7 9/-
DF92 2/6	EF50 2/-	OM6 6/-	U35 14/-	6BQ7A 7/-	1457 18/-
DF96 6/-	EF80 5/-	OM10 12/8	U37 15/8	6BR7 10/8	19A05 7/8
DK32 7/9	EF86 6/3	OZ4 4/-	U261 12/8	6BW6 7/8	19B06G 19/8
DK91 5/-	EF89 5/8	PABC80 6/9	U301 13/-	6BW7 8/8	20L1 15/-
DK91 5/-	EF91 3/3	PC86 2/8	U404 6/-	6C4 2/9	20P1 10/8
DK96 6/8	EF183 9/-	PC88 9/-	U801 18/8	6CD6G 22/8	20P3 17/-
DL33 6/8	EL32 3/-	PC84 5/8	UABC80 5/8	6D6 2/9	20P4 17/-
DL6 15/-	EL33 17/8	PC89 10/-	UAF42 8/9	6F6G 4/-	25L6GT 4/8
DL91 5/-	EL34 9/6	PCC189 10/-	UCR21 21/-	6F14 12/8	25V4GT 12/8
DL94 5/9	EL38 10/-	PCC282 10/8	UCL83 8/9	6F16 9/-	25Z6GT 7/-
DM70 5/-	EL38 15/8	PCF80 6/8	UF89 6/-	6F19 6/8	27S1 20/-
DW4-350	EL41 8/8	PCF84 8/-	UL41 8/9	6F32 11/-	30P11 13/8
	EL83 6/-	PCF84 8/-	UL44 20/-	6F66 2/6	30P12 13/8
DY86 6/8	EL86 7/6	PCF86 8/-	UL84 6/-	6H8G/GT13	30P14 12/8
DY87 7/9	EL88 20/-	PCL82 7/-	U06 13/8	6J5M 6/8	30L1 5/8
E80F 17/6	EM80 7/-	PCL83 8/8	U07 13/8	6K7G 1/3	30L15 12/8
E88CC 12/-	EM84 7/-	PCL84 7/3	UY41 8/3	6K8G 3/-	30P4 14/-
EB11 18/-	EM87 7/-	PC85 20/8	UY85 20/-	6K47 7/-	30S5 5/9
E180CC 8/-	EY11 7/-	PEN44 20/-	YMP4G 17/-	LI 9/6	30P19 14/-
E180F 16/-	EY88 6/6	PENB4 20/-	YU111 6/-	6L6G 7/8	30P14 14/-
E181CC 12/-	EY87 8/6	PEN45 6/-	YU120 12/8	6L8 7/8	35L6GT 5/8
E182CC 14/-	EZ35 4/9	PEN45DD	YU120A12/8	6N7G 6/9	35W4 4/8
EABC80 5/9	EZ40 7/-		YU508 30/-	6P28 10/-	35Z4GT 3/9
EAB42 7/8	EZ41 5/-	PEN453DD	W81 5/-	6Q7G 5/8	50E5 5/9
EB91 18/-	EZ80 5/-	W149 10/-	X14 7/-	6K47 7/-	50D6G 32/6
EBC33 6/-	EZ81 5/-	PL33 8/9	X78 26/-	6S77 2/6	50L6GT 6/-
EBC41 8/3	EZ90 3/6	PL36 9/-	X79 41/-	6SL7GT 4/9	53K U 12/8
EBC81 6/3	GZ30 8/6	PL38 15/-	X81 18/8	6SN7GT 4/-	80 5/-
EBC80 3/9	GZ32 9/6	PL41 6/8	Z66 17/8	6U4GT 6/8	85A2 8/8
EBF80 6/8	GZ34 10/-	PL82 6/8	1T4 5/-	6V6G 3/6	90A6 32/6
EBF89 6/8	H83 5/-	PL83 6/-	154 5/8	6X4 3/8	90A8 15/8
EBL1 17/8	HABC80 9/-	PL84 6/8	1T4 5/8	6X5G 4/0	90C1 15/8
EBL21 10/8	HL23DD 9/-	PL500 14/6	2B26 12/8	7B8 11/-	90CV 22/8
EBL31 27/8	IW4-350 5/-	PX4 18/8	2C34 3/6	727 7/-	185BT 30/-

S.A.E. for list of 4,000 types. Postage 6d. per valve.

# RADIO • HI-FI • COMPONENTS • TEST EQUIPMENT

ALL ITEMS SENT POST FREE



**CP.110 11-PIECE CHASSIS PUNCH SET**  
Top grade machined steel. Contains 7", 1", 1/2", 1" and 1 1/2" punches, complete with gripper and accessories in carrying case. **£3.12.6**




**ALL TRANSISTOR MONO & STEREO PRE AMPLIFIERS**  
Provide extra stage of amplification for use with magnetic cartridges, tape and microphone inputs. Both models feature wide band pass range, 20-20,000 cps. **PRE 301 MONO £4.12.6**  
**PRE 302 STEREO £5.15.0**



**EAGLE FMT41. FM TUNER**  
Sub-miniature 6 transistor 3 diode F.M. Tuner. Covers 88-108 Mc. Operates from 9-volt battery, micro miniature circuit giving brilliant FM reception. Ready to use, simply connect to your Hi-Fi amplifier. Instructions supplied. **£8.10.0**



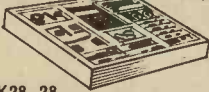**REMOTE CONTROL STEREO HEADPHONE STATION LS.2**  
A junction box for connecting stereo headphones to a stereo or monaural system. Separate controls for each channel. On/off switch. Stereo sockets allow two sets of headphones to be used. With instructions and 20 ft. of 5 conductor cable. **£3.5.0**



**EEK28. 28 PROJECT CONSTRUCTIONAL KIT**  
This advanced educational kit is excellent for beginners as well as the more advanced experimenter. Not even a soldering iron is needed. Complete with 60-page booklet giving full details of suggested circuits. **£6.10.0**



**LA9P. AC ELIMINATOR**  
with a double wound step down transformer to operate 9v. Realsos, etc., from AC Mains. **£1.8.6**



**SPECIAL OFFER! GOOSENECK PENCIL TYPE DYNAMIC MICROPHONE**  
Imp.: 50K ohm. Output -52db. Response 40-13,500 c.p.s. With base with on/off switch, stand adaptor and cable. **USUAL PRICE 4 GNS. SPECIAL OFFER PRICE 59/6.**



**AIWA. TP. 712 2-SPEED 5' REEL MAINS AND BATTERY TAPE RECORDER**  
Loaded with features hitherto only found in more expensive tape recorders: AVC system adjusts recording volume level. TWO-WAY OPERATION: AC mains or batteries. TWO HOURS OF RECORDING TIME: using 1.5 mil 600 ft. REMOTE CONTROL: TONE CONTROL: LEVEL METER: indicates recording and battery levels. Other features include 1 1/2 and 3 1/4 tape speeds, smooth operating push-button keyboard, input for radio, record player, TV, etc., socket for an external speaker. Complete with Dynamic microphone, earphone, 5' 600' tape, 5' empty reel, batteries and AC lead. Size: 12 1/2" x 10 1/2" x 3 1/2". **26 1/2 gns.**

**EAGLE PRODUCTS. MAGNETIC STEREO CARTRIDGES**

As reviewed in Hi-Fi News, Sept. 1965.  
**M1007G. GOLD** Response: 20-20,000cps Output: 5MV at 1Kc/5 cm/Sec. Stylus: 0.5 Mill diamond Tracking Pressure 1-2.5 grams. **£6.12.6**



Both feature singularly smooth reproduction and incisive separation of stereo channels

**EAGLE SA100. 10W INTEGRATED STEREO AMPLIFIER**



A compact, versatile reproduction unit for monaural or stereophonic reproduction from record player, tape recorder and tuner. Power output 3 watts per channel. Frequency response 40-20,000 c.p.s. **£18.0.0**

**EAGLE AFM100. AM-FM TUNER**

Combines a host of advanced features that easily make it the finest AM-FM tuner in its class. A tuned RF stage on FM, APC circuit and a heavy flywheel giving smooth but effortless tuning, built in AM Ferrite aerial. FM.88-108Mc. AM.535-1605 K/s. **£29.0.0**

**MS80. 20W ROSEWOOD SPEAKER SYSTEM**


The perfect answer for the music lover who wants full range fidelity in a compact system. Features an 8in. full range high compliance speaker with an output capacity of 20 watts RMS. Frequency response: 30-30,000 c.p.s. Resonant frequency: 30-40 c.p.s. Sensitivity: 97 db/w. Flux density: Over 12,000. Impedance: 16 ohm. Size 14 1/2in. high x 10 1/2in. wide x 8in. deep. **£14.14.0**



As well as this beautifully designed speaker there are two other models MS85. 10 watts RMS at £12.12.0 and MS84 5 watts RMS £9.10.0. All three speakers are finished in magnificent rosewood and the entire cabinet filled with acoustic damping material.

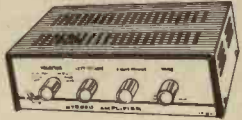**SA. 80N. 8-WATT INTEGRATED STEREO AMPLIFIER**

Recognised as the leading low price stereo amplifier. 4 watts per channel. Inputs for Pick-up (100mV) and Tuner (100mV). Frequency response 50-15,000 cps 200/250v. AC. Styled in Grey and Silver with metal knobs. **£12.0.0**



**AIWA. P.172 3-SPEED 3-BAND MAINS AND BATTERY RADIO-RECORD PLAYER**  
Plays all records, 33 1/3, 45 and 78 r.p.m., plus built-in LW/MW/FM radio. All in a smartly designed portable, offering the best of both worlds: battery or AC mains operation. Large oval speaker gives exciting reproduction of your records and favourite radio stations anywhere and everywhere you go. 13-transistor circuit produces big power output. Complete with earphone, batteries, AC lead, carrying handle and 3 1/2 rpm test record. Size: 10 1/2" x 15 1/2" x 4". **29 1/2 gns.**

FOR FULL DETAILS OF THESE AND MANY OTHER ITEMS SEND FOR FREE COMPREHENSIVE CATALOGUE, EAGLE NEWS AND ORDER FORM. ALL ITEMS AVAILABLE POST FREE AND COVERED BY 12 MONTHS' GUARANTEE.

CALLERS WELCOME AT OUR HI-FI SHOWROOM



**TT.144. Dynamic Transistor Tester**  
Tests in-circuit or out of circuit. Identifies PNP and NPN types. Indicates electrode open circuits, short circuits and current drain. Complete with instructions. **£4.10.0**



**TT.145. De luxe Transistor Diode Tester. £9.7.6**  
**KY.102 SEMI-AUTOMATIC BUG KEY**  
7 adjustments for speed and comfort. Key adjustment for tension, swing, speed, etc. Precision, toolled anti rust, nickel-plated, brass and stainless steel operating parts. Variable speed capable of 5 to approx. 60 wpm. Complete with cord and transparent dust cover. **£5.12.6**




**RF.40 RF FIELD INDICATOR**  
Broad tuning covers 1-250 Mc/s in five call bands. Can also be used as a frequency checker. Detects undesired radiation or spurious frequencies. RF is measured on an accurate 200 uA panel meter. **£4.10.0**



**WI-2. TRANSISTORISED WIRELESS INTERCOM**  
No wires, no installation needed, simply plug them into AC power point and talk. Units have press-to-talk lock switch and on-off volume control. Ideal Intercom or Baby Alarm for home, office, **£14.12.0** plate.

**DP303. DOOR PHONE INTERCOM**

Ultra sensitive transistorised intercom designed so that you may answer the door from within for greater convenience and safety. **£4.12.6** Other intercoms available.

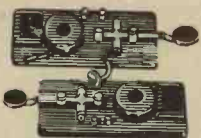

**MCK.2. MORSE CODE KIT**  
Two station morse code kit supplied with instructions, 50ft. of connection wire and morse code charts. **£2.2.0**

**WIRELESS MICROPHONES**

**WM909** (as illustrated) Pocket FM Wireless transmitter complete with tie-pin microphone. Transmits clearly up to 100 yds. and is fully tunable over the entire FM band. Simply used with an FM radio or tuner. **£14.0.0**

Also available **WM808** Professional stick type FM Wireless Microphone. **£21.0.0**  
These cannot be operated in U.K.

**RELDA RADIO LTD.** (Dept. P.E.16), 87 Tottenham Court Road, London, W.1

# THE AMPLIFIER FOR CERAMIC PICKUPS



## 222 STEREO AMPLIFIER

There are a number of ceramic pickups capable of giving excellent results with a good amplifier.

Our 222 was expressly designed for these pickups. It has all the facilities you look for in a high fidelity amplifier and a choice of matching FM and AM-FM tuners.

For those who wish to use a magnetic pickup there is the 221 amplifier, which has other additional facilities.

221 STEREO AMPLIFIER	£35 10 0
222 STEREO AMPLIFIER	£28 15 0
223 AM-FM TUNER	£31 9 0
224 FM TUNER	£25 2 3

OPTIONAL CASE, teak and vinyl hide as illustrated. All models £3 10 0

M5 STEREO RADIO DECODER £14 10 0

For full details and technical specifications of all models, plus list of stockists, post coupon or write mentioning 4PE67.

ARMSTRONG AUDIO LIMITED  
WARLTERS ROAD, LONDON, N.7  
Telephone: NORTH 3213



AUDIO FAIR. ENQUIRY ROOM 539  
BOOTH 45 DEMONSTRATION ROOM 538

name .....

address .....

4PE67 .....

## RADIOGRAM CABINETS 19 Gns.



An elegant Stereogram Cabinet in modern Veneered Mahogany and Cloth covered Front Panel  
BLACK LEATHERETTE SIDE PANELS  
Dimensions : 52 x 17½ x 12  
Speaker positions for Twin 10" x 5" Speakers  
OTHER MODELS—SEND FOR LIST

## TWO-YEAR GUARANTEE EX-RENTAL TELEVISIONS

★ Tube

★ Valves

★ Components

17 in. £11.10.0

3 star Guarantee

Channels for all areas  
Insured Carriage 30/-

## FREE ILLUSTRATED LIST

Slim line models

17" — 19" — 21" — 23"

A wide range of sizes, models and prices.

Demonstrations daily



TRANSISTOR CASES  
7/6. 9½" x 6½" x 4½"  
P. & P. 3/6.

TRANSISTOR CASES  
19/6. Cloth covered, many colours. Size 9½" x 6½" x 3½"  
P. & P. 3/6. Similar cases in plastic 7/6.

RECORD PLAYER CABINETS 49/6.  
Latest designed covered cabinets. Takes any modern Autochanger. P. & P. 7/6.

SINGLE PLAYER CABINETS 19/6.  
P. & P. 7/6.



T.V.  
TURRET  
TUNERS  
2/6.

New Less  
Valves.  
Slim Models  
5/- Press  
Button  
Models 19/6.  
P. & P. 2/6.

DUKE & CO. (LONDON) LTD.  
621/3 Romford Road, Manor Park, E.12  
Phone: ILFord 600-1-2-3. Stamp for Free List.

Keep those Contacts CLEAN  
by using a

## DIACROM SPATULA

The "Diacrom" is a metal spatula upon which diamond powder has been deposited by a special process. No deep scratches are possible because density is controlled and the polishing of the contacts is achieved by a gentle brushing motion. With coloured nylon handle for complete insulation and easy size identification.



Manufactured in France  
British Patents applied for

- Grain size 200, thickness 55/100 mm., both faces diamonded. For quick cleaning of industrial relays and switching equipment, etc.
- Grain size 300, thickness 55/100 mm., both faces diamonded. For smaller equipments, like telephone relays, computer relays, etc.
- Grain size 400, thickness 25/100 mm., one face diamonded. For sensitive relays and tiny contacts. Two close contacts facing each other can be individually cleaned, because only one face of the spatula is abrasive.

Sole Distributors for the United Kingdom

## SPECIAL PRODUCTS (DISTRIBUTORS) LTD.

81 Piccadilly, London, W.1. Phone: (01) 629 9556

As supplied to the War Office, U.K.A.E.A., Electricity Generating Boards, British Railways and other public authorities; also to leading electronic and industrial users throughout the United Kingdom.

# Why

## NOT BUILD ONE OF OUR PORTABLE TRANSISTOR RADIOS...

**FIRST FOR PERFORMANCE, QUALITY & PRICE!**

**BACKED BY OUR SUPER AFTER SALES SERVICE**

"A wonderful range of transistor radios using first grade components guaranteed results."

### NEW ROAMER SEVEN Mk IV

7 WAVEBAND PORTABLE OR CAR RADIO


Amazing performance and specification ★ Now with PHILCO MICRO-ALLOY R.F. TRANSISTORS  
**FULLY TUNABLE ON ALL WAVEBANDS** ● 9 stages—7 transistors and 2 diodes  
 Covers Medium and Long Waves, Trawler Band and three Short Waves to approx. 15 metres. Push-pull output for room filling volume from rich toned 7" x 4" speaker. Air spaced ganged tuning condenser. Ferrite rod aerial for M & L Waves and telescopic aerial for S Waves. Real leather-look case with gilt trim and shoulder and hand straps. Size 9" x 7" x 4" approx.



The perfect portable and the ideal car radio. (Uses PP7 batteries, available anywhere.)  
 ★ EXTRA BAND FOR EASIER TUNING OF LUXEMBOURG, etc. Total cost of parts now only **£5.19.6** P. & P. 5/6

Parts Price List and easy build plans 3/- (Free with kit)

### NEW MELODY MAKER SIX

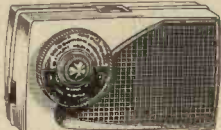

● 8 stages—6 transistors and 2 diodes  
 Covers Medium and Long Waves and Extra Band for EASIER tuning of LUXEMBOURG, etc. Top grade 3in. Loudspeaker for quality output. Two R.F. stages for extra boost. High 'Q' 6in. Ferrite Rod Aerial. Approx. 350 Milliwatts push pull output. Handsome pocket size case with gilt fittings. Size 6½ x 3½ x 1½in. (Uses long-life PP6 battery).

This amazing receiver may be built for only **£3.9.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

**QUICK CHECK TRANSISTOR TESTER.** Checks gain of R.F. and Audio Transistors. Also checks for noise level and duds. All parts ready to be assembled in attractive grey case with red grille, complete with Dial, Knobs, and Dynamic Speaker. Simple assembly instructions free with set of parts. 29/6. P. & P. 2/6.



**FAULT TRACER.** A versatile Signal Injector. Something no constructor should be without. This ingenious device generates an audible signal through the Audio and R.F. ranges. With variable output. Telescopic Probe. Pocket size slim line case measures 4½ x 3½ x ¾in. Complete set of parts with full instructions. 19/6. P. & P. 2/-.

### NOW WITH 3IN. SPEAKER! NEW TRANSONA FIVE



"Home, Light, A.F.N. Lux. all at good volume" G.P., Durham  
 ● 7 stages—5 transistors and 2 diodes

Fully tunable over Medium and Long Waves and Trawler Band. Incorporates Ferrite rod aerial, tuning condenser, volume control, new type fine tone super dynamic 3 in. speaker, etc. Attractive case. Size 6½ x 4½ x 1½in. with red speaker grille. (Uses 1289 battery available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

### POCKET FIVE NOW WITH 3in. SPEAKER!



● 7 stages—5 transistors and 2 diodes.  
 Covers Medium and Long Waves and Trawler Band, a feature usually found in only the most expensive radios. On test Home, Light, Luxembourg and many Continental stations were received loud and clear. Designed round supersensitive Ferrite Rod Aerial and fine tone 3 in. moving coil speaker, built into attractive black and gold case. Size 5½ x 1½ x 3½in. (Uses 1289 battery, available anywhere.)

Total cost of all parts now only **42/6** P. & P. 3/6

STOP PRESS!  
 Pocket 5 Med and Long wave version with miniature speaker  
**29/6** P. & P. 3/-

Parts Price List and easy build plans 1/6 (FREE with Kit)

### NEW ROAMER SIX NOW WITH PHILCO MICRO-ALLOY R.F. TRANSISTORS



● 6 WAVEBAND!!  
 ● 8 stages—6 transistors and 2 diodes

Listen to stations half a world away with this 6 waveband portable. Tunable on Medium and Long Waves, Trawler Band and two Short Waves. Sensitive Ferrite rod aerial and telescopic aerial for short waves. Top grade transistors. 3-inch speaker, handsome case with gilt fittings. Size 7½ x 5½ x 1½in. (Carrying Strap 1/6 extra.)

★ EXTRA BAND FOR EASIER TUNING OF LUX, ETC. Total cost of all parts now only **£3.19.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

### TRANSONA SIX




● 8 stages—6 transistors and 2 diodes  
 This is a top performance receiver covering full Medium and Long Waves and Trawler Band. High-grade 3in. speaker makes listening a pleasure. Push-pull output. Ferrite rod aerial. Many stations listed in one evening including Luxembourg loud and clear. Attractive case in grey with red grille. Size 6½ x 4½ x 1½in. (Uses PP4 battery available anywhere.) Carrying Strap 1/- extra.

Total cost of all parts now only **59/6** P. & P. 3/6

Parts Price List and easy build plans 1/6 (Free with kit)

### MELODY SIX

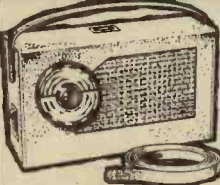


● 8 stages—6 transistors and 2 diodes

Our latest completely portable transistor radio covering Medium and Long Waves. Incorporates pre-tagged circuit board, 3in. heavy duty speaker, top grade transistors, volume control, tuning condenser, wave change slide switch, sensitive 6in. Ferrite rod aerial. Push-pull output. Wonderful reception of B.B.C. Home and Light, 208 and many Continental stations. Handsome leather-look pocket size case, only 6½ x 3½ x 1½in. approx. with gilt speaker grille and supplied with hand and shoulder straps.

Total cost of all parts now only **£3.9.6** P. & P. 3/6 Parts Price List and easy build plans 2/- (Free with kit)

### SUPER SEVEN

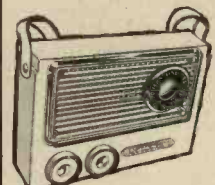

● 9 stages—7 transistors and 2 diodes

Covers Medium and Long Waves and Trawler Band. The ideal radio for home, car, or can be fitted with carrying strap for outdoor use. Completely portable—has built-in Ferrite rod aerial for wonderful reception. Special circuit incorporating 2 RF Stages, push-pull output, 3in. speaker (will drive large speaker). Size 7½ x 5½ x 1½in. (Uses 9v battery, available anywhere.)

Total cost of all parts now only **£3.19.6** P. & P. 3/6

Parts Price List and easy build plans 2/- (Free with kit)

Callers side entrance Barratts Shoe Shop.

## RADIO EXCHANGE Ltd

Open 9—5 p.m.  
 Saturdays 9—12.30 p.m.

61a HIGH STREET, BEDFORD. Phone: 52367

# RECORD HOUSING



Whatever your set-up there's a Record Housing Cabinet to meet your needs. Amplifiers, tuners, turntables, loudspeakers, records, tapes, tape decks and even a complete tape recorder—you name it—we'll house it! The illustration shows our Nielson Equipment Cabinet (19 Gns.) with matching Folded Horn Loudspeaker Enclosure (£11.19.0). These units are only part of the Record Housing range of equipment cabinets, speaker cabinets and record cabinets—send for free catalogue showing 20 different models plus 4 brand new designs to be shown at the Audio Fair or see them now at your local stockist.

**FREE HI-FI HOUSING ADVISORY SERVICE**  
**RECORD HOUSING** (Dept. P.E.4)

Brook Road, London, N.22. Tel.: BOWes Park 7487

## TELEVISION RECEIVER THEORY :

### Part I

A Textbook for Students and Technicians

G. H. HUTSON

35s. net

The first of two volumes which together provide a systematic course in television receiver theory, including a study of both positively and negatively modulated systems and embracing both valve and transistor circuitry.

## ELECTRICAL SCIENCE FOR ELECTRICAL INSTALLATION STUDENTS: Part I

J. A. MYERS

12s. 6d. net

The first of two volumes written to cover the syllabus of Electrical Science for Electrical Installation Course 'B' of the City and Guilds of London Institute. It is also suitable for students preparing for Course 'A' and for other courses where a practical approach to the subject of Electrical Science is required together with an emphasis on calculations.

*A catalogue containing information on all technical publications can be obtained on request from the publisher.*

**EDWARD ARNOLD** 41 Maddox Street, London, W.1

# A New Martin Recordakit

designed specially for the MAGNAVOX 363

3 WATTS OUTPUT

OUTLET FOR HI-FI AMP

SOLDERING NOT NECESSARY

SEPARATE RECORDING LEVEL AND VOLUME CONTROLS



Get the best out of your MAGNAVOX STUDIOMATIC TAPE DECK with a Martin Recordakit assembly. This comprises everything you want to make a superb two or four track 3-speed recorder (taking 7 in. reels) at a price that will save you pounds. The basic Martin units are assembled and tested, making it necessary for you simply to fit and connect them together in accordance with the detailed instructions book supplied. When built, your Martin Recorder appears as shown here. The lid is detachable. Case with speaker, and deck also available. Details on request. MARTIN RECORDAKITS have long been famous for their high performance standards, quality of materials, simplicity and dependability. The latest is the best yet.



KIT M4 less case and deck (four track) but inc. valves, screws, wire, track switching, etc. £15.19.6

KIT M2 less case and deck (two track) but incl. valves, wire, screws, etc. £14.19.6

## Martin Audiokits for Hi-Fi

The uniquely reliable kits with "Add-on-ability"

No other system allows you to enlarge your installation stage by stage as Audiokits do. They comprise a wide range of very well made prefabricated transistorised units in which connections are standardised throughout and from which anything from a simple straight amplifier to an elaborate hi-fi stereo amplifier with FM tuner can be built. The Recordakit described above can be combined with your Audiokit assembly if you wish.

- 5-stage input Selector £27.6
- Pre-amp/vol. control £11.17.6
- Pre-amp/tone controls £3.2.6
- 10 watt amp. (3 ohms) £5.12.6
- 10 watt amp. (15 ohms) £6.12.6
- Mains power supply £2.15.0

### FROM PRE-AMP TO A HI-FI STEREO/FM ASSEMBLY

Martin Recordakits and Audiokits are obtainable from good stockists everywhere. In cases of difficulty please write direct. Trade enquiries invited.

**MARTIN ELECTRONICS LTD** 154/155 HIGH ST., BRENTFORD M'SEX Phone: ISLeworth 1161/2

#### MARTIN ELECTRONICS LTD.

154 High St., Brentford, Middlesex

Full details of  Recordakits  Audiokits please

NAME .....

ADDRESS .....

(Block letters)

P.E.47

## NEW BARGAINS

Moving coil meter, 2 1/2 in. flush mounting 5-0-5 M.A. centre zero, 25/- each.

Moving coil meter, 2 1/2 in. flush mounting 250-0-250 micro amps centre zero, 29/6 each.

50 ohm 50 watt wire wound pot-meter 3/6 each.

20 K wire wound pot-meter, 20 watt type made by Colvren complete with control knob 11/0 each.

1 meg. miniature pot-meter Morganite standard 1/2 in. spindle 1/- each, 9/- per dozen.

1 meg. miniature pot-meter Morganite pre-set screwdriver control, 9d. each, 8/- per dozen.

Pre-set 100 K by Welwyn with Intron bakelite knob, 1/- each, 9/- per dozen.

100 K pot-meter miniature type with double pole switch and standard 1/2 in. spindle, by Morganite 2/- each, 15/- per dozen.

25 K pot-meter standard size with double pole switch by Egan with full length 1/2 in. spindle 3/- each, 36/- per dozen.

Blanketstat glass enclosed, normally closed circuit, will open should blanket overheat, 4/8 each.

Thermal Relay. Can be used to delay the supply of HT while heaters warm up, or will enable 10 amp. loads to be controlled by miniature switches or relays. Regular list price over £2, price 7/6 each.

Siemens high speed relay. Twin 1000 ohm coils. Platinum points changeover contacts. Ex equipment 3/6 each.

Electrolytic condenser, 500 MF 50v. working, 5/- each, 48/- per dozen.

Waterproof heating element, 26 yards length, 70 watt. Self regulating temperature control, 10/- post free.

Footswitch. Two snap-action switches in metal box with flex lead. Ideal to control tape-recorder, tank room lamp, etc. 15/6 plus 2/9 postage and insurance.

Toggle Switch Bargain. 10 amp. 250 volt normal one hole fitting, 2/9 each or 30/- per dozen.

Electric Lock. 24 volt coil, but rewindable to other voltages, 4/6 each.

Compression Trimmers. Twin 100PF, 1/- each, 9/- per dozen.

Miniature Relay. American make. 630 ohm coil 20/30 volt operation. 2 pole changeover, 3/- each, 30/- per dozen.

Precision Wheatstone Bridge. Opportunity to build cheaply. 100K wire wound pot. 15 watt rating only 5/-.

Sheet Facsimile. Ideal for transistor projects. 12 panels each 5 x 8in. 5/-.

3in. PM Loudspeakers. 3 ohm 12/6. 80 ohm 13/6.

Transistor Ferrite Slab Aerial with medium and long wave coils 7/6 each.

Slide Switch. Sub miniature double pole changeover 2/- each, 15/- per dozen.

Masslips (Selsyn) American made transmitter and receiver 27/6 each. Post 4/6 for any one or the pair.

## SEMI-CONDUCTOR BARGAINS

Type	Price	Type	Price	Type	Price
2N1227	15/-	MAT101	8/6	OC71	3/6
2N1228	10/-	MAT100	7/6	OC72	5/-
2N1742	25/-	MAT121	8/6	OC75	6/-
2N1747	25/-	OA5	5/-	OC76	5/-
2N1748	10/-	OA10	6/-	OC77	7/-
AC107	9/-	OA47	3/-	OC78	7/6
AC127	9/-	OA70	2/-	OC78D	5/-
ACY17	6/6	OA79	6/6	OC81	5/-
ACY18	5/6	OA81	2/6	OC81D	5/-
ACY19	6/6	OA85	2/6	OC82	5/-
ACY20	5/6	OA90	2/6	OC83	5/-
ACY21	6/-	OA91	2/6	OC84	8/6
ACY22	4/6	OA90	3/6	OC139	8/6
AF114	7/-	OA202	4/3	OC140	12/6
AF115	6/6	OC22	10/-	OC170	5/-
AF116	7/-	OC23	17/6	OC171	6/-
AF117	5/-	OC24	15/-	OC200	9/-
AF118	10/-	OC26	7/6	OC201	12/6
AF129	12/6	OC26	15/-	OC202	13/6
AF186	17/6	OC29	17/6	OC203	12/6
AFZ12	15/-	OC35	12/6	OC271	15/6
ASZ21	15/-	OC36	15/-	ORP12	8/6
BC107	14/6	OC42	6/6	ORP60	5/6
BY100	4/6	OC44	4/-	SB078	8/6
BZ13	7/6	OC45	3/6	SB305	8/6
MAT100	7/9	OC70	7/-	SB201	10/-

## S.C.R.s (THYRISTORS)

100 v, 1 amp, 6/6, 3 amp, 7/6, 12 amp, 15/-, 400 v, 1 amp, 15/-, 3 amp, 17/6, 5 amp, 22/6, 25 amp, £3, 50 v, 1 amp, 8/6, 3 amp, 7/6, 10 amp, 10/-, 25 amp, 30/-.

**SILICON PLANAR TRANSISTORS**

2N2926 - general purpose type. Suitable for A.F. or R.F. up to 200 mcs, 3/- each or 4 for 10/-.

## SILICON RECTIFIERS

Tested and guaranteed

750mA 100v. 1/3	1 Amp 100v. 3/-
200v. 1/6	200v. 4/6
400v. 3/6	400v. 6/6
3A 100v. 3/6	10 Amp 100v. 9/6
200v. 5/-	200v. 12/6
400v. 7/6	400v. 14/6
600v. 9/6	

Sub miniature glass enclosed—only approx. 1in. long wire ended.

750mA 50v. 1/6	100v. 2/6
200v. 4/6	400v. 6/6

## FLUORESCENT LIGHT KITS

Comprising choke, lampholders, starter and two chrome tube clips. 20 watt 19/8, 40 watt 11/6, Super Silent 40 watt 17/6. 80 watt 17/6. 55 watt 19/6. All 4/6 P. & P.

## HEAT AND LIGHT UNIT

Bring luxury to your bathroom—have comforting heat where you now only have light—all the parts to build a full size (16in. diameter) model are now available—you will build it in an hour—12in 750 watt circular silica glass encased element—opal bowl for up to 100 watt lamp—non-rust spun reflector—white enamelled base heat shield—pull switch—magnificent unit as sold normally at £4.5.0 only 49/6 plus 7/6 carr. and insurance.



## NIM COMPUTER


This computer will play games and do simple tricks and will provide endless amusement as well as education into computerisation. Kit comprises all the components, the printed front panel and full instructions. The box is not included but this can be made very simply from plywood. Price £4.17.6 plus 3/6 post and insurance.


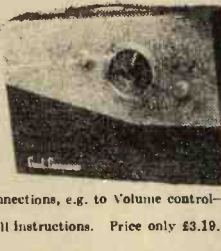
## SUPERTONE G.C.V.

Saves you work—It's partly built Like its predecessors this latest Companion has full f/p performance—such as only a good wooden cabinet and biflux speaker can give, and due to its being partly built you will have it going in an evening. Note these features:

- All Mullard Transistors including 3 x AF117.
- Two-tone Cabinet, size 11 x 8 x 3in.
- All circuit requirements—Push pull output—A.V.C. and feed back, etc.
- Printed circuit board all wired only connections, e.g. to Volume control—W.C. Switch and Tuning Condenser.
- Pre-aligned IF stages complete with full instructions. Price only £3.19.8 plus 6/6 post and insurance.



## THIS MONTH'S SNIP

### THE VECTRONOME CAPSTAN DRIVEN TAPE RECORDER



This is a truly portable self-contained instrument with built-in microphone and loudspeaker using a 7 transistor amplifier with P.P. output and suitable for operation from mains or by chargeable batteries. Tape capacity is 25 minutes on easily change spools.

A tape position indicator gives quick reference to any part of dictation. Recording level is automatically preset during dictation and can be adjusted to suit operator. Interlock prevents unintentional erasures. Tape speed controlled by fly wheel driven capstan. Very portable in neat case with carrying handle, overall size of which is approximately 8 1/2 x 7 1/2 x 2in. Price with tape and mains unit but less batteries, £5.19.8 (rather less than 1/3 original price). Postage and insurance 7/6. Unusual and in perfect working order.

## F.M. TUNER

of exceptional quality, giving really fantastic results with virtually no noise. Suitable for mains or battery operation. 6 transistors—three IF stages—double tuned discriminator. Complete, new, and built up all ready to work on chassis. Size 6in x 4in. x 2in. with tuning scale and slow motion drive. A £12.12.0 tuner for only £8.10.0.



## FINE RECORD PLAYERS ARE GARRARDS



and because they have been making record players for so long, GARRARD are your best choice—big range always in stock.

2000	£6 9 6	LAB80	£25 0 0
3000	£7 19 6	SRP12	£3 9 0
AT60	£11 11 0		Complete with service sheet and template.
SP25	£10 9 0		

## HALF PRICE PROPRIETARY TAPES

brand new, unused and guaranteed perfect and not second in any way—a connoisseur's tape on normal spools and in normal boxes.

Standard Play 5in.	600ft 9/-	Long play 5in.	900ft 11/6
	3in.	900ft. 11/6	5in. 1,200ft. 18/-
			7in. 1,800ft. 23/-

£3 post free otherwise add 2/- post and ins.

## MINIATURE WAFER SWITCHES

### Number of Positions

1 pole	2	3	4	6	12
2 pole	3/6	3/6	3/6	3/6	3/6
3 pole	3/6	3/6	3/6	3/6	3/6
4 pole	3/6	3/6	3/6	3/6	3/6

Any 12 switches ordered together 40/-.

## MAINS TRANSISTOR POWER PACK

Designed to operate transistor sets and amplifiers. Adjustable output 6v. 9v. 12 volts for up to 500 mA (class B working). Takes the place of any of the following batteries: PP1, PP3, PP4, PP6, PP7, PP9, and others. Kit comprises: mains transformer-rectifier, smoothing and load resistor, 5,000 and 500 mfd. condensers, Zener diode and instructions. Real snip at only 14/6, plus 3/6 postage.

## HI-FI SPEAKER BARGAIN

12in. High fidelity loudspeaker. High flux permanent magnet type with either 3 or 15 ohm speech coils. Will handle up to 10 watts. Brand new by famous maker. Price 29/6 with built-in tweeter 36/- plus 3/6 post and insurance.



## TUBULAR HEATERS

New and unused made by G.E.C. rated at 60 watts per ft.—these are ideal in airing cupboards, bedrooms, offices, stores, greenhouses, etc., curtains or papers can touch them without fear of scorching or fire. Supplied complete with fixing brackets and available in the following sizes. Prices which are about 1/2 of list price includes carriage by B.R.S. 8ft. 30/-; 10ft. 36/-; 12ft. 42/-.

Also in twin assemblies (one pipe above the other) 4ft. 40/-; 5ft. 46/-; 6ft. 52/-.

## 750mW TRANSISTOR AMPLIFIER

4 transistors including two in push-pull input for crystal or magnetic microphone or pick-up—feed back loops—sensitivity 5 mV.

Price 19/6 Post and insurance 2/6. Speakers 3in. 12/6; 5in. 13/6; 6 x 4in. 14/6.

## PHOTO ELECTRIC KIT

All parts to make light operated switch/burglar alarm/counter, etc. Kit comprises printed circuit, Laminated Boards and chemicals, Latching relay, Infra-red sensitive Photocell and Hood, 2 Transistors, cond., Terminal block, Plastic case, Essential data, circuits and P.C. chassis plans of 10 photo electric devices including auto. car parking light, modulated light alarm, simple invisible ray switch—counter—stray light alarm—warming tone electronic alarm—projector lamp stabiliser, etc., etc. Only 39/6 plus 2/- post and insurance.

## 2 1/2kW FAN HEATER

3 heat positions to suit changes in weather: 1kW, 1 1/2kW and 2 1/2kW; also blows cool for summer. Has thermostatic safety cut out "Proper" twice £5.17.6. Yours for only £3.15.0. Plus 7/6 post and insurance.



## MOVING COIL METER BARGAIN

Panel meters are always being needed and they are really costly when you have to buy them in a hurry—so you should take advantage of this offer: 2in. moving coil flush mounting meters only 5/6. These are actually R.F. meters and cost about £3 each but if you don't want them for R.F. then all you have to do is to remove the thermocouple and you will have a 2-3 ohm meter which you can make into almost anything by adding shunts or series resistor. These are ex-Government, of course.

PF3 Eliminator—play your pocket radio from the mains! Save £s. Complete component kit comprises 4 rectifiers—mains dropper resistances, smoothing condenser and instructions. Only 6/6 + 1/- post.

## SEED AND PLANT RAISING

Soil heating wire and transformer. Suitable for standard size garden frame. 19/6 plus 3/6 post and ins.

## NEON MAINS TESTER

Good length leads 2/6. Where postage is not definitely stated as an extra then orders over £3 are post free. Below £3 add 2/6.

# ELECTRONICS (CROYDON) LIMITED

(Dept. PE), 102/3 TAMWORTH RD., CROYDON, SURREY (Opp. W. Croydon Stn.)

also at 266 LONDON ROAD, CROYDON, SURREY

# Which type of Shopper are you?



Poor shopper "A" looks ready to die of exposure; while the worst that can happen to "B" is that, being so absorbed in his Home Radio Catalogue, he might burn his toast! The fact is that "A", in spite of his brave search for all the electronic components he needs, may return with only a shocking cold to show for his trouble; whereas "B" can order in leisure and comfort, knowing that all his requirements will be supplied within 24 hours.

You too can join the merry throng of contented "B"'s (there must be about 80,000 of them!). It's very simple; just post off the coupon with 9/- P.O. or cheque (7/6 + 1/6 P & P) and before you can say "There's no place like Home" you'll receive your Home Radio Catalogue, which automatically makes you a fully paid up member! And remember—each catalogue contains 5 vouchers worth a total of 5/- if used as directed. So what are you waiting for?

Please write your Name and Address in block capitals

Name.....

Address.....

Home Radio Ltd., Dept. PE, 187 London Rd., Mitcham, Surrey  
CR4 2YQ



## FALSE ECONOMY

WHICH consideration is uppermost in most amateurs' minds when the building of a piece of equipment is contemplated—is it technical performance, or is it cost?

Just as when purchasing a piece of commercially made equipment, "you get what you pay for" broadly speaking. But in this case you are paying for materials alone. (Other considerations apart, there is always a built-in economy in any self-made equipment since the labour is free; indeed, this provides an additional bonus in the form of the pleasure and satisfaction arising from a job well done.)

The amateur is thus left to decide whether the material cost is of prime importance, or whether the aim first and foremost is to achieve a performance and reliability of a high standard of excellence.

Certainly the materials involved and hence the cost of the project cannot be lightly regarded in any case, particularly if one is without an accumulated stock of components upon which to draw. The amateur will naturally enough look for a design which is not unnecessarily extravagant in components, but which will provide the desired performance.

This is where a pitfall looms for the unwary. . . . Superficial examination of a particular circuit diagram may provoke the thought that this could be reduced to a simpler form and considerable economy thus effected in component costs.

Often it is very tempting to see if the desired function can be obtained with a more rudimentary form of circuit. A component or two may appear superfluous in the published design and indeed the device may operate (apparently quite efficiently) without their aid. Alas, the initial good fortune of the innovator may well prove to be but an illusion and sudden failure or deterioration in performance, or the emergence of other defects, may cause unwarranted incriminations to be levelled at the original designer!

We would be the last to discourage individual enterprise. Published designs are frequently amenable to modification—sometimes for the better. But we do suggest that the would-be innovator makes certain he is well acquainted with the philosophy underlying the circuit design and that the intention of the original designer is understood before seeking to effect improvements.

This caution applies equally well whether the motivation to introduce changes arises from economic or from technical considerations.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

MILK-O-STAT	260
FIELD STRENGTH METER	268
VALVE VOLTMETER AND OHMMETER	279
DOOR SLAVE	288

### SPECIAL SERIES

THE ELECTRONIC ORGAN—5	271
------------------------	-----

### GENERAL FEATURES

ULTRASONICS AT WORK	256
INGENUITY UNLIMITED	264
COMPONENT SELECTION CALCULATOR	267
THE OSCILLOSCOPE AND ITS APPLICATIONS	294

### NEWS AND COMMENT

EDITORIAL	255
MARKET PLACE	278
ELECTRONORAMA	286
NEWS BRIEFS	305
DETACHED PARTICLES	306
READOUT	309

*Our May issue will be published on  
Friday, April 14*

# ULTRASONICS

By C. P. Wright


Dawe Instruments Limited

ULTRASONICS—acoustic energy above the hearing range of the normal human ear—has been in use for several years, although the discovery of new applications is still a common occurrence. The actual working power of ultrasonics is obtained when the ultrasonic sound energy is converted, by a transducer, into mechanical energy at the same frequency, i.e. above 20,000Hz.

There are two main ways in which this power is employed, the first being the use of the vibration as a means of performing a task and the second, by using the energy as the active part in various non-destructive testing techniques. The frequency ranges for these operations being ideally 20–40kHz for the former and 1–15MHz for the latter.

In order to give a clear picture of the practical uses of ultrasonics the two sections are described separately. First, ultrasonic agitation, incorporating ultrasonic cleaning, plastics welding, and processing. Second, non-destructive testing of materials incorporating thickness measurement, flow detection, and leak detection.

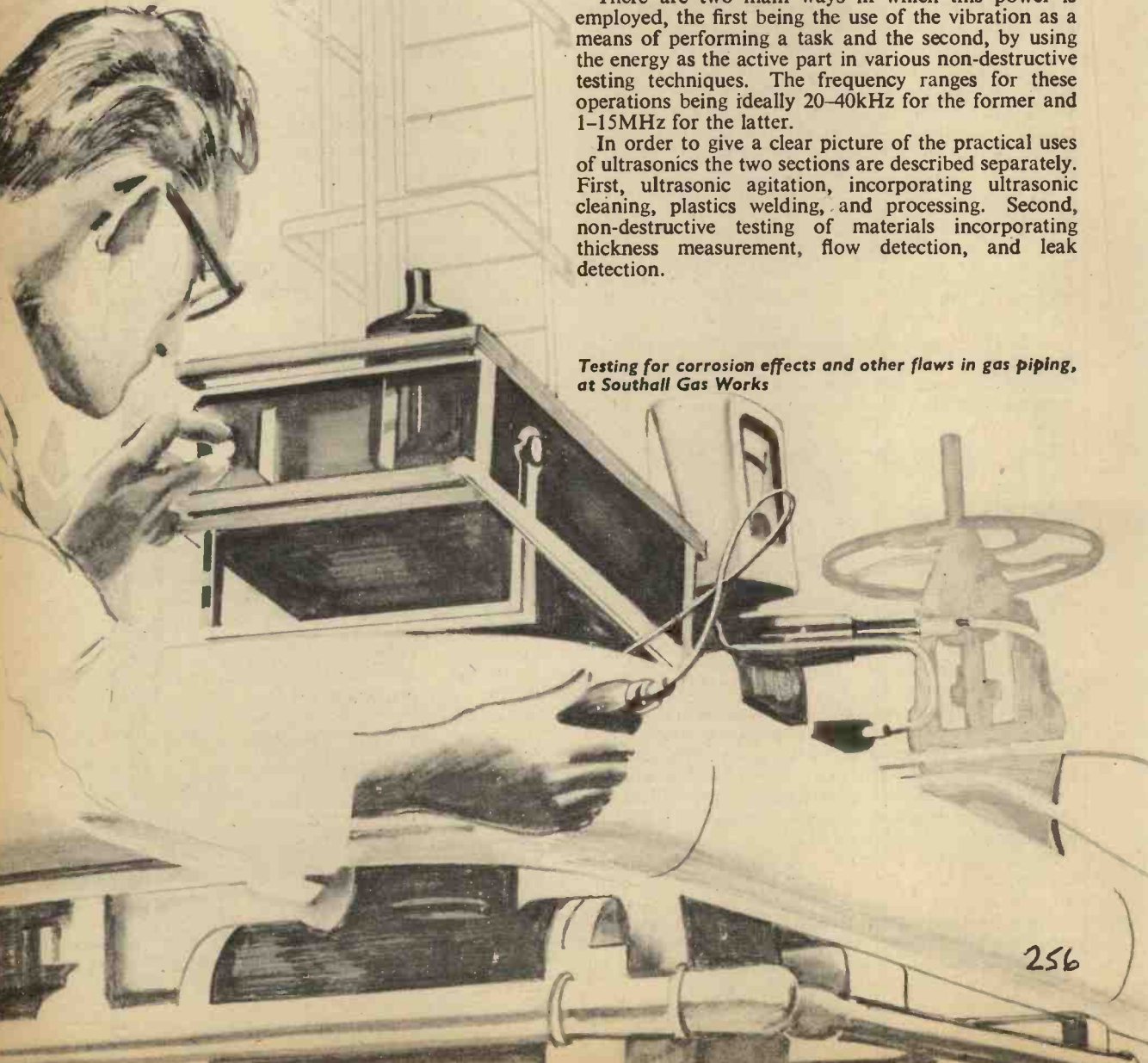*Testing for corrosion effects and other flaws in gas piping, at Southall Gas Works*



# AT WORK

## ULTRASONIC CLEANING

Ultrasonics provides an unrivalled method of cleaning small and delicate parts, large complex castings and even complete assemblies both quickly and thoroughly without risk of damage.

Three basic components are required, an ultrasonic generator or power supply, a transducer and a cleaning tank. A high voltage at a frequency of, say, 25kHz from the generator is applied to the transducer, where it is converted into mechanical vibrations of the same frequency.

The active part of the transducer is a piezo-electric, ceramic, or magneto-strictive element having a very high transfer efficiency (electrical energy to mechanical energy) which will physically vibrate when the output from the generator is applied to it. Multiples of these transducers are attached to the underside of the radiating surface of either a stainless steel cleaning tank or a waterproof immersible container.

The ultrasonic energy from the transducer is transmitted into the cleaning fluid where, at a sufficient power level, the liquid will be caused to cavitate. The cavitation of the liquid produces a scrubbing action on the surface of the part to be cleaned and removes extremely tenacious soil.

There are many occasions where the part to be cleaned has some almost inaccessible surfaces, e.g. complete electrical assemblies or blind holes in complex castings. The ultrasonic vibrations will penetrate even the smallest crevice.

A recent development uses automatic generators which are self-tuning to give high cleaning efficiency regardless of changes in the operating conditions of the cleaning tank, i.e. load, liquid level, temperature. This type of generator is suitable for production line cleaning. In some instances, the application demands special treatment which is not suited to a standard generator and cleaning tank combination. In such cases special ultrasonic cleaning units, incorporating several generators, tanks, filters and ancillary equipment are usually designed by the manufacturer.

To take an example, a unit has recently been installed to clean stainless steel hypodermic needles. The point of the needle is formed by a grinding process during which time each needle, held on a piece of sticky tape, picks up swarf or grinding wheel abrasive which is removed by ultrasonic cleaning. The taped needles are rolled and placed vertically into a tray which is immersed into each tank in turn.

The first tank contains an alkaline solution. The second tank rinses this solution off the needle by using hot water. The third tank contains a heated acid solution and is agitated by ultrasonic transducers. The tank is fitted with two immersible transducers, which are driven by a manually tuned ultrasonic generator, having an average power output of 300 watts, housed at the end of the console.

The fourth tank contains a hot water rinse and the needles are finally rinsed in de-ionised water in the fifth tank.

The solutions in the first, third and fourth tanks are continually filtered, the filter for the third tank being designed to remove all particles larger than 5 microns (approximately 0.0002in).

## PLASTICS WELDING

Similarly it is possible to weld together rigid thermoplastic parts without the use of solvents, adhesives or heat. The ultrasonic energy is transformed into mechanical vibrations by the vertically mounted transducer. The ultrasonic vibrations, emitted from the horn, are coupled into the plastics by touching the tip against either of the two parts being joined. The vibrating plastics remains perfectly cool, except at the periphery, where there is a rapid dissipation of energy and an instantaneous weld occurs around the periphery of the object.

This process was introduced to this country fairly recently for the manufacture and assembly of two-tone plastics bowls. Each bowl consisted of an injection moulded inner and outer skin, joined together at the rim by ultrasonic welding. No finishing operation is necessary after welding.

Further developments are currently being carried out on this technique and it has already been found possible to weld metal inserts into plastics by ultrasonics.

## ULTRASONIC PROCESSING

The use of ultrasonic power for processing biological cells, performing or accelerating chemical activity in liquids or for other similar operations is performed by a similar system to that used for ultrasonic cleaning.

A generator converts the electrical input to ultrasonic power at about 20kHz and this is fed to a vertically mounted sonic converter, the active element of which is a piezo-electric ceramic, lead zirconate titanate, which transforms the ultrasonic power to mechanical vibrations. Energy from the transducer is concentrated and intensified by a "step-horn" and focused in the tip. The resulting energy radiates from the tip into the material being treated.

Using this equipment, with adjustment to output level and period of application, it is possible to perform the following processes: the disruption of individual cells; the homogenisation of cell components; the fragmentation of tissue into its component cells; the acceleration of enzymatic and chemical activity; the stimulation or inhibition of bacterial activity; the homogenisation and emulsification of immiscible liquids; the dispersion of solids in liquids and the de-gassing and de-aerating of liquids.



*Vertical sonic-converter, fitted with a "step-horn" to intensify the energy*

## NON-DESTRUCTIVE TESTING

Over the past decade, ultrasonics has become an established science for testing, gauging, quality control and maintenance in many forms of industry. The basic theory behind its use is in the interpretation of the behaviour of vibrational waves in materials.


From this information it is possible to measure the thickness of the material, successfully detect and locate flaws and discontinuities, obtain knowledge of the material's own properties and determine its hardness. Recent developments have enabled accurate location of leaks from pressurised vessels to be made.

## THICKNESS GAUGING AND FLAW DETECTION


There are two basic methods of testing by ultrasonics which are classified as pulse-echo and resonance techniques.

The operating principle of the pulse-echo technique is similar to that used for measuring the depth of the sea. An electrical pulse is generated in the instrument and transmitted, via a cable to the transducer. There it is converted to mechanical energy and transmitted through a "coupling", normally oil, water or

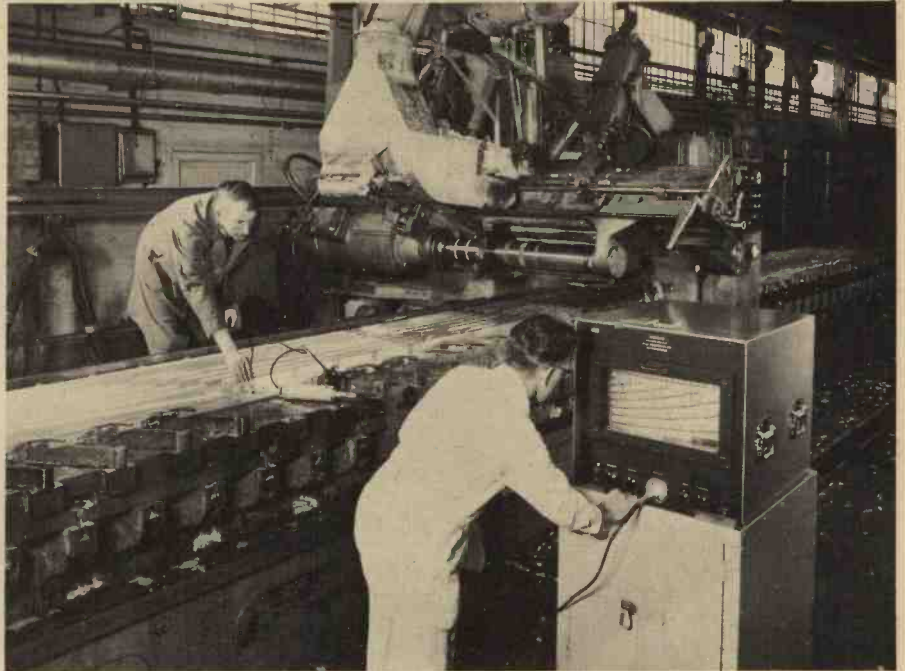*Thickness gauge employed in production line testing of aircraft wing components*



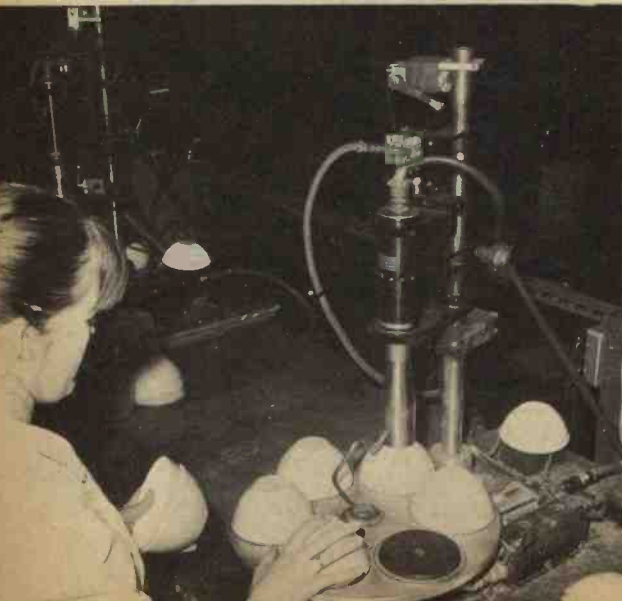*Ultrasonic plastics welding equipment being used for joining two colour skins of plastics bowls*



glycerine, into the material to be tested, as a pulse of high frequency sound.

The ultrasonic pulse continues through the material until it strikes a reflecting boundary. This could be the far side of the material or a flaw which obstructs the course of the beam. It is then reflected back to the transducer where the sound energy is converted back into electrical energy and returned to the measuring unit.

Signals from the test piece are amplified and displayed on a cathode ray tube as vertical deflections of the timebase. The position of a flaw signal, in relation to the initial pulse, is proportional to the depth of the flaw in the part. The magnitude of the flaw signal indicates the relative size of the flaw.

This type of instrument is used for flaw detection and thickness gauging up to 450 inches in, for example, large complex machinery or castings.

## RESONANCE TECHNIQUE

The resonance method of thickness gauging is ideal for very thin materials and is carried out by an instrument consisting of a sweep oscillator which generates a signal which is converted into ultrasonic power to drive a transducer coupled to the material as before. However, with this method the energy is transmitted as part of a continuous wave train.

Each material of a given thickness has its own natural resonant frequency. At this frequency (or multiples of it), when the transmitted and reflected waves are in phase, there will be a relatively large increase in the amplitude of the waves in the material. When the material is under resonant conditions, occurring at the fundamental frequency applied, the thickness is determined by its inverse relationship to this frequency, which is also directly proportional to the velocity of sound in the material.

The material is also resonant to a lesser degree at harmonics (multiples of the fundamental frequency). Since the velocity of sound in a given material is a known constant, the fundamental frequency required to produce resonance is an accurate and reliable measure of an unknown thickness.

As the oscillator sweeps through the resonant frequency of the material, or any harmonics of this frequency, a vertical resonance indication appears on a cathode ray tube display. Accuracies can be very high with this technique, in many cases it is possible to measure to within 0.001 in.

## MATERIALS TESTING

The ultrasonic testing of heterogeneous materials, such as concrete, timber, rock, and graphite, is performed by using a comparatively low ultrasonic frequency and transmission technique.

Vibrational waves in the frequency range 60kHz to 150kHz are injected into the material and the velocity of their propagation measured. The transmitting and receiving transducers are held in contact with opposite faces of the material, which may be up to 10ft thick. The time taken by the vibrations to traverse the material is measured by the associated equipment to an accuracy of  $\pm 0.1$  microseconds.

As the leads from the transducers to the main instrument may be up to 100ft long there is no difficulty in using this method to evaluate very large structures, such as the walls of a concrete building.

## HARDNESS TESTING

A far more recent development than those described so far is the ultrasonic method of determining the surface compliance or hardness of material, particularly metal.

A diamond tipped magnetostrictive rod is resonated at its natural frequency of about 18 to 20kHz, depending on the dimensions of the rod. When the diamond tip is brought into contact with a workpiece, using a predetermined engagement pressure, the diamond slightly penetrates the surface of the testpiece.

This penetration shortens the effective length of the rod, thereby causing the resonant frequency of the rod to shift to a higher value. Since, under constant pressure conditions, the penetration of the diamond tip is proportional to the hardness of the material, the amount of the frequency shift indicates this degree of hardness.

This method leaves a surface indentation of less than 0.005 in and therefore, since it is so minute, it is well within the bounds of the term "non-destructive" and very much smaller than with conventional methods. Unlike mechanical testers this type of equipment does not require optics, high pressure, or an impact force for measurement.

## LEAK DETECTION

Ultrasonic energy is generated by gas or steam as it leaks from any pressurised container. The frequency of this energy depends on the velocity of the escaping gas, which in turn is dependent on the pressure and the dimensions of the orifice. In all cases, however, there is a broad frequency spectrum in the 40kHz region and this fact may be utilised even though there may be considerable audible sound in the same area.

The detector consists of a highly directional ceramic microphone type transducer which is coupled to a tuned 40kHz transistor amplifier. Visual and audible output is indicated on a meter and headphones when the instrument is directed towards a leak. The accurate location of the leak is then determined by following through in the direction of the source of ultrasonic energy. By using this technique it is possible to locate accurately a leak from an orifice as small as 0.01 in diameter at a pressure of less than 10 lb/in<sup>2</sup> at a distance of 45 ft. ★

*The location of a leak is now nearing completion with the Ultrasonic Leak Detector*





ARE YOUR "SOFT" EGGS ALWAYS HARD?  
 DOES OVERFLOWING BOILING MILK ON  
 THE COOKER ALWAYS ANNOY YOU?  
 DO YOU DISLIKE OVERCOOKED FOOD?

**LET THE MILK-O-STAT TAKE THE WORRY OUT OF IT ALL!**

**T**HE Milk-o-Stat can be very loosely termed an electronic thermostat. It incorporates a uni-junction transistor timer and a heat sensitive bridge amplifier to control a thyristor operated alarm.

When in operation, the Milk-o-Stat is designed to emit an audible warning in the following cases:

- (a) Whenever the liquid being boiled reaches a certain predetermined temperature, e.g. when the milk is about to boil over;
- (b) whenever a certain prearranged time has lapsed;
- (c) After a combination of cases (a) and (b).

As well as giving an audible alarm the Milk-o-Stat automatically switches itself off. This minimises human error and power consumption. The saving in battery life is thus considerable. Under normal conditions of use the battery should last well over a year.

**HEAT MONITOR**

The circuit diagram of the Milk-o-Stat is shown in Fig. 1. The essential sensing element is a thermistor  $R_x$ , an obvious choice for its heat sensitive characteristics.

This is coupled to the base circuit of TR1—a *pnp* type directly coupled to the *npn* transistor TR2 to form a high gain "unbalance" amplifier. TR1 and TR2 are combined with a Wheatstone bridge network comprising  $R_1$ ,  $R_x$ , VR1, and R2. Transistor TR1 detects any unbalance in the bridge and passes a current on to TR2 to be amplified to operate the relay.

With reference to Fig. 1, suppose VR1 is set so that the resistance between points A and B equals the resistance between points B and D. Also assume that the temperature is such that the resistance of the thermistor equals the resistance of  $R_1$ .

From simple potential divider principles, it will be observed that the emitter and base of TR1 are at the same potential. Little or no current thus flows into the base of TR2 and this transistor is effectively cut off. The relay in the collector circuit of TR2 remains off also.

Suppose now that the slider of VR1 is moved towards the positive end of its track. The base of TR1 effectively becomes more negative with respect



**MILK-O-STAT**

By  
**Peter B. Walker**

# COMPONENTS . . .

## Resistors

R1 6.8k $\Omega$  5%  $\frac{1}{2}$ W high stability  
 R2 560 $\Omega$  R4 33 $\Omega$   
 R3 47 $\Omega$  R5 220 $\Omega$   
 All 10%  $\frac{1}{2}$ W except R1

## Potentiometers

VR1 5k $\Omega$  linear wirewound  
 VR2 100k $\Omega$  log. carbon with d.p.s.t. switch S2

## Capacitor

C1 1,000 $\mu$ F elect. 15V

## Thermistor

R<sub>x</sub> VA1010 (Mullard) or TH6 (Radiospares)  
 9.6k $\Omega$  cold, 240 $\Omega$  at 100mA hot

## Thyristor

SCR1 50V 1A (e.g. type SCR01 International Rectifier)

## Transistors

TR1 OC44  
 TR2 OC139 or 2N1302  
 TR3 OC71  
 TR4 2N492 or 2N2160

## Diode

D1 OA81

## Relay

RLA 185 $\Omega$  6V with 2 pole changeover contacts  
 (Keyswitch Relays Ltd.)

## Switches

S1 Single pole on/off push button  
 S2 Double pole on/off ganged to VR2

## Battery

BY1 9V type PP9

## Plugs and Sockets

PL1, PL2, PL3 Wander plugs (3 off)  
 SK1, SK2, SK3 Sockets for wander plugs (3 off)

## Miscellaneous

Veroboard 0.15 in matrix  $2\frac{1}{2}$  in  $\times$   $3\frac{3}{4}$  in  
 Plywood for case (see text)  
 Laminated plastics sheet (see text)  
 Miniature Terry clips (2 off)  
 Glass tube—0.25in bore  
 Pointer knobs  
 Battery connectors

to the emitter. TR1 is now forward biased. The base of TR2 will become progressively more positive and TR2 also will become forward biased. Increased current will flow in TR1 collector and when a sufficient value of current has been reached, say 8mA, the relay will switch on.

The circuit is now primed ready for operation. The thermistor, mounted in a suitable waterproof tube is immersed in the liquid to be boiled. As the temperature of the liquid rises, the resistance of the thermistor will drop. When the liquid reaches boiling point, and assuming VR1 has been set correctly, TR1 will cut off

again, followed by TR2. The relay will release, turning off the Milk-o-Stat via RLA1. At this point it is arranged that an audible warning signal is brought into operation via RLA2 contacts, a warning which summons the housewife to tell her the milk is ready.

## PRESET TIMER

With S2a and S2b closed, the time circuit is switched on. By varying the value of VR2 any time delay from a few seconds up to five minutes can be obtained.

An important feature of the unijunction transistor TR4 is the high impedance across the base 1-emitter


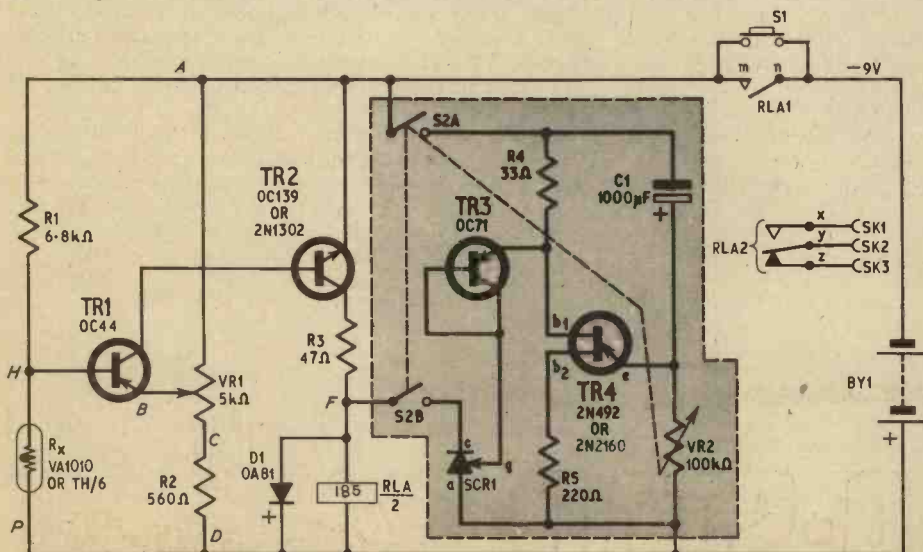


Fig. 1. Complete circuit diagram of the Milk-o-Stat. The shaded area is the timer section of the circuit which may be excluded if not required

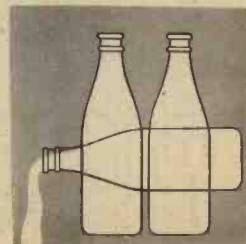

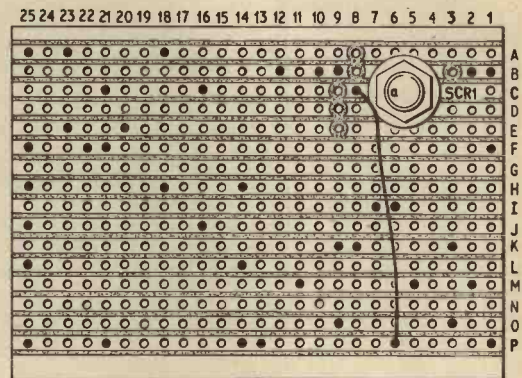
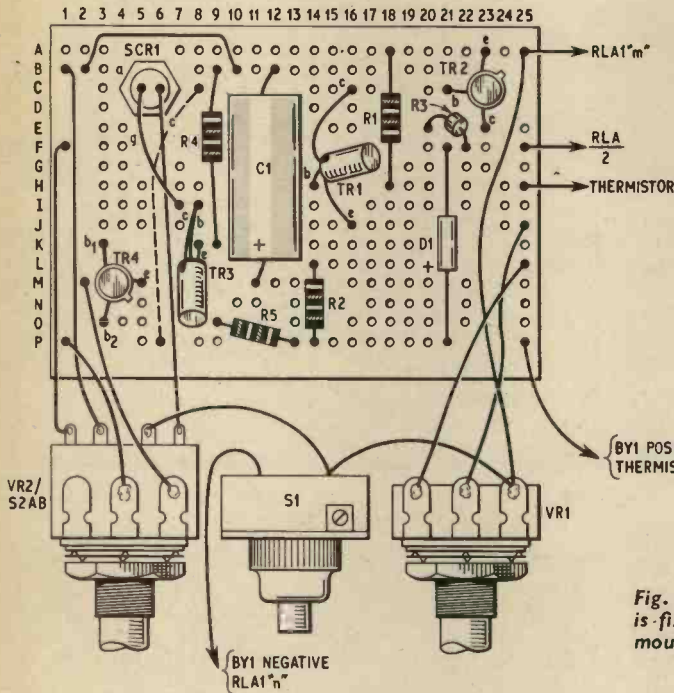


Fig. 2. Layout of the components on the board. The relay is fixed to the case; the controls VR1, VR2, and S1 are mounted on the sloping front panel

junction. However, as C1 charges up through VR2, the potential of the eb<sub>1</sub> junction will rise progressively. When the emitter reaches a certain potential, say 6 volts positive with respect to b<sub>1</sub>, the resistance of the junction will suddenly drop to a very low value, and C1 will discharge through this junction and R4. The resultant sharp-edged positive going pulse is applied to the gate of the thyristor SCR1 via TR3, and triggers the thyristor into the on state. Thus, after the specified time delay, SCR1 fires, shorting out the relay and turning it off.

The relay "hold" contacts are simultaneously broken, and the Milk-o-Stat thus turns itself off. R3 acts as a current limiting resistor to ensure that TR2 is not overloaded when SCR1 fires. TR3 is an OC71 wired up with its base and collector strapped together. Wired in this mode, TR3 acts as a diode with a very low forward resistance, typically 10 ohms. This ensures that the SCR1 gate receives adequate trigger current of the correct polarity.

**AUDIBLE WARNING**

For optimum simplicity, reliability, and minimum cost, an existing battery transistor portable radio would be a good choice for the audible alarm. Even a small transistor radio tuned to a suitable station could make enough noise to be heard by the housewife.

A simple way of adapting your radio to operate in conjunction with the Milk-o-Stat is to connect points

x and y (SK1 and SK2) or y and z (SK2 and SK3) of RLA2 contacts in series with the radio battery. An electric bicycle horn or electric bell will function just as well if a radio set is not available. The important point is that audible warning must be given immediately the relay operates, therefore valve radio sets are unsuitable.

**AUTO-HOLD**

Auto-hold is achieved by S1 in parallel with RLA1 contacts. By pressing S1, the momentary contact switch, the Milk-o-Stat relay is activated, and RLA1 closes holding the circuit on. When RLA is released the auto-hold circuit is opened and the Milk-o-Stat turns itself off automatically.

**ASSEMBLING THE COMPONENTS**

The circuit was built up on a piece of Veroboard 3.75in x 2.5in (Fig. 2). The positions of the components are not critical and the actual wiring up of the circuit presents no particular problems.

The thermistor used is fairly sensitive to changes in temperature and can be obtained quite cheaply.

It is housed in a piece of glass tubing which is sealed at one end (See Fig. 3). The glass tubing is about 5in long with an inner diameter of 0.25in, sufficient to accept the thermistor and a thin wire side by side. The tube is carefully sealed by heating the glass at one end until it melts



After sealing the tube and allowing it to cool, test to see if it is watertight by holding the sealed end under running water, and check for any water droplets in the inside of the tubing. If any water droplets are found, heat the end of the tubing again and repeat the test procedure until the seal is watertight. It is essential for the reliable operation of the Milk-o-Stat, that no water comes into contact with the sensitive thermistor.

The case for the Milk-o-Stat is made from stout plywood with the following dimensions:

- (a) Baseboard 6in × 4in × ½in thick;
- (b) Side panels 6in × 3in × ¼in thick;
- (c) Back panel 5in × 3in × ¼in thick.

The top, sloping front, and trim front pieces are laminated decorative plastics sheet such as Formica or Waverite (see heading picture). These pieces are cut to fit after the wooden panels are glued and pinned together.

Before finally fitting the plastics panels, drill appropriate holes to accept the controls VR1 and VR2 (½in diameter), the push button switch S1 (to suit component size), and 6 B.A. clearance holes (No. 32 drill) for Terry clips to hold the probe sensor. The exact positions of these is not important. Wander plug sockets are mounted on the side of the box to provide connection between RLA contacts and the external audible warning device.

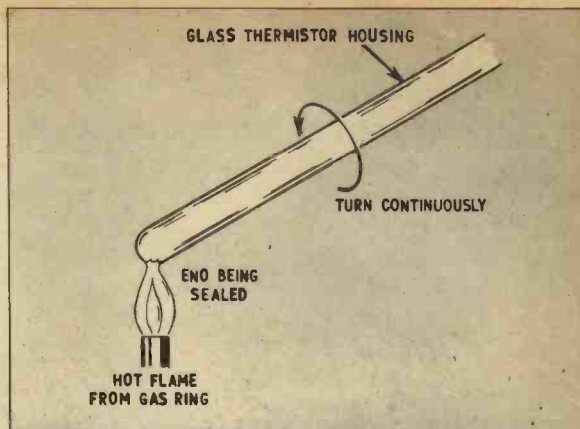


Fig. 3. The glass tube is heated by a bunsen burner or gas ring to seal the end

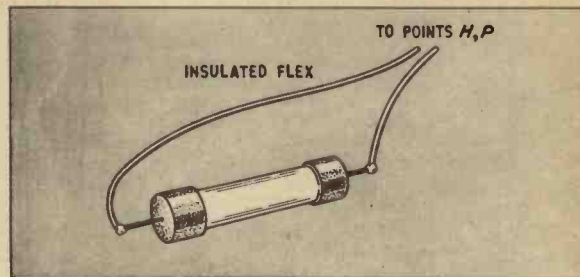


Fig. 4. The thermistor has flexible wires connected to it before insertion in the glass tube

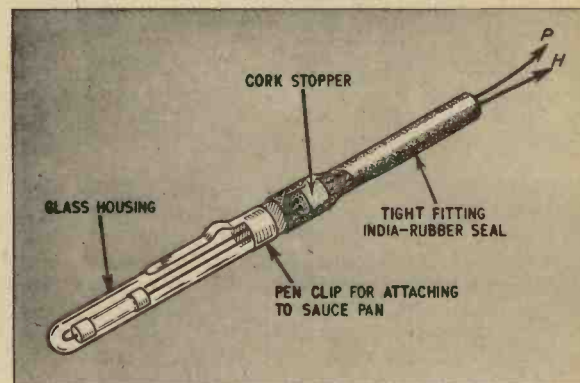


Fig. 5. The finished probe with pen clip for attaching to the pan and rubber seal to exclude moisture from the thermistor

## CALIBRATION AND SETTING-UP PROCEDURE

1. Check that the timer is switched off.
2. Insert an ammeter (0–20mA) between relay RLA and the positive pole of the battery.
3. Connect up battery.
4. Set VR1 to about the mid-position of the track.
5. Press S1 to switch the unit on.

Put the sensor in cold milk and gradually bring to the boil. The current should gradually drop from 15mA to 5mA as the temperature of the milk increases.

Ideally the Milk-o-Stat should turn itself off when the milk is about to boil. However, if the alarm sounds too early, i.e. before boiling point is reached, turn VR1 slider a little more to the positive end (clockwise). If the alarm sounds after the milk is boiling, turn VR1 slider counter-clockwise.

When the slider has been correctly positioned, calibrate VR1, marking the point found as "MILK". Similarly calibrate for water or any other requirement.

For various positions of VR2 note the time delay accurately, using a watch with a seconds hand, and mark the time delays so found on VR2 dial.


It is advisable to keep the glass probe scrupulously clean. This can be done by rinsing in warm water then inserting into Milton. Never insert the tube into boiling water rapidly.


Do not let any part other than the glass tube come into contact with food or water for the sake of hygiene.
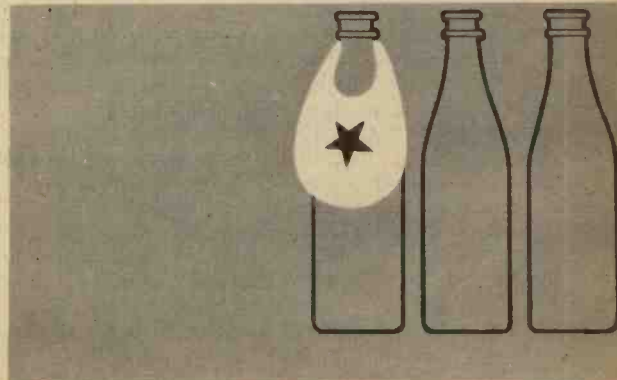
## BOILED!

There should be no more mess now! Switch on the Milk-o-Stat, tune in to your favourite radio programme, put the milk pan on the cooker—and walk away. Use the Milk-o-Stat as an egg timer: a 3 minute egg will be soft, a 5 minute egg should be hard. You can tell when the water for boiling the egg boils—an electronic "whistling" kettle! All you need to do is to repeat the calibration procedure, but using water.

As a short period timer the Milk-o-Stat should also come in very handy in the amateur photographer's dark room.



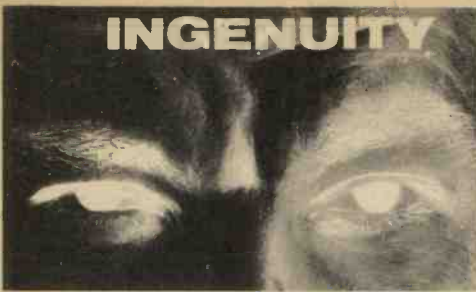


IN THIS feature we hope, from time to time, to be able to publish suggestions submitted by some of our readers on the possible improvement of projects previously described in PRACTICAL ELECTRONICS; short contributions on other subjects may be included. The aim is not to find fault or undermine the abilities or knowledge of our contributors. It may well be that the original article is *par excellence* but it could be improved or adapted to suit individual requirements. The views expressed by readers are not necessarily those of the Editor.

## RELIABLE SYNCHRONISER

I THOUGHT you might be interested in a modification that I have made to the *Slide Synchroniser* project that you published in September 1965. I made this synchroniser about a year ago, but was unable to obtain the small 150 ohm relay mentioned. The nearest I could get was a somewhat cumbersome 150 ohm Post Office type. Whereas this was operated satisfactorily by the pulse direct, it was a chancy business when the recorded pulse was in operation.

I added a further stage of amplification but felt that this might tend to overload the OC81 a little, besides being somewhat extravagant from a financial point of view. Eventually I added an OC81DM in a switching capacity to provide the relay with practically full battery potential, whatever the strength of d.c. pulse emanating from TR3. The modified device has provided me with hours of reliable service so far.

J. Davies,  
East Grinstead,  
Sussex.

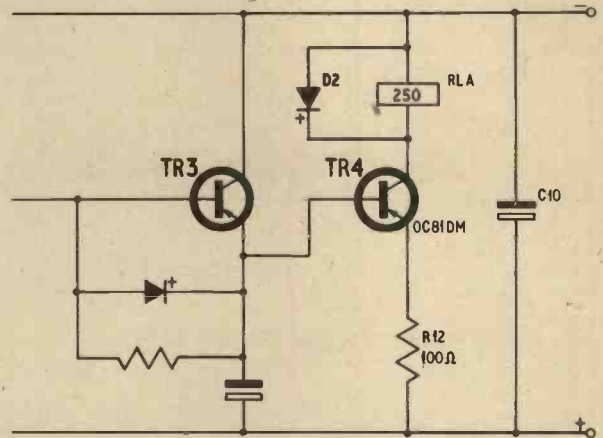

## COMBINED AIDS FOR THE MOTORIST


THE other day I overheard someone complaining about having to pay a fine for driving through the town centre after dark without lights, having forgotten to switch them on.

I took two circuits from the May 1966 issue of PRACTICAL ELECTRONICS, modified them, and combined them to switch on the side lights and give a flashing warning when darkness falls.

The lights are switched on by the same relay that switches on the parking light, but does not become operative until the ignition is switched on. As this circuit becomes operative the small dash light keyed by the multivibrator begins to flash.

It will continue to flash until switch S1 is returned to the off position. The l.d.r. parking light also is switched off by S1.

I. W. Berry,  
Huddersfield.

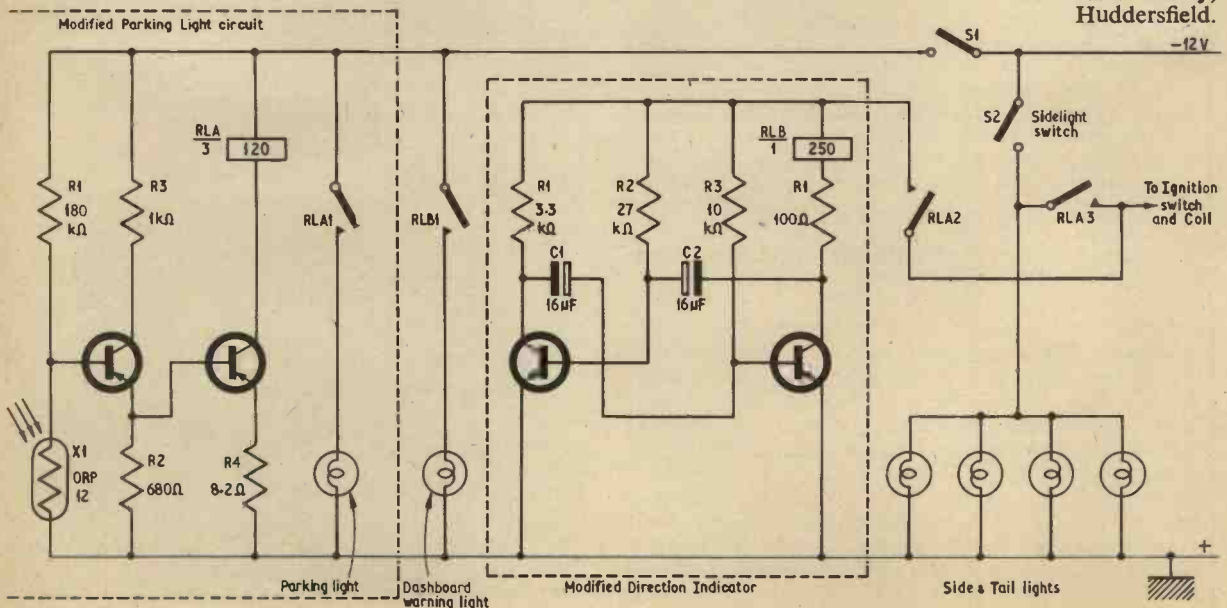



## ...High Fidelity Amplifier by Wharfedale

Yes, designed by Wharfedale in their own laboratory to extremely high standards, to take its place in the professional studio yet handsomely styled to be equally at home in domestic surroundings.

Wharfedale Amplifier TYPE No. WHF-20 incorporates every refinement to ensure that the programmes fed into it from your tuner, pick up or tape recorder are amplified with precise accuracy at all volume levels.

Every necessary control is incorporated but there are no gimmicks. Whilst the

technical expert will favour the flexibility of the controls and the reserves of power available, the layman will be delighted to find that here is a professional instrument that is easily controlled and handled.

*To whet your appetite here is a brief specification:*  
Stereophonic high fidelity integrated control unit and power amplifier using silicon transistors throughout.

20 watts (continuous) per channel into 8 ohm load with total distortion of less than 0.2%.

Power response -3 db at 10 Hz and 60 kHz (Ref 0 db = 20 watts)  
Tone control range  $\pm 17$  db at

40 Hz and  $\pm 12$  db at 10 kHz. Filter slope variable from 0 db to 20 db per octave above 7 kHz. Switched loudness control gives up to 10 db of bass lift at low volume control settings.

Disc input sensitivities of 3.5 mV or 50 mV (by switch) to match magnetic or ceramic cartridges. Switched rumble filter - 3 db at 40 Hz, -18 db at 20 Hz.

Tape input and output levels of 100 mV switched to allow tape monitoring.

Tuner and auxiliary inputs with 100 mV sensitivity.



For full details of this amplifier post this coupon now to:

**RANK WHARFEDALE  
LIMITED  
IDLE BRADFORD  
YORKSHIRE**

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

TOWN \_\_\_\_\_

COUNTY \_\_\_\_\_

PE 4

**RANK WHARFEDALE LTD IDLE BRADFORD YORKSHIRE**



# BARGAINS IN MODERN QUALITY KITS, COMPONENTS & EQUIPMENT

## TRANSISTOR KITS

**PEAK SOUND S48-8** Integrated 14 transistor stereo amp. for good ceramic and crystal pickups. 16-17 watts output into two 5 ohm speakers. Anyone can assemble it. Separate treble and bass controls. Easy to follow instructions. Complete down to last screw. £12/19/6. Peak Sound Power Pack £3/15/-.

**SINCLAIR Z12** Combined amp. and pre-amp. 12 watts r.m.s. into 1.5 ohm load. Suitable for any loudspeaker. Two can be used in stereo. Price, each assembled 89/6.

**SINCLAIR STEREO 25** Combined high sensitivity pre-amplifier and control unit. Ideal for two Z.12's. Assembled £9/19/6. PZ3. Power pack £3/19/6.

**T.R.S. MULLARD F.M. STEREO DECODER** 6 transistor kit with built-in indicator. Can be used with existing transistor or valve systems £4/19/6. With pre-aligned inductors £5/5/-.

**MULLARD** Four watt popular stereo amplifier in course of preparation. S.A.E. brings details.

## STEREO HI-FI & RADIO

**SINCLAIR MICROMATIC KIT** 59/6  
Ready built 79/6  
**SINCLAIR MICRO F.M. KIT** 25/19/6  
"CIR-KIT" Circuit board kit No. 3 as advertised. 15/-

## GARRARD UNITS

LM.3000 charger with 9TA stereo cartridge. 8 gns.  
AT.60 De-Luxe charger with 10 1/2" cast T/table less cart. 9 1/2 gns.  
SF.25 De-Luxe single player less cartridge. 9 1/2 gns. Carr. and packing on above 7/6 each.  
**GARRARD PLINTHS** in teak for any of above, with plastic cover 7/6. Carr. and packing 5/-.

**SEND 3D Stamp for MARCH Bargain** List of everything of value to the keen constructor. **PACKED WITH BARGAINS.**

## DE-LUXE RECORD PLAYER KIT

An elegantly designed quality instrument that builds into a superb reproducer. With 4 Sp. Garrard Auto-Slim unit and special Mullard high quality 3 watt printed circuit valve amplifier, vol. bass and treble controls, 8" x 5" 10,000 line speaker. Contemporary styled 2-tone cabinet, charcoal-grey and off-white with matching blue-velvet. Size 17 1/2" x 16" x 8". A stylish unit capable of quality reproduction. Circuit and const. details 2/6 (free with kit).

**COMPLETE KIT £13.19.6**

Carr. and Ins. 12/6  
Ready wired 39/- extra. Illuminated perspex control panel escutcheon, 7/6 extra. Four contemporary mounting legs, 6in. 10/6; 9in. 11/6; 12in. 12/6 extra.



## TRS KITS FOR MULLARD AMPLIFIERS

(STEREO VERSIONS IN COURSE OF PREPARATION—SEND S.A.E.)

**MULLARD "3-3"** 3-valve Hi-Fi quality at reasonable cost. Bass Boost and Treble controls, quality sectional output transformer (8 and 15 ohms). 40 c/s-25 kc/s + 1 dB. 100 mV. for 3W., less than 1% distortion. Bronze escutcheon panel. Complete Kit only £27/10/-, Carr. 5/-, Wired and tested £29/10/-.

**MULLARD "5-10"** 5 valves 10 W., 3 and 15 ohms output. Mullard's famous circuit with heavy duty ultra-linear quality output tr. Basic amplifier kit price. £9/19/6. Carr. 7/6. Ready built 11 Gns.

2 valve pre-amp. Mullard Circuit. £6/12/6 (P. & P. 5/6). Assembled £8/10/-.

## TRANSFORMER SERVICE

We manufacture all types Radio Mains, Transformers, Chokes, etc., for prototypes for small production runs. Enquiries invited. Prompt reply assured.

## POSTAL AND PACKING CHARGES

Terms: C.W.O. or C.O.D., post and packing 1lb. 1/-, 1lb. 1/9, 3lb. 3/-, 5lb. 3/9, 8lb. 4/6, etc.

## T.R.S. RADIO COMPONENT SPECIALISTS

ESTABLISHED 1946

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY

(A few doors from Thornton Heath Station, Southern Railway)

Telephone: THO 2188. Hours: 9 a.m.—6 p.m. daily. 1 p.m. Wed.

# YOURS FREE FOR 7 DAYS


The New 'Picture-Book' way of learning

# BASIC

- ELECTRICITY (5 Vols)
- ELECTRONICS (6 Vols)
- ELECTRONIC CIRCUITS (2 Vols)
- INDUSTRIAL ELECTRICITY (2 Vols)
- SYNCHROS & SERVOMECHANISMS (2 Vols)

You'll find it easy to learn with this outstandingly successful new pictorial method—the essential facts are explained in the simplest language, one at a time; and each is illustrated by an accurate cartoon-type drawing.

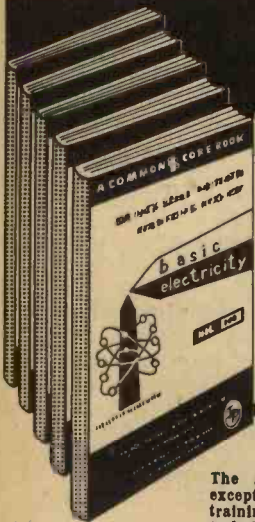The books are based on the latest research into simplified learning techniques. This has proved that the Pictorial Approach to learning is the quickest and soundest way of gaining mastery over these subjects.



The series will be of exceptional value in training mechanics and technicians in electricity, Radio and Electronics.

## WHAT THIS MONTH'S ENTHUSIASTIC READERS SAY

- ... The Basic Electricity volumes, were readily understood by my 13 year old son... J.B., WOLVERHAMPTON
- ... I have every confidence in your common core series for creating a sound basis on which to build a successful future... J.R., BIRMINGHAM
- ... I am well pleased with this pictorial system. Everything is clearly set out in diagrams... L.P., CO. ARMAH

## TO SELRAY BOOK CO. 60 HAYES HILL, HAYES, BROMLEY, KENT

Please send me Without Obligation to Purchase, one of the above sets on 7 Days Free Trial. I will either return set, carriage paid, in good condition within 7 days or send the following amounts. Basic Electricity 70/- Cash price or Down Payment of 15/- followed by 4 fortnightly payments of 15/- each. Basic Electronics 82/- Cash Price or Down Payment of 15/- followed by 5 fortnightly payments of 15/- each. This offer applies to U.K. only. Overseas customers cash with order.

Tick set required (only ONE set allowed on free trial)

- |                                       |                          |                        |                          |
|---------------------------------------|--------------------------|------------------------|--------------------------|
| BASIC ELECTRICITY 70/-                | <input type="checkbox"/> | BASIC ELECTRONICS 82/- | <input type="checkbox"/> |
| BASIC ELECTRONIC CIRCUITS 40/-        | <input type="checkbox"/> |                        | <input type="checkbox"/> |
| BASIC INDUSTRIAL ELECTRICITY 40/-     | <input type="checkbox"/> |                        | <input type="checkbox"/> |
| BASIC SYNCHROS & SERVOMECHANISMS 38/- | <input type="checkbox"/> |                        | <input type="checkbox"/> |
- ALL PRICES INCLUDE POSTAGE

PE 4

Signature..... (If under 21, signature of parent or guardian)

NAME.....  
FULL POSTAL ADDRESS.....  
BLOCK LETTERS BELOW


**POST NOW FOR THIS OFFER!**

## LUMOSTAT HINTS

I would like to express my appreciation for the articles on the *Lumostat*. I have made this, and it promises to be an indispensable aid in the darkroom.

May I offer the following advice to anyone constructing this equipment. In the "auto" function, particularly during long exposures, the circuit insulation is critical. The auto/time switch, S8 in particular may be found to be at fault. Various toggle switches tried were found to have leakage resistance of about 300 megohms which is too small to be tolerated in this circuit. A satisfactory substitute was found to be a rotary ceramic type, with leakage resistance greater than 10,000 megohms.

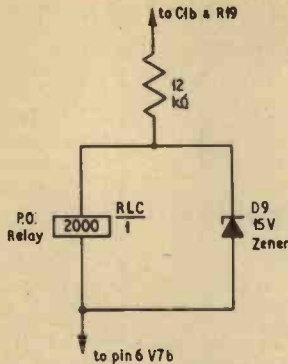With this substitution, it was found that certain capacitors associated with S9 had to be altered



to give the correct logarithmic time intervals. Correct values were found to be: C28 0.017 $\mu$ F; C29 0.027 $\mu$ F; C30 0.033 $\mu$ F and C31 0.05 $\mu$ F. The values given in the article are obviously not in keeping

with the rest of the capacitors, probably as a result of leakage at switch S8.

Some saving in cost is possible by using P.O. relays. Almost any 24V type may be used for relay B. Relay C is more difficult, but a satisfactory substitution, using a 2,000 ohm P.O. relay, operating at 6mA is shown in the circuit diagram. A slip of paper between core and armature suppresses any tendency to bounce. The saving on the Zener diode is also appreciable.

Finally, a word of warning! The photocell 90AV is not sensitive to normal darkroom illumination, but it is sensitive to light from an electric fire. Switch this off during calibration of the unit.

S. C. Hooson,  
Liverpool, 16.

# HOW TO USE THE COMPONENT SELECTION CALCULATOR

GIVEN FREE WITH THIS ISSUE OF PRACTICAL ELECTRONICS

## Component Tolerance Calculator

IT FREQUENTLY occurs that the constructor requires to select a certain value of component from several (e.g. resistor, capacitor, etc.) with a close nominal value, i.e. the value given on the component.

If, for example, 80 kilohms is required the tolerance calculator can find what nominal values can be used to select, by measurement, the required value. Set the centre line of each grey panel on the slide in turn against the required exact value in this case against 80 on the lower scale. It will be seen that near preferred values for selection could be: 82k $\Omega$  at 5, 10, or 20 per cent; 75k $\Omega$  at 10 or 20 per cent; 68k $\Omega$  at 20 per cent; 91k $\Omega$  at 20 per cent. Now you have a wide range of components from which 80k $\Omega$  may be found by more accurate measurement.

Conversely, if you have a component of a given nominal value (e.g. 100k $\Omega$   $\pm$  20 per cent) the range of values within this tolerance can be found by setting the centre line of the appropriate grey panel against the nominal value and reading off the adjacent scale. In this example, for 100 $\Omega$   $\pm$  20 per cent, the actual component value may be between 80k $\Omega$  and 120k $\Omega$ .

It is important that the decimal multiplier, although not given on this calculator, is easily taken care of by memory. This will be obvious from the examples given. The upper scale is continued on the lower scale with some overlap—40 to 50. This makes calculation easier within this range so that either scale is selected for convenience.

From 8 to 20 the upper scale is marked in halves, but if intermediate values are required you can transfer to the lower scale and use 80 to 200. Again allow for the decimal multiple.

This procedure is the same for any component.

## Time Constant Calculator

THE calculation of time constants ( $T = CR$ ) usually involves awkward multiple and submultiple values of capacitance and resistance and this Time Constant calculator was designed to offset these difficulties.

The range of time constants available on the calculator is from 0.01 to 10<sup>9</sup> microseconds enabling rapid evaluation to be made of the choice of timing components that are so commonly encountered in pulse circuits, RC oscillators, waveform shapers and tone control filters, to mention but a few.

- Set lower limit of chosen kilohm scale, i.e. A, B, C or D against chosen capacitor value (p or  $\mu$  scale).
- Read off the number that coincides with the multiplying resistance on the p or  $\mu$  scale.
- The multiple of this number of microseconds is found directly above or below it by the lines referenced by the scales involved, for example, Ap, B $\mu$ , etc., and so provides the time constant.

It will be appreciated that the formula can be manipulated. For example, the components for a particular time constant would be realised by using the converse of the operations as set out before.


As an example, find the time constant of a 4 $\mu$ F capacitor and a 50 kilohm resistor.

50 kilohms appears on the slide scale B, so the lower limit 10 on this scale is aligned with the 4 $\mu$ F mark on the  $\mu$  scale. The figure that concurs with 50 kilohms on the  $\mu$  scale is the number of the time constant, i.e. 2. To interpret this value in microseconds, refer to the scale B $\mu$  which provides directly the limits of reference in microseconds for the number read off, namely 10<sup>5</sup> and 10<sup>6</sup>, therefore the time constant is 2  $\times$  10<sup>5</sup> microseconds.

# FIELD STRENGTH METER

## for 27 MHz MODEL CONTROL BAND

By P. W. HAND

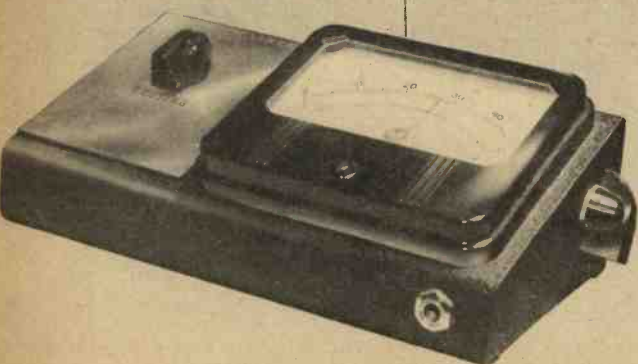


**T**HIS field strength meter will be a useful addition to any radio control enthusiast's equipment. The main function of this instrument is to enable the transmitter or transmitter aerial to be checked. It may also be used for modulation checks and also to ascertain whether another transmitter is operating on one's own frequency or an adjacent frequency.

The basic circuit arrangement for a field strength meter is shown in Fig. 1. It consists of a tuned circuit VC1, L1, a diode detector D1, and a microammeter M1 to measure the diode current. Calibration of the meter is of no great consequence, and may be in milliamps, volts, or decibels; the instrument is used for comparative measurements only. This elementary circuit suffers from the disadvantage that a sudden increase in signal strength may readily damage the meter movement.

In the design to be described in this article, a transistor amplifier has been incorporated; this increases the sensitivity of the instrument, and also provides a degree of protection for the meter movement.
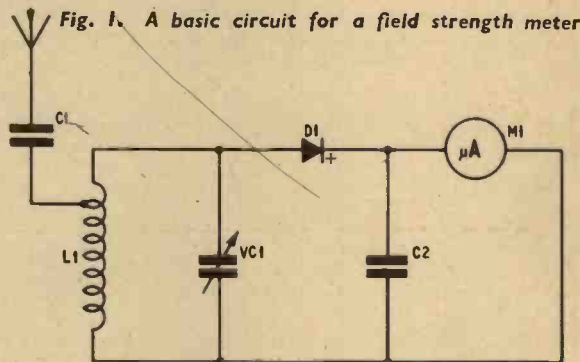
### THE FINAL CIRCUIT

Referring to the circuit diagram Fig. 2, upon receipt of a signal the diode D1 conducts, and causes a positive voltage to be applied to the base of transistor TR1 so reducing the collector current. The meter M1 is in the collector circuit, and so registers a fall in current with an incoming signal.



The diode D1 is connected to a tapping one turn from the bottom, or "earthy" end, of the coil L1 to prevent damping the coil unduly. This tapping may be moved to the second or third turn for an increase in sensitivity, with only a slight increase in damping on the coil.

The coil L1 consists of 11 turns of 18 s.w.g. enamelled copper wire, wound on a 1in former and the winding is spaced to occupy 1in. This coil is tuned to 27MHz by a 65pF air spaced variable capacitor VC1 in series with a 30pF Phillips concentric trimmer TC1. The trimmer is adjusted to bring the operating frequency to the centre of the dial.

A phone jack JK1 is included for audio monitoring of the signal when making modulation checks.

### CONSTRUCTION

As the illustrations show, the prototype was built in a metal case with a sloping front panel. This style of case enhances the general appearance as well as facilitating reading the meter. This is not an essential feature of course, and any metal box or case of approximately the same dimensions will be quite satisfactory.

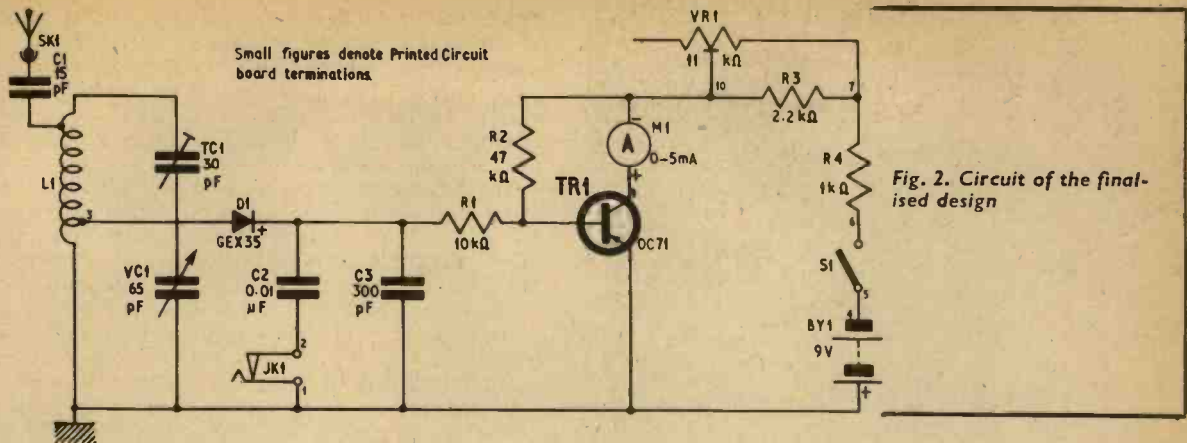


Fig. 2. Circuit of the finalised design

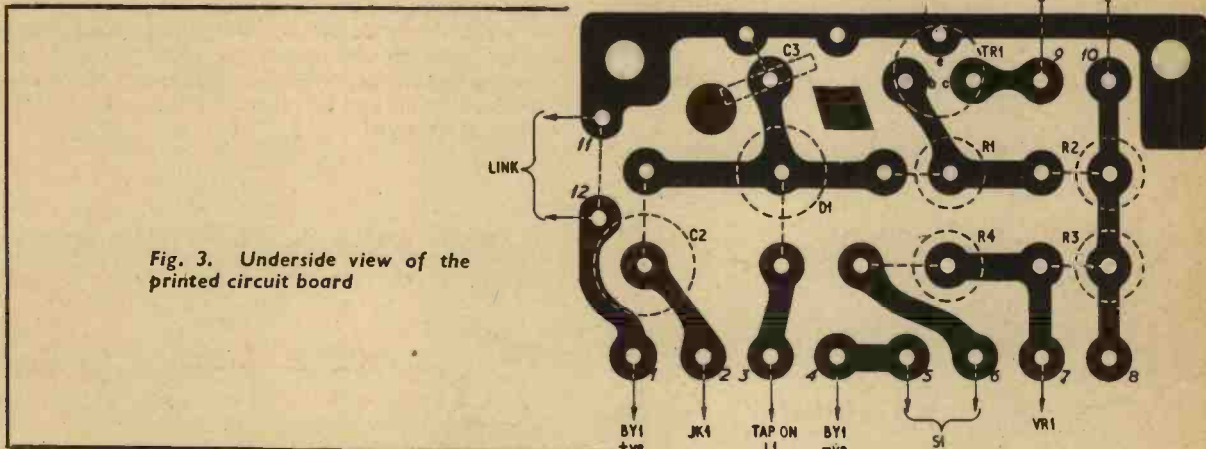


Fig. 3. Underside view of the printed circuit board

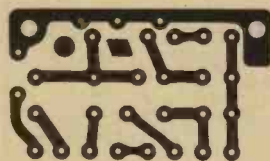


Fig. 4. The printed circuit board reproduced actual size

The arrangement of the components can be seen in the photograph, and the wiring is given in Fig. 6.

### PRINTED CIRCUIT BOARD

All the smaller components are mounted on a printed circuit board. Since this method of construction may be unfamiliar to some readers, the technique involved in the preparation of this printed circuit board will be described in some detail.

Initially all component sizes and their lead spacing were noted. Then several small sketches were made until a satisfactory layout was obtained. (It should be mentioned here that the writer was endeavouring to make the printed circuit as small as possible.) The printed circuit was then drawn to an enlarged scale in indian ink. This drawing was photographed on to Kodak Lith film with the aid of an ordinary photographic enlarger. Next a negative was made of the correct size to contact print direct onto the copper laminate which had previously been coated with Kodak Printed Circuit Resist. The printed board is shown actual size in Fig. 4. For component layout see Fig. 5.

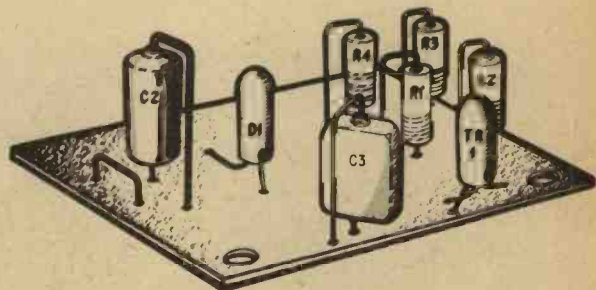


Fig. 5. Top view of the printed circuit board with the components in position

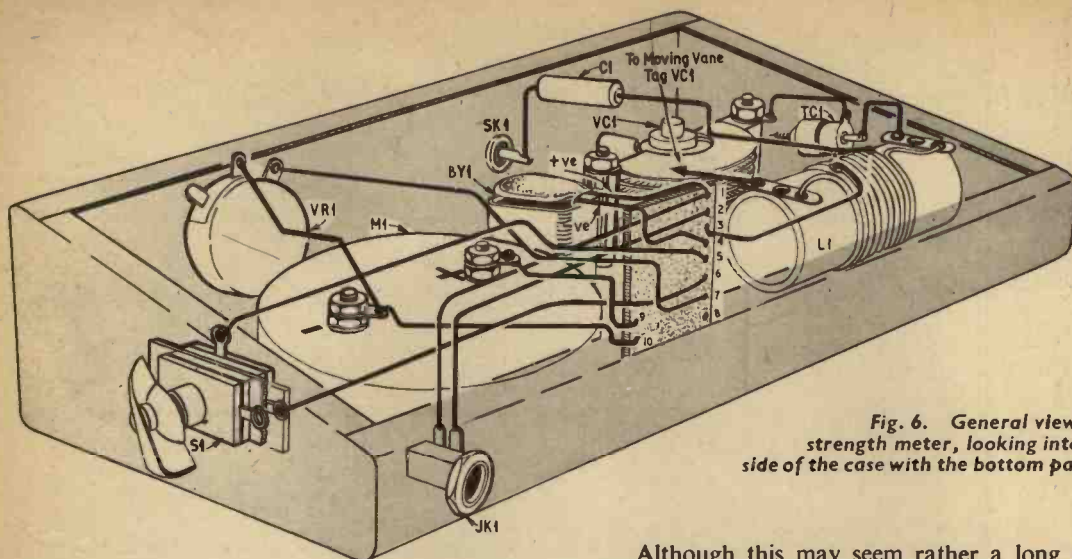


Fig. 6. General view of the field strength meter, looking into the underside of the case with the bottom panel removed

## COMPONENTS . . .

### Resistors

R1	10k $\Omega$	R3	2.2k $\Omega$
R2	47k $\Omega$	R4	1k $\Omega$
All $\pm 10\%$ , $\frac{1}{2}$ W carbon			

### Potentiometer

VR1 11k $\Omega$  preset

### Capacitors

C1	15pF mica or ceramic
C2	0.01 $\mu$ F paper
C3	300pF mica
VCI	65pF air spaced tuning capacitor
TC1	30pF concentric trimmer (Phillips type)

### Miscellaneous

DI	Germanium diode, GEX35 or equivalent
TR1	Transistor, OC71
M1	Moving coil meter, 5mA f.s.d.
JK1	Open circuit jack socket
SK1	Aerial socket
S1	Single pole on/off switch
BY1	9V battery, PP3
Material for case. Copper clad board for printed circuit and escutcheon. Two knobs.	

## TUNING ESCUTCHEON

The escutcheon for the tuning control was made of copper laminate in the same manner as the circuit board, except that a positive was used here. Thus the letters and the dial engraving were etched away, leaving the majority of the copper surface intact.

## OPERATION

A length of 16 s.w.g. copper wire should be attached to the aerial socket SK1 at the rear of the case. If the same length of pick-up wire is always used, fairly accurate comparative results can be obtained by always positioning the meter the same distance from the transmitter aerial. The distance will depend on the sensitivity of the meter, and the aerials used. It may be five yards, or so, and farther away for more powerful transmitters.


First it is necessary to adjust VR1 for full scale deflection of the meter pointer with *no signal input applied*. The instrument is now ready for normal use.

Tuning is performed by adjusting VCI for *minimum* reading on the meter. Adjustments to the aerial, or the transmitter, are directed towards *reducing* the meter reading; this indicates an *increase* in signal strength.

If the reading is reduced to zero, then the field strength meter should be moved farther away from the transmitter, when some deflection will be obtained.

This reading should then be reduced again if possible by careful retuning of the instrument.

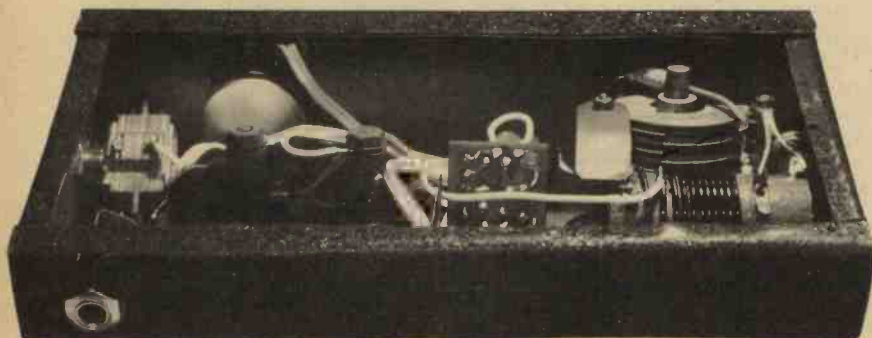Audio monitoring can be performed by inserting a pair of headphones into JK1. In this way the modulation of the transmitter may be checked. It is also possible to check whether any interference is likely from other transmissions on the same or adjacent frequency. ★





# THE ELECTRONIC ORGAN

## PART FIVE

By ALAN DOUGLAS, Sen. Mem. I.E.E.

### TONE FORMING FILTER CIRCUITS

WE all know that the appeal of an organ does not rest with any one particular sound, but rather on a number of harmonious blends of the different voices built into the instrument. Of course, there are sounds found *only* in the organ—the diapason, tibia, the ponderous basses which exist nowhere else. But we must not fly too high, for whilst one could truthfully say that there is no limit to the voicings possible from organ pipes, there is a definite limit to the tonal differences possible from electronic circuits.

If we have a common waveform, that is, one waveform only (of whatever kind) to cover a range of 61 notes or a frequency ratio of approximately 32:1, it is quite evident that with any one passive filter network we are going to find some parts of the compass where it does not work at all, and at best the action of any tone circuits must be very severe to greatly modify the tone.

#### BASIC FILTER CIRCUITS

The single tone network is the most commonly encountered, some of its deficiencies being mitigated by the fact that extremes of the compass are not much used; and that by combining stops, the resultant juggling with harmonics tends to obscure weaknesses in other stops. On the other hand, certain circuits with certain waveforms work very well.

The basic or elementary forms of the common filters have been so often described that it is hardly necessary to go over all this again; but briefly, low pass cascaded sections will attenuate high notes, though with considerable loss of signal strength, Fig. 5.1a. The inversion of this circuit, the high pass filter, will remove low frequencies, Fig. 5.1b. And the resonant, band pass or band stop filter accentuates some frequencies at the expense of others, Figs. 5.1c and d.

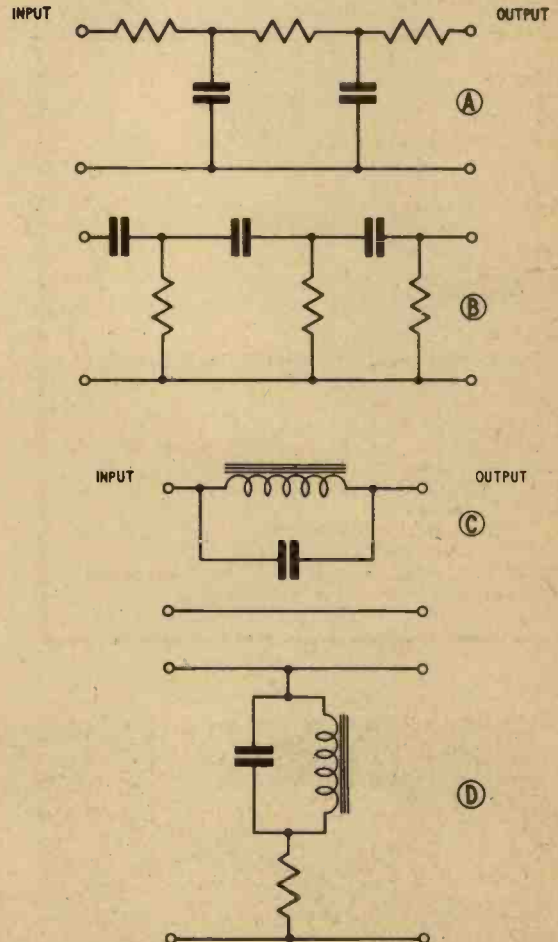


Fig. 5.1. Basic filter circuits. (a) low-pass cascaded sections, attenuates high frequencies; (b) high-pass cascaded sections, attenuates low frequencies; (c) resonant band-stop filter; (d) resonant band-pass filter

All of these circuits can be extended or combined, and all can have more than one waveform injected. Such tone circuits are called subtractive, because we are removing unwanted frequencies from a complex waveform.

One of the basic organ tones is the flute; if made considerably louder, we could call it a tibia—the foundation stop of the theatre organ. Organ flutes have quite a number of harmonics, in general quite small in amplitude. Fig. 5.2a shows the harmonic content of a soft flute note, and Fig. 5.2b that of the same note twice as loud. It will be seen that some harmonics barely alter, but the second and fourth become very powerful. If we subdue these we still have a good flute, but if we take away the 4th, 6th and 8th we find only a very dull sound remaining. Later on

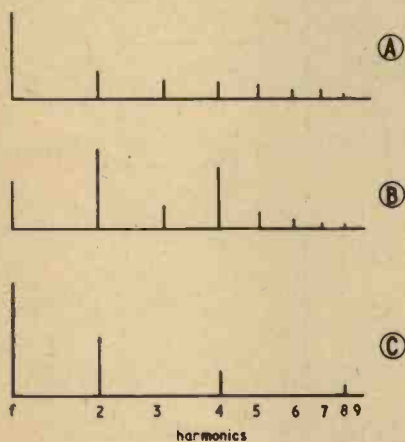


Fig. 5.2. Harmonic content for organ flute. (a) soft flute tone; (b) same note twice as loud; (c) required content

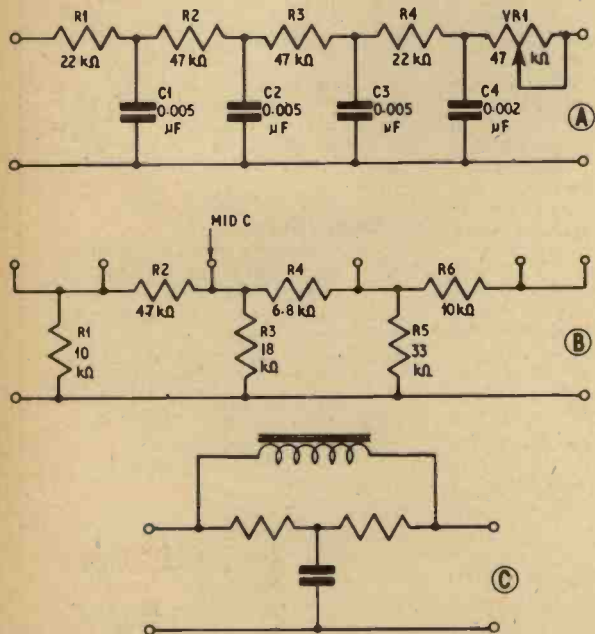


Fig. 5.3. Passive equalising circuits. (a) flute forming circuit; (b) attenuator for upper harmonics; (c) circuit for progressive attenuation of upper harmonics

we will see examples of tone circuits to simulate this condition, but in the organ to be described later we actually generate the required waveform directly (Fig. 5.2c) and the small adjustments to be carried out (which are greatly dependent on the loudspeakers and the room in which they are used) can be made *note by note* if required, which would be quite impossible with a frequency divider system. Nonetheless we do use flutes from our dividers and these are formed as shown in Fig. 5.3a.

The constants for the four-section filters are of course related to the pitch range involved, but even with a sawtooth wave there are inclined to be too many upper harmonics and these are equalised as far as possible by attenuators between the adjacent octaves of the busbars, Fig. 5.3b.


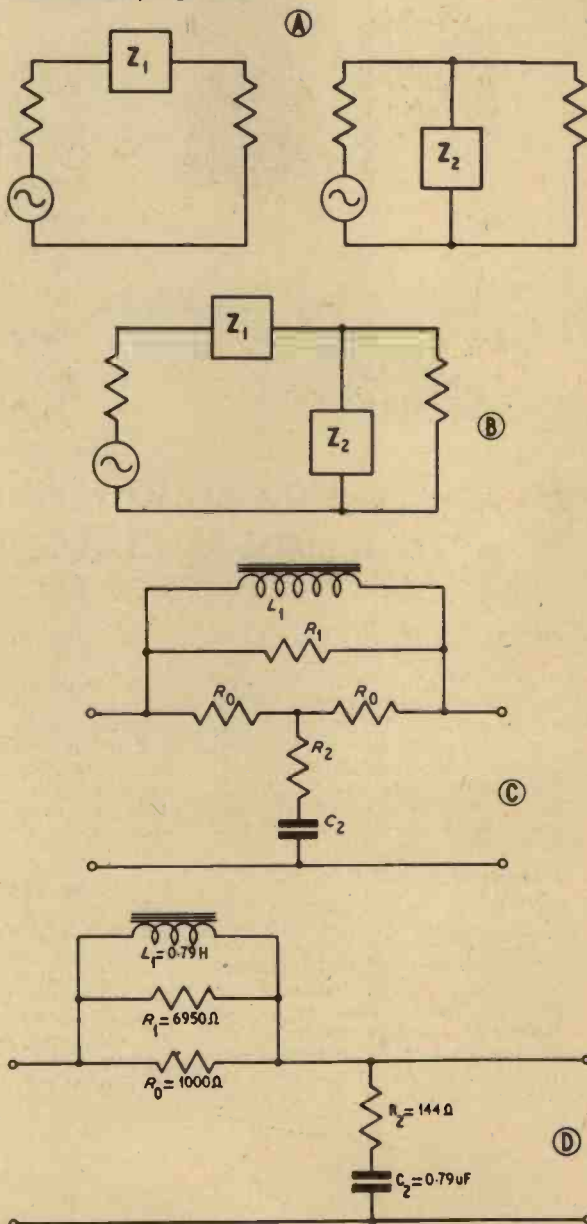


Fig. 5.4. Reactive filters. (a) general principles, series and shunt reactances; (b) combined series and shunt reactances; (c) bridged-T filter; (d) complete equaliser

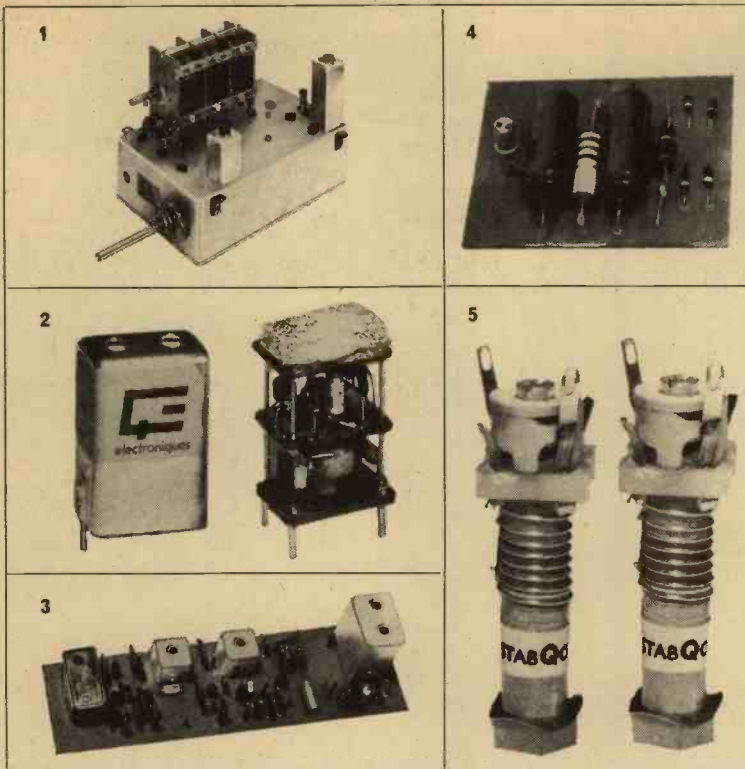

I should like a copy of the *Electroniques Hobbies Manual*. Enclosed is a cheque/P.O. for 10/6.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

P.E. 4

## Below, we've summarised 2 pages from the **Electroniques Hobbies Manual** 606 PAGES REMAIN TO BE SEEN (when you've got your Manual)

With the new Hobbies Manual, you can obtain these—and over 11,000 other items—direct from Electroniques or through your Local Electroniques dealer! The service is fast; the range is the most comprehensive ever offered. And the components, which are supplied by 85 leading manufacturers, meet every kind of need—whether the project is advanced or elementary!

### 1 Transistor Coil Packs (Coilpax)

These silicon transistor units are available in General Coverage and Hamband versions. The IF frequency is 1620 Kc/s, ready for use with our filters and IF amplifiers as well as existing receivers as the second IF. The Manual contains comprehensive technical data and other useful information on these items.

### 2 Oscillator Modules

Fully transistorised, these oscillator units can be used for BFO, VFO or CIO applications. The BFO units include a variable capacitance diode as the tuning element, permitting remote control by linear law potentiometer. Extremely stable (better than .002% per degree C), they have an exceptionally pure oscillator waveform.

### 3 IF Strips and Filters

Two units are available—one at 1.62 Mc/s IF for use with Coilpax, the other for use at 455 Kc/s as a second conversion IF strip or as a main 455 Kc/s unit. Both include a half lattice crystal filter, AGC control, AM and SSB detection and BFO injection for CW reception. A third unit, also at 455 Kc/s, uses a ceramic filter.

### 4 Power Modules

These small stabilised power units operate directly from 6.3V AC heater supply. Two outputs available: 6.2V at 50mA Zener stabilised, and 9.0V at 70mA MAX un-stabilised. Either polarity can be earthed providing AC supply is floating.

### 5 Coils (Stabcoils)

A comprehensive range of transistor coils is available for intermediate frequencies of 455 Kc/s and 1.62 Mc/s, together with a complementary range of IF transformers.

Send now for your Manual, on the coupon above, to this address: Electroniques (Prop.-STC Ltd.) Edinburgh Way, Harlow, Essex. Telephone: Harlow 26777.

High-grade components for amateur communications



**YOU CAN  
NOW BUY THE  
WORLD'S FINEST  
SPEAKER VALUE  
DIRECT FROM**

**R&A**

The 700 Mark V Range

Specially designed to provide outstanding range, smoothness and uniformity of frequency response with freedom from self generated forms of distortion up to levels more than adequate for domestic listening. The speakers in this range all have a highly developed dual radiating system with optimum termination of both cones — voice coil impedance 15 ohms.



Power handling capacity in appropriate enclosures:—

- |   |                   |
|---|-------------------|
| 780 Mk. V   | Price £3 . 19 . 7 |
| 8 in. 6 watts r.m.s. 12 watts peak. (inc. 11/7 P.T. and P. & P.)  |                   |
| 7100 Mk. V  | Price £4 . 14 . 3 |
| 10 in. 8 watts r.m.s. 15 watts peak. (inc. 13/9 P.T. and P. & P.) |                   |
| 7120 Mk. V  | Price £4 . 18 . 6 |
| 12 in. 10 watts r.m.s. 18 watts peak. (No P.T. but inc. P. & P.)  |                   |

Send for full technical data sheet with suggestions for enclosures to:

REPRODUCERS AND AMPLIFIERS LTD.  
Frederick Street, Wolverhampton England

LOUD SPEAKER MANUFACTURERS TO THE  
RADIO INDUSTRY SINCE 1930

**EXCEL**

*in*

**ELECTRONICS**

**Through this ICS  
3-way Training Method:**

**1**

MASTER THE THEORETICAL SIDE

From basic principles to advanced applications, you'll learn the theory of electronic engineering, quickly and easily through ICS. That's because each course is set out in easy-to-understand terms.

**2**

MASTER THE PRACTICAL SIDE

ICS show you how to develop your practical abilities in electronic engineering—*alongside* your theoretical studies. It's the only sure way to success. All training manuals are packed with easy-to-follow illustrations.

**3**

MASTER THE MATHEMATICAL SIDE

To many this aspect is a bitter problem. Even more so because no electronic engineer is complete without a sound working knowledge of maths. But new ICS teaching makes mathematics easier to learn.

Wide range of courses available include:  
Radio/T.V. Engineering and Servicing, Closed Circuit T.V.,  
Electronics, Electronics Maintenance, Instrumentation and  
Servomechanisms, Telemetry, Computers, etc.  
NEW! Programmed Course on Electronic Fundamentals

EXPERT COACHING FOR:

INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS  
CITY AND GUILDS TELECOMMUNICATION TECHNICIANS  
CITY AND GUILDS SUPPLEMENTARY STUDIES  
R.T.E.B. RADIO/T.V. SERVICING CERTIFICATE  
RADIO AMATEURS' EXAMINATION  
P.M.G. CERTIFICATES IN RADIOTELEGRAPHY

And there are practical "learn as you build" radio courses as well.

Member of the Association of British Correspondence Colleges

FOR **FREE** HANDBOOK POST THIS COUPON TODAY

I.C.S., Dept. 151, INTERTEXT HOUSE,  
PARKGATE ROAD, LONDON, S.W.11

NAME .....

ADDRESS .....

OCCUPATION.....AGE..... 4/67

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

A rather better way to reduce the harmonics is by an equalising circuit as in Fig. 5.3c. Here we progressively cut down higher harmonics until they assume roughly the same values as the lowest frequency required, as follows. But first note that the equalisation is far from perfect because we cannot terminate the circuit with exactly correct impedances.

## REACTIVE COMPONENTS

The simple low pass filter produces a loss which increases without limit as the frequency rises, and the inverse applies to the simple high pass circuit. But if we introduce reactive components, such as inductances, we can regulate the frequencies between which the filter is effective.

Taking the simple case of Fig. 5.4a, we find a generator, source impedance, load impedance and a series impedance  $Z_1$  or a shunt impedance  $Z_2$ , more commonly combined as a complete section Fig. 5.4b. In this, if  $Z_1$  is a series capacitor, it will reduce the level of low frequencies; equally, an inductance  $Z_2$  acts as a variable shunt, allowing high frequencies to pass whilst reducing low frequencies. Thus the whole of the circuit attenuates low frequencies. The converse is true, if  $Z_1$  is an inductance low frequency signals can pass to the load whilst a capacitor  $Z_2$  in shunt reduces the high frequency response.

Again, if  $Z_1$  is a series resonant circuit and  $Z_2$  an anti-resonant circuit at the same frequency, then at resonance,  $Z_1$  is a short circuit to this frequency which passes unaltered to the load. At all other frequencies the impedance of  $Z_1$  is greater than zero, so signals arriving at the load are reduced in amplitude.  $Z_2$  is an open circuit at resonance but at other frequencies is less than infinite, so it acts as a shunt across the load, thus, the output falls off away from resonance. It is clear that by choosing the  $Q$  of these circuits, or shunting them with resistors, many alternative frequency bands may be accentuated or diminished.

Later on we will see working examples of this kind of circuit, which is essential for the simulation of reeds. All such physical tone producers consist of a vibrating system coupled to a resonating tube, and this coupled system induces certain bands of frequencies which are common to many fundamental notes and are called formants. It is by simulating formants or exciting them and their harmonics that we are able to imitate the sounds of reed pipes, because the range and level of all the formants have been known and measured for many organ pipes and orchestral instruments.

## BRIDGED-T EQUALISER

We mentioned that it might be desirable to limit the attenuation of a low pass filter so that, after a certain frequency is reached, the loss does not increase. This can be achieved with a circuit like that of Fig. 5.4c which is a bridged-T equaliser.

In this,  $Z_1$  is a parallel combination of resistance and inductance and  $Z_2$  is a series arrangement of capacitance and resistance. If we take  $Z_1$  alone; at very low frequencies the reactance of  $L_1$  is quite small, and effectively short circuits  $R_1$ , so there is little loss. As the frequency rises, so does the reactance of  $L_1$ , increasing the loss. Should the frequency continue to rise, the reactance of  $L_1$  eventually reaches a value at which it is 10 times greater than  $R_1$ . At this frequency, by the rule of parallel circuits,  $Z_1$  is approximately equal to  $R_1$ ; further increases in frequency have no effect.

Now looking at  $Z_2$ , at very low frequencies the reactance of  $C_2$  is almost an open circuit so  $Z_2$  introduces little loss. As the frequency increases, the loss rises and eventually the reactance drops to a value  $\frac{1}{10}$ th that of  $R_2$ , so that  $Z_2$  is approximately equal to  $R_2$ . Thus, looking at the whole circuit, the effect of  $X_{L1}$  is nil because it is too large and  $X_{C2}$  is negligible because it is too small.

What is left is a bridged-T pad providing a constant loss at all frequencies above that at which  $X_{L1} = 10R_1$  and  $X_{C2} = R_2/10$ . The resulting pad loss, as it is called, is found from  $D = 20 \log_{10} N$  decibels from which can be found by transposing:

$$N = \log^{-1} \frac{D}{20}$$

where

$$N = \frac{V_{\text{out}}}{V_{\text{in}}}$$

We find then that with a circuit of this kind we have both a low and a high frequency stop band, with a slope between formed by the constants  $R_1$ ,  $R_2$ ,  $L_1$  and  $C_2$  and to some extent by the source and load impedances; for such equalisers work tolerably well between very different impedances. So without wearying the reader with the complete calculations, we could suppose that for a pedal 8ft flute stop we have a waveform which is (or can be made so by the circuit constants) flat up to 100Hz and then increases by 18dB at 2kHz, where again it is held by the equaliser constants. Then, to flatten this curve so that the response from 100Hz to 2kHz is practically uniform, the constants given in Fig. 5.4d will produce the result required, assuming a source impedance of 1,000 ohms, which is not unrealistic for transistor preamplifiers.

## TRIAL AND ERROR

Resonant and antiresonant circuits can be assembled in the same way, and in fact many examples of these are to be found in commercial organs; but clearly the slope or linearity of the applied basic waveform has a profound effect on the success of these circuits and this is the reason why a linear sawtooth is so much preferable to a square wave when real fidelity is required.

On the other hand, such voices as the clarinet, bassoon, lieblich gedackt, etc. must have a square wave since they contain no even harmonics. Moreover, it may be desirable to inject more than one waveform into a complex tone circuit or, having modified the pass band by a filter or equaliser, it might be desirable to *rectify* the wave and then subject it to further treatment. So it is evident that the successful employment of tone filters is largely a matter for trial and error. This also follows from the fact that one maker's concept of (say) an organ trumpet is not the same as another maker's. Nowhere is this more noticeable than in the pipe organ world.

The natural outcome of many years' experience yields a certain number of circuits which are really effective if supplied with the correct initial waveform, whilst dozens of theoretically good networks do not produce anything of value. We therefore conclude this section by illustrating two groups of tone networks, one of which requires a sawtooth input and the other, a square wave. In any event, if all the tone networks are to be terminated in a busbar feeding a common amplifier, then of course there must be appreciable series resistance left in each filter to prevent short circuits.

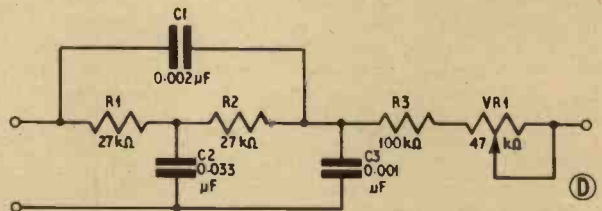
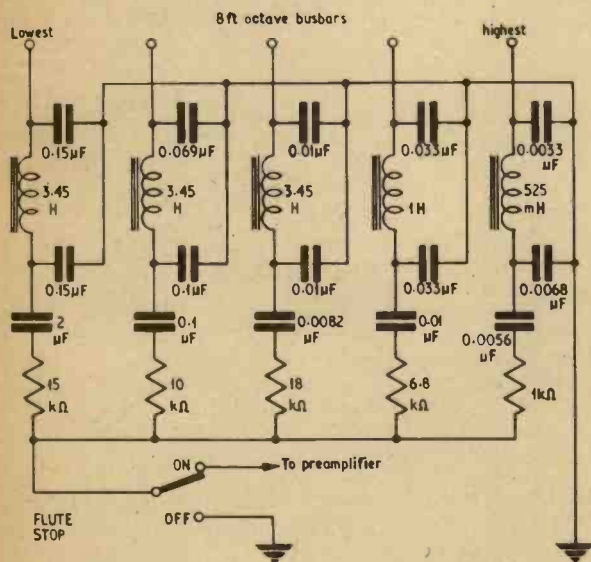
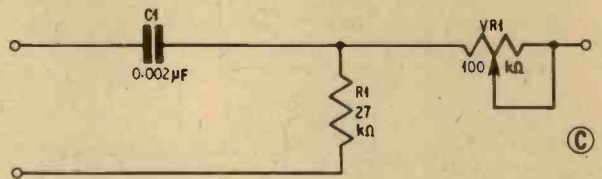
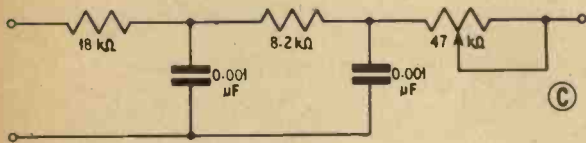
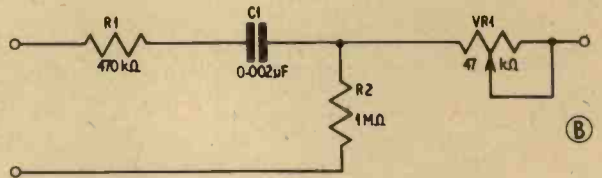
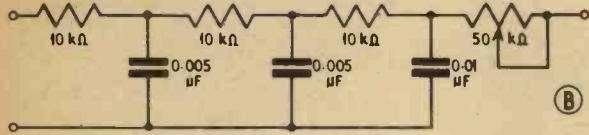
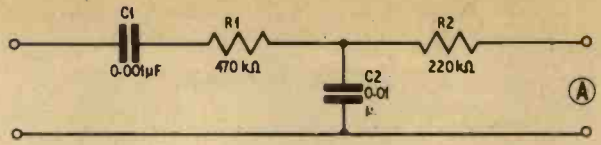
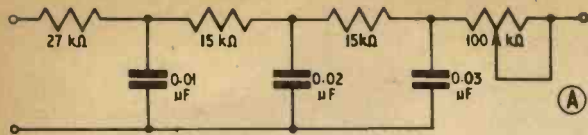


Fig. 5.6. String tone filters. (a) 16ft violes; (b) 8ft violes; (c) 4ft violes; (d) 8ft violes

The alternative is to feed each tone circuit into its own amplifier which is much more costly but sometimes desirable.

### SAWTOOTH INPUT

Taking the flute-like tones first, in Fig. 5.5 we see a 16ft Bourdon at a, an 8ft flute at b and a 4ft flute at c. All require a sawtooth input. At d we find an 8ft flute extracted from a square wave, and this is also required for the 16ft contra tibia of Fig. 5.5e. Note the input circuits for the 8ft flute above, derived octave by octave rather in the manner of the equaliser just described.

String tone pipes always present a problem in stability, but we have an advantage here in that any sufficiently strong cluster of high harmonics will resemble a string organ pipe quite reasonably well.

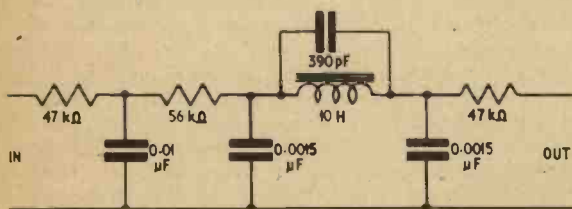


Fig. 5.5. Commercial flute networks. (a) 16ft Bourdon; (b) 8ft flute; (c) 4ft flute; (d) highly corrected flute; (e) 16ft contra tibia

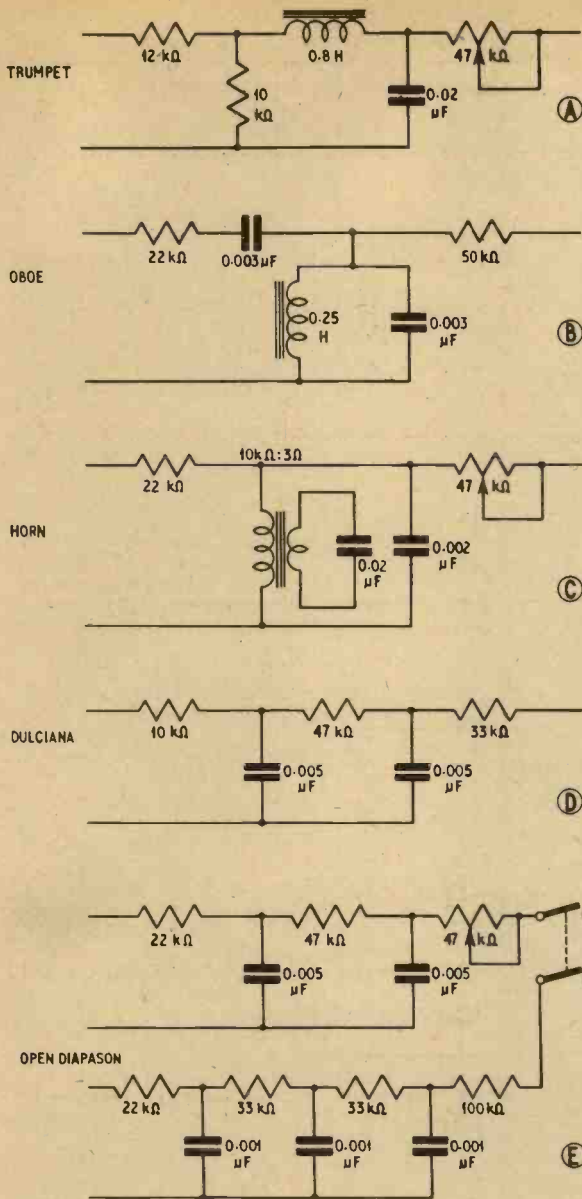


Fig. 5.7. Circuits for deriving conventional organ voices from sawtooth inputs

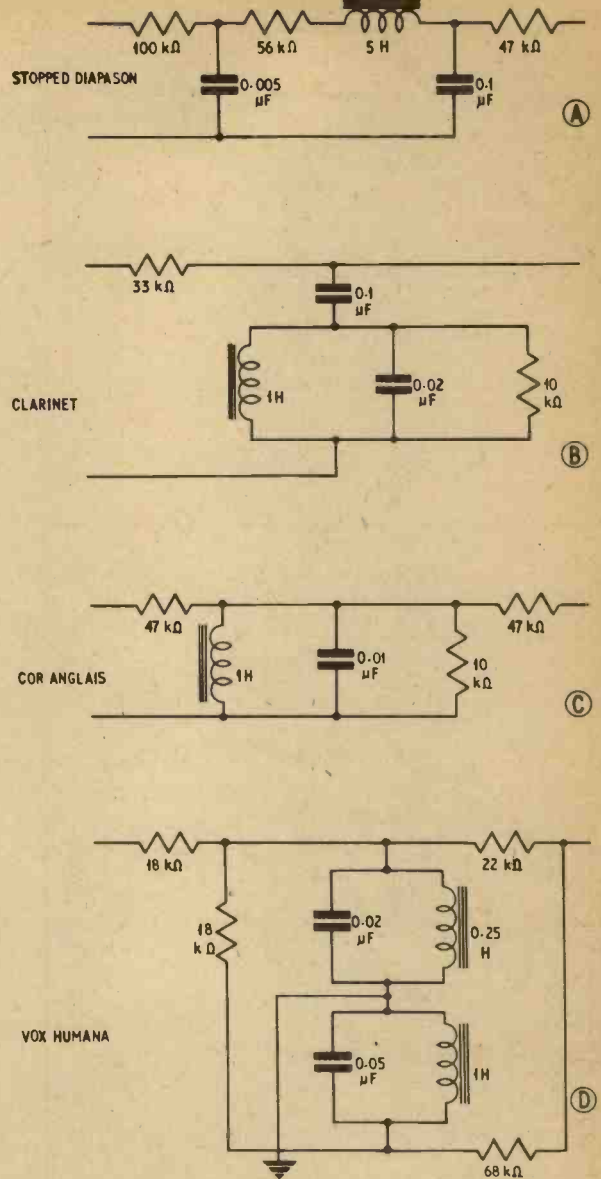


Fig. 5.8. Circuits for organ voices, derived from square wave inputs

Accordingly we show, in Figs. 5.6a, b, c, both 16, 8 and 4ft violes for a sawtooth input, also an 8ft viole for a square wave input (Fig. 5.6d).

In the matter of more conventional organ voices, assuming a sawtooth input, we can show circuits in Fig. 5.7 for 8ft trumpet, oboe, horn, dulciana, and open diapason. Note that this latter voice requires injection from a 4ft sawtooth as well as the 8ft basic pitch.

Finally, some interesting effects can be obtained from overlapping resonant circuits joined in series across a sawtooth line. This process has, in particular, been carried much further in the Bode Melochord, where contacts on each key continually retune resonant circuits so that the inevitable change in tone quality at the extremes of the compass is overcome.

## SQUARE WAVE INPUT

Those organ sounds dependent on a square wave comprise the stopped diapason, clarinet, and cor anglais. There are, of course, many others, but we would not find them of much value in practice. Tone shapers for these voices are illustrated in Figs. 5.8a, b, c. An interesting circuit for an 8ft vox humana is given in Fig. 5.8d and requires a square wave.

In applying any or all of the foregoing, we must not forget that the loudness at which each voice is set greatly influences both its fidelity and its mixing properties. And all of these effects can be enhanced or reduced by the application of vibrato in various forms, and by the loudspeaker system and its placement in the room. We will examine these matters next month.

## TRANSISTORS

With so much happening in the world of electronics it is practically impossible to keep step with the lightning pace of the large organisations. But some of the "giants" of industry realise that the amateur market is no small market and make most of their components available to good recommended retailers.

Mullard is a typical example and they have just announced the addition of seven new *pn*p types to their range of silicon planar transistors. Five have power rating of 600mW and two power ratings of 350mW. Because of their linear gain/current characteristics all the new types are suitable for both switching and linear applications. Their *pn*p characteristic permits complementary operation in conjunction with established Mullard *np*n types.

The two 350mW devices are numbered BCY70 and BCY72. The former has a high  $V_{ce0}$  of 40V and a low saturation voltage. It is primarily intended for medium speed switching applications. The general purpose transistor type BCY72 is suitable for use in switching and amplifying applications requiring less stringent operational requirements.

A low leakage current, low saturation voltage and a high cut-off frequency, generally in excess of 200MHz, are features of the new 600mW transistor types 2N2904, 2N2904A, 2N1131, 2N1132 and 2N3133.

Applications for the 600mW group of devices are similar to those recommended for the lower rated devices although the high power rating also makes them suitable for use in driver and output stages.


The silicon diffused junction rectifier BY105 is a newcomer to the Brimar range. Rated at 800V, and using metal "top hat" encapsulation, the BY105 can operate at 1.1A. This gives it a substantial advantage over the earlier BY100 (even though this has now been uprated to 750mA), since both types are offered at the same price.

Whilst still on the subject of rectifiers a new addition to the existing range of Sanken silicon rectifiers is the type HF SA-3A from Photain Controls Ltd., Randalls Road, Leatherhead, Surrey.

The peak reverse voltage is 600V with a r.m.s. input voltage of 420V and d.c. output current of 1.5A. Reverse current is  $1\mu$ A at peak reverse voltage, forward voltage drop is 0.93V and recovery time is 1 $\mu$ s. Junction temperature is 150 degrees centigrade and surge current is 100A for 10ms.

International Rectifier Co. Ltd., have introduced a new selection of Zener diodes. Called the Zecon range they are available in 1 watt ratings up to 35 degrees centigrade and voltage values range from 3.9 to 30 volts in standard +10 per cent tolerance gradings.


# MARKET PLACE

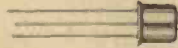

BCY70 transistor from Mullard



Sinclair "Micromatic" Receiver

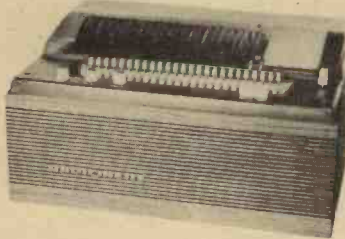

Radionette Multiplayer 50



"Commodore" portable receiver by KB

## HOME LISTENING

Claimed to be the smallest receiver in the world the Sinclair Micromatic is housed in an elegant black plastics case with a polished aluminium front panel. Measuring only  $1\frac{1}{2}$  in  $\times$   $1\frac{1}{8}$  in  $\times$   $\frac{1}{2}$  in it contains a six-stage transistor circuit, ferrite rod aerial and two Mallory Mercury cells type ZM312 or RM312, which give up to 70 hours playing time.

The new circuit uses three special Sinclair transistors to assure good selectivity and reception from a wide range of stations over the medium waveband. The set is switched on by inserting a lightweight earpiece, withdrawing it automatically switches the set off.

Available in kit form for 59s 6d complete with earpiece and instructions, or ready built for 79s 6d, the Micromatic is covered by a five year guarantee.

The Radionette Multiplayer 50 is a compact transistorised multiple record player in a teak cabinet with Perspex cover, now being imported from Norway by Denham & Morley Ltd., 173-5, Cleveland Street, London, W.1.

This automatic "juke box" is capable of playing 25 discs or 50 sides in any pre-arranged order. Operated by push-button controls you can start, stop or replay any record or have six hours continuous music. Incorporating a 15watt amplifier with separate bass and treble controls, it plays at two speeds, 33 and 45 r.p.m., selected by a simple changeover switch. The frequency range is 47 to 17,000Hz  $\pm$  3dB at 1W output.

We recently had the opportunity of trying out a new KB portable radio, Commodore (model KR022). This set doubles as self-contained portable and car radio. For the latter function, the directional properties of the internal rod aerial are nullified by plugging the car aerial into the socket provided.


Lively performance was obtained in various locations. A sensible feature is the bandspreading of medium waves. Two wave bands (555-275m and 280-185m) simplify accurate tuning of the multitude of stations. The third band covers long waves.

Vital statistics: Seven transistors plus diode; earpiece socket; tape recording socket; car aerial socket; 7 in  $\times$  12 $\frac{1}{2}$  in  $\times$  2 $\frac{1}{2}$  in.; 4 lb 8 $\frac{1}{2}$  oz. 18 gns plus 5s 3d tax surcharge.

One black mark: back panel slightly bowed; suggest this would be prevented if two securing screws were provided at ends rather than the single screw at top centre of the panel.

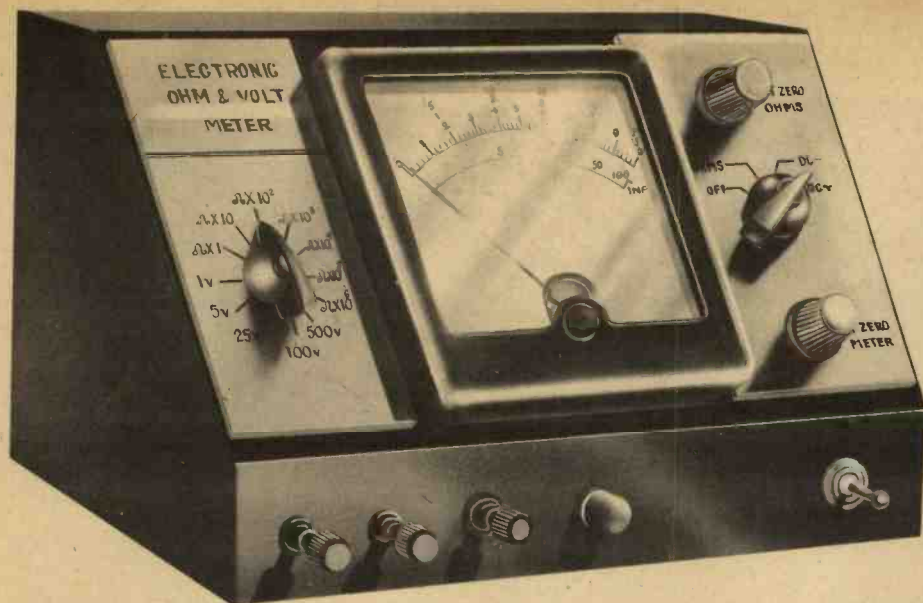Finally, look for the new modular techniques in hi fi at the Audio Festival and Fair (Hotel Russell, London, W.C.1. March 30 to April 2).





By H. T. KITCHEN

# VALVE VOLTMETER & OHMMETER

## SPECIFICATION

### HIGH RESISTANCE VOLTMETER

Five d.c. ranges up to:

1V, 5V, 25V, 100V, 500V f.s.d.

Input resistance 10M $\Omega$

Accuracy better than  $\pm 5\%$  at f.s.d.

Linearity better than  $\pm 5\%$  at f.s.d.

### MULTI-RANGE OHMMETER

Seven ranges based on left-hand zero, 10 ohms calibration at centre of scale, and 100 ohms near to right-hand end: Scale X1; X10; X100; X1,000; X100,000; X1,000,000

Reference voltage 1.5 volts from dry cell

Accuracy better than  $\pm 5\%$  at f.s.d.

SINCE good test equipment is essential to the serious hobbyist, one item, the valve voltmeter (v.v.m.), is one of the most useful units to grace the workbench. This article presents the design of a good and reliable, yet simple and inexpensive v.v.m. together with an exposition of why it is necessary and how it works.

In order to explain why a v.v.m. is necessary it is essential to have at least an elementary knowledge of an ordinary voltmeter. All voltmeters extract power, however minute, from the circuits to which they are connected so that the less power they extract the more accurate the final result—provided the initial meter calibration is correct.

This is particularly applicable to high impedance circuits which, as a rule, have very small currents flowing through them. A typical example is a voltage amplifying valve stage with a very high value of anode load resistor.

The effect of connecting voltmeters of differing sensitivities into such a circuit is shown in Fig. 1. In Fig. 1a,  $R_L = 100$  kilohms, the h.t. supply is 300 volts, and the anode current is 1mA. Now by Ohm's law, 1mA through 100 kilohms will cause a voltage drop of 100V across  $R_L$  leaving 200V on the anode which is the true anode d.c. voltage.

If a voltmeter with a sensitivity of 1,000 ohms per volt, is connected as shown in Fig. 1b, the current drawn by the meter will be 1mA for full scale deflection.

Since the valve requires 1mA and the meter also requires 1mA the total current flowing through  $R_L$  will be 2mA, which by Ohm's law will cause 200V to be dropped across  $R_L$  leaving 100V on the anode—and this is the voltage the meter will indicate, an error of no less than 50 per cent. The unwary could go chasing non-existent faults unnecessarily.

Now consider a 20,000 ohms per volt meter with a full scale deflection of 50 $\mu$ A (Fig. 1c). This would show a truer picture since it only requires one twentieth of the current used by the first meter. The total current passing through  $R_L$  is now 1.05mA, causing a voltage drop of 210V, and leaving 90V on the anode, which would be indicated by the meter. Although not absolutely correct, this is a more reliable reading than the first example.

### VALVE VOLTMETER

A valve voltmeter with a very high input resistance, typically 10M $\Omega$ , would be better still since it would cause only an additional 20 $\mu$ A to flow through  $R_L$ , increasing the voltage drop to 102V and leaving 198V on the anode.

A valve voltmeter uses a kind of impedance converter which allows a milliammeter or microammeter with an inherently low impedance to be connected into a high impedance circuit without adversely affecting the true value being measured.

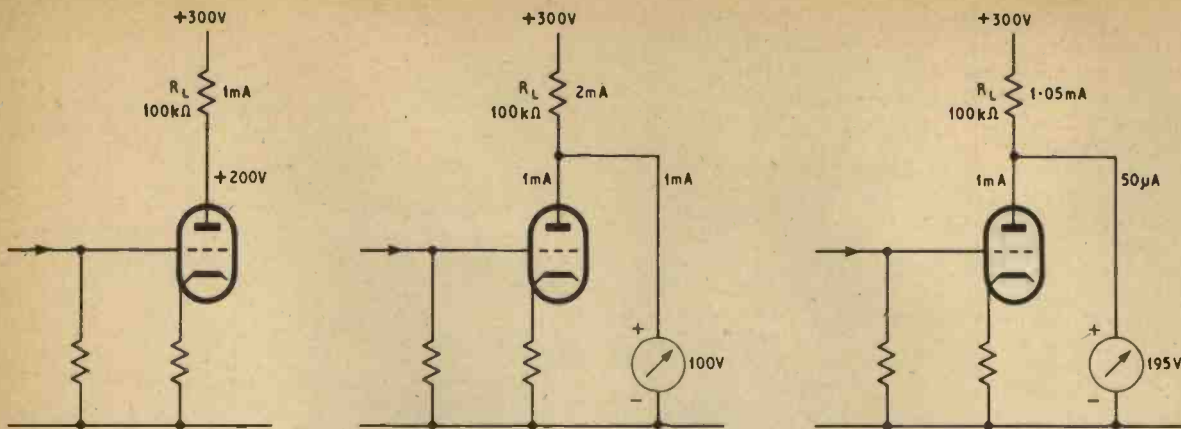


Fig. 1. Illustrating the effect of circuit loading on anode voltage when using meters of differing sensitivity

The ideal v.v.m. would be one having infinite input impedance and zero output impedance which are in practice unattainable, although a number of proven circuits do go a long way towards the ideal. They are necessarily comparatively complex and correspondingly expensive. However, it is possible for most amateur needs to be fulfilled by simpler and cheaper circuits.

Impedance conversion is not the only function of a v.v.m. for it has also to provide a degree of current amplification. On the 1 volt range for instance the current extracted from the circuit under test is  $0.1\mu\text{A}$ . This gives an f.s.d. reading on the meter of  $50\mu\text{A}$  necessitating an amplification of 500 times or 54 decibels.

The valve operates as a push-pull cathode follower, the two halves of the double triode V1a and V1b being balanced for current equality by means of the potentiometer VR1, when of course the meter will not register (see Fig. 2). The circuit is in effect a balanced bridge which is unbalanced when a voltage is applied upon either grid, the unbalance being shown by a deflection on the meter. This unbalance will depend on the polarity of this voltage, so that a centre-zero meter would register either way.

In practice it is preferable, and usual, to use an ordinary meter and use a polarity reversal switch which adds a slight complication but effectively doubles the scale length of the meter. The grid of V1a is connected to the potential dividing resistors R1 to R5 via R13 which reduces the ratio of maximum to minimum grid resistance as S1 is rotated. Without R13 the maximum resistance in circuit is  $10\text{M}\Omega$  on the 1V range and  $20\text{k}\Omega$  on the 500V range—a ratio of 500:1.

With R13 in circuit the maximum grid resistance is about  $13\text{M}\Omega$  and the minimum about  $3\text{M}\Omega$ , a ratio of 4.3:1. This reduces the variations in zero setting due to grid current which would be caused by the extreme variation in grid resistance without R13. This variation is also reduced still further by running the valve with a very low anode potential.

The potentiometer VR1 enables the electrical zero to be set to coincide with the mechanical zero. It also enables the pointer to be positioned anywhere on the scale, which is a most useful facility since it enables the v.v.m. to be used as a centre-zero meter for f.m. receiver alignment.

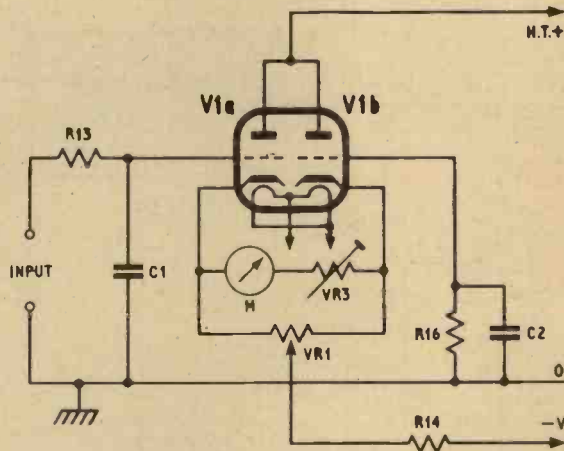


Fig. 2. Circuit diagram of a basic bridge valve voltmeter

VR2 and VR3 are selected as required by S2 and fulfil the following functions. VR3 allows the meter to be calibrated for a given input and is not used after initial calibration is complete, it is made a preset control. VR2 allows the meter to be set to full scale deflection for resistance measurement. Since it will require periodical adjustment, it is brought out as a front panel control.

S2 also reverses the meter polarity so that either a positive or a negative potential (with respect to chassis) can be measured, when VR3 will be in circuit. On the "ohms" range VR2 is brought into use. In the "off" condition the meter is disconnected from circuit and a short circuit placed across it, which effectively damps the movement, protecting the needle from excessive swinging during transit. When not in use the unit must also be disconnected from the power supply by S3.

#### OHMMETER

The ohmmeter is part of the v.v.m. circuit and allows a very wide range of resistance to be measured, which in the prototype was made from  $1\Omega$  to  $100\text{M}\Omega$ .

The top range could be increased to 1,000M $\Omega$  if a standard 100M $\Omega$  resistor is obtainable. The circuit operates by measuring the voltage present at the junction of the standard resistor R5 and the unknown resistor Rx both of which are connected in series across the reference voltage (see Fig. 3).

In the complete circuit the standard resistor is replaced by resistors R6 to R12 and the reference voltage is provided by a 1.5V pen torch cell; full-scale deflection is set by VR2.

In this context it must be explained that the electronic ohmmeter works in reverse to the normal type in which f.s.d. corresponds to zero resistance. If the unknown resistor Rx is now connected in circuit the meter will indicate the reading which is proportional to the ratio of Rx to Ry. When Rx = Ry the meter will read mid-scale.

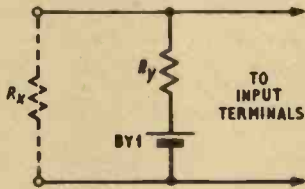


Fig. 3. Ohmmeter grid divider circuit showing how input voltage varies with terminal resistance

## POWER SUPPLY

The power supply requirements are very modest so that a comparatively simple circuit is quite adequate. The h.t. required is -65V, +65V at 3.5mA, the negative supply being used for grid biasing. Smoothing is provided by C3, C4 and R19, the negative voltage being developed across R18.

## COMPONENTS

Fig. 4 shows the complete circuit with the voltage dividing network R1-R5 for selecting the appropriate voltage range. The standard resistors for the ohms ranges are selected by S1b.

Stability of indication is as important as initial calibration accuracy, for it is pointless calibrating a meter to a fine accuracy if it is going to be wildly inaccurate on a subsequent occasion.

Variations due to fluctuating h.t. and heater supplies are largely cancelled out due to the push-pull operation, so one has to look further afield for possible sources of trouble.

The potential divider resistors R1-R5 must be of the highest quality possible, preferably 1 per cent high stability types, though 5 per cent hi-stabs could be used if one is prepared to accept a reduction in overall accuracy. Resistors R6 to R12 should also be 1 per cent hi-stab types, these being R13 and R16 although here accuracy can be relaxed to 5 per cent or even 10 per cent.

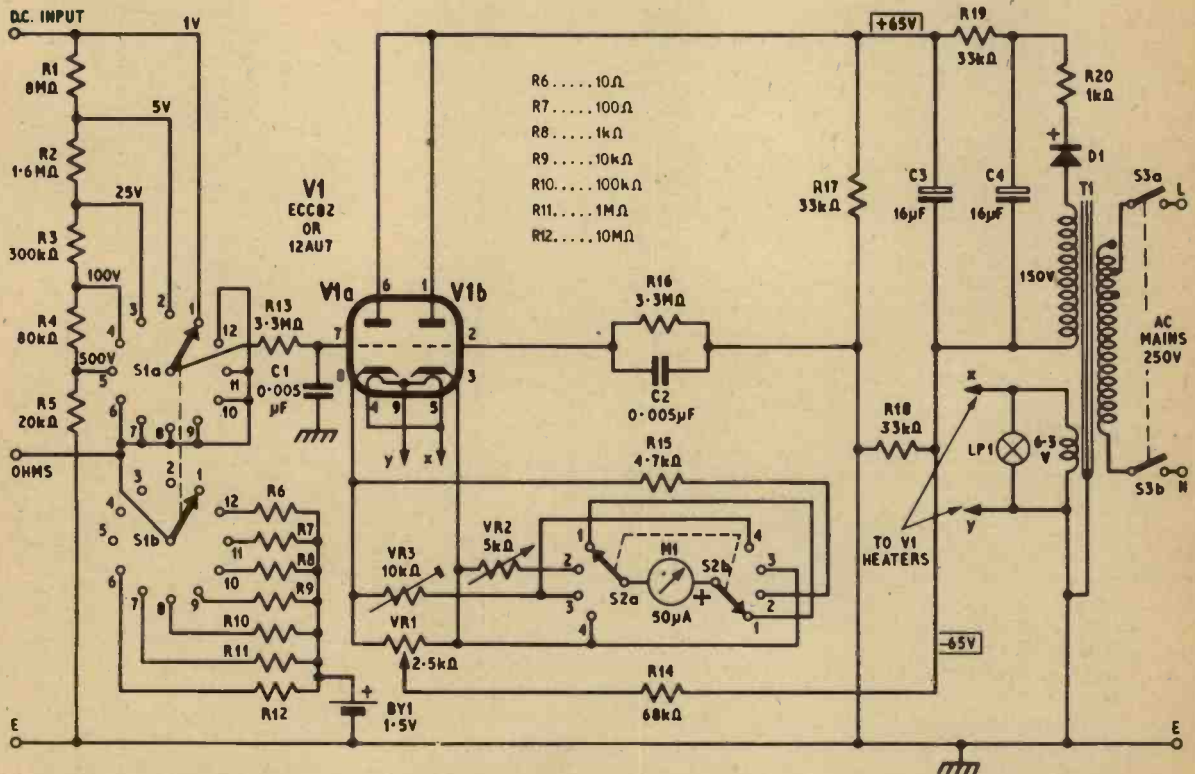


Fig. 4. Circuit diagram of the valve voltmeter and ohmmeter. The following are the function ranges for S1 and S2

D.C. Volts (S1)		Ohms (S1)		S2 Ranges	
Position 1	1V	Position 6	$\Omega \times 10^2$	Position 1	Meter Off
Position 2	5V	Position 7	$\Omega \times 10^3$	Position 2	Ohms
Position 3	25V	Position 8	$\Omega \times 10^4$	Position 3	D.C. Negative Volts
Position 4	100V	Position 9	$\Omega \times 10^5$	Position 4	D.C. Positive Volts
Position 5	500V	Position 10	$\Omega \times 10^2$		
		Position 11	$\Omega \times 10$		
		Position 12	$\Omega \times 1$		

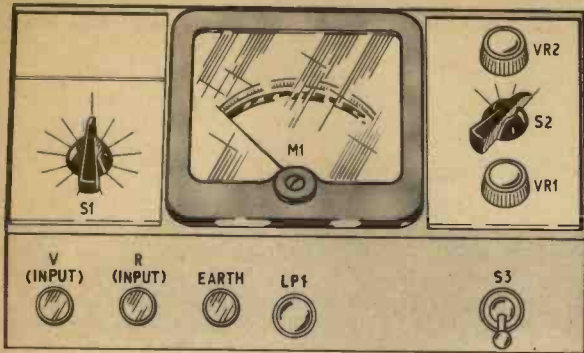


Fig. 5. Front panel layout

The only capacitors deserving special mention are C1 and C2, which decouple both grids against any a.c. signals which may reach them. Although the actual value is unimportant their insulation properties must be absolutely first class. Since they are both connected across very high resistances, any leakage will adversely affect the v.v.m. Any value from 0.001 $\mu$ F to 0.01 $\mu$ F should prove suitable particularly if they are polystyrene or silver mica types.

The range switch S1 must be of good quality. Although the author was fortunate enough to possess an instrument quality stud switch, it is possible that most constructors will not have one to spare—and they are expensive items to buy new. The wafer switch specified should however prove quite satisfactory. S2 can also be a wafer switch with only 4 of the 6 ways used.

The meter will almost certainly be the most expensive single item. The larger the meter the more accurately and easily can readings be made. It must be borne in mind that some meters are accurate only if used vertically or horizontally.

The valve can be any medium impedance double triode such as the one specified. The valve holder should preferably have either ceramic or p.t.f.e. insulation to minimise capacitance leakage between adjacent pin connectors.

### CONSTRUCTION

The cabinet was constructed from  $\frac{1}{2}$ in softwood for the sides and hardboard for the front, rear, and bottom. Many of the dimensions given in Fig. 6 are the inside ones and are given for guidance only. It is possible that the positions of some holes may require altering to suit different components.

The final angle or slant on the cabinet was chosen because it permits easy meter viewing whether one is standing or sitting, a great convenience although it

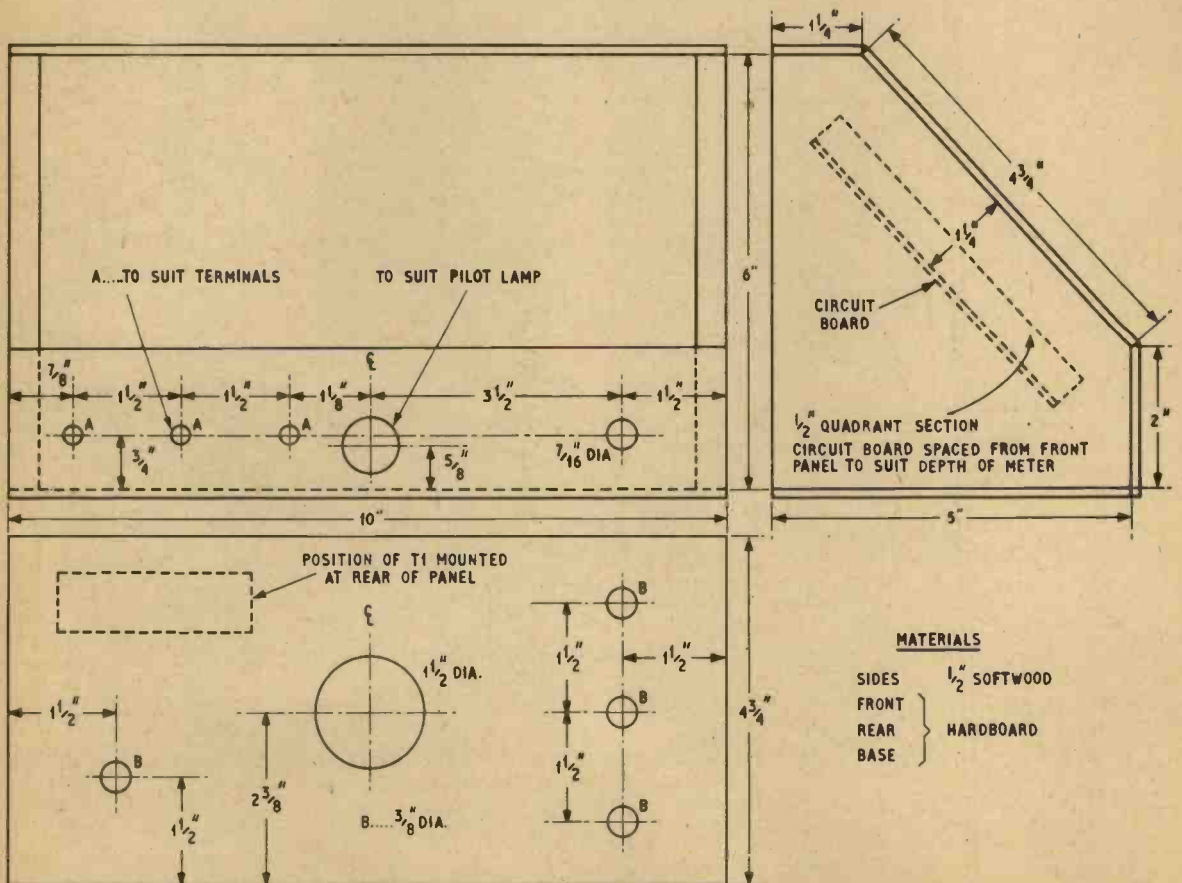


Fig. 6. Constructional and drilling details of panel assembly

# COMPONENTS . . .

## Resistors

- R1 8M $\Omega$  (4.7M $\Omega$  + 3.3M $\Omega$  in series)
- R2 1.6M $\Omega$  (3.3M $\Omega$  + 3.3M $\Omega$  in parallel)
- R3 300k $\Omega$  (150k $\Omega$  + 150k $\Omega$  in series)
- R4 80k $\Omega$  (47k $\Omega$  + 33k $\Omega$  in series)
- R5 20k $\Omega$  (10k $\Omega$  + 10k $\Omega$  in series)
- R6 10 $\Omega$  1%,  $\frac{1}{4}$ W (metal film) (Waycom)
- R7 100 $\Omega$
- R8 1k $\Omega$
- R9 10k $\Omega$
- R10 100k $\Omega$
- R11 1M $\Omega$
- R12 10M $\Omega$
- R13 3.3M $\Omega$  5%,  $\frac{1}{4}$ W
- R14 68k $\Omega$  10%,  $\frac{1}{4}$ W
- R15 4.7k $\Omega$  10%,  $\frac{1}{4}$ W
- R16 3.3M $\Omega$  5%,  $\frac{1}{4}$ W
- R17 33k $\Omega$  10%, 1W
- R18 33k $\Omega$  10%, 1W
- R19 33k $\Omega$  10%, 1W
- R20 1k $\Omega$  10%, 1W

All 1% high stability,  $\frac{1}{4}$ W except where otherwise stated. Alternative resistor combinations shown in brackets should also be 1%

## Potentiometers

- VR1 2.5k $\Omega$  linear carbon
- VR2 5k $\Omega$  linear carbon
- VR3 10k $\Omega$  linear carbon preset

## Capacitors

- C1 0.005 $\mu$ F mica 350V
- C2 0.005 $\mu$ F mica 350V
- C3, 4 16+16 $\mu$ F elect. 350V

## Transformer

- T1 Mains Transformer:  
Pri. 200-250V mains;  
Sec. 1. 150V 5mA; Sec. 2. 6.3V 0.4A

## Valve

- V1 ECC82 or 12AU7

## Rectifier

- D1 250V 50mA contact cooled, half wave

## Meter

- M1 50 $\mu$ A f.s.d. 1,100 $\Omega$  int. resistance (type Sifam M202) or MR3P (Henry's Radio)

## Switches

- S1 2 pole 12 ways (2 bank wafer switch)
- S2 2 pole 6 ways (2 ways not used)
- S3 Double pole on/off toggle switch (see text for notes on S1 and S2)

## Miscellaneous

- BY1 1.5V pen torch cell
- LPI Lamp 6V m.e.s. with holder
- Valveholder B9A ceramic or p.t.f.e.
- Insulated screw terminals (3 off)
- Turret tags and soldering eyelet tags
- Four knobs

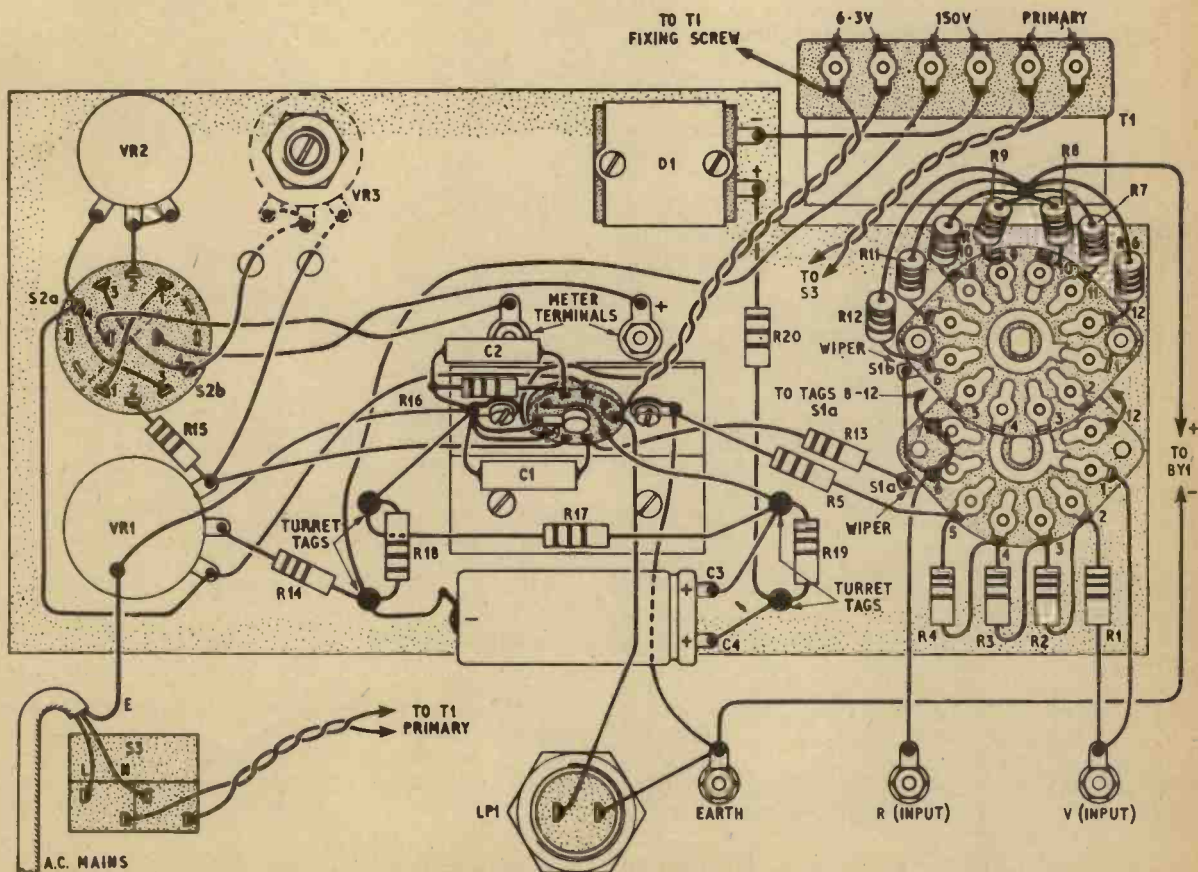


Fig. 7. Component assembly and wiring details

must be stressed that most accurate readings are made by viewing straight in line with the meter needle. Use of a mirror which is sometimes fitted behind the needle of a high quality meter, is recommended for accurate interpretation of the meter reading. Ventilation holes are drilled along the top and bottom edges of the cabinet to allow the heat from the valve to escape.

Almost the entire circuit is assembled on a sheet of s.r.b.p. measuring  $9\text{in} \times 4\frac{1}{2}\text{in}$  (Fig. 7). This is fixed to the cabinet by  $\frac{1}{2}\text{in}$  quadrant section supports glued to the cabinet sides. The distance of these pieces from the front panel will depend upon the depth of the meter casing within the cabinet, since the connecting terminals of the meter also serve to hold it in place (see Fig. 8). If the meter holds the board quite firmly, these quadrant pieces may not be necessary.

The potentiometers and switches that have their spindles protruding through the front panel should be

## TESTING

The v.v.m. is now ready for testing but before the mains are connected the controls should be set as follows: S1 to 5 volts range; S2 to d.c. positive; VR1 to approximately mid-position; VR2 and VR3 with maximum resistance in circuit. The mains supply can then be connected and switched on.

As the valve warms up the meter needle will swing from side to side and then take up a definite position at or near the zero position. If not VR1 must be adjusted to bring the needle to zero. If zero can only be obtained with VR1 at one end of its track the valve is unbalanced and another specimen should be tried. If zero is obtained with VR1 at its mid-position, the two triodes are passing near equal cathode currents and all is well. The zero setting should not alter as S1 is run through all ranges, or if S2 is switched to d.c. negative or ohms.

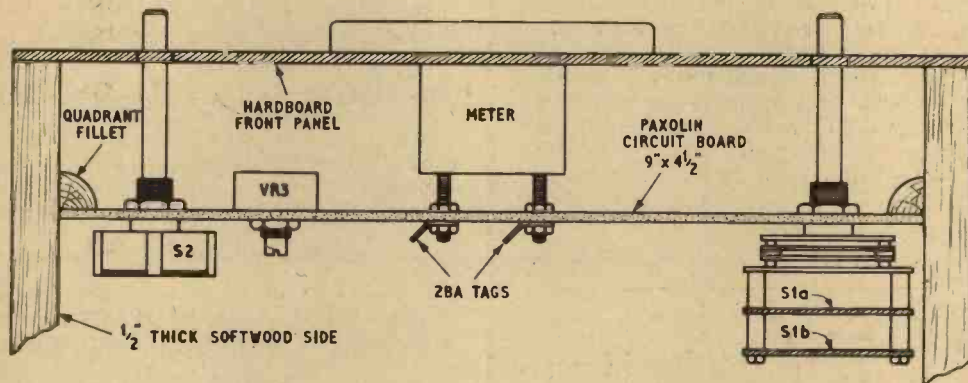


Fig. 8. Component board disposition relative to front panel. Note that fillet fixing distance will depend on the meter depth

fixed in position on the panel and corresponding holes drilled through the box. The s.r.b.p. panel is offered up to the front panel of the box from behind and the positions of the holes scribed on to the rear of the box front panel. Remove the s.r.b.p. panel then drill out the holes in the box.

A piece will have to be cut out of the s.r.b.p. to clear the mains transformer which is bolted to the front panel by 4 B.A. nuts and bolts. Four turret tags or 4 B.A. soldering tags are inserted into the s.r.b.p. in the positions shown to support R18, C3, C4, and R19.

The 1.5V pen cell is fixed to the side of the box, first removing the cardboard cover so that connection is made between the zinc case and the metal clip. A soldering tag is held under the clip fixing screw. This tag is then connected to the common earth terminal. A short piece of insulated wire is soldered to the battery positive terminal, the other end going to the junction of the resistance standards—a common tag situated as convenient for resistors R6 to R12.

Although wiring should be straight forward it is advisable to treat the high stability resistors with some care. The use of a heat shunt is advisable while soldering, for even the best hi-stabs will fail if roughly treated to an overdose of heat from the soldering iron. To avoid any risk of damage to the meter it should not be fixed in position until wiring is complete. It is advisable to reset the wiring and to remove any stray pieces of solder or wire that can have such disastrous results if overlooked.

## CALIBRATION

Calibration can be carried out after allowing ample time to settle down (about 10 minutes) using the circuit of Fig. 9. The  $10\text{k}\Omega$  linear potentiometer is adjusted until the standard meter reads precisely 5V when VR3 can be adjusted to allow the v.v.m. to read correspondingly. The zero setting should be checked and if necessary readjusted and then the full-scale reading rechecked. The two are slightly interconnected and several adjustments may have to be made. The battery and v.v.m. polarities should be reversed and the full-scale reading checked for a negative input. This reading should be identical whether one measures positive or negative voltages both, of course, with respect to earth.

The linearity of the v.v.m. scale can be checked by reducing VR1 slowly, comparing the standard and v.v.m. readings every 0.5V. The deviation should not exceed 5 per cent.

The calibration of the ohms ranges is somewhat more complicated, requiring the use of a resistance substitution box or a collection of 1 per cent standards. Five or 10 per cent standards could no doubt be used but, taking into account human, electrical and mechanical errors, the net result would not be of much use apart from rough resistance checks. Ideally also, each resistance range should be individually calibrated, a quite formidable task requiring a wide selection of standards.

It may be possible to calibrate one range (e.g. 10k $\Omega$ ) to a reasonable accuracy and assume the others to be calibrated automatically. Checks above and below with the occasional 1 per cent hi-stab resistors showed very little error, so that it is not unreasonable to suppose that overall accuracy is sufficient for most servicing needs.

#### NON-STANDARD RESISTOR VALUES

Some constructors may find it difficult to obtain the exact resistance values suggested for R1 to R5 as most of them are non-standard. These were chosen to allow a voltage step of 5:1 from range to range as this permits rather more overlaps at the bottom end of each range resulting in improved accuracy. Alternative combinations are given in the components list. Where 10 to 1 steps aren't objected to or where the specific values for R1 to R5 cannot be obtained, a change can be made in resistance values and R1 to R5 changed to 10M $\Omega$ , 1M $\Omega$ , 100k $\Omega$ , and 10k $\Omega$  allowing voltages of 1V, 10V, 100V, and 1,000V respectively to be measured. R5 can be deleted.

It is most inadvisable to replace this with a 1k $\Omega$  resistor and to try for a 10kV range as the insulating properties of the input terminal and S1a will almost certainly be inadequate. The quoted values for R1-R5 can be made up using two or more resistors in series or parallel in each case.

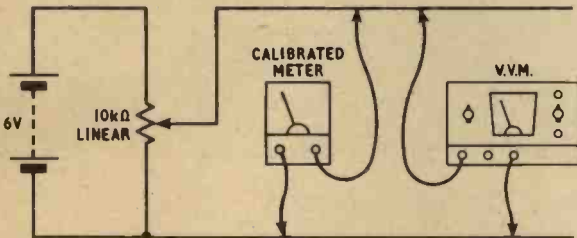


Fig. 9. Test set-up for calibration of the valve voltmeter

Some 12-way wafer switches are actually 11-way types; the twelfth position being used to switch off when the wafer is left on its input wiper position. In this case the seven resistance ranges can be retained and the voltage range converted to the 1V, 10V, 100V and 1,000V sequence, resulting in a total of 11 ranges. The switch must never be left "off" when the v.v.m. is switched on as the grid will be "floating" with consequently possible damage to the valve.

It is desirable to mark the scales on the meter dial. Particular care is necessary when removing the meter movement from its case. Before doing so turn S2 off to damp the movement. Be careful not to touch the needle otherwise it may be easily damaged or bent. A fine mapping pen is suitable for marking the dial. Switch S1 and S2 to the appropriate positions for calibration. On completion of calibration switch S2 to off and carefully replace the movement in the case.

In conclusion, a word of warning. Always bear in mind that one meter lead is earthed so that any attempt to measure directly across a floating voltage may have dire consequences. A floating voltage is one that has a certain potential difference across, for example, a resistor, both ends being above chassis potential. ★

# CONSTRUCTION PROJECTS

## in Next Month's Issue

### LIGHT-OPERATED STOPWATCH

This photo-electric detection device operates a stopwatch to ensure accurate timing from start to finish at athletics meetings, motor rallies, and similar sporting events.

### SCOOTER ALARM SYSTEM

An instant alarm system to prevent a scooter and its accessories from being stolen.


### BASS GUITAR

Detailed plans and instructions for the construction of an electronic bass guitar. Volume and tone controls are included.



MAY ISSUE ON SALE APRIL 14  
Order your Copy Now!

# ELECTRONORAMA

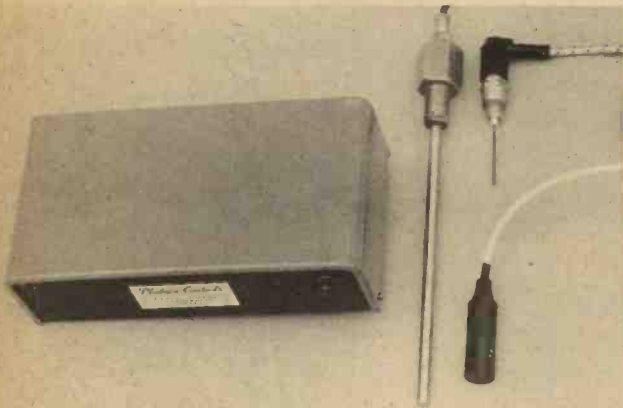

## Capacitance Probe Proximity Detectors


CAPACITANCE type proximity detectors often depend upon a change of capacitance relative to earth to alter the balance in a bridge network. These systems are not always suitable for all applications because the area of capacitance between probe and "earth" becomes a factor which limits the use of such probes near pipes and girders.

Photain Controls of Leatherhead have a Patent Application on a system, which overcomes this difficulty, using a high frequency oscillator. Two equally balanced coils form a balanced bridge with no reference to earth other than by fixed capacitors. The probe area can be to any required dimension and the capacitance detection area is fully directional. Our photograph above shows the control unit with three probes for different applications such as counting, limit switching, conveyor process control, or liquid level control.


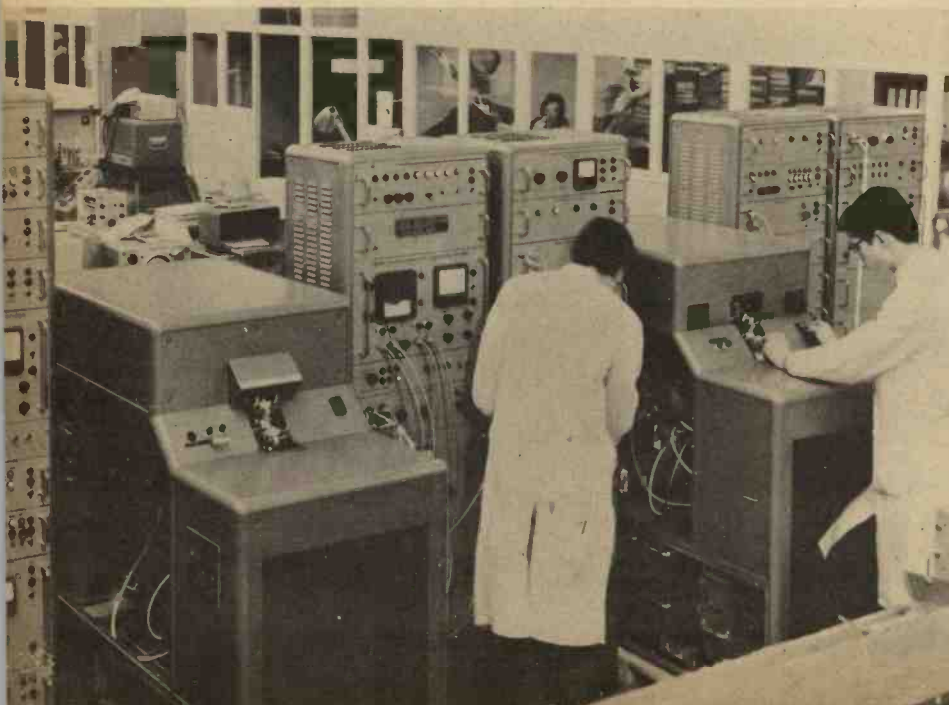
## Micro-integrated Computer

AN English Electric Leo Marconi computer production centre, now under construction at Winsford, Cheshire, will produce the new System 4 computers under the managership of Mr I. H. Owen, who is seen top right with System 4 magnetic tape units at Kidsgrove. These computers are said to be Britain's most advanced third generation machines and use micro-integrated circuits.



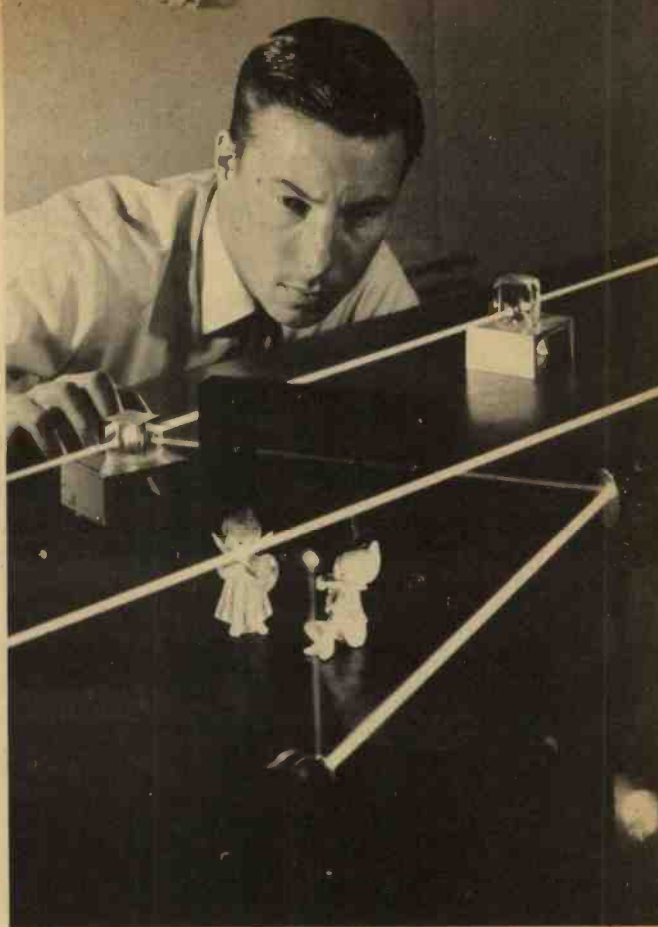
## Automatic Sorters for Capacitors

THESE clean-line consoles (left) are German Klemt automatic capacitor sorters being tested by engineers of the U.K. agents Livingstone Electronics.


An operator places components to be tested in the sixty sets of jaws on a large rotating wheel. Pre-programmed tests are carried out as the wheel rotates, then components are sorted into grade or reject bins. The programmed test equipment is housed in the adjacent racks.




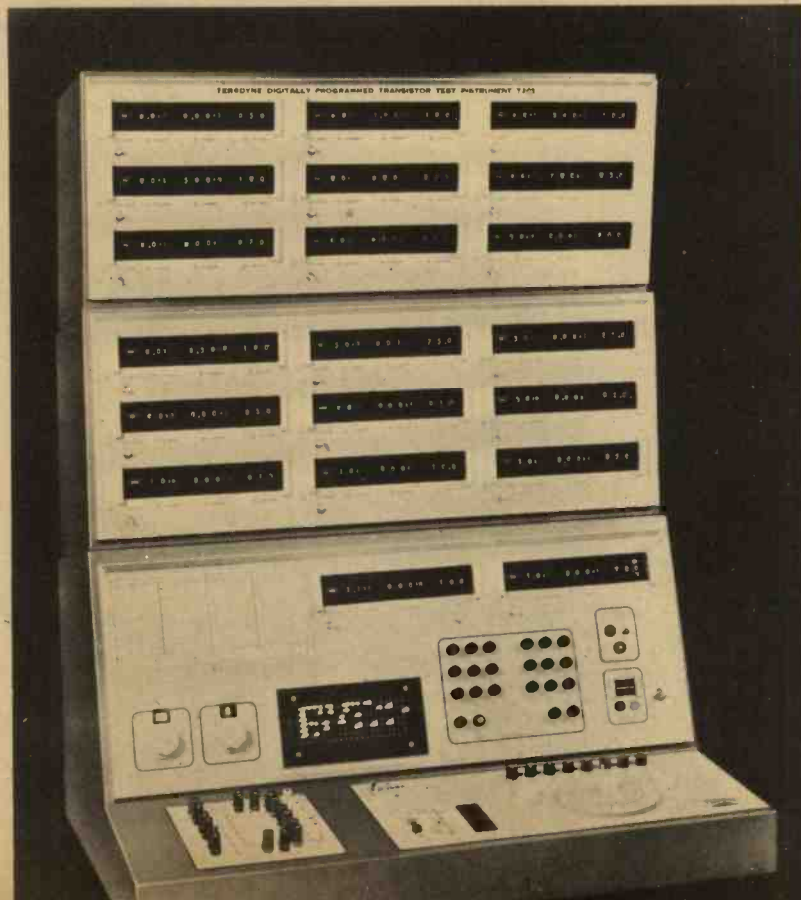
## Laser Photography

**H**OLOGRAPHY, a technique of lensless photography, is one of the latest uses of the laser's "light fantastic". Dr Ronald Lundgren of Hughes Aircraft Company's research laboratories in California is shown (right) recording a "hologram", a true three-dimensional image, without the use of a lens. In the holographic reconstruction of the image, by playing the laser light back through the plate, one can see the pixie-like figurines in foreground in true three-dimensional form from any angle, as if looking through a window. Scientists believe that holographic techniques may someday be used for target recognition from air to ground, and that we may eventually have holographic movies and television.



## A Mere Bagatelle!

**T**HIS machine may look a bit like a pin-table indicator board but, in fact, is a highly sophisticated transistor tester, the Teradyne T207. This is an automatic, high-speed, go/no-go instrument for production line testing. Standard industrial d.c. tests are performed in 35 milliseconds per semiconductor.

On automatic handling over 4,000 transistors are tested per hour.

Programming all conditions for each test is easily performed at a single position on the front panel. Programming switches are so arranged and test circuits are so designed that it is not possible to damage inadvertently the device under test, the test instrument, or even the operator.

For highly complex classification and for data logging requirements, the T207 is readily modified for control by a digital computer.

Modular construction with digital readout is under a 10 year guarantee. The price?—around £7,000. A Rolls Royce or a mere bagatelle?

S.T. ANDREWS  
AUTHOR

Some time ago the writer developed a form of constitutional laziness, this being an objection to shouting "come in!" over the noise of an office, whenever anyone knocked on the door. It was therefore decided to build some simple electronic gadget which would give a visible signal, for example the lighting of a lamp, whenever there was a sharp tap on the door.

Such a device was built, tested, and is the subject of this article.

There are almost unlimited variations on the application of the circuit described, both in its basic use, and in the method of display of the results.

THE Door Slave is, essentially, a sound-sensitive switch: whenever a sound is picked up by a microphone a relay closes for a few seconds, then it is de-energised and the circuit returned to the resting state. The relay is made to operate a lamp or whatever other function may be required. The circuits required to do this are simple and form the basic unit. Modifications and extensions can be added later and will be discussed at the end of this article.

# DOOR SLAVE

COME  
IN

ENGAGED

BACK  
LATER



## THE BASIC UNIT

The block diagram of the basic unit is given in Fig. 1 and the circuit diagram in Fig. 2.

TR1 and TR2 form a conventional two-stage voltage amplifier with a voltage gain of about 200 times, consequently an input of a few millivolts will give up to one volt output across resistor R9. The actual gain is dependent on the sensitivity control, VR1, and the method of setting this will be described later. TR1 and TR2 are decoupled from the rest of the circuit by R10 and C8. As it stands the circuit is best fed from a crystal microphone; this can be a cheap type since the fidelity is obviously not important, but anything giving an output of a few millivolts will do.

## INTEGRATOR

The output from TR2 is taken to a very simple form of integrating circuit, D1, R11, R12 and Cx. The function of this circuit is to take the a.c. signal output of the amplifier and convert it into a short d.c. pulse which is then amplified by TR3. The value of Cx in this circuit is very variable; it may need to be several  $\mu$ Fs in order to get a good output pulse but, conversely, as in the writer's prototype, it may work best with Cx missing entirely. TR3 is merely a d.c. amplifier and in the resting stage it is biased to cut-off. A sudden signal applied to the amplifier will be converted, by the integrator, to a negative-going pulse tending to cause TR3 to conduct and producing a positive-going pulse across R14.

TR4 and TR5 together form a monostable switch, or flip-flop. In the resting state TR4 is conducting and the voltage developed across the collector load is

passed to TR5 via R17 keeping TR5 cut off and its collector negative. When a positive-going pulse is applied to TR4 base this transistor is temporarily cut off and TR5 conducts instead. This condition lasts, however, only for a short time, until C7 has charged enough to allow TR4 to begin conducting again; an avalanche action then occurs and the circuit flops back to its initial state with TR5 cut off. The triggering voltage pulse appearing across R14 is coupled to the flip-flop by C6 and R15.

The flip-flop cannot, as it stands, drive a relay directly and so a current amplifier is needed. This is the function of TR6 which is coupled to TR4 via R21 and has the relay RLA as its collector load. As long as TR4 is conducting and its collector is at nearly the zero line voltage, this transistor will be held cut off. When the flip-flop is triggered and TR4 ceases to conduct temporarily, then the base of TR6 rises to near the  $-9$  volt line, the transistor conducts and the relay operates.

The circuit action can be summarised as follows: When a sound of sufficient amplitude is picked up by the microphone it is amplified, converted to a d.c. voltage pulse, and used to trigger a flip-flop. As long as this remains in the triggered state the relay will be closed and the appropriate action will occur. After a short time the flip-flop will revert spontaneously to the stable state and the relay will be de-energised.

## REMOTE CONTROL UNIT

So far only the most basic circuit has been described and to make the device into a practical unit, some form of control unit is very desirable. This is simply to enable the Door Slave to be controlled from where the operator normally sits.

The recommended system of wiring between the control unit, the main unit, and the lamp unit is given in Fig. 3. It will be seen that a 9-way cable connects the control unit to the main unit, and a 4-way cable links the latter with the lamp unit.

Controls mounted on the control unit are: S1, overall on/off; S4, the lamp selector, i.e. "come in", "engaged",



Fig. 1. Block diagram of the basic unit


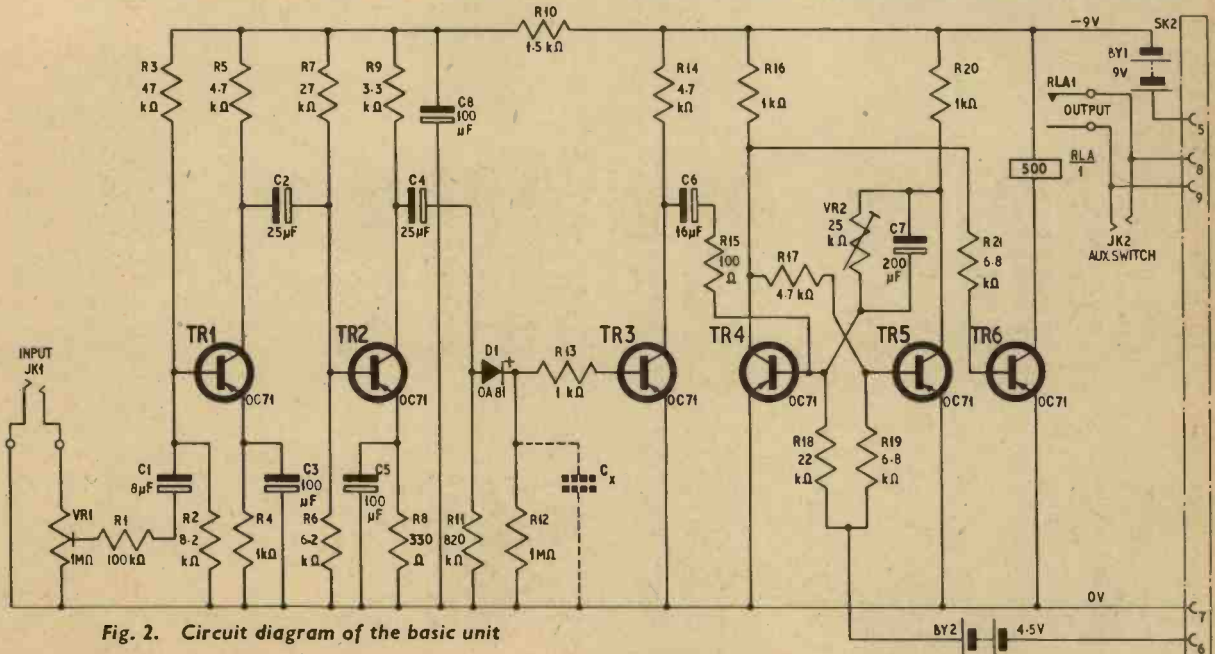


Fig. 2. Circuit diagram of the basic unit

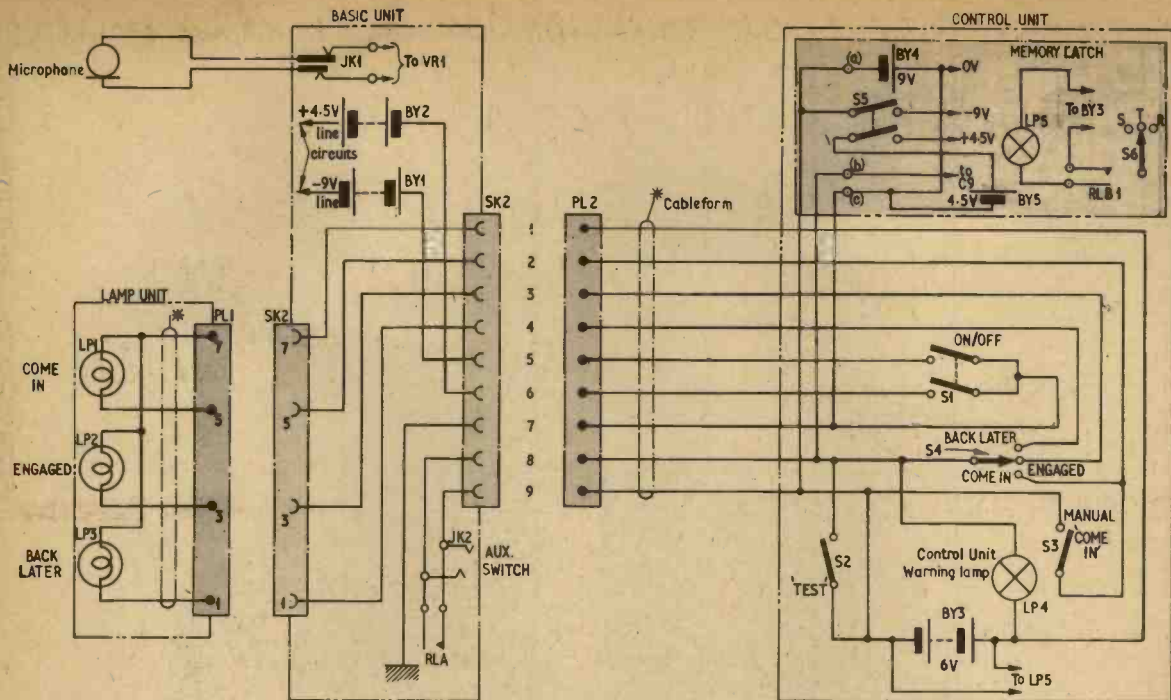

## COMPONENTS . . .

### Resistors

R1 100k $\Omega$	R8 330 $\Omega$	R15 100 $\Omega$
R2 8.2k $\Omega$	R9 3.3k $\Omega$	R16 1k $\Omega$
R3 47k $\Omega$	R10 1.5k $\Omega$	R17 4.7k $\Omega$
R4 1k $\Omega$	R11 820k $\Omega$	R18 22k $\Omega$
R5 4.7k $\Omega$	R12 1M $\Omega$	R19 6.8k $\Omega$
R6 6.2k $\Omega$	R13 1k $\Omega$	R20 1k $\Omega$
R7 27k $\Omega$	R14 4.7k $\Omega$	R21 6.8k $\Omega$

All  $\pm 10\%$ ,  $\frac{1}{4}$ W carbon

### Potentiometers

VR1 1M $\Omega$ Preset
VR2 25k $\Omega$ Preset

### Capacitors

C1 8 $\mu$ F 12V	C5 100 $\mu$ F 6V
C2 25 $\mu$ F 12V	C6 16 $\mu$ F 12V
C3 100 $\mu$ F 6V	C7 200 $\mu$ F 15V
C4 25 $\mu$ F 12V	C8 100 $\mu$ F 12V

All miniature electrolytic.

### Transistors

TRI-6 OC71 (6 off)

### Diode

D1 OA81

### Relay

RLA 500 $\Omega$  coil. One make-break contact.

### Switches

- S1 Double pole on/off
- S2 Single pole on/off
- S3 Single pole on/off
- S4 Single pole 3-way  
(may be separate component or ex G.P.O. telephone switchboard—see text)

### Plugs and Sockets

- SK1, 2 B9A valveholder (2 off)
- PL1, 2 B9A plug (2 off)
- JK1, 2 Open circuit jack socket 2 (off)

### Batteries

- BY1 9V
- BY2 4.5V
- BY3 6V

### Lamps

LPI (etc.) 6V 0.3A (quantity as required)

### Miscellaneous

**BASIC UNIT:** Wooden baseboard 6in  $\times$  7in; metal or wooden case 6in  $\times$  7in  $\times$  4in.  
Two 20-way group boards, or tag strips  
Crystal microphone and jack plug

**CONTROL UNIT:** \*Metal panel 12in  $\times$  4in  
Baseboard 12in  $\times$  9in. Metal or wooden case 12in  $\times$  4in  $\times$  9in

(\*not required if ex G.P.O. telephone switchboard is used)

**LAMP UNIT:** Plywood for case. Three M.E.S. batten type lamp holders. Connector block. Perspex sheet 3in  $\times$  1 $\frac{1}{2}$ in  $\times$  8in  
Wire for inter-unit connections

### MEMORY UNIT

Components for the Memory Unit will be given next month

# G

## GET A GOLDRING HI-FI TURNTABLE UNIT FOR YOUR AMPLIFIER



### GOLDRING-LENCO G.99

Incorporates the unique Goldring-Lenco continuously variable speed control and vertical drive features. Machined 8 lb. non-magnetic turntable. Push-button switching. Neon-lit stroboscope. Speed constant within 1% for up to 13% mains voltage change. £21.19.5d.

### GOLDRING-LENCO GL 68

Continuously variable speed control with adjustable click-in positions for standard speeds. Arm takes interchangeable head-slides, and is raised and lowered by on/off switch. Wired for mono and stereo. £19.10.7d.



There's a Goldring, or Goldring-Lenco unit to match *any* amplifier—whether you build it or buy it. At the modest end of the scale there's the G.66 integrated hi-fi unit that comes complete with pick-up arm and cartridge for as little as 11 gns. Then there's the highly popular GL 68 (see left) and, for the man who wants the best he can get there's the GL 70 transcription unit with integrated transcription arm at a little under £30, or the sophisticated G 99 without arm, at around £22. Goldring hi-fi equipment includes transcription arms from 7 gns. upwards and a wide choice of cartridges. The coupon will bring you full descriptive leaflets.

### GOLDRING HI-FI EQUIPMENT

AUDIO FAIR — BOOTH No. 41 and ROOM No. 334



To: GOLDRING MANUFACTURING CO. (G.B.) LTD., 486-488 High Road, Leytonstone, London, E.11.

Please send me descriptive leaflets on

- TURNTABLE UNITS     TRANSCRIPTION ARMS  
 MONO & STEREO CARTRIDGES     HI-FI ACCESSORIES

Name \_\_\_\_\_

Address \_\_\_\_\_

To: Goldring Manufacturing Co. (G.B.) Ltd., 486 High Road, Leytonstone, London, E.11. Telephone: Leytonstone 8343


**HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT Type TA1**

- Peak output in excess of 1½ watts.
- All standard British components.
- Built on printed circuit panel, size 6 x 3in.
- Generous size Driver and Output Transformers.
- Output transformer tapped for 3 ohm and 15 ohm speakers. ● Transistors (GET 114 or S1 Mullard OC81D and matched pair of OC10 (p/p) x 9 volt operation. ● Everything supplied, wire, battery clips, solder, etc. ● Comprehensive easy to follow instructions and circuit diagram 1/6 (Free with Kit). All parts sold separately. SPECIAL PRICE 45/- P. & P. 3/-. Also ready built and tested, 52/6. P. & P. 3/-. A pair of TA1s are ideal for stereo.



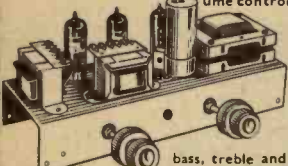**STEREO AMPLIFIER**

Incorporating 2 ECL86s and 1 E280, heavy duty double wound mains transformer. Output 4 watts per channel into 3 ohm speakers. Full tone and volume controls. Absolutely complete.



**ONLY £4.19.6**  
P. & P. 8/-

Super Deluxe version with ECL86 valves, sep. bass, treble and balance controls, full feedback, 4 watts per channel into 3 ohm speakers. 8 gns. P. & P. 8/-.

**WELL-KNOWN MAKERS' SURPLUS ONE TRANSISTOR PRE-AMP.**

Suitable for use with Medium or High Impedance mics, guitars, gram pickups, tape decks, etc. For operation from 200/300 volt H.T. rail or 9 volt battery. Gain approx. 14:1. Fully isolated input by Mu-Metal screened transformer. Size 4" x 1" x 1". Ready built complete with full circuit diagram and instructions. ONLY 15/- Post free.

**SPECIAL PURCHASE! TURRET TUNERS**

By famous maker. Brand new and unused. Complete with PCC84 and PCF80 valves 34-38 Mc/s I.F. Biscuits for Channel 1 to F 8 and 9. Circuit diagram supplied. ONLY 25/- each. P. & P. 3/9.

**GÖRLER F.M. TUNER HEAD**

88-100 Mc/s 10.7 Mc/s I.F., 15/-, plus 2/- P. & P. (ECC85 valve, 8/6 extra).

**TAPE DECKS**

B.S.R. MONARDECK (Single speed) 3½in. per sec., simple control, uses 5½in. spools, £6/13/-.

LATEST COLLARO MAGNAVOX 363 TAPE DECK DE LUXE. Three speeds, 2 track, takes up to 7 in. spools. 10 gns. Plus 7/6 carr. and ins. on each. (Tapes extra on both.)

**QUALITY PORTABLE TAPE RECORDER CASE.** Brand new. Beautifully made. Few only at 49/6. P. & P. 8/6.

**ACOS CRYSTAL MIKES.** High imp. For desk or hand use. High sensitivity, 18/6. P. & P. 1/6.

**TSL CRYSTAL STICK MIKE.** Listed at 45/-. Our price, 18/6. P. & P. 1/6.

**TWIN TELESCOPIC AERIAL.** Two 3-section heavily chromed rods. Closed 12-in. each extending to 32 in. Completely adjustable. Universal mounting brackets, coax lead and plug. Ideal for F.M. or T.V. 12/6. P. & P. 2/6.

**QUALITY RECORD PLAYER AMPLIFIER Mk II**

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, EZ80 valves. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3in. d. x 6in. h. Ready built and tested. PRICE 69/6. P. & P. 6/-.

ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 69/6. P. & P. 7/6.

**DE LUXE QUALITY PORTABLE R/P CABINET**

Uncut motor board size 14½in. x 12in. clearance 2in. below, 5½in. above. Will take above amplifier and any B.S.R. or GARRARD Autochanger or Single Player Unit (except AT60 and SP25). Size 18in. x 15in. x 8in. PRICE £39/6. P. & P. 9/6.

**4-SPEED PLAYER UNIT BARGAINS**

All brand new in maker's original packaging.  
SINGLE PLAYERS  
B.S.R. TU/12 ..... £39/6. Carr. 5/6.  
GARRARD SP25 De Luxe... £10/10/0. Carr. 5/6.  
B.S.R. GU7 with unit mounted pickup arm. £4/18/8. Carr. 5/6.

**AUTO. CHANGERS**

Latest B.S.R. UA25 Super sli... £6 2 6  
GARRARD 1000 with special Hi-Fi cart. £6 19 6  
GARRARD 2000 ..... £7 10 0  
GARRARD 3000 ..... £8 13 0  
GARRARD AT60 £9.19.6. Carr. 6/6 on each.  
All the above units are complete with 1½ mono head and sapphire sli or can be supplied with compatible stereo head for 12/6 extra.

**BRAND NEW CARTRIDGE BARGAIN!**

ACOS GP67. Mono complete. List price 21/-. Our price 13/6. P. & P. 2/-.

**BRAND NEW. 12" 15w. H/D Speakers, 3 or 15 ohm.** Current production by well-known British maker. Offered below list price at 89/6. P. & P. 5/-.  
Guitar models: 25w. £5.5.0.; 35w. £8.8.0.

**BRAND NEW 3 OHM LOUSPEAKERS**  
5 in. 12/6; 6½ in. 15/-; 8 in. 21/-; 10 in. 25/-; 7 in. x 4 in. 15/-; 10 in. x 6 in. 26/-.  
E.M.I. 8 in. x 5 in. with high flux magnet 21/-.  
E.M.I. 13½ x 9 in. with high flux ceramic magnet, 42/- (15 ohm, 45/-). P. & P. 4/- 5" 2½", 6½" & 8" 2/6, 10" & 12" 3/6 per speaker.

**E.M.I. PLASTIC CONED TWEETER.**  
2½". 3 ohm. Limited number: 12/6 each, P. & P. 1/6.

**SPECIAL OFFER!**

Limited number of 12 in. 10 watt "R.A." Speakers: 3 ohm 25/-; 15 ohm, 27/6. P. & P. 3/6.

**VYNAIR and REXINE SPEAKER AND CABINET FABRICS** app. 54 in. wide. Usually 35/- yd., our price 13/6 per yd. length (min. 1yd.) P. & P. 2/6. S.A.E. for samples.

**7-10 watt OUTPUT TRANSFORMERS** to match pair of ECL 86's in push-pull to 3 ohm output. ONLY 11/- P. & P. 2/6.


**MAINS TRANSFORMER** for resistor power supplies. Tapped pri 200-250v. Sec. 40-0-40 at 1 amp (with electrostatic screen) and 6.3v. at .5 amp for dial lamps etc. Drop thro mounting. Stack size 14" x 3½" x 3½" 27/6. P. & P. 4/6.

**MATCHED PAIR OF 10 WATT TRANSISTOR DRIVER AND OUTPUT TRANSFORMERS.** Stack size 1½ x 1½ x 8 in. Output trans. tapped for 3 ohm and 15 ohm output. 10/- pair plus 2/- P. & P.

**SPECIAL OFFER! FM/AM TUNER HEAD**

Beautifully designed and precision engineered by Dormer and Wadsworth Ltd. Supplied ready fitted with twin .0005 tuning condenser for AM connection.

Prefined FM section covers 86—102 Mc/s. I.F. output 10.7 Mc/s. Complete with ECC85 (12V) valve and full circuit diagram of tuner head. Another special bulk purchase enables us to offer these at 27/6 each. P. & P. 3/-. Order quickly!

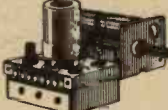Limited number also available with precision geared 3:1 reduction drive. 30/- P. & P. 3/-.  


**3-VALVE AUDIO AMPLIFIER MODEL HA34**



Designed for Hi-Fi reproduction of records. A.c. Mains operation. Ready built on plated heavy gauge metal chassis, size 7½in. w. x 4in. d. x 4½in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer matched for 3 ohm speaker.

and output transformer separate Bass, Treble and volume controls. Negative feedback line. Output 4½ watts. Front panel can be detached and leads extended for remote mounting of controls. The HA34 has been specially designed for us and our quantity order enables us to offer them complete with knobs, valves, etc., wired and tested for only £45.0 P. & P. 6/-.

**£45.0**  
P. & P. 6/-

**HSL 'FOUR' AMPLIFIER KIT**

A.C. Mains 200/250v., 4 watt, using ECC83, EL84, EZ80 valves




★ Heavy duty double-wound mains transformer with electrostatic screen.  
★ Separate Bass, Treble and volume controls, giving fully variable boost and cut with minimum insertion loss.  
★ Heavy negative feedback loop over 2 stages ensures high output at excellent quality with very low distortion factor.

★ Suitable for use with guitar, microphone or record player. ★ Provision for remote mounting of controls or direct on chassis. ★ Chassis size only 7½ in. wide x 4 in. deep. Overall height 4½ in. All components and valves are brand new. ★ Very clear and concise instructions enable even the inexperienced amateur to construct with 100% success. ★ Supplied complete with valves, output transformer (3 ohms only), screened lead, wire, nuts, bolts, solder, etc. (No extras to buy.) PRICE 79/6. P. & P. 6/-.

Comprehensive circuit diagram, practical layout and parts lists 2/6 (free with kit). This kit although similar in appearance to HA34 employs entirely different and advanced circuitry.

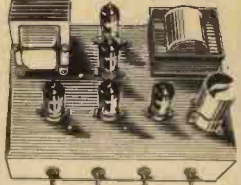**10/14 WATT HI-FI AMPLIFIER KIT**

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, E86, and EZ80 rectifier. Simple instruction booklet 1/6. (Free with parts.) All parts sold separately. ONLY £79/6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, £95/5-. P. & P. 8/6. Carrying Case for above 28/6. P. & P. 7/6.



MATCHED PAIR AM/FM I.F.'s, Comprising 1st I.F. and 2nd I.F. discriminator. (465 Kc/s/10.7 Mc/s). Size 1" x 1½" x 2½" H. Will match FM/AM Tuner head on left. 11/- pair. P. & P. 2/-.

**HARVERSON SURPLUS CO. LTD.**

170 HIGH ST., MERTON, S.W.19 ChErroywood 3985  
Open all day Saturday Early closing Wed. 1 p.m.  
A few minutes from South Wimbledon Tube Station. (Please write clearly)  
OVERSEAS P. & P. CHARGED EXTRA. S.A.E. with all enquiries

**FANTASTIC SELL-OUT SALE FANTASTIC**

OWING TO THE EVER-INCREASING DEMAND FOR A LARGE SELECTION OF SEMICONDUCTORS WE ARE CLOSING OUR COMPONENT SECTION. THIS ENABLES US TO OFFER THESE FANTASTIC BARGAIN PACKS TO YOU. DON'T MISS THEM ORDER NOW!

- 25 ASSORTED TRANSISTOR ELECTROLYTICS POPULAR VALUES.
- 100 ASSORTED HI-STABILITY RESISTORS 0.1%, 1%, 2%, 5%.
- 200 ASSORTED ¼, ½, 1 WATT RESISTORS, P.C. TYPES INCLUDED.
- 100 SILVER MICA AND CERAMIC CAPACITORS POPULAR VALUES.
- 12 ASSORTED POTENTIOMETERS, INC. TANDEM, W.W., PRESET, ETC.

**FREE FREE FREE**  
WITH ANY SIX PACKS ORDERED ONE SUPER BARGAIN PACK INC. TAG STRIPS, TAG BOARDS, PRINTED CIRCUITS, KNOBS, TERMINALS, TRANSFORMERS, PLUGS, SOCKETS, RECTIFIERS, TRIMMERS, FERRITE RODS, COILS, BULBS, ETC., ETC.

- 10 ASSORTED SWITCHES, INC. SLIDER TOGGLE, PUSH BUTTON, ROTARY, ETC.
- 100 ASSORTED WIREWOUND AND CARBON RESISTORS, 1 WATT—5 WATT.
- 100 ASSORTED PAPER AND POLYESTER CAPACITORS. 125 v.wg—500 v.wg.
- 12 MAGNETIC MINIATURE EARPIECES WITH LEAD.
- 10 ASSORTED TV AND RADIO ELECTROLYTICS INC. 8 MFD, 16 MFD, 32 MFD, ETC.

ALL PACKS 10/- EACH  
**WENTWORTH RADIO**  
POST AND PACKING 1/- PER PACK  
**1a WENTWORTH COURT, ALSTON ROAD, BARNET, HERTS.**

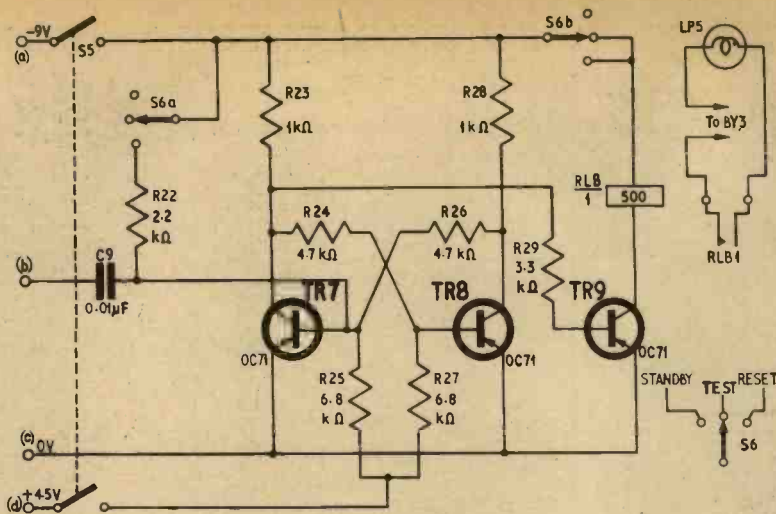


Fig. 4. Circuit diagram of the memory latch

“back later”; S3, a separate switch to illuminate the “come in” lamp; S2, a “test” switch which is wired across the relay contacts and can be used to illuminate any of the lamps for testing. Two extra switches will also be required if the memory latch—to be described later—is included in the system.

### MEMORY LATCH

A very useful feature which can be added at very little extra cost is a memory latch. This is a circuit which remembers if there are any callers when the device is left unattended.

The circuit is given in Fig. 4 and is seen to consist of two parts, a bistable switch and a current amplifier similar to the one used in the basic unit. S5 is the on/off switch and supplies power to the bistable only. S6 has three positions: “Standby”, “Test”, and “Reset”. It is normally left in the “Standby” position.

To use the memory unit it is turned on by S5 and S6 is depressed to the “Reset” position and then returned

to “Standby”. S6b at this point shorts TR1 base to the -9 volt line via R7 thus ensuring that the bistable has TR1 conducting and TR2 cut off. If left undisturbed, i.e. if no-one comes, then the circuit will remain in this state permanently. However, if someone knocks on the door, the relay closes and re-opens (lighting, presumably, the “back later” lamp) and the voltage pulse across the relay contacts is applied to TR1 via C1, causing it to cut off and permitting TR2 to conduct instead. The circuit will remain thus set indefinitely, and further triggering pulses will not affect it.

When the owner returns and moves S6 to the “Test” position TR3 will conduct heavily if TR1 is cut off, this causes the relay to operate and the lamp to light, indicating that someone had called during the owner’s absence. If no-one had been then TR1 would still be conducting, its collector would be at about 0 volt and TR3 would remain cut off when S6 was moved to “Test”.

Constructional details will be given next month.

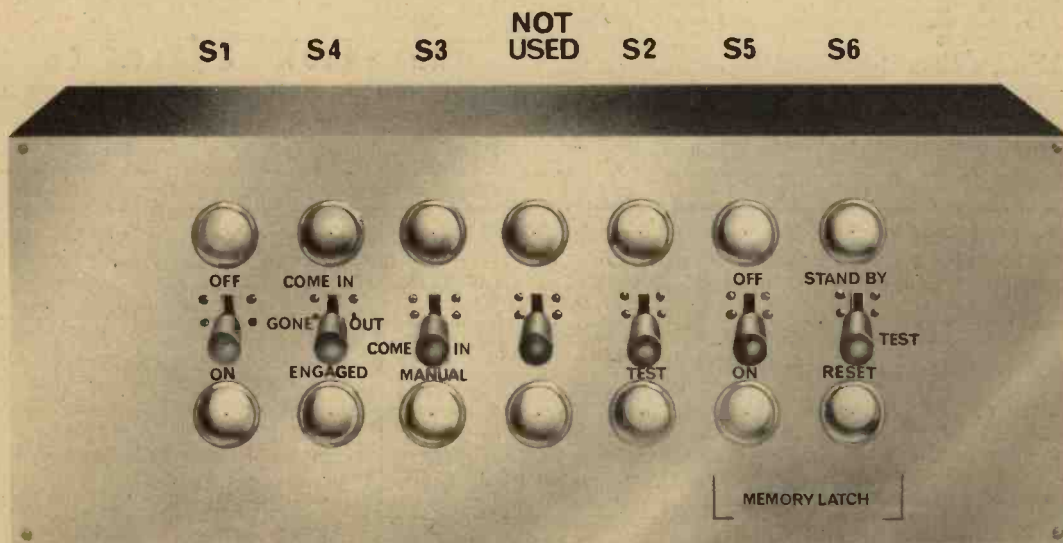


Fig. 5. The control unit



# THE Oscilloscope

PART TWO

and its applications  
By P. Cairns

The two commercial instruments shown illustrate extremes in oscilloscope design. The Tektronix 547, with automatic display switching, is used in specialised laboratory applications; plug-in units adapt the instrument to a wide range of measurement capability. The Advance OS12 oscilloscope, with its simple control panel, is intended as an educational aid or systems monitor in colleges and industry.

**T**HE oscilloscope, when used in conjunction with a signal generator can prove very useful in radio and television servicing. With a suitably modulated signal injected into the receiver input, the function of each stage can be examined in detail. If a wobulator or frequency modulated ganging oscillator is available the response curve of each i.f. stage in the receiver can be displayed or an overall response curve shown.

## SERVICING AID

The wobulator signal is injected into the grid of the frequency changer, care being taken not to overload the receiver. If an overall response curve is required it is injected into the aerial. The frequency of the injected signal is that of the i.f. of the receiver under test.

The circuit may be set up as in Fig. 8, the output developed across the second detector being applied to the c.r.o. Y input. The wobulator sweep is often obtained by applying the sawtooth waveform from the c.r.t. X deflection plate to the wobulator sweep input socket; this also gives automatic sync. During these tests ensure that the receiver a.v.c. is shorted out and the local oscillator short circuited.

The i.f. transformers are then trimmed in turn, beginning with the last one, i.e. the i.f. transformer nearest the second detector. The trace on the screen will depend upon the degree of error in the i.f. alignment, the trace to be aimed for having steep sides with a reasonably flat top. Typical traces are shown in Figs. 9a to e.

If the receiver is badly out of alignment it may be found necessary to increase the input signal to begin with so as to obtain a reasonable deflection, the signal being gradually reduced as the i.f. circuits are tuned to resonance. This method of aligning receivers is

extremely accurate, particularly where staggered tuning is necessary. Only the general outline of these tests can be given as the procedure and set up may vary between different types of wobulators and receivers.

Similar tests can be carried out when aligning f.m. and television receivers, though the procedure is rather more involved and beyond the scope of this article due to space limitations.

The oscilloscope is particularly useful when tracing hum troubles. The ripple on the h.t. line should be only a very small percentage of the h.t. d.c. level. This ripple can be measured by connecting the Y amplifier input across the smoothing filter output, the trace appearing as in Fig. 10a. With a faulty smoothing circuit the ripple will appear as in Fig. 10b and have a much greater amplitude.

A.C. coupling to the Y amplifier is necessary, the input capacitor blocking the large d.c. component of voltage and allowing the small ripple value to be displayed. A relatively high sensitivity setting on the Y amplifier is necessary.

In the case of television receivers the waveforms are often much more complex, and while the linearity of the line and frame time base circuits can be checked on most oscilloscopes, an instrument having a Y amplifier with a good frequency response is necessary for viewing the composite video signal at the video output stage. Special triggering facilities are also sometimes required, many modern oscilloscopes providing both internal frame and line synchronising.

An important point to be remembered when testing television receivers and many radio receivers is that they employ the a.c./d.c. type of power supply. The chassis may thus be at mains potential. As the common input point on the oscilloscope is normally earthed, connecting this point to the chassis of a receiver *could be extremely*




# BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—  
obtainable from your local Retailer

Retail enquiries to:  
**NORMAN ROSE (ELECTRICAL) LTD.**  
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

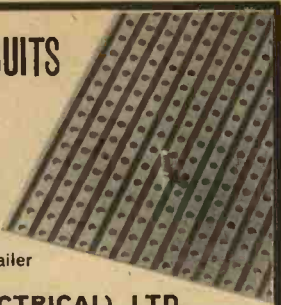Technical enquiries to:  
**VERO ELECTRONICS LTD.**  
Industrial Estate, Chandler's Ford, Hants




## The most accurate pocket size CALCULATOR in the world

The 66 inch OTIS KING scales give you *extra* accuracy. Write today for free booklet, or send 75/- for this invaluable spiral slide rule on approval with money back guarantee if not satisfied.

**CARBIC LTD.** (Dept. PE10)  
54 Dundonald Road, London, S.W.19



# BEST RECORDER VALUE anywhere!

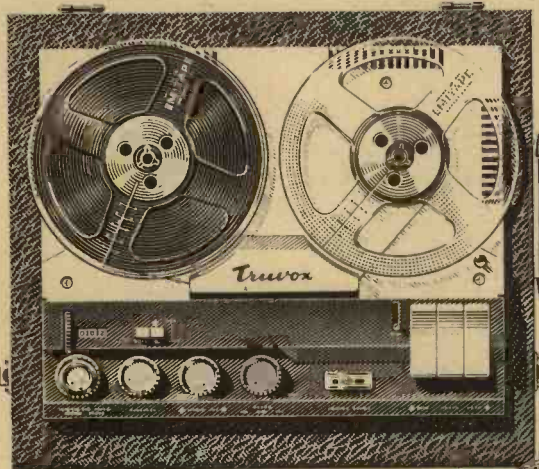

**FABULOUS NEW TRUVOX 40** - the professional recorder with the amateur price tag!

Nowhere, anywhere, such fantastic value for money. Real 'living sound' and BIG recorder performance, yet compact, portable, and ABC-easy to operate! Record anything - speech, music, effects - up to 17 hours on one tape! And positively no servicing problems - it's British built from top grade components; no delays for foreign spares or servicing know-how!




### CHECK THESE STAR FEATURES!

- \* 3 watts output \* 3 speeds \* V.U. recording level meter
- \* 2 or 4 tracks - same price \* solid state circuitry \* 7" reel capacity even when closed
- \* full mixing facilities \* monitoring \* pause control and 3 digit counter
- \* interlocked controls \* all-wood, acoustically matched cabinet \* moving coil mike, tape, lead, all included \*

All this, plus guaranteed Truvox quality for an amazing

**47** GNS

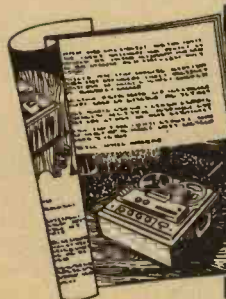Easy HP terms available from your Truvox dealer



**POST NOW FOR FREE**  
**12 PAGE COLOUR BOOKLET**

To: Truvox Limited, Neasden Lane, London N.W.10. Please rush me FREE illustrated colour brochure on Truvox 40 Recorder and other Truvox audio equipment. Also tell me where I can have a personal demonstration, free and without any obligation whatsoever.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

PE 1




### HA-63A COMMUNICATION RECEIVER OUTSTANDING VALUE

High class receiver covering 530 kc/s.-31 Mc/s. on 4 bands. Incorporates 7 valves plus rectifier, RF stage, illuminated "N" meter, 1.5µV sensitivity, electrical bandspread on the 80/40/20/13 and 10 metre bands, slide rule dial, aerial trimmer, B.F.O., noise limiter. Output for phones or speaker. Operates on 115/220/240 v. A.C. Supplied brand new and guaranteed with manual. 24 gns. Carr. 10/-.
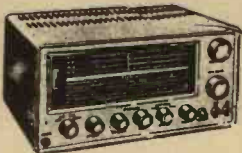
### LAFAYETTE KT-340 COMMUNICATION RECEIVER SEMI-KIT

Build this wonderful receiver and save Pounds! Supplied semi-completed, main components ready mounted, R.F. Section already wired and aligned. Full and precise instructions supplied. Specification: 8 valves + rectifier, 4 bands covering 550 Kc/s.-30 Mc/s. Incorporates 1 R.F. and 2 I.F. stages, "Q" multiplier, B.F.O., A.N.L. "S" meter, bandspread, aerial trimmer, etc. Operation 115/230v. A.C. Price 25 GNS. Carr. 10/-.



### HAM-I. 4 BAND COMMUNICATION RECEIVER

4 wavebands covering 535 kc/s-30 Mc/s. valve superhet circuit. Incorporates S meter, B.F.O., BANDSPREAD TUNING, BUILT-IN 4in. SPEAKER, FERRITE AERIAL AND EXTERNAL TELESCOPIC AERIAL. Operation 220/240v. A.C. Supplied brand new with handbook. £16/18/0. Carr.10/-.



### GARRARD RECORD PLAYERS

BRAND NEW AND GUARANTEED  
 8RP12 Player, mono or stereo £4 4 0  
 1000 Changer, mono or stereo £5 19 8  
 2000 Changer, mono or stereo £8 19 8  
 A50 Changer, mono or stereo £7 10 0  
 3000 Changer, mono or stereo £8 19 8

AT6 Mark II Changer, mono or stereo £9 19 8  
 SP23 Player, mono or stereo £9 19 8  
 AT 60 Changer, mono or stereo £10 19 8  
 A70 Changer (less cart.) £19 19 0  
 LAB80 Changer (less cart.) £25 0 0  
 401 Transcription £27 6 0

All plus P. & P. 5/-.

### MAIN LONDON AGENTS FOR CODAR EQUIPMENT

All items available as advertised

### SINCLAIR TRANSISTOR AMPLIFIERS

Z12 Amplifier 89/6; Z12 Power Pack 79/6; Stereo 25 Perc. Amplifier £9.19.6; Micro FM Radio Kits £5.19.6; Micro 6 Radio Kit 59/6; Micromatic Radio Kit 59/6, ready built 79/6. Post Paid.

### TRANSISTORISED TWO-WAY TELEPHONE INTERCOM.

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £8.10.0. pair. P. & P. 3/6.

### MAGNAVOX 363 TAPE DECKS

New 3-speed tape deck, superseded old Collaro studio deck. 2-track £10.10.0. 4-track £13.10.0. Carr. Paid.

### AMERICAN TAPE

First grade quality American tapes. Brand new. Discounts for quantities.

3in., 225ft. L.P. acetate 4/-  
 3 1/2in., 600ft. T.P. mylar 10/-  
 5in., 600ft. std. plastic 8/6  
 5in., 900ft. L.P. acetate 10/-  
 6in., 1,200ft. D.P. mylar 18/-  
 6in., 1,800ft. T.P. mylar 35/-  
 5 1/2in., 1,200ft. L.P. acetate 12/6  
 5 1/2in., 1,800ft. D.P. mylar 22/6  
 5 1/2in., 2,400ft. T.P. mylar 45/-  
 7in., 1,200ft. std. mylar 12/6  
 7in., 1,800ft. L.P. acetate 15/-  
 7in., 1,800ft. L.P. mylar 20/-  
 7in., 2,400ft. T.P. mylar 25/-  
 7in., 3,600ft. T.P. mylar 58/6  
 Postage 2/- Over £3 post paid.

### SILICON RECTIFIERS

200 v. P.I.V. 200mA 2/6  
 200 v. P.I.V. 6 amp. 5/6  
 400 v. P.I.V. 3 amp. 7/6  
 1,000 v. P.I.V. 650 mA 6/6  
 800 v. P.I.V. 500mA 5/6  
 800 v. P.I.V. 5 amp. (S.C.R.) 7/6  
 400 v. P.I.V. 500mA 3/6  
 70 v. P.I.V. 1 amp. 3/6  
 150 v. P.I.V. 165mA 1/-  
 150 v. P.I.V. 25 amp. 19/6  
 700 v. P.I.V. 100 amp. 49/6  
 400 v. P.I.V. 3 amp. (S.C.R.) 10/-  
 100 v. P.I.V. 5 amp. (S.C.R.) 13/6  
 200 v. P.I.V. 5 amp. (S.C.R.) 15/6  
 400 v. P.I.V. 5 amp. (S.C.R.) 17/6  
 Discounts for quantities. Post extra.

### MODEL IQM TRANSISTOR CHECKER

It has the fullest capacity for checking on A, B and Leo. Equally adaptable for checking diodes, etc. Specs. A: 0-7; 0-9957; B: 2-200; Leo: 0-50 microamps, 0-5 mA. Resistance for diode 200Ω - 1 MΩ. Supplied complete with instructions, battery and leads. £8/19/6. P. & P. 2/6.

### VARIABLE VOLTAGE TRANSFORMERS

Brand New - Fully Shrouded. Input 230v. 50/60 c/s. Output 0-250 Volts.

1 Amp. £4.10.0  
 2.5 Amp. £5.17.6  
 5 Amp. £9.0.0  
 8 Amp. £13.10.0  
 10 Amp. £17.6.0  
 12 Amp. £19.10.0  
 20 Amp. £32.10.0  
 2.5 Amp Portable - Metal Case with Meter-Fuses, etc. £9/17/6.

### CALLERS WELCOME

Open 9 a.m. to 6 p.m. every day. Monday to Saturday. Trade supplied.



Current: 0/20 K, 200 K, 2 megohms. Decibels - 20 to + 22 db. £5/10/0. P. & P. 2/6.

### TEST EQUIPMENT

#### PORTABLE OSCILLOSCOPE CT.52

A compact (9" x 8" x 16 1/2") general purpose scope. T/B 10 c/s-40 kc/s. Band width 1 Mc/s. Mullard DG 7/3 2 1/2" CRT. For operation on 200/250 v. A.C. Supplied complete with metal transit case, strap, test leads, and visor hood. Brand new. £22.10.0. Carr. 10/- . Complete with instructions



#### F.M. WIRELESS MICROPHONE

94-104 Mc/s. Transistorised. Operates from 9 v. battery. Complete with additional secret tie-clip microphone. List £12.10.0. ONLY £7.10.0. P. & P. 2/6.  
 These cannot be operated in U.K.



#### ERSKINE TYPE 13 DOUBLE BEAM OSCILLOSCOPE

Time base 2 c/s-750 kc/s. Calibrators at 100 kc/s and 1 Mc/s. Separate Y1 and Y2 amplifiers up to 5.5 Mc/s. Operation 110/230 volt A.C. Supplied in perfect working order. £22/10/- . Carriage 20/-.

#### TE-20 RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120 kc/s.-250 Mc/s on 6 bands. Directly calibrated. Variable R.F. attenuator, Operation 200/240 v. A.C. Brand new with instructions, £12.10.0. P. & P. 7/6.  
 S.A.E. for details.



#### LAFAYETTE TE-46 RESISTANCE CAPACITY ANALYZER

2 PF-2,000 MFD. 2 ohms - 200 Megohms. Also checks impedance, turns ratio, insulation 200/250v. A.C. Brand New £15. Carr. 7/6.

#### TE-900 20,000 Ω/VOLT GIANT MULTI-METER

6 in. full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000 V. A.C. 0/25/125/510/50/250/1,000/5,000 V. D.C. 0/50µA/110/100/500 mA/10 amp. D.C. 0/2K/200K/20 MEG. OHM. £12/19/6. P. & P. 5/-.



#### TE22 SINE SQUARE WAVE AUDIO GENERATORS

5ine 20 cps to 200 kc/s. on 4 bands. Square: 20 cps to 20 kc/s. Output impedance 5,000 ohms. 200/240 v. A.C. operation. Supplied Brand New and Guaranteed with instructions, £15. Carr. 7/6.



#### ★ TRANSISTORISED FM TUNER ★

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6in. x 4in x 2 1/2in. 3 I.F. stages. Double tuned discriminator. Ample output to feed most amplifiers. Operates on 9 volt battery. Coverage 88-108 Mc/s. Ready built ready for use. Fantastic value for money. £8.19.6. P.P. 2/6.



#### CLEAR PLASTIC PANEL METERS

First grade quality, Moring Coil panel meters, available ex-stock. S.A.E. for illustrated leaflet. Discounts for quantity. Available as follows: Type MR. 38P. 1 21/32in.

100-0-100µA	27/6	200mA	22/6	100V D.C.	22/6
500-0-500µA	22/6	300mA	22/6	150V D.C.	22/6
1-0-1mA	22/6	500mA	22/6	300V D.C.	22/6
1mA	22/6	750mA	22/6	500V D.C.	22/6
2mA	22/6	1A D.C.	22/6	750V D.C.	22/6
5mA	22/6	2A D.C.	22/6	15V A.C.	22/6
10mA	22/6	5A D.C.	22/6	50V A.C.	22/6
20mA	22/6	3V D.C.	22/6	150V A.C.	22/6
50mA	22/6	10V D.C.	22/6	300V A.C.	22/6
100mA	22/6	20V D.C.	22/6	500V A.C.	22/6
150mA	22/6	50V D.C.	22/6	"B" Meter 1mA 29/6	

POST EXTRA. Larger sizes available—send for lists.

#### TE-51 NEW 20,000Ω/VOLT MULTIMETER

0/6 60/120/1,200V. A.C.  
 0/3/30/60/300/600/3,000V. D.C.  
 0/60µA/600/600 MA.  
 0/6K/60K/6 Meg. 60 Meg. 0 50 PF.  
 2 MFD. £5.19.6. P. & P. 3/6.



#### NEW MODEL 500.

30,000 o.p.v. With mirror scale. 0/511/2.5/10/25/100/250/500/1,000v. D.C. 0/2.5/10/25/100/250/500/1,000v. A.C. 0/50µA/5/50/300mA. 12 amp. D.C. 0/60K/6 Meg./60 Meg. 0 50 PF. £8/17/6 Post Paid.



#### PROFESSIONAL 20,000 o.p.v. LAB. TYPE MULTITESTER

With automatic overload protection, mirror scale. Ranges: 0/10/30/250/500/1,000 volts, D.C./0/60µA/0-500 µA, 10 mA, 250 mA. A.C. 0-500V. Decibels - 20 to + 22 db.

# G. W. SMITH & CO (RADIO) LIMITED

Phone: GERRARD 8204/9155  
 Cables: SMITHEX LESQUARE  
 3-34 LISLE STREET, LONDON, W.C.2

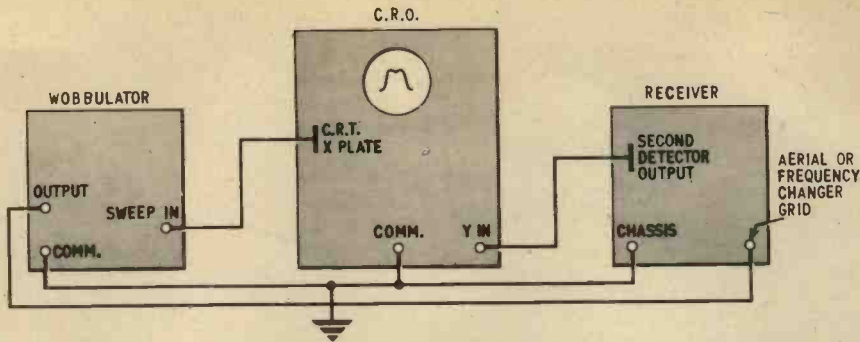


Fig. 8. Test set-up for checking or aligning the i.f. stages of a receiver




(a) c.r.o. time base sweep speed too slow. Increase sweep speed until trace is linear

(b) overloading of i.f. stage. Reduce input drive

(c) good broad response curve. Overall effect of staggered tuning as required by some receivers

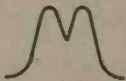(d) linear trace with correct sweep speed. Good overall response curve



(e) effect of off-tuning

Fig. 9. Typical traces obtained using the set-up as in Fig. 8



(a) slight h.t. hum ripple



(b) aggravated ripple due to faulty smoothing circuit

Fig. 10. Comparative examples of ripple voltage

dangerous. Some oscilloscopes overcome this to a certain extent by means of an internal link which can be removed so as to isolate the common input line from chassis and earth. Another and simpler method is to connect a 1 : 1 ratio isolating transformer of suitable VA between the receiver under test and the mains.

### LISSAJOUS FIGURES

One very important application of the oscilloscope is in frequency measurement and comparison. This can be carried out by means of either Lissajous figures or spot wheel patterns. In both of these applications the time base is dispensed with.

In the case of Lissajous figures, one frequency is applied to the Y input and the other to the X input, the appropriate gains being adjusted to give a similar deflection in each plane. The resultant pattern obtained will depend upon the frequency difference between the signals. Normally one signal is of a fixed known frequency, say 50Hz, and the other unknown and variable. When the unknown signal frequency is adjusted to give a circle on the screen, both signals are of the same frequency.

As the variable frequency is increased various patterns are obtained, the frequency ratio between the two signals being found by counting the number of "crowns" in the pattern. In practice this method is generally only usable for a frequency difference of about six or eight to one as the number of "crowns" becomes difficult to count due to the pattern tending to revolve as one or both of the oscillators drift slightly. This

method is extremely accurate however as errors as low as a few cycles per minute can be observed, the oscillators being exactly in step only when the pattern remains completely stationary.

This system can be conveniently used when calibrating an unknown variable frequency source against a known fixed or variable source. Some typical Lissajous figures are shown in Figs. 11a to f with the frequency ratios they represent. The pattern for a particular figure may appear to change, the appearance of the pattern depending upon the point at which it is "locked" on the screen.

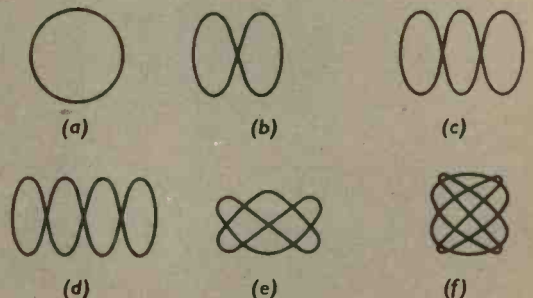


Fig. 11. Typical Lissajous figures showing relative frequency ratios (a) 1 : 1 ; (b) 2 : 1 ; (c) 3 : 1 ; (d) 4 : 1 ; (e) 3 : 2 ; (f) 3 : 4

## SPOT WHEEL PATTERNS

The spot wheel method can be used over a much larger frequency ratio and is simpler to compute. The spot wheel pattern is obtained by means of an external phase shift circuit and intensity modulation of the c.r.t. First the known frequency signal source is fed into the phase shift unit, again the 50Hz mains is a good basic reference. The phase shift unit should have, or be adjusted to, a 90 degree shift. The two output signals with this 90 degree phase difference are then fed into the X and Y input terminals on the c.r.o. If both gain controls are adjusted to give the same sensitivity, a circular trace results.

The unknown frequency is then fed into the intensity modulation terminal on the c.r.o. or if one is not available it can be fed via a  $0.1\mu\text{F}$  capacitor to either the grid or cathode of the c.r.t. The capacitor should be of suitable voltage working as the tube electrodes may be at a high potential with respect to earth. When the amplitude of this signal is increased a number of blank spaces will appear symmetrically in the circular trace, the number of spaces (or sections of trace remaining) represents the ratio between the known and unknown frequencies.

The action of this circuit is quite straightforward. When the unknown frequency is applied to the grid of the c.r.t., every negative half cycle blanks the trace out as the tube will be driven past cut-off during this period. Similarly, with the signal applied to the cathode each positive half cycle cuts the tube off. Thus, each complete cycle is represented by one space and one section of trace. This method can be used quite

successfully with frequency ratios up to 30:1 or even higher. A stationary trace represents an exact ratio; with a slight frequency difference the trace appears to be slowly revolving. A typical test circuit is shown in Fig. 12, while some resultant patterns appear in Fig. 13.

## Z MODULATION

A simple modification to the oscilloscope designed by the present writer and published in this periodical<sup>1</sup> is shown in Fig. 14. This allows an intensity modulation input point to be added for the addition of only three components. This circuit may also be used on many other oscilloscopes which do not include an intensity modulation point.

The purpose of R1 is to give some isolation between the input signal to the grid and the e.h.t. d.c. supply. The clipping diode D1 prevents the grid being driven positive on positive half cycles. This should be connected in all such circuits as the tube could be damaged if the grid were repeatedly driven positive over long periods. C1 gives the necessary d.c. isolation between the input point and the tube electrode circuit. When viewing spot wheel patterns the brilliance should be turned as low as possible. A signal of at least 10 volts r.m.s. and preferably larger is necessary to modulate the circuit described. Some commercial oscilloscopes include an internal intensity modulation amplifier to allow much smaller values of modulation signal to be applied.

1. An Inexpensive Oscilloscope (March, April and May 1965).

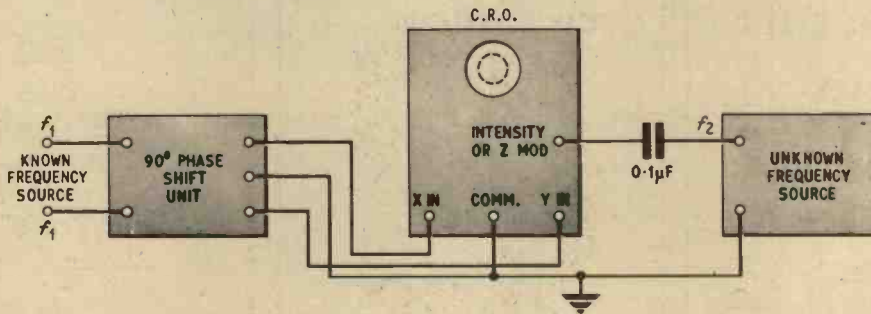


Fig. 12. Test set-up for producing spot wheel patterns




Fig. 13. Some typical spot wheel patterns using the set-up as in Fig. 12

# LOOK!

**PRACTICAL!**

**VISUAL!**


**EXCITING!**

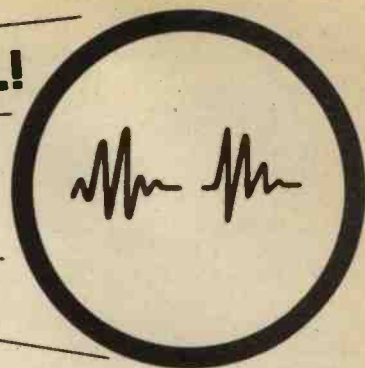

a new 4-way method of mastering  
**ELECTRONICS**  
by doing — and — seeing . . .


**1** ▶ **OWN and HANDLE** a

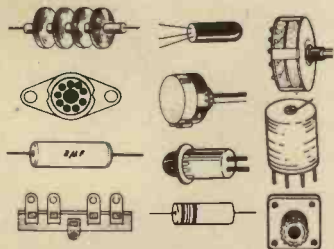complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



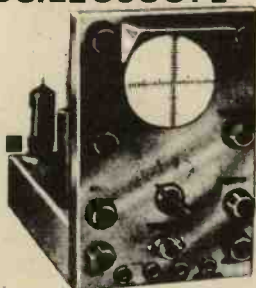
**2** ▶ **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



**3** ▶ **READ and DRAW and**

**UNDERSTAND**  
**CIRCUIT DIAGRAMS**

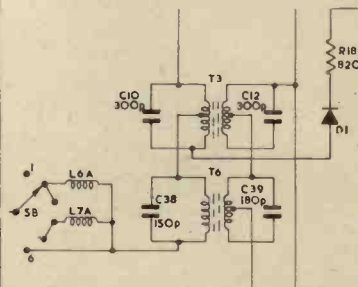

**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME.....BLOCK CAPS

ADDRESS.....PLEASE PE 4

# VARIABLE VOLTAGE TRANSFORMERS



**PORTABLE TYPE**  
£8. 10. 0.



£3.3.0.



50 AMPS

INPUT 230/240v. A.C. 50/60—  
OUTPUT VARIABLE 0-260v.  
**BRAND NEW Carriage Paid.**  
Buy direct from the importer,  
keenest prices in the country.  
All Types (and Spares) from  
£1 to 50 amp. from stock.

**OPEN TYPE (Panel Mounting)**  
½ amp, £3. 3. 0. 1 amp, £4. 10. 0.  
2½ amps, £5. 12. 6.

**SHROUDED TYPE**  
1 amp, £4. 10. 0. 2.5 amps,  
£5. 17. 0. 4 amps, £8. 7. 6.  
5 amps, £9. 0. 0. 8 amps,  
£13. 10. 0. 10 amps, £17. 0. 0.  
12 amps, £19. 10. 0. 15 amps,  
£22. 0. 0. 20 amps, £32. 10. 0.  
37.5 amps, £65. 0. 0. 50 amps,  
£85. 0. 0.

1.5 amp. portable fitted metal case  
voltmeter, lamp, switch, etc. £8.10.0  
P. & C. 10/-. Similar to above 2.5  
amp. £9.17.6. P. & C. 10/-.

## 100 WATT POWER RHEOSTATS (NEW)

AVAILABLE IN THE FOLLOWING VALUES

1 ohm, 10 a.; 5 ohm, 4.7 a.; 10 ohm, 3 a.;  
25 ohm, 2 a.; 50 ohm, 1.4 a.; 100 ohm, 1 a.;  
250 ohm, .7 a.; 500 ohm, .45 a.; 1,000 ohm,  
280 mA.; 1,500 ohm, 230 mA.; 2,500 ohm, .2 a. Diameter  
3½ in. Shaft length ¾ in., dia. ¼ in. All at 27/6 each.  
P. & P. 1/6.

## 25 WATT POWER RHEOSTATS

10 ohm, 1.5 a.; 25 ohm, 1 a.; 50 ohm, .75 a.; 100 ohm, .5 a.;  
250 ohm, .3 a.; 500 ohm, .2 a.; 1,000 ohm, .15 a.; 1,500 ohm,  
.12 a.; 2,500 ohm, .1 a.; all at 14/6. P. & P. 1/6.

## "GABY" MULTI-RANGE TEST METER

Model B40. D.C. volt, 0-5 v., 2-5 v. at 10,000 ohm per volt. Ideal for transistor circuit testing. A.C. and D.C. volt, 10 v., 50 v., 250 v., 500 v., 1,000 v. at 4,000 ohm per volt. Resistance, 2 K ohm, 200 K ohm, 2 meg., 20 meg. Repair service available. Price includes Test Leads, Battery, Instruction book, Packing and Post (U.K.). £6.2.6. 3 additional models available from 54/- to £14.14.0. Leaflet gladly sent on request.

## 5 A. AD/DC VARIABLE VOLTAGE OUTPUT UNIT

Input 230v. AC  
Output 0-260v. DC  
Output 0-240v. AC  
Fitted large Scale  
Ammeter and Voltmeter, Neon Indicator, Fully Fused. Strong attractive metal case 15" x 8½" x 6". Weight 24lbs. Infinitely Variable, smooth stepless Voltage Variations over full range. Price £30. C. & P. £2.

## SENSITIVE GALVANOMETER

Centre Zero 300-0-300. Micro amp. 90 ohm. approx. Calibrated 30-0-30 in clear divisions. Mounted in sturdy sloping front case with top terminals. Price £4.10.0. P. & P. 2/6. Matching volt meter calibrated 0-3 and 0-15 v. D.C. £4.10.0. P. & P. 2/6. D.C. Ammeter 0-6a and 0-3a. £4.10.0. P. & P. 2/6. Set of 3 matching instruments. £12.19.0. P. & P. 4/6.

## CONSTANT VOLTAGE TRANSFORMER

Input 185-250 v. A.C. Output 230 v. A.C. Capacity 250 watt. Attractive metal case. Fitted red signal lamp. Rubber feet. Weight 17 lbs. Price £11.10.0. P. & P. 15/-.



## LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt D.C. op. price 25/- plus 2/6 P. & P. ORP 12 including circuit, 10/6 each, plus 1/- P. & P.

**A.C. MAINS MODEL** Incorporates Mains Transformer, Rectifier and special relay with 3, 5 amp mains c/o contacts. Price inc. circuit 47/6 plus 2/6 P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with focusible lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP. 12 or similar cell. Both units are single hole fixing. Price per pair £2.10.0. P. & P. 3/6.

## UNISELECTOR SWITCHES

75 ohm coil 24 v. D.C.  
6 Bank 25 position, 5 non-bridging 1 Bridging Wiper  
5 Bank 25 position, 4 non-bridging 1 Bridging Wiper  
6 Bank arranged to give 3 bank, 50 positions  
8 Bank arranged to give 4 bank, 50 positions  
These switches have been carefully removed from equipment. All at 35/- each. P. & P. 2/6.

**BRAND NEW** 4 Bank 25 Way Uniselector, 3 Bank 4 Homing 25 ohm coil. 12-24v. D.C. operation £4.17.6 plus 2/6 P. & P.

## SOUND POWER OPERATED EX-ADMIRALTY HEAD AND BREAST SETS

Two such sets connected up will provide perfect intercom. No batteries required. Will operate up to ¼ mile. Price 17/6 each plus P. & P. 3/- or 32/6 per pair. P. & P. 5/6.



## METERS

2½" Flush Round A.C. AMMETERS 0-1, 0-5, 0-10, 0-15, 0-20 Amp. All 21/- each, p. & p. extra. A.C. VOLTMETERS 0-25, 0-50, 0-150V. All 21/- each, p. & p. extra. 0-300 V. A.C. m/c Rectifier £19.0.

## UNIVERSAL DEMONSTRATION TRANSFORMER

A complete composite apparatus, comprising a Transformer and electro-magnet with removable coils and pole pieces. Coil tapped for 230v, 220v, 110v, 115v; 6, 12, 36, 110v. A.C. These coils are also used for D.C. experiments. Complete with all accessories as shown. £17 + 15/- carriage. Leaflet on request.



## WIMSHURST ELECTROSTATIC GENERATORS

£13/17/6, carr. U.K. (B.R.S.) 10/-. Leaflet on request.

## BUILD AN EFFICIENT STROBE UNIT

FOR ONLY 37/6. We supply a simple circuit diagram and all electrical parts including the NSP2 Strobe tube which will enable you to easily and quickly construct a unit for infinite variety of speeds, from 1 flash in several seconds to several thousands per minute. 37/6 plus 3/- P. & P.

## COMPACT HEAVY DUTY 6 volt DC RELAY

6-9 volt DC operation 30 ohm coil 2 x 10 amp c/o contacts, will handle up to 250 volt A.C. Size 1½" high x 2¼" x 1½". Price 7/6 plus 1/6 P. & P. 3 for 20/- post paid.

**230 VOLT A.C. GEARED MOTORS** 5 r.p.m. 1-7 lb. inch £2.9.6. P. & P. 2/6. 13 r.p.m. 1-45 lb. inch £2.17.6. P. & P. 2/6. 80 r.p.m. 26 lb. inch £2.2.0. P. & P. 2/6.


## L.T. TRANSFORMERS

All primaries 220-240 volts.

Type No.	Sec. Taps	Price Carr.
1	30, 32, 34, 36 v. at 5 amps.	£3.5.0 7/6
2	30, 40, 50 v. at 5 amps.	£5.5.0 9/-
3	10, 17, 18 v. at 10 amps.	£3.10.0 7/6
4	6, 12 v. at 20 amps.	£4.17.6 7/6
5	17, 18, 20 v. at 20 amps.	£5.12.6 10/6
6	6, 12, 20 v. at 20 amps.	£5.5.0 9/-
7	24 v. at 10 amps.	£3.15.0 7/6
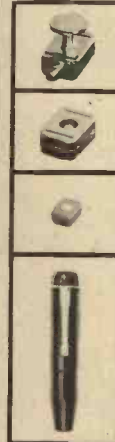
# MICRO miniature microphones

The Sennheiser sensation that shook the United States.



**MM 23** magnetic lapel microphone  
Cable with jack on request £5.15.0

**MM 26** magnetic subminiature microphone.  
For built-in application £3.10.0

**MM 301** magnetic microphone.  
Ultra sensitive. For built-in application £4.18.0

**MM 61** 'fountain pen' microphone.  
Ultra output. Special cable on request £5.19.0

For further details of all Sennheisers dynamic microphones contact your dealer or send C.W.O. to

## Audio Engineering Ltd

33 Endell Street London WC2 TEM 0033

# THE MOTOROLA SEMICONDUCTOR DATA BOOK

- lists more than 10,500 semiconductors.
- includes data sheets for more than 2,800 devices from diodes to integrated circuits.
- has 16 edge referenced sections for fast fact finding.
- 1,500 page hard bound for 40/- including postage.

**BASIC ELECTRONICS**, by Grob. 36/-. Postage 1/6.

**BASIC ANALOGUE COMPUTER TECHNIQUES**, by Stewart & Atkinson. 21/-. Postage 1/-.

**RADIO COMMUNICATION**, by W. F. Lovering. 70/-. Postage 2/-.

**TRANSISTOR SPECIFICATIONS & SUBSTITUTION HANDBOOK, 1967**, Tech. P. 21/-. Postage 1/-.

**RADIO VALVE DATA**, 8th ed., "W.W." 9/6. Postage 1/-.

**TAPE RECORDER SERVICING MANUAL**, by H. W. Hellyer. 63/-. Postage 2/6.

# THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS  
British and American Technical Books

19-21 PRAED STREET  
LONDON, W.2

Phone: PADdington 4185

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
57 BRIDGMAN ROAD, LONDON, W.4 Phone 995 1560  
SHOWROOM NOW OPEN CLOSED SATURDAY

Personal callers only  
9 LITTLE NEWPORT ST.  
LONDON, W.C.2. Tel. GER 0576



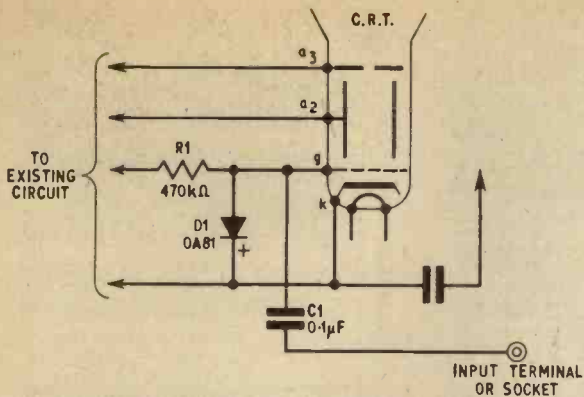


Fig. 14. Modifications to oscilloscope for the addition of an intensity modulation input

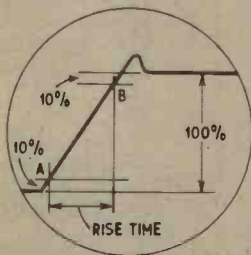

(a)

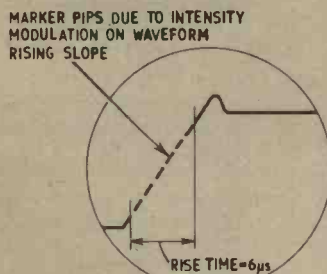

(b)

Fig. 15. Measurement of stepped function rise times

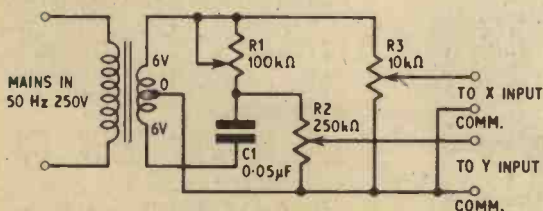


Fig. 16. Circuit diagram of phase shift unit

Intensity modulation can also be used for the accurate measurement of stepped function rise times, particularly where the time base sweep speed is not fast enough to expand the step into a measurable slope in the horizontal direction. With the c.r.o. working in the conventional manner and a stepped waveform or square wave displayed on the screen, the time base and Y amplifier gain controls are adjusted to give a picture similar to that in Fig. 15a. To measure the rise time a signal of appropriate frequency and of sufficient amplitude to intensity modulate the c.r.t. is applied via the intensity or Z modulation terminal. If the rise time is in the  $\mu\text{s}$  region a 1MHz signal would be suitable, 1 cycle being equal to  $1\mu\text{s}$ . A series of gaps at  $1\mu\text{s}$  intervals would thus appear on the slope of the waveform as in Fig. 15b. The number of gaps (or sections) are then counted, this being the rise time of the slope in  $\mu\text{s}$ . Normally the rise time is taken as that part of the slope lying between -10 per cent and +10 per cent of the maximum and minimum peak values, this is shown in Fig. 15a.

To measure such a rise time by dropping two lines from these points (A and B) to the time base scale and trying to measure this on the time calibration is not only difficult but tends to be rather inaccurate, whereas the method described is as accurate as the frequency of the intensity modulation signal. For faster rise times this signal can be increased as high as 10MHz ( $0.1\mu\text{s}$ ), for slower rise times a 100kHz or 500kHz. I.e. ( $10\mu\text{s}$  or  $2\mu\text{s}$ ) signal may be used.

Some oscilloscopes, particularly those designed for pulse applications, have one or more intensity modulation oscillators built into the c.r.o., these being switched in as required. This makes rise and duration times in pulse measurements much simpler and obviates the use of an external signal source.

### PHASE SHIFT NETWORK


The writer has at various times in this article advocated the use of a phase shift network, such a unit being very useful in oscilloscope work. A suitable circuit which can be made into a very compact unit will therefore be described. The circuit is adjustable in phase between 0 degrees and approximately 110 degrees, both outputs also being adjustable in amplitude being sufficient to drive both X and Y amplifiers of the majority of oscilloscopes.

The circuit is driven from the 50Hz mains supply, this being the reference frequency. The circuit could however be driven from a variable frequency source of sufficient output though the capacitor would have to be decreased in value as the frequency was increased. The complete circuit with component values is shown in Fig. 16.


The action of the circuit is quite easy to follow, the phase shift in the voltage across the C1-R1 divider occurring due to the presence of the capacitive reactance in the resistive circuit. A phase shift of exactly 90 degrees will occur when the reactance of the capacitor at 50Hz) C1 is equal to the value of the resistor R1.

The phase angle is reduced as R1 is decreased in value, the reactance of C1 then being greater than the value of R1. The circuit and vector diagram in Fig. 19 shows the function of the circuit quite clearly. Referring to this diagram shows that the output voltage V is of constant amplitude but lags the supply voltage E by an angle  $\theta$  which depends upon the value of R. It can be seen from the figure that in the relation between R and  $\theta$  is by no means linear and that the extreme case  $\theta$  approaches 180 degrees, requiring R to approach


Fig. 20. **OSCILLOGRAMS**

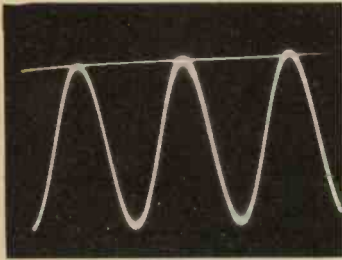


(a) Sine wave input

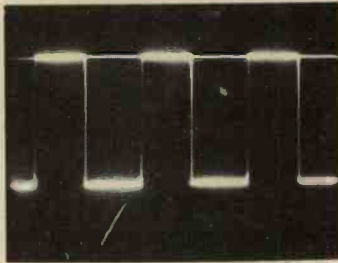


(b) Square wave input

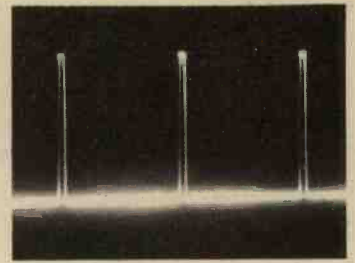

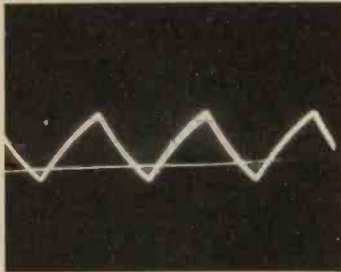
(c) 20ms marker pulses (1ms wide) derived from square wave




(d) Integrated square wave

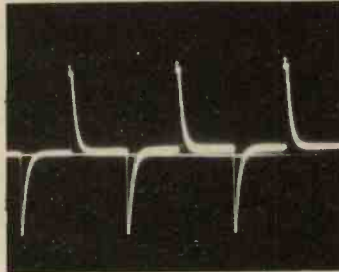


(e) Differentiated square wave

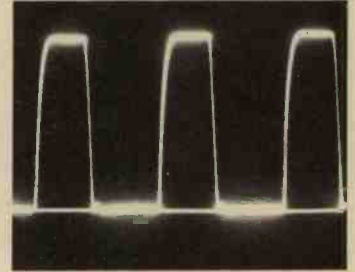

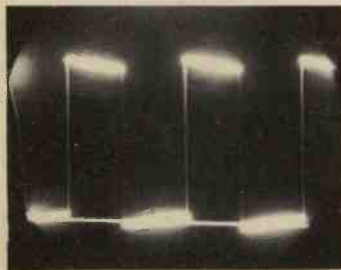
(f) Slight h.f. reduction with parasitic ringing



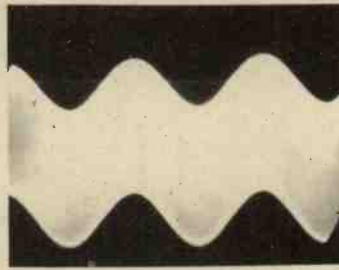
(g) Slight l.f. reduction due to a.c. coupling




(h) 50Hz hum on h.f. carrier

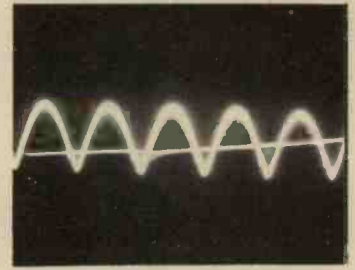

(i) 100Hz ripple on h.t. line

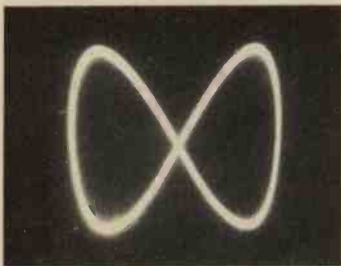

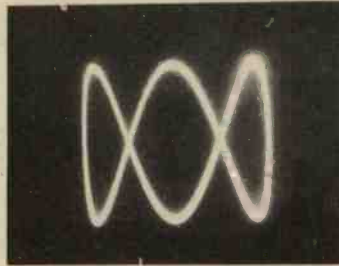
(j) Lissajous pattern showing 2:1 frequency ratio




(k) Lissajous pattern showing 3:1 frequency ratio



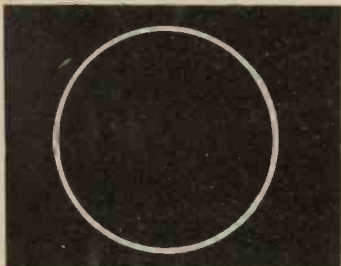
(l) Small angle phase shift due to reactive circuit



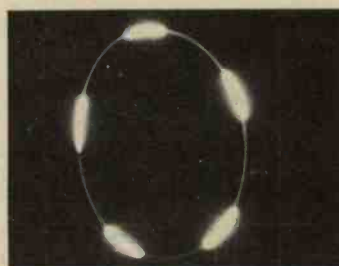(m) 90 degree phase shift of X and Y input



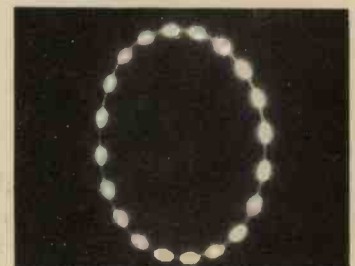(n) Spot wheel pattern where  $f_2 = 5 \times f_1$  (see text)



(o) Spot wheel pattern where  $f_2 = 20 \times f_1$  (see text)





### POCKET MULTI-METER

Size 3 1/2" x 2 1/4" x 1 1/2". Meter size 2 1/2" x 1 1/2". Sensitivity 1000 O.P.V. on both A.C. and D.C. volts. 0-15, 0-150, 0-1000. D.C. current 0-150mA. Resistance 0-100k  $\Omega$ . Complete with test prods, battery and full instructions, 42/6. P. & P. 3/6. **FREE GIFT** for limited period only. 30 watt Electric Soldering Iron value 15/- to every purchaser of the Pocket Multi-Meter



### 3 to 4 WATT AMPLIFIER

3-4 watt Amplifier built and tested. Chassis size 7 x 3 1/4 x 1 in. Separate bass, treble and volume control. Double wound mains transformer, metal rectifier and output transformer for 3 ohms speaker. Valves ECC81 and 6v6. £2.5.0 plus 5/6 P. & P. The above in Kit Form, £1.14.6 plus 5/6 P. & P.

### CYLDON U.H.F. TUNER

complete with PC.88 and PC.86 Valves. Full variable tuning. New and unused. Size 4 1/2" x 5 1/2" x 1 1/2". Complete with circuit diagram. 35/- plus 3/6 P. & P.



### MULTIPLEX DECODER for receiving Stereo FM

Now is your chance to benefit in full from the new B.B.C. stereo transmissions with our Multiplex Decoder. Design features: Highly efficient Mullard vinkor pot cores. Two semiconductor diodes. Double purpose valve. Printed circuit type construction high input impedance. Specification: Cross talk minus 26 dB at 1 kc/s. Input requirements 0.5-1.5 RMS. Stability plus or minus 0.1%. Voltage requirements H.T. 190-250 volts. D.C. at 5 ma. Heaters 6-3 volts A.C. at 300 ma. Self-powered unit shortly available, price to be announced. Size 5 1/2" x 3 1/2" x 1". Fully built and tested, price £4.4.0 plus 3/- P. & P. charges.



### Type E MOTOR

Small A.C. mains motor 230/250 volts complete with gearbox, 6 r.p.m. Price 15/- plus 4/- P. & P. Similar to above motor but without gearbox. Price 9/6 plus 3/- P. & P.

### SILICON RECTIFIERS

250 v. P.I.V. 750 milliamps. Six for 7/6, Post paid.




### NEW Transistorised SIGNAL GENERATOR

Size 5 1/2" x 3 1/4" x 1 1/2". For IF and RF alignment and AF output, 700 c/s frequency coverage 460 Kc/s to 2 Mc/s in switched frequencies. Ideal for alignment to our Elegant Seven and Musette. Built and tested. 39/6. P. & P. 3/6.


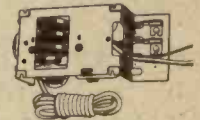
### TRANSISTORISED 1 1/2 WATT AMPLIFIER

comprising 2AC 128, 20C 75 and 2 AA129 separate bass and treble volume controls. Complete with Power Supply AC mains 240 v. Size 7 1/2" x 3 3/4" x 2". Price 50/- plus 2/6 P. & P.



### TRANSISTOR INVERTOR

50 v. D.C. Input. Output 240 v. A.C. 40 watts incorporating transformers, choke, condensers and 2 Mullard OC28 in solid 16 gauge Aluminium Case. Size 15" x 6" x 2 1/2" by famous manufacturers. 19/6 plus 7/- P. & P.



### 40W FLUORESCENT LIGHT KIT

Incorporating GEC Choke size 8 1/2" x 1 1/2" 12", 2 bi-pin holders, starter and starter-holder. 11/6. P. & P. 5/6. Similar to above: 80 W. Fluorescent Light Kit incorporating GEC Choke size 11 1/2" x 1 1/2" x 1 1/2", 2 bi-pin holders, start and starter holder 17/6. P. & P. 6/6. Twin 40 W Choke instant start for 2 x 2 ft. tubes 17/6. P. & P. 5/6.



### POWER SUPPLY KIT

A.C. MAINS 200-250 V Incorporating "C" core type mains transformer, full wave metal rectification and smoothing condenser. Smooth output 250 v. 250 mA and 6.3v. 4 amp. for Heaters. 25/- P. & P. 9/6.



## Special offer ELEGANT SEVEN mk IIa

**SPECIAL OFFER.** 7" x 4" P.M. Speaker at no extra charge. Power supply kit to purchasers of 'Elegant Seven' parts, incorporating mains transformer, rectifier and smoothing condenser, A.C. mains 200/250 volts. Output 9v. 100 mA. 7/6 extra.

Buy yourself an easy to build 7 transistor radio and save at least £10.0.0. Now you can build this superb 7 transistor superhet radio for under £4.10.0. No one else can offer such a fantastic radio with so many de luxe star features.

- ★ De luxe grey wooden cabinet size 12 1/2" x 8 1/2" x 3 1/2".
- ★ Horizontal easy to read tuning scale printed grey with black letters, size 11 1/2" x 2".
- ★ High 'Q' ferrite rod aerial.
- ★ I.F. neutralisation on each separate stage.
- ★ D.C. coupled push pull output stage with separate A.C. negative feedback.
- ★ Room filling output 350mW.
- ★ Ready etched and drilled printed circuit board back printed for foolproof construction.
- ★ Fully comprehensive instructions and point to point wiring diagrams.
- ★ Car aerial socket.
- ★ Fully tunable over medium and long wave, 168-535 metres and 1250-2000 metres.
- ★ All components, ferrite rod and tuning assembly mount on printed board.
- ★ Full after sales service.
- ★ Parts list and circuit diagram 2/6, free with parts.



**ONLY £4.4.0**

Plus 7/6 Post & Packing

### BSR Tape deck

AC 200/250 v., tape speed 3 1/2 twin track.

**Special price £5.19.6**

Post and packing 7/6



### EXTRACTOR FAN

AC Mains 230/250v complete with pull switch. Size 6" 6" x 4". Price 27/6 plus 5/- P. & P.

### 8-WATT 4-VALVE PUSH-PULL AMPLIFIER & Metal RECTIFIER



Size 9" 6" x 1 1/2". A.C. Mains, 200-250 v. 4 valves. For use with Std. or L.P. records, musical instruments. All makes of pick-ups and mikes. Output 8 watts at 5 per cent of total distortion. Separate bass and treble lift control. Two inputs, with controls for gram. and mike. Output transformer tapped for 3 and 15 ohm speech coils. Built and tested. £4.4.0. P. & P. 11/- 8" x 5" Speaker to suit. Price 14/6 plus 1/6 P. & P. Crystal Mike to suit 12/6 plus 1/6 P. & P.


### GEC DOORBELL

Complete with mains transformer 240v A.C. and illuminated bell push. Price 12/6 plus 5/6 P. & P.


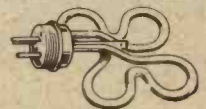
### GEC KETTLE ELEMENT

3,000W WITH AUTOMATIC EJECTION 200/240 v. size of hole required 1 1/8". List Price 32/- Our PRICE 15/- P. & P. 1/6.



## RADIO AND T.V. COMPONENTS (ACTON) LTD.

21D HIGH STREET, ACTON, LONDON, W.3

Shop hours 9 a.m. to 6 p.m. Early closing Wednesday. Goods not despatched outside U.K. All enquiries stamped addressed envelope. Terms C.W.O.

Also at 323 EDGWARE ROAD, LONDON, W.2  
Early closing Thursday  
**PERSONAL SHOPPERS ONLY**  
All orders by post must be sent to our Acton Address



# NEWS BRIEFS

infinity, which is not possible. The simple circuit thus has certain imperfections (a non-linear scale) but it has been described because it illustrates the principle of deriving the phase shift of a voltage of constant amplitude by exploiting the semicircular locus which is a common feature of many electrical circuit responses.

The value of  $R_1$  was chosen so that at maximum value it was greater than the reactance of  $C_1$ , thus allowing phase shifts of greater than 90 degrees to be obtained. The amplitude of the output voltages to the c.r.o. are individually adjustable by means of  $R_2$  and  $R_3$ . With these voltages set to give equal deflection in both vertical and horizontal planes on the c.r.t. screen, and the phase shift control set to exactly 90 degrees, a circular trace will be obtained. If the phase shift control is varied above and below this point an ellipse having various magnitudes of minor axis will be observed. The phase shift control can be calibrated by means of one or both of the methods described at the beginning of this article, see Figs. 2d and e.

While the transformer used is shown as a 12 volt heater transformer with a centre tapped winding, a transformer having two 6.3 volt windings could be used, the windings being connected in series and the centre tap taken from the junction. If such a transformer is

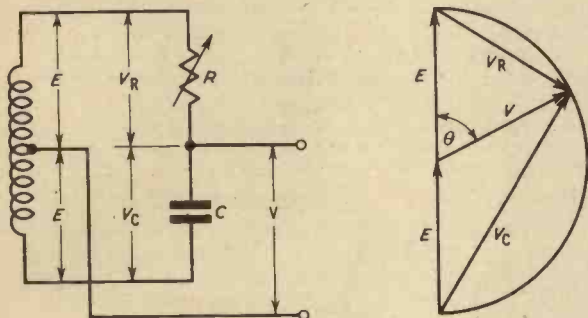


Fig. 19. Illustrating the function of the phase shift unit

used the finish of the first winding must be taken to the start of the second winding. If they were connected in reverse order, no output would result due to the windings being in opposition. This unit, when completed and calibrated, is not only very useful for general oscilloscope work but may also be used for demonstration purposes.

## OSCILLOGRAMS

Finally a number of oscillograms are shown in Figs. 20a to o, these being photographic records of actual oscilloscope traces. These oscillograms illustrate very clearly some of the points and oscilloscope techniques discussed in this article. These records were taken at various times, no special apparatus being used other than the test circuits described in this article.

It is hoped that this rather brief summary of the oscilloscope and some of its more everyday applications show that it is not simply a device for "viewing waveforms" but an extremely versatile and reliable instrument capable of a relatively high degree of accuracy. It can be used to carry out tests and achieve results which would be possible on no other instrument, its limitations often being simply the limitations of the user. ★

## Radar and Electronics Association

CONGRATULATIONS to the Radar and Electronics Association on "becoming of age".

Twenty-one years ago the Radar Association was founded at R.A.F. 60 Group Headquarters, Leighton Buzzard. From then the Association has steadily progressed, and with the change of name some years ago, is now a fully recognised body of ex-Service personnel and technicians. Among the members are some of the world's greatest scientists, as well as students from all parts of the world and a large number of ex-members of the forces.

Membership is open to those who have worked on radar or other branches of electronics for 3 years or more, in industry or the armed forces.

Particulars can be obtained from The Secretary, 43 Grove Park Road, Chiswick, London, W.4.

## Audio Festival and Fair

THE Audio Festival and Fair will be held at the Hotel Russell, Russell Square, London, W.C.1 from March 30 to April 2. Tickets may be obtained free of charge through the usual retail shops.

## Russian Premier sees British Electronics

IN response to his request to be shown the most advanced automation equipment in Britain, the Russian Prime Minister, Mr Alexei Kosygin was invited to tour the Borehamwood factory of Elliott-Automation where exhibits of particular interest to Russia were assembled including microelectronics, space research and laser applications.

Highlights of the exhibition were the microminiature 920M computer and part of the blind landing system for the Anglo-French Concorde supersonic airliner. Mr Kosygin was accompanied on his tour by the Minister of Technology, the Rt. Hon. Anthony Wedgwood Benn, M.P., and Sir Leon Bagrit, Chairman of Elliott Automation. The visit was part of a very full programme of engagements on February 8.

## Larger R.S.G.B. Show

THE R.S.G.B. International Radio Engineering and Communications Exhibition is to be enlarged and held this year at the Royal Horticultural New Hall, London, S.W.1.

The new venue will provide twice the space of previous exhibitions and Government services are expected to give support.

The dates to note (earlier than usual) are Wednesday, September 27 to Saturday, September 30 inclusive.

## BBC Handbook 1967

THIS compilation of facts and figures, provides an informative guide to the structure of the BBC and its programme services and engineering. This latter section describes briefly the transmitters used on the broadcast bands and includes comprehensive lists of the frequencies and channels used, with practical tips on achieving optimum reception. Coloured maps provide the locations and service areas of BBC-1 and BBC-2 television channels and v.h.f. regional sound radio stations.

Containing 264 pages of information with a considerable number of photographs, this handbook is available from the BBC Publications Dept., 35 Marylebone High Street, London, W.1. — price 7s 6d.

# detached particles

JOHN VALENCE

## COMMUNICATIONS THE KEY

Are our political leaders overselling technology as the key factor in our future prosperity? There are certainly plenty of critics who listen disbelievingly to pleadings that we must strive and make even greater efforts in this field.

If such unbelievers fail to be swayed by the urgent voices crying out in their own country, maybe they will heed the words of an outsider. Here I am referring to Mr R. W. Sarnoff, President of the Radio Corporation of America. In a recent address to a group of British business men, Mr Sarnoff stated that Britain stands on the threshold of its greatest era of prosperity since the Victorian age—*provided it makes full use of new communications and information technology.*

Let me remind the faint hearts and doubters amongst us that we have not done so badly in the field of communications in the past. It was due to the encouragement and financial backing from the British Post Office that young Marconi was able to develop his early experimental work into the resounding practical achievement of long distance communication without wires. That was in 1896.

Today the Post Office (despite much belabouring from less informed members of the public) is still very much on its toes and ready to seize opportunities for sponsoring and exploiting new techniques.

Currently the P.O. is pioneering in the field of pulse code modulation. Its new EMPress exchange, due to be operational at the end of this year, will be the world's first pulse code modulation tandem exchange.

Another knock at our doubting Thomas's: Pulse code modulation was the brain child of an Englishman, Mr A. H. Reeves. It would be fair to add that this invention of the 1930's was not capable of practical implementation until the transistor was born, and we must acknowledge the American parentage of this particular electronic marvel.

A final thought on communications brings me back to politicians again. Surely it was an inspired gesture for our Prime Minister to present Mr Kosygin with a Pye Pocketfone system during the Soviet P.M.'s visit to Britain. A symbol of some significance, let us hope.

## MARRIAGE COUNSEL

Since electronic computers are now entering the field as matchmakers, it behoves electronics technology to do all in its power to ensure the permanency of the marriages it may have instigated.

I don't know how many cases in the divorce courts stem from one of the partners' habit of snoring. If of sufficient repetition rate and peak audio power, this kind of interference could I suppose be considered to constitute a form of cruelty and lead to the dissolution of the marriage.

However, should you be an inveterate snorer, do not despair that your marriage will end on the rocks... there is hope in the form of an electronic device now being tested on patients in a Sussex hospital.

A throat microphone picks up the snores and this signal triggers off a tiny pulse generator strapped to the

patient's arm, and an electric impulse is received. It is claimed that the "shocks" are not strong enough to wake the person, but they do set up a mental block against snoring. Eventually the apparatus can be dispensed with but the effect continues, so they say.

Just another of electronics' gifts to humanity.

## TAKE-OFF TRANQUILISER


The well meaning attempt by British Rail to entertain their passengers in main line termini has been badly received, as I mentioned last month. But the British traveller is not always so adamant in his objection to background music. Apparently his views change remarkably when he takes to the air.

In response to popular demand (!) British European Airways will as from this April play recorded music to their passengers both before and after take-off. Trident and Comet aircraft have been equipped to provide this new service. Light music of the "My Fair Lady" type (pops are definitely *out*) will be reproduced from cassette type tape recorders operated by the cabin staff.

I was at first a little mystified by the official statement that "... light music is to be played before and after take-off. BEA cabin staff will ensure that the music IS turned off when the aircraft is airborne." Then it dawned on me. Just a short spell of sweet, soothing soporific music to carry us over those anxious moments as our aircraft shrieks down the runway. (Even seasoned air travellers will admit to a certain apprehension during these few moments).

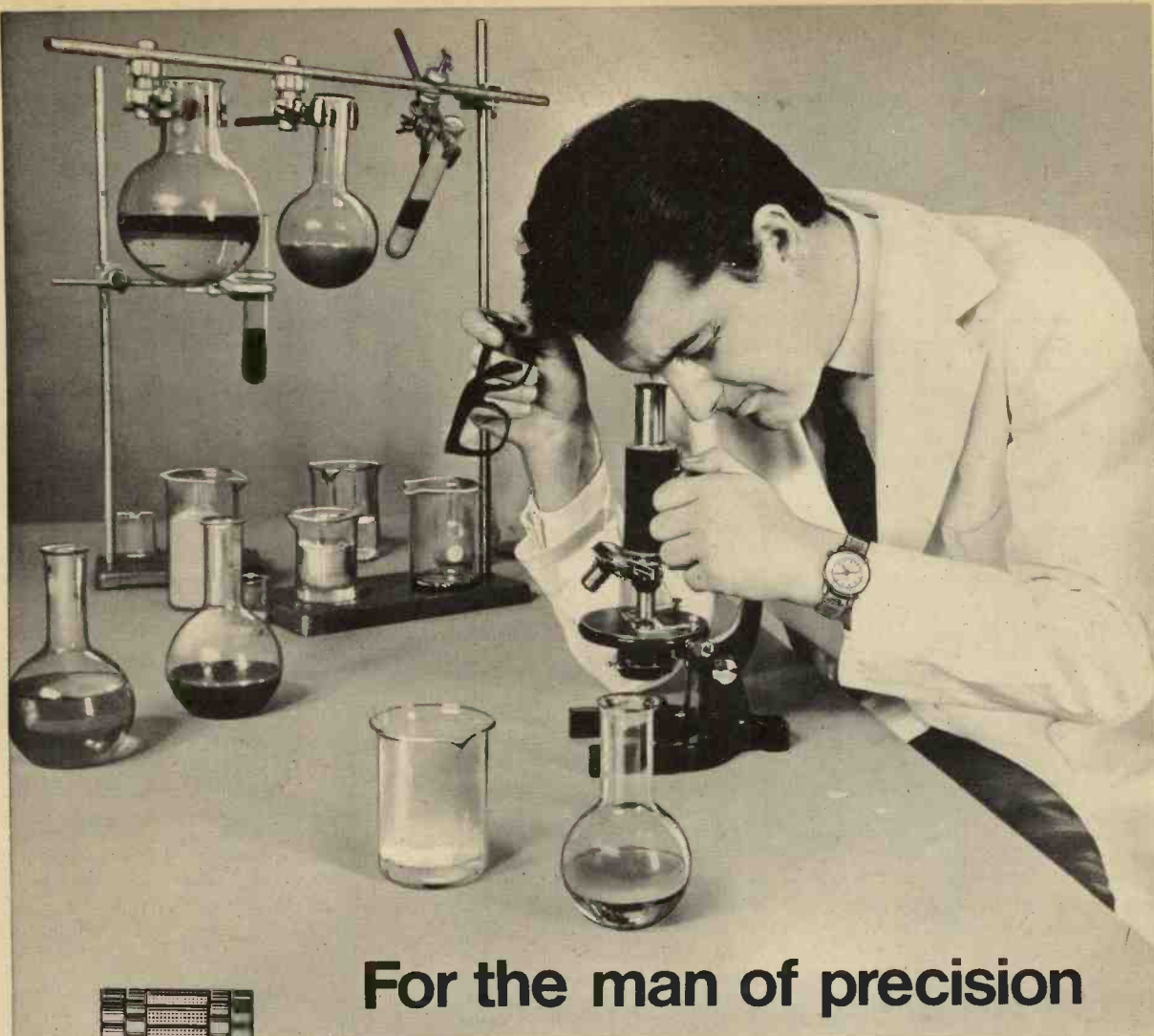... From Ringway, back to Piccadilly, Manchester: perhaps British Rail can take heart from the fact that *their* passengers do not (it seems) require any such sweet sounds to cajole them to board the London bound express. Something here, methinks, for the BR publicity people to turn to good account. A chance for some real oneupmanship, if they are *really* clever.





**For the man of precision**

## Seiko World Time Watch

Now made available to readers of *PRACTICAL ELECTRONICS* for £21 . 9 . 6d.

**WITH A 100% MONEY-BACK GUARANTEE  
IF NOT COMPLETELY SATISFIED**

SEIKO watches are precision time-keeping instruments produced with painstaking care under a strict quality control system.

The SEIKO WORLD TIME AUTOMATIC gives you at any time of day or night, the exact time in 24 of the world's leading capitals, as well as Greenwich Mean Time and the date of the Month. This 17-jewel watch has a built-in antimagnetic hairspring, unbreakable mainspring and full rotor finely poised over six ball bearings, and is shockproof. It is fully guaranteed to give you accuracy, pleasure and absolute dependability.

The World-wide reputation of Seiko won them the honour of producing all the high-precision timing equipment for the 1964 Olympic Games.



**USE THIS 100% MONEY-BACK GUARANTEE FORM**

Please send me a SEIKO WORLD TIME WATCH. My remittance is enclosed and I understand it will be refunded if I am not completely satisfied.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

(E)

Cheques and postal orders must be crossed and made payable to Watch Division, WSR Limited, Dept. E, 30/32 Southampton Street, London, W.C.99. Cheques should have name and address on the reverse. This offer is available only to U.K. readers.

# BI-PAK

(DEPT. E)

8 Radnor House  
93/97 Regent St.  
London, W.1



# SGS FAIRCHILD

BRAND NEW—FROM USA  
SCOOP PURCHASE—8 LEAD  
EPOXY CASE—LOW COST—

- μ L 900 "Buffer" 19/6
- μ L 914 "Gate" 19/6
- μ L 923 "J.K." 35/-

COMPLETE  
DATA AND  
CIRCUITS SEND  
1/6 OR FREE  
WITH ALL IC  
ORDERS

THESE  
DEVICES OPEN UP A WHOLE NEW CON-  
CEPT IN THE WORLD OF ELECTRONICS

## INTEGRATED CIRCUITS

Our vast stocks change daily with hundreds of Semi-conductor bargains becoming available. Just send 2/6 to cover 3 months mailing of our latest stock lists, eqvt. charts, circuits, etc.

Minimum Order 10/- CASH WITH ORDER  
PLEASE. Add 1/- postage and packing per Order.  
GUARANTEED by return postal service. Overseas add extra for Airmail.

### VALUE PAKS FOR '67

NEW UNTESTED

120 GERM. SUB-MIN. DIODES 10/-

20 ALL TYPES MIXED VOLTS ZENERS 10/-

25 SIL. NPN 200 M/cs TRANSISTORS 10/-

20 1 Amp. GERM. up to 300 PIV RECTIFIERS 10/-

60 SILICON 200 mA DIODES 10/-

16 SILICON 750 mA TOP-HAT RECTIFIERS 10/-

50 MIXED GERM. TRANSISTORS 10/-

10 STUD. 2 AMP SILICON RECT. 10/-

10 SCR'S UNMARKED, UNTESTED VOLTAGE RANGE 1 Amp 50-400 PIV 20/-

### SCR's (THYRISTORS)

PIV	1 AMP (TO-5 can)	7 AMP (STUD)	16 AMP (STUD)	30 AMP (STUD)
25		7/6		30/-
50		8/6	10/6	35/-
100	7/6	8/6	15/-	45/-
200	12/6	15/-	20/-	55/-
300	15/-	20/-	25/-	
400	17/6	25/-	35/-	80/-
500		30/-	45/-	95/-
600		40/-	50/-	

### NEW SILICON RECTIFIERS TESTED

PIV	750 mA	3 AMP	10 AMP	30 AMP
50	2/-	3/-	4/6	9/6
100	2/3	3/6	6/-	15/-
200	2/6	4/6	6/6	20/-
300	3/-	4/9	8/-	22/-
400	3/6	6/-	9/-	25/-
500	4/-	6/6	9/6	30/-
600	4/3	7/-	10/-	37/-
800	4/9	8/-	15/-	40/-
1000	6/-	10/-	17/6	50/-

750 mA TOP HAT TYPE 3, 10 & 30A STUD STPE



### NEW—SILICON BRIDGE RECTIFIERS —TESTED

600 PIV 2 Amp at 55°C 25s. each.  
800 PIV 2 Amp at 55°C 30s. each.

### TUNNEL DIODES

AEY11 Full Data 15/- each  
STC 1050 m/cs

647 PAGE, BY G.E. (USA) TRANSISTOR MANUAL  
CIRCUITS, APPLICATIONS S.C.R. CHARACTERISTICS THEORY BY G.E.

(30/- EACH) INCLUDING THE LIGHT P.P. 2/6 ACTIVATED S.C.R. AND GATE TURN-OFF SWITCH THEORY/RATINGS/APPLICATIONS

ALL THE INFORMATION YOU NEED 7TH EDITION

ALSO COVERING THE BROADEST LINE OF RECTIFIER COMPONENTS  
409 PAGES 3RD EDITION

### LOWEST PRICE YET LARGEST RANGE EVER



### NEW TESTED VALVE PAKS

3 OC139 Trans. NPN Mullard	10/-
2 Drift Trans. 2N1225 100 M/Cs PNP	70/-
6 Matched Trans. OC44/45/81/81D	10/-
4 OA10 Diodes Mullard	10/-
15 Red Spot AF Trans. PNP	10/-
15 White Spot RF Trans. PNP	10/-
3 Sil. Rects. 3A 100/400 PIV	10/-
4 NPN Trans. Switching	10/-
2 10 Amp. Sil. Rect. 50/100 PIV	10/-
8 Diodes 4 OA70, 4 OA79	10/-
1 5 AMP SCR 100 PIV	10/-
3 Sil. Trans. 28303 PNP	10/-
5 GE1884 Trans. Eqvt. OC44	10/-
10 Assorted Computer Diodes	10/-
4 Zeners 5, 12 Vits Mixed	10/-
4 2G417 Trans. Eqvt. AF116/117	10/-
2 200 M/Cs Sil. Trans. BSY26/27	10/-
2 Bi-directional Trans. ASY66	10/-
4 High Current Trans. OC42	10/-
2 Power Trans. OC26/35	10/-
5 Sil. Rects. 400 PIV 250mA	10/-
3 OC71 Trans. Mullard	10/-
3 OC75 Trans. Mullard	10/-
3 NPN Sil. Trans. 70 M/Cs	10/-
1 Power Trans. OC20 100 Vits	10/-
5 OA47 Gold Bonded Diodes	10/-
4 OA202 Sil. Diodes Sub-Min	10/-
3 OC77 Trans. Mullard	10/-
8 OA81 Diodes CV448	10/-
3 Sil Rects. 400 PIV 500 mA	10/-

FREE One 10/- Pack of your own choice free with orders valued £4 or over FREE

3 High vit. AF Trans. PNP ACY17	15/-
3 BSV95A Sil. Trans. STC	15/-
3 Sil. Trans. OC200 Mullard	15/-
2 Sil. Power Rect. 6 Amp. 200 PIV BVZ13	15/-
1 AF139 GERM. Trans. 1500 M/Cs	15/-
1 Sil. Power Trans. 100 M/Cs TK201A NPN	15/-
6 Zener Diodes 3-15 Vits. Mixed 400mW	15/-
5 OA5 Gold Bonded Diodes Mullard	15/-
1 2N1132 PNP PLANAR Trans. Sil	15/-
2 2N697 NPN PLANAR Trans. Sil	15/-
4 GERM. Power Trans. eqvt. OC16 Mullard	15/-
1 UNIJUNCTION Trans. 2N2646 G.E.	15/-
2 Sil. Trans. 60VCB 200 M/Cs. ZT63/84	15/-
1 Sil. PLANAR Trans. BSY25 NPN 1000 M/Cs	15/-
1 Sil. Trans. 1S104 150 M/Cs MFS 200 NPN	15/-
2 SCR's 50 PIV 1 Amp. TO-5 can	10/-
1 Tunnel Diode 1N370 (TD-5) G.E.	15/-
1 2N2160 UNIJUNCTION Trans. TO-5 can	15/-
2 Sil. Rect. 5 Amp. 400 PIV Stud	15/-
2 GERM. Power Trans. OC28/29	15/-
2 ZENERS 25 Watt 18 & 22 Vits	15/-
5 Sil. Rect. Type BY100 800 PIV 500mA	20/-
8 Sil. Rect. 400 PIV 200/500mA	20/-
25 Mixed Sil. & GERM. Trans. New Marked	30/-
40 Mixed Semiconductors New Marked	40/-
1 Logic Module Handbook & Catalogue	17/6

BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

# Readout —

## A SELECTION FROM OUR POSTBAG

### Battle cry

Sir—May I join the valve versus transistor battle? I have been unable to find any decent transistor designs. To give one example, look at Mr. R. Hirst's stereo amplifier (December 1966), and compare it with the Mullard 5-20 circuit of 1955 vintage. On paper, my stereo version of this costs the same as Mr. Hirst's to build, and the amplifier occupies approximately the same space; (it uses a separate power supply box, which may be hidden) but here the similarity ends.

The basic valve amplifier has a better signal to hum and noise ratio (90dB below 20W r.m.s. as opposed to 90dB below 10W) at approximately the same sensitivity (250mV into 1M $\Omega$ ); a vastly superior frequency response (30Hz–20kHz  $\pm$ 0.5dB at 27W r.m.s.); excellent rise time (5 $\mu$ s); very low overall phase-shift (20 degrees at 20kHz); and a remarkable damping factor of 50 (into 15 $\Omega$ ) and hence excellent stability, compared with the transistor amplifier.

Although some people will say that a maximum output power in excess of 100W (music power) is too much, just think how well it will perform at lower outputs, remembering that it costs the same as an inferior transistor amplifier. The 5-20 will give 20W r.m.s. at 0.05% distortion, rising to only 0.1% at 27W. Inter-modulation and beat-note distortion products total 0.7% of carrier amplitude at 27W r.m.s. There is, of course, no crossover distortion with valves. Using d.c. heating, a hum and noise figure as good as, if not better than, the transistor pre-amp may be achieved with EF86 (–70dB). All this, coupled with the fact that no 'scope is required for setting up, and that earth return impedances are not critical, you have to admit that the valve amplifier using the ubiquitous EL34, easy to obtain, hard to destroy, not requiring

matched valves (where on earth does one get matched NKT403 from, and for how much?), is far better value for money than the semiconductor one.

For those with very small rooms, the famous 5-10 amplifier has identical performance to Mr. Hirst's but costs a very great deal less to build, and need not occupy very much more space. Printed circuit panels for valve amplifiers are very easy to design (i.e. both 5-20 and 5-10) and etch since there is only a quarter of the components involved. This could lead to greater reliability in those of us whose soldering is not quite what it should be, since there will only be a quarter of the joints involved as well.

Please could someone explain the purpose of the f.e.t. input of this transistor amplifier. The best ceramics give 100mV into 250pF, and all the speakers (both ESL & EMLs) that I have ever heard of cut off below 30Hz, so presumably there will be insufficient signal to drive the amplifier, and to drown the l.f. oscillations (rumble) that many enclosures seem to give without high-pass filters (the 5-20 amplifies down to 15Hz easily, but Mullard recommends that signals below 30Hz be attenuated, presumably for this reason.) What sort of phono (ugh!) gives 250mV and needs 50M $\Omega$  anyway?

\* These figures were obtained from a Mullard publication, "Mullard Book of Audio Amplifiers".

F. Middleton,  
London, S.W.2.

*It would appear from your recent letter that you find very little use for any unit that may be transistorised and this seems to be based on quite a quota of incorrect assumptions which I have listed below.*

*To contain a stereo version of the Mullard 20 Watt amplifier with it's associated pre-amplifiers, a cabinet area of approximately 3000 cubic inches is required and yet for my 10 Watt transistorised design which incidentally will*

*deliver 17 Watts per channel, an area of approximately 700 cubic inches is required.*

*The delight of listening to an amplifier capable of giving an output with a distortion content of less than 0.05% must be immense. I have yet to meet any listening expert capable of determining better than 0.2% under normal listening conditions.*

*Output valves are notorious for becoming inefficient in emission in a relatively short period of time whereas transistors could have a useful life of 25 years or more, depending upon the treatment.*

*Nothing is simple in the design of a high fidelity system, even the printed circuit board, and it is entirely incorrect to assume that earth return paths are of no consequence in a valve system.*

*Economically the entire transistorised version may be purchased for less than it would cost to buy the transformers and valves for a valve version.*

*The signal to noise ratio for the Mullard Unit is not 90dB as you assume but 53dB, not quite up to the 90dB of the transistor version (Ref.: page 79 "Mullard Circuits for Audio Amplifiers").*

*You also may notice that reference is made to the inadequacy of the 100k $\Omega$  input impedance (page 79) and notice the 35dB of compensation required to restore the bass response to something of it's original value. With a standard transducer having a capacitive output in the order of 1000pF then it would be necessary to ensure that the input impedance of the amplifier is in excess of 5 megohms to have a relatively flat output at 70Hz.*

*The explanation that you require is contained in the following equation showing that the output from a capacitive source will be 3dB down when,  $X_C$  = the input impedance of the amplifier.*

*Later works by P. Tharma of Mullard Ltd. described in detail transistor power amplifiers, obviously for some good reason.*  
—R.H.

### Wanted!

Sir—Young radio enthusiasts willing to form a club in South London for young people (up to about 20 years). Meetings will be made as interesting and varied as possible with outings, competitions, etc., and always at least one "ham" station on the air.

If the turnout is reasonable, the Sir Philip Game Boy's Club (near East Croydon station) will let us use part of their premises.

Will anyone interested please contact me at the address below. All letters will be answered giving details of meetings when known.

A. D. A. Hansen, G3VLJ  
(aged 16),  
99, Stretton Road,  
East Croydon, Surrey.

continued

## Cold comfort

Sir—In the *Detached Particles* page in the January issue, under the above heading, it is suggested that the Electricity Council's "peep into the future" failed to take account of the impact of the younger branches of technology such as transistors and cold cathode fluorescent lamps which, on your reckoning, will lead to reduced heat gains.

The fact is that fluorescent lighting, despite its relatively high efficiency, is today the major source of heat from light. Incidentally, cold cathode fluorescent lamps produce, paradoxically enough, more heat for the same light output than the hot cathode lamps which are mostly used today, while electroluminescent panels produce far more heat than either!

If we were prepared to accept green light we could get nearer to the cold light ideal, failing which we have to accept a definite limitation, imposed by our visual mechanism, on the efficiency of production of white light.

The best present day light sources are closer to this optimum efficiency than is often realised and, with artificial lighting levels still only a fraction of natural lighting levels, we must expect heat from light to become even more important in the future.

As to transistors, they may produce less heat than thermionic valves but this factor is infinitesimal compared with the inevitable increase in the energy controlled by them.

Finally, may I correct the impression given in your comment that the all-electric new town represents a "peep into the future". It can be built *now*, it makes sense *now*, and it might well be the only sort of new town which will still make sense when it is finished.

R. H. Phillips,  
The Electricity Council,  
EDA Division,  
London, S.W.1.


## Temperature loss

Sir—I am writing in connection about the article *Remote Temperature Measurement* which appeared in the January issue.

I have constructed the circuit and have found it to be unsatisfactory for these reasons:

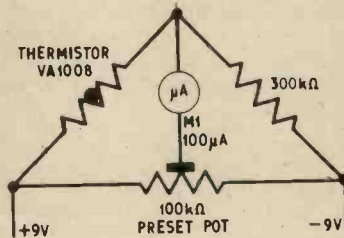1. costly to build
2. tends to be large in size
3. not very sensitive

To combat these problems I have reconstructed the circuit entirely and based it on a simple d.c. resistance network (see diagram).



The circuit has worked very well indeed and using a Radiospares MR26 meter I have obtained a f.s.d. of 100 degrees centigrade and a zero for 0 degrees centigrade. The negative temperature coefficient resistor used was sealed in a glass tube using Araldite.

L. G. Jones,  
Worksop,  
Notts.

The reply to Mr Jones' three main objections to my article are as follows:

1. Costly to build.  
No, the electronic circuitry is in effect used as a d.c. amplifier and uses cheap transistors. The total cost of the parts mounted on the Veroboard could be as little as 15s 0d, this virtually offsets the addition of a 100µA as against a 1mA meter. Whatever system is used, a meter, thermistors and potentiometer are required.
2. Tends to be large in size.  
No, the size is controlled by the meter and switching arrangement, the Veroboard and components take up a small volume compared with these.
3. Not very sensitive.  
No, this system was used to greatly improve sensitivity and enables various temperature ranges to be accommodated.

Mr. Jones' design requires a setting up potentiometer for each temperature measurement, as does the published design. The meter reading is dependent on battery voltage to a large degree.

The thermistor will suffer from self heating effects due to the current flowing through it. The 100µA meter is more expensive than a 1mA meter which can be used in the published design. The MR26 meter costs £6 retail. 1mA meters are obtainable for 10s 0d. This was the main reason for using the pulse amplifier method.

Switching for more than one range will be more complicated due to having to switch two of the potentiometer connections and one of the thermistor. There is no padding of the thermistor which adjusts for the variation in the thermistor law. Other types of thermistors may be used in the published circuit, as long as they are between 100kΩ and 300kΩ at 20 degrees centigrade; the A25 may be obtained at much reduced cost from L.S.T. Components, 23 New Road, Brentwood, Essex.

The VA 1008 is cheaper but has too wide a tolerance for multi-range use.

I think Mr Jones has made the mistake which quite a lot of people do when first looking at a diagram; it is often easy to visualise something far more rudimentary which will seemingly perform the desired function but it is only when such devices are put to the test that the need for a more refined circuit becomes apparent.—A.T.

## Idle pinch

Sir—Having just read the article *Tape Recorder Auto-Switch* by Mr P. Rush in your January issue, I feel that it should be pointed out to your readers that damage may be caused to their tape recorders if it is used.

With the device described the tape recorder will have to be left with its function switch to the "record" position for a period of time during which the motors are not running, and this will cause damage to both the pinch wheel and idler, which in turn will result in a permanent increase in the "flutter" level.

T. J. Ledger, B.Tech.  
Longlands,  
Middlesbrough.

We admit that this device has certain limitations and that this was not made clear in the article itself. Apart from this, however, the auto-switch as described is an ideal device for use with inexpensive recorders. The author tells us he has not been able to detect any trace of wow or flutter as a result of its use. No doubt, if an expensive recorder was involved, such deficiencies would certainly come to light but, on the other hand, one assumes that owners of more sophisticated equipment would in fact invest in a more advanced switching system. In fact, the higher quality tape recorders do often incorporate electro-magnetic devices for enabling remote control of the pinch wheel.



## DE LUXE PLAYERS

4-Speed Players 9-tone Cabinets 17" x 15" x 9". High quality loudspeaker and High Quality Amplifiers ready built. Quality output. Volume and Bass controls. Special instructions enable assembly in 30 minutes, only 5 wires to join. 12 months' guarantee.



### TO BUILD YOURSELF

Post 2/6 per item.

**PORTABLE CABINET** As illustrated. To fit standard player or autochanger. **69/6**  
**RCS AMPLIFIER 3** WATT. Ready made and tested with UCL82 triode pentode valve. Volume and tone controls with knobs. Quality Loudspeaker. **89/6**  
**AUTOCHANGE UNITS**  
 Garrard SERP12 £4.19.6  
 Garrard SP25 £10.19.6  
 Philips AG1016 £12. 8.6  
 Garrard AT0 £20.19.6  
 Garrard LAB80 £24.19.6  
 Garrard 470 £20.19.6

**GARRARD TEAKWOOD BASE Wb1** Ready cut for mounting 1000, 2000, 3000, SP25, AT50. **72/6**

**INTEGRATED STEREO AMPLIFIER** 4 watt per channel. A splendid example of functional design and value. Grey/Silver Grackle cabinet size 10" x 8 1/2" x 3 in. 200-250V. A/c. Separate Gram and Tuner sections. Self contained pre-amp. and controls. Post 2/6 **£10.10.0**

### Q MAX CHASSIS CUTTER

Complete: a die, a punch, an Allen screw and key  
 1/4 in. 14/8 1/4 in. 15/9 1 1/4 in. 18/- 1 1/4 in. 20/8 2 1/4 in. 37/9  
 1/4 in. 14/8 1/4 in. 18/- 1 1/4 in. 18/8 1 1/4 in. 22/8 2 1/4 in. 44/9  
 1/4 in. 18/8 1 1/4 in. 18/- 1 1/4 in. 20/- 2 1/4 in. 34/3 3 in. sq. 31/6

**BARGAIN X-TAL PICK-UP ARM** Complete with ACOS LP-78 Turnover Head and Stylus 20/-; Stereo 30/-  
**SPEAKER** FRET Tigan various colours, 5 1/2 in. wide, 10/-; 2 1/2 in. wide, 5/- H. SAMPLES S.A.E.  
**EXPANDED METAL** Gold or Silver 12 x 12 in. 6/-  
**NEW GARRARD GRAM MOTORS** 100-1300 A.C. 15/- pair for 200/250V. (in series), or 10/- each Post 2/6.

**FULL WAVE BRIDGE SELENIUM RECTIFIERS:**  
 2 or 12 V outputs, 1 1/2 amp., 8/9; 2 a. 11/3; 4 a. 17/6  
**CHARGER TRANSFORMERS.** P & P 2/8. Input 200/250V. For charging at 2 or 6, 12 or 1 1/2 amps, 17/6; 2 amps. 21/-; 4 amps. 25/- . Circuit free. Ammeter 0 to 5 amp. 10/8.

**MOVING COIL MULTIMETER TK 25.** 47/6  
 0-1.000V. A.C./D.C., ohms 0 to 100k, etc.  
**MOVING COIL MULTIMETER EP10K.** 79/6  
 0-1.000V. A.C./D.C., ohms 0 to 3 meg. etc.  
**MOVING COIL MULTIMETER EP20K.**  
 0-2.500V. D.C. 20,000 ohms per volt, 0-1.000V. A.C. Ohms 0 to 6 meg. 50 Microamps full scale. **99/6**

**NEW MULLARD TRANSISTORS**  
 OC71 6/-; OC72 7/6; OC81D 6/-; OC81 6/-; AF15 8/-; AF14 8/6; OC4 8/-; OC45 8/-; OC91 7/-; OC170 8/6; AF117 7/-; OC26 12/6; AD140 15/-; OC35 15/- Holders 1/3.

**ARDENTE TRANSISTOR TRANSFORMERS**  
 D0035, 7.3 CT. 1 Push Pull for 3 ohms for OC72, OC81 11/-  
 D0034, 1.75 1 CT. Push Pull Driver for OC72, OC81 11/-  
 D0038, 1.15 1 Output to 3 ohms for OC72, OC81 11/-

**TRANSISTOR MAINS ELIMINATORS.** FAMOUS "POWER MITE", 9 VOLT. SAME SIZE AS P99 BATTERY. **45/-**  
**FULLY SMOOTHED.** 150mA. FULL WAVE CIRCUIT.

**WEYRAD P50 - Transistor Coils**  
 RA2W 6 in. Ferrite Aerial Spare Cores..... 6d.  
 with car aerial coil..... 12/6  
 Driver Trans. LFDTA..... 9/6  
 Osc. P50/LAC..... 5/4  
 Printed Circuit, P50A..... 9/6  
 L.F.P50/2CC 470 kc/s..... 5/7  
 J.B. Tuning Gang..... 10/6  
 3rd L.F. P50/3CC..... 6/-  
 Weyrad Booklet..... 2/-

**Volume Controls 80 Ohm Coax 6d** yd.  
 Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG set  
 L.N. 1/8 3/4. D.P. 5/-  
**STEREO S/L 10/8, D.P. 14/6.**  
 Semi-air spaced Cable 40 yd. 17/6. 60 yd. 25/-  
**FRINGELOWLOSS 1/6** yd.  
 Ideal 625 lines

**COAXIAL PLUG 1/1-** PANEL SOCKETS 1/1- LINE SOCKETS 2/-  
**OUTLET BOXES, SURFACE OR FLUSH 4/6.**  
**BALANCED TWIN FEEDERS 6d.** yd., 60 or 300 ohms  
**TELESCOPIC CHROME AERIALS.** 6in. extends to 23in. 6/6 each. CAR AERIAL PLUGS 1/6. Sockets 1/3.

### TV REMOTE CONTROL

For PHILIPS 19TG111A, 121A, 125A, 142A, 23TG111A, 113A, 121A, 181A, STELLA T21033A 39A, 43A, 53A, COSSOR CT91810A, 21A, CT8310A, 21A, 31A PHILIPS Price: 3 gns.  
 Our Price **12/6** 2/6  
 Brand New. Includes 11ft. 7-way cable, MULLARD OAB2 12 pots., 3 switches, 5 resistors



**RETURN OF POST DESPATCH** Post and Packing 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/-

## BLANK COMPONENT SPECIALISTS

Written guarantee with every purchase. (Export: Send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door, S.R. Stn. Selhurst. Tel: THO 1665

**'STELLA RECORD PLAYER AMPLIFIER'**  
 4 watt. 2 stage. 3 to 7 ohm. Neg. feed back. UCL82. UY85. 200-250V. A.C. tapped input. Chassis size 8 x 2 1/4 x 4 in. high. Gold/Walnut knobs. Volume and Tone controls on separate Polish Wood Panel 6 x 2 in. Brand new with makers' guarantee. **BARGAIN PRICE P & P. 78/6**

**NEW TUBULAR ELECTROLYTICS | CAN TYPES**

2350 v. 2/3	100/25 v. 2/-	8/600 v. 9/6
4350 v. 2/3	250/25 v. 2/8	16/600 v. 12/6
9/450 v. 2/3	500/25 v. 3/-	16-16/500 v. 7/6
18/450 v. 3/-	8+8/450 v. 3/6	32-32/450 v. 6/-
32/450 v. 3/9	8+16/450 v. 3/9	50+50/350 v. 7/-
25/25 v. 1/9	16+16/450 v. 4/3	60+100/350 v. 11/6
50/50 v. 2/-	32-32/350 v. 4/6	100+200/275 v. 12/6

**PAPER TUBULARS**  
 350v.-0.1 9d., 0.5 2/6; 1 mfd. 3/-; 2 mfd. 150v. 3/-  
 500v.-0.001 to 0.05 9d.; 0.1 1/-; 0.25 1/8; 0.5 3/-  
 1,000v.-0.001, 0.0022, 0.0047, 0.01, 0.02, 1/8; 1, 0.047, 0.1 2/6.  
 E.H.T. CONDENSERS. 0.001mfd. 7kV., 6/8; 20kV. 10/8.

**SUB-MIN. ELECTROLYTICS.** 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 250 mfd. 15v. 2/8; 500, 1000 mfd. 15v. 3/6; 2000 mfd. 25v. 7/-  
**GERAMIC.** 500 v. 1 p.f. to 0.01 mfd. 9d. Discs 1/-  
**SILVER MICA.** Close tolerance (plus or minus) p.f. 5 to 47 p.f. 1/- ditto 1% 50 to 800 p.f. 1/-; 1,000 to 5,000 p.f. 2/-  
**TWIN GANG.** 0-0.9 208 p.p.f. + 176 p.f. 10/8; 365 p.f. min. tolerance 10/-; 500 p.f. standard with trimmers 9/-; 500 p.f. midgate less trimmers 7/8; 500 p.f. slow motion standard 9/11  
**SHORT 3-gang 500 p.f. 18/8.** Single 0.007 365 p.f. 7/6. Twin 10/-  
**SMALL TUNE.** Single 10 p.f. 25 p.f. 25 p.f. 75 p.f. 100 p.f. 160 p.f. 5/6 each. Can be ganged. Couplers 9d. each.  
**TUNING.** Solid dielectric. 100 p.f., 300 p.f., 500 p.f., 3/6 each.  
**TRIMMERS.** Compression ceramic 30, 50, 70 p.f. 9d.; 100 p.f., 150 p.f., 1/3; 250 p.f., 1/6; 600 p.f., 750 p.f., 1/9.  
**250v. RECTIFIERS.** Selenium 1/6 wave 100mA 5/- BY 100 10/- CONTACT COOLED 1/6 wave 60mA 7/6; 85mA 9/6. Full wave 75mA 10/-; 150mA 19/8; T.V. rectis. 10/-

**SPECIAL OFFER! NEW B.A.S.F. TAPE**  
 7 in. L.P. 1,800 ft. (Cat. LGS35) 45/-  
 7 in. D.P. 2,400 ft. (Cat. LGS26) 70/-  
 Spare Spools 2/6. Tape Splicer 5/- Leader Tape 4/6.  
 Tape Heads: Collaro 2 track 28/6 pair. B.S.R. 4 track 99/8

### MAINS TRANSFORMERS

**E.M.I. 280-0-280, 100 mA.** 6.3 v. 4 a. 6.3 v. 2 a. 19/6  
 250-0-250. 50 mA. 6.3 v. 3.5 a. Rectifier 6.3 v. 25/-; 1 a. or 5 v. 2; Diodes 350-0-350, 29/8.  
 M.T. 510 300-0-300 v. 120 mA. 6.3 v. 4 a. 29/6  
**MINIATURE 200 v. 20 mA.** 6.3 v. 1 a. 10/8  
**MIDGET 220 v. 45 mA.** 6.3 v. 2 a. 15/8  
**SMALL 300-0-300 v. 70 mA.** 6.3 v. 4 a. 19/8  
**HEATER TRANS.** 6.3 v. 1 1/2 a., 7/6; 6.3 v. 4 a. 10/8  
**Ditto tapped sec.** 1.4 v. 2, 3, 4, 5, 6.3 v. 1 1/2 amp., 10/6  
**GENERAL PURPOSE LOW VOLTAGE.** Outputs 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v. at 2 a. 25/-  
 1 amp., 5 v. 10, 15, 20, 25, 30, 35, 40, 55, 60, 29/8; 2 a. 47/6  
 Sub-Min. Mains to 9 v. 80 mA. 1/4 x 1 1/4 in. 7/8  
**AUTO TRANSFORMERS 0-115-230 v.** Input/Output, 60w. 18/6; 150w. 28/-; 500w. 92/6; 1000w. 175/-

### CRYSTAL MIKE INSERTS

1 1/2 in. 6/8; BM3 1 x 1 in. 7/8; ACOS 1 1/2 x 1 in. 8/8  
**TANNOY CARBON MIKE** with Switch 5/8  
**MOVING COIL HEADPHONES** 1000 ohms (ex. Govt.) 12/8  
**H.R. HEADPHONES** 2000 ohms 12/8, 4000 ohms 15/-  
**H.R. HEADPHONES** 2000 ohms Super Quality 25/-

### 1967 GRAM CHASSIS

**Post 5/-**  
 Three Wavebands: Long, Med., Short Gram. EB81, EL5A, E280.  
 12 month guarantee. A.C. 200 250 v. Ferrite Aerial 5 watts 3 ohm. Chassis 13 1/2 in. x 7 in. x 5 in. dial size 13 in. x 4 in. Two pilot Lamps. Four Knobs. **£10.10**  
 Aligned calibrated. Chassis isolated from mains  
**DE LUXE STEREO GRAM CHASSIS v.H.F., M.W. SW** 19-50m, SW 60-180m. Magic eye, push buttons. **£19.19**  
 8 valve plus rect. Size 15" x 7" x 6" high

**HIGH GAIN TV. PRE-AMPLIFIER BAND I B.B.C.**  
 Tunable channels 1 to 5. Gain 18 dB. ECC84 valve.  
 Kit price 32/6 or 55/- with power pack. Details 6d.  
**BAND III L.T.A.** - same prices. Tunable channels 7 to 13.  
**BAND I or III.** Coils and circuit only, 9/8. Chassis 4/8 1/2  
**B.B.C. 2 SUPER BOOSTER** transistor model. Ready built 75/-

**BLANK ALUMINIUM CHASSIS.** 18 s.w.k. 2 1/2 in. sides. 7 x 4 in. 5/6; 8 x 7 in. 6/6; 11 x 13 in. 6/6; 11 x 7 in. 7/8; 13 x 9 in. 9/8; 12 x 11 in. 12/8; 15 x 14 in. 15/-  
**ALUMINIUM PANELS 18 s.w.k.** 12 in. 5/6; 14 x 9 in. 4/8; 12 x 9 in. 3/8; 10 x 7 in. 2/8; 8 x 6 in. 2/-; 6 x 4 in. 1/6

**ALL PURPOSE TRANSISTOR PRE-AMPLIFIER**  
 Gain 14: 1.250v. or 9v. input. Ready built with Mu Metal input transformer for Mikes, Pick-Ups, Tuners. **15/-**  
 Instructions and circuit supplied. Post 2/6.

**THE INSTANT BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER**  
 200/250 v. A.C. Leadet S.A.E. **Post 35/-**  
 2/6



**RETURN OF POST DESPATCH** Post and Packing 1/6 unless otherwise stated. C.O.D. 5/- extra. Full List 1/-

## 337 WHITEHORSE ROAD, WEST CROYDON

Written guarantee with every purchase. (Export: Send remittance and extra postage, no C.O.D.) Buses 133, 68 pass door, S.R. Stn. Selhurst. Tel: THO 1665

**BAKER 12 in. STANDARD**  
 The ideal High Fidelity Loudspeaker.  
 Now with built in high efficiency tweeter cone.  
 Voice Coil impedance 15 ohms- Max. Power ..... 20 watts  
 Bass Res. .... 40/50 cps. Flux ..... 14,000 gauss.  
 Voice Coil diameter ..... 1 1/2 in.  
 Voice Coil material ..... Copper  
 Resonance ..... 40-14,500 cps.  
 Magnet material ..... Alcomax  
 Overall dia. .... 12 1/2 in.  
 Overall depth ..... 6 in.  
**PRICE £8 POST FREE**



**CATALOGUE S.A.E.**  
**GROUP MODELS FOR VOCALS**  
**BASS, LEAD AND RHYTHM GUITARS**  
 30-10,000 cps. Voice Coils 15 ohms. Heavy duty  
**'Group 25' 'Group 35' 'Group 50'**  
 25w. 5gns. 12in. 8 1/2gns. 15in. 5w. 18gns.

**LOUDSPEAKERS P.M. 3 OHMS.** 2 1/2 in., 3 in., 4 in., 5 in., 7 in. x 4 in., 15/8 each; 8 in., 22/6; 6 in., 18/6; 10 in., 30/-; 12 in., 30/-; 15 ohms 35/-; 10 x 6 in., 30/-; 8 x 5 in., 21/-; E.M.I. Double Cone 13 x 8 in., 3 or 15 ohm models, 45/- W.B. 10 in. HF1012, £5.10.0; 8 in. HF812, £4.10.0. Crossover 35/-, Horn Tweeters 3-18 Kc/s. 10 w 29/6; 20 w 20 Kc/s. 99/6.  
**JACK SOCKETS** 5ld. open-circuit 2/6, close-circuit 4/6. Chrome Lead Socket 7/6. DIN 3-pin 1/3; Lead 3/6. Phono Plugs 1/-, Socket 1/6. Banana Plugs 1/6. Sockets 1/6.  
**JACK PLUGS STANDARD.** Chrome 3/6. DIN 3-pin 3/6. WAVE-CHANGE SWITCHES WITH LONG SPINDLES. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way 3/6 each. 1 p. 12-way, or 4 p. 2-way, or 4 p. 3-way, 3/6 each.  
 Wave-changes 'MAKITS' 2 p. 16-way, 2 p. 6-way, 3 p. 4-way, 4 p. 3-way, 8 p. 2-way. Prices include click spindles, adjustable stops, spaces, etc., 1 wafer, 10/6; 2 wafers, 15/-; 3 wafers, 19/6.  
**TOGGLE SWITCHES,** sp. 2/-; sp. dt. 3/6; dp. 3/6; dp. dt. 4/-.

**DE LUXE TAPE SPLICER** Cuts, trims, joins for editing and repairs. With 3 blades. **14/6**

**4 CHANNEL TRANSISTOR MICROPHONE MIXER.** Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. **59/6**  
**2 WAY INTERCOM and BABY SITTER.** All transistor. 2 way call buzzer. Desk or wall mounting. Very good volume. For home office or shop. **59/6**  
 With long leads, battery, etc.

**FM TUNER 98-108 Mc/s** Six Transistor. Superbet. Ready built. Printed circuit. Calibrated slide dial **£8.10.0**  
 tuning. Size 6" x 4" x 2"

**3 WATT QUALITY AMPLIFIER.** 4 Transistor 1/6  
 Push-Pull Ready built, with volume control **75/-**

**NEW MANUFACTURERS SURPLUS UHF BBC 2 AERIALS**  
 BBC 2 Double Gold Ring Set Top Model ..... 22/6  
 BBC 2 Five Element Loft Model ..... 32/6; Outdoor 42/6

**\* RADIO BOOKS \* (Postage 9d.)**

Radio, T.V. Valves, Diodes, Transistor equivalents.....	10/8
High Fidelity Speaker Enclosures and Plans.....	5/-
Transistor Superbet Commercial Receivers.....	7/6
Mullard Audio Amplifier Manual.....	8/6
Radio Valve Guide, Books 1, 2, 3, 4, or 5.....	each 5/-
Practical Radio Inside Out.....	4/8
Transistor Audio Amplifier Manual.....	5/6
Shortwave Transistor Receivers.....	3/6
Transistor Communication Sets.....	6/-
Mullard Audio Radio Station.....	2/6
Modern Transistor Circuits for Beginners.....	2/8
Sub-Minature Transistor Receivers.....	5/-
Wireless World Radio Valve Data.....	9/8
At a glance Valve equivalents.....	6/-

**RESISTORS.** Preferred values, 10 ohms to 10 meg. 1 w. 1 w. 1 w. 20% 4d.; 1 w. 5d.; 1 w. 1 w. 10%; 8d. **HIGH STABILITY.** 1 w. 1 w. 2/- Preferred values, 10 ohms to 10 meg. 5% 5d.; 10 ohms to 22 meg. 3d. 5 watt 1 w. 1 w. 0.5 to 8.2 ohm 3 w. 1 w. 1 w. 10 ohms to 8,500 ohms 1 w. 1 w. 15K, 15K, 20K, 25K, 68K, 10W.  
**INTERCOM DROPPERS.** Midset. With sliders. 0.3 a., 1 K., 0.2 a., 1.2 K., 0.15 a., 1.5 k., 6/- each. **LINCORD** 100 ohms 1/2 in. twin plus resistance. 1/- ft.

**WIRE-WOUND 3-WATT WIRE-WOUND 4-WATT**  
**POTS.** T.V. Type. Values STANDARD SIZE POTS. 10 ohms to 30 K., 3/3, LONG SPINDLE VALUES  
 Carbon 30 K. to 2 meg., 3/- 50 OHMS to 100 K., 7/6.

**VALVE HOLDERS.** Int. Oct. 6d. Mazda Oct. 8d.; 87G, 88A, 88G, 89A. Mounted 9d. Ceramic 1/-; 87G, 89A Cans 1/-; Valve base plugs 87G, 89A. Int. Oct. 2/3.

**C.R.T. BOOSTER TRANSFORMERS**  
 for heater cathode short or failing emission. 25% and 50% optional boost, 200/250V. AC input. State tube voltage required, 2 or 6 or 13 v. Post 2/6. **15/6**

**BRAND NEW QUALITY EXTENSION LOUDSPEAKER**  
 In tough cream plastic cabinet with 20W, lead and adaptors. For transistor radio, intercom, mains radio, tape recorder, etc.  
 3 to 15 ohm matching Size: 7 1/2" x 5 1/2" x 3" **30/-** Post 2/6



**CALLERS WELCOME**

# Practical Electronics Classified Advertisements

The pre-paid rate for classified advertisements is 1/- per word (minimum order 12/-), box number 1/6 extra. Semi-displayed setting £3.5.0 per single column inch. All cheques, postal orders, etc., to be made payable to PRACTICAL ELECTRONICS and crossed "Lloyds Bank Ltd." Treasury notes should always be sent *registered post*. Advertisements, together with remittance, should be sent to the Advertisement Manager, PRACTICAL ELECTRONICS, George Newnes Ltd., Tower House, Southampton Street, London, WC2, for insertion in the next available issue.

## SERVICE SHEETS

**SERVICE SHEETS** for all makes Radio, T/V, Tape Recorders, 1925-1966. Prices from 1/- Catalogue 6,000 models, 2/6. Free fault-finding guide with all sheets. Please send stamped addressed envelope with all orders/enquiries. HAMILTON RADIO, Western Rd., St. Leonards, Sussex.

**SERVICE SHEETS**, Radio, TV, 5000 models. List 1/6. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**RADIO TELEVISION**, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6. SHE 8441.

## SERVICE SHEETS

4/- each, plus postage.

We have the largest supply of Service Sheets for all makes and types of Radios and Televisions, etc. in the country. Speedy Service.

To obtain the Service Sheet you require, please complete the attached coupon:

From:

Name: .....

Address: .....

### To: S.P. DISTRIBUTORS

35/36 Great Marlborough Street, London, W.1  
Please supply Service Sheets for the following:

Make: .....

Model No.: ..... Radio/TV

Make: .....

Model No.: ..... Radio/TV

Make: .....

Model No.: ..... Radio/TV

I also require the new 1967 list of Service Sheets at 1/6 plus postage. (please delete items not applicable)

I enclose remittance of ..... which includes postage

MAIL ORDERS ONLY Apr. PE

## MISCELLANEOUS

**ALUMINIUM CHASSIS. PANELS**, Etc. Quick service. 'One-offs' welcome. Send sketch for quotation (Stamp please). Trade Supplied. FAIRISGRADES LTD., Barling, Nr. Southend, Essex.

## MISCELLANEOUS

(continued)

**CONVERT ANY TV SET** into an Oscilloscope. Diagrams and Instructions, 12/6. REDMOND, 42 Dean Close, Portslade, Sussex.

"PRACTICAL ELECTRONICS" Proximity Detector. Photoflash Slave Unit. Radiation Counter. Auto Calendar. Doorbell Repeater. Car Burglar Alarm. Tape Recorder Control Unit. Recording Level Indicator. Integrated Stereo Amplifier, and all constructional projects going back to Issue 1. Send a.s.e. for your choice of itemised price lists. AJAX ELECTRONICS, 18A, Rumbold Road, Fulham, London, S.W.6.

### BERNIESOUND (AUDIO ENGINEERS)

Design-Build-Repair-Modify  
All types of Electronic Equipment  
For estimates write to:—  
Mr. Brown, 1 Effie Place, London, S.W.6.

**SWITCHING CIRCUITS.** A simple way of making (4 or 6) pole 2 way rotary switches suitable for breadboard layouts to designers of low voltage computer circuitry costing less than 1/- to make, materials can be purchased anywhere. Instructions and diagrams, 1/6. Send stamped addressed envelope to HOGANS, 67 Adelaide Road, Liverpool 7, Lancs.

2/-	OC 71	2/-
Due to bulk purchase, we are able to offer these fantastically popular transistors at the give-away price of only 2/- ea. Greater reductions for quantities. £1 per doz., £2 for 25, £5 for 100.		
PHOTO-TRANSISTORS—OCP 71.		
5/- ea.	3 for 10/-	
SUB-MIN ELECTROLYTICS—15 volt.		
8, 10, 30, 50 & 100 µF.	1/- ea.	
SUB-MIN MYLAR CAPACITORS—		
100 volt.	.001, .002, .005, .02, & .05 µF	9d. ea.
5% ±W HIGH STABILITY RESISTORS		
Your choice of values—only 4d. ea.		
BY 100 SILICON RECTIFIERS		
3/6 ea.	12/- for 4.	
GERMANIUM DIODES—OA 81 equiv.		
6d. ea.	5/- doz., 30/- per 100.	
For a quality tape transport system you require the three head tape monitoring facilities of the superb "MANHATTAN" tape pre-amplifier. Write for details.		
BEEJAY ELECTRONICS 106 Reddicap Heath Road, Sutton Coldfield, Warwickshire.		

## HEATHKITS

R.F. SIGNAL GENERATOR Model RF-1 5" Oscilloscope. Model 10-12U Signal Tracer. Model T-4 Vacuum Tube Voltmeter. Model UYA Capacitor Tester. Model CT-1 Universal. Avo Bridge. Offers. BOX No. 7.

## EDUCATIONAL

**HOME STUDY COURSES** in Practical Electronics. Free Brochure without obligation from: BRITISH NATIONAL RADIO SCHOOL, Reading, Berks.

## EDUCATIONAL

(continued)

**ALDERMASTON COURT POSTAL TRAINING** for B.Sc. (Eng.) Part 1, A.M.I.E.R.E., A.M.S.E., City & Guilds, G.C.E., etc. prepares you privately for high pay and security as Technician or Technologist. Thousands of passes. For details of Exams and Courses in all branches of Engineering, Building, Electronics, etc. (including latest information on C.Eng.), write for 132-page Handbook—FREE. Please state interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, (Dept. 125K), Aldermaston Court, Aldermaston, Berks.

**STUDY RADIO, TELEVISION & ELECTRONICS** with the world's largest home-study organisation. I.E.R.E., City & Guilds, R.T.E.B., etc. Also practical courses with equipment. No books to buy. Write for FREE prospectus stating subject to I.C.S., Intertext House, Parkgate Road (Dept. 577), London, S.W.11.

## TELEVISION SERVICING RADIOTELEGRAPHY RADAR MAINTENANCE

Full and Part-time Training Courses

Apply:—Director, British School of Telegraphy, 20 Penywern Road, Earls Court, London, S.W.5

A.M.S.E. (Elec.), City & Guilds, G.C.E., etc., on "Satisfaction or Refund of Fee" terms. Wide range of Home Study Courses in Electronics, Computers, Radio, T.V., etc. 132-page Guide—FREE. Please state subject of interest. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Dept. 124K), Aldermaston Court, Aldermaston, Berks.

**CHAMBERS GUIDE (New).** Details of 293 Careers and spare-time Business, Technical and Examination Courses. A Mine of friendly "know-how" for go-aheads. For free copy write—CHAMBERS COLLEGE (Dept. 856K), 148 Holborn, E.C.1.

**SEMICONDUCTOR EXPERIMENTS;** the practical way of learning electronics at home. With each experiment you receive all components, full instructions, test circuits, tabulation and graph sheets with sample results. Also low cost test equipment kits. Details free.

### ELECTRONIC EXPERIMENTS

49 HEATH LANE, BRINKLOW, RUGBY

## SITUATIONS VACANT

**ARE YOU INTERESTED IN ELECTRONICS?** Do you want an interesting job making, testing and installing specialist sound equipment? If you do, write to the Managing Director, STAGESOUND (LONDON) LTD., 11/12 King Street, Covent Garden, W.C.2.

20-25  
logical thinker  
ONC/HNC  
electrical  
OR  
electronic  
OR  
mechanical

Engineer

IBM Engineer

## with a great future in computers

This is an exciting opportunity for young engineers—the chance to join IBM's fast moving computer industry as a Field Transfer Engineer, working at the Data Processing Division's engineering centre at South Ruislip, Middlesex.

Initially they will overhaul and repair punched card equipment and this, along with day release education, will give them the progressive experience required to move on to computers—including the highly sophisticated System/360. And since IBM promotes solely on merit, and from within the company, aptitude and ability can enable them to advance to Data Processing Customer Engineers.

Starting salaries will be up to £1,100 a year, with non-contributory Pension and Life Assurance Plans and excellent working conditions.

This is an interesting and rewarding position in a rapidly expanding industry, and it offers outstanding career prospects to young men! So if you feel you can handle a really big future in computers just write, giving details of age, education and experience, to: R. F. Snelling, IBM United Kingdom Limited, Stonefield Way, South Ruislip, Middlesex, quoting reference DP/PE/715.

IBM

### RADIO TECHNICIANS

A number of suitably qualified candidates are required for permanent and pensionable employment (mostly in Cheltenham, but from time to time there are some vacancies in other parts of the U.K. including London). There are also opportunities for service abroad.

Applicants must be 19 or over and be familiar with the use of Test Gear, and have had practical Radio/Electronic workshop experience. Preference will be given to candidates who can offer "O" Level GCE passes in English Language, Maths and/or Physics, or hold the City and Guilds Telecommunications Technician Intermediate Certificate or equivalent technical qualifications.

Pay according to age, e.g. at 19—£747, at 25—£962 (highest age pay on entry) rising by four annual increments to £1,104.

Prospects of promotion to grades in salary range £1,032—£1,691. There are a few posts carrying higher salaries.

Annual Leave allowance of 3 weeks 3 days, rising to 4 weeks 2 days. Normal Civil Service sick leave regulations apply.

Application forms available from:

Recruitment Officer (RT)  
Government Communications Headquarters  
Oakley  
Priors Road  
CHELTENHAM, Glos.

## TECHNICAL TRAINING by ICS IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

I C S

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Electronics, Computers, etc. Expert coaching for:

- INSTITUTION OF ELECTRONIC AND RADIO ENGINEERS.
- C. & G. TELECOMMUNICATION TECHNICIANS' CERTS.
- C. & G. SUPPLEMENTARY STUDIES.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- P.M.G. CERTIFICATES IN RADIOTELEGRAPHY.

Examination Students Coached until Successful.

#### NEW SELF-BUILD RADIO COURSES.

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter—all under expert tuition.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES.

INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS

A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU !

International Correspondence Schools  
(Dept. 152), Intertext House, Parkgate Road,  
London, S.W.11.

NAME .....  
Block Capitals Please

ADDRESS .....

4.57

## TAPE RECORDERS, TAPES, ETC.

**TAPES TO DISC**—using finest professional equipment—45 r.p.m. 18/- S.A.E. leaflet. DEROY, High Bank, Hawk Street, Carnforth, Lancs.

**20% CASH DISCOUNT** on most famous makes of Tape Recorders, Hi-Fi equipment, Cameras, etc. Join England's largest Mail Order Club now and enjoy the advantages of bulk buying. Send 5/- for membership card, catalogues, price lists and ask for quotation on any item. C.B.A. (Dept. A18), 370 St. Albans Road, Watford, Herts.

**SAVE UP TO 20%** on most new, guaranteed, Hi-Fi and Tape Recorders. Large s.a.e. details. MICROSERVICE, Fourways, Morris Lane, Halsall, Lancs.

## RECEIVERS AND COMPONENTS

Very good general purpose transistors, type GET3, perfect for switching, multi-vibrators, etc. Sample 1/- Makers sealed pack of 10, 8/6. Silicon rectifiers. 50 p.p.v. 1.5A. 400 p.p.v. 0.75A, 2/6. 12V 5V. I.W. zeners, 3/6. J. COOPER, Outwell, Wisbech, Cambs.

**REPANCO** Transistor Coils and Transformer. For the Constructor. Send stamp for lists **RADIO EXPERIMENTAL PRODUCTS LTD.**, 33 Much Park Street, Coventry.

## R. & R. RADIO & TV SERVICE

Dept. P.E.

44 Market Street, Barup, Lancs. Tel. 465

Salvage Valves	Good Emission	Guaranteed
EF80 1/6	30P4 7/-	30FL1 5/-
ECC82 3/-	EB91 1/-	PL82 4/6
ECL80 3/6	EF85 5/-	PL36 7/-
30F5 5/-	30PL1 5/-	
PCF80 4/-	EY86 4/-	PCC84 4/-
PL81 5/-	6U4GT 5/-	PY81 3/6
PZ30 5/-	PY33 6/-	U301 6/-

**SPEAKERS** Ev Tx 3 ohm imp. 5" Rnd. and 6" x 4" 3/6. 8" Rnd. 6/-. Post 2/6.  
BY100, Rectifiers complete with 10 watt res. 6/-. Post 6d. Fireball Tuners, less cover caps 9/- post paid.

Ekco line o/p trans, U26 type 35/- post paid. Ferg line O/P 406T 30/-. Ferg 306 type. New, 70/- Cylidon type 'C' tuners 15/- post 2/-.


S.A.E. with all enquiries.  
9 x 4 Envelope for lists.

**COMPUTER BOARDS.** Two types, average 30, Planar Epitaxial Transistors, ZT708 or equiv., 300 Megs, 30 Diodes, Hstab Resistors 19/6 each. Polystyrene Capacitors, 350v. 680, 820, 1,800, 2,200, 2,700, 5,600, 6,800, 0-018, 0-022, 0-033, 125v. 1,000, 1,200, 1,500, 1,800, 3,300, 3,900, 4,700, 8,200, 0-01, 0-012, 0-015, 2/- dozen any selection. Heat Sinks 10W finned, 5/-. Miniature Relays, 1" x 1/2" x 1/2", 950 ohm, 2 pole change over 10/-. Electrolytics, 5,000 MFD, 50v. 6/8. 1,000 MFD, 60v. 5/-. 1,000 MFD, 30v. 4/-. 3,000 MFD, 10v. 2/-. Gold Bonded Diodes, 75v. P.I.V. 75mA. cards of 25, 10/-. Wire Wound Pots 5, 10, 25, 50, 100, 250, 500, 1k, 2k, 2.5k, 5k, 10k, 20k, 25k, 50k, 100k, not presets, 2/- each. Minimum order 5/-, post 1/-. **NEW CROSS RADIO**, 6 Oldham Road, Manchester 4.

## RECEIVERS AND COMPONENTS

(continued)

2N2926 4/-, OC71 3/9, OA81 1/9, 850v, 1/4 Rectifiers 4/-, 1W 5% H.S. resistors 4d. Add 6d. p.p. Discount on 10 and up. A. P. ROBSON, 41 Thunder Lane, NORWICH.



### NEW COMPONENTS

- ★ ASSORTED TRANSISTORS—6 Tested A.F. Devices ..... 9/6
- ★ ASSORTED RESISTORS—Hi-Stab. 300 off (5%, 10%, 1%, 1/2 watt, worth £3) ..... 15/-
- ★ SELECTED COMPONENTS—Over 100 Hi-Stab... Capacitors, Pots, Rectifiers, Switches, etc..... 10/-
- ★ TRANSISTORS—Matched Output Kite: OC81D and 2-OC81 ..... 9/6  
R.F. Kit: OC44 and 2-OC45 ..... 9/6  
OC44, 45, 70, 71, 72, 81 and 81D Equivalent, each ..... 3/-
- ★ GRAMOPHONE AMPLIFIER—Guaranteed, 1 watt, for 8 ohm speaker, 9 v. supply, 6 Transistor Unit..... 19/-

(P. & P. 1/6 per order, C.W.O.)

**ELMBRIDGE INSTRUMENTS LTD.**  
Island Farm Avenue, West Molesey, Surrey

**TRANSCEIVERS**, 5 trans., batts. As widely advertised. Limited number. Reduced to **£7.12.6** pair, p.p. 5/-. Refund guarantee. (Not for use in U.K.). **BORDER MAIL ORDER**, 18 Glendevon Road, Edinburgh.

### FAMOUS TRANS/RECEIVER



Covers 2-4.5, 4.5-8 Mc/s. (150-37 metres) in two bands. 230/250v. A.C. Mains. 11 valve superhet receiver and transmitter designed for voice and C.W. Incorporates test and tuning 500  $\mu$ A meter for voltages, aerial loading and current tests.



Panel controls Freq. P.A. Tuning Gain MCW, CVT RT, Het Tone, Nesting, On/Off, Quench, Aerial, AVC, LT-HT Tests. Supplied complete. Fully tested and working. Price £12.10.0. Carr. £1.0.0.

**RCA AR88D. RECEIVER** (Brand New) Freq. 540 Kc/s—32 Mc/s. 6 waveband, Mechanical Band spread with Logging scale, Auto and Man. Vol. control, disto Noise Limiter, BFO, Pitch and Var. HF Tone controls, RF & AF Gain, Var. selectivity with Crystal Filter. Complete with Instructions/Service Manual, £70. USED MODEL Fully tested and working £45. Carr. £2 on each.

**NATIONAL H.R.O. SENIOR RECEIVERS 5T MODEL**



In excellent tested condition. Complete with 9 coils 50 Kc/s—30 Mc/s and Power Unit. £31.10.0. Carr. 30/-.

**32 ft. TELESCOPIC AERIAL MASTS**  
Comprising 20 ft. 4 section tubular steel telescopic mast and 12 ft. folding whip; Can be erected in less than 5 minutes. Closes to 5ft. 9 in. Weight 21 lbs. Must have cast well over £20. Price 67/6. Carr. 7/6.

**ROTARY TRANSFORMER.** 12v. D.C. input, 250v. D.C. output at 125 mA. Size 3 1/2 x 5 1/2 in. Brand new 17/6. P. & P. 5/-.

**ALL 19 SETS AND PARTS AVAILABLE**  
Complete list of other bargains, 1/-. S.A.E. all enquiries. Credit Terms Available.

**A. J. THOMPSON (Dept. P.E.)**  
"EILING LODGE", CODICOTE, HITCHIN, HERTS.  
Phone: CODICOTE 242

## NOTICE

**BI-PAK SEMICONDUCTORS (REG.) MANUFACTURE AND DISTRIBUTE SEMICONDUCTOR AND SOLID STATE DEVICES IN PRE-PACKED FORM AND HAVE NO OTHER AUTHORISED EXCLUSIVE DISTRIBUTOR IN THE U.K. FOR ALL YOUR SEMICONDUCTOR REQUIREMENTS SEE OUR ADVERTISEMENT ON PAGE 308 OF THIS MAGAZINE OR WRITE TO BI-PAK SEMICONDUCTORS, 8 RADNOR HOUSE, 93/97 REGENT ST., LONDON, W.1.**

## RECEIVERS AND COMPONENTS

(continued)

### ECONOMY SEMICONDUCTORS

**New Ceramic Transistors made in U.S.A.**  
CS2926 red 855-110 3/6. Silicon Planar.  
CS2926 orange 890-180 3/9. 120 Mc/s ft. typ.  
CS2926 yellow 9150-300 4/-. 18V 300mW max  
CS2926 green 9235-470 4/9. Low noise NPN.

**Ultra High Gain Ceramics, U.S.A.**  
6645 red 8250-550 3/6. Silicon Planar.  
6645 blue 8500-1000 4/3. 15V 300mW NPN.

**Medium Power Silicon Planar**  
2N3053 NPN 60V, 1W max, 100 Mc/s ft. min.  
11/6. 40319 PNP 40V, 1W max, 100 Mc/s ft. min. 15/6.

These are 2W max. with heat sinks, 9d. each.  
**High Power H.F. Silicon Planar, NPN**  
2N3054 16W @ 100°C case. 90V, 4A, 25 Mc/s ft. typ. 26/-. GP407 15W @ 75°C case, 60V, 10A. 100 Mc/s ft. min. 56/3.

**High Power Silicon NPN**  
2N3055 65W @ 100°C case, 100V, 15A max.  
22/9. 40250 16W @ 100°C case. 50V, 4A max. 17/-.

**Germanium Low Power**  
2N1304 NPN } 20V 15W max. high gain  
2N1305 PNP } 8120 typical 4/3 each.

**Germanium High Power PNP**  
NKT401 90V, 10A max. 815-45 @ 6A, 50W, 17/-. NKT403 80V, 10A max. 850-150 @ 1A, 50W, 16/3. 2N3731 300Vpk, 6A max. 815 min. @ 6A, 5W, 19/6.

**Complementary Matched Pairs**  
2N1304/2N1305 9/-. 2N2926/2N3702, 9/-.  
2N3705/2N3702, 11/2 2N3053/40319, 27/6

**Reduced prices:**  
BC107 45v, 8125-500 7/3.  
BC108 20v, 8125-500 6/3.  
BC109 20v, 8240-900 (low noise) 7/3.  
Resistors 1W 5% carbon film 2/3 doz. 17/3 100.  
Skeleton presets 100  $\Omega$  to 10M  $\Omega$ .  
Horizontal or vertical mounting 1/-.  
Disc ceramics, 50V, 01 5d, 02, 05 6d.  
Cir-Cit, kit including board 15/-.  
Extra sheet, strip, boards available.  
Peak Sound Stereo Amplifier kit £12.19.6.  
Power Supply kit £2.10.0. P. & P. 5/6.  
Discount of 10% on orders over £3.  
Catalogue 6d.

### ELECTROVALUE

6 Mansfield Place, Asco6, Berkshire

## TRANSISTORS AND COMPONENTS

1 OC44 + 2 OC45 + 1 OA81 + 1 OC81D + 2 OC81, 12/6 + 4d. p.p.  
ORP60 Cadmium Sulphide Cells (light sensitive), 5/6 each. ORP12 as above, 7/9.

**SILICON RECTIFIERS (GRADE I)**  
BYZ19 200 P.I.V. 6 amps, 5/4 each.  
BY100 (branded Mullard) 800 P.I.V. 550 m/a, 5/- + 4d. p.p. any quantity 48/- doz.  
BYZ15 (Grade I) 200 P.I.V. 40 amps, £2.1.0 each.  
800 P.I.V. 5 amps, 6/6 each.  
800 P.I.V. 400 m/a, 4/- each + 4d. p.p. any quantity.

**TEXAS TRANSISTORS**  
2N1302=ASY28, 6/6 each. 2G302=GET872, 7/6 each. 2G301=GET873, 6/6 each. 2G339A=AC127, 2/6 each. 2G374=OC75, 2/4 each. 25301 audio, 2/6 each. GM0290A u.h.f. cut of freq. 700 M/c/s, 19/6 each.

**MULLARD TRANSISTORS**  
ASY28, 7/6. AC126, 7/6. OC83, 5/6. OC81D, 3/-. AF115, 4/-. OC45, 3/-. AFY19, 7/6. OC169, 3/-. AF119, 3/-. OC172, 3/-. AF118, 3/-. AF117, 3/-. MAT121, 8/6. MAT101, 8/6. MAT100, 7/9. MAT120, 7/9. OC26, 6/6. AC127, 2/6. OC71, 2/9. ACY22, 3/6. ACY18, 3/6. NKT279A, 3/4. NKT713, 12/6. NKT278, 6/6. NKT773, 10/-. NKT771, 8/-. NKT224, 6/6. NKT275, 6/6. BSY95A S.T.C., 10/6. Denco DTB4 TECM Bull, 2/-. XTAL Ear Piece, 3/6. ECC85 Valves, 4/6 each, 48/- doz.  
1/2 watt Res. grade 1 labgear, 5d. each + 4d. p.p. any quantity.

**J. ROBINSON (RADIO T.V.)**  
4 HIGHCLIFF ROAD  
BLACKLEY  
MANCHESTER 9

## RECEIVERS AND COMPONENTS

(continued)

### SPECIAL OFFER

1 Watt S.T.C. 300 MC/S N.P.N. Silicon Planer. Transistors. With data. Limited Stocks. £1 for 6.

3/- each. OC44, OC45, OC70, OC71, OC81, OC81D, OC200, Get 16, Get 20.

4/- each. AF114, AF115, AF116, AF117, OC170, OC171.

5/- each. OC139, OC140, Get 7, Get 8, Get 9, XCI41, BY100, OA211.

### ZENER DIODES

3.9v. to 26 volt, 1/4w. 3/6 each, 1.5w. 5/-, 7w. 6/- each.

Send 6d. for full lists: Inc. S.C.R. Zeners.

BSY 27, 7/6 each. OC20, 10/- each.

## Cursons


78 Broad Street  
Canterbury  
Kent

## EXPERIMENTER'S PRINTED CIRCUIT CHASSIS KIT

### BUILD 30 TRANSISTORISED PROJECTS

on a printed circuit chassis with parts and transistors from your spare box. Latest very efficient designs for Radios, Amplifiers, Scientific Devices, etc., etc., to suit everyone's needs and interests. The kit comprises 4 assorted PC laminate boards, etchant, resist, solvent, degreaser, 16-page etching manual "Printed Circuits for Amateurs", 2 miniature Radio Dials. Also Essential Design Data, Circuits and Printed Circuit. Chassis Plans for building

### 30 SUGGESTED PROJECTS

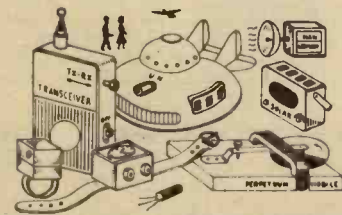

Many recently developed circuits published for the first time including THE SMALLEST 3 RADIOS IN THE WORLD: Ring Radio (70 x .70 x .55in.), Wristwatch Radio (1.15 x .80in.), Postage Stamp Radio (1.6 x .95in.). Recently invented Triple Reflex with self-adjusting regeneration. (Pat. Pen.). Neutralised Double Reflex. Pocket Transceiver (licence required). Solar Loudspeaker Radio. Bacteria Powered Radio. Control of Models by Induction (not Radio). Light-seeking Robot. Guided Missile. Electronic Man/Woman Discriminator. Perpetual Motion Machine. 4 Pocket Transistor Radios. 4 Amplifiers. 2 Intercoms. Burglar Alarm. 4 Unusual Crystal Sets, etc., etc. All designs suit PC boards enclosed. (U.K.) Price of Kit: 8/6. Post and Pack. 1/6. (U.K.) Send S.A.E. for full details and Photographs.

### YORK ELECTRICS

181a, YORK ROAD, LONDON, S.W.11

## RECEIVERS AND COMPONENTS

(continued)

VALVES USED, but guaranteed. Single valves post 7d. 103 Evelyn Road, Dunstable.

EF80	1/3	EZ40	2/6
FL81	3/9	EY86	4/9
PCC84	1/9	PY33	4/9
PCF80	1/9	PCL83	2/9
ECL80	1/3	PCC89	3/-
PLL82	3/9	PCF86	6/3
ECC82	4/-	10F1	1/-
PY82	1/3	30L15	1/9
PY81	1/3	30F5	4/3
		30L1	2/-

33% OFF. BRAND NEW Record Players. All Types. Auto., Valve, Transistor. Transistor Radios. Tape Recorders. Electronic Components. Speakers. Transistor Televisions. Turntables. Amplifiers, Tape. Brand New and Secondhand. 175 Newbury Gardens, Stoneleigh, Surrey. Phone: Ewell 5834.

2N3054 21/-	BC107 7/9	FET.2N3819 25/-
2N3055 22/6	BC108 7/6	FET.2N3820 25/-
2N3702 5/6	BC109 7/6	ALL.2N2926 2/-
2N3704 5/6	ME101 2/6	SCR.2N3525 25/-
ME4001 4/6	ME301 2/6	UJT.TIS43 13/-
ME4002 4/9	OC83 4/6	T.D.IN3716 25/-
ME4003 5/3	N-TYPE ECONOMY FET 14/-	

### MILLTRONICS

1 ULLSWATER ROAD, LEVERSTOCK GREEN  
HEMEL HEMPSTEAD, HERTFORDSHIRE  
C.W.O. Post Free S.A.E. List Mail Order Only

## FOR SALE

SEE MY CAT. for this and that. Tools, materials, mechanical and electrical gear—lots of unusual stuff. This Cat. is free for the asking. K. R. WHISTON (Dept. CPE), New Mills, Stockport

MANUFACTURERS' varied surplus, experimenters send for list. HATFIELD, 7 St. George Bungalow, Hildenborough, Kent.

### A 59/11d COMPUTER FOR FUN?

Not exactly. DIGI-COMP is a model working mechanical digital computer that you programme for binary calculations, logical problems, and games, such as nim. The basic Instruction Manual was written with eleven-year-olds in mind, while the Advanced Booklet analyses all the problems and discusses them in terms of boolean algebra and symbolic logic—then you can write your own programmes for DIGI-COMP.

Send 59/11 (or £3/10/6 to include the Advanced Booklet). to:—

I-COR SYSTEMS (Computer Projects)  
18 Stamford Hill, London, N.16

CRACKLE PAINT. Black or Grey, 1 pint tins 4/-, post 6d. from the component specialists. SERVO RADIO, 156-8 Merton Road, Wimbledon, London, S.W.19.

## HAMMERITE

HAMMER PATTERN BRUSH PAINT FOR PANELS, METALWORK

3/6 TIN • JUST BRUSH ON • WITHSTANDS 150°C, OIL, WATER, Etc.  
21 oz. tins 3/6 1 gallon 35/-  
1 pint 7/6 1 gallon 58/-  
1 pint 15/- (\* sent by road)  
Carriage: Orders up to 5/-, 9d; up to 10/-, 1/9; over 10/-, 3/-. Colours: Blue, Silver, Black or Bronze. Return of post service, Monday to Friday. From your component shop or direct from the manufacturer:

FINNIGAN SPECIALITY PAINTS (PE)  
Mickley Square, Stockfield, Northumberland  
Tel. Stockfield 2280

Exciting new illustrated catalogue, no. 17. Government and manufacturers' surplus electronic equipment. Also a large selection of new miniature components and semiconductors. Ready end of January. Send for your copy NOW. 3/- Post Free. ARTHUR SALLIS, Radio Control Ltd., 93 North Road, Brighton.

## FOR SALE

(continued)

TIME SWITCHES reconditioned 14 day clock once on once off every 24 hours, fully guaranteed, Vener, 15 amp. 37/6, 5 amp. with Horstmann clock, 32/6. P. & P. A. R. BATCHELOR (P.E. Dept.), 4 Park Road, Bromley, Kent.

## ELECTRIC SOLDERING IRON



### FANTASTIC BARGAIN OFFER ONLY

10/-

Lightweight Pistol Grip handle. 40 wats. 240 - 250v. A.C. detachable handle forms cover for iron when not in use. With 4ft. Safety 3-core flex. Indispensable for every home handyman. A boon to model makers and a necessity for every electronics enthusiast. Offered to you at this new amazing price.

C. H. SERVICE (Dept. PE)  
Lusted Hall Lane, Tatsfield, Kent.

FOR SALE. Oscilloscopes — Galvanometers — Evershed & Vignoles Meggers. Also other items and components. Free list. Stamp please. R. & E. MART, Box 9, G.P.O., Tunbridge Wells, Kent.

## MORSE MADE!

The Famous RHYTHM RECORDED COURSE cut the practice time down to an absolute minimum. One student, aged 20, took only 13 DAYS, and another, aged 98, took under a week to read 18 wpm. If you wish to read Morse easily and naturally please enclose 8d. in stamps or two International reply coupons for full explanatory leaflet to: G3CHS/H. 45 Green Lane, Purley, Surrey. UPLands 2896

## BOOKS AND PUBLICATIONS

### SURPLUS HANDBOOKS

19 set Circuit and Notes ..... 4/6 P.P. 6d  
1155 set Circuit and Notes ..... 4/6 P.P. 6d  
H.R.O. Technical Instructions ..... 3/6 P.P. 6d  
38 set Technical Instructions ..... 3/6 P.P. 6d  
46 set Working Instructions ..... 3/6 P.P. 6d  
88 set Technical Instructions ..... 5/- P.P. 6d  
BC. 221 Circuit and Notes ..... 3/6 P.P. 6d  
Wavemeter Class D Tech. Instr. 3/6 P.P. 6d  
18 set Circuit and Notes ..... 3/6 P.P. 6d  
BC.1000 (31 set) Circuit & Notes 3/6 P.P. 6d  
CR.100/B.28 Circuit and Notes 8/6 P.P. 9d  
R.107 Circuit and Notes ..... 5/- P.P. 6d  
A.R.88D. Instruction Manual ..... 15/- P.P. 1/6  
62 set Circuit and Notes ..... 4/6 P.P. 6d  
52 set Sender & Receiver Circuits 6/- post free  
Circuit Diagrams 3/- each post free.  
R.1116/A, R.1224/A, R.1355, R.F. 24, 25, & 26.  
A.1134, T.1154, CR.300, BC.342. BC.312.  
BC.348, J.E.M.P. BC.624. 22 set.  
Resistor colour code indicator, 1/6 P.P. 6d.  
S.A.E. with all enquiries please.  
Postage rates apply to U.K. only.  
Mail order only to:

Instructional Handbook Supplies  
Dept. P.E., Talbot House, 28 Talbot Gardens  
Leeds 8

## WANTED

A COMPLETE SET OF PRACTICAL ELECTRONICS from No. 1 up to and including October 1966 (incomplete sets accepted). Will pay up to £4 and postage. SUTHER, Alban House, Holly Hill Lane, Salisbury, Southampton, Hants.

## CRESCENT RADIO LTD.

ELECTRONIC COMPONENT SPECIALISTS

40 Mayes Rd., Wood Green, N.22

Telephone: BOWES PARK 3206

### TRANSISTORS

OC36 5/- GET/114 1/6d.  
V30/30P 5/- AC/127 1/6d.

### DIODES

OA6 3/6d. OA81 2/6d.  
OA10 4/- OA85 2/6d.  
OA70 2/6d. OA91 2/-  
OA79 2/- OA95 2/6d.

### ZENER DIODES

Ferranti  
KS39/A 7.5 volt 6/-  
KS41/A 9.1 volt 6/-

### SPECIAL LINES

S.C.R. Thyristor, 400 volt, 3 amp. 6/-  
O.R.P.12 10/-  
Electroluminescent Mains Indicator  $\frac{1}{4}$  inch  
fixing. Red, Yellow, Green. 3/9d.  
Single Pole Arrow Toggle Switches 2/- each  
P.U. Cartridge with both Stylis 8/6d. each

### SPEAKERS & TWEETERS

2 $\frac{1}{2}$  inch Tweeter @ 3 ohm. 9/6d. each  
3 inch " @ 8 ohm. 13/6d. each  
2 $\frac{1}{2}$  inch Speaker @ 80 ohm. 5/6d. each  
3 inch " @ 20 ohm. 9/6d. each  
5 inch " @ 3 ohm. 11/6d. each

### PRINTED CIRCUIT BOARDS

9 x 5 in. 1/11d. ea. 12 x 12 in. 3/3d. ea.  
12 x 4 in. 2/- ea. 12 x 6 in. 2/3d. ea.

### VERO BOARD

Vero Pack 5 boards & cutter 9/6d. each  
2 $\frac{1}{2}$  x 5 in. 3/8d. ea. 5 x 3 $\frac{1}{2}$  in. 5/6d. ea.  
2 x 3 $\frac{1}{2}$  in. 3/- ea. 3 $\frac{1}{2}$  x 3 $\frac{1}{2}$  in. 3/8d. ea.  
Vero Pins 1/- per doz.

We have large stock of electronic components and feel that a visit to our premises would be to your advantage. Send 1/- for our catalogue. Please include postage with orders.

**Basic guides for the enthusiast — a new series in question and answer form:**

## Q. & A. ON AUDIO

Clement Brown

104 pages. 80 line diagrams.

## Q. & A. ON ELECTRONICS

Clement Brown

112 pages. 60 line diagrams.

## Q. & A. ON TRANSISTORS

Clement Brown

96 pages. 60 line diagrams.

## Q. & A. ON RADIO AND TELEVISION

H. W. Hellyer

128 pages. 70 line diagrams.

each 8s. 6d.

from booksellers or 9s. 6d. by post from **GEORGE NEWNES, Tower House, Southampton Street, W.C.2**

## SPECIAL OFFERS?

(No... Just normal Bothwell bargains)

**H.F. SIRENS:** Have you found another use for our powerful yet miniature high frequency horns? Already they are being used in burglar and fire alarms, and for all types of equipment where a clear penetrating sound is required. 1.5/4.5V. D.C. only 3/6 each plus 1/- P. & P. per horn.

**AERIAL WIRE:** Pure copper, insulated: still available in 76 ft. reels at excellent price of 5/- plus 1/- P. & P.

### RELAYS:

1. Miniature plug-in with 2 light duty c/o contacts. Coil 185 ohms. 4 $\frac{1}{2}$ /18V. D.C. 15/-.
2. Miniature plug-in with 4 light duty c/o contacts. Coil 130 ohms. 9/15V. D.C. 18/9.
3. Heavy duty car alarm relay 6/12V. D.C. 3 heavy duty c/o contacts. 27/6. P. & P. on above items 1/- each.
4. Base for item (2), 3/9 plus 6d. P. & P.

**LOUDSPEAKERS:** We carry a range of speakers to suit every application. Typical examples are:

1. Westwell 0.2W.; 8 ohm; 2 $\frac{1}{2}$ in. dia., 7/9.
2. Westwell 0.2W.; 8 ohm; 3in. dia., 9/6.
3. Richard Allen 12in., 3 ohm with tweeter, 37/6 plus 3/- P. & P.

**TEST METERS:** ITI-2. A superb buy for the discerning engineer with a limited budget. 20K. ohms/V.: with all the usual desirable features for testing and experimenting. A snip at 69/6 plus 3/- P. & P.

**TEST LEAD KITS:** Complete with plastic case. 6/9 plus 1/3 P. & P.

**RECORD PLAYER AMPLIFIER:** Powerful single valve amplifier (EL84) with metal rectifier. Complete with volume and tone controls. 220/250V. A.C. only 59/6 plus 3/- P. & P. And, of course, all Stclair and Lander products always in stock.

Write or call now for our components list



**BOTHWELL ELECTRIC SUPPLIES** (Glasgow) LTD.  
54 EGLINTON STREET  
GLASGOW, C.5. Tel. 041 800TH 2904  
Member of the Lander Group

**HIGH SPEED MAGNETIC COUNTERS** (4 x 1 x 1in.). 4 digit. 12/24/48V. (state which) 8/6 each, P. & P. 1/-.

**RE-SET H.S. MAGNETIC COUNTERS** (3 x 1 x 2in.), 3 digit. 12/24/48V. (state which) 32/6 each. P. & P. 2/6.

**COPPER LAMINATE BOARD** (8 $\frac{1}{2}$  x 5 $\frac{1}{2}$  x  $\frac{1}{16}$ in.). 2/6 each. 5 for 10/-.

**PRINTED CIRCUIT CONNECTORS**, 13 way 'In-line', Gold Plated Pins. 4/8 Pr. P. & P. 6d.

### BULK COMPONENT OFFERS

- 100 Capacitors (latest types) 50pF to 50pF.
- 250 Carbon Resistors  $\frac{1}{4}$  &  $\frac{1}{2}$ W. (Transistor types).
- 250 Carbon Resistors  $\frac{1}{4}$  & 1W.
- 100 High-Stab Resistors  $\frac{1}{4}$  & 1W.
- 100 Ceramic Capacitors 2—1000 pF.
- 25 Vitreous W/V Resistors (5%).
- 12 Precision Resistors (1%).
- 25 Close Tolerance Caps. (2%).

ANY ITEM 10/- . ANY 5 ITEMS £2.

**SILICON CONTROLLED RECTIFIERS**, CRS 1/30 (380 P.I.V. 1 amp) 7/6 each. CRS 3/40 (460 P.I.V. 3 amp) 10/- each.

**PHOTOFASH ELECTROLYTIC** 2000 $\mu$ F, 276V. 17/6. P. & P. 2/6.

**ELECTROLYTICS** 100 $\mu$ F, 60V. 2/8; 200 $\mu$ F, 250V. 3/8; 100 & 400 $\mu$ F, 275V. 6/8; 500 $\mu$ F, 100V. 4/-; 1000 $\mu$ F, 50V. 5/-; 3000 $\mu$ F, 100V. 7/6; 5000 $\mu$ F, 50V. 7/6. P. & P. 2/6 in. £1.

## PATRICK & KINNIE

81 Park Lane  
Romford, Essex  
ROMford 44473

Please mention

## PRACTICAL ELECTRONICS

when replying to

Advertisements

### TRANSISTORISED AUDIO FREQUENCY SIGNAL GENERATOR

**Frequency:** 15 c/s - 20 kc/s  
Constant in 3 ranges

Amplitude over the whole frequency range

**Output Voltage:** 0-1 volt R.M.S. continuously variable

**PRICE £10. 15. 6 (Complete with Battery)**  
Mail order only. Cash or P.O. with order. Include 5/6 for P. & P. U.K. only.

Comprehensive range of .25 w. Carbon Film Resistors, Miniature Carbon Potentiometers, Silicon Rectifiers.

Please send for technical literature of the above components enclosing 1/- in postage stamps to:

**O. & R. ELECTRONICS LTD.**  
54 MYDDELTON ST., LONDON, E.C.1



Frequency reading direct off the scale

Battery life more than 300 hours

Harmonic distortion less than 1%

### SILICON TRANSISTOR AUDIO PACKS

Set of Fairchild Silicon Transistors and Diodes. Complete with Circuit. AF10 8-10 watts 30/-; AF11 20 watts 78/-.

**HEAT SINKS**—4 $\frac{1}{2}$ " x 3" x 1" or 3 $\frac{1}{2}$ " x 3" x 2" Finned, Alclad Finish, 1-2 Power Transistors. Undrilled 3/9 each. P.P. 6d.

**FAIRCHILD ZENERS** 250MW 15%, 6.9, 9.4, 12.7, 17.2, 23.2, 31 volts. 5/6 each.

**1 P.D.T MIDGET POWER RELAY** (3 Amp) 230 volt A.C. 10/9 each. P.P. 1/-.

S.A.E. for details of Silicon Transistors and Diodes.

All our Products have full maker's Guarantee.

**VIBRAY MOULDINGS LTD.**

3 Kings Road, Slough, Bucks.

Mail Order only



## Masterbox


kits afford the quickest, easiest method of assembling control boxes, indicator panels, small switchboards, etc., using a screwdriver only and in a matter of minutes.

The modular principle of construction of Masterbox is unique—units can be bolted together in any combination to build larger assemblies—can be altered, extended and adapted indefinitely to meet altered requirements.

Masterboxes are ideal for all kinds of experimental work, combining convenience with smartness, strength and adaptability. Write to Cockrobin for details of Masterbox—or send 9d. for full lists.

### COCKROBIN CONTROLS

36 Villiers Avenue, Surbiton, Surrey

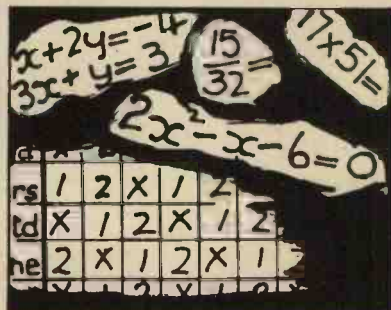

Simple Electrical Analogue circuits to solve the above, 4/6d.

**PLANET INSTRUMENT CO.**  
25 (E), DOMINION AVE., LEEDS 7

**PRE-PAK SEMICONDUCTORS** DISTRIBUTED BY **DAVIS & WHITWORTH LTD.**  
 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
 PHONE: SOUTHDEN (0502) 46344

PRE-PAK FOR QUALITY		PRE-PAK FOR VALUE		PRE-PAK FOR SERVICE	
No.	PRICE	TRANSISTORS	PRICE	TRANSISTORS	PRICE
A1.	6—Silicon rectifiers BY100 type	AC107	6/-	OC81	2/6
A2.	10—Relays, mixed types and voltages	AC126	2/6	OC81D	2/6
A3.	20—Mixed, marked and tested trans.	AC127	2/6	OC83	4/-
A5.	8—Sil. recs. 100-400PIV, 0.5-1A	AC128	3/6	OC139	2/6
A7.	1—500 Mc/s epitaxial mesa, PNP 2N700	AC17	5/-	OC140	5/-
A8.	6—Sub. min. zeners, 3-6-15V, 400mW	AF14	4/-	OC170	2/6
A9.	1—2N174 real power trans. 80v., 150W	AF15	3/-	OC171	4/-
A12.	1—High power, high volts, 2S024, 100V 100W	AF116	3/-	OC200	5/-
A13.	25—Assorted trans. and diodes, all new	AF117	4/-	OC201	8/-
A14.	4—2N601 p/trans. germ. 30V 10Mc/s	AF118	3/6	2G301	2/6
B1.	50—Unmarked, untested, trans. new	AF119	3/6	2G302	2/6
B2.	4—Solar cells, inc. Book of ins.	AF178	10/-	2G344	2/6
B3.	4—OAS gold bonded diodes, Mullard	ASV66	2/-	2G371	2/6
B5.	6—Matched set, OC44/45/810/81	BCZ11	5/-	2G417	2/6
B8.	2—Power trans. OC26/35 type	BF50	15/-	2N697	5/-
B9.	1—Light sensitive cell, ORP12 type	BSY25	10/-	2N706	5/-
B11.	2—Comp. pair, AC128, AC176	BSY26	5/-	2S303	2/6
B13.	7—BA115 G.B. diodes T.V. video	BSY27	5/-	POWER TRANSISTORS	
B15.	8—Bi-directional trans., ASV66	BSY28	5/-	OC20	10/-
B20.	4—Assorted NPN trans., TO-5, TO-18	BSY29	5/-	OC23	10/-
B32.	4—1 amp. recs. 200/300PIV	BSY95A	5/-	OC25	8/-
B33.	10—Germ diodes, assorted types	GET102	2/6	OC26	5/-
B34.	8—Silicon diodes, assorted types	GET114	2/6	OC28	7/6
B35.	2—Zener diodes 11V., 7 and 10 volts	NKT213	2/6	2N601	2/6
B36.	10—Gold bonded, diodes, assorted	NKT252	2/6	DIODES	
B41.	3—2G339A NPN audio, texas	OC41	2/6	OA10	1/6
B42.	5—TK22C germ. switching trans.	OC44	2/6	OA70	2/6
B43.	4—15100 sil. recs. 100 PIV, 2 amp	OC45	2/6	OA79	1/9
B44.	1—Tunnel diode AEY11, 1050Mc/s	OC71	2/6	OA81	1/9
		OC72	2/6	OA182	2/6
		OC73	3/6	IN914	1/6

**THE LARGEST RANGE OF LOW PRICED SILICON CONTROLLED RECTIFIERS (THYRISTORS) IN GT. BRITAIN.**

1 amp PIV	(TO 5 can) each	7 amp (stud) PIV	16 amp (stud) PIV	FREE SCR literature including circuit diagrams for light dimmers, speed controllers, AC power switch, etc., with all SCR orders on request
100	9/6	100	10/6	
400	25/-	200	15/-	
		300	25/-	
		400	30/-	
		500	40/-	
		600	45/-	

**SCR.** Clearance line 25 PIV, 50 amp. ... 30/-

**FIRST EVER LOGIC KITS.** Learn for yourself how computers work, even make one for yourself. Full instructions for a noughts and crosses machine, binary counters, timers, etc. L.1. 5 gns. L.2. 10 gns. No need to purchase both kits, you can start with L.2. which incorporates L.1. DETAILS FREE.

**MAKE A REV. COUNTER FOR YOUR CAR.** THE 'TACHO BLOCK'. This encapsulated block will turn any O-lmA meter into a perfectly linear and accurate rev. counter for any car. State 4 or 6 cylinder. **20/- each**

**NO CONNECTION WITH ANY OTHER FIRM.** MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. For complete lists and substitution charts send 1/- in stamps, add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

## The RADIO AMATEURS HANDBOOK 40/-

1967 Ed. by A.R.R.L. Postage 4/6

World Radio and TV Handbook, 1967 Ed. by Johansen. 33/-.

101 Ways to use your Oscilloscope, by Middleton. 22/-.

Electronic Motor Control, by Lytel. 31/3.

Transistor Circuit Manual, by Lytel. 36/3.

Transistor Specification and Substitution Handbook, by Techpress. 22/6.

Rapid Servicing of Transistor Equipment, by King. 31/3.

Circuits for Audio and Tape Recording, by Judd. 8/3.

Q. and A. on Electronics, by Brown. 9/3.

Building and Using Sound Mixers, by Steele. 31/-.

Transistor Pocket Book, by Hibberd. 26/3.

All prices include U.K. postage  
 Where possible 24-hour service guaranteed

## UNIVERSAL BOOK CO.

12 LITTLE NEWPORT ST., LONDON, W.C.2  
 (Leicester Square Tube Station)

## ELECTRONICS GALORE!

### IN THE NEW dca CATALOGUE

THE CONVENIENT WAY TO SHOP FOR ALL YOUR ELECTRONIC NEEDS.

EVERYTHING FROM SINGLE COMPONENTS TO COMPLETE EQUIPMENT ALL AT BEST VALUE PRICES.

SEND 1/6d. NOW FOR YOUR COPY TO:—Dept. PE/4

### dca ELECTRONICS LIMITED

28 UXBRIDGE ROAD, EALING, W.5

### BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 9v; 7.5v; 6v; 4.5v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4.5v + 4.5v (two separate outputs) 42/6 each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.  
 (Dept. P.E.), 11 Oliver Road, London, E.17

## 4-STATION INTERCOM



£6/9/6

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Businesses, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 6/6.

### INTERCOM/BABY ALARM

Usually ~~£6/9/6~~  
 Our Price ONLY **49/6**



Modernize business or home with this new two-way Portable Transistor Intercom, consisting of Master and Sub, in strong plastic cabinets with chromium stands. Designed as a two-way instant communication system. Call/talk/listen from Master to Sub and Sub to Master. Operates on one 9V battery. Complete with 60 ft. wire and battery. P. & P. 2/6

### Telephone Amplifier 55/-



Why not boost business efficiency with this incredible De-luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A status symbol? Yes, but very useful one. On/off switch. Volume Control. Operates on one 9V. battery supplied for 2/6 extra. P. & P. 2/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/4)  
 169 KENSINGTON HIGH STREET, LONDON, W.8.

# "X"-LINE

MODULES  
YOU CAN OPEN

Now for the first time, solid state semiconductor modules which you can open. OPEN, to see the high grade components used, OPEN, and modify to your exact requirements, OPEN, to service if needed; (but X-Line has reliability built in right from the design stage). If you would like more information send us a stamped addressed envelope — Trade enquiries welcomed. Phone Brentwood 7904.

X — 161	General purpose amplifier — 2 watts	35/-
X — 191	Guitar amplifier (contact microphone) 2 watts	35/-
X — 141	Record player amplifier — 2 watts	35/-
X — 181	Intercom. Use with 2 speakers and DPDT switch	35/-
X — 481	Audio Booster. Buck up your transistor radio	30/-
X — 461	Siren. Upward wailing tone, train sirens, etc.	35/-
X — 471	Burglar alarm. Will wake the soundest sleeper	35/-
X — 661	Metronome. Adjustable 30-240 beats per min.	30/-
X — 761	Morse code practice oscillator	20/-
X — 671	Single high power lamp flasher	32/6
X — 691	Double lamp flasher. Displays, warnings, etc.	30/-

AND: NEVER BEFORE IN THIS COUNTRY:

X — 261	FM microphone transmitter	} 35/-
X — 271	FM telephone transmitter	
X — 241	FM record player transmitter	
X — 291	FM Guitar transmitter	
X — 371	FM Wireless entry	

## FIRST GRADE SEMICONDUCTORS — FULLY GUARANTEED

AC128	4/-	NKT121	9/-	NKT271	3/6	OC83	4/-	2N2926	4/-	OC71	10/6
AC118	7/6	NKT122	6/5	NKT272	3/6	OC123	17/8	2N3707	7/10	equiv.	9/8
AC120	5/8	NKT123	5/8	NKT273	3/6	OC170	4/-	ORP12	9/8	CR74	27/6
AD161	7/8	NKT124	8/5	NKT274	3/6	OC171	7/8				
AD162	7/8	NKT125	6/5	NKT275	3/6	OC205	10/8				
ADT140		NKT141	6/-	NKT678	4/4	X4702	6/-				
	15/-	NKT142	5/1	NKT713	6/6	ZT402	25/5				
AF102	18/-	NKT143	5/-	NKT773	5/-	2N697	12/-				
AF110	4/-	NKT162	5/-	NKT774	5/-	2N706	5/-				
AF116	4/-	NKT212	4/7	OC28	15/-	2N1132	19/6				
AF117	4/-	NKT216	8/8	OC29	19/-	2N1302	5/5				
BC107	7/8	NKT217	8/-	OC38	12/8	2N1303	5/5				
BC108	7/8	NKT218	4/4	OC41	3/8	2N1304	6/8				
BC211	18/8	NKT221	5/-	OC44	3/-	2N1305	6/8				
BFY25	22/-	NKT227	8/8	OC45	3/-	2N2646	14/8				
BFY26	7/-	NKT228	4/4	OC71	4/-	2N3819	29/8				
BFY61	9/8	NKT361	3/8	OC72	4/8	2N3820	29/8				
BUY11	89/8	NKT382	3/8	OC73	2/9	1B40K10					
GET105	4/8	NKT317	8/-	OC76	3/-						
NKT0013		NKT364	3/8	OC81	2/8						
	12/-	NKT268	3/6	OC81D	3/-	2N2147	20/8				

## BARGAIN PARCELS:

OC76, OC81D, OC81, OC73	any 4 for 10/-
Output set OC81D + 2 OC81	for 7/-
RF set OC44 + 2 OC45	for 8/6
High Current OC83	4 for 10/-
BY100 Mullard Rectifiers	6 for 8/-

Special bargain:  
Transistors  
60 unmarked/untested  
10/-

# L.S.T. 23 NEW ROAD, BRENTWOOD, ESSEX COMPONENTS

Callers welcome  
Postage & Packing 9d.

YOU CAN AFFORD! AN INDIVIDUALLY MANUFACTURED

# ENGRAVED FACIA PANEL

WE OFFER A COMPLETELY NEW SERVICE TO ELECTRONIC ENTHUSIASTS WHO WISH TO MAKE THEIR APPARATUS INDISTINGUISHABLE FROM THE MOST EXPENSIVE PROFESSIONALLY MADE EQUIPMENT.

FOR FREE QUOTATION AND FURTHER INFORMATION SEND S.A.E. AND WORKING DRAWING OF APERTURES AND WORDING REQUIRED TO:—

GREYMEL LTD., 34 PANCRAS RD., LONDON, N.W.1

# RAPID SERVICING OF TRANSISTOR EQUIPMENT

By GORDON J. KING

Directed to the service technician changing from valves to transistors, students starting a career in electronics, and the enthusiastic amateur, it describes semiconductors and transistors, their operating principles and circuitry, together with basic test procedures, and then concentrates on fault diagnosis in the various fundamental types of circuit—audio and video amplifiers, R.F. circuits and oscillators—each section concluding with a Fault Diagnosis Summary Chart. Chapters are devoted to the ordinary transistor portable receiver and practical advice on repair procedures.

160 pages, 90 line and half-tone illustrations. 30s.

FROM ALL BOOKSELLERS

or in case of difficulty, 32s. by post from:

NEWNES Tower House, Southampton St., W.C.2

## NEW RANGE U.H.F. AERIALS FOR BBC 2 (625) line transmissions

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays. 7 element, 35/-; 11 element, 42/6; 14 element, 50/-; 18 element, 57/6. Wall Mounting with Cranked Arm. 7 element, 60/-; 11 element, 67/-; 14 element, 75/-; 18 element, 82/6. Mast Mounting with 2in. clamp. 7 element, 42/6; 11 element, 55/-; 14 element, 62/-; 18 element, 70/-; Chimney Mounting. Arrays. Complete. 7 element, 72/6; 11 element, 80/-; 14 element, 87/6; 18 element, 95/- . Complete assembly instructions with every unit. Low Loss Cable. 1/6 yd. U.H.F. Pre-amps from 75/- . State clearly channel number required on all orders.

## BBC · ITV · F.M. AERIALS



BBC (Band 1). Telescopic mast, 31/- . External S/D, 30/- . "H", £2.10.0.

ITV (Band 3). 3 element loft array, 25/- . 5 element, 35/- . Wall mounting, 3 element, 35/- . 5 element, 45/- .

Combined BBC/ITV. Loft 1+3, 41/3; 1+5, 48/9; Wall mounting 1+3, 56/3; 1+5, 63/9; Chimney 1+3, 63/9; 1+5, 71/3.

VHF transistor Pre-amps from 75/- .

F.M. (Band 2). Loft S/D, 12/6, "H", 30/- . 3 element, 52/6. External units available. Co-ax. cable, 8d. yd. Co-ax. plugs, 1/3. Outlet boxes, 4/6. Diplexer Crossover Boxes, 12/6. C.W.O. or C.O.D. P. & P. 5/- . Send 6d. stamps for illustrated lists. Quotations for special arrays available on request

## K.V.A. ELECTRONICS (Dept. P.E.)

27 Central Parade, New Addington  
Surrey—CRO-OJB  
LODGE HILL 2266

## GOING SUBMIN?

We hate fiddling about with  $\frac{1}{2}$  watt resistors. So when we made our prototype Sensitive TRF we used nice big  $\frac{1}{2}$  watt ones, and 12v. electrolytics instead of 3v. But if you do like that sort of thing, you'll find that our circuit lends itself. Two r.f. stages, high-gain detector, and output stage for phones or high impedance speaker. Works from 3v., 3mA. And it's so simple. Tuning components, five fixed resistors, one volume control, two electrolytics, two paper. A child of two could build it (with 10 years' practice). We don't sell the components, only the transistors. All silicon, brand new, first grade. Complete set, 11/-. The circuit is free with the transistors but cautious types can get one in advance: 3d. stamp, please.

Silicon Transistors. ME101, ME301, 2/-; 2N2926 from 3/6; 2N3702, 5/-; 2N3704, 6/-; 2N3705, 5/-; 2N3707, 6/-; T1407, 6/-; BC107, 6/-; BC109, 6/-; B-3000 (25w.), 10/-.

C.W.O. Mail order only. No C.O.D.

AMATRONIX LTD., 396 Selsdon Road  
Croydon CR2 0DE

Please mention

## PRACTICAL ELECTRONICS

when replying to

Advertisements

## TELECOM Mk. II

portable V.H.F.  
118-136 Mc/s

## AIRCRAFT-BAND TRANSISTOR RECEIVER

with R.F. stage, telescopic aerial, internal loudspeaker and battery.

£23. 10. 0d.

carr. paid in U.K.

## BRITEC LIMITED

17 Charing Cross Road  
LONDON, W.C.2  
Tel. 01-930 3070



## Laboratory Components

Resistors. 1W, 10% High Stab. Class 1. Low Noise 3/- per Doz.

Capacitors. Min. Electrolytics, Ass or Single value 9/- per Doz. Polystyrene sub-min. 25V. 10% Ass. 8/- per Doz.

Transistors. Matched Output Kit, OC81D + 2 x OC81 7/8 per set Germanium, Ass, PNF, NFN AF Types 10/6 per doz. Germanium, Low Leakage, RF Types 12/- per doz. Type 1020, PNP, Germanium, AF, 50mW 8/- per Doz. Type 1021, PNP, Germanium, AF, 200mW 12/6 per Doz. Type 1024, PNP, Low Leakage, RF, 17/8 per Doz. 4mc/s Type OC44, OC45, OC70, OC71, ACY22, OC81D 2/3 each

Power Transistors. (OC26 7/8) (OC25 8/8) (OC36 10/-)

For complete list of Laboratory Components send S.A.E. to:

LABORATORY EQUIPMENT (ELEC)  
38 Crawford St., London, W-1

All goods C.W.O. and P.P. 1/6



# No.1 Just Out!

A NEW MAGAZINE FOR  
EVERY HOME HANDYMAN



No.1 OF THE *NEW* HOW-TO-DO-IT MAGAZINE  
**PRACTICAL** MARCH 1967  
**Decorating & Building**  
PRICE 2/6

**FREE!**  
QUANTITY  
CALCULATOR  
for Glass,  
Cement, Paint  
and Wallpaper.

**EXTRA!**  
8-Page  
Supplement  
**ALL ABOUT  
CEMENT AND  
CONCRETE**

**EXTRA!**  
Fold-out Data  
Sheet on  
**FITTING WINDOWS**



Backed by the full resources of Newnes famous 'Practical' group, PRACTICAL DECORATING AND BUILDING has been planned to bring every type of decorating and building job, however extensive or difficult, within the scope of the home handyman. Month by month it will include clear how-to-do-it instructions on a wide range of projects indoors and out . . . all about the latest techniques, ideas tools and materials . . . and expert guidance on a hundred and one aspects of modern home improvement that will save you pounds on every job. In short, it's a must for every handyman. Go for No. 1, now!

**Packed with new ideas  
and detailed know-how on  
major home improvements**



**Hurry - Make  
sure of your  
copy NOW! 2/6**




(14)



(12)



(13)

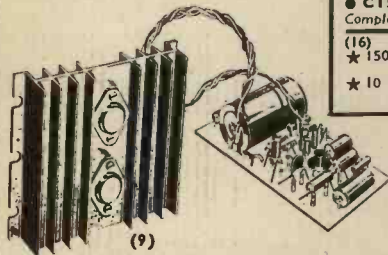

(15)

**HENRY'S RADIO LTD.**  
303 EDGWARE RD., LONDON, W.2  
PADDINGTON 1008/9 (STD: 01-723 1008)  
Open Mon. to Sat. 9-6. Thurs. 1 p.m.  
Open all day Saturday

**SEE BACK COVER FOR MORE ITEMS OF INTEREST**

**12 AND 20 WATT MONO AND STEREO TRANSISTOR AMPLIFIERS**

(9) **POWER AMPLIFIERS.** 12 watts RMS output. 100mV input. 30 c/s to 20 k/c/s  $\pm$  1dB. 6-Transistor. Push-pull. Panel size 4 X 2 1/2 X 1 in. H/5 4 X 4 in. Leaflet on request.  
MPA10/3 3.5 ohm spkr. £4.10.0, p.p. 2/6.  
MPA10/15 8-16 ohm spkr. £5.5.0, p.p. 2/6  
(Mains unit 1 or 2 amplifiers, 59/6, p.p. 2/6)

**The Finest High Fidelity at Unbeatable Prices**

**25 WATT AMPLIFIER**  
8-Transistor design. Push-pull output for 7 1/2 to 16 ohm speaker. 150mV input. 30c/s to 20k/c/s  $\pm$  1dB. For use with valve or transistor pre-amplifiers as item (10) above.  
**PRICE BUILT AND TESTED £7.19.6 P.P. 3/-**  
(Mains unit 79/6, p.p. 2/6)

(13) **MULTI-METERS SCOPE**  
PT34 1kv 39/6 EP30k 30kV £9.10.0  
TP10 2kV 75/- EP50k 50kV £9.19.6  
ITI-2 20kV 69/6 500 30kV £8.17.6  
TP55 20kV £5.19.6 EPI00k 100kV £10.10.0  
● CT52 Scopes £22.10.0, p.p. 10/-  
Complete range of test equipment in stock

(16) **NOMBREX TEST UNITS**  
★ 150 kc/s—350 mc/s RF Generator £10.10.0. All Transistor.  
★ 10 c/s—100 kc/s Transistor. £16.19.6 Audio Generator.

**(15) GARRARD BATTERY 2-SPEED TAPE DECK**

Brand New with R/P head, erase/osc. head, tape cassette. Specifications and osc. circuits. 2 speed 2-track 9 volt operated. List Price 13 gns.  
**PRICE £8.19.6 P. & P. 3/6**

**COMPONENTS AND EQUIPMENT.** The largest range in the country. 8/6 buys 1967 200-page catalogue with discount vouchers.

(10) **PREAMPLIFIERS.** 8 input selector. Treble, bass, volume, filter controls. 1 1/2 mV to 100mV inputs. Battery operated or from Mains Unit. Output up to 150mV. LEAFLETS ON REQUEST.

MP2 Mono 9 1/2 X 2 1/2 X 2 in. £5.10.0, p.p. 2/6 (grey and gold front panel 8/6).  
SP4 Mono/Stereo. 9 X 3 1/2 X 1 1/2 in. £10.19.6, p.p. 3/6 (front panel plate 12/6)  
● ALL UNITS BUILT AND TESTED

**(12) MW/LW QUALITY TRANSISTOR RADIO TUNER**

Fully tunable superhet with excellent sensitivity and selectivity. Output up to 1/2 volt peak. Complete with front panel, etc. 9 volt operated. For use with any amplifier or tape recorder.  
**TOTAL COST TO BUILD £3.19.6 P.P. 2/6**

**(14) VHF FM TUNER**

Supplied as 2 Preamplified Panels, plus metal work Superhet design, 88-108 Mc/s, 9 volt operated. 6 Mullard Transistors  
Total cost to assemble £12.17.6, p.p. 2/6

**STABILISED POWER SUPPLY**

Two outputs. 3.6 volt and 9.6 volt up to 250mA each. Transistorised and Zener stabilised. 110 to 250 volt mains input. In case with leads. **PRICE 67/6, p.p. 2/6.**

**(17) 5 WATT AMPLIFIER**

6-Transistor Push-pull, 3 ohms. 6mV into 1K. 12/18V supply. 2 1/2 X 2 X 1 1/2 in.  
**BUILT AND TESTED 69/6 P.P. 2/-**  
(optional mains units 54/-)  
1 1/2 watt version 59/6.  
Matching Preamplifier, 6 inputs, treble/bass selector/volume controls. 6-10mV o/p ut. 9-18V supply. 79/6, p.p. 2/-.  
For use with any Transistor Amplifier  
LEAFLET ON REQUEST.

**FMT41 FM TUNER.** 6-transistor, 3 diode design. Completely built and tested

£8.10.0 P.P. 2/-  
(19) AMT31, Med. Wave Tuner. Built ready to use. 79/6, p.p. 2/-.



(16)



(17)



(13)



(15)

**MAKE 5 DIFFERENT RADIOS FOR 39/6**  
Amazing Radio Construction Set! Become a radio expert for 39/6. A complete Home Radio Course. No experience needed. Parts including Instructions for each design. Step-by-Step plan, all Transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Box size 14" X 10" X 2" (parts available separately). Originally £8. NOW 39/6 plus 4/6 P. & P.

**PERSONAL TRANSCIVER SETS Our Price £5.19.6**  
You've heard about them—you've read about them. NOW YOUR CHANCE TO OWN THEM. Highly sensitive two-way transistor transceiver sets have individual volume control and talk-listen switch. Telescope aerial puts in the voice from the other set over tremendous distances—no wires—a genuine transceiver as used by official bodies and forces. 500 sets only. These cannot be used in U.K.

**UNIQUE NEW PORTABLE RADIO FULLY TRANSISTORISED READY BUILT**  
with Full Variable waveband. NOW A FRACTION OF THE NORMAL PRICE **29/6 WHY PAY MORE?**  
All the latest refinements are packed into this new MULTI-STATION All Transistor radio—the internal aerial picks up even the remote stations and the powerful built-in speaker gives room filling volume. Individual tuning, first-class reception. Purchase with confidence—packed in original manufacturer's cartons. (Personal earpiece and battery 4/6). Send 29/6 plus 4/6 p. & p.

**AMAZING No soldering CIGARETTE RADIO ONLY 25/-**  
Yes, a perfectly ordinary packet of cigarettes! But watch your friends astonishment on hearing six ranges of stations loud and clear. Holds 10 cigarettes—yet conceals sensitive, fully transistorised circuit (including tiny battery). A young boy can assemble it in 2 hours. No soldering. Only 16 connections to make. ALL PARTS including semi-conductors, ABC Plans, etc. ONLY 25/- plus 2/6 P. & P. Parts available separately.

**CONCORD ELECTRONICS LIMITED (Dept. P.E. 30) 77 NEW BOND STREET LONDON, W.1**

**TECHNICAL TRADING Co.**  
All items previously advertised available, also see items advertised in Practical Wireless. Huge Hi-Fi and Components stocks at all branches.

**ROBOPHONE ORDERS**  
Your C.O.D. order exceeding £1 can be telephoned to BRIGHTON 680722 at any time day and night

**JASON TAPE** Top British nylon/P.V.C.

Standard Play		Double Play	
3"	160ft. 2/3	3"	300ft. 4/-
4"	300ft. 4/8	4"	600ft. 8/-
5"	600ft. 7/6	5"	1200ft. 15/-
6"	900ft. 10/6	6"	1800ft. 19/6
7"	1200ft. 13/6	7"	2400ft. 27/-
Long Play		Triple Play	
3"	225ft. 2/9	4"	900ft. 13/-
4"	450ft. 5/8	5"	1800ft. 25/-
5"	900ft. 10/8	6"	2400ft. 34/-
6"	1200ft. 13/-	7"	3600ft. 44/-
7"	1800ft. 18/6		

Post 1/-      Quadruple Play 600ft. 8/-

10 TOTTENHAM COURT RD., LONDON, W.1 . Tel.: MUS 2639  
350/352 FRATTON RD., PORTSMOUTH. Tel: 22034  
72 EAST STREET, SOUTHAMPTON. Tel: 25851  
132 MONTAGUE STREET, WORTHING. TEL: 2585  
ALL MAIL ORDER AND RETAIL SHOP  
**PARK CRESCENT PLACE, BRIGHTON**

**YUKAN SO PROFESSIONAL THE YUKAN SELF-SPRAY AEROSOL WAY —**  
Get these **AIR DRYING GREY HAMMER** or **BLACK WRINKLE (CRACKLE)** Finishes

Yukan Aerosol spraykit contains 16 ozs. fine quality durable easy instant spray. No stove baking required. Hammers available in grey, blue, gold, bronze. Modern Eggshell Black Wrinkle (Crackle) all at 14/1 at our counter or 15/11, carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (12 ozs. self-spray cans only) 13/11 carriage paid.  
**SPECIAL OFFER:** I can plus optional transferable snap-on trigger handle (value 5/-) for 18/11, carriage paid. Choice of 13 selfspray plain colours and primer (Motor car quality) also available.

Other Yukan Air Drying Aerosols include:  
Zinc Chromate Primer.  
Clear Lacquer.  
Anti-Tarnish Gold and Metallic Finishes.

Please enclose cheque or P.O. for total amount to: YUKAN, Dept. PE/4 307a Edgware Rd., London W.2.  
Open all day Saturday. Closed Thursday afternoons.

# VALUABLE NEW HANDBOOK FREE TO AMBITIOUS ENGINEERS

Have you had your copy of "Engineering Opportunities"?

The new edition of "ENGINEERING OPPORTUNITIES" is now available—without charge—to all who are anxious for a worthwhile post in Engineering. Frank, informative and completely up to date, the new "ENGINEERING OPPORTUNITIES" should be in the hands of every person engaged in any branch of the Engineering industry, irrespective of age, experience or training.

## On 'SATISFACTION OR REFUND OF FEE' terms

This remarkable book gives details of examinations and courses in every branch of Engineering, Building, etc., outlines the openings available and describes our Special Appointments Department.

## WHICH OF THESE IS YOUR PET SUBJECT?

### ELECTRONIC ENG.

Advanced Electronic Eng.—  
Gen. Electronic Eng.—Applied  
Electronics—Practical  
Electronics—Radar Tech.—  
Frequency Modulation—  
Transistors.

### ELECTRICAL ENG.

Advanced Electrical Eng.—  
General Electrical Eng.—  
Installations—Draughtsmanship—  
Illuminating Eng.—  
Refrigeration—Elem. Elec.  
Science—Elec. Supply—  
Mining Elec. Eng.

### CIVIL ENG.

Advanced Civil Eng.—  
General Civil Eng.—Municipal  
Eng.—Structural Eng.—  
Sanitary Eng.—Road Eng.—  
Hydraulics—Mining—  
Water Supply—Petrol Tech.

WE HAVE A WIDE RANGE OF COURSES IN OTHER SUBJECTS INCLUDING CHEMICAL ENG., AERO ENG., MANAGEMENT, INSTRUMENT TECHNOLOGY, WORKS STUDY, MATHEMATICS, ETC.

Which qualification would increase your earning power?  
A.M.I.E.R.E., A.M.I.Mech.E., A.M.S.E., A.M.I.C.E., B.Sc.,  
A.M.I.P.E., A.M.I.M.I., A.R.I.B.A., A.I.O.B., A.M.I.Chem.E., A.R.I.C.S.,  
M.R.S.H., A.M.I.E.D., A.M.I.Mun.E., C.ENG., CITY & GUILDS, GEN.  
CERT. OF EDUCATION, ETC.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE

## THIS BOOK TELLS YOU

- ★ HOW to get a better paid, more interesting job.
- ★ HOW to qualify for rapid promotion.
- ★ HOW to put some letters after your name and become a key man . . . quickly and easily.
- ★ HOW to benefit from our free Advisory and Appointments Depts.
- ★ HOW you can take advantage of the chances you are now missing.
- ★ HOW, irrespective of your age, education or experience, YOU can succeed in any branch of Engineering.

132 PAGES OF EXPERT CAREER - GUIDANCE

### PRACTICAL EQUIPMENT

Basic Practical and Theoretical Courses for beginners in Radio, T.V., Electronics, Etc., A.M.I.E.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio and Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment Ask for details.

## B.I.E.T.

You are bound to benefit from reading "ENGINEERING OPPORTUNITIES"—send for your copy now—FREE and without obligation.

## POST NOW!

TO B.I.E.T., 316A ALDERMASTON COURT, ALDERMASTON, BERKSHIRE.

3d. stamp if posted in an unsealed envelope.

Please send me a FREE copy of "ENGINEERING OPPORTUNITIES." I am interested in (state subject, exam., or career).

NAME .....

ADDRESS .....

WRITE IF YOU PREFER NOT TO CUT THIS PAGE



**THE B.I.E.T. IS THE LEADING INSTITUTE OF ITS KIND IN THE WORLD**



# 1967 CATALOGUE 200 PAGES PLUS!


COMPLETELY NEW EDITION — HUNDREDS OF NEW LINES

● Contains the largest and most comprehensive range of components and equipment available. Over 5,000 stock lines with more data more stock lines. Information and illustrations. Hundreds of bargain lines. You cannot afford to be without a copy of this catalogue. Supercedes all previous editions. Price 7/6, p.p. 1/-.

● 5 FREE VOUCHERS  
Total value 10/- for use on purchases. Pays for catalogue after use.



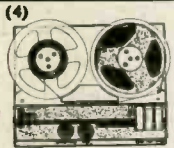● Unbeatable value — 200 packed pages — 10/- value discount vouchers ●



**MARRIOT TAPE HEADS**  
1 Track R/PP/3 Med z, 7/8. R/PP/1 High x, 8/9. R/PP/1 High z + R/E/1 erase on block, 19/6. 1 Track L/RP8/12 High z, 15/-, L/RP8/7 Med z, 19/6. L/ES/9 erase, 12/6. Also HR-RP single track Rec/Play Med z, 6/8

**DEAC RECHARGEABLE BATTERY**  
● 9.6 volt 225mA/H 20/-, P.P. 1/6

**DEAC CHARGER**

To charge 3.6 volt and 9.6 volt packs. Fully mains isolated. In moulded case. **45/-** P.P.

(4) **BUILD A QUALITY 2 OR 4 TRACK TAPE RECORDER**

3-speed version using '363' decks  
● TWO-TRACK. Deck £10.10.0. Martin Amplifier. £14.19.6. Cabinet and speaker 7 zns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **27 gns.** P.P. 15/- Today's Value £45.

● FOUR-TRACK. Deck £13.10.0. Martin Amplifier £15.19.8. Cabinet and speaker 7 zns. Complete kits with FREE 7in. 1200ft. tape, spare spool. **30 gns.** P.P. 15/- Today's Value £50.

(6) **GARRARD DECKS — BRAND NEW FULLY GUARANTEED**

1000 mono	£5 19 6	SP25 stereo	£10 19 6	401 less cart./arm	£27 10 0
AT5 mono	£6 9 6	SP25 Deram	£13 19 6	AT6 mono Mk. II	£8 18 6
2000 mono	£6 9 6	AT60 less cart.	£10 18 6	AT6 stereo Mk. II	£9 10 0
2000 stereo	£6 19 6	AT60 mono	£11 10 0	AT6 Deram	£11 19 0
3000 1 in stereo	£7 19 6	AT60 stereo	£11 19 6	Decadeck Mk. II	£17 17 0
SP25 less cart.	£9 19 6	AT60 Deram	£14 19 6	A70 less cart.	£17 17 0
SP25 mono	£10 10 0	LAB80 less cart.	£25 0 0		

All other makes of decks and cartridge in stock

(7) **GLOBEMASTER MW/LW/SW PORTABLE RADIO TO BUILD**

Full 3-waveband tuning. Push-button wave-change. Superhet printed circuit design. Black-chromed cabinet 11 x 7 1/2 x 3 1/2 in. (SW 17-50 metres). Ear/Record sockets. 1 watt Push/Pull output. 6 Mullard Transistors. Handbook **TOTAL COST £7.19.6** P.P. on request **TO BUILD** 3/6

(8) **TOURMASTER TRANSISTOR CAR RADIO**

7-Transistor MW/LW Car Radio. 12 volt operated. 3 watt output. Push-button wave-change. RF stage. Supplied built, boxed, ready to use with Speaker and Battery. Car fixing kit and manufacturers' current guarantee. Special Bargain Offer. Buy Now! **LIST PRICE 15 GNS. £9.90** P.P. 3/6

**CAR MONO/STEREO AND MONO TAPE PLAYERS—TERRIFIC QUALITY**

12 volt pos. or neg. earth operated. Uses Musicassettes. Either your own recordings or EMI/Philips prerecorded tapes. Fits any car. Full range of controls bass/treble/volume. Provides 50 mins. from one tape. Supplied complete with speakers, fixing kit, instructions and 50 min. prerecorded tape.

Prices. Mono **26 gns.** Mono/Stereo **32 gns.** Leaflet on request. British Made.

**SUPPLIERS OF QUALITY COMPONENTS AND EQUIPMENT FOR MORE THAN 20 YEARS**

**RADIO CONTROL RECEIVER**

"TINYTONE" 27 mc/s band receiver. Printed circuit construction. Sensitive 4-transistor design. Size only 2" x 2" x 1". Complete with circuit and instructions. **TOTAL COST** P.P. **TO BUILD 55/-** 1/6 (Circuit etc. 1/3 separately).

**TUNNEL DIODES**

1mA 22/8; 5mA 15/-; 15mA 12/6. Brand new at fraction of normal price. Free Specs. supplied.

**TRANSISTOR CATALOGUE**

Completely new 24-page 1967 edition. Hundreds of new types with details. The largest range available with data, information, illustrations, etc. Send 1/- for your copy.

**INVERTOR KITS**

12 volt input. Output 230 volts, 50 c/w. ● 16 watt ... 67/8. P.P. 3/6 ● 40 watt ... 97/8. P.P. 6/6

(1) **REGENT-6 MW/LW POCKET RADIO TO BUILD**

6-Transistor superhet. Geared tuning. Push-pull speaker output. Moulded cabinet 5 x 3 x 1 1/2 ins. Phone socket. **TOTAL COST** P.P. **TO BUILD 69/6** 2/- Full tuning on both bands

**HI-FI EQUIPMENT** from stock: **ARMSTRONG QUAD** THORENS requirements for **GOODMANS** special price quote. **WHARFEDALE** Hi-fi demonstration **CELESTION** room open. **GOLDRING ROGERS, TRUVOX, LEAK ETC.**

**WE CAN SUPPLY FROM STOCK MOST OF THE PARTS SPECIFIED ON CIRCUITS IN THIS MAGAZINE. SEND LIST FOR QUOTATION.**

**OR BETTER STILL — BUY THE NEW 1967 CATALOGUE. EVERYTHING YOU NEED IS AVAILABLE FROM STOCK.**

**HENRY'S RADIO LTD.**

303 EDGWARE RD., LONDON, W.2  
PA Ddington 1008/9 (MTD 01-723 1008)  
Open Mon. to Sat. 9-6. Thurs. 1 p.m.  
Open all day Saturday

## ★ MAYFAIR PORTABLE ELECTRONIC ORGAN—

**Build the World's first All-Transistor Portable Electronic Organ Kit**

● Plug-in printed circuits ● 170 transistors and devices ● 10 selected tone colours ● Fully sprung keyboard ● Vibrato ● 6 Octaves of generators ● Simple locked-in tuning ● 110/250 volt mains unit ● Cabinet size 30 1/2" x 15 1/2" x 9" ● Weight 35 lb. Cabinet with detachable legs, music stand and foot swell pedal ● Fully detailed building manual with photos, drawings and full circuits.

Designed by L. W. Roche



**ORGAN COMPONENTS FROM STOCK**

- ★ Gold clad wire and Rhodium bars
- ★ Chokes
- ★ Panels
- ★ Pedal Boards
- ★ Amplifiers
- ★ Reverberation Equipment
- ★ Stop Units
- ★ Key Boards
- ★ Pedal Switches
- ★ Expression Pedals
- ★ Relay Units
- ★ Coupler Switches
- ★ Etc. etc.

**LIST ON REQUEST**

**START BUILDING FOR AS LITTLE AS £5—BUILD THE MAYFAIR A SECTION AT A TIME**

**TO BUILD YOURSELF IN EASY STAGES ALL PARTS AVAILABLE SEPARATELY**

- ★ COMPLETE KIT 99 gns. (Carr. 30/-).
- ★ DETAILED LEAFLET ON REQUEST
- ★ HP FACILITIES AVAILABLE.
- ★ COMPLETE RANGE OF ORGAN COMPONENTS IN STOCK.

**REVERBERATION**  
Transistorised mains operated unit for use with any organ or audio equipment. 18 GNS.

See page 320 for more stock items

Britain's best selling Hi-Fi transistorised 5, 12 and 25 watt amplifiers and preamplifiers—AM and FM Tuners—New catalogue is a must—Order Yours NOW!

● SEE FOR YOURSELF CALL IN FOR DEMONSTRATION

**NEW!** VHF FM plus MW and Longwave Car Radio. 3 watts O/P. Pos. or neg. earth 12 volt. British Made. Complete with speaker, etc. **25 gns.**