

PRACTICAL

# ELECTRONICS

FEBRUARY 1971

3/6 (17½ NEW PENCE)



## TAPE / SLIDE SYNCHRONISER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64 for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.


### \*Additional Stock Bits (illustrated) available

#### COPPER

- B 38**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 24**  $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE
- B 12**  $\frac{1}{16}$ " — 4.75 mm EYELET BIT
- B 58**  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE
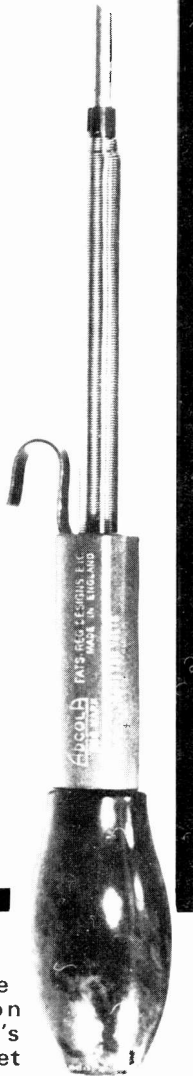
#### LONG LIFE

- B 42 LL**  $\frac{1}{16}$ " — 4.75 mm CHISEL FACE
- B 38 LL**  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE
- B 14 LL**  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE
- B 44 LL**  $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\* Write for price list and catalogue



**ADCOLA PRODUCTS LTD.,**  
(Dept. L), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

## EX RENTAL TV's

17" SLIMLINE 405 ONLY £11.19.0

2 YEARS' GUARANTEE FREE ILLUSTRATED LIST OF TELEVISIONS 17"—19"—21"—23"

19" SLIMLINE 405/625 BBC 2 £29.19.0



WIDE RANGE OF MODELS DEMONSTRATIONS DAILY



CARR. INS. 30/-

STEREO RECORD PLAYER CABINET & MATCHING EXTERNAL SPEAKER CABINET £5.19.6



Cloth covered. Two tone Blue/Black. Size 14 1/2" x 24" x 8 1/2". P. & P. 10.6.

TV TUBES REBUILT GUARANTEED 2 YEARS



14"—79.6, 17" & 19"—119., 21" & 23"—129.-. Exchanged Bowls. Carr. 10.6.

SPEAKERS. BRAND NEW 10.-. P. & P. 1.-. 2 1/2" x 8.0.

TRANSISTOR CASES, 5.- each. Cloth covered & plastic. P. & P. 3.-.

PRESS BUTTON SWITCHING UNITS. 4 Banks 3.6. 6 Banks 5.6. P. & P. 1.-.


TRANSISTORS 2.6 EACH. OC44, OC45, OC71, OC81, OC81D, AF114, AF117, AC128.

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Phone 01-478 6001-2-3 Stamp for Free List
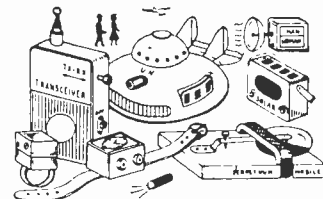
## PRINTED CIRCUIT KIT

BUILD 40 INTERESTING PROJECTS ON A PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminated Boards 4 1/2" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser Degreaser. (8) 16-page Booklet 'Printed Circuits for Amateurs'. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit. (10) Essential Design Data, Circuits, Chassis Plans, etc. for 40 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



EXPERIMENTER'S PRINTED CIRCUIT KIT 8/6

Postage & Pack. 1.6 (UK)

Commonwealth: SURFACE MAIL 2/- AIR MAIL 8/- Australia, New Zealand South Africa, Canada.

- (1) Crystal Set with base Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamic Loud-speaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loud-speaker Radio. The smallest 5 designs yet offered to the Home Constructor for anywhere in the World. (10) 3 Subminiature Radio Receivers based on the "Tri-Ton" circuit. Let us know if you know of a smaller design published anywhere. (11) Postage Stamp Radio. Size only 1-62" x .95" x .25". (12) Wristwatch Radio 1-15" x .80" x .55". (13) Ring Radio 7-0" x 7-0" x .55". (14) Battery-powered Radio. Runs on sugar or bread. (15) Radio Control Tone Receiver. (16) Transistor P.P. Amplifier. (17) Intercom. (18) 1-cable Amplifier. (19) Reliable Burglar Alarm. (20) Light-Seeking Annual Guided Missile. (21) Perpetual Motion Machine. (22) Metal Detector. (23) Transistor Tester. (24) Human Body Radiation Detector. (25) Man/Woman Discriminator. (26) Signal Injector. (27) Pocket Transceiver (License required). (28) Constant Volume Intercom. (29) Remote Control of Models by Induction. (30) Inductive-Loop Transmitter. (31) Pocket Triple-Reflex Radio. (32) Wristwatch Transmitter. (33) Wireless Microphone. (34) Rain Alarm. (35) Ultrasonic Switch Alarm. (36) Stereo Pre-amplifier. (37) Quality Stereo Push-Pull Amplifier. (38) Light-Beam Telephone "Photophone". (39) Light-Beam Transmitter. (40) Silent TV Sound Adaptor. (41) Ultrasonic Transmitter. (42) Thyristor Drill Speed Controller.

**YORK ELECTRICS, Mail Order Dept.**  
335 BATTERSEA PARK ROAD, LONDON, S.W.11

Send a S.A.E. for full details, a brief description and Photographs of all Kits and all 52 Radio, Electronic and Photoelectric Projects Assembled.

# knight-kits

# FANTASTIC LOW PRICES!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 7/6 CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

## KG-865 50 Watt Stereo Amplifier Kit

### DELUXE FEATURES


All Silicon Transistors for Stability, Cleaner Sound • Extremely Wide Power Bandwidth and Frequency Response • 50W IHF Power Output • Specially Selected Low-Noise Preamp Transistors • Two Printed Circuit Boards for Fast Easy Assembly • Convenient Front-Panel Stereo Headphone Jack • Teak-finished Extruded Aluminium Front Panel • Two a.c. Convenience Outlets.



Output: 50W IHF, 25W per channel; 34V continuous sine wave • Response:  $\pm 1dB$ , 18 to 30,000Hz • Output Impedances: 4 through 16 ohms, plus stereo headphones • IM Distortion: under 1% at 60Hz and 7,000Hz mixed 4:1 at rated power • Input Sensitivity: Magnetic Phono, 5mV; Tuner and Auxiliary, 500mV • Power Requirement: 230-250V, 50Hz a.c. Recommended List Price £34.19.6: 26 GNS. Assembled 29 GNS. Teak Case £5 Extra
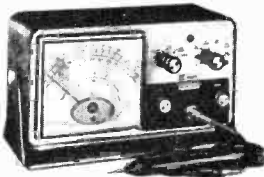
## KG-625 Deluxe 6in Vacuum Tube Voltmeter Kit

Huge 6in Meter Scale • Ranges: a.c. 0-0.5-1.5-5-15-50-150-500-1,500V full scale. • Accuracy:  $\pm 3\%$  of full scale reading • Input Resistance: 11M $\Omega$  to 1,500V • Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale. 0-1-2-4-12-140-420-1,400-4,200V full scale • Accuracy:  $\pm 5\%$  • Frequency Response:  $\pm 1dB$ , 30Hz to 3MHz;  $\pm 3dB$ , 30Hz to 3MHz • Ohmmeter Ranges: 0-1,000-10,000 ohms; 0-1-10-100-1,000M $\Omega$  • Battery: 1.5V 1.2. Recommended List Price £24.19.6: 12 GNS.




## KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests

It's several trailers in one... do all this

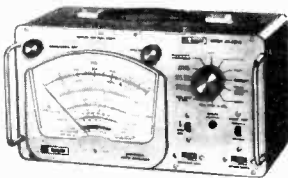Set Engine Idle and Automatic Transmission Shift Points • Detect Condition of Point Surfaces • Detect Distributor Wear • Check Voltage and Current Regulators • Check Generators for both Current and Voltage Output • Find Poor or Open Earth Circuits • Detect Variation in Dwell Angle. Recommended List Price £25.17.6: 16 GNS. Assembled Price 21 GNS.



### WHY NOT BUY THE PAIR?

## KG-371 Deluxe Solid-State Timing Light

Performance surpasses assembled units costing much more

Helps Set Ignition Timing • Checks Synchronisation of Double Breaker Arms • Checks for Sticking Automatic Spark-Advance Mechanism • Checks Distributor Cam Wear • Built-in d.c. Power Supply • Reliable Solid-State Circuit • Your car gives More miles per gallon; Improved performance; Greater reliability. Recommended List Price £12.10.0: 9 GNS. Available Assembled Only.



## KG-620 4 1/2" VTVM KIT ★ NEW!

### SPECIFICATIONS



Ranges: 0-1.5-5-15-50-150-500-1,500V full scale; with optional High-Voltage Probe, to 25,000V. Accuracy:  $\pm 3\%$  of full scale reading. Input Resistance: 11 megohms (1 meg in probe) up to 1,500V. Ranges (rms): 0-1.5-5-15-50-150-500-1,500V full scale (p-p); 0-4-2-14-42-140-420-1,400-4,200V full scale. Decibels: -10 to +65 in 7 ranges. Response:  $\pm 1dB$ , 30Hz to 3MHz;  $\pm 3dB$ , 30Hz to 5MHz; with optional H.F. Probe, to 250MHz. Accuracy:  $\pm 5\%$  of full scale reading. Ranges: 0-1,000-10,000-100,000 ohms; 0-1-10-100-1,000 megohms. Centre Scales: 10, 100, 1,000, 10,000, 100,000 ohms; 1 and 10 megohms. Battery 1.5V size U2.

Recommended List Price £18.3.6: 9 1/2 GNS. Assembled Price £14. (RR Price £30.0.0)

## KG-790 Stereo AM-FM Tuner Kit

SUPERB CHASSIS MODEL WITH PERFORMANCE NEVER BEFORE ATTAINABLE IN A SOLID-STATE STEREO TUNER KIT

- Has that "Factory-bullit" Look of the Finest Stereo Hi-Fi Tuners available
- Four Double-tuned IF Stages for Super-Sensitivity
- 22 Transistors, 14 Diodes
- Whistle Filter
- Built-in Tuning Meter
- Size 5 x 16 1/2 x 15 1/2 in
- Automatic Stereo FM Switching



### FM SECTION

- Usable IHF Sensitivity:  $\pm 5\mu V$  for 30dB quieting
- Range: 87.5 to 108.5 MHz
- Hum and Noise: -60dB
- IF Bandwidth: 300kHz
- Response:  $\pm 2dB$ , 50Hz to 15kHz
- Distortion: less than 0.75% at 1-volt output
- Aerial: unbalanced 300-ohm input

### AM SECTION

- Sensitivity: 3.5 $\mu V$  for 20dB S/N ratio; 1.5 $\mu V$  for 10dB S/N ratio.
- IF Bandwidth: 7.5kHz
- IF Rejection: 60dB min
- Image Rejection: 70dB min at 1kHz
- 10-ke Rejection: 40dB min
- Listed £92.12.11 49 GNS.

## Introducing The New

## Jason "Delta" Loudspeaker Enclosure.

Incorporating the famous EMI 150 set consisting of a 13x8in. bass unit with a high flux ceramic magnet and a concentric tweeter impedance 8 $\Omega$  20 watt peak handling power (10 watts RMS).

Heavy duty 16mm infinite baffle case in superb quality genuine golden teak veneers with solid mahogany contrasting leading edges. High quality foam loaded cloth fret. Acoustically loaded "Jason" rotating badge in genuine gold leaf for horizontal or vertical operation. Size 19in. x 10in. x 10 1/2 in. Weight 16lbs. A price break through at only £12.10.0 each. Carriage etc 10/- singly. Carriage free in pairs.

## PLINTHS & COVERS

for Garrard (all take current models except heavy transcription types) Beautiful heavy solid perspex top with "stereo" badge high quality base with solid wood sides machined ready for R/P deck to drop in without any further work. Terrific value at only 68/- complete. Carr. & Insurance 7/6.



We offer you fully tensilised polyester/nylon and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT

Standard	Long	Double	Triple
3in. 150ft.	2/3 3in. 225ft.	2/9 3in. 300ft.	4/- 4in. 900ft. 13/-
4in. 300ft.	4/6 4in. 450ft.	5/6 4in. 600ft.	8/- 5in. 1,800ft. 25/-
5in. 600ft.	7/6 5in. 900ft.	10/8 5in. 1,200ft.	15/- 5 1/2 in. 2,400ft. 34/-
5 1/2 in. 900ft.	10/8 5 1/2 in. 1,200ft.	13/- 5 1/2 in. 1,800ft.	19/- 7in. 3,600ft. 44/-
7in. 1,200ft.	12/8 7in. 1,200ft.	18/8 7in. 2,400ft.	27/- Quadruple 3in. 600ft. 8/6

Post free less 5% on three reels. Quality and Trade enquiries invited. NOTE. Large tape stocks at all branches.

Stockists of Leak, Quad, Sharp, Goodman, Garrard, Akai, Eagle, Rodgers, Crown, Teleton, Wharfedale, etc.

# TECHNICAL TRADING

## FREE FLOG LIST NO 2 Scores Special Bargains

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

PERSONAL CALLERS Welcomed at branches listed to right where there are large Hi-Fi and Component stocks at the keenest prices including:

All Mail Orders Only to Arundel.


★ ARUNDEL 15-17 Queen Street Tel. 3280

★ BRIGHTON 6 Queen's Road Tel. 23975

★ PORTSMOUTH 350-352 Fratton Road. Tel. 22034

★ SOUTHAMPTON 72 East Street Tel. 25851

# DISCOSOUND

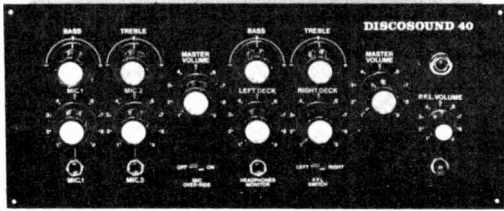

## DISCOSOUND 40 PRE-AMP

The Discosound 40 offers the same specification as the D.J. Disco Amp without the power output stage. Size 16in x 7in x 7in. Self powered and ideal for use with the Discosound 100 Power Amplifier below and one of the outstanding features is that it is capable of running ten of these Power Amplifiers (Total 1,000W).

PRICE £40.10.0 inc. P. & P.


## DISCOSOUND 100 POWER AMPLIFIER



A 100W RMS (8 Ohms) High Fidelity power Amplifier which utilises all silicon transistors of modular construction and features full automatic overload protection against short or open circuits. Frequency response: 20-20,000Hz ± 2dB. The High output is ideally suited for discotheques, groups, clubs, etc., or anywhere where reliability and quality are required. This unit is the companion model for use with our control pre-amp Discosound 40, or can be used with any other high quality pre-amp control unit. Completely built and tested on steel Chassis.

PRICE £49.10.0 inc. P. & P.

## DJ70S INTEGRATED MIXER-AMPLIFIER

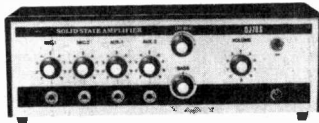

One of the finest units available on the market today, regardless of price. The front end of the unit consists of a four channel mixer with separate inputs and volume controls, plus a separate bass, treble and master volume control. One of the main features of this remarkable amplifier is its elaborate protection against short and open circuit and we can guarantee that it is virtually indestructible. Allied to this is its very high power output (70W R.M.S.) a frequency response (30-20,000Hz ± 3dB) that is superb, and distortion that is well below 1%, even at full output. The unit is suitable for use with discotheques, groups, P.A., clubs, etc., or anywhere that high quality high output is required. Size: 15½in x 5in x 6in.

PRICE £63.0.0 inc. P. & P.

Also available DJ105S 30W P.A. Amplifier. Similar specification to above.

PRICE £41.0.0 inc. P. & P.

For full details of these and all Discosound Products write direct to:

# DISCOSOUND

122 BALLS POND ROAD, LONDON, N.1. Tel. 01-254 5779

Full money back guarantee if returned within 10 days  
All Discosound Products are guaranteed for 12 months  
Demonstrations given at any time

# KONTAKT 60

FOR INACCESSIBLE CONTACTS—More than just a cleaner. KONTAKT 60 guarantees perfect cleaning of contacts chemically in accordance with today's technology.

KONTAKT offers the following advantages:—

1. Dissolves oxides and sulphides the safe way without attacking contact substances.
2. Contains carefully selected solvents which do not attack plastics whereas they do dissolve resinified contact greases and dirt.
3. Contains no silicone.
4. Contains a light lubricant in order to avoid the contact paths being corroded.
5. Prevents further oxidation setting in.
6. Prevents "creep" currents.

Because of these outstanding properties KONTAKT 60 is one of the best and most popular contact cleaning agents in the world.



Users include: Rolls Royce Ltd., C.E.G.B., South of Scotland Electricity Board, Trinity House Workshops, Kolster Brandes, Mullard, Plessey Cos., etc.

OTHER KONTAKT PRODUCTS ARE:

- |                                  |                                   |
|----------------------------------|-----------------------------------|
| 70 Protective Lacquer            | 80 Special Siliconized Polish     |
| 72 Insulating Spray              | 100 Antistatic Agent For Plastics |
| 75 Cold Spray For Fault Location | 101 Dehydration Fluid             |

Write for full details of above complete range of Kontakt products to:—

## SPECIAL PRODUCTS DISTRIBUTORS LIMITED

81 Piccadilly, London, W.1 01-629 9556

## 1 MILLION SILICON PLANAR TRANSISTORS

### NPN-PNP PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed no open or short circuit units. Ideal cheap transistors for radio enthusiasts, manufacturers, schools and colleges.

#### TYPE STN18

Silicon Planar Transistors npn TO-18 Metal Can. Types similar to: 2N706, 2N2220, BSY27-95A, BSX44-76-77.

Price: 500 £9, 1,000 £15

#### TYPE STP18

Silicon Planar Transistors pnp TO-18 Metal Can. Types similar to: BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as complementary to the above npn type device type STN18.

Price: 500 £9, 1,000 £15

#### TYPE STNL

Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA, 300mW medium to high gain, available in npn or pnp and types similar to: NPN 2N2926 — 2N2711 — 2N3391 — 2N3707 — 2N3711 — BC167-8-9.

Price: 500 £7.10.0; 1,000 £13

#### TYPE STPL

As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061 and 2N3702-3. Also used as complementary to the above npn devices type STNL.

Price: 500 £7.10.0; 1,000 £13

#### TYPE STNK

Silicon Planar Plastic Transistor npn with TO-18 pin circular lead configuration, I.C. 200mA, 300mW and similar to BC107-8-9, BC170, BC173, BC182-184, BC237-8-9 and BC337-8.

Price: 500 £9.10.0; 1,000 £16

When ordering, please state type required, i.e., STNK or STN18, etc.

All goods Ex-stock sent by return. Cash with order please to:

## DIOTRAN SALES

P.O. Box 5, WARE, Herts.

S.A.E. For full list of surplus semiconductors

# ROC ELECTRONICS

## 20 PROJECT SOLAR ELECTRONIC KIT Mod. R.128



This ultra modern Project Kit is shaped for the space age. Carried inside a transparent domed 4 1/4" capsule the R.128 comes complete with a self-contained solar cell to power any one of 20 projects ranging from a one transistor radio to a morse set complete with key and morse training code. Supplied complete with easy to follow instructions, and even the cement to assemble this unique electronic space capsule.

PRICE £4.10.0



## 2 OCTAVE ELECTRONIC ORGAN KIT Mod. R.129

Complete with a music book containing 10 easy to play songs the R.129 solid state organ kit covers 2 full octaves. Moulding into a fitted hardwood case the top panel carries the key assemblies and all the components including the loudspeaker. Like all Roc Electronic Kits every item is included down to the last nut and bolt so that the constructor can start assembly within minutes of opening the package.

PRICE £4.10.0

## 10 PROJECT INTEGRATED CIRCUIT KIT

### Model R.127

Using a robust Solid State Integrated circuit the R.127 kits will build any one of these projects: (1) Germanium Radio. (2) Test Oscillator. (3) Morse Telegraph Training Set. (4) I.C.T. Transistor Radio. (5) Germanium 1 Transistor Radio. (6) Record Player Amp. (7) Continuity Tester. (8) A.F. Signal Tracer. (9) Radio Transmitter. (10) Water Purity Tester.

PRICE £3.10.0

## 2 TRANSISTOR SOLAR RADIO KIT Model R.126

Like all Roc Electronic Kits the R.126 uses reliable no-solder connections to produce a complete 2 transistor radio in under 2 hours. As well as battery operation the kit is supplied complete with a solar cell to provide power from the Sun or any strong light source.

PRICE £2.10.0



## CRYSTAL RADIO KIT Model R.125

This easy to build Radio is based on the same circuit developed by Marconi for the very first radio transmission but uses a modern ferrite aerial for maximum efficiency. A perfect introduction to Radio Theory.

PRICE £1.10.0




## 5 WATT STEREO INTEGRATED AMPLIFIER

### CHASSIS Model R.123

Mounted on a heavy gauge chassis the fully transistorised R.123 stereo amplifier is completely self-contained even down to gangol volume and separate tone controls. For a simple stereo amplifier of excellent quality all you have to provide is the cabinet and control knobs.

**SPECIFICATION:**  
Output: 5W total, 2.5W per channel.  
Input sensitivity: 600mV at 2.2Mohms.  
AC 240V operation.

PRICE £4.19.0

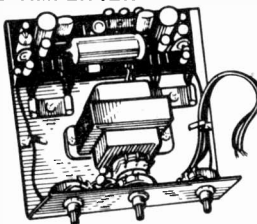

## 5 WATT 8 TRACK CARTRIDGE STEREO AMPLIFIER Model R.133

Just slot in one of the many 8 track cartridge tapes available for a continuous programme of your favourite music. A manual programme override switch enables you to switch from one track to the next at the push of a button at the same time a numbered indicator lights up to show which track is playing. Beautifully finished in an oiled walnut cabinet the R.133 is mechanically engineered to provide long and reliable service.

**SPECIFICATION:**—Tape speed: 9.5 cm/sec (32 i.p.s.). Wow & flutter: better than 0.3%. Frequency range: 40-12,000Hz. Cross talk: better than 45dB at 1,000Hz. Output: 5W total, 2.5W per channel. Amplifier outputs: 200mV.

PRICE £36.0.0



## 40 WATT STEREO AMPLIFIER

### Model R.131



Looking as good as it sounds the R.131 stereo amplifier offers excellent quality and value for money. Housed in a handsome wooden cabinet this new Roc Amplifier uses the latest solid state circuit techniques to give a specification second to none at the price.

**SPECIFICATION:**—Output: 40W total 20W per channel. Frequency Range: 20-30,000Hz. Inputs: Phono: Mag, 3.6mV R.I.A.A.; Xtal, 100mV; tape, 200mV; tuner, 200mV. Control: Bass, treble, volume left, volume right, selector main/remote speakers, power on/off, loudness and stereo/mono.

PRICE £25.0.0



## AM/FM/MPX STEREO TUNER

### Model R.132

Matching the R.131 amplifier in both styling and performance the R.132 tuner covers AM and FM including stereo multiplex channels. A separate meter indicates signal strength and tuning on both AM and FM Bands. A usable FM sensitivity of 3µV means that the R.132 can be found anywhere, even in different stereo reception areas.


**SPECIFICATION:** FM: frequency range: 87-108MHz. Usable sensitivity: 3µV for 20dB quieting. Stereo separation: 30dB at 1KHz. Image rejection: 60dB. AM: frequency range: 525-1605Hz. Usable sensitivity: 250µV.

PRICE £36.0.0



## FOUR BAND SHORT WAVE RECEIVER KIT

### Model R.140

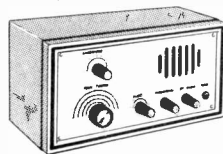

This excellent transistorised battery operated kit will not only provide hours of entertainment when made up but also in its construction. It receives the normal broadcast band 550kHz to 1.6MHz and on short wave 1.5-30MHz in three bands.

The 32-page manual not only shows step by step instructions on how to assemble the kit but also includes a guide on broadcasting stations throughout the world.


PRICE £9.8.0



## PROFESSIONAL SOLID STATE FOUR BAND COMMUNICATION RECEIVER Model R.135

This is the communication receiver that you have long been waiting for. Fully transistorised and continuous coverage from 550kHz to 30MHz in four bands including illuminated electronic bandspread for 160-10 metres. Also incorporated is an internal speaker, automatic noise limiter, M8B/AM/CW Switch, AVC switch, 8 Meter, Receive and Standby Switch, external socket for headphone or speaker, bandspread control, RF control, on/off/A.F. gain, band selector, antenna trimmer and RF gain. The R.135 will run off of 240V a.c. dry batteries or any 12V d.c. negative ground source.

PRICE £45.0.0

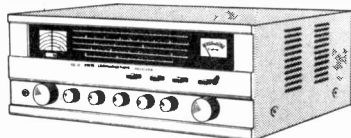

## 10 WATT TRANSISTOR STEREO AMPLIFIER

### Model R.137



With separate tone and volume controls on each channel and inputs for both phono and tuner, this 10 transistor amplifier is the ideal start to an excellent budget system. Frequency response 70-20 KHz. Output impedance 8-16 ohm. Attractively styled with brushed aluminium front panel.

PRICE £9.10.0



## 10 WATT BUDGET STEREO ALL TRANSISTOR AMPLIFIER Model R.136



Ideal as a second stereo system or for the newcomer to Hi-Fi who wishes to upgrade existing equipment the R.136 sounds every bit as good as it looks. As well as inputs for crystal or ceramic cartridge the R.136 has a Stereo Tuner input which accepts the matching R.134 Stereo AM/FM Tuner.

The Satin Finish front panel carries a stereo headphone socket as well as volume, balance, tone (all ganged) speaker, mode and selector controls. Supplied complete with offal walnut enclosure.

**SPECIFICATION:** Output: 10 watts total, 5 watts per channel. Frequency Range: 35-18,000Hz. Inputs: Phono and Tuner.

PRICE £13.0.0



## STEREO FM/AM/MPX TUNER AMPLIFIER

### Model R.124

Another Roc Exclusive offering top value for money performance the R.124 is a Stereo Tuner/Amp with facilities only usually found in much more expensive units. Features like separate bass and treble controls, automatic frequency control switch and stereo headphone socket give the R.124 a price to specification ratio second to none.

Housed in a handsome walnut cabinet the classical lowline styling of the R.124 will grace any home.

**SPECIFICATION:** FM: Frequency Range: 88-108MHz. Usable sensitivity: 20µV. Stereo Separation: 20dB at 1KHz, 20dB minimum. Image Rejection: 55dB. AM: Frequency Range: 535-1600Hz. Usable Sensitivity: 300µV. Audio Section: Total Output Power: 4W. Phono Input: 200mV at 1MΩ. Tape Input: 100mV at 100KΩ.

PRICE £29.19.0



H.P. Terms available for personal callers on purchases over £50.

## RETURN OF POST MAIL ORDER SERVICE Dept. PE

Orders under £10 please add 5/- post and packing. Orders over £10 sent post free.

**ROC ELECTRONICS LIMITED**  
193 EDGWARE ROAD LONDON W2 1ET

TELEPHONE: 01-723 6211

Shop open 9-6 Monday-Saturday (Thurs. 1 p.m.)

# Lasky's

## Garrard

### TMK METER KIT

This meter kit by TMK offers the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full constructional, circuit and operating instructions:

**MODEL 200** 20,000 O.P.V. Multimeter.  
 Features 24 measurement ranges with mirror scale. Large 3x2in meter. Full scale accuracy: DCV and current:  $\pm 2\%$ , ACV:  $\pm 3\%$ , resistance  $\pm 3\%$ . Special 0.6V DC range for transistor circuit measurements.

**SPECIFICATION**  
 ● DCV: 0-0.6-6-30-120 600-1,200V at 20K/OPV.  
 ● ACV: 0-0.6-6-600-1,200V at 10K/OPV. ● DC Current: 0-0.6-6-600mA. ● Resistance: 0-10K 100K-1M-10M/ohms (58-580-5.8K-58K at mid-scale).  
 ● Capacitance: 0.002-0.2 $\mu$ F (AC 6V range). ● Decibels -20 to +63dB. ● Output: 0.05 $\mu$ F blocking capacitor. Uses two 1.5V (U7 type) batteries. Black bakelite cabinet—Size 5 $\frac{1}{2}$  x 3 $\frac{1}{4}$  1 $\frac{1}{2}$ in. Complete with test leads.



**KIT PRICE ONLY £4.59** POST 15p

## JUST ARRIVED

### Lasky's COMPACT CASSETTES

Exclusively made for us in U.S.A. Great Savings!

	Each	Post	Five	Post	Ten	Post
C60—	37p	5p	£1.65	20p	£3.10	25p
C90—	37p	5p	£2.75	20p	£5.25	25p
C120—	87p	5p	£3.75	20p	£6.75	25p

U.S.A. Cassette head cleaner, 56p. Post 5p




## INTERNATIONAL

**MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES**

3in. Message tape, 150ft.	13p	5 $\frac{1}{2}$ in. Long play, 1200ft.	75p
3in. Message tape, 225ft.	19p	5 $\frac{1}{2}$ in. Mylar, 1800ft.	175p
3in. Message tape, 300ft.	38p	5 $\frac{1}{2}$ in. Triple play, 2400ft.	175p
3 $\frac{1}{2}$ in. Triple play, 600ft. Mylar	50p	7in. Standard play, 1200ft.	63p
5in. Double play, 1200ft.	75p	7in. Acetate	63p
5in. Long play, 900ft. Acetate	50p	7in. Mylar	63p
5in. Standard play 600ft.	43p	7in. Long play, 1800ft.	98p
5in. Double play, 1800ft. Mylar	113p	7in. Mylar	125p
5 $\frac{1}{2}$ in. Long play 1200ft. Acetate	75p	7in. Double play, 2400ft. Mylar	125p
5 $\frac{1}{2}$ in. Standard play 900ft. PVC	63p	7in. Long play 1800ft. Acetate	75p
		7in. Triple play 3600ft. Mylar	250p

P. & P. 1/- extra per reel, 4 reels and over P. Free. Special quotes for quantities.

## AUDIO DEVELOPMENT

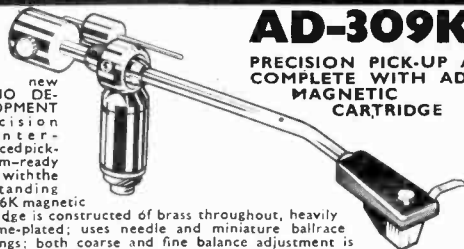

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm—ready fitted with the outstanding AD-76K magnetic

cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard 5in. mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in. dia. mounting hole.

**LASKY'S PRICE £8.50** Post Free

### AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response 20-20,000Hz. Output: 5mV. Stylus: **£4.50** Post Free

Diamond LP. Compliance. Tracking force: 2 gms  $\pm 0.5$  gm. Replacement stylus type JS.PI 41/- post free.

### AUDIO DEVELOPMENT AD-96K

Stereo Magnetic Cartridge. Frequency response 20-20,000Hz. Output: 5mV. Stylus: **£5.93** Post Free

Diamond LP. Compliance. Tracking force: 2 gms. Replacement stylus type Y.9605 51/6, post free.

### SL-55 SPECIAL OFFER

Four-speed auto-changer: NOW AT LASKY'S SPECIAL PRICE. Complete with SONOTONE 9TA STEREO CARTRIDGE. £10.95.

#### AUTOCHANGERS

SL72B	£24.95
2025TC with stereo cartridge	£8.95
3000 complete with STAHC stereo cartridge	£9.95
SL65B	£15.50
SL95B	£35.00
SL75B	£28.00

#### SINGLE PLAYERS

AP 75, £18.50. AP75 with AD76K mag. cart., £21.50. 401 Transcription Unit, £20.00.

#### BASES AND COVERS FOR GARRARD UNITS

Type WB1 and WB5 for models AT60 Mk II, 2025TC, 3000, SL65B, SL55, 1025, SP25 Mk. II. Price WB1 £3.83. WB5 £5.63. Type WB4 for models SL72B, SL75B, SL95B. Price £5.63. Perspex covers: SP C1 for WB1 £3.71. SP C4 for WB4 and WB5 (allows unit to be played with the cover in place—Price £4.40. LASKY'S BASE AND COVER FOR ABOVE UNITS £4.75. Post 20p.




Now available the new **GARRARD SP25 Mk. III**

four speed single player with automatic player/return and cue control facilities.

## MULTIMETERS

### MODEL C-1051

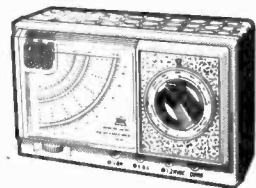

20 K/ohms/V MULTIMETER

Miniaturised version of Model C-1052 employing similar ultra compact

slimline impact resistant cabinet. Buff/green finish, size 4 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. Features—large easy to read meter with mirror scale, D'Arsonval movement. Overload protection circuit. Fine calibration gives extremely high standard of accuracy on all ranges. Ohms zero adjustment. Click-stop range selection switch. Colour coded scales.

- DC/V: 0-3-15-150-300-1.2KV at 20K/ohms/V.
- AC/V: 0-6-30-300-1.2KV at 10K/ohms/V.

- DC current: 0-60 $\mu$ A-300mA.
- Resistance: 0-60K-6M/ohms.
- Decibels: -20dB to +17dB.
- Complete with battery and test leads.

**LASKY'S PRICE ONLY £4.25** POST 13p

## NEW MODEL C-1050



100,000 ohms/V WITH MIRROR SCALE AND BUILT-IN TEST LEAD COMPARTMENT

A completely new design "slimline" meter of very smart appearance with unique integral test lead compartment with hinged lid. Large 3in. meter with mirror scale permits extremely easy reading. D'Arsonval movement. Overload protection circuit. Superbly finished black impact resistant cabinet with brushed aluminium trim panels.—Size 5 $\frac{1}{2}$ in. x 3 $\frac{1}{2}$ in. x 1 $\frac{1}{2}$ in. Positive click-in selector for 12 different ranges, plus dB. Operates on one penlight cell.

- DC/V: 0-3-15-150-600-1.2KV at 10K/ohms/V.
- AC/V: 0-6-30-300-1.2KV at 5K/ohms/V.
- DC current: 120 $\mu$ A; 300mA.
- Resistance: 0-5K, 0-5m ohms.
- Decibels: -20 to +17dB.
- Complete with battery, test leads and instructions.

**LASKY'S PRICE £5.95** POST 13p

# Astrad ORION

# McDONALD

## THE WORLD'S SMALLEST TWO WAVEBAND, 6 TRANSISTOR RADIO



Music, news, sport, wherever you are, 7-day money back guarantee if you are not absolutely delighted with the results. Make no mistake, this is a real radio, not a toy or crystal set! Fully built and tested, ready for immediate use. NO EXTRAS. This minute radio will play anywhere—any time, beach, garden, park, home, office, school, etc. The super sensitive 6 transistor circuit is fully tuneable over both long and medium wavebands, with built-in ferrite rod aerial to provide excellent selection. The Orion operates from one tiny battery, either mercury or nickel cadmium, for long life and economical running cost. The output is via a crystal-type personal earphone, giving extreme clarity, which prevents disturbing other people when used in public parks, open spaces, etc. The small size of the Orion allows it to be carried easily in the pocket or handbag, and it is also supplied with an attractive presentation case. Complete with earpiece, battery and carrying case. **Specification.** Waveband coverage: Medium 525kc/s to 1,605kc/s; Long 150kc/s to 308kc/s. Sensitivity: 35mV/m max. Selectivity (at -30kc/s detuning) -10dB. Power consumption: 4mA max. Power source: 1 x 1.4V Mercury battery. Mallory type RM625 or equivalent. Mallory battery is not rechargeable.

**COMPLETE WITH EARPIECE ONLY POST RECHARGEABLE BATTERY POCKET CARRYING CASE £1.48 18p**

\*Spare rechargeable battery 18p extra—post FREE with radio.

## BARGAIN PACKAGE

COMPRISING—1 ORION RADIO 1 RECHARGEABLE BATTERY AND BATTERY CHARGER **£2 20p** POST

### BATTERY CHARGER

THE BATTERY WE SUPPLY WITH THE ORION IS A RECHARGEABLE TYPE. BATTERY CHARGERS ARE AVAILABLE TO RECHARGE THE BATTERY AGAIN AND AGAIN. OPERATES ON HOME MAINS 200/240 VOLTS A.C.

Battery life is approx. 10 hours. Charging time: 10 hours. A spare battery will enable you to keep your Orion constantly in use.

**LASKY'S PRICE 85p POST FREE WITH RADIO**

## SONICS AS-57

### BUDGET BOOKSHELF SPEAKER SYSTEMS


The AS-57 is a real space saver. This fine miniature high-fidelity speaker system will provide good quality sound anywhere in your home at remarkably low cost. Designed for use where space is at a premium, the AS-57 system is ideal for the small apartment or isolated listening area. The special high efficiency 5 7/8 in. full range speaker has a frequency range of 70-18,000Hz with a peak handling capacity of 10 watts. Imp. 8 ohms. Finish: oiled walnut. Size 5 1/2 x 1 1/2 x 8/16 in.

**LASKY'S PRICE £15 per PAIR POST FREE**

## SOUND-SCAN AUDIO TRANSDUCERS
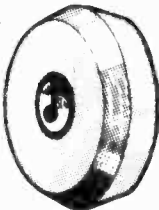
### TURN ANY SURFACE-WALL-DOOR-WINDOW INTO A SPEAKER!!

The Sound Scan method employs a newly developed audio transducer which converts whole areas into sound reproducing surfaces. Sound just flows from walls, ceilings, windows, tables and chairs when fitted with these new units. Easily adaptable to most conventional radios, recorders and other music systems, the Sound Scan will reproduce efficiently when mounted on glass, plastic, fibre board, plaster board, wood, etc. Input impedance 8 ohms. Designed to work with amplifiers with an output of between 2-12 watts. Size: 4in. dia. x 1 1/2 in.



**LASKY'S PRICE £9.95 EACH Post 20p Each 2 FOR £18.75**

## MP.60

## PROFESSIONAL SERIES FOUR SPEED SINGLE PLAY UNIT

High-precision low-mass fully counter-balanced pick-up arm, heavy balanced turntable, simply operated controls, viscous cueing device, slide in cartridge carrier, four pole motor.



**LASKY'S PRICE £11.50 POST 35p.**

complete with plinth and cover **£15.00 POST 40p.**

## 610 AUTOMATIC TURNTABLE

Same specifications as the MP60 but with synchronous four pole motor and full automatic change facilities.

**LASKY'S PRICE £13.95 POST 35p.** WITH PLINTH AND COVER £17.75 POST 40p.

## 510 AUTOMATIC TURNTABLE

Counter balanced pick-up arm, pressed steel turntable, bias compensator, viscous cueing and synchronous four pole motor.

**LASKY'S PRICE £11.75 POST 35p.** WITH PLINTH AND COVER £15.50 POST 40p.

## 310 AUTOMATIC TURNTABLE

Low mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide in cartridge carrier, four pole motor.

**LASKY'S PRICE £9.95 POST 35p.** WITH PLINTH AND COVER £13.75 POST 40p.

## BSR McDONALD PACKAGES

### PACKAGE No. 1

BSR McDONALD 510 4 Speed Autochange	£16.03
AUDIO DEVELOPMENT AD76K Magnetic Cartridge	£ 4.50
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
<b>Recommended retail price</b>	<b>£28.14</b>

**LASKY'S PRICE £23.25 POST 40p.**

ADD £5.50 if M2100/E is preferred  
ADD £6.50 if Shure M44/5 is preferred

### PACKAGE No. 2

BSR McDONALD 310 4 Speed Autochanger	£12.95
AD76K Magnetic Cartridge	£ 4.50
BSR Afromosia Plinth with black mounting board	£ 4.44
BSR Smoked Perspex Dust Cover	£ 3.17
<b>Recommended retail price</b>	<b>£25.06</b>

**LASKY'S PRICE £21.50**

ADD 50p if BSR Ceramic Cartridge is preferred

## NOW AVAILABLE LASKY'S EXCLUSIVE

LASKY—McDONALD plinth and cover available separately at **£4.75 POST 25p**

## OUT NOW LASKY'S NEW 1971 AUDIO-TRONICS CATALOGUE

See page 174 for further details

# Lasky's Radio Limited

207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3721  
33 TOTTENHAM CT. RD, LONDON, WIP 9RB. Tel: 01-636 2605  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday

109 FLEET STREET, LONDON, E.C.4. Tel: 01-353 5812  
152/3 FLEET STREET, LONDON, E.C.4. Tel: 01-353 2833  
Open all day Thursday, early closing 1 p.m. Saturday

HIGH FIDELITY AUDIO CENTRES  
42-45 TOTTENHAM CT. RD, LONDON, WIP 9RD. Tel: 01-580 2573  
Open all day, 9 a.m. - 6 p.m. Monday to Saturday

118 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 9789  
Open all day Saturday early closing 1 p.m. Thursday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E1 2BN Tel: 01-790 4821



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry? In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

**Who created Eduputer?** The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

**Jobs galore!** The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

**Telephone: (01) 437 9906 NOW!**

**Or post the coupon today** for full details FREE and without obligation.



**London Computer Operators Training Centre,**  
B75, Oxford House, 9/15 Oxford Street, London, W.1.  
Telephone (01) 437 9906.

127/131 The Piazza, Dept. B75, Piccadilly Plaza, Manchester 1.  
Telephone (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel.: \_\_\_\_\_



## PRACTICAL ELECTRONICS

Specify

**CONTIL  
MOD-2  
CASES**



PRACTICAL ELECTRONICS specify CONTIL MOD-2 CASES for housing the P.E. GEMINI AMPLIFIER, P.E. AURORA LIGHT DISPLAY SYSTEM, P.E. DIGITAL CLOCK. ALSO AVAILABLE READY PUNCHED—SINCLAIR FOR PROJECT 60 SYSTEM and ACTIVE FILTER UNIT.

PVC COATED MATERIALS.	PVC	WIDTH	HEIGHT	DEPTH	I OFF
easy to clean, surface is scuff resistant.	A	4.5"	3"	6.5"	37/-
PVC/ALUMINIUM FOR FRONT AND BACK PANELS.	C	4.5"	10"	6.5"	54/6
PVC/STEEL FOR SIDES, TOP AND BOTTOM. LOW COST.	G	13"	3"	6.5"	59/6
	N	Woodgrain	7"	13"	72/6
					59/6

★ See January issue for full prices and all sizes. Send for free leaflet.



**WEST HYDE DEVELOPMENTS LTD.,** RYEFIELD CRESCENT NORTHWOOD, MIDDX., HA6 1NN.

Telephone: Northwood 24941/26732. Telex 923231 WEST HYDE NTHWD

## BUILD YOUR CIRCUITS ON VEROBOARD

—the Universal Wiring Board—  
obtainable from your local Retailer

Trade enquiries to:  
**NORMAN ROSE (ELECTRICAL) LTD.**  
8 St. Chad's Place, Gray's Inn Road, London, W.C.1

Technical enquiries to:  
**VERO ELECTRONICS LTD.**  
Industrial Estate, Chandler's Ford, Hants

## BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts  
Bass Resonance 35 c.p.s.  
Flux Density 15,000 gauss  
Voice coil impedance 8 or 15 ohms models  
Useful response 20-14,000 c.p.s.  
Nett weight 15 lbs.

**£19**  
POST FREE

GUITAR MODEL "GROUP 50" 50 watt rating £19  
Latest catalogue 1/- with enclosure plans



**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665



# Send for your copy of the **HEATHKIT** 1971 CATALOGUE ... ...it's **FREE** on request



**MARINE**





**SPEAKERS**


**HI-FI & AUDIO**



**CONSUMER**

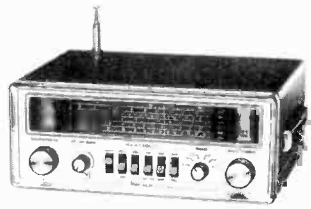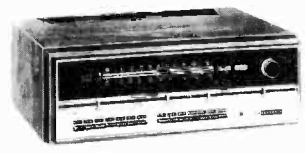

**SHORTWAVE**

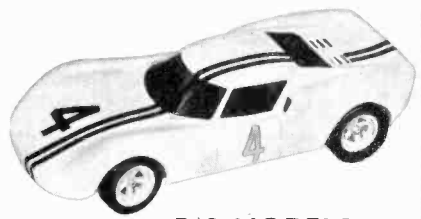

**R/C MODELS**

Here's the bumper Heathkit catalogue for you. Read about the wonder and fascination of kit building . . . see in full colour the world's best values in Hi-Fi Radio, and even model radio control. Get up to date with what's new in scientific instrumentation . . . instruments for test and service . . . in fact there is a Heathkit for almost every purpose, in every walk of life. A wealth of information is all yours for the price of a postage stamp, in the Free Heathkit Catalogue.

- ★ No previous knowledge of electronics required.
- ★ The constructional manual supplied with every kit shows you how.
- ★ Building Heathkit models is so economic.
- ★ Save up to 50% over factory built equipment.
- ★ Money saving direct from factory prices.



A Schlumberger Company

**HEATH** (Gloucester) LTD., GLOUCESTER GL2 6EE

Many other models in wide range

(BLOCK CAPITALS PLEASE)

**FILL IN THE COUPON FOR YOUR  
FREE CATALOGUE TODAY**

Name .....

Address .....

Post Code .....

25/2

# BI-PAK WAREHOUSE CLEARANCE

Over 1 Million Semiconductors must be sold.  
Order any or all of these. Bargain "SALE" PAKS  
Listed Below "NOW"  
UNSORTED/UNTESTED/UNCODED/UNBEATABLE  
VALUE

PAK Order No.	Qty.	Description	Price per PAK
SA1	150	Germ. Trans PNP Mixed lots	10/-
SA2	200	Germ. & Sil. Alloy Trans. PNP	10/-
SA3	100	Germ. A.F. Trans. 300mW PNP	10/-
SA4	200	Sil. Alloy Low gain switching Trans. PNP	10/-
SA5	100	Sil. planar plastic trans. PNP	10/-
SA6	100	Sil. plastic planar trans. PNP	10/-
SA7	100	Sil. planar Trans. TO5 plastic PNP 800mW	20/-
SA8	100	Sil. planar Trans. TO18 plastic PNP 500mW	20/-
SA9	100	Sil. planar trans. plastic PNP med. & high gain.	20/-

PAK Order No.	Qty.	Description	Price per PAK
SB1	200	GERM Diodes Gen. P.	10/-
SB2	200	GERM Gold Bonded	10/-
SB3	200	Sil. Switching Diodes 50mA	10/-
SB4	200	Sil. Gen. P. Diodes 300mA	10/-
SB5	300	Sil. & Germ. Mixed Diodes	10/-

The following are all new and Fully Tested Transistor Packs.  
ST1 30 PNP Trans Mixed all coded Germ. 20/-  
ST2 40 NPN Germ. To-5 2C339 Evt. 2N1302 AC127 10/-  
ST3 40 PNP Germ. AF 2C371B OC71-75 type 20/-  
ST4 30 PNP Germ. VHF 2C407L AF17=OC170 uncoded 20/-  
ST5 30 PNP Metal Alloy VHF 800m/cs Trans. 20/-  
ST6 40 PNP/NPN Assorted Trans all coded 20/-  
ST7 40 D1374 RF Trans Evt. ABY52 OC44/43 20/-  
ST8 40 2N706 NPN Switching Sil. Trans. 20/-  
ST9 30 2N709 NPN Sil. Trans. 20/-  
ST10 30 B8Y28 NPN Sil. Trans. 20/-  
ST11 25 2N3703 PNP Sil. Trans. 20/-  
ST12 25 TIS48=2N2368 NPN 400m/cs 20/-  
ST13 25 8E/2N3646 NPN TO-18 plastic 350m/cs 20/-  
ST14 40 2N3010 Sil. Alloy Trans PNP TO5 20/-

WHEN ORDERING PLEASE MENTION PAK, ORDER NO. IN ALL CASES. CLUBS, SCHOOLS & OTHER ORGANISATIONS REQUIRING LARGER QUANTITIES (1,000 MIN. SA & SB) (100 MIN. ST) MAY SUBMIT THEIR OFFERS NOT LATER THAN 1st FEB. 1971.

## ★ NEW STOCK ITEMS ★

### 1 AMP SILICON RECTIFIERS (MINIATURE PLASTIC CASE)

Type	Price each	Quantity Price
IN4001	50	1/- 10d. 9d.
IN4002	40	1/- 10d. 9d.
IN4003	200	1/3 1/1 11d.
IN4004	400	1/4 1/1 1/8
IN4005	600	2/- 1/8 1/8
IN4006	800	2/8 2/- 2/8
IN4007	1000	3/- 2/8 2/8

### 300mW GLASS SILICON RECTIFIERS Do-7 Case

VOLTAGE RANGE 50-1000V AND PRICE AS FOLLOWS:

VOLTS	1-49	50-99	100up.
50V	9d. each	8d. each	7d. each
100V	10d. ..	9d. ..	8d. ..
200V	11d. ..	10d. ..	9d. ..
400V	1/2 ..	1/1 ..	1/- ..
600V	1/4 ..	1/3 ..	1/2 ..
800V	1/1 ..	1/10 ..	1/9 ..
1000V	2/3 ..	2/2 ..	2/- ..

### GENERAL PURPOSE GERM. PNP POWER TRANSISTORS

Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR: OC25-28-29-30-35-36. NKT401-403-404-405-406-450-451-452-453. TI3027-3028. 2N2504, 2N456A-457A-458A. 2N311-511 A & B. 2G-290-222. ETC.

SPECIFICATION: VCBO 80V VCEO 50V IC 10A PT 30 WATTS HFE 30-170

PRICE	1-24	25-99	100up.
8/8 each	8/- each	7/3 each.	

### GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Coded GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR: 2N3055, BDY20, BDY11.

SPECIFICATION: VCBO 100V. VCEO 60V. IC 15AMPS. PT. 115 WATTS. Hfe 20-100. FT1 MHZ.

PRICE.	1-24	25-99	100+
11/- each	10/- each.	9/8 each.	

### SEMICONDUCTOR HANDBOOK

240 PAGES OF SUGGESTED CIRCUITS—TRANSISTOR OUTLINES AND SEMICONDUCTOR SPECIFICATIONS. INTRODUCTION AND EXPLANATION IN 11 LANGUAGES: ENGLISH, DUTCH, FRENCH, GERMAN, INDONESIAN, SWEDISH, SPANISH, PORTUGUESE, ITALIAN, ARABIAN, SERBO-CROATHIAN. A HANDBOOK FOR ALL SEMICONDUCTOR USERS. (DUTCH PUBLICATION). PRICE 28/6 incl. P. & P.

**SEND ALL ORDERS FOR BY-RETURN SERVICE**



# BI-PAK = LOW COST I.C.'s

BI-PAK Semiconductors now offer you the largest and most popular range of I.C.'s available at these EXCLUSIVE LOW PRICES. TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.



BI-PAK Order No.	Similar Types to:- Description	Price and qty. prices
		1-24 25-99 100 up
BP00 7400N	Quad 2-Input NAND GATE	8/6 5/8 4/8
BP01 7401N	Quad 2-Input NAND Gate—OPEN COLLECTOR	6/6 5/8 4/6
BP04 7404N	HEX INVERTER	6/6 5/8 4/6
BP10 7410N	Triple 3-Input NAND GATE	6/6 5/8 4/6
BP20 7420N	Dual 4-Input NAND GATE	6/6 5/8 4/6
BP30 7430N	Single 8-Input NAND GATE	6/6 5/8 4/6
BP40 7440N	Dual 4-Input BUFFER GATE	6/6 5/8 4/6
BP41 7441N	BCD to decimal decoder and NIT Driver	22/6 20/- 17/8
BP42 7442N	BCD to decimal decode (TTL O/P)	22/6 20/- 17/8
BP50 7450N	Dual 2-Input AND/OR/NOT GATE—expandable	6/6 5/8 4/6
BP53 7453N	Single 8-Input AND/OR/NOT GATE—expandable	6/6 5/8 4/6
BP60 7460N	Dual 4-Input—expandable	6/6 5/8 4/6
BP70 7470N	Single JK Flip-Flop—edge triggered	9/- 8/- 7/-
BP72 7472N	Single Master Slave JK Flip-flop	9/- 8/- 7/-
BP73 7473N	Dual Master Slave JK Flip-flop	10/- 9/- 8/8
BP74 7474N	Dual D Flip-flop	10/- 9/- 8/8
BP75 7475N	Quad Bistable Latch	11/- 10/- 9/6
BP76 7476N	Dual Master Slave Flip-flop with preset and clear	11/- 10/- 9/6
BP83 7483N	Four Bit Binary Adder	26/- 22/6 20/-
BP90 7490N	BCD Decade Counter	22/6 20/- 17/8
BP92 7492N	Divide by 12 4 Bit binary counter	22/6 20/- 17/8
BP93 7493N	Divide by 16 4 Bit binary counter	22/6 20/- 17/8
BP94 7494N	Dual Entry 4 Bit Shift Register	22/6 20/- 17/8
BP95 7495N	4 Bit Up-Down Shift Register	22/6 20/- 17/8
BP96 7496N	5 Bit shift register	24/- 21/- 18/6

Data is available for the above Series of Integrated Circuits in booklet form, price 2/6.

### BRAND NEW... FULL TO MANUFACTURERS' SPECIFICATION

Operational Amplifier, dual-in-line 14 pin package = 8N7209 and similar to MIC709 and ZLD709C.	Price each
	1-24 25-99 100 up
	10/6 9/- 8/-

This is a high performance operational amplifier with high impedance differential inputs and low impedance output.

### TTL INTEGRATED CIRCUITS

Manufacturers "Fall outs"—out of spec. devices including functional units and part functional but classed as out of spec. from the manufacturers very rigid specifications. Ideal for learning about I.C.'s and experimental work, on testing, some will be found perfect.

PAK No.	Price	PAK No.	Price
UIC00 = 5 x 7400N	10/-	UIC73 = 5 x 7473N	10/-
UIC01 = 5 x 7401N	10/-	UIC74 = 5 x 7474N	10/-
UIC02 = 5 x 7402N	10/-	UIC75 = 5 x 7475N	10/-
UIC03 = 5 x 7403N	10/-	UIC76 = 5 x 7476N	10/-
UIC04 = 5 x 7404N	10/-	UIC80 = 5 x 7480N	10/-
UIC05 = 5 x 7405N	10/-	UIC82 = 5 x 7482N	10/-
UIC10 = 5 x 7410N	10/-	UIC83 = 5 x 7483N	10/-
UIC20 = 5 x 7420N	10/-	UIC86 = 5 x 7486N	10/-
UIC40 = 5 x 7440N	10/-	UIC90 = 5 x 7490N	10/-
UIC41 = 5 x 7441N	10/-	UIC92 = 5 x 7492N	10/-
UIC42 = 5 x 7442N	10/-	UIC93 = 5 x 7493N	10/-
UIC51 = 5 x 7451N	10/-	UIC94 = 5 x 7494N	10/-
UIC56 = 5 x 7456N	10/-	UIC95 = 5 x 7495N	10/-
UIC70 = 5 x 7470N	10/-	UIC96 = 5 x 7496N	10/-
UIC72 = 5 x 7472N	10/-	UICX1 = 20 x ASS'D 74's	30/-

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

### DUAL-IN-LINE LOW PROFILE SOCKETS

14 and 16 lead sockets for use with Dual-in-Line Integrated Circuits.

Order No.	Price each
	1-24 25-99 100 up
T8014 14 pin type	7/6 6/- 5/3
T8016 16 pin type	10/- 8/6 7/9

### RTL FAIRCHILD (U.S.A.) I.C.'s

RTL Micrologic Circuits	Qty.	prices each
Epoxy case To-5 temp. range 15°C to 55°C	1-11 12-24 25-99	100 +
µL 900 Buffer	8/- 7/-	8/6 5/8
µL 914 Dual two-input GATE	8/- 7/-	8/6 5/8
µL 923 J-K Flip-Flop	10/8 10/-	9/6 9/8

Full data and circuitry for IC's in Booklet form price 1/8 each.  
µA703E Linear RF-IF AMPLIFIER 11/- 10/- 9/- 8/3  
PLASTIC CASE TO-5 6 lead up to 100 m/cs.

### DTL DIGITAL I.C.'s

DTL dual in-line package.	Price
Type MC844P expandable dual 4-input NAND Power Gate	10/- each
Type MC846P Clocked Flip-Flop	18/- each
Type 882 Triple 3 Input NAND/NOR Gate	10/- each

### FULL DATA SUPPLIED WITH UNITS

Please send all orders direct to our warehouse and despatch department.

**BI-PAK SEMICONDUCTORS**  
P.O. BOX 6, WARE, HERTS.

Postage and packing add 1/-. Overseas add extra for Airmail. Minimum order 10/-.. Cash with order please.

# VALUE ALL THE WAY

## LINEAR INTEGRATED CIRCUITS

### BI-PAK MONOLITHIC AMPLIFIERS (TO-5 8 lead)

- BP709C, Operational amplifier, 15/- each.  
BP701C, Operational amplifier with Zener output, 12/6 each.  
BP702C, Operational amplifier (with direct output), 12/6 each.  
BP501, Wide band amplifier, 18/- each.  
BP21, Logarithmic wide band amp., 14/- each.  
BP20(C), General purpose amplifier (TO-5 8 lead), (voltage or current amp.), 12/6 each.  
1.C, Operational Amplifier with Zener output.  
Type 701C. Ideal for P.E. Projects. 8 Lead TO-5 case. Full data.

Our price **12/6** each 5 off 11/- each. Large Qty. Prices quoted for.

### SIL. G.P. DIODES

- 300mV 100 . . . 10/-  
10PIV (Min.) 30 . . . 30/-  
Sub-Min. 3000 . . . 25/-  
Full Tested 1,000 . . . \$9  
Ideal for Organ Builders.

### OA200/OA202

- Each 1/9  
SILICON Diodes  
35 + 1/6  
100 + 1/3  
500 + 1/1

**★ TRADE ★**  
SEND FOR YOUR FREE CATALOGUE

### MULLARD I.C. AMPLIFIERS

- TAA243, Operational amplifier, 70/- each.  
TAA263, Linear A.F. amplifier, 15/- each.  
TAA293, General purpose amplifier, 19/6 each.

### CA3020 RCA (U.S.A.) LINEAR INTEGRATED CIRCUITS

- Amlfo Power Amplifier, 30/- each.

### OTHER MONOLITHIC DEVICES

- B13D1 Silicon Unilateral switch 10/- each.  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

### Silicon Microwave Diodes—Sylvania (U.S.A.)

- 1N218 and 1N218R matched pair 8/- Band mixer. Max. overall noise figure 13.7dB at 3,000mc/s. Brand new and boxed. Clearance Price 6/- pair.

### EX-EQUIPMENT MULLARD

- AF117 transistors. Large cut 4 lead type. Leads cut short but still usable, real value at 15 for 10/-.

## ADI161 NPN

## ADI162 PNP

MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.

For mains driven output stages of Amplifiers and Radio receivers.  
OUR LOWEST PRICE OF 12/6 PER PAIR

HIGH POWER SILICON PLANAR TRANSISTORS. TO-3.

FERRANTI ZT1487

NPN VCB90 1-6A

TT. 1M/cs

VECF40 Ptot. 75W

VER18 HFE15-45

PRICE 6/- EACH

2H3055 115 WATT SIL. POWER NPN

OUR PRICE 12/6 EACH

### FULL RANGE OF ZENER DIODES

VOLTAGE	RANGE
2-33V.	400mV (DO-7 Case) 2/6 ea. 1/1W (Top-Hat) 3/8 ea. 10W (No-10 Stud) 5/- ea. All fully tested 5% tol. and marked. State voltage required.

### BRAND NEW TEXAS GERM. TRANSISTORS

Matched and Guaranteed.

Code No. Q4VPT

T1 8 2G371A OC71

T2 8 2G374 OC75

T3 8 2G374A OC81D

T4 8 2G381A OC81

T5 8 2G382P OC82

T6 8 2G344A OC44

T7 8 2G345A OC45

T8 8 2G378 OC78

T9 8 2G309A 2N1302

T10 8 2G417 AF117

All 10/- each pack

### 2N2080 NPN SIL. DUAL TRANS. CODE D1899

TEXAS. Our price 5/- each.

### 120 VCB NIXIE DRIVER TRANSISTOR.

8 pin. B8X21 & C407. 2N1893

FULLY TESTED AND CODED N D120. 1-24 3/6 each. TO-5 N.P.N. 25 up 3/- each.

### Sil. trans. suitable for P.E. Organ. Metal TO-18

Egypt. ZTY300 1/- each. Any Qty.

### FREE

One 10/- Pack of your own choice free with orders valued \$4 or over.

AF239 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 900 MHz. USE AS REPLACEMENT FOR AF139-AF196. 100's OF OTHER USES IN VHF OUR SPECIAL LOW PRICE: 1-24 7/6 each. 25-99 6/9 each 100 + 6/- each.

### FET'S

- 2N 3819 . . . . . 7/-  
2N 3820 . . . . . 18/8  
MPP102 . . . . . 8/-

### LOW COST F.E.T.'s

Fully Tested, Guaranteed Peranctors equnit. to 2N3819, MPP102, 2N-5459, 1-24 7/6 each; 25-99 6/3 each; 100 up 5/6 each. Coded FE19. Full data sent. TO-72 case.

### CADMIUM CELLS

ORP12 8/6

ORP60, ORP51 8/- each

### PHOTO TRANS.

OCPT1 Type. 8/6

## KING OF THE PAKS

## SUPER PAKS

Unequaled Value and Quality

## NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back. Pak No.

- U1 120 Glass Sub-min. General Purpose Germanium Diodes . . . . . 10/-
- U2 60 Mixed Germanium Transistors AF/RF . . . . . 10/-
- U3 75 Germanium Gold Bonded Diodes sim. OA5, OA47 . . . . . 10/-
- U4 40 Germanium Transistors like OC81, AC128 . . . . . 10/-
- U5 60 200mA Sub-min. Sil. Diodes . . . . . 10/-
- U6 30 Silicon Planar Transistors NPN sim. B8Y95A, 2N706 . . . . . 10/-
- U7 16 Silicon Rectifiers Top-Hat 760mA up to 1,000V . . . . . 10/-
- U8 50 Sil. Planar Diodes 250mA OA/200/202 . . . . . 10/-
- U9 20 Mixed Volts 1 watt Zener Diodes . . . . . 10/-
- U11 30 PNP Silicon Planar Transistors TO-5 sim. 2N1132 . . . . . 10/-
- U13 30 PNP-NPN Sil. Transistors OC290 & 2N104 . . . . . 10/-
- U14 150 Mixed Silicon and Germanium Diodes . . . . . 10/-
- U15 25 NPN Silicon Planar Transistors TO-5 sim. 2N697 . . . . . 10/-
- U16 10 3-Amp Silicon Rectifiers Stud Type up to 1000 PIV . . . . . 10/-
- U17 30 Germanium PNP AF Transistors TO-5 like ACY 17-22 . . . . . 10/-
- U18 8 6-Amp Silicon Rectifiers BYZ13 Type up to 600 PIV . . . . . 10/-
- U19 25 Silicon NPN Transistors like BC105 . . . . . 10/-
- U20 12 1.5-amp Silicon Rectifiers Top-Hat up to 1,000 PIV . . . . . 10/-
- U21 30 A.F. Germanium alloy Transistors 2G300 Series & OC71 . . . . . 10/-
- U23 30 Mads' like MAT Series PNP Transistors . . . . . 10/-
- U24 20 Germanium 1-amp Rectifiers GJM up to 300 PIV . . . . . 10/-
- U25 25 300Mc/s NPN Silicon Transistors 2N708, B8Y27 . . . . . 10/-
- U26 30 Fast Switching Silicon Diodes like 1N914 Micro-min . . . . . 10/-
- U28 Experimenters' Assortment of Integrated Circuits, untested. Gates, Flip-Flops, Registers, etc., 8 Assorted Pieces . . . . . 20/-
- U29 10 1 amp SCR'S TO-6 can up to 600 PIV CR51/25-600. . . . . 20/-
- U31 20 Sil. Planar NPN trans. low noise AUN 2N3707 . . . . . 10/-
- U32 25 Zener diodes 400mW D07 case mixed Volts, 3-18 . . . . . 10/-
- U33 15 Plastic case 1 amp Silicon rectifiers 1N4000 series. . . . . 10/-
- U34 30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4 . . . . . 10/-
- U35 25 Sil. Planar trans. PNP TO-18 2N2906 . . . . . 10/-
- U36 25 Sil. Planar NPN trans. TO-5 BFY505/1/52 . . . . . 10/-
- U37 30 Sil. alloy trans. 80-2 PNP. OC200 28322 . . . . . 10/-
- U38 20 Fast Switching Sil. trans. NPN. 400mc/s 2N3011 . . . . . 10/-
- U39 30 RF Germ. PNP trans. 2N1303/5 TO-5 . . . . . 10/-
- U40 10 Dual trans. 6 lead TO-5 2N2060 . . . . . 10/-
- U41 25 RF Germ. trans. TO-1 OC45 NKT72 . . . . . 10/-
- U42 10 VHF Germ. PNP trans. TO-1 NKT667 AF117 . . . . . 10/-

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked

### NEW LOW PRICED TESTED S.C.R.'s

IA	3A	7A	16A	30A		
(TO-5)	(TO-6)	(TO-48)	(TO-48)	(TO-48)		
case)	case)	case)	case)	case)		
PIV	each	each	each	PIV each		
50	4/6	5/-	9/6	10/6	25	20/-
100	5/-	6/6	10/6	12/6	50	23/-
200	7/6	7/6	11/6	15/-	100	28/-
400	8/6	9/6	12/6	18/6	200	32/-
600	10/6	11/6	15/6	25/-	400	35/-
800	12/6	14/-	18/-	30/-	600	80/-

### 2A POTTED BRIDGE RECTIFIERS. 200V 10/-

### DIACS FOR USE WITH TRIACS

BR100 . . . . . 7/6 each

### PRINTED CIRCUITS EX-COMPUTER

Packed with semiconductors and components 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards 10/-, Plus 2/- P. & P.

PLEASE NOTE. To avoid any further increased Postal Charges to our Customers and enable us to keep our "By Return Postal services" which is second to none, we have re-organised and streamlined our Despatch Order Department and we now request you to send all your orders together with your remittance, direct to our Warehouse and Despatch Department, postal address: BI-PAK SEMICONDUCTORS, Despatch Dept., P.O. BOX 4, WARE, HERTS. Postage and packing still 1/- per order. Minimum order 10/-

### SIL. RECTS. TESTED

PIV	750mA3A	10A 30A
50	1/-	2/9 4/3 8/6
100	1/3	3/3 4/6 15/-
200	1/9	4/- 4/9 20/-
300	2/3	4/6 8/6 25/-
400	2/6	5/6 7/6 25/-
500	3/-	6/- 8/6 30/-
600	3/3	6/9 9/- 37/-
800	3/6	7/6 11/- 40/-
1000	5/-	9/3 12/6 50/-
1200	6/6	11/6 15/-

### TRIACS

VWOM	2A	6A	10A
(TO-18)	(TO-18)	(TO-18)	(TO-18)
100	14/-	15/-	22/6
200	17/6	20/-	28/-
400	20/-	24/-	35/-
VWOM - Blocking voltage in either direction.			

### LUCAS 35A SIL. RECTS. Branded. 400 PIV. Special Price, stud type, flying lead, 22/6 each.

### UNIJUNCTION

- UT46. Eqv. 2N2646, Eqv. T1843. BEN3000 5/8 each, 25-99 5/-, 100 UP 4/-.

### NPN SILICON PLANAR

- BC107/8/9, 2/- each; 50-99, 1/10; 100 up, 1/8 each; 1,000 off, 1/4 each. Fully tested and coded TO-18 case.

### SILICON HIGH VOLTAGE RECTIFIERS

- 10 Amp 3-K.V. 3900 P.I.V. Stud Type with Flying Leads, 18/- each.

## QUALITY-TESTED PAKS

- 6 Matched Trans. OC44/46/81/8110 . . . . . 10/-
- 20 Red Spot AF Trans. PNP . . . . . 10/-
- 16 White Spot RF Trans. PNP . . . . . 10/-
- 5 Silicon Rects. 3 A 100-400 PIV . . . . . 10/-
- 2 10 A Silicon Rects. 100 PIV . . . . . 10/-
- 2 OC1 140 Trans. NPN Switching . . . . . 10/-
- 1 12 A SCR 100 PIV . . . . . 10/-
- 3 Sil. Trans. 28303 PNP . . . . . 10/-
- 3 200 Mc/s Sil. Trans. NPN BS126/27 . . . . . 10/-
- 3 Zener Diodes 1W 33V 5% Tol. . . . . 10/-
- 4 High Current Trans. OC42 Egv. . . . . 10/-
- 2 Power Transistors 1 OC26 1 OC35 . . . . . 10/-
- 5 Silicon Rects. 400 PIV 250mA . . . . . 10/-
- 4 OC75 Transistors . . . . . 10/-
- 1 Power Trans. OC20 100V . . . . . 10/-
- 10 OA202 Sil. Diodes Sub-min. . . . . 10/-
- 2 Low Noise Trans. NPN 2N295/30 . . . . . 10/-
- 1 Sil. Trans. NPN VCB 100 ZT96 . . . . . 10/-
- 8 OA81 Diodes . . . . . 10/-
- 4 OC72 Transistors . . . . . 10/-
- 4 OC77 Transistors . . . . . 10/-
- 4 Sil. Rects. 400 PIV 600mA . . . . . 10/-
- 6 GET884 Trans. Eqv. OC44 . . . . . 10/-
- 5 GET883 Trans. Eqv. OC45 . . . . . 10/-
- 2 2N708 Sil. Trans. 300Mc Gain . . . . . 10/-
- 3 GT31 LF Low Noise Germ. Trans. . . . . 10/-
- 6 1N914 Sil. Diodes 75 PIV 75mA . . . . . 10/-
- 8 OA86 Germ. Diodes Sub-min. IN69 . . . . . 10/-
- 3 NPN Germ. Trans. NKT773 Eqv. . . . . 10/-
- 2 OC22 Power Trans. Germ. . . . . 10/-
- 2 OC25 Power Trans. Germ. . . . . 10/-
- 4 AC128 Trans. PNP High Gain . . . . . 10/-
- 4 AC127/128 Comp. pair PNP/NPN . . . . . 10/-
- 3 2N1307 PNP Switching Trans. . . . . 10/-
- 7 CG62H Germ. Diodes Eqv. OA71 . . . . . 10/-
- 3 AF116 Type Trans. . . . . 10/-
- 12 Assorted Germ. Diodes Marked . . . . . 10/-
- 4 AC125 Germ. PNP Trans. . . . . 10/-
- 4 Silicon Rects. 100 PIV 750mA . . . . . 10/-
- 3 AF117 Trans. . . . . 10/-
- 7 OC81 Type Trans. . . . . 10/-
- 3 OC717 Trans. . . . . 10/-
- 5 2N2926 Sil. Epoxy Trans. . . . . 10/-
- 7 OC71 Type Trans. . . . . 10/-
- 4 GT701 Sil. Trans. Texas . . . . . 10/-
- 2 10 A 600 PIV Sil. Rects. 1845R . . . . . 10/-
- 3 BC108 Sil. NPN High Gain Trans. . . . . 10/-
- 1 2N910 NPN Sil. Trans. VCB 100 . . . . . 10/-
- 2 1000 PIV Sil. Rect. 1.5 A R63310 AF . . . . . 10/-
- 3 B8Y96A Sil. Trans. NPN 200Mc/s . . . . . 10/-
- 1 OC200 Sil. Trans. . . . . 10/-
- 4 GT660 Low Noise Germ. Trans. . . . . 10/-
- 1 AF139 PNP High Freq. Trans. . . . . 10/-
- 3 NPN Trans. 1KT141 & 2MT140 . . . . . 10/-
- 4 Mads' 2 MAT101 & 2MAT120 . . . . . 10/-
- 3 Mads' 2 MAT101 & 1 MAT121 . . . . . 10/-
- 4 OC4 Germ. Trans. AF . . . . . 10/-
- 3 AC127 NPN Germ. Trans. . . . . 10/-
- 1 2N3906 Sil. PNP Trans. Motorola . . . . . 10/-
- 2 Sil. Power Rects. BYZ13 . . . . . 18/-
- 1 Sil. Power Trans. NPN 100Mc/s. TK201A . . . . . 18/-
- 2 2N1132 PNP Epitaxial Planar Sil. . . . . 18/-
- 3 2N697 Epitaxial Planar Trans. Sil. . . . . 18/-
- 4 Germ. Power Trans. Eqv. OC16 . . . . . 18/-
- 1 Unijunction Trans. 2N2646 . . . . . 18/-
- 2 Sil. Trans. 200Mc/s 60Veb ZTR8/84 . . . . . 18/-
- 20 NKT Trans. AF. RP. VHF. Coded + Eqv. List . . . . . 10/-
- 2 2N2712 Sil. Epoxy Planar HFE225 . . . . . 18/-
- 8 BY100 Type Sil. Rects. . . . . 20/-
- 25 Sil. and Germ. Trans. Mixed, all marked, New . . . . . 30/-

### SEMICONDUCTORS FOR "P.E." 50+50AMP.


TYPE	EACH	TYPE	EACH
2N1613	4/6	1N914	1/-
2N3055	12/6	OA200	1/-
2N3703	3/-	BFY51	3/6
2N3704	3/6	BVZ13	4/6
2N3707	3/9	40362	14/6
2N3819	8/-	22V 11W Zener	3/8

CIRO No. 388-7006

63A High Street WARE Herts.

# KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

# South East London's

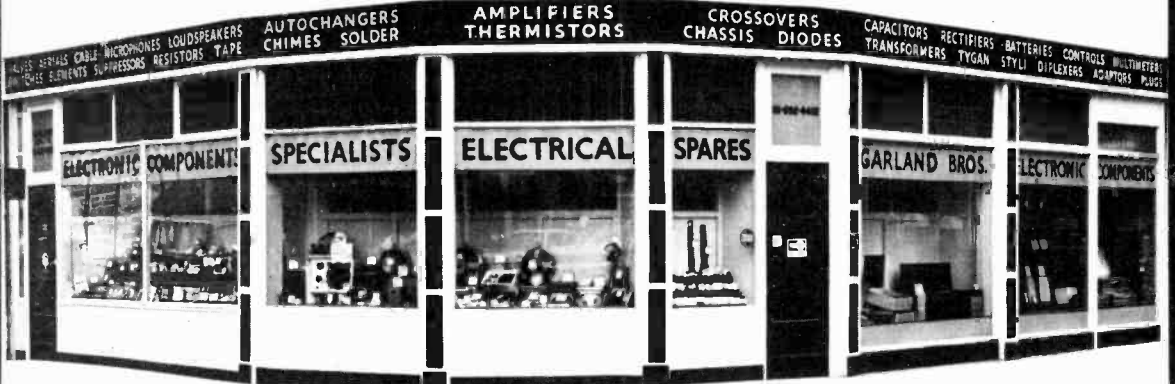

## leading components store

OPEN DAILY  
9.15 a.m. - 6 p.m.  
(Closed all day  
Thursday)


# Garland Bros. Ltd.

TELEPHONE  
01-692 4412

DEPTFORD BROADWAY (Corner of Brookmill Road)  
LONDON, S.E.8
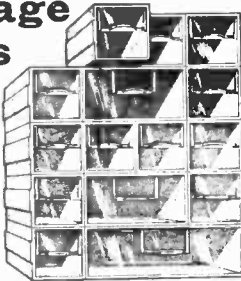
### NEW! HANDY! TIDY! multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

A PLACE  
FOR  
EVERYTHING  
IN ITS  
PLACE!



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

#### BUY AT TRADE PRICES!

**SINGLE UNITS** (5ins x 2ins x 2ins)  
Usually 2 1/11 each, **OUR PRICE:** 27/- DOZEN  
**DOUBLE UNITS** (5ins x 4ins x 2ins)  
Usually 4/11 each, **OUR PRICE:** 45/- DOZEN

#### PLUS QUANTITY DISCOUNTS!

Order £15 and over DEDUCT 1/- in the £  
Orders £10 and over DEDUCT 1/6 in the £  
Orders £20 and over DEDUCT 2/- in the £

**PACKING/POSTAGE CARRIAGE:** Add 6/- to all orders under £5. Orders £5 and over, packing/postage carriage free.

**QUOTATIONS FOR LARGER QUANTITIES**  
ALL PRICES TAX PAID

**IVORYET LIMITED** (Dept. PE2) 31 ALBERT RD.  
HENDON, LONDON, NW4

### THE NEW **JULIETTE** MPR 3065

is a high quality  
**COMMUNICATIONS  
RECEIVER**

(replaces NA 5018A)  
Recommended Price  
£42 0 0

Our Price **36 Gns.**



(Cash only) plus 9/- p. & p. Complete with standard batteries and earpiece. BFO (optional extra) add 35/-.

**IT NOT ONLY RECEIVES** Aircraft, Shipping (VHF & SW), Taxis, Ambulances, Fire Service, T.V. Sound, Hams, Gas and Electric Boards, Public Services and many other radio telephone mobiles—**BUT ALSO** Classical Music, Pop and all that Jazz.

**TURN ON AND TUNE IN!!!** The MPR 3065 is a communications receiver and entertainment source in one neat, transistorised, portable package. It keeps aircraft, shipping, RT mobiles, FM and AM broadcasts at your fingertips. Features a colour coded illuminated tuning dial and band selector, AFC, squelch, BFO (optional extra), large speaker. Ext. Aerial Socket. Works off mains or batteries. Size: 10 1/2 x 7 1/2 x 4 inches. 22 Transistors/Diodes.

**FREQUENCIES:** Medium Wave, 540-1600 Kcs.; Marine, 1.6-4.6 Mcs.; FM/VHF, 88-108 Mcs.; Aircraft, 108-136 Mcs. (Military, Civil and Ground control); High VHF/PB, 146-176 Mcs. (Commercial and Industrial RT mobiles). Availability of mobile transmissions depend on operators in each area.

Enclose 5d. stamp for reply. Trade supplied  
**STOCKTON PARTNERS (Dept. P.E.)**  
Importers and Distributors  
Brighowgate, Grimsby, Lincs.  
Tel. 0472 64196/58815

### OSMABET LTD.

We make transformers amongst other things

#### MAINS TRANSFORMERS

Prim 200/240V a.c. TX1 425-0-425V 250 mA, 6.3V 4A CT, 6.3V 4A CT, 0-5-6V 3A, 135/-; TX2, 250-0-250V 150 mA, 6.3V 4A, CT, 0-5-6.3V 3A, 78/8; TX3 300-0-300V 250 mA, 6.3V 2A, CT, 6.3V 2A, 6.3V 1A, 78/8; TX8 250-0-250V 65 mA, 6.3V 1.5A, 42/-; MT1 200V 30 mA, 6.3V 1A, 24/-; MT2 230V 45 mA, 6.3V 1.5A, 28/8; MT2A 250V 60 mA, 6.3V 2A, 37/8; MT3 Prim 110/240V Sec 250V 100 mA, 6.3V 2A, 45/-.

#### MULTIVOLT TRANSFORMERS

Prim 200/240V a.c. OMT4/1 one tapped sec: 5-20-30-40-60V giving 5-10-15-20-25-30-35-40-55-60, 10-0-10, 20-0-20, 30-0-30V a.c. 1A, 45/-; ditto transformer 2A OMT4/2, 87/8; OMT5/1 one tapped sec: 40-60-60-80-90-100-110V, giving 10-20-30-40-50-60-70-80-90-100-110V, 10-0-10, 20-0-20, 30-0-30, 40-0-40, 50-0-50V a.c. 1A, 87/8.

#### LOW VOLTAGE TRANSFORMERS

Prim 200/240V a.c.: 6.3V 1.5A, 16/8; 3A, 20/-; 6A CT, 34/-; 12V 1.5A, 21/-; 3A CT, 34/-; 6A CT, 45/-; 18V 1.5A CT, 28/8; 24V 1.5A CT, 34/-; 3A CT, 56/8; 5A, 75/-; 8A, 112/8; 12A, 165/8.

#### MIDGET RECTIFIER TRANSFORMER

For FW rectification, size 12 x 2 x 1 1/2 in, Prim 200/240V a.c., output PPT1 9-0-9V 0.3A, PPT2 12-0-12V 0.25A, PPT3 20-0-20V 0.15A, 22/6 each.

**O/P TRANSFORMERS, P.P.**, sec. tapped 3-7-5-15 ohms, A-A 6-6K 30 watts (KT66, etc.) 78/8; 50 watt 3K (EL34, KT88, etc.) 135/-; 100 watt 3K (EL34, KT88, etc.) 225/-.

**LOUDSPEAKERS** Ex-equipment, perfect, 3 ohms only 5ins, at 7/6 each, plus 2/- min p.p.

#### LOUDSPEAKERS, HI-FLI, P.A., GUITARS, ETC.

New, boxed, famous makes: 25W, 110/-; 35W, 150/-; 60W, 200/-; 80W, 240/-; 100W, 400/-; E.M.I. 13 x 8in, 10W, 3, 8 and 15 ohms, 45/- each; 13 x 8in, HI-FLI, fitted two tweeters, crossover network, 3, 8 and 15 ohms, 80/- each.

#### BULK TAPE ERASERS

Instant erasure of magnetic tape, demagnetizing of tape heads. 300/240V a.c. 47/8 post 2/6, leaflet S.A.E.

#### LT FLUORESCENT LIGHTING

12V fittings with tube, 8 watt 75/-; 13 watt 120/-; Inverters 12V, 20 watt 150/-; twin 20 or single 40 watt 180/-; twin 30 or single 50 watt 220/-; Extensive range. List S.A.E.

Carriage extra all orders

S.A.E. ALL ENQUIRIES PLEASE. MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 8YG  
Tel. 958 9314

# COMPLETE STEREO SYSTEM

FOR ONLY

# 39 GNS

CARRIAGE 35/-



**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends: Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required £14.19.6. Carr. 7/6). **Now Available MATCHING F.M. TUNER 21gns.**

## PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.

**PREMIER PRICE 45 Gns. Carr. 36/-**


## MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in streamline cabinets.

	Model 19-520	Model 19-542
Specifications	19 transistors, 12 diodes, 2 varistors	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz FM Stereo Multiplex AM 535-1635 kHz	FM 88-108 MHz FM Stereo Multiplex AM 535-1605 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency Response	50-17,000 Hz	35-20,000 Hz
Power Output	2 1/2 watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Ceramic phono	Magnetic/Ceramic phono and aux.
Speaker Impedance	4-8 ohm	8 ohm
Controls	Power on/off, Volume, tone, balance, tuning, AFC. Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC. Stereo indicator
Function	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	13" 8 1/2" 2 1/2"	16 1/2" 9 1/2" 3 1/2"
PRICE	29 GNS. Carr. & Ins. 10/-	42 GNS. Carr. & Ins. 10/-



MODEL 19-520

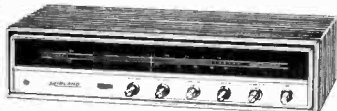

MODEL 19-542

## TELETON SAQ203E STEREO AMPLIFIER



A small but powerful amplifier designed for stereo hi-fi reproduction. 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal), Tuner and Auxiliary. Tape Record output. Controls: Volume, Balance, Bass, Treble, Stereo/Mono slide switch. Stereo headphone socket. Attractive oiled walnut cabinet with brushed aluminium front panel. List Price £28.7.0. **PREMIER PRICE 22 Gns. P. & P. 10/-**

## E.M.I. 13 x 8 in. HI-FI SPEAKERS



Fitted two 2 1/2 in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new.

**69/6 P. & P. 7/6**



## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2 1/2 in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

**49/6 P. & P. 5/-**

STEREO STETHOSCOPE SET Low imp. 25/- P. & P. 2/-  
MONO STETHOSCOPE SET Low imp. 10/6 P. & P. 2/-

## VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 x 3 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phonoplug output. Attractive teak wood grain finish case.



**Mono Model 59/6 Stereo Model 69/6 P. & P. 2/6**

**POCKET SIZE MULTI-TESTER** With wide angle, jewelled meter. Movement, ceramic long-life, low-loss switching, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C.  
**19 Ranges:** 0-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-50µA-250µA-2500µA D.C. 0-6000 ohms-6 megohms, 10µf-0-001 mfd-1 mfd. -20 to +22dB. Complete battery, test lead and instructions.




**£4.19.6 P. & P. 3/6**

## PREMIER STEREO SYSTEM "FOUR"

Teleton SAQ203E Amplifier (as above)	£23.2.0
Garrard SP25	£11.19.6
Bure MSD	£6.19.6
Teak base and cover	£5.10.0
Pair of Hi-Fi Enclosures fitted E.M.I. Speakers	£26.5.0
<b>Total cost if purchased separately</b>	<b>£73.16.0</b>

**PREMIER PRICE 65 GNS. Carr. 35/-**

## SPECIAL OFFER!

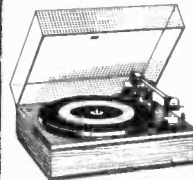

Garrard SP25 Mk. II Single Record Player. Fitted Audio Technica AT66 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover. Total list Price over £24. **PREMIER PRICE 18 Gns. P. & P. 10/-**



## TAPE CASSETTES

C60 (60 min.)	7/6 3 for 21/-
C90 (90 min.)	12/6 3 for 36/-
C120 (120 min.)	17/6 3 for 51/-

P. & P. 1/-

All cassettes can be supplied with library cases at 6d extra each.



## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped attractively boxed.

LP3 3" 250'	P.V.C.	5/6	LP8 5 1/2" 1200'	P.V.C.	12/6
TT3 3 1/2" 450'	POLYESTER	7/6	DT5 5 1/2" 1800'	POLYESTER	22/6
DT3 3 1/2" 600'	POLYESTER	11/6	TT5 5 1/2" 2400'	POLYESTER	37/6
SP5 5" 600'	P.V.C.	8/6	SP7 7" 1200'	P.V.C.	12/6
LP5 5" 900'	P.V.C.	10/-	LP7 7" 1800'	P.V.C.	15/-
DT5 5" 1200'	POLYESTER	15/-	DT7 7" 2400'	POLYESTER	25/-
			TT7 7" 3600'	POLYESTER	50/-

**TAPE SPOOLS** 3" 1 1/2", 5", 5 1/2", 7" 1 1/2".  
Post and Packing 3" 1 1/2", 5", 5 1/2", 7" 1 1/2". (3 reels and over Post Free.)

# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



# New - a 5lb. oscilloscope for £56 - generous h. p. terms too !



Meteronic's new oscilloscope is unique. Portable enough to carry around anywhere. Inexpensive enough for anyone to afford. Tough and long-lasting—with a year's guarantee. No wonder several top TV rental companies are already using this brilliant British design!

Solid-state, it has a DD-4.5 MHz bandwidth at 50mV/div. All this is compressed into a compact 8 x 6 x 4½ inch plastic-coated steel case, and weighs just 5 lbs.

#### H.P. Terms

For just £2 extra, you can spread payments for your oscilloscope over a yearly period. You put £22 down—and your oscilloscope will be dispatched immediately. You then pay £3 per month for 12 months.

To order—or for the detailed specification, complete and post this coupon now.


To: Meteronic Ltd.,  
Birchen Napps Platt,  
Borough Green,  
Nr. Sevenoaks, Kent.

- Please send me a detailed specification by return of post.  
 Please send me hire purchase forms and a specification sheet.  
I enclose a cheque/money order for £..... Please send.....  
oscilloscope(s) immediately.

Name.....

Address.....

Tel.....

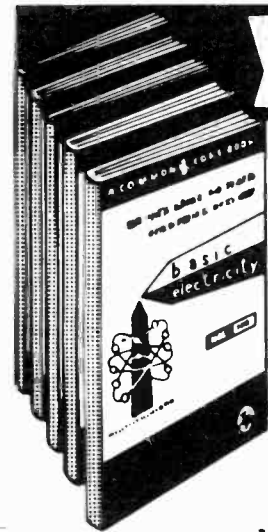

## YOURS FREE FOR 7 DAYS

### The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

**TO TRY IT, IS TO PROVE IT**

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

#### WHAT READERS SAY

‘... carefully written ...’

... I am very satisfied with these carefully written and well expressed manuals ... *A.W., Shanklin.*

‘... valuable assistance ...’

... Your valuable assistance has enabled me to find a good position as a Radio and TV Engineer ... *D.S., Bristol.*

‘... they are invaluable ...’

... I find that as a base for a course in Electronics they are invaluable and I have yet to find anything even to approach the same standard ... *H.N., Rotherham.*

**A TECH-PRESS PUBLICATION**

**POST NOW FOR THIS OFFER !!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts: **BASIC ELECTRICITY 90/-**. Cash Price or Down Payment of 20/- followed by 4 fortnightly payments of 20/- each. **BASIC ELECTRONICS 105/-**. Cash Price or Down Payment of 20/- followed by 5 fortnightly payments of 20/- each. This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

**BASIC ELECTRICITY**

**BASIC ELECTRONICS**

Prices include Postage and Packing.

Signature .....

(If under 18 signature required of parent or guardian)

NAME .....




BLOCK LETTERS

FULL POSTAL

ADDRESS .....



# Project 60

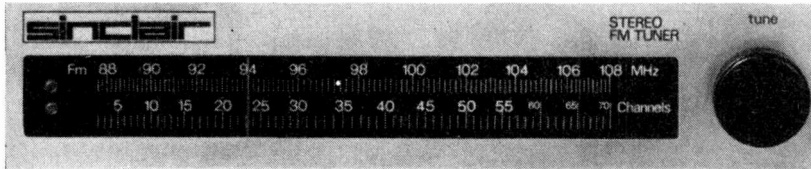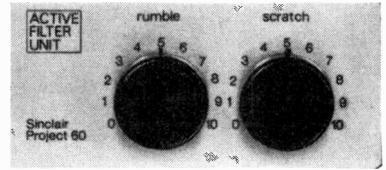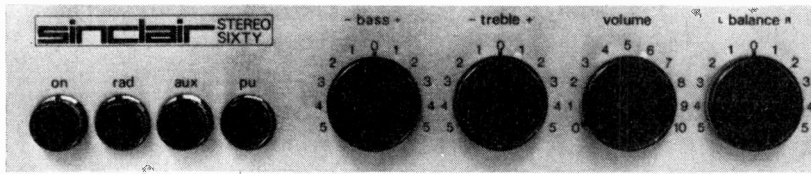

the world's most advanced high fidelity modules

With the introduction of an entirely new and original high fidelity stereo F.M. tuner, the Project 60 range can be said at this stage to be complete. It offers the constructor a most attractive choice of modular arrangements whereby a high fidelity system can be selected to suit the user's personal requirements. Equally, it is possible to use any Project 60 modules separately or partially grouped and so benefit greatly from the flexibility in use these modules afford. The chart below shows some of the most popular applications for constructors to assemble. The Project 60 manual (free with the modules) suggests others as well and its 48 pages are packed with valuable information. The new tuner, for example can be used with any good high fidelity system as well as Project 60.

Project 60 now falls into four interdependent groups: - 1. The Z.30 and Z.50 amplifiers which have only 0.02% distortion at all output levels and are useful in a wide variety of other applications. 2. The control units comprising the Stereo 60 preamp and control unit and the Active Filter Unit (A.F.U.) with which both high pass and low pass filtering can be introduced between control unit and power amplifiers. 3. The Stereo F.M. tuner as described opposite; and 4. The power supply units PZ.5,

PZ.6 and PZ.8. For most requirements when using Z.30 power amplifiers, the PZ.5 will be perfectly adequate; if low efficiency (high quality) loud speakers are used, the PZ.6 stabilised power supply unit will be used. The PZ.8 will be needed with Z.50s which can be used for any Project 60 system.

Project 60 modules incorporate some of the most advanced circuitry in the world to achieve unsurpassed standards of high fidelity and modern manufacturing techniques enable these modules to be sold at exceptionally attractive prices. Assembling the modules requires no skill or previous experience since the manual supplied with the modules explains clearly how everything can be done with nothing more than the simplest of domestic tools.

#### Project 60 manuals

How to assemble and use Project 60 modules to best advantage in the above and other applications will be found in the fully descriptive Project 60 manual included with Project 60 systems. This 48 page manual is available separately, price 2/6d including postage.

System	The Units to use	In conjunction with	Cost of Units	+ Project 60 tuner
A Car Radio	Z.30	Existing car radio, Sinclair Micromatic	89/6	
B Simple battery powered record player	Z.30	Crystal pick-up, 12V or more battery supply and volume control	89/6	
C Mains powered record player	Z.30 and PZ.5	Crystal or ceramic P.U. Volume control etc.	£9.9.0	£34.9.0
D 20+20 watts R.M.S. stereo amplifier for most needs	Two Z.30s, Stereo 60 and PZ.5	Crystal, ceramic or magnetic P.U., most dynamic speakers, F.M. tuner etc.	£23.18.0	£48.18.0
E 20+20 watts R.M.S. stereo amplifier for use with low efficiency (high performance) speakers	Two Z.30s, Stereo 60 and PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc All dynamic speakers	£26.18.0	£51.18.9
F 40+40 watts R.M.S. de-luxe stereo amplifier	Two Z.50s, Stereo 60 PZ.8 and mains transformer	As for E	£32.17.6	£57.17.6
G Outdoor public address system	Z.50	Microphone, up to 4 P.A. speakers, 12V car battery with converter, or 45V d.c., controls	£5.9.6	
H Indoor P.A.	One Z.50, PZ.8 and mains transformer	Microphone, guitar, heavy duty speakers etc., controls	£17.8.6.	
J High pass and low pass filters	A.F.U.	D, E or F as above	£5.19.6	

# sinclair

Sinclair Radionics Limited, London Road, St. Ives, Huntingdonshire  
Telephone: St. Ives (04806) 4311



## Z.30 & Z.50 power amplifiers

The Z.30 together with the Z.50 are both of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use the Z.30 or Z.50 power amplifiers in your Project 60 system will depend on personal preference, but they are the same physical size and may be used with other units in the Project 60 range equally well. For operating from mains, for the Z.30 use PZ.5 for most domestic requirements, or PZ.6 if you have very low efficiency loudspeakers. For Z.50, use the PZ.8 described below.

### SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).

#### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms, using 35V: 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms from 40 volts: 30 watts R.M.S. into 8 ohms, using 50 volts.

**Frequency response** 30 to 300,000 Hz  $\pm$  1dB

**Distortion** 0.02% into 8 ohms

**Signal to noise ratio** better than 70dB unweighted

**Input sensitivity** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size  $3\frac{1}{2} \times 2\frac{1}{4} \times \frac{1}{2}$  ins.



Z.50


Z.30

**Z.30**  
Built, tested and guaranteed with circuits and instructions manual  
**89/6**

**Z.50**  
Built, tested and guaranteed with circuits and instructions manual  
**109/6**
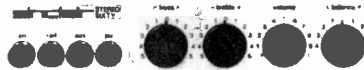
## Stereo 60 pre amp/control unit

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.



### SPECIFICATIONS

● Input sensitivities – Radio – up to 3mV. Mag. p.u. – 3mV: correct to R.I.A.A. curve  $\pm$  1dB: 20 to 25,000Hz. Ceramic p.u. – up to 3mV: Aux. – up to 3mV.

● Output – 250mV.

● Signal-to-noise ratio – better than 70dB.

● Channel matching – within 1dB.

● Tone controls – TREBLE +15 to -15dB at 10kHz: BASS +15 to -15dB at 100Hz.

● Front panel – brushed aluminium with black knobs and controls.


● Size  $8\frac{1}{2} \times 1\frac{1}{2} \times 4$  ins.

Built, tested and guaranteed **£9.19.6**
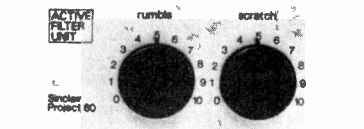
## Active Filter Unit

For use between Stereo 60 unit and two Z.30s or Z.50s, the Active Filter Unit matches the Stereo 60 in styling and is as easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The Sinclair A.F.U. is suitable also for use with any other amplifier system.

Two stages of filtering are incorporated – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (-3dB)



variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Filter slope, both sections 12dB per octave. Distortion at 1kHz (35V supply) 0.02% at rated output.

Built, tested and guaranteed **£5.19.6**

## Power Supply Units

The units below are designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 power supply unit to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


**PZ-5** 30 volts un stabilised **£4.19.6**

**PZ-6** 35 volts stabilised **£7.19.6**

**PZ-8** 45 volts stabilised

(less mains transformers) **£5.19.6**


**PZ-8** mains transformer **£5.19.6**

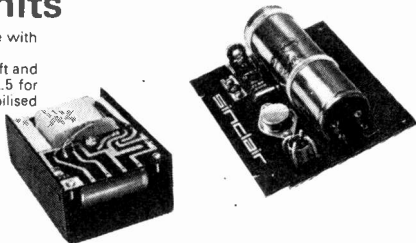

**GUARANTEE** If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

# sinclair

## Stereo FM tuner

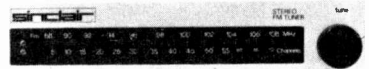

### first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time the principle has been applied to an FM tuner with fantastically good results. By the inclusion of other original features such as varicap diode tuning, printed circuit coils and an I.C. in the specially designed stereo decoder, the tuner has an unsurpassed specification, which also incorporates a squelch circuit for silent tuning between stations, A.F.C. and A.G.C. Sensitivity is such that good reception becomes possible in difficult areas, foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of high fidelity, this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. Although the tuner is intended primarily for use with a Project 60 system, it can be used to advantage with any other high fidelity system. It is easily mounted into any cabinet as shown in the manual supplied with it.

### Specifications

Number of transistors 16 plus 20 in I.C.

Tuning range 87.5 to 108 MHz

Capture ratio 1.5dB

Sensitivity  $2\mu\text{V}$  for 30dB quieting  
 $7\mu\text{V}$  for full limiting

Squelch level  $20\mu\text{V}$

A.F.C. range  $\pm$  200 KHz

Signal to noise ratio > 65dB

Audio frequency response 10Hz–15kHz ( $\pm$  1dB)

Total harmonic distortion 0.15% for 30% modulation

Stereo decoder operating level  $2\mu\text{V}$

Pilot tone suppression 30dB

Cross talk 40dB

I.F. frequency 10.7 MHz


Output voltage  $2 \times 150\text{mV}$  R.M.S.

Aerial Impedance 75 Ohms

Indicators Mains on; Stereo on; tuning indicator

Operating voltage 25-30 VDC

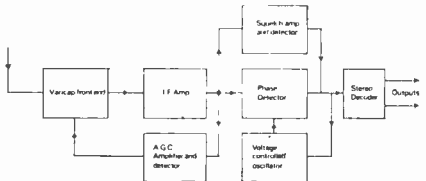Size  $3.6 \times 1.6 \times 8.15$  inches:  $91.5 \times 40 \times 207$  mm



Price: **£25** built and tested. Post free.

To: Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire

Please send

NAME

ADDRESS

for which I enclose cash/cheque money order

PE/27

# Sinclair IC10/Q16/Micromatic

## IC10



### The world's most advanced high fidelity amplifier

This is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, having 5 watts RMS output (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, and is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is more rugged and has considerable performance advantages, including complete freedom from thermal runaway and very low level of distortion. The IC10 is primarily intended as a full performance high fidelity power and preamplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. It may also be used in other applications including car radios, electronic organs, servo amplifiers (it is dc coupled throughout), etc.


#### Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. Generous negative feedback round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory. Each IC10 is sold with a comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include oscillators, etc. The pre-amp section can be used as an RF or IF amplifier without any additional transistors.

#### Specifications

Output: 10 watts peak, 5 watts RMS continuous.  
 Frequency response: 5Hz to 100kHz - 1dB.  
 Total harmonic distortion: Less than 1% at full output.  
 Load impedance: 3 to 15 ohms.  
 Power gain: 110dB (100,000,000,000 times) total.  
 Supply voltage: 8 to 18 volts.  
 Size: 1.04 x 0.2 in plus heat sink and tags.  
 Sensitivity: 5mV.  
 Input impedance: Adjustable externally up to 2.5 Mohms.  
 Price (with manual) 59/6.

## Q16

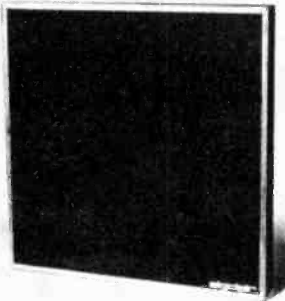

### High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies.

This shelf-mounted speaker brings genuine high fidelity within reach of every music lover.

#### Specifications

**Construction:** Special sealed seamless sound or pressure chamber with internal baffle.  
**Loading:** up to 14 watts RMS.  
**Input impedance:** 8 ohms.  
**Frequency response:** From 60 to 16,000Hz, confirmed by independently plotted B and K curve.  
**Driver unit:** Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension.  
**Size and styling:** 9 1/2 in square on face 4 1/2 in deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.  
**Price:** £8 19 6.

## Micromatic



### Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver meticulously designed to provide remarkable standards of selectivity, power and quality. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute and attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist-watch, and dependable under the severest listening conditions.

#### Specifications

Size: 46 x 33 x 13mm, (1 3/4 x 1 1/8 x 1/2 in).  
 Weight: including batteries, 28.4 gm (one ounce).  
 Case: black plastic with anodised aluminium front panel and spun aluminium dial.  
 Tuning: medium wave band with bandspread at higher frequencies, (550 to 1,600kHz).  
 Earpiece: magnetic type.  
 On/off switching: by inserting and withdrawing earpiece plug.  
 Kit in pack with earpiece, case, instructions and solder 49/6.  
 Ready built, tested and guaranteed, with earpiece 59/6.  
 Two Mallory Mercury batteries type RM675 required. From radio shops, chemists, etc.

To: SINCLAIR RADIONICS LTD. · LONDON ROAD · ST. IVES · HUNTINGDONSHIRE

Please send

NAME

ADDRESS

for which I enclose cash/cheque money order

PE 27

# sinclair

Sinclair Radionics Ltd., London Road,  
 St. Ives, Huntingdonshire.  
 Tel.: St. Ives (048 06) 4311

# BRAND NEW FULLY GUARANTEED TRANSISTORS SEND FOR NEW LIST • NEW PRICES

1N4001	1/8	AAZ12	4-	BPY10	1/8	6
1N4002	1/8	AAZ13	2/8	BSX20	3/8	6
1N4003	2-	AAZ14	2	BSX21	4	6
1N4004	2-	AC126	5-	BSX76	3/-	6
1N4005	2/8	AC127	5-	BSY27	4/-	6
1N4006	3/-	AC127Z	10-	BSY28	5/-	6
1N4007	4/-	AC128	5/-	BSY29	5/-	6
1N4009	1/8	AC133	4/-	BSY50	5/-	6
1N4148	1/8	AC154	3/-	BSY53	5/-	6
2G210	12/8	AC169	3/-	BSY66	5/-	6
2G240	4/8	AC176	5/-	BSY67	5/-	6
2G301	4/-	AC187	8/-	BSY95A	4/8	6
2G302	4/8	AC188	8/-	BSY95	3/-	6
2G303	5/-	ACV17	8/-	BY100	3/8	6
2G306	6/-	ACV18	4/-	BY103	4/8	6
2G308	6/-	ACV19	5/-	BY126	3/-	6
2G309	6/-	ACV20	4/-	BY127	4/-	6
2G371	4/8	ACY21	4/8	BYZ10	8/-	6
2G374	5/8	ACY22	3/8	BYZ11	7/-	6
2G381	5/-	ACY28	3/8	BYZ12	6/-	6
2G382	6/-	ACY34	4/-	BYZ13	4/-	6
2G383	5/-	ACY36	5/-	BYZ15	20/-	6
2N404	4/8	ACY39	11/-	BYZ16	12/8	6
2N696	3/-	ACY40	3/-	GET102	6/-	6
2N697	3/8	AD140	10/-	GET103	4/8	6
2N698	8/8	AD149	10/-	MFF102	8/8	6
2N700	2/8	AD161	7/8	MFF103	7/-	6
2N706A	2/8	AD162	7/8	MFF104	7/8	6
2N707	9/8	AF102	12/8	MFF105	8/-	6
2N708	3/-	AF114	6/8	OA5	3/-	6
2N914	4/8	AF115	6/8	OA7	4/-	6
2N916	4/8	AF116	6/8	OA9	2/-	6
2N918	7/8	AF117	5/-	OA10	5/-	6
2N919	4/8	AF118	12/8	OA37	2/-	6
2N920	5/-	AF124	8/-	OA70	2/-	6
2N922	8/8	AF125	5/-	OA71	2/-	6
2N930	5/-	AF126	4/-	OA73	2/-	6
2N1131	8/-	AF127	4/-	OA74	2/-	6
2N1132	6/-	AF139	6/-	OA79	2/-	6
2N1303	4/8	AF176	8/8	OA80	2/-	6
2N1304	5/-	AF18	8/8	OA85	2/8	6
2N1305	5/-	AF186	8/-	OA86	4/-	6
2N1306	5/-	AF239	8/-	OA90	2/-	6
2N1307	5/-	AFY19	22/8	OA91	1/8	6
2N1308	6/-	AFZ11	12/8	OA95	1/8	6
2N1309	5/-	AFZ12	15/8	OA900	1/8	6
2N1313	4/8	ASV26	5/-	OA204	2/-	6
2N147	15/-	ASV27	7/8	OA210	5/-	6
2N160	13/8	ASV28	5/-	OA211	7/8	6
2N287	20/8	ASV29	6/-	OA225	7/8	6
2N246	10/8	ASV67	9/8	OA228	7/8	6
2N264	6/-	ASZ21	8/8	OA229	8/8	6
2N2905	7/8	AU310	10/8	OA231	9/8	6
2N2925	4/-	B3M	18/8	OA234	2/-	6
2N2926	2/8	BA110	5/-	OA238	9/8	6
2N3011	5/-	BA131	2/-	OC16	8/8	6
2N3053	5/-	BC107	2/8	OC19	7/8	6
2N3054	10/-	BC108	2/8	OC20	19/8	6
2N3055	15/-	BC109	2/8	OC25	8/8	6
2N3702	2/8	BC113	3/8	OC27	10/-	6
2N3703	2/8	BC116	8/-	OC24	10/-	6
2N3704	3/8	BC118	7/8	OC25	7/8	6
2N3705	3/8	BC134	7/8	OC26	5/-	6
2N3707	3/8	BC135	6/-	OC28	12/8	6
2N3709	2/8	BC136	6/-	OC30	12/8	6
2N3710	2/8	BC137	6/-	OC35	15/8	6
2N3711	2/8	BC138	8/-	OC36	12/8	6
2N3730	13/8	BCY30	5/8	OC41	5/-	6
2N3731	12/8	BCY31	6/-	OC42	8/-	6
2N3794	2/8	BCY32	10/-	OC43	8/-	6
2N3819	7/8	BCY33	4/-	OC44	7/8	6
2N3820	17/8	BCY34	5/-	OC45	4/8	6
2N3823	17/8	BCY38	6/-	OC46	5/8	6
2N4058	3/8	BCY39	9/8	OC70	2/8	6
2N4061	3/8	BCY40	8/8	OC71	3/-	6
2N4286	3/8	BCY42	5/-	OC72	5/-	6
2N4288	3/8	BCY43	5/-	OC73	5/-	6
2N4289	6/8	BCY76	8/-	OC74	4/8	6
2N4290	3/8	BCZ11	7/8	OC75	5/-	6
2N4291	3/8	BC147	3/8	OC76	5/-	6
2N4292	3/8	BC148	2/8	OC77	8/-	6
40361	11/-	BC149	4/-	OC78	5/-	6
40392	12/-	BF152	6/8	OC81	5/-	6
28001	10/-	BF194	4/8	OC91D	4/8	6
28002	10/8	BF195	3/8	OC82	5/-	6
28003	9/8	BD124	12/8	OC83	5/-	6
28004	9/8	BEN3000	5/-	OC84	5/-	6
28005	14/-	BF115	5/-	OC122	10/-	6
28012	25/-	BF164	8/-	OC123	10/-	6
28013	20/-	BF158	8/-	OC139	5/-	6
28017	15/-	BF159	12/-	OC140	7/8	6
28054	12/8	BF163	8/-	OC141	15/-	6
28036	25/-	BF167	5/-	OC169	4/-	6
28320	9/-	BF173	6/-	OC170	5/-	6
28321	6/-	BF180	7/8	OC171	6/-	6
28322	7/8	BF181	7/8	OC200	9/8	6
28323	10/-	BFX30	6/-	OC201	9/8	6
28324	12/8	BFX88	5/-	OC292	12/8	6
28512	9/8	BFY20	12/8	OC203	7/8	6
28701	8/8	BFY50	4/8	OC204	8/-	6
28702	11/-	BFY51	4/-	OC205	12/8	6
28731	8/8	BFY52	4/8	OC206	15/-	6
28732	8/8	BFY53	3/8	OC207	15/-	6
28733	9/8	BFY64	8/8	OC271	19/8	6
AA178	8/8	BLY10	20/-	ORP12	11/-	6
AA172	5/-	BLY11	22/8	ORP60	8/-	6

## INTEGRATED CIRCUITS

Type	I	12+	25+	100+500+
UL914	9/9	9/-	8/-	7/3 6/6
UL923	12/6	11/9	11/-	10/- 9/3
SL403A	42/6	41/-	40/-	37/6 35/-
MC1303	52/6	48/-	45/-	40/- 35/-
MC1304	55/-	50/-	47/6	42/6 37/6
PA246	52/6	48/-	45/-	40/- 35/-

2N3055	15/-	2N3819	7/-
Mullard 115 watt Silicon Power		Texas F.E.T.	
25 + 13/-		25 + 6/-	
100 + 11/-		100 + 5/3	
		500 + 4/9	

2N2926	2/6	2N2646	10/6
NPN Planar All Colours		Motorola Unijunction	
25 + 1/8		25 + 8/9	
100 + 1/6		100 + 7/6	
		500 + 6/9	

AF139	6/-	AF186	8/-
Siemens V.H.F.		Mullard V.H.F.	
25 + 5/3		100 + 6/-	
100 + 4/6		500 + 5/-	

OB170	5/-	BY126	3/-
25 + 4/3		Mullard 800v 1 amp Plastic	
100 + 3/6		25 + 2/6	
		100 + 2/3	

OC171	6/-	BYZ13	4/-
25 + 5/3		Mullard 6a 2000v	
100 + 4/6		25 + 3/6	
		100 + 3/2	
		500 + 2/10	

BY127	4/-	BC107/8/9/2/6 ea.	
Mullard 1000v 1 amp Plastic		I.T.T. Planars	
25 + 3/3		25 + 2/3	
100 + 3/-		100 + 2/-	
		500 + 1/9	

BT102/500R	15/-	OCPT1	19/6
Mullard Thyristor 500 p.v. 6.5a		Mullard Photo	
25 + 12/6		25 + 17/3	
100 + 11/-		100 + 14/9	
		500 + 13/6	

OA200/OA202	1/9	OC28	12/6
SILICON Diodes		Mullard Power	
25 + 1/6		25 + 11/-	
100 + 1/3		100 + 10/-	
500 + 1/1		500 + 8/6	

OC42	6/-	OC71	3/-
Mullard		Mullard	
25 + 5/3		25 + 2/3	
100 + 4/9		100 + 2/-	
500 + 4/3		500 + 1/9	

OC45	3/6	BCY34	5/-
Mullard		Mullard	
25 + 3/-		25 + 4/3	
100 + 2/6		100 + 3/9	
500 + 2/-		500 + 3/6	

OC75	5/-	IN4001/2/3	1/6
Mullard		1 amp 100-300v	
25 + 4/3		25 + 1/4	
100 + 3/6		100 + 1/2	
500 + 3/-		500 + 1/-	

OC20	19/6	ZENER DIODES	
Mullard 100v		400 MW 5%	
25 + 15/9		BZY88 Range	
100 + 14/6		All Voltages	
500 + 13/3		3.3v-33v 3/6	

IN4004/5	2/6		
400-600v 1 amp			
25 + 2			
100 + 1/9			
500 + 1/6			

IN4006/7	3/-		
800-1000v 1 amp			
25 + 2/10			
100 + 2/6			
500 + 2/3			

OC139	5/-	OC140	7/6
Mullard		Mullard	
25 + 4/-		25 + 6/-	
100 + 3/3		100 + 5/-	
500 + 3/-		500 + 4/-	

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new TECHNATRON Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical "know-how"—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable TECHNATRON Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The TECHNATRON Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it's as fascinating as a hobby.**

Among many other interesting experiments the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a "non-technical" type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

## New Specialist Booklet

If you wish to make a career in Electronics, send for your FREE copy of "OPPORTUNITIES IN TELECOMMUNICATIONS, TV AND RADIO". This brand new booklet—just out—tells you all about TECHNATRON and B.I.E.T.'s full range of courses.

**FREE**

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. 371B, ALDERMASTON COURT, READING RG7 4PF

ENSURE YOUR COPY BY POSTING COUPON NOW!

To B.I.E.T. Dept. 371B, Aldermaston Court, Reading RG7 4PF  
Please send books and full information — free and without obligation.



NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

OCCUPATION \_\_\_\_\_

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**

PLEASE NOTE MINIMUM ORDER SHOULD BE 10/-  
Quantity prices 100 + Phone (01) 723 0401 Ex. 4. All listed devices are from stock at time of going to press. Please add 1/6 post packing to your order.

NEW AUTUMN LIST, NEW DEVICES, NEW PRICES. ASK FOR LIST 36, SEND FOR FREE COPY TODAY. Discounts 10% on 12 + any one type. 15% on 25 + any one type.

**HENRY'S RADIO**  
303 EDGWARE ROAD LONDON, W.2  
(01) 723 1008/9  
OPEN MON-SAT 9am-6pm THURS 9am-1pm


# R+TV RADIO & TV COMPONENTS (Acton) Ltd.

Post to: 21d High St., Acton, London W3 6NG  
 Personal shoppers to 323 Edgware Road, London, W.2  
**ALL ORDERS BY POST TO OUR ACTON BRANCH**  
 Terms C.W.O. All enquiries S.A.E.

## Complete Stereo System
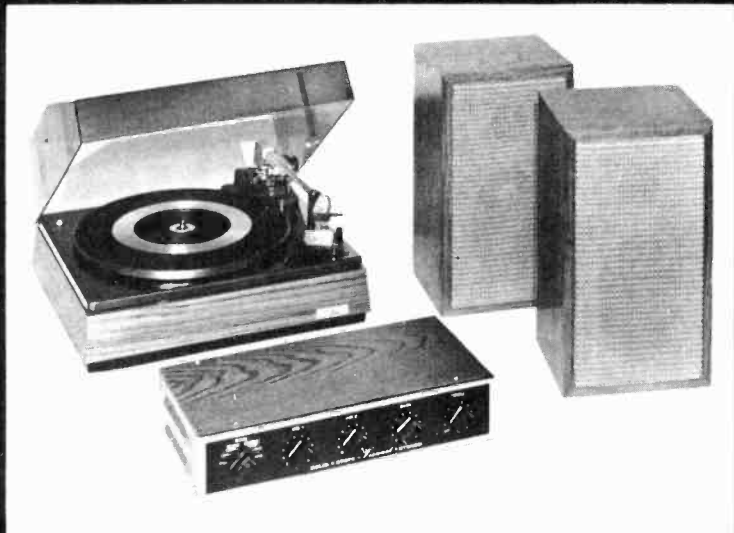
### £41

WITH  
**VISCOUNT F.E.T.**  
 FIELD EFFECT TRANSISTORS  
**AMPLIFIER**



This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½in × 10½in × 6½in, the Duo type 2 speakers are beautifully finished in teak veneer. They incorporate a 10½in × 6½in drive unit and high frequency speaker, both of which are of 3 ohms impedance. The Duo-speaker system is also available separately at **£6.6.0 (£6.30)** each plus 15/- (75p) P. & P.

Complete stereo system **£41** plus £2.10.0 (£2.50) P. & P.

With Mk. II Amplifier and Magnetic Cartridge **£45** plus £2.10.0 (£2.50) P. & P.



### The Classic

Simulated teak case  
**£9.10.0 (£9.50)**  
 Plus P. & P. 10/- (50p)

**SPECIFICATION:** Sensitivities for 10 watt output at 1KHz into 3 ohms. Tape Head: 3mV (at 3½ i.p.s.) Mag. P.U.: 2 mV. Cer. P.U.: 80mV. Tuner: 100mV. Aux. 100mV. Tape/Rec. Output. Equalisation for each input is correct to within +2dB (R.I.A.A.) from 20Hz to 20KHz. Tone Control Range: Bass: 13dB at 60Hz. Treble: ±14dB at 15KHz. Total Distortion: (for 10 watt output) < 1.5%. Signal Noise: < -60dB. A.C. Mains 200-250V. Size 12½in long, 4½in deep, 2½in high. Built and tested.



### THE RELIANT Mk. II

**SOLID STATE GENERAL PURPOSE AMPLIFIER**  
**£7.5.0 (£7.25)** Plus P. & P. 7/6 (37p)  
 Simulated teak case

**SPECIFICATION:** Output: 10 watts into a 3 ohms speaker. Inputs: (1) for mike (10mV). Input (2) for gram. radio (250mV). Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ × 4½ × 2½in.



### ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board —back printed for foolproof construction. **MAINS POWER PACK KIT: 9/6 (47p) extra.**  
**£5.5.0 (£5.25)** Plus P. & P. 7/6 (37p). Circuit 2/6 (13p). Free with parts.

### THE DORSET (600mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 × 8 × 3in. **MAINS POWER PACK KIT: 9/6 (47p) extra.**  
**£5.5.0 (£5.25)** Plus P. & P. 7/6 (37p). Circuit 2/6 (13p). Free with parts.



### The Viscount F.E.T. Mk. I £14.5.0 (£14.25)

Plus 10/- (50p) P. & P.  
 High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

#### SPECIFICATION

Output per channel—10W rms. Frequency bandwidth 20Hz to 20kHz ±1dB @ 1W. Total distortion @ 1kHz @ 9W 0.5%. Input sensitivities—CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100KΩ; Tape 100mV into 100KΩ. Overload Factor—Better than 26dB. Signal to noise ratio—70dB on all inputs (with vol. max).

**Mk. II (MAG. P.U.) £15.15.0 (£15.75)** Post & packing 10/- (50p) extra. Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner.

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono), separate vol. controls for left and right channels. Bass ±14dB @ 60Hz; Treble (with D.P.S. on/off) ±12dB @ 10kHz. Tape recording output sockets on each channel. Size 12½in × 6in × 2½in in simulated teak case. Built and tested. Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ±1dB RIAA. Signal to noise ratio—65dB (vol. max.).


#### LIQUIDATED STOCK

## DANSETTE

### TOURISTE MK3

### CAR RADIO

### ALL TRANSISTOR

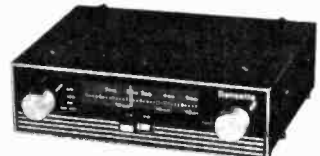

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" × 2" × 4½" deep.

Originally sold completely built for £15.4.6 (£15.23)

#### SET OF PARTS

Circuit diagram 2/6 (13p), free with parts Speaker, baffle and fixing kit **25/- (£1.25)** extra plus 4/- (20p) P. & P.

**£6.6.0** plus 7/6 (37p) P. & P.  
 (£6.30)

Speaker postage free when ordered with parts

# SOUND 50


## SOUND 50 AMPLIFIER AND SPEAKER SYSTEM

The Sound Fifty valve amplifier and speakers are sturdily constructed with smart housings and thoroughly tested electronics. They are designed to last—to withstand the knocks and bumps of life on the road. Built for the small and medium sized gig, they are easy to handle and quick to set up and can be relied upon to come over with all the quality and power you need.

**Output Power** 45 watts R.M.S. (Sine wave drive). **Frequency response**—3db points 30 Hz at 18 KHz. **Total distortion** less than 2% at rated output. **Signal to noise ratio** better than 60db. **Speaker Impedance** 3, 8 or 15 ohms. **Bass Control Range** ±13db at 60 Hz. **Treble Control Range** ±12db at 10 KHz. **Inputs** 4 inputs at 5 mV into 470 K. Each pair of inputs controlled by separate volume control. 2 inputs at 200 mV into 470 K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.

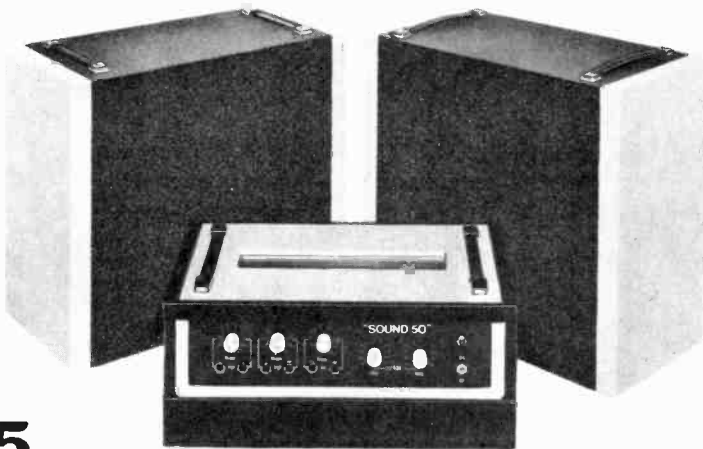**SPEAKERS** Size 20" x 20" x 10" incorporating Baker's 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.



**COMPLETE SYSTEM £45**

plus £4 P. & P.

Amplifier £28.10.0 (£28.50) plus £1 P. & P.

Speakers each £12.10.0 (£12.50) plus 30/- (£1.50) P. & P.

**RADIO & TV COMPONENTS (ACTON) LTD.**

Post to:—21d High Street, Acton, London W3 6NG

Personal shoppers to 323 Edgware Road, London, W.2

Goods not despatched outside U.K.

Terms C.W.O.

All Enquiries S.A.E.



**for fast, easy, reliable soldering**

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

**SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.**

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 75p



**THIN GAUGE SOLDER, ESSENTIAL FOR soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 75p**



**A RANGE OF SOLDERS IN HANDY DISPENSERS.**

REF.	ALLOY	SWG	
4A	60/40	18	15p*
Size 5 (illustrated)	Savbit	18	15p*
15	60/40	22	20p*

\*Recommended Price



**INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p**



**Take your Wellerchoice\* in Soldering**



**Low Initial Cost \***

Low initial cost Marksman irons, to cover most soldering needs. Screw-in tips on 15W and 25W make it easier to change the tips, which are nickel-plated and factory pre-tinned for longer life. The shanks are stainless steel to concentrate heat at the tips.

**Instant Heat for Rapid Soldering \***



Instant heat soldering guns to deal with intermittent soldering. Working heat is reached within seconds of pressing the trigger, so the job is finished in less time than it takes for a normal iron to heat up. Expert dual heat (100/140W) and Heavy Duty (275W) models available. Alternative tips available for plastics working.



**Weller Electric Limited**


Redkirk Way, Horsham, Sussex

Tel: 0403 61747

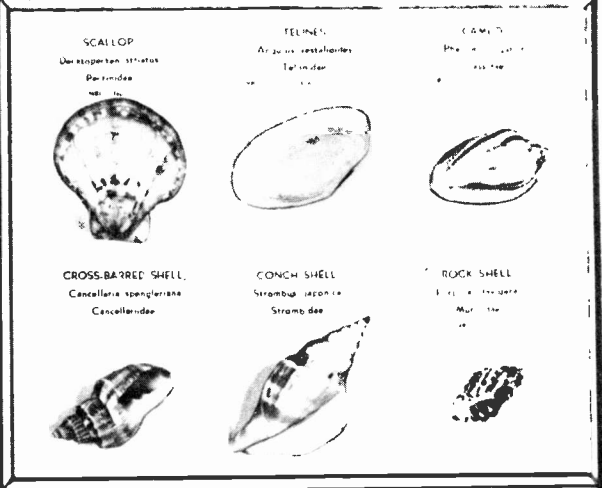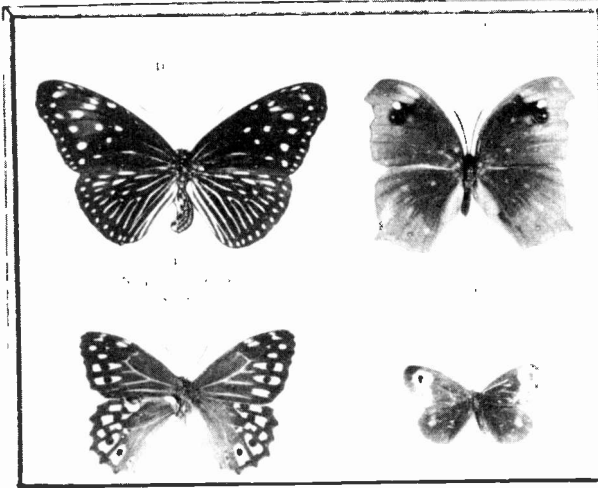

**SORRY** we can't help you with your collection of Coins, Butterflies, Shells, Stamps, etc.

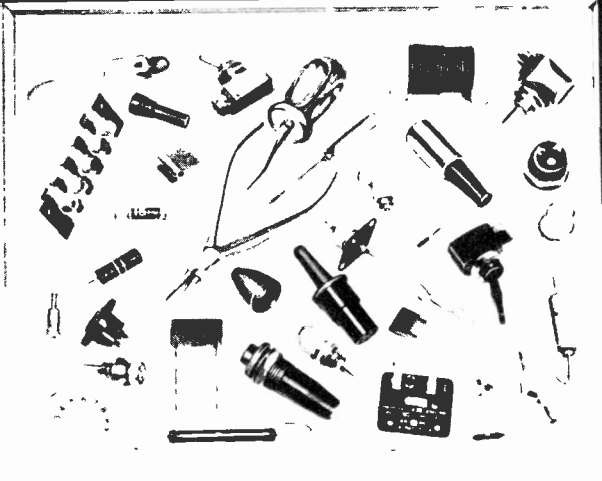**BUT** when it comes to Electronic Components we certainly can!!



We realise of course that you don't want components for displaying in a case, but for putting to good use in your latest radio or electronic project. You want to be able to get just what you need quickly and easily, preferably from a single supplier. That's where the Home Radio Components Catalogue comes to your aid.

In its pages are listed over 8,000 items, more than 1,500 of them illustrated. A cross-reference index makes it simplicity itself to find just the parts you need, and the Price Supplement puts you in the picture price-wise. On receipt of your written or telephoned order we despatch your components by return post. The catalogue is yours for only 12/6 (8/6 plus 4/- p & p). Wonderful value, especially as every copy contains six vouchers each worth 1/- when used as directed.

**POST THIS COUPON NOW** with your cheque or P.O. for 12/6

The price of 12/6 applies only to catalogues purchased by customers residing in the U.K.

Please write your Name and Address in block capitals

Name \_\_\_\_\_

Address \_\_\_\_\_



**Home Radio (Components) Ltd.**  
Dept. PE, 234-240 London Road, Mitcham, CR4 3HD

VOL. 7  
February

No. 2  
1971

# PRACTICAL ELECTRONICS

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES  
Advertisement Manager D. W. B. TILLEARD

## ASTRONAUTS OR AUTOMATONS?

THE landing of the unmanned vehicle *Lunokhod-1* on the moon's surface and its subsequent control from earth some 239,000 miles away was a unique and outstanding technical achievement: model control *par excellence!* This Soviet exploit has demonstrated quite clearly that man can devise and build automated equipment that will extend his influence over vast distances in space without incurring hazard to himself.

In everyday earthbound affairs, automation—which generally relies upon electronics for its brain power—has already made its indelible mark. Introduced primarily for sound economic reasons to overcome manpower shortage and to provide improved all-round efficiency, it brings about undoubted social improvements by removing many unattractive and irksome tasks from human hands. While automation can already supplant man to a lesser or greater degree in many activities, the ultimate extent of this takeover by machines is hard to predict. But the indications are that it will be determined by man's wishes, rather than by any technological limitations.

Clearly there are particular areas where man will not willingly abdicate his personal involvement in favour of a robot. The challenge of the unknown has impelled men to embark upon heroic adventures from the beginning of time. The mere invention of more speedy and comfortable means of conveyance has not extinguished the pioneer spirit that feels the urge to circumnavigate the globe alone, or to climb some colossal mountain peak. When all the formidable tasks of exploration presented by this earth have been successfully undertaken, man must needs look elsewhere for fresh fields to conquer. He is already looking impatiently out into space.

In this connection the achievement of the Russian lunar vehicle is especially interesting. It adds further fuel to the argument concerning whether it is wise or not to send men to the moon when the same kind of information they bring back can be gathered by an unmanned vehicle equipped with measuring and sensing devices and telemetry apparatus for transmitting data back to earth; and when rock specimens can be cored from the moon's surface and then be brought back to earth entirely by automatic means.

On a purely rational basis it would seem more sensible and logical to opt for the automated approach. Human lives would not be put in jeopardy and the cost would be a fraction of that for a comparable manned mission. But technical competence and cost efficiency will never dampen the human instinct to go and see for oneself; nor will risk to the person. The American astronaut Aldrin, the second man on the moon, afterwards remarked of "... the human need to do these things ...". This is certain, man will not be satisfied with exploring by remote control alone.

F.E.B.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

TAPE/SLIDE SYNCHRONISER	110
"P.E. GEMINI" DUAL PURPOSE STEREO AMPLIFIER	116
SUBMARINE CHASER	130
SONIC OBSTACLE LOCATOR	140
P.E. DIGITAL CLOCK	153

### SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—8	125
---------------------------------	-----

### GENERAL FEATURES

WOMEN IN ELECTRONICS	136
----------------------	-----

### NEWS AND COMMENT

EDITORIAL	109
SPACEWATCH	122
MARKET PLACE	135
NEWS BRIEFS	138
BOOK REVIEWS	139
READOUT	162

Our March issue will be published on  
Friday, February 19

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2 5s. 0d. (£2.25)  
Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202

# TAPE/SLIDE SYNCHRONISER

By  
F. C. JUDD

A COLOUR slide show can be enhanced with a well spoken commentary, background music and even sound effects which, if recorded on magnetic tape, leaves the projector operator free to concentrate on changing the slides in time with the recording.

If the slide projector is an automatic one, normally operated from a remote control box, then it can be directly controlled from the tape on which the commentary has been recorded, which means that the slides can be changed automatically in accordance with the sound track.

## CONTROL SYSTEMS

The operator's slide change button on the projector remote control box simply actuates a make and break contact which, in turn, applies current to the mechanism for changing the slides. This contact needs only to be

replaced by a relay contact which can be operated electronically by impulses recorded on the magnetic tape containing the sound track.

One way of doing this is to record sub-audio impulses on the same track as the commentary and music but this necessitates filter circuits in the sound replay amplifier chain. One could, of course, fit an extra record/replay head on the tape deck so that impulses could be recorded on an unused track. This is fine providing there is space for the head and that it could be fitted without spoiling the tape deck.

The ideal system is one which can be used with any conventional tape recorder, stereo or mono, half-track or quarter-track, at any of the standard tape speeds and without any modification whatsoever to the tape recorder or of tape cutting and splicing.

The impulse control system to be described can be used with any automatic slide projector that requires only a single make and break contact to change the slides.

## AUTOMATIC PROJECTORS


Automatic slide projectors are normally controlled from a push button on a small remote control box attached to the projector by a long cable. When the button is pressed the slide is changed and the slide carrier moves up ready for the next slide.

The remote control box has additional buttons for remote focusing and for reversing the slide change. These functions are not affected in any way by the use of an impulse controller and all that is required for impulse control is a pair of leads connecting the impulse control unit to the two contacts of the slide change button in the manual control box.

Most automatic slide projectors do in fact have a socket on the projector for connection to an impulse controller.
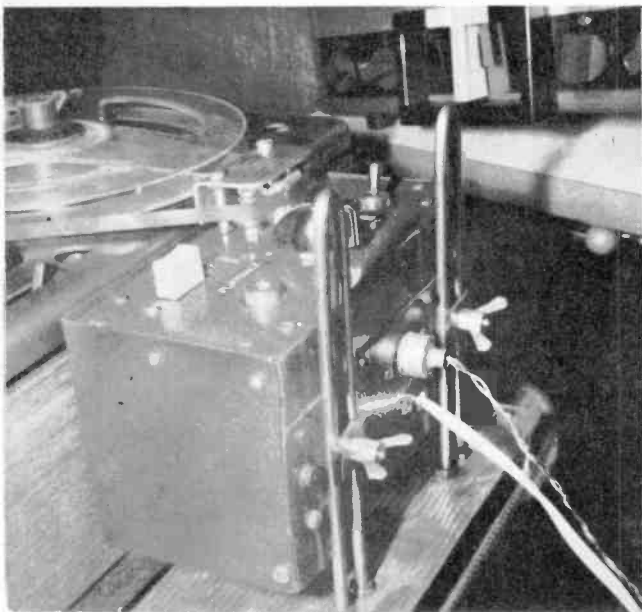
## CIRCUIT DESCRIPTION

The circuit diagram shown in Fig. 1 is designed to record 100Hz pulses on to the lower half or quarter-track of standard  $\frac{1}{4}$  in wide tape. The pulses can be recorded whilst listening to the pre-recorded sound track.





When the tape is running through the controller the pulse track is being constantly erased by a direct voltage applied to the head X1, via R10 and S2a. With the controller switched to "Record" the record indicator lamp will also be switched on.

When the pulse record button is depressed the direct erase voltage is disconnected and a 100Hz pulse, derived from the rectified supply input, is connected to the record/replay head. This pulse will be recorded on the tape. About one second is quite sufficient for the pulse time.

As the pulse button is depressed the 100Hz signal is also applied to the D1, C7, R12 network and consequently to the base of TR3 which will now conduct and

close the relay. This means that whilst the pulses are being recorded the slides will automatically change.

When the pulses have been recorded the controller is switched to "Playback", the tape rewound and the projector re-loaded. The whole programme can now be run entirely from the tape recorder as the projector will change slides automatically and in synchronism with the sound track.

During playback the pulses from the tape are picked up by the record/replay head on the controller, amplified by TR1 and TR2 and applied to the network C7, D1 and R12. On each pulse TR3 will conduct, the relay will operate and a slide will be changed.

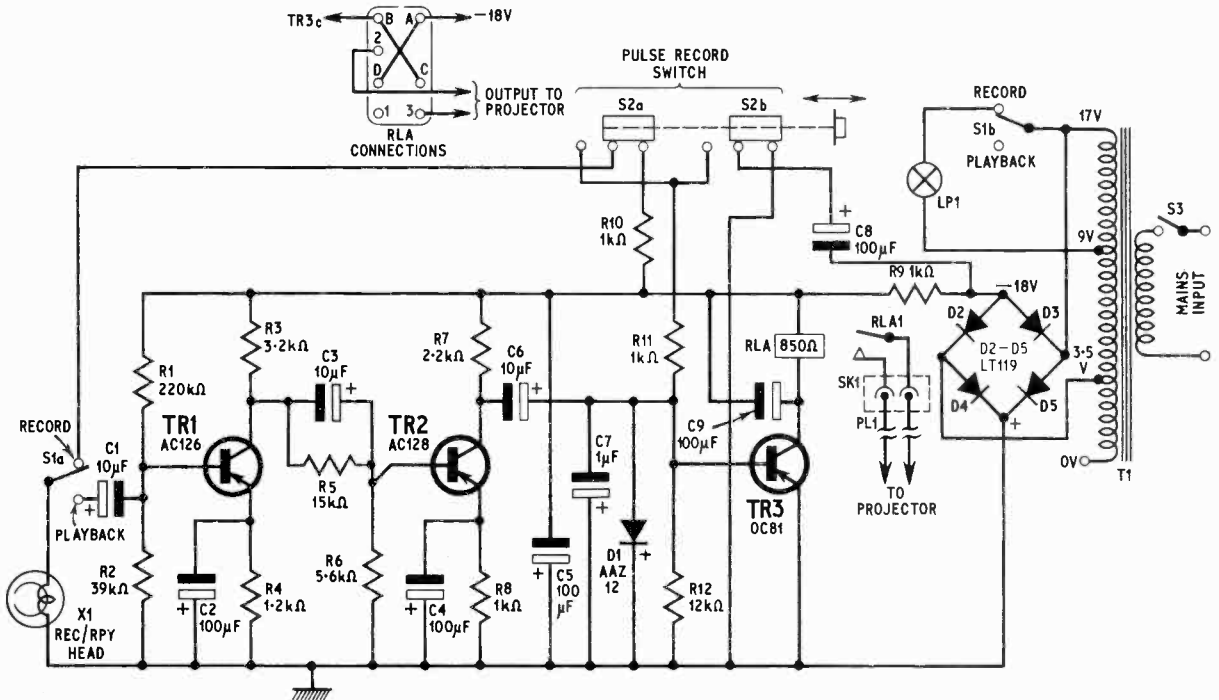


Fig. 1. Circuit diagram of tape/slide synchroniser

## COMPONENTS . . .

### Resistors

R1 220k $\Omega$	R4 1.2k $\Omega$	R7 2.2k $\Omega$	R10 1k $\Omega$
R2 39k $\Omega$	R5 15k $\Omega$	R8 1k $\Omega$	R11 1k $\Omega$
R3 3.2k $\Omega$	R6 5.6k $\Omega$	R9 1k $\Omega$	R12 12k $\Omega$

All  $\frac{1}{4}$  watt, 10% carbon

### Capacitors

C1 10 $\mu$ F elect. 12V	C6 10 $\mu$ F elect. 25V
C2 100 $\mu$ F elect. 12V	C7 1 $\mu$ F elect. 12V
C3 10 $\mu$ F elect. 12V	C8 100 $\mu$ F elect. 25V
C4 100 $\mu$ F elect. 12V	C9 100 $\mu$ F elect. 25V
C5 100 $\mu$ F elect. 25V	

### Transistors

TR1 AC126	TR2 AC128	TR3 OC81
-----------	-----------	----------

### Diodes

D1 AAZ 12 (Mullard)
D2-D5 Bridge rectifier Type LT119 (Henry's Radio)

### Switches

S1 2-pole, 2-way wafer switch
S2 6-pole, 2-way; push on, release off (Henry's Radio)

S3 Single pole, on-off toggle switch

### Transformer

T1 Mains transformer Type CT1/1 (Henry's Radio)

### Record/Replay Head

X1 Marriott R/RPI half track

### Relay

RLA 1,700 $\Omega$  + 1,700 $\Omega$  single pole changeover (Henry's Radio)

### Lamp

LP1 12 V 0.1A MES Pilot lamp

### Miscellaneous

Universal Chassis 6in  $\times$  4in  $\times$  3in and 6in  $\times$  4in bottom plate (Home Radio)  
 18 s.w.g. aluminium base plate 7 $\frac{1}{2}$ in  $\times$  3 $\frac{1}{2}$ in  
 Mild steel rod 14in  $\times$   $\frac{3}{8}$ in (2 off)  
 Brass rod or sleeves for guides  $\frac{1}{8}$ in dia (2 off)  
 4B.A. wing nuts (2 off), s.r.b.p. board and pins  
 SK1, PL1 Two pin plug and socket


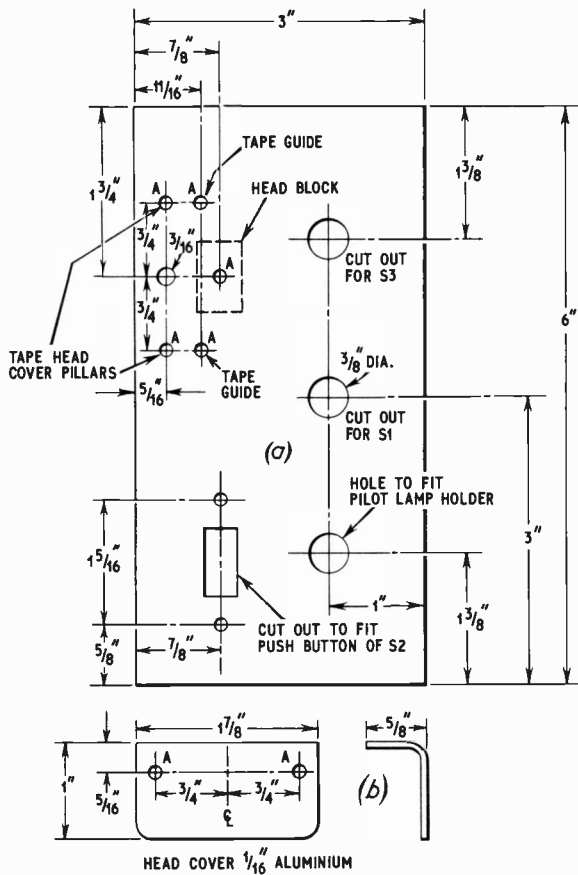
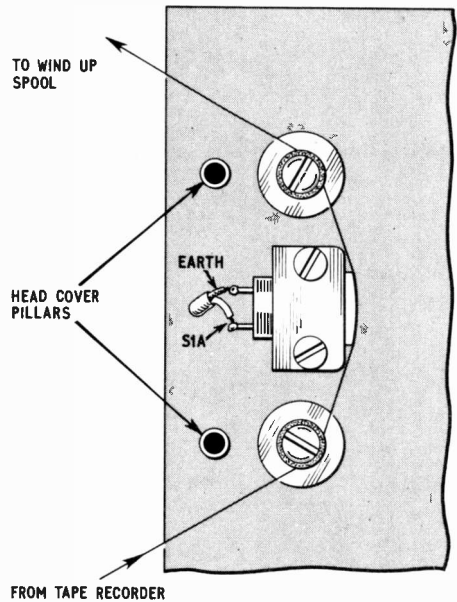


Fig. 2 (above). (a) Cutting and drilling details of top panel; (b) drilling and bending details of head cover


Fig. 3 (top right). Head mounting clock assembly details

Fig. 4 (below). (a) Construction and mounting details of the head cover pillars; (b) tape guide assembly and mounting details

Fig. 5 (right) (a) Showing the mounting of the pillars and guides on the control panel. The spooling direction at the head is made clear by reference to the photograph on page 000; (b) alignment of tape for half-track pulse recording; (c) alignment for quarter-track recording

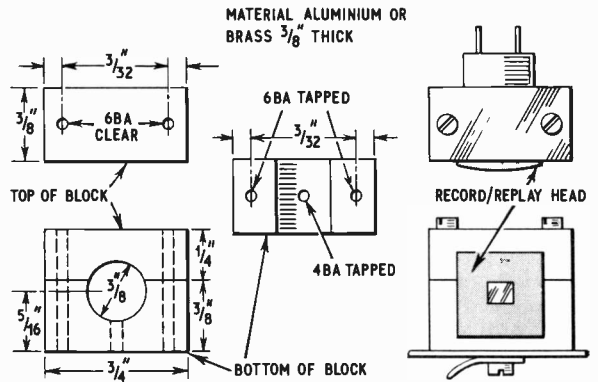


(a)

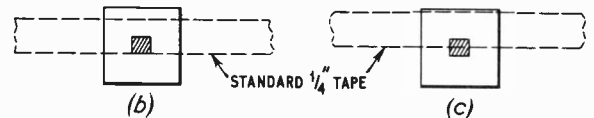

(b)

(c)

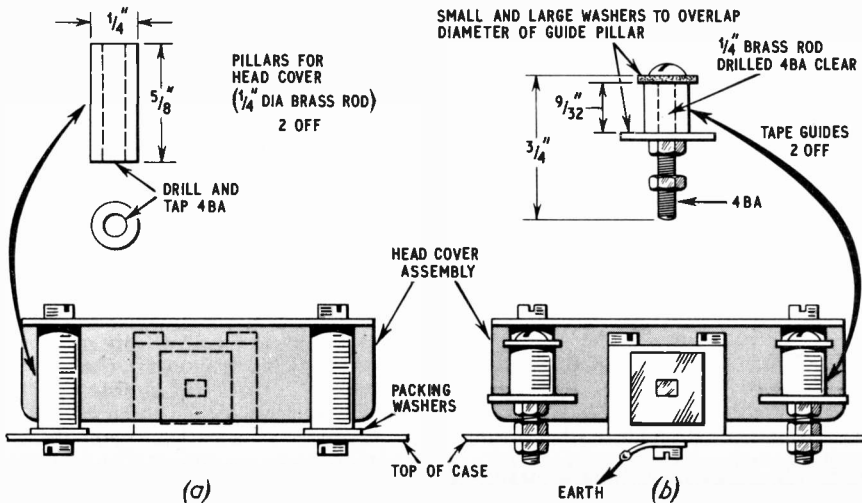

(a)

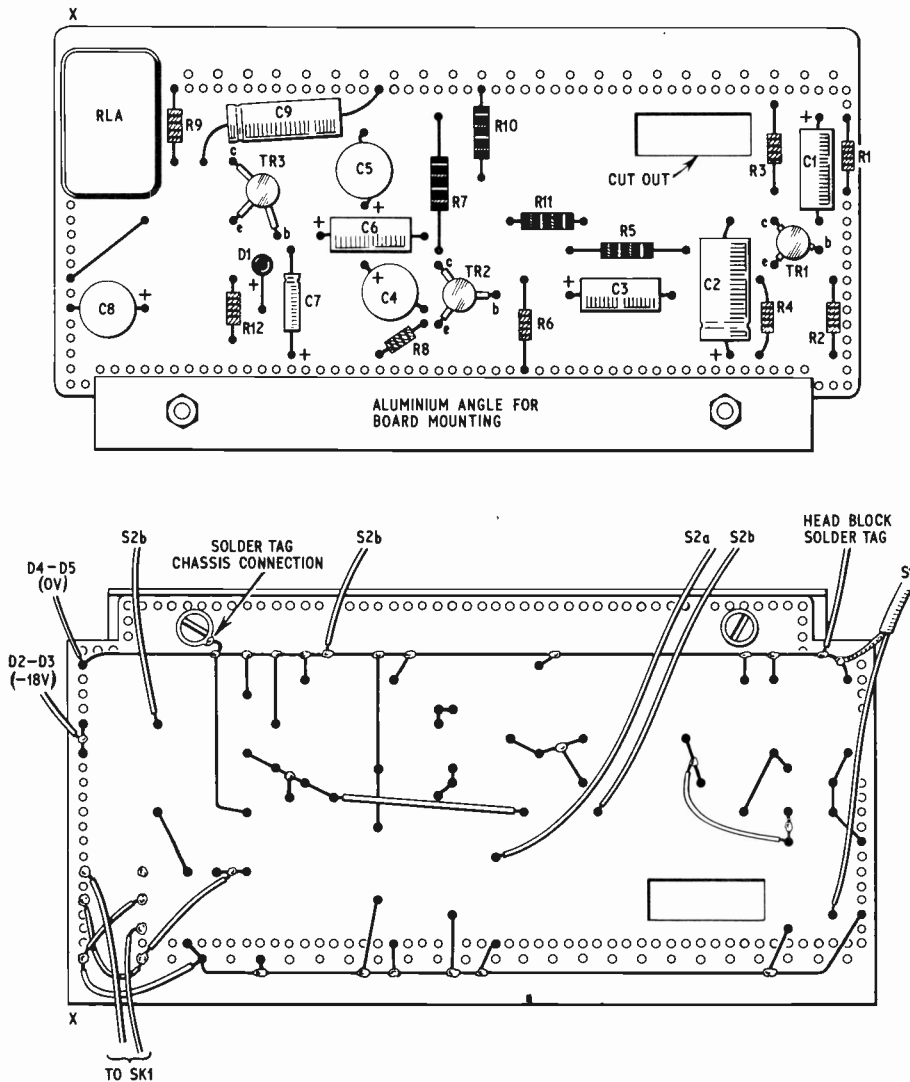


Fig. 6. Top and underside details of component mounting and wiring on plain Veroboard. Details of the relay wiring is given in Fig. 1

### CONSTRUCTION

The prototype unit was made up of 20 s.w.g. aluminium, but 18 s.w.g. is to be preferred for the extra rigidity afforded. A Universal chassis, 6in by 4in by 3in with a bottom plate, is suitable for housing and mounting the various parts.

Drilling and cutting details for the top panel are given in Fig. 2 (a). Fig. 2 (b) shows the tape head cover which is made from aluminium.

The tape head specified is a Marriott R/RP1 high impedance type, and is supplied without a mounting. Details of the mounting block are given in Fig. 3.

This forms a clamp for the cylindrical body of the head and can be made from brass or aluminium to the dimensions given. The centre hole, tapped 4B.A. at the base of the block, is for the bolt which secures it to the top of the controller box.

Next for construction are the tape guides as shown in Figs. 4 (a) and (b). These can be adjusted for height so aligning the tape with the head gap as seen in Fig. 5.

### BOARD ASSEMBLY

The transistors and small components are mounted and wired on a piece of plain Veroboard, 3in by 5½in as in Fig. 6. The cut-out at the end allows for the projection of the S2 switch assembly inside the case.

The relay has a double winding which, in this particular application, is connected in parallel to give a total resistance of 850 ohms. On the prototype no screws were needed to fix the relay to the board as the solder connections at the pins were sufficient to retain it in position.

### CHASSIS ASSEMBLY

The tape head assembly and pillars should first be mounted on the drilled top panel followed by the various controls as shown in Fig. 7. The chassis base plate bears the mains transformer T1, the bridge rectifier and the two-pin socket which carries the twin lead to the projector automatic control socket or remote control, whichever is applicable.

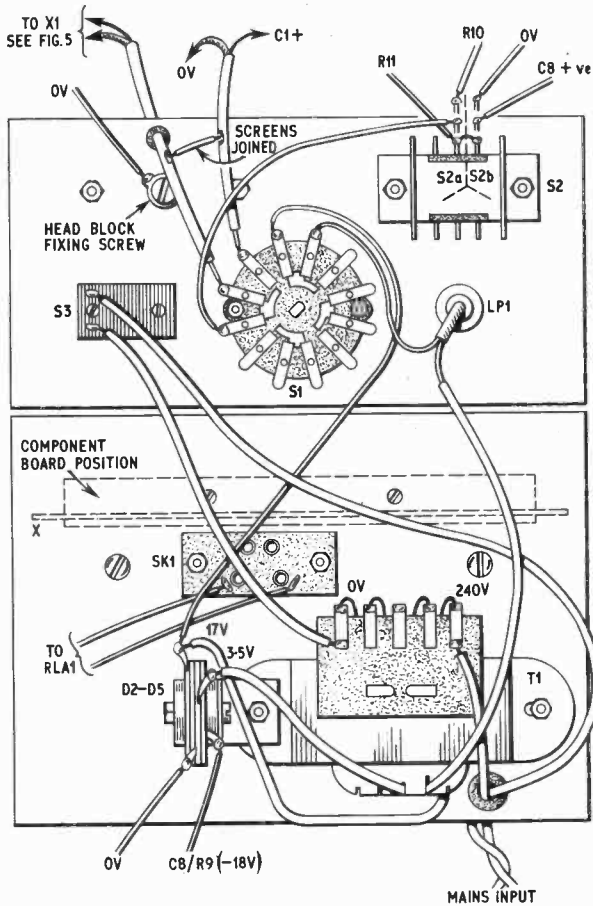


Fig. 7. Interwiring between control panel and base plate components. For Verboard connections Fig. 6 should be consulted


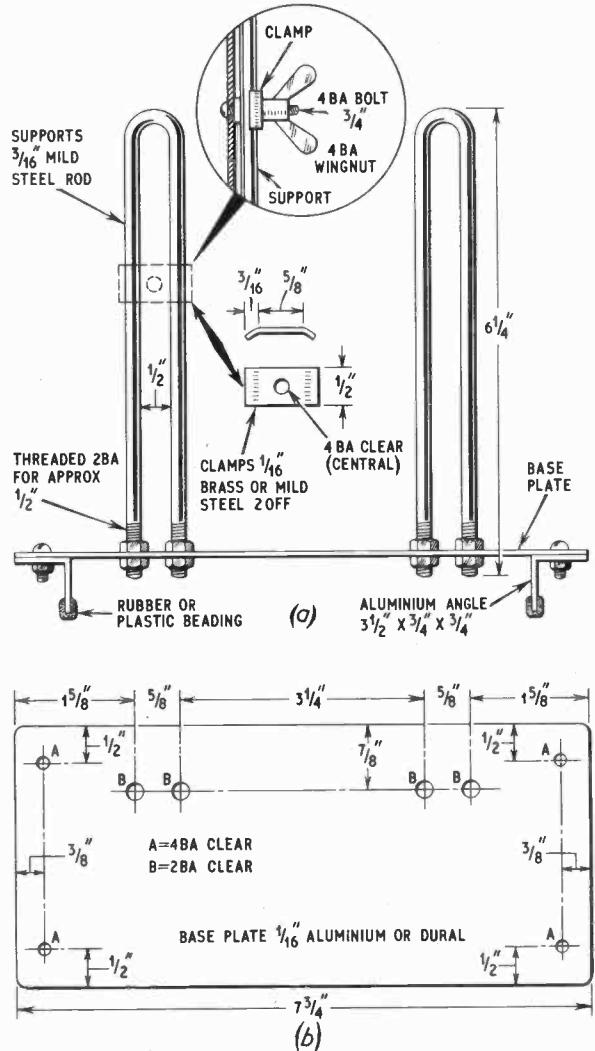


Fig. 8. (a) Supports and fixing clamps which allow the synchroniser to be positioned relative to the tape recorder deck; (b) base plate for support mounting

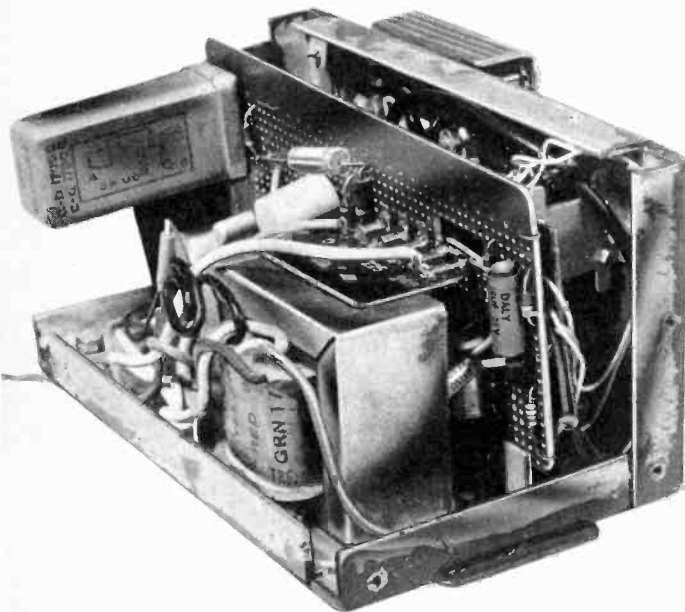

Interior view of the tape slide synchroniser

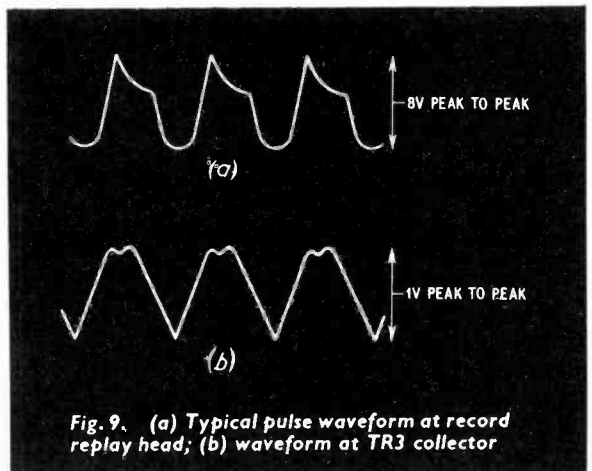


Fig. 9. (a) Typical pulse waveform at record replay head; (b) waveform at TR3 collector

Mount the assembled board on a piece of aluminium angle,  $\frac{3}{4}$ in by  $\frac{3}{4}$ in by 5in, then fix this to the chassis, where indicated, using kalons.

Interwiring should now be completed using Figs. 6 and 7. Note that screened leads must be used for the head connections with the screening braid earthed at the solder tag under the head block fixing screw.

### CONTROLLER STAND

The stand for the controller unit allows the height of the tape head to be varied from about  $4\frac{1}{2}$  to over 8 inches above table top level so that it can be used with almost any domestic tape recorder.

Details for the base of the stand and the two main supports and the remainder of the assembly are given in Fig. 8. Note that the  $\frac{3}{4}$ in, 4B.A. bolts on which the wing nuts are used, go through from the inside of the box and are then secured with 4B.A. nuts. The clamps and wing nuts will firmly hold the box at any height on the supports.

### CHECKING OPERATION

The measured supply should be approximately 18V at the junction of R9 and C8 with the unit switched to "Playback". The total current measured at this point should be approximately 8mA.

When the unit is switched to "Record" and S2 button depressed the line voltage should fall to about 14V and the current will increase to around 18mA.

With the unit still switched to "Record" but with the impulse button off, the voltage across the record/playback head should be approximately 1V.

With the controller switched to "Playback" the voltage at the junction of R7 and R9 should be about 14V.

If an oscilloscope is available, the waveforms and their respective peak to peak amplitudes at the record/replay head and at TR3 collector can be checked as shown in Fig. 9.

### TRACK ALIGNMENT

The tape head and guides can be aligned for either the lower half or quarter-track width as shown in Figs. 5 (b) and (c). With half-track recorders the upper half-track is used for sound. With quarter-track recorders the two inner tracks could be used for sound and the two outer tracks for pulses, which means that

two different programmes could be accommodated on one length of tape.

Accurate azimuth alignment of the head is not necessary and so long as the gap is vertical, it will operate efficiently. It is more important to get the track width aligned so that the pulse track does not overlap the sound track. If this should occur the pulses would be audible whilst playing the sound track.

### USING THE CONTROLLER

First the sound track should be completed in its entirety, then the projector set up and the slide carrier loaded with all the slides in the correct order. Set the tape recorder for replay so that the sound track is audible and set the controller to "Record". The tape is taken off the tape recorder, around the controller head and back onto the wind up spool.

Set the tape recorder running and then simply press the pulse record button for about half to one second each time a slide is to be changed. When the pulses have been recorded, switch the controller to replay, disengage the tape from the controller head and rewind it.

If the tape is rewound whilst still in contact with the controller head and with the controller switched to record, all the pulses will be erased. If rewound with the controller set to replay then the slide projector mechanism will be rapidly operated.

For entirely automatic projection of the slides in synchronism with the sound track, it is only necessary to load the slides, connect up the controller and play the tape.

### CONNECTING TO A PROJECTOR

For connections to a projector, twin leads should be suitably terminated with a two-pin plug for connection to the controller output socket SK1.

If the projector has a socket for connection to a controller, and most of them do, simply connect the free lead ends to this as instructed in the manufacturer's booklet.

Both the manual button on the projector control box and the pulse button on the controller can be used to override the recorded pulses during replay, but this will, of course, throw the slide sequence out of synchronism with the sound track. ★

View of the control panel. Here the head cover is removed



**FE**  
**GEMINI**

# DUAL PURPOSE PART FOUR STEREO AMPLIFIER

By **D. S. GIBBS** and **I. M. SHAW** (FERRANTI LTD)

HAVING introduced the pre-amplifier circuit briefly last month and given some of the individual circuit descriptions, we now go on to describe the rest of the circuit parts in detail, give the components list and start construction details of the pre-amplifier. Now that we are able to specify all the components, it is possible to say that the approximate cost of the complete amplifier and pre-amplifier will be £45. This cost is made up of £28 for the main amplifier and £17 for the pre-amplifier; prices of components vary by large amounts for some items and this price is only to give readers an approximate estimate of overall cost.

## STEREO-MONO SWITCHING

Stereo-mono switching (Fig. 30) is performed by switch S5 which cross-connects the inputs so that

equal amounts of left and right are fed into each of the input mixers. This facility is useful when playing mono records with a stereo pick-up as it cancels out certain distortion products present in the output of the pick-up. It also enables a stereo recording to be converted to mono so that it may be recorded on a mono tape recorder.

## TREBLE FILTER

The treble filter has two sections. The first section comprises capacitors C40 to C43 which appear in parallel with the amplifier feed-back resistor R60. These capacitors cause the gain of the amplifier to fall at 6dB per octave above the cut-off frequency. The second section is provided by inductor L2 and capacitors C36 to C39 which give a further 12dB per

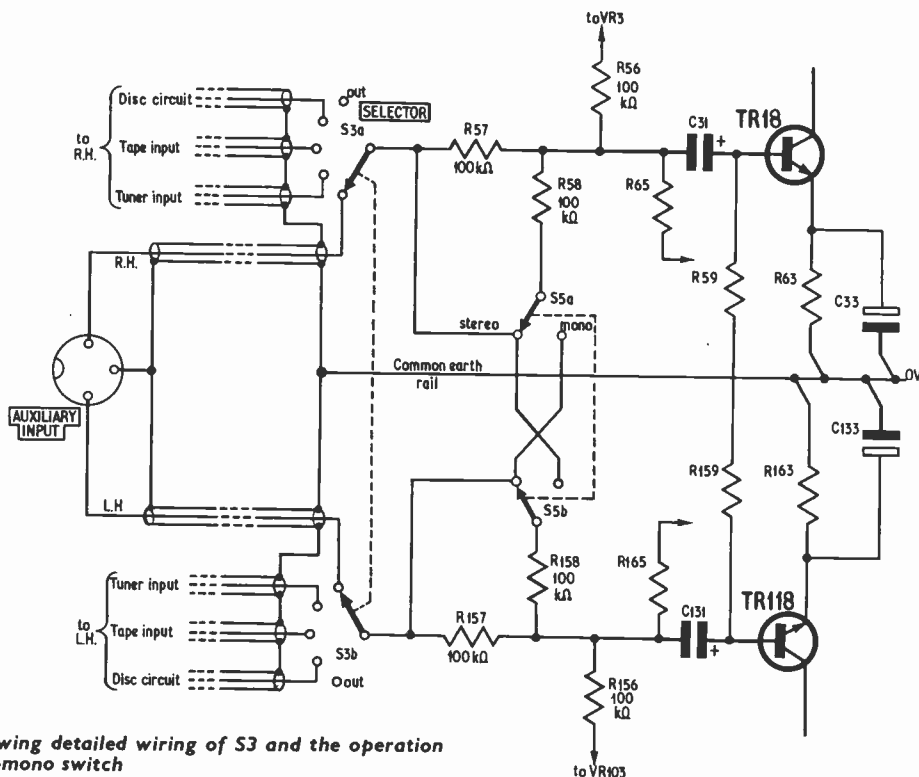


Fig. 30. Showing detailed wiring of S3 and the operation of the stereo-mono switch



octave to give a total slope of 18dB per octave. The LC section has been designed to give a peak of about 3dB before its cut-off to compensate for the initial slowly falling frequency response of the amplifier section.

The overall frequency response is quite flat up to the cut-off point and has a sharp knee as shown in Fig. 31. Four cut-off frequencies have been provided. The 5, 7 and 10kHz positions can be used to remove spurious noise or harsh treble from poor recordings, whilst the 15kHz filter makes very little difference to the reproduced sound but gives a worthwhile reduction in the 19kHz and 38kHz components present in the output of a stereo v.h.f. tuner. In the out position the frequency response is -3dB at 40kHz.

The transient response of the treble filter is illustrated by Figs. 32a to 32e which show that the ringing produced is very well damped and inoffensive. Generally speaking the sharper the cut-off in the frequency response the worse the transient response becomes so that one has to strike a compromise which gives both a well damped transient response and a satisfying clean frequency response. The popular "parallel T" type of treble filter is particularly difficult in this respect.

## TONE CONTROL

The tone control circuit comprising TR20, TR21, TR120 and TR121, uses the popular Baxendall configuration. In this design the tone control circuit is after the volume control so that it does not impose any limitation on the dynamic range of the pre-amplifier. When the tone control is placed before the volume control the dynamic range is reduced by the amount of boost employed, i.e., assuming such a pre-amplifier with a dynamic range of 20dB, turning up the bass control to give 15dB of bass boost will cause the dynamic range at low frequencies to be reduced to 5dB.

However when the tone control is placed after the volume control one has to take particular care to achieve a low noise level, since the noise output remains constant instead of being proportional to the setting of the volume control. The noise level generated by this design is 90dB below maximum output (-100dB weighted) and with loudspeakers of average efficiency this is inaudible at more than about three feet away from the loudspeakers. With loudspeakers of very high efficiency the noise level may be just perceptible under normal listening conditions. If this is found to

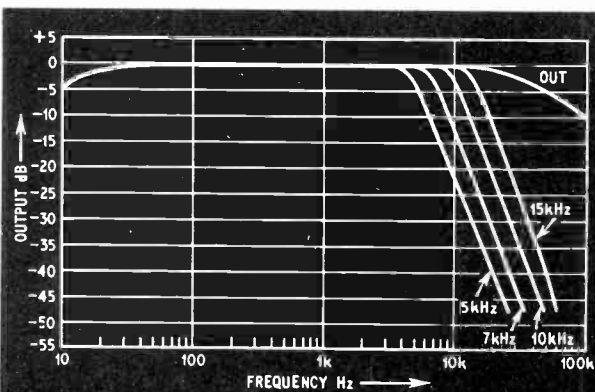


Fig. 31a. Frequency response curves of mixer and treble filter

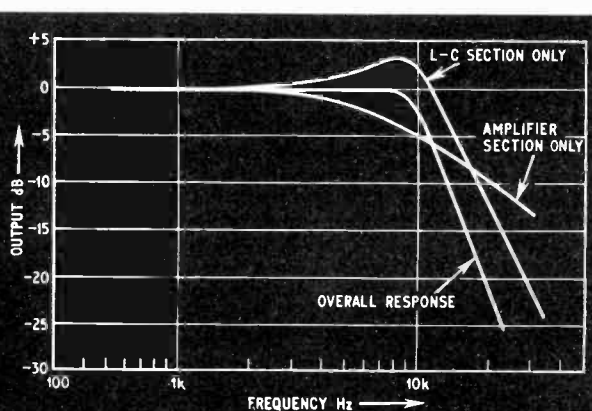


Fig. 31b. Showing how the frequency responses of the amplifier and LC sections combine to give a flat frequency response within the pass-band and a sharp cut-off (10kHz filter shown)

## PRE-AMPLIFIER

(both channels—components for L.H. channel are R.H. numbers plus 100)

### Resistors

R32 R132	47k $\Omega$	R57 R157	100k $\Omega$
R33 R133	2.7k $\Omega$	R58 R158	100k $\Omega$
R34 R134	1M $\Omega$	R59 R159	100k $\Omega$
R35 R135	1M $\Omega$	R60 R160	220k $\Omega$
R36 R136	100k $\Omega$	R61 R161	27k $\Omega$
R37 R137	56k $\Omega$	R62 R162	27k $\Omega$
R38 R138	390 $\Omega$	R63 R163	22k $\Omega$
R39 R139	180k $\Omega$	R64 R164	3.3k $\Omega$
R40 R140	10k $\Omega$	R65 R165	4.7k $\Omega$
R41 R141	10k $\Omega$	R66 R166	47k $\Omega$
R42 R142	4.7k $\Omega$	R67 R167	3.3k $\Omega$
R43 R143	1M $\Omega$ $\pm$ 10%	R68 R168	3.3k $\Omega$
R44 R144	470 $\Omega$ $\pm$ 10%	R69 R169	47 $\Omega$
R45 R145	10M $\Omega$ $\pm$ 10%	R70 R170	100k $\Omega$
R46 R146	470k $\Omega$	R71 R171	330k $\Omega$
R47 R147	470k $\Omega$	R72 R172	100k $\Omega$
R48 R148	470k $\Omega$	R73 R173	220k $\Omega$
R49 R149	100k $\Omega$	R74 R174	2.2k $\Omega$
R50 R150	56k $\Omega$	R75 R175	10k $\Omega$
R51 R151	10k $\Omega$	R76 R176	1k $\Omega$
R52 R152	470 $\Omega$	R77	100k $\Omega$ $\pm$ 10%
R53 R153	56 $\Omega$	R77 is not required if the neon lamp has a built in resistor.	
R54 R154	4.7k $\Omega$		
R55 R155	10k $\Omega$		
R56 R156	100k $\Omega$		

Unless otherwise stated all resistors are  $\frac{1}{2}$  watt carbon film or metal oxide of 5% tolerance or better. 2 off each except R77.

### Potentiometers

VR3 VR103	100k $\Omega$ log twin-gang (single gang for mono microphone—see text)
VR4 VR104	10k $\Omega$ log twin gang
VR5 VR105	470k $\Omega$ linear twin gang
VR6 VR106	100k $\Omega$ linear twin gang
VR7	10k $\Omega$ linear single gang wirewound (see text)

### Capacitors

C16 C116	250 $\mu$ F elect. 40V	Mullard
C17 C117	1 $\mu$ F plastic film 63V	WIMA MKS
C18 C118	50 $\mu$ F elect. 40V	Mullard
C19 C119	0.022 $\mu$ F polyester 160V	Mullard
C20 C120	1500pF polystyrene 125V	Radiospares
C21 C121	8200pF polystyrene 125V	Radiospares
C22 C122	47pF polystyrene 125V	Radiospares
C23 C123	20 $\mu$ F elect. 16V	Mullard
C24 C124*	1 $\mu$ F plastic film 63V	WIMA MKS
C25 C125	1 $\mu$ F plastic film 63V	WIMA MKS
C26 C126	1 $\mu$ F plastic film 63V	WIMA MKS
C27 C127	50 $\mu$ F elect. 40V	Mullard
C28 C128	47pF polystyrene 125V	Radiospares
C29 C129	20 $\mu$ F elect. 16V	Mullard
C30 C130*	1 $\mu$ F plastic film 63V	WIMA MKS
C31 C131*	1 $\mu$ F plastic film 63V	WIMA MKS
C32 C132	10pF polystyrene 125V	Radiospares
C33 C133	20 $\mu$ F elect. 16V	Mullard
C34 C134	5 $\mu$ F elect. 64V	Mullard
C35 C135*	1 $\mu$ F plastic film 63V	WIMA MKS
C36 C136	1500pF polystyrene 125V	Radiospares
C37 C137	2200pF polystyrene 125V	Radiospares
C38 C138	3300pF polystyrene 125V	Radiospares
C39 C139	4700pF polystyrene 125V	Radiospares
C40 C140	220pF polystyrene 125V	Radiospares
C41 C141	150pF polystyrene 125V	Radiospares
C42 C142	100pF polystyrene 125V	Radiospares
C43 C143	47pF polystyrene 125V	Radiospares
C44 C144	2.5 $\mu$ F elect. 64V	Mullard

C45 C145	6800pF polyester 400V	Mullard
C46 C146	6800pF polyester 400V	Mullard
C47 C147	1500pF polystyrene 125V	Radiospares
C48 C148	2.5 $\mu$ F elect. 64V	Mullard
C49 C149	10pF polystyrene 125V	Radiospares
C50 C150	20 $\mu$ F elect. 16V	Mullard
C51 C151	8 $\mu$ F elect. 40V	Mullard
C52	500 $\mu$ F elect. 64V	Mullard

\* plastic film 1 $\mu$ F capacitors are recommended for these positions but as these are rather expensive 1 $\mu$ F 40V electrolytic capacitors may be used instead if desired. The correct polarity is shown on the circuit diagram. 2 off each except C52.

### Semiconductors

T14 T114	ZTX 107 Ferranti
T15 T115	ZTX 531 Ferranti
T16 T116	ZTX 107 Ferranti
T17 T117	ZTX 503 Ferranti
T18 T118	ZTX 107 Ferranti
T19 T119	ZTX 107 Ferranti
T20 T120	ZTX 107 Ferranti
T21 T121	ZTX 107 Ferranti
	2 off each

### Switches

S1	DPDT toggle or slide switch
S2	DPDT ditto
S2	2 pole 5 way rotary Maka switch
S4	6 pole 5 way rotary Maka switch
S6	DPDT rotary mains switch

### Inductors


L2 L102	FX2239 pot core assembly with DT2204 coil former wound with 228 turns of 34 s.w.g. enamelled wire tapped as follows (2 off):
	5kHz full winding
	7kHz tapped at 196 turns
	10kHz tapped at 162 turns
	15kHz tapped at 134 turns

Note that two FX2239 Ferrite cups are required for each complete pot core.

### Miscellaneous

SK5-10	DIN 180° 3 pin or 5 pin socket (6 off)
SK11 SK12	DIN 300° 5 pin socket (2 off)
SK13	3 pin mains plug & socket (Bulgin P429 and P430)
LPI	neon panel lamp
	Control knobs: Eagle type k30/3 used on the prototype (8 off)
Case	Contil MOD-2 size G obtainable from West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middlesex.
	Printed circuit board
	Capacitor clamp
	$\frac{1}{2}$ in spacers 6B.A. 4 off
	6B.A. fixings
	Aluminium panel 12 $\frac{3}{4}$ $\times$ 2 $\frac{3}{4}$ $\times$ 18 s.w.g. for dummy front panel (cut from unused main amplifier chassis)
	C3-2800 $\mu$ F 100V Mullard is obtainable from Home Radio Ltd.
	Electronics address is Edinburgh Way, Harlow, Essex.




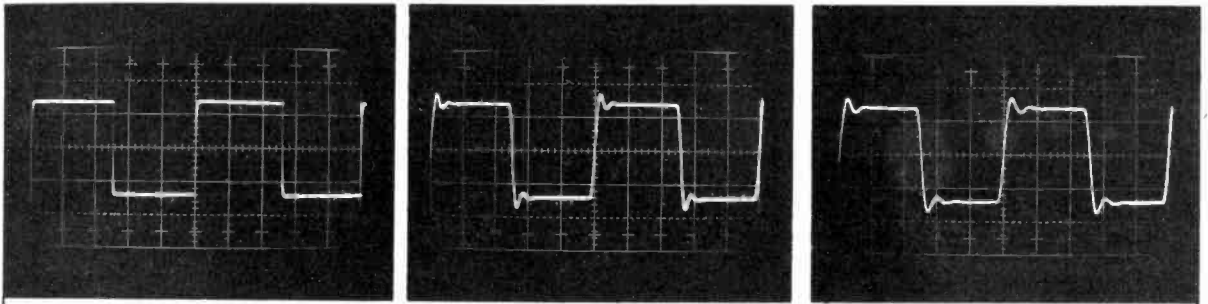


(a)

(b)

(c)

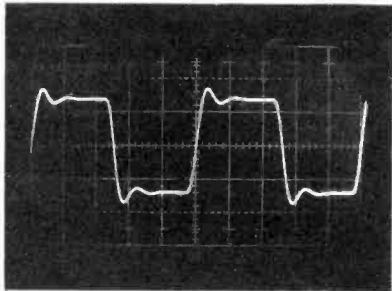

(d)

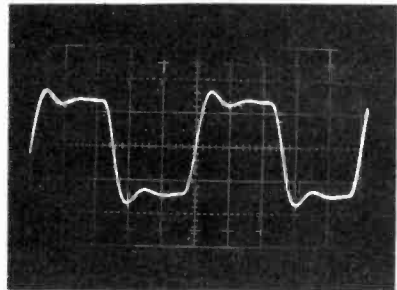

(e)

Fig. 32. Treble filter transient response (a) filter out—1kHz signal, (b) 15kHz position—1kHz signal, (c) 10kHz position—1kHz signal, (d) 7kHz position—1kHz signal, (e) 5kHz position—1kHz signal

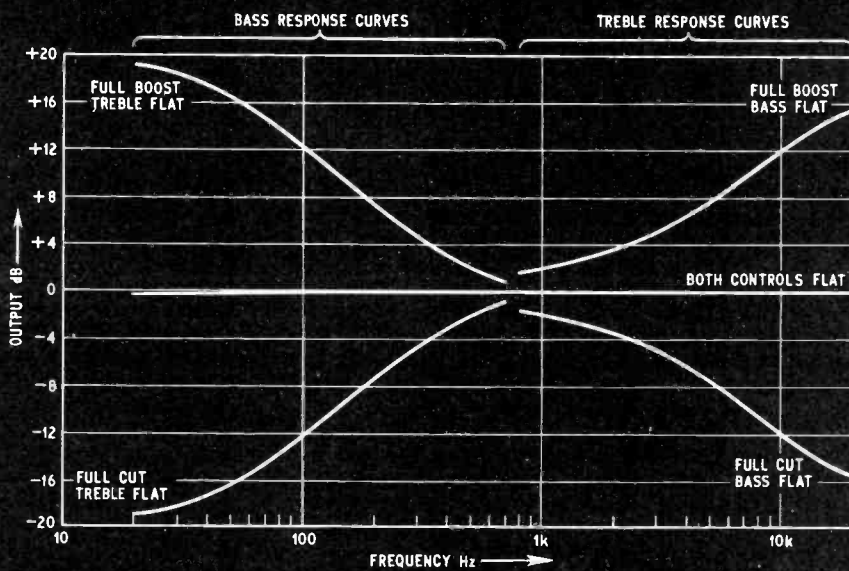


Fig. 33. Tone control characteristics

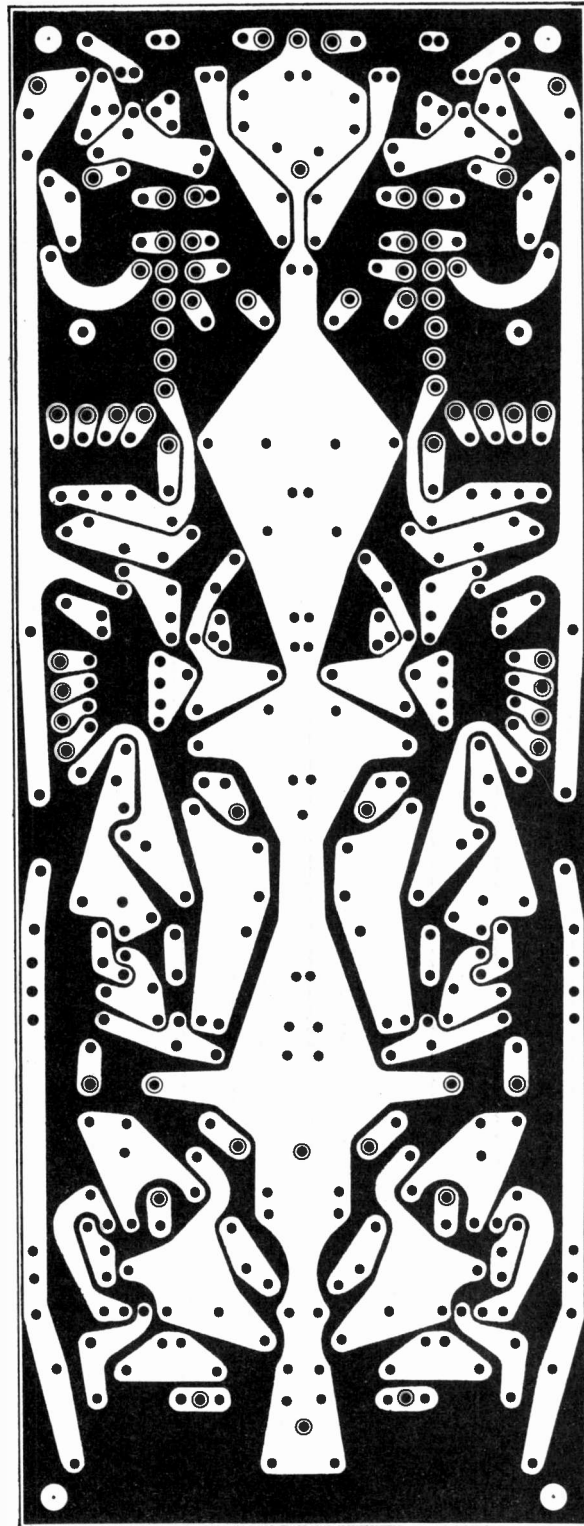
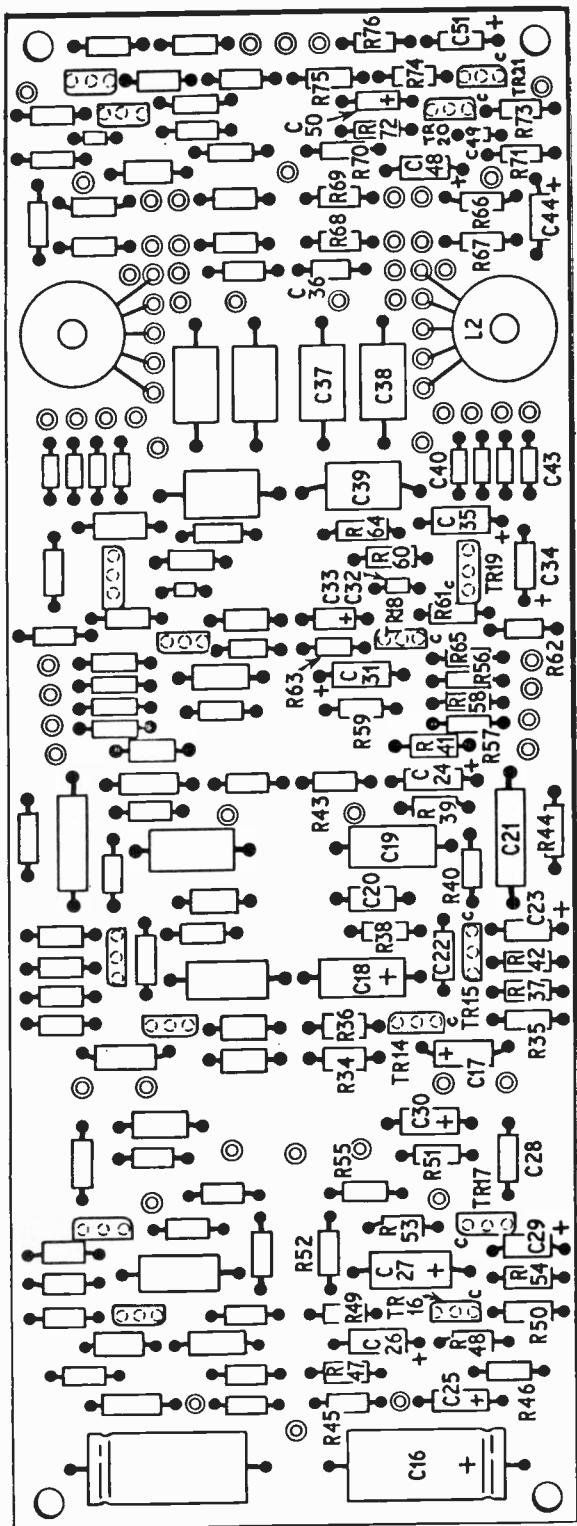


Fig. 34. Layout diagram of both channels of the pre-amplifier printed circuit board. Components for the left-hand channel have not been designated as this section is a mirror image of the right-hand channel—designations are right-hand channel numbers plus 100. The finished size of this board is 10½in by 4½in

Fig. 35 (right). Tag numbering and wiring details of the printed circuit board. Care must be taken when wiring up that left and right channel leads are identified and wired to the correct switch, potentiometer or socket positions

be the case the situation can be improved by increasing R76 and R176 to 4.7 kilohms or 10 kilohms, giving a 6 or 10dB reduction.

The tone control circuit uses two transistors instead of the usual single transistor to enable a very low noise

level to be obtained and to minimise distortion. The distortion generated is below 0.01 per cent at maximum output between 100Hz and 10kHz. The balance control is connected to the output of the tone control and works by progressively shorting out one channel or the other so that either channel can be completely cut off. To minimise cross-talk a wire wound potentiometer is preferred for VR7 but excellent results can be obtained with the ordinary carbon type.

Full rotation of the bass control gives a cut or boost of  $\pm 12\text{dB}$  at 100Hz and  $\pm 18\text{dB}$  at 30Hz. The treble control gives  $\pm 12\text{dB}$  at 10kHz and  $\pm 15\text{dB}$  at 20kHz. The frequency response curves of the tone control are shown in Fig. 33.

### POWER SUPPLY

The complete stereo pre-amp requires approximately 35mA at 40 volts. A 470 ohm dropping resistor (R7) is included on the power supply board previously described and the h.t. line is decoupled in the pre-amp by C52 (500 $\mu\text{F}$  64V).

The mains supply lead is connected to the pre-amplifier where the earth is connected, the live and neutral leads being switched by S6 and fed out to the main amplifier together with the earth. This part of the circuit must be carefully screened from the rest of the pre-amplifier, the small chassis supplied with the case specified being ideal for this.

### CIRCUIT BOARD CONSTRUCTION

The pre-amplifier components are mounted on one large fibreglass printed circuit board, Fig. 34. Sixty-seven turret tags are used, numbered 36 to 102 as indicated in Fig. 35. The high frequency filter coils L2 and L102 should be wound as indicated in the pre-amplifier components list, with the wires colour coded with sleeves for identification. The coils are fastened to the printed circuit board with either nylon or brass 4B.A. bolts and connected as follows:—

L2 Start-82, 15kHz-83, 10kHz-84, 7kHz-85, 5kHz-86.  
L102 Start-68, 15kHz-69, 10kHz-70, 7kHz-71, 5kHz-72.

The component values should be thoroughly checked at this stage since it will be difficult to rectify mistakes after the 67 tags have been wired up.

Note: In Fig. 23 (December 1970 issue) the lead from the neutral connection on SK4 should go to the OV tag on T1 and not to the screen as indicated.

Next month: final construction details.


## P.E. PROJECTS ON VIEW


The P.E. Gemini aroused much interest when it was demonstrated, together with the P.E. Aurora Lighting Display, last Autumn at the London Audio Fair.

It is hoped to provide a further opportunity for readers to hear this amplifier during the Public Address Engineers' Exhibition "Sound 71" to be held at Camden Town Hall, London, from March 16-19.

The P.E. Aurora Lighting Display, due to commence publication in a few months' time, will also be on show at "Sound 71," and additionally, at the "Electric Theatre" Exhibition organised by the Institute of Contemporary Arts, and to be held in London, mid-March to mid-April.

Further details will appear next month.

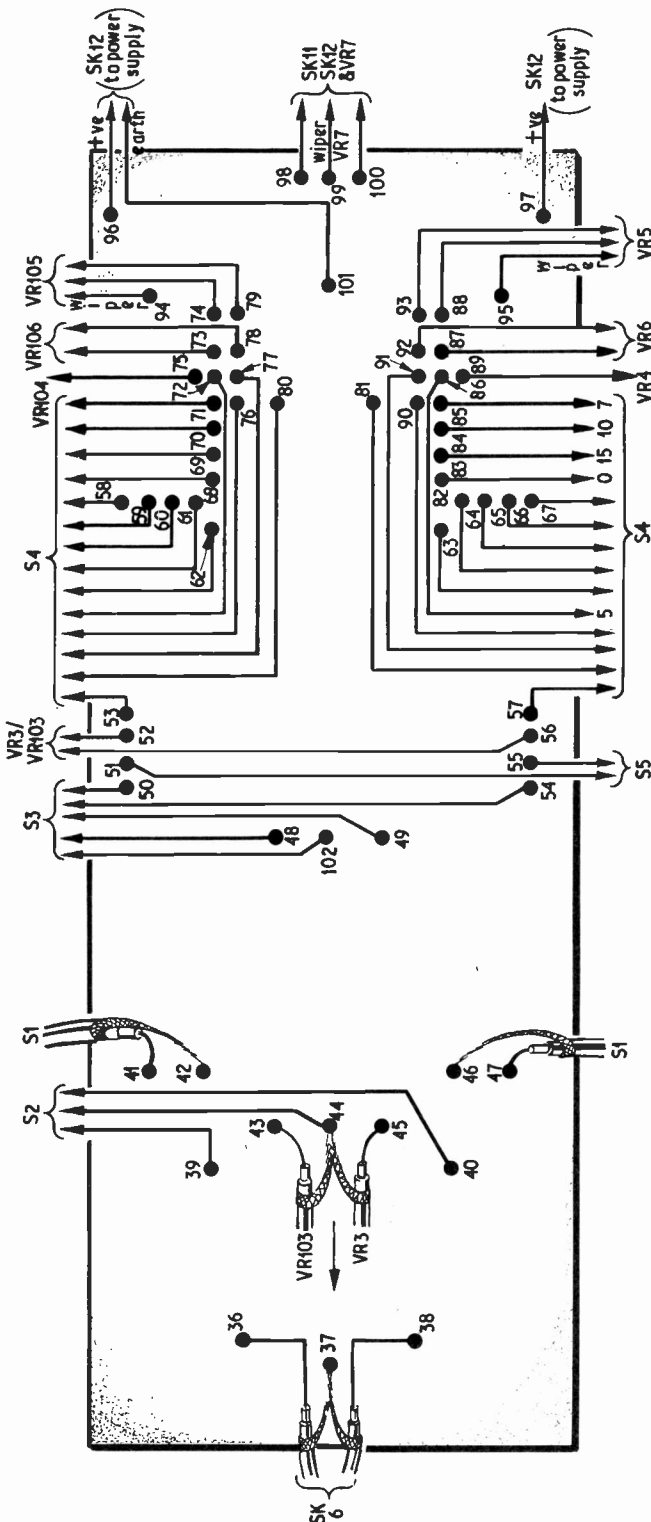

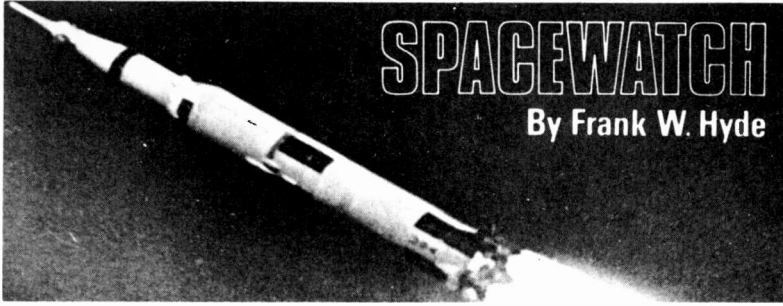

## THE MAN WHO CAME BACK

The United States' first man in space, Alan B. Shepard, watched with satisfaction the slow movement of the *Saturn-Apollo* rocket moonship to become *Apollo 14* as it moved toward the launching pad on November 9, 1970.

He first made history in the space age when he made a 15 minute suborbital flight almost ten years ago on May 5, 1961. From then, he became almost forgotten for he was grounded by a condition of the inner ear.

During the remainder of the 60's he remained on the sidelines, although still in the "astronaut corps", where he helped to train young and new astronauts, some of whom became heroes of space. Now he comes back as mission commander for the *Apollo 14* flight.

Captain Shepard undertook, on his own decision, to have an operation for the minor problem of his inner ear. Although he was perfectly fit on the ground, space doctors were afraid that his balance might be affected under space conditions. This has now been cured and the first astronaut becomes the leader of the *Apollo 14* mission to the Fra Mauro region.

## SPIN-OFF FROM SPACE RESEARCH

When space research comes up in conversation, there are still many who do not appear to be aware of the advantages that have affected the daily life of the community. Indeed, many would be surprised at the number of new techniques that are in common use, which were the direct result of some specialised facet of a space requirement.

A few of these are given here and will help perhaps to act as a reminder of the number of things that are taken for granted with no thought given to their origin.

The latest example is an automated technique for the detection of urinary tract infections. The device uses a very sensitive photo-electronic recorder to detect a flash of light when certain chemicals (luciferin and luciferase) contact bacteria in the urine sample.

A single specimen can be tested in 15 minutes and the instrument can accept a further sample in one

minute after completion of the previous one. This compares with the normal 24-48 hour period required with the bacteria culture methods.

This new technique opens up many possibilities. With such rapid testing there is no need to treat patients with anti-biotics while waiting for results. The new device also paves the way for inexpensive mass testing of people for suspected infections like diabetes, kidney and bladder diseases. Experienced microbiology staff would be freed for more advanced work.

The testing of urine is a common diagnostic tool in many hospitals no matter what the suspected ailment may be. The origin of this particular device came from the design of an instrument to detect life on other planets.

The chemicals responsible for the "cold light" emitted by fireflies, spark when coming into contact with a high energy biochemical called adenosine triphosphate. This compound is found universally in living organisms so that the activation of the chemicals would indicate that a form of life was present.

## OTHER EXAMPLES

A few more examples of spin-off are listed below with their origins.

(a) A special computer technique developed to enhance the television pictures sent back from Venus and Mars is now in use to clarify X-ray photographs in medical centres.

(b) A minute instrument developed to measure air pressures on small flight models used in wind tunnels has been applied to medicine. The instrument is so small that it can be introduced into an artery through a hypodermic needle, then manoeuvred through the artery to the heart, where it measures the blood pressure.

(c) In order to prevent the icing of spacecraft a special canopy was developed. This has been adapted as a cradle type of cover for the precise temperature control of a unit for housing premature babies. It has also been adapted for adults and a number of severely burned patients have been successfully treated.

(d) A sensor developed for astronauts sounds an alarm within ten seconds when a patient is threatened with the clogging of the trachea and

there is danger of strangulation. Immediate efforts to restore the breathing can be made.

(e) A new switch which is controlled by small movement of the head alone was developed for astronauts. This is now being used for handicapped patients who, with what is virtually another "arm", can operate a call board or even manipulate an electric wheel chair.

(f) Spray-on electrodes are now available so that a patient's electrocardiogram, taken while he is being rushed to hospital, can be radioed ahead to the waiting doctor, who can take immediate action on the patient's arrival.

(g) New alloys, that have been developed for space use, can be adapted for use in artificial limbs and joints. The alloys are the result of a discovery by NASA metallurgists that hexagonal crystals make better bearings than the normal cubic crystal structure.

(h) A lunar walker with eight legs has been applied to the relief of handicapped people. It allows a considerable freedom of movement and can be controlled from a chin cup by those who are not able to use arms or hands.

## MAKING WATER ON THE MOON

A new and important step toward the sustaining of life on the moon has been made at the Manned Spacecraft Centre of the U.S. Space Agency. The first experiments provided a pound of water from 100 pounds of soil. This could be increased to 14 pounds per 100 pounds of soil, if it were concentrated magnetically.

The process is a simple one and ideally suited to the moon (though it can be used on earth). A mirror is used to concentrate the sun's rays on a container of soil and raise its temperature to between 600 and 1,300 degrees centigrade. Hydrogen is then introduced into the container. It reduces the oxygen atoms in the soil to form steam. When this is cooled it condenses to water.

To obtain oxygen, steam is passed through an electrolysis cell where the steam separates into oxygen and hydrogen. The oxygen can come from an iron-titanium oxide called ilmenite. This is abundant in the lunar soil as revealed by the samples brought back by the *Apollo 11* and *Apollo 12* astronauts.

The hydrogen would have to be taken to the moon but it could be recirculated and used many times over to produce more oxygen.

None of the lunar specimens have been used for the purpose of this experiment. The soil was made from the proper proportions of ground basalt from Hawaii and ilmenite from Canada. However, the scientists responsible have sufficient faith in the process to have taken out a patent for the process.

# take a good look at **ANTEX** miniature soldering irons



G 18 watts. Fitted 3/32" bit for miniature work on production lines. Interchangeable spare bits, 1/8", 3/16" and 1/4" available. For 240, 220 or 110 volts. £1.80 (36/-)



E 20 watts. Fitted with 1/4" bit. Interchangeable spare bits 3/32", 1/8", 3/16" available. For 240, 220, 110 volts. From £1.80 (36/-)




ES 25 watts. Fitted with 1/8" bit. Interchangeable bits 3/32", 3/16" and 1/4" available. Ideal for high speed production lines. For 240, 220, 110, 24 or 12 volts. From £1.80 (36/-)



F 40 watts. Fitted 5/16" bit. Interchangeable bits 1/4", 3/16", 1/8", 3/32" available. Very high temperature iron. For 240, 220, 110, 24 or 20 volts. From £2.35 (47/-) Spare bits and elements for all models and voltages immediately available from stock.

### Complete precision soldering kit

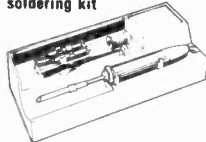

PLUS 36-page booklet on "How to Solder"—a mine of information for amateur and professional

This kit—in a rigid plastic "tool-box"—contains

- Model CN 15 watts miniature iron, fitted 3/32" bit interchangeable spare bits 3/32", 1/8"
- Reel of resin-cored solder
- Felt cleaning pad
- Stand for soldering iron

From Electrical and Radio Shops or send cash to Antex. £2.75 (55/-)



Model CN 240/2  
15 watts - 240 volts £1.70 (34/-)  
Fitted with nickel plated bit (3/32") and in handy transparent pack. From Electrical and Radio Shops or send cash to Antex.



### PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone Plymouth 67377/8  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following irons
- | Quantity | Model | Bit Size | Volts | Price |
|----------|-------|----------|-------|-------|
| .....    | ..... | .....    | ..... | ..... |
| .....    | ..... | .....    | ..... | ..... |

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

.....PE2

# VARIABLE VOLTAGE TRANSFORMERS

## LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt d.c. op. price £1.25 plus 12p P. & P. ORP12 including circuit. 62p each. Post Paid.



**A.C. MAINS MODEL.** Incorporates Mains Transformer, Rectifier and special relay with 1 make, 1 break H.D. contacts. Price inc. circuit £2.75 plus 12p P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75 P. & P. 18p.



## SANWA MULTI RANGE METERS

New Model U-50DN Multi tester. 20,000 OPV, mirror scaled with overload protection. Ranges—d.c. volts: 100mV, 0.5V, 5V, 250V, 1,000V; a.c. volts: 2.5V, 10V, 50V, 250V, 1,000V; d.c. current: 5µA, 0.5mA, 5mA, 50mA, 250mA. Complete with battery and test probe. £8.00 post paid.

TEN OTHER MODELS. LEAFLET ON REQUEST.

## 'AVO' MODEL 48A

Ex-Admiralty in good condition with instructions, leads, plus d.c. Shunts for 120 amp and 480 amp a.c. Transformer for 60 amp and 240 amp. Multiplier for 3,600V. Complete outfit in fitted case. £15.00. P. & P. 50p.

## ELECTRONIC ORGAN KIT

Easy to build, Solid State.

Two full octaves (185 sharps and flats). Fitted hardwood case. Powered by two penlite 1½V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Have all the pleasure of building this instrument and finish with a functional and instructive gift for any boy or girl. Price £3.00. P. & P. 22p.

## 50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7.75. P. & P. 30p.

## RECHARGEABLE BUTTON CELLS

2 x 1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp 10 hour rate, complete with 200/250V a.c. charger. Fully tested and unused. Price 48p each plus 8p P. & P. or 2 units for £1.00 post paid.



## UNISELECTOR SWITCHES

**NEW** 4 Bank 25 24V d.c. operation. £5.88, P. & P. 12p. 6 Bank 25 24V d.c. operation. £6.50, P. & P. 12p. 8 Bank 25 24V d.c. operation. £7.62 plus 22p P. & P.



## VENNER Electric Time Switch

200/250V Ex. GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75, 15A £3.25, 20A £3.75. P. & P. 18p. Also available with solar dial ON dusk. OFF dawn. Price as above.



INPUT 230/240V a.c. 50/60  
OUTPUT VARIABLE 0-260V

**BRAND NEW**  
Keenest prices in the country.  
All Types (and Spares) from  
1/2 to 50 amp from stock.



8 AMP

**SHROUDED TYPE**  
1 amp, £5.50. 2.5 amp, £6.75. 5 amp, £9.75. 8 amp, £14.50. 10 amp, £18.50.  
12 amp, £21.00 15 amp, £25.00. 20 amp, £37.00. 37.5 amp, £72.00. 50 amp, £92.00.



1/2 AMP

**OPEN TYPE (Panel Mounting)** 1/2 amp, £3.92. 1 amp, £5.50. 2 1/2 amp, £6.62. Carr. extra on open types.

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard, S.C.R. Unijunction Xenon Tube and instructions £3.25, plus 25p P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £9.45 38p P. & P.


## HY-LYGT STROBE

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 ioules. Price £10.88. P. & P. 38p.

## 7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 52p. P. & P. 12p or post paid with kits.
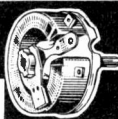
## Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 3/4 in, dia. 1/2 in. All at £1.50 each. P. & P. 7p.

50 WATT. 1 1/2/10/25/50/100/250/500/111-1/2-5/5kΩ. All at £1.12 each. P. & P. 7p.

25 WATT. 10/25/50/100/250/500/111-1/2-5/5kΩ. All at 78p each. P. & P. 7p.

## RELAYS NEW SIEMENS, PLESSEY, Etc. MINIATURE RELAYS - COMPETITIVE PRICES

	1	2	3	4	1	2	3	4
52	6-9	6M	42p*	700	12-24	2 c/o	6M	62p*
180	6-12	2 c/o E-E	42p*	700	16-24	6M	62p*	
185	6-12	4 c/o E-E	50p*	1250	24-36	4 c/o	6M	62p*
230	6-12	2 c/o	62p*	1250	36-45	6M	62p*	
280	6-12	2 c/o	73p*	2500	36-45	6M	62p*	
780	16-25	4M 2B	62p*	5800	80-85	4 c/o	62p*	
700	16-24	4 c/o	78p*	9000	40-70	2 c/o	50p*	
				15K	85-110	6M	50p*	

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price E-E Ex. Equipment. All Post Paid.

## MAINS RELAY

230V a.c. coil 3 c/o. 10 amp a.c. contacts, 72p plus 8p P. & P.

## HOSIDEN DH-02-S Stereo Headphones

8 ohm impedance 20-12,000Hz. Adjustable head band. Price only £2.38. P. & P. 12p. Complete with lead and stereo jack plug.


## MOTOROLA MAC II/16 PLASTIC TRIAC 400 PIV. 8 AMP

Now available **EX STOCK**. Supplied with full data and applications sheet. Price £1.5 plus 7p P. & P.

## PARVALUX TYPE SD19 230/250 VOLTS A.C.
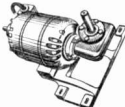
### REVERSIBLE GEARED MOTOR

30 r.p.m. 40lb in. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first class running order. A really powerful motor offered at a fraction of makers' price. £6.30. P. & P. 50p.



## NEW 9TH EDITION RADIO VALVE AND TRANSISTOR DATA

Characteristics of 3,000 Valves and Cathode Ray Tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits

Compiled by A. M. Ball

15/-

Postage 2/-

HI FI YEAR BOOK 1971  
£1. Postage 2/-.

ELECTRONICS POCKET BOOK by J. P. Hawker/J. A. Reddihough. 28/-, Postage 1/-.

TAPE RECORDERS by H. W. Hellyer. 45/-, Postage 1/6.

TUNERS & AMPLIFIERS by John Earl. 42/-, Postage 1/6.

BEGINNER'S GUIDE TO RADIO by Gordon J. King. £1. Postage 1/-.

TRANSISTOR AUDIO & RADIO CIRCUITS (Mullard) 30/-, Postage 1/-.

TRANSISTOR MANUAL (G.E.C.) 21/-, Postage 1/6.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books  
19-21 PRAED STREET  
LONDON, W.2  
Phone: PADdington 4185  
Closed Saturday 1 p.m.

## P.E. GEMINI STEREO AMPLIFIER

Preamplifier P.C.B. (Stereo) 39s (£1.95)  
Main amplifier P.C.B. (Stereo) 29s (£1.45)  
Power Supply P.C.B. 12s (60p)  
Preamplifier Semiconductors (Stereo) 35s (£1.75)  
Main amplifier Semiconductors (Stereo) 145s (£7.25)  
Power Supply Semiconductors 50s (£2.50)  
Packing & Postage on all orders 3s (15p)  
The fibreglass P.C.B.'s are drilled and roller tinned.

Mail order only, C.W.O., from:  
**I. M. SHAW & D. S. GIBBS**  
4 ELEANOR ROAD, ROYTON, OLDHAM, LANCs.

Your local component stockist

East Anglia  
**E**agle  
**E**lectronics  
agle St.

**IPSWICH** 58075

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. P.E. 87 BRIDGMAN ROAD, LONDON W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0576

# MAKING THE MOST OF LOGIC IC's

## PART EIGHT—By R. W. GOLES

### TTL SYSTEMS

HAVING discussed TTL gates and flip-flops in previous articles, let us now see how these circuits can be put together to perform specific tasks.

#### SYNCHRONOUS COUNTER

These counters can become quite complex when counts which are not binary multiples are required, and it is beyond the scope of this article to delve into the design procedure necessary.

Straight binary counts are, however, quite simple in design. As an example, have a go at a divide-by-sixteen counter of this type. Remember that a JK flip-flop will change state when both its J and its K input, or inputs, are at 1. If they are anything other than this, the information presented will merely be stored in the flip-flop. The truth table of a binary counter shows that any given flip-flop in the chain is required to change state only when all the flip-flops preceding it are in the 1 state.

If all the stages are clocked simultaneously, but only the J and K inputs of any stage are at 1 when the preceding flip-flop outputs are also 1, the flip-flop acts as a synchronous counter. By feeding the Q outputs of the earlier stages into an AND gate, and feeding its output into the J input (the K input may be left as a permanent one), the required JK inputs are satisfied.

Fortunately, flip-flops are available with this AND gate built in. The 7472 will be ideal as a synchronous counter and is shown in Fig. 8.1. Note that with this type of counter the number of AND gate inputs increases linearly with the number of stages in the counter.

If a five stage version is required, external gates would be needed because there are only three inputs to the internal J gates on the 7472.

#### SHIFT REGISTERS

Shift registers are used in logic circuitry as a form of temporary storage, or memory, and may contain either a number or some form of instruction which is represented by a number. The basic shift register would consist of a string of flip-flops with the outputs of the first connected to the inputs of the second and so on. A common clock line initiates the propagation of information down the register when required.

If JK flip-flops are employed in such a register, the Q outputs are connected to the J inputs of the following flip-flop, and the  $\bar{Q}$  outputs are connected to the K inputs. If, on the other hand, a type D flip-flop is employed, only one interconnection is needed, i.e. Q output to D input. For this reason, it is easier to deal with the type D for such use, and the diagrams will be simpler as a result.

#### SERIAL INPUTS

A basic shift register is shown in Fig. 8.2a. If the register is in the all 0 state, and the data input is connected to the output of a similar register which contains a binary word, say 10101, then on the first clock pulse (both registers clocked), a 1 will be entered into the first flip-flop.

On the second clock pulse a 0 will be shifted into the first flip-flop, and the one which it contained previously will be shifted into the second flip-flop.

On the third clock pulse another 1 will be entered into the first stage, a 0 will be entered into the second stage and a 1 into the third stage.

This process continues until after five clock pulses; the word which was in the first register has been transferred completely into the second. If the input of the first register had been connected to a permanent 0 during this period, it would now contain all 0.

This type of shift register operation is termed serial-in/serial-out, and although it is the primary way in which registers are employed, it is by no means the only way. Consider Fig. 8.2b; the register shown here is identical to the first except that all the Q outputs are taken out at once, enabling us to extract the stored word in parallel form, perhaps to drive indicator lamps, or even another register.

This kind of register is operating in the serial-in/parallel-out mode, and its operation is obvious.

#### PARALLEL INPUTS

Its complement, the parallel-in/serial-out register, shown in Fig. 8.2c, takes advantage of the type D flip-flop asynchronous inputs to enter data into the register.

This input data could come from the type of register described previously or from a bank of switches or relays. The only thing to bear in mind in this case is that a "low" voltage on the preset input sets the Q output to 1 (high voltage level) and a low voltage on the clear input sets the  $\bar{Q}$  output to a 1.

To start the sequence the register must be cleared by applying a low input to the common clear line, so that all the stages contain zeros. Next the input data to be stored is connected in parallel to the preset inputs; this must be inverted data, because a low input sets up a high output.

When the data is required to be shifted out, five clock pulses are applied to the clock line, and the output data is taken from the final stage of the register in serial form.

As an alternative, the circuit in Fig. 8.2d could be employed to achieve the same result if both the "true" and the "not" version of the input data is available. In

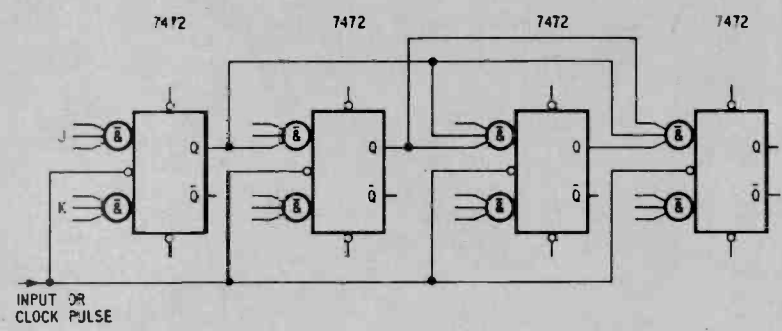


Fig. 8.1. Synchronous counter to divide by sixteen

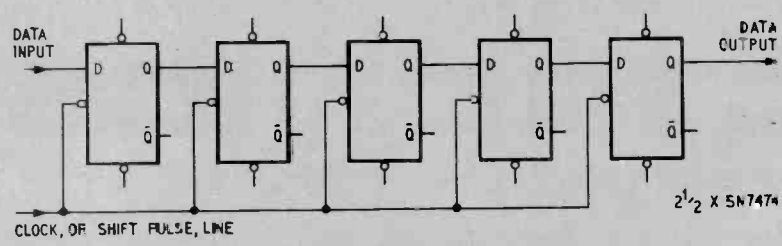


Fig. 8.2a. Serial in, serial out register

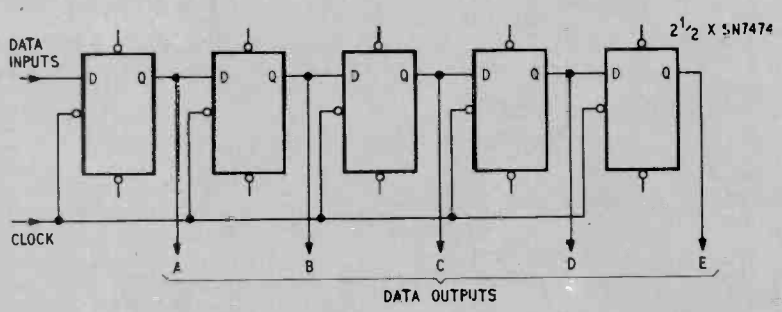


Fig. 8.2b. Serial in, parallel out register

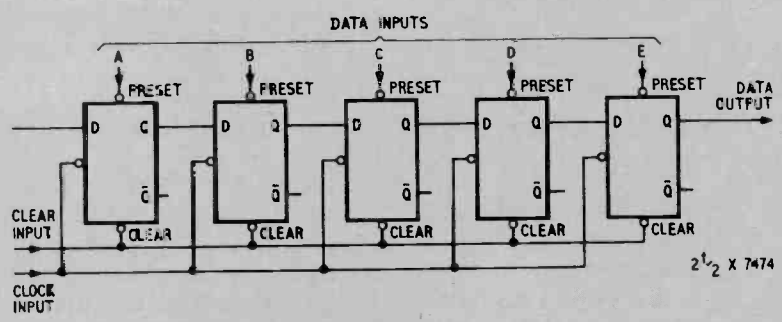


Fig. 8.2c. Parallel in, serial out register

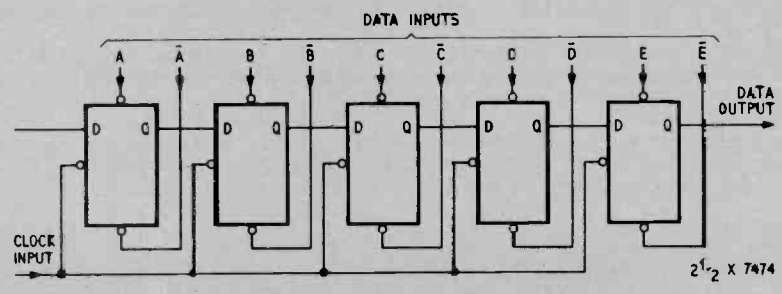


Fig. 8.2d. Alternative version of Fig. 8.2c




# LOOK!

**PRACTICAL!**

**VISUAL!**


**EXCITING!**

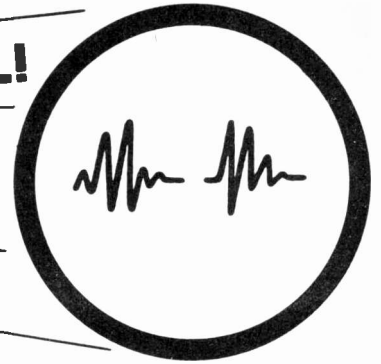

a new 4-way method of mastering  
**ELECTRONICS**  
 by doing — and — seeing . . .


**1** ▶ **OWN and HANDLE** a

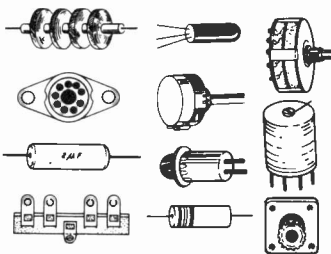complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**




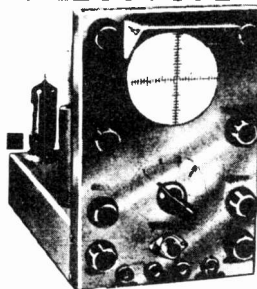**2** ▶ **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



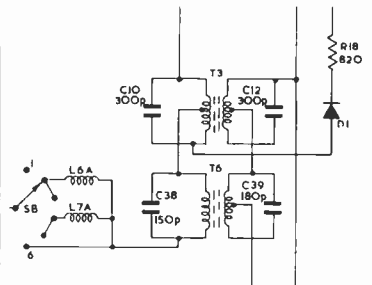**3** ▶ **READ and DRAW and UNDERSTAND** **CIRCUIT DIAGRAMS**



**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- AMPLIFIERS
- OSCILLATORS
- SIGNAL TRACER
- PHOTO ELECTRIC CIRCUIT
- COMPUTER CIRCUIT
- BASIC RADIO RECEIVER
- ELECTRONIC SWITCH
- SIMPLE TRANSMITTER
- A.C. EXPERIMENTS
- D.C. EXPERIMENTS
- SIMPLE COUNTER
- TIME DELAY CIRCUIT
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
 for  
**BROCHURE**

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... **BLOCK CAPS**

ADDRESS..... **PLEASE P.E. I**

# STEPHENS

## ELECTRONICS P.O. BOX 26 AYLESBURY BUCKS.

### SEND S.A.E. FOR LISTS GUARANTEE Satisfaction or money refunded

The Diamond Tip is .007in radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.  
**BRITISH MADE**  
EXPORT ENQUIRIES WELCOMED

### CARTRIDGES

ACOS	Inc. P.T.	each	Inc. P.T.
GP79	12/6	8X6M S/S	36/3
GP91-18C	21/-	8X6H S/S	36/3
2-11	17/9	8X5M D/S	39/11
12-49	15/6	8X5H D/S	39/11
50-500	13/6	X4N D/S	27/3
GP91-28C	As above	<b>GOLDRING</b>	
GP91-38C	As above	850	£5.50
Suitable to replace TCR, etc.		(1800)	£7.70
GP92	26/5	(800E)	£15.00
GP93-1	24/9	(4300 Super E)	£19.10.0
GP94-1	31/-	<b>RONETTE</b>	
GP94-5	36/-	105 S/S	19/10
GP95	24/9	106 S/S	19/10
GP96	31/6	DC400 S/S	14/-
Acos 104 1-10	41/10	DC400C S/S	14/-
11-25	39/9	103 D/S	22/4
25-50	38/3	106 D/S	22/4
51-499	35/5	DC400S D/S	16/9
		DC400C D/S	16/9
<b>B.S.R.</b>		<b>SOMOTONE</b>	
X3M S/S	27/9	8TA D/S	25/-
X3H S/S	27/9	9TA D/S	35/10
X5M S/S	27/9	9TAHC D/S	35/10
X5H S/S	27/9		

### STYLI

ACOS	Sapphire	Diamond	ELAC KST9	Sapphire	Diamond
GP39	2/6	7/6	(PE1B)	6/6	9/6
GP65	2/6	7/6	ER5ME	6/6	9/6
GP67	2/6	7/6	ER6MX	2/6	7/6
GP73-1	6/6	9/6	ER5 SB	6/6	9/6
GP73-2	2/6	7/6	ER60 Stereo	6/6	9/6
GP79	6/6	9/6	<b>DECCA</b>		
GP81-1	2/6	7/6	Gerrard... diamond-only		27/9
GP81-1	6/6	9/6	DEC	2/6	7/6
GP82	6/6	9/6	EV26 Stereo	2/6	7/6
GP91-3	6/6	9/6	GC8	2/6	7/6
GP91-18C	6/6	9/6	GC12	2/6	7/6
GP91-38C	6/6	9/6	GC810/1	2/6	7/6
GP93-1	6/6	9/6	GC810/2	2/6	7/6
GP94-1	6/6	9/6	S 1-2-3	2/6	7/6
GP95-1	6/6	9/6	TS1	6/6	9/6
GP96	6/6	9/6	TS2	6/6	9/6
HG P37	2/6	7/6	TS3	6/6	9/6
104	6/6	9/6	<b>GOLDRING</b>		
<b>B.S.R.</b>			CM50	2/6	7/6
BSR C1 (ST3)	6/6	9/6	CM00	2/6	7/6
BSR TC8H	2/6	7/6	MX1	2/6	7/6
BSR TC8M	2/6	7/6	MX2	2/6	7/6
BSR ST8	6/6	9/6	Stereo CS80	2/6	7/6
BSR ST9	6/6	9/6	<b>PERPETUUM ERNER</b>		
BSR ST10	6/6	9/6	PE188	6/6	9/6
BSR X1M	6/6	9/6	<b>PHILIPS</b>		
BSR X1H	6/6	9/6	AG3016	2/6	7/6
BSR X3M	6/6	9/6	AG3063	2/6	7/6
BSR X3H	6/6	9/6	AG3306	6/6	9/6
BSR X5H	6/6	9/6	AG3310/3006	6/6	9/6
BSR X4H	6/6	9/6	AG3400	2/6	7/6
<b>COLLARO</b>			<b>RONETTE BINOFLUID</b>		
Collaro Studio			BF40	2/6	7/6
Collaro-Ronett			DC284	2/6	7/6
TX88	2/6	7/6	<b>SOMOTONE</b>		
Collet SK1	2/6	7/6	2T	6/6	9/6
Dual CBS2/CD53			3T	6/6	9/6
(DN2)	6/6	9/6	9TA	6/6	9/6
Dual CDS/320			9TA	6/6	9/6
(DN3)	6/6	9/6	9TA/H	6/6	9/6
ELAC KST9	6/6	9/6	19T	6/6	9/6
(PE10)	6/6	9/6	20T	2/6	7/6

### DE BANKS MAGNETIC RECORDING TAPES

POLYESTER				POLYESTER				
Length	Spool Size in.	Price	Length	Spool Size in.	Price	Length	Spool Size in.	
Standard Play			900 ft.	5	14/-	1800 ft.	3	17/-
600 ft.	5	10/-	1800 ft.	3	20/-			
850 ft.	5 1/2	12/6	Double Play					
1200 ft.	7	14/-	1200 ft.	5	17/6			
Long Play			1800 ft.	3	22/-			
210 ft.	7	5/6	2400 ft.	7	26/-			
450 ft.	4	3/6						
<b>EMPTY TAPE REELS</b>			<b>CASSETTES</b>					
3 in. 1/6			Based in Plastic Library Packs					
4 in. 1/10			C60 10/6					
5 in. 2/3			C90 12/6					
9 1/2 in. 2/6			C120 17/6					
7 in. 2/7								

P. A. P. 1/6 on all orders.

### SEMICONDUCTORS - BRAND NEW - MANUFACTURERS' MARKINGS - NO REMARKED DEVICES

2N388A	12/6	2N2613	7/-	2N3708	3/6	2N5267	52/6	AC128	4/-	BC115	6/6	BD132	19/6	BFY30	10/-	D16P4	8/-	NKT238	5/-	OC22	10/-
2N404	4/6	2N2614	6/6	2N3709	3/6	2N5306	7/6	AC154	4/6	BC116	12/6	BDY10	27/6	BFY41	10/-	GET102	6/-	NKT240	5/6	OC23	10/6
2N690	4/-	2N2646	11/6	2N3710	4/-	2N5306	8/-	AC176	5/6	BC16A	7/6	BDY11	37/6	BFY43	12/6	GET113	4/-	NKT241	5/6	OC24	11/6
2N697	4/-	2N2696	6/6	2N3711	4/-	2N5307	7/6	AC187	12/6	BC117	7/9	BDY17	37/6	BFY50	4/6	GET114	4/-	NKT242	4/-	OC25	10/-
2N698	5/6	2N2711	6/6	2N3713	5/6	2N5309	7/6	AC188	7/6	BC118	6/6	BDY18	48/6	BFY51	4/6	GET119	4/6	NKT243	12/6	OC26	6/6
2N699	12/6	2N2712	6/6	2N3714	5/6	2N5309	12/6	AC187	5/6	BC121	6/6	BDY19	6/6	BFY52	6/6	GET119	4/6	NKT243	3/6	OC28	12/6
2N706	2/6	2N2713	5/6	2N3819	7/-	2N5310	8/6	AC198	5/-	BC122	4/-	BDY20	30/6	BFY53	4/6	GET120	10/6	NKT245	4/-	OC29	15/-
2N707A	2/6	2N2714	6/6	2N3823	22/6	2N5354	5/6	AC199	5/-	BC125	11/-	BDY38	19/6	BFY56A	11/6	GET873	2/6	NKT261	4/-	OC35	8/-
2N708	3/-	2N2865	12/6	2N3826	6/-	2N5355	5/6	ACY20	5/-	BC126	11/-	BDY60	30/-	BFY75	6/6	GET880	6/6	NKT264	6/6	OC36	12/6
2N709	12/6	2N2904	7/6	2N3864	5/6	2N5356	6/6	ACT21	5/-	BC134	11/6	BDY61	30/-	BFY76	6/6	GET887	4/-	NKT264	6/6	OC38	4/6
2N718	5/-	2N2904A	8/-	2N3884	5/6	2N5365	9/6	ACY22	4/-	BC140	7/6	BDY62	27/6	BFY77	11/6	GET889	4/6	NKT272	4/-	OC42	5/-
2N718A	6/6	2N2905	6/6	2N3885	5/6	2N5366	6/6	ACT28	4/-	BC147	3/6	BDY66	27/6	BFY80	13/6	GET890	4/6	NKT274	4/-	OC44	4/-
2N726	5/6	2N2905A	6/6	2N3886	6/6	2N5367	11/6	ACT49	4/6	BC148	3/6	BF117	6/6	BFW58	6/6	GET896	4/6	NKT275	6/6	OC45	2/6
2N727	6/6	2N2906	6/6	2N3886	6/6	2N5457	7/6	ACY41	5/-	BC149	3/6	BF163	7/-	BFW59	5/-	GET897	4/6	NKT281	4/-	OC46	3/-
2N914	3/6	2N2906A	6/6	2N3886A	7/-	2N5005	15/-	ACY44	8/-	BC152	3/6	BF167	6/6	BFW60	5/-	GET898	4/6	NKT401	17/6	OC70	3/-
2N916	3/6	2N2907	8/-	2N3888	5/-	2N5020	37/6	AD140	8/-	BC157	4/-	BF173	6/6	BPX25	37/-	MAT100	6/-	NKT402	18/-	OC71	2/6
2N918	6/6	2N2907C	3/6	2N3888A	6/-	2N5102	6/6	AD149	11/6	BC158	3/6	BF177	6/6	BPX29	36/-	MAT101	6/-	NKT403	15/-	OC72	2/6
2N929	4/6	2N2924	3/6	2N3889	5/6	2N5103	6/6	AD150	12/6	BC159	4/-	BF178	7/-	BPY10	28/-	MAT120	6/-	NKT404	12/6	OC74	6/6
2N930	5/6	2N2925	3/6	2N3889A	6/6	2N5104	6/6	AD161	12/6	BC160	12/6	BF179	14/6	BPY19	3/6	MAT121	6/-	NKT405	15/-	OC75	4/6
2N987	10/6	2N2949	6/6	2N3889A	6/6	2N5107	7/6	AD162	7/6	BC167	3/6	BF180	7/6	BPY20	3/6	MJ400	21/6	NKT406	12/6	OC76	4/6
2N1131	5/6	Green	2/6	2N3886	30/-	2N5602	5/6	AF106	8/6	BC168B	2/9	BF181	6/6	B8N21	7/6	MJ420	22/6	NKT451	12/6	OC77	5/6
2N1132	6/6	Yellow	2/6	2N3877	5/6	2N5603	5/6	AF114	5/6	BC168C	3/6	BF184	5/6	B8N26	9/6	MJ421	22/6	NKT462	12/6	OC78	5/6
2N1302	3/6	Orange	2/6	2N3877A	6/-	3N863	37/6	AF115	6/6	BC169B	2/9	BF185	8/6	B8N27	9/6	MJ430	20/6	NKT463	9/6	OC81	4/6
2N1303	3/6	2N3011	6/6	2N3900	7/6	3N128	18/6	AF116	5/6	BC169C	2/9	BF194	4/6	B8N28	6/6	MJ440	19/6	NKT603F	6/6	OC81D	4/6
2N1304	4/6	2N3014	6/6	2N3900A	8/-	3N140	19/6	AF117	5/6	BC170	3/6	BF195	5/6	B8N60	16/6	MJ480	19/6	NKT613F	6/6	OC83	5/6
2N1305	4/6	2N2053	6/6	2N3901	19/6	3N141	19/6	AF118	12/6	BC171	3/6	BF196	8/6	B8N61	12/6	MJ481	25/-	NKT674F	6/6	OC84	5/6
2N1306	5/6	2N3054	11/-	2N3902	7/6	3N142	19/6	AF119	4/6	BC172	3/6	BF197	8/6	B8N76	4/6	MJ490	20/6	NKT677F	6/6	OC85	5/6
2N1307	5/6	2N3055	15/-	2N3904	7/6	3N143	12/6	AF124	5/6	BC175	5/6	BF198	8/6	B8N77	5/6	MJ491	27/6	NKT678	6/6	OC139	6/6
2N1308	6/6	2N3133	6/6	2N3905	7/6	3N152	22/6	AF125	4/6	BC182	4/6	BF200	7/4	B8N78	5/6	MJ1800	43/6	NKT717	8/6	OC140	6/6
2N1309	6/6	2N3134	6/6	2N3906	7/6	R.C.A.		AF125	4/6	BC183	4/6	BF224	6/-	B8Y10	5/6	MJE340	12/6	NKT734	5/6	OC170	6/6
2N1507	5/6	2N3135	5/-	2N4058	5/6	4000A	13/6	AF127	3/6	BC184	4/6	BF225	6/-	B8Y11	5/6	MJE520	17/6	NKT736	7/6	OC171	6/-
2N1613	5/6	2N3136	5/-	2N4059	5/6	40250	10/-	AF139	7/6	BC182L	4/-	BF237	6/6	B8Y24	3/6	MJE521	17/6	NKT773	5/6	OC200	6/6
2N1631	8/6	2N3340	19/6	2N4060	5/6	40261	19/6	AF178	9/6	BC183L	3/6	BF238	6/6	B8Y25	3/6	MJF105	8/6	NKT781	8/6	OC201	6/6
2N1632	8/6	2N3340	26/-	2N4061	4/6	40309	8/6	AF179	9/6	BC184	4/6	BF237	6/6	B8Y26	3/6	MJF105	8/6	NKT781	8/6	OC202	6/6
2N1637	8/6	2N3350	7/6	2N4062	4/6	40310	11/6	AF180	10/6	BC187	5/6	BF224	9/6	B8Y27	3/6	MJF104	7/6	NKT10339	6/6	OC202	6/6
2N1638	7/6	2N3391	4/-	2N4244	9/6	40311	9/6	AF181	8/6	BC121L	4/6	BFX12	4/6	B8Y28	3/6	MJF105	7/6	NKT10419	6/6	OC203	6/6
2N1639	7/6	2N3391A	6/6	2N4245	8/6	40312	12/6	AF186	13/4	BC213L	5/4	BFX13	4/6	B8Y29	3/6	MKS3638	6/6	NKT10439	7/6	OC204	6/6
2N1701	32/6	2N3392	4/-	2N4254	8/6	40314	9/6	AF189	9/6	BCY10	5/6	BFX29	7/-	B8Y32	5/6	NP10013					

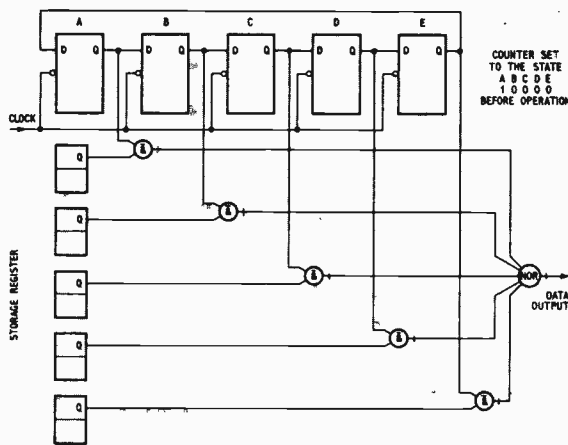


Fig. 8.3. Unitary or ring counter

this case there is no need for a common clear input, as any residual data in the register is "overwritten" by the input data.

Perhaps it would be as well to mention here that it is also possible to perform the parallel-in/serial-out function using the synchronous flip-flop inputs, but this does require extra gating to allow the D input to be connected either to the input data, or the preceding stage. A control line to order the register to "enter data" or "shift data" would also be necessary.

This winds up the subject of shift register construction and operation, but before leaving them, have a look at

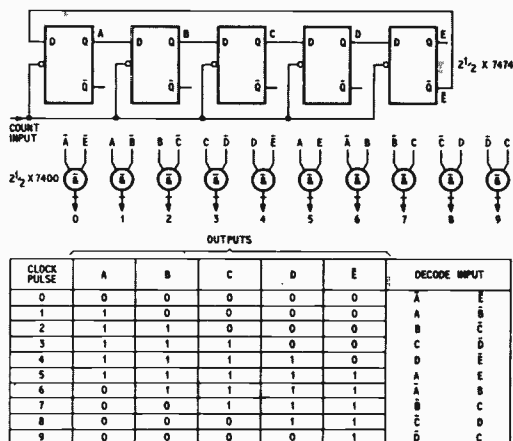


Fig. 8.4. Johnson decade counter with decoding

some uses of these registers, apart from simple data storage.

## RING COUNTER

Several types of counter can be built using a shift register, the simplest being the "unitary counter" or commutator. In this application the register is set, by means of the asynchronous inputs to the state 100000 . . . ; that is, a 1 in the first stage and zeros in all the others. The output is connected back to the input. On receipt of clock pulses, the 1 in the first stage is propagated down the register, round the end and back into the first stage again.

This process gives rise to another name for it, the "ring-counter", as all the stages of the register form a complete loop. These counters need a separate stage for each of the required counter states, but they have the advantage that no gates are necessary to decode a particular state.

A typical application of this kind of counter is shown in Fig. 8.3. Here the 1 travelling round the counter is used to enable each of the five NAND gates in turn, the other inputs of which are connected to a storage register. The outputs of the NAND gates are fed to a NOR gate, to convert the parallel data stored in the parallel register into serial form; the output is taken from the output of the NOR gate. If a binary counter is used in this position, decoding gates would be necessary.

## TWISTED RING COUNTER

A similar sort of arrangement is used to construct a "Johnson", or "twisted ring" counter, only in this case the Q output of the final stage is fed back to the input, not the Q output as before. These counters require only half as many stages as the unitary counters of the same cycle length, and do not normally need to be set to any special starting state, although this depends on the cycle length employed.

Their main advantages over binary counters are that they are synchronous and also any state, no matter how long the cycle length, can be decoded with only a 2-input gate. A typical application is shown in Fig. 8.4, a decade (divide by ten) counter, with decoding to decimal so that it could be used in frequency counters or similar equipment, where the outputs are used to drive "Nixie" indicator tubes.

## TTL MEDIUM SCALE INTEGRATION

When the manufacturers of logic integrated circuits were in full volume production of gate and flip-flop families, and the "bugs" were ironed out of the manufacturing process, so that a high yield was being obtained from each slice of silicon, it was a relatively straightforward process to increase the amount of logic contained in each package. The results of this second generation of i.c. manufacture are now readily available, under the name "medium scale integration" (MSI) or "complex function devices".

The logic family which has by far the greatest range of these is TTL.

Next month's article will consider the advantages of medium scale integration (MSI), in which several logic circuits are contained in one package, such as is used in the "Digi-Clock".

# SUBMARINE CHASER

Another war game by D. R. DAINES.

This can be added to Operation Seasearch, published in December 1970, or built on its own

**S**UBMARINE CHASER is very different from Operation Seasearch (December 1970 issue), but because both games utilise co-ordinate switching the opportunity has been taken to enclose both in the same unit, the game to be played being selected by a two-way four-pole rotary switch. As before we have North/South and East/West co-ordinates but with the added dimension of depth. To the submarine player, the depth represents the actual depth he is supposed to be; to the destroyer player the depth represents that at which his depth charges are set to explode.

By far the greater difference between this and last month's game, however, is in the method of search. Hunting the raider in Operation Seasearch was very largely blind; Submarine Chaser uses a pseudo Asdic.

## ASDIC

It is fair to say that the invention of asdic revolutionised anti-submarine warfare in World War 2, and the present game arose out of a desire to simulate as closely as possible the conditions arising out of the use of it, in game form. In real life, a searching vessel emits a high-frequency sound at regular intervals. The sound wave travels underwater at a regular speed dependent upon the temperature and salinity of the water. If the sound wave strikes a solid object it is reflected back and detected by listening gear. Obviously,

the time taken for the sound wave to travel the double journey is a fair indication of distance. If the reflecting body is a submarine, a series of readings taken over a period will enable course and speed to be determined.

The asdic used in this game works on a completely different principle, but is utilised in the same way and gives a convincing impression of genuine asdic. The difference of position between the submarine and the destroyer is represented by electrical resistance which affects the rate of a slow-running multivibrator. The multivibrator gates a high frequency audio tone which is monitored by both players through earpieces. The closer together the two vessels are supposed to be, the faster is the repetition rate. Means are provided whereby each player may obtain a "fix" on the position of the other.

## ASDIC PRINTED CIRCUIT BOARD

The asdic circuit is mounted on Veroboard, and comprises nine transistors (Fig. 1). Transistors TR1 and TR2 together comprise a fast-running multivibrator giving a high frequency square wave output taken off through D31. The variable clock circuit is formed by TR3 and TR4. The base voltage of TR4 is varied through a series of resistors shown in Fig. 2 (R18 to R27). The output is taken through D30, which, together with D31 and R7 comprises the gate.

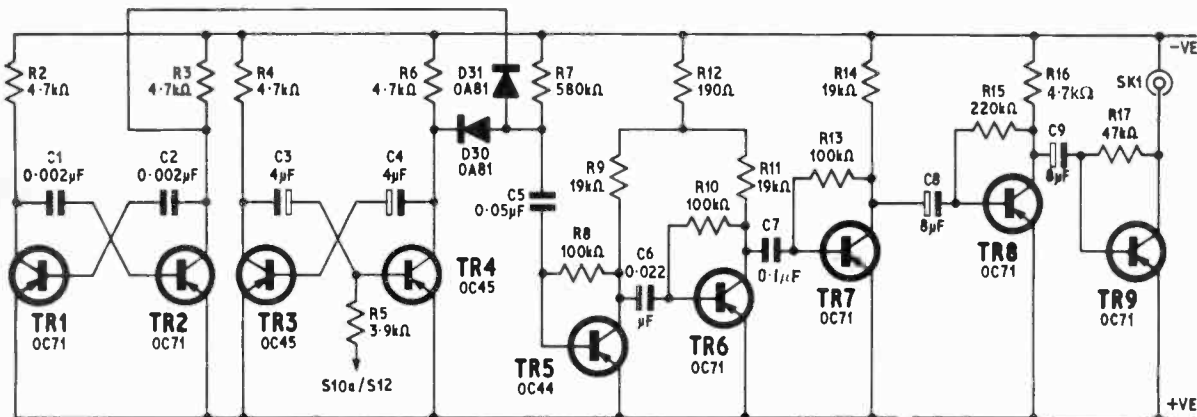


Fig. 1. Circuit diagram of the asdic board used in the Submarine Chaser game

The signal from TR2 will not pass forward unless a pulse is also present from TR4. Capacitor C5 is a d.c. de-coupler feeding the simple amplifier formed by TR5 to TR9. Final output from TR9 is fed to a miniature jack socket (SK1) into which a crystal ear-piece may be plugged. This is situated at the side of the unit, between the two players.

### DIRECTION FINDING

Referring briefly to Operation Seasearch, switches S5 and S6 controlled the horizontal co-ordinates of the destroyer. Here they do so again, but whereas switches S7 and S8 controlled the cruiser, S7 must now control the depth of depthcharges and S8 becomes redundant. Therefore the connecting link between S7 and S8 must be disconnected at "X".



In a similar way, switches S3 and S4 originally controlled the position of the supply ship. Switch S3 must now control the submarine depth and S4 becomes redundant. The two depth control switches S3 and S7 therefore work together and since this is a third dimension, extra wiring is called for here as well as an extra wafer on each; Fig. 2 will establish the idea.

Fig. 2a. Block diagram of Submarine Chaser

Fig. 2b. Wiring diagram of the switching arrangements for Submarine Chaser. If only this game is to be built, switch S15 can be omitted and this diagram and Fig. 1 then give the complete circuit

It will be realised that what is required for accurate direction finding of the opponent is a method of sampling the various co-ordinate lines. If this could be done, the one that gives the fastest repetition rate on the asdic will be the one which by-passes all the resistors and hence the one which corresponds with the position of the opponent's switch. If this is done with the North/South lines and the East/West lines, a very accurate "fix" can be achieved; Fig. 2 illustrates the method—the sampling switch is S14. As this switch passes through the left half of its sweep, it progressively by-passes resistors R18 to R22. When it coincides with the position of switch S1a (shown as position 5) the voltage applied to the asdic board will be at maximum, giving the fastest repetition rate. The player will therefore have detected the position of switch S1a.

In the right half of the sweep, the sampling switch will detect the position of switch S6, which is the player's own. This half of the sweep is therefore used by the

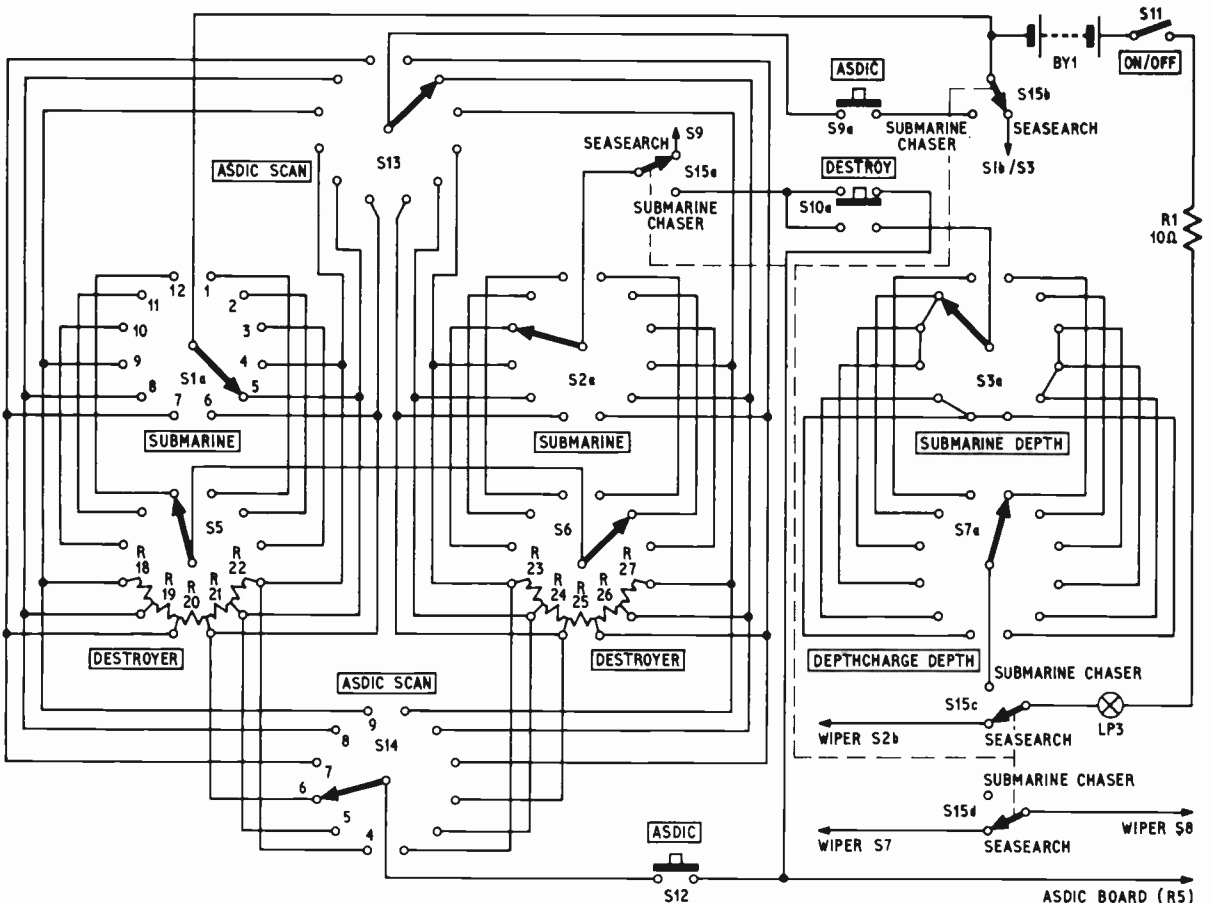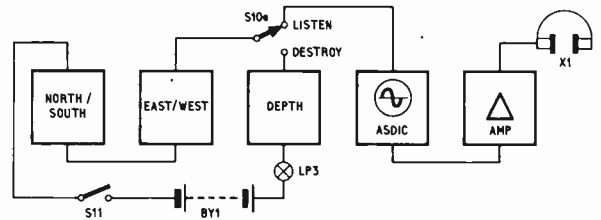

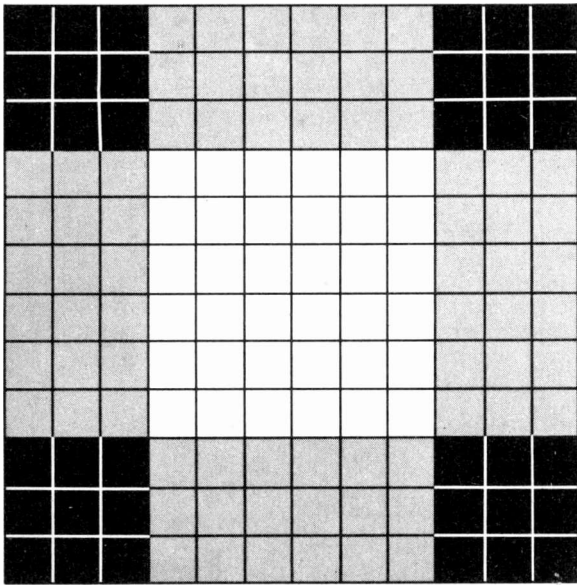


Fig. 3. Asdic detection pattern; white area—total detection; shaded area—partial detection; black area—no detection

opponent. It will be seen that two sampling switches are needed, the second is S13, which will detect switches S2a and S5. In use, the players in turn will use both switches but at opposite parts of the sweep. For convenience, the two halves of each sweep are given a dab of colour; red and blue corresponding to the Redland or Blueland player.

The sampling switches do not give a total fix, but only sample the centre six lines in each direction. This gives a detection pattern as in Fig. 3, where the white areas denote total detection, the shaded areas partial detection, and the black areas no detection at all. The game was designed in this way partly on the grounds of economy and partly because it was felt that total detection overall would not lead to such an interesting game. Readers who would prefer total detection will be able to adapt the circuit, but of course four sampling switches would be required instead of two.

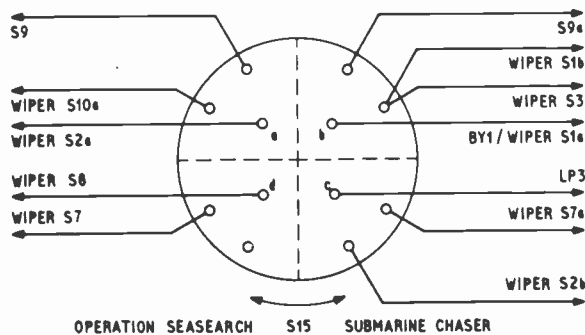


Fig. 4. Wiring of the game change switch S15

## CONSTRUCTION

Readers who built Operation Seasearch will have no difficulty if they installed the recommended switches. All wires are severed at the points marked "X" in the Seasearch diagram and taken to the game-change switch, which is a four pole changeover switch—not three pole. Then the wiring to switches S13 and S14 (Fig. 2) is added, as well as the wiring to the second wafers of S3 and S7. Constructors interested in this game only will find a complete parts list in this article; Fig. 1 and Fig. 2 form the complete circuit, game change switch S15 may be omitted if one game only is built.

## COMPONENTS . . .

### Resistors

R1	10Ω	(not required if Seasearch has been built)	R10	100kΩ
R2	4.7kΩ	R11	19kΩ	
R3	4.7kΩ	R12	190Ω	
R4	4.7kΩ	R13	100kΩ	
R5	3.9kΩ	R14	19kΩ	
R6	4.7kΩ	R15	220kΩ	
R7	580kΩ	R16	4.7kΩ	
R8	100kΩ	R17	47kΩ	
R9	19kΩ	R18 to R27	2.2kΩ (10 off)	
All ¼W, ±10% carbon				

### Capacitors

C1	0.002μF	C6	0.022μF
C2	0.002μF	C7	0.1μF
C3	4μF elect. 12V	C8	8μF elect. 12V
C4	4μF elect. 12V	C9	8μF elect. 12V
C5	0.05μF		

### Switches

	For Submarine Chaser only	Additional to Operation Seasearch
S1	1p 12w	
S2	1p 12w	
S3	1p 12w	
S5	1p 12w	
S6	1p 12w	
S7	1p 12w	
S9	1p make push button	
S10	2p 2w push button	1p 2w
S11	S.P.S.T. toggle	
S12	1p make push button	1p make
S13	1p 12w	1p 12w
S14	1p 12w	1p 12w
S15		4p 2w

(S15 is a four pole two-way switch, not three pole as stated in Seasearch article)

All rotary wafer switches except where stated

### Semiconductors

TR1, 2	OC71 (2 off)
TR3, 4	OC45 (2 off)
TR5	OC44
TR6-9	OC71 (4 off)
D30, 31	OA81 (2 off)

### Miscellaneous

- SK1 Miniature jack socket
- LP3 6.3V 0.06A (MES bulb, clip-on holder—not required if Seasearch has been built)
- BY1 9V battery type PP6 (not required if Seasearch has been built)
- Case components (see list in Dec. 70 issue)
- Three knobs with pointers
- Crystal earpiece lead and jack plug
- Veroboard
- 6B.A. fixings and spacers

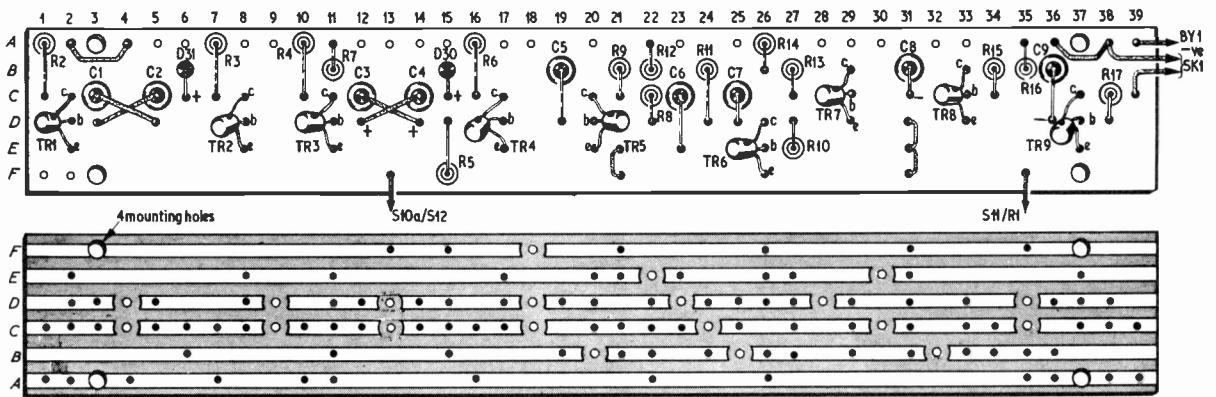


Fig. 5. Component layout and wiring of the asdic board

S10 is a two-pole change-over type, a d.p.d.t. switch may be used, but when playing, care must be taken to leave it in the off position; one pole is of course used for Operation Seasearch, and the other pole for this game. Switches S9 and S12 are labelled "Asdic" and S10 labelled "Destroy". In the off position S10 shunts the output from S2a to the asdic board. When depressed, the output goes to the depth wafers, switches S3a and S7a. If these are set at the correct depth lamp LP3 is lit and a hit registered. The asdic board is constructed as shown in Fig. 5 and fitted under the chassis near the lamps.

Switches S13, S14 and S15 are inserted through the three holes made in the side of the case described in the previous article. Push-button S12 is inserted in the spare hole on the top panel and SK1 can be sited in any position convenient to both players and the asdic board. The switches can be labelled as shown in Fig. 2.

Submarine Chaser is designed to be built in conjunction with Operation Seasearch but where the reader wishes to build Submarine Chaser alone it can be constructed in a case similar to that shown in the photographs. No map details are required for this game, the map—which is 7 inches square—is simply lettered to designate the co-ordinates. The case is constructed of aluminium and when bent to shape is pop riveted; the case shown measures 15 × 9½ × 3½ inches.

Lamps LP1, LP2 and LP3 are arranged under the map to illuminate corresponding numbers.

### DEPTH

It will be seen that no Asdic detection is used for the destroyer player to determine depth. This is partly off-set by grouping the depth lines in the following way. The first position of the submarine switch (S3a) denotes that the sub is on the surface—this line is left on its own. The second line denotes periscope depth; the last denotes that the sub is sitting on the bottom; these two are also solo lines. The other nine positions are grouped in threes by shorting links on S3a (Fig. 2), which are optional and left to the constructor's discretion. It is felt that if the destroyer player has to guess the submarine depth it is asking too much for him to choose from 12 positions.


### METHOD OF PLAY


The co-ordinates of the destroyer are adjusted so that he is at any peripheral square. Since the action is assumed to take place in a section of open sea, map details are totally ignored. A token is placed on the map to correspond with the destroyer's position. The submarine's position is adjusted to any one of the four central squares and at any depth he chooses. Only if he chooses to be on the surface must a token be placed because of course each ship can see the other. If he chooses depth two (periscope depth) the destroyer token remains but the submarine token is removed, whereas if he is any deeper both tokens are removed as neither can see the other. This simple rule of course applies throughout the game.

The destroyer moves first—or a coin is tossed. The destroyer moves a knight's move of two forward and one to the side, or one forward and two to the side. He may "drop" depth charges on each square through which he passes, he does this by pressing the "destroy" button. The depth charges may be adjusted for depth once each move.

The submarine moves minimum while submerged. That is, one square in any direction and one square up or down. Only while on the surface may he move two squares.

For the destroyer the game is thus quite simple—the destruction of the submarine, signalled as soon as the lamp is lit. For the submarine, life is a little more complicated. He can win the game either by escape or by sinking the destroyer. He escapes when he manages to reach the edge of the playing area, but with this one proviso—if the opponent can correctly guess the very first time to which edge he has gone, the game must continue for at least another ten moves.

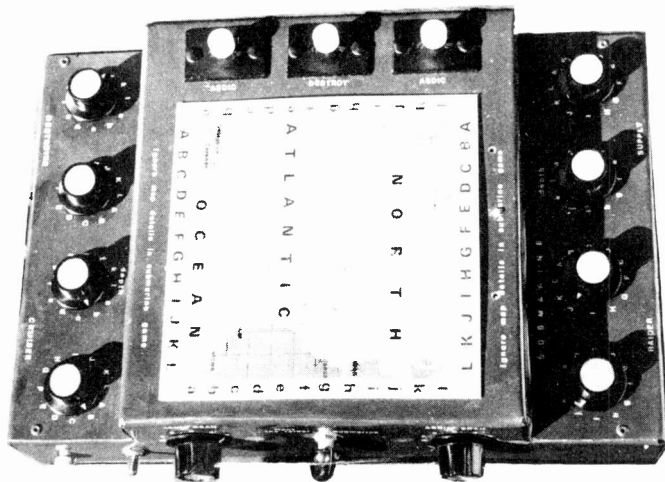

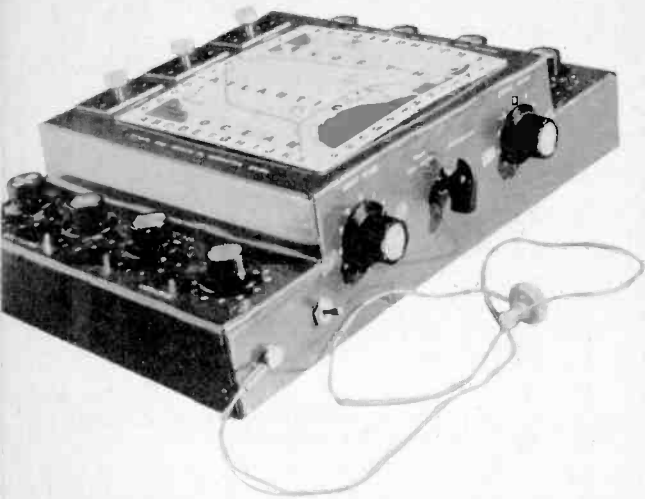

### TORPEDOES

The submarine can sink the destroyer by means of torpedoes. Only one is required. He may fire torpedoes only whilst on the surface or at periscope depth, but may not rise and fire in the same turn. A torpedo is fired when he is in line with the destroyer—a queen's move of any number of squares up, down, across, or diagonally. Here he simply claims the hit and reveals the positions of his controls.

### VARIATIONS

For a really exciting game, try using a stopwatch or kitchen timer, allowing each player 30 seconds to listen and move. Better still, allow the first player one minute, but each succeeding move must be made in less time than the one preceding. Another variation would render it impossible for vessels to reverse direction in succeeding moves. The destroyer would then move in a series of loops, and the submarine would turn a maximum of 45 degrees on each move. The submarine might be allowed to sit on the bottom with engines off. Disconnect the Asdic and allow the destroyer three or four runs before giving up.

### USING BOTH GAMES TOGETHER

The two games can be used together in a variety of ways. For example, the "Blue" player might run a convoy from Halifax to Britain, trying to avoid the submarine wolf-pack lying in wait. If contact is made the Red player scores one ship sunk before the destroyer escort is alerted. Play then transfers to the second game. If the sub escapes, play goes back to the first, and so on, until either the remnants of the convoy reaches Britain, or (say) five submarines are sunk. It might also be pointed out that the third dimension need not necessarily be depth. It might just as well be height. For submarines, read "bombers" and for asdic read radar. The two games together really have very wide scope, but perhaps enough has been said to get readers thinking for themselves.

Some readers might want to have their submarines rising to the surface in order to use deck guns as well as torpedoes, but here we are entering the very complicated world of naval gunnery. For this we really need the subject of a future article—a naval gunnery computer. ★

# IT'S LIGHTING UP TIME!!

A combined automatic lighting up reminder and parking light for the motorist.

With this unit you will never drive away without switching on your lights and you will never have to worry about turning on your parking light at dusk and off at dawn.

A simple invaluable project for motorists.

**WE CONTINUE OUR  
SERIES OF SPECIAL  
PROJECTS FOR THE  
BEGINNER WITH.....**

***A Simple Receiver***

**PRACTICAL  
ELECTRONICS**

MARCH ISSUE  
ON SALE FEBRUARY 18

**ORDER YOUR COPY NOW!**



# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## I.C. POWER AMPLIFIER

We have recently received a comprehensive pamphlet describing four types of hybrid audio power amplifiers. These integrated circuit amplifiers require only the addition of a power supply, coupling capacitor and loudspeaker to form a high quality audio amplifier capable of giving 10, 20, 25 or 50 watts continuous output power, depending on the type.

Manufactured by Sanken Electric Co. Ltd. (Japan) and available through Photain Controls Ltd., Randalls Road, Leatherhead, Surrey, the amplifiers have the following brief specification:

Harmonic Distortion at Full Power Level 0.8 per cent maximum.

for S1-1010A (10W) and SH020B (20W), 0.5 per cent maximum

for S1-1020A (25W) and S1-1050A (50W)

Frequency range at 1W output 20Hz to 100kHz for all types. Price S1-1010A—£5, S1-1020B—£7, S1-1020A—£8, S1-1050A—£11.

The amplifiers must be driven from a preamplifier or other source giving approximately 1V audio output to the amplifier. A feedback resistor is incorporated to give a voltage gain of about 30dB and the circuits will withstand an output short circuit for more than 5 seconds.

The modules are intended for use in hi-fi, public address and musical instrument applications, and should prove excellent due to their small size and high output power.

## COMPONENT SPARES

Many readers like to carry out their own repairs to their television receivers but often find great difficulty in replacing components.


We have been informed that the firm of Claygate Electronics specialise in radio and television replacement components and as a result of recent expansion plans are now able to supply readers with any of their large range of components in small quantities.

As a result of the expansion they are now approved stockists for: Plessey, Hunts, ITT, Lemco, Egen Electric, Erie, Morganite, Newmarket, Multicore and Solderstat components. For small items like resistors and capacitors they can only supply a minimum number of five components. But for larger items they are prepared to supply "one off's".

At the time of going to press they were preparing to publish a catalogue and details and further information can be obtained from Claygate Electronics Ltd., 2, Stoke Newington High Street, London, N.18.
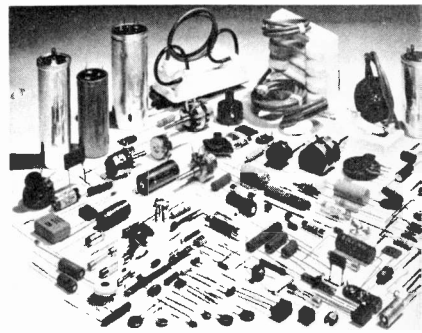
## IRON ACCESSORIES

New from Solderstat (manufacturers of the Elremco-Wolf range of soldering tools) are a snap on iron transit cover and a universal iron stand. The transit cover is for use with the firm's MS and HMS series of miniature and heavy duty miniature soldering irons. This inexpensive accessory is particularly useful where soldering irons are used for servicing and maintenance work, since it allows the user to pack away the iron without waiting for it to cool down;



Group of television components available from Claygate Electronics

for this reason the transit cover has been included in the new Solderstat 12 volt motorist pack.

Suitable for the same range of irons as the transit cover, the universal stand is a die cast aluminium alloy stand that can either be fixed to a vertical or horizontal surface. The stand contains a bit cleaning pad, is finished in stove enamel and retails at around 27s (£1.35).

## MULTI-PURPOSE PLIER

A useful tool for the workshop is the Hunter 55 multi-purpose plier that can cut, strip and crimp wires, now being marketed by Henri Picard and Frere Ltd.


A serrated edge between the handles and the plier joint has six notches in graduated standard sizes to strip wires. Just between the serrated edge and the pivot joint the handles are sharpened to form a cutting edge for wire trimming.

The standard corrugated plier snout is extra long and has, close to the joint, a pair of specially designed shapes for crimping wires together.



The price of the Hunter 55 is 21s (£1.05) and details of local stockists can be obtained from Henri Picard & Frere Ltd., 34 Furnival Street, London, E.C.4.



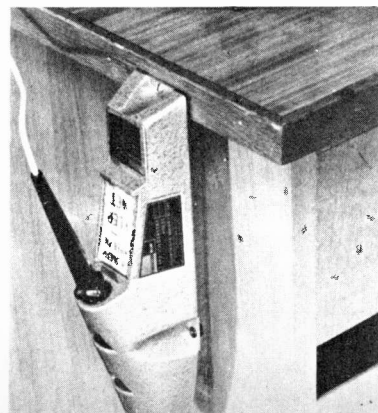Solderstat snap-on transit cover and universal soldering iron stand



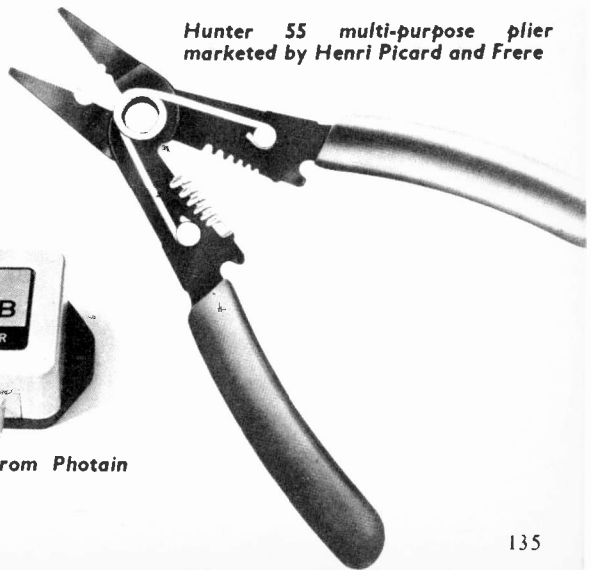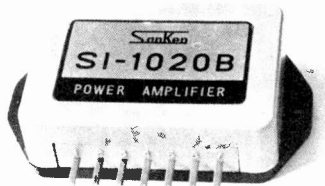Sanken i.c. amplifier from Photain Controls (half size)



Hunter 55 multi-purpose plier marketed by Henri Picard and Frere

# Meet the ladies...

**W**HY are there not *more* women in the electronics industry? It is undoubtedly one of the most popular branches of engineering for women, partly because it is a profession which can be applied in many widely differing fields; partly because it is a relatively new science with little tradition attached; and partly because the Second World War introduced many women into the vagaries of electronics. Yet only one engineer in the U.K. out of every 500 is a woman.

Perhaps some may think that girls don't have the capability, but this is far from the truth. Girls in other countries take up engineering as a career in far greater numbers, so why not British girls. It can't be lack of opportunity. There is a strong need for good engineers today, and Universities and Colleges up and down the country, offer places to suitably qualified girl students.

It seems that, in too many cases, girls, parents and teachers don't even consider electronics as a possible career for a girl. How many girls are brought up in such a way that, any innate interest in what is considered as boys' games and hobbies, is discouraged from a very early age. At school, girls are encouraged to take domestic science and biology rather than maths or physics. But in spite of all this, women have shown that they can be just as good as the men in electronics, if given the training and the opportunity.

There are organisations that do try to further the aims and interests of women in engineering, and especially in the electronics field. More about this later, but first let us look quickly at some typical examples.

## **ELSIE: INDUSTRIAL AUTOMATION**

Elsie's favourite subjects at school were maths and physics. After passing her G.C.E. "O" levels she took a post as Laboratory Assistant at a large local electronics factory, and studied electrical engineering on a part-time day release basis at the local technical college.

She worked first in the Test Department where she learned to use a wide variety of measuring and test instruments, and went on to designing and building special test equipment, under supervision of course.

Later she worked as one of a team of engineers on the digital control system for a satellite communications station, and as her interest in digital work increased she started to specialise in digital data transmission systems. Later she became a Contracts Engineer, responsible for more than one project, and discussing customers' problems, finding the solutions, and evolving detailed system specifications.

Now she has moved into industrial automation where she is Head of the Data Transmission Group, responsible for the profitability of all contracts within her Group and for the day-to-day supervision of 17 design and commissioning engineers.

## **ANNE: MICROWAVE ENGINEERING**

Anne graduated in physics but now works as a microwave engineer in an industrial research laboratory. Although her physics course covered the fundamentals, Anne was very unfamiliar with the practical aspects of microwave engineering.

However, she soon gained experience of using microwave instruments and applying microwave measuring techniques, and after a year or so was given a small project of her own, to develop a microwave Colometer for measuring microwave power. She has been given increasing responsibility involving the direction of junior engineers, the planning and costing of her work and liaison with the customer.

# WOMEN IN ELECTRONICS

By Dr. Elizabeth Laverick

PhD., F.I.E.E., F.Inst.P., S.M.I.E.E.E.





*Looking at the spectrum of a microwave solid state oscillator* (Elliott Bros. (London) Ltd)



*Setting up a problem on an analogue computer*

### **PAT: PROGRAMMING**

Another application of electronics very much to the fore nowadays is associated with computers, the design of computers and the use of computers in the business world, i.e. the scientific world, solving problems and in automation.


Pat joined an electronics firm at the age of 18 when they offered to sponsor her for a four year sandwich course in Applied Physics at City University. She worked for one year before her course started, and then spent alternate six month periods at College and at the firm, gaining practical experience in laboratory applications.

On graduating she decided to go in for programming, and she joined a project team in the Computing Research Laboratory, investigating the feasibility of computer aided design, in particular, the automatic production of a printed circuit master from a logic diagram.
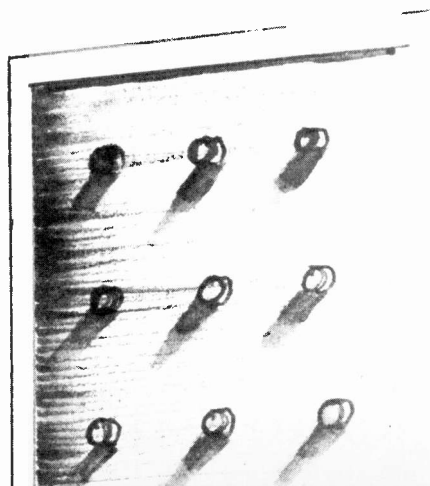
### **SUSAN: COMPUTER AIDED DESIGN**

Susan, too, works in computing. Unlike Pat she went for a full-time degree at Cambridge where she qualified as a physicist. Equipped with a degree, she moved into the computing industry. She became a project leader on computer aided design.

Women can also be found in production and in sales associated with electronics, the latter area involving much travel and liaison with customers.



### **THE WOMEN'S ENGINEERING SOCIETY**

In the light of the success which these women have made as electronic engineers, what can be done to encourage more girls to take this up as a career?

The Women's Engineering Society (which celebrated its fiftieth anniversary last year) does a considerable amount of voluntary work in this direction. The Society is a group of women with a common interest in a profession which is still generally considered to be a male preserve, and with a desire to help other girls and women who would like to be engaged in engineering, including electronics.

The coverage of the membership of the Society is large including every branch of professional engineering and the allied fields of metallurgy, physics, chemistry, mathematics and even personnel work. It covers also the fields of technical and scientific teaching, of technical writing and information services, and of engineering factory inspection.

The two most important aims of the Society are

- (i) To promote the study and practice of engineering among women, and
- (ii) To enable technical women to meet and correspond and to facilitate the exchange of ideas respecting the interests, training and employment of technical women and the publication and communication of information on such subjects.

It has been responsible for launching in 1923 the Women's Electrical Association to "interest the non-technical woman in electrical development". The name was soon changed to the "Electrical Association for Women", and as the E.A.W. it has grown exceedingly, now having several thousands of members throughout the country.

### **UNIVERSITY SCHOLARSHIPS**

This Society, the Caroline Haslett Memorial Trust, is a charitable body whose aims are to provide scholarships, travelling exhibitions and other educational opportunities for women who are seeking or already pursuing careers in the electrical industry or in other related fields requiring qualifications in science, engineering or domestic science. Among other things the trust awards university scholarships to girls in science, engineering and mathematics.

The Society maintains a list of engineering companies willing to train and employ women. A booklet on the

training of women for engineering under the title "Training and Opportunities for Women in Engineering", is available from the Society's offices.

### CAREERS ADVISORY COMMITTEE

The Society is actively engaged in careers work, taking part in conferences and exhibitions, contributing to careers conventions, giving talks at schools, answering careers enquiries, and giving advice and information on request to parents, careers teachers, Youth Employment Officers, and anyone who requires some guidance.

As a result of increasing government and public interest in women engineers, the Society has set up a Careers Advisory Committee as a Working Party to co-ordinate the Society's interests and activities in the fields of education, training and careers advice.

### CAREER AND MARRIAGE

Why, you may ask, should girls train for a career when they will almost certainly marry, and have a family? Well, there are several reasons. Quite apart from the fact that all young people, irrespective of sex, should be encouraged to develop their capabilities to the full, it is worth knowing that already more than one third of the jobs in this country are held by women. Statistics show that the average young lady of the 1970's will have finished having her family by the time she is thirty, leaving another thirty years in which to fulfil herself in other directions. It is also worth remembering that many semi-skilled jobs are being taken over slowly but surely by automation.

All of the four girls described in this article married early in their careers, and have managed to find time for hobbies, home and husband (not necessarily in that order!) as well as their careers.

It is quite surprising how many women have entered electronic engineering through a maths or physics degree, or have graduated or otherwise qualified through alternative training schemes.

Electronics as a career can be hard work but the rewards are good in all senses. There are equal opportunities in the majority of firms today—and equal pay—so if you have a daughter who wants to help you when you're building that latest circuit, don't discourage her—you may have a budding electronics engineer in the family after all. ★

The following organisations may be approached for further information appropriate to this article:

The Women's Engineering Society, and The Electrical Association for Women, 25 Foubert's Place, London, W.1.

Central Office of Information, Hercules Road, London, S.E.1.

Council of Engineering Institutions, 2 Little Smith Street, London, S.W.1.

The Careers Centre, 42 Conduit Street, London, W.1.

Women's Employment Federation, 251 Brompton Road, London, S.W.3.

Student Advisory Centre, 44 Albion Street, London, W.2.

# NEWS BRIEFS

## Radio Controlled Lunar Vehicle

THE *Luna-17* automatic station soft landed on the moon in the area of the Sea of Rains on November 17. Installed on board was a self-propelled moon vehicle *Lunokhod-1*. This vehicle has made short excursions over the moon's surface under direct radio control from the Russian earth station, where a crew of six technicians "drive" the vehicle and monitor the data transmitted from the many scientific devices carried aboard.

A programme of scientific studies and tests is being carried out by this automatic station, including investigation of cosmic rays, panoramic survey of the terrain, analysis of the chemical and physical properties of the lunar surface soil and rock, and the measurement of different parameters inside the vehicle.

In December, following a 2-week hibernation during the lunar night, *Lunokhod-1* resumed exploration activities upon command from earth control.

## 100 Years of Telecommunications in the City

SIR Peter Studd, in entering his year as Lord Mayor of the City of London, has chosen Communications as a theme for his year of office. This is an appropriate choice, since 1870 marked the centenary of the Post Office responsibility for telecommunications. In 1870, the Post Office took over the inland telegraph system. Nine years later the first telephone exchange in Britain was opened in the City of London. There were 13 names in the first telephone directory.

## Video Recording

VIDEO recording is a fast moving business at the present time and we are constantly receiving news of new products, processes and business agreements. In our December issue we published an *Electronorama* feature on this subject and since then we have received news of a portable recorder from Akai—the VT100—and two new licence agreements made by the E.V.R. Partnership.

The V100 recorder is said to be the first fully portable record/playback video recorder and it uses  $\frac{1}{4}$  inch tape. The Rank Organisation are marketing the complete Akai system consisting of the VT100 recorder, a camera with 4:1 zoom lens, clip on 3 inch monitor and batteries. The complete system costs £568 and a  $\frac{1}{4}$  inch tape giving 20 minutes recording time costs £4. The VT100 is intended for non-domestic use and is shown below.

The E.V.R. Partnership have recently announced two licence agreements, one with Mitsubishi Electric of Japan for the manufacture and distribution of EVR teleplayers internationally (with the present exception of the USA and Canada), and a similar agreement with Hitachi Ltd. of Tokyo. The agreement with Hitachi was concluded first and preceded the Mitsubishi agreement by less than one week.

These new agreements with giants in the powerful Japanese electronics industry add immensely to the international strength of the EVR organisation. In Great Britain, Rank Bush Murphy has announced that it will bring its new colour teleplayer into full production early in 1971.





# BOOK REVIEWS

## THE MUSIC LOVER'S ALL-IN-ONE GRAMOPHONE BOOK

By Vivian Capel  
Published by Focal Press Ltd.  
196 pages, 7in × 4½in. Price 15s (75p)

WITH a title brief like this the author has had to bend over backwards to compound an embracing 'all' in one slim volume. Whether he succeeds depends on the degree of technical sophistication of the music lover; certainly for the man who is a prospective equipment purchaser and who wishes to be led painlessly through the edge of the hi-fi jungle, this is a good buy.

From an opening chapter on the price versus quality aspect of reproducing equipment, the author goes on to examine sound and what constitutes music.

The translation of sound to disc, or the recording process is dealt with briefly with a succeeding chapter on simple stereo technicalities.

A comprehensive chapter on pickups and gramophone mechanics is simple and instructive, as is the chapter on amplifiers which also clarifies the bogey of specifications.

Loudspeakers and enclosures have a chapter to themselves and the advantages of earphones are discussed.

The remaining half of the book covers choice of equipment, improvements to existing equipment, practical hints on wiring, record selection and equipment maintenance.

Apart from a chapter describing the instrument members of the orchestra, which seemed rather misplaced in the context, I found this book both interesting and instructive.

G.G.

## RADIO AND AUDIO SERVICING HANDBOOK

By Gordon J. King  
Published by Newnes-Butterworths  
283 pages 10in × 6½in. Price 60s (£3.00)

THE second edition of this established work contains most of the original material published in the 1965 and 1967 editions, but includes up-dated information relevant to recent design techniques. These include field effect transistors, integrated circuits, stereo broadcasting and reception, stereo amplifiers, tuner amplifiers, compact music systems, cassette recorders.

A great deal of general information and advice is given in a straightforward manner. Some sections on valve equipment have been retained because of the large quantity still in everyday domestic use.

Although transistor equipment is usually very reliable, there are occasions when an understanding of principles goes a long way to avoid accidental damage during servicing, the most likely cases being during the insertion of semiconductors and testing. Several examples of different types of circuit are given to explain these principles and assist with fault location.

M.A.C.

## TUNERS AND AMPLIFIERS

By John Earl  
Published by Fountain Press Ltd.  
184 pages 8½in × 5½in. Price 42s (£2.10)

THIS is the first of a new series in the Fountain "How to Choose and Use" range of books. The author of this one uses his extensive background in the testing and description of commercial hi fi equipment to bring home to the hi fi enthusiast recent trends in equipment design in a very readable manner.

Technical descriptions are given in very plain language, so that the reader can attempt to unravel the many expressions appropriate to the subject.

Circuit design has progressed quite considerably during the past five years or so. In fact, much of the criticism levelled at transistor tuners and amplifiers in the past can be answered in the newest designs to be made available. Examples are the improved performance and reliability from the use of integrated circuits, varicap diodes for tuning, field effect transistors for front end amplification, inter-station muting, ceramic "crystal" i.f. resonators, overload protection circuits.

The merits of these and alternative designs are described in some detail. For those readers who have some background in audio and radio techniques, this book will help to up-date the image of quality sound reproduction, where it may have previously become prejudiced by old well-established valve equipment.

M.A.C.

## DICTIONARY OF TELECOMMUNICATIONS

By R. A. Bones  
Published by Newnes-Butterworths  
200 pages. 7½in × 5in. Price 45s (£2.25)

As stated in the title, this dictionary is concerned basically with telecommunications and only relates to associated electronic fields such as radio broadcasting and television where these fields overlap. However, taking into account the specified field of the book, one gets the impression that there can be very few terms not listed or adequately described by Mr Bones. In his preface he states that he gives the most recent terminology and that at the time of going to press the dictionary was as up to date as possible, and this is evident from the text.

Terms consisting of two or more words are adequately cross referenced and the descriptions given are concise if a little basic in some cases. No lengthy descriptions on operation of components or instruments are given, simply a description of the item and its function. A comprehensive and useful book for students and engineers alike.

M.K.

## RADIO AND TELEVISION YEAR BOOK 1970/71

Edited by Eric Ickinger  
Published by IPC Electrical-Electronic Year  
Books Ltd.  
226 pages 8½in × 5½in. Price 20s (£1.00)

TELEVISION has been included in the title of this, the third edition, colour and monochrome receivers being listed. Special attention is given to the "unit audio" type of system up to about £150. An introductory article on this subject is given at the beginning of the book. These and other equipments are listed with specifications and prices on the same lines as in the Hi Fi Year Book, and include radio and television receivers, tape recorders and record players.



# SONIC OBSTACLE

In this, the second and final article, the construction of the various sub-assemblies, setting up and final calibration of the locator will be dealt with.

## TRANSMITTER CIRCUIT PANEL

The layout and underside connections of the transmitter panel is shown in Fig. 9. Here a 4.1in by 1.7in Veroboard is bolted to a 3in by 1.8in sheet of 16 s.w.g. aluminium, which acts as a heat sink for TR7, and a mount for the transformer T1.

The complete transmitter panel assembly is bolted to the baseplate of the aluminium box by means of screws and stand-off spacers; this method of mounting also applies to the receiver circuit panels.

Drill holes to accept mounting screws for T1, and TR7. The two holes, where the circuit board bolts to the heat sink, should be reinforced with a solder tag soldered to the copper strip.

## TRANSFORMER ASSEMBLY

To prepare transformer T1, first remove the bobbin from inside the pot core by undoing the four clamp screws, taking care not to drop or otherwise damage the ferrite pot. Wind on by hand two layers (15 turns) of 20 s.w.g. enamelled copper wire for L2, and secure with a layer of plastics insulating tape. Slip red and blue sleeving onto the L2 leads, as shown in Fig. 10a.


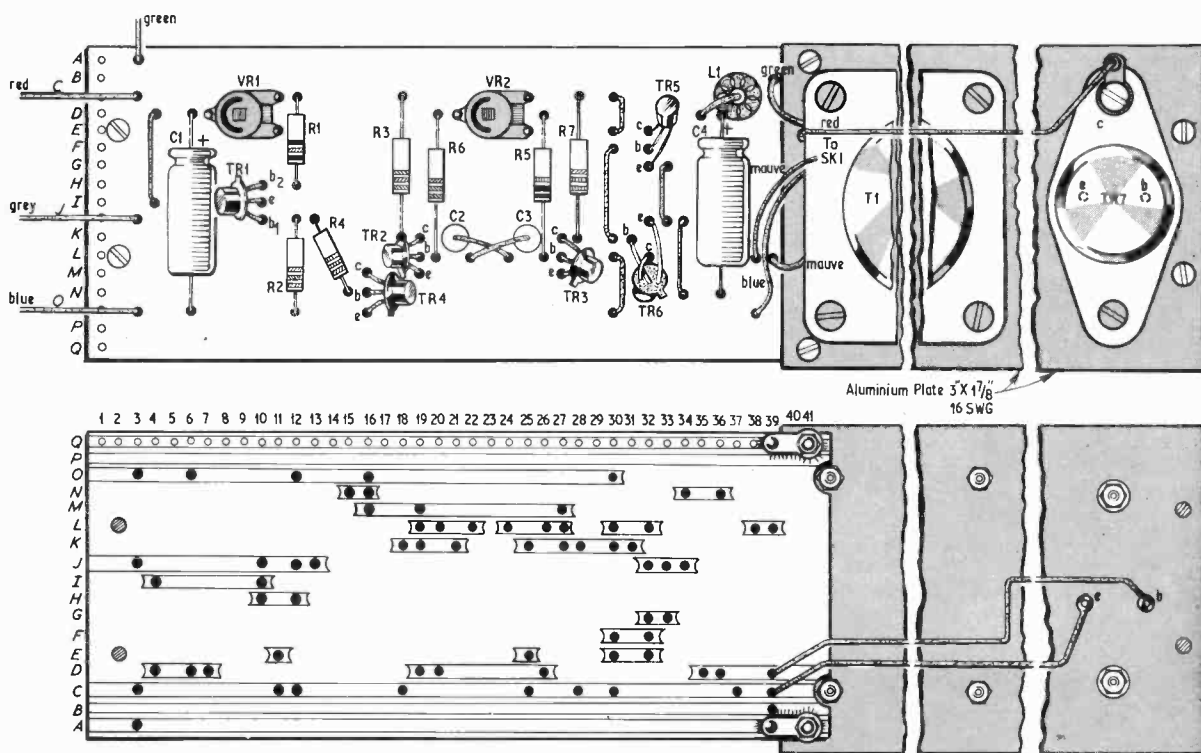


Fig. 9. Component layout and underside connections for transmitter panel

# LOCATOR

By D. Bollen

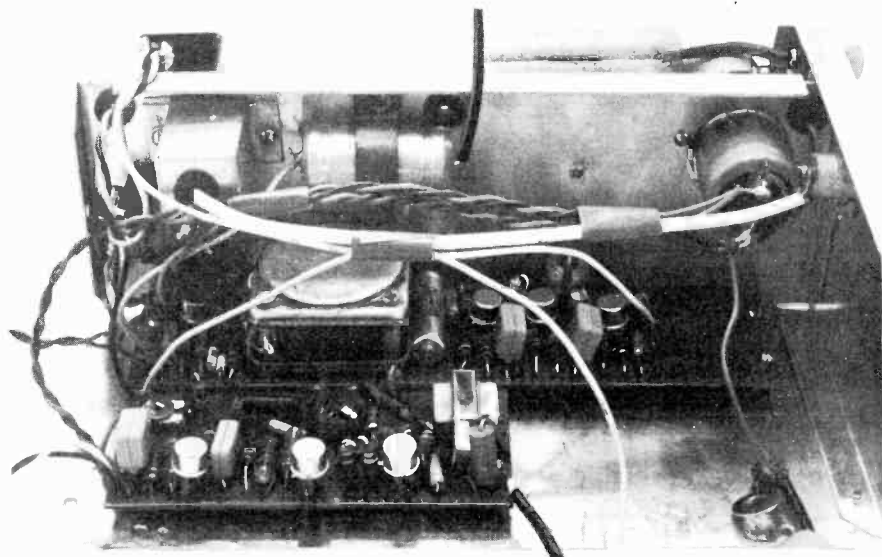

*View of the sonic locator interior showing the tuned amplifier panel and the decoder, the latter in the foreground. The transmitter panel is screened by the metal partition and so prevents circuit interaction. This can be seen more clearly in Fig. 13*

L3 consists of four layers of the same wire (30 turns) similarly secured with tape, and with mauve and green sleeving on the leads.

Bolt the assembled transformer to the heat sink, and mount TR7 complete with mica insulating washer, spacers, and collector solder tag.

When components have been assembled on the Veroboard, scrape the enamel off the ends of T1 leads, tin them, and insert in appropriate holes in the circuit board, then bolt the board to the heat sink and complete all wiring.

## PRELIMINARY TRANSMITTER TESTS

Connect a small 3 ohm loudspeaker to the green wire from the transmitter circuit panel and the mauve wire from T1. Place a non-polarised capacitor of about  $4\mu\text{F}$  in parallel with the loudspeaker.


Rotate VR1 and VR2 to the mid-track position, then join red and blue wires to a 12V battery. If the transmitter is working correctly, regular, loud clicks should come from the loudspeaker.

To check transmitter output, measure the peak to peak amplitude of the output at the loudspeaker with an oscilloscope, and convert the result to r.m.s.

If an oscilloscope is not available, temporarily short the collector and emitter of TR4. Connect an a.c. voltmeter across the speaker, and re-connect the battery

leads briefly. If all is well, an output in the region of 10–15V r.m.s. will be obtained.

Bearing in mind that the circuit is intended for pulsed operation, do not leave the battery connected for more than a few seconds while TR4 is shorted, otherwise the loudspeaker and output transistor could overheat.

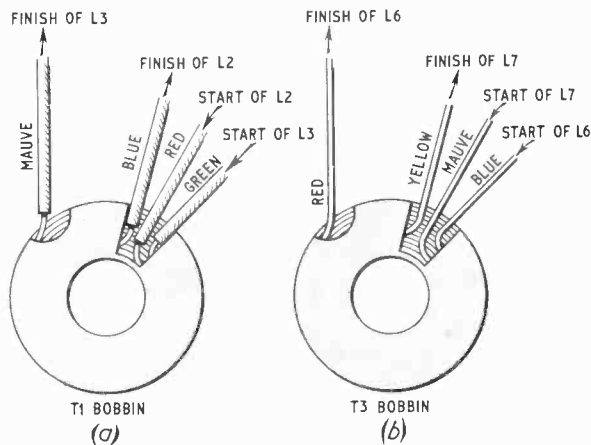

**Fig. 10.** (a) Coloured sleeves applied to T1 leads for identification; (b) sleeves applied to T3

## TUNED AMPLIFIER CIRCUIT PANEL

Drill mounting holes in the 6.9in by 1.6in amplifier Veroboard panel, according to Fig. 11.

An easy method of winding transformer T3 bobbin is as follows. A mandrel to take the bobbin is made by cutting a short length of dowel and inserting a twist drill tightly in its centre. If the dowel is a sloppy fit in the bobbin hole, it can be built up with Selotape.

With the mandrel twist drill gripped in the chuck of a hand-drill, which is mounted horizontally in a vice, L6 and L7 turns can be wound on quickly.

The fine 40 s.w.g. enamelled wire used for the T3 windings needs to be terminated by soldering on leads

VR5 and C11, and orange and blue wires to the screened cable of a 50 kilohm output impedance moving coil microphone. Note that the cable outer screen should connect to the blue wire.

Modifications to the microphone will be described later in the article.

Green and grey wires are left disconnected during the following tests. First, place a milliammeter in series with the red wire and the positive terminal of a 12V battery, then touch the remaining blue wire to the negative battery terminal. When assured that the amplifier current consumption is around 4mA, the milliammeter can be removed.

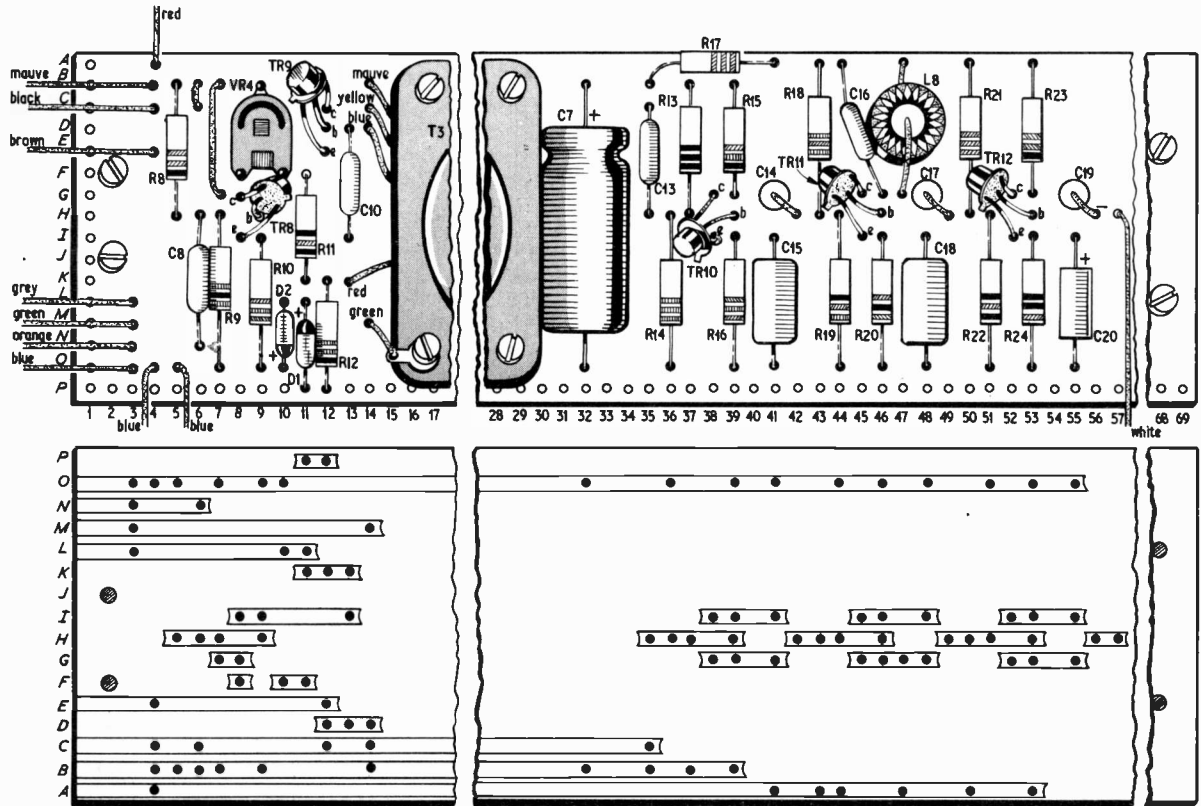


Fig. 11. Component layout and underside connections for tuned amplifier panel

of thin, multi-stranded (7/40) plastics covered wire; the joints thus made should be insulated with small pieces of plastics tape.

Starting with a mauve lead, wind on as evenly as possible 500 turns of 40 s.w.g. wire for L7. Finish off with a yellow lead, and secure the winding with tape.

L6 starts with a blue lead and consists of 100 turns of 40 s.w.g. wire wound in the same direction as L7, and is then terminated with a red lead. Bobbin details for T3 are given in Fig. 10b.

After gluing the completed transformer to the Veroboard, proceed with the assembly of the other components.

## PRELIMINARY TUNED AMPLIFIER TESTS

For the purposes of the following tests, the tuned amplifier circuit panel can be laid on a table top with the associated controls grouped around it.

Referring to Fig. 13, solder black and mauve circuit panel wires to TC1 and C12; blue and brown wires to

## USING THE TELEVISION SET

Position the microphone close to a 405 line television set, first making sure that the amplifier panel is some distance away to prevent stray inductive pick up from the TV line transformer.

Clip an a.c. voltmeter onto the white amplifier output lead and to battery negative, and re-couple the red lead to battery positive. With VR5 at half-track the a.c. voltmeter should read zero.

If there is a steady meter reading this will be caused by tuned amplifier instability. To minimise unwanted stray feedback, rearrange the meter leads and microphone cable, and slightly reduce the VR5 setting.

Now switch on the TV set and, with the volume control at minimum, obtain a steady picture. A 10-125kHz sound signal, picked up from the line transformer by the microphone, should now cause the a.c. voltmeter to read somewhere in the region of 1-4V. Tune the amplifier by adjustment of TC1 for a peak in output voltage.





## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 2 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response  $\pm 3\text{dB}$  12-30,000Hz. Sensitivity better than 50mV into 16 $\Omega$ . Full power bandwidth  $\pm 3\text{dB}$  12-15,000Hz. Bass boost approx. to  $\pm 12\text{dB}$ . Treble cut approx. to  $-16\text{dB}$ . Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide 8" deep 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or sent 3/6 plus large S.A.E.

**PRICES**  
AMPLIFIER KIT, £10.10.0. P. & P. 3/-.  
POWER PACK KIT, £5.0.0. P. & P. 5/-.  
CABINET, £5.0.0. P. & P. 5/-.  
(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.10.0. Post Free.

*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosqueue use, etc.*

**FANTASTIC 'POLY PLANAR' WAFFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER**  
Size only 11" x 14" x 1 1/2" deep. Weight only 19 ozs. Can replace one speaker in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature  $-20^{\circ}\text{F}$  to  $+175^{\circ}\text{F}$ . Power handling 10 watts rms (50 watts peak). Impedance 8 ohm only. Response 40 Hz—20 KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £5.15.0 each. P. & P. 5/-.

**MAGNA VOX DESK TYPE MOVING COIL MICROPHONE.**  
Medium impedance. Brand New—Special Price £2/-.  
P. & P. 2/-.

**SINGLE HEADPHONE.** With aluminium headband. Approx. 200 ohm. 5/-, P. & P. 1/6.

**CRYSTAL MIKES.** High Imp. for desk or hand use. High sensitivity. 1/8 $\text{p}$ . P. & P. 1/6.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE 8/1-. P. & P. 1/6.

**HIGH IMPEDANCE DYNAMIC STICK MIKES.** High sensitivity. 2/6 $\text{p}$ . P. & P. 2/6.

**SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG.** 400pF + 145pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s I.F. Price approx. 2 x 1 1/2 in. Only 8/6. P. & P. 2/6.

**HONEYWELL MICROSWITCHES S/P. C/O.** Push-button action. Rating 250v. AC at 15 amps. Size approx. 1 1/2" x 1" x 1". 5/- each. P. & P. 1/6 (6 or more post free).

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 6 section Lacquered Brass. Extends from 6" to approx. 20 1/2". Maximum diameter 1/4". 5/- each. P. & P. 1/6.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-20-30, 30-0-30V. at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. Price 35/6. P. & P. 6/-.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 14/-, P. & P. 2/6. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 17/6. P. & P. 2/6. Pri. 200/240V. Sec. 10-0-10 at 2 amp. 27/6. P. & P. 3/6. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 18/6. P. & P. 2/6.

**BATTERY CHARGER TRANSFORMERS.** 200/240V. Input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3 x 2 1/2 x 2 1/2 in. Brand New. Price 21/6. P. & P. 5/-.

**HIGH GRADE COPPER LAMINATE BOARDS**  
8 x 6 x 1/4 in. FIVE for 10/-. P. & P. 2/-.

**Open 9-5.30 Monday to Saturday**  
**Early closing Wed. 1 p.m.**  
*A few minutes from South Wimbledon Tube Station*

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2 in wide x 10 in deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.P. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £8.8.0.** Carr. 10/-.  
Also available in 8 ohm with EMI 13in x 8in bass speaker with parasitic tweeter, £6.10.0. Carr. 10/-.

### LOUDSPEAKER BARGAINS

3in 4 ohm 10/-, P. & P. 1/6. 6in 3 ohm 16/-, P. & P. 3/-.  
7 x 4in 3 ohm 21/-, P. & P. 4/-, 10 x 6in 3 or 15 ohm 25/-, P. & P. 6/-, E.M.I. 8 x 5in 3 ohm with high flux magnet 26/-, P. & P. 4/-, E.M.I. 13 1/2 x 8in 3 ohm with high flux ceramic magnet 42/-, (15 ohm 45/-), P. & P. 6/-, E.M.I. 13 x 8in, 3 or 15 ohm with two inbuilt tweeters and crossover network 4 gu. P. & P. 6/-.

**BRAND NEW.** 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiDux ceramic ferrobar magnet assembly £5.10.0. P. & P. 7/6. Guitar model: 25w £6.10.0. 35w £9.10.0.

**E.M.I. 5in HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3, 8 or 15 ohm 16/6 each. P. & P. 2/6.

**12in "RA" TWIN COME LOUDSPEAKER**  
10 watts peak handling. 3 or 15 ohm, 27/6. P. & P. 6/-.  
**35 OHM SPEAKERS.** 3in 14/-, P. & P. 2/6.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexilum earpiece. Wired and fitted with standard stereo 1/4 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE 59/-. P. & P. 3/-.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.C. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.P. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 x 1/2 in. Brand new—complete with instructions. Price 17/6. P. & P. 2/6.

**BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST.** Fitted mono t/o stylus and cartridge for LP/78. ONLY 20/-, P. & P. 1/6.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. W. x 3 1/2 x 6 in. Ready built and tested. PRICE 78/-. P. & P. 6/-. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE 97/6. P. & P. 7/6.

**DE LUXE QUALITY PORTABLE R/P CABINET MK II**  
Unit motor board size 14 1/2 x 12in., clearance 2in. below, 6 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 1/2 x 15in. PRICE 79/6. P. & P. 9/6.


### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 2-15 $\Omega$  speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 2/6 (Free with kit). All parts sold separately. ONLY 27.19.6. P. & P. 8/6. Also available ready built and tested complete with std. input sockets, £9.19.6. P. & P. 5/6.

**BRAND NEW TRANSISTOR TRANSFORMERS.** GET 15 (Matched Pair) 15/-; V15/10p, 10/-; OC71 5/-; OC76 6/-; AF117 3/6; 2G339 (NPN) 3/-.  
Set of Mullard 6 transistor OC44, 2-OC45, AC128D, matched pair AC128 25/-; ORP12 Cadmium Sulphide Cell 10/6. All post free.

**VERY POWERFUL COMPACT MOTOR**  
For 12V. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" x 1 1/2" dia. Free shaft 1/8" dia. x 1/2" L. Ideal for Model Makers, etc. ONLY 7/6 each P. & P. 1/-.  
3 or more post free (A few 6v. versions also available).

## DE LUXE STEREO AMPLIFIER

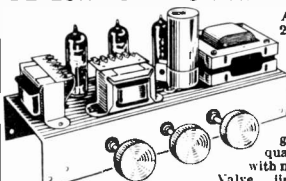

A.c. mains 200-240 volts. Using heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up:—2 x ECL86 Triode Pentodes.

1 x E280 as full wave rectifier. Two auto potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts total), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. W. x 4in. X. Overall height including valves 5in. Ready built and tested to a high standard. PRICE £8.18.6. P. & P. 8/-.

**4-SPEED RECORD PLAYER BARGAINS**  
Mains models. All brand new in manufacturer's pack. LATEST B.S.R. C109/A21 4-SPEED AUTOCHEANGER. With latest mono compatible cartridge £6.18.6. Carr. 6/6. With stereo cartridge £7.18.6. Carr. 6/6.

**SUITABLE PLINTE UNIT FOR ABOVE** with rigid plastic cover. £5.15.0 complete. P. & P. 8/6.  
**LATEST GARRARD MODELS.** All types available 1025, 3025, 3025, 3025, AT60, etc. S.A.E. for Latest Prices.  
**PLINTE UNITS cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc.** With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.15.0 complete. P. & P. 8/6.

**LATEST ACOS GFS1/18C Mono Compatible Cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. 30/-. P. & P. 1/6.

**ACOS HI-G Single sided mono cartridge** for LP & EP. ONLY 10/-, Post Free.

**SCORPION STEREO COMPATIBLE STEREO CARTRIDGE T/O stylus.** Diamond Stereo LP and Sapphire 78. ONLY £2.10.0. P. & P. 2/-.

Also available fitted with twin Diamond T/O stylus for Stereo LP. ONLY £3. P. & P. 2/-.

**LATEST MONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. 32/6. P. & P. 2/-.

**LATEST MONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono or stereo records on mono equipment. 30/-. P. & P. 2/-.

**HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT**  
Type TAP. Output in excess of 1 1/2 watts. All standard British components. Built on printed circuit panel size 6 x 3in.

Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GET114 or 81 Mullard AC 128D and matched pair of AC128 o/p). 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Complete easy to follow instructions and circuit diagram 2/6 (Free with kit). All parts sold separately. SPECIAL PRICE 49/6. P. & P. 3/-.

Also ready built and tested, 55/-, P. & P. 3/-.

**2-VALVE AUDIO AMPLIFIER B54 MK II**  
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. W. x 4 in. D. x 4 1/2 in. H. Incorporates ECC83, EL84, E280 valves. Heavy duty double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and lends extended for remote mounting controls. Complete with 20 valves, etc., wired and tested for only £4.15.0. P. & P. 6/-.

**H34 "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. 79/6. P. & P. 6/-.

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 5in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.

**OUR ROCK BOTTOM BARGAIN PRICE** 55/- P. & P. 6/-.

**HARVERSON SURPLUS CO. LTD.**  
170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985  
SEND STAMPED ADDRESSED ENVELOPE WITH ALL REQUIREMENTS

(Please write clearly)  
PLEASE NOTE: P. & P. CHARGES QUOTED ARE U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

As a double check, to make sure that there is no spurious oscillation from the unscreened tuned amplifier, and that the amplifier is really responding to the signal, alter the timebase frequency by adjustment of the TV line hold control, whereupon the whistle note will change and the amplifier output voltage should drop.

The tuned amplifier is now ready for final assembly and the flexible, coloured leads can be unsoldered from the potentiometers and trimmer capacitor. Avoid altering the TC1 setting.

Make up the chassis and mark all panels for later identification, not forgetting the screen partition, then dismantle it completely.

Take the box baseplate and mark and drill mounting holes for the three circuit panels. Ensure that there will be sufficient clearance between the decoder panel and the crystal insert X2.

Fix the tuned amplifier and decoder circuit panels to the baseplate, with lockwashers under the mounting nuts, but leave the transmitter panel unmounted for the time being.

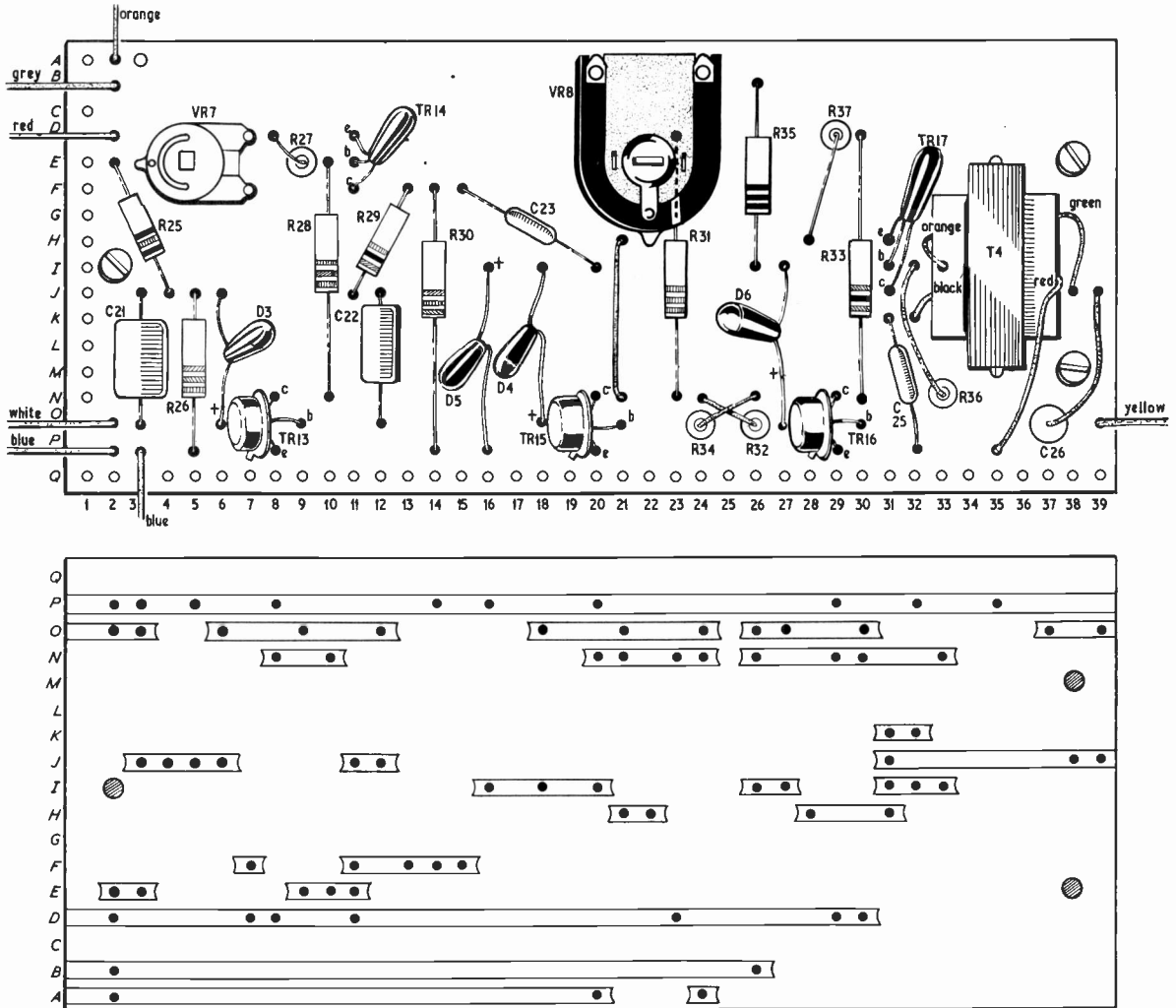


Fig. 12. Component layout and underboard wiring for decoder panel

### DECODER CIRCUIT PANEL

The decoder panel layout appears in Fig. 12, and construction of this unit is quite straightforward. Holes are drilled to accept mounting screws, and existing holes are enlarged to take VR8 and T4 tabs.

The finished decoder can only be tested after final assembly.

### FINAL ASSEMBLY

Details of the internal arrangement of the chassis housing, the circuit panels and other components are given in Fig. 13.

Drill the front panel according to Fig. 14; if desired, an identically drilled plastics laminate faceplate can be glued to the front panel to enhance the finished appearance. Mount VR3, VR5, and VR6, also the meter, on the front panel. Glue a small square of loudspeaker grille material to the inside of the crystal insert front panel aperture, then glue X2 to the grille.

### SCREEN PARTITION

Drilling details will not be given for the screen partition as the size of components used for T2, C5, C6, and C9 may vary.

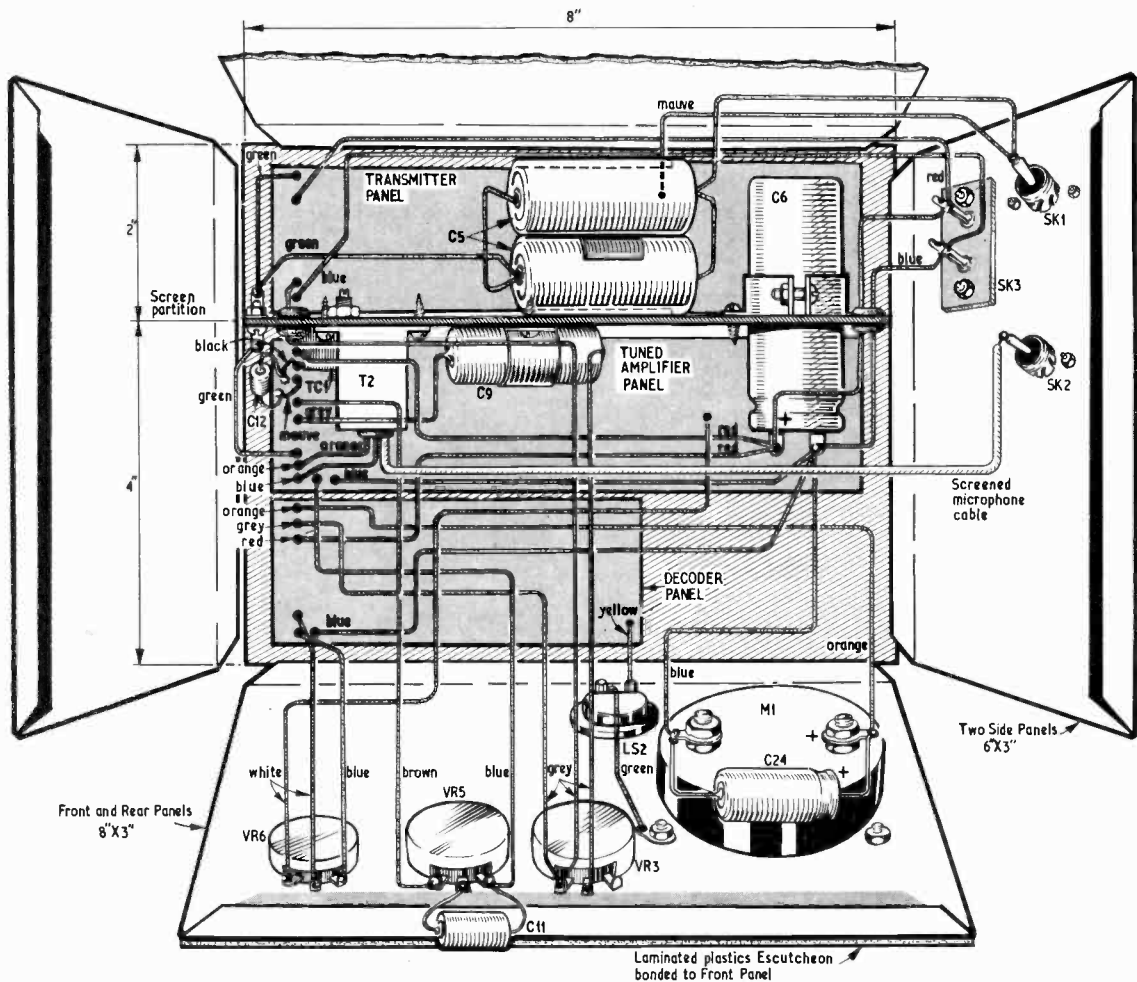


Fig. 13. Internal arrangement of plate mounted components and panel boards on chassis

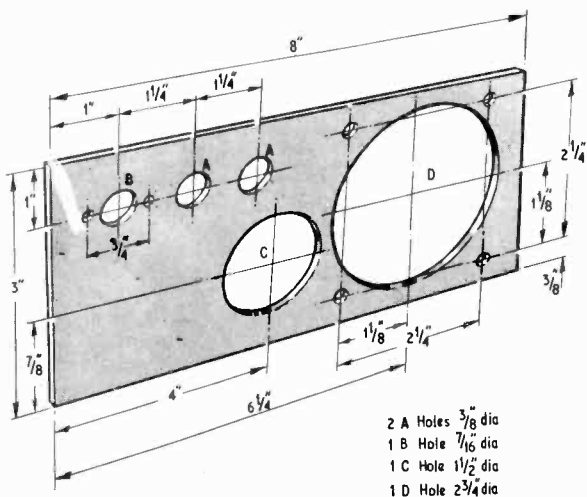


Fig. 14. Drilling details for front control panel

It is obviously a simple matter to find the best position for components on the partition when circuit panels and partition are in place on the baseplate; then the partition can be removed for drilling.

With the prototype, T2 was taken from inside a moving coil stick microphone (see Fig. 16), and was then enclosed in an old I.F. transformer can.

To obtain maximum transmitter output, C5 must be adjusted in value to suit individual loudspeaker resonances. A single  $2\mu\text{F}$  capacitor can be mounted in the C5 position on the partition, and can be padded later by wiring another capacitor in parallel, as depicted in Fig. 13.

Mount the front panel, partition, transmitter circuit panel, and right-hand box side with sockets on the baseplate, then proceed with all interconnecting wiring. The remaining box side panels and top plate are left until after the unit has been tested and calibrated.

# LST

## ELECTRONIC COMPONENTS LTD = BETTER QUALITY, SERVICE, PRICES & LARGEST STOCKS

AC107	7/7	BA111	6/-	BFY51	3 9	NKT127	10/6	NKT263	4/8	NKT12429	OC205	9/-	40316	9/3	2N709	8/6	2N3707	2/10	3N142	10/9	
AC126	5/-	BA114	3/-	BFY52	4/6	NKT128	10/6	NKT264	4/3	OC206	15/-	40317	15/-	40317	7/3	2N711	7/6	2N3708	1/10	3N143	13/3
AC127	4/-	BA113	1/6	BFY53	3/2	NKT129	8/6	NKT265	5/6	NKT13329	OC207	15/-	40319	10/9	2N711A	7/6	2N3709	7/6	3N152	17/3	
AC127Z	9/6	BC113	5/6	BFY54	13/6	NKT135	6/1	NKT270	6/1	OC208	19/6	40320	19/6	40320	7/3	2N743	4/6	2N3710	2/3	AA119	2/3
AC128	4/-	BC115	6/6	BSX19	3/3	NKT137	6/1	NKT271	2/10	NKT13429	ORP12	8/-	40323	6/6	2N744	6/-	2N3711	2/6	AA111	2/3	
AC128	4/-	BC118	7/6	BSX20	3/3	NKT141	10/6	NKT272	2/10	3/11	ORP60	8/-	40324	9/3	2N911	10/-	2N3819	7/7	AA130	1/7	
AC187	6/-	BC125	11/-	BSX21	7/6	NKT142	10/-	NKT273	3/8	NKT16229	ORP61	8/-	40326	7/3	2N914	3/11	2N3820	18/9	AAZ12	6/2	
AC188	6/-	BC126	11/-	BSX26	4/-	NKT143	9/6	NKT274	2/10	8/5	ORP63	9/-	40329	4/9	2N918	8/5	2N3826	6/-	AA113	3/2	
ACY17	5/9	BC143	15/-	BSY27	4/-	NKT144	8/-	NKT275	3/4	NKT20329	P346A	3/9	40344	5/3	2N929	5/3	2N3866	25/6	BA110	6/-	
ACY18	4/-	BC145	15/-	BSY29	5/-	NKT151	6/-	NKT276	3/6	8/8	RA5508AF	6/8	40347	7/6	2N930	6/-	2N4037	15/6	BA111	6/-	
ACY19	4/-	BC147	2/9	BSY95	3/2	NKT153	6/-	NKT279A	2/6	NKT20339	15/-	40348	10/3	2N1131	6/-	2N4058	3/4	BA112	18/-		
ACY20	3/10	BC149	3/3	BSY98A	2/11	NKT154	6/-	NKT281	5/2	6/4	S1M	19/-	40360	8/6	2N1132	3/7	2N4059	5/6	BA115	1/6	
ACY21	3/10	BC169C	3/9	BZ15	33/3	NKT162	6/-	NKT302	12/5	15/9	ST2	9/-	40362	11/6	2N1303	4/6	2N4061	4/6	BA130	3/6	
ACY22	3/6	BC171	2/-	C111	18/1	NKT163	6/-	NKT303	17/6	OC19	5/-	TI407	9/8	2N1304	4/11	2N4062	4/6	BA131	2/6		
ACY27	3/6	BC182L	2/3	C112	12/-	NKT164	6/8	NKT304	9/10	OC20	19/6	TIC45	8/-	2N1305	4/11	2N4284	3/6	BY100	4/6		
ACY28	7/8	BC183L	1/10	C426	8/3	NKT165	6/-	NKT351	10/6	OC22	8/1	TIS34	17/6	2N1306	6/-	2N4287	3/6	BY127	4/6		
AD140	12/6	BC184L	3/3	CRI-051C	8/-	NKT201	6/-	NKT352	17/6	OC23	10/1	TIS44	1/9	40432	27/6	2N1307	6/-	2N4288	3/6	BYX10	4/6
AD149	11/6	BC121L	3/4	CRI-401C10	8/-	NKT202	6/8	NKT361	20/6	OC24	10/1	TP31A	12/4	40462	11/3	2N1308	6/3	2N4289	3/6	BYX36/150	2/6
AD161	7/6	BCY12	12/6	GET16	12/6	NKT205	6/-	NKT401	14/6	OC26	6/6	TP32A	14/10	40600	11/6	2N1613	4/6	2N4291	3/6	BYX36/300	2/6
AD162	7/6	BCY30	5/6	GET102	6/-	NKT206	6/-	NKT402	15/6	OC28	12/6	V205	20/6	40601	11/6	2N1711	5/6	2N4292	3/6	BYX36/600	2/10
ADZ11	32/6	BCY32	10/6	GET103	5/6	NKT208	6/-	NKT403	14/9	OC29	15/6	V405A	9/3	40602	8/-	2N2147	16/3	2N4871	6/9	BYX36/600	3/9
ADZ12	39/6	BCY33	4/6	GET111	5/6	NKT210	4/2	NKT404	11/6	OC35	10/6	ZTX107	2/7	1B08T10	10/-	2N2148	12/6	25001	10/6	BYZ21	25/6
AF102	12/6	BCY38	4/6	GET113	4/6	NKT211	3/9	NKT405	11/6	OC36	12/6	ZTX108	2/2	IN34A	4/6	2N2160	12/6	25002	12/6	BYZ23	26/3
AF106	7/6	BCY38	6/-	MI481	2/7	NKT213	4/7	NKT42028	11/6	OC42	4/6	ZTX300	2/7	IN60	3/9	2N2369	3/14	25003	12/6	BYZ25	31/6
AF114	5/-	BCY39	9/6	MI490	22/6	NKT214	3/5	NKT451	9/11	OC43	4/6	ZTX301	2/8	IN82A	9/6	2N2613	7/6	25004	15/6	BYZ142	3/9
AF115	5/-	BCY70	3/10	MI491	29/6	NKT215	3/7	NKT452	9/6	OC44	3/6	ZTX302	3/8	IN87A	4/6	2N2614	4/6	25005	15/6	BYZ10	8/6
AF116	5/-	BCY71	7/8	MPF102	8/6	NKT216	7/6	NKT453	6/6	OC45	3/6	ZTX303	3/8	IN191	5/6	2N2646	10/6	25017	15/6	BYZ12	6/6
AF117	5/-	BCY72	3/2	MPF103	7/6	NKT217	9/6	NKT603F	4/8	OC70	2/6	ZTX304	5/5	IN914	3/6	2N2904	8/10	25018	17/6	BYZ13	5/6
AF118	8/10	BCZ11	7/6	MPF104	7/6	NKT218	6/-	NKT613F	5/2	OC71	2/6	ZTX310	1/5	IN3713	30/6	2N2904A	9/9	25019	19/6	CG66	4/6
AF121	6/6	BD121	22/6	MPF105	8/6	NKT219	4/6	NKT617	4/8	OC72	4/6	ZTX311	2/1	IN377	30/6	2N2905	12/11	25020	19/6	CG67	2/6
AF124	5/-	BD123	22/6	NKT11	7/6	NKT221	7/6	NKT675	6/8	OC74	8/6	ZTX312	2/1	IN4148	1/6	2N2905A15	11/11	25020	20/6	EA003	3/6
AF125	4/2	BD124	20/8	NKT12	5/5	NKT222	6/-	NKT676	5/6	OC75	4/6	ZTX313	2/2	IS44	1/6	2N2906	8/10	25104	12/6	EB383	3/6
AF126	3/6	BDY20	20/8	NKT32	6/6	NKT223	5/-	NKT677F	5/6	OC76	5/6	ZTX314	2/3	IS100	3/6	2N2906A	5/6	25104	8/6	EC401	5/6
AF127	3/6	BF163	9/6	NKT42	6/-	NKT224	3/7	3/10	OC77	3/6	ZTX320	6/1	IS107	6/6	2N2906A	5/6	25107	10/10	EC402	4/8	
AF139	15/-	BF167	5/-	NKT43	6/-	NKT225	3/6	NKT703	8/10	OC81	4/6	ZTX321	5/11	IS410	5/1	2N2923	4/6	25303	10/6	GEX45/1	4/6
AF178	9/6	BF173	6/-	NKT72	3/9	NKT226	11/6	NKT713	3/10	OC82	4/6	ZTX330	3/7	IS410R	5/1	2N2924	4/6	25304	12/6	GJ6M	4/6
AF179	11/6	BF178	10/6	NKT73	3/7	NKT227	9/6	NKT734	4/11	OC83	11/6	ZTX331	4/6	2C302	5/2	2N2925	3/6	25306	15/6	OA5	3/8
AF180	12/6	BF179	12/6	NKT101	6/-	NKT228	6/6	NKT734	4/11	OC82	5/6	ZTX341	3/7	2G339A	3/7	2N3055	5/6	25320	9/6	OA10	5/8
AF186V	8/-	BF180	7/6	NKT102	6/-	NKT229	3/11	NKT736	6/2	OC82D	3/6	ZTX342	4/2	2G371	3/6	2N3054	12/6	25321	6/6	OA47	1/8
AF186W	8/-	BF181	7/6	NKT103	6/-	NKT231	6/-	NKT773	3/7	OC83	4/6	ZTX500	3/2	2G371B	3/6	2N3055	15/6	25322	8/6	OA70	1/8
AF239	7/6	BF184	5/-	NKT104	6/-	NKT232	6/-	NKT774	6/1	OC84	5/6	ZTX501	3/3	2G374	5/6	2N3391A	6/-	25323	10/6	OA73	1/8
AFZ11	8/-	BF185	5/6	NKT105	6/-	NKT237	5/9	NKT0013	6/6	OC123	7/6	ZTX502	3/11	2G381	5/6	2N3393	5/6	25701	8/6	OA79	1/8
ASV26	4/5	BF194	3/6	NKT106	6/-	NKT238	4/6	NKT10419	3/10	OC139	5/6	ZTX503	3/4	IN174	16/6	2N3394	4/9	25702	11/4	OA81	1/8
ASV27	6/-	BF200	7/6	NKT108	6/-	NKT240	3/10	NKT10519	OC141	12/6	ZTX504	7/11	2N385A/1	15/6	2N3402	5/6	25703	12/6	OA85	1/8	
ASV28	4/5	BFX13	5/-	NKT109	6/-	NKT241	3/9	OC170	5/6	40250	10/9	2N404	4/6	2N3404	7/6	25712	34/6	OA91	1/8		
ASV29	7/6	BFX29	6/2	NKT121	10/6	NKT242	2/11	NKT10339	OC171	6/-	40309	6/6	2N696	3/6	2N3525	21/9	25720	25/6	OA95	1/8	
ASZ21	4/5	BFX44	8/-	NKT122	10/6	NKT243	12/11	4/7	OC200	7/6	40310	9/6	2N697	3/6	2N3702	2/6	25732	8/6	OA200	2/6	
AUY10	30/-	BFX84	5/2	NKT123	9/6	NKT244	3/11	NKT10439	OC201	9/6	40311	6/9	2N698	6/-	2N3703	2/5	25733	13/9	OA21	8/6	
B2M	12/6	BFX85	6/9	NKT124	6/5	NKT245	3/6	5/5	OC202	12/6	40312	9/6	2N706	2/4	2N3704	3/2	3N128	13/9	OA211	8/6	
B3M	15/-	BFX88	5/3	NKT125	4/6	NKT261	4/3	NKT12329	OC203	7/6	40314	7/3	2N706A	2/6	2N3705	2/8	3N140	15/3	SD19	7/6	
BA102	9/-	BFY50	4/6	NKT126	4/4	NKT262	4/3	OC204	8/-	40315	7/3	2N708	3/3	2N3706	2/3	3N141	14/6	TD716	12/6		

**BC107/8/9** 2/9  
NPN Planar transistors  
BC107 & 9  
25 + 2.5 100 - 2/2  
BC108 25 2/3 100 2-

**2N4871** 6/9  
Motorola unijunction  
25 + 5/9 100 + 4/9

**2N3055** 15/-  
115 watt silicon power transistor  
25 + 13/- 100 + 11/-

**2N3819** 7/-  
Texas FET  
25 + 6/- 100 + 5/3

**2N2926** 2/-  
NPN Planar transistors  
25 1/8 100 1/6

**OA91 SPECIAL OFFER**  
Mullard Diode  
25 9d. 100 3/7d.

**TOSHIBA**  
**20 WATT IC**  
**AMPLIFIER £4.9.6**  
NOW EX-STOCK  
DATA 1/-  
SPECIAL HEATSINK 9/-

**BF195** 2/6  
Mullard Lock-fit  
25 1/2- 100 1/9


**CHEAP LOGIC !!**  
(Fairchild-USA)  
1-11 12-24 25-99 100 +  
8/- 7/- 6/6 5/6  
uL914 Dual 2 Input Gate  
8/- 7/- 6/6 5/6  
uL 923 J-K Flip Flop  
10/6 10/0 9/6 9/-  
Data and circuits article, 5-page, at 2/6.  
Article '30 Suggested Circuits' for 'Micro-Logic', at 3/-.  
TOS to DL conversion spreaders adaptors at 1/6 each.

**SILICON RECTIFIERS**  
1 Amp Miniature Moulded Junction Rectifiers.  
P./V. 1-24 25 + 100 + 500 +  
IN4001 50 1/6 1/4 1/2 1/-  
IN4002 100 1/6 1/4 1/2 1/-  
IN4003 200 2/- 1/9 1/6 1/3  
IN4004 400 2/2 1/9 1/6 1/3  
IN4005 600 2/6 2/1 1/9 1/6  
IN4006 800 3/- 2/10 2/6 2/3  
IN4007 1000 4/- 3/3 2/9 2/6

In the event of any IN4000 series going temporarily out of stock we reserve the right to send higher voltage types at no extra charge. 1000 + and over prices on application.

**ZENER DIODES**  
400mW 10% GLASS CASE. TEXAS Mfr.  
IS2036 3.6 volt IS2082 8.2 volt  
IS2039 3.9 volt IS2100 10 volt  
IS2043 4.3 volt IS2110 11 volt  
IS2047 4.7 volt IS2120 12 volt  
IS2056 5.6 volt IS2160 16 volt  
IS2062 6.2 volt IS2180 18 volt  
IS2068 6.8 volt IS2270 27 volt  
IS2075 7.5 volt IS2300 30 volt  
PRICES: 1-24 3/6 25-99 2/9 100 + 2/3

**ULTRASONIC TRANSDUCERS**  
Operate at 40kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive.  
**FREE:** With each pair our complete transmitter and receiver circuit.  
PRICE £5.18.0 Pair (Sold only in pairs)



**INTEGRATED CIRCUITS**  
Some R.C.A. Linear Types

CA3005 23/6	CA3020 25/3	CA3028B 21/-	CA3043 27/6
CA3011 14/9	CA3021 31/3	CA3035 24/6	CA3044 24/-
CA3012 17/9	CA3022 26/-	CA3036 14/6	CA3045 24/6
CA3013 21/-	CA3023 25/3	CA3039 16/9	CA3046 15/2
CA3014 24/9	CA3026 20/-	CA3041 21/9	CA3048 40/9
CA3018 16/9	CA3028A 14/9	CA3042 21/9	CA3051 26/9

Application Notes for each individual 2/6d. per copy.

PA234	GE IC 1 Watt Amplifier	17/6
PA237	GE IC 2 Watt Amplifier	37/6
PA246	GE IC 5 Watt	

# TECHNICAL TRAINING

## in radio television and electronics

Whether you are a newcomer to radio and electronics, or are engaged in the industry and wish to prepare for a recognized examination, ICS can further your technical knowledge and provide the specialized training so essential to success. ICS have helped thousands of ambitious men to move up into higher paid jobs—they can help you too! Why not fill in the coupon below and find out how?

Many diploma and examination courses available, including expert coaching for:

- C. & G. Telecommunication Techns'. Certs.
  - C. & G. Electronic Servicing
  - R.T.E.B. Radio/T.V. Servicing Certificate
  - Radio Amateurs' Examination
  - Radio Operators' Certs.
  - General Certificate of Education, etc.
- Now available, Colour T.V. Servicing

Examination Students coached until successful

## NEW SELF-BUILD RADIO COURSES

Learn as you build. You can learn both the theory and practice of valve and transistor circuits, and servicing work while building your own 5-valve receiver, transistor portable, and high-grade test instruments, all under expert tuition. Transistor Portable available as separate course.

### POST THIS COUPON TODAY

for full details of ICS courses in Radio, T.V. and Electronics



**INTERNATIONAL  
CORRESPONDENCE SCHOOLS**

Dept. 151, Intertext House, Stewarts Rd., London, S.W.8

Please send me the ICS prospectus—free and without obligation.

(state Subject or Exam.).

NAME \_\_\_\_\_ AGE \_\_\_\_\_

(Block Capitals Please)

ADDRESS \_\_\_\_\_

2/71

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# RST VALVE MAIL ORDER CO.

BLACKWOOD HALL,  
WELLFIELD RD., S.W.16

SPECIAL EXPRESS MAIL ORDER SERVICE

All orders post free!

1N21	3/6	AC127	5/-	BF173	6/-	GJ4M	7/6	OC43	8/-
1N23	4/0	AC128	5/-	BF181	7/6	GJ5M	5/-	OC44	3/6
1N85	17/6	AC187	6/-	BF184	5/-	GJ7M	7/6	OC44M	3/6
1N253	10/0	AC188	6/-	BF185	5/-	HG1005	10/-	OC45	3/6
1N256	10/0	ACY17	6/-	BF194	3/6	K8100A	4/-	OC45M	3/6
1N645	5/0	ACY18	5/-	BF195	3/-	MAT100	5/-	OC46	5/6
1N725A	4/-	ACY19	5/-	BF196	5/6	MAT101	6/-	OC57	12/-
1N914	1/6	ACY20	4/6	BF197	5/6	MAT120	5/-	OC58	12/-
1N4007	4/6	ACY21	4/6	BF861	5/6	MAT121	6/-	OC39	13/-
18021	4/-	ACY22	3/6	BF898	5/6	MJE520	17/6	OC66	10/-
18113	3/-	ACY27	5/-	BFX12	5/6	MJE2955	35/-	OC70	2/6
18130	2/6	ACY28	3/6	BFX13	4/6	MJE3055	18/6	OC71	3/6
18131	2/6	ACY39	11/-	BFX29	6/-	NKT128	6/-	OC72	5/6
18202	4/6	ACY40	3/-	BFX30	6/6	NKT129	6/-	OC73	6/-
2G240	39/6	ACY41	5/-	BFX35	19/6	NKT211	5/-	OC74	5/6
2G301	3/6	ACY44	7/6	BFX63	10/-	NKT213	5/-	OC75	5/6
2G302	4/6	AD140	10/-	BFX84	6/-	NKT214	3/-	OC76	5/6
2G306	6/-	AD149	10/-	BFX85	8/-	NKT216	7/6	OC77	8/-
2G371	4/6	AD161	7/6	BFY86	6/6	NKT217	8/-	OC78	4/6
2Q381	5/-	AD182	7/6	BFX87	6/6	NKT218	22/6	OC78D	2/6
2G414	6/-	AF106	6/-	BFX88	5/-	NKT219	6/6	OC79	4/6
2G417	4/6	AF114	6/6	BFY10	20/-	NKT222	4/-	OC81	5/-
2N214	8/6	AF115	6/6	BFY11	25/-	NKT224	4/6	OC81D	4/6
2N247	5/0	AF116	6/6	BFY17	5/-	NKT251	4/9	OC81M	4/6
2N250	10/-	AF117	5/-	BFY18	5/-	NKT271	5/-	OC81DM	3/6
2N2404	4/6	AF118	12/6	BFY19	5/-	NKT272	5/-	OC81Z	11/-
2N697	3/6	AF119	4/-	BFY20	9/-	NKT273	17/6	OC82	5/6
2N698	8/6	AF124	5/-	BFY44	20/-	NKT274	4/-	OC82D	3/6
2N706	2/-	AF125	4/-	BFY50	4/6	NKT275	5/-	OC83	5/6
2N706A	2/6	AF126	3/6	BFY51	4/-	NKT277	4/-	OC84	5/6
2N708	3/-	AF127	3/6	BFY52	4/6	NKT278	5/-	OC114	7/6
2N709	12/6	AF139	6/6	BFY53	3/6	NKT301	6/-	OC122	10/6
2N711	7/6	AF178	9/6	BFY64	8/6	NKT302	7/6	OC123	10/6
2N987	10/6	AF179	9/6	BFY90	13/6	NKT303	15/-	OC139	5/6
2N1090	6/-	AF180	10/6	BSX27	10/-	NKT404	12/6	OC149	7/6
2N1091	6/6	AF181	10/6	BSX60	14/6	NKT678	6/-	OC141	12/6
2N1131	6/-	AF186	8/-	BSX76	3/-	NKT713	5/6	OC169	4/6
2N1132	6/-	AFY19	22/6	BSY26	3/6	NKT773	5/6	OC170	5/6
2N1302	4/-	AFZ11	12/6	BSY27	4/-	NKT777	7/6	OC171	6/-
2N1303	4/6	AFZ12	15/-	BSY51	10/-	078B	7/6	OC200	7/6
2N1304	5/-	ASV26	5/6	BSY95A	3/-	0A6	2/6	OC201	9/6
2N1305	5/-	ASV27	6/6	BSY95	3/-	0A6	2/6	OC202	12/6
2N1306	5/6	ASV28	5/6	BT102	7/6	0A7	2/6	OC203	7/6
2N1307	5/6	ASV29	5/6	500R	15/-	0A70	2/6	OC204	8/6
2N1308	6/6	ASV36	5/6	BTY42	18/6	0A71	2/6	OC205	12/6
2N1309	5/6	ASV50	3/6	BTY79	10/-	0A73	2/6	OC206	15/6
2N1420	18/6	ASV51	8/-	100R	15/-	0A74	2/6	OC207	15/6
2N1507	5/6	ASV53	4/-	BTY79	10/-	0A79	2/6	OC480	4/6
2N1526	7/6	ASV55	4/-	400R	35/-	0A81	2/6	OC470	6/6
2N1909	45/-	ASV62	5/-	BY100	3/6	0A85	2/6	OC711	19/6
2N2147	15/-	ASV96	6/6	BY126	3/-	0A86	3/6	ORP12	10/6
2N2148	12/-	ASZ21	8/6	BY127	4/-	0A90	2/6	ORP60	8/6
2N2160	12/6	ASZ22	8/6	BY182	15/-	0A91	1/6	ORP61	8/6
2N2218	6/-	ASZ23	15/-	BY213	5/-	0A95	1/6	S19T	6/6
2N2219	6/6	AU101	10/6	BYZ10	8/6	0A200	1/6	SAC40	5/6
2N2287	20/6	BC107	2/6	BYZ11	7/-	0A202	2/6	SFT308	7/6
2N2297	6/-	BC108	2/6	BYZ12	6/-	0A210	3/6	ST722	7/6
2N2369A	4/-	BC109	2/6	BYZ13	5/-	0A211	7/6	0A211	12/6
2N2613	5/6	BC113	5/6	BYZ15	20/-	OAZ200	11/-	SX68	4/6
2N2646	19/6	BC115	6/6	BYZ16	12/6	OAZ201	10/6	SX631	4/6
2N2712	5/-	BC116	8/6	BYZ88C3V3	3/6	OAZ202	8/6	SX635	6/6
2N2784	10/-	BC118A	9/6	C11	13/-	OAZ203	8/6	SX640	5/6
2N2846	45/-	BC119	7/6	CR81/05	5/6	OAZ204	8/6	SX641	5/6
2N2848	8/6	BC121	4/-	CR81/40	9/6	OAZ205	8/6	SX642	7/6
2N2904	6/6	BC122	4/-	CS4B	30/-	OAZ206	8/6	SX644	9/6
2N2904A	6/6	BC125	13/6	CS1B	62/6	OAZ207	8/6	SX645	15/6
2N2906	6/-	BC126	13/-	DD000	3/-	OAZ209	6/6	V1530P	10/6
2N2907	7/6	BC140	11/6	DD003	3/-	OAZ210	6/6	V60/201P	7/6
2N2922	4/6	BC147	3/6	DD006	3/6	OAZ211	6/6	V60/201P	7/6
2N2923	3/6	BC148	2/6	DD007	8/6	OAZ222	8/6	XA101	2/6
2N2926	2/6	BC149	4/-	DD008	7/6	OAZ223	8/6	XA102	3/6
2N3054	10/-	BC157	4/-	G3	6/6	OAZ224	7/6	XA151	3/6
2N3055	15/-	BC158	4/-	G4	1/-	OAZ241	4/6	XA152	3/6
2N3702	2/6	BC160	12/6	G5	6/6	OAZ242	4/6	XA161	5/6
2N3703	3/6	BC169	2/6	GDB	5/6	OAZ244	4/6	XA162	5/6
2N3706	4/6	BCY31	6/6	GD12	1/-	OAZ246	4/6	XB103	8/6
2N3707	3/6	BCY32	10/-	GET102	6/6	OC220	7/6	XB102	2/6
2N3709	2/6	BCY33	4/-	GET103	4/6	OC16	8/6	XB103	5/6
2N3710	2/6	BCY34	5/-	GET113	4/-	OC16T	7/6	XB113	2/6
2N3711	2/6	BCY38	6/6	GET114	3/-	OC19	7/6	XB121	8/6
2N3819	7/-	BCY39	8/6	GET115	9/-	OC20	19/6	ZR24	12/6
2N3820	17/6	BCY40	9/6	GET116	10/-	OC22	9/6	Z8170	2/6
2N3823	15/-	BCY42	3/-	GET120	5/6	OC23	10/-	Z8271	3/6
2N5027	10/6	BCY47	4/6	GET872	8/6	OC24	10/6	Z8281	5/6
2N5088	6/6	BCY71	6/6	GET875	5/6	OC25	7/6	ZT43	5/6
28005	15/-	BCZ10	6/6	GET880	7/6	OC26	5/6	ZTX107	3/6
28301	8/6	BCZ11	7/6	GET881	5/6	OC28	12/6	ZTX108	3/6
28304	12/6	BD121	13/6	GET882	5/6	OC29	12/6	ZTX300	2/6
28301	7/6	BD123	16/6	GET885	4/6	OC30	8/6	ZTX304	5/6
28703	12/6	BD124	12/6	GEX44	1/6	OC35	10/6	ZTX500	3/6
AA129	4/-	BDY11	32/6	GEX45/1	1/6	OC36	12/6	ZTX503	4/6
AAZ13	2/6	BF115	5/-	GEX94/1	3/-	OC41	5/6	ZTX531	6/6
AC107	7/6	BF117	10/-	GJ3M	3/-	OC42	6/6		
AC126	5/-	BF167	5/-						

### SEMI-CONDUCTOR SET FOR P. E. GEMINI AMPLIFIER £12-19-0

SEND S.A.E. FOR LIST OF 3,000 TYPES VALVES, TUBES AND TRANSISTORS

Open daily to callers: Mon-Sat 9 a.m.-5.30 p.m.

Closed Sat. 1.30 p.m. - 2.30 p.m.

Terms C.W.O. only | Tel. 01-769 0199/1649

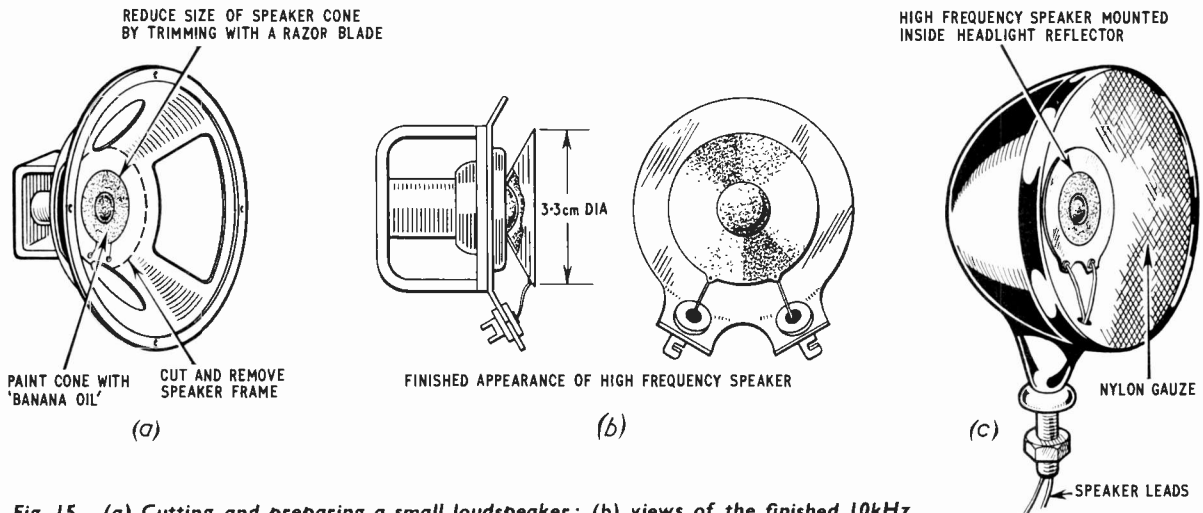


Fig. 15. (a) Cutting and preparing a small loudspeaker; (b) views of the finished 10kHz radiator; (c) the radiator mounted in a car headlight

### TRANSMITTER LOUDSPEAKER

If there is a choice of small 3 ohm loudspeakers, select one that gives the loudest output when coupled to the sonic transmitter.

With a sharp razor blade or modelling knife, cut away the outer section of the loudspeaker cone (see Fig. 15a) taking care not to sever the pigtail leads leading to the voice coil. The remaining part of the cone, Fig. 15b, should be close to 3.3cm diameter—the wavelength of 10kHz sound—and is stiffened by applying two or three coats of modelmaker's banana oil.

The loudspeaker metal frame should also be cut away with tin snips or a hacksaw, but make sure that iron filings are not collected by the loudspeaker magnet.

A suitable mount for the high frequency loudspeaker is a car headlamp as shown in Fig. 15c. The headlamp reflector will not make a significant contribution to the loudspeaker directional characteristic but side and back radiation will be reduced if the headlamp interior is filled with acoustic wadding or felt.

Protection against small flying stones is afforded by nylon gauze across the front of the reflector, attached to the headlamp rim.

### RECEIVER MICROPHONE

Fig. 16 shows how a conventional dynamic microphone can be converted for use with the Obstacle Locator. After completely dismantling the microphone, the rear of the "stick" is cut away. The microphone transformer is removed for use as T2.

Holes to take three screw eyes are drilled 120 degrees apart around the microphone casing, and a hole is also drilled to take the microphone cable.

Epoxy resin glue can be employed to retain the screw eyes, as well as the aluminium disc which is inserted to block off the opening in the end of the casing.

When re-assembling the microphone after soldering the screened cable to the insert terminals, fill the inside of the casing with plastic foam material.

### HEADLAMP MOUNTING

The microphone is suspended at the focus of a parabolic headlamp reflector by rubber bands; facing inwards towards the back of the reflector as shown in Fig. 17. Other forms of mounting were tried, but the rubber band method gave better noise rejection.

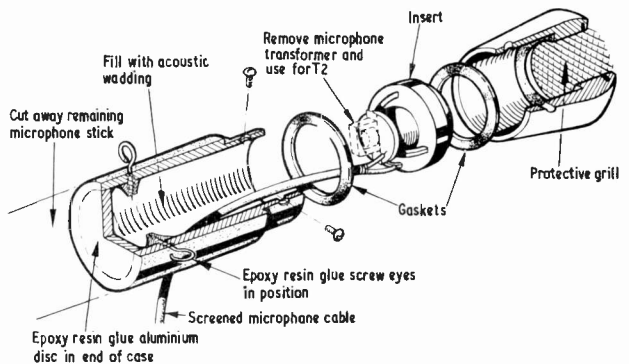


Fig. 16. Converting a dynamic stick microphone for use as a receiver

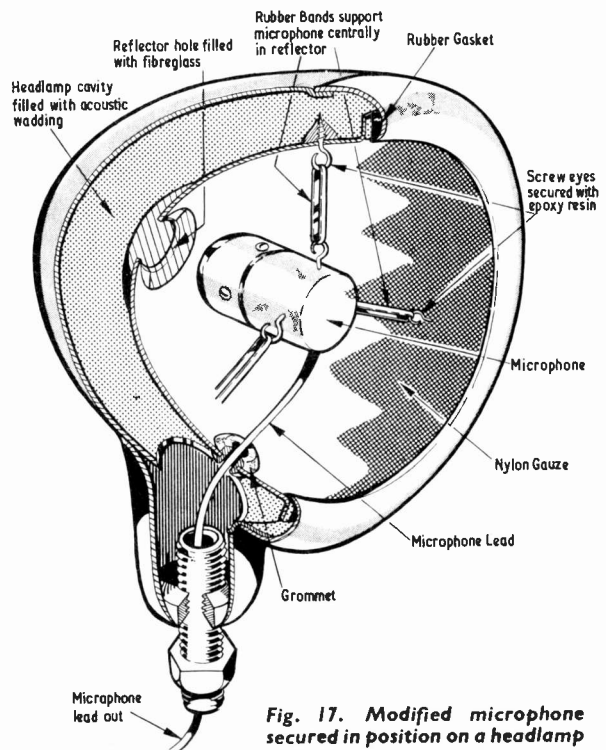


Fig. 17. Modified microphone secured in position on a headlamp

Before preparing the headlamp, measure the distance from the bulb filament to the back of the reflector, to find the focal point. Fill the hole in the back of the reflector with a fibreglass compound, and sandpaper when dry to conform with the reflector contour.

Position the microphone diaphragm at the focal point of the reflector and mark the location of holes for the reflector screw eyes, opposite those on the microphone casing, and in the same vertical plane.

Fix the screw eyes to the reflector and drill a hole to take the microphone cable, then attach the microphone to the reflector with rubber bands.

As with the loudspeaker, nylon gauze covers the opening in the headlamp to protect the microphone. Finally, fill the inside of the headlamp with acoustic wadding.

It is difficult to fully waterproof both headlamps without reducing efficiency, therefore, when the Obstacle Locator is not being used the headlamps should be covered with thick polythene bags.

### SETTING UP

As a preliminary to setting up the Obstacle Locator, adjust VR1, VR2, and VR5 to a mid-track setting; VR3 to minimum resistance; VR4 and VR7 to maximum resistance; and rotate VR6 fully anti-clockwise.

Leaving loudspeaker and microphone plugs disconnected from SK1 and SK2, couple the power supply to SK3, making sure that the aluminium chassis is earthed either to the positive or negative supply rail, and switch on.

Set VR8 to give a full scale meter reading.

In the absence of a signal (VR6 fully anti-clockwise) full scale deflection of the meter needle indicates battery condition.

With VR5 and VR6 rotated fully clockwise, an almost continuous note should be heard from the crystal insert X2 and the meter reading will drop to almost zero. Back off VR5 to just beyond the point where the note ceases and the meter again reads full scale.

### CALIBRATION

Find an open area of ground with a fairly flat surface, uncluttered by large stones and other objects. Position loudspeaker and microphone headlamps side by side, about 18in off the ground, and facing some large reflective object at exactly 20 feet distance.

Rotate VR6 fully anticlockwise, but do not alter any other settings. Connect up the loudspeaker cable to SK1, microphone cable to SK2, and power supply to SK3, and switch on.

Advance VR6 slowly until a regular bleep note is heard from X2, and the meter reading drops to somewhere near 20.

Calibrate by means of VR1 for an exact meter reading of 20.

No difficulty should be experienced in obtaining a response at 20 feet, even with the transmitter off tune. If an echo is not received, try connecting a pair of high impedance headphones across the track of VR6, to the tuned amplifier output. A regular click from the transmitter output will be clearly audible.

Now adjust tuning control VR2 and listen for additional echo clicks at a particular setting of VR2. If necessary, also trim TC1, VR7, and VR5 for a response.

### SENSITIVITY ADJUSTMENT

The purpose of the next test is to establish optimum sensitivity. An oscilloscope can be coupled to the tuned amplifier output to display echo waveforms and

noise levels, but failing this, the following procedure should be adopted.

Set up loudspeaker and microphone 50 feet away from a large wall, in an area free from other echo producing objects.

Switch on, then, with VR6 set fully clockwise, rotate VR7 until a response is obtained. The meter should now read 50 and the mark-space ratio of the bleep from X2 will be equal.

Back off VR6 to the point where the signal ceases. Now adjust VR2, VR7, and VR5 for maximum response at the lowest possible setting of VR6. Also try placing various capacitors in parallel with C5 to bring up the transmitter sonic output.

It will be found that, when the loudspeaker and microphone are close to the ground, back-scatter echoes will be received, if the surface is at all rough, when VR3 is turned anti-clockwise. The range of back-scatter control presented by VR3 is fixed later by suitable adjustment of VR4.

Finally, see if a strong signal can be received from a large wall or a building at 95 feet distance; in this case the note from X2 will be of such short duration that it sounds like a click.

### USING THE LOCATOR


In uncluttered conditions, where the equipment is working over a smooth area of water or tarmac, and the best possible response to small objects at near distances is desired, set VR4 to mid-track and advance VR3 until a suitable response is achieved.

Where there are numerous small objects in front of the loudspeaker transducer, VR3 should be left at minimum resistance.

The only control likely to need adjustment under operating conditions is VR6. In difficult, built-up areas for example, VR6 will be set low, to avoid spurious echoes, but in more open situations a high setting of VR6 will give long range working.

When visibility is constantly changing, the equipment can be left ready on stand-by with VR6 rotated fully anticlockwise.

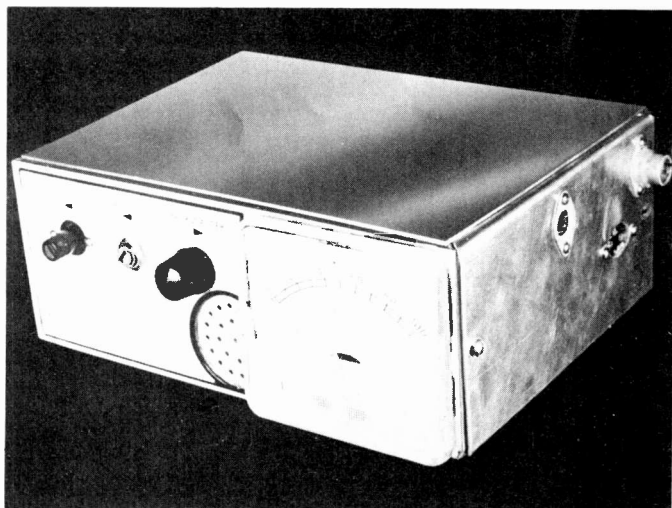If the Sonic Obstacle Locator is to be used at sea, adequate precautions must be taken to thoroughly moisture proof all aluminium parts against corrosion, including the interior of the microphone unit; this can be done with a varnish. ★





# TRANSISTOR RADIOS TO BUILD YOURSELF


Backed by after sales service

## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous make 7 x 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **£6.19.6** P. & P. 7/6

Overseas P. & P. 17/-

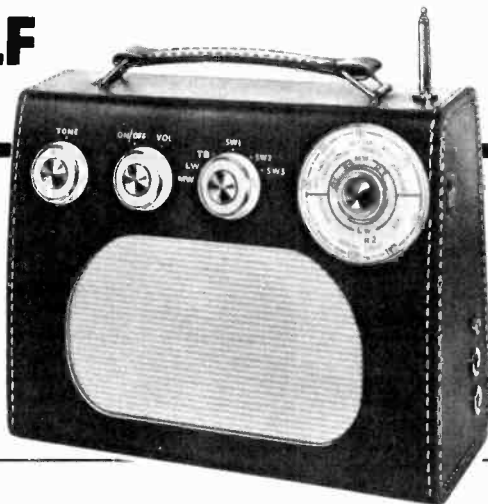

## roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak Short Wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous make 7 x 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control, wave change switches and tuning control. Attractive case with carrying handle. Size 9 x 7 x 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 3/- (FREE with parts).

Total building costs **£5.19.6** P. & P. 7/6  
Overseas P. & P. 17/-

Personal Earpiece with switched socket for private listening, 5/- extra.




## NEW! transeight

### SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 5/- (FREE with parts).

Total building costs **89/6** P. & P. 5/6

Overseas P. & P. 13/-

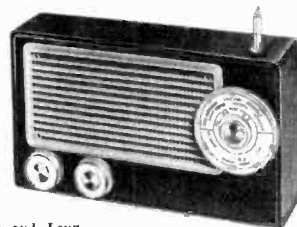

Earpiece with switched socket for private listening 5/- extra.

## pocket five

### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 3 1/2 in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages—5 transistors and 2 diodes, superregenerative rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).



Total building costs **44/6** P. & P. 3/6  
Overseas P. & P. 10/-

## transona five

### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2 in. 7 stages—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 1/6 (FREE with parts).




Total building costs **47/6** P. & P. 3/9  
Overseas P. & P. 10/-

## IMPROVED MODEL! roamer six
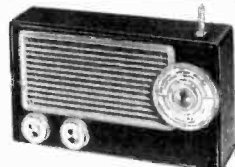
### SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 x 5 1/2 x 2 1/2 in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 2/- (FREE with parts).



Total building costs **79/6** P. & P. 4/6  
Overseas P. & P. 13/-

## RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

ROAMER EIGHT	<input type="checkbox"/>	ROAMER SEVEN	<input type="checkbox"/>
TRANSEIGHT	<input type="checkbox"/>	POCKET FIVE	<input type="checkbox"/>
TRANSONA FIVE	<input type="checkbox"/>	ROAMER SIX	<input type="checkbox"/>

Parts price list and plans for.....

Name.....

Address.....

PE 26

\* Callers side entrance Stylo Shoe Shop

\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

# G. F. MILWARD

# Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS ELECTRONIC COMPONENTS

Wholesale/Retail : 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

WIRE-ENDED TYPES				NOTE: IT IS ESSENTIAL THAT REFERENCE NUMBER IS QUOTED WHEN ORDERING THESE CAPACITORS						
REF. No.		REF. No.		REF. No.		REF. No.				
G1/13	40/50V	1/-	H1/11 8/6V	6d	G4/13 400/50V	2/-	H7/2 20/15V	1/-	H7/10 60/15V	1/6
G2/5	10/6V	9d	H2/1 32/150V	1/-	G4/14 500/4V	9d	H7/2A 20/6.4V	9d	H7/11 64/25V	1/6
G2/6	8/12V (REV)	9d	H2/2 64/2.5V	9d	H5/3A 500/25V	2/-	H7/3 25/12V	9d	H7/13 75/15V	1/6
G3/7	100/25V	2/-	H2/6A 24/275V	1/-	H5/6A 40/3V	6d	H7/4 25/25V	1/6	H7/14 100/1V	1/-
G3/14	100/180V	2/-	H2/8 21/150V	1/-	H5/7 30/6V	6d	H7/4A 25/20V	1/6	H8/2 2/50V	1/-
G5/9	8/8/450V	1/-	H2/9A 21/150V	1/-	H5/11 400/6.4V	9d	H7/5 40/15V	1/6	H8/3 3/50V	1/-
G6/13A	40/450V	2/-	H2/10A 16/32/350V	2/-	H5/12 320/10V	1/-	H7/6 50/3V	6d	H8/6 8/50V	1/-
H1/1	1/6V	6d	H2/11A 32/275V	1/6	H5/14 5/6V	6d	H7/6A 26/50V	1/6	H8/7 12/52V	1/6
H1/3	4/4V	6d	H3/7A 500/12V	1/6	H6/1 100/50V	1/6	H7/7 50/12V	1/6	H8/7A 15/15V	1/6
H1/4	6/6V	6d	H3/8 750/12V	1/6	H6/6 200/3V	6d	H7/7A 50/10V	1/6	H8/10 2/275V	1/-
H1/7	20/6V	6d	H3/10A 30/10V	6d	H6/7 200/16V	1/6	H7/8 50/15V	1/6	H8/11A 250/12V	2/6
H1/9	50/6V	6d	H3/12 16/50 (REV)	2/-	H6/13 500/5V	9d	H7/9 60/12V	1/6	H8/13 100/25V	1/6
			H4/1 20/4/275V	1/6	H7/1 10/12V	9d				

CAN TYPES										
REF. No.		REF. No.		REF. No.		REF. No.				
G2/1	6,000/30V	7/6	G4/1 300/700/320V	7/6	G5/4A 500/100V	3/-	G6/9 60/200/300V	5/-	H3/4 1,000/50V	6/-
G2/5	125/200V (REV)	5/-	G4/5A 60/350V	1/-	G5/5 400/275V	3/-	G6/11A 400/300V	3/-	H3/4A 3,000/25V	3/-
G2/10	50/50V	1/-	G4/6 60/200/275V	2/6	G5/7 100/400/300V	7/6	G6/12A 1,000/12V	3/-	H3/6 2,500/9V	2/6
G2/11	100/350V	2/-	G4/7 40/40/275V	1/6	G5/7A 45,000/12V	15/-	H5/4 325/25V	1/6	H3/6A 5,000/18V	4/-
G3/2	200/200/350V	6/-	G4/7A 40/40/450V	2/6	G6/1 12,000/15V	15/-	G6/14 400/275V	3/-	H3/9 100/275V	2/-
G3/2A	200/200/100/350V	7/6	G4/11 2,000/25V	3/-	G6/2 2,500/40/60V	7/6	H1/5 2,000/18V	3/-	H3/13 16/16/375V	2/-
G3/4	650/300V	7/6	G4/12 150/30V	1/-	G6/2A 2,500/50V	7/6	H1/6 125/200V	2/-	H4/3 500/12V	1/6
G3/9	100/200/250V	6/-	G4/13 100/200/16/275V	6/-	G6/3 2,000/50V	7/6	H1/12 200/275V	2/-	H4/5 32/32/350V	2/-
G3/10	40/20/10/10/350V	3/-	G5/1 8,000/70V	10/-	G6/3A 2,000/15V	3/-	H1/15 100/200/60/275V	5/-	H4/9 500/6V	1/6
G3/10A	200/350V	2/-	G5/2 300/300/350V	4/-	G6/5 1,000/1,500/25V	7/6	H2/6 50/275V	1/6	H4/11 75/400/16/275V	7/6
G3/13A	2,000/30V	5/-	G5/2A 30,000/40V	15/-	G6/5A 1,600/80V	7/6	H2/9 16/16/450V	1/6	H6/10 250/25V	7/6
			G5/3 35,000/15V	15/-	G6/6 1,000/60V	6/-	H2/10 1,000/100V	7/6	H8/13 6,000/6V	4/-
			G5/4 39,000/10V	10/-	G6/8 200/250V	3/-	H3/2 2,500/100V	7/6		

TAG ENDS										
REF. No.		REF. No.		REF. No.		REF. No.				
G1/4	4/150V	1/-	G4/4 40/300V	1/6	G4/9 8/8/350V	2/-	G6/7 100/275V	2/-	H5/2 250/25V	1/6
G1/5	8/275V	1/-	G2/13 100/50V	1/-	G4/10 350/25V	2/-	G6/12 1,000/12V	2/-	H4/7A 32/32/275V	2/6
G1/5A	32/350V	1/6	G4/3A 200/25V	1/6	G6/1A 3,000/15V	3/-	H1/9A 50/150V	1/-	H4/12 500/50V	2/-
G1/7	16/16/275V	2/-	G4/5 16/300V	1/-	G6/4 1,000/50V	6/-	H3/5 250/150V	2/-	H5/6 250/50V	2/-
G1/12	40/450V	2/-								

PRINTED CIRCUIT, CAN TYPE										
REF. No.		REF. No.		REF. No.		REF. No.				
G1/6	16/32/450V	2/-	G3/12 100/200/16/16/300V	5/-	G5/14 8/8/275V	1/6	H3/9 100/275V	2/-	H5/2 64/32/8/275V	2/-
G1/8A	16/350V	1/-	G3/13 64/275V	2/-	G6/4A 1,000/25V	2/6	H3/10 100/250V	2/-	H5/3 500/25 (REV)	2/6
G1/10	32/275V	1/6	G4/3 250/150V	2/-	G6/1 40/350V	1/6	H3/13A 16/16/275V	1/6	H5/3 32/32/275V	1/6
G1/14	16/275V	1/-	G4/4 50/50/200V	2/-	G6/12 250/25V	2/-	H4/3A 500/50V	1/6	H5/9 100/100/150V	2/-
G2/10	100/100/350V	3/-	G4/8 40/40/450V	2/-	H1/10A 10/10/350V	1/6	H4/4 400/6 (REV)	2/-	H5/13 32/32/8/300V	2/-
G2/12	100/150V	2/-	G5/6 60/100/275V	2/6	H1/12 200/275V	2/-	H4/6 64/275V	2/-	H5/9 50/50/50/350V	3/-
G2/14	20/10/10/450V	2/-	G5/8A 100/65/250V	2/-	H1/13 250/150V	2/-	H4/7 32/32/350V	2/-	H6/4 150/150V	1/6
G3/1	60/100/350V	3/-	G5/10 100/100/50/350V	3/-	H2/4 100/300/300V	2/6	H4/8 8/8/8/275V	2/6	H6/14 1,000/20V	2/-
G3/6	100/250V	2/-	G5/11 100/200/25V	2/-	H2/5 100/100/100/275V	2/6	H4/10 10/10/425V	2/6	H8/11 250/25V	2/-
G3/6A	50/50/350V	2/-	G5/12 100/40/10/350/20/50V	2/6	H2/12 50/275V	1/6	H4/13 400/250V	3/-	H8/12 3,000/6V	2/-
G3/8A	100/25V, 100/12V	2/6	G5/13 40/100/350V	2/6	H2/11 32/32/250V	1/6	H5/1 150/200V	2/-	H8/13A 100/25/200/25V	1/6
G3/11	100/350V	2/6	G5/13A 40/40/40/350V	2/6	H2/12 50/50/150V	1/6			H8/11 150/200V	2/-

PRINTED CIRCUIT TYPE, WIRE LEADS										
REF. No.		REF. No.		REF. No.		REF. No.				
H1/9	16/275V	1/6	H3/15 350/12V	1/6	H6/10 300/9V	1/-	H7/12 65/15V	1/6	H8/4 5/15V	1/-
H2/7	10/25V	1/6	H5/1 150/30V	1/6	H6/11 300/15V	1/6	H7/15 100/16V	1/6	H8/8 20/9V	1/-
H2/12A	350/12V	1/6	H5/14A 1,100/10V	2/1	H6/14A 900/15V	2/1	H8/1 1/350V	1/-	H8/9 40/15V	1/-
H2/15	12.5/40V	1/6	H6/5 150/25V	1/6						

**SPECIAL 10/- PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE!!!!**

RESISTORS, 1/4 watt assorted	100	10/-	P.N.P. Untested but mainly O.K.	50	10/-
Wire-wound 1 to 3 watt	20	10/-	N.P.N. Untested but mainly O.K.	50	10/-
5 to 7 watt	15	10/-	OC P 71 equivalent	5	10/-
10 watts	10	10/-	Light-sensitive Diodes	10	10/-
Multi-tapped	12	10/-	(These produce up to 1ma from light)		
PAPER CONDENSERS	50	10/-	OC 44 Mullard 1st grade	4	10/-
TV types	100	10/-	OC45 Mullard Boxed	4	10/-
Miniature	100	10/-	2G37 Output, Marked	4	10/-
ELECTROLYTIC CONDENSERS	10	10/-	2G371 Driver, Marked	4	10/-
Suitable for Mains	20	10/-	ASY 22, Marked	5	10/-
Radio/TV	15	10/-	BY 127 Rectifiers	4	10/-
Transistor types	100	10/-	IN4007 Rectifiers	4	10/-
Mixed (both types)	15	10/-	DIODES (0A 81 & 0A 91)	40	10/-
POLYSTYRENE CONDENSERS	100	10/-	WIRE		
MULLARD POLYESTER COND.	50	10/-	Solid Core, Insulated 100yds.	10/-	
SILVER MICA	100	10/-	Stranded ditto	50yds.	10/-
WIRE-WOUND 3-Watt	15	10/-	SOLAR CELLS		
SLIDERS	5	10/-	Large Selenium	2	10/-
VOLUME CONTROLS	5	10/-	Small	3	10/-
Assorted	100	10/-	(6 cells will power a Micromatic radio)		
NUTS AND BOLTS, Mixed length/type	100	10/-	CO-AXIAL CABLE	15yds.	10/-
8 B.A.	100	10/-	Semi Air-spaced	15yds.	10/-
6 B.A.	100	10/-	CRYSTAL TAPE RECORDER	1	10/-
4 B.A.	100	10/-	CRYSTAL EARPIECES	2	10/-
2 B.A.	100	10/-	3.5mm Plug	2	10/-
METAL SPEAKER GRILLS	6	10/-	TRANSISTORISED Signal	1	10/-
7in. x 3in.	6	10/-	Injector	1	10/-
EARPIECES, Magnetic	6	10/-	TRANSISTORISED Signal	1	10/-
No Plug	6	10/-	METERS	1	10/-
2.5mm Plug	4	10/-	TRANSISTORISED CAR REV. COUNTER KIT (Needs 1ma. meter as indicator)	1	10/-
3.5mm Plug	4	10/-			
500 MICRO-AMP LEVEL					
VEROBOARD, TRIAL PACK 5 BOARDS + CUTTER	10/-				

**MULLARD 'UNILEX' AMPLIFIERS**  
In our opinion these units are the best value for money ever offered. A complete stereo unit consisting of Control unit, Pre-amplifier, Two Main Amplifiers and Power Pack complete and ready for use—NO extra components to buy—yours for £15. (Normal retail price is £16.10s.)

**GARRARD SP 25 UNITS** also offered at a discount. Our price only £12.10s. Postage 9/-.

**SINCLAIR AMPLIFIERS AND SPEAKERS.** Complete range in stock All at 10 per cent discount on list.

**VEROBOARD**  
2 1/2in. x 3in. .15 1/3 Sin. .32in. .15 5/6 3 1/2in. x 3 1/2in. .14 9/16  
3 1/2in. x 2 1/2in. .15 3/3 1 7/8in. x 2 1/2in. .15 1 1/8in. Sin. x 2 1/2in. .14 7/8  
3 1/2in. x 3 1/2in. .15 3/11 1 7/8in. x 3 1/2in. .15 1 1/8in. Sin. x 3 1/2in. .15 5/6  
Sin. x 2 1/2in. .15 3/11 3 1/2in. x 2 1/2in. .14 7/8  
Spot Face Cutter 7/6. Pin Insert Tool 9/6. Terminal Pins (1 or 15) 3/6 for 36.  
Special offer pack consisting of 5 2 1/2in. x 1in. boards and Spot Face Cutter .10/-

**TRANSISTOR RADIOS**  
Once again we have a supply of these excellent radios which offer superb quality sound and excellent sensitivity. They are packed in a colourful presentation box complete with battery, earpiece and carrying case. Each one is guaranteed. You would expect to pay at least £5—but our price due to a bulk purchase is only 37/6. Many of our customers have made a considerable profit by buying these radios and re-selling them to friends!

**RECORD PLAYER CARTRIDGES.** Well below normal shop price!  
ACOS GP 67/2 15/-. (Mono). ACOS GP 91/3 20/-. (Compatible) ACOS GP 93/1 25/-. (Stereo) ACOS GP 94/- 30/-. (Stereo, Ceramic). ACOS GP 93/- DIAMOND 32/6. ACOS 94/1 DIAMOND 37/6.

**TRANSISTORISED FLUORESCENT LIGHTS.** 12 volt. All with Reverse Polarity protection. 8 watt 59/6. 15 watt 79/6. 13 watt 99/6. Postage 3/- per fitting. These can be sent on approval against full payment. Thousands already sold.

**MULLARD POLYESTER CONDENSERS**  
1,000 pf., 1,200 pf., 1,800 pf., 2,200 pf., 400 volts, 3d. each. 25 per cent discount 100 any type. .15uf., .22uf., .27uf., .160 volts, 6d. each. 25 per cent discount 100 any one type.

**RESISTORS.** Most values in stock. 10/- per 100 of any one value. 2/- dozen. 3d. 1 and 1 watt. MAINS DROPPER TYPE. Hundreds on values from .7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered 'assorted'. 10/- per dozen.

**SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS**  
Large range in stock. 15/- per 100 of any one value. 3/- per dozen. Singles 6d. each.

**RECORDING TAPE BARGAIN!** The very best British Made low-noise, high-quality Tape! Sin. Standard, 7/6. Long-play 9/-. Long-play 12/-, 7in. Standard 12/-. Long-play 16/3. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock available!

**£5 WORTH OF COMPONENTS FREE!!!!**  
Thinking of learning another language? If so, apply to us for details of Linguaphone courses. We will GIVE you £5 worth of components of your selection when you purchase a language course!!!!

**G. F. MILWARD, Drayton Bassett, Tamworth, Staffs.** Postage (minimum) per order 2/-.

# DIGI-CLOCK

By R. W. Coles

Part 3

**T**HIS month we give details of the alarm board construction, discuss the power supplies, and give the high voltage regulator board details.

## CONSTRUCTION OF BOARD "B"

The wiring of the alarm board follows the same general principle as that employed with the clock board described last month. In this case there are a large number of discrete components and it must be admitted that wiring up is quite tricky because of this.

It is best to construct the regulator first and test its operation before attempting the alarm circuit; the connection diagram for this circuit is given in Fig. 13. Note that there are three breaks to be made in the printed copper power supply strips, so that these tracks can be used for other connections, and also that the wire to the 200V supply does not pass through the edge contacts.

In all there are two wires which leave the board in this way, due to the shortage of edge contacts on the 22-way version used in the prototype. If desired the DL109/44 type of "Dualine" card could be used to prevent this.

## REGULATOR TESTS

To test the regulator it is desirable to have the power supplies already built, but any power supply providing the correct voltages can be used. It is also possible to drive the 12V bias line from a 20V supply if a 680 ohm resistor is used instead of the 15 kilohm R14 required when a 200V supply is employed.

The MJE521 power transistor is mounted on the chassis near the regulator, and is insulated with a mica washer which should be supplied with the device. A smear of silicon grease on either side of this washer helps heat transfer and should be used if available.

This transistor is much easier to mount compared with the traditional TO-3 packaged devices, only a single hole being required, facilitating its attachment to a temporary heat sink if desired for testing purposes—remember to bolt the transistor down with the brass collector tab next to the heat sink, and do not forget the washer.


When the test arrangement is wired up, connect the power supplies and monitor the output voltage, which should be somewhere between 3 and 8V. Adjust VR1 to obtain the required 5V, preferably with a load of about 20 ohms connected.

If all is well, decrease the load to about 4 ohms; the output voltage should drop under the control of the

current limiter. As the final test, short out the output while monitoring the current. The output voltage will drop to zero, and with any luck the current will drop to about 400mA. If it does not, there is probably something wrong with the wiring, and you may need a new output transistor.
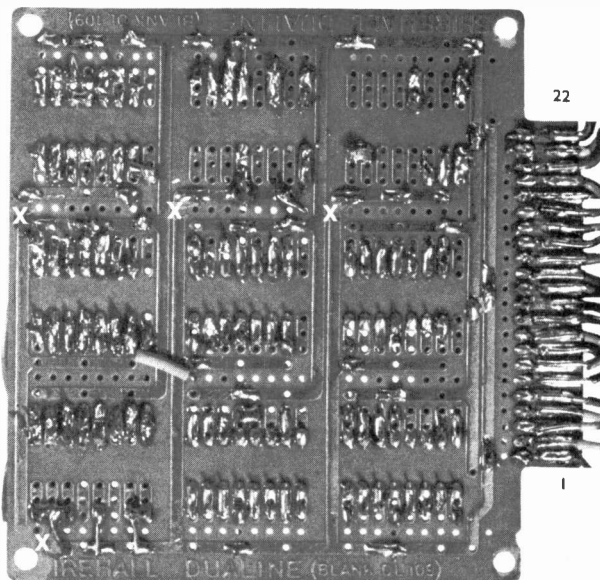
## ALARM CIRCUIT WIRING

When the regulator is tested and performs satisfactorily, the wiring of the alarm circuit can be carried out, first the package interconnections, then the discrete components and finally the wiring to the edge connector. The wiring on the plain side is shown in Fig. 13 with the edge connector wiring. Testing this circuit is difficult to achieve in isolation, and in this case it is better to wait until the clock is nearing completion. There is no reason why the alarm oscillator should not be checked with an oscilloscope or even an earphone.



*Underside view of the Alarm Board B showing positions of cuts in copper strips at four places marked X*

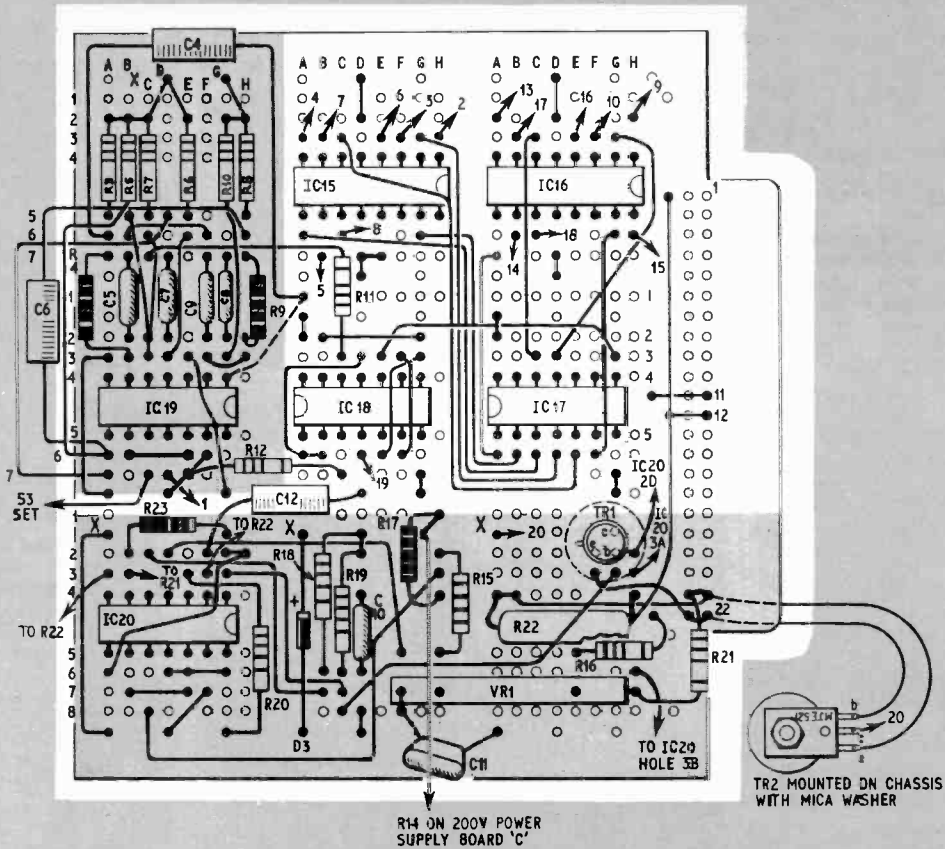


Fig. 13. Layout and wiring of the complete Board "B" incorporating the alarm circuit and 5V regulator

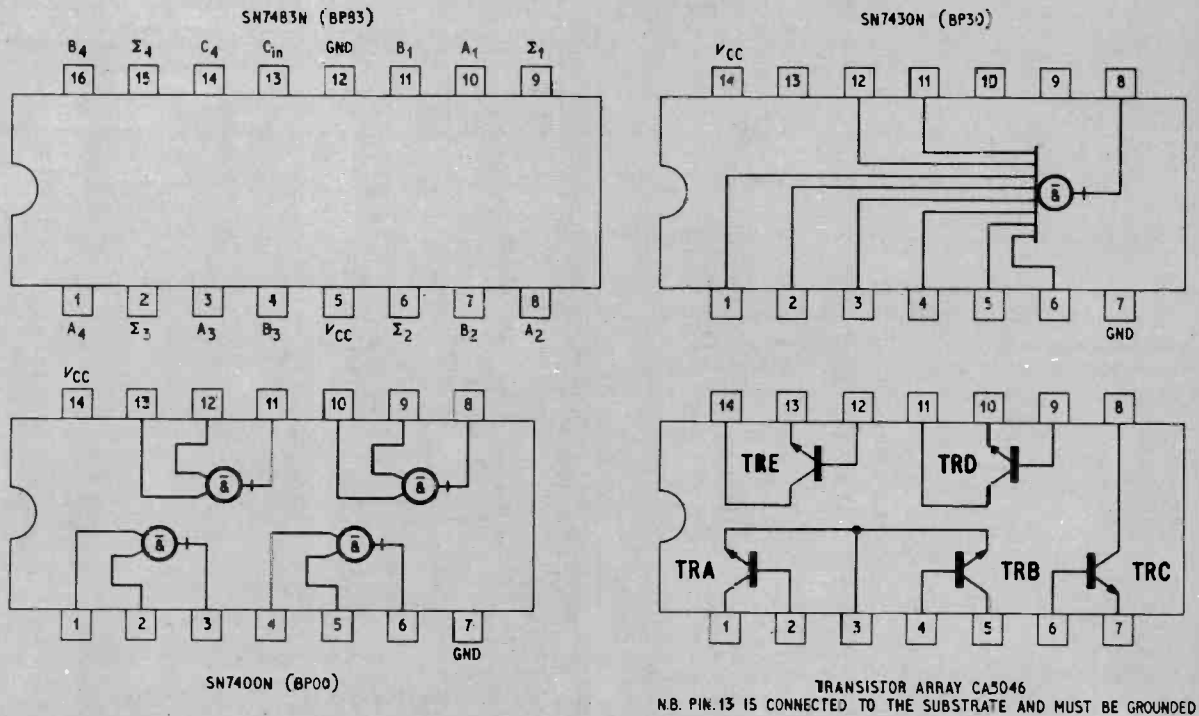


Fig. 14. Integrated circuit diagrams and pin connections for Board "B"

**ELECTRIC CLOCK WITH 25 AMP SWITCH**  
 Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only **39/6**, less than the value of the clock alone—post and insurance 2/9.



**20 AMP ELECTRICAL PROGRAMMER**

Learn in your sleep: Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smiths Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp Switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 in., deep. Metal encased, glass fronted with chrome surround. Offered at 47/6 plus postage and insurance.



**MAINS CONNECTOR**

A quick way to connect equipment to the mains safely and firmly; disconnection by plug prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. 12/6 each.



**DRILL CONTROLLER**

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions 29/6, plus 2/6 post and insurance.



**40 WATT 12in. HI-FI SPEAKER**

Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 40 watts R.M.S.—Cone moulded fibre—Freq. response 30-10,000 c.p.s.—specify 3 or 15 ohms. Chassis diam. 12in.—12 1/2in. over mounting flange. Overall height 5 1/2in. A £10 speaker offered this month for **£8.19.6** plus 7/6 post and ins.



**FLUORESCENT CONTROL KITS**

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-tinned, mostly resin filled. Kit A—15-20 w. 19/6. Kit B—30-40 w. 19/6. Kit C—80 w. 23/6. Kit E—65 w. 23/6. Kit F for 8ft. 125 w. tube 25/-. Kit MF1 is for 6 in., 9in. and 12in. miniature tubes, 19/6. Kit MF2 for 21in. 13 w. miniature tube, 20/-. Postage on Kits A and B 4/6 for one or two kits then 4/6 for each two kits ordered. Kits C, D and E 4/6 on first kit then 3/6 for each kit ordered. Kit F 5/6 on first kit then 4/6 for each kit ordered. Kit MF1 3/6 on first kit then 3/6 on each two kits ordered.

**BLANKET SWITCH**

Double pole with neon let into side to luminesce 6/8 dark, ideal for dark room light or for use with waterproof element—new plastic case. 8/6 each. 3 heat model 7/6.



**BLANKET SIMMERSTAT**

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using up to 1A. Listed at 27/6 each we offer these while our stocks last at only 12/6 each.


**INTEGRATED CIRCUIT BARGAIN**

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, 30-10,000 c.p.s.—specify 3 or 15 ohms. Chassis diam. 4 of the ICs are single silicon chip (P amplifiers). The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices 5/- upwards with circuits and technical data of each. Complete parcel only **£1** post paid. DON'T MISS THIS TERRIFIC BARGAIN.

**THIS MONTH'S SNIP**

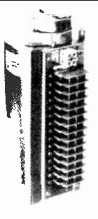**HONEYWELL PROGRAMMER**

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 16 changeover micro switches each of 10 amp type operated by the trips thus 15 circuits may be changed per revolution. Drive motor is mains operated 6 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from Makers probably over £10 each. Special snip price **£5.15.0**, plus 5/- post and insurance. Don't miss this terrific bargain.



**REED SWITCHES**

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types:

- Miniature. 1in long x approximately 1/4 in diameter. Will make and break up to 1A up to 300 volts. Price 2/6 each, 24/- dozen.
- Standard. 2 1/8 long x 1/4 in diameter. This will break currents of up to 1A, voltages up to 250 volts. Price 3/- each, 18/- per dozen.
- Flat. Flat type, 2in long, just over 1/4 in thick, flattened out, so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price 6/- each, 48/- per dozen.

**HIGH CAPACITY ELECTROLYTICS**

- Brand new, not ex-equipment.
- 100 mfd. 25V, 1/8 each 12/- doz.
- 200 mfd. 25V, 1/8 each 15/- doz.
- 250 mfd. 50V, 3/8 each 32/- doz.
- 400 mfd. 40V, 4/4 each 46/- doz.
- 400 mfd. 12V, 2/- each 11.0 doz.
- 500 mfd. 25V, 3/8 each 36/- doz.
- 500 mfd. 50V, 4/6 each 48/- doz.
- 500 mfd. 350V, 8/8 each 44.10.0 doz.
- 1000 mfd. 12V, 3/- each 41.10.0 doz.
- 1000 mfd. 18V, 3/4 each 34/- doz.
- 1000 mfd. 64V, 7/4 each 50/- doz.
- 2000 mfd. 25V, 6/8 each 79/- doz.
- 5000 mfd. 12V, 4/9 each 42.8.0 doz.
- 10,000 mfd. 6V, 5/9 each 43.0.0 doz.
- 10,000 mfd. 15V, 8/6 each 44.10.0 doz.
- 16,000 mfd. 10V, 10/6 each 45.0.0 doz.
- 60,000 mfd. 8V, 22/- each 110.0.0 doz.
- 70,000 mfd. 13V, 40/- each 120.0.0 doz.

**3 AMP 18V BATTERY CHARGER KIT**

comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier 22/6 + 4/6 post.

**18V 1A AMP POWER PACK.** This comprises double-wound 230/240V. mains transformer with full wave rectifier and 2,000 m.f.d. smoothing. Price 27/6.

**SONOTONE STEREO CARTRIDGE.** Turnover type, ref. No. 19 71. This fits most British pickups and is a really excellent reproducer. Limited quantity, 18/6.

**5 AMP 3 PIN SOCKETS.** These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size, 12 for 13/- plus 4/6 post.

**DITTO WITH SWITCH.** 12 for £1 plus 4/6 post.

**13 AMP SOCKETS, FLUSH MOUNTING.** Bakelite, cream, less switch, 6 for £1.


**2 AMP 3 PIN SWITCHED SOCKETS** for surface mounting, brown bakelite. Made by famous maker, 2/6 each or 24/- dozen.

**100 ASSORTED SILICON RECTIFIERS G.P. AND SWITCHING DIODES.** Small and very small sizes. A real snip for experimenters, 12/6 per 100.

**MAINS SUPPRESSION ADAPTOR** for preventing mains interference caused by vacuum cleaners, razors, sewing machines, etc, rated at 4 amps, simply plug this into your 5 amp 3 pin socket, 6/- each.

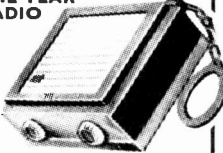**BARGAIN OF THE YEAR MICROSONIC KEYCHAIN RADIO**

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in. complete with soft leather zipped bag. Specification: Circuit: 7 transistor superheterodyne. Frequency range: 530 to 1,600 Kc/s. Sensitivity: 5 mv/m. Intermediate frequency: 465Kc/s or 465Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only **24/6** plus 2/6 post and insurance, less batteries. 6 for 27, post free. Rechargeable batteries 8/6 pair. Charger 8/6.




**TANGENTIAL HEATER UNITS**

These heater units are the very latest type, most efficient, and quiet running. As fitted in Hoover and blower heaters costing £15 and more. Comprises motor, impeller, and two elements allowing variable heat switching and with thermal safety cut out. Can be fitted into any metalline case or cabinet. Only need control switch. 1 1/2 K.W. model 39/6, 2 1/2 K.W. 60/6 and 3 K.W. model 79/6. Postage and insurance 6/6. Control switch 8/6.



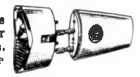**RE-CHARGEABLE TORCH**

Neat flat torch, fits unobtrusively in your pocket, contains 2 NiCad cells and built-in charger. Plugs into shaver adaptor and charges from our standard 200/240 volt mains. American made; sold originally at over 4 dollars. Our price only 19/6 each.



**19-PIECE SOCKET SET**

Complete with wall or bench rack. An ideal gift for the motorist. 15/6 + 4/6 post and insurance.



**PLINTH AND COVER**

Suitable for most auto-changers, teak base with tinted perspex cover. Specially made for Balfour. 85/- plus 6/6 postage.



Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. Semiconductor add 1/- post. Over £1 post free. S.A.E. with enquiries please.


**BALANCED ARMATURE UNIT**

500 ohm, operates speaker or microphone, so useful in Intercom or similar circuits, 6/6 each, £3.10 doz.



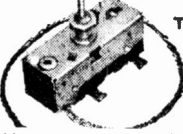**PROTECT VALUABLE DEVICES FROM THERMAL RUN-AWAY OR OVERHEATING**

Thyristors, rectifiers, transistors, etc., which use heat-sensitive components can be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg. F. or with the dial removed range setting is between 80 to 800deg. F. Price 10/-.




**THERMOSTAT WITH PROBE**

This has a sensor attached to a 15A switch by a 14in length of flexible capillary tubing—control range is 20°F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at 12/6 each. Postage and insurance 2/9.

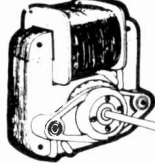
**MAINS MOTOR**

Precision made — as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at 9/6. Postage 3/- for first one then 1/- for each one ordered.



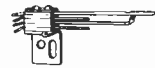
**NEED A SPECIAL SWITCH? Double Leaf Contact**

Very slight pressure closes both contacts, 1/8 each, 12/- doz. Plastic push-rod suitable for operating, 1/- each, 9/- doz.



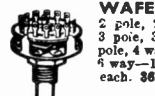**MINIATURE WAFER SWITCHES**

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 6 way—1 pole, 12 way. All at 4/6 each. 36/- dozen, your assortment.



**WATERPROOF HEATING ELEMENT**

26 yards length 70W. Self-regulating temperature control. 10/- post free.

**MICRO SWITCH**

5 amp. changeover contacts, 1/8 each, 18/- doz. 15 amp Model 2/- each or 21/- doz.



**ELECTRONICS (CROYDON) LTD**  
 Dept. PE, 266 London Road, Croydon CR0 2TH  
 Also 102/3 Tamworth Road, Croydon

# ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC. • LARGE STOCKS • NO SURPLUS

## BARGAINS IN NEW SEMICONDUCTORS


## PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



**12 + 12 watts RMS per channel!**

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel £38.90. Cabinet kit only £6. These prices nett.

## BAXANDALL SPEAKER SYSTEM

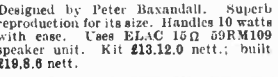

Designed by Peter Baxandall. Superb reproduction for its size. Handles 10 watts with ease. Uses ELAC 15Ω 59RM109 speaker unit. Kit £13.12.0 nett.; built £19.8.6 nett.

## MAINLINE AMPLIFIER KITS

RCA/SGS designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω.			
Power	Kit price	including components	Suitable unreg. power supply kit
12W	168/- nett		82/-
25W	190/- nett		N/A
40W	210/- nett		115/1
70W	252/- nett		138/10

## 30 WATT BAILEY AMPLIFIER KIT

Sensitivity 1.2V for full output into 8Ω. Transistors and PCB for one channel £7.5.6. Transistors and PCBs for two channels £14.11.0. Capacitors and resistors (metal oxide) 40/- per channel. Complete unregulated power supply kit £4.15.0.

Many items at new reduced prices. All power types supplied with free insulating sets

1N914	1/3	2N3706	2/8	40512	39/-	BC147	4/-	BFY51	4/-
1N3764	4/-	2N3707	2/8	40602	9/6	BC148	3/9	BSX20	3/9
1N4148	1/9	2N3708	2/8	AC107	14/6	BC149	10/-	BY184	10/-
1N6064	4/-	2N3709	2/8	AC126	4/-	BC153	7/-	BY238	3/8
18940	1/-	2N3710	2/8	AC127	4/-	BC154	7/8	BY238 (C106B)	14/8
2N696	3/8	2N3711	2/8	AC128	4/-	BC157	3/9	MCJ40	5/-
2N697	3/8	2N3731	24/-	AC176	6/-	BC158	3/9	MCJ41	27/-
2N1131	2/9	2N3794	3/-	ACY22	4/8	BC159	3/9	MJ491	30/-
2N1132	6/8	2N3819	7/-	ACY40	4/-	BC167	2/8	MFF102	7/8
2N1302	4/-	2N3820	12/-	ACY41	5/-	BC168	6/8	NKT403	18/8
2N1303	4/-	2N3904	7/8	AD142	14/3	BC169	2/8	NKT405	15/-
2N1304	4/6	2N3906	7/8	AD149	12/-	BC177	6/-	O447	1/9
2N1305	4/6	2N4058	4/-	AD161 AD162	14/8	BC179	6/-	OA90	1/3
2N1613	8/-	2N4059	4/-	(matched) 14	10/-	BC182L	2/8	OA91	1/3
2N1711	7/-	2N4060	4/-	AF114	7/-	BC183L	2/8	OA99	3/-
2N2147	19/-	2N4061	4/-	AF116	8/8	BC184L	8/8	OA200	1/11
2N2218	9/3	2N4062	4/-	AF117	8/8	BC186	8/8	OA202	2/-
2N2219A	16/8	2N4284	3/-	AF124	7/8	BC2121	7/-	OC71	7/8
2N2483	8/3	2N4286	3/-	AF127	7/-	BC213L	5/3	TIP31A	16/-
2N2484	9/8	2N4289	3/-	AF127	7/-	BC214L	5/3	TIP32A	20/-
2N2646	10/9	2N4291	3/-	AF139	9/8	BCY70	4/-	ZTX300	3/8
2N2904	11/-	2N4410	4/9	AF239	9/9	BD123	21/-	ZTX301	3/8
2N2924	2/8	2N4059	12/3	ASY26	8/8	BD123	21/-	ZTX302	3/8
2N2925	4/8	2N6163	5/-	ASY27	8/3	BD124	20/-	ZTX303	3/8
2N2926	2/8	2N5192	25/-	ASY28	8/3	BF167	8/8	ZTX304	4/8
2N3053	5/8	2N5195	28/8	B5041	15/-	BF178	10/8	ZTX305	4/8
2N3054	14/3	2N5457	9/8	BA102	4/-	BF180	12/-	ZTX306	5/-
2N3055	15/-	2N5458	9/8	BA106	4/-	BF194	7/-	ZTX307	6/-
2N3225	10/9	40250	14/3	BA145	4/8	BF195	7/8	ZTX500	5/-
2N3863	11/6	40361	12/8	BC107	2/8	BFX29	5/8	ZTX502	6/-
2N3702	2/8	40362	16/-	BC108	2/8	BFX85	7/-	ZTX503	5/-
2N3703	2/8	40406	16/3	BC109	2/8	BFX87	5/9	ZTX504	12/-
2N3704	2/8	40408	14/8	RC125	11/-	BFX88	5/3	ZTX530	5/5
2N3705	2/8	40430	37/-	BC126	11/-	BFY50	4/8	ZTX531	6/9

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	120W	5%	82Ω - 220kΩ	E12	18d	16d	15d
C	4W	5%	47Ω - 330kΩ	E24	25d	24	175d
C	1W	10%	47Ω - 10MΩ	E12	25d	24	175d
C	1W	5%	47Ω - 10MΩ	E24	3d	2.5d	225d
C	1W	10%	47Ω - 10MΩ	E12	8d	5d	4.5d
MO	1W	2%	10Ω - 1MΩ	E24	9d	9d	7d
WW	1W	10%	0.22Ω - 3.9Ω	E12	1/8d all quantities		
WW	3W	5%	12Ω - 10kΩ	E12	1/8d all quantities		
WW	7W	5%	12Ω - 10kΩ	E12	1/8d all quantities		

CODES: C = carbon film high stability low noise. MO = metal oxide Electrofilm TR5 ultra low noise. WW = wire wound Plesey.

VALUES: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating. NOT mixed values. (Ignore fractions of 1d on total resistor order.)

## INTEGRATED CIRCUIT AMPLIFIERS

**SINGULAR IC.10** complete with instruction book giving amplifier circuit details and range of applications. 58/8 nett. Components pack for stereo inc. mains transformer, controls, etc., £4.15.0 nett.

**PLESSEY SL403A.** Only 42/8 each nett. 3W into 7.5Ω for 18V supply. Application data 2/- free with two or more.

## WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W . . . . . 4/9 each

**SLIDER SWITCHES** D.P.D.T. . . . . . 3/- each

## NEON INDICATOR LAMPS

all 200/250V. Square bezel, red only . . . . . 3/9  
Round chrome bezel red, amber, clear . . . . . 4/9 each  
Toggle switches, 250V a.c. 1.5A. Chrome dolly and chrome milled nut S.P.S.T. T. 3/8; S.P.D.T. 4/8; D.P.D.T. 5/8; S.P.D.T. centre off 5/-.

S-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. S-DeC (70 points) only 20/-. Compact T-DeC. Increased capacity, may be temperature-cycled. T-DeC (208 points) only 50/-. Full range stocked.

## MULLARD POLYESTER C280 series

250V 20%: 0.01, 0.022, 0.033, 0.047, 8d ea.; 0.068, 0.1, 9d ea.; 0.15, 11d; 0.22, 1/-; 10%; 0.33, 1/5; 0.47, 1/8; 0.68, 2/3; 1μF, 2/9; 1.5μF, 4/2; 2.2μF, 4/9.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 1/3 each  
Values (μF/V): 0.04/64, 1/40, 1/6/25, 2.5/16, 2.5/64, 4/10, 4/40, 6/64, 6.4/16, 6.4/25, 8/4, 8/40, 10/2.5, 10/16, 10/64, 12/16, 25, 16/40, 20/16, 20/16, 20/64, 25/6.4, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/2.5, 50/6.4, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/6.4, 126/4, 125/10, 125/16, 160/2.5, 200/6.4, 200/10, 250/4, 320/2.5, 320/6.4, 400/4, 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 5/6; 1000/50 8/2; 1000/100 16/3; 2000/25 7/4; 2000/50 11/4; 2000/100 28/8; 2500/64 15/5; 2500/70 19/6; 5000/25 12/8; 5000/50 21/11; 5000/100 58/3; 10000/15 17/-; 10000/25 24/8; 10000/50 44/-; 10000/70 61/-.

## MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 1/9; 100/25 1/9; 100/50 2/8; 250/25 2/8; 330/25 2/8; 250/50 3/8; 500/25 3/8; 500/50 4/8; 1000/25 4/-; 1000/50 8/-; 2000/25 8/-.

## SMALL ELECTROLYTICS

Axial leads: 4.7/10, 4.7/25, 5/50, 1/- ea. 10/10, 10/25, 10/50, 33/10, 50/10, 1/- ea. 25/25, 25/50, 47/25, 100/10, 220/10, 1/8 ea.

## ENAMELLED COPPER WIRE

even No. SWG. only; 2 oz. reels: 16-22 SWG 4/3; 24-30 SWG 5/-; 32, 34 SWG, 5/8; 36, 38 SWG, 6/3. 4 oz. reels: 16-22 SWG only 7/6.

## ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 3/8 ea. 1W: 6.8V to 82V 9/- ea. 1.5W: 4.7V to 75V 12/- ea. Clip to increase 1.5W rating to 3 watts (type 266F) 9d.

## CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level.	
Single gang linear	220Ω to 2.2MΩ 2/8
Single gang log	47KΩ to 2.2MΩ 2/6
Dual gang linear	47KΩ to 2.2MΩ 8/8
Dual gang log	47KΩ to 2.2MΩ 8/8
Log/antilog	10K, 47K, 1MΩ only 8/8
Dual antilog	10K only 8/8
Any type with 1A D.P. mains switch, extra 2/3.	
Please note: only decades of 10, 22 and 47 are available within ranges quoted.	

## CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting 1/- each.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on postages).

## NETTING AND PACKING

Free on orders over £2. Please add 1/6 if under. Overseas orders welcome: carriage charged at cost.

## HAVE YOU HAD YOUR ELECTROVALUE CATALOGUE?

48 pages—thousands of items—packed with information, generously illustrated with product pictures and technical diagrams—2/- post free. Add 4/- if sent overseas by air mail.

## POWER SUPPLIES AND CONSTRUCTION

The power supplies that provide the various d.c. voltages required by the Digi-Clock circuitry are quite conventional in design, as can be seen from Fig. 15. Outputs required from the supplies are:

- (a) 10 volts (nominal) at 1A (max), from which the regulated 5 volt supply is derived.
- (b) 180 volts at 10mA (nominal), which is used to drive the anodes of the "Nixie" tubes and decimal-point indicator.
- (c) 200 volts (nominal) at 25mA (max), which is used to supply the 180 volt regulator, and to drive the 12 volt bias line of the 5 volt regulator.

In addition a 6.3V r.m.s. (50Hz) low current supply is required to provide the clock timing waveform.

No on/off switch was fitted to the prototype, as permanent use when plugged into the 230/250V a.c. mains supply makes it unnecessary. A mains switched socket with fused plug or a fused spur outlet is recommended for installation. A clock will normally be left on permanently, only being switched off at holiday times or other occasions when the house is vacated for long periods.

If the constructor's house wiring uses the non-fused type of plug then it is vital that a separate fuseholder be incorporated in the clock design to provide protection of the transformer primaries. While on the subject of fuses, remember that all fuses used in this design are necessary for safety, the clock is intended to run continuously, often unattended, and the only way safety can be assured is by proper fusing.

## LOW VOLTAGE SUPPLY

Two power transformers were used in the prototype to provide the necessary a.c. supplies (Fig. 15). This proved to be necessary because of the difficulty of finding a single transformer with suitable ratings and of the correct physical size.

The transformer selected for the low voltage supply not only provides the required 10V at 2A, but also has the highly desirable feature of an interwinding screen, which reduces the coupling of mains-borne r.f. interference into the logic supply lines.

Constructors who may prefer to use a different case design from that used in the prototype, may like to know that West Hyde Developments make a single transformer that will supply all the voltages required by the clock. This is type TRA which is too large to fit into the specified Case "C".

An encapsulated bridge rectifier (D4 to D7 in Fig. 15) with a current rating of 1A (continuous) is used as the low voltage full wave rectifier, and this is followed by a 5,000 $\mu$ F smoothing capacitor C10 in the usual way. Two "protection" components are included in this circuit.

When switching on, a very large surge current flows for a short period as the capacitor is charged. This current would be limited only by the internal impedance of the transformer, and might exceed the 8A surge rating of the bridge, were it not for the inclusion of R24 between it and C10. The resistor, of course, imposes a large voltage drop under surge conditions, and ensures that the current cannot exceed 8A, whereas during normal operation the voltage drop across it will only be an insignificant half-volt or so.


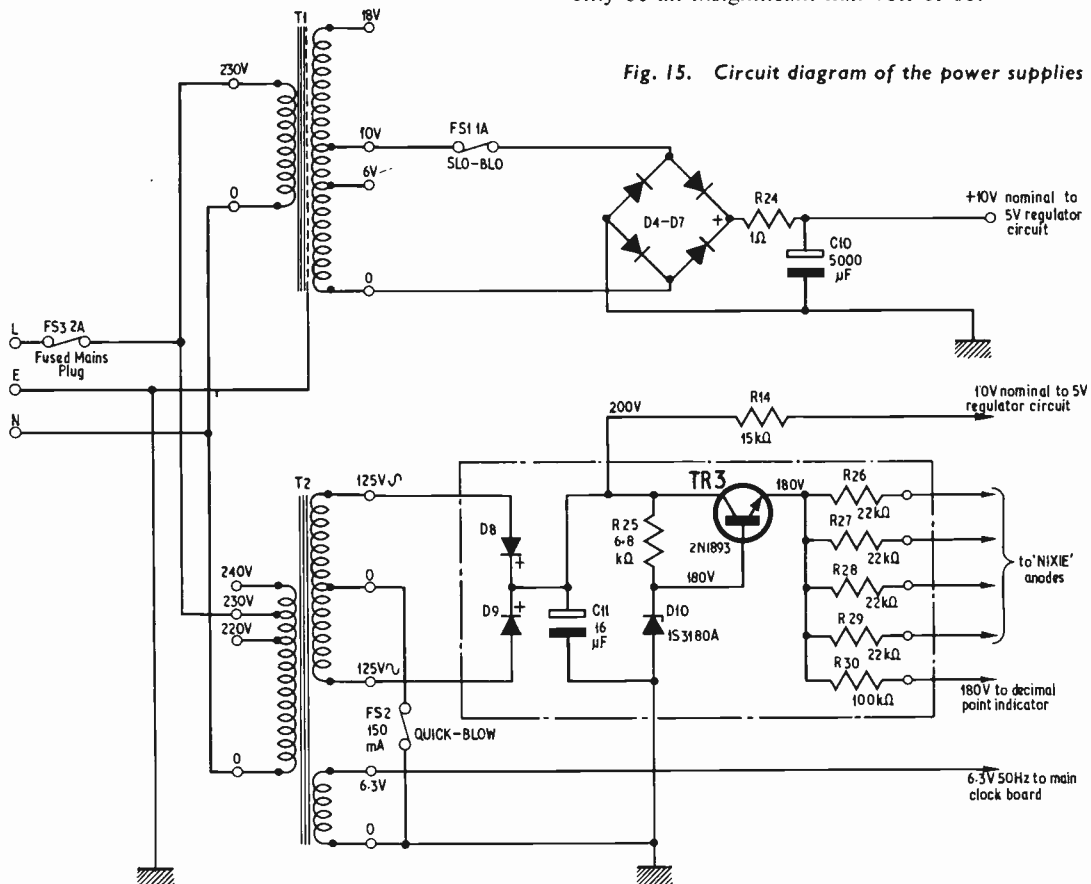


Fig. 15. Circuit diagram of the power supplies

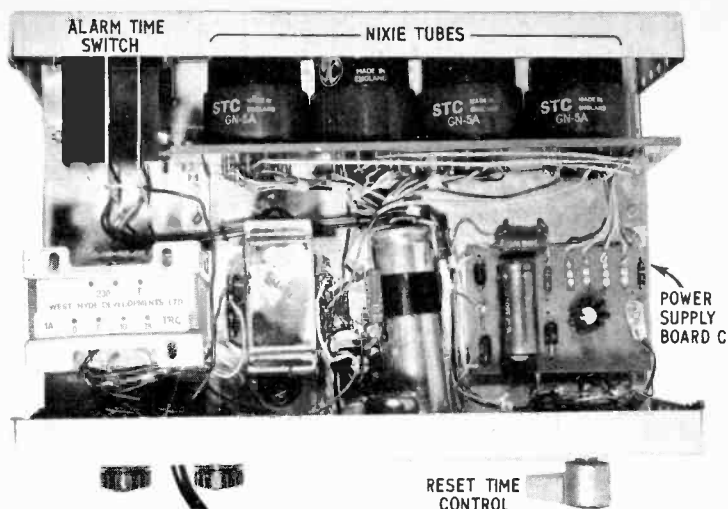Top view of the chassis showing power supply components



The increase in the impedance of the supply caused by its inclusion does not pose a problem because the final 5V output is provided by a feedback regulator, which as we have already seen, reduces the supply impedance to a fraction of an ohm.

The use of an anti-surge fuse in this supply allows very close protection of the bridge and transformer, without having to increase the fuse rating to accommodate surge currents, as would be the case with quick-blow devices. Fuse FS1 ignores short duration current transients, but will blow within a few tens of milliseconds should its rating be continuously exceeded.

The smoothing capacitor C10 should be a good quality type with a high ripple-current rating. Components inadequate in this respect will have a reduced life in this type of circuit.

## COMPONENTS . . .

### POWER SUPPLIES

#### Resistors

R24	1 $\Omega$ 3W wirewound	R28	22k $\Omega$
R25	6.8k $\Omega$	R29	22k $\Omega$
R26	22k $\Omega$	R30	100k $\Omega$
R27	22k $\Omega$		

All  $\pm 5\%$ ,  $\frac{1}{2}$ W high stab. except R24

#### Capacitors

C10	5,000 $\mu$ F elect. 15V
C11	16 $\mu$ F elect. 350V

#### Diodes

D4 to D7	Bridge rectifier 1B10J10 100 p.i.v. 1A (Texas)
D8, D9	PL4004 (General Instruments) or any 400 p.i.v., >50mA
D10	IS3180A (Texas) or ZX180. Zener 180V, >2mA

#### Transistor

TR3	2N1893
-----	--------

#### Transformers

T1	Mains primary; 10V 1A secondary with interwinding screen (e.g. Type TRC by West Hyde Developments Ltd., Ryefield Crescent, Northwood Hills, Northwood, Middlesex).
T2	Mains primary; 250V c.t. 25mA and 6.3V 1A secondary (e.g. "Midget Mains 250V" type by Radiospares).

#### Loudspeaker

LS1	80 $\Omega$ 2 $\frac{1}{2}$ in diameter
-----	---

### HIGH VOLTAGE SUPPLY

Transformer T2 is used to provide the high voltage supply for the display and 6.3V a.c. for the timing circuits. The two diodes (D8 and D9) and the smoothing capacitor C11 complete the full-wave rectification circuit as shown in Fig. 15.

The nominal 200V supply developed across C1 is fed to the 5V regulator via R14. This resistor should be mounted as close to the board as possible to reduce the risk of direct short circuits, but it cannot be mounted on the board because of the amount of heat it dissipates. Although not used in the prototype, a small tag-strip could be employed to support it, and allow air circulation.

The 180V regulator is simply an emitter follower circuit with the base voltage of transistor TR3 set by the breakdown voltage of a 180V Zener diode D10.

### Display Tubes

V1 to V4 GN-5A (S.T.C.) "Nixie" numerical indicators or similar (Electroniques (S.T.C.) Ltd., Edinburgh Way, Harlow, Essex)  
LPI Neon indicator lamp miniature (e.g. type 1M8)

### Switches

- S1 3-pole, 3-way rotary wafer switch.
- S2 Decade thumbwheel switch, 2 banks with 2 side plates. (Type SB10N1248, Birch Stolec Ltd.). Alternatively 2 wafer thumbwheel switches, 4-pole, 10 way
- S3 Single-pole changeover miniature toggle

### Fuses

- FS1 1A Slo-Blo cartridge with fuseholder
- FS2 150mA cartridge with fuseholder "Behind-panel" depth not more than 1in


### Miscellaneous

- Case Contil Mod-2 Type C (West Hyde Developments)
- Display panel, s.r.b.p. 8in  $\times$  2 $\frac{1}{2}$ in  $\times$   $\frac{1}{2}$ in
- Printed circuit Board "C" copper clad 3in  $\times$  2in
- Aluminium brackets for display panel 2 $\frac{1}{2}$ in  $\times$  1in  $\times$   $\frac{1}{2}$ in wide
- Capacitor clip for C10
- Perspex sheet orange translucent 7 $\frac{1}{2}$ in  $\times$  2 $\frac{3}{4}$ in
- Heatsinks, clip-on for TR1 and TR3 (see photos)
- Thin flexible connecting wire different colours
- Nuts and bolts 4 B.A. and 6 B.A.  $\times$  1in
- Grommets and soldering tags. Lettering transfers





# LIND-AIR AUDIO

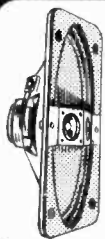


### E.M.I. LOUDSPEAKERS

MODEL 450. 13 1/2 in. x 8 in. elliptical with twin tweeters. 8 ohm impedance. 10W. Brand new, guaranteed. Lind-Air Price 79/6. P. & P. 4/6.

MODEL 150. 13 1/2 in. x 8 in. elliptical. 3 and 15 ohm impedance. 10W. Lind-Air Price 59/6. P. & P. 4/6.

### C1001 MULTI-TESTER

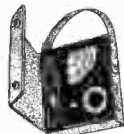


Overload protection 20,000 ohms per volt; a.c. volts 10, 50, 250, 1,000V; d.c. volts 5-25, 125, 500, 2,500V; d.c. current 0-50µA, 0-250mA; Resistance 0-60kΩ 0-6MΩ; decibels -20 to +22dB. Size of meter 4 1/2 in. x 3 1/2 in. Complete with case. 85/-, P. & P. 3/6.

### 62D MULTI-TESTER

20,000 ohms per volt; d.c. voltage 5, 25, 50, 250, 500V, 2.5kV (20,000 ohms per volt), a.c. voltage 10, 50, 100, 500, 1,000V (10,000 ohms per volt); d.c. current 0-50µA, 0-250mA; resistance 0-6kΩ, 0-6MΩ (300 ohms and 30kΩ at centre scale); capacitance 10F to 0.001mF, 0.001µF to 0.1µF; decibels -20 to +22dB. Size 4 1/2 in. x 3 1/2 in. 71/-, P. & P. 3/6.



### SINCLAIR PROJECT 60

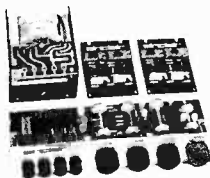

An attractive alternative for the enthusiast prepared to assemble these excellent modules to make a stereo assembly. Z.30 24W Power Amplifier 89/6 (2 required). Stereo Sixty Control/Pre-amplifier 29.19.6. PZ.5 Power Supply Unit 24.19.6. **SINCLAIR PROJECT 60** Package deal price 19 Gns. P. & P. 12/6. Project 60 is supplied complete with instruction manual and templates for plinth mounting.

**SINCLAIR IC-10 INTEGRATED CIRCUIT 10W Amplifier.** Size only 1 in. x 0.4 in. x 0.2 in. A true hi-fi amplifier complete with manual giving details of a wide range of applications and instructions. Guaranteed 5 years. **ONLY 59/6.** P. & P. 1/6. **SPECIAL TRANSFORMER FOR OPERATING SINCLAIR IC-10** from a.c. mains 230/250V. Output 13V at 0.3A. 16/6. P. & P. 2/4.



## SAVE OVER £11

### LA20 STEREO SYSTEM

Only takes a few minutes to set up ready for use.

Lind-Air LA20 Amplifier ..... £23.2.0  
Garrard 5-200 Changer with Sonotone Cartridge ..... £11.7.6  
Pair of Lind-Air General Purpose Speakers ..... £19.0.0  
Recommended Retail Price ... £53.9.6


(Also available with Garrard 3000 changer 4 gns. extra)

### LIND-AIR PRICE

## 39 1/2 GNS.

Carr. & Ins. 35/-

### SAVE ON AKAI!

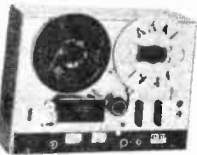

4000 Stereo Tape Recorder. List £124.18.0.

**Our Price 99 Gns.**

Carr. 35/-

4000D STEREO TAPE DECK. List £89.19.1.

**Our Price 69 Gns.**

Carr. 35/-

1710L STEREO TAPE RECORDER. List 89 gns.

**Our Price 69 Gns.**

Carr. 35/-

### TELETON SAQ203 TRANSISTOR STEREO AMPLIFIER



Superb quality hi-fi 10 watts per channel music power. Inputs for Gram (Magnetic and Crystal). Tuner and Auxiliary, Tape Record output. Controls: Volume, Balance, Bass, Treble. Attractive oiled walnut cabinet and brushed aluminium front panel. List Price £28.7.0.

### LIND-AIR PRICE

## 22 Gns.

P. & P. 10/-

### SPECIAL LIND-AIR PURCHASE!

**FANTASTIC SANSUI 200 AM/FM MULTIPLEX STEREO TUNER AMPLIFIER**  
Solid state 17 watts music power. Fully tunable over Medium wave and VHF/FM Stereo. Inputs for gram and tape etc. Host of outstanding features—details on request. Rec. Retail Price £89.19.10. LIND-AIR PRICE £75.12.0. P. & P. 10/-.



### Hi-Fi Catalogue



100 pages fully illustrated with 8 page P.A. section. All leading makes and accessories plus details of Budget Stereo Systems. 5/-, P. & P. 1/-.

### UNILEX MODULES

**BUILD A STEREO AMPLIFIER FOR ONLY £16.15.0**  
P. & P. 7/6

**PACKAGE DEALS**  
Unilex Modules ..... £16.15.0  
Garrard 2025 ..... £11.14.1  
Celestion Speakers ..... £5.17.0

£24. 6.1  
**LIND-AIR PRICE** P. & P. 20/-  
28 GNS.

Unilex Modules ..... £16.15.0  
Garrard 8P25 Mk II ..... £15.11.4  
B.S.R. CI Cartridge ..... £3.17.3  
Celestion Speakers ..... £5.17.0

£42. 0.7  
**LIND-AIR PRICE** P. & P. 20/-  
35 1/2 GNS.




### DE-LUXE STEREO HEADPHONES

With soft rubber earpieces. Impedance 8-16ohms. Frequency response 23-13,000Hz. With lead and stereo plug. **Only 59/6.** P. & P. 3/6.


### SOLDERING GUN

### WELLER "EXPERT"

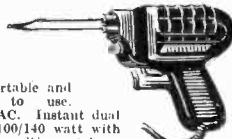

Comfortable and easy to use. 240V AC. Instant dual heat 100/140 watt with two position trigger control. **OUR PRICE** 67/6. P. & P. 2/-.

### S-DEC BREADBOARD

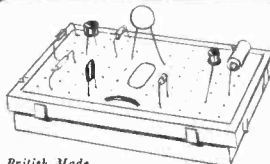

*British Made*  
Solderless breadboard panels, for fast reliable component connections. Single DeCa. One S-Dec with Control Panel, Jig and Accessories for solderless connections to controls, etc., with booklet "Projects on S-Dec" giving construction details for a variety of circuits. 29/6. P. & P. 2/6. 4-DeC KIT. Four S-Decs with two Control Panels, Jigs and Accessories and the booklet "Projects on S-Dec" all contained in a strong attractive plastic case. Ideal for the professional user. £17.18. P. & P. 3/6. T-DeC KIT £2.10.0. P. & P. 3/6.

### Garrard HI-FI TURNTABLES



2025 T/C with stereo cartridge ..... £8.19.6  
3000 with Sonotone 9TAHC1 stereo cartridge ..... £10.19.6  
8P25 Mk. II ..... £10.19.6  
8P25 Mk. III ..... £12.19.6  
SL65B ..... £15.19.6  
Base and cover for above ..... £5.19.6  
AF75 ..... £18.19.0  
SL72B ..... £24.19.6  
SL75B ..... £28.7.0  
SL95B ..... £39.9.0  
Base and cover for above ..... £8.19.6  
401 ..... £28.10.0  
P. & P. Decks, 12/6; Base and Cover, 10/-; Deck/Base/Cover, 17/6.

**SPECIAL OFFERS!**  
8P25 Mk. II with base ..... £14.10.0  
P. & P. 15/-  
8P25 Mk. II with Sonotone 9TAHCD cartridge and base ..... £15.15.0  
P. & P. 15/-  
Sonotone 9TAHCD cartridge ..... £2.15.0  
P. & P. 1/6

18/19, 25 & 53 TOTTENHAM COURT ROAD, LONDON W.1.  
Tel: 01-580 2225/4532/7679  
Open 9-6 Mon-Sat (Thurs until 7)

All Mail Orders and correspondence to Dept. PE14, Kirkman House, 54a Tottenham Court Road, London, W.1. Tel: 01-580 7041/2.

94-96, UPPER PARLIAMENT STREET, NOTTINGHAM  
Tel: Nottingham 40403 (STD 0602)  
Open 9-6 Mon-Sat (Weds until 7.30)



### 2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blades cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £8.18.0. Post and ins. 7/6.

**12 volt Car Battery Trickle Charger.** Made in Japan, this is very small and neat. Regular use will keep your car battery in good trim throughout the winter. Silly price, 25/- plus 4/6 postage and insurance.

### QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. 24/6, post and insurance 2/9. 12v. car model also available 19/6.



### PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover. 85/- plus 6/6 postage. Special set for Balfour autochanger 85/- plus 6/6 postage.



### THRYSITOR LIGHT DIMMERS

Will dim incandescent lighting up to 600 w. from full brilliance to out. Assembled and wired ready to install. 59/6.



### AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.18.6 plus 5/- post and ins.



### COMPUTER TAPE

2,400 ft. of the best magnetic tape money can buy. Made by E.M.I., 1in. wide almost unbreakable and on a 10 1/2in. metal computer spool. Users have claimed successful results with video as well as sound recordings. 19/6 plus 6/6 post. Cassette to hold spool 10/- extra.




**HORSTMANN "TIME & SET" SWITCH** (A 30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price 29/6. Post and ins. 4/6.

### 1 HOUR MINUTE TIMER

Made by famous Smiths company, these have a large clear dial, size 4 1/2in. x 3 1/2in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch, 22/6.



### THE FULL-FI STEREO SIX

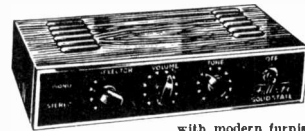

The amplifier sensation of the year. You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and teak finished to blend

with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is £2.19.6 plus 7/6 post and insurance.

### STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 1/8in spindle 2in long—with locking washer and nut.

No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way
1 pole	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6
2 poles	6/6	6/6	6/6	6/6	6/6	6/6	6/6	6/6	10/6
3 poles	6/6	6/6	6/6	6/6	10/6	10/6	10/6	14/6	14/6
4 poles	6/6	6/6	6/6	6/6	10/6	10/6	10/6	18/6	18/6
5 poles	6/6	6/6	10/6	10/6	14/6	14/6	14/6	22/6	22/6
6 poles	6/6	10/6	10/6	10/6	14/6	14/6	14/6	28/6	28/6
7 poles	10/6	10/6	10/6	14/6	18/6	18/6	18/6	30/6	30/6
8 poles	10/6	10/6	10/6	14/6	18/6	18/6	18/6	34/6	34/6
9 poles	10/6	10/6	14/6	14/6	22/6	22/6	22/6	38/6	38/6
10 poles	10/6	10/6	14/6	18/6	22/6	22/6	22/6	42/6	42/6
11 poles	10/6	14/6	14/6	18/6	28/6	28/6	28/6	46/6	46/6
12 poles	10/6	14/6	14/6	18/6	28/6	28/6	28/6	50/6	50/6

Where postage is not stated then orders over £5 are post free. Below £5 add 2/9. S.A.E. with enquiries please.

### SPARTAN Portable RADIO

Long and medium wave, 7 transistor, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case. £2.15.0. plus 5/- post and ins.



### MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available. 500, 850, and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter 5in. long. Price 17/6 plus 4/6 post and ins.



### MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 x 2in. 19/6 each.



### DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 10/- each, plus 3/6 post and insurance, 6 or more post free.



### 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 2/6 each, 24/- doz.



**ELECTRONICS (CROYDON) LTD**  
Dept. PE, 266 London Road, Croydon CR0 2TH  
Also 102/3 Tamworth Road, Croydon

## You should read the Goodmans High Fidelity Manuals

Goodmans High Fidelity Manuals are of vital interest to you, and contain constructive and informative articles on all aspects of High Fidelity sound.

One manual contains specifications, descriptions and full colour illustrations of the entire current range of loudspeaker cabinets, systems, amplifiers and F.M. tuners. The construction manual contains the information needed by those enthusiasts who prefer to make their own High Fidelity or musical instrument loudspeaker systems.

These manuals are available free from

### Goodmans Loudspeakers Limited

Axlom Works Lancelot Road Wembley Middx. Tel: 01-902 1200

Please send me:  
Full colour manual  (Tick as required)  
Construction manual   
Name \_\_\_\_\_  
Address \_\_\_\_\_

P.E.2

## YUKAN SELF-SPRAY SO PROFESSIONAL THE YUKAN AEROSOL WAY— Get these air drying GREY HAMMER NOW! OR BLACK WRINKLE (CRACKLE) finishes

Yukan Aerosol spraykit contains 453g fine quality, durable easy instant spray. No stove baking required. Hammers available in grey, blue.

Modern Eggshell Black Wrinkle (Crackle) all at 85p at our counter or 90p carriage paid, per push-button self-spray can. Also Durable, heat and water resistant Black Matt finish (399g self-spray cans only) 75p carriage paid.

SPECIAL OFFER: 1 can plus optional transferable snap-on trigger handle (value 25p) for 90p carriage paid. Choice of 13 self-spray plain colours and primer (Motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:

DEPT: YUKAN, 307A, EDGWARE ROAD, LONDON, W2 1BN

We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too.

Open all day Saturday. Closed Thursday afternoons.

Other Yukan Air Drying Aerosols. 453g at 90p curr. paid include:  
Zinc Chromate  
Clear Lacquer  
Metallics: Grey, Blue.



## AMAZING MINI-DRILL

FOR PRECISION MODEL WORK



+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) 79/6 p.p. 2/6. De Luxe Professional Kit with 17 tools 130/- p.p. 4/6. Money Ref. Guarantee.

### MERLIN SUPPLY CO.

Dept. PE2D, Nailsea, Bristol BS19 2LP

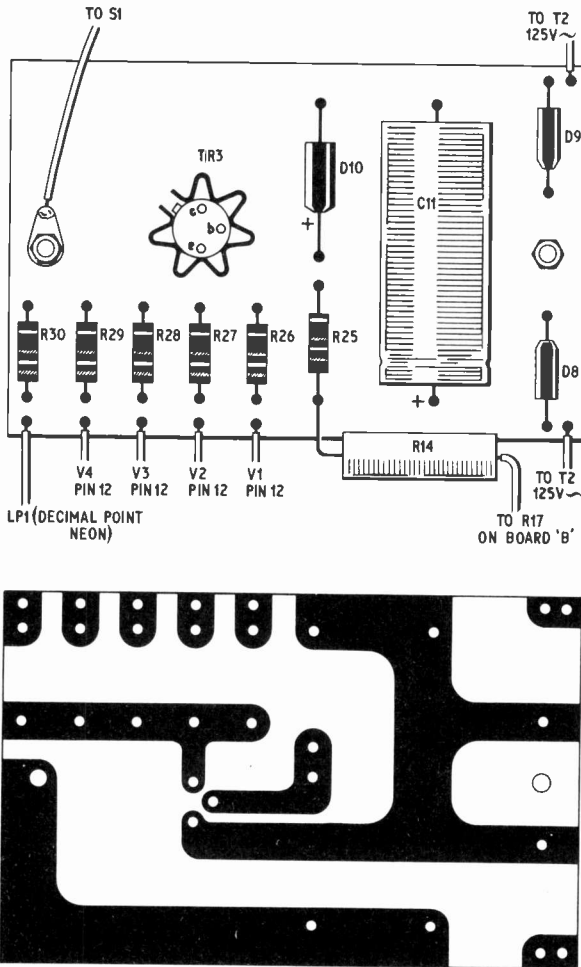


Fig. 16. Layout of components on Board "C", the high voltage regulator—shown full size

The transistor used in this position must have a high  $V_{cb}$  rating to allow for the difference between the unregulated input and the regulated output voltage, even under transient conditions. The regulator may be called on to provide up to 10mA at 180V.

If the nominal 200V supply rises to more than 220V, the transistor would get quite hot; hence the clip-on heat sink used in the prototype. The anode resistors R26 to R30 for the four "Nixie" tubes and the decimal-point indicator are mounted alongside the regulator on the same printed circuit board to give a neat appearance and to reduce the risk of a damaging short circuit.

Shorting the individual anode outputs to earth will not harm the regulator, because these resistors limit the current to a safe value. However, if the 180V output is shorted, the transistor will be instantly destroyed. In fact, in this design, the series pass transistor is used as a "fuse", it being impossible to use a conventional fuse link to afford any protection to a device operated under these conditions.

The 150mA fuse FS2 in the "earthy" line of the transformer will only be able to act fast enough to protect the diodes and the transformer itself, and the only way the transistor can be protected is by using a current limiter similar to that used in the 5V regulator, a course considered unnecessarily expensive in the prototype.

## PRINTED CIRCUIT

The printed circuit used for the 180V regulator is of a simple design which lends itself to home production using the "paint and etch" system of printed circuit board construction which many readers will have used before.

The layout is shown in Fig. 16, which also gives component mounting details. It is recommended that the holes be drilled before the printed pattern is painted on, as this gives a good guide, and enables more accurate painting to be achieved.

If the constructor does not have facilities for producing printed circuits there is no reason why a tag-board of similar dimensions should not be used to support the regulator components, though the appearance would not be as neat in this case.

## NIXIE DISPLAY

The drivers and power supplies used in the Digi-Clock are capable of handling any type, or make, of gas filled numerical indicator tubes currently available, and alternatives may be directly substituted for the STC GN5A used in the prototype, with appropriate wiring changes according to the pin connections.

Manufacturer's data on "Nixie" tubes usually states that the highest anode voltage available should be used to drive these devices, and readers may be a little puzzled by the choice of 180V for this design, as this is very close to the minimum voltage allowable.

The reason for the choice of such a low voltage is that the SN7441AN decoder driver is only guaranteed to "hold off" 55V; a Zener diode connected to each output breaks down if this voltage is exceeded. This means that the maximum voltage differential which can be achieved across the tube is 55V.

In our case, the voltage across the tube when it is supposed to be off is 180-55V which means that 125V can still be applied in these circumstances. Obviously, if the anode supply is raised too far, the 55V differential will be insufficient to ensure that the cathodes, which are supposed to be off, do not conduct.

## COLOUR FILTER

If these cathodes do conduct, an unpleasant background haze is produced which impairs the readability of the display, and in extreme cases more than one numeral could become lit within the same tube. For a clear "Nixie" display with the view of the unlit numerals completely suppressed, it is important that a red or orange coloured filter be employed between the tubes and the observer.

Although tubes are available with this filter applied as a lacquered coating on the outside of the glass envelope, by far the best system is to use clear tubes with a common external filter sheet. In this design the filter is produced from a sheet of ordinary orange tinted Perspex, which performs admirably in this role, mounted on the front of the clock to form the viewing window.

The decimal point separating the two "minutes" indicators from the "hours" section has to be provided separately when using the GN5A "Nixies", as these devices do not have integral points as do some other types. In the prototype a Hivac type 1MH "Minicator", miniature neon, performed well in this role, and was driven from the 180V supply via a 100K resistor. Any small neon lamp, such as used for mains indicators, could be used with the correct value of series resistor R30.

**Next month: Final wiring and testing**

# Readout —

## A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

### Time expense

Sir—I have been a faithful reader of PRACTICAL ELECTRONICS for a good many years now, and I have not until this month's issue (December 1970), come across a Digital Clock.

But I would like to express my disappointment when I saw the circuit, and found the cost of it was in the region of twenty-five to thirty pounds to produce. This puts the clock well beyond my, and I should imagine many other readers' grasp, and even then with a little too much heat on one of the pins the complete project could be destroyed.

I have also seen on the market a digital clock using a cold cathode display, costing under twenty pounds, so I was naturally assuming that your project would cost much less,—but it doesn't.

I'm sure many other readers must feel the same way about the high cost, and I cannot see many readers attempting the project.

C. Honeyands,  
Cosford,  
Wolverhampton.

The estimated cost of making the complete "Digi-Clock" using the components specified is in the region of £40. No doubt many readers will be able to find ways of reducing this cost, but in order to build an all-electronic digital clock the degree of circuit complexity involved, whether using integrated circuits or discrete components, is bound to make this an expensive project. However, one must consider the accuracy and reliability together with long life in comparing the cost with any clock using electro-mechanical devices.—M.A.C.

### Not for Fun?

Sir—Congratulations! You are now printing some really worth while designs in P.E. I am specifically thinking of the "Digital Clock" and the "P.E. Gemini Amplifier", and the forthcoming Sound/Light Controller. We want far more articles of this calibre, not designs for radios, metal detectors, electronic dice, war games,

etc. You should take a poll of readers' wants—I am sure that the majority of them, like me, want to build *useful* things, not toys!

M. J. Clarke,  
London, S.E.1.

I am pleased to learn that you have reacted favourably to some of our recent designs. On the other hand, I cannot agree with you so far as your comments relating to metal detectors, war games, etc. Electronics is a servant to all, and we must be very broad-minded concerning the applications of this technology.

I certainly see no reason why amusements such as "War Games" should not be described. After all, the electronic circuitry involved can be as technically fascinating as that used for more prosaic projects, i.e. commercial computers.—Ed.

### Biased view

Sir—I have been a regular reader of your magazine for many years, and find it very enjoyable to read, and the circuits are really up-to-date. I also attend day-release Technical College and have an Intermediate Certificate in City and Guilds Radio and T.V. Servicing.

Nevertheless, I have come across a problem which no-one can explain, and I can find no book in the whole of Cambridgeshire which can give me an answer, so I am writing to you in the hope that you can help me before I go mad!

In the latest circuits, for example, audio amplifiers, which are d.c. coupled, it often appears that the a.c. signal input is fed straight to the base of the first transistor, without the transistor having any d.c. base bias on it (from resistors, potential dividers, etc.). Therefore is it possible for a transistor to amplify the input a.c. signal without having any base bias?

Also, in a transistor configuration such as the "Super-Alpha pair", the first transistor usually has a base bias resistor, but the second transistor's base is connected straight to the first transistor's emitter.

Even in PRACTICAL ELECTRONICS the text usually just states that the

emitter current of the first transistor is the base current of the second transistor; but how can that be—if there is no base bias resistor on the second transistor, there can be no voltage on the base, hence no current (Ohm's Law).

I must apologise if my query has a very simple explanation, which I should know, but technical college lecturers tend to show you a circuit of a transistor amplifier, and just say, "The signal goes in there, and comes out here," and expect you to accept it!

J. Hammond,  
Great Abington.

When an alternating voltage is present at the collector of a transistor, this consists of an alternating direct voltage. If this is passed to a succeeding stage by way of a capacitor, only the alternating component is passed. If this component is passed to an unbiased transistor, this signal will be rectified and amplified; an audio signal so treated would be distorted.

With d.c. coupled linear amplifier, the d.c. component from the previous stage is so arranged to correctly bias the succeeding transistor so that an exact reproduction of the a.c. component is made.

A "Super-Alpha" pair is a compound of two transistors, d.c. coupled to form, in effect, a high gain transistor. This gain, ideally, approaches the product of the individual transistor gains, hence "Super-Alpha" as a description.

For pulse amplification, such combinations do not need a second transistor base resistor. In a.f. amplifier applications, this resistor is required.—G.G.

### DECIMAL CURRENCY AND P.E.

Readers in the U.K. are probably aware that British currency will be decimalised with effect from February 15, 1971. The following notes are issued for their guidance when writing to Practical Electronics.


1. Cheques and postal orders should show amounts payable in decimal currency.

2. Readers' cheques and postal orders written in £ s d will not be accepted by the banks or Post Office after February 15, 1971.

3. Handwritten cheques of more than £1, which include new pence, should use a hyphen in place of the decimal point (e.g. £7-80, £30-06).

4. Postage rates on and after February 15 will be 2½p second class and 3p first class for up to 4 ounces. Old £ s d stamps used on and after this date must be at the new rate of 6d second class, 7d first class for up to 4 ounces. Readers requiring a reply to correspondence are asked to use the correct postage rate on s.a.e.

### TYPE 13A DOUBLE BEAM OSCILLOSCOPES




An excellent general purpose double beam oscilloscope. T.B. 2 c/s-750KHz. Bandwidth 5-5 MHz. Sensitivity 33mV/cm. Operating voltage 0/110/200/250V a.c. Supplied in excellent working condition. **\$22.10.0.** Carriage 30/-.

### AVO CT471A MULTIMETER

Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12mA to 1.2 Amp. Resistance 12 ohm to 120 mΩ HF, VHF, UHF. Voltage with multiplier 4v to 400v up to 50 Mc/s. 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. **\$55 each.** Carr. 10/-.

### CRYSTAL CALIBRATORS No. 10

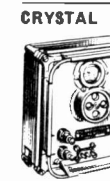


Small portable crystal controlled wavemeter. Size 7 1/2" x 4". Frequency range 500 Kc/s. 10 Mc/s (up to 30 Mc/s on harmonics). Callibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.3A. Excellent condition. **89/6.** Carr. 7/6.

### TAPE CASSETTES

Top quality in plastic library boxes. C60 60 min 8/3 3 for 24/6. C90 90 min 12/6 3 for 36/- C120 120 min 15/- 3 for 43/6. Cassette Head Cleaner 11/3. All Post Extra.

### CLASS D WAVEMETERS




A crystal controlled heterodyne frequency meter covering 1-7.8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. **\$5.19.6.** Carr. 7/6, or brand new **\$7.19.6.** Carr. 7/6.

### B.C. 221 FREQUENCY METERS

latest release 125KHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **\$27.10.0.** each. Carr. 10/-.

### AM/FM SIGNAL GENERATORS




Oscillator Test No. 2. A high quality precision instrument manufactured by Airmeq. Frequency coverage 20-80 Mc/s. AM C.W./P.M. Incorporates precision dial, level meter, precision attenuator 1μV-100μV. Operation from 12V d.c. or 0/110/200/250V a.c. Size 12 x 8 1/2" 9in. Supplied in brand new condition, complete with all connectors fully tested. **\$45.** Carr. 20/-.

### AVO CT.38 ELECTRONIC MULTIMETERS


High quality precision instrument which measures a.c. and d.c. Voltage, Current, Resistance and Power Output Ranges d.c. volts 250mV-10,000V (10 megΩ-110 megΩ input). D.C. current 10μA-25A. Ohms. 0-1,000 megΩ a.c. volt 100mV-250V (with R.F. measuring head up to 250MHz) a.c. current 10μA-25A. Power output 50 mWatts-5 watts. Operation 0/110/200/250V a.c. Supplied in perfect condition complete with circuit lead and R.F. probe. **\$25.** Carr. 13/-.

### ADMIRALTY 62B RECEIVERS



High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 100-300 Kc/s, 5, 45, 450 Kc/s-1.5 Mc/s, 3.9-30.5 Kc/s. I.F. 500/KHz. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.P.O. calibrator for frequency. Operation 150/230V a.c. Size 19 1/2" x 13 1/2" x 10in. Weight 114lb. Offered in good working condition. **\$22.10.0.** Carr. 30/-, With circuit diagrams. Also available B41 L.F. version of above. 15KHz-700KHz. **\$17.10.0.** Carr. 30/-.

### TO-2 PORTABLE OSCILLOSCOPE

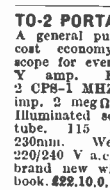

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CF8-1 MHz. Input imp. 2 megΩ 25 P.F. Illuminated scale. 2in. tube. 115 180 230mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **\$22.10.0.** Carr. 10/-.

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS!

### CLEAR PLASTIC METERS

TYPE SW. 100	TYPE S-80
100 x 80 mm	80 mm square fronts
1mA ..... 59/6	50μA ..... 62/6
20V d.c. .... 59/6	100μA ..... 59/6
50V d.c. .... 59/6	500μA ..... 59/6
1A d.c. .... 59/6	1mA ..... 49/6
5A d.c. .... 59/6	20V d.c. .... 49/6
300V a.c. .... 59/6	50V d.c. .... 49/6
7V U meter .... 75/-	1A d.c. .... 49/6

### "SEW" CLEAR PLASTIC METERS

TYPE MR.85P. 4 1/2in. 4 1/2in. fronts.	TYPE MR.38P. 1 1/2" 3/2in square fronts.
10mA ..... 52/-	150mA ..... 27/6
50mA ..... 52/-	200mA ..... 27/6
100mA ..... 52/-	300mA ..... 27/6
500mA ..... 52/-	500mA ..... 27/6
1A ..... 52/-	750mA ..... 27/6
5A ..... 52/-	1A ..... 27/6
15A ..... 52/-	2A ..... 27/6
30A ..... 52/-	5A ..... 27/6
20V d.c. .... 52/-	10A ..... 27/6
50V d.c. .... 52/-	15V d.c. .... 27/6
150V d.c. .... 52/-	15V d.c. .... 27/6
300V d.c. .... 52/-	20V d.c. .... 27/6
15V a.c.* ..... 52/-	3V d.c. .... 27/6
300V a.c.* ..... 52/-	10V d.c. .... 27/6
8 Meter 1mA ..... 57/6	15V d.c. .... 27/6
VU meter ..... 72/-	20V d.c. .... 27/6
1A a.c.* ..... 52/-	100V d.c. .... 27/6
5A a.c.* ..... 52/-	150V d.c. .... 27/6
10A a.c.* ..... 52/-	300V d.c. .... 27/6
20A a.c.* ..... 52/-	500V a.c. .... 27/6
30A a.c.* ..... 52/-	8 Meter 1mA ..... 32/-
	VU meter ..... 42/-

### TYPE MR.62P. 2 1/2in square fronts.

50μA ..... 40/-	5A ..... 30/-
500-500μA ..... 42/-	10V d.c. .... 30/-
100μA ..... 42/-	20V d.c. .... 30/-
100-100μA ..... 42/-	30V d.c. .... 30/-
200μA ..... 42/-	50V d.c. .... 30/-
500μA ..... 42/-	100V d.c. .... 30/-
600-500μA ..... 42/-	150V d.c. .... 30/-
1mA ..... 42/-	300V d.c. .... 30/-
2mA ..... 42/-	500V a.c. .... 30/-
10mA ..... 42/-	8 Meter 1mA ..... 32/-
20mA ..... 42/-	VU meter ..... 42/-
50mA ..... 42/-	
100mA ..... 42/-	


### "SEW" BAKELITE PANEL METERS

#### TYPE MR.65P. 3 1/2in square fronts.

500μA ..... 35/-	5A ..... 30/-
1A ..... 35/-	10V d.c. .... 30/-
15A ..... 35/-	20V d.c. .... 30/-
30A ..... 35/-	30V d.c. .... 30/-
5V d.c. .... 35/-	50V d.c. .... 30/-
10V d.c. .... 35/-	100V d.c. .... 30/-
20V d.c. .... 35/-	150V d.c. .... 30/-
50V d.c. .... 35/-	300V d.c. .... 30/-
150V d.c. .... 35/-	500V a.c. .... 30/-
300V d.c. .... 35/-	8 Meter 1mA ..... 37/6
500V a.c. .... 35/-	VU meter ..... 45/-
1A a.c.* ..... 35/-	1A a.c.* ..... 30/-
5A a.c.* ..... 35/-	5A a.c.* ..... 30/-
10A a.c.* ..... 35/-	10A a.c.* ..... 30/-
20A a.c.* ..... 35/-	20A a.c.* ..... 30/-
30A a.c.* ..... 35/-	30A a.c.* ..... 30/-
50V a.c.* ..... 35/-	
VU meter ..... 65/-	

### \* MOVING IRON — ALL OTHERS MOVING COIL

Please add postage

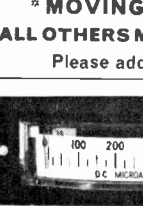

25μA ..... 70/-	500μA ..... 52/-
50μA ..... 47/6	1mA ..... 47/6
500-500μA ..... 45/-	10mA ..... 47/6
100μA ..... 45/-	300V a.c. .... 47/6
100-100μA ..... 45/-	200μA ..... 55/-
1mA ..... 35/-	5A ..... 35/-
1-10mA ..... 35/-	10A ..... 35/-
5mA ..... 35/-	50A ..... 35/-
10mA ..... 35/-	100mA ..... 35/-
50mA ..... 35/-	
100mA ..... 35/-	

### EDGWISSE METERS


Type PE.70. 3 1/2" 3 1/2" x 1 1/2" 3 1/2" x 2 1/2" deep.

### POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, 1in. dia. shafts. Bulk quantities available.

25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms, 14.6. P. & P. 1.6.
50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, 21. P. & P. 1.6.
100 WATT. 1/15/10/25/50/100/250/500/1,000 or 2,500 ohms, 27/6. P. & P. 1.6.

### FTC-401 TRANSISTOR TESTER




Full capabilities for measuring A, B and ICO, *npn* or *ppn*. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. **\$6.19.6.** P. & P. 3/-.

### MARCONI TF142E DISTORTION FACTOR METERS

Excellent condition. Fully tested. **\$20.** Carr. 15/-.
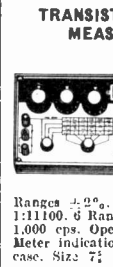
### TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE




A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-111 megΩ. 6 Ranges -1.1% L. 1μH - 1.11 HENRY. 8 Ranges -2% C. 10pF - 1.110 mF d. 6 Ranges ±2%. TURNS RATIO 1:1/1000-1:1100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts, 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2" 3" 2in. **\$20.** P. & P. 5/-.

### COSSOR 1049 DOUBLE BEAM OSCILLOSCOPES

D.c. coupled. Band width 1Kc/s. Perfect order. **\$25.** Carr. 30/-.

### TE-20D RF SIGNAL GENERATOR



Accurate wide range signal generator covering 120Kc/s to 600Mc/s on 6 bands. Directly calibrated. Variable RF attenuator, audio output. Xtal coupled for calibration. 200/240V a.c. Size 140 215 170mm. Brand new with instructions. **\$15.** Carr. 7/6.

### LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS

Frequency 0-20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V a.c. Supplied in perfect order. **\$12.10.0.** Carr. 10/-.

### TE22 SINE SQUARE WAVE AUDIO GENERATORS




Since 20c/s to 200 Kc/s on 4 bands. Square: 20c/s to 30 Kc/s. Output impedance 5,000 ohms. For calibration. 200/240V a.c. Supplied brand new and guaranteed with instructions manual and leads. **\$16.10.0.** Carr. 7/6.

### MARCONI TF85 VIDEO OSCILLATORS

0-3MHz. Sine Square Wave. **\$45.** Carr. 20/-.
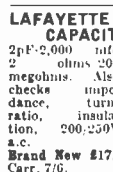
### LAFAYETTE TE46 RESISTANCE CAPACITY ANALYSER



2pF-5,000 mfd 5 mA. 200 megohms. Also checks impedance, turns ratio, insulation. 200-250V a.c. Brand New **\$17.10.0.** Carr. 7/6.

### 270 500 MICROAMP METER

Incorporated in Radio Attitude Indicator 1D-14A.PN. Ideal for Rev. counter, etc. 15/6. P. & P. 3/-.

### ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons.

#### J1B. AUDIO SIGNAL GENERATOR.

15 c/s to 50 Kc/s. Sine wave. Output 600 ohms or 5 ohms. **\$30.0.0.**

#### VM79. UHF MILLIVOLT METER.

100 Kc/s to 1,000 Mc/s. a.c. 10 mV to 3V. D.c. 10 mV to 3V. Current 0.01 μA to 0.3 mA. Resistance 1 ohm to 10 megohms. **\$25.0.0.**

### TT15 TRANSISTOR TESTER.

Full range of facilities for testing PNP or NPN transistors in or out of circuit. **\$37.10.0.** Carriage 10/- per item.

### MARCONI TF195M BEAT FREQUENCY OSCILLATORS

0-40KHz. **\$20.** Carr. 30/-.

G. W. SMITH & CO (RADIO) LTD.  
Also see next two pages

# SEMI-CONDUCTORS & VALVES

BRAND NEW & FULLY GUARANTEED

TRANSISTORS				VALVES			
1N914	1/4	AC128	5/-	B8Y38	4/-	11L4	2/6
1N4001	1/4	AC154	3/-	B8Y39	4/6	1R5	7/-
1N4002	1/4	AC176	5/-	B8Y61	6/6	1S5	5/-
1N4003	2/-	AC187	6/-	B8Y66	6/6	2A2	14/6
1N4004	2/-	AC190	6/-	B8Y95A	3/-	3U4	6/-
1N4005	2/4	AC197	6/-	BY100	3/6	3U5	9/6
1N4006	3/4	AC198	5/-	BY124	3/6	3OA2	6/6
1N4007	4/4	AC199	5/-	BY126	3/-	3OB2	6/6
1N4148	4/4	AC200	4/6	BY127	4/6	3OZ4	6/6
1N5054	4/6	AC221	4/6	BY210	8/6	4A5	2/6
3C301	4/4	AC222	3/6	BY211	7/6	2D21	6/6
2C302	4/4	AC223	6/-	BY212	6/6	6X4	9/6
2C303	5/4	AC240	3/-	BY213	5/6	3A4	7/6
2C306	7/6	AD140	10/-	MJ480	19/6	3V4	8/6
2C308	6/6	AD149	10/-	MJ481	26/6	3V5	11/6
2C309	6/6	AD161	7/6	MFF102	8/6	5U4	6/6
2C371	4/6	AD162	7/6	MFF103	7/6	6X4	9/6
3C374	5/6	AF114	6/6	MFF104	6/6	6Y3	6/6
2C381	5/4	AF127	6/6	MFF105	8/6	5Z4G	7/6
2N696	3/6	AF116	6/6	NKT213	5/-	6J0L2	15/6
2N697	3/6	AF117	5/6	NKT214	3/6	6AC7	4/6
2N698	3/6	AF118	12/6	NKT216	7/6	6AG7	7/6
2N706	2/4	AF124	5/6	NKT217	8/6	6AU6	6/6
2N708	4/6	AF129	3/6	NKT221	4/6	6B6E	11/6
2N916	4/6	AF139	6/6	NKT271	5/6	6AQ5	6/6
2N918	7/6	AF178	6/6	NKT272	5/6	6A86	6/6
2N929	4/6	AF180	10/6	NKT274	4/6	6AT6	5/6
2N930	5/6	AF181	8/6	NKT275	5/6	6AU6	6/6
2N1131	6/6	AF186	8/6	NKT278	5/6	6BA6	6/6
2N1132	6/6	AF239	8/6	NKT279	5/6	6B6E	6/6
2N1202	4/6	AF238	6/6	NKT403	15/6	6BE6	5/6
2N1303	4/6	AS727	6/6	NKT404	12/6	6BH6	6/6
2N1304	5/6	AS728	5/6	NKT405	15/6	6BJ6	6/6
2N1305	5/6	AS217	8/6	NKT773	7/6	6BQ7A	7/6
2N1306	5/6	AUY10	19/6	NKT10430	7/6	6BR7	17/6
2N1307	6/6	BAY31	1/6	0A5	3/6	6BW6	16/6
2N1308	6/6	BC107	2/6	0A19	5/6	6BW7	13/6
2N1309	5/6	BC108	2/6	0A17	5/6	6BZ6	6/6
2N1613	4/6	BC109	2/6	0A70	2/6	6C4	6/6
2N1711	5/6	BC113	5/6	0A79	2/6	6CA6	23/6
2N1889	6/6	BC116	8/6	0A81	2/6	6CL6	19/6
2N1890	10/6	BC125	11/6	0A85	2/6	6CW4	12/6
2N2147	15/6	BC126	11/6	0A80	2/6	6F1	12/6
2N2160	12/6	BC147	10/6	0A82	12/6	6F6G	5/6
2N2193	9/6	BC148	2/6	0A85	1/6	6F13	7/6
2N2217	5/6	BC148	2/6	0A200	1/6	6F42	12/6
2N2218	6/6	BC167	3/6	0A202	2/6	6F4	11/6
2N2219	6/6	BC172	3/6	0A210	3/6	6F18	8/6
2N2369	3/6	BC177	7/6	0C19	7/6	6F23	15/6
2N2369	4/6	BC186	7/6	0C20	19/6	6H6	3/6
2N2484	4/6	BC182L	4/6	0C23	10/6	6I4	9/6
2N2613	7/6	BC184L	4/6	0C24	10/6	6J5	4/6
2N2646	10/6	BCY30	5/6	0C25	7/6	6J6GT	11/6
2N2904	6/6	BCY31	6/6	0C26	6/6	6J7	8/6
2N2923	3/6	BCY32	10/6	0C28	12/6	6K8G	12/6
2N2924	3/6	BCY33	4/6	0C35	12/6	6L6GT	12/6
2N2925	3/6	BCY34	5/6	0C38	12/6	6LD20	6/6
2N2926	2/6	BCY38	6/6	0C41	5/6	6S47	7/6
2N2926V	2/6	BCY38	4/6	0C42	3/6	6S67	7/6
2N3053	5/6	BCY71	6/6	0C44	3/6	6S77	7/6
2N3064	10/6	BCY72	3/6	0C45	3/6	6SK7	6/6
2N3065	15/6	BCZ11	7/6	0C46	3/6	6SL7	6/6
2N3391A	6/6	BD121	13/6	0C70	2/6	6SN7	5/6
2N3416	7/6	BD123	16/6	0C71	6/6	6S7	8/6
2N3470	2/6	BD124	16/6	0C72	5/6	6U4	12/6
2N3702	17/6	BF115	5/6	0C73	6/6	6V6G	6/6
2N3703	2/6	BF117	9/6	0C74	6/6	6V6GT	6/6
2N3704	3/6	BF167	5/6	0C75	5/6	6X4	5/6
2N3705	3/6	BF173	6/6	0C76	5/6	6X6G	5/6
2N3706	4/6	BF180	7/6	0C77	8/6	6X6GT	5/6
2N3707	3/6	BF181	6/6	0C78	9/6	6Y3	10/6
2N3708	3/6	BF184	6/6	0C81	5/6	10P1	18/6
2N3709	2/6	BF184	6/6	0C81D	4/6	10P13	14/6
2N3710	2/6	BF185	5/6	0C83	5/6	10P14	20/6
2N3711	2/6	BF194	3/6	0C84	5/6	12A7	5/6
2N3819	7/6	BF195	3/6	0C139	9/6	12A7T	4/6
2N3903	7/6	BF200	7/6	0C140	7/6	12A7E	5/6
2N3904	7/6	BF224	6/6	0C169	6/6	12AX7	6/6
2N3906	7/6	BF224	6/6	0C170	6/6	12AV6	6/6
2N3906	7/6	BF244	6/6	0C171	6/6	12BA6	6/6
2N4058	3/6	BFX12	4/6	0C200	12/6	12BE6	6/6
2N4059	3/6	BFX13	4/6	0C201	9/6	12BH7	6/6
2N4061	3/6	BFX29	6/6	0C202	12/6	19AQ5	6/6
2N4062	4/6	BFX30	6/6	0C203	7/6	20D1	9/6
2N4286	3/6	BFX44	7/6	0C205	7/6	20F2	15/6
2N4287	3/6	BFX45	8/6	0C205	12/6	20L1	20/6
2N4288	3/6	BFX86	6/6	0C207	15/6	20L2	10/6
2N4289	3/6	BFX87	6/6	0C211	18/6	20P3	12/6
2N4290	3/6	BFX88	5/6	0RP12	10/6	20P4	12/6
2N4291	3/6	BFY18	5/6	0RP90	8/6	20P5	20/6
2N4292	3/6	BFY20	12/6	0P40A	2/6		
2N5354	5/6	BFY21	12/6	PL4001	2/6		
2N5355	5/6	BFY22	12/6	PL4002	3/6		
28102	5/6	BFY62	4/6	PL4003	3/6		
28103	7/6	BFY90	18/6	PL4004	3/6		
28104	7/6	B8X19	3/6	PL4005	3/6		
40250	10/6	B8X20	3/6	PL4006	4/6		
40361	11/6	B8X21	7/6	PL4007	4/6		
40362	11/6	TS43	3/6	PL4008	4/6		
AC107	7/6	B8Y26	3/6	TR844	2/6		
AC126	5/6	B8Y27	4/6	TR845	2/6		
AC127	5/6	B8Y28	3/6	TS46	3/6		

THYRISTORS					
PIV	50	100	200	350	400
1A	5/-	5/6	7/6	8/-	9/-
3A	8/-	7/6	8/-	9/-	10/-
5A	11/-	11/-	13/-	14/-	15/-
10A	—	—	—	50/-	55/-

# HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



# GARRARD

FULL CURRENT RANGE OFFERED, BRAND NEW AT FANTASTIC SAVINGS


2025T/C stereo	£8.17.6	SL72B	£24.19.6
40 MK11 stereo	£8.8.0	AF76	£22.10.0
3000 stereo	£9.19.6	SL75	£25.19.6
SP25 MK111	£11.15.0	SL95B	£37.10.0
SL55	£11.12.8	A70/11	£11.19.6
BL65B	£14.19.6	401	£25. 0.0

Carriage 7/6 extra each item.



- TEAK PLINTHS AND PERSEK COVERS**
- For SP25, SL65, SL55, 3000, 2025T/C, 2025, 1000. £3.19.6
  - For AP75, SL75, SL95. £5.19.6
  - For SP25 etc. to operate with lid in place £5.19.6
- Carriage 7/6 extra each type. Full range of Garrard accessories available.

## TELETON SPECIAL OFFER!

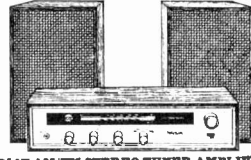

**CR10 AM/FM STEREO TUNER AMPLIFIER WITH MATCHING PAIR SALOOS SPEAKER SYSTEMS**

Output 4 watts per channel. Excellent reception AFC, built-in MPX, Cer/XTAL input. Total L £50.5.0. O.T.R PRICE £29.19.0, Carr. 12/6.

Also available with Garrard 2025T/C Record Changer, Plinth, cover and stereo cartridge. Ready wired. £45. Carr. 20/6.

## TELETON SAQ203E STEREO AMPLIFIER



Solid state, 10W per channel music power, 6W r.m.s. Inputs for mag, ceramic, tuner, aux.

SPECIAL PRICE £20. Carr. 7/6.

## HOSIDEN DH-02S STEREO HEADPHONES



Wonderful value and excellent sound. Impedance combined. Adjustable head-band, 8 ohm impedance. 20-12,000 cps. Complete with lead and stereo jack plug. ONLY 2/6.

## HOSIDEN DH-08S DE LUXE STEREO HEADPHONES



Features unique mechanical 2-way units and fitted adjustable level controls. 8 ohm impedance. 20-20,000cps. Complete with spring lead & stereo jack plug £19.19.6. P. & P. 2/6.

## SPECIAL OFFERS!

Garrard SP25/III fitted Goldring G800 cartridge and wooden plinth and plastic cover. Ready wired. Total list price £36. OUR PRICE £22.10.0, Carr. 10/6. GOLDRING G800 fitted Goldring G800 cartridge complete with de luxe base and cover. Total list price £50.16.0. OUR PRICE £29. Carr. 20/6.

## SINCLAIR EQUIPMENT


Project 60. Package offers. 2 x Z30 amplifier, stereo 60 pre-amp. P25 power supply. £19.0.0, Carr. 7/6. Or with P26 power supply, £21. Carr. 7/6. 2 x Z50 amplifier, stereo 60 pre-amp. P23 power supply. £21.10.0, Carr. 7/6. Transformer for P28, 50/6 extra. Add to any and £16 for a pair of Q16 speakers. Project 60 FM Tuner £20.19.6, Carr. 7/6. All other Sinclair products in stock. 2,000 amplifier, £22, Carr. 7/6. 3000 Amplifier £36, Carr. 7/6. Neoteric amplifier £46, Carr. 7/6.

## ★ TRANSISTORISED FM TUNER ★

6 TRANSISTOR HIGH QUALITY TUNER, SIZE ONLY 6" x 4" x 2 1/2". 5 I.P. stages. Double tuned discriminator. Amp. output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready for use. Fantastic value for money. £6.7.6. P. & P. 2/6. Stereo multiplex adaptors 99/6.
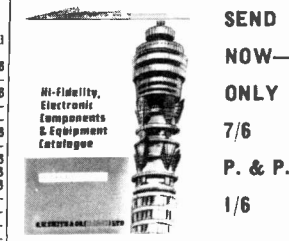
# Latest Catalogue

Our latest edition giving full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT AND COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 10/-, 248 pages, fully illustrated and detailing thousands of items at bargain prices.



SEND

NOW—

ONLY

7/6

P. & P.

1/6

**ZENER DIODES**  
400mw. (3.3 to 33v) 3/-  
1.5 watt (2.4 to 200v) 4/-  
10 watt (3.9 to 100v) 5/-

**SEND SAE FOR FULL LISTS!**

**DISCOUNTS**  
10% on 12 or more  
one type.  
15% on 25+ any one type.  
Large quantity discounts on application Postage—  
Semi  
Conductors  
Valves 3/-

**INTEGRATED CIRCUITS**  
L900 9/9; L914 9/9; L923 12/6; IC-10 50/-; SL403 42/6; MC1303 52/6; MC1304 55/-; PA246 52/6; CA3005 25/6; CA3011 10/6; CA3052 6/6; FCH131 10/-; FCH 161 10/-; FJH141 10/-; FJH171 10/-; FJH181 10/-; FJH221 10/-; FJH231 10/-; FJH241 10/-; FJH251 10/-; FJH261 10/-; FJH271 10/-; FJH281 10/-; FJH291 10/-; FJH301 10/-;

## AMERICAN TAPE

First grade quality American tapes. Brand new Discount on quantities.  
3in. 25ft. L.P. acetate ..... 3/6  
3in. 50ft. L.P. mylar ..... 10/6  
5in. 50ft. std. plastic ..... 9/6  
15% on 10/-  
5in. 1,200ft. D.P. mylar ..... 18/6  
5in. 1,200ft. L.P. acetate ..... 12/6  
5in. 1,800ft. D.P. mylar ..... 22/6  
5in. 1,200ft. L.P. mylar ..... 39/6  
7in. 1,200ft. std. acetate ..... 12/6  
7in. 1,800ft. L.P. acetate ..... 15/6  
7in. 1,800ft. L.P. mylar ..... 20/6  
7in. 2,400ft. D.P. mylar ..... 28/6  
7in. 3,600ft. T.P. mylar ..... 45/6  
Postage 2/- Over £3 post paid.

**RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES**  
5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2 $\mu$ sec to 100msec/cm. Supplied complete with all accessories and instructions. £97. Carr. paid.




**MARCONI CT44/TF956 AF ABSORPTION WATTMETER**

1  $\mu$ watt to 6 watts.  
£20. Carr. 20/-.

**TE111. DECADE RESISTANCE ATTENUATOR**  
Variable range 0-111dB. Connections. Balanced T and Bridge T. Impedance 600  $\Omega$  range (0.1dB + 10) + (1dB  $\times$  10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200KHz. Accuracy: 0.05dB. + Indication dB  $\times$  0.01. Maximum input less than 4W (50V). Built in 400  $\Omega$  load resistance with internal/external switch. Brand new £27.10.0. P. & P. 6/-.



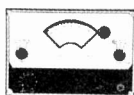**BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR**



Attractive two-tone case 7 1/2in  $\times$  5in 2 1/2in.  
Price £17.10.0 Carr. 3/6.



**TE-16A Transistorised Signal Generator.** 5 ranges 400 kHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V batteries. Wide, easy to read scale. 800 kHz modulation. 5:1  $\times$  3 1/2. Complete with instructions and leads. £7.19.6. P. & P. 4/-.

**BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR**



New high quality portable instrument. Sine/Hz to 100KHz. Square 20Hz to 20KHz. Output max. +10dB (10K $\Omega$ ). Operation 220/240V a.c. Size 215mm  $\times$  150mm  $\times$  120mm.  
Price £27.10.0. Carr. 3/6.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER**



10 meg. input 10 ranges: 0.1 / 0.03 / .1 / .3 / 1 / 3 / 10 / 30 / 100 / 300 V. R.M.S. 4c/s. -1.2Mc/s. Decibels -40 to +60dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.10.0. Carr. 5/-.

**TE-65 VALVE VOLTMETER**



High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. £17.10.0. P. & P. 6/-. Additional Probes available: R.F. £2/6. H.V. 50/-.


**AUTO TRANSFORMERS**

0/115/230V. Step up or step down. Fully abrouded.  
150 W. £2.7.6. P. & P. 3/6  
300 W. £3.5.0. P. & P. 4/6  
500 W. £4.19.6. P. & P. 6/6  
1,000 W. £7.5.0. P. & P. 7/6  
1,500 W. £8.19.6. P. & P. 8/6

**SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS**

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V.  
Model MB2305 5A 68  $\times$  46 43mm. £8.7.6. Model MB2310 10A 90  $\times$  68  $\times$  60mm. £11.19.6. Postage 2/6.

**MULTIMETERS for EVERY purpose!**

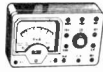

**TECH PT-34.** 1,000 O.P.V. 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. d.c. 0/100K. 30/6. P. & P. 2/6.



**MODEL TE-200.** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50/500/500mA. 0/60K/6 meg. -20 to  $\times$  62dB. 75/- P. & P. 3/-.



**MODEL 500.** 30,000 O.P.V. with overload protection, mirror scale 0/1.5/12.5/100/250/500/1,000V d.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/50  $\mu$ A/5/50/500 mA. 12 amp. d.c. 0/60K/6 Meg./60 Meg.  $\Omega$ . £8.17.6. Post paid.



**MODEL TE-70.** 30,000 O.P.V. 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30  $\mu$ A/3/30/300mA. 0/16K/160K/1.6M/16 meg. £5.10.0. P. & P. 3/-.



**TMK MODEL TW-50K.** 46 ranges, mirror scale. 50K/Volt d.c. 5K/Volt a.c. D.c. volts: 0.125, 0.25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50  $\mu$ A, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +81.5dB. £8.17.6. P. & P. 6/6.




**TE-900 20,000 O/VOLT GIANT MULTIMETER.** Mirror scale and overload protection. 6in full view meter, 2 colour scale. 0/2.5/10/25/100/1,000/5,000V a.c. 0/25/125/100/500/1,000/5,000V d.c. 0/50  $\mu$ A/1/10/100/500mA/10A d.c. 0.2K/200K/20 meg. ohm. £15.0.0. P. & P. 5/-.



**MODEL 5025.** 57 ranges, giant 5 1/2in meter, polarity reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. volts: 0.125, 0.25, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50  $\mu$ A, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 2K, 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +86dB. £12.10.0. P. & P. 3/6.

**AVOMETER MOVEMENTS**

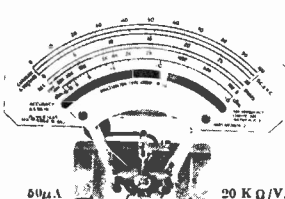

Spare movements for Model 8 or 9. (Fitted with Model 9 scale) or basis for any multimeter. Brand New Boxed 69/6. P. & P. 3/6.

**HOMER TE.10A.** 20K  $\Omega$ /Volt 5/25/50/250/500/2,500V a.c. 10/50/100/500/1,000V a.c. 0/50  $\mu$ A/2-5mA 250mA d.c. 0/6K/6 meg. ohm. -20 to +22dB. 10-0, 100 mfd. 0-100-0-1 mfd. 69/6. P. & P. 3/-.



**MODEL TE-300.** 30,000 O.P.V. Mirror scale, overload protection 0/0-6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30  $\mu$ A 6mA / 50mA / 300mA/600mA. 0/8K/80K/800K/8 meg. -20 to +63dB. £5.19.6. P. & P. 3/-.



**MODEL TE 90.** 20,000 O.P.V. 0/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V d.c. 0-5mA. 5/50/500mA. 0/6K/60K/600K/6 Meg. £4.17.6. P. & P. 3/-.



**MODEL TE-60.** 50,000 O.P.V. Mirror scale, overload protection. 003/13/60/300/600/1,200V d.c. 0/6/30/120/300/1,200V a.c. 0/30  $\mu$ A/3/30/300mA. 0/16K/160K/1.6/16 meg. -20 to +63dB. £7.10.0. P. & P. 3/-.



**TMK MODEL TW-200CB.** Features Resettable Overload Button. Sensitivity: 20K  $\Omega$ /Volt d.c. 5K  $\Omega$ /Volt a.c. D.c. volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 0-2.5, 10, 50, 250, 1,000V. D.c. currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 meg. Decibels: -20 to +52dB. £11.10.0. P. & P. 3/6.



**MODEL AS-100D.** 100K  $\Omega$ /Volt. 5in, mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10  $\mu$ A/60/300mA/12V. 0/2K/200K/2M/200M. -20 to +17dB. £12.10.0. P. & P. 3/6.



**TMK LAB TESTER.** 100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5/Volt a.c. D.c. volts: 0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10/100  $\mu$ A, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg., 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle, size 7 1/2in  $\times$  9 1/2in  $\times$  3 1/2in. £18.18.0. P. & P. 6/-.



**SKYWOOD SW-500**



50 K  $\Omega$ /Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20  $\mu$ A/60/600mA. Resistance 10K/100 K/1Meg/10 Meg. Decibels -20 to +57dB £7.10.0. P. & P. 3/-.

**270° WIDE ANGLE**

**1mA METERS**  
MW1-6 60mm square £3.19.6. MW1-8 80mm square £4.19.6. P. & P. extra.



**"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS**

Excellent quality . Low price . Immediate delivery

MODEL S-260 General Purpose Bench Mounting	MODEL S-260 B Panel Mounting	
1A £5.10.0	1A £5.10.0	
2.5A £8.15.0	2.5A £6.12.6	
5A £9.15.0	Please add postage	
10A £14.10.0	ALL MODELS INPUT 230 VOLTS. 50/60 CYCLES, OUTPUT VARIABLE 0-250 VOLTS	
12A £21.0.0	Special discounts for quantity	
20A £27.0.0		




**UNR-30 RECEIVER**  
4 Bands covering 500KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15.15.0. Carr. 7/6.

**WS85 TRANSCEIVERS**  
Large quantity available for EXPORT! Excellent condition. Enquiries invited.



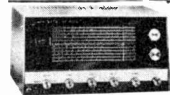**UR-1A SOLID STATE COMMUNICATION RECEIVER**  
4 Bands covering 50KHz-30MHz. FET, 8 Meter, Variable BFO for 8BB. Built in Speaker, Telescopic Aerial, Bandspread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in  $\times$  4 1/2in  $\times$  7 1/2in. Brand new with instructions. £25. Carr. 7/6.



**LAFAYETTE HA-600 RECEIVER**

General coverage 150-400KHz, 500KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Bandspread, 32 Gain. 15 1/2in  $\times$  9 1/2in  $\times$  8 1/2in. 220/240V a.c. or 12V d.c. Brand new with instructions. £45. Carr. 10/-.

**LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER**



3-6, 4, 7-7.3, 14-14.35, 21-21.45, 28-29.7, 50-64MHz. Dual conversion, 2 mech. filters, product detector, variable BFO, 8 Meter, 100KHz calibrator. 220/240V a.c. or 12V d.c. 16 1/2in  $\times$  9 1/2in  $\times$  8 1/2in. 18lb. Brand new with instructions. £27.10.0. Carr. paid (100KHz Crystal 39/6 extra).



**LAFAYETTE PFS0 VHF FM RECEIVER**

Solid State. 152-174MHz. Fully tuneable or crystal controlled (not supplied). Built in Speaker, Squelch and Volume Controls. 220/240V a.c. or 12V d.c. Brand new with instructions. £37.10.0. Carr. 10/-.

**FULL RANGE OF TRIO EQUIPMENT**

**VOLTAGE STABILISER TRANSFORMERS**  
180-260V input. Output 230V. Available 150W or 225W. £12.10.0. Carr. 5/-.

**EDDYSTONE VHF RECEIVERS MODEL 770R.** 29-165 Mc/s. Excellent condition. £150.

**INTERCOM/BABY SITTER**

Transistorised In-home, Ideal for home/office/workshop, etc. 2-way buzzer call system. For desk or wall mounting. Supplied complete with connecting wire and batteries. 2 station 55/9.6. P. & P. 2/6. 4 station £6.12.6. P. & P. 5/-.

**TRANSISTORISED TWO-WAY TELEPHONE INTERCOM**

Operative over amazingly long distances. Separate call and press to talk buttons, 2-wire connection. 1000's of applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. £6.19.6. P. & P. 3/6.



**G.W.SMITH & CO. (RADIO) LTD**

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
3 Lisle Street, London, W.C.2 Tel: 01-437 8204  
34 Lisle Street, London, W.C.2 Tel: 01-437 9155  
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to -  
147, Church Street,  
London, W.2  
Tel: 01-262 6562  
(Trade supplied)

## 20 Solid State Projects for the Car and Garage

R. M. Marston

Eighteen of the twenty projects described are intended for use in the car. These range from hazard warnings such as ice and overheating, to those that ease the driver's task and allow him to concentrate on driving: for example the Anti-sleep alarm, the wind-screen wiper controller and the automatic sidelight switch. Clear descriptions of the operation and construction of each circuit together with the detailed lists of components, make each project simple, and the book will be useful to the car owner, student and electrical apprentice.

122 pages illustrated 1970  
 0 592 02866 6 case £1.80 (36s)  
 0 592 00048 6 limp £1.20 (24s)

Available from leading booksellers or

**The Butterworth Group**  
 88 Kingsway London WC2B 6AB



## 4-STATION INTERCOM



£6.15.0

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 7/6.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.19.0. P. & P. 9/- extra.

## INTERCOM/BABY ALARM



3 Gns

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 2/6. P. & P. 4/6.

### Transistor TELEPHONE AMPLIFIER




59/6

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 2/6 extra. P. & P. 3/6. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/12)  
 189 KENSINGTON HIGH STREET, LONDON, W.8

## NEW Mk. 2 Psychedelic Lighting Unit

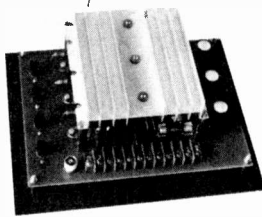

This new psychedelic lighting unit offers even greater sensitivity than our original unit, requiring typically only 1V r.m.s. for full drive. It features higher input impedance circuitry for less loading of speaker lines and is now manufactured on professional fibre-glass printed-circuit board material.

Drive voltage is derived directly from amplifier output or across speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

Uses latest full-wave triac circuitry and incorporates signal input level and minimum ambient light level controls. Will drive up to 1.5kW per channel at 240V a.c. Complete printed-circuit board assembly built and tested. Size 8 1/2 in. x 6 1/2 in. x 3 1/2 in. £17.50 net plus 50p carriage

## INSTRUMENTAL AUDIO EFFECTS NOW AVAILABLE IN KIT FORM

CREATE "PHASE" on your tape recordings, records, etc., unique electronic circuitry enables you to create "phase" at the turn of a knob. Just connect between pre-amp. and power-amp.

This is not waa-waa, white-noise or swish but genuine phase-shift created electronically. Input and output impedances match to 10-50kΩ. Operates from 9V battery. Complete printed-circuit assembly, built and tested. Size 4 in. x 2 1/2 in. x 1 1/2 in. £3.25 plus 10p carriage.

OR £2.50 plus 10p carriage in KIT FORM

**SUPER "FUZZ" UNIT.** Connects between guitar and amplifier. Operates from 9V battery. Complete printed-circuit board assembly, built and tested. Size 3 1/2 in. x 2 1/2 in. x 1 1/2 in. £3.25 plus 10p carriage.


OR £2.50 plus 10p carriage in KIT FORM

Kinetic Lighting Effects units and 100W. Mixer/Amplifier as advertised Dec. and Jan. P.E. still available. Please send 5p in stamps for further details.

MAIL ORDER ONLY  
 S.a.e. for all enquiries

**Dabar Electronic Products**  
 98a Lichfield Street, Walsall, Staffs.
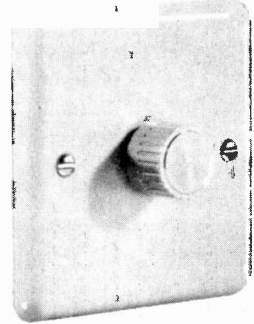
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3. 4. 0d plus 1/6d post and packing Kit Form: £2. 14. 0d plus 1/6d post and packing Please send C.W.O. to:-

**DEXTER & COMPANY**  
 1 ULVER HOUSE, 19, KING STREET,  
 CHESTER CH1 2AH. Tel: 0244-25883.  
 As supplied to H.M. Government Departments,  
 Hospitals, Local Authorities, etc.

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element-grid reflectors.

Loft Mounting Arrays, 7 element, 45-; 11 element, 52.6; 14 element, 60-; 18 element, 70-; Wall Mounting with Cranked Arm, 7 element, 65-; 11 element, 75-; 14 element, 82.6; 18 element, 90-; Chimney Mounting Arrays Complete, 7 element, 80-; 11 element, 87.6; 14 element, 95-; 18 element, 105-. Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 18 yd. King Teleboosters—Labgear U.H.F. Boosters from 75-. Belling Lee "Concord" all Band V.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8-. Accessories 3-. C.W.O. or C.O.D.

## BBC. ITV. FM AERIALS



B.B.C. (Band D), Loft, 25-; Wall S.D. 32.6. "H" array, 60-; I.T.V. (Band 3), 5 element loft array, 45-; 7 element, 55-; Wall mounting 5 element, 65-; Combined BBC ITV loft 1 + 5; 55-; 1 + 7.67.6. Wall mounting 1 + 5. 77.6. Chimney mounting 1 + 5. 90-. Pre-amps from 75-.

Combined BBC/ITV BBC2 Aerials, 1 + 5 + 9; 80-; 1 + 5 + 14. 90-; 1 + 7 + 14. 100-. Available loft only.

F.M. Radio Loft S.D. 19.6. "H", 38.6. 3 element array, 57.6. Standard co-axial cable, 1 - yd. Coax plugs, 1.8. Outlet boxes, 6-. Diplexer crossover boxes, 17.6. p.p. Aerials, 8-; accessories, 3-. C.W.O. or C.O.D. (min. C.O.D. charge 3.6.) 1- for fully illustrated Lists.

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS (Dept. P.E.)**  
 40-41 Monarch Parade  
 London Road, Mitcham, Surrey  
 01-648 4884



# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

AC107	3/-	OC170	4/6
AC126	2/6	OC171	4/6
AC127	3/6	OC200	5/-
AC128	2/6	OC201	5/-
AC176	5/-	2G301	2/6
AC177	3/-	2G303	2/6
AF239	7/6	2N711	4/-
AF186	10/-	2N1302-3	4/-
AF139	7/6	2N1304-5	5/-
BC154	5/-	2N1306-7	6/-
BC171 = BC107	2/6	2N1308-9	7/-
BC172 = BC108	2/6	2N3819FET	9/-
BF194	3/-		
BF274	3/-		
BFY50	4/-		
BSY25	7/6		
BSY26	2/6		
BSY27	2/6		
BSY28	2/6		
BSY29	2/6		
BSY95A	3/-		
OC41	2/6		
OC44	2/6		
OC45	2/6		
OC71	2/6		
OC72	2/6		
OC73	3/6		
OC81	2/6		
OC81D	2/6		
OC83	4/-		
OC139	2/6		
OC140	3/6		

### Power Transistors

OC20	10/-
OC23	6/-
OC25	5/-
OC26	5/-
OC28	6/-
OC35	6/-
OC36	5/6
AD149	6/-
AUY10	25/-
2S034	5/-
2N3055	12/6

### Diodes

AA42	2/-
OA95	2/-
OA79	1/9
OA81	1/9
IN914	1/6

## CLEARANCE LINES

**DON'T MISS THIS LAST CHANCE ONLY A FEW LEFT**

**UHF/VHF T.V. TUNER UNITS**

TU.2 CONTAINING 2 AF186's & 2 AF178's

PRICE 10/- P. & P. 2/6 EACH UNIT

All the units have many other components, e.g. Capacitors, Resistors, Coils and tuning condensers, etc. Although these are manufacturers rejects they are not beyond repair as has been proven by many of our customers.

**ALL TUNER UNITS ARE SUPPLIED WITH CONNECTION DATA**

## COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25 kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

**ONLY £1 each post and packing 4/6**

## SPECIAL LINE

1 AMP Bridge rectifiers, 1 1/2" Square 100 PIV. = 5/- 400 PIV. = 6/6 800 PIV. = 8/-

**PAK F.3. 2/6**  
Complementary Set. PAIR  
NPN/PNP Germ. Trans.

## BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

**2 LBS IN WEIGHT FOR £1**  
Post and packing 4/6

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	10/-
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output. Pair	10/-
B81	10	Reed Switches, mixed types large and small	10/-
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	10/-
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	10/-
B92	4	NPN. Sil. Trans. AO6 = BSX20, 2N2369 500 MHz, 360mW	10/-
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	10/-
B99	200	Mixed Capacitors. Postage 2/6. Approx. quantity, counted by weight	10/-
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	10/-
H4	250	Mixed Resistors. Postage 2/-, Approx. quantity, counted by weight	10/-
H7	40	Wirewound Resistors. Mixed types and values. Postage 1/6	10/-
H8	4	BY127 Sil. Recs 1000 PIV. 1 amp. plastic	10/-
H9	2	OCP71 Light Sensitive Photo Transistor	10/-

# FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 10/- WITH ORDERS OVER £4

## OUR VERY POPULAR 6d. TRANSISTORS

FULLY TESTED & GUARANTEED

TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.

TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.

TYPE "D" NPN Silicon planar, plastic TO-18 case. Audio preamplifier or 500 mW output stage, of the BC113/4/5 range.

TYPE "E" PNP Germanium AF or RF - please state on order. Fully marked and tested.

## RETURN OF THE UNBEATABLE P.I PAK.

**NOW GREATER VALUE THAN EVER**

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.1 ONLY 10/- 2/- P. & P. on this Pak.

## Make a Rev. Counter for your Car. The 'TACHO BLOCK'.

This encapsulated block will turn any 0-1mA meter into a linear and accurate rev.

counter for any car. **20/- each**

## FREE CATALOGUE AND LISTS FOR: -

**ZENER DIODES TRANSISTORS, RECTIFIERS FULL PRE-PAK LISTS & SUBSTITUTION CHART**

MINIMUM ORDER 10/- CASH WITH ORDER PLEASE. Add 1/- post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

## P.O. RELAYS 8 FOR

Various Contacts and Coil Resistances. No individual selection. Post & Packing 5/- **20/-**

**SPECIAL OFFER**  
**GERMANIUM BRIDGE RECTIFIERS**  
**GEX 541 FINNED**  
SINGLE PHASE | THREE PHASE  
12 Amp. 48 Volts | 18 Amp. 74 Volts  
Ideal for Battery Chargers or Power Units  
Offered at fraction of makers' cost Only **12/6** Each  
Post & Packing 2/6

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	10/-
B83	200	Trans. manufacturer's rejects all types NPN, PNP, Sil. and Germ.	10/-
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	10/-
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	10/-
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	10/-
B60	10	7 Watt Zener Diodes Mixed Voltages	10/-
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	10/-
H10	25	Mixed volts, 1 1/2 watt Zeners. Top hat type	10/-
H11	30	MAT Series "alloy" pnp Transistors	10/-
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	10/-
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied.	10/-
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts	10/-

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

**BI-PRE-PAK LTD** DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344


# Sensational News from Russia! for Every Lover of HI-FI!

Complete  
*DE LUXE* HI-FI STEREO  
**RADIOGRAM System**

**TRANSWORLD**  
6 WAVEBAND VHF AM/FM  
26 Transistors Plus 11 Diodes

Comprising **4** magnificent  
**UNITS!**

**GUARANTEED £140** *PERFORMANCE!*

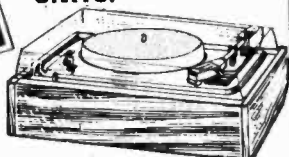

**FROM US  
FANTASTIC!**

**NOW ONLY 49! GNS**  
**2 COMPLETE**  
**CARR. ETC 2 GNS**

PLEASE DON'T CONFUSE WITH 'HOTCH POTCH' SYSTEMS MADE INTO A SET FROM PARTS OBTAINED FROM A VARIETY OF DIFFERENT SOURCES. THIS magnificent system from a famous Russian manufacturer is a miraculous achievement of Russian technology and only Shopertunities bring you this fantastic system (comparable with specifications costing around £140) brand spanking new with written 12 months' guarantee for the unbelievable price of only 49! gns., carriage, etc., 2 gns. You'll never appreciate the wonderful reproduction possible from your old stereo or mono records until you listen to them on this superb Hi-Fi Audio Unit. It's a breathtaking experience, but wait, with the 6 Waveband Radio you can get thousands of transmissions from all over the world including ham radio, ships at sea, Continental and international stations. Amazing clarity of tone and incredible station selection. Just read the magnificent specification of this compact fully transistorised high quality sound reproduction equipment in matching unit form: **Four-speed single Record Player deck**, lightweight arm with "turnover" sapphire stylus and transparent deck cover, etc. (15 1/2" x 12" x 6 1/2" approx.). **Two Speaker Cabinets** (each 18 1/2" x 9 1/2" x 8" approx), each containing 8" high efficiency units and 3" cone tweeter. **Fully transistorised Tuner/Amplifier** (26 transistors, 11 diodes) (18 1/2" x 9 1/2" x 8" approx), incorporating **VHF AM/FM plus automatic frequency control, LONG, MEDIUM AND 3 SHORT WAVEBANDS**. Yes, **Six WAVEBANDS in all!** All instantaneous Press Button Top Panel Controls! Push-pull output stage. Frontally controlled rotatable ferite rod aerial, internal FM aerial, meter type tuning indicator, stereo balance control, separate variable bass and treble controls give superb balance and tone, plus all usual extension sockets. 110, 127, 220, 240V a.c. All cabinets very strongly constructed—with beautiful gleaming walnut polyester finish—doesn't stain—retains high gloss indefinitely! Long negotiations and a final purchase for cash made this incredible offer possible! Please don't ask questions—just hurry! Only 500 will be lucky! Spares and U.K. Service constantly available. Send only 49! gns. plus carriage, crating, handling, etc., 2 gns., and test on 7-day approval. No more to pay! **OR CALL.** \*U.K. Trade distributors claim that British models comparing with this specification could cost you £140! We guarantee to refund your money if YOU don't agree! Send quickly or call. Personal shoppers welcome at both stores. (Commercial Travellers welcome at Holborn Store.)

**SHOPERTUNITIES LTD. SL**

Dept PE/2 164 UXBIDGE ROAD, LONDON W12 8AQ  
(facing Shepherd's Bush Green) (THURSDAY 1, FRIDAY 7),  
Also at 37/39 High Holborn, LONDON, W.C.1, (Wed, 1,  
Thurs, 7). Both stores open MON-SAT. 9 a.m.-6 p.m.

## LOW VOLTAGE AMPLIFIER


3 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output. With high I.M.P. input this amplifier will work as a record player, baby alarm, etc., amplifier. Few only at **£1.75** plus 75p P. & P.



WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN  
LONDON — SEND S.A.E. FOR FREE LISTS

**CRESCENT** RADIO LTD.  
11 & 40 MAYES ROAD, N22 6TL 888 3206

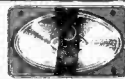MAIL ORDER  
DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL



**EMI LOUDSPEAKER 450**  
10W 13in 8in — two 2 1/2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 In 3-8-15 ohm imp. **£3.25** plus 37 1/2p P. & P. each.

## PSYCHEDELIC LIGHT CONTROL UNIT



Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.50** plus 37 1/2p P. & P.

If you require more information please send S.A.E.



## SHELF UNIT

Two teak finish shelves on a black frame (overall size: 28in x 25in x 12in). Ideal for hi fi equipment: amplifiers speaker cabinets, etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting. **£2.50** plus 37 1/2p P. & P.

**EMI LOUDSPEAKER 150**  
10 watts, 13 8 base unit. Plus a flared centre cone. Designed to handle the higher frequencies. Please state imp required, 3, 8, 16 Ohm. A bargain at **£2.50** plus 37 1/2p P. & P. each.

## BATTERY ELIMINATOR



Plug your Transistor Radio, Amplifier, cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2in 2in 3in approx. 4V **£1.50**, 6V **£1.50**, 9V **£1.50**, 7 1/2 V complete with cable and plug for Philips Cassette. **£2** plus 75p P. & P. each.



## CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 37 1/2p, C90 62 1/2p, C120 87 1/2p plus 3p P. & P.

## HIGH QUALITY IMPORTED HEADPHONES

1,000 Ohm per phone ... 80p  
2,000 Ohm per phone ... 87p  
Plus 10p P. & P. per pair.



## STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2.50** plus 10p P. & P.



## STEREO JUNCTION BOX

For stereo amplifiers without stereo jack socket. **£1.25** plus 7 1/2p P. & P.



## EMI SINGLE PLAYER

EMI single 4 speed record player deck complete with P.C. arm and cartridge. Ideal for a record player at a modest cost. Our Price. **£3** plus 32 1/2p P. & P.

## IMPORTED PANEL METERS

KA-38C 1 1/2in 1 1/2in. 50uA, 100uA, 500uA 1M/A, 5M/A, 8 meter 1M/A, 300V. All at **£1.50** plus 7 1/2p P. & P.



KA-65C 3 1/2in 3 1/2in. 300V, 8 meter 500uA, 1M/A. All at **£2** plus 7 1/2p P. & P.

All modern design and made to high standards.

## BRITISH RECORDING TAPE

of the finest quality (all guaranteed). 5in 600ft, 42 1/2p each, 3 for **£1.20**, 5 1/2in 900ft, 50p each, 3 for **£1.42**, 7in 1,200ft 57 1/2p each, 3 for **£1.85**. Please include 7 1/2p on each order for P. & P.



## CHROME TV STAND

25in 8 1/2in 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at: **£1.62 1/2** plus 25p P. & P.



## LEGS

18 1/2in high, 7 1/2in wide at top, 13in wide at bottom. In modern matt black finish ideal for all types of cabinets, loudspeaker plinth, record player, etc. **75p** per pair plus 15p P. & P.



**BRAND NEW GUARANTEED**

**SEMICONDUCTORS & COMPONENTS**

RETURN OF POST SERVICE

CHOICE OF 1000'S OF DEVICES

**TRANSISTORS**

2G301	4/-	2N3402	4/6	3N142	11/-	BC160	12/6	BFY50	4/6	NKT229	6/-
2G302	4/-	2N3403	4/6	3N143	13/6	BC167	3/6	BFY51	4/-	NKT237	7/-
2G303	4/6	2N3404	6/6	3N152	17/6	BC168	3/6	BFY52	4/6	NKT238	5/-
2G306	4/6	2N3405	6/6			BC169	3/6	BFY53	3/6	NKT240	3/6
2G308	6/-	2N3414	4/6	R.C.A.		BC168C	3/6	BFY56A	6/-	NKT281	3/6
2G309	6/-	2N3415	4/6	40050	10/6	BC169	3/6	BFY77	8/-	NKT713	4/-
2G371	3/-	2N3416	7/6	40251	17/6	BC169B	2/9	BFY78	11/6	NKT781	6/-
2G374	4/-	2N3417	7/6	40309	6/6	BC169C	3/-	BFY85	9/-	NKT10419	9/-
2G381	4/6	2N3570	25/-	40310	9/-	BC170	2/6	BFY90	13/6		6/-
2N409	4/6	2N3573	19/6	40311	7/-	BC171	3/-	BPX25	37/-	NKT10439	7/6
2N696	4/6	2N3623	5/6	40312	9/6	BC172	3/6	BPX27	37/-	NKT10519	6/6
2N697	4/6	2N3606	5/6	40314	7/6	BC175	4/6	BSV41	8/6	NKT20329	9/6
2N698	5/-	2N3607	4/6	40320	7/6	BC182	2/6	BSV41	8/6		9/6
2N706	2/6	2N3662	7/6	40323	6/6	BC182L	2/-	BSV70	5/6		9/6
2N706A	2/6	2N3663	7/6	40324	9/6	BC183	2/6	BSX19	3/6		7/6
2N708	3/-	2N3702	2/6	40326	7/6	BC184	3/-	BSX20	3/6		7/6
2N709	12/6	2N3703	2/6	40329	6/6	BC121L	2/6	BSX21	7/6		18/6
5N718	5/-	2N3704	3/6	40344	5/6	BCY30	3/6	BSX26	9/6		18/6
2N726	6/-	2N3705	3/-	40346	11/6	BCY31	7/6	BSX27	9/6		19/6
2N727	6/-	2N3706	2/6	40348	10/6	BCY32	7/6	BSX28	6/6		18/6
2N914	3/6	2N3707	3/-	40360	8/6	BCY33	4/-	BSX28	6/6		18/6
2N916	3/6	2N3708	2/-	40361	9/6	BCY34	4/6	BSX61	12/6		22/6
2N918	4/6	2N3709	2/-	40362	11/6	BCY38	4/6	BSX76	4/6		18/6
2N920	4/6	2N3710	2/6	40370	6/6	BCY39	10/6	BSX77	5/6		18/6
2N921	5/-	2N3704	3/6	40406	11/6	BCY40	7/6	BSX78	5/6		18/6
2N1090	4/6	2N3715	2/6	40408	10/6	BCY43	4/6	BSY24	3/-		18/6
2N1091	4/6	2N3716	58/-	40408	10/6	BCY43	4/6	BSY25	3/6		18/6
2N1131	5/-	2N3791	55/-	40410	12/6	BCY54	6/6	BSY26	3/6		18/6
2N1132	5/-	2N3819	7/-	40467A	11/6	BCY58	4/6	BSY27	3/6		18/6
2N1302	3/6	2N3823	19/6	40468A	7/-	BCY59	4/6	BSY28	3/6		18/6
2N1303	3/6	2N3854	5/6	40600	14/6	BCY60	19/6	BSY29	3/6		18/6
2N1304	4/6	2N3854A	6/6	AC107	6/-	BCY70	8/6	BSY29	3/6		18/6
2N1305	4/6	2N3855	5/6	AC107	6/-	BCY71	8/6	BSY32	5/-		18/6
2N1306	5/-	2N3855A	6/-	AC127	5/-	BCY72	5/6	BSY32	5/-		18/6
2N1307	5/-	2N3856	6/-	AC128	4/6	BCZ10	5/6	BSY36	5/-		18/6
2N1308	6/-	2N3856A	7/-	AC154	4/6	BCZ11	8/6	BSY37	5/-		18/6
2N1309	6/-	2N3858	5/-	AC176	5/-	BD116	22/6	BSY38	4/6		18/6
2N1507	3/6	2N3858A	6/-	AC187	12/-	BD121	13/-	BSY39	4/6		18/6
2N1613	3/-	2N3859	6/6	AC188	7/6	BD123	16/6	BSY40	6/6		18/6
2N1631	6/-	2N3859A	6/6	AC192	12/6	BD124	12/6	BSY41	6/6		18/6
2N1632	6/-	2N3860	6/6	ACY18	5/-	BD131	19/6	BSY51	6/6		18/6
2N1637	6/-	2N3866	30/-	ACY19	5/-	BD132	19/6	BSY52	6/6		18/6
2N1638	5/6	2N3877	8/-	ACY20	5/-	BDY10	27/6	BSY53	7/6		18/6
2N1639	5/6	2N3877A	8/-	ACY21	5/-	BDY11	32/6	BSY56	18/-		18/6
2N1711	3/6	2N388A	12/6	ACY22	4/6	BDY17	30/-	BSY79	9/-		18/6
2N1809	6/6	2N3890	7/6	ACY28	4/6	BDY18	35/-	BSY82	10/6		18/6
2N1893	4/6	2N3900A	8/6	ACY40	5/-	BDY19	39/6	BSY90	11/6		18/6
2N2147	16/6	2N3901	19/6	ACY41	5/-	BDY20	22/6	BSY95A	2/6		18/6
2N2148	11/6	2N3903	7/-	ACY44	8/-	BDY38	19/6	D16P2	7/6		18/6
2N2160	11/6	2N3904	7/-	AD140	10/6	BDY60	25/-	D16P2	7/6		18/6
2N2193	8/-	2N3905	7/6	AD149	12/6	BDY61	25/-	D16P4	8/-		18/6
2N2193A	8/-	2N3906	7/6	AD150	12/6	BDY62	20/-	D16P4	8/-		18/6
2N2194	6/6	2N4058	6/6	AD161	7/6	BF115	5/-	GET102	6/-		18/6
2N2217	5/6	2N4059	2/-	AD162	7/6	BF117	7/6	GET113	4/6		18/6
2N2218	6/-	2N4060	2/6	AF106	8/6	BF163	7/6	GET114	4/6		18/6
2N2219	6/-	2N4061	2/6	AF106	8/6	BF173	5/-	GET118	4/6		18/6
2N2220	5/-	2N4062	2/6	AF115	6/6	BF173	6/6	GET118	4/6		18/6
2N2221	6/-	2N4244	9/6	AF116	5/-	BF177	6/6	GET120	6/6		18/6
2N2222	5/-	2N4285	3/6	AF117	5/-	BF178	10/6	GET873	3/-		18/6
2N2287	2/6	2N4286	3/6	AF118	12/6	BF179	10/6	GET880	6/-		18/6
2N2297	5/-	2N4287	3/6	AF119	4/6	BF180	7/-	GET887	4/-		18/6
2N2303	5/-	2N4288	3/6	AF119	4/6	BF181	6/6	GET889	4/6		18/6
2N2368	5/-	2N4289	3/6	AF125	4/-	BF184	5/-	GET890	4/6		18/6
2N2369	3/-	2N4290	3/6	AF126	4/-	BF185	8/6	GET896	4/6		18/6
2N2369A	3/-	2N4291	3/6	AF127	3/6	BF194	3/6	GET997	4/6		18/6
2N2410	8/6	2N4292	2/6	AF139	7/6	BF195	4/-	GET998	4/6		18/6
2N2483	5/6	2N4303	9/6	AF178	8/6	BF196	8/6	GET998	4/6		18/6
2N2484	6/6	2N5027	10/6	AF178	8/6	BF197	8/6	MCI40	6/6		18/6
2N2539	4/6	2N5028	11/6	AF180	10/6	BF198	8/6	M1400	2/6		18/6
2N2540	4/6	2N5029	9/6	AF181	8/6	BF200	10/6	M1420	22/6		18/6
2N2613	7/6	2N5030	8/6	AF239	8/6	BF224	4/6	M1430	20/6		18/6
2N2614	1/6	2N5172	2/6	AF279	9/6	BF225	4/6	M1430	20/6		18/6
2N2646	1/6	2N5173	10/6	AF280	12/6	BF227	4/6	M1440	19/6		18/6
2N2696	6/6	2N5175	10/6	AF211	6/6	BF238	4/6	M1480	19/6		18/6
2N2711	5/-	2N5176	9/-	ASV26	5/-	BF244	6/6	M1481	25/-		18/6
2N2712	5/-	2N5232	5/6	ASV26	5/-	BFW58	5/6	M1490	20/-		18/6
2N2713	5/6	2N5232A	6/6	ASV28	5/6	BFW59	5/-	M1491	27/6		18/6
2N2714	6/-	2N5245	8/6	ASV29	5/6	BFW60	5/6	M1800	22/6		18/6
2N2865	12/6	2N5246	8/6	ASV36	5/-	BFX61	4/6	MJE340	17/6		18/6
2N2904	6/6	2N5249	13/6	ASV36	5/-	BFX12	4/6	MJE520	17/6		18/6
2N2904A	6/6	2N5249A	13/6	ASV50	5/-	BFX13	4/6	MJE521	17/6		18/6
2N2905	7/6	2N5265	65/-	ASV54	5/-	BFX29	6/-	MJE2801	21/-		18/6
2N2905A	8/-	2N5265	65/-	ASZ20	7/6	BFX30	6/-	MJE2901	21/-		18/6
2N2906	5/-	2N5267	52/6	ASZ21	8/6	BFX43	7/6	MPE102	8/6		18/6
2N2906A	5/6	2N5268	8/6	AUY10	30/-	BFX48	7/6	MPE103	7/6		18/6
2N2907	6/-	2N5306	8/6	BC107	2/6	BFX68A	13/6	MPE105	7/6		18/6
2N2923	3/-	2N5307	7/6	BC108	2/6	BFX84	5/6	MPE105	7/6		18/6
2N2924	3/-	2N5308	7/6	BC109	2/6	BFX85	6/6	MPSA65	5/-		18/6
2N2925	3/-	2N5309	12/6	BC113	5/6	BFX86	5/-	NKTA66	5/6		18/6
2N2926	3/-	2N5310	8/6	BC115	8/6	BFX87	5/6	NKTA66	5/6		18/6
Green 2/9	2N5354	5/6	BC115	8/6	BFX87	5/6	NKTA66	5/6		18/6	
Yellow 2/6	2N5356	6/6	BC118	6/6	BFX89	12/6	NKTI25	8/6		18/6	
Orange 2/6	2N5365	9/6	BC121	4/-	BFX92A	12/6	NKTI26	5/6		18/6	
2N3011	6/-	2N5366	6/6	BC122	4/-	BFX93A	14/-	NKTI28	5/6		18/6
2N3014	6/6	2N5367	11/6	BC125	11/-	BFY10	6/6	NKTI35	5/6		18/6
2N3053	7/6	2N5367	11/6	BC126	11/-	BFY11	8/6	NKTI37	6/6		18/6
2N3054	10/6	2N5368	15/6	BC134	6/6	BFY12	4/6	NKTI40	6/-		18/6
2N3055	15/-	25020	40/-	BC135	8/6	BFY13	4/6	NKTI41	6/6		18/6
2N3133	6/-	25102	10/6	BC136	7/6	BFY17	4/6	NKTI212	6/-		18/6
2N3134	6/-	25103	3/-	BC140	7/6	BFY18	6/6	NKTI213	6/-		18/6
2N3135	5/-	25104	5/6	BC147	3/6	BFY19	6/6	NKTI214	4/6		18/6
2N3136	5/-	25501	6/6	BC148	2/6	BFY20	12/6	NKTI215	4/6		18/6
2N3190	5/-	25502	7/6	BC149	3/6	BFY21	8/6	NKTI216	7/6		18/6
2N3191	4/-	25503	5/6	BC152	3/6	BFY24	9/6	NKTI217	8/6		18/6
2N3391A	6/-	3N83	8/6	BC154	4/6	BFY30	10/6	NKTI219	6/-		18/6
2N3392	3/6	3N128	14/-	BC157	4/6	BFY30	10/6	NKTI223	5/6		18/6
2N3393	3/-	3N140	15/6	BC158	3/6	BFY41	10/6	NKTI224	5/6		18/6
2N3394	3/-	3N141	14/6	BC159	4/6	BFY43	12/6	NKTI225	4/6		18/6

**PANEL METERS**

38 Series—FACE SIZE .52 x .42mm. All prices for 1-9 pieces.  
 50µA, 37/6; 100µA, 35/-; 200µA, 32/6; 500µA, 27/6; 50-0-50µA, 35/-; 100-0-100µA, 32/6; 500-0-500µA, 25/-; 10A, 25/-; 25A, 25/-; 50MA, 25/-; 100MA, 25/-; 500MA, 25/-; 1A, 25/-; 5A, 25/-; 10V, 25/-; 20V, 25/-; 50V, 25/-; 300V, 25/-; 500V, 25/-; ALL METERS ARE D.C.

**SILICON RECTIFIERS**

PIV	50	100	200	400	600	800	1000	1200
1A	2/-	2/6	3/-	3/3	3/6	3/9	4/-	—
3A</								

# Practical Electronics Classified Advertisements

RATES: 1/6 per word (minimum 12 words). Box No. 1/6 extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London, E.C.4

## MISCELLANEOUS

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND 95/- NOW

TO: 'BOFFIN PROJECTS'  
DEPT. K2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send S/5d. stamps NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 10s.). No callers please, mail-order ONLY.

**AUDIOSCAN** Dept. P.E.2  
4, PRINCES SQUARE  
HARROGATE, YORKS.

### BIG BARGAIN PARCEL 13/- POST PAID

Containing multi-contact relay, transistors, resistors (some high stab), rectifiers, diodes, capacitors, pots, knobs, etc.

### 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed **72/6** POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

**CIRCUIT BOARD ETCHING KITS**, full instructions, 19/6d. C.W.O. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

**HOLIDAY FOR BOYS**, 14/16 years August 1971, specialising in engineering, electronics, photography. Tuition and practical work including karting. 11 days—£15. Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, 47 Marylebone Lane, London, W1M 6AX.

## FIBRE OPTICS

### CONTINUOUS LIGHT GUIDE

0.031" dia. 5 feet at £1

EXTRA QUANTITIES 3/- per foot

0.063" dia. 5 feet at £3

EXTRA QUANTITIES at 10/- per foot

Strictly C.W.O.

FIBRE LIGHT, P.O. BOX 25  
CROWTHORNE, BERKSHIRE

**CLEARING LABORATORY**, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

## MISCELLANEOUS (continued)

### NEW LOW PRICE


Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 1/9d. each or

Any 16 transistors for only £1.

ACY22	BSY27	OC201	2N3702
BC108	OC45	OC202	2N3703
BC109	OC71	ZTX300	2N3705
BFY51	OC72	2N3000	2N3706
BFY52	OC200	2N2926	2N3708

MONEY BACK GUARANTEE. P. & P. 1/-  
J. M. KING (A)

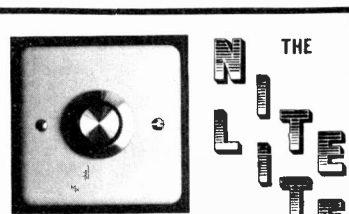17 Buckridge, Portpool Lane, London, E.C.1



### Dimmerswitch

Will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

Complete Kit: £2.85 (12/1)

PRICE: Built & tested: £3.35 (12/1)

### Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK.  
£0.10 postage & packing

**BUILD IT IN A DEWBOX** quality cabinet 21u x 24u x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

**10 PRINTED CIRCUITS EX COMPUTER.** Contents: 2 x OC200 Transistors on Heat-sink. 3 Potted Transformers. 90 Capacitors. 100 Transistors, Audio and Switching Types. 250 Diodes includes Zeners, OA10. 350 Resistors includes Trimmers. Over 800 Items for 20/-. P. & P. 7/-. BUNTING, 18 Oakfield Road, Rugby.

### 6 or 12 volt FLUORESCENT LIGHTS

12 ins. 8 watt tube, ample light for camping, caravan or boats, etc. fully transistorised, low battery drain.

Only 65/- post paid  
or in kit form 57/6 post paid

### 4 watt GRAM AMPS

Quality gram amplifier, volume/on, off and tone controls, A.C. mains operation, 3Ω output, dimensions 4 1/2 x 4 1/2 x 5 1/2 ins. app. new and boxed.

Unbeatable at 67/6 post paid  
or in kit form 59/6 post paid

**ELECTRONIC INDUSTRIES (SHROPSHIRE)**  
4 Longden Green, Shrewsbury, Shropshire

**SCRAP VALVES WANTED.** Type TY5-500, TY6-800, TY6-1250A, TY7-6000A, TY8-5-3000, ESA1500, 16P13, BW1169, also similar types. ELECTRONIC HEAT CO., 352 Lower Addiscombe Road, Croydon. Tel. 01-854 7172.

## MISCELLANEOUS (continued)

### NEW! NEW!! NEW!!!

### The Sweetest Sound You Ever Heard

An exciting new, all silicon, power amplifier module to a completely NEW design. Minimum cross-over distortion, not dependent on supply voltage, eliminates unpleasant 'transistor sound'. Specially designed to work well from simple, unregulated power supply, 50-58 v. 11 transistors, short circuit proof, unconditionally stable, temperature stabilised, 400 m/v input for 30 watts RMS (8 ohms). Output impedance 8-16 ohms. Completely built on 16 swg heatsink. Neat, space-saving, upright mounting. Fully tested and guaranteed with comprehensive instructions.

£8.17.6 each. P. & P. 2/6. Stereo pair. Post free

## ELECTRONIC SUPPLIES

P.O. BOX 148, SHEFFIELD S17 3EX

**NEW P.8.U.'s ROBAND.** One-third list. Other bargains. S.A.E. Lists. D. G. SMITH, 12 Channel Heights, Weston-super-Mare.

## PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use R.F. SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"!

DON'T PUT IT OFF! SEND 3/- for your list—NOW

### BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY  
Designs by GERRY BROWN and JOHN SALMON  
and presented on TV

**STUDENTSHIPS WITH GRANTS.** Careers. England, Europe, U.S.A. S.A.E.—PARA-PHYSICAL LABORATORY, Downton, Wilts.

## MUSICAL MIRACLES

**WAA-WAA Pedal.** Complete kit of all parts: robust cabinet, mechanism and instructions. Huge sales, well proven design. Only 49/- complete. Or built and tested £4.15a, post free. Rhythm Box. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtrot, etc., costs under £17. Organ Percussion units £14. Bass pedal and other fascinating effects, fuzz, tremolo, etc. Send s.a.e. for list: D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset

## SERVICE SHEETS

## LARGE SUPPLIER OF SERVICE SHEETS

T.V., RADIO, TRANSISTORS, TAPES, CAR RADIOS  
5/- EACH, MANUALS FROM 10/-  
PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES AND ORDERS  
(Uncrossed P.O.'s please, original returned if service sheets not available.)  
FREE TV FAULT TRACING CHART OR TV LIST ON REQUEST WITH ORDER

**C. CARANNA**  
71 BEAUFORT PARK, LONDON, N.W.11  
MAIL ORDER ONLY

## SERVICE SHEETS (continued)

**SERVICE SHEETS.** Radio, TV, etc., 8,000 models. List 2/-. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**RADIO TELEVISION,** over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherds Bush Rd., London, W.6 (01-743 8441).

**SERVICE SHEETS (1925-1970)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 1/-. Over 8,000 models available. Catalogue 2/6. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

**WE BUY NEW VALVES.** Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

## TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types

**KENSINGTON SUPPLIES**

(B) 367 Kensington Street  
Bradford 8, Yorks.

## COURSES

# TRAINEE RADIO TECHNICIANS

A PROGRESSIVE CAREER  
IN THE FIELD OF RADIO  
AND ELECTRONICS

Applications are now invited for an intensive training course of two years, leading to appointment as a fully qualified RADIO TECHNICIAN, with further prospects of progression to the Telecommunications Technical Officer Class.

Generous Pay and Conditions while under training.

Candidates must be over 16 and under 21 years of age as at 6th September, 1971, on which date training commences.

Minimum educational qualifications required are passes at GCE 'O' Level in English Language, Mathematics and Physics (already held or expected to be obtained in the Summer, 1971). Equivalent passes in Scottish or Northern Ireland Certificates and CSE Grade I passes are also acceptable. Closing date for receipt of applications 26th February, 1971.

Apply for full details and application form to:

**THE RECRUITMENT OFFICER (TRT/54)  
GOVERNMENT COMMUNICATIONS  
HEADQUARTERS  
OAKLEY, PRIORS ROAD  
CHELTENHAM, GLOS. GL52 5AJ**

## SITUATIONS VACANT

**EAGLE INTERNATIONAL** require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-636 0961.

## WANTED (continued)

**HIGHEST CASH PRICES** for tape recorders. 9.30-5. Immediate quotations. 01-472 2185.

**PRACTICAL ELECTRONICS** wanted Dec. 1969 to May 1970. Telephone DRAKE, Brownhills 3167 or write Box No. 34.

**PRACTICAL ELECTRONICS** Dec. 1969 to Jan. 1970 wanted. State price. Box No. 33.

## FOR SALE

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

## MORSE MADE EASY !!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 8d. stamp for explanatory booklet to:

**GSHSC (Box 19), 45 GREEN LANE, FURLEY SURREY**

**NEW CATALOGUE** No. 18, containing credit vouchers value 10/-. now available. Manufacturers' new and surplus electronic and mechanical components, price 4/6, post free. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

**INTEGRATED CIRCUIT TESTER BY UNIVAC.** Repair required. Fair condition. \$25. Telephone: Brentwood 225877 evenings.

## EDUCATIONAL

**HUNDREDS OF TOP PAID JOBS** in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

**A.M.S.E. (Elec.),** City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV., etc. Send for full details and illustrated book — FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

## COLOUR TV SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV engineer technician, and approved by leading manufacturer. Full details from ICS (D.561), Intertext House, London, S.W.8, or phone 01-720 1983.

## SITUATIONS VACANT



Established 1891

# TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

## NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS**

**A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!**

**International Correspondence Schools**  
(Dept. 152), Intertext House, Stewarts Road,  
London, S.W.8

NAME.....  
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 2/71

## LADDERS

**VARNISHED TIMBER** from manufacturer; Lowest prices anywhere: 15ft. ext., \$5.10; 17ft. ext., \$5.15; 20ft. ext., \$6.5; 21ft. ext., \$7; 24ft. ext., \$8.5; 29ft. ext., \$9.5; 31ft. ext., \$11.2.6; 38ft., triple ext., \$14.10. Carr. 13/6. Free Lists Also aluminum ext. and loft ladders. (Callers welcome. Dept. PEE, HOME SALES, Baldwin, Road, Stourport, Worcs. Tel. Stourport 2574.

## TAPE RECORDERS

**TAPE BARGAINS.** Double play AMPEX. 7in. 2,400ft reels, packed in RECOTAPE sealed boxes. Superb quality, fully guaranteed. 2 for 57/6, 6 for 150/- 5 1/2in. 1,800ft reels as above. 2 for 42/-, 6 for 107/6. 7in. 1,800ft L.P., 2 for 41/6, 6 for 120/- 5 1/2in D.P. 1,800ft, 2 for 45/6, 6 for 130/- 5 1/2in L.P. 1,200ft, 2 for 27/6, 6 for 77/6. Money back if not delighted. 2/6 P. & P. on all orders under £5. MUSIC TAPES MAIL ORDER, 38 High Street, Salisbury, Wilts.

## NOW SAVE ON CASSETTES

AUDEMAG Compact Cassettes, fully guaranteed top quality, in plastic library boxes with giant 6" x 4" label giving double writing space.

CG8	21/6	6	30
CG9	31/6	58/-	100/-
CL80	38/6	78/6	130/-

2/6 P. & P. on all orders under £3.

Money back if not satisfied.

**MUSIC TAPES MAIL ORDER**  
38 High Street, Salisbury, Wilts.

## ELECTRICAL

**240 VOLT  
ELECTRICITY  
ANYWHERE**



**BEST EVER 200/240 VOLT "MAINS" SUPPLY FROM 12 VOLT CAR BATTERY**  
Exclusive World Scope Purchase. The fabulous Mk.12D American Heavy Duty Dynamotor Unit with a Massive 220 watt output and giving the most Brilliant 220/240 volt performance of all time. Marvellous for Television, Drills, Power Tools, Mains Lighting, AC Fluorescent Lighting and all 200/240 volt Universal A.C.D.C. mains equipment. Made at tremendous cost for U.S.A. Govt. by Delco-Remy. This magnificent machine is unobtainable elsewhere. Brand New and Fully Tested. Only £6.19.6 + 10/6 postage. C.O.D. with pleasure, refund guarantee. Please send S.A.E. for illustrated details.

Dept. PE, STANFORD ELECTRONICS  
Near Derby Road, North Promenade,  
Blackpool, Lancashire

## MUSICAL INSTRUMENTS

## ELECTRONIC ORGAN DIVIDER CIRCUITS

These i.c. divider circuits contain one master oscillator and six dividers. The output is square wave with a rise time of approximately 20µ secs. and size is only 2 1/2" x 1 1/2" x 1 1/2".  
Price 75/- (£3.75) each or £42 per dozen, postage paid. Cash with order please, to:

**AUDICION, 105 Anson Road  
Great Wyrley, Walsall WS6 6JP**

## RECEIVERS AND COMPONENTS

**BRAND NEW ELECTROLYTICS** 15/16V 0.5, 1, 2, 5, 10, 20, 30, 40, 50, 100µF, 0d. E12 series 5% resistors, Carbon Film 1/4W 1Ω to 1MΩ, 1.5d. Wirewound 5W 15Ω to 15kΩ, 10d. Postage 1/-. The C.R. SUPPLY CO., 127, Chesterfield Rd., Sheffield, S8 0RN.

**AD161/AD162 POWER PAIRS**, matched, for Mullard amplifier circuits. Mint, 12/6 pair, U.K. post paid. List 6d. **AMATRONIX LTD.**, 386 Selsdon Rd., S. Croydon, Surrey, CR2 0DE.

## RECEIVERS AND COMPONENTS

(continued)

### PRINTED CIRCUIT BOARDS FOR P.E. PROJECTS

All boards drilled and roller tinned complete with layout drawing.

#### EXAMPLES

Marine Tachometer (May 1970) 5/- ea. Musical Stave (May 1970) 8/- ea.  
Waa-Waa pedal Vol. 4 No. 7 2/9 ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 8/6 ea.  
S.A.E. for List. Now available from:- **HENRY'S RADIO LTD.**, Edgware Road, London, W.2  
**P.H. ELECTRONICS**, Industrial Estate, Sandwich, Kent. Tel. 2517

### DRY REED INSERTS



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250v D.C. Gold clad contacts. 12/6d. per doz.; 75/- per 100; £27.10.0 per 1,000; £250 per 10,000. All carriage paid.

**G.W.M. RADIO LTD.**  
40/42 Portland Road, Worthing, Sussex 0903 34897

## NEW MODEL V.H.F. KIT 'MK2

Our latest Kit, improved design and performance plus extra Amplifier Stage, receives Aircraft, Amateurs, Mobile, Radio 2, 3, 4, etc.

This novel little set will give you endless hours of pleasure and can be built in one evening. Powered by 9 Volt battery, complete with easy to follow instructions and built in Jack Socket for use with Earphones or Amplifier.

Only 68/- P. & P. Free U.K. only

Postal Orders, Cheques to:

Dept. P.E.  
Gallean Trading Co., 25 Avelon Road,  
Romford, Essex

**A CORNUCOPIA OF COMPONENTS!** Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

**CAPACITORS.** Dubllier, 0.1µF 500V, 6/- doz., 42/- 100. Hunts, 0.04µF 500V, 3/- doz., \$1 per 100; 0.001µF and 0.005µF 350V, 3/- doz., \$1 per 100. Skeleton Presets, 2kΩ, 1/3, Co-ax Sockets on isolation panel, 1/3, 12/- doz. Jack Plugs, Standard, 1/9; 3.5mm, 1/3; 400-200-50-16µF 300V, 6/-, \$3 per doz. Recording Tape, 5in LP, 9/-, 5 1/2in LP, 12/-, Post and packing on all orders 2/-. Send S.A.E. for list. M. DZUBAS, 158 Bradshawgate, Bolton, Lancs.

## ANDOR ELECTRONICS LTD

for  
MULLARD COMPONENTS  
for  
AUDIO CIRCUITS  
178 HIGHER HILLGATE

## STOCKPORT

061-480 9791

## RECEIVERS AND COMPONENTS

(continued)

**KX COMPUTER PRINTED CIRCUIT PANELS** 2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 10/-, P. & P. 1/6. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for \$1, P. & P. 3/6. With a guaranteed minimum of 55 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 10/-, P. & P. 1/6.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for 50/-, P. & P. 6/-.

**LARGE CAPACITY ELECTROLYTICS**  
10,000µF 30V } 7/6 each. P. & P. 1/6.  
16,000µF 12V }  
or \$3.10.0 per doz. Carr. 10/-.

**250 MIXED RESISTORS** 12/6  
1/2 & 1/4 watt.

**150 MIXED HI STABS** 12/6  
1/2, 1 & 1 watt 5% & better.

**EXTRACTOR/BLOWER FANS (PAPST)**  
100 CFM 2,800 RPM 4 1/2in x 4 1/2in x 2in. Ideal for kitchen extraction, instrument cooling, etc. etc. 50/- each. P. & P. 5/-, 240V a.c. 50 Q.

**DIODES EX EGPT. SILICON**  
1 Amp 1,000 PIV 4 for 10/-  
20 Amp 150 PIV 4 for \$1.  
P. & P. 1/-.

## BARGAIN RELAY OFFER

Single pole change over silver contacts 25V up to 50V. 2.5kΩ coil. 8 for 10/-, P. & P. 1/-.

**KEYTRONICS** mail order only  
52 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

## R & R RADIO

51 Burnley Road, Rawtenstall  
Rossendale, Lancs

Tel.: Rossendale 3152

VALUES TESTED & GUARANTEED

EBF80	3/-	PCC84	3/-	PY81	3/6
EBF89	3/6	PCF80	3/-	PY82	3/-
ECC82	3/-	PCL82	4/-	PY800	3/6
ECL80	3/-	PCL83	4/-	PY801	3/6
EF80	1/6	PL36	5/-	UI91	4/6
EF85	3/-	PL81	4/-	30F5	2/6
EY86	4/-	PL83	4/-	30C15	5/-
EZ40	4/6	PY33	5/-		

POST, ONE VALVE 9d. TWO TO SIX 6d.  
OVER SIX POST PAID.

## RADIO CONTROL AT A PRICE YOU CAN AFFORD RADIO CONTROL PRODUCTS

FOR THE REMOTE CONTROL OF MECHANISMS OF ALL KINDS

### TRANSMITTER

NEW SMALLER UNIT  
CRYSTAL CONTROLLED

ON 27 MHZ

9V OPERATION

SILICON TRANSISTORS

TRANSMITTER £6.10.0

### RECEIVER

NEW TINY RELAYLESS  
SIZE ONLY 3.5 x 2.8 x 20CMS  
WEIGHT 20 gms  
4.5V WORKING

WILL OPERATE LIGHTS,  
MOTORS OR ACTUATORS  
DIRECT

RECEIVER £4.10.0

RELAY VERSION + 25/-

### EXCELLENT RANGE AND PERFORMANCE

Transmitter and matched Superhet Receiver £18.10.0. Relay + 25/-  
Digital proportional equipment also available.

ALL UNITS ARE CAREFULLY  
TESTED BEFORE SALE AND  
ARE FULLY GUARANTEED

**RADIO CONTROL PRODUCTS**  
123 BEWLEY HILL  
KIDDERMINSTER, WORCS.

## RECEIVERS AND COMPONENTS

(continued)

### TRANSFORMER KITS

Consisting of:- CLAMPS, WINDING BOBBIN AND LAMINATIONS

Max. Rating	Ref. No.	Price	P. & P.
5 VA	74/63	8/3	1/6
10 VA	35/75	10/6	2/6
15 VA	147/88	14/9	3/6
25 VA	29/1	20/6	4/6
50 VA	78/125	35/6	5/6
75 VA	78/150	47/6	6/6
100 VA	120/125	55/-	7/6

Transformer designs up to 100VA  
10/- ea., larger kits and designs available on request.

Supplied by:

**WEST DIDSURY TRANSFORMERS**  
Brooks Street, Higher Hillgate  
Stockport, Cheshire SK1 3EU  
Tel. 061-480 6479

**POLYETHYLENE CAPACITORS.** 125 or 350V, 150, 180, 330, 390, 560, 680, 820, 1,800, 2,200, 2,700, 5,600, 6,800, 8,200; 125V, 18, 22, 120, 220, 1,200, 1,600, 3,300, 3,900, 0-01, 0-012, 0-015; Paper 100V, 100, 1,000, 2,000, 5,000, 3/- doz. Post 1/6.

**COMPUTER PANELS.** 5-BC108 diodes 3/- ea. 4 for 10/-, Post 1/6. 8-OC76 or OC72 or OC42, 8-OA10, 7/6. 8-OC48 or GET876, 24 OAS1, 7/6. 8-OC170 diodes, etc., 7/6. 2-OC170, 2 GET875 or 4 MDS84, 5-100MFD 12V electrolytics, post core, etc., 8/-, 10-B8X26. 550MEG silicon npn diodes, etc., 7/6.

**MIXED TRANSISTORS ON PANELS.** 50 for 12/6. 100 for 20/-. Panels with capacitors, resistors, diodes, 6for 5/-. Air spaced trimmers, 25 and 100pF, 2/-. Ceramic 40, 50, 25pF, 6d.

**SEL. RECTIFIER AND VARIABLE RESISTOR** in neat case. Input 15V, output 0-12V at 1amp 8/-.  
**MIDGET RELAYS** 1in x 1in x 1in, weigh 1oz. D.P.D.T. carry 2amp at 28V, 700 ohm coil, 10/6. With base, 12/6 Post free.

**M.C. METERS** 2in and 2 1/2in. 3 assorted for 21/-. M.C. Phones and mike, 45ohm, 12/6. P. & P. 2/- unless stated otherwise.

### J.W.B. RADIO

75 Hayfield Rd., Salford 6, Lancs.  
MAIL ORDER ONLY

Microcircuits:

709 .. 50p 741 .. £1.05 PA230 .. 92p  
PA234 .. 87p PA237 .. £1.57 D40C1 .. 67p

### VALUE FOR MONEY

Plessey Microelectronics made a large number of microcircuit audio amplifiers. They tested these. The best ones were marked SL403A. The next best were marked SL402A. Some reject devices were sold as scrap.

We sell Plessey marked SL402A for £1.75 complete with full data, circuits, etc.

### JEF ELECTRONICS (P.E.2)

York House, 12 York Drive, Grappenhall  
Warrington, Lancs.

Mail Order only. C.W.O. P. & P. 10p per order  
Overseas 75p. Money back if not satisfied

### E.R.S.

**ELECTRONIC REPAIR & SERVICES**  
807 LONDON RD., WESTCLIFF-ON-SEA  
ESSEX SOUTHDOWN 77129

### BRAND NEW COMPONENTS

2N3703	2/-	AF116	4/6	NKT163	3/-
2N3705	2/-	AF126	3/-	NKT164	4/6
AF114	4/6	BCY43	3/6	ZF8-2	2/6
AF115	5/-	NKT162	5/-	BZY94	2/6

MIN. POTS 1MΩ, 500K 3/6, 1000μF, 50V 5/6  
HEAT SINKS TOS FINNED 3/-, TO3 2/3  
XTALS SURPLUS 10XJ8790 (70-32) 3/-  
S.A.E. FOR BARGAIN SMALL QUANTITY COMPONENTS, METERS, ETC.  
P. & P. 1/-

### CONSTRUCTORS' COMPONENT KITS

**YOUR SEARCH ENDS HERE!**  
SEND US YOUR COMPONENT LISTS OR ARTICLES AND WE WILL MAKE THEM UP COMPLETE WITH HARDWARE  
**D-B-S ELECTRONICS**  
ONE LETTER GETS YOU THE LOT!  
THE PARADE, CADNAM, HANTS

## RECEIVERS AND COMPONENTS

(continued)

**FULL SPECIFICATION TRANSISTORS:** Texas, S.G.S., etc. BC108B 11p; BC109C 12p; 2N3705 14p; BFY51 17p. 5p Postage S.A.E. List. GREENWELD, 24 Goodhart Way, W. Wickham, Kent.

### PRINTED CIRCUITS

PE 'Gemini' STEREO AMPLIFIER (Dec. 1970)  
Twin Channel Main Amplifier. Stabilised Power Supply.  
Total price 22/6. P.P. 1/6.  
All boards are fibreglass, drilled and tin plated with reverse side screen printed for easy component and connection identification.

SAE for PC board list of other current projects.  
**SERVITRON ELECTRONICS, 18 Beckdale Ave., Poulton-Le-Fylde, Blackpool, Lancs. FY6 8BG**

### TELERADIO ELECTRONICS

JOIN THE FASCINATING HOBBY OF RADIO CONTROL. BUILD A SINGLE CHANNEL SYSTEM FOR ABOUT £12 OR A SOPHISTICATED PROPORTIONAL SYSTEM FOR £80

Details from the specialists: **TELERADIO CO. (P.E.)**  
325-7 FORE STREET, EDMONTON, N.9

### AUDIO EFFECTS

5 SHAW LANE, HALIFAX, YORKS.

Buy with confidence and obtain the right results. Refunds without question if any of our products fail to give 100% satisfaction.

### AMATEUR BANDS ALL TRANSISTOR SUPERHET RECEIVER KIT.

No fuse, no drilling. Just fit the components on our printed circuit. Slow Motion tuning. Simple IF alignment. Perspex front panel. Push pull AF amp drives your 8-15 ohm speaker. Amp can be used separately. Designed to accept a BFO signal. Uses Denco plug in coils. 2T. 0.5 to 1.64 Mhz 3T. 1.67 to 5.3 Mhz 4T. 5.0 to 13 Mhz 5T. 10.5 to 31.5 Mhz Range 3T normally supplied with kit. Uses 9 Volt battery. Easy step by step instructions. Complete Kit. £8.19.6 plus 5/6 P.P. & Ins. Extra ranges 12/- per range.

**POWER CONTROLLER.** Power at your finger tips. Not merely half wave control but full wave. A single variable control gives zero to full power. Uses latest 15 amp 3kW triac and special triggering device. Ideal for all types of lighting, fires, motors, drills, etc. Complete with box, power socket, cables, etc. In kit form with easy to follow instructions £8.9.6. Ready built £9.4.6 plus 5/6 P.P. & Ins.

**REVERBERATION AMPLIFIER.** Self contained transistorised, battery operated. An entirely different approach to sound reproduction. Normally, sound reproduction from a single source, has a flat one dimensional effect. With this unit, proper sound delay through reverberation, tones, are created with a truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug microphone, guitar, etc., in, and the output into your amplifier. Supplied in a beautiful walnut cabinet 7in x 3in x 4in. £10.4.0. P.P. & Ins. 6/-.

**VOX SWITCH.** This sound operated switch is ideal for mobile TX work, tape recorder switching, etc. You speak, it switches. High and medium imp. inputs. AF take off point. Drives your 12 volt relay. In kit form with full instructions 49/6. Ready built, tested and guaranteed. 69/6 post paid.

**METRONOME UNIT.** Variable beat. Listen while you play and keep in time. Easily built, pocket size with personal mini earphone. In kit form 27/6, post paid. Ready built in an attractive polythene case, 37/6 post paid.

**MORSE OSCILLATOR.** PC board, transistors, high stab. components, battery carrier, ear piece. Adjustable tone. Just attach your key. Drives phones or speaker. In kit form 17/6 post paid. Ready built in similar case as above 27/6 post paid.

**STRAIGHT FROM THE PRESS.** Latest Mullard manual: Audio Amps, FM tuners, Stereo decoder, Receiver circuits, Hi Fi, Tape, etc., etc. 32/6 post paid.

**TEXAS TRANSISTORS.** Complementary symmetry. Driver, NPN, PNP output. The set of three ONLY 6/6 post paid.

## BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) 39/6 each. P. & P. 2/9. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) 50/- each. P. & P. 2/9. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.E.), 31 Oliver Road, London, E.17

## WAH-WAH PEDAL KIT

**SELECTIVE AMPLIFIER MODULE.** The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design, £1.75. (35/-) Assembled and tested module £2.13. (42/6)

**FOOT VOLUME CONTROL PEDAL.** Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module.

Pedal unit now only £5.13. (£52.6)  
Complete kit for Wah-Wah pedal now only £6.50. (£6.10.0)

All post free.

Send 15p (3/-) for our catalogue of components, testmeters, musical electronics and more details of the above items.

Callers welcome.

**WILSIC ELECTRONICS LIMITED**  
6 COPLEY ROAD, DONCASTER  
YORKSHIRE

If you have difficulty  
in obtaining


## PRACTICAL ELECTRONICS

Please place a regular  
order with your news-  
agent or send 1 year's  
subscription (£2-5-0) to

Subscription  
Department

Practical Electronics  
Tower House  
Southampton Street  
London, W.C.2

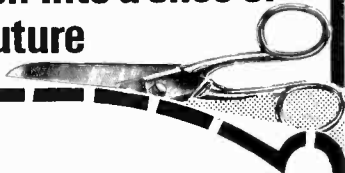If you're a telecommunications man and match up to the qualifications below cut yourself into a slice of Britain's future



Become a

# Radio Technician

in the fast-growing world of Air Traffic Control

Please send me an application form and details of how I can join the fascinating world of Air Traffic Control Telecommunications

Name .....

Address .....

PET/E3

Not applicable to residents outside the United Kingdom

To: A J Edwards, C Eng, MIEE,  
The Adelphi, Room 705, John Adam Street,  
London WC2N 6BQ,  
marking your envelope 'Recruitment'

**Sending this coupon could be your first step to a job that's growing in importance every year.**

The National Air Traffic Control Service needs Radio Technicians to install and maintain the vital electronic aids that help control Britain's ever-increasing air traffic.

This is the kind of work that requires not only highly specialised technical skills but also a well developed sense of responsibility, and candidates must be prepared to undergo a rigorous selection process. Those who succeed are assured a steadily developing career of unusual interest and challenge. Starting salary varies from £1044 (at 19) to £1373 (at 25 or over); scale maximum £1590 (higher rates at Heathrow). There is a good annual leave allowance and a non-contributory pension for established staff.

You must be 19 or over, with at least one year's practical experience in telecommunications, ('ONC' or 'C and G' qualifications preferred).

## NATCS


National Air Traffic Control Service

# NOW AVAILABLE LASKY'S AUDIO TRONICS CATALOGUE 1971

THERE'S MORE &  
MORE & MORE  
FOR EVERYONE!

The great new 1971 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 44 newspaper size pages—many in full colour—are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio accessories, and introduces LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

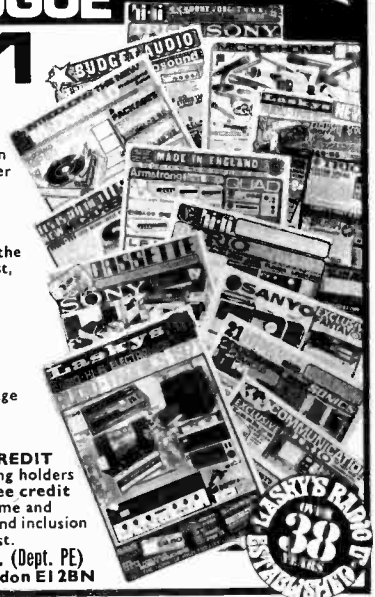**LASKY'S RADIO LTD. (Dept. PE)**  
3-15 Cavell Street, London E1 2BN



## VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 3R4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for 20/6. DAF96, DF96, DK96, DL96, 4 for 29/-

1A7GT 7/6	26L6GT 5/-	DL35 5/-	EL84 4/9	PCL82 7/3	UAF42 10/3
1H6GT 7/8	28U4GT11/6	DL92 5/9	EL90 5/3	PCL83 12/-	UBC41 10/6
1N6GT 7/9	30F11 6/6	DL94 7/6	EL500 13/6	PCL84 7/6	UBF80 5/9
1R5 5/9	30C15 12/9	DL96 7/3	EM80 8/3	PCL85 9/-	UBF89 6/9
185 4/3	30C17 16/-	DY86 5/9	EM81 8/3	PCL86 8/3	UCC84 7/-
1T4 3/-	30C18 13/6	DY87 5/9	EM84 6/9	PCL88 14/6	UCC85 7/3
384 5/9	30F5 15/6	EAC80 6/6	EM87 7/6	PCL80015/6	UCF80 7/3
3V4 7/6	30FL1 12/9	EAF42 10/-	EY61 7/3	PEN44 8/6	UCH42 12/6
5Y3GT 6/-	30FL1214/6	EB91 2/3	EY86 6/6	PEN86C14/-	UCB41 6/6
5Z4G 7/9	30FL14 14/-	EB33 5/-	EZ40 8/9	PFL20011/9	UCL82 7/-
6/30L2 11/9	30L1 6/6	EB41 10/6	EZ41 8/9	PL36 9/9	UCL83 11/-
6AL5 2/3	30L15 13/-	EB90 4/6	EZ80 4/6	PL81 9/3	UF41 12/6
6AM6 2/9	30L17 14/9	EBF80 6/9	EZ81 4/6	PL81A 10/3	UF89 6/9
6AQ5 5/3	30P4 13/-	EBF89 6/3	GZ32 8/9	PL82 6/-	UL41 12/-
6AT6 4/6	30P12 13/9	ECC81 3/9	GZ34 9/9	PL83 7/-	UL44 20/-
6AX6 4/6	30P19 13/-	ECC82 4/9	KT41 15/6	PL84 6/6	UL84 7/-
6BA6 4/6	30PL1 12/9	ECC83 7/-	KT61 9/9	PL500 13/-	UM60 5/-
6BE6 4/9	30PL13 14/6	ECC85 5/9	KT66 16/9	PL504 13/6	UM84 4/6
6BQ6 8/6	30PL14 14/-	ECC80A 12/-	LN319 12/9	PL508 23/6	UY41 8/3
6CD6G 22/-	30PL15 14/6	ECF80 6/-	LN329 14/6	PMS4 7/6	UY85 5/9
6F14 9/-	36L6GT 8/9	PCF82 6/-	LN339 12/9	PX25 23/6	VP48 15/9
6F23 13/9	36W4 4/6	ECH35 6/-	N78 12/6	PY32 11/-	W19 7/-
6FAZ 12/6	3Z4GT 5/-	ECH42 12/9	PAB80 7/-	PY33 11/-	Z77 3/6
6K7G 2/6	807 9/-	ECH81 5/9	PC86 10/3	PY81 5/3	AC107 3/6
6K8G 3/6	6063 12/6	ECH83 8/3	PC88 10/3	PY82 5/3	AC127 3/9
6SN7GT 4/6	AC/VP215/8	ECH84 7/6	PC96 8/6	PY83 5/9	AD140 7/6
6SL7GT 5/8	AZ31 9/6	ECL80 7/-	PC97 8/-	PY88 6/9	AF116 4/-
6V6G 3/6	B349 13/-	ECL82 6/9	PC90 7/6	PY800 7/6	AF116 4/-
6V6GT 6/6	B729 12/6	ECL86 8/-	PC94 6/6	PY801 6/6	AF117 4/6
6X4 4/9	CL33 13/6	EF37A 6/6	PC85 6/-	R19 6/6	AF118 9/9
6X6GT 5/9	CY31 6/9	EF41 11/9	PC88 9/9	R20 13/-	AF125 3/6
10F18 7/-	DAC32 7/3	EF80 4/6	PC89 9/9	U26 13/9	AF127 3/6
10F13 12/-	DAF91 4/3	EF85 6/3	PC80813/-	U47 13/9	OC44 2/6
12A8 11/9	DAF96 7/3	EF86 6/3	PCF50 6/8	U49 13/-	OC45 2/6
12A7 3/9	DF96 7/3	EF89 5/3	PCF82 6/-	U78 4/9	OC71 2/6
12AU7 4/9	DF91 3/-	EF91 2/9	PCF86 9/8	U191 12/6	OC72 2/6
12AX7 4/9	DF96 7/3	EF183 5/9	PCF80013/6	U193 8/6	OC75 2/6
12X6GT 7/3	DH77 4/6	EF184 6/6	PCF801 6/9	U251 14/6	OC81 2/6
19B6G617/6	DK32 7/6	EH90 8/6	PCF802 9/-	U301 10/6	OC81D 2/6
20F2 13/6	DK91 5/9	EL33 9/9	PCF806 13/6	U325 14/6	OC82 2/6
20P3 11/9	DK92 8/6	EL34 9/9	PCF80813/3	U801 19/6	OC82D 2/6
20P4 13/6	DK96 7/3	EL41 11/-	PCF80814/-	UABC80 6/6	OC870 4/6

## READERS RADIO (P.E.)

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441

Postage on 1 valve 9d. extra. On 2 valves or more, postage 6d. per valve extra. Any Parcel Insured against Damage in Transit 6d. extra.



Send 1/- for New Comprehensive I.C. and Semiconductor price list (24 pages)

# INTEGRATED CIRCUITS

NEW LOW PRICES • FULLY GUARANTEED

IC#	PRICE	MOTOROLA	1-9	10+	25+	MULLARD	
CA3000	36/-	MC7083	18/3	10/8	15/4	LINEAR	
3005	23/6	MC724P	13/3	11/1	TAA241	32/6	
3007	23/6	MC788P	16/6	13/9	242	85/-	
3011	14/9	MC785	13/3	11/1	243	30/-	
3012	17/9	MC790P	13/3	20/8	253	15/6	
3013	21/-	MC792P	13/3	11/1	293	19/6	
3014	24/9	MC799P	13/3	11/-	300	35/-	
3018	16/9	MC1303L	54/-	45/-	310	25/-	
3018A	22/-	MC1304P	72/-	60/-	320	14/6	
3019	16/9	MC388P	109/9	91/6	350	35/-	
3020	25/3	MC1353A	89/-	76/9	455	29/6	
3020A	32/-	MC1435L	89/-	57/6	521	26/6	
3021	31/3	MC1709C	19/-	16/6	522	72/-	
3022	26/-	Data sheets 2/6 extra			530	89/-	
3023	25/3				811	89/-	
3026	20/-	FAIRCHILD			TAB101	19/6	
3025A	14/9	1.900	8/8	8/-	TAD100	39/6	
3028B	21/-	L914	8/6	8/-	TAD110	39/6	
3029	17/6	L923	12/6	11/9			
3030	27/6	702C	22/6	21/-	17/-	MULLARD DTL	
3035	24/6	709A	15/-	13/6	13/-	FCH101	17/6
3036	14/6	710C	15/-	13/6	13/-	FCH121	21/-
3039	16/9	711C	15/-	13/6	12/6	FCH201	26/6
3041	21/9	716C	56/-	50/-	11/-	FCH231	30/-
3042	21/9	741C	19/6	18/6	17/-	FCJ101	32/6
3043	27/6	N.B. 709C and 741C TO-5 or DIL package			15/-	FCJ111	31/-
3044	24/-					FCJ201	36/-
3045	24/6	TEXAS TTL				FCJ311	55/-
3046	16/3	SN7400N	10/-	FJH101	17/6	FCX101	87/6
3047	27/6	SN7401N	10/-	FJH121	17/6	FCY101	21/-
3048	40/9	SN7402N	10/-	FJH141	17/6		
3049	32/-	SN7403N	10/-	FJH161	17/6		
3050	36/9	SN7404N	10/-	FJH181	18/3		
3051	26/9	SN7405N	10/-	FJH221	17/6	PLESSEY	42/6
3052	33/-	SN7410N	10/-	FJH101	27/6	SL701C	20/-
3053	9/3	SN7413N	10/-	FJH121	37/6	SL702C	20/-
3054	21/9	SN7420N	10/-	FJH141	62/6		
3055	49/-	SN7441N	52/6	FJH191	37/6	GENERAL ELECTRIC	87/6
3059	33/-	SN7490N	10/-	FJH251	62/6	PA220	25/6
3064	24/-	SN72709P	17/6	FJY101	16/-	PA234	21/6

DATA SHEETS ALL 1/- PER TYPE EXCEPT L900, 914/923 AND PLESSEY 2/6.  
 8 Pin TO-5 I.C. Holders, 10/8  
 14 Pin Dual-In-Line I.C. Holders, 6/6  
 16 Pin Dual-In-Line I.C. Holders, 9/-  
 Post & Packing 2/- per order.  
**A. MARSHALL & SONS LTD.** 21422  
 28 CRICKLEWOOD ROADWAY, LONDON, N.W.2  
 CALLERS WELCOME 9-5.30 SATURDAY 9-5  
 SEE OUR MAIN ADVERTISEMENT ON PAGE 169 FOR SEMICONDUCTORS

## Selections from FELSTEAD ELECTRONICS' Winter List

(Sent free for stamped addressed envelope to address below)

**Transistors, etc.** AC126 2/6, AF116 3/6, AF116 3/6, AF117 4/-, OA5 1/6, OA10 1/6, OA11 1/6, OA6 1/6, OC23 6/6, OC23 8/6, OC29 7/6, OC28 8/6, OC35 8/6, OC44 2/9, OC45 2/6, OC71 2/6, OC72 2/6, OC75 2/6, OC81 2/6, OC811 2/6, OC82D 2/6, OC176 4/-, OC171 2/6. Many more in list. **S.D.R.** BY100 800pF 2/10. **6 Amp series:** BY713 300 pF 4/-. BYZ12 600pF 5/-. BYZ11 900pF 6/-. BYZ10 1200pF 7/- (charges 1/- unit to 11, paid for 12 and over). **Sub-Min Transformers:** OUTPUT (3Ω for OC73, etc.) 2/9 (Up to 6 1/2). **MULTIMETER.** Our famous 20000 Ω per V £4.12.6 (2/6). Details and other in list. **SOLDERING IRON.** Slim, modern, British high-speed 81", all parts replaceable, highest quality, fully guaranteed: 21/- (1/6). **DIAMOND SYLLI Replacements** for BBR TC8/LP, TC8/S, TUBELPSTEREO; COLLARO 00; RONETTE BP40LP; GAR-RARD GC2/LP and GC8/LP; ACOS GP63/67, all at 7/6 (1/-); ACOS GP73, GP91; HARR-STA (8T3, 8T5), 8T8 (8T9); SONOTONE STA, 9TA, 9TAC; PHILIPS AG3306, 3060 (3063, 3066, 3301, 3302, 3304); Garrard GKS26 all at 15/- (1/-). All are of the very highest quality. **Double Diamond:** ST4 (8T3, 8T5); ST10 (8T3, 8T8); 9TA, 9TAC, 3306, GP91 (For GP92, GP93, GP94 cartridges); GP918C for all GP91-9C cartridges; All at 30/- each (1/-). **PICK-UP CARTRIDGES** All standard fittings and stylus. **MONO** (PG67) 15/- **STEREO-COMPATIBLE (MONO) GP91/SC (21/-)**. **STEREO GP99 26/6**. **STEREO CERA-MIC GP94 38/6**. **SONOTONE STEREO 9TAC (DIA.) 47/6**. **GOLDRING 6850 87/6** (880 22.10.0). **G800E £13.10.0**. **G800 SUPER E £18.10.0** (1/- all types). Reg. Post 4/- **SYLLI FOR ALL ABOVE TYPES**, including GOLDRING available. **RECORDING TAPE.** Still the finest quality British Mylar available: Standard 5" 600 ft. 7/3 5" 900 ft. 10/- 7" 1200 ft. 11/2. **LONG PLAY** 5" 900 ft. 10/- 7" 1200 ft. 11/2 1800 ft. 12/6 (1/3 on 5" and 5 1/2" 1/6 on 7"). **MICROPHONES** Crystal Mic. 12" hand/desk 16/8. MIC45 Curved metal hand/pig 20/-. CM21 Grey hand/desk 10/8. Stick 60" 20/8 CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands 29/8 (All 1/6 LAPEL or hand) with clip 6/6 (1/-). All are fitted with leads. **Dynamic.** Cream hand/tablet MINY 16/6 (1/6) MS10, 50K Ω for desk, tapered with base and slide-out adaptor 39/6 MS11, similar, but fixed on swivel swan neck to switch-fitted base 42/6. (Either 2/6). Type 209 Cartridge has money card but 2/6. DM160 Non-Dir. Ball, 50K Ω, switch, cable, adaptor 77/6 (5/- either). **MICROPHONE INSERTS.** Dia. 1.75" OR 0.9" either size 5/6 (1/-). **EARPIECES** with lead & min. jack plug (2.5 or 3.5mm, state which) Magnetic 1/8 Crystal (3.5 only) 4/9. (1/- to 3 for 1/- on any). **HEADPHONES** De Luxe STEREO 8-16 ohms, 47/6. Same, fitted vol. control each earpiece, 67/6. Both have lead and stereo jack plug, (3/-). **HIGH RES.** 2000 ohm. Adjustable 18/6 (2/-) **SPARKERS.** 12" 8Ω full tweeter, 3" 15 Ω (state which) 37/6 (5/6) or for Stereo 80/- pair, car. paid. 2 1/2" 3 OR 8 Ω (state which) 7/8 (1/2) 2 1/2" powerful transistor replacement, high ohms 6/- (1/-). **EMI 13" x 8" x 3" or 15 Ω (State which) 42/6** (4/6) with single flared para. tweeter cone 8 or 15 Ω (state which) 45/6 (4/6); with two tweeters and crossover network 8 or 15 Ω (state which) 75/- (5/-). **VIBRATORS.** Genuine Plessey 12V 4-pin non-synch. 121H04, 2 1/2" ex. pins 5/6. Am. 12V 4-pin, non-synch. 716ths, longer. 4 1/2 12V 7-pin synch. (28R7) 12/6 (All types 1/- per vibrator). **CONNECTING WIRE.** Packs of 5 coils std. coils, ea. coil 50c. Solid core 2/8 (1/-). Flexible 3/8 (1/3). Super thin for transistor wiring 3/3 (1/-). **PICK-UP WIRE.** Super thin twin flex, screened and sheathed 1/3 yd. (1/- up to 6yds., over, free). **RETRACTABLE Flex. Leads.** (Cables) 6ft, phono plug ea. end 4/6. 12ft. 7/8. 6ft. phono plug/phone socket other end 5/- 12ft. 8/8 (1/- per lead, all types). **SEND SAE** for full free lists—Teleton and small 3W and 7W trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aerials, Meters, Test prods, all types of Brit. & cont. standard and min. plugs and sockets, SDR's, Thyristors, eroc, clips (various), terminals, etc. etc. and many "Special Offer" lines at lowest possible prices.

**FELSTEAD ELECTRONICS (PE38)**  
 LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE  
 Cash with order only. No COD or Caller Service. Charges (Min. 1/-) in brackets after all items. Regret Orders under 5/- unacceptable. SAE please for enquiries or cannot be replied to. Charges apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

# YATES ELECTRONICS

(FLITWICK) LTD.

**RESISTORS**  
 High stability carbon film. Very low noise. 0.5W 5% 4-7Ω to 2.2MΩ 2.5d each, 100 + 2d each, 0.5W 10% 4-7Ω to 10MΩ 2d each, 100 + 1.75d each. Quantity price applies for any selection. Ignore fractions on total order.

**DEVELOPMENT PACK**  
 0.5 watt 5% resistors 5 off each value 4-7Ω to 1MΩ  
 325 resistors E12 series 50/-.  
 650 resistors E24 series 100/-.

**MULLARD POLYESTER CAPACITORS C296 SERIES**  
 400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 6d.  
 0.0068μF, 0.01μF, 0.015μF, 0.022μF, 0.033μF, 7d. 0.047μF, 9d.  
 0.068μF, 0.1μF, 10d.  
 160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 7d.  
 0.1μF, 9d. 0.15μF, 0.22μF, 10d. 0.33μF, 1/3. 0.47μF, 1/6.  
 0.68μF, 2/3. 1.0μF, 2/6.

**MULLARD POLYESTER CAPACITORS C280 SERIES**  
 250V: P.C. mounting miniature 20%: 0.01μF, 0.015μF, 0.022μF, 7d. 0.033μF, 0.047μF, 0.068μF, 8d. 0.1μF, 9d.  
 0.15μF, 0.22μF, 1/- 0.33μF, 1/4.

**MYLAR FILM CAPACITORS**  
 100V: 0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 6d. 0.05μF, 0.1μF, 8d.

**CAPACITOR DEVELOPMENT PACK**  
 Selection of ceramic and polyester capacitors 100pF to 1.0μF.  
 Total 100 capacitors, £2.18.0.

**MINIATURE ELECTROLYTIC CAPACITORS**

50μF	6V	16μF	10V	10μF	12V	40μF	16V	16μF	40V
100μF	6V	64μF	10V	16μF	12V	6.4μF	25V	50μF	40V
100μF	6V	125μF	10V	50μF	12V	25μF	25V	2.5μF	64V
320μF	6V	200μF	10V	100μF	12V	8μF	40V	10μF	64V

**POTENTIOMETERS**  
 5kΩ to 1MΩ log or linear, 2.6.  
**GANGED STEREO POTENTIOMETERS**  
 1/2 watt carbon track 5kΩ + 5kΩ to 1MΩ + 1MΩ log or linear 8/- each.

**SKELETON PRE-SET POTENTIOMETERS**  
 Linear: 100, 250, 500 ohms and decades to 5M ohm 20%  
 ≤ 250kΩ, 30%, 250kΩ. Horizontal or vertical P.C. mounting (0-1 matrix). Sub-miniature 0-1 watt 10d each. Miniature 0-3 watt 1/- each.

**TRANSISTORS**

AC126 3/6	BC108 2/6	2N2926 2/3	2N3707 3/8
AC127 3/6	BC109 2/9	2N3055 1/6	2N3708 2/6
AC128 3/6	BFY50 4/6	2N3702 3/-	2N3709 2/3
AD140 8/6	BFY51 3/9	2N3703 2/10	2N3710 2/5
AF115 3/6	BFY52 4/6	2N3704 3/6	2N3711 2/10
AF117 3/6	BSY56 6/6	2N3705 3/-	ORP12 4/6
BC107 2/9	BSX21 5/6	2N3706 2/5	ZTX302 9/6

**DIODES**—OA85, OA91, OA202, 1/6 each  
**ZENER DIODE**  
 400mW 5% 3.3V to 30V 3/6

**SILICON RECTIFIERS**

IN4001 50V IA	1/6	IN4006 800V IA	3/6
IN4002 100V IA	2/-	IN4007 1000V IA	3/6
IN4003 200V IA	2/3	BY124 100V 1/4	1/3
IN4004 400V IA	2/6	BYZ10 800V 6A	7/6
IN4005 600V IA	2/9	BYZ13 200V 6A	4/6

**VEROBOARD**

0-15	0-1	0-15	0-1
Matrix	Matrix	Matrix	Matrix
2 1/2 x 3 1/2	3/3	4/6	17 x 3 1/2 (plain)
2 1/2 x 5	4/9	4/9	17 x 2 1/2 (plain)
3 1/2 x 3 1/2	4/9	4/9	2 1/2 x 5 (plain)
3 1/2 x 5	5/6	5/6	2 1/2 x 3 1/2 (plain)
17 x 3 1/2	15/-	—	Pin insertion tool
17 x 2 1/2	11/6	—	Spot face cutter
17 x 5 (rotary)	15/-	—	Pkt. 36 pins

**JACK PLUGS AND SOCKETS**


Standard Screened	3/6	2.5mm Insulated	1/6
Standard Insulated	2/9	3.5mm Insulated	1/6
Stereo Screened	7/-	3.5mm Screened	2/6
Standard Sockets	3/-	2.5mm Socket	1/6
Stereo Sockets	3/6	3.5mm Socket	1/6

**BRUSHED ALUMINIUM PANELS**  
 Self adhesive backing approx. 13 x 2 1/2 2/-.

**EXPORT ENQUIRIES WELCOME**  
 C.W.O. please. 1/6 post and packing on orders under £1.  
 C.W.O. please. 1/6 post and packing on orders under £1.

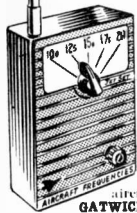**8E39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD**

**LISTEN TO AIRCRAFT COMMUNICATIONS**  
new **V.H.F. AIRCRAFT BAND CONVERTER**



ONLY **47/6**

Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting conversations between pilots, ground approach, ground control, airport towers. Hear for yourself the disciplined voices of jet engines as take down. Be with them when they have to take nerve rippling decisions in emergencies, tune in to the international distress frequency. Covers aircraft frequency band including HEATHROW, GATWICK, LUTON, BINGWAY, PRESTWICK, ETC. This fantastic fully transistorised instrument can be built by anyone in under two hours. (Our design team built four - everyone worked first time). No soldering necessary. Fully illustrated simply worked instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2in x 3in x 1 1/2in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radio). NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. SEND NOW. ONLY 47/6 for all parts, including case, nuts, screws, wire, etc. (parts available separately).

"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS—TEST THEIR MENTAL ABILITY, ETC. ASTONISHING



**ELECTRONIC BRAINBOX**


ONLY **57/6**

If you've seen a giant computer on show at an electronics exhibition, you will have seen people of all ages queuing to pit their abilities against the giant electronic brain. There is tremendous fascination that attracts ordinary people and professional engineers alike to electronic games of skill, chance and mystery. With this "Brainbox" you will be able to perform mind-boggling feats. THE MIND READING DEVICE will make people swear you have telepathic powers. THE AMAZING CARD TRICK UNIT completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. THE ELECTRONIC NERVES TESTER puts your friends to a very lively test. It gives out faint finish signals (the winner is the person with lowest number of full signals). Can be adjusted from the weakest to strongest person. THE ELECTRONIC MAZE tests the mental ability of the player because it uses psychology with electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 18in x 12in x 6in (Max.) You can play all these games and more beside. WE GUARANTEE THAT ANYONE CAN EASILY ASSEMBLE THESE PROJECTS IN UNDER ONE HOUR! No soldering, pictorial, step-by-step illustrated instructions. ONLY 57/6 plus 6/6 P. & P. for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. etc. Uses standard PP3 battery. (PARTS AVAILABLE SEPARATELY). FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.

Examine at home for 7 days. Your money back if not delighted.

**CONCORD ELECTRONICS LTD.** (P.E.15) · 8 WESTBOURNE GROVE · LONDON · W.2  
(Near Bayswater Tube) Callers welcome. 9-6 including Saturdays

**REAL WORKING ELECTRONIC ORGAN**

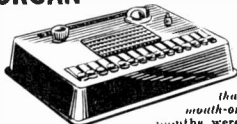

ONLY **55/-**

Don't confuse with ordinary electric organs that simply blow air over mouth-organs tape reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised, no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne" and lots of similar tunes on this real working electronic organ. Size 13 1/2in x 10in x 2 1/2in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. Play it anywhere. No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. ONLY 55/- + 4/6 P. & P. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

**FIND BURIED TREASURE!**

**TREASURE LOCATOR—NOW IT'S HERE AT LAST.**



after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototype, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects. It signals exact location (no phones used—uses only transistor radio which clips inside—no connections needed). **FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head 13 1/2in x 10in x 2 1/2in. **Great demand expected at this remarkably low price**—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now 47/6 plus 6/6 P. & P. (Telescopic handle as illustrated 25/- extra.) Parts available separately. Made up looks worth £15.

ONLY **47/6**

**ENAMELLED COPPER WIRE**

S.W.G.	1/2lb. Reel	1lb. Reel
18-22	11s. 3d.	16s. 6d.
23-30	11s. 9d.	17s. 6d.
31-35	12s. 3d.	18s. 6d.
36-40	15s.	24s.
41-44	17s. 9d.	29s. 6d.

Orders despatched by return of post.  
Please add 1/- per item P. and P.

Supplied by:  
**BANNER TRANSFORMERS**  
(Dept. PE), Brooks Street  
Higher Hillgate, Stockport, Cheshire

**Build the Hardcastle-Texas Amplifier**

Choose output power from 10-30 watts, output impedance either 8 or 15 ohms. 3dB response 10Hz-40kHz.

Design and Application Book, lists all components and wiring 6/6 (inc. P. & P.)  
Printed circuit board for stereo

use, 2 pre amp. and 2 power amp. locations, drilled, silk-screened fibre glass £2.

Gueneo Texas Transistors

BC182L	4/-	TIP31a	17/6
BC184L	4/-	TIP32	19/-
BC212L	5/-	TIP32a	23/9
BC214L	5/-	TIP33	30/-
BF244B	13/-	TIP33a	32/6
1S3030A	3/-	TIP34	61/-
TIP31	16/6	TIP34a	66/-

Postage and packing free for orders over £2, otherwise add 5/-.

**OMNI**  
components Ltd.  
P.O. Box 43, Woking, Surrey

**AMPLIFIER & PREAMP PRINTED CIRCUIT BOARDS FOR MULLARD CIRCUITS**

High quality Printed Circuit Boards for the following circuits shown in the Mullard publication Transistor Audio and Radio Circuits.

10 W high quality audio amplifier	(p.102)	13/2d
25 W high quality audio amplifier	(p.106)	14/0d
10/25 W high quality audio preamplifier	(p.108)	14/7d

Price each including postage and packing. Cash with order.

All boards are tinned to prevent oxidation and to aid soldering and have the component identification printed on the reverse.

**BIBOND PRINTED CIRCUITS LTD.**  
Terminus Road, Chichester, Sussex

# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.L.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomm.**  
C. & G. Telcomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT—SO COULD YOU

"My income has almost trebled... my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept 316A, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept 316A, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name ..... Age .....

Address .....

Occupation .....

**B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**


# HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES

HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER




## BUILD YOURSELF A QUALITY RADIO

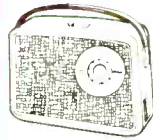

Excellent printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6.19.6. p.p. 6/6. All parts sold separately. Ask for Leaflet No. 1.
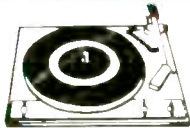
## YOU CAN SAVE 25%

on Garrard, Goldring and McDonalds Decks.



*SL65B	£14. 9.6.
*SL72B	£25. 0.0.
MP610	£13.19.6.
GL75	£32. 0.0.

*SP25 Mk III	£11.15.0.
*AP75	£16.19.6.
MP60	£10.19.6.
GL69 II	£23. 0.0.

(p.p. 7/6 any type)

### PLINTHS AND COVERS

\* Standard 89/6 p.p. 4/6. \* Deluxe £8.15.0. p.p. 6/6.  
† Deluxe £8.15.0. p.p. 6/6.

**SPECIAL OFFER!** The above decks supplied with 9TAH/C Diamond, add £2; 940 magnetic, add £3; G850 or AT66, add £5; G800, add £7.10.0; GP91 SC, add £1 (Also applies to MP60/PC).

**SPECIAL!** SP25 fitted G800 with plinth/cover wired and mounted, £20.19.6. p.p. 10/- Mk III, £22.10.0. 2025TC with 9TAH/C diamond, plinth and cover wired and mounted, £13.19.6. p.p. 10/- GL69 II fitted G800 plinth and cover wired and mounted, £35.0.0. p.p. 12/6.

Also in Stock—2025TC/9TAHC diam., £8.17.6; 3000 LM 9TAHC diam., £9.15.0; 3500/K540A, £12.10.0; MP60 fitted plinth and cover (see above for cartridges), £17.12.6. p.p. 10/-  
\* FREE—Complete Lists Nos. 16/17 on request.

## SINCLAIR SAVE £££'s

### PROJECT 60 PACKAGE DEALS


2xZ30 amplifier, stereo 60 pre-amp, PZ5 power supply, £19.0.0. Carr. 7/6. Or with PZ6 power supply, £21. Carr. 7/6. 2xZ50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £21.10.0. Carr. 7/6. Transformer for PZ8, 59/6 extra. Any of the above with Active Filter unit add 97/6 or with pair Q16 speakers add £16. \* NEW FM TUNER, £12.19.6.

## BUILD THIS VHF FM TUNER



5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. PARTS TOTAL COST £6.19.6. p.p. 3/6. MULTIPLEX DECODER £5.19.6 (FOR STEREO) p.p. 3/-  
Ask for Brochure No. 3.

## ELECTRONIC ORGANS

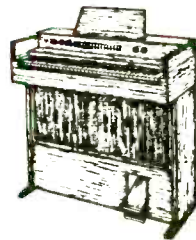

You can build our Mayfair Portable for

£99. p.p. 30/-

All parts available separately—several models to choose from—visit our new showrooms at 309 Edgware Road.

## DISCOTHEQUE —PA CENTRE

All the latest equipment in stock. Call and see for yourself or send for latest lists.



## HENRY'S LATEST CATALOGUE

Latest edition. Now 350 pages. \* COMPONENTS, TEST GEAR \* EQUIPMENT, MODULES \* SPECIAL OFFERS. Etc., Etc. Everything for the constructor. Complete with 10/- value discount voucher for use with purchase. Price 7/6. p.p. 2/-  
WHY NOT SEND AWAY TODAY? FREE 8-page SEMI-CONDUCTOR LIST No. 36. New ranges and a few circuits.

## HI-FI TO SUIT EVERY POCKET

FREE—Stock Lists Nos. 16/17 on request—BEST VALUE IN U.K.

## 100 STEREO SYSTEMS



and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only).

## SPECIAL STEREO SYSTEMS

C5/8 Teleton 203E. 6+6W amplifier, SP25 or MP60 with deluxe plinth/cover, pair of 3-way 10W bookshelf speakers, all cables, leads, magnetic cartridge (List £79.10.0). PRICE £59. p.p. 30/-

C1/8 Nova 505 Amplifier, 2025TC with 9TAH/C diamond, plinth and cover, pair of 3-way 10W bookshelf speakers, cables/leads, etc. (List £65). PRICE £49. p.p. 30/-

C9A/8 Sinclair 2000 amplifier, SP25 or MP60 with G800, plinth and cover, pair of 3-way 10W bookshelf speakers, cables/leads, etc. (List £88). PRICE £69. p.p. 30/-

B11/8 Teleton F2000 (or F2300) MW/FM/STEREO Tuner amplifier, SP25 or MP60 with 9TAHC diamond, pair of 3-way 10W speakers, cables/leads, etc. (List £100). PRICE £79. p.p. 30/-


(All systems add £12 for Dentons, £19 for Super Lintons.)

## FREE LISTS OF 100 STEREO SYSTEMS.

STEREO HEADPHONES (P. & P. 3/-) 8 + 8 ohms. Soft padded earpieces. DHO25 45/-; SE20 £5.19.6; AES20 £7.10.0; K6 £11.5.0; SE50 £14.19.6; PRO4AA £25.
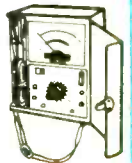
## TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE

- AF105 50k/V multimeter (illus.). Price £8.10.0. p.p. 3/6. Leather case 28/6.
- 200H 20k/V. Price £3.17.6. p.p. 3/6. Case 12/6.
- 500 30k/V multimeter. Price £8.17.6. p.p. 3/6. Leather case 30/-
- THL33 2k/V. Price £4.2.6. p.p. 3/-
- Leather case 22/6.
- TE65 Valve voltmeter (illus.). £17.10.0. p.p. 7/6.
- SE250B Pocket pencil signal injector 35/- p.p. 1/6.
- SE500 Pocket pencil signal tracer 29/6 p.p. 1/6.
- TE20D RF generator. Price £15. p.p. 7/6.
- TE22D Matching audio generator. Price £17. p.p. 7/6.
- TE15 Grid dip meter. Price £12.10.0. p.p. 3/6.
- TO3 Scope 3in tube. Price £37.10.0. p.p. 10/-
- TE22 Audio Generator. £17. p.p. 8/6.



## NEW SELF-POWERED PREAMPLIFIERS



Designed for use with PA25 and PASO Amplifiers.


GOLD AND SILVER FINISH. Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.

\* FET9/4. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.10.0. p.p. 4/-

\* FET154 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.10.0. p.p. 4/6.

\* I.C. STEREO All facilities plus headphone socket without amplifiers. Uses IC's, FET's, etc. Price £24.0.0. p.p. 5/6.

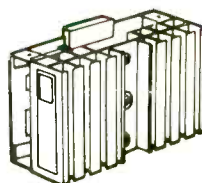SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS, FET's and IC's. DIN SOCKETS, ETC. fitted. Self powered PUSH-BUTTON SELECTION, 20dB BASS AND TREBLE BOOST AND CUT. All inputs provided plus TAPE RECORD and REPLAY.



## 25 WATT & 50 WATT SILICON AMPLIFIERS

### LOOK AT THE SPECIFICATIONS!

- At full power 0.3% distortion.
- Rise time 2usec.
- At full power—1dB 11c/s to 40 kc/s.
- Short circuit proof plus limiting cct.
- Response—1dB 11 c/s to 100 kc/s.

PA25 10 transistor all silicon differential input 400mV sensitivity. 25W Rms into 8 ohms. Supplied with edge connector harness size 5in x 3in x 2in.  
PA50 12 transistor version 50W Rms into 3 to 4 ohms. Size 5in x 3in x 4in.  
MU442. Power supply for one or two PA25 or one PA50.  
PA25. £7.10.0. PA50. £9.10.0. MU442. £6. P. & P. 4/6 each.

## SIMPLICITY TO MOUNT EASY TO USE

All units no soldering — just edge connectors and plugs

DESIGNED FOR QUALITY, PERFORMANCE AND PRICE  
As specified for many "Practical Wireless" 1970 projects

Electronic Components & Test Gear Centre  
356 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402-4736

High Fidelity Sales & Demonstrations Centre  
354 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-402-5854

Electronic Organs,  
P.A. & Discotheque Centre  
309 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723-6963

Mail Order and Industrial Sales Dept.  
303 EDGWARE ROAD,  
LONDON, W.2.  
Tel: 01-723-1008/9

OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY — 9 a.m. to 1 p.m. THURSDAYS — OPEN ALL DAY SATURDAY