

PRACTICAL

# ELECTRONICS

APRIL 1971

17½p (3/6)

## AURORA

MUSIC  
INSPIRED  
LIGHT AND  
COLOUR

*Also inside*

- ★ BOAT SPEED INDICATOR
- ★ DOOR YODELLER

# ADCOLA Soldering Instruments add to your efficiency

## ADCOLA 64

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.

Standard temp. 360°C at 23 watts.

Special temps. from 250°C—410°C.

### \*Additional Stock Bits

(illustrated) available

#### COPPER

B 38  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{1}{16}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{4}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE

B 42 LL  $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 33 LL  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{3}{32}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{16}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service... reliability... from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\* Write for price list and catalogue



**ADCOLA PRODUCTS LTD.,**

(Dept. L.), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4.

Telephone: 01-622 0291/3 - Telegrams: Soljoint London Telex - Telex: Adcola London 21851

# NOW AVAILABLE LASKY'S AUDIO TRONICS CATALOGUE 1971

THERE'S MORE & MORE & MORE FOR EVERYONE!

The great new 1971 edition of Lasky's famous Audio-Tronics catalogue is now available FREE on request. The 44 newspaper size pages many in full colour are packed with 1000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast, Electronics Hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals), Tape recording and Audio accessories, and introduces LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME offering holders one month's interest free credit up to £50. Send your name and address and 15p for post and inclusion on our regular mailing list.

**LASKY'S RADIO LTD.** (Dept. PE)  
3-15 Cavell Street, London E1 2BN



## PRACTICAL ELECTRONICS

Specify

**CONTIL MOD-2 CASES**



PRACTICAL ELECTRONICS specify CONTIL MOD-2 CASES for housing the P.E. GEMINI AMPLIFIER, P.E. AURORA LIGHT DISPLAY SYSTEM, P.E. DIGITAL CLOCK. Also available ready punched for Sinclair Project 60, with or without active filter unit. Full kit of hardware is also available, including capacitors, for use with Z30 or Z50 at £3.63.

PVC COATED MATERIALS, PVC easy to clean, surface is scuff resistant. PVC/ALUMINIUM FOR FRONT AND BACK PANELS. PVC/STEEL FOR SIDES, TOP AND BOTTOM. LOW COST.	A	4.5	3"	6.5	£2.10
	C	4.5	10	6.5	£3.93
	G	13	3	6.5	£3.33
	G	Woodgrain			£4.28
	G	Woodgrain Sinclair drilled			£4.53
	N	4.5	7"	13"	£3.33

★ See January issue for all sizes. Send for free leaflets and price list.



**WEST HYDE DEVELOPMENTS LTD.,** RYEFIELD CRESCENT NORTHWOOD, MIDDXX., HA6 1NN.

Telephone: Northwood 24941/26732. Telex 923231 WEST HYDE NTHWD

# knight-kits

# HURRY! STOCKS GOING FAST!

Due to huge purchase these superb U.S.A. construction kits can be offered at 25%—50% off recommended list prices. Absolutely complete with most detailed construction and operating books. Available from all branches or by mail order for 37½p CARRIAGE AND PACKING on each kit. Two kits or more carr. free.

## KG-620 4½" VTVM KIT ★ NEW!

### SPECIFICATIONS




Ranges: 0-1.5-5-15-50-150-500-1,500V full scale; with optional High-Voltage Probe, to 25,000V.  
Accuracy: ± 3% Of full scale reading.  
Input Resistance: 11 megohms (1 meg in probe) up to 1,500V.  
Ranges (r.m.s.): 0-1.5-5-15-50-150-500-1,500V full scale (p-p); 0-2-14-12-140-120-1,300-1,200V full scale.  
Decibels: -10 to +65 in 2 ranges.  
Response: ± 1dB, 30Hz to 3MHz; ± 3dB, 30Hz to 5MHz; with optional H.F. Probe, to 250 MHz.  
Accuracy: ± 5% of full scale reading.  
Ranges: 0-1,000-10,000-100,000 ohms; 0-1-10-100-1,000 meg-ohms.  
Genie Scales: 10, 100, 1,000, 10,000, 100,000 ohms; 1 and 10 megohms.  
Battery 1½ V size U2.

Recommended List Price £18.27; **£9.95** Assembled Price £14 (RR Price £30)
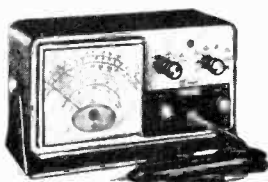
## KG-625 Deluxe 6in Vacuum Tube Voltmeter Kit

Huge 6in Meter Scale ● Ranges: d.c. 0-0.5-1.5-5-15-50-150-500-1,500V full scale.  
● Accuracy: ± 3% of full scale reading  
● Input Resistance: 11MΩ to 1,500V  
● Ranges: a.c. 0-1.5-5-15-50-150-500-1,500V full scale. 0-1-2-11-12-110-120-1,300-1,200V full scale ● Accuracy: ± 5% ● Frequency Response: ± 1dB, 30Hz to 3MHz; ± 3dB, 30Hz to 3MHz ● Ohmmeter Ranges: 0-1,000-10,000 ohms; 0-1-10-100-1,000MΩ ● Battery: 1½ V U2.  
Recommended List Price £24.97; **£12.60**




## KG-375A Deluxe Solid-State Auto Analyzer Kit

Tune-up and trouble-shoot any car, perform actual road tests

It's several testers in one... do all this

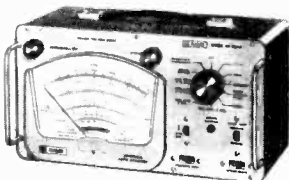Set Engine Idle and Automatic Transmission Shift Points ● Detect Condition of Point Surfaces ● Detect Distributor Wear ● Check Voltage and Current Regulators ● Check Generators for both Current and Voltage Output ● Find Poor or Open Earth Circuits ● Detect Variation in Dwell Angle.  
Recommended List Price £23.87; **£16.80**



Assembled Price £22.05

### WHY NOT BUY THE PAIR?

## KG-371 Deluxe Solid-State Timing Light

Performance surpasses assembled units costing much more

Helps Set Ignition Timing ● Checks Synchronisation of Double Breaker Arms ● Checks for Sticking Automatic Spark-Advance Mechanism ● Checks Distributor Cam Wear ● Built-in d.c. Power Supply ● Reliable Solid-State Circuit ● Your car gives more miles per gallon; Improved performance; Greater reliability.  
Recommended List Price £12.50.  
Available Assembled Only. **£9.95**



We offer you fully tensilised polyester/mylar and P.V.C. tapes of identical quality hi-fi, wide range recording characteristics as top grade tapes. Quality control manufacture. They are truly worth a few more coppers than acetate, sub-standard, jointed or cheap imports. TRY ONE AND PROVE IT

	STANDARD	LONG	DOUBLE	TRIPLE
3in 150ft	12p	3in 225ft	13p	3in 300ft
4in 300ft	22½p	4in 450ft	27p	4in 600ft
5in 600ft	45p	5in 900ft	52½p	5in 1,200ft
5in 900ft	52p	5in 1,200ft	55p	5in 1,800ft
7in 1,200ft	62½p	7in 1,800ft	92p	7in 2,400ft
				QUADRUPLE
				3in 600ft 42p

Post free less 5% on three reels. Quality and Trade inquiries invited. NOTE: Large tape stocks at all branches.

## SINCLAIR EQUIPMENT (Post 15p per order)

Z30—£3.95 | PZ5—£4.25  
Z50—£4.95 | PZ6—£6.95  
Stereo 60—£8.75 | PZ8—£5.25

Package Price: 1 x PZ5, 1 x Stereo 60 & 2 x Z30—£18.90  
MICROMATIC KIT—£2.30  
MICROMATIC BUILT £2.75

## E.M.I. LOUDSPEAKERS (Post 30p per order)


Quantity inquiries invited  
Hi-Fi 13in x 8in ceramic magnet, 10,000 line, 10 watts R.M.S.  
20 watts peak, 3, 8 or 15 ohms—£1.60  
ditto with crossover and E.M.I. 2in hi-fi tweeter, 8 or 15 ohms—£2.40  
ditto with flared parasitic tweeter cone, 3 or 8 ohms—£1.85

## CAR AERIALS (Post 15p per order)

Quantity inquiries invited  
Wingtop 54in, chromed, triple extension, pivoted with 53in lead/plug (value £1.60)—85p  
Retractable lock-down, chromed, 44ins, 5 sections (with 2 keys)  
47in screened lead and plug (value £2.45)—85p  
Send S.A.E. for free sale list of special items


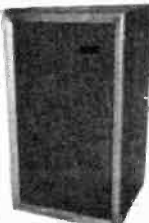
## Introducing The New "Delta" 10 watt Enclosure



Incorporating the famous EMI 150 set consisting of a 13 x 8in. bass unit with a high flux ceramic magnet and a concentric tweeter impedance 8Ω 20 watt peak handling power (10 watts RMS) or 20 watts peak.

Heavy duty 16mm infinite baffle case in superb quality genuine golden teak veneers with solid mahogany contrasting leading edges. High quality foam loaded cloth fret. Acoustically loaded "Jason" rotating badge in genuine gold leaf for horizontal or vertical operation. Size 19in x 10in x 10in. Weight 16lbs. A price break through at only Carriage etc. 50p singly. **£12.50** each  
Carriage free in pairs.



## "GAMMA" 20 WATT ENCLOSURE

As above but with super heavy duty bass unit with 3-6lb magnet in Magnadure II material with 1.5in speech coil and super tweeter giving frequency range of 20-20,000 Hz. Standard 8Ω impedance in beautifully finished heavy teak veneers. Size 12½ x 12 x 23in. 20 Watts RMS, 40 watts peak. At a super keen price. Carriage and ins. 85p. Carriage price in pairs **£19.50**

## PLINTHS & COVERS

For Garrard (take all current models except heavy transcription types). Beautiful heavy solid perspex top with "stereo" badge high quality base with solid wood sides machined ready for R/P deck to drop in without any further work. Terrific value at only **£3.45** complete. Carr. and Insurance 37½p.

Stockists of Leak, Quad, Sharp, Goodman, Garrard, Akai, Eagle, Rodgers, Crown, Teleton, Elizabethan, Wharfedale, etc.

# TECHNICAL TRADING

## FREE FLOG LIST NO 2

SEND S.A.E. OR CALL AT ANY BRANCH FOR YOURS

PERSONAL CALLERS Welcomed at branches listed to right where there are large Hi-Fi and Component stocks at the keenest prices including:  
All Mail Orders Only to Arundel.

★ ARUNDEL 15-17 Queen Street Tel. 3280

★ BRIGHTON 6 Queen's Road Tel. 23975

★ PORTSMOUTH 350-355 Fratton Road. Tel. 22034

★ SOUTHAMPTON 72 East Street Tel. 25851

Scores Special Bargains

# HOW TO TELL A STEREO SYSTEM THAT LOOKS GOOD FROM A STEREO SYSTEM THAT SOUNDS GOOD—BEFORE YOU PART WITH YOUR MONEY.

There's only one way to buy stereo equipment. Listen to it. Lots of it. Until you find the sound you like for the money you've got.

Sound advice. But try acting on it in 99% of hi-fi dealers and you'll be asked to show the colour of your money. We at Roc think that's unfair. So we fitted out our store in the Edware Road with a series of sound systems, so you can hear all the stereo you want until you find the equipment you like. With no hustling.

But if you're one of those poor unfortunates who cannot make it in person, we'll sell you a system by mail. We've got the best range in town from single speakers to complete stereo set-ups.

Here are just six of the systems we've got in stock.

Fill in the coupon and we'll have our systems brochure back to you by return.





Name \_\_\_\_\_  
 Address \_\_\_\_\_

**R**  
**ROC ELECTRONICS LIMITED**  
 193 EDGWARE ROAD LONDON W2 1ET  
 TELEPHONE: 01-723 6211

**System I.** Price: £39.90  
 Amplifier Output: 4 Watts per channel  
 Frequency Response: 50-10000 Hz.  
 Inputs: Tuner, Ceramic Cartridge  
 Controls: Volume, Tone & Balance  
 Speakers: Capacity: 6 Watts  
 Frequency Response: 40-16000 Hz.  
 Turntable: Garrard 2025TC, Ceramic Cartridge, Base and Cover  
 Matching AM/FM/FM Stereo Tuner

**System II.** Price: £49.90  
 Amplifier Output: 8 Watts per Channel  
 Frequency Response: 40-18000 Hz.  
 Inputs: Tuner, Tape, Ceramic Cartridge  
 Controls: Volume, Bass, Treble and Balance  
 Speakers: Capacity: 10 Watts  
 Frequency Response: 40-19000 Hz.  
 Turntable: As system I.

**System III.** Price: (A) £59.90 (B) £69.90  
 Amplifier Output: 15 Watts per Channel  
 Frequency Response: 30-18000 Hz.  
 Inputs: Tuner, Tape, Magnetic & Ceramic  
 Controls: Volume, Bass, Treble and Balance  
 Speakers: As System II  
 Turntable: System IIIA Garrard 2025TC, Ceramic Cartridge, Base and Cover  
 System IIIB Garrard SP.25 MK III, Magnetic Cartridge, Base and Cover

**System IV.** Price: £79.90  
 Amplifier Output: 20 Watts per Channel  
 Frequency Response: 25-20000 Hz.  
 Inputs: Tuner, Tape Magnetic & Ceramic Cartridge  
 Controls: 2 Volume, Bass, Treble and Loudness  
 Speakers: Capacity: 20 Watts  
 Frequency Response: 35-20000 Hz.  
 Turntable: Garrard SP.25 MKIII, Magnetic Cartridge, Base and Cover  
 Matching AF/FM/FM Stereo Tuner: £36.00

**System V.** Price: £115.00  
 Tuner Amplifier Output: 18 Watts per Channel  
 Frequency Response: 30-20000 Hz.  
 Inputs: Tape & Magnetic Cartridge  
 Controls: 2 Volume, Bass, Treble and Tuning  
 FM Sensitivity: 2.5 micro volts  
 AM Sensitivity: 100 micro volts  
 Speakers: Capacity: 20 Watts  
 Frequency Response: 35-20000 Hz.  
 Turntable: As System IV

**System VI.** Price: £182.00  
 Amplifier Output: 30 Watts per Channel  
 Frequency Response: 20-30000 Hz.  
 Inputs: Auxilliary, Magnetic & Ceramic Cartridge  
 Controls: Volume, Bass, Treble, Balance, Loudness and Monitor  
 Speakers: Capacity: 30 Watts  
 Frequency Response: 35-20000 Hz.  
 Turntable: Thorens TD150AB Magnetic Cartridge, Base & Cover

# DISCOSOUND




## D.J. DISCO-AMP

Designed specifically for use with discotheques and has many exclusive features not normally found on P.A. amplifiers. The unit will be of use to the professional D.J. as well as in clubs and mobile discotheques.

A complete Pre-fade listen (P.F.L.) cueing monitor section is featured with separate input for headphones (either stereo or mono) with an independent volume control for headphone monitoring, and a P.F.L. switch, so that either turntable can be monitored for accurate cueing up of records. A mic over-ride switch is also added which cuts the music volume by half. Specification: Output power 70 watts R.M.S.  $\pm$  1 db at 8 ohms. Frequency response: 30-20,000 Hz  $\pm$  3db. Harmonic distortion: Less than 1% at full output. Signal/noise ratio: Better than -65db. Inputs: Mic 1 & 2.5 mV at 50 K ohms. Turntable 1 & 2 100 mV at 1 meg ohm.

50 ohm or 600 ohm mic inputs may be ordered at extra cost. Size: Front Panel 16 1/2 in x 7 in. Cut out 15 1/2 in x 6 in. Fuses A.C. 1.5 amp (B.S.) mounted on back panel.

PRICE £85 inc. P. & P.

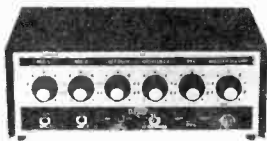


## D.J. 102 DISCOTHEQUE MIXER PRE-AMPLIFIER

Consists of a 4 channel mixer each with its own volume control and a complete P.F.L. monitoring system. Also features a mike cut down switch. For use with amplifiers having tone controls but not having the above facilities. Frequency response 20-20,000 Hz  $\pm$  2db. Distortion less than 1%. Signal to noise ratio better than -65db. Size 10 1/2 in x 4 in x 4 in. Self powered.

PRICE £25 inc. P. & P.
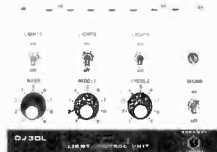
## D.J. 30L PSYCHEDELIC LIGHT CONTROL UNIT

3 channel light control unit that handles up to 1,000 watts per channel. Separate bass, middle and treble controls for full frequency separation. Completely built and tested



PRICE £37.50 inc. P. & P.

For full details of these and all Discosound Products write direct to

# DISCOSOUND

122 BALLS POND ROAD, LONDON, N.1. Tel. 01-254 5779

Full money back guarantee if returned within 10 days

All Discosound Products are guaranteed for 12 months

Demonstrations given at any time

ERSIN



5 CORE SOLDER

## for fast, easy, reliable soldering

Contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux required.

### SAVBIT ALLOY ALSO REDUCES COPPER BIT WEAR.

Economically packed for general electrical and electronic soldering. 75 ft. 18 gauge on plastic reel. Recommended retail price 75p



### THIN GAUGE SOLDER, ESSENTIAL FOR

soldering small components and thin wires. High tin content, low melting point, 60/40 alloy, 170 ft. 22 gauge on plastic reel. Recommended retail price 75p



### A RANGE OF SOLDERS IN HANDY DISPENSERS.

REF. ALLOY SWG

4A	60/40	18	15p *
Size 5 (fil-ustra-15)	Savbit	18	15p *
15	60/40	22	20p *

\*Recommended Price



### INVALUABLE FOR STRIPPING FLEX, THE NEW AUTOMATIC OPENING BIB WIRE STRIPPER AND CUTTER, easily adjustable for all standard diameters. Plastic covered handles can also be used as wire cutter. Recommended retail price 50p



From Electrical and Hardware shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

### Selections from FELSTEAD ELECTRONICS' List

(Sent free for stamped addressed envelope to address below)

Transistors, etc. AC126 12/p. AF114 15p. AF117 20p. OA5 7/p. OA10 7/p. OA81 7/p. OA85 7/p. OC23 32/p. OC25 30p. OC26 37/p. OC28 42/p. OC32 42/p. OC44 14p. OC45 12/p. OC71 12/p. OC72 12/p. OC75 12/p. OC81 12/p. OC81D 12/p. OC82D 12/p. OC170 20p. OC171 12/p. OC72 12/p. OC75 12/p. BY100 800piv 14p. 6 Amp series: BY213 300piv 20p. BY212 600piv 25p. BY211 900piv 30p. BY210 1200piv 35p. (Charges 6/p up to 11, paid for 12 and over.) Sub-Min. Transformers: OUTPUT (3n for OC72, etc.) 14p. (1p to 6 6/p). MULTIMETER. Our famous 20000  $\Omega$  per V £4.92 (15p). Details and notes for 18K TCR LP, TCMS, TRSLP/STEREO, COLLARO 'O', RONETTE BF40LP, GARRARD GC/LP and GC/LP, ACOS GP65 67, all at 40p (6p) ACOS GP73, GP91, BSR ST4 (ST3, ST5), ST8 (ST9), SONOTONE STA, 9TA, 9TAHC, PHILIPS AC6306, 3050 (3053, 3056, 3301, 3302, 3304) Garrard GK825 all at 75p (6p). All are of the very highest quality. Double Diamond: ST4 (ST3, ST5), ST10 (ST9, ST8), 9TA, 9TAHC, 3206, G91 (For TP), GP93, GP94 cartridges; GP91SC for all GP91-SC cartridges. All at £1.50 (6p). PICK-UP CARTRIDGES. All standard fittings and stylus. MONO GP672 75p STEREO-COMPATIBLE (MONO) GP91/SC (£1.05). STEREO GP93 £1.27. STEREO CERAMIC GP94 £1.92. SONOTONE STEREO 9TAHC (DIA.) £2.37. GOLDRING G850 £4.87. G800 £13.50. G800E £13.50. G800 SUPER £19.50 (6p) all types or Reg. Post 22/p). STYLII FOR ALL ABOVE TYPES, including GOLDRING available. RECORDING TAPE. 8 1/2 in the finest quality Mylar available. Standard 3 1/2 in. 36p. 9 1/2 in. 50p. 7 1/2 in. 40p. 5 1/2 in. 50p. LONG PLAY 7 1/2 in. 50p. 5 1/2 in. 1200 ft. 56p. 7 1/2 in. 1800 ft. 80p. (7/p on 5 1/2 and 7 1/2) 9p on 7 1/2. MICROPHONES Crystal Mic 91, hand/desk 81p. MIC45 Curved metal handgrip £1. CM21 Grey hand/desk 52/p. Stick '60' £1.02. CM70 "Planet" machined metal tapered stick type with neck cord, adaptor to fit floor stands £1.47 (All 6p LAPEL (or hand) with clip 32/p (6p)). All are fitted with leads. Dynamic Cream hand/table MINY 77/p (9p) MS10, 50K  $\Omega$  for desk, tapered with base and slip-out adaptor £1.97. MS11, similar, but fixed on swivel swan neck to swivel-fitted base £2.21 (Either 15p). Type 200 Cardiod ball, 50K/600  $\Omega$ , omnidir., built-in vol. control, on/off switch, special lead, handle (as good as money can buy) £6.30. DM160, Non-Dir. Ball, 50K  $\Omega$ , switch, cable, adaptor £3.87 (27/p either). MICROPHONE INSERTS. Dia. 1.75" OR 0.9" either size 27/p (6p). EARPIECES with lead & min. jack plug (2.5 or 3.5mm, state which) Magnetic 9p Crystal (3.5 only) 24p. (Up to 3 for 6p on any.) HEADPHONES De Luxe STEREO 8-15 ohms, £2.47. Same, fitted vol. control each earpiece, £2.20. Both have lead and stereo jack plug (17/p). HIGH RES. 2000 ohms. Adjustable 92/p (12/p). SPEAKERS. 12" ROUND, fitted tweeter, 3 or 15  $\Omega$  (state which) £1.87 (27/p) (or for Stereo £4.25 pair, carr. paid. 2 1/2" 3 OR 8  $\Omega$  (state which) 37/p (6p). EMI 13" x 8", 3, 8 or 15  $\Omega$  (state which) £2.12 (25p) with single tapered para. tweeter cone 8 or 15  $\Omega$  (state which) £2.27 (25p); with two tweeters and crossover network 8 or 15  $\Omega$  (state which) £3.75 (25p). VIBRATORS. Genuine Plessey LVA 4-pin non-synch. 121H14, 2 1/2 ex. pins 27/p. Ann. 12V 4-pin, non-synch. 7466, longer, 22/p. 12V 7-pin synch. (12SR7) 82/p (all types 61p per vibrator). CONNECTING WIRE. Packs of 5 coils asstd. coils, ea. coil yds. Solid core 14p (6p). Flexible 16p (71p). Super thin for transistor wiring 16p (6p). PICK-UP WIRE. Super thin twin flex, screened and sheathed 6p yd. (6p up to 6yds.—over, free). RETRACTABLE Flex. Leads. (Curles) 611, phono plug ea. end 22/p. (2ft. 39p. 6ft. phono plug/phone socket other end 25p 12ft. 42/p (6p per lead, all types). BATTERY ELIMINATOR. 240 a.c. input 3, 6, 7 1/2 and v. 42/p (6p per lead, all types). APPLIANCE INCL. all makes cassette recorder and players £3.15 (24p). SEND S.A.E. for full free lists—Teleton and small 3W and 7 1/2W trans. amplifiers, Electrolytics, Vol. Controls, all types of radio switches, car and portable expanding aereals, Meters, Test procs, all types of Brit. & Cont. standard and min. plugs and sockets, SDR's, Thyristors, croc. clips (various), terminals, etc. etc. and many "Special Offer" lines at lowest possible prices.

FELSTEAD ELECTRONICS (PE503)

LONGLEY LANE, GATLEY, CHEADLE, CHES. SK8 4EE

Cash with order only. No C.O.D. or Caller Service. Charges (Min. 6p) in brackets after all items. Regret Orders under 25p excluding postage unacceptable. S.A.E. please for inquiries or cannot be replied to. Changes apply G.B. and Eire only. Overseas orders welcomed (lists free overseas).

# Britains most popular kits..


**Heathkit the beginner as well as the experienced mans first choice.**  
**Want to know more . . .** the unique Heathkit one-step-at-a-time construction manual is your guarantee to kit building success. To see for yourself how easy it all is, simply order the manual for the model of your choice (price only 10/- each). If you order a kit at a later date the manual price can be deducted. Your first step is to send for the Free catalogue, yours for only the price of a postage price stamp.

## Stereo Record Player



Exciting Sound — Budget Price  
 Kit: K/SRP-1 - - £32.50  
 Carr. 80 NP

## 'SEVERN' AM/FM Radio

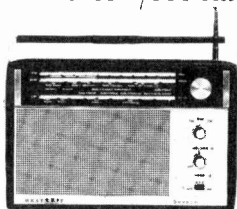


Beautiful Looks — Luxury Sound  
 Kit: K/SEVERN - £19.90  
 Carr. 50 NP

## Powerful Car Radio




Heathkit Value—Powerful Output  
 Kit: K/CR-1 (Less Speaker) £13.80  
 Carr. 30 NP

## 30W Stereo Amplifier

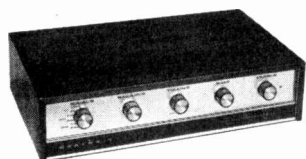


Stereo Gram, Radio, Aux inputs  
 Kit: K/TSA-12 £36.00  
 (cab extra) Carr. 50 NP

## Economy SW Receiver

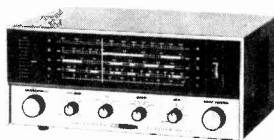

World-wide Reception  
 1 to 30 MHz plus 550-1620 KHz  
 Kit: K/GR-64 - - £25.00  
 Carr. 50 NP

## Stereo tuner/amplifier

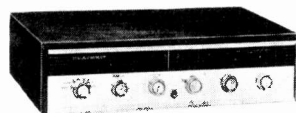

One of todays best values  
 Kit: K/AR-14 £59.00  
 (cab. Extra) Carr. 60 NP


## Portable 'VVM'



For Hobbyists — Householders  
 Kit: K/IM-17 - - £17.30  
 Carr. 30 NP
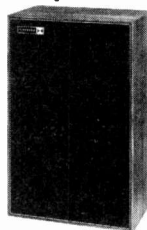
## Ambassador Speaker

Remarkable  
 sound  
 quality for  
 its price



Kit: K/AMBASSADOR £33.00  
 Carr. 80 NP

## Auto Tune-up Meter



For D.I.Y. Car Mechanics  
 Kit: K/ID-29 - - £15.80  
 Carr. 30 NP



A Schlumberger Company

**HEATH (Glos.) LTD.**  
**GLOUCESTER GL2 6EE**

Many more wonderful kits to choose from

Please send me FREE Catalogue

NAME.....

ADDRESS..... POST CODE.....

Prices and specifications subject to alteration without notice

25/4/71

# The Gerry





# y Adler Story.

Once upon a time Gerry Adler worked a 25 hour day making and selling valve filament testers. And very efficient they were too.

But at that time the Japanese could make them for about half the price, and sent Gerry one to prove it. It was as good as the ones he was making, so he sold it. And every other one he could get into the country.

After a time Gerry decided to go one step further. He designed some electronic equipment and had it built to his specification in Japan. Then he sold it here under the brand name 'Eagle'. Nothing particularly remarkable about that. But Gerry couldn't stand the idea of a barrier between him and his manufacturers. So he went to Japan. He poked his nose into all the electronics factories to find out how the Japanese worked. And when he got back he started to learn Japanese, and to study their history, culture and way of life. That way he had fewer communication problems and could get what he wanted.

That's what matters to Gerry. He's very fussy about what goes out under the Eagle banner. Because Eagle aren't in the filament testing business any more. They make just about everything electronic: amplifiers, test equipment, PA systems, intercoms, old uncle substation and all. Eagle is now twelve years old, and has opened offices in New York, Tokyo and Brussels.

This isn't just so much chest expansion on Gerry's part. He puts his money where his mouth is. If you think one of his products is not as good as a rival's, or it's faulty, or it's not all it should be, Gerry wants to know.

So write to him personally. He'll do something about it. He wants to make sure the Gerry Adler story has a happy ending.

**Eagle International**  
we don't stand still.

Coptic Street, London WC1A 1NR.  
Telephone 01-636 0961

# NEW FROM TRS

This money saving **STEREO 8 + 8 AMPLIFIER** in a new **PRE-ASSEMBLED MODULAR PRESENTATION**

A new conception in modular assembly which makes construction even easier than ever and results even better. Two pre-amp and two power amp modules, factory built, tested and guaranteed by a world famous maker come to you ready mounted with mains power unit on chassis forming part of the attractive TRS cabinet which simply need wiring for immediate use. A generous 8 watt RMS output per channel into 3-5 ohms is assured. Cabinet with aluminium front, charcoal grey top and wood sides measures 12in x 8in x 2in. Very attractive appearance.

- Frequency resp.: 50Hz-16kHz  $\pm$  3dB.
- Input: 110mV per P.U., radio 240mV.
- Output: 8W per channel, RMS into 3-5 $\Omega$ . Slightly less per 8-15 $\Omega$  speakers.
- Record and playback facilities
- Bass/Treble/Volume/Balance/ Input/On-off controls.
- Extra easy to install.



Complete kit assembled ready to wire up with mains lead and instructions. Unsurpassed value at only

**£17.50**

Carriage and packing 38p in U.K.  
Descriptive leaflet on request

## COMPONENTS CORNER

**VYNAIR** speaker and cabinet covering by ICI. Send 5p for samples—refundable on purchase. 12 $\frac{1}{2}$ p per sq. ft. £1.38 per yd. 48in wide.

**BONDACOUST** speaker wadding 1in thick, 18in wide, per yard 42 $\frac{1}{2}$ p.

**VEROBOARD** in all latest sizes and forms. inc. 2 $\frac{1}{2}$ in x 3 $\frac{1}{2}$ in, 16p; 2 $\frac{1}{2}$ in x 5in or 3 $\frac{1}{2}$ in x 3 $\frac{1}{2}$ in, 23p; 3 $\frac{1}{2}$ in x 5in, 26p; 17in x 3 $\frac{1}{2}$ in, 75p.

**VOLUME CONTROLS.** Long spindles all values 5Kohms to 2meg., log or lin., less switch 17 $\frac{1}{2}$ p; with switch 25p.

Twin ganged stereo, 5K to 2meg. less switch, 48p; with switch 100K to 2meg. 52p.

**STEREO BALANCE CONTROLS.** Log/Anti-log 5K, 10K,  $\frac{1}{2}$ , 1 or 2meg., 55p.

**RESISTORS, CAPACITORS, WIRE,** etc., etc.

## MORE AMPLIFIERS FROM TRS

### MULLARD VALVE AMPLIFIERS

5-10 basic kit (mono) £18.99. Carr. 28p.  
2 valve mono pre-amp basic kit for above £7-65. Carr. 28p.  
10-10 stereo amplifier kit £18.99. Carr. 63p.

### TRS 50 WATT VALVE AMPLIFIER

A ruggedly built unit in ventilated steel case with carrying handles: size 12in x 8in x 8in. Two input channels mixable (10mV and 150mV) bass and treble controls. EL 34's output (mono) in push-pull, with fixed bias. Excellent for P.A., musical group work, etc. Brand new and guaranteed £30. Carriage 75p.

# TRS RADIO COMPONENT SPECIALISTS

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY  
Tel. 01-654 2188

## FOR YOUR STEREO 8+8 OR OTHER HI-FI SYSTEMS

Plinth and motor assembly comprising modern style teak finished plinth cut to take famous Garrard AT6 auto/single playing unit wired for stereo, with hard smoke grey perspex lid, Plinth and AT6 less cartridge **£12.50** (Carr. and packing 53p).

### SPECIAL CARTRIDGE OFFER TO PURCHASERS OF ABOVE ONLY


Acos stereo 6P93-1 (sapphire) £1.25.  
Sonatone 9TA/HC (diamond) £2.  
AD96K (Mag., diamond) £3.50.  
Various magnetic types from £3.50.

### TRS SPEAKER BARGAIN

Ready now — SPEAKER AND CABINET ASSEMBLY comprising 8" unit (4 ohms) and easy to put together flat-pack cabinet ported and lined, size 18" x 12" x 9". **£5.90** (Carr. 40p).

Open all day  
Sats., Weds.—1 p.m. Almost next to  
Thornton Heath Stn. (S.R.)
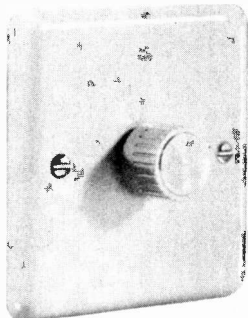
## Vary the strength of your lighting with a DIMMASWITCH



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The ivory mounting plate of the DIMMASWITCH matches modern electric fittings. The bright chrome control knob activates an on-off switch and controls 40-600 watts of all lights except fluorescents at mains voltages from 200-250 V, 50 Hz. The DIMMASWITCH has built-in radio interference suppression. Price: £3.20 plus 7p post and packing. Kit Form: £2.70 plus 7p post and packing. Please send C.W.O. to:—

**DEXTER & COMPANY**  
1 ULVER HOUSE, 19 KING STREET  
CHESTER CH1 2AH Tel: 0244-25883  
As supplied to H.M. Government Departments, Hospitals, Local Authorities, etc.

## NEW RANGE U.H.F. TV AERIALS

All U.H.F. aerials now fitted with tilting bracket and 4 element grid reflectors.

Loft Mounting Arrays. 7 element, 45-; 11 element, 52.6; 14 element, 60-; 18 element, 70-; Wall Mounting with Cranked Arm, 7 element, 65-; 11 element, 75-; 14 element, 82.6; 18 element, 90-; Chimney Mounting Arrays Complete, 7 element, 80-; 11 element, 87.6; 14 element, 95-; 18 element, 105-. Complete assembly instructions with every aerial. Low Loss Co-axial Cable, 1.8 yd. King Teletesters—Labgear U.H.F. Boosters from 75-. Bellini Lee "Concord" all Band V.H.F. U.H.F. mains operated pre-amp £7.10.0. State clearly channel number required on all orders. p.p. Aerials 8-. Accessories 3-. C.W.O. or C.O.D.

### BBC · ITV · FM AERIALS

B.B.C. (Band 1). Loft, 25-; Wall S.D. 32.6, "H" array, 60-; I.T.V. (Band 3). 5 element loft array, 45-; 7 element, 55-; Wall mounting 5 element, 65-; Combined BBC/ITV loft 1 + 5, 55-; 1 + 7, 67.6; Wall mounting 1 + 5, 77.6; Chimney mounting 1 + 5, 90-. Pre-amps from 75-.

Combined BBC/ITV BBC 2 Aerials, 1 + 5 + 9, 40-; 1 + 5 + 14, 90-. 1 + 7 + 14, 100-. Available loft only.

F.M. Radio Loft S.D. 19.6, "H", 38.6, 3 element array, 57.6, Standard co-axial cable, 1 - yd. Coax plugs, 1.8. Outlet boxes, 6-. Diplexer crossover boxes, 17.6. p.p. Aerials, 8-; accessories, 3-; C.W.O. or C.O.D. (min. C.O.D. charge 3.6.) 1 - for fully illustrated Lists.

CALLERS WELCOMED

OPEN ALL DAY SATURDAY

**K.V.A. ELECTRONICS (Dept. P.E.)**  
40-41 Monarch Parade  
London Road, Mitcham, Surrey  
01-648 4884

## 4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 Master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

### MAINS INTERCOM

No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £12.95. P. & P. 50p extra.

## INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 12p. P. & P. 25p.

### Transistor TELEPHONE AMPLIFIER



Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 12p extra. P. & P. 18p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE/4)  
189 KENSINGTON HIGH STREET, LONDON, W.8


# TRANSISTOR RADIOS TO BUILD YOURSELF

Backed by after sales service
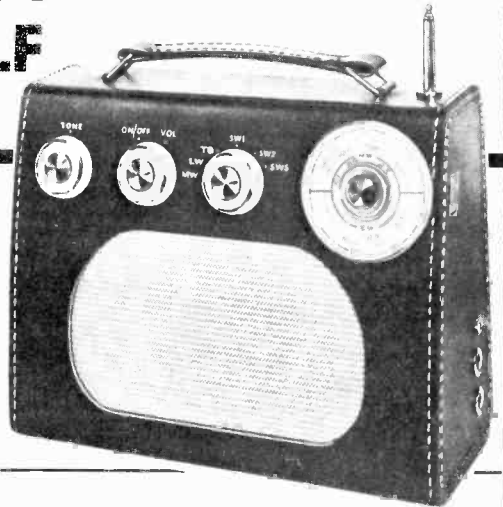
## NEW! roamer eight mk 1 WITH VARIABLE TONE CONTROL

7 Tunable Wavebands: Medium Wave 1, Medium Wave 2, Long Wave, S.W.1, S.W.2, S.W.3 and Trawler Band. Built-in ferrite rod aerial for Medium and Long Waves. 4 section 24in. retractable chrome plated telescopic aerial for Short Waves for maximum performance. Push-pull output using 600Mw type transistors. Socket for car aerial. Tape record socket. Selectivity switch. Switched earpiece socket complete with earpiece for private listening. 8 transistors plus 3 diodes. Famous mkrke 7 4in speaker. Air spaced ganged tuning condenser. On/off switch volume control. Wave change switch and tuning control. Attractive case in rich chestnut shade with gold blocking. Size 9 7 4in approx. Easy to follow instructions and diagrams make the Roamer Eight a pleasure to build. Parts price list and easy build plans 25p (6/-) (FREE with parts).


**Total building costs** **£6.98** P. & P. 38p (7/7) Overseas P. & P. 85p (17/-)  
(£6.19.7)


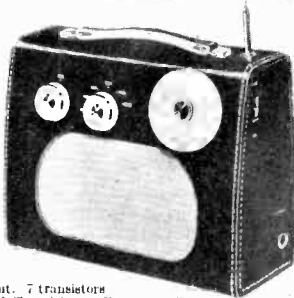
## roamer seven mk IV

7 FULLY TUNABLE WAVEBANDS—M.W.1, M.W.2, L.W., S.W.1, S.W.2, S.W.3 and Trawler Band. Extra Medium waveband provides easier tuning of Radio Luxembourg, etc. Built in ferrite rod aerial for Medium and Long Waves. Retractable 4 section 24in chrome plated telescopic aerial for peak short wave listening. Socket for Car Aerial. Powerful push-pull output. 7 transistors and two diodes including Micro-Alloy R.F. Transistors. Famous mkrke 7 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off control. Wave change switches and tuning control. Attractive case with carrying handle. Size 9 7 4in approx. Easy to follow instructions and diagrams make the Roamer 7 a pleasure to build. Parts price list and easy build plans 15p (3/-) (FREE with parts).

**Total building costs** **£5.98** P. & P. 38p (7/7) Personal Earpiece with plug and switched socket for private listening, 30p (6/-) extra.  
(£5.19.7) Overseas P. & P. 85p (17/-)




## NEW!
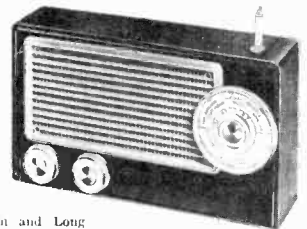
## transeight SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive case in black with red grille and black knobs and dial with spun brass inserts. Size 9 7 5 1/2 2 1/2in. approx. Tunable on Medium and Long Waves, 3 Short Waves and Trawler Band. Sensitive ferrite rod aerial for M.W. and L.W. Telescopic aerial for Short Waves. 8 improved type transistors plus 3 diodes. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (6/-) (FREE with parts).


**Total building costs** **£4.48** P. & P. 28p (5/7) Earpiece with plug and switched socket for private listening, 30p (6/-) extra.  
(£4.9.7) Overseas P. & P. 65p (13/-)



## pocket five
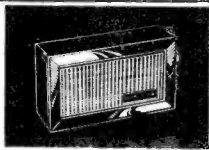
### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive black and gold case. Size 5 1/2 x 1 1/2 x 2 1/2in. Tunable over both Medium and Long Waves with extended M.W. band for easier tuning of Luxembourg, etc. 7 stages 5 transistors and 2 diodes, sensitive ferrite rod aerial, fine tone moving coil speaker. Easy build plans and parts price list 8p (1/7) (FREE with parts). Earpiece with plug and switched socket for private listening, 30p (6/-) extra.



**Total building costs** **£2.23** P. & P. 18p (3/7)  
(£2.4.7) Overseas P. & P. 50p (10/-)

## transona five

### MEDIUM WAVE, LONG WAVE AND TRAWLER BAND PORTABLE WITH SPEAKER

Attractive case with red speaker grille. Size 6 1/2 x 4 1/2 x 1 1/2in. 7 stages 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Easy build plans and parts price list 8p (1/7) (FREE with parts). Earpiece with plug and switched socket for private listening, 30p (6/-) extra.




**Total building costs** **£2.38** P. & P. 19p (3/9)  
(£2.7.7) Overseas P. & P. 50p (10/-)

## IMPROVED MODEL !
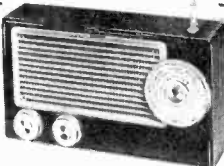
### roamer six SIX WAVEBAND PORTABLE WITH 3in. SPEAKER

Attractive black case with red grille and black knobs and dial with spun brass inserts. Size 9 7 5 1/2 2 1/2in. approx. Tunable on Medium and Long Waves, two Short Waves, Trawler Band plus an extra M.W. band for easier tuning of Luxembourg, etc. Sensitive ferrite rod aerial and latest telescopic aerial for Short Waves. Improved circuit. 8 stages—6 transistors and 2 diodes including Micro-Alloy R.F. Transistors, etc. Easy build plans and parts price list 10p (2/-) (FREE with parts). Earpiece with plug and switched socket for private listening, 30p (6/-) extra.



**Total building costs** **£3.98** P. & P. 23p (4/7)  
(£3.19.7) Overseas P. & P. 65p (13/-)

## RADIO EXCHANGE LTD

61a, HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £ ..... please send items marked  
 ROAMER EIGHT  ROAMER SEVEN   
 TRANSEIGHT  POCKET FIVE   
 TRANSONA FIVE  ROAMER SIX

Parts price list and plans for

Name .....  
 Address .....

\* Callers side entrance Barratts Shoe Shop

\* Open 10-1, 2.30-4.30 Mon.-Fri. 9-12 Sat.

PE 28

# YATES ELECTRONICS

## FLITWICK LTD

### RESISTORS

$\frac{1}{2}$ W Iskra high stability carbon film—very low noise—capless construction.  $\frac{1}{4}$ W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W Erie wire wound.

Power watts	Tolerance	Range	Values available	Price
$\frac{1}{2}$	5%	4.7 $\Omega$ -2.2M $\Omega$	E24	1-99 100+
$\frac{1}{4}$	10%	3-3M $\Omega$ -10M $\Omega$	E12	1-0p 0-7p
$\frac{1}{4}$	10%	1 $\Omega$ -3.9 $\Omega$	E12	1-0p 0-7p
$\frac{1}{4}$	5%	4.7 $\Omega$ -1M $\Omega$	E12	1-0p 0-7p
$\frac{1}{4}$	10%	1 $\Omega$ -10 $\Omega$	E12	7 $\frac{1}{2}$ p 7 $\frac{1}{2}$ p

Quantity price applies for any selection. Ignore fractions on total order.

### DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7 $\Omega$  to 1M $\Omega$ .

E12 pack 325 resistors £2.20.

E24 pack 650 resistors £4.20.

### MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001 $\mu$ F, 0.0015 $\mu$ F, 0.0022 $\mu$ F, 0.0033 $\mu$ F, 0.0047 $\mu$ F, 2 $\frac{1}{2}$ p. 0.0068 $\mu$ F, 0.01 $\mu$ F, 0.015 $\mu$ F, 0.022 $\mu$ F, 0.033 $\mu$ F, 3p. 0.047 $\mu$ F, 0.068 $\mu$ F, 0.1 $\mu$ F, 4p. 0.15 $\mu$ F, 6p. 0.22 $\mu$ F, 7 $\frac{1}{2}$ p. 0.33 $\mu$ F, 11p. 0.47 $\mu$ F, 13p. 160V: 0.01 $\mu$ F, 0.015 $\mu$ F, 0.022 $\mu$ F, 0.033 $\mu$ F, 0.047 $\mu$ F, 0.068 $\mu$ F, 3p. 0.1 $\mu$ F, 0.15 $\mu$ F, 0.22 $\mu$ F, 4p. 0.33 $\mu$ F, 6p. 0.47 $\mu$ F, 7 $\frac{1}{2}$ p. 0.68 $\mu$ F, 11p. 1.0 $\mu$ F, 12 $\frac{1}{2}$ p.

### MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01 $\mu$ F, 0.015 $\mu$ F, 0.022 $\mu$ F, 3p. 0.033 $\mu$ F, 0.047 $\mu$ F, 0.068 $\mu$ F, 3 $\frac{1}{2}$ p. 0.1 $\mu$ F, 4p. 0.15 $\mu$ F, 0.22 $\mu$ F, 5p. 0.33 $\mu$ F, 6 $\frac{1}{2}$ p. 0.47 $\mu$ F, 8 $\frac{1}{2}$ p. 0.68 $\mu$ F, 11p. 1.0 $\mu$ F, 13p.

### MYLAR FILM CAPACITORS

100V: 0.001 $\mu$ F, 0.002 $\mu$ F, 0.005 $\mu$ F, 0.01 $\mu$ F, 0.02 $\mu$ F, 2 $\frac{1}{2}$ p. 0.04 $\mu$ F, 0.05 $\mu$ F, 0.068 $\mu$ F, 0.1 $\mu$ F, 3 $\frac{1}{2}$ p.

### CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

### CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1.0 $\mu$ F, £2.90.

### ELECTROLYTIC CAPACITORS—One Price—5p Each

Mullard C426 series ( $\mu$ F/V): 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 16/10, 32/10, 64/10, 125/10, 200/10, 10/16, 20/16, 40/16, 80/16, 125/16, 6.4/25, 12.5/25, 25/25, 50/25, 80/25, 4/40, 8/40, 16/40, 32/40, 50/40, 2.5/64, 5/64, 10/64, 32/64. Miniature P.C. mounting ( $\mu$ F/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

### POTENTIOMETERS

Carbon track 5k $\Omega$  to 1M $\Omega$ , log or linear (log  $\frac{1}{2}$ W, lin  $\frac{1}{2}$ W).

Single, 12 $\frac{1}{2}$ p. Dual gang (stereo), 40p.

### SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 $\Omega$  and decades to 5M $\Omega$ . Horizontal or vertical P.C. mounting (0-1 matrix).

Sub-miniature 0.1 watt, 4p each. Miniature 0.25 watt, 5p each.

### SEMICONDUCTORS

AC126 15p	BFY52 22 $\frac{1}{2}$ p	OC81 15p	2N3055 72p
AC127 15p	BSY56 30p	OC82 15p	2N3702 15p
AC128 15p	BSX21 25p	ORP12 47 $\frac{1}{2}$ p	2N3703 14p
AD140 40p	BY124 7 $\frac{1}{2}$ p	IN4001 7 $\frac{1}{2}$ p	2N3704 17 $\frac{1}{2}$ p
AF115 17 $\frac{1}{2}$ p	BYZ10 30p	IN4002 10p	2N3705 15p
AF117 17 $\frac{1}{2}$ p	BYZ13 20p	IN4003 11p	2N3706 12p
BC107 14p	OA85 7 $\frac{1}{2}$ p	IN4004 12 $\frac{1}{2}$ p	2N3707 18 $\frac{1}{2}$ p
BC108 10p	OA91 7 $\frac{1}{2}$ p	IN4005 14p	2N3708 10p
BC109 10p	OA202 7 $\frac{1}{2}$ p	IN4006 15p	2N3709 11p
BFY50 22p	OC71 15p	IN4007 16p	2N3710 12p
BFY51 19p	OC72 15p	2N2926 11p	2N3711 14p

### ZENER DIODES

400mW 5% 3.3V to 30V, 17 $\frac{1}{2}$ p.

### VEROBOARD

2 $\frac{1}{2}$ x 3 $\frac{1}{2}$	0-1 22p	0-15 16p	17 x 3 $\frac{1}{2}$ (plain)	0-15 52 $\frac{1}{2}$ p	0-1 —
2 $\frac{1}{2}$ x 5	24p	24p	17 x 2 $\frac{1}{2}$ (plain)	37 $\frac{1}{2}$ p	—
3 $\frac{1}{2}$ x 3 $\frac{1}{2}$	24p	24p	2 $\frac{1}{2}$ x 5 (plain)	17 $\frac{1}{2}$ p	—
3 $\frac{1}{2}$ x 5	27p	27p	2 $\frac{1}{2}$ x 3 $\frac{1}{2}$ (plain)	15p	—
17 x 2 $\frac{1}{2}$	75p	57 $\frac{1}{2}$ p	Pin insertion tool	47 $\frac{1}{2}$ p	47 $\frac{1}{2}$ p
17 x 3 $\frac{1}{2}$	100p	75p	Spot face cutter	37 $\frac{1}{2}$ p	37 $\frac{1}{2}$ p
17 x 5 (plain)	—	75p	Pkt. 3 $\phi$ pins	15p	15p

### ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 22 $\frac{1}{2}$ p.

### PLUGS AND SOCKETS

Standard $\frac{1}{4}$ in screened	17 $\frac{1}{2}$ p	2.5mm insulated	7 $\frac{1}{2}$ p
Standard $\frac{1}{4}$ in insulated	14p	3.5mm insulated	7 $\frac{1}{2}$ p
Stereo $\frac{1}{4}$ in screened	35p	3.5mm screened	12 $\frac{1}{2}$ p
Standard $\frac{1}{4}$ in socket	15p	2.5mm socket	7 $\frac{1}{2}$ p
Stereo $\frac{1}{4}$ in socket	17 $\frac{1}{2}$ p	3.5mm socket	7 $\frac{1}{2}$ p

### BRUSHED ALUMINIUM PANELS

12" x 6" = 25p; 12" x 2 $\frac{1}{2}$ " = 10p; 9" x 2" = 7p.

C.W.O. please. Post and packing, please add 7 $\frac{1}{2}$ p to orders under £2. Data sheets are available for most of the components listed, and will be sent free on request.

BE39 ELSTOW STORAGE DEPOT, KEMPSTON HARDWICK, BEDFORD

Send 5p for New Comprehensive I.C. and Semiconductor price list (24 pages)

## INTEGRATED CIRCUITS

### NEW LOW PRICES • FULLY GUARANTEED

RCA	4p	MOTOROLA	1-9	10+	20+	MULLARD	4p
CA3000	1-80	MC708G	0.91	—	0.76	LINEAR	—
3005	7	MC724P	0.66	—	0.65	TAA241	1.62 $\frac{1}{2}$
7	2-65	MC788P	0.82	—	0.69	242	4.25
11	0.75	MC789P	0.66	—	0.66	243	1.60
12	0.90	MC790P	1.24	—	1.08	263	0.77 $\frac{1}{2}$
13	1.05	MC792P	0.66	—	0.66	293	0.97 $\frac{1}{2}$
14	1.25	MC799P	0.66	—	0.65	300	1.75
18	0.85	MC1303L	2.70	—	2.25	310	1.25
18A	1.10	MC1304P	3.60	—	3.00	320	0.72 $\frac{1}{2}$
19	0.85	MC1582G	4.61	—	3.84	320	1.75
20	1.30	MC1435L	3.45	—	2.87	435	1.47 $\frac{1}{2}$
20A	1.60	MC1590G	0.95	—	0.82	521	1.32 $\frac{1}{2}$
21	1.60	Data sheets	0.12	extra	—	522	3.60
22	1.80	FAIRCHILD	1-5	6-11	12+	530	4.95
23	1.80	29	2p	3p	4p	511	—
26	1.00	29A	1-65	0.40	0.37	520	0.97 $\frac{1}{2}$
28A	0.75	30	1.40	0.40	0.37	TAD100	1.97 $\frac{1}{2}$
28B	1.05	35	1.25	0.40	0.37	TAD110	1.87 $\frac{1}{2}$
29	0.90	36	0.75	1.05	0.97	MULLARD DTL	—
29A	1.65	39	0.85	0.60	0.57	FCH101	0.87 $\frac{1}{2}$
30	1.40	41	1.10	0.75	0.67	FCH121	1.05
35	1.25	42	1.10	0.75	0.67	FCH201	1.32 $\frac{1}{2}$
36	0.75	43	1.40	1.20	1.00	FCH231	1.50
39	0.85	44	1.20	0.75	0.67	FCJ101	1.82 $\frac{1}{2}$
41	1.10	45	1.25	0.85	0.75	FCJ111	1.55
42	1.10	46	0.75	—	—	FCJ201	1.80
43	1.40	47	1.40	—	—	FCJ211	2.75
44	1.20	48	2.05	—	—	FCJ101	4.37 $\frac{1}{2}$
45	1.25	49	1.60	—	—	FCY101	1.05
46	0.75	50	1.85	—	—	PLESSEY	2p
47	1.40	51	1.35	—	—	SL403A	2.12 $\frac{1}{2}$
48	2.05	52	1.65	—	—	SL701C	1.00
49	1.60	53	0.60	—	—	SL702C	1.00
50	1.85	54	1.10	—	—	GENERAL	—
51	1.35	55	2.40	—	—	ELECTRIC	4p
52	1.65	59	1.65	—	—	PA222	4.37 $\frac{1}{2}$
53	0.60	64	1.30	—	—	PA230	1.12 $\frac{1}{2}$
54	1.10					PA234	1.07 $\frac{1}{2}$
55	2.40					PA237	1.87 $\frac{1}{2}$
59	1.65					PA246	2.62 $\frac{1}{2}$
64	1.30					PA424	2.25

Post & Packing 10p per order.

TELEPHONE 01-452 0161 **A. MARSHALL & SONS LTD.** TELEX 21422  
28 CRICKLEWOOD BROADWAY, LONDON, N.W.2  
CALLERS WELCOME 9.5-30 SATURDAY 9.5 THURSDAY 9.1  
SEE OUR MAIN ADVERTISEMENT ON PAGE 363 FOR SEMICONDUCTORS

# Simple do-it-yourself stereo

The book that tells how to build a stereo system, with only a screw-driver and no knowledge of electronics. At only 25p it's just right for the D.I.Y. enthusiast. From your local Audio dealer or post this coupon with a 25p postal order to:



**Mullard UNILEX** 13 Walpole Road Twickenham, Middx.

Name \_\_\_\_\_

Address \_\_\_\_\_



## TRANSISTORISED TWO-WAY TELEPHONE INTERCOM

Operative over amazingly long distances. Separate call and press to talk buttons. 2-wire connection. 1000's applications. Beautifully finished in ebony. Supplied complete with batteries and wall brackets. **£8-97.** P. & P. 17p.



**AVO CT471A MULTIMETER**  
Battery operated, fully transistorised. Sensitivity 100mΩ/v. Measures AC/DC Voltages 12mV to 1,200V. AC/DC Current 12uA to 1.2 Amp. Resistance 12 ohm to 120 MΩ HF, VHF, UHF. Voltage with multiplier 4v to 400v up to 50 Mc/s, 40mV to 4V up to 1,000 Mc/s. Offered in perfect condition. **£55 each.** Carr. 50p.

### CRYSTAL CALIBRATORS No. 10

Small portable crystal controlled wavemeter. Size 7" x 7" x 4". Frequency range 500 Kc/s, 10 Mc/s (up to 30 Mc/s on harmonics). Calibrated dial. Power requirements 300 V.D.C. 15mA and 12 V.D.C. 0.2A. Excellent condition. **£3-47.** Carr. 37p.

**B.C. 221 FREQUENCY METERS**  
latest release 125kHz to 20MHz. Excellent condition. Fully tested and checked and complete with calibrator charts. **£27-50 each.** Carr. 50p.

### AM/FM SIGNAL GENERATORS

Oscillator Test No. 2. A high quality precision instrument manufactured by the Ministry by Airtec. Frequency coverage 20-80 Mc/s. AM C.W./F.M. Incorporates precision dial, level meter, precision attenuator 1μV-100mV. Operation from 12V d.c. or 0/10/200/250V a.c. Size 12" x 8" x 9". Supplied in brand new condition complete with all connectors fully tested. **£45.** Carr. £1.

### AVO CT-38 ELECTRONIC MULTIMETERS

High quality 97 instrument which measures a.c. and d.c. Voltage. Current. Resistance and Power Output Ranges d.c. volts 250mV-10,000V (10 megΩ-110 megΩ input). D.c. current 10uA-25A. Ohms. 0-1,000 megΩ a.c. volt 100mV-250V (with R.F. measuring head up to 250MHz) a.c. current 10uA-25A. Power output 50 micro-watts-5 watts. Operation 0/10/200/250V a.c. Supplied in perfect condition complete with circuit lead and R.F. probe. **£25.** Carr. 75p.

### ADMIRALTY 62B RECEIVERS

High quality 10 valve receiver manufactured by Murphy. Coverage in 5 bands 150-300 Kc/s; 500 Kc/s-1.5 Mc/s; 3-9-30.5 Kc/s. I.F. 500/KHz. Incorporates 2 R.F. and 3 I.F. stages, bandpass filter, noise limiter, crystal controlled B.F.O. calibrator I.F. output, etc. Built-in speaker, output for phones. Operation 150/230V a.c. Size 19" x 13" x 16". Weight 114lb. Offered in good working condition. **£22-50.** Carr. £1-50. With circuit diagrams. Also available B41 L.F. version of above. 15KHz-700Hz. **£17-50.** Carr. £1-50.

### TO-2 PORTABLE OSCILLOSCOPE

A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CF8-1 MHz. Input imp. 2 megΩ 25 P.F. Illuminated scale. 2in. tube. 115 x 180 x 330mm. Weight 8lb. 220/240 V a.c. Supplied brand new with handbook. **£22-50.** Carr. 50p.

### TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity 0.1V/cm. Bandwidth 1.5 cps-1.5MHz. Input imp. 2 megΩ 25P.F. X amp. sensitivity 0.9V p-p/cm. Bandwidth 1-cps-800KHz. Input imp. 2 megΩ 20P.F. Time base. 3 ranges 10 cps-300KHz. Synchronization. Internal/external. Illuminated scale 140 x 215 x 330 mm. Weight 13lb 220/240V. A.C. Supplied brand new with handbook. **£27-50.** Carr. 50p.

# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
● LOW COST ● QUICK DELIVERY ● OVER 100 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
500uA	£3-12	50uA	£3-12
1mA	£2-97	50-0-50uA	£2-97
20V d.c.	£2-97	100uA	£2-97
50V d.c.	£2-97	100-0-100uA	£2-87
300V d.c.	£2-97	500uA	£2-62
1A d.c.	£2-97	1A d.c.	£2-47
50-0-50uA	£2-37	20V d.c.	£2-47
100uA	£2-37	50V d.c.	£2-47
100-0-100uA	£2-25	300V a.c.	£2-62
		800V d.c.	£2-47
		VU Meter	£2-37

## "SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/4" x 4 1/4" fronts.		Type MR.82P. 1 21/32" square fronts.	
50mA	£2-60	150mA	£1-37
100mA	£2-60	200mA	£1-37
500mA	£2-60	300mA	£1-37
1A	£2-60	500mA	£1-37
5A	£2-60	750mA	£1-37
15A	£2-60	1A	£1-37
30A	£2-60	2A	£1-37
20V d.c.	£2-60	5A	£1-37
50V d.c.	£2-60	10A	£1-37
150V d.c.	£2-60	3V d.c.	£1-37
300V d.c.	£2-60	15V d.c.	£1-37
15V a.c.	£2-60	20V d.c.	£1-37
300V a.c.	£2-60	100V d.c.	£1-37
8 Meter	£2-60	150V d.c.	£1-37
		300V d.c.	£1-37
		500V d.c.	£1-37
		750V d.c.	£1-37
		15V a.c.	£1-37
		50V a.c.	£1-37
		150V a.c.	£1-37
		300V a.c.	£1-37
		500V a.c.	£1-37
		8 Meter	£1-60
		VU meter	£2-10

Type MR.52P. 2 1/2" square fronts.		Type MR.45P. 2 1/2" square fronts.	
50uA	£2-10	50uA	£2-25
50-0-50uA	£2-60	50-0-50uA	£2-10
100uA	£2-60	100uA	£2-10
100-0-100uA	£2-37	500-0-500uA	£1-37
500-0-500uA	£2-25	1mA	£1-60
1mA	£2-60	5mA	£1-60
5mA	£2-60	10mA	£1-60
10mA	£2-60	50mA	£1-60
50mA	£2-60	100mA	£1-60
1A	£2-60	5A	£1-60
5A	£2-60	10A	£1-60
10V d.c.	£2-60	20A a.c.	£1-60
		30A a.c.	£1-60

Type MR.65P. 3 1/2" x 3 1/2" fronts.		Type MR.65 Series 3 1/2" square fronts.	
50uA	£3-37	500mA	£1-75
50-0-50uA	£2-75	1A	£1-75
100uA	£2-75	5A	£1-75
100-0-100uA	£2-60	15A	£1-75
200uA	£2-60	30A	£1-75
500uA	£2-37	50A	£1-75
500-0-500uA	£2-10	75A	£1-75
1mA	£2-10	100A	£1-75
5mA	£2-10	500mA	£1-60
10mA	£2-10	1A	£1-60
50mA	£2-10	5A a.c.	£1-60
100mA	£2-10	10A a.c.	£1-60
5A	£2-10	50A a.c.	£1-60
15A	£2-10	100A a.c.	£1-60
10A	£2-10	20A a.c.	£1-60
15A	£2-10	30A a.c.	£1-60
20A	£2-10		
30A	£2-10		
50A	£2-37		
5V d.c.	£2-10		
10V d.c.	£2-10		

## "SEW" BAKELITE PANEL METERS

Type MR.65 Series 3 1/2" square fronts.	
500mA	£1-75
1A	£1-75
5A	£1-75
15A	£1-75
30A	£1-75
50A	£1-75
75A	£1-75
10V d.c.	£1-75
20V d.c.	£1-75
50V d.c.	£1-75
150V d.c.	£1-75
300V d.c.	£1-75
50V a.c.	£1-75
150V a.c.	£1-75
300V a.c.	£1-75
500mA a.c.	£1-75
1A a.c.	£1-75
5A a.c.	£1-75
10A a.c.	£1-75
15A a.c.	£1-75
20A a.c.	£1-75
30A a.c.	£1-75
50A a.c.	£1-75
100mA	£1-75
VU meter	£2-10

## \* MOVING IRON - ALL OTHERS MOVING COIL Please add postage

## "SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to working. Available in the following ranges:

50uA	£4-50	20V d.c.	£3-97
100uA	£4-25	50V d.c.	£3-87
1mA	£3-97	300V d.c.	£3-87
50-0-50uA	£4-25	Dual range	
1-0-1mA	£3-97	500mA/5A d.c.	£4-25
1A d.c.	£3-97	5V/50V d.c.	£4-25
5A d.c.	£3-97	Triple range	
10V d.c.	£3-97	1mA/10mA/100mA	

MARCONI TF142E DISTORTION FACTOR METERS. Excellent condition. Fully tested. **£20.** Carr. 75p.

## TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1Ω-11.1 megΩ 6 Ranges ±1%. L. 1μH-111 HENRY8 6 Ranges -25%. C. 10pF-1110 pF d. 6

Ranges ±2%. TURNS RATIO 1:1/1000-1:1/100. 6 Ranges ±1%. Bridge voltage at 1,000 cps. Operated from 9 volts, 100uA. Meter indication. Attractive 2 tone metal case. Size 7" x 3" x 2 1/2". **£20.** P. & P. 25p.

COSON 1049 DOUBLE BEAM OSCILLOSCOPE. D.c. coupled. Band width 1kc/s. Perfect order. **£25.** Carr. £1.50.

TE-16A Transistorised Signal Generator. 5 ranges 400 KHz-20 MHz. An inexpensive instrument for the handyman. Operates on 9v battery. Wide, easy to read scale. 800 kHz modulation. 5 1/2" x 5 1/2" x 3 1/2". Complete with instructions and leads. **£7-97.** P. & P. 20p.

LELAND MODEL 27 BEAT FREQUENCY OSCILLATORS Frequency 0-20 Kc/s on 2 ranges. Output 500Ω or 5kΩ. Operation 200/250V. A.C. Supplied in perfect order. **£12-50.** Carr. 50p.

MARCONI TF885 VIDEO OSCILLATORS. 0-5MHz. Sine Square Wave. **£45.** Carr. £1.

## LAFAYETTE TE48 RESISTANCE CAPACITY ANALYSER

2P.F.-2,000 mid 2 ohms-200 megohms. Also checks impedance, turns ratio, insulation, 200/250V a.c. **Brand New £17-50** Carr. 37p.


## CLASS D WAVEMETERS

A crystal controlled heterodyne frequency meter covering 1.7-8 Mc/s. Operation on 6V d.c. Ideal for amateur use. Available in good used condition. **£2-97.** Carr. 37p. or brand new. **£7-97.** Carr. 37p.

MARCONI TF185M BEAT FREQUENCY OSCILLATORS. 0-40KHz. **£20.** Carr. £1-50.
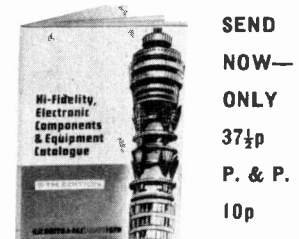
# Latest Catalogue

Our latest edition giving full details of a comprehensive range of HI-FI/EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p (10/5), 248 pages, fully illustrated and detailing thousands of items at bargain prices.



SEND NOW— ONLY 37p P. & P. 10p

G. W. SMITH & CO (RADIO) LTD.  
Also see next two pages

# SEMI-CONDUCTORS/VALVES

BRAND NEW & FULLY GUARANTEED

# HI-FI EQUIPMENT

SAVE UP TO 33 1/3% OR MORE

SEND S.A.E. FOR DISCOUNT PRICE LISTS AND PACKAGE OFFERS!



# GARRARD

FULL CURRENT RANGE OFFERED, BRAND NEW AT FANTASTIC SAVINGS

- 2023T/C stereo \$9-87 8L72B \$26-97
  - 40 MKII stereo \$8-40 AP76 \$20-97
  - 3000 stereo \$10-50 8L75B \$30-75
  - SP25 MKIII \$11-75 8L95B \$40-97
  - 8L65B \$14-97 401 \$29-37
- Carriage 37ip extra each item.
- TEAK PLINTHS AND PERSPEX COVERS
- For SP25, 8L65, 8L55, 3000, 2023T/C, 2025, 1000. \$3-97!
  - For AP75, 8L75, 8L95. \$5-97!
  - For SP25 etc. to operate with lid in place \$5-97!
- Carriage 37ip extra each type.



Full range of Garrard accessories available.

## TRANSISTORS

1N914	7p	AC187	30p	BY100	15p	OB2	38p	25Z4	30p	EL55	35p
1N4001	8p	AC188	30p	BY124	15p	OB2	45p	25Z5	45p	EM80	40p
1N4002	8p	AC189	30p	BY125	15p	OB2	50p	25Z6	50p	EM81	50p
1N4003	10p	AC190	30p	BY126	15p	OB2	55p	30C15	55p	EM84	55p
1N4004	10p	AC191	25p	BY210	40p	1R5	35p	30C17	55p	EM85	55p
1N4005	10p	AC192	25p	BY211	35p	1R5	25p	30C18	75p	EM87	43p
1N4006	15p	AC211	25p	BY212	30p	1T4	25p	30F5	85p	EY51	40p
1N4007	20p	AC222	17p	BY213	25p	IU5	50p	30FL1	70p	EY86	40p
1N4148	7p	AC228	17p	MJ480	97p	1U5	50p	30FL12	92p	EY87	40p
1N5004	15p	AC240	15p	MPF102	11-25	2D21	30p	30FL14	75p	EZ40	45p
2G301	20p	D140	50p	MPF103	45p	304	40p	30L10	85p	EZ41	45p
2G302	25p	AD149	50p	MPF103	45p	384	35p	EZ80	50p	EZ80	25p
2G303	25p	AD161	37p	MPF104	37p	3V4	45p	30P12	80p	EZ81	25p
2G306	30p	AD162	37p	MPF105	40p	5R4	40p	30P19	80p	GZ32	48p
2G308	30p	AF114	25p	NK T213	25p	5U4	45p	30P17	70p	GZ34	60p
2G309	30p	AF115	25p	NK T214	25p	5V4	45p	30P13	90p	KT86	11-70
2G311	25p	AF116	25p	NK T216	37p	6A6	45p	30P14	80p	KT88	11-75
2G312	25p	AF117	25p	NK T217	37p	6Z4G	40p	30P11	85p	PA8C90	50p
2G381	25p	AF118	82p	NK T224	32p	630L2	75p	35L6	50p	MU14	50p
2N696	17p	AF119	20p	NK T241	27p	6AC7	25p	33W4	30p	PA8C90	50p
2N697	17p	AF124	20p	NK T261	20p	6AG7	40p	35Z4	30p	PC86	60p
2N698	42p	AF126	17p	NK T271	25p	6AK5	30p	35Z5	45p	PC87	45p
2N706	15p	AF127	17p	NK T272	25p	6AK6	57p	50B5	45p	PC90	45p
2N708	15p	AF128	30p	NK T274	30p	6AL5	20p	50C5	40p	PC98	40p
2N714	25p	AF190	82p	NK T275	25p	6B4E	30p	63A2	45p	PC98	40p
2N716	25p	AF181	42p	NK T281	27p	6AQ5	35p	63W4	30p	PC98	50p
2N718	37p	AF186	40p	NK T403	75p	6AT8	37p	16Z5	50p	PC98	50p
2N729	22p	AF239	42p	NK T404	82p	6AU6	25p	5763	70p	PC98	50p
2N930	25p	AS926	25p	NK T405	75p	6AV6	30p	6146	11-50	PCF80	30p
2N931	25p	AS927	25p	NK T407	25p	6BE6	30p	6A231	50p	PCF82	34p
2N1132	20p	AS928	25p	NK T473	25p	6BE6	30p	CY31	35p	PCF84	50p
2N1302	20p	ASZ17	42p	OA5	20p	6BH6	45p	DAF91	25p	PCF86	60p
2N1303	25p	AU10	97p	OA10	25p	6BJ6	45p	DAF96	45p	PCF86	60p
2N1304	25p	BAY31	7p	OA47	10p	6BQ7A	40p	DF91	25p	PCF80	50p
2N1305	25p	BC107	12p	OA70	10p	6BR7	85p	DP96	40p	PCF80	50p
2N1306	25p	BC108	12p	OA79	10p	6BR8	85p	DK91	35p	PCF80	50p
2N1307	25p	BC109	12p	OA81	10p	6BW6	85p	DK92	35p	PCF80	50p
2N1308	25p	BC113	25p	OA85	12p	6BW7	75p	DK96	42p	PCF80	50p
2N1309	25p	BC116	40p	OA90	10p	6BZ6	30p	DL82	42p	PCF82	35p
2N1613	25p	BC125	55p	OA91	7p	6C4	33p	DL84	45p	PCF82	35p
2N1711	25p	BC126	55p	OA95	7p	6D16	50p	DL96	42p	PCF82	35p
2N1888	32p	BC147	17p	OA200	7p	6CL6	50p	DM70	32p	PCF82	35p
2N1893	32p	BC148	17p	OA201	7p	6C4	50p	DY86	32p	PCF82	35p
2N2147	75p	BC149	20p	OA210	17p	6CW4	60p	DY87	32p	PL200	70p
2N2160	65p	BC167	15p	OC19	37p	6F64	30p	E88CC	65p	PL26	55p
2N2193	47p	BC172	17p	OC20	97p	6F13	30p	E180F	65p	PL26	55p
2N2217	40p	BC177	25p	OC22	50p	6F14	65p	E180F	65p	PL26	55p
2N2218	40p	BC182L	10p	OC23	60p	6F15	65p	EAF42	35p	PL43	45p
2N2219	40p	BC184L	12p	OC24	60p	6F18	45p	E8B1	20p	PL48	40p
2N2368	37p	BC196	25p	OC25	37p	6F23	45p	EBC41	35p	PL500	75p
2N2369	20p	BC212L	12p	OC26	25p	6H6	20p	EBC81	35p	PL504	80p
2N2369A	20p	BCY30	25p	OC28	62p	6J4	20p	EF80	40p	PY32	55p
2N2454	30p	BCY31	30p	OC29	62p	6J5	20p	EF83	40p	PY32	55p
2N2455	30p	BCY32	30p	OC30	62p	6J5GT	20p	EF89	35p	PY80	35p
2N2646	50p	BCY33	25p	OC36	25p	6J6	20p	ELB21	60p	PY81	30p
2N2647	50p	BCY34	25p	OC41	25p	6J7	20p	E8C6	60p	PY81	30p
2N2923	17p	BCY38	40p	OC42	30p	6K6G	35p	E8C8	60p	PY88	38p
2N2924	17p	BCY42	15p	OC44	17p	6L6GT	35p	ECU40	60p	PY88	38p
2N2925	17p	BCY43	20p	OC45	17p	6L20	40p	ECU84	60p	PY88	38p
2N2926G	12p	BCY71	30p	OC46	17p	6QD2	40p	EC88	40p	U25	75p
2N2926Y	12p	BCY72	15p	OC70	12p	68A7	40p	ECF80	35p	U26	75p
2N2926O	12p	BCZ11	15p	OC71	15p	68G7	35p	ECF82	35p	U50	32p
2N3053	25p	BD123	25p	OC72	25p	68T7	35p	ECF86	65p	U52	33p
2N3054	50p	BD123	30p	OC73	30p	68T7	35p	ECH21	57p	U191	65p
2N3055	75p	BD124	80p	OC74	30p	68L7	35p	ECH35	60p	U281	40p
2N3391A	30p	BF115	25p	OC75	25p	68N7	35p	ECH42	70p	U282	40p
2N3416	37p	BF117	40p	OC76	25p	68Q7	35p	ECH81	30p	U301	40p
2N3370	11-25	BF167	25p	OC77	40p	6V	20p	ECH83	40p	U801	21
2N3702	12p	BF178	25p	OC78	25p	6V6G	25p	ECL80	40p	UABC80	35p
2N3703	12p	BF180	27p	OC81	25p	6X5GT	30p	ECL82	35p	UAF42	55p
2N3704	17p	BF181	27p	OC81B	20p	6X5GT	30p	ECL83	35p	UFC41	60p
2N3705	15p	BF182	25p	OC83	25p	6X6G	40p	ECL86	40p	UFC42	60p
2N3706	25p	BF184	25p	OC84	25p	6X6GT	27p	EP37A	40p	UBF80	40p
2N3707	15p	BF185	25p	OC139	25p	10C2	50p	EF39	60p	UBF89	35p
2N3708	17p	BF194	17p	OC140	37p	10F1	50p	EF40	60p	UCC84	48p
2N3709	15p	BF195	15p	OC169	20p	10P13	55p	EF41	60p	UC85	40p
2N3710	12p	BF200	30p	OC170	25p	10P14	11-10	EF42	70p	UC86	55p
2N3711	12p	BF224	30p	OC171	30p	12A76	30p	EF80	60p	UC87	55p
2N3819	35p	BF225	30p	OC200	40p	12A77	30p	EF85	50p	UC87	55p
2N3903	25p	BF244	47p	OC201	60p	12A77	30p	EF86	30p	UCHR1	35p
2N3904	25p	BFX12	25p	OC202	75p	12A76	30p	EF89	28p	UCL82	35p
2N3905	30p	BFX13	25p	OC203	60p	12A77	30p	EF91	35p	UCL83	60p
2N3906	30p	BFX19	30p	OC204	40p	12A7X	30p	EF92	40p	UF41	60p
2N4058	17p	BFX30	30p	OC205	62p	12B86	35p	EF193	30p	UF80	35p
2N4059	25p	BFX44	37p	OC207	75p	12B87	40p	EP184	45p	UF85	40p
2N4061	15p	BFX85	40p	OC207	75p	12B87	40p	EP184	45p	UF85	40p
2N4062	15p	BFX86	40p	OC207	75p	12B87	40p	EP184	45p	UF85	40p
2N4286	15p	BFX87	35p	ORP60	40p	20D1	45p	EL33	11-25	UF89	35p
2N4287	17p	BFY90	25p	P346A	25p	20F2	75p	EL34	25p	UL41	60p
2N4288	15p	BFY18	25p	PL4001	14p	20L1	11-10	EL41	55p	UL41	30p
2N4289	17p	BFY20	65p	PL4002	16p	20P1	50p	EL42	55p	UL84	45p
2N4290	15p	BFY50	25p	PL4003	16p	20P3	60p	EL41	55p	UR85	30p
2N4291	15p	BFY51	20p	PL4004	17p	20P4	11-10	EL84	25p	VR150/30	35p
2N4292	15p	BFY52	25p	PL4005	17p	20P5	11-20	EL85	45p	VR150/30	35p
2N4354	27p	BFY90	67p	PL4006	20p	25L6	45p	EL81	32p	VR150/30	35p
2N4355	27p	B8X19	17p	PL4007	24p						
28102	25p	B8X20	17p	T1843	40p						
28103	37p	B8X21	37p	T1844	12p						
28104	37p	B8X76	17p	T1845	17p						
40220	50p	B8Y26	15p	T1846	17p						
40361	50p	BC107/8/9	15p								
40362	60p	BC107/8/9	15p								
AC107	37p	B8Y38	20p	25+	10p						
AC126	25p	B8Y39	25p	100+	9p						
AC127	25p	B8Y39	25p	500+	7p						
AC128	25p	B8Y39	25p	2N3055							
AC154	15p	B8Y56	90p	100+	65p						
AC176	25p	B8Y93A	15p	100+	50p						

## VALVES

38p	25Z4	30p	EL55	35p
45p	25Z5	45p	EM80	40p
50p	25Z6	50p	EM81	50p
55p	30C15	55p	EM84	55p
55p	30C17	55p	EM85	55p
25p				

### RUSSIAN C1-16 DOUBLE BEAM OSCILLOSCOPES

5MHz Pass Band. Separate Y1, Y2 amplifiers. Calibrated triggered sweep from 0.2µsec to 100msec/cm. Supplied complete with all accessories and instructions. £87. Carr. paid.



### MARCONI CT44/TF956 AF ABSORPTION WATTMETER

1 µwatt to 6 watts. £20. Carr. £1.

### TELLI DECADE RESISTANCE ATTENUATOR

Variable range 0-11dB. Connections. Unbalanced T and Bridge T. Impedance 600 Ω range (0-1dB × 10) + (1dB × 10) + 10 + 20 + 30 + 40dB. Frequency: d.c. to 200kHz. (—3dB). Accuracy: 0.05dB. + indication 0.5 × 0.01. Maximum input less than 4W (50V). Built in 600 Ω load resistance with internal/external switch. Brand new £27.50. P. & P. 25p.




### BELCO AF-5A SOLID STATE SINE SQUARE WAVE C.R. OSCILLATOR



Sine 18-200,000Hz; Square 18-50,000Hz. Output max +10dB (10K Ω). Operation internal batteries.

Attractive two-tone case 7 1/2" × 5 1/2" × 2 1/2". Price £17.50. Carr. 17p.
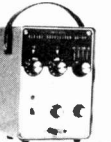
### BELCO DA-20 SOLID STATE DECADE AUDIO OSCILLATOR



New high quality portable instrument. Sine 1Hz to 100kHz. Square 20Hz to 20kHz. Output max +10dB (10K Ω). Operation 220/240V a.c. Size 215mm × 150mm × 120mm. Price £27.50. Carr. 25p.

### T.E.40 HIGH SENSITIVITY A.C. VOLTMETER

10 meg. input 10 ranges: -0.1 / -0.03 / -1 / -3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s. ±1-2mV. Decibels -40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. £17.50. Carr. 25p.



### TE-65 VALVE VOLTMETER



High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. £17.50. P. & P. 30p. Additional Probes available: R.F. £2.12; H.V. £2.50.

### 230 VOLT A.C. 50 CYCLES RELAYS



Brand New. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 15p. £100 lots £40. Quantities available.

## MULTIMETERS for EVERY purpose!



**TECH PT-34, 1,000 O.P.V.** 0/10/50/250/500/1,000V a.c. and d.c. 0/1/100/500mA. d.c. 0/100K. £1.97; P. & P. 12p.



**MODEL TE-200, 20,000 O.P.V.** Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/30/1A/250MA. 0/60K/6 meg. -20 to +62dB. £3.75. P. & P. 15p.



**MODEL 500, 30,000 O.P.V.** with overload protection, mirror scale 0/5/25/125/1,000V d.c. 0/2.5/10/25/100/250/500/1,000V a.c. 0/50/500/50/1,000 mA. 12 amp. d.c. 0/60K/6 Meg./60 Meg. £3.87; Post paid.



**MODEL TE-70, 30,000 O.P.V.** 0/3/15/60/300/600/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30/1A/3/30/300MA. 0/16K/160K/1.6M/16 meg. £5.50. P. & P. 15p.




**TMK MODEL TW-50K, 46 ranges, mirror scale.** 60K Volt d.c. 5K/Volt a.c. D.c. volts: 0.125, 0.25, 1.25, 2.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 10K, 100K, 1 meg., 10 meg. Decibels: -20 to +81.3dB. £3.87; P. & P. 17p.



**TE-900 20,000 VOLT GIANT MULTIMETER.** Mirror scale and overload protection. 6in full view meter. 2 colour scale. 0/2.5/10/250/1,000/5,000V a.c. 0/25/125/510/500/250/1,000V d.c. 0/50µA/1/10/100/500/10A. d.c. 0/2K/200K/20 meg. ohm. £15. P. & P. 25p.



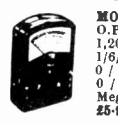**MODEL 5025, 57 ranges, giant 6 1/2in meter, polarity reverse switch.** Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. Volts: 0.125, 0.25, 1.25, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50µA, 2.5, 5, 25, 50, 250, 500mA, 5, 10A. Resistance: 2K, 10K, 100K, 1 meg, 10 meg. Decibels: -20 to +85dB. £12.50. P. & P. 17p.



**MODEL TE12, 20,000 O.P.V.** 0/0.6/30/120/600/1,200/3,000/6,000V d.c. 1/6/30/120/600/1,200V a.c. 0/60µA/3/5/60/600MA. 0/1K/600K/6meg./60Megohm 30PF. 2 MF. £5.97; P. & P. 17p.

### FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and IC0, npn or pnp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £3.97; P. & P. 15p.



**HONOR TE.10A, 20k Ω/Volt** 5/25/50/250/500/2,500V a.c. 10/50/100/500/1,000V a.c. 0/50/1A/250MA. 0/60K/6 meg. ohm. -20 to +22dB. 10-0, 100 mfd. 0.100-0.1 mfd. £3.47; P. & P. 15p.

**MODEL TE-300, 30,000 O.P.V.** Mirror scale, overload protection 0/0.6/3/15/60/300/1,200V d.c. 0/6/30/120/600/1,200V a.c. 0/30/1A/300MA/600MA/600MA/8 meg. -20 to +63dB. £5.97; P. & P. 15p.

**MODEL TE 80, 20,000 O.P.V.** 0/10/50/100/500/1,000V. a.c. 0/5/25/50/250/500/1,000V d.c. 0.5µA. 5/50/500MA. 0/6K/60K/600K/6 Meg. £4.87; P. & P. 15p.

**MODEL TE-90, 50,000 O.P.V.** Mirror scale, overload protection. 0/0.13/60/300/600/1,200V d.c. 0/6/30/120K/1,200V d.c. 0/6/30/60K/600MA. d.c. 16K/160K/1.6/16 meg. -20 to +63dB. £7.50. P. & P. 15p.

**TMK MODEL TW-200B.** Features: Resettable Overload Button. Sensitivity: 20K Ω/Volt d.c. 5K Ω/Volt a.c. D.c. volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 0-0.5, 0.5, 5, 50, 500mA. Resistance: 0-5K, 50K, 0-500K, 5 meg. Decibels: -20 to +62dB. £11.50. P. & P. 17p.

**MODEL AB-100D, 100K Ω/Volt.** 5in. mirror scale. Built-in meter protection 0/3/12/60/120/300/600/1,200V d.c. 0/6/30/120/300/600V a.c. 0/10µA/6/60/300/12A. 0/2K/200K/2M/200M. -20 to +17dB. £12.50. P. & P. 17p.


**TMK LAB TESTER, 100,000 O.P.V.** 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5/Volt a.c. D.c. volts: 0.5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100µA, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: -10 to +40dB. Plastic case with carrying handle, size 7 1/2" × 6 1/2" × 3 1/2". £18.90. P. & P. 25p.

### SKYWOOD SW-500



50 K Ω/Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20µA/6/60/600mA. Resistance 10K/100K. -20 to +57dB. £7.50. P. & P. 15p.

### 270° WIDE ANGLE

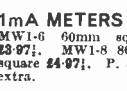

**1mA METERS** MW1-6 60mm square £3.97; MW1-8 80mm square £4.97; P. & P. extra.



**UNR-30 RECEIVER** 4 Bands covering 550KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15.75. Carr. 37p.

**WS62 TRANSCEIVERS** Large quantity available for EXPORT! Excellent condition. Enquiries invited.



**UR-IA SOLID STATE COMMUNICATION RECEIVER** 4 Bands covering 55KHz-30MHz. FET, 8 Meter, Variable BFO for 8RB. Built in Speaker, Brandread, Sensitivity Control. 220/240V a.c. or 12V d.c. 12 1/2in. 4 1/2in. 7in. Brand new with instructions. £25. Carr. 37p.



**LAFAYETTE HA-600 RECEIVER** General coverage 150-400KHz, 500KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, 8 Meter, Brandread, RF Gain. 15in. × 9 1/2in. × 8 1/2in. 220/240V a.c. or 12V d.c. Brand new with instructions. £45. Carr. 30p.



**LAFAYETTE HA-800 SOLID STATE AMATEUR COMMUNICATION RECEIVER** 3-5-4, 7-7-3, 14-14-35, 21-21-45, 28-29-7, 30-54MHz. Dual conversion, 2 mech. filters, product detector, variable BFO, 8 Meter, 100KHz calibrator. 220/240V a.c. or 12V d.c. 15in. 9 1/2in. 8 1/2in. Brand new with instructions. £57.50. Carr. paid (100KHz Crystal £1.97; extra).

### FULL RANGE OF TRIO EQUIPMENT

**EDDYSTONE VHF RECEIVERS MODEL 7702.** 19-185 Mc/s. Excellent condition. £150.

**VOLTAGE STABILIZER TRANSFORMERS** 150-260V input. Output 230V. Available 150W or 225W. £12.50. Carr. 25p.

**AUTO TRANSFORMERS** 0/115/230V. Step up or step down. Fully shrouded. 150W. £2.37; P. & P. 17p. 300W. £3.25. P. & P. 22p. 500W. £4.97; P. & P. 32p. 1,000W. £7.25. P. & P. 37p. 1,500W. £8.57; P. & P. 42p.

### SOLID STATE VARIABLE A.C. VOLTAGE REGULATORS

Compact and panel mounting. Ideal for control of lamps, drills, electrical appliances, etc. Input 230/240V a.c. Output continuously variable from 20V to 230V. Model MR2305 5A 68 × 46 × 43mm, £3.87; Model MR2310 10A 90 × 68 × 60mm, £11.97; Postage 12p.

### "YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality - Low price - Immediate delivery

MODEL S-260 General Purpose Bench Mounting	MODEL S-260 B Panel Mounting
1A .....	1A .....
2.5A .....	2.5A .....
5A .....	5A .....
8A .....	8A .....
10A .....	10A .....
12A .....	12A .....
20A .....	20A .....

ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-260 VOLTS Special discounts for quantity

### POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiper. Continuous rating. Wide range ex-stock. Single hole fixing, in. dia. shafts. Bulk quantities available. 25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 3,000 ohms, 72p; P. & P. 7p. 50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms, £1.05. P. & P. 7p. 100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms, £1.37; P. & P. 7p.

### ADVANCE TEST EQUIPMENT

Brand new and boxed in original sealed cartons. **VM79. UHF MILLIVOLT METER.** 100 Kc/s to 1,000 Mc/s. a.c. 10 mV to 3V. D.c. 10 mV to 3V. Current 0.01 µA to 0.3 mA. Resistance 1 ohm to 10 megohm. £125. **TT15. TRANSISTOR TESTER.** Full range of facilities for testing PNP or NPN transistors in or out of circuit. £37.50. Carriage 50p per item.

## G.W.SMITH & CO. (RADIO) LTD

27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715  
 3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204  
 3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155  
 311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387  
 OPEN 9-6 MONDAY TO SATURDAY (EDGWARE ROAD 1/2 DAY THURSDAY)

All Mail Orders to - 11-12, Paddington Green, London, W.2. Tel: 01-262 5562 (Trade supplied)

# Catering to your particular service and production requirements

# Speciproduct

Our range includes:

**Aerosol Aids:** From Kontakt, Antistatic spray—Cold spray—Fluid spray—Graphite spray—Oil spray—Plastic spray—Soldering Lacquer—Switch and contact cleaners—Video spray for cleaning tape heads.

**Allen and Bristol Keys:** L Type. Standard and Long Arm.

**Contact Cleaners:** Diacrom Diamond Spatulas and Kontakt aerosols.

**Nutdrivers:** Hex—A.F.—Metric. Solid and hollow shaft and Palnut.

**Pliers, Seizers and Nippers:** Quality Precision made hand tools from Xcelite, and other leading makes of special tools.

**Screwdrivers:** Allen—Ball head—Bristol—Clutch head—Hold-e-Zee—Phillips and slotted.

**Soldering Equipment:** Resistance and heat controlled units. Also thermal wire stripping equipment from American Beauty and Waseco.

**Tweezers:** Quality Swiss made electronic tweezers.

**Ultrasonic Cleaners:** Bench models and accessories from American Beauty.

**Work Positioners:** The versatile Panavise 300 series for modern precision and allied industries.

**Work Viewers:** Distortion free Ednalite viewers and optical glass lenses for single and group viewing.

For catalogues and other information on the above write:

Special Products Distributors Ltd  
81 Piccadilly, London W1V 0HL

Tel: 01-629 9556  
Cables: Speciproduct London W1



### 2kW FAN HEATER

Three position switching to suit changes in the weather. Switch up for full heater (2kW), switch down for half heat (1kW), switch central blows cold for summer cooling—adjustable thermostat acts as auto control and safety cut-out. Complete kit £3.75. Post and ins. 38p.

12 volt Car Battery Trickle Charger. Made in Japan, this is very small and neat. Regular use will keep your car battery in good trim throughout the winter. Silly price £1.25 plus 23p postage and insurance.

### QUICK CUPPA

Mini Immersion Heater, 350w. 200/240v. Boils full cup in about two minutes. Use any socket or lamp holder. Have at bedside for tea, baby's food, etc. £1.25, post and insurance 14p. 12v. car model also available £1.



### PLINTH AND COVER

Suitable for most auto changers, teak base with tinted perspex cover, £4.25 plus 33p postage. Special set for Balfour autochanger £4.25 plus 33p postage.



### THYRISTOR LIGHT DIMMERS

Willdim incandescent lighting up to 600 w. from full brilliance to out. Assembled and wired ready to install. £3.



### AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in. or fully retractable. Suitable for 12v. positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.95 plus 25p post and ins.



### COMPUTER TAPE

2,400 ft. of the best magnetic tape money can buy. Made by E.M.I., 1in. wide almost unbreakable and on a 10 1/2in. metal computer spool. Users have claimed successful results with video as well as sound recordings £1 plus 33p post. Cassette to hold spool 50p extra.



### HORSTMANN "TIME & SET" SWITCH

(A 30 Amp Switch.) Just the thing if you want to come home to a warm house without it costing you a fortune. You can delay the switch on time of your electric fires, etc., up to 14 hours from setting time or you can use the switch to give a boost on period of up to 3 hours. Equally suitable to control processing. Regular price probably around £5. Special snip price £1.50. Post and ins. 23p.

### 1 HOUR MINUTE TIMER


Made by famous Smiths company, these have a large clear dial, size 4 1/2in. x 3 1/2in., which can be set in minutes up to 1 hour. After preset period the bell rings. Ideal for processing, a memory jogger or, by adding simple lever, would operate micro-switch. £1.15.



### THE FULL-FI STEREO SIX
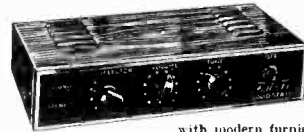
#### The amplifier sensation of the year

You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled and teak finished to blend



with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6 watts R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include "treble lift and cut", "balance" and separate mains on/off switch. Price is £9 plus 38p post and insurance.

### STANDARD WAFER SWITCHES

Standard size 1 1/2 wafer—silver-plated 5-amp contact, standard 3/4in spindle 2in long—with locking washer and nut. No. of Poles 2 way 3 way 4 way 5 way 6 way 8 way 9 way 10 way 12 way

1 pole	33p	33p	33p	33p	33p	33p	33p	33p	33p
2 poles	33p	33p	33p	33p	33p	33p	33p	55p	55p
3 poles	33p	33p	33p	33p	55p	55p	55p	75p	75p
4 poles	33p	33p	33p	55p	55p	55p	55p	95p	95p
5 poles	33p	33p	55p	55p	75p	75p	75p	£1.15	£1.15
6 poles	33p	55p	55p	55p	75p	75p	75p	£1.35	£1.35
7 poles	55p	55p	55p	75p	95p	95p	95p	£1.55	£1.55
8 poles	55p	55p	55p	75p	95p	95p	95p	£1.75	£1.75
9 poles	55p	55p	75p	75p	£1.15	£1.15	£1.15	£1.95	£1.95
10 poles	55p	55p	75p	95p	£1.15	£1.15	£1.15	£2.15	£2.15
11 poles	55p	75p	75p	95p	£1.35	£1.35	£1.35	£2.35	£2.35
12 poles	55p	75p	75p	95p	£1.35	£1.35	£1.35	£2.55	£2.55

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. S.A.E. with enquiries please.

### SPARTAN Portable RADIO

Long and medium wave, 7 transistor, size 6in. x 4in. x 1 1/2in. with larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, carplug and case. £3.75 plus 25p post and ins.



### MULTI-SPEED MOTOR

Replacement in many well known food mixers. Six speeds are available. 500, 850, and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixers normally go) and 8,000, 12,000 and 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. Very powerful and useful motor size approx. 2in. diameter 5in. long. Price 80p plus 23p post and ins.



### MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10A. Extremely well made by a German Electrical Company. Overall size 2 1/2 x 2 1/2 in. £1 each.



### DOUBLE ENDED MAINS MOTOR

On feet with holes for screw-down fixing. To drive models, oven, blower heater, etc. 50p each, plus 18p post and insurance, 6 or more post free.



### 0.005mFd TUNING CONDENSER

Proved design, ideal for straight or reflex circuits. 13p each, £1.20 doz.



**ELECTRONICS (CROYDON) LTD**  
Dept. PE, 266 London Road, Croydon CR0 2TH  
Also 102/3 Tamworth Road, Croydon



### ELECTRIC CLOCK WITH 25 AMP SWITCH

Made by Smith's, these units are as fitted to many top quality cookers to control the oven. The clock is mains driven and frequency controlled so it is extremely accurate. The two small dials enable switch on and off times to be accurately set. Ideal for switching on tape recorders. Offered at only a fraction of the regular price—new and unused only **£2**, less than the value of the clock alone—plus insurance 14p.



### FLUORESCENT CONTROL KITS

Each kit comprises seven items—Choke, 2 tube ends, starter, starter holder and 2 tube clips, with wiring instructions. Suitable for normal fluorescent tubes or the new "Grolux" tubes for fish tanks and indoor plants. Chokes are super-silicon, mostly resin filled. Kit A—15-20W. Kit B—30-40W. Kit C—60W. Kit D—80W. Kit E—65W. Kit F—150W. Kit G—81 125W tube **£1.75**. Kit H is for 6in, 9in and 12in miniature tubes, **£1**. Kit MF2 for 2 1/2in 13W miniature tube, **£1**. Postage on Kits A and B 23p for one or two kits then 23p for first kit then 18p for each kit ordered. Kit C, D and E 23p on first kit then 18p for each kit ordered. Kit F 33p then 23p for each kit ordered. Kit H 18p on first kit then 18p on each two kits ordered.

### BLANKET SWITCH

Double pole with neon let into side so luminous in dark, ideal for dark room light or for use with waterproof element—new plastic case **30p** each. 3 heat model **40p**.



### BLANKET SIMMERSTAT

Although looking like, and fitted as an ordinary blanket switch, this is in fact a device for switching on for varying time periods, thus giving a complete control from off to full heat. Although suitable for controlling the temperature of any other appliances using 230V AC, listed at **£1.40** each we offer these while our stocks last at only **65p** each.

### REED SWITCHES

Glass encased, switches operated by external magnet—gold welded contacts. We can now offer 3 types: **Miniature**, 1in long x approximately 1/4in diameter. Will make and break up to 1A up to 300 volts. Price **13p** each, **£1.20** dozen. **Standard**, 2in long x 1/4in diameter. This will break currents of up to 1A, voltages up to 260 volts. Price **10p** each, **90p** per dozen. **Flat**, Flat type, 2in long, over 1/4in thick, flattened out so that it can be fitted into a smaller space or a larger quantity may be packed into a square solenoid. Rating 1 amp 200 volts. Price **30p** each, **£3** per dozen. Small ceramic magnets to operate these reed switches **8p** each, **80p** dozen.

### HIGH CAPACITY ELECTROLYTICS

Brand new, not ex-shipment.  
100 mfd. 25V, **8p** each **60p** doz.  
200 mfd. 25V, **8p** each **75p** doz.  
250 mfd. 50V, **16p** each **£1.65** doz.  
400 mfd. 40V, **22p** each **£2.30** doz.  
500 mfd. 12V, **10p** each **£1.05** doz.  
500 mfd. 25V, **18p** each **£1.80** doz.  
500 mfd. 50V, **24p** each **£2.40** doz.  
500 mfd. 350V, **43p** each **£4.50** doz.  
1000 mfd. 12V, **15p** each **£1.50** doz.  
1000 mfd. 18V, **17p** each **£1.70** doz.  
1000 mfd. 64V, **37p** each **£4** doz.  
2000 mfd. 25V, **34p** each **£3.95** doz.  
5000 mfd. 12V, **24p** each **£2.40** doz.  
10,000 mfd. 6V, **29p** each **£3** doz.  
10,000 mfd. 15V, **43p** each **£4.50** doz.  
15,000 mfd. 10V, **53p** each **£5** doz.  
60,000 mfd. 8V, **£1.10** each **£11** doz.  
70,000 mfd. 13V, **£2** each **£20** doz.

**8 AMP 18V BATTERY CHARGER KIT**—comprising 230/40 mains transformer with 3 amp secondary and 3 amp rectifier **£1.15** + 23p post. **12 VOLT 1 AMP POWER PACK**, This comprises double-wound 230/240V mains transformer with full wave rectifier and 2000 n/f/d smoothing. Price **£1.40**.

**SOXOTONE STEREO CARTRIDGE**. Turnover type, ref. No. 15 T1. This fits most British pickups and is a really excellent reproducer. Limited quantity, **£1**.

**5 AMP 3-PIN SOCKETS**. These are always good stock, you never know when you will need some. Famous make, brown bakelite, standard size, 12 for **65p** plus 13p post.

**DITTO WITH 5 AMP**, 12 for **£1** plus 23p post. **13 AMP SOCKETS, FLUSH MOUNTING**. Bakelite, cream, less switch, 6 for **£1**.

**BAKELITE PANELS, MANY THICKNESSES**. We have just taken delivery of approximately 10 tons of bakelite in varying thicknesses from 2in. to a few thou. If you have a need for any of this then we would be glad to supply. The thickest is very heavy and could be used, for instance, as a bed for a motorised unit. Medium thickness is useful for front panels of instrument, etc., etc. Cut to your size price is **30p** per lb. plus **30p** cutting charge plus carriage.

**2 AMP 3-PIN SWITCHED SOCKETS** for surface mounting, brown bakelite. Made by famous maker. **13p** each or **£1.20** dozen.

**100 ASSORTED SILICON RECTIFIERS G.P. AND SWITCHING DIODES**. Small and very small sizes. A real snip for experimenters, **65p** per 100.

### 20 AMP ELECTRICAL PROGRAMMER

**Learn in your sleep:** Have Radio playing and kettle boiling as you awake—switch-on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an Electrical Programmer. Made by the famous Smith's Instrument Company. This is essentially a 230/240 volt mains operated Clock and a 20 amp switch, the switch-off time of which can be delayed up to 12 hours (continuously variable not stepped). Similarly the switch-on time can be delayed. This is a beautiful unit, size 5 1/2 x 3 1/2 in. deep. Metal encased, glass fronted with chrome surround. Offered at **£2.40** plus postage and insurance 23p.



### HI-FI SPEAKERS (15, 30, 40 & 100W)

**FULL FI 12 INCH LOUSPEAKER**. This is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi load and Rhythm Guitar and public address. Flux Density 11,000 gauss—Total Flux 44,000 Maxwells—Power Handling 15 watts R.M.S. Cone Moulded fibre—Freq. response 30-10,000 c.p.s.—Specify 3 or 15 ohms—Mains resonance 60 c.p.s.—Chassis Diam. 12in.—12 1/2in. overall length—Baffle hole 11 in. diam.—Mounting holes 4 holes—1 1/2 in. diam. on pitch circle 1 1/2 in. diam.—Overall height 5 1/2 in. A 66 speaker offer for only **£4**, plus 37p p. & p. 12in. 40 watt **£7** carr. 43p. 15in. 25 watt **£8** carr. 53p. 18in. 100 watt **£19.50** carr. **£1.50**.




### INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A one-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip (GP amplifiers). The 5th is a monolithic NPN matched pair. Regular price of parcel well over **£5**. Full circuit details of the ICs are included and in addition you will receive a list of many different ICs available at bargain prices **25p** upwards with circuits and technical data of each. Complete parcel only **£1** post paid. **DON'T MISS THIS TERRIFIC BARGAIN.**

### THIS MONTH'S SNIP

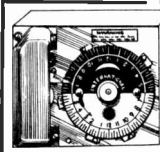
#### ELECTRIC TIME SWITCH

Made by Smith's these are AC mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. Completely adjustable time periods per 24 hours, 3 amp changeover contacts will switch circuit on or off during these periods. **£2.50**, post and ins. 23p. Additional time contacts 50p pair.


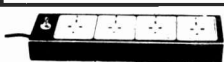
#### DISTRIBUTION PANELS


Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, **£2** less plug; **£2.25** with fitted 13 amp plug; **£2.40** with fitted 15 amp plug, plus 23p P. & I.



### BARGAIN OF THE YEAR
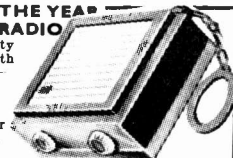
#### MICROSONIC KEYCHAIN RADIO

7 transistor Key chain Radio in very pretty case, size 2 1/2 x 2 1/2 x 1 1/2 in.—complete with soft leather zipped bag. Specification—Circuit: 7 transistor superheterodyne. Frequency range: 630 to 1,600 Kc/s. Sensitivity: 5 mV/m. Intermediate frequency: 465Kc/s or 455Kc/s. Power output: 40mW. Antenna: ferrite rod. Loudspeaker: Permanent magnet type. In transit from the East these sets suffered slight corrosion as the batteries were left in them but when this corrosion is cleared away they should work perfectly—offered without guarantee except that they are new. Price only **£1.25** plus 13p post and insurance, less batteries. 6 for **£7**, post free. Pair of rechargeable batteries and charger **85p**.



### 4 AMP VARIAC CONTROLLERS

With this you can vary the voltage applied to your circuit from zero to 270 volts without generating undue heat. One obvious application therefore is to dim lighting. Ex equipment but little used—as good as new offered at approx. half price—**£5** plus 70p post and ins.



### 19-PIECE SOCKET SET

Complete with wall or bench rack. An ideal gift for the motorist, **80p** + 23p. post and insurance. Most useful sizes from 1/4in to 1 1/2in.



### HONEYWELL PROGRAMMER

This is a drum type timing device, the drum being calibrated in equal divisions for switch setting purposes with trips which are infinitely adjustable for position. They are also arranged to allow 2 operations per switch per rotation. There are 15 changeover micro switches each of 10 amp type operated by the trips. The 15 circuits may be changed per revolution. Drive motor is mains operated 5 revs per min. Some of the many uses of this timer are Machinery control, Boiler firing, Dispensing and Vending machines, Display lighting animated and signs, Signalling, etc. Price from Makers probably over **£10** each. Special snip price **£5.75** plus 25p post and insurance. Don't miss this terrific bargain.



Where postage is not stated then orders over **£5** are post free. Below **£5** add 14p. Semiconductor add 5p post. Over **£1** post free. S.A.E. with enquiries please.

### MAINS CONNECTOR

A quick way to connect equipment to the mains safely and firmly; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection; cable inlets firmly hold one hair wire on up to four 7,029 cables. **65p** each.



### CONTROL DRILL SPEEDS

### DRILL CONTROLLER

Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1.50**, plus 13p post and insurance.



### BALANCED ARMATURE UNIT

500 ohm, operates speaker or microphone, so useful in intercom or similar circuits, **33p** each, **£3.50** doz.


### PROTECT VALUABLE DEVICES

**FROM THERMAL RUN-AWAY OR OVERHEATING:** Thyristors, rectifiers, transistors, etc., which use heat-sinks can easily be protected. Simply make the contact thermostat part of the heat-sink. Motors and equipment generally, can also be adequately protected by having thermostats in strategic spots on the casing. Our contact thermostat has a calibrated dial for setting between 90deg. to 190deg.F. or with the dial removed range setting is between 80 to 800deg.F. Price **50p**.



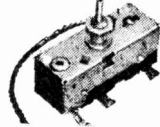
### THERMOSTAT WITH PROBE

This has a sensor attached to a 15A switch by a 14in length of flexible capillary tubing—control range is 20 F to 150°F so it is suitable to control soil heating and liquid heating especially when in buckets or portable vessels as the sensor can be raised out and lowered into the vessel. This thermostat could also be used to sound a bell or other alarm when critical temp. is reached in stack or heap subject to spontaneous combustion or if liquid is being heated by gas or other means not controllable by the switch. Made by the famous Teddington Co., we offer these at **65p** each. Postage and insurance 14p.


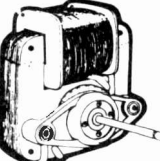
### MAINS MOTOR

Precision made—as used in record decks and tape recorders—ideal also for extractor fan, blower, heaters, etc. New and perfect. Snip at **60p**. Postage 15p for first one 5p for each one ordered.



### NEED A SPECIAL SWITCH? Double Leaf Contact

Very slight pressure closes both contacts, **6p** each, **60p** doz. Plastic push-rod suitable for operating, **5p** each, **45p** doz.



### MINIATURE WAFER SWITCHES

2 pole, 2 way—4 pole, 2 way—3 pole, 3 way—4 pole, 3 way—2 pole, 4 way—3 pole, 4 way—2 pole 3 way—1 pole, 12 way. All at **18p** each. **£1.50** dozen, your assortment.



### WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. **50p** post free.

### MICRO SWITCH

5 amp. changeover contacts, **9p** each, **£1** doz. 15 amp Model **10p** each or **£1.05** doz.




## ELECTRONICS (CROYDON) LTD

Dept. PE, 266 London Road, Croydon CR0 2TH  
Also 102/3 Tamworth Road, Croydon

# Laskys
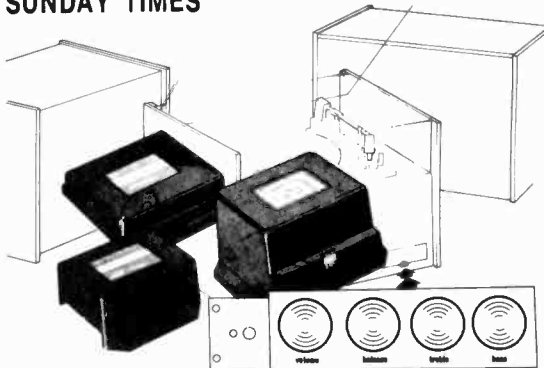
## MULLARD UNILEX AUDIO MODULES

Do-it-yourself stereo as featured in the SUNDAY TIMES



With nothing more than simple tools and the parts described below, you can build your own stereo system with excellent results guaranteed. The heart of the system comprises our Mullard Unilex modules and a control unit. All the modules and the control unit are supplied to you fully built and only require connecting together. Screw terminals and each module is housed in a tough plastic case, giving you complete freedom to use any of the recommended cabinets or your own design to suit your home.

- Control Unit:** Fitted with Bass, Treble, Volume and Balance controls. A metal fascia panel is supplied and all wires are ready fitted for connecting to the pre-amp. Size 5in. x 10in. x 1in. Plus 2in. long control shafts. **£3.25**
- Pre-amplifier Module Type EP-9001:** Input impedance: P/U 2.2M Tuner 1M Input Sens.: P/U 320mV, Tuner 140mV. Treble control range—14dB to 14dB at 16KHz. Bass control range—14dB to 14dB at 60Hz. Size: 4in. x 5in. x 1in. **£3.10**
- Amplifier Module Type EP-9000:** Output 4 watts per channel to 12 ohms to 15 ohms or 8 ohms with series resistor. Frequency resp. (to 3dB at 50mW): 50Hz to 16KHz. Harmonic distortion less than 2% at typical listening level. Size: 30in. x 4in. x 10in. **£5.80 per pair**
- Power Supply Module Type EP-9002:** For use with control unit, EP-9001 and 2 x EP-9000. For 220/250 volt AC mains. Size 50in. x 30in. x 3in. **£4.60**

### PACKAGE DEAL

Two EP-9000 Modules **£5.80** • EP-9002 Module **£4.60** • EP-9001 Module **£3.10** • Control Units **£3.25** • Instruction Book 25p. **TOTAL LIST PRICE £17.00**  
**PACKAGE PRICE £14.95** post 20p.

## FANTAVOX 105

### MODEL VHF 105


An item for the radio enthusiast bringing instant reception of the ground-to-air, air-to-ground waveband. For use with any standard AM or FM radio covering 535-1600 KHz 88-108 MHz respectively — with no electrical conversion or connection required. The model VHF-105, self powered by one 9V (PP3 type) battery, is merely placed close to the receiving set and then tuned over 110 to 135 MHz which covers the whole aircraft communications band. Volume and reception effectiveness is adjusted by moving both sets to the most favourable position and balancing the vol. controls of each accordingly. The Model VHF-105 has a smartly designed black plastic cabinet with brushed metal front panel and 18in. chrome telescopic antenna, size only 4 x 2 1/4 x 2 1/4 in. (inc. knobs) Complete with battery and full instructions.



**LASKY'S PRICE £3.60** Post 10p
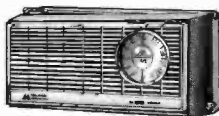
### MIDLAND 10-406 AM/AIRCRAFT RADIO

The first pocket size receiver of its type allowing you to tune-in to the entire air communications band covered by 108-137 MHz in addition to full AM medium wave Intermediate frequencies: AM 455 KHz; VHF 10.7 mc/s. Output power: 200mW 2 1/4 in. P.D. 8 ohm speaker. A built in ferrite rod aerial is provided for AM reception. The 10-406 is finished in blue with chrome trim, chrome telescopic antenna. Size 6 1/2 x 3 1/4 x 1 1/4 in. Complete with batteries, magnetic earphone, instructions and circuit data.



**LASKY'S PRICE £8.35** Post 13p

## ADC 40 PRECISION PICK-UP ARM

The ADC 40 Mk II is a complete low inertia arm with side thrust compensator and anti-drag lead out arrangement. Single-thrust ball bearings used at four points. Accurately machined walnut non-resonant arm. Adjustable counter-weight. Plug-in head shell accommodates nearly all cartridges. Easy installations. Built-in arm rest. Arm length 10 1/4 in. overall. Pivot to stylus tip 9 in. Rear overhang 1 1/4 in.

List Price **£19.41**

OUR PRICE

**£6.95**

Post 18p



## AUDIO DEVELOPMENT

### AD-309K

PRECISION PICK-UP ARM COMPLETE WITH AD-76K MAGNETIC CARTRIDGE

The new AUDIO DEVELOPMENT precision counter-balanced pick-up arm — ready fitted with the outstanding AD-76K magnetic

cartridge is constructed of brass throughout, heavily chrome-plated; uses needle and miniature ballrace bearings; both coarse and fine balance adjustment is provided. The fixed head has standard jin, mounting centres and is finished in black enamel with chrome lifting spur. Completely wired, with all fixing nuts and washers. Arm rest also supplied. Tech. details: Overall length 285mm; needle to pivot length 223mm; offset angle 24°; overhang 10mm. Requires single 7/16in. dia. mounting hole.

**LASKY'S PRICE £8.50** Post Free

### AUDIO DEVELOPMENT AD-76K

Stereo Magnetic Cartridge. Frequency response 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms — 0.5 gm. Replacement stylus type JS.P1 £2.05 post free. **£4.50** Post Free

### AUDIO DEVELOPMENT AD-96K

Stereo Magnetic Cartridge. Frequency response 20-20,000Hz. Output: 5mV. Stylus: Diamond LP. Tracking force: 2 gms. Replacement stylus type Y.960S £2.57 post free. **£5.93** Post Free

## Lasky's COMPACT CASSETTES

C60 • C90 • C120

Exclusively made for us in USA Great Savings.

	Each	Post	Five for	Post	Ten for	Post
C60—	37p	5p	£1.65	20p	£5.95	25p
C90—	57p	5p	£2.75	20p	£9.90	25p
C120—	87p	5p	£3.75	20p	£12.10	25p

U.S.A. Cassette head cleaner, 53p Post 5p



## INTERNATIONAL

MAGNETIC RECORDING TAPE FROM THE U.S.A. AT LASKY'S RECORD LOW PRICES

3in	Message tape, 150ft.	13p	5 1/2in	Long play, 1200ft. Mylar	75p
3in	Message tape, 225ft.	19p	5 1/2in	Triple play, 2400ft.	£1.75
3in	Message tape, 300ft.	38p	7in	Standard play, 1200ft.	63p
3 1/4in	Triple play, 600ft. Mylar	50p		Acetate	
5in	Double play, 1200ft.	75p	7in	Standard play, 1200ft.	63p
5in	Long play, 900ft. Acetate	50p		Mylar	
5in	Standard play 600ft.	40p	7in	Long play, 1800ft. Mylar	98p
5 1/2in	Double play, 1800ft. Mylar	£1.13	7in	Double play, 2400ft. Mylar	£1.25
5 1/2in	Long play 1200ft. Acetate	75p	7in	Long play 1800ft. Acetate	75p
5 1/2in	Standard play 900ft. PVC.	63p	7in	Triple play 3600ft. Mylar	£2.50

P. & P. 5p extra per reel, 4 reels and over Post Free. Special quotes for quantities.

# SONY FM-8030L

**BARGAIN SCOOP**

## HIGH PERFORMANCE 11 TRANSISTOR THREE WAVEBAND PORTABLE BATTERY MAINS RADIO

This is a really top performance, top quality solid state receiver packed with SONY know-how and backed by the outstanding reliability for which SONY are renowned. Now this outstanding set is available from Laskys at over 27% below the manufacturers list price making it without a doubt the NUMBER ONE SCOOP of 1971! Just look at these outstanding features: Covers MW, LW and FM (VHF). 11 transistor circuit for high sensitivity and stability. Powerful output to 5" P.M. Dynamic speaker with rich clear tone quality. AFC for drift free VHF reception. Push button wavechange selectors and tone control.

Choice of three power sources—9V battery, household mains or car battery with suitable adaptors. Dial light for use in the dark. External jacks for earphone, tape recording, external power input and car aerial. Ultra modern styling and superb finish with padded leatherette covered cabinet for superior sound damping with chrome trim, strong carrying handle.

The SONY FM 8030L will enliven your leisure hours anywhere, anytime with exciting sound, news, sport, music, etc. Technical specification: Freq. range, FM 87-108MHz, LW150-285kHz, MW530-1, 605kHz. Circuit: 11 transistors, 7 diodes and 2 thermistors. Aerial System: Directional telescopic for FM, internal ferrite bar for LW/MW. Power Output: 1.85W max. Speaker PM Dynamic—4Ωimp. Power Source: 9v power pack battery (Ever-Ready PP9 or equiv.), AC mains with adaptor, Car battery with adaptor. Size: 9½(W) x 8½(H) x 3½(D). Complete with earphone and battery and full instruction manual.

MANUFACTURERS LIST PRICE £29.75

LASKY'S SPECIAL OFFER PRICE **£21.50**


Optional Extras. SONY AC-90e AC adaptor £4.00 DCC-126 stabilised car battery £6.00. Both post FREE if purchased with radio.

Post 35p



# EXCLUSIVE McDONALD

## DIGITAL CLOCK SCOOP!

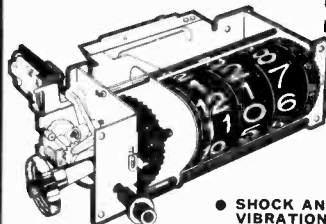

SPECIAL QUOTATIONS FOR QUANTITIES

- SHOCK AND VIBRATION PROOF
- BUILT IN ALARM BUZZER

- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION
- 12 HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR

This unique DIGITAL CLOCK is now available EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing that you choose. All settings are achieved by two dual-concentric controls at the front including: ON-OFF-AUTO and AUTO ALARM, "sleep" switch, 10 minute division "click" set alarm (up to 12 hour delay), time adjustment. Ultra simple mechanism and high quality manufacture guarantee reliable operation and long life.

The sleep switch will automatically turn off any appliance—radio, TV, light, etc., at any pre-set time up to 60 min. and in conjunction with the AUTO setting will switch on the appliance again next morning.

The clock measures 4½W x 1½H x 3½D (overall from front of drum to back of switch). SPEC: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions. HUNDREDS OF APPLICATIONS.


COMPLETE WITH KNOBS.

LASKY'S PRICE **£6.95** Post 18p
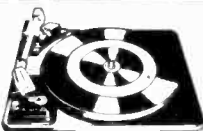
## GARRARD SP25 Mk III

The SP 25 series record deck has proved to be one of the most popular of its type in the world. Styled in black and silver, this moderately priced three-speed unit complies with the Din 45-500 Hi-Fi performance standard. The tubular low resonance aluminium pick-up arm is counter-balanced by a resiliently mounted weight. Stylus force is adjusted by an optical-type knurled knob, finely calibrated from 0.5 grm. in steps of 1 grm. Bias compensation is set with a finger-tip adjustment, the scale being calibrated to correspond with the stylus force. The viscous damped cue control facilitates raising and lowering the pick-up arm onto the track required without damage to either the record or stylus. The 10½in. aluminium turntable is driven by the well-proven Garrard 4-pole high and low voltage induction motor. Actual size including max. rear and side overhang of pick-up arm 15¼in. wide x 12½in. front to rear x 12½in. above and 2½in. below edge of unit plate.

LASKY'S PRICE **£12.50** WITH 9TA CARTRIDGE Post 35p



## PROFESSIONAL SERIES FOUR-SPEED SINGLE PLAY UNIT

### MP60

High-precision low-mass fully counterbalanced pick-up arm, heavy balanced turntable, simple to operate controls, viscous cueing device, slide-in cartridge carrier, four pole motor.



LASKY'S PRICE **£12.50** Post 35p

complete with plinth and cover **£15.75**

Post 40p

## 610 AUTOMATIC TURNTABLE

Same specifications as the MP60 but with synchronous four pole motor and full automatic change facilities.

LASKY'S PRICE **£15.45** Post 35p

WITH PLINTH AND COVER **£18.75** Post 40p

## 510 AUTOMATIC TURNTABLE

Counterbalanced pick-up arm, pressed steel turntable, bias compensator, viscous cueing and synchronous four pole motor.

LASKY'S PRICE **£13.45** Post 35p

WITH PLINTH AND COVER **£16.95** Post 40p

## 310 AUTOMATIC TURNTABLE

Low-mass square section pick-up arm, cue and pause lever, visual stylus pressure indicator, slide-in cartridge carrier, four pole motor.

LASKY'S PRICE **£9.95** Post 35p

WITH PLINTH AND COVER **£13.45** Post 40p

## NOW AVAILABLE LASKY'S EXCLUSIVE

LASKY-McDONALD plinth and cover available separately at

**£4.75** Post 25p

# Lasky's Radio Ltd

Branches

207 EDGWARE ROAD, LONDON, W.2

Tel.: 01-723 3271

33 TOTTENHAM CT. RD., LONDON, W.1

Tel.: 01-636 2605

Open all day, 9 a.m.—6 p.m. Monday to Saturday

152/3 FLEET STREET, LONDON, E.C.4 Tel.: 01-353 2833


Open all day Thursday, early closing 1 p.m. Saturday

High Fidelity Audio Centre

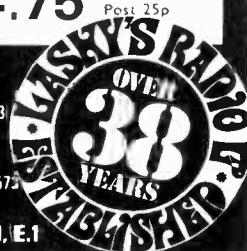42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel.: 01-580 2575

Open all day, 9 a.m.—6 p.m. Monday to Saturday


ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL STREET, TOWER HAMLETS, LONDON, E.1






# LIND-AIR AUDIO

## C.1001 MULTI-TESTER

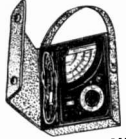

Overload protection  
20,000 Ω per volt;  
a.c. volts 10, 50,  
250, 1,000V; d.c.  
volts 5-25, 125; 500,  
2,500V; d.c. current  
0-50mA, 0-250mA;  
Resistance 0-60kΩ  
0-6MΩ; decibels  
-20 to +22dB. Size  
of meter 4 1/2 in x 3 1/2 in x 1 in. Complete with case. **£4.25, P. & P. 17 1/2p.**


## C.1050 MULTI-TESTER

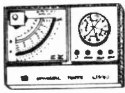

Ranges:  
D.C. Voltage: 0.3,  
15, 150, 600, 1,200V  
(10,000 Ω per V).  
A.C. Voltage: 0.6,  
30, 300, 1,200V  
(5,000 Ω per Volt).


D.C. Current: 0-120μA 0-300mA.  
Resistance: 0-50kΩ, 0-5 MΩ (R x R)  
(R x 1K). Decibels: -20 to +17dB.  
**£5.97 1/2, P. & P. 17 1/2p.**

## C.1052 MULTI-TESTER

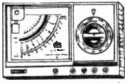

Ranges:  
A.C. Voltage: 6, 30,  
120, 300, 1,200  
(15,000 Ω/V).  
D.C. Voltage: 0.6-3,  
15, 60, 300, 1,200  
(30,000 Ω/V). D.C. Current: 0, 0.03, 3, 30,  
300mA. Resistance: 0, 6Ω, 60Ω, 600Ω,  
6MΩ. Decibels: -20 to +63dB. **£7.25,  
P. & P. 17 1/2p.**

## E.M.I. LOUSPEAKERS

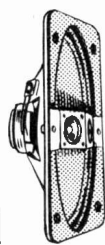

**MODEL 450.** 13 1/2 in x 8 in  
elliptical with twin tweeters.  
8 Ω impedance. 10 watts.  
Brand new, guaranteed.

Lind-Air Price  
**£3.97 1/2**  
P. & P. 22 1/2p each.

**MODEL 150.** 13 1/2 in x 8 in  
elliptical, 3 and 15 Ω  
impedance. 10 watts.

Lind-Air Price  
**£2.97 1/2**  
P. & P. 22 1/2p each.

## SANYO COLORANO AM/FM PORTABLE RADIO



10 transistor circuit,  
covers long, medium and  
VHF/FM wavebands,  
and will receive your  
local VHF stations.  
Internal aerial plus tele-  
scopic aerial for peak  
reception. Size 7 in x  
4 1/2 in x 2 in. New in  
makers' cartons with  
1-year guarantee. Complete with earphone  
for private listening. List Price **£13.75.**  
(Batteries 16p extra).  
Price **£9.97 1/2, P. & P. 27 1/2p.**

## GARRARD HI-FI TURNTABLES




2025 T/C with stereo cartridge ..... **£8.97 1/2**  
3000 with Sonotone 9TAHCD stereo  
cartridge ..... **£10.97 1/2**  
8P25 Mk. III ..... **£12.97 1/2**  
8L65B ..... **£15.97 1/2**  
Base and cover for above ..... **£2.97 1/2**  
AP76 ..... **£19.50**  
8L72B ..... **£24.97 1/2**  
8L73B ..... **£23.35**  
8L95B ..... **£30.45**  
Base and cover for above ..... **£2.97 1/2**  
401 ..... **£28.50**  
P. & P. Decks, 62 1/2p; Base and Cover, 60p;  
Deck/Base/Cover, 87 1/2p.

### THIS MONTH'S SPECIAL OFFERS!

8P25 Mk. III with base ..... **£12.97 1/2**  
P. & P. 27 1/2p.  
8P25 Mk. III with Sonotone ..... **£15.97 1/2**  
9TAHCD cartridge and base ..... **£15.77 1/2**  
P. & P. 75p.

## S-DeC BREADBOARD

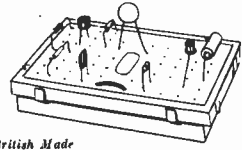

British Made  
Solderless breadboard panels, for fast  
reliable component connections.  
Single DeCs. One 8-DeC with Control  
Panel, Jig and Accessories for solderless  
connections to controls, etc., with booklet  
"Projects on 8-DeC" giving construction  
details for a variety of circuits. **£1,  
P. & P. 17 1/2p.**  
4-DeC KIT. Four 8-DeCs with two Control  
Panels, Jigs and Accessories and the book-  
let "Projects on 8-DeC" all contained in a  
strong attractive plastic case. Ideal for  
the professional user. **£3.98, P. & P. 17 1/2p.**  
T-DeC KIT **£2.50, P. & P. 17 1/2p.**  
8-DeC STOR **£2.50, P. & P. 17 1/2p.**

## WELLER "EXPERT" SOLDERING GUN



Comfortable and easy to use  
240V A.C. Instant dual  
heat 100/140 watt with  
two position trigger  
control. **£3.37 1/2, P. & P. 27 1/2p.**

**18/19, 25 & 53 TOTTENHAM  
COURT ROAD, LONDON W.1.**  
Tel: 01-580 2225/7679  
Open 9-6 Mon-Sat (Thurs until 7)

All Mail Orders and inquiries to Dept. PE4,  
Kirkman House, 54a Tottenham Court Road,  
London, W.1. Tel: 01-637 1601.

**94-96, UPPER PARLIAMENT  
STREET, NOTTINGHAM**  
Tel: Nottingham 40403 (STD 0602)  
Open 9-6 Mon-Sat (Weds until 7.30)

## I MILLION SILICON PLANAR TRANSISTORS NPN-PNP PLASTIC AND METAL CAN TYPES

Clearance of manufacturers' seconds, selected in types and guaranteed  
no open or short circuit units. Ideal cheap transistors for radio  
enthusiasts, manufacturers, schools and colleges.

### TYPE STN18

Silicon Planar Transistors npn TO-18 Metal Can. Types similar to:  
2N706, 2N2220, BSY27-95A, BSX44-76-77. Price: 500 **£9, 1,000 **£15****

### TYPE STP18

Silicon Planar Transistors pnp TO-18 Metal Can. Types similar to:  
BCY70-72, 2N2906-7, 2N2411 and BC186-7. Also used as comple-  
mentary to the above npn type device type STN18. Price: 500 **£9, 1,000 **£15****

### TYPE STNL

Silicon Plastic Epitaxial Planar Transistors TO-92 case. I.C. 200mA,  
300mW medium to high gain, available in npn or pnp and types similar to:  
NPN 2N2926 — 2N2711 — 2N3391 — 2N3707 — 2N3711 — BC167-8-9.  
Price: 500 **£7-50; 1,000 **£13****

### TYPE STPL

As above but in pnp and similar to types 2N5354-56, 2N4058-2N4061  
and 2N3702-3. Also used as complementary to the above npn devices  
type STNL. Price: 500 **£7-50; 1,000 **£13****

### TYPE STNK

Silicon Planar Plastic Transistor npn with TO-18 pin circular lead  
configuration, I.C. 200mA, 300mW and similar to BC107-8-9, BC170,  
BC173, BC182-184, BC237-8-9 and BC337-8. Price: 500 **£9-50; 1,000 **£16****

When ordering, please state type required, i.e., STNK or STN18, etc.  
All prices in pounds and new pence.  
All goods Ex-stock sent by return. Cash with order please to:

**DIOTRAN SALES**  
P.O. Box 5, WARE, Herts.  
S.A.E. For full list of surplus semiconductors

## EX RENTAL TV's

17"  
SLIMLINE  
405 ONLY  
**£19.95**

2 YEARS' GUARANTEE  
FREE ILLUSTRATED  
LIST OF TELEVISIONS  
17"-19"-21"-23"

19"  
SLIMLINE  
405/625  
BBC 2  
**£29.95**



WIDE RANGE OF MODELS  
DEMONSTRATIONS DAILY



CARR. INS.  
**£1-50**

## STEREO RECORD PLAYER CABINET

**£5.97 1/2**



Cloth covered. Two tone Blue/Black.  
Size 14 1/2" x 24" x 8 1/2". P. & P. 53p.

## TV TUBES REBUILT GUARANTEED 2 YEARS



14"-£3.95, 17"-£5.95, 21"  
23"-£6.45.  
Exchanged Bowls. Carr. 53p.

PRESS BUTTON SWITCHING UNITS. 4 Banks 17p. 6 Banks 27p.  
P. & P. 5p.

TRANSISTORS 15p EACH. OC44, OC45, OC71, OC81, OC81D, AF114,  
AF117, AC128.

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Phone 01-478 6001-2-3 Stamp for Free List



# STEPHENS

**ELECTRONICS**  
P.O. BOX 26  
AYLESBURY  
BUCKS.

**SEND S.A.E. FOR LISTS**  
**GUARANTEE**  
Satisfaction or money  
refunded

The Diamond Tip is .007in radius, thus making it compatible to play stereo records on mono equipment without damage to the record; and of course full stereo.  
**BRITISH MADE**  
**EXPORT ENQUIRIES WELCOME**

## CARTRIDGES

ACOS		Inc. P.T. each	GOLDRING		Inc. P.T. each
GP79	-1	85p	(800)		45-25
GP91-18c	-1	£1-05	(800E)		£15
2-11		89p	G800 Super E		£19-50
12-49		77p			
50-500		87p			
GP91-28c		As above			
GP91-38c		As above			
Suitable to replace TC8, etc.					
GP92-1		£1-32			
GP93-1		£1-24			
GP94-1		£1-24			
GP94-5		£1-80			
GP95		£1-24			
GP96		£1-57			
Acos 104 1-10		£2-09			
11-25		£1-99			
26		£1-91			
51-499		£1-77			
B.S.R.					
X3M	8/S	£1-39			
X3H	8/S	£1-39			
X3M	8/S	£1-39			
X3H	8/S	£1-39			

## DE BANKS MAGNETIC RECORDING TAPES

POLYESTER			POLYESTER		
Length	Spool Size in.	Price	Length	Spool Size in.	Price
Standard Play			900ft	3	70p
600ft	5	50p	1200ft	3	85p
850ft	5	63p	1800ft	7	£1
1200ft	7	70p	Double Play		
Long Play			1200ft	5	87p
210ft	3	87p	1800ft	7	£1-10
450ft	4	87p	2400ft	7	£1-30

## EMPTY TAPE REELS

3in	7p
4in	9p
5in	11p
5 1/2in	18p
7in	18p

## CASSETTES

Boxed in Plastic Library Packs  
C60 53p  
C90 65p  
C120 87p  
P. & P. 7p on all orders.

## STYLII

ACOS	Sapphire	Diamond	ELAC	KST9	Sapphire	Diamond
GP59	13p	37p	(PE1B)		33p	47p
GP65	13p	37p	ER5MB		33p	47p
GP67	13p	37p	ER5MX		13p	37p
GP73-1	33p	47p	ER58B		33p	47p
GP73-2	33p	47p	ER60 Stereo		33p	47p
GP78	13p	37p				
(P81-1)	13p	37p				
GP91-1	33p	47p				
GP91-2	33p	47p				
GP91-3	33p	47p				
GP91-18c	33p	47p				
GP91-38c	33p	47p				
GP92-1	33p	47p				
GP94-1	33p	47p				
GP95-1	33p	47p				
GP96	33p	47p				
HCP37	13p	37p				
104	13p	37p				
B.S.R.						
BSR CI (8T3)	33p	47p				
BSR TC8H	13p	37p				
BSR TC8M	13p	37p				
BSR ST8	33p	47p				
BSR ST9	33p	47p				
BSR ST10	33p	47p				
BSR X1M	33p	47p				
BSR X1H	33p	47p				
BSR X3M	33p	47p				
BSR X3H	33p	47p				
BSR X5H	33p	47p				
BSR X4H	33p	47p				
COLLARO						
Collaro Studio						
"O"	13p	37p				
Collaro-Ronett						
TX88	13p	37p				
Collet SK1	13p	37p				
Dual CDS2/CD83 (DN2)	33p	47p				
Dual (CDS/320 (DN3)	33p	47p				
ELAC KST9 (PE10)	33p	47p				
DECCA						
Derain diamond only						£1-39
GARRARD						
EV38 Stereo	13p	37p				
GC2	13p	37p				
GC8	13p	37p				
GCE12	13p	37p				
GC810-1	13p	37p				
GC810-2	13p	37p				
81-2-3	33p	47p				
TS1	13p	37p				
TS2	33p	47p				
TS3	33p	47p				
GOLDRING						
CM50	13p	37p				
CM60	13p	37p				
MX1	13p	37p				
MX2	13p	37p				
Stereo C860	13p	37p				
PERPETUUM EBNER						
PE188	33p	47p				
PHILIPS						
AG3016	13p	37p				
AG3063	13p	37p				
AG3306	33p	47p				
AG3310/3306	33p	47p				
AG3406	13p	37p				
RONETTE BINOFLUID						
BF40	33p	47p				
DN294	13p	37p				
SONETONE						
3T	33p	47p				
3T	33p	47p				
8T4A	33p	47p				
9TA	33p	47p				
9TA/HC	33p	47p				
1T	13p	37p				
20T	13p	37p				

## SEMICONDUCTORS · BRAND NEW · MANUFACTURERS' MARKINGS · NO REMARKED DEVICES

2N388A	62p	2N3810	35p	2N3708	17p	2N2927	£2-02	AC128	20p	BC115	32p	BD132	97p	BFY41	50p	GET113	20p	NKT242	20p	OC20	75p
2N404	25p	2N2614	30p	2N3709	17p	2N3305	37p	AC134	22p	BC116	62p	BDY10	£1-37	BFY43	62p	GET114	20p	NKT243	62p	OC22	50p
2N696	20p	2N2646	57p	2N3710	20p	2N3306	25p	AC136	25p	BCY36	37p	BDY11	£1-87	BFY52	22p	GET115	20p	NKT244	17p	OC23	45p
2N697	20p	2N2696	32p	2N3711	20p	2N3307	37p	AC187	62p	BC117	33p	BDY17	£1-87	BFY51	22p	GET118	20p	NKT245	20p	OC24	57p
2N698	20p	2N2711	30p	2N3713	£1-50	2N3308	37p	AC188	27p	BC118	33p	BDY18	£2-47	BFY52	22p	GET120	52p	NKT261	20p	OC25	50p
2N699	62p	2N2712	30p	2N3714	£1-75	2N3309	62p	AC187	27p	BC121	20p	BDY19	£3-12	BFY53	22p	GET123	12p	NKT264	30p	OC26	32p
2N705	18p	2N2713	27p	2N3819	35p	2N3310	42p	ACY18	25p	BC122	20p	BDY20	£1-52	BFY56	67p	GET880	30p	NKT271	20p	OC28	62p
2N706A	12p	2N2714	30p	2N3823	£1-15	2N3314	27p	ACY19	25p	BC125	55p	BDY30	£1-80	BFY75	30p	GET887	20p	NKT272	20p	OC29	75p
2N708	15p	2N2665	62p	2N3828	35p	2N3315	27p	ACY20	25p	BC134	57p	BDY61	£1-80	BFY77	57p	GET890	22p	NKT275	50p	OC33	45p
2N709	68p	2N2904	35p	2N3854	27p	2N3326	32p	ACY21	25p	BC140	37p	BDY62	£1-37	BFY90	67p	GET896	22p	NKT281	20p	OC41	22p
2N718	25p	2N2904A	40p	2N3854	27p	2N3365	47p	ACY22	20p	BC147	17p	BF115	25p	BFW58	27p	GET897	22p	NKT401	87p	OC42	25p
2N718A	30p	2N2905	40p	2N3855	27p	2N3366	32p	ACY28	20p	BC148	15p	BF117	47p	BFW59	25p	GET898	22p	NKT402	90p	OC44	20p
2N726	30p	2N2906	40p	2N3855A	30p	2N3367	37p	ACY40	20p	BC149	17p	BF163	35p	BFW60	25p	MAT100	30p	NKT403	75p	OC46	15p
2N727	30p	2N2906	30p	2N3856	30p	2N3477	37p	ACY41	25p	BC152	17p	BF167	35p	BFX25	£1-35	MAT101	30p	NKT404	62p	OC48	15p
2N914	17p	2N2906A	32p	2N3856A	35p	2N3505	27p	AD144	40p	BC157	20p	BF178	35p	BFX28	35p	MAT120	30p	NKT405	62p	OC70	15p
2N916	17p	2N2907	40p	2N3858	25p	2N3520	£1-87	AD140	40p	BC158	17p	BF177	32p	BFY10	£1-45	MAT121	30p	NKT406	62p	OC71	12p
2N918	30p	2N2923	17p	2N3858A	30p	2N3512	32p	AD149	57p	BC159	20p	BF178	35p	BFX29	17p	MJ400	£1-07	NKT451	62p	OC72	12p
2N929	22p	2N2924	17p	2N3859	27p	2N3513	32p	AD150	57p	BC160	62p	BF179	72p	BFX29	17p	MJ421	£1-12	NKT452	62p	OC74	32p
2N930	27p	2N2925	17p	2N3860	30p	2N3514	27p	AD162	37p	BC167	15p	BF180	35p	BFX31	35p	MJ430	£1-02	NKT453	47p	OC75	22p
2N987	52p	2N2926	17p	2N3861	30p	2N3515	27p	AD166	42p	BC168	17p	BF181	32p	BFX32	35p	MJ440	85p	NKT603	32p	OC76	22p
2N1131	27p	2N2927	17p	2N3862	£1-50	2N3516	27p	AD174	42p	BC169	15p	BF184	25p	BFX33	35p	MJ440	85p	NKT613F	32p	OC77	27p
2N1132	32p	Yellow	12p	2N3877	40p	2N3517	27p	AD183	£1-87	BC195	15p	BF195	42p	BFX38	32p	MJ480	85p	NKT613F	32p	OC78	27p
2N1302	17p	Orange	12p	2N3877A	40p	3N83	£1-87	AD183	£1-87	BC196	15p	BF195	42p	BFX38	32p	MJ481	£1-25	NKT613F	32p	OC81	20p
2N1303	17p	2N3811	30p	2N3900	37p	3N128	92p	AD186	25p	BC170	17p	BF195	27p	BFX38	32p	MJ490	£1	NKT674F			

# R+TV

**RADIO & TV COMPONENTS (Acton) Ltd.**

Post to: 21d High St., Acton, London W3 6NG  
 Personal shoppers to 323 Edgware Road, London, W.2  
**ALL ORDERS BY POST TO OUR ACTON BRANCH**  
 Terms C.W.O. All enquiries S.A.E.

## Complete Stereo System £43

**WITH VISCOUNT F.E.T. AMPLIFIER**  
 FIELD EFFECT TRANSISTORS




This superb stereo system is a real price breakthrough. It comprises the VISCOUNT F.E.T. Mk. I amplifier on which full details are given below, the famous Garrard SP25 (including teak veneer base and transparent cover) with diamond cartridge or 2025 TC and the very successful DUO type 2 speakers.

Measuring 17½ in × 10½ in × 6½ in, the Duo type 2 speakers are teak finished with matching Vynair grills. They incorporate a 3 ohm 13 in × 8 in drive unit with parasitic tweeter. Maximum power handling 10 watts, price:

**£13-50** per pair plus £1-50 P. & P.

Complete stereo system **£43** plus P. & P. **£2-50**

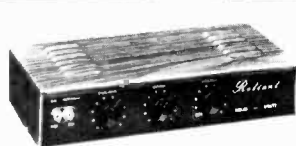With Mk. II Amplifier and Magnetic Cartridge **£48** plus P. & P. **£2-50**



### THE RELIANT Mk. II SOLID STATE GENERAL PURPOSE AMPLIFIER

**£7-25** Plus P. & P. 50p  
 Simulated teak case

**SPECIFICATION:** Output: 10 watts into a 3 ohms speaker. Inputs: (1) for mike (10mV). Input (2) for gram, radio (250mV). Transistors: 4 silicon and three germanium. Mains input: 220/250 volts. Size: 10½ × 4½ × 2½ in.



### ELEGANT SEVEN Mk. III (350mW Output)

7-transistor fully tunable M.W.-L.W. Superhet portable. Set of parts. Complete with all components, including ready etched and drilled printed circuit board—back printed for foolproof construction. **MAINS POWER PACK KIT: (47p) extra.**

**£5-25** Plus P. & P. 50p. Circuit 13p + Free with parts.

### THE DORSET (600mW Output)


7-transistor fully tunable M.W.-L.W. Superhet portable with baby alarm facility. Set of parts. The latest modulated and pre-alignment techniques makes this simple to build. Sizes: 12 × 8 × 3 in.

**MAINS POWER PACK KIT: 47p extra.**

**£5-25** Plus P. & P. 50p. Circuit 13p. Free with parts.


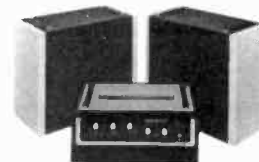
### SOUND 50 50 WATT AMPLIFIER AND SPEAKER SYSTEM



**Output Power:** 45 watts R.M.S. (Sine wave drive). Frequency response:—3dB points 30Hz at 18kHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB.

**Speaker Impedance:** 3, 8 or 15 ohms. **Base Control Range:** ± 13dB at 60Hz. **Treble Control Range:** ± 12dB at 10 kHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the **SPEAKERS!** Size 20" × 20" × 10" incorporating Baker 12" heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two-tone colour scheme—Black and grey.

amplifier to be used at half power.

### The Viscount F.E.T. Mk. I £14-25

Plus 50p P.&P.

High fidelity transistor stereo amplifier employing field effect transistors. With this feature and accompanying guaranteed specifications below, the Viscount F.E.T. vastly surpasses amplifiers costing far more.

Output per channel—10W rms. into 3 ohms. Frequency bandwidth 20Hz to 20kHz ± 1dB @ 1V. Total distortion @ 1kHz @ 9W 0-5%. Input sensitivities—CER. P.U. 100mV into 3 MΩ; Tuner 100mV into 100kΩ; Tape 100mV into 100kΩ. Overload Factor—Better than 26dB. Signal to noise ratio—70dB on all inputs (with vol. max).

**Mk. II (MAG. P.U.) £15-75** Post & packing 50p extra.

Specification same as Mk. I, but with the following inputs: Mag. P.U. CER. P.U. Tuner.

Controls—6 position selector switch (3 pos. stereo and 3 pos. mono); separate vol. controls for left and right channels. Bass ± 14dB @ 60Hz; Treble (with D.P.S. on/off) ± 12dB @ 10kHz. Tape recording output sockets on each channel. Size 12½ in × 6 in × 2½ in in simulated teak case. Built and tested.

Spec. on Mag. P.U. 3mV @ 1kHz input impedance 47kΩ. Fully equalised to within ± 1dB RIAA. Signal to noise ratio—65dB (vol. max.).

### LIQUIDATED STOCK

## DANSETTE

TOURISTE MK3

CAR RADIO

ALL TRANSISTOR


Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1 MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7" × 2" × 4½" deep.

Originally sold completely built for (£15-23)  
 Circuit diagram 13p, free with parts  
**£1-25** extra plus P. & P. 25p

### SET OF PARTS

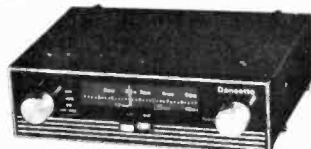**£6-30**

Speaker postage free when ordered with parts



### COMPLETE SYSTEM £50

Plus £4 P. & P.

Sound 50 amp and 2 speakers

or available separately  
 Amplifier: £28-50 plus £1 P. & P.  
 Speaker: £12-50 each plus £1-50 P. & P.

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES  
Advertisement Manager D. W. B. TILLEARD

## ONE GOOD REASON

**T**HERE are all sorts of reasons why people build electronic equipment for themselves. A very good one is, simply, that unless they do, they go without!

No wild exaggeration, this. While the semiconductor industry can turn out vast quantities of thought-provoking circuit devices—originally developed for professional applications, it is true—is it not strange that equipment manufacturers have not seized upon these to embody in a host of imaginative functional products for the domestic consumer?

Oh yes, for sure the radio, television, and audio equipment business is well saturated, as the shop windows and showrooms in every high street testify. But the very proliferation of traditional entertainment products from both home and overseas factories induces a lop-sided view of electronics and what it can do for everyman and his wife. For instance, light and heat sensitive semiconductors, and power switching thyristors and triacs, are all crying out for more general use; to say nothing of logic systems based on miniature integrated circuits which offer possibilities for programming routine switching operations within the home.

There has been plenty of pie-in-the-sky talk of the electronics-run home of the future. When will the big breakthrough occur?

While prodding the commercial world to venture into these unusual and as yet scarcely explored domestic regions, we do see that this is not so simple nor (perhaps) as profitable as satisfying mass market needs for standardised conventional products like radio and audio equipment. Many installed automatic systems, such as intruder detectors, and environment sensing and controlling equipments, have to be tailored to suit specific needs and situations. And coping with a number of possible combinations from a wide range of units in order to build up an ideal installation for one customer would give the retailer some headaches, no doubt.

This is, of course, where we came in: if you do require something rather special in this particular line of electronics, the chances are you will have to build it yourself. This is just one further demonstration of the paradoxical situation we now have, and which arises directly from the highly productive semiconductor industry: the general availability of mass produced, efficient and versatile devices is helping in the preservation of individual craftsmanship. F.E.B.

### PRICE INCREASE

As from next month, the price of PRACTICAL ELECTRONICS will be 20p (4s). We regret the necessity for this increase, which is due to rising production costs.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

P.E. AURORA	286
TOUCH SWITCH	293
BOAT SPEED INDICATOR	310
DOOR YODELLER	322

### SPECIAL SERIES

MAKING THE MOST OF LOGIC IC's—10	326
----------------------------------	-----

### GENERAL FEATURES

PROTECTION CIRCUITS	296
DESIGN OF OHMMETERS	301
INGENUITY UNLIMITED	316

### NEWS AND COMMENT


EDITORIAL	285
NEWS BRIEFS	308, 325
SPACEWATCH	309
MARKET PLACE	298, 321
OVER THE CHANNEL	337
BOOK REVIEWS	338

*Our May issue will be published on Friday, April 16*

Create living colour that "moves" with the mood of your music.

**P.E. AURORA** is a controlled lighting system that can be as simple or as complex as you like to make it.

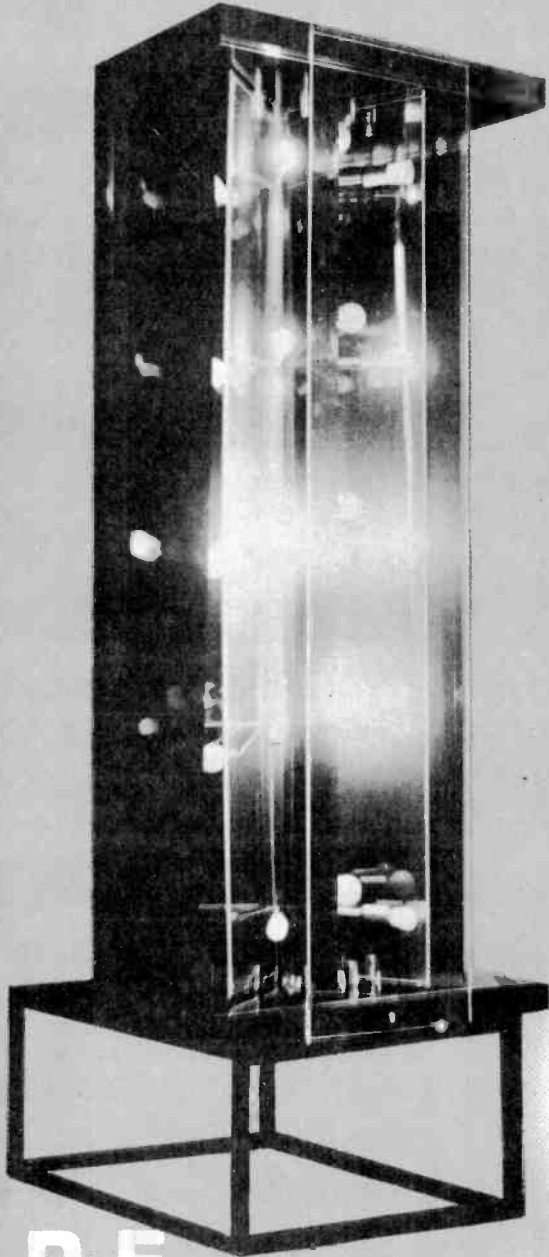The selected audio frequency ranges can be "coloured" and the lighting arranged in whatever domestic decor you choose.



**S**OUND controlled colour light displays can be arranged to provide several kinds of visual effects some of which have been exploited for television and discotheques. The growing interest in this idea among amateurs and professionals was obvious at the recent Audio and Music Fair, when PRACTICAL ELECTRONICS presented to the public a versatile system called "P.E. Aurora".

This is a do-it-yourself design capable of exploitation to provide domestic mood lighting appropriate to any kind of music (serious, classical, jazz, or pop), and can be controlled from any audio amplifier or pre-recorded sequencer programme.

Any such system calls for three basic pieces of equipment:

1. A source of instructions to provide the light control information;
2. A piece of equipment which will convert these instructions into controlled power which is then applied to the lights;
3. The light system itself.

This series of articles describes an overall system which is driven by the signal from an audio amplifier; describes other methods of providing the initial instructions to drive a single general purpose power controller, and a novel technique for displaying the final effect.

At the end of the constructional series several alternative application systems will be described—some which have been successfully used by the designer and others, which are food for thought for further experimentation.

**MUSIC  
INSPIRED  
AND LIGHT  
COLOUR**

**P.E.  
AURORA**


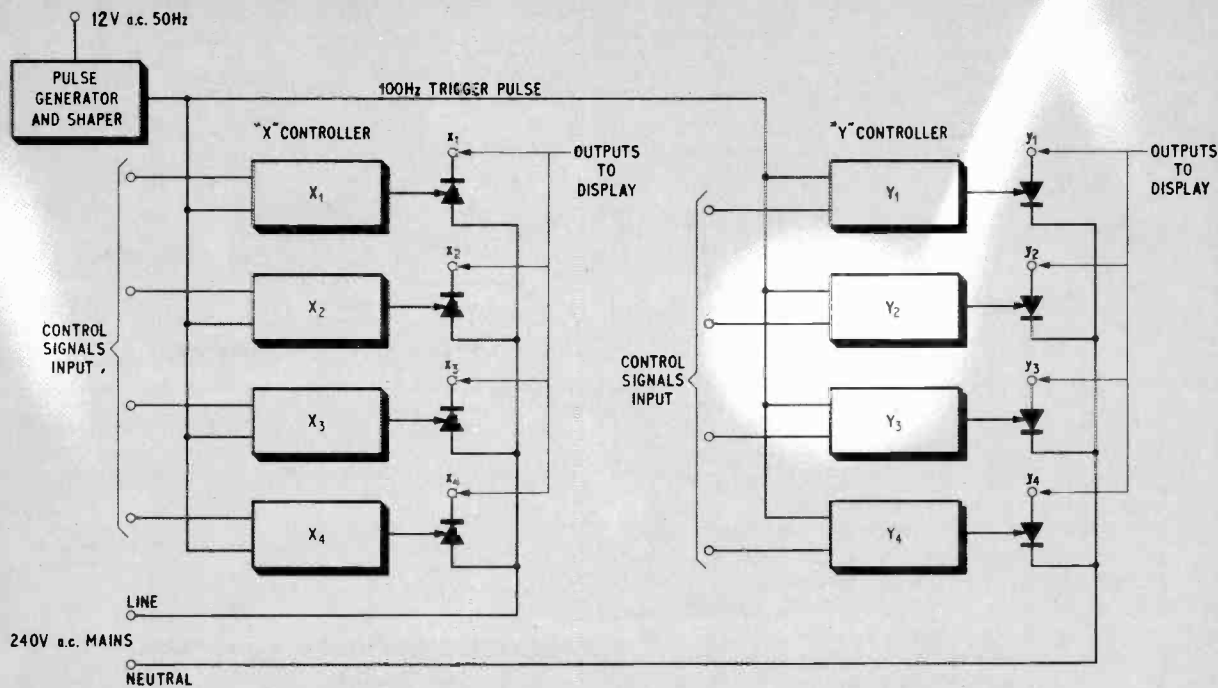


Fig. 1. Basic eight channel thyristor switching system used to operate a 16-lamp matrix of P.E. Aurora

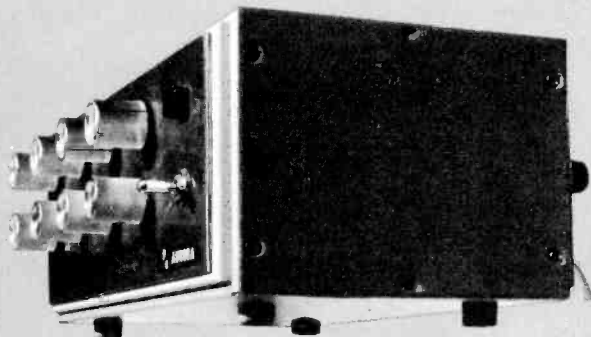

## PART 1 BY M. J. HUGHES M.A.

The P.E. Aurora system was specially commissioned by Practical Electronics and is the result of close collaboration with M. J. Hughes, M.A., who designed the electronics, and M. Leonard, A.R.J.B.A., who was responsible for the artistic presentation of this light display shown at the "Audio & Music Fair" and the "Electric Theatre" exhibition.

### THYRISTOR OR TRIAC CONTROL

The heart of the system to be described is a d.c. voltage controlled phase shifter, coupled to a trigger circuit, which in turn fires either triacs or thyristors early or late within the mains a.c. waveform. The controller's input is of high impedance and has a linear control over input voltages ranging from 0.5V to 1.0V d.c.

The input is 100 per cent isolated from the output, thus the control voltages can be derived with safety from many forms of semiconductor circuitry. Two such circuits will be described in detail: a narrow band filter unit—for sound to light control, and a self programming digital unit which provides constantly changing light patterns.

Other input circuits, which will be discussed later, include tape control (using a conventional  $\frac{1}{4}$  in or cassette tape recorder) and several types of optical feedback control.

The system to be described will be based on eight individual control channels supplying a matrix of 16 lamp nodes, but individuals can tailor their systems to suit the application or their pockets. The basic system is shown in block form in Fig. 1.

### DESIGN SPECIFICATIONS

As the original intention was to make the "P.E. Aurora" a versatile piece of equipment the following design parameters were self-imposed:

1. Ultimate a.c. power control should be by readily available thyristors or triacs and the

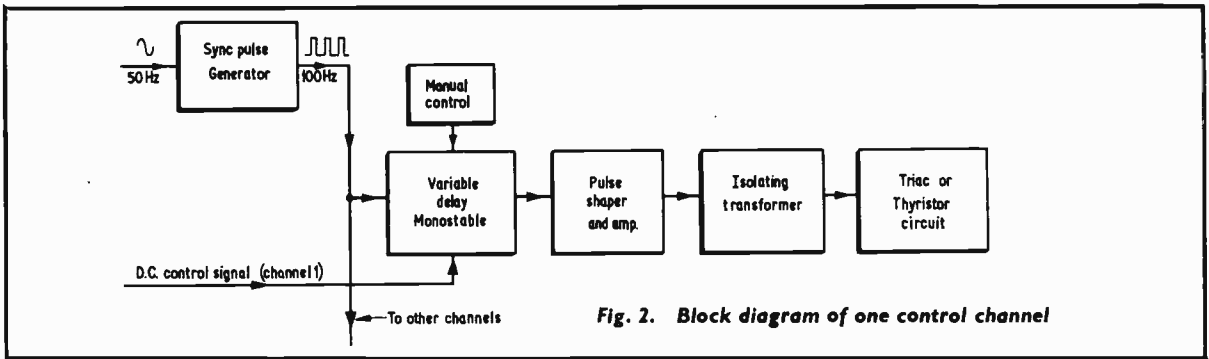


Fig. 2. Block diagram of one control channel

equipment should interface with as wide a range of trigger requirements as possible, in conjunction with the a.c. mains frequency.

2. Either triacs or thyristors could be used without any change in circuitry, provided they are capable of operation from the voltage and current source of the switching circuit.
3. The power side of the controller should be isolated from the input for safety reasons—this isolation should not be by optical means (which is quite often specified) because it presents difficulties in producing a simple mechanical construction.
4. Phase angle control should be over a range of as near 180 degrees as possible to obtain full lamp brightness and as near full extinction as possible.
5. Input signal requirements should be as wide as possible and be such that the equipment can be used with semiconductor circuitry.
6. Simple unstabilised power supplies should be used. All circuitry should be simple, should use low price components, and should need no specialised test equipment for setting up, apart from a multimeter and possibly an audio signal generator.

7. Perhaps the most difficult of the specifications to achieve; that the lamp brightness should appear linearly related to the input control signal.

All the above parameters have been met in the equipment to be described.

### FREQUENCY LOCKED SWITCHING

Fig. 2 shows a block diagram of a single control channel. All thyristor or triac phase control systems should be accurately locked to the mains frequency so that linear control may be effected by firing the device early or late within a single mains frequency cycle or half-cycle.

The triacs require a trigger pulse every positive and negative half-cycle of the mains while a thyristor—a unidirectional switching device—requires trigger pulses during positive half-cycles only. The sync pulse generator produces a single positive going pulse at the start of every positive and negative going half-cycle of the mains frequency. This pulse is applied to all channels in parallel (the present generator will satisfactorily drive up to 10 control channels).

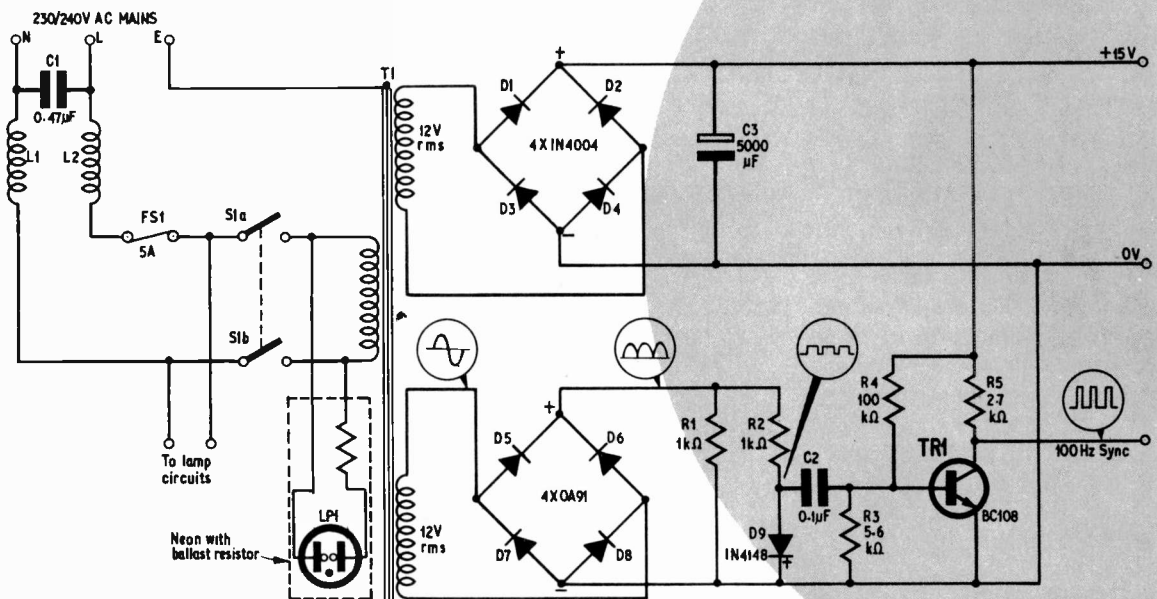


Fig. 3. Circuit diagram of the power supply and sync pulse generator





Considering a single channel; the arrival of this pulse fires the monostable multivibrator, the output of which rises to approximately +10V and dwells at this level for a period which is set either by the manual control or the input d.c. control signal. It is this dwell time that controls the phase angle of the final trigger pulse and is designed to be in the range of 2 to 9ms (this gives a range of firing angles of approximately 36 to 160 degrees).

After the dwell period the output of the monostable falls back to zero volts and this negative going transition is detected and amplified by the pulse shaper, which is coupled to the primary winding of a simple pulse transformer. This provides isolation between the mains and low voltage parts of the circuit. The secondary of this transformer is directly coupled across the cathode and gate of the thyristor or main terminal 1 and gate of the triac.

Trigger pulses will arrive at the transformer every 0.01sec and thus will fire a triac on every half-cycle. If a thyristor is used only alternate pulses will fire the device—pulses arriving during negative excursion half-cycles will be ignored.

### POWER SUPPLY AND SYNC PULSE GENERATOR

As the power supply and sync generator are closely coupled to the mains transformer, both units are shown in Fig. 3. T1 is a straightforward mains transformer having two separate secondary windings each providing 12V a.c. One of the windings rated at 500mA is connected to a standard bridge rectifier comprising diodes D1, 2, 3, and 4. The smoothed output of this supplies sufficient power to drive all the circuitry required for the eight channels.

The inductors L1 and L2 together with C1 provide a satisfactory degree of interference suppression. The rating of fuse FS1 will depend on the total power the controller will eventually be driving. In the case of the prototype a 5A fuse was sufficient. Later we will deal with modifications necessary for higher power operation.

The main switch S1 only serves to isolate the electronics from the mains—it does not disconnect the main power to the lamps owing to problems in obtaining a suitably rated panel switch of reasonable mechanical proportions.

The second winding of T1 is connected to a bridge comprising four germanium diodes—D5, 6, 7, and 8. This provides a full wave rectified signal across the nominal load R1.

For those constructors having access to an oscilloscope, approximate waveforms are shown on the circuit diagram. Diode D9 is a small signal silicon type connected in a forward biased direction. The 600mV forward drop across this device serves to clamp the full positive excursion of the bridge producing a waveform closely resembling a square wave with fairly fast negative going edges. This waveform is inverted and its level restored to approximately 10V (off load) by transistor TR1.

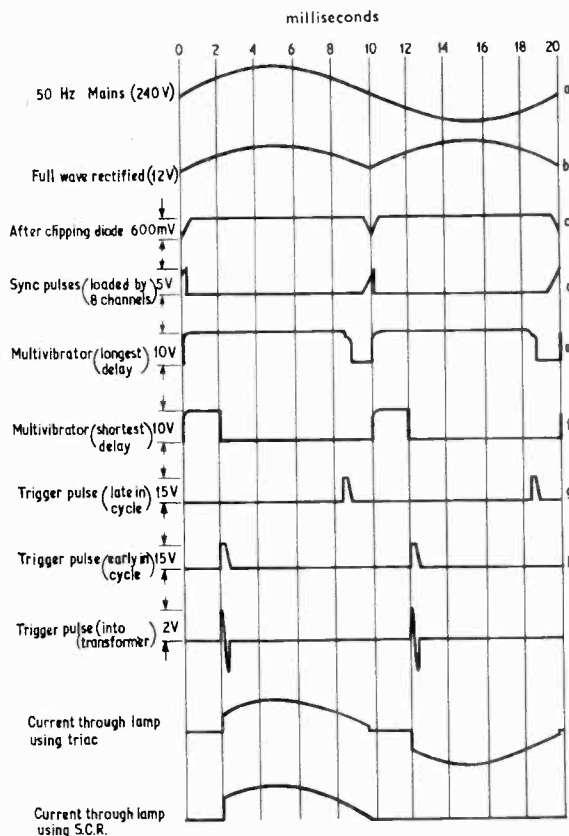


Fig. 4. Waveform timing diagram as measured on an oscilloscope. Typical amplitudes are shown. All levels are measured relative to the zero voltage rail. Waveforms (g) and (h) show the extremes of firing angle, 36 to 160 degrees

The output is a 100Hz sync pulse which is then applied to all the monostable stages for triggering the thyristors. On full load the amplitude of the positive going pulses at the collector of TR1 falls to approximately 5V.

The waveform timing diagram shown in Fig. 4 shows the relationship of sync pulses to the original mains waveform (a, b, c, and d).

However, due to the trigger sensitivity of the monostables (which require approximately 4 volts for reliable triggering) the monostable does not fire until the sync pulse reaches this voltage which occurs almost exactly at the moment the mains waveform crosses the zero voltage line (Fig. 4c).

## MONOSTABLE AND TRIGGER CIRCUIT

Fig. 5 shows the circuit of the monostable and trigger for a single channel. In this system eight such circuits are required; for other systems more or fewer can be built.

TR3 and TR4 form the main monostable, these being cross coupled by C5 and R11. Sync pulses are applied to the base of TR3 via C4 and D10. In the absence of such pulses TR4 is normally "on", its base being returned to the positive rail by R9 and the parallel combination of VR1 (a preset potentiometer), VR2 (the manual control) and TR2.

On the arrival of a sync pulse at TR3 this transistor switches on rapidly; the negative going transition at its collector is transmitted via C5 to TR4 which turns off and stays off for the duration of the time constant of C5 together with R9, VR1, VR2, and TR2. R9 guarantees a minimum dwell time (in this case approximately 2ms); as will be seen later this corresponds to maximum lamp intensity.

This resistor can be safely reduced to 22kΩ if absolute maximum brightness is required, but if this

is done the circuit begins to operate on the edge of stability. In actual fact, very little increase of light output was apparent by firing earlier in the cycle than 36 degrees which is what 2ms represents.

The maximum dwell time is set by VR1. This is necessary to prevent the possibility of the monostable "hanging on" into the next mains half-cycle. The effect of deliberately causing this to happen will be described during the setting up procedure. Maximum dwell time should be approximately 9ms for stability—this also allows for variations in mains frequency.

Having set the minimum and maximum dwell times, intermediate periods can be set by adjusting VR2 (the front panel control) or by causing TR2 to draw current. Voltage control of this dwell time is effected by drawing base current through TR2 by a voltage applied to the input of R6. It is important to note that the control voltage must be negative with respect to the positive rail as TR2 is a *pnp* transistor.

No control is effected until the input voltage exceeds the emitter-base forward voltage drop (500–600mV). As the input voltage increases the collector current of TR2 increases in proportion and thus linearly reduces the dwell time of the monostable. See Fig. 4e and 4f.

As it is the dwell time which determines the position of the ultimate trigger pulse within the mains half-cycle, it is the negative going excursion of the collector of TR4 that is used. This is differentiated by C6 and R13 before being applied to TR5 which provides the trigger pulse drive into the isolating transformer T2.

The output of T2 is directly connected across the cathode and gate of the thyristor or triac. The amount of gate current to the thyristor is determined by the tuned circuit C7 and T2 primary. If this gate current is insufficient for the device used C7 can be

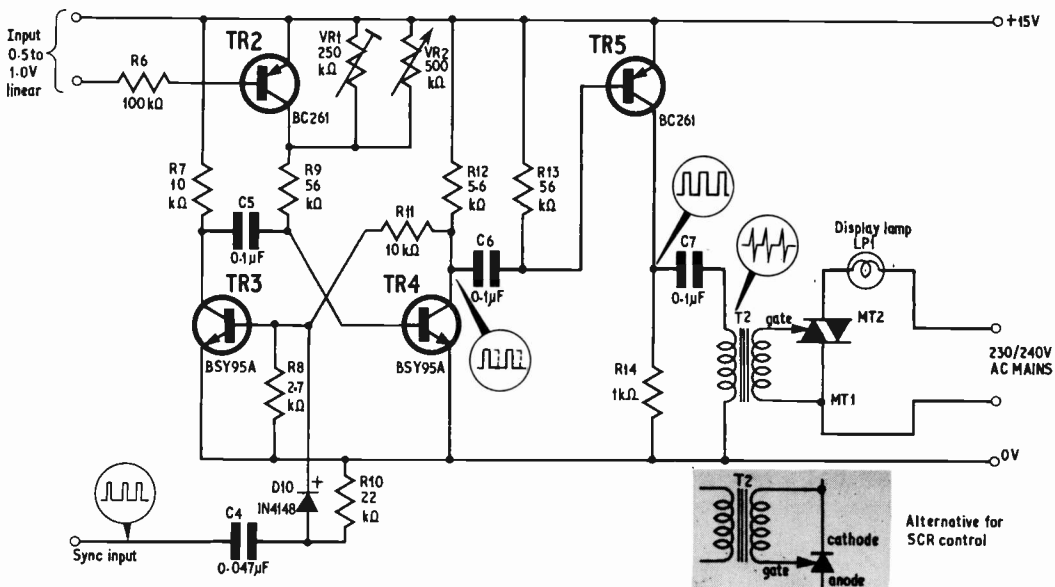


Fig. 5. Circuit diagram of the monostable timing and trigger for one channel

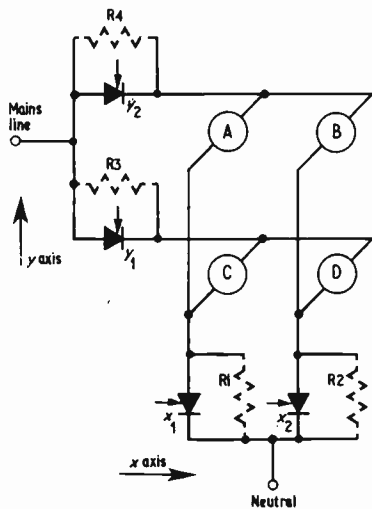


Fig. 6. Simple thyristor matrix of two by two. It is necessary to include the ballast loads (R1 to R4 shown dotted) in the form of 15 watt lamps. These will have a higher resistance than the lamps at the matrix nodes, but still low enough to provide at least 20mA holding current for the thyristors. Each lamp node should not be less than 40 watts to minimise interaction

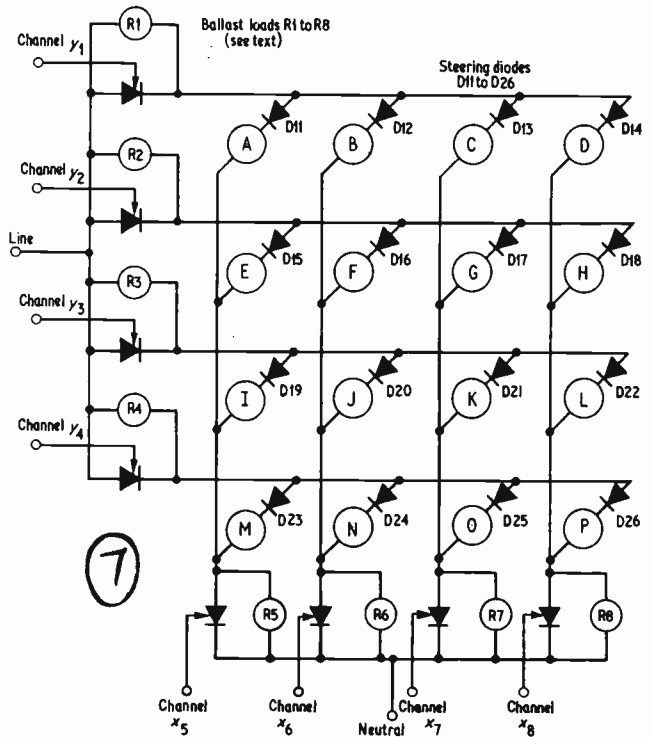


Fig. 7. A complete four-by-four matrix where symbols A to P represent the lamp nodes (40 watts each), symbols R1 to R8 represent the ballast loads (15 watt bulbs), D11 to D26 steering diodes to avoid interaction are rated at 600V 1A for each lamp node. Thyristors for channels 1 to 8 must each be rated at four times the current through each node.

increased to a value up to 0.2 $\mu$ F. Trigger current for the thyristors or triacs is not greater than 30mA 3V. Polarity of the output of T2 is not important owing to differentiation of the waveform.

### TRIAC AND THYRISTOR MATRIX

It was mentioned earlier that a novel type of output was available from the controller, and it is worth discussing at this point as it requires a slight variation in thyristor orientation. If it is desired, each control channel can be used independently of any other, thus one can control up to eight lamp circuits. If this is all that is required then the following details can be ignored and the circuits wired up exactly according to Fig. 5.

Provided one is prepared to use thyristors, it is possible to obtain up to 16 lamp control channels from the eight basic trigger circuits. This is done by matrixing four of the channels against the remaining four.

The principle of the matrix is shown in Fig. 6, which represents four lamp circuits controlled by four thyristors (x1, x2, y1, and y2). One side of lamps A and B are commoned and taken to the cathode output of thyristor at y2; similarly one side of C and D is taken to y1. Conversely the free side of A is commoned with C and taken to x1; similarly with B and D to x2.


Note, however, that the commoned sides of A and C with B and D go to the anode ends of thyristors x1 and x2. The anodes of the thyristors on the Y axis are both taken to one side of the mains (say "line") and the cathodes of those on the X axis to "neutral". All the thyristors can be individually controlled by trigger pulses from the control channels.

If one ignores the fact that a thyristor needs a holding current to sustain conduction, one can simply say that if y1 and x1 are triggered, lamp A will go on; y2 with x1 and x2 will light A and B and so on. In practice, however, this simple concept will not work unless trigger pulses arrive at the x and y thyristors simultaneously.

Assume that y2 is triggered but neither x1 or x2; no current will flow through y2 and hence it will immediately extinguish at the end of the trigger pulse. If a trigger pulse was to arrive at x1 or x2 later but within the same half-cycle, neither of these would hold on.
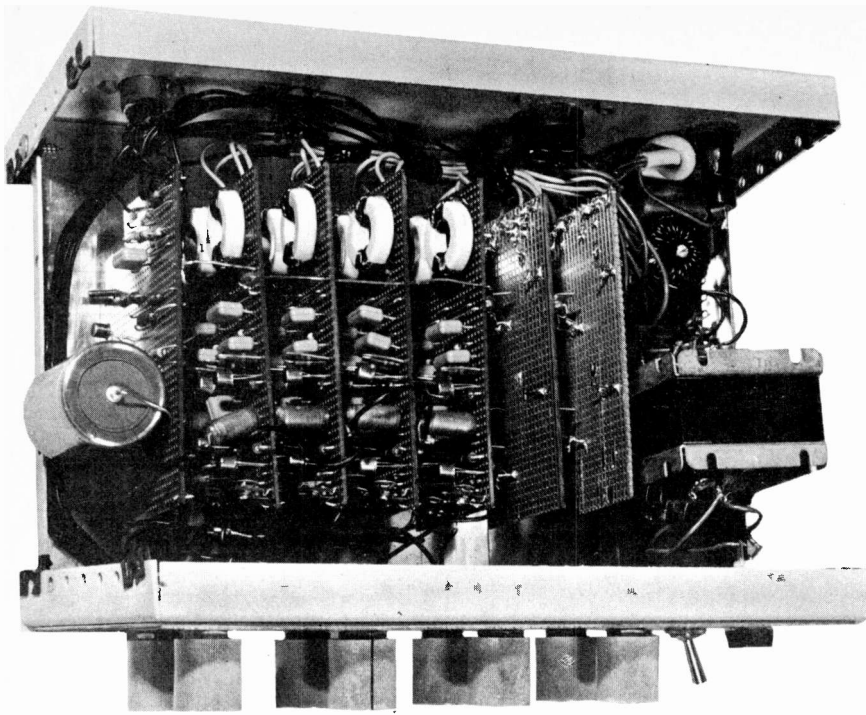
### HOLDING CURRENT

For the matrix to work we must provide some holding current when either axis switches. This holding current can be provided by the resistors shown dotted as R1 to R4 (Fig. 6). If either of the thyristors on the Y axis are now triggered they will



Top view of the controller chassis showing the circuit boards and power unit

draw current through either R1 or R2. Likewise for devices on the X axis through R3 or R4.

The values of these resistors must be carefully chosen so that they pass sufficient holding current, but not sufficient current for any apparent illumination of the main lamps A, B, C, and D, which are in effect in a complicated series parallel arrangement with the resistors. In operation the thyristors work by bypassing the resistors rather like toggle switches.

A few moments puzzling over a network analysis of the equivalent circuit under all combinations of switching will show that the problem is extremely complex. If the circuit was scaled up to a four-by-four matrix the problem could only be satisfactorily solved by computer.

Without going into the complicated mathematics it is sufficient to say that the problem can be solved in two ways:

1. The holding current resistors should be of very high resistance compared with the lamps, or
2. We allow current only to flow in one direction through the main lamps by using steering diodes.

The author has used both methods and quite definitely the diode solution, although more expensive, is by far the best.

Even with diodes one still has to provide holding current and the simplest solution to obtaining resistors of sufficient power rating is to use low power mains rated lamps (these can ultimately be incorporated as part of the display). This holding current is provided by 15W bulbs which allow a reasonable matrix effect if the main display lamps are not less than 40W each.

If diodes (of sufficient voltage and current rating) are also used they should be connected in series with each main lamp in the same direction as the thyristors.

## LAMP LOADS


Using 40W bulbs in the main display, a perfect matrix display, with no parasitic interaction, is obtained. Fig. 7 shows the complete circuitry for the four-by-four matrix using diodes as recommended.

It is important to note that each thyristor on each axis must be capable of handling the load of all four lamps to which it is commoned. In this article we shall be considering 1A thyristors without heat sinks, thus the maximum current that may be drawn by each lamp node is 250mA (i.e. approximately 60W). This can easily be extended by using higher current rated thyristors mounted on heat sinks; however, for domestic use 16 lamps of 60W each are more than adequate.

No advantage is obtained by using triacs in the matrix when diodes are in use. They will, of course, increase the available light in the simple resistor only matrix but will exaggerate the interaction of current paths.
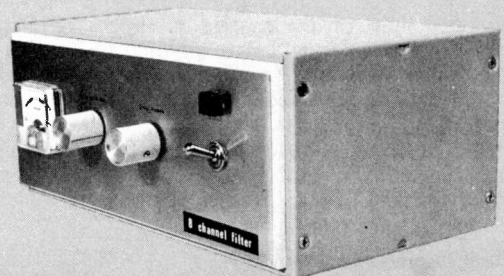
## Next month: construction of the lamp control unit

P.E. AURORA AUDIO BAND SPLITTING FILTER UNIT FOR OPERATION WITH SOUND WILL BE DESCRIBED IN PART THREE





## F.E.T. INPUT

The circuit of the touch switch is shown in Fig. 1. A field effect transistor, TR1, is used at the input to provide a very high input impedance, to the noise voltages developed across the resistor chain R1-R6 through contact with the touch plate.

The source, gate and drain electrodes of the n-channel f.e.t. are closely analogous to the cathode, grid and anode of the triode valve. The voltage drop across source load R2 biases the gate negative with respect to the source. With the values shown, the f.e.t. is biased close to pinch-off, corresponding to valve cut-off.


## TOGGLE ACTION

On touching the touch plate, the stray noise introduced raises the mean drain/source current and the potential across C1 rises. When the touch is removed the potential falls. This negative swing is passed by C3 and C5 to cause the bistable circuit of TR2 and TR3 to change state.

When TR2 is conducting, its collector is close to earth potential and TR3 is biased off via VR1. TR2 is held in conduction by current through R10 and therefore this state is stable. The small current through the relay is insufficient to energise it.

If now a negative pulse is fed to TR2 base via C3 and D1, TR2 turns off. Its collector goes positive and TR3 is turned on via VR1. The collector of TR3 swings towards earth so that TR2 is no longer biased on. The circuit is now in its other stable state where there is sufficient current in the relay to energise it.

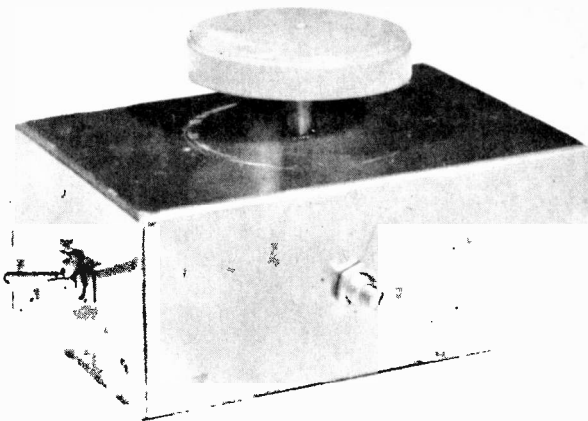A negative pulse fed to TR3 base via C5 and D2 causes the circuit to change state again. The relay contacts switch the power to the equipment to be controlled. Thus the switch provides a touch-on, touch-off operation.



As TR3 has an inductive load, its turn on time has to be speeded up by the addition of C4. It is also protected by diode D3 against transient voltages induced in the relay.

The a.c. gain of TR2 is reduced by C2 to prevent relay chatter.

The times taken for C3 and C5 to charge through R9 and R11 respectively affect the rate at which the bistable states can be changed and these time constants are made large to ensure stable operation.

## RESISTOR CHAIN

The large total value of the resistor chain R1-R6 was found to give good sensitivity. It is obtained by connecting six, 10 megohm carbon resistors in series and arranging for them to be self supporting to avoid leakage problems.

Higher resistance values will provide a higher input impedance and hence more sensitivity but there is a diminishing return as the f.e.t. gate impedance becomes more significant in comparison. If the resistance of R1 is made infinite, or in other words R1 is just an open circuit, the input impedance is so high that the f.e.t. responds to static charges.

Electrolytic capacitors cannot be used for C3 or C5 as these capacitors receive charges of opposite polarity in the two bistable states. Small paper or polyester types are suitable.

## CONSTRUCTION

The circuit components are arranged on a small piece of Veroboard (Fig. 2) mounted inside an aluminium chassis as shown in Fig. 3. The chassis is connected to battery negative to provide screening for the circuit. Layout is not critical and the unit can be made smaller provided it is fully screened.

If mains equipment is to be controlled a piece of metal, bolted to the chassis, should be used to screen the relay contacts from the rest of the circuit.

The supply is made up of three 9V batteries connected in series to give 27V; the circuit will work well on any voltage between 18V and 30V.

A tin lid can be used for the touch plate. This is supported above the chassis by a short piece of Bakelite tube as it is important to maintain a high insulation and a low capacity between the touch plate and the chassis.

## COMPONENTS . . .

### Resistors

R1-R6	10M $\Omega$ (6 off)
R7	6.8k $\Omega$
R8	10k $\Omega$
R9	470k $\Omega$
R10	1M $\Omega$
R11	470k $\Omega$
All $\pm 10\%$ $\frac{1}{2}$ watt carbon	

### Capacitors

C1	64 $\mu$ F elect. 40V
C2	0.1 $\mu$ F polyester
C3	1 $\mu$ F polyester
C4	0.01 $\mu$ F ceramic
C5	1 $\mu$ F polyester

### Transistors

TR1	2N3819
TR2-TR3	ZTX302 (2 off)

### Diodes

D1-D3	OA81 (3 off)
-------	--------------


### Relay

RLA	700 $\Omega$ , 2-pole C/O relay type 43 (Radiospares) or type MH2 (Omron)
-----	--

### Miscellaneous

BY1-9V batteries (3 off), Veroboard $2\frac{1}{2}$ in $\times$ 3in 0.1in matrix, 6in $\times$ 4in $\times$ $2\frac{1}{2}$ in aluminium.	
--	--



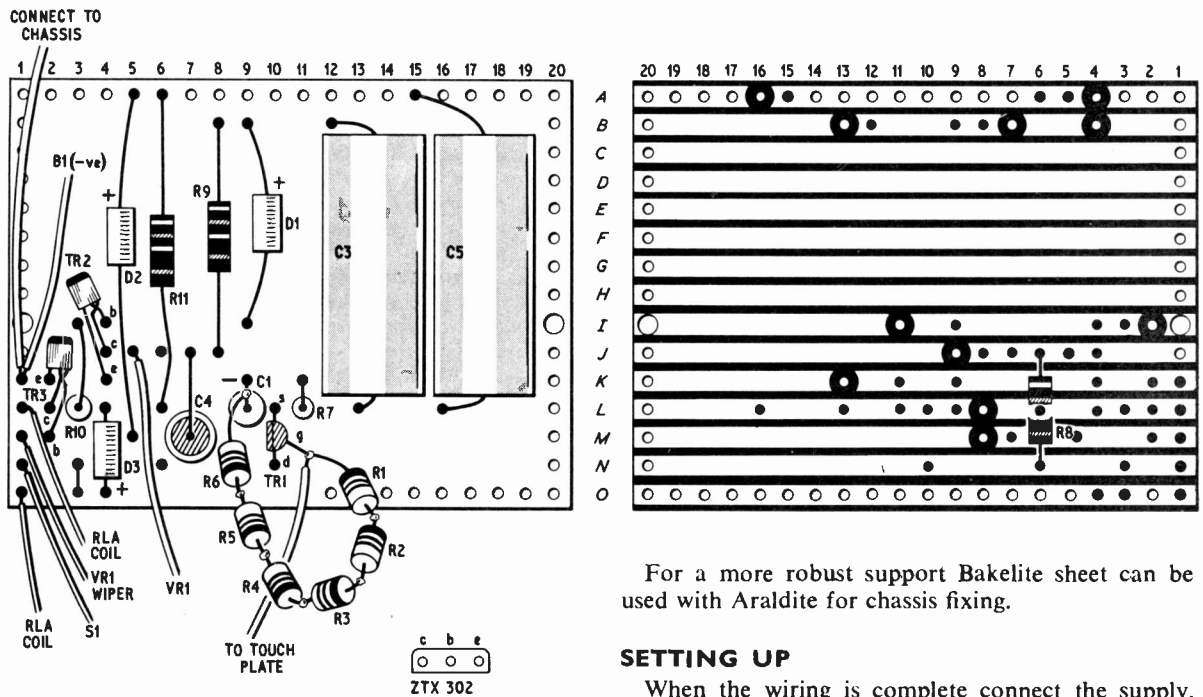

**Fig. 2.** Assembly and wiring details of topside and underside of Veroboard sub-assembly. Resistor R8 is shown on the underside, broken to reveal the connection at hole 6L for R11

For a more robust support Bakelite sheet can be used with Araldite for chassis fixing.

### SETTING UP

When the wiring is complete connect the supply. Set VR1 to mid-position and switch on. The bistable will immediately go into one of its two stable states and the relay may energise.

Touch the touch plate to see if this will trigger the bistable. VR1 must be carefully adjusted to give proper action and equal "on" and "off" sensitivity and stability. If the resistance is set too high, TR3 will not conduct hard enough to keep the relay energised.

As VR1 resistance is reduced, a point may be reached where touching the touch plate causes the relay to chatter. Reducing the resistance a little more will give the proper operating point. If the resistance is too low the relay will remain permanently energised; if this should happen for all settings of VR1 it may be necessary to reduce R5 to 820k $\Omega$  or 680k $\Omega$ .


If the circuit fails to work, the f.e.t. stage can be checked by connecting a voltmeter across C1. Touching the plate should cause an increase in deflection.

The bistable can be checked by connecting a lead to battery negative and touching it to the base of whichever of TR2 and TR3 is conducting. This should cause the bistable to change state.


### SENSITIVITY

When the switch is used in a building, it responds to the mains radiation transferred by bodily contact with the touch plate. When used away from mains wiring it responds to radio frequencies and is somewhat less sensitive. It will not work in a completely screened room or react to the touch of a person who is well "earthed".

If C2 is reduced in value or removed, the touch switch becomes slightly more sensitive and mere body proximity may be enough to cause switching. But under these conditions the setting of VR1 is extremely critical and the switch is less stable. ★

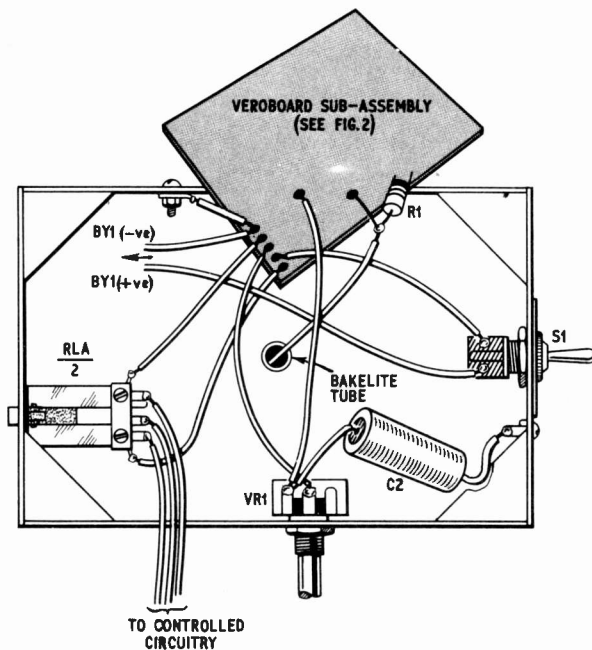

**Fig. 3.** Chassis mounted components and Veroboard wiring details. The precise details of connecting the relay contacts will depend on the circuit application

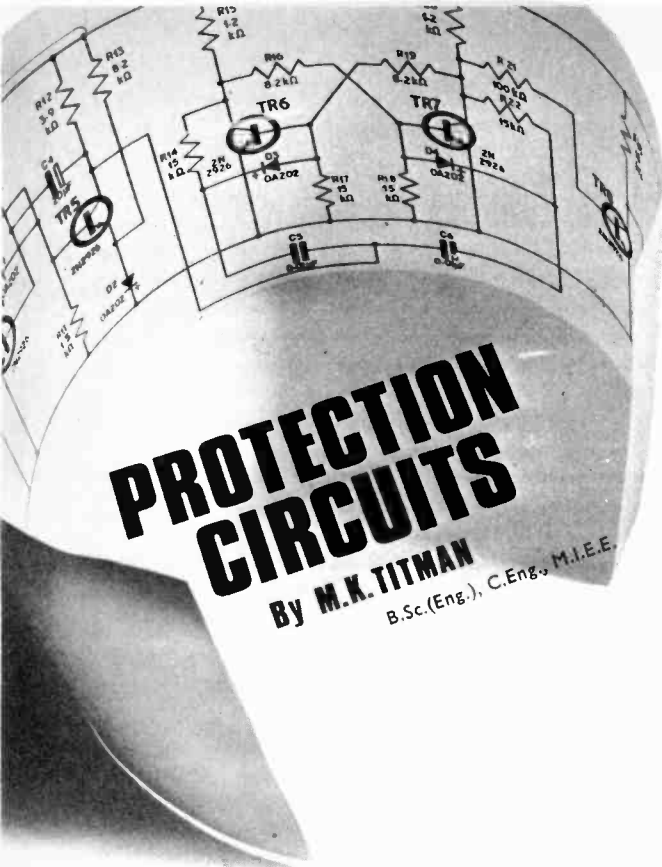

where  $I_{Dp}$  = maximum diode current  
 $V_{in}$  = supply voltage  
 $V_{Dp}$  = Zener voltage  
 $R_s$  = series resistance in ohms

Assuming an integrated circuit supply having an input voltage of 12V and an output rating of 5.1V at 1A, the resistor  $R_s$  would normally have a value of 4 ohms. Consequently the 6.2V protection Zener should be capable of carrying 1.5A continuously, and therefore a 10W, 6.2V Zener diode mounted on a heatsink would be required.

It should be noted that the power rating of the series resistor must be capable of 9W continuous dissipation.

From this it can be seen that the protection Zener diode must be capable of holding and dissipating the full output power of the supply, therefore it is only suitable for low power stabilised supplies.

As an example a 24V d.c. supply capable of delivering 1A would require a protection diode of 26 to 30W rating and clearly this is impractical. For higher power circuits, therefore, crowbar protection circuits are utilised.

### CROWBAR PROTECTION

Crowbar protection circuits operate by effectively causing a short circuit across the supply until the line fuse ruptures. Unlike Zener protection where an intermittent fault would result in a return to normal working after the fault cleared, crowbar circuits positively isolate the faulty power supply.

This can be an advantage in very complex systems. Any failure condition can be used to operate the crowbar circuit and these include overvoltage, overcurrent and overpower.

WITH the increasing complexity of modern semiconductor circuitry, any form of power supply failure can be extremely costly. To forestall this, power supply and circuit failure protection circuits are commonly employed.

In general, overvoltage protection prevents damage to the fed circuit if the power supply voltage increases. Overcurrent and overpower protection prevents damage to the power supply if the fed, or external, circuit fails.

The two forms of protection circuit presented here are the self-resetting and crowbar circuits.

### ZENER DIODE PROTECTION

Of the self-resetting overvoltage protection circuits, the simplest relies on a Zener diode. Fig. 1 shows a typical low power stabilised supply circuit used to power integrated circuits.

The output voltage is held at 5.1V and the supply current of 175mA is limited by the series resistor  $R_s$ .

If the stabiliser diode  $D_s$  failed and went open circuit, this would normally result in an increase in output voltage towards a peak value of 12V. However, with the protection Zener diode  $D_p$  connected the output voltage is held at 6.2V.

### DIODE POWER RATING

For overvoltage protection of larger current stabilised supplies the power rating of the protection diode must be calculated.

In Fig. 1, the maximum current  $I_{Dp}$  likely to be taken by  $D_p$  is determined by the value of  $R_s$ . To evaluate this the following equation should be used.

$$I_{Dp} = \frac{V_{in} - V_{Dp}}{R_s}$$

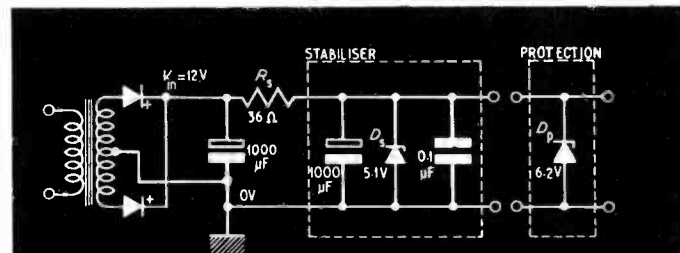


Fig. 1. Zener diode overvoltage protection

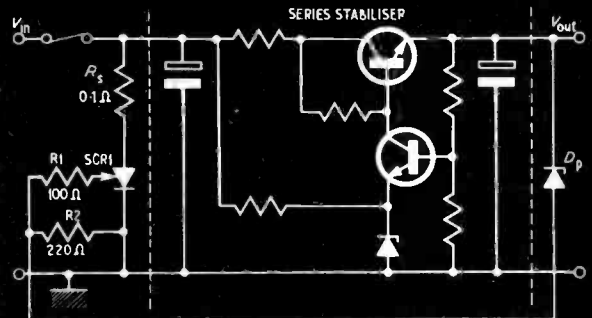


Fig. 2. Overvoltage crowbar protection

## OVERVOLTAGE CROWBAR

In Fig. 2 is shown a typical overvoltage crowbar system operating in conjunction with a high power series stabiliser.

Any overvoltage at the output causes the sensing Zener diode  $D_p$ , to conduct, so passing current to the thyristor gate. The thyristor SCR1 switches on and causes a heavy current to flow through the fuse until it ruptures.

Since the circuit operates only for a very short period the Zener diode can be of 100mW rating as can the thyristor gate resistor.

The thyristor is chosen for its peak transient current rating which can be 25A to 100A for a TO-5 case thyristor. The series resistor  $R_s$  is a low value wire-wound resistor which simply limits the peak transient current.

Whilst an actual overvoltage condition must occur before the crowbar circuit operates, the overvoltage acts for a very short period.

Since the turn-on time of the thyristor is 10 to 20 $\mu$ s and following this a large current flows through the fuse, the supply voltage reduces almost immediately. Consequently the circuitry operated from the power supply receives an overvoltage transient of only 10 to 20 $\mu$ s duration which is usually insufficient time to cause circuit failure.

Because the ratings are based on transient effects, low cost components can be used.

## OVERCURRENT CROWBAR CIRCUIT

One form of overcurrent crowbar circuit is illustrated in Fig. 3 and it can be seen that a certain amount of increased complexity, and therefore expense, is involved.

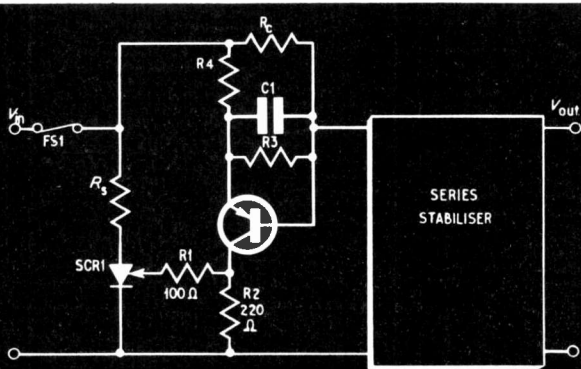


Fig. 3. Overcurrent crowbar protection

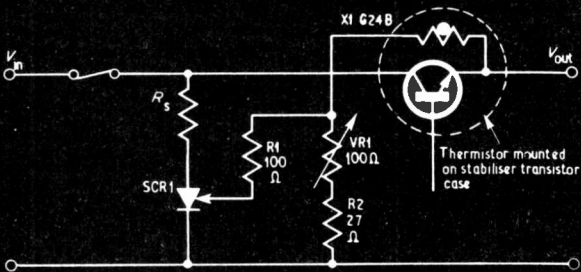


Fig. 4. Overpower crowbar circuit

The current level is sensed by resistor  $R_e$  which is chosen to give approximately 0.5 to 0.75 voltage drop at the fusing current. Generally the fusing current is chosen to be 150 to 200 per cent of full load current. When the current reaches this level the transistor conducts and operates the crowbar thyristor.

The resistor capacitor combination  $R_4$ ,  $R_3$ , and  $C_1$  are incorporated to limit the speed of response of the circuit. This is a vital precaution since the capacitors in the stabiliser and following circuitry usually require a heavy switch-on charging current, consequently the time constant  $C_1R_4$  must be longer than any switch-on surge current periods.

Typical component values using a transistor series stabiliser are  $R_4 = 680\Omega$ ,  $R_3 = 1.8k\Omega$ ,  $C_1 = 10\mu F$ .

## COMPARISON WITH A FUSE

With the increased complexity and difficulties inherent in the design of overcurrent trip circuits, the usefulness of this type of circuit is doubtful. For the vast majority of applications the simple fuse is adequate. However, occasionally this form of circuit is necessary for the protection of complex power equipment.

The main advantages over the simple fuse are a more definite fuse current, increased speed of response and greater reliability.

Reliability is perhaps the most important aspect, since the fuse incorporated with the crowbar circuit can be two or three times the rated current. This increased rating could well increase fuse life by three to ten times above the 1,000 hours usually quoted.

## OVERPOWER CROWBAR CIRCUIT

The overpower crowbar circuit is seldom employed but can have very useful applications. The simplest form of circuit is given in Fig. 4 and consists of a thermistor for temperature sensing together with the thyristor crowbar.

In this example, the directly heated bead type thermistor is located on the surface of the series transistor of the stabiliser. Any excess power dissipation in the series transistor, such as produced by a short circuit, would result in overheating and consequent reduction in thermistor resistance. After a thermal delay period the minimum gate voltage will be exceeded and the thyristor triggers.

Since the body of the thermistor is isolated, any critical or expensive component in any part of the circuit can be monitored. Therefore this form of protection is extremely versatile.

Unfortunately, this form of protection requires a fairly large temperature change for reliable operation and is suitable only for non-critical operation. For more critical operation a single transistor comparator circuit can be used to give an accuracy of temperature measurement to  $\pm 5$  degrees Centigrade.

## APPLICATIONS

The Zener diode protection circuits are only suitable for low power supplies, although they are useful for high current low voltage integrated circuit power supplies.

The thyristor crowbar circuits can be used for any size power supply, and it can be arranged for any type of fault condition to fire the thyristor. The crowbar circuits given can be combined to give a comprehensive protection device using a single thyristor, sensing Zener diode, thermistor and transistor. All the circuits are separate to the basic power supply and modifications to this are not required. ★

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## STEREO TAPE CARTRIDGE

Offering 40 minutes and 80 minutes recording time, compared with the 30 and 60 minute version currently available, is the main feature of the new Scotch 8-track tape cartridges, type S-8TR-40 and S-8TR-80, from the **3M Company**.

The Scotch 8-track cartridges may be used in any cartridge system having recording facilities and may, of course, be played back on any 8-track stereo equipment. The extra 10 minutes on the S-8TR-40 permits the complete recording of an average 12in. LP record.

Recommended retail prices are £1.50 for the 40 minute cartridge, and £1.80 for the 80 minute version.

## MOULDED TRACK POTENTIOMETER

Potentiometers, types T and TS, of all-moulded construction, including the bush and fixing nut, are announced by Plessey.

The type TS is identical to the Type T except that it incorporates a single-pole switch which is suitable for low voltage battery circuits.




Scotch 8-track stereo tape cartridge from the 3M Company

The case is in two halves and is ultrasonically welded together to provide a completely insulated potentiometer.

These potentiometers are particularly suitable for portable transistor receivers and other equipment where a miniature moulded track potentiometer is required.

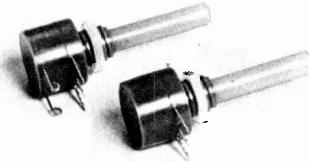Full details and technical specifications can be obtained from Painton Electronic Components, Kingsthorpe, Northampton, NN2 6NA.



Plessey type TS and T miniature moulded potentiometers

## FLASH TUBE

A new photographic flash tube, the Type CD13, has been introduced by the Electronic & Display Equipment Division of Ferranti as an addition to its range of tubes for photographic and similar applications.

A high intensity xenon-filled flash tube for electronic flash equipment, the CD13 produces a white light which is a good match to daylight and is suitable for "daylight" colour films. This device is a straight tube 210mm long.

Operating voltage of the tube ranges between a minimum 400V and a maximum 1,000V, and the typical operating level is 900V. The CD13 is not polarised and the charging voltage and discharge capacitor may be connected across the leads without regard to polarity.

Details of price and local stockists can be obtained from Ferranti Ltd., Electronic and Display Equipment Division, Gem Mill, Chadderton, Oldham, Lancashire.

## CIRCUIT BOARDS

Quality printed circuit boards are now available for the circuits shown in the Mullard book "Transistor Audio and Radio Circuits". The boards manufactured by **Bribond Printed Circuits Limited**, Terminus Road, Chichester, Sussex, are made to the same standards as their industrial boards.

The boards are manufactured from high electrical grade s.r.b.p. laminate clad with 0.0015in copper. The copper tracks are tinned to aid soldering and give protection against oxidation. To aid construction, the

component identification is printed on the reverse in white.

At the moment the following circuits are available:—

- 10W high quality audio amplifier (p. 102) 66p
  - 25W high quality audio amplifier (p. 106) 70p
  - 10/25W high quality audio pre-amplifier (p. 108) 73p
  - 10W audio amplifier (p. 39) 66p
  - 10W audio preamplifier (p. 42) 69½p
- Price each including postage and packing.

## LITERATURE

The new component catalogue from **A. Marshall & Son (London) Ltd.**, is now available to readers. The catalogue lists many new items but probably the most interesting, to our readers, is the section on integrated circuits. This section contains one of the largest selections of I.C.'s available to the amateur we have seen. Apart from the English manufacturers there is a large range from American firms.

Request for copies should be addressed to, A. Marshall & Son (London) Ltd., 28 Cricklewood Broadway, London, N.W.2.

All the new editions of the component catalogues from **Henry's Radio, Home Radio (components), G. W. Smith & Co. (Radio), and LST Components** are up to their usual high standard and make a useful reference for the workshop.

Of particular interest to designers is a revised designers' guide to mercury and alkaline manganese primary power systems published by **Mallory Batteries**.

In addition to describing the two primary cell systems, the guide explains their advantages under widely differing environmental conditions.

It provides detailed specifications of over 100 different cells with the object of giving designers such basic information as capacity, nominal voltage and dimensions.


The designers' guide is also available in French and German and full details can be obtained from **Mallory Batteries Ltd.**, Gatwick Road, Crawley, Sussex.

Containing more than 70 new products, ranging from an 8-track stereo cartridge player for cars to a multi-meter for test engineers, **Eagle International's** new 45-page catalogue is now available from **Eagle International**, Coptic Street, London, WC1A LNR, price 20p.

Divided into sections on hi fi equipment, hi fi accessories and peripherals, radio and tape equipment, office intercoms, public address, test equipment, electronics and accessories, the catalogue carries illustrations, detailed specifications and prices of over 400 products.

# introducing the New SK2 KIT to the Antex range


**£2.40** recommended retail price

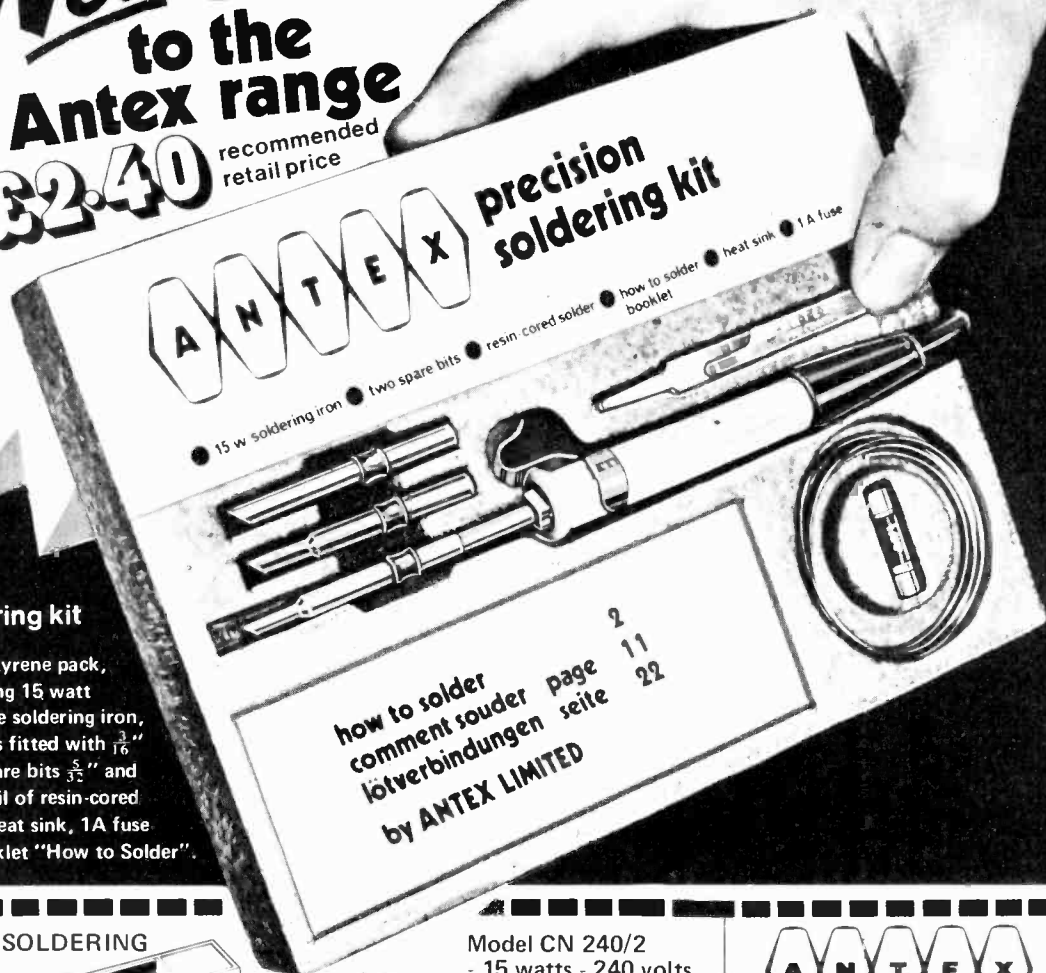

## SK2 Soldering kit

In polystyrene pack, containing 15 watt miniature soldering iron, 240 volts fitted with  $\frac{3}{16}$ " bit, 2 spare bits  $\frac{5}{32}$ " and  $\frac{1}{8}$ ". Coil of resin-cored solder, heat sink, 1A fuse and booklet "How to Solder".

## SK1 SOLDERING KIT

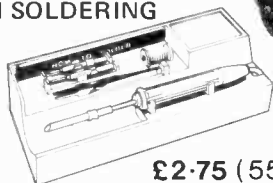

£2.75 (55/-)

In rigid plastic "tool box" containing Model CN - 15 watts - 240 volts miniature iron fitted  $\frac{3}{16}$ " bit. Spare bits  $\frac{5}{32}$ " and  $\frac{3}{32}$ ". Reel of resin-cored solder, heat sink, cleaning pad, stand and booklet "How to Solder"

Model CN 240/2  
- 15 watts - 240 volts



£1.70 (34/-)

Fitted with nickel plated  $\frac{3}{32}$ " bit and packed in handy transparent box.



Model G - 18 watts. Fitted  $\frac{3}{32}$ " bit. Spare bits  $\frac{1}{8}$ ",  $\frac{3}{16}$ " and  $\frac{1}{4}$ " available. For 240 or 220 volts. £0.87 (17/5).



Model F - 40 watts. Fitted  $\frac{5}{16}$ " bit. Spare bits  $\frac{3}{32}$ ",  $\frac{1}{8}$ ",  $\frac{3}{16}$ " and  $\frac{1}{4}$ " available. For 240, 220, 110, 20 volts. From £2.35 (47/-).

Model E - 20 watts. Fitted  $\frac{1}{4}$ " bit. Spare bits  $\frac{3}{32}$ ",  $\frac{1}{8}$ " and  $\frac{3}{16}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).

Model ES - 25 watts. Fitted  $\frac{1}{8}$ " bit. Spare bits  $\frac{3}{32}$ ",  $\frac{3}{16}$ " and  $\frac{1}{4}$ " available. For 240, 220 or 110 volts. From £1.80 (36/-).



## PRECISION MINIATURE SOLDERING IRONS

Antex, Mayflower House, Plymouth, Devon.  
Telephone: Plymouth 67377/8.  
Telex: 45296. Giro No. 2581000.

- Please send me the Antex colour catalogue
- Please send me the following
- Quantity Model Bit Size Volts Price

I enclose cheque/P.O./cash value

NAME .....

ADDRESS .....

PE.4



# RST

## VALVE MAIL ORDER CO.

BLACKWOOD HALL,  
WELLFIELD RD., S.W.16

SPECIAL EXPRESS MAIL ORDER SERVICE

All orders post free!

1N21	0-18	AC127	0-25	BF173	0-30	GJ4M	0-38	OC43	0-40
1N23	0-20	AC128	0-25	BF181	0-38	GJ5M	0-25	OC44	0-18
1N85	0-88	AC187	0-30	BF184	0-25	GJ7M	0-38	OC44M	0-18
1N253	0-60	AC188	0-30	BF185	0-25	HG1005	0-60	OC45	0-15
1N256	0-60	ACV17	0-30	BF194	0-18	H8100A	0-20	OC45M	0-18
1N645	0-25	ACV18	0-25	BF195	0-15	MAT100	0-25	OC46	0-28
1N725A	0-20	ACV19	0-25	BF196	0-25	MAT101	0-30	OC47	0-20
1N914	0-08	ACV20	0-25	BF197	0-25	MAT120	0-25	OC58	0-60
1N4007	0-23	ACV21	0-23	BF861	0-28	MAT121	0-30	OC59	0-65
18021	0-20	ACV22	0-18	BF898	0-28	MJE520	0-88	OC66	0-50
18113	0-15	ACV27	0-25	BFX12	0-28	MJE2955	1.75	OC70	0-13
18130	0-13	ACV28	0-18	BFX13	0-23	MJE3055	0-88	OC71	0-15
18131	0-13	ACV39	0-25	BFX29	0-30	NKT128	0-30	OC72	0-25
18202	0-23	ACV40	0-15	BFX30	0-28	NKT129	0-30	OC73	0-25
2G240	0-08	ACV41	0-25	BFX35	0-08	NKT211	0-25	OC74	0-30
2G301	0-18	ACV44	0-38	BFX63	0-50	NKT213	0-25	OC75	0-25
2G302	0-23	AD140	0-50	BFX84	0-30	NKT214	0-15	OC76	0-25
2G306	0-30	AD149	0-50	BFX85	0-40	NKT216	0-38	OC77	0-40
2G371	0-23	AD161	0-38	BFX86	0-33	NKT217	0-40	OC78	0-20
2G381	0-25	AD162	0-38	BFX87	0-33	NKT218	1.13	OC78D	0-13
2G414	0-30	AF106	0-30	BFX88	0-38	NKT219	0-30	OC79	0-25
2G417	0-23	AF114	0-30	BFY10	1.00	NKT222	0-20	OC81	0-25
2N214	0-43	AF115	0-30	BFY11	1.25	NKT224	0-23	OC81D	0-20
2N247	0-25	AF116	0-33	BFY17	0-25	NKT251	0-24	OC81M	0-20
2N260	0-50	AF117	0-25	BFY18	0-25	NKT271	0-25	OC81DM	0-18
2N404	0-23	AF118	0-23	BFY19	0-25	NKT272	0-25	OC81Z	0-55
2N897	0-18	AF119	0-20	BFY24	0-45	NKT278	0-30	OC82	0-50
2N298	0-43	AF120	0-25	BFY44	1.00	NKT274	0-20	OC82D	0-15
2N706	0-10	AF123	0-30	BFY50	0-23	NKT275	0-25	OC83	0-25
2N706A	0-13	AF126	0-18	BFY51	0-20	NKT277	0-20	OC84	0-25
2N708	0-15	AF127	0-18	BFY52	0-23	NKT278	0-25	OC114	0-38
2N709	0-03	AF139	0-30	BFY53	0-18	NKT301	0-30	OC122	0-50
2N711	0-38	AF178	0-48	BFY64	0-43	NKT304	0-35	OC129	0-50
2N897	0-43	AF179	0-48	BFY90	0-48	NKT349	0-75	OC139	0-25
2N1090	0-30	AF180	0-53	BX27	0-50	NKT404	0-63	OC140	0-38
2N1091	0-33	AF181	0-43	BX260	0-93	NKT678	0-30	OC141	0-63
2N1131	0-30	AF186	0-40	BX276	0-15	NKT713	0-25	OC169	0-20
2N1132	0-30	AFY19	1.13	BX266	0-18	NKT773	0-25	OC170	0-25
2N1302	0-20	AFZ11	0-63	BX277	0-20	NKT777	0-38	OC171	0-30
2N1303	0-23	AFZ12	-0.75	BY51	0.50	OT873	0-35	OC200	0-38
2N1304	0-25	AFY28	0-25	BY95A	0.15	OA5	0-15	OC201	0-48
2N1305	0-25	ASY27	0-33	BY95	0.15	OA6	0-13	OC202	0-63
2N1306	0-25	ASY28	0-25	BT102/500R	0-25	OA47	0-10	OC203	0-38
2N1307	0-25	ASY29	0-30	0.75	OA70	0.10	OC204	0-40	
2N1308	0-30	ASY36	0-25	BTY42	0.75	OA71	0.10	OC205	0-63
2N1309	0-25	ASY50	0.18	BTY79/100R	0.75	OA73	0.10	OC206	0.75
2N1420	0-20	ASY51	0.20	0.75	OA74	0.10	OC207	0.75	
2N1507	0-28	ASY53	0-20	BTY79/400R	0-20	OA79	0.10	OC460	0-20
2N1526	0-38	ASY55	0-20	1.75	OA81	0.10	OC470	0-30	
2N1909	0-25	ASY62	0-25	BY100	0-18	OA85	0-13	OCP71	0-28
2N2147	0-75	ASY66	0-33	BY126	0-15	OA86	0-15	ORP12	0-50
2N2148	0-60	ASZ21	0-43	BY127	0-20	OA90	0-10	ORP60	0-40
2N2149	0-63	ASZ23	0-25	BY182	0-75	OA91	0-08	ORP61	0-43
2N2218	0-30	AY10	0-40	BY213	0-25	OA95	0-08	S19T	0-30
2N2219	0-33	AU101	1.50	BY213	0-25	OA200	0-08	SAC40	0-25
2N2287	1-03	BC107	0-25	BYZ10	0-40	OA202	0-10	SFT308	0-38
2N2297	0-30	BC108	0-25	BYZ11	0-35	OA210	0-25	SFT72	0-38
2N2309A	0-20	BC109	0-25	BYZ12	0-30	OA211	0-25	STX231	0-63
2N2613	1-25	BC113	0-25	BYZ13	0-25	OA2300	0-55	SX560	0-20
2N2646	0-53	BC115	0-25	BYZ15	1.00	OA2201	0-43	SX631	0-20
2N2712	0-25	BC116	0-40	BYZ15	1.00	OA2202	0-43	SX635	0-30
2N2784	0-60	BC116A	0-45	BYZ16	0-63	OA2208	0-43	SX640	0-25
2N2846	2-25	BC118	0-38	BY288C8V3	0-38	OA2204	0-43	SX641	0-25
2N2848	0-43	BC121	0-20	C111	0-18	OA2205	0-43	SX642	0-38
2N2904	0-30	BC122	0-20	CR81/05	0-65	OA2206	0-43	SX644	0-38
2N2904A	0-30	BC123	0-65	CR81/40	0-48	OA2208	0-48	SX645	0.75
2N2906	0-30	BC126	0-25	CS4B	2.50	OA2209	0-33	V15/30P	0-38
2N2907	0-38	BC140	0-55	CS10B	3-13	OA2210	0-33	V30/201P	0-38
2N2924	0-23	BC147	0-18	DD000	0-15	OA2211	0-33	V60/201P	0-38
2N2925	0-18	BC148	0-13	DD003	0-15	OA2222	0-40	XA101	0-10
2N2926	0-13	BC149	0-20	DD006	0-18	OA2223	0-40	XA102	0-18
2N3055	0-75	BC157	0-20	DD007	0-40	OA2224	0-38	XA151	0-15
2N3702	0-13	BC158	0-20	DD008	0-38	OA2241	0-22	XA152	0-15
2N3705	0-15	BC160	0-83	GD3	0-33	OA2242	0-22	XA161	0-25
2N3706	0-23	BC169	0-13	GD4	0-05	OA2244	0-23	XA162	0-25
2N3707	0-15	BCY31	0-30	GD5	0-33	OA2246	0-22	XB101	0-43
2N3709	0-13	BCY32	0-50	GD8	0-25	OA2249	0-38	XB102	0-10
2N3710	0-13	BCY33	0-20	GD12	0-05	OC16	0-38	XD103	0-25
2N3711	0-13	BCY33	0-20	GET102	0-30	OC16T	0-38	XB113	0-10
2N3819	0-35	BCY34	0-25	GET103	0-23	OC19	0-38	XB121	0-43
2N3820	0-88	BCY38	0-30	GET113	0-20	OC20	0-98	ZR24	0-63
2N3823	0-75	BCY39	0-48	GET114	0-15	OC22	0-48	ZR24	0-63
2N3927	0-53	BCY40	0-48	GET115	0-45	OC23	0-60	ZR170	0-10
2N3988	0-30	BCY42	0-45	GET116	0-50	OC24	0-50	ZR271	0-18
28005	0-75	BCY70	0-20	GET120	0-25	OC25	0-38	ZT21	0-25
28301	0-43	BCY71	0-30	GET872	0-30	OC26	0-25	ZT43	0-25
28304	0-63	BCZ10	0-30	GET875	0-25	OC28	0-63	ZTX107	0-15
28501	0-38	BCZ11	0-38	GET880	0-38	OC28	0-63	ZTX108	0-15
28703	0-63	BD121	0-65	GET881	0-25	OC29	0-63	ZTX300	0-13
AA129	0-20	BD123	0-63	GET882	0-25	OC30	0-40	ZTX304	0-18
AA212	0-30	BDY11	1.63	GET885	0-20	OC35	0-50	ZTX500	0-15
AA213	0-13	BF115	0-25	GEX44	0-08	OC36	0-63	ZTX503	0-20
AC107	0-88	BF117	0-50	GEX45/1	0-15	OC41	0-25	ZTX531	0-30
AC126	0-25	BF167	0-25	GJ3M	0-25	OC42	0-30		

### SEMI-CONDUCTOR SET FOR P. E. GEMINI AMPLIFIER £12.95

SEND S.A.E. FOR LIST OF 3,000 TYPES VALVES, TUBES AND TRANSISTORS

Open daily to callers: Mon.-Sat. 9 a.m.-5.30 p.m.  
Closed Sat. 1.30 p.m.-2.30 p.m.

Terms C.W.O. only | Tel. 01-769 0199/1649

Brought to you for your listening enjoyment from the


# Connoisseur

PRECISION IN SOUND

## COLLECTION
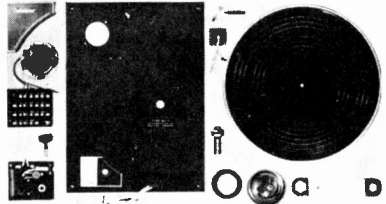
### B.D.1. TURNTABLE KIT

The famous B.D.1. turntable which operates at 33 $\frac{1}{3}$  or 45 r.p.m. incorporates a flexible belt drive system, virtually eliminating vibration and transmission noise — AND IS NOW AVAILABLE IN KIT FORM! So simple to construct — such a beautiful performance, and now it's so easy to own the best!



Rec. Retail Price **£13.28**

Price list and illustrated literature on request to

**A. R. SUGDEN & CO. (Engineers) LTD.**  
Market Street, Brighouse HD6 1DX, Yorkshire. Tel. 2142

## Fingers

The more 'fiddly' the job, the more you depend on your finger-tips. Make sure minor burns and blisters don't rob them of their skill.

Apply BURNEZE, pronto! This unique scientific aerosol cools the heat out of a burn in just 8 seconds, anaesthetizes pain, reduces swelling. BURNEZE — the clever tip for burnt finger-tips. From chemists.



Potter & Clarke Ltd Croydon CR9 3LP



## AMAZING MINI-DRILL

FOR PRECISION MODEL WORK




+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 $\frac{1}{2}$  volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.50 p.p. 13p. De Luxe Professional Kit with 17 tools £7 p.p. 23p. Money Ref. Guarantee.

**MERLIN SUPPLY CO.**

Dept. PE4D, Nailsea, Bristol BS19 1LP

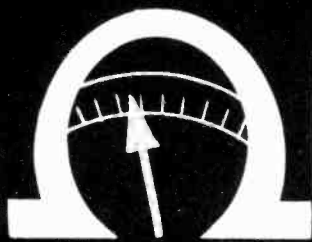

# DESIGN OF OHMMETERS

BY H.A. COLE, C.ENG. M.I.E.R.E.

THERE are many ways of making an ohmmeter circuit; the most popular circuits can be reduced to either of two basic types which, for convenience, we will designate A and B.

In the A-type circuit (Fig. 1), a battery is connected in series with a fixed resistor ( $R_1$ ), a variable resistor ( $VR_1$ ), and the indicating meter ( $M_1$ ).  $R_m$  is the internal resistance of the meter and  $R_t$ , the total resistance in the circuit, is equal to  $R_1 + R_{VR} + R_m$ .

## SIMPLE MEASUREMENT

The unknown resistor ( $R_x$ ) is connected between the two ohmmeter terminals X and Y, which places it in series with the rest of the circuit. To determine the value of  $R_x$ , the X and Y terminals are first shorted together (so as to simulate  $R_x = 0$  ohms);  $VR$  is then carefully adjusted so that  $M_1$  just indicates full-scale-deflection (f.s.d.). This procedure is called zeroing the ohmmeter, and is necessary to compensate for ageing of the battery.

The short-circuit between X and Y is then replaced with  $R_x$  and the meter indication, which will now be less than f.s.d., gives an indication of the value of  $R_x$ ; the greater the value of  $R_x$ , the smaller the deflection.

## CALIBRATION

To illustrate how this circuit works, let the battery voltage  $V_b$  equal 1.5V and let the f.s.d. of  $M_1$  equal  $50\mu A$ . When the ohmmeter is zeroed,  $VR_1$  must be adjusted so that the meter current ( $I_m$ ) equals  $50\mu A$ , which means that  $R_t = \frac{1.5V}{50\mu A} = 30k\Omega$ . Leaving  $R_t$  set at  $30k\Omega$ , now connect to the X and Y terminals, an unknown resistor ( $R_x$ ) of such a value that  $I_m$  is reduced to  $25\mu A$  (mid-scale). From Ohms law,

$$I_m = \frac{V_b}{R_x + R_t} \quad (1)$$

$$\text{or} \quad R_x = \frac{V_b}{I_m} - R_t \quad (2)$$

$R_x = \frac{1.5}{25 \times 10^{-6}} - 30 \times 10^3 = 30,000$  ohms which is the same as  $R_t$ .

This is the first important point to notice about the A-type circuit; the mid-scale resistance value is equal to the value of  $R_t$  corresponding to  $R_x = 0$ .

Knowing that  $V_b$  equals 1.5V, and that  $R_t$  equals  $30k\Omega$  for  $I_m = 50\mu A$  ( $R_x = 0$ ), a table of  $R_x$  for corresponding values of  $I_m$  can be compiled by substituting values of  $R_x$  in equation 1 above (Table 1).

From this table a suitable ohms scale may be produced, which can then be marked on the meter dial face; this is illustrated in Fig. 2, for a few values of  $R_x$ .

TABLE 1

Resistor on test $R_x$ (ohms)	Meter current $I_m$ ( $\mu A$ )
0	50 (f.s.d.)
100	49.8
1k	48.4
10k	37.5
30k	25
100k	11.52
1M	1.5
Infinity	0

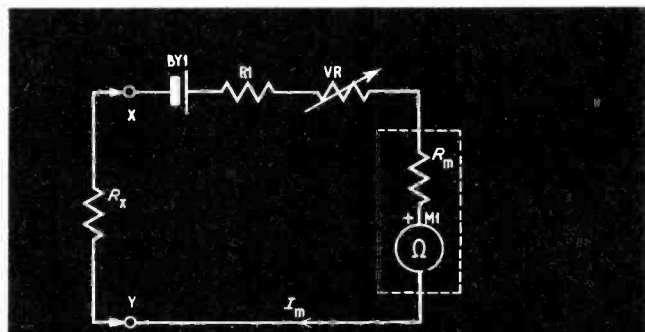


Fig. 1. "A"-type circuit where the battery, meter and variable resistor are all in series

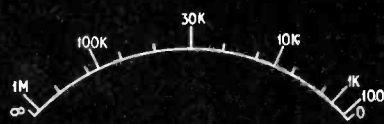


Fig. 2. Typical dial calibration for the example described with Table 1

## SCALE CRAMPING

Note that zero ohms ( $I_m = 50\mu\text{A}$ ) occurs at the right-hand end of the scale, and that infinite resistance ( $I_m = 0\mu\text{A}$ ) corresponding to  $R_x = \text{open-circuit}$ , occurs at the left-hand end.

The scale is also non-linear, following a line of  $1/R$ . It appears severely cramped at the high-resistance end and open at the low resistance end. In fact, if we assume  $1\mu\text{A}$  to be the smallest discernible deflection of the meter pointer (corresponding to 2 per cent of f.s.d.), then we can say that the largest measurable resistance with this particular circuit is about  $1.5\text{M}\Omega$ , using equation 2. Even so, cramping is so severe in this region of the scale that anything greater than about  $1\text{M}\Omega$  is almost unmeasurable.

To measure greater resistance values with this particular circuit (without changing to a more sensitive meter), it is necessary to increase the value of  $V_b$ .

## INCREASING RANGE

Increasing  $V_b$  from 1.5V to 15V increases the measurable resistance by ten times, and also the value of  $R_t$  required for the zero-ohms setting from  $30\text{k}\Omega$  to  $300\text{k}\Omega$ , as is the mid-scale resistance indication.

The advantage of providing a tenfold increase in the value of  $V_b$  means that a single ohms scale can be used for a two-range ohmmeter, the readings corresponding to the higher range being multiplied by ten by the user. This is common practice; typical basic two-range ohmmeter circuits might look like those shown in Fig. 3.

In Fig. 3a, separate VR controls are provided, whereas in Fig. 3b a single VR control is shared by the two ranges. The advantage of having separate controls means that once the two ranges have been zeroed properly it is possible to change from one range to the

other without having to re-zero each time. The only disadvantages of having two controls are additional expense and greater panel space needed to accommodate them.

In the case of one control types of circuit, it is usually fairly coarse in operation, i.e. small adjustments bring about comparatively large changes in the meter indication, which makes zeroing rather difficult.

We have recently seen that the required value of  $R_t$  for the  $\text{OHMS} \times 1$  range ( $V_b = 1.5\text{V}$ ) is  $30\text{k}\Omega$ , and that for the  $\Omega \times 10$  range ( $V_b = 15\text{V}$ ) it is  $300\text{k}\Omega$ . The value of VR1 in Fig. 3b should be made as small as possible for the  $\text{OHMS} \times 10$  range, so that it is no larger than absolutely necessary when it is used for the  $\text{OHMS} \times 1$  range (a resistance value which is small compared with  $300\text{k}\Omega$  is likely to be large when compared with  $30\text{k}\Omega$ ).

## BATTERY AGEING

The batteries used in most ohmmeter circuits are of the carbon-zinc type, a type which is notorious for the variations which occur in its terminal p.d. throughout its life. Because of this, when a new battery is purchased, its terminal p.d. is quite likely to be higher than its nominal voltage, even when delivering a small load current.

In time, however, even if not used, its p.d. will fall and its internal resistance will increase considerably—so much so that it will be unable to deliver the required voltage for the circuit. When it has reached this state the battery is considered as being fully discharged and should be replaced.

## AGEING COMPENSATION

In view of this, the resistance of VR1 must be sufficient to compensate for changes in  $V_b$  ranging from about 13V to 16V on the  $\text{OHMS} \times 10$  range, and from about 1.3V to 1.6V on the  $\text{OHMS} \times 1$  range.

Taking the  $\text{OHMS} \times 10$  range first; when  $V_b$  is 16V, the value of  $R_t$  required to limit  $I_m$  to f.s.d. ( $50\mu\text{A}$ ) when zeroing the ohmmeter is

$$R_{t(\text{max})} = \frac{16\text{V}}{50\mu\text{A}} = 320\text{k}\Omega.$$

Similarly, when  $V_b = 13\text{V}$

$$R_{t(\text{min})} = \frac{13\text{V}}{50\mu\text{A}} = 260\text{k}\Omega.$$

It is the difference between these two required values of  $R_t$  which must be compensated for by VR1; the value of VR1 should therefore be  $60\text{k}\Omega$ .

Since this is not a standard value for a potentiometer, we must either accept a value of  $50\text{k}\Omega$ , which means we won't be able to compensate completely for all changes in  $V_b$ , or one of  $100\text{k}\Omega$ , which would be much too coarse when used on the  $\text{OHMS} \times 1$  range ( $R_t$  for the  $\text{OHMS} \times 1$  range is only  $30\text{k}\Omega$ ). The sensible thing to do then is to select the  $50\text{k}\Omega$  value and to accept the limitation on  $V_b$  compensation.

## RANGE RESISTOR

The next thing to do is select suitable values for R1 and R2. Now, since  $R_{t(\text{max})}$  for the  $\text{OHMS} \times 10$  range is  $320\text{k}\Omega$ , and VR1 is  $50\text{k}\Omega$ , then  $R_2 = (320 - 50)\text{k}\Omega = 270\text{k}\Omega$ —which happens to be a preferred value resistor.

Unfortunately, we run into another problem here, and that is the selection tolerance of R2. For cheapness a  $\pm 20\%$  type could be used, but the value of VR1 (which itself will have a tolerance of  $\pm 10\%$ ) would have to be large enough to compensate for tolerance differences in R2 ( $\pm 20\%$  of  $270\text{k}\Omega = \pm 54\text{k}\Omega$ ), as well as for changes in  $V_b$ .

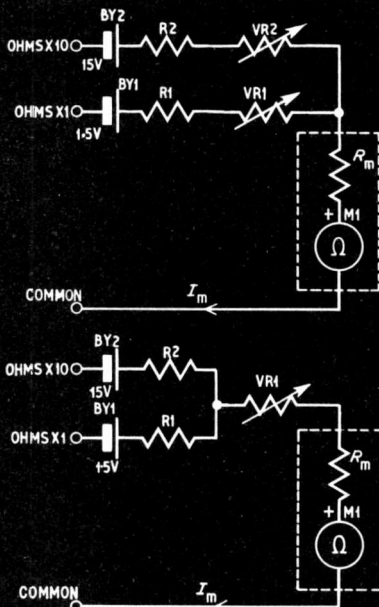


Fig. 3. Basic two-range ohmmeter circuit with (a) two separate controls and (b) one common control

**BRAND NEW**

**SEMICONDUCTORS & COMPONENTS**

**GUARANTEED**

**TRANSISTORS**

2G301	20p	2N3405	45p	40309	32p	BC172	15p	88W70	27p	NKT238	25p
2G302	20p	2N3414	22p	40310	40p	BC175	22p	88X19	17p	NKT240	27p
2G303	20p	2N3420	22p	40311	30p	BC180	12p	88X21	17p	NKT241	27p
2G306	42p	2N3416	37p	40312	47p	BC183	12p	88X21	37p	NKT242	27p
2G308	30p	2N3417	37p	40314	37p	BC184	15p	88X26	45p	NKT243	62p
2G309	30p	2N3570	11-25	40320	47p	BC212L	12p	88X27	47p	NKT244	17p
2G371	15p	2N3572	97p	40323	32p	BCY30	27p	88X28	32p	NKT245	20p
2G374	20p	2N3605	27p	40324	47p	BCY31	27p	88X60	82p	NKT261	20p
2G381	22p	2N3606	27p	40326	37p	BCY32	37p	88X61	62p	NKT262	30p
2G384	22p	2N3607	22p	40329	30p	BCY33	20p	88X76	22p	NKT264	20p
2N696	20p	2N3702	12p	40344	47p	BCY34	22p	88X77	27p	NKT271	20p
2N697	20p	2N3703	12p	40347	57p	BCY38	22p	88X78	27p	NKT272	20p
2N698	25p	2N3704	17p	40348	57p	BCY39	52p	88X79	27p	NKT273	20p
2N706	12p	2N3705	15p	40360	47p	BCY40	37p	88Y10	27p	NKT275	27p
2N708	12p	2N3707	12p	40361	47p	BCY42	15p	88Y11	27p	NKT281	27p
2N709	15p	2N3707	15p	40362	57p	BCY43	15p	88Y24	15p	NKT401	87p
2N709	62p	2N3708	9p	40370	32p	BCY54	32p	88Y25	15p	NKT402	90p
2N718	25p	2N3709	10p	40406	57p	BCY58	22p	88Y26	17p	NKT403	75p
2N726	30p	2N3710	11p	40407	40p	BCY59	22p	88Y27	17p	NKT404	62p
2N727	30p	2N3711	12p	40408	52p	BCY60	27p	88Y28	17p	NKT405	75p
2N914	17p	2N3715	22-25	40410	62p	BCY70	20p	88Y29	17p	NKT406	62p
2N916	15p	2N3720	22-25	40467A	57p	BCY71	42p	88Y32	25p	NKT451	62p
2N919	30p	2N3791	22-25	40468A	30p	BCY72	17p	88Y33	22p	NKT452	62p
2N929	27p	2N3819	35p	40600	57p	BCZ10	27p	88Y37	25p	NKT453	47p
2N930	27p	2N3823	97p	40601	42p	BCZ11	42p	88Y38	22p	NKT603F	32p
2N1090	22p	2N3854	27p	40602	15p	BD116	11-12p	88Y39	22p	NKT613F	32p
2N1091	22p	2N3854A	27p	40603	15p	BD121	65p	88Y40	32p	NKT674F	32p
2N1131	25p	2N3855	27p	40604	25p	BD123	82p	88Y51	32p	NKT677F	30p
2N1132	25p	2N3855A	27p	40605	25p	BD124	82p	88Y52	32p	NKT679	30p
2N1302	15p	2N3856	27p	40606	30p	BD131	37p	88Y53	37p	AA129	10p
2N1303	17p	2N3856A	35p	40607	22p	BD132	37p	88Y54	40p	AAZ13	10p
2N1304	22p	2N3858	25p	40608	25p	BDY10	11-37p	88Y56	90p	NKT10439	37p
2N1305	22p	2N3858A	30p	40609	27p	BDY11	11-62p	88Y78	47p	NKT10139	32p
2N1306	25p	2N3859	27p	40610	27p	BDY17	11-50	88Y79	45p	NKT20329	37p
2N1307	25p	2N3859A	32p	40611	25p	BDY18	11-75	88Y82	52p	NKT20339	37p
2N1308	30p	2N3860	30p	40612	25p	BDY19	11-87p	88Y99	57p	NKT451	12p
2N1309	30p	2N3866	30p	40613	22p	BDY22	11-21	88Y95A	12p	NKT80113	97p
2N1507	17p	2N3877	40p	40614	20p	BDY38	97p	C111	75p	NKT80211	92p
2N1613	25p	2N3877A	40p	40615	20p	BDY60	81-25	C124	24p	NKT80212	92p
2N1631	35p	2N3900	37p	40616	20p	BDY61	21-25	C125	55p	NKT80213	92p
2N1632	30p	2N3900A	40p	40617	20p	BDY62	21-25	C126	55p	NKT80214	92p
2N1637	30p	2N3901	37p	40618	20p	BF115	25p	C425	37p	NKT80215	92p
2N1638	30p	2N3902	37p	40619	20p	BF117	25p	C428	37p	NKT80216	92p
2N1639	27p	2N3904	35p	40620	40p	BF163	37p	C744	30p	NKT80216	92p
2N1711	25p	2N3905	37p	40621	52p	BF167	32p	D16P1	37p	OC20	75p
2N1889	32p	2N3906	37p	40622	52p	BF173	32p	D16P2	37p	OC21	50p
2N1893	37p	2N405X	17p	40623	37p	BF177	32p	D16P3	37p	OC22	50p
2N2147	82p	2N4059	10p	40624	42p	BF178	32p	D16P4	40p	OC23	50p
2N2148	57p	2N4060	12p	40625	42p	BF179	78p	GET102	30p	OC24	50p
2N2160	57p	2N4061	12p	40626	42p	BF180	35p	GET113	20p	OC25	50p
2N2193	40p	2N4062	12p	40627	42p	BF181	32p	GET114	20p	OC26	50p
2N2193A	42p	2N4244	47p	40628	30p	BF184	25p	GET115	20p	OC27	50p
2N2194A	30p	2N4283	17p	40629	25p	BF185	25p	GET116	20p	OC28	27p
2N2217	27p	2N4286	17p	40630	62p	BF194	17p	GET117	20p	OC29	62p
2N2218	82p	2N4287	17p	40631	20p	BF195	20p	GET118	20p	OC30	62p
2N2219	32p	2N4288	17p	40632	22p	BF196	42p	GET119	20p	OC31	62p
2N2220	25p	2N4289	17p	40633	22p	BF197	42p	GET120	52p	OC32	62p
2N2221	25p	2N4290	17p	40634	22p	BF198	42p	GET121	52p	OC33	62p
2N2222	30p	2N4291	17p	40635	17p	BF199	42p	GET122	52p	OC34	25p
2N2287	1-107p	2N4292	12p	40636	17p	BF224	20p	GET123	12p	OC42	20p
2N2297	30p	2N4303	47p	40637	22p	BF225	20p	GET124	12p	OC43	12p
2N2298	17p	2N4304	57p	40638	22p	BF227	22p	GET125	12p	OC44	12p
2N2369	17p	2N5028	57p	40639	72p	BF238	22p	GET126	12p	OC45	12p
2N2410	42p	2N5030	42p	40640	52p	BF244	32p	GET127	12p	OC46	12p
2N2483	27p	2N5172	12p	40641	42p	BFW38	27p	GET128	12p	OC47	12p
2N2484	32p	2N5174	52p	40642	27p	BFW59	25p	GET129	12p	OC48	12p
2N2539	25p	2N5175	52p	40643	62p	BFW60	25p	GET130	12p	OC49	12p
2N2540	22p	2N5176	42p	40644	32p	BFX11	22p	GET131	12p	OC50	12p
2N2613	35p	2N5232A	30p	40645	25p	BFX12	22p	GET132	12p	OC51	12p
2N2614	30p	2N5245	45p	40646	25p	BFX13	22p	GET133	12p	OC52	12p
2N2646	57p	2N5246	42p	40647	27p	BFX29	30p	GET134	12p	OC53	12p
2N2696	32p	2N5249	67p	40648	25p	BFX30	30p	GET135	12p	OC54	12p
2N2711	25p	2N5256	27-75	40649	25p	BFX43	37p	GET136	12p	OC55	12p
2N2713	27p	2N5267	22-62	40650	32p	BFX44	37p	GET137	12p	OC56	12p
2N2714	30p	2N5305	37p	40651	32p	BFX68	67p	GET138	12p	OC57	12p
2N2865	62p	2N5306	40p	40652	32p	BFX84	35p	GET139	12p	OC58	12p
2N2904	30p	2N5307	37p	40653	42p	BFX85	32p	GET140	12p	OC59	12p
2N2904A	32p	2N5308	37p	40654	27p	BFX86	27p	GET141	12p	OC60	12p
2N2905	37p	2N5309	62p	40655	27p	BFX87	27p	GET142	12p	OC61	12p
2N2905A	40p	2N5310	42p	40656	27p	BFX88	25p	GET143	12p	OC62	12p
2N2906	25p	2N5354	27p	40657	27p	BFX89	62p	GET144	12p	OC63	12p
2N2906A	27p	2N5355	27p	40658	27p	BFX90	62p	GET145	12p	OC64	12p
2N2907	30p	2N5356	32p	40659	12p	BFY11	12p	GET146	12p	OC65	12p
2N2923	15p	2N5365	47p	40660	12p	BFY17	12p	GET147	12p	OC66	12p
2N2924	15p	2N5366	47p	40661	12p	BFY18	12p	GET148	12p	OC67	12p
2N2925	15p	2N5367	57p	40662	12p	BFY19	12p	GET149	12p	OC68	12p
2N2926	15p	2N5457	37p	40663	12p	BFY21	12p	GET150	12p	OC69	12p
.. Green	14p	28005	75p	40664	12p	BFY24	12p	GET151	12p	OC70	12p
.. Yellow	12p	28020	42p	40665	12p	BFY25	12p	GET152	12p	OC71	12p
.. Orange	12p	28102	50p	40666	12p	BFY26	12p	GET153	12p	OC72	12p
2N3014	32p	28103	25p	40667	12p	BFY27	12p	GET154	12p	OC73	12p
2N3014	32p	28104	25p	40668	12p	BFY30	12p	GET155	12p	OC74	12p
2N3033	25p	28501	32p	40669	12p	BFY41	12p	GET156	12p	OC75	12p
2N3054	25p	28502	35p	40670	12p	BFY43	12p	GET157	12p	OC76	12p
2N3055	75p	28503	27p	40671	12p	BFY50	12p	GET158	12p	OC77	12p
2N3133	30p	3N83	40p	40672	12p	BFY51	12p	GET159	12p	OC78	12p
2N3134	25p	3N128	70p	40673							

# VARIABLE VOLTAGE TRANSFORMERS

## LIGHT SENSITIVE SWITCH

Kit of parts, including ORP12 Cadmium Sulphide Photocell, Relay, Transistor and Circuit, etc., 6-12 volt d.c. op. price £1.25 plus 12p P. & P. ORP12 including circuit. 63p each. Post Paid.



**A.C. MAINS MODEL.** Incorporates Mains Transformer, Rectifier and special relay with 1 make, 1 break H.D. contacts. Price inc. circuit £2.38 plus 20p P. & P.

## LIGHT SOURCE AND PHOTO CELL MOUNTING

Precision engineered light source with adjustable lens assembly and ventilated lamp housing, to take MBC bulb. Separate photo cell mounting assembly for ORP12 or similar cell. Both units are single hole fixing. Price per pair £2.75 P. & P. 18p.



INPUT 230/240V a.c. 50/60  
OUTPUT VARIABLE 0-260V

### BRAND NEW

Keenest prices in the country. All Types (and Spares) from ½ to 50 amp from stock.

### SHROUDED TYPE

1 amp, £5.50. 2.5 amp, £6.75. 5 amp, £9.75. 8 amp, £14.50. 10 amp, £18.50. 12 amp, £21.00. 15 amp, £25.00. 20 amp, £37.00. 37.5 amp, £72.00. 50 amp, £92.00.

### OPEN TYPE (Panel Mounting) ½ amp, £3.93.

1 amp, £5.50. 2½ amp, £6.63. Carr. 40p on open types.



50 AMPS



½ AMP

## STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

### EXPERIMENTERS' ECONOMY KIT

Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £5.25 plus 25p P. & P.

### NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil plastic thyristor. Speed adjustable 1-80 f.p.s. Price £9.45 50p P. & P.

### HY-LYGH T STROBE

This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. Price £10.88. P. & P. 50p.

### 7-inch POLISHED REFLECTOR

Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

## Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230 mA; 2.5 kΩ, 2A; 5kΩ, 140 mA. Diameter 3½in. Shaft length ½in, dia. ¼in. All at £1.50 each. P. & P. 50p.

50 WATT. 1/5/10/25/50/100/250/500/1/1/5/2/5/5kΩ. All at £1.12 each. P. & P. 11p.

25 WATT. 10/25/50/100/250/500/1/1/5/2/5/5kΩ. All at 78p each. P. & P. 15p.

## RELAYS NEW SIEMENS, PLESSEY, Etc.

### MINIATURE RELAYS - COMPETITIVE PRICES

	1	2	3	4	1	2	3	4
52	6-9	6M	63p*	700	12-24	2 c/o	6M	63p*
180	6-12	4 c/o E-E	43p*	700	16-24	6M	63p*	
185	6-12	4 c/o E-E	63p*	1250	24-36	4 c/o	63p*	
230	6-12	2 c/o	63p*	1250	36-48	6M	63p*	
280	6-12	2 c/o	73p*	2500	36-45	6M	63p*	
700	16-25	4M 2B	63p*	5800	80-85	4 c/o	63p*	
700	16-24	4 c/o	78p*	9000	40-70	2 c/o	50p*	
				15K	85-110	6M	50p*	

\* Including Base  
(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price E-Ex. Equipment. All Post Paid.

### MAINS RELAY

230V a.c. coil 3 c/o. 10 amp a.c. contacts, 50p plus 8p P. & P.

### HOSIDEN DH-02-S Stereo Headphones

8 ohm impedance 20-12,000Hz. Adjustable head band. Price only £2.38. P. & P. 12p. Complete with lead and stereo jack plug.

### MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 8 AMP

Now available EX STOCK. Supplied with full data and applications sheet. Price £1.05. P. & P. 7p. Suitable direct (RCA 40583) 30p each.

### BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, 38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 28 amp. The above two precision made U.S.A. motors are offered in "as new" condition. Input voltage of motor 115V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3.15 plus 35p P. & P. or less transformer £2.13 plus 27p P. & P.



## SANWA MULTI RANGE METERS

New Model U-50DN Multi tester, 20,000 OPV, mirror scaled with overload protection. Ranges—d.c. volts: 100mV, 0.5V, 5V, 250V, 1,000V; a.c. volts: 2.5V, 10V, 50V, 250V, 1,000V; d.c. current: 5µA, 0.5mA, 5mA, 50MA, 250MA. Complete with battery and test probe. £8.00 post paid.

TEN OTHER MODELS. LEAFLET ON REQUEST.

### 230v AC SOLENOID

Extremely powerful with approx. 14lb. pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2½" wide, 3" high. £2.00 incl. P. & P.



### INSULATED TERMINALS

Available in red, white, yellow, black, blue and green. New price 10p each.

### 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4½" x 2½" dia. Price 95p inc. post.



### 200-250 VOLT I.R.P.M. MOTOR

Dimensions: 4" x 3" x 2½". Spindle length 13/16", diameter ¼". Manufactured by SEC. Price £1.13 plus 15p P. & P.



### 200-230 v. ½ R.P.M. MOTOR

Manufactured by Smith. Price 75p inc. post.

### RECHARGEABLE BUTTON CELLS

2x1.2V, 250 MA HR Nickel Cad. Cells, connected to give 2.4V @ 25 milliamp 10 hour rate, complete with 200/250V a.c. charger. Fully tested and unused. Price 48p each plus 8p P. & P. or 2 units for £1.00 post paid.



### UNISELECTOR SWITCHES

NEW 4 Bank 25 Way 24V d.c. operation. £5.88. P. & P. 22p. 6 Bank 25 Way 24V d.c. £6.50. P. & P. 22p. 8 Bank 25 Way 24V d.c. operation. £7.63 plus 22p P. & P.



### VENNER Electric Time Switch

200/250V Ex. G.P.O. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2.75. 15A £3.25. 20A £3.75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



Your local component stockist

East Anglia

EAGLE  
Electronics

Eagle St.

IPSWICH 50075

## AUDIO EFFECTS

5 SHAW LANE, HALIFAX, YORKS.  
LATEST DESIGN—BUY WITH CONFIDENCE  
FROM PROVEN DESIGNERS

### Radio Control

Single channel T.X. Small compact crystal controlled printed circuit. Easy to build and tune. Push Pull O/P. All silicon transistors. Micro action tone switch. Bottom loaded aerial. Coil on P.C. board. Fantastic O/P. Everything bar case in kit form at £6 post paid. Coils ready wound 10/- (50p) extra. Undrilled alloy case 8/- (40p). Ready built in case £8.5.0 (£8.25) post paid.

### Superregen EX

Miniature, lightweight, supersensitive. Uses PP3 or pen cels. Silicon transistors. Front end works straight off. O/P without relay (drives actuator direct) or through 6V 300 ohm relay (not provided). Ideal for model aircraft. In kit form at only £3.5.0 (£3.25) post paid.

### Available Shortly

Superhet kit with cascade front end, dual AGC loops. Super selective. Recommended soldering iron Antex 15 watt 32/8 (£1-02).

### Ham Band Transistor Superhet Receiver Kit

Uses Denco plug in coils 500kHz to 30kHz in 4 ranges. Normally supplied with kit 1-5MHz to 5MHz extra ranges 12/- (60p) each. Slow motion tuning. Push pull audio output to your 8 ohm speaker, black perspex drilled front panel. In kit form at £9.12.6 (£9-02) ready built, calibrated and guaranteed at £15.5.0 (£15-25).

### Power Controller

Pull wave control using braded tric rated 15 amp 3kV. Single control zero to full power. In strong metal box with 13 amp main socket outlet, ideal for fires, drills, floodlights, motors, etc. Ready built at £9.15.0 (£9-75) post paid. In kit form with full instructions £7.5.0 (£7-25) post paid.

### Voice Switch

Make a noise, it switches, high Imp. L/P for XTL mike. Drives your 12 volt relay. Ready built £21.0.0 (£20-00) or in kit form £22.7.6 (£22-37).

### Reverberation Amplifier

Self contained transistorised. Batt. operated. Entirely different approach to sound reproduction. With this unit proper sound delay through reverberation, tones are created truly third dimension for concert hall originality. Two controls adjust volume and reverberation. Simply plug in microphone, guitar, etc., and O/P into your amplifier. Encased in beautiful walnut cabinet 7½" x 3" x 4½" at only £10.15.0 (£10-75) post paid.

### Pocket Metronome

Variable beat. Drives your speaker or earpiece provided, uses PP3. In attractive plastic case at £11.7.6 (£11-37) or as a kit at £11.7.6 (£11-37) both post paid.

### More Oscillator

Just attach your key. Drives your speaker or earpiece provided. Works on pen cells. Ready built in case as above £1.5.0 (£1-25) as a kit 17/8 (87½) both post paid. Latest Mullard manual on audio amps, etc., 32/8 (£1-02) post paid.

### Texas Transistors

Driver, NPN and PNP complementary symmetry. Pack of three 7½/- (35p) post paid.

## BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc. Types available: 6v, 9v, 12v, 18v (single output) £2 each. P. & P. 15p. 9v + 9v; 6v + 6v; or 4½v + 4½v (two separate outputs) £2.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.

R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.E.), 31 Oliver Road, London, E.17

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0576



To be able to do this, VR1 would have to be made 100k $\Omega$ , which is unacceptably large for the OHMS  $\times$  1 range. The simplest solution would be to use a closer tolerance resistor for R2 and accept a reduction in the compensating ability of VR1. Ideally, this should be of  $\pm 1\%$  tolerance before an acceptable result is obtained.

### OHMS $\times$ 1 RANGE RESISTOR

Having settled on the value of R2 in Fig. 3b, we must now turn our attention to the OHMS  $\times$  1 range and determine the value of R1.

Since  $V_{b1}$  is one-tenth of  $V_{b2}$ , then the corresponding values of  $R_{t(max)}$  and  $R_{t(min)}$  for maximum and minimum values of  $V_{b1}$  will be one-tenth of those values determined for  $R_{t(max)}$  and  $R_{t(min)}$  for  $V_{b2}$ . For the OHMS  $\times$  1 range then,  $R_{t(max)} = 32k\Omega$  and  $R_{t(min)} = 26k\Omega$ .

This means that VR1 for this range, should ideally be equal to the difference between these two values, i.e. 6k $\Omega$ . However, VR1 has already been selected as being 50k $\Omega$  which is nearly ten times greater than 6k $\Omega$  and VR1 is already greater than the largest value ever required for R1.

In this case we don't need R1 at all since VR1 (50k $\Omega$ ) is more than big enough to cope with all required values of  $R_t$ . However, if R1 is dispensed with altogether, there would be no built-in protection for the meter if VR1 should inadvertently be set to zero. By insertion of a large value for R1, the operation of VR1 is even coarser than it is already (it is almost ten times greater than it need be).

Resistor R1 must be made large enough to provide a substantial degree of overload protection for the meter, and yet small enough to have little effect on the sensitivity of VR1.

If the meter current is limited to a value equal to ten times the f.s.d. current (most meters will just about stand a 10 : 1 instantaneous overload) then the overload current will be 500 $\mu$ A and the corresponding value for  $R_t$  (assuming VR1 is set to zero, and  $V_{b1}$  is at its highest value of 1.6V) will be equal to  $\frac{1.6V}{500\mu A} = 3.2k\Omega$ .

Then,  $R_1 = R_t - R_m = 1.7k\Omega$ . The nearest preferred value is 1.8k $\Omega$ .

### INDICATION ACCURACY

Before leaving the A-type ohmmeter circuit, it is important to note a very serious drawback concerning its indication accuracy. The validity of the mid-scale indications (the OHMS  $\times$  1 range is 30k $\Omega$ , and on the OHMS  $\times$  10 range it is 300k $\Omega$ ) only applies when the battery voltages are 1.5V and 15V, respectively. See what happens to the indications when the battery voltages are first high, and then low; this need only be done for one ohmmeter range because the overall effect will be the same for both ranges.

Taking the OHMS  $\times$  1 range, and a  $V_{b(min)}$  value of 1.3V, the value of  $R_t$  required to achieve f.s.d. (50 $\mu$ A) is 26k $\Omega$ . The value of VR1 will be adjusted during the zeroing procedure so that it equals 26k $\Omega$ .

From earlier deductions, the value of  $R_t$  required to bring about f.s.d., is also equal to the value of an external resistor ( $R_x$ ) required to bring about half-f.s.d. (25 $\mu$ A). Consequently, the mid-scale indication of the OHMS  $\times$  1 range when  $V_b$  is 1.3V (instead of 1.5V) is 26k $\Omega$ , instead of 30k $\Omega$ , i.e. 4k $\Omega$  below normal. This represents an indication error of about -13%, which is almost the same as the corresponding reduction in the value of  $V_b$ .

For a  $V_{b(max)}$  value of 1.6V (about 7% above the 1.5V normal value), the indication inaccuracy will be about +7%.

From these calculations we may deduce that the indication accuracy of the A-type ohmmeter circuit (quoted at mid-scale) is correct only when  $V_b$  is equal to 1.5V, and that the inaccuracy of this indication will vary from about +7% when the battery is new, to about -13% when it is ready for replacement. These facts are worth knowing, especially when using the ohmmeter to select a close tolerance resistor.

This completes the examination of the A-type ohmmeter. The reasons for going into its circuit in such detail were to illustrate the difficulties in reaching a suitable compromise for the component values, and to highlight its undesirable indication inaccuracies.

### PARALLEL POTENTIOMETER OHMMETER CIRCUIT

The B-type of circuit (Fig. 4) is basically very similar to the A-type circuit shown in Fig. 1, except that the variable resistor VR1 is connected in parallel with the meter (M1) instead of in series with it. The zeroing procedure is exactly the same except that, in this case, the meter current ( $I_m$ ) is adjusted to f.s.d. by shunting the excess current ( $I_s$ ) through VR1.

The total circuit current ( $I_t$ ) is equal to the sum of  $I_s$  and  $I_m$  ( $I_t = I_s + I_m$ ), and is therefore greater than the corresponding value of  $I_t$  for the A-type circuit in which  $I_t$  was always equal to  $I_m$ . This type of circuit therefore consumes more power than the previous type.

The B-type circuit, for the same number of components, is much more flexible than the A-type and the zeroing control VR1 is much smoother in operation. The reason for this, as you will see, is that almost any value can be chosen for VR1, which means that it may

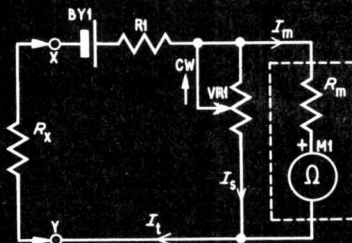


Fig. 4. "B"-type circuit where the variable resistor is in parallel with the meter

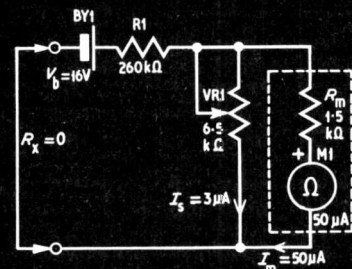


Fig. 5. Component values for the "B"-type circuit to allow for change of battery voltage

be used to determine the overall resistance range of the ohmmeter; in addition to its normal role of compensating for changes in  $V_b$ .

### BATTERY $V_b$ COMPENSATION

Let us first consider the fundamental requirement of compensating for a change in  $V_b$ , assuming a nominal value of 15V for  $V_b$  and a mid-scale resistance indication of 300k $\Omega$  (the same as the corresponding indication for the A-type circuit).

Since the battery voltage  $V_b$  is likely to change from about 13V (for old battery) to about 16V when renewed,  $I_m$  will increase from 50 $\mu$ A (13V/260k $\Omega$ ) to 61.5 $\mu$ A (16V/260k $\Omega$ ). In order to compensate for this change in  $I_m$ , VR1 must be set to such a value that it will bypass the excess 11.5 $\mu$ A at present flowing in  $R_m$ .

The value of VR1 should be 50/11.5 or approximately 4.33 times greater than the value of  $R_m$ ; VR1 should therefore be 6.5k $\Omega$ . This is illustrated in Fig. 5.

What we have just done is to determine the minimum value that VR1 is ever required to have in order to compensate for the maximum likely value of  $V_b$ . One obvious advantage with this type of circuit is that no matter how large  $V_b$  might be, the excess current can always be fully absorbed by VR1 since its value can, if necessary, be reduced to zero—thereby bypassing all the current.

### VR UPPER LIMIT

There is no upper limit for the value of VR1 since we have already shown that  $I_t$  can never exceed 61.5 $\mu$ A (with  $R_1 = 260$ k $\Omega$ ), and that setting VR1 to 6.5k $\Omega$  can take care of that current which is in excess of the 50 $\mu$ A required by the meter.

It is, however, necessary to employ a reasonably large value for VR1 so that when set to its maximum value its shunting effect on  $R_m$  is negligible. This is important in order to ensure that 50 $\mu$ A f.s.d. is still possible when  $V_b$  is approaching its minimum value of 13V. If VR1 is set to a maximum value of 10k $\Omega$  (by using a 10k $\Omega$  variable resistor), then  $I_m$  would equal 43.5 $\mu$ A when  $V_b = 13$ V and 6.5 $\mu$ A would flow in VR1, giving a total ( $I_t$ ) of 50 $\mu$ A.

This means that it would not be possible to obtain f.s.d. when  $V_b$  had fallen to 13V. Looking at it another way, we can say that the minimum value of  $V_b$  which can be tolerated with a 10k $\Omega$  value for VR1 is about 15V. The circuit as it stands, therefore, isn't going to be very useful because the battery will need replacing as soon as its potential has fallen to 15V; a value which is only a little less than its value when new.

### COMPROMISE

The alternatives are to reduce the value of  $R_1$ , or increase the value of VR1. If the value of  $R_1$  is reduced, then the mid-scale indication of the ohmmeter will also be reduced. On the other hand, if VR1 is increased then its rate of adjustment will be more coarse, making it difficult to zero the ohmmeter, particularly when the battery is new and a comparatively low-value setting is required for VR1.

The final choice for VR1 is a compromise between mid-scale resistance indication and ease of zeroing adjustment. A useful rule-of-thumb in selecting a value for VR1 in this type of circuit is that its value should not exceed about ten times the value of  $R_m$  (the resistance of the meter). In the example we have just considered,  $R_m$  is 1.5k $\Omega$ , therefore VR1 should not

exceed 15k $\Omega$ . The initial selection of 10k $\Omega$  for VR1 appears to be quite reasonable; the compromise required in this example must be made with the value selected for  $R_1$ . This may be done as follows.

### SET MID-SCALE INDICATION

If a value of 10k $\Omega$  is selected for VR1, then the maximum acceptable value for  $R_1$  may be determined by assuming a  $V_{b(\min)}$  value of 13V. With  $I_m = 50\mu$ A (f.s.d.), then 7.5 $\mu$ A ( $I_s$ ) will flow in VR1 (determined from  $I_s = R_m \times I_m / R_{VR1}$ , making  $I_t$  equal to 57.5 $\mu$ A.  $R_s$  is determined by  $V_{b(\min)} / I_t$ , which equals 13V/57.5 $\mu$ A = 226k $\Omega$  (220k $\Omega$  is a preferred value).

The mid-scale indication of the ohmmeter is thus 220k $\Omega$ , which is not very different from the corresponding indication of 260k $\Omega$  determined for the A-type circuit when  $V_b$  equalled 13V.

In the B-type circuit, however,  $R_1$  is fixed at 220k $\Omega$  irrespective of the variations which occur in  $V_b$ , since the parallel combination of VR1 and  $R_m$  is always small enough to be neglected. This is very different from the A-type circuit in which the mid-scale indication changed from 320k $\Omega$  to 260k $\Omega$  (due to adjustment variations in VR1) when  $V_b$  changed from 16V to 13V.

This is a very important observation since it shows that the B-type circuit is inherently more accurate than that of the A-type. Actually, this statement ignores the relative abilities of the two circuits to compensate for variations in the internal resistance ( $R_b$ ) of the batteries. However,  $R_b$  is relatively small in the low-current circuits considered so far, and may therefore be ignored.

### RANGE SELECTION

Now consider the second feature of the B-type circuit—the ability to select a particular resistance range by suitable choice of VR1.

We have just seen that a 10k $\Omega$  value for VR1 sets the mid-scale resistance indication at 220k $\Omega$ . Assuming a low-resistance range with a mid-scale indication of about 1k $\Omega$  (30 times smaller than that obtainable with the corresponding A-type circuit) when  $V_{b(\min)} = 1.3$ V, then  $I_t = \frac{V_{b(\min)}}{(R_1 + R_p)}$  where  $R_p = \frac{R_m \times R_{VR1}}{(R_m + R_{VR1})}$ .

The value  $R_p$  is now comparable with  $R_1$  and cannot be ignored; at least, not just yet. Since the mid-scale indication is 1k $\Omega$ , then  $(R_1 + R_p)$  must equal 1k $\Omega$ .

Thus,  $I_t = \frac{1\text{k}\Omega}{1.3\text{V}} = 1.3\text{mA}$ . When the meter is indicating f.s.d. ( $I_m = 50\mu$ A), the current ( $I_s$ ) which flows in VR1 must equal  $(I_t - I_m)$ , i.e.  $I_s = 1.3\text{mA} - 50\mu\text{A} = 1,250\mu\text{A}$ . The value of VR1 required to absorb this amount of current is therefore equal to  $I_m \times R_m / I_s = 60$  ohms.

This is the maximum value that VR1 is ever likely to require. Now, since this value is so small compared with  $R_m$  (1,500 $\Omega$ ), the value of  $R_p$  can be assumed to equal 60 ohms. Furthermore, since  $R_p$  is also very small compared with  $R_1 + R_p$ , i.e. 1k $\Omega$ , we may further assume that  $R_1$  equals 1k $\Omega$ . The value required for VR1 when  $V_{b(\max)} = 1.6$ V and when  $I_m = \text{f.s.d.}$  (50 $\mu$ A) is equal to  $I_m \times R_m / I_s = 48$  ohms.

This is the minimum value that VR1 is ever likely to require. From these two sets of calculations, VR1 is required to vary between 48 and 60 ohms, depending upon the value of  $V_b$ ; a 100 ohms variable resistor would therefore be a very satisfactory choice.

When using such a resistor value, the minimum setting of 48 ohms would represent a setting of 48 per cent of maximum, which would yield very smooth adjustment during the zeroing procedure. The circuit for this particular ohmmeter is shown in Fig. 6.

### TWO-RANGE OHMMETER CIRCUIT

The B-type circuit can also be used to provide two resistance ranges and, like the A-type circuit, this may be achieved by using two batteries and a single zero-adjustment control. In order to make a more direct comparison with the A-type circuit (Fig. 3), a B-type two-range circuit will be designed using battery voltages of 15V and 1.5V, attempting to achieve the same approximate mid-scale indications.

The mid-scale indication for the OHMS  $\times 10$  range of the A-type circuit, using  $V_b = 15V$ , was found to be  $300k\Omega$ . The nearest approach to this figure using the corresponding B-type circuit, and a value of  $10k\Omega$  for  $VR_1$ , was  $220k\Omega$ .

By replacing  $V_b$  of the B-type circuit with a battery of 1.5V, so as to produce an OHMS  $\times 1$  range, then the mid-scale indication will be reduced by a factor of ten, making  $R_1 = 22k\Omega$ . The mid-scale indications are, therefore, not widely different from those of the A-type circuit.

However, as was explained when the A-type circuit was examined, the zeroing adjustment of  $VR_1$  on the OHMS  $\times 1$  range of that circuit was expected to be very coarse, because of the compromise which had to be made concerning the choice of value for  $VR_1$ . Let us now see what the sensitivity of the zeroing adjustment is like in the B-type ohmmeter.

The sensitivity is all right on the OHMS  $\times 10$  range because  $VR_1$  was selected to make it so.

### LOW RESISTANCE SETTING

On the OHMS  $\times 1$  range, the lowest resistance setting required for  $VR_1$  occurs when  $V_{b(max)} = 1.6V$ ; the total current ( $I_t$ ) in the circuit during the zeroing procedure is equal to  $V_{b(max)}/R_1 \approx 73\mu A$ . In this condition, therefore, the value of  $VR_1$  must be adjusted so that it absorbs the  $23\mu A$  which is in excess of  $I_m$ , the f.s.d. current of the meter.

Since  $I_s = 23\mu A$ , and  $I_m = 50\mu A$ , then the required value of  $VR_1$  must equal  $I_m \times R_m / I_s = 3,260$  ohms. A setting of this value represents 33 per cent of  $R_{VR(max)}$ , which represents a substantial angular rotation of the control shaft: the zeroing adjustment will, therefore, be quite smooth in this worst-case condition, and will be even better when the battery is relatively new. The circuit diagram of this particular two-range ohmmeter is shown in Fig. 7.

### SHUNT OHMMETER

In the shunt ohmmeter (Fig. 8), the indicating meter  $M_1$ , is connected directly across the input terminals in parallel with the unknown resistor ( $R_x$ ). The circuit is normally used for measuring very low resistance values (typically 0.01 to 2,000 ohms), and is therefore ideally suitable for measuring the winding resistances of coils and transformers.

The resistance scale differs greatly from the other types of ohmmeters so far examined in that it reads from left-to-right instead of from right-to-left, i.e. zero ohms corresponds to zero deflection and infinite resistance corresponds to f.s.d.

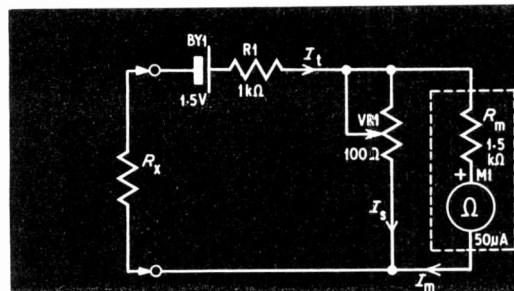


Fig. 6. Single-range parallel control ohmmeter circuit

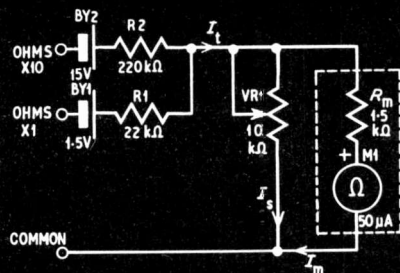


Fig. 7. Two-range parallel control ohmmeter circuit

### SET ZERO

The zeroing procedure is very similar to that adopted for previously described circuits, except that it is carried out with the input terminals open-circuit (corresponding to infinite resistance) instead of with them short-circuit.

To zero this type of ohmmeter, the input terminals are left open and  $VR_1$  is adjusted until the meter indicates f.s.d. ( $VR_1$  and  $R_1$  have the same purpose as in previously described circuits, and their values are determined by the same procedures.) Having done this the unknown resistor ( $R_x$ ) is then connected to the input terminals. This causes the meter current ( $I_m$ ) to be bypassed to some extent and a reduced indication results; the degree of the reduction depending upon the value of  $R_x$ . If a short-circuit is connected to the terminals then all of  $I_m$  is bypassed and zero indication results.

### RANGE SELECTION

The range of the ohmmeter may be changed by connecting an internal resistor across the meter. This reduces the effective sensitivity of the meter and hence more total current ( $I_t$ ) is required to achieve f.s.d.

On the OHMS  $\times 1$  range no ranging resistor is added and the mid-scale resistance indication is equal to the meter resistance  $R_m$ , i.e. 1,500 ohms. Thus, if a resistor ( $R_x$ ) of the same value as  $R_m$  is connected to the terminals, then  $I_t$  will be shared equally between  $R_x$  and the meter;  $25\mu A$  will flow in each.

In order to produce the OHMS  $\div 10$  range provided for in Fig. 8, an internal resistor  $R_2$  must be connected across the meter so that the parallel combination of  $R_2$  and the meter is equal to  $R_m/10$ , or  $\frac{R_2 \times R_m}{R_2 + R_m}$ . Rearranging this expression and substituting known values, we get  $R_2 = R_m/9 = 1,500/9 = 166.6$  ohms.

# NEWS BRIEFS

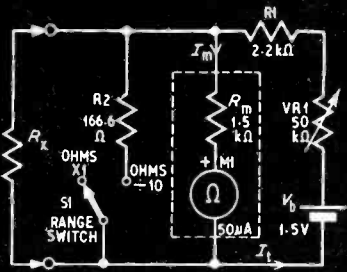


Fig. 8. Shunt ohmmeter in which the meter is connected directly across the terminals and the range selector

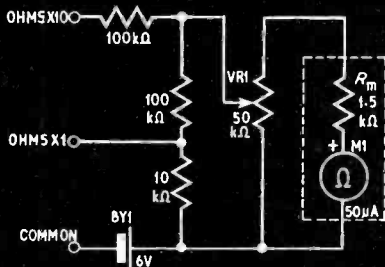


Fig. 9. Constant resistance ohmmeter

## Silicon Pictures

A NEW TV camera tube incorporating a silicon target is being developed by English Electric Valve Co. Ltd. The target of this tube—The Sidicon—is in the form of a mosaic of isolated silicon diodes and its production follows a sequence of modified micro-circuit practices resulting from improved microlithographic techniques.

Results of developments so far, have shown these tubes, which are interchangeable with 1 inch vidicons, to be mechanically, thermally and electrically very rugged, with high sensitivity throughout the visible and infra-red range. The Sidicon has considerably less lag than conventional vidicons and much higher sensitivity. The nature of the targets allows full high-vacuum processing, so ensuring a long life expectancy.

## Brain Box

A SMALL sensitive electronic amplifier no larger than a packet of cigarettes is helping surgeons at the London Hospital, Whitechapel, to trace brain activity during operations for Parkinson's disease.

This is achieved by picking up and monitoring very small signals from the brain through an electrode implanted in it. The amplifier enables the surgeon to track with greater accuracy the exact portion of the brain in which he is working while carrying out this extremely delicate operation.

Made by the British company, Fenlow Electronics Ltd., it is the first miniature data amplifier the firm has produced for medical use. Using f.e.t.'s the amplifier is constructed to stringent safety specifications and costs only £40.

## Transportable Tactical Centre

THE photograph below shows test pattern symbols on the screen of a lightweight display console being checked with a microscope at Hughes Aircraft Company, America, to verify their sharpness and clarity. The console, along with high-speed computers and other electronic equipment, is being built by Hughes for the U.S. Air Force Electronic Systems Division's 407L programme, an advanced concept of tactical air control.

The equipment will be housed in inflatable, modular operations centres that can be transported anywhere in the world and set up in a matter of hours. Hughes is producing 31 of these tactical centres along with two training systems designed to give the Air Force flexible and mobile response to fast-changing battlefield situations.



The same result may be achieved by using the expression

$$R_2 = \frac{R_m}{n - 1}$$

where  $n$  is the number of times that the f.s.d. is to be multiplied. When operating on this range,  $I_t$  is increased by a factor of ten ( $500\mu A$ ), 90 per cent of which flows in  $R_2$ , and the mid-scale indication equals  $R_m/10$  or 150 ohms.


## CONSTANT RESISTANCE OHMMETER

In the constant resistance type of ohmmeter (Fig. 9), the variable resistor VR1 is connected in such a way that the total resistance of the circuit is maintained near-constant as VR1 is adjusted to compensate for changes in  $V_b$ . This is accomplished by connecting VR1 across the meter in such a way that it is used as a potentiometer.

Adjusting VR1 in one direction causes more resistance to be added in series with the meter and a lower value of resistance to be connected in parallel with  $R_x$ ; the reverse occurs when VR1 is adjusted in the opposite direction. This arrangement maintains an almost constant total circuit resistance, and hence the accuracy of the indication is very little affected by the setting of VR1.

Fig. 9 shows a two-range ohmmeter based upon this type of circuit. Only one battery is used and the mid-scale indications on the OHMS  $\times 1$  and OHMS  $\times 10$  ranges are 10k $\Omega$  and 100k $\Omega$ , respectively. The zeroing procedure is conventional and is carried out with the input terminals short-circuited; the ohmmeter scale reads from right-to-left.

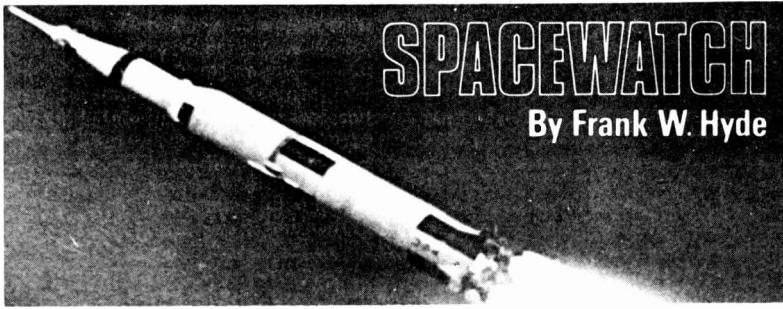This completes this examination of various ohmmeter circuits; there are a great many other types of circuits but these are, in many cases, simply variants of those just described. ★



## WHAT THE ASTRONAUTS SAW

All crews of the *Apollo* missions reported seeing flashes and streaks before their eyes even when closed. It is supposed that this is the result of the passage of ionised cosmic ray particles through the head.

It has been suggested that the light comes from the passage of the high energy particles through the jelly-like medium in the eyeball where light has a lower velocity. Another explanation is that it is the impact of the particles on the retinal cells.

The particles also affect the astronauts' space helmets which are made of a polycarbonate plastic. This plastic is of the long-chain polymer class and as a result of radiation the molecules are broken up. It is known in biological systems that ionising radiations damage cells by disturbing the replication of long-chain molecules.

It has been found that the damage to the space helmets can be studied by etching the streaks caused by the particles. Silicone casts can be made of the holes in the plastic and the rate of etching indicates the degree of ionisation that takes place. The shape of the rubber allows the measurement of the ionisation from point to point along the track. Comparison with the effects of known ions enables the particular particle to be identified.

## RADIO TELESCOPE

Germany's new 100m radio telescope, the largest steerable dish in the world, is nearing completion at Effelsberg some 40km from Bonn. The site is a deep valley in an area of minimum interference.

The design of this telescope has made use of the most advanced principles of structural engineering to ensure that in all positions of the dish the effects of loading both static and variable cause the least departure from paraboloid form. It is expected that the surface accuracy will hold to less than 1mm.

The actual construction of the reflecting surface is interesting, the inner section of 60m diameter is formed from an aluminium sandwich with a honeycomb inner unit bonded to the outer formed sheets. Trial measurements show that the r.m.s. accuracy of the surface of this construction is of the order of 0.22mm.

The next 20m of the surface is covered by formed sheets of aluminium supported by aluminium sections. The standard of accuracy reached in this section of the dish is 0.27mm. The outer section of this ring of panels is connected to the rest of the surface, made up of 6mm square stainless steel mesh panels, by perforated aluminium panels to maintain the aerodynamic conditions required. The accuracy of the outer mesh is about 0.55mm.

The overall efficiency of the telescope is expected to be capable of operation down to a wavelength of 5cm. The central 60m section will, it is hoped, enable wavelengths of 8mm to be used.

Round the outer rim of the dish a collar has been added to reduce the effects of local interference.

## FOCUSING ACCURACY

The focus to diameter ratio is midway between that of the Jodrell Bank and Parkes telescopes. Jodrell Bank Mk1 is 0.25 and Parkes 0.41 with the German dish at 0.3.

The Gregorian system has been adopted which enables both prime focus and secondary focus work to be carried out. For prime focus operation a tube will project through the centre of the sub-reflector to house a prime focus receiver. The intention is to use multibeam methods of observation and as many as nine feeds will be available at the secondary focus. Space receivers at wavelengths of 6cm, 11cm, and 13cm will be provided at the secondary focus.

With such a sophisticated type of radio telescope it is not surpris-

ing that the receiving installation is very elaborate. Cryogenically cooled amplifiers and low noise front ends are being provided.

The timing system will use a rubidium clock as reference for the universal oscillator in line measurements for Pulsar timing and very long base line observations. Continuum measurements will be made by Radiometers.

## COMPUTER CONTROL AND PROCESSING

Data processing is also very elaborate and the basic data processor and steering computer is an ARGUS 500 by Ferranti. This digital computer will co-ordinate transformations, control the telescope drive and process real time data.

From a control desk an observer can choose the astronomical coordinates he needs and the method of scanning. The computer will then carry out the transformations and instruct the drives of the telescope in the necessary velocities in azimuth and elevation.

Since this occupies only a portion of the computer cycle, time is available for storing of data on magnetic tape, operate a fast line printer and Calcomp plotter and have time available for some on-line data processing.

## SUPPORT FOR THE GENERAL THEORY OF RELATIVITY


Working with *Mariners 6* and 7 probes, the team at the Jet Propulsion Laboratory led by Dr J. Anderson have obtained data which, they claim, confirms Einstein's predictions with an accuracy of 2 to 4 per cent.

Previous work by Muhleman and Shapiro using the passive radar technique by bouncing signals off planets close to the sun's limb showed an accuracy of 5 per cent.

The first results with active radar are now available from the 210ft dish at Goldstone. A narrow beam of radio signals at 250kW is sent out to impinge on *Mariner 6* or 7, which are now some 250 million miles beyond the sun. The spacecraft collect the signals, amplify them, and transmit them to the dish at Goldstone. The round trip takes about 43 minutes and can be timed within a microsecond.

The most important source of error is the very considerable dispersion of radio waves by the sun and the results depend on the type of model of the sun's atmosphere that is used.

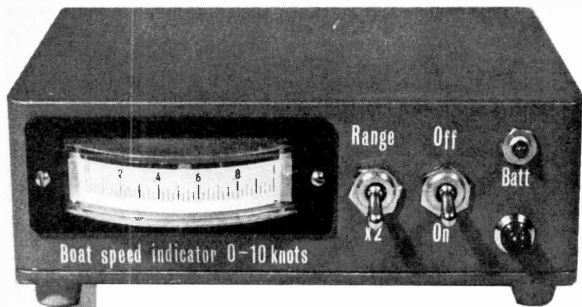Dr Anderson's results conflict with the gravitational theories which show about 7 per cent error.



# BOAT SPEED INDICATOR

By M. KENWARD

**O**WNERS of small boats, both power and sail, often find the need for a boat speed indicator. The speed indicator is useful for a variety of reasons including engine tuning, propeller selection, water skiing, sail trimming, arrival time estimation, and the observance of speed limits. The device described here uses a potentiometric transducer in a simple circuit to produce a linear speed reading on a moving coil meter.

## TRANSDUCER DESIGN

One of the most difficult problems when designing and building a speed indicator is to arrive at a transducer design that is effective, reasonably accurate, yet easy to construct, using limited resources. The design finally arrived at uses a horizontal underwater probe that is turned about its fixed end by the pressure of water moving past it. The probe rotates the shaft to which it is affixed which in turn revolves a potentiometer (VR1) in Fig. 1 by means of two gears. These gears are used to increase the angle by which VR1 revolves, thus decreasing wear on the potentiometer and making for greater accuracy; the probe will only turn through 90 degrees.

A spring is used to give torsional resistance to the probe. Providing this spring has a good number of turns, the torsional resistance will be similar at all probe angles.

The transducer is housed in a suitable round plastics container, the top of which is screwed to a brass plate that is soldered or brazed to the shaft. This gives some degree of water protection to the unit, although the transducer will not be completely waterproof unless the container is carefully sealed after installation. A high quality sealed, carbon track potentiometer is used for VR1.

## CIRCUIT THEORY

From the description of the transducer it will be noted that the resistance of VR1 is varied with the speed of the boat. The variation of resistance will not be linear as the area of the probe exposed to the flow of water effectively reduces as the probe revolves about the shaft; this gives a variation corresponding to  $\text{Cos}^2\theta$  (where  $\theta$  is the rotated probe angle).

With the boat stationary, and the probe at right angles to the fore and aft axis of the boat, the maximum value of resistance will be across output leads a and b (Fig. 1) from the transducer. As the boat speeds up the resistance will be reduced and reach its lowest possible value when the probe is in line with the fore and aft axis of the boat. By inserting potentiometer VR1 in the circuit shown in Fig. 1, the variation can be arranged to give an almost linearly increasing reading, directly proportional to boat speed, on meter M1. However, this reading is only proportional to speed for probe angles up to 45 degrees—due to the shape of the  $\text{Cos}^2\theta$  curve. Thus the transducer is only used in this range of angles.

As stated, the resistance of VR1 is varied as  $\text{Cos}^2\theta$ . The curve of  $\text{Cos}^2\theta$  is shown in Fig. 2 as graph (a). If we arrange for the circuit to give a meter reading that varies to  $\text{Sine}^2\theta$ , the two variations will cancel and give a meter reading corresponding linearly to boat speed. Graph (b) is the actual graph of meter reading against probe angle, taken from 0 to 45 degrees; graph (c) is the result of (a) minus (b). Graph (c) is not quite a straight line—as it should be for complete accuracy—but is within 0.3 of a knot or 5 per cent of the true reading, whichever is the greater, and it is felt that this is sufficiently accurate for most purposes.

The boat speed indicator circuit could, of course, have been made to give a perfect straight line for



(c), but this would make it more complicated and expensive to build. If greater accuracy is required a graph such as (c) can be plotted for the completed unit over the full range of speeds, and this graph used for correcting the speed indicated.

A times 2 range is provided to give greater meter movement at low boat speeds and in this mode the accuracy of the unit will depend mainly on the transducer construction.

### CIRCUIT OPERATION


The input voltage is stabilised by R1 and Zener diode D1 so that variations in battery voltage will not affect the circuit function unduly.

The resulting 10V is applied across VR1 and VR2 and the varying voltage at VR1 wiper is taken via

range switch S3 to a voltmeter circuit. The voltmeter circuit consists of the appropriate range resistors—R3 and VR3 or R4 and VR4—diode D2 and the 500 $\mu$ A f.s.d. moving coil meter M1. The diode is used as a low voltage Zener; its breakdown voltage in the forward bias condition is 0.6V. This means that up to 0.6V can be present across D2 without the meter indicating any current. Once the breakdown voltage is exceeded the diode resistance drops to a low value and the circuit acts essentially as a normal voltmeter.

Potentiometer VR2 is preset to give a reading of 0.01 milliamps on M1 with the wiper of VR1 turned towards VR2 end; this indicates that D2 is just beginning to conduct and as soon as VR1 is varied M1 will indicate the voltage present at its wiper.

Fig. 1. Circuit diagram of the boat speed indicator. Reference is made in the text to the supply voltage, R1 and LP1. The tinted panel indicates the potentiometer used in the transducer.

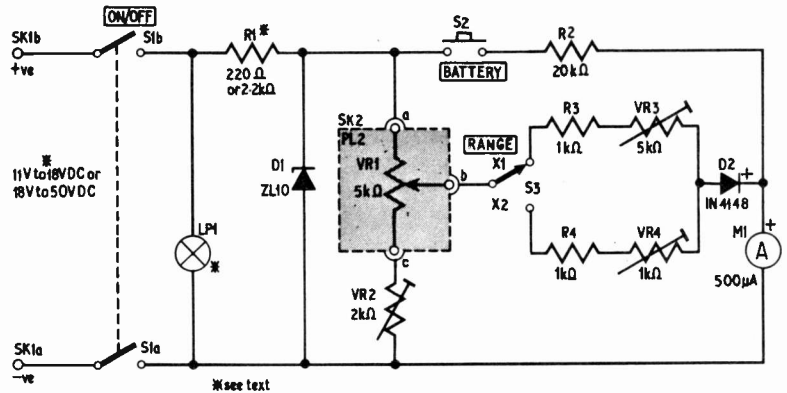

## COMPONENTS . . .

### Resistors

- R1 220 $\Omega$  or 2.2k $\Omega$  (see text)
- R2 20k $\Omega$
- R3 1k $\Omega$
- R4 1k $\Omega$
- All  $\frac{1}{4}$ W,  $\pm$  10% carbon

### Potentiometers

- VR1 5k $\Omega$  high quality sealed carbon lin (see text)
  - VR2 2k $\Omega$
  - VR3 5k $\Omega$
  - VR4 1k $\Omega$
- } wirewound trimmers

### Diodes

- D1 ZL10 1.5W, 10V Zener
- D2 IN4148 silicon

### Switches

- S1 D.P.D.T. toggle
- S2 S.P.S.T. pushbutton
- S3 S.P.D.T. toggle

### Miscellaneous

- M1 500 $\mu$ A f.s.d. moving coil meter (S.E.W. edge-wise type)
- SK1/PL1 Two pin DIN plug and socket
- SK2/PL2 Three pin DIN plug and socket
- LPI Miniature indicator lamp and holder (voltage to suit supply)
- Veroboard 2 $\frac{1}{2}$ in  $\times$  3 $\frac{1}{2}$ in  $\times$  0.15in matrix
- Diecast case 6 $\frac{1}{2}$ in  $\times$  4 $\frac{1}{2}$ in  $\times$  2 $\frac{1}{4}$ in
- Connecting wire, transducer connection wire—3 core plastics covered mains lead; supply connection wire—2 core plastics covered mains lead.
- 6B.A. fixings
- Foam rubber, paint and Letraset

The action of D2 provides the required circuit response to variation of VR1.

Switch S2 and resistor R2 provide a circuit voltage checking position that will indicate, by way of M1, when the battery voltage is too low to operate the circuit. Resistor R1 will be either 220 ohms or 2.2 kilohms to accommodate supplies of 11V to 18V or 18V to 50V d.c. respectively; LP1 will, of course, have to be the correct voltage for the supply.


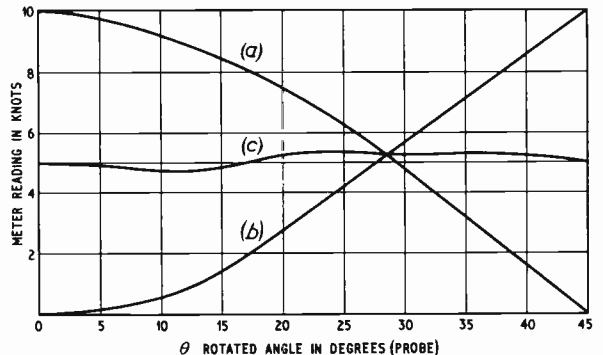


Fig. 2. Graph of probe rotation against meter reading (b) subtracted from the  $\text{Cos}^2\theta$  graph (a) to give the resultant curve (c). For an accurate instrument curve (c) should be a straight line

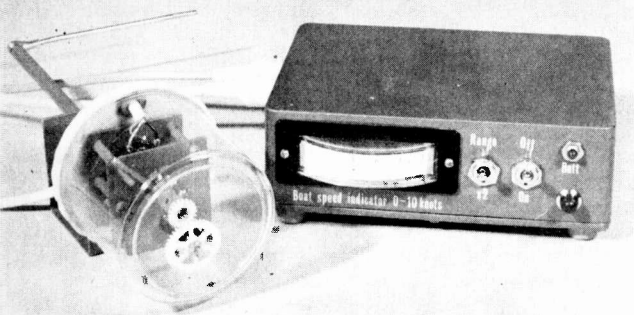

### TRANSDUCER CONSTRUCTION

The transducer must be constructed of materials that will not be affected by water; in the prototype brass was used throughout. The shaft is a model boat propeller shaft and the gears are nylon, 2 to 1 ratio, also supplied for model making. The torsion spring can be any  $\frac{1}{8}$  in diameter coil spring that is of fairly light construction. Particular attention should be paid to accuracy since any unnecessary friction or play in the unit will result in inaccurate and erratic readings when in use.

The gears should be arranged to mesh closely and there should be as little play in the potentiometer bearings as possible; because of this a metal encased potentiometer may prove best in this application—this can be sealed with epoxy resin or paint if necessary. Before using the transducer all surfaces should be protected with paint or varnish, the shaft and potentiometer bearing packed with grease and the container sealed with a rubber ring.

Details of the transducer are given in Fig. 3. Three  $\frac{1}{8}$  in diameter brass rods are used to position the two plates; one of these rods forms a locating pin to ensure correct orientation of the probe with respect to boat axis.

The other two pins form rotation limiters for the arm connected to VR1 and a spring anchoring point. The locating pin slides into a hole in the mounting bracket (shown in Fig. 3), that is fixed to the transom of the boat. The complete transducer can be lifted clear of the water, for breaching purposes or mooring, without completely removing the unit.

### TRANSDUCER ASSEMBLY

Assembly of the transducer may prove slightly tricky, but is fairly easy once the correct sequence is known. When all parts have been made to the details shown in Fig. 3 the three rods can be soldered or brazed to the lower plate—the one with no potentiometer mounting hole. The locating pin should be affixed so that its top end is about  $\frac{1}{16}$  in above the position of the upper plate—determined by the depth of VR1. The remaining two pins are mounted so that their lower end is flush with the underside of the lower plate.

Next, VR1 should be mounted on the upper plate approximately in the centre of the slightly elongated hole. It is not necessary to tighten the fixing fully at this stage since the horizontal position of VR1 will have to be adjusted. Fit the spacers over the pins and place the two plates together, holding them with the two screws and two further spacers; the case lid should not be included under the screw heads at this stage.

The next operation is to mount the small gear on the potentiometer using the spindle coupler. The shaft can then be inserted through the two plates and the larger gear attached by tapping the brass bush 4B.A. and screwing it to the spindle.


### SHAFT ALIGNMENT

The vertical position of the shaft can now be adjusted so that the two gears align—a small washer should be inserted under the large gear—the shaft is then soldered or brazed to the lower plate. The two screws can be removed and the case lid slid over the shaft and locating pin and the whole thing screwed together. The rotation limit arm is inserted so that with the arm touching the anti-clockwise limit pin, VR1 is turned so that it is a few degrees off its fully anti-clockwise position. VR1 can now be adjusted so that the two gears mesh correctly and its fixing tightened fully.


The torsion spring can now be fixed, the spindle revolved so that slight torsion is applied and, with the mounting bracket in place, the probe bolted in position. A washer should be included between the shaft and the probe and the probe fixed so that there is no vertical play on the spindle. The probe is made by hammering flat one end of a  $\frac{3}{16}$  in diameter brass rod, shaping and drilling the flattened end.

### INDICATOR CONSTRUCTION

The four resistors, the two diodes, D1, D2 and VR2, VR3 and VR4, are mounted on a small piece of Veroboard, as shown in Fig. 4. Veroboard is used as it provides good support to the components and is not badly affected by water, as some tag panels are.

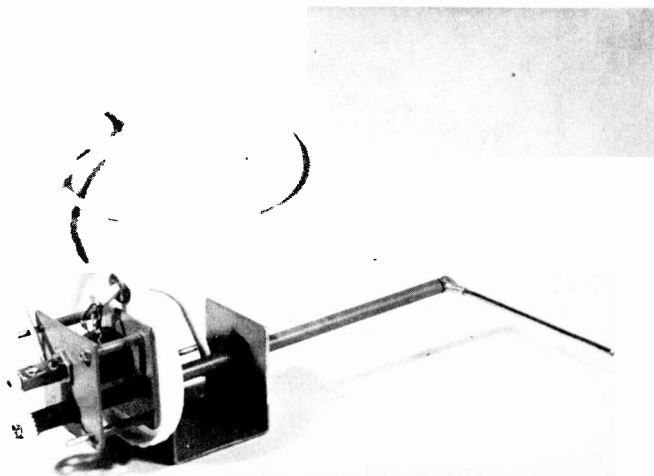


**Fig. 3a. Exploded view of the complete transducer, the torsion spring is shaped from a long tension spring and is affixed to one of the locating pins and the large gear wheel. It is under slight tension at all times.**

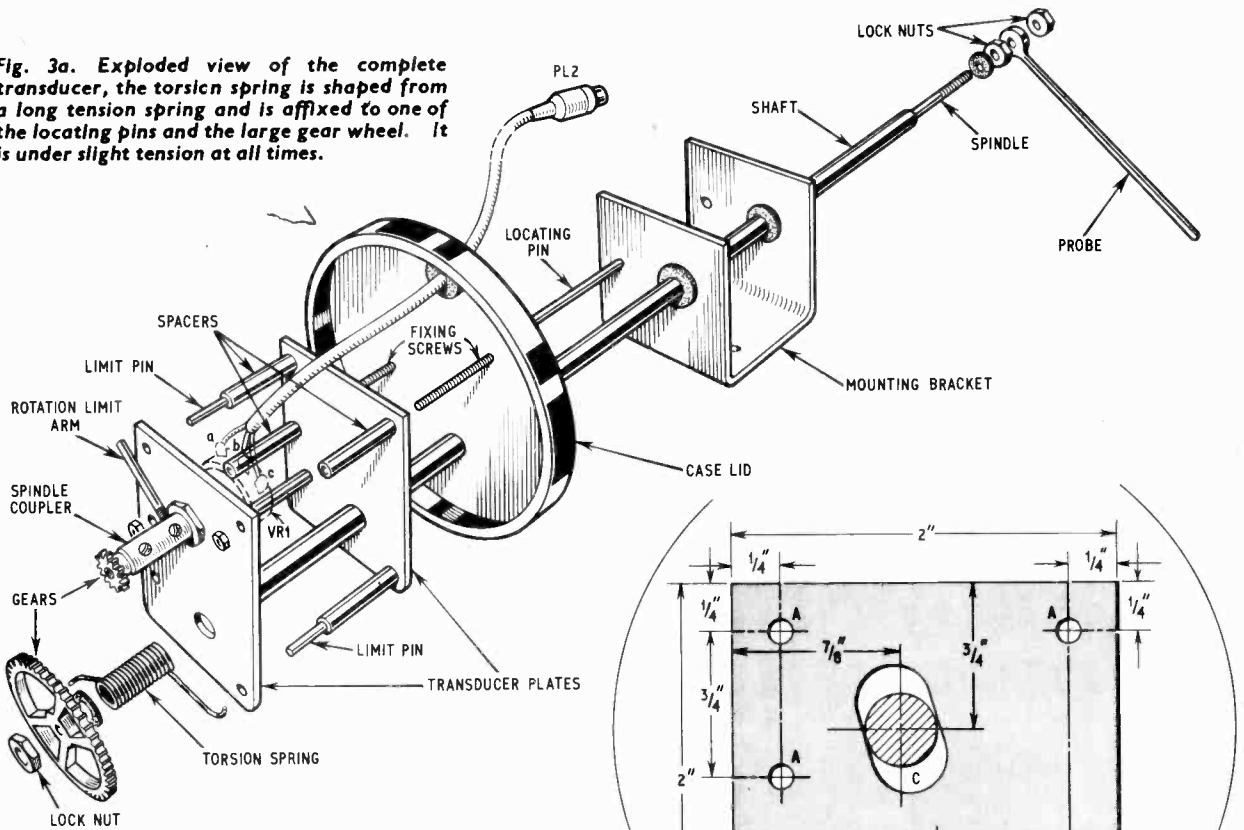

## TRANSUCER MATERIALS. . .

- 16 s.w.g. brass plate, 2in x 10in—for plates and bracket;  $\frac{1}{8}$ in diameter brass rod, 8in—for pins;  $\frac{3}{16}$ in diameter brass rod, 6in—for probe
- Model boat propeller shaft and spindle—see text
- Model makers' nylon gears 2 : 1 reduction with  $\frac{1}{4}$ in diameter brass bushes
- Spindle coupler  $\frac{3}{4}$ in long, for  $\frac{1}{4}$ in diameter spindles
- Spacers  $1\frac{1}{2}$ in x  $\frac{1}{4}$ in internal diameter, brass (4 off)
- 6B.A. screws  $1\frac{1}{2}$ in long (3 off) for fixing screws and rotation limit arm
- Case, 3in internal diameter plastics container with flat screw top
- Spring  $\frac{1}{2}$ in diameter tension spring of light construction at least  $1\frac{1}{2}$ in long.
- Grommets (3 off)—2 to suit shaft and 1 for connection lead; 4BA and 6BA nuts and washers



**Fig. 3b. Drilling details of the transducer plates. The distance between the two plates is determined by the depth of the potentiometer body—thus rod and spacer length will vary. Two plates are required and these should be drilled while clamped together. The elongated hole is only drilled through one plate. The position of the plates when mounted inside the case is indicated**

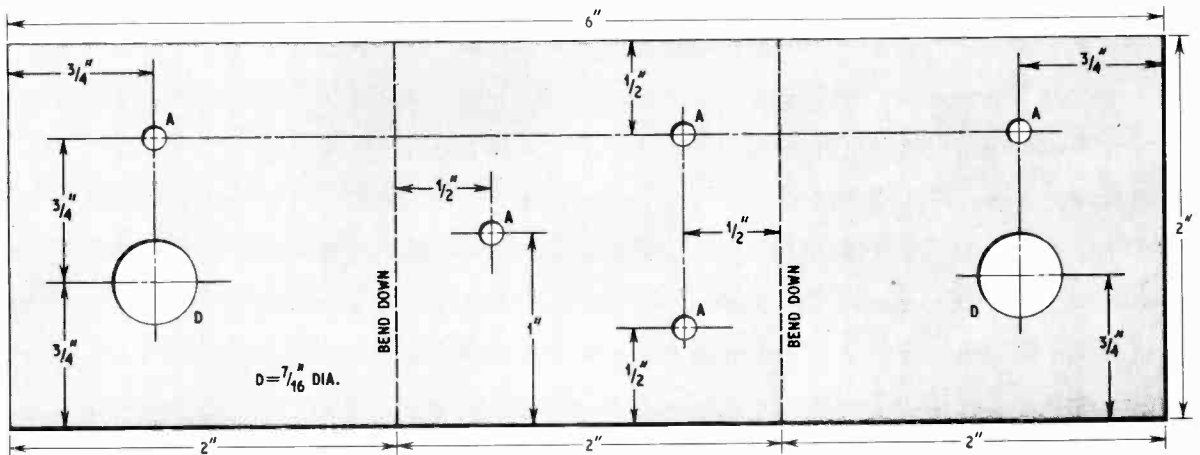

**Fig. 3c. Transducer mounting bracket details. Holes marked "D" must line up when the bracket is bent, their size will depend on the shaft and grommet diameter**

**Fig. 4. Veroboard layout and wiring diagram. The potentiometers may be designated as shown on the board, for easy identification during setting up and calibration**

**Fig. 5. Layout and wiring diagram of all components mounted in the die-cast case. The lid to the case forms the base of the unit and the view shown is of the underside with the base plate removed**

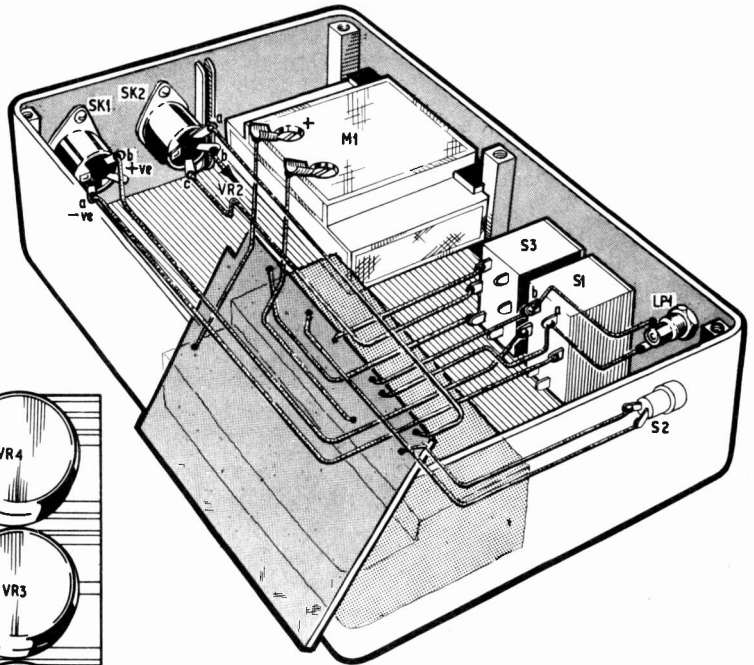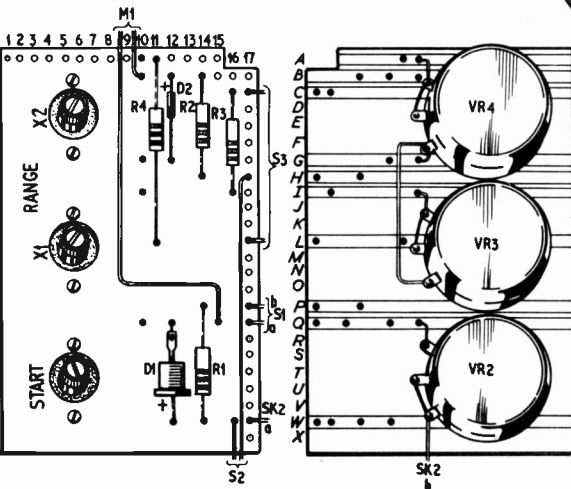

The remainder of the components are mounted directly to the die-cast case used to house the unit, see Fig. 5. This case should be carefully painted inside and out, after drilling, to prevent it being corroded by salt water; the base plate should be sealed with rubber strips. Sockets are provided for the leads to the transducer and the supply; these leads should be of good quality plastics insulated flex.

The meter is mounted on a rubber pad to provide some shock protection and prevent water from entering the case. The meter specified has no external apertures and the mechanical zero is adjusted through a hole in the top of the case which is plugged with a small piece of rubber when not in use. The Veroboard is mounted by sandwiching it between two pieces of foam rubber.

Layout and wiring of all components mounted in the indicator case is shown in Fig. 6. Internal batteries may be used if a larger housing is provided; in this case LP1 should be omitted to conserve the battery.

## INSTALLATION

The mounting bracket is fitted to the transom of the boat so that the lowest part of the bracket is about 1in above the highest possible water line. The bracket should be fitted well away from propellers on power craft or any obstruction that could interfere with the water flow.


The length of the shaft used will depend on the type and speed of the boat. The prototype, which was intended for a sailing dinghy, used a 9in shaft,

but power yachts may require a greater length to keep the probe below and the unit above, the water level at all speeds (the transducer body should also be clear of the water when going astern).

The indicator unit can be fitted in a convenient position and a good quality piece of 3 core mains lead made the correct length and wired to PL2. The transducer could be fitted through the bottom of larger craft but a special adaptor will have to be manufactured for this.
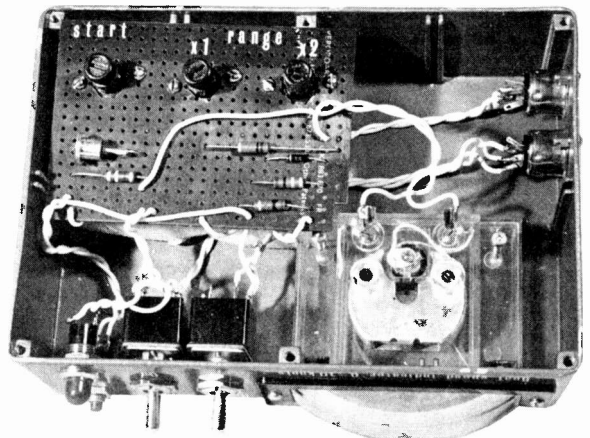
## CALIBRATION

The first step in calibration of the unit is to mark the correct supply level on M1. To do this a d.c. voltmeter is used to measure the voltage across D1; this voltage should be 10V—providing the battery is in good condition and D1 is functioning. Once this has been checked S2 can be depressed and the reading of M1 noted and marked on the scale or meter face; VR1 should be in circuit at its stationary position for this operation.




Switch S3 can then be set to the first range ( $\times 1$ ) and VR2 adjusted so that the meter shows a reading of  $10\mu\text{A}$ . Once this is done the meter can be zeroed when the circuit is energised, using the mechanical zero adjustment.

The maximum possible speed of the boat should be estimated and this speed marked at the full scale deflection point on M1. The scale should then be divided equally to indicate the intermediate speeds. With the probe rotated through 45 degrees, VR3 should be set to indicate full scale deflection on M1.
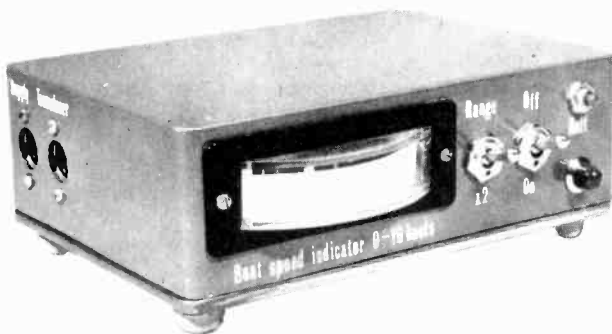
### INITIAL SETTING

Initial setting of VR3 can be made without installing the unit. Once this is completed the unit should be installed for further calibration in the boat in which it is to be used, in the correct position with the transducer lead of the required length.

Initial calibration is by means of variation of probe length and diameter (prototype used a 4in shaft of  $\frac{3}{16}$ in diameter brass) and torsion spring. Probe diameter may easily be increased by sliding a length of plastics flex insulation over it. Fine calibration may be effected by adjustment of VR3. The unit should be calibrated as near the maximum speed as possible, since this is the point at which the circuit is most accurate (refer to Fig. 2).




There are two ways of speed calibrating the unit: by comparison with another speed indicator or by timing the boat over a measured distance. If the second method is used the measured distance should be as large as practicable and the boat speed held constant by means of the indicator, any error can then be adjusted after a second run in the opposite direction.

To calibrate the times 2 range it is only necessary to hold the probe in such a position that half full scale deflection is indicated with S3 in the  $\times 1$  position; then switch S3 to  $\times 2$  (with the probe in the same position) and adjust VR4 to give full scale deflection on M1. When this has been done the probe fixing can be soldered over, to protect it and prevent it becoming corroded, and finally painted.

Designations may then be added to the unit as required, using Letraset, and given a coat of clear varnish to protect them. The unit is then ready for use.

If it is found that the meter is too sensitive to slight variations in speed or that the needle tends to flicker in use, the movement can be damped by placing a 2,000 $\mu\text{F}$  15V electrolytic capacitor directly across the meter terminals—observing polarity. ★

# MAY '71

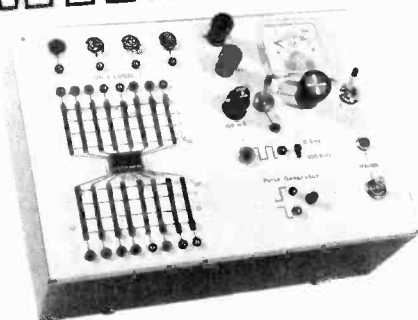

## DIGITAL INTEGRATED CIRCUIT TESTER

Testing a digital i.c. package can be a time consuming task. With this tester TTL, DTL and RTL devices can be rapidly checked for correct logic functioning with a visual go no-go readout.

## MAGNETIC FISH BITE INDICATOR

Independent of the rod and with no complicated line linkage, this unit provides an audible indication when a fish bites.

Utilising a simple magnetic reed switch it provides an ideal electronic overseer for unattended rods.

## WINDSCREEN WASHER TIMER

A simple unit for holding on an electric windscreen washer for a pre-set time interval. May also be used as a short interval timer.

PRACTICAL  
**ELECTRONICS**

May issue on sale  
FRIDAY APRIL 16  
Price 20p (4s)



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merit.

## DIGITAL DICE

PERHAPS your readers would be interested in the following circuit for an Electronic Dice.

The circuit is basically three binary stages with feed-back to give a count of six, being driven at high frequency by a free running multivibrator. When the count is stopped by pressing the display button S1 the output of the six counter is fed via gates to light lamps LPI to LP6, giving a display in the familiar dice combinations, i.e. with the centre lamp only lit for a "one", the six outer lamps for a "six", etc. The dice requires only four decoding circuits;

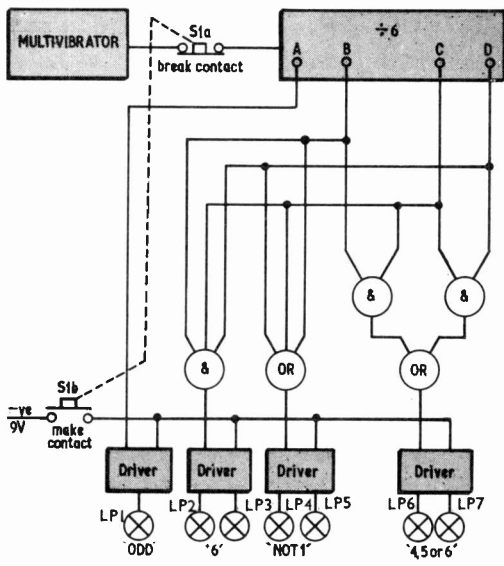


Fig. 1. Block diagram of the electronic dice

the first of these decides "even or odd"—if the count is odd only the centre lamp lights. The next gate decides "not one" which lights two diagonally opposite lamps (except during a one). A third gating circuit decides four, five or six and lights the two remaining diagonally opposite bulbs on these counts. The final gate decides "six" and lights the two remaining bulbs on this count. A little thought will show that these combinations will automatically light the proper number of bulbs in the correct pattern for each dice position. The block schematic diagram of the dice is shown in Fig. 1; Figs. 2, 3, 4 and 5 show the sections of circuitry, Fig. 2 being the driving multivibrator; Fig. 3 is the divide by 6 counter; Fig. 4 shows the five gates that together form the three gating circuits and Fig. 5 shows the lamp driver circuits.

The display panel is made up of a square of holes drilled in the positions shown in Fig. 6. A piece of coloured translucent perspex is fitted over a blanking panel, so that only the illuminated lamps can be seen as spots of light on the perspex.

If required, the dice may be built up as a double unit in which case the divider board, gates and lamp display should be duplicated and the second divider board input driven from point "D" on the first divider board; this ensures independent displays on the two dice.

The circuit may be powered either by a nine volt dry battery or by a d.c. nine volt, one amp, mains power supply. The mains power supply is preferable due to the current drain of the lamp display.

J. D. CROFT,

Warrington, Lancashire.

Count	Output from ÷ counter				Binary
	A	B	C	D	
1	NEG	POS	POS	POS	0 0 0
2	POS	NEG	POS	POS	0 0 1
3	NEG	POS	NEG	POS	0 1 0
4	POS	NEG	NEG	POS	0 1 1
5	NEG	POS	NEG	NEG	1 1 0
6	POS	NEG	NEG	NEG	1 1 1

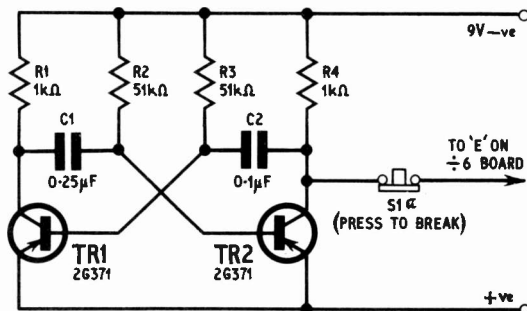


Fig. 2. Multivibrator driver for the dice



Fig. 3. The divide by six counter

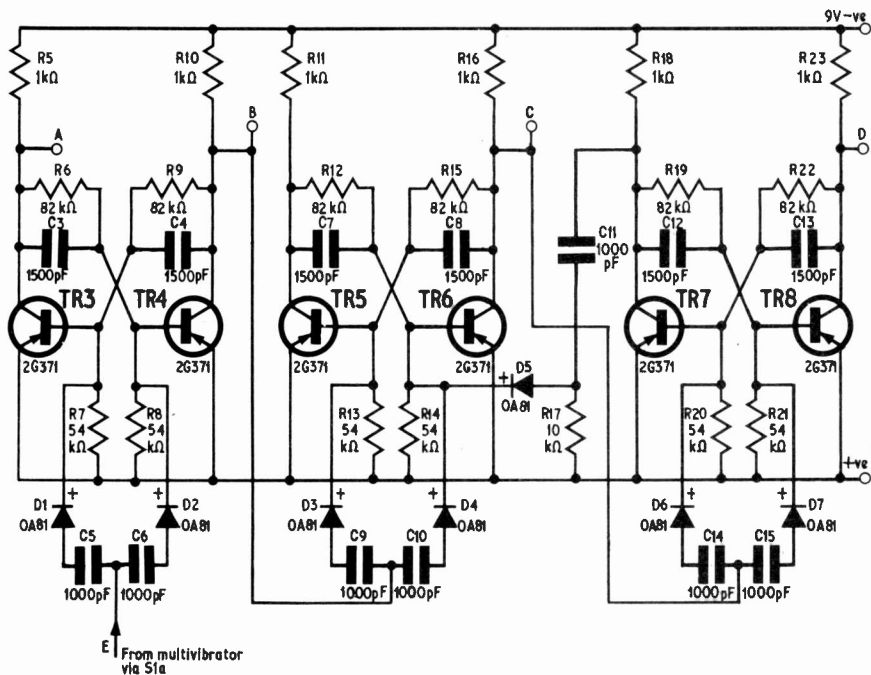


Fig. 4. Gate circuits used in the dice


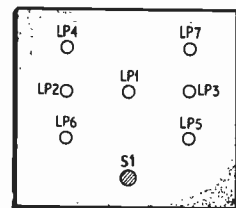
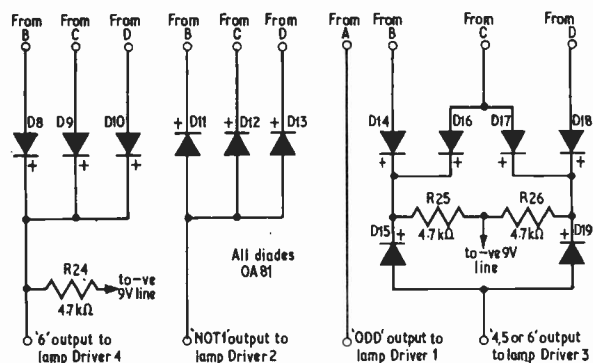


Fig. 6. Lamp and switch positions

Fig. 5. Lamp driver circuits; all lamps 6.3V 0.04A

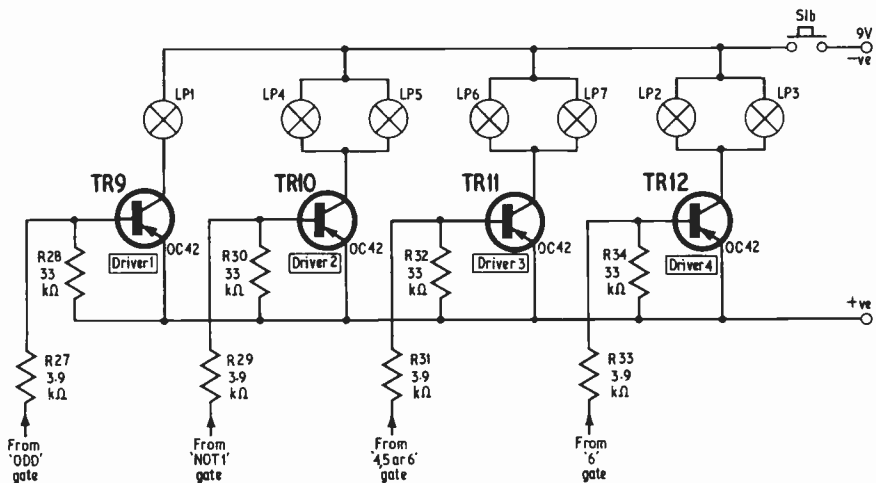

# DIGITAL TO ANALOGUE CONVERSION

It is often required to obtain a staircase waveform output from 1, 2, 4, 8 counter or logic outputs. The methods usually used are combinations of integrators and diode pumps of various descriptions. The circuit used here, however, is purely digital and the minimum of design application and components are required. The components used may be four transistors, used as single input gates, four Zener diodes and a load resistor. All of the components could probably be incorporated economically on a single i.c.

For operation of this circuit, I will refer to the circuit diagram (Fig. 1) where the resistors R1, R2, R3, and R4 ensure that the transistors TR1, TR2, TR3 and TR4 are saturated when the inputs 1, 2, 4, and 8 are at logic "1", (which must be 10V or more in this circuit).

In "0" output condition the transistors TR1, TR2 and TR3 and TR4 will all be saturated and the output will be at a level of  $V_{ce(sat)} \times 4$  above zero volts or ground, this gives a level of approximately 1.2V. Now assume input 1 is taken to zero volts or ground, TR1 will thus switch off; the voltage across which will rise until D1 Zener diode break-down level is reached. This break-down voltage level is selected to be 1 volt plus the  $V_{ce(sat)}$  of TR1, this will give a step of 1 volt at the output. The voltage  $1 \times V_{ce(sat)}$  is added to each Zener voltage to maintain linear 1 volt steps at the output, as without taking this into account the voltage output will vary depending on the number of transistors saturated or not.

Assume the inputs to be obtained from a binary counter then input 2 will become zero and input 1 will

go to a positive voltage. Thus TR1 will saturate shorting out Zener diode D1, but TR2 is now switched off—the voltage across which rises to the Zener break-down voltage of D2. This has been selected as 2 volts plus  $V_{ce(sat)}$  of TR2 which gives an output level of 2 volts above the zero level of  $V_{ce(sat)} \times 4$ .

This is continued for inputs 1 and 2 where both TR1 and TR2 are switched off which allows the output to rise by 3 volts i.e., D1 plus D2, and like-wise all the way along the chain of a 1, 2, 4, 8 counter or other input.

The output will start at  $V_{ce(sat)} \times 4$  (which is zero) and ascend in one volt steps until the output voltage reaches ten volts, our count of ten plus  $V_{ce(sat)} \times 4$ , this gives a total of 11.2 volts, and it goes without saying the steps may ascend in level by reversing the logic input levels.

The beauty of this circuit is that it is entirely independent of frequency and voltage levels, providing  $V_{CC}$  does not fall to below the sum of the total Zener voltage levels, i.e.  $V_{CC}$  may be 100 volts (if the components will take it) and the output levels obtained will not vary considerably from those when  $V_{CC}$  was at 12 volts. So it can be seen that the only design consideration is one of upper operating frequency which is dependent upon the components used and not so much the circuit; by selecting the appropriate Zener voltage levels this circuit may be used on various coded outputs quite easily.

D. W. Lloyd,  
Stotfold, Herts.

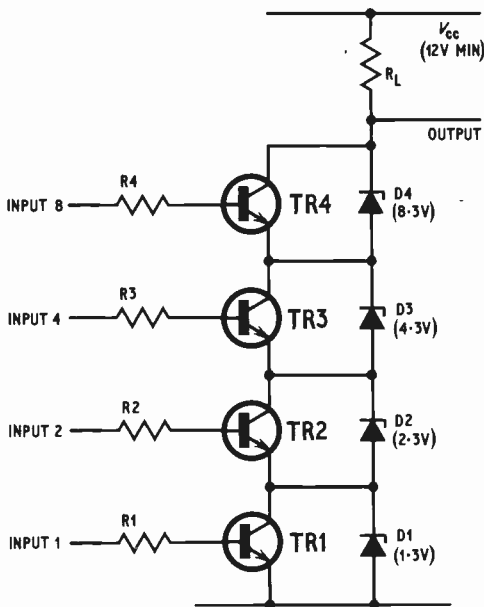


Fig. 1.


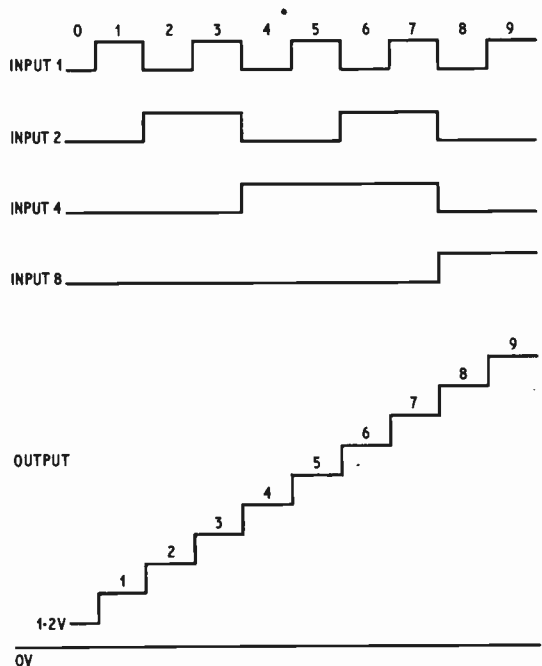


Fig. 2.
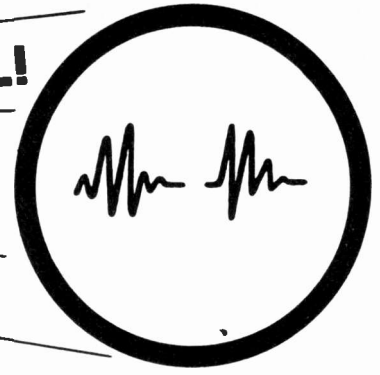
# LOOK!


**PRACTICAL!**  
**VISUAL!**  
**EXCITING!**



a new 4-way method of mastering  
**ELECTRONICS**  
by *doing* — and — *seeing* . . .


**1** ▶ **OWN and HANDLE** a

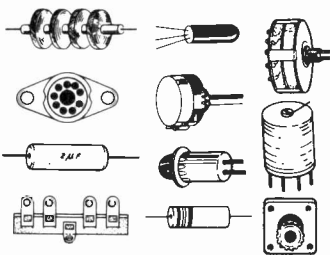complete range of present-day **ELECTRONIC PARTS** and **COMPONENTS**



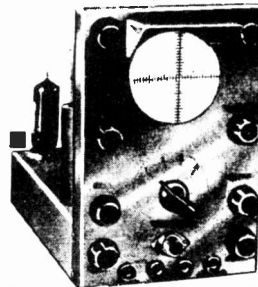
**2** ▶ **BUILD and USE**

a modern and professional **CATHODE RAY OSCILLOSCOPE**



**3** ▶ **READ and DRAW** and

**UNDERSTAND** **CIRCUIT DIAGRAMS**

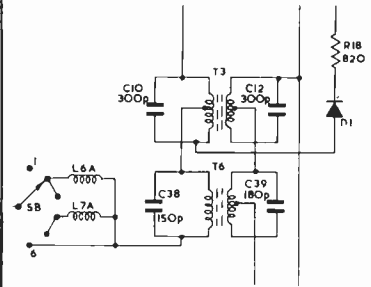

**4** ▶ **CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK . . . INCLUDING . . .**

- VALVE EXPERIMENTS
- PHOTO ELECTRIC CIRCUIT
- A.C. EXPERIMENTS
- TRANSISTOR EXPERIMENTS
- COMPUTER CIRCUIT
- D.C. EXPERIMENTS
- AMPLIFIERS
- BASIC RADIO RECEIVER
- SIMPLE COUNTER
- OSCILLATORS
- ELECTRONIC SWITCH
- TIME DELAY CIRCUIT
- SIGNAL TRACER
- SIMPLE TRANSMITTER
- SERVICING PROCEDURES

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of Electronic equipment, Radio and TV receivers, etc.

**FREE** POST NOW  
for  
BROCHURE

or write if you prefer not to cut page

To: **BRITISH NATIONAL RADIO SCHOOL, READING, BERKS.** Please send your free Brochure, without obligation, to: we do not employ representatives

NAME..... BLOCK CAPS

ADDRESS..... PLEASE P.E. 4

# G. F. MILWARD

Mail Orders: DRAYTON BASSETT, TAMWORTH, STAFFS

## ELECTRONIC COMPONENTS

Wholesale/Retail :

369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

**4,000,000 DIODES**  
**SILICON · GERMANIUM · ZENER**  
 LOTS OF 100,000 — **£150**  
 10,000 — **£20**  
 1,000 — **£3**  
 500 — **£2**

**1,000,000**  
**GERMANIUM TRANSISTORS**  
 LOTS OF 100,000 — **£250**  
 10,000 — **£30**  
 1,000 — **£3.50**  
 500 — **£2**

**SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! !**

**RESISTORS, 1/2 Watt**  
 assorted 100 50p  
 Wire-wound 1 to 3W 20 50p  
 5 to 7W 15 50p  
 10W 10 50p  
 Multi-tapped 12 50p  
**PAPER CONDENSERS**  
 TV types 50 50p  
 Miniature 100 50p  
**ELECTROLYTIC CONDENSERS**  
 Suitable for Mains  
 Radio/TV 10 50p  
 Transistor types 20 50p  
 Mixed (both types) 15 50p  
**POLYSTYRENE**  
 CONDENSERS 100 50p  
**MULLARD POLYESTER**  
 CONDENSERS 50 50p  
**SILVER MICA**  
 WIRE-WOUND 3-Watt  
 SLIDERS 15 50p  
**VOLUME CONTROLS**  
 Assorted 5 50p  
**NUTS AND BOLTS.**  
 Mixed length/type  
 8 B.A. 100 50p  
 6 B.A. 100 50p  
 4 B.A. 100 50p  
 2 B.A. 100 50p  
**METAL SPEAKER GRILLES**  
 7/16in 3/16in 6 50p  
**EARPIECES, MAGNETIC**  
 No Plug 6 50p  
 2.5mm Plug 4 50p  
 3.5mm Plug 4 50p  
**500 MICRO-AMP LEVEL**  
 METERS 1 50p  
**VEROBOARD. TRIAL**  
**PACK 5 BOARDS**  
 + CUTTER 50p

**TRANSISTORS**  
 P.N.P. Untested but  
 mainly O.K. 50 50p  
 N.P.N. Untested but  
 mainly O.K. 50 50p  
 OCP71 equivalent 5 50p  
 Light-sensitive Diodes 10 50p  
 (These produce up to 1mA from light)  
 OC44 Mullard 1st grade 4 50p  
 OC45 Mullard Boxed 4 50p  
 2G378 Output, Marked 4 50p  
 2G371 Driver, Marked 4 50p  
 ASY22, Marked 5 50p  
 BY127 Rectifiers 4 50p  
 IN4007 Rectifiers  
 (1200V peak) 4 50p  
 STC3/4 Rectifiers 6 50p  
 DIODES (OA81 & OA91) 40 50p  
**WIRE**  
 Solid Core, Insulated 100yds 50p  
 Stranded ditto 50yds 50p  
**SOLAR CELLS**  
 Large Selenium 2 50p  
 Small 3 50p  
 (6 cells will power a  
 Micromatic radio)  
**CO-AXIAL CABLE**  
 Semi Air-spaced 15yds 50p  
**CRYSTAL TAPE**  
 RECORDER MIKES 1 50p  
 CRYSTAL EARPIECES 2 50p  
 3.5mm Plug  
**TRANSISTORISED Signal**  
 Injector 1 50p  
**TRANSISTORISED Signal**  
 Tracer 1 50p  
**TRANSISTORISED CAR**  
**REV. COUNTER KIT**  
 (Needs 1mA meter as  
 indicator) 1 50p

**SINCLAIR AMPLIFIERS AND SPEAKERS: Complete range in stock. All at 10% discount on list.**

### VEROBOARD

2 1/2in 1in 0.15in 6p 5in 3 1/2in 0.15in 28p 3 1/2in 3 1/2in 0.1in 24p  
 3 1/2in 2 1/2in 0.15in 16p 17in 2 1/2in 0.15in 55p 5in 2 1/2in 0.1in 23p  
 3 1/2in 3 1/2in 0.15in 20p 17in 3 1/2in 0.15in 74p 5in 3 1/2in 0.1in 28p  
 5in 2 1/2in 0.15in 20p 3 1/2in 2 1/2in 0.1in 21p  
 Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0.1 or 0.15)  
 36 for 18p. Special Offer Pack consisting of 5 2 1/2in 1in boards and a  
 Spot Face Cutter—50p.

### RECORD PLAYER CARTRIDGES. Well below normal prices!

G90 Magnetic Stereo Cartridges, Diamond Needle, 6mV output, £4.  
 ACOS GP 67/2 (Mono, Crystal) 75p. ACOS GP 91/3 (Compatible,  
 Crystal) £1. ACOS GP 93/1 (Stereo, Crystal, Sapphire) £1.25. ACOS  
 GP 93/1D (Stereo, Crystal, Diamond) £1.63. ACOS GP 94/1 (Stereo,  
 Ceramic, Sapphire) £1.50. ACOS GP 94/1D (Stereo, Ceramic, Diamond)  
 £1.88. ACOS GP 95/1 (Stereo, Crystal with two L.P./Stereo needles)  
 £1.25.

**TRANSISTORISED FLUORESCENT LIGHTS, 12 volt. All with reverse polarity protection. 8 watt type with reflector, suitable for tents, etc., £3. Postage/Packing 25p. 15 watt type, batten fitting for caravans £4. Postage/Packing 25p. 13 watt type, batten with switch. 22in 2in 1in £5. Postage/Packing 25p. THESE CAN BE SENT ON APPROVAL AGAINST FULL PAYMENT.**

### MULLARD POLYESTER CONDENSERS

1,000pf, 1,200pf, 1,500pf, 1,800pf, 2,200pf, 15p per dozen (all 400V working). 0.15µf, 0.22µf, 0.27µf, 30p per dozen (all 160V working). 25% discount for lots of 100 of any one type.

### RESISTORS

1/2 and 1 watt. Most values in stock. 50p per 100. 10p per dozen of any one value. WIRE-WOUND MAINS DROPPERS. Hundreds of values from 0.7 ohm upwards. 1 watt to 50 watts. A large percentage of these are multi-tapped droppers for radio/television. Owing to the huge variety these can only be offered "assorted" at 50p per dozen.

### SILVER MICA/CERAMIC/POLYSTYRENE CONDENSERS

Large range in stock, 75p per 100 of any one value. 15p per doz.

**RECORDING TAPE BARGAIN! The very best British Made low-noise high-quality Tape! 5in Standard 38p. Long-play 45p. 5 1/2in Standard 45p. Long-play 60p. 7in Standard 60p. Long-play 82p. We are getting a fantastic number of repeat orders for this tape. Might we suggest that you order now whilst we still have a good stock at these low prices!**

### £5 WORTH OF COMPONENTS FREE ! ! ! !

Thinking of learning another language? If so apply to us for details of LINGUAPHONE courses. We will GIVE you £5 worth of components of your selection quite free of charge when you purchase a course ! ! ! !

### MULLARD "UNILEX" AMPLIFIERS

In our opinion these units are the best value for money ever offered. A complete stereo unit consisting of Control unit, Pre-amplifier, Two Main Amplifiers and Power Pack complete the ready for use—NO extra components to buy—yours for £15. (Normal retail price is £16.50.)

**GARRARD SP 25 UNITS** also offered at a discount. Our price only £12.50. Postage 50p.

### TRANSISTOR RADIOS

Once again we have a supply of these excellent radios which offer superb quality sound and excellent sensitivity. They are packed in a colourful presentation box complete with battery, earpiece and carrying case. Each one is guaranteed. You would expect to pay at least £5—but our price due to bulk purchase is only £1.88.

**G. F. MILWARD, DRAYTON BASSETT, TAMWORTH, STAFFS. Postage (minimum) per order 10p**

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## LOUDSPEAKERS AND ENCLOSURES

An increasing number of cost conscious hi fi enthusiasts are home constructing loudspeaker systems from the expanding range of multi-unit kits and individual loudspeakers now available.

One of these multi-unit kits is the Peerless 20-3 from P. F. & A. R. Helme. This is a 3-way system consisting of a low frequency "woofer" loudspeaker with rubber roll surround, a mid-range speaker, a "tweeter" high frequency speaker and a printed circuit board crossover unit.

Recommended for amplifiers of 10 to 40 watts, the maximum power input of the system is 40 watts. The frequency range is claimed to be 40 to 20,000Hz and the crossover frequencies are 1,500 and 6,000Hz. All speakers have voice coils wound on an aluminium coil former and have standard impedances of 4, 8 or 16 ohms.

The Peerless 20-3 kit costs approximately £18.87 and full details will be supplied by A. F. & A. R. Helme, Summerbridge, Harrogate, Yorkshire, HG3 4DR.

For those readers who do not feel sufficiently proficient to make their own enclosures, Messrs. Omar Skinner & Sons produce ready built enclosures to makers' specifications for the more popular systems.

The enclosures are soundly constructed and available in a variety of finishes. The baffle boards are cut to order and they claim they can supply an enclosure for every need.

Our photograph shows the Omar Skinner enclosure for the four loudspeaker EMI 750 kit. The 750 kit consists of a bass, mid-range and two treble speakers, which together are capable of handling 20 watts and cover the frequency range of approximately 30-20,000Hz. A crossover unit with a choice of switching frequencies, wiring harness and full instructions is included and the complete EMI 750 kit costs £27.50.

Details of enclosures may be obtained from Messrs. Omar Skinner & Sons, Warfield Park

Workshops, Warfield Park, Bracknell, Berkshire, and enquiries for information on EMI loudspeaker kits and enclosures should be addressed to EMI Sound Products Ltd., Blythe Road, Hayes, Middx.

## TOOL KITS

During the last few years manufacturers have been gradually gearing themselves to continental specifications and component practices when designing equipment. The result of this gradual changeover has meant that numerous pieces of equipment have contained both U.K. and continental components, i.e. Phillips, Allen, and standard screws.

One of the problems encountered by this situation is the lack of necessary tools when carrying out service repair work. **Special Products Distributors** seem to have recognised this problem and are now introducing the well-known Xcelite tools from America to the British market.

The first tools to be marketed are a 19-piece screwdriver kit, 14-piece socket set and a 5-piece screwdriver kit.

The XL-70 19-piece kit contains a selection of Allen keys, slotted and Phillips screwdrivers, reversible ratchet and extension handle. The ratchet can be attached to the extension handle for added torque if required. This kit is particularly useful for television service engineers.

The 1001 14-piece socket set includes sockets from  $\frac{1}{8}$ in. to  $\frac{1}{2}$ in., 2in. extension, reversible ratchet and extension handle.

Included amongst the sockets are two 10-point sockets,  $\frac{1}{4}$ in. and  $\frac{3}{8}$ in., which are dual purpose to fit both square and hexagonal nuts. The reversible ratchet in this kit is fully enclosed to keep out dirt and grit.

The XL75 5-piece kit is contained in a plastics wallet and is a small set of slotted and Phillips screwdrivers with an offset ratchet handle, again extremely useful for working in awkward and confined spaces.




The XL70 screwdriver kit costs £6.25, the 1001 socket set costs £7.18 and the XL75 costs £2.10.

Both the XL70 and the 1001 kits are housed in moulded high impact plastics cases. Full particulars of these tools are available from Special Products Distributors Ltd., 81 Piccadilly, London, W1V 0HL.




Peerless 20-3 kit from P. F. & A. R. Helme

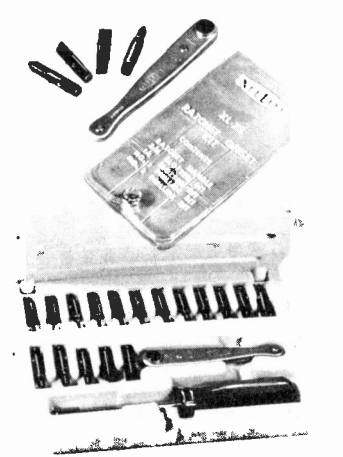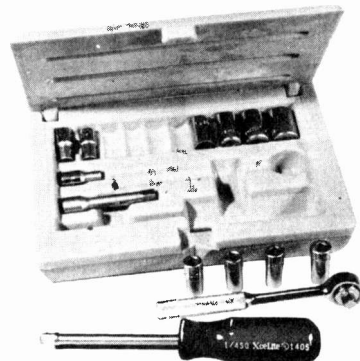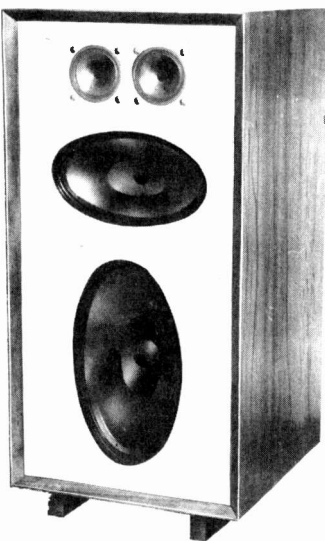EMI 750 kit housed in an Omar Skinner enclosure



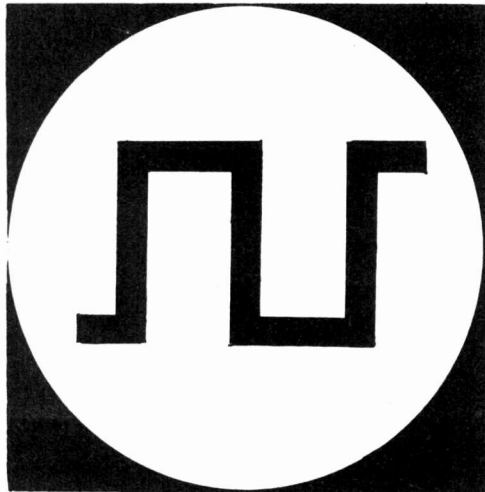The 1001, XL75 and XL70 kits marketed by Special Products Distributors



# DOORBELL YODELLER

K. J. Turvey, B.Sc.(Eng.)

**T**his article describes the construction of a completely electronic door bell which is simple, cheap, and does not require accurate adjustment. The rhythm and melody are continually changing so that each time the bell push is depressed a different sound is produced.

## CIRCUIT BLOCKS

In the block diagram of the unit shown in Fig. 1, the 250Hz multivibrator produces the basic note. The base resistors controlling the frequency are divided into two so that the two low frequency (1Hz) multivibrator circuits can short circuit the upper resistors. A total of four notes is thus obtained using only three switching circuits.

Since the multivibrator circuits run asynchronously the rhythm will be continually changing which means that a different tune will be obtained each time the bell push S1 is depressed.

The output from the 250Hz multivibrator is fed via an AND gate to amplifier A2 to drive the loudspeaker LS1. The signal is allowed through the gate when the monostable is pulsed, the duration of which may be adjusted between 0.5 and 12 seconds.

A buffer amplifier, A1, precedes the monostable stage and provides the triggering action when the bell push is used.

## DETAILED OPERATION

Transistors TR3 and TR4 in Fig. 2 form the main astable circuit which provides low frequency calculated by  $1/0.7[C_3(R_6 + R_7) + C_4(R_8 + R_9)]Hz$ .

In order that diodes D1 and D2 effectively short circuit R6 and R8, R7 must be greater than R6 and R9 must be greater than R8.

TR5 and TR6 form another astable circuit working at a very low frequency of about 1Hz. With  $R_{12} = R_{13}$  and  $C_5 = C_6$  the frequency is given by  $1/1.4 C_5 R_{12} Hz$ .

When TR5 is hard on, the collector is almost zero volts and diode D2 is back biased since the junction of R8 and R9 is always positive. When TR5 is cut off the collector is +6V and D2 is forward biased which effectively short circuits R8 and consequently changes the operating frequency of the 250Hz astable.

The action of TR1/TR2 astable circuit is identical to this but is applied to D1.

## GATING THE OUTPUT

The output is taken from TR3 collector and gated at the input of the amplifier A2 by diode D3. With the bell switch not made TR11 in the monostable circuit will be normally hard on and thus the collector will be nearly at zero volts. Here the diode D4 is forward biased and the junction of R28 and R29 will be held at zero volts irrespective of the input to D3.

TR9 is held on by the positive voltage appearing at the junction of R19 and the lamp. When the bell push is depressed the base of TR9 is brought to nearly zero volts so that it switches off.

With TR9 cut off, the collector will change from zero volts to +6V. This positive going voltage turns TR10 on via C10 and R23 thus triggering the monostable action of TR10 and TR11. TR11 is turned off and the collector changes to +6V which reverse biases diode D4, so allowing D3 to pass the output of TR3 to the amplifier A2.

Irrespective of whether the bell push is maintained depressed or not the monostable action will end after a time given by  $0.7 \times C_{11} \times (VR1 + R_{25})$ . In this period a short burst of notes will be obtained. With VR1 set to zero the duration will be approximately 0.5 seconds. Set to maximum resistance it will be about 12 seconds.

R21 is included to reduce the voltage to the astable and monostable circuits so that 6V working capacitors can be used. C9 decouples the astable circuits.

## POWER SUPPLY

The circuit diagram of the power supply is shown in Fig. 3. Here the total current required will depend, in the main, on the rating of LP1.

If a Friedland bell push is used the lamp voltage will probably be 8-15 volts. Thus a 12 volt transformer would be suitable.

The prototype was powered from a 12-0-12 volt transformer and using a Friedland Type 'A' lamp the following measurements were made.

Normal current	150 mA
Bell operating	500 mA
Bell push held depressed	1.2 amps

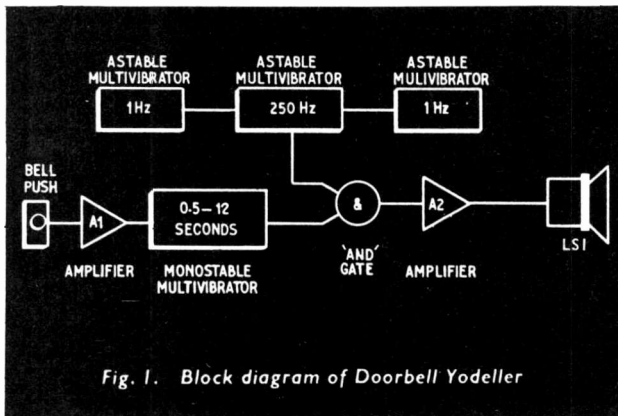


Fig. 1. Block diagram of Doorbell Yodeller



# Components . . .

## Resistors

R1 1k $\Omega$	R11 1k $\Omega$	R21 220 $\Omega$ $\frac{1}{2}$ W
R2 22k $\Omega$	R12 22k $\Omega$	R22 1k $\Omega$
R3 22k $\Omega$	R13 22k $\Omega$	R23 100k $\Omega$
R4 1k $\Omega$	R14 1k $\Omega$	R24 1.8k $\Omega$
R5 3.3k $\Omega$	R15 6.8k $\Omega$	R25 2.2k $\Omega$
R6 22k $\Omega$	R16 150 $\Omega$	R26 22k $\Omega$
R7 33k $\Omega$	R17 10 $\Omega$ 2W	R27 1.8k $\Omega$
R8 27k $\Omega$	R18 15 $\Omega$ 2W	R28 1k $\Omega$
R9 33k $\Omega$	R19 15 $\Omega$ 10W	R29 1k $\Omega$
R10 3.3k $\Omega$	R20 5.6k $\Omega$	

All 10%,  $\frac{1}{4}$ W carbon except where stated

## Potentiometers

VR1 47k $\Omega$ Vertical preset
VR2 25 $\Omega$ Preset

## Transformer

T1 12V 2A centre tapped (Douglas MT71)

## Capacitors

C1 32 $\mu$ F elect. 6V	C7 250 $\mu$ F elect. 15V
C2 32 $\mu$ F elect. 6V	C8 250 $\mu$ F elect. 15V
C3 0.01 $\mu$ F	C9 250 $\mu$ F elect. 6V
C4 0.01 $\mu$ F	C10 0.1 $\mu$ F
C5 32 $\mu$ F elect. 6V	C11 250 $\mu$ F 6V
C6 32 $\mu$ F elect. 6V	C12 5,000 $\mu$ F elect. 15V

## Transistors

TR1-TR7 BC108 (7 off)  
 TR8, OC28  
 TR9-TR11 BC108 (3 off)

## Diodes

D1-D4 OA90 (4 off)      D5-D8 RS50AF (4 off)

## Miscellaneous

S1 (see text), LS1 3-15 ohms loudspeaker,  
 Veroboard 0.1in matrix  $4\frac{1}{2}$ in  $\times$  6in and  $2\frac{1}{2}$ in  $\times$  5in.



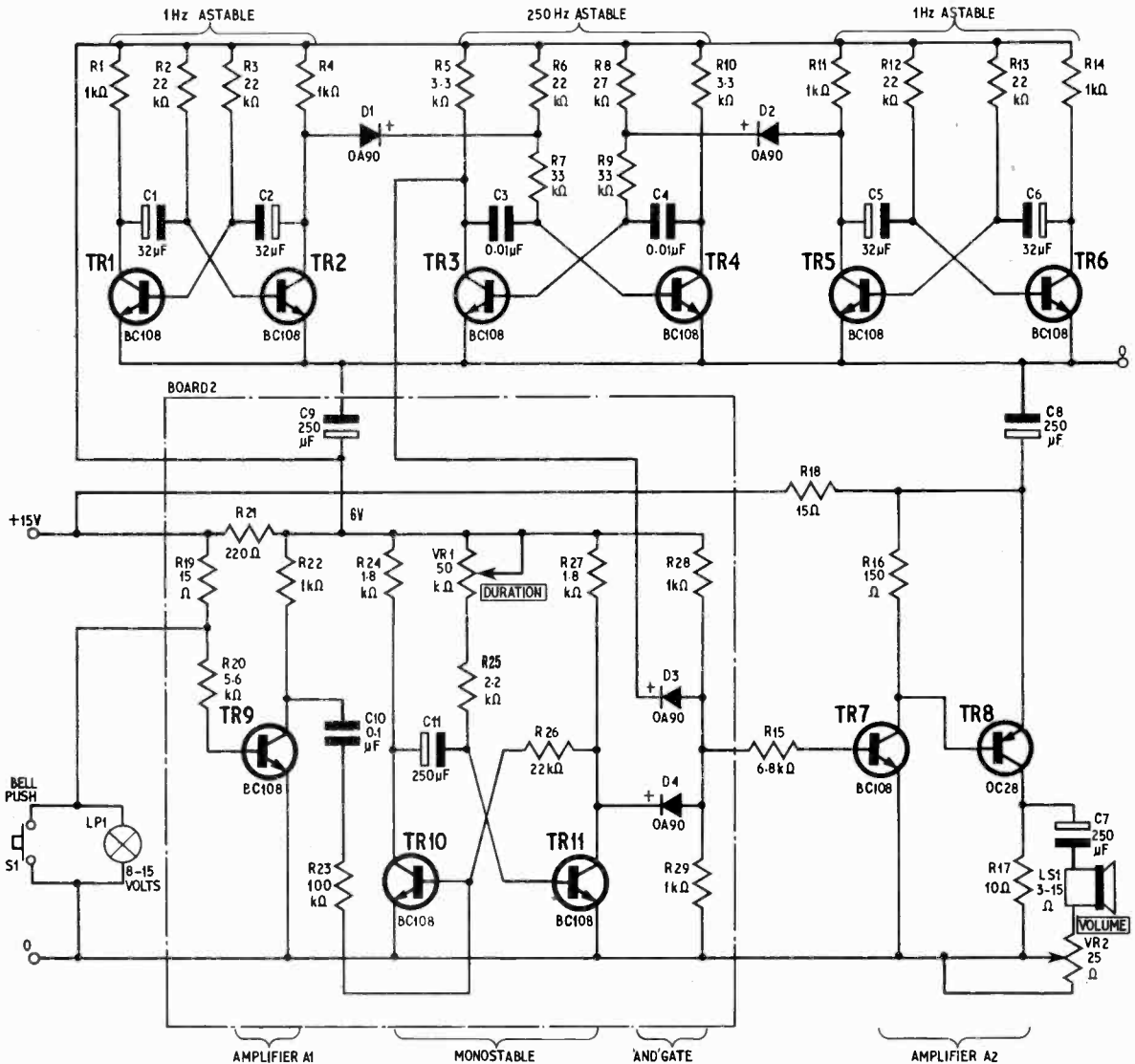
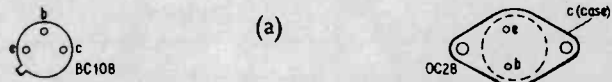


Fig. 2. Circuit diagram of Doorbell Yodeller

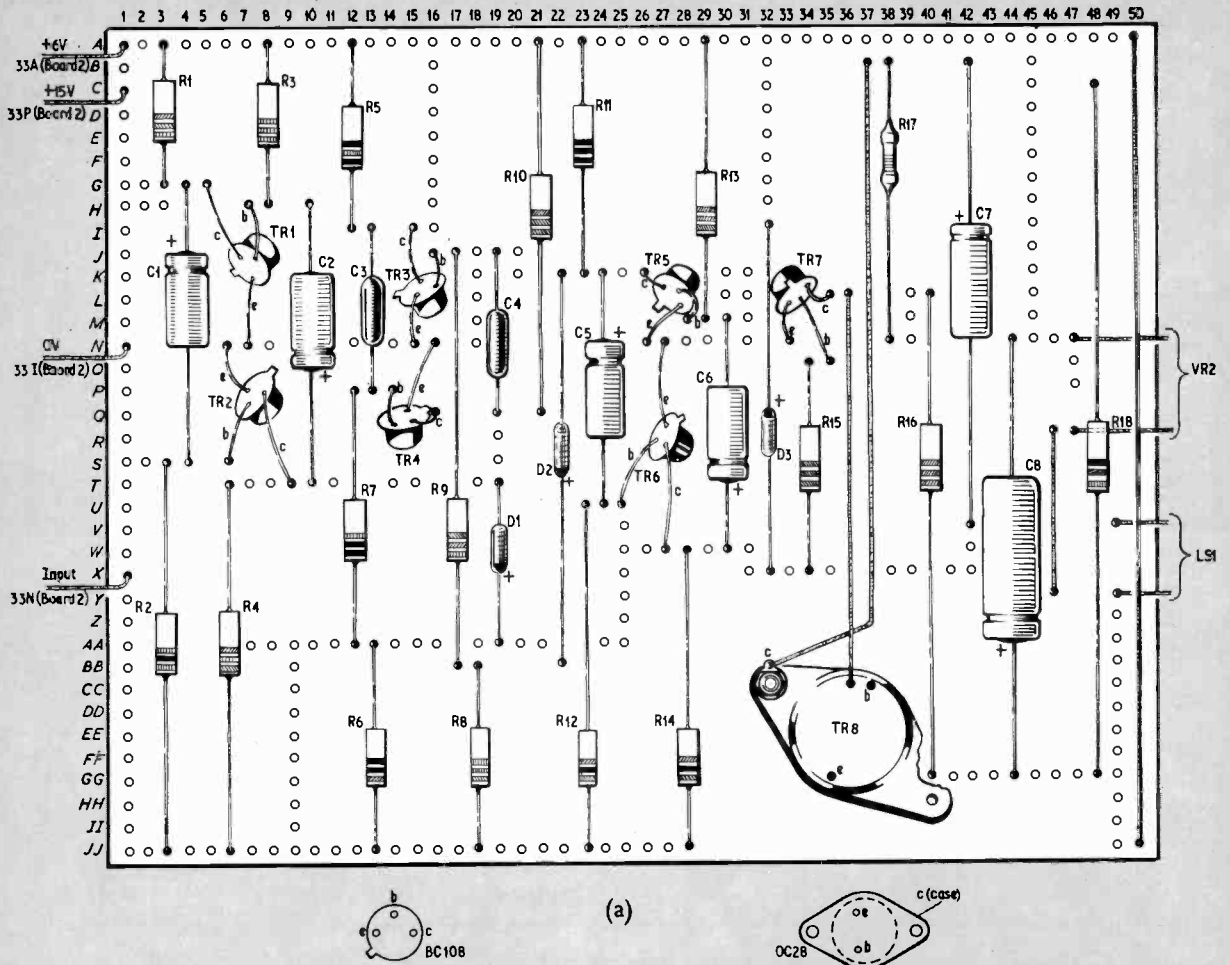

**Fig. 4. Component assembly of (a) the astable and amplifier circuit; (b) the monostable and switching amplifier. Assembly may be combined on a single Veroboard**

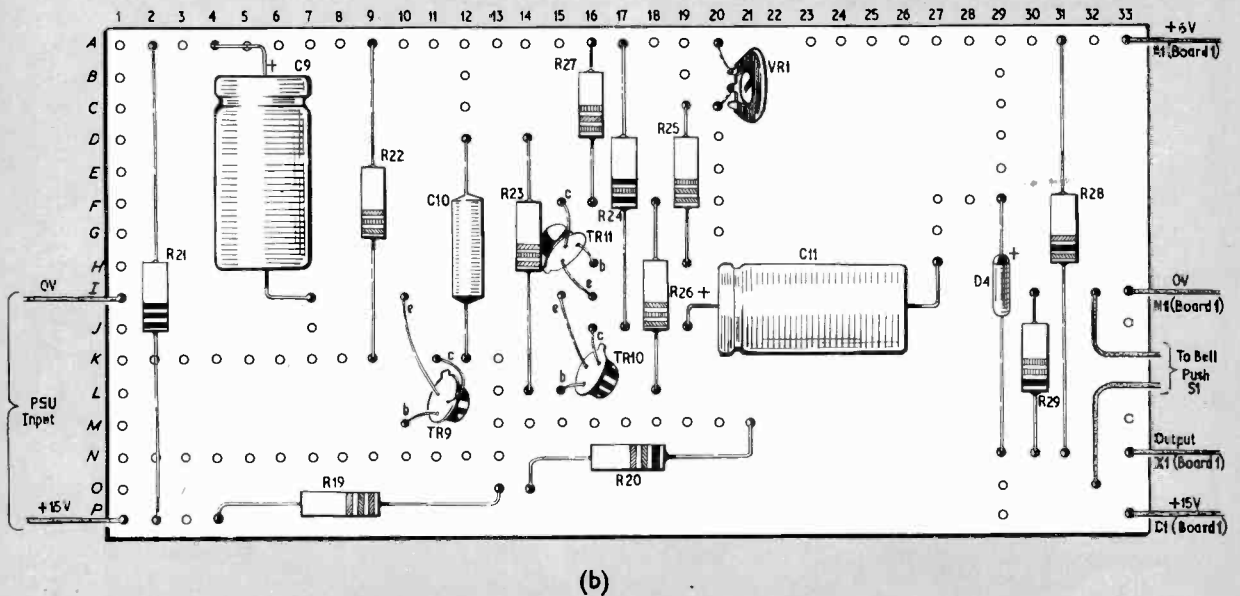

# NEWS BRIEFS

## Trinitron T.V.

A NEW colour television tube—called the Trinitron has been announced by Sony Ltd. The tube uses only one electron gun that projects three electron beams; the beams are converged and focused through two large diameter electron "lenses" and a pair of deflectors. Because a large diameter single "lens" can be used to focus all three beams from the Trinitron gun, greater brightness and better focus are claimed to be achieved.

The tube (shown below next to a conventional tube) also utilises a new colour selection method named "Aperture Grill" which uses a vertical slotted grill and vertical lines of phosphors rather than the holes and dots of the normal shadowmask tube. The single gun can also be used with either a shadowmask tube, or a chromatron tube, as can be seen from the drawing below.

The new tube has been incorporated in a 13in screen colour television which, when recently demonstrated to the press, gave a good account of itself. The set will be on the market in this country in April '71 and will retail at just under £200. It will be interesting to see if Telefunken A.E.G. are prepared to allow Sony to market this set, if it infringes their patent on the P.A.L. colour system, without a legal fight. It is not yet possible to say if the set infringes P.A.L. patent since Sony will give no technical circuit data, it will also be interesting to see if Sony can make larger screen sets—even if, as they state, they do not wish to market them in this country.

A—CHROMATRON

B—APERTURE GRILL

C—SHADOW MASK

TRINITRON GUN—  
CAN BE USED WITH A,  
B, OR C.

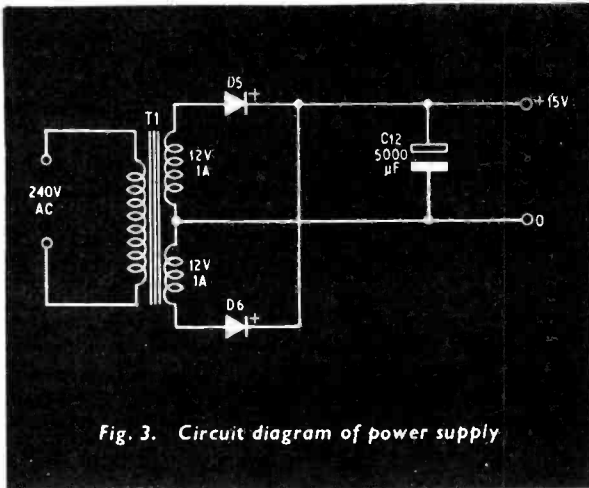
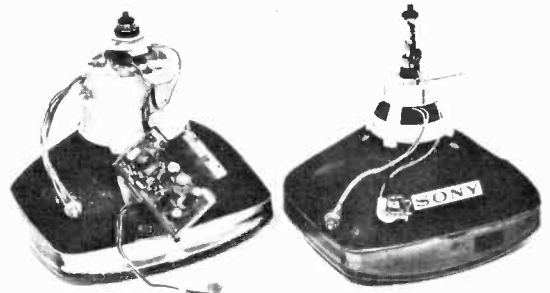
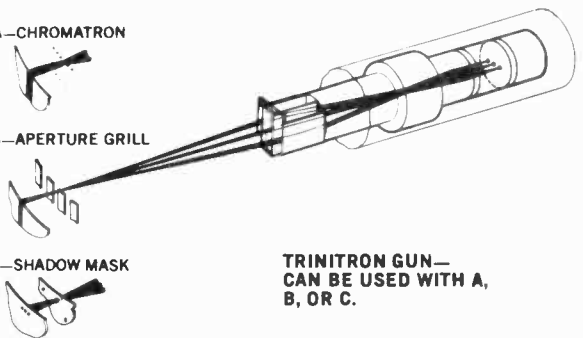


Fig. 3. Circuit diagram of power supply

## CONSTRUCTION

In the prototype the astable and amplifier circuits were built on a piece of 6in by 4½in Veroboard as given in Fig. 4. Here there is ample room for the components and no breaks in the copper strip are required.

A 2½in by 5in Veroboard is used for assembling the monostable circuit and switching transistor TR9. The reason for this separate board construction is because the monostable is dispensable since it only provides an interval of tones, the period of which can be set by VR1.

Since there is nothing critical in the layout, single board construction for the complete circuit, including power supply, can be made.

## CHECK OUT

If the completed unit fails to function with the supply applied, the following check out procedure should be undertaken.

First disconnect D4 to isolate the monostable. If a tone is not apparent, connect a headset via crocodile clips between TR3 collector and emitter. No sound points to either TR3 or TR4 being defunct.

If the stage is alright, apply the 'phones to TR7 and TR8 collectors, in that order, to determine the offending transistor.

To check the operation of the low frequency astables, a voltmeter should be connected to the collectors. This method can be used to establish the switching action at TR9 collector, the swing here being between 0 and 6V when the bell push is depressed.

Once the circuit is functioning correctly R6 can be replaced by a preset potentiometer if any time adjustment is required.

## VARIATIONS

As already mentioned the monostable section could be omitted. Simply omit TR10, TR11 and their associated components. Also omit C10 and R23 and connect the collector of TR9 directly to D4.


If an illuminated bell push is not used connect a 100 ohm resistor across the bell push contacts. This can be done on the component board.

If the monostable action is not required and a non-illuminated bell push is used, connect TR3 collector directly to R15, the base resistor of TR7. The bell push may then be used to connect the dc supply to the circuit. A 6 volt transformer could be used in this case.

A wooden box, or metal case, can be used for housing the completed circuitry, here the only external control item will be the potentiometer VR2. ★

# MAKING THE MOST

# OF LOGIC IC'S

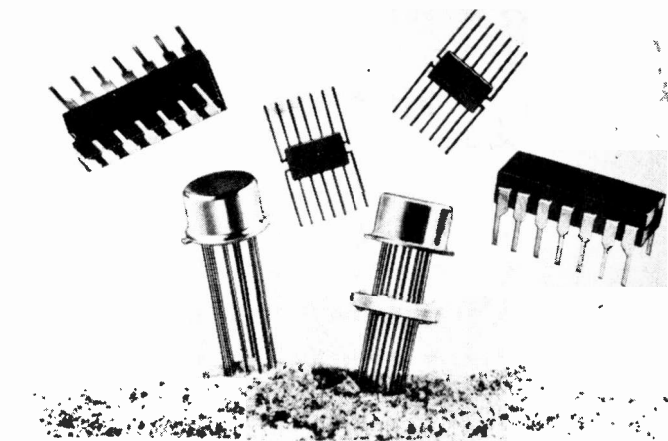

## PART TEN—By R. W. GOLES

### METAL OXIDE SILICON LOGIC (MOS)

It was mentioned in an earlier article in this series, that a further two logic families have been elevated to positions which rank them alongside the three originally basic groups RTL, DTL, and TTL.

This article concerns itself with the first of these two comparative newcomers, Metal Oxide Silicon Logic, usually referred to simply as MOS.

#### MOS DEVICE CAPABILITY

MOS logic is a very different family from any of the others discussed, both in fabrication and application. Instead of conventional bipolar transistors, insulated gate field effect devices are employed, and in general no linear resistors or diodes are used at all.

MOS is used with negative supply voltages of up to 30V, with consequently large logic swings which render the mixing of this family with, say, TTL a complicated business usually requiring special "interface" circuitry.

Registers and gates in the MOS range will not run at the high speeds associated with TTL either, a limit of 1 MHz being common in the specification of a shift register package.

In the light of all these apparent disadvantages one may well ask why anyone should bother with these devices at all, and the answer to this is that MOS is very simple indeed to produce, an advantage which makes it possible to incorporate vast quantities of logic elements on a single chip, and still achieve an economic yield.

A bipolar device, whether it be a single transistor or an MSI counter, requires well over one hundred process steps in its manufacture from a silicon "chip". An MOS circuit on the other hand is produced in less than forty steps of comparable complexity, which means less chance of manufacturing discrepancies and a correspondingly lower reject rate on circuits of the same magnitude as their bipolar counterparts.

Usually this improvement is used to advantage to enable large logic arrays, such as dual 100-bit serial shift registers, to be built on one chip, rather than duplicate the bipolar circuits. This slant towards large scale integration (LSI) is also helped by the fact that an MOS transistor, being a low current, high impedance device, takes up only about one fiftieth of the chip area that a typical bipolar device needs.

MOS techniques are beginning to revolutionise many areas of logic design because of this capability of producing complete systems in one package. As an example, a recently introduced three digit multi-meter uses a single LSI MOS chip which contains all the analogue-to-digital conversion logic and display decoding required, all in a 16-pin dual in-line package.

#### STRUCTURE

Transistors of the MOS type have been around for some time now, and have appeared in many designs, in particular the "front ends" of communications receivers, and high impedance input stages for audio amplifiers. Readers will be more familiar with them as field effect transistors (f.e.t.).

Just as there are *pnp* and *npn* bipolar devices, so there are *p*-channel and *n*-channel f.e.t.s, but in this case there is a further division into "enhancement" and "depletion" modes of operation, giving four device types in all. MOS logic circuits generally employ *p*-channel enhancement mode devices, although there is a recent form which uses complementary (*p*- and *n*-channel) logic on the same chip. The difference between *p*- and *n*-channel devices will be obvious to most readers, but "enhancement" and "depletion" may call for some explanation.

Fig. 10 shows the operation of these two devices in diagrammatic form. F.e.t.s have three electrodes known as the source, the drain, and the gate, and in the MOSFET the aluminium deposition known



**SCOOP PREVIEW!** **SAVE £31.50 NOW!**

**BRAND NEW 1971 MODEL** **fabulous PORTABLE/MAINS**

**\*NO MORE COSTLY OUTDOOR AERIALS!** **FULLY TRANSISTORISED**

**with BIG 12" SCREEN!** **MINI-TELE** **FIRST CLASS MARKERS!**

\* Gets all BBC1, BBC2, and ITV.  
\* Brilliant 625 lines picture.  
\* Full after sales service.  
\* 12 months written guarantee.

**OUR FANTASTIC DISCOUNT PRICE** **20% CARR. P. ETC. £1**

**ONLY £51.97** **RECOMMENDED RETAIL PRICE £83.47**



First Class Makers—We Must Not Mention Name! **THIS OFFER ONLY FROM US!** Due to Shopertunities' sensational scoop purchase of entire advance shipment for cash not only do you get this fabulous, brand spanking new, 1971 model, fully transistorised, portable/main, 625-line TV with BIG 12in SCREEN well ahead of everyone else but you **SAVE £31.50 AS WELL!** Even if you've got the biggest, most expensive colour TV already—you'll love this! And at our amazing price you could even afford to buy one as a second set! Brilliantly designed incorporating the very latest techniques and refinements! Beautifully made and finished. Superb performance! Carry it from room to room as desired, simply plug in—no waiting, no "warming-up," no old fashioned outside aerials—perfect sound and crystal clear vision almost instantly! Control sound from a whisper to a roar—no image rejection, even on maximum volume! Full range of simple controls. Extra smooth station selection dial. Size overall approx. 15 1/2in x 11in x 11 1/2in. Weight 19 1/2lb approx. 220/240V a.c. Yes, only £51.97, carr. etc. £1. (Certified guarantee sent with every set.) No more to pay! This fantastic offer may never be repeated—so why not get two or more, while the going's good? Get one for grandma! Get one for the children! Get one for the bedroom! Get one as a gift! At our incredible price you just can't lose! Shopertunities for bargains! Send today or call.

**ONLY FROM US! FIRST SHIPMENT JUST ARRIVED!**

**BRAND NEW 1971 Model** **RUSSIAN WORLD BEATER!** **WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!**

**6 WAVEBAND** **10 TRANSISTOR**

**WORLDWIDE RECEPTION** **£9.97**

THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER! **BOX POST ETC. 43p**


**NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!**



What everyone's been waiting for—**THE LATEST 1971 MODEL SUPERSEDING ALL PREVIOUS MODELS. THE FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6 WAVEBAND PORTABLE RADIO. DESIGNED FOR WORLD WIDE RECEPTION.** Only finally put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at £9.97—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £34 radios! \*You can't lose. Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection! Once again the Russians have proved their fantastic ability in the field of electronics by brilliantly reflecting their advanced micro-circuitry techniques in the field of spacechip and satellite communications. **YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO ITS TRUE VALUE!** Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over the world—nothing is secret! The radio enthusiast can have the world in the palm of his hand! Superb, sweet tone—controlled from a whisper to a roar that will fill a hall! Genuine push pull output! Separate ON/OFF volume and Treble/Bass tone controls. Take it anywhere—runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33 1/2in length. It's also a fabulous **CAR RADIO**—any speed, requires no additional aerial. **UNIQUE!** Elegant Magnificently designed and made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97, POST, ETC., 43p.** Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address. Refund if not delighted.


**SHOPERTUNITIES LTD** Dept. PE/3, 164 UXBRIDGE ROAD (facing Shepherd's Bush Green), LONDON W12 8AQ (Thurs. 1, Fri. 7). Also at 37 High Holborn, London, W.C.1 (Wed. 1, Thurs. 7). Both stores open MON-SAT 9-6.

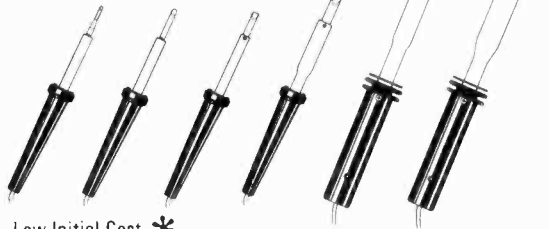**Take your Wellerchoice\* in Soldering**



**Low Initial Cost \***  
Low initial cost Marksman irons, to cover most soldering needs. Screw-in tips on 15W and 25W make it easier to change the tips, which are nickel-plated and factory pre-tinned for longer life. The shanks are stainless steel to concentrate heat at the tips.

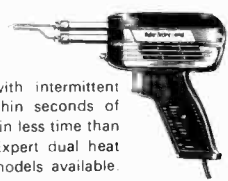**Instant Heat for Rapid Soldering \***  
Instant heat soldering guns to deal with intermittent soldering. Working heat is reached within seconds of pressing the trigger, so the job is finished in less time than it takes for a normal iron to heat up. Expert dual heat (100/140W) and Heavy Duty (275W) models available. Alternative tips available for plastics working.



**Weller Electric Limited**

Redkln Way, Horsham, Sussex Tel: 0403 61747

**VALVES SAME DAY SERVICE**

**NEW! TESTED! GUARANTEED!**

SETS		1R6, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.45	
	5p	5p	5p
1A7GT	0-37 25U4GT	0-57 DL92	0-28 EL90
1H5GT	0-36 30C1	0-32 DL94	0-37 EL500
1N5GT	0-38 30C15	0-83 DL96	0-30 EM80
1R5	0-28 30C17	0-80 DY86	0-28 EM81
185	0-21 30C18	0-87 DY87	0-28 EM84
1T4	0-18 30F3	0-78 EAC80	0-32 EM87
384	0-28 30FL1	0-83 EAF42	0-50 EY51
3V4	0-37 30FL12	0-72 EB91	0-11 EY86
5Y8GT	0-30 30FL14	0-72 EBC33	0-40 EZ40
5Z4G	0-37 30L1	0-32 EBC41	0-52 EZ41
6J0L2	0-58 30L15	0-85 EBC90	0-22 EZ80
6AL5	0-11 30L17	0-73 EBF80	0-33 EZ81
6AM6	0-13 30P4	0-65 EBF89	0-31 GZ32
6AQ5	0-26 30P12	0-77 ECG91	0-18 GZ34
6AT8	0-22 30P19	0-65 ECC82	0-23 K741
6AU6	0-22 30P11	0-83 ECC83	0-35 K761
6BA6	0-22 30P13	0-88 EOC85	0-28 K766
6BE6	0-23 30P14	0-70 EOC80A	0-60 LN319
6BJ6	0-42 30P15	0-72 EOCF80	0-30 LN329
6BW7	0-00 35L6GT	0-43 ECF89	0-30 LN339
6CD6G	1-10 35W4	0-22 ECH35	0-30 N78
6F14	0-45 35Z4GT	0-25 ECH42	0-83 PAB30
6E23	0-73 807	0-45 ECH81	0-28 PC86
6E25	0-82 6053	0-88 ECH83	0-41 PC88
6K7G	0-12 AC/VP2	0-77 ECH84	0-37 PC89
6K8G	0-17 AZ31	0-47 ECL80	0-35 PC87
6L8GT	0-97 B49	0-85 ECL89	0-33 PC900
6V5G	0-17 H729	0-82 ECL86	0-40 PC84
6V6GT	0-32 CCH35	0-87 EY39	0-23 PC88
6X4	0-23 CL33	0-92 EY41	0-58 PC88
6X5GT	0-28 CY31	0-33 EY80	0-23 PC89
10F18	0-35 DAC32	0-38 EY184	0-32 PCF800
10F13	0-60 DAF91	0-21 EY85	0-31 PCF801
12A7	0-25 DAF96	0-28 EL33	0-48 PCF802
12A7U	0-18 DF33	0-38 EY89	0-26 PCF80
12AU6	0-23 DF91	0-16 EY91	0-13 PCF82
12AU7	0-23 DF96	0-36 EY183	0-28 PCF82
12AX7	0-23 DH77	0-22 EY184	0-32 PCF800
19BG6G	0-87 DK32	0-47 EL90	0-42 PCF801
20F2	0-67 DK91	0-28 EL33	0-48 PCF802
20P3	0-85 DK92	0-42 EL34	0-47 PCF805
20P4	0-92 DK96	0-36 EL41	0-55 PCF806
25L6GT	0-25 DL35	0-25 EL84	0-24 PCF808
			0-78 UAF42
			0-51 OC170
			0-22 UBC31
			0-60 UBF80
			0-37 UBF89
			0-41 UCL84
			0-45 UCL84
			0-41 UCB85
			0-72 UCF80
			0-77 UCH42
			0-42 UCH81
			0-70 UCL82
			0-58 UCL83
			0-48 UF41
			0-46 UF89
			0-51 UL41
			0-30 UL84
			0-35 UM80
			0-32 UM84
			0-65 UY41
			0-87 UY85
			0-37 VP41
			0-83 WY19
			0-55 Z77
			0-22
			0-55 Transistors
			0-26 AC107
			0-26 AC127
			0-26 AC170
			0-26 AD140
			0-37 AF116
			0-37 AF116
			0-25 AF118
			0-85 AF123
			0-17 AF125
			0-85 AF127
			0-85 OC26
			0-25 OC26
			0-72 OC81
			0-72 OC81D
			0-12 OC71
			0-24 OC75
			0-12 OC75
			0-72 OC81
			0-52 OC81D
			0-72 OC81D
			0-88 OC82
			0-88 OC82
			0-32 OC82D
			0-25 OC170

**READERS RADIO (P.E.)**

85 TORQUAY GARDENS, REDBRIDGE, ILFORD, ESSEX. Tel. 01-550 7441  
Postage on 1 valve 5p extra. On 2 valves or more, postage 3p per valve extra. Any Parcel Insured against Damage in Transit 3p extra.



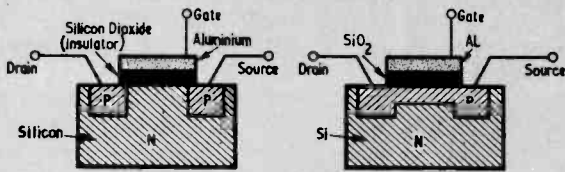


Fig. 10.1a. P-channel enhancement mode device

Fig. 10.1b. P-channel depletion mode device

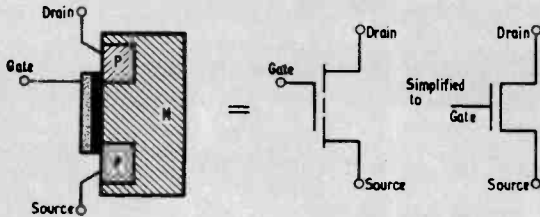


Fig. 10.2. Construction of the f.e.t. in MOS logic (left) with theoretically correct and simplified versions of the circuit symbol

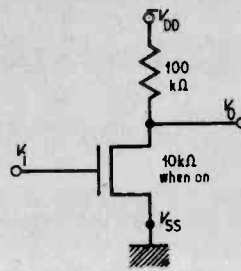


Fig. 10.3a. Logic inverter with discrete resistor as a load

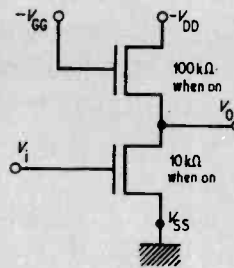


Fig. 10.3b. Using a MOS transistor in place of the resistive load

as the gate is insulated from the other sections of the device by a layer of silicon dioxide. There is therefore no d.c. current flow into or out of the gate, and the input impedance is extremely high, only the field set up by the gate voltage is used to modulate the current flow from source to drain.

When the gate voltage is such that there is a current flow between the other two terminals, a "channel" is said to exist between them. It is the type of bias necessary to form this channel which sets the difference between the enhancement and depletion devices.

### ENHANCEMENT MODE

In the enhancement mode a channel does not exist between source and drain until an appropriate gate bias is applied, whereas in the depletion mode a channel exists with zero gate bias, and a bias has to be applied to cut off current flow. In Fig. 10.1a, for example, the p-channel enhancement mode device requires a negative bias on the gate before it will form a channel, but in Fig. 10.1b the p-channel depletion mode device will have a channel unless the gate is biased positively.

Of these two types the enhancement device is more suited for use as a logic switch, because it is off until turned on by a negative bias from a previous stage.

Fig. 10.2 compares the construction of the f.e.t.s used in MOS logic with the correct circuit symbol and the simplified version usually employed for logic circuits.

### THRESHOLD VOLTAGE

The MOS device is commonly used in logic circuitry as a switch, and performs very well in this role. On resistance can be varied by the manufacturer by altering the geometry of the device, but is usually chosen to be about 10 kilohms, whereas off resistance is closer to the ideal open circuit than

can be approached with bipolar devices, and is typically  $10^{11}$  ohms.

Fig. 10.3a shows a single MOS used with a discrete resistor to form a logic inverter. As the gate voltage is increased negatively, a point is reached when the device resistance drops to the on value, reducing the output voltage to a low level, which would have the effect of turning off any following stage. The actual voltage at which an MOS turns on is referred to as the "threshold voltage", and it usually lies at about 3V. The threshold is not very abrupt, however, so this is only a nominal value.

Using conventional diffused silicon resistors in an MOS i.c. would unfortunately take up a great deal of space on the chip, losing the size advantage of the MOS active device. A diffused resistor such as is used in TTL circuits would in fact be about 1,000 times larger than a single MOS.

### MOS TRANSISTOR AS A LOAD

To sidestep this problem the arrangement in Fig. 10.3b is employed. Here another MOS transistor is used as a load resistor, only in this case the device geometry is chosen to give an on resistance of the required 100 kilohms. The gate of this load element can either be wired permanently to the  $-V_{DD}$  negative supply, holding the device permanently on, or all the gates of devices used for this purpose can be brought out to a  $-V_{GG}$  common line which is held at a voltage even more negative than  $-V_{DD}$ . This also has the effect of keeping the load on. A third alternative uses these devices as "clock-line" switches as we shall see later.

### BASIC GATE CIRCUITS

Because of the "ideal switch" characteristics of MOS, biasing problems, a feature of bipolar designs, do not arise. MOS devices are used almost as simply as relay contacts or toggle switches in gate circuits,

making them very simple to understand, once the initial unfamiliarity of the symbols is overcome.

Fig. 10.4 shows some examples of gates made with MOS alongside their relay equivalents. With this family there is no "standard" gate, both NOR and NAND logic are used as it suits the designer, though it is normal practice to define gates in the negative logic convention, unlike TTL. There really seems little need to explain the action of the gates in Figs. 10.4a and 10.4b; with the understanding of

an MOS transistor action and the relay version to refer to, readers will be able to work this out for themselves, with the knowledge of logic systems given earlier in this series.

Fig. 10.4c demonstrates how easy it is to expand MOS logic. Here two NAND gates are used in the wired-OR configuration, to generate the AND/OR/INVERT function. Interested readers may like to compare this very simple arrangement with the equivalent TTL circuitry.

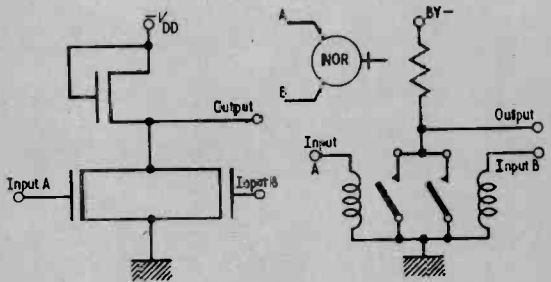


Fig. 10.4a. MOS NOR configuration

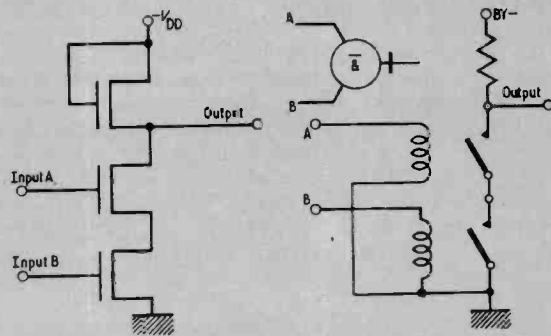


Fig. 10.4b. MOS NAND configuration

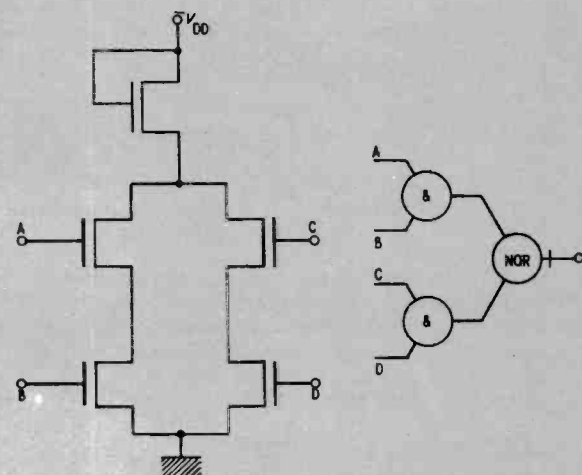


Fig. 10.4c. MOS wired-OR configuration (AND/OR/INVERT)

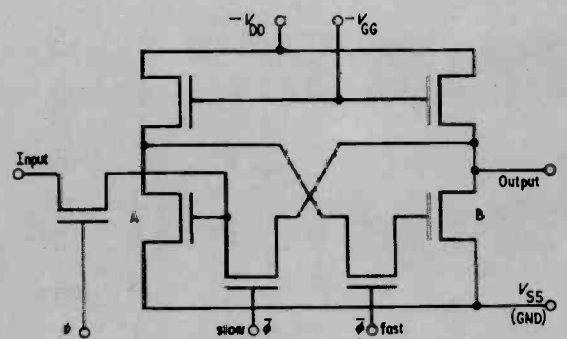


Fig. 10.5. Static shift register cell and clock waveforms


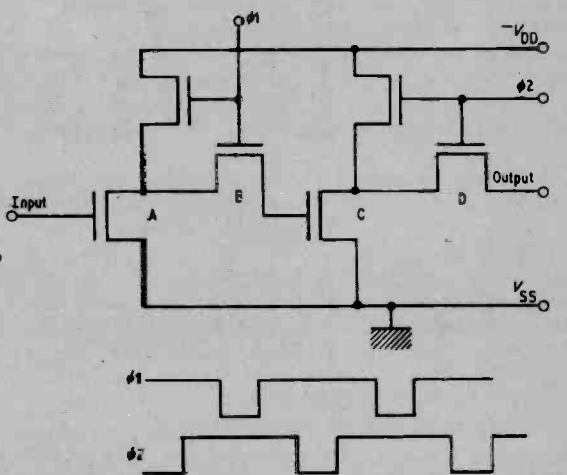


Fig. 10.6. Dynamic shift register cell and clock waveforms

It costs

**ONLY 63p**  
post paid

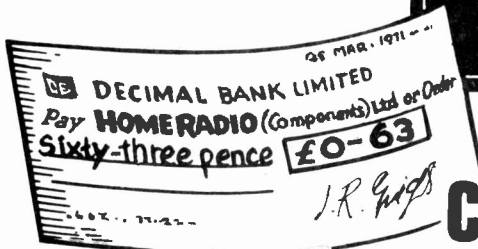

# for today's MOST USEFUL COMPONENTS CATALOGUE



The price of 63p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Many radio and electronic enthusiasts say that our catalogue is "priceless"! Be that as it may, we charge you only 63 pence. What is more the catalogue contains 6 vouchers, each worth 5 pence when used as indicated. And for good measure, we throw in a useful Bookmark giving electronic abbreviations and a 30-page Price Supplement. *Why are you waiting?* By the way, if it suits you to call at our shop you save yourself another 20 pence—the post and packing costs.

## POST THIS COUPON



Please write Name and Address in block capitals

with your cheque or P.O. for 63p

Name  
Address



**HOME RADIO (Components) LTD.**  
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

## TRANSISTOR AUDIO AND RADIO CIRCUITS

for Radio Receivers, Radiograms, Record Players, Tape Recorders and Hi-Fi Equipment.

A Mullard Publication

£1-50

Postage 5p

**ELECTRONIC DESIGNER'S HANDBOOK.** A practical guide to transistor circuit design. T. K. Hemingway. £3-40. Postage 10p.

**20 SOLID STATE PROJECTS FOR THE CAR & GARAGE.** R. M. Marston. £1-20. Postage 5p.

**COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM.** G. N. Patchett. £2-50. Postage 5p.

**SECURITY ELECTRONICS.** John E. Cunningham. £1-70. Postage 5p.

**RADIO & AUDIO SERVICING HANDBOOK.** Gordon J King. £3. Postage 10p.

**TRANSISTOR POCKET BOOK.** R. G. Hibberd. £1-40. Postage 5p.

**1971 WORLD RADIO-TV HANDBOOK.** J. M. Frost. £2-10. Postage 12p.

**RADIO VALVE & TRANSISTOR DATA.** A. M. Ball. 75p. Postage 9p.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET

LONDON, W.2


Phone: PADdington 4185

Closed Saturday 1 p.m.

NEW! HANDY! TIDY!
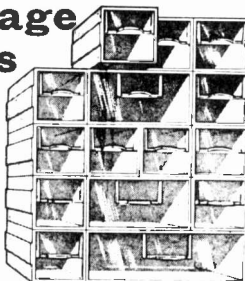
## multi-drawer I-N-T-E-R-L-O-C-K-I-N-G storage units

A PLACE FOR EVERYTHING EVERYTHING IN ITS PLACE!



Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units, interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

### BUY AT TRADE PRICES!

**SINGLE UNITS** (5ins x 2½ins x 2½ins) Usually 15p each, **OUR PRICE: £1-35 DOZEN**  
**DOUBLE UNITS** (5ins x 4½ins x 2½ins) Usually 25p each, **OUR PRICE: £2-25 DOZEN**

### PLUS QUANTITY DISCOUNTS!

Order £5 and over DEDUCT 5% in the £  
Orders £10 and over DEDUCT 7½% in the £  
Orders £20 and over DEDUCT 10% in the £

PACKING/POSTAGE/CARRIAGE: Add 30p to all orders under £5. Orders £5 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID



(Dept. PE4) 31 ALBERT RD. HENDON, LONDON, NW4

## OSMABET LTD.

We make transformers amongst other things

**MAINS TRANSFORMERS**  
Prim 200/240V a.c. TX1 425-0-425V 250mA, 6-3V 4ACT, 6-3V 4ACT, 0-5-0, 3V 3A, £8-75; TX2 250-0-250V 150mA, 6-3V 4ACT, 0-5-0-3V 2A; £3-92; TX3 300-0-300V 120mA, 6-3V 2ACT, 6-3V 2A, 6-3V 1A, £3-92; TX8 250-0-250V 65mA, 6-3V 1-5A, £2-10; MT1 200V 30mA, 6-3V 1A, £1-20; MT2 230V 45mA, 6-3V 1-5A, £1-50; MT2A 250V 60mA, 6-3V 2A, £1-87; NT3 Prim 110/240V See 250V 100mA, 6-3V 2A, £2-25.

**MULTIVOLT TRANSFORMERS**  
Prim 200/240V a.c. OMT4/1 one tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-35-40-55-60, 10-0-10; 20-0-20, 30-0-30V a.c. 1A, £2-25; ditto trans. 2A OMT4/2, £3-37; OMT3/1 one tapped sec. 40-50-60-80-90-100-110V a.c. 1A, £3-37.

**LOW VOLTAGE TRANSFORMERS**  
Prim 200/240V a.c. 6-3V 1-5A, 85p; 3A, £1; 6A CT, £1-70; 12V 1-5A, £1-05; 3A CT, £1-70; 6A CT, £2-25; 18V 1-5A CT, £1-32; 24V 1-5A CT, £1-75; 3A CT, £2-90; 5A, £3-75; 8A, £5-02; 12A, £8-75.

**MIDGET RECTIFIER TRANSFORMERS**  
For FW rectification, size 1½ x 2 x 1½in. Prim 200/240V a.c. output, PPT1 9-0-9V 0-3A; PPT2 12-0-12V 0-25A; PPT3 20-0-20V 0-15A, £1-12; each; ditto size 2 x 2½ x 1½in. MVT1 9-0-9V 1A; MVT2 12-0-12V 1A; MVT3 20-0-20V 0-75A, £1-12; each.

**O/P TRANSFORMERS**  
P.P. sec tapped 3-7-5-15 ohms, A-A 6-6K 30W (KT66, etc.), £3-92; 50W, 3K (EL34, KT88, etc.), £6-75; 100W 3K (EL34, KT88, etc.), £11-25.

**LOUDSPEAKERS**  
Ex equipment perfect, 3 ohms only, 5in at 40p each, p.p. 15p min.

**LOUDSPEAKERS, HI-FI, P.A., GUITARS, ETC.**  
New, boxed, famous makes, 25W, £5-50, 35W, £6-50; 50W, £10; 60W, £12; 100W, £20; E.M.I. 13 x 8in, 10W, 3, 8 and 15 ohms, £2-25; fitted two tweeters crossover network, HI-FI, 3, 8 and 15 ohms, £4. Horn Tweeters 2-16Hz, 8 or 15 ohms, £1-50.

**MULTI-WAY CONNECTORS (BELLING LEE)**  
18 way, new, for line, inter chassis, etc., pair, 25p.

**LT FLUORESCENT LIGHTING**  
12V fittings with tube, 8W, £3-75; 13W, £6-25; Inverters 12V, 20W, £7-50; twin 20W or single 40W, £8; twin 30W or single 50W, £11; Extensive range, lists S.A.E.

Carriage extra all orders.  
S.A.E. ALL ENQUIRIES PLEASE, MAIL ORDER ONLY

46 Kenilworth Road, Edgware, Middx. HA8 9YG  
Tel. 01-958 9314

# ELECTROVALUE

EVERYTHING BRAND NEW & TO SPEC. ● LARGE STOCKS ● NO SURPLUS

## BARGAINS IN NEW SEMICONDUCTORS

Many items at new reduced prices. All power types supplied with free insulating sets

2N696	20p	2N2924	20p	40361	55p	BC148	14p	BFX87	29p
2N697	22p	2N2925	22p	40362	68p	BC149	15p	BFX88	26p
2N706	12p	2N2926	11p	AC107	46p	BC153	35p	BFY50	23p
2N930	29p	2N3053	27p	AC126	20p	BC154	38p	BFY51	20p
2N1131	36p	2N3325	54p	AC127	20p	BC157	18p	BFY52	23p
2N1132	40p	2N3702	13p	AC128	20p	BC158	17p	DBX20	16p
2N1302	19p	2N3703	13p	AC138K	25p	BC159	18p	C407	17p
2N1303	19p	2N3704	13p	AC176	27p	BC167	13p	MC140	25p
2N1304	23p	2N3705	13p	ACY20	20p	BC168	11p	MPS6531	35p
2N1305	23p	2N3706	13p	ACY22	16p	BC169	13p	MPS6534	30p
2N1306	33p	2N3707	13p	AD140	56p	BC177	17p	NKT211	25p
2N1307	33p	2N3708	13p	AD142	71p	BC178	15p	NKT212	25p
2N1308	36p	2N3709	13p	AD149	60p	BC179	17p	NKT214	23p
2N1309	36p	2N3710	13p	AD161	40p	BC182L	13p	NKT274	18p
2N1613	23p	2N3711	13p	AD162	40p	BC183L	11p	NKT403	65p
2N1711	26p	2N3794	15p	AF154	30p	BC184L	13p	NKT405	79p
2N1893	54p	2N3904	35p	AF115	30p	BC212L	25p	OC71	29p
2N2147	95p	2N3906	35p	AF117	28p	BC213L	25p	OC81	25p
2N2518	33p	2N4058	20p	AF124	39p	BC214L	25p	OC81D	25p
2N2918A	43p	2N4059	29p	AF127	28p	BCY70	18p	ZTX300	17p
2N2919	43p	2N4060	20p	AF139	48p	BCY71	33p	ZTX301	17p
2N2919A	53p	2N4061	20p	AF239	49p	BCY72	15p	ZTX302	22p
2N2920	62p	2N4062	20p	ABY26	27p	BF115	38p	ZTX303	22p
2N2969A	19p	2N4124	18p	ABY28	27p	BF167	43p	ZTX304	25p
2N2483	35p	2N4126	27p	BC107	14p	BF173	14p	ZTX500	25p
2N2484	42p	2N4284	15p	BC108	12p	BF194	17p	ZTX501	25p
2N2904	38p	2N4286	15p	BC109	14p	BF195	18p	ZTX502	30p
2N2904A	42p	2N4289	15p	BC125	55p	BFX29	31p	ZTX503	25p
2N2905	44p	2N4291	15p	BC126	55p	BFX84	25p	ZTX504	60p
2N2905A	47p	2N4292	15p	BC147	15p	BFX85	34p		

## PEAK SOUND PRODUCTS ENGLEFIELD AMPLIFIER



12 + 12  
watts RMS  
per channel

Stereo amplifier in modular kit form (including cabinet) 12 watts per channel £38.45. Cabinet kit only £6. These prices nett.

## BAXANDALL SPEAKER SYSTEM



Designed by Peter Baxandall. Superior reproduction for its size. Handles 10 watts with ease. Uses ELAC 15 D 5BRM109 speaker unit. Kit £13.80 nett; built £18.40 nett.

## MAINLINE AMPLIFIER KITS

RCA/808 designed main amplifier kits. Input sensitivity 500-700mV for full output into 8Ω.		Input sensitivity
	Kit price	Suitable unreg.
Power	including components	power supply kit
12W	£8.40 nett	£4.60
25W	£9.50 nett	N/A
40W	£10.50 nett	£5.75
70W	£12.60 nett	£6.94

## 30 WATT BAILEY AMPLIFIER KIT

Sensitivity 1.2V for full output into 8Ω. Transistors and PCB for one channel £7.30. Transistors and PCBs for two channels £14.60. Capacitors and resistors (metal oxide) £2 per channel. Complete unregulated power supply kit £4.78.

## ZENER DIODES

5% full range E24 values: 400mW: 2.7V to 30V 19p ea. 1W: 6.8V to 82V 33p ea. 1.5W: 4.7V to 75V 60p ea. Clip to increase 1.5W rating to 3 watts (type 266F) 4p.

## CARBON TRACK POTENTIOMETERS, long spindles.

Double wiper ensures minimum noise level.	
Single gang linear	220Ω to 2.2MΩ 12p
Single gang log	4.7KΩ to 2.2MΩ 12p
Dual gang linear	4.7KΩ to 2.2MΩ 42p
Dual gang log	4.7MΩ to 2.2MΩ 42p
Log/antilog	10K, 47K, 1MΩ only 42p
Dual antilog	10K only 42p
Any type with 1A D.P. mains switch, extra 12p.	
Please note: only decades of 10, 22 and 47 are available within ranges quoted.	

## CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only 100Ω, 220Ω, 470Ω, 1K, 2K, 4K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 5M, 10MΩ. Vertical or horizontal mounting 5p each.

## TYGON SPEAKER MATERIAL

Seven designs, 36in x 27in sheets, £1.57. Pattern books, send R.A.E. plus 3p in stamps.

## COMPONENT DISCOUNTS

10% on orders for components for £5 or more. 15% on orders for components for £15 or more (No discount on nett items).

## POSTAGE AND PACKING

Free on orders over £2. Please add 10p if under. Overseas orders welcome: carriage charged at cost. IMPORTANT—Please ensure that cheques dated on and after February 15th are drawn in decimal currency. Otherwise they cannot be accepted.

## RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99 (see note below)	100 up
C	1/20W	5%	82Ω-220kΩ	E12	7p	6p	6p
C	1/4W	5%	4.7Ω-330kΩ	E24	1p	0.8p	0.7p
C	1/2W	10%	4.7Ω-10MΩ	E12	1p	0.8p	0.7p
C	1/4W	5%	4.7Ω-10MΩ	E24	1.5p	1p	0.9p
C	1W	10%	4.7Ω-10MΩ	E12	2.5p	2.5p	1.9p
MO	1/4W	2%	10Ω-1MΩ	E24	4p	3.5p	3p
WW	1W	10% ± 1/20Ω	0.22Ω-3.9Ω	E12	7p	7p	6p
WW	3W	5%	12Ω-10kΩ	E12	7p	7p	6p
WW	7W	5%	12Ω-10kΩ	E12	9p	7p	8p

CODES: C - carbon film high stability low noise. MO - metal oxide Electrofil TR5 ultra low noise. WW - wire wound Plesey.

VALUES: E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Prices are in pence each for same ohmic value and power rating. NOT mixed values. (Ignore fractions of 1p on total resistor order.)

## INTEGRATED CIRCUIT AMPLIFIERS

SINCLAIR IC.10 complete with instruction book giving amplifier circuit details and range of applications. £2.85 nett. Components pack for stereo inc. mains transformer, con'trols etc. £4.75 nett.

PLESSEY SL403A. Only £2.75 each nett. 3W into 7.5Ω for 18V supply. Application data 10p; free with two or more.

## WAVECHANGE SWITCHES LONG SPINDLES

1P 12W; 2P 6W; 3P 4W; 4P 3W 24p each

## SLIDER SWITCHES D.P.D.T.

15p each

## NEON INDICATOR LAMPS all 200/250V

Square bezel, red only 19p  
Round chrome bezel red, amber, clear 28p  
Toggle switches, 250V a.c. 1.5A. Chrome (only) and chrome plated nut S.P.S.T. 19p; S.P.D.T. 22p; D.P.D.T. 28p; S.P.D.T. centre off 25p.

8-DeC's put an end to "birdnesting". Components just plug in. Saves valuable time. Use components again and again. 8-DeC (70 points) only £1. Compact T-DeC increased capacity, may be temperature-cycled. T-DeC (208 points) only £2.50. Full range stocked.

## MULLARD POLYESTER C280 series

±50V 20%; 0.01, 0.022, 0.033, 0.047, 3p ea.; 0.068, 0.1, 0.15, 4p ea.; 0.22, 5p, 10%, 0.33, 7p; 0.47, 8p; 0.68, 11p; 1μF, 13p; 1.5μF, 21p; 2.2μF, 24p.

## MULLARD SUB-MIN ELECTROLYTIC

C426 range axial lead 6p each. Values (μF/V): 0.64/64, 1/40, 1.6/25, 2.5/16, 2.5/64, 4/10, 4/30, 5/64, 6.4/6.4, 6.4/25, 8/4, 8/40, 10/2.5, 10/15, 10/64, 12.5/25, 16/40, 20/16, 20/64, 25/64, 25/25, 32/4, 32/10, 32/40, 32/64, 40/16, 40/2.5, 50/6.4, 50/25, 50/40, 64/4, 64/10, 80/2.5, 80/16, 80/25, 100/6.4, 125/4, 125/10, 125/16, 160/2.5, 200/6.4, 200/10, 250/4, 320/2.5, 320/6.4, 400/4, 500/2.5.

## LARGE CAPACITORS

High ripple current types: 1000/25 28p; 1000/50 41p; 1000/100 82p; 2000/25 37p; 2000/50 57p; 2500/64 84p; 2500/70 87p; 5000/25 82p; 5000/50 £1-10; 5000/100 £2-91; 10000/15 85p; 10000/25 £1-28.

## MEDIUM RANGE ELECTROLYTICS

Axial leads: 50/50 9p; 100/25 9p; 100/50 12p; 250/25 12p; 330/25 12p; 250/50 18p; 500/25 18p; 500/50 22p; 1000/25 20p; 1000/50 30p; 2000/25 30p.

## SMALL ELECTROLYTICS

Axial leads: 4.7/10, 4.7/25, 5/50, 5p ea. 10/10, 10/25, 10/50, 33/10, 50/10, 5p ea. 25/25, 25/50, 47/25, 100/10, 220/10, 6p ea.

## ENAMELLED COPPER WIRE even No. 8WG.

only: 2 oz. reels: 16-22 SWG 28p; 24-30 SWG 27p; 32, 34 SWG 29p; 36, 38 SWG, 34p; 4 oz. reels 16-22 SWG only 41p.

# ELECTROVALUE

Dept. PE371, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Hours: 9-5.30; Sat. 1 p.m. Tel.: Egham 5533 (STD 0784-3). Telex 264475

## SHIFT REGISTERS

MOS is rarely used to build general purpose flip-flops such as the JK type, although a manufacturer's catalogue may contain a single device of this sort to enable a system to be built entirely of MOS. It is included for the sake of completeness, and it is unlikely that these devices could stand on their own merit for economic reasons.

As we have already seen, the strength of MOS lies in its ability to be produced in the LSI form, and this advantage is put to good use in the range of shift registers available. Shift registers in this family are mainly of the "serial-in/serial-out" type, and their operation may be either static or dynamic.

The static type of register uses more devices per stage than the dynamic type, but data is stored by means of cross-coupled flip-flops, and there is no minimum clock rate. Dynamic registers use the capacitor inherent in the gate construction to store data, and are not capable of storing information indefinitely as a result. A minimum clock frequency of about 1kHz at 25°C is common for these registers which are used in continuously circulating applications such as delay lines.

The unit storage cells in both types of register bear little or no relation to the circuitry employed in any of the bipolar logic forms.

## STATIC REGISTER

The emphasis in MOS is on simplicity at the expense of clock circuit complexity. Fig. 10.5 shows the circuit used for a static register cell; the cross coupled flip-flop configuration is immediately apparent.

In all, three separate clock waveforms are necessary to operate this circuit, although in an LSI chip it is usual to have a circuit which generates all these from a single external timing waveform. The  $\phi$  clock corresponds to the external waveform and  $\bar{\phi}$  fast is the  $\phi$  clock inverted,  $\bar{\phi}$  slow comes on sometime after  $\phi$  fast, and usually, although not necessarily, ends before it. Fig. 10.5 shows some typical waveforms.

A negative logic level would be transferred from the input to the gate of device A when  $\phi$  comes on, and this would turn on A, pulling its output to ground. As soon as  $\phi$  goes off,  $\bar{\phi}$  fast comes on and transfers the ground on the output of A to the gate of B which starts to turn off. During this operation  $\bar{\phi}$  slow comes on and the rising negative at the output of B is transferred to the gate of A, holding it on. If the clock is stopped with  $\phi$  off (and hence  $\bar{\phi}$  fast and  $\bar{\phi}$  slow on) data can be stored indefinitely.

The gate of an MOS transistor can be considered to be a capacitor, the insulating silicon dioxide layer acting as the dielectric, and the aluminium and silicon acting as the plates. This capacitor is of very low value, perhaps 0.5pF, but because of the extremely high input impedance of an MOS device any charge stored on this gate capacitor will take quite a long time to leak away. (Remember that time constant equals C times R.)

## DYNAMIC REGISTER

In the dynamic register this effect is used to store digital information, but because the charge will eventually leak away in any event, it is necessary

to quote a minimum clock frequency which is temperature dependent.

Fig. 10.6 shows the circuit of one cell of a dynamic register, and as can be seen there is no cross-coupled flip-flop, only two gated inverters. The load MOS devices are used as switches controlled by the clock, and further devices gate information between stages. The clock waveforms  $\phi 1$  and  $\phi 2$  are in antiphase and must not overlap.

Assuming a negative input to the cell shown, this will be stored on the gate of device A, and will turn it on as soon as the  $\phi 1$  clock comes on. While  $\phi 1$  is present, the output of A will be pulled to ground, and this level will be gated through B to C, the gate capacitor of which will now hold a "ground" charge.

With no negative stored on its gate, C will not turn on when its load is enabled by  $\phi 2$ , and the output gated through D will be the negative we started with delayed by one clock period.

Dynamic registers may seem pretty useless at a first glance because they cannot stand still and must keep their contents moving, but in fact there are many occasions when this is not a disadvantage.

When this is so the dynamic register has several points in its favour. First, it is about twice as fast in operation than the static type; secondly, because the loads are clocked, at low frequencies the power consumption of each cell is extremely low, typically 10 microwatts at 10kHz. This last feature is due to the fact that power is only dissipated when the gate capacitors are charged, which makes the power consumption frequency dependent. At 1MHz a power drain of 1 milliwatt per bit is common.

## APPLICATIONS

MOS circuits are still in their infancy, but are certain to be one of the most important advances ever to be made in the world of data processing and allied fields. Their biggest impact will be in the consumer area, and it will not be long before our homes will have the benefit of a "domestic" computer made possible by the advent of cheap MOS LSI.

A home computer could become adaptable to the telephone (which has push button dialling) so that by ringing our own number from a remote call box, and then dialling a coded message, we could instruct the computer to cook the dinner or turn on the central heating. At work the desk calculator could replace the slide rule, giving answers to all arithmetic problems at the touch of a few keys, and electronic digital test equipment such as frequency counters and digital voltmeters will shrink to pocket size.

On the way home in our car, exhaust emission will be nullified by electronic fuel injection, and the wheels will be unable to lock and skid because of another electronic system. Relaxing in our home we will be able to programme the hi fi system to soothe us in any way we fancy without leaving our armchair or sorting through piles of records.

All these things are possible now, but it will be MOS which makes them economically viable for the many.

## AVAILABLE MOS I.C.'s

Many readers may be hoping for some MOS circuits which are available to do a practical job in

amateur projects right now. Talk of dual 100-bit shift registers in a TO-5 can will, perhaps, only interest those who like to build, or dream about, the amateur built computers of the future.

MOS circuits of simple nature are beginning to appear, and, as an example, look at a couple of Marconi-Elliott i.c.s which are intended for use in electronic organs, the MA60 and the MA70. These two devices are housed in TO-5 cans and operate from -26V. Inputs and outputs are compatible with DTL and TTL.

The MA60 contains six binary dividers arranged as two chains of three, each chain has three outputs, divide-by-two, four, and eight. If the two chains are used in series, a total division of 64 is obtained. The MA60 is shown in Fig. 10.7.

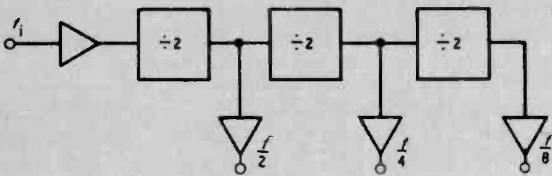


Fig. 10.7. Block diagram of the MA60 i.c. divider

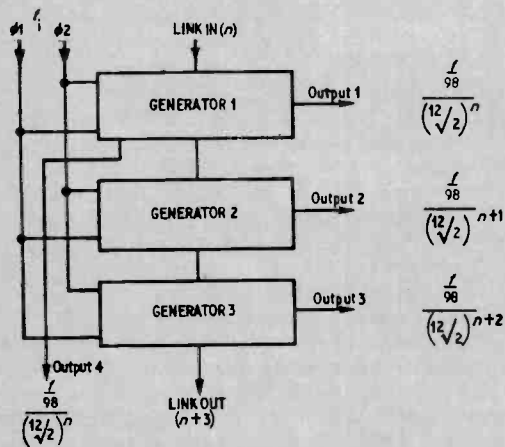


Fig. 10.8. Block diagram of the MA70 i.c. divider

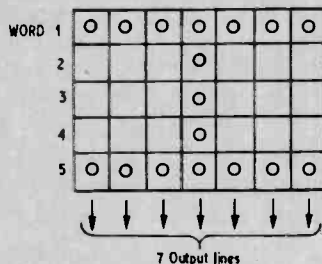


Fig. 10.9. Display programme for one character (letter H) of the Texas read-only memory

The MA70 is rather more complex than the previous device and is intended to produce three separate semitones from a single oscillator. MA70 can be cascaded if required, and when used in conjunction with the MA60 they enable complex organs to be built on a single p.c.b. The block diagram is given in Fig. 10.8.

These are circuits available to amateurs, and they do give a hint of MOS capabilities, but to get a glimpse of advanced applications, it is necessary to return to computer and process control electronics which are finding that MOS memories are becoming increasingly attractive.

## COMPUTER MEMORY CIRCUITS

In the past the main memory in a computer has been built using ferrite core matrices, or core stores. This type of memory is of the "random access" type, as it is possible to address any location and read or write into it immediately.

Another type of memory used is the magnetic drum, which provides bulk storage but which is rather slower to address because the revolving drum may have to make a complete revolution before the correct data location is available.

Some memories are programmed during manufacture by the wiring in of diodes where data is required, these are used as fixed programmes to control computer sub-routines, or sometimes as "tables" to store constants. These memories are of the "read-only" type, and cannot be written into.

MOS LSI techniques are now being used to simulate all three of these memory systems, and the solid state versions are proving to be superior on many counts. As an example, the Texas TMS-2A-4824-MH read-only memory contains 2,240 bits of data which are programmed during manufacture to provide the information necessary to produce 64 alphabetical and numerical characters on a c.r.t. display.

Each character is stored as five seven-bit words which are used to modulate a dot matrix on the tube face. Fig. 10.9 shows how one of the characters is stored and formed. When a particular dot location has to be brightened up on the display a "one" is stored in the memory, each dot position is displayed in sequence, and the information to be displayed is used to address the correct character location.

This type of circuit can also be programmed to customer requirements to contain any information required, a set of sine tables for example, or a sequence programme for an industrial machine.

## DEVELOPMENTS

MOS technology is being continuously improved, and these improvements are making this type of circuit ever more easy to use.

"Silicon gate" MOS devices are now being made with threshold voltages low enough so that they can be driven directly from bipolar logic, without the need for the voltage interface circuits that were necessary with the earlier types. The silicon gate technique uses polycrystalline silicon instead of aluminium for the gate electrode, and apart from giving lower threshold voltages, this also reduces the capacitance inherent in the construction and allows higher operating speeds.



# COMPLETE STEREO SYSTEM

FOR ONLY

**£40.95**  
CARRIAGE £1.75



**PREMIER STEREO SYSTEM "ONE"** Consists of an all transistor stereo amplifier. Garrard 2025 T/C auto/manual record player unit fitted stereo/mono cartridge and mounted in teak finish plinth with perspex cover and two matching teak finish loudspeaker systems. Absolutely complete and supplied ready to plug in and play. The 10 transistor amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector. Power on/off, stereo/mono switch. Brushed aluminium front panel. Black metal case with teakwood ends. Size 12 x 5 1/2 x 3 1/2 in. high (Amplifier available separately if required **£14.95**. Carr. 40p).

## PREMIER STEREO SYSTEM "TWO"

As system "ONE" above but with Garrard SP25.

**PREMIER PRICE £47** Carr. £1.75


## MIDLAND AM/FM STEREO TUNER AMPLIFIERS

Two new all solid state receivers from Midland at economical prices. Beautifully styled in slimline cabinets.

	Model 19-520	Model 19-542
Specifications	19 transistors, 12 diodes, 2 conductors 2 variators	22 transistors, 12 diodes
Tuning range	FM 88-108 MHz FM Stereo Multiplex AM 535-1635 kHz	FM 88-108 MHz FM Stereo Multiplex AM 535-1635 kHz
Aerial	Internal AM and external FM	Internal AM and external FM
Frequency Response	50-17,000 Hz	35-20,000 Hz
Power Output	2 1/2 watts rms per channel (8 watts music power)	4 watts rms per channel (18 watts music power)
Inputs	Ceramic phono	Magnetic/Ceramic phono and aux.
Speaker impedance	4-8 ohm	8 ohm
Controls	Power on/off, Volume, tone, balance, tuning, AFC, Stereo indicator	On/off, Volume, bass, treble, balance, tuning, AFC, Stereo indicator
Function	AM, FM, FM Stereo, Phono (Stereo indicator light)	AM, FM, FM Stereo, Ceramic, Magnetic, Aux.
Size	15" 8 1/2" 3 1/2"	16 1/2" 9 1/2" 3 1/2"
PRICE	<b>£30.45</b> Carr. & Ins. 50p	<b>£44</b> Carr. & Ins. 50p



MODEL 19-520

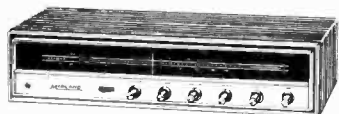


MODEL 19-542

## PREMIER STEREO SYSTEM "SIX" SAVE OVER £16

Comprises Midland AM/FM Stereo Tuner Amplifier Model 19-542. Pair of loudspeaker systems as System "ONE" Garrard SP25 Mk. III fitted Goldring 8850 Stereo Cartridge with teak plinth and cover. Total rec. list price over £91.

**PREMIER PRICE £75** Carr. & Ins. £1.75
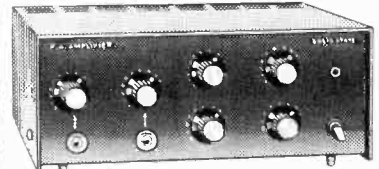
## 50 WATT PUBLIC ADDRESS AMPLIFIER MODEL PA-5000



A top quality amplifier giving 50 watts rms power output (80W peak). Incorporates 8 transistors and 4 silicon diodes (silicon output transistors). Inputs for 2 microphones each with individual volume controls, plus phono/aux input. Master volume control and Bass and Treble Controls. Well presented front panel for ease of operation, on/off power flick switch and pilot light. Output impedance 4/8/16 ohms Mike 1 and 2 sensitivity 2mV (50k Ohm). Phono/Aux 300mV (100k Ohm). Frequency response 50-20,000Hz. Padded output and thermal overload protection. A.C. Mains 220-250V, 50/60Hz. Size 13 1/2 x 9 in x 5 in.

**PREMIER PRICE £39** P. & P. 50p

## E.M.I. 13x8in. HI-FI SPEAKERS

Fitted two 2in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new.

**£3.47** P. & P. 40p



## VERITAS V-149 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 6 3/4 x 3 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phono plugs output. Attractive teak wood grain finish case.

**Mono £3 Stereo £3.47** P. & P. 12p



## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2in. speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

**£2.47** P. & P. 25p

STEREO STETHOSCOPE SET Low imp. **£1.25**. P. & P. 10p  
MONO STETHOSCOPE SET Low imp. **52p**. P. & P. 10p

**POCKET SIZE MULTI-TESTER** With wide angle, jewelled meter movement, ceramic long-life, low-loss wiring, tough impact resisting case. Sensitivity 20,000 ohms/volt D.C. 10,000 ohms/volt A.C.  
19 Ranges: 0-5-25-50-250-500-2500 volts D.C. 0-10-50-100-500-1000 volts A.C. 0-30µA-25mA-250mA. D.C. 0-6000 ohms-6 megohms, 10µF-0.001 mid-1 mfd. -20 to +22dB. Complete battery, test lead and instructions.

**£4.90** P. & P. 17p



## SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring 8850 Magnetic Stereo Cartridge. Complete in Teak Plinth with Rigid Perspex Cover.

Total list Price over £29.  
**PREMIER PRICE £19.90**  
P. & P. 50p

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped - attractively boxed.

LP3 3' 250' P.V.C.	28p	LP8 5 1/2' 1200' P.V.C.	62p
TT3 3' 450' POLYESTER	37p	DT8 5 1/2' 1800' POLYESTER	£1.12
DT3 3 1/2' 800' POLYESTER	57p	TT6 3 1/2' 2400' POLYESTER	£1.87
SP5 5' 900' P.V.C.	42p	SP7 7' 1200' P.V.C.	82p
LP5 5' 900' P.V.C.	50p	LP7 7' 1800' P.V.C.	75p
DT5 5' 1200' POLYESTER	75p	DT7 7' 2400' POLYESTER	£1.25
		TT7 7' 3600' POLYESTER	£2.50

TAPE SPOOLS 3' 5p, 5', 5 1/2', 7' 9p.  
Post and Packing 3' 5p, 5', 5 1/2' 8p, 7' 10p. (3 reels and over Post Free.)



## TAPE CASSETTES

C60 (60 min.)	37p	3 for £1.05
C90 (90 min.)	62p	3 for £1.80
C120 (120 min.)	87p	3 for £2.55

P. & P. 5p

All cassettes can be supplied with library cases at 3p extra each.

# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451



# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	2N711	0-50
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-25
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15		
BFY50	0-20		
BSY25	0-57		
BSY26	0-13		
BSY27	0-13		
BSY28	0-13		
BSY29	0-13		
BSY95A	0-15		
OC41	0-13		
OC44	0-13		
OC45	0-13		
OC71	0-13		
OC72	0-13		
OC73	0-17		
OC81	0-13		
OC81D	0-13		
OC83	0-20		
OC139	0-13		
OC140	0-17		

OC20	0-50
OC23	0-30
OC25	0-25
OC26	0-25
OC28	0-30
OC35	0-25
OC36	0-37
AD149	0-30
AUY10	1-25
2S034	1-25
2N3055	0-63
Diodes	
AA42	0-10
OA95	0-10
OA79	0-09
OA81	0-09
IN914	0-07

## FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## CLEARANCE LINES

DON'T MISS THIS LAST CHANCE ONLY A FEW LEFT UHF/VHF T.V. TUNER UNITS TU.2 CONTAINING 2 AF186's & 2 AF178's PRICE 50p. P. & P. 13p EACH UNIT

All the units have many other components, e.g. Capacitors, Resistors, Coils and tuning condensers, etc. Although these are manufacturers' rejects they are not beyond repair as has been proven by many of our customers.

ALL TUNER UNITS ARE SUPPLIED WITH CONNECTION DATA

## COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

ONLY £1 each post and packing 23p.

## SPECIAL LINE

1 AMP Bridge rectifiers 2in Square 100 PIV. = 25p. 400 PIV. = 33p. 800 PIV. = 40p.

PAK F.3. 13p  
Complementary Set. PAIR  
NPN/PNP Germ. Trans.

## BUMPER BUNDLES

These parcels contain all types of surplus electronic components, printed panels, switches, potentiometers, transistors and diodes, etc.

2 LBS IN WEIGHT FOR £1  
Post and packing 23p.

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0-3 to 0.5V, 0.5 to 2mA.	50p
B77	2	AD161-AD162 NPN/PNP Trans. Comp. Output, Pair	50p
B81	10	Reed Switches, mixed types large and small	50p
B89	2	5SP5 Light Sensitive Cells. Light Res. 400Ω Dark 1MΩ	50p
B91	8	NKT163/164 PNP Germ. TO-5 equivalent to OC44, OC45	50p
B92	4	NPN, Sil. Trans. AO6 = BSX20, 2N2369 500MHz, 360mW	50p
B93	5	GET113 Trans. equiv. to ACY17-21 PNP Germ.	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
B98	10	XB112 and XB102 equiv. to AC126, AC156, OC81/2, OC71/2, NKT271, etc.	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OCF71 Light Sensitive Photo Transistor	50p

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "D" NPN Silicon planar, plastic TO-18 case. Audio preamplifier or 500mW output stage, of the BC113/4/5 range.
- TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.

## RETURN OF THE UNBEATABLE P.I PAK.

NOW GREATER VALUE THAN EVER

FULL OF SHORT LEAD SEMICONDUCTORS AND ELECTRONIC COMPONENTS, APPROX. 170. WE GUARANTEE AT LEAST 30 REALLY HIGH QUALITY FACTORY MARKED TRANSISTORS PNP AND NPN, AND A HOST OF DIODES AND RECTIFIERS MOUNTED ON PRINTED CIRCUIT PANELS. IDENTIFICATION CHART SUPPLIED TO GIVE SOME INFORMATION ON THE TRANSISTORS.

PLEASE ASK FOR PAK P.I ONLY 50p  
10p P. & P. on this Pak.

Make a Rev. Counter for your Car. The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

## FREE CATALOGUE AND LISTS for:—

ZENER DIODES  
TRANSISTORS, RECTIFIERS  
FULL PRE-PAK LISTS  
& SUBSTITUTION CHART

MINIMUM ORDER 50p CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR AIRMAIL.

P.O. RELAYS **8 FOR £1**  
Various Contacts and Coil Resistances. No individual selection. Post & Packing 25p

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series "alloy" pnp Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

**SPECIAL OFFER**  
**GERMANIUM BRIDGE RECTIFIERS**  
**GEX 541 FINNED**

SINGLE PHASE 12 Amp. 48 Volts | THREE PHASE 18 Amp. 74 Volts

Ideal for Battery Chargers or Power Units

Offered at fraction of makers' cost Only **63p** Each  
Post & Packing 13p.

FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS

**BI-PRE-PAK LTD** DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
TELEPHONE: SOUTHEND (0702) 46344

The RCA COS-MOS family uses both *n*- and *p*-channel MOS f.e.t.s on the same chip, providing circuits that will run from 5V positive supplies with extremely low quiescent power consumption and a speed of up to 5MHz.

The latest introduction to the MOS field is a processing system which uses low temperature doping by bombardment with ions. This process is rather complex and expensive at present but it produces circuits which will operate at the same sort of speed as TTL, a great improvement.

### PRACTICAL POINTS

MOS devices come in a wide range of package outlines, especially the more complex circuits which require large numbers of pins. Hermetically sealed packages are almost universally used, because the normal MOS chip needs to be well protected from contamination, and this rules out the simple plastic

d.i.l. packages. The TO-5 can is very popular because this style can provide enough pins, and for the more complex devices a type of ceramic d.i.l. package, or a flatpack is employed.

### PRECAUTIONS WHEN HANDLING

Because of the extremely high input impedance of the MOS, it is possible for a static charge on the gate to exceed the breakdown voltage of about 60V, and so short out the silicon dioxide layer and ruin the device. Some circuits use protective Zener diodes to prevent this, but it is advisable to be sure by consulting the data sheet. Leakage from an un-earthed soldering iron could provide the minute current necessary to destroy a device. It is often recommended that pins should be shorted together whilst in store, to prevent static build up.

### Next month: Emitter Coupled Logic (ECL)



ONE OF the extra pleasures for the electronics enthusiast going abroad is the chance to observe the effect of electronics on daily life abroad, particularly if one can stay for any length of time in a foreign household. This I was privileged to do recently—just over the channel.

It is very interesting to see high-definition French television on 819 or 625 lines and note the clarity and excellence of the picture as well as the fact that the French programme directors are as hard put as ours to fill the screen with sixty minutes of excellence per hour.

It was interesting for me to meet two French clergymen-schoolmasters, who are fervent radio amateurs, and to visit their "shacks" from where they work the world on 2 metres. Incidentally, I did not know before that for this amateur band the French authorities do not require proficiency in morse; merely the equivalent of the City & Guilds written examination.

### APPLIED ELECTRONICS

In the line of applied electronics the Continentals are not slow to make use of the automation made possible by modern techniques. It is probably now well known that in the Renault factories most of the production of major parts, such as the boring of engine cylinder blocks, is performed and controlled by electronically based automative processes.

At the other end of the scale I recently noticed a most effective use for the light-controlled relay that has done so much to automate town-lighting systems, lift doors, car parking lights and the rest. I went into the "Messieurs" in a newly completed and finely appointed hotel in Montreux, Switzerland

and, on approaching the sanitary porcelain, noticed, coming from a metal panel in the wall, the unmistakable "clack" of a well fed relay slamming shut. The noise coincided with a flush of clean water where it would do most good. On looking down, I noticed that my calves had interrupted a light beam aimed at a photo-cell in the side wall and, presumably, the relay thus activated had turned on a plunger-tap

### GAS LIGHTER

Another gadget I noticed in three separate French households I stayed in this year was a new form of gas lighter, driven direct from the mains. The lighter looks like a small, six inch long, plastic torch, with a perforated brass cap where the light bulb should be and a press-button switch on one side. When Madame wishes to light the gas ring, she takes this little "torch", applies the perforated head to the burner and presses the button. The lighter produces a noise like a rattle-snake and a bright spark inside the head immediately lights the gas.

Enquiries in two households as to how this device worked drew shrugs, no solid information, and no enthusiasm in response to my wish to take it to pieces. Finally, in the third family I met sympathy—from the clergyman ham, who affirmed that it worked like an electric bell, but was dissuaded from dismantling it there and then by his sister, who kept house for him. However, I was later able to obtain such a lighter, and no sooner had I returned to my home den than I took it to pieces and found that it does, indeed, work like an electric bell, as my friend had said.

The d.c. resistance of the coil in the specimen examined was 150 ohms, wound from 42 s.w.g. wire. At 230 volt mains a current of about 1.5 amp is broken at the contact bosses and for such slender wire, the sheer temerity of the concept might at first appear alarming. It must be remembered, however, that with such a healthy spark the gas is lit immediately, so that the button switch is released after a few seconds and no fuses blow.

Anyway, these lighters are in use in thousands of French homes, are on general sale at the equivalent of approximately 37 $\frac{1}{2}$ p each and their construction must therefore be presumed to have the approval of Electricité de France, the central electricity authority of France. ★



# BOOK REVIEWS

## TAPE RECORDERS

H. W. Hellyer  
Published by Fountain Press  
239 pages, 8½ in × 5½ in. Price £2.25 (45s)

WRITTEN by the author of the Tape Recorder Servicing Manual, this, in like vein, is an essentially practical book that sets out to educate the reader painlessly into tape recorder techniques and simple maintenance.

From an opening chapter sketching the birth, development and growth prospects, the author embarks on a very readable breakdown on machine principles, naming of parts and functions, all being punctuated with some valuable workshop observations.

Guidelines to recorder and microphone choice will no doubt appeal to prospective buyers although it seems the yardstick axiom of "You only get what you pay for" must eternally prevail.

Chapters on maintenance for both tape and deck are very well illustrated. A final chapter on tests and measurements embraces choice of service equipment, bench tips and typical measurement hook-ups for determining wow and flutter, distortion levels and signal to noise ratios, etc.

All in all, a must for any user of tape recorders, as it affords a useful reference that is very easily dipped into. G.G.

## FOUNDATIONS OF WIRELESS AND ELECTRONICS Eighth edition

By M. G. Scroggie B.Sc., C.Eng., F.I.E.E.  
Published by Iliffe Books  
521 pages, 8½ in × 5½ in. Price £3 (60s)

THERE must be thousands who have built their hobby, or even their career, upon Mr. M. G. Scroggie's "Foundations". First published in 1936, this well known work has re-appeared in new editions from time to time. The present edition, the eighth, is noteworthy for the addition of "electronics" to the title. This is justified by the inclusion of two new chapters providing brief but useful accounts of such subjects as waveform generators and computers.

Apart from this extension of its range, the general character and arrangement of the book has not changed over much, and wireless transmission and reception remains the dominant theme. But much of the material has been completely re-written, and semi-conductors have now nearly, but not entirely, ousted thermionic valves.

Those not already familiar with Mr. Scroggie's classic can be assured that no previous knowledge of radio or electronics is assumed. The text excels in clarity and exposition, and there is little demand upon mathematics. Starting with first principles of electricity and circuit elements, the book proceeds to electronic devices, both thermionic and semiconductor, and explains their function in straightforward descriptive terms. Only in chapter 12 does the going become tough (as the author warns the reader) when transistor and valve equivalent circuits are evolved. Full understanding of this chapter is not, however, vital at the elementary stage.

The application of all the foregoing principles is demonstrated with stage by stage description of the various processes involved in a radio communications system. The principles of cathode ray tubes, television and radar are also outlined.

The two new chapters provide a sound, concise introduction to the many other uses of electronics which stem mainly from pulse switching techniques, as distinct from the generation, detection, and amplification of sinusoidal signals. F.E.B.

## RADIO VALVE AND TRANSISTOR DATA

Compiled by A. M. Ball  
Published by Butterworth & Co. Ltd.  
232 pages, 10½ in × 8½ in. Price £0.75 (15s)

SUBSTANTIALLY revised and added to, this is the ninth edition of a very popular reference on valve and semiconductor electrical characteristics.

Additions to the previous contents list are colour tubes, f.e.t.s, tunnel diodes and i.c.s, the latter including both digital and linear references.

Full marks must be given for the choice of a larger type face in the data presentation. This has meant, inevitably, some considerable pruning in obsolete device information, so don't just throw away that older edition as it will prove to be a valuable complement.

I suppose that in a work of this nature, errors can occur, but those that I found are inexcusable.

In the Amplifier Triodes section, the headings  $g_m$  and  $r_a$  should be transposed. The data for the PCC89 given in the Mullard Valve Data Book includes the description "Variable-mu frame-grid double triode".

In the Integrated Circuits section, the pin layout diagrams (p.199) do not include identification of mode connections. If one has to refer to manufacturers' data for this, then there was little point in including the technical data. It should also be made clear which view is shown in the drawings.

Finally, it would be very much easier to locate transistor types on the data pages if some semblance of alphabetical order were adopted. G.G.

## BEGINNERS GUIDE TO RADIO Seventh Edition

By Gordon J. King  
Published by Newnes-Butterworths  
194 pages, 7½ in × 5 in. Price £1

THIS book is an updated version of an original of the same title by F. J. Camm, it is not just a rewrite in parts but a completely new book. The author's explanations of the basic principles are excellent and this book would prove useful to all studying electronics as well as basic radio. It is unfortunate that most of the work is based on valve theory and practice, however the radio principles are unaffected by this and there is a useful section on transistor theory and function and some transistor circuits are given and described in the text.

Sections 11 and 12 are concerned with "Disc Record Players and Radiograms" and "Hi-Fi Reproduction". Although these items may seem rather out of context under the title of this book they are both worthwhile sections describing the principles involved and giving block diagrams of the systems.

A selection of circuit symbols is given at the front of the book together with a brief description of each and lists of abbreviations and a wavelength/frequency conversion table are given at the back. Also included is an index of words and terms described in the text. M.K.

# LOW COST ELECTRONIC & SCIENTIFIC EQUIPMENT & COMPONENTS

## MOTORS

### CONTINUOUS TAPE CASSETTE

Suitable for sleep-learning, teaching programmes, programming machine tools, telephones answering, etc. Complete with replay/record head and separate erase head; 1/2 in tape single track. Speed 3 1/2 in per sec. Length of tape 88ft, but will hold three times this amount, 230V 50Hz supply. **£4.50.** Post free.

### DIGITAL INDICATORS KGM TYPE M3

A neat compact indicator providing selective display 0-9. Fig. Ht. 18mm. Panel mounting. 6mm tubular midjet flange lamps. Supplied with 28V bulbs. Finished matt black anodized. W. 1in, H. 2in, Wt. 4oz. **£3.25.** Post free.

### SINGLE SPEED TAPE DECK

1/2 in single track on 7in spools. 1 1/2 in per sec. 3 motors. Capstan 240V, others 130V. Series operated. Facility for remote control operation. Recording heads with separate erase head. Ex equipment. Less spools. Bargain price **£5.95.** P. & P. 75p. Buy now while stock exists.

### KEYNECTOR

Connects anything electrical in seconds without plugs or sockets. No more worries about dangerous live wires. Now you can make electrical connections safely, in seconds with the revolutionary new KeyNECTOR. Cuts out plugs, sockets and saves time. A hundred different uses in the home, and a must for the do-it-yourself enthusiast. Only **£2.33** plus P. & P. 25p. Or send for a leaflet.

### GRAMPHON AMPLIFIERS

Type 385B. 50W mains powered. 200 ohm O/P. Audio Power Amplifiers. Only a few available. Selling at well below list price: **£15.50** each. Carriage £2.

### TELEPHONE DIALS

Clear Perspex, very good condition. No markings. **75p** each. P. & P. 25p.

### LOW TORQUE HYSTERESIS MOTOR MA23

Extremely quiet running motor with high starting torque. Has many uses such as chart drives, discoloration wheels, etc. 1/20 r.p.m., 1/12 r.p.m., 1 r.p.m., 120V 50Hz, 1/12, 1/18, 1/24, 1/240 r.p.m., 1/20, 1/60, 1/16, 1/15, 1 r.p.m., 20 r.p.m. **£1.50** post free.

### SYNCHRONOUS MOTORS

200/250V 50Hz. New condition, ex-equipment. 8.7 r.p.m. and 1 r.p.m. Self starting, complete with gearing shaft 1/2 in dia., 1/2 in long. **£1.50.**

### ELECTRIC CLOCK MOTOR

NEW 200-250V, 50Hz, 3W. Synchronous induction motor. 2 revs. per hour. O/P shaft, 1/2 in dia., 1/2 in long. Clockwise rotation. Three-holed mounting at 120° on 2 1/2 in PCD. Price **£1** post free.

**GOOD QUALITY INSTRUMENTS TAKEN IN PART EXCHANGE OR PURCHASED FOR CASH!**

## BRAND NEW CAPACITOR REVERSIBLE SINGLE PHASE PARVALUX MOTORS

230/250V, 50Hz, 2,800 r.p.m.; 1/30 h.p. cont. rated; 1/2 in dia. shaft; 3 1/2 in long foot mounting; wt. 6lb. **£5.75.** Post free.

### E.H.T. GENERATOR. BRAND NEW D.C. CONVERTER MULLARD TYPE 1049

Input 12V d.c., 0-3A. Output 1,800V (min.) at 1mA, 2,500V (min.) on no load. Full spec. and circuit provided. Encapsulated module. L. 3 1/2 in, W. 2 1/2 in, H. 1 1/2 in. **£5.50.** Post free.

### DELAY LINE LEXOR MDN 2484D

Miniature resin encapsulated module. Total delay 50nsec to 10µsec. Tapped at 10% intervals. Impedance 75 ohms to 10 k.Ω. 30V wkg. Attenuation 0.5 dB/µsec. 2 1/2 in x 1 1/2 in x 2 1/2 in. **£1.50.** Post free.

### BATTERY OPERATED TRANSISTOR TESTER

Battery powered for checking leakage current and gain of P.N.P. transistors, meter and audio indication. Siemens Erlawan Type R2925. W. 7 1/2 in, H. 4 1/2 in, D. 2 in. **£5.50.** Post free.

### MEMORY CORE STORES

42 x 22. 2kΩ bit ferrite core store. C/W quantity OAI0 load diodes. Ideal for building computer stores, holding information, teaching experiments, demonstrations, etc. Price **£2.25.** P. & P. 38p.

### NEW ENICRON SHADED POLE MOTORS

240/250V, 50Hz, 2,500 r.p.m. (no load). Shaft 1/2 in dia, x 1 1/2 in long. Suitable record player, blower motor, etc. **65p.** Post free.

### NEW FRACTIONAL H.P. CAPACITOR MAINS MOTORS

230V, 50Hz, 0.65A, 1/20 h.p., 2,850 r.p.m. Cont. rated. Shaft 1/2 in dia, x 2 1/2 in long. Circular clamp mounting. **£3.50.** Post free.

### AVOMETERS

These well-known portable test instruments have been overhauled and are offered complete with leads, crocodile clips and probes.

Model D	£14
Model 40, 47A, 48A	£16
Model 7	£17
Model 7X	£19.50
Model 8	£23
Model 8X	£23
Model 11R	£20

Model 48A complete with voltage multiplier for 480V and 3600V. Current shunts for 120A and 480A. A.C. Current transformer for 20A and 60A. In special wooden box. 47A and 48A are Admiralty patterns of the model 40. **£16.75.** P. & P. 75p.

### RESET TIMERS — ACRO TIMER BY HAYDON

Synchronous motor driven timer providing manual adjusted delay. Delay time is set on graduated dial. Press button closes contact and drives motor which drives an arm until it actuates the load switch. The arm then returns to initial position for repeat action. Various ranges available. 230V 50Hz. Load contacts 1.5A 230V. **£5.**

### WIDE RANGE OF PRECISION MULTI-TURN POTENTIOMETERS IN STOCK

### TACHOMETERS

Instruments by Smiths. Incorporating 4 mechanically selected ranges of 500, 1,000, 5,000 and 50,000 r.p.m. Within 2% accuracy, supplied with accessories and carrying cases. A neat and compact instrument. Bargain at **£19.50.** P. & P. 25p.

## MEMORY PLANES

Ferrite core memory planes with wired Ferrite cores. Used for building your own computer or as an interesting exhibit in the demonstration of a computer. Mounted on plastic material, frame 5 x 8in. Consisting of matrices 40 x 25 x 4 cores each one individually addressable and divided into 2 halves with independent sense and inhibit wires. **£6.50.** P. & P. 15p.

### LINEAR THYRISTOR CONTROLLED LIGHT DIMMER—BRAND NEW

High grade full wave bridge circuit gives linear control of light brightness. Ideal for controlling room lighting and a.c./d.c. commutator motors fitted to portable electric hand drills. Fits standard 2in conduit box. 240V, 50Hz, 400W. Price **£2.99.** P. & P. 13p.

### MINIATURE MOVING COIL RELAY 5115

By Sangamo Weston, suitable for D.C. circuit. A high sensitivity relay more sensitive than the electromagnetic type. Single Coil Resistance 310 micro amps. 315Ω. List price **£4.50.** Our price **£1.15.**

### 6 DIGIT RESETTABLE COUNTER

Totalising 240V 50Hz. Viewing window 2 1/2 x 2 1/2 in. Ex-equipment. Price **£2.75.** P. & P. 25p.

### 6 DIGIT TOTALISING NON-RESETTABLE COUNTER

Mechanical operation. Chromium finish. Length 1 1/2 in x 2 1/2 in x 2 1/2 in with viewing window 1 1/2 x 1 1/2 in. Ex-equipment. Price **48p.** P. & P. 13p.

### BERKELEY DECIMAL COUNTING UNIT 0-9

Direct reading octal base plug in unit electronic counter. The number counts received is indicated by one of ten neon lamps behind acetate panel. The unit counts from 0-9, the tenth pulse resetting to zero and simultaneously generating an o/p signal. Circuits can be connected in cascade. Power supply 6.3V d.c. Cut on/Cut off 15V. Price **£3.50** p. & p. free.

### MINIATURE DIGITAL DISPLAY

Operates on a rear projection 6.3V pilot lamp. Character size 1/2 in high. 0-9 digits with 0-9 symbol, i.e. (4'). Dimensions 1 in wide, 3/2 in deep, 1 1/2 in high. List price 6 gns. Our price **£2.73.**

1in characters **£3.**  
4in characters **£9.** Post free.

### EAC DIGIVISOR Mk. II DIGITAL READ-OUT DISPLAY

Uses a sensitive moving coil movement to project digits 0-9 on to a viewing screen via an optical lens system. Image height 1/2 in. Lamp 6.3V. Sensitivity 250 micro-amp Dimensions L. 4 1/2 in, W. 2 1/2 in, H. 1 1/2 in. Price **£3.50.** P. & P. 25p.

## OVERHAULD AVOMETERS

Models 40, 47A, 48A. (Models 47A and 48A are Admiralty pattern.) D.C. volts: 0-12, 1.2, 12, 120, 480, 1,200. A.C. volts: 12, 120, 480, 1,200. Amps: 0-0.12, 0-1.2, 1.2, 12. Ohms: 1,000, 10,000. Ohms/Volt when divided by two button is pressed on both a.c. and d.c. ranges. **£18.** P. & P. 75p. Complete with voltage multiplier for 480V and 3,600V. Current shunts for 120A and 480A. A.C. current transformer for 20A and 60A. In special wooden box. **£18.50.** P. & P. £1.

Due to demand it may not always be possible to supply a particular model, and a different type to that ordered may be dispatched. These models are electrically identical.

### STOCK CLEARANCE

All items are sold in as seen condition. **CREED MORSE RECEIVERS.** Model 7B. **£15.** Carriage £3. **OSCILLOSCOPE COSSOR 1038.** £10. Carriage £3. **OSCILLOSCOPE EMI TYPE WM3 PORTABLE.** £15. Carriage £2. **VALVE VOLTMETER.** Fuzehil 3781B/2. 1mV, 5 ranges. **£3.50.** Post free. **UHF SIGNAL GENERATOR.** RCA Type 710-A, I/P 117V, 60Hz, 50W. 370-560 MHz modulation. Carrier (metered) scaled O/P. **£15.** Carriage £1. **VALVE VOLTMETER.** Marconi FT248, a.c./d.c. 5 ranges 1.5V. **£3.** Carriage **£1.50.**

### WIDE RANGE OSCILLATOR.

Daves type 400C. 0.1Hz-1kHz. O/P control. C.R.T. monitor. **£10.** Carriage **£2.50.** **ONE ONLY—Type 400A.** 20Hz-20kHz. O/P control (metered). O/P Z 500, 600, 2,000 ohm. **£2.** Carriage **£2.50.** **VALVE VOLTMETER CT54 MICOVAC.** A.C./D.C. plus ohms. 5 ranges, 2.4-480V. 1kΩ-10MΩ in 5 ranges. Probe facility battery powered. Very good condition. **£18.** Carriage **£1.** **VOLTMETER "AS NEW"** Ex G.P.O. Superior quality 5in moving coil 200 ohms/volt. A.C./D.C. 0-150V and 0-300V. Mirror scale. Ernest Turner Model 32 in teak carrying case. 10 1/2 in x 8 1/2 in x 4 1/2 in. **£10.** Post free.

### MIDGET POWER RELAY ONRON Mk I

230V, 50Hz. IPDT unused. Faulty painting on frame. **5 for £1.50.** Post free.

### NUMICATOR PRICE LIST

Quantity	Price each (less base)
1-3	£1.40
4-10	£1.35
11-25	£1.30
26-100	£1.20

Price Base. Bases 20p each.

Side Reading

XN3/FA	38m/m Lead	(Amber)
XN3/F	38m/m Lead	(Red)
XN3A/F	6m/m Lead	(Red)
XN3A	6m/m Lead	(Clear)
XN11/F	38m/m Lead	(Red)
XN23/FA	38m/m Lead	(Amber)
1-3	£1.15 each	
4-10	£1.10 each	
11-25	£1.05 each	
26-100	95p each	

All Post Free

### NEW LOW INERTIA INTEGRATING MOTORS

Electro-Methods Models 901 and 906PL. Permanent magnet d.c. motor. High sensitivity. Ideal for instrument-type servo mechanisms, light loads, driving mechanical counters performing integration, or as small power generators. Will operate directly off a photo-cell or thermocouple, etc. Nominal typical parameter. Starting voltage (no load) 10mV at 0.375mA. Full load speed 1,845 r.p.m. (approx.). Moment of inertia of armature 1.8g. cm/cm. Weight of Motor 300g. (approx.). **£15.** P. & P. included.

### RAPID HEAT SOURCE . . .

from brand new Infra Red Tubular Quartz Lamps. Ideally suited as heat source for Drying Ovens, Egg Hatching, Incubators, etc., 240V, 1,440V, 20,000 Angstroms. Length 12in x 1/2 in dia. Price **75p.** P. & P. 25p.

**ELECTRONIC BROKERS LTD.**  
(Dept. PE), 49-53 PANCRAS RD · LONDON NW1  
01-837 7781 · TELEX 267307  
Open Mon.—Fri. 9—6 p.m.

# Sinclair Project 60



the world's most advanced high fidelity modules

**Sinclair Project 60** presents high fidelity in such a way that it meets every requirement of performance, design, quality and value and now that the remarkable phase lock loop stereo FM tuner is available, it becomes the most versatile of high fidelity systems. With Project 60, it is possible to start with a

modest mono record reproducer and expand it to a sophisticated stereophonic radio and record reproducing system of fantastically good quality to hold its own with any other equipment, no matter how expensive. Project 60 is a unique high fidelity module system where compactness and ease of assembly are combined with

circuitry that is far in advance of any other manufacturer in the world. Thus it is extraordinarily easy to assemble any combination of modules using nothing more complicated than the simplest of tools, and you certainly do not have to be experienced to build with complete confidence. The 48 page manual free with Project 60 equipment makes everything easy and you can house your assembly in an existing cabinet, motor plinth, free standing cabinet or virtually any arrangement you wish. Once you have completed your assembly you will have superlatively good equipment to give you years of service and enjoyment. You will have obtained superb value for money because Project 60 is the best selling modular system in Europe and can therefore be produced at extremely competitive prices and with excellent quality control.

Sinclair Radionics Ltd., London Road, St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311


**sinclair**

System	The Units to use	together with	Cost of Units
A Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
B Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
C 20+20 W. R.M.S. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., most dynamic speakers, F.M. tuner etc.	<b>£23.90</b>
D 20+20 W. R.M.S. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner. Tape Deck, etc.	<b>£26.90</b>
E 40+40W. R.M.S. de-luxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains trsfmr</b>	As for D	<b>£34.88</b>
F Outdoor P.A. system	<b>Z.50</b>	Mic., up to 4 P.A. speakers controls, etc.	<b>£5.48</b>
G Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>
H High pass and low pass filters	<b>A.F.U.</b>	C, D or E	<b>£5.98</b>
J Radio	<b>Stereo F.M. Tuner</b>	C, D or E	<b>£25.00</b>



# Sinclair Project 60

## Z.30 & Z.50 power amplifiers

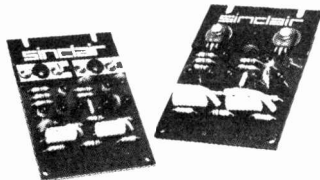

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z50 units are interchangeable with Z.30s in all applications).**  
**Power Outputs**

Z.30 15 watts R.M.S. into 8 ohms using 35 volts;  
 20 watts R.M.S. into 3 ohms using 30 volts.

Z.50 40 watts R.M.S. into 3 ohms using 40 volts;  
 30 watts R.M.S. into 8 ohms, using 50 volts.

**Frequency response:** 30 to 300 000 Hz  $\pm$  1dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB un-weighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

Size  $3\frac{1}{2} \times 2\frac{1}{2} \times \frac{1}{2}$  in.

Z.30

Built, tested and guaranteed with circuits and instructions manual


**£4.48**

Z.50

Built, tested and guaranteed with circuits and instructions manual.

**£5.48**

## Power Supply Units

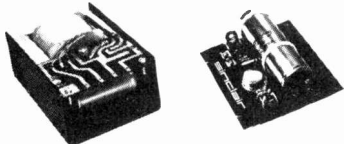

Designed specially for use with the Project 60 system of your choice.

Illustration shows PZ.5 to left and PZ.8 (for use with Z.50s) to the right. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.

**PZ-5 30 volts un-stabilised £4.98**

**PZ-6 35 volts stabilised £7.98**

**PZ-8 45 volts stabilised**


(less mains transformer) **£7.98**

**PZ-8 mains transformer £5.98**

## Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

## Stereo 60 pre-amp/control unit

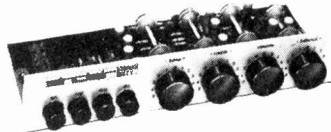

Designed for the Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.

### SPECIFICATIONS

**Input sensitivities:** Radio—up to 3mV. Mag. p.u. 3mV; correct to R.I.A.A. curve  $\pm$  1dB; 20 to 25,000 Hz. Ceramic p.u.—up to 3mV; Aux—up to 3mV.

**Output:** 250mV

**Signal-to-noise ratio:** better than 70dB.

**Channel matching:** within 1dB.

**Tone controls:** TREBLE + 15 to -15dB at 10KHz; BASS + 15 to -15dB at 100Hz.


**Front panel:** brushed aluminium with black knobs and controls.

**Size:**  $8\frac{1}{2} \times 1\frac{1}{2} \times 4$  in.

Built, tested and guaranteed.

**£9.98**

## Active Filter Unit

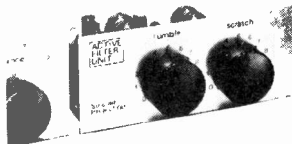

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two stages of filtering are incorporated—rumble (high pass) and scratch (low pass). Supply voltage - 15 to 35V. Current - 3mA. H.F. cut-off (-3dB) variable from 28kHz to 5kHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1kHz (35V. supply) 0.02% at rated output.

Built, tested and guaranteed

**£5.98**

## Stereo FM Tuner



### first in the world to use the phase lock loop principle

Before production of this tuner, the phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio over other systems. Now, for the first time, the principle has been applied to an FM tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Sensitivity is such that good reception becomes possible in difficult areas. Foreign stations can be tuned in suitable conditions and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

### SPECIFICATIONS:

**Number of transistors:** 16 plus 20 in I.C.

**Tuning range:** 87.5 to 108 MHz

**Capture ratio:** 1.5dB

**Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for full limiting.

**Squelch level:** 20 $\mu$ V.

**A.F.C. range:**  $\pm$  200 KHz

**Signal to noise ratio:** >65dB

**Audio frequency response:** 10Hz—15KHz ( $\pm$ 1dB)

**Total harmonic distortion:** 0.15% for 30% modulation

**Stereo decoder operating level:** 2 $\mu$ V

**Pilot tone suppression:** 30dB

**Cross talk:** 40dB

**I.F. frequency:** 10.7 MHz


**Output voltage:** 2 x 150mV R.M.S.

**Aerial impedance:** 75 Ohms

**Indicators:** Mains on; Stereo on; tuning indicator

**Operating voltage:** 25-30 VDC

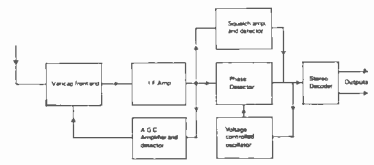**Size:** 3.6 x 1.6 x 8.15 inches; 91.5 x 40 x 207 mm



Price: **£25** built and tested. Post free

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

\_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

for which I enclose cash/cheque/money order.

Name

\_\_\_\_\_

Address

\_\_\_\_\_

\_\_\_\_\_

# Sinclair IC10/Q16/Micromatic

## IC10



### The world's most advanced high fidelity amplifier

This is the world's first monolithic integrated circuit high fidelity power amplifier and pre-amplifier. The circuit itself is a chip of silicon only a twentieth of an inch square by one hundredth of an inch thick, having 5 watts RMS output (10 watts peak). It contains 13 transistors (including two power types), 2 diodes, 1 zener diode and 18 resistors, and is encapsulated in a solid plastic package which holds the metal heat sink and connecting pins. This exciting device is more rugged and has considerable performance advantages, including complete freedom from thermal runaway and a very low level of distortion. The IC10 is primarily intended as a full performance high fidelity power and pre-amplifier, for which application it only requires the addition of such components as tone and volume controls and a battery or mains power supply. It may also be used in other applications including car radios, electronic organs, servo amplifiers (it is dc coupled throughout) etc.


### Circuit Description

The first three transistors are used in the pre-amp and the remaining 10 in the power amplifier. Class AB output is used with closely controlled quiescent current which is independent of temperature. There is generous negative feedback round both sections and the amplifier is completely free from crossover distortion at all supply voltages, making battery operation eminently satisfactory. Each IC10 is sold with a comprehensive manual giving circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include oscillators, etc. The pre-amp section can be used as an RF or IF, amplifier without any additional transistors.

### Specifications:

Output: 10 watts peak, 5 watts RMS continuous  
 Frequency response: 5Hz to 100kHz  $1 \pm$  dB.  
 Total harmonic distortion: Less than 1% at full output.  
 Load impedance: 3 to 15 ohms.  
 Power gain: 110 dB (100,000,000,000 times) total.  
 Supply voltage: 8 to 18 volts. (A Sinclair power unit, PZ.7 is available for mains operation).  
 Size: 1 x 0.4 x 0.2 in. plus heat sink and tags.  
 Sensitivity: 5 mV.  
 Input impedance: Adjustable externally up to 2.5 Mohms.  
 Price (with manual) **59/6** (£2.97½) post free.

## Q16

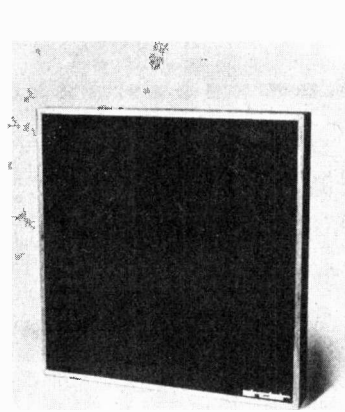

### High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

### Specifications:

Construction: Special sealed seamless sound or pressure chamber with internal baffle.  
 Loading: up to 14 watts TMS.  
 Input impedance: 8 ohms.  
 Frequency response: From 60 to 16,000 Hz, confirmed by independently plotted B and K curve.  
 Driver unit: Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and a special cone suspension for excellent transient response.  
 Size and styling: 9½ in square on face x 4½ in. deep with neat pedestal base. Black all-over cellular foam front with natural solid teak surround.  
 Price **£8.19.6**. (£8.97½).

## Micromatic



### Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute and attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

### Specifications:

Size: 36 x 33 x 13 mm ( $1\frac{1}{5} \times 1\frac{3}{10} \times \frac{1}{2}$  in.)  
 Weight: including batteries, 28.4 gm (1 oz.).  
 Case: Black plastic with anodised aluminium front panel and spun aluminium dial.  
 Tuning: medium wave band with bandspread at higher frequencies. (550 to 1,600 Hz).  
 Earpiece: Magnetic type.  
 On/off switching: By inserting and withdrawing earpiece plug.  
 Kit in pack with earpiece, case, instructions and solder **49/6** (£2.47½).  
 Ready built, tested and guaranteed, with earpiece **59/6** (£2.97½).  
 Two Mallory Mercury batteries type RM675 required. From radio shops, chemists, etc.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_ for which I enclose cash/cheque/money order.

PE.4

Sinclair Radionics Ltd., London Road  
 St. Ives, Huntingdonshire PE17 4HJ.  
 Tel: St. Ives (046 06) 4311

**sinclair**

# YOURS FREE FOR 7 DAYS



## The 'New Picture-Book' way of learning BASIC ELECTRICITY (5 VOLS.) BASIC ELECTRONICS (6 VOLS.)

You'll find it easy to learn with this outstandingly successful NEW PICTORIAL METHOD—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on the latest research into simplified learning techniques. This has proved that the PICTORIAL APPROACH to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

... able to understand the basic facts ... This is the first time I have been able to understand the basic facts ... L.P., Edenbridge.

... these manuals are my biggest asset ... I am delighted to tell you that these manuals are my biggest asset, a possession that I shall never part with ... S.A., Davenport.

... they live up to your publicity in every way ... I am pleased to write and say that your manuals live up to your publicity in every way ... L.D.N., Liverpool.

A TECH-PRESS PUBLICATION

**POST NOW FOR THIS OFFER!!**

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP

Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. BASIC ELECTRICITY £4.50. Cash Price on Down Payment of £1 followed by 4 fortnightly payments of £1 each (Total £5). BASIC ELECTRONICS £5.40. Cash Price or Down Payment of £1 followed by 5 fortnightly payments of £1 each (Total £6). This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)

BASIC ELECTRICITY  BASIC ELECTRONICS

Prices include Postage and Packing.

Signature .....  
(If under 18 signature required of parent or guardian)

NAME .....  
BLOCK LETTERS  
FULL POSTAL  
ADDRESS .....

**LOW VOLTAGE AMPLIFIER** Few only at **£1-75**  
5 transistor amplifier complete with volume control, is suitable for 8V d.c. and a.e. supplies. Will give about 1W at 8 ohm output. With high I.M.P. input this amplifier will work as a record player, baby alarm, etc., amplifier.

plus 12½p P. & P.




**ACOS STETHOSET.** 200 ohm d.c. Res. stetho- set complete with 5ft. of wire. Ideal for private listening on radio and tape recorder. These stethosets are made to very high standards, they are used but in good condition and are all guaranteed. Well below original Price at 30p plus 7½p P. & P.



**CRESCENT RADIO LTD.**  
11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

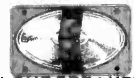**MAIL ORDER DEPT.**  
No. 11 MAYES RD. LONDON N22 6TL



**EMI LOUDSPEAKER 450**  
10W 13in x 8in — two 2½in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp. **£3-25** plus 37½p P. & P. each.

### PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 600W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18-50** plus 37½p P. & P.



If you require more information please send S.A.E.



### SHelf UNIT

Two teak finish shelves on a black frame (overall size: 28in x 25in x 12in). Ideal for hi fi equipment: amplifiers, speaker cabinets, etc. The perfect answer for housing unit audio and equipment. This unit is wall mounting. **£2-50** plus 37½p P. & P.

**EMI LOUDSPEAKER 150**  
10 watts, 13 x 8 base unit. Plus a flared centre cone. Designed to handle the higher frequencies. Please state imp required. 3.8.15Ω. A bargain at **£2-50** plus 37½p P. & P. each.

**BATTERY ELIMINATOR**  
Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.e. mains through this compact eliminator. 2½in, 2in, 3in approx. 4½V **£1-50, 6V £1-50, 9V £1-50, 7½V** complete with cable and plug for Philips Cassette. **£2** plus 7½p P. & P. each.



**CRESCENT CASSETTES**  
Top quality cassettes at unbeatable prices (complete with standard storage case): C60 37½p, C90 62½p, C120 87½p plus 5p P. & P.

**HIGH QUALITY IMPORTED HEADPHONES**  
1,000Ω per phone ... **80p** TTC  
2,000Ω per phone ... **87½p** G1105  
Plus 10p P. & P. per pair.



**MAINS KEYNECTOR**  
Keynector connects any Electrical Equipment to the mains supply in seconds. Ideal for bench, garage, demonstrations, etc. Multi connections can be made (max. load 13A fused). **ONLY £2-32½** P. & P. Free on this item.



**BARGAIN BOARDS**  
Components galore for the experimenter. Ex computer boards with: Resistors, Capacitors and useful Transistors—at least 4 transistors per board. **BARGAIN PRICE 30p** per board 5 BOARDS **£1-20**. P. & P. Free on this item.



**BRIGHTNESS CONTROL**  
Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a MK. Box. Enjoy the pleasure of having the precise amount of light you require at any time. Our Price **£2-75** plus 5p P. & P. each.



**STEREO HEADSET**  
8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2-50** plus 10p P. & P.  
**STEREO JUNCTION BOX**  
For stereo amplifiers without stereo jack socket. **£1-25** plus 7½p P. & P.



**CHROME TV STAND**  
28in 8½in 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at: **£1-62½** plus 25p P. & P.




**WE HOLD THE LARGEST STOCK OF RETAIL COMPONENTS IN LONDON — SEND S.A.E. FOR FREE LISTS**

**Our new shop now open at 13 SOUTH MALL, EDMONTON, N.9**  
carries our complete stock of electronic components and hi-fi


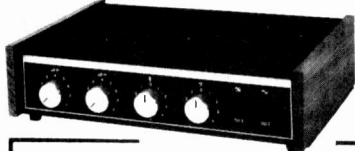
## HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response —3dB 12-30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ±3dB 12-15,000Hz. Bass boost approx. 10dB. Treble cut approx. —16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide 8" deep × 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES** AMPLIFIER KIT. £10.50 P. & P. 15p. POWER PACK KIT. £3 P. & P. 25p. CABINET. £3 P. & P. 25p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discoteque use, etc.*

**FANTASTIC 'POLY PLANAR' WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER**

Size only 1 1/2" × 1 1/2" × 1 1/2" deep. Weight only 10 ozs. Can replace cone speakers in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature —20°F to +125°F. Power handling 10 watts rms (20 watts peak). Impedance 8 ohm only. Response 40 Hz—20 KHz. Can be mounted on ceilings, walls, doors, under tables, etc. and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

**MAGNAVOX DESK TYPE MOVING COIL MICROPHONE.** Medium impedance. Brand New—Special Price £2.10. P. & P. 10p.

**SINGLE HEADPHONE.** With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p.

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity. 95p. P. & P. 8p.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.05. P. & P. 8p.

**HIGH IMPEDANCE DYNAMIC STICK MIKES.** High sensitivity. £1.95. P. & P. 13p.

**PIANO KEY TYPE SWITCHES.** 8 press buttons plus 1 cancel button. Each of the 8 sections contains 62 contacts (total 40 s.p.c.o.). Brand new—limited quantity only. Original manufacturing cost £1.37. OUR PRICE 75p. P. & P. 13p (3 or more post free).

**SPECIAL OFFER! PLESSEY TYPE 29 TWIN TUNING GANG.** 400pF + 145pF. Fitted with trimmers and 5:1 integral slow motion. Suitable for nominal 470 kc/s. I.F. Size approx. 2 × 1 × 1/2 in. Only 43p. P. & P. 13p.

**HONEYWELL MICROSWITCHES S/P. C/O.** Push-button action. Rating 250V. AC at 15 amps. Size approx. 1 1/2 in. × 3/4 in. × 1/2 in. 25p each. P. & P. 5p (6 or more post free).

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 6 section telescopic. Brass. Extends from 6in. to approx. 22 1/2 in. Maximum diameter 1/2 in. 25p each. P. & P. 5p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: Sec. 10-0-10 to 2 amp. £1.85. P. & P. 18p. Tapped Primary 200-220-240V. Sec. 21-5V at 500mA. 65p. P. & P. 13p.

**BATTERY CHARGER TRANSFORMERS.** 200/240V. input. Nominal output for 6 or 12V. batteries 3 amps. Size approx. 3 × 2 1/2 × 2 1/2 in. Brand New. Price £1.05. P. & P. 20p.

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2 in high × 10 1/2 in wide × 8 1/2 in deep. Fitted with E.M.I. Ceramic Magnet 13in × 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £8.40**

Carr. 50p.  
Also available in 8 ohm with EMI 13in × 8in. bass speaker with parasitic tweeter. £6.50. Carr. 50p.

### LOUDSPEAKER BARGAINS

3in 4 ohm 50p. P. & P. 13p. 5in 3 ohm 80p. P. & P. 15p. 7 × 4in 3 ohm £1.05. P. & P. 20p. 10 × 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 × 5in 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13 1/2 × 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 × 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" × 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

**BRAND NEW.** 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with Hiflux ceramic ferrobar magnet assembly £5.50. P. & P. 38p. Guitar models: 25w £6.50. 35w £8.50.

**E.M.I. 3in HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3, 8 or 15 ohm 98p each. P. & P. 13p.

**12in "RA" TWIN CONE LOUDSPEAKER**  
10 watts peak handling. 3 or 15 ohm. £1.88. P. & P. 30p. **35 OHM SPEAKERS.** 3in 70p. P. & P. 13p.

### HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2 in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. PRICE £2.95. P. & P. 15p.

**GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER.** For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 × 1 1/2 × 1/2 in. Brand new—complete with instructions. Price 85p. P. & P. 13p.


**BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST.** Fitted mono t/o stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.

**QUALITY RECORD PLAYER AMPLIFIER MK II**  
A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. × 3 d. × 6 h. Ready built and tested. PRICE £3.75. P. & P. 30p. ALSO AVAILABLE mounted on board with output transformer and speaker ready to fit into cabinet below. PRICE £4.98. P. & P. 38p.

**DE LUXE QUALITY PORTABLE B/P CABINET MK II**  
Uncut mono board size 14 1/2 × 12in. clearance 2in. below. 5 1/2 in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 × 10 × 8 1/2 in. PRICE £3.98. P. & P. 48p.
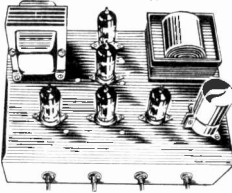
### 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF96 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately, ONLY £7.97. P. & P. 43p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 43p.




A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF96 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately, ONLY £7.97. P. & P. 43p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 43p.

**BRAND NEW TRANSISTOR BARGAINS.** GET 15 (Matched pair) 75p; V15/10p, 50p; OC71 25p; OC76 30p; AF117 18p; 2U339 (NPN) 15p. Set of Mullard 6 transistors OC44, 2—OC45, AC128D, matched pair AC128 £1.25; ORP12 Cadmium Sulphide Cell 55p. All post free.

**VERY POWERFUL COMPACT MOTOR**  
For 12v. D.C. operation. Off load consumption approx. 100mA. Totally enclosed. Quiet in operation with high starting torque. Overall size approx. 1 1/2" L × 1 1/2" dia. Free shaft 3/8" dia. × 3/16" L. Ideal for Model Makers, etc. ONLY 35p each. P. & P. 5p.  
3 or more post free (A few 6p. versions also available).

**HIGH GRADE COPPER LAMINATE BOARDS**  
8 × 6 × 1/4 in. FIVE for 50p. P. & P. 10p.

## DE LUXE STEREO AMPLIFIER

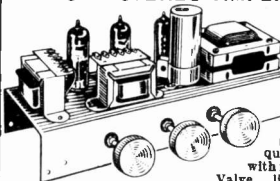

A.c. mains 200-240 volts. Using heavy duty fully insulated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2 × ECL86 Triode Pentodes. 1 × E280 as full wave rectifier. Two dual potentiometers are provided for bass and treble control, giving bass treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knob chassis size 11in. w × 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. Price £2.92. P. & P. 40p.

**4-SPEED RECORD PLAYER BARGAINS**  
Main models. All brand new in maker's packing. **LATEST B.S.R. G109/A2 4-SPEED AUTOCHEANGER.** With latest mono compatible cartridge £9.97. Carr. 33p. With stereo cartridge £7.97. Carr. 33p. **SUITABLE PLINTH UNIT FOR ABOVE** with rigid plastic cover. £5.75 complete. P. & P. 43p. **LATEST GARRARD MODELS.** All types available 1025, 1025, SP25, 3000, AT60, etc. S.A.E. for Latest Prices! **FLINTH UNITS** cut out for Garrard models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.75 complete. P. & P. 43p.

**LATEST ACOS GP91/18C Mono Compatible Cartridge** with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p. **ACOS HI-G Single sided mono cartridge** for LP & EP. ONLY 50p. Post Free. **SONOTONE PHONO COMPATIBLE STEREO CARTRIDGE** T10 stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p. Also available fitted with twin Diamond T10 stylus for Stereo LP. ONLY £3. P. & P. 10p. **STEREO BONETTE T/O Stereo Compatible Cartridge** for EP/LP/Stereo/78. £1.63. P. & P. 10p. **LATEST BONETTE T/O Mono Compatible Cartridge** for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

**HIGH GAIN 4 TRANSISTOR PRINTED CIRCUIT AMPLIFIER KIT**  
**TYPE TAI**  
Peak output in excess of 11 watts. All standard components. Built on printed circuit panel size 6 × 3in. Generous size Driver and Output Transformers. Output transformer tapped for 3 ohm and 15 ohm speakers. Transistors (GFT114 or 81 Mullard AC 128D and matched pair AC128 9p). 9 volt operation. Everything supplied, wire, battery clips, solder, etc. Comprehensive easy to follow instructions and circuit diagram 13p (Free with Kit). All parts sold separately. SPECIAL PRICE £2.48. P. & P. 15p. Also ready built and tested, £2.75. P. & P. 15p.

**3-VALVE AUDIO AMPLIFIER HA34 MK II**  
Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2 in. × 4 1/2 in. × 4 1/2 in. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 30p.

**HL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 30p.

**HARVERSON'S SUPER MONO AMPLIFIER**  
A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3 1/2 watts. Volume and tone controls. Chassis size only 7in. wide × 3in. deep × 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY.

**OUR ROCK BOTTOM BARGAIN PRICE** £2.75 P. & P. 30p

Open 9-5.30 Monday  
to Saturday  
Early closing Wed. 1 p.m.  
A few minutes from South West London  
Tube Station

## HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTE BRITISH U.K. ONLY. P. & P. OVERSEAS ORDERS CHARGED EXTRA.



who wants a **£2,000+p.a.** opportunity in the dynamic new computer industry?

In only **4 weeks** you're in – and only the incredible **Eduputer** can make it possible.

Now for the first time anybody can train **outside** the computer industry for a lucrative career as a computer operator, **with actual experience on an Eduputer.**

**Who created Eduputer?** The internationally famous company Programming Science International. They developed it to the specific requirements of the massive New York city training board and its practical results have been one amazing success story.

We are proud to have been selected as the only commercial training organisation permitted to use the Eduputer in the U.K. **Thanks to Eduputer, nine out of every ten can learn to operate the most advanced computers in only four weeks. Unlike Computer Programming, no special educational qualifications and no maths required. Just you and the incredible Eduputer!**

**Jobs galore!** The moment you qualify, our exclusive computer appointments bureau introduces you to computer users everywhere with good jobs to offer (up to £40 a week full-time, £50 a week as a temporary). More than enough to go round, too—because 144,000 new operators will be needed over the next five years alone.

This is your big opportunity to get out of a rut and into the world's fastest-growing industry. And remember—LCOT is the only commercial computer school to have Eduputer. It means a lot to employers.

**Telephone: (01) 734 2874 NOW!**

**Or post the coupon today for full details FREE and without obligation.**



**London Computer Operators Training Centre,**  
C22, Oxford House, 9/15 Oxford Street, London, W.1.  
Telephone (01) 734 2874.

127/131 The Piazza, Dept. C22, Piccadilly Plaza, Manchester 1.  
Telephone (061) 236 2935.

Please send me your free illustrated brochure on exclusive Eduputer "hands on" training for computer operating.

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel.: \_\_\_\_\_



## BI-PAK = LOW COST I.C.'s

**NOW LOWER THAN EVER PRICES—GREATER RANGE**

BI-PAK Semiconductors offer you the largest and most popular range of I.C.'s available at these **EXCLUSIVE LOW PRICES.** TTL Digital 74N Series fully coded, brand new. Dual in-line plastic 14 and 16 pin packages.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24	25-99	100 up
		£p	£p	£p
BP00 = 7400	Quadruple 2-input NAND gate	0-23	0-20	0-15
BP01 = 7401	Quadruple 2-input positive NAND gate (with open collector output)	0-23	0-20	0-15
BP02 = 7402	Quadruple 2-input positive NOR gates	0-23	0-20	0-15
BP03 = 7403	Quadruple 2-input positive NAND gates (with open-collector output)	0-23	0-20	0-15
BP04 = 7404	Hex Inverters	0-23	0-20	0-15
BP10 = 7410	Triple 3-input positive NAND gates	0-23	0-20	0-15
BP13 = 7413	Dual 4-input Schmitt trigger	0-35	0-32	0-29
BP20 = 7420	Dual 4-input positive NAND gates	0-23	0-20	0-15
BP30 = 7430	8-input positive NAND gates	0-23	0-20	0-15
BP40 = 7440	Dual 4-input positive NAND buffers	0-23	0-20	0-15
BP41 = 7441	BCD to decimal nixie driver	0-87	0-77	0-67
BP42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-87	0-77	0-67
BP47 = 7447	BCD-seven-segment decoder/drivers (15V outputs)	1-40	1-30	1-20
BP50 = 7450	Expandable dual 2-input and-or-invert	0-23	0-20	0-15
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-23	0-20	0-15
BP53 = 7453	Quad 2-input expandable and-or-invert	0-23	0-20	0-15
BP54 = 7454	4-wide 2-input and-or-invert gates	0-23	0-20	0-15
BP60 = 7460	Dual 4-input expander gates	0-23	0-20	0-15
BP70 = 7470	Single-phase J-K flip-flop	0-35	0-32	0-29
BP72 = 7472	Master-slave J-K flip-flop	0-35	0-32	0-29
BP73 = 7473	Dual master slave J-K flip-flop	0-43	0-40	0-37
BP74 = 7474	Dual D type flip-flop	0-43	0-40	0-37
BP75 = 7475	Quad latch	0-47	0-45	0-43
BP76 = 7476	Dual J-K with pre-set and clear	0-87	0-77	0-67
BP78 = 7480	Gated full adders	0-87	0-77	0-67
BP81 = 7481	16-bit read/write memory	1-35	1-25	1-15
BP82 = 7482	2-bit binary full adders	1-30	1-20	1-00
BP83 = 7483	Quad full adder	0-87	0-77	0-67
BP86 = 7486	Quad 2-input exclusive or gates	0-80	0-70	0-60
BP90 = 7490	BCD decade counter	0-87	0-77	0-67
BP81 = 7491	Divide-by-twelve counters	1-21	1-00	0-87
BP93 = 7493	4-bit binary counters	0-87	0-77	0-67
BP94 = 7494	Dual entry 4-bit shift register	0-87	0-77	0-67
BP95 = 7495	4-bit up-down shift register	0-87	0-77	0-67
BP96 = 7496	5-bit parallel in parallel out shift register	1-10	1-00	0-90
BP100 = 74100	8-bit bistable latches	1-75	1-65	1-55
BP118 = 74118	Hex set-reset latches	1-30	1-20	1-00
BP121 = 74121	Monostable multivibrators	0-87	0-77	0-67
BP141 = 74141	BCD-to-decimal decoder/driver	0-87	0-77	0-67
BP145 = 74145	BCD-to-decimal decoder/drivers	1-80	1-70	1-60
BP151 = 74151	8-bit data selectors (with strobe)	1-40	1-30	1-20
BP153 = 74153	Dual 4-line-to-1-line (data selectors/multiplexers)	1-40	1-30	1-20
BP191 = 74191	Binary counter reversible	3-50	3-25	3-00

**PRICE-MIX.** Devices may be mixed to qualify for quantity prices.

**PRICES** for quantities in excess of 500 pieces mixed, on application.

Data is available for the above Series of Integrated Circuits in booklet form, price 13p.

### TTL INTEGRATED CIRCUITS

Manufacturers' "Full out"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7430N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC50 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC61 = 12 x 7431N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC78 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p
	UICX1 = 25 x Ass'd 74's £1-50	

Packs cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries our BI-PAK Satisfaction or money back GUARANTEE.

### BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	1-24	25-99	100 up
BP 201C—SL201C	TO-5	8	G.P. Amp	63p	58p	45p
BP 701C—SL701C	TO-5	8	OP Amp	63p	58p	45p
BP 703C—SL703C	TO-5	8	OP Amp Direct OP	63p	58p	45p
BP 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p	45p	40p
BP 709—72709	D.I.L.	14	High OP Amp	53p	45p	40p
BP 709P—µA709C	TO-5	8	High Gain OP Amp	53p	45p	40p
BP 711—µA711	TO-5	10	Dual comparator	58p	50p	45p
BP 741—72741	D.I.L.	14	High Gain OP Amp (Protected)	75p	60p	50p
µA 703C—µA703C	TO-5	6	R.F.—I.F. Amp	43p	35p	27p
TAA 263—	TO-72	4	A.F. Amp	70p	60p	55p
TAA 293—	TO-74	10	G.P. Amp	90p	75p	70p

RTL MICROLOGIC CIRCUITS			Dual-in-Line Low Profile Sockets		
Epoxy TO-5 case	Price each		14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits		
uL900 Buffer	35p	33p 27p			
uL914 Dual 2i/p gate	35p	33p 27p			
uL923 J-K flip-flop	50p	47p 45p			
Data and Circuits Booklet for I.C.'s	Price 7p.				
			Price each		
Order No.	1-24	25-99	100 up		
T80 14 pin type	30p	27p	25p		
T80 16 pin type	35p	32p	30p		

### BI-PAK SEMICONDUCTORS

P.O. BOX 6, WARE, HERTS.

Postage and packing add 7p. Overseas add extra for Airmail. Minimum order 50p. Cash with order please. Giro No. 398-7006.



# VALUE ALL THE WAY

## NEW LOW PRICE TESTED S.C.R.'s

PIV	1A		3A		7A		10A		16A		30A	
	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66
50	0-23	0-25	0-47	0-50	0-47	0-50	0-53	0-53	0-75	0-75	1-13	1-13
100	0-25	0-33	0-53	0-58	0-58	0-63	0-83	0-83	1-40	1-40	1-40	1-40
200	0-35	0-37	0-57	0-61	0-61	0-75	1-60	1-60	1-60	1-60	1-60	1-60
400	0-43	0-47	0-67	0-75	0-75	0-93	1-75	1-75	1-75	1-75	1-75	1-75
600	0-53	0-57	0-77	0-97	0-97	1-25	2-00	2-00	2-00	2-00	2-00	2-00
800	0-63	0-70	0-90	1-20	1-20	1-50	2-50	2-50	2-50	2-50	2-50	2-50

## SIL. RECTS. TESTED

PIV	300mA		750mA		1A		1.5A		3A		10A		30A	
	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66	TO-5	TO-66
50	0-04	0-05	0-05	0-07	0-14	0-21	0-21	0-47	0-47	0-47	0-47	0-47	0-47	0-47
100	0-04	0-06	0-05	0-13	0-16	0-23	0-75	0-75	0-75	0-75	0-75	0-75	0-75	0-75
200	0-05	0-09	0-08	0-14	0-20	0-24	1-00	1-00	1-00	1-00	1-00	1-00	1-00	1-00
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25	1-25	1-25	1-25	1-25	1-25	1-25	1-25
600	0-07	0-16	0-10	0-23	0-34	0-46	1-85	1-85	1-85	1-85	1-85	1-85	1-85	1-85
800	0-10	0-17	0-13	0-25	0-37	0-55	2-00	2-00	2-00	2-00	2-00	2-00	2-00	2-00
1000	0-11	0-25	0-15	0-30	0-46	0-63	2-50	2-50	2-50	2-50	2-50	2-50	2-50	2-50
1200	—	0-33	—	0-33	0-57	0-75	—	—	—	—	—	—	—	—

## TRIACS

VBOM	2A		6A		10A	
	TO-1	TO-66	TO-1	TO-66	TO-1	TO-66
100	0-50	0-63	1-00	1-00	1-00	1-00
200	0-70	0-90	1-25	1-25	1-25	1-25
400	0-90	1-00	1-60	1-60	1-60	1-60

**SILICON HIGH VOLTAGE RECTIFIERS**  
10-Amp 3-K.V. (3000 P.I.V.) Stud Type with Flying Leads, 80p each.

**DIACS WITH TRIACS**  
BR100... 37p each

## 2A POTTED BRIDGE RECTIFIERS 200V 50p

**UNIJUNCTION**  
UT46. Evt. 2N3646, Evt. T1843. BEN3000 27p each, 25-99 25p 100 UP 20p.

**NPN SILICON PLANAR**  
BC107/8/9, 10p each, 50-60, 9p; 100 up, 8p each; 1000 off, 7p each. Fully tested and coded TO-18 case.

## FREE

One 50p Pack of your own choice free with orders valued \$4. or over.

AF239 NPN GERM. SIEMENS VHF TRANS. SISTERS. RF MIXER & OSC. UP TO 900 MHZ. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USE IN VHF. OUR SPECIAL LOW PRICE—1-2437p each, 25-99 34p each 100 + 30p each.

## FET'S

2N 3819 ..... 35p  
2N 3820 ..... 83p  
MPF105 ..... 40p

## CADMIUM CELLS

ORP12 43p  
ORP60, ORP61 40p each

## PHOTO TRANS.

OCPT71 Type 43p

## EX-EQUIPMENT MULLARD

AF117 transistors. Large can 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

## SIL. G.P. DIODES

300mW 30... 0-50  
40PIV (Min.) 100... 1-50  
Sub-Min. 300... 5-00  
Full Tested 1,000... 9-00  
Ideal for Organ Builders.

## D13D1 Silicon Unilateral

switch 50p each. A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**ADI161 NPN**  
**ADI162 PNP.**

**MATCHED COMPLEMENTARY PAIRS OF GERM. POWER TRANSISTORS.**  
For main driven output stage of Amplifiers and Radio receivers. OUR LOWEST PRICE OF 63p PER PAIR

**HIGH POWER SILICON PLANAR TRANSISTORS, TO-3.**  
FERRANTI ZT1487

VCE160 Ic 6A PNP FT. 1M/cs  
VCE40 Ptot. 75W VEB8 hFE15-45  
PRICE 30p EACH

**2N3055 115 WATT SIL. POWER NPN**  
OUR PRICE 63p EACH

**FULL RANGE OF ZENER DIODES VOLTAGE RANGE 2-33V. 400mW (DO-7 Case) 13p ea. 11W (Top-Hat) 18p ea. 10W (80-10 Stud) 25p ea. All fully tested 75% tol. and marked. State voltage required.**

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed

Pak No. EQVT  
T1 8 2G371A OC71  
T2 8 2G374 OC75  
T3 8 2G374A OC81D  
T4 8 2G381A OC81  
T5 8 2G382T OC82  
T6 8 2G344A OC44  
T7 8 2G345A OC45  
T8 8 2G378 OC78  
T9 8 2G399A 2N1302  
T10 8 2G417 AF117  
All 50p each pack

**2N2080 NPN SIL. DUAL TRANS. CODE D1699 TEXAS.** Our price 25p each.

**180 VCB NIXIE DRIVER TRANSISTOR.** Sim. BRX21 & C407. 2N1893 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Evt. ZTX300 6p each. Any Qty.

## KING OF THE PAKS Unequalled Value and Quality

### SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0-50
U2	60 Mixed germanium transistors AF/RF	0-50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0-50
U4	40 Germanium transistors like OC81, AC128	0-50
U5	90 200mA sub-min. Sil. diodes	0-50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0-50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1,000V	0-50
U8	30 Sil. planar diodes 250mA, OA/200/202	0-50
U9	20 Mixed volts 1 watt Zener diodes	0-50
U11	30 PNP silicon planar transistors TO-5 sim. 2N132	0-50
U13	30 PNP-NPN sil. transistors OC200 & 28104	0-50
U14	150 Mixed silicon and germanium diodes	0-50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0-50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0-50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-50
U18	8 6-Amp silicon rectifiers BZY213 type up to 600 PIV	0-50
U19	25 Silicon NPN transistors like BC108	0-50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0-50
U21	30 A.F. germanium alloy transistors 2G300 series & OCT1	0-50
U23	30 Madt's like MAT series PNP transistors	0-50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0-50
U25	25 300Mc's NPN silicon transistors 2N708, BSY27	0-50
U26	30 Fast switching silicon diodes like 1N914 micro-min.	0-50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc. 8 assorted pieces	1-00
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1-00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0-50
U32	25 Zener diodes 400mW D07 case mixed volts, 3-18	0-50
U33	15 Plastic case 1 amp silicon rectifiers 1N4000 series	0-50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 28302/4	0-50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0-50
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	0-50
U37	30 Sil. alloy trans. SO-2 PNP. OC200 28322	0-50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0-50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0-50
U40	10 Dual trans. 6 lead TO-5 2N2060	0-50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0-50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117	0-50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

## GENERAL PURPOSE GERM., PNP POWER TRANSISTORS

Code1 GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR: 0K25-28-29 30-35-36. NKT401-403-404-405-406-407-408-409-410-411-412-413. T13027-3028, 2N250A, 2N456A-457A-458A, 2N511-511 A & B. 2G220-222. ETC. SPECIFICATION VCEO 80V VCE0 50V IC 10A PT 30 WATTS HFE 30-170. PRICE 1-24 25-99 100 up 43p each 40p each 36p each

## GENERAL PURPOSE SILICON NPN POWER TRANSISTORS

Code1 GP300. BRAND NEW TO-3 CASE. POSSIBLE REPLACEMENT FOR: 2N3055, BDY20, RBY11. SPECIFICATION VCEO 100V. VCE0 60V. IC 15AMPS. PT. 115 WATTS. Hie 20-100. FTI MHZ. PRICE 1-24 25-99 100 up 55p each 50p each 47p each

## GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N708/8, BSY27/28/95A.

All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

Code	Price
20 For	0-50
50 For	1-00
100 For	1-75
500 For	7-50
1000 For	13-00

**SURPLUS A.E.I. 40A GERM. JUNCTION RECTIFIERS.** For Power Applications  
Type G-P6C20 400PIV 40p each  
G-P6C30 600PIV 50p each

**ALL PRICES QUOTED IN NEW PENCE.**

Please send all orders direct to our warehouse and despatch department.  
**BI-PAK SEMICONDUCTORS**  
P.O. BOX 6, WARE, HERTS.  
Postage and packing add 7p. Overseas add extra for Airmail. Minimum order. 50p. Cash with order please.

## NEW QUALITY TESTED PACKS

Pack	Description	Price
Q1	20 Red spot trans. PNP	0-50
Q2	16 White spot R.F. trans. PNP	0-50
Q3	4 OC77 type trans.	0-50
Q4	6 Matched trans. OC44/45/81/81D	0-50
Q5	4 OC73 transistors	0-50
Q6	4 OC72 transistors	0-50
Q7	4 AC128 trans. PNP high gain	0-50
Q8	4 AC126 trans. PNP	0-50
Q9	7 OC81 type trans.	0-50
Q10	7 OC71 type trans.	0-50
Q11	2 OC127/128 comp. pairs PNP/NPN	0-50
Q12	3 AF116 type trans.	0-50
Q13	3 AF117 type trans.	0-50
Q14	3 OC171 H.F. type trans.	0-50
Q15	5 2N2926 sil. epoxy trans.	0-50
Q16	2 GET880 low noise germ. trans.	0-50
Q17	3 NPN 1 8T141 & 2 8T140	0-50
Q18	4 Madt's 2 MAT 100 & 2 MAT 120	0-50
Q19	3 Madt's 2 MAT 101 & 1 MAT 121	0-50
Q20	4 OC44 germ. trans. A.F.	0-50
Q21	3 AC127 NPN germ. trans.	0-50
Q22	20 NKT trans. A.F. R.F. coded	0-50
Q23	10 OA202 sil. diodes sub-min.	0-50
Q24	8 OA81 diodes	0-50
Q25	6 1N914 sil. diodes 75PIV 75mA	0-50
Q26	5 1N915 germ. diodes sub-min. 1N909	0-50
Q27	2 10A 600PIV sil. rects. 1S40R	0-50
Q28	2 Sil. power rects. BZY13	0-50
Q29	4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30	7 Sil. switch trans. 2N706 NPN	0-50
Q31	6 Sil. switch trans. 2N708 NPN	0-50
Q32	3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0-50
Q33	3 Sil. NPN trans. 2N1711	0-50
Q34	7 Sil. NPN trans. 2N2369, 600MHZ.	0-50
Q35	3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0-50
Q36	7 2N3646 TO-18 plastic 300MHZ NPN	0-50
Q37	3 2N3053 NPN sil. trans.	0-50
Q38	7 PNP trans. 4 x 2N3703, 3 x 2N3702	0-50
Q39	7 PNP trans. 4 x 2N3704, 3 x 2N3705	0-50
Q40	7 PNP amp. 4 x 2N3707, 2 x 3N3708.	0-50
Q41	3 Plastic NPN TO-18 2N3904.	0-50
Q42	6 NPN trans. 2N3172	0-50
Q43	7 BC107 NPN trans.	0-50
Q44	7 NPN trans. 4 x BC108, 3 x BC109.	0-50
Q45	3 BC113 NPN TO-18 trans.	0-50
Q46	3 BC112 NPN TO-5 trans.	0-50
Q47	6 NPN high gain 3 x BC167, 3 x BC168	0-50
Q48	4 BCY70 NPN TO-18	0-50
Q49	4 NPN trans. 3 x BFY51, 2 x BFY52	0-50
Q50	7 BSY28 NPN switch TO-18	0-50
Q51	7 BSY93A NPN trans. 300MHZ	0-50
Q52	8 BY100 type sil. rect.	1-00
Q53	25 Sil. & germ. trans. mixed all marked new	1-50

## PRINTED CIRCUITS—EX-COMPUTER

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards £3. P. & P. 30p.

## TRANSISTOR EQUIVALENTS BOOK.

A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 75p each.

## GERM. POWER TRANS.

Type	Price each
OC20	50p
OC22	30p
OC23	33p
OC24	25p
OC28	25p
OC29	40p
OC27	40p
OC28	33p
AD140	40p
AD142	40p
AD149	43p

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductor. All available Ex-Stock at very competitive prices.

# KING OF THE PAKS BI-PAK GUARANTEE SATISFACTION OR MONEY BACK

# Practical Electronics Classified Advertisements

RATES: 7½p per word (minimum 12 words). Box No. 7½p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

## MISCELLANEOUS

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for HOUSE-TO-HOUSE USE, SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'  
DEPT. K2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

**FASCIA PANELS**, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwicks.

## MUSICAL MIRACLES

**WAA-WAA Pedal**. Complete kit of all parts, robust cabinet, mechanism and instructions. Huge sales, well proven design. Only £2.45 complete. Or built and tested £4.75 post free. **Rhythm Box**. Build your own from our pre-built electronic circuit modules, e.g. box giving waltz, foxtro, etc., costs under £17. **Open Percussion units** £14. Bass pedal and other fascinating effects, fuzz, tremolo, etc. Send s.a.e. for list: D.E.W. LTD., 254 Ringwood Road, Ferndown, Dorset

## 12 VOLT FLUORESCENT LIGHTS

12 ins. 8 Watt tube ample light for caravan, tent, etc. Fully transistorised, low battery drain. Unbeatable at £3.27½ post paid

or in kit form £2.87½

## BIG BARGAIN PARCEL 75p

POST PAID

Containing multi-contact relay, transistors, resistors rectifiers, diodes, capacitors, pots, knobs, etc.

## 4 WATT GRAM AMPS.

Volume and tone controls, mains operation, 3Ω output, new and boxed £3.63 POST PAID

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop  
Shrewsbury, Shropshire S.A.E. for lists

## ORIGINAL DESIGNS

NEW IDEAS · PATENTS

Mechanical · Electronic  
Automotive

If you possess any of the above, suitable for mass production, contact one of Britain's oldest manufacturers of automobile accessories.

It could be financially rewarding

**SYDNEY RUSSELL LTD.**  
Wednesbury Road Works · Walsall  
Tel. 23144

## MISCELLANEOUS (continued)

### NEW! NEW!! NEW!!!

#### The Sweetest Sound You Ever Heard

An exciting new, all silicon, power amplifier module to a completely NEW design. Minimum cross-over distortion, not dependent on supply voltage, eliminates unpleasant "transistor sound". Specially designed to work well from simple, unregulated power supply, 50-58v. II transistors, short circuit proof, unconditionally stable, temperature stabilised. 400 m/v input for 30 watts RMS (8 ohms). Output impedance 8-16 ohms. Completely built on 16 swg heatsink. Neat, space-saving, upright mounting. Fully tested and guaranteed with comprehensive instructions.

£8.75 each. P. & P. 25p. Stereo pair. Post free

## ELECTRONIC SUPPLIES


P.O. BOX 148, SHEFFIELD S17 3EX

We stock all those components and materials required by the home Hi-Fi constructor, including speaker grille fabrics, BAF wadding, Peerless speaker kits, Helme Cabinet Kits, cross-over networks, inductors, etc. Special offers also available. Send stamps to value of 10 new pence NOW for your copy of our new fully illustrated catalogue (catalogue cost refunded against purchases over 50p). No callers please, mail-order ONLY.

**AUDIOSCAN** Dept. P.E.3  
4, PRINCES SQUARE,  
HARROGATE, YORKS.

**COMPONENTS, SPEAKERS, CABINETS, JG80** Speaker System, Bass Tweeter, teak case, £10.66. Garrard SP25 with cartridge, £15. Garrard 2025 with cartridge, £11.75. Plinths to suit, with cover, £5.25. Full details, list available, send S.A.E. Open Saturdays. J. & G. ELECTRONICS, 22a Baldock Street, Ware, Herts.

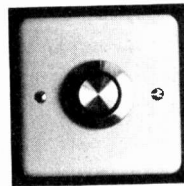"**DIRECTORY**". 450 parapsychical cases, Britain. Unusual electrical effects, £2. **PARALABORATORY**, Downton, Wilts.



THE  
NITE  
LITE

## Dimmerswitch

Will dim up to 400 watts of incandescent lighting from zero to full brilliance. This unit simply replaces the normal light switch, and is fitted in a matter of minutes. An MK mounting frame is supplied, for use when more depth is required.

PRICE: Complete Kit: £2.85 (12/3)  
Built & tested: £3.35 (12/3)

## Diathane Ltd.

111, Sheffield Road, Wymondham, NORFOLK.  
£0.10 postage & packing

## MISCELLANEOUS (continued)

**HOLIDAY FOR BOYS**. 14/16 years August 1971, specialising in engineering, electronics, photography. Tuition and practical work including karting. 11 days—£15. Write for free brochure: INTER-SCHOOL CHRISTIAN FELLOWSHIP, 47 Marylebone Lane, London, W1M 6AX.

**CLEARING LABORATORY**, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

**BUILD IT** in a DEWBOX quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

## PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"! DON'T PUT IT OFF! SEND 15p for your list—NOW

## BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY  
Designs by GERRY BROWN and JOHN SALMON  
and presented on TV

## WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London. W.7. 01-567 5400/2971.

**WE BUY NEW VALVES**. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

## TOP PRICES PAID

for new valves and components

Popular T.V. and Radio types


**KENSINGTON SUPPLIES**

(B) 367 Kensington Street  
Bradford 8, Yorks.

**HIGHEST CASH PRICES** for tape recorders. 9.30-5. Immediate quotations. 01-472 2185.
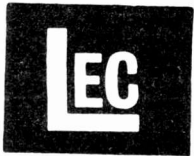
## LADDERS

**VARNISHED TIMBER LADDERS** from manufacturer, LOWEST PRICES anywhere: 15ft ext., £6.20; 17ft ext., £6.50; 20ft ext., £7; 21ft ext., £7.75; 24ft ext., £8.90; 29ft ext., £10.25; 31ft triple ext., £12.25; 36ft. triple ext., £16. Carr. 80p. Free Lists. Also Aluminium Ext. and Loft Ladders. Callers welcome. Dept. P.E. HOME SALES, Baldwin Road, Stourport, Worcs. Phone: 02-993 2574. Placing order on C.O.D.



# TELEVISION AND RADIO TRAINING

## (DAY ATTENDANCE COURSES)

This private College provides theoretical and practical training in Radio and TV Servicing. Courses of one year's duration, with daily attendance, are available for beginners and shorter courses for men with previous training in Electronics and Radio. Training courses in Radar and Radio Transmission are also available following the TV course. Write for prospectus to: London Electronics College, Dept. B/3, 20 Penywern Road, Earls Court, London, S.W.5. Tel. 01-373 8721.

### TAPE RECORDERS

**TAPE BARGAINS.** Double play AMPEX, 7in, 2,400ft reels, packed in RECOTAPE sealed boxes. Superb quality, fully guaranteed, 2 for **£2-87½**, 6 for **£7-50**. 5½in, 1,800ft reels as above, 2 for **£2-10**, 6 for **£5-37½**. 7in, 1,800ft L.P., 2 for **£2-07½**, 6 for **£6**. 5½in D.P., 1,800ft, 2 for **£2-27½**, 6 for **£6-50**. 5½in L.P., 1,200ft, 2 for **£1-37½**, 6 for **£3-87½**. Money back if not delighted. 12½p. P. & P. on all orders under £5. MUSIC TAPES MAIL ORDER, 36 High Street, Salisbury, Wilts.

### NOW SAVE ON CASSETTES

AUDEMAG Compact Cassettes, fully guaranteed top quality, in plastic boxes with giant 6 x 4 label giving double writing space.

	3	6	10
C80	£1.71	£2.71	£3.50
C90	£1.57½	£2.90	£5
C120	£1.92½	£3.87½	£6.50

12½p P. & P. on all orders under £3.

Money back if not satisfied.

MUSIC TAPES MAIL ORDER  
36 High Street, Salisbury, Wilts.

### RECEIVERS AND COMPONENTS

**A CORNUCOPIA OF COMPONENTS!** Scarce valves, selected TV components, speakers and cabinets. Computer panels—long leads, NOT printed circuits. Transistors, resistors—new and recovered. State your requirements. S.A.E. for details MAIL-MART, 6 Eastbourne Road, Pevensey Bay, Sussex.

**FULL SPECIFICATION TRANSISTORS:** Texas, S.G.S., etc. BC108B 11p; BC109C 12p; 2N3705 14p; BFY51 17p. 5p Postage S.A.E. List. GREENWELD, 24 Goodhart Way, W. Wickham, Kent.

**CAPACITORS.** Dubillier, 0.1µF 500V, 30p doz., £2-10 per 100. Hunts 0.04µF 500V, 15p doz., £1 per 100; 0.001µF and 0.005µF 350V, 15p doz., £1 per 100. Skeleton Presets, 2KΩ, 6p, Co-ax Sockets on isolation panel, 6p, 60p doz. Jack Plugs, Standard, 9p; 3.5mm, 6p; 400-200-50-16µF 300V, 30p, £3 per doz. Recording Tape, 5in LP, 45p, 5½in LP, 60p. Post and packing on all orders 10p. Send S.A.E. for list. M. DZIUBAS, 158 Bradshawgate, Bolton, Lancs.

## R & R RADIO

51 Burnley Road, Rawtenstall

Rossendale, Lancs

Tel.: Rossendale 3152

### TESTED VALVES—3 MONTHS GUARANTEE

EBF80	15p	PCC84	15p	PY800	17½p
EBF89	17½p	PCF80	15p	PY801	17½p
ECC82	15p	PCL82	20p	U191	22½p
ECL80	15p	PL36	25p	30C15	25p
EF80	10p	PY33	25p	PCF86	25p
EF85	15p	PY81	17½p	PCL85	25p
EY86	20p	PY82	15p	PCL84	25p

Copper Laminate Board, for etching, 1p per sq.in. Double sided 1½p per sq.in. Any size cut, min. order 50p plus 10% P. & P.

Postage on Valves: one valve 4p, up to 6 2½p, over 6 post paid.

**HI-STAB RESISTORS** mixed bag, 100, 50p; 250, £1. Please send cash with order to ELM-BRIDGE INSTRUMENTS LTD., Island Farm Avenue, West Molesey Trading Estate, Surrey.

**ZZ ELECTRONICS**, 141 Morning Lane, Hackney, E.8. TV and Electrical repairs. Spares Specialist. Valves and TV tubes tested.

### FOR SALE

**SEEN MY CAT?** 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

**"PRACTICAL ELECTRONICS"**. Every issue. Offers. 2 Lydford Way, Birtley Co. Durham

## MORSE MADE !!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2896 or send 4p stamp for explanatory booklet to:

GSHSC (Box 19), 45 GREEN LANE, PURLEY, SURREY

**CATALOGUE NO. 18**, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

### SITUATIONS VACANT

**EAGLE INTERNATIONAL** require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-636 0961.

### EDUCATIONAL

**HUNDREDS OF TOP PAID JOBS** in engineering await qualified men. Get a certificate through B.I.E.T. Home Study—Mech., Elec., Auto., Radio, TV, Draughts., Electronics, Computers, Building, etc. Send for helpful FREE book, B.I.E.T., Department 125K, Aldermaston Court, Reading, RG7 4PF.

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

**A.M.S.E. (Elec.)**, City & Guilds, R.T.E.B. Cert., Radio Amateurs' Cert., etc., on "Satisfaction or Refund" terms. Wide range of courses in Elec. Engineering, Design, Installation, Repairs, Refrigeration, Electronics, Radio and TV, etc. Send for full details and illustrated book—FREE. BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY, Dept. 124K Aldermaston Court, Reading, RG7 4PF.

**MEN!** You can earn £50 p.w. Learn Computer Operating. Send for FREE brochure—LONDON COMPUTER OPERATORS TRAINING CENTRE, C95 Oxford House, 9-15 Oxford Street, London, W.1.



Established 1891

# TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- C. & G. ELECTRONIC SERVICING.
- R.T.E.B. RADIO AND TV SERVICING CERTIFICATE.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

### NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ASSOCIATION OF BRITISH CORRESPONDENCE COLLEGES

**INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS**

**A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!**

**International Correspondence Schools**  
(Dept. 152), Intertext House, Stewarts Road,  
London, S.W.8

NAME.....  
Block Capitals Please

ADDRESS.....

AGE..... OCCUPATION..... 4/71

RECEIVERS AND COMPONENTS (continued)

<b>Microcircuits:</b>			
709	47p	MEL11	47p
PA234	87p	7420	28p
SL402A	£1.80	PA230	92p
7410	28p	D40C1	67p
741	88p	DIL Conn.	30p
PA237	£1.57	7430	15p
<b>Transistors:</b>			
ME0402	21p	2N4059	15p
ME4102	12p	ME4101	11p
2N5172	9p	MPB111	35p
ME0412	20p	2N3055	65p
ME6101	15p		
<b>Rectifiers:</b>			
IN4001	7p	PL4003	11p
IN4002	8p	WO2	40p
PL4002	10p	IN4005	12p
W005	37p	IN4006	14p
IN4003	9p	PL4004	12p
IN4004	10p	FD40	62p
40583 Diac Trigger Diode	26p		

**JEF ELECTRONICS (P.E.4)**

York House, 12 York Drive, Grappenhall Warrington, Lancs. Mail Order Only C.W.O. P. & P. 5p per order. Overseas 40p Money back if not satisfied

**PRINTED CIRCUIT BOARDS FOR P.E. PROJECTS**

All boards drilled and roller tinned complete with layout drawing.  
**EXAMPLES**  
 Marine Tachometer (May 1970) 25p ea. Musical Slave (May 1970) 40p ea. Waa-Waa pedal Vol. 4 No. 7 14p ea. Audio Sig. Gen. (Sine and Square on one board) Vol. 5 No. 10 42p ea.  
 S.A.E. for List. Now available from:- HENRY'S RADIO LTD., Edgware Road, London, W.2  
**P.H. ELECTRONICS**, Industrial Estate, Sandwich, Kent. Tel. 2517

**TRANSFORMER KITS**

Consisting of:- CLAMPS, WINDING BOBBIN AND LAMINATIONS

Max. Rating	Ref. No.	Price	P. & P.
5 VA	74/63	45p	7p
10 VA	35/75	52p	12p
15 VA	147/88	75p	17p
25 VA	29/11	£1.02½	22p
50 VA	78/125	£1.77½	27p
75 VA	78/150	£2.37½	32p
100 VA	120/125	£2.75	37p

Transformer designs up to 100VA 50p ea., larger kits and designs available on request.

Supplied by:

**WEST DIDSBURY TRANSFORMERS**  
 Brooks Street, Higher Hillgate  
 Stockport, Cheshire SK1 3EU  
 Tel. 061-480 6479

**DRY REED INSERTS**



Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250v D.C. Gold clad contacts. 62p per doz.; £3.75 per 100; £27.50 per 1,000; £250 per 10,000. All carriage paid.

G.W.M. RADIO LTD.  
 40/42 Portland Road, Worthing, Sussex 0903 34897

**EX COMPUTER PRINTED CIRCUIT PANELS**  
 2 1/2 x 4 1/2 packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p. P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to OC28 on each board—components 2 boards (4 x OC28) 50p. P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 1 3/4 x 4 1/4. 4 for £1, P. & P. 25p.

**LARGE CAPACITY ELECTROLYTICS**  
 10,000MFD 30V } 40p each, P. & P. 6p.  
 18,000MFD 12V }  
 or £2.50 per doz. Carr. 50p.

**250 MIXED RESISTORS** 62p  
 ½ & ¼ watt.

**150 MIXED HI STABS** 62p  
 ½, ¼ & 1 watt 5% & better.

**EXTRACTOR/BLOWER FANS (PAPST)**  
 100 CFM 2,800 RPM 4 1/4 x 4 1/4 x 2 1/4. Ideal for kitchen extraction, instrument cooling, etc. £2.50, P. & P. 25p. 240V a.c. 50 cycles

**DIODES EX EQPT. SILICON**  
 1 Amp 1,000 PIV 4 for 50p  
 20 Amp 150 PIV 4 for £1.  
 P. & P. 5p.

**BARGAIN RELAY OFFER**  
 Single pole change over silver contacts 25V to 50V. 2-5k coil. 8 for 50p. P. & P. 6p.

**KEYTRONICS** mail order only  
 52 EARLS COURT ROAD  
 LONDON, W.8 01-478 8499

**COMPUTER BOARDS**, with about 10 silicon transistors, mainly npn similar 2N706, 20 silicon diodes, quality resistors, capacitors, etc., some have trim pots and zeners, 17p each, 70p for 5. £2.50 for 25. **LOGIC I.C.'s** from 5p each on boards. **MIXED COMPONENTS** including resistors, capacitors, diodes, I.C.'s transistors, some damaged but well worth 65p per lb or money back. **THYRISTORS** 2N1505, 50 PIV, 1A, 65p for 8 on board. All post paid. S.A.E. for list and all data. PAWSON, 114 South Street, Armadale, W. Lothian, Scotland.

**PRINTED CIRCUITS**

PE 'Gemini' STEREO AMPLIFIER (Dec. 1970)  
 Twin Channel Main Amplifier. Stabilised Power Supply  
 Total price £1.13. P/P. 8p.

All boards are fibreglass, drilled and tin plated with reverse side screen printed for easy component and connection identification.

S.A.E. for PC board list of other current projects.  
**SERVITRON ELECTRONICS**, 1B Beckdean Ave., Poulton-Le-Fylde, Blackpool, Lancs. FY6 8BG

**COMPUTER PANELS.** 5-BC108 diodes, 15p (3/-), post 5p (1/-), 4—50p (10/-), post 15p (3/-), 8-OC76/OC72/OC42, 80A10 diodes, 40p (8/-), post 10p (2/-) per panel. 8-OC170 diodes, 40p (8/-), post 8p (1/7) per panel. 2-OC170, 2-GET875 or 4MDS34, 5-100mfd 12V Electrolytics, pot core, etc. 30p (6/-), post 8p (1/7) per panel.

**PANELS WITH VHF NPN AND/OR PNP SILICON TRANSISTORS.** resistors, diodes, capacitors, etc. Panels with 4 transistors 10p (2/-), with 6-8, 15p (3/-), 10-12, 25p (5/-), 14-16, 30p (6/-), 24, 40p (8/-), 30-32, 50p (10/-). Post up to four 15p (3/-), five or over, 25p (5/-).

**MIXED TRANSISTORS ON PANELS.** 60 for 80p (16/-). 100 for £1.35 (27/-). C.P. panels with resistors, caps, and diodes, 6 for 25p (5/-). Post 15p (3/-) for six.

**POLYSTYRENE CAPACITORS.** 125V, 18, 22, 120, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p (3/-) dozen. Post free with other goods otherwise 10p (2/-).

**ASSORTED COMPONENTS.** 7lb. £1 (20/-) C.P.  
 J.W.B. RADIO  
 75 Hayfield Road, Salford 6, Lancs.  
 MAIL ORDER ONLY

**BRAND NEW COMPONENTS BY RETURN.** Electrolytics 15 or 25V 1-10mfd, 3½p. 20-100 mfd, 4p. Mylar Film 100V 0-001, 0-002, 0-005, 0-01, 0-02, 2p. 0-04, 0-05, 0-1, 2½p. Mullard miniature Carbon Film Resistors E12 Series ¼W 1Ω-10Ω, 8 for 5p. Postage 5p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, S8 0RN.

**MINI MAINS PACK KIT.** Safe double-wound transformer, Si rects, 1,000µF and instructions for 9V, 120mA eliminator. Can be built to size of PP6 battery. U.K. post paid 95p. S.A.E. list. **AMATRONIX LTD.**, 396 Selsdon Rd., S. Croydon, Surrey, CR2 0DE.

**SERVICE SHEETS**

**RADIO TELEVISION**, over 8,000 Models. JOHN GILBERT TELEVISION, 1b Shepherd Bush Ltd., London, W.6 (01-743 8441).

**SERVICE SHEETS.** Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Maudland Bank, Preston.

**SERVICE SHEETS** (1925-1971) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex.

**TELERADIO ELECTRONICS**

**JOIN THE FASCINATING HOBBY OF RADIO CONTROL. BUILD A SINGLE CHANNEL SYSTEM FOR ABOUT £12 OR A SOPHISTICATED PROPORTIONAL SYSTEM FOR £80**

Details from the specialists: **TELERADIO CO. (P.E.)**  
 325-7 LOWER FORE STREET, EDMONTON, N.9

**AMPLIFIER & PREAMP. PRINTED CIRCUIT BOARDS FOR MULLARD CIRCUITS**

High quality Printed Circuit Boards for the following circuits shown in the Mullard publication **Transistor Audio and Radio Circuits**.

10 W high quality audio amplifier	(p.102)	66p
25 W high quality audio amplifier	(p.106)	70p
10/25 W high quality audio preamplifier	(p.108)	73p

Price each including postage and packing. Cash with order.

All boards are, tinned to prevent oxidation and to aid soldering and have the component identification printed on the reverse.

**BRIBOND PRINTED CIRCUITS LTD**  
 Terminus Road, Chichester, Sussex

**WAH-WAH PEDAL KIT**

**SELECTIVE AMPLIFIER MODULE.** The basis of the Wah-Wah pedal. Kit contains all the components to build a 2-transistor circuit module, also the sockets, control, etc., required for the constructor to assemble his own design. £1.75 (35/-). Assembled and tested module £2.13 (42/6).

**FOOT VOLUME CONTROL PEDAL.** Foot pedal unit in very strong fawn plastic. Fitted with output lead and plug for connection to guitar amplifier. May be used for volume control or converted to Wah-Wah by adding the module. Pedal unit now only £5.13 (£52.6).

Complete kit for Wah-Wah pedal now only £6.50 (£6.10.0). All post free.

Send 15p (3/-) for our catalogue of components, testmeters, musical electronics and more details of the above items. Callers welcome.

**WILSIC ELECTRONICS LIMITED**  
 6 COPLEY ROAD, DONCASTER, YORKSHIRE

# TRANSISTORS

BRAND NEW FULLY GUARANTEED  
NEW LIST—NEW PRICES  
SEND FOR FREE COPY TODAY

2N404	22p	2N404	22p	2N404	22p
2N696	17p	2N696	17p	2N696	17p
2N697	17p	2N697	17p	2N697	17p
2N706	10p	2N706	10p	2N706	10p
2N706A	12p	2N706A	12p	2N706A	12p
2N930	25p	2N930	25p	2N930	25p
2N1131	30p	2N1131	30p	2N1131	30p
2N1132	30p	2N1132	30p	2N1132	30p
2N1302	20p	2N1302	20p	2N1302	20p
2N1303	22p	2N1303	22p	2N1303	22p
2N1304	25p	2N1304	25p	2N1304	25p
2N1305	25p	2N1305	25p	2N1305	25p
2N1306	25p	2N1306	25p	2N1306	25p
2N1308	30p	2N1308	30p	2N1308	30p
2N1309	25p	2N1309	25p	2N1309	25p
2N1613	22p	2N1613	22p	2N1613	22p
2N1711	25p	2N1711	25p	2N1711	25p
2N2147	75p	2N2147	75p	2N2147	75p
2N2160	65p	2N2160	65p	2N2160	65p
2N2218	30p	2N2218	30p	2N2218	30p
2N2219	30p	2N2219	30p	2N2219	30p
2N2222	30p	2N2222	30p	2N2222	30p
2N2222A	37p	2N2222A	37p	2N2222A	37p
2N2369	20p	2N2369	20p	2N2369	20p
2N2484	35p	2N2484	35p	2N2484	35p
2N2646	50p	2N2646	50p	2N2646	50p
2N2904	30p	2N2904	30p	2N2904	30p
2N2904A	30p	2N2904A	30p	2N2904A	30p
2N2905	37p	2N2905	37p	2N2905	37p
2N2906	30p	2N2906	30p	2N2906	30p
2N2906A	32p	2N2906A	32p	2N2906A	32p
2N2907	37p	2N2907	37p	2N2907	37p
2N2926	12p	2N2926	12p	2N2926	12p
2N3011	25p	2N3011	25p	2N3011	25p
2N3053	25p	2N3053	25p	2N3053	25p
2N3054	50p	2N3054	50p	2N3054	50p
2N3055	75p	2N3055	75p	2N3055	75p
2N3525	£1.10	2N3525	£1.10	2N3525	£1.10
2N3702	12p	2N3702	12p	2N3702	12p
2N3703	12p	2N3703	12p	2N3703	12p
2N3704	17p	2N3704	17p	2N3704	17p
2N3705	15p	2N3705	15p	2N3705	15p
2N3707	15p	2N3707	15p	2N3707	15p
2N3709	12p	2N3709	12p	2N3709	12p
2N3710	12p	2N3710	12p	2N3710	12p
2N3819	35p	2N3819	35p	2N3819	35p
2N3820	60p	2N3820	60p	2N3820	60p
2N4058	17p	2N4058	17p	2N4058	17p
2N4061	15p	2N4061	15p	2N4061	15p
2N4547	35p	2N4547	35p	2N4547	35p
2N4548	37p	2N4548	37p	2N4548	37p
2N4549	50p	2N4549	50p	2N4549	50p
2S301	50p	2S301	50p	2S301	50p
2S302	50p	2S302	50p	2S302	50p
2S303	50p	2S303	50p	2S303	50p
2S304	50p	2S304	50p	2S304	50p
40250	50p	40250	50p	40250	50p
40361	55p	40361	55p	40361	55p
40362	60p	40362	60p	40362	60p
AA30	10p	AA30	10p	AA30	10p
AA42	15p	AA42	15p	AA42	15p
AA113	12p	AA113	12p	AA113	12p
AA217	10p	AA217	10p	AA217	10p
AC107	37p	AC107	37p	AC107	37p
AC126	25p	AC126	25p	AC126	25p
AC127	25p	AC127	25p	AC127	25p
AC128	25p	AC128	25p	AC128	25p
AC176	25p	AC176	25p	AC176	25p
AC187	30p	AC187	30p	AC187	30p
AC188	30p	AC188	30p	AC188	30p
AC17	30p	AC17	30p	AC17	30p
AC18	25p	AC18	25p	AC18	25p
AC19	25p	AC19	25p	AC19	25p
AC20	25p	AC20	25p	AC20	25p
AC21	25p	AC21	25p	AC21	25p
AC22	17p	AC22	17p	AC22	17p
AC23	17p	AC23	17p	AC23	17p
AC24	17p	AC24	17p	AC24	17p
AD140	50p	AD140	50p	AD140	50p
AD149	30p	AD149	30p	AD149	30p
AD161	37p	AD161	37p	AD161	37p
AD162	37p	AD162	37p	AD162	37p
AF14	25p	AF14	25p	AF14	25p
AF15	25p	AF15	25p	AF15	25p
AF16	25p	AF16	25p	AF16	25p
AF17	25p	AF17	25p	AF17	25p
AF18	62p	AF18	62p	AF18	62p
AF124	25p	AF124	25p	AF124	25p
AF125	20p	AF125	20p	AF125	20p
AF126	17p	AF126	17p	AF126	17p
AF127	17p	AF127	17p	AF127	17p
AF139	30p	AF139	30p	AF139	30p
AF178	47p	AF178	47p	AF178	47p
AF179	47p	AF179	47p	AF179	47p
AF180	52p	AF180	52p	AF180	52p
AF181	42p	AF181	42p	AF181	42p
AF186	40p	AF186	40p	AF186	40p
AF239	42p	AF239	42p	AF239	42p
AS26	25p	AS26	25p	AS26	25p
AS27	32p	AS27	32p	AS27	32p
AS28	25p	AS28	25p	AS28	25p
AS29	30p	AS29	30p	AS29	30p
AS297	47p	AS297	47p	AS297	47p
AS21	42p	AS21	42p	AS21	42p
BA15	7p	BA15	7p	BA15	7p
BA16	10p	BA16	10p	BA16	10p
BA13	6p	BA13	6p	BA13	6p
BA15	7p	BA15	7p	BA15	7p
BA17	7p	BA17	7p	BA17	7p
BSY38	17p	BSY38	17p	BSY38	17p
BSY106	12p	BSY106	12p	BSY106	12p
BSY107	12p	BSY107	12p	BSY107	12p
BSY108	12p	BSY108	12p	BSY108	12p
BSY110	12p	BSY110	12p	BSY110	12p
BSY111	12p	BSY111	12p	BSY111	12p
BSY112	12p	BSY112	12p	BSY112	12p
BSY200	12p	BSY200	12p	BSY200	12p

# HENRY'S LOW COST INTEGRATED CIRCUITS

WE OFFER FROM STOCK AN EXCLUSIVE RANGE OF BRAND NEW CERAMIC FULL SPECIFICATION LOW COST TTL 7400 RANGE OF INTEGRATED CIRCUITS

Part No.	Description	Price	Price	Price	Price
7400	Quad 2-Input NAND Gate	1.49	50-99	100	500
7401	Quad 2-Input NAND Gate Open Collector	25p	2		

# FIND BURIED REAL WORKING ELECTRONIC TREASURE! ORGAN

TREASURE LOCATOR—


NOW IT'S HERE AT LAST.



after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location (no phones used—uses only transistor radio which fits inside—no connections needed). **FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground. Can be built with ease in one short evening with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions. Fully transistorised—no valves. Uses standard PP3 battery.

ONLY **£2-37** (47/6)

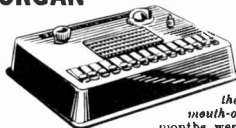necessary. Size of detector head 13in x 10in x 2in. Great demand expected at this remarkably low price—All parts including detector head case, nuts, screws, wire, simple instructions, etc. Send now **£2-37 + 33p P. & P.** (47/6 + 6/6) (Telescopic handle as illustrated **£1-75** (35/-) extra). Parts available separately. Made up looks worth £15.



ONLY **£2-75** (55/-)

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised, no valves. Proper self-contained loudspeaker. Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", "Silent Night", "Auld Lang Syne", and lots of similar tunes on this real working electronic organ. Size 13in x 10in x 2in. Uses standard battery. Have the thrill and excitement of building it together with the pleasure of playing a real electronic organ. Play it anywhere. No soldering necessary. Easy as A.B.C. to make following the fully illustrated, step-by-step instructions. **BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT** at our low price. ONLY **£2-75 + 23p P. & P.** (55/- + 4/6) for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformers, volume control, wire, nuts, screws, instructions, etc. (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

## MAKE 5 PROJECTS INCLUDING 3 TRANSISTOR LOUDSPEAKER RADIO




LIMITED QUANTITY **£1-97** (39/6)

Amazing Radio Construction set for **£1-97** (39/6). A complete Home Radio Course. No experience needed. Parts including illustrated step-by-step instructions, personal phone, knobs, screws, etc., all you need. Presentation box as illustrated **37p** extra (7/6) if reqd. (parts avail. separately). Send only **£1-97 + 23p P. & P.** (39/6 + 4/6).

Examine at home for 7 days. Your money back if not delighted.
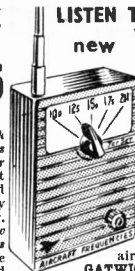
## LISTEN TO AIRCRAFT COMMUNICATIONS new V.H.F. AIRCRAFT BAND CONVERTER



ONLY **£2-37** (47/6)

Listen in to AIRLINES, PRIVATE PLANES, JET PLANES. Eavesdrop on exciting groundtalk between pilots, ground approach, ground control, airport tower. Hear for yourself the disciplined voices hiding tenseness or talk down. Be with them when they have to take nerve ripping decisions in emergencies—tune in to the international distress frequency. Covers aircraft frequency band including **HEATHROW, GATWICK, LUTON, BINGWAY, PRESTWICK, ETC.** This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time). No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4in x 3in x 1in. All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny pocket radio). **NO CONNECTIONS WHATSOEVER NEEDED.** Use indoors or outdoors. Send now ONLY **£2-37 + 23p (4/6) P. & P.** for all parts, including case, nuts, screws, wire, etc. (parts available separately).

## SHORTWAVE TRANSISTOR RADIO



ONLY **£2-25** (45/-)

CAN BE BUILT IN ONE EVENING At last! After trying countless circuits searching for easy build, work-first-time short wave. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-A.B.C. fully illustrated instructions. (We built ten prototypes and every one worked first time) no soldering necessary, 76 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on annual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3in x 4in x 1in. As tremendous demand anticipated price held to only **£2-25 + 17p P. & P.** (45/- + 3/6) for all parts incl. cabinet, screws, instr., etc. Parts available separately.

**CONCORD ELECTRONICS LTD.**

(P.E.17) • 8 WESTBOURNE GROVE • LONDON W.2 (Near Bayswater Tube) Callers welcome. 9-6 including Saturdays

# ENAMELLED COPPER WIRE

S.W.G.	1/2 lb. Reel	1 lb. Reel
18-22	62 1/2 p	92 1/2 p
23-30	65 p	97 1/2 p
31-35	67 1/2 p	£1 02 1/2
36-40	82 1/2 p	£1 32 1/2
41-44	97 1/2 p	£1 62 1/2

Orders despatched by return of post. Please add 12 1/2 p per item P. and P.

Supplied by:

**BANNER TRANSFORMERS**  
(Dept. PE), Brooks Street  
Higher Hillgate, Stockport, Cheshire

**YUKAN SELF-SPRAY** SO PROFESSIONAL THE YUKAN AEROSOL WAY—  
Get these air drying GREY HAMMER OR BLACK WRINKLE NOW! (CRACKLE) finishes

Yukan Aerosol spraykit contains 453g. fine quality, durable easy instant spray. No stove baking required. Hammers available in grey and blue. 90p carr. pd. Modern Eggshell Black Wrinkle (Crackle) producing a 3D textured finish. 90p carr. pd. all at 85p per push-button self-spray can at our counter. Also durable, heat and water resistant Black Matt finish (339g. self-spray cans only) 75p carr. pd.

SPECIAL OFFER: One can plus optional transferable snap-on trigger handle (value 25p) for 96p carr. pd. Choice of 13 self-spray plain colours and primer (motor car quality) also available.

Please enclose cheque or crossed P.O. for total amount direct to:  
**DEPT: K3 YUKAN, 307A EDGWARE ROAD, LONDON W2 1BN**  
We supply many Government Departments, Municipal Authorities, Institutes and Leading Industrial Organisations—We can supply you too. Now British—  
Open all day Saturday. Closed Thursday afternoons. even better

Other Yukan Air Drying Aerosols: 453g at 90p carr. pd. include Zinc Chromate Clear Lacquer Metallics Grey. Blue

**BAKER 15in. AUDITORIUM**  
A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power 35 watts  
Bass Resonance 35 c.p.s.  
Flux Density 15,000 gauss  
Voice coil impedance 8 or 15 ohms models  
Useful response 20-14,000 c.p.s.  
Nett weight 15 lbs.

**£19** POST FREE

GUJAR MODEL "GROUP 50" 50 watt rating £19  
Test catalogue 5p with enclosure plans

**Baker Reproducers Ltd**  
Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684 1665



# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn on 'SATISFACTION - OR REFUND OF FEE' terms. If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecommis.**  
C. & G. Telecommis.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Constructional**  
A.M.S.E. (Civ.)  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpenters & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

### THEY DID IT—SO COULD YOU

"My income has almost trebled... my life is fuller and happier." - Case History G/321.

"In addition to having my salary doubled, my future is assured." - Case History H/493.

"A turning point in my career - you have almost doubled my standard of living." - Case History K/662.

"Completing your Course meant going from a job I detested to a job I love." - Case History B/461.

### FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept 316A, Aldermaston Court, Reading RG7 4PF.

(Write if you prefer not to cut this page)



## POST THIS COUPON TODAY

To: B.I.E.T., Dept 316A, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name ..... Age .....

Address .....

Occupation .....

**B.I.E.T. - IN ASSOCIATION WITH THE SCHOOL OF CAREERS - ALDERMASTON COURT, BERKSHIRE**

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/asia) Ltd. - South Africa - Central News Agency Ltd. - Rhodesia and Zambia - Kingstons Ltd. - East Africa - Stationery and Office Supplies Ltd. Subscription Rate (including postage). For one year to any part of the world £2 5s. 0d (£2-25). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LIMITED




ENGLAND'S LEADING ELECTRONIC CENTRES  
HI-FI · COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

## TRANSISTOR AMPLIFIERS NEW RANGES NOW IN STOCK

(Leaflets Ref. No.: 6 and 8).  
Post, etc., 20p (4/-).

4-300 4TR 9V 300mW	£1.75 (35/-)
104 4TR 9V 1W	£2.12 (42/5)
304 4TR 9V 3W	£2.47 (49/5)
555 6TR 12V 3W	£2.75 (55/-)
PA7 6TR 16V 7W	£3.62 (72/5)
608 6TR 24V 10W	£4.12 (82/5)
410 4TR 28V 10W	£4.97 (99/5)
MPA12/3 6TR 18V 12W	£4.50 (90/-)
MPA12/15 6TR 36V 12W	£5.25 (105/-)
Z30 9TR 30V 20W	£3.75 (75/-)
PA25 10TR (Special) 25W	£7.50 (150/-)
Z50 30V 40W	£5.47 (109/5)
PA50 12TR (Special) 50W	£9.50 (190/-)
100 100W with power supply	£45 post 45p (9/-)

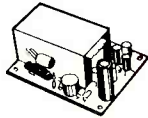

### OPTIONAL POWER SUPPLIES


Post, etc., 20p (4/-)

P500 Switchable (One or Two) for 104, 304	£2.62 (52/5)
PS20 Switchable (One or Two) for PA7	£3.47 (69/5)
MU42/40 Switchable (One or Two) for MPA12/3 or MPA12/15	£4.50 (90/-)
PZ5 for Z30	£3.97 (79/5)
PZ8 for Z50	£5.97 (119/5)
P11 for 608	£2.87 (57/5)
MU442 for 1 or 2 PA25 or 1 only PA50	£15.00 (300/-)

### PROJECT 60 PACKAGE DEALS

2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £19. Carr. 40p. Or with PZ6 power supply, £21. Carr. 40p. 2 x Z50 amplifier, stereo 60 pre-amplifier PZ8 power supply, £21.50, p.p. 40p. Transformer for PZ8 £2.25 extra. Any of the above with Active Filter unit add £4.87 or with pair Q16 speakers add £16. Also NEW FM TUNER, £21.

## BUILD THIS VHF FM TUNER

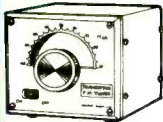

5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 and 7. TOTAL £6.97 (129/-), p.p. 20p (4/-). Cabinet £1. Decoder Kit £5.97, Tuning meter £1.75. Mains unit (optional) Model PS900 £2.47 (49/5). Mains unit for Tuner and Decoder PS1200 £2.62 (52/5).

## BUILD YOURSELF A QUALITY RADIO



Excellent printed circuit design with full power output. Fully tunable on both MW/LW bands. 7 Mullard transistors. Fitted 5in speaker. Room filling power. Easy to build with terrific results. Two colour leathercloth cabinet with silvered front. All local and continental stations. Complete detailed instructions. Total cost £6.98 (£6.19.6), p.p. 35p (7/-). All parts sold separately. Ask for Leaflet No. 1.

## HI-FI TO SUIT EVERY POCKET



### CHOOSE FROM 100 STEREO SYSTEMS

and a complete range of individual units in stock—Demonstrations all day—visit our new Hi-Fi Store. LOW CASH OR CREDIT/HP TERMS (Credit terms from £30 purchase—callers only). FREE—Stock Lists Nos. 16/17 on request—BEST VALUE IN U.K.

## HENRY'S LATEST CATALOGUE



Now 350 pages

WHY NOT SEND AWAY TODAY?

- COMPONENTS, TEST GEAR
- EQUIPMENT, MODULES
- SPECIAL OFFERS, Etc., Etc.

Everything for the constructor. Complete with 50p value discount vouchers for use with purchase. Price 50p, post free.

FREE 8 page Transistor, IC, Diode lists No. 36

FREE 20 page Organs to Build brochure No. 9

FREE Decks and Hi-Fi Stocks Lists No. 16/17


FREE PA, Disco and Lighting List No. 18

FREE Quotations for all Electronics—send list and S.A.E.
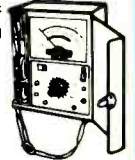
## TEST EQUIPMENT FOR HOME, SCHOOL & PROFESSIONAL USE




AF105 50k/V multimeter (illus.). Price £8.50 (190/-), p.p. 20p (4/-). Leather case £1.42 (28/5). 200H 20k/V. Price £3.87 (77/5), p.p. 20p (4/-). Case 62p (12/5). 500 30k/V multimeter. Price £8.87 (177/5), p.p. 20p (4/-). Leather case £1.50 (30/-). TH133 2k/V. Price £4.12 (82/5), p.p. 15p (3/-). Leather case £1.15 (23/-). TE65 Valve voltmeter (illus.). Price £17.50 (350/-), p.p. 40p (8/-). SE150B Pocket pencil signal injector £1.75 post paid. SE500 Pocket pencil signal tracer £1.50 post paid.



TE20D RF generator. Price £15, p.p. 40p (8/-). TE22D Matching audio generator. Price £17, p.p. 40p (8/-). TE15 Grid dip meter. Price £12.50, p.p. 40p. TO3 Scope 3 in. tube. Price £37.50, p.p. 50p. TE22 Audio Generator. £17, p.p. 40p.

(Get a copy of our latest catalogue for full specifications and further ranges.)
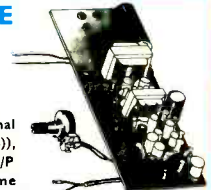
## NEW MINIATURE LOW COST AMPLIFIER MODEL 4-300



9V operated or mains unit optional transformer (MT98 70p (14/-)), 1-10mV adjustable sensitivity. P/P output for 3-8 ohms. Fitted volume control and leads. Size 5 1/2 in x 1 1/2 in x 3/4 in. Thousands of uses—takes magnetic, dynamic and crystal inputs direct. Output 300mW—very high gain—built in rectifier circuit.

Price £1.75 (35/-), p.p. 15p (3/-). Complete with FREE leaflet No. 8.

## STC TIME DELAY MODULE



Ideal for experimenters, educational projects, as well as for practical uses. Delay adjustable 3-15 secs. Operates 9-12 volts. Heavy Duty Relay Contacts. Complete with suggested applications sheet. Price £1.75 (35/-) post paid.

## GARRARD TAPE DECK




Price £9.97

199/6, p.p. 33p (6/6) (3 1/2 in. tape 300ft. and spool 40p (8/-)).

9V operated 2-speed tape deck fitted Record/Play + track and Erase/Bias Osc. Head. Complete with Oscillator/Record head circuit. Unit size 9 in x 6 1/2 in x 1 1/2 in and 2 1/2 in below motor board. Takes up to 4 in spools. Supplied Brand New.
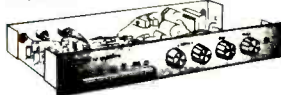
## HENELEC SELF-POWERED PREAMPLIFIERS

Designed for use with PA25 and PA50 Amplifiers.



SLIM MODERN DESIGNS USING THE LATEST SILICON TRANSISTORS, FET's and IC's, DIN SOCKETS, ETC. fitted. Self powered. PUSH-BUTTON SELECTION. ±20dB BASS AND TREBLE BOOST AND CUT. All inputs provided plus TAPE RECORD and REPLAY.

GOLD AND SILVER FINISH. Mains operated. Supplied with all plugs, etc. ADJUSTABLE OUTPUT UP TO 1 VOLT.


- FET/9. Mono with built-in mic. mixer. Accepts any ceramic or crystal cartridge. Plus tuner, tape, etc. Price £12.50 (£12.10), p.p. 20p (4/-).
- FET/15 STEREO (illus.). Magnetic cart. input, tuner, tape, etc. Beautiful stereo sound. Price £16.50 (£6.10), p.p. 25p (5/-).
- Also suitable for use with any power amplifier. Suggested types PA25, PA50, MPA12/3, MPA12/15.

SIMPLICITY TO MOUNT

EASY TO USE

All units no soldering—just edge connectors and plugs

## 25 WATT & 50 WATT SILICON AMPLIFIERS

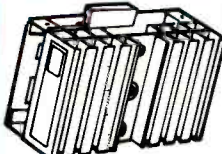

LOOK AT THE SPECIFICATIONS!

- At full power 0-3% distortion.
- At full power—1dB 11 c/s to 40 kc/s.
- Response—1dB 11 c/s to 100 kc/s.
- Rise time 2usec.
- Short circuit proof plus limiting cct.

FREE LEAFLET No. 25 on request

PA25 10 transistor all silicon differential input 400mV sensitivity. 25W Rms into 8 ohms. Supplied with edge connector harness size 5in x 3in x 2in. PA50 12 transistor version 50W Rms into 3 to 4 ohms. Size 5in x 3in x 4in. MU442. Power supply for one or two PA25 or one PA50. PA25, £7.50. PA50, £9.50. MU442, £6. P.P. 20p each.

DESIGNED FOR QUALITY, PERFORMANCE AND PRICE

As specified for many "Practical Wireless" 1970 projects

Electronic Components & Test Gear Centre

356 EDGWARE ROAD, LONDON, W.2.

Tel: 01-402 4736

OPEN 9 a.m. to 6 p.m. MONDAY TO SATURDAY

High Fidelity Sales & Demonstrations Centre

354 EDGWARE ROAD, LONDON, W.2.

Tel: 01-402 5854

OPEN 9 a.m. to 1 p.m. THURSDAYS

Electronic Organs, P.A. & Discotheque Centre

309 EDGWARE ROAD, LONDON, W.2.

Tel: 01-723 6963

OPEN ALL DAY SATURDAY

Mail Orders, Special Bargain Shop, Industrial Sales

303 EDGWARE ROAD, LONDON, W.2.

Tel: 01-723 1008/9

OPEN ALL DAY SATURDAY