

PRACTICAL

# ELECTRONICS

DECEMBER 1971

20p



LOGICAL  
RADIO  
CONTROL

**SPECIAL SUPPLEMENT:** Digital and Linear Integrated Circuits... Survey of Available Types

# ADCOLA Soldering Instruments add to your efficiency

## THE NEW 'INVADER'

### ADCOLA L.646

for Factory Bench Line Assembly

A precision instrument—supplied with standard 3/16" (4.75 mm) diameter, detachable copper chisel-face bit\*.  
Standard temp. 360°C at 23 watts.  
Special temps. from 250°C—410°C.

PRICE  
£1.85

\*Additional Stock Bits  
(illustrated) available

#### COPPER

B 38  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 24  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE

B 12  $\frac{1}{8}$ " — 4.75 mm EYELET BIT

B 58  $\frac{1}{2}$ " — 6.34 mm CHISEL FACE

#### LONG LIFE

B 42 LL  $\frac{1}{8}$ " — 4.75 mm CHISEL FACE

B 38 LL  $\frac{1}{8}$ " — 3.2 mm CHISEL FACE

B 14 LL  $\frac{3}{16}$ " — 2.4 mm CHISEL FACE

B 44 LL  $\frac{1}{4}$ " — 4.75 mm SCREWDRIVER FACE



Don't take chances. We don't. All our ADCOLA Soldering Instruments are of impeccable quality. You can depend on ADCOLA day after day. That's why they're so popular. You get consistent good service . . . reliability . . . from our famous thermally controlled ADCOLA Element and the tough steel construction of this ideal production tool.

\* Write for price list and catalogue



**ADCOLA PRODUCTS LTD.,**  
(Dept. L.), ADCOLA HOUSE, GAUDEN RD., LONDON, S.W.4  
Telephone: 01-622 0291/3 • Telegrams: Soljoint London Telex • Telex: Adcola London 21851

# SAFELOC

## of robust construction


Safe, quick and secure it connects 2-core and 3-core bare-ended flexible leads to the mains (A.C. only).

The concept was pioneered by Rendar, and introduced to the market 13 years ago.

Safebloc saves time. No need to fit a plug for tests. No danger, as no current can pass with the lid open.

Invaluable for testing and demonstrations in industry and shops, the work bench and the home.

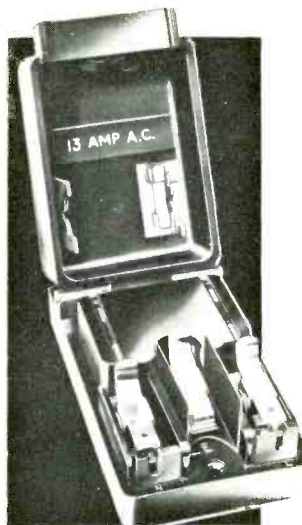Ask for Safebloc at your local stockist — or you can order it direct from the manufacturer.



If ordering by post, send cash with order.

PRICE £2.60 + 10p P.&P. EACH

Special bulk order wholesale and industrial rates on application




# RENDAR®

Rendar Instruments Ltd., Victoria Road,  
Burgess Hill, Sussex. Tel. Burgess Hill 2642
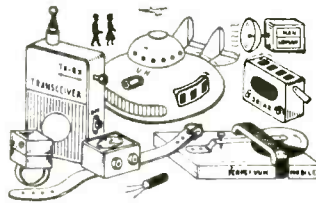
## PRINTED CIRCUIT KIT

BUILD 50 INTERESTING PROJECTS on a PRINTED CIRCUIT CHASSIS with PARTS and TRANSISTORS from your SPARES BOX

CONTENTS: (1) 2 Copper Laminate Boards 4 1/4" x 2 1/2". (2) 1 Board for Matchbox Radio. (3) 1 Board for Wristwatch Radio, etc. (4) Resist. (5) Resist Solvent. (6) Etchant. (7) Cleanser/Degreaser. (8) 16-page Booklet *Printed Circuits for Amateurs*. (9) 2 Miniature Radio Dials SW/MW/LW. Also free with each kit: (10) Essential Design Data, Circuits, Chassis Plans, etc. for 50 TRANSISTORISED PROJECTS. A very comprehensive selection of circuits to suit everyone's requirements and constructional ability. Many recently developed very efficient designs published for the first time, including 10 new circuits.



EXPERIMENTER'S  
PRINTED CIRCUIT KIT  
**60p**

Postage & Pack. 10p (UK)

Commonwealth:

SURFACE MAIL 15p

AIR MAIL 60p

Australia, New Zealand,  
South Africa, Canada

(1) Crystal Set with biased Detector. (2) Crystal Set with voltage-quadrupler detector. (3) Crystal Set with Dynamo Loudspeaker. (4) Crystal Tuner with Audio Amplifier. (5) Carrier Power Conversion Receiver. (6) Split-Load Neutralised Double Reflex. (7) Matchbox or Photocell Radio. (8) "TRI-FLEXON" Triple Reflex with self-adjusting regeneration (Patent Pending). (9) Solar Battery Loudspeaker Radio. The smallest 3 designs yet offered to the Home Constructor anywhere in the World. 3 Subminiature Radio Receivers based on the "Triflexon" circuit. Let us know if you know of a smaller design published anywhere. (10) Postage Stamp Radio. Size only 1.62in x 0.95in x 0.55in. (11) Wristwatch Radio 1.15in x 0.80in x 0.55in. (12) Ring Radio 0.70in x 0.70in x 0.55in. (13) Bacteria-powered Radio. Runs on sugar or bread. (14) Radio Control Tone Receiver. (15) Transistor P.P. Amplifier. (16) Intercom. (17) 1-valve Amplifier. (18) Reliable Burglar Alarm. (19) Light-Seeking Animal, Guided Missile. (20) Perpetual Motion Machine. (21) Metal Detector. (22) Transistor Tester. (23) Human Body Radiation Detector. (24) Man/Woman Discriminator. (25) Signal Injector. (26) Pocket Transceiver (Licence required). (27) Constant Volume Intercom. (28) Remote Control of Models by Induction. (29) Inductive-Loop Transmitter. (30) Pocket Triple Reflex Radio. (31) Wristwatch Transmitter/Wireless Microphone. (32) Rain Alarm. (33) Ultrasonic Switch/Alarm. (34) Stereo Pre-amplifier. (35) Quality Stereo Push-Pull Amplifier. (36) Light-Beam Telephone "Photophone". (37) Light-Beam Transmitter. (38) Silent TV Sound Adaptor. (39) Ultrasonic Transmitter. (40) Thyristor Drill Speed Controller. Plus 10 Photoelectric Circuits, Simple Alarms, Long Range Alarms, Projector Modulators, etc.

**YORK ELECTRICS, Mail Order Dept.**  
**335 BATTERSEA PARK ROAD, LONDON, S.W.11**

Send a S.A.E. for full details and a brief description of all kits and Projects.

# LASKY'S SCOOP

## HI-FI BARGAIN OF THE CENTURY save up to 35% on LEAK recommended list prices!


As the United Kingdom's leading High-Fidelity Retailers, we are proud to offer you the "Scoop of the Century", Leak Hi-Fi Amplifiers, tuners, turntables and speakers at fantastic prices. Each piece of equipment is brand new and covered by Leak's full guarantee. Leak have been the U.K.'s leading Manufacturer since the birth of High-Fidelity—their quality has always been used as a yardstick for true High-Fidelity.



**Leak Stereo 70 amplifier** (cased only) Power output (both channels linewave driven): 35 watts r.m.s. each channel into 8 ohm loudspeakers. Total harmonic distortion: 0.1% for all power levels up to 25 watts r.m.s. each channel at 1KHz into 8 ohm loudspeakers. Crosstalk: Between left and right channels 50dB up to 1KHz and 30dB at 10KHz. Dimensions: 13in (W) x 4½in (H) x 9½in (D) LIST PRICE £75.00 **LASKY'S PRICE £55.00** carriage and packing £1.00.



**Leak Stereofetic FM tuner**—Frequency range: 87-108MHz. Frequency response: ±1dB 40Hz to 15KHz. Frequency drift: Less than 25KHz without A.F.C. Sensitivity: 2½ microvolts for 3dB signal/noise. Output impedance: 200 ohms. Distortion: Less than 0.5% for full deviation, i.e., less than ¼% for average modulation. Signal/Noise: 60dB A.M. suppression: 50dB. Dimensions (cased) 12in (W) x 4½in (H) x 9½in (D) (chassis) 11½in (W) x 4½in (H) x 7½in (D). **CASED LIST PRICE £69.80 LASKY'S PRICE £45.00.** **CHASSIS LIST PRICE £64.03 LASKY'S PRICE £39.50** carriage and packing £1.00 on chassis or cased model.

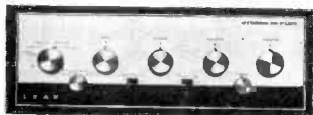


**Leak Stereo 30 Plus amplifier** (cased only) Power outputs (both channels sinewave driven) 15 watts r.m.s. each channel into 8 ohms loudspeakers. Music power outputs 20 watts r.m.s. each channel into 8 ohm loudspeakers. Total harmonic distortion 0.1% for all power levels up to 10 watts r.m.s. each channel at 1KHz into 8 ohm loudspeakers. Crosstalk: Between left and right channels 50dB up to 1KHz and 30dB at 10KHz. Dimensions: 13in (W) x 4½in (H) x 9½in (D). LIST PRICE £62.50 **LASKY'S PRICE £45.00** carriage and packing £1.00.



**Leak Truspeed Transcription Turntable Mk. III**  
A low speed (250 r.p.m.) synchronous 12-pole hysteresis motor (100 130V, or 200 250V, 15mW), gives constant turntable speed independent of mains voltage fluctuations. Speeds: 33½ r.p.m. and 45 r.p.m. Wow: Less than 0.15%. Flutter: Less than 0.02%. Frequency ranges: 20Hz-20KHz. Stereo separation: Better than 25dB at 1KHz. Dimensions: 12½in x 15½in x 7½in inc. cover. Complete with arm, tone arm, base and tinted perspex cover and Shure M75/6 cartridge. Made to sell for £69.50 **LASKY'S PRICE £47.50 C. & P. £1.50.**

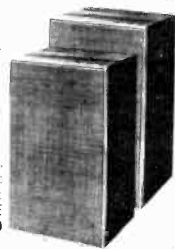**Leak 200 speaker system**—A Stainless Steel woven mesh grille cloth for maximum acoustic transparency and an attractive teak cabinet finished off with aluminium trim all round housing a 3 speaker system worthy of LEAK's name. Impedance 8 ohms, nominal. Frequency response: 60Hz to 18KHz. Power handling capacity 18 watts r.m.s. Resonance of bass unit (free air): 45Hz. Finish: Teak. Dimensions: 15½in x 10in x 8½in LIST PRICE £49.90 **LASKY'S PRICE £31.50 (pair) C. & P. £2.00.**



## fantastic LEAK packages

### Package 1

Stereo 30 Plus (cased) .....	£62.50
Stereofetic (chassis) .....	£64.03
Total Rec. Retail Price .....	£126.53

**LASKY'S PRICE £84 C. & P. £1.50**

### Package 2

Stereo 70 (cased) .....	£75.00
Stereofetic (chassis) .....	£64.03
Total Rec. Retail Price .....	£139.03

**LASKY'S PRICE £94 C. & P. £1.50**

### Package A

LEAK ST30 Plus (cased) .....	£62.50
LEAK 200 Spks (pr) .....	£49.90
LEAK Truspeed T/T system .....	£69.50
Total Rec. Retail Price .....	£181.90

**LASKY'S PRICE £120 post £2.00**

### Package B

LEAK ST70 (cased) .....	£75.00
LEAK 200 Spks (pr) .....	£49.90
LEAK Truspeed T/T system .....	£69.50
Total Rec. Retail Price .....	£194.40

**LASKY'S PRICE £130 C. & P. £2.00**

### Package C

LEAK ST30 Plus (cased) .....	£62.50
LEAK Stereofetic (cased) .....	£69.80
LEAK 200 spks (pr) .....	£49.90
LEAK Truspeed, T/T system .....	£69.50
Total Rec. Retail Price .....	£251.70

**LASKY'S PRICE £160 C. & P. £3.00**

### Package D

LEAK ST70 (cased) .....	£75.00
LEAK Stereofetic (cased) .....	£69.80
LEAK 200 Spks (pr) .....	£49.90
LEAK Truspeed T/T system .....	£69.50
Total Rec. Retail Price .....	£264.20

**LASKY'S PRICE £170 C. & P. £3.00**

### Package E

LEAK ST30 Plus (cased) .....	£62.50
Wharfedale Denton Spks. (pr) .....	£39.90
BSR McDonald MP60 .....	£15.20
Lasky's base and cover .....	£4.75
AD76K magnetic cartridge .....	£4.35
Total Rec. Retail Price .....	£126.70

**LASKY'S PRICE £92 C. & P. £2.00**

### Package F

LEAK ST70 (cased) .....	£75.00
Wharfedale Triton Spks (pr) .....	£59.90
Garrard AP76 .....	£27.85
Garrard base and cover .....	£9.75
Shure M44/E magnetic cart .....	£11.63
Rec. Retail Price .....	£184.73

**LASKY'S PRICE £129 C. & P. £3.00**

### Package G

LEAK ST30 Plus (cased) .....	£62.50
Lasky's Criterion Mk. X Spks. .....	£25.00
BSR McDonald MP60 .....	£15.20
Lasky's base and cover .....	£4.75
AD76K magnetic cartridge .....	£4.35
Rec. Retail Price .....	£111.80

**LASKY'S PRICE £85 C. & P. £2.00**

### Package H

LEAK ST70 (cased) .....	£75.00
LEAK Stereofetic (cased) .....	£69.80
LEAK Truspeed T/T system .....	£69.50
LEAK 600 spks (pr) .....	£99.00
Rec. Retail Price .....	£313.30

**LASKY'S PRICE £225 C. & P. £4.00**

These are only a few of our package bargains incorporating LEAK equipment, many more can be arranged. If none of the packages here suit you please send us details of your requirements and we will be pleased to quote.

# SUPER SONY SCOOP!



**DIGITAL  
CLOCK RADIO 8FC-59WA** **SAVE  
£12.19**

Sony's elegantly designed digital alarm clock radio. The digital clock shows you the time minute by minute with matchless accuracy, and once set the Digimatic will wake you up at the same time every morning without having to be re-set. The radio section features Sony's unique sleep button, you fall gently to sleep lulled by the sweet tone of the radio, which switches itself off at a pre-determined time. Available in either black or white. Frequency range: 530-1,605KHz (AM); 87-108MHz (FM). Uses 8 transistors and 8 semi-conductors, built-in ferrite aerial and 3 $\frac{1}{2}$ in loudspeaker. Power requirements: 230V a.c. 50Hz. Dimensions: 12 $\frac{1}{2}$ in 3 $\frac{1}{2}$ in 5 $\frac{1}{2}$ in.

**LIST PRICE LASKY'S  
£28.94 PRICE £16.75** Post 25p

# OUT NOW! '72 AUDIO-TRONICS




The great new 1972 edition of Lasky's famous Audio-Tronics Catalogue is now available — **FREE** on request. The 44 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiast. Electronics hobbyist, Serviceman and Communications Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio accessories and don't miss **LASKY'S AUDIO-TRONICS CREDIT CARD SCHEME** offering holders one month's interest free credit up to £50 and the fantastic £1,000 plus colour TV competition. Send your name and address and 15p for post and inclusion on our regular mailing list.

# NEW From Lasky's
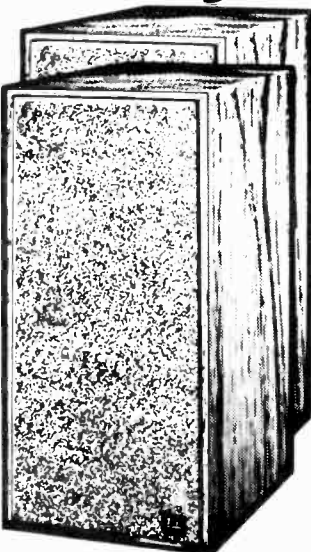
## CRITERION Mk. X

Because of the increasing demand for inexpensive, high quality bookshelf speakers, we have seen fit to introduce the Criterion Mk. X bookshelf system. The speaker is a sealed infinite baffle type enclosure using 8in woofer, a 5in mid. range and 2 $\frac{1}{2}$ in tweeter. The compact cabinet is finished in oiled walnut and black woven speaker grille cloth. Frequency response: 40Hz—20KHz. Power handling capacity: Max. 20 watts. Impedance: 8 ohms. The Criterion is fitted with two types of speaker lead connections — screw terminal and phono. Size: 18 $\frac{1}{2}$ in (H) — 9 $\frac{1}{2}$ in (W) — 9 $\frac{1}{2}$ in (D). Operational horizontally or vertically.



**LASKY'S  
AMAZING  
PRICE** **£25** C & P 50p  
£13.50 each

# a sound future

Lasky's Radio for over 38 years Great Britain's Leading Radio, High Fidelity, Tape Recorder and Electronics Specialists have vacancies in their West End and City Branches for both male and female Sales Assistants. We are seeking intelligent young men and women sales personnel to join our expanding organisation (already the largest in Europe) on a career basis with the finest prospects for early promotion and financial advancement. Working with our energetic sales teams in any of our six West End and City branches will bring you into contact with people from every walk of life including Pop Stars, film and television personalities, royalty and above all enthusiasts in every field of Audio, Hi-Fi and Electronics-people who expect you to share their enthusiasm and interest.


Knowledge of Hi-Fi and electronics is not essential although it will help—all that we require as the basic qualities needed for a successful application are willingness to learn and a common-sense approach to the business of selling. Salary ranges from £850 to £1,850 plus, three weeks' holiday after one year, and Incentive Bonus Schemes are added benefits of working in our progressive organisation. Holiday arrangements will be honoured. If you are interested in a career in Audio and Hi-Fi write at once to: **Kenneth Lasky, Lasky's Radio Limited, 3-15 Cavell Street, London E1 2BN.**

*Interviews will be arranged to suit your convenience.*

## SUPER SPEAKER BARGAINS

### WHARFEDALE DENTONS

A compact system sold in matched pairs for a perfectly balanced stereo system. Each Denton contains an 8in bass unit with 3in pressure unit, coupled by a Wharfedale crossover network. Rated input: 15 watts maximum. Frequency response: 65-17,000Hz. Impedance: 4/8 ohms. Cabinet 9 1/2in x 14in x 8 1/2in. Available in oiled teak finish and are small enough to blend in with most surroundings.

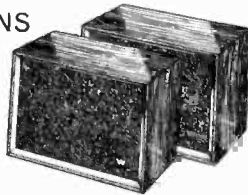

Post 50p

LIST PRICE £39.90 **LASKY'S PRICE £29.00**

### WHARFEDALE TRITONS

A new and exciting addition to the Wharfedale range, this three-speaker system will satisfy the most ardent Hi-Fi enthusiast. Shelf or floor standing—hand finished in oiled teak. Frequency response: 55-22,000Hz. C.A.B. Dome pressure unit. Bass unit 8in. Mid-range unit 5in. Treble unit 2in. Impedance: 8 ohms. Size: 21 1/2in x 9 1/2in x 9in.



Post 50p

LIST PRICE £59.90 **LASKY'S PRICE £39.00**

## EXCLUSIVE TM-1

### MODEL TM-1 MINI-TESTER

The first of Lasky's new-look top value meters, the TM-1 is a really tiny pocket multimeter providing "big" meter accuracy and performance. Precision movement calibrated to 3in of full scale. Click stop range selection switch. Beautifully designed and made impact resistant black case with white and metallic red/green figuring. Ohms zero adjustment.

#### Size Only

- 3 1/2in x 2 1/2in x 1 1/2in
- DC/V: 0-10-50-250-1,000 at 1k OPV
- AC/V: 0-10-50-250-1,000 at 1k OPV
- DC CURRENT: 0-1mA, 100mA

- Resistance: 0-150k
- Decibels: -10dB to 22dB
- Complete with test leads, battery and instructions



LIST PRICE £1.95 **LASKY'S PRICE £1.95** POST 13p

## TM-5 5K ohms/V POCKET MULTIMETER

Another new look pocket multimeter from Lasky's providing top quality and value. The "slimline" impact resistant case, size 4 1/2in x 2 1/2in x 1 1/2in, fitted with extra large 2 1/2in square meter. Readability is superior on all low ranges; making this an excellent instrument for servicing transistorised equipment. Recessed click stop selection switch. Ohms zero adjustment. Buff finish with crystal clear meter cover.

- DC/V: 3-15-150-300-1,200 at 5k OPV
- AC/V: 6-30-300-600 at 2.5k/OPV
- DC Current 0-300µA, 0-300mA
- Resistance: 0-10k/ohms, 0-1M/ohm
- Decibels: -10dB to +16dB
- Complete with test leads, battery and instructions.

LIST PRICE £2.95 **LASKY'S PRICE £2.95** POST 13p

## LASKY'S NEW "LOW NOISE" CASSETTES FROM THE U.S.A.

Model	Singles	5	10	20
C.60	32p	£1.52	£2.96	£5.60
C.90	50p	£2.37	£4.62	£8.75
C.120	69p	£3.28	£6.38	£10.85

Post Each 5p. 5-20p. 10-25p. 20-50p.

## TRIO KA.2002 PACKAGE DEAL TOP VALUE

- TRIO KA.2002 ..... £39.50
- Pair Wharfedale Dentons .. £39.90
- BSR MP60 ..... £15.20
- LASKY BASE & COVER ..... £4.75
- AD76K CARTRIDGE ..... £4.35

Total list price **£103.70**

## PACKAGE PRICE £79.50

Carriage in U.K. £2.00

ADD £9 if Wharfedale TRITONS are preferred to Dentons

## TMK MODEL 200 METER KIT

TMK offer the unique opportunity of building a really first-class precision multimeter at a worthwhile saving in cost. The cabinets are supplied with the meter scale and movement mounted in position. The highest quality components and 1% tolerance resistors are used throughout. Supplied complete with full construction circuit and operating instructions.

#### Specification


20,000 P.O.V. Multimeter. Features 24 measurement ranges with mirror scale accuracy. DC/V and current: 2%. A.C./V: 3%. Resistance 3%. Special 0-6V DC range for transistor circuit measurements.



ONLY

LIST PRICE £4.60 **LASKY'S PRICE £4.60** POST 13p

## DIGITAL CLOCK SCOOP

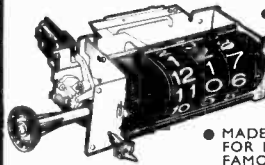

- SHOCK AND VIBRATION PROOF
- 12-HOUR ALARM
- AUTO "SLEEP" SWITCH
- HOURS, MINUTES AND SECONDS READ-OFF
- FORWARD AND BACKWARD TIME ADJUSTMENT
- SILENT OPERATION SYNCHRONOUS MOTOR
- MADE ESPECIALLY FOR LASKY'S BY FAMOUS MAKER
- MAINS OPERATION

- BUILT-IN ALARM BUZZER


EXCLUSIVELY FROM LASKY'S in chassis form for you to mount in any housing. The clock measures 4 1/2W x 1 1/2H x 3 1/2D (overall from front of drum to back of switch). SPEC.: 210/240V AC, 50Hz operation; switch rating 250V, 3A. Complete with instructions.

HUNDREDS OF APPLICATIONS. COMPLETE WITH KNOBS

LIST PRICE £6.50 **LASKY'S PRICE £6.50** POST 18p

SPECIAL QUOTATIONS FOR QUANTITIES
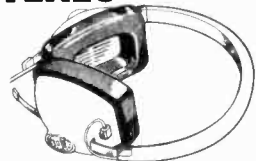
## TRIO HS.1 HS.2. STEREO HEADPHONE BARGAINS



Models HS.1 and HS.2. Both these sets by TRIO offer really superb stereo reproduction in a lightweight, fully adjustable headset designed for optimum comfort. Listening fatigue is unknown with TRIO headphones. Brief spec. both models: Input imp. 8 nominal (matching 4 to 8); max. input 0.5W; frequency response 20-19k Hz; output sensitivity at 1mW input: HS.1 118dB, HS.2 111dB; weight 0.66lb. Identical in appearance—both models are finished in ivory with contrasting foam-filled ear pads and head band.

HS.1. List Price £8.40.

HS.2. List Price £6.75.

Lasky's Price **£5.00**

Lasky's Price **£4.00** Post 18p

## Lasky's Radio Limited

#### Branches

207 EDGWARE ROAD, LONDON, W.2 Tel: 01-723 3271  
 33 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-636 2605  
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
 152/3 FLEET STREET, LONDON, E.C.4 Tel: 01-353 2833  
 Open all day Thursday, early closing 1 p.m. Saturday

#### The Home of High Fidelity

42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01-580 2573  
 Open all day, 9 a.m. - 6 p.m. Monday to Saturday  
**NEW CITY BRANCH NOW OPEN**  
 109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812  
 Open all day Thursday, early closing 1 p.m. Saturday

ALL MAIL ORDERS AND CORRESPONDENCE TO: 3-15 CAVELL ST. TOWER HAMLETS, LONDON, E.1 Tel: 01-790 4821



THE ULTIMATE IN COMMUNICATIONS RECEIVERS

# WORLD MASTER 8 WAVE BANDS

+ WORLD MAP & TIME ZONE DIAL



**Brings instant World Wide Reception at the touch of a button.**

The five continents to your armchair. What can we say about this superb radio—it gets everything! 2 short waves to cover the world! America—India—Africa—You name it—it gets it!

**MARINE BAND** (1.6-4mcs)  
**Medium Wave** 535-1605kcs.  
**Long Wave** 150-350kcs.  
**FM-VHF** 88-108mcs for B.B.C., Local Radio Stations.  
**AIRCRAFT** 108-135mcs. The complete aircraft band, hear the pilots talking to control. Police and Public Service Bands. 135-175mcs. Hundreds of shipping, "Private", RT calls, ambulances, taxis, gas boards, Radio Hams, etc. etc.  
 Battery/or Mains with A.F.C., tone control, volume control, internal and external aerials. Finished in black leatherette and stainless steel.  
**TRULY A COMPLETE COMMUNICATIONS RECEIVER**

CASH PRICE **£35.50**

+ 50p p. & p. or sent for £7.50 dep. + 50p p. & p. & 6 monthly payments of £5.60 (Total £41.10)

## PORTABLE COMMUNICATIONS RECEIVER

ONE OF THE WORLD'S MOST EXCITING RADIOS  
 - NO LESS THAN THREE V.H.F. BANDS

± THE ORDINARY MEDIUM BANDS

Yes, this is it—THE SUPER SNOOPER of all Radios! GETS all the usual BBC and Continental stations PLUS—AIRCRAFT (Civil and Military), TAXIS, FIRE BRIGADES, A.A., R.A.C., SHIPPING, LIFEBOATS, GAS BOARDS, ELECTRICITY BOARDS, RADIO HAMS, AMATEURS, AMBULANCES, "PRIVATE CONVERSATIONS" even TV SOUND and hundreds of other PUBLIC SERVICE TRANSMISSIONS—some we're not allowed to mention! Picks up all the Pop-pirates, Local Radio stations (those already transmitting and those planned for the future) both BBC and Commercial.

Hours and hours of endless enjoyment—a complete hobby in itself. One minute you can be listening to your favourite programme on BBC and then—at the flick of a switch—you can hear a crippled airliner being talked down to safety. YES! You can actually eavesdrop on the exciting conversations between pilot and control. **MAKES A SMASHING CAR RADIO!** Frequency range. Medium wave 540-1600kcs, FM-VHF 88-108mcs, AIR-VHF 108-136mcs. **PUBLIC SERVICE BANDS-VHF** 136-175mcs. Automatic Frequency Control to pinpoint station—locks on and completely eliminates drift. 16 Transistors, 7 diodes, 1 thermistor, **TWO AERIALS** one internal ferrite rod and one external telescopic antenna. Uses standard batteries. Beautifully finished in black grained leatherette with the latest push-button controls and slide rule tuning dials. Complete with hi-fidelity earphone and full written guarantee—spares always available. Size 10in x 6in x 4in. Instant cash refund if not satisfied.

Also available Battery/or mains Super de Luxe upright model. Same frequencies—but with built-in mains adaptor and battery re-charger (no need to buy batteries again!) **ONLY £18 POST FREE**



**NOW ONLY £16.80** +20p P&P  
 PREVIOUSLY SOLD THIS YEAR AT OVER £19.00

**SCIENTIFIC & TECHNICAL (PE1), 507-511 LONDON ROAD · WESTCLIFF · ESSEX**


## TV'S 19" NOW £11.95

TWO YEARS' GUARANTEE ALL MODELS


405/625: 19" £25.95; 23" £35.95

FREE CATALOGUE

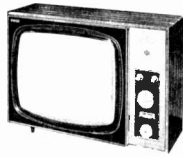DAILY DEMONSTRATIONS FOR PERSONAL SHOPPERS



**TEAK HI-FI STEREO CABINETS £14.95**

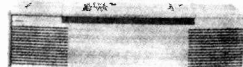

Brand new 44in wide x 16in deep x 18in high with legs. A superb piece of furniture. Carriage £1. **WHILE STOCKS LAST.**

**HI-FI VALUE**

(1) Garrard SP25 Mk. III: £11.50, P.P. 50p.

(2) Teak Plinth and Tinted Cover: £4.95, P.P. 35p.

(3) Sonatone 9TAHC Diamond Cartridge: £2.50.

1, 2, 3 Bargain Package. £17.95. P.P. 85p.



### COMPONENTS MUST BE CLEARED

**Transistor Radio Cases:** 25p each. Size 9 1/2in x 6 1/2in x 3 1/2in. Post 15p. **Speakers:** 35p, 2 1/2in 8Ω. Brand new. Post 15p.

**VHF/FM Tuners:** 95p. 88-108 mcs. takes EEC85 valve (extra). Post 15p.

**Pots:** 25p each. Post 5p. D/SW 500/500 KΩ. D/SW 500/100 KΩ. D/SW 1 meg./100 KΩ. S/SW 500/500 KΩ. S/SW 500/1 meg.

**Precision Tape Motors:** £1.95 200/250V. Famous German manufacturer. Post 20p.

**Transistor Gang Condensers:** 20p. Miniature AM. Post free. **Modern Gang Condensers:** 30p. AM/FM or AM only 20p. Post 10p.


**Transistors** 15p each. Post free. AC126, AC128, AF114, AF117, OC45, OC71, OC81, OC81D.

**Valve ELL80** 50p. Only stock in the country.

**DUKE & CO. (LONDON) LTD.**

621/3 ROMFORD ROAD, MANOR PARK, E12 Phone 01-478 6001-2-3
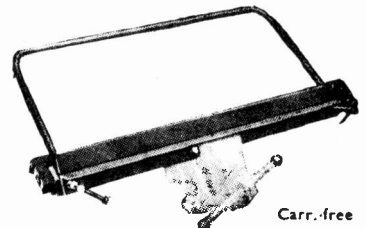
## PARKERS SHEET METAL FOLDING MACHINES HEAVY VICE MODELS



With Bevelled Former Bars

Carrr.-free

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £15
- No. 2. Capacity 18 gauge mild steel x 24in. wide ... £10
- No. 3. Capacity 16 gauge mild steel x 18in. wide ... £10

Also new bench models. Capacities 36in. x 18 gauge £30. 24in. x 16 gauge £29. Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 27 1/2p per ft. Other models 17 1/2p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

## FETS N CHANNEL FETS FULLY TESTED AND MARKED

Type	BVgss (Min.)	Igss (Max.)	Vp (Max.)	IDss (Max.)	R on (Max.)	Case
GP25*	20V	1nA	10V	20mA	—	TO72
GP71	20V	1nA	12V	150mA	190Ω	TO18

\* Similar to 2N3819

**ANY 6 — 60p**

PACKING AND POSTAGE FREE

SEND TO:

**DURHAM ELECTRONICS**  
 FREE POST • PETERLEE • CO. DURHAM  
 BUSINESS ENQUIRIES WELCOME • MINIMUM ORDER VALUE 60p  
 TERMS STRICTLY CASH WITH ORDER

**MAIL ORDER DIVISION**

**distronic LTD**

**THE POWER HOUSE**

**28 BURNT MILL  
ELIZABETH WAY  
HARLOW ESSEX  
HARLOW 32947**

**Why wait weeks? — ALL OUR ORDERS  
DISPATCHED BY RETURN OF POST!**  
Transistors, Diodes and Integrated Circuits

A) DIODES & RECTIFIERS			ACI87K } Matched ACI88K } pr. 50p ACI91 15p ACI92 15p ACI93 20p ACI93K } Matched ACI94K } pr. 60p ACI94 20p AD143 50p AD262 } Matched BD162 } pr. 90p AD262 35p AD263 40p AF106 25p AF109 35p AF139 31p AF166 18p AF170 18p AF172 25p AF200 30p AF201 40p AF239 45p AF239S 45p AL102 50p AL103 50p AU103 £1			BC109 11p BC113 20p BC114 20p BC115 25p BC116A 30p BC117 30p BC125 20p BC126 30p BC132 20p BC134 20p BC137 30p BC142 35p BC143 40p BC144 35p BC145 30p BC147 15p BC148 11p			BFX86 30p BFX87 30p BFX88 25p BFY34 30p		
Compare our prices			Please note minimum order 50p			2N3055 70p 115 Watt 15 Amp					
WOOS 40p WO1 45p WO4 48p WO6 50p			Send 10p for price list or free with order			2N3053 22p 1 Amp TO-5					
B) TRANSISTORS			Component Discounts 10% on orders over £5			BC107 11p Also BC108 and BC109					
2N696 15p 2N930 25p 2N930A 30p 2N1613 22p 2N1711 25p 2N2369 20p 2N2484 34p 2N2605 45p 2N2904 36p 2N2904A 41p 2N2905 46p 2N2905A 60p 2N3053 22p 2N3055 70p 2N3442 £2 2N3638 25p 2N3866 £1-50 2N4347 £1-50 2N4356 35p 40411 £2-50 AC138 15p AC141 20p AC141H 25p AC142 15p			AU106 95p AU107 70p AU108 65p AU110 £1 AU111 70p AUY21A 60p AUY22A 70p AUY35 45p AUY37 60p BC107 11p BC108 11p			BCY70 26p BCY71 26p BCY72 26p BF152 25p BF153 25p BF158 25p BF159 35p BF160 28p BF177 25p BF178 35p BF179C 40p			ME0404-1 12p ME0404-2 13p ME1001 10p ME1002 11p ME2001 10p ME2002 11p ME3001 20p ME3002 25p ME4001 10p ME4002 11p ME6001 15p ME6002 18p ME8001 20p ME8002 30p ME8003 30p ME9001 15p ME9002 15p MEL11 40p MEL12 50p MEU21 40p MEU22 50p OC25 37p		
C) INTEGRATED CIRCUITS			709C (TO-99) 95p 709C (DIP) 95p 741C (TO-99) 25p 741C (DIP) £1-25			2N3866 £1-50 1 Watt output at 400MHz					
			741C £1-25			BC114 20p High gain: 200 at 1mA					
						741C £1-25 High gain operational amp. S/C proof					

**POSTAGE & PACKING PLEASE ADD 10p TO YOUR ORDER**

**SEND FOR  
BONUS VOUCHER  
FREE WITH EVERY  
£1 ORDER**

\*Redeemable upon receipt of subsequent order value £5 or more, received before March 31, 1972

**BONUS VOUCHER**

Some things are more than money. Some things are more than money. Some things are more than money. Some things are more than money.

**distronic LTD**

28 BURNT MILL, ELIZABETH WAY, HARLOW, ESSEX







**LARGEST STOCKS  
WIDEST RANGE**

**SEMICONDUCTORS & COMPONENTS**

**BRAND NEW  
GUARANTEED**

**TRANSISTORS**

2G301	20p	2N3405	45p	4031	85p	BC172	15p	BSW70	271p	NKT238	25p
2G302	20p	2N3414	221p	40312	471p	BC175	221p	BSX19	171p	NKT240	271p
2G303	20p	2N3415	221p	40314	371p	BC182	10p	BSX20	171p	NKT241	271p
2G306	421p	2N3416	371p	40320	471p	BC183	9p	BSX21	371p	NKT242	271p
2G307	20p	2N3417	371p	40323	321p	BC184	11p	BSX26	45p	NKT243	271p
2G308	20p	2N3418	371p	40324	13p	BC184	11p	BSX27	471p	NKT245	271p
2G371	15p	2N3472	271p	40326	371p	BC184	11p	BSX26	45p	NKT245	271p
2G374	20p	2N3605	271p	40329	371p	BCY31	30p	BSX60	821p	NKT261	271p
2G381	221p	2N3606	271p	40347	571p	BCY32	50p	BSX61	621p	NKT262	30p
2N404	221p	2N3607	221p	40347	571p	BCY33	25p	BSX76	221p	NKT264	20p
2N696	20p	2N3702	11p	40348	571p	BCY34	30p	BSX77	271p	NKT271	20p
2N697	20p	2N3703	10p	40360	421p	BCY38	40p	BSX78	271p	NKT272	20p
2N698	20p	2N3704	11p	40361	471p	BCY39	60p	BSX78	271p	NKT274	20p
2N706	121p	2N3705	10p	40362	571p	BCY42	15p	BSY10	271p	NKT275	20p
2N708A	121p	2N3706	10p	40370	321p	BCY42	15p	BSY11	271p	NKT281	271p
2N708	15p	2N3707	11p	40406	571p	BCY43	15p	BSY11	271p	NKT281	271p
2N709	621p	2N3708	7p	40406	571p	BCY43	15p	BSY11	271p	NKT281	271p
2N718	25p	2N3709	9p	40407	571p	BCY43	15p	BSY11	271p	NKT281	271p
2N726	30p	2N3710	10p	40407	571p	BCY43	15p	BSY11	271p	NKT281	271p
2N727	30p	2N3711	12p	40410	621p	BCY43	15p	BSY11	271p	NKT281	271p
2N914	171p	2N3715	15p	40467A	571p	BCY60	971p	BSY27	171p	NKT405	75p
2N916	171p	2N3716	21-30	40468A	85p	BCY71	20p	BSY28	171p	NKT406	621p
2N918	30p	2N3791	22-30	40600	571p	BCY72	171p	BSY32	25p	NKT451	621p
2N929	221p	2N3819	30p	40673	85p	BCZ10	271p	BSY36	25p	NKT452	621p
2N930	271p	2N3823	971p	AC107	30p	BCZ11	421p	BSY37	25p	NKT453	471p
2N1090	221p	2N3854	271p	AC126	20p	BD116	21-121	BSY38	221p	NKT613F	321p
2N1091	221p	2N3854A	271p	AC127	20p	BD121	65p	BSY39	221p	NKT614F	30p
2N1131	20p	2N3859	271p	AC128	20p	BD123	821p	BSY41	321p	NKT677F	30p
2N1132	20p	2N3855A	30p	AC154	221p	BD129	1-55p	BSY42	321p	NKT713	25p
2N1390	221p	2N3856	30p	AC176	25p	BD131	75p	BSY43	371p	NKT781	30p
2N1392	20p	2N3856A	35p	AC187	621p	BD132	85p	BSY43	371p	NKT781	30p
2N1304	221p	2N3858	25p	AC188	371p	BDY10	21-371	BSY44	40p	NKT10419	30p
2N1305	221p	2N3858A	30p	ACY17	271p	BDY11	21-621	BSY46	90p	NKT10439	371p
2N1306	20p	2N3859	271p	ACY18	25p	BDY17	21-60	BSY78	45p	NKT10519	321p
2N1307	20p	2N3859A	30p	ACY19	25p	BDY18	21-75	BSY79	45p	NKT20329	471p
2N1308	30p	2N3860	30p	ACY21	25p	BDY19	21-82	BSY82	571p	NKT20339	371p
2N1309	30p	2N3866	21-50	ACY21	25p	BDY20	21-121	BSY90	571p	NKT80111	721p
2N1507	171p	2N3877	40p	ACY22	20p	BDY38	971p	BSY95A	121p	NKT80112	971p
2N1613	25p	2N3877A	40p	ACY28	20p	BDY60	21-25	C111	75p	NKT80113	121p
2N1621	35p	2N3900	371p	ACY40	20p	BDY61	21-25	C424	271p	NKT80211	121p
2N1632	20p	2N3900A	40p	ACY41	25p	BDY62	21	C425	55p	NKT80212	921p
2N1637	30p	2N3901	971p	ACY44	40p	BF117	471p	C426	40p	NKT80213	921p
2N1638	271p	2N3903	35p	AD140	521p	BF115	371p	C428	371p	NKT80214	921p
2N1671B	81p	2N3904	35p	AD149	571p	BF167	18p	C744	30p	NKT80215	921p
2N1711	25p	2N3905	371p	AD150	621p	BF173	18p	D18T1	621p	NKT80216	921p
2N1889	321p	2N3906	371p	AD161	371p	BF177	30p	D18P1	371p	OC20	75p
2N1893	371p	2N4058	171p	AD162	371p	BF178	30p	D18P2	371p	OC22	50p
2N2147	821p	2N4059	10p	AF106	421p	BF179	30p	D18P3	371p	OC23	60p
2N2148	821p	2N4060	121p	AF114	421p	BF180	35p	D40N1	75p	OC24	60p
2N2160	571p	2N4061	121p	AF115	25p	BF181	35p	GET102	30p	OC25	50p
2N2193	40p	2N4062	121p	AF116	25p	BF184	25p	GET113	20p	OC28	271p
2N2193A	421p	2N4244	471p	AF117	25p	BF185	421p	GET114	20p	OC29	621p
2N2184	80p	2N4285	171p	AF118	621p	BF194	171p	GET118	30p	OC36	50p
2N2217	271p	2N4286	171p	AF119	221p	BF195	15p	GET119	30p	OC36	621p
2N2218	25p	2N4287	171p	AF120	221p	BF196	421p	GET120	521p	OC41	221p
2N2220	25p	2N4289	171p	AF123	20p	BF197	421p	GET123	121p	OC42	25p
2N2221	25p	2N4290	171p	AF125	20p	BF198	421p	GET124	30p	OC43	25p
2N2222	20p	2N4291	171p	AF127	171p	BF200	521p	GET128	30p	OC44	20p
2N2287	21-07p	2N4292	121p	AF139	371p	BF224	14p	GET187	20p	OC45	121p
2N2287	20p	2N4303	471p	AF178	421p	BF225	19p	GET189	221p	OC46	15p
2N2289	171p	2N4307	521p	AF179	781p	BF227	23p	GET189	221p	OC70	15p
2N2366	171p	2N4308	471p	AF180	521p	BF244	23p	GET189	221p	OC71	121p
2N2369A	171p	2N4309	471p	AF181	421p	BF248	271p	GET189	221p	OC72	121p
2N2483	271p	2N5172	121p	AF239	421p	BF259	25p	GET189	221p	OC74	321p
2N2484	321p	2N5174	521p	AF279	471p	BF260	25p	MJ400	21-07	OC75	221p
2N2539	20p	2N5175	521p	AF280	521p	BF261	25p	MJ420	21-07	OC76	221p
2N2640	221p	2N5176	521p	AF281	221p	BF262	471p	MJ421	21-07	OC77	221p
2N2613	35p	2N5232A	40p	AFY26	25p	BFX13	221p	MJ430	21-07	OC78	221p
2N2614	30p	2N5245	45p	AFY27	271p	BFX29	30p	MJ440	971p	OC81D	221p
2N2646	521p	2N5246	421p	AFY28	271p	BFX30	30p	MJ480	971p	OC82	25p
2N2696	321p	2N5249	671p	AFY29	271p	BFX43	371p	MJ481	21-25	OC84	35p
2N2711	25p	2N5256	23-25	AFY36	25p	BFX44	371p	MJ490	21-371	OC140	321p
2N2712	20p	2N5265	27-28	AFY50	25p	BFX68	671p	MJ491	21-371	OC170	30p
2N2713	271p	2N5267	22-25	AFY51	321p	BFX82	25p	MJ530	22-171	OC171	30p
2N2714	30p	2N5305	371p	AFY60	321p	BFX85	25p	MJ530	22-171	OC200	40p
2N2865	621p	2N5306	40p	AFY64	321p	BFX86	25p	MJ530	22-171	OC201	60p
2N2901	30p	2N5307	371p	AFY86	321p	BFX87	271p	MJ530	22-171	OC202	60p
2N2904A	321p	2N5308	371p	ABZ21	421p	BFX88	25p	MJ530	22-171	OC203	421p
2N2905	371p	2N5309	621p	AU103	21-25	BFX89	621p	MJ530	22-171	OC204	421p
2N2905A	45p	2N5310	421p	BC107	10p	BFY9A	70p	MJE521	75p	OC205	421p
2N2906	25p	2N5354	271p	BC108	10p	BFY10	321p	MJE521	75p	OC206	90p
2N2906A	271p	2N5355	271p	BC109	10p	BFY11	221p	MJE521	75p	OC207	75p
2N2907	30p	2N5356	321p	BC110	10p	BFY12	221p	MJE521	75p	OC208	75p
2N2923	15p	2N5385	471p	BC111	15p	BFY18	221p	MJE521	75p	OC209	75p
2N2924	15p	2N5386	321p	BC115	15p	BFY19	221p	MJE521	75p	OC210	75p
2N2925	15p	2N5387	571p	BC116A	10p	BFY20	221p	MJE521	75p	OC211	75p
2N2926	15p	2N5457	371p	BC118	10p	BFY21	221p	MJE521	75p	OC212	75p
.. Green	14p	2N805	75p	BC121	20p	BFY24	45p	MJE521	75p	OC213	75p
.. Yellow	121p	2N802	22	BC122	20p	BFY25	45p	MJE521	75p	OC214	75p
.. Orange	121p	2N810	60p	BC125	20p	BFY26	20p	MJE521	75p	OC215	75p
2N3011	30p	2N8103	25p	BC126	20p	BFY29	50p	MJE521	75p	OC216	75p
2N3014	321p	2N8104	25p	BC140	371p	BFY30	50p	MJE521	75p	OC217	75p
2N3053	30p	2N8101	25p	BC147	10p	BFY43	621p	MJE521	75p	OC218	75p
2N3054	45p	2N8502	35p	BC148	10p	BFY44	621p	MJE521	75p	OC219	75p
2N3055	62p	2N8503	271p	BC149	10p	BFY50	23p	MJE521	75p	OC220	75p
2N3133	30p	2N3128	70p	BC152	171p	BFY51	20p	MJE521	75p	OC221	75p
2N3134	30p	2N3139	21-271	BC157	20p	BFY52	23p	MJE521	75p	OC222	75p
2N3135	25p	2N3140	771p	BC158	171p	BFY53	171p	MJE521	75p	OC223	75p
2N3136	20p	2N3141	75p	BC159	12p	BFY54	571p	MJE521	75p	OC224	75p
2N3380	25p	2N3142	671p	BC160	621p	BFY76	421p	MJE521	75p	OC225	75p
2N3391	20p	2N3143	671p	BC167	11p	BFY77	571p	MJE521	75p	OC226	75p
2N3391A	30p	2N3152	871p	BC168B	10p	BFY90	671p	MJE521	75p	OC227	75p
2N3392	171p	R.C.A.:	—	BC169C	11p	BPX25	21-85	MJE521	75p	OC228	75p
2N3393	15p	40050	55p	BC170	12						


# JUST BEGINNING?

Then try out **8-Watt, 10-Transistor Stereo Amplifier R.137**

**ROC price**  
**£10.50**

Separate tone and volume controls for each channel, inputs for turntable (ceramic cartridge), tuner and tape. Attractive black crackle finish with brushed aluminium front. Frequency response: 70-20,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 80mV; tuner/aux 80mV.

Normal retail price: **£14.70**

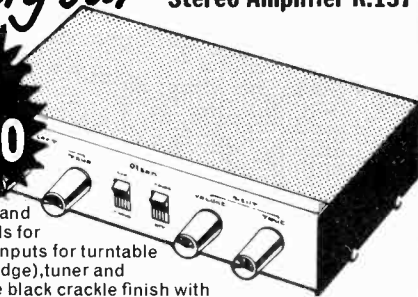


# FIRST STEP TO STEREO!

**5-Watt Transistor Stereo Amplifier Chassis R.123**

Completely self-contained, fully transistorised, mains-powered (240V AC) amplifier, needing only cabinet and knobs. Ideal for adapting mono players to stereo. Frequency response: 40-17,000 Hz  $\pm$  3dB. Output: 2.5 watts per channel @ 8 ohms. Input: Phono 600mV.

Normal retail price: **£7.30**

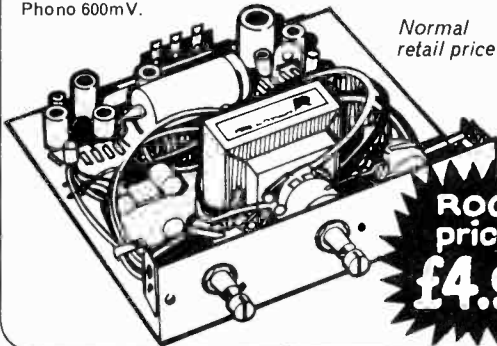

**ROC price**  
**£4.95**


# SOUNDS SENSATIONAL

**AM/FM/MPX Stereo Tuner Amplifier R.124**

A top quality amplifier with facility for receiving stereo broadcasts. Separate bass and treble controls, automatic frequency response, stereo headphone socket, output power: 8 watts. FM frequency range 88-108 MHz; AM frequency range 535-1605 KHz. Inputs for turntable (ceramic cartridge) and tape. Frequency response: 50-10,000 Hz  $\pm$  3dB. Output: 4 watts per channel @ 8 ohms. Inputs: Phono 200mV, tape 100mV. FM: Sensitivity 20 $\mu$ V, stereo separation 26dB, image rejection 55dB. AM: Sensitivity 300 $\mu$ V.

Normal retail price: **£42.00**

**ROC price: £29.95**

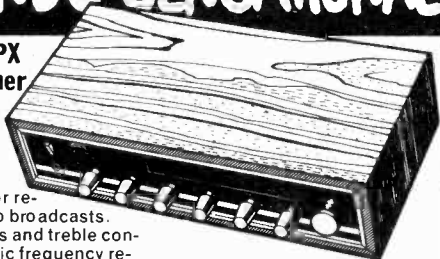


# World wide reception

**Professional Solid-state, Four-band Communications Receiver R.135**

Fully transistorised with continuous coverage from 555K Hz to 30 MHz in four bands (with illuminated bandspread for 160-10 metres). Incorporates internal speaker, automatic noise limiter, SSB/AM/CW switch, AVC switch, S Meter, Receive and Standby switch, external socket for headphone or speaker, bandspread control, BFO control, on/off/AF gain, band selector, antenna trimmer and RF gain. Runs off 240 v AC, batteries or any 12 v DC negative ground source. Frequency ranges (in MHz): Band A, 535-1.6; B, 1.55-4.5; C, 4.5-13; D, 13-30. Sensitivity: 0.5 $\mu$ V @ 30mHz. Bandsread: 10-160 metres.

Normal retail price: **£65.00**

**ROC price:**  
**£45.00**

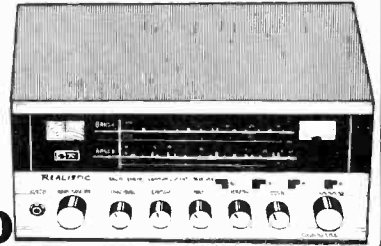


# AMAZING OFFER!

**Stereo Cassette Tape Unit R.142**

Complete stereo record and playback unit with line and microphone inputs. Fitted with tape counter, separate pause control, recording level metres for each channel, pop-up cassette ejection. Supplied complete with two pencil microphones. Wow & flutter better than 0.3%, frequency response 100-10,000 Hz. Tape speed: 1 1/2 IPS, 4.75 CMS. Rewind time: Better than 60 sec (C.60 cassette).  
Normal retail price: **£65.00**

**ROC price**  
**£49.50**

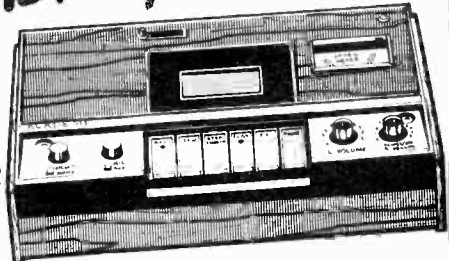


# We don't want you to

Every piece of electronic or audio-equipment we sell is built to our specifications. It comes complete with a Guarantee. And it's tested before it leaves us.

We bend over backwards in our advertising to make sure everything we say is factually accurate. But, buying mail-order, even though you're buying from us, we accept you could still end up with a piece of equipment that's not exactly what you wanted. And we think that's unfair.

# FANTASTIC BARGAIN

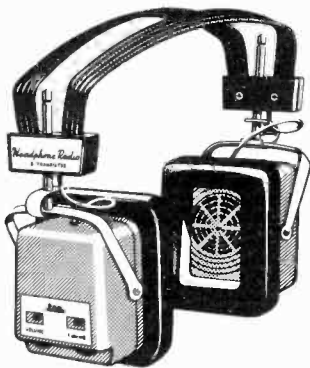


**Headphone Radio R.143**  
For completely private listening without the distortion of the ordinary earphone adaptor. Battery operated; PP3. Fully transistorised. Frequency range: 535-1600 K Hz, Medium Wave Band. Maximum output: 300mW.

**ROC price**  
**£6.90**

Normal retail price: £9.40

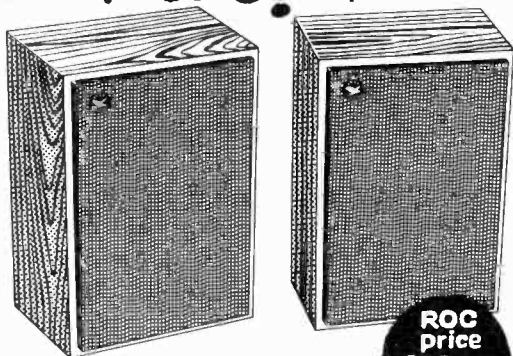**2 for the price of one!** **Matched Stereo Speakers R.446**



Heavily lagged teak finish cabinets each with large dual cone base unit and separate tweeter. Power handling: 10 watts peak; frequency range: 40-18,000 Hz, impedance: 8 ohms. Size: 14 x 8½ x 6½.

Normal retail price: £19.60

**ROC price**  
**£16.40**

## pay for your mistakes

So we've got a proposition for you. If you buy a piece of Roc equipment, and it's not quite what you expected, send it back within seven days, and as long as it's as good as new we'll give you your money back. O.K?

Return of post mail-order service; orders over £10 post free, (U.K. only) add 25p for p & p to orders under £10. HP terms available.

**ROC ELECTRONICS LIMITED**  
193 B Edgware Road, London W2 1ET. Phone: 01-723 6211.

Callers at Shop welcome 9-6 Mon to Sat (Thurs 1pm)

# STEREO headphones

only  
**£2.40**




**Stereo Headphones R.328**

Light and comfortable, with a frequency response of 30-15,000 Hz for real listening pleasure. Complete with jack plug. Impedance 8-16 ohms. Normal retail price: £2.95
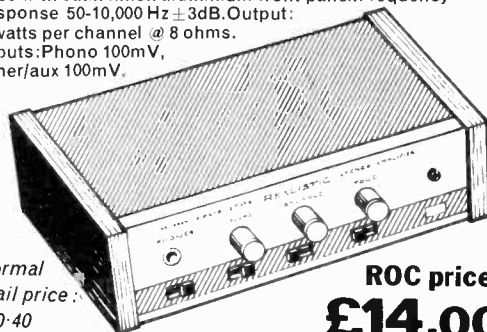
## Don't read this!

**10-watt Transistor Stereo Amplifier R.136**  
Ganged volume, balance and tone controls. Inputs for turntable (ceramic cartridge), tuner (see R.134) or tape. Oiled walnut case with satin finish aluminium front panel. Frequency response 50-10,000 Hz ± 3dB. Output: 5 watts per channel @ 8 ohms. Inputs: Phono 100mV, tuner/aux 100mV.



Normal retail price: £20.40

**ROC price: £14.00**

## The Perfect match!



**AM/FM/MPX Stereo Tuner R.134**

Matching unit to the R.136 amplifier. Covers AM and FM tuning bands with automatic stereo signal light. FM frequency range: 88-108MHz; AM frequency range: 535-1605kHz. FM: Sensitivity 5µV, stereo separation 25dB@1kHz, image rejection 50dB. AM: Sensitivity 250µV.

Normal retail price: £28.60

**ROC price**  
**£22**

# THE BIG DISCOUNT HOUSE

## TURNTABLES p.p. 80p

	£p
Garrard SP25 Mk. III	9.95
Garrard 2025 tc with Sonatone 9TAHCD cart.	8.50
Garrard A70 Mk. II (Transcription Deck)	9.95
Garrard SL65b	13.25
Garrard AP76	18.50
Garrard 401	26.00
Garrard SL72b	24.00
Garrard SL75b	25.00
Garrard SL95b	34.00
Garrard ZERO 100	35.00
B.R.S. McDonald Range in stock	
Sonab 75s and 85s in stock	
Transcriptors range in stock	
Goldring GL85	47.50
Goldring GL85/P	57.00
Goldring LID85	5.25
Goldring GL75	28.50
Goldring GL75/P	36.50
Goldring Plinth 75	7.00
Goldring LID75	3.75
Goldring GL72	23.00
Goldring GL72/p	31.00
Goldring Plinth 72	7.00
Goldring LID72	3.75
Goldring G.99	22.00
Goldring G.99	9.00
Goldring G101/p	22.00
Philips GA202	53.00
Philips GA160	27.00
Philips GA105	15.50
Philips GA308	30.00
Thorens TD150AB	40.00
Thorens TD150A	36.00
Thorens TX11	3.90
Thorens TD150	31.50
Thorens TD125	61.00
Thorens TD125AB	92.00
Thorens TX25	7.50
Connoisseur	p.o.a.

## SPECIAL OFFER

FREE 10" LP for personal callers buying a complete system Monday to Thursday

## CARTRIDGES p.p. 15p

	£p
Goldring G.850	4.10
Goldring G.800	6.75
Goldring G.800/E	11.75
Goldring G.800/SE	17.00
Sonatone 9TAHCD	1.65
Shure M3D	4.95
Shure M44 5/7	6.75
Shure M44/E	7.95
Shure M55/E	8.75
Shure M75E type II	14.00
Shure M75EJII	13.50
Shure M756	10.50
Shure V15 II	27.25
Ortofon MF15E	18.75
Audio Technica AT66	4.10
Audio Technica AT55	3.75
ADC10E II	21.00
ADC26	47.00
ADC27	39.00
ADC550XE	14.00
Empire 100ZE	50.00
Empire 999E/X	34.75
Empire 999E/X	20.75
Empire 999E/X	16.75
Empire 999E/X	12.50
Empire 999/X	10.00
Empire 909E/X	9.75
Empire 909/X	7.60
Empire 90EE/X	7.70

## SPEAKER KITS priced per pair

p.p. (a) £1. (b) £1.50	£p
Wharfedale Unit 3	20.00 a
Wharfedale Unit 4	27.00 b
Wharfedale Unit 5	37.00 b
Richard Allan Twin Assembly	18.00 a
Richard Allan Triple Assembly	27.50 b
Richard Allan Super Triple	35.00 b
KEF	p.o.a.
Goodmans DIN 20 Kit	19.95 a
Peerless 20-2	22.00 a
Peerless 20-3	31.00 b
Peerless 43-12	38.00 b

## FULL RANGE OF SINCLAIR PRODUCTS IN STOCK

SEND A LARGE S.A.E. FOR OUR COMPLETE LISTING OF ALL HI-FI EQUIPMENT

CREDIT FACILITIES AVAILABLE  
SEND STAMPED ADDRESSED ENVELOPE FOR FURTHER INFORMATION

PERSONAL CALLERS WELCOME

### OPEN

Mon. to Wed. 9.30 am - 6 pm Fri. open until 8.00 pm  
Half day Thurs. until 1.00 pm Sat. 9.30 am - 6 pm

Personal callers please note that Cheques are only accepted if backed by a relevant bank cheque card. Payment by Barclaycard accepted by arrangement.

All prices subject to change without notice as and when necessary

# AUDIO SUPPLIES

Dept PE12, 50 STAMFORD HILL, LONDON N16

Telephone: 01-806 3611

We are easy to find, 50 yds from Stoke Newington (BR) Station. 106, 67, 149, 76, 73, 249, 243, 247 Buses pass our door.

# Give us six months, and we'll turn your hobby into a career.

You have a hobby for a very good reason. It gives you a lot of pleasure.

So if you can find a job that involves your hobby, chances are you'll enjoy your work more, and you'll do better work.

Now CDI can help you find such a job. A job where you'll be responsible for the maintenance of a computer installation. A job that pays well too. If you're interested in mechanics or electronics (without necessarily being a

mathematical genius), have a clear, logical mind and a will to work, then we can train you to be a Computer Engineer inside six months.

So give us a call. CDI. We're the Education Division of one of the world's largest computer manufacturers. And we have the experience to know if you can make it. A ten minute talk with us, and you could be on the way to spending the rest of your life with your hobby.

Ring

## 01-637 2171

between 9 a.m. and 9 p.m. and ask for Mr Potter

It's quicker and easier to phone, but if you prefer, send this coupon to: Control Data Institute, Wells House, 77 Wells Street, London, W.1.

Please give me further information.

Name \_\_\_\_\_

Address \_\_\_\_\_

Age \_\_\_\_\_

Phone \_\_\_\_\_

4L1

**CONTROL DATA INSTITUTE**

**CONTROL DATA LIMITED**

The Education Division of one of the world's largest Computer manufacturers.

# BI-PRE-PAK LIMITED

## FULLY TESTED AND MARKED

	£p		£p
AC107	0-15	OC170	0-23
AC126	0-13	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-13	OC201	0-25
AC176	0-25	2G301	0-13
ACY17	0-15	2G303	0-13
AF239	0-37	BC113	0-10
AF186	0-50	2N1302-3	0-20
AF139	0-37	2N1304-5	0-25
BC154	0-25	2N1306-7	0-30
BC171 = BC107	0-13	2N1308-9	0-35
BC172 = BC108	0-13	2N3819FET	0-45
BF194	0-15		
BF274	0-15	<b>Power</b>	
BFY50	0-20	<b>Transistors</b>	0-50
BSY25	0-57	OC23	0-30
BSY26	0-13	OC25	0-25
BSY27	0-13	OC26	0-25
BSY28	0-13	OC28	0-30
BSY29	0-13	OC35	0-25
BSY95A	0-15	OC36	0-37
OC41	0-13	AD149	0-30
OC44	0-13	AUY10	1-25
OC75	0-13	25034	0-25
OC72	0-13	2N3055	0-63
OC73	0-17	<b>Diodes</b>	
OC81	0-13	AA742	0-10
OC81D	0-13	OA95	0-10
OC83	0-20	OA79	0-09
OC139	0-13	OA81	0-09
OC140	0-17	IN9114	0-07

## FREE!

PACKS OF YOUR OWN CHOICE UP TO THE VALUE OF 50p WITH ORDERS OVER £4

## CLEARANCE LINES

**COLOUR T.V. LINE OUTPUT TRANSFORMERS.** Designed to give 25KV when used with PL509 and PY500 valves. As removed from colour receivers at the factory. **NOW ONLY 50p each.** Post and Packing 25p.

1 Amp. Plastic Rectifiers. These are voltage, reverse polarity and other rejects from the BY127 range. Ideal for low voltage Power Units, etc. Price: £1 per 100.

	1-10	10-50	50+
BB105 Varicap Diodes	10	8	6
OC71 or 72 Fully tested Unmarked	5	5	4
Matched sets, 1-OC44 & 2-OC45's, Per Set	25	20	15
Matched Sets of OC45's 1st & 2nd IF	15	12	10
OA47 Gold Bonded Diodes, Marked & tested	3	3	2
1 Watt Zener Diodes 7.5, 24, 27, 30, 36, 43, Volts	5	4	3
10 Watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 20, 100v.	20	17	15
Micro Switches, S/P, C/O.	25	20	15
1 Amp. Bridge Rect. 25v.	25	22	20

## INTEGRATED CIRCUITS

SL403D Audio Amp. 3 Watt	200	1-95	1-80
709C Linear Opp. Amp.	50	40	35
Gates Factory Marked & Tested by A.E.I.	25	22	20
J.K. Flip Flops Factory Marked & Tested, A.E.I.	40	35	30
PA234 1 Watt Audio Amp.	1-00	90	80
UL914 Dual 2 I/P Gate	40	35	30

## NEW TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA.	50p
B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors. Postage 13p. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Postage 10p. Approx. quantity, counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values. Postage 8p	50p
H8	4	BY127 Sil. Recs. 1000 PIV. 1 amp. plastic	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H12	50	NKT155/259 Germ. diodes, brand new stock clearance	50p
H18	10	OC71/75 uncodded black glass type PNP Germ.	50p
H19	10	OC81/81D uncodded white glass type PNP Germ.	50p
H28	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H29	20	OA47 gold bonded diodes coded MCS2	50p

## F.E.T. PRICE BREAKTHROUGH !!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819.

Data sheet supplied with device.

1-10 30p each, 10-50 25p each, 50+ 20p each.

**Make a Rev. Counter for your Car.** The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car. **£1 each**

**FREE CATALOGUE AND LISTS for:—**  
**TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS,**  
**FULL PRE-PAK LISTS & SUBSTITUTION CHART**

**MINIMUM ORDER 50p CASH WITH ORDER PLEASE.** Add 10p post and packing per order. **OVERSEAS ADD EXTRA FOR AIRMAIL.**

## 8 RELAYS FOR £1

Various Contacts and Coil Resistances. No individual selection. Post and Packing 25p

## OUR VERY POPULAR 3p TRANSISTORS

FULLY TESTED & GUARANTEED

- TYPE "A" PNP Silicon alloy, metal TO-5 can. 2S300 type, direct replacement for the OC200/203 range.
- TYPE "B" PNP Silicon, plastic encapsulation, low voltage but good gain, these are of the 2N3702/3 and 2N4059/62 range.
- TYPE "E" PNP Germanium AF or RF—please state on order. Fully marked and tested.
- TYPE "F" NPN Silicon plastic encapsulation, low noise amplifier of the 2N3708, 9, 10, 11.

## BULK BUYING CORNER

NPN/PNP Silicon Planar Transistors, mixed, untested, similar to 2N706/6A/8, BSY26-29, BSY95A, BCY70, etc. £4-25 per 500; £8 per 1,000.

Silicon Planar NPN Plastic Transistors, untested, similar to 2N3707-11, etc., £4-25 per 500; £8 per 1,000.

Silicon Planar Diodes, DO-7 Glass, similar to OA200/202, BAY31-36, £4-50 per 1,000.

NPN/PNP Silicon Planar Transistors, Plastic TO-18, similar to BC113/4, BC153/4, BF153/160, etc., £4-25 per 500; £8 per 1,000.

OC44, OC55 Transistors fully marked and tested, 500+ at 8p each; 1,000+ at 6p each.

OC71 Transistors, fully marked and tested, 500+ at 6p each; 1,000+ at 5p each.

3823E Field effect Transistors. This is the 2N3823 in Plastic Case, 500+ 13p each; 1,000+ 10p each.

**1 amp Miniature Plastic Diodes:**  
 IN4001, 500+ 3p each; 1,000+ 3p each.  
 IN4004, 500+ at 5p each, 1,000+ at 4p each.  
 IN4006, 500+ at 6p each, 1,000+ at 5p each.  
 IN4007, 500+ at 8p each, 1,000+ at 7p each.

## NEW UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN916 types	50p
B88	50	Sil. Trans. NPN, PNP, equiv. to OC200/1, 2N706A, BSY95A, etc.	50p
B60	10	7 Watt Zener Diodes Mixed Voltages	50p
H6	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H10	25	Mixed volts, 1½ watt Zeners. Top hat type	50p
H11	30	MAT Series " alloy " npn Transistors	50p
H15	30	Top Hat Silicon Rectifiers, 750mA. Mixed volts.	50p
H16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H20	20	BY126/7 Type Silicon Rectifiers, 1 amp plastic. Mixed volts.	50p

**FREE! A WRITTEN GUARANTEE WITH ALL OUR TESTED SEMICONDUCTORS**

**BI-PRE-PAK LTD** DEPT. A, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX  
 TELEPHONE: SOUTHEND (0702) 46344

# YATES ELECTRONICS

(FLITWICK LTD)

## RESISTORS

1/4W Iskra high stability carbon film—very low noise—capless construction.  
1/4W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm. 4W Erie wire wound.

Power watts	Tolerance	Range	Valves available	Price
1/4	5%	4.7Ω-22MΩ	E24	1-99 100+
1/4	10%	3.3MΩ-10MΩ	E12	1-0p 0-8p
1/4	10%	1Ω-3.9Ω	E12	1-0p 0-8p
1/4	5%	4.7Ω-1MΩ	E12	1-0p 0-8p
1/4	10%	1Ω-10Ω	E12	6p 5-5p

Quantity price applies for any selection. Ignore fractions on total order.

## DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.  
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

## POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log 1/2W, lin 1/4W).  
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

## SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C. mounting (0-1 matrix).  
Sub-miniature 0-1W, 5p each. Miniature 0-25W, 6p each.

## SEMICONDUCTORS

AC126	12p	BFY52	22p	OC81	12p	2N3055	72p
AC127	12p	BSY56	30p	OC82	12p	2N3702	15p
AC128	12p	BSX21	25p	ORP12	48p	2N3703	14p
AD140	40p	BY124	71p	IN4001	71p	2N3704	171p
AF115	20p	BYZ10	20p	IN4002	10p	2N3705	15p
AF117	20p	BYZ13	20p	IN4003	11p	2N3706	12p
BC107	10p	OA85	7p	IN4004	12p	2N3707	181p
BC108	10p	OA91	5p	IN4005	13p	2N3708	10p
BC109	10p	OA202	7p	IN4006	13p	2N3709	11p
BFY50	22p	OC71	12p	IN4007	13p	2N3710	12p
BFY51	22p	OC72	12p	2N2926	11p	2N3711	14p

## ZENER DIODES

400mW 5% 3-3V to 30V, 15p.

## ROTARY SWITCHES

2P2W, 1P12W, 2P6W, 3P4W, 4P3W, 23p.

## BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2 1/2in = 10p; 9in x 2in = 7p.

ELSTOW STORAGE DEPOT,  
KEMPSTON HARDWICK,  
BEDFORD

C.W.O. PLEASE. POST AND PACKING  
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the components listed will be sent free on request. 5p stamp appreciated.

10% DISCOUNT TO ALL CALLERS ON SATURDAYS

## MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0-001μF, 0-0015μF, 0-0022μF, 0-0033μF, 0-0047μF, 2 1/2p, 0-0068μF, 0-01μF, 0-015μF, 0-022μF, 0-033μF, 3p, 0-047μF, 0-068μF, 0-1μF, 4p, 0-15μF, 6p, 0-22μF, 7 1/2p, 0-33μF, 11p, 0-47μF, 13p.  
160V: 0-01μF, 0-015μF, 0-022μF, 0-033μF, 0-047μF, 0-068μF, 3p, 0-1μF 3 1/2p, 0-15μF 4 1/2p, 0-22μF, 5p, 0-33μF, 6p, 0-47μF, 7 1/2p, 0-68μF, 11p, 1-0μF, 13p.

## MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0-01μF, 0-015μF, 0-022μF, 3p, 0-033μF, 0-047μF, 0-068μF, 3 1/2p, 0-1μF, 4p, 0-15μF, 0-22μF, 5p, 0-33μF, 6 1/2p, 0-47μF, 8 1/2p, 0-68μF, 11p, 1-0μF, 13p, 1-5μF, 20p, 2-2μF, 24p.

## MYLAR FILM CAPACITORS 100V

0-001μF, 0-002μF, 0-005μF, 0-01μF, 0-02μF, 2 1/2p, 0-04μF, 0-05μF, 0-068μF, 0-1μF, 3 1/2p.

## CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

## CAPACITOR DEVELOPMENT PACK

Selection of 100 ceramic and polyester capacitors, 100pF to 1-0μF, £2.90.

## ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

(μF/V): 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4, 400/4, 6-4/6-4, 25/6-4, 50/6-4, 100/6-4, 200/6-4, 320/6-4, 4/10, 16/10, 32/10, 64/10, 125/10, 200/10, 2-5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1-6/25, 6-4/25, 12-5/25, 25/25, 50/25, 80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0-64/64, 2-5/64, 5/64, 10/64, 20/64, 32/64.

## ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

## VEROBOARD

	0-1	0-15
2 1/2 x 3 1/2	22p	16p
2 1/2 x 5	24p	24p
3 1/2 x 3 1/2	24p	24p
3 1/2 x 5	27p	27p
17 x 2 1/2	75p	57 1/2p
17 x 3 1/2	100p	78p
17 x 5 (plain)	—	82p
17 x 3 1/2 (plain)	—	60p
17 x 2 1/2 (plain)	—	42p
2 1/2 x 5 (plain)	—	12p
2 1/2 x 3 1/2 (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

## JACK PLUGS AND SOCKETS

Standard screened	18p	2-5mm insulated	8p
Standard insulated	12p	3-5mm insulated	8p
Stereo screened	35p	3-5mm screened	13p
Standard socket	15p	2-5mm socket	8p
Stereo socket	18p	3-5mm socket	8p

## D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin  
Plug 12p. Socket 8p.

## BATTERY ELIMINATOR


Same size as PP9 battery. £1.50

9V mains power supply.



S.D.C. FESTIVE

# BONANZA

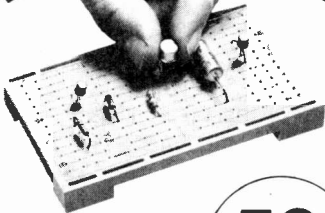

T-DeC  
SPECIAL OFFER

50p  
OFF

(1) YES! The ideal present for any electronics enthusiast, so do not miss this great opportunity.

(2) JUST TAKE THIS COUPON TO YOUR LOCAL STOCKIST WHO WILL SUPPLY ONE T-DeC for only £2.38

(3) OR in case of difficulty send coupon and cash to:—

S.D.C. ELECTRONICS (SALES) LTD., 34 ARKWRIGHT ROAD  
ASTMOOR INDUSTRIAL ESTATE, RUNCORN, CHESHIRE WA7 1NU

Name .....

Address .....


.....

(4) Offer closes January 31, 1972.



## AMAZING MINI-DRILL

FOR PRECISION  
MODEL  
WORK

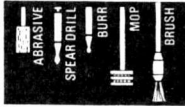

+ 6 TOOLS

Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4 1/2 volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.50 p.p. 13p. De Luxe Professional Kit with 17 tools £7 p.p. 23p. Money Ref. Guarantee.

MERLIN SUPPLY CO.

Dept. PE12D, Nailsea, Bristol BS19 2LP



P.E. SCORPIO  
IGNITION SYSTEM



Complete kit of high quality components — £10.75. p.p. 50p  
All parts available separately send S.A.E. for list

AMC ELECTRONICS LTD.,  
160, DRAKE ST., ROCHDALE, LANCs.

## FIND BURIED TREASURE! TREASURE LOCATOR TRANSISTORISED

NOW IT'S HERE AT LAST, after experimenting for four and a half months with a multitude of different circuits and carrying out actual field tests with prototypes, our design team have come up with this real winner. This fully portable transistorised metal locator detects and tracks down buried metal objects—it signals exact location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, LOST COINS, JEWELLERY, KEYS, WAR SOUVENIRS, ARCHAEOLOGICAL PIECES, METALLIC ORE, NUGGETS, ETC., ETC.** Outdoors or indoors. *Extremely sensitive, will signal presence of certain objects buried several feet below ground!* No knowledge of radio or electronics required. Can be built with ease in one short evening by anybody from nine years of age upwards, with the wonderfully clear, easy to follow, step-by-step, fully illustrated instructions—it really is easy as ABC. Transistorised—no valves. Uses standard PP3 battery. No soldering necessary. Size of detector head: 13 1/2" x 10" x 2 1/2". Great demand expected at this remarkably low price—ORDER WHILE PRESENT STOCKS LAST.



Makes fantastic Christmas Gift

ONLY £2-37 (47/6)

Includes detector head case, nuts, screws, wire, simple instructions, etc., etc. ONLY £2-37 (47/6) + 27p (5/6) p. & p. (Sectional handle as illustrated 75p (15/-) extra). Parts available separately. Made up looks worth £15!

## BUILD 5 RADIO AND ELECTRONIC PROJECTS




Will make an exciting Christmas present

TOTAL BUILDING PRICE £1-97 (39/6)

Amazing Radio Construction set! Become a radio expert for £1-97 (39/6). A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step loudspeaker, personal plans, all transistors, etc. Presentation Box 37p (7/6) extra as illus. (if required) (extra parts available separately) no soldering necessary. Send only £1-97 (39/6) + 23p (47/6) p. & p.

## EAVESDROP ON THE EXCITING WORLD OF AIRCRAFT COMMUNICATIONS—JUST OUT

### V.H.F. AIRCRAFT BAND CONVERTER

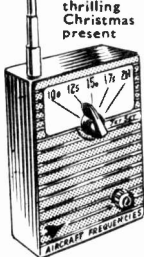


Makes a thrilling Christmas present

ONLY £2-37 (47/6)

Plus P. & P. 23p

Many thousands of v.h.f. Aircraft Band Converters now selling in U.S.A. Listen in to AIRLINES, PRIVATE PLANES, JETPLANES. Eavesdrop on exciting crosstalk between pilots, ground approach control, airport tower. Hear for yourself the disciplined voices hiding tenseness on talk downs. Be with them when they have to take nerve ripling decisions in emergencies—Tune into the international distress frequency. Covers the aerial frequency band including HEATHROW, GATWICK, LUTON, RINGWAY, PRESTWICK ETC., ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone nine to ninety in under two hours. (Our design team built four—everyone worked first time.) No knowledge of radio or electronics required. No soldering necessary. Fully illustrated simply worded instructions take you step-by-step. Uses standard PP3 battery. Size only 4 1/2" x 3" x 1 1/2". All you do is extend rod aerial, place close to any ordinary medium-wave radio (even tiny portables) NO CONNECTIONS WHATSOEVER NEEDED. Use indoors or outdoors. THERE WILL BE ENORMOUS DEMAND FOR THIS NEW DESIGN. SEND NOW. ONLY £2-37 (47/6) + 23p (4/6) p. & p. for all parts, including case, nuts, screws, wire, etc., etc. (parts available separately).

## REAL WORKING ELECTRONIC ORGAN

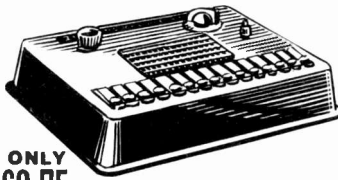

ONLY £2-75 (55/-)

ANYONE FROM NINE YEARS UPWARDS can build it easily in one short evening following the fully illustrated, step-by-step, simply worded instructions. BIG DEMAND ANTICIPATED FOR THIS UNIQUE INSTRUMENT at our low, low building price. ONLY £2-75 (55/-) + 23p (4/6) p. & p. for all parts, including case, loudspeaker, transistors, condensers, resistors, knobs, transformer, volume control, wire, nuts, screws, simple (but full) instructions, etc., etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting Christmas gift for someone.

Don't confuse with ordinary electric organs that simply blow air over mouth-organ type reeds, etc. Eight months were spent in creating and testing this superb, revolutionary electronic organ. Fully transistorised—no valves. Proper self-contained loudspeaker. *Pipes separate keys upon two full octaves—play the "Yellow Rose of Texas" and play "Silent Night" play "Auld Lang Syne", play lots and lots of similar tunes on this real working electronic organ. Although it's no theatre organ it's certainly no tiny thing, it measures 13 1/2" x 10" x 2 1/2". You have the thrill and excitement of building it together with the pleasure of playing a real, live, throbbing electronic organ. *Make it anywhere—play it anywhere. NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED—NONE WHATSOEVER.* No soldering necessary, it really is as simple as ABC to make.*

## GET A GOOD NIGHT'S SLEEP—EVERY NIGHT! INGENIOUS ELECTRONIC SLEEP INDUCER

Ideal Xmas Gift

only £2-75 (55/-)



CAN'T SLEEP AT NIGHTS? DO YOU WAKE UP IN THE NIGHT AND CAN'T GET OFF TO SLEEP AGAIN? WOULD YOU LIKE TO BE GENTLY SOOTHED OFF TO SATISFYING SLEEP EVERY NIGHT? Then build this ingenious electronic sleep inducer. *It even stops by itself so you don't have to worry about it being on all night!* The loudspeaker produces soothing audio-frequency sounds, continuously repeated—but as time goes on the sounds gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about two hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries—extremely economical. Size only 3" x 4 1/2" x 1 1/2"—fits in anywhere. All parts including case, loudspeaker, condenser, nuts, wire, screws, etc., etc. THERE WILL BE A GREAT DEMAND FOR THIS UNIQUE NEW DESIGN—SEND NOW £2-75 + 25p (5/- + 5/-) p. & p. (parts available separately).



Ideal Xmas Gift

ONLY £2-25 (43/-)


## SHORTWAVE TRANSISTOR RADIO Can be built in one evening

At last! After trying countless circuits searching for easy build, work first-time short waver. Giving advanced world-wide performance, we chose this "Sky Roma". Anyone from 9 years up can follow the step-by-step, easy-as-ABC, fully illustrated instructions. (We built ten prototypes and every one worked first time), no soldering necessary. 75 stations logged on rod aerial in 30 mins.—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Transistorised (no valves). Size only 3" x 4 1/2" x 1 1/2". As tremendous demand anticipated price held to only £2-25 (43/-) + 17p (3/6) p. & p. for all parts incl. cabinet, screws, instructions, etc. (Parts available separately).

## SOOTHE YOUR NERVES, RELAX WITH THIS AMAZING RELAXATRON

Ideal Xmas Gift

only £2-25 (45/-)

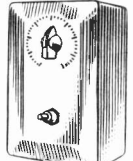


CUTS OUT NOISE POLLUTION—SOOTHS YOUR NERVES! Don't underestimate the uses of this fantastic new design—the RELAXATRON is basically a pink noise generator based on avalanche operated transistors. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well-known type of pink noise. A group of Dentists have experimented on patients with this pink noise—NO ANAESTHETICS WERE USED! The noise ostensibly created a most definite reaction in these patients' nervous systems with the results that their pain systems were blocked. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then Relaxatron. Once used you will never want to be without it—use the amazing pink noise generator whenever you feel uneasy, can't relax or wish to concentrate. TAKE IT ANYWHERE, pocket sized. Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, Nuts, Screws, Wire, etc., etc. no soldering. Send only £2-25 + 25p (48/- + 5/-) p. & p. (Parts available separately.)

## FIND BURIED TREASURE WITH THIS READY BUILT & TESTED

### Treasure Locator Module

Only £4-95 (99/-)

Makes an exceptional Christmas present

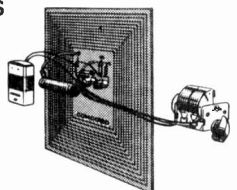

BRAND NEW FULLY TRANSISTORISED PRINTED CIRCUIT METAL DETECTOR MODULE. Ready built and tested—just plug in a PP3 battery and it's working. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £50! Extremely sensitive—penetrates through earth, sand, rock, wood, dirt, water, etc.—EASILY LOCATE COINS, GOLD, SILVER, WATCHES, JEWELLERY, NUGGETS, METALLIC ORE, HISTORICAL RELICS, BURIED PIPES, KEYS, NAIL-IN-TREES, ETC., ETC. Signals exact location by "beep" pitch increasing as you near buried metallic objects. PRINTED CIRCUIT SEARCH COIL so stable and sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ONE COIN! You could even pay for your holidays with two or three days electronic beachcombing—it's almost like having a licence to print money! Unclaimed treasure now exceeds the combined wealth of all nations. ORDER NOW WHILE PRESENT STOCKS LAST. THERE WILL BE ENORMOUS DEMAND EXPECTED AT THIS REMARKABLY LOW PRICE. DEMONSTRATIONS DAILY. ORDERS DESPATCHED IN STRICT ROTATION. SEND NOW £4-95 + 30p carr. (99/- + 6/-), etc. (High quality Danish Stethoscope headphones £2-75 (55/-) extra if required.)

EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

**CONCORD ELECTRONICS LTD (Dept. PE25)**  
(STAFF WANTED FOR ALL DEPARTMENTS)

**8 Westbourne Grove, London W.2.**  
(Nr. Bayswater & Queensway Tubes. 1 minute ABC Cinema)  
Callers Welcome 9 a.m.-6 p.m. inc. Saturday

# 28watts, r.m.s. 40Hz to 40kHz $\pm$ 3dB



## Viscount III Audio Suite complete £49

There are two stereo amplifiers—the R100 for ceramic cartridges, the R101 for magnetic and ceramic. Both incorporate FETs (FIELD EFFECT TRANSISTORS), just like top-priced units. FETs give you more of the signal you want, and almost none of the background hiss you don't. Both units have a jack socket to plug in headphones and there's a separate output for tape recorder. Filters (an unusual feature in this price range) and tone controls give a wide range of bass and treble adjustment which compensate for input deficiencies and domestic acoustic conditions.



### PRICES SYSTEM 1

Viscount III R101 amplifier	£22+90p	P.&P.
2 x Duo Type II speakers	£14+£2	P.&P.
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23+£1.50	P.&P.
<b>Total</b>	<b>£59</b>	

**Available complete for only £52+£3.50 P.&P.**

### SYSTEM 2

Viscount III R101 amplifier	£22+90p	P.&P.
2 x Duo Type III speakers	£32+£3	P.&P.
Garrard SP25 Mk. III with MAG. cartridge, plinth and cover	£23+£1.50	P.&P.
<b>Total</b>	<b>£77</b>	

**Available complete for £69+£4 P.&P.**

### SYSTEM 3

Viscount III R100 Amplifier	£17+90p	P.&P.
2 x Duo Type II speakers	£14+£2	P.&P.
Garrard SP25 Mk. III with CER. diamond cartridge, plinth and cover	£21+£1.50	P.&P.
<b>Total</b>	<b>£52</b>	

**Available complete for only £49+£3.50 P.&P.**

### SPEAKERS Duo Type II

Size approx. 17in x 10½in x 6½in. Drive unit 13in x 8in with parasitic tweeter. Max. power 10W, 3 ohms. Simulated Teak cabinet. **£14 pair + £2 P. & P.**  
 Duo Type III Size approx. 23½in x 11½in x 9½in. Drive unit 13½in x 8½in with H.F. speaker. Max. power 20W at 3 ohms. Frequency range 20Hz to 20kHz. Teak veneer cabinet. **£32 pair + £3 P. & P.**

### SPECIFICATION R100/101

14 watts per channel into 3 to 4 ohms. Total distortion @ 10W @ 1kHz 0.1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within  $\pm$ 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities; headphone socket, power out 250mW per channel. *Tone controls and filter characteristics.* Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. *Signal to noise ratio:* (all controls at max.) R101—P.U.1. and radio—65dB. P.U.2—58dB. R100 same as R101 but P.U.2 (for crystal cartridges) 450mV into 3 Meg. *Cross talk* better than -35dB on all inputs. *Overload characteristics* better than 26dB on all inputs. Size approx. 13½ x 9in x 3½in.

# R+TV

Radio and TV Components (Acton) Ltd, 21d High Street, Acton, London, W3 6NG  
 323 Edgware Road, London, W.2. Mail orders to Acton. Terms C.W.O. All enquiries S.A.E.

Goods not dispatched outside U.K.



Selecting new equipment.  
Finding out who makes it.  
Getting value for money.  
Picking up information on the audio scene.

## Sometimes every hi-fi enthusiast could do with a bit of help.



What you need is the Hi-Fi Year Book, 1972. 22 sections; specifications and prices of over 2200 products; directories of retailers, distributors and manufacturers; a guide to brand names; articles on a comprehensive range of important audio topics.

Isn't that the kind of help you'd really like? Fill in the coupon and get your copy of the Hi-Fi Year Book, 1972.

# Coupon

To: Cashiers, IPC Business Press (S&D) Ltd., P.O. Box 147,  
40 Bowling Green Lane, London EC1P 1DB

Please send me  a copy(ies) of Hi-Fi Year Book 1972  
at £1.25 per copy plus 20p postage.

I enclose remittance value

Name

Address

Signature

Date

## TOURIST

### MARK 3 CAR RADIO

#### ALL TRANSISTOR

Beautifully designed to blend with the interiors of all cars. Permeability tuning and long wave loading coils ensure excellent tracking, sensitivity and selectivity on both wave bands. R.F. sensitivity at 1MHz is better than 8 micro volts. Power output into 3 ohm speaker is 3 watts. Pre-aligned I.F. module and tuner together with comprehensive instructions guarantees success first time. 12 volts negative or positive earth. Size 7in x 2in x 4in deep.



#### SET OF PARTS


£6.30 Plus P. & P. 50p

Speaker postage free when ordered with parts

Circuit diagram 13p, free with parts Speaker, baffle and fixing kit  
£1.25 extra plus P. & P. 25p

## SOUND 50

### 50 WATT AMPLIFIER & SPEAKER SYSTEM

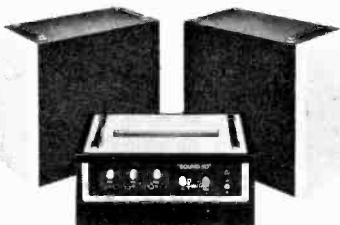

Output Power: 45 watts R.M.S. (5ine wave drive). Frequency response:  $\pm 3$ dB points 30Hz at 18KHz. Total distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Speaker Impedance: 3, 8 or 15 ohms. Bass Control Range:  $\pm 13$ dB at 60Hz. Treble Control Range:  $\pm 12$ dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470K.

To protect the output valves, the incorporated fail safe circuit will enable the amplifier to be used at half power.  
**SPEAKERS!** Size 20in x 20in x 10in incorporating 12in heavy duty 25 watt high flux, quality loudspeaker with cast frame. Cabinets attractively finished in two tone colour scheme—Black and grey.

**COMPLETE SYSTEM** £50 Plus £6 P. & P. or available separately  
Amplifier: £28.50 plus £1.50 P. & P.  
Speaker: £12.50 each plus £2.25 P. & P.



## RELIANT MK. IV

The Reliant Mk.IV provides a high standard of sound reproduction, with full mixing facilities. Its versatility makes it suitable for: Discotheque, P.A., Home Entertainment Applications, etc.

- ★ Five Electronically Mixed Inputs
- ★ Three Individual Mixing Controls
- ★ Separate bass and treble controls common to all five inputs
- ★ Mixer employing F.E.T. (Field Effect Transistor)
- ★ Solid State Circuitry
- ★ Attractive Styling

1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 and 5 are suitable for a wide range of medium output equipment (Gram, Tuner, Monitor, Organ, etc.). All 250mV sensitivity.


**CONTROLS:** 3 Volume controls. Bass control range  $\pm 13$ dB @ 60 Hz. Treble control range  $\pm 12$ dB @ 15KHz. Separate ON/OFF Switch. Neon Indicator.

**POWER OUTPUT:** 12 Watts R.M.S. into 3 to 4 ohms speaker.  
**SIGNAL/NOISE:** Better than  $-60$ dB on inputs 3, 4 and 5 and  $-50$ dB on 1 and 2.  
**SUPPLY:** 220 to 250V A.C. Mains.  
**SIZE:** 12in x 6in x 3in.

**PRICE**  
**£9.50**

Plus P. & P. 60p
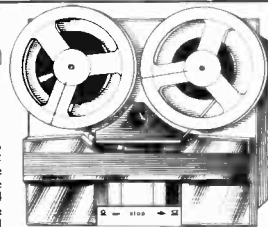
## CONTINENTAL 4-TRACK, 3-SPEED TAPE DECK



with high impedance heads  
R.C. 74 tape deck. Three speeds—7 $\frac{1}{2}$ , 3 $\frac{1}{2}$  and 1 $\frac{1}{2}$  i.p.s. 4-track record/playback head. Plus 4-track erase head. Positive pressure pad system. Takes any tape spool up to and including 7in. The R.C. 74 is driven by a powerful 200/250V 50-cycle a.c. motor. A heavy, accurately balanced flywheel brings wow and flutter levels down to approx. 0.3% total at 3 $\frac{1}{2}$  and 7 $\frac{1}{2}$  i.p.s. Fast rewind in both directions. Controls couldn't be simpler! Just five push buttons that interlock to cut out accidental tape damage. Efficient servo-action type braking. Easy drop-in tape loading.

The R.C. 74 comes with an attractive moulded deck cover, which has positions for tone and volume controls. The unit is built into a rigid die-cast frame, and overall size of the whole unit is 12 $\frac{1}{2}$  x 11 $\frac{1}{2}$  x 6in. Every single deck fully tested before dispatch. Spools not supplied. Price complete £15. Plus 75p P. & P.

**R TV** RADIO & TV COMPONENTS  
(ACTON) LIMITED

See opposite page for addresses

# Music at midnight

Midnight is a time for listening. Let the music be as late and as loud as you like; with headphones, it disturbs no one. Let the headphones be A.K.G. and you will find the quality staggeringly good. Made by a company whose professional microphones are known throughout the world and much used in this country, A.K.G. stereo headphones reflect the same fine quality of design and meticulous manufacture. They are just about as good as anything you can buy at any price. Go to the dealer displaying the A.K.G. Superhead and hear for yourself, without obligation. Shown here, Model K.60 R.R.P. £15.00.

# A K G

A.K.G. Equipment Ltd.

Eandley House

182-184 Campden Hill Rd. W8 7AS



Brought to you for your listening enjoyment from the


# Connoisseur

PRECISION IN SOUND

## COLLECTION
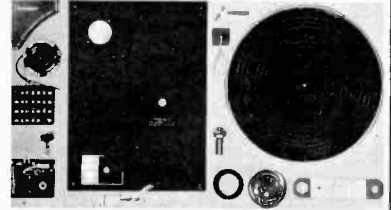
### B.D.1. TURNTABLE KIT

The famous B.D.1. turntable which operates at 33 $\frac{1}{3}$  or 45 r.p.m. incorporates a flexible belt drive system, virtually eliminating vibration and transmission noise — AND IS NOW AVAILABLE IN KIT FORM! So simple to construct — such a beautiful performance, and now it's so easy to own the best!




Rec. Retail Price **£12.82**

Price list and illustrated literature on request to

**A. R. SUGDEN & CO. (Engineers) LTD.**  
Market Street, Brighouse HD6 1DX, Yorkshire. Tel. 2142
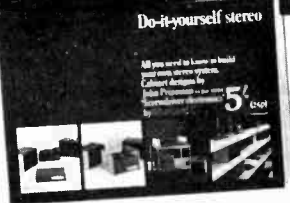
# STEREO - NOW YOU CAN BUILD YOUR OWN

Mullard Unilex modules need no soldering, no knowledge of electronics. They make the stereo amplifier so simple that anyone can build it in an hour, for around £16. Connect the record deck and speakers and you've built your stereo system. For the comprehensive instruction book 'Do-it-yourself Stereo' and stockist list post this coupon today with a 25p P.O.



## Mullard UNILEX

Room 512,  
Mullard House,  
Torrington Place,  
London WC1E 7HD.

Name \_\_\_\_\_

Address \_\_\_\_\_

PE 12.71



**CN.240/2** Miniature soldering iron 15 watt 240 volts, fitted with nickel plated 3/32" bit and packed in transparent display box. Also available for 220 volts. Price **£1.70**

**CN.240** Miniature soldering iron 15 watt 240 volts, fitted with iron coated 3/32" bit. Up to 18 interchangeable spare bits obtainable. This iron can also be supplied for 220, 110, 50 or 24 volts. Price **£1.70**

**G.240** Miniature soldering iron 18 watt 240 volts extensively used by H.M. Forces. Suitable for high speed soldering and fitted with iron coated 3/32" bit. Also available for 220 volts. Spare bits 1/8", 3/16" and 1/4" are obtainable. Price **£1.83**.




**CCN.240** New model 15 watt 240 volts miniature soldering iron with ceramic shaft to ensure perfect insulation (4,000 v A.C.). Will solder live transistors in perfect safety: fitted with 3/32" iron coated bit. Spare bits 1/8" 3/16" and 1/4" available. Can also be supplied for 220 volts. Price **£1.80**

**CCN.240/7** The same soldering iron fitted with our new 7-star high efficiency bit for very high speed soldering. The triple-coated bits are iron, nickel and chromium plated. Price **£1.95**



**E.240** 20 watt 240 volts soldering iron fitted with 1/4" iron coated bit. Spare bits 3/32", 1/8" and 3/16" available. Can also be supplied for 220 and 110 volts. Price **£1.80**.

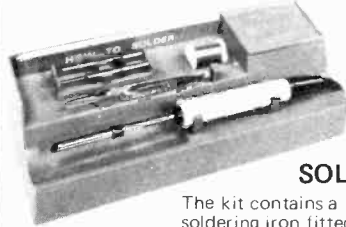**ES.240** 25 watt 240 volts soldering iron fitted with 1/8" iron coated bit and packed in a transparent display box. Spare bits 3/32", 3/16" and 1/4" available. Can also be supplied for 220 and 110 volts. Price **£1.83**



### SK.1 SOLDERING KIT

The kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, heat sink, cleaning pad, stand and booklet "How to Solder". Also available for 220 volts.


Price **£2.75**



### SK.2 SOLDERING KIT

This kit contains a 15 watt 240 volts soldering iron fitted with a 3/16" bit, nickel plated spare bits of 5/32" and 3/32", a reel of solder, Heat Sink, 1 amp fuse and booklet "How to Solder"

Price **£2.40**

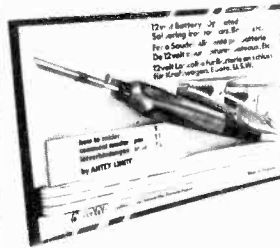

### MES. 12

A battery operated 12 volts 25 watt soldering iron complete with 15' lead, two crocodile clips for connection to car battery and a booklet "How to Solder" packed in a strong plastic wallet. Price **£1.95**.

# cut out this coupon and answer your soldering problems



from electrical, radio or car accessory shops or from **Antex Ltd., Freepost** (no stamp required) **Plymouth**  
**PL1 1BR** Telephone 0752 67377/8

Please send the Antex colour catalogue.

Please send the following:

\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_

I enclose cheque/P.O./Cash (Giro No. 2581000)

Name \_\_\_\_\_  
Address \_\_\_\_\_

PE 12

# The largest selection

**NEW LOW PRICE TESTED S.C.R.'s**

PIV	1A	3A	7A	10A	16A	30A
	TO-5	TO-66	TO-66	TO-48	TO-48	TO-48
50	0-23	0-25	0-47	0-50	0-53	1-15
100	0-25	0-33	0-53	0-58	0-63	1-40
200	0-35	0-37	0-57	0-61	0-75	1-80
400	0-43	0-47	0-57	0-75	0-83	1-75
600	0-53	0-57	0-77	0-97	1-25	
800	0-63	0-70	0-90	1-20	1-50	4-00

**SIL. RECTS. TESTED**

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
50	0-04	0-05	0-05	0-07	0-14	0-21	0-47
100	0-04	0-05	0-05	0-13	0-16	0-23	0-75
200	0-05	0-06	0-06	0-14	0-20	0-24	1-00
400	0-06	0-13	0-07	0-20	0-27	0-37	1-25
600	0-07	0-16	0-10	0-23	0-34	0-45	1-85
800	0-10	0-17	0-13	0-25	0-37	0-55	2-00
1000	0-11	0-25	0-15	0-30	0-46	0-63	2-50
1200		0-33		0-33	0-57	0-75	

**TRIACS**

VBO	2A	6A	10A
	TO-1	TO-66	TO-88
100	0-50	0-63	1-00
200	0-70	0-90	1-25
400	0-90	1-00	1-60

**LUCAS SILICON RECTIFIERS**  
35 amp, 400 P.I.V. Stud type. £1-10 each.

**DIACS**  
FOR USE WITH TRIACS  
BR100 . . . . . 37p each

**2A POTTED BRIDGE RECTIFIERS 200V 50p**

**UNIUNION**  
UT46. Evt. 2N2046, Evt. T1843, BEN3000 27p each, 25-99 25p 100 UP 20p.

**NPN SILICON PLANAR**  
BC107/8/9, 10p each; 50-99, 8p; 100 up, 8p each; 1,000 up, 7p each. Fully tested and coded TO-18 case.

**FREE**  
One 50p Pak of your own choice free with orders valued £4 or over.

AF239 PNP GERM. SIEMENS VHF TRANSISTORS. RF MIXER & OSC. UP TO 900 MHZ. USE AS REPLACEMENT FOR AF139-AF186 & 100's OF OTHER USES IN VHF. OUR SPECIAL LOW PRICE—1-24 37p each, 25-99 34p each 100 + 30p each.

**FET'S**

2N 3819 . . . . . 35p  
2N 3820 . . . . . 83p  
MPF105 . . . . . 40p

**CADMIUM CELLS**  
ORP12 43p  
ORP60, ORP61 40p each

**PHOTO TRANS.**  
OCP71 Type, 43p

**SIL. G.P. DIODES** £p  
300mV 30 . . . . . 0-20  
40PIV (Min.) 100 . . . . . 1-50  
Sub-Min. 500 . . . . . 5-00  
Full Tested 1,000 . . . . . 9-00  
Ideal for Organ Builders.

**D13D1 Silicon Unilateral switch 50p each.**  
A Silicon Planar, monolithic integrated circuit having thyristor electrical characteristics, but with an anode gate and a built-in "Zener" diode between gate and cathode. Full data and application circuits available on request.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed  
Pak No. . . . . QVVT  
T1 8 2G371A OC71  
T2 8 2G374 OC75  
T3 8 2G374A OC81D  
T4 8 2G381A OC81  
T5 8 2G382T OC82  
T6 8 2G344A OC44  
T7 8 2G345A OC45  
T8 8 2G378 OC78  
T9 8 2G399A 2N1302  
T10 8 2G417 AF117  
All 50p each pak

**2N2060 NPN SIL. DUAL TRANS. CODE D1899 TEXAS.** Our price 25p each.

**120 VOB NIXIE DRIVER TRANSISTOR.** Sim. BEN1 & C407, 2N1669 FULLY TESTED AND CODED ND120. 1-24 17p each. TO-5 N.P.N. 25 up 15p each.

Sil. trans. suitable for P.E. Organ. Metal TO-18 Evt. ZEN300 5p each. Any Qty.

**EX-EQUIPMENT MULLARD**  
AF117 transistors. Large can 4 leads type. Leads cut short but still usable, real value at 15 for 50p.

**KING OF THE PAKS Unequalled Value and Quality**

**SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS**

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0-50
U2	60 Mixed germanium transistors AF/RF	0-60
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0-50
U4	40 Germanium transistors like OC81, AC128	0-50
U5	60 200mA sub-min. Sil. diodes	0-50
U6	30 Silicon planar transistors NPN sim. 8BY95A, 2N706	0-50
U7	16 Sil. rectifiers Top-Hat 750mA up to 1,000V	0-50
U8	50 Sil. planar diodes 250mA, OA/200/202	0-50
U9	20 Mixed volts 1 watt Zener diodes	0-50
U11	30 PNP silicon planar transistors TO-5 sim. 2N1132	0-50
U13	30 PNP-NPN sil. transistors OC200 & 2S104	0-50
U14	150 Mixed silicon and germanium diodes	0-50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0-60
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0-50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0-50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0-50
U19	25 Silicon NPN transistors like BC108	0-50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0-50
U21	30 A.F. germanium alloy transistors 2G300 series & OC71	0-50
U23	30 Madt's like MAT series PNP transistors	0-50
U24	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0-50
U25	25 300Mc/s NPN silicon transistors 2N708, BSY27	0-50
U26	30 Fast switching silicon diodes like IN914 micro-min	0-50
U28	Experimenters' assortment of integrated circuits, untested. Gates, flip-flops, registers, etc., 8 assorted pieces	1-00
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CR81/25-600	1-00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0-50
U32	25 Zener diodes 400mV D07 case mixed volts, 3-18	0-50
U33	15 Plastic case 1 amp silicon rectifiers IN4000 series	0-50
U34	30 Sil. PNP alloy trans. TO-5 BCY26, 2S302/4	0-50
U35	25 Sil. planar trans. PNP TO-18 2N2906	0-60
U36	25 Sil. planar NPN trans. TO-5 BFY50/51/52	0-50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2B322	0-50
U38	20 Fast switching sil. trans. NPN, 400Mc/s 2N3011	0-50
U39	30 RF germ. PNP trans. 2N1303/5 TO-5	0-50
U40	10 Dual trans. 6 lead TO-5 2N2060	0-50
U41	25 RF germ. trans. TO-1 OC45 NKT72	0-50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF117	0-50

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

**NEW QUALITY TESTED PAKS**

Pak Description	Price
Q1 20 Red spot trans. PNP AF	0-80
Q2 16 White spot R.F. trans. PNP	0-50
Q3 4 OC77 type trans.	0-50
Q4 6 Matched trans. OC44/45/81/81D	0-50
Q5 4 OC75 transistors	0-50
Q6 4 OC72 transistors	0-50
Q7 4 AC128 trans. PNP high gain	0-50
Q8 4 AC126 trans. PNP	0-50
Q9 7 OC81 type trans.	0-50
Q10 7 OC71 type trans.	0-50
Q11 2 AC127/128 comp. pairs PNP/NPN	0-50
Q12 4 AF118 type trans.	0-50
Q13 3 AF117 type trans.	0-50
Q14 3 OC171 H.F. type trans.	0-50
Q15 3 2N2925 sil. epoxy trans.	0-50
Q16 2 GE7880 low noise germ. trans.	0-50
Q17 3 NPN 1 ST141 & 2 ST140	0-50
Q18 4 Madt's 2 MAT 100 & 2 MAT 120	0-50
Q19 3 Madt's 2 MAT 101 & 1 MAT 121	0-50
Q20 4 OC44 germ. trans. A.F.	0-50
Q21 3 AC127 NPN germ. trans.	0-50
Q22 20 NKT trans. A.F. R.F. cooled	0-50
Q23 10 OA202 sil. diodes sub-min.	0-50
Q24 8 OA81 diodes	0-50
Q25 8 IN914 sil. diodes 75PIV 75mA	0-50
Q26 8 OA95 germ. diodes sub-min. IN69	0-50
Q27 2 10A 600PIV sil. rect. 1843H	0-50
Q28 2 Sil. power rect. BYZ13	0-50
Q29 4 Sil. trans. 2 x 2N696, 1 x 2N697, 1 x 2N698	0-50
Q30 7 Sil. switch trans. 2N708 NPN	0-50
Q31 6 Sil. switch trans. 2N708 NPN	0-50
Q32 3 PNP sil. trans. 2 x 2N1131, 1 x 2N1132	0-50
Q33 3 Sil. NPN trans. 2N1711	0-50
Q34 7 Sil. NPN trans. 2N3369, 500MHZ.	0-60
Q35 3 Sil. PNP TO-5 2 x 2N2904 & 1 x 2905	0-50
Q36 7 2N3646 TO-18 plastic 300MHZ NPN	0-50
Q37 3 2N3053 NPN sil. trans.	0-50
Q38 7 PNP trans. 4 x 2N3703, 3 x 2N3702	0-50
Q39 7 NPN trans. 4 x 2N3704, 3 x 2N3705	0-50
Q40 7 NPN amp. 4 x 2N3707, 3 x 2N3708	0-50
Q41 3 Plastic NPN TO-18 2N3904	0-50
Q42 6 NPN trans. 2N5172	0-50
Q43 7 BC107 NPN trans.	0-50
Q44 7 NPN trans. 4 x BC108, 3 x BC109	0-50
Q45 3 BC113 NPN TO-18 trans.	0-50
Q46 3 BC113 NPN TO-5 trans.	0-50
Q47 6 NPN high gain 3 x BC107, 3 x BC108	0-50
Q48 4 BCY70 NPN trans. TO-18	0-50
Q49 4 NPN trans. 2 x BFY51, 2 x BFY52	0-50
Q50 7 8BY28 NPN switch TO-18	0-50
Q51 7 8BY95A NPN trans. 300MHZ.	0-50
Q52 8 BY100 type sil. rect.	1-00
Q53 25 Sil. & germ. trans. mixed all marked new	1-50

**PRINTED CIRCUITS—EX-COMPUTER**

Packed with semiconductors and components, 10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P. & P. 100 Boards £3. P. & P. 30p.

**GENERAL PURPOSE GERM. PNP POWER TRANSISTORS**  
Coded GP100. BRAND NEW TO-3 CASE. POSS. REPLACEMENTS FOR: OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-431-452-453. T13027-3028, 2N2504, 2N4564-4574-4584, 2N511 A & B. 2G220-222, FFC.

**SPECIFICATION**  
V<sub>CEO</sub> 80V V<sub>CE0</sub> 50V IC 10A PT. 30 WATTS Hie 30-170.  
Hie 20-100. FTI MHZ

PRICE	1-24	25-99	100 up
	43p each	40p each	36p each

**GENERAL PURPOSE SILICON NPN POWER TRANSISTORS**  
Coded GP300. BRAND NEW TO-3 CASE. POSS. REPLACEMENT FOR:—2N3055, BDY26, B1Y11.

**SPECIFICATION**  
V<sub>CEO</sub> 100V, V<sub>CE0</sub> 60V, IC 15AMP/8, PT. 115 WATTS. Hie 20-100. FTI MHZ

PRICE	1-24	25-99	100 up
	55p each	50p each	47p each

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706/8, BSY27/28/95A.** All usable devices no open or short circuits. ALSO AVAILABLE IN PNP Sim. to 2N2906, BCY70. When ordering please state preference NPN or PNP.

	£p	100	For	1-75	
20	For	0-50		500	
50	For	1-00		1000	
				For	13-00

**JUMBO COMPONENT PAKS**

**MIXED ELECTRONIC COMPONENTS**

Especially good value (no rubbish)

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 310s in weight. Price incl. P. & P

**£1-50 only**

Plus our satisfaction or money back guarantee.

**NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK.** A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each.

**GERM. POWER TRANS.**

Type	Price each	Type	Price each
OC20	50p	OC29	40p
OC22	30p	OC35	33p
OC23	35p	OC36	40p
OC25	25p	AD140	40p
OC26	25p	AD142	40p
OC28	40p	AD149	43p

**OUR STOCKS** of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Block at very competitive prices.

**SILICON PHOTO TRANSISTOR.** TO-18 Lens end. NPN Sim. to BP x 25 and P21. BRAND NEW. Full data available. Fully guaranteed.

Qty.	1-24	25-99	100 up
Price each	45p	40p	35p

**RTL MICROLOGIC CIRCUITS**

	Price each
Epoxy TO-5 case	1-24 25-99 100 up
uL900 Buffer	35p 32p 27p
uL914 Dual 2 1/p gate	35p 33p 27p
uL923 J-K flip-flop	50p 47p 45p

Data and Circuits Booklet for I.C.'s

**Dual-in-Line Low Profile Sockets**  
14 and 16 Lead Sockets for use with Dual-in-Line Integrated Circuits

Order No.	1-24	25-99	100 up
T80 14 pin type	30p	27p	25p
T80 16 pin type	35p	32p	30p

# -the lowest prices!

## 74 series T.T.L. I.C.'s DOWN AGAIN IN PRICE

Check our 74 Series List before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed.

BI-PAK Order No.	Similar Types to:—Description	Price and qty. prices		
		1-24	25-99	100 up
BP00 = 7400	Quad 2-input NAND gate	0-15	0-14	0-12
BP01 = 7401	Quad 2-input pos. NAND gate (with open collector output)	0-15	0-14	0-12
BP02 = 7402	Quad 2-input pos. NOR gates	0-15	0-14	0-12
BP03 = 7403	Quad 2-input pos. NAND gates (with open collector output)	0-15	0-14	0-12
BP04 = 7404	Hex Inverters	0-15	0-14	0-12
BP05 = 7405	Hex Inverter (with open-collector output)	0-15	0-14	0-12
BP10 = 7410	Triple 3-input pos. NAND gates	0-15	0-14	0-12
BP13 = 7413	Dual 4-input Schmitt trigger	0-29	0-28	0-24
BP20 = 7420	Dual 4-input pos. NAND gates	0-15	0-14	0-12
BP30 = 7430	8-input pos. NAND gates	0-15	0-14	0-12
BP40 = 7440	Dual 4-input pos. NAND buffers	0-15	0-14	0-12
BP41 = 7441	BCD to decimal nixie driver	0-67	0-64	0-58
BP42 = 7442	BCD to decimal decoder (4-10 lines, 1 of 10)	0-67	0-64	0-58
BP46 = 7446	BCD-to-seven-segment decoder/driver	2-00	1-75	1-50
BP47 = 7447	BCD-seven-segment decoder/drivers (15V outputs)	0-97	0-94	0-88
BP48 = 7448	BCD-to-seven-segment decoder/driver	0-97	0-94	0-88
BP50 = 7450	Expandable dual 2-input and-or-invert	0-15	0-14	0-12
BP51 = 7451	Dual 2-wide 2-input and-or-invert gates	0-15	0-14	0-12
BP53 = 7453	Quad 2-input expandable and-or-invert	0-15	0-14	0-12
BP64 = 7464	4-wide 2-input and-or-invert gates	0-15	0-14	0-12
BP60 = 7460	Dual 4-input expander	0-15	0-14	0-12
BP70 = 7470	Single-phase J-K flip-flop	0-29	0-28	0-24
BP72 = 7472	Master slave J-K flip-flop	0-29	0-28	0-24
BP73 = 7473	Dual Master slave J-K flip-flop	0-37	0-35	0-32
BP74 = 7474	Dual D type flip-flop	0-37	0-35	0-32
BP75 = 7475	Quad latch	0-47	0-45	0-42
BP76 = 7476	Dual J-K with pre-set and clear	0-43	0-40	0-38
BP80 = 7480	Gated full adders	0-67	0-64	0-58
BP81 = 7481	16-bit read/write memory	0-97	0-94	0-88
BP82 = 7482	2-bit binary full adders	0-97	0-94	0-88
BP83 = 7483	Quad full adder	1-10	1-05	0-85
BP86 = 7486	Quad 2-input exclusive NOR gates	0-32	0-30	0-28
BP90 = 7490	BCD decade counter	0-87	0-84	0-58
BP91 = 7491	8-bit shift registers	0-87	0-84	0-78
BP92 = 7492	Divide-by-twelve counters	0-87	0-84	0-58
BP93 = 7493	4-bit binary counters	0-87	0-84	0-58
BP94 = 7494	Dual entry 4-bit shift register	0-77	0-74	0-68
BP95 = 7495	4-bit up-down shift register	0-77	0-74	0-68
BP96 = 7496	3-bit parallel in parallel out shift register	0-77	0-74	0-68
BP100 = 74100	8-bit bistable latches	1-75	1-65	1-55
BP104 = 74104	Single J-K flip-flop equivalent 9000 series	0-97	9-94	0-88
BP105 = 74105	Single J-K flip flop equivalent 9001 series	0-97	9-94	0-88
BP107 = 74107	Dual Master slave flip-flops	0-40	0-38	0-36
BP110 = 74110	Gates master-slave flip-flops	0-55	0-53	0-50
BP111 = 74111	Dual data lock-out flip-flop	1-25	1-15	1-00
BP118 = 74118	Hex set-reset latches	1-00	0-95	0-90
BP119 = 74119	Hex set-reset latches, 24-pin	1-35	1-25	1-10
BP121 = 74121	Monostable multivibrators	0-67	0-64	0-58
BP141 = 74141	BCD-to-decimal decoder/driver	0-67	0-64	0-58
BP145 = 74145	BCD-to-decimal decoder/driver O/C	1-60	1-40	1-30
BP150 = 74150	16-bit data selector	1-80	1-70	1-60
BP151 = 74151	8-bit data selectors (with strobe)	1-00	0-95	0-90
BP153 = 74153	Dual 4-line-to-1-line data	1-20	1-10	0-95
BP154 = 74154	4-to-16 line decoder	1-60	1-50	1-60
BP155 = 74155	Dual 2- to 4-line decoder	1-40	1-30	1-20
BP156 = 74156	Dual 2- to 4-line decoder O/C	1-40	1-30	1-20
BP160 = 74160	Sync. decade counter	1-80	1-70	1-60
BP161 = 74161	Sync. 4-bit binary counter	1-80	1-70	1-60
BP190 = 74190	Sync. up-down BCD counter	3-50	3-25	3-00
BP191 = 74191	Sync. binary up-down counter (single clock line)	3-50	3-25	3-00
BP192 = 74192	Sync. up-down decade counter	2-10	1-95	1-75
BP193 = 74193	Sync. binary up-down counter (two clock lines)	2-10	1-95	1-75
BP196 = 74196	Pre-settable 50MHz decade counter	1-80	1-70	1-60
BP197 = 74197	Pre-settable 50MHz binary counter	1-80	1-70	1-60
BP198 = 74198	8-bit parallel L-R shift register	5-60	5-00	4-00
BP199 = 74199	8-bit parallel access shift register	5-50	5-00	4-00

Devices may be mixed to qualify for quantity price. Larger quantities—prices on application (TTL 74 Series only). Data is available for the above series of I.C.'s in booklet form. Price 13p.


### TTL INTEGRATED CIRCUITS

Manufacturers' "Fall outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

PAK No.	PAK No.	PAK No.
UIC00 = 12 x 7400N 50p	UIC42 = 5 x 7450N 50p	UIC80 = 5 x 7480N 50p
UIC01 = 12 x 7401N 50p	UIC50 = 12 x 7450N 50p	UIC82 = 5 x 7482N 50p
UIC02 = 12 x 7402N 50p	UIC51 = 12 x 7451N 50p	UIC83 = 5 x 7483N 50p
UIC03 = 12 x 7403N 50p	UIC60 = 12 x 7460N 50p	UIC86 = 5 x 7486N 50p
UIC04 = 12 x 7404N 50p	UIC70 = 8 x 7470N 50p	UIC90 = 5 x 7490N 50p
UIC05 = 12 x 7405N 50p	UIC72 = 8 x 7472N 50p	UIC92 = 5 x 7492N 50p
UIC10 = 12 x 7410N 50p	UIC73 = 8 x 7473N 50p	UIC93 = 5 x 7493N 50p
UIC20 = 12 x 7420N 50p	UIC74 = 8 x 7474N 50p	UIC94 = 5 x 7494N 50p
UIC40 = 12 x 7440N 50p	UIC75 = 8 x 7475N 50p	UIC95 = 5 x 7495N 50p
UIC41 = 5 x 7441AN 50p	UIC76 = 8 x 7476N 50p	UIC96 = 5 x 7496N 50p
	UICX1 = 25 x 74x50	

Paks cannot be split but 20 assorted pieces (our mix) is available as PAK UICX1. Every PAK carries out BI-PAK Satisfaction or money back GUARANTEE.

## ANOTHER BI-PAK FIRST!

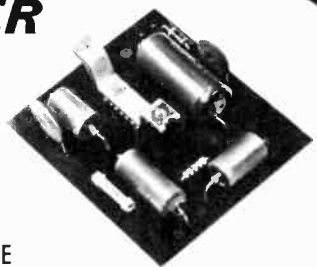

THE NEW S.G.S.  
EA 1000 AUDIO  
AMPLIFIER MODULE

\*GUARANTEED NOT LESS THAN 3 WATTS RMS

Especially designed by S.G.S. incorporating their proven Linear I.C. Audio Amp. TA/621 providing unlimited applications for the enthusiast in the construction of radios, record players, Audio and Stereo units. Also ideal for intercom systems, monitoring applications and phone answering machines. OTHER USES: portable applications where supply rails as low as 9V are of prime importance.

- Sensitivity 40 mV for 1 watt
- VOLTAGE GAIN 40dB but can be varied up to 73dB for some applications.
- Signal to Noise Ratio 86dB.
- Frequency response better than 50 KHz to 25 KHz for -3dB.
- Normal supply Voltage 9-24V.
- Suitable for 8-16 OHM Loads.
- Overall Size 2" x 3" x 1".
- Typical Total Harmonic distortion at 1 watt less than 1%.
- Supply voltage (Vs) = 24V 15ohm load.

Module Tested and Guaranteed

Quantity 1-9 10-25  
Price each £2.63 £2.28

Larger quantities quoted on request

Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.

### ROCK BOTTOM PRICES—CAN'T BE BEATEN!

LOGIC Type No.	DTL 930 SERIES Function	Price 1-24	Price 25-99	Price 100 up
BP930	Expandable dual 4-input NAND	12p	11p	10p
BP932	Expandable dual 4-input NAND buffer	13p	12p	11p
BP933	Dual 4-input expander	13p	12p	11p
BP935	Expandable Hex Inverter	13p	12p	11p
BP936	Hex Inverter	13p	12p	11p
BP944	Dual 4-input NAND expandable buffer without pull-up	13p	12p	11p
BP945	Master-slave JK or RS	25p	24p	22p
BP946	Quad, 2-input NAND	12p	11p	10p
BP948	Master-slave JK or RS	25p	24p	22p
BP951	Monostable	65p	60p	55p
BP962	Triple 3-input NAND	12p	11p	10p
BP983	Dual Master-slave JK with separate clock	40p	38p	35p
BP994	Dual Master-slave JK with separate clock	40p	38p	35p
BP997	Dual Master-slave JK with Common Clock	40p	38p	35p
BP999	Dual Master-slave JK Common Clock	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

### BRAND NEW LINEAR I.C.'s—FULL SPEC.

Type No.	Case	Leads	Description	Price 1-24	Price 25-99	Price 100 up
BF 201C—BL201C	TO-5	8	G.P. Amp	63p	58p	45p
BF 701C—BL701C	TO-5	8	OP Amp	63p	50p	45p
BF 702C—BL702C	TO-5	8	OP Amp Direct OP	63p	50p	45p
BF 702—72702	D.I.L.	14	G.P. OP Amp (Wide Band)	53p	46p	40p
BF 709—72709	D.I.L.	14	High OP Amp	53p	46p	40p
BF 709P—7A709C	TO-5	8	High Gain OP Amp	53p	46p	40p
BF 711—7A711	TO-5	10	Dual comparator	58p	50p	45p
BF 741—72741	D.I.L.	14	High Gain OP Amp (Protectel)	75p	60p	50p
7A 703C—7A703C	TO-5	6	R.F.—L.F. Amp	43p	35p	27p
TAA 263—	TO-72	4	A.F. Amp	70p	60p	55p
TAA 293—	TO-74	10	G.P. Amp	80p	75p	70p

All prices quoted in new pence Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

# BI-PAK

P.O. BOX 6, WARE · HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

**C**  
**H**OME RADIO  
**H**OME RADIO  
**P**  
**H**OME RADIO  
**N**  
**H**OME RADIO  
**E**  
**R**ADIO  
**T**  
**S**

HOME RADIO (Components) Ltd.  
 Dept. PE, 234-240 London Road,  
 Mitcham CR4 3HD. 01-648 8422

**When you think  
 of COMPONENTS  
 think of HOME RADIO**

Some things in life are just about inseparable—eggs and bacon, sausage and mash, Tweedle Dum and Tweedle Dee! Think of one and you think of the other. That's how thousands of radio and electronic enthusiasts think of Components and Home Radio Ltd. When they need the first they automatically contact the second. They simply flip through their Home Radio Catalogue, locate the items they need and telephone or post their order.

If you have not yet experienced the simplicity and satisfaction of linking Components and Home Radio, why not make a start now? First of all you'll need the catalogue . . . in its 315 pages are listed more than 8,000 components, over 1,500 of them illustrated. Every copy contains 10 vouchers, each worth 5p when used as instructed. The catalogue costs 70p including postage and packing. Drop us a line or use the coupon below.

**POST THIS  
 COUPON  
 with your  
 cheque or  
 postal order  
 for 70p**




Please write your Name and Address in block capitals

Name.....

Address.....

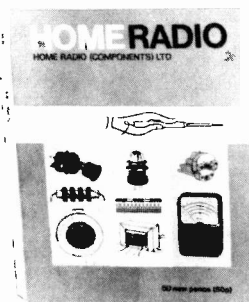**HOME RADIO (Components) LTD.**  
 Dept. PE, 234-240 London Road, Mitcham CR4 3HD



**Phone  
 24-hour  
 Phone  
 Service.  
 Ring  
 01-648 8422**

**Ask for  
 details of  
 our Credit  
 Account  
 Service.**

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial Assistants D. BARRINGTON G. GODBOLD M. KENWARD  
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY P. A. LOATES  
Advertisement Manager D. W. B. TILLEARD

## TODAY'S ICs AND TOMORROW'S

THE profusion of integrated circuit devices on the retail market offers great opportunities for equipment designing and building. Yet the formidable lists of type numbers must be daunting to many a reader as he peruses those advertisements featuring i.c.s. Clearly there is a requirement for a guide that identifies the more common types, indicates function and provides basic application data. This need we have attempted to meet in the Linear and Logic IC Survey which is the subject of this month's special supplement.

It will be appreciated that this Survey is not, and indeed could not be, exhaustive. Only those types of integrated circuit known currently to be available via retailers are included. This in fact makes the Survey all the more valuable, since no reader is likely to be sent on a wild goose chase after some rare device that cannot be obtained, unless one has special connections within the industry.

★ ★ ★

Having (hopefully) clarified the current i.c. situation to some extent and produced two separate lists, one for linear, the other for logic devices, we learn that this orderly and simple segregation into just two clearly defined categories may not always be possible in the years to come. By strange chance, just as our Survey was completed news was released of what is claimed to be a revolutionary development in i.c. design and manufacture by a British firm. The Collector Diffusion Isolation (CDI) method now perfected by Ferranti permits both digital and linear circuits to be formed on the same monolithic chip; it combines the linear high performance and digital high speed capability of the bipolar method with the high circuit density capability offered by the MOS technique.

The developers of CDI have suggested that this new bipolar process will cause a general widening of MSI and LSI applications particularly in areas involving analogue-digital techniques; they have mentioned, specifically, desk calculators, fuel injection systems, washing machine controls, and model control as examples where CDI will have great impact.

It is good to hear of a UK firm making an outstanding contribution to the development of new i.c. techniques. Just how important and significant the CDI method actually is, time will tell. But there are already two American contenders in the field. Both Fairchild and Raytheon have developed their own methods for increasing the component density on a single chip. Are we about to witness another price war? With mammoth production runs, technical considerations tend to play a minor role—the more economical process usually wins the day.

F.E.B.

## THIS MONTH

### CONSTRUCTIONAL PROJECTS

LOGICAL RADIO CONTROL	982
P.E. SCORPIO	998
I.C. DIGITAL DICE	1004
LABPACK POWER SUPPLY	1018

### SPECIAL SERIES

RADIO ASTRONOMY TECHNIQUES — 7	1009
-----------------------------------	------

### GENERAL FEATURES

ELECTROLUMINESCENCE	989
SUBSTITUTES FOR ZENERS	1030

### NEWS AND COMMENT

EDITORIAL	981
PATENTS REVIEW	986
NEWS BRIEFS	1012
INDUSTRY NOTEBOOK	1015
ELECTRONORAMA	1016
SPACEWATCH	1029
MARKET PLACE	1038

### SPECIAL SUPPLEMENT

LINEAR AND LOGIC IC SURVEY

*Our January issue will be published on  
Friday, December 10.*

© IPC Magazines Limited 1971. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Subscription Rates including postage for one year, to any part of the world, £2.65 (£2 13s. 0d).

Practical Electronics, Fleetway House, Farringdon St., London, E.C.4. Phone: Editorial 01-634 4452; Advertisements 01-634 4202



# LOGICAL

By A.J. Dunn

*A proportional control system, using integrated circuits, suitable for use with most types of radio control transmitter or receiver.*

THE vast number of integrated circuits now on the market has lowered the cost to levels whereby they can be used for many applications. Although the circuitry for the system described would be possible with discrete components, the complexity would be such as to deter many from contemplating a sophisticated system, whereas with integrated circuits, the modules are simple and easy to build.

This article deals with the coder and decoder sections only; a block diagram of a typical system is shown in Fig. 1a. These may be built and tested against each other (Fig. 1b) the interface or coupling units being simple stages allowing, for example, a transmitter with a  $-12\text{V}$  supply to be used with the coder which requires  $+5.2$  to  $5.7\text{V}$ .

The system is described for six channels although it can easily be varied for three to nine channels. It is not economic to have less than three channels; for more than nine channels some compromise is necessary with regard to proportionality and the time rate of control.

Printed circuit boards are necessary for this project and care should be taken to make these of a high standard since one interconnection short can cause complete malfunction and may be hard to trace; time taken wiring up is amply repaid.

Alternative forms of coder are described and it is not advisable to attempt construction without considering the corresponding decoder. Positive logic (output high = 1, low = 0) is used throughout.

## PULSE CONTROL TECHNIQUES

The control system involves the production of a train of (positive going) pulses, each pulse corresponding to a channel and being independently and proportionally variable in length from about  $0.5$  to  $4\text{ms}$ .

As shown in Fig. 2a, the pulses occur sequentially but their position relevant to the start of the train is determined by the length of the other pulses and the interval time between pulses  $-\frac{1}{3}\text{ms}$ .

The pulse train is repeated at intervals  $\tau_1$  of 25 to 50ms or 20 to 40 times a second. This is the rate at which the pulse lengths are measured and changes detected. Allowing five measurements (but preferably ten) for the detection of a small change and servo initiation, this gives a system response time of about  $\frac{1}{3}$  to  $\frac{1}{2}$  second.

Due to the inertia of the motor and load, the servo has a response time which must be added to the above; a model aircraft flying at 60 m.p.h. would move 22ft in  $\frac{1}{4}$  second before, say, the rudder servo started operating.

## PULSE LENGTH

The pulse train repetition time  $\tau_1$  for  $n$  channels is made up of  $(n - 1) \times \frac{1}{3}\text{ms}$  intervals,  $n$  pulses of maximum length  $\tau_3\text{ms}$  and a synchronising period  $\tau_2$  used in the decoder to determine the start of the pulse train. This synchronising period  $\tau_2$  must be  $1\frac{1}{2} \times \tau_3$  or preferably  $3 \times \tau_3$ .

A four-channel system with a maximum pulse length ( $\tau_3$ ) of say  $4\text{ms}$  would therefore give as a minimum  $(4 \times 4) + (3 \times \frac{1}{3}) + (1\frac{1}{2} \times 4) = 23$  milliseconds.

The sharp-edged pulses used in the coder and decoder are "softened" to approximately sine wave shape, before actual transmission and reception (as shown in Fig. 3), the pulse interval period being then approximately  $0.5\text{ms}$  wide corresponding to a 2kHz tone. This allows a factor of approximately two for the bandwidth performance of any existing receiver, it being equally convenient to use a tone modulator transmitter or to use the i.c.w. mode and to detect the 27MHz carrier only in the receiver.

The maximum pulse length ( $\tau_3$ ) is determined as a reasonable relationship with regard to the interval time, being restricted to contain  $\tau_1$  to less than 50ms. If a slower system response time can be tolerated, as in the case of a scale model boat, the maximum pulse length could be increased to 10ms or alternatively more channels could be used.





# RADIO CONTROL

Use integrated circuits to simplify control functions

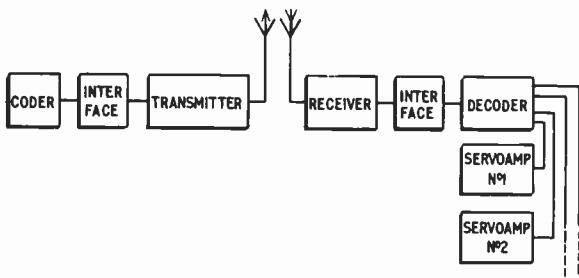


Fig. 1. Block diagram of a typical radio control installation

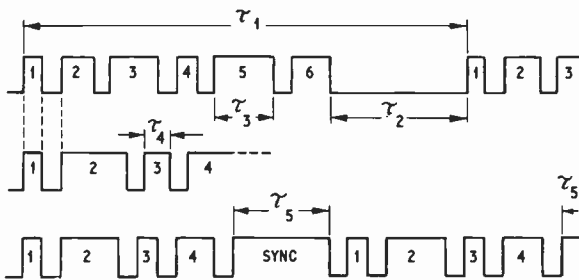


Fig. 2. Variable pulse lengths for proportional control

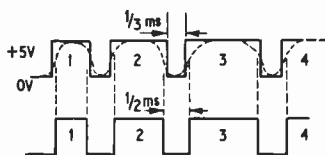


Fig. 3. The coder pulses are "softened" to almost sine wave shape for transmission to avoid troubles with short propagation times of square wave pulses

If only one channel, e.g. rudder, was required for maximum sensitivity, the corresponding maximum pulse length could be increased provided that the other channels in use were restricted operationally to prevent all the pulses being at maximum length, hence encroaching into the sync period  $\tau_5$ .

## CODER VARIANTS

Three variants of coder are described: coders 1 and 2A are similar in form providing alternative construction dependent upon the use of components that may be to hand. The cost of the timing capacitors becomes comparable with that of the "active" components. In these cases, the period  $\tau_1$  is fixed by using a multivibrator.

The coder 2B simply uses a longer positive-going pulse to provide the synchronising period shown as  $\tau_5$  in Fig. 2b; the channels are no longer being completely independent,  $\tau_1$  not being fixed. In this case the end of the synchronising pulse  $\tau_5$  is used to initiate the next pulse train.

The particular advantage is that, with some of the channel controls at minimum, a shorter system response time is possible. The disadvantage is that, operating any control, the corresponding pulse length is changed, in turn changing the total cycle time, and hence changing the measurement rate of the other pulses and their corresponding output.

Considering the case of a six-channel coder with all controls in the mid-position a pulse length of 2ms cycle time =  $(6 \times 2) + (6 \times \frac{1}{4}) + 6$  (synchro pulse) = 20ms. If one control is changed to maximum and its corresponding pulse length to 4ms, then the cycle time becomes 22ms.

The output signal derived from these pulses changes in the ratio  $\frac{2}{20} : \frac{4}{22}$  not 2 : 4 and the other channels outputs change by 20 : 22.

The greater the number of channels used, the less marked the loss of complete channel independence, and the greater the gain with respect to cycle and system response time.

**Table 1: MAKERS LOGIC I.C. TYPE NUMBERS**

Description	Logic type	Ferranti	Motorola	Mullard	SGS	Signetics	S.T.C.-I.T.T.
Quad 2-input NAND gate	TTL	ZN7400E	MC7400P	FJH131	6900259		
8-input NAND gate	DTL	ZN346E	MC846		6994659		MIC9495D
8-input NAND gate	TTL	ZN7430E	MC7430P	FJH101		N7430A	
Dual JK flip-flop	TTL	ZN7473E	MC7473P	FJJ121		N7473A	
Monostable	TTL	ZN7470E		FJJ101		N7470A	
Retriggerable Monostable	TTL				9601		
Monostable	DTL				T118		
Dual 4-input NAND gate with node	DTL	ZN330E	MC830P		6993059		MIC9305D

**DECODER**

The decoder consists of two parts, the sync separator using a retriggerable monostable, and a shift register formed from a chain of JK flip-flops.

The received positive-going pulses repeatedly trigger the special monostable which has a full back-off time of at least  $1\frac{1}{2} \times$  the maximum signal pulse length. It can change state therefore only during the sync period, this change of state being used to produce a special pulse which is applied to all the "clear" inputs of the JK flip-flops.

During the sync period the outputs of the flip-flops are set to "0", awaiting the train of signal pulses which are applied to all the "clock" inputs. One flip-flop is used to store a "1" which is successively moved down the chain (shift register) in steps coincident with the signal pulses.

The final individual output pulses from each flip-flop output is equal to the period of the signal pulse together with the following interval ( $\frac{1}{2}$ ms). Either one more flip-flop than the number of channels is used (to store a "1") or the last output is gated out as shown, the gating being associated with the decoder or one servo unit as desired.

**SUPPLY VOLTAGE**

For reliable operation the supply should be constant and between + 5.2 and + 5.7V. The most convenient way of obtaining this voltage for the coder is by the use of a good 6V battery in series with a 150mA diode. Precaution should be taken to prevent more than 6V being applied even momentarily, a Zener diode being used with the decoder.


**CODER I**

The first coder is for six channels of positive going pulses. Four i.c.s only are used, one being an 8-input NAND gate (SN7430) to collate the outputs derived from an array of NAND gates (Fig. 4).

Pairs of these gates are used with a timing resistor and capacitor to give the signal pulse (for example, input 3 from G5 and G6 to G13) or the interval period ( $\frac{1}{3}$ ms) from G4 and G5.

The quad 2-input gate i.c. (SN7400) is used, therefore, to produce three timing periods and the series can be extended as desired. Eight channels would be a convenient limit unless G13 in IC7 is replaced by two or more gates followed by further grouping.

*continued on page 1003*

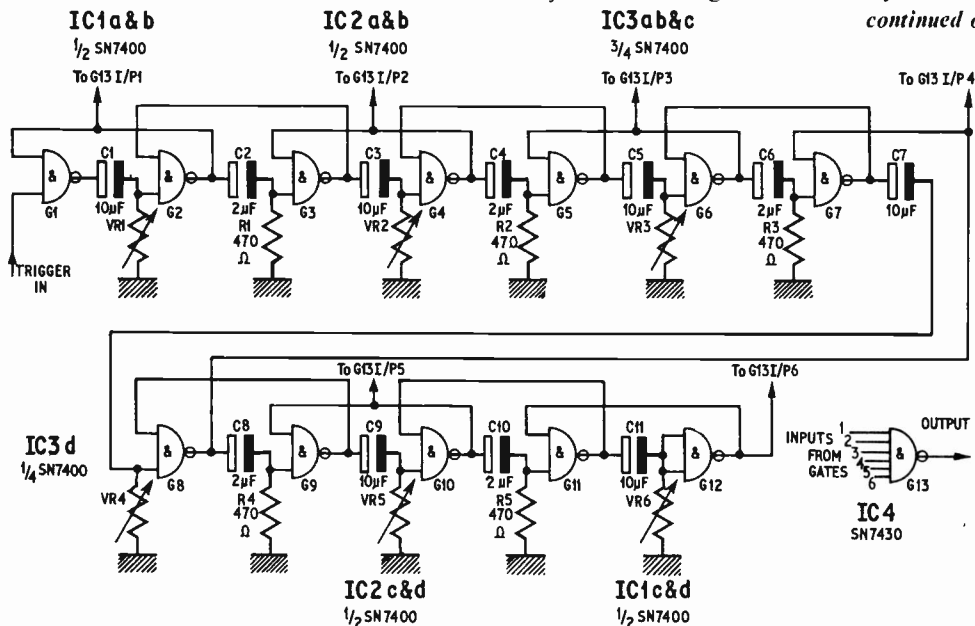

**Fig. 4.** The pulse lengths are determined and set by the potentiometers in the timing circuits. NAND gates are used to determine the timed sequence of pulses being fed to the master control gate G13

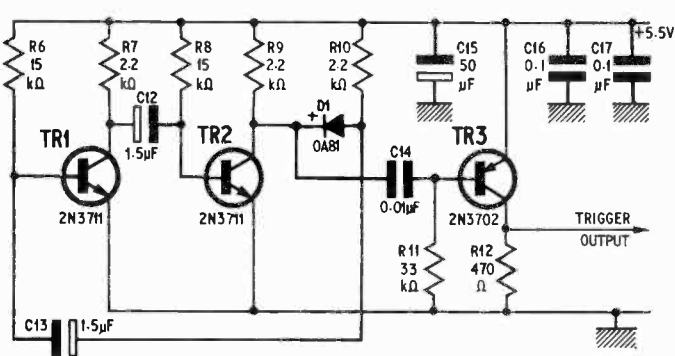


Fig. 5. Triggering is dependent on coincidence of an incoming clock pulse from this multivibrator and trigger circuit

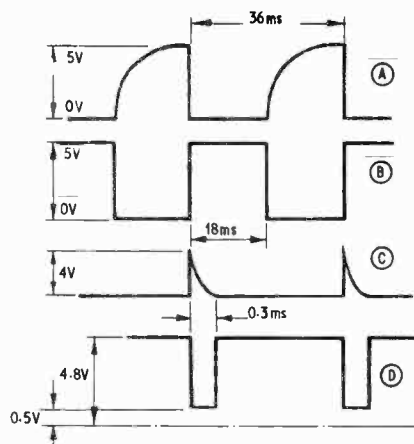


Fig. 6. The waveforms appearing at (a) TR1 collector, (b) TR2 collector, (c) TR3 base, (d) TR3 collector

## COMPONENTS . . .

CODER 1 (Figs. 4, 5, and 8)

### Resistors

- R1 to R5 470Ω (5 off)
- R6 15kΩ
- R7 2.2kΩ
- R8 15kΩ
- R9 2.2kΩ
- R10 2.2kΩ
- R11 33kΩ
- R12 470Ω
- All ±5%, 1/4W carbon

### Potentiometers

- VR1 to VR6 2.5kΩ for pre-selection of values, then replacement by fixed resistors (see text)

### Capacitors

- C1, C3, C5, C7, C9, C11 10μF tantalum or elect. 20V (6 off)
- C2, C4, C6, C8, C10 2μF polarised tantalum or elect. 25V (5 off)
- C12, C13 1.5μF elect.
- C14 0.01μF disc ceramic
- C15 50μF elect. 15V
- C16, C17 0.1μF disc ceramic (2 off)

### Integrated circuits

- IC1, IC2, IC3 SN7400 quad 2-input NAND gate (3 off)
- IC4 SN7430 8-input NAND gate

### Transistors

- TR1, TR2 2N3711 npn silicon
- TR3 2N3702 pnp silicon

### Diode

- D1 OAB1 or any 100mA signal diode

### Miscellaneous

- Fibreglass printed circuit board (see Fig. 7)

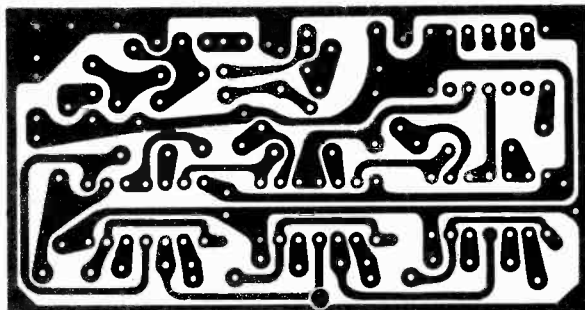


Fig. 7. The whole of "Coder 1" and clock pulse generator is made up on fibreglass printed circuit board; the pattern here is reproduced full size

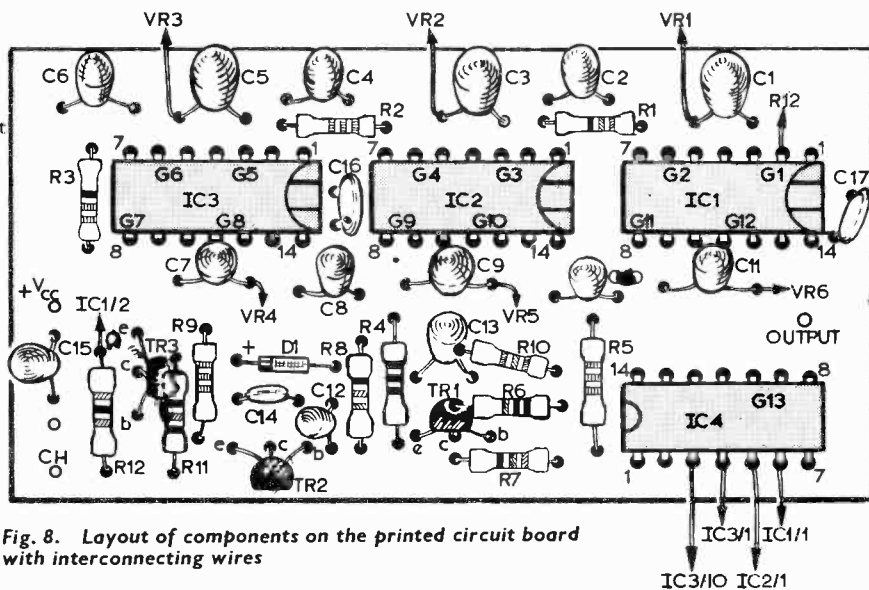


Fig. 8. Layout of components on the printed circuit board with interconnecting wires

# PATENTS REVIEW...

## INFLAMMABLE LIQUID LEVEL MONITOR

**A**n interesting new use of fibre optics occurs in BP 1 223 769 which is in the name of Maria and Giuseppe Panerai. Their Patent Specification is predominantly concerned with gauging the level of liquids in tanks.

Reading between the lines their main interest is in sensing the level of highly inflammable liquids such as petroleum where it is obviously far from ideal to use any electrical system in contact with the liquid. Of course, simple mechanical systems tend to be unreliable, especially if they are gravity dependent.

What these Italian inventors suggest is to arrange a sequence of prisms or equivalents in a vertical line, up from the base of the liquid tank, so that as the tank fills more and more prisms are submerged.

The prisms protrude from a removable pipe, each one backing onto a photosensitive cell. A lamp is fixed to the top of the tank so as to illuminate the interior. It is quite easy to see that, as the liquid level goes down, so more and more prisms will be exposed and illuminated and more and more photocells activated. The cells can be linked to any simple electronic circuitry outside the tank by wires with a consequent minimal risk of sparking and explosion.

But none of this concerns fibre optics so far. It turns up almost as an afterthought in one of the

examples given in the specification where it is suggested that instead of putting the photocells directly behind the prisms, i.e. in the pipe which is submerged in the liquid, the photocells can be arranged elsewhere and the light from the prisms taken to them by light pipes or optic fibres.


## AUTOMATIC FINGERPRINT IDENTITY

**T**HE North American Rockwell Corporation have a new British Patent BP 1 225 083 which applies to the automation of fingerprint


straightforward "off-the-shelf" electronics to provide means for scanning the fingerprint area. The major scan pattern has a minor scan pattern repeatedly superimposed over it.

The major scan pattern is a pre-determined linear pattern, which scans through a succession of relatively small area portions, and the minor pattern scans over each of these portions in a polar mode. This minor scan produces signals indicative of the pattern at that portion and these are stored in a bank of storage elements. The states of selected signals in these

BP 1 225 083

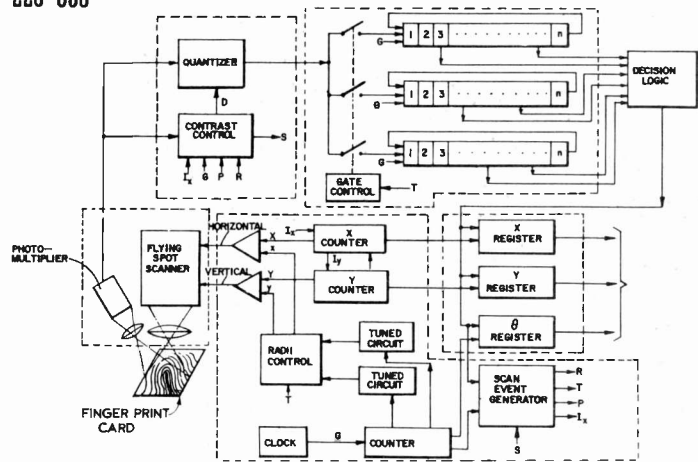

BP 1 223 769

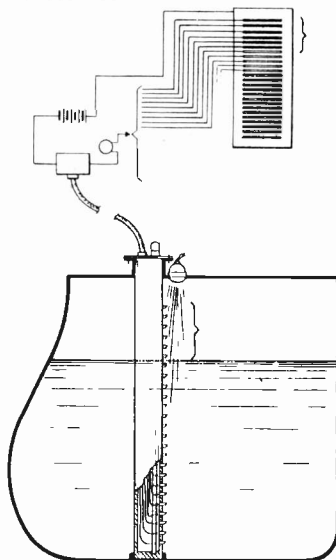

checking. Rockwell start their specification with some sobering facts.

For instance, the FBI in America has a fingerprint file of over 182 million fingerprint cards, each having ten prints on it. So, if checking a suspect's prints against the records is to be finished in his lifetime, sophisticated automation is obviously necessary. What's more, with lost or stolen credit cards being an escalating problem, it may well be necessary one day to identify a legitimate card-holder by his fingerprints at the time of purchase.

Rockwell remind us that recognising the minutiae of a fingerprint is basically a problem in pattern recognition, which is complicated by the obvious fact that the minutiae occur at arbitrary orientations.

Whereas others have tended to concentrate on new techniques such as holography (matching prints with known masks), Rockwell propose a system which uses

storage elements are then sensed.

In more detail, Rockwell suggest the use of a flying spot scanner to derive an electrical analogue signal indicative of the fingerprint pattern at each small portion. This analogue signal is converted into digital form for storage and there is constant circulation of the signal in the memory through each of the storage elements so as to help the recognition of minutiae regardless of angular orientation.

An automatic contrast control circuit adjusts the detection process as a function of the general overall fingerprint image so that characteristics like ridge endings will produce distinctive light and dark areas to be encountered by the flying spot scanner moving in the orbits suggested.

Rockwell give plenty of details on suitable scanning techniques giving a total of 300,000 individual locations scanned on a single print. For present purposes, their block diagram gives the general picture.

# RUSSIAN WORLD BEATER!

**JUST ARRIVED!**

The Fabulous BRAND NEW 1971

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

**VEF 204**  
**8 WAVEBAND**

10 TRANSISTOR PLUS DIODES PORTABLE RADIO


AND NOW WITH SHIP-TO-SHORE MARINE BAND

BATTERY MODEL **£13.97**  
BOX POST ETC. 50p

MAINS/BATTERY ELIMINATOR **£13.30** extra

WE COULDN'T EVEN MAKE THEM FOR OUR FANTASTIC PRICE!

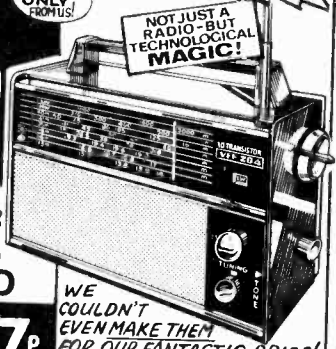\*COMPARE IT'S PERFORMANCE with **£42** RADIOS!



NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

Important! This latest 1971 model incorporates all the latest technological improvements... **DESIGNED FOR WORLD WIDE RECEPTION**—it probably make your present radio seem like a "crystal set"! It even incorporates a special **MARINE WAVEBAND** to receive spoken communications from ship-to-shore! We're almost giving them away at only **£13.97**—a mere fraction of even today's Russian miracle price! Compare performance with £42 radios! \*Refund if not astounded! Purer and sweeter tone than ever! Wider band spread for "pin-point" station selection! The Russians have really surpassed themselves this time proving again their ability in the field of space communications. Yes, 8 separate wavebands, including Standard Long, Medium and Short waves to cover the world, PLUS special "ship-to-shore" **MARINE BAND!** Thousands of different transmissions and stations at your fingertips 24 hours a day, including ships at sea, etc., and messages from all over world—truly nothing is secret! You must hear it to believe it! Separate ON/OFF volume and Treble/Bass tone controls! Push-pull output illumination! Take it anywhere—economically on standard batteries or telescopic aerial. It's also a fabulous **CAR RADIO!** Black and Chrome case with **WRITTEN GUARANTEE**, manual with simple operating instructions, and circuit diagram. **ONLY £13.70** extra. Can also be used through extension amplifier, tape recorder or public address system. Send today or call. (**SORRY**—we cannot change these new radios for any earlier model already purchased.)

**SAVE £20.25 NOW!**

THIS FANTASTIC OFFER ONLY FROM US!

Fabulous BRAND NEW **SOLID STATE**

This equipment's got EVERYTHING!

BATTERY/MAINS AC/DC

Combined V.H.F. AM/FM RADIO and CASSETTE TAPE RECORDER & PLAYER

WITH REMOTE CONTROL MICROPHONE



RECOMMENDED RETAIL PRICE **£44**

OUR PRICE **£23.75** CARR. ETC. 35p

FANTASTIC (even by our standards!) Brand new—the latest sensation in the world of sound! First Recorder and Player combined, but it also runs off standard batteries or mains (simply plug in the built-in 220/240V a.c. line cord). Now you can record and play back anything, and where! You can even tape direct from the radio as you listen! **RECOMMENDED RETAIL PRICE! GENUINELY £44 YET WE OFFER AT ALMOST HALF PRICE!** Just look at the wonderful features:—\*Press-button Keyboard Control panel! \*New "pop-up" Cassette Ejection system! \*"**MAGIC EYE**" Visual Battery check/recording level indicator! \*Separate ON/OFF, volume and HI-LO volume tone controls! Heavy duty built-in speaker! \*Ear-Phone (for personal listening or "monitoring") and extension speaker sockets! \*Remote control microphone! \*Built-in swivel telescopic extension overall approx. 12in. Magnificently made case, size 11in x 9in x 3in 120 minute Philips Cassette Tapes obtainable everywhere. But wait, the amazing and incredible station selection—Unique rotating Station Selector Dial—get all local city and regional stations in every part of the country plus BBC National VHF. Picks up dozens of foreign stations and short mobile transmissions. Also fabulous in your car! You could pay **££££** more for a Car Radio or Car Cassette Player ALONE! OUR FANTASTIC PRICE, **ONLY £23.75** carr. or Car 35p. Complete with simple instructions, personal listening earphone, remote control microphone with on/off switch and microphone stand. **WITH WRITTEN GUARANTEE, BONUS OFFER—Standard Batteries and Cassette Tape 25p extra. Refund guaranteed.**

fabulous 1971 model **SAVE £13.98 NOW!**  
FIRST CLASS MAKER'S **DE LUXE MODEL!**

BRAND NEW **Cassette TAPE RECORDER and PLAYER**



RECOMMENDED LIST PRICE **£26.97**  
OUR PRICE **£12.99**  
POST ETC. 10p

WITH REMOTE CONTROL MICROPHONE

ONLY FROM US! LATEST SHIPMENT JUST ARRIVED!

BRAND NEW 1971 Model

**RUSSIAN WORLD BEATER!**

WE COULDN'T EVEN MAKE THEM FOR THIS PRICE!


**6 WAVEBAND**

10 TRANSISTOR PLUS DIODES PORTABLE RADIO

**WORLD WIDE RECEPTION**  
THOUSANDS OF TRANSMISSIONS AND STATIONS THE WORLD OVER!

**£9.97**

BOX POST ETC. 43p

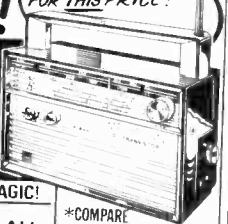

NOT JUST A RADIO—BUT TECHNOLOGICAL MAGIC!

\*COMPARE IT'S PERFORMANCE with **£34** RADIOS!

THE LATEST 1971 MODEL, SUPERSEDING ALL PREVIOUS MODELS—FANTASTIC BRAND NEW RUSSIAN "MERIDIAN" 6-WAVEBAND PORTABLE RADIO, DESIGNED FOR WORLD WIDE RECEPTION. Only put into production after incorporation of every conceivable possible up-to-date technological improvement had been carefully considered and thoroughly examined. So advanced it will probably make your present radio seem like a "crystal set"! It's far better than any 6-wave radio even they have produced! Finest value we've ever offered! We're almost giving them away at **£9.97**—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of **£34** radios! \*Instant refund if you are not astounded! Purer and sweeter tone than ever! Much wider band spread than hitherto for "pin-point" station selection. Includes wider band spread have proved their fantastic ability in electronics—brilliantly reflecting their advanced micro-circuitry techniques in the field of space and satellite communications. YOU GET THIS AMAZING SET FROM US AT A PRICE THAT BEARS NO RELATION TO TRUE VALUE! Yes, 6 separate wavebands, including Standard Long, Medium and Short Waves to cover the world! Unique side control waveband selection unit gives incredible ease of station tuning! Thousands of different transmissions and stations at your fingertips 24 hours a day, even ships at sea and messages from all over world—nothing is secret! The radio enthusiast has the world in his hand! Separate ON/OFF volume and Treble/Bass tone controls! Push-pull output! Runs economically on standard batteries. Internal ferrite rod aerial plus built-in telescopic aerial extending to full 33in length. It's also a fabulous **CAR RADIO**—any speed, requires no additional aerial. **UNIQUE!** Elegant Black, magnificently designed, made to give years of perfect service. With **WRITTEN GUARANTEE**, manual with simple operating instructions and circuit diagram. **ONLY £9.97**, POST ETC. 43p. Standard batteries 25p extra. Can also be used through extension amplifier, tape recorder or public address.

## SHOPERTUNITIES LTD. SL

Dept. PE/11, 164 UXBRIDGE RD. (facing Shepherd's Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thursday 7 p.m.). BOTH STORES OPEN MONDAY-SATURDAY FROM 9 a.m.-6 p.m.

A VISIT TO SHOPERTUNITIES COULD SAVE YOU £££'s!

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the practical way.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

**You LEARN—but it's as fascinating as a hobby.**

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course—but it teaches the real thing. The easy to understand, practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

**New Specialist Booklet**

If you wish to make a career in Electronics, send for your **FREE** copy of “**OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO**”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.

## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF



### POST THIS COUPON FOR FREE BOOK

To B.I.E.T. Dept. B12, Aldermaston Court, Reading RG7 4PF  
Please send books and full information — free and without obligation.



NAME \_\_\_\_\_ AGE \_\_\_\_\_  
BLOCK CAPITALS PLEASE

ADDRESS \_\_\_\_\_

OCCUPATION \_\_\_\_\_

**BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY**  
Accredited by the Council for the Accreditation of Correspondence Colleges.

# TRANSFORMERS

**MAINS ISOLATING SERIES**  
PRIMARY 200/250V, SEC. 240V, C.T. 120V, & EARTH SHIELDED

ALSO AVAILABLE WITH 115/120V, SEC. WINDINGS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P
61	100	5 12	10.2 x 8.9 x 8.3	£ 2.28 Np 52
62	250	12 4	9.3 x 12.7 x 11.4	5.05 67
63	500	27 0	17.1 x 11.4 x 15.9	9.74 *
92	1000	40 0	17.8 x 17.1 x 21.6	17.94 *
128	2000	63 0	24.1 x 21.6 x 15.2	29.66 *
129	3000	84 0	21.6 x 21.6 x 20.3	46.38 *
190	6000	178 0	31.1 x 35.6 x 17.1	76.11 *

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P
113	20	11 7	7.3 x 4.3 x 4.4	0-115-210-240	0.74 Np 20
64	75	14 7	7.0 x 6.4 x 6.0	0-115-210-240	1.44 30
4	150	3 0	8.9 x 6.4 x 7.6	0-115-200-220-240	1.74 36
66	300	6 0	10.2 x 10.2 x 9.5	.. ..	3.38 52
67	500	12 8	14.0 x 10.2 x 11.4	.. ..	5.03 67
84	1000	16 0	11.4 x 14.0 x 14.0	.. ..	9.12 82 *
93	1500	28 9	13.5 x 14.9 x 16.5	.. ..	13.22 *
95	2000	40 0	17.8 x 16.5 x 21.6	.. ..	17.26 *
73	3000	45 8	17.4 x 18.1 x 21.3	.. ..	23.47 *

**TOTALLY ENCLOSED 115V AUTO TRANSFORMER**  
115V 500 Watt totally enclosed auto transformer, complete with mains lead and two 115V outlet sockets, £6.85, P & P 67np.

**LOW VOLTAGE SERIES (ISOLATED)**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Windings	P & P
111	0.5	0.25	12 7.6 x 5.7 x 4.4	0-12V at 0.25A x 2	0.74 Np 22
213	1.0	0.5	1 0 8.3 x 5.1 x 5.1	0-12V at 0.5A x 2	0.88 22
71	2	1	0 7.0 x 6.4 x 5.7	0-12V at 1A x 2	1.16 22
18	4	2	7.0 x 7.0 x 7.0	0-12V at 2A x 2	6.2 36
70	6	3	12 10.2 x 7.6 x 8.6	0-12V at 3A x 2	1.95 42
72	10	5	6 3 7.9 x 10.8 x 10.2	0-12V at 5A x 2	2.56 52
17	16	8	7 8 12.1 x 9.5 x 10.2	0-12V at 8A x 2	3.95 52
115	20	10	11 13 12.1 x 11.4 x 10.2	0-12V at 10A x 2	5.03 67
187	30	15	16 12 13.3 x 12.1 x 12.1	0-12V at 15A x 2	9.28 82 *
226	60	30	34 0 17.0 x 14.5 x 12.5	0-12V at 30A x 2	17.05 *

**30 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P
112	0.5	1 4	8.3 x 3.7 x 4.9	0-12-15-20-24-30V	0.88 Np 22
79	1.0	2 0	7.0 x 6.4 x 6.0	.. ..	1.16 36
3	2.0	3 2	8.9 x 7.0 x 7.6	.. ..	1.75 36
20	3.0	4 4	10.2 x 8.9 x 8.6	.. ..	2.16 42
21	4.0	6 0	10.2 x 10.0 x 8.6	.. ..	2.56 52
51	5.0	6 8	12.1 x 10.0 x 8.6	.. ..	3.18 52
117	6.0	7 8	12.1 x 10.0 x 10.2	.. ..	3.79 52
89	10.0	12 2	14.0 x 10.2 x 11.4	.. ..	6.21 67

**50 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P
102	0.5	1 11	7.0 x 7.0 x 5.7	0-19-25-33-40-50V	1.16 Np 30
103	1.0	2 10	8.3 x 7.3 x 7.0	.. ..	1.69 36
104	2.0	5 0	10.2 x 8.9 x 8.6	.. ..	2.34 42
105	3.0	6 0	10.2 x 10.2 x 8.3	.. ..	3.18 52
106	4.0	9 4	12.1 x 11.4 x 10.2	.. ..	4.20 52
107	6.0	12 4	12.1 x 11.4 x 13.3	.. ..	6.21 67
118	8.0	18 9	13.3 x 13.3 x 12.1	.. ..	8.10 92
119	10.0	19 12	16.5 x 11.4 x 15.9	.. ..	10.15 97

**60 VOLT RANGE**

Ref. No.	Amps.	Weight lb oz	Size cm.	Secondary Taps	P & P
124	0.5	2 4	8.3 x 9.5 x 6.7	0-24-30-40-48-60V	1.18 Np 36
126	1.0	3 0	8.9 x 7.6 x 7.6	.. ..	1.64 36
127	2.0	5 6	10.2 x 8.9 x 8.6	.. ..	2.56 42
125	3.0	8 8	11.9 x 9.5 x 10.0	.. ..	3.90 52
123	4.0	10 6	11.4 x 9.5 x 11.4	.. ..	5.03 67
120	6.0	16 12	13.3 x 12.1 x 12.1	.. ..	7.28 82
122	10.0	23 2	16.5 x 12.7 x 16.5	.. ..	12.05 *

\*Carriage via B.R.S.

**LEAD ACID BATTERY CHARGER TYPES**

Ref. No.	Amps.	Weight lb oz	Size cm.	For Charging	P & P
45	1.5	1 9	7.0 x 6.0 x 6.0	6 OR 12 VOLT BATTERIES	1.17 Np 30
5	4.0	3 11	10.2 x 7.0 x 8.3	Please note, these units do not include rectifiers	1.77 42
86	6.0	5 12	10.2 x 8.9 x 8.3	.. ..	2.67 52
146	8.0	6 4	8.9 x 10.2 x 10.2	.. ..	3.04 52
50	12.5	11 14	13.3 x 10.8 x 12.1	.. ..	4.52 67

All ratings are continuous. Standard construction: open with solder tags and wax impregnation. Enclosed styles to order.

**FULL SPEC. SEMICONDUCTOR DEVICES**

AD 161/162 Output pair, with mica & bushes. 60 np pair.

ZN 3055 with mica & bushes. 68 np each.

BC 107 BC 108 BC 109 all 9 np each.

Below 10 pieces BC range add 10 np for postage and packing.

★ Ex stock items same day service

★ Quantity prices on application

Also stocked: SEMICONDUCTORS · VALVES


MULTIMETERS · MAINS KEYNECTOR

ELECTROSIL METAL OXIDE RESISTORS
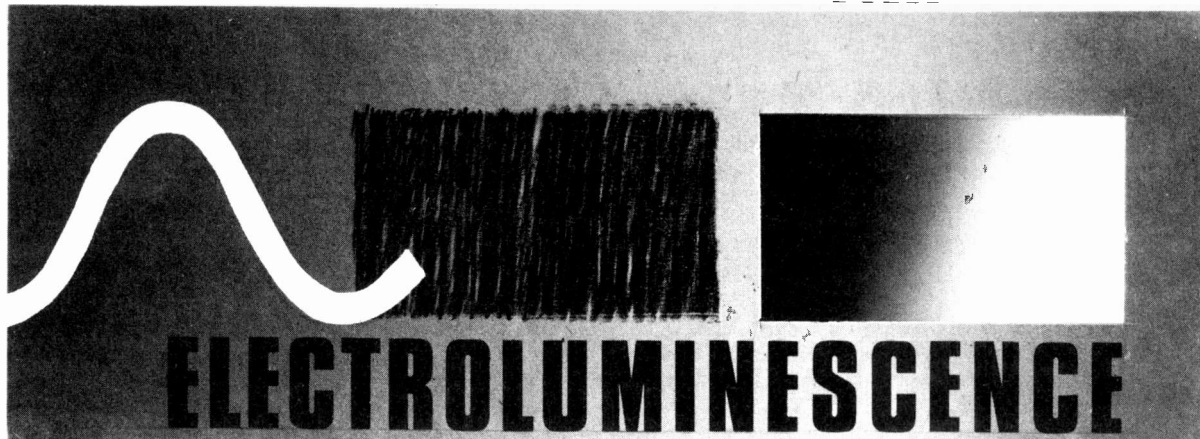
## BARRIE electronics

11 MOSCOW ROAD, QUEENSWAY  
LONDON W2 4AH Tel: 01-229 6681/2

NEAREST TUBE STATIONS: BAYSWATER, QUEENSWAY



By **K. J. Matthews** M.Sc.

**L**UMINESCENCE is the general term which is applied to the production of light, either visible or infra-red, by the direct conversion of some other form of energy. The general term is then subdivided to denote the particular energy conversion involved.

Therefore, the production of light from heat, an effect which has been known for some considerable time, is designated thermoluminescence. A more modern, but very popular effect, is cathodoluminescence. This is light from kinetic energy or particle bombardment and keeps millions of T.V. screens active.

**ELECTROLUMINESCENCE**

Other forms include chemiluminescence, and bioluminescence, which is a division of chemiluminescence and occurs in some deep sea fish and in glow-worms. Photoluminescence is a special case as it involves a light to light conversion, the emitted light differing from the stimulating radiation in frequency.

Finally, electroluminescence is the emission of light by direct conversion of electrical energy. The standard abbreviation for the effect is written EL. This process is not to be confused with the ordinary tungsten filament bulb, where there is an intermediate stage of heat making the process thermoluminescent.

A few EL devices are now available to the public. Unfortunately these are as yet only infra-red emitters, but visible light devices do exist and are certain to become available in the near future.

**USES**

Uses for these devices are self evident. In most cases they can be substituted wherever small panel lamps are employed, and their higher efficiency will

make them suitable for use with battery powered equipment. Numerical displays have been fabricated and because conventional read-out tubes require high voltages, EL devices of this type are likely to become very popular.

At the present stage in the development of EL devices, their use for general lighting seems a little remote. They cannot compete with fluorescent lighting for efficiency and only give monochromatic light.

It is not the aim of this article to describe practical applications but to give some insight into the mechanism of EL and of trends in present day research.

**SEMICONDUCTOR BAND STRUCTURE**

Some knowledge of semiconductor band theory is necessary before any understanding of electroluminescence is possible. Unfortunately this can be very complex and it is only possible to scratch the surface of the topic.

Fig. 1 depicts a semiconductor in energy band form. It consists of two bands, the conduction band and the valence band with an energy gap separating them. Electrons cannot exist with energies within this gap, and for this reason it is known as the forbidden gap or region.

For an electron to move from a valence band to a conduction band, it must "jump" the energy gap. A gradual transition is not allowed.

If the semiconductor has no energy, the conduction band will be void of electrons and the valence band full. In this state it is electrically inert—an insulator. However, a semiconductor always has some energy by virtue of its temperature, and this causes electrons to be propelled across the gap into the conduction band.

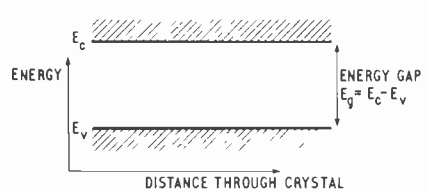


Fig. 1. Simple energy band diagram of a semiconductor

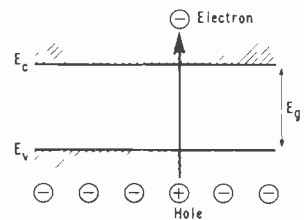


Fig. 2. The excitation process

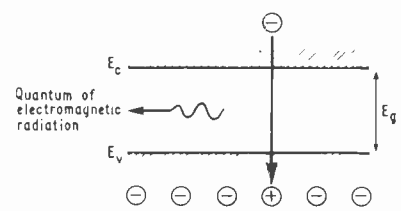


Fig. 3. Radiative recombination

To do this it is necessary that an electron receives an amount of energy at least equal to the energy represented by the width of the forbidden gap to enable it to make the jump. If it receives less it will not be able to do so. As we will see later, the size of the gap is constant for a particular semiconductor and is measured in terms of energy, in electron-volts (eV).

## EXCITATION

When an electron receives sufficient energy to jump the gap to the conduction band, it leaves behind in the valence band a vacancy known as a "hole." See Fig. 2. It is convenient to think of these holes as positive electrons, but with reduced mobility.

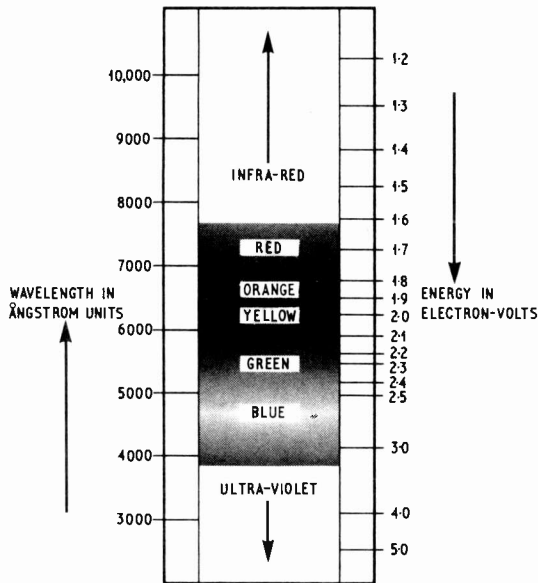


Fig. 4. Wavelength to energy conversion chart

If energy is now injected into the semiconductor for a short time and then removed, the internal equilibrium of the semiconductor is upset. There will be too many electrons in the conduction band and the semiconductor is said to be in an excited state.

There are many ways in which equilibrium may be restored. Here are three of the more important processes:

- (1) the electrons may be ejected from the material entirely—similar to thermionic emission.
- (2) the electrons may impart their energy to the crystal lattice of the semiconductor causing its atoms to vibrate. These vibrations are known as phonons.
- (3) the electrons may fall back across the gap to occupy holes in the valence band, emitting as it does so, quanta of electromagnetic radiation, the frequency of which is determined by the width of the forbidden gap. This process, known as electron-hole recombination, is illustrated in Fig. 3.

These three processes, and others unmentioned, all occur in any semiconducting material simultaneously competing with each other. It is obviously the latter radiative process which is of interest to

EL, and it is desired that this be the main process if good light emitting efficiencies are to be obtained.

## CRITERIA FOR ELECTROLUMINESCENT MATERIAL

In some semiconducting materials a radiative transition can only be achieved after a process of the phonon type has occurred. This is a characteristic of the material and cannot be altered. As this process is a two stage one, the energy gap of the semiconductor is known as indirect, or the material is called an indirect semiconductor.

In other materials, known consequently as direct semiconductors, the radiative transition occurs singly. Other processes still compete but these are minor compared to the serious drawback of an indirect energy gap. They can in any case often be minimised by reducing the temperature of operation of the semiconductor if super-efficiency is required.

Clearly then, the first criterion for an electroluminescent material is that it be direct. The second is the width of the energy gap, as this determines the frequency of the emitted light.

According to quantum physics, energy and frequency of light are related by the equation.

$$\text{Energy} = h \times \text{frequency}$$

where  $h$  is Planck's constant =  $6.62 \times 10^{-27}$

$$\text{Since frequency} = \frac{\text{velocity}}{\text{wavelength}}$$

the energy equation becomes

$$\text{Energy} = \frac{h \times \text{velocity of light}}{\text{wavelength of light}}$$

Substituting for  $h$  and velocity of light and converting to convenient units yields

$$\text{Wavelength in angstrom units (\AA)} = \frac{12,400}{\text{Energy in electron volts (eV)}}$$

The visible spectrum runs from 8,000Å (red) to 4,000Å (blue) which on conversion gives red as equivalent to 1.55eV and blue to 3.0eV.

To recapitulate, the semiconductor must have a direct gap, and this must lie within the range, 1.55 to 3.00eV for visible light emission. If the gap is narrower than 1.55eV, infra-red emission will be obtained. See Fig. 4.

## DEVICES


Before investigating the available EL materials consideration must be given to the method of its use in the production of a useful device.

As we have seen the trick lies in the method by which non-equilibrium conditions are set up in the semiconducting material. This can be done by any form of energy input, but for EL it must obviously be brought about by electrical energy. There are two known ways of doing this, and this causes a split in the research into EL devices as the resulting products are so unlike.

The older method is the electroluminescent panel in which excitation is brought about by a high electric field although the full theory is not understood.




### PHILIPS PORTABLE PLAYER CABINET

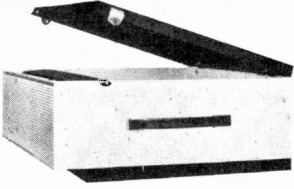

Size 18 x 15 1/2 in. Cut for BSR UA12/14/15/16/25 deck. Amplifier space 14 x 5 x 3 in. Satin aluminium front grille. Really smart appearance. Post Black/White. Chrome fittings. £4 25p
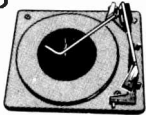
### BSR C.109 SUPERSLIM STEREO & MONO

Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR's reliability with 12 months' guarantee. AC 200/250V. Size 13 1/2 x 11 in. Above motor board 3 1/2 in. below motor board 2 1/2 in.



with STEREO and MONO XTAL £7-75 Post 25p.

### GARRARD SINGLE PLAY TA Mk II

Ideal Discobooth or Hi-Fi. Stereo/Mono. £10

### GARRARD PLAYERS with Sonotone 9TA Cartridges

Stereo Diamond and Mono Sapphire. SP25 Mk II £15. Model 3500 Stereo and Mono Autochanger £14. Post 25p.

### RECORD PLAYER PORTABLE CABINET

With space for R.C.S. Amplifiers and most modern autochangers. Two-tone rexine covered. Post 25p.

### RCS DE-LUXE 3 WATT AMPLIFIER

2-stage with triode pentode valve. Ready made tested. 2-stage with triode pentode valve. Ready made tested. Tone and volume controls. Isolated mains transformer. Knobs, loudspeakers, valves ECL82, EZ80. Response 50-12,000 cps. Sensitivity 200mV. Post 25p. £4

### R.C.S. TEAKWOOD BASE

Ready cut out for mounting (state player make and model). £2-75

### R.C.S. PLASTIC COVERS FOR ABOVE BASE

Durable tinted plastic, attractive appearance. £2-75

### EMI PICK-UP ARM

With mono xtal and stylus £1-25.

### HI-FI PICK UP CARTRIDGES

Diamond Stereo/Mono 9TA £2-50; GP94 £2-50; GP93 £2-00; Mono GP91 £1-50; GC8 £1-25; ACOS LE. only 50p.

### AM - FM/VHF GANG

Super quality small size 1 1/2 x 1 1/2 in. 365 + 365 pF with 25 + 25 pF. British made. Geared slow motion drive 6:1. Plastic dust cover. 6BA tapped front fixing. 50p

### WEYRAD P50 - TRANSISTOR COILS

RA2W Ferrite Aerial. 65p Spare Cores. 30p Osc. P50/1A. 30p Driver Trans. LFD74. 50p I.F. P50/2CC 470 kc. 33p Printed Circuit. P0A1. 50p 3rd I.F. P50/3CC. 33p J.W. Tuning Gang. P51/1 or P51/2. 33p Y.B. Winding Booklet. 10p P50/3V. 33p OPT1. 50p Mullard Ferrite Rod 8 x 1/2 in. 25p. 6 x 1/2 in. 25p.

### VOLUME CONTROLS

20ohm Coax 4p. yd. Long spindles. Midget Size 5 K. ohms to 2 Meg. 100 or LIN. L/S 15p. D.P. 25p. STEREO L/S 55p. D.P. 75p. FRINGE LOW LOSS 10p Edge 5K. 5 P. Transistor 25p. Ideal 625 and colour

### WIRE-WOUND 3-WATT POTS.

Small type with small knob. Values 10 K to 30 K. 25p

### WIRE-WOUND 3-WATT STANDARD SIZE POTS.

Values 10 K to 30 K. 25p

### VEROBOARD 015 MATRIX

2 1/2 x 5 in. 19p. 2 1/2 x 3 1/2 in. 16p. 3 1/2 x 3 1/2 in. 19p. 3 1/2 x 5 in. 26p.

### EDGE CONNECTORS

16 way 25p; 24 way 38p. PINS 36 per packet 17p. FACE CUTTERS 36p.

### S.R.B.P. Board 0-15 MATRIX

2 1/2 in. wide 4p per lin. 5 in. wide 5p per lin. (up to 17 in.). S.R.B.P. undrilled 1/4 in. Board 10 x 8 in. 15p.

### BLANK ALUMINIUM CHASSIS

18 s.w.g. 2 1/2 in. sides 6 x 4 in. 49p; 8 x 6 in. 53p; 10 x 7 in. 55p; 12 x 8 in. 59p; 14 x 9 in. 90p; 16 x 6 in. 90p; 12 x 7 in. 55p.

### ALUMINIUM PANELS

18 s.w.g. 6 x 4 in. 9p; 8 x 6 in. 15p; 14 x 3 in. 16p; 10 x 7 in. 19p; 12 x 5 in. 20p; 12 x 8 in. 28p; 16 x 6 in. 28p; 14 x 9 in. 34p; 12 x 12 in. 40p.

### 1 inch DIAMETER WAVECHANGE SWITCHES

2p. 2-way, or 2p. 6-way, or 3p. 4-way 25p each. 1 p. 1-2-way, or 4 p. 2-way, or 4 p. 2-way 25p.

### TOGGLE SWITCHES

sp. 14p; dp. 18p; dp. dt. 23p.

### "THE INSTANT" BULK TAPE ERASER AND RECORDING HEAD DEMAGNETISER



£2-35 Post 15p

Minimum Post and Packing 15p. RETURN OF POST DESPATCH. HI-FI STOCKISTS.

### RADIO COMPONENT SPECIALISTS

List 5p. Written guarantee with every purchase. (Export: Remit cash and extra postage.) Buses 50, 68, 159 pass door. S.R. Stn. Selhurst. Tel. 01-684-1885

### R.C.S. STABILISED POWER PACK KIT

All parts and instructions with Zener Diode, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less PLEASE STATE VOLTAGE REQUIRED. £2 Post Free Details S.A.E.

### R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guiitar, etc. Can be used with Battery 9-12v. or H.T. line 200-300V. D.C. operation. Size 1 1/2 x 1 1/2 in. Response 25 c.p.s. to 25 Kc/s, 26 db gain. For use with valve or transistor equipment. Full instructions supplied. Brand new. 90p Post 10p Guaranteed. Details S.A.E.

### NEW TUBULAR ELECTROLYTICS CAN TYPES

2/350V	14p	250/25V	14p	16-16/500V	55p
4/350V	14p	500/25V	20p	50-50/350V	35p
8/450V	14p	1000/25V	35p	60-100/350V	55p
16/450V	15p	1000/50V	47p	32-32/250V	18p
32/450V	20p	8+8/450V	18p	32-32/450V	33p
25/25V	10p	8+16/450V	20p	350+50/325V	50p
50/50V	10p	16+16/450V	25p	32+32+32/350V	43p
100/25V	10p	32+32/350V	25p	100+50+50/350V	48p

### SUB-MIN. ELECTROLYTICS 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p; 500, 1000mF 12V 18p; 2000mF 25V 35p.

CERAMIC 1pF to 0.01mF, 4p. Silver Mica 2 to 5000pF, 4p. PAPER 350V-0.1pF, 0.5 13p; 1mF 15p; 2mF 150V 15p. 500V-0.001 to 0.05 4p; 0.1 6p; 0.25 8p; 0.47 25p. SILVER MICA. Close tolerance 1%, 2-2-500pF 5p; 560-2,200pF 10p; 2,700-5,600pF 20p; 6,800pF-0.01, mid 30p each. TWIN GANG. "0-0" 208pF+178pF, 50p; 500pF slow motion, standard 45p; small 3-gang 50p £1.60.

SHORT WAVE SINGLE. 25pF, 50pF, 55p. CERAMIC TELESCOPE. 25pF, 55p. SWIVEL BASE 20p. TUNING. Solid dielectric. 100pF, 500pF, 35p each. TRIMMERS. Compression 30, 50, 70pF, 5p.

FULL WAVE BRIDGE RECTIFIERS 500mA 50p; 1250pF, 10p. SILICON REC. 40-LUCAS 2D5500 Bridge 70v. 5 amp £1. RECTIFIERS CONTACT COOLED half wave 80mA 38p; 85mA 48p. SILICON BYZ13 30p; BY100 30p; BY127 30p. Full wave Bridge Rectifier 75mA 50p; 150mA 98p.

EX-GOVT. RECTIFIERS 250V 200mA £2-500pF 5p; NEON PANEL INDICATORS 250V AC/DC Red or Amber 20p. RESISTORS. 1/4, 1/2, 1w, 2w, 5w, 10, 20, 50, 100, 100M. HIGH STABILITY. 1/2 w. 2%, 10 ohms to 1 meg., 10p. Ditto 5%. Preferred values 10 ohms to 10 meg., 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10 ohms to 100K 10p each; 2 1/2 watt, 1 ohm to 8-2 ohms 10p.

### PHILIPS TRANSISTOR FM STEREO MULTIPLEX DECODER

As used in LEAK Troughline Tuner. Brand New. Pre-aligned with 9 semiconductor. 24V d.c. at 6mA. Complete with 1/2 in. x 1/2 in. connection details. £4 Post Free 3 1/2 x 2 x 1 in.

### MAINS TRANSFORMERS

250-0-250 80 mA, 6.3 v. 4 p.	£1.40
250-0-250 80 mA, 6.3 v. 3.5 a, 6.3 v. 1 a, or 5 v. 2 a.	£2
350-0-350 80 mA, 6.3 v. 5.5 a, 6.3 v. 1 a, or 5 v. 2 a.	£2
300-0-300 v. 120 mA, 6.3 v. 4 a, C.T. 6.3 v. 2 a.	£2.50
MINIATURE 200 v. 20 mA, 6.3 v. 1 a, 2 1/2 x 2 1/2 in.	75p
MIDGET 220 v. 45 mA, 6.3 v. 2 a, 2 1/2 x 2 1/2 in.	90p
P.E. AURORA TRANS. 12+12v. 500mA	£1.50
MINI-MAINS 20v. 100mA, 1 1/2 x 1 1/2 in.	50p
HEATER TRANS. 6.3 v. 3a.	80p
Ditto tapped 6.3 v. 4.5, 6.3, 1 1/2 amp.	80p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30 v.	£2
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.	£2
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60.	£3
AUTO TRANSFORMERS. 115v to 230v or 230v to 115v. Input output. 500w. 25, 50, 100w. 212	
CHARGER TRANSFORMER. 115v 200/250v.	£2
6 or 12v. 1 1/2 amp. £1-20; 2 amp. £1-50; 4 amp. £2	
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12v. outputs. 1 1/2 amp; 2 amp; 55p; 4 amp; 85p.	

### E.M.I. 13 1/2 x 8 in. LOUDSPEAKERS

With twin tweeters. £4 Post 15p. And crossover. 10 watt. State 3 or 8 or 15 ohm. 4 illustrated.

With hared tweeter cone and ceramic magnet, w. w. magnet, w. w. magnet. Base res. 45-60 cps. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 15p

Recommended Teak Cabinet Size 18 - 10 in. Post 25p. £5

### 10W MINI-MODULE £3-25 LOUDSPEAKER KIT

Post 25p. Triple speaker system combining on ready cut baffle. 1 in. chipboard 15 in. 8 1/2 in. Separate Bass, Middle and Treble loudspeakers and crossover condenser. The heavy duty 5 in. Bass Woofer unit has a low resonance cone. The Mid-Range unit is specially designed to add drive to the middle register and the tweeter recreates the top end of the musical spectrum. Total response 20-15,000 cps. Full instructions for 3 or 15 ohm. TEAK VENEERED BOOKSHELF ENCLOSURE. 16 1/2 x 10 1/2 x 6 in. Modern design, dark grey Tegan covered baffle. Or with Fluted Wood Front. 16 x 10 x 9 in. £5 Post 25p

### ALL MODELS "BAKER SPEAKERS" IN STOCK

### BAKER 12 in MAJOR £9



30-14,500 c.p.s., 12in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 8 or 15 ohm. Post Free.

### BAKER "BIG-SOUND" SPEAKERS

Group 27	Group 35	Group 50
12 inch £7	12 inch £9	15 inch £19
25 watt	35 watt	50 watt
3 or 8 or 15 ohm	3 or 8 or 15 ohm	8 or 15 ohm

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11-50

### TEAK HI-FI SPEAKER CABINETS

Fluted wood front. For 12 in. dia. speaker 20 x 13 x 9 in. £9 Post 25p. For 13 x 8 in. speaker 16 x 10 x 9 in. £5 Post 25p. For 10 x 6 in. speaker 16 x 8 x 6 in. £4 Post 25p. LOUDSPEAKER CABINET WADDING 18 in. wide, 15p tf

### GOODMANS HI-FI 6 in. WOOFER

8 ohm, 10 watt. Large ceramic magnet. Special Cambric cone surround. Frequency response 30-12,000 cps. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. £4

### ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 cps to 15,000 cps. Size 3 1/2 x 3 1/2 in. dia. Rating 10 watt, 3 ohm or 15 ohm models. £1-90 Post 10p

### Horn Tweeters 2-16Kc/s, 10W 8 ohm or 15 ohm £1-50.

De Luxe Horn Tweeters 2-18 Kc/s, 15W 8 ohm £2. SPECIAL OFFER: 80 ohm, 2 1/2 in. dia.; 35 ohm, 2 in.; 3 in. 25 ohm, 2 in. dia.; 3 in. dia.; 6 4 in.; 8 5 in. £1 EACH 15 ohm, 3 1/2 in. dia.; 7 4 in.; 8 5 in. 8 ohm, 6 x 4 in.; 3 ohm, 2 in. dia.; 5 in. 3 in. 5 in. 3 in. 7 4 in. LOUDSPEAKERS P.M. 3 OHMS 6 in. £1-10; 8 x 5 in. £1-25; 8 x 2 in. 90p; 8 in. £1-75; 10 x 6 in. £1-90. 5 in. WOOFER, 8 w. max. 20-10,000 cps, 8 or 15 ohm £1-80. ELAC 10 in. 10w. Twin Cone. De Luxe Ceramic 8 ohm £4. RICHARD ALLAN TWIN CONE LOUDSPEAKERS 8 in. dia. 4 watt; 10 in. dia. 5 watt; 12 in. dia. 6 watt. 3 or 8 or 15 ohm models £1-95 each. Post 15p. OUTPUT TRANS. EL84, etc. 25p. MIKE TRANS. 50-1 25p. SPEAKER COVERING MATERIALS. Samples large S.A.E. GOODMANS OUTPUT TRANSFORMERS. Full post pull for values EL84, etc. 3 A and 15 ohms 85p. Post 20p.

### BAKER 100 WATT ALL PURPOSE POWER AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. AC. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £39 Post Free

### ALL EAGLE PRODUCTS

SUPPLIED AT LOWEST PRICES. ILLUSTRATED EAGLE CATALOGUE 20p. Post free

### BARGAIN AM TUNER

Medium Wave. Transistor Superbet. Ferrite aerial. 9 volt. £4

### BARGAIN 4 CHANNEL TRANSISTOR MIXER

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. £3

### BARGAIN FM TUNER 88-108 Mc/s Six Transistor

9 volt. Printed Circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 1/2 x 4 1/2 inch BARGAIN FM TUNER as above. £7-50

### BARGAIN 3 WATT AMPLIFIER

4 Transistor Push-Pull Ready built, with volume control. 9v. £3-50

### COAXIAL PLUG 6p, PANEL SOCKETS 6p. LINE 18p.

OUTLET BOXES. SURFACE OR FLUSH 25p. BALANCED TWIN FEEDERS 5p yd. 80 ohms or 300 ohms. JACK SOCKET Std. open-circuit 14p. closed circuit 23p; Chrome Lead Socket 45p. Phone Plug 5p. Phone Socket 5p. JACK PLUGS Std. Chrome 15p; 3-5mm Chrome 14p. DIN SOCKETS Chassis 3-pin 10p; 5-pin 10p. DIN SOCKETS Lead 3-pin 18p; 5-pin 25p. DIN PLUGS 3-pin 18p; 5-pin 25p. VALVE HOLDERS, 5p; CERAMIC 8p; CANS 5p.

### E.M.I. TAPE MOTORS, 120v. or 240v.

AC. 1,200 r.p.m. 4 pole 135mA Spindle 0-187 x 0-75 in. Size 3 1/2 x 2 1/2 in. (illustrated). Post 15p. £1-25

### BALFOUR GRAM. MOTORS.

120v. or 240v. AC. 1,200 r.p.m. 4 pole 50mA Spindle 1 x 3/20. Size. 85p 2 1/2 x 2 1/2 in. Post 15p

### Minimum Post and Packing 15p. RETURN OF POST DESPATCH. HI-FI STOCKISTS. CUSTOMERS FREE CAR PARK. CALLERS WELCOME


### 337 WHITEHORN ROAD, CROYDON

Open 9-6 p.m. (Wednesdays 9-1 p.m., Saturdays 9-5 p.m.)

Buses 50, 68, 159 pass door. S.R. Stn. Selhurst. Tel. 01-684-1885

991

### BODINE TYPE N.C.I. GEARED MOTOR

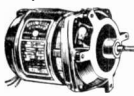

(Type 1) 71 r.p.m. Torque 10lb. inch. Reversible. 1/70th h.p., 50 cycle, 0.38 amp. (Type 2) 28 r.p.m. Torque 20lb. inch. Reversible. 1/80th h.p., 50 cycle, 0.28 amp.

"As new" condition. Input voltage of motor 15V a.c. Supplied complete with transformer for 230/240V a.c. input. Price, either type £3-15 plus 35p P. & P. or less transformer £2-13 plus 27p P. & P.

### 12 VOLT DC MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 RPM complete with external gear train (removable) giving final speed of 125 RPM. Size: 4 1/2" x 2 1/2" dia. Price 95p inc. post.



### 230V/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 1 rev. per hour. Clockwise rotation. 1 rev. per hour. Anti-clockwise rotation. 2 revs. per hour. Clockwise rotation. 3 revs. per hour. Anti-clockwise rotation. 60 revs. per hour. 1 r.p.m. Clockwise. Fraction of makers' price. All at 75p incl. P. & P.



### MICRO SWITCH

5 amp. c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20)



### MINIATURE LEVEL METER

Approximately 300 micro amp basic, as fitted to Tape Recorders, etc. Strip type dual coloured dial. 50p + 8p P. & P.



### ELECTRONIC ORGAN KIT

Easy to build, Solid State. Two full octave (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2 batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3-00. P. & P. 22p.

### 50 in 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sound Level Meter, 2 Transistor Radio, Amplifier, etc. Price £7-75. P. & P. 30p.

### CRYSTAL RADIO KIT

Complete set of parts, including: Crystal Diode, Ferrite Aerial, Drilled Chassis, and Personal Ear Piece. No soldering, easy to build, full step by step instructions. £1-75 inc. post.

### 230v AC SOLENOID

Extremely powerful with approx. 14lb. pull, 1" travel. Fitted with mounting feet. Size: 4" long, 2 1/2" wide, 3" high. £2-00 incl. P. & P.



### VENNER Electric Time Switch

200/250V Ex GPO. Tested. Manually set 2 on, 2 off every 24h. Override switch: 10A £2-75, 15A £3-35, 20A £3-75. P. & P. 20p. Also available with solar dial ON dusk, OFF dawn. Price as above.



### THIS MONTH'S SNIP !! PROXIMITY SWITCH (NEW)

Useful black, crackle finish, metal case. Size 9 1/2" x 5" x 2 1/2". Containing, one 12V LT transformer, three OC170, one AC128, one AF186, one 38-334 MHz crystal, mains neon, S.P. toggle, miniature fuse holder, pots, etc., etc. Sold for component value only, we have no details regarding usage or circuits. Bargain price ONLY 80p + 30p P. & P.

### VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V.

All Types (and Spares) from 1/2 to 50 amp from stock.

### SHROUDED TYPE

1 amp, £7-00 2.5 amp, £8-05  
5 amp, £11-75  
10 amp, £22-50. 20 amp, £49-00.  
15 amp, £25-00. 25 amp, £58-00.  
37.5 amp, £82-00. 50 amp, £98-00.



2.5 AMP


OPEN TYPE (Panel Mounting) 1/2 amp, £4-75. 1 amp, £7-00. 2 1/2 amp, £8-05.

### Superior Quality Precision Made NEW POWER RHEOSTATS

100 WATT. 1 ohm, 10A; 5 ohm, 4-7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1-4A; 100 ohm, 1A; 250 ohm, 0-7A; 500 ohm, 0-45A; 1 kΩ, 280 mA; 1-5 kΩ, 230 mA; 2-5 kΩ, 2A; 5kΩ, 140 mA. Diameter 3 1/2 in. Shaft length 1 in, dia. 1 1/8 in. All at £1-50 each. P. & P. 5p.

50 WATT. 1/5/10/25/50/100/250/500/1/1-1/5/2-5/5kΩ. All at £1-12 each. P. & P. 11p.

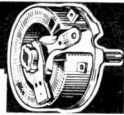25 WATT. 10/25/50/100/250/500/1/1-1/5/2-5/3-5/5kΩ. All at 78p each. P. & P. 15p.



### STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

**EXPERIMENTERS' ECONOMY KIT**  
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard, S.C.R., Unijunction Xenon Tube and instructions £6-30 plus 25p P. & P.

**NEW INDUSTRIAL KIT**  
Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10-50. P. & P. 50p.

**HY-LYGHST STROBE MK III**  
This strobe has been designed and produced for use in large rooms, halls and the photographic field, and utilizes a silica plug-in tube for longer life expectancy, printed circuit for easy assembly, also a special trigger coil and output capacitor. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12-00. P. & P. 50p.

**SPECIALLY DESIGNED, FULLY VENTILATED METAL CASE.** Including reflector. £4-00 P. & P. 45p. Post paid with kit.

### AND NOW! THE 'SUPER' HY-LYGHST KIT

Approx. four times the light output of our well proven Hy-Lyghst strobe. Incorporating:

- Heavy duty power supply
  - Variable speed from 1-23 flash per sec.
  - Fantastic Octal based tube with massive electrodes.
  - Reactor control circuit producing an intense white light.
- The brilliant light output of the "SUPER" HY-LYGHST gives fabulous effects with colour filters. Never before a Strobe Kit with so HIGH an output at so LOW a price. ONLY £20 plus 75p P. & P.
- ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE** specially designed for the Super Hy-Lyghst Kit including reflector. £7-00 P. & P. 45p. 7-inch POLISHED REFLECTOR. Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

### RELAYS SIEMENS, PLESSEY, Etc.


#### MINIATURE RELAYS - COMPETITIVE PRICES

1				2				3				4			
45	6-9	2 HD M	50p	700	15-35	2 c/o HD	73p*	185	6-12	4 c/o	73p*	700	16-24	6M	63p*
230	9-12	4 c/o	78p*	1,250	24-36	4 c/o	63p*	280	9-12	2 c/o	73p*	2,500	36-45	6M	63p*
600	18-32	4 c/o	78p*	2,400	30-48	4 c/o	50p	700	16-24	4M 2B	63p*	5,800	40-70	4 c/o	63p*
700	16-24	4 c/o	78p*	9,000	40-70	2 c/o	50p*	700	16-24	4 c/o	63p*	15k	85-110	6M	50p*

(1) Coil ohms; (2) Working d.c. volts; (3) Contacts; (4) Price (HD) Heavy Duty. All Post Paid. \*Including Base.

**MAINS RELAY**  
230V a.c. coil 3 c/o. 10 amp a.c. contacts, 50p plus 8p P. & P.

# VEROBOARD

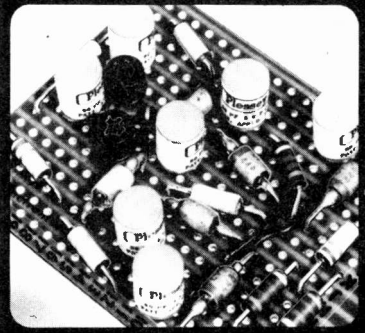

## VEROBOARDS GIVE A PROFESSIONAL FINISH TO YOUR WORK

0.1" and 0.15" pitch, plain and copper clad universal circuit boards.

AVAILABLE FROM YOUR LOCAL RETAILER.

TRADE DISTRIBUTOR N. Rose (Electrical) Ltd., London, W.C.1.



VERO ELECTRONICS LTD.  
Industrial Estate, Chandler's Ford,  
SO5 3ZR Tel: Chandler's Ford 2821

### 4-STATION INTERCOM



Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in de-luxe plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft. and other accessories. P. & P. 40p.

**MAINS INTERCOM**  
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £14-50. P. & P. 50p extra.

### INTERCOM/BABY ALARM



Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft. connecting wire. Battery 14p. P. & P. 20p.

### Transistor TELEPHONE AMPLIFIER

Why not boost business efficiency with this incredible De-Luxe Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Battery 14p extra. P. & P. 22p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE12)  
169 KENSINGTON HIGH STREET, LONDON, W.8

# SERVICE TRADING CO

All Mail Orders—Also Callers—Ample Parking Space  
Dept. P.E. 57 BRIDGMAN ROAD, LONDON W4 5BB  
Phone 01-995 1560 SHOWROOM NOW OPEN MON.-FRI.

Personal callers only. Open Sat.  
9 LITTLE NEWPORT ST.  
LONDON WC2H 7JJ 01-437 0576

This method has been known for some time but modern materials research has improved the EL panel vastly, making d.c. operation feasible where before only a.c. was possible.

### STRUCTURE OF PANEL

The basic construction of a panel is simple, see Fig. 5, although more complicated, and more efficient geometries have been produced. In a d.c. display, the backing electrode which is the cathode is made of aluminium.

The anode, through which the light must pass, is of glass treated in such a way as to make it conductive. This is accomplished by placing a very thin coating of tin oxide on its surface, by vacuum evaporation or by a chemical method, so that it remains transparent.

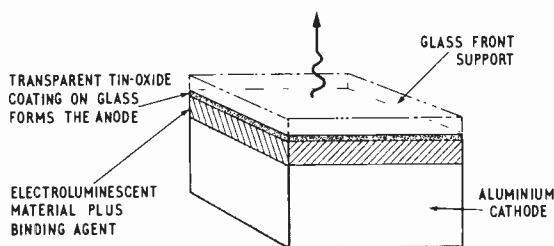


Fig. 5. Structure for a simple type of EL panel

The electroluminescent material is then mixed with a binding agent and spread very thinly between these electrodes, so that a high field is produced by a comparatively low voltage, typically 50 microns for 20 to 30 volt operation.

A newer method of stimulating EL and one which has been causing a great deal of interest, is based on the pn junction. The theory of this method of operation is better understood than the EL panel which still presents large areas of mystery.

If we suppose that a suitable material is available in both forms, i.e. *p*- and *n*-type, then a pn junction may be formed to make a diode.

In any junction diode, recombination of electrons and holes occurs at the junction when the diode is conducting in the forward direction as this is basic to its operation. If the semiconductor favours radiative recombination then the result will be light emission from the junction, produced directly by the passage of electric current through the diode.

To enable the light to escape the device, special geometries have to be employed in the manufacture of a crystal lamp if the bulk of the material is not to re-absorb it. Basically this means making a large area junction and arranging the emitting surface so that total internal reflection does not occur, which is by no means an easy job with the high refractive indices of most semiconductors. One type of arrangement is shown in Fig. 6.

### MATERIALS FOR ELECTROLUMINESCENCE

How many materials are useful or potentially useful semiconductors? Germanium and silicon certainly and gallium arsenide is by now fairly well

known, but the list doesn't stop there. Hundreds more are possible of which only a few as yet have been investigated. It would seem therefore that suitable EL materials would be commonplace but, unfortunately, this does not appear to be the case.

In the crystal lamp field if not in EL panels there is a desperate need for a good semiconductor. This shortage has led to the employment of one or two sophisticated tricks but the problem is by no means satisfactorily solved.

Consider the common semiconductors to see how they conform to the criterion laid down earlier. Germanium—indirect gap of 0.66eV, silicon—indirect gap of 1.08eV, both clearly of little use being so far in the infra-red as to make them inconvenient even if they were direct.

Gallium arsenide however is clearly much more

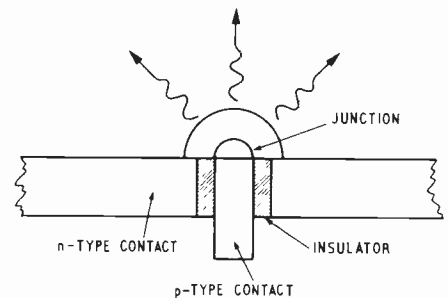


Fig. 6. Hemispherical structure of crystal lamp


promising, having a direct gap of 1.5eV, tantalisingly close to visible. The available devices, 56CAY, MGA100, are made from gallium arsenide.


### PERIODIC TABLE

Why is gallium arsenide a semiconductor? A glance at a section of the periodic table of the elements, Fig. 7, throws some light on this question and indicates where we may look for additional material.

We see that germanium and silicon lie in group IV as do tin and carbon. As diamond can be regarded as a semiconductor and so, under certain

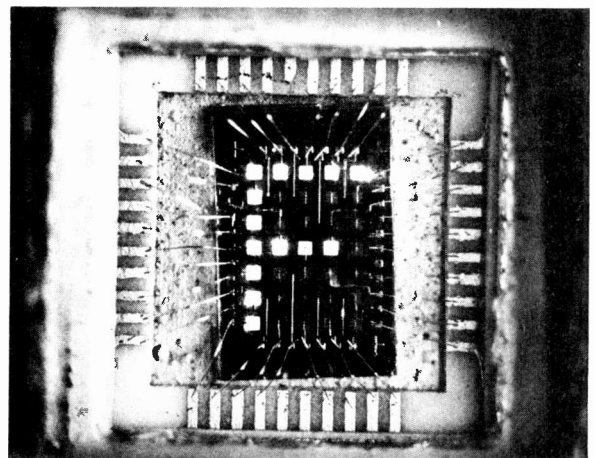**An array of 35 gallium phosphide lamps within a package overall size  $\frac{1}{4}$ in  $\times$   $\frac{1}{2}$ in approximately. In this photograph, the lamps have been illuminated to form the initial letter of the maker's name, Ferranti**



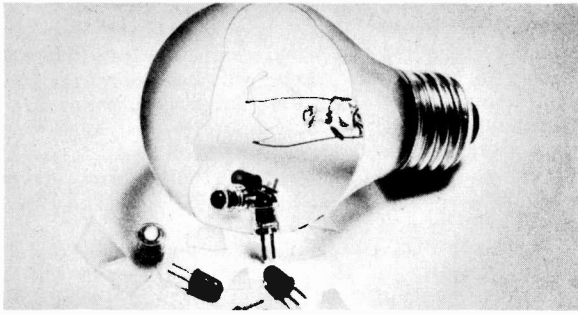

**Plastic encapsulated gallium arsenide phosphide red light emitting diodes made by Hewlett-Packard. These solid state lamps are designed for panel mounting or for printed circuit board mounting**

conditions, can tin, there seems to be something about group IV elements which have some connection with semiconducting properties.

If one element from group III is combined with one from group V, this also produces a semiconductor. These are known as compound semiconductors or compounds and gallium arsenide falls into this class.

II	III	IV	V	VI
	B	C	N	O
	Al	Si	P	S
Zn	Ga	Ge	As	Se
Cd	In	Sn	Sb	Te
Hg	Tl	Pb	Bi	Po

**Fig. 7. Section of the Periodic table of the elements**

In a similar fashion II-VI compounds are possible. Thus many semiconducting materials are possible and the more well known ones are listed in Table I, with their relevant parameters.

Confining ourselves to direct gap materials restricts the field considerably. All of the group IV elements are excluded, as well as three of the III-V compounds, the potentially useful three moreover. This leaves gallium arsenide as the compound with the largest direct gap, but this as we have seen is not good enough for visible EL.

At first sight the II-VI compounds are much more promising, zinc and cadmium sulphides both seem ideal, and indeed they are employed in the EL panel form of device. These materials, however, resist all attempts to grow them in both *p* and *n*-type forms and therefore crystal lamps cannot be constructed from them.

## DOPING

The position for visible light crystal lamps would appear then to be hopeless, but two tricks are possible which partially solve the problem. Firstly, an indirect gap material with a larger than necessary gap can be used. Doping agents can be added to them which will create energy levels in the forbidden gap, effectively reducing it in size and giving it the characteristics of a direct gap.

Gallium phosphide doping in this way with zinc and oxygen will give a red emitting diode and the highest efficiency that has recently been obtained is in the order of 7 per cent. Inefficient green luminescence may also be produced from gallium phosphide, of approximately 0.1 per cent but this is

stretching the material's capabilities. Gallium phosphide of the high quality needed cannot, as yet, be consistently produced.

## MIXED CRYSTALS

The second trick consists of the formation of a mixed crystal. Most of the III-V compounds are intermixable, that is, they can be grown together as a single, homogenous crystal. If in the growing of gallium arsenide for example, a proportion of phosphorus is added to the molten material, the resultant crystal contains a percentage of gallium phosphide.

This is a mixed crystal and should not be considered to be a mixture of gallium arsenide and gallium phosphide, but as a crystal of gallium arsenide phosphide, written  $GaAs_xP_{1-x}$ , the *x* indicating a whole range of compositions from pure gallium arsenide to pure gallium phosphide.

As gallium arsenide is direct and gallium phosphide is indirect, somewhere in the mixed crystal composition there must be a change over from the one type of de-excitation to the other, and it is possible to increase the energy gap for a considerable way before it becomes indirect.

Red emitting lamps from gallium arsenide phosphide are possible if the crystal is grown with the correct composition. These lamps are becoming quite common in professional areas and it must only be a matter of time before they are generally available.

This is the state of the art at present as regards the crystal lamp field. Several other mixed systems have been tried and are workable propositions but they still only produce red light diodes. Present research is searching, rather desperately, for an efficient green emitter.

**Table I: PROPERTIES OF THE BETTER KNOWN SEMICONDUCTORS**

Material	Type	Formula	$E_g$ (eV)	De-Excitation Process
Diamond	IV	C	5.2	indirect
Silicon	IV	Si	1.08	indirect
Germanium	IV	Ge	0.66	indirect
Silicon Carbide	IV	SiC	2.9	indirect
Gallium Arsenide	III-V	GaAs	1.5	direct
Gallium Phosphide	III-V	GaP	2.25	indirect
Gallium Antimonide	III-V	GaSb	0.67	direct
Indium Arsenide	III-V	InAs	0.36	direct
Indium Phosphide	III-V	InP	1.29	direct
Indium Antimonide	III-V	InSb	0.17	direct
Aluminium Phosphide	III-V	AlP	3.00	indirect
Aluminium Antimonide	III-V	AlSb	1.62	indirect
Zinc sulphide	II-VI	ZnS	3.7	direct
Cadmium Sulphide	II-VI	CdS	2.6	direct
Cadmium Telluride	II-VI	CdTe	1.45	direct
Cadmium Selenide	II-VI	CdSe	1.74	direct

# ATTRACTIVE DISCOUNTS!

# ELECTROVALUE

## Electronic Component Specialists

EVERYTHING BRAND NEW TO SPEC • LARGE STOCKS • NO SURPLUS

### BARGAINS IN NEW SEMI-CONDUCTORS

MANY AT NEW REDUCED PRICES - ALL POWER TYPES WITH FREE INSULATING SETS

40361	55p	2N2905	44p	2N4291	15p	BC148	9p	BFX87	29p
40362	68p	2N2905A	47p	2N4292	15p	BC149	10p	BFX88	26p
2N696	17p	2N2924	20p	AC107	46p	BC153	19p	BFY50	23p
2N697	18p	2N2925	22p	AC126	20p	BC154	20p	BFY51	20p
2N706	12p	2N2926	11p	AC127	20p	BC157	12p	BFY52	23p
2N930	29p	2N3053	27p	AC128	20p	BC158	11p	BSX20	16p
2N1131	29p	2N3055	60p	AC133K	22p	BC159	12p	C407	17p
2N1132	29p	2N3702	13p	AC176	16p	BC167	11p	MCI40	25p
2N1302	19p	2N3703	13p	ACY20	20p	BC168	10p	MPS6531	35p
2N1303	19p	2N3704	13p	ACY22	16p	BC169	11p	MPS6534	30p
2N1304	26p	2N3705	13p	AD140	63p	BC177	14p	NKT211	25p
2N1305	26p	2N3706	13p	AD142	50p	BC178	13p	NKT212	25p
2N1306	33p	2N3707	13p	AD149	58p	BC179	14p	NKT214	23p
2N1307	33p	2N3708	10p	AD161	33p	BC182L	11p	NKT274	18p
2N1308	36p	2N3709	11p	AD162	36p	BC183L	10p	NKT403	65p
2N1309	36p	2N3710	13p	AF114	24p	BC184L	11p	NKT405	79p
2N1613	23p	2N3711	13p	AF115	24p	BC212L	16p	OC71	38p
2N1711	26p	2N3819	23p	AF117	22p	BC213L	16p	OC81	25p
2N1893	54p	2N3904	35p	AF124	24p	BC214L	16p	OC81D	25p
2N2147	95p	2N3906	35p	AF127	22p	BCY70	7p	ZTX300	14p
2N2181	33p	2N4058	13p	AF139	33p	BCY71	13p	ZTX301	16p
2N218A	44p	2N4059	11p	AF239	16p	BF15	15p	ZTX302	16p
2N2219	38p	2N4060	11p	ASY26	27p	BF15	23p	ZTX303	22p
2N2219A	53p	2N4061	11p	ASY28	27p	BF167	18p	ZTX304	27p
2N2270	62p	2N4062	12p	BC107	12p	BF173	19p	ZTX500	18p
2N2369A	19p	2N4124	18p	BC108	11p	BF194	14p	ZTX501	21p
2N2483	35p	2N4126	27p	BC109	12p	BF195	15p	ZTX502	25p
2N2484	42p	2N4284	15p	BC125	15p	BFX29	31p	ZTX503	23p
2N2646	47p	2N4286	15p	BC126	15p	BFX29	25p	ZTX504	52p
2N2904A	42p	2N4289	15p	BC147	10p	BFX85	52p		

Appointed distributors for  
**SIEMENS (U.K.) LTD.**

Appointed stockists  
**NEWMARKET TRANSISTORS  
RADIOHM POTENTIOMETERS**

### SAVE £6.25 ON THE NEW ENGLEFIELD 840 AMPLIFIER

This latest Peak Sound high fidelity amplifier incorporates many strikingly original features including facility for adding in stereo FM tuner. Superb performance characteristics and luxurious styling. Electrovalue choice of simulated soft leather covering in black, blue, red or dark green. As now advertised at £49.50. Our price, nett **£38.75**

**MAINLINE AMPLIFIER KITS**  
70W. power amplifier, £12.60 nett.

### 30 WATT BAILEY AMPLIFIER PARTS

Transistors and PCB for one channel £6.46  
Capacitors, resistors (metal oxide), and transistors, one channel. £8.41.  
Complete unregulated power supply pack, £4.75  
Suitable heatsink 10DN 400C, 55p

### SIEMENS TTL INTEGRATED CIRCUITS

We stock a large range of all Siemens types for a very wide range of applications. For details, see our latest catalogue.

#### S-DeC RANGE

S-DeC, £1.44; DeCSTOR, £2.88; 5 DeC 4-pack, £3.10; T-DeC, £2.88;  $\mu$ DeC A, £3.18;  $\mu$ DeC B, £3.94.

Accessory prices increased by approx. 20% (pp. 51-53 in our catalogue). Guide prices unchanged.

#### INDICATOR LAMPS

NEON chrome bezel, round red NR/R, 24p; chrome bezel, round amber NR/A, 24p; chrome bezel, round clear NR/C, 24p. Neon, square red type LS5C/R, 18p; amber type LS5C/A, 18p; clear type LS5C/C, 18p. All above are for 240V mains operation. Filament types: 6V, 0.04A square red type LS5C/R-6V, 30p; 6V, 0.04A amber type LS5C/A-6V, 30p; 6V 0.04A clear type LS5C/C-6V, 30p; 6V 0.04A green type LS5C/G-6V, 30p; 12V 0.04A LS5C/R-12V, 34p; 34V 0.04A LS5C/R-28V, 45p.

### SIEMENS 5% TOLERANCE POLYCARBONATE CAPACITORS

250V up to 0.1mF: 100V 0.1mF and above  
0.01, 0.012, 0.015, 0.018, 0.022, 0.027 5p  
0.033, 0.039, 0.047, 0.056, 0.068, 0.082, 0.1, 0.12, 0.15, 0.18, 0.22 6p  
0.27, 7p; 0.33, 9p; 0.39, 9p; 0.47, 10p; 0.56, 13p; 0.68, 15p.

#### DIN CONNECTORS

Loudspeaker	2-pole	plug	socket
Audio	3-pole	13p	10p
Audio	4-pole	14p	12p
Audio	5-pole 180deg.	15p	12p
Audio	5-pole 240deg.	15p	12p
Audio	6-pole	15p	13p

### HAD YOUR COPY YET? ELECTROVALUE CATALOGUE

64 pages plus covers. Thousands of items plus classified information and illustrations. Post free **10p**

### RESISTORS

Code	Power	Tolerance	Range	Values available	1 to 9	10 to 99	100 up
C	1/20W	5%	82 $\Omega$ -220K $\Omega$	E12	9	8	7
C	1/8W	5%	4.7 $\Omega$ -470K $\Omega$	E24	1	0.8	0.7
C	1/4W	10%	4.7 $\Omega$ -10M $\Omega$	E12	1	0.8	0.7
C	1/2W	5%	4.7 $\Omega$ -10M $\Omega$	E24	1-2	1	0.9
CO	1W	10%	4.7 $\Omega$ -10M $\Omega$	E12	2-5	2	1.9
WW	1/2W	2%	10 $\Omega$ -1M $\Omega$	E24	4	3-5	3
WW	1W	10% $\pm$ 1/20 $\Omega$	0.22 $\Omega$ -3.9 $\Omega$	E12	7	7	6
WW	3W	5%	12 $\Omega$ -10K $\Omega$	E12	7	7	6
WW	7W	5%	12 $\Omega$ -10K $\Omega$	E12	9	9	8

Codes: C=carbon film, high stability, low noise.  
MO=metal oxide, Electrofil TR5, ultra low noise.  
WW=wire wound, Plessey.

Values:  
E12 denotes series: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.  
E24 denotes series: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

**ZENER DIODES** 5% full range E24 values: 400mV: 2.7V to 30V, 15p each; 1W: 6.8V to 82V, 27p each; 1.5W: 4.7V to 75V, 60p each.  
Clip to increase 1.5W rating to 3 watts (type 266F), 4p.

**CARBON TRACK POTENTIOMETERS**, long spindles. Double wiper ensures minimum noise level.

Single gang linear 100 $\Omega$  to 2.2M $\Omega$ , 12p; Single gang log, 4.7K $\Omega$  to 2.2M $\Omega$ , 12p; Dual gang linear 4.7K $\Omega$  to 2.2M $\Omega$ , 42p; Dual gang log, 4.7K $\Omega$  to 2.2M $\Omega$ , 42p; Log/antilog, 10K, 47K, 1M $\Omega$  only 42p; Dual antilog, 10K only, 42p. Any type with  $\frac{1}{2}$ A D.P. mains switch, 12p extra.  
Only decades of 10, 22 and 47 available in ranges quoted.

#### CARBON SKELETON PRE-SETS

Small high quality, type PR, linear only: 100 $\Omega$ , 220 $\Omega$ , 470 $\Omega$ , 1K, 2K, 4K7, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M2, 4M7, 10M $\Omega$ . Vertical or horizontal mounting, 5p each.

**COLVERN** 3 watt Wire-wound Potentiometers. 100 $\Omega$ , 15 $\Omega$ , 25 $\Omega$ , 50 $\Omega$ , 100 $\Omega$ , 150 $\Omega$ , 250 $\Omega$ , 500 $\Omega$ , 1K, 1.5K, 2.5K, 5K, 10K, 15K, 25K, 50K, 32p each.

Handbook of transistor equivalent and substitutes, 40p. (Postage 3p if ordered alone).

Prices are in pence each for quantities of the same ohmic value and power rating, NOT mixed values. Ignore fractions on total value of resistor order.)

**MULLARD polyester C280 series**  
250V 20%: 0.01, 0.022, 0.033, 0.047 3p each; 0.068, 0.1, 4p each; 0.15, 4p; 0.22, 5p; 10%: 0.33, 7p; 0.47, 8p; 0.68, 11p; 1 $\mu$ F, 14p; 1.5 $\mu$ F, 21p; 2.2 $\mu$ F, 24p.

**MULLARD SUB-MIN. ELECTROLYTICS**  
C246 range, axial lead 6p each  
Values ( $\mu$ FV): 0.64/64; 1/40; 1.6/25; 2.5/16; 2.5/64; 4/10; 4/40; 5/64; 6.4/16; 6.4/25; 8/4; 8/40; 10/2.5; 10/16; 10/64; 12.5/25; 16/40; 20/16; 20/64; 25/6.4; 25/25; 32/4; 32/10; 32/40; 32/64; 40/16; 40/2.5; 50/6.4; 50/25; 50/40; 64/4; 64/10; 80/2.5; 80/16; 80/25; 100/6.4; 125/4; 125/10; 125/16; 160/2.5; 200/6.4; 200/10; 250/4; 320/2.5; 320/6.4; 400/4; 500/2.5.

**LARGE CAPACITORS**  
High ripple current types: 1000/25, 28p; 1000/50, 41p; 1000/100, 82p; 2000/25, 37p; 2000/50, 57p; 2000/100, £1.44; 2500/64, 77p; 2500/70, 98p; 5000/25, 62p; 5000/50, £1.10; 5000/100, £2.91; 10000/50, £2.40.

● ● ● COMPONENT DISCOUNTS  
10% on orders for components for £5 or more.  
15% on orders for components for £15 or more.  
(No discount on nett items.)

**POSTAGE AND PACKING**  
Free on orders over £2. Please add 10p if orders under £2.

Overseas orders welcome: carriage and insurance charged at cost. Prices subject to alteration without notice.

**U.S.A. CUSTOMERS**  
U.S.A. orders charged at special prices as advertised by ELECTROVALUE AMERICA, P.O. Box 27, Swarthmore, PA 19081.

**ELECTROVALUE** DEPT. P.E.1271, 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY  
Hours: 9-5.30, 1.0 p.m. Saturdays. Phone: Egham 5533 (STD 0784-3) Telex 264475

# CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER  
DEPT.  
No. 11  
MAYES RD.  
LONDON  
N22  
6TL

**COMPONENTS AND HI FI  
FOR THE HOME CONSTRUCTOR**  
OUR SHOPS ARE OPEN ALL DAY  
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY  
(WE CLOSE ALL DAY THURSDAY)  
13 SOUTH MALL, EDMONTON, N.9 803 1685

**"CRESCENT" D.J. PARTY AMPLIFIER "P100"**  
A completely new style 100W Amplifier especially designed for the D.J. who expects his equipment to look and sound really good, and still keep a moderate price:  
10-30,000Hz response.  
All loudspeaker systems suitable.  
Full output into 4 ohm.

All silicon transistors. F.E.T. at front end. Real value at **£42** plus £1 P. & P. and insurance.

★ **£2 DISCOUNT** ★

If purchased at the same time as the **Psychedelic Light Control Unit**. If you require more information please send a S.A.E.

### STEREO HEADSET

8 ohm impedance, complete with plug and 5ft lead. A very comfortable phone set. Listen to stereo without noise interrupting the pleasure. Wonderful value. **£2-50** plus 10p P. & P.



### MINI LOUDSPEAKERS


2 1/2in 8 ohm = 33p | 2 1/2in 25 ohm = 33p  
3in 8 ohm = 40p | 2 1/2in 75 ohm = 38p  
Plus 3p P. & P. on each Speaker

### LOW VOLTAGE AMPLIFIER

Few only at **£1-75** plus 18p P. & P.

5 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.

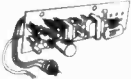With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



**EMI LOUDSPEAKER 450**  
10W 13in x 8in ± two 2-2in tweeters and cross-over. All wired and ready for use. This ever-popular 450 in 3-8-15 ohm imp.  
**£3-50** plus 38p P. & P. each.

### PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass-Middle-Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed)  
**£18-50** plus 38p P. & P.

If you require more information please send S.A.E.

**CHROME TV STAND**  
28in 8 1/2in 16in high. This modern design TV stand would make an ideal base for a coffee table and is a bargain at:  
**£1-63** plus 25p P. & P.



**LEGS**  
15 1/2in high, 7 1/2in wide at top, 13in wide at bottom. In modern matt black finish, ideal for all types of cabinets, loudspeaker plinth, record player, etc.  
**75p** per pair plus 15p P. & P.

**CRESCENT CASSETTES**  
Top quality cassettes at unbeatable prices (complete with standard storage case): C50 38p, C90 63p, C120 88p plus 5p P. & P.

**HIGH QUALITY IMPORTED HEADPHONES**  
1,000 Ω per phone ..... **80p** TTC  
2,000 Ω per phone ..... **88p** G1105  
Plus 10 P. & P. per pair.

### EA1000 3 WATT AUDIO AMPLIFIER MODULE

An Audio Amplifier designed around the TAA821 Linear I.C. —  
Supply Voltage ..... 9-24V  
Speaker Imp. .... 8-16 ohm  
Frequency ..... 30Hz-25kHz  
Overall Size ..... 2in x 3in x 1/2in  
Ideal Amplifier for radios, record players, stereo units, etc.  
Full technical data and diagrams with each module. All guaranteed and a bargain at



### BRIGHTNESS CONTROL

Full control over 300 watts of incandescent lighting. Thyristor light dimmer mounted on a standard switch block ready to fit into a M.K. Box. Enjoy the pleasure of having the precise amount of light you require at any time.  
Our Price **£2-75** plus 8p P. & P. each.



### BATTERY ELIMINATOR

Plug your Transistor Radio, Amplifier, Cassette, etc., into the a.c. mains through this compact eliminator. 2 1/2in x 2in x 3in approx.  
**£1-50**, 6V **£1-50**, 9V **£1-50**, 7 1/2V complete with cable and plug for Philips Cassette.  
**£2** plus 8p P. & P. each.



### SMC101 MAGNETIC STEREO CARTRIDGE

A fine quality cartridge, standard fixing. Complete with fixing kit and full specifications. Frequency response: 20-20,000Hz. Output: 5mV at 1000Hz. Tracking pressure: 3-5 grams. Stylus: 0-7 mil. diamond. Bargain price: **£4-75**  
Sonotone 9TAVC  
**£2-38**. Please include 10p P. & P. on each cartridge.



**£2-63** + 5p P. & P.

# YOURS FREE FOR 7 DAYS

## The 'New Picture-Book' way of learning **BASIC ELECTRICITY (5 VOLS.)** **BASIC ELECTRONICS (6 VOLS.)**

You'll find it easy to learn with this outstandingly successful **NEW PICTORIAL METHOD**—the essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate, cartoon-type drawing. The books are based on

the latest research into simplified learning techniques. This has proved that the **PICTORIAL APPROACH** to learning is the quickest and soundest way of gaining mastery over these subjects.

TO TRY IT, IS TO PROVE IT



The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

### WHAT READERS SAY

#### "EXCELLENT PUBLICATION"

"Thank you for the excellent publication: the best in form and type I have ever come across."

T.L.O., Shanklin

#### "READABLE AND INTERESTING"

"The Manuals are so readable and interesting that I do not think this magazine does full justice to the wonderful contents."

S.T.P., Bangor

#### "REAL HELP"

"I find the Basic Manuals the best in their class and a real help in my work in phototype electronics."

C.L.P., Cardiff

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT BR2 7HP  
Please send me WITHOUT OBLIGATION TO PURCHASE, one of the above sets on 7 DAYS FREE TRIAL, I will either return set, carriage paid, in good condition within 7 days or send the following amounts. **BASIC ELECTRICITY £4-50**. Cash Price on Down Payment of £1 followed by 4 fortnightly payments of £1 each (Total £5). **BASIC ELECTRONICS £5-40**. Cash Price or Down Payment of £1 followed by 5 fortnightly payments of £1 each (Total £6). This offer applies to UNITED KINGDOM ONLY. Overseas customers cash with order, prices as above.

Tick Set required (Only one set allowed on free trial)


**BASIC ELECTRICITY**  **BASIC ELECTRONICS**

Prices include Postage and Packing.

Signature .....  
(If under 18 signature required of parent or guardian)

NAME .....  
BLOCK LETTERS  
FULL POSTAL ADDRESS .....

**POST NOW FOR THIS OFFER !!**

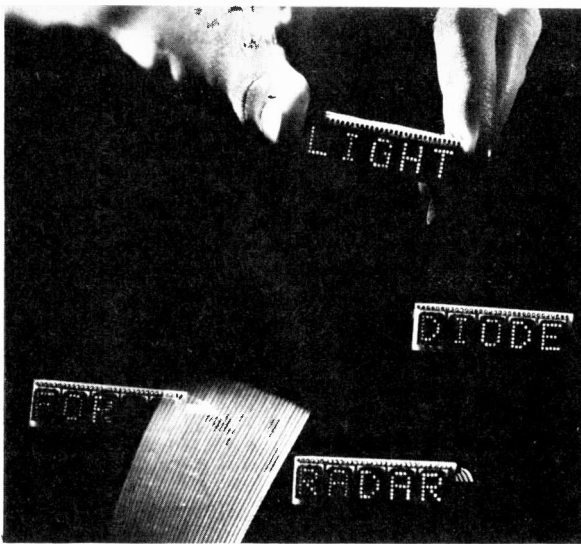

**A data display developed by Marconi.** *Tiny slices of glass ceramic each carry a  $7 \times 5$  matrix of gallium arsenide phosphide light emitting diodes; can be switched on to provide a pattern of high contrast letters, numbers, or symbols. The complete five letter words shown occupies only 32.5mm by 8.5mm*

The crystal systems  $\text{In}_x\text{Ga}_{1-x}\text{P}$  and  $\text{In}_x\text{Al}_{1-x}\text{P}$  are the most promising materials as yet investigated as they can provide direct energy gaps of the order of 2.2eV. These materials are exceptionally difficult to grow, however, and while InP-GaP can be grown to the right composition, InP-AlP has not yet been produced.

Even if these materials were available, they only give green, what do we do to obtain blue? At this stage we enter the realms of conjecture, the nitrogen III-V compounds, largely unknown, appear to hold out some promise although they have a different crystal structure to all of the other semiconductors mentioned here. Aluminium nitride and gallium nitride appear to be the favourites for investigation.

#### FOR THE FUTURE

With their limitations therefore, both crystal lamps and EL panels are working propositions. The red crystal lamp is quite well established and will undoubtedly become a part of the vast range of common semiconducting devices, but the EL panel is held up by one snag—its short working lifetime. This is caused by impurities slowly diffusing into the luminescent material and is a major problem, which until it can be overcome, will limit its usefulness seriously.

The "flat" television screen seems to be a very long term project indeed. A panel's electrodes can be patterned so that any particular part of the screen may be addressed in a similar manner to a computer memory matrix, but the definition possible by this method is severely limited and in any case only one colour is possible.

When green and blue crystal lamps are available perhaps this will provide the answer, but the inter-connection problems with such a vast number of individual elements is enough to make even the bravest engineer apprehensive.

However, these problems are not insurmountable since the Sony Corporation have shown, by presenting full colour TV on a large screen consisting of a vast array of red, green and blue light bulbs. It remains therefore to obtain the devices and then await the consequences.



## PHOTO-PRINT PROCESS CONTROL UNIT...

If you do your own photo printing; in colour or monochrome, this three-in-one unit will go a long way towards ensuring reliable results. It combines the assessment of tonal balance with stabilised lamp voltage and accurate timing to produce first-class prints from your best negatives

## I.C. AUDIO MIXER

Any easy-to-build three channel mixer that combines microphone or tuner inputs into a single channel. Ideal for multiple recording on a single tape recorder track

## PART 2 LOGICAL RADIO CONTROL

Further details on making two more coders and a decoder

**ALL INCLUDED IN THE  
JANUARY ISSUE OF**

**PRACTICAL  
ELECTRONICS**

**PLUS ALL THE  
REGULAR FEATURES!**

**ON SALE FRIDAY, DECEMBER 10**

In this the second and final part, constructional details for the electronic ignition system are given together with installation instructions and testing procedures, for both positive and negative earth cars.

## CONSTRUCTION

The prototype system was housed in a  $7\frac{1}{4}$ in  $\times$   $4\frac{1}{2}$ in  $\times$  2in Eddystone die-cast box. All the components are mounted on the printed circuit board (Fig. 11) with the exception of the transformer, TR4, TR5 and the thyristor. These are bolted to the case which acts as a heatsink.

## PRINTED CIRCUIT BOARD

It is strongly recommended that turret tags be used to make connection to the printed circuit board and these should be inserted and soldered before any of the components are mounted. Fig. 12 shows the component locations.

## INVERTER TRANSFORMER

The inverter transformer T1 is wound on a Mul-lard FX2243 pot core with a DT2206 bobbin and should preferably be impregnated when finished to keep out moisture which could cause leakage or damage to the windings of the transformer.

The first job is to wind on 400 turns of 34 s.w.g. enamelled wire in eight neat layers of fifty turns, with thin insulation between each layer. Take great care not to cross adjacent turns. This high voltage winding is now insulated from the others with about four layers of insulation tape.

Now wind on 12 turns of 20 s.w.g. bifilar (i.e. two wires wound together) in two layers, and lastly the three turns of 30 s.w.g. bifilar feedback winding. The wires should be colour coded with sleeves as shown in Fig. 13 and another layer of insulation tape wrapped around the bobbin. Try to ensure that the sleeves go as far as possible into the bobbin so that when it is placed inside the ferrite cups the enamel insulation is not scratched by the core.

If the core cannot be impregnated then it is recommended that the faces are firmly joined with a thin layer of Araldite or the transformer may shriek objectionably. This does not happen of course if the transformer is impregnated.

The reliability of the whole system depends on the care with which the transformer is made.


## UNIT ASSEMBLY

The box should be drilled as shown in Fig. 14 and the holes deburred with larger drills, taking care to remove any roughness where the mica washers are to be placed for TR4, TR5 and the thyristor.

All the components can now be assembled in the box ready for the final wiring. Cadmium plated nuts and bolts should be used, with the exception of the bolt securing the thyristor, since steel ones will soon rust.

Interwiring details for the ignition system are given in Fig. 15.

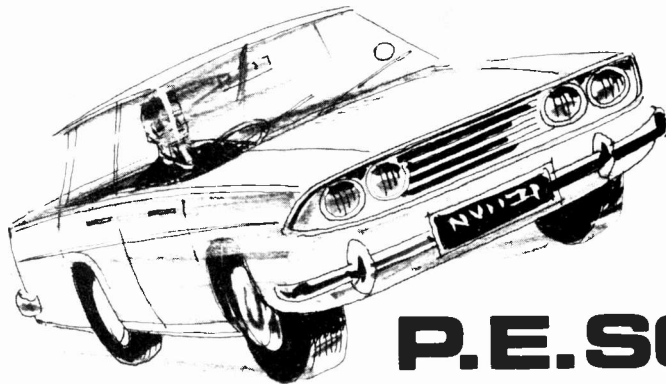The thyristor should be mounted with a nylon bolt to remove the possibility of any flash over at this point due to the high voltages. The transistors



# P.E. SCORPIO CAR IGNITION

By **D. S. GIBBS** and **I. M. SHAW** (Ferranti Ltd)



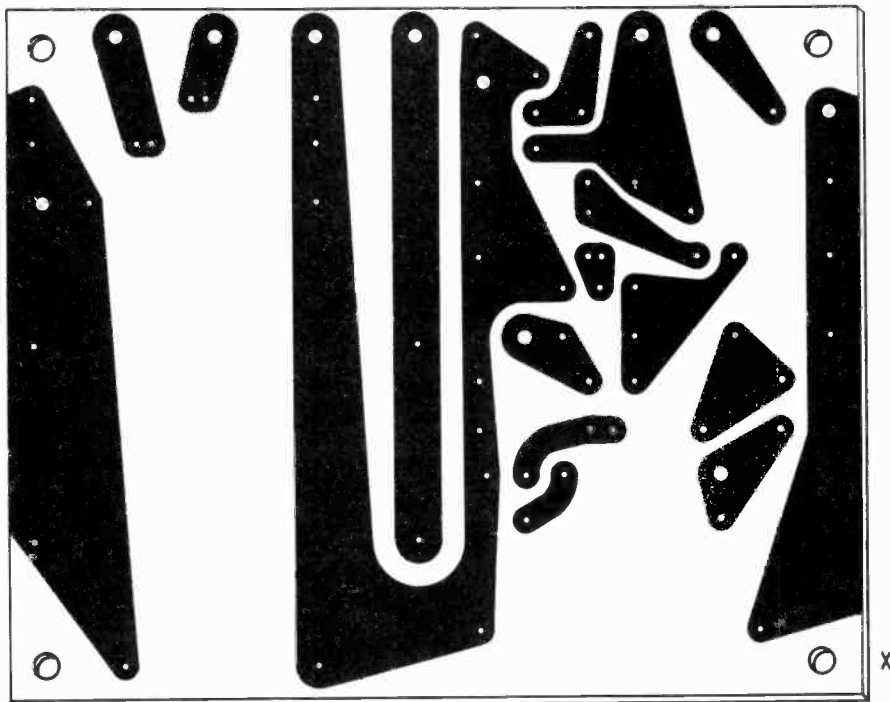


Fig. 11. Printed circuit board for ignition system, shown full size

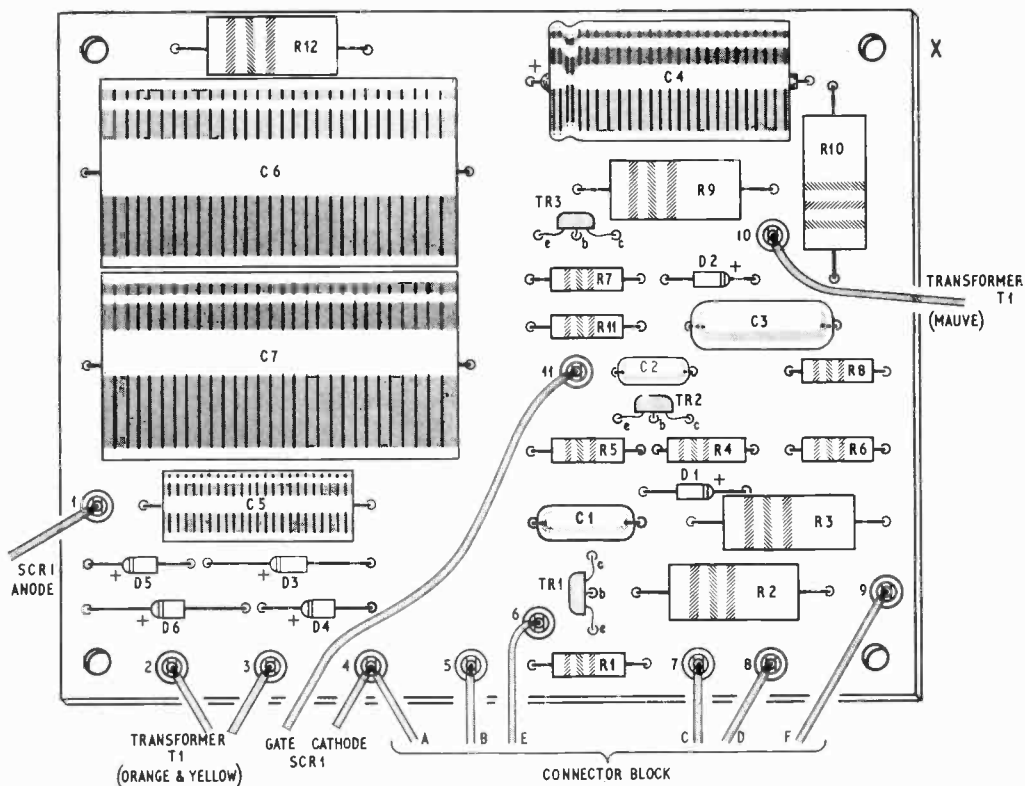


Fig. 12. Component layout and wiring for printed circuit board

... reliability depends on careful transformer construction

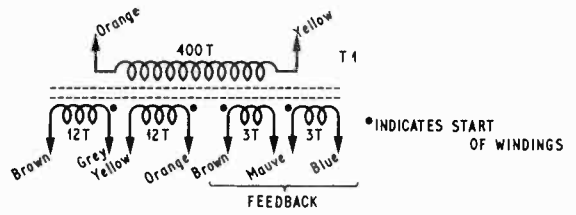


Fig. 13. Winding details, for inverter transformer

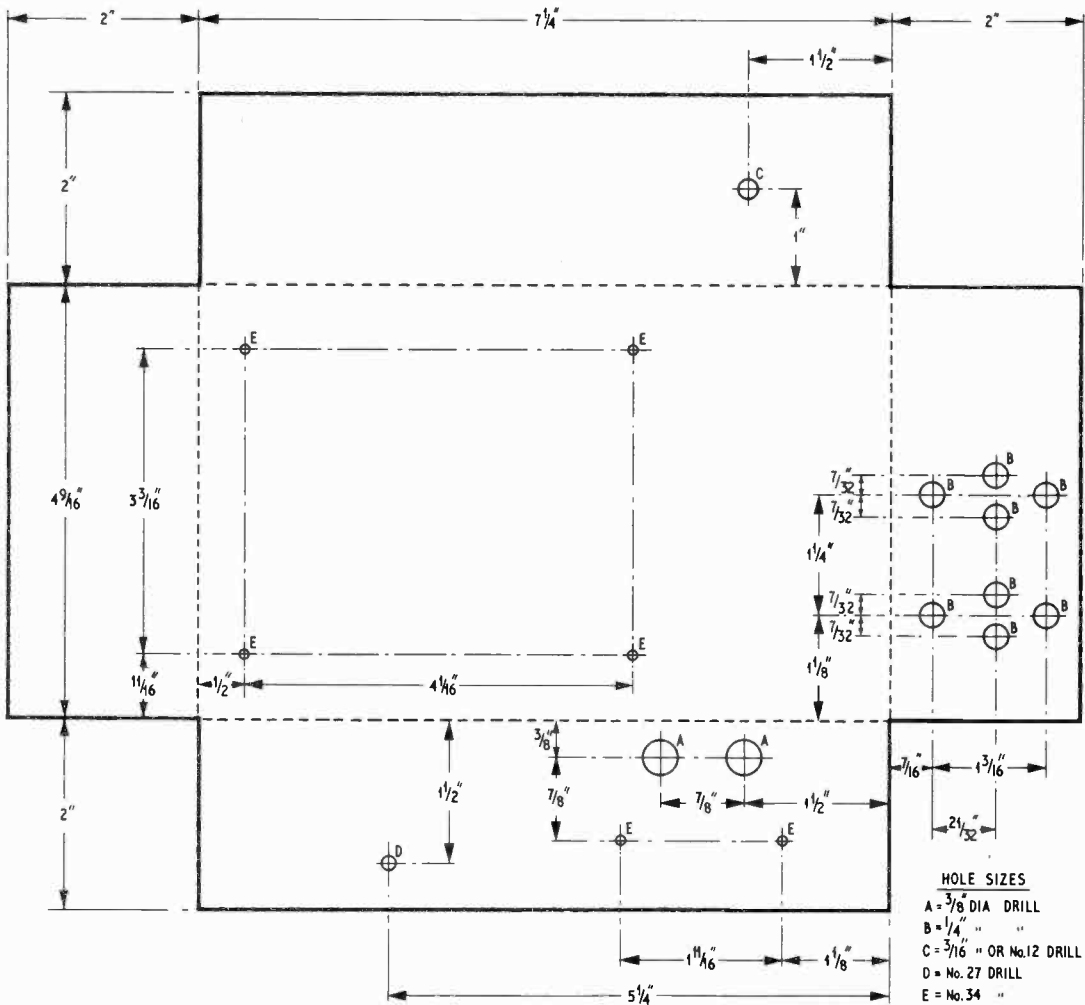


Fig. 14. Drilling details for die-cast box

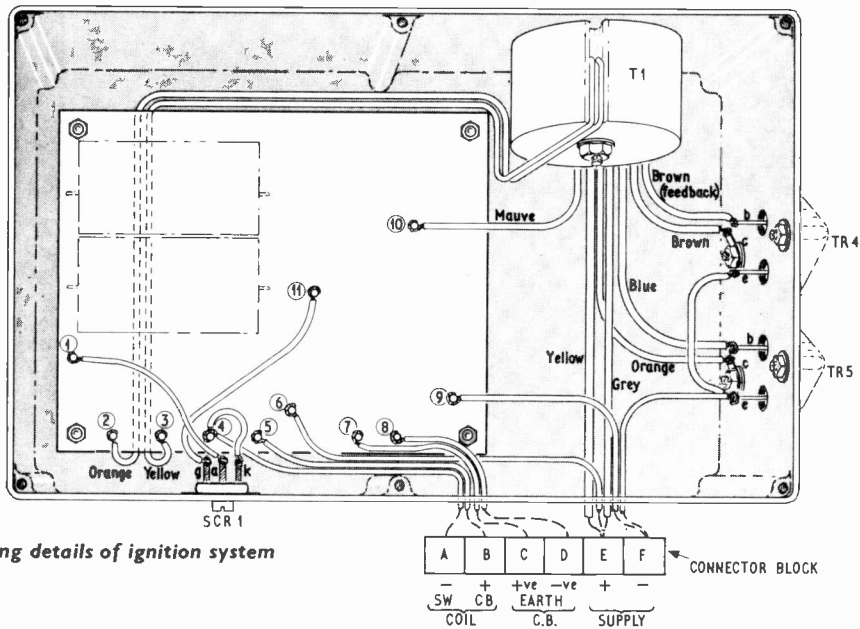
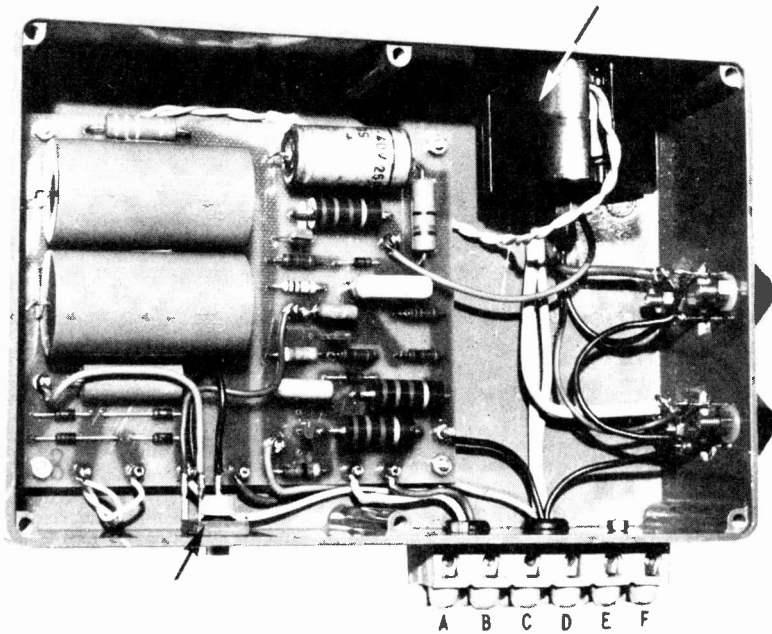


Fig 15. Interwiring details of ignition system


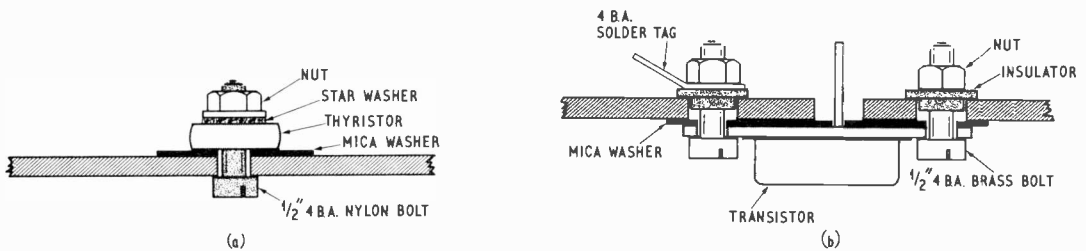


Fig 16. (a) Mounting details for thyristor. (b) mounting details for inverter transistors

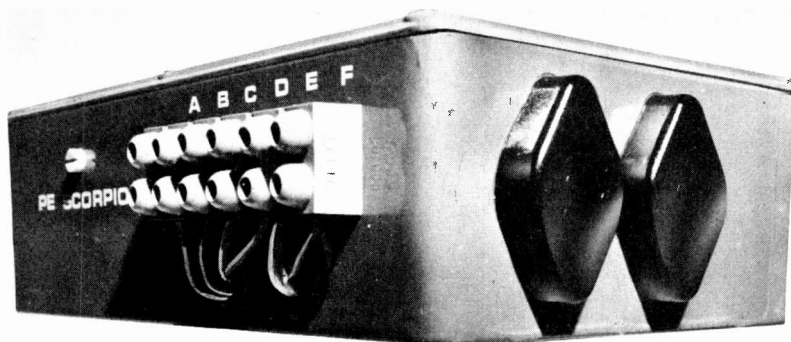

Plastic covers are fitted over the inverter transistors to prevent accidental short circuits

TR4 and TR5, and the thyristor, must be mounted on mica insulating washers as indicated in Fig. 16 with solder tags on the lower two transistor fixing screws for the collector connections. Plastic covers should be fixed to the transistors to prevent accidental short circuits when the unit is installed in the car.

The printed circuit board is mounted on spacers of about  $\frac{1}{4}$  in length. Use a spring washer between the transformer mounting bolt and the core so that the transformer can be secured firmly without danger of cracking the ferrite core.

The unit can now be wired with 14/0076 wire in assorted colours for identification. Care must be taken to connect the transformer windings correctly or the inverter will not oscillate.

The wires to the six-way connector block are brought out via two grommets just below it.

### CHECKING THE UNIT

After checking the wiring carefully some simple checks should be performed before installation, if the constructor does not have facilities to fully test the operation of the unit.

If the construction has been carried out as described using only good quality components the only check necessary is that the inverter transformer windings have been correctly connected and that it delivers the correct output voltage.

To do this connect the car battery between (E) and (F) on the connector block. The transformer should be heard to "sing" immediately and approximately 500 volts d.c. can be measured between tags 1 and 4 on the printed circuit board (positive on tag 1). If this is not correct then the phases of the transformer windings will have to be examined and corrected before installation.

The current taken from the battery is approximately 500mA when the inverter is operating correctly.

### INSTALLATION

All connections from the car for both positive and negative earth are made to the connector block, but since there are some differences they will be explained separately.

First, a suitable place in the engine compartment should be found to mount the unit so that the wires can be cut to the correct lengths. In both systems the wire connecting the ignition coil to the contact breaker must be removed but kept, so that the car can be reconstructed to the conventional system if necessary at any time.

### POSITIVE EARTH CARS

The wire or wires connected to the SW or negative terminal of the ignition coil for positive earth systems, must be connected instead to the negative supply input to the unit (F) since this supply is via the ignition switch.

The two connections between the unit and the coil are made next; SW or negative to (A) and CB or positive to (B). These must be the only connections to the coil terminals.

The contact breaker is connected to (C) and good earth from the car chassis or positive battery terminal to (E). There are a total of five wires to the unit for positive earth cars with contact (D) left disconnected.

### NEGATIVE EARTH CARS

The connections for negative earth cars are somewhat simpler since the wires to the positive terminal of the coil can be left connected and the positive supply terminal of the unit (E) connected to it.

The contact breaker is connected to (D) and the negative coil terminal to (B). Contact (F) is earthed making a total of four wires to the unit with contacts (A) and (C) left unconnected.

The astute reader will deduce that the first half cycle of the spark in the negative earth system is positive and not negative as is usually recommended. This can be corrected by reversing the connections to the coil. In some cases this may be inconvenient as the positive terminal is sometimes used as a junction point for leads from other equipment and the coil is supplied with more than one tag on the positive side to accommodate them. It is not really necessary to go to the trouble of reversing the initial spark polarity since the unit generates a dual polarity spark (Fig. 6a, Part One).

The unit can now be fitted to a convenient place in the engine compartment by drilling at least two suitable holes in the bottom of the box, and the car, and screwing the unit in place with self tapping screws.

### COLD START COILS

Some cars are fitted with a "cold start" coil, which is a low voltage coil with a series ballast resistor that is shorted out when starting, to give an increased spark voltage under cold starting conditions. The ballast resistor is usually attached to one of the terminals of the coil but it may take the form of a resistance cable between the ignition switch and the coil.

**. . . . never attempt to remove spark plug leads while engine is running**

It does not actually make any significant difference to the spark produced by the unit whether the resistor is left in series with the coil or not, but the resistance cable should not be used to supply power to the unit as there will be a considerable loss of voltage along it. In this case it is best to remove the resistance cable and replace it with a length of wire. In all cases the connection between the coil and the starter solenoid *must* be removed.

## PRECAUTIONS

Because of the high open circuit voltage produced by this unit *never* attempt to remove the spark plug leads whilst the engine is running, since not only is there a danger of breaking down the insulation of the coil but the experimenter stands a good chance of getting a nasty shock.

In addition the thyristor can be exposed to transient voltages of up to 1,000V under these conditions and may be destroyed.

## PERFORMANCE

In most capacitor discharge ignition systems the usual fault is for the thyristor to "latch on" with the short circuit current available from the inverter, especially when an iron cored transformer is used. This cannot occur in the system described here as explained in Part One.


The spark gap of the plugs may be increased with advantage for smoother idling, but not above 0.04in or the insulation of the ignition coil will be unduly taxed, especially in cars with high compression engines ( $> 10:1$ ).

The unit will perform satisfactorily down to at least 8 volts thus giving a good spark at the plugs even under very cold starting conditions when the battery is at its lowest capacity.

The points and timing should be checked when installing the unit since from now on they can be left for many thousands of miles. Cars fitted with this unit can be expected to operate more economically since the car is kept in "peak tune" all the time. This is because the points do not wear and the timing and dwell angle do not change with time, except for the very slight wear on the heel of the contact breaker.

Four units as described in this article have been built and tested in various types of British car under different driving conditions and it can be stated that "P.E. Scorpio" is without doubt an effective transistor ignition system achieving improved performance.

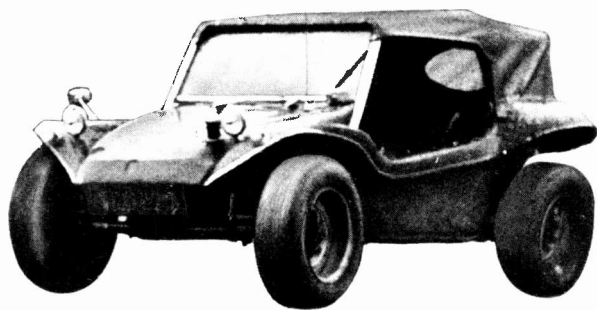Brake horse power has been measured on a "rolling road" and has shown to be about 5 per cent higher with a subsequent improvement in the "liveliness" of the car. One particular feature is the more consistent performance of the car after tuning has occurred from thousands of miles of driving. ★



# LOGICAL RADIO CONTROL

continued from page 985

## TIMING COMPONENTS

The interval timing resistors R1 to R5 have a maximum value of approximately 490 ohms due to the input threshold of the gates; lower values may be used with a corresponding change (increase) in the capacitors C2, C4, C6, C8, C10 but the CR product must remain the same.

The signal pulse timing potentiometers VR1 to VR6 will provide a maximum and minimum value. The minimum value of approximately 200 ohms corresponding to a pulse length of approximately 0.5ms and the point at which the following gate will just open. The maximum value is given as 1.2 kilohms. With 10 $\mu$ F capacitors for C3, C5, C7, C9, C11, a pulse of 2ms will be given, while 800 ohms setting for the potentiometers will provide 6ms pulses.

The recommended arrangement is 240 $\Omega$  in series with a 500 $\Omega$  potentiometer to ground. The cycle time is derived from the trigger circuit (Fig. 5) in which TR1 and TR2 form a multivibrator, the period of which is approximately 1.4CR. If C12 is 1.5 $\mu$ F and R6 and R8 are both 15 kilohms, the pulse time will be approximately 18ms (Fig. 6).

The positive going edges at the collector of TR1 are slowed by the action of the timing capacitors, so the output is taken from TR2. Diode D1 and R10 form an isolation circuit so that C13 will not discharge through the trigger circuit. The output waveform is differentiated by C14 and R11 to give a positive pulse of time constant approximately 0.3ms (Fig. 6c). The trigger transistor TR3 switches off producing the sharp-edged negative going pulse (Fig. 6d) to the trigger output every 36ms.

## LAYOUT

Fig. 7 shows the printed circuit layout full size; it is recommended that extra space along one side is provided for mounting purposes. All holes should be drilled clean and vertical from the copper side with an HSS or tungsten carbide number 58 drill, and a small clean tipped soldering iron used.

Fig. 8 shows component layout, the i.c.s being inserted and soldered in first, followed by the fixed resistors and capacitors. Using thin flexible covered wire the four final interconnections to IC7 should be made as shown in Fig. 9, together with the trigger connections, supply leads and six various coloured wire leads which go to the control panel for connection to VR1 to VR6.

**Next month: Two more coders and a decoder**


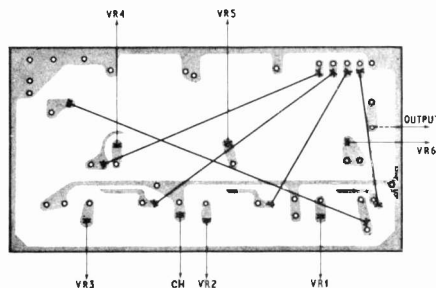


Fig. 9. Potentiometer connections to Coder 1

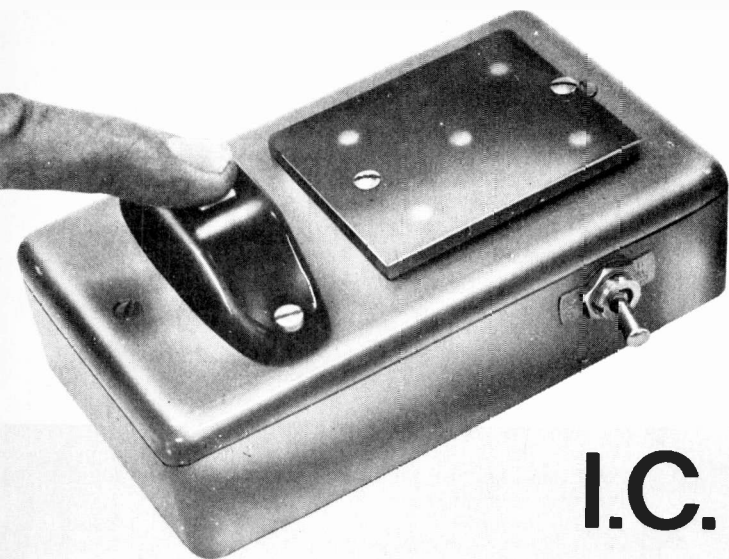

BY J. D. CROFT

# I.C. DIGITAL DICE

**T**HIS circuit is a revised version of the circuit published in "Ingenuity Unlimited," April 1971, now using integrated circuits.

When re-designing the circuit to use integrated circuits it was found that not only is the finished dice smaller and neater, but by using the low price i.c.s. now available, it is also cheaper to build.

## THEORY

The logic diagram of this dice is shown in Fig. 1.

The circuit is basically a divide-by-six counter driven via the control gate G11 by a 4.8kHz clock pulse.

The count is stopped by the control gate when the player presses the play button, and the binary output of the counter is decoded by gates one to nine to light lamps LP1-LP7 set in the usual dice pattern.

The binary output is decoded into four lamp outputs, the first of which decides "even or odd." If the count is odd, the centre lamp, LP3, lights. Next, gate G1 decides "NOT 1" which lights two diagonally opposite lamps LP6 and LP7—except during a "1."

A third gated output, gates G5, G6 and G7 decide 4, 5, or 6 and lights the two remaining diagonally opposite lamps, LP4 and LP5 on these counts. The last output, gates G8 and G9, decide "6" and lights the two remaining lamps on this count. A little thought will show that these combinations will automatically light the correct number of bulbs in the correct patten for each dice position.

Player intervention is prevented in two ways. Firstly, by extinguishing the display lights while the counter is operating, and secondly, by the high clock pulse speed adopted which is far higher than any human reflex.

## CIRCUIT CONSTRUCTION

The circuit is built on a piece of Veroboard (0.1in matrix) as shown in Fig. 2. The board should be cut to size and some strips cut as shown in Fig. 3, before the integrated circuits are fitted.

It is recommended to leave the soldering of the i.c.s. until all the other components and straps have been fitted as it is almost impossible to remove them should they be soldered in the wrong position.

When soldering on 0.1in matrix Veroboard great care should be taken as the solder easily bridges the closely spaced strips, and if the strips are overheated they could come adrift from the laminate causing intermittent faults.

## COMPONENTS . . .

### Resistors

R1, R2, R3, R4 4.7k $\Omega$  (4 off)  
R5 47 $\Omega$   
R6 100 $\Omega$   
All 5%, 1/4W carbon

### Capacitors

C1, C2 0.1 $\mu$ F 15V (2 off)

### Semiconductors

TR1, TR2, TR3, TR4 2N3704 (4 off)  
D1, D2 OA91 (2 off)

### Integrated circuits

IC1, IC3, IC4 SN7400 (BPOO) Quad 2-input gates (3 off)  
IC2 SN7492 (BP92)  $\div$  12 counter  
IC5 SN7410 (BP10) triple 3-input gate

### Switches

S1 Single pole on/off toggle  
S2 Single pole push button

### Lamps

LP1-7. 6V 0.3W l.e.s. type (7 off)

### Miscellaneous

Lampholders for lamps (7 off)  
Veroboard, 2 1/2in  $\times$  2 1/2in (0.1in matrix)  
Battery 6V (4  $\times$  1.5V in series, type HP7)

### CASE

The dice case may be varied to suit individual requirements and materials available. The case in the suggested design is a standard M.E.M. plastics box for mounting a double mains socket, fitted with the appropriate blanking plate. This will make a neat, strong case, which will accommodate the circuit board and lamp display and also four pen-light cells in a four-cell battery holder.

If due to anticipated prolonged use a larger battery or 6V mains power unit is required, a larger case should be used which can be constructed from wood or Perspex.

The lamp display in the author's unit was wired for miniature 6V l.e.s. lamps and lampholders held in position by using stout copper wire, which acts as both support and electrical common positive bus bar. If required the lampholders could be secured in their correct position by using Araldite.

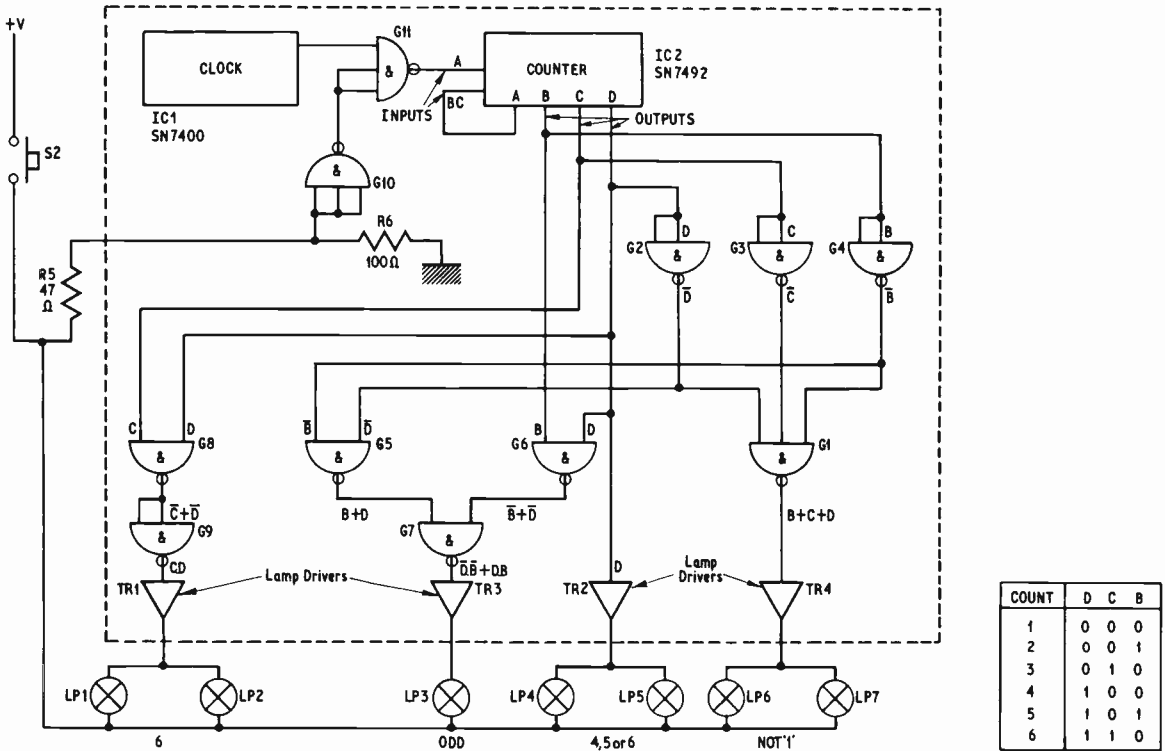


Fig. 1. Circuit diagram of the electronic dice with the logic gates "taken out" of the integrated circuit packs. Circuitry within the grey area is mounted on the 0.1in matrix Veroboard

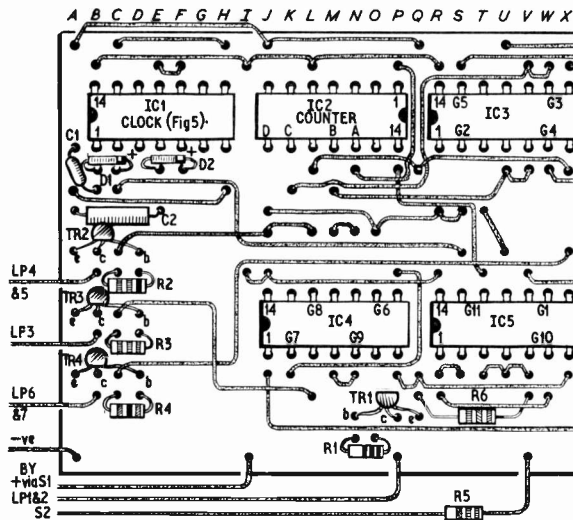


Fig. 2. Wiring and layout of the logic integrated circuits and lamp drivers

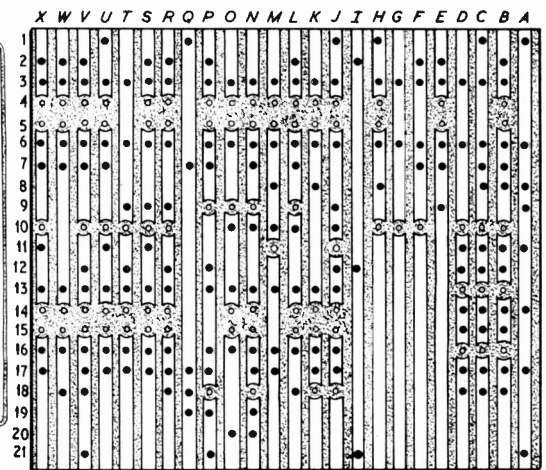


Fig. 3. View of the underside of the Veroboard showing the copper regions that must be removed

## DISPLAY PANEL

The holes for the display are covered by a piece of  $\frac{1}{4}$  in translucent Perspex to hide the non-illuminated holes.

This Perspex should be chosen with care, as some colours tend to diffuse the light spots making reading of the display panel difficult.

The Perspex may be selected by holding a sample against a piece of cardboard with a small hole in it and viewing it against background illumination to check that a clean-edged spot can be seen. A blue or violet Perspex was found to be best.

## CHECKING

After assembling the dice, the connections should be rechecked before fitting the batteries since a single wrong strap could easily permanently damage an integrated circuit.

If desired the correct working of the dice can be verified in the following manner.

## CLOCK CHECK

The clock output can be checked by connecting an oscilloscope between holes 8C and 8A on the Veroboard where a 4.8kHz square wave should be observed. In the absence of an

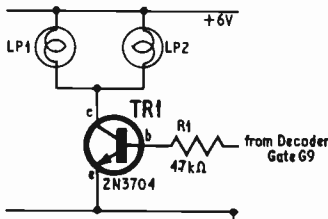


Fig. 4 (a). The lamp driver circuit that amplifies the output from the 4 decoders to light the lamps; (b) Pictorial view of the transistor used in this circuit showing base connections


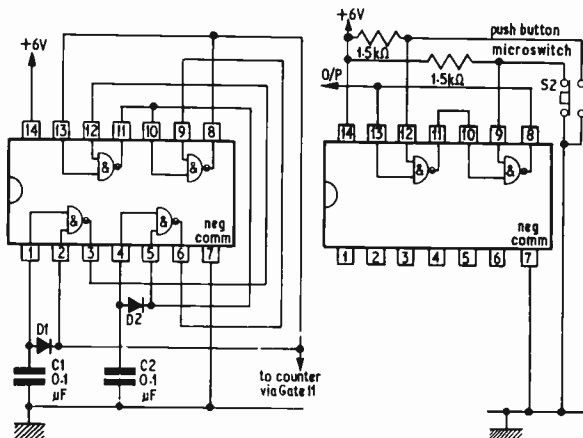


Fig. 5. Wiring of the SN7400N Quad 2-input nand gate to give a 4.8kHz multivibrator for use as clock

Fig. 6. Use of half a SN7400N to provide test input signals to the counter

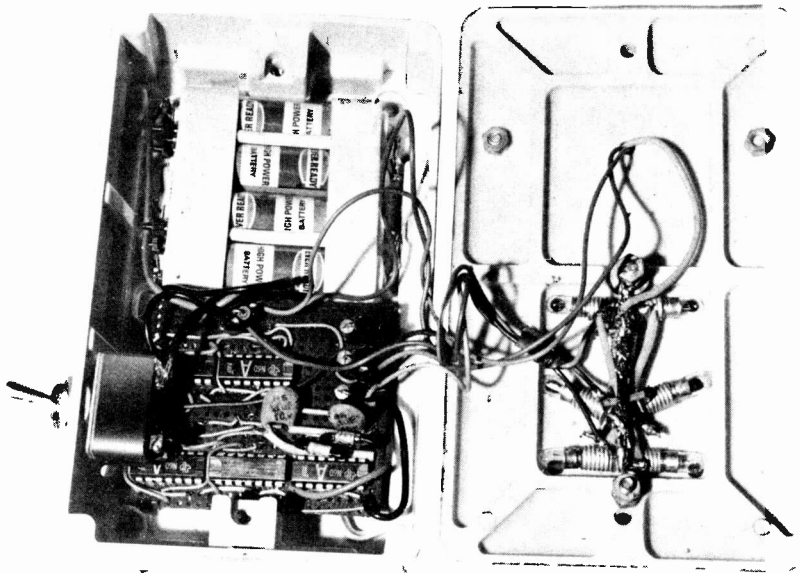

oscilloscope, a pair of high resistance headphones in series with an  $0.1\mu\text{F}$  capacitor may be used to detect the output from the clock which will be observed as a high pitch whistle.

## TESTING COUNTER AND DECODER

The counter and decoding gates may be checked by injecting test signals into the counter.

This is done by the use of a microswitch buffered by a bistable to remove switching transients. The bistable is constructed from half a SN7400N quad 2-input gate i.c. connected as shown in Fig. 8. This circuit is worth building as a permanent unit as it is invaluable in all testing work on TTL and DTL circuits.

The output from the bistable should be connected to hole 7P on the Veroboard with the wire to 13T temporarily removed. On operating the microswitch the display should be found to advance one count for every two depressions of the microswitch. The reason why two pulses are required to step the display by one count is that the SN7492N is a divide-by-twelve counter, and in the present application the "A" stage output is not used. The reset line of the counter SN7492N is disabled by applying a permanent "O" on pin 7 of the reset gate, which is the  $R_0$  gate in this package.

## SWITCHING TRANSIENTS

If any trouble is experienced due to an uneven count, noise on the supply line may be the cause, in which case this is rectified by connecting  $0.1\mu\text{F}$  capacitors between the negative and positive supply lines as near to the i.c.s as possible. This should remove the sharp fronts of any switching transients transmitted on to the supply lines.

This expedient should not be required if the unit is powered by batteries but may be required if the unit incorporates a mains power supply.

As the i.c.s are already working at 0.75 volts over the manufacturers' recommended working voltage, on no account must the supply voltage be raised above six volts.


Providing this value is not exceeded, no damage to the i.c.s should occur.







# I.L.P. (Electronics) Ltd

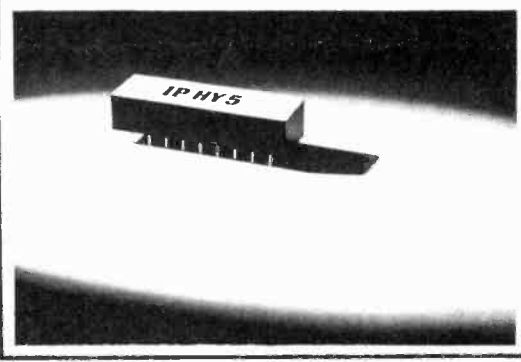

## HY40 IS POWER AMP PERFECTION

Lets face it — an immediate success, the HY40 is here to stay. HY40 means Hybrid Power, power neatly locked away inside an Integrated Circuit. Power the modern way, simply mount only five additional components on a printed circuit board (all of which are supplied with the HY40). Power not only for Hi-Fi, power for Groups, for public address, for industry, power for all.


### HY40 is HI-FI POWER ILP are POWER PROUD

In addition to the P.C. board and manual supplied with the HY40 we now include the five remaining components, at minimal cost, needed to complete the assembly of a High Performance Power Amplifier.

By merely combining two HY40s with a Stereo Preamplifier (2 x HY5) and simple Power Supply (PSU45), premium quality stereo may be obtained for a very modest outlay.

The free manual supplied with the HY40 gives clear, easy build instructions for Power Supply; volume, bass, treble and balance controls, together with inputs for Ceramic and Magnetic Pick-ups, Tape, Tuner and Auxiliary functions.

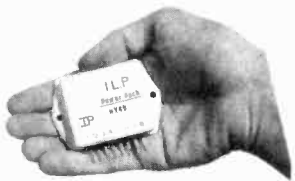Internally the HY40 is based on conventional and proven circuit techniques developed over recent years.



- OUTPUT POWER** British Rating 40 WATTS PEAK, 20 watts RMS continuous.
- LOAD IMPEDANCE** 4—16 ohms
- INPUT IMPEDANCE** 22Kohms at 1Khz.
- INPUT SENSITIVITY** 300 mV for maximum output.
- VOLTAGE GAIN** 30db at 1KHz.
- FREQUENCY RESPONSE** 5Hz-60KHz + 1db.
- TOTAL DISTORTION** less than 1% (typical 0.1%) at all output powers.
- SUPPLY VOLTAGE**  $\pm$  22.5 volts D.C.
- SUPPLY CURRENT** 0.8 amps maximum.
- PRICE:** including comprehensive manual, P.C. Board and FIVE EXTRA COMPONENTS.  
MONO £4-40 STEREO £8-80 all post free.

### A WORLDS FIRST TO JOIN THE WORLDS BEST

The HY5 is a unique and revolutionary concept in High-Fidelity pre-amplifiers. Thanks to the latest techniques, all feedback and equalization networks are, for the first time, combined into an integrated pre-amplifier circuit.

Simply by adding volume, treble, bass potentiometers and only three stabilizing capacitors, which are supplied, your HY5 is complete and ready for use.

The HY5 provides equalization for almost every conceivable input. This years developments in equalization technique enables precise correction for both output voltage and frequency response for any crystal or ceramic cartridge. Yet another feature of the HY5 is its inbuilt stabilization circuit, allowing it to be run off any unregulated power amplifier supply.

The HY5 contains a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo preamplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY40 and PSU45 forms a completely integrated system.

- INPUTS**  
Magnetic Pick-up (within  $\pm$ 1db RIAA curve) 2mV.  
Tape Replay (external components to suit head). 4mV.  
Microphone (flat) 10mV.  
Ceramic Pick-up (equalized and compensatable) 20 — 2000mV variable.  
Tuner (flat) 250mV.  
Auxiliary 1 250mV.  
Auxiliary 2 2—20mV.
- OUTPUTS**  
Main Pre-amp output 500mV.  
Direct tape output 120mV.
- ACTIVE TONE CONTROLS**  
Treble +12db.  
Bass +12db.

**INTERNAL STABILIZATION**  
Enables the HY5 to share an unregulated supply with the Power Amplifier.

**SUPPLY VOLTAGE**  
15—25 volt.


**SUPPLY CURRENT**  
5mA approx.

**OVERLOAD CAPABILITY**  
better than 28db on most sensitive input infinite on tuner and auxl.

**OUTPUT NOISE VOLTAGE**  
0.5mV.

**PRICE**  
Mono £3-60 Stereo £7-20

### POWER SUPPLY PSU45

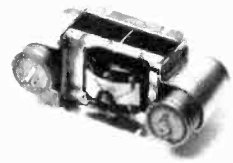

The PSU45 is specifically designed to supply, simultaneously, your HY40 (in mono or stereo format) and one or two HY5s.

Spec.


PSU45  $\pm$  22.5 volts, 2 amps simultaneously.

**PRICE:** £4-50 including Postage and Packing

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT  
TELEPHONE: CANTERBURY 63218

# Toshiba

**20 WATT  
Amplifier  
KITS**

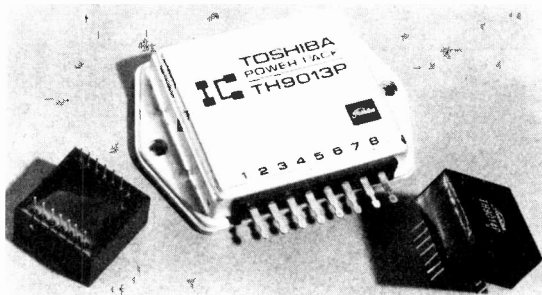

**Toshiba** —TH9013P 20 watt  
Hi-Fi Power Amplifier **£4.57** each.

**Toshiba** —TH9014P. Pre-Amplifier. Voltage gain 75dB (typical). Output noise voltage 0.1 mV (typical) **£1.50** each.

## SPECIAL OFFER

COMPLETE KIT OF ALL RESISTORS, CAPACITORS, AND POTENTIOMETERS (GANGED FOR STEREO) TO MANUFACTURERS' CIRCUIT, WHEN ORDERED WITH AMPLIFIER AND PRE-AMPLIFIER AS ABOVE.

**STEREO — £6.95**

All prices include full post and packing charges (UK only).

Send s.a.e. for full manufacturers' data

**TOO LATE TO GO TO PRESS**  
P.C. Board now available

# Hawnt

OFFICIALLY APPOINTED DISTRIBUTORS FOR  
ERIE, MULLARD, Etc.

**Hawnt and Co. Ltd.**  
Dept. PE1

**112-114 Pritchett Street  
Birmingham B6 4EN**

Telephone 021-359 4301

## YOUR OWN PROFESSIONAL SOLID STATE CLOSED CIRCUIT TELEVISION CAMERA

**ONLY  
£70 INCLUDING LENS  
& VIDICON TUBE**

Designed by the Mullard Educational Service, and shown on the BBC's 'Tomorrow's World' programme, the Linstead camera provides a composite output comprising sync. pulse and picture information.  
**Free 78-page manual**  
We give you a superb, fully illustrated 78-page construction and service manual with this kit. Apart from full assembly instructions, a complete description of basic camera principles, vidicon tube operation and circuit diagram, this manual shows all waveforms within the circuitry. We also supply a copy of the BBC Test Card F.

**Linstead**  
ELECTRONICS



The basic kit, excluding lens and tube costs only **£45**

**A COMPLETE FULLY CONSTRUCTED AND TESTED CAMERA COST ONLY £99.85**

Components are also available separately (for instance mains transformer £2.50 each).

For full details, send S.A.E. today.

Dept. P.E.  
Roslyn Works, Roslyn Rd.  
LONDON, N.15  
Telephone: 01-802 5144

## VALVES

**SAME DAY SERVICE  
NEW! TESTED! GUARANTEED!**

### SETS

1R5, 1R5, 1T4, 3B4, 3V4, DAF91, DF91, DK91, DL92, DL94.  
Set of 4 for £1.02, DAF96, DF96, DK96, DL96, 4 for £1.48.

1R5	-.28	30C1	-.28	DY87	-.25	EL500	-.82	PCL82	-.32	UABC80	-.32
1R5	-.22	30C15	-.58	DY802	-.35	EM80	-.41	PCL83	-.57	UAF42	-.51
1T4	-.16	30C17	-.79	EABC80	-.32	EM81	-.41	PCL84	-.64	UBC41	-.52
3B4	-.26	30C18	-.61	EAF42	-.50	EM84	-.32	PCL85	-.38	UBF80	-.34
3V4	-.37	30F5	-.69	EB41	-.40	EM87	-.36	PCL86	-.39	UBF89	-.32
5U4G	-.26	30FL1	-.61	EB91	-.11	EY51	-.33	PCL88	-.85	UCB84	-.33
5V4G	-.35	30FL12	-.70	EBC33	-.40	EY86	-.29	PCL800	-.75	UCB85	-.35
6T3GT	-.26	30FL14	-.68	EB41	-.54	EZ40	-.43	PEN A4	-.77	UCF80	-.33
3Z4G	-.25	30L1	-.59	EBC90	-.22	EZ41	-.43	PEN30C	-.70	UCH42	-.58
6J30L2	-.54	30L15	-.57	EBF80	-.32	EZ80	-.22	PFL200	-.53	UCH81	-.38
6AL5	-.11	30L17	-.71	EBF89	-.29	EZ81	-.23	PL36	-.49	UCL82	-.32
6AM6	-.13	30P4	-.57	ECC81	-.17	G230	-.35	PL81	-.44	UCL83	-.55
6AQ5	-.22	30P12	-.72	ECC82	-.20	GZ32	-.40	PL81A	-.49	UF41	-.56
6AT6	-.20	30P19	-.57	ECC83	-.35	GZ34	-.48	PL82	-.31	UF89	-.30
6AU6	-.20	30PL1	-.62	ECC86	-.26	K741	-.77	PL83	-.33	UL41	-.57
6BA6	-.50	30PL13	-.78	ECC90A	-.54	K761	-.55	PL84	-.30	UL44	£1.00
6BE6	-.21	30PL14	-.65	ECCF80	-.27	K766	-.78	PL500	-.62	UL84	-.30
6BJ6	-.41	30PL15	-.90	ECCF82	-.26	LN319	-.63	PL604	-.63	UM84	-.42
6BW7	-.52	35L6GT	-.45	ECH35	-.30	LN329	-.72	PM84	-.35	UY41	-.22
6CD6G	£1.07	35W4	-.25	ECH42	-.61	LN339	-.63	PX25	£1.00	UY85	-.25
6F14	-.42	35Z4GT	-.25	ECC81	-.29	N78	-.87	PY32	-.55	VP4B	-.77
6P23	-.69	807	-.45	ECH83	-.56	P61	-.45	PY33	-.55	Z77	-.22
6P25	-.57	6063	-.62	ECH84	-.36	PABC90	-.34	PY81	-.25	Transistors	
6K7G	-.12	AC/VP2	-.77	ECL80	-.30	PC86	-.47	PY82	-.25	AC107	-.17
6K8G	-.17	B349	-.65	ECL82	-.31	PC88	-.47	PY83	-.28	AC127	-.18
6Q7G	-.27	B729	-.82	ECL96	-.36	PC96	-.42	PY88	-.33	AD140	-.37
68N7GT	-.30	CCH35	-.67	EP39	-.38	PC97	-.39	PY800	-.34	AP115	-.20
6V8G	-.23	CP31	-.30	EP41	-.60	PC90	-.38	PY901	-.34	AP116	-.20
6V6GT	-.31	DAF91	-.22	EP80	-.23	PC94	-.29	R19	-.30	AP117	-.20
6X4	-.23	DAF96	-.36	EP85	-.28	PC85	-.27	R20	-.58	AF118	-.48
6X5GT	-.28	DF33	-.38	EP86	-.30	PC88	-.42	U25	-.64	AF125	-.17
7B7	-.33	DF91	-.16	EP89	-.29	PC89	-.45	U26	-.58	AF127	-.17
10P13	-.58	DF96	-.36	EP91	-.13	PC189	-.48	U47	-.64	OC26	-.25
12AT7	-.17	DI77	-.20	EP98	-.65	PC305	-.58	U49	-.58	OC44	-.12
12AU6	-.20	DK32	-.37	EP183	-.28	PCF90	-.28	U50	-.39	OC82	-.12
12AU7	-.20	DK91	-.28	EP184	-.31	PCF82	-.31	U52	-.31	OC71	-.12
12AX7	-.22	DK92	-.38	EP90	-.37	PCF86	-.45	U78	-.24	OC72	-.12
19BG6G	-.87	DK96	-.38	EL33	-.55	PCF800	-.58	U191	-.59	OC75	-.12
20F2	-.67	DL35	-.40	EL34	-.45	PCF801	-.30	U193	-.42	OC81	-.12
20F3	-.80	DL32	-.28	EL41	-.54	PCF802	-.40	U251	-.68	OC81D	-.12
20P4	-.62	DL94	-.37	EP183	-.28	PCF805	-.61	U301	-.39	OC82	-.12
25U6GT	-.20	DL96	-.38	EL90	-.28	PCF806	-.58	U329	-.68	OC82D	-.12
25U4GT	-.57	DY86	-.25	EL95	-.33	PCF808	-.68	U801	-.98	OC170	-.22

## READERS RADIO

**85 TORQUAY GARDENS, REDBRIDGE, ILFORD,  
ESSEX. Tel. 01-550 7441.**

Postage on 1 valve 5p, on 2 or more valves 3p per valve extra.  
Any parcel insured against damage in transit 3p extra.

# LINEAR & LOGIC I.C SURVEY

A look at most of the linear and logic integrated circuits now readily available to experimenters, private constructors and designers. More detailed technical information and pin connection diagrams are usually to be found in manufacturers' literature, often available from i.c. suppliers. Devices shown as being in TO5 packages may also be in similar packages (e.g. TO99, TO100, etc.) but with a different number of lead-outs.

## PART 1 LINEAR I.Cs

THE first linear integrated circuits to be produced were operational amplifiers designed for instrumentation and similar applications. Introduced by Fairchild in 1963 the "A702 gave a performance equal to or better than the available discrete component amplifiers at a similar cost. The first "high performance" operational amplifier was the "A709 which Fairchild introduced in 1965. It had more gain, a reduction of input offset current, and allowed a higher output level.

While all operational amplifiers have many characteristics in common, some conditions peculiar to individual amplifiers may be found. For example, the "A702 has a limited input voltage range of +1.5V to -6.0V indicating the possibility of "latch-up" if this is exceeded.

The "A709 output stage uses complementary emitter followers with no bias between the two bases. This produces a dead zone which can cause an excessive distortion of the output signal when only a small amount of overall negative feedback is used.

The first of the "second generation" amplifiers was the "A741. This has built-in frequency compensation, short-circuit protection, no crossover distortion, an offset voltage null capability, low power consumption, no latch-up, and a large common-mode and differential voltage range.

At first sight this built-in frequency compensation appears to solve the problems of operating down to an overall gain of unity, without instability occurring and without using external components. However, it means that the frequency compensation is NOT optimum for overall gains greater than unity.

For a 40dB gain the 741 has a bandwidth of 10kHz compared with the 1MHz bandwidth obtainable with the 709 and recommended compensation.



Circuit Function	*Package	Ferranti	Motorola	Mullard	National Semi- conductor	RCA	RS Com- ponents	Siemens	SGS	Texas
High speed differential comparator 710C	TO5 DIL		MC1710CG MC1710CP		LM710C LM710CN		710MOPA 710 OPA		U5B771039X U6E7710393	SN72710L SN72710N
General purpose operational amplifier 702C	TO5 DIL		MC1712CG MC1712CP	TAA241		CA3032			U5B771239X U6E7712393	SN72702L SN72702N
High performance operational amplifier 709C	TO5 DIL	ZLD709C ZLD709CE	MC1709CG MC1709CP	TAA521	LM709C LM709CN		709MOPA 709 OPA	TAA251	U5B770939X U6E7709393	SN72709L SN72709N
Dual version of 709C in one package	DIL		MC1437P							SN72709DN
Frequency compensated high performance operational amplifier	TO5 DIL	ZLD741C ZLD741CE	MC1741CG MC1741CP	TBA221	LM741C LM741CN	CA3056	741 OPA	TBA221	LI41TI LI41BI	SN72741L SN72741N
Version 741C without compensation 748C	TO5			TAA811	LM748C					SN72748L
Dual version of 741C	DIL				LM747C				LI47BI	SN72747N

\* DIL packages here are 14-lead versions except 7410PA which has 8 leads. Texas also make SN72709P, SN72741P, SN72748P in 8-lead DIL  
Most manufacturers make operational amplifiers and comparators

# FERRANTI

## A.C. AMPLIFIERS

TYPE	FUNCTION	CASE
ZLA10	Wideband linear amplifier for video and i.f. stages	T05
ZLA15	Wideband linear amplifier, improved version of ZLA10	T05

## D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
ZLD2S/T/U	Differential d.c. amplifiers	T05
ZLD12C/D	Complementary output stages for ZLD2 series	T05
ZLD709C	Operational amplifier	T05
ZLD709CE	Operational amplifier	DIL
ZLD741C	Operational amplifier	T05
ZLD741CE	Operational amplifier	DIL

## OTHER CIRCUITS

TYPE	FUNCTION	CASE
ZN400E	Analogue switch	DIL
ZN402E	Gated operational amplifier	DIL
ZN403E	Servo amplifier	DIL

# GENERAL ELECTRIC

## A.C. AMPLIFIERS

TYPE	TYPE	FUNCTION
Old Number	New Number	
PA222	GEL222FI	800mW audio amplifier. 22Ω load
PA230	GEL230FI	Low level audio preamplifier. 72db gain
PA234	GEL234FI	1W audio amplifier. 22Ω load
PA237	GEL237FI	2W audio amplifier. 16Ω load
PA239	GEL239FI	Stereo version of PA230
PA246	GEL246SI	5W audio amplifier. 16Ω load
PA263	GEL263SI	3.5W audio amplifier
PA266	GEL266FI	1.6W audio amplifier

## OTHER CIRCUITS

TYPE	TYPE	FUNCTION
PA264	GEL264SI	Voltage regulator
PA265	GEL265SI	Voltage regulator
PA424	GEL300FI	Zero voltage switch
PA436	GEL301FI	Phase controller for SCR
PA494	GEL304AI	Threshold detector

All the above devices have a special package

# MOTOROLA

## A.C. AMPLIFIERS

TYPE	FUNCTION	CASE
MC1303L	Stereo pre-amplifier. 68dB gain. 60dB separation	DIL
MC1304P	Stereo demodulator for f.m.	DIL
MC1305P	Stereo demodulator for f.m.	DIL
MC1306P	Complementary amplifier and pre-amplifier	DIL
MC1307P	Stereo demodulator for f.m. No audio mute	DIL
MC1330P	Low level video detector	DIL
MC1350P	I.F. amplifier with a.g.c.	DIL
MC1445L	Wideband amplifier circuits 16dB gain	DIL
MFC6010	F.M./I.F. differential amplifier 40dB gain at 10MHz	S
MFC8000	Dual differential amplifiers designed for input stage of stereo power amplifiers	S
MFC8001		S
MFC8002		S
MFC8010		S
MFC8020	1W audio amplifier and preamp	S
MFC8030	Class B driver	S
MFC8030	Flexible differential amplifier, 32dB gain	S
MFC8040	Audio preamp 3dB noise, 80dB gain	S
MFC9000	4W audio amplifier and preamp	S
MFC9010	2W audio amplifier and preamp	S

## D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
MC1430P	Operational amplifier 69dB gain	DIL
MC1433G	Operational amplifier 89dB gain	T05
MC1435G	Dual operational amplifiers of 71dB gain	T05
MC1435L	Dual operational amplifiers	DIL
MC1435P	Dual operational amplifiers	DIL
MC1437L	Dual MC1709	DIL
MC1439G	Internally compensated operational amplifier of 84dB gain	T05
MC1709CP	Differential amplifier	DIL
MC1710CP	Differential comparator	DIL
MC1712CP	Operational amplifier	DIL
MC1741CP	Fully compensated op. amplifier	DIL

## OTHER CIRCUITS

TYPE	FUNCTION	CASE
MC1460G	Voltage regulator 2.5 to 17V 250mA	T05
MC1461G	Voltage regulator 2.5 to 32V 250mA	T05
MC1463G	Voltage regulator 3.8 to 32V 250mA	T05
MC1466L	Wide range voltage and current regulator	DIL
MC1459R	Voltage regulator 2.5 to 32 volts 600mA	*
MFC4060	Regulator 4V 200mA	S
MFC6030	Regulator 4V 200mA	S
MFC6040	Electronic attenuator	S

S Special package

\* 9-lead small power transistor case

# NATIONAL SEMICONDUCTOR & SILICON GENERAL

## D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
LM709CN/SG709CN	Operational amplifier	DIL
LM710CN/SG710CN	Differential comparator	DIL
LM711CN/SG711CN	Core memory sense amplifier	DIL
LM741C/SG741CT	Fully compensated operational amplifier	T05
LM748C/SG748CT	As LM741C without compensation	T05

## OTHER CIRCUITS

TYPE	FUNCTION	CASE
LM103*	Voltage regulator 1.8V to 5.6V available	T046
LM305/SG305T	Positive voltage regulator 4.5 to 30V 20mA	T05
LM309/SG309T	Voltage regulator 5V 200mA. No external components	T05
LM309K/SG309K	Voltage regulator 5V 1A. No external components	T03

\*LM103 is specified as "LM103-1-8" etc. depending on voltage required.

# MULLARD

## A.C. AMPLIFIERS

TYPE	FUNCTION	CASE
TAA263	Three stage cascade amplifier	T072
TAA293	Medium frequency, general purpose amplifier	T074
TAA300	Audio amplifier. 1 watt into 8ohms	T074
TAA310	Low noise audio preamplifier for tape recorders	T074
TAA320	Metal oxide silicon i.f. preamplifier	T018
TAA350	Wideband limiting f.m./i.f. amplifier	T074
TAA570	Limiting—amplifier with f.m. detector	T05
TAA960	Three stage active filter amplifier. 39dB gain per stage	T074
TAA970	Microphone amplifier	T074
TAB101	Four transistor ring modulator/demodulator	T074
TAD100	A.M. receiver circuit	DIL
TAD110	A.M./F.M. i.f. amplifiers, three gain blocks	DIL

## D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
TAA241	Operational amplifier (702C)	T05
TAA242	Operational amplifier (702)	T05
TAA521	Operational amplifier (709C)	T05
TAA811	Operational amplifier (741C with-out compensation)	T05
TBA221	Fully compensated operational amplifier (741C)	T05
TBA222	Fully compensated operational amplifier (741)	T05

## OTHER CIRCUITS

TYPE	FUNCTION	CASE
TBA281	Voltage regulator 2 to 37V 150mA	T074
TBA673	Modulator/demodulator. Ring of four transistors	T074
TBA750	Limiting amplifier	16DIL

# PLESSEY

## A.C. AMPLIFIERS

TYPE	FUNCTION	CASE	TYPE	FUNCTION	CASE
SL201B	Video amplifier, current gain 26, 15MHz BW	T05	SL621C	SSB a.g.c. generator used with SL610/11/12	T05
SL301B	Matched pair of transistors, $h_{FE}$ 25 to 250, $f_T$ 600MHz	T05	SL630C	Microphone/headphone amplifier with a.g.c. Gain 40dB	T05
SL303B	Matched trio of transistors, $h_{FE}$ 25 to 250, $f_T$ 600MHz	T05	SL640C	Double balanced modulator	T05
SL403D	3 watt audio amplifier 8 ohms load, 18V supply	*	SL641C	Receiver mixer, double balanced modulator	T05
SL610C	R.F./I.F. amplifiers. 18dB gain at 30MHz. 4dB noise. 85MHz BW	T05	SL701B/C	D.C. AMPLIFIERS	
SL611C	R.F./I.F. amplifiers. 24dB gain at 30MHz. 4dB noise. 50MHz BW	T05	SL702B/C	Operational amplifier, output symmetrical about earth	T05
SL612C	R.F./I.F. amplifiers. 32dB gain at 1.7MHz. 3dB noise. 10MHz BW	T05		Operational amplifier, output not symmetrical. The minimum gain is 66dB, open loop bandwidth 250kHz on all SL701, 702 i.c.s	T05
SL620C	Voice operated gain adjusting device used with SL630C	T05			

## TEXAS

Texas Instruments produce all the common operational amplifier circuits (702, etc.)  
SN76013N 4W audio amplifier similar to Sinclair IC12

\* Special package with heat sink, DIL style  
SL201 B/C are now maintenance types

# R.C.A.

## A.C. AND D.C. AMPLIFIERS

TYPE	FUNCTION	CASE	TYPE	FUNCTION	CASE
CA3000	Differential amplifier gain 28dB BW 650kHz	T05	CA3019	Package with six diodes	T05
CA3001	Differential amplifier gain 16dB BW 16MHz	T05	CA3020	Wideband amplifier gain 75dB BW 8MHz	T05
CA3002	R.F./I.F. amplifier gain 19dB BW 11MHz	T05	CA3021	Wideband amplifier gain 50dB BW 800kHz	T05
CA3005	R.F./I.F. differential amplifier gain 16dB BW 120MHz	T05	CA3022	Wideband amplifier gain 50dB BW 3MHz	T05
CA3007	Differential audio amplifier gain 20dB BW 20kHz	T05	CA3023	Wideband amplifier gain 50dB BW 10MHz	T05
CA3010	Operational amplifier gain 57dB BW 200kHz	T05	CA3026	Two darlington transistor pairs $h_{FE}$ of 110 $f_T$ of 550MHz	T05
CA3011	Wideband amplifier gain 65dB BW 20MHz	T05	CA3028A	R.F./I.F. differential amplifier gain 35dB BW 5MHz	T099
CA3012	Wideband amplifier gain 65dB BW 20MHz	T05	CA3029	Operational amplifier gain 57dB BW 200kHz	DIL
CA3013	Wideband amplifier gain 65dB BW 20MHz	T05	CA3030	Operational amplifier gain 66dB BW 200kHz	DIL
CA3014	Wideband amplifier gain 65dB BW 20MHz	T05	CA3035	Wideband amplifier gain 40dB BW 2.5MHz	T05
CA3015	Operational amplifier gain 66dB BW 200kHz	T05	CA3036	Two darlington pair transistors $h_{FE}$ 82 $f_T$ 150MHz	T05
CA3018	Package with transistors $h_{FE}$ of 30 $f_T$ 300MHz	T05	CA3039	Six diodes 5V p.i.v. 25mA max. current	T05

## R.C.A.

TYPE	FUNCTION	CASE	TYPE	FUNCTION	CASE
CA3040	Wideband amplifier gain 34dB BW 40MHz	T05	CA3055	Voltage regulator 1.8 to 34V 115mA	T05
CA3041	Wideband amplifier/f.m. detector/a.f. preamp	14Q	CA3056	Operational amplifier gain 86dB (741C)	T05
CA3042	Wideband amplifier/f.m. detector/a.f. preamp	14Q	CA3059	Zero voltage switch for thyristor control 105mA	DIL
CA3043	I.F. amplifier/limiter/f.m. detector/audio preamp	T05	CA3060	Operational amplifier, characteristics can be varied by user	DIL
CA3044	Wideband amplifier/phase detector, for a.f.c. systems	T05	CA3062	Photo detector and power amplifier	T05
CA3045	Five transistors $h_{FE} 110 f_T 300\text{MHz}$	DIL	CA3065	I.F. amplifier, limiter, f.m. detector, audio driver	14Q
CA3046	Five transistors $h_{FE} 110 f_T 300\text{MHz}$	DIL	CA3070	Television chroma system, chroma signal processor	DIL
CA3047	Operational amplifier gain 84dB BW 20kHz	DIL	CA3071	Television chroma system, chroma amplifier	DIL
CA3048	Audio amplifier 53dB gain BW 250kHz	DIL	CA3072	Television chroma system, chroma demodulator	DIL
CA3049	Six npn transistors $f_T 1.3\text{GHz}$	T05	CA3075	F.M./I.F. amplifier, limiter, detector, audio preamplifier	14Q
CA3050	Two darlington differential amplifiers $f_T 600\text{MHz}$	DIL	CA3078	Operational amplifier gain 80dB BW 20MHz	T05
CA3051	Two darlington differential amplifiers $f_T 600\text{MHz}$	DIL			
CA3052	Audio amplifier gain 53dB BW 300kHz	DIL			
CA3053	R.F./I.F. differential amplifier gain 35dB BW 5MHz	T099			
CA3054	Differential amplifier gain 32dB	DIL			

Most of the values given for RCA i.c.s are minimum values, except that in some cases the bandwidth figures for wideband devices are the maximum useful frequency, not the 3dB down frequency

## S.G.S. A.C. AMPLIFIERS

TYPE	FUNCTION	CASE
TAA611B	2W audio amplifier	S
TAA611C	3W audio amplifier	S
TAA621	3W audio amplifier	S
TAA621A	4W audio amplifier	S
TAA661B	F.M./I.F. amplifier and detector	S
TBA231	Dual low noise operational amplifier gain 70dB	DIL
TBA271	Voltage stabiliser for varicap diode	T018
TBA311	Television signal processing	DIL
TBA581	I.F./F.M. amplifier, detector, preamp	S
TBA591	I.F./F.M. amplifier, detector, preamp	S
TBA641A	2.5W audio amplifier	S
TBA641B	4W audio amplifier	S
TBA651	A.M. receiver circuit	S
TBA631	Television sound circuit	S

### D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
$\mu$ A710C	High speed differential comparator	T05
$\mu$ A702C	General purpose operational amplifier	T05
$\mu$ A709C	High performance op.-amplifier	T05
$\mu$ A741C	Fully compensated op.-amplifier	T05

Q = quad-in-line

## SIEMENS A.C. AMPLIFIERS

TYPE	FUNCTION	CASE
TAA141	Three stage audio amplifier 70dB gain 20kHz BW	T072
TAA151	Three stage audio amplifier 70dB gain 600kHz BW	T0100
TAA420	Low noise five stage amplifier 70dB gain 20kHz BW	T0100
TAA435	Audio amplifier for driver stages	T0100
TBA120	F.M./I.F. amplifier and demodulator 60dB gain	DIL
TBA400	Broadband amplifier r.f./i.f. 75dB power gain at 35MHz	S
TBA450	Stereo decoder	S
TBA460	A.M./F.M. i.f. l.f. amplifier	S

### D.C. AMPLIFIERS

TYPE	FUNCTION	CASE
TAA521	Operational amplifier (709C)	T05
TAA522	Operational amplifier (709)	T05
TAA861	Operational amplifier 70mA output current 90dB gain	T078

S = Special package

## APPLICATIONS OF LINEAR I.C.s

Both the 709 and 702 require several external components to frequency-compensate the amplifier so that it is stable under closed-loop conditions and cannot oscillate. The 702, 709 and the 710 comparator were the "first generation" amplifiers.

Although fully compensated, operational amplifiers can be used in any feedback circuit without instability occurring, and without external compensation components, bandwidth and slew rate are reduced. The 710, 702, 709, 741 are produced by many manufacturers. A "C" suffix (for example 702C) has a slightly reduced temperature range and specification over the version without the suffix.

### SERIES 741C OPERATIONAL AMPLIFIER


Although operational amplifiers are perhaps the most useful of the vast range of available linear integrated circuits, with varied applications from multivibrators to active filters, many circuits are designed for specific applications. A glance at this survey will reveal a small part of the range available to commercial and industrial organisations. Most of those listed are also readily available to the home constructor.

### UNITY GAIN VOLTAGE FOLLOWER



Input impedance 400M $\Omega$   
Output impedance 1 $\Omega$   
Bandwidth 1MHz


### INVERTING AMPLIFIER

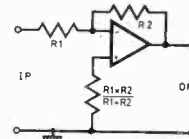

Gain	R1	R2	BW
1	10k $\Omega$	10k $\Omega$	1MHz
10	1k $\Omega$	10k $\Omega$	100kHz
100	1k $\Omega$	100k $\Omega$	10kHz
1000	100 $\Omega$	100k $\Omega$	1kHz

$R_{in} < 10k\Omega$

### NON-INVERTING AMPLIFIER

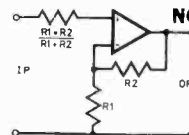

Gain	R1	R2	BW
10	1k $\Omega$	9k $\Omega$	100kHz
100	100 $\Omega$	9.9k $\Omega$	10kHz
1000	100 $\Omega$	99.9k $\Omega$	1kHz

$R_{in} > 50M\Omega$

**Logic integrated circuits have opened up a whole new science in systems design that does not necessitate deep technical knowledge of the circuit inside the package. Given a basic set of parameters, logic i.c.s can be built into large systems with little difficulty.**

**R**EPRESENTING almost unbelievable value for money in terms of components per penny (the 7400 TTL gate, for example, can be purchased for as little as 15p and contains sixteen transistors, sixteen resistors and four diodes), the logic i.c. families are now available to the amateur from many suppliers who stock an incredibly wide range of types.

To those readers put off by such mystic terms as "fan-out", "flip-flop" and "truth-table", take heart, almost anything that can be built with logic i.c.s can also be built (mentally at least) using relays. Logic gates are simply switches with an "on" and

"off" state, and all the more complicated devices, such as bistables, can be built with gates. Logic really is easy to pick up and after a start has been made, the subtleties can be appreciated one by one.

For those who have always wanted to design something electronic, but have been put off by simultaneous equations and slide rules, this is the scene for you; after a comprehension of the principles is obtained, all you need to start designing is common sense; all the maths has been done by the manufacturers.

## LOGIC FAMILIES

The three main families are RTL, DTL, and TTL, while MSI (medium scale integration) uses TTL methods and incorporates several TTL circuits in each package to give a complex function, for example, a counter.


The tables given here are far from exhaustive because of the several manufacturers' different type numbers, but they do represent the majority of devices available through retail outlets.

RTL is gradually losing favour because of the competitive lowering of prices of the DTL and TTL.

In the DTL range, although a common coding can be found among many manufacturers, it is also worth obtaining the leaflets and handbooks on other types. Mullard and Siemens operate Pro Electron codings but they are not always interchangeable equivalents in all cases. Ferranti use different codings again for their Micronor series, prefixed ZS, which is divided into a 20ns range, medium speed range (15ns), and a high speed range (9ns).

Readily available types in the DTL range are mostly given a coding which includes digits 930 and 9090 upwards, other letters and figures being added according to manufacturers' choice. The Mullard range uses Pro Electron numbering prefixed by FC.

The widest range is TTL which extends into medium scale integration MSI. Again because of space limitations we have listed the most common in the 74 series, various manufacturers adding their own personal identity prefix. It is worth pointing out here that although many of the Mullard and Siemens TTL types (prefix FJ) are similar to the 74 series, they are not all identical.

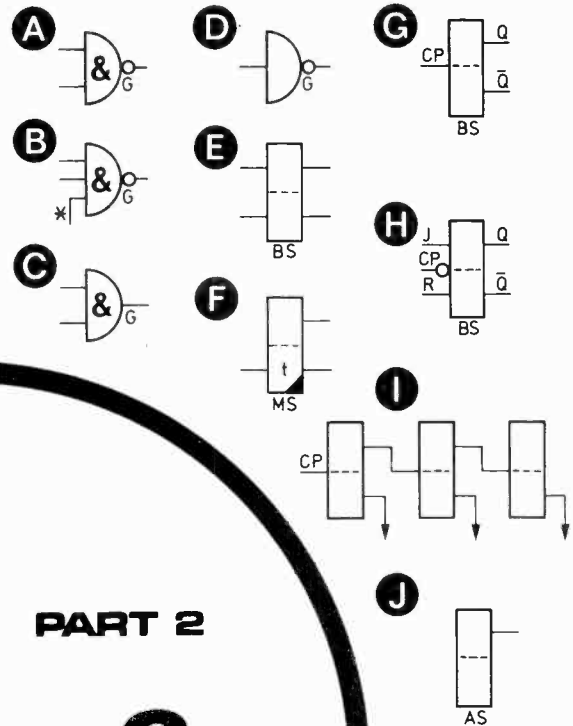

**PART 2**

**&**

**LOGIC I.C.s**

## POSITIVE LOGIC

A—2-INPUT NAND GATE

B—2-INPUT NAND GATE EXPANDABLE

C—2-INPUT AND GATE

D—INVERTER

E—BISTABLE WITH NORMAL INPUTS AND OUTPUTS

F—MONOSTABLE MULTIVIBRATOR

G—BISTABLE WITH CLOCK INPUT

H—BISTABLE WITH CLOCK INPUT, SET AND RESET

I—MULTI-STAGE BISTABLE USED AS DIVIDER OR COUNTER

J—ASTABLE MULTIVIBRATOR

FAIRCHILD	FERRANTI	ITT	MOTOROLA	MULLARD	NATIONAL	SIEMENS	TEXAS
9002	ZN7400E	9002	MC7400P	FJH131	DM8000N	FLH101	SN7400N
	ZN7401E		MC7401P	FJH231	DM8001N	FLH201	SN7401N
	ZN7402E		MC7402P	FJH221	DM8002N	FLH191	SN7402N
				FJH291	DM8003N		SN7403N
	ZN7403E	9016	MC7404P	FJH241	DM8004N		SN7404N
9003	ZN7410E	9003	MC7410P	FJH121	DM8010N	FLH111	SN7410N
9004	ZN7420E	9004	MC7420P	FJH111	DM8020N	FLH121	SN7420N
	ZN7430E		MC7430P	FJH101	DM8030N	FLH131	SN7430N
9009	ZN7440E	9009	MC7440P	FJH141	DM8040N	FLH141	SN7440N
	ZN7441E			FJL101	DM8840N		SN7441AN
				FJH151	DM8842N		SN7442N
9005	ZN7450E	9005	MC7450P	FJH161	DM8050N	FLH151	SN7450N
	ZN7451E		MC7451P	FJH161	DM8051N	FLH161	SN7451N
	ZN7453E	9008	MC7453P	FJH171	DM8053N	FLH171	SN7453N
	ZN7454E		MC7454P	FJH181	DM8054N	FLH181	SN7454N
9006	ZN7460E	9006	MC7460P	FJY101	DM8060N	FLY101	SN7460N
	ZN7472E		MC7472P	FJJ111	DM8540N	FLJ111	SN7472N
	ZN7473E		MC7473P	FJJ121	DM8501N	FLJ121	SN7473N
	ZN7474E		MC7474P	FJJ131	DM8510N	FLJ141	SN7474N
	ZN7475E		MC7475P	FJJ181	DM8550N	FLJ151	SN7475N
	ZN7476E		MC7476P	FJJ191	DM8500N	FLJ131	SN7476N
				FJJ141	DM8530N	FLJ161	SN7490N
				FJJ251	DM8532N		SN7492N
			MC7493P	FJJ211	DM8533N		SN7493N

# RESISTOR TRANSISTOR LOGIC

# RTL

## General Characteristics

- Gate speed 30ns, power 20mW
- Supply  $\pm V_{CC}$  3-6V  $\pm 10\%$
- Frequency range 8MHz
- Noise immunity 0-3V

These RTL circuits are suitable for many simple switching operations where relatively medium speed operation is acceptable, for example, as an electronic relay.

## FAIRCHILD

- |             |                                                |     |
|-------------|------------------------------------------------|-----|
| $\mu$ L 910 | Single inverter/driver                         | T05 |
| $\mu$ L 914 | Dual 2-input gate, positive NOR, negative NAND | T05 |
| $\mu$ L 923 | Single JK flip-flop with preset and clear      | T05 |

## MOTOROLA

- |        |                              |        |                                       |
|--------|------------------------------|--------|---------------------------------------|
| MC711G | 4-input OR/NOR gate          | MC780P | Decade counter                        |
| MC714G | Dual 2-input NOR gate        | MC785P | Quad 2-input expander                 |
| MC715P | Dual 3-input NOR gate        | MC787P | 1 JK flip-flop, 1 inverter, 2 buffers |
| MC717P | Quad 2-input NOR gate        | MC788P | Dual 3-input buffer, non-inverting    |
| MC718P | Dual 3-input NOR gate        | MC789P | MC889P Hex inverter                   |
| MC719P | MC819P Dual 4-input NOR gate | MC790P | MC890P Dual JK flip-flop              |
| MC722P | JK flip-flop                 | MC791P | Dual JK flip-flop                     |
| MC723P | JK flip-flop                 | MC792P | MC892P Triple 3-input NOR gate        |
| MC724P | MC824P Quad 2-input NOR gate | MC793P | Triple 3-input NOR gate               |
| MC726P | JK flip-flop                 | MC799P | Dual buffer                           |
| MC7269 | JK flip-flop                 | MC825P | Dual 4-input NOR gate                 |
| MC778P | Dual D-type flip-flop        |        |                                       |

Suffix G — T05

P — plastic DIL

MC700 Series  $\pm 15^\circ\text{C}$  to  $\pm 55^\circ\text{C}$

MC800 Series 0 to  $\pm 75^\circ\text{C}$

# DIODE TRANSISTOR LOGIC

# DTL

## General Characteristics

The following type characteristics apply to all manufacturers' DTL i.c.s using the coding given in the DTL tables.

- Gate speed 25ns, power 5mW
- Supply  $\pm V_{CC}$  5V  $\pm 5\%$
- Frequency range 20MHz
- Input forward current — 10mA
- Input reverse current 1mA
- Noise immunity 0-7V at 25°C
- Temperature range 0°C to 75°C
- Case outline DIL

DTL is suitable for most medium speed applications and is compatible with TTL. Positive logic usually applies to DTL circuit descriptions.






Temperature range  $-55^\circ\text{C}$  to  $+125^\circ\text{C}$

## Common Code Digits

- |        |                                     |      |                                                                     |
|--------|-------------------------------------|------|---------------------------------------------------------------------|
| MC830P | Expandable dual 4-input NAND gate   | 930  | Dual 4-input NAND gate (expandable) fan-out 8                       |
| MC831P | Clocked flip-flop                   | 932  | Dual 4-input NAND driver gate (exp) fan-out 25                      |
| MC833P | Dual 4-input expander               | 933  | Dual 4-input expander                                               |
| MC836P | Hex inverter                        | 935  | Hex inverter (expandable)                                           |
| MC846P | Quad 2-input NAND gate              | 936  | Hex inverter fan-out 8                                              |
| MC848P | Clocked flip-flop                   | 944  | Dual 4-input NAND with open collector, lamp/relay driver fan-out 27 |
| MC849P | Quad 2-input NAND gate              | 945  | RS flip-flop with preset and clear (master/slave) fan-out 14        |
| MC851P | Monostable multivibrator            | 945  | Quad 2-input NAND gate fan-out 8                                    |
| MC856P | Dual JK flip-flop                   | 948  | RS flip-flop with preset and clear (master/slave) fan-out 13        |
| MC862P | Dual 2-input NAND gate and inverter | 951  | Monostable multivibrator fan-out 10                                 |
| MC886P | Dual 4-input expander               | 962  | Triple 3-input NAND gate fan-out 8                                  |
|        |                                     | 9093 | Dual JK flip-flops with preset inputs                               |
|        |                                     | 9094 | Dual JK flip-flops with preset inputs                               |
|        |                                     | 9097 | Dual JK with preset inputs and common clear                         |
|        |                                     | 9099 | Dual JK with preset inputs and common clear                         |
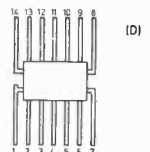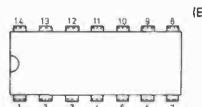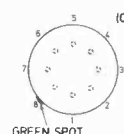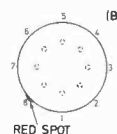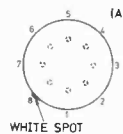
## CASE OUTLINES (view from above case)

- A — T05 — RTL  $\mu$ L900
- B — T05 — RTL  $\mu$ L914
- C — T05 — RTL  $\mu$ L923
- D — Flat-pack — 14 leads
- E — Dual-in-line — 14 leads
- F — Dual-in-line — 16 leads
- G — Dual-in-line — 24 leads





# TRANSISTOR TRANSISTOR LOGIC

# TTL

## General Characteristics

The following type characteristics apply to all manufacturers' TTL i.c.s using the 74 series coding given in the TTL table.

- Gate speed 10ns, power 10mW
- Fan-out 10
- Supply  $\pm V_{CC} 5V \pm 5\%$
- Frequency range 10MHz
- Input forward current  $-1.6mA$  (logic 0)
- Input reverse current 1mA
- Noise immunity 1V
- Temperature range (74 series) 0°C to +70°C
- Temperature range (54 series)  $-55^{\circ}C$  to  $+125^{\circ}C$

Case outlines: mainly DIL (suffix N), flat pack, TO5 can. TTL is the most comprehensive range of logic i.c.s. It is used in high speed low power applications, where very short connecting lines (12in) can be used to avoid unwanted triggering from noise spikes. Positive logic applies to TTL circuit descriptions. TTL is compatible with DTL, ECL, MSI, using current sinking logic.

Suffix H indicates high speed (6ns) series, 22mW per gate, and fan-out of 8. Suffix L indicates low power (1mW) series, low speed (33ns), high fan-out 49.

Suffix N indicates a dual-in-line package although not shown in this list. Some suppliers omit the N in their lists so check before buying whether DIL or flat-pack is available; DIL is usually cheaper and easier to use. DIL package holders are recommended for easy insertion and removal of the i.c.

## TTL GATES, BUFFERS, DRIVERS

- 7400 Quad 2-input positive NAND
- 7401 As 7400 but with open collector outputs
- 7402 Quad 2-input positive NOR
- 7403 As 7401 but pin connections as in 7400
- 7404 Hex inverters
- 7405 Hex inverters, open collector outputs
- 7406 Hex inverters, open collector buffer/drivers
- 7407 Hex buffers/drivers, open collector outputs
- 7408 Quad 2-input positive AND gates
- 7409 As 7408 but with open collector outputs
- 7410 Triple 3-input positive NAND gates
- 7413 Dual 4-input Schmitt triggered positive NAND gates
- 7420 Dual 4-input positive NAND gates
- 7430 Single 8-input positive NAND gate
- 7440 Dual 4-input positive NAND buffer
- 7450 Dual two-wide, 2-input AND-OR-INVERT (expandable)
- 7451 As 7450 but not expandable
- 7453 Single four-wide, 2-input AND-OR-INVERT (expandable)
- 7454 As 7453 but not expandable
- 7460 Dual 4-input expander for 7450 or 7453
- 7486 Quad 2-input exclusive-OR gates



## TTL FLIP-FLOPS

- 7470 Single edge-triggered JK with preset and clear
- 7472 JK master/slave flip-flop with preset and clear
- 7473 Dual JK master/slave flip-flops with clear inputs
- 7474 Dual D-type edge-triggered flip-flops with preset and clear
- 7475 Quad D-type 4-bit bistable latches with paired clocks (no clear)
- 7476 Dual JK master/slave flip-flops with preset and clear
- 74107 Dual JK master/slave flip-flops as 7473, different connections
- 74118 Hex set/reset latch with common reset
- 74119 Hex set/reset latch with common and separate reset
- 74121 Gated or d.c. triggerable monostable multivibrator

## MSI
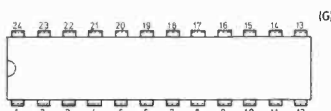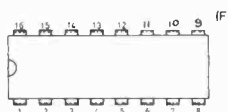
## TTL MEDIUM SCALE INTEGRATION

- 7441A BCD to decimal decoder/drivers
- 7442 BCD to decimal decoders
- 7445 BCD to decimal decoder drivers high power 30V output
- 7445 BCD to seven segment display decoder/drivers open collector outputs 30V
- 7447 As 7446 but 15V output
- 7448 As 7445 but with passive pull-up outputs
- 7449 BCD to seven segment display decoder/drivers, open collector outputs, blanking input
- 7480 Gated full adder
- 7481 Sixteen-bit active-element read/write memory
- 7482 Two-bit binary full adder
- 7483 Four-bit binary full adder
- 7484 As 7481 but with gated write-amplifier inputs
- 7488 256-bit read-only memory
- 7490 Decade ripple counter with reset and preset to 9
- 7491A Eight-bit shift register (serial-in, serial-out)
- 7492 Divide-by-two and divide-by-six counter ( $\div 12$ ) with reset
- 7493 Four-bit binary counter with reset ( $\div 16$ )
- 7494 Four-bit shift register, dual entry parallel-in, serial-out
- 7495 Four-bit right-shift left-shift register
- 7496 Five-bit shift register, parallel-in, parallel-out
- 74100 Eight-bit bistable latches
- 74141 Improved version of 7441 to minimise switching transients
- 74145 Four-line to ten-line decoder, open collector outputs
- 74150 16-bit multiplexer with strobe input
- 74151 8-bit multiplexer with strobe input
- 74153 Dual 4-bit multiplexer with strobe inputs
- 74154 Four-line to sixteen-line decoder with strobe input
- 74155 Dual two-line to four-line decoder with strobe inputs
- 74156 As 74155 but with open collector outputs
- 74160 Synchronous decade counter with parallel inputs
- 74161 Synchronous binary counter with parallel inputs
- 74190 Synchronous up/down decade counter
- 74191 Synchronous up/down binary counter
- 74192 Synchronous up/down BCD counter
- 74193 Synchronous up/down 4-bit binary counter




# APPLICATIONS OF LOGIC I.C.s

Fig. 1 shows a simple double pulse detector using a couple of DTL devices, especially handy for detecting index marks in position sensing equipment. If the input trigger pulses are derived from slowly


**Fig. 1**  
**DOUBLE LINE PULSE DETECTOR**

Gives an output pulse when a double pulse occurs. Monostable triggers on negative edge of input pulse. One application is to detect a double slot in rotating discs using a photo-electric cell

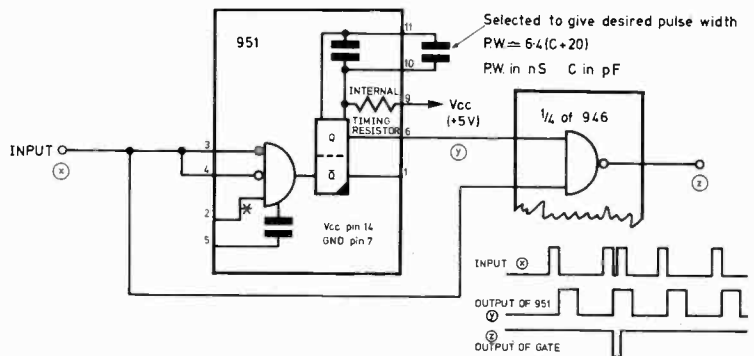

**Fig. 2**  
**SOLID STATE STEPPING SWITCH**

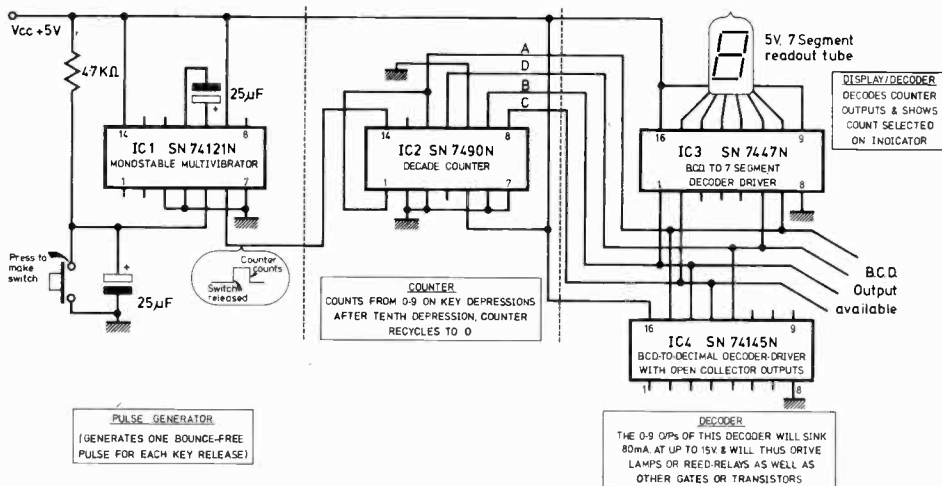This switch uses four TTL/MSI integrated circuits and provides seven segment digital readout for ten position channel selection



changing sources a couple of gates will be required ahead of the circuit shown to speed up the edges ready to fire the monostable (these are available anyway in the 946 range of DTL).

Fig. 2 shows a scheme for a solid state stepping switch which could be useful for example for channel selection in a radio or television receiver.

The operation is simple, the single push-button control is pushed an appropriate number of times until the required channel number is displayed on the readout. At this point the selected output of the 74145 is low, and can be used to drive a wide variety of external circuitry.

Many variations of this circuit are possible, and the whole thing can be made little larger than a cigarette packet. This example illustrates an interesting substitute for a wafer switch for some applications.

## I.C. SUPPLIERS

The following advertisers in this magazine specialise in the supply of integrated circuits to readers:

A. Marshall & Son (London) Ltd  
 Henry's Radio Ltd  
 G. W. Smith & Co (Radio) Ltd  
 Bi-Pak  
 Distronic Ltd

Distributors for Newmarket Transistors Ltd  
 Diotran Sales  
 Electrovalue  
 Bi-Pre-Pak Ltd  
 LST Electronic Components Ltd  
 Sinclair Radionics Ltd  
 Chromasonic Electronics Ltd  
 Distributors for Ferranti Ltd



An example of a complex group of sunspots. This was an extremely active area on the sun which lasted for several days. The small spot below the main group is about the size of the earth. The magnitude of the group is apparent from this comparison.

# RADIO ASTRONOMY TECHNIQUES

By F. W. Hyde

PART 7

HAVING now had some experience in the operation of the simple radio telescope, the "feel" of the subject will no doubt have been acquired. After the experience of sorting out what is interference, what is random noise, and what is the real signal to be acquired, the limitations of the simple unit will be apparent. However, although this article will begin the description of interferometers and details of their construction, it is recommended that the observer should continue with the programme of the first project for two reasons.

The first reason is that it takes some time to become facile at recognition of the many different forms of interference, some of which will be man-made and some random signals due to odd reflections from the upper atmosphere. The second reason is that the data acquired and entered in the log will be of considerable importance when compared with the measurements made with the interferometer.

Of course, some constructors will not have the space to set up an interferometer and so must in any case continue with the single aerial unit. Bearing this in mind, some suggestions that may help these people will be given in the last article of this series.

## IDENTIFICATION OF SPACE SIGNALS

If the unit has been used during the night with the aerial pointed upwards, it is certain that there will be some signs of the radiation from the sources in Cygnus and Andromeda, and also the Crab Nebula. Also, the general rise in level of the recording at different times during each successive day and night will enable the positive identification of extra terrestrial radiation.

This was, in fact, the way in which the original pioneer Karl Guthe Jansky identified the existence of signals or radiation from space. To quote from his original paper, "In conclusion data have been presented which show the existence of electromagnetic waves in the Earth's atmosphere which apparently come from a direction that is fixed in

space. The data obtained give for the coordinates of this direction a right ascension of 18.00 hours and a declination of  $-10^{\circ}$ ."

Bearing in mind that the width of the aerial beam is quite wide in the vertical direction, tip the aerial so that the dipoles are directed at the Milky Way. Let the system run for a week every night or every three nights if this is more convenient. After the run compare the recordings by laying them side by side with the time marks aligned so that the same time is shown. Examine them for some significant event and check the difference in time that has elapsed. There should be a change of some 15 minutes in three days and some 30 minutes in a week. The exact times can be checked from the charts and the figures given are for the purpose of guidance only.

If it is possible obtain a copy of the *Ephemeris* issued by the Nautical Almanack Office. This may be available from the library or it can be obtained from the Stationery Office Bookshop in Holborn, London.

Table 7.1 indicates some of the radio sources that should be detectable quite easily on the simple radio telescope. Since there are bound to be satellites recorded, it will be quite clear from the table which these are, because they can be compared with the tracings shown in Part 6 of this series.

## SIDEREAL TIME

The table gives the usual astronomical coordinates of hour angle and declination. This involves certain corrections on the part of the observer for the hour angle or right ascension. This hour angle is in *Sidereal Time* which differs from ordinary astronomical time by an acceleration of 10 seconds in each hour, or approximately four minutes per day. The time is reckoned from the entry of the first point of ARIES which occurs between the twenty-first and twenty-third of March each year. This is the Vernal Equinox, 00.00 hours right ascension. All of this may appear a little complicated but it can be reduced to fairly simple terms for the purpose of the project.

In Table 7.2 a summary is given of the sidereal time for noon G.M.T. for each day of the year. This is approximate, but will not vary by more than about five minutes for each day and this error is insignificant with the system being used. In any case the source will be well within the beam of the aerial.

### SIMPLE INTERFEROMETER

The simple two-aerial interferometer was briefly described in Part 2 of this series, and the modification required to convert the existing simple telescope is really one of addition. Firstly the existing aerial must be duplicated, together with the pre-amplifier if this is located at the aerial. The two aerials should be set up preferably on an east to west baseline. Within certain limits this is not an absolute requirement, but this will be dealt with later in this article. The distance between the aerial centres should be, if possible, at least five wavelengths. At the frequency that has been adopted this will mean a distance of 36 feet.

It is necessary to connect the aerials together. This may be done at the observing point, or if this distance is greater or about the same length as the distance between the aerials, then the following alternative arrangement is possible.

Having set up the aerials, cut two lengths of cable which will leave sufficient slack for the aerials to be moved further apart and to facilitate stowage. These

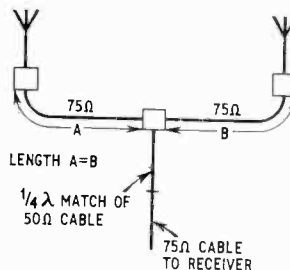


Fig. 7.1. Coupling two aerials together as a simple interferometer

two lengths of cable must be exact to within about one half inch, and of the same type of cable. These two points are very important. As both ends of the cables will terminate in coaxial plugs the equality of length includes the plugs. At the junction of the two aerial cables there will be a connection box as shown in Fig. 4.6 of Part 4. The outlet from this box will go to the converter in the same way as for the simple telescope, that is, with the matching section of 50 ohm cable followed by the 75 ohm cable. The diagram in Fig. 7.1 gives the layout.

The importance of the length of the cables has been stressed because the operation of the two aerial system depends on the combining of the signals which are alternately in phase and out of phase with the other.

TABLE 7.1. LIST OF RADIO SOURCES

CONSTELLATION	I.A.U. NO.	RIGHT ASCENSION	DECLINATION	IDENTIFICATION
*Cassiopeia	00N6A	00h 22m ± 2m	64° 15' ± 35'	(12) Supernova 1572 (no visible remnants)
Andromeda	00N4A	00h 40m 15s ± 30s	40° 50' ± 20'	(11) M31 NGC224
Perseus	03N4A	03h 16m 37s ± 4s	41° 25' ± 6'	(17) NGC1275 Colliding galaxies?
Auriga	04N4A	05h 08m ± 4m	46° ± 1°	(13) Angular size of source is 1° 4' Identified with galactic nebulosity
*Taurus	05N2A	05h 31m 35s ± 5s	22° 04' ± 5'	(4) M1 NGC1952 Crab Nebula
Orion	05S0A	05h 33m 0 ± 0m 2	-05° 27' ± 5'	(18) Orion Nebula M42 NGC1976
Gemini	06N2A	06h 13m 37s ± 4s	22° 38' ± 5'	(19) IC443
Monoceros	08S0A	08h 08m ± 10m	-06° ± 30°	(13)
Lynx	08N4A	08h 09m ± 2m	48° ± 1°	(8)
Puppis	08S4A	08h 20m ± 4m	-42° 30' ± 1°	(13) Galactic nebulosity
Lynx	09N4A	09h 16m ± 4m	47° ± 1°	(8)
Hydra	09S1A	09h 16m ± 2m	-12° ± 2°	(13)
Ursa Major	09N6A	09h 51m 20s ± 2m	69° ± 1°	(15) NCG3031
Vela	10S4A	10h 10m ± 4m	-42½° ± 20'	(2)
Ursa Major	10N5B	10h 30m ± 2m 5	57° ± 2°	(11)
Crater	11S1A	11h 38m ± 8m	-15° ± 2°	(13)
Canes Venatici	12N4A	12h 15m ± 3m	47° ± 1½°	(11) NGC4258
Virgo	12N1A	12h 28m 11s ± 37s	12° 41' ± 10'	(1) M87 NGC4486
Centaurus	13S4A	12h 22m 24s ± 1m	-42° 37' ± 8'	(1) NGC5128
Canes Venatici	13N4A	13h 27m 30s ± 3m	47° ± 1°	(11) NGC5195
Boötes	14N5A	14h 10m ± 2m	51° 30' ± 1°	(11) NGC5457
Serpens Caput	15N1A	15h 10m ± 4m	11° ± 1½°	(2)
Triangulum Australe	16S6A	16h 10m ± 8m	-60½° ± 5'	(2)
Hercules	16N4A	16h 36m ± 10m	41° ± 2°	(13)
Hercules	16N0A	16h 45m ± 2m	6° ± 1° 5	(2)
Sagittarius	17S2A	17h 42m ± 1m	-28° 5' ± 0° 2	(21) May be associated with the galactic nucleus. The presence of neighbouring intense emission regions makes the measurements of flux density difficult
Ophiuchus	18S0A	18h 16m ± 4m	-8° ± 2°	(13)
Sagittarius	18S1A	18h 17m 9 ± 0m 2	-16° 14' ± 5'	(18) Omega Nebula M17 NGC6618
*Cygnus	19N4A	19h 57m 44s ± 2½s	40° 35' ± 1½'	(3) Colliding galaxies
*Cygnus	20N4A	20h 22m	40°	(11) Cyg X extended source possibly associated with galactic nebulosity
*Cassiopeia	23N5A	23h 21m 36s ± 30s	58° 35' ± 10'	(11) Galactic nebulosity

\* Very strong sources

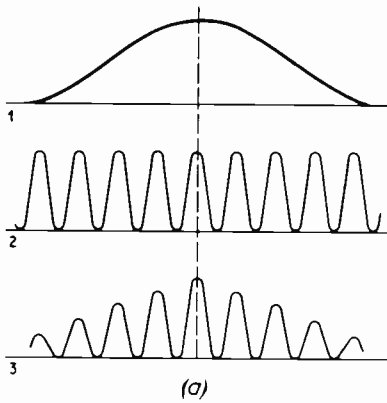


Fig. 7.2a. The effects of differing aerial parameters. (1) Single aerial pattern. (2) Two aerial pattern. (3) Interferometer pattern (point source)

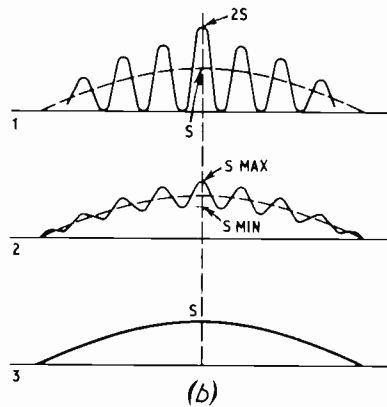


Fig. 7.2b. (1) Point source pattern. (2) Uniform extended source comparable but smaller than lobe spacing. (3) Uniform extended source equal to or greater than lobe spacing

When using an interferometer it is usual to have the aerials aligned and fixed in azimuth facing south in the northern hemisphere and north in the southern hemisphere. The altitude will depend on the section of sky to be observed, but each will normally be at the same angle of altitude. This will apply to each sweep of the sky. The sweeping will be done by the rotation of the earth so that in the course of 24 hours the whole 360 degrees of sky, as seen from the earth, will be scanned by the width of the aerial beam.

### RESOLUTION

The resolution or ability to distinguish between sources will be dependent on two parameters. One is the distance between the aerials, for this governs the width of the fringes, and the width of a fringe

determines the size of the smallest source that can be recognised. The diagrams in Fig. 7.2a and b illustrate the effects of these varying conditions.

It is essential that the beginner goes through this step of the simple interferometer in order to make practical observations and again have experience of the working conditions.

### FRINGE WIDTH

Before moving on to the more complicated phase-switched interferometer there are one or two points which need to be covered. Firstly, the simple calculation to be made to determine the fringe width. The relationship between the fringes and the distance between the two aerials is in this form. The beam width between first null points (the fringe spacing) is  $1/D\lambda$  radians which equals  $57.3/D\lambda$ .

TABLE 7.2

DAY	JAN.	FEB.	MAR.	APR.	MAY	MONTH JUNE	JULY	AUG.	SEPT.	OCT.	NOV.	DEC.
1	18 40	20 43	22 33	00 35	02 33	04 36	06 34	08 36	10 38	12 37	14 39	16 37
2	44	46	37	39	37	40	38	40	42	41	43	41
3	48	50	41	43	41	43	42	44	46	44	47	45
4	52	54	45	47	45	47	46	48	50	48	51	49
5	56	58	49	51	49	51	50	52	54	52	55	53
6	19 00	21 02	53	55	53	55	54	56	58	56	59	57
7	04	06	57	59	57	59	58	09 00	11 02	13 00	15 02	17 01
8	08	10	23 00	01 03	03 01	05 03	07 01	04	06	04	06	05
9	12	14	04	07	05	07	05	08	10	08	10	09
10	16	18	08	11	09	11	09	12	14	12	14	13
11	20	22	12	15	13	15	13	16	18	16	18	17
12	24	26	16	18	17	19	17	19	22	20	22	20
13	28	30	20	22	21	23	21	23	26	24	26	24
14	32	34	24	26	25	27	25	27	30	28	30	28
15	35	38	28	30	29	31	29	31	34	32	34	32
16	39	42	32	34	33	35	33	35	37	36	38	36
17	43	46	36	38	36	39	37	39	41	40	42	40
18	47	50	40	42	40	43	41	43	45	44	46	44
19	51	53	44	46	44	47	45	47	49	48	50	48
20	55	57	48	50	48	51	49	51	53	52	54	52
21	59	22 01	52	54	52	54	53	55	57	55	58	56
22	20 03	05	56	58	56	58	57	59	12 01	59	15 02	18 00
23	07	09	24 00	02 02	04 00	06 02	08 01	10 03	05	14 03	06	04
24	11	13	04	06	04	06	05	07	09	07	10	08
25	15	17	08	10	08	10	09	11	13	11	13	12
26	19	21	11	14	12	14	12	15	17	15	17	16
27	23	25	15	17	16	18	16	19	21	19	21	20
28	27	29	19	22	20	22	20	23	25	23	25	24
29	31		23	26	24	26	24	27	29	27	29	28
30	35		27	29	28	30	28	30	33	31	33	31
31	39		31		32		32	34		35		35

SIDEREAL TIME FOR NOON G.M.T. FOR 0° LONGITUDE

Using three examples of spacing, the first five wavelengths, the second 10 wavelengths, and a third 20 wavelengths, the approximate figures are 11.5 degrees, 5.73 degrees, and 2.86 degrees respectively. Since this is the point of the nulls the actual fringe width is half each value given at the half power points. The half power points were explained in Part I and illustrated in Fig. 1.4.

### CHART SPEED

The second point to be noted is the appropriate speed of the chart on the pen recorder consistent with obtaining a useful trace.

Taking the case of the least spacing 11.5 degrees, it will take 46 minutes for passing from the one null to the next, since it takes about four minutes of time for the earth to move 1.0 degree of arc. Therefore in this instance it will be wise to choose a slow speed for the recorder in order that the fringes may be clearly visible. A preferred speed would be 0.5 inches per hour, though 1.0 inch per hour would

be permissible. For the widest spacing quoted a speed of 3.0 inches per hour would give best results. It will be clear from this that the greater spacing offers a better chance of detecting sources than the lesser spacing.

### THE BASE LINE

Finally the setting up of the base line must be considered—for those who have the space to accommodate the interferometer. It is not sufficient to set up the south point using a compass, though this is a first step. The south point required is *geographical south* and this differs by several degrees. The exact amount of difference is obtainable for each year from ordnance survey maps. It was 8 degrees 40 minutes West in 1948, and decreasing by about 8 minutes annually.

Next month's article will be concerned with the phase-switched interferometer.

## NEWS BRIEFS

### TRAFFIC SPEED METER

A COMPLETELY new road traffic speed measurement system is being developed by GEC-Marconi Electronics, under contract to the Director of Telecommunications, Home Office.

The new system uses an optical method of measurement and the complete system can be contained in a single unit which can be placed at the side of the road. The unit looks at right angles to the traffic flow and as soon as a vehicle passes, and comes within the field of view of the optical system, its speed will be measured almost instantaneously, and shown on a three-digit display, probably using a liquid crystal system.

The image of the vehicle is split into a succession of vertical strips, which are viewed by a photodiode. Any irregularities in the image, whether bright spots or shadow, will move across the slits of the "virtual" grating and produce a fluctuation of the light falling on the diode. The frequency of this fluctuation is measured and, from it, solid-state micrologic circuitry calculates the speed of the vehicle.

### EUROPE'S FIRST FULLY AUTOMATIC NAVIGATIONAL BUOY

IN ALMOST every field nowadays man is rapidly being replaced by electronic equipment. This is the case at Portland Bill, Dorset, where a fully automatic navigational buoy has recently replaced the manned Shambles lightship.

The 84 ton buoy, made by Hawker Siddeley Dynamics and named Lanby (Large Automatic Navigational Buoy) has a 40ft latticework mast topped with a main light beacon giving a luminous range of 16 miles. Also on board is a powerful fog signalling device, with an audible range of more than 3 miles.

The buoy is monitored every 30 minutes by a shore control station using a radio telemetry link. Should any failure occur, standby services operate automatically, and the nature of the fault is relayed to the control station.

The buoy can be moored in depths from 30 to 300ft, and can withstand winds up to 100 mph, waves up to 40ft and tidal currents up to seven knots.

### UNDERWATER TELEVISION EQUIPMENT

THE present system of searching for and locating underwater wreckage, such as crashed aircraft and sunken ships by use of drag lines towed by surface craft seems soon to be superseded by a more efficient electronic method. This is evident following recent trials carried out by EMI Systems & Weapons Division, Middlesex, with their newly developed "low light" television equipment.

The television camera can quickly scan large underwater areas where visibility is poor and transmit clear pictures of the sea bed to a mother ship on the surface where they can be viewed and recorded. The television equipment will be housed in a midget submarine capable of depths down to 3,000ft.

The "low light" television camera used in the trial is claimed to be the smallest in Britain, measuring 128 × 128 × 152mm. Its ability to obtain clear pictures in very low lighting conditions is provided by an E.M.I. Ebitron tube. This intensifier-vidicon is 300 times more sensitive than a normal 26mm vidicon tube.

### COMPUTER NURSE

THE United Birmingham Hospitals have received approval from the Department of Health and Social Security to proceed with the purchase of a UNIVAC 418-111 computer as part of the Department's experimental programme in hospital computing. Delivery will be made early in 1972 and specially designed accommodation to house it is nearing completion at the Queen Elizabeth Medical Centre. The first real-time application is expected to go live early in 1973.

The initial configuration will provide for complete patient administration and laboratory reporting systems for the Queen Elizabeth Hospital. It is planned to introduce other experimental systems such as laboratory requesting, drug prescribing, nursing records, physical examination of the patients and other medical applications at later stages in the project.

### NORTH MIDLANDS READERS *Please note*

A short course of six evening lectures entitled "Practical Electronics" will be held at North Staffordshire Polytechnic, College Road, Stoke-on-Trent, commencing Wednesday, January 12. The lecturers include well-known contributors to this Magazine.

Further details will be given next month.

## SPECIAL PURCHASE!


**BRAND NEW FM MULTIPLEX STEREO DECODER UNITS.** Manufactured by PHILIPS, Size 2 1/2" x 1 1/2". All transistor 24V, at 6mA. Supplied pre-aligned with full circuit diagram and connection details. 24 each. Post free.

**LEAK MK 1 TRANSCRIPTION PICK-UP ARMS.** Using the world famous gimbal pivot system. Complete but less pick-up head. £2.50. P. & P. 20p.

**INPUT MATCHING TRANSFORMER.** Beautifully made in heavy Mu-metal cylindrical case for minimum hum pick-up. Size 1 1/2" high x 1 1/4". Ratio 150:1 approx. Especially suitable for matching dynamic or ribbon mikes or pick-up from low to high impedance or vice versa. 75p each. Post Free.

**BLACK ANODISED 16g. ALUMINIUM HEAT SINKS.** For TO3, complete with mica's and bushes. Size 2 1/2" x 3". 25p pair. P. & P. 2p.
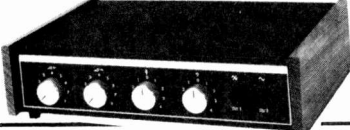
## HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



**NEW IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED PRINTED CIRCUIT BOARD FOR EASY CONSTRUCTION**

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board, attractive front panel, knobs, wire, solder, nuts, bolts, no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response 1.3dB 12-20,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth 1.3dB 12-15,000Hz. Bass boost approx. to 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide 8" deep 2 1/2" high. Fully detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

**PRICES** AMPLIFIER KIT, £1.50 P. & P. 15p.  
POWER PACK KIT, £3 P. & P. 30p.  
CABINET, £3 P. & P. 30p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

*Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discosque systems, etc.*

**SPECIAL PURCHASE OF MANUFACTURER'S GURANTEED** All Transistor 10M under head with twin A.M. Gang incorporated. Beautifully engineered with precision geared reduction drive. F.M. R.F. Transistor, oscillator/Mixer and first I.F. stage (10.7 Mc/s output) with optional APC connection. Built on printed circuit panel and fully screened. Extremely stable over range 88-160 Mc/s. Brand new and pre-aligned. Size 2 1/2" H. x 1 1/2" W. x 2 1/2" D. For 6V D.C. or 2.8mA. A.M. Gang fitted with trimmers which can be connected to standard A.M. aerial and oscillator circuits if required. LIMITED NUMBER, only £2.25 post free. Connection details supplied.

**TELESCOPIC AERIALS WITH SWIVEL JOINT.** Can be angled and rotated in any direction. 5 section Lacquered Brass. Extends from 6in. to approx. 22 1/2in. Maximum diameter 1/4in. 25p each. P. & P. 5p.

**BRAND NEW MULTI-RATIO MAINS TRANSFORMERS.** Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-60V half wave at 1 amp or 10-10-10, 20-0-20, 30-0-30V, at 2 amp full wave. Size 3in. 3 1/2in W x 3in D. Price £1.75. P. & P. 30p.

**MAINS TRANSFORMER.** For transistor power supplies. Pri. 200/240V, Sec. 9-0-9 at 500mA. 70p. P. & P. 15p. Pri. 200/240V, Sec. 10-0-10 at 1 amp. 85p. P. & P. 15p. Pri. 200/240V, Sec. 10-0-10 at 2 amp. £1.38. P. & P. 30p. Tapped Primary 200-220-240V, Sec. 21-5V at 500mA. 65p. P. & P. 15p.

**4 AMP BATTERY CHARGER TRANSFORMER** Brand new. For 6 or 9V. 24 Pin. Secondary volts r.m.s. off load 0 and 16.5V. Overall size approx. 2 1/2in x 2 1/2in x 3in. Weight 3lb. Limited number at £1.35. P. & P. 35p.

**Open 9-5.30 Monday to Saturday**  
**Early closing Wed. 1 p.m.**  
*A few minutes from South Wimbledon Tube Station*

## SPECIAL OFFER!! HI-FI LOUDSPEAKER SYSTEM

Beautifully made peak finish enclosure with most attractive Tygan-Vynair-front. Size 16 1/2in high x 10 1/2in wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

**Our Price £8.40** Carr. 65p.

CABINET AVAILABLE SEPARATELY £4.50. Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £8.50. Carr. 60p.

### LOUDSPEAKER BARGAINS

5in 3 ohm 80p. P. & P. 15p. 7 x 4in 3 ohm £1.05. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 6in 3 ohm with high flux magnet £1.62. P. & P. 20p. E.M.I. 13 x 8in 3 ohm with high flux ceramic magnet £2.10 (15 ohm £2.25). P. & P. 30p. E.M.I. 13 x 8in, 3 or 8 or 15 ohm with two inbuilt tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 13" x 8" twin cone (parasitic tweeter) 8 ohm £2.25. P. & P. 30p.

**BRAND NEW.** 12in 15w H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiLux ceramic ferrobar magnet assembly £5.50. Guitar models: 25w £6.50, 35w £8.50. P. & P. 35p each.

**E.M.I. 3in HEAVY DUTY TWEETERS.** Powerful ceramic magnet. Available in 3, 8 or 15 ohm 90p each. P. & P. 15p.

**13in "RA" TWIN CONE LOUSPEAKER** 10 watts peak handling, 3, 8 or 15 ohm, £2.20. P. & P. 30p. **35 ohm SPEAKERS 3".** ONLY 63p. P. & P. 15p. **VYNAIR & REXINE SPEAKERS & CABINET FABRICS** approx. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

**SPEAKER CABINET BARGAIN** Beautifully made all wooden construction medium walnut front, gold anodised expanded aluminium grille and dark sides. Approx. size overall 11 1/2in high x 5in deep x 13 1/2in wide at base. Battle out unit for 8in speaker. Could accommodate amplifier or radio together with speaker. FEW LEFT ONLY £1.38 post free.

## HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexion ear-muffs. Wired and fitted with standard stereo 1/4in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. PRICE £2.95. P. & P. 15p.

**SINGLE HEADPHONE.** With aluminium headband. Approx. 200 ohm. 25p. P. & P. 8p.

**CRYSTAL MIKES.** High imp. for desk or hand use. High sensitivity. 93p. P. & P. 8p.

**HIGH IMPEDANCE CRYSTAL STICK MIKES.** OUR PRICE £1.05. P. & P. 8p.

**GENERAL PURPOSE HIGH STABILITY TRANSDUCER PRE-AMPLIFIER.** For P.T. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 26dB. Solid encapsulation size 1 1/2 x 1 1/2 x 1/2in. Brand new - complete with instructions. Price 85p. P. & P. 13p.


**BRAND NEW E.M.I. LIGHTWEIGHT PICK-UP ARM WITH ARM REST.** Fitted mono t/o stylus and cartridge for LP/78, ONLY £1. P. & P. 8p.

**QUALITY RECORD PLAYER AMPLIFIER MK II** A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w. x 3 1/2" h. Ready built and tested. PRICE £5.75. P. & P. 40p. ALSO AVAILABLE mounted on output transformer and speaker ready to fit cabinet below. PRICE £4.98. P. & P. 50p.

**DE LUXE QUALITY PORTABLE R/P CABINET MK II** 1/2net motor board size 14 1/2in., clearance 2in. below. 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. PRICE £4.75. P. & P. 50p.

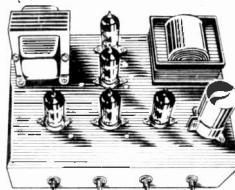
## 10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84, ECC83, EPP6 and E280 rectifier. Simple instruction booklet 13p (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 55p. Also available ready built and tested complete with std. input sockets, £9.97. P. & P. 55p.



**FANTASTIC "POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER** Size only 1 1/2in x 1 1/2in x 1 1/2in deep. Weight only 190g. Can replace cone speakers in any application and is particularly useful for those with limited space. Extremely rugged and shockproof. Operating temperature -20°F to +175°F. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

## DE LUXE STEREO AMPLIFIER

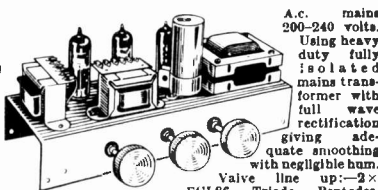


A.C. mains 200-240 volts. Using heavy duty fully fitted 4:1 A.C. mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up 2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w. x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. Price £8.92. P. & P. 45p.

**4-SPEED RECORD PLAYER BARGAINS** Mains models. All brand new in maker's packing. **LATEST B.S.R. C109/A21 4-SPEED AUTOCHANGER.** With latest mono compatible cartridge £6.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p. **SUITABLE PLINTH UNIT FOR ABOVE** with rigid plastic cover. £5.75 complete. P. & P. 25p. **LATEST GARRARD MODELS.** All types available 1025, 2025, SP25, 3000, AT60, etc. S.A.E. for latest Prices! **PLINTH UNITS** cut out for Garrard Models 1025, 2025, 2000, 3000, 3500, etc. With rigid transparent plastic cover. Special design enables above models to be used with cover in position. Also suitable for housing AT60 and SP25. OUR PRICE £5.75 complete. P. & P. 50p.

**LATEST ACOS GP91/18C Mono Compatible Cartridge with stylus for LP/EP/78.** Universal mounting bracket. P. & P. 8p.

**100% TONE STYLUS COMPATIBLE STEREO CARTRIDGE** with stylus. Diamond Stereo LP and Sapphire 78. ONLY £6.50. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p. **LATEST RONETTE T/O Stereo Compatible Cartridge for LP/EP/78/78.** £1.63. P. & P. 10p. **LATEST RONETTE T/O Mono Compatible Cartridge for LP/EP/78 mono or stereo records on mono equipment.** £1.50. P. & P. 10p.

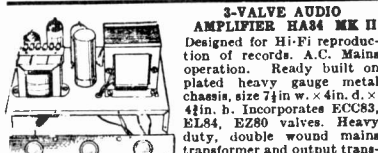

**3-VALVE AUDIO MK II AMPLIFIER HA34 MK II** Designed for Hi-Fi reproduction of record and A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2in. w. x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

**HSL "FOUR" AMPLIFIER KIT.** Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

**HARVERSON'S SUPER MONO AMPLIFIER** A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. AC mains 200/240V. Supplied absolutely Brand New, completely wired and tested with good quality output transformer. FEW ONLY. **OUR ROCK BOTTOM BARGAIN PRICE** £2.75 P. & P. 35p

**HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES** A must for servicemen and home constructors. 1971 edition including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

**HIGH GRADE COPPER LAMINATE BOARDS** 8 x 6 x 1/4in. FIVE for 50p. P. & P. 13p.

# HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)  
PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

# NEW

## from Goodmans for constructors


### Din 20 Kit

20 watt, high fidelity loudspeaker kit contains all parts necessary to complete the system, except timber and other material for the cabinet itself, with detailed, illustrated instructions.

**Specification:** 20 Watts DIN, 4 ohms impedance, 8 ins bass unit, dome HF radiator, crossover frequency 4,000 Hz.




### Axent 100

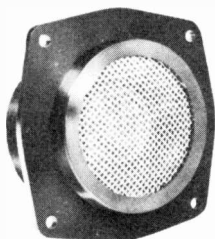

Dome HF Radiator with integral crossover. Capable of high frequency sound reproduction with negligible distortion in systems rated up to 30 Watts DIN, this 'state of the art' drive unit has an integral crossover which cuts frequencies below 3kHz at a rate of 12dB/Octave.
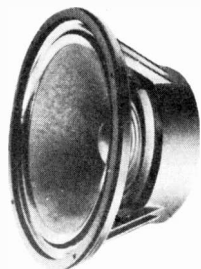
### Audiom 100

12 inch high fidelity bass loudspeaker. For use as a bass unit in two-way systems, the sensitivity and high frequency roll-off of the Audiom 100 has been tailored to match the Axent 100.



# Goodmans

Please send Free leaflets on Constructors Equipment

Name .....  
Address .....  
..... PE12

**Goodmans Loudspeakers Ltd.,**  
Downley Road, Havant, Hampshire PO9 2NL

# JERMYN

## 50p BARGAIN PACKS

All fully coded, all from well-known manufacturers and now available, while stocks last, at better than bulk-buyer's prices! Cash with order only.

### THIS MONTH:

<b>2N2926</b> (Red)	NPN Silicon Transistor Hfe 55-110	8 for 50p
<b>C6U</b>	1.6 amp general purpose 25V SCR in TO5 case	3 for 50p
<b>D16P4</b>	(Equals 2N5306) Darlingtion transistor Hfe min = 7000	3 for 50p
<b>2N3390</b>	Silicon NPN ultra high gain transistor Hfe 400-800	3 for 50p
<b>2N3391A</b>	Silicon high gain low noise transistor (better than BC109)	3 for 50p


Post and packing 10p for 1 or 2 packs; 3 packs or more post free.

Order any quantity, till sold (but we regret packs cannot be subdivided).

P.O. or Cheque payable Jermyn Industries,  
Vestry Estate, Sevenoaks, Kent.



# JUST A SECOND HOME CONSTRUCTOR

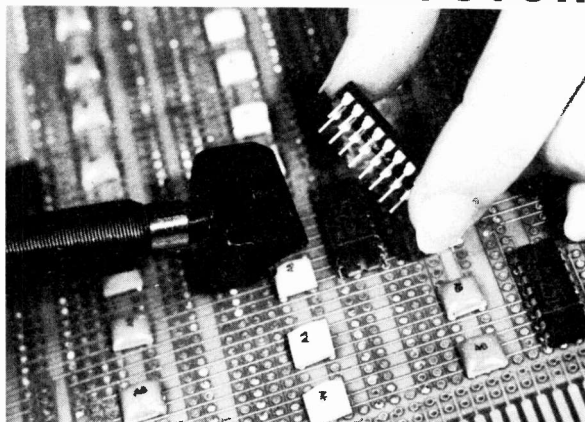

Yes, about a second, to remove dual-in-line I.C. and T.O.5 type transistor from those ex-computer printed-circuit boards, experimental circuits, etc.

DILKIT comprises a high performance soldering iron, long-life bits specially shaped to unsolder all leads of a component in a single operation, and a length of solder-absorbing wick.

Automatic component extractors also available.

TO: ORIENTATION LTD., MAYFIELD, COVERACK, CORNWALL.  
PLEASE SEND

	DILKIT £7-40	
	DIL EXTRACTOR £2-25	
	T.O.5 EXTRACTOR £2-25	
CHEQUE/P.O.	VALUE	



## SURPRISE SURPRISE!!

The decision by RCA to pull out of the computer mainframe business sent a chill down the spine of the United States' electronics industry—and of Europe too.

Everyone was taken by surprise. It happened almost exactly a year after RCA chairman Robert W. Sarnoff had announced firm plans for a frontal attack on the market held so lucratively by IBM. As recently as July, Sarnoff was still denying that RCA had any intention of pulling out.

The RCA debacle follows a similar withdrawal by U.S. General Electric a year earlier. GE's move, however, was well regulated and involved lengthy negotiations before the sale of its computer interests to Honeywell.

Industry experts on both sides of the Atlantic are asking themselves: if giants like U.S. General Electric and RCA can't stand the pace, who can? Except, of course, the almighty IBM.

Unstoppable IBM has 70 per cent the U.S. domestic market and not far short of that figure in the rest of the world. RCA's share was under 4 per cent with a growth target of 10 per cent of the market by 1975. The crunch came when it was realised that another £200 million of capital, on top of the £200 million already spent, would be required before breaking into profit.

Now the RCA market share will be distributed among the survivors with the bulk going to IBM, still further tightening IBM's stranglehold.

## THE AFTERMATH

Britain's ICL is involved only through System 4, a development of RCA's Spectra 70 Series. ICL say they will remain unaffected. But Siemens in Germany will be affected because they rely strongly on close technical links with RCA.

RCA customers have been told that all existing orders and service contracts will be honoured. But the demise of two major mainframe manufacturers in a period of 16 months will influence new buyers toward the most stable source which means even more business for IBM.

Component suppliers to RCA such as Motorola, Signetics and Advanced Memory Systems will all suffer from the closure. Some smaller suppliers stand to lose 10 per cent of their total business.

At the time of writing there was no firm news that RCA had been able to sell its computer interests either in whole or in part. In the present depressed state of the computer market few firms are interested in acquiring extra plant and manufacturing capacity.

One possibility emerging from the debacle is that Britain's ICL and Germany's Siemens could now get together to form a new and potentially extremely powerful computer force in Europe.

## DATA SATELLITE

The computer industry may be suffering at the moment but the demand for data processing and data transmission will continue to increase at a growing rate. In 1970 there were 14,000 data terminals in Britain. By 1980 there might be, and probably will be, 300,000. This figure will be matched by other major European nations and so far no international agreements on data network standards have been made.

An interesting new development is a study contract awarded to Marconi Communications Systems Ltd. by the European Space Research Organisation (ESRO). The idea is that data links should be through a geo-stationary satellite used in conjunction with large numbers of small and inexpensive earth terminals.

The earth terminals would have dishes no larger than 9ft in diameter sited within 100yds of the data terminal. Use of such a system, dedicated entirely to data transmissions, would obviate many of the difficulties of international connections through existing public telephone and data networks where data rates are comparatively low due to line variations.

The preliminary study, involving analysis of present and future traffic, prospective users and costs of the system, should be completed by April 1972

## WHERE THE GIANTS MAY GO


Although the great electronic exhibitions aimed at industry such as the IEA and ILECS at Olympia are by no means on the way out, increasing costs have been forcing companies to look more closely at the less expensive small shows which tend to be more cost-effective.

One of the brightest operators in the field is John McNeill, managing director of Electromation Exhibitions Ltd. I have just seen the company's forward programme with electronics shows starting at Birmingham in November and moving round the country to Harrogate, Southend, Stevenage, Portsmouth, Croydon, Glasgow, Dublin, Bristol, Manchester and back to Birmingham in November 1972. This is an impressive programme which includes, apart from exhibitor stands at each venue, a technical convention. Admittance is reserved for professional engi-

neers and you need an invitation before you can get admission.

Another bright operator in small exhibitions is Evan Steadman who has already sold out for his Seminec due to be held next April. This one is for semiconductor manufacturers. Yet another is Gordon Johns who organised the successful Compec '71 computer peripheral exhibition in London last September.

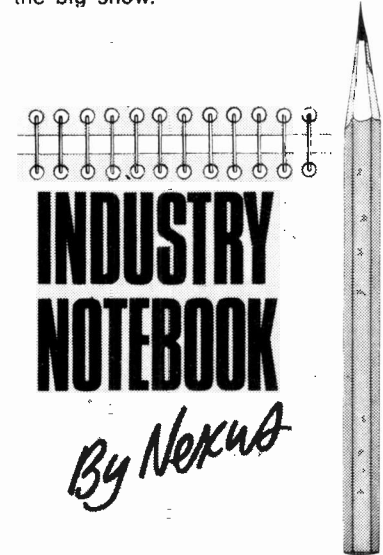
It is too early to predict the effect of this type of exhibition on the IEA at Olympia next year but one thing seems certain. With Mullard, TI, Fairchild, RCA, Emihus, Ferranti, to name but a few who have already booked for Seminec and its accompanying technical symposium, it seems clear that the bulk of the semiconductor companies have already opted out of the big show.



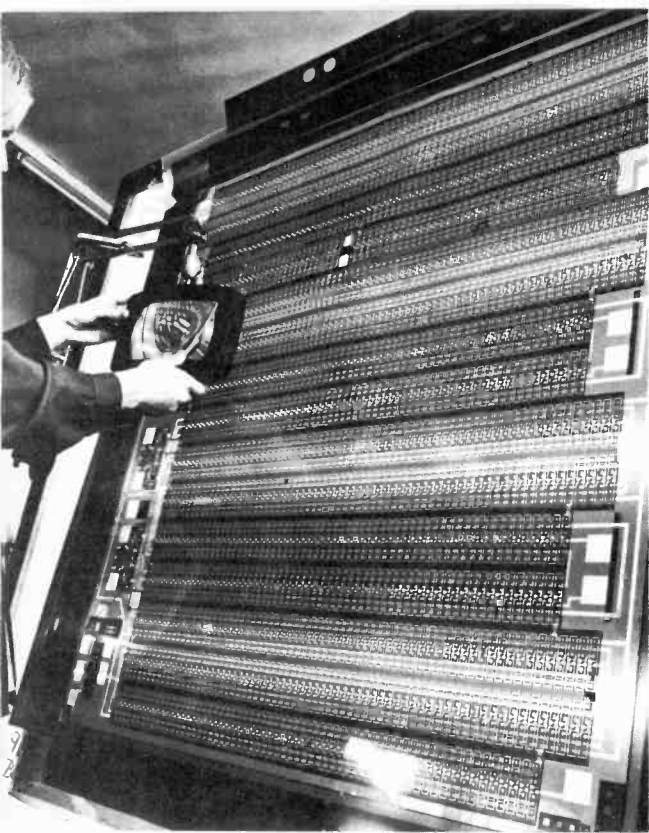
## BRIGHTER OUTLOOK— BUT SLOW

Sir John Clark, chairman of Plessey, thinks the worst may be over but it will be a long haul back to the halcyon days of pre-recession. Ernie Harrison, Rascal chairman, believes that it could be another 18 months before business takes off in any big way. Dr F. E. Jones, managing director of Mullard was not exactly cheerful when we last met despite the boom in colour TV sales.

On the whole, however, I have found most industry leaders optimistic. Smaller companies with their greater level of flexibility have in many cases proportionately weathered the storm better than the giants. But 1972 could see further "re-structuring" of the industry through takeover or merger. On one thing they all agree. Even if the bottom has now passed, don't expect a dramatic revival. Recovery will be slow.



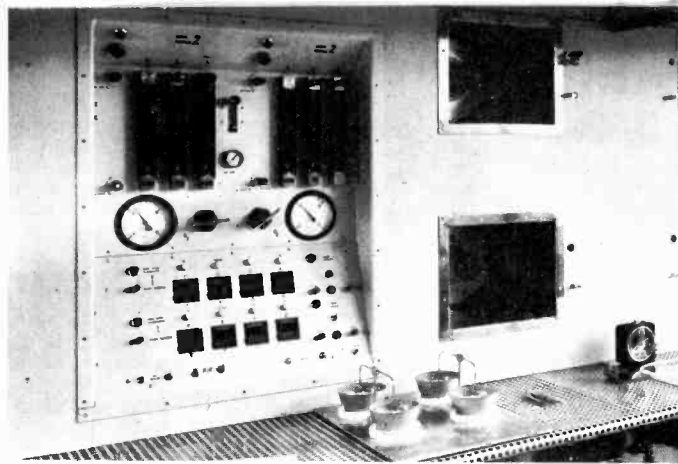Physical inspection of rubyliths (artwork) of a 1,024-bit CDI shift register



Part of the pre-production line for CDI

## New LSI Combines Logic and Linear Functions on one chip

How does the thought of a high performance computer on a single slice or even a chip strike you—impossible? Well it is not as far fetched as it may seem. While we are just getting accustomed to MOS integrated circuit technology, along comes another—the CDI process of producing LSI (large scale integration).

CDI (collector diffusion isolation) is a simple bipolar process originally developed in the Bell Laboratories in the U.S.A. and has now been further developed by Ferranti at Manchester for large scale




## Ultrasonic Car Safety Belt System

ONE of the results of a new car safety belt system, developed by Mullard and the Ford Motor Co., means that even the car thief will have to strap himself in if he wishes to make off with his "booty". The belt must not only be fastened but also be correctly positioned across the wearer.


As the block diagram shows, before the ignition will function the driver must occupy his seat, activating a pressure switch fitted beneath it, buckle the belt across his lap and close the belt switch. Provided the belt is worn correctly a 40kHz signal emitted from an ultrasonic transmitter, mounted in the belt, is received by a detector built in the windscreen pillar, which in turn completes the ignition circuit. If the front passenger seat is occupied then a 50kHz signal must be received from the passenger's



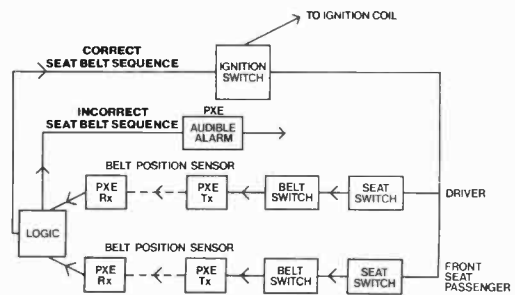Layout of the car safety belt system as installed in a car. Note the narrow ultrasonic beam directed at the receiver mounted in the windscreen pillar



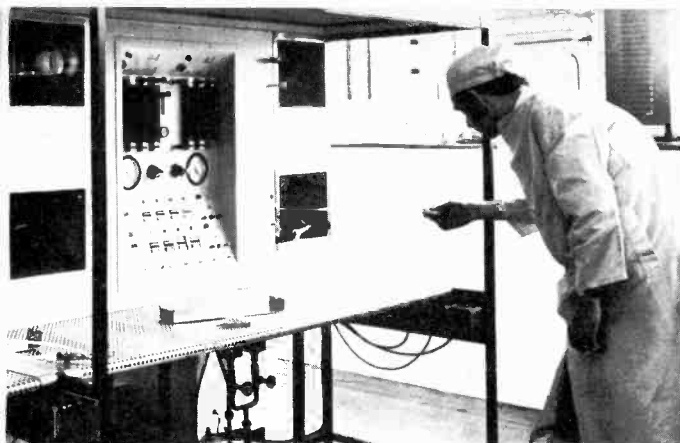Block diagram of the car safety belt system




*bipolar integrated circuits at Ferranti*

production at an economic cost. This is said to be the first time that LSI has become a practical proposition, combining the high complexity of MOS with the performance advantages of bipolar technology.

The breakthrough is in the combination of both high speed switching logic and linear capability for a common supply of 5V on the same monolithic chip. The system is completely compatible with existing TTL i.c.s.

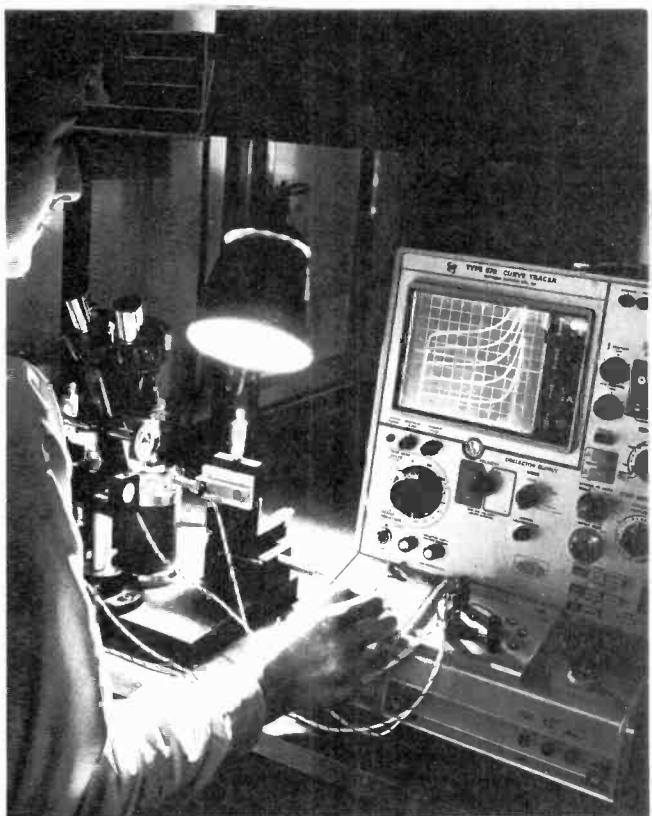Only five masking operations are required compared with nine steps involved in current bipolar processing. It is expected that this new bipolar LSI technology will be used where digital and analogue control, computers and telecommunications already require complex and sophisticated circuitry.



*An operator carrying out a process control check using a curve tracer which shows the collector-emitter characteristics of a CDI transistor in a digital array*

# NORAMA

safety belt before the ignition switch will be functional.

If the correct sequence has not been carried out a logic circuit will trigger an audible and visible alarm mounted on the dashboard.

The system can be arranged so that if the belt is unfastened while the car is moving the ignition is not immediately affected. Instead, the alarm is sounded and if, at the end of a specified time, the belt still remains unfastened, the ignition will then be cut out.

For very short operations, such as parking or garaging the car, the logic arrangement can be adjusted to allow for car movement in first or reverse gear for a specified time without the driver being belted.


As a method of enforcing the wearing of safety belts by driver and passengers, thus cutting down the death and injury toll on the roads, this contribution to road safety should be closely looked at by the Police and the Ministry of Transport.



*The ultrasonic transmitter (top) and receiver circuit boards*

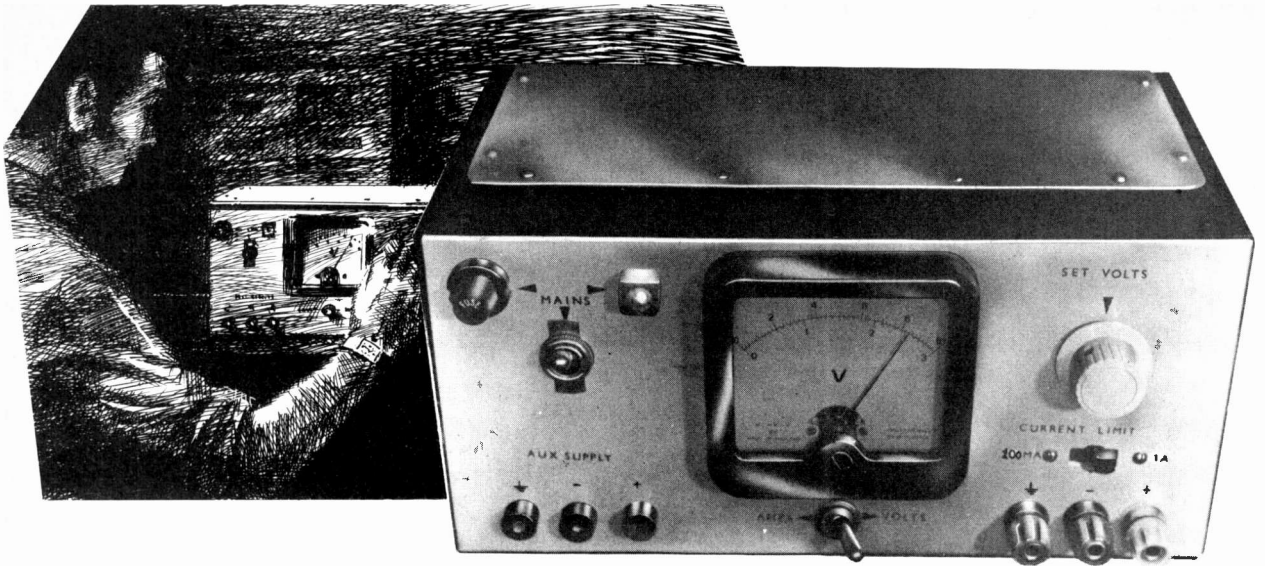*The ultrasonic transmitter mounted on a car safety belt*





# Labpack Power Supply

BY H.T. KITCHEN

THE stabilised power supply to be described was designed and built to provide a power source for transistorised equipment undergoing development. As such, it had to fulfil certain basic requirements.

A long and varied experience of development and service work had shown the need for a power supply capable of being varied from near zero to a maximum of some 25V, with a maximum current capacity, within this voltage range, of 1A.

A further requirement was that the output voltage had to be regulated. The output current also had to be controlled, so that even if the load terminals were made short circuit, the maximum current rating could not be exceeded.

The final requirement was that the maximum current output should be capable of being adjusted

to values less than the 1A maximum. In the prototype, two switched ranges of 1A and 100mA are provided.

A block diagram of the power supply is shown in Fig. 1 which should be studied in conjunction with the circuit diagram of Fig. 2.

## SERIES REGULATOR

The regulator element of this design is of the series type and is made up of the transistors TR5, TR6 and TR7.

This is a compound configuration where TR5 controls the base to emitter voltage of the output pair TR6 and TR7. The base feed resistor of TR5 also functions as the collector load of TR2. This transistor, together with TR1, constitute a differential amplifier.

## DIFFERENTIAL AMPLIFIER

The differential amplifier provides an output voltage which is proportional to the difference of the input voltages applied to the transistor bases. At the base of TR1 is connected a fixed Zener voltage which is derived from a double diode rectifier and filter circuit.

This stable reference at one base means that any changes in the output voltage—either up or down—will be fed back by way of VR2 to provide a collector current change through R5. If the current flow is low the volt drop at this resistor is low, which corresponds to a movement of the base potential of TR5 towards the collector potential. Increased emitter current therefore flows, and as this current is into the bases of TR6 and TR7, their emitter currents also increase.

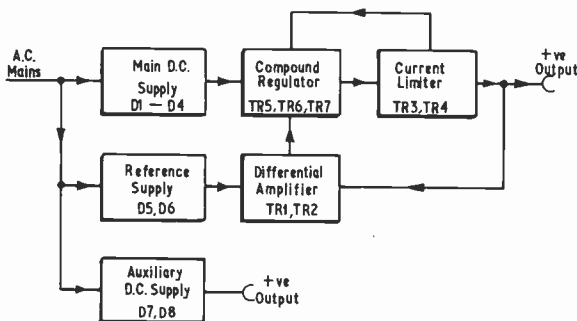


Fig. 1. Block diagram of power supply

If the output load is a resistive one, this will result in an increase of output voltage. A converse feedback action will decrease the output.

The overall gain of TR2, TR5 and the output pair is very high, and very small changes in output voltage can be sensed and automatically corrected. Rapid changes in output voltage, corresponding to a residual 100Hz ripple, or the signal frequency of a connected high power amplifier, can also be sensed and corrected. In this instance, feedback is via C5, again to the base of TR2 which treats it also as an error signal.

### CURRENT LIMITING

The current limiter circuit comprises TR3 and TR4, in conjunction with VR3, R8 and VR4 and R10.

The transistor TR3 is connected so as to function as a cheap form of Zener diode which fixes the emitter potential of TR4. Under no load or small load conditions TR4 is reverse biased and does not pass any collector current.

Dependent on the switch position of S2 and limit setting of VR3 or VR4, load current limiting occurs when the voltage drop across these resistance combinations is sufficient to drive TR4 out of its cut-off state.

With TR4 conducting the volt drop across its shared load resistor R5 will increase. The polarity of this voltage is such as to reduce the  $V_{be}$  of TR5 and so reduces the emitter current passed by TR6 and TR7.

By controlling the  $V_{be}$  of TR5 it is possible to set a limit to the maximum current that can be drawn from TR6 and TR7, even if the output is short circuited.

### CHOICE OF LIMITING RESISTANCE

Since any volt drop across R8 and R10 is lost to the output voltage, and since a certain minimum voltage at the base of TR4 is necessary for reliable current limiting, the absolute minimum resistance


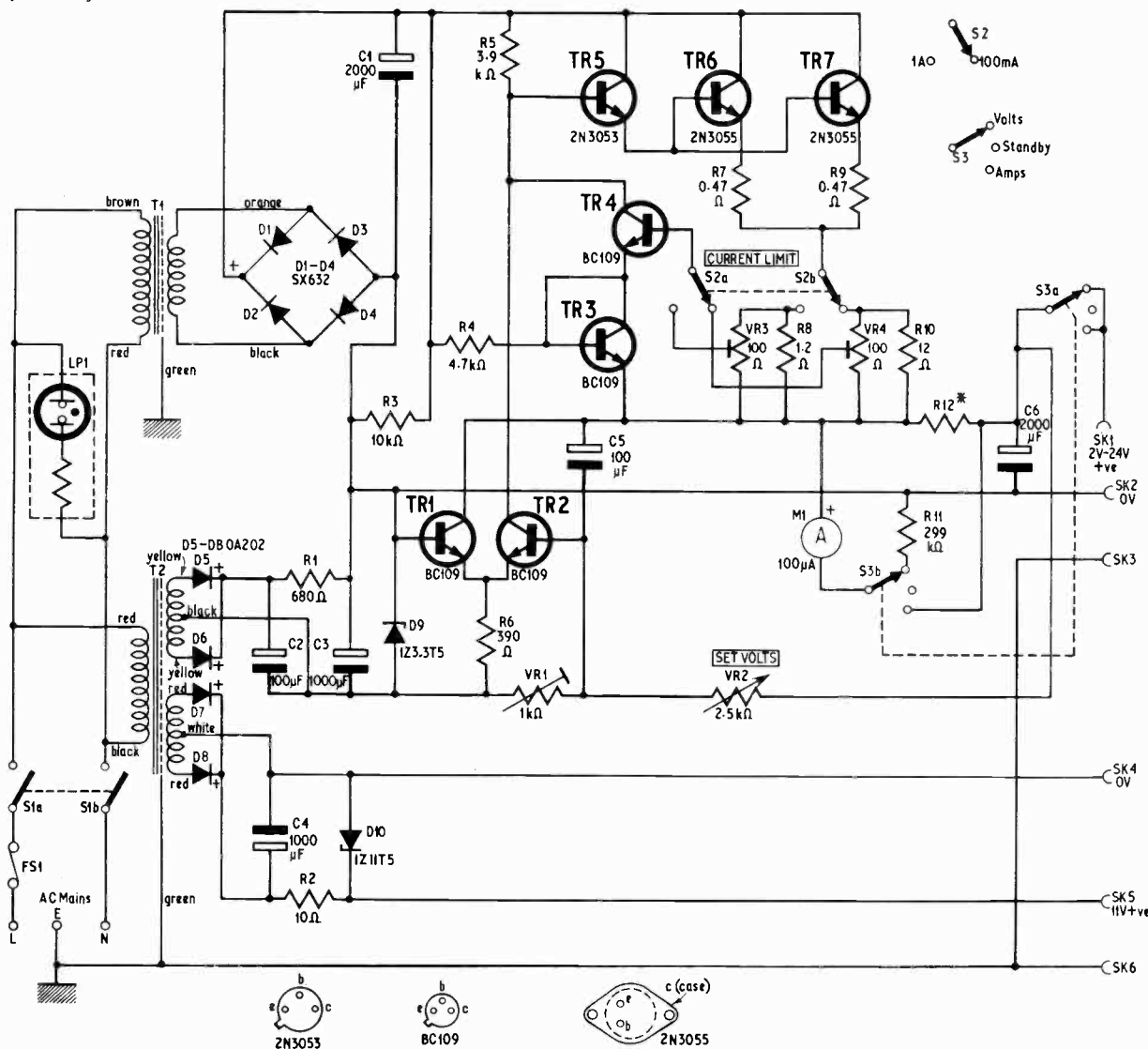


Fig. 2. Circuit diagram of power supply

# SPECIFICATION...

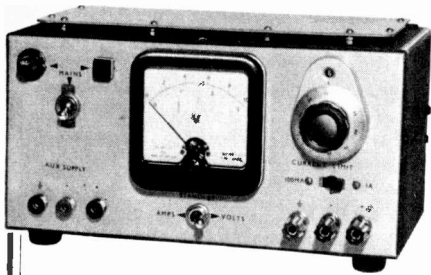

## MAIN SUPPLY

**Output Voltage** 2V to 24V  
**Output Current** 1A max  
**Current Limiting** 1A and 100mA  
**Output Resistance** 50 milliohms at 1A  
**A.C. Ripple** With no load is 250 $\mu$ V r.m.s.  
 At 20V, 1A is 5mV r.m.s.  
**A.C. Ripple**  
**Output Variation** 0.1% for 10% mains variation

## AUXILIARY SUPPLY

**Output Current** 30mA max  
**Output Voltage** 11V  $\pm$  5% at 30mA


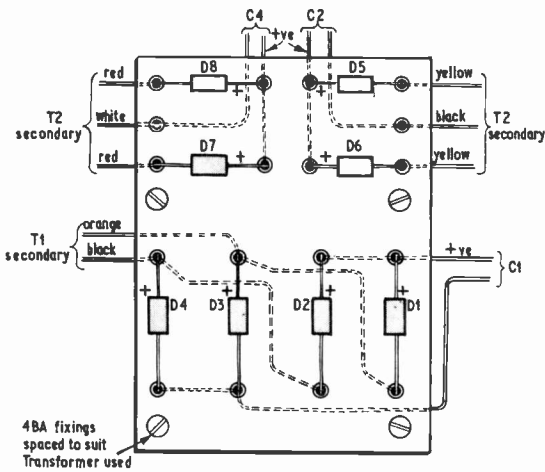
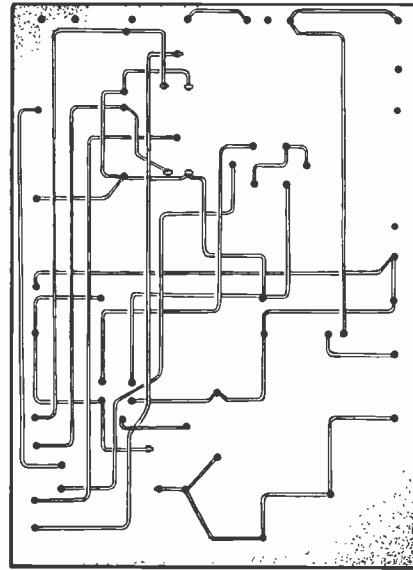
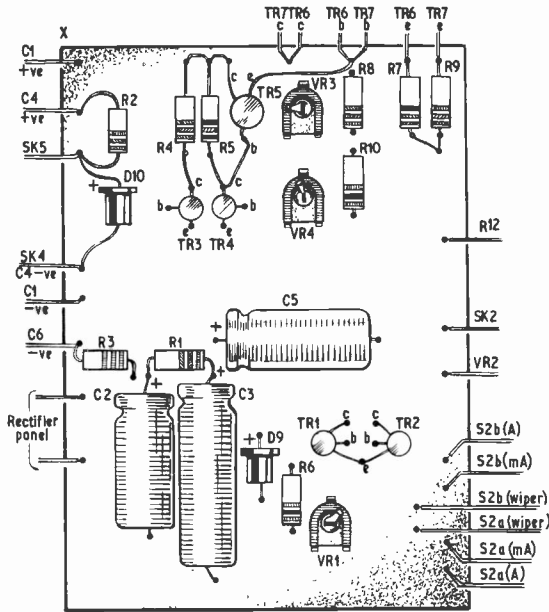


Fig. 4. Component layout and wiring of rectifier panel

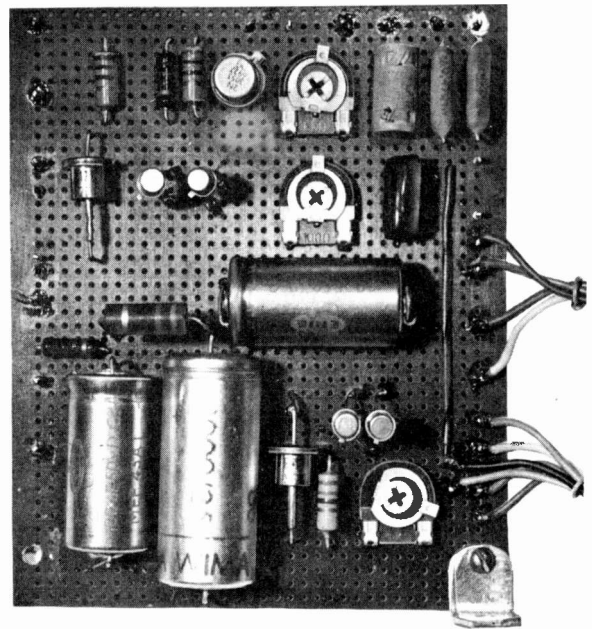

values must be selected. The exact values used may require some adjustment, dependent on the gains of the transistors used in individual versions.

The action of the limiting circuit is not an abrupt one. The limiting process on the 1A range begins at about 0.8A and gradually increases. This will affect the output resistance above and below about 1A.

## AUXILIARY SUPPLY

The transformer T2 has two windings, one of which provides the reference voltage for the differential amplifier, the other provides a stabilised 11V

## COMPONENTS...

### Resistors

R1	680Ω	R7	0.47Ω	1W	wirewound
R2	10Ω	R8	1.2Ω	2.5W	wirewound
R3	10kΩ	R9	0.47Ω	1W	wirewound
R4	4.7kΩ	R10	12Ω	2.5W	wirewound
R5	3.9kΩ	R11	299kΩ	1%	metal film (see text)
R6	390Ω	R12*	See text		

All 5%, ¼ watt carbon except where shown

### Capacitors

C1	2,000μF	elect.	50V	C4	1,000μF	elect.	50V
C2	100μF	elect.	50V	C5	100μF	elect.	50V
C3	1,000μF	elect.	50V	C6	2,000μF	elect.	50V

### Transistors

TR1-TR4	BC109	(4 off)
TR5	2N3053	
TR6-TR7	2N3055	(2 off)

### Diodes

D1-D4	SX632	(4 off)
D5-8	OA202	(4 off)
D9	1Z3-3T5	1W 3.3V Zener
D10	1Z11T5	1W 11V Zener

### Potentiometers

VR1	1kΩ	miniature	horizontal	preset
VR2	2.5kΩ	multi-turn	potentiometer	(see text)
				(R.S. Components)
VR3-VR4	100Ω	miniature	horizontal	presets
				(2 off)

### Switches

S1	Double pole	mains on/off	switch
S2	Double pole,	double throw	slide switch
S3	Double pole,	double throw	"centre-off"
			toggle switch

### Meter

M1	100μA	Type MR26	(R.S. Components)
----	-------	-----------	-------------------

### Transformers

T1	Mains transformer:	Primary 0-240V
		Secondary 26V at 1.6A
		Type X6705 (Belclere Ltd)
T2	Mains transformer:	
		Primary 0-240V
		Secondaries 26-0-26V, 23mA
		and 11-0-11V, 33mA
		Type X676X (Belclere Ltd)

### Miscellaneous

LPI	Mains neon	indicator, FS1	500mA fuse with
			holder, 3½in × 4½in
			pegboard 0.1in pitch, 2½in ×
			3½in pegboard, 0.15in
			pitch, 20 s.w.g. aluminium
			sheet cut as required
			Heat sink 4.875in × 1.05in
			extruded aluminium
			4in long with eight pairs
			of fins, SK1-SK6 insulated
			sockets (6 off)

at 33mA and can be used for powering any permanently attached piece of equipment, provided it does not draw current in excess of the rated figure.

## METER CIRCUIT

For monitoring purposes a fairly large 100μA meter is used. The one on the prototype was arbitrarily scaled 0-3 and 0-10, which is convenient, since with the multiplier R11 and shunt R12 no scale marking is necessary for the ranges 0-30V and 0-1A.

A two pole, two way, "centre-off" switch (S3) provides the measurement requirement. The centre position provides a standby facility which can be used when changing connections or reversing supply polarities.

The multiplier resistor R11, should ideally have a resistance of 299 kilohms and can be ordered with the meter. It is possible to use a 300 kilohm, 1 per cent type as the loss of accuracy is not severe.

The construction of the meter shunt will be dealt with later.

## OUTPUT TRANSISTORS

The more knowledgeable constructor will have noticed the use of two 2N3055 transistors for the series regulator TR6 and TR7, when one would suffice.

For maximum dissipation to occur in these transistors requires the output to be made short circuit and is approximately 45W. Clearly, a good heatsink and ample ventilation are required, for even under normal load conditions the dissipation can be as much as 30W.

Since the unit was intended to be used for long periods at fairly high dissipations, it was decided to use two output transistors for the reliability offered.

## CONSTRUCTION

The disposition of the components, whilst permitting the use of a relatively small cabinet, does result in a high packaging density.

Most of the semiconductors, capacitors and resistor are mounted on a 3½in × 4½in plain piece of 0.1in pitch pegboard as in Fig. 3. Veroboard can be used if desired.

The rectifier panel of Fig. 4 is a 2½in × 3½in plain pegboard of 0.15in pitch. This should be drilled for mounting to the frame of T1 (see photograph). When the rectifiers are mounted the panel should be attached to the transformer using 4B.A. nuts and bolts and ½in spacers.

## INTERWIRING

Interwiring details for the complete power supply are given in Fig. 5. The arrowed connections to the boards can be determined by referring to Figs. 3 and 4.

The front panel carries all the controls, the meter, fuse, indicator neon and output terminals (Fig. 5). On the prototype, the output voltage control, VR2 was a ten turn potentiometer, though somewhat expensive it is to be recommended since it enables precise setting to be achieved. Of course, an ordinary wirewound potentiometer can be substituted.

Transformer T2 is one of the clamp type of construction and is secured to the rear wall of the case. So too is a five way tag strip, to which the mains input is connected, and the heat sink for TR6 and TR7.

# LABPACK INTERWIRING

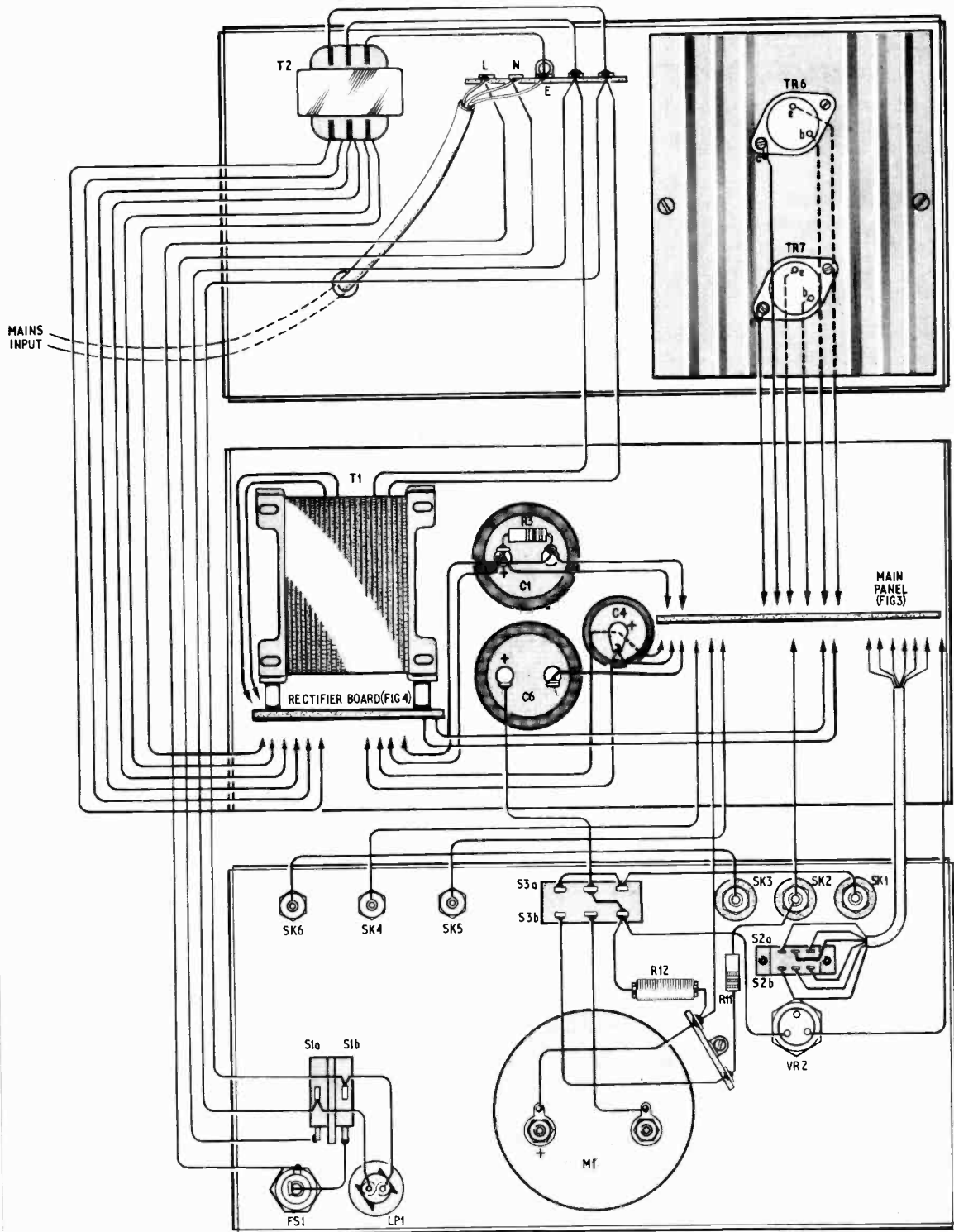


Fig. 5. Interwiring details of power supply



# Build yourself a TRANSISTOR RADIO

## NEW! ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS. MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS AND AIRCRAFT BAND.


Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. Switched earpiece socket complete with earpiece. 10 transistors plus 3 diodes. 7in x 4in speaker. Air spaced ganged tuning condenser with VHF section. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts).

TOTAL BUILDING COSTS


**£8.50**

P.P. & INS. 50p  
(OVERSEAS P. & P. £1)

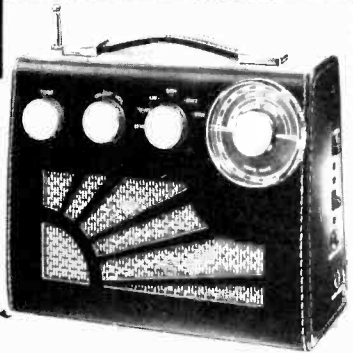

### ROAMER EIGHT Mk. I


NOW WITH VARIABLE TONE CONTROL

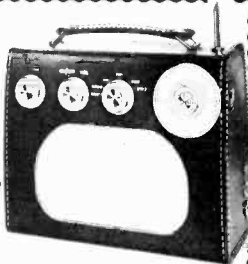

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. Switched earpiece socket complete with earpiece. 8 transistors plus 3 diodes. 7in x 4in speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)


### ROAMER SEVEN Mk. IV

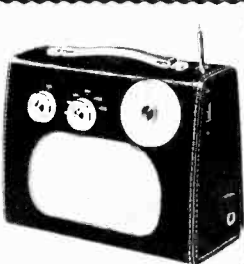

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Radio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for SW. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. 7in x 4in P.M. speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening, 30p extra.

TOTAL BUILDING COSTS **£5.98** P.P. & INS. 41p (OVERSEAS P. & P. £1)


### ROAMER SIX

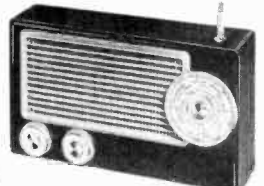

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 6in x 5 1/2in x 2 1/2in approx. Easy build plans and parts price list 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£3.98** P.P. & INS. 26p (OVERSEAS P. & P. £1)

### POCKET FIVE

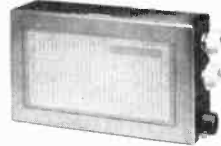

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages—5 transistors and 2 diodes, supersensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5 1/2in x 1 1/2in x 3 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£2.23** P.P. & INS. 21p (OVERSEAS P. & P. 63p)

### TRANSONA FIVE




#### NOW WITH 3in SPEAKER

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage—5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone 3in moving coil speaker. Attractive case with red speaker grille. Size 6 1/2in x 4 1/2in x 1 1/2in. Easy build plans and parts price list 10p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.


TOTAL BUILDING COSTS **£2.50** P.P. & INS. 22p (OVERSEAS P. & P. 63p)

### TRANS EIGHT

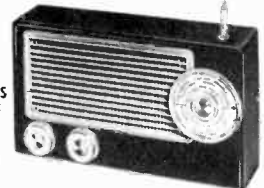

8 TRANSISTORS AND 3 DIODES  
6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5 1/2in x 2 1/2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

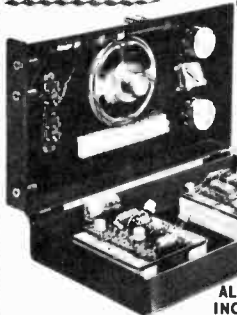TOTAL BUILDING COSTS **£4.48** P.P. & INS. 31p (OVERSEAS P. & P. £1)



### NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAMS. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 4" x 2" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs.

Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 31p (OVERSEAS P. & P. £1)

## RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD. Tel. 0234 52367

I enclose £..... please send items marked

- |               |                          |              |                          |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN    | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT  | <input type="checkbox"/> | TRANS EIGHT  | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX   | <input type="checkbox"/> |
| POCKET FIVE   | <input type="checkbox"/> | EDU-KIT      | <input type="checkbox"/> |

Parts price list and plans for.....

Name.....

Address.....

FULL AFTER SALES SERVICE

- ★ Callers side entrance Barratts Shoe Shop
- ★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday

P.E. 36

Professional receivers, supplied to Govt. Depts., Industry, Laboratories, Radio and TV Authorities, etc.

BUY DIRECT AT PRICES 15% BELOW RETAIL VALUES

THE NEW **JULIETTE** MPR 3065

is a high quality COMMUNICATIONS RECEIVER

(replaces NA 5018A)  
Recommended Price  
£42

£37-80




(Cash only) plus 62p P. & P. Complete with standard batteries and earpiece. BFO (optional extra) add £1-75.

IT NOT ONLY RECEIVES Aircraft, Shipping (VHF and SW), Taxis, Ambulances, Fire Service, TV Sound, Hams, Gas and Electric Boards, Public Services and many other radio telephone mobiles—BUT ALSO Classical Music, Pop and all that Jazz.

The MPR 3065 is a communications receiver and entertainment source in one neat, transistorised, portable package. Features a colour coded illuminated tuning dial and band selector, AFC, squelch, BFO (optional extra), large speaker, Ext. Aerial Socket. Works off mains or batteries. Size: 10½in x 7½in x 4in. 22 Transistors/Diodes.

FREQUENCIES: Medium Wave, 540-1,600Kcs.; Marine, 1.6-4.6Mcs.; FM/VHF, 88-108Mcs.; Aircraft, 108-136Mcs. (Military, Civil and Ground control); High VHF/PB, 146-176Mcs. (Commercial and Industrial RT mobiles).

MODEL MPR 3016 6 BAND

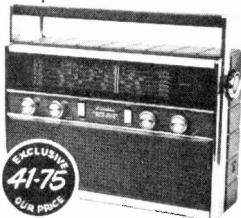

EXCLUSIVE 4-75 OUR PRICE


SAME BANDS AND FREQUENCIES AS MODEL MPR 3065 PLUS ADDED FEATURE OF SW 5.0-12.0Mcs. (with Fine Tuner). Batts. and Earpiece incl. Plus 62½p P. & P. Styled in elegant black case with luxury Chrome trim, soft padded speaker grille, die-cast sides and walnut insert. Size 8½in x 11in x 3½in. Wt. 5½lb approx. Enclose 5d stamp for reply. Trade supplied

NEW!  
FROM "LAFAYETTE"

4 Band TV Sound Battery Portable with PB Mobile Band (146-176MHz). TV sound channels 2-13, VHF/FM local and national radios, PSB RT mobiles. Our Price £27-95 Plus 50p P. & P. complete with batteries, earpiece, circ. diagram, AC adaptor socket; external aerial socket.

STOCKTON PARTNERS (Dept. "PE")  
Importers and Distributors  
Brighowgate, Grimsby, Lincs.  
Tel. 0472 64196/58815
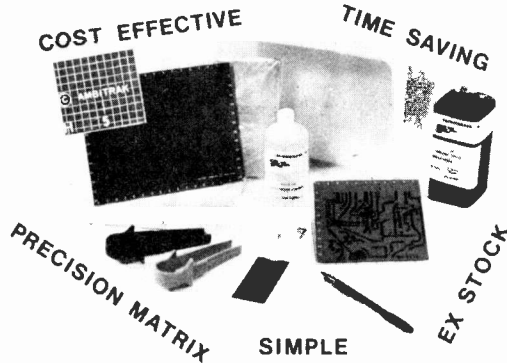
## AMBITRAK—THE NEW D.I.Y. PRINTED CIRCUIT



Ambitrak the system whereby one-off and prototype Printed Circuit Boards can be made quickly and accurately by means of a precision 0.1in matrix superimposed upon the entire copper surface. Around the edge of the board there is an alphanumeric gradation which allows precise coordinates to be located. The circuit is easily drawn onto the copper surface with an etchant resist pen and then etched using

materials provided.

2 Standard Kits are available with either S.R.B.P. or E.B.G.F. 8in x 6in Boards. Both ¼in thick and 1oz copper.

Each Kit contains 3 Boards of either type,

S.R.B.P. Kit £5-35.

E.B.G.F. Kit £6-25.

All parts of the Kit are available separately.

Patents applied for and pending.

For further information contact:

**TECHNOMARK BOROUGH GREEN · SEVENOAKS · KENT**  
TEL.: BOROUGH GREEN 3669

## THE MAZDA BOOK OF PAL RECEIVER SERVICING

by D. J. Seal. £3.50. Postage 15p.

110 INTEGRATED CIRCUIT PROJECTS FOR THE HOME CONSTRUCTOR, by R. M. Marston. £1-20. Postage 10p.

GUIDE TO PRINTED CIRCUITS, by Gordon J. King. £2-50. Postage 10p.

RCA SOLID STATE HOBBY CIRCUITS MANUAL, by RCA. £1-05. Postage 10p.

MULLARD TRANSISTOR AUDIO & RADIO CIRCUITS, £1-50. Postage 10p.

FOUNDATIONS OF WIRELESS & ELECTRONICS, by M. G. Scroggie. £1-80. Postage 20p.

RADIO & ELECTRONIC LABORATORY HANDBOOK, by M. G. Scroggie. £4-75. Postage 20p.


MAKING TRANSISTOR RADIOS, A BEGINNER'S GUIDE, by R. H. Warring. £1-10. Postage 10p.

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books  
19-21 PRAED STREET  
LONDON W2 1NP  
Phone: PADDINGTON 4185  
Closed Saturday 1 p.m.
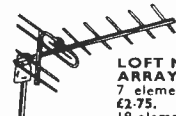
## U.H.F. TV AERIALS

SUITABLE FOR COLOUR & MONO-CHROME RECEPTION



All U.H.F. aerials now fitted with tilting bracket and 4 element reflector.

LOFT MOUNTING ARRAYS

7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75.

WALL MOUNTING c/w WALL ARM AND BRACKET. 7 element £3-25. 11 element £3-75. 14 element £4-25. 18 element £4-75. CHIMNEY MOUNTING ARRAYS c/w MAST AND LASHING KIT. 7 element £4. 11 element £4-50. 14 element £4-75. 18 element £5-25.

MAST MOUNTING arrays only 7 element £2-25. 11 element £2-75. 14 element £3-25. 18 element £3-75. Complete assembly instructions with every aerial. LOW LOSS coaxial cable 9p yd.

KING TELEBOOSTERS from £3-75. LABGEAR all band V.H.F.—U.H.F.—F.M. radio mains operated pre-amps £7-50. State clearly channel number required on all orders. P. & P. on all aerials 50p accs. 15p. C.W.O. min. C.O.D. charge 25p.

BBC-ITV-FM AERIALS

BBC (band 1) Wall 5/D £2. LOFT inverted 'T' £1-25. EXTERNAL 'H' array only £3. ITV (band 3) 5 element loft array £2-50. 7 element £3. COMBINED BBC-ITV loft 1+5 £2-75. 1+7 £3-50. WALL AND CHIMNEY UNITS ALSO AVAILABLE. Pre-amps from £3-75.

COMBINED U.H.F.-V.H.F. aerials 1+5+9 £4. 1+5+14 £4-50. 1+7+14 £5. F.M. RADIO loft 5/D £1. 3 element £3-25. 4 element £3-50. Standard coaxial plugs 9p. Coaxial cable 5p yd. Outlet box 30p. P. & P. all aerials 50p, accs. 30p. C.W.O. min. C.O.D. charge 25p. Send 5p for fully illustrated lists.

CALLERS WELCOMED  
OPEN ALL DAY SATURDAY

K.V.A. ELECTRONICS

40-41 Monarch Parade, London Rd.  
Mitcham, Surrey  
Telephone 01-648 4884


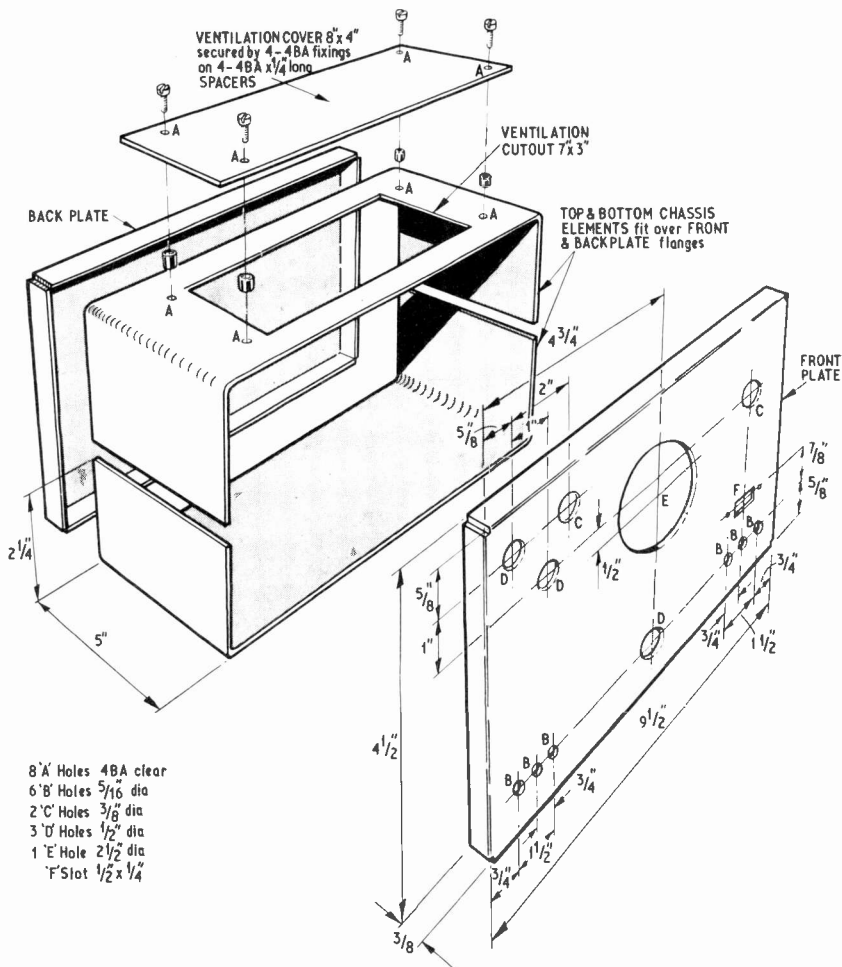
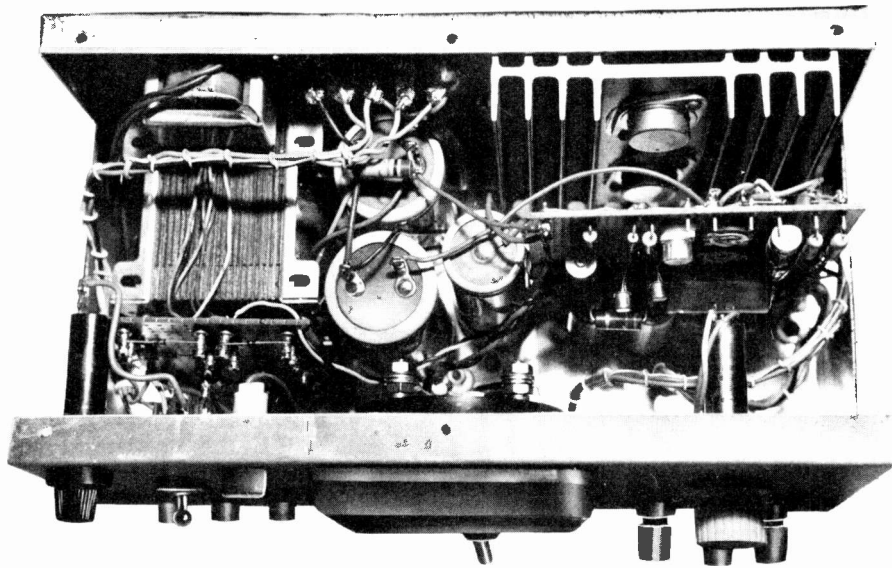


Fig. 6. Case assembly and drilling details. Self tapping screws are used for all fixings

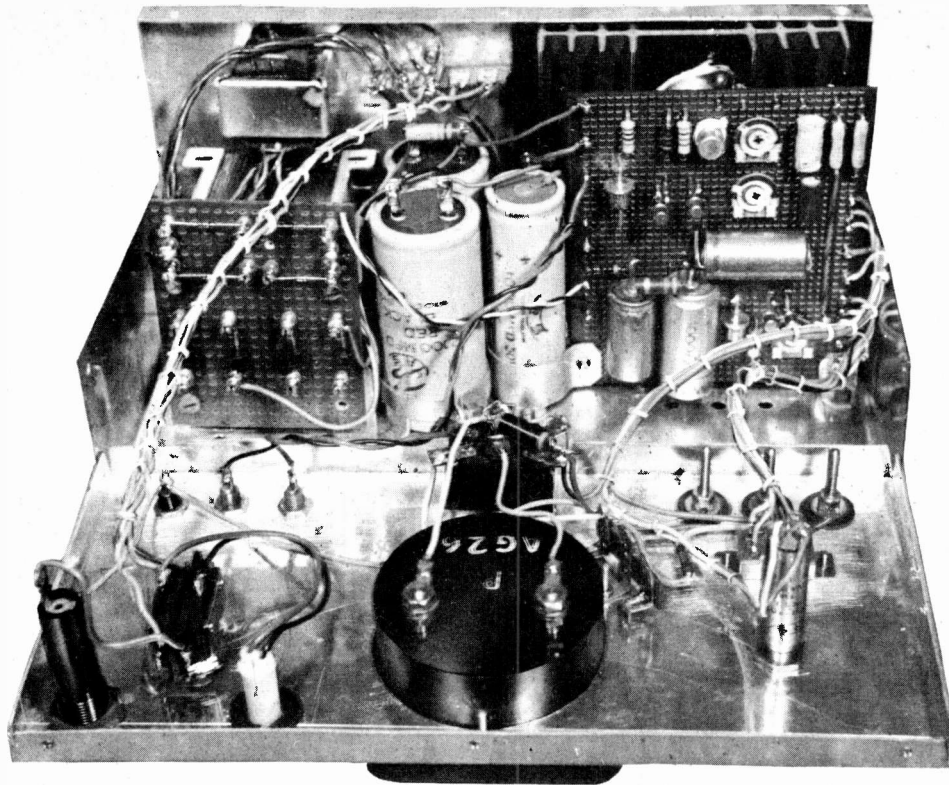

Transformer T1 and capacitors C1, C4 and C6 are mounted on the cabinet base. The main component board is attached vertically at its two lower corners, one corner by means of a small right angled bracket, the other by the clamp of C4.

### MAKING THE CASE

The cabinet used for the prototype was made from 20 s.w.g. aluminium, bent and cut as in Fig. 6. In assembling, the various panels are all secured together by small self tapping screws.

Ventilation must be adequate and is effected by means of a rectangular hole 3in  $\times$  7in cut out of the top panel. This is covered by an aluminium plate 4in  $\times$  8in separated from the top by  $\frac{1}{4}$ in spacers.

To maintain air flow through this port  $\frac{1}{8}$ in holes should be drilled below the heat sink and around T1.

### TESTING

When all of the components have been assembled and connected, a careful check for wiring errors should be made. If everything appears satisfactory set VR1 and VR2 for maximum resistance, and VR3 and VR4 to mid-range. S3 should be set for a voltage reading. A load is not required.

With the unit connected to the mains and switched on, the voltmeter should indicate. VR2 should be rotated anti-clockwise, when the voltage should fall, then rise again as VR2 is returned to its original fully clockwise position.

The preset VR1 should now be set for a maximum output voltage of 24V.

### METER SHUNT

The meter shunt, R12, is made up of resistance wire with a measured value of 0.125 ohms. Since the formula for calculating this includes the meter resistance the meter specified, or one with a resistance of 1,250 ohms, must be used.

To actually construct the shunt, a length of resistance wire, somewhat longer than is required, is connected in the position of R12. With S3 set to "Volts" adjust the output of the unit for 10V. Switch off and connect a 10 ohm, 10W resistor, in series with a multimeter switched to 1A d.c., across the output terminals.

If S3 is switched to "Amps" and the unit switched on, R12 can be adjusted so that 1A flows in the multimeter when meter M1 registers full scale deflection.

A high value resistor can be used as a mounting for the resistance wire, it being simply wrapped round the resistor body with the wire ends soldered to the resistor leads.

### CURRENT LIMIT SETTING

Having set the output voltage, attention can now be turned to the current limiting potentiometers VR3 and VR4.

With S2 switched to the 1A range a multimeter switched to the 1A d.c. range can be connected directly across the output terminals and VR3 adjusted for a reading of 1A.

The time taken for this adjustment should be a minimum as the dissipation in the output transistors is high. Adjustment for the 100mA range is identical with suitable multimeter range switching. Here, of course, VR4 is adjusted.

**0-8 Ammeter**, 2in square full vision face for flush mounting. Moving iron instrument. Ideal for charger. Price **43p** each. 10 for **£3.90**.

**9 Volt Gramophone Unit**. Collaro battery operated with pick up on unit plate. 4 speed auto-stop turnover cartridge. Price **£2.50** plus 40p post and insurance.

**Buy Time Slot Meter**. Made by Sangano Weston. 3 types—one for each coin, 21p, 5p or 10p. Price **£1.75** each plus 25p post and insurance.

**Photo Electric Kit**. Contains photo cell, relay, transistor and all parts to make light operated switch. Originally £2. Limited quantity to clear. **£1.25** plus 20p post and insurance.

**Desk/Hand Mike**. Made by Aco. Crystal insert in neat plastic case which opens at right angles for desk or opens completely for hand holding. Good general purpose mike. Price **85p** each.

**Printed Circuit Kits**. Hagato Pk. 3 facilities in kit form include printing, etching, resist removal, polishing and complete manufacture of printed sets to own specifications. Price **£1.25 + 20p**.

**4 Station Transistorised Intercom**. Solid state three transistor printed ckt. master and 3 substation push button/press talk system. 200mW output complete with installation accessories and 9V. Eveready power pack. Approx. dimensions: Master 4½ x 1½ x 2½in. Substation 3 x 1½ x 4in. Price **£2.50 + 20p**.

**Laboratory Instruments**. For horizontal use in strong black reinforced bakelite cases with screw down terminals especially suitable for experiments and demonstrations. All have precision meters (manufacturers quoted accuracy of better than 1.5%). Following available:

**D.C. Voltmeter 0-300V I.s.d.** moving coil mirror scale meter size approx. 5 x 4½ x 1½in. Price **£1.75**.

**D.C. Voltmeter, 0-30V I.s.d.** moving coil mirror scale meter. Size approx. 5 x 4½ x 1½in. Price **£1.75**.

**A.C./D.C. Milliameters 3 range**, moving iron mirror scale meter. Range selection 25, 50 and 100mA by selection switch mirror scale (coil resistance marked) size. 7½ x 5 x 3½in type 3599/1. Price **£2.75**.

**Micrommeter 100 micro amps I.s.d.** moving coil mirror scale precision meter (coil resistance marked) size 5 x 4½ x 2½in type M/109/1. Price **£3**.

**Galvanometer 20-0-20 I.s.d.** moving coil precision laboratory instrument of extremely high sensitivity (3 10-7A per division). Size approx. 6½ x 3½ x 2in. Price **£5**.

### SPARTAN Portable RADIO

Long and medium wave 7 transistor, size 6 in x 4 in x 1½ in. With larger than usual speaker giving very good tone. Built-in ferrite aerial and telescopic aerial for distant stations. A real bargain complete with leather case, carry sling, earplug and case **£3.75** plus 25p post and ins.



**Parmeko Neptune Series C. Core Transformers**. These transformers are beautifully made, steel encased, stove enamelled black, upright mounting. All have normal 50cps primary 250/240V with primary screen and are new and unused. Small quantities only of each type available as follows:

**Model 6000/79**. 275-0-275V at 330mA and 6-3V at 4-6A. Price **£4.50**. 50p post.

**Model 6000/71**. 290-215-0-215-290 at 125mA and 2 at 6-3V 6A. Price **£4.50 + 40p** post.

**Model 49**. 250V at 10mA. 6-3V at 3A. 5V at 0-75A. Price **£2 + 30p**.

**Model 47**. 200-0-200 at 9mA. 4V at 1A. Price **£4.50 + 40p** post.

**Parmeko Neptune C. Core Chokes**. These are encased and match the transformers above.

**Model 6000/78**. 4H at 500mA. **£2.50 + 40p** post.

**Model 55**. 10H at 1mA. **£2.50 + 40p** post.

**Model 49**. 10H at 70mA. **£1.50 + 30p** post.

**Model 69**. 10H at 10mA. Price **£2 + 40p** post.

### RHYTHMETRON

As featured in November issue. Electronic parts kit, less case and knobs, but including Vero panels. **£4.25p + 20p** post.

**Electronic Car Ignition**. In addition to the kits for 12V cars we can also supply systems for 6V cars. These are not kits but made up and ready to work. Price **£5.50 + 30p** post.

**Carbon Resistors**. We are now stocking these in a big way and will be pleased to quote special prices to quantity buyers. Made by Erie, Morganite or Duibler.

	Price per each
1-9	10-99
1 Watt	1p 8p 6p 5p
1 Watt	2p 18p 15p 125p
2 Watt	4p 32p 30p 275p

**Special Resistor Assortment Offer (1)**. 100 x ½W resistors made up of 2 each of 50 different values fairly evenly spaced between 1 ohm and 10 meg. Price **50p**.

**Special Resistor Assortment Offer (2)**. 1,000 x ¼W resistors made up of 20 each of 50 different values fairly evenly spaced between 1 ohm and 20 meg. Price **£4**.

**Special Resistor Assortment Offer (3)**. As offer 1 but 1W. Price **£1**.

**Special Resistor Assortment Offer (4)**. As offer 2 but 1W. Price **£8**.


**12 Way Sub-Mixture Multi-core Cable** 7-0076 copper cores each core p.v.c. insulated and of different colour. P.v.c. covered overall and approx. ¼in thick. Price **20p** per yard.

### MICROSONIC KEYCHAIN RADIO

7 transistor Keychain Radio in very pretty case, size 2½ x 2½ x 1½in—complete with soft leather zippered bag. 7 transistor, ferrite rod. Loudspeaker.

In transit from the East these sets suffered corrosion as the batteries were left in them but when this corrosion is cleared away they should work—offered without guarantee except that they are new. Price only **£1.25** less batteries plus 13p, post 6 for **£7** post free.

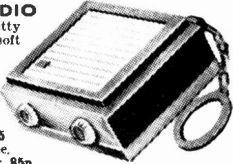
Pair of rechargeable batteries and charger **85p**.



### 24-HOUR TIME SWITCH

Made by Smiths, these are a.c. mains operated, NOT CLOCKWORK. Ideal for mounting on rack or shelf or can be built into box with 13A socket. 2 completely adjustable time periods per 24 hours, 5A changeover contacts will switch circuit on or off during these periods. **£2.50** post and ins. 25p. Additional time contacts **50p** pair.

### THE FULL-FI STEREO SIX

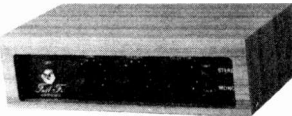

The amplifier sensation of the year

You will be amazed at the fullness of reproduction and at the added qualities your records or tuner will reproduce. Built into metal cabinet elegantly styled in simulated teak finished to blend with modern furnishings, this amplifier uses an integrated solid state circuit with an output power of 6W R.M.S. split over the two channels. The amplifier is ideal for use with normal pick-ups and tuners, it has a double wound mains transformer and ganged volume and tone controls—also switching for Mono to Stereo, tuner or pick-up. Other controls include 'treble lift and cut', 'balance' and separate mains on/off switch. UNREPEATABLE PRICE is **£29** plus 38p post and insurance.

### THIS MONTH'S SNIP

#### POCKET CIRCUIT TESTER

Test continuity of any low resistance circuit, house wiring, car electrics. Tests polarity of diodes and rectifiers. Also ideal size for conversion to signal injector (circuit supplied) **30p** or **2** for **50p**, post paid.




### TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient and quiet running. Is as fitted in Hoover and blower heaters costing **£15** and more. We have a few only. Comprises motor, impeller, 2kW, element and 1kW element allowing switching 1, 2 and 3kW, and with thermal safety cut-out. Can be fitted into any metal line case or cabinet. Only needs control switch. **£3.50**. 2kW. Model as above except 2 kilowatts **£2.50**. Don't miss this. Control Switch **35p**. P. & P. 40p.



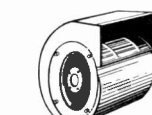
### CENTRIFUGAL FAN

Mains operated, turbo-blower type. Pressed steel housing contains motor and aluminium impeller. Motor is 1/10th h.p. giving considerable air flow but virtually no noise. Approx. dimensions 10½in wide by 12in dia. Outlet into trunking 10½in x 4½in. **£4.95 + £1**.


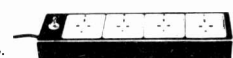
### DISTRIBUTION PANELS

Just what you need for work bench or lab. 4 x 13A sockets in metal box to take standard 13A fused plugs and on/off switch with neon warning light. Supplied complete with 7 feet of heavy cable. Wired up ready to work, **£2** less plug **£2.25** with fitted 13A plug; **£2.40** with fitted 15A plug, plus 25p post and ins.



### CAPACITOR DISCHARGE CAR IGNITION

This system which has proved to be amazingly efficient and reliable was first described in the Wireless World about a year ago. We can supply kit of parts for improved and even more efficient version, (P.W. June), price **£4.95**. When ordering please state whether for positive or negative systems. Plus 30p post.



### 2 OCTAVE MINI ORGAN

As featured in P.W. Kit of Electronic parts **£4.50** plus 20p post. Gold wire and other metal parts **£1.50**.



### 15 WATT 12in HI-FI SPEAKER

Is undoubtedly one of the finest loudspeakers that we have ever offered, produced by one of the country's most famous makers. It has a die-cast metal frame and is strongly recommended for Hi-Fi and public address. Handling 15W R.M.S.—Cone moulded fibre—Freq. response 30 10,000 c.p.s.—specify 3 or 15 ohms. Chassis dia. 12in—12½in over mounting legs. Overall height 5½in. A 150 speaker offered this month for **£3.75** plus 30p. post and ins.



### DIGITAL COUNTER TIMER

Very stable and reliable crystal controlled circuit. Capable of work in excess of 15MHz. Construction simplified by use of 15 integrated circuits. Complete kit with case **£37.50**, or construction data and price list **30p**.



Where postage is not stated then orders over **£5** are post free. Below **£5** add 20p. Semiconductors add 5p post. Over **£1** post free. S.A.E. with enquiries please.



### TREASURE TRACER

Complete Kit (except wooden battens) to make the metal detector as the circuit in Practical Wireless August issue. **£2.95** plus 20p post and insurance.

### DRILL CONTROLLER NEW 1KW MODEL



Electronically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. **£1.80** plus 13p post and insurance. Made up model also available, **£2.25** plus 13p post & p.

**Snap Action Slide Switch**. Rated 5A 240V. Made by Arrow. Type fitted in the handles of electric drills, vacuums, etc. **5p** each, 10 for **45p**.

**Numeric Tubes**. For digital instruments, counters, timers, clocks, etc. Hi-vac XN, 3. Price **£1.45** each, 10 for **£13**.

**Pressure Switch**. Containing a 15A change over switch operated by a diaphragm which in turn is operated by air pressure through a small metal tube. The operating pressure is adjustable but is set to operate in approx. 10in of water. These are quite low pressure devices and can in fact be operated simply by blowing into the inlet tube. Original use was for washing machines to turn off water when tub has reached correct level but no doubt has many other applications. **50p** each, 10 for **£4.50**.

**Papst Miniature Extractor Fans**. Beautifully made as are all Papst motors. Intended for cooling computers but suitable for any equipment. Size 4½in square and 1½in thick. Price **£2** each. Post and insurance 20p.

**Commutator Motor**, Small Size approx. 3in plus 1in of shaft, 3in high x 1½in wide, but high speed and very powerful. These motors operate from the mains. Are particularly useful as they can be speed controlled by our thyristor kit or by variable resistor. **£1** each.

**Auto Light Kit**. The circuit for this appeared in Practical Wireless, October issue. It is a simple circuit but has many uses: Parking light, porch light, etc. Uses light cell and two transistors. Complete kit, no case **95p**. Suitable case **20p**.

**Charger Kit**. Comprises of 3A transformer, 5A rectifier and a pair of hefty crocodile clips. With wiring diagram. **£1.40** plus 20p post and ins.

**24 hr. Clock Switch**. In metal case with 13A socket. Smiths movement, 2 ons and 2 ofs per 24 hours. Very neatly made and finished. Original retail price **£7** each. Few only, new and perfect. **£4.00** each.

**Neon Indicator Lamps**. With amber lens, standard type with built in resistor for mains. **10p** each, 10 for **80p**.

**Condensers**. Another addition to our range. 500µF at 50V. **15p** each, 10 for **£1.25**.

**Thermistor Bead Type**. For instruments, medical applications, etc. I.T.T. No. GL23. **75p** each, 10 for **£6.75**.

**3 Core Mains Leads**. Special offer this month is a 6ft lead with 23/38 cores and coloured according to the new code L. E. Brown—live; Yellow/Green—earth; Blue—neutral. Price **6p** each 10 for **50p**.

### DIGITAL DICE

as featured in this issue. Send S.A.E. for parts list.

### MAINS RELAY BARGAIN


Special: this month are some single, double and treble pole changeover relays. Contacts rated at 15 amps. Operating coil wound for 240V A.C. Good British Make. Ex-unused equipment. Size approx. 1½in x 1in.



Open construction  
Single pole 25p each 10 for **£2.25**  
Treble pole 40p each 10 for **£30.6**
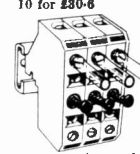
### FLEX CONNECTOR

A quick way to connect equipment to the mains safely and firmly—L, N and E. coded to new colour scheme; disconnection by plugs prevents accidental switching on; has sockets which allow insertion of meter without disconnection, cable inlets firmly hold one hair wire on up to four 7-029 cables. **85p** each.



### THYRISTOR LIGHT DIMMER

For any lamp up to 200W. Mounted on switch plate to fit in place of standard switch. Virtually no radio interferences. Price **£1.99** plus 20p post and insurance.



# J. BULL (ELECTRICAL) LTD.

Dept. (P.E.) 7, Park Street, Croydon CRO 1YD  
Callers 102/3 Tamworth Road, Croydon

# Great new OFFER from DIOTRAN

## TRANSISTORS

### BRAND NEW FULLY GUARANTEED DEVICES

AC107	15p	AF115	17p	BC140	35p	BCY31	22p	BF272	80p	EC403	15p	ORP60	40p	2N918	30p	2N2714	25p	2N3704	15p
AC113	20p	AF116	17p	BC141	35p	BCY32	25p	BF273	30p	GET880	27p	ORP61	40p	2N929	22p	2N2904	25p	2N3705	12p
AC115	17p	AF118	20p	BC142	45p	BCY33	17p	BF274	30p	MAT103	15p	ST140	12p	2N930	25p	2N2904A	30p	2N3706	12p
AC125	17p	AF120	20p	BC143	45p	BCY34	20p	BF308	35p	MAT101	17p	ST141	17p	2N1131	20p	2N2905	25p	2N3707	13p
AC126	17p	AF124	21p	BC145	45p	BCY70	17p	BF309	37p	MAT120	15p	TIS43	40p	2N1132	22p	2N2905A	30p	2N3708	8p
AC127	17p	AF125	20p	BC147	17p	BCY71	30p	BF316	75p	MAT121	17p	UT46	27p	2N1302	17p	2N2906	25p	2N3709	8p
AC128	17p	AF126	20p	BC148	12p	BCY72	15p	BF310	15p	MPF102	43p	V405A	25p	2N1303	17p	2N2906A	27p	2N3710	10p
AC141K	17p	AF127	20p	BC149	17p	BCZ11	20p	BF329	20p	MPF105	43p	V410A	45p	2N1304	20p	2N2907	25p	2N3711	10p
AC142K	17p	AF139	33p	BC150	17p	BD121	85p	BFX84	20p	OC19	30p	2G301	19p	2N1305	20p	2N2907A	30p	2N3819	40p
AC151	15p	AF178	50p	BC151	20p	BD123	85p	BFX85	27p	OC20	50p	2G302	19p	2N1306	22p	2N2923	13p	2N3820	1p
AC154	15p	AF179	50p	BC152	17p	BD124	75p	BFX86	22p	OC22	30p	2G303	30p	2N1307	22p	2N2924	13p	2N3903	25p
AC155	17p	AF180	50p	BC153	27p	BD131	80p	BFX87	25p	OC23	33p	2G304	20p	2N1308	27p	2N2925	13p	2N3904	27p
AC156	17p	AF191	50p	BC154	30p	BD132	80p	BFX88	22p	OC24	45p	2G306	35p	2N1309	27p	2N2926	13p	2N3905	25p
AC157	17p	AF186	45p	BC157	20p	BDY20	£1	BFY50	20p	OC25	25p	2G308	35p	2N1613	17p	(G)	12p	2N3906	27p
AC165	17p	AF239	37p	BC158	17p	BF115	22p	BFY51	20p	OC26	25p	2G309	35p	2N1711	20p	2N2926(Y)	11p	2N4058	15p
AC166	17p	AF211	37p	BC159	20p	BF117	45p	BFY52	20p	OC28	20p	2G339	17p	2N1893	35p	2N2926	35p	2N4059	10p
AC167	20p	AF212	45p	BC167	13p	BF118	60p	BFY53	17p	OC29	40p	2G339A	15p	2N1890	35p	(O)	10p	2N4060	12p
AC168	20p	AL102	85p	BC168	13p	BF119	70p	BSX19	15p	OC35	33p	2G344	15p	2N1893	35p	2N3010	45p	2N4061	12p
AC169	14p	AL103	85p	BC169	13p	BF152	35p	BSX20	15p	OC36	40p	2G345	15p	2N2148	60p	2N3011	20p	2N4062	12p
AC176	23p	ASV26	25p	BC170	12p	BF153	35p	BSY25	15p	OC41	20p	2G371	13p	2N2149	60p	2N3012	20p	2N5172	12p
AC177	20p	ASV27	30p	BC171	13p	BF154	35p	BSY26	15p	OC42	22p	2G371B	10p	2N2192	30p	2N3055	63p	2N5459	43p
AC187	30p	ASV28	25p	BC172	13p	BF157	45p	BSY27	15p	OC44	15p	2G374	17p	2N2193	30p	2N3391	17p	2S034	75p
AC188	30p	ASV29	25p	BC173	13p	BF158	25p	BSY28	15p	OC45	12p	2G377	27p	2N2194	27p	2N3391A	20p	2S034	75p
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC70	15p	2G378	15p	2N2217	27p	2N3392	17p	2S034	75p
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC71	9p	2G382	15p	2N2218	25p	2N3393	15p	2S034	75p
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC72	12p	2G401	10p	2N2219	27p	2N3394	15p	2S034	75p
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC73	12p	2G401	10p	2N2220	25p	2N3395	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC74	12p	2G414	12p	2N2221	22p	2N3402	22p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC75	15p	2G417	25p	2N2222	22p	2N3403	22p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC76	12p	2G417	25p	2N2223	22p	2N3404	22p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC77	25p	2N388A	50p	2N2224	22p	2N3405	45p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC78	15p	2N404	22p	2N2225	22p	2N3406	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC79	15p	2N404A	30p	2N2226	22p	2N3407	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC80	15p	2N404A	30p	2N2227	22p	2N3408	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC81	15p	2N404A	30p	2N2228	22p	2N3409	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC82	15p	2N404A	30p	2N2229	22p	2N3410	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC83	15p	2N404A	30p	2N2230	22p	2N3411	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC84	15p	2N404A	30p	2N2231	22p	2N3412	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC85	15p	2N404A	30p	2N2232	22p	2N3413	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC86	15p	2N404A	30p	2N2233	22p	2N3414	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC87	15p	2N404A	30p	2N2234	22p	2N3415	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC88	15p	2N404A	30p	2N2235	22p	2N3416	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC89	15p	2N404A	30p	2N2236	22p	2N3417	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC90	15p	2N404A	30p	2N2237	22p	2N3418	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC91	15p	2N404A	30p	2N2238	22p	2N3419	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC92	15p	2N404A	30p	2N2239	22p	2N3420	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC93	15p	2N404A	30p	2N2240	22p	2N3421	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC94	15p	2N404A	30p	2N2241	22p	2N3422	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC95	15p	2N404A	30p	2N2242	22p	2N3423	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC96	15p	2N404A	30p	2N2243	22p	2N3424	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC97	15p	2N404A	30p	2N2244	22p	2N3425	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC98	15p	2N404A	30p	2N2245	22p	2N3426	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC99	15p	2N404A	30p	2N2246	22p	2N3427	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC100	15p	2N404A	30p	2N2247	22p	2N3428	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC101	15p	2N404A	30p	2N2248	22p	2N3429	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC102	15p	2N404A	30p	2N2249	22p	2N3430	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC103	15p	2N404A	30p	2N2250	22p	2N3431	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC104	15p	2N404A	30p	2N2251	22p	2N3432	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC105	15p	2N404A	30p	2N2252	22p	2N3433	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC106	15p	2N404A	30p	2N2253	22p	2N3434	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC107	15p	2N404A	30p	2N2254	22p	2N3435	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC108	15p	2N404A	30p	2N2255	22p	2N3436	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC109	15p	2N404A	30p	2N2256	22p	2N3437	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC110	15p	2N404A	30p	2N2257	22p	2N3438	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC111	15p	2N404A	30p	2N2258	22p	2N3439	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC112	15p	2N404A	30p	2N2259	22p	2N3440	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p	BF159	25p	BSY29	15p	OC113	15p	2N404A	30p	2N2260	22p	2N3441	20p	2S035	£1
AC189	30p	ASV30	25p	BC174	13p</														

## RADIO FREQUENCIES USED IN SPACECRAFT

A large number of enquiries are received about the communication frequencies used by the *Apollo* missions and other spacecraft.

The frequencies that are used on spacecraft depend on the matter to be transmitted and also on the propagation conditions. There are normally three bands in use. These are the h.f., v.h.f. and u.h.f. bands. The latter includes the S-band which is of considerable importance since it is less susceptible to propagation anomalies and has perhaps the best noise level characteristic. Noise is at a minimum on this band.

Taking the *Apollo* spacecraft as an example, there are three units involved. These are the command module, the service module and the lunar module. Communication between ground and the spacecraft from the count down through launch and into earth orbit is maintained by v.h.f. on frequencies of 259MHz and 296MHz (exact values for *Apollo 15* were 259.7MHz and 296.8MHz). The command and lunar modules also operate on these frequencies. Within the spacecraft the u.h.f. frequencies are used as well as sound frequencies.

After leaving earth orbit and heading toward the target, communications change to the S-Band. These frequencies are 2273.5MHz for the television channel and 2106.4MHz for speech and exchange of data between the spacecraft and earth. Another channel on 2287.5MHz gives a link between the command module and the ground for speech, directly given data on the course position and other real time information.

The lunar module has two transceivers one of which is used for speech and data and operates on a frequency of 2101.8MHz. The other channel uses a frequency of 2282.5MHz and can be used for data, speech or television. In addition to these systems the craft operates another transceiver which uses a frequency of 10,006MHz. The powers that are used are quite low being 2.8 watts and 11.2 watts on the S-band.

## PARACHUTE TESTING

NASA is to carry out free-flight tests on the *Viking* landers to test the parachute system to be used in the *Viking* spacecraft when they are launched in 1975. This is a new departure in technique for no parachute landing of spacecraft has been attempted before.

The *Viking* system is operated by a mortar which is fired automatically and deploys a 50ft diameter parachute. During tests units will be dropped from 50,000ft and drogue parachutes will slow a ten foot container to the speed at which the mortar will fire.



BY FRANK W. HYDE

## PROJECT EOLE

The new French *Eole* world wide system of weather watch reported previously ran into difficulties.

One hundred and forty-one balloons had been launched in the southern hemisphere and when the satellite was instructed to interrogate it sent instead a destruct signal to 72 balloons which were lost with all their sensors. This occurred on the 364th orbit.

The origin of the wrong signal was traced to one of the control centres at Bretigny. The French space organisation, CNES, consider that the programme will still be valuable since up to 500 balloons will be released during the 180 day period of observation.

## SEARCH FOR EXTRA-TERRESTRIAL LIFE

At the final session of a Conference on Communication there was a discussion for a programme to organise a search for intelligent beings in the space of the galaxy. The conference was attended by many countries and the delegates were from many disciplines: astro-physicists, theoretical astronomers, radio astronomers, sociologists, archaeologists and anthropologists.

## LUNOKHOD

The Russian roving vehicle Lunokhod was shut down after its eleventh day. The last test period resulted in a movement of only 100 metres. It has been shut down because Russian scientists are unwilling to risk the possible misalignment of the on-board laser reflector.

## LAST LUNAR MISSION

The *Apollo 17* is, at the moment, the last lunar mission of the series for manned landing on the Moon. The planning of its landing site is therefore of considerable importance. Last June the target decided upon was the area near the crater Alphonsus. It still is the prime candidate.

There are important reasons for the examination of this area. It was from here that the Russian astronomers noted the emission of gases and changes in the spectrum which suggested vulcanism. Since then, this area has been the subject of close study by professionals and amateurs. Many instances of transient changes in the crater have been noted, some of them detected by spacecraft photographs.

However, after examination of the *Apollo 15* data, recovered with much new information, it may be that another site would be of greater scientific value. This sets a problem because the time for crew training is affected particularly as this is the last mission.

## SPACECRAFT COMPUTER

A low power spacecraft computer has been developed by Honeywell. It is suitable for a wide range of unmanned spacecraft missions and its power requirements are only 26.9 watts. It provides a one microsecond memory cycle time.

NASA's satellites for application technology will use two of these computers in parallel. The package weighs 23lb and is known as *HDC 401*.

## SATELLITE GANYMEDE

Ganymede is one of the four satellites originally discovered by Galileo to revolve round Jupiter. It has virtually no atmosphere and it was thought, till recently, that the surface would be like that of the Moon. Recent observations, however, have shown that the atmosphere is below one millibar and the surface may be rock powder or ammonia snow.

These observations were carried out at a wavelength of 25 micrometres at the University of Hawaii. Led by Dr. D. Morrison the team at the University and the Los Alamos Scientific Laboratory observed the satellite before, during and after the eclipse by Jupiter, revealing that except for the presence in the spectrum of features which suggest ammonia frost, the surface is indeed moonlike in character.

The presence in the spectrum of features which suggest ammonia frost still leaves some puzzling questions.

# Substitutes for ZENERS

By J. N. WATT

THE regulation of fairly low voltages using Zener substitutes is fairly straightforward, if a little unconventional, as was illustrated last month. In this final part we shall look at the application of these substitutes in power supply circuits and give some examples of their applications.

## SHUNT REGULATOR

Fig. 9 shows a typical shunt regulator, where the extra transistor handles the additional power.

The Zener substitute and the power transistor's base-emitter voltage hold the output voltage at  $V_o = V_Z + V_{BE}$ .

The resistor R2 ensures that sufficient current flows through the Zener substitute to give stability.

The current through the shunt transistor is about  $h_{FE}$  times that through the Zener substitute (ignoring the current in R2). It is this that gives the greater power handling capability, which is that of the shunt transistor. This latter could well be one of the unmarked npn devices mentioned earlier as being suitable for use as a Zener substitute.

Calculation of the value of R1 follows the same procedure as in the simple shunt regulator in Fig. 2.

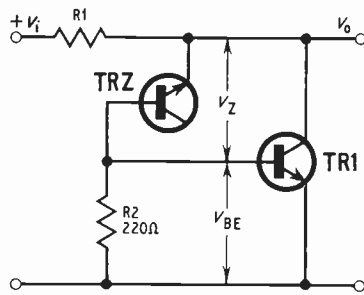


Fig. 9. Transistor shunt regulator


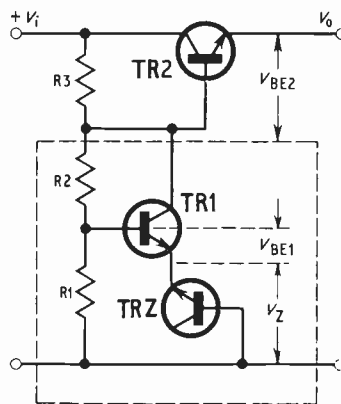
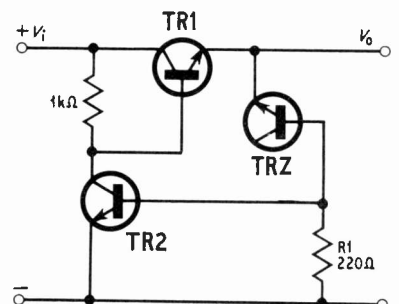


Fig. 10 (left). Simple series regulator

Fig. 11 (above). Series regulator using an "amplified Zener"

Fig. 12 (above right). Division of Zener voltage

Fig. 13 (right). Shunt regulator with improved performance

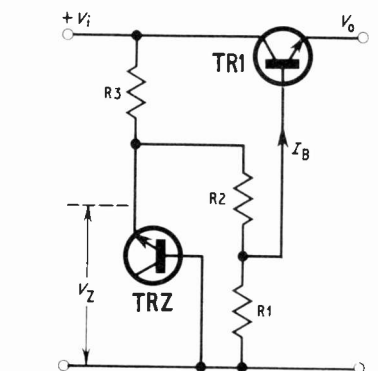



# BUDGET HIGH-FIDELITY STEREO SYSTEMS



**PREMIER STEREO SYSTEM "ONE"** consists of an all transistor stereo amplifier, Garrard 2025 T/C auto manual record player unit fitted stereo mono-ceramic cartridge with diamond stylus and mounted in teak finish plinth with perspex cover and two matching teak finish loud-speaker systems. Absolutely complete and supplied ready to plug in and play. 2500 amplifier has an output of 5 watts per channel with inputs for pick-up, tape and tuner, also tape output socket. Controls: Bass, Treble, Volume, Balance, Selector, Power on/off. Solid teak cabinet with aluminium front panel. Size: 12½in x 4½in x 3½in high (Amplifier available separately if required £14.95. Carr. 40p).

**ONLY £40-95**  
carr. £1-75

**PREMIER STEREO SYSTEM "TWO"**, as above but with Garrard SP25 Mk III—**ONLY £47.** Carr. £1-75.

**PREMIER STEREO SYSTEM "THREE"**. This consists of Klinger K9003 stereo amplifier giving 6 watts rms per channel with Base, Treble, Volume and Balance Controls. Inputs for Magnetic and ceramic pick-up, tuner, tape in and out, Stereo headphone socket. Garrard SP25 Mk III in teak finish plinth with cover and fitted Sonotone 9TAHCD diamond stereo cartridge. A pair of HMF Speakers size 16½in x 10½in x 9in and fitted EMI units complete the matching system.

**ALL SYSTEMS SUPPLIED WITH FREE LEADS AND PLUGS**

**ONLY £57-75**  
carr. £1-75

## PREMIER HI-FI OFFERS!

Amstrad 8000 Stereo Amplifier (List £25-95) **£16-75**  
Philips 580 Stereo Amplifier (List £29-00) **£21-00**  
Rogers Ravensbrook 11 Stereo Amplifier in teak case (List £52-50) **£39-50**  
Rogers Ravensbourne Stereo Amplifier in teak case (List £64) **£49-00**

**NOW AVAILABLE AGAIN!!**  
MODEL SAQ203 Stereo Amplifier—Return of this popular model. 1000's have been sold. **NOW AT NEW LOW PRICE £19-50**

Metrosound ST20E Stereo Amplifier in teak case (List £39-50) **£28-50**  
Goldring GL75 less cartridge (List £41-61) **£29-00**  
Garrard SP25 111 less cartridge **£11-90**  
Garrard SP25 111 with Goldring G800 cartridge (List £28-35) **£15-50**  
Garrard AP76 less cartridge **£19-50**

Garrard 3500 with Sonotone 9TAHC stereo cartridge (List £15-50) **£9-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge **£8-97**

Garrard 2025 T/C with Sonotone 9TAHC Diamond Cartridge ready wired in teak plinth with cover **£14-00**

Carriage and Insurance 50p extra any item.

## SP25 Mk III SPECIAL!



Garrard SP25 Mk. III Single Record Player. Fitted Goldring G800 Magnetic Stereo Cartridge as available Complete in Teak Plinth with Rigid Perspex Cover.

Total list Price over £34.

**PREMIER £18-90**  
PRICE P. & P. 60p



## HI-FI STEREO HEADPHONES

Designed to the highest possible standard. Fitted 2½in speaker units with soft padded ear muffs. Adjustable headband. 8 ohm impedance. Complete with 6ft. lead and stereo jack plug.

**£2-47** P. & P. 35p



STEREO STETHOSCOPE SET Low imp. £1-25.

P. & P. 10p

MONO STETHOSCOPE SET Low imp. 52p. P. & P. 10p



**E.M.I. 13x8in. HI-FI SPEAKERS**

Fitted two 2½in tweeters and crossover network. Available with 8 or 16 ohm impedance. Handling capacity 10W. Brand new.

**£3-47** P. & P. 40p



## "WELLER EXPERT" SOLDER GUN

Saves time and simplifies soldering in the home and service dept. Two position trigger gives instant dual heat 100/140 watt. 240 volt A.C. P. & P. 30p



"Weller Marksman" Soldering Iron Lightweight, 3/4 pencil bit, 25 watt. 240 volt A.C. £1-50 P. & P. 10p.

## VERITAS V-49 MIXER

Battery operated 4-channel audio mixer providing four separate inputs. Size 4 1/2 x 3 1/2 in. suitable for crystal microphone, low impedance microphone with transformer, radio, tape, etc. Max. input 1.5V, max. output 2.5V, gain 6dB. Standard jack plug socket inputs, phono-plugs output. Attractive teak wood grain finish case.



Mono Model £3 Stereo Model £3-47 P. & P. 12p



## TAPE CASSETTES

C60 (60 min.) 37p £1-05  
C90 (90 min.) 62p £1-80  
C120 (120 min.) 87p £2-55  
P. & P. 5p

**FREE** Cassette Head Cleaner with every 10 cassettes purchased  
**All cassettes can be supplied with library cases at 3p extra each.**

## "VERITONE" RECORDING TAPE

SPECIALLY MANUFACTURED IN U.S.A. FROM EXTRA STRONG PRE-STRETCHED MATERIAL. THE QUALITY IS UNEQUALLED.

TENSILISED to ensure the most permanent base. Highly resistant to breakage, moisture, heat, cold or humidity. High polished splice free finish. Smooth output throughout the entire audio range. Double wrapped—attractively boxed.

LP3 3" 250' P.V.C.	28p	LP8 5 1/2" 1200' P.V.C.	75p
TT3 3" 450' POLYESTER	37p	DT6 5 1/2" 1800' POLYESTER	£1-12
DT3 3 1/2" 600' POLYESTER	57p	TT6 5 1/2" 2400' POLYESTER	£1-87
SP5 5" 600' P.V.C.	42p	SP7 7" 1200' P.V.C.	62p
LP5 5" 900' P.V.C.	50p	LP7 7" 1800' P.V.C.	75p
DT5 5" 1200' POLYESTER	75p	DT7 7" 2400' POLYESTER	£1-25
		TT7 7" 3600' POLYESTER	£2-50

TAPE SPOOLS 3" 5p, 5", 5 1/2", 7" 8p.  
Post and Packing 3" 5p, 5", 5 1/2" 8p, 7" 10p. (3 reels and over Post Free.)




# PREMIER RADIO

10 & 23, TOTTENHAM COURT ROAD, LONDON, W.1 TEL: 01-636 3451/2639  
HEAD OFFICE & MAIL ORDER DEPT. 23, TOTTENHAM CT. RD. TEL: 01-636 3451

OXFORD ST.



## BLACK LIGHT

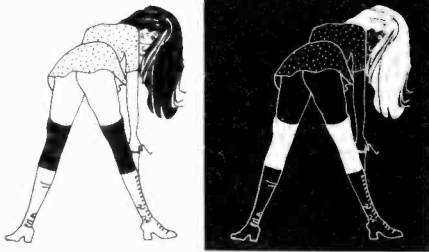

## THE OUT OF SIGHT LIGHT



This kit consists of a high-pressure mercury discharge lamp enclosed in a deep blue-violet outer bulb. This absorbs all visible light given by the discharge but transmits the long-wave ultra-violet rays.

The unit performs in a similar fashion to the fluorescent tube type units in use in some discotheques but instead uses a 3-pin B.C. lamp fitted into a high intensity spot-fitting with fully adjustable swivel bearing. The reflector is also fully adjustable and the unit may be mounted in any position and focused as desired.

White shirts and dresses glow "Whiter than white". Paint scenes on walls, etc., with our special fluorescent paint, focus the black-light from across the room and switch-on. The pictures glow brilliantly as if by magic!

Full kit includes lamp, reflector, control-gear, generous samples of five different colours of fluorescent paint and full instructions. Price £25 carr. paid. S.A.E. with all inquiries.

## AUDIO MIXER MODULES



A range of audio Pre-amplifier Modules is now available enabling the construction of custom-built audio mixers for studio, P.A. and discotheque installations; at reasonable cost and with many facilities usually available only on expensive systems. The modules, constructed on fibre-glass printed-circuit boards are complete with anodised aluminium black facia plates and four control knobs.

A comprehensive range of input modules is available, together with mixer/line amplifier and V.U. meter, power unit and 100W slave amp. See Aug. and Sept. *Practical Electronics* for further details or send 25p for manual showing mixing arrangements, connection data, etc. Trade inquiries welcome.

## PSYCHEDELIC LIGHTING UNIT Mk. 3




This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source.

The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 carr. paid. S.A.E. with all inquiries.
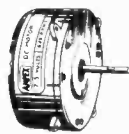
## DABAR ELECTRONIC PRODUCTS

98a LICHFIELD STREET, WALSALL, STAFFS WS1 1UZ  
WALSALL 34365  
MAIL ORDER ONLY



**AMPEX 7.5v. D.C. MOTOR.** This is an ultra-precision tape motor designed for use in the AMPEX model AG20 portable recorder. Torque 450GM/CM. Stall load at 500 ma. Draws 60 ma on run, 600 rpm + 5% speed adjustment, internal AF/RF suppression 1/2" dia. 1" spindle, motor 3" dia. 1 1/2". Original cost enclosure available 75p each.

£16.50. Our price £4.25. P. & P. 25p. Mu-metal enclosure available 75p each.

### SYNCHRONOUS MOTORS

**SMITHS.** 250v. 50 Hz. Available in the following R.P.M. 2-3-6-10-30-60. Price 75p each. Carr. paid.

**CRUZET.** 220/380v. 50/60 Hz. 250-300 rpm 75p. Carr. paid.

**MAINS INDUCTION MOTOR.** Open frame, 1/2" spindle, weight 1/2 lb. Powerful. 88p each. P. & P. 12p.

### GEARED MOTORS

**ELECTRO CONTROL (CHICAGO).** Shaded pole 240v. 50 Hz. 200 rpm. 10lb. in. £2.50. P. & P. 25p.

**MYCALEX.** Open frame, shaded pole motors, 240v. 50 Hz. 7 rpm. 28 lb. in. 80 rpm. 12 lb. in. £2.25 each. P. & P. 25p.

"**CRUZET**" TYPE 965. 115/240v. 50 Hz. 47/68 watts. 50 rpm. Stoutly constructed. Size: 2 1/2" dia. x 3 1/2" long plus spindle 1 1/2" dia. Anticlock. £2.75. P. & P. 25p.

Same as above, but 3 rpm. £3. P. & P. 25p.

"**MALLORY**" LONG LIFE BATTERIES. Type RM12 cell 1.35v. 3,600 ma/H. CAP. 250/300 ma cont. current. Size: 2" x 1 1/2" x 1 1/2". 5 for £1.00 or £2.00 per doz. Carr. Paid. Type B. Comprises 8 x RM 625 cells. Nom. volts. 1.35 each/10.5v. Overall, 350 ma/H CAP. 20/25 ma cont. current. Size: 2 1/2" x 1 1/2" x 1 1/2". 3 for £1.00 or £3.00 per doz. Carr. Paid.

**A.C./D.C. M/IRON AMMETERS.** 0-5 amps or 0-8 amps (suitable battery chargers, etc.). Perspex front. Size: 1 1/2" x 1 1/2". Any 2 for £1.10. Carr. Paid.

**ERNEST TURNER 800µA METER** 160µ movement, 2" case elliptic, plastic front, Green-Red-Green uncalibrated scale £1.50 each. C.P.

### PROGRAMME TIMER BY HONEYWELL



A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 rpm). Originally cost £15.00 plus. Many applications such as lighting effects, etc. New in original makers cartons. First class value at £5.75 plus 25p P. & P.

### PRECISION FAN CO. (SMITHS INDUSTRIES) DOUBLE ENTRY CENTRIFUGAL FAN/BLOWER

This is a beautifully balanced, particularly quiet running unit giving approx. 90 cubic ft./min. The motor is a 2 pole shaded pole Mycalex, drawing only 240 ma on run. Weight 2 1/2 lbs. Sizes: case dia. 3 1/2 ins. width (case only) 3 1/2 ins. Width overall (inc.) 5 25 ins. Aperture 3 1/2 ins. 1 85 ins. Offered well below makers price at £2.95. P. & P. 25p.

### RELAYS

Perspex enclosed, plug in, with base. Size 1 1/2" x 1 1/2" x 1 1/2". 2" MQ 308 600 Ω 24v. 4 c/o. 60p ea., £5.00 per doz. MQ 508 10,000 Ω 100v. 4 c/o. 50p ea., £4.50 per doz.

S.T.C. Midget Sealed Relay type 4109EC. 12v. 40 mA 170 Ω, single H.D. make. 53p each.

"B. & R." 3 c/o. 10 amp. contacts (silver) operates on 2 volts D.C. Draws approx. 1 amp. Size: 2" x 1 1/2" x 1 1/2". £1.00.

"**OMRON**" OCTAL BASE. A.C. mains. 2 x 5 amp. C/O contacts. Perspex enclosed. 88p.

**NEW "F.I.R.E." PLUG-IN RELAY.**—115v. Coil 50/60 c.p.s. 3 heavy duty silver change-over contacts. Very robust. 63p.

**NEW "ISKRA" 240v. A.C. RELAY.**—3 x 6 amp. Changeover contacts. 63p.

**SIEMENS HIGH SPEED RELAY.** Type 89L. 1,700 Ω + 1,700 Ω coil. New 63p each.

**6 DIGIT NON-RESET COUNTER** by E.N.M. Ltd. 240v. a.c. Size: 2 1/2" high x 1 1/2" x 1 1/2". £2.25.

Special offer of AMPEX professional tape heads, mu-metal shrouded. (Designed for model AG20). Full track record, or playback, £3.00. Erase head £2.00. Set of 3 with mounting bracket and cover £7.50. Half track record only, £3.00 each. Carriage paid.



"**BENSON BROS.**" 12v. D.C. HEAVY DUTY SOLENOID. Size: 3" overall x 1 1/2" x 1". Very powerful, with secondary low current hold coil. Cont. rated £1.00 each. P. & P. 15p.

"**DECCO**" MAINS SOLENOID. Compact and very powerful. 16 lb. pull. 3/4" travel which can be increased to 1" by removing captive-end-plate. Overall size 2" x 2 1/2" x 2 1/2" high. £1.50. P. & P. 25p.

"**MAGNETIC DEVICES**" Mains Solenoid:—2" x 1 1/2" x 1 1/2" approx. 2lb. pull. Plunger Travel 1 1/2". New in makers boxes; offered at half original cost. 75p. P. & P. 25p.

**L.T. TRANSFORMERS.** Prim. 0-110-240v. Sec. 4.5-0-4.5v. at 1 amp. Size 1 1/2" x 1 1/2" x 1 1/2". 60p. P. & P. 15p.

Prim. 220/240v. Sec. 0-5-10-15-20v. at 2 amps. £1.25. P. & P. 15p.

Prim. 200/240v. Sec. 0-1-56-58-60 at 3.5 amps plus 0-90 at 100 ma. Wax impregnated with screw term. blocks. Weight 10 lbs. £3.60, plus 40p P. & P.

"**WODEN.**" Prim. 10-0-200-240v. Sec. two separate windings 6v. at 4 amps each. £2.50, plus 30p P. & P.

"**WODEN.**" Prim. 0-110-200-220-240v. Sec. 34-36-38v. at 600va. £7.50, plus 50p P. & P.


**H.T. TRANSFORMER.** Prim. 240v. sec. 0-380-400-420-440v. 40va. £3. Carr. paid

**SLIDER SWITCHES.** 3 amp. type D.P.D.T. 1 1/2" x 1 1/2" x 1 1/2" deep. 1 amp. type 3 P.D.T. 1 1/2" x 1 1/2" x 1 1/2" deep. £1.25 per doz. Either type or mixed as required. Carr. Paid.

**CURRENT FLOW INDICATOR.** Ideal for all types of battery operated equipment (portable machines, recorders, etc.). Four white segments appear when current flows. Coil is 600 Ω 6/12v. Drawing only 8 ma on function. Neat in appearance. Size: dia. 1 1/2" x 1 1/2" deep. Fixing centres 1 1/2" x 1 1/2" each. Carr. Paid.
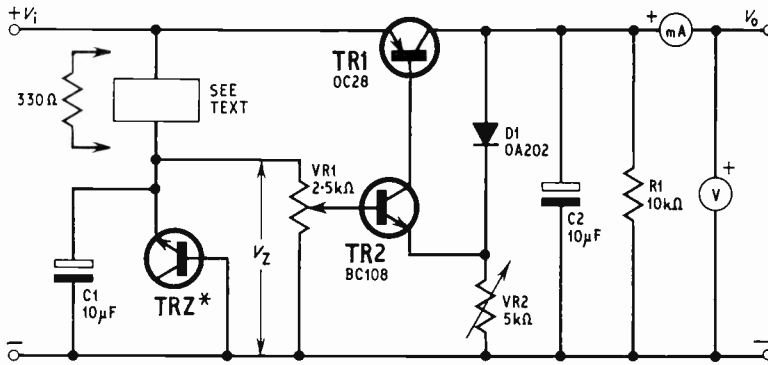
## ELECTRO-TECH SALES

BUSINESS HOURS 301 EDGWARE ROAD, LONDON W2 1BN  
9 a.m.—6 p.m. MON. TO SAT. (PE 12) Tel. 01-262 2251/2



\* TRZ is a silicon planar npn transistor, e.g. BSY95A, BC107, BC108, 2N2926

Fig. 14. Stabiliser with variable output voltage and short circuit protection

It is as well, therefore, by suitable choice of  $R_1$  to arrange for the current through the latter to be, say, 50% greater than this value of  $I_B$ .

With no load current, the current taken from the supply is only that through the Zener substitute. However, as it stands the arrangement is unprotected against short circuit of its output, an event which would be most likely to destroy the series transistor, unless protective measures are taken.

### SHUNT TO SERIES CONVERSION

To provide an output voltage greater than  $V_Z$ , the circuit in Fig. 6 can be adapted to series operation, as shown in Fig. 11.

$$V_o = \frac{R_1 + R_2}{R_1} (V_Z + V_{BE1}) - V_{BE2}$$

An output voltage less than the Zener voltage is easy to arrange by simple division of  $V_Z$ .

$$V_o = \frac{R_1}{R_1 + R_2} V_Z - V_{BE}$$

This is shown in Fig. 12.

With these last two circuits sufficient base current must be supplied to permit the series transistor to pass the required full load current.

Thus in Fig. 12,  $R_1$  and  $R_2$  should be chosen to allow a standing current of, say, five times  $I_B$  to flow through them. This current can be looked upon as the load of the simple circuit comprising the Zener substitute and its series resistor  $R_3$ .

With  $R_1$  and  $R_2$  so chosen,  $R_3$  can be selected as before.

### VOLTAGE AMPLIFIER

Regulation of the output voltage can be improved by incorporating a further transistor, used as a voltage amplifier, shown in Fig. 13.

If  $V_o$  tries to rise in level, then so does the voltage at the base of TR2, since the Zener substitute has a constant voltage developed across it. Transistor TR2 amplifies this change, with reversal of sign, so that a larger fall in voltage appears at TR1 base. Emitter follower action in TR1 thus tends to reduce  $V_o$ , so correcting the original rise. TR1 can be a member of the OC28 to OC36 family, while TR2 can be almost any of the popular silicon npn devices so readily available.

Besides the better regulation given by the gain of TR2, it is noteworthy that the Zener substitute is driven by the regulated output voltage,  $V_o$ . Since this is constant, better stability of Zener voltage is obtained. In those circuits where the Zener is fed from the unregulated supply, some change of Zener voltage can occur with variation in that supply, due to change of current through the Zener.

An alternative method of obtaining better Zener voltage stability will be mentioned later.

### STABILISED POWER SUPPLY

Having thus briefly described many of the circuits in which Zener substitutes can be employed, we can now turn to the design of a stabilised power supply, using a circuit configuration not previously mentioned, see Fig. 14. It has the following advantages:

1. Being a series regulated supply, it can efficiently handle moderately large currents—up to 1A or even greater, depending on the transistor and heat sink employed.
2. It gives a variable stabilised output.
3. Despite the series regulator configuration, short circuit protection is provided.
4. Constant current output, in place of constant voltage output, is possible, the level of such constant current being easily adjustable.

### SERIES RESISTANCE FOR ZENER

Initially, consider the "black box" (between  $V_i$  and TRZ) feeding the Zener substitute to consist of a resistor of an appropriate value, say 330 ohms. Alternative components for the "black box" will be considered later.

Let us assume that an output current of 1A is required. Then the base current of TR1 will be  $I_{B1} = 1/h_{FE1}$ . Since this current is provided by TR2, its base current will be  $I_{B2} = 1/(h_{FE1}h_{FE2})$ .

Assuming  $h_{FE1} = 25$  (OC28 family) and  $h_{FE2} = 100$  (BC108), then the base current of TR2 is  $400\mu A$ .

We should allow, say, 10 times this current to flow through VR1 as a standing current, i.e. 4mA. If  $V_Z$  is made 8 volts (a reasonable value for a Zener substitute), then the value of VR1 is equal  $V_Z/4 = 2k\Omega$ .

A 2.5k $\Omega$  potentiometer will be suitable; it does of course give us the means of providing a variable stabilised output.

Capacitor C1 ensures that the Zener voltage is held smoothly, despite any rapid, large changes in supply voltage ( $V_i$ ) which could occur if the mains were used

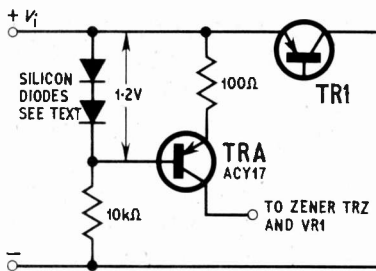


Fig. 15. Constant current drive for Zener substitute

as a primary supply, while C2 reduces any similar changes at the output due to rapid variations in load current. Resistor R1 is necessary to turn on TR1, thereby providing control, by drawing a small load current when no, or only a very small, load current would otherwise be taken. Without R1,  $V_0$  could rise above the stabilised voltage, due to leakage in TR1.

### SHORT CIRCUIT PROTECTION

Turning now to D1 and VR2, it is these components that provide the short circuit protection and constant current output facility.

In normal running, D1 is forward biased. Should a short circuit be applied to the output of the power supply, it will no longer be so biased, since its anode will then be at negative rail potential (via the short circuit). This results in TR1 passing a current determined by its then existing base current; this will be set largely by the value of VR2, since the lower end of VR2 is now connected directly to the collector of TR1 (via the short circuit).

Thus by choice of an appropriate setting of VR2, limiting of the current to any desired value is obtained.

The constant current mode is brought into play by ensuring that the output voltage setting is such as to attempt to deliver more current than the setting of VR2 allows. Output current is then constant despite supply voltage changes and load changes, provided of course the necessary output voltage can in fact be reached by the supply.

The short circuit protection and constant current output facility are possible in this way because of the method of connection of TR1. It is not, as in previous examples of series stabilised supplies, connected so that emitter follower action takes place. With the output

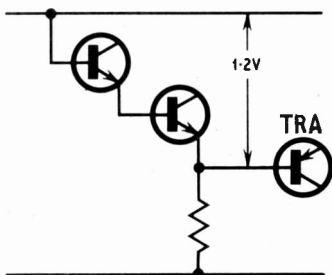


Fig. 16. Use of npn transistors in place of the silicon diodes shown in Fig. 15

taken from the collector as shown, the output impedance is still low, however, because of the heavy negative feedback present.

### CONSTANT SERIES CURRENT FOR ZENER

There is, of course, a disadvantage in this method of connection.

It has been noted above, in connection with the circuit in Fig. 13, that better output voltage stability is obtained if the Zener substitute is driven from the stabilised supply,  $V_0$ . Because of the circuit arrangement, in Fig. 14, of the series transistor being used with its collector as the output, it is not possible to drive the

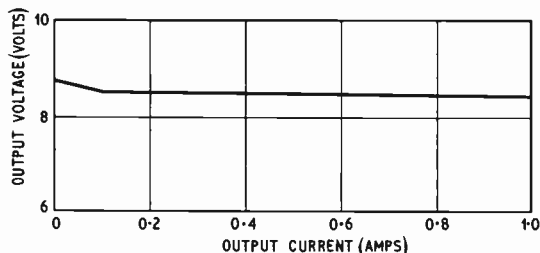


Fig. 17a. Graph of output voltage versus output current for the circuit in Fig. 15


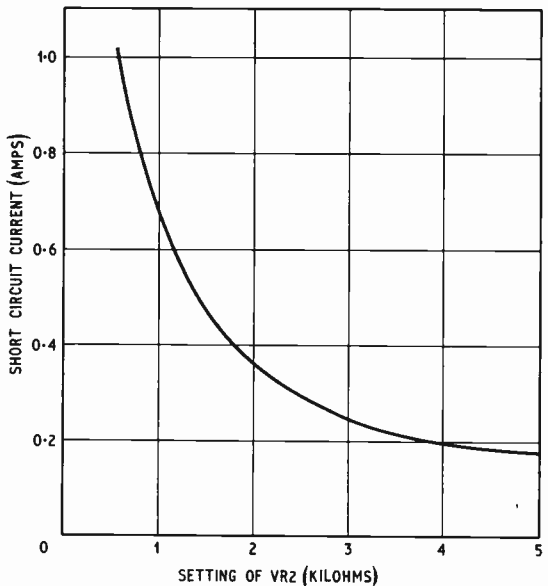


Fig. 17b. Output short circuit current versus setting of VR2

Zener substitute from the stabilised side. Consequently, other means of providing a more constant voltage need to be investigated.

That adopted here concerns the replacement of the "black box" with a constant current circuit similar to that in Fig. 7. The arrangement of this is given in Fig. 15, where a current of 7mA is given by TR1, 4mA through VR1, and 3mA through the Zener substitute.

# electronics mastered!\*

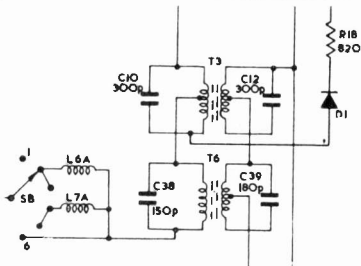


by our highly practical  
**BUILD, SEE & LEARN** system

Step by step we take you through the apparent intricacies of electronics and show you how easily you can master the subject. Write for the brochure which shows, in full detail, how you can do it.

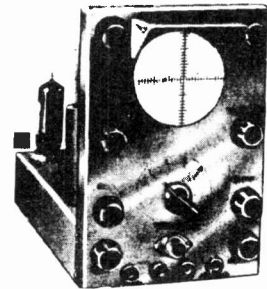**1**

We provide a full range of components and sub-assemblies, with details of what they do, so that you learn to recognise all the 'bits and pieces'. Using some of these you are instructed in how to build this oscilloscope, simply and quickly.




**2**

You are shown how to read and understand circuit diagrams so that you can later build more advanced equipment or draw your own diagrams.

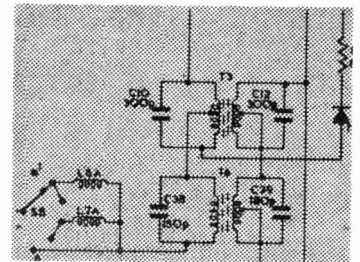**3**

You can construct over 40 kits, including:—

- Valve experiments
- Transistor experiments
- Amplifiers
- Oscillators
- Signal tracer
- Photo electric circuit
- Computer circuit
- Basic radio receiver
- Electronic switch
- Simple transmitter
- a.c. experiments
- d.c. experiments
- Simple counter
- Time delay circuit
- Servicing procedures



This course has been designed to help even those who are complete newcomers to electronics. **No Maths needed!**

**POST NOW**  
**FOR**  
**FREE BROCHURE**  
BLOCK CAPITALS PLEASE

To: **British National Radio School, Reading, Berks.**  
Please send your free Brochure, without obligation, to:

NAME .....

ADDRESS .....

P.E.12

**FREE**

**SPECIAL ELECTRONIC GIFT**  
to all our Students **POST COUPON NOW!**

# BUY YOUR HI-FI AT LOW-FI PRICES!

## Save upto 33 1/3% or more

**Huge savings on AKAI**

Model	S.S.A. Price	£p
Model 1720L Stereo Recorder	62.25	62.25
Model 4000D Stereo Tape Deck	66.50	66.50
Model X 18008D Reel/8-Track Stereo Recorder	118.95	118.95
Model CR80D 8-Track Stereo Deck	64.50	64.50
Model CR80 8-Track Stereo Recorder	80.50	80.50

P. & P. 75p.

**Stereo Amplifiers—save £££s**

Model	S.S.A. Price	£p
Armstrong 521	42.50	42.50
Ferroglyph F307	44.00	44.00
*New Leak Delta 30 cased only	51.90	51.90
*New Leak Delta 70 cased only	63.50	63.50
Metrosound ST20E	29.50	29.50
Nikko TRM 30	29.95	29.95
Nikko TRM 40	39.50	39.50
Nikko TRM 50	49.50	49.50
Pioneer SA900	95.95	95.95
Teleton SAQ206	18.50	18.50
*New Wharfedale Linton Amp	46.75	46.75

\*New Release. P. & P. 75p.

**Sinclair Project 60 special package deals save £££s**

2x230 Stereo Amp 60 Pre-amp P25 Power Supply	£16.75	(P. & P. 40p.)
2x250 Stereo Amp 60 Pre-amp P25 Power Supply	£20.50	(P. & P. 40p.)
Active Filter for above	£4.90	(P. & P. 20p.)
Project 60 FM Tuner	£20.25	(P. & P. 40p.)
Pair of Q16 Speakers	£13.95	(P. & P. 50p.)
IC10 IC12 Integrated Circuit 10W amp	£2.50	(P. & P. 20p.)

All other Sinclair products in stock. P. & P. 75p.

**Turntables**

Model	S.S.A. Price	£p
Garrard SP75 Mk 111	10.75	10.75
Garrard AP76	19.25	19.25
Garrard SL72B	24.95	24.95
Garrard SL75B	27.50	27.50
Garrard SL85B	36.95	36.95
Garrard 401	28.50	28.50

**SPECIAL OFFER**  
Garrard Decks supplied wired with Base and Cover and fitted cartridge.

**Speaker systems**

Model	S.S.A. Price	£p
Garrard SP25 111 with Goldring G800	18.95	18.95
Garrard AP7 with Goldring G800	29.95	29.95
Goldring GL69/2 with Goldring G800	37.95	37.95
Goldring GL75 with Goldring G800	42.75	42.75
Base and Covers for Garrard SP25 111, 2025 TU, 3000 SL65B	4.95	4.95
AP76, SL72B, SL75B, SL85B	4.95	4.95

P. & P. 35p. **NEW WHARFEDALE AND LEAK TURNTABLES NOW IN STOCK**

**Speaker systems**

Model	S.S.A. Price	£p
Celestion Ditton 120	18.00	18.00
Celestion Ditton 15	25.50	25.50
Celestion Ditton 25	50.95	50.95
Goodmans Minister	19.95	19.95
Goodmans Magister	47.95	47.95
Goodmans Mezzo 3	24.95	24.95
Goodmans Magnum K2	32.00	32.00
*New Wharfedale Denton 2, PR	32.50	32.50
*New Wharfedale Linton 2	20.50	20.50
*New Wharfedale Melton 2	28.50	28.50
Wharfedale Triton PR	33.50	33.50
Wharfedale Unit 3 Kit	48.50	48.50
Wharfedale Unit 4 Kit	10.25	10.25
Wharfedale Unit 5 Kit	13.75	13.75
Wharfedale Unit 6 Kit	19.95	19.95

\*New Release. P. & P. 75p.

**Tuner/Amplifiers**

Model	S.S.A. Price	£p
Armstrong 525 FM	71.70	71.70
Armstrong 526 AM/FM	81.30	81.30
Nikko STA301	88.95	88.95
Nikko STA501	103.85	103.85
Nikko STA701	115.50	115.50
Wharfedale 100-1	114.50	114.50
*New Leak Delta 75 AM FM	127.50	127.50

\*New Release. P. & P. 80p.

**Tuners**

Model	S.S.A. Price	£p
Armstrong 523 AM/FM	40.50	40.50
Armstrong 524 FM	31.75	31.75
Armstrong M8 Decoder	7.95	7.95
*New Leak Delta FM	61.95	61.95
*New Leak Delta FM/AM	78.95	78.95
Nikko FAM10	42.00	42.00
Nikko FAM12	55.75	55.75
Nikko FAM14	79.75	79.75

\*New Release. P. & P. 75p.

**Headphones**

Model	S.S.A. Price	£p
Akai ASE9	5.50	5.50

\*New Release. P. & P. 35p.

All goods supplied are brand new and carry manufacturer's guarantee. All prices correct at time of going to press (E. & G.E.) and are subject to alteration without notice.

**Sonic Sound Audio Ltd**  
DEPT. SS.1, 372 EDGWARE ROAD, LONDON, W.2  
Telephone 01-723 0094

# INST VALVE MAIL ORDER CO.

BLACKWOOD HALL  
16a WELLFIELD ROAD, LONDON SW16 2BS  
SPECIAL EXPRESS MAIL ORDER SERVICE  
Express postage 1p per transistor, over ten post free

Inst	Sp	Inst	Sp	Inst	Sp	Inst	Sp
1N21	0-17	AC127	0-25	BF173	0-30	GJ43M	0-38
1N23	0-20	AC128	0-20	BF181	0-35	GJ5M	0-28
1N85	0-88	AC187	0-25	BF184	0-20	GJ7M	0-37
1N253	0-50	AC188	0-25	BF185	0-20	HG1005	0-50
1N256	0-50	ACY17	0-30	BF194	0-17	H8100A	0-20
1N845	0-25	ACY39	0-50	BF237	0-25	NKT218	0-40
1N725A	0-20	ACY19	0-25	BF196	0-15	MAT101	0-30
1N914	0-07	ACY20	0-20	BF197	0-15	MAT120	0-25
1N4007	0-20	ACY21	0-20	BF861	0-28	MAT121	0-30
1B021	0-20	ACY22	0-10	BF898	0-28	MJE520	0-87
1B113	0-15	ACY27	0-25	BFX12	0-20	MJE255	1.37
1B130	0-18	ACY28	3-17	BFX13	0-25	MJE3055	0-87
1B131	0-13	ACY39	0-50	BFX27	0-25	NKT218	0-40
1B929	0-23	ACY40	0-15	BFX30	0-25	NKT219	0-30
2G240	1-98	ACY41	0-15	BFX35	0-98	NKT211	0-25
2G301	0-20	ACY44	0-25	BFX63	0-20	NKT213	0-25
2G302	0-22	AD140	0-50	BFX84	0-25	NKT214	0-15
2G306	0-30	AD149	0-50	BFX85	0-25	NKT216	0-37
2G371	0-22	AD161	0-37	BFX86	0-25	NKT217	0-35
2G381	0-25	AD162	0-37	BFX87	0-25	NKT218	0-40
2G414	0-30	AF106	0-30	BFX88	0-25	NKT219	0-33
2G417	0-22	AF114	0-25	BFY10	1.00	NKT222	0-20
2N214	0-43	AF115	0-25	BFY11	1.25	NKT224	0-22
2N247	0-25	AF116	0-25	BFY17	0-25	NKT231	0-24
2N250	0-50	AF117	0-25	BFY18	0-25	NKT271	0-25
2N404	0-20	AF118	0-25	BFY19	0-25	NKT272	0-25
2N497	0-15	AF119	0-25	BFY21	0-45	NKT273	0-25
2N698	0-40	AF124	0-25	BFY44	1.00	NKT274	0-20
2N706	0-10	AF125	0-20	BFY50	0-22	NKT275	0-25
2N706A	0-12	AF126	0-17	BFY51	0-20	NKT277	0-20
2N708	0-15	AF127	0-17	BFY52	0-22	NKT278	0-25
2N709	0-37	AF139	0-30	BFY53	0-17	NKT301	0-40
2N711	0-37	AF178	0-55	BFY64	0-45	NKT304	0-75
2N767	0-45	AF179	0-45	BFY90	0-65	NKT403	0-75
2N1090	0-30	AF180	0-62	BSX27	0-60	BT7404	0-55
2N1091	0-32	AF181	0-42	BSX60	0-93	NKT678	0-30
2N1131	0-25	AF186	0-40	BSX76	0-15	NKT713	0-25
2N1132	0-25	AFY19	1-13	B8Y26	0-18	NKT773	0-25
2N1302	0-18	AFY21	0-10	B8Y27	0-17	NKT777	0-38
2N1303	0-23	AFY21	0-50	BSY61	0-50	BT818	0-38
2N1304	0-25	ASY26	0-25	BSY95A	0-12	OA5	0-20
2N1305	0-22	ASY27	0-32	BSY95	0-12	OA6	0-12
2N1306	0-25	ASY28	0-25	BT102/500R	0A47	0-10	OC204
2N1307	0-25	ASY29	0-30	BTY42	0-92	OA70	0-10
2N1308	0-25	ASY36	0-25	BTY79/100R	0A73	0-10	OC205
2N1309	0-25	ASY50	0-17	BTY79/400R	0A79	0-10	OC206
2N1420	0-93	ASY51	0-20	0A73	0-10	OC207	0-30
2N1507	0-28	ASY53	0-20	0A79	0-10	OC208	0-30
2N1526	0-38	ASY55	0-20	0A81	0-10	OC209	0-40
2N1909	0-25	ASY62	0-25	0A85	0-12	OC210	0-30
2N2147	0-75	ASY86	0-35	0A86	0-15	ORP12	0-50
2N2148	0-60	ASZ21	0-42	0A90	0-08	ORP16	0-42
2N2149	0-75	ASZ23	0-75	0A91	0-08	ORP21	0-50
2N2218	0-20	ALY10	0-88	BY182	0-85	OA95	0-07
2N2219	0-20	AU101	1-50	BY213	0-25	OA97	0-07
2N2287	1-03	BC107	0-10	BZ210	0-35	OA202	0-10
2N2297	0-20	BC108	0-10	BZ211	0-32	OA210	0-25
2N2369A	0-15	BC109	0-10	BZ212	0-30	OA215	0-30
2N2613	0-28	BC113	0-15	BZ213	0-25	OAZ200	0-55
2N2646	0-45	BC115	0-20	BZ215	1.00	OAZ201	0-50
2N2712	0-25	BC116	0-25	BZ216	0-25	OAZ202	0-40
2N2784	0-50	BC116A	0-30	BZ216	0-62	OAZ203	0-42
2N2846	0-75	BC118	0-25	BYZ88C3V3	0A204	0-30	OX642
2N2848	0-42	BC121	0-20	0-15	OAZ205	0-42	OX644
2N2904	0-20	BC122	0-20	0-85	OAZ206	0-42	OX645
2N2904A	0-33	BC122	0-33	0-25	OAZ207	0-37	V1730P
2N2906	0-20	BC126	0-65	CRS14/20	0-32	V30-201P	0-75
2N2907	0-23	BC140	0-45	CS48	0-60	OAZ209	0-83
2N2924	0-23	BC147	0-15	CS10B	3-13	OAZ210	0-32
2N2925	0-15	BC148	0-12	DD000	0-18	OAZ211	0-32
2N2926	0-10	BC149	0-20	DD003	0-15	OAZ222	0-45
2N3054	0-50	BC157	0-15	DD006	0-18	OAZ223	0-45
2N3055	0-75	BC157	0-40	DD007	0-40	OAZ224	0-45
2N3702	0-10	BC158	0-12	DD008	0-38	OAZ241	0-22
2N3705	0-10	BC160	0-63	GD3	0-33	OAZ242	0-23
2N3706	0-23	BC169	0-12	GD4	0-05	OAZ244	0-23
2N3707	0-12	BCY31	0-30	GD5	0-33	OAZ246	0-23
2N3709	0-13	BCY32	0-55	GD8	0-25	OAZ290	0-38
2N3710	0-13	BCY33	0-25	GD12	0-05	OC18	0-50
2N3711	0-10	BCY38	0-20	GET102	0-30	OC19	0-38
2N3819	0-35	BCY34	0-30	GET103	0-22	OC19	0-37
2N3823	0-60	BCY38	0-40	GET113	0-20	OC20	0-98
2N3823	0-75	BCY39	1-00	GET114	0-15	OC22	0-50
2N5027	0-53	BCY40	0-50	GET115	0-45	OC23	0-60
2N5088	0-33	BCY42	0-25	GET116	0-50	OC24	0-60
2S005	1-00	BCY70	1-15	GET120	0-25	OC25	0-37
2S801	0-50	BCY71	0-20	GET872	0-30	OC25	0-37
2S804	0-75	BCZ10	0-35	GET875	0-25	OC26	0-25
2S801	0-32	BCZ11	0-50	GET880	0-37	OC28	0-60
2S703	0-62	BD121	0-65	GET881	0-25	OC29	0-60
AA129	0-20	BD12					

A modification of the original constant current circuit is employed, due to the need for it to function correctly with a varying supply voltage,  $V_1$ . The two silicon diodes (these can be of any low power type, or alternatively two *npn* silicon transistor base-emitter junctions, forward biased as shown in Fig. 16) provide a constant voltage at the base of TRA—constant, that is, with respect to the positive supply line. With the base and hence emitter so held constant, the 100 ohm resistor passes a constant 7mA current through TRA and hence to the TRZ and VR1 in parallel.

It was from this configuration that the graphs in Fig. 17 were obtained, to show how output voltage varies with output current, and how the level of short circuit current varies with the setting of VR2.

In passing, note that the driving of the TRZ from the input voltage allows the output voltage to be made variable down to zero volts. If TRZ is driven from the output side, output voltages of less than Zener voltage would cease to give regulation.

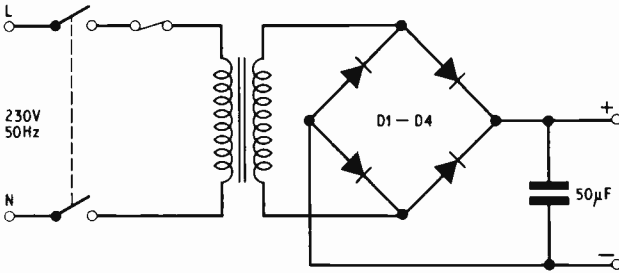


Fig. 18. Suggested mains supply unit for the stabiliser shown in Fig. 14

### VOLTAGE FEEDER

Practical construction of such a stabilised power supply can follow usual techniques. After maximum output current and maximum output voltage have been decided upon, a decision is made on the method of driving the regulator. A simple mains unit is shown in Fig. 18, and the voltage rating of the transformer secondary is chosen to give, at full load current, a value of  $V_1$ , about 4 volts more than the maximum regulated output voltage. Alternatively, a battery or accumulator could provide power.

### HEAT SINK FOR TR1

As for the size of the heat sink required for TR1, calculate first the maximum power dissipated in that transistor. This will be:

$$V_1 - (\text{minimum output voltage used}) \times \text{maximum load current}$$

It is at minimum output voltage and maximum load current that maximum power will be dissipated in TR1, and a suitable heat-sink should be chosen.

Generally speaking, for an OC28 or similar transistor, bolted to a heat-sink with an insulating mica washer, a rise in heat-sink temperature of about 40°C above ambient room temperature can be permitted.

Heat-sinks of various °C/watt ratings are readily available from components stockists.

As an example, for a 1A 9 volts output, driven from a 13 volts supply, with operation down to 3 volts expected, maximum power dissipated in TR1 is  $(13 - 3) \times 1 = 10$  watts, so a heat-sink of 4°C/watt is needed for an OC28. About 20 sq in of 16 s.w.g. aluminium sheet will suffice.

Having thus decided on transformer and heat-sink requirements, the size of the final unit can be settled. VR1, and possibly VR2, are front panel controls, but otherwise layout is unimportant, and can be adapted to suit individual requirements.

### TRICKLE CHARGER FOR SMALL BATTERIES

Mention was made earlier of deriving the supply from an accumulator and this is a useful way of obtaining a good general purpose stabilised voltage for powering many circuits. Recharging of the accumulator can be carried out overnight or a trickle charger can be used while the power supply is in use.

It is worth noting that many 12 volt car batteries can still provide a handy 1A even after their useful life in a car is over.

Constant current output can prove useful in the charging of some types of small batteries.

Batteries such as nickel-cadmium have a low internal resistance; hence, when in a discharged state, they would draw very large currents if the usual constant (or almost constant) voltage charging system is employed. This large current could give rise to overheating, tending to reduce the internal resistance still further and hence allowing thermal runaway to take place, and so leading to destruction of the battery.

However, for battery charging applications, adjust VR2 to give the required current, ensuring that VR1 is set to give a high enough voltage to charge the battery in question when it reaches its full final voltage. The battery manufacturer's instructions should be followed if in doubt.

Otherwise, the constant current circuitry is used as an overload limiter. With VR2 at maximum resistance, short circuit the output terminals; then bring down VR2 until the output current is a little greater than the maximum expected to flow in the unit being powered, under normal conditions.

Thereafter, should excessive current attempt to flow due to a fault, such current will be safely limited to that previously set by VR2.

Although the uses of Zener substitutes so far described have been in power supplies, this does not exhaust their usefulness.

### OTHER USES

Clipping and limiting of waveforms to specific amplitudes can easily be accomplished. In the design of d.c. amplifiers, shifts of voltage by the constant voltage of the Zener substitute enable large gains to be achieved without limiting due to saturation of later stages.

With the ready availability of *npn* silicon transistors for use as substitute Zeners, it is hoped that experimenters will be encouraged to make greater use of them in stabilised power supplies, on the lines suggested, with corresponding improvement in equipment performance. ★

# MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.

## PHOTOCONDUCTIVE CELL DESIGNERS' KIT

Designed primarily for educational establishments as well as industrial organisations interested in developing light activated controls, **Photain Controls** have produced a Photoconductive Cell Designers' Kit which readers may like to experiment with.

The kit consists of five different photoconductive cells together with 13 circuit diagrams each complete with a brief explanation of the circuit. Each diagram enables the student to build devices embracing light intensity measurement; feedback gain controllers; photo switches; signal modulating and musical instrument volume controller.

The kit is available from Photain Controls Ltd., Randalls Road, Leatherhead, Surrey, price £2.

## SOLDERING ACCESSORIES

Leaving one hand free to hold the work piece, the Anextra Solder Feed fits the majority of soldering irons and carries up to 4oz reels of flux cored solder.

Solder from 22 to 18 s.w.g. can be used and is fed to the joint by operating the solder feed trigger.

Supplied with an initial 1oz reel of 60/40 cored 22 s.w.g. solder, the recommended retail price is £4.25. Further details of the Solder Feed is obtainable from **Anextra Ltd.**,

Chiltern Works, 77-78 Chiltern View Road, Uxbridge, Middlesex.

Standard package integrated circuits, despite their numerous advantages, suffer from one major drawback as far as the amateur is concerned. The removal of these units from printed circuit boards, since it is necessary either to remove all traces of solder from all the connecting pin joints or melt all the joints simultaneously.

A range of desoldering heads for the Solderstat HMS miniature irons is an accessory which, using the method of simultaneous desoldering, removes the standard dual-in-line packages within a few seconds is claimed by **Solderstat Ltd.**

The desolder head is placed on the iron in place of the copper bit and aligned with the i.c. connecting pins on the printed circuit board. Both 14-way and 16-way dual-in-line heads are available.

Readers can, of course, use standard i.c. holders available from advertisers when they construct prototype circuits.

## LOW VOLTAGE TOOLS

A range of battery-operated miniature tools capable of operating drills, cleaning brushes, abrasive stones, cutting burrs, polishing mops and other tools for precision work has been introduced by **Expo (Drills) Ltd.**

Two basic models are available. The "Reliant" designed for lighter work such as model making, and has a full load current of 1.5A, and the "Titan Super". Rated torque of the "Reliant" is 1.38oz in (100gm cm.).

For jobs requiring a more powerful tool and for professional applications the "Titan Super", rated at 3.5A on full load, should be used. It has a rated torque of 350 c.m.p. operating at 4,000-9,000 r.p.m.

Accessories include a diamond bonded drill, for gem stones up to 7MOHS, various types of abrasives, cutters and saws. Different

collets and accessories are supplied according to model.

Prices range from £3 to £5.50 and full details are obtainable from Expo (Drills) Ltd., 62 Neal Street, London, W.C.2.

## INSTANT LETTERING

To help finish-off equipment **Instant Plastic Ltd.** have introduced a range of p.v.c. self-adhesive plastic lettering kits.

Designated type K, the kits consist of 40 different sets in five colours, sizes from 10mm ( $\frac{3}{8}$ in) high upwards, in capitals and lower case letters and numerals.

The smallest set contains 578 letters and numerals and the number in each set reduces as the letter size increases.

The K sets cost approximately £1 per set, and details of their other ranges can be obtained from Instant Plastic Ltd., 101 Bramley Road, London, W.10.

## PRINTED CIRCUIT BOARDS

A new price list of printed circuit boards for previously published P.E. projects has just been issued by **P.H. Electronics.**

Copies of the price list can be obtained from P.H. Electronics, Industrial Estate, Sandwich, Kent.

## SWITCH KIT


The mention of the versatile switch kit in the September issue should have included the following firms who are all part of the buying group set up by Home Radio (Components Ltd.).

Crescent Radio, 40 Mayes Road, London, N.22.

Garland Bros., Chesham House, Deptford Broadway, London, S.E.8.

Radioparts, 5 Market Way, Plymouth, Devon.

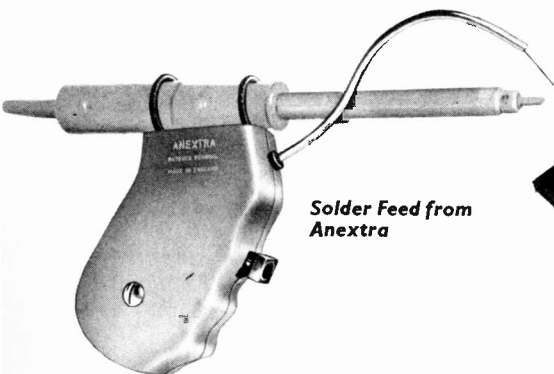Servio Radio, 156-158 Merton Road, Wimbledon, London, S.W.19.



Solder Feed from Anextra



Solderstat I.C. Desolder Heads

Miniature electric tool made by Expo (Drills) Ltd





# SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.  
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

## NEW "SEW" DESIGNS! CLEAR PLASTIC METERS BAKELITE PANEL METERS

TYPE SW. 100 100 x 80 mm		TYPE S-80 80 mm square fronts	
500μA	\$3-35	50μA	\$3-20
1mA	\$3-10	50-0-50μA	\$3-10
20V d.c.	\$3-10	100μA	\$2-75
50V d.c.	\$3-10	100-0-100μA	\$3-10
300V d.c.	\$2-10	500μA	\$3-00
1A d.c.	\$3-10	1mA	\$2-60
5A d.c.	\$3-10	20V d.c.	\$2-60
300V a.c.	\$3-10	50V d.c.	\$2-60
100-0-100μA	\$3-45	300V d.c.	\$2-60
50μA	\$3-60	1A d.c.	\$2-60
50-0-50μA	\$3-45	5A d.c.	\$2-60
100μA	\$3-20	300V a.c.	\$2-60
100-0-100μA	\$3-45	VU Meter	\$3-37

### "SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in. 4 1/2in. fronts.		Type MR.38P. 1 21/32in. square fronts.	
50μA	\$3-60	150mA	\$1-60
50-0-50μA	\$3-10	200mA	\$1-60
100μA	\$3-10	300mA	\$1-60
100-0-100μA	\$3-00	500mA	\$1-60
200μA	\$3-00	750mA	\$1-60
500μA	\$2-80	1A	\$1-60
100-0-500μA	\$2-80	2A	\$1-60
1mA	\$2-80	5A	\$1-60
5A a.c.*	\$2-80	10A	\$1-60
10A a.c.*	\$2-80	30V d.c.	\$1-60
1-0-1mA	\$2-80	15V d.c.	\$1-60
5mA	\$2-80	20V d.c.	\$1-60
10mA	\$2-80	100V d.c.	\$1-60
		150V d.c.	\$1-60
		300V d.c.	\$1-60
		500V d.c.	\$1-60
		1A	\$1-60
		2A	\$1-60
		5A	\$1-60
		10A	\$1-60
		30V a.c.	\$1-70
		15V a.c.	\$1-60
		20V d.c.	\$1-60
		100V d.c.	\$1-60
		150V d.c.	\$1-60
		300V d.c.	\$1-60
		500V d.c.	\$1-60
		1A	\$1-60
		2A	\$1-60
		5A	\$1-60
		10mA	\$1-60
		20mA	\$1-60
		50mA	\$1-60
		100mA	\$1-60
		1mA	\$1-70
		VU meter	\$2-10

Type MR.52P. 2 1/2in. square fronts.		Type MR.45P. 2 1/2in. square fronts.	
50μA	\$3-10	50μA	\$2-10
50-0-50μA	\$2-60	50-0-50μA	\$2-10
100μA	\$2-60	100μA	\$1-90
100-0-100μA	\$2-60	100-0-100μA	\$1-75
200μA	\$2-60	200μA	\$1-75
500μA	\$2-60	500μA	\$1-65
100-0-500μA	\$2-60	500-0-500μA	\$1-60
1mA	\$2-60	1mA	\$1-60
5A a.c.*	\$2-60	2mA	\$1-60
10A a.c.*	\$2-60	5mA	\$1-60
10V d.c.	\$2-60	10mA	\$1-60
		20mA	\$1-60
		50mA	\$1-60
		100mA	\$1-60
		1mA	\$1-70
		VU meter	\$2-10

Type MR.65P. 3 1/2in. 3 1/2in. fronts.		"SEW" BAKELITE PANEL METERS	
50μA	\$3-37	500μA	\$1-90
50-0-50μA	\$2-75	1A	\$1-90
100μA	\$2-75	5A	\$1-90
100-0-100μA	\$2-65	15A	\$1-90
200μA	\$2-65	30A	\$1-90
500μA	\$2-40	50A	\$1-90
100-0-500μA	\$2-20	5V d.c.	\$1-90
1mA	\$2-20	10V d.c.	\$1-90
5A a.c.*	\$2-20	15V d.c.	\$1-90
10A a.c.*	\$2-20	30V d.c.	\$1-90
10V d.c.	\$2-20	50V d.c.	\$1-90
		150V d.c.	\$1-90
		300V d.c.	\$1-90
		500μA a.c.*	\$1-95
		1mA a.c.*	\$1-95
		5A a.c.*	\$1-95
		10A a.c.*	\$1-95
		50A a.c.*	\$1-95
		500μA a.c.*	\$1-95
		1mA a.c.*	\$1-95
		5A a.c.*	\$1-95
		10A a.c.*	\$1-95
		50A a.c.*	\$1-95
		VU meter	\$2-10

**\* MOVING IRON — ALL OTHERS MOVING COIL**  
 Please add postage


### "SEW" EDUCATIONAL METERS



Type ED.107. Size overall 100mm x 90mm x 108mm. A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible to working. Available in the following ranges:

50μA	\$5-00	20V d.c.	\$4-40
100μA	\$4-65	50V d.c.	\$4-40
1mA	\$4-40	300V d.c.	\$4-40
50-0-50μA	\$4-65	Dual range	
1-0-1mA	\$4-40	500mA/5A d.c.	\$4-65
1A d.c.	\$4-40	5V/50V d.c.	\$4-65
5A d.c.	\$4-40		
10V d.c.	\$4-40		

### EDGEWISE METERS

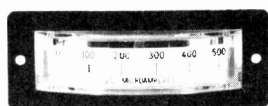

PE.70 3 1/2in. 1 1/2in. deep.	
50μA	\$3-10
50-0-50μA	\$3-00
100μA	\$3-00
100-0-100μA	\$2-90
200μA	\$2-90
500μA	\$2-75
1mA	\$2-45
300V a.c.	\$3-45
VU meter	\$3-40

# MULTIMETERS for EVERY purpose!

**MODEL TE-200.** 20,000 O.P.V. Mirror scale, overload protection. 0/5/25/125/1,000V d.c. 0/10/50/250/1,000V a.c. 0/50μA/200mA. 0/60K/6 Meg. —20 to +62dB. \$3.75. P. & P. 15p.

**TKM MODEL MD.120.** Mirror scale. 20kΩ/volt. 60/300/600/3,000V d.c. 60/120/1,200V a.c. Current 0-60μA/0-12/0-300mA. 0-60kΩ/0-6MΩ —20 to +63dB. \$4.62. P. & P. 15p.

**MODEL 500.** 80,000 O.P.V. with overload protection, mirror scale 0/5/25/100/250/500/1,000V d.c. 0/25/10/25/100/250/500/1,000V a.c. 0/50μA/50/600 mA. 12 amp. d.c. 0/60K/6 Meg. 62 Meg. Ω. \$3.75. Post paid.

**TKM LAB TESTER.** 100,000 O.P.V. 6 1/2in. scale buzzer short circuit check. Sensitivity: 100,000 OPV d.c. 5/Volt a.c. D.c. volts: 0.5, 2.5, 10, 50, 250, 1,000V. D.c. current: 0.5, 2.5, 10, 50, 250, 1,000μA. Resistance: 1K, 10K, 100 meg. Decibels: —10 to +49dB. Plastic case with carrying handle, size 7 1/2in x 6 1/2in x 3 1/2in. \$18.90. P. & P. 25p.

**ROUND SCALE TYPE PENCIL TESTER MODEL TS.68**

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V d.c. 2.5/10/50/250/500/1000V a.c. D.c. current 100 mA / 1 / 10 / 100mA/A. Resistance: 300 ohms / 3 / 30 / 300Ω / 3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$25.97 P. & P. 25p

**TKM MODEL 117 F.E.T. ELECTRONIC VOLTMETER**  
 Battery operated, 11 meg input, 26 ranges. Large 4 1/2in mirror scale. Size 5 1/2in x 4 1/2in. D.c. volts 0.3-1,200V. A.c. volts 3-300V R.M.S. 8.0-800V P-P. D.c. current 0.12-12mA. Resistance up to 2,000MΩ. Decibels —20 to +61dB. Complete with leads/instructions. \$17.50. P. & P. 25p.

**T.E.40 HIGH SENSITIVITY A.C. VOLTMETER**  
 10 meg. input 10 ranges: -01 / -003 / -1 / -3 / 1 / 3 / 10 / 30 / 100 / 300V. R.M.S. 4c/s. 1-2Mc/s. Decibels —40 to +50dB. Supplied brand new complete with leads and instructions. Operation 230V a.c. \$17.50. Carr. 25p.

**TE22 SINE SQUARE WAVE AUDIO GENERATORS**  
 8ine: 20c/s to 200 kc/s on 4 bands. Square: 20c/s to 30 kc/s. Output imped-ance 5,000 ohms. 200/250V a.c. Supplied brand new and guaranteed with instruction manual and leads. \$16.50. Carr. 37p.

**TE-20RF SIGNAL GENERATOR**  
 Accurate wide range signal generator covering 120 kc/s-260 Mc/s on 6 bands. Directly calibrated variable R.F. attenuator. Operation 200/240V a.c. Brand new with instructions. \$16. P. & P. 37p. S.A.E. for details.

**270° WIDE ANGLE 1mA METERS**  
 MW1-6 60mm square \$3.75. MW1-8 80mm square \$4.97. P. & P. extra.

**MODEL PL436.** 20kΩ/Volt d.c. 8kΩ/Volt a.c. Mirror scale. 0-6/3/12/30/120/600V d.c. load. 0-30/120/600V a.c. 50/600μA/600mA. 10/100k/1Meg/10 meg Ω. —20 to +46dB. \$6.97. P. & P. 12ip.

**MODEL 5025.** 57 ranges, giant 5 1/2in meter. Sensitivity reverse switch. Sensitivity: 50K/Volt d.c. 5K/Volt a.c. D.c. Volts: 0-125, 0-25, 1.5, 5, 10, 25, 50, 125, 250, 500, 1,000V. A.c. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1,000V. D.c. current: 25, 50, 100, 250, 500mA. 5, 10A. Resistance: 2K, 10K, 100K, 1 meg. 10 meg. Decibels: —20 to +85dB. \$12.50. P. & P. 17ip.

**TKM MODEL TW-200B.** Features Resetttable Overload Protection. Sensitivity: 20KΩ/Volt d.c. 5KΩ/Volt a.c. D.c. volts: 0-0.5, 2.5, 10, 50, 250, 1,000V. D.c. currents: 0-0.05, 0.5, 5, 50, 500mA. Resistance: 0-5K, 0-5, 0-500K, 5 meg. Decibels: —20 to +52dB. \$11.60. P. & P. 17ip.

**RUSSIAN 22 RANGE MULTIMETER**  
 Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V d.c. 2.5/10/50/250/500/1000V a.c. D.c. current 100 mA / 1 / 10 / 100mA/A. Resistance: 300 ohms / 3 / 30 / 300Ω / 3MΩ. Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE \$25.97 P. & P. 25p

**TO-2 PORTABLE OSCILLOSCOPE**  
 A general purpose low cost economy oscilloscope for everyday use. Y amp. Bandwidth 2 CPS-1 MHz. Input Imp. 2 meg Ω 25 P.F. Illuminated scale. 9 1/2in. tube. 115 x 180 x 230mm. Weight 8lb. 220/240V a.c. Supplied brand new with hand-book. \$22.50. Carr. 50p.

**HONEYWELL DIGITAL VOLTMETER VT.100**  
 Can be panel or bench mounted. Basic meter measures 1 volt d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug-in cards. Specification: Accuracy: ± 0.2, ± 1 digit. Resolution: 1mV. No. of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1.999) Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110-230V a.c. 50/60 cycles. Overall size: 5 1/2in. x 2 3/16in. x 8 3/16in. AVAILABLE BRAND NEW AND FULLY GUARANTEED AT APPROX. HALF PRICE \$49.97 Carr. 50p

**G. W. SMITH & CO (RADIO) LTD.**  
 Also see next two pages

# SEMI-CONDUCTORS / VALVES

## ALL DEVICES BRAND NEW AND FULLY GUARANTEED

Transistors	2N3414	2N3445	35p	BC114	15p	BFW90	22p	NK2119	30p
2G301	2N3416	2N3459	40p	BC115	15p	BFW91	20p	NK2223	27p
2G302	2N3417	2N3460	40p	BC116	15p	BFW92	20p	NK2224	27p
2G303	2N3418	2N3461	40p	BC117	15p	BFW93	20p	NK2225	27p
2G410	2N3525	2N3568	40p	BC224	15p	BFW200	20p	NK2332	27p
2G411	2N3526	2N3569	40p	BC225	15p	BFW20			



# DISCOUNTS UP TO

# 60% ON BRANDED GOODS

ALL BRAND NEW in manufacturer's sealed cartons GUARANTEED 12 MONTHS

SONY · LEAK · SINCLAIR · TELETON · ARMSTRONG · THORENS · PHILIPS · K.E.F. · TEAC · ROGERS · PIONEER

**SPECIAL OFFER £18**

Garrard SP25 Mk. III  
Goldring G800H  
Teak plinth and tinted cover.  
Ready wired for immediate use.  
Please add £1.25 for post and packing.

Sansui 555 £62.00  
Sansui AU666 £75.00  
Rotel 301 £32.75  
Rotel 601 £49.80  
Sinclair 2000 Mk. II £22.50  
Sinclair 3000 £32.50  
Sinclair PRO 60/2 + Z30 PZ5 £15.00  
Sinclair PRO 60/2 + Z30 PZ6 £17.75  
Sinclair PRO 60/2 + Z50 PZ8/Trans £22.95  
Sinclair AFU £4.70  
Teleton SAQ206B (New Prod.) £19.95  
Wharfedale £49.75  
Sinclair IC12 integrated circuit amplifier £1.85

## TURNTABLES

Please add 50p for P. & P.  
Garrard SP25 Mk. III £9.95  
Garrard 2025TC with stereo cart. £8.00  
Garrard 2025TC with Sonotone 9TAHC £8.95  
Garrard 3000 with Sonotone 9TAHC £10.25  
Garrard SL65B £13.25  
Garrard AP76 £19.95  
Garrard 401 £27.00  
BSR MP60 £36.00  
Pioneer PL12AC £10.00  
Thorens TD125 £62.50  
Thorens 150ABII £42.50  
Goldring GL69/2 £19.50  
Goldring GL69 P2 £26.50  
Goldring GL75 £27.50  
Goldring GL75 P £35.75

## CARTRIDGES

Please add 10p for P. & P.  
Goldring G850 £3.75  
Goldring G800 £4.95  
Goldring G800 £4.95  
Goldring G800E £10.50  
Goldring G800SE £15.25  
Sonotone 9TAHC Diamond £1.75  
Shure M3DM £4.75  
Shure M445/7/C £7.00  
Shure M55 £8.75  
Shure M75E £12.50  
Shure M45 Type 2 £28.00  
Shure M14 £7.00  
Shure M31E £8.50  
Shure M32E £8.00  
Audio Technica AT66 £4.95  
Audio Technica AT35 £12.95

## AMPLIFIERS

Please add 50p for P. & P.  
Alpha Highgate FA212 £27.50  
Alpha Highgate FA300 £29.00  
Alpha Highgate FA400 £33.00  
Armstrong 521 (cased) £41.95  
Amstrad 8000 Mk. II £18.95  
Amstrad 8000 £17.70  
Amstrad IC2000 £34.00  
Dulci 207 £15.95  
Dulci 207m £21.00  
Leak 30 Delta Range (New Prod.) £50.25  
Leak 70 Delta Range (New Prod.) £60.25  
Metrosound ST20 £24.75  
Metrosound ST20E £26.00  
Philips R500 £18.00  
Pioneer SA500 £36.00  
Pioneer SA700 £65.00  
Pioneer SA900 £92.00  
Rogers R/brook Chassis £35.00  
Rogers R/brook Cased £39.00  
Rogers R/bourne Chassis £43.75  
Rogers R/bourne Cased £48.00  
Sansui AU101 £32.00

## PLINTHS & COVERS

(as illustrated)



**£2.95**

(As illustrated) Plus 55p post and packing. Finished in real teak veneer with tinted dust cover. Ready to use (fully assembled). Suitable for Garrard SP25, 2025TC, 3000, AT50, 2000, 2500, 3500, 5100, 1025, SL65B; Also for BSR, McDonald MP60 and others.

For AP76; AP75; SL72B; SL75; SL95B; £4 plus 55p P. & P. Also finished in walnut to match Japanese equipment—at no extra charge.

# GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE4) 174 Pentonville Road, London, N1. Telephone 01-278 1769  
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. LATE NIGHT FRIDAY 7 p.m.

**MAIL ORDERS.** Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. CALLERS: Please note that cheques can only be accepted together with cheque cards (not Barclay Card).

2 minutes from KING'S CROSS EUSTON & ST PANCRAS on main road leading to the East and West Country

# LST FOR SIEMENS, NEWMARKET, IR, RCA MULLARD, TEXAS, FERRANTI, GE

AC107 37p	BSY29 25p	NKT781 29p	IN4007 20p
AC126 25p	BSY95A 15p	NKT10339 25p	IN4148 7p
AC127 25p	BY100 20p	NKT10419 19p	2G302 19p
AC128 20p	BYX10 15p	NKT10519 22p	2G371 15p
AC151 12p	BYZ10 40p	NKT20329 30p	2G374 25p
AC176 25p	BYZ12 30p	0013 31p	2N174 80p
AC187 30p	BYZ13 20p	NKT80111 67p	2N385A/ 2N388A 75p
AC188 30p	BZV8/ 15p	NKT80112 83p	2N404 20p
ACV17 29p	C3V3 15p	NKT80113 1.00	2N696 15p
ACV18 20p	C3V6 15p	NKT80211 75p	2N697 75p
ACV19 20p	C3V9 15p	NKT80212 75p	2N698 30p
ACV20 19p	CAV3 15p	NKT80213 75p	2N706 10p
ACV21 19p	CAV7 15p	OA5 25p	2N706A 12p
ACV22 19p	CSV1 15p	OA7 8p	2N708 16p
ACV40 15p	CSV6 15p	OA7 8p	2N711 37p
AD140 55p	C6V2 15p	OA7 8p	2N711A 37p
AD149 57p	C6V8 15p	OA7 8p	2N914 20p
AD161 37p	C7V5 15p	OA7 8p	2N918 42p
AD162 37p	C8V2 15p	OA7 8p	2N1090 30p
AF106 24p	C8V2 15p	OA7 8p	2N1091 33p
AF114 25p	C9V1 15p	OA7 8p	2N1131 30p
AF115 25p	C10 15p	OA7 8p	2N1132 30p
AF116 25p	C11 15p	OA7 8p	2N1133 30p
AF117 25p	C12 15p	OA7 8p	2N1134 30p
AF118 44p	C13 15p	OA7 8p	2N1135 30p
AF124 25p	C15 15p	OA7 8p	2N1136 30p
AF126 17p	C16 15p	OA7 8p	2N1137 30p
AF139 33p	C18 15p	OA7 8p	2N1138 30p
AF186 40p	C21 15p	OA7 8p	2N1139 30p
AF239 37p	C24 15p	OA7 8p	2N1140 30p
ASV26 25p	C27 15p	OA7 8p	2N1141 30p
ASV27 30p	C30 15p	OA7 8p	2N1142 30p
ASV28 30p	D13T1 45p	OA7 8p	2N1143 30p
ASZ19 37p	MJES20 75p	OA7 8p	2N1144 30p
ASZ21 37p	MJ480 97p	OA7 8p	2N1145 30p
AUY10 £1.50	MJ481 97p	OA7 8p	2N1146 30p
BA115 8p	MJ490 £1.00	OA7 8p	2N1147 30p
BC107 12p	MJ491 £1.35	OA7 8p	2N1148 30p
BC108 12p	MPF102 43p	OA7 8p	2N1149 30p
BC109 12p	MPF103 37p	OA7 8p	2N1150 30p
BC147 15p	MPF104 37p	OA7 8p	2N1151 30p
BC148 15p	MPF105 40p	OA7 8p	2N1152 30p
BC149 15p	NKT124 30p	OA7 8p	2N1153 30p
BC158 17p	NKT125 30p	OA7 8p	2N1154 30p
BC167 11p	NKT126 37p	OA7 8p	2N1155 30p
BC168 10p	NKT128 25p	OA7 8p	2N1156 30p
BC169 19p	NKT135 26p	OA7 8p	2N1157 30p
BC169C 19p	NKT137 32p	OA7 8p	2N1158 30p
BC182 12p	NKT210 25p	OA7 8p	2N1159 30p
BC182L 10p	NKT211 25p	OA7 8p	2N1160 30p
BC183 9p	NKT212 25p	OA7 8p	2N1161 30p
BC183L 9p	NKT213 25p	OA7 8p	2N1162 30p
BC184 15p	NKT214 23p	OA7 8p	2N1163 30p
BC184L 15p	NKT215 21p	OA7 8p	2N1164 30p
BC212 17p	NKT216 46p	OA7 8p	2N1165 30p
BC212L 12p	NKT217 50p	OA7 8p	2N1166 30p
BCY30 25p	NKT218 25p	OA7 8p	2N1167 30p
BCY31 48p	NKT219 25p	OA7 8p	2N1168 30p
BCY32 50p	NKT223 27p	OA7 8p	2N1169 30p
BCY33 20p	NKT224 25p	OA7 8p	2N1170 30p
BCY34 25p	NKT225 21p	OA7 8p	2N1171 30p
BCY38 30p	NKT229 29p	OA7 8p	2N1172 30p
BCY70 19p	NKT237 31p	OA7 8p	2N1173 30p
BCY71 37p	NKT238 19p	OA7 8p	2N1174 30p
BCY72 10p	NKT239 23p	OA7 8p	2N1175 30p
BD121 £1.10	NKT240 20p	OA7 8p	2N1176 30p
BD123 £1.10	NKT241 21p	OA7 8p	2N1177 30p
BD124 £1.03	NKT242 15p	OA7 8p	2N1178 30p
BD131 75p	NKT243 56p	OA7 8p	2N1179 30p
BD132 75p	NKT244 17p	OA7 8p	2N1180 30p
BDY20 £1.05	NKT245 17p	OA7 8p	2N1181 30p
BF115 25p	NKT261 21p	OA7 8p	2N1182 30p
BF163 40p	NKT262 19p	OA7 8p	2N1183 30p
BF167 25p	NKT264 21p	OA7 8p	2N1184 30p
BF173 30p	NKT271 18p	OA7 8p	2N1185 30p
BF177 25p	NKT272 17p	OA7 8p	2N1186 30p
BF178 52p	NKT274 18p	OA7 8p	2N1187 30p
BF180 37p	NKT275 23p	OA7 8p	2N1188 30p
BF181 37p	NKT279A 12p	OA7 8p	2N1189 30p
BF184 25p	NKT281 29p	OA7 8p	2N1190 30p
BF185 25p	NKT282 87p	OA7 8p	2N1191 30p
BF194 17p	NKT304 79p	OA7 8p	2N1192 30p
BF195 15p	NKT351 75p	OA7 8p	2N1193 30p
BF196 15p	NKT402 77p	OA7 8p	2N1194 30p
BF200 35p	NKT403 65p	OA7 8p	2N1195 30p
BFX13 25p	NKT404 60p	OA7 8p	2N1196 30p
BFX29 31p	NKT405 79p	OA7 8p	2N1197 30p
BFX84 26p	NKT406 62p	OA7 8p	2N1198 30p
BFX85 34p	NKT420 £1.83	OA7 8p	2N1199 30p
BFX86 25p	NKT451 58p	OA7 8p	2N1200 30p
BFX87 30p	NKT452 58p	OA7 8p	2N1201 30p
BFX88 25p	NKT453 58p	OA7 8p	2N1202 30p
BFY50 23p	NKT454 50p	OA7 8p	2N1203 30p
BFY51 19p	NKT603F 30p	OA7 8p	2N1204 30p
BFY52 20p	NKT613F 30p	OA7 8p	2N1205 30p
BFY53 16p	NKT674F 30p	OA7 8p	2N1206 30p
BFY90 67p	NKT676F 30p	OA7 8p	2N1207 30p
BSX19 16p	NKT677F 28p	OA7 8p	2N1208 30p
BSX20 16p	NKT678F 28p	OA7 8p	2N1209 30p
BSX21 37p	NKT717 44p	OA7 8p	2N1210 30p
BSY27 20p	NKT773 25p	OA7 8p	2N1211 30p
BY29 25p	BY29 25p	OA7 8p	2N1212 30p
BY100 20p	BY100 20p	OA7 8p	2N1213 30p
BYX10 15p	BYX10 15p	OA7 8p	2N1214 30p
BYZ10 40p	BYZ10 40p	OA7 8p	2N1215 30p
BYZ12 30p	BYZ12 30p	OA7 8p	2N1216 30p
BYZ13 20p	BYZ13 20p	OA7 8p	2N1217 30p
BZV8/ 15p	BZV8/ 15p	OA7 8p	2N1218 30p
C3V3 15p	C3V3 15p	OA7 8p	2N1219 30p
C3V6 15p	C3V6 15p	OA7 8p	2N1220 30p
C3V9 15p	C3V9 15p	OA7 8p	2N1221 30p
CAV3 15p	CAV3 15p	OA7 8p	2N1222 30p
CAV7 15p	CAV7 15p	OA7 8p	2N1223 30p
CSV1 15p	CSV1 15p	OA7 8p	2N1224 30p
CSV6 15p	CSV6 15p	OA7 8p	2N1225 30p
C6V2 15p	C6V2 15p	OA7 8p	2N1226 30p
C6V8 15p	C6V8 15p	OA7 8p	2N1227 30p
C7V5 15p	C7V5 15p	OA7 8p	2N1228 30p
C8V2 15p	C8V2 15p	OA7 8p	2N1229 30p
C8V2 15p	C8V2 15p	OA7 8p	2N1230 30p
C9V1 15p	C9V1 15p	OA7 8p	2N1231 30p
C10 15p	C10 15p	OA7 8p	2N1232 30p
C11 15p	C11 15p	OA7 8p	2N1233 30p
C12 15p	C12 15p	OA7 8p	2N1234 30p
C13 15p	C13 15p	OA7 8p	2N1235 30p
C15 15p	C15 15p	OA7 8p	2N1236 30p
C16 15p	C16 15p	OA7 8p	2N1237 30p
C18 15p	C18 15p	OA7 8p	2N1238 30p
C21 15p	C21 15p	OA7 8p	2N1239 30p
C24 15p	C24 15p	OA7 8p	2N1240 30p
C27 15p	C27 15p	OA7 8p	2N1241 30p
C30 15p	C30 15p	OA7 8p	2N1242 30p
D13T1 45p	D13T1 45p	OA7 8p	2N1243 30p
MJES20 75p	MJES20 75p	OA7 8p	2N1244 30p
MJ480 97p	MJ480 97p	OA7 8p	2N1245 30p
MJ481 97p	MJ481 97p	OA7 8p	2N1246 30p
MJ490 £1.00	MJ490 £1.00	OA7 8p	2N1247 30p
MJ491 £1.35	MJ491 £1.35	OA7 8p	2N1248 30p
MPF102 43p	MPF102 43p	OA7 8p	2N1249 30p
MPF103 37p	MPF103 37p	OA7 8p	2N1250 30p
MPF104 37p	MPF104 37p	OA7 8p	2N1251 30p
MPF105 40p	MPF105 40p	OA7 8p	2N1252 30p
NKT124 30p	NKT124 30p	OA7 8p	2N1253 30p
NKT125 30p	NKT125 30p	OA7 8p	2N1254 30p
NKT126 37p	NKT126 37p	OA7 8p	2N1255 30p
NKT128 25p	NKT128 25p	OA7 8p	2N1256 30p
NKT135 26p	NKT135 26p	OA7 8p	2N1257 30p
NKT137 32p	NKT137 32p	OA7 8p	2N1258 30p
NKT210 25p	NKT210 25p	OA7 8p	2N1259 30p
NKT211 25p	NKT211 25p	OA7 8p	2N1260 30p
NKT212 25p	NKT212 25p	OA7 8p	2N1261 30p
NKT213 25p	NKT213 25p	OA7 8p	2N1262 30p
NKT214 23p	NKT214 23p	OA7 8p	2N1263 30p
NKT215 21p	NKT215 21p	OA7 8p	2N1264 30p
NKT216 46p	NKT216 46p	OA7 8p	2N1265 30p
NKT217 50p	NKT217 50p	OA7 8p	2N1266 30p
NKT218 25p	NKT218 25p	OA7 8p	2N1267 30p
NKT219 25p	NKT219 25p	OA7 8p	2N1268 30p
NKT223 27p	NKT223 27p	OA7 8p	2N1269 30p
NKT224 25p	NKT224 25p	OA7 8p	2N1270 30p
NKT225 21p	NKT225 21p	OA7 8p	2N1271 30p
NKT229 29p	NKT229 29p	OA7 8p	2N1272 30p
NKT237			

# BEST BUY IN TTL!!

SIEMENS QUALITY PLUS BARGAIN PRICES PLUS LST SERVICE  
A full design range of high quality TTL available from LST your Officially Appointed Siemens Distributors

Equal to	Description	Part No.	1-24	25-99	100 up	Equal to	Description	Part No.	1-24	25-99	100 up	Equal to	Description	Part No.	1-24	25-99	100 up
7400	Quadruple 2-input NAND gate	FLH 101	20p	16p	14p	7444	Excess 3 gray to decimal decoder	371	£1.45	£1.20	£1.08	7486	Quadruple 2-input exclusive-OR element	341	33p	27p	23p
7401	Quadruple 2-input NAND gate with open collector output	201	20p	16p	14p	7450	Expandable dual 2-wide 2-input AND-OR-INVERT gate	151	20p	16p	14p	7490	Decade counter	161	80p	67p	57p
7402	Quadruple 2-input NOR gate	191	20p	16p	14p	7451	Dual 2-wide 2-input AND-OR-INVERT gate	161	20p	16p	14p	7491A	8-bit shift register	221	£1.28	£1.07	92p
7403	Quadruple 2-input NAND gate with open collector output	291	20p	16p	14p	7453	Expandable 4-wide 2-input AND-OR-INVERT gate	171	20p	16p	14p	7492	Divide-by-12 counter	171	85p	71p	61p
7404	Hex inverter	211	25p	21p	18p	7454	4-wide 2-input AND-OR-INVERT gate	181	20p	16p	14p	7493	4-bit binary counter	181	80p	67p	57p
7405	Hex inverter with open collector output	271	25p	21p	18p	7460	Dual 4-input expander	101	20p	16p	14p	7494	4-bit shift register	231	£1.13	94p	81p
7408	Quad 2-input positive AND gate	381	25p	21p	18p	7470	J-K flip flop	101	45p	37p	32p	7495	4-bit shift register	191	87p	72p	62p
7409	Quad 2-input positive AND gate open collector	391	25p	21p	18p	7472	J-K master-slave flip-flop	111	32p	27p	23p	7496	5-bit shift register	261	£1.48	£1.21	£1.05
7410	Triple 3-input NAND gate	111	20p	16p	14p	7473	Dual J-K master-slave flip-flop	121	45p	40p	35p	74107	Dual J-K master-slave flip-flop with preset and clear	301	£1.64	£1.37	£1.17
7413	Schmitt Trigger	351	35p	29p	25p	7474	Dual D-type edge triggered flip-flop	141	46p	38p	33p	74121	Monostable multivibrator	271	52p	43p	36p
7420	Dual 4-input NAND gate	121	20p	16p	14p	7475	Quad bistable latch	151	45p	40p	37p	74141	BCD to decimal decoder and nixie driver	101	£1.22	£1.02	87p
7430	8-input NAND gate	131	20p	16p	14p	7476	Dual J-K master-slave flip-flop with preset and clear	131	45p	40p	36p	74190	Synchronous up down 4-bit decade counter with one line mode control	201	£1.80	£1.48	£1.27
7440	Dual 4-input NAND buffer	141	24p	20p	17p	7480	Gated full adder	221	67p	56p	48p	74191	Synchronous up down 4-bit binary counter with one line mode control	211	£1.80	£1.48	£1.27
7442	BCD to decimal decoder TTL output	281	£1.16	94p	81p	7482	2-bit binary full-adder	231	87p	73p	62p	74192	Synchronous up down 4-bit decade counter	241	£1.74	£1.45	£1.25
7443	Excess 3 to decimal decoder	361	£1.45	£1.20	£1.08	7483	Four-bit binary full adder	241	£1.32	£1.16	£1.00	74193	As above—binary counter	251	£1.74	£1.45	£1.25

TYPES MAY BE MIXED TO QUALIFY FOR PRICE BREAKS DATA BOOKLET 20p

## CONTRACT ORDER PRICES AND BULK QUANTITY PRICES QUOTED ON REQUEST

### NEW PRODUCT !!

7 SEGMENT INDICATOR  
3015F @ £2.00.

NOW IN STOCK AT LST—MINIATURE DUAL-IN-LINE PACKAGE HOUSING. A 7-SEGMENT INDICATOR WHICH SHOWS 0.9 PLUS A DECIMAL POINT. IDEAL FOR DIGITAL CLOCKS ETC. USE WITH SIEMENS DECODER DRIVER. IC FL1121/SN7447 (£1.32).

### NEW PRODUCT !!

LOW COST DIL SOCKETS

16 PIN DUAL IN LINE 17p  
14 PIN DUAL IN LINE 15p

BZY88 SERIES ZENERS 400mW 5%

All voltages available 3:3 to 33 Volt

25 + 12p 100 + 10p  
500 + 9p 1000 + 8p

### SPECIAL OFFER IN 4000 SERIES 1 AMP RECTIFIERS

p.i.v.	1-49	50+	100+	
IN4001	50	070	060	050
IN4002	100	070	065	060
IN4003	200	090	085	070
IN4004	400	100	090	080
IN4005	600	120	100	090
IN4006	800	140	130	110
IN4007	1000	190	150	120

p.i.v.	500+	1000+	
IN4001	50	045	040
IN4002	100	055	045
IN4003	200	060	050
IN4004	400	070	060
IN4005	600	075	070
IN4006	800	100	085
IN4007	1000	110	100

Should any item be out of stock we reserve the right to supply at higher voltage rated item at no extra charge.

TERMS: Cash with order please. Postage: 10p inland, 25p Europe. Elsewhere—send plenty—will refund excess. All goods carry manufacturers' warranty. Counter Sales—Same Address.

### Mullard Metallised Polyester C280 series

Mfd.	250v.	350v.	500v.
0.01	...	...	3p
0.015	...	...	3p
0.022	...	...	3p
0.033	...	...	3p
0.047	...	...	4p
0.068	...	...	4p
0.1	...	...	4p
0.15	...	...	5p
0.22	...	...	5p
0.33	...	...	7p
0.47	...	...	8p
0.68	...	...	11p
1.0	...	...	14p
1.5	...	...	20p
2.2	...	...	24p

### Mullard Electrolytic C437 series

Mfd.	Volt.	Wkg.
250	16	9p
160	16	12p
640	16	15p
1,000	16	18p
160	25	9p
250	25	12p
400	25	15p
640	25	18p
100	40	9p
160	40	12p
250	40	15p
400	40	18p

### Mullard Sub-Miniature Ceramic Plate C333 series

63 volt working. Range 18pf to 220pf (usual pref. values). Packs of 6 (any values) 15p

### CAPACITORS—Mullard Miniature Electrolytic C426 series

Mfd.	Volt.	Wkg.
2.5	16	8p
10	16	6p
20	16	6p
40	16	6p
80	16	6p
1.6	25	8p
6.4	25	6p
12.5	25	6p
25	25	6p
50	25	6p
80	25	6p
1	40	8p
4	40	6p
8	40	6p
16	40	6p
32	40	6p
50	40	6p

### ENCAPSULATED BRIDGES

Type No.	Current	Rms. Volts.
W005	1 Amp	50
W06	1 Amp	600

### R.C.A.

CA3004	£1.80
CA3005	£1.20
CA3011	75p
CA3013	£1.05
CA3014	£1.25
CA3018	85p
CA3020	£1.30
CA3028A	75p
CA3035	£1.25
CA3043	£1.40
CA3044	£1.20
CA3046	75p
CA3047	£1.40
CA3048	£2.05
CA3049	£1.60
CA3052	£1.65
CA3090Q	£3.46

### BARGAIN OP-AMPS!!

LM709C	60p
LM741CN	95p

### TRIACS

2N5755	2.5A (RMS) 400 PIV TO-5 Mod.	95p
40486	6 Amp (RMS) 400 PIV TO-5 Mod.	£1.20
40430	6 Amp (RMS) 400 PIV TO-66	£1.01
40432	6 Amp (RMS at 75° Amb.) 400 PIV* TO-5 Mod.	£1.50
40512	2.2 Amp (RMS at 25° Amb.) 400 PIV*	£1.45
40576	15A (RMS) 400 PIV TO-66	£1.70

### LINEAR AND DIGITAL ICs

Fairchild	1-11	12-24	25+
µL900	40p	35p	32p
µL914	40p	35p	32p
µL923	53p	50p	47p

### G.E. (U.S.A.)

PA230	Pre-amp	£1.10
PA234	1 watt Amp	£1.00
PA237	2 watt Amp	£1.87
PA246	5 watt Amp	£2.63
PA424	Zero Volt Switch	£2.45

### Mullard

TAA263	Linear Amp.	75p
TAA293	Gen. Purp. Amp	£1.00
TAA310	Record/Playback Amp	£1.50
TAA320	MOS LF Amp	65p
TAD100	IC Receiver	£1.97
TAD110	AM/FM Receiver	£1.97

### BARGAIN TRIAC OFFER

40533 RCA 400V 2.5 AMP 60p

### THYRISTORS

CR1/051C	1 Amp 50 PIV TO-5	40p
CR1/401C	1 Amp 400 PIV TO-5	50p
2N3525	5 Amp 400 PIV TO-66	£1.09
40739	10 Amp 400 PIV Stud Mtg.	£1.65

### ULTRASONIC TRANSDUCERS



Operate at 40 kc/s. Can be used for remote control systems without cables or electronic links. Type 1404 transducers can transmit and receive. FREE: With each pair our complete transmitter and receiver circuit. PRICE (Sold only in pairs) £5.90

## LST ELECTRONIC LTD

Mail Order Dept.: (PE) 7 Coptfold Road, Brentwood, Essex  
Industrial Sales Dept.: Tel.: Brentwood 226470/1 Telex 99443


# A new magazine

**everyday** DEC.71  
**electronics** 15p


**A NEW MAGAZINE  
BRINGING A FASCINATING  
HOBBY TO EVERYONE**  
PROJECTS EASY TO CONSTRUCT  
THEORY SIMPLY EXPLAINED

**CIRCUIT BUILDING  
DEMO-DECK**  
FOR THE BEGINNER


...AND THE EXPERIMENTER

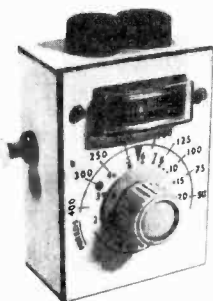


**PHOTOGRAPHIC  
COLOUR METER**

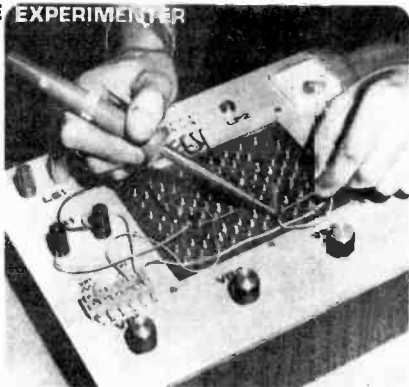

**FUZZ BOX**

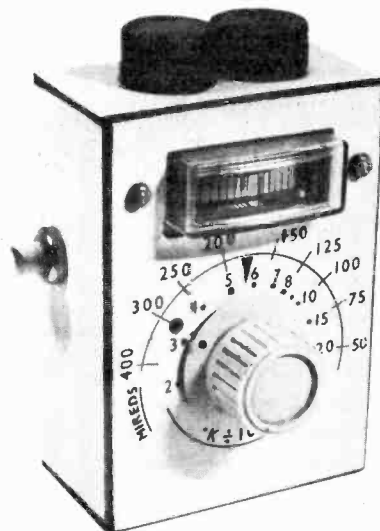

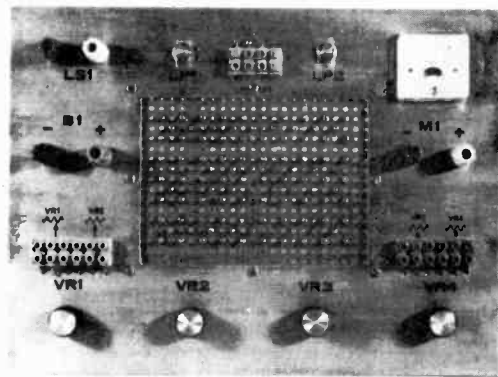**NO. 2**  
*Out Friday, November 19*  
**TO AVOID SELL-OUT  
DISAPPOINTMENT  
ORDER THIS EXCITING  
NEW MAGAZINE  
TODAY**



PUBLISHED BY IPC MAGAZINES LTD.

# *bringing a fascinating hobby to everyone*

## **PROJECTS EASY TO CONSTRUCT THEORY SIMPLY EXPLAINED**

This exciting new magazine presents easy-to-follow, step-by-step illustrated articles on useful and imaginative electronic gadgets for the home, car and other hobbies.

*BUILD THESE USEFUL PROJECTS . . .*

### **'FUZZ' BOX**

Build this ingenious little unit in a matter of hours . . . gives an interesting effect to guitar playing!

### **PHOTOGRAPHIC COLOUR TEMPERATURE METER**

Are you a keen photographer . . . then make this inexpensive colour temperature meter for a quick indication of the colour filters necessary for correction in any light!

### **DEMO DECK**

Are you apt to experiment . . . this circuit-building deck has been specially designed for the 'Teach-In' series. It will also be useful for general experimental work and for prototype testing.

*ALSO—TEACH-IN . . .* A beginner's series dealing with the theory and practice of electronics . . . this month—the electric current, resistance and resistors.

# **everyday** only 15p **electronics**

# G. F. MILWARD 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

**SPECIAL 50p PACKS. ORDER 10 PACKS AND WE WILL INCLUDE AN EXTRA ONE FREE ! ! ! !**

<b>RESISTORS, 1/4 watt</b>	
assorted	100 50p
Wire-wound 1 to 3 watt	20 50p
5 to 7 watt	15 50p
10 watts	10 50p
Multi-tapped	12 50p
<b>PAPER CONDENSERS</b>	
Tv types	50 50p
Miniature	100 50p
<b>ELECTROLYTIC CONDENSERS</b>	
Suitable for Mains	
Radio/Tv	10 50p
Transistor types	20 50p
Mixed (both types)	15 50p
<b>POLYSTYRENE CONDENSERS</b>	
MULLARD POLYESTER COND.	50 50p
SILVER MICA WIRE-WOUND 3-Watt	100 50p
<b>SLIDERS</b>	
VOLUME CONTROLS	15 50p
Assorted	5 50p
<b>NUTS AND BOLTS. Mixed length/type</b>	
8 B.A.	100 50p
6 B.A.	100 50p
4 B.A.	100 50p
2 B.A.	100 50p
<b>METAL SPEAKER GRILLES</b>	
7in. x 3in.	6 50p
<b>EARPIECES, MAGNETIC</b>	
No Plug	6 50p
2.5mm Plug	4 50p
3.5mm Plug	4 50p
<b>500 MICRO-AMP LEVEL METERS</b>	
VEROBOARD. TRIAL PACK	1 50p
5 BOARDS + CUTTER	50p

<b>TRANSISTORS</b>	
P.N.P. Untested but mainly O.K.	50 50p
N.P.N. Untested but mainly O.K.	50 50p
OCP 71 equivalent	5 50p
Light-sensitive Diodes (These produce up to 1ma from light)	10 50p
OC44 Mullard 1st grade	4 50p
OC45 Mullard	5 50p
2G378 Output, Marked	5 50p
ASY 22, Marked	5 50p
BY 127 Rectifiers	4 50p
IN4007 Rectifiers (1200V peak)	4 50p
STC 3/4 Rectifiers	6 50p
DIODES (0A 81 & 0A 91)	40 50p
<b>WIRE</b>	
Solid Core. Insulated 100yds.	50p
Stranded ditto	50yds. 50p
<b>SOLAR CELLS</b>	
Large Selenium	2 50p
Small	3 50p
(6 cells will power a Micromatic radio)	
<b>CO-AXIAL CABLE</b>	
Semi Air-spaced	15yds. 50p
<b>CRYSTAL TAPE RECORDER MIKES</b>	
CRYSTAL EARPIECES	1 50p
3.5mm Plug	2 50p
<b>TRANSISTORISED Signal Injector Kit</b>	
TRANSISTORISED Signal Tracer Kit	1 50p
<b>TRANSISTORISED CAR REV. COUNTER KIT (Needs 1 ma. meter as indicator)</b>	
	1 50p

**Unrepeatable Offer ! ! ! !**  
**Surplus VEROBOARDS, 3 3/4" x 2 1/2" x .15"**  
**Only 10p each or £1.00 per dozen**

## TANTALUM CAPACITORS. COMPARE THE PRICE—ONLY 10p EACH ! ! ! !

<b>Sub-miniature types</b>		<b>Miniature types</b>			
0.047µF	50 volts	0.022µF	20 volts	5.6 µF	35 volts
0.056µF	50 volts	0.033µF	20 volts	8.2 µF	10 volts
0.07 µF	20 volts	0.047µF	20 volts	8.2 µF	35 volts
0.1 µF	20 volts	0.068µF	35 volts	15 µF	35 volts
0.1 µF	50 volts	0.1 µF	35 volts	18 µF	35 volts
0.18 µF	20 volts	0.12 µF	35 volts	22 µF	15 volts
0.33 µF	35 volts	0.15 µF	35 volts	27 µF	120 volts
0.47 µF	35 volts	0.22 µF	50 volts	56 µF	15 volts
0.68 µF	20 volts	0.47 µF	50 volts	56 µF	20 volts
1.0 µF	15 volts	0.68 µF	35 volts	150 µF	6 volts
2.2 µF	3 volts	1.0 µF	50 volts		
2.7 µF	15 volts	1.0 µF	75 volts	<b>Standard</b>	
2.7 µF	35 volts	1.8 µF	20 volts	6.8 µF	50 volts
3.0 µF	15 volts	1.8 µF	20 volts	7.5 µF	20 volts
10.0 µF	1.5 volts	2.2 µF	20 volts	8.2 µF	150 volts
		2.7 µF	50 volts	12 µF	35 volts
		3 µF	12 volts	12 µF	50 volts
		3.3 µF	15 volts	39 µF	20 volts
		4 µF	20 volts	82 µF	20 volts
		4.7 µF	35 volts	150 µF	15 volts
		5.6 µF	6 volts	270 µF	6 volts

## NEW ! NEW ! NEW ! NEW !

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.  
**Method:** Spray copper laminate board with light-sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.)  
**Spray with developer, rinse and etch in normal manner.**  
 Light sensitive aerosol spray . . . . . **£1**  
 Developer spray . . . . . **50p**

### STOCKTAKING CLEARANCE! IMPOSSIBLE TO REPEAT!

We have huge numbers of components in quantities too small to advertise individually. In order to "clear the decks" we have made up parcels containing a mixture of carbon and wire-wound resistors, electrolytic and paper condensers, controls, transistors, diodes etc., for a tiny fraction of normal price. It is emphasised that these are mixed parcels only—contents cannot be stipulated! Sold only by weight.


Gross weight 2 lb. . . . . **£1** (postage 20p)  
 Gross weight 5 lb. . . . . **£2** (postage 30p)

**G. F. MILWARD, Drayton Bassett, Tamworth, Staffs.** Postage (minimum) per order 15p.



**S.D.C. FESTIVE**

# BONANZA

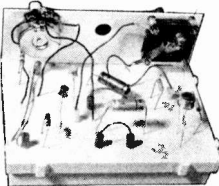

**S-DeC SPECIAL OFFER**

**25p OFF**

- YES!** The ideal present for any electronics enthusiast, so do not miss this great opportunity.
- JUST TAKE THIS COUPON TO YOUR LOCAL STOCKIST WHO WILL SUPPLY ONE S-DeC for only £1.19**
- OR** in case of difficulty send coupon and cash to:—

**S.D.C. ELECTRONICS (SALES) LTD., 34 ARKWRIGHT ROAD ASTMOOR INDUSTRIAL ESTATE, RUNCORN, CHESHIRE WA7 1NU**

Name.....  
 Address.....  
 .....

(4) Offer closes January 31, 1972.

## ELEKON CLEARANCE OFFERS

Pye Transistorised Car Radio Panels includes 2 x Double Tuned IFs, 5 NKT Transistors, etc., etc. Your bargain for 50p, post 10p U.K.  
 Assorted Coil Formers includes Aladdin types, etc., etc. Amazingly cheap. 100 for £1.50, post free U.K.  
 Assorted Paxolin Panels marked A.E. Speaker, P.U., etc., etc. Look at the price! 100 for only £1.50, post free U.K.  
 Assorted Paxolin Voltage Panels. Various mains voltage markings. An absolutely fantastic selection. 100 for £1.50, post free U.K.  
 Assorted Valve Holders. A lot of old types that you never expected to see again. So many for so little. 100 for £1.50, post free U.K.  
 Assorted Fibre Washers. Miniature types rarely ever advertised. Knock-out price, 1,000 for 25p, post free U.K.  
 Assorted Plessey Moulded Track Potentiometers. Don't miss these. 10 for 50p, post 14p U.K.  
 For other bargains see our advert on page 542 October Practical Wireless. Our location near Goudge St. Station, opposite Heals of Tottenham Court Road.

**ELEKON ENTERPRISES**  
**12A TOTTENHAM STREET, LONDON W1P 9PQ**  
**TELEPHONE 01-580 7391**

## IN 15 MINUTES YOU COULD HAVE CAPACITIVE DISCHARGE ELECTRONIC IGNITION FITTED TO YOUR CAR

Capacitive Discharge Ignition is recognised as being the most efficient ignition system and will give you:

- CONTINUAL PEAK PERFORMANCE
- UP TO 20% REDUCED FUEL CONSUMPTION
- EASIER ALL-WEATHER STARTING
- INCREASED ACCELERATION & TOP SPEED
- LONGER SPARK PLUG LIFE
- INCREASED BATTERY LIFE
- CONTACT BURN ELIMINATED
- PURER EXHAUST GAS EMISSION
- RADIO INTERFERENCE SUPPRESSED



For all petrol engines—cars, boats, etc. Guaranteed for 5 yrs.


Complete Installation Kit for 12-volt vehicles £12.95 + 35p P. & P. State earth polarity of vehicle POSITIVE or NEGATIVE earth. Unit Construction Kit also available for the radio electronics constructor £9.95 + 35p P. & P. The construction kit includes instructions and all components for wiring as positive or negative earth, and is complete with the stove enamelled steel case and aluminium base. All components are available separately.

**ELECTRONIC DESIGN ASSOCIATES** 82 BATH STREET, WALSALL WS1 3DE



# new

## Super IC-12

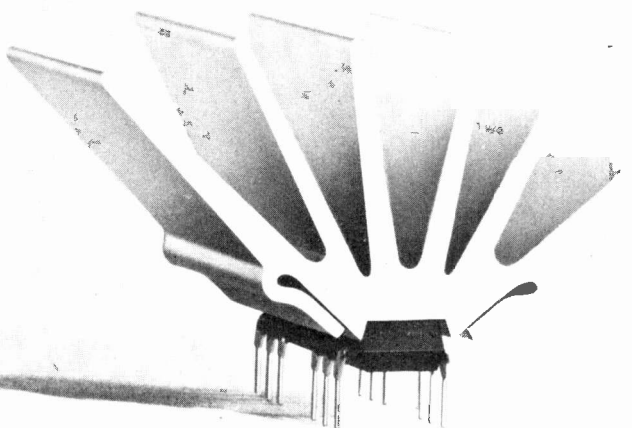

### High fidelity Monolithic Integrated Circuit Amplifier

Two years ago Sinclair Radionics announced the World's first monolithic integrated circuit Hi-Fi amplifier, the IC.10. Now we are delighted to be able to introduce its successor, the Super IC.12. This 22 transistor unit has all the virtues of the original IC.10 plus the following advantages:

1. Higher power.
2. Fewer external components.
3. Lower quiescent consumption.
4. Compatible with Project 60 modules.
5. Specially designed built-in heat sink. No other heat sink needed.
6. Full output into 3, 4, 5 or 8 ohms.
7. Works on any voltage from 6 to 28 volts without adjustment.
8. NEW 22 transistor circuit.

**Output power** 6 watts RMS continuous (12 watts peak).

**Frequency Response** 5 Hz to 100KHz  $\pm$  1 dB.

**Total Harmonic Distortion** Less than 1%. (Typical 0.1%) at all output powers and all frequencies in the audio band.

**Load Impedance** 3 to 15 ohms.

**Power Gain** 90dB (1,000,000,000 times) after feedback.


**Supply Voltage** 6 to 28 volts (Sinclair PZ-5 or PZ-6 power supplies ideal).

**Size** 22 x 45 x 28 mm including pins and heat sink.

**Input Impedance** 250 Kohms nominal.

**Quiescent current** 8mA at 28 volts.

With the addition of only a very few external resistors and capacitors the Super IC.12 makes a complete high fidelity audio amplifier suitable for use with pick-up, F.M. tuner etc. Alternatively, for more elaborate systems, modules in the Project-60 range such as the Stereo 60 and A.F.U. may be added. The comprehensive manual supplied with each unit gives full circuit and wiring diagrams for a large number of applications in addition to high fidelity. These include car radios, oscillators etc. The very low quiescent consumption makes the Super IC.12 ideal for battery operation.

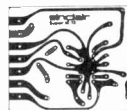

Price, inc. **FREE** printed circuit board for mounting.

**£2.98** Post free



Sinclair Radionics Ltd, London Rd, St. Ives Huntingdonshire PE17 4HJ  
Telephone St Ives (048 06) 4311

**sinclair**

**SINCLAIR GENERAL GUARANTEE**  
Should you not be completely satisfied with your purchase when you receive it from us, return the goods without delay and your money will be refunded in full, including cost of return postage, at once and without question. Full service facilities are available to all Sinclair customers.
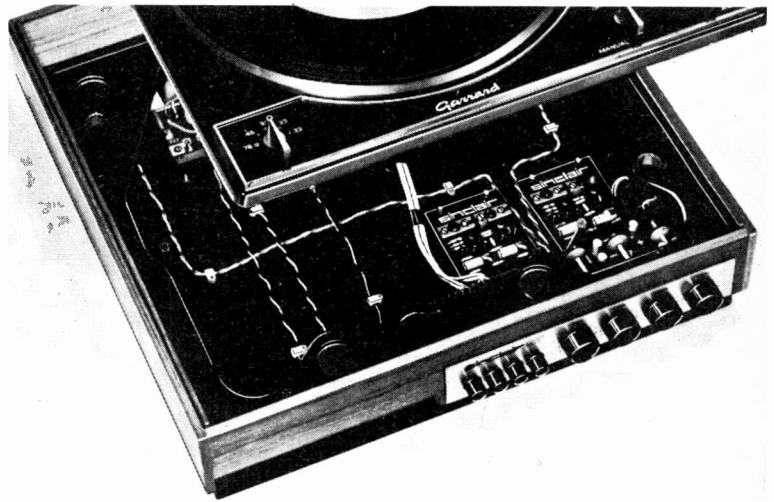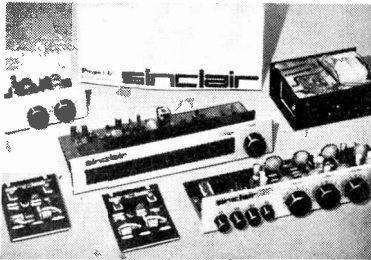
# Sinclair Project 60

The World's leading range of high fidelity modules



## New! Project 605

The easy way  
to buy and  
build  
Project 60



Project 605 is one pack containing: one PZ.5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

All you need for a superb 30 watt high fidelity stereo amplifier.

Sinclair Radionics Limited, London Road,  
St. Ives, Huntingdonshire PE17 4HJ.  
Tel: St. Ives (048 06) 4311

**sinclair**

Project 60 offers more advantage to the constructor and user of high fidelity equipment than any other system in the world.

Performance characteristics are so good they hold their own with any other available system irrespective of price or size.

Project 60 modules are more versatile – using them you can have anything from a simple record player or car radio amplifier to a sophisticated and powerful stereo tuner-amplifier. Either power amplifier can be used in a wide variety of applications as well as high fidelity. The Stereo 60 pre-amplifier control unit may also be used with any other power amplifier system, as can the AFU filter unit. The stereo FM tuner operates on the unique phase lock loop principle to provide the best ever standards of sensitivity and audio quality. Project 60 modules are very easily connected together by following the 48 page manual supplied free with all Project 60 equipment. The modules are great space savers too and are sold individually boxed in distinctive white and black cartons. With all these wonderful advantages, there remains the most attractive of all – price. When you choose Project 60 you know you are going to get the best high fidelity in the world, yet thanks to Sinclair's vast manufacturing resources (the largest in Europe) prices are fantastically low and everything you buy is covered by the famous Sinclair guarantee of reliability and satisfaction.


### Typical Project 60 applications

System	The Units to use	together with	Cost of Units
Simple battery record player	<b>Z.30</b>	Crystal P.U., 12V battery volume control	<b>£4.48</b>
Mains powered record player	<b>Z.30, PZ.5</b>	Crystal or ceramic P.U. volume control etc.	<b>£9.45</b>
20 + 20 W. stereo amplifier for most needs	<b>2 x Z.30s, Stereo 60, PZ.5</b>	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	<b>£23.90</b>
20 + 20 W. stereo amplifier with high performance spkrs.	<b>2 x Z.30s, Stereo 60, PZ.6</b>	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	<b>£26.90</b>
40 + 40 W. R.M.S. de-luxe stereo amplifier	<b>2 x Z.50s, Stereo 60 PZ.8, mains transformer</b>	As above	<b>£34.88</b>
Indoor P.A.	<b>Z.50, PZ.8, mains transformer</b>	Mic., guitar, speakers, etc., controls	<b>£19.43</b>

F.M. Stereo Tuner (**£25**) & A.F.U. Filter Unit (**£5.98**) may be added as required.

# from a simple amplifier to a complete stereo tuner amplifier with Project 60 modules

## Z.30 & Z.50 power amplifiers

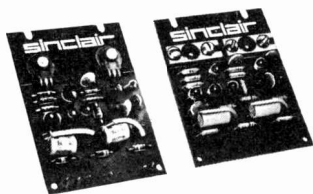

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to achieve unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at full output and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and may be used with other units in the Project 60 range equally well.

**SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).**

### Power Outputs

**Z.30** 15 watts R.M.S. into 8 ohms using 35 volts; 20 watts R.M.S. into 3 ohms using 30 volts.

**Z.50** 40 watts R.M.S. into 3 ohms using 40 volts; 30 watts R.M.S. into 8 ohms using 50 volts.

**Frequency response:** 30 to 300,000Hz  $\pm 1$  dB.

**Distortion:** 0.02% into 8 ohms.

**Signal to noise ratio:** better than 70dB unweighted.

**Input sensitivity:** 250mV into 100 Kohms.

For speakers from 3 to 15 ohms impedance.

**Size:** 14 x 80 x 57 mm.

### Z.30

Built, tested and guaranteed with circuits and instructions manual.

**£4.48**

### Z.50

Built, tested and guaranteed with circuits and instructions manual.

**£5.48**

## Power Supply Units

Designed special for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 where a stabilised supply is essential.


**PZ.5** 30 volts un stabilised **£4.98**

**PZ.6** 35 volts stabilised **£7.98**

**PZ.8** 45 volts stabilised

(less mains transformer) **£7.98**

**PZ.8** mains transformer **£5.98**

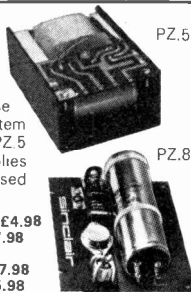

## Project 60 Stereo F.M. Tuner



*First in the world to use the phase lock loop principle*

The phase lock loop principle was used for receiving signals from space craft because of its vastly improved signal to noise ratio. Now, Sinclair have applied the principle to an F.M. tuner with fantastically good results. Other original features include varicap diode tuning, printed circuit coils, an I.C. in the specially designed stereo decoder and squelch circuit for silent tuning between stations. Good reception is possible in difficult areas, and often a few inches of wire are enough for an aerial. In terms of a high fidelity this tuner has a lower level of distortion than any other tuner we know. Stereo broadcasts are received automatically as the tuning control is rotated, a panel indicator lighting up as the stereo signal is tuned in. This tuner can also be used to advantage with any other high fidelity system.

**SPECIFICATIONS—Number of transistors:** 16 plus 20 in I.C. **Tuning range:** 87.5 to 108 MHz. **Capture ratio:** 1.5dB. **Sensitivity:** 2 $\mu$ V for 30dB quieting; 7 $\mu$ V for lock-in over full deviation. **Squelch level:** 20 $\mu$ V. **A.F.C. range:**  $\pm 200$  KHz. **Signal to noise ratio:** > 65dB. **Audio frequency response:** 10 Hz – 15 KHz ( $\pm 1$ dB). **Total harmonic distortion:** 0.15% for 30% modulation. **Stereo decoder operating level:** 2 $\mu$ V. **Cross talk:** 40dB. **Output voltage:** 2 x 150mV R.M.S. **Operating voltage:** 25-30 VDC. **Indicators:** Power on/tuning/stereo.

**Size:** 93 x 40 x 207 mm.

**£25**

Built and tested. Post free.

## Stereo 60 Pre-amp/control unit



Designed for Project 60 range but suitable for use with any high quality power amplifier. Again silicon epitaxial planar transistors are used throughout, achieving a really high signal-to-noise ratio and excellent tracking between channels. Input selection is by means of push buttons and accurate equalisation is provided for all the usual inputs.


**SPECIFICATIONS—Input sensitivities:** Radio – up to 3mV, Mag. p.u. 3mV; correct to R.I.A.A curve  $\pm 1$ dB; 20 to 25,000 Hz. Ceramic p.u. – up to 3mV; Aux – up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE + 15 to –15dB at 10 KHz; BASS + 15 to –15dB at 100Hz.

**Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

**£9.98**

Built, tested and guaranteed.

## A.F.U. High & Low Pass Filter Unit

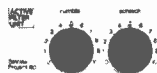

For use between Stereo 60 unit and two Z.30s or Z.50s, and is easily mounted. It is unique in that the cut-off frequencies are continuously variable, and as attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. Two filter stages – rumble (high pass) and scratch (low pass). Supply voltage – 15 to 35V. Current – 3mA. H.F. cut-off (–3dB) variable from 28KHz to 5KHz. L.F. cut-off (–3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V, supply) (0.02% at rated output. **Size:** 66 x 40 x 90 mm.

Built tested and guaranteed. **£5.98**

## The Sinclair Guarantee

If within 3 months of purchasing Project 60 modules directly from us, you are dissatisfied with them, we will refund your money at once. Each module is guaranteed to work perfectly and should any defect arise in normal use we will service it at once and without any cost to you whatsoever provided that it is returned to us within 2 years of the purchase date. There will be a small charge for service thereafter. No charge for postage by surface mail. Air-mail charged at cost.

To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send

Name

Address

I enclose cash/cheque/money order.

P.E. 1271

# Sinclair Q16/Micromatic

## Q16 High fidelity loudspeaker

The Q16 employs the well proven acoustic principles specially developed by Sinclair in which a special driver assembly is meticulously matched to the characteristics of the uniquely designed cabinet. In reviewing this exclusive Sinclair design, technical journals have justly compared the Q16 with much more expensive loudspeakers. Its shape enables the Q16 to be positioned and matched to its environment to much better effect than is the case with conventionally styled enclosures. A solid teak surround with a special all-over cellular foam front is used as much for appearance as its ability to pass all audio frequencies without loss.

This elegantly designed shelf mounting speaker brings genuine high fidelity within reach of every music lover.

## Specifications:

**Construction:** Special sealed seamless sound or pressure chamber with internal baffle.

**Loading:** up to 14 watts RMS.


**Input Impedance:** 8 ohms.

**Frequency response:** From 60 to 16,000 Hz, confirmed by independently plotted B and K curve.

**Driver unit:** Special high compliance unit having massive ceramic magnet of 11,000 gauss, aluminium speech coil and special cone suspension for excellent transient response.

**Size and styling:** 9 $\frac{3}{4}$  in. square on face x 4 $\frac{3}{4}$  in. deep with neat pedestal base. Black all over cellular foam front with natural solid teak surround.

**Price £8.98.**

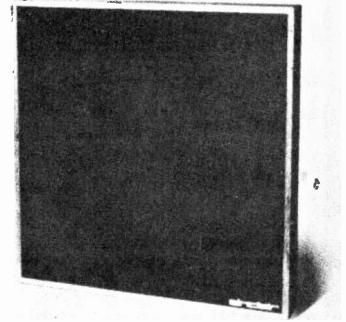

## Britain's smallest radio

Considerably smaller than an ordinary box of matches, this is a multi-stage AM receiver brilliantly designed to provide remarkable standards of selectivity, power and quality for its size. Powerful AGC counteracts fading from distant stations; bandspread at higher frequencies makes reception of Radio 1 easy. The plug-in magnetic earpiece provided, matches the Micromatic's output to give wonderful standards of reproduction. Everything including the special ferrite rod aerial and batteries is contained within the minute attractively designed case. Whether you build a Micromatic kit or buy this amazing receiver ready built and tested, you will find it as easy to take with you as your wrist watch, and dependable under the severest listening conditions.

## Specifications:

**Size:** 36 x 33 x 13 mm (1.8 x 1.3 x 0.5 in.)

**Weight:** including batteries, 28.4 gm (1 oz.)

**Case:** Black plastic with anodised aluminium front panel and spun aluminium dial.

**Tuning:** medium wave band with bandspread at higher frequencies (550 to 1,600 KHz).

**Earpiece:** Magnetic type.

**On/off switching:** By inserting and withdrawing earpiece plug.

Kit in pack with earpiece, case, instructions and solder **£2.48.**

Ready built, tested and guaranteed, with earpiece **£2.98.**

Two Mallory Mercury batteries type RM675 required from radio shops, chemists, etc.



To: SINCLAIR RADIONICS LTD LONDON ROAD ST. IVES HUNTINGDONSHIRE PE17 4HJ

Please send \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

for which I enclose cash/cheque/money order

P.E. 1271

Sinclair Radionics Ltd., London Rd, St. Ives  
Huntingdonshire PE17 4HJ.

Telephone St. Ives (048 06) 4311

**sinclair**

**HENRY'S** FOR **LOW COST** **FIRST GRADE** BRAND **NEW** **BRANDED** GERMANIUM and SILICON TRANSISTORS, DIODES, RECTIFIERS, TRIACS, FETS, ZENERS, BRIDGES and INTEGRATED CIRCUITS  
 BY **ATES · EMIHUS · FAIRCHILD · FERRANTI · I.T.T. · MULLARD · NEWMARKET · PHILIPS · R.C.A. · TEXAS**

# TRANSISTORS

A SELECTION FROM OUR LIST

AA730 10p	BD115 75p	OC16 80p	2N1303 18p
AA742 15p	BD123 85p	OC20 85p	2N1304 22p
AAZ13 10p	BD124 80p	OC22 50p	2N1305 22p
AAZ15 10p	BD131 75p	OC35 60p	2N1306 25p
AAZ17 10p	BD132 75p	OC24 60p	2N1307 25p
AC107 85p	BDY11 80p	OC25 60p	2N1308 25p
AC126 20p		OC26 25p	2N1308 25p
AC127 25p	BDY17 80p	OC28 60p	2N1309 25p
AC127Z 50p		OC29 60p	2N1613 20p
AC128 20p	BDY38 65p	OC35 60p	2N2147 75p
AC176 20p	BDY60 80p	OC36 60p	2N2180 60p
AC187 25p		OC42 40p	2N2217 25p
AC188 25p		OC43 60p	2N2218 20p
AC17 30p	BF115 25p	OC44 15p	2N2218A
AC18 30p	BF164 80p	OC45 15p	
AC19 25p	BF168 15p	OC70 15p	2N2219 20p
AC20 25p	BF169 85p	OC71 15p	2N2219A
AC21 20p	BF180 85p	OC72 20p	
AC22 20p	BF181 85p	OC73 25p	
AC23 20p	BF195 15p	OC76 25p	2N2220 25p
AC24 20p	BF196 15p	OC77 40p	2N2221 20p
AC25 20p	BF197 15p	OC81 20p	
AC26 20p	BF198 15p	OC82 20p	2N2222 20p
AD140 50p	BFX29 25p	OC81Z 40p	2N2222A
AD149 50p	BFX30 25p	OC83 25p	
AD161 35p	BFX31 25p	OC84 25p	2N2369 15p
AD162 35p	BFX32 25p	OC139 25p	2N2369A
AD163 35p	BFX33 25p	OC140 40p	
AD164 35p	BFX34 25p	OC141 60p	2N2646 40p
AD165 35p	BFX35 25p	OC170 25p	2N2904 20p
AD166 35p	BFX36 25p	OC171 30p	2N2904A
AD167 35p	BFX37 25p	OC200 40p	
AD168 35p	BFX38 25p	OC201 75p	2N2905 25p
AD169 35p	BFX39 25p	OC202 80p	2N2906 25p
AD170 35p	BFX40 25p	OC206 65p	
AD171 35p	BFY90 65p	OC271 97p	2N2906 20p
AD172 35p	BFY91 65p	ORP12 50p	2N2906A
AD173 35p	BFY92 65p	ORP40 40p	
AD174 35p	BFY93 65p	RT140 15p	2N2907 25p
AD175 35p	BFY94 65p	RT141 20p	2N2907A
AD176 35p	BFY95 65p	RT142 20p	
AD177 35p	BFY96 65p	RT143 20p	
AD178 35p	BFY97 65p	RT144 20p	
AD351 35p	BFY270 65p	RT317 20p	
AD352 35p			

# Practical Electronics Classified Advertisements

RATES: 7½p per word (minimum 12 words). Box No. 7½p extra. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

## MISCELLANEOUS

### NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get all the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

GET YOURS! SEND £5.20 NOW

TO: 'BOFFIN PROJECTS'  
DEPT. KE2010  
4 CUNLIFFE ROAD  
STONELEIGH, EWELL, SURREY

**HARDWARE FOR CONSTRUCTORS.** Screws, nuts, brackets, spacers, etc. S.A.E. list. R. A. MARSH, 29 Shelbourne Road, Stratford-on-Avon, Warwicks.

**CLEARING LABORATORY**, scopes, V.T.V.M's, V.O.M's, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

**RECORD T.V. SOUND** using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included, 70p + 10p P. & P. CROWBOROUGH ELECTRONICS (P.E.), Eridge Road, Crowborough, Sussex.

**FASCIA PANELS**, hi-fi equipment, etc., etched aluminium to individual specifications, S.A.E. details. R. MARSH, 29 Shelbourne Road, Stratford on Avon, Warwicks.

### JOHN SAYS . . .

**RING MODULATOR** by Dewtron is professional, transformerless, 5-transistor, has adjustable F1/F2 rejection. Module £7. Unit £8-90. WAA-WAA Pedal kit of all parts, including all mechanics and instructions ONLY £3-95. **AUTO RHYTHM** from Dewtron modules. Simple unit for waltz, fox-trot, etc. Costs under £20 in modules. **SYNTHESISER MODULES** and other miracles! Send 15p for illustrated list. **D.E.W. LTD.**, 254 Ringwood Road, Ferndown, Dorset

**HAS SOMEONE CALLED WHILE YOU WERE OUT?** Make door message recorder unit, for visitors. Standard kits, suitable for battery recorders such as "Hit Parade", etc. Engraved plastic block (drilled, grey). Crystal mike. Cable. Push switch. 2½ and 3mm plugs. Instructions. Screws. £2-52. PYLE, 7 The Lookout, CP, Stoborough, Wareham.

**PSYCHEDELIC LIGHTS.** Ideal discos, clubs, groups, etc. No connections to amplifier, only one lead to mains required. Uses four separate randomly programming channels, each driving a coloured 150 watt reflector bulb and a 40 watt standard coloured bulb. Unit contained in open box 39in long, 9in high and 6½in wide. Finished in black leather-cloth with carrying handle and mains socket. Money back guarantee if returned in perfect condition within 14 days of date of purchase. Price £17 each + £1 (Securicor delivery). Send 15p for colour photo of unit in action. Orders to: "ORCHARD MEADOW", Uffington Road, Stamford, Lincs.

## MISCELLANEOUS (continued)

### ★ ELECTRONIC MUSIC ★

I-C Ring Modulator • Electronic Phasing Oscillators • Sub-Octave Generator Fuzz, Waa-Waaa • White Sound Effects Printed-Circuit assemblies supplied with constructional guide to making complete units. Mail Order only. Catalogue 10p from:

**TAYLOR ELECTRONIC MUSIC DEVICES**  
TEGID HOUSE . BALA . MERIONETH

### TOP TRANSISTORS

Brand New and Individually Tested Transistors supplied unmarked, but packed separately for identification and guaranteed to be within their correct specification or money refunded. All at 9p. each or Any 25 transistors for only £1-90

ACY22	BFY51	OC72	2N3702
BC108	BFY52	OC202	2N3703
BC109	BSY27	ZTX300	2N3705
BC168	OC45	2N706	2N3706
BC169	OC71	2N2926	2N3708

Money back guarantee. P. & P. 10p.

J. M. KING (R)

17 Buckridge, Portpool Lane, London, E.C.1

**DO-IT-YOURSELF . . .** we stock a large range of audio and electronic components at very competitive prices, e.g.: Chassis speakers, cross-over networks, hi-fi speaker kits (Wharfedale and Peerless), BAF sound absorbent, speaker grille fabrics, inductors, resistors, electrolytics (reversible and polarised), transistors, etc. Send for FREE list. (2 × 3p stamps for fabric samples). Mail order ONLY. No callers please.

**AUDIOSCAN** Dept. P.E.12  
4, PRINCES SQUARE,  
HARROGATE, YORKS.

**CIRCUIT BOARD ETCHING KITS**, full instructions, £1-25, c.w.o. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

**HOLIDAY FOR BOYS.** 14/16 years, Summer 1972. Tuition and practical work in electronics (and tape recording), engineering, (Karting), photography. 11 days in Norfolk—£16. Write for free brochure. INTER-SCHOOL CHRISTIAN FELLOWSHIP, c/o 1 Hubbard Road, London, SE27 9PJ.

### LIGHTWEIGHT TREASURE-PROBE

Look for BURIED COINS, silver, gold and metal relics PROFESSIONALLY with the BOFFIN solid-state TREASURE-PROBE. An extremely EASY-TO-BUILD kit that REALLY DOES WORK! SIMPLE-TO-FOLLOW INSTRUCTIONS. It comes to your doorstep with maximum copper PRINTED-CIRCUIT BOARD plus ALL ELECTRONIC COMPONENTS including search-coil and ear-phone. Think of the fun you'll have BEACH-COMBING with the sensitive TREASURE-PROBE, and the expectancy of hearing its LOUD 'BEEP' tell you "YOU'RE ON TO SOMETHING".

GET YOUR TREASURE-PROBE!

SEND £6-95 NOW!

### BOFFIN PROJECTS

4 CUNLIFFE ROAD, STONELEIGH  
EWELL, SURREY  
Designed by GERRY BROWN and JOHN SALMON and presented on TV

## MISCELLANEOUS (continued)

### PSYCHEDELIC LUMINOPHONICS

Or is this just another way of referring to FANTASY? Either way, our Projects 24 and 1014 probably come within this category—THINK OF THE FUN YOU WOULD HAVE WITH SOMETHING LIKE THIS AT A PARTY! There are MANY OTHER UNUSUAL PROJECTS TOO—how about an ELECTRONIC STETHOSCOPE for LISTENING THROUGH WALLS, etc., or a TRANSMITTER/RECEIVER that doesn't use RF, SO LICENCE WORRIES ARE OVER! Then there's another project for a "LEARNING" MACHINE—imagine one of these in YOUR BACKROOM; YOUR FRIENDS WOULD BE AMAZED! If REALLY UNUSUAL projects interest you, then WE'VE GOT WHAT YOU WANT. In a few days from now YOU COULD BE IN THE "SCIENCE-FICTION" WORLD OF "BOFFIN"!

DON'T PUT IT OFF! SEND 15p for your list—NOW

### BOFFIN PROJECTS

4 CUNLIFFE RD., STONELEIGH, EWELL, SURREY  
Designed by GERRY BROWN and JOHN SALMON and presented on TV

### SYNTHESISER MODULES

Send S.A.E. for details of voltage-controlled modules for synthesiser construction to:

### D.E.W. Ltd.

254 Ringwood Road, Ferndown, Dorset

### 12 VOLT FLUORESCENT LIGHTS



Beat Power Cuts, 12 ins 8 watt Tube, ideal for Caravan, Tent, Emergency Lighting, etc. Fully Transistorised, Low Battery Drain. With ON/OFF Switch and 12V Socket to run other Lights or 12V Equipment.

Unbeatable at **£3-30**  
or in kit form **£2-90** post paid

**SALOP ELECTRONICS** Callers welcome  
23 Wyle Cop Shrewsbury, Shropshire S.A.E. for lists

### PROFESSIONAL CONTROL PANELS

with **FASCIA KIT**

MAKE YOUR OWN PANELS IN PERMANENT, ANODISED, SELF-ADHESIVE ALUMINIUM. NO SPECIAL EQUIPMENT NEEDED. EASY TO FOLLOW INSTRUCTIONS. CHOICE OF SILVER ON BLACK, RED, BLUE, GREEN.

TRIAL KIT £1-28 Carr. Paid  
No. 1 KIT £1-88 Carr. Paid  
No. 2 KIT £2-39 Carr. Paid

M.P.E. Ltd., BRIDGE ST., CLAY CROSS, DERBYS.

**BUILD IT IN A DEWBOX** quality cabinet 2in x 2½in x any length. DEW LTD., Ringwood Road, Ferndown, Dorset. S.A.E. for leaflet. Write now—right now.

**AARVAK ELECTRONICS.** 3-channel sound-light converters, £17. Strobes, £16. Rainbow Strobes, £96. 74 Bedford Avenue, Barnet, Herts. 01-449 1268.

### LADDERS

**LADDERS.** 20ft, £7. Order C.O.D. Phone 02-993 5222. HOME SALES, Baldwin Road, Stourport, Wores. Callers welcome.

## FOR SALE

**SEEN MY CAT?** 5,000 Items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

**CATALOGUE NO. 18**, Electronic and Mechanical Components, new and manufacturers' surplus. Credit vouchers value 50p. Price 23p, including post. ARTHUR SALLIS RADIO CONTROL LTD., 28 Gardner Street, Brighton, Sussex.

**PERFECT SPEAKERS EX TV**  
P.M. 3 OHM (Minimum order 2)  
5" round or 8" x 2 1/2" 12ip each, add 7ip per speaker P. & Pkg.  
100 SPEAKERS for £15 delivered  
200 SPEAKERS for £25 delivered  
**UHF TUNERS EX TV (Complete with Valves)**  
£2.50 each + 50p p. & pkg.  
or 10 for £23 post free  
**TRADE DISPOSALS (Dept. PE)**  
Thornbury Roundabout, Leeds Road, Bradford  
Telephone 665670

## MORSE MADE !!

**FACT NOT FICTION.** If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected).

Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

For details and course C.O.D. ring S.T.D. 01-660 2898 or send 4p stamp for explanatory booklet to:

**QSHBC (Box 19), 45 GREEN LANE, PURLEY, SURREY**

**PRACTICAL ELECTRONICS Journals.** November 1964 to October 1971 in Hardcover Binders with indexes for 1964-1970 + all enclosures. £12. Haverhill 3674.

## TEST EQUIPMENT

**MULTI-RANGE FREQUENCY METER,** 0-1MHz in 5 ranges. Solid state, large scale meter readout, 230V a.c. Brand new and fully guaranteed. £26. P. & P. 374p, c.w.o. CLEARWAY ELECTRONICS LTD., Church Hill House, Eythorne, Dover, Kent.

## EDUCATIONAL

**GET INTO ELECTRONICS**—big opportunities for trained men. Learn the practical way with low-cost Postal Training, complete with equipment. R.T.E.B., City & Guilds, Radio, TV, Telecoms, etc. For free informative Guide, write CHAMBERS COLLEGE (Dept. 856K), Aldermaston Court, Reading, RG7 4PF.

**ENGINEERS**—get a technical certificate. Exams and Certificate Postal Courses in all branches of Engineering, Electronics, Radio and TV, Computers, Draughts., Building, etc. Write for helpful Free Book—BIET (Dept. H.4), Aldermaston Court, Reading, RG7 4PF.

**BRUNEL TECHNICAL COLLEGE, BRISTOL**  
Department of Marine & Aero-Electronics

Applications invited for following posts. Duties to commence as soon as possible.

### TECHNICIAN GRADE 3 (two vacancies)

Candidates should be over 21 years of age and hold Intermediate City & Guilds in Electronics or Radio Communications, or other appropriate qualifications. Duties include servicing and maintenance of electronic and electrical equipment as used in Merchant Ships and Civil Aircraft.

Salary in range £1,194-£1,395, according to age, experience and qualifications. Further particulars and application forms (returnable by 14 days after the appearance of this advertisement) from Registrar (S), Brunel Technical College, Ashley Down, Bristol BS7 9BU. Please quote post ref. No. 71/58.

## SITUATIONS VACANT

**EAGLE INTERNATIONAL** require Audio Engineers. Excellent prospects. Must be fully conversant with Stereo Amplifiers, Tuners, Multiplex, etc. Contact MR. MORROW 01-903 0144.

## SERVICE SHEETS

**SERVICE SHEETS (1925-1971)** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. HAMILTON RADIO, 54 London Road, Bexhill, Sussex. Telephone, Bexhill 7097.

## COLOUR T.V. TROUBLESHOOTER

there's a good job for you at Baird with pay to match!

If you have experience of Colour T.V. and would like to join a highly efficient production team earning top wages we've a place for you at Baird. A progressive Company, we offer excellent working conditions plus many other benefits including:

- 21 days' Holiday
- Generous Discounts in our Staff Shop
- Canteen and Active Social Facilities

ALSO EXCELLENT OPPORTUNITY FOR EXPERIENCED MONOCHROME ENGINEERS TO LEARN COLOUR T.V. TRAINING GIVEN BY THE COMPANY.

INTERESTED? Then drop a line giving brief details of your qualifications and experience to:

MR. G. BRIER (PERSONNEL MANAGER) BRITISH RADIO CORPORATION (BRADFORD) LTD., BAIRD TELEVISION, BECKSIDE LANE, BRADFORD BD7 2EQ TELEPHONE: BRADFORD 7555



# BAIRD

BRITISH RADIO CORPORATION (BRADFORD) LTD.



Established 1891

## TECHNICAL TRAINING IN RADIO, TELEVISION AND ELECTRONIC ENGINEERING

First-class opportunities in Radio and Electronics await the ICS trained man. Let ICS train YOU for a well-paid post in this expanding field.

ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma courses in Radio/TV Engineering and Servicing, Colour TV Servicing, also Electronics, Computers, etc.

Expert coaching for:

- C. & G. TELECOMMUNICATION TECHNICIANS' CERTIFICATES.
- RADIO AMATEURS' EXAMINATION.
- RADIO OPERATOR CERTIFICATES.

Examination Students coached until successful.

### NEW SELF-BUILD RADIO AND ELECTRONIC COURSES

Build your own 5-valve receiver, transistor portable, signal generator and multi-meter. All under expert guidance.

POST THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

MEMBER OF THE ABCC

ACCREDITED BY THE CACC

**INTERNATIONAL  
CORRESPONDENCE  
SCHOOLS**

**A WHOLE WORLD  
OF KNOWLEDGE  
AWAITS YOU!**

**International Correspondence Schools**  
(Dept. 152), Intertext House, Stewarts Road,  
London SW8 4UJ

NAME .....

Block Capitals Please

ADDRESS .....

AGE ..... OCCUPATION ..... 12/71

## Service Sheets and Manuals

BOOKS, TELEVISIONS, TAPE RECORDERS, RECORD PLAYERS, ETC. FROM 1933 UP-TO-DATE  
MAY - 1971 SERVICE SHEET INDEX LIST 20p. - S.A.E. WITH ENQUIRIES PLEASE

### NEW BOOKS & PUBLICATIONS

	Price + Post
ATED CIRCUIT SYSTEMS by D.J. Walter. 234 pages	£3.50 25p
NTS OF TRANSISTOR PULSE CIRCUITS by T.D. Towers. 168 pages	£1.75 15p
TRONIC COUNTING CIRCUITS by Mullard Ltd. 224 pages	£1.40 15p
ER ENGINEERING USING THYRISTORS Vol.1 by Mullard Ltd. 228 pages	£1.50 15p
ANSISTOR AUDIO AND RADIO CIRCUITS by Mullard Ltd. 205 pages	£1.50 15p
PHOTO-ELECTRONIC DEVICES by J.B. Dance. 165 pages	£2.10 15p
SOLID-STATE DEVICES AND APPLICATIONS by R. Lewis. 264 pages	£3.00 15p
SEMICONDUCTORS: BASIC THEORY AND DEVICES by I. Kampel. 272 pages	£2.50 15p
FOUNDATIONS OF WIRELESS AND ELECTRONICS by M.G. Scroggie. 552 pages	£3.00 15p
PRACTICAL INTEGRATED CIRCUITS by A.J. McEvoy & L. McNamara. 144 pages	£0.90 10p
HIGH QUALITY SOUND PRODUCTION & REPRODUCTION by H. Burrell Hodden. 274 pages	£2.10 15p

Send S.A.E. for 'FREE' List of Practical and Technical Books on Radio & Television now available to -

**BELL'S TELEVISION SERVICES**  
Albert Place, Harrogate, Yorkshire. Telephone 0423-86844

**RADIO, TELEVISION AND TAPE RECORDERS.** 50 mixed odd sheets 50p. Also large stock of obsolete and current valves. JOHN GILBERT TELEVISION, 1b Shepherds Bush Road, London, W.8 (01-743 8441). S.A.E. enquiries.

**SERVICE SHEETS.** Radio, TV, etc., 8,000 models. List 10p. S.A.E. enquiries. TELRAY, 11 Mauldland Bank, Preston.

**SERVICE SHEETS** with Free Fault Finding Chart 35p, plus stamped addressed envelope. LESMAR, 15 Conholt Road, Andover, Hants.

### WANTED

**CASH PAID** for New Valves. Payment by return. WILLOW VALE ELECTRONICS, 4 The Broadway, Hanwell, London, W.7. 01-567 5400/2971.

**TOP PRICES PAID**  
for new valves and components  
Popular T.V. and Radio types  
**KENSINGTON SUPPLIES**  
(B) 367 Kensington Street  
Bradford 8, Yorks.

**WE PAY THE HIGHEST PRICES** for new valves. Cash sent by return. A.D.A. MANUFACTURING CO., 116 Alfreton Road, Nottingham.

**WANTED.** Practical Electronics, November 1964 to September 1966. Offers to 5 Leyland Road, Rainford, St. Helens.

**HIGHEST POSSIBLE CASH** prices for Akai, B. & O., Brenell, Ferrograph, Revox, Sanyo, Sony, Tandberg, Uher, Vortexion, etc. 9.30-5.00. 01-242 7401.

### RECEIVERS AND COMPONENTS

## PE GEMINI STEREO AMPLIFIER

(Dual purpose, 30W per channel)

All the components to build this high quality amplifier, as featured in "Practical Electronics," Nov. 1970 - Feb. 1971, are now available from one source.

ALL PARTS CAN BE PURCHASED SEPARATELY.

Please send foolscap size S.A.E. for free complete lists. Return post service.

MAIL ORDER ONLY

## ELECTROSPARES

21 BROOKSIDE BAR  
CHESTERFIELD, DERBYSHIRE  
QUALITY • VALUE • SERVICE

## CONTROL YOURSELF!

**WE DON'T SHOW YOU NIPPY LADIES**  
but we will show you Nippiboards  
Our booklet reveals the secrets of a  
**NEW PRINTED WIRING BOARD**  
Send 2½p stamp to find how you can get the  
best out of multi-purpose  
**NIPPIBOARD**

Range 'A' single pattern 15p  
Double pattern 2A or 2AS 28p  
Quad pattern 4A or 4AS 44p  
Also 3A, 5A, 6AS, 8AS, 10AS at low prices  
up to 90p for ten patterns. Please add 5p  
for postage and packing. Cash with order  
**TRADE INQUIRIES INVITED**  
**ALSO SL403D** i.c. amplifier £1.99 plus 9p  
postage and packing.

DEPARTMENT NB/E12, NIP ELECTRONICS  
P.O. BOX 11, ST. ALBANS, HERTFORDSHIRE

### "P.E. DIGITAL CLOCK I.C.'s"

SN7441AN/SN9315 50p; SN7476 30p;  
SN7475 30p; SN7495 35p; SN7403 20p;  
SN7410 20p; SN7400 20p.

Numerical indicator tubes. GN-7A side  
view with decimal point 70p. OA47 5p.

Other components, hardware, transistors,  
metal oxide resistors, etc., in stock. S.A.E.  
for lists.

### "AQUA-GEM" ELECTRONICS

8 Pound Lane, BOWERS GIFFORD,  
BASILDON, ESSEX  
P. & P. 7p. MAIL ORDER ONLY

**BRAND NEW COMPONENTS.** Carbon Film  
Resistors, ½ watt 5% Iskra E24 series; ¼ watt  
5% Mullard C25 series; E12 series, all at  
1½p each. Electrolytic Capacitors 10/16,  
20/16, 40/16, 80/16, 125/16, at 6p each.  
Copper Laminated P.C. Board 1/8 F/glass,  
single sided 1½p per sq. in.; double sided 2p  
per sq. in. P.P. plus 10%, minimum 5p.  
FREEMANTLE, 18 Pennine Rd., Southamp-  
ton.

**RAZOR-SHARP I.F. SELECTIVITY** with  
Brush Clewite ceramic i.f. resonators. Set of  
four TF04-442, 455kHz, with circuits, £1-50,  
U.K. post 5p. S.A.E. list. AMATRONIX  
LTD., 396 Selsdon Rd., S. Croydon, Surrey,  
CR2 0DE.

## TRAMPUS ELECTRONIX

**NEW. TOP GRADE. GUARANTEED.**  
**NUMERICAL INDICATOR** Computer  
type 9mm, 7 bar display 0-9DP. 5V 8mA bar  
£1.95. Plugs into D.I.L. 16-pin socket 35p.  
TL7447 driver from BCD to suit £1.45.  
**NUMERICAL INDICATOR**, side reading,  
12mm neon 0-9 190V flying leads £1.25.  
**LIGHT EMITTING DIODE INDICATOR**,  
visible red 2V 10mA brighter 40mA 67p.

**TRANSISTORS**, FT2N3819 35p. Unijunction  
EQV2N2646 45p. TL163 npn sil. **PHOTO**  
**TRANSISTOR** 67p. OCP71/M 60p. BC107,  
8,9 11p. ORP12 90p. **SILICON RECTIFIERS** 1A  
190V 8p. 400V 10p.

**INTEGRATED CIRCUITS** 7400 TTL.  
7400, 1, 2, 3, 4, 10, 20, 30, 40, 50, 51, 53, 54, 21p.  
7413, 70, 72, 45p. 73, 74, 75, 67p. 7441, 141,  
90, 92, 93, 95p. 7481, 82, 95 £1.29.  
709 IC HIGH GAIN OP AMP TO5 8 LEAD 50p.  
Mail Order only. Data Sheets 7p each.  
C.W.O. P.P. 8p. Overseas 40p min.

P.O. BOX 29, BRACKNELL, BERKS.

## PRINTED CIRCUIT BOARDS for P.E. PROJECTS

All boards drilled and roller tinned complete  
with layout drawing.

### EXAMPLES

Marine Tachometer (May 1970) 25p ea. Musical  
Stave (May 1970) 40p ea.  
Waa-Waa pedal Vol. 4 No. 7 14p ea. Audio Sig.  
Gen. (Sine and Square on one board) Vol. 5 No.  
10 42p ea.

S.A.E. for List. Now available from: HENRY'S  
RADIO LTD., Edgware Road, London, W.2  
P.H. ELECTRONICS, Industrial Estate,  
Sandwich, Kent. Tel. 2517

## LOW PRICED

### SEMICONDUCTORS

All our stocks are brand new, no rejects. No  
seconds. All guaranteed. P. & P. 5p.

TRANSISTORS			
AC187K	} 45p	ZN3065	55p
AC188K		AD142	50p
Matched pair		BC107	8p
AC141K	20p	BC108	8p
AC142K	20p	BC109	8p
AL102	60p	BC142	8p
AU103	80p	BC143	8p
AD282	} 70p	ZN3866	£1.55
BD162		BFY61	10p
Matched pair		BFY62	10p

**DIODES & RECTIFIERS**  
400mW Zener diode 6.8V, 7.5V, 8.2V, IN4001 7p  
9-1V 15p IN4004 8p  
IN4148 6p

Send for free price list, includes hundreds of  
transistors, cap's, T.T.L.'s, etc. Free equivalent  
charts.

**C. HADLEY (P.E.)**  
24 WOODHILL, HARLOW, ESSEX

## EX COMPUTER PRINTED CIRCUIT PANELS

2in x 4in packed with semi-conductors and top  
quality resistors, capacitors, diodes, etc. Our  
price 10 boards 50p. P. & P. 7p. With a guaran-  
teed minimum of 35 transistors. Data on  
transistors included.

**SPECIAL BARGAIN PACK.** 25 boards for £1,  
P. & P. 18p. With a guaranteed minimum of 85  
transistors. Data on transistors included.

**PANELS** with 2 power transistors similar to  
OC28 on each board—components 2 boards (4 x  
OC28) 50p, P. & P. 6p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14  
Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875.  
All long leaded on panels 13in x 4in. 4 for £1,  
P. & P. 25p.

**709C OPERATIONAL AMPLIFIER TO5**  
8 lead I.C. 1 off 50p. 50 off 35p.  
100 off 20p.

**250 MIXED RESISTORS** 62p  
½ & ¼ watt.

**150 MIXED HI STABS** 62p  
1, ½ & ¼ watt 5% & better.

### QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights,  
projectors, etc. 50p each. P. & P. 5p.

### QPO EXTENSION TELEPHONES

with dial but without bell. 95p each. P. & P. 30p.  
£1.75 for 2. P. & P. 50p.

### BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to  
50V. 2-5kΩ coil. 8 for 50p. P. & P. 6p.

**KEYTRONICS** mail order only

44 EARLS COURT ROAD  
LONDON, W.8 01-478 8499

## HIGH QUALITY SILICON TRANSISTORS

Surplus to our manufacturing requirements.  
NPN exact to BC107B specification.  
VCEO 45V IC 100 MA PC 300 MW hfe  
240 to 500.

Pack of 6 for 50p. BC178B  
PNP as above but VCEO 25V. BC178B  
Pack of 5 for 50p.

New and guaranteed, mail order only.  
C.W.O. P. & P. 5p per order.

**CROSS ELECTRONICS**  
Red Lodge, North Cove, Beccles,  
Suffolk



## RECEIVERS AND COMPONENTS

(continued)

### CHROMASONIC electronics

supply only brand new guaranteed goods

#### LOW NOISE HI-STABS

4 watt 5% all E24 values 3 for 2p plus p. & p. 6p. for up to 50 resistors + 1p for each additional 50.

#### INTEGRATED CIRCUITS

PA234 85p MFC4000P 52p  $\mu$ A709C 45p  
PA237 1-55 MFC4010P 75p  $\mu$ A710 45p  
PA246 1-60 TAA700 22  $\mu$ A741C 70p

#### TRANSISTORS & DIODES

AC187/88 30p BC147 15p 2N3708/9/10/11 12p  
AD161 63p BC148 12p 2N3055 55p  
AD162 pair BC149 15p 2N2926 O/Y 15p  
BC107 12p 2N3702/3 12p 2N1711 25p  
BC108 11p 2N3704 17p 2N91/90/91 7p  
BC109 12p 2N3705/6/7 15p BZ788 15p

F.M. STEREO I.P. STRIP 23-60 + p. & p. 25p  
F.M. FRONT END 23-00 + p. & p. 25p  
F.M. STEREO DECODER 23-25 + p. & p. 25p

#### 100 $\mu$ F 16V 4p each

Mullard C431 series capacitors:  
500 $\mu$ F 40V 22p 2000 $\mu$ F 25V 42p 4000 $\mu$ F 25V 65p  
1250 $\mu$ F 25V 36p 2500 $\mu$ F 40V 63p 4000 $\mu$ F 40V 77p  
1250 $\mu$ F 40V 42p 2500 $\mu$ F 64V 77p also  
C426 (6p), C437, C280, C333, 8. MICA & polystyrene

CARBON TRACK POTS, Single gang Log or Lin 12p  
Dual gang Log or Lin 40p, Mains Sw. 12p extra.  
SKELETON PRESETS, Vert. or Horiz. 0-1W 5p.  
0-25W 7p, Mains Transformer Sec. 250V 25mA  
& 6-3V 1.2A 1-10.

#### 1972 CATALOGUE 10p post free

P. & P. on all orders other than resistors 6p.  
36 FORTIS GREEN ROAD, LONDON N10 3HN

#### BRAND NEW COMPONENTS BY RETURN.

Electrolytics 15 or 25V 1, 2, 5, 10 mfd—3p, 25, 50—4p, 100—5p. Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02—2p; 0-04, 0-05—2 1/2p; 0-068, 0-1—3p. Mullard miniature carbon film resistors third watt E12 series 1 $\Omega$ —10M $\Omega$ , 8 for 5p, insured postage 8p. The C.R. SUPPLY CO., 127 Chesterfield Rd., Sheffield, S8 0RN.

#### CAPACITORS, -005 $\mu$ F, 500V. Discs, 2p each.

100 for 1-75. p + p 5p. Various other components, enquiries s.a.e. SHEMMING, 9 Branhihall Close, Ipswich.

#### ZTX300, BC108, OC42, 5K PC Pots, 3p each.

ACY20, ASZ21, BSX26, 5p each, post free. S.A.E. Lists other items. D.U.M. 1 (one) Newton St., Ulverston, Lancs.

#### 5k $\Omega$ P.C. POTs, 3p; 100 solder tags, 12 1/2p.

ZTX300, 3p. Lists S.A.E. 1 Newton Street, Ulverston, Lancs.

#### BRAND NEW FULL SPEC. DEVICES BY RETURN — ORDER WITH CONFIDENCE

Microcircuits  
SN76013 (like IC12) 1-50; 709 36p; 741 36p; PA230 90p; PA234 86p; PA237 1-55; SL402A 1-75; SL702C 40p; TTL Gates 15p.  
Transistors  
2N3055 54p; BC107B 9p; BC108C 9p; BC109C 9p; BCY70 14p; BFx86 15p; MEO402 21p; MEO411 20p; MEO412 20p; MEO413 15p; ME1002 11p; ME4101 11p; ME4102 12p; ME6101 15p; ME6102 19p; ME8001 17p; MP8111 35p.  
Amp Rectifiers  
50V 3p; 100V 4p; 200V 5p; 400V 6p.  
3 Amp Rectifiers: 400V 12p.  
Printed Circuit Resist 8p.  
Discounts start at 10 off.

JEF ELECTRONICS (PE12)  
York House, 12 York Drive, Grappenhall, Warrington Mail Order Only  
C.W.O. P. & P. 7p per order. Overseas 65p. Money back if not satisfied. List free on application.

#### DRY REED INSERTS

Overall length 1.85" (Body length 1.1"). Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62p per doz.: 1-75 per 100; 1-27-50 per 1,000; 1-250 per 10,000. All carriage paid.  
G.W.M. RADIO LTD.  
40/42 Portland Road, Worthing, Sussex BN903 34897

COMPUTER PANELS. 5-BC108 Diodes, 15p, post 6p; 4-50p, post 10p. AMERICAN PANELS. Total at least 50 transistors, first grade components, 4-55p, post 10p. Small panels with 3 VHF silicon transistors, diodes, 5p, post 3p each, 6-35p, post paid. MIXED TRANSISTORS ON PANELS (at least 4) 50-65p, post 10p. LIST OF PANELS AVAILABLE, send large S.A.E. for copy.  
ASSORTED I.C. Fall Outs, 5-10p, post 3p. Type and pin connections given. Same on small panels but o.k., 8p each, post 3p. LA2 POT CORES, 20 in all. box plus 20 1% caps, 1-15, post 27p. Singles 18p c.p.

SYNCHRONOUS MOTORS with gear train 200-250V, 30p post free. ORP20 of 20 MEMOS, wire ended, 60p, post 7p. ORP12 on panel ex equip., 35p c.p.  
ELECTROLYTICS, 5,000 M.F.I. 25V, 40p post paid.  
POLYSTYRENE CAPACITORS, 125V, 150, 180, 220, 330, 390, 560, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,600, 6,800, 8,200, 0-01, 0-012, 0-015, 15p dozen, post 10p.  
ASSORTED COMPONENTS, 7lb., 1-15 c.p.  
ASSORTED COMPUTER PANELS, 2lb., 1-25 c.p.

J.W.B. RADIO  
75 HAYFIELD ROAD, SALFORD 6, LANCs.  
MAIL ORDER ONLY

## hot news

Nippiboard Range 'B'  
NEW FIBREGLASS TYPE  
Version of the srp range 'A'

#### NOW AVAILABLE:

Dept. NB/E12. NIP Electronics  
P.O. Box 11, St. Albans, Herts.

#### SPECIALISTS IN RADIO CONTROL


Teleradio are the largest suppliers of kits and designs for home construction of radio remote control systems.

Send S.A.E. for leaflets or 10p for full parts catalogue.

#### Teleradio SPECIAL PRODUCTS

325/7 Lower Fore Street  
Edmonton, London, N.9  
Telephone 01-807 3719

## INTER-LOCKING PLASTIC STORAGE DRAWERS

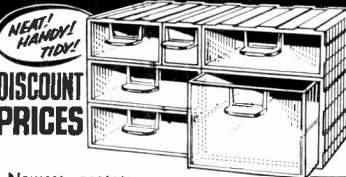

Neatest, neatest system ever devised for storing small parts and components: resistors, capacitors, diodes, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots/removable space dividers. Build up any size cabinet for wall, bench or table top.

#### BUY AT TRADE PRICES!

SINGLE UNITS (1D) (Sins 2 1/2ins x 2 1/2ins), 1-35 DOZEN.  
DOUBLE UNITS (2D) (Sins x 4 1/2ins x 2 1/2ins) 1-25 DOZEN.  
TREBLE (3D) 1-35 for 8.  
DOUBLE TREBLE 2 draws, in one outer case (6D2), 1-35 for 8, EXTRA LARGE SIZE (6D1) 1-35 for 8.

#### PLUS QUANTITY DISCOUNTS!

Orders 15 and over DEDUCT 5% in the 1- Orders 10 and over DEDUCT 7% in the 1- Orders 120 and over DEDUCT 10% in the 1- PACKING/POSTAGE/CARRIAGE: Add 35p to all orders under 15. Orders 15 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES ALL PRICES TAX PAID

IVORYET LIMITED (Dept. PE12) 124 Cricklewood Broadway, London, N.W.2 Tel. 01-450 4844

## VISUAL MORSE MEMOR

Difficulty with memorising Morse? A new, ingenious, pictorial method enables you to remember each letter and number in relation to its own particular coding. Mental jumbling is eliminated and recall positive and confident. Basically simple, the code can be learnt extremely rapidly, even within hours. The 'Modulator' costs only 18p.  
Mellit System  
School Road, Gt. Barton, Suffolk

## BATTERY ELIMINATORS

The ideal way of running your TRANSISTOR RADIO, RECORD PLAYER, TAPE RECORDER, AMPLIFIER, etc., Types available: 6v, 9v, 12v, 18v (single output) 12 each. P. & P. 15p. 9v + 9v; 6v + 6v; or 4 1/2v + 4 1/2v (two separate outputs) 12.50 each. P. & P. 15p. Please state output required. All the above units are completely isolated from mains by double wound transformer ensuring 100% safety.  
R.C.S. PRODUCTS (RADIO) LTD.  
(Dept. P.E.), 31 Oliver Road, London, E.17

## OSMABET LTD.

We make transformers amongst other things

MAINS TRANSFORMERS  
Prim. 200/240V a.c. TX6, 425-0-425V, 500 MA, 6-3V 4A CT, 6-3V 6A, 12-75; TX1, 425-0-425V, 250MA, 6-3V 4A CT, 6-3V 4A CT 0-5-6-3V, 3A, 27-50; TX2, 250-0-250V, 150MA, 6-3V 4A CT, 0-5-6-3V, 3A, 24-05; TX3, 300-0-300V, 120MA, 6-3V 2A CT, 6-3V, 2A, 6-3V, 1A, 24-05; TX8, 250-0-250V, 65MA, 6-3V, 1-5A, 22-10; MT1, 200V, 30MA, 6-3V, 1A, 1-1-20; MT2, 230V, 45MA, 6-3V, 1-5A, 1-1-20; MT3A, 250V, 60MA, 6-3V, 2A, 1-1-85; MT3 Prim. 110/240V, Sec. 250V, 100MA, 6-3V, 2A, 22-25.

AUTO TRANSFORMERS  
30 to 4000 watt ex stock, up to 1000 watt to order.

MULTIVOLT TRANSFORMERS  
Prim. 200/240V a.c. OMT4/1. One tapped sec. 5-20-30-40-60V giving 5-10-15-20-25-30-40-45-55-60, 10-10-10, 20-20-20, 30-0-30V a.c. 1A, 22-25; OMT4/2 ditto, 2A, 23-45; OMT5/1 one tapped sec. 40-50-60-80-90-100-110V a.c. 1A, 23-45. Duo 12V 4A-12V 4A 23-60; Duo 0-10-20-25V 2A-0-10-20-25V 2A 23-60.

LOW VOLTAGE TRANSFORMERS  
Prim. 200/240V a.c. 6-3V, 1-5A, 85p; 3A, 21-13; 6A CT, 1-1-80; 12V, 1-5A, 21-13; 3A CT, 1-1-80; 6A CT, 22-70; 18V, 2-5A CT, 1-1-80; 24V, 1-3A CT, 1-1-80; 3A CT, 22-70; 5A, 23-75; 8A, 22-12A, 23-40; 40V, 3A CT, 23-45.

MIDGET RECTIFIER TRANSFORMERS  
For FW rect., size 1 1/2 x 2 x 1 1/2in. Prim. 200/240V a.c. output, PPT1 9-0-9V, 0-3A, PPT2 12-0-12V, 0-25A, PPT3 20-0-20V, 0-15A, 1-1-20 each; ditto, size 2 x 2 1/2 x 1 1/2in. MTV1 0-9-0V, 1A, 95p; MTV2 12-0-12V, 1A, 10V 3 20-0-20V, 0-75A, 1-1-20 each.

O/P TRANSFORMERS FOR POWER AMPLIFIERS  
(P.P. sec. tapped 3-7-5-15 ohms, A-A 6-6k $\Omega$ , 30W (KT66, etc.), 24-05; 50W, 3k $\Omega$ , A-A, 23-75; 100W, 3k $\Omega$ , A-A, EL34 (KT88, etc.) 21-40 with and to 400W.

LOUDSPEAKERS FOR POWER AMPLIFIERS  
New, famous makes, 15W with tweeter, 24-75; 25W, 25-80; 35W, 27-20; 50W, 10-100; 100W, 22-1-50; E.M.I. 13 1/2 x 8in 10W, 3 or 8 or 15 ohms, 22-25. Ditto with two tweeters and Xover, 24-00; Horn Tweeters 2-16kHz 10W 8 or 16 ohms, 1-1-50. HI-FI, 8 x 3in 8 $\Omega$ , 1-1-85; 10 x 6in 3 $\Omega$ , 21-95.

MANUAL OF POWER AMPLIFIERS  
issued by G.E.C. Five detailed valve circuits 30 to 400 watts. With price list 25p.

LOUDSPEAKERS  
2in 35 $\Omega$ , 2 1/2in 8 or 80 $\Omega$ , 2 1/2in 25 $\Omega$ , 3in 30 $\Omega$ , 60p each; 3in 3 $\Omega$ , 4in 15 $\Omega$ , 5 x 3in 3 or 8 or 15 or 25 $\Omega$ , 80p each; 6 x 4in 3 or 8 or 15 $\Omega$ , 7 x 4in 3 or 8 or 35 $\Omega$ , 8 x 2 1/2in 3 $\Omega$ , 6 1/2in 3 $\Omega$ , 11-08; 8 x 3in 3 or 15 or 25 $\Omega$ , 11-35; 8in 3 $\Omega$ , 1-1-85; 10in 3 or 15 $\Omega$ , 22-25; 10 x 6in 3 or 8 or 15 $\Omega$ , 21-95.

SPEAKER AUTO MATCHING TRANSFORMER 12W 3 to 8 or 15 ohms, up or down, 75p. P. & P. 15p.

100 WATT POWER AMPLIFIER  
4 inputs, variable tone controls, mixing controls, response 25-20kHz, for a.c. 200/250V, new and guaranteed. S.A.E. details. 239.

BULK TAPE ERASERS  
Instant erasure, tape spools and cassettes, demagnetizes tape heads, a.c. 200/250V, 12-40 plus 24p P. & P.

AIRBRAFT BAND COVER  
Covers entire aircraft band, 110-135MHz, fully tunable, works in proximity of any a.m. receiver, with battery, instructions, 24-25 plus 25p P. & P.

NEW TUNER-STEREO AMPLIFIER  
5W per channel, P.U. input, output for tape recorder, 8W, 1/2 wave coverage, complete with all plugs and leads. Stylish chassis, British manufacturer, 18 x 7 x 3 1/2in. Guaranteed 223-50. S.A.E. details.

CONDENSERS  
Paper: 0-01/2kV, 12 1/2p; 0-22/800V a.c. 25p; 0-47/700V, 15p; 40/150V, 25p; 4/500V 25p. Electrolytics: 6,000/15V, 10p; 10,000/15V, 49p; 100 x 50/450V 25p; 350 x 50/325V, 25p; 100 x 400/275V, 25p.

P.E. SCORPIO IGNITION SYSTEM  
Transformer as specified on Mullard Pot Core 23-45; Eddystone Diecast Box as specified 21-85.

Carriage extra on all orders

S.A.E. INQUIRIES-LISTS. MAIL ORDER ONLY  
46 Kenilworth Road, Edgware, Middx. HA5 8YG  
Tel. 01-968 9314

# HOME SOLDERING?

Our miniature irons are used all over the world in that most exacting market—the modern electronics industry, the rapidly developing technology of which has made possible the enormous growth of activities available to the technical hobbyist.

He now also requires equipment to the highest commercial standards. Like our soldering irons, for example.

Look at the ADAMIN Model 15. If there is a smaller iron for mains use, we haven't seen it. It weighs a mere ½ oz (less flex) and is about 7 inches long.

But it has a big performance. Used with interchangeable bits from  $\frac{3}{16}$  in to  $\frac{3}{8}$  in it is suitable for all work, from Hearing Aids to Colour Television.

Use the mains version at home or clip the 12 volt model to the car battery or 12 volt power unit (consumption only 1.25A).

Send for HOBBY PACK 37 consisting of Model 15 iron with four bits,  $\frac{3}{16}$  in,  $\frac{3}{8}$  in,  $\frac{1}{2}$  in,  $\frac{3}{4}$  in and tube of Bit Lubricant. State voltage required—12V or 220/240V.

**PRICE: HOBBY PACK £2.30**  
**P. & P. FREE**

## LIGHT SOLDERING DEVELOPMENTS LTD.

28 Sydenham Road, Croydon CR9 2LL  
Telephone 01-688 8589 and 4559



## BRUNEL TECHNICAL COLLEGE BRISTOL

DEPARTMENT OF MARINE AND  
AERO-ELECTRONICS

### MARINE RADIO OFFICERS

The Department offers the following courses for prospective Radio Officers in the Merchant Navy—2 years' full-time course leading to the Ministry of Posts and Telecommunications General Certificate in Radiocommunications. 1 term full-time course leading to the Department of Trade and Industry Radar Maintenance Certificate. Conversion Course from 1st or 2nd class MPT R/T Licences (Full and Restricted). Marine Electronics Diploma. Advanced Marine Electronics Diploma.

### LICENSED AIRCRAFT RADIO ENGINEERS (Civil Aviation)

A full-time course of two years' duration commences in September of each year. This leads to the award of the Aircraft Maintenance Engineers Category R Licence issued by the Air Registration Board.

All instruction and practice is carried out with modern equipment and test instruments, in well-equipped laboratories and workshops at the College and on the Department's own aircraft at Bristol Airport.

The Department also offers a course for the Board of Trade Civil Aeronautical RT Licence.

For further information apply to — Head of Department of Marine and Aero-Electronics,

**Brunel Technical College, Ashley Down**

**BRISTOL BS7 9BU**

## LIGHT SENSITIVE INTEGRATED CIRCUIT

ARE YOU STILL USING  
PHOTOTRANSISTORS, DIODES AND  
OTHER PHOTOCELLS?

—KEEP UP TO DATE

WE ARE OFFERING THE COMPLETE  
SWITCH—

PHOTODETECTOR +  
AMPLIFIER +  
TRIGGER +

DRIVER—ALL IN A SINGLE 4 mm. DIA.  
CAN

—WILL DRIVE RELAY OR TRIAC FOR  
AUTOMATIC LIGHT SWITCHING  
CONTROL: BURGLAR ALARM BEAM/  
BREAK DETECTOR: AUTOMATIC  
DOOR CONTROL AND MANY OTHER  
APPLICATIONS.

P.O. CHEQUES payable to ELBON and crossed

LITE-IC. ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX



PRICE ONLY 65p each  
+ 5p post and packing, with  
full operating instructions.  
10 for £5 75 (post free).

## BAKER 15in. AUDITORIUM

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home.

Maximum Power	35 watts
Bass Resonance	35 c.p.s.
Flux Density	15,000 gauss
Voice coil impedance	8 or 15 ohms models
Useful response	20-14,000 c.p.s.
Nett weight	15 lbs.

**£19**  
POST  
FREE

GUITAR MODEL "GROUP 50" 50 watt £19  
Latest catalogue 5p with enclosure plans

**Baker Reproducers Ltd**

Bensham Manor Road Passage, Thornton Heath, Surrey. 01-684-1665



# In just 2 minutes, find out how you can qualify for promotion or a better job in Engineering...

That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. Home Study Course gets results fast - makes learning easier and something you look forward to. There are no books to buy and you can pay-as-you-learn.

If you'd like to know how just a few hours a week of your spare time, doing something constructive and enjoyable, could put you out in front, post the coupon today. No obligation.

## WHICH SUBJECT WOULD INTEREST YOU?

**Mechanical**  
A.M.S.E. (Mech.)  
Inst. of Engineers  
Mechanical Eng.  
Maintenance Eng.  
Welding  
General Diesel Eng.  
Sheet Metal Work  
Eng. Inspection  
Eng. Metallurgy  
C. & G. Eng. Crafts  
C. & G. Fabrication

**Draughtsmanship**  
A.M.I.E.D.  
Gen. Draughtsmanship  
Die & Press Tools  
Elec. Draughtsmanship  
Jig & Tool Design  
Design of Elec. Machines  
Technical Drawing  
Building

**Electrical & Electronic**  
A.M.S.E. (Elec.)  
C. & G. Elec. Eng.  
General Elec. Eng.  
Installations & Wiring  
Electrical Maths.  
Electrical Science  
Computer Electronics  
Electronic Eng.

**Radio & Telecomms.**  
C. & G. Telecomms.  
C. & G. Radio Servicing  
Radio Amateurs' Exam.  
Radio Operators' Cert.  
Radio & TV Engineering  
Radio Servicing  
Practical Television  
TV Servicing  
Colour TV  
Practical Radio & Electronics (with kit)

**Auto & Aero**  
A.M.I.M.I.  
MAA/IMI Diploma  
C. & G. Auto Eng.  
General Auto Eng.  
Motor Mechanics  
A.R.B. Certs.  
Gen. Aero Eng.

**Management & Production**  
Computer Programming  
Inst. of Marketing  
A.C.W.A.  
Works Management  
Work Study  
Production Eng.  
Storekeeping  
Estimating  
Personnel Management  
Quality Control  
Electronic Data Processing  
Numerical Control  
Planning Engineering  
Materials Handling  
Operational Research  
Metrication

**Construction**  
A.M.S.E. Civ.  
C. & G. Structural  
Road Engineering  
Civil Engineering  
Building  
Air Conditioning  
Heating & Ventilating  
Carpentry & Joinery  
Clerk of Works  
Building Drawing  
Surveying  
Painting and Decorating.  
Architecture  
Builders' Quantities

**General**  
C.E.I.  
Petroleum Tech.  
Practical Maths.  
Refrigerator Servicing.  
Rubber Technology  
Sales Engineer  
Timber Trade  
Farm Science  
Agricultural Eng.  
General Plastics

**General Certificate of Education**  
Choose from 42 'O' and 'A' Level subjects including:  
*English*  
*Chemistry*  
*General Science*  
*Geology*  
*Physics*  
*Mathematics*  
*Technical Drawing*  
*French*  
*German*  
*Russian*  
*Spanish*  
*Biology*  
*B.I.E.T. and its associated schools have recorded well over 10,000 G.C.E. successes at 'O' and 'A' level.*

**WE COVER A WIDE RANGE OF TECHNICAL AND PROFESSIONAL EXAMINATIONS.**

*Over 3,000 of our Students have obtained City & Guilds Certificates. Thousands of other exam successes.*

## THEY DID IT— SO COULD YOU

"My income has almost trebled... my life is fuller and happier."—Case History G/321.

"In addition to having my salary doubled, my future is assured."—Case History H/493.

"Completing your Course meant going from a job I detested to a job I love."—Case History B/461.

## FIND OUT FOR YOURSELF

These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you.

# Free!

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). We'll send you full details and a FREE illustrated book. No obligation and nobody will call on you... but it could be the best thing you ever did.

## BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept B4, Aldermaston Court, Reading RG7 4PF.

Accredited by the Council for the Accreditation of Correspondence Colleges.



(Write if you prefer not to cut this page)

**B.I.E.T.—IN ASSOCIATION WITH THE SCHOOL OF CAREERS—ALDERMASTON COURT, BERKSHIRE**

## POST THIS COUPON TODAY

To: B.I.E.T., Dept B4, Aldermaston Court, Reading RG7 4PF  
Please send me book and details of your Courses in

Name ..... Age .....

Address ..... BLOCK CAPITALS PLEASE .....

..... Occupation .....

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (Asia) Ltd.; South Africa—Central News Agency Ltd.; Rhodesia and Zambia—Kingstons Ltd.; East Africa—Stationery and Office Supplies Ltd. Subscription Rate (including postage): For one year to any part of the world £2.95 (£2.13.0). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# HENRY'S RADIO LIMITED

## LEADING ELECTRONIC CENTRES



COMPONENTS · TEST · PA · DISCOTHEQUE · ELECTRONIC ORGANS · MAIL ORDER

NEW

**350** pages fully detailed and illustrated covering every aspect of Electronics — plus data and information

**10,000** Stock lines at Special Low Prices and Fully Guaranteed

**PRICE 55p** POST PAID (40p FOR CALLERS)

**PLUS! FIVE 10p VOUCHERS FOR USE WITH PURCHASES**


Send to this address: **HENRY'S RADIO LTD. (DEPT. PE), 3 ALBEMARLE WAY, LONDON, E.C.1.** For catalogue only. (All other mail to "303" as below).

**A NEW HENRY'S CATALOGUE IS A MUST FOR ELECTRONICS TODAY!**
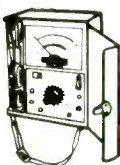
### TEST EQUIPMENT FOR EVERY PURPOSE



- AF105 50kV multimeter (illus.). Price £8.50, p.p. 20p. Leather case £1.42.
- 200H 20kV. Price £3.87, p.p. 20p. Case 62p.
- 500 30kV multimeter. Price £8.87, p.p. 20p. Leather case £1.50.
- THL33 2kV. Price £4.12, p.p. 15p. Leather case £1.15.
- TE65 Valve voltmeter. Price £17.50, p.p. 40p.
- SE250B Pocket pencil signal injector £1.75, p.p. 15p.
- SE500 Pocket pencil signal tracer £1.50, p.p. 15p.
- TE20D RF generator. Price £15, p.p. 40p.
- TE22D Matching audio generator. Price £17, p.p. 40p.
- TE15 Grid dip meter. Price £12.50, p.p. 40p.
- TO3 Scope 3in tube. Price £37.50, p.p. 50p.
- TE21 Audio Generator. Price £17, p.p. 40p.
- CI-5 Pulse Scope. Price £39, p.p. 50p.



### PANEL METERS

Complete range in stock. 38, 65 and 85 types plus large range Edge types also 240°-250° types. (Get a copy of our latest catalogue for full specifications and further ranges.)


**MORE OF EVERYTHING. LOW PRICES ALWAYS FROM HENRY'S**

★ COMPONENTS IN STOCK FOR ALMOST ALL PUBLISHED DESIGNS. YOUR ENQUIRIES INVITED. SEND LARGE SAE (with list) FOR PARTS QUOTE FOR ALL CIRCUITS.

See our advertisement inside this magazine for the largest range of transistors and I.C.'s, etc. available in U.K. Free list No. 36 on request.

**HENRY'S SUPPLY ALL YOUR AUDIO-ELECTRONIC NEEDS!**

### TRANSISTOR AMPLIFIERS

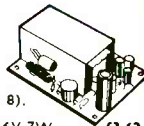

- (Leaflets Ref. Nos. 6 and 8). Post, etc. 20p.
- 4-300 4TR 9V 300mW £1.75
  - 104 4TR 9V 1W £2.12
  - 304 4TR 9V 3W £2.47
  - 555 6TR 12V 3W £2.75
  - PA7 6TR 16V 7W £1.62
  - 608 6TR 24V 10W £4.12
  - 410 4TR 28V 10W £4.97
  - MPA12/3 6TR 18V 12W £4.50
  - MPA12/15 6TR 36V 12W £5.25

- OPTIONAL POWER SUPPLIES** Post, etc., 20p
- P500 (1 or 2) for 104, 304 £2.62
  - PS20 (1 or 2) for PA7 £1.47
  - MU2/4/40 (1 or 2) for MPA12/3 or MPA12/15 £4.50
  - P11 for 608 £2.87
  - P15 for 410 £2.62

### SINCLAIR PROJECT 60

**PACKAGE DEALS—SAVE POUNDS!**

- 2 × Z30 amplifier, stereo 60 pre-amp, P25 power supply. £16.75. Carr. 40p. Or with P26 power supply £18.25. Carr. 40p.
- 2 × Z50 amplifier, stereo 60 pre-amp, P28 power supply £20.25. Carr. 40p.
- Transformer for P28 £2.45 extra. Any of the above with Active Filter unit add £4.75 or with pair Q16 speakers add £16. Also new FM Tuner £21. 2000 Amplifier £24.50. P/P 50p. 3000 Amplifier £31.50. P/P 50p. Also IC12 £2.50

### LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2in × 8 1/2in

- TYPE 150 6 watt, 3, 8 or 15 ohms. £2.12. Post 22p.



- TYPE 150TC Twin cone version. £2.75. Post 22p.
- TYPE 450 10 watt with twin tweeters and crossover. 3, 8 or 15 ohms. £3.50. Post 25p.
- TYPE 350 20 watt with tweeter and crossover. 8 and 15 ohms. £7.50. Post 28p.



**POLISHED CABINETS** For 150, 150TC and 450 £4.50. Post 30p.

**TERRIFIC RANGE OF SPEAKERS, KITS AND CABINETS IN STOCK. SEE CATALOGUE OR YOUR ENQUIRIES INVITED.**

### MONO, STEREO AND MIXING EQUIPMENT. HIGH QUALITY WITH LOW PRICES



### SELF-POWERED SILICON —FET CONTROL UNITS/ PREAMPLIFIERS

- FET 9/4 Mono or single channel. Adjustable levels. All facilities plus microphone. Mixing. £12.50.
  - FET 154 Stereo with all facilities, magnetic cart. input, etc. £16.50.
  - SILICON POWER AMPLIFIERS FOR USE WITH ABOVE**
  - PA25 25 watts into 8 ohms £7.50.
  - PA50 50 watts into 4 ohms £9.50.
  - MU442 Power Supply for 1 or 2. PA25's or 1 only PA50 £6. Post 20p.
- Free Brochure No. 25 on request. No soldering—all units interconnecting. On demonstration at "356".

### NIXIE TUBES

XN3 or XN13 0-9 side view with data sheet, 85p each. GN4 end view 0-9 with socket and data, £1.75. All I.C.'s for Digital Clocks in stock. HENRY'S CLOCK CIRCUIT No. 29/2. 15p.

### 20 WATT I.C. AMPLIFIER

Toshiba 20 watt Power Amplifier, £4.57. Toshiba Pre-Amplifier I.C., £1.50. Data and suggested circuits No. 42, 10p. SL403D 3 watt I.C. amp £1.50 with data and circuits.

### HI-FI TO SUIT EVERY POCKET



TELETON "206". Garrard SP25 Mk III. Goldring G800 Series Cart. Plinth/Cover, 10 watt 3 way bookshelf Speaker Systems, all leads, etc. (Rec. price £81).

SAVE £26.00 **£54.95** Carr. £2

(OR WITH U.K. MADE HL.SA707 (same performance) £56.95).

### PLUS FREE PAIR STEREO HEADPHONES

TELETON F2000 Med. Wave. Stereo FM Tuner. Amplifier. Garrard 2025 TC. 9TAHC Diam. Plinth/Cover, 10 watt Speaker Systems as above, all leads, etc. (Rec. Price £91).

SAVE £31.00 **£59.95** Carr. £2

### PLUS FREE PAIR STEREO HEADPHONES

**THE TWO MOST POPULAR SYSTEMS EVER— PLUS FULL 12 MONTHS' GUARANTEE AS WITH ALL "HENRY'S" OFFERS!**

**FREE** 10-page Audio — Hi-Fi Stock and Stereo Systems terms discounts lists, save up to 40% N. Demonstrations and credit terms (to callers). Plus 12 months' guarantee.

### BUILD THIS VHF FM TUNER

5 MULLARD TRANSISTORS 300kc/s BANDWIDTH. PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately.



Free Leaflet Nos. 3 and 7. TOTAL £6.97, p.p. 20p. Cabinet £1, Decoder Kit £5.97. Tuning meter £1.75. Mains unit (optional) Model PS1000 £2.47. Mains unit for Tuner and Decoder PS1200 £2.62.

### NEW "BANDSPREAD" PORTABLE TO BUILD

Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave bands plus Medium Wave Bandsread for extra selectivity. Also slow motion geared tuning, 600mW push-pull output, fibre glass PVC covered cabinet, car aerial socket. Attractive appearance and performance. TOTAL COST TO BUILD £7.98, p.p. 32p (Battery 22p). All parts sold separately—Leaflet No. 2. "7T" PORTABLE (as previously advertised), £6.98, p.p. 35p from stock. (Leaflet No. 1.)



Electronic Components, Audio and Test Gear Centre  
356 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 4736

High Fidelity Sales & Demonstrations Centre  
354 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-402 5854

Electronic Organs, P.A. & Discotheque Centre  
309 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 6963

Mail Orders, Special Bargain Shop, Industrial Sales  
303 EDGWARE ROAD, LONDON, W.2.  
Tel: 01-723 1008/9

"354" & "356" OPEN SIX FULL DAYS A WEEK 9 am to 6 pm MONDAY TO SATURDAY