

A.C.A.

PRACTICAL

ELECTRONICS

DECEMBER 1972

20p

... for Christmas




HOOTING
OWL

**RALLY
DRIVING
GAME**


Solder a friendship!

Give Antex this Christmas

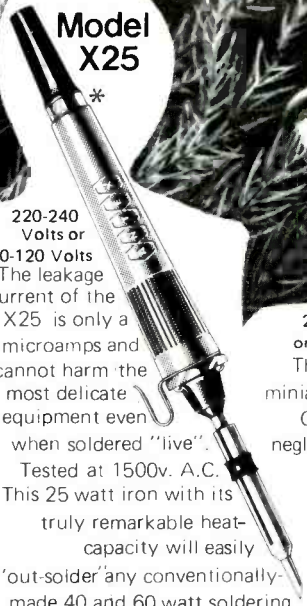

Model X25 *

220-240 Volts or 100-120 Volts
The leakage current of the NEW X25 is only a few microamps and cannot harm the most delicate equipment even when soldered "live".
Tested at 1500v. A.C.
This 25 watt iron with its truly remarkable heat-capacity will easily "out-solder" any conventionally-made 40 and 60 watt soldering irons, due to its unique construction advantages. Fitted long-life iron-coated bit 1/8". **2 other bits available 3/32" and 3/16"** Totally enclosed element in ceramic and steel shaft **Bits do not "freeze" and can easily be removed** PRICE: £1.75 (rec. retail)
Suitable for production work and as a general purpose iron

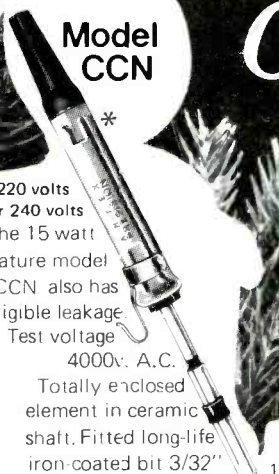

Model CCN *


220 volts or 240 volts
The 15 watt miniature model CCN also has negligible leakage.
Test voltage 4000v. A.C.
Totally enclosed element in ceramic shaft. Fitted long-life iron-coated bit 3/32"
4 other bits available, 1/8" 3/16" 1/4" and 1/16"
PRICE: £1.80 (rec. retail)
OR Fitted with triple-coated, (iron, nickel and Chromium) bit 1/8" £1.95 (rec. retail)





Model CN *

Miniature 15 watt soldering iron fitted 3/32" iron-coated bit. Many other bits available from 1/16" to 3/16".
Voltages 240, 220, 110, 50 or 24
PRICE £1.70 (rec. retail)

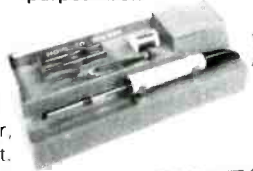Model SK.1 Kit
contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, stand and "How to Solder" booklet.
PRICE £2.75 (rec. retail)



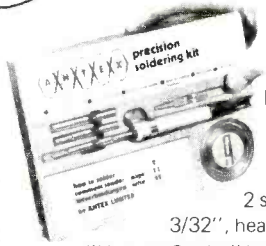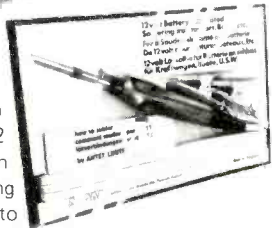Model MES Kit
Battery-operated 12v. 25 watt iron fitted with 15' lead and 2 heavy clips for connection to car battery. Packed in strong plastic wallet with booklet "How to Solder". PRICE £1.95 (rec. retail) *



Model SK.2 Kit
contains 15 watt miniature iron fitted with 3/16" bit, 2 spare bits 5/32" and 3/32", heat sink, solder, and "How to Solder" booklet.
PRICE £2.40 (rec. retail)



From radio or electrical dealers, car accessory shops or, in case of difficulty direct from: —
ANTEX LIMITED FREEPOST
(no stamp required) **PLYMOUTH,**
PL1 1BR Tel. 0752 67377

- Please send the ANTEX colour catalogue.
- Please send the following

I enclose cheque/P.O./Cash (Giro No. 258 1000)

NAME _____

ADDRESS _____



JUST PUBLISHED '73 AUDIO-TRONICS

The great new 1973 edition of Lasky's famous Audio-Tronics catalogue is now available—FREE on request. The 48 newspaper size pages—many in full colour—are packed with 1,000's of items from the largest stocks in Great Britain of everything for the Radio and Hi-Fi enthusiasts, Electronics hobbyist, Serviceman and Communication's Ham. Over half the pages are devoted exclusively to every aspect of Hi-Fi (including Lasky's budget Stereo Systems and Package Deals). Tape recording and Audio Accessories—see the great new Lasky's Credit Plan Scheme—enabling you to buy your ideal choice of equipment on easy terms. Send your name and address and 15p for post and inclusion on our regular mailing list.

LEAK TEAK CASES

Teak or Walnut case for Stereofonic tuner only.

LIST PRICE £7-37 **LASKY'S PRICE £2.50** C & P 25p

Double case to hold Stereo 30 or Stereo 70 and Stereofonic tuner in Teak or Walnut.

LIST PRICE £10-37 **LASKY'S PRICE £4.95** C & P 35p

LEAK TRUSPEED

2-speed 45 and 33 $\frac{1}{2}$ rpm belt drive turntable complete with plinth, cover and Shure cartridge.

LIST PRICE £69.50


LASKY'S PRICE £47.50 C & P £1-50

SINCLAIR PHASE LOCK LOOP STEREO FM TUNER

Incorporates varicap diodes, printed circuit, coils, squelch circuit I.C. Decoder, etc., supplied completely built and tested and ready to be mounted into any cabinet you choose. It may be used with any High Fidelity Amplifier. Power requirements 25/30V DC.

LIST PRICE £25-00 **LASKY'S PRICE £15.75** C & P 25p

BSR TAPE DECK SCOOP

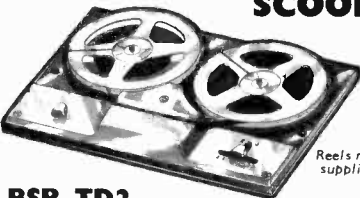

Reels not supplied

BSR TD2

FANTASTIC VALUE. ONLY Lasky's can offer you a tape deck at such an amazing price. The BSR TD2 tape deck operates by a simple reliable mechanism using the minimum of controls.

With $\frac{1}{2}$ track mono heads. Incorporates fast wind and fast rewind, records at 3 $\frac{1}{2}$ ips. giving up to 3 hrs playing time, takes up to 5 $\frac{1}{2}$ in. spools. Size 13in. 8 $\frac{1}{2}$ in. front to rear, 2 $\frac{1}{2}$ in. below plate, 1 $\frac{1}{2}$ in. above plate.

ALSO SUITABLE FOR USE AS A TAPE TRANSPORTER

LASKY'S PRICE £8.95 C & P 35p

BELTEK C5700 8 TRACK

Stereo car Player

Accepts all standard pre-recorded 8 track stereo cartridges. Features include automatic head cleaner, channel select and channel repeat push buttons, slider type volume and tone controls, channel balance. Output 5 watts per channel, frequency response 50Hz-10kHz. Output imp. 4 ohms, size 4 $\frac{1}{2}$ (W) x 1 $\frac{1}{2}$ (H) x 6 $\frac{1}{2}$ (D) in. Operates on 12V DC negative earth. Beautifully styled with black ivory and chrome trim.

BELTEK C5700 complete with mounting brackets and 8 track pre-recorded demonstration cartridge.

£21.00 C & P 30p

BELTEK RS310 FM TUNING ADAPTOR

Matches the C5700, the ideal car stereo system.

LASKY'S PRICE £18.95 C & P 25p

Add £3.75 to any BELTEK car player for pair of FANTAVOX KS701 car speakers.

AKAI TAPE RECORDER SCOOP!

(C & P 75p on all Tape Decks.)

AKAI 4000D illustrated
List Price £93.65 **Lasky's Price £61.50**
AKAI 1720L
List Price £87.36 **Lasky's Price £58.95**
AKAI X1800SD
List Price £162.79 **Lasky's Price £102.50**
AKAI X200D
List Price £157.93 **Lasky's Price £100.50**
2 CSS-8 Speakers
List Price £25.00 (pair) **Lasky's Price £15.95** C & P 50p

2 ADM 11/8 mics. Suitable for use on all Akai tape recorders. List Price £11.90.
Lasky's Price (pair) £7.50. C & P 15p.

NEW WELLER MINI WORKSHOP KIT MODEL 600K

LASKY'S PRICE £17.95 C & P 35p

Powered by a 25,000 rpm, 115V, 75A Universal motor. This small versatile, easy to handle, power tool is ideal for handymen, hobbyists and professionals. The wide selection of bits helps you grind, sharpen, drill, rout, cut, etc. Perfect for delicate work and hard to reach places. The complete MINI-WORKSHOP is housed in a strong plastic carrying case. For 240V a.c. mains operation.

MODEL 600K place Kit contains: ● Model 600 Power Unit ● Accessory Caddy ● 8 Grinding/Sharpening Bits ● 3 polishing Wheels ● 4 Cleaning Bits ● 8 Abrasive Discs ● 3 Abrasive Bands ● Expanding Drum ● Drill Bit ● Mandrell ● Chuck Wrench ● Dressing Stone ● Plastic polish ● Jewellers Rouge ● Complete with owners' manual ● Size of power unit only 7 $\frac{1}{2}$ in.

LEAK SPEAKERS

150 Speakers (pair) £39.90 C & P
250 £52.00 £2.50
600 £69.95

DIGITAL CLOCK

EXCLUSIVELY FROM LASKY'S

The clock measures 5 $\frac{1}{2}$ " (W) x 2 $\frac{1}{2}$ " (H) x 3" (D) (overall from front of drum to back of switch). SPEC: 210/240V a.c. 50Hz operation; switch rating 250V, 3A. Complete with instructions. NOW WITH ILLUMINATED DIGITAL COMPLETE WITH 11 KNOBS FEATURES: ● MAINS OPERATION ● 12-HOUR ALARM ● AUTO "SLEEP" SWITCH ● HOURS, MINUTES AND SECONDS READ-OFF ● FORWARD AND BACKWARD TIME ADJUSTMENT ● SILENT OPERATION ● SHOCK AND VIBRATION PROOF ● BUILT IN ALARM BUZZER SPECIAL QUOTES LASKY'S **£6.50** C & P FOR QUANTITIES PRICE 25p



BSR TD8S 8 TRACK STEREO CARTRIDGE PLAYER

The TD8S is suitable for use with most modern stereo amplifiers and delivers a pre-amp output of 125mV. Power requirements: 210/250V AC, 50Hz. Frequency response: 50Hz-10kHz. 4 pole dynamically balanced synchronous motor. Black and woodgrain plastic cabinet. Size: 8 $\frac{1}{2}$ (W) x 3 $\frac{1}{2}$ (H) x 10 $\frac{1}{2}$ (D) in.

LIST PRICE £24.20 **LASKY'S PRICE £17.50**

Garrard Record Players

SP25 Mk. III Deck Only

SP25 Mk III £10-85
AP76 £18-85
SL95B £32-50
SL95B on base with 9TA cart. £44-00
SL72B £23-95
401 £28-95
40B £9-50
2025TC with stereo 9TA cart. £7-95
Zero 100 £39-95
Zero 100S £37-50

NEW RECORD PLAYER MODULES

These new "Module" systems from Garrard and Lasky's enable you to buy your record player complete with attractive wood plinth, tinted acrylic dust cover and high quality compatible stereo magnetic cartridge—together offering optimum performance and appearance.

GARRARD MODULES

Garrard SP25 Mk. III turntable with Shure M75/6 cartridge £23-95
Garrard AP76 turntable with Shure M75/6 cartridge £33-95
Garrard AP96 turntable (single play version of SL95B) £38-75
Garrard Zero 100S turntable with Shure M93/E cartridge £52-75 C. & P. 75p.

LASKY MODULES

Lasky's (Garrard) SP25 Mk. III turntable with Goldring G800 cartridge £20-50
Lasky's (Garrard) AP76 turntable with Goldring G800 cartridge £30-50
Lasky's (Goldring) GL75 turntable with Goldring G800 cartridge £45-00
Lasky's (Goldring) GL75 turntable with Goldring G800/e cartridge £49-50 C. & P. 75p.

Lasky's

MAIL ORDERS AND CORRESPONDENCE
3-15 CAVELL STREET
LONDON E1 2BN 01-790 4821

West End and City Branches
42-45 TOTTENHAM CT. RD., LONDON, W.1 Tel: 01- 636 0845
207 EDGWARE ROAD, LONDON, W.2. Tel: 01-723 3271
33 TOTTENHAM CT. RD., LONDON, W.1. Tel: 01-636 2605
Open all day 9a.m. - 6p.m. Monday to Saturday.
109 FLEET STREET, LONDON, E.C.4 Tel: 01-353 5812
Open all day Thursday, early closing 1p.m. Saturday


Connoisseur

B.D.2 Press button speed change turntable



The Connoisseur BD2 belt drive turntable with press button speed change is an integrated turntable and pickup arm assembly, the raise/lower device of which is operated by the knob at the front right hand corner. The head shell allows for the lateral adjustment of the cartridge. The BD2 is supplied as a chassis unit or spring mounted on a wood plinth complete with dust cover.

B.D.1 Turntable kit

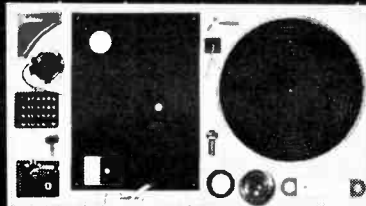


The B.D.1 well known for its superb performance and quality two speed working through a flexible belt drive system is now available in kit form. Construction is simplicity itself with no soldering required. Now it's so easy to own the best.

A.R. SUGDEN & CO. (ENGINEERS) LTD.

Market Street, Brighouse HD6 1DX, Yorkshire. Telephone: 2142.

Are you alright for Jacks?

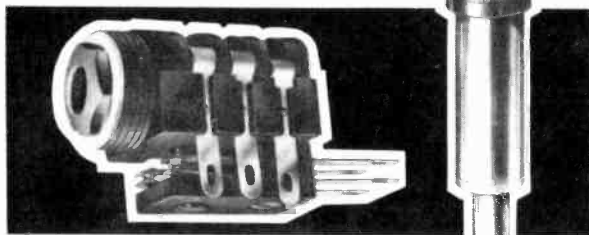

Ask for Rendar Jack plugs and sockets at your local stockist. They come in a wide variety of configurations, and in cases of difficulty can be ordered DIRECT from the Rendar factory.

Standard, mini and sub-miniature sizes... plugs in both screened and unscreened versions... socket bodies in high melting point thermoplastic... several unique features (some protected by UK and US Patents)... Post Office and NATO specifications.

If you want to study all the facts and figures, all the ingenious construction details, send for the Rendar Electronic Components Catalogue of technical data sheets covering their entire range of products.

The cost of the catalogue is 25p, including P & P, and it's money very well spent!



RENDAR®

Rendar Instruments Ltd., Victoria Road Burgess Hill, Sussex. Tel. Burgess Hill 2642-4 Cables: Rendar, Burgess Hill

SOUND BARGAINS



GIANT POWER MULTI-WAVEBAND COMMUNICATIONS RECEIVER

WITH 3 in 1 AC/DC POWER SUPPLY SYSTEM
MAINS/BATTERY plus BUILT-IN BATTERY BOOSTER

OUR PRICE £10.50
+40p P. & P.

THIS NEW 1972 RADIO. No less than 3 VHF BANDS. Picks up Aircraft Transmissions, Pop Pirates, Taxis, Ambulances, Local Radio, Continental and all BBC, VHF Stations plus fascinating Public Service Transmissions we are not allowed to mention! Even TV sound in certain areas. PLUS A SPECIAL WEATHERBAND. Frequency ranges: MW 40-1500kHz, FM 98-108MHz, Airband 108-135 MHz, VHF 145-174 MHz, 23 semiconductors—12 transistors, 11 diodes and thermistors. Automatic frequency control. 31in telescopic aerial. Runs off mains a.c. 230/250V or off 4 U11 batteries, or use re-chargeable nickel alkali cell. Finished in strong leather grained case with carrying handle. Approx. size 10 1/2in x 6 1/2in x 3 1/2in. Written guarantee. Special magnetic ear-piece for personal listening, dry batteries free. HURRY! Limited quantity only from Marktyme.

OUR PRICE £28.95
+50p P. & P.



Tune into the world with this amazing communications receiver. A truly exceptional unit in performance and looks—leatherette with stainless steel trim. Looks good anywhere. Use either as a portable with standard batteries or plug it directly into 220-240V domestic mains supply. 14 transistors; 9 diodes; 1 thermistor. Internal ferrite rod antenna plus telescopic aerial. Separate tone, volume and tuning controls with push-button selectors for the 8 WAVEBANDS. Complete with Hi-Fi earphone for personal listening. Frequency ranges: Long wave 150-350 kHz. Medium 350-1605 kHz. Marine 1.6-4.3 MHz. Short Wave 12-24 MHz. FM/VHF 88-108 MHz. Aircraft 108-135 MHz. PUBLIC SERVICE BANDS 135-174 MHz. Fully guaranteed.

N.B. The Ministry of Post & Telecommunications has pointed out that a licence (not generally available to the public) is required for reception of transmissions by Fire Brigade, Aircraft, Shipping, etc.

SONIC SOUND AUDIO LTD.

(Dept. PE7), 372 EDGWARE ROAD LONDON, W.2. Tel. 01-723 0094
Callers welcome Mon. to Sat. 9 a.m.-6 p.m.

SAXON ENTERTAINMENTS

STANDARD and CUSTOM-BUILT AUDIO and ELECTRONIC EQUIPMENT
NEW and SECONDHAND MUSICAL INSTRUMENTS. MAIN DISTRIBUTORS
FOR A.K.G. HIGH QUALITY MICROPHONES

SA25-SA35-SA100

LOW-PRICED AUDIO MODULES FOR
DOMESTIC and COMMERCIAL USE



THESE THREE MODULES HAVE ENJOYED UNPARALLELED SUCCESS DURING THE FIRST FEW MONTHS OF THEIR BEING MADE AVAILABLE TO THE GENERAL PUBLIC. WE ARE PLEASED TO ANNOUNCE THAT WE CAN NOW OFFER FAST DISPATCH ON MOST OF OUR ADVERTISED ITEMS, INCLUDING THESE THREE MODULES.

SA25 £2-95 carr. free

25 WATTS R.M.S. 7 transistors, 7 diodes

SA35 £4-45 carr. free

35 WATTS R.M.S. 7 transistors, 7 diodes

SA100 £10-90 carr. free

100 WATTS R.M.S. 11 transistors, 6 diodes

ALL THREE MODULES HAVE OPEN AND SHORT CIRCUIT PROTECTION, AND THE SA100 IS PROOF AGAINST OVER-DISSIPATION AND FAULTY INDUCTIVE LOADS.

ONLY ADVANCED DESIGN TECHNIQUES MAKE THESE EXTRAORDINARILY LOW PRICES POSSIBLE.

BRIEF SPEC. FOR ALL THREE MODULES

Freq. response	15-40,000Hz \pm 1dB
Distortion	0.2% at 1kHz
Loads	4 to 16 ohms
Quiescent current	15mA
Noise	Better than -75dB
Supply voltage	25-45V, SA25/35 40-70V, SA100
Size	4 1/2 in \times 4 in \times 1 in (SA100) 4 in \times 3 in \times 1 in (SA25, SA35)

Circuits, connecting instructions and application data are supplied free with all modules.

POWER SUPPLIES FOR THE SA25/35 and SA100 AUDIO MODULES

PS45	Stabilised module for 2 SA25's or two SA35's, £35-0, carr. free
MT45	Transformer for above, heavy duty, £2-85, carr. 20p
MT30	Transformer for unstabilised supply complete with rectifier diodes mounted, £3-50, carr. 20p
PU70	Unstabilised supply for one or two SA100, £7-75, carr. 40p
PS70	Stabilised supply module for one or two SA100's, £4-90, carr. free
MT70	Transformer for PS70, £4-90, carr. 40p

ALL MODULES ARE BUILT ON GLASS FIBRE P.C. BOARD

OTHER SAXON PRODUCTS . . .

120 WATT HEAVY DUTY MODULE

Featuring a rugged class A driver stage, this module will run from all our mixers etc., and most other makes of mixer. It delivers 120W into an eight ohm load and employs 4 TO3 can (115W) output transistors.

SPECIFICATION

Power output	120W into 8 ohms
Freq. response	20-20,000Hz \pm 2dB
Input sensitivity	200mV into 10K
Construction	Fibreglass board
Size	8 in \times 4 in \times 4 in (5 in with supply)
Low distortion parallel push-pull output stage.	

£13-90 + 20p carr. or with supply £18-95 + 40p carr.




NEW: 160 Watt version + supply £27-90

SINGLE CHANNEL SOUND/LIGHT CONVERTER

This compact and reliable unit operates from amplifiers with outputs from 5-100W. Does not impose a heavy load on the amplifier, or, if connected in the wrong polarity, cause any damage, as with some units.

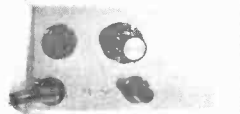Operation is simplicity itself and the unit is fully fused. The unit is supplied to function from bass notes but may easily be converted to respond only to treble or mid-range notes by the addition of components costing less than 5p.



£8-90 carr. free

THREE CHANNEL SOUND TO LIGHT UNIT

Handling the total of 3,000W (3kW) this unit is unique for its price in that not only bass middle and treble but also master controls are provided. Two amplifier sockets eliminate the need for split leads, etc. Supplied in tough white steel case with a blue steelevite hooded cover. Fully guaranteed.

£19-75 30p

MONO VERSION £6-50, carr. 20p
(As illustrated below, S.A.E. details. 9V operation)
OUTPUTS UP TO 1V RMS



£15-80 carr. 30p
SAXON STEREO CONTROL UNIT


Two decks, and full headphone monitoring. The unit is mains operated and measures 17 1/2 in \times 3 in \times 4 in deep and is finished with a smart white on black facia. The controls are: Left/Right deck fader, volume, bass, treble, headphone selector and volume, microphone volume, bass, treble, mains on/off. THIS IS A MUST FOR THE HOME BUILT HIGH QUALITY DISCO-THEQUE AND IS COMPARABLE TO UNITS AT OVER TWICE THE PRICE.

COMPLETE AMPLIFIERS

THE CS 100. £34-90 carr. free

This versatile unit is now available in a black vynide case and so represents even better value than ever, delivering speech and music powers of up to 100W R.M.S. and continuous signal outputs of 70W.

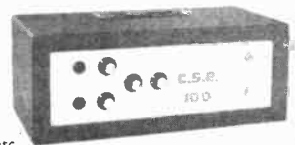Two individually controlled inputs with wide range bass and treble controls. Ideal for small groups, D.J.'s, etc.



The SAXON 100. £48-50, carr. free.



With an R.M.S. output of 120W speech and music, 100W continuous power, four individually controlled F.E.T. input stages and wide range bass and treble controls, this amplifier has established itself as a unit offering quality and reliability at low cost.

LOUDSPEAKERS British made bargains !!!

12in 25W 8/15 ohms £5-95, carr. 30p. 15in 50W 8/15 ohm, £14-50, carr. 50p.

12in 40W 15,000 gauss magnet system 8/15 ohm, £11-50, carr. 40p.

A.K.G. MICROPHONES suitable for disco, group or general P.A. use

D11DHL r.r.p. £11, our price £9-45 post free.

D190C High Z r.r.p. £21-50, our price £17-45 post free.

D1000C 24 ct. gold plate r.r.p. £37, our price £32 post free.

SEND S.A.E. FOR OUR A.K.G. PRICE LIST. DISCOUNTS ON ALL MICS.

CALLERS AND MAIL ORDER:
327-331 Whitehorse Rd.,
West Croydon, Surrey
CRO 2HS Tel. 01-684 6385

CALLERS ONLY: OUR NEW DISTRIBUTORS.
CIRCLE SOUND
328-330 The Banks
Rochester.
Medway 404199

BUSINESS HOURS:
9.30 a.m. to
5.30 p.m.

TERMS OF BUSINESS: C.W.O. or C.O.D. (35p extra). All cash in regd. envelopes please! Telephone orders to our CROYDON BRANCH. TRADE AND EXPORT ENQUIRIES INVITED

E.M.I. WOOFER AND TWEETER KIT

£5.75 THE PAIR Post 25p. (Available separately. Woofer £4.25; Tweeter £1.50).

Comprising a fine example of a Woofer 10 1/2 in. with a massive Ceramic Magnet, 44oz, Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 in. square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN DESIGN. TEAK WOOD FINISH



£9 Post 25p

8 in. or 10 in. ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 60-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 8 in. 10 watts, 10 in. 12 watts music power. £3.75


TEAK HI-FI SPEAKER CABINETS

MODEL "A". 20 x 13 x 9 in. For 12 in. dia. or 10 in. speaker. £9 Post 25p

MODEL "B". 16 x 10 x 9 in. For 13 x 8 in. or 8 in. speaker. £5 Post 25p


MODEL "C". 16 x 8 x 6 in. For 10 x 6 in. or 6 in. speaker. £4 Post 25p

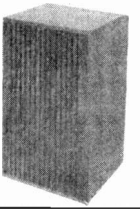LOUDSPEAKER CABINET WADDING 18 in. wide, 1 1/2 ft



BARGAIN AM TUNER.

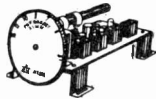Medium Wave. Transistor Superhet. Ferrite aerial. 9 volt. £4.95



BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER.

Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt. battery operated. £3.95



STEREO VERSION OF ABOVE £5.95

BARGAIN FM TUNER

88-108 Mc/s Six Transistor. 9 volt. Printed circuit. Calibrated slide dial tuning. Walnut Cabinet. Size 7 x 5 x 4 in. £14.85



BARGAIN FM TUNER £9.85

as above less cabinet
BARGAIN 3 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built, with volume control. 9 volt battery operated. £4.50

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER.

Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. £2.50 Post 15p



WAFER HEATING ELEMENTS THIN

OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse, factory (available in manufacturing quantities). Approx. size 10 1/2 x 8 1/2 in. Operating voltage 200/250V. a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopiers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for Heating Pads, Food Warmers, Convectector Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryers, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in the greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY 40p EACH (FOUR FOR £1.50)
ALL POST PAID—Discounts for quantity.

BAKER 12in MAJOR £9



30-14,500 c.p.s., 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c.p.s. Rated 20 watts. State 3 or 15 ohm. Post Free.

Module kit, 30-17,000 c.p.s. with tweeter, crossover, baffle and instructions. £11.50


BAKER "BIG-SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" £8 Post Free
12 in. 25 watt
3, 8 or 15 ohms.

GROUP "35" £9 Post Free
12 in. 35 watt
3, 8 or 15 ohms.

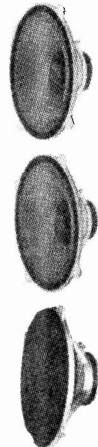GROUP "50" £20 Post Free
15 in. 50 watt
3, 8 or 15 ohms.



BAKER 100 WATT

ALL PURPOSE TRANSISTOR AMPLIFIER

4 inputs speech and music. Mixing facilities. Response 10-30,000 cps. Matches all loudspeakers. A.C. 200/250V. Separate Treble and Bass controls. Guaranteed. Details S.A.E. £49 Post Free




CALLERS ONLY: DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mikes, Discos, Organs, Guitars, etc 4, 8 and 15 ohm matching. £55


Q MAX CHASSIS CUTTERS

A die, punch and Allen Screw		
1 in. Round	88p	1 in. Round 88p Key "B" for above 8p
1 1/4 in. Round	75p	1 1/4 in. Round 98p 2 in. Round £2.05
Key "T" for above	5p	1 1/2 in. Round 98p 2 1/2 in. Round £2.30
1 in. Round	83p	1 1/4 in. Round £1.05
1 1/4 in. Round	83p	1 1/2 in. Round £1.05 above 12p
1 in. Round	83p	1 1/4 in. Round £1.05 2 in. Round £4.10
1 1/4 in. Round	88p	1 1/2 in. Round £1.10 2 in. Round £5.25
1 in. Round	88p	1 1/4 in. Round £1.10 3 in. Round £8.10
1 1/4 in. Round	89p	Key "E" for above 18p
1 in. Round	90p	1 in. Round £1.43 1 in. Square with key £1.93
Key "A" for above	5p	1 1/4 in. Round £1.50

SLIDER VOLUME CONTROLS

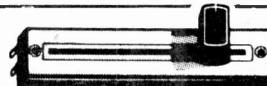

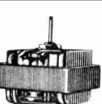Available in both LOG and LINEAR type. Size 3 1/2 x 1 1/2 in. with knobs. 5K, 10K, 25K, 50K, 100K, 250K, 500K, 1 MEG. 2 MEG. 65p EACH



E.M.I. TAPE MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 135mA. Spindle 0-187 0.75 in. Size 3 1/2 x 1 1/2 in. (illustrated). Post 15p. £1.25

BALFOUR GRAM MOTORS. 120v. or 240v. AC. 1,200 r.p.m. 4 pole 30mA. Spindle 1/2 in. 3/20. Size. 85p

E.M.I. GRAM MOTORS. 120v or 240v a.c. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 x 2 1/2 in. 75p Post 15p

BAKER HI-FI SPEAKERS


HIGH QUALITY — BRITISH MADE

REGENT

12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver. Bass Resonance 45cps
Flux Density 12,000gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models

£8 Post Free

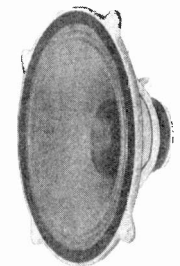


DE-LUXE Mk II

12 in. 15 watts

Especially designed to provide full range reproduction at an economical cost. Suitable for use with an hi-fi system. Built-in concentric tweeter cone. Bass Resonance 30cps
Flux Density 14,000gauss
Useful response 25-16,000cps
8 or 15 ohms models

£10 Post Free

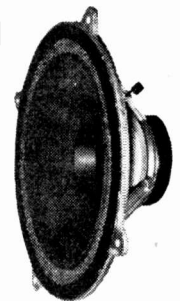


SUPERB

12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register. Bass Resonance 25cps
Flux Density 16,500gauss
Useful response 20-17,000cps
8 or 15 ohms models

£15 Post Free

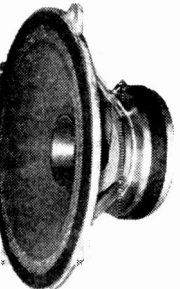


AUDITORIUM

12 in. 25 watts

A full range reproducer for high power. Electronic Guitars, public address, multi-speaker systems, electronic organs. Ideal for Hi-Fi and Discotheques. Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 25-16,000cps
8 or 15 ohms models

£14 Post Free

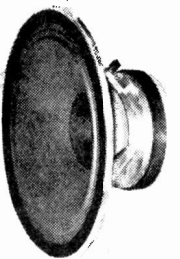


AUDITORIUM

15 in. 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic instruments and the home. Bass Resonance 35cps
Flux Density 15,000gauss
Useful response 20-14,000cps
8 or 15 ohms models

£20 Post Free

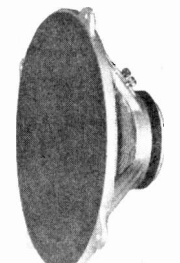

Hi-Fi Enclosure Manual containing 20 plus designs, crossover data and cubic tables. 42p. Post Free.

CALLERS WELCOME • CUSTOMERS FREE CAR PARK

SPECIALISTS

(Export: Remit cash and extra postage.)

337 WHITEHORSE ROAD • GROYDON

OPEN 9-6 p.m. (WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home—the fast, modern way. Give yourself essential technical “know-how”—like reading circuits, assembling standard components, experimenting, building—quickly and without effort, and enjoy every moment. B.I.E.T.’s simplified study method and the remarkable **TECHNATRON** Self-Built Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors—even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.


You LEARN—but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build—and it's a good one—is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course—but it teaches the real thing. The easy to understand, 'practical projects—from a burglar-alarm to a sophisticated Radio set—help you master basic Radio and Electronics—even if you are a “non-technical” type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

Specialist Booklet

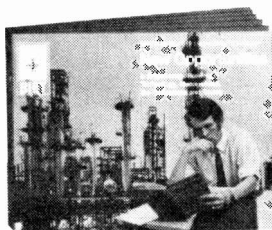If you wish to make a career in Electronics, send for your FREE copy of “NEW OPPORTUNITIES”. This brand new booklet—just out—tells you all about **TECHNATRON** and B.I.E.T.’s full range of courses.



FREE
BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B12, ALDERMASTON COURT, READING RG7 4PF
Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

B12

NAME
(BLOCK CAPITALS)

AGE

ADDRESS

SUBJECT OF INTEREST

Save on FERRANTI

All devices Top grade Brand new. Fully guaranteed.

		* DIODES *		* ZENERS *	
BFS59	13p	ZTX313	10p	ZS120	7p
BFS60	18p	ZTX314	11p	ZS121	9p
BFS61	18p	ZTX320	28p	ZS122	11p
BFS96	13p	ZTX330	13p	ZS123	14p
BFS97	21p	ZTX331	14p	ZS124	16p
BFS98	18p	ZTX382	11p	ZS140	22p
ZTX107	8p	ZTX383	13p	ZS141	39p
ZTX108	7p	ZTX384	16p	ZS142	30p
ZTX109	10p	ZTX450	15p	ZS170	9p
ZTX114	20p	ZTX451	15p	ZS171	11p
ZTX212	12p	ZTX500	10p	ZS172	14p
ZTX213	12p	ZTX501	11p	ZS174	15p
ZTX214	13p	ZTX502	15p	ZS176	21p
ZTX300	10p	ZTX503	12p	ZS178	34p
ZTX301	11p	ZTX504	39p	ZS270	10p
ZTX302	15p	ZTX510	15p	ZS271	14p
ZTX303	12p	ZTX530	19p	ZS272	16p
ZTX304	19p	ZTX531	20p	ZS274	17p
ZTX310	8p	ZTX550	15p	ZS276	23p
ZTX311	9p	ZTX551	15p	ZS278	33p
ZTX312	9p	2N3055	65p		

MOTOROLA. MJE2955, £1-06; MJE3055, 65p; 2N4444, £2-25.

R.C.A. CA3075, £1-35; CA3090Q, £4-30.

GEMINI TUNER. Full set of semiconductors, £7-60.

P.E. ELECTRONIC PIANO—SPECIAL BULK PRICES!

350 ZS170, £20; 110 ZTX300, £9-50; 24 ZN7474E, £14-40; 14 KS047A, £2-30; ZT3055, 65p each; ZT3053, 16p each.

We can supply all Ferranti semiconductor devices used in this instrument.

Postage and packing 10p. Free over £2. Send S.A.E. for Ferranti data.

WE CAN SUPPLY ANY FERRANTI DEVICE. Send S.A.E. for quotation.

WE SELL ONLY THE BEST

DAVIAN ELECTRONICS

PO BOX 38, OLOHAM, LANCS. OL2 6XJ.

NEW COMPONENTS

Post and Package free for orders over £1-50. Include 10p P. & P. for each single pack under £1-50.

200 Mixed Resistors, all types, 50p.

100 Mixed Modern and Miniature Resistors, 50p.

10mF 64V Electrolytic Caps, 5 for 25p; 12 for 50p.

640mF 16V Electrolytic Caps, 3 for 30p; 7 for 60p.

100 New Mixed Caps, 60p.

10mF 63V Wima non-Electrolytic, 15p each.

TRANSISTORS

Any 6 of the following 50p or 10p each. OC71, BFY50, 2N3702, CV8615 (BSY95A), NTG885.

CONSTRUCTORS' ITEMS

P. & P. free for orders over £3-50. Half-hour timers—consisting of: 12.0.12 T/F Transistors, Diodes and Capacitors, 40p each, P. & P. 16p; or 3 for £1, P. & P. 20p.

Subminiature Omron 12V d.c. Relays. Mounted on CCT Board, 3 for 60p, P. & P. 9p. Mounted on CCT Board with components, 2 for 60p, P. & P. 7p.

G.P.O. Relays various, 200 Ω –7,000 Ω , 30p each. Uniselectors, 10 pole, 25-way, £1 each, P. & P. 25p. Dictating Machines working with Mic. etc., £6-50, P. & P. 75p. Requiring attention, £2-50. Ideal for spares. Motor, power pack, rec./play electronics.

THIS MONTH'S HI-FI BARGAINS

Quadraphonic cartridge player with slider controls plus 4 speakers. Cartridges available. List on application, our price £100.

GARRARD SP25, Mk. 3, £11; SONOTONE 9TAHCD, £2-10; GOLDRING G800, £8-65; GOLDRING G850, £5-70; GOLDRING G101/P/T UNIT, £22-50. ALL ABOVE POST FREE.

EX COMPUTER CIRCUIT BOARDS

10 Boards, 50p, P. & P. 8p.

25 Boards, £1, P. & P. 18p.

2 Boards with 2 Power Transistors, i.e. 4 x OC28 type, 50p, P. & P. 7p.

LAWBAK ELECTRONICS

18 High Road, Swaythling, SOUTHAMPTON
Telephone: Southampton 58479

NO HALF DAY CLOSING

CRESCENT RADIO LTD

11 & 40 MAYES ROAD, LONDON N22 6TL 888 3206

MAIL ORDER
DEPT.
No. 11
MAYES RD.
LONDON
N22
6TL

COMPONENTS AND HI FI FOR THE HOME CONSTRUCTOR

OUR SHOPS ARE OPEN ALL DAY
FROM 9 A.M. TO 6 P.M. 6.30 P.M. ON FRIDAY
(WE CLOSE ALL DAY THURSDAY)
13 SOUTH MALL, EDMONTON, N.9 803 1685

LOW VOLTAGE AMPLIFIER

3 transistor amplifier complete with volume control, is suitable for 9V d.c. and a.c. supplies. Will give about 1W at 8 ohm output.
With high IMP input this amplifier will work as a record player, baby alarm, etc., amplifier.



£1.75
plus 13p P. & P.

TRI-VOLT BATTERY ELIMINATOR

Enables you to work your Transistor Radio, Amplifier or Cassette, etc., from the a.c. mains through this compact Eliminator. Just by moving a plug you can select the voltage you require, 6, 7½ or 9 volt. This means all your transistor power pack applications can be handled by this one unit. Approx. size 2½in x 2½in x 3½in. Our Price **£2.75** plus 10p P. & P. Same model suitably wired for the Philips Cassette **£3** plus 10p P. & P.



DIGITAL CLOCK KIT

24-hr. Nixie dig. clock kit. We supply a complete set of components; a complete set of easy to follow instructions; printed circuits made to make construction as simple as possible; a cabinet and front panel to give a professional finish. All for the price of the components. **£32.50** + 50p P. & P. Please send S.A.E. if you require more information.



EA1000 3 WATT AUDIO AMPLIFIER

An Audio Amplifier designed around the TAA821 Linear I.C.—
Supply Voltage 9-24V
Speaker Imp. 8-16 ohm
Frequency 50Hz-25kHz
Overall Size 2½in x 3½in x 1½in
Ideal Amplifier for radios, record players, stereo units, etc.
Full technical data and diagrams with each module. All guaranteed and a bargain at **£2.63** + 5p P. & P.



£2.63
+ 5p P. & P.

IB4K05

Bridge Rectifier (Texas) Plastic encapsulated 50V at 4A. Approx. size 1½in. x 1½in. x ½in. Our Price **60p** each.




MINI LOUSPEAKERS

2½in 8 ohm 50p
2½in 80 ohm 50p
2½in 40 ohm 50p
Please include 5p P. & P. on each L.S.



PRINTED CIRCUIT KIT

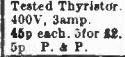BARGAIN S.O.R. Everything you producing your own Printed Circuits. **£1.40** plus 10p P. & P.



CRESCENT MINI-STROBE

- Approx. 1 Joule output
- Variable speed
- A.C. 220-250V
- Approx. size—6" x 4" x 4"



Ideal for Discos, etc. Working and Guaranteed **£16.50** + 38p P. & P.
For more details send a S.A.E.

TRI-VOLT CAR SUPPLY

Enables you to work your Transistor Radio, Amplifier or Cassette, etc. from the 12 volt car supply. Positive or negative earth. Approx. size = 2in. x 3½in. x 1½in. This converter supplies 6, 7½ or 9 volts and is transistor regulated. A real money saving device for **£2.50** plus 10p P. & P.

MINIATURE RELAY

6 volt 70 ohm. Single Pole Changeover — **40p** plus 5p P. & P. Approx. size = 1½in. x 1in. x 1½in.

ADD LUXURY TO YOUR CAR

WITH A MOTOR DRIVEN CAR AERIAL

Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p
Control Switch. **£5.75** P. & P.



CRESCENT CASSETTES

Top quality cassettes at unbeatable prices (complete with standard storage case): C60 28p, C90 38p, C120 48p plus 5p P. & P.

PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass—Middle—Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 500W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed) **£18.50** plus 38p P. & P.



If you require more information please send S.A.E.

S. G. BROWN HEADPHONES

Used! But in good working condition. These Type "P" phones are 4,000 Ω imp. **50p** P. & P. per pair



CRESCENT 100W STEREO


A new style 100 watt per channel stereo amplifier. All loudspeaker systems, 8-15 ohm are suitable. This amplifier is designed for the D.J. and group who must have good looking and reliable equipment. A bargain at **£62**. We also have a mono 100 watt at **£45**. Please include £1 P. & P. and insurance. If you require more information please send S.A.E.



MULTI MINI VICE AND STAND

£8.95

26p P. & P.

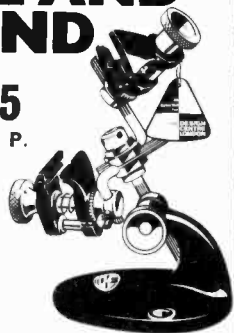

IDEAL XMAS PRESENT

This unique all purpose vice is just like a "third hand" countless uses for the electronics enthusiast—assembly, soldering, gluing, wiring, drilling, etc. Firm base, positive grip for all shapes of work, with independently adjustable twin jaws.

Truly a precision made bargain.

Also single jaw model **£5.45** (22p P. & P.)

FREEBORN LTD. (Dept. PE12)
Beechfield House • West Bar
Banbury • Oxon

Also available at your local model shop

EX COMPUTER PRINTED CIRCUIT PANELS
2in x 4in packed with semi-conductors and top quality resistors, capacitors, diodes, etc. Our price 10 boards 50p, P. & P. 7p. With a guaranteed minimum of 35 transistors. Data on transistors included.

SPECIAL BARGAIN PACK. 25 boards for **£1**, P. & P. 18p. With a guaranteed minimum of 85 transistors. Data on transistors included.

PANELS with 2 power transistors similar to OC28 on each board—components 2 boards (4 OC28) 50p, P. & P. 5p.

9 OA5, 3 OA10, 3 Pot Cores, 26 Resistors, 14 Capacitors, 3 GET 872, 3 GET 872B, 1 GET 875. All long leaded on panels 13in x 4in. 4 for **£1**, P. & P. 25p.

709C OPERATIONAL AMPLIFIER TO5

8 lead I.C. 1 off 50p. 50 off 35p. 100 off 20p.

250 MIXED RESISTORS **62p**
½ & ¼ watt.

150 MIXED HI STABS **62p**
½, ¼ & 1 watt 5% & better.

QUARTZ HALOGEN BULBS

With long leads. 12V 55W for car spot lights, projectors, etc. 50p each. P. & P. 5p.

GPO EXTENSION TELEPHONES

with dial but without bell. 85p each. P. & P. 30p. **£1.75** for 2. P. & P. 50p.


BARGAIN RELAY OFFER

Single pole change over silver contacts 25V to 50V. 2.5k Ω coil. 8 for 50p. P. & P. 5p.

KEYTRONICS mail order only
44 EARLS COURT ROAD
LONDON, W.8 01-478 8499

VEROSTRIP

LENGTH 8'5"

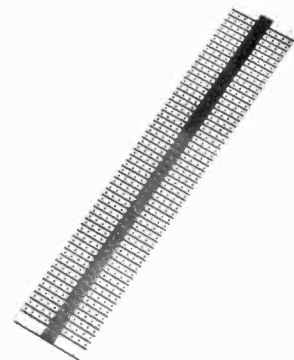

WIDTH 1.5"

Available from your Local Retailer

0.1 and 0.15 pitch Vero Strip is suitable for all applications where Tag Boards can be used.



VERO ELECTRONICS LTD.
INDUSTRIAL ESTATE
CHANDLERS FORD HANTS.

SEW PANEL METERS

USED EXTENSIVELY BY INDUSTRY, GOVERNMENT DEPARTMENTS, EDUCATIONAL AUTHORITIES, ETC.
 ● LOW COST ● QUICK DELIVERY ● OVER 200 RANGES IN STOCK ● OTHER RANGES TO ORDER

NEW "SEW" DESIGNS!

CLEAR PLASTIC METERS

TYPE SW. 100	TYPE S-80
100 x 80 mm	80 mm square fronts
500μA £3-50	50μA £3-50
1mA £3-40	500-50μA £3-40
20V d.c. £3-40	100μA £3-40
50V d.e. £3-40	100-0-100μA £3-30
300V d.e. £3-40	500μA £3-35
1A d.e. £3-40	1mA £2-35
50V d.e. £3-40	20V d.e. £2-85
300V a.c. £3-40	50V d.e. £2-85
VU Meter £4-15	300V d.e. £2-85
	VU Meter £3-70

"SEW" CLEAR PLASTIC METERS

Type MR.85P. 4 1/2in fronts.

50μA £3-95	500μA £3-10
50-0-50μA £3-40	100mA £3-10
100μA £3-40	500mA £3-10
100-0-100μA £3-30	1A £3-10
200μA £3-30	5A £3-10
500-0-500μA £3-10	15A £3-10
1mA £3-10	30A d.c. £3-20
1-0-1mA £3-10	30V d.e. £3-10
5mA £3-10	50V d.e. £3-10
10mA £3-10	150V d.e. £3-10
	300V d.e. £3-10
	300V a.c. £3-10
	S Meter £3-15
	1mA £3-95
	VU Meter £3-95
	5A a.c. £3-10
	10A a.c. £3-10
	20A a.c. £3-10
	30A a.c. £3-10

Type MR.85P. 2 1/2in square fronts.

50μA £2-30	20V d.e. £2-20
50-0-50μA £2-25	50V d.e. £2-20
100μA £2-25	300V d.e. £2-20
100-0-100μA £2-15	15V a.c. £2-30
500μA £2-55	300V a.c. £2-30
1mA £2-20	S Meter £2-20
5mA £2-20	1mA £2-30
10mA £2-20	VU Meter £2-30
50mA £2-20	1A a.c. £2-20
100mA £2-20	5A a.c. £2-20
1000mA £2-20	10A a.c. £2-20
5A £2-20	20A a.c. £2-20
10V d.c. £2-20	30A a.c. £2-20

Type MR.52P. 2 1/2in square fronts.

50μA £2-30	20V d.e. £2-20
50-0-50μA £2-25	50V d.e. £2-20
100μA £2-25	300V d.e. £2-20
100-0-100μA £2-15	15V a.c. £2-30
500μA £2-55	300V a.c. £2-30
1mA £2-20	S Meter £2-20
5mA £2-20	1mA £2-30
10mA £2-20	VU Meter £2-30
50mA £2-20	1A a.c. £2-20
100mA £2-20	5A a.c. £2-20
1000mA £2-20	10A a.c. £2-20
5A £2-20	20A a.c. £2-20
10V d.c. £2-20	30A a.c. £2-20

Type MR.52P. 3 1/2in fronts.

50μA £3-70	20V d.e. £2-40
50-0-50μA £3-00	50V d.e. £2-40
100μA £3-00	150V d.e. £2-40
100-0-100μA £2-80	300V d.e. £2-40
200μA £2-80	15V a.c. £2-55
500-0-500μA £2-85	50V a.c. £2-55
1mA £2-40	150V a.c. £2-55
5mA £2-40	300V a.c. £2-55
10mA £2-40	500V a.c. £2-55
60mA £2-40	S Meter £2-55
100mA £2-40	1mA £2-60
500mA £2-40	VU meter £2-70
1A £2-40	5A a.c. £2-40
5A £2-40	100mA a.c. £2-40
10A £2-40	200mA a.c. £2-40
15A £2-40	500mA a.c. £2-40
30A £2-40	1A a.c. £2-40
50A £2-40	5A a.c. £2-40
50V d.c. £2-40	10A a.c. £2-40
5V d.c. £2-40	20A a.c. £2-40
10V d.c. £2-40	30A a.c. £2-40

"SEW" BAKELITE PANEL METERS

Type MR.85 3 1/2in square fronts.

50μA £3-85	1A £2-15
50μA £3-85	15A £2-15
50-0-50μA £2-80	150A £2-15
100μA £2-80	30A £2-15
100-0-100μA £2-50	50A £2-15
500μA £2-45	5V d.e. £2-15
500-0-500μA £2-15	10V d.e. £2-15
1mA £2-15	20V d.e. £2-15
1-0-1mA £2-15	50V d.e. £2-15
5mA £2-15	150V d.e. £2-15
10mA £2-15	300V d.e. £2-15
50mA £2-15	50mV d.e. £2-40
100mA £2-15	100mV d.e. £2-40
500mA £2-15	50V a.c. £2-20
	100V a.c. £2-20
	150V a.c. £2-20
	300V a.c. £2-20
	500V a.c. £2-20
	500mA a.c. £2-15
	1A a.c. £2-15
	5A a.c. £2-15
	10A a.c. £2-15
	20A a.c. £2-15
	30A a.c. £2-15
	VU meter £3-40

* MOVING IRON - ALL OTHERS MOVING COIL

Please add postage

"SEW" EDUCATIONAL METERS

Type ED.107. Size overall 100mm x 90mm x 108mm.

A new range of high quality moving coil instruments ideal for school experiments and other bench applications. 3" mirror scale. The easily accessible internal meter movement is demonstrate internal in the following ranges:

50μA £5-50	20V d.e. £4-85
100μA £5-10	50V d.e. £4-85
1mA £4-85	300V d.e. £4-85
50-0-50μA £5-10	Dual range
1-0-1mA £4-85	500mA/5A d.c. £5-10
1A d.o. £4-85	5A d.c. £4-85
5A d.o. £4-85	5V/60V d.c. £5-10
10V d.c. £4-85	

EDGEWISE METERS

PE.70 3 1/2x3 1/2in - 1 1/2x3 1/2in - 2 1/2in deep.

50μA £3-40	500μA £3-05
50-0-50μA £3-30	1mA £2-70
100μA £3-30	300V a.c. £2-70
100-0-100μA £3-20	VU meter £3-75
200μA £3-20	

MULTIMETERS for EVERY purpose!

ROUND SCALE TYPE PENCIL TESTER MODEL TS.68

Completely portable, simple to use pocket size tester. Ranges: 0/3/30/300V AC and DC at 2,000 ohm^s. Resistance 0-20K ohms. ONLY £1.97. P. & P. 13p.

SKYWOOD SW-500

50 K Ω /Volt. Mirror scale DC Volts 0.6/3/12/30/300/600. AC Volts 3/30/300/600. DC Current 20mA/6/60/600mA. Resistance 10K/100 K/1Meg/10 Meg. Decibels -20 to +57dB. £7.50. P. & P. 15p

TMK LAB TESTER.

100,000 O.P.V. 6 1/2in scale buzzer short circuit check. Sensitivity: 100,000 O.P.V. d.c. 5Volt a.c. D.c. volts: 5, 2.5, 10, 50, 250, 1,000V. A.c. volts: 3, 10, 50, 250, 500, 1,000V. D.c. current: 10, 100μA, 10, 100, 500mA, 2.5, 10A. Resistance: 1K, 10K, 100K, 10 meg, 100 meg. Decibels: -10 to +49dB. Plastic case with carrying handle. Size 7 1/2 x 9 1/2 in. £18.90. P. & P. 25p.

TE-20D RF SIGNAL GENERATOR

Accurate wide range signal generator covering 120Kc/s to 500Mc/s. 6 bands. Directly calibrated Variable R.F. attenuator, audio output. Xtal socket for calibration. 220/240V. A.C. Brand new with instructions. £15. Carr. 37 1/2p. Size 140 x 215 x 170 mm.

TMK MODEL TW-50K 46 ranges, mirror scale, 60K/Volts.

D.C. 5K/Volt A.C. D.C.: Volts -25, -25, 1.25, 2.5, 5, 10, 25, 50, 125, 500, 1000V. A.C. Volts: 1.5, 3, 5, 10, 25, 50, 125, 250, 500, 1000V. D.C. Current: 25, 50μA, 2.5, 5, 25, 50, 250, 500mA, 5, 10 amp. Resistance: 10K, 100K, 1 MEG, 10 MEG Ω . Decibels: -20 to +48.5db. £8.60. P. & P. 17 1/2p.

TO-3 PORTABLE OSCILLOSCOPE

3in tube. Y amp. Sensitivity 0.1V/pp/CM. Bandwidth 1.2 cps to 1.5MHz. Input imp. 2meg Ω 25PF X amp. sensitivity 0.9V -800KHz. Input imp. 2 meg Ω 20 pF. Time base, 5 ranges 10cps-300KHz. Synchronisation. Internal illuminated scale 140 x 215 x 330 mm. Weight 15 1/2lb 220/240V a.c. Supplied brand new with handbook. £40. Carr. 50p.

240° WIDE ANGLE 1mA METERS

MW1-6 60mm square £3.97. MW1-8 80mm square £4.97. P. & P. extra.

TRANSISTORISED L.C.R. A.C. MEASURING BRIDGE

A new portable bridge offering excellent range and accuracy at low cost. Ranges: R. 1 Ω -11 Ω meg Ω 6 Ranges: 1% to 100%. L.C. 1 μ H to 100 μ H HENRY'S 6 Ranges -2%, 0, 10pF -1110 mF d. 6 Ranges \pm 2%. TURNS RATIO 1:1/1000-1:11000. 6 Ranges \pm 1%. Bridge voltage at 1,000 cps. Operated from 9 volts, 100μA. Meter indication. Attractive 2 tone metal case. Size 7 1/2 x 3 1/2 in. £20. P. & P. 25p.

230/240V SMITH'S SYNCHRONOUS MOTORS

Built in gearbox. All brand new and boxed. 30RPH. CW: 2RPH CW: 20RPH CW: 2RPH ACW: 30RPH CW: 50p each. Post 12p

HIOKI MODEL 720X 20,000 O.P.V.

Overhead protection. 5/25/100/500/1000V D.C. 0/10/50/250/1000V A.C. 50μA/250mA, 20K/2 meg ohm. -5 to +62db. £4.97. P. & P. 15p.

Model S-100TR MULTIMETER TRANSISTOR TESTER

100,000 o.p.v. MIRROR SCALE OVERLOAD PROTECTION

0/12/6/3/12/30/120/600 V.D.C. 0/6/30/120/600 V.A.C. 0/12/600μA/12/300mA/12 AMP D.C. 0/10K/1 MEG/100 MEG. -20 to +45 db. 0.01 - 2 MFD. Transistor tester measures Alpha, Beta and Ico. Complete with batteries, instructions and leads. £18.50. P. & P. 25p.

MODEL 500.

30,000 O.P.V. with overload protection, mirror scale 0/1/5/2.5/10/25/100/250/500/1,000 V d.c. 0/2.5/10/25/100/250/500/1,000 V. a.c. 0/50μA/5/50/500 mA, 12 amp. d.e.g. 0/60K/6 meg/60 meg Ω . £8.71. Post paid.

TE-16A Transistorised Signal Generator, 5 ranges

400 KHz-30 MHz. An inexpensive instrument for the handyman. Operates on 9V battery. Wide, easy to read scale. 800 cps. R.F. modulation. 5 1/2 x 5 1/2 x 3 1/2. Complete with instructions and leads. £7.97. P. & P. 20p.

RUSSIAN 22 RANGE MULTIMETER

Model U437 10,000 o.p.v. A first class versatile instrument manufactured in U.S.S.R. to the highest standards. Ranges: 2.5/10/50/250/500/1000V d.c. 2.5/10/50/250/500/1000V a.c. d.c. current 100 mA / 1 / 10 / 100mA / A. Resistance 300 ohms / 30 / 300K Ω / 3M Ω . Complete with batteries, test leads, instructions and sturdy steel carrying case. OUR PRICE £5.97. P. & P. 25p.

FTC-401 TRANSISTOR TESTER

Full capabilities for measuring A, B and Ico, μ pa or μ pp. Equally adaptable for checking diodes. Supplied complete with instructions, battery and leads. £7.50. Post 20p.

HONEYWELL DIGITAL VOLTMETER VT. 100

Can be panel or bench mounted. Basic meter measures 1 volt d.c. but can be used to measure a wide range of a.c. and d.c. volt, current and ohms with optional plug-in cards. Accuracy: \pm 0.2, \pm 1 digit. Resolution: 1mV. No. of digits: 3 plus fourth overrange digit. Overrange: 100% (up to 1999). Input impedance: 1000 Meg ohm. Measuring cycle: 1 per second. Adjustment: Automatic zeroing, full scale adjustment against an internal reference voltage. Overload: to 100V d.c. Input: Fully floating (3 poles). Input power: 110-230V a.c. 50/60 cycles. Overall size: 5 1/2 in x 2 1/2 in x 8 3/16 in. AVAILABLE BRAND NEW AND FULLY GUARANTEED. £35. Carr. 50p

G. W. SMITH & CO (RADIO) LTD.

Also see next two pages

HI-FI EQUIPMENT

SAVE UP TO
33 1/3% OR MORE

SEND S.A.E. FOR
DISCOUNT PRICE LISTS
AND PACKAGE OFFERS!

RECORD DECKS

B.S.R.			
C123 Mono	£8-50		
C137*	£8-35		
MP60	£9-75		
MP60	£12-65	GOLDRING	
610	£14-07	GL92/2	£18-50
910	£31-25	GL99/2/P	£24-20
MP60/G800*	£12-95	GL72	£20-85
MP60/TPD1	£18-05	GL72/P	£27-50
MP60/TPD1/		GL75	£26-95
G800*	£19-50	GL75/P	£35-25
MP60/TPD2	£14-35	Plinth 69/72	£7-02
610 TPD1	£18-95	LI075	£3-60
510 TPD1	£17-95	LI072	£3-25
210 Package*	£8-75	C99	£18-25
HT70	£38-99	CL75/P	£56-85
HT70/G800*	£17-25	LI085	£20-50
HT70 Package	£20-35	C101	
HT70/Pack/			
G800*	£23-95		

GARRARD		PIONEER	
2025T/C*	£9-50	PL15C	£33-95
40B STEREO	£9-25	PLA35	£51-35
SP25 III	£10-25	PLA35	£82-65

SP25 Module/		THORENS	
M75-6	£23-50	TD125 II	£86-50
SL42B	£23-75	TD125 AB II	£99-95
AP76	£17-95	TX25	£6-95
AP76 Modul-/		TD160C	£56-95
M75-6	£33-80	TD150	£28-95
SL72B	£21-95	TD150A II	£35-95
SL93B	£23-25	TD150AB II	£39-95
401	£25-85	TD130 Plinth	£3-80
ZERO 100A	£38-95	TX11	£3-60
ZERO 100S	£36-95		

*Stereo cart. All others less cartridge.
Carriage 50p extra any model.

RECORD DECK PACKAGES

Decks supplied with cartridge ready wired in teak veneered plinth with cover.

Garrard 2025TC/STAHCD	£12-75
Garrard SP25 III/STAHCD	£15-85
Garrard SP25 III/M75-6	£18-50
Garrard SP25 III/M44-7	£19-75
Garrard SP25 III/M44-E	£20-95
Garrard SP25 III/M55E	£22-40
Garrard AP76/G800	£27-95
Garrard AP76/M75-6	£28-25
Garrard AP76/M55E	£30-50
Garrard AP76/M75E.I	£32-50
Garrard AP76/G800E	£30-75
Garrard AP76/M44E	£30-50
Garrard AP76/M75E.D	£38-95
BSR McDonald MP60/G800	£17-50
BSR McDonald MP60/M44-7	£18-50
BSR McDonald MP60/M44-E	£20-25
Golding (GL75)/G800	£34-50
Golding (GL75)/G800	£38-95
Golding (GL75)/G800E	£41-95

Carriage 50p any item


SINCLAIR EQUIPMENT



Project 60 Package offers 2 x Z30 amplifier, stereo 60 pre-amp. PZ5 power supply, £15-95. Carr 374p. Or with PZ6 power supply, £18-00. Carr. 371p. 2 x Z50 amplifier, stereo 60 pre-amp, PZ8 power supply, £20-25 Carr. 371p. Transformer for PZ8, £2-97 extra. Add to any of the above £4-45 for active filter unit and £13 for pair of Q16 speakers. New Project 605 £20-97. Carr. 37p. All Sinclair products in stock. IC12 £1-80. P. & P. 10p. 2,000 amplifier, £21-95. Carr. 374p. 3,000 Amplifier, £28-50. Carr. 371p. Neoteric amplifier, £45-95. Carr. 371p.

LATEST CATALOGUE

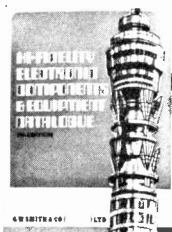Our 7th edition gives full details of a comprehensive range of HI-FI EQUIPMENT COMPONENTS, TEST EQUIPMENT and COMMUNICATIONS EQUIPMENT. FREE DISCOUNT COUPONS VALUE 50p. 320 pages, fully illustrated and detailing thousands of items at bargain prices.



SEND NOW ONLY **40p** P. & P. 10p




TELEPHONE F.2000 AM/FM STEREO TUNER AMPLIFIER



Probably the most popular budget Tuner/Amp. and now offered at a ridiculous low price. 5 watts r.m.s. per channel. Tape/Car phone inputs. APC/Built-in MPX. OUR PRICE £28-25. Carr. 50p.

SKYWOOD CX203 COMMUNICATION RECEIVER

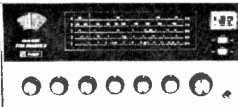

Solid state. Coverage on 5 bands 200-420 KHz and 0-55 to 30 MHz. Illuminated slide rule dial. Bandspread. Aerial tuning. BFO. AVC. ANL. 'S' meter. AM/CW/SSB. Integrated speaker and phone socket. Operation 220, 240V AC or 12V DC. Size 325 x 266 x 150mm. Complete with instructions and circuit. £30-00. Carr. 50p.

WHARFEDALE MID-RANGE HI-FI UNITS

As used in world famous system. 5" dia. Impedance 4/8 ohms. High flux ceramic magnet. 20 watts rms Brand new. £1-50. Carr. 37p.

★ TRANSISTORISED FM TUNER ★

6 TRANSISTOR HIGH QUALITY TUNER. SIZE ONLY 6x4x2 1/2in. 3 I.F. stages. Double tuned discriminating Amplifier output to feed most amplifiers. Operates on 9V battery. Coverage 88-108 MHz. Ready built ready to use. Fantastic value for money. £6-37p. P. & P. 124p. Stereo multiplex adaptors £4-97p.

TAPE CASSETTES. Top quality HI FI Low Noise in Philips Library cases. C60 3 for 75p 10 for £2-35 P. & P. C90 3 for £1-05 10 for £3-30 10p C120 3 for £1-35 10 for £4-20 extra Tape Head Cleaner 30p each

HA-10 STEREO HEADPHONE AMPLIFIER



All silicon 10 transistor amplifier operates from magnetic, ceramic or tuner inputs with twin stereo headphone outputs and separate volume controls for each channel. Operates from 9V battery. Inputs 5MU/100MU. Output 50mW. £5-97. P. & P. 15p.

TE-65 VALVE VOLT METER



High quality instrument with 28 ranges. D.c. volts 1.5-1,500V. A.c. volts 1.5-1,500V. Resistance up to 1,000 megohms. 220/240V a.c. operation. Complete with probe and instructions. £17-50. P. & P. 30p. Additional Probes available: R.F. £2.121. H.V. £2-50


SINCLAIR IC-12



List Price £2-98
OUR PRICE
£1-80 P. & P. 10p.

HOMER INTERCOMS

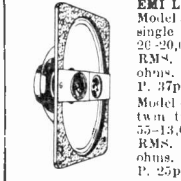Ideal for home, office, stores, factories, etc. Supplied complete with batteries, cable and free instructions.
2 Station £2-97. P. & P. 15p.
3 Station £5-25. P. & P. 15p.
4 Station £6-62. P. & P. 17p.



EMI LOUSPEAKERS
Model 450. 13" x 8" with single tweeter/crossover. 20-20,000Hz. 15 watt RMS. Available 8 or 15 ohms. £7-25 each. P. & P. 37p.
Model 450. 13" x 8" with twin tweeters/crossover. 55-13,000Hz. 8 watt RMS. Available 8 or 15 ohms. £3-62 each. P. & P. 25p.

TE 1018 DE-LUXE MONO HIGH IMPEDANCE DANCE HEADSET

Sensitive, soft earpads, adjustable headband, Magnetic impedance 2,600 ohms. £1-97. P. & P. 15p.




MP7 MIXER PREAMPLIFIER

3 microphone inputs each with individual gain controls enabling complete mixing facilities. Battery operated. 9 1/2" x 5" x 3". Inputs Mics: 3 x 3mV 50K, 2 x 3mV 500 ohms. Phone meg. 4mV 50K. Phone ceramic 100mV 1 meg. Output 520mV 100K. £8-97. P. & P. 20p.

1021 STEREO LISTENING STATION

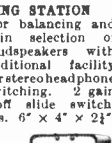For balancing and gain selection of loudspeakers with additional facility for stereo/headphone switching. 2 gain controls, speaker on-off slide switch, stereo headphone sockets. 6" x 4" x 2 1/2". £2-25. P. & P. 15p.



MCA 220 AUTOMATIC VOLTAGE STABILISER

Input 88-125 VAC. Output 120 VAC or 176-250V input output 240 VAC. 200 VA rating. £11-97. Carr. 50p.



230 VOLT A.C. 50 CYCLES RHEOSTATS

Brand New. 3 sets of changeover contacts at 5 amp rating. 50p each. P. & P. 10p (100 lots £40). Quantities available.

POWER RHEOSTATS

High quality ceramic construction. Windings embedded in vitreous enamel. Heavy duty brush wiring. Continuous rating. Wide range ext-stock Single hole fixing. In. dia. shafts. Bulk quantities available.
25 WATT. 10/25/50/100/250/500/1,000/1,500/2,500 or 5,000 ohms. 90p. P. & P. 74p.
50 WATT. 10/25/50/100/250/500/1,000/2,500 or 5,000 ohms. £1-15. P. & P. 74p.
100 WATT. 1/5/10/25/50/100/250/500/1,000 or 2,500 ohms. £1-85. P. & P. 74p.

"YAMABISHI" VARIABLE VOLTAGE TRANSFORMERS

Excellent quality. Low price. Immediate delivery

S-260 General Purpose Bench Mounting	
1A	£7-00
2-5A	£8-05
5A	£11-75
8A	£15-90
10A	£22-50
12A	£23-80
20A	£49-00
25A	£58-00
40A	£92-50

S-260B Panel Mounting
1A £7-00
2-5A £8-05
Please add postage

ALL MODELS INPUT 230 VOLTS, 50/60 CYCLES, OUTPUT VARIABLE 0-250 VOLTS
Special discounts for quantity

SPECIAL OFFER!

PHILIPS GA308 TRANSCRIPTION TURNTABLE

2 speeds 33 1/3 and 45 rpm. Lightweight tubular counter-balanced arm. Belt driven low speed synchronous motor. Viscous damped pick up lift/lower device. Complete with teak plinth and hinged cover. GA308 less cartridge (List £36-55). OUR PRICE £24-50. P. & P. 50p.
GA308 PI with GP400 stereo magnetic cartridge (List £47-65). OUR PRICE £29-95. P. & P. 50p.

U4312 MULTIMETER

Extremely sturdy instrument for general electrical use. 667 o.p.v. 0/31.5/7.5/30/60/150/300/600/900 VDC and 75mV. 0/31.5/7.5/30/60/150/300/600/900 VAC. 0/300uA/1.5/6/15/60/150/600mA/1.5/6 AMP. D.C. 0/1.5/6/15/60/150/600MA/1.5/6 AMP. A.C. 0/200 uA/3/30/300 uA. Accuracy DC 1%, AC 1.5%. Knife edge pointer, mirror scale. Complete with sturdy metal carrying case, leads and instructions. £9-50 plus P. & P. 25p.



LB3 TRANSISTOR TESTER

Tests ICO and B, PNP/NPN. Operates from 9V battery. Complete with all instructions. £3-95. P. & P. 20p.



UNR-30 RECEIVER

4 Bands covering 550KHz-30MHz. B.F.O. Built in Speaker 220/240V a.c. Brand new with instructions. £15-75. Carr. 37p.



LAFAYETTE HA-600 RECEIVER

General coverage 150-400KHz, 500KHz-30MHz. FET front end, 2 mech. filters, product detector, variable B.F.O., noise limiter, S Meter, Bandspread, RF Gain. 15in x 9 1/2in x 8 1/2in. 220/240V a.c. or 12V d.c. Brand new with instructions £50. Carr. 50p.



G.W.SMITH & CO. (RADIO) LTD

10 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-637 2232
27 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-636 3715
257/258 TOTTENHAM CT. RD. LONDON, W.1 Tel: 01-580 0670
3 LISLE STREET, LONDON, W.C.2 Tel: 01-437 8204
34 LISLE STREET, LONDON, W.C.2 Tel: 01-437 9155
311 EDGWARE ROAD, LONDON, W.2 Tel: 01-262 0387

CALLERS WELCOME MONDAY TO SATURDAY 9AM-6PM

All Mail Orders to - 11-12, Paddington Green, London, W.2 Tel: 01-262 6562

MULLARD BOOKS ON ELECTRONICS

FOR THE ENGINEER ENTHUSIAST AND STUDENT

APPLICATIONS OF INFRA-RED DETECTORS

152 pages, illustrated £2 00 + 15p P & P

POWER ENGINEERING USING THYRISTORS VOL. 1

TECHNIQUES OF THYRISTOR POWER CONTROL

240 pages, illustrated £1 50 + 15p P & P

TRANSISTOR AUDIO AND RADIO CIRCUITS - 2nd EDITION

288 pages, illustrated £1 80 + 15p P & P

ELECTRONIC COUNTING : CIRCUITS, TECHNIQUES, DEVICES

220 pages, illustrated £1 40 + 15p P & P

MAGNADUR MAGNETS D.C. MOTORS

52 pages, illustrated £0 75 + 15p P & P

COLOUR TELEVISION

46 pages, illustrated in Colour £0 87 + 10p P & P

MULLARD DATA BOOK

188 pages, illustrated £0 30 + 5p P & P

FIELD EFFECT TRANSISTORS

132 pages, illustrated £1 80 + 15p P & P

ALSO MULLARD MINI BOOKS

an Educational series, Principles of X-rays £0 20 (5p P & P), Principles of Electrostatics £0 20 (5p P & P), Thyristors £0 50 (8p P & P), Semiconductor Devices £0 37 (5p P & P), Magnetic Core Memories £0 40 (5p P & P).

AND SIMPLE MEASUREMENT SERIES

experiments for education and training.

Simple Transistor Measurements £0 25 (5p P & P)
Simple Oscilloscope Measurements £0 25 (5p P & P)
Simple Valve Measurements £0 25 (5p P & P)
A programmed Book on Semiconductor Devices £0 62 (10p P & P)
The Diagnostic X-ray Tube £0 50 (8p P & P)

HOW TO GET YOUR COPY

From your local bookseller or cash with order plus postage and packing from:

Selray Book Company Limited
60 Hayes Hill, Hayes, Bromley, Kent BR2 7HP
Or send for full list of Mullard titles from
Dept. C I H, Mullard Limited
New Road, Mitcham, Surrey CR4 4XY

BEDFORD ELECTRONICS

2 GROVE PLACE, BEDFORD

(continuation of Lurke Street)
Tel.: Bedford 51961

MULLARD C296 POLYESTER FILM CAPACITORS

400V: 0-001, 0-0015, 0-0022, 0-0033, 0-0047, 21p, 0-0068, 0-01, 0-015, 0-022, 0-033, 3p, 0-047, 0-068, 0-1, 4p, 0-15, 51p, 0-22, 7p, 0-33, 101p, 0-47, 12p, 160V: 0-01, 0-015, 0-022, 0-033, 0-047, 0-068, 3p, 0-1, 31p, 0-15, 4p, 0-22, 41p, 0-33, 51p, 0-47, 7p, 0-68, 10p, 1-0, 12p.

MULLARD C280 METALLISED FILM CAPACITORS 250V

0-01, 0-015, 0-022, 3p, 0-033, 0-047, 0-068, 31p, 0-1, 4p, 0-15, 0-22, 41p, 0-33, 6p, 0-47, 71p, 0-68, 10p, 1-0, 12p, 1-5, 18p, 2-2, 21p.

CERAMIC CAPACITORS 50V (Square plaquette body)

E12 Series 22pF-1,000pF, 11p, 0-0015-0-01, 2p, 0-015-0-047, 21p.

HIGH VOLTAGE CAPACITORS 1000V d.c. (300V a.c.)

0-001, 0-0022, 0-0033, 0-0047, 7p, 0-0068, 0-01, 0-022, 10p, 0-047, 0-1, 12p, 0-22, 20p, 0-47, 22p.

POLYSTYRENE CAPACITORS 125V, 21%

Values in pF: 5, 10, 15, 22, 33, 47, 56, 68, 100, 150, 220, 330, 470, 560, 680, 820, 1000, 31p.

SOLID TANTALUM RESIN DIPPED BEAD CAPACITORS

µF/V: 0-1/35, 0-22/35, 0-47/35, 1-0/35, 2-2/35, 4-7/35, 10/6-3, 10/16, 10/25, 22/16, 47/6-3, 100/3, 15p.

MULLARD 015/016/017 ELECTROLYTICS (Replaces C426/C437)

µF/V: 1/63, 1-5/63, 2-2/63, 3-3/63, 4-7/63, 6-8/63, 10/25, 10/63, 15/10, 15/63, 22/25, 22/63, 33/16, 33/40, 47/10, 68/16, 100/4, 100/10, 100/25, 150/16, 220/16, 5p, 47/63, 470/6-3, 51p, 68/63, 330/16, 9p, 100/63, 150/63, 680/16, 1500/6-3, 11p, 220/63, 470/40, 1000/16, 15p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6-3, 18p.

RESISTORS

Type	Tolerance	Range	Values	Price each
ISKRA 1/2W	5%	4R7-2M2	E24	1p
ISKRA 1/2W	10%	3M3-10M	E12	1p
MULLARD 1/3W	10%	1R-3R9	E12	1p
MULLARD 1/5W	5%	4R7-1M	E24	1p
METAL FILM 1W	5%	27R-1M	E12	11p
WIREFOUND 2-5W	10%	R22-R47	E12	9p
WIREFOUND 2-5W	5%	1R-270R	E12	7p
PRESETS 100R, 250R, 500R and Decades to 5M, 0-1W, 5p, 0-25W, 6p.				

Post and packing 10p on orders under £2; overseas at cost.
FULL CATALOGUE ON REQUEST.

NEW LIGHT SENSITIVE SWITCHES

TWO NEW LITE-IC'S - COMPLETE LIGHT SWITCHES CONSISTING OF PHOTODETECTOR + AMPLIFIER + TRIGGER + DRIVER - All in a single 4mm. dia. can.



NEW FEATURES: WIDER VOLTAGE SUPPLY RANGE - LITE-IC 2 11V to 20V LITE-IC 3 20V to 30V HIGHER OUTPUT CURRENT DRIVE - to 40mA.

APPLICATIONS INCLUDE: Relay, Triac or Logic Drive, Automatic Light Switching and Door Control, Beam/Break Detection - Burglar Alarm, Batch Counting and Code Reading.
PRICE ONLY 95p each with full operating instructions. 10 off for 80p each. Postage free in the U.K. P.O./CHEQUES made payable to ELBON and crossed (with order).
LITE-IC, ELBON, SUMMERFIELD, THE CRESCENT, WEST WITTERING, SUSSEX

P.E. 'GEMINI' STEREO AMPLIFIER

30 watts (R.M.S.) per Channel into 8 ohms!

Total Harmonic Distortion 0.02%!

Frequency Response (-3 dB) 20Hz-100kHz!

This high quality Stereo Amplifier for the Home Constructor was described in a series of articles in "Practical Electronics", from November 1970 to March 1971. It is now recognised as practically the ultimate in High Fidelity and is certainly equal to anything one can buy, no matter what the cost, but is well within the capabilities of the ambitious constructor.

WE CAN NOW SUPPLY A REPRINT OF THE ARTICLES IN BOOKLET FORM, PRICE 55p, PLUS 4p POSTAGE, WITH FREE COMPLETE COMPONENT PRICE LIST.

For free price list only, or a complete free specification, please send a foolscap size S.A.E.

ALL PARTS AVAILABLE SEPARATELY



ELECTRO SPARES
21 BROOKSIDE BAR
CHESTERFIELD, DERBYSHIRE

QUALITY • SERVICE • VALUE

ALMOST UNBELIEVABLE! Think of the year 1984 and what might be produced then—now get the fantastic **ASTRAD 17** and SEE for yourself that the incredible Russians have done it all NOW! It's the radio perfectionist's dream come true! **THIS ONE SUPERSEDES ALL EARLIER MODELS!** It will probably make your present radio seem like a "crystal set"! Complete with optional battery eliminator for both battery and mains use! We're almost giving them away at only £20.75—a mere fraction of even today's Russian miracle price! We challenge you to compare performance and value with that of £80 radios! *Test 7 days, we'll refund instantly if you are not astounded! Elegant black & chrome finish facia, set in fabulous Cabinet built case—constructed of fine Russian hardwood in beautiful Teak Veneer finish—prevents vibration, ensures purer & sweeter tone than ever! Volume controlled from a whisper to a roar that would fill a hall! Much wider band spread, for absolute "pin-point" station selection! Plus "MAGIC EYE" tuning level indicator for ultra perfect tuning sensitivity! Yes, the Russians have surpassed themselves, proving again their fantastic ability in the field of electronics and brilliantly reflecting their advanced micro-circuitry techniques in the field of spaceship and satellite communications. Yes, **EVERY WAVEBAND** instantly at your fingertips including Standard Long, Medium, Short and Ultra Short Waves to cover the four corners of the earth 24 hours a day including all normal transmissions. VHF, AM, FM, MW, LW, USW, plus local & new stations not yet operational, and messages from all over the world! Expensive TURRET TUNER side control waveband selection unit (as used on expensive T.V.'s). Every waveband clicks into position giving incredible ease of station tuning! Genuine push-pull output! ON/OFF volume and separate Treble and Bass tone controls for utter perfection of reproduction and tone! Press-button dial illumination! Take it anywhere—runs economically on standard batteries (obtainable everywhere) or direct through battery eliminator from 220/240V AC mains supply. Internal ferrite rod aerial plus built-in "rotatable" telescopic aerial extending to 39ins approx. It's also a fabulous **CAR RADIO**. Can also be used through extension amplifier, tape recorder or public address system. **SIZE** 14ins x 10ins x 4ins overall approx. Magnificently designed, made to give years of perfect service. (U.K. service facilities & spares available for years & years to come, if ever necessary!). With **WRITTEN GUARANTEE** manual with simple operating instructions & circuit diagram. **ONLY £20.75** (with mains/battery eliminator £1.48 extra). **BOX, POST, ETC. 50p.** ***BUT WAIT,** for only 55p extra you get the sensational **"COMPUTERISED" WORLD TUNING GUIDE** (it enables you to time, pinpoint & get transmissions the whole world over—even a child can do it in a flash—it even lets you know when to tune into the U.K. when abroad. **NO GUESSING! NO MESSING!**) **PLUS** Standard 'longlife' batteries **PLUS** ultra sensitive earphone for personal listening. (Sorry—We cannot change these new radios for any earlier model purchased.) **HURRY!** Send today or call at either store.

JUST ARRIVED! **THIS YEAR'S NEW *RUSSIAN MIRACLE! COMPUTERISED!**

BRAND NEW "SPACE AGE" model - SO FAR AHEAD OF ITS TIME IT WILL STILL BE MAKING MANY LOOK OUT OF DATE IN 1984!

THE FABULOUS ASTRAD 17

PORTABLE RADIO & COMMUNICATIONS RECEIVER

WORLD WIDE RECEPTION
THOUSANDS OF TRANSMISSIONS & STATIONS POUR IN FROM THE FOUR CORNERS OF THE EARTH!

"MAGIC EYE" tuning level indicator

***COMPARE ITS PERFORMANCE with £80 RADIOS!**

28 TRANSISTORS AND DIODES!

WAVEBANDS:
STANDARD LONG and MEDIUM
Plus 5 SHORT WAVEBANDS
Plus ULTRA SHORT WAVES
(V.H.F. AM, FM, MW, LW, USW.)

BATTERY MODEL £20.75 **BOX POST ETC. 50p**

MAINS/BATTERY ELIMINATOR £1.48 extra

FIRST TIME EVER!
***NOW AVAILABLE WITH fabulous "COMPUTERISED" WORLD TUNING GUIDE!**
NO MORE GUESSWORK—INSTANT DATA at your fingertips—enables you to TUNE IN A FLASH to transmissions the world over!

ANOTHER EAST EUROPEAN MIRACLE!

FANTASTIC 2-in-1 PERSONAL PORTABLE and CAR RADIO

NOW WORLD WIDE RECEPTION

IN YOUR CAR TOO! (RUNS OFF 12V. CAR BATTERY)

4 WAVEBAND VHF AM FM LONG & SHORT WAVEBANDS

FANTASTIC PRICE £9.95 **TRY AND MATCH IT FOR UNDER £35!**

Position it for CAR RADIO, results will justify! OR detach & use carry handle for PORTABLE with its own batteries!

FANTASTIC! Brand spanking new from East Europe—we bring you this incredible 2-in-1 Radio! First class makers—because of our crazy price, contract stipulates we must NOT mention name! Beautifully made 9 1/2 x 5 1/2 inches overall approx. Every up-to-date technological improvement. **15 SEMI-CONDUCTORS**, 9 Transistors, 5 Diodes and Stabiliser! **FOUR WAVEBANDS!** Yes, VHF model with AM/FM Long and Short wavebands! Will get stations

around the world, including Standard Long, Medium and Short Wave, also local and new stations not yet operational! Built-in internal ferrite aerial plus 5 section 26in. swivel telescopic aerial. On/off/volume and tone controls. Clear Station Selector Dial. Waveband selector! Equally wonderful in CAR or HOME! **TWO Tuning Dials** for flat or upright use as illustrated. **RUNS OFF 12 VOLT BATTERY!** (AS A PORTABLE it runs on standard batteries.) **PLUG IN 12 VOLT ADAPTOR JACK PROVIDED** and automatically cut out internal batteries, using car battery only! Don't you think it's miraculous? Span the Oceans and pull in hundreds of transmissions day and night, including short wave—even in car! **BUT WAIT—** simply remove Radio from car, "snap on" optional carry handle **AND YOU HAVE A DE-LUXE PORTABLE**, with additional upright tuning dial. **WRITTEN GUARANTEE.** Only £9.95 box, post 45p. *Sprung all metal matching detachable carry handle (as illus.) + batteries only 25p ex. if required. Match with sets costing £35 or more. Test 7 days—refund if not delighted. Order by post to Uxbridge Road address, or call at either store.

COMMERCIAL TRAVELLERS NOTE: Merchandising office at Holborn Store.

FIRST TIME EVER! *SAVE £14.48!

BRAND NEW AC/DC BATTERY/MAINS

Cassette TAPE RECORDER & PLAYER

FIRST CLASS MAKERS

With remote control microphone.

WE COULD CHARGE UP TO £26.97!
OUR PRICE £12.49 **POST ETC. 31p**

THE ONE STEP FORWARD EVERYONE HAS WAITED FOR! Now a superb de-luxe portable **BATTERY/MAINS** tape recorder and player—and Shopertunities bring it to you for only £12.49! Due to price we cannot name first-class makers—but rest assured you're getting one of the BEST! Expensive "PIANO KEYBOARD" CONTROL PANEL for latest MASTER SWITCH CONTROL and AUTOMATIC LEVEL CONTROL. No fiddling with awkward tape and reels, just "slap-in" a cassette and off you go! Takes 30, 60 or 90 minute standard cassette (tapes obtainable everywhere). Amazing performance ensures perfect tapings and superb reproduction! Remote control microphone. Rapid rewind! Fast forward! Beautiful tone from a whisper to a roar! Completely self contained—record anywhere, indoors or out! Runs on batteries AND 220/240V AC mains. Separate jacks for remote control microphone, etc. Size 9 1/2 in x 5 1/2 in approx. Designs can vary slightly. With carry handle. **WRITTEN G'TEE and Instructions.** **ONLY £12.49, post etc., 31p.** *Refund if you don't agree we could charge up to £26.97! **BONUS OFFER** (one per customer)—Cassette tape, set of standard batteries AND microphone stand 50p ex. if req. **ALSO** super de-luxe model fitted with VHF, AM/FM Radio **ONLY £23.75, carr. 35p** (standard batteries and cassette tape 25p extra).

Send quickly to Uxbridge Rd. for either model and Test 7 days. Refund if not delighted. Or call.

SHOPERTUNITIES LTD.

Dept. PE/23, 164 UXBRIDGE RD. (facing Shepherds Bush Green), LONDON W12 8AQ. (Thurs. 1, Fri. 7). Also at 37/39 HIGH HOLBORN (opposite Chancery Lane), LONDON, W.C.1. (Thurs. 7 p.m.) **BOTH STORES OPEN FROM MONDAY TO SATURDAY FROM 9 A.M. UNTIL 6 P.M.**

PRACTICAL ELECTRONICS
"SCORPIO"
ELECTRONIC IGNITION
SYSTEM



This Capacitor-Discharge Electronic Ignition system was described in the November and December issues of Practical Electronics. It is suitable for incorporating in any 12V ignition system in cars, boats, go-karts, etc., of either pos. or neg. earth and up to six cylinders. The original coil, plugs, points and contact-breaker capacitor fitted in the vehicle are used. No extra or special components are required. Helps to promote easier starting (even under sub-zero conditions), improved acceleration, better high-speed performance, quicker engine warm-up and improved fuel economy. Eliminates excessive contact-breaker point burning and the need to adjust point and spark-plug gaps with precision. Construction of the unit can easily be completed in an evening and installation should take no longer than half an hour. A complete complement of components is supplied with each kit together with ready-drilled roller-tinned professional quality fibre-glass printed-circuit board, custom-wound transformer and fully-machined die-cast case. All components are available separately. Case size 7½in x 4½in x 2in approx. Complete assembly and wiring manual 25p, refundable on purchase of kit. Price: £10.50 plus 50p P. & P.

DABAR LIGHTING EFFECTS

NEW! NEW! NEW! NEW! NEW! NEW!



SINGLE CHANNEL
SOUND TO
LIGHT UNIT
STL/1

Single channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. Switchable for response to High, Mid and Low frequency audio input signals, selected by fascia control. D.J. Pulse-Flash push button fitted to fascia for manual flashing of lamp load. Neon load indicator fitted. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections via Cinch printed circuit connector. Maximum Load 1KW at 250V 50Hz. R.F.I. filtered. Price: £13 each post free U.K.

S.A.E. All Enquiries please



THREE CHANNEL
SOUND TO
LIGHT UNIT
STL/3

Three channel "Sound to Light" unit with slider fader controls for audio trigger level and background load dimmer. An attractive unit with independent control of High, Mid and Low frequency audio trigger levels. Slider fader background or dimmer controls on each channel. D.J. Pulse-Flash push buttons on each channel together with neon load indicators. Constructed on glassfibre printed circuit material with attractive black anodised fascia panel. Input and load connections at rear so unit is ideally suited for mounting into disco-console. Maximum Load 1.5kW per channel at 250V 50Hz. R.F.I. filters incorporated. Price: £38.50 each post free U.K.

Trade enquiries Welcome

PSYCHEDELIC LIGHTING
UNIT Mk. 3



This unit represents a natural progression from our phenomenally successful Mk. 1 and 2 Units. As before the drive voltage is derived directly from the amplifier output or across the speakers. The unit converts the audio frequency signals into a three-coloured light display; the colour depending on the frequency of the signal and the intensity on the loudness of the audio source. The unit is constructed on professional fibre-glass printed-circuit board material and uses latest full-wave triac circuitry. There is a master-level control, together with independent sensitivity controls for each channel. The original minimum ambient light level controls have been redesigned permitting their use as faders; allowing dimming from max. to zero at the turn of a knob. R.F.I. suppression is now incorporated as standard as well as provision for D.J. "Pulse-Flash" controls. The choice of two inputs enables operation from both high and low power amplifiers. Max. power 1.5kW per channel at 240V a.c. Complete assembly built and tested. Size 9in x 7in x 3in. Price £25 each, paid.

DABAR ELECTRONIC PRODUCTS
98a Lichfield Street, Walsall
Staffs. WS1 1UZ
TELEPHONE: WALSALL 34365
TELEGRAMS: DABELEC Walsall Staffs.

FM TUNER THOUSANDS
NELSON-JONES NOW IN USE
Reduced prices

Approved parts of this outstanding design (W.W. April 1971). Featuring 0.75µV sensitivity. Mosfet front end. Ceramic I.F. strip. Triple gang tuning, ½V r.m.s. output level, suitable for phase locked decoder, as below. Designer's own P.C.B. NEW Solid State Tuning Indicator and Dial-Chassis Kit. Tuner parts with box. Less than £11.50. S.A.E. please for lists. High Performance Decoder also available. NEW IC Stabilised PSU. SC, overload protected, low ripple. £3.55 p.p. 19p.

ELECTRONIC CALCULATOR
MODEL BC806 Pocket Size

MOS LSI Calculating Chip with 8 Digit Led Display, Overflow and Negative Number Indicators. Leading Zero Suppression.

Full 4 Function—will perform Addition, Subtraction, Multiplication and Division including Chain or Mixed Multiplication or Division as well as true credit balance. Constant Key: Fixed or Floating decimal point. Calculator dimensions: 6in. x 3½in. x 1½in. Weight: 8oz. THE BC806 IS FULLY ASSEMBLED, TESTED AND GUARANTEED FOR 12 MONTHS, AND IS SUPPLIED COMPLETE WITH BATTERIES AND FULL OPERATING INSTRUCTIONS.

PRICE ONLY £46.25 (POST FREE)

A.C./D.C. Adaptor available shortly. Leather Carrying case supplied FREE with calculator.

LIGHT EMITTING DIODES (Red)

Improved Type panel or PCB mounting with free mounting clip—clear or black. Order LED1A. Please add postage. Monsanto miniature PCB mounting with radial leads. Order LED2. Please add postage.

NOW ONLY 35p each with connection data.

RESISTORS. ¼W 5% Low Noise Carbon Film, 10 ohms—4.7M E12. 1-9 1p, 10-99 0.9p each. Please add postage.

INTEGREX LIMITED, DEPT. P.E.

P.O. BOX 45, DERBY DE1 1TW. Tel. 0283 89 3580

PARKERS SHEET
METAL FOLDING
MACHINES
HEAVY VICE
MODELS



With Bevelled Former Bars Carr. free

- No. 1. Capacity 18 gauge mild steel x 36in. wide ... £17
 - No. 2. Capacity 18 gauge mild steel x 24in. wide ... £12
 - No. 3. Capacity 16 gauge mild steel x 18in. wide ... £12
- Also new bench models. Capacities 36in. x 18 gauge £35. 24in. x 16 gauge £32. Carriage free.

End folding attachments for radio chassis. Tray and Box making for 36in. model, 27½p per ft. Other models 17½p. The two smaller models will form flanges. As supplied to Government Departments, Universities, Hospitals.

One year's guarantee. Money refunded if not satisfied. Send for details.

A. B. PARKER, Folding Machine Works, Upper George St., Heckmondwike, Yorks. Heckmondwike 3997

AMAZING MINI-DRILL



Indispensable for precision drilling, grinding, polishing, etching, gouging, shaping. Precision power for the enthusiast. Shockproof. Completely portable power from 4½ volt external battery. So much more scope with MINI-DRILL. Super Kit (extra power, interchangeable chuck) £4.95 p.p. 13p.

De Luxe Professional Kit with 17 tools £7.65 p.p. 23p. Money Ref. Guarantee.

FOR PRECISION MODEL WORK

- ABRASIVE
- SPEAR DRILL
- BURR
- MOP
- BRUSH

+ 6 TOOLS

ONLY £2 R & P. 10p

MERLIN SUPPLY CO

Dept. PE12D, Nailsea, Bristol BS19 2LP

Eliminators



9 volt @ 20mA (PP3)	£1.25
6 volt @ 50mA	£1.50
9 volt @ 50mA	£1.50
6 + 9 volt, 50mA	£2.50
9 + 9 volt, 50mA	£2.50
7½ volt for cassette recorders	£2.00
6, 7½ or 9 volt	£3.00
3, 4½, 6, 7½, 9, 12 @ 500mA	£3.99
Car Battery Converter fully stabilised to provide 6, 7½ or 9 volts (illustrated)	£4.99
(p. & p. 15p. on all types)	

DIL Sockets




14 and 16 pin

16p

(including ZIG-ZAG)

THE TEXAN

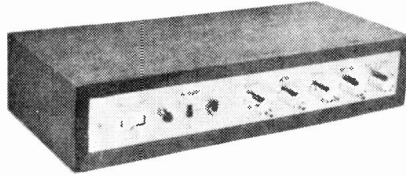

Complete Kit (inc. Teak Case) **£28.50** PGP 45p

20 Watts per channel integrated stereo amplifier developed by engineers of 'Texas Instruments Ltd.' This designer approved kit, has a state-of-the-art specification, including distortion of only 0.09% at 20 Watts into 8 ohms and a bandwidth of 5 - 35,000 at -3db. The semiconductor complement of this superb kit includes no less than 6 integrated circuits, 10 Silicon transistors, 4 rectifiers and 2 zeners. Controls include bass, treble, volume, balance, on/off, 'on' indicator, headphone sockets, scratch filter, rumble filter; inputs for magnetic phono; tuner, aux or tape, tape head etc.; input, selector, mono/stereo switch. The construction of this kit was featured in 'Practical Wireless' May - Aug. 1972.

Veroboard

	Copperclad	Plain
0 1"	0.15"	0.15"
2½" x 1"	6p	6p
2½" x 3½"	20p	16p (9)
2½" x 5"	24p	21p (7)
3½" x 3½"	24p	21p (8)
3½" x 5"	27p	27p (10)
17" x 2½"	67p	50p
17" x 3½"	90p	70p
17" x 5"	-	75p

Spot-face Cutter 36p
Pin Insertion Tool 47p
Terminal Pins 18p per pack of 36

Aluminium Boxes

Including baseplate and screws

No.	L.	W.	D.	Price	p. & p.
(7)	2½"	5"	1½"	35p	8p
(8)	4"	4"	1½"	35p	8p
(9)	4"	2½"	1½"	35p	8p
(10)	4"	5½"	1½"	40p	8p
11	4"	5½"	2"	35p	8p
12	3"	2"	1"	32p	9p
13	6"	4"	2"	50p	10p
14	7"	5"	2½"	58p	12p
15	8"	6"	3"	75p	18p
16	10"	7"	3"	85p	20p

Resistors

½ watt 5% Carbon Film - low noise Hi-Stabs
All E24 values 1p. each plus p. & p. 7p. for up to 50 Resistors and a further 2p for each additional 50. Deduct 33 1/3% for 100 of one type or 25% for mixed orders over £1 in value.

1 watt 10% Carbon Composition 3p. each
2 watt 10% Carbon Composition 6p. each
2½ W 5% Wire wound 9p. each
5 W Wire wound 9p. each
10 W Wire wound 10p. each
plus p. & p. 7p. for up to 25 resistors plus 1p. for each additional 25.

Semiconductors

AC107	25p	AI-239	30p	BF197	15p	2N1304	22p	AA120	9p
AC126	17p	BC107	10p	BU105	£2	2N1893	30p	AA129	9p
AC127	15p	BC108	10p	MPF102	40p	2N2926	10p	BA100	15p
AC128	15p	BC109	10p	MPF103	37p	2N3053	23p	BA154	13p
AC176	20p	BC147	10p	MPF104	37p	2N3055	49p	BA155	14p
AC187	25p	BC148	10p	MPF105	40p	2N3702	12p	BA156	15p
AC187K	25p	BC149	10p	MPF106	45p	2N3704	17p	OA47	10p
AC188	25p	BC157	12p	OC28	40p	2N3819	35p	OA79	9p
AC188K	25p	BC158	10p	OC35	40p	IN914	4	OA81	7p
AD140	40p	BC159	12p	OC44	15p	IN4148	6p	OA90	7p
AD149	40p	BC169	15p	OC45	15p	IN4001	6p	OA91	7p
AD161	40p	BF180	25p	OC71	11p	IN4002	7p	OA200	10p
AD162	60p	BF181	30p	OC72	17p	IN4003	8p	OA202	10p
AF114	18p	BF184	25p	OC170	23p	IN4004	8p	SL403D	£1.50
AF115	18p	BF185	25p	OC171	30p	IN4005	10p	µA709C	45p
AF116	18p	BF194	15p	2N697	18p	IN4006	12p	µA710	45p
AF117	18p	BF195	15p	2N706	12p	IN4007	15p	µA741C	50p
AF139	28p	BF196	15p	2N708	15p	AA119	9p	µA723C	£1.05

Thermistors



RS3	£1.32
VA1005	15p
VA1026	13p
VA1033	13p
CZ1	15p
CZ4	13p
CZ13A	13p
GL16	£1.00
GL23	£1.00
A15B	75p

Heat Sinks

TOS	TO18	5p	TO66	14p
			TO3	15p
			Power Tab	13p
			DIP10/2 for SL403D	15p
			10D	50p

CHROMASONIC electronics

Capacitors

Mylar - 100V

Value	2p	3p
1000pf	0.04µF	3p
2000pf	0.05µF	3p
5000pf	0.068µF	4p
0.01µF	1.0µF	4p
0.02µF	2.0µF	5p

Polystyrene - 160V

10pf to 10,000pf all 3p. each in multiples of 10, 15, 22, 33, 47 & 68.

Mullard C280 - 250V

0.01µF	3p	0.22µF	5p
0.015µF	3p	0.33µF	6½p
0.022µF	3p	0.47µF	8p
0.033µF	3p	0.68µF	11p
0.047µF	3p	1µF	13p
0.068µF	3½p	1.5µF	20p
0.1µF	4p	2.2µF	24p
0.15µF	4p		


Mullard C281 - 400V

0.01µF	4½p	0.1µF	7p
0.015µF	4½p	0.15µF	8p
0.022µF	4½p	0.22µF	10p
0.033µF	5½p	0.33µF	14p
0.047µF	6p	0.47µF	15p
0.068µF	6p		

Mullard C426, 015

G016 all 6p each

Voltage	10	16	25	40	63			
2.5 4 6.4	10	16	25	40	64			
Capacity µF	22	15	10	6.8	1			
	47	68	22	47	2.2			
	100	150	47	100	4.7			
	220	100	10	10				
		150						
		1.6		1	0.64			
	40	32	25	16	10	6.4	2.5	
	80	64	50	32	20	12.5	8	5
	160	125	100	64	40	25	16	10
	320	250	200	125	80	50	32	20
	500	400	320	200	125	80	50	32

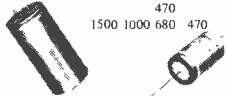

We also hold Mullard C333 ceramics 1 8pf 330pf 63V. 5p
Silvered Mica 1½, 500V, 2.2pf 820pf 7p
Feedthrough ceramic 1000pf, 350V. 5p
Disc ceramics, monolithic ceramic, high voltage types: tantalums etc.

Mullard C431

10	16	25	40	64	
2000	1250	800	500	320	33p
3200	2000	1250	800	500	40p
5000	3200	2000	1250	800	50p
10000	6400	4000	2500	1600	74p
16000	10000	6400	4000	2500	93p

HT Electrolytics

1, 2, 4; 8µF	450V	14p
16µF	450V	15p
32µF	450V	20p
50µF	350V	20p

TV & Radio Types

8 + 8µF, 450 V.W	18p	32 + 32µF, 350 V.W	25p
8 + 16µF, 450 V.W	20p	32 + 32µF, 450 V.W	43p
16 + 16µF, 450 V.W	25p	50 + 50µF, 350 V.W	35p
16 + 100 + 100 + 300µF, 275 V.W.			£1.23
32 + 100 + 125 + 200µF, 275 V.W.			£1.23
32 + 100 + 200 + 200µF, 300 V.W.			£1.23
100 + 100 + 100 + 150 + 150µF, 320 V.W.			£1.66
100 + 100 + 200 + 300µF, 275 V.W.			£1.23
60+100+200µF, 300 V.W	93p		
100+200+200µF, 300 V.W	£1		
100+200µF, 275 V.W	75p		
100+400µF, 275 V.W	£1.15		
200µF, 275 V.W.	50p	300+300µF, 300 V.W	£1.90

MAIL ORDERS. Where no p. & p. charge is shown, a minimum of 7p. applies. P. & P. on overseas orders is charged at cost.
ADDRESS: TO: Mail Order Dept.,
56, Fortis Green Road, London, N10 3HN.
TELEPHONE 01-883 3705

Potentiometers



5KΩ	50KΩ	500KΩ
10KΩ	100KΩ	1MΩ
25KΩ	250KΩ	2MΩ
log or lin less switch		12p
log or lin with switch		24p
dual less switch		40p
dual with switch 10K, 100K & 1M log only		52p
10K log + 10K antilog less switch		40p

Slider Pots

Single	Dual	
10K	10 + 10K	log or lin
25K	25 + 25K	
50K	50 + 50K	
100K	100 + 100K	
30p	50p	
Knobs	10p.	

Presets



Vertical or Horizontal	0.1 watt 5K	0.25 watt 7p			
	1K	10K	100K	1M	
	250	2.5K	25K	250K	2.5M
	500	5K	50K	500K	5M

RTVC THE

THE FABULOUSLY SUCCESSFUL VISCOUNT III AUDIO £52 complete

14 + 14 watts r.m.s. 40Hz to 40kHz \pm 3dB. Total distortion at 10 watts at 1kHz — 0.1%.

This is real value for money! We have designed 2 systems and the heart of them all is the Viscount III amplifier. A unit of great eye appeal with teak finished cabinet. FET's (Field effect transistors) are incorporated on the input stages, just like top priced units. FET's give you more of the signal you want and almost none of the hiss you don't. Both units have output sockets for headphones and tape recorder. Filters and tone controls give a wide range of bass and treble adjustment.

For both systems we have chosen the famous Garrard SP25 Mk. III deck, with fitted magnetic cartridge, which comes complete with simulated teak plinth and tint acrylic cover.

The exclusive Duo loudspeaker systems are incomparable for quality within their price range. Large speakers in extremely substantial cabinets. There's a choice of the Duo II's for the smaller room or the big Duo III's for real bass response.

SPEAKERS

Duo Type II Size approx. 17in. \times 10 $\frac{1}{2}$ in. \times 6 $\frac{1}{2}$ in. Drive unit 13in. \times 8in. with parasitic tweeter. Max power 10 watts, ohms. Simulated Teak cabinet. £14 pair + £3 p & p.

Duo Type III Size approx. 23 $\frac{1}{2}$ in. \times 11 $\frac{1}{2}$ in. \times 9 $\frac{1}{2}$ in. Drive unit 13 $\frac{1}{2}$ in. \times 8 $\frac{1}{2}$ in. with H.F. speaker. Max power 20 watts at 3 ohms. Freq. range 20Hz to 20kHz. Teak veneer cabinet. £32 pair + £3 p & p.

SPECIFICATION R101

14 watts per channel into 3 to 4 ohms (suitable 3-15 ohms). Total distortion @ 10W @ 1kHz 0.1%. P.U.1. (for ceramic cartridges) 150mV into 3 Meg. P.U.2. (for magnetic cartridges) 4mV @ 1kHz into 47K equalised within \pm 1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power.) Tape out facilities: headphone socket, power out 250mW per channel. Tone controls and filter characteristics. Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. Signal-to-noise ratio: (all controls at max) — P.U.1. and radio — 65dB, P.U.2 — 58dB. Cross talk better than -35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 $\frac{1}{2}$ in. \times 9in. \times 3 $\frac{1}{2}$ in. Send S.A.E. for fully illustrated brochure. 12 MONTHS' WRITTEN GUARANTEE. British made. S.A.E. for illustrated leaflet.

PRICES: SYSTEM 1

Viscount III R 101 amplifier	£22.00 + 90p p&p
2 \times Duo Type II speakers	£14.00 + £2 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
Total	£59.00

Available complete for only **£52**
+ £3.50 p & p

PRICES: SYSTEM 2

Viscount R 101 amplifier	£22.00 + 90p p&p
2 \times Duo Type III speakers	£32.00 + £3 p&p
Garrard SP25 Mk. III with MAG. cartridge plinth and cover	£23.00 + £1.50 p&p
Total	£77.00

Available complete for **£69** + £4 p & p

— ONLY FROM US



MUSIC MAKERS

UNISOUND FOR THE NEW SOUND

AT £25

The whole system is complete including superb cabinets in simulated teak—just simply screw together the components and you save pounds!

Amplifier is based on the famous Mullard Unilex system. Garrard 2025TC turntable complete with stereo ceramic cartridge, teak simulated plinth and tinted acrylic cover. Plus the big 13in. x 8in. EMI Twin-cone speakers ready for mounting in their elegant cabinets, which simply need screwing and gluing together. All glue and screws supplied.

Easy to follow step-by-step instructions guide you quickly and effortlessly to taking the wraps off truly realistic stereo sound.


£25 complete plus £2.80 p. & p. Diamond Stylus £1.25 extra.

Power output: 4 watts per channel into 8 ohms. Inputs: 120 mV (for ceramic cartridges). Stereo headphones with adaptor £4.00.

UNISOUND MODULES ONLY £6.95

If you prefer, you can buy the three modules—pre-amplifier power supply/dual power amplifier, and control panel—by themselves for only £6.95. P. & P. 50p extra.

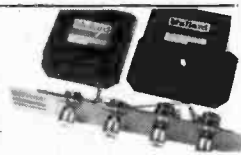No soldering, just simply screw together with screwdriver supplied. Their overall specification is the same as shown for the complete Unisound console, using the high efficient I.C. monolithic power chips to ensure very low distortion at all power levels, correct operation in all ambient temperatures, full power over the audio spectrum.



AN|R|T|V|C|EXCLUSIVE DESIGN

S.A.E. for illustrated leaflet

A 'NATURAL' ONLY FROM R T V C

THE TOURIST PB CAR RADIO KIT

Apart from the output stage, which is an integrated circuit, the only other electronic components that need soldering are some capacitors, resistors, etc. The kit includes a pre-built RF tuner unit, and fully modulated IF stages which are pre-aligned before despatch. As well as electronic components, this kit also contains 2 diamond-spun aluminium knobs, elegant matching front panel, dial, washers, screws and wire.

The Tourist PB is suitable for 12 volt working on both negative and positive earth vehicles. It covers the full medium and long wave bands. Four push-buttons for medium wave, one for long wave. It is permeability tuned and sturdily constructed. Output is a full 2.5 watts into an 8 ohm speaker. But the Tourist PB will operate into any loud-speaker from 8 to 15 ohms. Power consumption is less than 1 amp.

The Tourist PB can be mounted in any standard size dash panel and it has an illuminated tuning scale for easy reading at night. Chassis size is: 7in wide, 2in. high and 4½ in. deep (excluding front panel, etc.).

★ Circuit diagram and comprehensive instructions 50p, free with parts.

★ Fully retractable lockable car aerial £1.25 post paid.

PRICE ONLY £7 + p & p 50p

8 ohm speaker with baffle and fixing strips £1.50 + 25p p & p, post free if brought with the kit. Send for illustrated leaflet

If you can solder on printed circuit board, you can build this push-button car radio kit. It's simple—just follow the step-by-step instructions.

ONLY
£7.00



RELIANT MK.IV

★ 5 Electronically Mixed Inputs. ★ 3 Individual Mixing Controls. ★ Separate bass and treble controls common to all 5 inputs. ★ Mixer employing F.E.T. (Field Effect Transistor). ★ Solid State Circuitry. ★ Attractive Styling. ★ Sides finished in solid teak.

INPUTS:—1. Crystal Mic. or Guitar 9mV. 2. Moving coil Mic. or Guitar 8mV. Inputs 3, 4 & 5 are suitable for a wide range of medium output equipment (Gram., Tuner, Monitor, Organ, etc.). All 250mV sensitivity.

CONTROLS:—3 Volume controls. Bass control range: 13dB @ 60Hz. Treble control range: ± 12dB @ 15KHz. Separate ON/OFF Switch. Neon indicator. **POWER OUTPUT:**—12 Watts R.M.S. into 3 to 4 ohms speaker. **SIGNAL NOISE:**—Better than —60dB on inputs 3, 4 and 5 & —50dB on 1 & 2. **SUPPLY:**—220-250 A.C. Mains. **SIZE:**—12½ in. x 6 in. x 3½ in.

£10.50
plus p & p 60p

VISIT OUR SHOWROOMS

R T V C

Radio and TV Components (Acton) Ltd.
21D High St., Acton, London W3 6NG
323 Edgware Road, London, W.2

Mail orders to Acton · Terms C.W.O. · All enquiries S.A.E.
Goods not dispatched outside U.K.

Go Hi-Fi yourself!

New Goodmans Din 20 loudspeaker kit specially designed to give the D.I.Y. enthusiast excellent hi-fi reproduction at moderate cost

This system has been thoroughly tested to Goodmans high standards. It will provide extremely satisfactory listening levels from amplifiers rated at 10 watts (per channel, in the case of stereo equipment) but it may also be operated from amplifiers of higher power.

The kit contains all parts needed to complete the system (except timber and other material for the cabinet itself) and has detailed, illustrated assembly instructions.

Contents

- 1 Bass unit 204mm (8in) diameter.
- 1 Dome HF radiator 25.4mm (1in) diameter.
- 1 Port tube.
- 1 Crossover panel with colour coded leads.
- 1 Terminal board.
- 1 Foam gasket.
- 1 Input lead complete with DIN plug and spade terminals.
- Acoustic wadding foam pad.
- Fixing screws and hardware.
- Cabinet template (on bottom of box).

Specification

20 watts DIN, 4 ohms impedance, 8in bass unit, dome HF radiator, crossover frequency 4,000Hz.

For further details and the name of your Goodmans dealer, send the coupon now



Goodmans
Sound reasoning.

Downley Road, Havant, Hampshire.
Please send me free leaflets on Constructors' equipment and the name of my Goodmans dealer.

THORN A member of the Thorn Group
Name

Address

PE12

EXCLUSIVE OFFER ONLY FROM GLOBAL



GARRARD 401
SME 3009/3012

**PLINTH
SYSTEM**

£12.50

PLUS £1 P & P

This superbly styled and sprung plinth system has been designed for us by one of Britain's leading Hi-Fi manufacturers. Finished in teak with black border, smoke tinted dust cover. Lid stays on when deck is in play. The system is already cut to just drop the Garrard 401 into. Enough space is provided for either the SME 3009 or SME 3012 pick-up arm to be cut and mounted. All this comes to you at the amazingly low price of £12.50 plus £1 carr.

GLOBAL AUDIO DISCOUNT WAREHOUSES


Dept. PE1 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

2 miles from EURE CROSS, TUSTON & ST. PARCELS

MAIL ORDERS: Order with Cheque, Bank Draft, Giro or Cash by Registered Money Order. Bank Draft, Giro or Cash by Registered Money Order. Please note that orders can only be accepted together with cheque cards (not Barclay Card).

A.M.C. ELECTRONICS LTD.

"GEMINI" FM STEREO TUNER

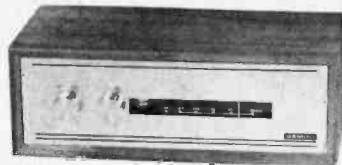


All components to build this outstanding phase lock easily aligned tuner as described in April/May/June P.E. We are offering an optional chassis and solid wood sleeve in ready to assemble form. S.A.E. for details and itemised prices. Complete kit £33.90.

SCORPIO ELECTRONIC IGNITION

Complete kit with comprehensive construction and fault finding data. £11. Post paid. Data 10p. Itemised prices, S.A.E. please.

**AMCEL, MAIL ORDER, 160 DRAKE ST.,
ROCHDALE Tel. 0706-46234**

LINDAIR (ELECTRO-TECH) LTD

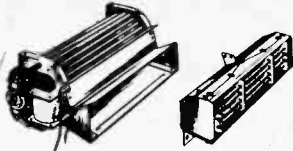

TANGENTIAL HEATER

Silently driven by a shaded pole Mynalex motor. Compact, powerful, and quiet running with aluminium impeller (outlet $5\frac{1}{2} \times 11$). Main voltage. PLUS matching heater unit with spiral element. May be switched for 500 or 1,000 watts. **PRICE ONLY P. & P. 40p**

£1.60

SYNCHRONOUS AUTO-RESET PROCESS TIMER

By LONDEX LIMITED

Type IMF Mk. 2. Brand New and Boxed. These well known timers are already in world-wide use and are perfect for Industrial Electronic Timing. Research and for all machine control timing problems. Repetitive accuracy better than 0.5% of full scale setting. Two or more can be interconnected to give control of a series of processes, 230/250v. 50Hz, also available 60Hz. 15 minutes full scale, 15 sec. per division. Driven by self-starting sync. motor. Contact rating 5 amp at 250v. a.c. Incorporates solenoid operated clutch. Also, lever actuated micro switches. Normal price probably in excess of £10. Complete with multi-pin connector as illustrated.

OUR PRICE ONLY

£6.50

SEEN THIS ?

This is the only way we could illustrate this fabulous item.

NORPLEX the famous American fibre-glass copper-clad laminate. Finest quality with Woven Glass base of Epoxy-resin. Excellent mech. and elec. conductive properties. Heat Resistant. Ideal for P.C.s, etc. **THIS IS A SPECIAL PURCHASE AND ONLY AVAILABLE WHILE STOCKS LAST.** Sizes: 12" x 12"; 24" x 12"; 24" x 24"; FULL SHEET 43" x 37" (11 sq. ft.). Single sided copper with thicknesses of $\frac{1}{16}$ ", $\frac{3}{16}$ ", $\frac{1}{8}$ ", $\frac{3}{16}$ " $\frac{1}{16}$ ", also Double sided $\frac{1}{16}$ ", $\frac{1}{16}$ ".

PRICE ONLY £1 per sq. ft. 25 per full sheet. P. & P. 25p up to 4 sq. ft. Over 4 sq. ft. (cut sizes only) Post FREE. Full sheets post by rail G.B. only £1 one or more sheets.

MICRO-LITES

Wonderful engineering—micro miniature incandescent lamp small enough to pass through the eye of a needle! 1,000's of uses. Will operate from the output of a transistor. Rating: 1.5v, 10-15ma. Size 4.4 x 1.4mm. dia. Leads 22mm. These fantastic lamps have a life expectancy of 1,000 hrs.

OUR PRICE

£3.25

per doz. Free p. & p.

NEW AND UNUSED


Postal or carriage charges are for Great Britain only. We welcome orders from established companies, educational depts., etc. All orders under £2.50, cash with order please.

FURTHER BULK PURCHASE SILVANA MAGNETIC SWITCH

HOW COMPLETE WITH REFERENCE MAGNET! A magnificently activated switch. Vacuum sealed in a glass envelope. Silver contacts normally closed, rated 3 amp at 120v. 1 1/2 amp at 240v. Size (approx.) 1 7/16" long 1" dia. Ideal for Burglar Alarms, Security systems, etc., and wherever non-mechanical switching is required. **New Lower Price. Only £2.10 for 12. 25 for 50 or £15 for 100 complete with magnet.**

£2.10

PROGRAMMER TIMER BY HONEYWELL

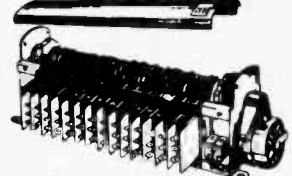

A bank of 15 micro-switches are each independently operated by 15 pairs of cams which in turn are individually adjustable to give switching periods of zero to 12 seconds with infinitely variable combinations. A mains synchronous motor drives the cam shaft at 1 rev. per 12 seconds (5 R.P.M.). Designed originally for vending machines at a cost of £18.00 plus. Many applications where continuous sequence programmes are required, such as lighting effects etc. **New in original makers cartons. First class value at £5.75 plus 25p P. & P.**

£5.75

315 EDGWARE ROAD, LONDON W2. Tel. 01-262 2251. Open 9 a.m.-6 p.m. MON to SAT

YOU MUST HEAR

**miniWISE audiLECT
YOUR
PERSONAL TUTOR**

**THE
No. 1
HIT**

Bring PLEASURE to your CAREER or HOBBY through Integrated LEARNING.

ORGANISED TUITION in your own HOME at your own SPEED—The TUTOR of YOUR CHOICE will give you rapid UNDERSTANDING—the key to SUCCESS.

ASSURE YOUR FUTURE IN RADIO, T.V. or ELECTRONICS FOR FREE DETAILS OF THIS UNIQUE sensible method just send us your name and address **Write now—right now to—**

**MINIWISE PRODUCTS
FREEPOST, BLETCHLEY, BUCKS.**

No one will call. (No stamp required) Or include only 90p to own a trial lesson* on either a C90 cassette in lib. case, or L.P. Tape (state which). *Your money INSTANTLY REFUNDABLE if not 100% convinced that this can be the turning point in your hobby or career

THE NATURAL WAY TO LEARN

TESL (ELECTRONICS)

37 TALGARTH ROAD, LONDON, W.14

MAIL ORDER ONLY

THE ONLY "SPEC" OF DIFFERENCE IS THE LOWER PRICE BRAND NEW FULLY GUARANTEED

RESISTORS

Full range of ISKRA carbon film resistors. All 5% (except values over 4.7M Ω)—high stability—very low noise—E12 values. $\frac{1}{2}W$, $\frac{1}{4}W$ 1p; 1W 2p.

POTENTIOMETERS

Carbon track 5K Ω to 2M Ω log or linear. Single 12p; Dual gang (stereo) 38p; Single D.P. switch 23p.

SLIDER POTENTIOMETERS

Overall length 86.6mm. Fixing centres 80mm. Single 10K, 25K, 50K, 100K, 35p each. Dual gang dual values as above, 50p each. Knob for above, 10p each.

TRANSISTORS

AC125	12p	AFI14	14p	BC147	9.5p
AC126	12p	AFI15	14p	BC148	9.5p
AC127	11p	AFI16	14p	BC149	9.5p
AC128	11p	AFI17	14p	2N2218A	13p
AC132	12p	BC107	7p	2N2222	13p
AC187	14p	BC108	7p	2N2222A	13p
AC188	14p	BC109	7p	2N3014	13p

Any one type
25+ 100+ 1,000+
Discounts 10% 20% 40%
Wholesale enquiries welcome

DIODES


ZENER—400mW 5% 3.3V to 30V, 12p each	709C, 25p each
SIGNAL—OA90, 4p; OA91, 4p	723, 51p each
RECTIFIER—IN4001, 4p; IN4004, 7p	741C, 30p each

Terms: C.W.O. please. P. & P. please add 10p for orders below £2. Discount 7 1/2% for orders above £10. Full CATALOGUE on request. S.A.E. appreciated.



"Where can I get exclusive units at lowest prices?..."

ROC ELECTRONICS!

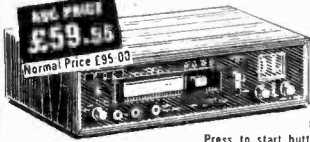

ROC PRICE £59.55
Normal Price £95.00

8-TRACK STEREO CARTRIDGE TAPE DECK MODEL RP-1000ST
The popular Lear-Jet type recording unit is the heart of the fantastic RP-1000ST, which has full record and playback facilities. Automatic track change with manual over-ride.

Press to start button. Stereo headphone and Left and Right Mic sockets on front panel. Dual recording level meter, and Left and Right volume controls. Built-in pre-amp. Tape speed $3\frac{1}{2}$ ips (9.5 cms). Frequency response: playback 30-10,000 Hz; recording/playback 30-8,000 Hz. Line output: fully variable 0-500mV. The RP-1000ST incorporates all the features you'd expect on a top quality Cartridge Tape Deck. Size 16" wide, 4" high, 3" deep. Cabinet in walnut. Including connecting leads.



As reviewed in "POPULAR HI-FI" February 1972

ROC PRICE £35.20
Normal Price £55.50

REALISTIC 30 WATT STEREO AMPLIFIER MODEL SA-500

A superb hi-fi amplifier with all the features you've ever wanted - for under £46.00. Saving over £10.00 on the normal retail value. Up-to-the-minute slider controls for bass and treble. Separate volume and balance controls. Headphone socket on front panel. Push-button input controls - magnetic phono (high/low) tuner, aux, mono, monitor. Loudness push-button control for perfect sound at low output levels. Left and right push-button on/off switches for speakers. Noise filtering and tape monitoring facilities. Two auxiliary AC outlets. Frequency response 20-20,000 Hz ± 1 db at full power. 15 watts rms per channel. Walnut cabinet with satin aluminium trims. Inputs: phono 2.5mV and 5mV RIAA; tuner/aux 250mV. Hum and noise: phono - 50db; tuner/aux - 65db. How's that for a specification! Size 14" wide, 3" high, 10" deep.



ROC PRICE £31.20
Normal Price £50.00

Ideal for use with any other amplifier. The RA-310 costs £10.00 less than the normal retail value... and yet it is a highly sophisticated unit, incorporating the latest solid state techniques. Operation is drift free for supreme station-holding capability. You can connect this Tuner to a stereo amplifier, to a tape deck or a tape recorder. And of course it covers all the stations in the AM and FM bands. FM: 87-108 MHz; AM: 525-1605 kHz. FM Sensitivities: FM, 3µV; AM, 250µV. Stereo separation 30dB at 1kHz, image rejection 80dB. Size: 11" wide, 4" high, 7" deep.



ROC PRICE £12.45
Normal Price £21.00

REALISTIC SA-100B 6-WATT STEREO AMPLIFIER
Here's a fabulous, exciting value in miniature! This high quality stereo amplifier measures only 9" wide x 3" high x 5" deep. And yet it has separate gated volume, balance and tone controls. Plus speaker in/out, mono/stereo, phono/tuner and power on/off slide switches. The ends are gilded walnut, with matching enamelled metal top. The front panel is satin aluminium and walnut-brown enamel. Frequency response is 50 to 10,000 Hz ± 3 db. Output 3 watts r.m.s. per channel into 8 ohms. Inputs are 100mV for both phono and tuner.

SPECIAL OFFER!

TEC HR-807 HEADPHONE RADIO
When you want to listen to the radio all by yourself then this will solve the problem. Separate volume and tuning controls with easy-to-use knobs. Frequency range is 535 to 1605 kHz medium wave band. Maximum output is 300 mW. Normal Price £7.65 ROC PRICE £5.00

EAGLE-1C.07 STEREO MOVING-MAGNET CARTRIDGE

Here's your opportunity to own a transcription cartridge for the price of a ceramic! It is specially designed to match top quality tone arms, and to get the very best from your hi-fi amplifier. 0.7 mil diamond stylus. Output: 7mV per channel. Frequency range: 20-21,000 Hz. Channel balance: ± 1 db. Channel separation: 28dB. Compliance: 12 x 10⁻⁶ cm/dyne. ROC PRICE £6.37



ROC PRICE £24.10
Normal Price £39.50

OLSON AM-375 40-WATT STEREO AMPLIFIER
An ideal unit for your new stereo separate system. It is more than £10.00 below the normal retail price! Making the AM-375 one of Britain's best hi-fi buys. It takes in signals from magnetic or ceramic pick-ups, tuners (see Olson RA-310) and tape decks. And it's got outputs for taping and for headphones. There are separate bass and treble controls, separate Left and Right channel volume controls. And a loudness switch for boosting the bass and treble notes when listening at low output levels. Frequency response: 20-20,000 Hz ± 3 db. Output: 20 watts r.m.s. per channel into 8 ohms. Inputs: magnetic phono 3.0mV RIAA, crystal phono 100mV, tape 160mV; tuner 180mV. Size 11" wide, 4" high, 7" deep. The specification reads well - sounds even better!



ROC PRICE £28.00
Normal Price £36.70

A-3000 36-WATT SOLID STATE STEREO AMPLIFIER
The A-3000 looks as good as it sounds! Giving you a big performance this superb audio amplifier has a full range of facilities on the front and rear panels. On the front - all the controls you're ever likely to need plus a headphone socket. On the rear - signal inputs, speaker outputs and a line fuse for circuit protection. Specifications: 18 watts rms per channel into 8 ohms. Frequency response 20-35,000 Hz (± 2 db) Inputs: Magnetic, Ceramic, Tuner, Tape, Aux, Tape Play. Size: 345mm x 300mm x 130mm.

CONSTRUCTORS' KITS

TWO TRANSISTOR RADIO KIT
Complete with solar cell
£2.50

10 PROJECT INTEGRATED CIRCUIT KIT
Build a radio, morse key, etc.
£3.50

SOLAR ELECTRONIC KIT
20 ways of harnessing the sun's energy
£4.50


TWO OCTAVE ELECTRONIC ORGAN KIT
Make your own music. Complete with speaker
£4.50

LIMITED STOCKS BUY NOW FOR XMAS!



ROC PRICE £17.80
Normal Price £25.00 per pair.

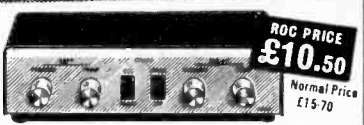R.446 3-WAY MATCHED SPEAKERS
These will do justice to your amplifier - and to your pocket. At only £17.80 a pair, they are real value-for-money. Each cabinet is heavily lagged and teak finished. They handle 16 watts rms (8 watts rms each). Each loudspeaker contains a large dual cone base unit, plus a separate tweeter. Frequency range 40 to 19,000 Hz. Size 14in. high, 9in. wide, 6 1/2in. deep.



ROC PRICE £10.50
Normal Price £15.70

OLSON AM400 4-WATT STEREO AMPLIFIER
Here's marvellous value for someone just starting to set themselves up in audio! At only £10.50, you get a fine amplifier in a scratch resistant metal cabinet, with a smart brushed aluminium front panel. It incorporates separate tone and volume controls for each channel. Inputs are provided for turntable (ceramic cartridge), tuner and tape deck or recorder. Frequency response: 70-20,000 Hz ± 3 db. Output: 2 watts r.m.s. per channel into 8 ohms. Inputs: phono 80mV, tuner/aux 80mV. Size 8" wide, 2 1/2" high, 4 1/2" wide.




ROC PRICE £27.25
Normal Price £39.95 each.

25-WATT 3-WAY CRYLER 'LIVING AUDIO' SPEAKER CE-5b
This high quality speaker has its own built-in 3-way sound response switch, giving you the ideal frequency response for hi-fi, natural or mood music listening. Its beautiful, heavy, oiled walnut cabinet incorporates two separate speaker units on 8" woofer, and a 5" mid-range with 2" concentric tweeter. Power handling capacity: 25 watts r.m.s. into 8 ohms. Overall frequency response: 35-20,000 Hz. Cabinet size: 10 1/2" x 7 1/2" x 8 1/2". Exactly right for matching the most modern decor.



ROC PRICE £27.55
Normal Price £42.00

PALACE AM/FM/MPX STEREO TUNER AMPLIFIER SSA-10
This is one of the lowest priced stereo tuner amplifiers on the market. It covers the full range of both AM and FM broadcast frequencies. And when you're switched to FM, an indicator lights up when a stereo signal is received - that's the time to switch to 'Stereo'! The SSA-10 has all the facilities you'd expect to find on tuners costing twice as much - separate volume, bass, treble, balance and tuning controls. Selector switch for tape, phono, AM, FM, stereo. Jack socket on front panel for stereo headphones. Frequency range: FM 88-108 MHz; AM 535-1605 kHz. Frequency response: 50-10,000 Hz ± 3 db. Power output: 4 watts total music power into two 8 ohm speakers. Size: 16" wide, 4 1/2" high, 8" deep.

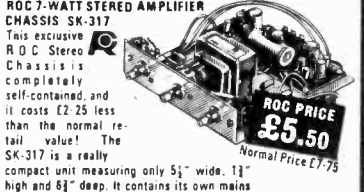

ROC PRICE £5.50
Normal Price £7.75


ROC 7-WATT STEREO AMPLIFIER CHASSIS SK-317
This exclusive R.O.C. Stereo Chassis is completely self-contained, and it costs £2.25 less than the normal retail value! The SK-317 is a really compact unit measuring only 5 1/2" wide, 1 1/2" high and 8 1/2" deep. It contains its own mains power supply, and has a gated volume control and separate treble controls for each channel. Specification: frequency response 40-17,000 Hz ± 3 db; output 3.5 watts music power per channel into 8 ohms; input, phono, 600mV; signal-to-noise ratio better than 45dB.



ROC PRICE £15.10
Normal Price £25.20

OLSON AM-372 18-WATT STEREO AMPLIFIER
Here's a really good amplifier at a really down-to-earth price - nearly £7 less than the normal retail value! Just look at what the AM-372 will do for you - reproduce signals from ceramic or crystal cartridges, AM and FM tuners, and tape recorders. And it gives you outputs for two sets of speakers, headphones and tape recorders. Frequency response is 30 to 20,000 Hz ± 3 db. Output 8 watts r.m.s. per channel music power into 8 ohm speakers. Phono input 200mV. Tuner input 200mV. Size: 12 1/2" wide, 3 1/2" high, 7 1/2" deep.

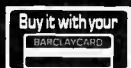ROC ELECTRONICS LTD
N. JORY Esq. 193 EDGWARE RD, LONDON, W2 1ET. 01-723 6211
CALLERS WELCOME 9-6 MON. TO SAT.
ALSO AT 87 TOTTENHAM COURT RD. LONDON W1
TEL: 01-580 3739 OPEN 9-6 MON.-FRI. SAT. 9-1



Return-of-post mail order service from Edgware Road. Orders over £10 post free (UK only). Add 25p for p & p to orders under £10. HP terms available for callers

DISCOUNTS UP TO

60%

Global's GOLDEN Guarantee

WE GUARANTEE THAT WITHIN 7 DAYS OF PURCHASE IF ANY ITEM OF GOODS IS FOUND TO BE GENUINELY DEFECTIVE WE WILL REPLACE THE SAID GOODS WITHOUT QUESTION. AFTER 7 DAYS GOODS ARE COVERED BY MANUFACTURERS 12 MONTHS GUARANTEE

SPECIAL OFFER
Garrard SP25 Mk. III £17.45
Goldring G800
Teak plinth and tinted cover.
All leads supplied.
Please add £1.25 for P. & P.

TURNTABLES

Please add 75p post & packing

Garrard SP25 Mk. III £9.95
Garrard AP76 £17.45
Garrard 5L65B £13.95
Garrard 1025T + cart. £5.97
Garrard 2025TC, Sonotone 9TAHC cart. £8.75
Garrard 401 £25.90
Garrard Zero 100 (Auto) £36.95
Garrard Zero 100 (Single) £9.40
BSR MP60 £9.40
Goldring GL72 £21.60
Goldring GL72/P £28.35
Goldring GL75 £26.90
Goldring GL75/P £33.90
Goldring GL85/P £57.95
Goldring 101/P.C. £20.00
Leak Delta £49.50
Wharfedale Linton + carr. £26.50
Thorens TD125AB Mk. II £91.75
Thorens TD150 Mk. II £26.95
Thorens TD150A Mk. II £32.95

AMPLIFIERS

Please add 75p post & packing

Amstrad 8000 Mk. II £13.95
Amstrad IC2000 £26.90
Amstrad Integra 4000 £21.95
Armstrong 521 (Teak cased) £44.40
Alpha Highgate 212 £24.95
Alpha Highgate FA300 £30.95
Alpha Highgate FA400 £34.50
Leak Delta 30 £44.85
Leak Delta 70 £54.95
Metrosound 5T20E £24.15
Metrosound 5T60 £45.50
Pioneer SA900 £85.00
Pioneer SA1000 £93.00
Rogers R/brook (Chassis) £35.80
Rogers R/brook (Cased) £38.00
Rogers R/bourne (Chassis) £41.80
Rogers R/bourne (Cased) £48.35
Rotel RA210 £24.50
Rotel RA310 £33.75
Rotel RA610 £50.75
Sinclair PR060 2 x Z30/PZ5 £14.70
Sinclair PR060 2 x Z30/PZ6 £16.70
Sinclair PR060 2 x Z50/PZ8/Trans £20.95
Sinclair AFU (Filter Unit) £4.20
Sinclair 605 £12.90
Sinclair 2000 £20.95
Sinclair 3000 £28.20
Wharfedale Linton £44.75
Eagle TSA149 £24.95
Eagle TSA151 £34.50
Teleton SAQ 206B £20.50
Teleton SAQ 307 £22.50

TUNERS

Please add 75p post & packing

Amstrad Multiplex 3000 £28.65
Armstrong 523 £39.50
Armstrong 524 £31.45
Rogers R/brook FET4 (Chassis) £31.00
Rogers R/brook FET4 (Cased) £34.95
Rogers R/bourne FET4 (Chassis) £43.00
Rogers R/bourne FET4 (Cased) £47.50
Sinclair PR060 (Module) £15.75
Sinclair 2000/3000 Tuner £31.00
Philips RH690 £33.00
Leak Delta FM (Cased) £53.75
Leak Delta AM/FM (Cased) £60.75

TUNER/AMPLIFIERS

Please add 75p post & packing

Armstrong 525 (Teak cased) £69.45
Armstrong 526 AM/FM (Teak cased) £77.75
Leak Delta 75 £120.95
Philips RH781 £50.00
Philips RH702 £82.50
Teleton 2100 £29.45
Goodmans One Ten £99.00
Rogers Ravensbrook (Teak cased) £77.50
Rogers R/brook (Chassis) £72.00
Goodmans Module 80 £118.00
Alpha Highgate 150 £44.25
Alpha FR 3000 £66.00

SPEAKERS

Please add £1.25 for post & packing Price per pair

Amstrad 138 £14.70
Wharfedale Denton 2 £28.50
Wharfedale Linton 2 £35.75
Wharfedale Melton 2 £47.45
Wharfedale Doveedale 2 £59.90
Celestion Ditton 10 £38.50
Celestion Ditton 15 £52.00
Celestion Ditton 25 £85.50
Celestion Country (new prod.) £35.50
Goodmans Double Maxim £47.85
Goodmans Mezzo 3 £46.95
Goodmans Magister £76.95
Sinclair Q16 £12.50

CARTRIDGES

Please add 10p post & packing

Goldring G850 £3.25
Goldring G800 £5.50
Goldring G800E £7.50
Goldring G800 Super E £14.15
Shure M1D £3.85
Shure M44E £4.85
Shure M55E £5.60
Shure M75E Type 2 £10.00
Sonotone 9TAHC £1.65

£3.20*

Plus 35p P. & P.
Finished in teak veneer with tinted dust cover. (Fully assembled). For Garrard SP25, 2025TC, 3000, AT60, 2000, 2500, 3500, 5100, 1025, 5L65B. Also for BSR, McDonald MP60 and others. For AP76, AP75, 5L72B, 5L75, 5L95B* £4.20 plus 35p P. & P.
Also finished in walnut to match Japanese equipment—at no extra.

GLOBAL AUDIO DISCOUNT WAREHOUSES

Dept. (PE16) 174 Pentonville Road, London, N1. Telephone 01-278 1769
Or: 4 High View Parade, Redbridge Lane East, Woodford Avenue, Ilford, Essex. Tel: 01-550 1086.

Open Monday to Saturday 9.30 a.m. to 6 p.m. **LATE NIGHT FRIDAY 7 p.m.**
MAIL ORDERS. Order with confidence. Send Postal Order, Cheque, Money Order, Bank Draft, Giro or Cash by Registered Mail. **CALLERS:** Please note that cheques can only be accepted together with cheque cards (not Barclay Card).



ERSIN
Multicore
3 CORE SOLDER

for fast, easy reliable soldering

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

IDEAL FOR HOME CONSTRUCTORS



Size 1 cartons all at 25p each in 40/60, 60/40, or Savbit alloys in 7 gauges.

EASY-TO-USE DISPENSERS



Size 5 (Savbit) 18swg, 18p (illustrated)
Size 19A (60/40 alloy) 18swg, 18p
Size 15 (60/40 alloy) 22swg, 22p

BIB WIRE STRIPPER AND CUTTER



NEW!

Model 3A. Strips insulation from cable or flex without nicking wire. 4 different settings, 4&6BA spanner ends, ground cutting edges Price 32p. Also available, de luxe Model 8. Price 58p.

From Electrical and Hardware Shops. If unobtainable, write to: Multicore Solders Ltd., Hemel Hempstead, Herts.

ELECTROKIT

Now available from one company are complete kits for many of the articles published in the Electronics, Radio and TV Journals. Examples of our range are:

SCORPIO IGNITION SYSTEMS (P.E. Nov. 1971), £10.50, including P. & P. This kit includes all the parts for the assembly of this popular and reliable system. The hardware and instruction data are included.

ELECTRONIC PIANO (P.E. Sept. 1972), price £41, including P. & P. This kit consists of all the resistors, capacitors, presets and semiconductors to complete this project. The hardware and keyboard are not included in the kit.

DRILL SPEED CONTROLLER (E.E. Aug. 1972). Kit consists of resistors, rectifiers, thyristor and tag board as specified in the article, price £1.05, including P. & P. Kit with M.K. box, plate and switch, price £2.05, including P. & P. We shall also be offering kits for most articles published in the P.E. and other popular electronics magazines and will be pleased to quote prices.

Send for details of Light Dimmer and Windscreen Wiper Delay Kits (please enclose S.A.E.). At present we can only accept orders by post but if you have any inquiries please phone 01-286 5282.


ELECTROKIT

126 Headstone Road • Harrow • Middlesex



I.L.P. (Electronics) Ltd

THE HY41

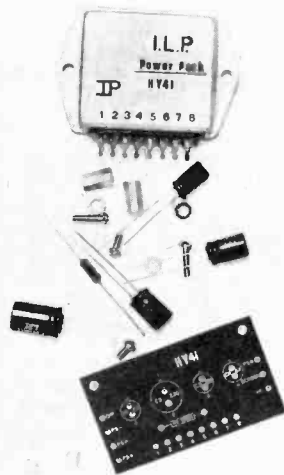

The HY41 supersedes the popular HY40 introduced by ILP last year. This highly improved module achieves true High Fidelity with a dramatic reduction in distortion (typically 0.05% at 1KHz into 8 ohms!) and is electronically and mechanically compatible with the HY40.

With this important improvement the HY41 retains all of the quality characteristics found in the earlier version and P.C. board, Resistor, Capacitors, Hardware Mountings and comprehensive manual are included in the basic kit. No further components are required to construct a complete power amplifier of extremely high performance sufficiently versatile to provide power not merely for Hi-Fi but also for public address systems and industry.

The free manual gives a full circuit diagram of the HY41 and its various applications including a complete stereo amplifier.

Like its predecessor the HY41 is based on conventional and proven circuit techniques developed over recent years.

OUTPUT POWER: British Rating 40 WATTS PEAK, 20 watts

R.M.S. continuous.

LOAD IMPEDANCE: 4-16 ohms.

INPUT IMPEDANCE: 30K ohms at 1KHz.

VOLTAGE GAIN: 30db at 1KHz

TOTAL HARMONIC DISTORTION: less than 0.15% (typical 0.05%) at 1KHz.

FREQUENCY RESPONSE: 5Hz-50KHz \pm 1db.

SUPPLY VOLTAGE: + 22.5volts D.C.

SUPPLY CURRENT: 0.8 amps maximum.

PRICE: inc. comprehensive manual, P.C. board, five extra components and P. & P.:-

MONO: £4.90

STEREO: £9.80

UNIQUE HYBRID PRE-AMPLIFIER

The HY5 has rapidly established a position in the WORLD as the sole hybrid pre-amplifier to contain all feedback and equalization networks within an integrated pre-amplifier circuit.

Supplied with the HY5 are two stabilizing capacitors and by the addition of volume, treble and bass potentiometers it is ready for use.

Internally the HY5 provides equalization for almost every conceivable input, the desired function is achieved by use of a multi-way switch or by direct interconnection.

Two distinctive features of the HY5 are its inbuilt stabilization circuit, allowing it to be run off any unregulated power supply from 16-25 Volts and a balance circuit which, when linked by a balance control to a second HY5, forms a complete stereo pre-amplifier.

Specifically and critically designed to meet exacting Hi-Fi standards, the HY5 combines extremely low noise with a high overload capability. When used in conjunction with the HY41 and PSU45 forms a completely integrated system.

INPUTS

Magnetic Pick-up (within \pm 1db RIAA curve)
2mV, 47K Ω

Tape Replay (external components to suit head)
4mV, 47K Ω

Microphone (flat) 10mV, 47K Ω

Ceramic Pick-up (equalized and compensatable)
20-2000mV, variable.

Tuner (flat) 250mV, 100K Ω

Auxiliary 1 250mV, 47K Ω

Auxiliary 2 2-20mV, 100K Ω

OUTPUTS

Main Pre-amp output 500mV.

Direct tape output 120mV.

ACTIVE TONE CONTROLS (Baxendall)

Treble + 12db.

Bass + 12db.

INTERNAL STABILIZATION


Enables the HY5 to share an unregulated supply with the Power Amplifier.

SUPPLY VOLTAGE

16-25 volts

PRICE: MONO: £3.60

STEREO: £7.20

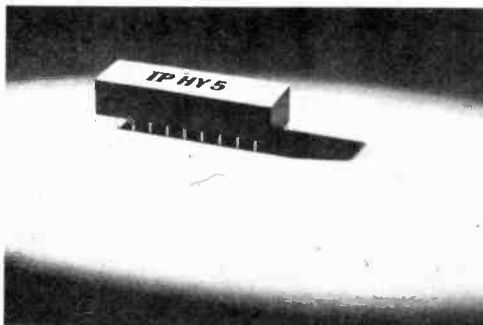

SUPPLY CURRENT

6mA approx.


OVERLOAD CAPABILITY

better than 26db on most sensitive input infinite on tuner and auxl.

OUTPUT NOISE VOLTAGE: 0.5mV.

POWER SUPPLY PSU45

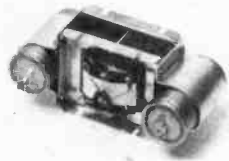The versatile P.S.U.45 is designed to supply your HY41's +HY5's in stereo or mono format.



Specification

Input: 200-240 Volts.

Output: \pm 22.5 Volts at 2 amps.

Overall Dimensions: L. 7"; D. 3.8"; H. 3.1"

PRICE: £4.50 inc. P. & P.

CROSSLAND HOUSE · NACKINGTON · CANTERBURY · KENT

CANTERBURY 63218



Christmas Presents a Problem!

We can take it for granted that she will be buying you the very thing you've set your heart on, so let's concentrate on that superb present you are so generously thinking of buying her! Simple—as everybody knows, today's finest range of radio and electronic components is to be found in the Home Radio Components Catalogue. You could buy her a copy, so that she can pick out just what she wants. On second thoughts, that might complicate matters. Better make the choice yourself. After all, you want it to be a surprise for her on Christmas morn! Moreover, you'll both have the Home Radio Components Catalogue, and can spend many hours together, browsing through it. The Catalogue is crammed full with details of 8,000 items, of which about 1,500 are illustrated. It costs

only 70 pence, including post and packing, and each copy contains 10 vouchers worth 5p each.

Of course, you can call at our shop (we're open 9 to 5.30 Monday to Saturday, except Wednesday 9 to 1) and get just what you want straight off the shelf. Incidentally, a catalogue bought this way will cost you only 50 pence. Whether you order by post or buy over the counter you should join our Credit Account Service. It's the simple and convenient way of buying all your radio and electronic components. We supply pre-paid envelopes and order forms, and no matter how many orders you send us you make only one payment per month. Full details and entry forms are in the catalogue.



The price of 70p applies only to catalogues purchased by customers in the UK and to BFPO addresses.



POST THIS COUPON with your cheque or postal order for 70 pence

Name

Address



HOME RADIO (Components) LTD.
Dept. PE, 234-240 London Road, Mitcham CR4 3HD

Editor F. E. BENNETT Assistant Editor M. A. COLWELL Editorial D. BARRINGTON G. GODBOLD S. R. LEWIS B.Sc. (Eng.)
Art Editor J. D. POUNTNEY Technical Illustrators J. A. HADLEY R. J. GOODMAN
Advertisement Manager D. W. B. TILLEARD

FIFTY YEARS OF BROADCASTING

ANNIVERSARIES are always useful when they provide an excuse to pause and look back over some really significant period. The pause is fully justified on the occasion of the BBC's 50th birthday. There is no question that these 50 years of broadcasting in the U.K. have had tremendous and lasting effect upon the individual and upon society as a whole. The history of broadcasting is also the history of the emergence of electronics, although the precise origins of both are indefinable or controversial, and go back certainly far beyond a half century.

In November 1922 the British Broadcasting Company was formed by a group of leading wireless manufacturers, at the behest of the G.P.O. This action followed years of agitation by various individuals and groups in this country. One of the most active pressure groups was the Wireless Society of London (later the Radio Society of Great Britain) representing the large number of amateur constructors and experimenters the new medium of wireless communication had already attracted. At the time, broadcasting was already in full swing in the United States where more than 300 registered stations were operating; in Europe regular broadcasts had been made from The Hague since 1920; while in this country irregular transmissions had been made throughout this period by the Marconi Company.

In 1926 the BBC was reconstituted as a public corporation by Royal Charter, fully committed to the public service concept by its indomitable chief executive J. Reith (later Lord Reith). High-minded principles and the uncompromising way in which they were applied produced a powerful, influential monopolistic organisation which has always been the centre of much controversy. The BBC during the past 50 years has been held up as an example of public service at its best, by some; while it has been condemned as an autocratic body out of touch with (or indifferent to) contemporary public opinion, by others. Political attitudes aside, all objective observers must acknowledge and pay respect to the integrity of purpose and high standards insisted upon and maintained consistently throughout these 50 years by the BBC, in both programme and engineering matters.

continued on page 1044

THIS MONTH

CONSTRUCTIONAL PROJECTS

RALLY DRIVER GAME	1018
HOOTING OWL	1032
P.E. ELECTRONIC PIANO—4	1038
P.E. DIGI-CAL—6	1050

SPECIAL SERIES

DESIGNING WITH I.C.s—3	1029
------------------------	------

GENERAL FEATURES

SUBSTITUTES FOR VARACTOR DIODES	1046
INGENUITY UNLIMITED	1058

NEWS AND COMMENT

EDITORIAL	1017
SPACEWATCH	1025
STRICTLY INSTRUMENTAL	1026
NEWS BRIEFS	1044
PATENTS REVIEW	1045
ELECTRONORAMA	1048
INDUSTRY NOTEBOOK	1057
MARKET PLACE	1065
READOUT	1066

*Our January issue will be published on
Friday, December 8*

RALLY DRIVING GAME

By
D. R. Daines

A game using a simple operational amplifier to simulate some of the characteristics of a car rally.

THE average car-race game suffers from two major drawbacks: all the cars taking part usually have identical characteristics and there is little or no room for skill. Here in a simple and inexpensive unit both drawbacks are overcome.

Not only are five different cars offered for use, with differing road-holding, braking and acceleration characteristics, but skill in manipulating brake and throttle is hard to come by. Players must use this skill in order to drift round corners at the maximum speed permissible without skidding off. Obviously, the winner will be the player who can acquire this skill the quickest.

The whole unit is completely self-contained and can be built for about £3, using spare materials for the case.


BASIC RALLY GAME IDEA

On the left of the front panel (see photograph) is a bank of five press-switches with the names of five cars, one of which must be selected before the unit can operate. Next to it is a variable resistance that is set to represent the present speed that the car is supposed to be travelling—from 0 to 100 m.p.h.

Brake and throttle are simulated by variable resistances, but other than identification labels there are no dial markings round the track of the pointer knobs; players must accustom themselves to their particular car and use judgement in their setting.

In the centre of the front panel is a flap that conceals a voltmeter and when the player has adjusted the previous controls he lifts the flap to read his resultant speed. Since 1 volt represents one square of advancement on a playing board and also represents 10 m.p.h., conversion is easy.

When the player's car enters a corner, he sets a rotary switch to represent the severity grading of the corner and then presses a push-button. If the lamp above lights up, the car is deemed to have skidded off. Full details on how to play the game are given at the end of this article.

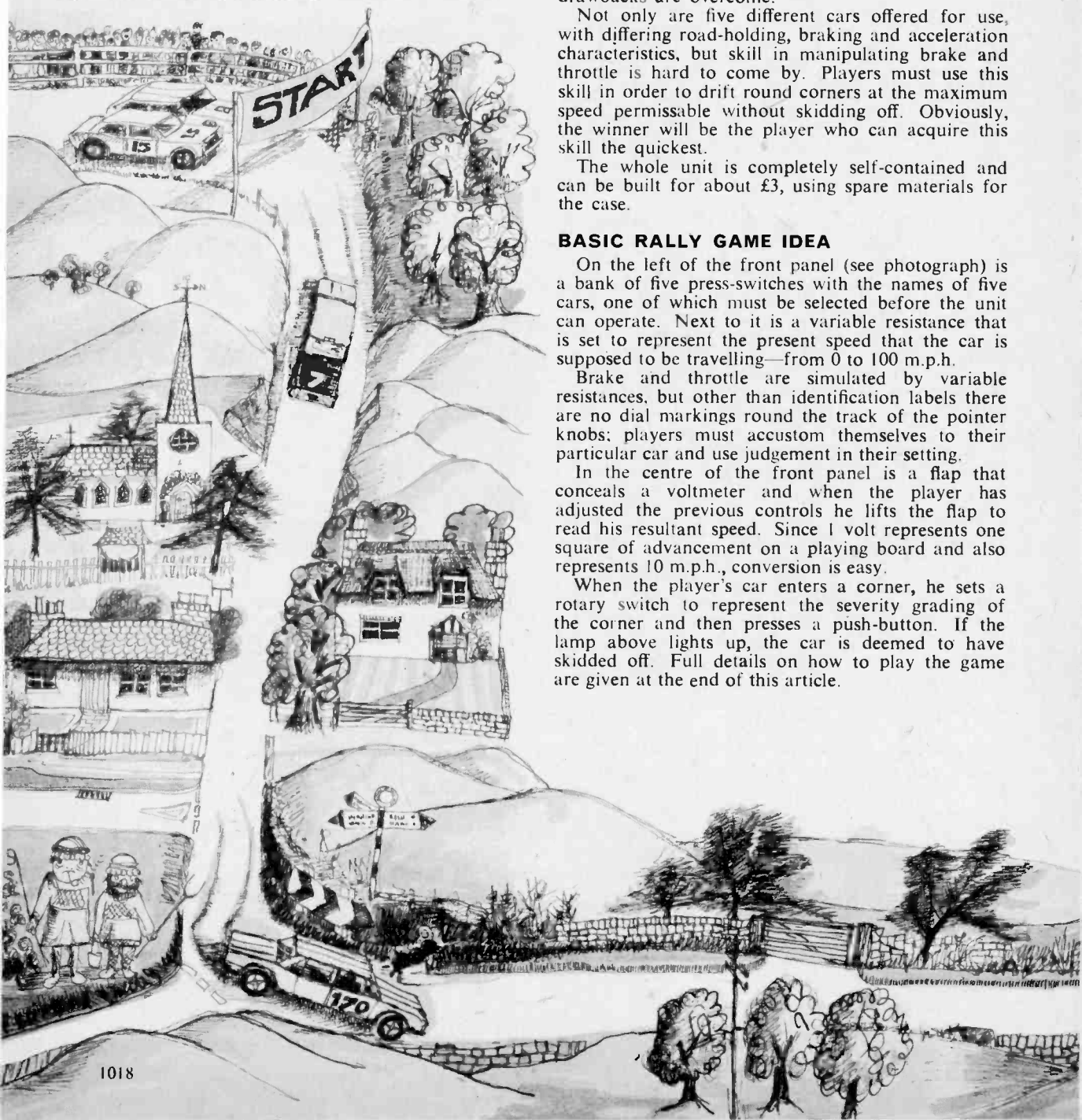

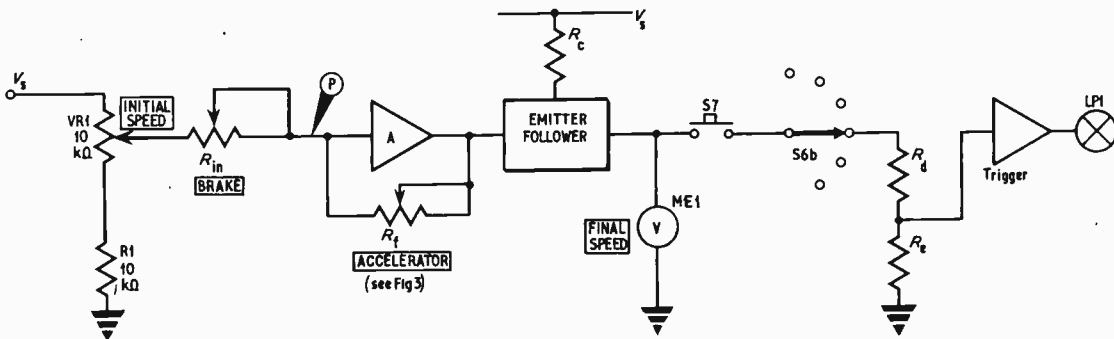


Fig. 1. Simplified circuit showing principle of operation

SIMULATION CIRCUIT

Fig. 1 shows a simplified schematic diagram of the whole unit. A 12V positive supply is presented to VR1, the SPEED control, which is arranged in a simple voltage divider system. Since R1 is equal to VR1, the minimum voltage output is half the supply, i.e. 6 volts.

The resistor is used because if VR1 was returned directly to earth, the input of the amplifier would also be earth and the output to the meter would be nil. Hence when starting off from rest the cars would achieve a speed of nothing; racing their engines without letting the clutch out, so to speak.

The next unit is a very interesting one that is really the heart of the system. It is a direct current amplifier with considerable negative feedback. Since it is direct current that is being amplified, capacitance coupling is out of the question and recourse must be made to direct coupling. The circuit used is a direct coupled d.c. amplifier which has a large input impedance, a very large gain, and considerable negative feedback, otherwise termed an operational amplifier.

OPERATIONAL AMPLIFIER

Let us assume that the gain of the amplifier is 10,000 and that the voltage out is 10 volts. This would mean that the voltage at point "P" in Fig. 1 is $10 \div 10,000 = 0.001$ volt and considerable current is flowing back through R_f to maintain this very low figure—virtually at earth potential. It follows that increasing the value of R_f will reduce this cur-


Table 1: VALUES OF INPUT VOLTAGE TO ACHIEVE 10V OUTPUT (where possible)

R_{in}	$R_f = 3.3k\ \Omega$	$R_f = 4.7k\ \Omega$	$R_f = 6.8k\ \Omega$	$R_f = 8.3k\ \Omega$
68k Ω	11.0V	8.5V	6.5V	5.75V
83k Ω	9.0V max	9.9V	7.5V	6.6V
97k Ω	5.4V max	11.5V	8.6V	7.6V
118k Ω	1.0V max	6.8V max	10.6V	9.3V

rent, raise the voltage at point "P" and raise the output voltage.

R_{in} has the opposite effect; raising this value will lower the voltage at point "P" and hence the output voltage. The analogy to accelerator and brake is obvious; R_f becomes the accelerator and R_{in} becomes the brake. See Table 1.

Of course R_{in} and R_f have upper and lower limits. The upper limits are no problem, but by adjusting the lower limits we may readily obtain different responses to the variable resistors. These are set to the individual car characteristics. (See Table 2 and Fig. 2). It will be seen from Fig. 2 that there is a choice of fixed resistors of differing values. Which one is chosen depends upon which switch is pressed. Then there is a small fixed resistor common to all and finally VR2, which is the brake. The total resistance equals R_{in} .

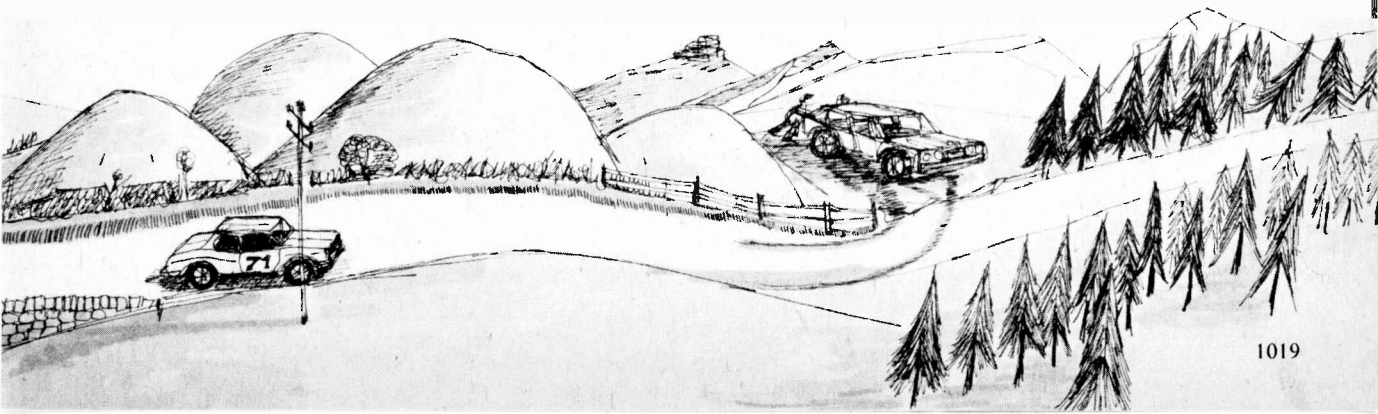

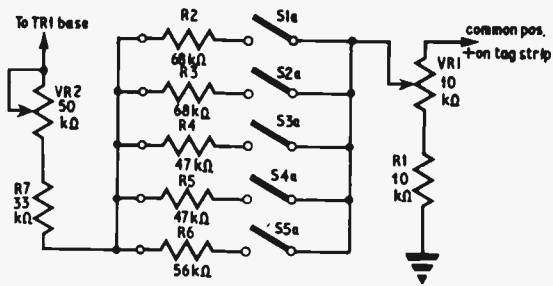


Fig. 2. Braking is simulated by R2 to R6 switched in the brake position R_{in}

Table 2: RESISTOR BIAS VALUES

CAR (switch no.)	R_{in} (brake)	R_f (accelerated)	R_c (max. speed)	R_e (road holding)
1	68k	2.2k	4.7k	6.8k
2	68k	3.3k	Nil	5.6k
3	47k	4.7k	4.7k	5.6k
4	47k	3.3k	2.2k	8.2k
5	56k	2.7k	Nil	Nil
VR	50k	5k	—	—

Fig. 3 shows the operational amplifier and its associated low output-impedance stage. The circuit is surprisingly simple; TR1 and TR2 form the amplifier. Since they are direct coupled as a super-alpha pair, their individual current gains are multiplied. Notice particularly from where the feedback is taken. At this point (TR2 emitter) the voltage rise is out of phase with the base of TR1 and hence negative feedback.

In the prototype, the car-selection switches were only two-pole (see components list), so another selection of fixed minimum values were not provided for the feedback. However, from experimental work that has been done on the prototype, and for those readers who might prefer to use three- or four-pole switches, values have been given in Table 2. Not much can be gained in this way, however, and those who wish to incorporate only two-pole switches can be happy in the knowledge that the system works well.

An emitter-follower TR3 provides a low-impedance output that will not load the previous stages. The meter is arranged so that the resistance of the meter coil provides the emitter resistance.

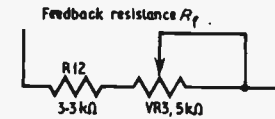
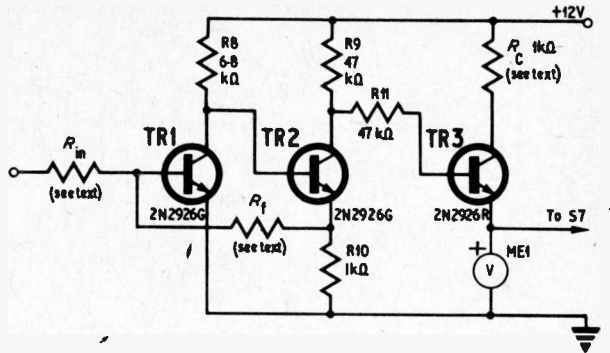


Fig. 3. The basic operational amplifier with the practical feedback resistance R_f

Normally, the collector is returned to the positive rail directly, but the insertion of resistor R_c in the collector lead will reduce the maximum output voltage. This is a useful facility for those who would like to limit the maximum speed of different cars; values are given in Table 2.

ROAD-HOLDING

From the meter, the current goes to a push-button (S7 in Fig. 1) which is included for three reasons. Firstly, there will be many game moves in which a corner is not encountered; secondly, illumination of the lamp would give players a valuable clue as to the position of the meter; and finally, current consumption is very low at 6mA, but jumps to over ten times that figure when the button is depressed and the lamp lights.

The corner selection switch S6 selects, in the first position, the battery on/off, while each of the other five positions selects a voltage-divider such as is shown as R_d and R_e . All resistors in R_d are connected together and fed to the Schmitt trigger, while those in R_e are selected by the car press switches. Thus the actual voltage division that takes place depends upon the severity of the corner and the car selected. See Fig. 4.

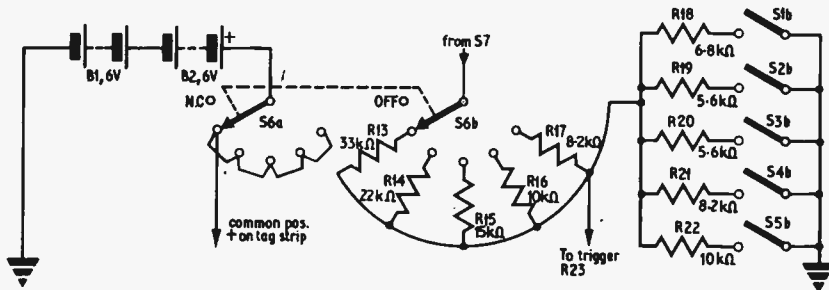


Fig. 4. Switching for road holding ability

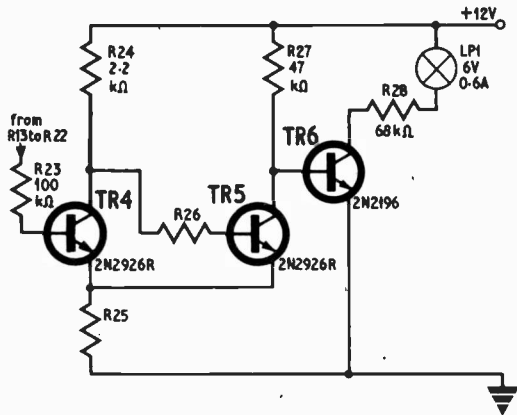


Fig. 5. Switch trigger and lamp driver




SCHMITT TRIGGER

Transistors TR4 and TR5 in Fig. 5 form a Schmitt trigger that will trigger the output of TR5 when the incoming voltage rises to 1.5 volts. When TR5 turns on, TR6 switches off, hence nearly 6V appears across the lamp, making it glow. The resistor in series with the lamp is a current limiter.

CONSTRUCTION

The constructor should start by obtaining his bank of press switches. There are many types available and many suitable as far as the circuitry is concerned. The panel may then be cut and drilled to suit, following the dimensions given in Fig. 6. The hole for the meter may require adjustment as well as extra fixing holes.

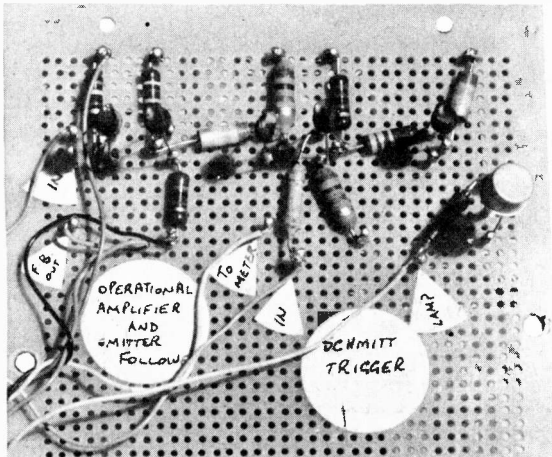The hole in the top right-hand corner is to view the lamp. This was just drilled and countersunk, but readers may prefer to use a coloured plastics lens.




Rally driver circuit board

Before the panel can be painted, the meter-cover flap must be made. (Fig. 7). The two small brackets were made from thin (24 s.w.g.) tinplate, while the flap was made from thicker (18 s.w.g.) aluminium; as was the panel. A small $\frac{1}{8}$ in \times $\frac{1}{8}$ in lug was left on each of the two top corners to fit in the $\frac{3}{16}$ in holes in the brackets. This provides a very simple hinge for the flap. Notice that the flap has a 30 degree bend across it so that it lies flat on the face of the meter. When complete, glue a strip of felt on the underside in order to prevent scratches on the cover glass.

When the flap has been fitted—the meter having just been offered in position—the panel can be painted and put to one side while the case is made.

Make the bottom of the case next, ensuring that it is the same length as the panel (Fig. 8). Cut this from $\frac{3}{8}$ in ply for rigidity, then cut two ends from $\frac{1}{4}$ in ply to the dimensions given; glue and pin them over the ends of the base. Cut the top also from a sheet of $\frac{1}{4}$ in ply. Make sure that it is exactly the length of the base plus the two ends, then glue and pin it on top of the ends.

Glue and pin $\frac{1}{4}$ in square fillets inside the front to take the panel, and on the base to hold the batteries. When the glue has set, smooth all surfaces and prepare for paint or polish. Fit rubber mushroom feet to the base.

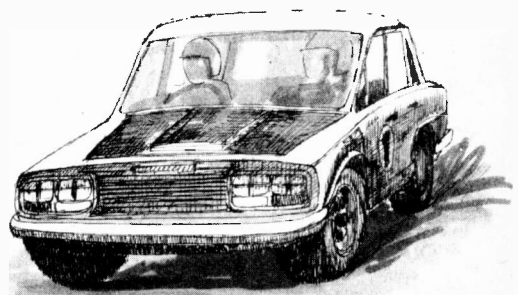

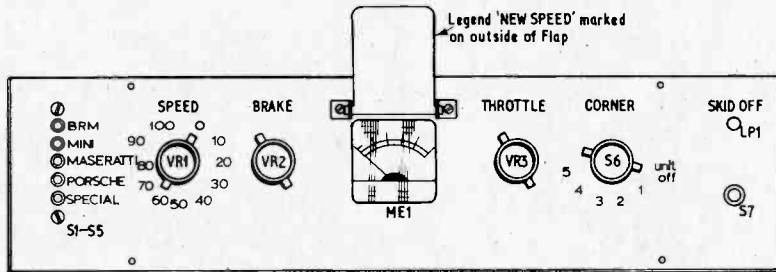
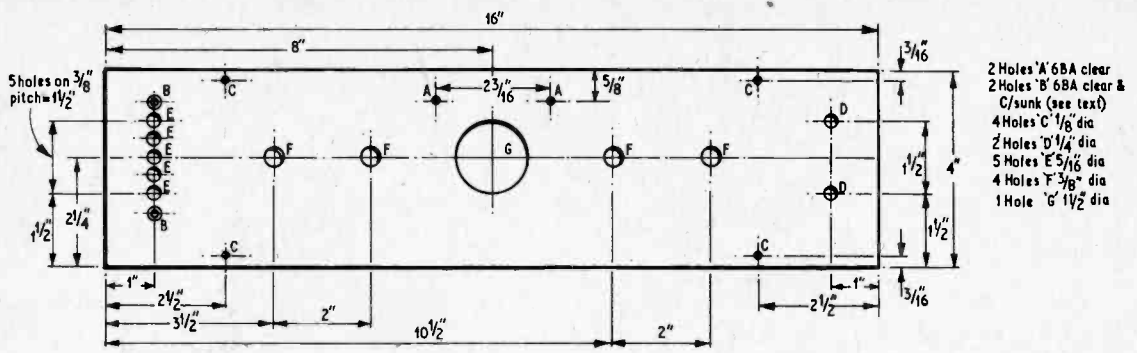


Fig. 6. Front panel drilling details and label layout

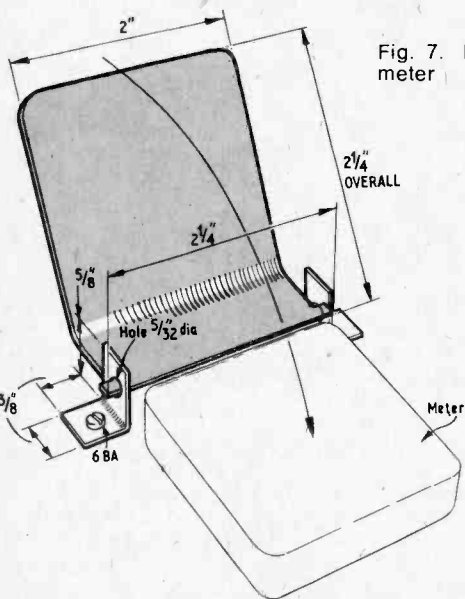


Fig. 7. Details of the brackets and flap for the meter

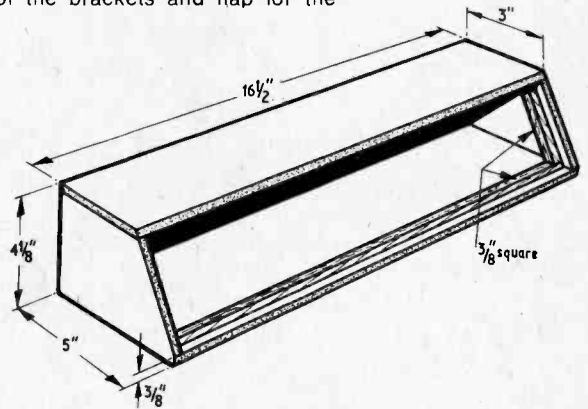


Fig. 8. Dimensions of case construction

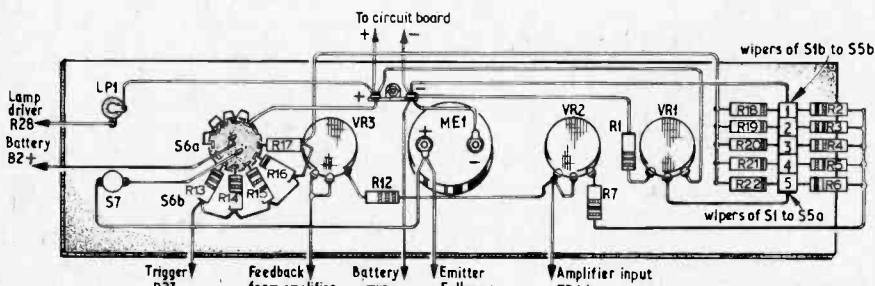


Fig. 9. Wiring of front panel components

WIRING

All the switches, potentiometers and the meter can now be mounted on the panel and the wiring as shown in Fig. 9 undertaken. Seven wires lead off to the circuit board; leave these at least 4in long. To save confusion, it is best if these wires are colour-coded. The battery clips are joined so as to connect the two 6V batteries in series; the negative wire is taken to the tag strip, and the positive to one central tag of S6.


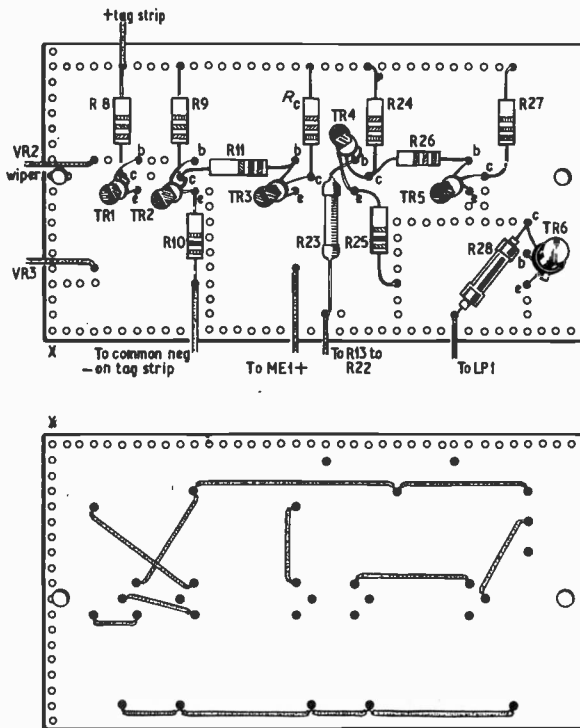


Fig. 10. Layout of components on s.r.b.p. circuit board and underside wiring

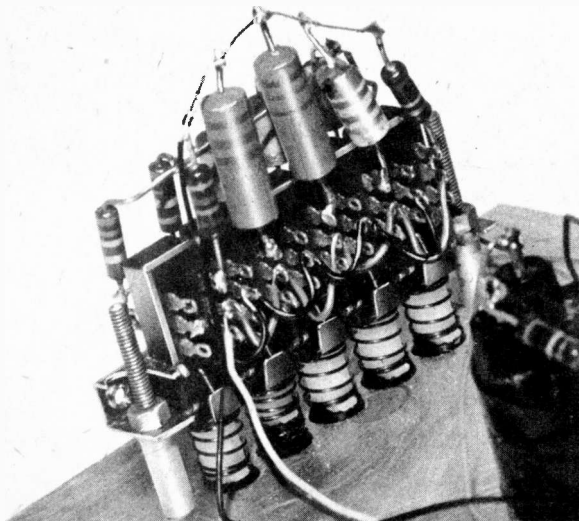

Wiring of switches S1-S5

CIRCUIT BOARD

It will be seen from the photographs that there is ample room inside the case and that a small circuit board will hold all the active components. The components are arranged in two distinct sections, sharing a common 12 volt supply line and a common earth. A suggested wiring layout is shown in Fig. 10.

Solder all the wires to appropriate points on the circuit board before putting it all into the case. Check all wiring against the circuits before connecting the batteries and testing. If for any reason the operational amplifier is not functioning as it should, adjustment of resistors in R_{in} or R_f or both may solve the difficulty.

When all is satisfactory it can be assembled in the case. The circuit board sits on top of the bottom front strip and on a similar strip at the back, while the batteries are held by similar wood strips glued to the case. The panel is fastened to the fillets by four $\frac{1}{4}$ in chrome-plated screws. Finally, a back of hardboard may be pinned into place, its edges chamfered and smoothed.

COMPONENTS . . .

Resistors

R1 10k Ω	R11 47k Ω	R21 8.2k Ω
R2 68k Ω	R12 3.3k Ω	R22 10k Ω
R3 68k Ω	R13 33k Ω	R23 100k Ω
R4 47k Ω	R14 22k Ω	R24 2.2k Ω
R5 47k Ω	R15 15k Ω	R25 1k Ω
R6 56k Ω	R16 10k Ω	R26 33k Ω
R7 33k Ω	R17 8.2k Ω	R27 47k Ω
R8 6.8k Ω	R18 6.8k Ω	R28 68 Ω
R9 47k Ω	R19 5.6k Ω	R_c See text and Table 2
R10 1k Ω	R20 5.6k Ω	

All $\pm 10\%$ $\frac{1}{4}$ watt carbon

Potentiometers

VR1 10k Ω linear carbon
VR2 50k Ω log. carbon
VR3 5k Ω linear carbon

Transistors

TR1, TR2 2N2926G
TR2, TR3, TR4, TR5 2N2926R or O
TR6 2N2196

Meter

ME1 Voltmeter 10V f.s.d. type MRA38 or similar
--

Lamp

LP1 6V 0.06A m.e.s. with holder.

Switches


- S1 to S5 Push button 2 or 4 pole changeovers on common frame with reset, or separate toggle switches
- S6 2-pole, 6-way rotary wafer switch
- S7 Single-pole, push button on/off

Batteries

B1, B2 6V each style PP1 (2 off)

Miscellaneous

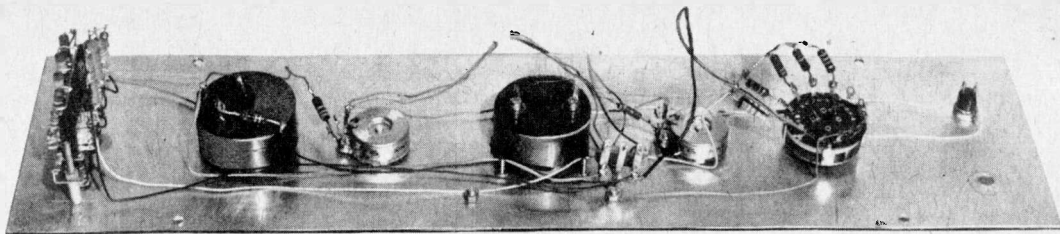- Battery connectors (2 pairs)
- Aluminium panel 16in \times 4in
- Plywood $\frac{1}{4}$ in for case and $\frac{1}{2}$ in square section strip
- Component wiring board or printed circuit board approx. 4.5in \times 4in or less
- Glue, pins, knobs



Components mounted on rear of rally driver front panel

GAME PREPARATION

A large sheet of card is obtained (the larger the better) and a road route marked out on it containing plenty of junctions, bends and corners of differing severity. Hazards, landmarks, buildings and other obstacles can be incorporated to choice. It is worth marking lanes into spaces or car-lengths. Mark a starting/finishing line, and grade each corner and hazard.

PLAY

Toy cars are placed in each lane at the starting line. Players may toss a coin for choice of lane. The last player to place his car has the privilege of moving off first. Each player specifies which type of car he is using and of course must stick to it throughout the game. A note is made of all choices. There is no limit to the number taking part, and any number of players may specify the same type of car.

In his turn, each player adjusts VRI to his present speed, presses the switch for his type of car, then adjusts brake and/or throttle to his satisfaction. He lifts the flap and reads the voltmeter to the nearest whole division. Once he has lifted the flap he cannot readjust the controls until his next turn; he must lower the flap again afterwards. The player then moves his car the number of car lengths equal to the meter reading up to a maximum of ten lengths.

If during the course of this move he encounters a corner, he sets S6 to the numbered grading of that corner, from 1 to 5, with "1" being a slight bend and "5" the inside track of a hairpin. He then presses the button and if the lamp lights he spins off the track and misses the next turn. The turn after that he restarts from where he spun off.

LANE DISCIPLINE

Only one car is allowed in a square at a time. Changing lanes is permissible, provided that in the lane into which he wishes to move or cross, there is no car nearer than four lengths behind; that is, there must be three clear lengths.

Cars wishing to overtake another may therefore be boxed in by a third and in these circumstances he must match his speed with the slower car in front. Failure to do so—that is, if his move would ordinarily take him beyond the car in front—means that he again must spin off the track and miss a turn.


Of course, players may use this technique deliberately to force a car behind off the road, and there will be many cases where a player over-compensates or grossly mishandles the brake, bringing his car to a halt in the path of another. Unless the one behind can overtake without hindering a third, or unless he too can halt, then he must spin off and miss a turn.

CONCLUSION

Constructors preparing a track may have as many bends as they wish, but at least one good straight should be included—particularly if the top speed of some cars is limited in the manner described. Hazards such as chicanes and islands could also be introduced and constructors should bear in mind that the inside lane on a bend may have fewer car-lengths in it, but rate a higher corner-severity.

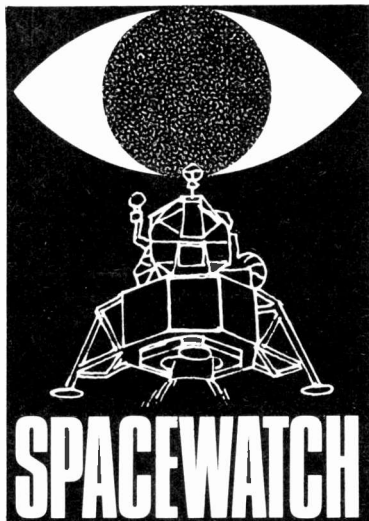Much of the success of the game and the enjoyment derived is in the road layout, and it will probably be worthwhile to collaborate on this with someone who has had real rally driving experience.★





BY FRANK W. HYDE

SOVIET SPACE PROBES

Some additional information has now become available from Russia which relates to the *Mars-2* and *Mars-3* space probes. Some of the work done by *Mars-3* has already been reported here. The additional information was obtained with infra-red radiometers operating in the 8 to 40 micrometre band.

The system of measurement was such that the tracks of the probes went from the southern hemisphere to the northern hemisphere of Mars, going through the seasons and all parts of the day. The temperature of the surface of Mars was plotted through these periods and showed that the variation was from -13°C to -93°C .

From this data a clue can be obtained as to the structure of the surface, and the climate can be assessed. The low temperatures at night seem to indicate that the surface cools quickly after sunset. If this is the case then it points to the heat conductivity of the surface as being low and consistent with dust or dry sand in a comparatively rarefied atmosphere.

Generally speaking, there was a difference between the dark areas or seas, and the light areas or continents. The seas were warmer by some 10°C and this is no doubt due to lower reflective power in these areas. This is true of one special area, a dark region known as *Cerberus*, which lies north of the *Chimærian sea*. It is likely that the higher heat conductivity is due to rocks projecting from the surface.

In February when the probe *Mars 3* was in the region of the northern ice cap the infra-red radiometer recorded a temperature of -110°C . Such a reading indicates that the polar cap consists mostly of solid carbon dioxide.

This cap remains all through the year. There is also indication of some water-ice. The southern ice cap disappears in summer.

DRY MARS

The Soviet scientists have said that it is possible that the north polar cap contains more carbon dioxide and water than in the whole of the Martian atmosphere. The actual precipitation of water on Mars is about 0.02 of that of the earth's atmosphere. Mars, therefore, is much drier than earth based experiments and measurements indicated.

The dust storms on Mars still remain a mystery. Measurements have shown that the particles of dust are about one micrometre in size. These would settle very slowly, thus these dust clouds often endure for up to three months. One thing that has been noted with these clouds is that an increase in wavelength of observation can make them more transparent to the scanning photometer. Some particles are found to be as much as ten micrometres in size but these settle very quickly.

It is interesting to note that the two spacecraft from the Soviet Union have relied on astrophysical instruments for their observations whereas the United States have relied mostly on television. Such combination of observations should yield a much more positive accumulation of data for comparison.

So far the information from the various probes since 1965 has led to comparisons of earlier measurements. For example, in 1969 *Mariner* probes 6 and 7 recorded atomic hydrogen levels substantially higher than those recorded by *Mars-2* and *Mars-3*. The possible explanation is that either there is now a smaller amount of water vapour present, or that the temperature has fallen.

Finally, the presence of a shock wave due to the solar wind interacting with the upper levels of the Martian atmosphere, was detected.

GALAXY THAT EXPANDS FASTER THAN LIGHT

Radio telescopes at California and Massachusetts, working as an interferometer with 100 million wavelengths as a base line, and enabling changes of 0.001 second of arc to be detected, were focused on the source 3C 120, a quasar.

Astronomers D. B. Shaffer, M. H. Cohen, David Jauncey and K. Kellerman were examining the fine structure of this source and when they compared the present results with some made about eight months before, they observed considerable structural changes in the source. The movements observed, when

reduced to a measurement of velocity, indicates that the "blobs" of matter were moving apart at two to three times the speed of light.

There have been previous records in two quasar explosions which indicated speeds faster than light. However, the uniqueness of this new result lies in the fact that whereas the two previous events were quasars with a high red shift, about which some astronomers now have doubts, the results from 3C 120 are from a source of quite low red shift. In this case there is no longer the criticism that the apparent high speed is because the distance from the earth is much less than supposed. The distance of 3C 120 is not in question. The situation has thrown the whole problem into a turmoil again.

CRUST OF THE MOON

The artificial production of seismic events on the moon by crashing spent stages and lunar module ascent stages plus one authentic meteorite of about six feet in diameter, have now provided a great deal of data from the seismic observatories on the moon. Altogether there have been about six artificial impacts and these have enabled the reflections from the various layers of the moon to be measured.

There is a sharp increase in velocity from 0.1km per second at the surface to 5km per second at a depth of 10 kilometres. These figures are consistent with the structure of the moon soil and fragmented rock. As the depth increases the velocity would be expected to increase due to the compacting of the rocks. At a depth of about 25km there is a sudden increase in velocity to 6.8km per second and this continues down to a depth of 65km. Down to 25km the structure is consistent with basalt but from there on to the 65km level there must be some other type of rock. At this level also there is another change in velocity which rises to 9km per second. The geologists working on the projects maintain that this indicates a major structural boundary which may be the junction of the crust and the mantle.

The meteoritic impact revealed that the upper mantle velocity was similar to that of the earth with a velocity of 8.2km per second. If this is so, the moon may have a mantle similar to earth.

The measurements also suggest that there is a core at a depth of about 600km. This is the first direct evidence of a core. Having got so far, the last opportunity for direct observation comes in December with *Apollo 17*. At the moment it would seem that the crust of the moon is twice as thick as that of the earth.

Strictly

by K. Lenton-Smith

ELECTRONIC MUSIC (as distinct from amplified conventional instruments) is often thought to be a relatively modern subject. In one sense it is, if *Music Concrete* is implied. In its real sense, the roots go back nearly 150 years, the recent pace having accelerated through technological advances.

C. G. Page described his music production methods in 1837 in the *American Journal of Science* in an article entitled "The Production of Galvanic Music". In the following year, C. E. L. Delezenne published a paper describing how a contoured iron wheel, rotated in front of an electromagnet, could produce a musical signal.

Professor Thaddeus Cahill patented his Teleharmonium in 1897, consisting of 58 alternators. As amplification was then unheard of, each alternator produced a musical frequency which could be played directly into a telephone system: the sine wave outputs could be mixed to produce various tone colours—so pointing the way for those who were to lay down, some 40 years later, the basic principles behind many modern electronic musical instruments.

MUSIC CONCRETE

The BBC Radiophonic Workshop and Daphne Oram are names that will be familiar to those interested in Music Concrete.

To produce this kind of music a tape recorder with 12 interchangeable capstans is required: with this, any sound may be recorded to produce a chromatic scale, provided that the source frequency is fairly steady. Re-recording this tape at different tape speeds on another machine will provide super- and sub-octaves of the sound source: careful cutting and splicing of these tapes can be done to produce a musical composition containing brilliant arpeggios and other unusual effects. A drum, cymbal (a very complex sound) or even a tap dripping into a basin are typical of the sound sources used in this work.

Rhythmic sounds are normally

produced by tape loops, perhaps using the basic source after its frequency has been taken down several octaves. After rhythm, melody, and special effects have been combined and reverberation added, the end result will either be fascinating or unpalatable—according to one's personal taste.

This type of work calls for several tape recorders and other special equipment, such as variable tone sources, re-iterators and reverberation devices. It is thus somewhat out of the amateur's field, except for the most rudimentary experimentation. The author admires the patience and skill of those prepared to make their music this way, but this type of work is not, of course, Strictly Instrumental.

EARLY INSTRUMENTS

No real progress was made until amplification became a reality. Then, many ingenious inventions followed, most of which are now merely interesting curios.

The Trautonium, developed by Dr Friedrich Trautwein of the Radio Research section at the Berlin Academy of Music, was demonstrated in Berlin in 1930 and created considerable public interest.

The circuitry was fairly simple—an amplified relaxation oscillator: later versions had some tonal variation and an improved fingerboard. It was the electronic equivalent of a one-string-fiddle, the charge-discharge characteristic of the neon tube being the same sawtooth as obtained by drawing a bow over a string.

Another early instrument was the Theremin, which employed the principle of heterodyning two r.f. oscillators to produce an audio beat-note. Frequency variation of one oscillator was achieved by hand capacitance, using a small antenna: the player thus had to "feel" for his pitch, much like a string player. Though rapid passages were impossible, it was effective as a legato, solo instrument: vibrato and glissando were easy to accomplish.

Martenot produced a similar instrument, using a fingerboard to alter capacitance in the inductively coupled circuit.

MONOPHONIC

It is easy to overlook the fact that a number of highly skilled musicians play monophonic instruments (brass and reeds, for example). Whereas the pianist or organist might be disinclined to consider a melody instrument, a monophonic device still has its uses.

The Hammond Solovox came on the scene about 30 years ago and was used by small bands as another solo voice. The fact that it soon had a number of imitators was proof of its success. The small, three-octave keyboard was designed to be fixed adjacent to the upper half of a piano keyboard, the master oscillator covering the entire 37 note range. Three divider stages followed and, with the master oscillator, their outputs were labelled, Soprano, Contralto, Tenor & Bass. Any one—or combination—of these could be switched to a common busbar feeding a series of five tone filters. With a knee-operated swell and controls for attack and vibrato, the Solovox was a useful instrument in any small "combo".

The monophonic instrument can only sound one note at a time (or its suboctaves), whereas the organ/electric piano is fully polyphonic. In looking at earlier instruments, the development of polyphonic instruments has been ignored on this occasion: this is because the youngest member of the monophonic family—the Synthesiser—is important to many of today's musicians and constructors. The last few paragraphs may thus have helped, in a way, to trace its ancestry.

THE SYNTHESISER


From the circuitry point of view, we have come a very long way from the Trautonium! The attraction of the modern synthesiser is, however, the same as it was over 40 years ago—an entirely new sound. Multiple recording can produce existing, and often weird results.

The complexity of voltage controlled oscillators, envelope and noise generators, modulators, etc. means that the polyphonic synthesiser is still a twinkle in the eye of its commercial father. I.C. manufacturers are going through the throes of over-capacity: it may well be that they will turn their attention to simplifying the production of a polyphonic synthesiser at some future date.

look! electronics really mastered

... practical
... visual
... exciting!

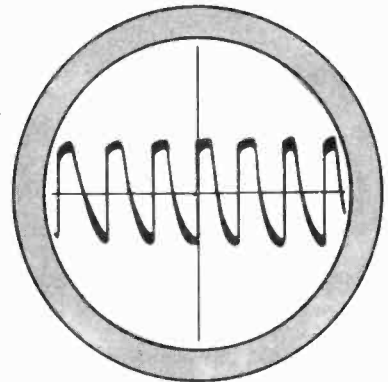no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

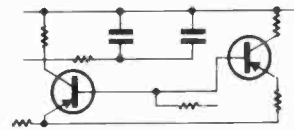2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

To **BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, P.O. BOX 156, JERSEY.** Please send your free brochure, without obligation, to: *we do not employ representatives*

NAME

BLOCK CAPS

ADDRESS

PLEASE EL122

special free gift also to all our students

TAPE HEADS

We are gradually obtaining more information about the Truxov tape heads we have, we're told that these have been wound in a very ingenious way so that winding may be coupled either in parallel or in series depending whether high or low impedance is required. We also have matching erase heads and now offer these in pairs, 1 record and 1 erase head. Price of the 2 track 45p per pair, 4 track 75p per pair. Pair mounted on plate 45p extra.

I.R.P.M. MOTOR

Made by the famous Smith's Company. 240V 50 cycle mains running. Ideal motor to drive clock mechanisms. Price £1 each or 10 for £9.

DRILL CONTROLLER NEW 1KW MODEL

Electrically changes speed from approximately 10 revs. to maximum. Full power at all speeds by finger-tip control. Kit includes all parts, case, everything and full instructions. £1.50 plus 13p post and insurance. Made up model also available. £2.25 plus 13p P. & P.

CONTROL DRILL SPEEDS

MAINS OPERATED CONTACTOR

220/240V 50 cycle solenoid with laminated core so very silent in operation. Closes 4 circuits each rated at 10 amps. Extremely well made by a German Electrical Company. Overall size 2 1/2 in x 2 in x 2 in. £1.50 each.

HIGH ACCURACY THERMOSTAT

Uses differential comparison I.C. with thermistors as probe. Designer claims temperature control to within 1/7th of a degree. Complete kit with power pack £5.50.

AUTO-ELECTRIC CAR AERIAL

with dashboard control switch—fully extendable to 40in or fully retractable. Suitable for 12V positive or negative earth. Supplied complete with fitting instructions and ready wired dashboard switch. £5.75 plus 25p post and insurance.

WATERPROOF HEATING ELEMENT

26 yards length 70W. Self-regulating temperature control. 60p post free.

MULTI-SPEED MOTOR

Replacement in many well-known food mixers. Six speeds are available 500, 850 and 1,100 r.p.m. from either or both of the nylon sockets (where the beaters of the food mixer normally go) and 8,000, 12,000 & 15,000 r.p.m. (ideal polishing speeds) from the main drive shaft. This drive shaft is 3/4 in diameter and approximately 1 1/2 in long. A further point about this motor is that being 230/240V a.c. line series wound its speed may be further controlled with the use of our Thyristor controller. This is a very powerful and useful motor size approx. 2 in dia. x 5 in long, mains 230/240V. Price 85p plus 23p postage and insurance. 12 or more post free.

15A ELECTRICAL PROGRAMMER

Learn in your sleep! Have radio playing and kettle boiling as you awake—switch on lights to ward off intruders—have warm house to come home to. All these and many other things you can do if you invest in an electrical programmer. Clock by famous maker with 15A on/off switch. Switch on time can be set anywhere to stay on up to 6 hours. Independent 60 minute memory jogger. A beautiful unit. Price £1.95 + 20p P. & P. or with glass front chrome bezel 70p extra.

0-8 AMMETER

2 in square full vision for flush mounting. Moving iron instrument. Ideal for charger. Price 60p each. 10 for £5.40.

NUMICATOR TUBES

For digital instruments, counters, timers, clocks, etc. Hi-vac. XN. 3. Price £1.45 each. 10 for £13.

12-WAY SUB-MINIATURE MULTI-CORE CABLE


7/0076 copper cores each core P.V.C. insulated and of different colour. P.V.C. covered overall and approx. 3/16 in thick. Price 20p per yard.

LIGHT CELL

Almost zero resistant in sun—light increases to 10K Ohms in dark or dull light, epoxy resin sealed. Size approx. 1 in dia. by 1/2 in thick. Rated at 600MW, wire ended. 43p with circuit. Also ORP 1 1/2 light cell 45p.

MULLARD 4 + 4 UNILEX AMPLIFIER

We demonstrate these daily and almost always a sale results; it really is a cracking amplifier. Only Mullard with their know how could have made it possible at this low price. SPEC:—Mains operated. 4 watts music or speech per channel. Double wired power supply eliminates cross talk. Harmonic distortion less than 2%. Frequency response 50Hz–16KHz. Input suitable for pick up tuner or microphone. 6 month guarantee. Only £9.95p + 30p postage and insurance.

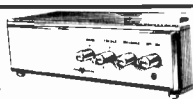

THYRISTOR LIGHT DIMMER

For any lamp up to 1kw. Mounted on switch plate to fit in place of standard switch. Virtually no radio interference. Price £2.95, plus 20p post and insurance.




TANGENTIAL HEATER UNITS

This heater unit is the very latest type, most efficient, and quiet running. Is as fitted in Hoover and blower heaters costing £15 and more. We have a few only. Comprises motor, impeller, 2kW element and 1kW element allowing switching 1, 2 and 3kW and with thermal safety cut-out. Can be fitted into any metal lined case or cabinet. Only need control switch. £3.50. 2kW. Model as above except 2 kilowatts £2.50. Don't miss this. Control Switch 35p. P. & P. 40p.



DISTRIBUTION PANELS

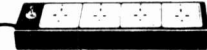Just what you need for work bench or lab. 4 x 13 amp sockets in metal box to take standard 13 amp fused plugs and on/off switch with neon warning light. Supplied complete with 6 feet of flex cable. Wired up ready to work. £2.25 plus 23p P. & P.



THIS MONTH'S SNIP

BATTERY MOTORS. A bargain parcel of 7 motors for £1. Some not as large as a postage stamp and only 2in thick, largest is 1 1/2 in x 1 1/2 in dia. Some work off 1 1/2 V some as high as 18V. These motors are used in racing cars, power toys, etc. The largest is so powerful that it will drive a Mini drill, model lathe, or similar. This is a 4 pole motor, optimum working 16.5V but very powerful even as low as 4V. Don't miss this wonderful snip.




TIMAC 24 hour 15 amp Clock Switch. Self-contained unit for flex connection to the mains. Clock switches 2 on/off per 24 hours. Operates a 15 amp switch. All neatly made up in an ivory moulded case with outlet socket. The only snag is that the outlet socket is the continental type. Plugs for these can be brought in this country alternatively you could fit a connector strip in place of the outlet socket. Overall size of this unit is approx. 4" x 2 1/2" x 3" and the clock has a clear perspex cover which is easily removable for reprogramming. Ideal for picnic controller, etc. Price £2.75 each.

STANDARD WAFER SWITCHES

Standard size 1 1/2 in wafer—silver-plated 5-amp contact, standard 2 in spindle 2 in long— with locking washer and nut.												
No. of Poles	2 way	3 way	4 way	5 way	6 way	8 way	9 way	10 way	12 way	13 way	14 way	15 way
1 pole	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p	40p
2 poles	40p	40p	40p	40p	40p	40p	40p	40p	40p	70p	70p	70p
3 poles	40p	40p	40p	40p	40p	70p	70p	70p	70p	95p	95p	95p
4 poles	40p	40p	40p	40p	70p	70p	70p	70p	70p	1.20	1.20	1.20
5 poles	40p	40p	70p	70p	95p	95p	95p	95p	1.45	1.45	1.45	1.45
6 poles	40p	70p	70p	70p	95p	95p	95p	95p	1.70	1.70	1.70	1.70
7 poles	70p	70p	70p	95p	1.20	1.20	1.20	1.20	1.95	1.95	1.95	1.95
8 poles	70p	70p	70p	95p	1.20	1.20	1.20	1.20	2.20	2.20	2.20	2.20
9 poles	70p	70p	95p	95p	1.45	1.45	1.45	1.45	2.45	2.45	2.45	2.45
10 poles	70p	70p	95p	1.20	1.45	1.45	1.45	1.45	2.70	2.70	2.70	2.70
11 poles	70p	95p	95p	1.20	1.70	1.70	1.70	1.70	2.95	2.95	2.95	2.95
12 poles	70p	95p	95p	1.20	1.70	1.70	1.70	1.70	3.20	3.20	3.20	3.20

MULLARD AUDIO AMPLIFIER MODULE

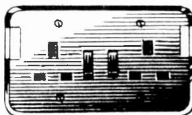Uses 4 transistors, and has an output of 500mW into 8 Ohms speakers. Input suitable for crystal mic, or pick-up. 9V battery operated. Size 2 in long x 1 1/2 in wide x 1 in high. SPECIAL SNIP PRICE 60p each. 20 for £5.40.



13 AMP TWIN GANG SOCKETS

Offered at less than wholesale price your opportunity to replace those dangerous adaptor—brown bakelite flush mounting—standard fitting. Unswitched 20p each, separately switched 30p each. Separately switched and with neon on/off indicators 45p each. Less 10% ten or more + 20p postage if order under £5.

INTEGRATED CIRCUIT BARGAIN

A parcel of integrated circuits made by the famous Plessey Company. A once-in-a-lifetime offer of Micro-electronic devices well below cost of manufacture. The parcel contains 5 ICs all new and perfect, first-grade device, definitely not sub-standard or seconds. 4 of the ICs are single silicon chip GP amplifiers. The 5th is a monolithic NPN matched pair. Regular price of parcel well over £5. Full circuit details of the ICs we included and in addition you will receive a list of many different ICs available at bargain prices 25p upwards with circuits and technical data of each. Complete parcel only £1 post paid. DON'T MISS THIS TERRIFIC BARGAIN.

MULLARD I.F. MODULE

MULLARD AUDIO AMPLIFIERS. All in module form, each ready built complete with heat sinks and connection in price 25p upwards. Data supplied. Model 1153 500m watt power output 75p. Model 1172 750m watt power output 85p. Model EP9000 4 watt power output £1.45p. 10% discount if 10 or more ordered.

Where postage is not stated then orders over £5 are post free. Below £5 add 20p. Semi-conductors add 5p post. Over £1 post free. S.A.E. with enquiries please.

POCKET CIRCUIT TESTER

Test continuity of any low resistance circuit, house wiring, car electric. Test polarity of diodes and rectifiers. Also ideal sign for conversion to signal injector (circuit supplied). 30p or 2 for 60p post paid.



AMPLIFIER IN CASE WITH SPEAKER

Marketed by British Relay under the name Luxitor. This is in a very neat looking cabinet and is ideal around the home or in the workshop for trouble shooting or for testing out a quick lash up. Size approx. 9 1/2" x 6 1/2" x 3 1/2" deep. Input is via a matching transformer and volume control and amplifier may be powered by an internal 9v battery or an external 110v source. Speaker is an R-A elliptical 6 1/2" x 3 1/2" 10,000 gauss. The amplifier proper is a Newmarket model Ref. P.C.4. Price £3.50 each, 10 for £31.50. Post and insurance 20p.

BAKELITE INSTRUMENT CASE

Size approx. 6 1/2" x 3 1/2" x 2 1/2" deep with brass inserts in four corners and bakelite panel. This is a very strong case suitable to house instruments and special rigs, etc. Price 45p each.



TELEPHONES

Complete as illustrated. Save your legs, time and temper, simply by putting in some telephones. Ex-G.P.O. not new—but guaranteed in good condition and serviceable. Supplied with diagram and instructions showing how to connect. Price 75p each + 30p post or 2 for £2 post paid. Also available separately, dials and handsets 50p each + 20p post.



ROCKER SWITCH

13 amp self-fixing into an oblong hole. Size approximately 1" x 1" 6p each, 10 for 64p.



SLIDE SWITCHES

Slide Switch, 2-pole changeover panel mounting by two 8BA screws. Size approx. 1 in. x 1 in. rated 250V lamp. 6p each, 10 for 64p. 10 for £5-10, 500 for £24. Ditto as above but for printed circuit 5p each, 10 for 45p. 100 for £4.25. 500 Miniature Slide Switch, DPDT 19mm (1 in. approx.)—with fixing centres. 15p each or 10 for £1.05.

EDUCATIONAL KITS—all with pictorial instructions

THIS BALANCE KIT FREE Eagle educational kits, Japanese made these are excellent value for money. We do not expect to be able to repeat this offer once stocks are sold. Brief description of each kit is given below and with 3 kits or more we give FREE an accurate 11 piece balance kit. Price of kits 40p each post paid. Special price for all 8 kits £3 with free balance kit. **KA2 Lens Kit.** Eleven parts, including candle one concave lens, one convex lens, stand and slit frame, etc. Watch light rays bend as they pass through different lenses. **KA3 Water Pump Kit.** Thirteen parts. Top of pump is transparent so that operating parts may be observed. Small parts are brightly coloured to be seen easily while working. Thirteen parts of pump may be made: Lift pump, Force Pump and Force Pump with reservoir and nozzle. **KA4 Burner Kit.** Eleven parts. Transparent covers allow the operation of burner to be seen. Illustrates and teaches how electromagnetism with an automatic switch results in an operating buzzer. **KA6 2-Pole Motor Kit.** Twenty-four parts including enamel wire, armature and pole piece, etc. Motor operates from 1 1/2 volt battery. Illustrates and teaches how electro-magnetism operates a motor. **SP Change over spring return 250V 1 amp 10p.** **KA7 Electro-Magnet Kit.** Fifteen parts, includes compass. Makes two electro-magnets, one with one layer of wire and one with several layers of wire. Picks up tacks, nails and any small parts showing how magnetism works. **KA8 Current and Resistance Kit.** Twenty-nine parts, including bench and light bulb. Conduct interesting and educational projects to learn the application of "OHM'S LAW" and see the difference in current and resistance with different types and lengths of wire. **KA9 Bell Kit.** Eight parts, including bell and push button switch. Build a complete electric bell and see how the hammer is triggered to make the bell ring. **KA10 Morse Key trigger and bell kit.** 25 part kit easy to construct, simple to operate.



J. BULL (ELECTRICAL) LTD.

(Dept. P.E.) 7 Park Street, Croydon CRO 1YD
Callers to 102/3 Tamworth Road, Croydon.

Designing with

Integrated Circuits

BY A. FOORD

3 Basic Operational Amplifiers

AN operational amplifier is essentially a high gain direct coupled amplifier which makes use of positive or negative feedback to control its overall characteristics. Originally the term operational amplifier denoted a circuit which performed a mathematical operation (such as, summation, differentiation, integration) in analogue computing. However, their applications are now extended to cover many fields; instrumentation and measurements are but two examples.

The required overall response of an operational amplifier is usually obtained by connecting feedback components externally from the output terminal back to the inputs. A differential input allows a considerable flexibility in the feedback configuration and also allows a reduction in d.c. drift because of the close matching of the input characteristics.

BASIC FORM

The basic form of the operational amplifier feedback circuit, illustrated in Fig. 3.1, shows that the voltage at the virtual earth (or summing point) is very small and tends to zero for an infinitely large amplifier gain.

For this type of circuit where the output is fed back towards the input in such a way as to reduce it, the overall characteristics become almost independent of A (the gain of the amplifier without feedback). The assumptions in the formula are that e is zero, no current flows into the amplifier terminals, and that A is much greater than G (the overall gain with feedback).

Summation of currents at the virtual earth point must always be zero. The overall gain is given by:

$$G = \frac{V_o}{V_i} = - \frac{R_2}{R_1}$$

The minus sign indicates a phase inversion.

Amplifiers of this type have a considerable isolation between input and output and many variations are

GLOSSARY

OPERATIONAL AMPLIFIER A low frequency amplifier, often used to perform mathematical operations.

DIFFERENTIAL INPUT An input applied between two input terminals.

VIRTUAL EARTH Low impedance signal point.

OFFSET ERRORS Errors produced by voltage or current imbalance in the input stages.

COMMON MODE INPUT RANGE The maximum signal which can be applied simultaneously to both inputs.

possible. The input impedance is equal to R_1 . If R_1 equals R_2 the circuit gives unity gain where a sign change (inversion) is required.

INVERTING AMPLIFIER AND ADDER

If a separate resistor is used for each input, as in Fig. 3.2, then current summing occurs at the virtual earth, with excellent isolation between inputs. For the first input the gain is

$$G = - \frac{R_{FB}}{R_1}$$

Therefore

$$V_o = - \left\{ \left(\frac{R_{FB}}{R_1} \right) V_1 + \left(\frac{R_{FB}}{R_2} \right) V_2 + \left(\frac{R_{FB}}{R_3} \right) V_3 + \dots \right\}$$

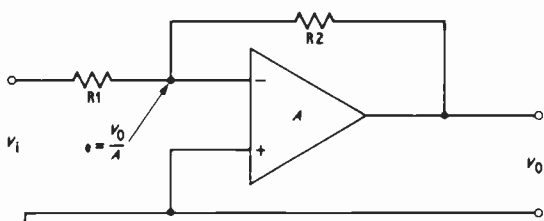


Fig. 3.1. Basic form for an operational amplifier

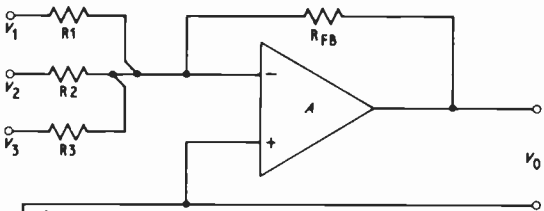


Fig. 3.2. Virtual earth addition amplifier

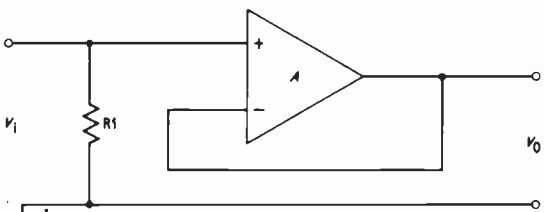


Fig. 3.3. Unity gain follower amplifier

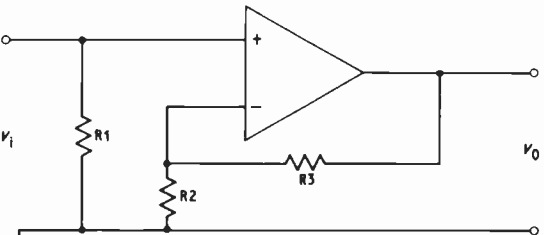


Fig. 3.4. Non-inverting amplifier with gain

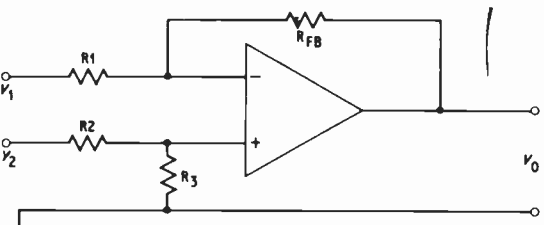


Fig. 3.5. Differential amplifier

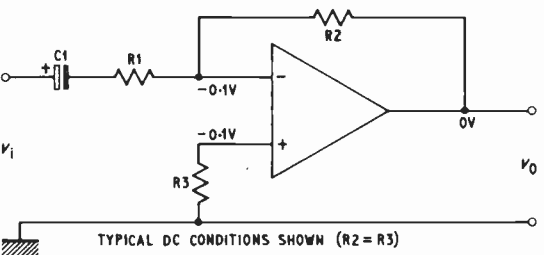


Fig. 3.6. AC coupled inverting amplifier



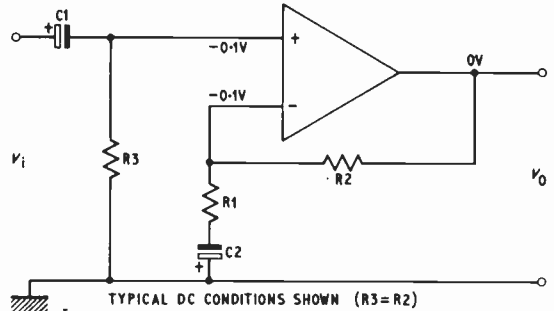



Fig. 3.7. AC coupled non-inverting amplifier
The amplifier input bias current in Figs. 3.6 and 3.7 provides the voltage drop across the resistors R2 and R3. Since this current is low, then low leakage capacitors are essential

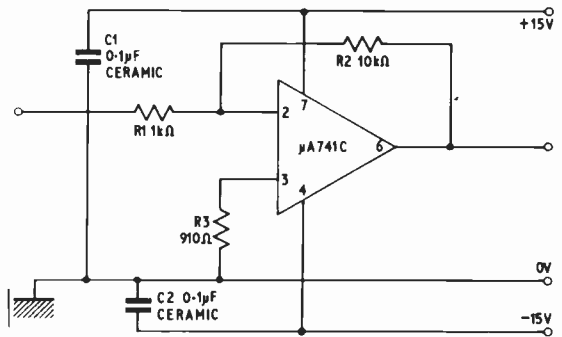

(a) DIRECT COUPLED

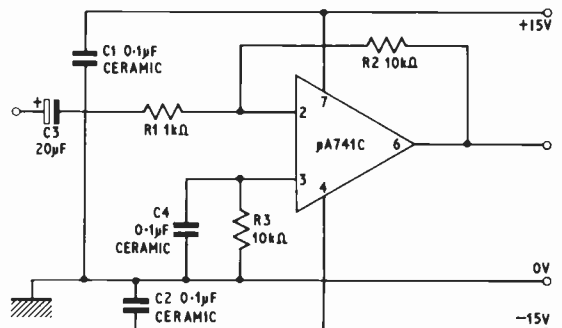

(b) AC COUPLED, DUAL SUPPLIES

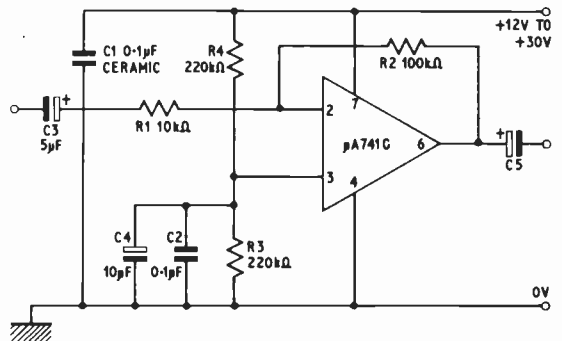

(c) AC COUPLED, SINGLE SUPPLY

Fig. 3.8. Practical inverting amplifiers with ten times gain

NON-INVERTING AMPLIFIER

For a non-inverting amplifier the input is connected to the non-inverting terminal of the i.c., while negative feedback is applied as shown in the diagrams. Feedback is now effectively in series with the input signal and care must be taken to make sure that the common mode input range of the amplifier is not exceeded.

A unity gain follower is shown in Fig.3.3 where all the output voltage is fed back in series with the input.

This gives a high input impedance, a low output impedance, and unity gain. The non-inverting amplifier with gain (Fig. 3.4) also has a reasonably high input impedance. The gain for this arrangement is

$$G = \frac{R_2 + R_3}{R_2} = 1 + \frac{R_3}{R_2}$$

DIFFERENTIAL AMPLIFIER

The amplifier in Fig. 3.5 uses both inputs to amplify the difference between two signals. The gain can be equal to, greater than, or less than unity.

$$V_O = \frac{R_{FB}}{R_1} (V_2 - V_1)$$

D.C. CONDITIONS

The amplifiers are designed to run from both positive and negative supplies with both input terminals and output terminal near earth potential (for a zero input signal) so that direct coupling can be used.

To maintain the correct d.c. conditions the amplifiers require a resistor from the output to the inverting input and a resistor from the non-inverting input to ground. Each input terminal should have the same d.c. source resistance to minimise the effects of input voltage and current offsets.

A.C. AMPLIFIERS

Although the amplifiers are basically designed for direct coupled use they are equally suitable for a.c. applications. In these cases d.c. blocking capacitors are used in the signal paths. When electrolytics are used, care must be taken with the d.c. biasing conditions since many circuits maintain little or no bias across the capacitors.

Low leakage tantalum capacitors are preferred, or two high grade electrolytics may be used back to back. This problem can sometimes be avoided by using a single supply rail.

For the inverting amplifier circuit of Fig. 3.6 the input impedance is equal to R_1 and the low frequency bandwidth is determined by R_1 and C_1 . For the non-inverting amplifier in Fig. 3.7 the input impedance is approximately equal to R_3 .

PRACTICAL CIRCUITS

Some practical circuits for a.c. and d.c. use with a 741C integrated circuit (or equivalent) are shown in Figs. 3.8 and 3.9. The connections given are for the TO5 version. The ceramic decoupling capacitors should be connected as close to the integrated circuit as possible. The capacitors in the a.c. coupled circuits with dual supplies only have a small bias across them and should be tantalum types.

Next month: Part 4 looks at one of the most useful i.c.s, the Schmitt trigger.

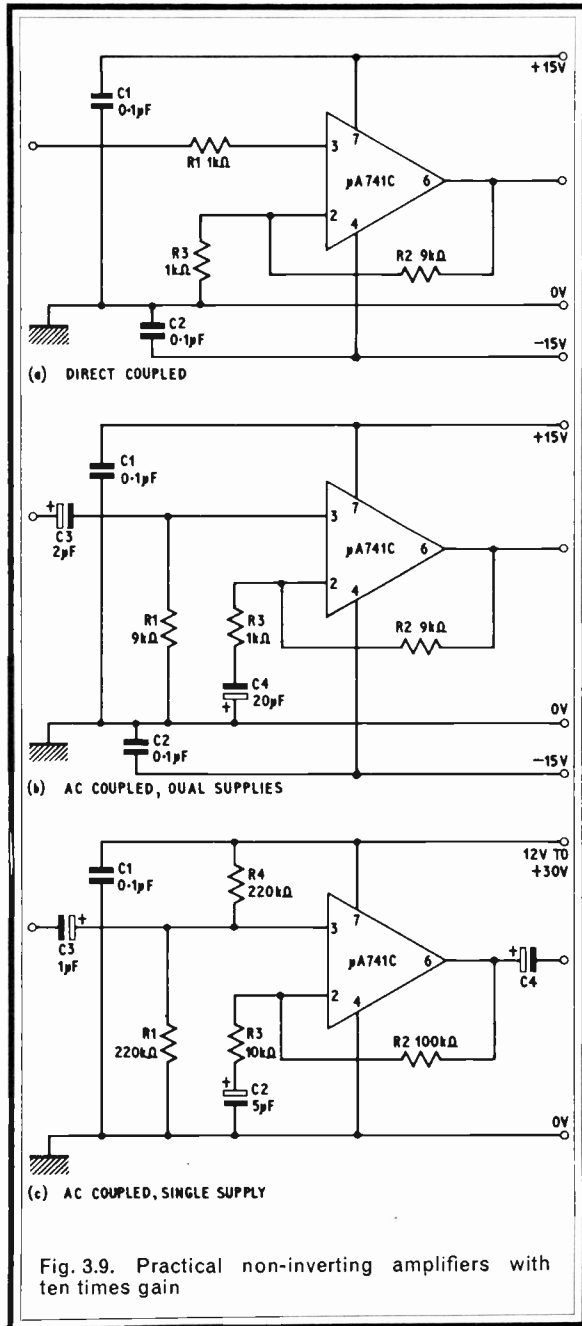


Fig. 3.9. Practical non-inverting amplifiers with ten times gain

BINDERS

Binders for P.E. are available price £1, including postage and packing. State Volume Number required.

Orders for Binders should be addressed to Binding Dept., IPC Magazines Ltd., 68, Great Queen Street, London, W.C.2.

HOOTING OWL



By A. R. Cuff

Simple to build and capable of endless variations, this toy will provide hours of amusement for children and adults alike.

THIS project describes some simple circuits for producing sounds which somewhat resemble the cries of small animals. It should interest readers who are looking for something amusing, which is easily constructed, and can be used to intrigue their friends.

The "owl" described here is just one of a large number of possible variations of the basic design and makes an ideal present for children or the girl friend.

Because the idea is so versatile it can be made simple for beginners or rather more complex for advanced constructors; in fact this is a very good first project as there are no problems with tolerances or setting up, and only the cheapest components need be used.

The finished animal can be made extremely attractive if a little care is taken with the external detail.

THE SIMPLE MODEL

The basic element in all the units is the astable multivibrator which is used in various combinations to produce a wide variety of animal and bird sounds.

In the simplest design as shown in Fig. 1 a single note astable is turned on and off by a mercury switch. The mercury switch (for those who have not encountered them before) is a sealed tube containing mercury which is free to move about. Two contacts sealed into the glass form a switch which is only closed when the mercury covers both. Thus when this switch is used in the model animal it can be arranged so that the animal only emits a noise when tilted.

Also shown in Fig. 1 is a capacitively-coupled single-transistor amplifier to provide sufficient volume to operate a small 8 ohm speaker, and also to avoid excessive loading of the oscillator.

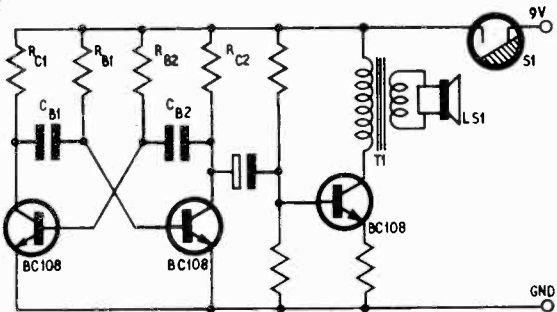


Fig. 1. With just a simple multivibrator and amplifier a toy animal can be built which emits a squeak each time it is lifted

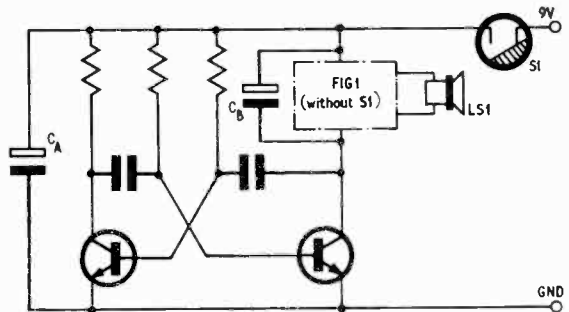


Fig. 2. With two multivibrators in cascade, a more complex sound is produced somewhat resembling the miaow of a cat

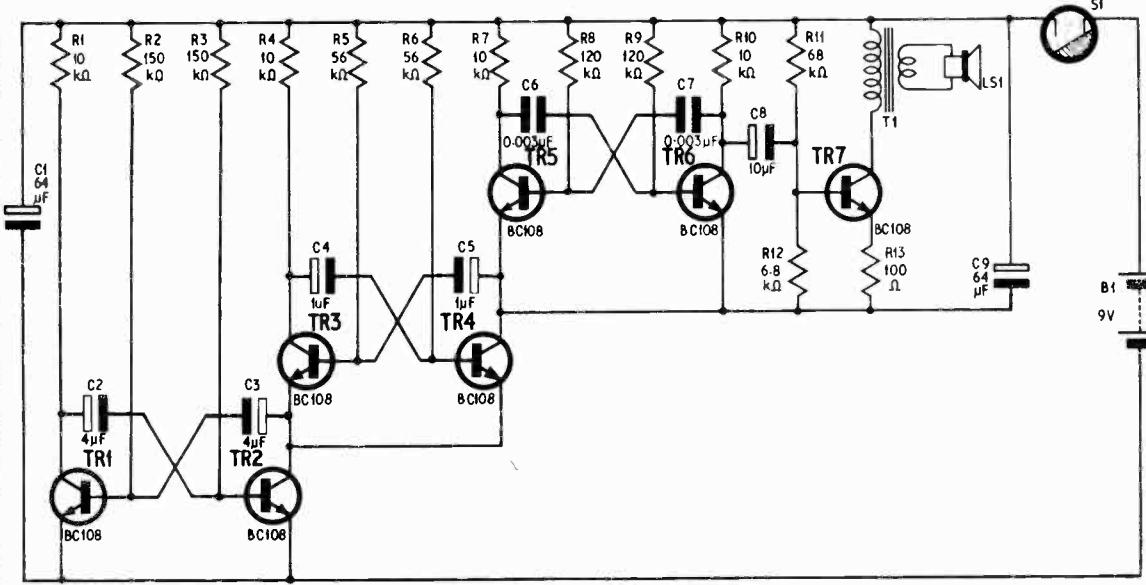


Fig. 3. With three multivibrators in cascade the owl sound can be produced. Variation of the base resistors or capacitors in any or all of the multivibrators will produce different sounds

Thus the creature remains silent until picked up when it mysteriously squeaks!

MULTIVIBRATOR DESIGN

In order to successfully design the astable of Fig. 1, two important points must be kept in mind. Firstly, that the frequency of the oscillation is given by the expression

$$f(\text{Hz}) = \frac{1}{0.69(R_{B1} \times C_{B1} + R_{B2} \times C_{B2})}$$

so that the approximate frequency must be decided before construction is started (1kHz gives a pleasing tone).

Secondly, to ensure oscillation the value of the base resistors must be small enough to provide sufficient base current to cause saturation of their respective transistors.

This can be written as $R_B \leq h_{FE} \times R_C$ where h_{FE} is the current gain of the transistor.





However, since most constructors will be unable to measure the current gain it is safer to ensure that the base resistors are not more than 10 to 15 times the value of the collector resistors, especially if unmarked transistors are to be used. Thus if R_C is 10 kilohms then R_B should not exceed 150 kilohms.

For the sake of simplicity the base resistors are made equal in this circuit.

ADDING SOPHISTICATION

The next step to improve the sound effect is to add a second astable as shown in Fig. 2.

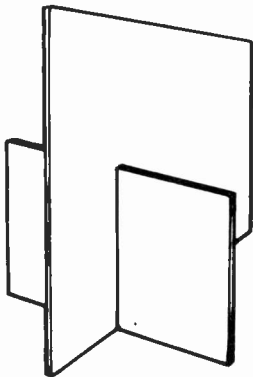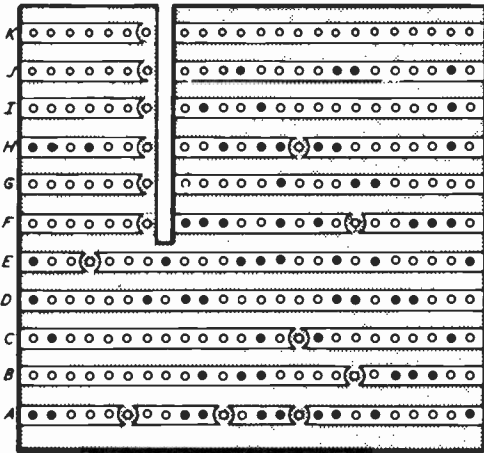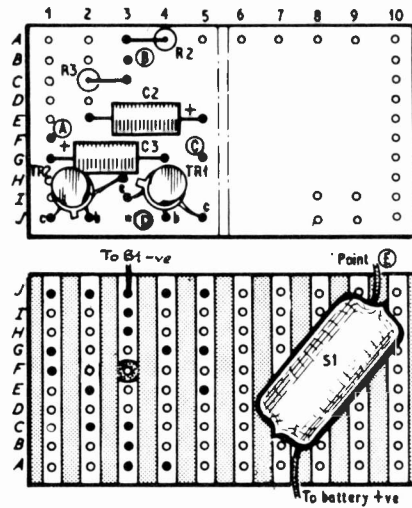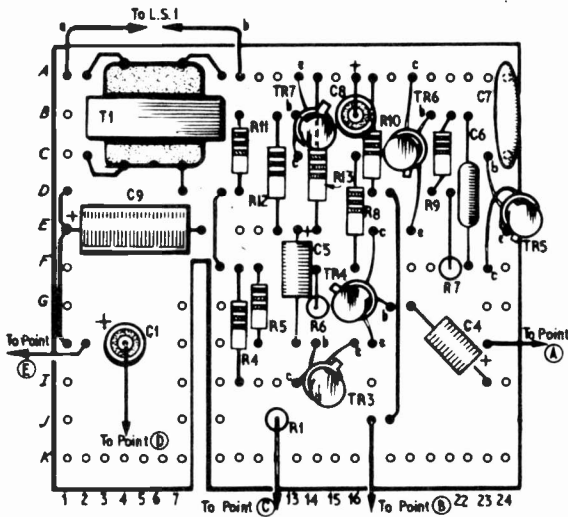In this version the entire circuit of Fig. 1 is used as the collector load for another, slower astable. The frequency at which this circuit oscillates can be varied from about 1Hz to approximately half the



The boards are slotted together and glued to the lid

Fig. 4. Layout of the components on the Veroboard panels. (Standard Veroboard was not used in the prototype. Miss alternate tracks if this layout is followed.)

COMPONENTS . . .

Resistors

- R1 10k Ω
- R2, R3 150k Ω (2 off)
- R4 10k Ω
- R5, R6 56k Ω (2 off)
- R7 10k Ω
- R8, R9 120k Ω (2 off)
- R10 10k Ω
- R11 68k Ω
- R12 6.8k Ω
- R13 100 Ω
- All $\frac{1}{4}$ W \pm 10% carbon

Capacitors

- C1 64 μ F 10V elect.
- C2, C3 4 μ F 10V elect. (2 off)
- C4, C5 1 μ F 10V elect. (2 off)
- C6, C7 0.003 μ F (2 off)
- C8 10 μ F 10V elect.
- C9 64 μ F 10V elect.

Transistors

- TR1-7 BC108 or similar (7 off)

Transformer

- T1 Transistor audio output transformer (Eagle LT700 or similar)

Switch

- S1 Mercury switch

Miscellaneous

- LS1 2 $\frac{3}{4}$ in 8 Ω speaker
- B1 9V battery type PP3
- 0.1in matrix Veroboard, custard tin (or similar), felt or other suitable material for decoration

FREE

*Information on our sophisticated but low-cost kits . . .

*New 1214 Audio Range. Build your system in a few evenings.

*New loudspeaker range.

*Unbeatable quality and specifications.

*Incredibly good value for your money.

*New continuous credit and no-deposit terms. Even includes instruments.

*Over 30 new models.

*Over 130 models in range.

*Packed full of invaluable information about the world's finest electronics . . .

It's New. It's the biggest Audio/Instrument kit catalogue in the U.K. And it's absolutely FREE.

Our new jumbo size Heathkit catalogue is full of good things: low-cost Testers and Instruments, Metal Detectors, Electronic Calculator, Intercoms., Amplifiers, Tuner/Amplifiers, Tuners and Loudspeakers – there's even a Battery Charger.

You name it, Heathkit can supply. What's more, you can build everything yourself. Heathkit help you each step of the way. Simply follow the Heathkit step-by-step construction manual. It's like painting by numbers but with something unique at the end of it. Fantastically satisfying, and less expensive than buying readymade. Our products are advanced in specification and performance. And they're regularly reviewed by leading journals. You have to be good to merit that sort of treatment.


We guarantee that by using the Heathkit step-by-step construction method you can build a piece of electronic equipment without needing to know the first thing about electronics.

Mail the coupon today for your copy of the free Heathkit catalogue. The kits shown take just one or two evenings, and we promise that whichever kit you choose it'll be more rewarding than washing the car or watching television.



Want to know more?

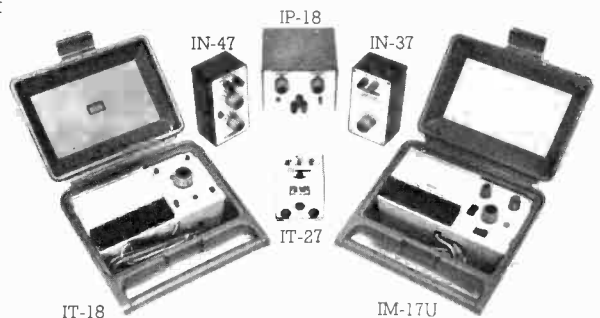Mail the coupon for a **FREE CATALOGUE**. Don't forget . . . This includes Instruments and low-cost Testers.



Why not visit your Heathkit Electronics Centres . . . and see our Instruments and Testers.

London 233 Tottenham Court Road. Telephone: 01 636 7349
Open hours: Monday – Saturday 9-6.00 p.m.

Birmingham 17-18 St. Martin's House, Bull Ring.
Telephone 021 643 4388 Open hours: Friday – Saturday 10-5.30 p.m.

Gloucester Cole Avenue Roundabout, Bristol Road.
Telephone 045229451 Open hours: Monday – Friday 9-5.00 p.m.
Saturday 9-12.30 p.m.

Please send me the FREE New 1972 Heathkit catalogue

Name

Address.....



HEATH (Gloucester) Ltd.,
Dept. PE 12/72
Gloucester GL2 6EE

VARIABLE VOLTAGE TRANSFORMERS

INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V
All Types

from 1 to 50 amp from stock.

SHROUDED TYPE

1 amp, £7-00
1.5 amp, £8-05
5 amp, £11-75
10 amp, £22-50
15 amp, £25-00

20 amp, £49-00
25 amp, £58-00
37.5 amp, £82-00
50 amp, £98-00

(Panel Mounting) 1/2 amp, £4-75.
1 amp, £7-00. 2 1/2 amp, £8-05. All carriage paid.



2.5 amp OPEN TYPE

12 VOLT D.C. MOTOR

Powerful 1 amp. REVERSIBLE motor. Speed 3,750 r.p.m. complete with external gear train (removable) giving approx. final speed of either 125 r.p.m. or 240 r.p.m. Size: 4 1/2 in x 2 1/2 in dia. Either type price 95p inc. post.



230/240V COMPACT SYNCHRONOUS GEARED MOTORS

Manufactured by either Sangamo, Haydon or Smith. Built-in gearbox. 1 r.p.m. cw. 1 r.p.h. a/cw. 12 r.p.h. cw. 12 r.p.h. a/cw. 20 r.p.h. cw. 20 r.p.h. a/cw. cw. = clockwise rotation; a/cw. = Anticlockwise. Fraction of makers' price. All at 75p P. & P.



REVERSIBLE SPLIT PHASE MOTOR

250 r.p.m. 100/115/210-240V a.c. 2in x 1 1/2 in. Ideal for rim-drive motors, display, etc. Extremely powerful for size inc. small capacitor. 75p post paid.


CONSTANT SPEED, PRECISION MADE 6 VOLT D.C. GOVERNED MOTOR

Seven pole armature, ballrace bearing. 2,750 r.p.m. Length 2 1/4. Dia. 1/2. Shaft length 3/8. Shaft dia. 5/64. No load 40 mA. Normal load 350 mA. Ideal for portable recorders, etc., etc. Price £1-25 P. & P.




PARVALUX TYPE SD19 230/250 VOLT A.C. REVERSIBLE GEARED MOTORS

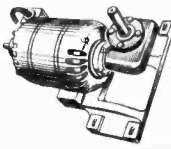30 r.p.m. 40 lb. spindle. Position of drive spindle adjustable to 3 different angles. Mounted on substantial cast aluminium base. Ex-equipment. Tested and in first-class running order. A really powerful motor offered at a fraction of maker's price. £6-30. P. & P. 50p.



PARVALUX Type: SD15/86896(C) 230/250V A.C. 50 r.p.m. 7 lb/1 in.

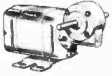Continuously rated. Less base. £6. P. & P. 30p.
TYPE: SD15/89400/OM 230/250V A.C. 50 r.p.m. 22 lb/in. Continuously rated. Incl. base. £7. P. & P. 30p.
The above motors are new and unused.



PARVALUX TYPE SD2. 200/250 VOLT A.C./D.C. HIGH SPEED MOTOR


Speed 9,000 r.p.m. approx. or 3,200 r.p.m. if used with built-in governor, or variable speed over a wide range if used in conjunction with our Dimmer Switch, illustrated below. PRICE £1-75. P. & P. 25p.



600 WATT DIMMER SWITCH. Easily fitted. Fully guaranteed by makers. Will control up to 600W of all lights except fluorescent at mains voltage. Complete with simple instructions. £3 incl. P. & P.

UNISELECTOR SWITCHES

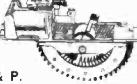NEW 4 Bank 25 Way 24V d.c. operation. £5-88. P. & P. 25p.
6 Bank 25 Way 24V d.c. £6-50. P. & P. 25p.
8 Bank 25 Way, 24V d.c. operation. £7-62 plus 25p. P. & P.



INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size 1 1/2 in. W. 4 in. H. 6 in. weight 6lb. 1,000V, 1,000 megohms, £34-00 carriage paid.
500V, 500 megohms, £28 incl. P. & P.



PROGRAMME TIMERS



240V A.C. 5 r.p.m. motor. 2 models available with either 10 or 15 cams. Each cam operating a 10 amp c/o micro switch. Cams are individually variable, allowing innumerable combinations. Ideally suited for machinery control, automation, etc. Also in the field of entertainment, for chaser lights, animated displays, etc. NEW 10 cam £4-75 P. & P. 25p. 15 cam £5-75 P. & P. 25p.

2 CAM PROGRAMMER

Crouzet 15 r.p.m. 240V. A.C. motor, drives 2 individually adjustable cams. Each cam operates 2 c/o micro switches. Mfg. Honeywell. £1-75 P. & P. 20p.

24-HOUR TIMER

Can be adjusted to give a switching delay of between 1 hr. to 24 hrs. Driven by 200/250V A.C. synchronous motor. 15 amp c/o contacts. Mfg. Crater Controls Ltd. Supplied with scale calibrated 0-12 (2 hrs. per division). Brand New. £1-75. P. & P. 25p.



STROBE! STROBE! STROBE!

Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 36 Flash per sec. All electronic components including Veroboard S.C.R. Unijunction Xenon Tube and instructions £6-30, plus 25p P. & P.

NEW INDUSTRIAL KIT

Ideally suitable for schools, laboratories, etc. Roller tin printed circuit. New trigger coil, plastic thyristor. Speed adjustable 1-80 f.p.s. Price £10-50. P. & P. 50p.

HY-LYGT STROBE MK III

Designed and produced for use in large rooms, halls and the photographic field and utilises a silica tube, printed circuit, also a special trigger coil. Speed adjustable 0-30 f.p.s. Light output approx. 4 joules. £12-00. P. & P. 50p. **SPECIALLY DESIGNED.**

THE 'SUPER' HY-LYGT KIT

Approx. four times the light output of our well proven Hy-Lyght strobe. Incorporating:

- Heavy duty power supply
- Variable speed from 1-23 flash per sec.
- Reactor control circuit producing an intense white light.

Never before a Strobe Kit with so HIGH an output at so LOW a price. **ONLY £20 plus 75p P. & P.**

ATTRACTIVE, ROBUST, FULLY VENTILATED METAL CASE specially designed for the Super Hy-Lyght Kit including reflector £7-00 P. & P. 45p.


For Hy-Lyght Kit including reflector. £4-00
7-inch POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 53p. P. & P. 13p or post paid with kits.

RAINBOW STROBE FOUR LIGHT CONTROL MODULE

In response to numerous requests, we now offer a mains operated fully isolated short-circuit-proof ready-built module, with variable flash rate. It will operate four of our Hy-Lyght or Super Hy-Lyght Strobes in either 1, 2, 3, 4 sequence; 2 + 2; or all together. Fantastic effects with or without colour filters. Modules can be connected together to operate 8 or 12 Strobes. Will work on long runs of up to 50 yards, so that your Strobes can be spaced out for maximum effect. Size of module is 5 x 6 1/2 in. Easily fitted into your own equipment, or into a separate case. Thoroughly tested and reliable. Complete with full connection instructions. Price, £18-50 plus 25p P. & P. Send S.A.E. for details.

COLOUR WHEEL PROJECTOR

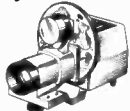Complete with oil filled colour wheel. 100W lamp. 200/240V a.c. Features extremely efficient optical system. £18-50 plus 35p P. & P.



6 INCH COLOUR WHEEL

As used for disco lighting effects, etc. £5-75 incl. P. & P.

BIG BLACK LIGHT

400W. Mercury vapour ultra violet lamp. Outer bulb designed to absorb visible light and transmit Long wave U.V. rays. Extremely compact and powerful source of U.V. rays. Ideal for stage, display, discos, etc. A P.F. ballast is essential with these bulbs. Price of matched ballast and bulb £16. P. & P. 50p. Spare bulb £7. P. & P. 30p.



Superior Quality Precision Made NEW POWER RHEOSTATS



100 WATT. 1 ohm, 10A; 5 ohm, 4.7A; 10 ohm, 3A; 25 ohm, 2A; 50 ohm, 1.4A; 100 ohm, 1A; 250 ohm, 0.7A; 500 ohm, 0.45A; 1 kΩ, 280 mA; 1.5 kΩ, 230mA; 2.5 kΩ, 2A; 3.5kΩ, 5 kΩ, 140mA. Diameter 3/8 in. Shaft length 1/2 in. dia. 1/2 in. All at £1-65 each. P. & P. 75p.
50 WATT. 1/5/11/25/50/100/250/500/111/1-5/2-5/5kΩ. All at £1-15 each. P. & P. 75p.
25 WATT. 10/25/50/100/250/300/500/111/1-5/2-5/3/5/5kΩ. All at 90p each. P. & P. 75p.
Black Silver Skirted knob calibrated in Nos. 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats, 18p ea.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Coil (ohms)	1	2	3	4
Coil (1)	52	3-6	2 c/o	63p*
Coil (2)	67	4-8	3 c/o HD	78p
Working d.c. volts	410	10-18	4 c/o	73p*
	600	12-24	4 c/o	78p*
	700	16-24	4M 2B	63p*
Coil (3)	700	16-24	4 c/o	78p*
Contracts	700	15-35	2 c/o HD	73p*
	700	16-24	6M	65p*
Coil (4)	700	6-12	1 c/o HD	50p*
Price	700	20-30	6 c/o	75p
	1,250	24-36	4 c/o	63p*
HD =	2,500	36-45	6M	63p*
Heavy duty	2,400	30-48	4 c/o	50p*
Incl. Base	9,000	40-70	2 c/o	30p
Post paid.	15k	85-110	6M	50p*

12 VOLT D.C. RELAY 140 ohm coil

Type 1: Three sets c/o contacts rated at 5 amps. 78p incl. P. & P. (Similar to illustration below)

Type 2: One set of c/o contacts. 60p incl. P. & P.

'DIAMOND H' 230 VOLT A.C. RELAYS (Unused)

Three sets c/o contacts rated at 5 amps. PRICE: 50p. P. & P. 10p. (100 lots £40 including P. & P.)



230 VOLT A.C. RELAYS MFG. KEY SWITCH

One set c/o contacts rated at 7.5 amps. Boxed. PRICE: 40p. P. & P. 5p. (100 lots £32 incl. P. & P.)

MINIATURE LATCHING RELAY

Manufactured by Clare-Elliott Ltd. Type F: 2 c/o permanent latching in either direction. Coil 1150 ohm, 15-30 Volt D.C. Size 7/8 high, 2 1/2 wide, 1 1/2 thick. Complete with 3 leads. New 73p, incl. P. & P.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1 1/2V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3. P. & P. 22p.

50 IN 1 ELECTRONIC PROJECT KIT

50 easy to build Projects. No soldering, no special tools required. The kit includes Speaker, Meter, Relay, Transformer, plus a host of other components and a 56-page instruction leaflet. Some examples of the 50 possible Projects are: Sensitive Meter, 2 Transistor Radio, Amplifier, etc. Price £7-75. P. & P. 30p.

DOUBLE ENDED BLOWER UNIT

Powerful, continuously rated, 2-speed. Blades easily removable. Either 6 or 12 volt D.C. operation. PRICE £1-75. P. & P. 25p.



MOTOROLA MAC II/6 PLASTIC TRIAC 400 PIV. 10 AMP

Now available **EX STOCK**. Supplied with full data and applications sheet. Price £1-05. P. & P. 7p. Suitable DIAC (RCA 40583) 30p each.

'HONEYWELL' PUSH BUTTON, PANEL MOUNTING MICRO SWITCH ASSEMBLY

Each bank comprises a c/o rated at 10 amps 240V. A.C. Black knob in. Fixing hole 1/2 in. ONE bank 30p; TWO bank 40p; THREE bank 55p; incl. P. & P. Quot. for quantity.



'HONEYWELL' LEVER OPERATED MICRO SWITCH

15 amps 250 volt A.C. c/o contacts. Types N39, N95, N100, N101 NEW in maker's carton. PRICE: 10 for £1-90 incl. P. & P.



Very special offer MICRO SWITCH

5 amp c/o contacts. Fitted with removable push button assembly. Ex. P.O. 20 for £1 inc. post. (Min. order 20.)

D.C. AMMETERS NEW!

1A, 5A, 15A, 20A, £1-75, incl. P. & P. 0-300V a.c., £1-90, incl. P. & P.



All Mail Orders—Callers—Ample Parking
Dept. PE11, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.

SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

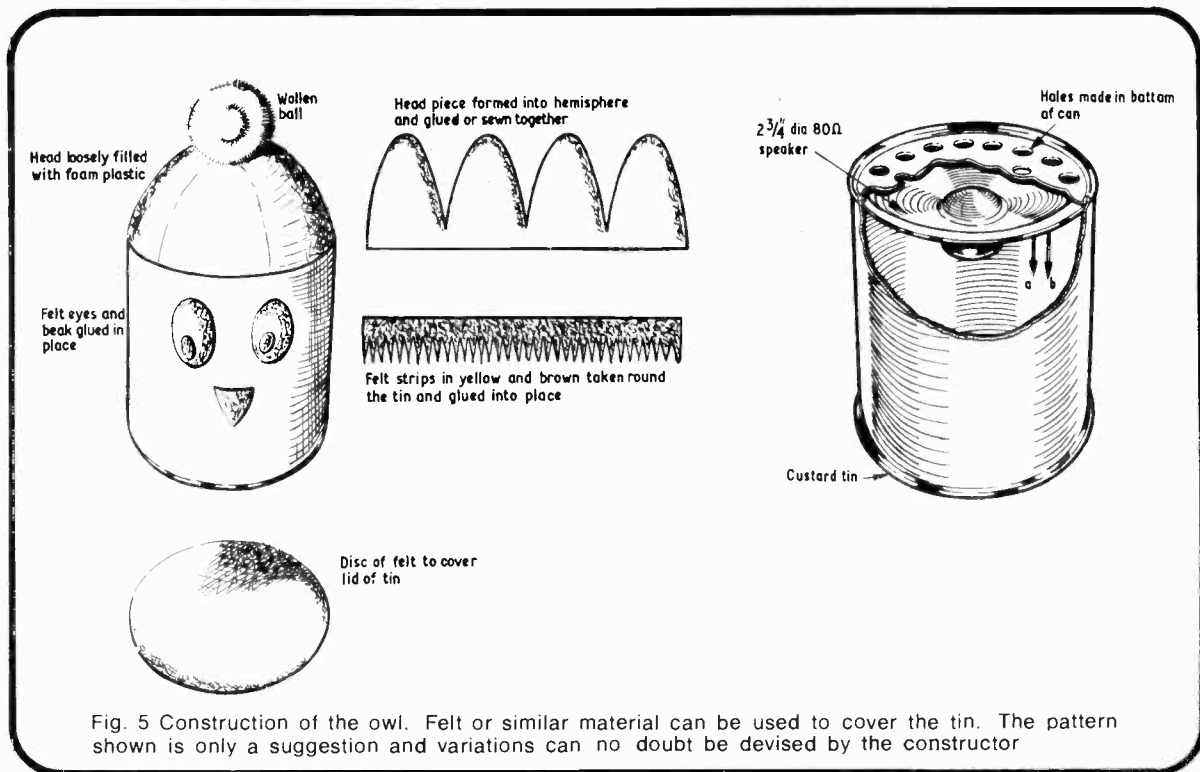


Fig. 5 Construction of the owl. Felt or similar material can be used to cover the tin. The pattern shown is only a suggestion and variations can no doubt be devised by the constructor

frequency of the first to provide some very interesting effects. At low frequencies the "squeak" is switched on and off and sounds something like a cat miaowing, at higher frequencies a warbling sound is produced.

In the prototype the addition of capacitors CA and CB of 100 μ F each was found to reduce the sharpness with which the circuit switched, and also enhanced the sound considerably. Of course the value of the capacitors is open to experiment.

HOOTING OWL CIRCUIT

By cascading astables as in Fig. 3, each time building on the existing circuit with a slower astable, very complex sounds can be made which are slow to repeat themselves exactly. (For more than three stages a higher battery voltage may be required.)

The circuit shown produces a sound somewhat like an owl, though other sounds can easily be made by changing the values of the capacitors in any or all of the astables.

A final point to remember when cascading stages is to ensure that each new stage can supply sufficient current to the existing stages. This means keeping the value of the base resistors as low as possible, in accordance with the desired frequency.

CONSTRUCTION


The scope for a suitable "carcass" is limitless, anything with sufficient space for the speaker and electronics will do. An ordinary 11oz size custard tin was found to be ideal for the owl.

First punch some holes in the metal end of the tin, and glue or solder the speaker in place (see Fig. 5). The circuitry is then built on Veroboard (Fig. 4) and soldered to the lid.

This method of construction allows sufficient room for the PP3 battery and the mercury switch as well as making access easy for battery replacement. The lid is just pushed home to seal the unit.

The outside of the tin can be disguised by using strips of coloured felt (see Fig. 5) and a very attractive finish can be obtained in a matter of an hour or so.

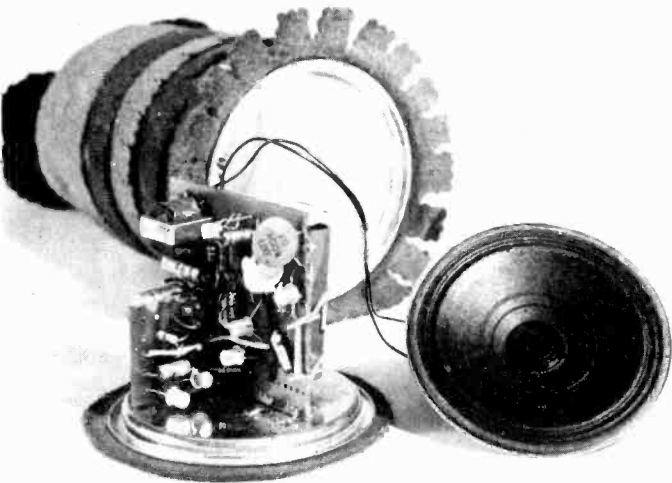When completed the owl stands upright and is switched off for convenience. The mercury switch can be arranged to close at any desired angle to activate the device. ★



ELECTRONIC PIANO



Part 4

By A. J. Boothman B.Sc.

LAST month the construction of the basic pitch p.c.b. was described of which 13 are required. To test these and to compensate for possible variations in output from the logic circuits, it is desirable to make up a simple jig. Such a construction also facilitates choice of tuning capacitors for the Hartley oscillator.

PITCH BOARD TEST JIG

The jig consists simply of a one foot square piece of wood to the edge of which is screwed two terminal blocks; one three-way and the other two-way.

The first block (3-way) connects to V_s , earth, and the pre-amp output on the pitch board under test, whilst the second block (2-way) anchors two floating leads at supply voltage. Response to keying action is checked by touching one of the floating leads against a key input pin on the pitchboard, whilst the other lead can be used to check the sustain action. See Fig. 4.1.

In order to ease the handling of the pitch boards during initial alignment, and to minimise the possibility of damage due to careless short circuiting of supply leads, etc. it is recommended that the p.c.b. frame is first built prior to any alignment.

P.C.B. FRAME

Fig. 4.2 shows the method of construction of the frame. If the final mechanics of the piano are to fit together satisfactorily it is important that this is assembled with care to ensure squareness. To ease this problem it is suggested that screws alone are used at this stage and that the glueing process is left until later when the rest of the mechanics has been built.

WIRING THE FRAME BLOCKS

The rear connector blocks, which have been cut into groups of three, carry the positive rail (V_s), pitch output, and earth line. The pre-amplifier/tremolo board is screwed onto the frame and panel, with the level tremolo depth and rate potentiometer spindles protruding from the frame side.

An eight-terminal connector is fixed to the bottom front bar at the right-hand side to provide the connections between the pre-amplifier board and other functions of the piano.

Red, blue and black wires for supply (V_s), pitch output and earth return are connected to each rear terminal block. From the last block this wiring is made to terminate at the pre-amplifier/tremolo board.

The black and blue terminations are shown as a screened lead on the pre-amplifier board layout shown earlier in Fig. 2.7, but this is not necessary provided that the leads between the last connector block and pre-amplifier board are kept as short as possible. The red and black leads are left long at the opposite end of the module in order to provide connections to the power supply.

The eight-terminal block takes leads shown in Fig. 2.7 as follows. The red and orange, that will finally connect to S3; the green, blue and red to S2; and the screened lead to the main amplifier.

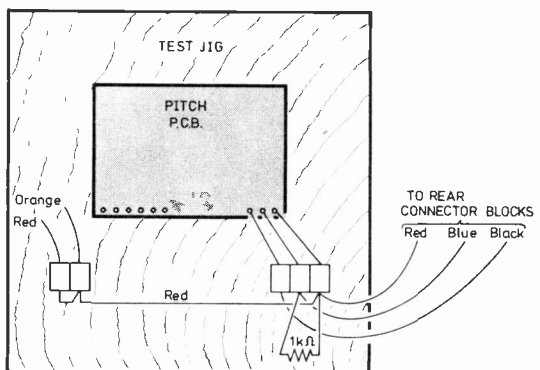
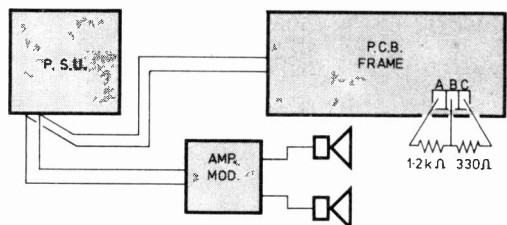


Fig. 4.1. Test set-up for individual pitch p.c.b.s

TEST SET UP

With the pitch p.c.b. module completed as above the initial setting up is almost ready to commence.

Fig. 4.1 shows the interconnection of the various units to give a test and initial setting up arrangement for the pitch boards. In order to make the system operational certain components have to be added during the test phase as follows.

Since the foot and keyboard level controls have not yet been constructed they must be simulated by soldering a short jumper between the VR3 red and yellow wiring pins on the pre-amplifier board (Fig. 2.7), and inserting two resistors in the terminal strips corresponding to S2 connections A-B and B-C. The resistor values should be $1.2k\Omega$ and 330Ω respectively.

As we are to test one pitch board at a time, the output load condition will be very different to the final situation when all boards are connected up so a $1k\Omega$ resistor is connected across the blue and black connections on the test jig terminal block.

From this point on the constructor could well be involved in a considerable amount of board removal and re-insertion, requiring repeated screwing

and unscrewing on the connector strips. It is strongly recommended that a good screwdriver be purchased for this purpose, and further that it should be the correct length for easy operation from above the pitch p.c.b. module.

INITIAL SETTING UP

The purpose of the initial setting up procedure breaks down into the following:—

- (a) Determine whether any catastrophic shorts are present on any of the assembled pitch boards. Also make sure correct fuses are inserted in FS1 and FS2 positions.
- (b) Determine whether any mistakes have been made during board assembly, e.g. diodes connected the wrong way round.
- (c) Correct for any large variations in logic output if necessary.
- (d) Correct for any large variations in individual note outputs due to transistor gain spreads if necessary.

In order to approach the operation systematically, the key touch sensitivity is not involved at this stage


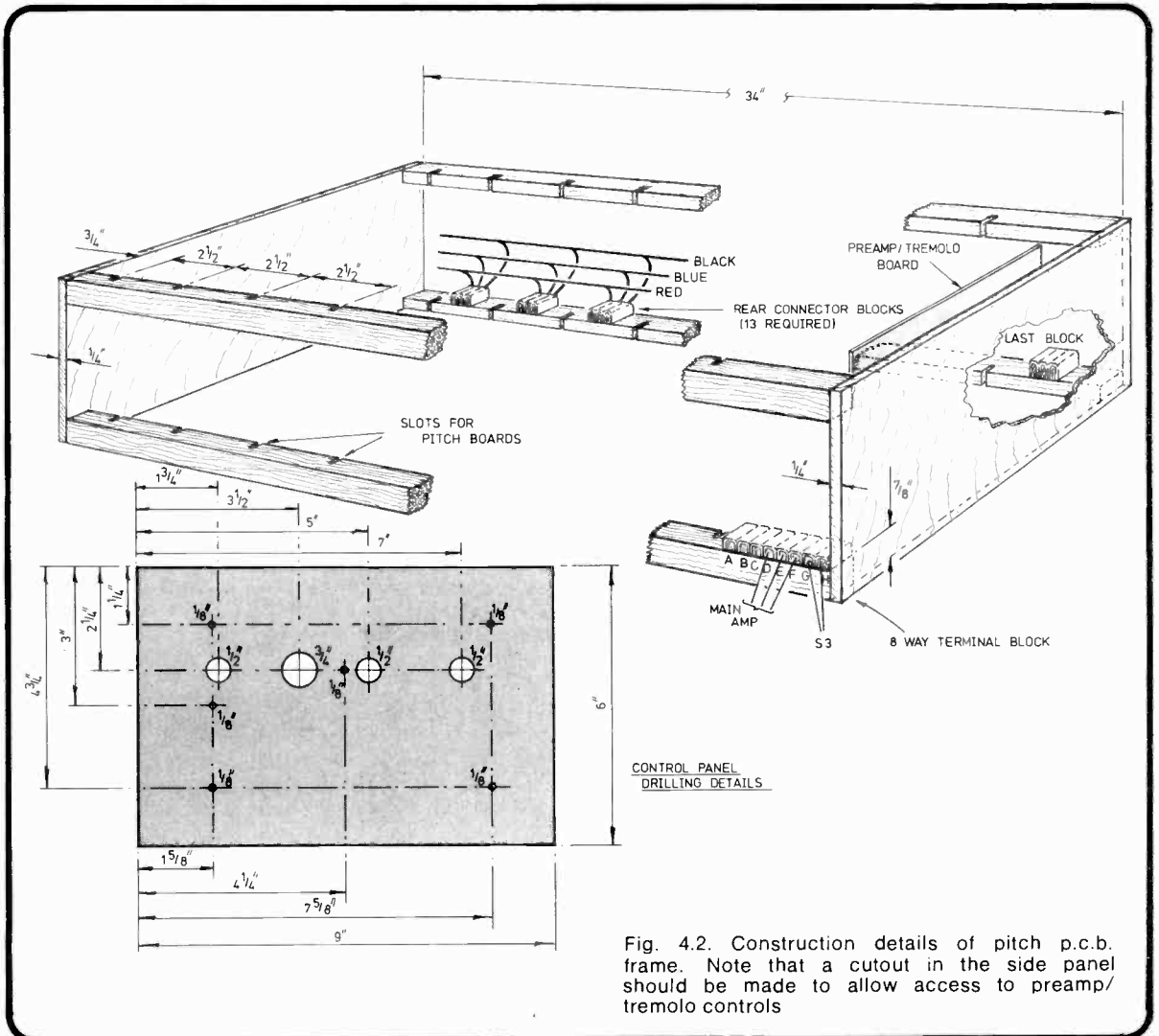


Fig. 4.2. Construction details of pitch p.c.b. frame. Note that a cutout in the side panel should be made to allow access to preamp/tremolo controls

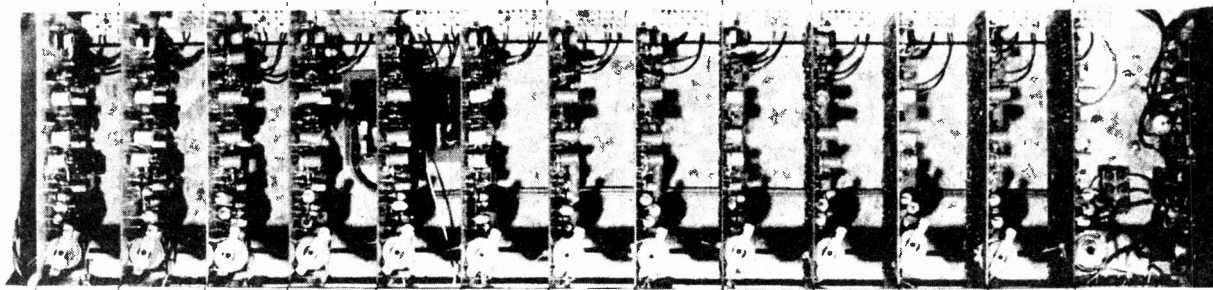

The thirteen pitch boards mounted in the wooden sub-frame

so that an acceptable balance is first achieved without the confusing element of touch variation.

TEST PROCEDURE

A board is first wired up to the test jig, with an $0.1\mu\text{F}$ or $0.2\mu\text{F}$ capacitor in position C48. On switching on the power, providing that everything is reasonably correct, a mixture of all the octaves of the note in question will be heard as a background noise.

Touching the test lead against any of the five key input terminals should cause the relevant note to trigger, and sustain in a fading manner for the period the test lead is held against the pin. Decay should be immediate on removal of the test lead, and it should be possible to simulate unkeyed sustain by connecting the second test lead to the sustain pin.

If, against the background noise, any particular note appears to be dominant, it may be desirable to reduce its level at this point. However some breakthrough will always occur, and the importance of this seems to diminish when the instrument is complete. It is therefore recommended that adjustments only be made if a note is extremely dominant, and the final decision as to the amount of time spent in this activity left until everything is built.

One point to remember here is that bass response is bound to be very low with the speakers mounted in this test arrangement with no cabinet resonance.

In order to adjust the breakthrough level on any particular note the value of R74 (or 75/76/77/78) is varied.

This is best carried out by soldering a second resistor across the $5.6\text{k}\Omega$ original to reduce its composite value, and thus reduce the signal to the relevant mixer. Convenient values to be tried are $56\text{k}\Omega$, $27\text{k}\Omega$ or $10\text{k}\Omega$.

Should any note require a higher output then a bridging resistor across R84 (85/86/87/88) can be used. When all the boards have been checked in this way they can be slotted into the pitch board module, and the $1\text{k}\Omega$ resistor removed from the test jig. Tuning (and C48 selection) could be attempted at this point, but since this is done by ear it would be very difficult without the keyboard for easy interval reference.

TUNING CAPACITOR

Capacitor C48 in the oscillator circuit is composed of a number of capacitors connected in parallel and whose values are chosen to give the required pitch at the central position of adjustment on the tuning

inductor. The range of capacitance required is approximately $0.1\mu\text{F}$ to $0.4\mu\text{F}$, and the selection process is carried out using the board test jig described earlier. The table gives suggested capacitor values with which to make the composite capacitor C48, but since winding the inductors by hand can result in quite a spread in inductance values, the capacitor values given should only be considered as a rough guide.

Table 1: Approximate capacity values for tuning pitch p.c.b.s

Pitch	Frequency (Hz)	Tuning Capacitor (C48)	Added Capacity (μF)
F	700	0.33	—
F#	740	0.22	0.057
G	784	0.22	0.022
A \flat	830	0.22	—
A	880	0.1	0.1
B \flat	932	0.1	0.069
B	988	0.1	0.047
C	1047	0.1	0.033
C#	1109	0.1	0.015
D	1174	0.1	—
E \flat	1245	0.047	0.043
E	1319	0.047	0.032
F	1397	0.047	0.022

PEDAL SOCKET BOARD

Figs. 4.3 and 4.4 show the circuits for the sustain and soft pedal sockets respectively. All components are mounted on the pedal socket p.c.b. The sustain voltage is dropped below V_s by Zener diode D34. This gives a sharper fall in voltage when a key is released with the sustain pedal depressed, such that rapid playing of a single note in the sustained mode produces a noticeable attack each time the note is pressed. Capacitor C51 prevents switching noise.

The soft pedal is simply a potentiometer, but R124 is connected on the p.c.b. as shown in order to present a similar load to the pre-amplifier when the soft pedal is disconnected. The piano can be played in this condition, and also with the sustain pedal unplugged. The jack socket is a stereo type in order to handle the three wires from the potentiometer.

In order to allow the pedals to be disconnected

from the instrument and packed away whilst being carried, they are connected to the piano by two screened leads and jack plugs. Mating sockets are mounted on a printed circuit board which is screwed to the base inside the piano, with suitable holes drilled in the base board to allow the plugs to pass through. See Fig. 4.5.

When the pedal p.c.b. is later fixed to the base board, supply leads are taken from the pitch board frame, and the sustain output is connected to the nearest sustain point on the key frame assembly. The soft pedal socket is connected via screen leads to the pre-amplifier board. These are the green, yellow and red leads shown in Fig. 2.7 (part two), which should in fact be screened.

PEDAL SHELL DETAILS

The outer construction is common for both pedals, and consists of a shaped $\frac{1}{4}$ in plywood box, with an extra $\frac{1}{4}$ in strip at the front to act as a platform for the hinge. Fig. 4.6 shows the complete shell, including the $\frac{1}{4}$ in plywood flap.

The shell should be fixed together using a good grade of wood glue, and panel pins. The final assembly can be painted or covered in a fabric, with rubber foot and base pads.

SOFT PEDAL DETAIL

There are many ways in which the action could be constructed, and the author would expect many builders to choose to use an alternative method to that described here.

The important fundamental is that pressure should not be exerted on the potentiometer spindle against the body either in a rotational sense or at right

SUSTAIN PEDAL

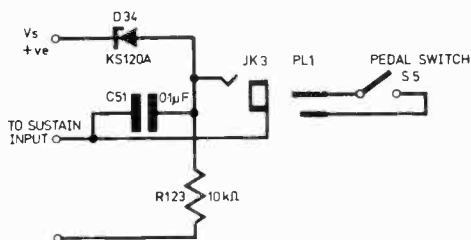


Fig. 4.3. Circuit diagram for the sustain pedal

SOFT PEDAL

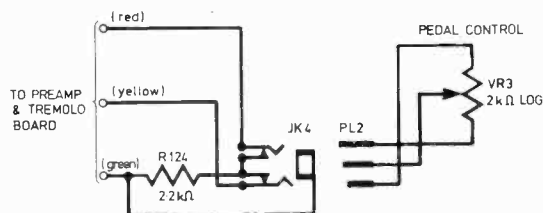


Fig. 4.4. Circuit diagram for the soft pedal

COMPONENTS . . .

Resistors

- R123 10kΩ
- R124 2.2kΩ
- R125 3.9kΩ
- All resistors $\pm 5\%$ $\frac{1}{4}$ watt

Capacitors

- C51 0.1µF 125V

Switches

- S5 Single pole microswitch
- S6 Single pole, 5-way rotary switch

Diodes

- D34 12V 400mW Zener diode
- D35-D40 ZS170 (6 off)

Miscellaneous

- JK3—Standard jack socket. JK4—Stereo jack socket. PL1—Standard jack plug. PL2—Stereo jack socket, knobs for keyboard control (4 off) (Bulgin)

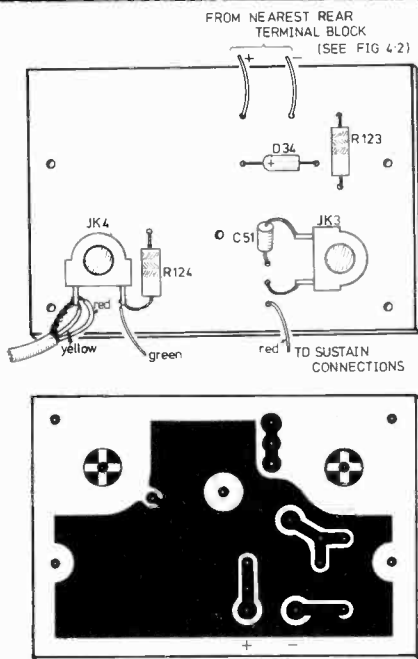


Fig. 4.5. Component layout and printed circuit details for pedal socket p.c.b.

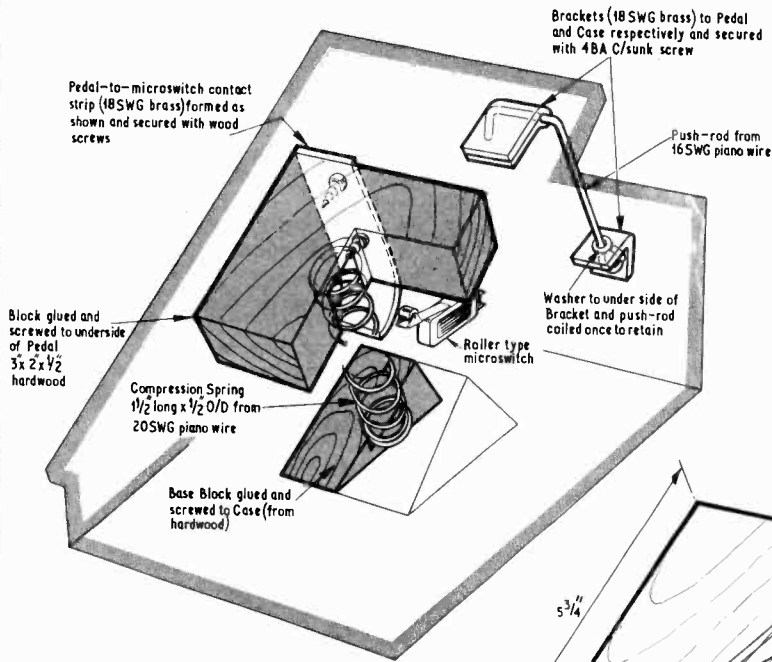


Fig. 4.8. Sustain pedal mechanics

Fig. 4.6. Shell construction of soft and sustain pedals

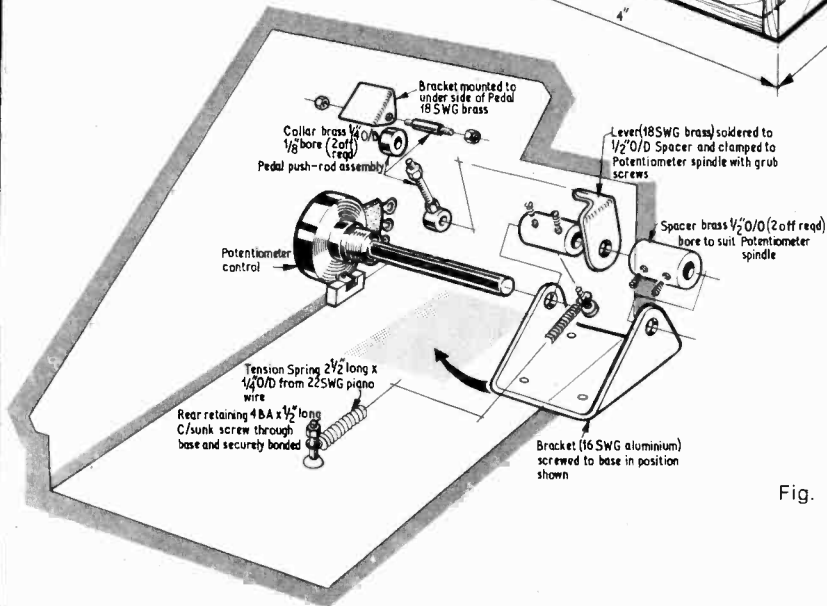
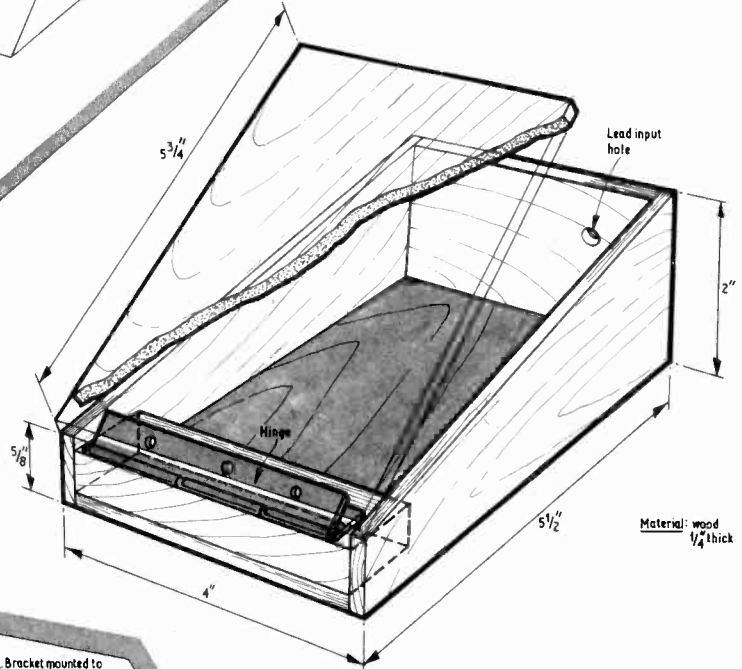


Fig. 4.7. Soft pedal mechanics

MATERIALS LIST FOR FOOT PEDALS

Shell Construction (Two Required)


- $5\frac{1}{2}$ in \times 2in \times $\frac{1}{4}$ in plywood (2 off)
- $5\frac{1}{2}$ in \times $3\frac{1}{2}$ in \times $\frac{1}{4}$ in plywood (base)
- $3\frac{1}{4}$ in \times $1\frac{3}{4}$ in \times $\frac{1}{4}$ in plywood (end plate)
- $3\frac{1}{4}$ in \times $\frac{3}{4}$ in \times $\frac{1}{4}$ in plywood (hinge platform)
- $5\frac{3}{4}$ in \times 4in \times $\frac{3}{8}$ in plywood (top flap)
- 3in hinge

Soft Pedal Detail

- $2\frac{1}{2}$ in \times $\frac{1}{4}$ in dia. tension spring
- 3in \times $\frac{1}{8}$ in dia. wire
- $3\frac{1}{2}$ in \times $2\frac{1}{4}$ in \times $\frac{1}{16}$ in aluminium sheet
- $\frac{1}{4}$ in brass spindle coupling
- Screws, spacers, and cable cleats as required

Sustain Pedal Detail

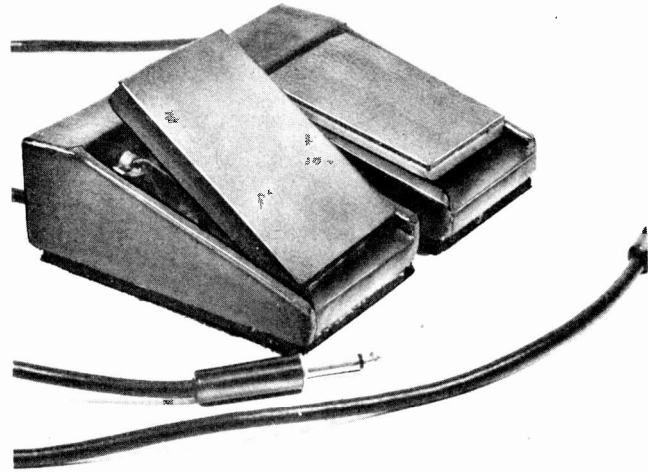- $1\frac{1}{2}$ in \times $\frac{1}{2}$ in dia. compressing spring
- 3in \times $\frac{1}{8}$ in dia. wire
- $1\frac{3}{4}$ in \times $\frac{1}{2}$ in \times $\frac{1}{16}$ in aluminium sheet (switch actuator)
- $1\frac{1}{4}$ in \times $\frac{1}{2}$ in \times $\frac{1}{16}$ in aluminium sheet (retaining bottom bracket for wire)
- Screws, spacers, and cable cleats as required.



The two prototype foot pedals

angles to the axis. The action should therefore only be built around the spindle, without clamping the body, but it is obviously necessary to provide a stop with which to prevent the body rotating.

Fig. 4.7 shows a possible solution. Lateral movement is prevented by positioning the support in such a position that the potentiometer body rests up against the shell side, whilst a small piece of wooden channel fixed to the base prevents rotating movement of the body. If brass bushes can be obtained, instead of relying on $\frac{1}{4}$ in holes in the aluminium, the action will be smoother.

The $\frac{1}{4}$ in spindle coupler is slipped over the spindle and secured with one screw, which also acts as a stop in the pedal off position. A further screw, with suitable spacer gives a lever on which to mount one of the cable cleats which acts as a bearing for the bent wire. The second cleat is fixed to the flap, and can be removed when access to the mechanics is required after the initial build.

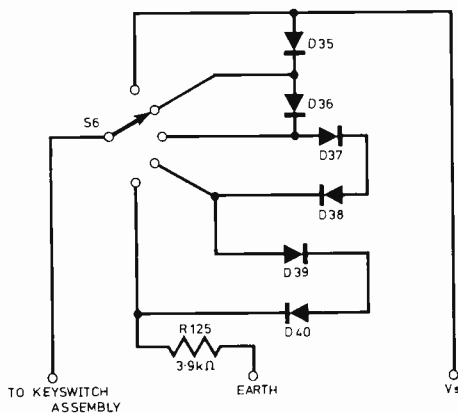


Fig. 4.9. Touch control circuit

SUSTAIN PEDAL

The same comments apply concerning alternative sustain pedal mechanics as for the soft pedal control. In the prototype the author used a commercial footswitch, but details of a suggested assembly are given in Fig. 4.8.

A $\frac{1}{2}$ in diameter compression spring provides the power to return the pedal after operation, and the upward travel is limited by a wire shaped to be captive in the top bearing (cable cleat), and retained within a slotted hole in the lower bracket. Access to the internal mechanics is again achieved by disconnecting the top bearing from the flap. The spring is seated within $\frac{1}{4}$ in diameter holes drilled in packing pieces which are attached to the flap and to the base.

Depending on the microswitch obtained a number of alternative configurations might be used.

TOUCH CONTROL

The touch control is mounted to the left of the keyboard, and gives preset selection of the maximum attack required at any particular time. The keyboard actuated touch sensitivity allows the player to reduce the attack below this maximum preset level by finger tip control.

The present variation in attack is achieved by controlling the voltage at the keyboard as seen in Fig. 4.9. Diodes D35-D40 give a range of attack voltages to suit the player. All diodes are mounted on the switch, which also has flying leads.

LEVEL CONTROL

This acts as a stepped potentiometer which allows rapid changes to be made in the playing volume. The resistors are mounted on the switch S2, as shown in Fig. 2.4. Normal playing position is position 2.

Next month: Keyboard, keyswitch assembly and cabinet details will be given.

Two major technical developments, each to have profound effect upon the social habits of millions, are part of the exciting BBC story. They are television and recording.

A late entrant into the field of sound broadcasting, Britain was to become first in the field of television. The all-electronic high-definition system developed by E.M.I. was adopted by the BBC when it commenced a regular television service in 1936, thus antedating the start of television in the U.S. by three years. So public service broadcasting stole a march on commercially-run broadcasting. This pioneering achievement demonstrated very forcibly the strength of a combination formed of a free enterprise industrial concern and a national institution devoted to public service, when working together with a definite objective in view.

Recording has greatly influenced the pattern of broadcasting in recent times. In its earliest years the BBC made limited and cautious use of recorded sound (as distinct from commercial discs) although a Blattnerphone steel tape recording machine was installed at Savoy Hill as early as 1931. Apart from the imperfection of the techniques then available opposition to the use of recorded material was based on a strongly held view that actuality was the very essence of broadcasting. However romantic such a view may seem to blasé listeners of today, most listeners of the 20's and 30's agreed that the direct and immediate reception of events as they were happening was one of the unique enchantments of the new "wireless" entertainment.

Today's prodigious output of sound and television owes very much to the great advances made in the audio and video recording techniques, notably due to contributions by commercial firms in Germany and U.S. All those hours of broadcasting we have become accustomed to can only be sustained with the aid of a stock of "convenience programmes" stored on disc or tape. With the insistent demand by the public for more broadcasting the "live" element is diminishing and thus the character of broadcasting is changing. There is a danger that broadcasting organisations will become merely carriers of other peoples' canned wares. (The automated sound broadcasting station with built-in magazines of audio tapes is already available as a "packaged deal." How long before the television counterpart makes its debut?)


This tendency will be accelerated with the introduction of commercial local radio next year, and with the possible granting of a second television channel to IBA. There is every reason therefore to ensure we preserve in its existing form our first and most experienced national broadcasting organisation with its unrivalled artistic production facilities that complement a justly renowned technical organisation. And champions of public service broadcasting do need to be vigilant. In anticipation of the expiry of the BBC's Charter and the Television Act in 1976, the pattern broadcasting will follow in the future is already undergoing careful examination.

F.E.B.

NEWS BRIEFS

Talking Book Library for Handicapped

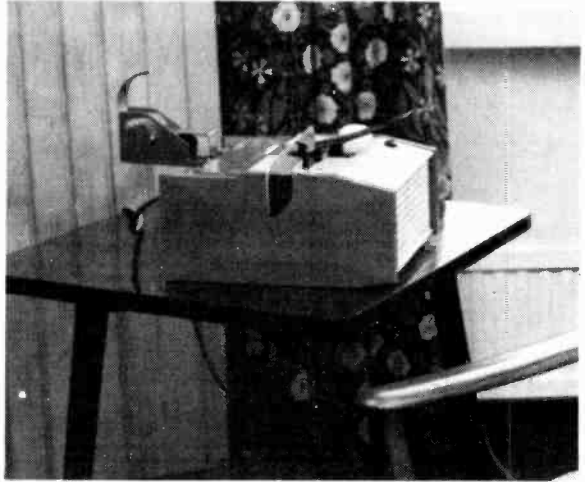A NATIONAL library has been established to help the many disabled people who are unable to read books in the normal manner. It is a library of talking books covering a wide range of subjects, all on purpose-made tape-cartridges containing up to 13 hours of reading.



The National Library of Talking Books is a registered charity and following a successful pilot scheme it already has a readership of 500 disabled people. It is hoped that Local Authorities and organisations for the handicapped will co-operate so that the talking books and playback machines may be made freely available to those in need. Further inquiries should be made to the National Library of Talking Books for the Handicapped, 49 Great Cumberland Place, London W1H 7LH.

Novel Educational Aid

AN EDUCATIONAL aid with a wide range of applications has just been introduced by Palca and is being distributed by Dixons Technical. Known as the Wireless Headphones System it makes use of a long loop of flex which surrounds an area within which communication is to take place. Anyone inside the loop and equipped with the special headphones, which are, in effect, self-contained receiver amplifiers, will hear the signal fed into the loop.

The loop acts as an induction loop aerial and its size can be extended to the requirements of the user. For instance it could surround a factory floor so that orders can be given in a noisy environment, or it could be used in a classroom with small groups of desks connected to different sources so that a number of lessons can carry on in the same room. Because the headphones are self-contained the wearer has complete freedom of movement allowing the system to be used for such applications as relaying information to footballers while the players are in motion.

The headsets cost only £7.50 each and the loop connector an extra £2 so making this a worthwhile and economic proposition.

Further inquiries should be addressed to Audio Visual Division, Dixons Technical Ltd., 3 Soho Square, London W1V 5DE.

PATENTS REVIEW...

CHECKING ENGINE IGNITION

The conventional way of checking ignition advance and engine speed is to use stroboscopic illumination of a timing mark on an engine part, such as the flywheel, the stroboscope being triggered by the lead to a sparking plug.

In BP1 273 496 Snap-On Tools Corporation of Delaware, USA, suggests a more sophisticated approach.

Their system relies on a meter with a dial calibrated to show both engine and distributor advance in degrees and engine and distributor speed in r.p.m.

Instead of using a stroboscope to illuminate the timing mark, the mark is covered with a small strip of reflective tape and is illuminated by a sensing device housing a lamp and a photocell. During operation the lamp is energised continuously and the light from it picked up by the photocell only when reflected back from the reflective tape over the timing mark. This produces a series of voltage pulses and the patent describes circuitry for comparing this series of pulses with another series of pulses obtained from inductive coupling with a spark plug lead (ignition pulses).

Fig. 1 shows how the spark plug voltage pulses are fed, via amplifier transistor TR1, to a one-shot multivibrator (transistors TR2 and TR3). The pulses from the photo-

cell X1 are used to control the thyristor SCR1. A train of pulses triggered by the spark plug pulses are fed to the base of TR4, while another train of pulses triggered by the photocell are fed to the base of TR5. The meter ME1 measures the time interval relative to engine period between successive pulses of the two pulse trains and converts this time interval into a direct read-out of degrees of engine or distributor rotation.

As engine timing is automatically advanced with increasing engine speed, the time interval between successive pulses becomes longer relative to rotation time and produces a higher reading in degrees on the meter. By reading the ignition advance in degrees for a series of engine speeds and checking against those recommended by the manufacturer, the engine can be subjected to rigorous testing.

WHEEL SPIN CORRECTION

Westinghouse Brake & Signal Co. Ltd., have patented (BP 1 277 474) some circuitry for use in testing devices for correcting spin or slide of a vehicle wheel.

These devices usually rely on deriving a rate of change of velocity signal depending upon the rate of change of the peripheral speed of the vehicle wheel. A modification circuit responds to a pre-selected value of this signal (indicative of the tendency of the wheel to spin or slide) and so modifies the braking forces.

A problem with such systems is that they are hard to check when stationary in a garage and the pre-selected signal values are hard to set. The Westinghouse invention attempts to tackle this problem.

The oscillator section of the patent is shown in Fig. 1. The unijunction transistor TR1 has b_1 base connected via R2 to the junction of R1 and Zener Diode D1. R1 and D1 are connected across a 30V supply and b_2 base is connected via R3 and the primary winding of T1 to the supply negative line.

The transformer T1 is part of a test device coupled through the secondary winding to a generator which produces a signal of which the frequency is proportional to the peripheral velocity of the vehicle wheel.

The emitter of TR1 is connected to the junction of diode D2 and capacitor C1, the other side of D2 being connected via R4 to one

side of switch S1. Capacitor C2 bridges R4, D2, C1 and is itself bridged by a discharge resistor R5. An exactly similar arrangement of components is made between TR1 emitter and switch S2 with R7 acting as the discharge resistor.

As mentioned above, the secondary winding of T1 is connected to the wheel generator of a spin or slide detection apparatus, the generator providing signals for the detection apparatus and the latter responding to a predetermined rate of change of peripheral wheel speed to initiate modification of braking.

As a service check a mechanic operates switches S1 and S2 to produce oscillations and inject them into the secondary winding.

Closing S1 causes oscillation by alternate charging of capacitor C1 via D2 up to a point at which the transistor conducts and discharges C1 via the emitter and b_2 base of TR1 into the primary winding of T1. The frequency initially depends on supply voltage, and in release of S1 changes at a rate dependent upon the rate of change of voltage applied to the emitter electrode of TR1 via C2. This is in turn dependent upon the discharge rate of C2 via R5. R5 is chosen to give a rate of change after release of S1 which corresponds to the minimum rate of change of speed of the wheel.

BP 1 277 474

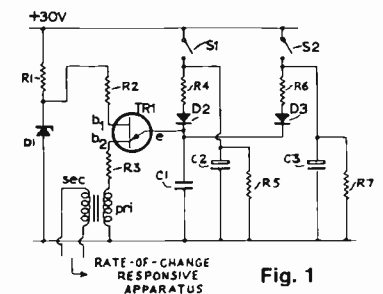


Fig. 1

Closure of S2 produces similar results but R7 is chosen such that the rate of change of frequency corresponds to a rate of wheel speed change to which the braking control is not required to respond.

Flipping switch S1 should trigger the modification circuit and flipping of S2 should not trigger the modification circuit. If the mechanic finds this is not the case, then adjustment of the sensing and braking equipment is called for.

BP 1 273 496

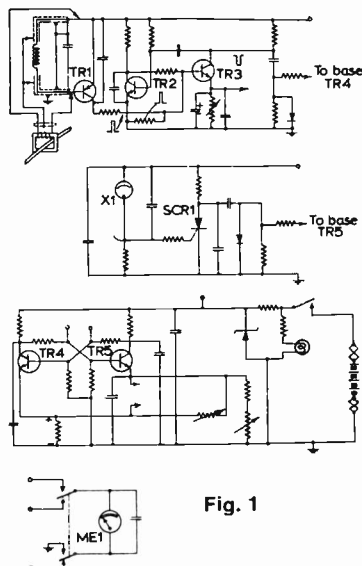


Fig. 1



Substitutes for VARACTOR DIODES

By B. Fistein

A REVERSE biased semiconductor diode has a high d.c. resistance. This is caused by the fact that the reverse voltage applied attracts current carriers (holes and electrons, in *p*- and *n*-type semiconductors respectively) away from the junction, leaving a region near the junction depleted of holes and electrons, called the "depletion layer". The greater the applied reverse voltage, the wider is the depletion layer.

Since the portions that are not depleted of carriers have a low ohmic resistance, a reverse-biased *pn* junction behaves as a capacitor in which the electrodes (i.e. the non-depleted regions) are separated by a thickness of dielectric (i.e. the depletion layer). The thickness of the dielectric, and hence the capacitance, can be varied by varying the reverse voltage applied.

The same principles apply to all semiconductor *pn* junctions and, in particular, *pn* junctions in transistors. Thus reverse biased junctions in transistors may be used as variable capacitors by varying the applied voltage.

Silicon transistors are particularly suitable for such use, as currents across their junctions when reverse biased are very small, resulting in a capacitance effect of very low leakage. Bias voltages that can be applied to vary the capacitance, range from a small fraction of a volt to a maximum which is the break-down (Zener) voltage of the junction.

The a.c. voltage applied to the variable capacitor, however, must be a small fraction of the bias voltage, otherwise detuning and the generation of harmonics will result.

TEST CIRCUIT

The circuit used for measuring the capacitance at different collector-base voltages is shown in Fig. 1. The inductance *L1* is of known value. A reverse voltage is applied to the junction under test through the potentiometer *VR1*, and the resonant frequency of the circuit is determined by means of a grid-dip meter. A low impedance path for a.c. is provided by capacitor *C1* to the potentiometer wiper.

A number of transistors were tried. Plastic planar transistors appear to function best. Transistors encapsulated in TO5 or TO18 style metal cans had higher capacitances than plastic ones, although the ratio of maximum to minimum capacitance was much the same for both types.

Fig. 2 shows capacitances for applied voltages between 0.15 and 12 in transistors of three different types. There was some variation among transistors of the same type, but most transistors tested showed a ratio of maximum to minimum capacitance of about 5:1. The greatest change in capacitance occurred at low voltages.

Within the limitations mentioned these transistors functioned satisfactorily as tuning capacitors for frequencies up to 20 MHz or higher, and with reasonable care in the layout of circuits, the highest frequency tuned with a given inductance was generally a little more than twice the lowest.

RECEIVER APPLICATION

The possible uses of voltage dependent capacitors are many, and include tuning, automatic frequency control, generation of harmonics, and others. As an illustration of the use of a transistor as a tuning capacitor, one was used in a simple reflex receiver for the medium wave band.

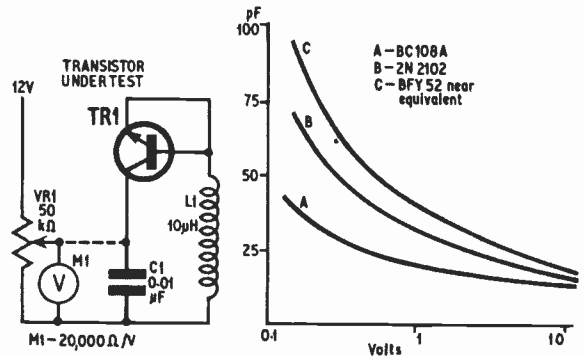


Fig. 1. (left). Circuit used to determine capacitance of a collector-base junction

Fig. 2. (right). The resultant voltage/capacitance characteristic of three sample transistors

The transistor used as a variable capacitor is TR1, in this case, type BC108. The variable voltage applied to it is obtained from the potentiometer VR1; as most of the change in capacitance occurs at low voltages, VR1 should be a logarithmic type. Since the capacitance (and hence the tuned frequency) depends on the applied voltage, the power supply to the receiver should be stabilised by means of a Zener diode.

The inductor L1 used for tuning consists of 200 turns of 36 s.w.g. enamelled wire, close-wound on a ferrite rod $\frac{3}{8}$ in diameter and 3in long. The secondary winding L2 consists of eight turns wound over the "earthy" end of L1, and wound in the opposite sense. The regeneration capacitor, C2 consists of two short lengths of thin p.v.c. insulated wire twisted together.

TUNED CIRCUIT

Because of the small tuning capacitances and relatively high inductance used in tuning, C2 is connected to a tap on L1, 40 turns from the earthy end, rather than to the "live" end as usually done in receivers of this type.

Alternatively, C2 may consist of a short length of p.v.c. insulated wire; one end is connected to the collector of TR2, the other end is bent to fit snugly over L1 for one half turn. This half turn is moved along the length of L1 until optimum regeneration without oscillation is obtained over the whole tuning range, and is then fixed to L1 in that position.

With reasonable care in the lay-out of components associated with TR1 and TR2 the receiver will tune over the greater part of the medium wave band. VR1 may be placed where convenient, preferably well away from L1 to reduce detuning by hand capacitance while operating it. L3 should not be close to L1, and the axes of these inductances should be at right-angles to each other to avoid mutual coupling between them. Audio output is taken from C5 to high impedance headphones, or to an audio amplifier for loudspeaker operation. ★

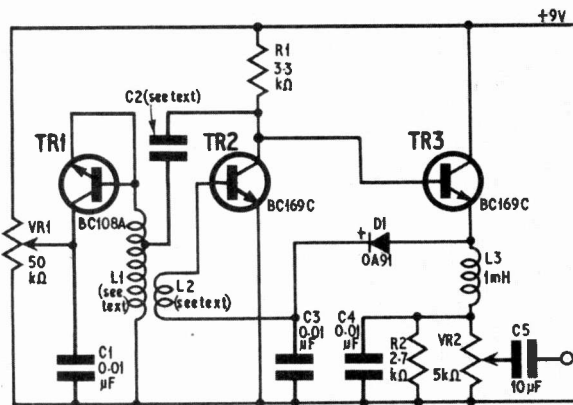


Fig. 3. An example of the practical application of the junction capacitance of a transistor. In this simple reflex receiver the "varactor" effect is achieved by feeding a preset voltage to the collector-base junction of TR1


NEXT MONTH...

A new area of interest, demonstrating how organic living systems and electronic systems can interact, is opened up with the publication next month of design and application data for a

Biological Amplifier

for detecting very low frequency signals produced by the brain.

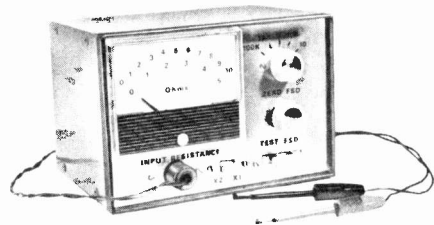In conjunction with various output stages, this amplifier can be safely employed for specific non-medical purposes: as an alphaphone to induce relaxation, with aural feedback between the brain and ear; or as a cardiophone where control of the heart rate is achieved by means of a visual feedback loop.



I.C. Linear Ohmmeter

Conventional ohmmeters have non-linear scales which, though providing large ohmic ranges, are difficult to interpolate and require special meter calibration. The I.C. linear ohmmeter gets round these difficulties using a cheap milliamp meter to provide three resistance ranges from 0-100kΩ.

PRACTICAL ELECTRONICS

January issue on sale December 8

Ensure your copy by ordering in advance from your newsagent.

ELECTRONORAMA

AIDS TO MOTORING SAFETY

The problems of traffic control and collision avoidance on the world's roads has long been a problem that many countries have been seeking to find a satisfactory solution. Two companies, in the U.K. and America, have been developing separate systems, both based on the principles of radar, to help combat the problems of safety on the roads. The great advantage of using radar is that it is able to penetrate fog.

At the moment these systems are still in the experimental stages but both RCA and Mullard, the developers, hold great hope for the future.

Radar "Cat's Eyes"

A traffic sensor has been devised at the Mullard Research Laboratories in Surrey, which could form part of a fully automatic system to control traffic, unaided by a human observer of traffic conditions.

One of the problems encountered with most radar traffic control systems has been that if more than one vehicle is in the beam it tends to confuse the equipment. But with the Mullard system the sensor device is very similar to the modern "cat's eyes" and is installed in the road in the centre of each lane. This way only the car passing directly over the sensor is detected.

The sensor device is a compact radar unit containing the transmitting aerial and receiving aerial and, as the cars passing overhead are detected, a second set of detectors activate circuits which measure the speeds of receding vehicles.

In a complete system, data derived from the radar "cat's eyes" installed in roads at strategic places would be routed to a central computer which would analyse the total traffic situation and control roadside warning lights and junction traffic lights accordingly.

Anti-collision radar

The RCA experimental auto radar system is designed to avoid rear-end collisions on the roads and help drivers to maintain reasonably safe distances between the car and the vehicle in front.

A feature of the system is its ability to eliminate false "targets" and "clutter". It is not "blinded" by

Tests being carried out on the RCA system. The radar units can be seen on the two cars, just above and below the licence plates



Artist's impression of how one of the traffic sensors, being developed by Mullard, would be installed in the road surface.

The radar signals of vehicles passing in either direction in adjacent lanes. The radar beam is narrow enough to avoid unwanted reflection when a car moves out into another lane to pass a car ahead. Consequently, the car can pass without a warning being sounded.


The compact radar, mounted on the front of a car, transmits a continuous 9GHz (X-band) signal which strikes the passive harmonic reflector on the obstacle ahead. This reflector re-radiates the second harmonic (18GHz) of the incident signal. The radar receiver is designed to accept only those radar echoes that are double the frequency of the transmitted signal.

The reflector is approximately the size of a number plate and can be affixed to the rear of any vehicle or to any sign designating a traffic hazard. By using this special reflector all vehicles and traffic hazard signs, no matter what size, provide the same reflected signal strength. Thus a small car or a "one-way-do-not-enter" sign will be picked up by the radar system as clearly as a large container lorry, and their radar echoes will not be swamped by the echoes of larger vehicles.

Eventually, it is hoped, an operational radar of this type might be integrated into a car so that it would automatically release the throttle and apply the brakes to keep distances between vehicles above a safe minimum. Furthermore, if special small reflectors were incorporated on the sides of motorways and on collision hazards such as bridges, the radar could automatically apply the brakes if the vehicle is approaching the hazards at an unsafe speed.

The RCA system still requires testing and refinement, but scientists believe that an operational system can be mass produced within five years.

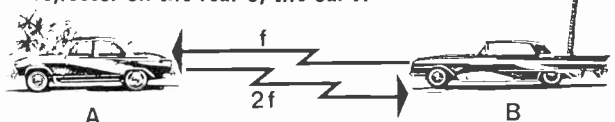Showing how the RCA system works. Radar on car B transmits a signal (f) which is reflected back at twice the frequency (2f) by a special reflector on the rear of the car A



Features MOTORWAY SAFETY and WEIGHING HAZARDOUS MOVING LOADS


Automatic "Headway" Control

ONE example of automatic control in which brake and accelerator are operated as a result of obstacle detection, is being developed at the Lucas Group Research Centre near Birmingham.


Intended primarily for use on motorways where lane discipline is essential, this investigation has as its objective, the automatic maintenance of "headway" or the distance between moving vehicles at varying speeds.

The equipment uses a 35GHz (8mm) continuous wave source, frequency modulated to give the required information on range and speed. The use of this high frequency enables both the transmitting and receiving "horns" to be compatible with automotive styling requirements while providing the narrow beam width required. An electronic computer carried on the vehicle makes calculations based on the reflected radar signals and relative velocity of the vehicle with respect to the leading vehicle. Brakes and throttle are then automatically adjusted to maintain a consistently "safe" distance.

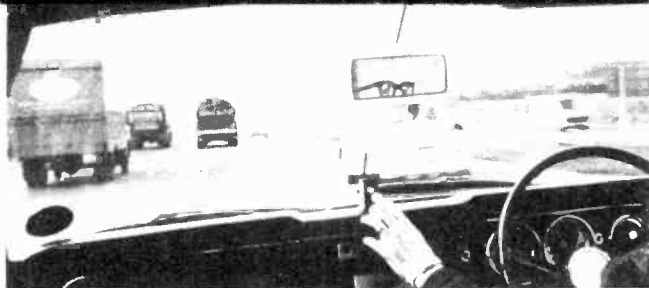The Government Department of the Environment are supporting the project with financial aid and facilities for testing at the Transport and Road Research Laboratory.



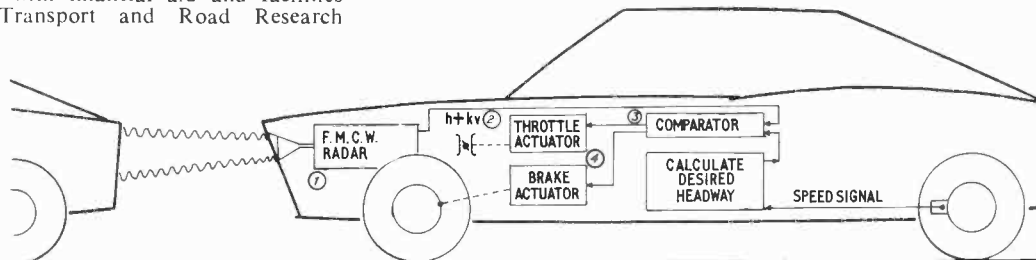1. FMCW is frequency modulated continuous wave radar which measures "headway" and relative vehicle velocity
2. The relative velocity kv caused by Doppler shift is such that it enhances the effect of headway h
3. Headway is compared with desired headway, calculated from time vehicle speed to produce an actuating signal
4. The actuating signal adjusts vehicle speed by means of brake and throttle actuators, so that headway spacing of one second is maintained



Weighing-in-Motion Scheme for Heavy Loads

ONE of the problems encountered in heavy industry is the need to weigh large and sometimes hazardous loads on a continuously moving production line. Movement can influence erroneous measurements unless strict control of load vibrations is exercised. W. & T. Avery Ltd. the large weighing machine company have produced a "weighing-in-motion" system using a 27ft load-cell weighbridge linked to electronic sampling, recording, and data transmission instrumentation.

Four 500,000 pound capacity load cells are equipped with free-motion units to isolate them from shear forces and transmit analogue weight signals to a static digitiser in the weigh office. An analogue to digital converter interfaces these signals to the digital display and teleprinter.



High frequency vibrations are attenuated by the rigid design of the weighing structure and a filter in the instrumentation. A digital filter eliminates the effects of low frequency vibrations. By sampling the resultant output signals at various time intervals, the readout displays the loading in increments of 0.1 ton. If the load is moving over the weighbridge too fast, an "excess-speed" signal inhibits the system until reset.

This system has been installed at the British Steel Corporation's Port Talbot Works, where up to 600 tons of molten iron is weighed *en route* to the steelmaking plant. The load is hauled in huge ladles on a railway which passes over the weighbridge.



PE



By R.W. COLES PART 6 ANSWER (A) AND Z REGISTERS

LAST month the construction of the ENTRY register was described together with the constant store and a fixed constant option. To follow this the logic and construction of the two registers which form the main part of the arithmetic section will be described, these being known as the ANSWER (A) register and the Z register.

"A" AND "Z" REGISTERS

The A (ANSWER) and Z registers, together with the adder to be described next month, form the heart of the arithmetic unit of Digi-Cal. These registers are identical in capacity, being four (B.C.D.) digits "wide" and ten (decimal) digits "long". They differ in the type of input and output facilities which include both serial and parallel transfers.

Both are right-shift types, and are capable of shifting data at more than one million bits per second in the serial mode, when supplied with suitable clocking signals.

The A register has an associated display multiplexer which is used to send the answer data down the display bus under the control of the display strobes provided by the display board previously described in Part 3.

The multiplexer is identical in principle to the ENTRY register version, but is two (decimal) digits longer to allow display of a full eight digit answer. The most significant two digits are not displayed and are used to allow error detection and decimal point manipulation.

A block diagram of the A and Z register sections of Digi-Cal is given in Fig. 6.1 and this should be studied in conjunction with the overall system block diagram (Fig. 1.3) from the July edition, which did not include the display multiplexer.

REGISTER PARTITIONING

The division of the register circuitry to suit the constraints of a standard printed circuit system requires a good deal of thought to produce an arrangement which:

- uses a minimum of "wasted" i.e. positions, and thus the minimum number of separate boards;
- shares the number of input/output connections equally between boards so that one board does not demand more edge connector positions than are available on the standard board; and

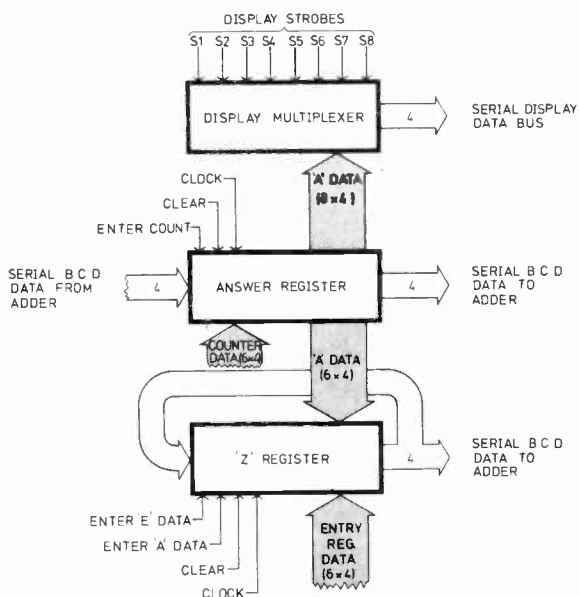


Fig. 6.1. Block diagram of the "A" and "Z" register sections of Digi-Cal

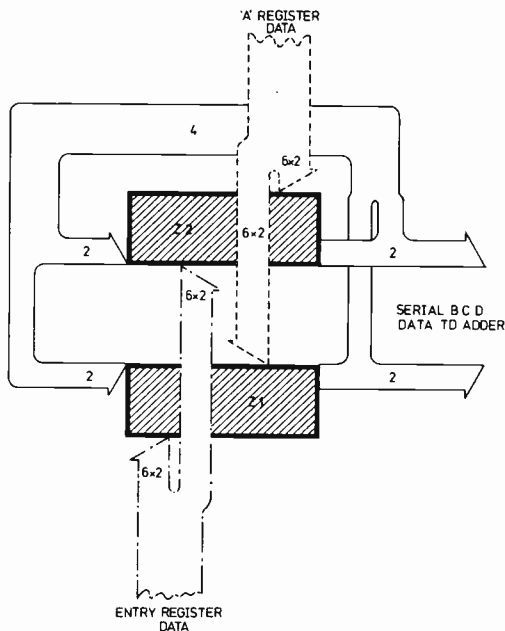


Fig. 6.2. The partitioning of the "Z" register is shown here, together with the inputs and outputs

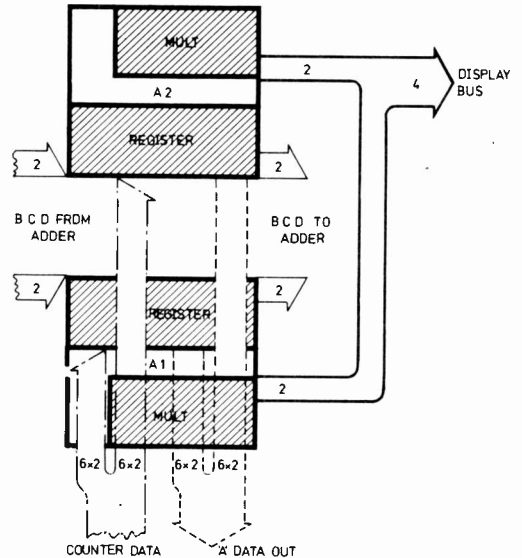


Fig. 6.3. The partitioning of the "A" register into the two halves known as the A1 and A2 registers is shown here

(c) gives a layout arrangement which permits the interchange of identical halves of the circuit and thus cuts down the number of different types of board required.

With the ENTRY register last month, the circuit was divided vertically into three boards each carrying a two digit long register of B.C.D. width, plus a separate multiplexer board.

The A and Z registers on the other hand are divided horizontally into two ten-digit long registers, each two digits wide, giving four boards in all. The A register multiplexer is also split in this way, and in this case is incorporated on the same boards as the register proper.

All this sounds a little complicated but is easier to understand with reference to Fig. 6.2 and Fig. 6.3.

"A" REGISTER

The A register is built on two DL109/44 cards, each of which houses eight TTL i.c.s, two resistors, and two decoupling capacitors.

Making a register ten digits long and four wide would require twenty SN7474 dual D-type flip-flops as used in the ENTRY register, and this number would take up a lot of room, as well as presenting a mammoth wiring-up problem.

Fortunately the TTL series of complex functions known as medium scale integration (M.S.I.) contains a number of ready-made shift register circuits, and it is one of these, the SN7496, which is employed in the A register circuit.

A diagram of the SN7496 is shown in Fig. 6.4, and as can be seen this i.c. consists of a complete five-bit serial shift register in a 16 pin D.I.L. package.

The register comes complete with gating to allow a five-bit parallel input transfer when the PRESET input is activated, and has a separate output from each stage to allow parallel output transfers.

The CLEAR input will set all the flip-flops to the logic "0" output state, and is used to erase the stored contents of the register.

By connecting two of these i.c.s in series a ten-digit register is formed, and by using four of these ten-digit sections, the required A register capacity is achieved, using eight SN7496 i.c.s (see Fig. 5.5).

OPERATION OF "A" REGISTER LOGIC

When an arithmetic programme is running, the data in the A register is shifted serially into the ADDER circuit, in synchronism with the data in the Z register which is either added to or subtracted from the A data.

The output of the ADDER forms the serial input of the A register, so that after a group of ten clock pulses, the A register contains the sum (or difference) of the original A and Z register contents.

If the arithmetic operation required is MULTIPLICATION, then the contents of the A register have to be duplicated in the Z register before the series of additions take place, and to facilitate this the parallel outputs of the A register are used to provide a single 24 bit transfer.

At the end of a DIVISION, the answer is represented by the state of the counter, and before this can be displayed it has to be transferred to the A register. This is also carried out in a single 24 bit transfer, this time using the parallel PRESET inputs of the SN7496s.

In each of these transfers the initiation is provided by a control pulse from the programme.

MULTIPLEXER

The multiplexer consists of a series of SN7401 open-collector gates, with their outputs "wired-OR" to give the required four-bit data-bus. It is formed in the same way as the ENTRY register multiplexer.

The eight strobes or "character call-up" lines are produced in a sequence starting at the most significant end of the register, each one activating a group of four gates to send a single B.C.D. group to the display.

In the case of this multiplexer, the data-bus is produced in two, two-bit halves as a consequence of the partitioning arrangement mentioned earlier. This division of the multiplexer into two physically separate sections means that the display strobes have to be connected to both board A1 and board A2.

"Z" REGISTER

Like the A register, the Z register is housed on two DL109/44 plug-in cards. This register is identical in size to the A register, being ten by four in format, but because of its different role in the arithmetic operations of the calculator, different integrated circuits are employed.

A glance at Fig. 6.1 shows that the Z register is required to accept parallel transfers from two sources, the A register and the ENTRY register. It is not required to provide parallel outputs, only serial outputs being needed to feed the ADDER.

These different input/output requirements preclude the use of SN7496 shift register elements, since these devices can only accept a single parallel input transfer without extensive external gating. Luckily, it is still possible to enjoy the advantages of M.S.I. in this circuit because another device which suits our needs, the SN7494, is available.

The SN7494 is a four-stage serial shift register element with provision for parallel loading from two separate sources, under the control of internal gating.

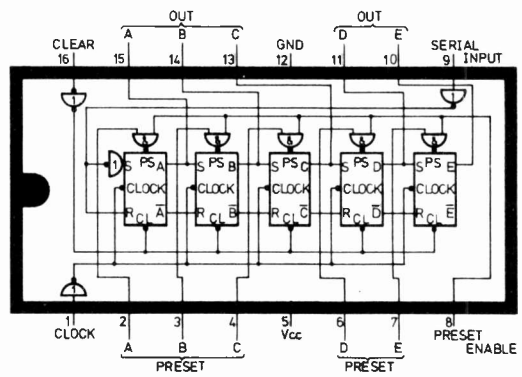


Fig. 6.4. The internal logic of the SN7496 integrated circuit

A logic diagram of this device is shown in Fig. 6.6 where it can be seen that the two sets of parallel inputs, 1A to 1D and 2A to 2D are presented to the PRESET inputs of the flip-flops via four AND-OR-INVERT gates, the appropriate set of input data being selected by the PRESET1 or PRESET2 control line.

Note that output connections are not provided from the A, B, and C flip-flops, which as previously stated, is quite satisfactory for this application.

REGISTER ASSEMBLY

Connecting two SN7494s in series gives a register eight digits long, which falls short of the requirement of ten digits. Therefore two more stages are added

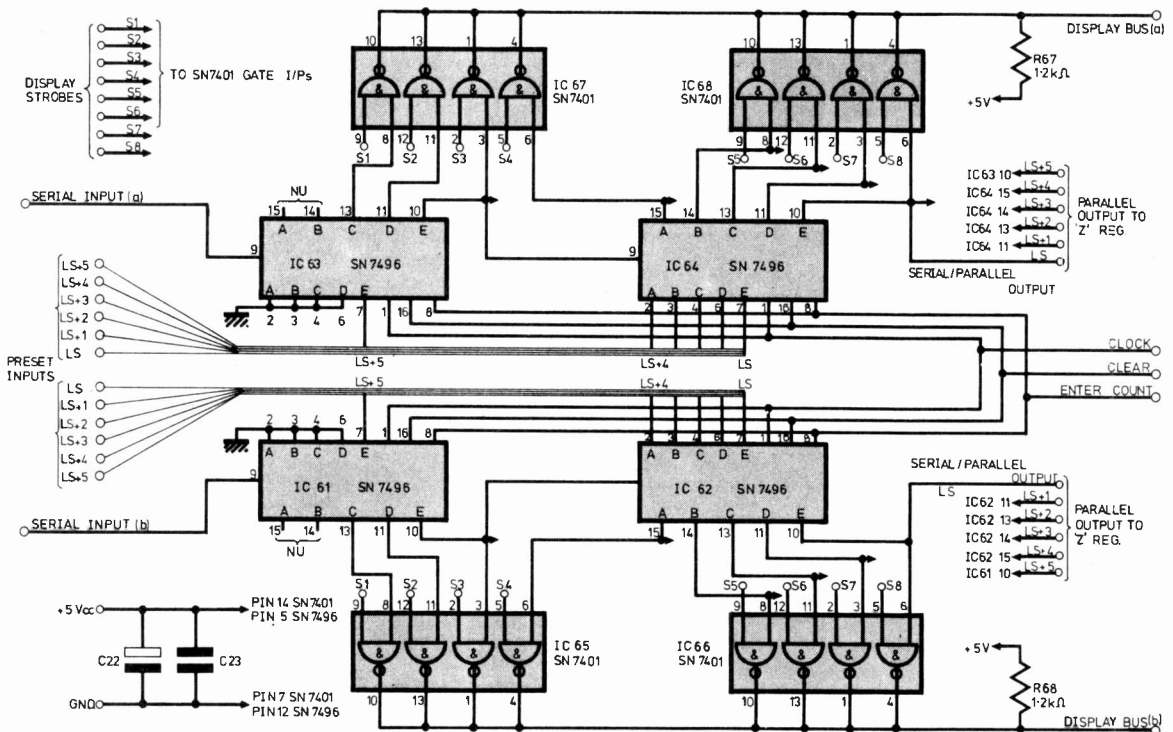


Fig. 6.5. The logic contained on the A1 register board. The A2 board is identical to this

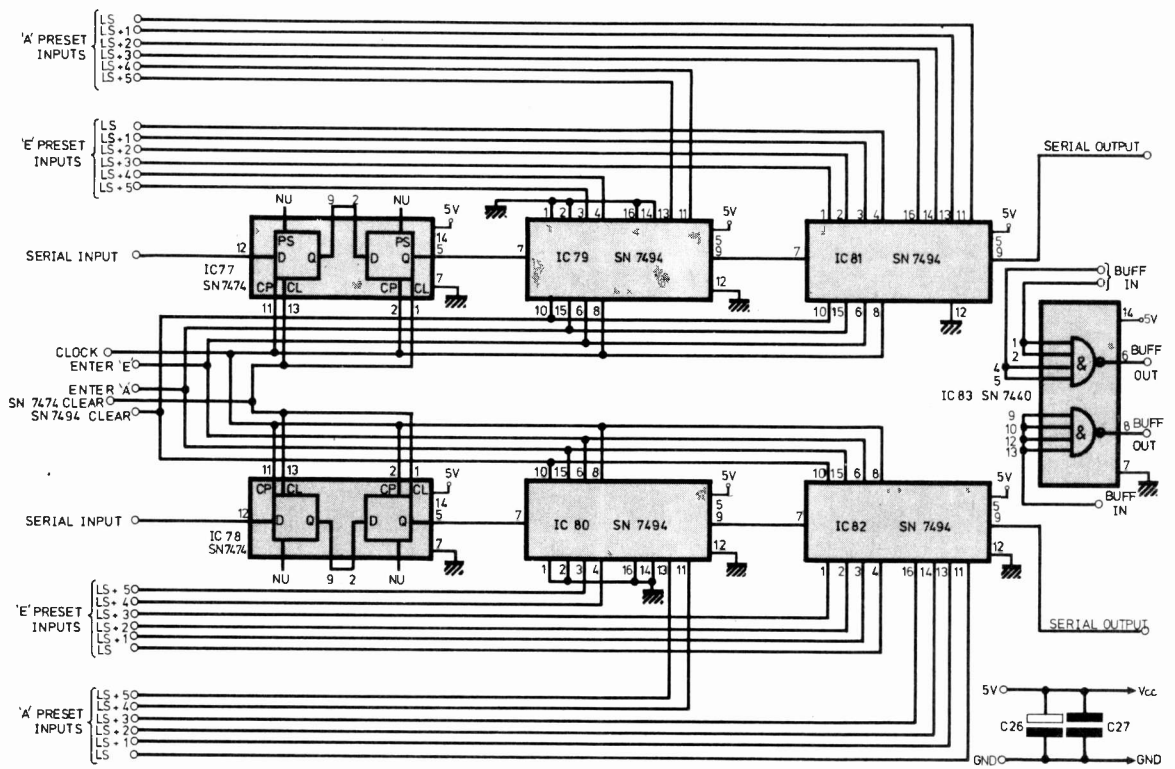


Fig. 6.7. The logic contained on the Z1 register board is shown here. The Z2 board is identical to this

in the form of an SN7474 dual D flip-flop. If these extra stages are placed at the "most-significant" end of the register, no extra input gating will be required since only the six "least-significant" stages are required to accept parallel input transfers. This is the approach adopted for the z register and the resulting circuit is assembled from eight SN7494s and four SN7474s, giving the required total number of 40 flip-flops.

The circuit of one of the two identical z register boards is shown in Fig. 6.7 where it can be seen that in addition to the shift register components, an SN7440 dual buffer gate is incorporated.

The connections to these gates are made external to the DL109 cards because these gates are used for different jobs on each of the two cards, and

internal connection would prevent interchanging these when required.

One of the four buffer gates is used to invert the CLEAR z signal from the programme to make it compatible with the CLEAR inputs of the SN7474 devices, which operate on *low* inputs, as opposed to the SN7494 CLEAR lines which operate on *high* inputs.

The remaining gates are used to buffer the z register PRESET1 and PRESET2 lines, and in the OVERFLOW logic.

"Z" REGISTER OPERATION

The most important operational aspect of the z register is that it operates in a recirculating mode, which means that not only is its output fed to the ADDER, but also back to its own input, to give an endless loop.

This feature is important because it means that the register contents are not altered no matter how many bursts of ten clock-pulses are applied in the course of an arithmetic operation.

This facility is required in the MULTIPLY and DIVIDE programmes, where the contents of the z register are continuously added to or subtracted from the contents of the A register until the result is produced.

In these programmes the contents of the register can be used up to one million times in a single computation. Of course, this is not to say that the register contents are completely invariant, for when a particular set of data is finished with the register will be cleared by a CLEAR pulse from the programme, ready for new data to be entered in parallel from the ENTRY or A registers.


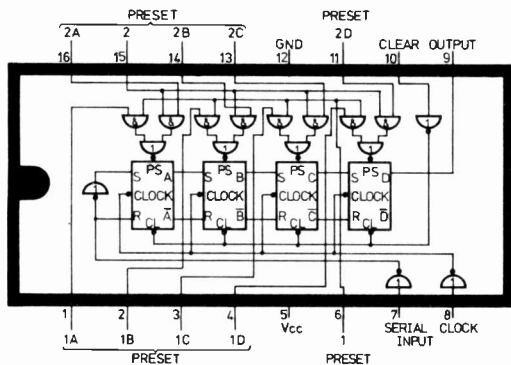


Fig. 6.6. The internal logic of the SN7494 integrated circuit


A AND Z BOARDS

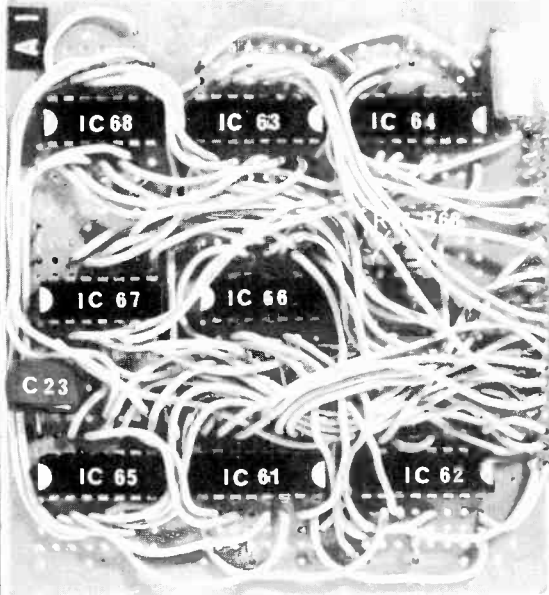

- 1 Serial i/p (IC63)
- 2 LS + 4 o/p (IC64)
- 3 LS + 4 o/p (IC62)
- 4 LS + 3 o/p (IC64)
- 5 LS + 3 o/p (IC62)
- 6 LS + 2 o/p (IC64)
- 7 LS + 2 o/p (IC62)
- 8 LS + 1 o/p (IC64)
- 9 LS + 1 o/p (IC62)
- 10 Serial o/p (IC64)
- 11 Serial o/p (IC62)
- 12 Disp. bus o/p (R67)
- 13 Disp. bus o/p (R68)
- 14 8
- 15 7
- 16 6
- 17 5 Display
- 18 4 strobes
- 19 3
- 20 2
- 21 1
- 22 Serial i/p (IC61)

- LS + 5 o/p (IC63) 23
- LS + 5 o/p (IC61) 24
- spare 25
- spare 26
- LS + 5 i/p (IC63) 27
- LS + 5 i/p (IC61) 28
- LS + 4 i/p (IC64) 29
- LS + 4 i/p (IC62) 30
- LS + 3 i/p (IC64) 31
- LS + 3 i/p (IC62) 32
- GND 33
- 5V 34
- LS + 2 i/p (IC64) 35
- LS + 2 i/p (IC62) 36
- LS + 1 i/p (IC64) 37
- LS + 1 i/p (IC62) 38
- LS i/p (IC64) 39
- LS i/p (IC62) 40
- spare 41
- CLOCK 42
- PRESET 43
- CLEAR 44

Fig. 6.8a. Layout of the i.c.s on the "A" register boards and function of the edge contacts, both boards being identical

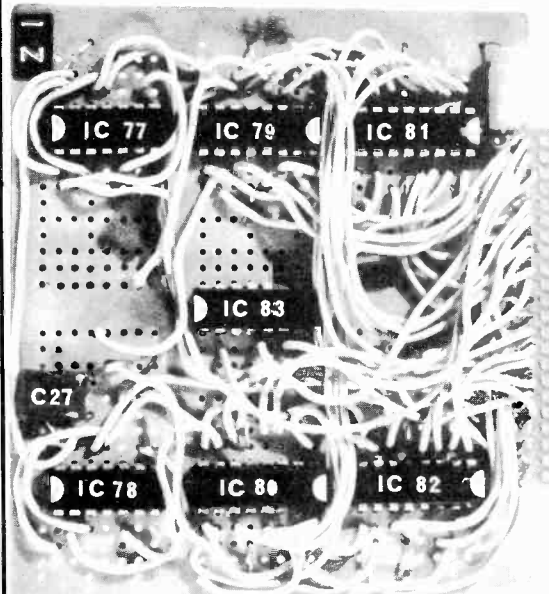

- 1 E LS + 5 i/p (IC79)
- 2 E LS + 5 i/p (IC80)
- 3 E LS + 4 i/p (IC79)
- 4 E LS + 4 i/p (IC80)
- 5 E LS + 3 i/p (IC81)
- 6 E LS + 3 i/p (IC82)
- 7 E LS + 2 i/p (IC81)
- 8 E LS + 2 i/p (IC82)
- 9 E LS + 1 i/p (IC81)
- 10 E LS + 1 i/p (IC82)
- 11 spare
- 12 spare
- 13 E LS i/p (IC81)
- 14 E LS i/p (IC82)
- 15 Enter E
- 16 Enter A
- 17 Serial o/p (IC81)
- 18 Serial o/p (IC82)
- 19 Serial i/p (IC81)
- 20 Serial i/p (IC82)
- 21 CLOCK
- 22 CLEAR (SN7496s)

- Buffer o/p 23
- Buffer i/p 24
- Buffer i/p 25
- spare 26
- A LS + 5 i/p (IC79) 27
- A LS + 5 i/p (IC80) 28
- A LS + 4 i/p (IC79) 29
- A LS + 4 i/p (IC80) 30
- A LS + 3 i/p (IC81) 31
- A LS + 3 i/p (IC82) 32
- GND 33
- 5V 34
- A LS + 2 i/p (IC81) 35
- A LS + 2 i/p (IC82) 36
- A LS + 1 i/p (IC81) 37
- A LS + 1 i/p (IC82) 38
- A LS i/p (IC81) 39
- A LS i/p (IC82) 40
- spare 41
- CLEAR (SN7474s) 42
- Buffer i/p 43
- Buffer o/p 44

Fig. 6.8b. Layout of the i.c.s on the "Z" register boards and function of the edge contacts, both boards being identical

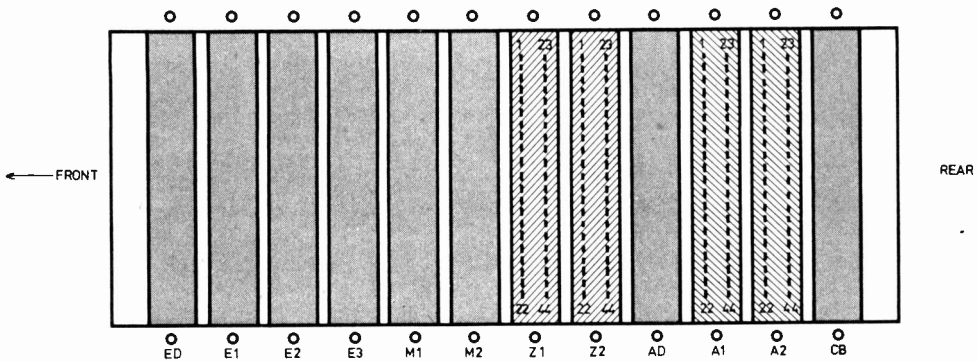


Fig. 6.9. Disposition of the edge connectors as seen from underneath the main chassis plate

CONSTRUCTION

The component layout arrangement for the A and Z register boards is shown in Fig. 6.8.

These boards have a good deal of wiring to the edge contacts due to the large number of parallel input/output wires required, and some care is required in laying this out so as not to produce very long wiring runs or large wiring concentrations.

The registers are required to perform serial shifts at high speed which means that the interconnections associated with this aspect of the circuit, i.e. everything except the parallel input/output wiring, should be kept as short as possible to reduce stray capacitance effects. With this in mind it is advisable to wire up the serial interconnections and clock lines before the rest of the wiring (which is not critical) is added.

Wiring is normally carried out on the component side of the DL109/44 boards, but it was found with the prototype that wiring congestion can be alleviated on the A1 and A2 boards by connecting the parallel output wiring to the edge contacts on the underside of the board.

EDGE CONNECTOR INTERCONNECTIONS

The edge connectors for these registers occupy the Z1, Z2, A1, and A2 positions on the chassis assembly (see Fig. 6.9), and are wired up in accordance with the wiring tables given. These tables (Fig. 6.10) are used by simply connecting the pin number required to the destination or destinations listed next to it in the table.

Each of these tables is complete, which means that a wire from the A register to the Z register will be listed in both the A and the Z register tables, so be sure to keep a record of wiring already carried out to prevent unnecessary duplication.

Again it is advisable to keep the wiring associated with serial transfers as direct as possible, and it is an idea to use a different coloured wire for these interconnections so that they may be easily identified later.

Where these serial data and clock lines exceed a few inches in length they should be routed as close to the chassis metal as possible to take advantage of its "ground-plane" properties. Interconnections to be treated with care are marked with an asterisk in Fig. 6.10.

Z1		Z2		A1		A2	
E3/9	1 23	E3/7	1 23	°AD/5	1 23	°AD/3	1 23
E3/10	2 24	E3/8	2 24	Z1/29	2 24	Z2/29	2 24
E3/15	3 25	E3/13	3 25	Z1/30	3 25	Z2/30	3 25
E3/16	4 26	E3/14	4 26	Z1/31	4 26	Z2/31	4 26
E2/9	5 27	E2/7	5 27	Z1/32	5 27	Z2/32	5 27
E2/10	6 28	E2/8	6 28	Z1/35	6 28	M2/26	6 28
E2/15	7 29	E2/13	7 29	Z1/36	7 29	M2/29	7 29
E2/16	8 30	E2/14	8 30	Z1/37	8 30	M2/30	8 30
E1/9	9 31	E1/7	9 31	Z1/38	9 31	M2/35	9 31
E1/10	10 32	E1/8	10 32	°AD/9, Z1/39	10 32	M2/36	10 32
not used	11 33	not used	11 33	°AD/10, Z1/40	11 33	GND	11 33
used	12 34	used	12 34	To display B	12 34	+5V	12 34
E1/15	13 35	E1/13	13 35	A	13 35	M1/25	13 35
E1/16	14 36	E1/14	14 36	8	14 36	M1/26	14 36
Z1/23	15 37	Z1/23	15 37	7	15 37	M1/29	15 37
Z2/23	16 38	Z2/23	16 38	6	16 38	M1/30	16 38
°Z1/19	17 39	°Z1/19	17 39	5	17 39	M1/35	17 39
°Z1/20	18 40	°Z2/20	18 40	4	18 40	M1/36	18 40
°AD/19, Z1/17	19 41	°AD/17, Z2/17	19 41	3	19 41	not used	19 41
°AD/20, Z1/18	20 42	°AD/18, Z2/18	20 42	2	20 42	CB/18°	20 42
°CB/1	21 43	°CB/1	21 43	1	21 43	CB/16	21 43
CB/13	22 44	CB/13	22 44	°AD/6	22 44	CLEAR (prog)	22 44
		Z1/15, Z2/15	Z1/16, Z2/16	Z1/27	Z1/28	Z2/27	Z2/28
		enter E (prog)	enter A (prog)	Z1/29	Z1/30	Z2/29	Z2/30
		from E* logic	not used	Z1/31	Z1/32	Z2/31	Z2/32
		not used	used	Z1/35	Z1/36	Z2/35	Z2/36
		A1/23	A2/23	Z1/37	Z1/38	Z2/37	Z2/38
		A1/24	A2/24	Z1/39	Z1/40	Z2/39	Z2/40
		A1/2	A2/2	Z1/41	Z1/42	Z2/41	Z2/42
		A1/3	A2/3	Z1/43	Z1/44	Z2/43	Z2/44
		A1/4	A2/4	Z1/45	Z1/46	Z2/45	Z2/46
		A1/5	A2/5	Z1/47	Z1/48	Z2/47	Z2/48
		A1/6	A2/6	Z1/49	Z1/50	Z2/49	Z2/50
		A1/7	A2/7	Z1/51	Z1/52	Z2/51	Z2/52
		A1/8	A2/8	Z1/53	Z1/54	Z2/53	Z2/54
		A1/9	A2/9	Z1/55	Z1/56	Z2/55	Z2/56
		A1/10	A2/10	Z1/57	Z1/58	Z2/57	Z2/58
		A1/11	A2/11	Z1/59	Z1/60	Z2/59	Z2/60
		not used	not used	Z1/61	Z1/62	Z2/61	Z2/62
		Z1/44	Z1/44	Z1/63	Z1/64	Z2/63	Z2/64
		CB/13	CB/13	Z1/65	Z1/66	Z2/65	Z2/66
		Z1/42, Z2/42	not used	Z1/67	Z1/68	Z2/67	Z2/68
			used	Z1/69	Z1/70	Z2/69	Z2/70
				Z1/71	Z1/72	Z2/71	Z2/72
				Z1/73	Z1/74	Z2/73	Z2/74
				Z1/75	Z1/76	Z2/75	Z2/76
				Z1/77	Z1/78	Z2/77	Z2/78
				Z1/79	Z1/80	Z2/79	Z2/80
				Z1/81	Z1/82	Z2/81	Z2/82
				Z1/83	Z1/84	Z2/83	Z2/84
				Z1/85	Z1/86	Z2/85	Z2/86
				Z1/87	Z1/88	Z2/87	Z2/88
				Z1/89	Z1/90	Z2/89	Z2/90
				Z1/91	Z1/92	Z2/91	Z2/92
				Z1/93	Z1/94	Z2/93	Z2/94
				Z1/95	Z1/96	Z2/95	Z2/96
				Z1/97	Z1/98	Z2/97	Z2/98
				Z1/99	Z1/100	Z2/99	Z2/100

Fig. 6.10. Interwiring details of the four edge connectors holding the "A" and "Z" register boards. The asterisks show connections which need special care

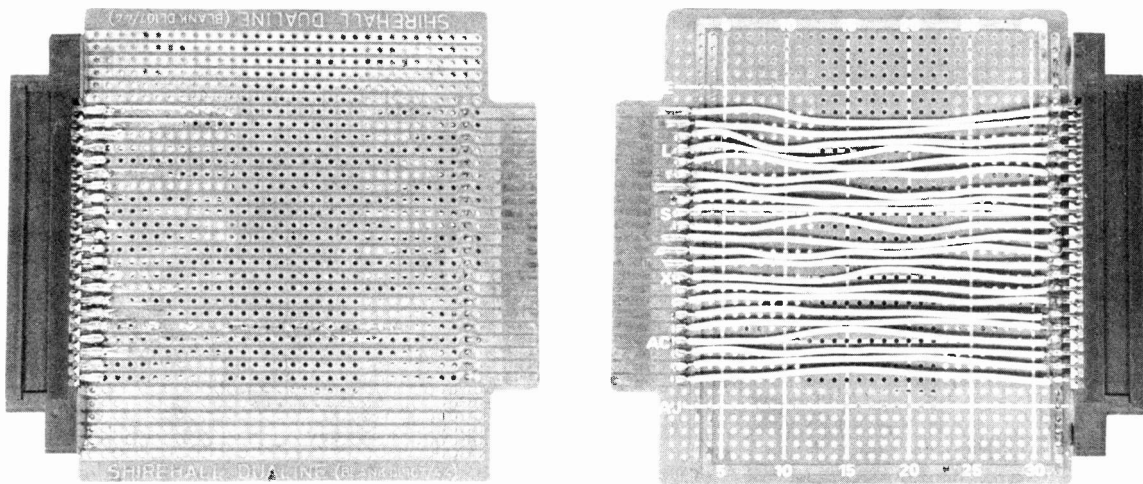


Fig. 6.11. Construction of a 44-way extension board which makes possible testing of boards in situ

TESTING

Testing these boards in an operational way is difficult at this stage and until the CLOCK board is constructed there is little that can be done except a check that the power supply lines are connected properly. For this reason it is essential that all wiring is double checked to remove wiring-up errors before proceeding.

EXTENSION BOARD

When the calculator nears completion and tests are possible in an operational situation, it will some times be required to measure a logic level, or inspect an interconnection while the logic boards are still connected in the circuit. As things stand this would prove difficult because of the close packing of the DL109 cards in their respective edge connectors.

To overcome this problem it is possible to construct an extension board which, when interposed between a particular board and its edge connector, has the effect of raising the board into a position where all its components and associated wiring are readily accessible, while still electrically connected to the rest of the circuit.

The layout for such an extension is shown in Fig. 6.11 where it can be seen that the component parts are simply an edge connector and a Shirehall DL107 board, together with some wiring.

The DL107 card is of the same physical size as a DL109, but instead of a printed wiring pattern to accept nine D.I.L. i.c.s, the DL107 has a Veroboard type of matrix, originally intended for wiring up discrete components.

The construction of the extension consists of simply soldering the 22 ways of one half of the edge connector to the DL107 strips which terminate in gold plated edge contacts, then using single core wire to connect the other 22 edge connector tags to the corresponding DL107 edge contacts on the reverse side of the board.

COMPONENTS . . .

A1, A2 BOARDS

Resistors

R67-R70 1.2k Ω $\frac{1}{4}$ W $\pm 10\%$ carbon

Capacitors

C22, C24 10 μ F 15V elect. (2 off)

C23, C25 0.047 μ F (2 off)

Integrated Circuits

IC61-64, IC69-72 SN7496 (8 off)

IC65-68, IC73-76 SN7401 (8 off)

Printed Circuit boards and sockets

Type DL109/44 boards (Shirehall) (2 off)

Type DPK165 edge connectors (Shirehall) (2 off)

Z1, Z2 BOARDS

Capacitors

C26, C28 10 μ F 15V elect. (2 off)

C27, C29 0.047 μ F (2 off)

Integrated Circuits

IC77, 78, 84, 85 SN7474 (4 off)

IC79-82, IC86-89 SN7494 (8 off)

IC83, IC90 SN7440 (2 off)

Printed Circuit Boards and Sockets

Type DL109/44 boards (Shirehall) (2 off)


Type DPK165 edge connectors (Shirehall) (2 off)

(In each case components are divided equally among the two boards which make up the A and Z registers)

The physical strength of the assembly can be improved by using a fillet of Araldite to join the edge connector and the DL107.

This simple servicing aid can come in very handy when testing any of the twelve Digi-Cal logic boards.

Next month: Clock Board.

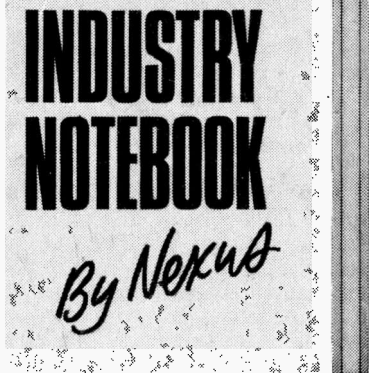

INDUSTRY NOTEBOOK

By Nexus

COLD SHIVERS

Cold shivers ran up and down quite a lot of spines for a few brief moments when Dave Griffin, Motorola's director of marketing, Northern Europe, suggested there might be another slump in the semiconductor market in 1975. There was a sharp turnaround in business in 1966/67 and the 1970/71 disaster is still painfully fresh in our memories. Is there a four-year cycle of slumps? Could be, says Griffin. Of course nobody really knows but Griffin's remarks got everybody crossing their fingers.

Griffin was speaking at a one-day seminar organised by component distributor Celdis Ltd. A hundred delegates turned up to hear the speakers in the Sculpture Gallery at Woburn Abbey. Their wives and girl friends were invited too, but they were hived off during the business sessions and enjoyed themselves watching wildlife in the Game Park and admiring the treasures in the Abbey itself.

But the sessions were by no means all gloom. Griffin came clean on Motorola forecasts which, among a great pile of statistics gave a U.K. semiconductor market worth £80 million by 1974. Big growth area was confirmed to be MOS devices which should reach £10 million worth of business in the same year. Big surprise is the market for germanium power devices which was expected to drop off very severely but which still has £4 million worth of business a year, even today.

This year, said Griffin, the U.K. market will have bought 40 million integrated circuits and 600 million discrete devices. Average selling prices have dropped since 1968. Then, the average price for a discrete device was 25 cents and for

an integrated circuit 1.8 dollars. Today the averages are 20 cents and 1.2 dollars, respectively (dollar values are used universally in this type of comparison in the semiconductor industry).

TIME AND MOTION

The automotive industry as a major consumer of semiconductors will not really take off until 1975. But electronic watches are already starting to be a good growth area. Motorola has an electronic kit which is sold to watch manufacturers. It consists of a quartz crystal, a CMOS oscillator, divider and buffer circuit equivalent to 312 transistors in a 6-lead ceramic package, and a microminiature stepping motor which drives the hands. Total power consumption is a mere 5 microamps from a 1.5V silver oxide battery which lasts for over a year.

Motorola has greatly improved the yield of the CMOS package for watches by the use of ion implantation in which dopant material is "fired" at the target at enormous velocities but in a manner which can be deliberately controlled.

Another of the speakers, Kim Morrell of Mullard, forecast expansion of the U.K. electronics industry to £1,800 million by 1980 of which some £260 million would be in components of all types. My own belief is that his figure is on the low side and we should do much better than that.

The Vice-President of RCA Solid State Europe, Dr Joe Donahue, spoke on his company's solid commitment to European operations and to broadening the market base. The decision to set up in Europe was taken only three years ago. Now, says Donahue, RCA Solid State has almost 1,000 employees in Europe, well over 500 of them at the new semiconductor plant at Liege.

TOGETHERNESS

On the theme of togetherness, Donahue reminded his audience that RCA grew out of the old British-owned American Marconi Company. That was way back in 1919 when RCA was formed at the request of the American government to acquire the Marconi interests. It was the first time I ever heard RCA even admitting British ancestry publicly, let alone boasting about it!

To round up an interesting day, Peter Turner of Hewlett-Packard spoke of the dramatic growth of the optoelectronics market. Apart from obvious uses such as displays, Turner stressed that a huge growth area lay in electrically isolated couplers. H-P has a new fast one

on the stocks promising a 20MHz bit rate with 2.5kV isolation, all in a small i.c. package. Overall optoelectronics sales in the U.K. could soar to £150 million per year by 1976 stated Turner.

So, on the whole, the news was good, especially for distributors who are currently handling some 20 per cent of all professional component supplies and are working hard to handle more.

CHATAWAY AT H-P

It was a great day for Dennis Taylor, managing director of Hewlett-Packard Ltd., when the Minister for Industrial Development, Mr Christopher Chataway, officially opened the 100,000sq ft extension to their South Queensferry plant. It more than doubles the area of the original unit built in 1966 and total employment at the plant has now risen to over 600.

Their total business in the U.K. is some £9 million and of total U.K. production 66 per cent is exported. Most famous of their instruments designed and built in the U.K. is the Microwave Link Analyser. To date over £4½ million worth have left the factory and 85 per cent went for export.

On the future, Taylor announced that they have just bought 33 acres of ground so we can expect further expansion although, chuckled Taylor, it will take a little time to expand into it. Hewlett-Packard has an R and D group of 50 people at South Queensferry and at least two completely new UK-designed instruments will be released by the end of the year.

RESETTLEMENT

An ex-editor in electronic publishing, T. Jeffrey Burton, and now a press relations consultant, has recently run a one-day seminar for RAF electronic technicians nearing the end of their service.

The idea was to give them a teach-in on the structure of the electronics industry and the job opportunities within it. Speakers include representatives of the electronics press, of the Society of Radio and Electronics Technicians (SERT), the Post Office and companies of the status of IBM and Exchange Telegraph.

Although the scientific and R and D ends of the business are not recruiting heavily at the moment, it seems that good technicians are hard to come by in the industry and are eagerly sought. The resettlement briefing, held at RAF Newton, near Nottingham, should help the boys in blue to ease themselves back into civvy street and do a good turn to the electronics industry as well.

INGENUITY UNLIMITED

A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. This is YOUR page and any idea published will be awarded payment according to its merits.

VISIBLE SPEED READOUT FOR A PROJECTOR

MANY home movie projectors rely for speed control on a rheostat which gives a film transport speed continuously variable from around 12 f.p.s. to around 25 f.p.s. This kind of control can have advantages over fixed (i.e. switched) controls, because many of the old silent films were shot at film speeds somewhere between 16 and 24 frames per second. Moreover, not all home movie cameras run at the same speed.

But anyone projecting films with a rheostat control will know that the snag with these controls is their unreliability as a positive guide to actual film speed. The same rheostat setting cannot be relied on to produce exactly the same speed on two occasions.

A few years ago I used a car tachometer or rev. counter to provide a direct visible readout of film speed.

Tachometers function by sensing the voltage pulses proportional to projector shaft speed; it is only necessary to produce low voltage pulses from the projector itself and feed them to an inductive load across which the tachometer is connected.

Experience shows that the most reliable source of pulses is from a make-and-break contact associated with the projector main drive shaft, but of course any positively driven shaft will do. All that is necessary is to attach a small spring metal strip (such as an old relay contact strip) to an insulating block which is secured (e.g. glued) to the projector chassis so that the spring strip presses against the shaft (Fig. 1).

A blob (or blobs—see later) of Araldite or other hard insulating material is painted on the shaft so that, as it revolves, the spring strip will alternately make with the metal shaft and break by contacting an insulating blob. By connecting leads between the spring strip and projector chassis (which will of course be electrically connected to the shaft) a make-and-break connection is easily achieved which can be used to produce low voltage pulses when in circuit with a low voltage source.

Tachometers or rev. counters come with two leads, one of which is red or marked "positive" for connection to the positive side of the supply.

The tachometer dial reading will not of course necessarily give a true r.p.m. reading for the projector shaft, but this is not important. By timing a film loop through the projector and marking the dial accordingly, points of reference for actual speeds of 16, 18 and 24 frames per second can be marked on the dial and the projector brought reliably to these speeds at any time in the future by operation of the rheostat.

By virtue of this arbitrary scaling, there is wide latitude of components, virtually any inductance or low voltage d.c. source that produces a healthy dial reading being acceptable. For guidance, 9 or 12 volts smoothed d.c. from a battery eliminator should be fed through the make-and-break contacts to the inductive load, for which the primary of a 5:1 transformer has proved ideal. To avoid radio or television interference, a 0.1 or 0.01 μ F capacitor should be connected across the contacts.

A. Hope,
London
N.W.3.


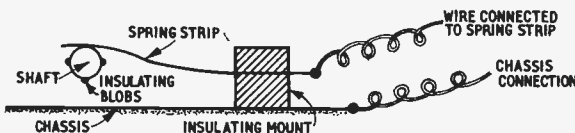


Fig. 1. Arrangement of the spring contact on the projector drive shaft. The insulating spots on the shaft can be any hard-setting glue

Fig. 2. Typical set-up for the visible speed control readout

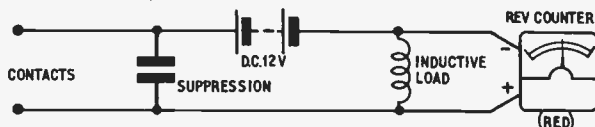

Build yourself a TRANSISTOR RADIO

WITH AFTER SALES SERVICE

ROAMER 10 WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS ALSO AIRCRAFT BAND.

Built-in ferrite rod aerial for MW/LW. Retractable, chrome plated telescopic aerial, for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Fine tone moving coil speaker. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in.

Easy to follow instructions and diagrams. Parts price list and easy build plans 30p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS


£8.50

P.P. & INS. 50p
(OVERSEAS P. & P. £1)



ROAMER EIGHT Mk. I


NOW WITH VARIABLE TONE CONTROL

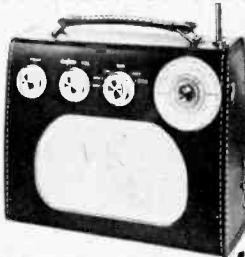

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Retractable chrome plated telescopic aerial for short waves. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 25p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£6.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)


ROAMER SEVEN Mk. IV

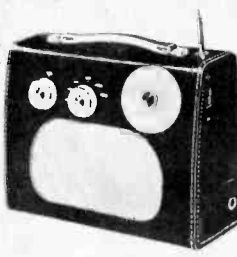

7 TUNABLE WAVEBANDS: MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Extra medium waveband provides easier tuning of Itadio Luxembourg, etc. Built-in ferrite rod aerial for MW and LW. Retractable 4 section 24in chrome plated telescopic aerial for 8W. Socket for car aerial. Powerful push-pull output. 7 transistors and 2 diodes, including micro-alloy R.F. transistors. Fine tone moving coil speaker. Air spaced ganged tuning condenser. Volume/on/off, tuning and wave change controls. Attractive case with carrying handle. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and easy build plans 15p (FREE with parts). Earpiece with plug and switched socket for private listening 30p extra.

TOTAL BUILDING COSTS **£5.98** P.P. & INS. 45p
(OVERSEAS P. & P. £1)


ROAMER SIX

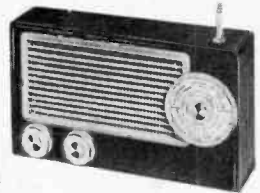

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages - 6 transistors and 2 diodes including micro-alloy R.F. transistors, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5in x 2in approx. Easy build plans and parts price list 15p (FREE with parts).

TOTAL BUILDING COSTS **£3.98** P.P. & INS. 30p
(OVERSEAS P. & P. £1)


POCKET FIVE

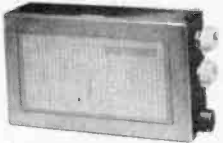

3 TUNABLE WAVEBANDS: MW, LW, TRAWLER BAND WITH EXTENDED MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. 7 stages - 5 transistors and 2 diodes, super-sensitive ferrite rod aerial, fine tone moving coil speaker. Attractive black and gold case. Size 5in x 1in x 3in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.29** P.P. & INS. 23p
(OVERSEAS P. & P. 63p)

TRANSONA FIVE

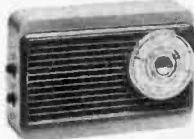


5 TRANSISTORS AND 2 DIODES

3 TUNABLE WAVE BANDS: MW, LW AND TRAWLER BAND. 7 stage - 5 transistors and 2 diodes, ferrite rod aerial, tuning condenser, volume control, fine tone moving coil speaker. Attractive case with red speaker grille. Size 6in x 4in x 1in. Easy build plans and parts price list 10p (FREE with parts).

TOTAL BUILDING COSTS **£2.50** P.P. & INS. 24p
(OVERSEAS P. & P. 63p)

TRANS EIGHT

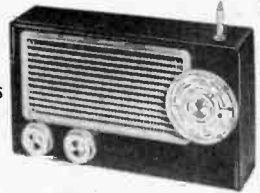

8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS: MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5in x 2in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and easy build plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£4.48** P.P. & INS. 32p
(OVERSEAS P. & P. £1)



NEW! "EDU-KIT"

BUILD RADIOS, AMPLIFIERS, ETC., FROM EASY STAGE DIAGRAM. FIVE UNITS INCLUDING MASTER UNIT TO CONSTRUCT. Components include: Tuning Condenser: 2 Volume Controls: 2 Slider Switches: 3" Speaker: Terminal Strip: Ferrite Rod Aerial: 3 Plugs and Sockets: Battery Clips: 4 Tag Boards Balanced Armature Unit: 10 Transistors: 4 Diodes: Resistors: Capacitors: Three 1/2in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction.

ALL PARTS INCLUDING CASE AND PLANS **£5.50** P.P. & INS. 32p
(OVERSEAS P. & P. £1)

RADIO EXCHANGE LTD

61 HIGH STREET, BEDFORD.

Tel. 0234 52367

I enclose £..... please send items marked

- | | | | |
|---------------|--------------------------|--------------|--------------------------|
| ROAMER TEN | <input type="checkbox"/> | ROAMER SEVEN | <input type="checkbox"/> |
| ROAMER EIGHT | <input type="checkbox"/> | TRANS EIGHT | <input type="checkbox"/> |
| TRANSONA FIVE | <input type="checkbox"/> | ROAMER SIX | <input type="checkbox"/> |
| POCKET FIVE | <input type="checkbox"/> | EDU-KIT | <input type="checkbox"/> |

Parts price list and plans for.....


Name

Address

P.E. 48

FULL AFTER SALES SERVICE

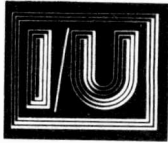★ Callers side entrance "Lavell" Shop
★ Open 10-1, 2.30-4.30 Monday-Friday, 9-12 Saturday



LIGHT CONTROL

RECENTLY I set about designing a system to enable me to remotely switch on and off two or more table lamps. I wished to be able to switch the lights on and off at any of three points regardless of the state of the switches at the other two.

This I decided could best be achieved by placing an electrically alterable bistable switch near the power point that fed the two lamps and running a twin flex lead from the bistable, connecting the three switches in parallel. Pushing on and releasing any switch would then change the bistable from on to off, or off to on depending on its history.

Since I had several suitable relays, and triacs are a little costly, I decided to use a relay to do the actual work of switching the lamps. The circuit I originally tried was the conventional type of bistable.

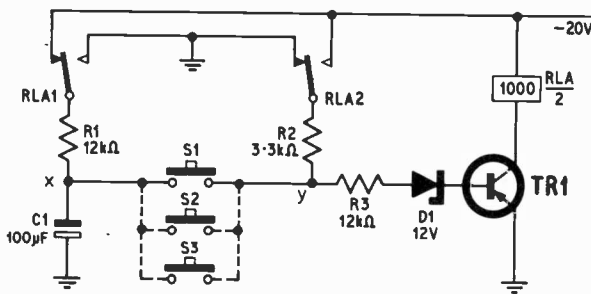


Fig. 1. Circuit diagram of the light control

Unfortunately, it had the disadvantage of requiring a fast edge to switch reliably, a faster edge than one could hope to regularly achieve with a mechanical switch. This meant, therefore, placing a monostable between the mechanical switch and the bistable. A rethink at this point produced the circuit shown in Fig. 1.

If TR1 is off and S1 is open, contacts RLA1 and RLA2 will be closed, point y will be at zero potential and capacitor C1 will charge to -20V through R1. If S1 is then closed, point y is reduced to the potential of point x, i.e. -20V. The Zener diode D1 then conducts, resistor R3 limiting the current, and TR1 switches on. The relay is energised and the relay switches over.

The circuit will now take the form shown in Fig. 2, points x and y at $\frac{12 \times 20}{3.3 + 12}$ negative volts (approximately -16V), which is just sufficient to maintain TR1 conducting. When S1 is opened again, point y goes to -20V potential maintaining TR1 in conduction; capacitor C1 discharges through R1 to zero.

When S1 is pressed close, point y is reduced instantaneously to zero, TR1 switches off and the relay contacts revert back to their original state.

Points x and y should now be at $\frac{3.3 \times 20}{3.3 + 12}$ negative volts (roughly -4V), insufficient to cause the Zener diode to conduct and TR1 remains off. When S1 is released (open) y goes to zero and x charges to -20V through resistor R1. The cycle may now be repeated.

Because of the delay in charging capacitor C1 the circuit will only change state when there is a minimum of two seconds delay between switching pulses, i.e. between S1 going off and coming on again. In certain circumstances this could be useful.

The delay could be reduced by reducing the values of R1 and R2 or C1. This is limited of course since C1 must not be allowed to charge or discharge through R2 in that instant when S1 is closed and the relay has not switched; in other words the minimum values of C1, R1 and R2 are primarily limited

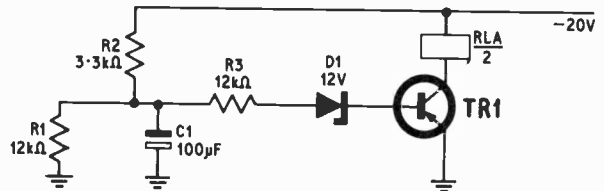


Fig. 2. Effective circuit when S1 is closed

by the inertia of the relay. It should also be remembered that lower values of R1 and R2 will require greater transient power pulses from the supply.

It was found that the bistable operated satisfactorily with up to about 50 ohms between S1 and point x. Line resistance to S1 is therefore not important.

The switch pulse duration may be any length from a few hundred milliseconds (sufficient to switch the relay) to infinity.

The power supply is not critical and a bell transformer driving an unregulated voltage doubler was found satisfactory. Using a G.P.O. 1,000 ohm relay the circuit uses approximately 20mA when switched on, and negligible current in the off state.

Any relay with double changeover contacts, other than very low coil resistance types, should work. The line voltage should be approximately the relay working voltage. The Zener diode should be $0.6 \times$ line voltage. Additional heavy duty contacts would be required for switching the lamps.

An *npn* transistor may be used in the circuit if preferred. In this case the Zener must be reversed, and the supply and electrolytic polarities changed.

P. King,
Withington,
Manchester.



THE circuit depicted in Fig. 1. was designed to automatically control the running of two trains through a single-line section, both trains always travelling in the same direction as each other.

Referring to Fig. 2, points A and B are set for the inner loop. Whilst train 2 is travelling round the single-line loop train 1 is held in isolating section X. Isolation of sections X and Y is controlled by the points blades at B. Track current is fed to either X or Y not both.

As train 2 passes position L, it interrupts a light beam focused on a light dependent resistor PCC1 (Fig. 1.) thereby triggering the desired sequence of switching operations. First point A changes to outer and then point B also changes to the outer track.

When point B is set for the outer section, current is fed to section X, train 1 starts up and proceeds around the single line section; the sense of points B will cause train 2 to halt in section Y.

from the collector of TR1 switches on TR2 and TR3, which in turn energises RLA.

Relay RLA, however, remains closed for a very short time until capacitor C1 has charged up and consequently switched off TR2 and TR3. Relays RLA and RLB are wired in a master-slave relationship, for while RLA is closed a secondary set of its contacts is being used to charge up capacitor C2, via R6 and the RLA1 contacts P and R. When RLA drops out contact P makes contact with contact Q (its normal state) and capacitor C2 discharges via R7 and TR4 base. This then switches on TR4 and TR5, but as before the pulse is momentary, until C2 has discharged sufficiently to reverse bias TR4.

After one cycle of operations has been completed, further triggering is not possible until after a delay (approximately 10sec) during which C1 discharges.

If desired, a variable resistor may be substituted for R2 to provide sensitivity control of the PCC1. The relays used were 12V types. The contacts on RLA2 need to be of the break-before-make type, but the contacts RLA2 and RLB1 need only be simple on-off types; normally off.

The light source used was an ordinary flashlight bulb masked to shine through a 1/4in aperture into a 3in long cardboard tube housing PCC1 at the far end.

J. Duffill, Southam.

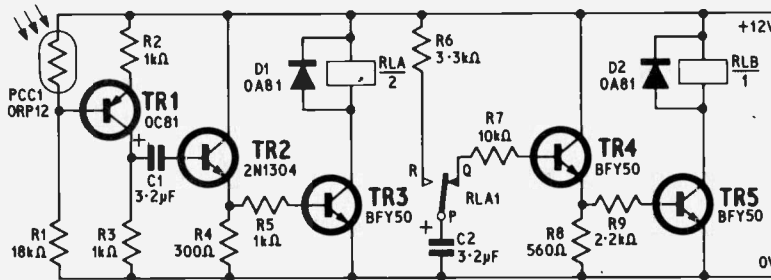


Fig. 1. Circuit diagram for the light operated model train controller. Note that C1 and C2 are electrolytics

As train 1 now passes position L it triggers off the same switching sequence as before, except this time the moving train is now on the outer loop and the points are therefore changed from outer to inner. By the time train 1 is halted in section X train 2 is on the move again, we are back at the beginning of the sequence of operations and the whole cycle repeats.

The points are actuated by point motors which consist of a 2-coil solenoid and an independently wired 2-way switch that changes synchronously with the points motor, see Fig. 3. Since for reliable operation these motors need a relatively high current, it was arranged to operate them in sequence. They also require a one-shot pulse to avoid overheating the coils.

The pulses are supplied by sets of contacts on the relays RLA2 and RLB1, which close in sequence. The cross-wiring of the 2-way switches on the points motors (Fig. 3) provides a flip-flop arrangement by which the closing of RLA2 causes point A to change to the sense determined by the setting of the switch S2 on the points motor M2. Similarly, when RLB1 closes, immediately on RLA2 dropping out, point B changes under control of the switch S1 on motor M1.

The circuit Fig. 1 comprises two relay buffer stages and a light-operated circuit for triggering. Interruption of the light beam at L causes TR1 to switch on because of the increased resistance of PCC1. Current

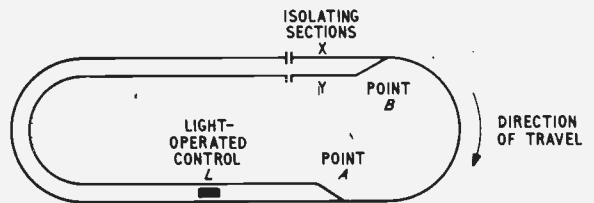


Fig. 2. Typical track layout

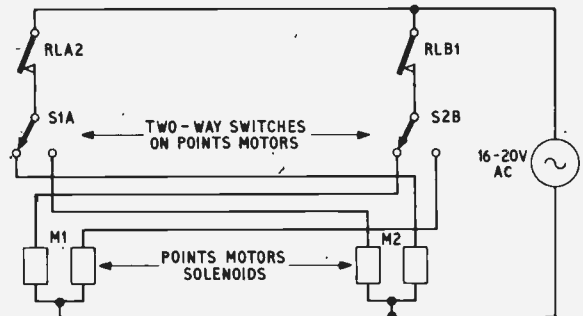


Fig. 3. Switch wiring arrangement

G. F. MILWARDMail Orders: **DRAYTON BASSETT, TAMWORTH, STAFFS.**

ELECTRONIC COMPONENTS

Wholesale/Retail

369 Alum Rock Road, Birmingham B8 3DR.

Tel. 021-327 2339

INDUSTRIAL USERS!

We have access to some of the largest stocks of transistors and I.C.s in Europe. Regret that it is not possible to supply less than 100 of any one type at these prices. Please phone or write for immediate quote should types you require not be listed.

AD 149	.. 34p each	2N 1711	.. 9p each	2N 5179	.. 38p each
AD 161/162	.. 35p pair	2N 3053	.. 11p each	709C (TO5 or DIL)	25p
BD 137/138	.. 46p pair	2N 3055	.. 31p each	741C (TO5 or DIL)	27p
2N 1613	.. 8p each	2N 3053/4037	.. 34p pair	723C (TO5 or DIL)	40p

NEWER THAN NEW!!!!

Fibre Glass Board pre-treated with light-sensitive lacquer enabling you to produce prototype printed circuits within five minutes.

75mm x 100mm	.. 33p
150mm x 100mm	.. 66p
150mm x 200mm	.. £1.32

Epoxy-Resin

75mm x 100mm	.. 22p
100mm x 150mm	.. 44p
150mm x 200mm	.. 88p

Plain Fibre Glass Board

290mm x 175mm	.. 45p
---------------	--------

Bakelite Laminated Board, 1.57mm thick

1 sq. foot	.. 50p
------------	--------

Special Offer Pack consisting of 5 2 1/2in x 1in boards and a Spot Face Cutter—50p. "ODDS & ENDS"—1p sq. in.

VEROBOARD

2 1/2in x 1in x 0.15in	6p
3 1/2in x 2 1/2in x 0.15in	16p
3 1/2in x 3 1/2in x 0.15in	20p
5in x 2 1/2in x 0.15in	20p
5in x 3 1/2in x 0.15in	28p
17in x 2 1/2in x 0.15in	55p
17in x 3 1/2in x 0.15in	74p
3 1/2in x 2 1/2in x 0.1in	21p
3 1/2in x 3 1/2in x 0.1in	24p
5in x 2 1/2in x 0.1in	23p
5in x 3 1/2in x 0.1in	28p

Spot Face Cutter 38p. Pin Insert Tool 48p. Terminal Pins (0-1 or 0-15) 36 for 18p.

NEW! NEW! NEW! NEW!

An aerosol spray providing a convenient means of producing any number of copies of a printed circuit both simply and quickly.

Method: Spray copper laminate board with light sensitive spray. Cover with transparent film upon which circuit has been drawn. Expose to light. (No need to use ultra-violet.) Spray with developer, rinse and etch in normal manner.

Light sensitive aerosol spray .. £1.00 plus

Developer and Etchant .. 50p postage

TRANSISTORS AND INTEGRATED CIRCUITS

FJH231/7401N	.. 12p	Quadruple 2-input positive gate	.. 12p
FJH111/7420N	.. 12p	Dual 4-input NAND gate	.. 12p
FJH141/7440N	.. 12p	Dual 4-input NAND buffer gate	.. 12p
FJH171/7453N	.. 12p	8-input AND/OR/NOT 2-level logic circuit	.. 12p
FJ1101/7470N	.. 24p	Master Slave JK flip-flop	.. 24p
FJ1131/7474N	.. 32p	Edge-triggered dual D-type flip-flop	.. 32p
FJH201/7482N	.. 88p	2-bit binary full adder	.. 88p
FJ1151/7491AN	.. 78p	8-bit shift register	.. 78p
and FJ1271	.. 58p	4-bit binary counter	.. 58p
FJ121/7492N	.. 58p	4-bit binary counter	.. 58p
FJ121/7493N	.. £1.00	64-bit read/write random access memory	.. £1.00
FEQ101	.. 27p	Operational amplifier	.. 27p
709	.. 35p	As 709 but with internal frequency compensation	.. 35p
741	.. 35p		

ELECTROLYTIC CAPACITORS	AXIAL LEADS		
2,000µf 25 volt Rev.	25p	250µf 25 volt	.. 10p
1,000µf 70 volt	.. 35p	500µf 25 volt	.. 13p
10,000µf 35 volt	.. 50p	1,000µf 25 volt	.. 16p
10,000µf 25 volt	.. 35p	2,000µf 25 volt	.. 25p
60µf + 200µf 300 volt	.. 30p	2,500µf 50 volt	.. 30p
10µf 6 volt	.. 2p	400µf 4 volt	.. 20p
10µf 25 volt	.. 4p	125µf 4 volt	.. 3p each
16µf 250 volt	.. 8p	400µf 6.4 volt	.. 3p each
32µf 275 volt	.. 8p	320µf 10 volt	.. 3p each
Miniature type. Both wires same end.	.. 16µf 16 volt	.. 320µf 2.5 volt	.. 3p each
5µf 10 volt	.. 3p each	125µf 4 volt	.. 3p each
30µf 10 volt	.. 3p each		
50µf 10 volt	.. 3p each		
220µf 25 volt	.. 3p each		

AEY131	£5.00	BTY95/100R	£3.00	CL7331	£20.00
AEY162	£10.00	BTY99/100R	£4.00	CL8370	£10.00
AEY173	£4.00	BTY99/200R	£5.00	CL8380	£10.00
AZ292 (9-lv, 7w)	25p	BTY99/300R	£5.00	CL8470	£40.00
BC108	7p	BTX37/500R	£4.00	CV7700	£1.00
BC109	7p	BTX37/700R	£5.00	CV7747 (BCY40)	25p
BCY71	10p	BTX50/110R	£5.00	CAY10	£5.00
BD112	25p	BTX66/500R	£5.00	DW7662 (BC115)	5p
BF194	7p	BTX66/600R	£5.00	GET113	5p
BF1804	25p	BTX66/700R	£7.00	OC41	3p
BFS18R	10p	BTX75/100R	50p	OC42	3p
BFS19	10p	BTX83/600R	£2.50	OC43	3p
BFR64	£1.00	BXY27	£1.00	OC46	3p
BFY53	5p	BXY28	£1.00	OC74	4p
BTY34/400	£1.00	BXY35C	£1.00	OCP70	50p

G. F. MILWARD, Drayton Bassett, Tamworth, Staffs. Postage (minimum) per order 15p



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO SCHOOL
READING, BERKS

NAME :

EB 122

ADDRESS :

BLOCK CAPS please

FAST, RELIABLE SERVICE

For
ELECTRONIC COMPONENTS

Send now for a

CATALOGUE


5th EDITION

and
DISCOUNT VOUCHERS
25p POST FREE (UK)

W.E.C. LTD.

High Street, Ripley, Surrey
ESTABLISHED 1954

6 WATT STEREO

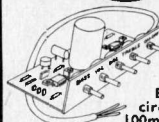

Base your own stereo system on one of these super quality stereo amplifiers. With low distortion levels (averaging 0.2%) and total power of 6W r.m.s. (8 load 3W/channel) they will give you a

rousing dynamic performance with good speakers. Each has two of the well proven Plessey integrated circuit amplifiers with built in pre-amp sections providing 100mV sensitivity and with a band width of 50-15kHz, are ideal for tuners and crystal pick-ups. The circuit features controls for Bass, Treble, Volume, and Mains on/off. All leads and Din Plugs and Sockets can be supplied. All units fully guaranteed.

602 Amplifier as above (5inW x 6jinD) £7.48

601 Amplifier as above but with single tone control (8jinW x 2jinD) £5.95

Mains Transformer (14V) for 600 series amps 98p

Lead, plug and socket set 38p

Cheques, P.O.'s. plus 25p post and packing, to:

the **AUTOTRON** company, Hixon, Stafford



Two flash units from Honeywell

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned.



Adcola Products Soldering pack

SOLDERING PACK

Certainly an ideal kit to present as a gift to anyone, particularly at this time of the year, the new **Adcola Products** soldering kit contains all the essentials for simple soldering jobs. The kit contains an Invader soldering iron, a stand, solder wire, two spare soldering tips and an instruction card providing useful hints on successful soldering.

The soldering iron is thermally controlled to provide a constant heat level for ease of soldering. The standard soldering tip provided is $\frac{1}{8}$ in diameter, but two replacement tips of $\frac{1}{16}$ in and $\frac{1}{4}$ in diameter are included to provide complete versatility for a 25W iron. The tips are merely inserted in the collar at the end of the iron to convert it from one task to another.

The stand provided with the kit features an integral sponge for cleaning excess solder from the tips and two holes to contain the spare tips. A spring holder is mounted on the base of the stand at an angle of about 45 degrees to take the iron when not in use.

The kit costs £3.99 and all the components are contained in a plastics tray featuring compartments for each component for safety in transit. The kit should be available from most d.i.y. shops, ironmongers or direct from Adcola Products Ltd., Adcola House, Gauden Road, London, S.W.4.

EMERGENCY LANTERN

With the forecast that power cuts are again probable this winter, it is wise to plan ahead for the eventuality and to have some form of emergency lighting handy.

A useful lamp is the "Safety Lantern" available from **Harris Marketing**. It is claimed to be virtually unbreakable, having a safe plastic dome which gives a 360 degree light and is powered by a 6V 996 battery.

It is particularly suitable around the home where there may be children or elderly people, for whom candles and other naked lights would be a danger, but it also makes a useful car, caravan or camping light.

Available direct from **Harris Marketing**, 16 Hillcroom Road, Sutton, Surrey, the lamp costs £1.85 plus 15p post and packing.


PHOTOGRAPHIC EQUIPMENT

Famous for their work in the computer field **Honeywell** have announced their entry into the photographic world with a range of electronic flash equipment, 35mm slide projectors and darkroom equipment.

Available in this country through **Photo-Science Ltd.**, the range of equipment includes automatic flash units and slave flash units.

Also included in their range of products are four automatic self-focusing projectors with a special built-in preview screen. These models enable the projectionist to see each slide on a small screen before it is projected to the audience.

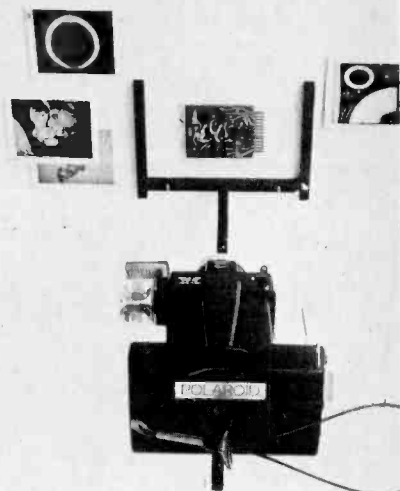Two of the flash units represent Honeywell's latest technological advancements in this field, which they call "strobe-eye" remote sensing. The sensor device is completely separated from the flash so that the light can be controlled from the camera or wherever the photographer desires.



Instant copying kit by Polaroid

These two flash units are described by Honeywell as the only system that will give accurate automatic exposure control of on-camera, off-camera and wall- or ceiling-bounce flash lighting.

Further particulars of the complete range of Honeywell photographic equipment can be obtained from **Photo-Science Ltd.**, Charfleet Road, Canvey Island, Essex.

INSTANT COPY KIT

An inexpensive instant copy kit and accessories, providing a complete photographic copying system, is being introduced by **Polaroid (UK) Ltd.** Both the copy kit and accessory unit are designed for use with any of three Polaroid instant picture cameras.

Ideal for making copies from a master design of printed circuit patterns to any required size, the Polaroid 105-1 kit gives a $\frac{3}{4}$: 1 reduction. The kit consists of a copy stand, close-up lens in mount, blue filter (for colour film used with tungsten light), polarising filter (for flash only), Colorpack 80 camera and a carrying case.

The complete kit costs £38.95; without a camera the kit retails at £24.

The 106 Instant Copy Kit accessory unit, comprising a copy stand and close-up lens for $\frac{1}{2}$: 1 copies, will retail for £15.00.

EXTENSION LEADS

It has been brought to our attention that the price quoted for the Portapower cable reels mentioned in our September issue does not include the cost of cable.

We apologise for any inconvenience this may have caused.

Readout—

A SELECTION FROM OUR POSTBAG

Correspondents wishing to have a reply must enclose a stamped addressed envelope. We regret we are unable to guarantee a reply on matters not relating to articles published in the magazine. Technical queries cannot be dealt with on the telephone.

Correct perspective

Sir—Mr Hickman (*Readout*, November issue) has raised the question of component cost in Australia, a point certainly omitted from the first *Report from Australia*. Detailed costings of parts were not quoted, as indeed many other aspects of home construction were omitted, due mainly to space considerations; it was intended only as an introduction.

However, since the subject has been raised, the question of component cost must be placed in the correct perspective. In Sydney and Melbourne, the BC108, if we are to use this device as an example, can be bought at the rate of 6 for \$2.00 (16p each) including sales (purchase) tax. The figures as quoted by Mr Hickman may be applicable to South Australia, but it is indeed a half-truth to suggest that his situation applies throughout Australia.

The cost of components generally must, in any case, be viewed against the background of higher salaries here. It has been stated that, for many professional occupations, salaries are very roughly 50 per cent higher than in the U.K.

I would agree with your correspondent's comments regarding Australian conditions, particularly those

in respect of the somewhat over-glamorised publications for which Australia House is now famous.

Finally, Mr Hickman is under the illusion that I am Australian, and tend to avoid comparisons. I myself migrated from England some five years ago.

J. Waldie,
Tamarama, N.S.W.,
Australia.

The defender

Sir—I would like to come to the defence of your constructional features in general and R. W. Coles' "P.E. Digi-Cal" in particular.

I doubt whether I will ever build the Digi-Cal, but the detailed way in which its operation is explained by the author has added measurably to my understanding of the logic functions involved. If such features are to be excluded because of a cost disadvantage compared with custom built devices, we amateurs will be deprived of much needed design know-how.

I have to confess that I jumped the gun by buying the Minitrans before the total cost of parts was revealed. Doubtless they will come

in handy one day—but it might be an idea if project-authors revealed the approximate cost of components at the outset and saved me impeccable constructors the embarrassment of having to abandon a project after buying a few of the items needed.

J. A. Burness,
Herts.

Valuable learning

Sir—I noticed a number of letters in the October issue of P.E. that objected to the Digi-Cal on monetary and aesthetic grounds. The question was raised, why should you publish an article outlining the construction of a calculator when the basic i.c. is now available.

I can certainly construct a very simple calculator around one of the many calculator integrated circuits that are now available, but this teaches me nothing new about digital electronics. Even though I may not want to build the Digi-Cal, I have certainly been able to follow along with the author and now I have a better understanding of how these devices work. Maybe I have also picked up some new ideas on how to do things such as keyboard multiplexing and readout demultiplexing. That is as valuable as learning the basic operations of a calculator.

Many electronic hobbyists here in the USA are all too ready to put together a kit that teaches them nothing and tests only their ability to follow directions. Most of the electronic publications here cater to these individuals and that is why I subscribe to P.E. Keep up the good work.

Jonathan T. Titus,
President,
Titus Labs,
Blacksburg, USA.

BACK NUMBERS WANTED

Anyone who can supply the undermentioned are asked to communicate directly with the reader.

March—April 1971

Mr R. Brown, P.O. Box 926, Chingola, Zambia.

July 1969

Mr K. Farrance, Charity Cottage, High Rougham, Bury St Edmunds, Suffolk.

February 1971

Mr D. J. Hitchcock, 38 Deakin Street, Hampton 3188, Melbourne, Victoria, Australia.

December 1966

Mr M. Robson, 8 Withipoll Street, Ipswich, Suffolk.

February, March, May 1971

Mr T. J. Hsieh, 39 Gold Jade Road, Kuching, Sarawak.

January 1968

Mr G. Hart, 41 Waterloo Road, London N19 5NJ.

August 1966

Mr R. A. Hume, 93 Sinclair Drive, Glasgow G42 9PU.

December 1970 to March 1971

Mr J. Jeffrey, 65 Sandmoor Road, Errington Park, New Marske, Redcar, Teesside.

May 1969 to March 1970

Mr L. W. Burton, 32 Castleton Farm, St Athan, Barry, Glamorgan.

April 1972

Mr M. P. Baker, 14 Cabell Road, Park Barn Estate, Guildford, Surrey.

September 1966, January, June, July, August 1967

Mr B. S. Stuck, 28 Chancelot Road, Abbey Wood, London SE2 0NB

July 1972

Mr P. J. Joyce, 21 Eggington Court, Loughborough University, Leicestershire.

December 1970 to March 1971

Mr A. Jones, Tyddyn Slaters, Pontrug, Caernarvon, North Wales.

November 1971 to March 1972

Mr C. Wright, 98 Swallow Road, Ipswich, Suffolk.

July 1969

Mr M. Armitage, Oakendean, 12 Shanter Way, Alloway, Ayrshire.

May to October, December 1969

Mr W. J. Miller, Dailard, 13 Adler Road, Glasgow S3.

November 1970 to March 1971

Mr J. Maplesden, 47 Oldford Crescent, Acklam, Middlesbrough, Teesside, TS5 7EH.

January—February 1971

Mr C. E. R. Flynn, A.P.C. Ltd., Dungeness Power Station, Romney Marsh, Kent.

May 1972

Mr N. Tawse, 25 Welland Road, Edith Weston, Oakham, Rutland, LE15 8JE.

May 1969 to February 1970

Mr S. P. Ganecki, 17 Belmont Close, Churchbridge, Cannock, Staffordshire.

November—December 1971

Mr H. D. Westwood, 12 Cairn Walk, Crumlin, Co. Antrim, N. Ireland.

June 1969

Mr J. E. Marshall, 4 Dellcott Close, Welwyn Garden City, Herts.

April—May 1971

Mr A. E. Thompson, 3 Uxbridge Court, Uxbridge Road, Kingston.

November 1971

Mr G. C. Street, 21 Linton Crescent, Hastings, Sussex.

July 1970 to May 1971

Mr R. Konarek, 573 Daws Heath Road, Hadleigh, Benfleet, Essex.

May, June, July, Sept., Oct., Nov., Dec. 1969, January to April, August 1970

Mr J. Shapero, 64 Tixall Road, Birmingham, B28 0RS.

April—July 1971

Mr K. McKegney, 21 Queen Street, Chesterfield, Derbyshire, S40 4SF.
Up to Oct. 5.

We regret that back numbers of Practical Electronics can no longer be supplied. We will try to publish announcements of readers' requirements (without a guaranteed date) free of charge.

introducing

ARROW ELECTRONICS LTD.

'Service the way it ought to be'

an associate Company of LST ELECTRONIC COMPONENTS LTD.

When it comes to retail distribution we're head and shoulders above the rest!

We're a new Company but our experience and ability in electronic components goes back a long way . . .

Here at Arrow Electronics fast, reliable service is law!

We offer a rapid, same day turn round on all mail received up to 3 p.m. on any given weekday.

What's more, when we promise to clear all orders on receipt, we really mean it!

A SELECTION FROM OUR CATALOGUE

COS-MOS-CIRCUITS

This range of COS-MOS Logic is stocked in DIL plastic encapsulation. This range offers High reliability, high speed operation, high level output compatability with low power TTL and high noise immunity.

Type No.	Description	Price each
CD4001AE	Quad 2 input NOR gate	72p
CD4009AE	Hex. buffer — inverting type	£1.56
CD4011AE	Quad 2 input NAND gate	72p
CD4012AE	Dual 4 input NAND gate	£1.16
CD4013AE	Dual "D" Flip-Flop	£1.48
CD4015AE	Dual 4 stage Shift Register	£3.90
CD4017AE	Decade Counter/Divider with Decimal outputs	£3.90
CD4018AE	Presetable divide by "N" Counter	£3.90
CD4020AE	14 Stage Ripple Binary Counter/Divider	£4.34
CD4024AE	7 Stage Counter (Buffered Reset)	£2.78

Order as "COSMOS" + Type No.

INTEGRATED CIRCUIT SOCKETS

These low cost sockets are moulded in Makrolon with Phosphor Bronze contacts, silver plated.

Type No.	Description	Price
DRD7	14 pin Dual in Line	14p each
DRD8	16 pin Dual in Line	15p each

Order as "DIL Sockets" + Type No.

LIGHT EMITTING DIODE

Type No.	Description	Price
TIL209	High brightness visible light source	35p each

OPTICALLY COUPLED ISOLATOR

Type No.	Description	Price
TI112	GA source optically coupled to NPN transistor giving high DC transfer ratio with high electrical isolation of 1.5kV.	£2.00 each

RECTIFIERS — MEDIUM CURRENT

Plastic cased rectifiers with 3A current capability. Miniature size and axial leads make them particularly useful for Printed circuitry.

Type No.	If (Amps)	PIV	Price
1N5400	3 A	50	14p each
1N5404	3 A	400	18p each
1N5408	3 A	1000	25p each

Shoot me your catalogue

Arrow Electronics Limited

Dept.

7 Coptfold Road

Brentwood Essex

Tel: Brentwood 219435

PE4

 / enclose P/O Cheque for 10p.
 Name _____
 Address _____

Have fun with electronics...



Radionic Construction Kits



NO SOLDERING BATTERY OPERATED

Build your own radio receiver and many exciting experiments with the unique printed circuit board and mounted components. Easy to build, no soldering, battery operated, plus a fully illustrated instruction manual giving precise directions for each experiment. Ideally suitable for both the experimenter and beginner.

Radionic Products Limited

St. Lawrence House, Broad Street, Bristol BS1 2HF.
Tel: 0272 25351

Member of the ESL BRISTOL Group of Companies.

Please send me literature on Radionic radio and electronics construction kits.


NAME _____

ADDRESS _____

PE 2

Sinclair Project 60

Project 60 Stereo FM Tuner

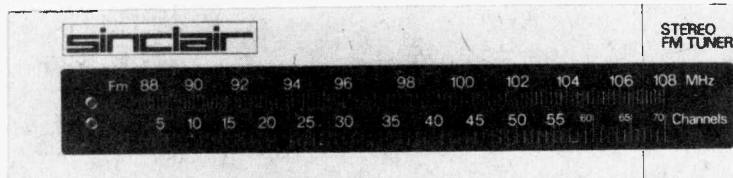

Built and tested.
Post free.
£25


with phase lock-loop principle

Amongst the many advanced electronic features to be found in this remarkable stereo tuner, use of the phase lock loop principle ensures standards of audio quality better than from any other method of detection yet used. Varicap diode tuning, accurately formed printed circuit coils, an I.C. in the special stereo decoder section and switchable squelch circuit for silent tuning between stations contribute to the unsurpassed performance of this tuner, irrespective of price consideration. But the Project 60 FM Stereo Tuner is far from expensive – indeed, it offers fantastic value for money and will bring the thrill of stereo radio to many who previously may not have been able to afford it. The tuner may be used with any good system as well as Project 60, but if you use it with other Project 60 modules, you will find the matching front panels particularly impressive in appearance as well as function.

SPECIFICATIONS

Number of transistors: 16 plus 20 in I.C.
Tuning range: 87.5 to 108MHz.
Sensitivity: 7µV for lock-in over full deviation.
Squelch level: typically 20µV.
Signal to noise ratio: ±65dB.
Audio frequency response: 10Hz–15KHz (±1dB).
Total harmonic distortion: 0.15% for 30% modulation.
Stereo decoder operating level: 2µV.
Cross talk: 40dB.
Output voltage: 2 x 150mV R.M.S. max. (typically 2 x 50mV, stereo)
Operating voltage: 25–30V DC at 100mA.
Indicators: Stereo on: tuning.
Size: 93 x 40 x 207mm.

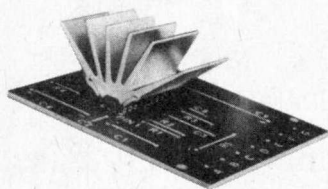Super IC.12 Integrated circuit high fidelity amplifier



Having introduced Integrated Circuits to hi-fi constructors with the IC.10, the first time an IC had ever been made available for such purposes, we have followed it with an even more efficient version, the Super IC.12, a most exciting advance over our original unit. This needs very few external resistors and capacitors to make an astonishingly good high fidelity amplifier for use with pick-up, F.M. radio or small P.A. set up, etc. The free 40 page manual supplied, details many other applications which this remarkable IC, make possible. It is the equivalent of a 22 tran-

sistor circuit contained within a 16 lead DIL package, and the finned heat sink is sufficient for all requirements. The Super IC.12 is compatible with Project 60 modules which would be used with the Z.50 and Z.30 amplifiers. Complete with free manual and printed circuit board.

SPECIFICATIONS

Output power: 6 watts RMS continuous (12 watts peak), 6–8Ω. **Frequency Response:** 5Hz to 100KHz±1dB. **Total Harmonic Distortion:** Less than 1%. (Typical 0.1%) at all output powers and frequencies in the audio band (28V). **Load Impedance:** 3 to 15 ohms. **Input Impedance:** 250 Kohms nominal. **Power Gain:** 90dB (1,000,000,000 times) after feedback. **Supply Voltage:** 6 to 28V. **Quiescent current:** 8mA at 28V. **Size:** 22 x 45 x 28mm including pins and heat sink.

Manual available separately 15p post free.

With FREE printed circuit board and 40 page manual.

£2.98 Post free

Project 605



The easy way to buy and build Project 60

Project 605 is one pack containing: one PZ5, two Z30's, one Stereo 60 and one Masterlink. This new module contains all the input sockets and output components needed together with all necessary leads cut to length and fitted with neat little clips to plug straight on to the modules. Thus all soldering and hunting for the odd part is eliminated. You will be able to add further Project 60 modules as they become available adapted to the Project 605 method of connecting.

Complete Project 605 pack with comprehensive manual, post free **£29.95**

Everything you need to assemble a superb 30 watt high fidelity stereo amplifier without having to solder.

sinclair

Sinclair Radionics Ltd, London Road, St. Ives, Huntingdonshire PE17 4HJ. Tel: St. Ives 64311


the world's most advanced high fidelity modules

Z.30 & Z.50 power amplifiers

Built, tested and guaranteed with circuits and instructions manual. **Z.30 £4.48** **Z.50 £5.48**

The Z.30 and Z.50 are of advanced design using silicon epitaxial planar transistors to provide unsurpassed standards of performance. Total harmonic distortion is an incredibly low 0.02% at 15w (8Ω) and all lower outputs. Whether you use Z.30 or Z.50 amplifiers in your Project 60 system will depend on personal preference, but they are the same size and are intended for use principally with other units in the Project 60 range. Their performance and design are such, however, that Z.50s and Z.30 may be used in a far wider range of applications.

SPECIFICATIONS (Z.50 units are interchangeable with Z.30s in all applications).— Power Outputs: **Z.30** 15 watts R.M.S. into 8 ohms using 35 volts: 20 watts R.M.S. into 3 ohms using 30 volts. **Z.50** 40 watts R.M.S. into 3 ohms using 40 volts: 30 watts R.M.S. into 8 ohms using 50 volts. **Frequency response:** 30 to 300,000Hz ± 1dB. **Distortion:** 0.02% into 8 ohms. **Signal to noise ratio:** better than 70dB unweighted. **Input sensitivity:** 250mV into 100 Kohms (for 15w into 8Ω). For speakers from 3 to 15 ohms impedance. **Size:** 14 x 80 x 57mm.

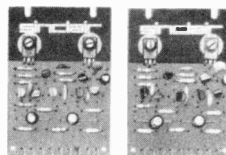


Stereo 60 Pre-amp/control unit

Built, tested and guaranteed. **£9.98**

Designed specifically for use on Project 60 systems, the Stereo 60 is equally suitable for use with any high quality power amplifier. Since silicon epitaxial planar transistors are used throughout, a really high signal-to-noise ratio and excellent tracking between channels is achieved. Input selection is by means of press buttons, with accurate equalisation on all input channels. The Stereo 60 is particularly easy to mount.

SPECIFICATIONS—Input sensitivities: Radio — up to 3mV. Mag. p.u. 3mV: correct to R.I.A.A. curve ±1dB: 20 to 25,000 Hz. Ceramic p.u. — up to 3mV: Aux — up to 3mV. **Output:** 250mV. **Signal to noise ratio:** better than 70dB. **Channel matching:** within 1dB. **Tone controls:** TREBLE +12 to -12dB at 10KHz: BASS +12 to -12dB at 100Hz. **Front panel:** brushed aluminium with black knobs and controls. **Size:** 66 x 40 x 207mm.

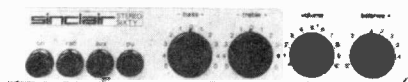

A.F.U. High & Low Pass Filter Unit

Built, tested and guaranteed. **£5.98**


For use between Stereo 60 unit and two Z.30s or Z.50s. The unit is very easily mounted and is unique in that the cut-off frequencies are continuously variable. As attenuation in the rejected band is rapid (12dB/octave), there is less loss of the wanted signal than has previously been possible. Amplitude and phase distortion are negligible. The A.F.U. is suitable for use with any other amplifier system. There are two filter sections — rumble (high pass) and scratch (low pass). H.F. cut-off (-3dB) variable from 28KHz to 5KHz. L.F. cut-off (-3dB) variable from 25Hz to 100Hz. Distortion at 1KHz (35V. supply) 0.02% at rated output. Operating voltage from 15 to 35V. Current 3mA. **Size:** 66 x 40 x 90mm.



Power Supply Units

Designed specifically for use with the Project 60 system of your choice. Use PZ.5 for normal Z.30 assemblies and PZ.6 or PZ.8 where a stabilised supply is essential.

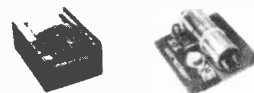PZ.5 30 volts un stabilised **£4.98**
PZ.6 35 volts stabilised **£7.98**
PZ.8 45 volts stabilised
 (less mains transformer) **£7.98**
PZ.8 mains transformer **£5.98**



Typical Project 60 applications

System	The Units to use	together with	Units cost
Simple battery record player	Z.30	Crystal P.U., 12V battery volume control, etc.	£4.48
Mains powered record player	Z.30, PZ.6	Crystal or ceramic P.U. volume control, etc.	£9.45
12W. RMS continuous sine wave stereo amp. for average needs	2 x Z.30s, Stereo 60; PZ.5	Crystal, ceramic or mag. P.U., F.M. Tuner, etc.	£23.90
25W. RMS continuous sine wave stereo amp. using low efficiency (high performance) speakers	2 x Z.30s, Stereo 60; PZ.6	High quality ceramic or magnetic P.U., F.M. Tuner, Tape Deck, etc.	£26.90
80W. (3 ohms) RMS continuous sine wave deluxe stereo amplifier. (60W. RMS into 8 ohms)	2 x Z.50s, Stereo 60; PZ.8, mains transformer	As above	£34.88
Indoor P.A.	Z.50, PZ.8, mains transformer	Mic., guitar, speakers, etc., controls	£19.43

F.M. Stereo Tuner (**£26**) & A.F.U. (**£5.98**) may be added as required.

Guarantee

If, within 3 months of purchasing any product direct from Sinclair Radionics Ltd., you are dissatisfied with it, your money will be refunded at once. Many Sinclair appointed Stockists also offer this same guarantee in co-operation with Sinclair Radionics Ltd.

Each Project 60 module is tested before leaving our factory and is guaranteed to work perfectly. Should any defect arise in normal use, we will service it at once and without any charge to you, if it is returned within two years from the date of purchase. Outside this period of guarantee a small charge (typically £1.00) will be made. No charge is made for postage by surface mail. Air Mail is charged at cost.

SINCLAIR RADIONICS, ST IVES, HUNTINGDONSHIRE PE17 4HJ

Please send

I enclose cash/cheque/money order.


Name

Address

PE12 7Z

sinclair

SUPERSOUND 13 HI-FI MONO AMPLIFIER

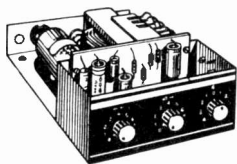


A superb solid state audio amplifier. Brand new components throughout. 5 silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13W r.m.s. into 8 ohm. Frequency response 12Hz-30KHz ±3db. Fully integrated pre-amplifier stage with

separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, etchcution panel, input and output plugs. Overall size 3in high x 6in wide x 7in deep. A.C. 200/240V.

PRICE £10.50 P. & P. 25p.

DE LUXE STEREO AMPLIFIER

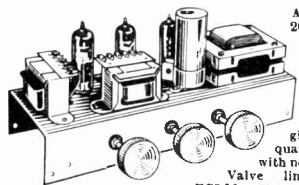

A.C. mains 200-240 volts. Using heavy duty fully insulated main transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line up—2x ECL86 Triode Pentode.

1 EZ80 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost and cut. A dual volume control is used. Balance of the left and right hand channels can be adjusted by means of a separate "balance" control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watt per channel (8 watts mono), into 3 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11in. w x 4in. x. Overall height including valves 5in. Ready built and tested to a high standard. **Price £8.92.** P. & P. 45p.

NEW! POWER SUPPLY UNIT

200/240V A.C. input. Four switched fully smoothed D.C. outputs giving 6V and 74V and 9V and 12V at 1 amp continuous (14 amp intermittent). Fitted insulated output terminals and pilot lamp indicator. Hammer finish metal case, overall size 6" x 3 1/4" x 2 1/2". Suitable for Transistor Radios, Tape Recorders, Amplifiers, etc., etc. Ready built and tested.

PRICE £4.50 P. & P. 35p.

BLACK ANODISED 18g. ALUMINIUM HEAT SINKS. For TO3, complete with mica's and bushes. Size 2 1/2in x 3in approx. 25p pair. P. & P. 5p.

HIGH GRADE COPPER LAMINATE BOARDS 8in x 6in x 1/4in. FIVE for 50p. P. & P. 13p.

LIMITED NUMBER! COILED SPRING BACK TELEPHONE CABLE. Closed approx. 10', extends to 36". 4 core or 6 core. 25p each. P. & P. 5p or more post free.

SPECIAL OFFER! MAINS TRANSFORMER. 200/240V A.C. input. 35V at 1 1/4 amp A.C. output. Overall size 2 1/2" x 2 1/2" x 3" approx. Suitable for drop through or vertical mounting. 75p. P. & P. 30p.

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations: 0-5-10-15-20-25-30-35-40-50V half wave at 1 amp or 10-0-10, 20-0-20, 30-0-30V, at 2 amps full wave. Size 3inL x 3 1/2inW x 3inD. Price £1.75. P. & P. 30p.

MAINS TRANSFORMER. For transistor power supplies. Pri. 200/240V. Sec. 9-0-9 at 500mA. 70p. P. & P. 13p. Pri. 200/240V. Sec. 12-0-12 at 1 amp. 88p. P. & P. 13p. Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.88. P. & P. 30p.

GENERAL PURPOSE HIGH STABILITY TRANSDUCER PRE-AMPLIFIER. For P.U. Tape, Mike, Guitar, etc., and suitable for use with valve or transistor equipment. 9-18V. Battery or from H.T. line 200/300V. Frequency response 15Hz-25KHz. Gain 25dB. Solid encapsulation size 1 1/2 x 1 1/2 x 1 1/2in. Brand new complete with instructions. Price 88p. P. & P. 13p.

HANDBOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES

A must for servicemen and home constructors. Including many 1000's of British, U.S.A., European and Japanese transistors. ONLY 40p. Post 5p.

Open 9-5.30 Monday to Saturday
Early closing Wed. 1 p.m.
A few minutes from South Wimbledon Tube Station

4-SPEED RECORD PLAYER BARGAINS
Mains models. All brand new in maker's packing. LATEST B.S.R. C109/C129 4-SPEED AUTOCHANGER. With latest mono compatible cartridge £8.97. Carr. 50p. With stereo cartridge £7.97. Carr. 50p. LATEST GARRARD MODELS. S.A.E. for Latest Prices!

SPECIAL BARGAIN OFFER!

PRECISION ENGINEERED PLINTHS
Beautifully constructed in heavy gauge "Colorcoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 3000, 3500, 5100, SP25 II and III, SL65E, AT60, etc., or B.S.R. C109, C129, A21, etc. Black leatherette finish. Size 12 1/2in x 14 1/2in x 3 1/2in high (approx. 7 1/2in high, including rigid smoked acrylic cover). **NOW ONLY £4.50** P. & P. 35p.

LATEST ACOS GP91/18C Mono Compatible Cartridge with t/o stylus for LP/EP/78. Universal mounting bracket. £1.50. P. & P. 8p.

SONOTONE STANC COMPATIBLE STEREO CARTRIDGE T/O stylus. Diamond Stereo LP and Sapphire 78. ONLY £2.50. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £3. P. & P. 10p.

LATEST SILICONE T/O Stereo Compatible Cartridge for EP/LP/Stereo/78. £1.83. P. & P. 10p.

LATEST RONETTE T/O Mono Compatible Cartridge for EP/LP/78 mono or stereo records on mono equipment. £1.50. P. & P. 10p.

QUALITY RECORD PLAYER AMPLIFIER MK II

A top-quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in. w x 3 1/4" x 6h. Ready built and tested. **PRICE £8.75.** P. & P. 40p. **ALSO AVAILABLE** mounted on board with output transformer and speaker ready to fit cabinet below. **PRICE £4.88.** P. & P. 50p. **DE LUXE QUALITY PORTABLE R/P CABINET MK II** Uncut motor board size 14 1/2 x 12in. Clearance 2in. below, 5 1/2in. above. Will take above amplifier and any B.S.R. or GARRARD changer or Single Player (except AT60 and SP25). Size 18 x 15 x 8in. **PRICE £4.75.** P. & P. 60p.

SPECIAL OFFER!!

HI-FI LOUSPEAKER SYSTEM

Beautifully made teak finish enclosure with most attractive Tygan-Vynair front. Size 16 1/2in high x 10 1/2in wide x 5 1/2" deep. Fitted with E.M.I. Ceramic Magnet 13in x 8in bass unit, two H.F. tweeter units and crossover. Power handling 10W. Available 3, 8 or 15 ohm impedance.

Our Price £8.40 Carr. 65p.

CABINET AVAILABLE SEPARATELY £4.50. Carr. 60p.

Also available in 8 ohm with EMI 13in x 8in. bass speaker with parasitic tweeter. £6.50. Carr. 65p.

LOUDSPEAKER BARGAINS

5in 3 ohm £1.05. P. & P. 15p. 7 x 4in 3 ohm £1.15. P. & P. 20p. 10 x 6in 3 or 15 ohm £1.90. P. & P. 30p. E.M.I. 8 x 5in 3 ohm with high flux magnet £1.82. P. & P. 20p. E.M.I. 13 1/2 x 8in with high flux ceramic magnet 3, 8, or 15 ohm £3.20. P. & P. 30p. E.M.I. 13 x 8in. 3 or 8 or 15 ohm with two built in tweeters and crossover network £4.20. P. & P. 30p. E.M.I. 15" x 8" twin cone parasitic (tweeter) 8 ohm £2.25. P. & P. 30p.

BRAND NEW. 12in 15W H/D Speakers, 3 or 15 ohm. Current production by well-known British maker. Now with HiFiux ceramic ferrobar magnet assembly £6.75. Guitar models: 25w £6.75. 35w £8.50. P. & P. 38p each.



SPECIAL OFFER!

LIMITED NUMBER OF BRAND NEW ELAC 10" TWIN CONE LOUSPEAKERS. With large ceramic magnet and plasticated cone surround. 8 ohm impedance. **£3.75.** P. & P. 25p.

12in "RA" TWIN CONE LOUSPEAKER 10 watts peak handling, 3, 8 or 15 ohm, £2.90. P. & P. 30p. **35 ohm SPEAKERS 3".** ONLY 63p. P. & P. 13p.

"POLY PLANAR" WAFFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER

Size 11 1/2in x 14 1/2in x 1 1/2in deep. Weight 19oz. Power handling 20W r.m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £5.75 each. P. & P. 25p.

VYNAIR & REXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Usually £1.75 yd., our price 75p yd. length. P. & P. 15p (min. 1 yd.). S.A.E. for samples.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable stereo earmuffs. Wired and fitted with standard stereo 1/4in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for mono. **PRICE £2.95.** P. & P. 15p.

HIGH IMPEDANCE CRYSTAL STICK MIKES. OUR **PRICE £1.05.** P. & P. 8p.

CENTRE ZERO MINIATURE MOVING COIL METER. 100µA for balance or tuning. Approx. size 1in x 1in x 1/2in. Limited number 75p. P. & P. 10p.

HARVERSON SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



NEW FURTHER IMPROVED MODEL WITH HIGHER OUTPUT AND INCORPORATING HIGH QUALITY READY DRILLED FIBRE GLASS PRINTED CIRCUIT BOARD WITH COMPONENT IDENTIFICATION CLEARLY MARKED FOR EVEN EASIER CONSTRUCTION

A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. (Very simple to modify to suit magnetic cartridge—instructions included). Output stage for any speakers from 5 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled fibre glass printed circuit board, smart brushed anodised aluminium front panel with matching knobs, wire solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specification: Power output 14W r.m.s. per channel into 5 ohms. Frequency response ±3dB 12-30,000Hz. Sensitivity better than 80mV into 1MΩ. Full power bandwidth ±3dB 12-15,000Hz. Bass boost approx. to 12dB. Treble cut approx. —16dB. Negative feedback 18dB over main amp. Power requirements 35V at 1.0 amp. Overall size—12" wide x 8" deep x 2 1/2" high.

Fullly detailed 7-page construction manual and parts list free with kit or send 18p plus large S.A.E.

PRICES AMPLIFIER KIT, £10.50 P. & P. 15p.


(Magnetic input components 30p extra)

POWER PACK KIT, £3 P. & P. 30p.

CABINET, £3 P. & P. 30p.

(Post Free if all units purchased at same time). Full after sales service. Also available ready built and tested, £20.50. Post Free.

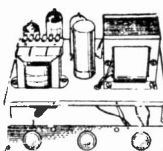Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin reted decks) and will (4x) and will (4x) and will (4x) and will (4x) facilities for medium powered Hi-Fi Discosque etc., etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II

Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis. Size 7 1/2in. w x 4in. d. x 4 1/2in. h. Incorporates ECC83, EL84, EZ80 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 4 1/2 watts. Front panel can be detached and 4 leads extend for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

HSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £3.98. P. & P. 40p.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully insulated mains transformer, rectifier and ECL86 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7in. wide x 3in. deep x 6in. high overall. A.C. mains 200/240V. Supplied absolutely Brand New, complete and 4 leads extend for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £4.75. P. & P. 35p.

OUR ROCK BOTTOM BARGAIN PRICE **£2.75** P. & P. 35p

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15Ω speaker and 2 independent volume controls, and separate bass and treble controls are provided giving good lift and cut. Valve line-up 3 EL84s, ECC83, EZ80 and 200 rectifier. Simple instruction booklet 13p. (Free with parts). All parts sold separately. ONLY £7.97. P. & P. 35p.

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

HARVERSON SURPLUS CO. LTD.

170 HIGH ST., MERTON, LONDON, S.W.19 Tel. 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

gspk

(Sales)

MICROSCOPE

An extremely modestly priced yet efficient microscope capable of magnification up to 750 times with clear, sharp images. This model is of the self-illuminating type and incorporates an easily rotatable four-position turret magnifying lens selector with rack and pinion focusing. The crackle black metal body houses the batteries for adjustable light illumination. Sample slide also provided.

Price each £4.95



G.I.III STEREO HEADPHONE

A particularly well designed stereo headphone with smooth response throughout its frequency range 23-13,000Hz. The rubber padded earpieces are adjustable for personal fitting. Model G.I.III is presented in two-tone grey with 4' matching lead and fitted plug. Impedance is 8 ohms.

Price each £2.90



AUTO BURGLAR ALARM

Designed for easy installation on any car (whether 6 or 12V) this device activates the horn when a theft is attempted of expensive equipment or personal belongings. This neat unit only 5 1/2 in x 2 3/4 in x 1 in deep on fixing backplate, reacts when the vehicle is disturbed or rocked and continues its warning for 15 seconds after tampering. The sensitivity of the device is adjustable and controlled by a separate On-Off panel which can be located wherever convenient. Supplied with connecting wires and screws, installation instructions and diagrams.

Price each 89p



Single push-pull 4-pole switches, 28p. 3 button 2 pole 6-way interlocking, interchange switches suitable for car radios D.I.Y. stereo and many other uses 49p.

NUMEROUS OTHER ITEMS AVAILABLE INCLUDE:

Switches. Comprehensive range of N.S.F. Toggle switches and Rotary Wafer switch kits (to enable you to make your own switch to your own specification).
Copper laminate and all materials available to make your own printed circuit boards.
Lamps and lampholders for every requirement. **Ready Built Circuits and Modules.**
Freezer and Cleaner aerosol sprays.
Jack plugs and sockets.
Variety of speciality products.
Resistors, Capacitors

All orders value £2 or over post free. Other orders please add 10p P. & P. We only sell new products—do not confuse with "seconds" or surplus stock. Because of our keen prices we regret the prices apply to U.K. and B.F.P.O. addresses only.

To GSPK (Sales) Limited
 Dept. P.E., Head Office, Hookstone Park, Harrogate, Yorkshire HG2 7BU

ALL
 CALLERS
 WELCOME

MON. TO FRI.
 9-5.00

Please fill in the coupon and send with 10p (refundable on ordering) for catalogue

Name

Address

..... P.E.

COMPARE OUR PRICES

Speaker Bargains	£p
E.M.I. 13in x 8in 3, 8 & 15 ohms	2.00
plain	2.25
with tweeter	3.50
twain tweeter	3.50
Type 350 -20 watt with tweeter 8 ohms. P.T. 37p.	7.50
8in x 5in 3, 8 & 15 ohms	1.30
7in x 4in 3 & 8 ohms	1.05
FANE 8in 8 ohm, dual cone	2.30
CELESTION 8in 15 ohm	1.50
GOODMAN 8 10in x 6in 3 ohm	1.60
BAKER GROUP 25 12in 25W 8 or 15 ohm	5.75
Postage 25p per speaker	
2 1/2in 8 or 64 ohm P.P. 10p	50
Kil-form cabinets, teak (17in x 10in x 6in)	2.75
with a 13in x 8in or 8in cut out (12in x 12in x 6in) with a 8in x 5in or 8in cut out.	2.25
(please specify cut out)	
Add 35p per Cabinet for post & packing	

Microphone Bargains	£p
MIC45 "ACOS" metal case, crystal hand	95
CM 20 Crystal Hand	45
DX166 Dynamic Stick	90
DX143 Dynamic, cassette-type stick	1.00
MIC60 "ACOS" stick crystal	1.00
CM70 PLANET stick metal, switch crystal	1.45
DM160 Dynamic uni-dir, ball metal	3.75
UD130 50K/600 ohm uni-dir, ball metal	4.50
TW209 Lesson dual imp ball metal uni-dir	5.75
Guitar mike	45
Lapel type, crystal	40
Postage 17p each	

Panel Meters	£p
2in sq.	
0-500mA, 0-1mA, 0-10mA, 0-100mA	
0-500mA, "S" METER	
£1.50 Postage 17p each	

Cartridges—with standard fittings & stylus	£p
ACOS GP91/28C or GP91/38C stereo compatible	1.05
ACOS GP94 stereo ceramic	1.90
ACOS GP95 stereo crystal	1.35
9THAC Sonotone stereo ceramic (diamond)	2.65
ACOS GP97/28C mono crystal	75
ACOS GP101 compatible crystal	75
19-TI Sonotone stereo crystal	90p
Postage 5p per cartridge	

Multitesters	£p
1,000 ohms/volts	£2-50
2,000 ohms/volts	£2-75
10,000 ohms/volts	£5-00
50,000 ohms/volts	£10-00
100,000 ohms/volts with transistor tester	£15-00
Postage 17p each	

Tapes—"MYLAR" base finest quality British made.	£p
5in 600ft	38p
5in 900ft	45p
5in 1200ft	60p
5 1/2in 900ft	49p
5 1/2in 1200ft	55p
5 1/2in 1800ft	85p
7in 1200ft	55p
7in 1800ft	80p
7in 2400ft	95p
Postage 9p each	

THIS MONTH'S SPECIAL OFFER

Solid state stereo amplifier 11-200, 10 watt/channel r.m.s. 8 ohm output imp. Delux Walnut Cabinet, brushed aluminium front. Switches for tape, tuner, crystal/mag. cartridge. Stereo reverse left and right channel. Source and monitor, independent bass and treble control for each channel. Headphone socket. ONLY £21 Whilst stocks last. P. & P. £1.

RIVERSDALE ELECTRONICS

ALL OUR MERCHANDISE IS FULLY GUARANTEED

Mail Order Dept. E12/72,
 P.O. Box 470,
 Manchester M60 4BU
 SEND 25p FOR
 COMPLETE CATALOGUE

1000's OF TEST EQUIPMENT BARGAINS!



A PROFESSIONAL DIGITAL MULTIMETER
BRAND NEW AT A FRACTION OF THE ORIGINAL PRICE!
 3 digit plus polarity indicator. Its 17 positions allow it to measure in the following ranges: d.c. volts 100V to 999V; a.c. volts 100V to 420V; d.c. 100µA; a.c. 100µA. Resistance 0-1Ω to 999KΩ. Operates from 230V 50Hz. 12V d.c. external. PLUS Dry cells or Ni Cad batteries. 50p P. & P.
OUR PRICE £55
 Original Price £89.

BRAND NEW DIGITAL PANEL VOLTMETERS
 10mV to 1.99V, 199 measuring points. Input Z=100MΩ Automatic zeroing. Dimensions 72mm H x 72mm W x 155mm D.
OUR PRICE £24.50 PLUS 50p P. & P.
 Original Price £52.

P. F. RALFE

10 CHAPEL STREET, LONDON, N.W.1
 Tel. 01-723 8753

-the lowest prices!

74 Series T.T.L. I.C's

BI-PAK STILL LOWEST IN PRICE. FULL SPECIFICATION GUARANTEED. ALL FAMOUS MANUFACTURERS



	1	25	100+		1	25	100+
SN7400	0.15	0.14	0.12	SN7489	£5.50	£5.25	£5.00
SN7401	0.15	0.14	0.12	SN7490	0.67	0.64	0.58
SN7402	0.15	0.14	0.12	SN7491	£1.00	0.95	0.90
SN7403	0.15	0.14	0.12	SN7492	0.67	0.64	0.58
SN7404	0.15	0.14	0.12	SN7493	0.67	0.64	0.58
SN7405	0.15	0.14	0.12	SN7494	0.77	0.74	0.60
SN7406	0.35	0.31	0.28	SN7495	0.77	0.74	0.60
SN7407	0.35	0.31	0.28	SN7496	0.87	0.84	0.78
SN7408	0.18	0.17	0.16	SN74100	£1.65	£1.60	£1.55
SN7409	0.18	0.17	0.16	SN74104	0.97	0.94	0.88
SN7410	0.15	0.14	0.12	SN74105	0.97	0.94	0.88
SN7411	0.25	0.24	0.23	SN74107	0.60	0.58	0.56
SN7412	0.35	0.31	0.28	SN74110	0.65	0.63	0.58
SN7413	0.29	0.26	0.24	SN74111	£1.25	£1.15	£1.10
SN7416	0.43	0.40	0.38	SN74118	£1.00	0.95	0.90
SN7417	0.43	0.40	0.38	SN74119	£1.35	£1.25	£1.10
SN7420	0.18	0.14	0.12	SN74121	0.60	0.57	0.54
SN7422	0.50	0.48	0.45	SN74122	£1.40	£1.30	£1.10
SN7423	0.50	0.48	0.45	SN74123	£2.00	£2.70	£2.60
SN7425	0.50	0.48	0.45	SN74141	0.67	0.64	0.53
SN7427	0.67	0.64	0.60	SN74145	£1.00	£1.00	£1.30
SN7428	0.70	0.65	0.60	SN74150	£3.00	£2.70	£2.50
SN7430	0.15	0.14	0.12	SN74151	£1.00	0.95	0.90
SN7432	0.45	0.42	0.40	SN74153	£1.20	£1.10	0.95
SN7433	0.80	0.75	0.70	SN74154	£1.00	£1.70	£1.60
SN7437	0.67	0.64	0.60	SN74155	£1.30	£1.30	£1.20
SN7438	0.84	0.82	0.80	SN74156	£1.40	£1.30	£1.20
SN7440	0.15	0.14	0.12	SN74157	£1.90	£1.80	£1.70
SN7441	0.47	0.44	0.50	SN74160	£1.00	£1.70	£1.60
SN7442	0.67	0.64	0.60	SN74161	£1.00	£1.70	£1.60
SN7443	£1.30	£1.25	£1.20	SN74162	£4.00	£3.75	£3.50
SN7444	£1.30	£1.25	£1.20	SN74163	£4.00	£3.75	£3.50
SN7445	£1.00	£1.77	£1.75	SN74164	£2.20	£2.15	£2.10
SN7446	£0.97	0.94	0.88	SN74165	£2.20	£2.20	£2.15
SN7447	£1.00	0.97	0.95	SN74166	£3.50	£3.25	£3.00
SN7448	£1.00	0.97	0.95	SN74174	£2.30	£2.20	£2.10
SN7450	0.15	0.14	0.12	SN74175	£1.60	£1.50	£1.40
SN7451	0.15	0.14	0.12	SN74176	£2.50	£2.40	£2.30
SN7453	0.15	0.14	0.12	SN74177	£2.50	£2.40	£2.30
SN7454	0.15	0.14	0.12	SN74180	£2.00	£1.60	£1.40
SN7460	0.15	0.14	0.12	SN74181	£5.50	£5.00	£4.75
SN7470	0.29	0.26	0.24	SN74182	£2.00	£1.80	£1.60
SN7472	0.29	0.26	0.24	SN74184	£3.00	£3.25	£3.00
SN7473	0.37	0.35	0.32	SN74190	£1.95	£1.90	£1.85
SN7474	0.37	0.35	0.32	SN74191	£1.90	£1.85	£1.80
SN7475	0.45	0.43	0.42	SN74192	£1.95	£1.90	£1.85
SN7476	0.40	0.39	0.38	SN74193	£2.00	£1.90	£1.75
SN7480	0.67	0.64	0.58	SN74194	£2.60	£2.60	£2.50
SN7481	£1.20	£1.15	£1.10	SN74195	£2.00	£1.90	£1.80
SN7482	0.87	0.86	0.85	SN74196	£1.00	£1.70	£1.60
SN7483	£1.10	£1.05	0.95	SN74197	£1.00	£1.70	£1.60
SN7484	0.67	0.65	0.60	SN74198	£5.00	£5.00	£4.50
SN7485	£3.60	£3.50	£3.40	SN74199	£5.50	£5.00	£4.50
SN7486	0.32	0.31	0.30				

ROCK BOTTOM PRICES LOGIC DTL 930 Series I.C's

Type No.	1-24	25-99	100 up
BP900	12p	11p	10p
BP932	13p	12p	11p
BP933	13p	12p	11p
BP936	12p	11p	10p
BP944	13p	12p	11p
BP945	25p	24p	22p
BP946	12p	11p	10p
BP948	24p	24p	22p
BP951	65p	60p	55p
BP962	12p	11p	10p
BP9093	40p	38p	35p
BP9094	40p	38p	35p
BP9097	40p	38p	35p
BP9099	40p	38p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only)


LINEAR I.C. - FULL SPEC

Type No.	1-24	25-99	100 up
BP201C - S1 201C	68p	58p	45p
BP701C - S1 701C	68p	50p	45p
BP702C - S1 702C	68p	50p	45p
BP702C - 72702	53p	45p	40p
BP709C - 72709	36p	36p	30p
BP709P - μ A709K	36p	34p	30p
BP710 - 72710	44p	42p	40p
BP711 - μ A711	45p	43p	40p
BP741 - 72741	75p	65p	50p
μ A70K - μ A70K	28p	26p	24p
TAA263 -	70p	60p	55p
TAA293 -	90p	75p	70p
TAA350 -	170p	158p	150p

BI-PAK DO IT AGAIN!

50W pk 25w (RMS)

0.1% DISTORTION!
HI-FI AUDIO AMPLIFIER

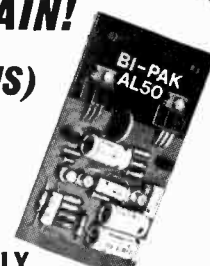


THE AL50

- ★ Frequency Response 15Hz to 100,000—1dB. **ONLY £3.25p each**
- ★ Load—3, 4, 8 or 16 ohms. **★ Supply voltage 10-35 Volts.**
- ★ Distortion—better than .1% at 1KHz. **★ Overall size 63mm x 105mm x 13mm.**
- ★ Signal to noise ratio 80dB.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE SPM80

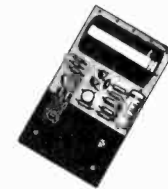

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm x 105mm x 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:- Disco Systems, Public Address, Intercom Units, etc. Handbook available, 10p **PRICE £2.95**

TRANSFORMER BMT80 £1.95 p. & p. 25p.

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.

SPECIFICATION

- Frequency Response 20Hz - 20KHz \pm 1dB
- Harmonic Distortion better than 0.1%
- Inputs : 1. Tape Head 1-25 mV into 60K Ω
- 2. Radio, Tuner 35 mV into 50K Ω
- 3. Magnetic P.U. 1-5 mV into 50K Ω
- All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within \pm 1dB. from 20Hz x 20KHz.
- Bass Control \pm 15dB at 20Hz
- Treble Control \pm 15dB at 20KHz
- Filters : Rumble (High Pass) 100Hz
- Scratch (Low Pass) 8KHz
- Signal/Noise Ratio better than - 65dB
- Input overload + 25dB
- Supply + 35 volts at 20mA
- Dimensions 292mm x 82mm x 35mm

ONLY £11.95
SPECIAL COMPLETE KIT COMPRISING 2 AL50's, 1 SPM80, 1 BMT80 & 1 PA100 ONLY £23.00 FREE p. & p.

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 7p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

NUMERICAL INDICATOR TUBES



MODEL	CD66	GE116	3015F Minitron
Anode voltage (Vdc)	170min	175min	5
Cathode Current (mA)	2-3	14	8
Numerical Height (mm)	16	13	9
Tube Height (mm)	47	32	22
Tube Diameter (mm)	19	13	12 wide
I.C. Driver Rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 x Decimal point. All side viewing. Full data for all types available on request.

RTL MICROLOGIC CIRCUITS

	Price each		
Epoxy TO-5 case	1-24	25-99	100 up
uL900 Buffer	35p	33p	27p
uL914 Dual 21/p gate	35p	33p	27p
uL923 J-K flip-flop	50p	47p	45p

Date and Circuits Booklet for IC's Price 7p.

DUAL IN LINE SOCKETS.

14 & 16 Lead Sockets for use with

DUAL-IN-LINE I.C.'s. TWO Ranges PROFESSIONAL & NEW LOW COST. PROF. TYPE No. 1-24 25-99 100up. TSO 14 pin type 30p 27p 25p TSO 16 " " 35p 32p 30p

LOW COST No.

BP8 14	15p	13p	11p
BP8 16	16p	14p	12p

YATES ELECTRONICS

(FLITWICK) LTD.

ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK
BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue which contains data sheets for most of the
components listed will be sent free on request.
10p stamp appreciated.

OPEN ALL DAY SATURDAYS

RESISTORS

1W Iskra high stability carbon film—very low noise—capless construction.
1W Mullard CR25 carbon film—very small body size 7.5 x 2.5mm.
2% ELECTROSIL TRS

Power watts	Tolerance	Range	Values available	Price
↓	5%	4.7Ω-2.2MΩ	E24	1p 0.8p
↓	10%	3.3MΩ-10MΩ	E12	1p 0.8p
↓	2%	10Ω-1MΩ	E24	3.5p 3p
↓	10%	1Ω-3.9Ω	E12	1p 0.8p
↓	5%	4.7Ω-1MΩ	E12	1p 0.8p
↓	10%	1Ω-10Ω	E12	6p 5.5p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Iskra resistors 5 off each value 4.7Ω to 1MΩ.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5kΩ to 2MΩ, log or linear (log ±W, lin ±W).
Single, 12p. Dual gang (stereo), 40p. Single D.P. switch 24p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500Ω and decades to 5MΩ. Horizontal or vertical P.C.
mounting (0.1 matrix).
Sub-miniature 0.1W, 5p each. Miniature 0.25W, 6p each.

TRANSISTORS

AC107 15p	BC108 10p	8FY51 22p	OCF71 40p	2N3703 12p
AC126 12p	BC109 10p	BFY52 22p	ORP12 50p	2N3704 13p
AC127 12p	BC147 10p	BSY 56 32p	2N2369 16p	2N3705 12p
AC128 12p	BC148 13p	OC26 45p	2N2646 60p	2N3706 11p
AC131 12p	BC149 13p	OC28 45p	2N2926R 9p	2N3707 12p
AC132 12p	BC157 13p	OC35 45p	2N2926Q 9p	2N3708 10p
AD140 50p	BC158 13p	OC42 12p	2N2926V 9p	2N3709 11p
AD161 33p	BC159 13p	OC44 12p	2N2926G 9p	2N3710 11p
AD162 36p	BD131 75p	OC45 12p	10p	2N3711 11p
AF114 20p	BD132 75p	OC70 12p	2N3054 58p	2N4062 12p
AF115 20p	BF179 32p	OC71 12p	2N3055 60p	ZTX500 16p
AF116 20p	BF181 25p	OC72 12p	2N3442	ZTX503 16p
AF117 20p	BF194 15p	OC72 12p	2N3442	140p
AF118 38p	BF195 15p	OC81 12p	2N3702 13p	40362 58p
BC107 10p	BFY50 22p	OC82 12p		

ZENER DIODES

400mW 5% 3.3V to 30V, 15p.

LINEAR I.C.'s (D.I.L.)

709 50p 741, 30p
710 50p 748, 50p

DIL Socket 14
and 16 pin. 16p

DIODES

RECTIFIER

BY127	1250V	1A	12p
BZV10	800V	6A	25p
BZY13	200V	6A	20p
IN4001	50V	1A	7p
IN4004	400V	1A	8p
IN4007	1000V	1A	12p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

BRUSHED ALUMINIUM PANELS

12in x 6in = 25p; 12in x 2½in = 10p; 9in x 2in = 7p.

SLIDER POTENTIOMETERS

86mm x 9mm x 16mm, length of track 59mm
SINGLE 10kΩ, 25kΩ, 50kΩ, 100kΩ, log or lin
DUAL GANG 10kΩ + 10kΩ, etc, log or lin
Knob for above
FRONT PANEL
20 gauge panel 12in x 4in with slots cut for use with slider pots.
Grey or matt black finish, complete with fixings for 4 pots.

MULLARD POLYESTER CAPACITORS C296 SERIES

400V: 0.001μF, 0.0015μF, 0.0022μF, 0.0033μF, 0.0047μF, 2½p, 0.0068μF, 0.01μF,
0.015μF, 0.022μF, 0.033μF, 3p, 0.047μF, 0.068μF, 0.1μF, 4p, 0.15μF, 6p, 0.22μF, 7½p,
0.33μF, 11p, 0.47μF, 13p.
160V: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 0.068μF, 3p, 0.1μF 3½p, 0.15μF 4½p,
0.22μF, 5p, 0.33μF, 6p, 0.47μF, 7½p, 0.68μF, 11p, 1.0μF, 13p.

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 3p, 0.033μF, 0.047μF, 0.068μF,
3½p, 0.1μF, 4p, 0.15μF, 0.22μF, 5p, 0.33μF, 6½p, 0.47μF, 8½p, 0.68μF, 11p, 1.0μF, 13p,
1.5μF, 20p, 2.2μF, 24p.

MYLAR FILM CAPACITORS 100V

0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF,
2½p, 0.04μF, 0.05μF, 0.068μF, 0.1μF, 3½p.

CERAMIC DISC CAPACITORS

100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS—MULLARD C426 SERIES

(μF/V) 10/2.5, 40/2.5, 80/2.5, 160/2.5, 320/2.5, 500/2.5, 8/4, 32/4, 64/4, 125/4, 250/4,
400/4, 6.4/6.4, 25/6.4, 50/6.4, 100/6.4, 200/6.4, 320/6.4, 4/10, 16/10, 32/10, 64/10, 125/10,
200/10, 2.5/16, 10/16, 20/16, 40/16, 80/16, 125/16, 1.6/25, 6.4/25, 12.5/25, 25/25, 50/25,
80/25, 1/40, 4/40, 8/40, 16/40, 32/40, 50/40, 0.64/64, 2.5/64, 5/64, 10/64, 20/64, 32/64.

MULLARD C437 SERIES

100/40, 160/25, 250/16, 400/10, 640/6.4, 800/4, 1000/2.5, 9p, 100/64, 160/40, 250/25,
400/16, 640/10, 1250/4, 1000/6.4, 1600/2.5, 12p, 160/64, 250/40, 400/2.5, 640/16,
2000/4, 1000/10, 1600/6.4, 2500/2.5, 15p, 250/64, 400/40, 640/25, 3200/4, 1000/16,
1600/10, 2500/6.4, 4000/2.5, 18p.

ELECTROLYTIC CAPACITORS Miniature P.C. mounting

(μF/V): 10/12, 50/12, 100/12, 200/12, 5/25, 10/25, 25/25, 100/25.

5p each.

VEROBOARD

2½ x 3½	22p	16p
2½ x 5	24p	24p
3½ x 3½	24p	24p
3½ x 5	27p	27p
17 x 2½	75p	57½p
17 x 3½	100p	78p
17 x 5 (plain)	—	82p
17 x 3½ (plain)	—	60p
17 x 2½ (plain)	—	42p
2½ x 5 (plain)	—	11p
2½ x 3½ (plain)	—	11p
Pin insertion tool	52p	52p
Spot face cutter	42p	42p
Pkt. 50 pins	20p	20p

JACK PLUGS AND SOCKETS

Standard screened	18p	2.5mm insulated	8p
Standard insulated	12p	3.5mm insulated	8p
Stereo screened	35p	3.5mm screened	13p
Standard socket	15p	2.5mm socket	8p
Stereo socket	18p	3.5mm socket	8p

D.I.N. PLUGS AND SOCKETS

2 pin, 3 pin, 5 pin 180°, 5 pin 240°, 6 pin
Plug 12p. Socket 8p.
4 way screened cable, 15p/metre.
6 way screened cable 22p/metre.

BATTERY ELIMINATOR £1.50

9V mains power supply. Same size as PP9 battery.

THERMISTORS

VA1055S 15p; VA1066S 15p; VA1077 15p; R53 £1.35.

COMPACT CASSETTES—IN PLASTIC LIBRARY BOX

C90 65p

C120 85p.

LARGE (CAN) ELECTROLYTICS

1600μF 64V	74p	3200μF 16V	50p
2500μF 40V	74p	4500μF 16V	50p
2500μF 50V	58p	4500μF 25V	£1.68
2500μF 64V	80p	5000μF 50V	£1.10
2800μF 100V	£3.00		

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF 10p	0.047μF 13p	0.22μF 20p
0.022μF 12p	0.1μF 13p	0.47μF 22p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values 4p each.

GUNTON ELECTRONIC IGNITION KIT

£7.95 + 35p P. & P.

READY BUILT UNIT £9.95 + 35p P. & P.

GUARANTEED 5 YEARS

Patents Pending. 12 volt only—state pos. or neg. earth.
Capacitive discharge ignition is recognised as being the most efficient
system and will give you:

- ★ Continual Peak-Tuned Performance
- ★ Up to 20% reduced fuel consumption
- ★ Easier All-Weather Starting
- ★ Increased Acceleration and Top Speed
- ★ Longer Spark Plug Life
- ★ Increased Battery Life
- ★ Elimination of Contact Breaker Burn
- ★ Purer Exhaust Gas Emission

Kit includes absolutely everything for assembly: Case, Cables, Coil
Connectors, Silicon Grease, etc. 8 page illustrated instructions cover
fitting of all types of tachometers. Call in for a workshop demonstration.
S.A.E. all enquiries please, or Phone 33652. (Many letters from satisfied
customers.)

SCORPIO: Transformer £1.85 + 25p P. & P. P.C.B. 65p + 10p P. & P.
Special interference filter 65p + 10p P. & P.

Dept. PE, ELECTRONICS DESIGN ASSOCIATES
82 BATH STREET, WALSALL WS1 3DE



Audio

The new-style magazine
for your greater enjoyment
of leisure listening

- Top name contributors . . .
- Outstanding features and illustrations . . .
- Comprehensive record reviews . . .
- Special DIY audio features . . .

Gordon J. King writes on the TEAC AG7000 tuner/amplifier . . .
Frederick Judd reviews the Marantz 1030 amplifier . . .
Stan Kelly reviews the Mordaunt Short MS235 loudspeaker . . .
P. Craddock Randall reports on Philips GP421 cartridge . . .
Jeff Chandler writes on accessories for record care and
record player maintenance . . .

PLUS Audionews . . . Tapetalk . . . Audio Encyclopedia . . .
December issue OUT NOVEMBER 17 20p

NOW YOU CAN CATCH SHOALS OF BIG FISH with new electronic miracle

First time marketed in England, this exciting electronic instrument the "Decoytron" is the one responsible for starting the electronic fish-rye in the U.S.A. just recently. Uses ingenious double-action method of attracting all kinds of fish from hundreds and hundreds of feet away... saltwater or freshwater. Why this device is so fantastically successful is because it *actually imitates the sound of wet insects milling about the surface*. These sound waves spread out hundreds of feet in all directions. Although this peculiar sonic frequency won't sound like much to you—but all the fish in the area it's their dinner bell! But that's not all... *electroluminescence neon tubes cunningly flicker intermittently*, penetrating the air for hundreds of feet around, at a frequency fish are unable to resist. The fish mistake this flickering glimmer for the soft phosphorescence glow given off by Plankton... a favourite delicacy of most fish! All you do is switch on, lower into the water (it's completely water resistant) allow around 5 minutes—then start reeling 'em in. We'll bet you won't be able to reel 'em in fast enough. Self-contained batteries last ages—cost pence. Kit of all parts including special easy as a,b,c. directions only **£2-50 + 25p P. & P.** (Parts available separately.)

special introductory offer **£2-50**

BUILD 5 RADIO AND ELECTRONIC PROJECTS

ONLY **£2-45**



Amazing Radio Construction set! Begeorge a radio expert for 22+ years. A complete Home Radio Course. No experience needed. Parts including simple instructions for each design. Illustrated step-by-step plans, all transistors, loudspeaker, personal phone, knobs, screws, etc., all you need. Presentation box 45p extra as illus. (if required) (parts available separately) no soldering necessary. Send **£2-45 + 20p p & p.**

SOOTHE YOUR NERVES RELAX WITH THIS AMAZING RELAXATRON


CUTS OUT NOISE POLLUTION—SOOTHES YOUR NERVES! Don't underestimate the use of this fantastic new design—the RELAXATRON is basically a pink noise generator. Besides being able to mask out extraneous unwanted sounds, it has other very interesting properties. For instance, many people find a rainstorm mysteriously relaxing, a large part of this feeling of well-being can be directly traced to the sound of falling raindrops—a well known type of pink noise. IF YOU WORK IN NOISY OR DISTRACTING SURROUNDINGS, IF YOU HAVE TROUBLE CONCENTRATING, IF YOU FEEL TENSED, UNABLE TO RELAX—then build this fantastic Relaxatron. Once used you will never want to be without it—TAKE IT ANYWHERE! Uses standard PP3 batteries (current used so small that battery life is almost shelf-life). CAN BE EASILY BUILT BY ANYONE OVER 12 YEARS OF AGE using our unique, step-by-step, fully illustrated plans. No soldering necessary. All parts including case, a pair of crystal phones, Components, nuts, screws, wire, etc., no soldering. **£2-75 + 25p P. & P.** (Parts available separately.)



ONLY **£2-75**

ELECTRONIC ORGAN

ONLY **£3-25**

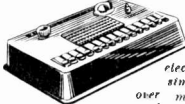

Don't confuse this ordinary electric organ that simply blows air over mouth-organ type reeds, etc. Fully transistorised. **SELF-CONTAINED LOUD-SPEAKER.** Fifteen separate keys span two full octaves—play the "Yellow Rose of Texas", play "Silent Night", play "Auld Lang Syne", etc. etc. You have the thrill and excitement of building it together with the pleasure of playing a real, live, portable electronic organ. **NO PREVIOUS KNOWLEDGE OF ELECTRONICS NEEDED.** No soldering necessary—single as a "B" to make it. *Anyone over nine years can build it easily in one short evening following the fully illustrated, step-by-step, simple instructions.* ONLY **£3-25 + 25p p & p** for kit, including case, nuts, screws, simple instructions, etc. Uses standard battery (parts available separately). Have all the pleasure of making it yourself, finish with an exciting gift for someone.

INGENIOUS ELECTRONIC SLEEP INDUCER

ONLY **£3-25**

Can't sleep at nights? Do you wake up in the night and can't get off to sleep again? Would you like to be gently lulled to a satisfying sleep every night? Then build this ingenious electronic sleep inducer. It even stops by itself so you don't have to worry about it being on all night! The loudspeaker produces soothing audio-frequency sounds, continuously repeated but as time goes on the sound gradually become less and less—until they eventually cease altogether, the effect it has on people is amazingly very similar to hypnosis. A control is provided for adjusting the length of times, etc., all transistor, can be built by anyone over 12 years of age in about 10 hours. No knowledge of electronics or radio needed. Extremely simple, easy-to-follow, step-by-step, fully illustrated instructions included. No soldering necessary. Works off standard batteries, extremely economical. Size only 3in x 4 1/2in x 1 1/2in—take it anywhere. Kit includes case, nuts, wire, screws, etc. **SEND £3-25 + 25p P. & P.** (Parts available separately.)



The amazing "Phototron" SOUND OPERATED FLASH

Take flash pictures at the exact instant of the bursting of a balloon. A champagne cork leaving the bottle. The split second a hammer strikes a light bulb. *The mind boggles at the possibilities of the "Phototron". . . the only limit is your imagination.* Now that inexpensive flash guns are on the market in quantity, it has made possible, with the production of a wide variety of exciting photography effects, one strictly limited to the professionals. The duration of an electronically produced flash is extremely brief and normally measured in Millionths. Now, providing the camera shutter is left open in a dark or subdued light, it is the timing of the flash that determines what is imprinted on the film—not necessarily anything done by the camera. As electronic flash guns are fired by making a switched connection then it becomes obvious that one of the latest Silicon Controlled Relay's can be used. If we make this S.C.R. operate by sound (with suitable sensitivity control for soft-toned sounds) some real "sway-on" photography effects can be captured forever on film. Easily built in a couple of hours so, the "Phototron" is fully solid state, uses self contained PP3 battery. No soldering necessary using our special terminal board (Pat. applied for). All parts including special pictorial step-by-step plans, transistors, microphone, S.C.R., potentiometers, switches, test lamp, case, nuts, screws, etc., etc., ONLY **£4-50 + 25p P. & P.** Made up must be worth at least £10. (Parts available separately.)

Eavesdrop on the exciting world of Aircraft Communications— V.H.F. AIRCRAFT BAND


ONLY **£2-85**

Listen in to AIRLINES, PRIVATE PLANES, JET-PLANES. Eavesdrop on exciting cross talk between pilots, ground approach control, airport tower. Hear for yourself the dispirited voices hiding tenseness on talk densers. Be with them when they have to take nerve ripping decisions in emergencies—Tune into the international distress frequency. Covers the aircraft frequency band including HEATHROW, GATWICK, LUTON, KINGFAY, FRETHERSWICK, ETC. ETC. CLEAR AS A BELL. This fantastic fully transistorised instrument can be built by anyone over nine in under two hours. No soldering necessary. Fully illustrated simple instructions take you step-by-step. Uses standard PP3 battery. All you do is extend lead aerial, plug close to any ordinary medium wave radio (even tiny portables) **NO CONNECTIONS WHAT-EVER NEEDED.** **SEND ONLY £2-85 + 20p p & p** for kit including case, nuts, screws, wire, etc. etc. (Parts available separately.)

TREASURE LOCATOR MODULE

ONLY **£4-50**

FULLY TRANSDISTORISED METAL DETECTOR MODULE. Uses PP3 battery and 'phones. Put it in a case, screw a handle on and YOU HAVE A PORTABLE TREASURE LOCATOR EASILY WORTH ABOUT £20! Extremely sensitive—penetrates through earth, sand, rock, water, etc.—EASILY LOCATES COINS, GOLD, SILVER, JEWELLERY, HISTORICAL RELICS, BURIED PIPES, ETC. No sensitive it will detect certain objects buried SEVERAL FEET BELOW GROUND! GIVES CLEAR SIGNAL ON ON COIN. **£4-50 + 30p carr.** for Kit. (High quality) Danish Stethoscope headphones **£2-75** extra (if required.)

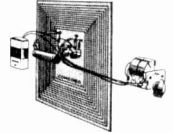

FIND BURIED TREASURE! Transistorised Treasure Locator

This fully portable transistorised metal locator detects and tracks down buried metal objects—signals and locates location with loud audible sound (no phones used)—uses any transistor radio which fits inside—no connections needed. **FINDS GOLD, SILVER, COINS, JEWELLERY, HISTORICAL LOGICAL PIECES, ETC. ETC.** Extremely sensitive, will signal presence of certain objects buried several feet below ground! No knowledge of radio or electronics required. Can be built with ease in our short evening by anybody from nine years of age upwards, with the clear, easy-to-follow, step-by-step, fully illustrated instructions uses standard PP3 battery. No soldering necessary. Kit includes nuts, screws, wire, etc. ONLY **£2-85 + 25p p & p.** (Sectional handle as illustrated 95p extra.) Parts available separately. Made up looks worth £15.

ONLY **£2-85**

Anyone on 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on tod aerial in 30 mins—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3in x 4 1/2in x 1 1/2in. ONLY **£2-75 + 20p p & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

SHORTWAVE TRANSISTOR RADIO

ONLY **£2-75**

Anyone on 9 years up can follow the step-by-step, easy as ABC, fully illustrated instructions. No soldering necessary. 76 stations logged on tod aerial in 30 mins—Russia, Africa, USA, Switzerland, etc. Experience thrills of world wide news, sport, music, etc. Eavesdrop on unusual broadcasts. Uses PP3 battery. Size only 3in x 4 1/2in x 1 1/2in. ONLY **£2-75 + 20p p & p.** Kit includes cabinet, screws, instructions, etc. (Parts available separately.)

UNIQUE RADIO FOR BEDROOM OR OFFICE

No batteries, no electricity. ONLY **£1-70** never wears out

Tune in your favourite programmes of the news, or sports in the Office or in your bedroom. Uses sensitive, germanium diode originally evolved from Wartime radar. Never buy a battery. Never use electricity. Never replace. Covers all medium wave frequencies with beautiful tone. Size 4 1/2in x 2 1/2in x 1 1/2in in beautiful case. ONLY **£1-70** almost blindfold in under 15 minutes! Ideal for absolute beginner from 8 years of age upwards. **SPECIAL PRICE TO CLEAR STOCKS OF COMPONENTS, ONLY £1-70 + 20p p & p** for all parts including beautiful case. Germanium semi-conductor, tuning condenser, personal phone, wire, nuts, screws, SIMPLE AS ABC INSTRUCTIONS (Parts available separately.)



AMAZING MAGIC MUSIC BOX

make electronic music waving your hands about

ONLY **£2-75**

Everyone's heard the weird, wonderful, but beautiful music used in Science Fiction Films, Horror Films, etc. also on Radio & Television. This unearthly, eerie music is almost always produced by a little known electronic device measuring only a few inches... called a Theremin. All you have to do is switch on your radio (almost any type will do) and place the Theremin close by, switch on the Theremin and proceed to wave your hands mysteriously in the air like a magician. The most fantastic musical sounds are then produced, and with a little practice people can learn to play all the well known tunes. Apart from its musical value, its small size allows it to be used to best advantage at parties, gatherings of friends, etc., where it attracts tremendous interest. Provides hours and hours of pleasure to young and old. Uses standard PP3 battery which lasts ages. The 3 Transistor circuit, though fairly advanced is simple to build with our pictorial step-by-step plans. No soldering necessary. Easily built in an hour or so using our special terminal board (Pat. applied for). All parts including nuts, bolts, case, etc., ONLY **£2-75 + 25p P. & P.** (Parts available separately.)



INGENIOUS ELECTRONIC SINGING & WARBLING CANARY!

ONLY **£4-50**

Actually whistles and warbles like a real bird! Amazing circuitry faithfully reproduces the Canary's beautiful song. Just switch on and you'll hear the bird sing for some seconds, suddenly breaking into a whistle—whistling down scale for some seconds, suddenly breaking into a whistle—whistling down scale for some seconds, then several seconds later shutting off for a second or two—only to start automatically again in a few seconds. People listen to the delightful song all day and never get bored! Relax, as the sweetest nerve-soothing birdsong takes you to leafy woods and glades. Provides countless hours of joy to young and old alike. Standard self-contained battery lasts ages. Easily built in an hour or so with special pictorial step-by-step plans. No soldering necessary. All parts including terminal board (Pat. applied for), transistors, loudspeaker, transistors, nuts, screws, wire, etc., plus case (which fits under cage—cage and toy bird not supplied). ONLY **£4-50 + 25p P. & P.** (Parts available separately.)



"READ PEOPLE'S MINDS"—TEST THEIR NERVES—BEAT THEM AT CARDS, ETC. WITH THIS ASTONISHING ELECTRONIC BRAIN BOX Only £2-87

With this "Brain-box" you will be able to perform mind-boggling feats. **THE MIND READING DEVICE** will make people swear you have "telepathic" powers. **THE AMAZING CARD TRICK** can't completely mystifies and baffles from one to six people. You correctly "guess" the two cards each person has selected at random from a pack they themselves shuffled. **THE ELECTRONICS NERVES TESTER** puts your friends to a very lively test. It gives out fail and finish signals (the winner is the person with lowest number of fail signals). *Can be adjusted from the weakest to strongest person.* **THE ELECTRONIC MAZE** tests the mental ability of the player because it uses psychology with an electronic twist to it. You can change the maze pathways in seconds to prevent the maze becoming too stale after lots of use. Completely safe and foolproof. Size 1 1/2in x 1 1/2in x 6in (max.). You can play all these games and more besides after building the "Brain-box". No soldering, you get pictorial, easy as ABC step-by-step simple instructions. ONLY **£2-87 + 30p P. & P.** for all parts including chassis, switches, stylus, signalling lights, wire, nuts, screws, etc. Uses standard battery. Presentation box 33p extra as illus. (if reqd.). **PARTS AVAILABLE SEPARATELY! FULL OPERATING DIRECTIONS WITH EACH OF THE PROJECTS.**



EXAMINE AT HOME FOR 7 DAYS. YOUR MONEY REFUNDED IN FULL IF NOT 100% DELIGHTED.

CONCORD ELECTRONICS LTD. (PE12), 8 Westbourne Grove, London, W.2. (Calls welcome. 9 a.m.-5.30 p.m.)

JAMES SCOTT

SALE OF SURPLUS ELECTRONIC EQUIPMENT

The following items are available for immediate delivery at very competitive prices—

SCANNING ALARM INDICATOR

Can be used for Automatic Monitoring of All Types of Test Points (Up to 25)


Incorporates Auto and Manual Facilities
Illuminated Digital Input Identification
Double Pole Gold Plated Contacts on Un-selector



Units Supplied Untested Less Indicating Meter Price £25 00
Carriage and Insurance (U.K. only) £1 50

DOSIMETER CHARGING UNIT TYPE 200

PORTABLE INSTRUMENTS USED TO CHARGE QUARTZ FIBRE TYPE POCKET DOSIMETER TO ZERO SUITABLE FOR USE WITH ALL STANDARD TYPES OF QUARTZ FIBRE DOSIMETERS HAVING A MAXIMUM OUTSIDE CHARGING END DIAMETER OF 0.605IN. TELEPHONE TYPE A.C. AND GENERATOR. THE OUTPUT OF WHICH IS RECTIFIED AND CHARGES UP A RESERVOIR CAPACITOR TO A MAXIMUM POTENTIAL OF ABOUT 300 VOLTS D.C. SUPPLIED LESS GENERATOR HANDLES PRICE £1 50. P & P 20p

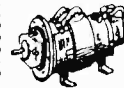

SEALED RELAYS (NATO APPROVED)

GEC 4 pole c/o 24V 670 ohm. GEC 2 pole on/off 24V 670 ohm. GEC 2 pole c/o 65V 5,000 ohm. STC 2 pole c/o 12V 170 ohm. Price each 75p. P & P 10p.



PC102 Supply voltage 220-250V a.c. Output voltages:
21 Volts d.c. at 350MA
21 Volts a.c. at 540MA

NEWMARKET TRANSISTORS

NKT351	73p	NKT12329	27p	2N2222	18p	NKT218	23p
NKT352	25p	NKT12429	27p	NKT112	30p	NKT221	30p
NKT406	90p	NKT13329	27p	NKT122	25p	NKT222	18p
NKT420	£1 90	NKT13429	27p	NKT73	22p	NKT223	25p
NKT450	30p	NKT16229	27p	NKT121	21p	NKT224	22p
NKT603	22p	NKT20329	29p	NKT124	28p	NKT227	25p
NKT613F	22p	NKT80111	65p	NKT125	38p	NKT237	28p
NKT674	18p	NKT80113	80p	NKT126	35p	NKT238	18p
NKT677	18p	NKT80125	80p	NKT127	23p	NKT249	28p
NKT713	27p	BC107	8p	NKT128	18p	NKT261	19p
NKT734	24p	BC108	8p	NKT129	22p	NKT270	18p
NKT736	23p	BC109	13p	NKT135	24p	NKT271	18p
NKT773	23p	BFY51	17p	NKT137	30p	NKT272	15p
NKT0216	20p	BSY95A	10p	NKT142	48p	NKT273	18p
NKT3055	23p	2N697	13p	NKT143	48p	NKT274	18p
NKT6817	23p	2N706	8p	NKT212	23p	NKT275	21p
NKT10339	23p	2N914	15p	NKT213	23p	NKT278	18p
NKT10419	17p	2N918	28p	NKT214	21p	NKT301	70p
NKT10439	25p	2N930	22p	NKT215	18p	NKT302	85p
NKT10519	20p	2N1990	22p	NKT217	48p	NKT303	70p
						NKT304	78p

S.T.C. RELAYS—BRAND NEW

TYPE	CONTACT FORM	NOMINAL VOLTAGE	COIL RESISTANCE (OHMS)	PRICE EACH
250 ARO	4 CHANGE/OVER	6V d.c.	52	£0 68
250 ABO	4 CHANGE/OVER	48V d.c.	2,500	£0 68


TYPE	CONTACT FORM	COIL VOLTAGE	SWITCHING CURRENT	PRICE EACH
SL722212	3 Pole on/off	12V a.c.	10A at 440V a.c.	£0 87
SL7622715	2 Pole C/O	220V a.c.	10A at 440V a.c.	£0 87

TYPE	CONTACT FORM	COIL VOLTAGE	COIL RESISTANCE	PRICE EACH
SP13372	Single Pole C/O	6V d.c.	140 ohm	£0 40
SP13366	Single Pole C/O	12V d.c.	350 ohm	£0 40
11301D	Single Pole C/O	18V d.c.	875 ohm	£0 40

UNISELECTOR SWITCHES

6 bank 25 way 75 coil 50V d.c. operation
Mounted on Modular Type Chassis with front panel containing 20 illuminated Push Button Switches. Completely wired for operation.

Price £15
P & P £0 55

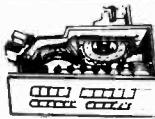

AUTOMATIC CYCLER UNIT

This unit generates stepping pulses (50V d.c.) at intervals of 6 pulses per min to 120 pulses per min—continuously variable. Can be used for Automatic Stepping of one or more uniselector switches shown above.

Price £12 50
P & P £0 45

NEWMARKET PACKAGED AUDIO AMPLIFIER

PC1 150mW Audio Amplifier. Price £1 00 each. P & P £0 10
PC10 Magnetic replay head amplifier supply voltage 9V d.c. input impedance 150. Price £0 90 each. P & P £0 10


WE HAVE A LARGE RANGE OF CAPACITORS AND RESISTORS. PLEASE SEND A STAMPED AND ADDRESSED FOOLSCAP ENVELOPE FOR YOUR CATALOGUE

POST & PACKING OVER £2—FREE OVER £1 AND UNDER £2—15p. UNDER £1—10p UNLESS SPECIFICALLY MENTIONED. P & P U.K. ONLY

JAMES SCOTT (ELECTRONIC ENGINEERING) LIMITED
CARNTYNE INDUSTRIAL ESTATE, GLASGOW G3 6AB
TEL: 041-778 4206

NOT JUST A RADIO BUT A COMPLETE COMMUNICATIONS RECEIVER BATTERY/MAINS PORTABLE RECEIVER

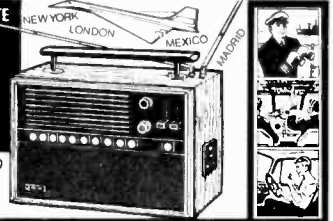WHAT RADIO PRICED AT UNDER £120 GIVES YOU SUCH A VARIED CHOICE OF TRANSMISSIONS?



8 WAVEBANDS
The most exciting radio ever!

CASH PRICE £49.50 + 50p P. & P. or £14.50 dep. + 50p P. & P. and 6 months at £7 (£56.50).

Picks up ALL THE USUAL BBC Programmes ★ All the new local radio stations ★ Continental ★ World-wide transmissions ★ Pop Pirates ★ Radio Hams ★ Aircraft ★ Shipping ★ Police ★ Taxis ★ RAC ★ AA ★ Fire Brigade ★ TV Sound ★ Ambulances and 1,000s more.

THE BEST PORTABLE RADIO EVER MADE! We think so. What radio priced at under £120 gives you such a varied choice of transmissions? As well as the standard long and medium wavebands it has three short wave bands (including the Marine and Trawler Band) AND NO LESS THAN THREE VHF BANDS, truly a complete WORLD-WIDE communications Receiver. JUST THINK! one minute you can be listening to your favourite BBC programme and then—at the flick of a switch—you can tune into the control tower and hear a "crippled airliner" being talked down to safety. Or listen to the trawlers and ocean-going liners—Eavesdrop on the taxi-cabs, fire brigades, ambulances, AA, RAC and 100s of other RT mobiles—even your local police! Extensive shortwave coverage can give you Australia, Pakistan, Luxembourg, North America, Far East, etc., you name it—it gets it! Manufactured by one of the world's leading specialists in communications and TV equipment, each set carries a FULL 3-YEAR WRITTEN GUARANTEE. Beautifully finished in Teak Wood and Stainless Steel—will add distinction to any living-room. Completely portable 12in x 9in x 4in, using standard batteries—or can be plugged directly into mains. 14 transistors, 6 diodes, 1 thermistor, internal ferrite rod aerial PLUS two external-telescopic antenna—with sockets for additional aerials. Complete with beat frequency oscillator for the real enthusiast or car aerials. Automatic Drift-Free Reception. Tone control. Fine squelch control. Hi-Fidelity earphone for private listening, local DX contacts. FREQUENCIES: Long W 150-350 Kcs. Medium W 540-1605 Kcs. Marine 1-6.4 Mcs. Short W 1 3.7-9 Mcs. Short W2 9-22 Mcs. FM (VHF) 88-108 Mcs. Aircraft (VHF) 108-136 Mcs. Public Service (VHF) 148-174 Mcs. THE ULTIMATE in communications receivers—used by professionals and amateur enthusiasts all over the world. INSTANT CASH REFUND if not overwhelmed by the superb tone clarity and performance range.

Note: Ministry of Posts and Telecommunications state that a licence not generally available to the public is required for the reception of Aircraft, Fire-brigade, Shipping, etc.

SCIENTIFIC AND TECHNICAL (PE12).

507-511 LONDON ROAD, WESTCLIFF, ESSEX

PCB's and KITS

For Designs Published in P.E.

All PCB's Fibreglass, Drilled, Roller-Tinned

(Circuit and assembly notes free with each PCB)

AURORA—Multichannel Sound Controlled Light

Designer Approved PCB and Kits
5/C's (excl. SCR's), R's, C's, Pots, Cores, 8 Ch. £17.75, 4 Ch. £10.15
Power Supply (will supply 8 channels), £2.85
PCB (4 1/2in x 1 1/2in) holds Pre-amp and 4 chans., incl. pots, £2.35
PCB (4 1/2in x 6 1/2in) holds PSU, Sync. Gen., 8 cores, 8 SCR's, £1.35

CALLERCORD—Automatic Answering Machine

Designer Approved PCB and Kits
5/C's, R's, C's, Pots, Switches, Relays, T/former, £12.15
PCB (4in x 7 1/2in) also holds edge-conn. and relays, £1.50
Parrot Tape Recorder, £6.95

DIGI-CAL—Details of PCB's on request

DOOR BELL YODELLER

5/C's, R's, C's, Pots, £4.20; PCB (3 1/2in x 3 1/2in), 90p

ELECTRONIC PIANO—Details of PCB's on request.

GEMINI PRE-AMP (Stereo set)
5/C's, C's, Pots, Maka-Sw's, 1/2W 2% MO R's, £13.45 (with 1/2W 5% CR R's, £10.75)

PCB (3 1/2in x 10 1/2in) Stereo. Also holds Pots and Maka-Sw's, £2.10

GEMINI MAIN AMP (30W per Channel)

PCB (3 1/2in x 5 1/2in) Stereo, £1.40; R's, C's, Pots (Stereo), £4.30

GEMINI POWER SUPPLY—PCB (2 1/2in x 4 1/2in) 75p; R's, C's, Pot, £3.70

GEMINI STEREO LOGIC—PCB (4 1/2in x 10 1/2in) as published, £1.80

LOGICAL RADIO CONTROL—PCB's as published, 60p each

MODEL SERVO CONTROL—PCB's as published

Servo-amps A and B, 60p each. Servo-amp C and Fail Safe, 50p each

MICROPHONE MIXER (April 1969)

5/C's, R's, C's, Pots, £2.90. PCB (3 1/2in x 4 1/2in) also holds pots, £1.20

PHOTOPRINT PROCESS UNIT

5/C's, SCR, LDR, R's, C's, Pot, Relay, Sw's, T/former, £7.60

PCB (3 1/2in x 5 1/2in) also holds Pots, Relay, Keyswitch, £1.20

SCORPIO CAR IGNITER—PCB as published, 95p

TAPE NOISE LIMITER—5/C's, R's, C's, Pot, PCB (1 1/2in x 3in) £2.20

Regulated PSU with PCB (1 1/2 x 2") will feed 2 units £3.20

ULTRASONIC TRANSMITTER-RECEIVER—Dual PCB (2" x 5 1/2")

75p; R's, C's, Pot, 5/C's (excl. Transducers) £2.20

VERSATILE LIGHT EFFECT UNIT—One Ch. Sound to Light

5/C's (excl. SCR), R's, C's, Pots, T/formers, Keyswitch, £8.85

PCB (5 1/2in x 5 1/2in) also holds Pots, Sw, T/former (T/77), £1.50

Other designs and PCB's available. S.A.E. for list.

U.K. orders 10p P & P. OVERSEAS P & P at cost.

PHONOSONICS

DEPT. PE12, 25 KENTISH ROAD, BELVEDERE, KENT. MAIL ORDER ONLY

ATTRACTIVE DISCOUNTS ON VERY MANY ITEMS WHEN YOU BUY FROM US

ELECTROVALUE Electronic Component Specialists

TRANSISTORS

Wide range. Up to date. Brand new —no 'seconds' or surplus. Highest quality and reliability.

Part No.	Price	Part No.	Price
IN4148	0-04	AF139	0-33
IN5399	0-24	AF239	0-38
2N2846	0-37	BC107	0-13
2N3056	0-65	BC108	0-12
2N3702	0-10	BC109	0-10
2N3703	0-10	BC148	0-10
2N3704	0-10	BC177	0-10
2N3819	0-25	BC184L	0-15
2N4286	0-15	BC212L	0-15
2N4289	0-15	BD130	0-15
2N4443	0-88	BD130	0-15
2N5082	0-42		
2N5088	0-46		
2N5192	0-46		
2N5195	0-46		
2N5457	0-46		
40361	0-46		
40362	0-46		
40432	0-46		
40512	0-46		
40669	0-46		
AC128	0-46		
AD142	0-46		
AD149	0-46		
AD161	0-46		
AD162	0-46		

Minitron DIGITAL

... in seg- com- andard power 9 from filament give height plus decimal point. ent 8mA from 5V d.c. per ited number of alphabetical ailable. In 16 lead DIL case



SOLDERSTAT SOLDER IRONS

As appointed distributors for well-known Eimco-Wolf "Solderstat" irons, we offer this model HM8 in 16 or 24 watt, a.c. mains, net

£1-87

INFINITELY VARIABLE TEMPERATURE CONTROLLED SOLDER IRON £9-20

DE-SOLDER BRAID

Per 6ft length, net 50p.

NIPPIBOARDS

A useful board for circuit building. Type 1A. Single basic pattern 2-2" x 1-7", 15p. Type 2A. Two pins, side by side, 28p. Type 2AS. Dual channel, 28p. Type 3A. 3 pins, side by side, 38p. Type 4AS. Dual channel, 2 above 2, 44p. Types in stock up to 10 patterns.

PUBLICATIONS

Resistor Equivalents, 40p. Handbook of Resistor Values (H. Ness), 40p. Radio & TV Codes & data wall chart, 15p. Resistor & Tables, 20p. (Add 3p postage for all orders bought separately.)

TTL

These prices are nett.

1 (7473)	45p
1 (7474)	45p
1 (7475)	45p
1 (7476)	45p
1 (80)	68p
1 (81)	87p
1 (7486)	1-33
1 (7490)	33p
1 (7491A)	80p
1 (7492)	1-28
1 (7493)	88p
1 (7494)	80p
1 (7495)	1-13
1 (7496)	87p
1 (7497)	1-48
1 (7498)	1-64
1 (7499)	43p
1 (7500)	58p
1 (7501)	48p
1 (7502)	1-80
1 (7503)	1-80
1 (7504)	1-74
1 (7505)	1-74

It's more than just a catalogue—and we give you a 25p REFUND VOUCHER with it!

ELECTROVALUE Catalogue No.6

Resistor Equivalents
Integrated Circuits
Components
Antennas
Materials
Equivalent Tables
Quality Diagrams

RESISTORS

Codes Power Tolerance

C	1/20W	5%
C	1/8W	5%
C	1/4W	10%
C	1/2W	5%
C	1W	5%
MO	1/2W	2%
WW	1W	10%
WW	3W	±1/20%
WW	7W	5%

Codes: C = carbon
MO = m.o.s.
WW = wirewound

Values:
E12 denotes ten decades. E24 denotes twenty decades. E48 denotes forty-eight decades. E96 denotes ninety-six decades. E192 denotes one hundred and ninety-two decades. E96 and E192 denote power rating, NOT minimum resistor order.

The Electrovalue Catalogue No. 6 (4th printing—96 pages) is as much a manual of valuable technical information as it is a comprehensive, up-to-date catalogue of semiconductors, components, accessories, materials, tools, etc. All items are brand new and to makers' specifications. Prices are competitive, there are attractive additional discounts offered, and now we include a refund voucher for 25p available for spending on orders for £5 or more. Send 25p for latest Electrovalue Catalogue now, post free.

- Hundreds of today's most wanted transistors with data and outlines
- Diodes, thyristors and tri-acs fully detailed
- I.C.'s plus schematics, theoretical and connection diagrams
- Slide and rotary potentiometers, knobs, plates, etc.
- Resistors and capacitors in very wide ranges
- Siemens pot cores
- Connectors, switches, relays
- Transformers, solder irons, etc.
- S-Dec, T-Dec, mounting boards
- Technical handbooks

BAYANAL

As desired wireless special case 10 watt

Speaker unit. Pack flat each. Finish with ink

SIEMENS TE 0-8A-400V, 50p. 3A-400V, 60p.

CARBON SKELETON
Small high quality, type 470Ω, 1K, 2K2, 4K7, 470K, 1M, 2M2, 5M, mounting, 5p each.

ZENER DIODES 5% tolerance. 2.7V to 36V, 14p each; 1.3W, 4.7V to 75V, 48p each. Clip to increase 1.5W rating to 3W.

MINIATURE TOGGLE SWITCHES 2A/250V. DP/DT, 48p.

MAINLINE AMPLIFIER KITS 70 watt power amp module kit, £12.60 net. Supply kit, £8.50 net.

PRICES APPEARING IN THIS ADVERTISEMENT ARE SUBJECT TO ALTERATION WITHOUT NOTICE.

LINEAR I.C.s

709C/5, 705 38p.
70C/5, 705 42p.

METERS

long spindles. 12p; Single gang linear 4.7kΩ to 22kΩ, 47kΩ, 1MΩ 42p. Any type with available in ranges

combination of P.20 knobs, pair 24p.

DIODES

to £15. No discount on items marked operation without notice.

SHIPPING AND PACKING

FREE unless otherwise stated. Handling surcharge 10p on all orders under £2. Overseas orders: carriage and insurance charged at cost. U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. 27, Swarthmore, PA 19081.

ENQUIRIES FROM TRADE AND OTHER LARGE QUANTITY BUYERS INVITED.

ELECTROVALUE

(Dept. PE 12) 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Hours: 9—5.30. Sat. 1 p.m. Tel.: Egham 3603 (STD 0784-3). Telex 264475
ELECTROVALUE LTD—AN INDEPENDENT COMPANY SINCE ITS ESTABLISHMENT IN 1965

BI-PRE-PAK

COMPLETE TELEPHONES



EX. G.P.O. NORMAL
HOUSEHOLD TYPE

ONLY 95p

POST & PACKING 35p EACH



TELEPHONE DIALS

Standard Post Office type.
Guaranteed in working order.

ONLY 50p
POST & PACKING 15p

TESTED AND GUARANTEED PAKS

- | | | | |
|-------------------------------|-----|--|-----|
| B2 | 4 | Photo Cells, Sun Batteries. 0.3 to 0.5V, 0.5 to 2mA | 50p |
| B79 | 4 | 1N4007 Sil. Rec. diodes. 1,000 PIV 1 amp. plastic | 50p |
| B81 | 10 | Reed Switches, mixed types large and small | 50p |
| B99 | 200 | Mixed Capacitors. Approx. quantity, counted by weight | 50p |
| H4 | 250 | Mixed Resistors. Approx. quantity counted by weight | 50p |
| H7 | 40 | Wirewound Resistors. Mixed types and values | 50p |
| H40 | 20 | BFY 50/2, 2N696, 2N1613, NPN Silicon uncoded TO-5 | 50p |
| H9 | 2 | OC71 Light Sensitive Photo Transistor | 50p |
| H28 | 20 | OC200/1/2/3 PNP Silicon uncoded TO-5 can | 50p |
| H30 | 20 | 1 Watt Zener Diodes, Mixed Voltages 6-8-43V | 50p |
| H35 | 100 | Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked | 50p |
| H38 | 30 | Short lead Transistors, NPN Silicon Planar types | 50p |
| H39 | 10 | Integrated circuits 6 gates BMC 962, 4 flip flops BMC 945 | 50p |
| UNMARKED UNTESTED PAKS | | | |
| B1 | 50 | Germanium Transistors PNP, AF and RF | 50p |
| B66 | 150 | Germanium Diodes Min. glass-type | 50p |
| B83 | 200 | Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ. | 50p |
| B84 | 100 | Silicon Diodes DO-7 glass equiv. to OA200, OA202 | 50p |
| B86 | 50 | Sil. Diodes sub. min. IN914 and IN916 types | 50p |
| B88 | 50 | Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc. | 50p |
| H6 | 40 | 250mW. Zener Diodes DO-7 Min. Glass Type | 50p |
| H15 | 30 | Top Hat Silicon Rectifiers, 750mA. Mixed volts | 50p |
| H16 | 15 | Experimenters' Pak of Integrated Circuits. Data supplied | 50p |
| H17 | 20 | 3 amp. Silicon Stud Rectifiers, mixed volts | 50p |
| H20 | 20 | BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts | 50p |
| H34 | 15 | Power Transistors, PNP, Germ. NPN Silicon TO-3 Can | 50p |

MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK'. This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

AC107	4p	OC170	4p
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-23
AC128	0-15	OC201	0-23
AC176	0-20	2N1302-3	0-15
AC177	0-20	2N1304-5	0-17
AF239	0-30	2N1306-7	0-20
AF186	0-20	2N1308-9	0-22
BC146	0-10	2N3819FET	0-40
BC154	0-20	2N4416FET	0-35
BC107	0-10		
BC108	0-10	Power Transistors	
BC109	0-10	OC20	0-40
BC169	0-12	OC23	0-25
3F194	0-15	OC25	0-25
BF274	0-20	OC26	0-25
BFY50	0-15	OC28	0-30
BSY25	0-13	OC35	0-25
BSY26	0-13	OC36	0-37
BSY27	0-13	AD149	0-35
BSY28	0-13	AU170	0-75
BSY29	0-10	2S034	0-25
BSY95A	0-15	2N3055	0-40
OC41	0-13		
OC44	0-10	Diodes	
OC45	0-10	AA42	0-10
OC71	0-10	OA95	0-07
OC72	0-10	OA79	0-07
OC81	0-13	OA81	0-07
OC81D	0-13	OA95	0-07
OC83	0-18	IN914	0-06
OC139	0-13		
OC140	0-15		

POWER TRANSISTOR PRICE BREAKTHROUGH!

Plastic Cased Silicon Power Transistors of latest design. 40 watts and 90 watts. PNP and NPN types. All types available at the most shattering low prices of all time. All are fully tested, marked and guaranteed!

40W NPN	1-12	13-25	26-50
40W PNP	20p	18p	16p
90W NPN	21p	19p	17p
90W PNP	24p	22p	20p
90W PNP	25p	23p	21p

PAKS of matched pairs:
MP40 40W + 40W 50p 48p 46p
MP90 90W + 90W 60p 58p 56p

A CROSS HATCH GENERATOR FOR £3.50!!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs £3.50, post paid.

A MUST for Colour T.V. Alignment.

Our famous PI Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.I. Only 50p. 10p P & P on this Pak.

FREE CATALOGUE FOR

TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS



8 RELAYS FOR VARIOUS TYPES £1

INTEGRATED CIRCUITS

Clocked Flip Flop, Ex. 2/4-input Buffer.	BMC931	20p	18p	16p
2/4-input Expander.	BMC932	12p	11p	10p
Hex. Inverter.	BMC933	12p	11p	10p
Hex. Inverter.	BMC934	12p	11p	10p
Hex. Inverter.	BMC935	12p	11p	10p
Hex. Inverter.	BMC936	12p	11p	10p
Hex. Inverter.	BMC937	12p	11p	10p
Decade Counter.	BMC938	25p	23p	21p
Div. by 16 Counter.	BMC939	25p	23p	21p
Hex. Inverter.	BMC940	12p	11p	10p
Hex. Inverter.	BMC941	12p	11p	10p
Type D Flip Flop.	BMC942	20p	18p	16p
Ex. 2/4-input Power.	BMC944	12p	11p	10p
Clocked Flip Flop.	BMC945	20p	18p	16p
Quad Inverter.	BMC946	11p	10p	9p
Clocked Flip Flop.	BMC948	20p	18p	16p
Quad Inverter.	BMC949	12p	11p	10p
Pulsed Trig. Binary.	BMC950	20p	18p	16p
Monostable Multivib.	BMC951	25p	23p	21p
Dual J/K Flip Flop.	BMC952	20p	18p	16p
Dual J/K Flip Flop.	BMC953	20p	18p	16p
Dual J/K Flip Flop.	BMC955	20p	18p	16p
Dual J/K Flip Flop.	BMC956	20p	18p	16p
Quad. 2-input Power.	BMC958	12p	11p	10p
2/4-input Gate.	BMC961	12p	11p	10p
3/3-input NAND Gate.	BMC962	11p	10p	9p
3/3-input NAND Gate.	BMC963	12p	11p	10p
Audio Amp. 3-watts.	SL403D	£1.50	£1.40	£1.36
Linear Op. Amp. 709C		25p	20p	15p
Decade Counter, SN7490		65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low
16 pin type at 16p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock.

These are just two of our popular lines:
B.P.I. Transistor Equivalents and Substitutes;

This includes many thousands of British U.S.A., European and C.V. equivalents.
The Iffife Radio Valve & Transistor Data Book 9th Edition;

Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.

Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME

ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX
TELEPHONE: SOUTHEND (0702) 46344

Practical Electronics Classified Advertisements

RATES: 9p per word (minimum 12 words). Box No. 20p extra. Semi-Display £7 per single column inch. Advertisements must be prepaid and addressed to Classified Advertisement Manager, "Practical Electronics" IPC MAGAZINES LTD., Fleetway House, Farringdon Street, London EC4A 4AD

BOOKS AND PUBLICATIONS



THE PICTURE BOOK METHOD OF LEARNING

BASIC ELECTRICITY 5pts £4.50. BASIC ELECTRONICS 6pts £5.40. BASIC TELEVISION 3pts £3.60

The quickest and soundest method of gaining mastery over these subjects. The clear and concise illustrations make study a real pleasure. P. & P. included Your Money Back Guaranteed. Free Illustrated Prospectus on request. SELRAY BOOK CO., 60, HAYES HILL, BROMLEY BR2 7HP.

FREE

ELECTRONIC COMPONENTS CATALOGUE
★ Everything from nuts and bolts to I.C.'s ★

ALL YOU HAVE TO DO IS
PHONE

03-742 79033

Or write **MAPLIN ELECTRONIC SUPPLIES**
P.O. Box No. 3, Rayleigh, Essex. No s.a.e. needed.

FOR SALE

MORSE MADE EASY!!
FACT NOT FICTION. If you start **RIGHT** you will be reading amateur and commercial Morse within a month (normal progress to be expected). Using scientifically prepared 3-speed records you automatically learn to recognise the code **RHYTHM** without translating. You can't help it, it's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

Beginner's Section only **£3.80**, complete course **£4.50** (Overseas £1 extra) details only, 4p stamp. **01-660 2896**
GBHC (Box 19), 45 GREEN LANE, PURLEY, SURREY

CATALOGUE NO. 18, Electronic and Mechanical Components and manufacturers' surplus. Credit vouchers value 50p. Price **23p**, including post. **ARTHUR SALLIS RADIO CONTROL LTD.**, 28 Gardner Street, Brighton, Sussex.

SEEN MY CAT? 5,000 items. Mechanical and Electronic Gear, and materials. S.A.E. K. R. WHINSTON, Dept. PE, New Mills, Stockport.

TELEQUIPMENT OSCILLOSCOPE and Audio Signal Generator, **£45**. Can sell separately. Tel. 01-289 0730.

EDUCATIONAL

GET INTO Electronics—opportunities for trained men. Learn at home. Postal courses in RTEB, City & Guilds, Radio, TV, Telecoms, etc. **FREE** informative guide: **"CHAMBERS COLLEGE (Dept. R.104), Aldermaston Court, Reading, RG7 4PE.**

ENGINEERS—get a technical certificate. Postal courses in Engineering, Electronics, Radio, TV, Computers, Draughtsmanship, Building, etc. **FREE** book from: **BIET (Dept. H.4), Aldermaston Court, Reading, RG7 4PE. Accredited by CACC.**

HI-FI EQUIPMENT

DISCOTHEQUE AND THEATRE EQUIPMENT. Custom built to 1,000W audio and 100kW lighting control. Made to measure design service. Inquiries to Box No. 44.

SITUATIONS VACANT

MEN! £50 p.w. can be yours

Jobs galore! 144,000 new computer personnel needed by 1977. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £2500+p.a. After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you **FREE** to world-wide opportunities. Write or 'phone **TODAY**, without obligation.

London Computer Operators
Training Centre
E83, Oxford House
E87, Oxford Street, W.1.
Telephone: 01-734 2874

127, The Piazza, Dept. E87,
Piccadilly Plaza, Manchester 1.
Telephone: 061-236 2935

WANTED

TOP PRICES PAID
for new valves and components
Popular T.V. and Radio types
KENSINGTON SUPPLIES
(B) 367 Kensington Street
Bradford 8, Yorks.

PRACTICAL ELECTRONICS. Back numbers wanted. B. W. HUGHES, 11 Henley Road, Ludlow, Salop.

LADDERS

LADDERS, 24ft **£9.80**, carr. 80p. Leaflet (Dept. PEE), **HOME SALES LADDER CENTRE**, Baldwin Road, Stourport, Worcs. Tel. 029-93 2574.

SERVICE SHEETS

★ **SERVICE SHEETS • MANUALS • BOOKS** ★
SERVICE SHEETS OVER 12,000 SERVICE SHEETS AND MANUALS IN STOCK
30p + Postage PLEASE ENCLOSE S.A.E. WITH ENQUIRIES... **SERVICE SHEET Catalogue 20p.**

NEW BOOKS & PUBLICATIONS	PRICE + P & P
32. SIMPLE SHORT WAVE RECEIVERS by Data Publications Ltd. 192 pages	£0.80 10p
33. RADIO CONTROL FOR MODELS by Data Publications Ltd. 140 pages	£0.75 12p
34. RADIO VALVE AND TRANSISTOR DATA 9th Edition by A.M. Ball. 340 pages	£0.75 15p
35. GUIDE TO BROADCASTING STATIONS 16th Edition. 160 pages	£0.50 8p
36. TRANSISTOR AND RADIO CIRCUITS by Mullard Ltd. 230 pages	£1.80 15p
37. 1971-72 MULLARD DATA BOOK. Data on Valves & Semiconductors	£0.50 7p
38. SERVICING WITH THE OSCILLOSCOPE by G.J. King. 176 pages	£1.80 15p
39. PRACTICAL OSCILLOSCOPE HANDBOOK by R.P. Turner. 236 pages	£1.80 15p
40. MEASURING OSCILLOSCOPE by J.F. Golding. 272 pages	£4.20 30p
41. QUESTIONS AND ANSWERS ON TRANSISTORS by C. Brown. 96 pages	£0.50 10p
42. SEMICONDUCTORS: BASIC THEORY AND DEVICES by I. Kampel. 272 pages	£2.50 20p
43. UNDERSTANDING THE SEMICONDUCTOR by C.N. Matthews. 128 pages	£1.30 10p
44. TAPE RECORDERS by H.W. Hallver. Guide to Purchase & Operating. 239 pages	£2.25 15p
45. PHOTO-ELECTRONIC DEVICES by J.B. Dance. 163 pages	£2.10 20p
46. AUDIO AMPLIFIERS by Data Publications Ltd. 128 pages	£0.55 10p
47. RAPID SERVICING OF TRANSISTOR EQUIPMENT by G.J. King. 160 pages	£1.50 15p
48. BEGINNER'S GUIDE TO ELECTRICITY by Clement Brown. Assoc. Brit. I.R.E.	£1.60 15p
49. BEGINNER'S GUIDE TO ELECTRONICS by Terence L. Squires. AMIERE	£1.30 15p
50. BEGINNER'S GUIDE TO TRANSISTORS by J.A. Reddihough	£1.00 15p
51. PRINCIPLES OF SEMICONDUCTORS by M.G. Scraggie, BSc. CEng. F.I.E.E. 156 pages	£1.50 15p
52. THE PRACTICAL AERIAL HANDBOOK by G.J. King. 232 pages	£2.70 20p
53. AERIALS by D.J.W. Stobbema. Practical Work. 110 pages	£0.80 10p
54. ELECTROACOUSTICS: MICROPHONES, EARPHONES AND LOUDSPEAKERS. 300 pages	£4.30 30p
55. MAGNETIC TAPE RECORDING by H.G.M. Sparat, BSc. F.I.E.E. 368 pages	£3.20 25p
56. MICROPHONES by A.E. Robertson, M.B.E., BSc. M.I.E.E. 359 pages	£3.75 30p
57. THE HI-FI AND TAPE RECORDER HANDBOOK by G.J. King. 304 pages	£2.00 15p
58. PRINCIPLES OF AERIAL DESIGN by H. Page MSc. F.I.E.E. 162 pages	£2.50 20p
59. A.C. MOTOR CONTROL by R.T. Lyhall. CEng. F.I.E.E. 148 pages	£2.60 20p
60. INTEGRATED CIRCUIT SYSTEMS by D.J. Walter. 234 pages	£3.50 20p
61. SOLID-STATE DEVICES AND APPLICATIONS by R. Lewis. 264 pages	£3.60 25p
62. GUIDE TO PRINTED CIRCUITS by G.J. King. 140 pages. 95 illustrations	£2.50 15p
63. ELECTRONIC COUNTING CIRCUITS by Mullard Ltd. 224 pages	£1.40 15p
64. PRACTICAL INTEGRATED CIRCUITS by A.J. McEvoy and L. McNamora. 144 pages	£0.90 12p
65. POWER ENGINEERING USING THYRISTORS VOL. 1. by Mullard Ltd. 228 pages	£1.50 15p

Send S.A.E. for free **LISTS** of Practical and Technical Books on Radio & Television now available to

BELL'S TELEVISION SERVICES

★ **Albert Place, Harrogate, Yorks. Tel. 0423-86844** ★

SERVICE SHEETS for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc. from **5p** with free Fault-Finding Guide. S.A.E. orders/inquiries. Catalogue **15p**. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 29066.

SERVICE SHEETS. Radio, TV, etc., 8,000 models. List **10p**. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

MUSICAL INSTRUMENTS

ELECTRONIC PIANO

Touch Sensitive Pedal Sustain
Adjustable Decay

Plug-in units for constructing 2, 4, 6 octave ELECTRONIC PIANO. Also, Touch Sensitive Percussion Units for Keyboard Bass or add Piano Sound to existing organ. S.A.E. details of these and other units.

To: **DIGICORD**
Duffryn Glywd House
Elm Road, Tokers Green
Reading, Berks.

RECEIVERS AND COMPONENTS

COMPUTER PANELS

Panel contains 2 x Mullard OC23 Transistors and 5 other Transistors, etc. 2 panels 50p p.p. 15p. Panel contains 2 x Mullard OC28 Transistors 2XBCY34, etc. 2 panels 50p p.p. 15p. Assorted Computer Panels contain many useful Transistors, Diodes, Trim Pots, etc. 4 Panels for £1 post free. Assorted Panels contain minimum of 10 integrated circuits, also Transistors, Diodes, etc. £1 p.p. 15p. Electrolytic Capacitors UF/V. 2,000/35, 10,000/15, 10,000/25, 12,500/35. All at 30p each p.p. 6p. 2,000/50, 2,500/50, 5,000/50, 10,000/50, 10,000/50, 50,000/15 all at 40p each p.p. 10p. Also available wide range motor start capacitors also block paper, etc. Send your exact requirements. Assorted miniature and subminiature Electrolytic Capacitors, 100 for £1-20 p.p. 15p.

Mail Order only

XEROZA RADIO

1 East Street, Bishop's Tawton, Devon

TV Line out-put Transformers

Replacement types ex-stock.

For "By-return" service, contact London 01-948 3702

Tidman Mail Order Ltd., Dept. PE,
236 Sandycroft Road,
Richmond, Surrey TW9 2EQ

Rectifiers and Frame out-put Transformers also stocked.
Callers welcome.

DRY REED INSERTS

Overall length 1.85" (Body length 1.1")
Diameter 0.14" to switch up to 500 mA at up to 250V D.C. Gold clad contacts. 62¢ per doz.; £3-75 per 100; £27-50 per 1,000; £250 per 10,000. All carriage paid.
G.W.M. RADIO, LTD.
40/42 Portland Road, Worthing, Sussex 0903 84897

5-N-Channel FETs 3819E—£1

Full specification devices complete with circuit details for building voltmeter, timer, ohmmeter, etc.
Send 10p for full list of field effect transistors and other top quality transistors available at bargain prices.

REDHAWK SALES LTD.
45 Station Road, Gerrards Cross, Bucks.
MAIL ORDER ONLY

BRAND NEW COMPONENTS BY RETURN.

Electrolytics 16V or 25V, 1, 2-2, 4-7, 10 mfd., 33p, 22, 47, 4p, 100, 5p, 50V, 1p extra. Subminiature bead-type tantalums, 0-1/35V, 0-22/35V, 0-47/35V, 1/35V, 2-2/35V, 4-7/35V, 10/16V, 8p, Mylar Film 100V, 0-001, 0-002, 0-005, 0-01, 0-02, 2p, 0-04, 0-05, 24p, 0-068, 0-1, 3p. Polystyrene 63V, 10p, 10-000p, E12 series, 2p. Mullard miniature Carbon Film Resistors, E12 series, third watt 1Ω-10 MΩ, 8 for 5p. Insured postage, 8p. THE C.R. SUPPLY CO., 127 Chesterfield Road, Sheffield, 88.

POLYSTYRENE CAPACITORS. 125V-100, 120, 150, 180, 220, 270, 330, 390, 500, 680, 820, 1,200, 1,500, 1,800, 2,200, 2,700, 3,300, 3,900, 5,000, 6,800, 8,200, 0-01, 0-012, 15p doz., 10p 10z, 0-015, 0-018, 0-022, 0-027, 0-033, 24p doz., post 10p.

COMPUTER PANELS. 3-BC108, diodes, etc., 4-50p, post 10p. American panels, 4-55p, post 12p. Panel type 773B, 8 silicon transistors, 40 diodes, 80p; 701B, 6 silicon transistors, 16 diodes, 12p, post 3p each. For lists of other types and components send large S.A.E.

UNIT WITH 4L4G POT CORES + CAPS. 50p, post 15p. LA2 ex. equipt., 20p, new and boxed, 30p. C.P. ORP12 ON PANEL EX. EQUIPT., 35p, C.P. M.C. METERS 2 and 3in, three ass., £1-05, post 25p.

WIRE ENDED NEONS. 10-45p, 20-75p, post 8p. **BANK OF FIVE WITH FIVE C407 DRIVER TRANSISTORS.** 45p. Car Bank of 30 with 30 transistors, 42-15, C.P. **NEW 46 WAY STEPPING SWITCH WITH RESET** for mains operation, £1-25, post 25p. **CROUZET GEARED SYN. MOTOR,** mains operation 15 r.p.m. a.c. wise, 75p, post 15p. **VELODYNE UNIT** 7 min. valves, w.w. res. caps, etc., 85p, post 15p. **IC 7400 SERIES** on panels, 10-75p, post 10p. **NEW COIL PACK LMSW** 8 piano key, no dupe, 50p, post 20p. **COPPER GLAD PAXOLIN,** single sheet, 2 1/2 x 3 1/2 in. 6 for 80p, post 10p.

ASSORTED COMPONENTS, 71b, £1-30, C.P. **ASSORTED COMPUTER PANELS,** 21b, £1-30, C.P. **MIXED POLYSTYRENE, S/MICA CAPS,** 100-40p, C.P.

MIXED TRANSISTOR AND I.C. FALL OUTS, 100 approx., 18p., C.P.

J.W.B. RADIO

75 HAYFIELD ROAD, SALFORD 6, LANCs.

Mail Order only

POTENTIOMETERS, carbon track, 10K, 100K, 1 meg. log. 2K, 50K lin. 9p; 250K, 1 meg. log. with D/P switch, 18p; 1 meg./1 meg. dual (stereo), 25p, P. & P. 5p. 8 assorted potentiometers, 60p, post paid. 8 assorted presets, 50p, post paid.

TAG STRIPS, 30 assorted pieces, 50p, post paid.

ROTARY WAFER SWITCHES, 6 mixed types, 50p, post paid.

MIXED component selection of ex-computer panels, potentiometers, tag-strips, knobs, capacitors, wafer switches, etc. £1-25, post paid.

WALKHAM ELECTRONICS

THE OLD MILL, COMMERCIAL ROAD
HORRABRIDGE, YELVERTON, DEVON

METERS, Motors, Relays, Valves, Electronics. At **ROGERS FASCINATING ESTABLISHMENT,** 31 Nelson Street, Southport.

Arbour Electronics Ltd.

EAST HANNINGFIELD INDUSTRIAL ESTATE, Near CHELMSFORD, ESSEX

Telephone: Hanningfield 700

EX COMPUTER COMPONENTS

5 multi contact relays 2-5K ohm coil, 50p. P. & P. 10p. 8 micro switches, mixed, 50p. P. & P. 10p. 240V motor with governor and slipping clutch 90p each. P. & P. 20p. 2-5A meters 3in x 3 1/2 in, 75p each P. & P. 10p. 5 printed circuits 4in x 4in, approx. 100 semiconductor, 50p. P. & P. 10p. Memory core stores ferrite cores 25 x 50 £1-50 each, 30 x 30 £1-00 each. P. & P. 30p.

300 mixed resistors/capacitors as new, 65p. P. & P. 5p. Cable 14/0076 600V, 100 yds, 65p. P. & P. 10p. Instrument cases, 8in x 6in x 6in, blue with white front panel, £1-60. P. & P. 25p.

SOUND SUPPLIES (Electronics) Co. Ltd.

P.A. EQUIPMENT. Marshall amps, instruments and guitars, etc. TOA and Eagle amps and accessories, Reslo mics, etc. **COMPONENTS.** Resistors, capacitors, plugs, sockets, cables, audio leads, semiconductor valves, vero board, etc., for the constructor. **Power packs and car droppers** for the cassette recorder or radio.

S.A.E. for list and enquiries. P.A. list 15p. 12 Smarts Lane, Loughton, Essex
Tel. 01-508 2715 Closed all day Thursday

Modern Computer Panels. with TO5 and plastic transistors, 6 for £1, 15p p. & p.

P/C Board S/S 5 1/2 in x 5 1/2 in. 10 for 50p + 15p p. & p. Panel with 8 OC43 + 24 OA81, 35p. p.p.

Transformers, 7-5 + 7-5V app. 1/2A, 60p, p.p. 18-0-18V 200mA + 24V 40mA 70p. p.p.

Brand New Min Jones Plugs and Sockets, 6V, 30p; 8V, 40p; 12V, 50p; 18V, 60p; 24V, 75p. All pairs p.p. 700 m/watt amp, 9V, 8Ω output, £1, p.p., with connections.

Transformers, 52-0-52V 1A + 22-0-22V 0-2A, £2, p.p. 34-0-34V 2A + 22-0-22V-2A, £2, p.p.

JEG1 Scope Tube, new, £1-75, p.p. **UHF Tuners,** transistorised, £1-50, p.p.

Veroboard 0-1 4in. x 2 1/2 in. 10 for £1 + 15p p. & p.

R.T. SERVICES (Mail order only)

77 Hayfield Road, Salford 6

NEW GUARANTEED DEVICES ORDER WITH CONFIDENCE

MICROCIRCUITS: 709 88p; 710 36p; 723 65p; 741 28p; 748 87p; 8N76013 (like IC1) £1-24; FET Op. Amp 84-88 74 Series TTL: 00 18p; 01 18p; 02 18p; 04 18p; 08 18p; 10 16p; 11 21p; 20 18p; 30 18p; 40 18p; 47 £1-35; 51 18p; 72 30p; 73 41p; 74 33p; 75 44p; 81 £1-28; 84 85p; 86 41p; 90 72p; 91 £1-21; 92 87p. **RECTIFIERS** 1 AMP: 50V 34p; 100V 4p; 200V 5p; 400V 6p; 600V 9p; 800V 12p; 1000V 14p; 3 AMP: 200V 11p; 400V 12p. **TRIAC** 10A 300V £1-20. **SCR** 1-6A 800V 75p; SCR 5-1A 400V £1-14. **TRANSISTORS:** 2N2926 RED 6p; OR. 7p; YEL. 8p; GRN. 9p; 2N3054 38p; 2N3055 45p; 2N3819 28p; AC127 128 10p; BC107B, BC108A, BC108C, BC108C all 8p; BFY50/51/52 10p; OC44/45/71/72 12p; OC81 8p. **ME SERIES:** 0401 19p; 0402 18p; 0404-2 16p; 0411 18p; 0412 18p; 0413 14p; 0414 24p; 1002 10p; 1120 18p; 3001 18p; 4002 12p; 4003 15p; 4101 10p; 4102 11p; 4103 10p; 6001 12p; 6002 14p; 6101 14p; 6102 18p; 8001 14p; 8003 15p; MEF 104 45p; MEL 11 35p; MEL 12 44p; MP8111 32p; MP8112 42p. **IC Sockets** 14 pin DIL 12p; **SOLDERCONS** 0-7p per pin. **LED Panel Lamp** 46p. Carbon 1W 5% **RESISTORS** 22 ohm to 2-2Meg. 1p each or 5p per 10 of one value. **ZENER DIODES** JZY88 Series 400mW 5% 2-7V to 33V 8p.

JEF ELECTRONICS (P.E.12)

YORK HOUSE, 12 YORK DRIVE, GRAPPENHALL, WARRINGTON, WA4 2EJ. Mail Order Only. C.W.O. P. & P. 9p per order. O/Sea 65p. Discounts start at 10% for 10+. List Free. **NEW FULL SPEC. GOODS. MONEY BACK GUARANTEE.**

KITS! KITS! KITS!

A new range of audio kits for discotheques, groups, musicians, etc. All parts guaranteed and full assembly instructions supplied.
REVERBERATION UNIT KIT
4 input 2 channel mix plus reverbation level control, etc. Battery operated. £10-50 + 50p P. & P.
100 WATT SLAVE AMPLIFIER KIT
A mains operated solid-state power amplifier for P.A. applications. Delivers 110 watts into 6 ohm load. £20 + £1 P. & P.
100 WATT INSTRUMENT/P.A. AMPLIFIER KIT
A professional amplifier using plug-in printed circuit boards. 4 input 2 channel mix with high-lift treble and bass controls on each channel. Separate master volume, etc. £30 + £1 P. & P.
FUZZ BOX KIT
A compact battery operated unit with pre-set fuzz/volume level controls and changeover switch. £3-50 + 25p P. & P.
SOUND-TO-LIGHT KIT
An effects lighting control unit featuring built-in amplifier and microphone. Modulates up to 1500 watts of lamps. Sensitivity fully variable. £8-50 + 50p P. & P.
The above kits are also available fully built and tested. S.A.E. for full details. Mail order to:

REID ELECTRONICS

43 Heaton Grove, Newcastle upon Tyne NE6 5NP

SPECIAL OFFER. 100 mixed resistors. Preferred Values 1/2W and 1/4W £1-25, including postage. 2-2mF 250V WKG 10p each, including P/P. **ALEXANDERS,** 16 Inverness Street, London, N.W.1. Tel. 485 5322.

PRECISION POLYCARBONATE CAPACITORS

FRESH STOCK — FULLY TESTED

Close tolerance. High stability. All 63V d.c.

0.47µF:	±5%	30p:	±2%	40p:	±1%	50p
1.0µF:	±5%	40p:	±2%	50p:	±1%	60p
2.2µF:	±5%	50p:	±2%	60p:	±1%	75p
4.7µF:	±5%	70p:	±2%	90p:	±1%	115p
6.8µF:	±5%	90p:	±2%	115p:	±1%	150p
10µF:	±5%	110p:	±2%	140p:	±1%	180p
15µF:	±5%	110p:	±2%	140p:	±1%	180p

TANTALUM BEAD CAPACITORS. Values available 0.22, 0.47, 1.0, 2.2, 4.7, 6.8µF at 35V, 10µF 25V, 15µF 20V, 22µF 15V, 33µF 10V, 47µF 6V, 100µF 3V—all at 9p each; 6 for 50p; 14 for £1. Special pack 6 off each value (72 capacitors) £5.

NEW TRANSISTORS. BC107, BC108, BC109. All at 9p each; 6 for 50p; 14 for £1. All brand new and marked. Full spec. devices. May be mixed to qualify for quantity prices.

POPULAR DIODES. IN914, 7p each; 8 for 50p; 18 for £1. 1N4148, 9p each; 6 for 50p; 14 for £1. 1N54, 5p each; 11 for 50p; 24 for £1. All brand new and marked.

NEW LOW PRICE — 400 mW Zeners. Values available 4.7, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15V. Tol. ±5% at 5mA. All new and marked. Price 10p each; 6 for 50p; 14 for £1.

RESISTORS. Carbon film 1/4W 5%. Range from 2.2Ω to 2.2MΩ in E12 series, i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades. High stability, low noise. All at 1p each; 8p for 10 of any one value; 70p for 100 of any one value. Special development pack—10 off each value 2.2Ω to 2.2MΩ (730 resistors) £5.

440V A.C. CAPACITORS. 0.1µF, size 1 1/2in X 1/2in, 25p; 0.25µF, size 1 1/2in X 1/2in, 30p; 0.47 and 0.5µF, size 1 1/2in X 1/2in, 35p; 1.0µF, size 2in X 1/2in, 45p; 2.0µF, size 2in X 1in 75p.

SILICON PLASTIC RECTIFIERS 1-5A— Brand new wire-ended DO27. 100PIV at 8p each or 4 for 30p; 400PIV at 9p each or 4 for 34p; 800PIV at 14p each or 4 for 50p.

5p post and packing on all orders below £5.

V. ATTWOOD, DEPT. D3, P.O. BOX 8, ALRESFORD, HANTS

Professional quality at budget prices! using Range 500 mixer modules. m.510 Microphone amplifier (6000Ω), £4; m.511 Equaliser (Bass & Treble), £4; m.512 Ceramic amplifier, £3-80; m.513 Line amplifier, £3-80; m.514 Buffer amplifier, £3-60; E.400 Phase amplifier, £3-30; B.30 Booklet on mixing circuits, 30p. 12p P. & P. Above 5 units free, above 10 units 15% discount.

Mixers and Effects equipment built to order. CRAIG AUDIO EQUIPMENT 54 Charles Street, Herne Bay, Kent

FORTRONIC IS EXPANDING

I/C Patchboard Kit £5

I/C Test Clips

Extended range of 7400 Series I/Cs. Development Kits of Carbon Film Resistors.

Range of 6v lamps and lampholders (4 different colours).

Neon instrument cases and cast zinc boxes.

Send s.a.e. for full lists

FORTRONIC (FIFE) LTD.

13 Knowhead, Crossford, Fife

100 WATT AMPLIFIER


Fully protected, transformerless, 9 transistor circuit. Input 500 mV. Output into 8 ohms. 0.1% distortion.

Printed circuit board and full instructions. £1-45p + 10p P. & P. S.a.e. for list of component bargains.

EDMUNDS COMPONENTS, 134 NORTH END ROAD, LONDON, W14. (Mail order only)

MINIATURE CARBON FILM RESISTORS. 5%, 1/4W, 1/2W, 1W, E12 Series. 220ohm to 1MΩ. 10 for 7p, 50 for 30p. Mixed values and wattages to your choice. ELECTRONIC COMPONENTS, Lake Bargain Centre, 113 Park Road, Didcot.

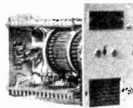RADIO & TELEVISION AERIAL BOOSTERS £2-95, five television valves 45p. 50p bargain transistor packs, bargain £1 resistor and capacitor packs. UHF-VHF televisions £7-50. Carr. £1-50. S.A.E. for 3 leaflets. VELCO ELECTRONICS, Bridge St., Ramsbottom, Bury, Lancs.



REED UNITS

Contains 31 1/4A 250V reeds mounted round a drum with magnet inside, also resistors sockets, etc., £1 (25p); 2 for £1-65 (35p). BC107-8-9 8p, 14 for £1; 2N435 35p; µA741C 25p; 2A709C 25p; Ferric Chloride, 1lb, 40p (15p), 10lb £3-50 (40p).

Capacitors: 250µ/25V 8p, 13 for £1; 500µ/25V 12p; 1000µ/25V 16p; 2000µ/25V 24p; 80 + 80 + 20µ/35V 10p, 10 for 75p (25p). Resistors: 300 5%, 60p (15p); 200 5%, Hi-Stabs 5p (12p); 100 1 and 2% 60p (10p); 100 Metal Oxide 60p (8p); one of each pack £2 (25p). Tape Amplifier, 4 valve, 20µV i/p 2W o/p, with speaker and case, £3 (£1).

GREENWELD (PE3), 24 Goodhart Way, West Wickham, Kent
Telephone 01-777 2001
Post in brackets, small parts 3p. S.A.E. List

Trampus electronic

All Brand New. Money Back Guaranteed. Fast Service. 5V DIGITAL INDICATOR 0-9DP, with socket and red Filter £1-45. NIXIE 999 IC GAS DETECTOR. Smoke, Butane, Vapour, etc. £2-19, data 9p. ULTRASONIC TRANSDUCER. Transmit or receive, £2. LIGHT EMIT DIODES. Visible red/panel clip/data, 30p. INFRA RED (invisible beam), £1-19.



IC digital clock

28 pin DIL 12/24 hr. 4/6 digit, £11-50, data 9p. PW Texan Kit, less chassis, £21-49. PAKS: Res, 80p; IC/semiconductor, 8p. All caps, £2-49; Transformer, £2-67; TIP 41/42, pair £1-70; 741/748, 39p ea. INTEGRATED CIRCUITS with data 741 op. amp. DIL, 30p; 709 TO5, 21p; DIL, 28p; 710, 33p; 748, 37p. Photo Detector/amp, 44p. Voltage Regulators: 1µ amp, 5 to 20V, £1-67; and 723, 50p; 555 TIMER/stab oscillator, £1-19. Audio amp., 3-5W, £1-24; Dual Preamp., £1-67. MC1310P MPX Decoder for any FMRX, £2-68.



740 TTL

BRANDED TEXAS/TIT etc. FULL RANGE

Gates, 7400/1/2/3/4/5/10/20/30/40/50, etc., 15p; 7413, 20p; 7470/72, 30p; 7474/74, 40p; 7447, £1-60; 7490, 59p; 7492, 59p; 74121, 49p; 74141, £1. DIL SOCKETS, high or low profile, 14 or 16 pin, 13p. SEMICONDUCTORS 2N3055, 40p. BC107, 8p. BC108, 7p. BC109, 8p. AC125/6/7/8, AC127/8, AC187/8, AF117, 16p; AD16/12, 35p; BC167/8/9, 17p; BC177/8/9, 15p; BC182/3/4, 8p; BC212/3/4, 9p; BCY70, 16p; BFY90/1/2, 17p; T1848 UJT, 29p; 2N706A, 12p; FET 2N3818, 28p; 2N2926 O. Y., 9p; 2N3053, 17p; 2N3702/3/4/5/6/7, 11p; 2N3708/9/10/11, 9p. 1A RECTS: 50V, 4p; 400V, 8p; 50V Bridge, 29p. 1N14/6, 5p; OA81/91, 7p; OA200/202, 10p. ZENERS: BZY88 400mW 11p; 5-1V/10W, 29p. 400V SCR: 1A, 23p; 5A, 49p; 4A, 55p. NEW: BC204/5/6/7/8, 11p; 2N3414/5/6/7, 18p.

Calculator

8 DIGIT. 4 FUNCTION. Fully built. Year Guarantee. 239 data S.A.E. CAPACITORS: 25/30V Electrolytic. 10/50/100µF, 5p; 200/500µF, 8p; 1,000µF, 15p. DISC: 22p thro' to 0.047µF, 8p; 0-01 to 0.6p. RESISTORS 1/4W 5%, 13p. PRESETS 0-25W, 5p. VERO 16p/8p, etc., DIN plugs, 13p; sockets, 8p. Stereo Amp. in case, £14-67. Light Dimmer, £3. ELECTRONIC CAR IGNITION KIT, £6-67. FREE CATALOGUE, S.A.E., Data 8ht., 6p each. CWO. P. & P. 7p, Overseas 35p. Discount 10 + 10%. P.O. BOX 29, BRACKNELL, BERKS.

VERNITRON CERAMIC RESONATORS for i.f. filtering. FM4, 10-7MHz (bandwidth 235kHz), matched pair, £1-50. 455kHz types: TF-01A, 38p; TO-02A, 45p; TF-04 442, 40p; TFN-3A kit, £1-60; TFN-3ADX, £1-50; TFN-205, 40p. Data supplied with orders. Mail order only, U.K. post 5p. AMATRONIX LTD., 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

MISCELLANEOUS

YOUNG SCIENTISTS

and not-so-young, whether beginner or advanced — we offer a range of over 35 SUPER projects.

Have you ever wanted to build A MACHINE THAT LEARNS? Or perhaps make a TEACHING DEVICE? Maybe you fancy the idea of an ELECTRONIC FANTASY MACHINE? How about a "Thing" capable of REPRODUCING ITSELF? Whatever your electronic turn-of-mind, there's just GOT TO BE LOADS TO INTEREST YOU in the science-fiction-world of BOFFIN.

GET YOUR CATALOGUE — SEND JUST 15p NOW! (S.A.E. for details).

TO: BOFFIN PROJECTS

4 CUNLIFFE ROAD
STONELEIGH, EWELL
SURREY

Designs by GERRY BROWN and JOHN SALMON and presented on TV.

CIRCUIT BOARD ETCHING KITS, full instructions, £1-25, e.w.o. ARVIN SERVICE COMPANY, 12 Cambridge Road, St. Albans, Herts.

CLEARING LABORATORY, scopes, V.T.V.M.'s, V.O.M.'s, H.S. recorders, transcription turntables, electronic testmeters, calibration units, P.S.U.'s, pulse generators, D.C. null-potentiometers, bridges, spectrum analysers, voltage regulators, sig-gens, M/C relays, components, etc. Lower Beeding 236.

CONSTRUCTION AIDS. Fascia panels, dials, nameplates in etched aluminum to individual specification. Sheet aluminum, printed circuits—drafting tapes, negatives supplied, boards manufactured, singles or small runs. Copper clad laminate supplied. Hardware for constructors. S.A.E. details. RAMAR CONSTRUCTOR SERVICES, 20 Shelbourne Road, Stratford-on-Avon, Warwks.

LSI Clock

At last BYWOOD can offer the amateur constructor an LSI Digital Clock chip. This MOS chip is built into a 28 pin package. Control inputs to the device select 50 or 60 Hz operation, 12 or 24 hour display, 4 or 6 digit output. Outputs are multiplexed BCD or seven segment lines plus digit select lines. Input controls enable rapid time setting and high currents limit the external component count.

Basic chip BYWMM5311 £11-50 pp 12p.

BYWOOD
ELECTRONICS

181 EBBERS ROAD, HEMEL HEMPSTEAD, HERTS.

RUN YOUR TAPE RECORDER OFF A.C. MAINS

Mains unit supplied complete and ready to plug into your cassette recorder. (State voltage, model and plug required.) P. & P. 15p. Also available for single outputs 6V, 9V, 12V, 18V, £2. P. & P. 15p.

R.C.S. PRODUCTS (RADIO) LTD. (Dept. P.E.), 31 Oliver Road, London, E.17

Build the Mullard C.C.T.V. Camera


Kits are now available with comprehensive construction manual (also available separately at 65p).

SEND 5'X7' S.A.E. FOR DETAILS TO CROFTON ELECTRONICS 15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

NO NEED TO WORRY ABOUT A TRANSMITTING LICENCE

because this GPO approved transmitter/receiver kit does not use R.F. and you can get one easily. Your transmissions will be virtually SECRET since they won't be heard by conventional means. Actually it's TWO KITS IN ONE because you get the printed-circuit boards and components for both the transmitter AND receiver. You're going to find this project REALLY FUN-TO-BUILD with the EASY-TO-FOLLOW instructions. An extremely flexible design with quite an AMAZING RANGE—has obvious applications for SCHOOL PROJECTS, LANGUAGE LABORATORIES, SCOUT CAMPS, etc.

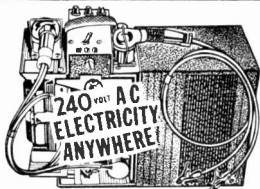GET YOURS! SEND £5.50 NOW (S.A.E. for details)
TO: 'BOFFIN PROJECTS'
DEPT. KE2010
4 CUNLIFFE ROAD
STONELEIGH, EWELL, SURREY



BEST EVER—INTERNATIONAL 230 VOLT A.C. "MAINS" PERFORMANCE from 12 volt car battery. R.C.A. INTERNATIONAL 230 volt A.C. POWER UNIT. Wonderful 230 volt a.c. performance with low battery drain. Marvellous for A.C. FLUORESCENT LIGHTING and hundreds of makes and types of 200/240 volt A.C. and UNIVERSAL A.C./D.C. APPLIANCES. Can be used for re-charging battery by using an ordinary motorist's 4 amp battery charger. Total weight of unit 21 lbs. New improved model only £6.90, plus £1 delivery. C.O.D. with pleasure. 7 days approval against cash.

Dept. PE BROADWAY DISTRIBUTORS, The Generator Centre, House of Time, 273 Broadway, Rossall, Fylde, Lancs.

METER REPAIRS. Ammeters, voltmeters, multi-range meters, etc. Send to METER REPAIRS, 39 Chesholm Road, London, N16 0DS.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London, N10 3HN. 40-page illustrated catalogue 20p post free.

FIBRE OPTICS

FLEXIBLE LIGHT PIPE used to convey light to inaccessible positions for inspection, panel indicators, photo-electric and other applications. **FIBROFLEX** Type 1 glass fibre flexible light conduit 1.14 mm active dia. bundle sheathed in P.V.C. Prices per metre (U.K. post free): 1-4, 70p; 5-9, 55p; 10+, 40p. 25 metres £6 per reel. **CROFON** (Trade mark of Du Pont) Type 1610 plastic flexible light conduit now available. 64 filaments. Active dia. 1.80 mm. Prices per metre: 1-4, £1 20; 5-9, £1; 10+, 80p. 25 metres £16 per reel.

Send S.A.E. for full range of products, price list and literature.

FIBRE OPTIC SUPPLIERS
P.O. BOX 702, LONDON W10 6SL

CAPACITORS FOR DISCHARGE IGNITION

Westock a range of 440V a.c. capacitors specially designed for use in popular ignition systems as the main discharge capacitors. Approved by the designers of "Scorpio" and also suitable for systems described in P.W. and W.W. More reliable than 1000V d.c. (300V a.c.) units in common use. 0-47 0.5µF 1½in x ¾in 35p each; 1µF 2in x ¾in 45p each; 2½µF 2in x 1in 75p each. Post and packing 5p per order.

Y. ATTWOOD, P.O. BOX 8, ALRESFORD, HANTS

ELECTRONIC MUSIC

CIRCUIT ASSEMBLIES for all your music projects, ready-to-use modules ideal for Synthesizers, Sound Effects, Organs, Instrument modifiers.

CHOOSE from over 25 circuits, including our new range of I-C designs for Synthesizer work. **OUR CATALOGUE** contains full technical details, explanations and definitions, suggestions for projects, and discount price details.

OUR PRICES are the lowest in this field and represent unbeatable value for money. Send only 20p for our latest catalogue:

TAYLOR ELECTRONIC MUSIC DEVICES
GREYFRIARS HOUSE • CHESTER

CALCULATOR KIT IDEAL FOR CHRISTMAS

COMPLETE—ONLY £39 + 75p
S.A.E. FOR DETAILS P. & P.

LSI CHIP, 8 DIGIT LED READOUT
PRINTED CIRCUIT BOARD, PLASTIC CASE
POWER SUPPLY, KEYBOARD, ETC.
CONSTANT, FIXED OR FLOATING DECIMAL

ALSO—SINCLAIR EXEC £69.00
RAPIDMAN 800 £32.00
ADVANCE MINI £45.00

BYWOOD
ELECTRONICS

181 EBBERNS RD., HEMEL HEMPSTEAD, HERTS

Versatile

10 in ONE



MINI-LAB

Comprising:

- AC and DC Voltmeter • Audio Generator • Ohm Meter • Resistance Substitution • Capacitance Substitution • DC Ammeter • Battery Supply • RF Signal Generator • RF Field Strength Indicator.

This new, unique instrument combines all you need for testing. Guaranteed, money back if not satisfied.

£11.25 plus 25p p.&p.
Cash with order or write for illustrated data sheet to:

R.S.L. COMPONENTS (Dept. PE2)
Cricklefield Lane, Bishop's Stortford, Herts

P.E. GEMINI. Etched aluminium fascia panels as detailed in latest publication. Printed circuit boards and other items. S.A.E. details. **RAMAR CONSTRUCTOR SERVICES**, 29 Shelbourne Road, Stratford-on-Avon, Warwick.

FOR ALL your Electronic Component requirements. Send for free list to **B.C. ELECTRONIC SUPPLIES**, 7 Regent Road, Huddersfield, HD1 4NR.

RECORD T.V. SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included, £1 post free. **CROWBOROUGH ELECTRONICS (P.E.)**, Bridge Road, Crowborough, Sussex.

EXPERIMENTERS! Hundreds unusual items at **GRIMSBY ELECTRONICS**, Lambert Road, Grimsby, Lines. Catalogue 5p.

12 VOLT FLUORESCENT LIGHTS (as illustrated)



Beat power cuts. Be independent. Ideal for caravans, tents, emergency lighting, etc. Works anywhere where 12v is available. Guaranteed for six months. Ready to use at:

12ins. 8 watt £3.60 post paid
21ins. 13 watt £4.60 post paid

SALOP ELECTRONICS, 23 WYLE COP SHREWSBURY, SHROPSHIRE. Callers welcome. For lists or enquiries, large, s.a.e.

CHRISTMAS GIFTS

PRIVATE — FOR WIVES ONLY

Men are hard to please at Christmas time. Your husband is an electronics man, so why not give him an original gift of top quality that he knows he will appreciate with all your love. We have arranged specially for readers' wives (and mums) a superb GIFT PACK of the popular types of MIP-7-BOARD printed circuit assembly components as described in the October issue.

The Gift Pack includes five different standardised printed circuit boards all ready to use, gold-plated edge connectors, handles, mounting pillars and details on how to make the best use of them in a fully illustrated brochure. He will be able to make several of the published designs on these boards very easily with the layout planning chart included.

The total retail value of these components is £4.24, but because we know that he will be pleased with such an original idea, we are offering all these for Christmas in an attractively styled presentation wallet for only £3.95. Due to heavy demand, we suggest that you send your order before November 30 to guarantee delivery before Christmas (P.O. permitting). We shall mark your parcel PRIVATE if you wish. Write now to


NIP ELECTRONICS, P.O. BOX 11
Beaconsfield Road, St. Albans, Herts.

If you have difficulty in obtaining

PRACTICAL ELECTRONICS

Please place a regular order with your newsagent or send 1 year's subscription (£2.65) to Subscription Department, Practical Electronics, Tower House, Southampton Street, London WC2E 8QX

BUILD A PROJECT 'X' SYNTHESISER

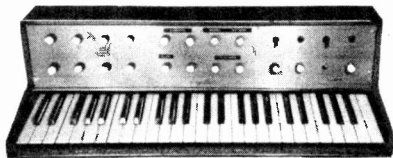

Typical Simplified Synthesiser

MAN-SIZED ROBUST PATCHBOARD

MAKE A "PATCH" AS IF YOU MEAN IT. "K-L-O-N-K" and it's MADE!

No fiddling with fragile patch pins. No cables.

Countless possible combinations giving **FULL RANGE EFFECTS**. Keyboards available for versatile "live" use.

Precision Voltage-controlled Oscillator

VCO-2 gives SINE, TRIANGULAR and SQUARE outputs, and is stable! 1 volt/octave control. Single £22 each. Matched and tracked £25 each.

SHE-1 SAMPLE, HOLD and ENVELOPE module gives sustain and variable env. to VCO signal. £15.

With over 7 years' unblemished reputation in these pages, **Dewtron** continues to lead in new technical developments in electronic sound effects! Ask any of our customers. See our products in the music stores, too. Suppliers of special equipment to a leading group. Our modules are used in professional equipment! Send s.a.e. for synthesiser details or send 15p for full catalogue of our famous musical effects.

D.E.W. LTD.

254 Ringwood Road, FERDOWN, Dorset BH22 9AR

using **Dewtron** (Regd. Trademark)

PROFESSIONAL MODULES

CASH SAVINGS

by buying modules and parts in bulk!

All modules are available separately:

Ring Modulator RM2, £8. Voltage-controlled Oscillator VCO1, £10-50, giving sawtooth and square-wave outputs. Envelope shapers, ES1, self-triggered or ES2 keyboard-triggered, either type £13. White noise type WN1, £7. Voltage-controlled amplifier VCA1, £11. Voltage-controlled selective amplifier (filter for waa-waa, etc.) SA1, £12. Voltage-controlled Phase PH1, £17. Automatic Announcement Fader module for fading of music by microphone announcement, AF1, £9. etc., etc. **ALL MODULES ARE BUILT, TESTED AND SEALED FOR LONG LIFE.** Simply connect coloured wire connections as per easy instructions, build cabinet and wire in controls and patchboard connections! Joystick controls £4-50.

POTENTIOMETERS Lin or Log, 12p; with DP switch, 23p; Dual ganged, 36p; Special offer 5K with DP switch, 15p; **WAVECHANGE SWITCHES**, 22p; Special offer miniature, 4p, 3W 16p. **AMPLIFIERS:** 1 Valve (EL84), £3; ½W Transistorised, £1; 10W Transistorised, £3-75. JB3 Junction Box, £1-20. 5in Plastic Library Cases, 10p. 500µA **TUNING METERS**, 50p. **CARTRIDGES:** Compatible ACOS GP91-3SC, 90p; Stereo GP93-1, £1-15; Ceramic with Diamond Stylus, £1-80. **CAPACITORS:** 100mF 25V, 5p; 220mF 25V, 5p; 400-200-50-16mF 300V, 30p; 0-1 500V D.C. 300V a.c., 3½p.

MINIATURE INDICATOR LAMPS (5 colours), 11p; 6V or 12V Bulbs for above, 4p. **MAINS NEONS** panel mounting (red, green, clear), 15p. 100 **MIXED RESISTORS**, 45p. **ROTARY SWITCHES** (on/off) 250V 2A, 10p. **PLUGS:** Jack Standard, 10p; Screened, 13p; 2-5mm and 3-5mm, 6p; Screened, 8p. **HEADPHONES:** High Impedance (2,000 ohm), 90p; STEREO, 8 ohm. £1-95; STEREO 8/16 ohm £2-10.

MICROPHONES: Lapel 28p; ACOS MIC. 45, 90p; Dual Impedance, Dynamic 600 ohm and 50k, £4-50. **RECORDING TAPE:** 5in LP 900ft, 45p; 5½in L.P. 1,200ft, 60p; 7in L.P. 1,800ft, 81p. **RESISTORS** carbon film 5%, 1½p. **ALUMINIUM CHASSIS** from 6in x 3in to 16in x 10in all 2½in deep. Transistors, Rectifiers, etc.

Large S.A.E. for list No. 4. Special Prices for quantity quoted on request. Add 10p for P. & P. on orders under £5.

M. DZIUBAS

158 Bradshawgate, Bolton, Lancs. BL2 1BA.

FERRANTI

SEMICONDUCTORS... COMPARE OUR PRICES

Transistors	ZTX320 .. 28p	BF561 .. 19p	ZS176 .. 21p
ZTX107 .. 8p	ZTX330 .. 13p	BF596 .. 13p	ZS178 .. 34p
ZTX108 .. 7p	ZTX331 .. 14p	BF597 .. 21p	ZS270 .. 10p
ZTX109 .. 10p	ZTX500 .. 10p	BF598 .. 18p	ZS271 .. 14p
ZTX114 .. 20p	ZTX502 .. 15p		ZS272 .. 16p
ZTX300 .. 10p	ZTX504 .. 15p	DIODES	ZS274 .. 17p
ZTX302 .. 15p	ZTX510 .. 15p	ZS140 .. 22p	ZS276 .. 17p
ZTX304 .. 19p	ZTX530 .. 19p	ZS141 .. 39p	ZS278 .. 33p
ZTX310 .. 8p	ZTX531 .. 20p	ZS142 .. 30p	P.E. PIANO
ZTX311 .. 9p	ZTX550 .. 15p	ZS170 .. 9p	Semiconductor
ZTX312 .. 9p	BF559 .. 13p	ZS171 .. 11p	Special Offer
ZTX313 .. 10p	BF560 .. 18p	ZS172 .. 14p	Send S.A.E.
ZTX314 .. 11p	BF561 .. 18p	ZS174 .. 15p	for Price List

Postage and Packing 10p. Free above £2. S.A.E. for full list

VALENCE ELECTRONICS

134 UNION STREET, ASHTON-U-LYNE, LANCs.

COLOUR T.V.

19" Tube £125 — 25" Tube £160

COMPLETELY OVERHAULED — SIX MONTHS' GUARANTEE
— VARIETY OF MAKES AND MODELS

FABULOUS WINTER VIEWING:

MONOCHROME

UHF — SINGLE STANDARD — PUSH BUTTON TUNER

20" Tube £34-95 — 24" Tube £44-95

Carr. + ins. £2-50. Famous make D/S chassis—Thoroughly overhauled—Fitted with "Square Screen" tube—Transistorised "Push Button" tuner—Fitted in an attractive cabinet, refinished in a choice of teak, walnut, or mahogany veneers (state 1st and 2nd choice)

12 month written guarantee with every set—Leaflet and copy guarantee sent on receipt of your stamped, self addressed envelope

The above models can be seen working in our Langley showroom.

Working and overhauled BBC 2 TV'S (Ferguson 900 and similar sets) £20 carr £2

**SUMIKS (P.E.), 7 HIGH STREET
LANGLEY, WARLEY, WORCS.**

FREE!

Over 150 ways to engineer a better future

HIGHER PAY

A BETTER JOB

SECURITY

find out how in just 2 minutes


That's how long it will take you to fill in the coupon below. Mail it to B.I.E.T. and we'll send you full details and a free book. B.I.E.T. has successfully trained *thousands* of men at home - equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost B.I.E.T. home study course gets results fast - makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn. Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course".—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects".—Student J.A.O. Dublin.
 "My training with B.I.E.T. quickly changed my earning capacity and, in the next few years, my earnings increased fourfold".—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

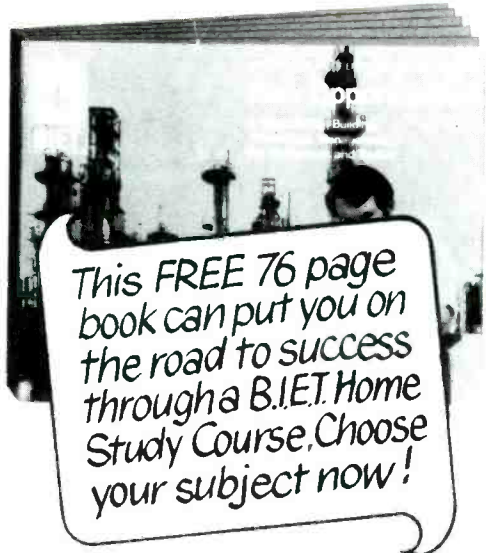These letters - and there are many more on file at Aldermaston Court - speak of the rewards that come to the man who has given himself the specialised know-how employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to B.I.E.T. Dept. B38, Aldermaston Court, Reading RG7 4PF



This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!

- | | | |
|--|---|--|
| <p>MECHANICAL
 A.M.S.E. (Mech)
 Boiler Inspection & Operation
 C & G Eng. Crafts
 C & G Fabrication
 Diesel Eng.
 Eng. Inspection
 Eng. Metallurgy
 Inst. Eng. & Tech.
 Inst. Motor Ind.
 Maintenance Eng.
 Mechanical Eng.
 Sheet Metal Work
 Welding</p> | <p>Man. Prod.—cont.
 Salesmanship
 Storekeeping
 Work Study
 Works Management
 DRAUGHTSMANSHIP
 A.M.I.E.D.
 Design of Elec. Machines
 Die & Press Tool Design
 Electrical Draughtsmanship
 Gen. Draughtsmanship
 Jig & Tool Design
 Technical Drawing</p> | <p>Constructional-cont.
 Building Drawing
 Building Foreman
 Carpentry & Join.
 Civil & Municipal Engineering
 Construction
 Engineering
 Construction Surveyors
 Institute Clerk of Works
 Council Eng.
 Geology
 Health Eng.
 Heat & Vent.
 Hydraulics
 Inst. of Builders
 Inst. Clerk of Works
 Inst. Works & Highway Supers.
 Painting & Dec.
 Public Hygiene
 Road Engineering
 Structural Eng.
 Surveying</p> |
| <p>ELECTRICAL & ELECTRONIC
 A.M.S.E. (Elec.)
 C & G Elec. Eng.
 C & G Elec. Inst.
 C & G Elec. Tech.
 Computer Elect.
 Elec. Maths
 Elec. Science
 Electronic Eng.
 Electrical Eng.
 Install. & Wiring
 Meters & Measuring Instruments</p> | <p>RADIO & TELE-COMMUNICATIONS
 Colour TV
 C & G Radio/TV/Electronics
 C & G Telecomm. Tech.
 Prac. Radio & Elec. (with kit)
 Radio Amateurs Exam.
 Radio Servicing & Repairs
 Radio & TV Eng.
 Transistor Course
 TV Main. & Serv.</p> | <p>GENERAL
 Agricultural Eng.
 Council of Eng. Inst.
 Farm Science
 General Education
 Gen. Plastics
 Pract. Maths
 Pract. Slide Rule
 Pure & Applied Maths
 Refrigeration
 Rubber Technology
 Sales Engineers
 Tech. Report Writing
 Timber Trade University Ent.</p> |
| <p>MANAGEMENT & PRODUCTION
 Automatic Control
 Computer Prog.
 Electronic Data Processing
 Estimating
 Foremanship
 Inst. Cost & Works
 Accountants
 Inst. Marketing
 Management
 Metrication
 Motor Trade Man.
 Network Planning
 Numerical Control
 Operational Research
 Personnel Man.
 Planning Eng.
 Production Eng.
 Quality Control</p> | <p>AUTO & AERO
 Aero Eng.
 A.M.I.M.I.
 A.R.B. Cert.
 Auto Engineering
 Auto Repair
 C & G Auto. Eng.
 Garage Management
 MAA/IMI Diploma
 Motor Vehicle Mechanics</p> | <p>G.C.E.
 58 'O' & 'A' LEVELS SUBJECTS
 Over 10,000 group passes</p> |

Coaching for many major exams, including HNC, ONC, C & G, etc.

POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept. B38, Aldermaston Court, Reading RG7 4PF B38

NAME _____
 Block Capitals Please
 ADDRESS _____

SUBJECT OF INTEREST _____ AGE _____
 Accredited by the Council for the Accreditation of Correspondence Colleges.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Published approximately on the 15th of each month by IPC Magazines Ltd, Fleetway House, Farringdon Street, London, E.C.4. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Gotch (A/S) Ltd. South Africa - Central News Agency Ltd. Rhodesia and Zambia - Kingstons Ltd. East Africa - Stationery and Office Supplies Ltd. subscription (late including postage): For one year to any part of the world £2.95 (21.5.0.). Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

U.K.'s LARGEST ELECTRONICS CENTRES! HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.



NOW OPEN!

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381
354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736
309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963
303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1BW
ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

BUILD THE TEXAN


20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

★ **FREE TEAK CASE** with complete kits!

FEATURES: New slim design with 6 ICs, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardners low field slim line transformer. Fibre glass PC panel. Complete chassis work.

HIGH QUALITY & STABILITY ARE PREDOMINATE FEATURES—DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

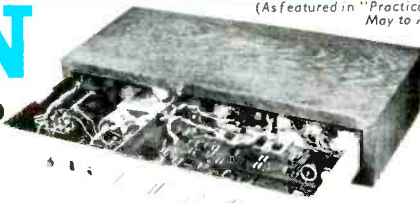FACILITIES: On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector: Mag. P.U., Radio Tuner, Aux. Can beatered for Mic, Tape, Tape head etc. (Parts list Ref. 20 on request). Constructional Details Ref. No. 21. 30p.



(As featured in "Practical Wireless" May to August 1972)

SPECIAL KIT PRICE
£28.50

P. & P. 45p

SLIM DESIGN WITH SILVER TRIM

Overall chassis size 14 1/2 in. x 8 in. x 2 in. high

COMPLETE WITH FREE TEAK CABINET

Designer approved kits distributed by Henry's!

LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2 in x 8 in and Ceramic Magnet

TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.

TYPE 150TC Twin cone version £3.75. Post 22p.

TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.

TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



POLISHED CABINETS 150, 150TC, 450 £4.60. Post 30p.
ASSEMBLED IN POLISHED CABINETS (8 OHM)
SERIES 6 (Assembled 150TC) per pair £16.50. Post 70p.
SERIES 8 (Assembled 450) per pair £18.95. Post 70p.

ML3 MW LW TUNER TO BUILD

Uses Mullard Module. Slow motion tuning. Built-in battery. Ferrite aerial. Overall size 7 in x 2 1/2 in x 3 1/2 in. TOTAL COST TO BUILD £4.85. Post 15p.



All parts sold separately—Leaflet No. 6.

"BANDSPREAD" PORTABLE TO BUILD


Printed circuit all transistor design using Mullard RF/IF Module. Medium and Long Wave Bands plus Medium Wave Bandspread for extra selectivity. 600mW push-pull output, fibre glass PVC covered cabinet, car aerial. Attractive appearance and performance. TOTAL COST TO BUILD £7.98, p.p. 32p (Batt. 22p). All parts sold separately—Leaflet No. 2.



TEST EQUIPMENT

Just a selection

- SE250B Pocket Pencil Signal Injector, £1.90
- SE500 Pocket Pencil Signal Tracer, £1.50
- THL33D Robust 2 K Volt, £4.55; with case £4.95
- TE15 Grid Dip Meter 440 KHz—280 MHz, £13.45
- 500 30 K/Volt Multimeter, £9.25; with leather case, £10.50
- 200H20 K/Volt Multimeter, £4.20; with case £4.95
- AF105 50K/V Multimeter, £8.50; with case, £9.50
- U4341 AC/DC Multimeter with transistor tester with steel case, £10.50
- TE20D RF Generator 120KHz—500MHz, £15.95. Carr. 35p
- TE22D Audio Generator 20Hz—200KHz, £17.50. Carr. 35p
- CI-5 3 in Pulse Scope 10Hz—10MHz, £39.00. Carr. 50p
- TE65 Valve Voltmeter 28 ranges, £17.50. Carr. 40p

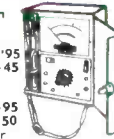

ALL NONMBRE MODELS IN STOCK

BUILD THIS VHF FM TUNER

5 TRANSISTORS 300kc/s BANDWIDTH PRINTED CIRCUIT, HIGH FIDELITY REPRODUCTION. MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7. TOTAL £6.97, p.p. 20p.



Decoder Kit £5.97. Tuning meter unit £1.75. Mains unit (optional) Model PS900 £2.47. Carr. 20p. Mains unit for Tuner and Decoder P5.6/12 £3.25. Post 20p.

PA-DISCO-LIGHTING

UK's Largest Range—Write phone or call in. Details and demonstrations on request.

- DJ30L 3 Channel sound to light unit, 3kW, £29.75
- DJ40L 3 Channel Mic (Built-in) to light, 3kW, £38.75
- DJ70S 70 watt Disco amp/mixer, £49.95
- DISCOAMP 100 watt Disco amp/mixer, £66.50
- DJ105S 30 watt Disco amp/mixer, £32.75
- Anti-Feedback Quality Mic, £11.50
- DJ500 50 watt PA amplifier, £44.00
- Group 300 150 watt rms Group Valve amplifier, £86.00




Everything for PA—Disco—Lighting. FREE Stock List Ref. No. 1B.

CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics—plus data, circuits and information. 10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE 55p (40p FOR CALLERS)
PLUS! FIVE 10p VOUCHERS

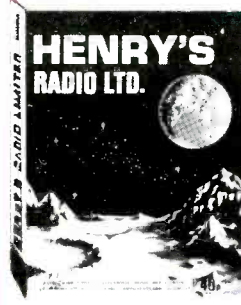Send to this address—Henry's Radio Ltd. (Dept. PE), Albermarle Way, London, E.C.1—for catalogue by post only. All other mail and callers to "303", see above.



SINCLAIR PROJECT 60 MODULES

—SAVE POUNDS

- Z30 £3.57 Z50 £4.37
- STEREO 60 £7.97 PZ5 £3.97
- PZ6 £6.37 PZ8 £4.77.



Transformer for PZ8 £2.95.
Active Filter Unit £4.45.
Stereo FM Tuner £16.95.
IC12 £1.80 Q16's £15 pair.
Post, etc. 20p per item.

PACKAGE DEALS Post 25p
2 x Z30, Stereo 60, PZ5 £15.95
2 x Z30, Stereo 60, PZ6 £18.00
2 x Z50, Stereo 60, PZ8 £20.25
Transformer for PZ8 £2.95
PROJECT 605 KIT £19.95

RECORD DECKS

CHASSIS (Post 50p)

- SP25/3, £10.25 HT70, £14.50
- MP60, £9.95 MP610, £12.95
- AP76, £17.95 GL75, £28.50
- PLINTH/COVERS (State Model)
- SP25/MP60/610 £3.30 (Post 40p)
- AP76 £4.50 (Post 40p)
- CART/PLINTH/COVER (Post 70p)
- (HL) MP60/G800H/PC £18.50
- MP610/SC5MD/TPD2/PC £19.95
- AP76/M7565M/PC £35.00
- AP96/M7565M/PC £39.95
- (HL) AP76/G800H/PC £28.25
- (HL) SP25/G800H/PC £18.95
- HT70/G800/TPD1/PC £24.50
- (HL) 2025/9TAHCD/PC £13.95
- MP60/SC5MD/PC £17.25
- (HL) GL75/G800/PC £41.95
- (HL) GL75/G800/PC £38.95

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. ideal remote switching and signalling. Complete with data and circuits. PRICE PER PAIR £5.90. Post 10p.

MARRIOT TAP HEADS

- 4 TRACK MONO or 2 TRACK STEREO
- "17" High Impedance £2.00
- "18" Med. Impedance £2.00
- "36" Med.-Low Imp. £3.50
- Erase Heads for above 75p
- "63" 2 track mono — High Impedance £1.75
- "43" Erase Head for above 75p

POWER INTEGRATED CIRCUITS

Plessey SL403D—3 watt with 8-page data, layouts and circuits £1.50. P.C. Boar 60p; Heat Sink 14p. Sinclair IC12—6 watt with data and circuits £1.80. TH9013P—20 watt Power Amp Module £4.57. TH9014P-IC Pre-amplifier £1.50. Data/Circuits (No. 42) for above 10p.

7 SEG & NIXIE TUBES

(Post 15p per 1 to 6)
XN3, XN13, GN6 0-9 side view with data, 85p.
GNP-7, GNP-8 0-9 side view with decimal points and data, 95p.
3015F 7 seg. £2 each, £7 per 4 with data.
12 and 24 hour clock circuits. Ref. No. 31 15p.

MINIATURE AMPLIFIER

5 transistor, 300mW o/p. Fitted volume and sensitivity control 9 volt operated. £1.75 each, p.p. 15p.

QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs. 5kΩ, 10kΩ, 25kΩ, 100kΩ, 250kΩ, 500kΩ, 1 meg. Log and Lin. 40p each, 10kΩ, 25kΩ, 50kΩ, 100kΩ, 250kΩ. Log and Lin. ganged. 60p each.

HI-FI AND TAPE EQUIPMENT

Acknowledged as U.K.'s Largest Stockist with Lowest Prices Plus 12 Months Guarantee. Write or call for FREE 16 page lists (Ref. No. 17)



MORE OF EVERYTHING ALWAYS AT HENRY'S

All the parts you need plus Data and Circuits. Get a Catalogue—it's all in there! Prices subject to change without notice. E. & O.E.

TRANSISTORS — IC's — SCR's — RECTIFIERS — TRIACS, etc. LATEST BROCHURE Ref. No. 36 on request or see our earlier page.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday.

H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H