

PRACTICAL

ELECTRONICS

JANUARY 1975

25p

FOR SCINTILLATING DECORATION

MAKE
THIS
**LIGHT
PIPE**

FOR SCINTILLATING SOUND
build the



PE ORION . . .
HI-FI STEREO AMPLIFIER

NEW EDU-KIT MAJOR

COMPLETELY SOLDERLESS ELECTRONIC CONSTRUCTION KIT
BUILD THESE PROJECTS WITHOUT SOLDERING IRON OR SOLDER

TOTAL BUILDING COSTS

£7-23 P.P. & INS. 44p
(Overseas P.P. £1-85p)
(+8% VAT 57p)

- 4 Transistor Earpiece Radio
- Signal Tracer
- Signal Injector
- Transistor Tester NPN - PNP
- 4 Transistor Push Pull Amplifier
- 5 Transistor Push Pull Amplifier
- 7 Transistor Loud-speaker Radio MW/LW.
- 5 Transistor Short Wave Radio
- Electronic Metronome
- Electronic Noise Generator
- Batteryless Crystal Radio
- 2 Transistor Regenerative Radio
- 3 Transistor Regenerative Radio
- Audible Continuity Tester
- Sensitive Pre-Amplifier

Components include:

- 24 Resistors ● 21 Capacitors ● 10 Transistors ● 31 Loudspeaker ● Earpiece ● Mica Baseboard
- 3 12-way Connectors ● 2 Volume Controls ● 2 Slider Switches ● 1 Tuning Condenser ● 3 Knobs
- Ready Wound MW/LW/SW Coils ● Ferrite Rod ● 6½ yards of wire ● 1 yard of sleeving, etc.
- Parts price list and plans 50p (free with parts)

NEW ROAMER NINE

WITH V.H.F. INCLUDING AIRCRAFT

Nine Transistors, 9 Tunable wavebands as Roamer Ten. Built in ferrite rod aerial for MW/LW. Retractable chrome plated telescopic aerial for VHF and SW. Push Pull output using 600 mW transistors. 9 Transistors and 3 diodes, tuning condenser with VHF section, separate coil for aircraft, moving coil loudspeaker, volume ON/OFF and wavechange controls. Attractive all white case with red grille and carrying strap. Size 9½in x 7in x 2½in approx. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£6-95** P.P. & INS. 44p
(+8% VAT 55p) (OVERSEAS P. & P. £1-85)

POCKET FIVE


NOW WITH 3" LOUDSPEAKER

3 Tunable wavebands, MW/LW and Trawler Band. 7 stages, 5 transistors and 2 diodes, supersensitive ferrite rod aerial, attractive black and gold case. Size 5½in x 1½in x 3½in approx. Plans and parts price list 15p (FREE with parts).

Total Building Costs

£2-50

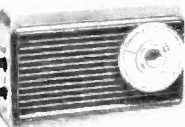(+8% VAT 20p) P.P. & Ins. 26p
(Overseas P.P. £1-25)



Total Building Costs **£2-75** P.P. & Ins. 26p
(+8% VAT 21p) (Overseas P. & P. £1-25)

TRANSONA FIVE NOW WITH 3" LOUDSPEAKER

Wavebands, transistors and speaker as Pocket Five. Larger Case with Red Speaker Grille and Tuning Dial. Plans and parts price list 15p (FREE with parts).

TRANS EIGHT 8 TRANSISTORS AND 3 DIODES

6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, SW3 AND TRAWLER BAND. Sensitive ferrite rod aerial for MW and LW. Telescopic aerial for short waves. 3in speaker. 8 improved type transistors plus 3 diodes. Attractive case in black with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Push-pull output. Battery economiser switch for extended battery life. Ample power to drive a larger speaker. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS

£4-48 P.P. & INS. 33p
(OVERSEAS P. & P. £1-25)
(+8% VAT 36p)

ROAMER SIX

CASE AND LOOKS AS TRANS EIGHT 6 TUNABLE WAVEBANDS, MW, LW, SW1, SW2, TRAWLER BAND PLUS AN EXTRA MW BAND FOR EASIER TUNING OF LUXEMBOURG, ETC. Sensitive ferrite rod aerial and telescopic aerial for short waves. 3in speaker. 8 stages—6 transistors and 2 diodes, etc. Attractive black case with red grille, dial and black knobs with polished metal inserts. Size 9in x 5½in x 2½in approx. Plans and parts price list 25p (FREE with parts).

TOTAL BUILDING COSTS

£3-98 P.P. & IN. 31p
(OVERSEAS P. & P. £1-85)
(+8% VAT 32p)

NEW EVERYDAY SERIES

Build this exciting New series of designs

EV5 5 Transistors and 2 diodes, MW/LW. Powered by 4½ volt Battery. Ferrite rod aerial, tuning condenser, volume control, and now with 3" loudspeaker. Attractive case with red speaker grille. Size 9in x 5½in x 2½in approx. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£2-95**

(+8% VAT 23p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)

EV6 Case and looks as above.

6 Transistors and 3 diodes. Powered by 9 volt Battery. Ferrite rod aerial, 3" loudspeaker, etc. MW/LW coverage. Push Pull Output. Parts price list and plans 15p (FREE with parts).

TOTAL BUILDING COSTS **£3-60**

(+8% VAT 29p)

P.P. & INS. 30p
(OVERSEAS P. & P. £1-25)

EV7 Case and looks as above.

7 transistors and 3 diodes. Six wavebands, MW/LW, Trawler Band, SW1, SW2, SW3, powered by 9 volt Battery Push Pull Output. Telescopic Aerial for Short Waves. 3" Loudspeaker. Parts price list and plans 20p. Free with parts.

TOTAL BUILDING COSTS **£4-08**

(+8% VAT 32p)

P.P. & INS. 31p
(OVERSEAS P. & P. £1-85p)

ROAMER EIGHT Mk. I

NOW WITH VARIABLE TONE CONTROL

7 TUNABLE WAVEBANDS:

MW1, MW2, LW, SW1, SW2, SW3 AND TRAWLER BAND. Built-in ferrite rod aerial for MW and LW. Chrome plated telescopic aerial can be angled and rotated for peak short-wave listening. Push-pull output using 600mW transistors. Car aerial and tape record sockets. Selectivity switch. 8 transistors plus 3 diodes. Latest 4" 2 watt Ferrite Rod Magnoloudspeaker. Air spaced ganged tuning condenser. Volume/on/off, tuning, wave change and tone controls. Attractive case in rich chestnut shade with gold blocking. Size 9in x 7in x 4in approx. Easy to follow instructions and diagrams. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£6-98**

(+8% VAT 56p)

P.P. & INS. 47p
(OVERSEAS P. & P. £1-85)

ROAMER TEN WITH VHF INCLUDING AIRCRAFT

10 TRANSISTORS. 9 TUNABLE WAVEBANDS, MW1, MW2, LW, SW1, SW2, SW3, TRAWLER BAND, VHF AND LOCAL STATIONS. ALSO AIRCRAFT BAND

Latest 4" 2 watt Ferrite Rod Magnoloudspeaker. Built-in ferrite rod aerial for MW/LW. Chrome plated 7 section telescopic aerial, can be angled and rotated for peak short wave and VHF listening. Push-pull output using 600mW transistors. Car Aerial and tape record sockets. 10 transistors plus 3 diodes. Ganged tuning condenser with VHF section. Separate coil for Aircraft Band. Volume/on/off, wave change and tone controls. Attractive case in black with silver blocking. Size 9in x 7in x 4in. Easy to follow instructions and diagrams. Parts price list and plans 30p (FREE with parts).

TOTAL BUILDING COSTS **£8-50**

(+8% VAT 68p)

P.P. & INS. 52p
(OVERSEAS P. & P. £1-85)

EDU-KIT

Build Radios Amplifiers, etc., from easy stage, diagrams.



Five units including master unit to construct.

Components include: Tuning Condenser; 2 Volume Controls; 2 Slider Switches; Fine tone 3" moving coil Speaker; Terminal Strip; Ferrite Rod Aerial; Battery Clips; 4 Tag Boards; 10 Transistors; 4 Diodes; Resistors; Capacitors; Three ½in Knobs. Units once constructed are detachable from Master Unit, enabling them to be stored for future use. Ideal for Schools, Educational Authorities and all those interested in radio construction. Parts price list and plans 25p (FREE with parts).

TOTAL BUILDING COSTS **£5-50**

(+8% VAT 44p)

P.P. & INS. 33p
(OVERSEAS P. & P. £1-85)

RADIO EXCHANGE LTD

*Callers side entrance "Lavelle's" shop
*Open 10-1, 2.30-4.30, Mon.-Fri. 9-12 Sat.

To RADIO EXCHANGE CO., 61a HIGH STREET, BEDFORD MK40 1SA
Tel. 0234 52867 Reg. No. 788372

I enclose £ _____ for

Name _____

Address _____

PRACTICAL ELECTRONICS

VOLUME 11 No. 1 JANUARY 1975

CONSTRUCTIONAL PROJECTS

- LIGHT PIPE** *by R. Gwynn* 28
A novel flexible lighting effect for the home, discotheque, or shop
- DIGITAL LEAF** *by J. S. Haggis* 32
Grow better greenhouse plants with this automatic moisture control circuit
- P.E. ORION—1** *by D. S. Gibbs & I. M. Shaw* 46
A high quality low cost 20 + 20W stereo amplifier
- P.E. MINISONIC—3** *by G. D. Shaw* 58
Details of the keyboard controller, ring modulator, noise generator, h.f. detector and oscillator, and power amplifiers

GENERAL FEATURES

- SURFACE ACOUSTIC WAVES** *by T. S. Fisher* 41
Is this the technique of the future?
- INGENUITY UNLIMITED** 66
Sound-to-Light Modulator—Serial Connection Multivibrator

NEWS AND COMMENT

- EDITORIAL**—The Triumphs of Radio Astronomy 27
- SPACEWATCH** *by Frank W. Hyde* 37
Mercury Again—More From Skylab
- NOBEL PRIZE FOR CAMBRIDGE RADIO ASTRONOMERS** *by Frank W. Hyde* 38
- ELECTROMUSE** *by Malcolm Pointon* 53
Electronics and Music
- THE NEXT DECADE** 54
Final selection of readers' predictions for the future
- INDUSTRY NOTEBOOK** *by Nexus* 69
What's happening inside industry
- MARKET PLACE** 70
Constructional Aid, Tapes, and News Briefs
- BOOK REVIEWS** 73
Selected new books we have received
- NEWS BRIEFS** 73
Audio Fair—Link-Up—Price Cut
- READOUT** 74
A selection of readers' letters

Our February issue will be published on Friday, January 10, 1975

© IPC Magazines Limited 1975. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press. Publisher's Subscription Rate including postage for one year, inland £3.25, Overseas £4.10. International Giro facilities Account No. 5122007. Please state reason for payment, "message to payee".

DISCOUNTS UPTO 60%

FANTASTIC OFFER
GARRARD SP25 Mk. IV
PLINTH AND COVER
 Garrard SP25 Mk IV
 deck Goldring G800
 Cartridge Task finished
 Plinth Cover (non hinged) All
 Leads
GLOBAL'S PRICE £19.95
 Carr & Ins £1.93

TURNTABLES
 Please add £1.05 for P. & P. & Ins.
 Garrard SP25 Mk IV Chassis £12.95
 Garrard 86SB P C Cart (Mod) £47.50
 Garrard 86SB Chassis £22.40
 Garrard 401 Chassis £33.25
 Goldring 101 Mk II P C G800 £23.70
 Goldring GL75 P C G800 £39.95
 Goldring GL78 P C G800 £44.40
 Goldring GL85 P C £66.95
 Pioneer PL 12D P.O.A.
 Sansul SR 212 P.O.A.
 Thorens TD125 Mk II £73.75

Thorens TD125AB Mk. II £111.95
 Thorens TD160 ABC £64.65
 Thorens TD165 ABC £53.95
 Transcripator Saturn with Vestigal Arm £63.95

AMPLIFIERS
 Please add £1.05 for P. & P. & Ins.
 Amstrad Inlegra 4000 Mk II £31.95
 Amstrad IC2000 Mk II £18.50
 Amstrad 8000 Mk III £43.10
 Eagle AA4 £51.25
 Eagle AA6 £28.95
 Metro-Sound ST20E Mk II £34.25
 Metro-Sound ST40 £46.75
 Sansul AU101 P.O.A.
 Sinclair 2000 £29.95
 Sinclair 4000 £44.95
 Teleton SAQ206B £20.50
 Teleton SAQ307D £27.20

COMBINATION UNITS
 Please add £1.10 for P. & P. & Ins.
 Goodmans Compact 80 (Teak) £131.15
 Goodmans Compact 90 £189.99
 Goodmans Compact 1-10 (Teak) £191.00

TUNERS
 Please add £1.05 for P. & P. & Ins.
 Amstrad MLX 3000 £26.25
 Eagle AA8 £47.50
 Eagle TST 152 £32.95
 Metro-Sound FMS 20 Mk II £33.35
 Teleton T300 £35.35
 Teleton ST202 £38.80
 Sinclair 2000 £29.95
 Sinclair 4000 £37.45

TUNER/AMPLIFIERS
 Please add £1.21 for P. & P. & Ins.
 Amstrad 5000 £56.95
 Goodmans Module 90 £92.90
 Goodmans 1-10 Module £110.50
 Goodmans 120 £113.95

CARTRIDGES
 Please add 12p for P. & P. & Ins.
 Goldring G800H £3.87
 Goldring G800E £6.20
 Goldring G800 £3.40
 Shure V15 Type 3 £28.40
 Shure M75EJ Type 2 £7.90
 Shure 91ED £9.10
 Shure 91ED £8.20
 Shure M3D £3.10
 Sonotone 9 TACHD £11.30

SPEAKERS
 Add £1.62 P. & P. & Ins. per Pair
 Amstrad 1500 £25.65
 Amstrad 2500 £29.95
 Celestion County £48.25
 Celestion Ditton 10 Mk II £42.95
 Celestion Ditton 15 £67.50
 Celestion Ditton 25 £132.50
 Celestion Ditton 44 £108.95

Celestion Ditton 66 £205.75
 Celestion Hadleigh £39.25
 Goodmans Dimension 8 £127.95
 Goodmans Havant SL £44.95
 Goodmans Magisters £107.75
 Goodmans Magnum K2 SL £85.95
 Goodmans Minster £36.00
 Goodmans Mezo 3SL £87.35
 Marsden Hall XL10/C N/P £31.95
 Marsden Hall XL15/C N/P £38.25
 Marsden Hall XL20/C N/P £44.95
 Marsden Hall XL30/C N/P £87.50
 Wharfedale Denton 2 £32.25
 Wharfedale Dove Dale £85.75
 Wharfedale Glendale £38.75

AMSTRAD IC2000 Mk. II
STEREO SYSTEM
 Amstrad IC2000 Mk. II with increased power
 25 + 25W amplifier. Complete with a pair
 of Amstrad Acousta 2500 speakers
 Garrard SP25 Mk IV deck G800 Cart.
 Plinth Cover (non hinged) All leads
GLOBAL'S PRICE £80.75
 Carr & Ins £3.30

STEREO HEADPHONES
 Please add 42p for P. & P. & Ins.
 Koss ESP 6 £48.85
 Koss ESP 9 £65.75
 Koss K7/11 Red Devil £10.89
 Koss 6 £11.70
 Koss K6/LC £13.25
 Koss KD 727E £14.90
 Koss 747 £19.75
 Koss HW1 1A N/P £20.85
 Koss HW11 C/A N/P £24.80
 Koss PRO 5/LC £28.15
 Koss K7/11 Black £9.90
 Sennheiser HD414 £10.75
 Sennheiser HD424 £15.55

GLOBAL AUDIO

Please Note Every effort is made to ensure prices listed are correct at time of going to press but are subject to alteration without prior notice - 1401s

FULL 12 MONTH AFTER SALES SERVICE
 We give a FULL 12 MONTH GUARANTEE on all products purchased at any branch. parts and labour absolutely FREE

BIRMINGHAM
 Iwolt Shopping Centre
 1536 Coventry Road, Yardley
 Tel. 021-706 9949

ESSEX
 4 High View Parade
 Redbridge Lane East
 Woodford Avenue, Ilford
 Tel. 01-550 1086

LONDON
 328 Edgware Road, W2
 Tel. 01 262 3847
 246 Pentonville Road, N1
 Tel. 01-837 5535

120 Notting Hill Gate, W11
 Tel. 01-229 1437
 50 Stamford Hill, N16
 Tel. 01-806 4699

PORTSMOUTH
 12 London Road, North End
 Tel. 0705 68321

READING
 46 Market Place
 Tel. 0734 595331

WATFORD
 105 St Albans Rd. Tel. 39832

H.P. FACILITIES
 AVAILABLE FOR
 PERSONAL CALLERS ONLY
MAIL ORDERS
 10 174 PENTONVILLE
 ROAD, LONDON, N1
 Order with confidence
 Send Postal Order,
 Cheque, Money Order,
 Bank Draft, Giro or
 Cash by Reg. Mail.

NO HIDDEN PRICES AT GLOBAL AUDIO - ALL OUR PRICES ARE SHOWN WITH VAT INCLUDED

PERSONAL CALLERS VERY WELCOME!
 COMPARE OUR PRICES WITH ANY IN THE '800s'
 OPEN MONDAY TO SATURDAY 9.30 am - 6 pm
 LATE NIGHT FRIDAY OPEN UNTIL 7 pm

PLEASE NOTE All Cheques, Money Orders, Postal Orders, Bank Draft, or Giro to be made payable to MAUTOMFAD LTD

★ **ELECTRONIC PIANO KIT**

★ **SYNTHESISER KIT**

★ **ELECTRONIC ORGAN KITS**



There are five superb Electronic Organ kits specially designed for the D-I-Y enthusiast. With the extreme flexibility allowed in design, you can build an organ to your requirements, which will compare with an organ commercially built costing double the price.

★ Portable organ with 4 octave keyboard, £145.29. ★ Console organ with 5 octave keyboard, £269.90. ★ Console organ with 2 x 4 octave keyboards and 13 note pedal board, £470.65. ★ Console organ with 2 x 5 octave keyboards and 32 note pedal board, £665. ★ Console organ with 3 x 5 octave keyboards and 32 note pedal board, £770. ★ W/W Sound Synthesiser Kit, £130. ★ W/W Touch Sensitive Electronic Piano, £100.

All components can be purchased separately, i.e., semiconductor devices, M.O.S. master oscillators, coils, keyboards, pedal boards, stop tabs, draw bars, key-contacts, etc.

Send 50p for catalogue which includes 5 x 10p vouchers or send your own parts list, enclosing S.A.E. for quotation.

ELVINS
ELECTRONIC MUSICAL INSTRUMENTS
 Designers and component suppliers to the musical industry.
 12 Brett Road, Hackney, London, E8 1JP. Tel. 01-986 8455.



Phoenix Electronics
 (Portsmouth) Ltd.
 139-141 Havant Road,
 Drayton, Portsmouth, Hants
 PO6 2AA

Full member of AFDEC—the industry's association of franchised electronic component distributors.

Our prices include VAT at the current rate—and carriage on all goods is free.

Send for our catalogue and price list—we'll mail that to you free, too.

THIS MONTH'S BARGAIN OFFER!
 Small signal silicon transistor kit—5 each BC108, BC178, BC205, BC208, BFY51, ME1120, ME8003, 2N2924, 2N2926, 2N3394, ACY28.—Catalogue value £7.
Bargain pack PEP2A, £4.90.

Please send your catalogue—free!

Name

Address

..... PEP/1A

NOW AVAILABLE IN THE U.K!

CHINAGLIA




PROFESSIONAL QUALITY TEST EQUIPMENT FROM ONE OF ITALY'S LEADING MAKERS

One example from the big range of sophisticated instruments

CORTINA MINOR

33 RANGE POCKET MULTIMETER

- SENSITIVITY 20,000Ω/VOLT (D.C.), 4,000Ω/VOLT (A.C.)
- ROBUST DIODE PROTECTED PRECISION MOVEMENT.
- 33 RANGES D.C. VOLTS 0-100mV, 1-5V, 5V, 15V, 50V, 150V, 500V, 1,500V. D.C. CURRENT 0-50μA, 5mA, 50mA, 500mA, 2.5A. A.C. VOLTS, 0-7.5V, 25V, 75V, 250V, 750V, 1,500V, A.C. CURRENT 0-25mA, 250mA, 2.5A, 12.5A. dB RANGES, -10 to +69. AF VOLTS RANGES 0-1,500V. RESISTANCE RANGES 10kΩ, 10MΩ F.S.D. CAPACITANCE RANGES 100μF IF F.S.D.
- ACCURACY—RESISTANCE, D.C. VOLTAGE AND CURRENT, 2.5%. A.C. VOLTAGE AND CURRENT 3.5%.
- RESISTANCE RANGES POWERED BY INTERNAL BATTERIES.
- COMPACT SIZE: 150 x 85 x 40mm, 350gr.
- CLEARLY CALIBRATED DIAL WITH ANTI-PARALLAX MIRROR.
- PROFESSIONAL QUALITY COMPONENTS EMPLOYED THROUGHOUT.
- FULLY GUARANTEED FOR 12 MONTHS.
- AFTER SALES SERVICE AND SPARES FACILITIES.
- SUPPLIED WITH ADDITIONAL SHOCKPROOF PLASTICS CARRYING CASE, TWO HIGHLY INSULATED TEST LEADS AND INSTRUCTION BOOKLET.
- SPECIAL 30KV PROBE FOR D.C. MEASUREMENT AVAILABLE AS AN OPTIONAL EXTRA.

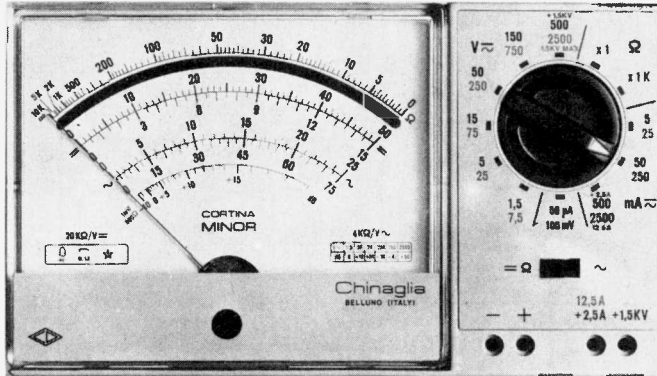

METER PRICE £15.40 (p & p 80p) PROBE £8.80 inclusive of V.A.T.

for further information on the "Cortina Minor" or other instruments from the exciting Chinaglia range write or telephone :-

CHINAGLIA (U.K.) LIMITED


19 Mulberry Walk, London S.W.3.

Telephone 01-352 1897

TRADE ENQUIRIES WELCOMED

INTER-LOCKING PLASTIC STORAGE DRAWERS

NEAT!
HANDY!
TIDY!
DISCOUNT PRICES

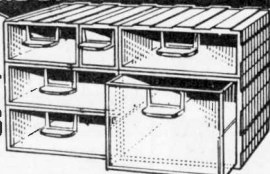

5 SIZES ALL INTERLOCK

Newest, neatest system ever devised for storing small parts and components: resistors, capacitors, transistors, etc. Rigid plastic units interlock together in vertical and horizontal combinations. Transparent plastic drawers have label slots. 1D and 2D have space dividers. Build up any size cabinet for wall, bench or table top.

BUY AT TRADE PRICES!

SINGLE UNITS (1D) (5ins x 2½ins x 2½ins) £2 DOZEN.

DOUBLE UNITS (2D) (5ins x 4½ins x 2½ins) £3.50 DOZEN.

TREBLE (3D) £3.50 for 8.

DOUBLE TREBLE 2 drawers, in one outer case (6D2), £4.90 for 8.

EXTRA LARGE SIZE (6DI) £4.50 for 8.

PLUS QUANTITY DISCOUNTS!

Orders £15 and over DEDUCT 5% in the £
Orders £30 and over DEDUCT 7½% in the £

PACKING/POSTAGE/CARRIAGE: Add 40p to all orders under £10. Orders £10 and over, packing/postage/carriage free.

QUOTATIONS FOR LARGER QUANTITIES
Please add 8% V.A.T. to total remittance

FLAIRLINE (Dept. PE1), 124 Crickwood
SUPPLIES (Broadway, London, N.W.2
Tel. 01-450 4844

OSMABET LTD.

We make transformers amongst other things.

AUTO TRANSFORMERS, 110/200/220/240V.
30W, £1.70; 50W, £2.40; 75W, £2.85; 100W, £3.80;
500W, £10.80; 750W, £14.25; 1000W, £18.00, etc.

LOW VOLTAGE TRANSFORMERS
Prim. 200/240V a.c. 6-3V 1.5A, £1.20; 3A, £1.50;
6A, £2.55; 12V 1.5A, £1.50; 3A, £2.55; 6A CT, £2.40;
18V 1.5A CT, £2.55; 24V 1.5A CT, £2.55; 3A CT,
£2.45; 5A, £2.80; 8A, £2.35; 12A, £1.85; 40V 3A
CT, £4.50; 50V 6A CT, £13.50; 25V 2A+25V 2A,
£4.90; 12V 4A+12V 4A, £4.90.

LT TRANSFORMERS TAPPED SEC. Prim. 200/240V
0-10-12-14-16-18V 2A, £2.60; 4A, £3.75;
0-12-15-20-24-30V 2A, £3.40; 4A, £4.50;
0-5-20-30-40-60V 1A, £3.40; 2A, £4.50;
0-40-50-60-80-90-100-110V 1A, £4.90.

MIDGET RECTIFIER TRANSFORMERS.
For PW rect. 200/240V a.c. 9-0-9V 0.3A; 12-0-12V
0.25A; 20-0-20V 0.15A, 6V 0.5A + 6V 0.5A; 9V
0.35A + 9V 0.35A; 12V 0.25A + 12V 0.25A or
20V 0.15A + 12V 0.15A at £1.65 each; 9-0-9V 1A,
£1.35; 12-0-12V 1A or 20-0-20V 0.75A £1.50 each.

MAINS TRANSFORMERS
Prim. 200/240V a.c. TX6 sec., 425-0-425 500 Ma.
6-3V CT 6A, 6-3V CT 6A, 0-5-8-3V 3A, £16.50;
TX1 425-0-425V 250 Ma, 6-3V CT 4A, 6-3V CT 4A,
0-5-6-3V 3A, £2.75; MTS Prim. 0-110-240V sec.
250V 100 Ma, 6-3V 2A, E/8, £2.70.

O/P TRANSFORMERS FOR POWER AMPLIFIERS
P.P. sec, tapped 3-5-15ohms, A-A, 6.6KΩ 30W,
£5.70; A-A 3KΩ 50W, £9.90; 100W (EL34 KT88,
etc.), £15.75; tapped Multi O/P 10W £3.

G.E.C. MANUAL OF POWER AMPLIFIERS
Covering valve amplifiers of 30W to 400W 35p.

LOUDSPEAKERS FOR AMPLIFIERS
BAKER 25W, £7.60; 35W, £8.40; HI-FI Major
Module 20W w/woofer Xover, £11.80; Baker speaker
lists: FANE: 50W, £10.50; 60W, £13.50; HI-FI
speakers, EMI bass 13x8in, £2.00; 8in 8Ω, £1.15;
7x4in 15Ω, £1.60; 8x5in 3, 8, 15, 25 or 80Ω,
£1.75 each.

LOUDSPEAKERS
2½in 8, 15 or 75Ω, 2½in 8 or 25Ω, 3in 3, 8, 25 or
35Ω, 3½in 8, 15 or 80Ω 90p each; 5in 3, 8 or 25Ω,
5x3in 3 or 8Ω, £1.05; 7x4in 3 or 15Ω, 6½in 3Ω,
£1.25; 10x6in 3Ω, £1.50.

SPEAKER MATCHING TRANSFORMERS
12W 3 to 8 or 15Ω up or down £1.30.

"INSTANT" BULK TAPE/ CASSETTE ERASER
Instant erasure, any diameter tape spools, cassettes,
demagnetises tape heads, 200/240V a.c. £3.25.

SYNCHRONOUS GEARED MOTORS, 230/240V.
Brand new, Smiths. Built-in gear box, 2 RPH,
75p each.

Carriage and VAT extra on all orders.
S.A.E. ENQUIRIES-LISTS, MAIL ORDER ONLY
46 Kenilworth Road, Edgware, Middx. HA8 8YG
Tel. 01-958 9314

TELEVISION CAMERA KITS

Complete kits are available for both "Mullard" and "P.E." design. Each kit includes a comprehensive construction manual, and a completely FREE technical back-up service to ensure your success.

VHF and UHF Modulator Kits also available to allow standard domestic T.V. to be used as monitor.

All parts available separately, including a wide range of lenses, vidicon tubes, special mains transformers and focus/scan coils, also available P.V.V. tele-tennis game.

Send 5" x 7" S.A.E. for full details or come along for a demonstration and a chat with our technical staff.

GROFTON ELECTRONICS

124 Colne Road, Twickenham
Middlesex TW2 6QS
Telephone 01-898 1569
Telex 934642 Cadanac LDN

SUPERSONIC 13 HI-FI MONO AMPLIFIER

A superb solid state audio amplifier. Brand new components throughout. 5 Silicon transistors plus 2 power output transistors in push-pull. Full wave rectification. Output approx. 13 watts r.m.s. into 8 ohms. Frequency response 12Hz. 30KHz \pm 3db. Fully integrated pre-amplifier stage with separate Volume, Bass boost and Treble cut controls. Suitable for 8-15 ohm speakers. Input for ceramic or crystal cartridge. Sensitivity approx. 40mV for full output. Supplied ready built and tested, with knobs, escutcheon panel, input and output plugs. Overall size 3" high x 6" wide x 7 1/4" deep. AC 200/240V. PRICE £11.80. P. & P. 50p.

DE LUXE STEREO AMPLIFIER

A.C. mains 200-240 v. U a l n g heavy duty fully isolated mains transformer with full wave rectification giving adequate smoothing with negligible hum. Valve line-up: 2 x ECL86 Triode Pentodes. 1 x E280 as rectifier. Two dual potentiometers are provided for bass and treble control, giving bass and treble boost or cut. A dual volume controls used. Balance of the left and right hand channels can be adjusted by means of a separate 'Balance' control fitted at the rear of the chassis. Input sensitivity is approximately 300mV for full peak output of 4 watts per channel (8 watts mono), into 8 ohm speakers. Full negative feedback in a carefully calculated circuit, allows high volume levels to be used with negligible distortion. Supplied complete with knobs, chassis size 11" x 4" d. Overall height including valves 5". Ready built and tested to a high standard. £10.22. P. & P. 50p.

POWER SUPPLY UNIT 200/240V. A.C. input. Four switched fully smoothed D.C. outputs giving 6v. and 7v. and 9v. and 12v. at 1 amp on lead. Fitted insulated output terminals and pilot lamp indicator. Hammer finished metal case overall size 6" x 3 1/4" x 2 1/4". Suitable for transistor Radios, Tape Recorders, Amplifiers etc. etc. Ready built and tested. PRICE £4.90. P. & P. 35p.

WYNAIR & BEXINE SPEAKERS & CABINET FABRICS app. 54 in. wide. Our price £1.10 yd. length. P. & P. 15p per yd. (min. 1 yd.). S.A.E. per sample.

HARVERSON'S SUPER MONO AMPLIFIER

A super quality gram amplifier using a double wound fully isolated mains transformer, rectifier and ECL82 triode pentode valve as audio amplifier and power output stage. Impedance 3 ohms. Output approx. 3.5 watts. Volume and tone controls. Chassis size only 7 1/2" wide x 3 1/2" deep x 6 1/2" high overall. A.C. mains 200/240V. Supplied absolutely Brand New completely wired and tested with good quality output transformer. £3.78 P. & P. 40p. BARGAIN PRICE

BRAND NEW MULTI-RATIO MAINS TRANSFORMERS. Giving 13 alternatives. Primary: 0-210-240V. Secondary combinations 0-5-10-15-20-25-30-35-40-60V. Half wave at 1 amp. 10-0-10, 20-0-20, 30-0-30V. at 2 amps full wave. Size 3in. long x 3 1/2in. wide x 3in. deep. Price £2.31. P. & P. 40p.

MAINS TRANSFORMER. For transistor power supplies. Pro. 200/240V. Sec. 9-0-9 at 500 mA. £1.10. P. & P. 25p.

Pri. 200/240V. Sec. 12-0-12 at 1 amp. £1.21. P. & P. 25p.

Pri. 200/240V. Sec. 10-0-10 at 2 amp. £1.32. P. & P. 35p.

HI-GRADE COPPER LAMINATE BOARDS 8" x 6". Five for 60p plus 30p P. & P.

GENERAL PURPOSE HIGH STABILITY TRANSISTOR PRE-AMPLIFIER

For P.U. Tape, Mike, Guitar, etc. and suitable for use with valve or transistor equipment. 9-18v. battery or on H.T. line 200/300V. Frequency response 10Hz-20KHz. Gain 20dB. Solid encapsulation size 1 1/2" x 1 1/2" x 1 1/2". Brand new complete with instructions. Price 95p. P. & P. 15p.

HANDBOOK OF TRANSISTOR EQUIVS. AND SUBS. A must for servicemen and home constructors. Including many 1000's of British, U.S.A. European and Japanese transistors. ONLY 40p. Post 5p.

3 Reference Encyclopedias for Electronic Engineers and Designers, covering between them transistor characteristics, diode and transistor equivalents. Many thousands of up to date European types listed. Diode Equivalents 50p. Transistor Equivalents 90p. Transistor Characteristics £1.10. POST FREE. All three together £2.80.


NEW ISSUE

Thyristor, Triac, Diac etc. encyclopedias 95p. Post Free.

8 pole 3 way 2 bank low loss Xaley type switches 1 1/2" sections. Standard spindle. 2 switches 64p + 10p P. & P.

Open 9.30-5.30 Monday to Friday, 9.30-5 Saturday
Closed Wednesday.
A few minutes from South Wimbledon Tube Station

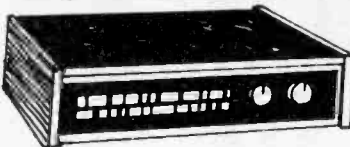HARVERSONIC MAINS OPERATED SOLID STATE STEREO FM TUNER



Enjoy Fabulous Stereo Radio at this Low Introductory Price!

Designed and styled to match our 10 + 10 amplifier but will suit any other standard stereo amplifier. The design incorporates the very latest circuitry techniques with high-gain, low noise IF stages. Automatic frequency control to "lock on" station and prevent drift. IC stereo decoder for maximum stereo separation. I.E.D. for stereo beacon indicator. Nominal output of tuner 100mV. Approximate size 12 1/2in wide x 8in deep by 2 1/2in high. Supplied ready built, fully tested and fully guaranteed (not available in kit form). Price £21.60. Post and Packing 50p.

STEREO-DECODER SIZE 2" x 3" x 1/2"

Ready built. Pre-aligned and tested. Sens. 20-500mV for 9-15V neg. earth operation. Can be fitted to almost any FM VHF radio or tuner. Stereo beacon light can be fitted if required. Full details and instructions (inclusive of hints and tips) supplied. £5 plus 10p P. & P. Stereo beacon light if required 40p extra.

PRECISION ENGINEERED PLINTHS Beautifully constructed in heavy gauge "Colorecoat" plastic coated steel. Resonance free. Designed to take Garrard 1025, 2000, 2025TC, 2500, 6000, 2500, 5100, SP25 II and III, SL65B, AT60 etc. for B.S.R. C109, C120, A21 etc. Black leatherette finish. Size 12 1/2" x 14 1/2" x 3 1/2" high (approx. 7 1/2" high, including rigid smoked acrylic cover). NOW ONLY £4.76. P. & P. 70p.

LATEST ACOS GP91/150 mono compatible cartridge with V/O stylus for LP/EP/78. Universal mounting bracket. £1.48. P. & P. 15p.

SONOTONE STACCOMPATIBLE STEREO CARTRIDGE T/O stylus Diamond Stereo LP and Sapphire 78. ONLY £2.27. P. & P. 10p. Also available fitted with twin Diamond T/O stylus for Stereo LP. £2.78. P. & P. 15p.

LATEST RONETTE T/O STEREO COMPATIBLE CARTRIDGE for EP/LP/78 stereo 78. £1.60. P. & P. 15p.

LATEST RONETTE T/O MONO COMPATIBLE CARTRIDGE for playing EP/LP/78 mono or stereo records on mono equipment. Only £1.47. P. & P. 15p.

QUALITY RECORD PLAYER AMPLIFIER MK. II A top quality record player amplifier employing heavy duty double wound mains transformer, ECC83, EL84, and rectifier. Separate Bass, Treble and Volume controls. Complete with output transformer matched for 3 ohm speaker. Size 7in wide x 3in deep x 6in high. Ready built and tested. PRICE £4.91. P. & P. 50p.

ALSO AVAILABLE mounted on board with output transformer and speaker. PRICE £6.20. P. & P. 60p.

HI-FI LOUSPEAKER SYSTEMS

Beautifully made teak finish enclosure with most attractively Tygan-Vynair front. Size 16" high x 10 1/2" wide x 6" deep. Fitted with E.M.I. Ceramic Magnet 13" x 8" bass unit, two H.F. tweeter units and crossover. Maximum power handling 10 watts. Available 3 or 8 or 15 ohms impedance. Carr. 75p.

OUR PRICE £9.10. Carr. 75p.

Cabinet Available Separately £4.88. Carr. 65p. Also available in 8 ohms with EMF 13" x 8" bass speaker with parasitic tweeter £7.60. Carr. 75p.

LOUDSPEAKER BARGAINS

5in. 3ohm £1.25. P. & P. 15p. 7 x 4in. 3ohm £1.40. P. & P. 20p. 10 x 6in. 3 or 15 ohm £2.10. P. & P. 30p. E.M.I. 8 x 5in. 3ohm with high flux magnet £1.70. P. & P. 20p. E.M.I. 13 1/2 x 8in. with high flux ceramic magnet with parasitic tweeter 3, 8 or 15 ohm £3.50. P. & P. 30p. E.M.I. 13 x 8in. 3 or 15 ohm with two inbuilt tweeters and crossover network £4.95. P. & P. 30p. E.M.I. tweeter. Approx. 3 1/4". Available 3 or 8 or 15 ohms. £1.25 + 20p. P. & P.


BRAND NEW. Bakers Loudspeakers at substantial discounts. 12in. 15w. H/D Speakers, 3, 8 or 15 ohms. State which. Current production by well-known British maker. Now with Hi Flux ceramic ferrobar magnet assembly £7.50. Guitar models: 25w. £7.50. 35w. £8.50. P. & P. 40p.

12in. "EA" TWIN CONE LOUSPEAKER. 10 watts peak handling. 3 or 8 or 15 ohm (state which) £2.70. P. & P. 35p.

"POLY PLANAR" WAFER-TYPE, WIDE RANGE ELECTRO-DYNAMIC SPEAKER. Size 11 1/2" x 14 1/2" x 1 1/2" deep. Weight 19oz. Power handling 20W. m.s. (40W peak). Impedance 8 ohm only. Response 40Hz-20KHz. Can be mounted on ceilings, walls, doors, under tables, etc., and used with or without baffle. Send S.A.E. for full details. Only £6.48 each. P. & P. 34p.


SPECIAL BARGAIN OFFER! Limited number of BSR C123 Auto Changer De Luxe with lightweight tubular arm and stereo cartridge. Brand new. ONLY £7.88 + p. & p. 60p.

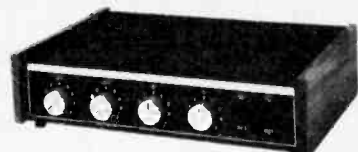HARVERSONIC SUPER SOUND 10 + 10 STEREO AMPLIFIER KIT



A really first-class Hi-Fi Stereo Amplifier Kit. Uses 14 transistors including Silicon Transistors in the first five stages on each channel resulting in even lower noise level with improved sensitivity. Integrated pre-amp with Bass, Treble and two Volume Controls. Suitable for use with Ceramic or Crystal cartridges. Very simple to modify to suit magnetic cartridge connections. Input output stage for any speakers from 8 to 15 ohms. Compact design, all parts supplied including drilled metal work, high quality ready drilled printed circuit board with component identification clearly marked, smart brushed anodised aluminium front panel with matching knobs, wire, solder, nuts, bolts—no extras to buy. Simple step by step instructions enable any constructor to build an amplifier to be proud of. Brief specifications: Power output: 14 watts r.m.s. per channel into 8 ohms. Frequency response \pm 3dB 12-30,000 Hz Sensitivity: better than 80mV into 1M Ω . Full power bandwidth: \pm 3dB 12-15,000 Hz. Bass boost approx. to \pm 12dB. Treble cut approx. to -16dB. Negative feedback 18dB over main amp. Power requirements 35v. at 1.0 amp. Overall Size 12" w. x 8" d. x 2 1/2" h. Fully detailed 7 page construction manual and parts list free with kit or send 18p plus large S.A.E. **AMPLIFIER KIT** £11.34 P. & P. 30p (Magnetic input components 33p extra) **POWER PACK KIT** £2.46 P. & P. 40p **CABINET** £3.46 P. & P. 40p (Post Free if all units purchased at same time)

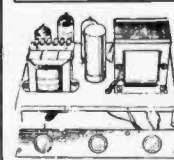Full after sales service. Also available ready built and tested £24.60. Post Free. Note: The above amplifier is suitable for feeding two mono sources into inputs (e.g. mike, radio, twin record decks, etc.) and will then provide mixing and fading facilities for medium powered Hi-Fi Discotheque use, etc.



3-VALVE AUDIO AMPLIFIER HA34 MK II Designed for Hi-Fi reproduction of records. A.C. Mains operation. Ready built on plated heavy gauge metal chassis, size 7 1/2" x 4 1/2" x 4 1/2" h. Incorporates ECC83, EL84, E280 valves. Heavy duty, double wound mains transformer and output transformer matched for 3 ohm speaker. Separate volume control and now with improved wide range tone controls giving bass and treble lift and cut. Negative feedback line. Output 41 watts. Front panel can be detached and leads extended for remote mounting of controls. Complete with knobs, valves, etc., wired and tested for only £5.90. P. & P. 45p.

BSL "FOUR" AMPLIFIER KIT. Similar in appearance to HA34 above but employs entirely different and advanced circuitry. Complete set of parts, etc. £4.92. P. & P. 45p.

10/14 WATT HI-FI AMPLIFIER KIT

A stylishly finished monoaural amplifier with an output of 14 watts from 2 EL84s in push-pull. Super reproduction of both music and speech, with negligible hum. Separate inputs for mike and gram allow records and announcements to follow each other. Fully shrouded section wound output transformer to match 3-15 Ω speaker and 2 independent volume controls and separate bass and treble controls are provided giving good lift and cut. Valve line-up 2 EL84s, ECC83, EF86 and E280 rectifier. Simple instruction booklet 15p x SAE (Free with parts). All parts sold separately. ONLY £9.60. P. & P. 60p. Also available ready built and tested £12.75. P. & P. 70p.

HI-FI STEREO HEADPHONES

Adjustable headband with comfortable flexifoam ear-muffs. Wired and fitted with standard stereo 3 1/2in jack plug. Frequency response 30-15,000Hz. Matching impedance 8-16 ohms. Easily converted for Mono. PRICE £3.24. P. & P. 25p.

PRICES INCLUDE VAT AT 8%

HARVERSON SURPLUS CO. LTD.

(Dept. P.E.) 170 HIGH ST., MERTON, LONDON, S.W.19 Tel.: 01-540 3985

SEND STAMPED ADDRESSED ENVELOPE WITH ALL ENQUIRIES

(Please write clearly)

PLEASE NOTE: P. & P. CHARGES QUOTED APPLY TO U.K. ONLY. P. & P. ON OVERSEAS ORDERS CHARGED EXTRA.

TRANSFORMERS

SAFETY MAINS ISOLATING TRANSFORMERS
Prim. 120/240V. Sec 120/240V Centre Tapped and Screened
ALSO AVAILABLE WITH 115/120V SEC. WINDING

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	P & P £	P & P p
07	20	1 8	7.0 x 6.0 x 6.0	2.55	38
149	60	7 12	9.9 x 7.7 x 8.6	3.98	45
150	100	5 8	9.9 x 8.9 x 8.6	4.45	45
151	200	8 0	12.1 x 9.3 x 10.2	7.39	53
152	250	13 12	12.1 x 11.8 x 10.2	8.93	73
153	350	15 0	14.0 x 10.8 x 11.8	10.80	73
154	500	19 8	14.0 x 13.4 x 11.8	12.41	91
155	750	29 0	17.2 x 14.0 x 14.0	18.65	*
156	1000	38 0	17.2 x 16.6 x 14.0	26.50	*
157	1500	46 0	21.6 x 13.4 x 18.1	30.23	*
158	2000	60 0	21.6 x 15.3 x 18.1	33.70	*

AUTO TRANSFORMERS

Ref. No.	VA (Watts)	Weight lb oz	Size cm.	Auto Taps	P & P £	P & P p
113	20	1 0	5.8 x 5.1 x 4.5	0-115-210-240	1.52	30
64	75	2 4	7.0 x 6.7 x 6.1	0-115-210-240	2.64	38
4	150	3 4	8.9 x 7.7 x 7.7	0-115-200-220-240	3.75	45
66	300	6 4	9.9 x 9.6 x 8.6	..	5.29	53
67	500	12 8	12.1 x 11.2 x 10.2	..	8.02	67
84	1000	19 8	14.0 x 13.4 x 14.3	..	12.44	91
93	1500	30 4	14.0 x 15.9 x 14.3	..	16.65	*
95	2000	32 0	17.2 x 16.6 x 14.0	..	22.00	*
73	3000	40 0	21.6 x 13.4 x 18.1	..	31.90	*

CASED AUTO TRANSFORMERS

115V mains lead input and U.S.A. 2-pin outlets, 20VA £2.85, P & P 38p. 500VA £9.50, P & P 80p. 1000VA £15.92, via B.R.S.

LOW VOLTAGE SERIES (ISOLATED)

PRIMARY 200-250 VOLTS 12 AND/OR 24 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Windings	P & P £	P & P p	
111	0.5	0.25	8	4-8 x 2.9 x 3.5	0-12V at 0.25A x 2	1.34	23
213	1.0	0.5	1.2	6.1 x 5.8 x 4.8	0-12V at 0.5A x 2	1.58	30
71	2	1	1.2	7.0 x 6.4 x 6.1	0-12V at 1A x 2	2.09	38
18	4	2	1.2	8.3 x 7.7 x 7.0	0-12V at 2A x 2	2.68	38
70	6	3	3.8	8.9 x 8.0 x 7.7	0-12V at 3A x 2	3.75	45
108	8	4	5.8	9.9 x 8.9 x 8.6	0-12V at 4A x 2	4.15	45
72	10	5	6.4	9.9 x 9.6 x 8.6	0-12V at 5A x 2	4.67	53
116	12	6	6.2	9.9 x 10.2 x 8.6	0-12V at 5A x 2	5.02	53
17	16	8	8.2	12.1 x 9.9 x 10.2	0-12V at 8A x 2	6.62	60
15	20	10	11.8	14.0 x 9.6 x 11.8	0-12V at 10A x 2	9.45	73
187	30	15	15.8	14.0 x 12.1 x 11.8	0-12V at 15A x 2	12.29	85
226	60	30	32.0	17.2 x 15.3 x 14.0	0-12V at 30A x 2	15.30	*

30 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £	P & P p	
112	0.5	1	4	6.1 x 5.8 x 4.8	0-12-15-20-24-30V	1.65	30
79	1.0	2	4	7.0 x 6.7 x 6.1	..	2.18	38
3	2.0	3	4	8.9 x 7.7 x 7.7	..	3.18	38
20	3.0	4	8	9.9 x 8.3 x 8.6	..	4.12	45
21	4.0	6	4	9.9 x 9.6 x 8.6	..	4.67	53
51	5.0	6	12	12.1 x 8.6 x 10.2	..	5.83	53
117	6.0	8	0	12.1 x 9.3 x 10.2	..	6.51	60
88	8.0	12	0	12.1 x 11.8 x 10.2	..	9.00	67
89	10.0	13	12	14.0 x 10.2 x 11.8	..	8.97	73

50 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £	P & P p	
102	0.5	1	12	7.0 x 6.4 x 6.1	0-19-25-33-40-50V	2.35	30
103	1.0	2	12	8.3 x 7.4 x 7.0	..	3.08	38
104	2.0	5	8	7.9 x 8.9 x 8.6	..	4.26	45
105	3.0	6	12	9.9 x 10.2 x 8.6	..	4.26	53
106	4.0	10	0	12.1 x 10.5 x 10.2	..	6.91	67
107	6.0	12	0	14.0 x 10.2 x 11.8	..	11.00	67
118	8.0	18	0	14.0 x 12.7 x 11.8	..	11.80	85
119	10.0	25	0	17.2 x 12.7 x 14.0	..	15.45	*

60 VOLT RANGE

Ref. No.	Amps	Weight lb oz	Size cm.	Secondary Taps	P & P £	P & P p	
124	0.5	2	4	7.0 x 6.7 x 6.1	0-24-30-40-48-60V	2.12	38
126	1.0	3	4	8.9 x 7.7 x 7.7	..	3.10	38
127	2.0	6	4	9.9 x 9.6 x 8.6	..	4.62	45
125	3.0	8	12	12.1 x 9.9 x 10.2	..	6.84	60
123	4.0	13	12	12.1 x 11.8 x 10.2	..	7.96	67
40	5.0	12	0	14.0 x 10.2 x 11.8	..	8.87	73
120	6.0	15	8	14.0 x 12.1 x 11.8	..	10.27	85
121	8.0	25	0	14.0 x 14.7 x 11.8	..	13.64	*
122	10.0	25	0	17.2 x 12.7 x 14.0	..	15.93	*
189	12.0	29	0	17.2 x 14.0 x 14.0	..	18.16	*

MINIATURE TRANSFORMERS WITH SCREENS


Ref. No.	mA	Weight lb oz	Size cm.	Volts	P & P £	P & P p	
238	200	2	2.8 x 2.6 x 2.0	3-0-3	1.40	10	
212	1A, 1A	1	6.1 x 5.8 x 4.8	0-6, 0-6	1.67	30	
13	100	2	4	3.8 x 2.6 x 2.9	0-9-9	1.28	18
235	330, 330	4	4	4.9 x 3.5	0-9-9	1.42	19
207	500, 500	1.00	6.1 x 5.4 x 4.8	0-8-9, 0-8-9	1.75	30	
208	1A, 1A	1	12	7.0 x 6.4 x 6.1	0-8-9, 0-8-9	3.00	38
236	200, 200	4	4.8 x 2.9 x 3.5	0-15, 0-15	1.30	19	
214	300, 300	1	4	6.1 x 5.8 x 4.8	0-20, 0-20	1.76	30
221	700 (d.c.)	1	8	7.0 x 6.1 x 6.1	20-12-0-12-20	1.98	38
204	1A, 1A	2	12	8.3 x 7.7 x 7.0	0-15-20, 0-15-20	3.15	38
203	500, 500	2	4	4.9 x 3.5	0-15-27, 0-15-27	2.73	38
204	1A, 1A	3	4	8.9 x 7.7 x 7.7	0-15-27, 0-15-27	3.50	38

*Carriage via B.R.S.

PLEASE ADD 8% FOR V.A.T. INCLUDING P & P.

BARRIE electronics
3, THE MINORIES, LONDON EC3N 1BJ
TELEPHONE: 01-488 3316/8
NEAREST TUBE STATIONS. ALDGATE & ALDGATE EAST

NEW PE SCORPIO Mk. 2

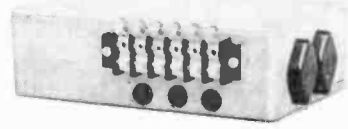

Following the phenomenally successful Scorpio Capacitor-Discharge Electronic Ignition system introduced in 1972 and proved by many thousands of satisfied motorists, we are happy to announce availability of all parts for the PE SCORPIO Mk. 2—

- * Now with added R.F.I. suppression.
- * Fully machined and painted die-cast case with AMP termination connector block.
- * Custom wound transformer.
- * NOW AVAILABLE IN 6V. and 12V.
- * Suitable for all types of Cars, Boats, Go-Karts, etc.
- * Promotes easier starting—even under sub-zero conditions.
- * Improves acceleration, gives better high speed performance and quicker engine warm up.
- * Eliminates excessive contact breaker burning and pitting.
- * PROMOTES FUEL ECONOMY.

Construction of the unit can easily be completed in an evening—installation should take about half an hour. A complete complement of components is supplied with each kit together with ready drilled, roller tinned professional quality fibreglass printed circuit board.—Uses original plugs, points and coil.—No special parts or extras required. (Case size: 7 7/16" x 4 1/2" x 2 1/4")

- * All components available separately.—S.A.E. with enquiries.
- * Construction manual available separately 25p.

Cost £11.78 incl. carr. and ins. or ready built and tested £14.49

Conversion kit from Mk. 1 to Mk. 2. For constructors already possessing Mk. 1 Kits.—Miniature P.C. assembly £1 incl. carr. and ins. With full conversion instructions.

PLEASE ADD VAT TO ALL U.K. ORDERS

(Carriage at cost outside U.K.—Export enquiries welcome.)

DABAR ELECTRONIC PRODUCTS



98 LICHFIELD STREET
WALSALL, Staffs WS1 1UZ



become a RADIO-AMATEUR!

learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence

free!

Brochure, without obligation to:

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL
Dept. EB124, P.O. BOX 156, JERSEY

NAME : _____

ADDRESS : _____ EB15

BLOCK CAPS please

**FREE NEW '74/75
SEMI-CONDUCTOR
AND VALVE LISTS**
Ref No. 36
on request



INTEGRATED CIRCUITS

74 SERIES & LINEAR

EXTRA DISCOUNTS

Semiconductors—Any one type or mixed
SN74 Series IC: 12—extra 10%, 25—extra
15%, 100—extra 20%.

SN7400N	0-15	SN7485N	1-63	SN74191N	2-00
SN7401N	0-16	SN7486N	0-47	SN74192N	2-00
SN7402N	0-16	SN7489N	3-87	SN74193N	2-00
SN7403N	0-16	SN7490N	0-70	SN74194N	1-30
SN7404N	0-16	SN7491AN	1-00	SN74195N	1-10
SN7405N	0-16	SN7492N	0-70	SN74196N	1-20
SN7406N	0-42	SN7493N	0-70	SN74197N	1-20
SN7407N	0-28	SN7494AN	0-80	SN74198N	2-77
SN7408N	0-42	SN7495N	0-90	SN74199N	2-52
SN7409N	0-28	SN7496N	0-95		
SN7410N	0-16	SN7497N	3-87		
SN7411N	0-25	SN74100N	1-89		
SN7412N	0-30	SN74104N	0-58	RCA	
SN7413N	0-36	SN74105N	0-53	CA3012	1-32
SN7414N	0-72	SN74107N	0-45	CA3014	1-80
SN7416N	0-36	SN74110N	0-58	CA3018	1-12
SN7417N	0-36	SN74111N	0-88	CA3019	-1-02
SN7420N	0-16	SN74116N	1-00	CA3020	1-80
SN7421N	0-33	SN74118N	0-90	CA3022	1-93
SN7422N	0-25	SN74119N	1-68	CA3028A	1-03
SN7423N	0-37	SN74120N	0-95	CA3036	1-08
SN7425N	0-37	SN74121N	0-50	CA3046	1-03
SN7426N	0-32	SN74122N	0-70	CA3048	2-76
SN7427N	0-37	SN74123N	0-60	CA3075	1-75
SN7428N	0-40	SN74125N	0-65	CA3081	1-80
SN7430N	0-16	SN74132N	0-72	CA3089E	2-94
SN7432N	0-37	SN74141N	0-90	CA3090	5-00
SN7433N	0-37	SN74145N	1-26	Signetics	
SN7437N	0-37	SN74150N	1-75	NE555	0-85
SN7438N	0-37	SN74151N	1-00	NE560B	5-00
SN7440N	0-22	SN74153N	0-95	NE561B	5-00
SN7441AN	0-92	SN74154N	2-00	NE562B	5-00
SN7442N	0-79	SN74155N	1-00	NE567B	3-50
SN7443N	1-27	SN74156N	1-00	Motorola	
SN7444N	1-27	SN74157N	0-95	MC1303L	1-42
SN7445N	1-80	SN74160N	1-38	MC1304P	1-79
SN7446N	1-80	SN74161N	1-38	MC1310P	2-91
SN7447AN	1-60	SN74162N	1-38	MC1456CP	0-77
SN7448N	1-27	SN74163N	1-38	MC1710CC	0-80
SN7450N	0-16	SN74164AN	1-76	MFC4000P	0-45
SN7451N	0-16	SN74165N	1-76	MFC4010P	0-55
SN7453N	0-16	SN74166N	1-60	MFC6040P	1-00
SN7454N	0-16	SN74167N	3-00	Others	
SN7460N	0-16	SN74170N	2-52	TBA800	1-50
SN7470N	0-36	SN74173N	1-66	SN76003N	1-50
SN7472N	0-38	SN74174N	1-57	SN72741P	0-81
SN7473N	0-41	SN74175N	1-10	702C	0-75
SN7474N	0-42	SN74176N	1-26	709C	0-39
SN7475N	0-59	SN74177N	1-26	723C	0-90
SN7476N	0-45	SN74180N	1-58	728C	0-45
SN7480N	0-60	SN74181N	3-95	741C	0-50
SN7481N	1-10	SN74182N	1-26	747C	1-00
SN7482N	0-87	SN74184N	1-80	748C	0-61
SN7483N	1-10	SN74185N	1-80	LM309K	2-00
SN7484N	1-00	SN74190N	2-00	TAA960	1-75

COSMOS INTEGRATED CIRCUITS. FULL RANGE IN STOCK

AAZ13	£ p	BLY36	£ p	TIP42A	£ p
AC107	0-51	BSX20	0-13	TIS43	0-28
AC128	0-15	BU105	2-20	V405A	0-22
AC187	0-21	BY100	0-27	ZTX108	0-08
ACY17	0-40	BY127	0-12	ZTX300	0-13
ACY39	0-78	BYZ13	0-42	ZTX302	0-18
AD149	0-50	C1080	0-54	ZTX500	0-16
AD161	0-44	GET111	0-72	2N697	0-13
AD162	0-24	GET115	0-90	2N706	0-12
AF117	0-24	GET880	0-60	2N930	0-18
AF118	0-57	LM309K	2-00	2N987	0-42
AF139	0-41	MAT121	0-25	2N1132	0-24
AF186	0-48	MJE340	0-47	2N1304	0-28
AF239	0-44	MJE520	0-63	2N1613	0-21
AF277	0-33	MJE3055	0-77	2N1671	1-20
BAX115	0-10	MJE2955	1-27	2N2147	0-78
BC107	0-05	MPF105	0-36	2N2160	0-78
BC108	0-14	NKT404	0-66	2N2926	0-12
BC109	0-13	OA5	0-72	2N3053	0-18
BC109C	0-16	OA81	0-18	2N3054	0-48
BC113	0-15	OA200	0-08	2N3055	0-45
BC147	0-10	OA202	0-06	2N3440	0-58
BC148	0-08	OC28	0-66	2N3442	-1-39
BC149	0-10	OC35	0-55	2N3525	-0-91
BC169C	0-15	OC36	0-60	2N3614	-0-65
BC182	0-12	OC44	0-20	2N3702	-1-11
BCY32	0-65	OC45	0-18	2N3714	-1-41
BCY39	1-50	OC71	0-18	2N3771	-1-77
BCY55	2-64	OC72	0-28	2N3773	-2-40
BCY70	0-18	OC77	0-54	2N3790	-2-10
BCY71	0-22	OC83	0-27	2N3819	-0-38
BCY72	0-12	OC140	0-27	2N3866	-0-72
BD124	0-65	OC170	0-30	2N3903	-0-15
BD131	0-42	OC200	0-54	2N4126	-0-15
BF115	0-20	OC202	0-90	2N4871	-0-34
BF180	0-36	ORP11	1-20	2N5457	-0-30
BF194	0-10	ORP12	0-60	2S303	-0-80
BFX13	0-26	ORP60	0-55	40550	-0-54
BFX34	0-70	P346A	0-18	40361	-0-45
BFX88	0-24	TIL209	0-20	40362	-0-40
BFY50	0-21	TIP29A	0-45	40408	-0-50
BFY51	0-20	TIP30A	0-57	40486	-0-85
BFY64	0-36	TIP31A	0-61	40636	-1-00
BFY90	0-31	TIP41A	0-74	40430	-0-85

TEST EQUIPMENT MULTI- METERS



(Carr/packing 35p) £ p
U4324 20kΩ/V with case 9-25
U435 20kΩ/V w/lt case 8-75
U4313 20kΩ/V with steel case 12-50
U4317 20Ω/V with case 18-50
U4341 33kΩ/V plus transistor steel case 10-50
U4323 20kΩ/V plus 1kHz OSC with case 7-70
ITI-2 20kΩ/V a/um type 5-65
THL330 (L330K) 2kΩ/V Robust 7-50
TP5N 20kΩ/V (Case £2) 8-25
TP105 2kΩ/V 8-25
TW205 20kΩ/V 10-25
TW50K 50kΩ/V 9-95
EP100N 10kΩ/V 12-50
AF105 50kΩ/V Deluxe (case £1-90) 22-50
S100TR 100kΩ/V plus transistor tester

GENERAL TEST EQUIPMENT

— Carr/packing 50p. *Carr/packing 30p) unless stated



NEW REVOLUTIONARY SUPERTESTER

680R £ p
680R Multi-tester 18-50

Accessories
Transistor tester 11-00
Electronic voltmeter 18-00
Amplamp 11-85
Temperature probe 11-85
Gauss meter 5-95
Signal injector 5-95
Phase sequence 5-95
EHT probe 5-95
Shunts 25/50-100A 4-50
†3100 IMA Strip chart recorder 44-50
†TK40 AC Multivoltmeter 18-75
†TK15 Grid dip meter 440kHz-28MHz 18-50
†TK65 28 Range valve voltmeter 22-50
†TK20D RF Generator 120kHz-500MHz 18-95
†TK22D AF Generator 20Hz-200kHz 18-95
*HM350 in circuit transistor tester 18-50
*C3025 Deluxe meter 1-300MHz 6-95
*TT145 Compact transistor tester 14-75

ELECTRONIC COMPONENTS

(Post/Packing 15p per 1-6 items G.B. unless stated)



Ceramic Filters

Miniature 10.7 mHz filters
40p pair
IC 1F Unit
CA3089 10.7 mHz
IC £2-94
IC Clock
MM 5314 single
chip clock with
CCT £9.
Radio IC Chip
ZN414 Radio IC
with circuit £1-20.



Ultrasonic transducers
With data/circuits £5-90
pair.

Stroke tubes

ZF778A (similar to 4A) £4.
ZF112A £5.

7 segment indicators

3015F with data £1-70 each.

Spring delay units

HP42 9in twin spring £3-30
(P. & P.) 20p. HR1 8in twin
spring £6-85 (P. & P.) 25p.

Fibre optics

0-01in dia. mono filament
£5-50 per 100 metres. 0-13in
dia. 64 fibres £1 per metre.
15mm dia. mare's tails
£10-50 each.

TAPE HEADS

MARRIOT XRPS/17 † Track High £2-50; XRPS/18 † Track Med.
£3-50; XRPS/36 † Track Med. £5-00; XRPS/63 † Track High
£1-75; Erase Heads for XRPS/17/18/36 (XES11) 75p; 13X12E 343
† Tr. Erase 75p.
H/RP Record/Play † Track 45p.
H/RP Single Track Rec./Play 35p.
Bogen Type UL290 Erase £1-50.
Miniature Stereo Cassette Rec./Play £2-25.

SILICON CONTROLLED RECTIFIERS

TO5 1 Amp	£ p	6 Amp	£ p
CRS1105AF	0-42	SC45A	0-98
CRS110AF	0-48	SC40B	0-97
CRS120AF	0-52	SC40D	1-20
CRS140AF	0-60	SC40E	1-50
CRS160AF	0-78	10 Amp	
TO48 3 Amp		SC45A	1-09
CRS31025AF	0-36	SC45B	1-12
CRS310AF	0-48	SC45D	1-50
CRS320AF	0-54	SC45E	1-65
CRS340AF	0-65	15 Amp	
CRS360AF	0-80	SC50A	1-46
TO48 7 Amp		SC50B	1-57
CRS7400	0-84	SC50D	1-80
CRS7600	1-14	SC50E	2-00
TO48 16 Amp		Also	
CRS16100	0-78	40430	0-85
CRS16200	0-85	40659	0-90
CRS16400	0-96	40486	0-85

BRIDGE SILICON RECTIFIERS

‡ Amp	£ p	£ p	£ p
B025/025	0-16	B2/20	0-40
B025/05	0-14	B2/40	0-44
1 Amp		B2/60	0-45
B1/05	0-20	B2/100	0-55
B1/10	0-21	4 Amp	
B1/20	0-24	B4/05	0-45
B1/60	0-25	B4/10	0-48
B1/100	0-30	B4/20	0-54
2 Amp		B4/40	0-60
B2/05	0-30	B4/60	0-70
B2/10	0-35	B4/80	0-90
		6 Amp	
		B6/05	0-50
		B6/10	0-58
		B6/20	0-68
		B6/40	0-75
		B6/60	0-87
		1 Amp Tubular	
		W005	0-27
		W01	0-29
		W02	0-30
		W06	0-33



PA-DISCO LIGHTING EQUIPMENT



Without doubt U.K.'s best range of modular and
complete equipment. Lighting, mixing, micro-
phones, accessories, speakers, amplifiers,
lenses, etc., etc.

FREE stock lists (Ref. No. 18) on request. CALL
IN AND SEE FOR YOURSELF AT HENRY'S DISCO
CENTRE, 309 EDGWARE ROAD. TEL. 01-723 6963

QUALITY CASSETTE

"Living Sound" made specially for
Henry's by EMP Tapes Ltd. 5 screw
type with library case. Post paid (G.B.).

	£	£	£	£
	3 for	6 for	10 for	25 for
C60	1-10	2-00	3-15	7-50
C90	1-47	2-85	4-85	11-37
C120	1-83	3-54	5-60	14-00

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Hi Fi and
Electronics
Centres Open
9 am - 6 pm

Prices correct at time of preparation. Subject to change without notice. E.&O.E.

The largest selection

EX COMPUTER BOARDS

Packed with transistors, diodes, capacitors and resistors - COMPONENT VALUE £1.50, 3 for ONLY 55p + P. & P. 30p.
SPECIAL one as above PLUS Power Transistors ONLY 55p each + P. & P. 15p.
PAXOLINE BOARDS 7½ × 9" approx. 4 for 30p + P. & P. 20p.

FIBRE-GLASS PRINTED CIRCUIT BOARDS

16½ × 4" approx. 2 for 55p

DECON-DALO 33PC Marker

Etch resistant printed circuit marker pen 99p each

VEROBOARDS

Packs containing approx. 300q. in various sizes, all 0-1 matric 55p

REPANCO CHOKES & COILS

RF Chokes
 CH1. 2.5mH 29p CH2. 5.0mH 30p
 CH3. 7.5mH 31p CH4. 10mH 30p
 CH5. 1.5mH 28p

COILS

DRX1 Crystal set 31p DRR2 Dual range 45p

COIL FORMERS & CORES

NORMAN 1" Cores & Formers 8p
 1" Cores & Formers 10p

SWITCHES

DP/DT Toggle 36p SP/ST Toggle 30p

FUSES

1½ and 20mm. 100mA, 200mA, 250mA, 500mA, 1A, 1.5A, 2A
 QUICK-BLOW 5p each.

EARPHONES

Crystal 2.5mm plug 42p
 Crystal 3.5mm plug 42p
 8 ohms 2.5mm plug 22p
 8 ohms 3.5mm plug 22p

DYNAMIC MICROPHONES

B1223. 200 ohms plus on/off switch and 2.5mm and 3.5mm plugs £1.85

3-WAY STEREO HEADPHONE JUNCTION BOX

H1012 £1.87

2-WAY CROSSOVER NETWORK

K4007. 80 ohms Imp. Insertion loss 3dB £1.21

CAR STEREO SPEAKERS

(Angled) £3.85 per pair.

BI-PAK

CATALOGUE AND LISTS

Send S.A.E. and 10p.

INSTRUMENT CASES



(Black Vinyl covered)

No. Length	Width	Height	Price
BV1 8" ×	5½" ×	2"	£1.10
BV2 11" ×	6" ×	3"	£1.45

ALUMINIUM BOXES

BA1 5½" ×	2½" ×	1½"	42p
BA2 4" ×	4" ×	1½"	42p
BA3 4" ×	2½" ×	1½"	42p
BA4 5½" ×	4" ×	1½"	50p
BA5 4" ×	2½" ×	2"	42p
BA6 3" ×	2" ×	1"	34p
BA7 7" ×	5" ×	2½"	70p
BA8 8" ×	6" ×	3"	80p
BA9 6" ×	4" ×	2"	58p

P. & P. 10p on each box

VISIT OUR COMPONENT SHOP

18 BALDOCK ST., WARE, Herts. (A10)

Open Mon.-Sat. 9-6.30 p.m. Tel. 61693

BIB HI-FI ACCESSORIES

De Luxe Groov-Kleen

Model 42 £1.95

Chrome Finish

Model 60 £1.50



Ref. 36A. Record/Stylus Cleaning Kit 33p
 Ref. 43. Record Care Kit £2.42
 Ref. 31. Cassette Head Cleaner 58p
 Ref. 32. Tape editing Kit £1.68
 Model 9. Wire Stripper/Cutter 83p
 Ref. 48. Spirit Level 62p

Ref. B. Stylus and Turntable Cleaning Kit
 Ref. P. Hi-Fi Cleaner 31p 34p
 Ref. 32A. Stylus Balance £1.37
 Ref. J. Tape Head Cleaning Kit 62p
 Ref. 58. Hi-Fi Stereo Hints and Tips 42p
 Ref. 45. Auto Changer Groove Cleaner £1.08

ANTEX SOLDERING IRONS

X25. 25 watt £2-05

CCN 240. 15 watt £2-48

Model G. 18 watt £2-26

SK2. Soldering Kit £3-25

STANDS: ST3, suitable for all models £1

SOLDER: 18SWG Multicores 7oz £1-61

22SWG 7oz £1-61. 18SWG 22ft 51p

22SWG Tube 33p

ANTEX BITS AND ELEMENTS

Bits No.

102 For model CN240 42p

104 For model CN240 42p

1100 For model CCN240 42p

1101 For model CCN240 42p

1102 For model CCN240 42p

1020 For model G240 42p

1021 For model G240 42p

1022 For model G240 42p

50 For model X25 48p

51 For model X25 48p

52 For model X25 48p

ELEMENTS

ECN 240 £1-30 ECCN 240 £1-32

EG 240 £1-07 EX 25 £1-16

ANTEX HEAT SINKS 10p

VAT included in all prices. Please add 10p P. & P. (U.K. only). Overseas orders—please add extra for postage.

NEW COMPONENT PAK BARGAINS

Pack	No.	Qty.	Description	Price
C1	200		Resistors mixed values approx. count by weight	0-55
C2	150		Capacitors mixed values approx. count by weight	0-55
C3	50		Precision Resistors 0-1%, 0-01% mixed values	0-55
C4	75		¼th W Resistors mixed preferred values	0-55
C5	5		Pieces assorted Ferrite Rods	0-55
C6	2		Tuning Gangs, MW/LW VHF	0-55
C7	1		Pack Wire 50 metres assorted colours	0-55
C8	10		Reed Switches	0-55
C9	3		Micro Switches	0-55
C10	15		Assorted Pots & Pre-Sets	0-55
C11	5		Jack Sockets 3 × 3.5m 2 × Standard Switch Type	0-55
C12	30		Paper Condensers preferred types mixed values	0-55
C13	20		Electrolytics Trans. types	0-55
C14	1		Pack assorted Hardware—Nuts/Bolts, Grommets, etc.	0-55
C15	5		Mains Slide Switches	0-55
C16	20		Assorted Tag Strips & Panels	0-55
C17	10		Assorted Control Knobs	0-55
C18	4		Rotary Wave Change Switches	0-55
C19	2		Relays 6—24V Operating	0-55
C20	1		Pack Sheets of Copper Laminate approx. 20 sq. ins.	0-55

PLUGS AND SOCKETS

PLUGS

PS 1	D.I.N. 2 Pin (Speaker)	0-11
PS 2	D.I.N. 3 Pin	0-12
PS 3	D.I.N. 4 Pin	0-15
PS 4	D.I.N. 5 Pin 180°	0-16
PS 5	D.I.N. 5 Pin 240°	0-16
PS 6	D.I.N. 6 Pin	0-17
PS 7	D.I.N. 7 Pin	0-18
PS 8	Jack 2.5mm Screened	0-18
PS 9	Jack 3.5mm Plastic	0-18
PS 10	Jack 3.5mm Screened	0-18
PS 11	Jack 1" Plastic	0-15
PS 12	Jack 1" Screened	0-22
PS 13	Jack Stereo Screened	0-36
PS 14	Phono	0-10
PS 15	Car Aerial	0-22
PS 16	Co-Axial	0-15

INLINE SOCKETS

PS 21	D.I.N. 2 Pin (Speaker)	0-14
PS 22	D.I.N. 3 Pin	0-20
PS 23	D.I.N. 5 Pin 180°	0-20
PS 24	D.I.N. 5 Pin 240°	0-20
PS 25	Jack 2.5mm Plastic	0-16
PS 26	Jack 3.5mm Plastic	0-16
PS 27	Jack 1" Plastic	0-30
PS 28	Jack 1" Screened	0-36
PS 29	Jack Stereo Plastic	0-30
PS 30	Jack Stereo Screened	0-38
PS 31	Phono Screened	0-18
PS 32	Car Aerial	0-22
PS 33	Co-Axial	0-22

SOCKETS

PS 35	D.I.N. 2 Pin (Speaker)	0-08
PS 36	D.I.N. 3 Pin	0-11
PS 37	D.I.N. 5 Pin 180°	0-11
PS 38	D.I.N. 5 Pin 240°	0-11
PS 39	Jack 2.5mm Switched	0-12
PS 40	Jack 3.5mm Switched	0-12
PS 41	Jack 1" Switched	0-20
PS 42	Jack Stereo Switched	0-30
PS 43	Phono Single	0-08
PS 44	Phono Double	0-10
PS 45	Co-Axial Surface	0-10
PS 46	Co-Axial Flush	0-20

LEADS

LS 1	Speaker Lead 2 pin D.I.N. plug to open ends approx 3 metres long (coded)	0-20
------	--	------

CABLES

CP 1	Single Lapped Screen	0-07
CP 2	Twin Common Screen	0-11
CP 3	Stereo Screened	0-12
CP 4	Four Core Common Screen	0-23
CP 5	Four Core Individually Screened	0-30
CP 6	Microphone Fully Braided Cable	0-10
CP 7	Three Core Mains Cable	0-09
CP 8	Twin Oval Mains Cable	0-07
CP 9	Speaker Cable	0-05
CP 10	Low Loss Co-Axial	0-18

CARBON POTENTIOMETERS

Log and Lin		
4-7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M		
VC 1	Single Less Switch	0-15
VC 2	Single D.P. Switch	0-28
VC 3	Tandem Less Switch	0-46
VC 4	1K Lin Less Switch	0-15
VC 5	100 K anti-Log	0-46

HORIZONTAL CARBON PRESETS

0-1 watt 0-06 each
 100, 220, 470, 1K, 2.2K, 4.7K, 10K, 22K, 47K, 100K, 220K, 470K, 1M, 2M, 4.7M

IT'S NEW IT'S POWERFUL (15 + 15w R.M.S.) AND — IT LOOKS GOOD!

THE LEGIONAIRE STEREO AMPLIFIER



ORDER NOW—
 ONLY £39.95 p. & p. 50p
 OR Write for full details

WORLD SCOOP JUMBO SEMICONDUCTOR PACK

Transistors, Germ. and Silicon Rectifiers, Diodes, Triacs, Thyristors, I.C.s and Zeners. ALL NEW AND CODED.

APPROX 100 PIECES

Offering the amateur a fantastic bargain Pak and an enormous saving—identification and data sheet in every Pak.

Only £2 p. & p. 20p

RECORD STORAGE/CARRY CASES

7in EP. 18½in × 7in × 8in (50 records) £2-10
 12in LP. 13½in × 7in × 12in (50 records) £2-95

CASSETTE CASES

Holds 12. 10in × 3½in × 5in. Lock and handle, £1.30.

SPECIAL PURCHASE

2N3055. Silicon Power Transistors NPN. Famous manufacturers out-of-spec devices free from open and short defects—every one abiel 115W. TO3. Metal Case.
 OUR SPECIAL PRICE 8 for £1

LOW COST CAPACITORS

0-01µF 400V. 3p each
 500µF 50V. Elect. 10p each

REPANCO TRANSFORMERS

240V. Primary. Secondary voltages available from selected tappings 4V, 7V, 8V, 10V, 14V, 15V, 17V, 19V, 21V, 25V, 31V, 33V, 40, 50 and 25V-0-25V.

Type	Amps	Price	P. & P.
MT50/1	1	£1-93	30p
MT50/1	1	£2-42	35p
MT50/2	2	£3-30	40p

CARTRIDGES

ACOS
 GP91-19C 200mV at 1.2cm/sec £1.85
 GP93-1 280mV at 1cm/sec £1.85
 GP96-1 100mV at 1cm/sec £2.80
 J-2005 Crystal/Hi Output £1.05
 J-2010C Crystal/Hi Output Compatible £1.20
 J-2096S Stereo/Hi Output £1.75
 J-2105 Ceramic/Med Output £1.95
 J-2103 Magnetic 5mV/5cm/sec, including stylus £4.95
 J-2203S Replacement stylus for above £3.00
 AT-55 Audio-technica magnetic cartridge 4mV/5cm/sec £3.30

CARBON FILM RESISTORS

The E12 Range of Carbon Film Resistors, ¼ watt available in PAKS of 50 pieces, assorted into the following groups:
 R1 50 Mixed 100 ohms-820 ohms 50p
 R2 50 Mixed 1K-8.2K 50p
 R3 50 Mixed 10K-82K 50p
 R4 50 Mixed 100K-1M 50p
 THESE ARE UNBEATABLE PRICES—JUST 1p EACH INCL. V.A.T.


BI-PAK SUPERIOR QUALITY LOW - NOISE CASSETTES

C80, 36p; C90, 48p; C120, 60p.

-the lowest prices!

BI-PAK QUALITY COMES TO AUDIO!

AL10/AL20/AL30 AUDIO AMPLIFIER MODULES

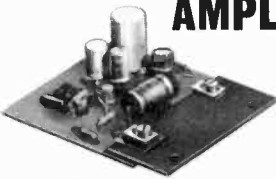

The AL10, AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 3 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the car and at home.

Parameter	Conditions	Performance
HARMONIC DISTORTION	Po = 3 WATTS f = 1KHz	0.25%
LOAD IMPEDANCE	—	8-16 Ω
INPUT IMPEDANCE	f = 1KHz	100 k Ω
FREQUENCY RESPONSE -3dB	Po = 2 WATTS	50 Hz-25KHz
SENSITIVITY for RATED O/P	Vs=25V. R1=8Ω f=1KHz	75mV. RMS
DIMENSIONS	—	3" × 2 1/2" = 1"

The above table relates to the AL10, AL20 and AL30 modules. The following table outlines the differences in their working conditions.

Parameter	AL10	AL20	AL30
Maximum Supply Voltage	25	30	30
Power out for 2% T.H.D. (RL = 8 Ω f = 1KHz)	3 watts RMS Min.	5 watts RMS Min.	10 watts RMS Min.

AUDIO AMPLIFIER MODULES

AL 10. 3 watts	£2-50
AL 20. 5 watts	£2-85
AL 30. 10 watts	£3-20

POWER SUPPLIES

PS 12. (Use with AL10, AL20, AL30) 95p
SPM 80. (Use with AL60) £3-25
FRONT PANELS FP 12 with Knobs £1-00

PRE-AMPLIFIERS

PA 12. (Use with AL10, AL20 and AL30)	£4-35
PA 100. (Use with AL60)	£13-15

TRANSFORMERS

T461 (Use with AL10) £1-60 P & P 15p
T538 (Use with AL20, AL30) £2-30 P & P 15p
BMT80 (Use with AL60) £2-75 P & P 25p

PA12 PRE-AMPLIFIER SPECIFICATION

The PA12 pre-amplifier has been designed to match into most budget stereo systems. It is compatible with the AL 10, AL 20 and AL 30 audio power amplifiers and it can be supplied from their associated power supplies. There are two stereo inputs, one has been designed for use with *Ceramic cartridges while the auxiliary input will suit most *Magnetic cartridges. Full details are given in the specification table. The four controls are, from left to right: Volume and on/off switch, balance, bass and treble. Size 152mm × 84mm × 35mm.

Frequency response—	20Hz-50KHz (-3dB)
Bass control—	± 12dB at 60Hz
Treble control—	± 14dB at 14KHz
*Input 1. Impedance	1 Meg. ohm
Sensitivity	300mV
*Input 2. Impedance	30 K ohms
Sensitivity	4mV

Look for our


SEMICONDUCTOR ADVERTISEMENTS in

Practical Wireless Wireless World Radio Constructor

ALL PRICES INCLUDE V.A.T.

The STEREO 20

The "Stereo 20" amplifier is mounted, ready wired and tested on a one-piece chassis measuring 20 cm × 14 cm × 5.5 cm. This compact unit comes complete with on/off switch volume control, balance, bass and treble controls, Transformer, Power supply and Power amps. Attractively printed front panel and matching control knobs. The "Stereo 20" has been designed to fit into most turntable plinths without interfering with the mechanism or, alternatively, into a separate cabinet. Output power 20w peak. Input 1 (Cer.) 300mV into 1M. Freq. res. 25Hz-25kHz. Input 2 (Aux.) 4mV into 30K. Harmonic distortion. Bass control ± 12dB at 60Hz typically 0.25% at 1 watt. Treble con. ± 14dB at 14kHz. £14-45

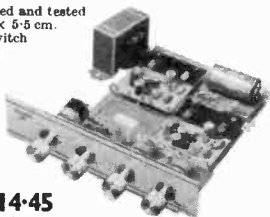

TC20 TEAK VENEERED CABINET

For Stereo 20 (front board undrilled) Size 10 1/2" × 8 1/2" × 3", £3-95 plus 30p postage.

SHP80 STEREO HEADPHONES

4-16 ohms impedance. Frequency response 20 to 20,000Hz. Stereo/mono switch and volume controls, £4-95


NOW WE GIVE YOU
50w PEAK (25w R.M.S.)
PLUS THERMAL PROTECTION!
The NEW AL60 Hi-Fi
Audio Amplifier FOR ONLY £3-95



- Max Heat Sink temp 90°C.
- Frequency Response 20Hz to 100KHz
- Distortion better than 0.1% at 1KHz
- Supply voltage 15-50 volts
- Thermal Feedback
- Latest Design Improvements
- Load — 3, 4, 8 or 16 ohms
- Signal to noise ratio 80dB
- Overall size 63mm × 105mm × 13mm

Especially designed to a strict specification. Only the finest components have been used and the latest solid state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast.

STABILISED POWER MODULE SPM80

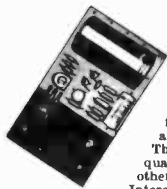

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watt (r.m.s.) per channel simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size: 63mm × 105mm × 30mm. These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including:—Disc Systems, Public Address, Intercom Units, etc. Handbook available 10p PRICE £3-25

TRANSFORMER BMT80 £2-15 p. & p. 28p

STEREO PRE-AMPLIFIER TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL60 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages. Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



SPECIFICATION

Frequency Response	20Hz-20KHz ± 1dB
Harmonic Distortion	better than 0.1%
Inputs: 1. Tape Head	3.25 mV into 50K Ω
2. Radio, Tuner	75 mV into 50K Ω
3. Magnetic P.U.	3 mV into 50K Ω
All Input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB. from 20Hz to 20KHz.	
Bass Control	± 15dB at 20Hz
Treble Control	± 15dB at 20KHz
Filters: Rumble (High Pass)	100Hz
Scratch (Low Pass)	8KHz
Signal/Noise Ratio	better than -65dB
Input overload	+ 26dB
Supply	+ 35 volts at 20mA
Dimensions	292mm × 82mm × 35mm

ONLY £13-15

MK 60 AUDIO KIT

Comprising: 2 × AL60, 1 × SPM80, 1 × BTM80, 1 × PA 100, 1 front panel, 1 kit of parts to include on-off switch, neon indicator, stereo headphone sockets plus instruction booklets. Complete Price: £28-75 plus 30p postage.

TEAK 60 AUDIO KIT

Comprising: Teak veneered cabinet size 16 1/2" × 11 1/2" × 3 1/2", other parts include aluminium chassis, heatsink and front panel bracket, plus back panel and appropriate sockets, etc. Kit price: £29-95 plus 30p postage.

Giro No. 388-7006

Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE · HERTS.

Postage and packing add 15p. Overseas add extra for airmail. Minimum order 55p. Cash with order please.

Guaranteed Satisfaction or Money Back

CRESCENT RADIO LTD.

11-15 & 17 MAYES ROAD, LONDON N22 6TL
(also) 13 SOUTH MALL, EDMONTON, N.9

MAIL ORDER DEPT.
11 MAYES ROAD, LONDON N22 6TL
Phone 888 3206 & (EDM.) 803 1685

ADD LUXURY TO YOUR CAR WITH A MOTOR DRIVEN CAR AERIAL
Spec.: 5 Section
Extended Length 100cm
Length under Fender 40cm
Cable Length 120cm
Supplied complete with Fixing Bracket and plus 25p Control Switch. **£7-50** P. & P.



"CRESCENT BEAT BRITE" SINGLE CHANNEL SOUND TO LIGHT UNIT
This fantastic little box approx. 4" x 3" x 2" when connected to the output of a sound source from 1 to 100 watts produces a psychedelic light display of up to 1000 watts. Complete with a sensitive level control the unit is fixed and cannot harm your amplifier. A Bargain at £7-50 plus 10p.

MINIATURE RELAYS
Brand new range of British made relays, size of: 1 1/2in x 1in x 1in. All top changeovers with 250V 1.5A contacts and suitable for fitting on 0.1in veroboard.
Type Volts Current Ohms
27/A 12V 17mA 700 All
21/A 12V 25mA/A 430 £1-90
12/A 6V 33mA/A 185 each
200/250V Mains Relay
Heavy duty contacts 2,500 ohm coll. All new and unused
D.P.D. D. mains relays 50p, Carr. free. Special quantity £40 per 100 off.

MIDGET MAINS TRANSFORMER
Varnish Impregnated
Size 45mm x 36mm x 31mm
PRI 240V
Sec 3.0-3 100mA
Sec 6.0-6 100mA
Sec 9.0-9 100mA
Sec 12.0-12 100mA
Sec 20.0-20 100mA
£1-23 10p P. & P.

CRESCENT BUBBLE LIGHT SHOW
This budget system compares very favourably with more sophisticated and higher priced models.
Specification:
Projector—150W convection cooled. At 30ft the projected image is 18ft.
Motor—1 rev. per 2 min.
Liquid Wheel—6in diameter multi colour.
The motor is fitted to the projector and can only be purchased as a single unit.
The liquid wheel is our standard model and may be purchased separately.
A bargain at: Projector, £16; Wheel, 25; Total £20. Plus 75p carr.

7in x 4in LOUDSPEAKER
A top quality speaker ideal where small size is important. Manufactured by F.M.I. for a well-known hi-fi set maker. Size: 7in x 4in. Impedance: 8 ohms. Flux: 38,000. Max. Free range: 90Hz to 12kHz. Power handling: 5W. Unbeatable. Price: £1-00. Free postage on this item.

U.K. CARRIAGE 15p UNLESS OTHERWISE STATED
VAT 8% VAT TO BE ADDED TO ALL ORDERS
SEND 20p FOR A CRESCENT CATALOGUE

"CRESCENT" 100 WATT R.M.S. ALL PURPOSE AMPLIFIER U. BUILD IT

We supply the three modules for you to build this Disco-Group-P.A. amplifier into the cabinet of your choice.

★ THE POWER AMP MODULE
170W r.m.s. sq. wave 300W instantaneous peak into 8 ohm (60W into 16 ohm).

★ THE PRE-AMP MODULE
Four control pre-amp, Vol. Bass, Treble. Middle controls. Designed to drive most amplifiers using F.E.T. first stage.

★ THE POWER SUPPLY
It supplied complete with the mains transformer. Complete fixing instructions are supplied and no technical knowledge is required to connect the three ready wired modules. A fantastic bargain. £25, carr. 75p. Send S.A.E. for further details on this or our ready built amplifiers.

12-0-12V 500M/A
240V primary transformer bargain. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our price £1-20.

18V 500M/A
240V primary. Approx. size: 60mm x 40mm x 50mm; fixing centres: 75mm. Our Price £1 each

BARGAIN BOX
Loud buzzer mounted in a metal box complete with two U2 battery size holder. Designed and can be used as a fire alarm but is ideal as a door or morse code practise buzzer. Approx. size: 2 1/2in x 8 1/2in x 1 1/2in. **OUR PRICE 50p**

ABS PLASTIC BOXES
Handy boxes for construction projects. Moulded extrusion rails for P.C. or chassis panels. Fitted with 1mm front panels. 1005, 105mm x 73mm x 46mm 51p; 1006, 150mm x 76mm x 47mm 66p; 1007, 184mm x 124mm x 60mm 98p; 1021, 106mm x 74mm x 45mm (sloping front) 50p.

BARGAIN BOARDS
Components galore for the experimenter. Es-Computer boards with resistors, capacitors and useful transistors—at least 4 transistors per board. Five boards £1.

2in. PANEL METERS
Size 59mm x 46mm
0-50uA—ME6 0-100mA—ME13
0-100uA—ME7 0-500mA—ME14
0-500uA—ME8 0-1A—ME15
0-1mA—ME9 0-50V a.c.—ME16
0-5mA—ME10 0-300V a.c.—ME17
0-10mA—ME11 8 meter—ME18
0-50mA—ME12 V.U. meter—ME19
£3 each. 10p P. & P.

POWER PACKS
PP1 Switched 3-6-7-9V 400M/A Transistor and Zener Stabilised On/Off switch and Polarity Reversal switch, in a black metal case, £2-25 each.
PP2 Switched 6-7-9V Battery Eliminator. Approx. size 2 1/2in x 2 1/2in x 3 1/2in. Ideal for cassette recorders, £2-75 each (Phillips type £3-00).
PP3 Car converter. From 12V Pos. or Neg. to 6-7-9V. Easy to fit and transistor regulated, £2-50 each.

3 KILOWATTS PSYCHEDELIC LIGHT CONTROL UNIT

Three Channel: Bass, Middle, Treble. Each channel has its own sensitivity control. Just connect the input of this unit to the loudspeaker terminals of an amplifier, and connect three 250V up to 1000W lamps to the output terminals of the unit, and you produce a fascinating sound-light display. (All guaranteed.)
£18-50 plus 38p P. & P.

MINI LOUDSPEAKERS
2 1/2in 8 ohm, 50p; 2 1/2in 40 ohm, 50p. Please include 5p P. & P. on each L.S.

ST VALVE MAIL ORDER CO.

16a WELLFIELD ROAD, LONDON SW16 2BS
SPECIAL EXPRESS MAIL ORDER SERVICE
Express postage 5p for first transistor, 1p thereafter, over ten post free. INTEGRATED CIRCUITS 6p + 1p each added

sp	sp	sp	sp	sp	sp	sp	sp
1N21	0-17	FAZ21	1-15	BY213	0-25	0A2265	0-45
1N23	0-85	AF21	8-00	BY210	0-45	Z8271	0-18
1N85	0-88	ASV26	0-95	BY211	0-40	0A2297	0-45
1N253	0-60	ASV27	0-30	BY212	0-40	0A2208	0-40
0N265	0-60	ASV28	0-25	BY213	0-35	0A2209	0-40
1N846	0-18	ASV29	0-30	BY215	0-25	0A2210	0-40
1N725A	0-20	ASV36	0-25	BY216	0-10	0A2211	0-40
1N914	0-08	ASV50	0-20	BZV88	0-60	0A2222	0-45
1N4007	0-12	ASV51	0-40	C111	0-55	0A2224	0-45
18113	0-25	ASV53	0-30	CR81/05	0-30	0A2241	0-25
18131	0-18	ASV62	0-25	CR81/40	0-45	0A2242	0-15
18202	0-22	ASV66	0-35	CS4B	1-90	0A2244	0-25
2G371	0-40	ASZ21	1-00	CS10B	3-50	0A2246	0-15
2G381	0-22	ASZ23	0-75	1E0000	0-15	0A2290	0-25
2G414	0-30	AU101	1-50	1D0003	0-15	OC16	1-00
2G417	0-25	AU110	0-00	1D0006	0-25	OC18T	1-00
2N404	0-22	BC107	0-12	1D0007	0-40	OC19	0-60
2N997	0-15	BC108	0-12	1D0008	0-38	OC20	2-00
2N998	0-20	BC109	0-12	1D0009	0-38	OC22	1-00
2N706	0-10	BC113	0-18	1D0010	0-38	OC23	1-25
2N706A	0-12	BC115	0-20	1D0011	0-38	OC24	1-10
2N708	0-15	BC116	0-20	1D0012	0-38	OC25	1-00
2N709	0-40	BC118	0-20	1D0013	0-38	OC28	0-40
2N1091	0-45	BC119A	0-20	1D0014	0-38	OC28	0-40
2N1131	0-25	BC121	0-20	1D0015	0-38	OC28	0-40
2N1132	0-25	BC122	0-20	1D0016	0-38	OC29	0-85
2N1302	0-18	BC122	0-20	1D0017	0-38	OC30	0-40
2N1303	0-18	BC125	0-68	1D0018	0-38	OC35	0-85
2N1304	0-22	BC126	0-65	1D0019	0-38	OC36	0-85
2N1305	0-22	BC140	0-55	1D0020	0-38	OC41	0-40
2N1306	0-28	BC148	0-10	1D0021	0-38	OC42	0-40
2N1307	0-28	BC149	0-12	1D0022	0-38	OC43	0-70
2N695	0-20	BC157	0-14	1D0023	0-38	OC44	0-18
2N1447	0-75	BC158	0-12	1D0024	0-38	OC44M	0-17
2N1448	0-60	BC160	0-63	1D0025	0-38	OC45	0-18
2N1600	1-00	BC169	0-14	1D0026	0-38	OC45M	0-18
2N2218	0-28	BCY3	1-50	1D0027	0-38	OC46	1-00
2N2219	0-25	BCY32	1-20	1D0028	0-38	OC47	0-60
2N3369A	0-18	BCY33	0-38	1D0029	0-38	OC48	0-60
2N2444	1-99	BCY34	0-45	1D0030	0-38	OC49	0-60
2N2613	0-28	BCY38	0-85	1D0031	0-38	OC50	0-60
2N2646	0-60	BCY38	0-85	1D0032	0-38	OC51	0-60
2N2904	0-20	BCY39	1-00	1D0033	0-38	OC52	0-60
2N2904A	0-25	BCY40	0-10	1D0034	0-38	OC53	0-60
2N2906	0-25	BCY70	0-15	1D0035	0-38	OC54	0-60
2N2907	0-25	BCY71	0-20	1D0036	0-38	OC55	0-60
2N2924	0-18	BCZ10	0-60	1D0037	0-38	OC56	0-60
2N2925	0-15	BCZ11	0-65	1D0038	0-38	OC57	0-60
2N2926	0-10	BD121	1-00	1D0039	0-38	OC58	0-60
2N3064	0-60	BD123	1-00	1D0040	0-38	OC59	0-60
2N3055	0-40	BD126	0-80	1D0041	0-38	OC60	0-60
2N3702	0-11	BDY11	1-45	1D0042	0-38	OC61	0-28
2N3705	0-15	BF115	0-22	1D0043	0-38	OC62	0-28
2N3706	0-11	BF117	0-10	1D0044	0-38	OC63	0-28
2N3707	0-13	BF171	0-60	1D0045	0-38	OC64	0-28
2N3709	0-10	BF172	0-25	1D0046	0-38	OC65	0-28
2N3710	0-11	BF173	0-25	1D0047	0-38	OC66	0-28
2N3711	0-11	BF184	0-25	1D0048	0-38	OC67	0-28
2N3711	0-11	BF184	0-25	1D0049	0-38	OC68	0-28
2N3819	0-85	BF183	0-22	1D0050	0-38	OC69	0-28
2N4299	0-20	BF194	0-13	1D0051	0-38	OC70	0-28
2N5027	0-43	BF195	0-13	1D0052	0-38	OC71	0-28
2N5088	0-33	BF196	0-15	1D0053	0-38	OC72	0-28
28201	0-59	BF197	0-15	1D0054	0-38	OC73	0-28
28204	1-15	BF197	0-15	1D0055	0-38	OC74	0-28
28501	0-75	BF198	0-15	1D0056	0-38	OC75	0-28
28503	1-00	BF198	0-15	1D0057	0-38	OC76	0-28
AA129	0-20	BF212	0-35	1D0058	0-38	OC77	0-28
AAZ12	0-75	BF213	0-25	1D0059	0-38	OC78	0-28
AAZ13	0-10	BF214	0-20	1D0060	0-38	OC79	0-28
AC107	0-35	BF215	0-25	1D0061	0-38	OC80	0-28
AC126	0-25	BF216	0-20	1D0062	0-38	OC81	0-28
AC127	0-25	BF217	0-20	1D0063	0-38	OC82	0-28
AC128	0-20	BF218	0-20	1D0064	0-38	OC83	0-28
AC187	0-20	BF219	0-25	1D0065	0-38	OC84	0-28
AC188	0-20	BF220	0-25	1D0066	0-38	OC85	0-28
AC189	0-25	BF221	0-25	1D0067	0-38	OC86	0-28
AC190	0-25	BF222	0-25	1D0068	0-38	OC87	0-28
AC191	0-25	BF223	0-25	1D0069	0-38	OC88	0-28
AC192	0-25	BF224	0-25	1D0070	0-38	OC89	0-28
AC193	0-25	BF225	0-25	1D0071	0-38	OC90	0-28
AC194	0-25	BF226	0-25	1D0072	0-38	OC91	0-28
AC195	0-25	BF227	0-25	1D0073	0-38	OC92	0-28
AC196	0-25	BF228	0-25	1D0074	0-38	OC93	0-28
AC197	0-25	BF229	0-25	1D0075	0-38	OC94	0-28
AC198	0-25	BF230	0-25	1D0076	0-38	OC95	0-28
AC199	0-25	BF231	0-25	1D0077	0-38	OC96	0-28
AC200	0-25	BF232	0-25	1D0078	0-38	OC97	0-28
AC201	0-25	BF233	0-25	1D0079	0-38	OC98	0-28
AC202	0-25	BF234	0-25	1D0080	0-38	OC99	0-28
AC203	0-25	BF235	0-25	1D0081	0-38	OC100	0-28
AC204	0-25	BF236	0-25	1D0082	0-38	OC101	0-28
AC205	0-25	BF237	0-25	1D0083	0-38	OC102	0-28
AC206	0-25	BF238	0-25	1D0084	0-38	OC103	0-28
AC207	0-25	BF239	0-25	1D0085	0-38	OC104	0-28
AC208	0-25	BF240	0-25	1D0086	0-38	OC105	0-28
AC209	0-25	BF241	0-25	1D0087	0-38	OC106	0-28
AC210	0-25	BF242	0-25	1D0088	0-38	OC107	0-28
AC211	0-25	BF243	0-25	1D0089	0-38	OC108	0-28
AC212	0-25	BF244	0-25	1D0090	0-38	OC109	0-28
AC213	0-25	BF245	0-25	1D0091	0-38	OC110	0-28
AC214	0-25	BF246	0-25	1D0092	0-38	OC111	0-28
AC215							

CHROMASONIC electronics

Dept. 2
56, Fortis Green Road, London, N10 3HN.
telephone: 01-883 3705

INDUCTORS

Denco Maxi-Q Coils

Ferrite Rod Aerials



FRA1 Long & Medium Wave band (300pf) 86p
FRA2 Long & Medium (500pf) 86p

Tuning Coils in two series:

Range		
1	150 kHz to	400 kHz
2	515 kHz to	1.545 MHz
3	1.67 MHz to	5.3 MHz
4	5 MHz to	15 MHz
5	10.5 MHz to	31.5 MHz
6	30 MHz to	50 MHz
7	45 MHz to	78 MHz

* 50 pf tuning, all others based on 300 pf.

Series A Transistor - 48p each

Only available in ranges 1 to 5 inc.

4 Coils complete each range:

Blue	Aerial Coil
Yellow	R.F. Interstage
Red	Osc. Coil for 465 kHz I.F.
White	Osc. Coil for 1.6 MHz I.F.

give range number ; letter 'T' and colour.

Series B Dual Purpose Coils 48p each

For FET or Valve Circuits

All ranges available

5 Coils complete each range:


Blue	Aerial
Yellow	Interstage R.F.
Green	R.F. plus reaction
Red	Osc. Coil for 465 kHz I.F.
White	Osc. Coil for 1.6 MHz I.F.

(Note use Red instead of White for ranges 6 & 7.)

Chokes



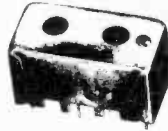We stock from 1 µH to 19 mH
Check levels & prices when ordering



Tuned Block Filter incorporating a Ceramic element. Pre-aligned to 470 KHz. 3db bandwidth 5K Hz. Zin 100K. Zout 100K.
LP1175 £1.46

I.F. Transformers

IFT 13	465 kHz 1st & 2nd d/tuned	65p
IFT 14	465 kHz Final single tuned	65p
IFT 15	10.7 MHz d/tuned	65p
IFT 16	1.6 MHz 1st & 2nd d/tuned	65p
IFT 17	1.6 MHz Final v/tuned	65p
IFT 18	465 kHz or 1.6 MHz d/tuned	75p

TUNING CONDENSERS

TYPE E



3 gang 310pf
£3.99

TYPE CB04



5pf 80p
10pf 80p
15pf 80p
20pf 80p
25pf 80p
30pf 80p
40pf 94p
75pf 94p
100pf 99p

TYPE OO



208 + 176 pf with screen & trimmers
£1.48

DILECON



100pf 69p
300pf 69p
500pf 69p

TYPE O



365 pf £1.07
365 x 365 pf £1.30

VEROBOARD



	COPPERCLAD	PLAIN	EXTRA
0.1"	0.15"	0.15"	P&P
2 1/2" x 1"	7p	7p	-
2 1/2" x 3 1/2"	26p	21p	12p
2 1/2" x 5"	30p	25p	13p
3 1/2" x 3 1/2"	30p	25p	-
3 1/2" x 5"	34p	34p	25p
17" x 2 1/2"	90p	69p	45p
17" x 3 1/2"	£1.21	75p	57p
17" x 5"	-	-	99p

D.I.P., Breadboard 4.15" x 6.15" £1.40
VEROSTRIP (State .1" or .15") 30p
Pin Insertion Tool (State .1" or .15") 63p
Spot Face Cutter £25.28
Terminal Pins In Pkts. of 50 (State .1" or .15") 22p

Details of I.C.'s; Rectifiers; Diodes; Bridges; Passive Components; LED's; Clocks; Triacs etc. can be seen on other pages and/or issues of Wireless World; Practical Wireless; and Practical Electronics.

DIODES

AA119	10p	BY103	22p	0A91	8p
AA120	10p	BY105	16p	0A200	11p
AA129	10p	BY126	16p	0A202	12p
BA100	10p	BY127	16p	ZS120	8p
BA102	27p	BY133	23p	ZS140	25p
BA110	44p	BY164	54p	ZS141	42p
BA115	19p	BY176	£1.62	ZS142	32p
BA144	20p	BY182	£1.62	ZS170	10p
BA145	22p	BZ250	27p	ZS270	11p
BA148	22p	BZ270	27p	ZS271	16p
BA154	20p	Series		ZS278	36p
BA155	15p	BZ198	11p	IN914	8p
BAX16	10p	0A47	11p	IN4009	7p
BB104	45p	0A79	10p	IN4148	5.3p
BB105B	41p	0A81	8p	IN4448	8p
BY100	16p	0A85	10p	1Z5 Series	19p
		0A90	8p		

TRANSISTORS

AC107	14p	BC213L	13p	D13V	52p	ZTX301	13p	2N3707	12p
AC126	13p	BC214L	13p	D40N3	59p	ZTX302	17p	2N3708	10p
AC127	13p	BC268	15p	MJ480	93p	ZTX303	14p	2N3709	10p
AC128	13p	BC407	16p	MJ481	£1.18	ZTX304	21p	2N3710	11p
AC176	15p	BCY70	17p	MJ490	£1.01	ZTX311	10p	2N3711	11p
AC187	22p	BCY71	22p	MJ491	£1.42	ZTX312	10p	2N3712	£2.00
AC187K	20p	BCY72	17p	MJ900	£1.42	ZTX341	22p	2N3791	£2.35
AC188	22p	BD115	73p	MJ1000	£1.22	ZTX384	16p	2N3819	27.5p
AC188K	25p	BD123	89p	MJ2955	£1.88	ZTX500	12p	2N3821	81p
ACY17	39p	BD124	90p	MJ3055	£1.21	ZTX501	13p	2N3829	99p
ACY17	38p	BD131	44p	MJ4000	£1.46	ZTX502	17p	2N3903	16p
ACY20	22p	BD132	52p	MJ4010	£1.95	ZTX503	16p	2N3904	19p
AD140	48p	BD131/2PR	£1.17	MJE340	45p	ZTX504	42p	2N3905	23p
AD149	48p	BD135	41p	MJE350	97p	ZTX531	22p	2N3906	15p
AD161	37p	BD136	43p	MJE2955	£1.20	ZTX550	17p	2N4056	23p
AD162	38p	BD201	£1.95	MJE3055	72p	2N697	16p	2N4059	19p
AD161/62MP	74p	BD202	£1.46	MPF102	27p	2N706	13p	2N4062	57p
AF114	17p	BF109	74p	MPF103	40p	2N708	16p	2N4289	19p
AF115	17p	BF115	25p	MPF104	44p	2N714	24p	2N4441	85p
AF116	17p	BF160	25p	MPF105	44p	2N930	22p	2N4442	£1.04
AF117	17p	BF167	24p	MPF106	49p	2N1302	20p	2N4443	£1.42
AF118	54p	BF173	24p	MPF111	22p	2N1303	24p	2N4444	£2.06
AF124	32p	BF178	28p	MPSU06	63p	2N1304	24p	2N4871	59p
AF139	34p	BF179	32p	MPSU56	77p	2N1305	24p	2N4901	£1.41
AF172	25p	BF180	32p	OC28	49p	2N1306	24p	2N5067	£1.07
AF239	40p	BF181	32p	OC35	49p	2N1307	27p	2N5129	27p
ASV26	32p	BF184	27p	OC36	49p	2N1308	34p	2N5172	11p
BC108	11p	BF185	27p	OC44	14p	2N1309	34p	2N5191	77p
BC109	12p	BF195	17p	OC45	14p	2N1711	26p	2N5194	91p
BC117	22p	BF196	16p	OC72	14p	2N1893	52p	2N5295	52p
BC147	10p	BF197	16p	OC75	15p	2N1818	22p	2N5449	16p
BC148	10p	BF200	31p	OC76	27p	2N1219	38p	2N5457	46p
BC149	10p	BF244B	27p	OC81	14p	2N1266	54p	2N5458	43p
BC157	13p	BF262	25p	OC83	25p	2N2694	97p	2N5459	43p
BC158	12p	BF263	25p	OC170	27p	2N2904	32p	2N5485	52p
BC159	14p	BF272	£1.19	OC171	32p	2N2905	30p	2N5777	48p
BC167	17p			OC171	32p	2N2924	14p	2N6068	44p
BC168	11p	BF597	23p	ORP12	65p	2N2925	18p	2N6069	51p
BC169	12p	BF598	20p	TIP29	53p	2N2926G	10p	2N6070	57p
BC171	20p	BFW10	65p	TIP31	67p	2N3053	19p	2N6071	62p
BC172	17p	BFX29	49p	TIP31A	67p	2N3054	50p	2N6073	67p
BC177	22p	BFX68	25p	TIP32A	79p	2N3054	51p	2N6075	£1.46
BC178	22p	BFY50	22p	TIP41A	79p	2N3375	£3.56	2N6076	161p
BC179	24p	BFY51	22p	TIP42A	97p	2N3442	£1.19	2N6111	54p
BC182L	11p	BFY90	£1.09	TIS43	30p	2N3566	16p	2N6288	60p
BC183L	12p	BR100	42p	TIS88A	36p	2N5638	20p	2N1400	99p
BC184L	12p	BRY39	43p	TIS91	32p	2N3702	13p	3N1411	87p
BC187	27p	BXS20	18p	ZTX107	10p	2N3703	12p	3N1513	87p
BC204	14p	BXS21	22p	ZTX108	10p	2N3704	13p	40321	54p
BC209	14p	BYS95A	14p	ZTX109	15p	2N3705	12p	40330	£1.39
BC212L	12p	BU105/02	£1.95	ZTX300	12p	2N3706	14p	40573	55p


Electrolytics

I.F.	4V	6.3V	10V	16V	25V	40V	63V	100V	160V	450V
1								8p		15p
1.5								6p		6p
2.2								6p		6p
3.3								6p		6p
4.7								8p		17p (4uF)
6.8								6p		6p
8								6p		8p
15								6p		8p
18								6p		8p
22								6p		11p
33								6p		6p
47								6p		8p
68								6p		11p
100								6p		8p
150								6p		11p
220								6p		14p
330								6p		11p
470								8p		25p
680								10p		25p
1000	13p							14p		25p
								19p		25p
								25p		33p (32uF)
								25p		25p (50uF)
								44p		350V
								68p		

R T V C FOR AUDIO ON A BUDGET

PUSH BUTTON CAR RADIO KIT

The Tourist II

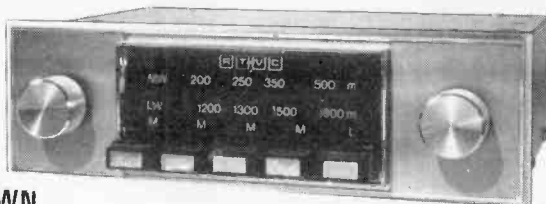

**NO SOLDERING
REQUIRED!**

NOW BUILD YOUR OWN PUSH BUTTON CAR RADIO

Easy to assemble construction kit comprising fully completed and tested printed circuit board on which no soldering is required. All connections are simple push fit type making for easy assembly. Fine tuning push button mechanism is fully built and tested to mate with printed circuit board.

Car Radio Kit £7.70 + 55p p & p

The Tourist I Kit For the experienced constructor
If you can solder on a printed circuit board you can build this model. Same technical specification as Tourist II
Price £6.60 + 55p p & p.

Technical specification:

- (1) **Output** 4 watts R.M.S. output. For 12 volt operation on negative or positive earth.
- (2) **Integrated circuit** output stage, pre-built three stage IF Module.

Controls volume manual tuning and five push buttons for station selection, illuminated tuning scale covering full, medium and long wave bands.

Size chassis 7" wide, 2" high and 4 1/4" deep approx

Speaker including baffle and fixing strip **£1.65+23p.p&p.**

Car Aerial Recommended — fully retractable

£1.37+20p. postage & packing



* STEREO 21 QUALITY SOUND FOR LESS THAN £20.00

Stereo 21, easy to assemble audio system kit. No soldering required.

The unit is finished in white P.V.C. and the acrylic top presents an unusually interesting variation on the modern deck plinth.

Includes: — **BSR 3 speed deck**, automatic, manual facilities together with ceramic cartridge.

Two speakers with cabinets.

Amplifier module. Ready built with control panel, speaker leads and full, easy to follow assembly instructions.

Specifications: For the technically minded:—

Input sensitivity 600mV. Aux. input sensitivity 120mV. Power output 2.7 watts per channel.

Output impedance 8–15 ohms. Stereo headphone socket with automatic speaker cutout. Provision for auxiliary inputs — radio, tape, etc., and outputs for taping discs. **Overall Dimensions.** Speakers approx. 15 1/2" x 8" x 4".

Complete deck and cover in closed position approx. 15 1/2" x 12" x 6".

Complete only £19.95 + £1.60 p & p. Extras if required. **Optional Diamond Styli £1.37.**

Specially selected pair of stereo headphones with individual level controls and padded earpieces to give optimum performance. **£3.85.**



BUILD YOUR OWN * STEREO AMPLIFIER

For the man who wants to design his own stereo — here's your chance to start with Unisound — pre-amp, power amplifier and control panel. No soldering — just simply screw together. 4 watts per channel into 8 ohms. Inputs: 120mV (for ceramic cartridge). The heart of Unisound is high efficiency I.C. monolithic power chips which ensure very low distortion over the audio spectrum. 240V. AC only.

£7.64 + 55p p & p

8 TRACK HOME CARTRIDGE PLAYER *



Elegant self selector push button player for use with your stereo system.

Compatible with Viscount III system,

Unisound module and the Stereo 21.

Technical specification Mains input,

240V. Output sensitivity 125mV

Comparable unit sold elsewhere at

£24.00 approx. Yours for only

£11.95 + 90p p & p.

COMPLETE* STEREO SYSTEM



System 1. £51.00

40 Watt Amplifier. Viscount III - R102 now 20 watts per channel.

System 1 includes:

Viscount III amplifier - volume, bass, treble and balance controls, plus switches for mono/stereo on/off function and bass and treble filters. Plus headphone socket.

Specification

20 watts per channel into 8 ohms. Total distortion @ 10W @ 1kHz 0-1%. P.U.1 (for ceramic cartridges) 150mV into 3 Meg. P.U.2 (for magnetic cartridges) 4mV @ 1kHz into 47K. equalised within -1dB R.I.A.A. Radio 150mV into 220K. (Sensitivities given at full power). Tape out facilities: headphone socket, power out 250mW per channel. **Tone controls and filter characteristics.** Bass: +12dB to -17dB @ 60Hz. Bass filter: 6dB per octave cut. Treble control: treble +12dB to -12dB @ 15kHz. Treble filter: 12dB per octave. **Signal to noise ratio:** (all controls at max.) -58dB. Crosstalk better than 35dB on all inputs. Overload characteristics better than 26dB on all inputs. Size approx. 13 3/4" x 9" x 3 3/4".

Garrard SP 25 Mk III deck with magnetic cartridge, de luxe plinth and hinged cover.

Two Duo Type II matched speakers - Enclosure size approx. 17 1/2" x 10 3/4" x 6" in simulated teak. Drive unit 13" x 8" with parasitic tweeter. 10 watts handling.

Complete System £51.00

System 2. £69.00

Viscount III amplifier (As System 1)

Garrard SP 25 Mk III deck (As System 1)

Two Duo Type III matched speakers - Enclosure size approx. 27" x 13" x 11 1/2"

Finished in teak veneer. Drive units 13" x 8" bass driver, and two 3" (approx.) tweeters.

20 watts R.M.S., 8 ohms frequency range - 20 Hz to 18,000 Hz.

Complete System £69.00

PRICES: SYSTEM 1

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type II speakers	£14.00 + £2.20 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£59.20

Available complete for only:

£51.00 + £3.50 p & p


PRICES: SYSTEM 2

Viscount III R102 amplifier	£24.20 + £1 p & p
2 Duo Type III speakers	£39.00 + £4.00 p & p
Garrard SP 25 with Mag. cartridge de luxe plinth and hinged cover	£21.00 + £1.75 p & p
total:	£84.20

Available complete for only:

£69.00 + £4.00 p & p

EMI SPEAKERS AT FANTASTIC REDUCTIONS

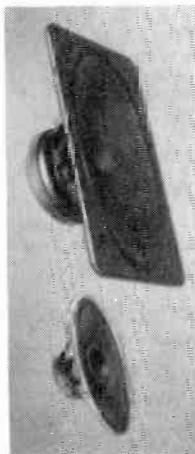

20 WATT SPEAKER SYSTEM

System consists of a 13" x 8" (approx) elliptical woofer unit with a 8" x 5" (approx.) mid range unit incorporating parasitic tweeter and crossover components.

Technical Specification:

Bass Unit

Flux density-100 K, speech coil-1 1/2"

Cone, Triple laminated paper with P.V.C. surround.

Mid Range Unit

Flux density-33K, speech coil-1" with parasitic tweeter.

Power Handling

20 watts R.M.S., impedance - 8 ohms, frequency response - 20 Hz to 18,000 Hz.

OUR PRICE

£6.60. Complete

+ 90p p & p.




15" 14A/780 BASS UNIT

Bass unit on a rigid diecast chassis. Superior cone material handles up to 50 watts RMS, and is treated to give a smooth frequency response. Resonance 30 Hz, flux density 360,000 Maxwells. Impedance at 1 kHz is 8 ohms. 3" voice coil.

Recommended retail price £40.80.

OUR PRICE £18.70 + £1.50 p&p

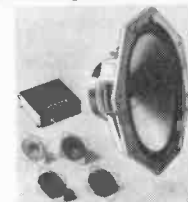

950 KIT

Five matched speakers and crossover unit for handling up to 45 watts, frequency response from 20 to 20,000 Hz.

Huge 19" x 14" (approx.) high efficiency Bass-Speaker with 16,500-gauss magnet built on a heavy diecast frame.

The four 10,000 gauss tweeters, each 3 1/2" dia. approx., are fed by the crossover which critically adjusts signal for maximum fidelity. Impedance at 1 kHz is 8 ohms. Bass coil 2", others 0.5" Recommended list price £44.00.

Special Offer

OUR PRICE £19.50 + £1.50 p&p

FOR DISCO PAGE AND DETAILS OF HOW TO ORDER - TURN OVER...




PORTABLE DISCO CONSOLE

INCORPORATES: Pre-Amp with full mixing facilities, including switched input for mic with volume control, switched input for auxiliary with volume control, bass and treble controls, volume control and blend control for turntables.

Two B.S.R. single play professional series decks, fitted with crystal cartridges.

The turntables are designed and precision engineered. They combine clean modern styling with superb reproduction. Their many special features include square section aluminium tonearms, (high precision low mass design fully counterbalanced, with calibrated stylus pressure control for perfect tracking), and conveniently grouped easy to read linear controls. The turntables have viscous cueing devices which allows the tonearms to be placed or lifted at any point on the record.

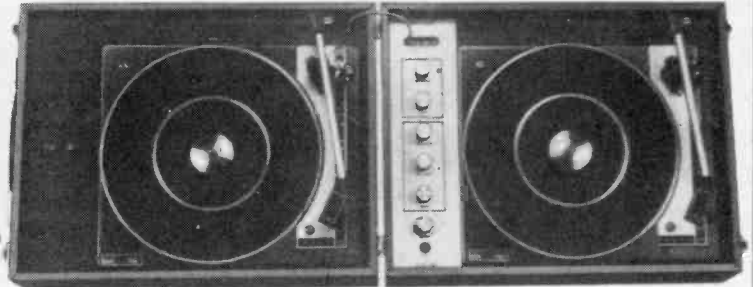The two lightweight cartridge shells have slide-in-holders to facilitate easy inspection of needles and cartridges.



TECHNICAL SPECIFICATION:

Pre-amp - Output - 200mV. Auxiliary inputs - 200mV and 750mV into 1 meg. Mic input - 6mV into 100K. 240 volt operation.

Turntables capacity - 7", 10" or 12" records.

Rumble, wow and flutter - Rumble - Better than -35dB. Wow - Better than 0.2%. Flutter - Better than 0.06% (Gaugmont kalee meter).

Finish - Satin black mainplate with black turntable mat inlaid with brushed aluminium trim. Tonearm and controls in black and brushed aluminium.

Console size - Unit Closed - 17 1/2" x 13 1/2" x 8 1/2" (approx.)
Unit Open - 35 1/2" x 13 1/2" x 4 1/2" (approx.)

This disco console is ideally matched for the Reliant IV and Disco 50 or any other quality amplifier.

The unit is finished in black PVC with contrasting simulated teak edging diamond spun control knobs with matching control panel.

Yours for only £45.00 + £3.50 P. & P.

DISCO 50



45 WATT R.M.S. MONO DISCOTHEQUE AMPLIFIER

Ideal for Disco Work. Output Power: 45 watts R.M.S. Frequency Response 3dB points 30Hz and 18KHz. Total Distortion: less than 2% at rated output. Signal to noise ratio: better than 60dB. Bass Control Range: 13dB at 60Hz. Treble Control Range: 12dB at 10KHz. Inputs: 4 inputs at 5mV into 470K. Each pair of inputs controlled by separate volume control. 2 inputs at 200mV into 470 K. Size: 19 1/4" x 10 1/2" x 8" (approx.) Amplifier £27.50 + £1.50 p. & p.



DISCO AMPLIFIER

Reliant Mk IV Mono Amplifier, ideal for the small disco or house parties. Outputs 20 watts R.M.S. into 8 ohms (suitable for 15 ohms).

Inputs *4 electrically mixed inputs. *3 individual mixing controls.

*Separate bass and treble controls common to all 4 inputs.

*Mixer employing F.E.T. (Field Effect Transistors) *Solid State circuitry.

*Attractive styling.

INPUT SENSITIVITIES

-Input - 1.) Crystal mic, guitar or moving coil mic, 2 and 10mV. (Selector switch for desired sensitivity).

-Inputs - 2), 3), 4). Medium output equipment - ceramic cartridge, tuner, tape recorder, organs, etc. - all 250mV sensitivity. AC Mains, 240V operation. Size approx: 12 1/2" x 6" x 3 1/2".

£15.00 + 60p. post & pack.



Mail orders to Acton. Terms C.W.O. All enquiries Stamped Addressed Envelope. Goods not despatched outside U.K. All prices include VAT at 8% rate

DO NOT SEND YOUR CARD

Just write your order giving your credit card number

Leaflets available for all items listed thus ✖
Send stamped addressed envelope.



Radio and TV Components (Acton) Ltd.

21 High Street, Acton, London W3 6NG
323 Edgware Road, London W2

Personal _____ Edgware Road: 9a.m.-5.30p.m. Half day Thurs.
Shoppers _____ Acton: 9.30a.m.-5p.m. Closed all day Wed.

SPARKRITE Mk II

Electronic Ignition...

Better on all points Because you keep your points!

The SPARKRITE MK.2 is a full capacitive discharge electronic system. Specifically designed to retain the points assembly with all the advantages and none of the disadvantages. No misfire because contact breaker bounce is eliminated electronically by a pulse suppression circuit which prevents the unit firing if the points bounce open at high rpm. Contact breaker burn is eliminated by reducing the current to about 1/50th of normal, thus avoiding arcing. But you can still revert to normal ignition if need be. In seconds. If points go (very unlikely) you can get replacements anywhere. All these advantages.

- Fitted in 15 minutes. ● Up to 20% better fuel consumption. ● Instant all weather starting. ● Cleans plugs - they last 5 times longer without attention. ● Faster acceleration. ● Faster top speeds. ● Coil and battery last longer. ● Efficient fuel burning with less air pollution.

The kit comprises everything needed

Ready drilled scratch and rust resistant case, metalwork, cables, coil connectors, printed circuit board, top quality 5 year guaranteed transformer and components. Full instructions to make positive or negative earth system, and 6 page installation instruction leaflet.

WE SAY IT IS THE BEST SYSTEM AT ANY PRICE!

PRICES

D.I.Y. Kit only £10.93 incl. VAT and P & P
Ready Built Unit £13.88 incl. VAT and P & P
(Both to fit all cars with coil/distributor ignition up to 8 cylinder)

We can supply units for any petrol-engined vehicle (boat, motorcycle etc) with coil/contact breaker ignition. Details on request. Call in and see us for a demonstration

ELECTRONICS DESIGN ASSOCIATES

(Dept PE1), 82 Bath Street, Walsall WS1 3DE Phone 33652

In a test comparing eight electronic ignition systems, conducted by Popular Motoring, Sparkrite came out best.



BI-PRE-PAK

Audio Bargains

STEREO DECODER

£4.50

incl. P. & P.

Ready-built unit, ready for connection to the IF stages of existing FM Radio or Tuner. The very latest 2nd Generation rail less integrated circuit design, operating on this phase locked loop system, offering even better stereo separation.

Only owing to our bulk buying capacity are we able to offer this at the old price. LED stereo indicator lights available. RED at 25p; GREEN at 40p


3 W.R.M.S. I.C. AMP

only £1.50


incl. P. & P.
Order Code I.C.A.1.

On P.C. Board with all components or 2 on one board for £2.60. Order Code I.C.A.1/5.

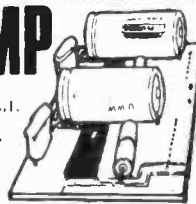These amps. are supplied with a free booklet on connecting up, specifications and easy-to-build projects using the I.C.A.1.



5W & 10W AMPS

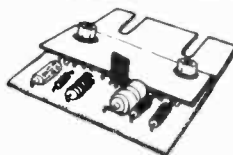

5W ONLY £1.80

10W ONLY £2.26

incl. P. & P.

These matchbox size amplifiers have an exceptionally good tone and quality for the price. They are only 2 1/4 in x 1 1/2 in. The 5W Amp will run from a 12V car battery making it very suitable for portable voice reinforcement such as public functions. Two amplifiers are ideal for stereo. Complete connection details and treble, bass, volume and balance control circuit diagrams are supplied with each unit. Discounts are available for quantity orders. More details on request. Cheapest in the U.K. Built and tested.

Now available for 5 & 10W AMPS

Pre-assembled printed circuit boards 2in x 3in available in stereo only, will fit 0-15 edge connector.

Stereo Pre-Amp 1 (Pre 1). This unit is for use with low gain or ceramic pick-up cartridges. **£1.10**

Stereo Pre-Amp 2 (Pre 2). This unit is for use with magnetic pick-up cartridges. **£1.55**

Stereo Tone Control (STC). This unit is an active tone control board and when used with the right potentiometers will give bass and treble boost and cut. **£1.10**

Instruction leaflet supplied with all units. Post and packing included in prices.

PLEASE ADD VAT AT CURRENT RATE

I enclose £.....for
.....Decoders/.....3W Amps/.....5W Amps
.....10W Amps/.....Stereo Pre-Amps 1
.....Stereo Pre-Amps 2.....Stereo Tone Controls
(Please insert quantities and delete those not applicable).

Name

Address

BI-PRE-PAK

Dept. A, 222/224 West Road,
Westcliff-on-Sea, Essex SS0 9DF.
Telephone: Southend (0702) 46344.

CJL PRICES INCLUDE P&P AND V.A.T.

AERIAL, telescopic, 15-120cm. £1.20

AERIAL, telescopic, h and v swivel, 15-80cm. £1.78

EARPHONE, stethoscope style, 8 ohm dynamic. £1.00

HAND DRILL, (Leytool), Compact precision drill .5/16" chuck. Gears totally enclosed, S/L bearings. £2.90

INTEGRATED CIRCUITS

AUDIO POWER AMPLIFIER (National) LM380 £1.00

A.M. RADIO RECEIVER (RCA) CA3123E £1.40

F.M. STEREO DECODER (Motorola) MC1310P £2.80

I/C TIMER (Signetics) NE555V £0.78

I.L. SOCKETS (pk of 3) 8 pin £0.50 14 pin £0.55

KEYNECTOR, rapid connect-single/multiple leads to mains. Built-in piano switches, neon & 13A fuse. £3.20

MICROPHONE, lightweight dynamic, remote start/stop 200 ohms, 100-10,000Hz, 6mV average output. £1.80

MULTIMETER, small and attractive, Vdc-10, 50, 250, 1,000. Vac-10, 50, 250, 1,000. Idc-100mA. R-150k. £4.95

POWER SUPPLY COMPONENTS

SILICON BRIDGE RECTIFIER, 100 P.I.V./2A £0.40

ELECTROLYTIC CAPACITOR, 2,200uF/50V £0.57

ELECTROLYTIC CAPACITOR, 5,000uF/25V £0.63

SILICON POWER TRANSISTOR, 2N3055 £0.60

VOLTAGE REGULATOR (Fairchild) uA7805 £1.70

VOLTAGE REGULATOR (Signetics) NE550A £0.80

SIGNAL INJECTOR produces audio through video signals, excellent servicing amplifiers, radios, televisions, etc. £3.92

SOLDERING IRON, 25 WATT, (Antex), X25, 240V, Very low leakage, 1/8" long life bit (interchangeable). £1.85

3/32" bit £0.45 3/16" bit £0.45 Element £0.95

STAND, (Antex), ST3, High grade base, chrome plated spring, sponges and accommodation for spare bits. £0.95

SPEAKER, miniature, 8 ohms, 70mm dia. £0.80

CJL

CJL LTD. P.O. BOX 34, CANTERBURY, CT1 1YT



FREE RESIST COATED CIRCUIT BOARD

For every order placed for any of the products listed below, each order will receive a piece of fibre glass circuit board, approx. size 6in x 6in, coated with negative resist.

DRILLING MACHINES AND DRILL KITS

Specially designed for engineers, lab workers, jewellers, engravers, sculptors, model makers and hobbyists. These powerful, low power, drilling machines are capable of drilling holes up to 3mm in diameter in any material. They will DRILL, SAW, GRIND, BURR, BRUSH AND POLISH.

Reliant Drill with 3 collets, 9,000 r.p.m. £3-68 (50p).

Reliant Drill Kit as illustrated 3 collets, 20 tools £8-34 (97p).

Drill Stand, used horizontally or vertically for drilling, sawing, buffing, or as a miniature lathe for turning small components between centres £8-34 (97p).

MAJOR DRILL KIT "for the man with everything". Contains 9,000 r.p.m. super drill, power unit, drill stand, 40 assorted tools, presentation box, normally £34-76 only £27-81 (£3-22).

SOLDERLESS MODULAR BREADBOARDS

These DEC breadboards are used throughout the world for making prototype and production working circuits. The patented contact allows components to be inserted over and over again without soldering.

S DEC. Discrete components only. Normally £1-98 only £1-32 (25p).

T DEC. Station for one integrated circuit normally £3-63 only £2-43 (39p).

U DEC A. Discrete and I.C. components normally £3-99 only £2-67 (40p).

Each Dec is boxed and has instructions, carriers, plugs, coloured leads are also available.

COPPER CLAD GLASS-FIBRE CIRCUIT BOARD

1/2 in Single sided normally 85p per sq. ft. only 55p per sq. ft. (29p).


1/2 in Double sided normally 93p per sq. ft. only 60p per sq. ft. (30p).

3/4 in Single sided normally £1-52 per sq. ft. only 75p per sq. ft. (31p).

3/4 in Double sided normally £1-60 per sq. ft. only 80p per sq. ft. (31p).

RESIST COATED FIBRE GLASS CIRCUIT BOARD

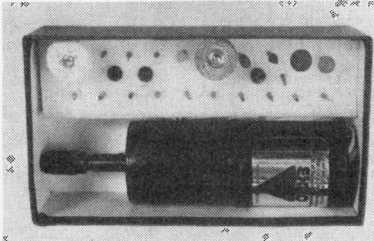Coated with positive or negative resist, we will cut fibre glass board to any size asked for, and will coat with negative or positive resist. The price of resist coated circuit board is 1p per sq. in.



Example positive or negative coated 4 x 3in 12p each + VAT & post. 5 x 5in 25p each + VAT & post. Please quote if positive or negative coated and size. Ferric chloride 5 litre etchant mix £1-50 (35p). Temperature controlled, air agitated etching tank £85-00 (£6-96). Car Radio, L.W., M.W., with speaker £7-50 (64p).

Please add to the sum shown in brackets after the price to cover the cost of post and VAT.

P.B. PRODUCTS LTD.

ELECTRONIC · SCIENTIFIC · INSTRUMENTS

57 HIGH STREET · SAFFRON WALDEN · ESSEX CB10 2DP · ENGLAND


Telephone: Saffron Walden 22876 Telex: 817201



for fast easy reliable soldering
EASY TO USE DISPENSERS AND REELS
IDEAL FOR HOME CONSTRUCTORS

Ersin Multicore Solder contains 5 cores of non-corrosive flux, instantly cleaning heavily oxidised surfaces. No extra flux is required.

SAVBIT handy solder dispenser



A coil of Ersin Multicore Savbit Solder in a dispenser 7ft 6 in of 18 s.w.g. (2.2 metres of 1.22mm). The Solder that reduces the wear of soldering iron bits.

Size 5 32p

SAVBIT solder for general purpose work

A handy plastic reel of SAVBIT alloy. 63ft of 18 s.w.g. (19.2 metres of 1.22mm)



Size 12 £1.72

ALU-SOL for soldering aluminium

New Multicore Alu-sol flux-cored solder in 16 s.w.g. No extra flux needed. Plastic reel holds 36ft. Supplied with full instructions. Also available in solder dispenser.



Size 4 £2.32

Fine gauge solder for soldering small components

Fine gauge solder for soldering small components 138ft of 22 s.w.g. (42.0 metres of 0.71mm) Ersin Multicore 5 core solder wound on a plastic reel. Suitable for intricate work and small components.



Size 10 £1.44

For soldering fine joints

Dispensers of Ersin Multicore Solder make those small jobs easier. 21ft of 22 s.w.g. (6.4 metres of 0.71mm) solder, specially suitable for soldering fine wires, small components and for repairing printed circuits.




Size 15 36p

Or size 19A for Kit wiring or Radio and T.V. repairs 7ft. (2.1 metres) of 18 s.w.g. (1.22mm) Ersin Multicore Solder.

Size 19A 34p

NEW BIB WIRE STRIPPER & CUTTER

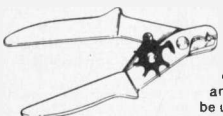

Fitted with unique 8 gauge selector with handle locking device and easy grip handles. Spring incorporated for automatic opening. Strips insulation from flex and cables in seconds and can also be used as a cutter.

Model 8B. 70p

NEW SOLDER WICK



Absorbs solder instantly, from tags and printed circuits. Only needs 40 to 50 Watt soldering iron. Quick and easy to use. Does not need flux and is non-corrosive.

Size 18 90p

Bib Hi-Fi Accessories Limited, Prices shown are recommended retail excluding V.A.T. From Electrical and Hardware Shops. If unobtainable, send 15p P&P. Sole U.K. Sales Concessionaires, P.O. Box 78 Hemel Hempstead, Herts. HP2 7EP. Prices and specifications subject to change without notice.

ELECTROVALUE

Present

APPOINTED STOCKISTS FOR SIEMENS QUALITY PRODUCTS

top quality electronic components for price-minded buyers

112p. CATALOGUE · FREE POSTAGE (U.K.) · ATTRACTIVE DISCOUNTS · SPECS. GUARANTEED

A 100 OF THE BEST

From our transistor stock

2N1307	47p	BC149C	14p
2N2646	51p	BC158B	15p
2N3053	26p	BC159B	15p
2N3054	60p	BC167B	13p
2N3055	60p	BC168B	12p
2N3702	11p	BC169B	15p
2N3703	10p	BC169C	13p
2N3704	11p	BC179B	26p
2N3705	10p	BC182L	26p
2N3794	18p	BC184L	26p
2N3819	25p	BC212L	12p
2N4062	11p	BC214L	14p
2N4443	52p	BC257A	14p
2N5052	42p	BC259B	14p
2N5163	20p	BCY58	30p
2N5459	32p	BD130	90p
40361	48p	BD131	48p
40362	44p	BD132	52p
40602	46p	BF135	37p
40636	46p	BD136	39p
40669	£1-10	BDY20	83p
AC128	17p	BF194	15p
AC151R	23p	BFR39	23p
AC153	27p	BFR79	23p
AC153K	37p	BFX25	33p
AC176	24p	BFX184	27p
AC176K	38p	BFY51	23p
AC187K	31p	BRY38	45p
AC188K	29p	BY164	51p
AD133	£1-92	C106B1	42p
AD136	£1-11	C106D1	62p
AD149	85p	C1406	73p
AD161	42p	MJ481	£1-20
AD182	40p	MJ491	£1-35
AF200U	40p	MJ2955	80p
AF239	60p	MJE371	89p
BI906	36p	MJE521	81p
BA158	31p	MJE2955	£1-12
BB103	24p	MJE3055	64p
BB105	34p	QA91	8p
BB109	48p	SD4	8p
BC107A	15p	TIP31A	70p
BC107B	15p	TIP32A	80p
BC108B	14p	TIP41A	80p
BC108C	14p	TIP42A	£1-00
BC109B	18p	WO2	30p
BC109C	18p	ZTX300	14p
BC147A	12p	ZTX304	23p
BC147B	13p	ZTX500	14p
BC148B	12p	ZTX504	45p

100s MORE IN CATALOGUE 7

BAXANDALL SPEAKER KIT

As designed by P. J. Baxandall and described originally in "Wireless World". Simple to assemble, fantastically good results and a greater money saver. Carries 10 watts RMS, 15 ohms impedance. Size 18in x 12in x 10in. Complete kit, including pack-flat cabinet, £14-80. The size and weight of this product obliges us to charge 70p part cost of carr. in U.K. Equaliser Assembly, £2-30. Loudspeaker Unit 59RM109, £2-45. Cabinet Kit (to Baxandall design), £10-45. Cross-over choke for additional woofer to above, £1-50.

DISCOUNTS

Available on all items except those shown with NETT PRICES. 10% on orders from £5 to £14 99. 15% on orders £15 and over.

FREE POSTAGE

In U.K. for pre-paid mail orders. For mail orders for £2 list value and under there is an additional handling charge of 10p. Overseas orders—carry charge added at cost. Giro A/C No.

38/671/4022

RESISTORS

Code	Watts	Ohms	1 to 9	10 to 99	100 up
C	1/3	4.7-470K	1-3	1-1	0.9 nett
C	1/2	4.7-10M	1-3	1-1	0.9 nett
C	3/4	4.7-10M	1-5	1-2	0.97 nett
C	1	4.7-10M	3-2	2-5	1.92 nett
MO	1/2	10-1M	4	3-3	2.3 nett
WW	1	0-22-3.9Ω	11	10	8 nett
WW	3	1-10K	9	8	6 nett
WW	7	1-10K	11	10	8 nett

Codes:
C = carbon film, high stability, low noise.
MO = metal oxide. Electrosl TR5 ultra low noise.
WW = wire wound, Plessey.

Values: All E12 except C ½W, C ¾W and MO ½W.
E12: 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and their decades.
E24: as E12 plus 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and their decades.

Tolerances:
5% except WW 10% ± 0.05Ω below 10Ω and MO ½W 2%.
Prices are in pence each for quantities of the same ohmic value and power rating. NOT mixed values. (Ignore fractions of one penny on total value of resistor order.) Prices for 100 up in units of 100 only

POTENTIOMETERS

ROTARY CARBON TRACK

Double wipers for good contact and long working life

P.20 SINGLE linear	100 ohms to 4.7 megohms.	each 14p
P.20 SINGLE log.	4.7 Kohms to 2.2 megohms.	each 14p
JP.20 DUAL GANG lin.	4.7 Kohms to 2.2 megohms.	each 48p
JP.20 DUAL GANG log.	4.7 Kohms to 2.2 megohms.	each 48p
JP.20 DUAL GANG Log/antilog	10K, 22K, 47K, 1 megohm only.	each 48p
JP.20 DUAL GANG antilog	10K only	each 48p

2A DP mains switch for any of above 14p extra

Decades of 10, 22 and 47 only available in ranges above.

Skeleton Carbon Presets, Type PR, horizontal or vertical each 6p

SLIDER

Linear or log mono 4.7K to 1 meg, in all popular values each 30p

STEREO, matched tracks, lin. or log, in all popular values from 4.7K to 1 meg. 60p

Escutcheon plates, mono, black, white or light grey, each 10p

Control knobs, blk/wh/red/yel/gmn/blue/dk. grey. lt. grey each 7p

ELECTROLYTIC CAPACITORS

Asial Lead	3V	6-3V	10V	16V	25V	40V	63V	100V
µF								
0.47	—	—	—	—	—	—	11p	8p
1.0	—	—	—	—	—	11p	—	8p
2.2	—	—	—	—	11p	—	8p	8p
4.7	—	—	—	11p	—	8p	8p	8p
10	—	—	—	—	8p	8p	8p	8p
22	—	—	8p	—	8p	8p	8p	10p
47	8p	—	8p	8p	8p	8p	10p	13p
100	8p	8p	8p	8p	8p	10p	12p	18p
220	8p	8p	8p	10p	11p	17p	24p	28p
470	8p	10p	11p	13p	17p	24p	24p	45p
1,000	11p	13p	13p	17p	29p	25p	41p	—
2,200	15p	18p	23p	26p	37p	41p	—	—
4,700	28p	30p	39p	44p	59p	—	—	—
10,000	42p	46p	—	—	—	—	—	—

MINITRON DIGITAL INDICATORS

3015F Seven segment filament compatible with standard logic modules. 0-9 and decimal point. 9mm characters in 16 lead DIL. £1-20
Suitable BCD decoder driver 7447. £1-15
3015G showing - or - & 1 & dec. pt. £1-20

LEDS (Light Emitting Diodes) 25p
Photo Cells cadmium sulphide each 40p

ANTEX Soldering Irons

CN340	£1-95	Spare bits	32p
CCN240	£2-30	Spare bits	40p

Order it from E.V. for dependable service.

DESOLDER BRAID

5ft atrip 66p

WAVECHANGE SWITCHES

1 pole 12 way; 2 pole 6 way
3 pole 4 way; 4 pole 3 way each 28p
TAG STRIP 28 way 11p

NUTS, SCREWS, etc.

In lots of 100 each
4BA NUTS 28p
8BA NUTS 28p
1 7/8 Screws 28p; 1 3/8 Screws 24p
Threaded pillars 8BA, 1 1/2 hexagonal £2-10
Plain spacers 1 1/2 round £1-40
Other sizes available

ENAMEL COPPER

WIRE in 2 ounce reels
16, 18, 20, 22 SWG 34p
24, 26, 28, 30 SWG 46p
32, 34 SWG 46p 36, 38, 40 SWG 54p

DIN CONNECTORS

	Socket	Plug
2 way loudspeaker	10p	12p
3 way audio	10p	12p
5 way audio 180	12p	15p
5 way audio 240	12p	15p
6 way audio	13p	15p

EV CATALOGUE 7

2nd printing—Green and yellow Cover 112 pages, thousands of items—illustrations, diagrams, much useful technical information. The 2nd printing has been updated as much as possible on prices. It costs only 25p post free, including refund voucher for 25p for spending when ordering goods list value £5 or more.

QUALITY GUARANTEE

All goods are sold on the understanding that they conform to manufacturers' specifications and satisfaction is guaranteed as such—no rejects, seconds or sub-standard merchandise is offered for sale. Prices quoted do not include V.A.T. for which 8% must be added to total nett value of order. Every effort is made to ensure the correctness of information and prices at time of going to press. Prices subject to alteration without notice.


ELECTROVALUE LTD

28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB
Telephone: Egham 3603 Telex 264475 Shop hours 9-5.30 daily; Sat. 9-1 p.m.
NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA
Telephone (061) 432 4945 Shop hours 9-5.30 daily; Sat. 9-1 p.m.
U.S.A. CUSTOMERS are invited to contact ELECTROVALUE AMERICA, P.O. Box 27. Swarthmore PA 19081.

All postal communications, mail orders etc. to Head Office at Egham address, Dept. PE1. S.A.E. with enquiries requiring answers.

ALL OUR PRICES INCLUDE V.A.T.

BSR HI-FI AUTOCHANGER STEREO & MONO



Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months' guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/2 in.

Above motor board 3 1/2 in. Below motor board 2 1/2 in.

with STEREO and MONO XTAL £7.95 Post 45p.

PORTABLE PLAYER CABINET

Modern design. Revs. covered. Large front grille. Lift-up Lid. Chrome fittings. Approx. size 17 in x 15 in x 7 in. Few only in red rexine. £4.50 Post 50p

BSR JUNIOR SINGLE PLAYER



Heavy duty 4-speed motor with separate pick-up arm fitted LP/78 turnover mono compatible cartridge. £4.95 Post 25p

R.C.S. DISCO DECK SINGLE RECORD PLAYER



Fitted with auto stop, Stereo/mono cartridge. Baseplate. Size 11 in x 10 in. Turntable. Size 7 in diameter. A.C mains. 200/250V motor has a separate winding 14 volt to power a small amplifier. Three speeds. Plays all records.

£5.50 Post 25p

SOLID MAHOGANY PLINTH

With P.V.C. Cover. Cut out for most B.S.R. or Garrard decks. Size 12 1/2 x 14 1/2 x 7 1/2 in.

£6.50 Post 45p

COMPACT PORTABLE STEREO HI-FI

Two full size loudspeakers 13 1/2 x 10 x 3 1/2 in. Player unit clips to loudspeakers making it extremely compact, overall size only 13 1/2 x 10 x 3 1/2 in. 3 watts per channel, plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls. 240V AC Mains.

Attractive Teak finish Weight 13 lb.

Bargain Price £25 85p Carriage

SPECIAL OFFER! SMITH'S CLOCKWORK 15 AMP TIME SWITCH 0 TO 60 MINUTES



Single pole two-way surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Fully insulated. Makers' last list price £4.50. Brand new and fully guaranteed.

OUR PRICE £1.95 Post 25p

BLANK ALUMINIUM CHASSIS. 18 s.w.g. 2 1/2 in sides 8 x 4 in 45p; 8 x 6 in 53p; 10 x 7 in 65p; 12 x 8 in 85p; 14 x 9 in 90p; 16 x 10 in 105p; 18 x 11 in 120p.

ALUMINIUM BOXES 3 x 3 in 60p; 4 x 4 in 70p; 6 x 4 x 4 in 80p; 9 x 4 x 4 in £1; 12 x 4 x 4 in £1.30.

ALUMINIUM PANELS 18 s.w.g. 6 x 4 in 12p; 8 x 6 in 19p; 14 x 3 in 20p; 10 x 7 in 24p; 12 x 5 in 25p; 12 x 8 in 34p; 16 x 6 in 34p; 14 x 9 in 40p; 12 x 12 in 47p; 16 x 10 in 60p.

PAKOLIN PANEL 10 x 8 in 30p.

1 1/2 inch DIAMETER WAVELENGTH SWITCHES, 45p ea. 2 p. 2-way, or 2 p. 6-way, or 3 p. 4-way. 1 p. 1. 2-way, or 4 p. 2-way, or 4 p. 3-way.

TOGGLE SWITCHES, sp. 20p; dp. 25p; dp. dt. 30p.

BRITISH FM/VHF TUNING HEART

88 to 108 Mc/s British made. 2 Transistors ready aligned - requires 10.7 Mc/s I.F. Complete with tuning gang. Connections supplied but some technical experience essential.

Our price £3.95 Post 20p

SUITABLE I.F. STRIP £4.95. DECODER £4.95

R.C.S. STABILISED POWER PACK KITS

All parts and instructions with Zener Diodes, Printed Circuit, Bridge Rectifiers and Double Wound Mains Transformer input 200/240V a.c. Output voltages available 6 or 9 or 12 or 15 or 18 or 20V d.c. at 100mA or less.

PLEASE STATE VOLTAGE REQUIRED. £2.20 Post 20p

Details S.A.E. Size 3 1/2 x 1 1/2 in.

R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER BRITISH MADE

Ideal for Mike, Tape, P.U., Guitar, etc. Can be used with Battery 9-12V or H.T. line 200-300V a.c. operation. Size: 1 1/2 x 1 1/2 x 3/4 in. Response 25 c/s to 25 kc/s, 26 dB gain. For use with valve or transistor equipment.

Full instructions supplied. Details S.A.E. £1.25 10p

R.C.S. POWER PACK KIT

12 VOLT, 750mA. Complete with printed circuit board and assembly instructions. £2.95 Post 25p

12 VOLT 300mA KIT, £2.75. 9 VOLT 1 AMP KIT, £2.95.

NEW TUBULAR ELECTROLYTICS	CAN TYPES	
2/300V 14p	250/25V 14p	50 + 50/300V 50p
4/350V 14p	100/25V 20p	32 + 32/350V 35p
8/350V 22p	1000/25V 35p	32 + 32/450V 60p
16/350V 30p	1000/50V 47p	350 + 50/325V 55p
32/500V 50p	8 + 8/450V 22p	16 + 16 + 16/275V 45p
25/25V 10p	8 + 16/450V 25p	32 + 32 + 32/350V 85p
50/50V 10p	16 + 16/450V 40p	900/350V 95p
100/25V 10p	32 + 32/350V 40p	4700/83V 95p

LOW VOLTAGE ELECTROLYTICS.

1, 2, 4, 5, 8, 10, 25, 30, 50, 100, 200µF 15V 10p.
1500µF 12V 15p; 25V 20p; 50V 30p.
1000µF 12V 20p; 25V 35p; 50V 47p; 100V 70p.
2000µF 6V 25p; 25V 42p; 50V 57p.
2500µF 6V 25p; 3000µF 25V 47p; 50V 65p.
5000µF 6V 25p; 12V 42p; 25V 75p; 35V 85p; 50V 95p.
CERAMIC 1pF to 0.1µF, 4p. Silver Mica 2 to 6000pF, 4p.
PAPER 350V-0.1µF; 0.5-15p; 1µF; 2µF 150V 15p.
500V-0.001 to 0.05-4p; 0.1-10; 0.25-8p; 0.47-25p.
TWIN GANG, "0-0" 208pF + 176pF, £1.10.
Slow motion drive 385pF + 365pF with 25pF + 25pF, 50p; Twin 500pF 75p. Twin 410pF 50p. Twin 120pF 50p.
SHORT WAVE SINGLE. 25pF, 45p; 50pF, 55p.

SHORT WAVE SINGLE GANG. Precision Silver Plated Gangable Tuning Condensers. 100pF. 50p each

NEON PANEL INDICATORS 250V AC/DC. Amber 30p. RESISTORS. 1W, 1/2W, 1/8W, 20% 1p; 2W, 5W, 10Ω to 10M. HIGH STABILITY. 1/2W 20Ω to 10Ω meg., 10p. Ditto 5%. Preferred values 10Ω to 10 meg., 4p.

WIRE-WOUND RESISTORS 5 watt, 10 watt, 15 watt, 10Ω to 10M 10p each.

TAPE OSCILLATOR COIL Valve type 35p.

FERRITE ROD 8 x 1/2 in 20p; 6 x 1/2 in 20p; 3 x 1/2 in 10p.

MAINS TRANSFORMERS ALL POST 25p each

250-0-250 80mA, 6-3V 2 amp £2.50
250-0-250 80 mA, 6-3V 3.5A 6-3V 1A or 5V 2A £4.00
300-0-300 80 mA 6-3V 3.5A, 6-3V 1A or 5V 2A £5.00
350-0-350 120mA, 6-3V 4A C.T., 6-3V 2A £6.00
MINIATURE 200V 20mA, 6-3V 1A 2 1/2 x 2 1/2 in 75p
MIDGET 220V 45mA, 6-3V 2A 2 1/2 x 2 1/2 in 90p
HEATER TRANS. 6-3V 1 amp 85p, 3 amp £1.20p
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs 4.2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V 24-90

1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 24-90
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 26-90
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 49-75
12, 36, 48V 2 amp, £2.20; 20V 3 amp £2.3, 5, 8, 10, 13 or 5-0-5V 5 amp, £1.50; 6-0-6V 500mA 90p; 9V 1 amp 95p; 12V 500mA 75p; 12V 500mA 95p; 12V 750mA 95p.

AUTO TRANSFORMERS. 15V 10p; 230V or 230V to 115V 150W £4.00; 500W £7.50; 750W £15; 1000W £18.
CHARGER TRANSFORMERS. Input 200/250V. for 6 or 12V, 1 1/2 amp £2.00; 2 amp £2.50; 4 amp £4.00
BATTERY CHARGERS. Ready built with leads and clips 1 1/2 amp £2; 4 amp £4; 5 amp £4.50.
FULL WAVE BRIDGE CHARGER RECTIFIERS: 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p

MAINS ISOLATING TRANSFORMER

Primary 0-110-240V. Secondary 0-240V 3 amps 720 watts. Insulated terminals. Varnish impregnated. Fully enclosed in steel case with fixing feet. £12 95p. Famous make (Value £18) OUR PRICE £12 95p. Can be used as 800 watt auto transformers 240-110V.

SET OF 3 MOTORS FOR COLLARO STUDIO 115 VOLT TAPE DECK

£1.50 Post 50p

VOLUME CONTROLS 80 ohm Coax 5p yd.

Long spindles. Midget Size 5 K. ohms to 2 Meg. LOG or LIN. L/S 20p. D.P. 35p. STEREO L/S 6p. D.P. 75p. PRINGE LOW LOSS 10p per Ideal 625 and colour.

BRITISH AERIALITE AERAXIAL-AIR SPACED 40 yd £2.00; 50 yd £3.00.
FRINGE LOW LOSS 10p per Ideal 625 and colour.

Wired wound controls 1 1/2 in diam. 3 watts. 10Ω to 100K British Made with long spindles 1/2 in dia. 85p each CARR. DUAL CONCENTRIC POT 500K LOG AND 500K LIN D.P. switch. Inner spindle 3 1/2 in; outer spindle 2 1/2 in 75p.

ALL PRICES INCLUDE VAT • 20p MINIMUM POST AND PACKING • CALLERS WELCOME •

RADIO COMPONENT

Illustrated Brochure, Radio Books & Component Lists 10p Written guarantee.

E.M.I. 13 1/2 x 8 in. SPEAKER SALE!

With twin tweeters. £4.50
And crossover. 10 watt. State 3 or 8 or 15 ohm. As illustrated. Post 25p

With farad tweeter cone and ceramic magnet. 10 watt. £2.75
Bass res. 45-60 c/s. Flux 10,000 gauss. State 3 or 8 or 15 ohm. Post 25p
13 x 8 in Bass unit 20 watt rubber cone surround 15 ohm £5.50



LOUDSPEAKER FRONT GRILLES

Teakwood strips mounted on cloth backing, easily glued on to baffles to modernise cabinets.

Size 18 1/2 in x 10 1/2 in. 75p Or size 10 1/2 in x 7 1/2 in. 45p

E.M.I. 6 1/2 in. HI-FI WOOFER


8 ohm. 10W. Large ceramic magnet. Special Rubber cone surround. £4
Frequency response 30-12,000 c/s. Ideal P.A. Columns. Hi-Fi Enclosure Systems, etc. Suitable Cabinet 12 x 8 x 6 24 Suitable Tweeter £2



ELAC CONE TWEETER

The moving coil diaphragm gives a good radiation pattern to the higher frequencies and a smooth extension of total response from 1,000 c/s to 15,000 c/s. Size 8 1/2 x 3 1/2 x 2 1/2 in deep. Rating 10W. 3 ohm. Crossover £1.25

£1.90 Post 20p.



GOODMANS 8 in. WOOFER

8 ohm 12 watt. Deep cone. Heavy ceramic magnet. Bass resonance 35 cps. Frequency response 30-8,000 cps. Ideal bass unit for Hi-Fi system. £3.75



SPECIAL OFFER LOUDSPEAKERS

3 ohm, 2 1/2 in; 2 1/2 in; 3 1/2 in; 5 in. 8 ohm, 2 1/2 in; 2 1/2 in; 5 in x 3 in; 3 in; 4 in; 5 in. 15 ohm, 3 1/2 in; 5 in; 6 x 4 in; 5 x 3 in; 7 x 4 in; 8 x 5 in. 25 ohm, 2 1/2 in; 5 x 3 in; 5 in. 35 ohm, 3 in; 5 in. 80 ohm, 2 1/2 in; 2 1/2 in. 120 ohm 3 in.

£1 EACH

LOUDSPEAKERS P.M. 3 OHMS. 7 x 4 in £1.25; 6 1/2 in £1.50; 8 x 5 in £1.60; 8 in £1.75; 10 x 6 in £1.90; 10 in £2.50

RICHARD ALLAN TWIN CONE LOUDSPEAKERS. 8 in diameter 4W £2.50, 10 in diameter 5W £2.95; Post 25p.

12 in diameter, 6W, £3.50; 3 or 8 or 15 ohm models.

SPEAKER COVERING MATERIALS. Samples Large S.A.E. Horn Tweeters 2-18Kc/s, 5W 8 ohm or 15 ohm £2.20. De Luxe Horn Tweeters 2-18Kc/s, 15W, 15 ohm £4.00.

TWO-WAY 3,000 c.p.s. CROSSEOVERS 3, 8 or 15 ohm £1.25.

CASSETTE MACHINE MOTOR. 6 Volt. Will replace many types £1.25.

R.C.S. 3 WAY CROSSOVER

Complete with 12 ft. twin lead fitted with din speaker plug. Ready assembled with leads for speakers, bass, mid and tweeter. Crossover frequencies—950 cps and £1.95 3,000 cps.

VALVE OUTPUT TRANSFORMER 50p.
MIKE TRANSFORMER MU metal 10p; £1.25.
PURE-FULL VALVE OUTPUT TRANSFORMERS.
50 watt £12.50 100 watt £15.00

ELECTRO MAGNETIC PENDULUM MECHANISM

1.5V d.c. operation over 200 hours continuous on SP2 battery, fully adjustable swing and speed. Ideal displays, teaching electro magnetism or for metronome, 95p 20p strobe, etc.

R.C.S. RECORD PLAYER AMPLIFIER

2 stage triode pentode valve. 3 watts output. Volume on/off and tone controls. Printed circuit £4.50 Post 35p

A.C. mains complete and tested. Complete with speaker.

COAXIAL PLUG 10P. PANEL SOCKETS 10p. LINE 18 OUTLET BOXES, SURFACE MOUNTING 25p.

BALANCED TWIN RIBBON FEEDER 300 ohms, 7p yd.

JACK SOCKET Std. open-circuit 14p. closed circuit 25p; Chrome Lead Socket 45p. Phono Plugs 7p. Phono Socket 7p

JACK PLUGS Std. Chrome 20p; 3-5mm Chrome 15p DIN SOCKETS Chassis 8-pin 10p; 8-pin 10p DIN SOCKETS Lead 8-pin 18p; 5-pin 25p. DIN PLUGS 8-pin 25p; 5-pin 25p.

VALVE HOLDERS 5p; CERAMIC 10p; CANS 6p.

ALL OUR PRICES INCLUDE V.A.T.

E.M.I. WOOFER AND TWEETER KIT

£5.75 THE PAIR, Post 45p. (Available separately. Woofer £4.25; Tweeter £1.90)

Comprising a fine example of a Woofer 10 1/2 x 6 1/2 in with a massive Ceramic Magnet, 46oz Gauss 13,000 lines. Aluminium Cone centre to improve middle and top response. Also the E.M.I. Tweeter 3 1/2 in square has a special lightweight paper cone and magnet flux 10,000 lines. Crossover condenser and full instructions supplied.

Impedance Standard 8 ohms
Maximum power 12 watts
Useful Response 35 to 18,000 cps
Bass Resonance 45 cps

SUITABLE ENCLOSURE 20 x 13 x 9 in.
MODERN DESIGN. TEAK WOOD FINISH.



£10.50
Post 75p

ANOTHER R.C.S. BARGAIN!

ELAC 9 x 5 in. HI-FI SPEAKER TYPE 59RM
This famous unit now available, 10 watts, 8 ohm.
Price **£2.95** Post 25p



8" or 10" x 6" ELAC HI-FI SPEAKER

Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 cps. Bass resonance 55 cps. 8 ohm impedance. 10 watts.

10 in round **£4.50**.

£3.75

TEAK VENEER HI-FI SPEAKER CABINETS

Fluted Wood Fronts


MODEL "A". 20 x 13 x 9 in
For 12 in. dia. or 10 in. speaker. **£10.50** Post 10in speaker. 75p

MODEL "B". 16 x 10 x 9 in
For 13 x 8 in. or 8 in. speaker. **£6.60** Post 8 in. speaker. 45p

MODEL "B" 2 ditto. Triangular Corner Version.

MODEL "C". 18 x 8 x 6 in.
For 8 x 5 in. speaker. **£4.95** Post speaker. 35p

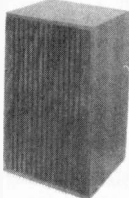LOUDSPEAKER CABINET
WADDING 18 in wide, 20p ft.



DECCA DOME TWEETER

3 1/2 in. diam. 18,000 C.F.S. 25 WATTS 8 Ω **£3.30**

BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER. Add musical highlights and sound effects to recordings. Will mix Microphone, records, tape and tuner with separate controls into single output. 9 volt battery operated. **£4.50**

STEREO VERSION OF ABOVE 25-95.

BARGAIN 8 WATT AMPLIFIER. 4 Transistor Push-Pull Ready built with volume, treble and bass controls. 18 volt battery operated. **£4.50**

THE "INSTANT" BULK TAPE ERASER & HEAD DEMAGNETISER. Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leadset S.A.E. **£3.75** Post 20p



WAFER HEATING ELEMENTS

THIN OFFERING 1001 USES for every type of heating and drying applications in the home, garage, greenhouse factory (available in manufacturing quantities). Approx. size 1 1/2 x 8 1/2 x 1/4 in. Operating voltage 200/250V a.c. 250 watts approx. Printed circuit element enclosed in asbestos fitted with connecting wires. Completely flexible providing safe Black heat. British-made for use in photocopyers and print drying equipment.

Ideal for home handymen and experimenters. Suitable for heating Fads, Food Warmers, Crossover Heaters, etc. Must be clamped between two sheets of metal or asbestos, etc., to make efficient clothes dryer, towel rails—ideal for airing cupboards. Ideal for anti-frost device for the garage—preventing frozen radiators or acting as oil sump heater. Use in greenhouse for seed raising and plant protection. Invaluable aid for bird houses, incubators, etc., etc. Can be used in series for lower heat. Or in parallel for higher heat applications.

ONLY **40p** EACH (FOUR FOR **£1.50**)
ALL POST PAID—Discounts for quantity.

BAKER MAJOR 12" £8.50



30-14,500 c/s, 12 in. double cone, woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s Rated 20 watts. NOTE: 3 or 8 or 15 ohms must be stated.

Module kit, 30-17,000 c/s with tweeter, crossover, baffle and instructions. **£10.95**

Please state 3 or 8 or 15 ohms.

BAKER "BIG SOUND" SPEAKERS

Robustly constructed to stand up to long periods of electronic power. As used by leading groups. Useful response 30-13,000 cps. Bass Resonance 55 cps.

GROUP "25" **£7.75**
12 in 25 watt
3, 8 or 15 ohms.

GROUP "35" **£8.50**
12 in 35 watt
3, 8 or 15 ohms.

GROUP "50" **£17.80**
15 in. 50 watt
8 or 15 ohms.
50 watt 12 in VERSION **£12.95**



MAJOR 100 WATT ALL PURPOSE TRANSISTOR AMPLIFIER

All purpose transistorised. Ideal for Groups, Disco and F.A. 4 inputs speech and music. 4 way mixing. Output 8/15 ohm a.c. Mains. Separate treble and bass controls. Guaranteed. Details S.A.E.



£49 Carr. £1.00

NEW MODEL MAJOR 50 WATT

4 inputs, 2 way mixing, £39.95. Carr. £1. Ideal disco amp. CALLERS ONLY! DE-LUXE 100 WATT AMPLIFIER CHASSIS. 7 Valve version, 4 inputs, 10 wide range controls. For Mixes, Discos, Organs, Guitars, etc. 4, 8 and 15 ohm Loudspeaker matching. **£69**

QUALITY LOUDSPEAKER ENCLOSURE

Teak veneered 3 in thick wood cabinet. Size 18 1/2 in x 14 1/2 in x 9 in. Weight 23 lbs. This cabinet features a wide mesh Silver Grill covering a separate compartment for mounting Tweeters or Mid-Range Horn. The fully sealed bass compartment is cut out for 6 in Woofer. £7.50. Carr. 85p. Rosewood Version £8.50. Carr. 85p.



SPECIAL OFFER 95p. Post 25p. 100 Ohm 20 watt Rheostat 2 1/2 in dia. Ceramic Former. Screw Terminals 3/4 in. dia. spindle.

20 Watt 100 ohm Rheostat 2 1/2 in dia. Ceramic former screw terminals 3/4 in dia. spindle. 95p. Post 25p.

R.C.S. STEREO DECODER

British made. Ready aligned and tested. Complete with instructions. Size 3 in x 2 in. **£4.95**

WEYRAD COILS

P50/20C 40p	RA2W 85p
P50/1AC 60p	OFT1 85p
P50/30C 40p	LFT4 85p
PCAL 85p	Twin gang £1.10

DELUXE 4 POLE MOTOR 1,400 r.p.m. reversible 42 Watt, spindle 1 1/2 x 7/32 in. size 3 1/2 x 3 in. As illustrated. 240V a.c. mains. **£2.25** Post 25p

E.M.I. GRAM MOTOR 120V or 240V a.c. 2,400 rpm. 2-pole 70mA. Size 2 1/2 x 2 1/2 in. **£1.00** Post 25p

BAKER HI-FI SPEAKERS HIGH QUALITY—BRITISH MADE REGENT

12 in. 15 watts

An inexpensive unit for the beginner in high fidelity and for general purposes. May be used to improve any Radio, Amplifier, Hi-Fi or Television receiver.

Bass Resonance 45cps
Flux Density 12,000 gauss
Useful response 45-13,000cps
3 or 8 or 15 ohm models.

£7.75

DE-LUXE Mk II

12 in. 15 watts

Especially designed to provide full range reproduction at an economical cost, suitable for use with any high fidelity system. Built-in concentric tweeter cone.

Bass Resonance 30cps
Flux Density 14,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£9.75

SUPERB

12 in. 20 watts

A high quality loudspeaker, its remarkable low cone resonance ensures clear reproduction of the deepest bass. Fitted with a special copper drive and concentric tweeter cone resulting in full range reproduction with remarkable efficiency in the upper register.

Bass Resonance 25cps
Flux Density 16,500 gauss
Useful response 20-17,000cps
8 or 15 ohms models.

£13.80

AUDITORIUM

12 in. 25 watts

A full range reproducer for high power, Electric Guitars, public address, multi-speaker systems, electric organs. Ideal for Hi-Fi and Discos-theques.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 25-16,000cps
8 or 15 ohms models.

£12.95

AUDITORIUM

15 in 35 watts

A high wattage loudspeaker of exceptional quality with a level response to above 8,000 cps. Ideal for Public Address, Discotheques, Electronic Instruments and the home.

Bass Resonance 35cps
Flux Density 15,000 gauss
Useful response 20-14,000cps
8 or 15 ohms models.

£17.80

Hi-Fi Enclosure Manual containing plans, designs, crossover data and cubic tables. 85p.

CUSTOMERS FREE CAR PARK

OPEN 9-6 p.m. WEDNESDAYS 9-1 p.m., SATURDAYS 9-5 p.m. (Closed for Lunch 1.15-2.30)

SPECIALISTS 337 WHITEHORSE ROAD · CROYDON

(Export: Remit cash and extra postage.)

Buses 50, 68, 159. Rail Selhurst

Telephone 01-684-1665

DISCO, SHOP, SOUND TO LIGHT, STAGE PHOTO-FLOOD LIGHT FITTINGS

TYPE B 3-BANK UNIT

Has two brackets to accept P/C Board. Transformers. Also has holes in ends for Potentiometers, Jack Socket, Cable, etc. Ideal for making Sound to Light and Strobes. Base Cover included. Less Lamps, only **£6.50**

inc. VAT. P. & P. 40p.

SOUND TO LIGHT

Three channel, using Type B unit. Ideal for small disco's and home entertainment. Complete with Lamps. Ready wired.

£25

inc. VAT. P. & P. 40p.

STROBE UNIT

Using Type B unit. Adjustable frequency. Single knob control. Complete with Lamps, just plug into mains—that's it.

£25

complete, inc. VAT. P. & P. 40p.

100 WATT SPOT LAMPS

Red, Pink, Green, Yellow, Blue, Violet, Clear. Only

80p

each. Minimum 3 Lamps = £2.40 inc. VAT, P. & P. 25p.

TRAFALGAR SUPPLIES

Dept H.T. · Standish Street · Burnley · Lancs



ONLY
£1.50
inc. VAT
Less Lamp
Plus 25p P. & P.

ENGINEERS

FREE

YOURSELF FOR A BETTER JOB WITH MORE PAY!

Do you want promotion, a better job, higher pay? "New Opportunities" shows you how to get them through a low-cost home study course. There are no books to buy and you can pay-as-you-learn.

This helpful guide to success should be read by every ambitious engineer. Send for this helpful 76 page FREE book now. No obligation and nobody will call on you. It could be the best thing you ever did.



This 76 page
FREE book
shows how!

CUT OUT THIS COUPON
CHOOSE A BRAND NEW FUTURE HERE!

Tick or state subject of interest. Post to the address below.

- | | | |
|---|---|---|
| <input type="checkbox"/> Practical Radio and Electronics (Technatron)
<input type="checkbox"/> Electronic Engineering
<input type="checkbox"/> Television Maintenance and Servicing
<input type="checkbox"/> General Radio and TV Engineering
<input type="checkbox"/> Radio Servicing, Maintenance and Repairs | <input type="checkbox"/> C. & G. Radio, TV Electronics, Mechanics
<input type="checkbox"/> Radio Amateurs
<input type="checkbox"/> Practical TV
<input type="checkbox"/> Colour Television
<input type="checkbox"/> Computer Electronics
<input type="checkbox"/> C. & G. LI Radio-TV Servicing cert.
<input type="checkbox"/> Post Master General 1st & 2nd class certs.
<input type="checkbox"/> C. & G. Electrical Engineering Practise | <input type="checkbox"/> C. & G. LI Installations and Wiring
<input type="checkbox"/> General Electrical Engineering
<input type="checkbox"/> Society of Engineers (Electrical Engineering)
<input type="checkbox"/> Electrical Installations and Wiring
<input type="checkbox"/> C. & G. Electrical Technicians (Primary)
<input type="checkbox"/> C. & G. Telecommunications |
|---|---|---|

To **ALDERMASTON COLLEGE**
Dept. EPE 01, Reading RG7 4PF

NAME (Block Capitals Please)

ADDRESS

POST CODE

Age

Other subjects Accredited by C.A.C.C.



Member of A.B.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

10 WATTS PER CHANNEL RMS STEREO AMPLIFIER

at less than 0.1% distortion. Max. RMS output in excess of 15 watts per channel.

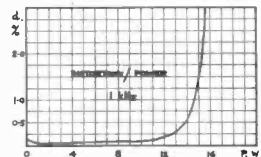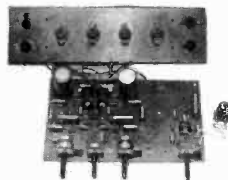- * 4-16 ohm Load
- * 15-50 kHz (-1dB)
- * 40 dB NFB
- * 150 mV input



Completely assembled PCB using top grade components (plus backplate/heatsink) including balance volume and tone controls plus mono-stereo switch. Operates from 22-24V d.c. Board also includes a single 2-stage mic. or guitar pickup preamp. (2 x BC149). Instructions are included for a simple mod. to adapt this for stereo operation giving 150mV at 1M ohm sensitivity. Full circuit supplied.

FANTASTIC AND UNREPEATABLE BARGAIN.
£9.90 plus 60p P. & P., inc. VAT. Power supply components to operate from the mains available, add £2.90 inc. VAT.

EDRICK ELECTRONICS LTD.

(DEPT. P6)

164 HIGH STREET, BARNET, HERTS.

Marshall's

Everything you need is in our
New Catalogue
available now price 20p
(100 pages of prices and data)

A. Marshall (London) Ltd Dept PE
42 Cricklewood Broadway London NW2 3DH Telephone 01-452 0161/2 Telex 21492
& 85 West Regent Street Glasgow G2 2QD Telephone 041-332 4133

Call in and see us 9-5.30 Mon-Fri
9-5.00 Sat

Trade and export enquiries welcome

Popular Semiconductors

2N456	0-80	2N2907	0-22	2N4061	0-11	AD150	0-63	BC171	0-13	BD135	0-43	BFY19	0-62	MJE2955	1-12
2N456A	0-80	2N2907A	0-24	2N4062	0-11	AD161	0-45	BC172	0-11	BD137	0-55	BFY20	0-50	MJE3059	0-68
2N457A	1-25	2N2924	0-14	2N4126	0-20	AD162	0-45	BC182	0-12	BD138	0-63	BFY50	0-23		
2N490	3-16	2N2925	0-17	2N4289	0-34	AD161 1/2	FR	BC183	0-09	BD140	0-87	BFY52	0-18	MPB111	0-32
2N491	3-58	2N2926	0-22	2N4499	0-99	AD162 1/2	FR	BC183L	0-09	BD140	0-87	BFY52	0-18	MPB112	0-40
2N492	3-99	Green	0-12	2N4920	0-99	AF108R	0-40	BC183L	0-09	BDY20	1-05	BFY53	0-21	MPB113	0-47
2N493	4-20	Yellow	0-11	2N4921	0-73	AF115	0-24	BC184	0-11	BF115	0-25	BFY50	0-75	MPF102	0-39
2N696	0-22	Orange	0-11	2N4922	0-84	AF116	0-25	BC184L	0-11	BF116	0-23	BRY39	0-23	MPSA05	0-25
2N697	0-16	2N3053	0-25	2N4923	0-83	AF117	0-20	BC186	0-25	BF117	0-23	BU104	2-00	MPSA06	0-26
2N698	0-40	2N3054	0-60	2N5172	0-12	AF118	0-55	BC187	0-27	BF119	0-58	BU105	2-07	MPSA05	0-26
2N699	0-45	2N3055	0-75	2N5174	0-22	AF124	0-30	BC207	0-12	BF121	0-45	C106A	0-46	NE555V	0-70
2N706	0-14	2N3390	0-26	2N5175	0-26	AF125	0-30	BC208	0-11	BF123	0-27	C106B	0-55	NE560	4-48
2N706A	0-18	2N3391	0-23	2N5176	0-36	AF126	0-28	BC212K	0-10	BF125	0-25	C106D	0-65	NE561	4-48
2N708	0-17	2N3391A	0-29	2N5190	0-92	AF127	0-28	BC212L	0-16	BF152	0-20	C106E	0-43	NE561	4-48
2N709	0-42	2N3392	0-13	2N5191	0-95	AF139	0-39	BC214L	0-16	BF153	0-21	CA3020A	1-80	NE565A	4-80
2N711	0-20	2N3393	0-13	2N5192	1-24	AF170	0-25	BC237	0-09	BF154	0-20	CA3046	0-70	OC23	1-35
2N718	0-53	2N3394	0-13	2N5195	1-46	AF172	0-25	BC238	0-09	BF158	0-09	CA3048	2-11	OC25	0-60
2N718A	0-28	2N3395	0-18	2N5245	0-49	AF176	0-55	BC259	0-09	BF159	0-27	CA3089E	1-90	OC26	0-50
2N720	0-50	2N3396	0-19	2N5247	0-45	AF179	0-65	BC261	0-20	BF160	0-23	CA3090Q	4-23	OC29	0-50
2N721	0-55	2N3440	0-59	2N5458	0-49	AF180	0-58	BC252	0-18	BF161	0-42	CD4000	0-51	OC45	0-32
2N914	0-22	2N3441	0-87	2N5459	0-49	AF186	0-46	BC253	0-23	BF163	0-32	CD4001	0-51	OC71	0-20
2N916	0-28	2N3442	1-25	40361	0-48	AF200	0-35	BC257	0-09	BF166	0-32	CD4002	0-51	OC72	0-25
2N918	0-32	2N3414	0-20	40362	0-50	AF239	0-51	BC258	0-09	BF167	0-21	CD4009	1-07	OC81	0-25
2N929	0-30	2N3415	0-21	40363	0-88	AF240	0-72	BC259	0-13	BF173	0-29	CD4010	1-11	OC83	0-24
2N1302	0-19	2N3416	0-34	40369	0-52	AF279	0-54	BC261	0-20	BF178	0-35	CD4011	0-51	OC83	0-25
2N1303	0-19	2N3417	0-24	40394	0-56	AF280	0-54	BC262	0-18	BF178	0-35	CD4015	2-66	RS3	1-20
2N1304	0-24	2N3638	0-15	40395	0-65	AL102	0-75	BC263	0-23	BF179	0-43	CD4016	1-02	RL54	1-05
2N1305	0-24	2N3638A	0-15	40406	0-44	AL103	0-70	BC300	0-36	BF180	0-35	CD4017	2-66	SC35D	1-68
2N1306	0-31	2N3639	0-27	40407	0-33	BC107	0-16	BC301	0-34	BF181	0-34	CD4020	2-96	SC36D	1-68
2N1307	0-22	2N3641	0-17	40498	0-50	BC108	0-15	BC302	0-29	BF182	0-40	CD4023	0-51	SC40D	1-89
2N1308	0-40	2N3702	0-12	40409	0-52	BC109	0-19	BC303	0-54	BF183	0-40	CD4024	1-90	SC41D	1-32
2N1309	0-36	2N3703	0-13	40410	0-52	BC111	0-15	BC307	0-11	BF184	0-30	CD4027	1-56	SC45D	1-89
2N1671	1-44	2N3704	0-14	40411	2-00	BC115	0-17	BC307A	0-10	BF185	0-30	CD4028	2-34	SC45D	1-96
2N1671A	1-54	2N3705	0-12	40414	3-55	BC116	0-17	BC308	0-12	BF194	0-12	CD4029	3-79	SC50D	2-60
2N1671B	1-72	2N3706	0-09	40430	0-85	BC116A	0-18	BC308A	0-12	BF195	0-12	CD4041	2-11	SC51D	2-39
2N1671C	4-32	2N3707	0-13	40583	0-23	BC117	0-21	BC308B	0-09	BF196	0-13	CD4044	2-11	SL414A	1-80
2N1711	0-45	2N3708	0-10	40601	0-67	BC118	0-11	BC309	0-10	BF197	0-15	CD4047	1-65	SL623	4-59
2N1907	5-50	2N3709	0-11	40602	0-46	BC119	0-29	BC309A	0-10	BF198	0-18	CD4049	1-65	SL623	4-59
2N2102	0-50	2N3710	0-12	40603	0-53	BC121	0-23	BC309B	0-10	BF199	0-18	CD4050	9-00	TA4350	2-10
2N2147	0-78	2N3711	0-11	40604	0-56	BC125	0-16	BC237	0-21	BF200	0-40	LM301A	0-48	TA621	2-03
2N2148	0-94	2N3712	0-06	40636	1-10	BC126	0-23	BC238	0-19	BF225J	0-19	LM304A	2-03	TA661B	1-00
2N2160	0-90	2N3713	1-20	40669	1-00	BC132	0-30	BC337	0-19	BF237	0-22	LM309K	1-88	TAD100	1-32
2N2192	0-40	2N3714	1-33	40673	0-70	BC134	0-13	BC338	0-19	BF238	0-22	LM702C	0-18	Filter	0-70
2N2192A	0-40	2N3715	1-50	AC107	0-51	BC135	0-13	BCY30	0-64	BF244	0-21	TO99	0-48	TA6271	0-84
2N2193	0-58	2N3716	1-80	AC113	0-46	BC136	0-17	BCY31	1-15	BF245	0-33	BD18	0-38	TBA641B	0-70
2N2193A	0-81	2N3717	2-20	AC117	0-20	BC137	0-17	BCY32	1-15	BF246	0-58	BD18	0-38	TBA641B	0-70
2N2194	0-73	2N3772	1-80	AC126	0-20	BC138	0-24	BCY33	0-45	BF247	0-49	14DL	0-40	TBA800	1-25
2N2194A	0-30	2N3773	2-65	AC127	0-20	BC140	0-34	BCY34	0-49	BF254	6-16	LM723C	0-90	TBA800	1-50
2N2218A	0-22	2N3789	2-06	AC128	0-29	BC141	0-29	BCY38	0-55	BF255	0-17	LM741	1-00	TBA810	1-50
2N2219	0-24	2N3790	2-40	AC151V	0-25	BC142	0-23	BCY39	1-50	BF257	0-46	TO99	0-40	TIL209	0-30
2N2219A	0-26	2N3791	2-35	AC152V	0-17	BC143	0-25	BCY40	0-87	BF258	0-59	BD18	0-40	TIP29A	0-49
2N2220	0-25	2N3792	2-69	AC153	0-25	BC147	0-21	BCY42	0-28	BF259	0-55	14DL	0-38	TIP30A	0-52
2N2221	0-18	2N3794	0-24	AC153K	0-33	BC149	0-12	BCY58	0-21	BFS21A	2-30	LM747	1-00	TIP31A	0-68
2N2221A	0-21	2N3819	0-37	AC154	0-20	BC148	0-13	BCY59	0-22	BFS28	0-92	LM748	0-92	TIP32A	0-74
2N2222	0-20	2N3820	0-64	AC176	0-23	BC149	0-12	BCY70	0-17	BF581	0-27	14DL	0-60	TIP33A	1-01
2N222A	0-25	2N3823	0-78	AC176K	0-33	BC153	0-18	BCY71	0-22	BF582	0-25	14DL	0-73	TIP34A	1-51
2N2368	0-35	2N3900	0-28	AC187K	0-33	BC154	0-18	BCY72	0-13	BF583	0-30	LM780S	2-00	TIP35A	2-09
2N2369	0-37	2N3901	0-42	AC188K	0-46	BC155	0-18	BCY87	3-54	BFX30	0-27	MC1303P	1-26	TIP36A	3-30
2N2369	0-41	2N3903	0-24	ACY18	0-24	BC158	0-13	BCY88	2-42	BFX44	0-33	MC1310	2-92	TIP41A	0-79
2N2646	0-55	2N3904	0-27	ACY19	0-27	BC159	0-14	BCY89	0-97	BFX63	2-48	MC1326	2-92	TIP42A	0-90
2N2647	1-12	2N3905	0-24	ACY20	0-22	BC160	0-37	BD115	0-75	BFX68	0-30	MC1458CP1	0-79	TIP295S	0-83
2N2904	0-22	2N3906	0-27	ACY21	0-26	BC167B	0-13	BD116	1-00	BFX84	0-24	JM480	0-90	TIP305S	0-60
2N2904A	0-24	2N4036	0-63	ACY28	0-20	BC168B	0-13	BD121	0-75	BFX85	0-30	MJ481	1-14	TIP300	0-19
2N2905	0-45	2N4037	0-37	SN7446	0-00	BC168C	0-11	BD123	0-67	BFX87	0-28	MJ481	1-14	TIP300	0-19
2N2905A	0-26	2N4058	0-16	AD142	0-59	BC169B	0-13	BD124	0-67	BFX88	0-25	MJ490	0-98	TIPX502	0-15
2N2906	0-19	2N4059	0-09	AD143	0-56	BC169C	0-13	BD131	0-40	BFX89	0-45	MJ491	1-38	TIPX500	0-15
2N2906A	0-21	2N4060	0-11	AD149V	0-60	BC170A	0-11	BD132	0-50	IBFY18	0-52	MJE340	0-45	TIPX530	0-21

PW TELE TENNIS KIT

As featured on BBC Nationwide and in the Daily Mail 2 Oct '74. Ideal game for whole family. No need to modify your TV set, just plug in to aerial socket.

Parts list as follows: A Resistor Pack £1.25 P & P 20p; B Potentiometer Pack £1.25 P & P 20p; C Capacitor Pack £1.50 P & P 20p; D Semiconductor Pack £14.50 P & P 25p; E IC Sockets £4 P & P 20p; F Transformer £1.15 P & P 25p; G PCBs £7.50 P & P 20p; H Switches £4.50 P & P 20p; I UNF Modular Kit £7.50 P & P 20p.

Special Prices—complete kit excluding case £42 P & P 50p. Sections A-F incl. £23.50 P & P 30p. Assembly instructions with complete kit or 75p on request.

P.C. Marker Pen Dalo 33PC

Price 87p
Zenora 400MW 2.7V-43V 11p. 1W 3.3V-120V 17p.

IC Sockets 8 DIL 16p. 14 DIL 17p. 16 DIL 20p.

Liquid Crystals—£13

Ex-stock S.A.E. for details of CMOS battery operated clock kit using LCD's.

Scorpio Car Ignition Kit—£11.50 + VAT
IMF40V £1-10.
BST 80246 £1-05. Transformer £2-75.
Minifonr £1-55.
DL707 £2-35 or 4 for £8.

Resistors

W	Tol	Price	Value	Price
1/4	5%	1p	0-1/35	14p
1/2	5%	1 1/2p	0-22/35	14p
1/2	5%	2p	0-47/35	14p
1	10%	2 1/2p	2-2/35	14p
2	10%	6p	4-7/35	18p
2 1/2	5%	7p	10/16V	18p
5	5%	9p	47/6 3V	20p
10	5%	10p	100/3V	20p

Veroboard

	Copper	Plain
	0-1	0-15
	0-1	0-15
2.5 x 3 1/2 in	30p	20p
2.5 x 5 in	30p	20p
3 x 3 in	30p	30p
3 1/2 x 5 in	34p	35p
3 1/2 x 17 in	£1-21	95p
78p	95p	

PE SCORPIO Mk2 ignition system kit new from ELECTRO SPARES

* 6 OR 12 VOLT
* +VE AND - VE GROUND

Here's the new, improved version of the original PE Scorpio Electronic Ignition System - with a big plus over all the other kits - the PE Scorpio Kit is designed for both positive and negative ground automotive electrical systems. Not just +ve ground. Nor just -ve ground. But both! So if you change cars, you can be almost certain that you can change over your PE Scorpio Mk. 2 as well.

Containing all the components you need, this Electro Spares PE Scorpio Mk. 2 Kit is simply built, using our easy to follow instructions. Each component is a branded unit by a reputable manufacturer and carries the manufacturer's guarantee. Ready drilled for fast assembly. Quickly fitted to any car.

When your PE Scorpio Mk. 2 is installed, you instantly benefit from all these PE Scorpio Mk. 2 advantages:

- ★ Easier starting from cold
- ★ Firing even with wet or oiled-up plugs
- ★ Smoother running at high speed
- ★ Fuel saving
- ★ More power from your engine
- ★ Longer spark plug life
- ★ No more contact-breaker burn.

Electro Spares prices:

De luxe Kit only £11.50 inc. VAT and p & p.

Ready Made Unit £14.75 inc. VAT and p & p.
State 6V or 12V system.

Send SAE now for details and free list.

FM VARICAP STEREO TUNER

As featured in the May 1973 issue of 'Practical Electronics'. Superb Hi-Fi tuner Kit now available from Electro Spares. Including cabinet and all components - pre-set Mullard modules for R.F. and I.F. circuits. Motorola I.C. Phase Lock Loop Decoder for perfect stereo reception. No alignment needed. Guaranteed first time results - or send it back, and we'll return it in perfect order (for a nominal handling charge). Electro Spares price only £28.50 inc. VAT and p & p.

'GEMINI' STEREO AMPLIFIER

A superb unit with a guaranteed output of 30 watts RMS per channel into 8 ohms. Full power THD is a mere 0.02%, and frequency response is -3 dB from 20 Hz to 100 kHz into 8 or 15 ohms. Electro Spares have already sold 100s and 100s of these Kits. Get yours now! Depending on your choice of certain components, the price can vary from £50 to £60 inc. VAT and p & p.

- ★ All components as specified by original authors, and sold separately if you wish.
- ★ Full constructional data book with specification graphs, fault finding guides, etc. 55p plus 4p postage.
- ★ Price List only. Please send S.A.E. (preferably 9 x 4 minimum) for full details.

ELECTRO SPARES

The Component Centre of the North
288 ECCLESALL RD., SHEFFIELD S11 8PE (D)
Tel. Sheffield (0742) 668888



MULTIMETER Model C-7081
GN Range Doubler 50,000 ohm/volt
High Sensitivity Meter
£14.40. 20p P. & P.

**TAPE
RECORDER
LEVEL
METER**

500µA, 70p. 5p P. & P.



**CARDIOD
DYNAMIC
MICROPHONE**

Model UD-130. Frequency response 50-15,000c/s. Impedance Dual 50K and 600 ohms, £6-55. 11p P. & P.



4 1/2 in x 3 1/2 in **METER.** 30µA, 50µA or 100µA, £3-65. 11p P. & P.

**MULTI-
METER**

Model D62
20,000 ohm/volt, £7-00.
15p P. & P.



**3 WATT STEREO
AMPLIFIER**

£4-30. 10p P. & P.

All above prices include 8% V.A.T. LARGE S.A.E. for List No. 10. Special prices for quantity quoted on request.

M. DZIUBAS

158 Bradshawgate • Bolton • Lancs. BL2 1BA

CALCULATOR OFFER!

SINCLAIR	TEXAS		
Cambridge	£17-25	T11500	£26-25
Cam. Memory	£24-00	T12000	£13-95
Executive	£23-90	T12550	£29-95
Exec. Memory	£28-45	T13500	£35-00
Scientific	£25-00	SR10	£31-85

**BUY IT
WITH
ACCESS,
etc.**

BC107 10p	BC184L 10p	TIP2955 85p	IN914 5p	7474 42p
BC108 10p	BC212L 12p	TIP3055 90p	IN916 5p	7475 60p
BC109 10p	BC213L 12p	TIS43 15p	IN4148 5p	7476 42p
BC177 22p	BC214L 12p	TIS74 50p	7400-5 20p	7483 £1-25
BC178 22p	BC182K 10p	ZTX304 26p	7410 20p	7486 46p
BC179 24p	BC183K 10p	ZTX504 35p	7413 38p	7490 66p
BC182 10p	BC184K 10p	OA10 30p	7420 20p	7492 70p
BC183 10p	BC212K 12p	OA47 7p	7430 20p	7493 66p
BC184 10p	BC213K 12p	OA73 6p	7440 20p	74107 45p
BC212 12p	BC214K 12p	OA81 6p	7442 85p	74121 51p
BC213 12p	TIP29A 52p	OA90 5p	7447 £1-30	74141 £1-00
BC214 12p	TIP30A 62p	OA91 5p	7470 34p	74151 £1-00
BC182L 10p	TIP41A 85p	OA200 6p	7472 34p	CA3026 90p
BC183L 10p	TIP42A 95p	OA202 9p	7473 45p	CA3046 82p

702 14 pin DIL 45p	741 8 pin DIL 36p	2N3242 £1-45	BFY52 22p
709 8 pin DIL 35p	741 TO-99 36p	2N3819 20p	OC24 50p
709 TO-99 35p	748 8 pin DIL 36p	2N3820 45p	OC28 70p
709 14 pin DIL 38p	747 14 pin DIL 90p	2N4442 80p	OC29 75p
710 14 pin DIL 39p	SL301B 75p	BCY70 14p	OC30 60p
710 TO-99 38p	2N1302 12p	BCY71 14p	OC35 60p
733 14 pin DIL £1-35	2N1304 13p	BCY72 13p	OC44 20p
741 14 pin DIL 39p	2N3053 16p	BFY50 25p	OC45 20p
	2N3055 48p	BFY51 21p	OC76 20p

DIECAST BOXES: 4 1/2 in x 2 1/2 in x 1 in. 50p; 4 1/2 in x 2 1/2 in x 2 in. 60p; 7 1/2 in x 4 1/2 in x 2 in. £1-50.
RESISTORS: TRS 2% E24, 2 1/2p; W.W. 2 1/2 W 10p, 6W 10p, 9W 12p, 12W 15p.
DALO PEN: 77p.
DISC CERAMICS, all values 10p. **TANTALUMS** 13p. I.C. **SOCKETS** 8 pin 15p; 14 pin 15p; 16 pin 16p. **SOLDER,** 18 S.W.G. £1-80 per kg; 22 S.W.G. £1-90 per kg.

No Lists. Prices too unstable. Phone for quote.

VAT INCLUSIVE! POST FREE OVER £3!

P.E.C. 49-51 ST. MARY'S ROAD, OTLANDS VILLAGE
WEYBRIDGE, SURREY, TEL. WALTON 21324
Mail Order Only. C.W.O. P. & P. 15p



INPUT 230/240V a.c. 50/60 OUTPUT VARIABLE 0-260V All Types SHROUDED TYPE

200 watt (1 amp) £9.00
0.5 KVA (2 amp) (MAX) £10.00
1 KVA (5 amp) (MAX) £14.70
2 KVA (10 amp) (MAX) £28.10
3 KVA (15 amp) (MAX) £31.25
4 KVA (20 amp) (MAX) £72.50
37.5 amp (MAX) £102.50
CARRIAGE AND PACKING EXTRA
OPEN TYPE 1 amp (panel mount) £9.00




300 VA ISOLATING TRANSFORMER

115/230-230/230 volts. Screened. Primary two separate 0-115V for 115 or 230 volt. Secondary two 115V at 150 VA each for 115 or 230 volt output. Can be used in series or parallel connections. Fully tropicalised. Length 13.5 cm. Width 11 cm. Height 13.5 cm. Weight 15 lb.
SPECIAL OFFER PRICE £5. Carr. 80p.

A.C. MAINS TIMER UNIT

Based on an electric clock, with 25 amp. single pole switch, which can be preset for any period up to 12 hrs. ahead to switch on for any length of time from 10 mins. to 6 hrs. then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets, etc. Attractive satin copper finish. Size 135 mm x 130 mm x 60 mm. Price £2. Post 20p. (Total incl. VAT and Post £2.30).

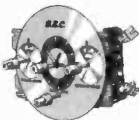

PROGRAMME TIMERS

230/240V a.c. 15 r.p.m. Motors. Each cam operates a c/o micro switch. Ideal for lighting effects, animated displays, etc. Ex equipment tested.
2 cam model. £2.00 post 30p.
4 cam model. £2.50 post 30p. 6 cam model. 3 r.p.m. 4 cam model. £3.25 post 30p. £3.25 post 30p.

MINIATURE UNISELECTOR SWITCHES

2 Bank, 11 position, 24 volt D.C. operation, full wiper with ancillary contacts. NEW Price £2.50. Post 20p. As above but with 5 Bank, 11 position. Price £3.50. Post 20p.



COIN MECHANISM (Ex London Transport)

Unit containing, selector mechanism for 1p, 2p and 5p coins. Micro switches, relays, solenoid operated hopper. 24 volt D.C. Precision built to high standard. Incredible VALUE at only £2.50. Post 60p.

230/250 VOLT A.C. SOLENOID

Approximately 1 1/8 pull. Size of feet 1 1/2" x 1 1/2". Price £1.00. Post 15p.

24 VOLT DC SOLENOIDS

UNIT containing 1 heavy duty solenoid approx. 25 lb pull 1 inch travel. Two X approx. 1 lb pull 1/2 inch travel. 1 x approx. 4oz. pull 1/2 inch travel. One 24 volt d.c., 1 heavy duty single make relay. Price £2.50. Post 60p.
ABSOLUTE BARGAIN.

230V FAN ASSEMBLY

Continuously rated, removable aluminium blades. Price £1. Post 20p.



PRECISION CENTRIFUGAL BLOWER

Mfg. Airflow Developments Ltd. Heavy Duty continuously rated, smooth running, 230/240V a.c. motor. Size: 16 x 14cm (case only). OAL 15cm. Aperture 6 x 6cm. £6.50. Post 50p.



230/240 VOLT A.C. EXTRACTOR FAN KIT

Comprising of impeller, continuously rated motor, motor housing and fixings as illustrated. Price £1.75. Post 25p. (Total incl. VAT and Post £2.16).



TRIACS GENERAL ELECTRIC POWER-GLAS TRIACS

10 amp. Glass passivated plastic triac. Latest device from U.S.A. Long term reliability. Type SC146E 10 amp, 500 PIV, £1.00. Post 5p. (Inclusive of data and application sheet.) Suitable Diac 18p.

600 WATT DIMMER SWITCH

Easily fitted. Fully guaranteed by makers. Will withstand up to 600W of lighting except fluorescent at mains voltage. Complete with simple instructions. £2.75. Post 25p.



Build a Strobe Unit, using the latest type Xenon white light flash tube. Solid state timing and triggering circuit. 230/250V a.c. operation.

EXPERIMENTERS' ECONOMY KIT
Speed adjustable 1 to 30 flash per sec. All electronic components including Xenon Tube and instructions £6.30. Post 30p.

INDUSTRIAL KIT
Ideally suitable for schools, laboratories, etc. Speed adjustable 1-80 f.p.s.
Approx 1/4 output of Hy-Light. Price £14.00. Post 50p.


HY-LIGHT STROBE MK III
For use in large rooms, halls and utilises a silica tube, printed circuit. Speed adjustable 0-20 f.p.s. Light output greater than many (so called 4 Joule) strobes. £14. Post 50p.

THE 'SUPER' HY-LIGHT KIT

Approx. four times the light output of our well proven Hy-Light strobe.
● Variable speed from 1-13 flash per sec.
● Reactor control circuit producing an intense white light. ONLY £22. Post 75p.
ROBUST, FULLY VENTILATED METAL CASE. For Hy-Light Kit including reflector £5.75. Post 25p.
Super Hy-Light case including reflector £8. Post 60p.
7-INCH POLISHED REFLECTOR
Ideally suited for above Strobe kits. Price 55p. Post 15p.

COLOUR WHEEL PROJECTOR

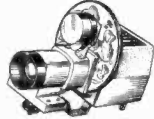Complete with oil-filled colour wheel. 100 watt lamp. 200/240V A.C. Features extremely efficient optical system. £18.50. Post 50p.
6 INCH COLOUR WHEEL
As used for Disco lighting effects, etc. Price £4.50. Post 30p.



BIG BLACK LIGHT

400Watt. Mercury vapour ultra violet lamp. Powerful source of u.v. P.F. ballast is essential. Price of matched ballast and bulb £16. Post £1. Spare bulb 75p. Post 40p.

BLACK LIGHT FLUORESCENT U.V. TUBES
4ft 40 watt. Price £5.50. Post 30p. (4ft to Personal callers only.) 2ft 20 watt, £4.25. Post 25p. (For use in standard bi-pin. MINI. 12in 8 watt, £1.60. Post 15p. 9in 6 watt, £1.30. Post 15p. Complete ballast unit and holders for 9in and 12in tube, £1.70. Post 25p. (9in and 12in measures approx.)

U.D.I. SINGLE CHANNEL

750 WATT MANUAL/AUTO DIMMER
750W Solid State Fader, with three functions: Manual fade; Auto fade-up; Auto fade-down. Automatic cycling up and down. Functions selected with 'three-position' rocker switch. Two ranges of cycling for 'Flashing' or 'Slow blending'. Ready built module 6" x 3" glass fibre board incorporating 10 amp TRIAC. Two or more modules for top quality colour blending and flashing effects. PRICE £15. Post 30p.



ELECTRONIC ORGAN KIT

Easy to build. Solid State. Two full octaves (less sharps and flats). Fitted hardwood case. Powered by two penlite 1.5V batteries. Complete set of parts including speaker, etc., together with full instructions and 10 tunes. Price £3.25. Post 35p.

INSULATION TESTERS NEW!

Test to I.E.E. Spec. Rugged metal construction, suitable for bench or field work, constant speed clutch. Size L.Bin. W.4in. H.6in. weight 6lb. 1,000V, 1,000 megohms, £24. Post 60p. 500V, 500 megohms, £28. Post 60p.



'GENTS' 6" ALARM BELL

200/250V AC/DC. Brand New. Price £5. Post 60p.

'STC' 6" RED ALARM BELL

24/48 volt DC. Brand New. Price £4. Post 50p.

All prices are subject to 8% VAT. (8p in the £)
To all orders add 8% VAT to total value of goods including carriage/packaging.

25 WATT 10/25/50/100/150/500/1k/ohm £1-15. Post 10p.
50 WATT 1/5/10/25/50/100/250/500 1-5k/ohm £1-60. Post 10p.
100 WATT 1/5/10/25/50/100/250/500/1k/1-5k/2-5k/3-5k/5k ohm £2-35. Post 15p.
Black Silver, Skirted knob calibrated in Nos. 1-9. 1/8in dia. brass bush. Ideal for above 22p each.

RELAYS SIEMENS, PLESSEY, Etc. MINIATURE RELAYS

Col. (1) Coil ohms	1	2	3	4
Col. (2) Working d.c. volts	58	5-9	6 c/o	80p
Contracts	150	4-9	2 c/o	70p
Col. (4) HD	185	8-12	6M	60p
Price	308	9-14	4 c/o	75p
Heavy duty	410	12-20	4 c/o	80p
	700	16-24	4M 2B	60p
	700	16-24	4 c/o	80p
	700	20-30	6 c/o	30p
	2,500	31-43	2 c/o HD	60p
	2,500	35-45	6M	60p
	9,000	40-70	2 c/o	60p
	15k	85-110	6M	60p

*Incl. Base. All prices incl. P. & P.
6 VOLT D.C. 1 make contacts 35p. Post 10p.
9 VOLT D.C. 2 make contacts 75p. Post 10p.
9 VOLT D.C. RELAY
3 c/o 5 amp contacts. 70 ohm coil. 75p. Post 10p.
12 VOLT D.C. RELAY
3 c/o 5 amp contacts. 120 ohm coil. 75p. Post 10p.
24 VOLT D.C. 3 c/o 75p. Post 10p.

DIAMOND 'H' Heavy Duty
230/240V a.c. 2 c/o, 25 amp RES. at 250V a.c. £2. Post 10p.

CLARE-ELLIOTT TYPE RP7641 G8
Miniature relay. 675 ohm coil. 24 Volt D.C. 2 c/o. 70p post paid.

100 VOLT A.C. 2 c/o sealed type, octal base
£1. Post 10p.

24 VOLT A.C. 3 c/o. 75p. Post 10p.
24 VOLT A.C. Mfg. by ITT. 2 h.d. c/o contacts.
55p. Post 10p.

240 VOLT A.C. RELAY. Mfg. by ITT. 240V A.C. 10 amp h.d. c/o contacts. Octal plug in base. Price 75p. Post 10p.

230/240 VOLT A.C. RELAY. Mfg. by Arrow 2 h.d. 15 amp c/o contacts. Amp connectors. Price £1. Post 10p.

220/240 VOLT A.C. RELAY
3 c/o 5 amp contacts. Sealed. Incl. 11-pin base £1.25. Post 10p.

HEAVY DUTY A.C. SEALED RELAYS
110V. 2 c/o. 20 amp contacts. £1.25. Post 10p.

VERY SPECIAL OFFER
MINIATURE ROLLER MICRO SWITCH. 5 amp. c/o contacts. Mfg. NEW. Price 10 for £1.50. Post 10p. (Min. order 10). Ditto press to make 20 for £1.50. Post 10p. Ditto press to break 20 for £1.50. Post 10p. AS above less roller lever, 20 for £2.00. Post 10p.



230/240 VOLT A.C. MINIATURE MOTOR.
20 R.P.M. Price £1. Post 10p.

BODINE TYPE N.C.I. GEARED MOTOR
(Type J) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 0.38 amp. (Type 2) 28 r.p.m. torque 20 lb. in. Reversible 1/80th h.p. 50 cycle 0.28 amp. The above two precision made U.S.A. motors are offered in 'as new' condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240V A.C. input. Price, either type £6.25. Post 50p or less transformer £3.75. Post 40p.



'FRACMO' 240 VOLT A.C. 50 cycle SINGLE PHASE GEARED MOTOR

33 r.p.m. 30 lb. ins. Reversible. Fitted with mounting feet. Brand New. £14. Post 60p. (Total price incl. VAT £15.77).



HIGH VISIBILITY PANEL MOUNTING LED'S. 0.25 inch mounting, 0.16 inch lens. Typical parameters 2V, 20M amps all type. Supplied complete with snap in mountings and data. Red 4 for £1, Green 3 for £1, Yellow 3 for £1. Post 10p. (in order) (£1).

LED READOUTS
7 series, 1/8" d.p. one-third high character. 14 pin D.I.L. Available in RED or GREEN. Price £1-65. Post 10p. 4 for £6. Post paid.



Personal callers only. Open Sat.

9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576

All Mail Orders—Callers—Ample Parking
Dept. PE1, 57 BRIDGMAN ROAD
CHISWICK, LONDON W4 5BB
Phone 01-995 1560
Showroom open Mon.-Fri.


SERVICE TRADING CO.

Personal callers only. Open Sat.
9 LITTLE NEWPORT STREET
LONDON WC2H 7JJ
Phone 01-437 0576


ACOS

FOR SOUND ENJOYMENT

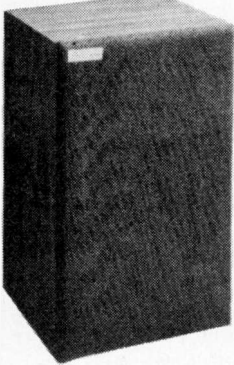
Magnificent Martin Speakers
These restyled, popular Hi-Fi speakers are available with an attractive wrap-around grill and a performance range to suit any system. Brilliance controls are provided which help to fit them into any setting.



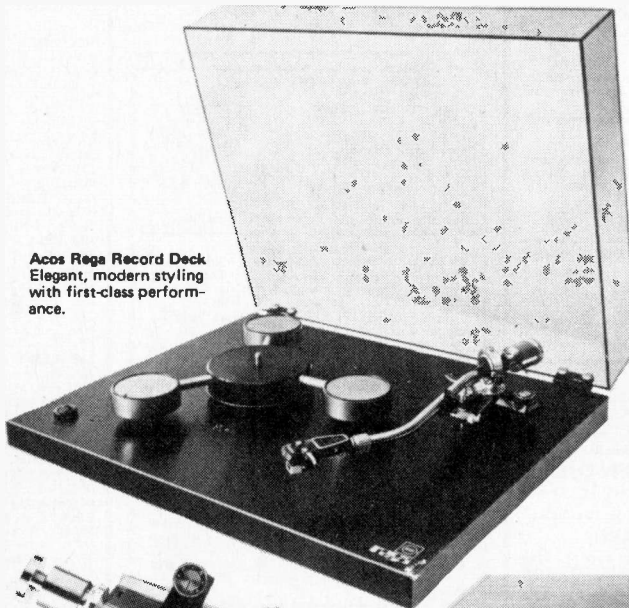Acos Rega Record Deck
Elegant, modern styling with first-class performance.




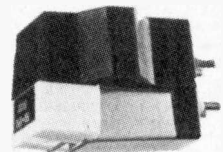The Acos M6 Range of Magnetic Cartridges are acknowledged to give high performance at low cost for two channel and four channel stereo.



Acos Lustre Tone Arm
Proven quality tone arm for the enthusiast, incorporating 'dial-a-magnet' anti-skating.

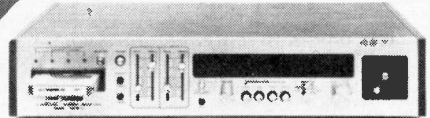Use Acos Care Accessories
Styli and replacement cartridges for your continued sound enjoyment.



Acos Eleanor Range of two channel and four channel stereo tuner amplifiers provide a new concept of sound enjoyment in any home setting.

Cosmocord Ltd, Eleanor Cross Rd, Waltham Cross, Hertfordshire EN8 7NX

Telephone: Waltham Cross 27331, Telex 24294.

Please send me full details of

NAME

ADDRESS



THE TRIUMPHS OF RADIO ASTRONOMY

THE charting of unimaginable depths of space has been assiduously carried out by radio astronomers in a number of countries since this science was formally established some 30 years ago. In Britain we can be especially proud of the achievements of our own radio astronomers, in particular those at Mullard Radio Astronomy Observatory, Cambridge, who have reached out to the furthestmost parts of the Universe. And now has come international recognition and reward. Two scientists chiefly responsible for the significant discoveries at Cambridge have been awarded the 1974 Nobel Prize for Physics (see page 38).

The triumphs of radio astronomy are scintillating examples of pure science working hand in hand with technology in the quest for knowledge of the very Universe itself. Undoubtedly this young science does deserve more general recognition.

Lacking any dramatic dynamic action and readily assimilable evidence like, for example, that which accompanies each Space Shot, radio astronomy has remained a distant and little understood or appreciated science so far as the general public is concerned. Radio telescopes in the popular mind are parabolical structures that can be rotated and aimed at any desired part of the sky, as exemplified by the very familiar Jodrell Bank telescope. In reality, radio telescopes can take diverse forms, and as often as not consist of static arrays of aerials bearing no resemblance to the general conception of a "telescope".

The emissions received from the far-off radio sources are recorded and provide data for computers and mathematicians to digest. It is only after the scientists have performed their analysis that the results can be presented in more tangible form that will be meaningful to the non-expert. This is of course in contrast to optical astronomy. Armed with even a modest telescope, anyone can make observations from his back garden. The results obtained will differ, essentially, only in degree of magnitude of resolution and distance covered with those of the professional optical astronomers.

With radio astronomy, as we have indicated, the observer has to be an expert interpreter, while the apparatus employed will comprise complex aerial arrays and highly sensitive receiving equipment—often unique and specially developed by members of a radio astronomy observatory staff for particular kinds of observations. Thus at both levels, science and technology, radio astronomy is almost exclusively the domain of the professionals. And in addition, so far as the larger observatories are concerned, generous financial backing is essential, from government or industrial bodies.

This does not mean that the amateur is precluded from undertaking any investigations in radio emissions from extra-terrestrial bodies. But it does mean that from practical considerations he is restricted to observations of the Solar System, our own Galaxy, and the more powerful sources of nearby galaxies. Here he will be following in the footsteps of the professionals, whose early work included extensive examination of these regions and, we should note, they themselves were following the pioneer investigations made by an American amateur named Grote Reber. It is indeed all too easy to assume that no significant discoveries are likely to reward amateur efforts today. But does one *really* know for sure?

F.E.B.

Editor

F. E. BENNETT

Editorial

R. D. RAILTON *Assistant Editor*
D. BARRINGTON *Production Editor*
G. GODBOLD *Technical Editor*
S. R. LEWIS B.Sc.

Art Dept.

J. D. POUNTNEY *Art Editor*
J. A. HADLEY
R. J. GOODMAN
K. A. WOODRUFF

Advertisement Manager

D. W. B. TILLEARD
Phone: 01-634 4202

P. J. MEW

Phone: 01-634 4210

C. R. BROWN, *Classified*

Phone: 01-634 4301

Editorial & Advertising Offices:
Fleetway House, Farringdon St.
London EC4A 4AD

Phone: *Editorial* 01-634 4452

Advertisements 01-634 4202

FOR SCINTILLATING DECORATION
... MAKE THIS

LIGHT PIPE

BY R. GWINN

MOBILE light displays are all the rage nowadays with multi-coloured displays driven by amplifiers a common feature of parties and dances. The flexibility of electronics has not yet been exploited fully in this area but this article, describing a plastic pipe down which light can be made to seem to flow, shows the potential available to constructors with imagination.

The light pipe consists of a plastic tube 24ft long, containing 144 miniature light bulbs which are flashed in a sequence which makes bars of light appear to move down the tube.

The bulbs are connected in four series chains of 36 bulbs, and at any time two adjacent bulbs are on and two are off. This pattern is repeated 36 times down the tube and to give the effect of motion, the rear bulb of a pair is turned off and the bulb in front is turned on. This sequence is shown in Fig. 1.

SEQUENCING LOGIC

The generation of the sequence switching is performed by five TTL i.c.s. In fact a variable pulse generator clocks two flip-flops which count up to four, providing the four possible states. The two-bit binary is decoded into one-of-four by four NAND gates in a 7400.

Besides decoding, these gates also invert the outputs. This is convenient because the next operation requires OR gating to turn on control channels for two consecutive states. This can be done with NAND gates, as these effectively become NOR gates in negative logic, which is the result of the one-of-four outputs being inverted.

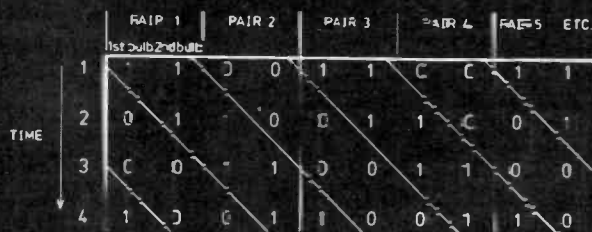


Fig. 1. The first ten bulbs in the Light Pipe showing the four switching states, 0 being the off condition and 1 the on condition. The diagonal pattern indicates the apparent direction of light motion.

THE CIRCUIT

The circuit diagram of Fig. 2 indicates the basic simplicity of the light pipe. Mains power drives the logic via a power supply circuit and a variable pulse generator, whilst the strings of bulbs in the light pipe are switched by thyristors CS1, 2, 3 and 4 under control of the logic output from IC5.

INTERFERENCE SUPPRESSION

IC4 gates through the information to IC5 only when the supply to the lamps, which it can be seen is pulsating d.c., is low. This is to reduce interference which could be caused if a large current was switched on very quickly by a thyristor.

As the pipe can be draped round loudspeakers and amplifiers, which if badly screened can pick up an objectionable clicking, it is good practice not to generate interference in the first place rather than try to eliminate it later.

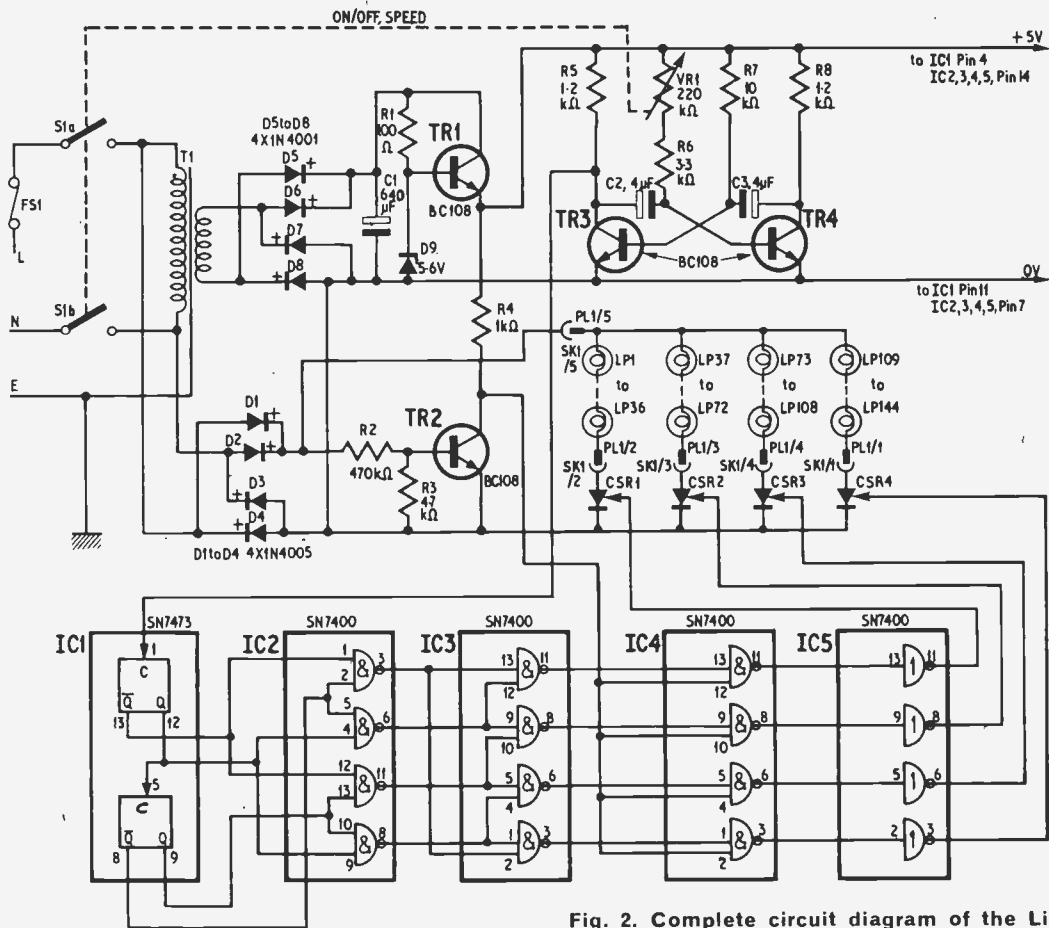


Fig. 2. Complete circuit diagram of the Light Pipe system showing the four columns of bulbs in dashed line. Note that the live side of the mains supply is connected to the logic 0V line through D4 and thus care is required in ensuring insulation of the circuitry from the case and controls

IC5 inverts the signals and directly drives the gates of the thyristors.

The zero-crossing pulses for IC4 are produced by TR2, which is on until the supply to the lamps falls below a given level.

POWER SUPPLIES

The logic 5V is obtained from a 6V transformer, rectified to give 8V d.c. regulated at 5V. The lamps are driven from full-wave rectified mains, so that the thyristors are operational in both positive and negative half cycles of the mains. The thyristor cathodes are connected to logic 0V, which means that this is **not** at the same potential as earth and **no connection should be made between this and the case**, which is earthed for safety.

CONSTRUCTION

As a wrong connection could have dramatic results, it is suggested that construction is done in stages, and each stage checked. The best order is logic power supply, multivibrator, counting and decoding i.c.s, mains rectifier and thyristors, and zero crossing pulse generator.

The Veroboard cuts and component layout are shown in Fig. 3 and the accompanying photographs. Individual constructors will no doubt modify this as they see fit to accommodate components of differing dimensions.

Check the board carefully for shorts between adjacent strips and for strips not cut in the right place. Note that there are not always seven cuts underneath i.c.s as sometimes it is necessary to join the opposite pins.

The thyristors used in the prototype had their anodes connected to their heat sinks. The wires to the output socket were soldered to the heat sinks rather than to the anode wire on the Veroboard, as this was more convenient.

The five-way connector used for the output should be as non-standard as possible for safety. A five-pin DIN would work but is almost bound to be connected to audio equipment at some time.

THE PIPE

The bulbs used in the prototype pipe were 8V, 150mA, 11mm diameter, Vitality type no. G537. A supplier for these is mentioned in the components list. They are a tight squeeze in the pipe, but once installed, the pipe may be bent round fairly sharp corners without danger of them breaking.

If a smaller bore pipe is being used, there is an electrically similar type, the 676W/E, which is wire ended and much smaller. They are, however,

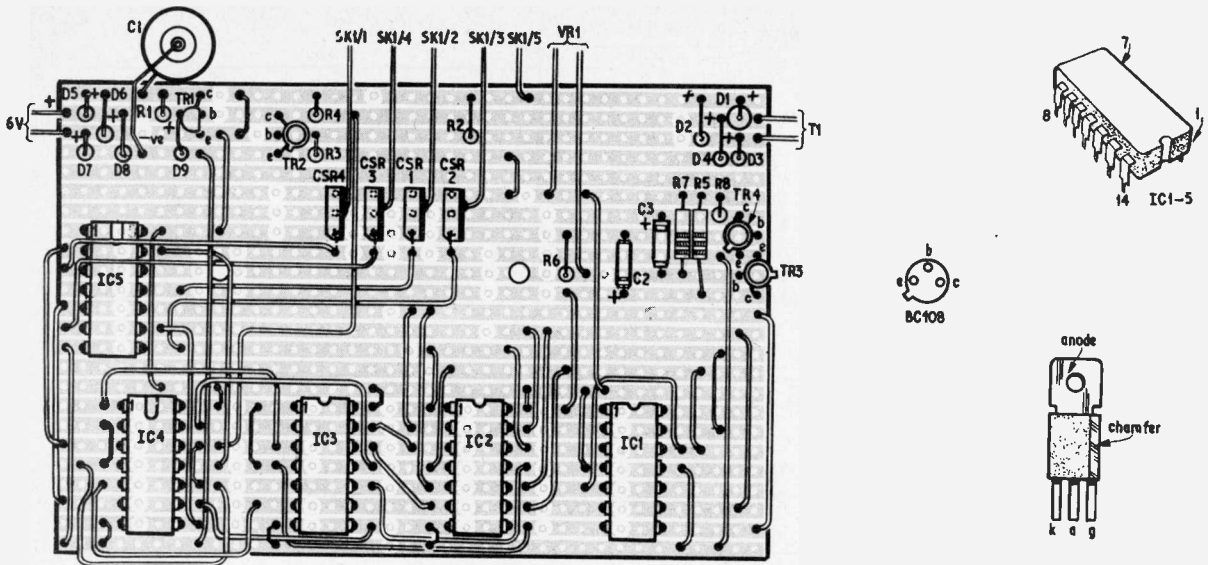


Fig. 3. Component layout and Veroboard cuts and interconnections for the Light Pipe showing connections to unmounted components

more expensive, and come in packs of 200. These are available from the same supplier.

As the lamps are somewhat inaccessible in the pipe it is important that there are as few failures as possible. The lamps are considerably underrun to increase their life. This also reduces light output and hence temperature. The pipe should be mildly warm after a few minutes running, but there is no danger of the plastic melting.

CONSTRUCTION OF THE PIPE

First, solder the bulbs into four chains of 36 bulbs. There should be 8in between each bulb for an overall length of eight yards. The connecting wire should be as thin as possible and multistranded. Some sort of jig to hold the bulbs while soldering is of great help in speeding up the operation.

The chains should be tested on the mains at this stage to find any blown or broken bulbs, or dry joints.


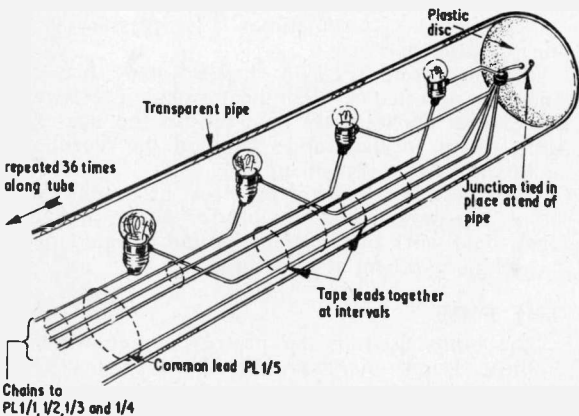


Fig. 4. Sketch showing the method of tying the light bulbs to draw them through the pipe. Note that particularly with the wire-ended bulbs the taping of the various conductors between each bulb is important in protecting the bulbs during installation

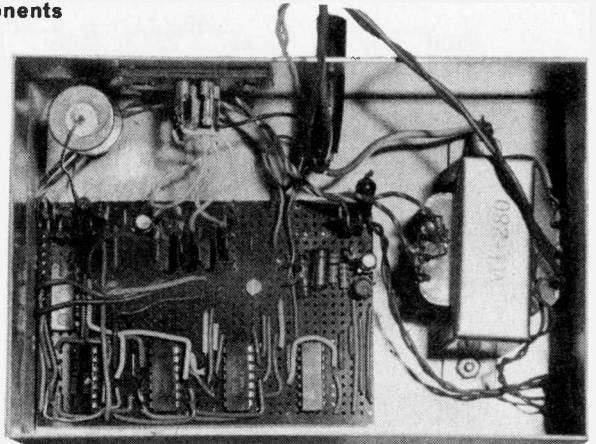

The four chains should be laid out so that there is 2in between each bulb, and taped together at intervals with a fifth common wire. The pipe is prepared for insertion by blowing talcum powder down it.

This reduces friction which otherwise might impose too great a strain on the bulbs during insertion.

To thread the lights, a piece of string must first be put through the pipe, using a piece of iron or steel and a magnet to pull it through. The string is used to pull the light chain back through. The bulbs should be pulled through with great care in order to avoid damaging them where the lead-out wires emerge from the envelope if the 676 type is used.

It is easier to fix the string at the far end of the pipe, and pull the pipe over the lamps, with liberal addition of talcum powder if it is difficult to pull.

The common wire should be joined at one end to the four other wires and held at the end by tying a piece of wire round the joint and tying this to a piece of plastic which is glued over the end of the pipe.

The wire leading to the pipe is two yards of five-core (four-core + screen audio will do), with a suitable plug, of which any metal parts should be well

insulated from the pins. The joint between it and the pipe is hidden by wide insulating tape wrapped round the pipe. The far end is similarly covered to improve appearance.

FAULT FINDING

In the event of a lamp failure, it is easier to cut into the tube and replace the lamp in situ rather than pull out all the lamps and deal with it externally.

The bulbs which have gone out should be marked on the outside of the tube with a felt pen. Then by pushing a pin through the tube it is possible to make contact with one side of the bulb and the continuity between it and the common line can be tested. If the first test is done in the centre, further tests can be made to subdivide the faulty section until the blown bulb is found.

Whilst cutting the tube might seem drastic it is certainly simple and providing a sharp knife or scalpel is used to give a clean cut it is not difficult to re-glue the cut faces using one of several fast

COMPONENTS . . .

Resistors

R1 100Ω
R2 470kΩ
R3 4.7kΩ
R4 1kΩ
R5 1.2kΩ
R6 3.3kΩ
R7 10kΩ
R8 1.2kΩ

Potentiometer

VR1 220kΩ linear with double pole mains switch

Capacitors

C1 640μF 10V electrolytic
C2, C3 4μF 10V electrolytic (2 off)

Transistors

TR1-4 BC108 (4 off)

Diodes

D1-4 1N4005 (4 off)
D5-8 1N4001 (4 off)
D9 5.6V Zener

Integrated Circuits


IC1 SN7473
IC2-5 SN7400 (4 off)

Thyristors

CSR1 to 4 CRS1/40 (1A, 400V)

Miscellaneous

144 type G537 8V 0.15A bulbs (Vitality) (Townsend-Coates Ltd., Coleman Road, Leicester, LE5 4LP. Valiant Electrical Wholesale, 20 Lettuce St., Fulham, London. Farnell Electronic Components)
8 yards green polythene tube (o.d. 2.3cm, i.d. 1.6cm) (Transatlantic Plastics, Surbiton)
Aluminium box type AB13
Veroboard 24 strips × 36 holes
Transformer Eagle MT280 6V, 280mA
Suitable 5-pin socket and plug assembly. 1A fuse and fuse-holder

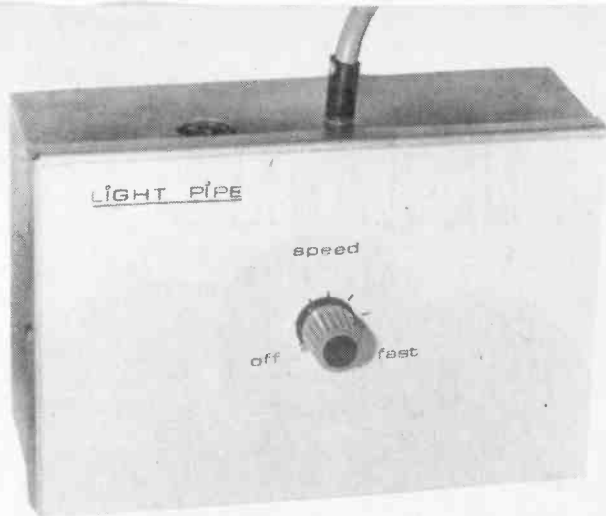

setting adhesives now on the market such as Thixofix or Araldite. Also the cut is usefully 'L'-shaped rather than through the whole pipe.

DEVELOPMENTS

The direction of apparent motion may be reversed by reversing the anode wires to CSR1 and CSR3, and if desired a switch may be included for this function.

There is no reason why several pipes may not be run off the same controller as the thyristors are rated at 1A and each chain takes only 150mA. It could be arranged to flash coloured lamps as well as the light pipe, provided the current is kept well within the ratings of the thyristors. 3A types could be substituted with no circuit modifications if a high power output is needed.

Any increase in demand for current will of course affect the choice of diodes D1 to 4 and these will need upgrading if demand exceeds 1A. ★

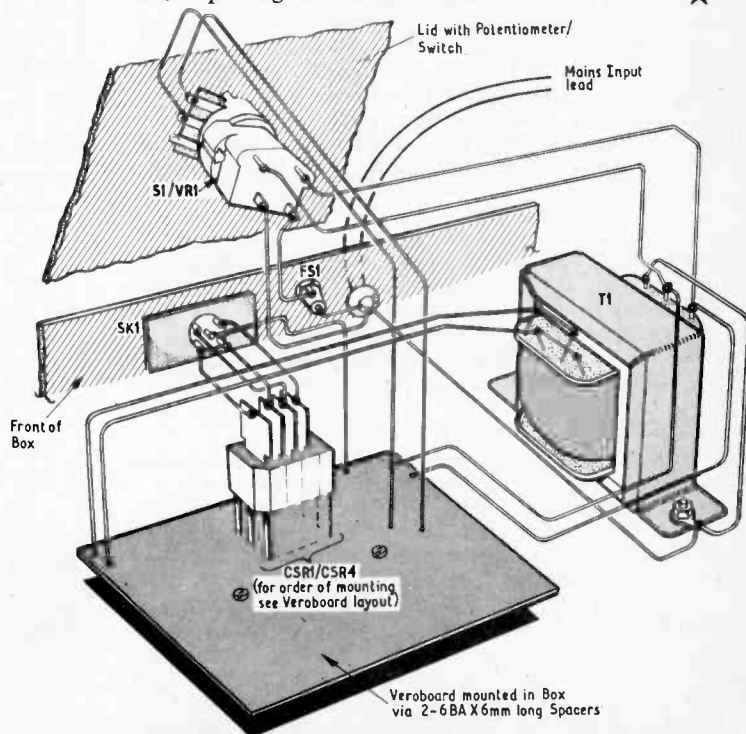


Fig. 5. Interwiring diagram

DIGITAL



LEAF

BY J. S. HAGGIS

ONE requirement for greenhouse owners whether amateur or professional is a system for keeping leaf surfaces moist. This is achieved by spraying the leaves, at intervals, with a fine water mist. The timing of the intervals depends on the rate of evaporation at any one time. This article describes the principle, theory, and construction of a device that will automatically control this process.

The system uses a sensor which consists of two electrodes placed approximately $\frac{1}{2}$ in apart and cast in an Araldite block. The surface of this block is machined flat so that when it is sprayed with water the two electrodes eventually become bridged with a blob of water. If no further spray is directed at the surface, evaporation soon starts to reduce the amount of water bridging the electrodes, until finally the bridge is broken. The time taken for this to happen depends on the rate of evaporation. On a hot summer day the time will be short, whereas on a damp cloudy day the time will be longer.

PRACTICAL CIRCUIT

The making and breaking of the sensor circuit can be used to operate the electronic circuit of Fig. 1. At first sight this might seem rather complex for such a simple operation, but as will be seen later the system allows for quite a degree of control, coupled with sound operation and reliability.

The object of the circuit is to actuate a standard mains operated solenoid water valve to feed water to a mist propagator when required, and to do this with no moving parts except the solenoid valve, i.e. relays, thus eliminating any trouble from corroded contacts which can easily happen in the greenhouse environment.

Electrode making and breaking is sensed by TR1 and here one of the prime requirements is to keep the current that flows through the sensor, when covered with water, as low as possible to reduce the effect of electrolysis which would soon fur-up the two electrodes.

With no water bridging the electrodes TR1 base is open-circuit therefore the collector is almost at supply potential. As soon as the electrodes are bridged the base goes high turning TR1 on, the collector then going to 0 volts.

At this stage it could be argued that no further circuitry is required other than a relay or thyristor to switch the mains. This would be fine if water behaved to our liking, but in fact this is not so. Once the sensor has been exposed to the atmosphere for some time the surface becomes slightly greasy. This causes the water droplets to have greater surface tension which means in practice that the sensor must be fully covered with water before the spray is stopped or intermittent operation of the circuit will take place, settling down once the surface has accumulated enough water.


TIMER

However, to overcome this problem and to give more choice of control a timer has been added. This takes the form of the now well-known 555 i.c. (IC2) discussed in depth in June 1973 PRACTICAL ELECTRONICS.

The 555 is used in the monostable mode and thus the trigger pulse must be shorter than the timing period. Differentiation of the input signal is achieved by R4 and C3. In order to provide a sharp pulse edge a Schmitt trigger is required and this also provides jitter-free operation.

The Schmitt used is a monolithic integrated, 14 pin package, type SN 7413 (IC1). The package contains two identical triggers. Each circuit functions as a four input NAND gate. All four inputs are held high by internal resistors and in this condition the output is held at logic 0. Any one input going to logic 0 sends the output to logic 1 level, i.e. 5V.

If any constructor wishes to omit the timer circuit and chance any intermittent switch-off, he can do so by leaving out the timer package and associated components.

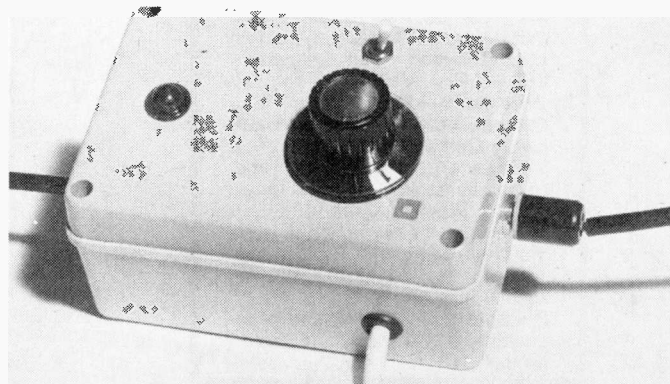

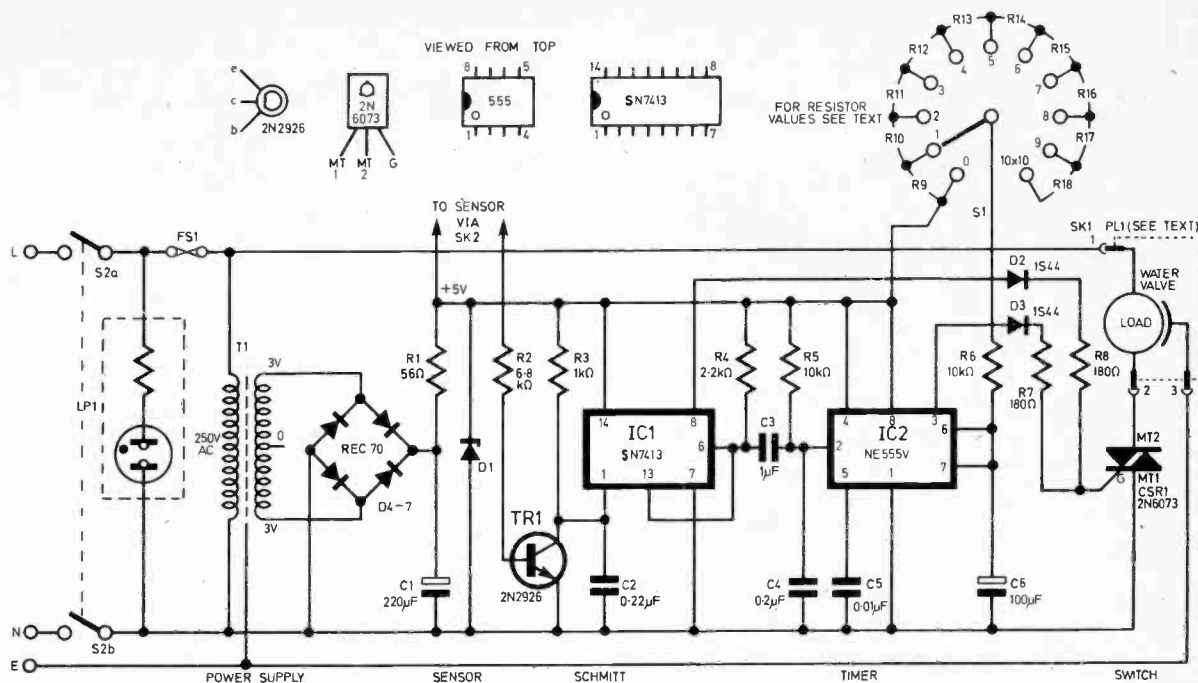


Fig. 1. Circuit diagram of the complete plant moisture control system. Note that the earth line is connected to the case of the control valve if possible and to any metal case parts if these are used

CIRCUIT DESCRIPTION

As can be seen, the power supply is not special. The 5 volt rail is Zener stabilised whilst the mains transformer T1 is an R.S. Components Ltd., sub. min. 3-0-3V device rated at 200mA. The total circuit consumption is 45mA. Even so the transformer gets quite warm but long tests have been given to the prototype with no ill effect.

As stated earlier, when the sensor X1 is bridged with a blob of water the collector of TR1 is at 0V. This state is fed to that trigger input whose output under these conditions is high. The requirement is to have a high output on C3, because the timer is started by a falling voltage.

When the blob of water has evaporated sufficiently to break the contact between the electrodes of the sensor, the base of TR1 becomes open circuit and the collector goes high. Thus the output of the Schmitt goes low and starts the timer, the output of which goes high, to approximately 5V. This is applied through a resistor to the gate of CSR1 thus turning it on.

The time the output of the timer remains in this state is determined by the setting of S1 which selects the series resistors R9 to R18.

The electrodes can be bridged again with the spraying water with no further effect on the timer. Once the time sequence is ended the circuit is set for the next sequence when evaporation dictates.

A brief look at the circuit diagram will reveal a direct connection through diode D2 and resistor R8 from the output of the second Schmitt to the gate of CSR1.

This has two functions, the first being if the operator wishes the sensor to control the "off" time as well as the "on", and accept the possibility of an unstable switch-off, he can do so by turning the time

COMPONENTS . . .

Resistors

R1	56 Ω	R6	10k Ω
R2	6.8k Ω	R7	180 Ω See text
R3	1k Ω	R8	180 Ω See text
R4	2.2k Ω	R9 to R18	See text
R5	10k Ω		
All ½ watt carbon			

Capacitors

C1	220μF elect. 40V printed circuit type
C2	0.22μF disc
C3	1μF non-elect 63V Wima
C4	0.2μF disc
C5	0.01μF disc
C6	100μF electrolytic 63V Wima

Semiconductors

TR1	2N 2926
CSR1	2N 6073
IC1	SN 7413
IC2	NE 555V
D1	4.7V, 1.3W Zener BZX61 series or IS2000A, IS7000A series (Doram)
D2 and D3	1S44 (2 off)
D4 to D7	Rec 70 (800mA 400V) Doram (4 off)

Miscellaneous

T1 3V type 200mA. Doram
 SK2/PL2 Jack and socket min.
 Case Sarel Ref. No. 308 from Hawnt and Co. Ltd., Pritchett Street, Birmingham B6 4EN.
 Mains cable 3 core P.V.C. Circuit board. Rubber flex connector (Woolworths). Neon indicator 250V miniature. Knob and dial skirt 'C' ¼in. Doram. Midget rotary switch 1 pole 12-way. Miniature toggle ON/OFF switch. Mains fuse and socket. Materials for sensor. Solenoid valve—see text.

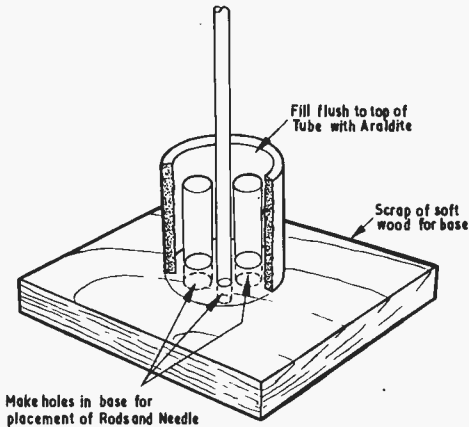
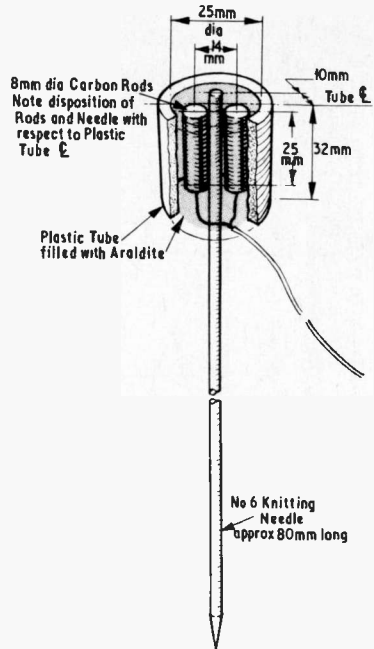
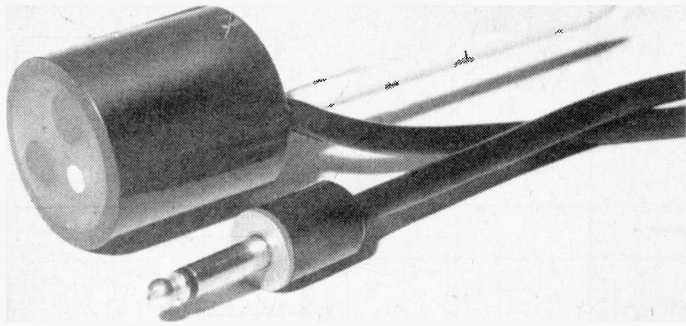


Fig. 2. A completed sensor (above) showing the dimensions in mm and simplicity of construction

Fig. 3. Manufacture of the sensor is also simple using this jig made up from a bit of scrap wood (left)

control to its minimum. Thus when the water breaks the contact the collector, as before, goes high, and starts a timing cycle which with the control turned to minimum, is only in the order of 1s and therefore of no consequence.

But the second Schmitt output volts are applied direct to CSR1 gate and this turns on CSR1 for as long as the electrodes remain open. Each Schmitt within the package inverts therefore the output from the first Schmitt must be fed into the input of the second which is in turn used for direct control of CSR1.

Without the D2, R8 connection and the timer interval inadvertently set too short to allow full coverage of the sensor with water, the timer would be triggered as before thereby turning on the spray. But if the spray were to cease before the sensor was properly bridged, no further action could be taken by the circuit. In fact if man did not intervene the circuit would remain stuck in this state for good. But with the direct connection from the Schmitt this cannot happen. The two diodes are to prevent any possible interaction.

SENSOR

The sensor X1 consists of two $\frac{1}{8}$ in carbon rods cast in Araldite at $\frac{1}{8}$ in centres (see Fig. 2).

The design of the sensor is quite critical. The relationship between the total diameter of the sensor, the diameter of the carbon rods, and their separation distance is important. Because of surface tension the blob of water that forms on the top of the sensor can roll about the surface and avoid the

carbons and even roll off the surface if the design is not correct.

SENSOR CONSTRUCTION

The sensor is best cast in a piece of plastic pipe with a 1in inside diameter. This has two advantages, the first being ease of casting and the second and more important being that the plastic edge surrounding the sensor surface tends to prevent the blob of water from rolling off.

The two carbon rods can be obtained from any used-up U2 type battery, the metal cap ends being used to solder the wire connections.

Cut the two carbon rods at $1\frac{1}{4}$ in long from the metal cap end. Drill two holes $\frac{1}{8}$ in dia. at $\frac{1}{8}$ in centres, $\frac{1}{4}$ in into a piece of scrap softwood. Drill a third hole to one side, as indicated in Fig. 3 to accommodate a No. 6 plastic knitting needle.

Push the two carbon rods into the holes as far as possible. Acquire a $4\frac{1}{4}$ in length of No. 6 knitting needle (sharp end if possible) and insert the blunt end into the third hole as far as it will go. Next place a $1\frac{1}{4}$ in length of 1in inside dia. plastic tube over the carbon rods and needle. All is now ready to attach the wires. Any twin cable with a plastic outer sheath is suitable. Solder one wire each onto the metal caps of the carbon rods. Ensure that the cable sheath is below the edge of the tube so that it will be well covered with Araldite.

When all is ready mix the Araldite resin as directed and heat until it runs quite freely, then pour it into the plastic tube ensuring that air bubbles are not trapped. Rotate the tube a little and position correctly round the carbons. Leave to set over night. One packet of Araldite is sufficient.

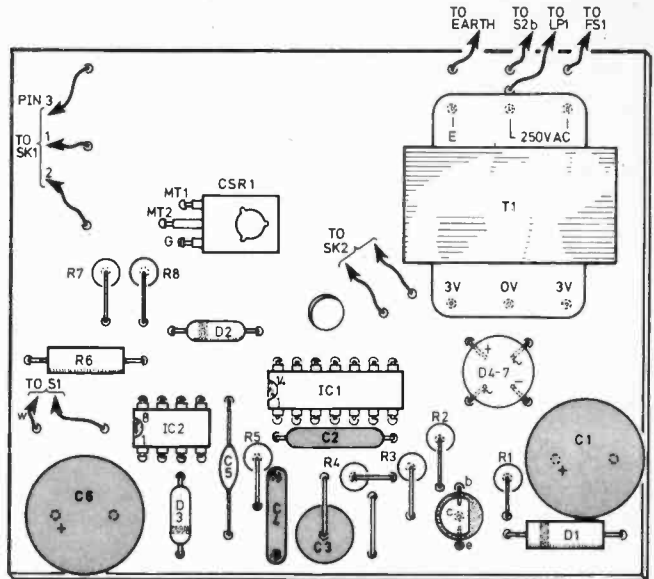
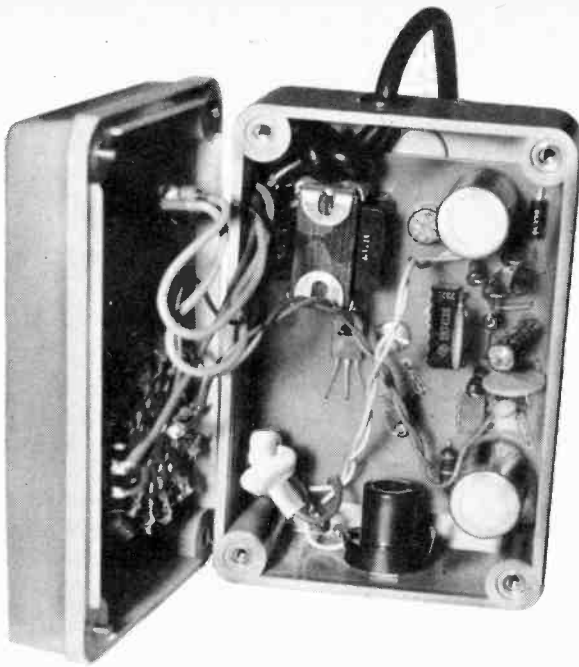


Fig. 4. Component layout on the prototype printed circuit board

Once the Araldite has hardened the timber can be split from around the ends of the carbon rods. Saw the carbons and needle flush across the surface of the sensor and then sandpaper the surface flat, finally finishing with a very fine sandpaper. Wipe the surface with methylated spirits. The sensor is now ready for use.

CIRCUIT CONSTRUCTION

In the prototype all components were mounted on one printed circuit board, including the mains transformer as shown in Fig. 4 and using the circuit layout of Fig. 5. If any constructor wishes to alter this arrangement there is no problem, the layout is not critical other than the necessity to adequately separate adjacent conductors carrying 230V a.c.

It might be noted here that the whole circuit is connected to the mains neutral line and care should be taken when handling the circuit board when switched on as full mains potential is on the board. Preferably the board should not be handled at all when power is connected.

The board is housed in a Sarel box measuring 4½ × 2¼ × 2in. The Sarel boxes are made from a tough plastic and are waterproof which makes them safe when containing mains in possibly damp conditions.

The three core mains lead enters the box through a tight fitting grommet and may either be wired direct into a fused distribution box or connected to the mains via a fused standard square pin 13A plug. It is suggested that this cable be black.

The cable to the load, in this case a water valve, again leaves the box through a tight fitting grommet and is terminated with a three pin rubber flex connection to which the water valve may be connected. It is suggested that this cable be white to eliminate any possible confusion.

The sensor X1 is plugged into the box using a normal jack plug PL1 and socket SK1. To enable the circuit to be tested or as a convenient way of


operating the water valve manually, the jack socket is wired such that when the jack is withdrawn the base of TR1 is left open circuit, thereby turning on CSR1 for as long as the jack remains out of the socket.

C2 should be mounted as closely as possible to the Schmitt input. This is best achieved by soldering it directly onto the package pins.

SETTING UP

First ensure that the circuit has the correct d.c. voltage, 5V, and if not change the value of R1 accordingly. For most practical purposes a maximum time value of 100 seconds in 10 second steps

Fig. 5. Printed circuit master as used in the prototype Leaf

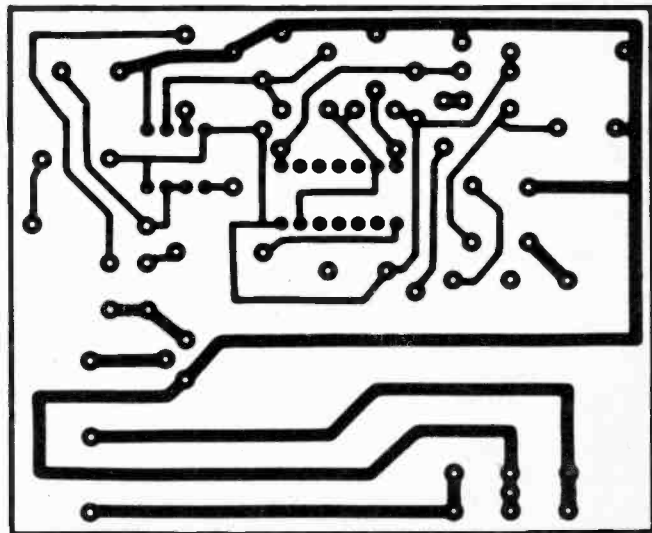

is quite adequate. But if longer or shorter time intervals are required it is only necessary to change the value of C6, and/or the values of R9 to R18 on the rotary switch S1.

S1 is a midget rotary 12 way switch set to give 11 positions and assembled with knob and dial skirt "C" in order to give indications from 0 to 10.

With C6 at $100\mu\text{F}$ and a maximum time of 100 seconds required, the total value of R9 to R18 is approximately $500\text{k}\Omega$. This will vary according to tolerance spread of different condensers.

In order to test and set-up the circuit, connect a 60W mains bulb in the load position SK1, pins 1 and 2. This gives clear indication of the operation of the circuit. Then stand the sensor up and cover the sensing surface with a small piece of very wet blotting paper. Turn the rotary switch to the 0 position, plug in the sensor, apply the mains and switch on.

If all is working correctly the bulb should light up as soon as the wet blotting paper is removed and remain lit as long as the paper is off the sensor. Replace the blotting paper and the light should extinguish about 1 second later.

If when the bulb is lit, it appears to flicker and not to be at full brilliance it is because CSR1 is not switched fully on. This could happen because of variations in sensitivity of individual devices and can be rectified by reducing the value of R7 and R8.

TIMING RESISTORS


If all is well up to this stage it now only remains to fit the individual timing resistors around S1. Solder into the first position a $47\text{k}\Omega$ resistor and select 1 on the dial (remember all these numbers on the dial are $\times 10$). Then with a suitable time piece handy, remove and replace the blotting paper and note the length of time the bulb stays illuminated. With preferred resistor values it may be difficult to time precisely, but times within 10 per cent can be achieved. If for instance, the $47\text{k}\Omega$ gives 11 seconds instead of the required 10 seconds, then in the next position solder a $33\text{k}\Omega$; this should then bring the 20 second timing to about 18 or 19 seconds. It is possible by carrying on in this manner to stay quite close to the required timing. More accuracy can be gained, if required, by making use of resistor tolerance spread.

The repeatable timings of the circuit are very good and this is what matters most. It does not matter much that a time of 62 seconds is given when 60 is wanted as long as it repeats.

INSTALLATION

Securely mount the control box and connect the circuit to the mains through a fuse box or a 13A square pin fused plug fitted with a 3A (or thereabouts) fuse. Connect up a suitable mains operated water valve for the spray system.

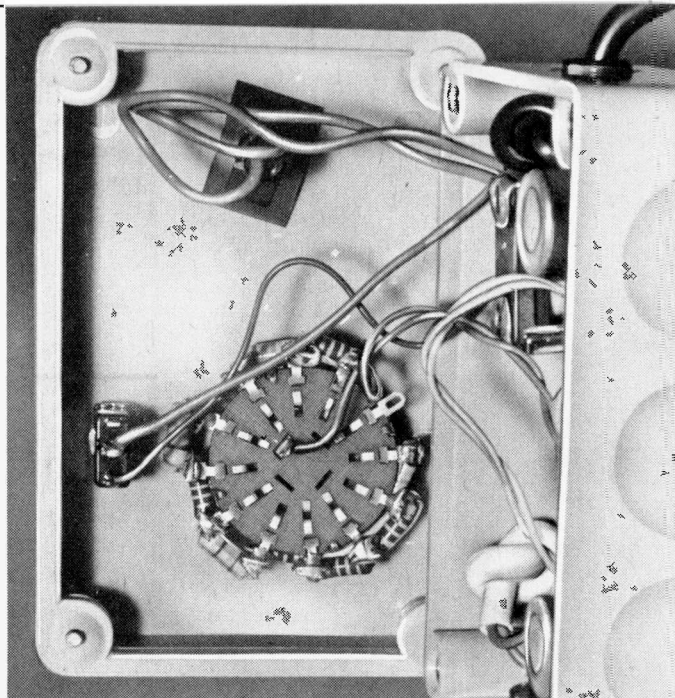CSR1 is rated at 4A and this load should not be exceeded or damage will occur. There is little advantage in fitting a fuse because in general CSR1 will blow before a fuse. If it is required to switch greater loads it will be necessary to select a different CSR1.



Stick the sensor spike into the soil at a convenient spot amongst the plants to be sprayed, but not covered by them. Wipe the top of the sensor with some methylated spirits to remove any grease. Select position 0 and switch on noting the length of time required for the sensor surface to become covered and the system to switch off.

It is unlikely that subsequent operations will take as long as the first because the subsequent operations will not be starting from a dry surface, but an idea of the time required can be gained. The unit can now either be left on "0" and control its own switch off time as stated earlier, or set to a time interval as suggested by the initial timing. Experience will soon enable a useful setting to be found.

MAINTENANCE

The only maintenance required is an occasional wipe of the sensor with meths.

If at any time it is required to test the unit it is only necessary to remove the sensor jack and replace it again and the system will operate for as long as the selected time interval set.

SOLENOID VALVE

The choice of valve used depends on the water pipe system in use, water pressure and availability. The author used one from C. W. Wheelhouse & Sons, 9-13 Bell Road, Hounslow, Middx. which had $\frac{1}{2}$ in B.S.P. fittings.

The EVJD10 and the EVD15 are $\frac{1}{2}$ in B.S.P. male and female fitting valves from Danfoss (London) Ltd., 6 Wadsworth Road, Perivale, Greenford, Middx. Both cover most water pressures which will be met and are available from stockists at around £12.

A d.c. operated valve could be accommodated by using a transformer to supply the correct voltage and a suitable rectifier.



MERCURY AGAIN

The second visit to Mercury by *Mariner 10* confirmed the previous assessment generally. The second fly-by was 50,000km. More than 500 high resolution pictures have been received, all of excellent quality. This pass was entirely on the sunlit side of the planet and covered some areas that had been checked on the first pass in March last year. There were no startling new discoveries.

The hemisphere observed showed that the planet has only one large impact basin. This area known as the Colaris Basin was on the terminator at the first pass. The floor of the crater would seem to be about the size of the Mare Imbrium of the Moon.

Many craters seem to have a central peak which suggests that the terrain was extremely soft at the time of impacts. There are also many craters within craters. A number of rayed craters exist and there is one large area near the south pole with the rays extending out through other craters. The south pole is inside a large crater.

There seem to be two distinct types of configuration of craters, those which are concentric and those which are in long chains. The concentric craters seem to be of the order of 200km in diameter.

Another feature is the large number of random scarps hundreds of kilometres long and of heights of the order of one to three kilometres. The stresses shown are compressional and the result of the compression produces these scarps. They appear to be random in direction and do not follow any particular pattern. The scarps appear to be antipodal to the Colaris Basin and a similar situation is indicated on the Moon in relation to Mare Imbrium.

It would appear that the condition in which Mercury is now found fits in very well with the current theories of early development of the Solar system. This means that there was a huge infall of large bodies on the emerging planets followed by a period of high internal heating with volcanic activity. This takes care of the changing surface features leaving the primordial conditions hardly discernible.

OPTICAL NAVIGATION IN SPACE

Another important experiment carried out by *Mariner 10* was to test the optical techniques for navigation. These techniques are vital to the missions to outer planets. The need to be able to dodge the satellites of Jupiter, Saturn and



BY FRANK W. HYDE

Uranus is imperative because of the sparse data as to the exact ephemerides of these bodies.

Previous navigation of deep space missions have relied on Earth-based radio measurements. *Mariner 10* carried out a real-time experiment as it approached Mercury. Over a hundred pictures were taken to show the angular between Mercury and the nearby (optically) stars. The experiment was successful and this means that spacecraft on long distant missions will be able to continuously monitor the space ahead and therefore automatically adjust course.

Provided *Mariner 10* can limit its fuel for modifying its course and not suffer another distraction because fast particles interfere with the sensor which is locked on Canopus, it should be possible for the spacecraft to make another pass of Mercury in 1975.

MORE FROM SKYLAB

Adding to the preliminary reports that have appeared about the effect of weightlessness and the general ability of the astronauts to be in a condition to carry out their tasks, some particular findings are now available. These were released at a symposium arranged by the American Astronautical Society.

Altogether there were 171 days of free orbital flight during the *Skylab* mission and not only has it been demonstrated that man can adapt indefinitely to the weightless environment, it has also shown that provided there has been adequate exercising during the mission the return to normal gravity presents no

problem. The state of the individual readily adapts to the return to Earth with no resultant effects. This settles the problems that were thought to exist for long missions into space.

Many ways of overcoming the weightless condition have been investigated and these are no longer required. All that is needed for an astronaut is a programme of physical exercises for 90 minutes each day during the flight.

ASTRONAUT PERFORMANCE

In each of the *Skylab* missions there was a progressive improvement in astronaut performance. This was due mainly to the increased exercise taken. The first crew were so occupied with the various technical problems that arose; little time was available for an intense study of the exercise aspect. Even when the extra vehicular activities continued to six hours at a stretch there were no "clinical" events to record.

No signs of heart deterioration appeared but there was the usual loss of red cell mass, this reduced as the exercising was extended and the flights were longer. Thus the first mission crew lost 14 per cent, the second crew 12.3 per cent but the third crew loss was down to 6.8 per cent. As on the *Apollo* missions there was a wide variation between individuals.

Post recovery was better in the case of the last mission of 84 days. The astronauts on the last mission lost least weight. Most of them gained in height, this averaged about an inch. There was a shifting of the body fluids. Some of the crew experienced slight malaise for the first two or three days. However, all got their "space legs" in a day or so and thereafter were immune.

The calorific requirements proved to be the same or thereabouts as their normal routine on Earth.

Testing the ability of these men as observers of the Earth from space, an analysis made of the observations and the ability to carry out the tasks allotted showed that in 850 observations and some 2,000 hand held camera shots, during the 84 days' mission covering 83 widely varied categories, led to these conclusions. The ability to recognise objects and patterns, to integrate these observations from a wide range of aspects and lighting angles, to reason, to make selected observations and describe them brings a new dimension into play. This ability transcended anything that could be programmed or made automatic.

NOBEL PRIZE FOR CAMBRIDGE RADIO ASTRONOMERS

By Frank Hyde

THE announcement that the Nobel Prize for Physics had been awarded to Professor Sir Martin Ryle FRS, now the Astronomer Royal, and Professor Anthony Hewish FRS, is a fitting reward for the work of these two quiet and unassuming men from the Mullard Radio Astronomy Observatory. It is a far cry from the angle iron and wire structures, which began a series of programmes more than two decades ago, to the 5km radio telescope now in operation at Lord's Bridge near Cambridge.

The official citation for the award ends with these words "for their pioneering research in radioastrophysics: Ryle for his observations and inventions, in particular the aperture-synthesis technique and Hewish for his decisive role in the discovery of pulsars".

Ryle, together with Hewish and Graham-Smith, were the original team. Hewish has stayed on but Graham-Smith moved to a Professorial Chair at Manchester and on the 1st January 1975 takes up the position of Director of the Royal Greenwich Observatory.

INTERFEROMETRY

The techniques of interferometry formed the basis of the work at Cambridge. The first telescopes were simple interferometers but very soon the phase switched interferometer came into being; the details of this were published about 1950 by Ryle and Vonberg.

From the early beginning the resolution obtained by these methods was better than the single aerial systems. The interferometer developed into a number of variations and gave rise to the more advanced technique of aperture synthesis for which Cambridge is famous. Digitation of observations led to a number of advances.

The first aperture synthesis aerials consisted of one long corner reflector and one movable one about forty feet long. In those days it was quite a sight to see the small reflector being carried to its new position by the observers and technician. This was followed by a more sophisticated cylindrical parabola driven in attitude by synchronous motors and the smaller complementary aerial fitted to a bogey on a railway system. Here the long aerial was set up east and west and the smaller one could travel on the rails north and south.

APERTURE SYNTHESIS

The technique of aperture synthesis can be described simply as two apertures moving relative to each other in such a way that they sweep out a narrow ring of large diameter. The apertures are the aerials and the rotation of the earth varies their orientation such that seen from the sky, one aerial appears to trace out an ellipse relative to the other. The interference patterns which are made by superimposing the signals of the two aerials are then synthesised. From this a chart of the structure of a source can be deduced.

The next major step was the One Mile Telescope which came into operation at the end of 1964. This was the first complete aperture synthesis purpose-built telescope. The sensitivity was extremely high. It was able to detect faint objects near the edge of the observable universe.

At that time the cosmological debate was in full flow. The first results from the new telescope showed quite clearly that the count of the sources at great distances (and therefore very old) was less than the number required by the "steady state" theory, but consistently supported the "big bang" theory. For most of the theorists this fact, together with discovery of the microwave background, which appeared universal, marked the end of support for the "steady state" protagonists.

MAPPING RADIO GALAXIES AND QUASARS

Leading on from the far-distant-source discoveries, the next successful objective was the mapping of the radio galaxies and quasars. The properties of the galaxies were of particular interest because they are enormous wasters of energy and among the largest objects known.

The detailed mapping of the galaxies and quasars enabled some conclusions to be drawn as to their birth, evolution and final demise. In this area Ryle not only made the initial discoveries but also showed that the exploding galaxies threw out on each side large clouds. These clouds appear to interact with the intergalactic medium. These great radio clouds seem to continue to receive energy from the optically observable nucleus of the original galaxy or quasar for millions of years.

In 1964 at the International Astronomical Union meeting in Hamburg, Anthony Hewish released the details of his method of finding quasars by their scintillation. A quasar is to the radio telescope a small object of high intensity. The interplanetary medium gives changes of density with the same effects as the atmosphere on light coming toward the Earth. The small apparent diameter of a quasar is comparable with the variations. In consequence a quasar is revealed by the amount of scintillation that takes place.

The preliminary work on this problem was undertaken with three stations, Cambridge, Thetford, and Clacton, roughly in an equilateral triangle. The particular quasar studied was 3C 48. This showed nearly 50 per cent scintillation: The pilot experiment was successful and the triangle was extended between Cambridge, Jodrell Bank, and Malvern.

DISCOVERY OF PULSARS

It was during the testing of the 18,000 square metre aerial at Cambridge that Jocelyn Bell first noticed the regular pulses. Later observations showed that the regularity and accuracy of the pulses was more reliable than any clock available. The team went to great lengths to establish what these pulses really were and what mechanism was involved. It became clear that what had been discovered were the playthings of the theoretical astronomers, the neutron stars. This discovery was extremely exciting, opening up as it did new possibilities in gravitational physics, the behaviour of very dense matter, and the effect on radiation physics.

SUPER-SYNTHESIS


The reward for enterprise had already been given by the Science Research Council in approving the setting up of the 5km aerial with its eight parabolas on the site of the old railway axed by Beeching. This system of aerials went one step further than aperture synthesis. It reached the stage of super-synthesis.

The principal task was to be the examination at the new high level of resolution, of quasars and radio galaxies. This was an opportunity to resolve some of the problems. In some of the observations there were more than two radio clouds associated with the explosions that took place. There were also bridge-like links between the areas of activity. The radio emission may come from the highly charged particles moving at speeds near that of light and trapped in a tangled magnetic field. They may well be accelerated by the gravitational collapse of groups of stars near the centres of visible galaxies.

All these problems and many others should respond to the high resolution of the 5km telescope. Since 1972 the telescope has already shown that its inception was more than justified.

THE MAKING OF HISTORY

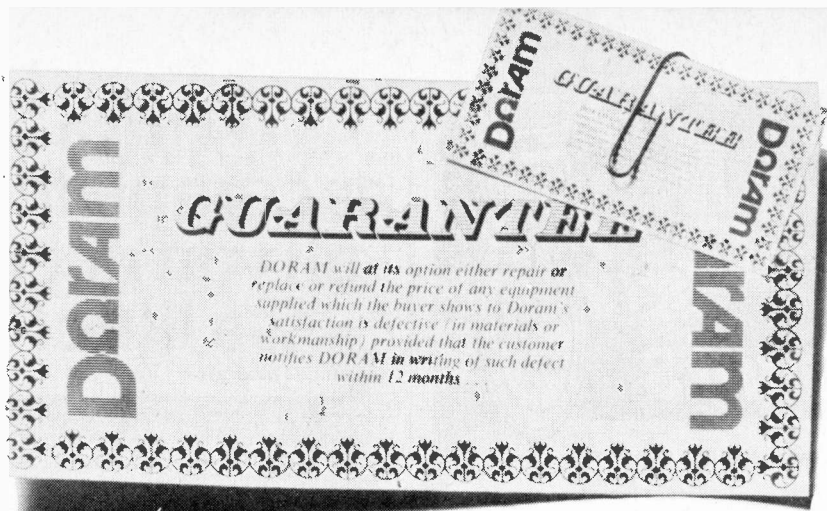The history of radio astronomy as made at the Mullard Radio Astronomy Observatory at Cambridge includes many activities which need a whole volume for description, but the story will go down in history of the time when two men, mainly responsible for that history, were honoured while still making it. ★



With the Doram catalogue, even the guarantee is guaranteed.

Doram is an entirely new way of buying electronic components.

So, to succeed, it's got to have something going for it, right?

We agree with you. And where Doram scores is in the security it gives the amateur buyer.

We'll give you peace of mind three ways.

No-quibble guarantee.

Firstly, we guarantee to replace any component which arrives faulty. Absolutely free of charge.

And secondly, our guarantee is backed by the biggest electronics distribution Group in Britain.

7-day service.

Thirdly, we guarantee you'll have your components within 7 days from our receipt of your orders.

We're so confident of our service that if we can't supply

the part you want within 7 days we'll give you an immediate refund.

So you'll never get a tedious wait.

You know just where you stand with Doram.

All branded goods.

All goods supplied by Doram are made by big-name manufacturers. And they're all to manufacturer's specifications. They're the best money can buy.

In fact, Doram gives the amateur the sort of service only professionals have enjoyed before.

Millions of components.

All in all, we're big enough to offer you stocks of millions of components, on over 4,000 product lines.

All you do is buy the Doram catalogue for 25p (that's a yearly reference book for the price of a pint of lager) and then take your pick from it.

Use the coupon now. Send today for the first-ever Doram catalogue. It can take a lot of worry out of amateur components buying.

And for 25p that's not bad, is it?

I ENCLOSE 25p* PLEASE SEND ME THE NEW DORAM CATALOGUE.

Name

Address.....


Doram Electronics Limited,
PO Box TR8,
Wellington Road Industrial Estate,
Wellington Bridge, Leeds LS12 2UF.

*This will be refunded on orders of £5 (less VAT) or more received by us before March 31st, 1975.

DORAM

PE1175

'BIG' Discounts

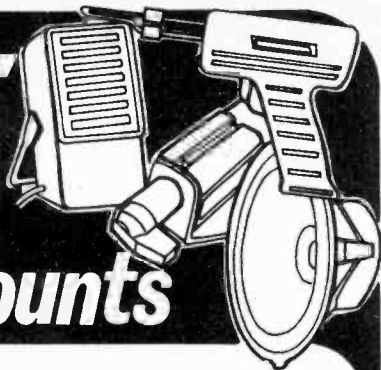

ALL PRICES INCLUDE V.A.T.


SPEAKER BARGAINS		£		£	
EMI 13in x 8in 3, 8 or 15 ohm	Plain	2-05	ELAC 10in 8 ohm Dual cone	3-50	
With Co-Axial Tweeter	8 ohm only	2-20	GOODMANS 6in 8 ohm Dual cone	2-15	
Twin Tweeter		3-70	FANE, 7in x 4in, 3 or 8 ohm	1-00	
Type 350, 8 ohm, 20W		7-50	ADASTRA 10in, 8 or 15 ohm, 10W	3-45	
6in, 8 ohm, 10W		2-40	BAKER GROUP 25 12in, 8 or 15 ohm, 25W	7-95	
8in, 8 ohm, 10W		3-75		P. & P. 0-30	
12in, 8 ohm, 20W		6-70	5in, 8 ohm, C/Mag.	0-85	
8in x 5in, C/Mag. 5W		1-25	2 1/2in, 8 ohm or 64 ohm	0-50	
8in x 5in, Dual cone 8 ohm, 10W		2-45		P. & P. 0-15	
ELAC 6in 8 ohm Dual cone		2-25			
TWEETER AND CROSSOVER			Dome Tweeter 8 ohm, 30W	5-40	
EMI 3 1/2in, 3 or 8 ohm C/Mag.		1-20	Crossovers CN23 (3 ohm), CN28 (8 ohm), CN216 (16 ohm)	1-20	
Cone Tweeter 8 or 15 ohm, 10W		2-40		P. & P. 0-15	
Cone Tweeter 8 ohm, 3W		1-45			
Horn Tweeter 8 ohm, 20W		6-40			
KIT FORM CABINETS, TEAK			12in x 8in cutout	3-50	
VERNER, 12in x 12in x 6in with 8in, 8in x 6in or 6 1/2in and 3 1/2in cutout		2-45	18in x 11in x 9in with 13in x 8in cutout for EMI 350	4-25	
17in x 10in x 9in with 8in or				P. & P. each 0-45	
MICROPHONES			TW209	5-75	
CM70 Flanet stick metal, switch crystal		1-55	CONDENSER MIKE 600 ohm, uni-dir	9-85	
DM160 Dynamic omni-dir, ball metal		3-85	Cassette Stick Mike with R. Control on/off switch (2-5 and 3-5mm J/Ply)	1-45	
UD130 50K/600 ohm, uni-dir, ball metal		5-95		P. & P. 0-20	
SOLDERING IRONS			spare Bib. etc.)	3-50	
ANTEX CN240 15W		1-90	X25 25W (low leakage)	1-80	
SK1 Kit (15 watt iron, 2				P. & P. 0-10	
CARTRIDGES AND STYLII			SONOTONE 9TAHC or 9TAHC/G diam.	1-80	
ACOS GP91/28C or 38C Stereo comp.		1-00	309 Stereo ceramic diam.	1-90	
GP93/1 or 90/1 Stereo crystal		1-85	GOLDRING G850	2-95	
GP94/1 or 99/1 Stereo ceramic		1-75	G800	3-95	
GP101 Crystal comp.		0-60	G800E	6-90	
GP104 Stereo ceramic		1-65		P. & P. 0-10	
BSR X3M or 5XH Crystal comp.		1-70	D. Diamond Stylus for above	1-25	
SX6M or SX6H Crystal comp.		1-90	G800/G850	1-95	
SC5M Stereo ceramic		2-60	G800E	3-95	
				P. & P. 0-05	
BATTERY ELIMINATORS			output) 6, 7-5 or 9 d.c. output at 300mA	2-80	
240V input 6, 7-5 or 9 300mA		2-95		P. & P. 0-15	
12V d.c. input (please specify					
TAPES		Std.	LP	DP	PLASTIC LIBRARY CASES
5in	50p	65p	1-25p	5in Reels 18p. 5 1/2in. 22p. 7in. 25p.	
5 1/2in	65p	80p	1-45p	P. & P. 1-39p each. 4 or more lot 30p	
7in	85p	1-10p	1-80p		
LOW NOISE CASSETTES					Cassette Head Cleaner
C60	35p	38p	30p		0-10
C90	45p	48p	40p		Cassette Cases
C120	55p	52p	50p		P. & P. 1-5 each
					6-10 lot
					11-20 post free
BIB ACCESSORIES					CALCULATORS
Tape Editing Kit, Ref. 23		1-35			SINCLAIR Cambridge
Recording Tape Splicer, Ref. 20		1-15			Scientific
Cassette Tape, Editing, Ref. 24		1-50			£19-00
Cassette Salvage Kit, Ref. 29		0-45			£29-00
12" s Cassette Case, Ref. 34		1-50			WHARFEDALE SPEAKER BARGAINS
Stylus Balance, Ref. 32A		1-20			Linton 2 Kit (pr.)
Spirit Level, Ref. 46		0-50			19-00 1-00
Hi-Fi Stereo Test Cassette		2-10			Glendale 3 Kit (pr.)
Groove-Kleen Record Cleaner		1-90			33-50 1-50
	P. & P.	0-10			Dovedale 3 Kit (pr.)
					52-00 1-00
					Denton 2 Speaker (pr.)
					30-00 2-00
					Linton 2 Speaker (pr.)
					39-50 2-00
					Dovedale 3 Speaker (each)
					42-00 2-00
					Glendale 3 Speaker (pr.)
					57-00 3-00
					Kingsdale 3 Speaker (each)
					59-95 3-00

Send 25p for COMPLETE CATALOGUE, refundable upon first order.
ALL OUR MERCHANDISE IS FULLY GUARANTEED
Subject to manufacturers' increase and availability

Riversdale Electronics

Mail Order Department PE1
P.O. Box 470, Manchester M60 4BU

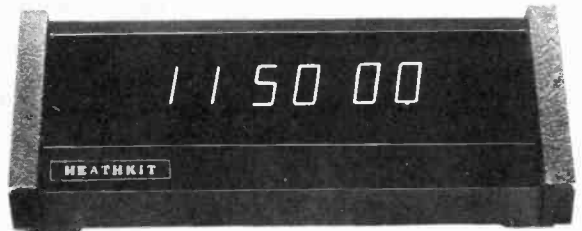With a kit as complete as this, all you need add is a little time.



You may have found, from past experience, that your definition of 'complete' is not quite the same as other people's. And your so called complete kit comes minus a cabinet, or knobs, or a multitude of other bits and pieces.

That won't happen with a Heathkit. Take our very popular digital alarm clock kit. Every part you need will be there, right down to the solder. And you'll also receive a very easy to understand instruction manual that makes light work of assembly.

In fact all you need are a few basic tools and a few enjoyable hours of your time.

After which you may like to try your hand at our AR-1214 stereo receiver. Or even a TV.

And how about an ultrasonic burglar alarm disguised as a book?

Or, for a bookful of other ideas, just clip the coupon and we'll send you the Heathkit catalogue.

Otherwise call in and see us at the London Heathkit Centre, 233 Tottenham Court Road. Or at our showroom in Bristol Road, Gloucester.

You'll find it well worth your time.

Heath (Gloucester) Limited, Dept. PE-15, Bristol Road, Gloucester, GL2 6EE. Tel: Gloucester (0452) 29451.



To: Heath (Gloucester) Limited, Dept. PE-15, Gloucester, GL2 6EE. My free Heathkit catalogue, please.


Name _____

Address _____

Postcode _____

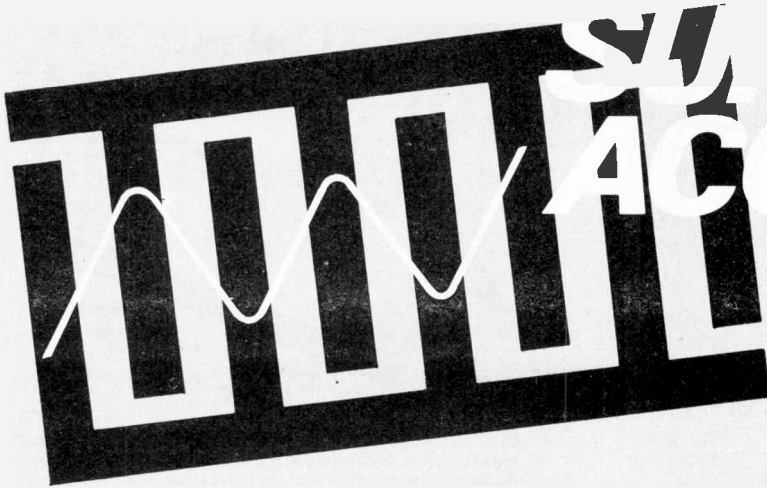Remember easy terms are available with the Heathkit Monthly Budget Plan.





So you've never heard of surface acoustic waves. Well you soon will. Progress has been astonishing in the last five years. Devices have moved from starry eyed physicists' dreams to commercial evaluation in electronic systems—a real case of fantasy to fact.

Imagine you are standing on your favourite holiday beach looking out to sea; a yacht rocks peacefully at the end of the breakwater whilst the waves are gently lapping the sand at your feet. You are witnessing the analogy of surface acoustic waves (S.A.W.).

Transfer the sea waves to the surface of a piece of flat polished crystal and you have S.A.W. Thin metal films deposited on the crystal surface enable the transfer between electrical and S.A.W. energy to be effected. By manipulating these waves on the crystal surface, oscillators, amplifiers, signal processors and delay lines have been constructed.

HISTORICAL VIEWPOINT

Lord Rayleigh is accredited with the identification of the surface acoustic wave. In 1885 he described waves travelling along the earth's surface after an earthquake, and subsequently a great deal of information has been gathered by seismologists.

It was not until the early sixties that the propagation of high frequency sound waves through a solid crystal was demonstrated. The development of a means of conversion between electrical energy and S.A.W. energy, the Interdigital Transducer (I.D.T.) in the mid and late sixties, meant that the breakthrough had come. S.A.W. exploitation was here.

THE NATURE OF S.A.W.

Surface Acoustic Waves are only one in a family of wave motions identified in crystalline materials. The property of all these waves is that of transferring acoustic energy from one part of the crystal structure to another.

In crystalline materials the particles are arranged in an orderly lattice type of structure, each particle being held in place by an elastic force generated between itself and its neighbours (imagine a lattice of billiard balls coupled by pieces of rubber band).

The longitudinal wave travels through an elastic material by alternately expanding and compressing the crystal lattice. This is definitely a bulk wave not found on the surface of the crystal.

The second type, the shear wave, vibrates the lattice at right angles to the direction in which the wave is travelling. The layers of the lattice slide up and down past each other. Again a bulk wave not found on the crystal surface.

The third type is the S.A.W. (Fig. 1a). It is a combination of the longitudinal and shear waves and is only associated with the surface of a crystal. To tie up the analogy with the waves on the surface of the sea, mentioned earlier, it is interesting to note that the motion of a particle travelling in a S.A.W. is also retrograde elliptical (Fig. 1b).

To digress for a moment; bulk waves occur in the familiar, so called, crystal oscillators which are widely used for highly stable frequency sources in, amongst other things, communications equipment.

It is easy to appreciate early fears that the frictional forces generated by this mechanical vibration of the crystal lattice would absorb the acoustic wave energy excessively when the frequency of oscillation got too high. Fortunately crystals of quartz and lithium niobate have been found to transmit frequencies from 30MHz to 10GHz acceptably.

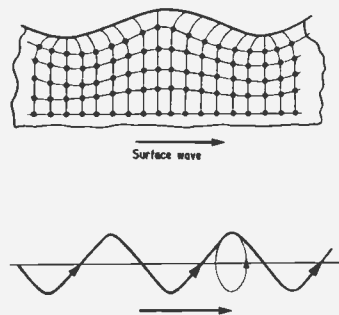


Fig. 1(a). Surface Acoustic Waves distort the crystal lattice as the wave moves along. A particle near the surface exhibits retrograde elliptical motion (b) directly analogous to waves in water

THE SPEED OF S.A.W.

We now come to one of the outstanding properties of S.A.W.—the velocity with which the waves travel along the crystal is around 10^5 times *slower* than the velocity of electromagnetic waves, i.e. the velocity of light. In other words an electronic signal that would occupy a cable one mile long could be contained on the surface of a piece of crystal only half an inch long. This means that the time taken for the signal to travel one mile in the cable would be the same as the time taken for it to travel just half an inch on the crystal.

It is now possible to glimpse how a delay line of incredible compactness might be constructed. But first a means of transferring the electrical signal to the surface of the crystal (into a S.A.W.) is needed. Ideally the process should be reversible so that the electrical signal can be recovered after it has been delayed. A transducer is required. Fig. 2 shows a delay line with input and output transducers.

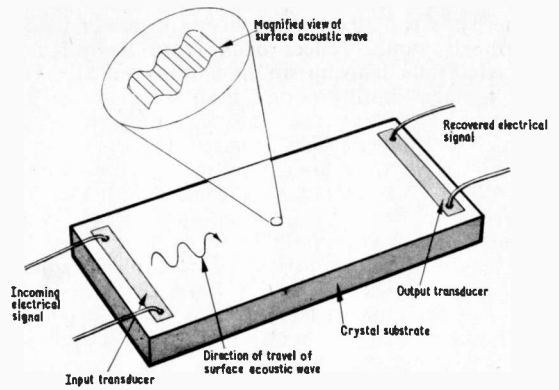


Fig. 2. A delay line consists of a crystal substrate with transducers separated by a distance depending on the delay required

THE TRANSDUCER

The transducing action for converting electrical energy to S.A.W. energy occurs in two parts. The first stage is a conversion of the incoming electrical signal to an electrical field which varies in strength and polarity as the incoming signal.

The second stage takes advantage of the property of piezo-electric materials to mechanically vibrate in sympathy with an applied electric field.

As mentioned above, suitable crystals for the transmission of S.A.W. are quartz and lithium niobate, both of which are also piezo-electric. Thus, all that is necessary to excite a S.A.W. is to apply a suitable temporally varying electric field to the piezo-electric crystal substrate which will also transmit the S.A.W. This is done using an Interdigital Transducer (I.D.T.).

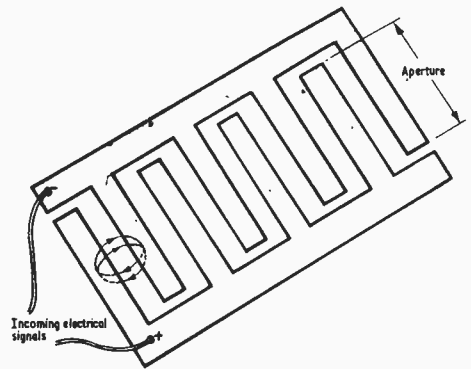


Fig. 3. An interdigital transducer is used to induce the S.A.W. into the crystal. At the instance depicted the polarity of the signal and the lines of force between two points of a finger pair are as shown. An alternating electric signal produces an alternating field.

THE INTERDIGITAL TRANSDUCER

Imagine the fingers of your left hand interleaved with your right and you have the form of an I.D.T. This shape is laid down on the crystal substrate as a thin aluminium film.

The incoming electrical signal is applied with each hand (in analogy only of course!) acting as the terminals. The electric field will be generated between the finger of each hand since there will be a time dependent potential between them due to the electric signal (Fig. 3).

The spacing between each of the fingers is equal to half the wavelength of the S.A.W. and the width of the fingers is typically a quarter wavelength. The wavelength is determined from a precise knowledge of the velocity of the S.A.W. on that particular crystal substrate and the frequency of the incoming electrical signal.

The aperture of the transducer (see Fig. 3) determines the impedance seen by the incoming electrical signal and where possible is made to match the line impedance, e.g. 50 ohms. This typically means an aperture of 20 to 100 wavelengths.

The transducer described generates a bi-directional S.A.W. The bandwidth of this I.D.T. is inversely proportional to the number of finger pairs in the transducer (see Fig. 3). The inverse of this same process of S.A.W. generation is used to detect S.A.W., i.e. to generate an electrical signal from an incoming S.A.W.

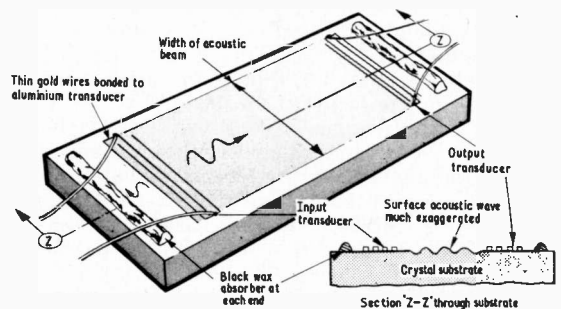


Fig. 4(a). Detailed structure of a delay line showing I.D.T.s and wax which absorbs waves so preventing unwanted reflections from the ends of the crystal. (b) shows the delay line in cross section.

DELAY LINES

Delay lines are perhaps the most fundamental S.A.W. devices. Their function is simply to provide a delay between the receipt of a signal and its onward transmission, leaving its form unchanged.

They comprise of an I.D.T. at either end of a crystal substrate. The length of the crystal determines the delay (see Fig. 4).

Since the I.D.T. is bi-directional, half the S.A.W. energy is radiated in the wrong direction and if not stopped would reflect back from the edge of the crystal thus causing an interfering signal. Thinking of the sea shore analogy, mentioned above, imagine the waves hitting the wall of a cliff or promenade and being reflected back out to sea.

Black wax is used to absorb these unwanted S.A.W. It is painted on the crystal surface and the effect can be likened to the sand of the sea shore which tends to dissipate the waves' energy.

Omni-directional transducers can be constructed but these have only two thirds the bandwidth of the bi-directional transducer. The delay possible with lithium niobate, for instance, is 2.88 microseconds per centimetre.

FABRICATION

The method of construction is common to most forms of S.A.W. device. Having selected the crystal required, cut and polished it, the I.D.T. thin metal films are deposited using conventional integrated circuit techniques.

Electrical connection to the I.D.T. is made via extremely fine gold wires bonded to the metal film. These wires are typically one to two thousandths of an inch in diameter.

The formation of the I.D.T. requires only one vacuum deposition stage and, once the master mask defining the areas to be covered with metal is made, mass production of devices is possible.

Obviously the cost of such a procedure is minimal and complete standardisation is assured. This compatibility with micro-electronic techniques and promise of inherently economic production are major reasons for the present flurry of keen commercial interest.

VARIABLE DELAYS

A variable delay line is clearly now possible using a multiplicity of output I.D.T.'s to give varying delays; electronic switching being used to select the delay required.

It can easily be appreciated that just as a wave on the sea is damped a little by a ship riding on top of it, so an I.D.T. riding on a S.A.W. will reflect some of the incident acoustic energy, i.e. attenuate the ongoing wave. This can give rise to unwanted signals as they bounce between adjacent I.D.T.'s. Special techniques have been developed to overcome these problems.

The variable delay line mentioned will give only discrete delays and for a linearly variable delay two crystal substrates are used. From Fig. 5 it will be seen that if the lower substrate is held stationary while the upper one is moved mechanically, a continuously variable delay is possible.

An alternative to using longer and longer crystal substrates to obtain larger delays, and incidentally the larger the crystal the more difficult it is to obtain, is to use the helical delay line (Fig. 6).

This is so called because the delay path is a helix, the signal travelling round and round a specially prepared crystal many times. As can be seen from the diagram, transducers are placed along the S.A.W. path giving many temporally spaced outputs. These outputs can be up to several milliseconds after the original input pulse.

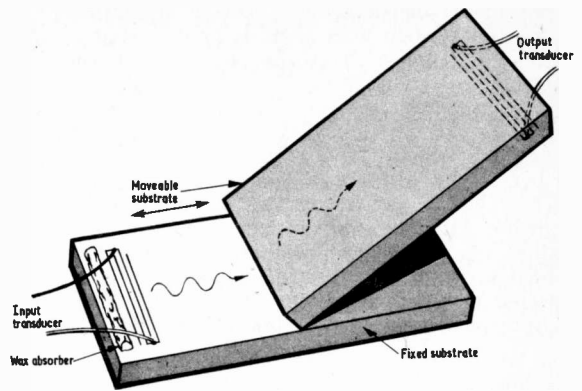


Fig. 5. A linearly variable delay line can be created by having a moveable substrate in contact with a fixed substrate

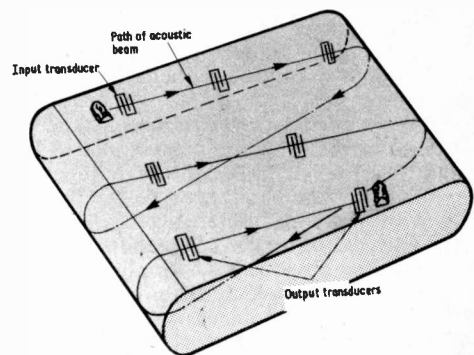


Fig. 6. For very long delays a specially prepared crystal substrate can be used to give a helical multiple-tap delay line

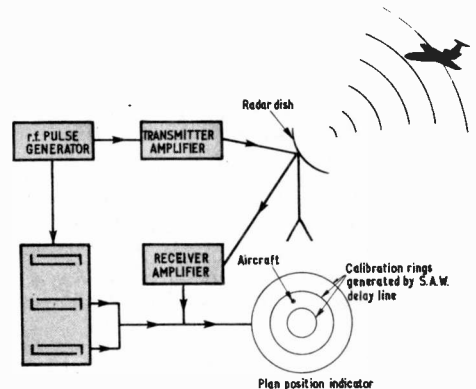


Fig. 7. A tapped delay line can be used in a radar system to give marker pips on a display screen

RADAR SYSTEMS

Applications for these types of delay lines include radar systems. Here the devices would provide range calibration and in featureless terrains simulate a background, i.e. clutter generation. Fig. 7 shows the simplified block diagram of such a radar range calibration system.

A pulse generated by the r.f. pulse generator is transmitted via the radar dish to the atmosphere. If an object such as a plane is encountered a reflection of that pulse is returned to the dish some time later.

The sensitive receiver amplifier then generates a pulse on the plan position indicator (p.p.i.) the distance of which, from the centre of the screen, indicates the distance of the plane from the radar dish. The r.f. generator also passes a pulse simultaneous with the transmitted pulse, to the S.A.W. delay line. The delay line then gives delayed outputs which correspond, when displayed on the p.p.i., to specific distances from the radar dish. Thus range calibration of the radar system is achieved.

FILTERS

The bandwidth of the I.D.T. can be closely controlled as mentioned earlier by varying the number of fingers.

Since the bandwidth is inversely proportional to the number of finger pairs, a filter, which allows only a limited range of frequencies through either side of its designed centre frequency, can be easily constructed.

The centre frequency is determined by the spacing between each finger, which is made equal to half the wavelength of the desired centre frequency. The resulting filter is of the bandpass type.

Filters with these characteristics are essential in every TV and radio, in the i.f. section for instance. The markets are obviously just right for a simple mass-produced device which requires no tuning up after fabrication. Enormous efforts have been turned in this direction and the complex requirements for a TV receiver are close to being obtained.

SIGNAL RECOGNITION

Suppose that we require a system whereby a plane flying around an airport control tower is able to tell the controller automatically that it wants to land. Let the plane have a transmitter which gives out a signal on a particular frequency.

The signal could be coded so that it is unique to that aircraft. A digital code would be suitable, i.e. a series of 1's and 0's, let these be modulated on the carrier as a bi-phase coding. This means that the carrier unchanged represents a 1 and a phase change of 180° of the carrier is a 0. If the code were four bits long, e.g. 1001 and two cycles of carrier are allotted to each bit, then the coded signal would be as shown in Fig. 8.

How can this signal of known form be recognised immediately it occurs notwithstanding the presence of much interference? Naturally S.A.W. come to our aid in the form of a tapped delay line or correlator.

The signal is first converted into a S.A.W. by the input I.D.T. As the signal feeds in it is compressed in length until it all lies along the substrate.

For simplicity the output I.D.T.s are made up of single finger pairs called taps. These taps will give a maximum output when a 1 or 0 bit of the S.A.W. appears beneath them, depending to which sum line the fingers are connected (Fig. 8). Thus if the taps are arranged 1001, as in the diagram, a S.A.W. of exactly that form at the correct frequency will cause them all to give a maximum output, simultaneously, when it appears beneath them.



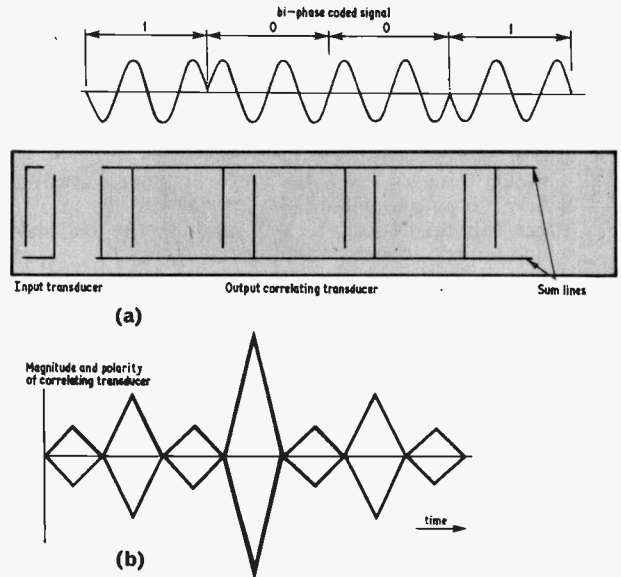


Fig. 8(a). A S.A.W. correlator may be used for detecting a particular sequence by arranging the taps to coincide with the desired signal. A typical output is shown in (b)

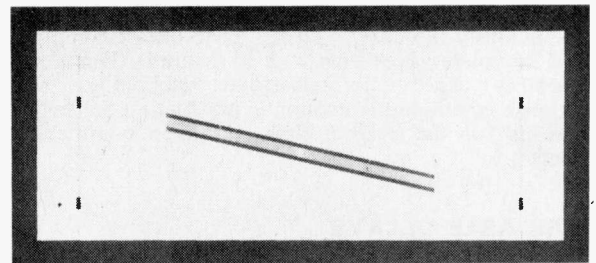

(a)

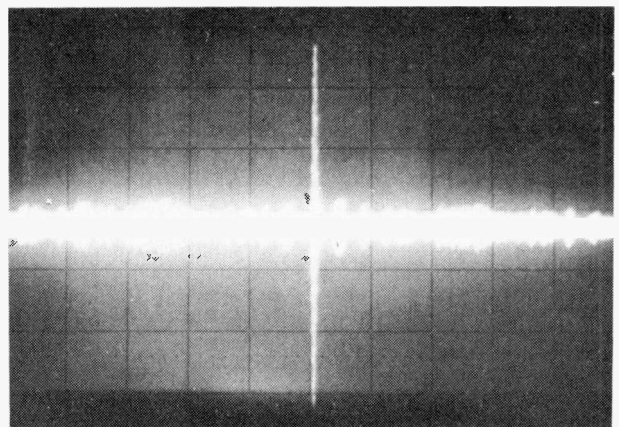

(b)

(G.E.C. Hirst
Research Centre)

Fig. 9(a). Photograph of an actual S.A.W. correlator which is capable of recognising a particular 127 bit sequence. The output transducer is inclined to minimise distortion due to its length. Photograph (b) shows the large peak produced when the sequence is recognised

The sum lines add these tap outputs to give a large pulse which indicates the signal has been recognised. Since the S.A.W. signal travels along the substrate under the taps it will cause small spurious signals before and after it is in the correct position to cause a large pulse; these are shown in Fig. 8b.

The photographs show a more ambitious example of a tapped delay line (Fig. 9a). It has 127 taps each

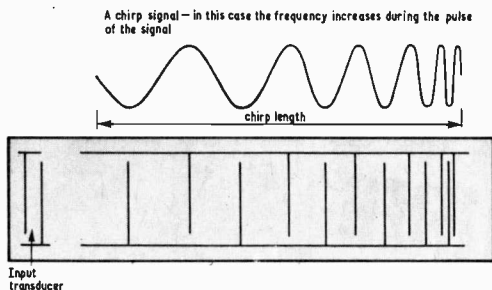


Fig. 10. By varying the spacing between taps as shown a "chirp" signal can be recognised

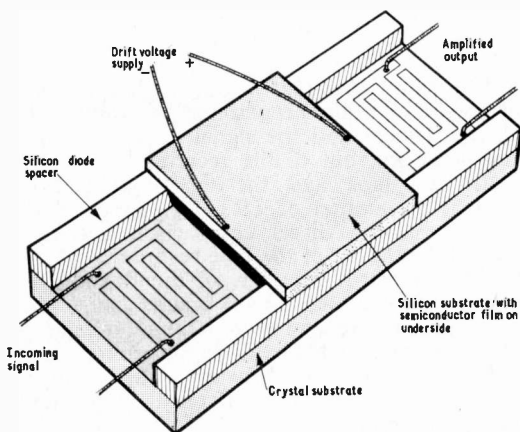


Fig. 11. The structure of an amplifier using S.A.W. principles

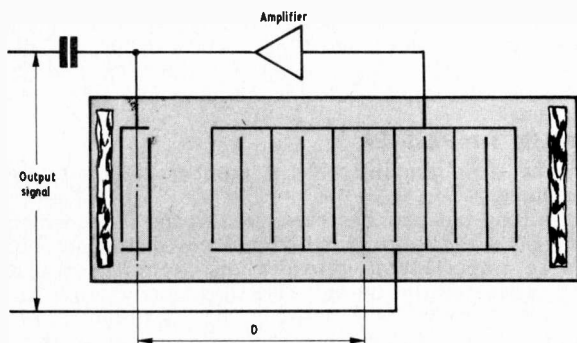


Fig. 12. A S.A.W. oscillator is produced by combining a bandpass filter with an external amplifier, the frequency of oscillation being determined by the spacing between taps on the S.A.W. crystal

of six finger pairs. Fig. 9b shows the output obtained from the large centre transducer, when the coded sequence is fed into the device. The detection pulse is easily recognised.

CHIRP DETECTION

If instead of bi-phase modulation a pulse of signal is used which is rising in frequency with duration, see Fig. 10. This could be detected by appropriately spacing the taps on a transducer as shown. The chirp system is common in radar systems.

AMPLIFIERS

The need for S.A.W. amplifiers is apparent in, say, a long delay line where attenuation of the wave by the crystal becomes the limiting factor in the achievable delay time.

The amplifier to be described makes use of the electric field generated by the S.A.W., travelling along a piezo-electric material, by causing it to interact with electrons travelling through this electric field.

Since the electric field is localised to the surface of the crystal, a conducting medium for the electrons has to be placed very near the surface, yet not touching, since this would distort the waves. Fig. 11 shows such an amplifier arrangement; a semiconductor film is used to conduct the electrons.

If the electrons are moving faster than the S.A.W. energy passes to the wave. Gains of up to 10^7 times are being achieved at present. These require voltages of several kilovolts across the semi-conductor film.

It is interesting to note that if the electrons in the semi-conductor film are travelling slower than the S.A.W., energy is removed from the S.A.W. and the electrons benefit. This property is useful in absorbing unwanted signals.

OSCILLATORS

The oscillator structure (Fig. 12) combines the filter layout mentioned earlier with an external amplifier. This amplifier returns the signal taken from the filter output I.D.T. to the input I.D.T. with an excess of gain. The frequency of oscillation is determined by the output I.D.T. and the spacing of the two transducers (D).

The number of finger pairs in the output I.D.T. determines the bandwidth whilst the spacing of the fingers sets the centre frequency. This bandpass filter then selects one of the many possible frequencies of oscillation, which are determined by the distance between the input and output I.D.T.s.

The range of frequencies presently possible is 20MHz to 1GHz. Oscillators above 300MHz will be small enough to fit inside transistor type TO-8 cans complete with their i.c. amplifiers.

Applications for these small, cheaply produced oscillators include TV tuners, low noise microwave sources and strain gauges.

SUMMING UP

It is seldom that one technique can achieve so much in such a short time. It is easy to see that this could be an area scheduled for intense activity and immense growth.

The combination of minimal power requirements (or none at all), microminiature construction, cheap mass production combined with a powerful signal processing capability must ensure the future of this branch of technology.



FOR SCINTILLATING SOUND



PE ORION

HI-FI STEREO AMPLIFIER

By D.S. GIBBS & I.M. SHAW C.Eng., M.I.E.E.*

THIS amplifier has been designed on a value for money basis to give the highest standard of performance compatible with a small case and a components budget of about £30. The result is a circuit with an output of over 20 + 20 watts into 8 ohm loads at less than 0.12 per cent distortion, in a case measuring only 14in × 6in × 2in.

This has been made possible by the use of a toroidal mains transformer, by the small size of the latest electrolytic capacitors and by the use of the case of the amplifier as a heatsink.

PRE-AMPLIFIER

The circuit of the pre-amplifier is shown in Fig. 1.1. Here TR1 and TR2 form a complementary feedback pair. This arrangement has excellent bias stability due to the d.c. feedback through R12. Both transistors are low noise types and TR1 is run at a bias current of only 150µA to minimise noise.

The equalisation components are connected in the feedback loop. R14, R15, C9 and C10 provide equalisation for magnetic pickups to within ± 1dB of the R.I.A.A. curve, between 20Hz and 20kHz, whilst R13 and C8 give a flat frequency response for the tuner and auxiliary inputs. No special equalisation has been provided for ceramic pickups as these seem to be falling out of favour nowadays, but ceramic pickups can be used with the magnetic equalisation by connecting passive matching networks of the type shown in Fig. 1.3 inside the record player plinth.

The frequency response of the disc, tuner, and auxiliary inputs is shown graphically in Fig. 1.2.

Emitter follower TR3 provides a high input impedance for the tape input and also enables a tape A/B facility to be provided. This is of particular value with tape recorders having separate recording and playback circuits as it enables one to make a direct comparison between the signal source and the

recording. For example, if one wishes to make a recording of a radio programme the input selector is set to "Tuner" and the signal passes through the input stages and out to the recorder. The signal is recorded on tape and the tape playback signal appears at the emitter of TR3. By operating S2 one can then make a direct comparison between the input and the output of the tape recorder.

The tone control circuit is of the Baxendall type and uses an integrated circuit operational amplifier. The very high gain and large output voltage swing of this i.c. are advantageous in obtaining very low distortion and a good dynamic range, whilst the signal level in this stage is sufficiently high to make the noise negligible.

The characteristics of the bass and treble controls are shown in Fig. 1.4. With the tone controls flat the circuit has an overall gain of 2 and gives an output of 200mV.

The scratch filter is a second order type and gives an initial slope of 12dB per octave from its 3dB point at 5kHz. The response of the filter and its effect on the treble control is shown in Fig. 1.5.

MAIN AMPLIFIER

The main amplifier has a number of interesting features.

A long tail pair has been used at the input which increases the loop gain and reduces distortion, but more important it provides an accurate ground reference for the output. The d.c. potential on the output terminal will normally be less than 50mV and this will ensure that any d.c. current through the loudspeaker is of negligible proportions. However, if an output transformer, or a loudspeaker containing a matching transformer (such as the Quad electrostatic) is used the d.c. resistance is then very

*Ferranti Ltd.

SPECIFICATION

Continuous Output Power

Load	Both channels driven	One channel driven
4 ohms	31+31 watts r.m.s.	44 watts r.m.s.
8 ohms	23+23 watts r.m.s.	30 watts r.m.s.
15 ohms	17+17 watts r.m.s.	19 watts r.m.s.

Measured at 1kHz

Toneburst Output Power

Load	Both channels driven	One channel driven
4 ohms	52+52 watts r.m.s.	57 watts r.m.s.
8 ohms	36+36 watts r.m.s.	42 watts r.m.s.
15 ohms	21+21 watts r.m.s.	22 watts r.m.s.

Measured with a 1kHz tone burst of 8 cycles on and 512 cycles off.

Distortion

15 ohm load—Less than 0.1 per cent at any power level up to 15 watts between 100Hz and 10kHz. Less than 0.02 per cent below 1 watt output.

8 ohm load—Less than 0.12 per cent at any power level up to 20 watts between 100Hz and 10kHz. Less than 0.02 per cent below 1 watt output.

4 ohm load—Less than 0.5 per cent at any power level up to 30 watts between 100Hz and 10kHz. Less than 0.05 per cent below 1 watt output.

Frequency Response

Tuner and Aux. inputs { —1dB at 28Hz and 15kHz
—3dB at 17Hz and 30kHz

Tape input { —1dB at 25Hz and 30kHz
—3dB at 14Hz and 60kHz

Disc input—Within 1dB of the RIAA curve between 20Hz and 20kHz

Tone Control

Bass ±12dB at 100Hz, ±18dB at 30Hz

Treble ±12dB at 10kHz, ±16dB at 20kHz

Scratch Filter

—3dB at 5kHz. Slope 12dB per octave

Inputs

Disc —3.5mV at 47k Ω RIAA equalised

Tuner—100mV at 100k Ω Flat response

Aux. —100mV at 100k Ω Flat response

Tape —100mV at 100k Ω Flat response

Tape Output

100mV at 4.7k Ω Tape A/B facility

Signal to Noise Ratios

Unweighted figures measured with a bandwidth of 20kHz.

Weighted figures follow CCIR C curve. Volume control at max.

Tuner, Aux. Unweighted —68dB,
Weighted —72dB

Disc. Unweighted —62dB,
Weighted —76dB

Tape Unweighted —76dB,
Weighted —82dB

(Figures are relative to an output of 20 watts into 8 ohms)

MAIN AMPLIFIER ONLY { Unweighted—96dB
(volume control at min.) { Weighted —100dB

Balance Control

Full rotation cuts off either channel

Dynamic Range

Disc input at 1kHz = 32dB (i.e. input of 150mV)

Interchannel Crosstalk

—50dB

Stability

Unconditionally stable. Will drive electrostatic loudspeakers

Output Impedance

Less than 0.1 ohms

Dimensions

14 × 6 × 2 in.


much lower than the speaker impedance and it is advisable to connect a resistor of about 0.5 ohms in series with the output of the amplifier.

This will reduce the output power by a few per cent but will minimise the d.c. current. In practice the resistance of the speaker leads will often be sufficient to provide the 0.5 ohm required.

The d.c. coupled output ensures that the speaker damping is maintained right down to d.c. giving a clean solid bass response. Normally, when a

speaker coupling capacitor is used, the reactance of this capacitor starts to become appreciable at low frequencies just when the most damping is required. The d.c. coupled output is made possible by the use of balanced positive and negative supply rails, and these also assist in obtaining clean symmetrical limiting under all load conditions.

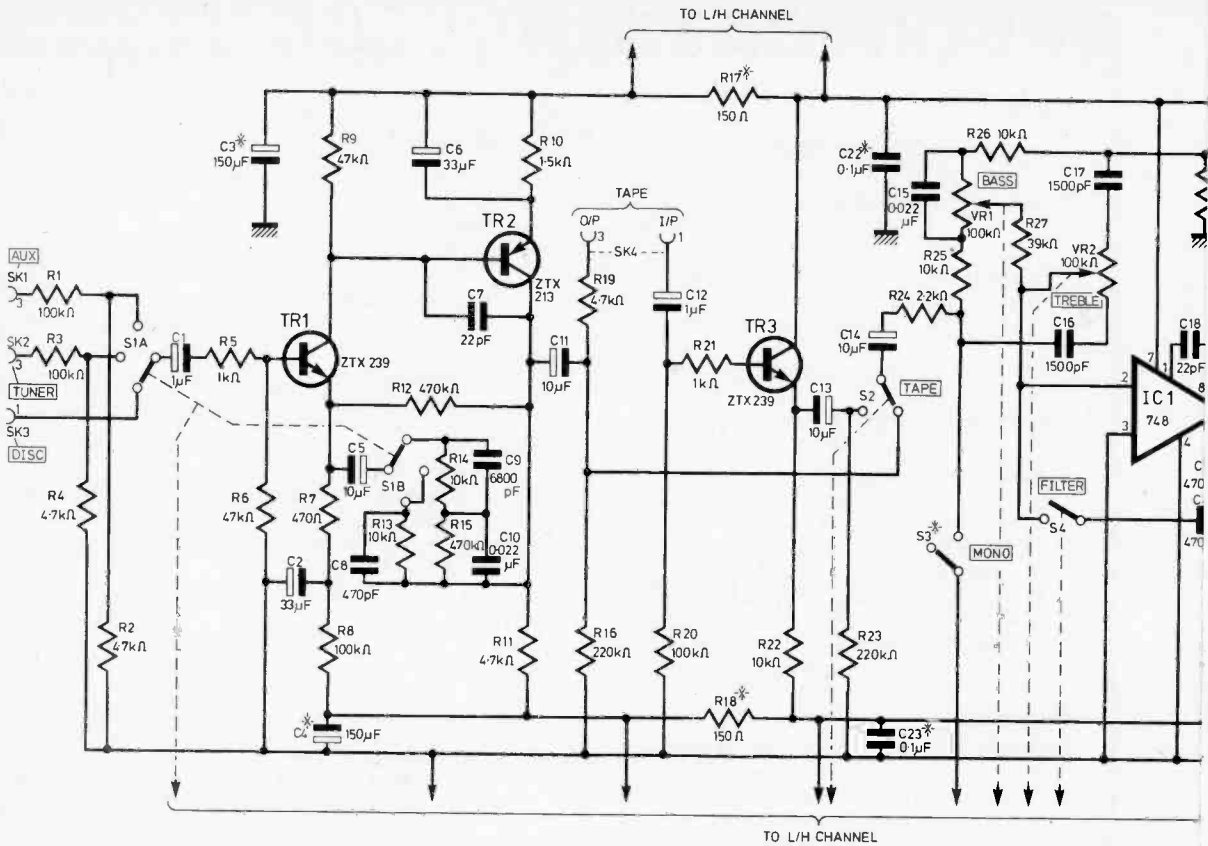The constant current source TR8 helps in obtaining low crossover distortion by providing a rapid transition of drive current between the two output



COMPONENTS . . .

Resistors

R1, R101	100kΩ	R25, R125	10kΩ
R2, R102	4.7kΩ	R26, R126	10kΩ
R3, R103	100kΩ	R27, R127	39kΩ
R4, R104	4.7kΩ	R28, R128	4.7kΩ
R5, R105	1kΩ	R29, R129	4.7kΩ
R6, R106	47kΩ	R30, R130	22kΩ
R7, R107	470Ω	R31, R131	1kΩ
R8, R108	100kΩ	R32, R132	2.2kΩ
R9, R109	47kΩ	R33*	470Ω 1W
R10, R110	1.5kΩ	R34*	470Ω 1W
R11, R111	4.7kΩ	R35, R135	100kΩ
R12, R112	470kΩ	R36, R136	1kΩ
R13, R113	10kΩ	R37, R137	22kΩ
R14, R114	10kΩ	R38, R138	4.7kΩ
R15, R115	470kΩ	R39, R139	3.3kΩ
R16, R116	220kΩ	R40, R140	1.2kΩ
R17*	150Ω	R41, R141	100kΩ
R18*	150Ω	R42, R142	4.7kΩ
R19, R119	4.7kΩ	R43, R143	100Ω
R20, R120	100kΩ	R44, R144	1.5kΩ
R21, R121	1kΩ	R45, R145	1kΩ
R22, R122	10kΩ	R46, R146	0.33Ω 2.5W
R23, R123	220kΩ	R47, R147	0.33Ω 2.5W
R24, R124	2.2kΩ	R48, R148	10Ω 1W

All $\frac{1}{2}$ W 5% carbon film unless otherwise rated
 Note: R17*, R18*, R33* and R34* are common to both channels; similarly for all other components asterisked

Potentiometers

VR1, VR101	100kΩ twin gang linear law (RS)
VR2, VR102	100kΩ twin gang linear law (RS)
VR3, VR103	10kΩ twin gang log law (RS)
VR4*	25kΩ single gang linear law (RS)
VR5, VR105	1kΩ skeleton preset (RS)

Capacitors

C1, C101	1µF 35V tantalum
C2, C102	33µF 16V elect.
C3*	150µF 16V elect.
C4*	150µF 16V elect.
C5, C105	10µF 25V tantalum
C6, C106	33µF 16V elect.
C7, C107	22pF 160V polystyrene
C8, C108	470pF 160V polystyrene
C9, C109	6,800pF 400V polyester
C10, C110	.022µF 160V polyester
C11, C111	10µF 25V tantalum
C12, C112	1µF 35V tantalum
C13, C113	10µF 25V tantalum
C14, C114	10µF 25V tantalum
C15, C115	.022µF 160V polyester
C16, C116	1,500pF 160V polystyrene
C17, C117	1,500pF 160V polystyrene
C18, C118	22pF 160V polystyrene
C19, C119	4,700pF 400V polyester
C20, C120	4,700pF 400V polyester
C21, C121	10µF 25V tantalum
C22*	0.1µF 30V disc
C23*	0.1µF 30V disc
C24*	470µF 25V elect.
C25*	470µF 25V elect.
C26, C126	1µF 35V tantalum
C27, C127	10µF 25V elect.
C28, C128	22pF 160V polystyrene
C29, C129	33pF 160V polystyrene
C30, C130	.1µF 250V polyester
C31, C131	22µF 63V elect.
C32, C132	22µF 63V elect.
C33, C133	.1µF 250V polyester
C34*	3,400 + 3,400µF 40V elect.
C35*	3,400 + 3,400µF 40V elect.
C36*	.01µF 750V disc

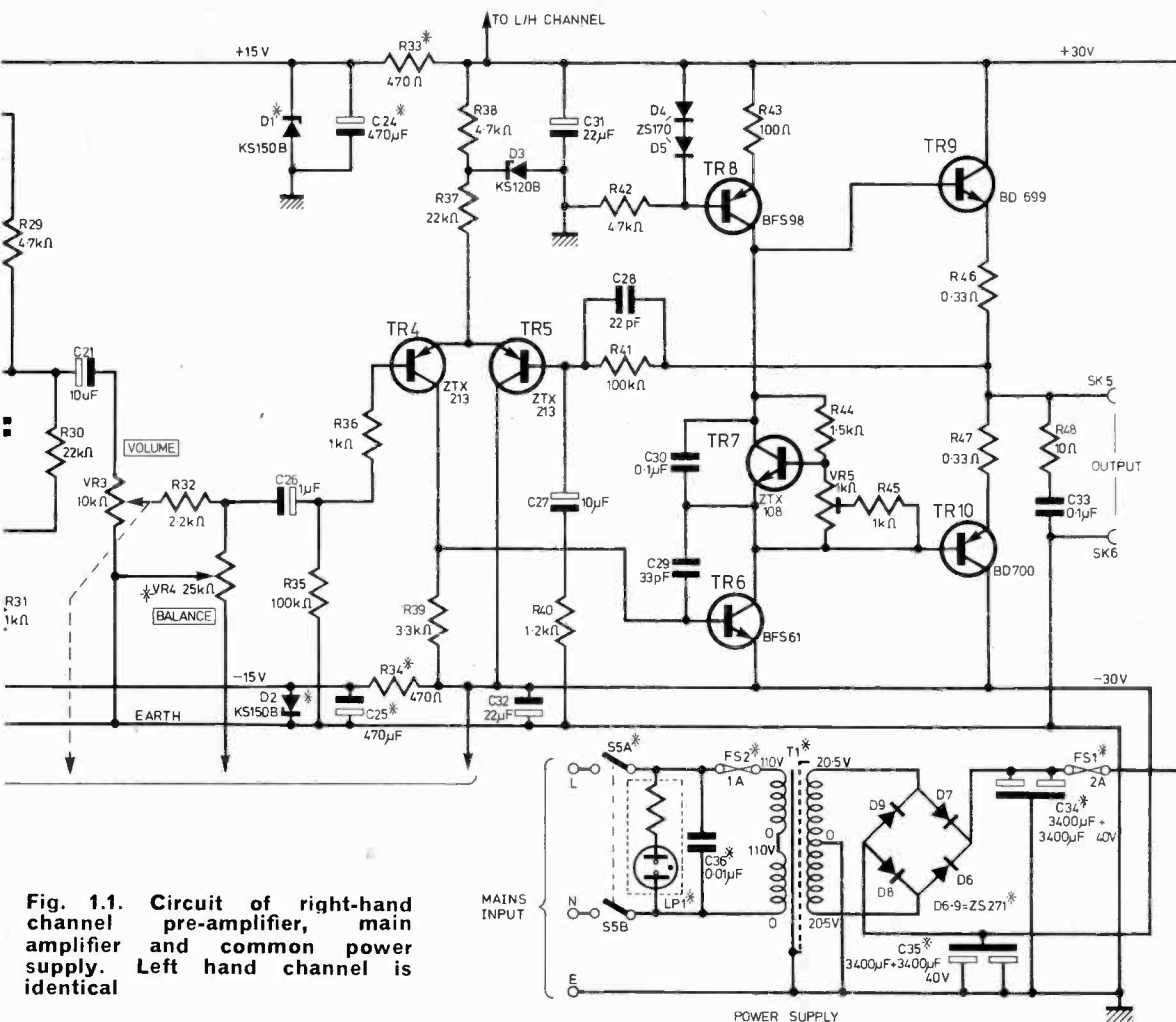


Fig. 1.1. Circuit of right-hand channel pre-amplifier, main amplifier and common power supply. Left hand channel is identical

Semiconductors

Recommended type	Alternatives
TR1, TR101 ZTX239 Ferranti	ZTX384, ZTX109C
TR2, TR102 ZTX213 Ferranti	ZTX214, ZTX530, ZTX502
TR3, TR103 ZTX239 Ferranti	ZTX384, ZTX109C
TR4, TR104 ZTX213 Ferranti	ZTX214, ZTX502, ZTX531
TR5, TR105 ZTX213 Ferranti	ZTX214, ZTX502, ZTX531
TR6, TR106 BFS61 Ferranti	ZTX451
TR7, TR107 ZTX108 Ferranti	ZTX238, ZTX239, ZTX109
TR8, TR108 BFS98 Ferranti	ZTX551
TR9, TR109 BD699 Motorola	BD699A
TR110, TR110 BD700 Motorola	BD700A
D1*, D2* KS150B Ferranti	KS150A
D3, D103 KS120B Ferranti	KS120A
D4, D104 ZS170 Ferranti	Any ZS170/270 series diode
D5, D105 ZS170 Ferranti	Any ZS170/270 series diode
D6*, D7*, D8*, D9* ZS271 Ferranti	ZS272, ZS274, ZS276 or ZS278
IC1, IC101 UA748CV Signetics	Texas SN72748P

Switches

- S1A, S1B, S101A, S101B 4-pole 3-way rotary (Lorlin)
- S2, S102 2-pole changeover pushbutton (RS)
- S3* 2-pole changeover pushbutton (RS)
- S4, S104 2-pole changeover pushbutton (RS)
- S5 D.p.s.t. rotary mains switch (RS)

Miscellaneous

- T1 Gardners mains transformer type SL8, 20.5-0-20.5 volts
- LP1 Neon panel lamp with internal resistor
- Case—H.M. Electronics type GB3
- Stereo jack socket, 4-DIN 5 way sockets, four 4mm sockets, five control knobs, three push-button switch buttons (RS), two Eagle 20mm fuseholders, 1A fuse, 2A fuse, four Lektrokit spring clips type LK2791 (1.5in), five way tag-strip, screws, spacers, grommets, aluminium angle, connecting wire.
- A glass fibre printed circuit board printed with component locations, and a kit of semiconductor devices for this project are available from Davian Electronics, PO Box 38, Oldham, Lancs.

transistors. Bias transistor TR7 operates in the "amplified diode" mode and is thermally coupled to the output transistors by being clamped to the heat-sink. This gives a great improvement in bias stability as any increase in heatsink temperature is compensated for by a reduction in bias.

OUTPUT TRANSISTORS

The output transistors TR9, TR10 on the circuit diagram are shown as single transistors for simplicity, but they are in fact monolithic Darlington pairs with a minimum current gain of 750 at 3 amps. These transistors have proven themselves to be electrically very robust and we have found that a 2 amp fuse in the positive rail is adequate to protect them against short circuits on the output.

Note that the fuse should be connected in the positive rail and not the negative rail. When the positive supply is removed the whole main amplifier is turned off because the bias is removed from the constant current source TR8, and also from the input stage TR4 and TR5. This in turn turns off TR6.

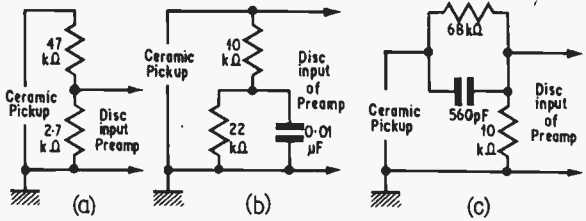


Fig. 1.3 (a). Circuit giving approximate matching for most types of ceramic pick-up; (b) circuit for matching the Decca Deram ceramic pick-up; (c) circuit for matching the Sonotone 9TAHC ceramic pick-up

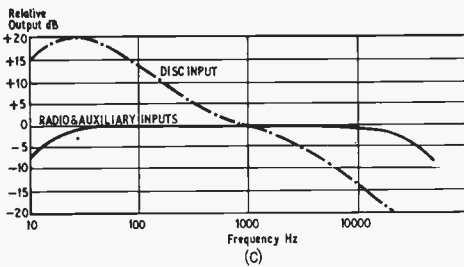


Fig. 1.2. Frequency response of disc, tuner and aux inputs

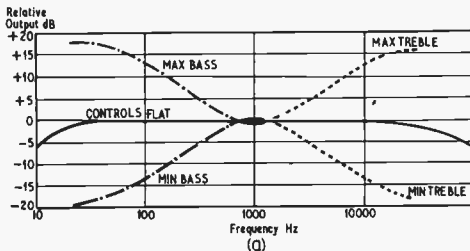


Fig. 1.4. Frequency response of the tone controls

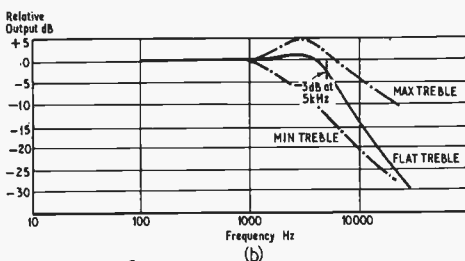


Fig. 1.5. Frequency response of the scratch filter

POWER SUPPLIES

When one is designing a small, low cost amplifier the finest refinement that one has to do without is the use of a stabilised power supply. This introduces a number of problems, but there are compensating advantages.

The problems arise because of the lack of stabilisation. To get 20 watts output into an 8 ohm speaker we need a power supply which will deliver 45 volts on load. But when the amplifier is not giving any output and there is only a light load on the power supply, its voltage can easily rise to 60V. If we allow for mains voltage variations, then under the worst conditions the supply voltage could reach nearly 70V. With a stabilised power supply output transistors rated at 50V would have been satisfactory, but with our unregulated supply we need output transistors which will stand at least 70V. Not only this but all the electrolytic capacitors need to be conservatively rated as well.

The unregulated power supply does however have one very great advantage. A musical signal has a low average power level with occasional peaks of high power. For a short period (until the power supply voltage drops)-an amplifier with an unregulated supply can deliver a power output very much greater than its continuous rating. This amplifier will deliver 23 watts per channel continuously into 8 ohms, but on a musical signal it is almost as good as a 35 watt amplifier.

Lastly it might be as well to clear up exactly what we mean by continuous power. With 15 ohm loads the power dissipation is sufficiently low for the amplifier to be run at full sinewave power continuously. With 8 ohm loads it will also safely run continuously provided that it is placed in a well ventilated position where air can circulate freely around it, but the back of the amplifier tends to become rather hot after about 30 minutes of full sinewave power. With 4 ohm loads the amplifier should not be run at full sinewave power for more than about 10 minutes at a time, or the temperature of the output transistors may become excessive.

One does not normally listen to sinewaves of course and with a normal music or speech input the amplifier can be run continuously at full volume without any reservations.

DISTORTION

At full output the distortion introduced by the other components in the hi-fi system will be much greater than that of any reasonable amplifier. Moving coil loudspeakers can generate up to 10 per cent distortion and even electrostatic types can give 0.5 per cent. A good modern f.m. tuner can generate 0.5 per cent., a tape recorder about 2 per cent, and a gramophone pickup can reach as much as 20 per cent on the inner grooves. Compared to these figures the performance of all but the most mediocre amplifiers is adequate at full output.

There lies the snag. All the signal sources may have considerable distortion at full output, but the distortion falls rapidly at lower levels. This is not necessarily the case with an amplifier. If crossover distortion is present the distortion may be only 0.1 per cent at full output but may easily rise to 1 per cent or more at low levels. Crossover distortion is particularly unpleasant because it generates high order harmonics, which are discordant and easily perceived.

For crossover distortion to be negligible it should be less than 0.1 per cent at all power levels. Low order harmonic distortion is less objectionable and up to 0.5 per cent can be tolerated. So we can say that our amplifier should have a distortion specification of no worse than 0.5 per cent at full output, and below 0.1 per cent at all power levels below 1 watt.

The use of a constant current source in this amplifier has helped us to achieve a very low level of crossover distortion—typically about 0.01 per cent at 1 watt—and with 8 or 15 ohm loads the harmonic distortion is below about 0.1 per cent at all power levels up to full output. With 4 ohm loads the performance does not reach quite the same standard, but it is still below 0.1 per cent at 1 watt and 0.5 per cent at full output.

FREQUENCY RESPONSE

Many constructors are firmly convinced that a very extended frequency response is a good thing. This is a complete fallacy because—

1. Human hearing extends from about 20Hz to 20kHz at the best. There is some evidence that transients containing harmonic components above 20kHz can be distinguished but there is certainly nothing to be gained by extending the response past 40–50kHz.
2. There are very few loudspeakers with any useful response below 30Hz or above 20kHz.
3. There are no radio signals with any audio above 15kHz.
4. There are no records or cassettes with any audio above 20kHz.

In fact the only audio signal available which might have anything above 20kHz would be a very high quality tape recording of a live performance.

A very extended frequency response can be a very bad thing. If the low frequency response is very extended then low frequency noise from turntable rumble, warped or off centre records, or tape recordings can get through the system and cause the

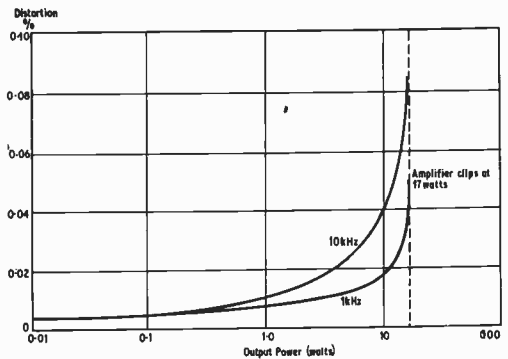


Fig. 1.6. Distortion against output power for 15 ohms measured at 1 and 10kHz

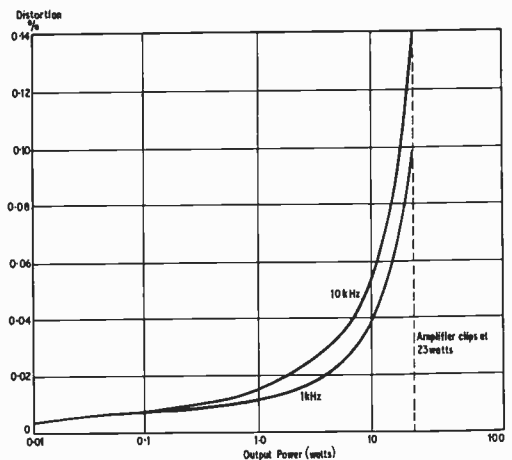


Fig. 1.7. Distortion against output power for 8 ohms measured at 1 and 10kHz

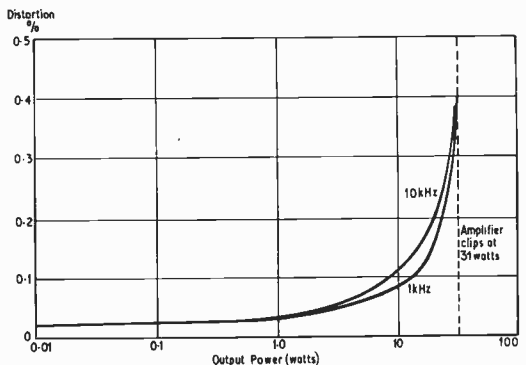


Fig. 1.8. Distortion against output power for 4 ohms measured at 1 and 10kHz

speaker cone to flutter violently. If the h.f. response is very extended then h.f. noise and multiplex sideband components can intermodulate with each other and with h.f. audio signals to produce audible distortion and noise. So what is the ideal response? Probably something like 20Hz to 50kHz \pm 3dB.

This amplifier has been designed so that the frequency response falls rapidly below 10Hz, and so

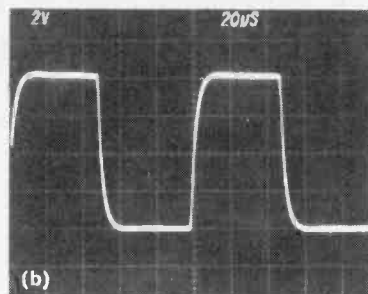
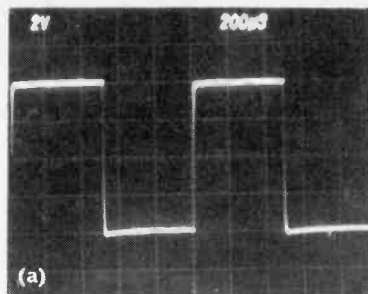
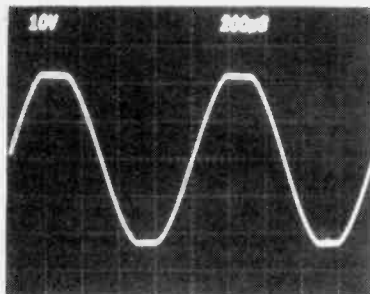


Fig. 1.9. Output waveform of the amplifier when slightly overdriven with a 1kHz sine wave showing the clean symmetrical limiting with freedom from latch-up

Fig. 1.10 (a). 1kHz square wave response with 8Ω resistive load; (b) 10kHz square wave response with 8Ω resistive load; (c) 10kHz square wave response with load of 8Ω and 0.1µF; (d) 10kHz square wave response with a load of 8Ω and 2µF

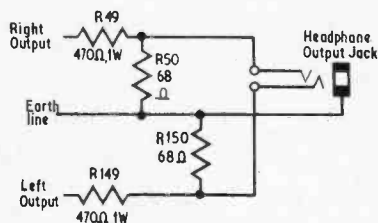
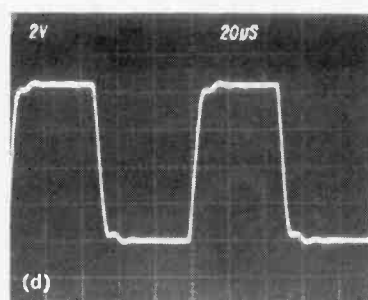
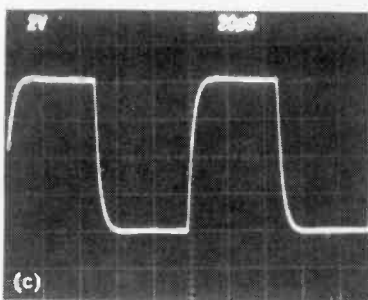


Fig. 1.11. Headphone attenuator circuit if required. Note that resistors have been omitted from Components List

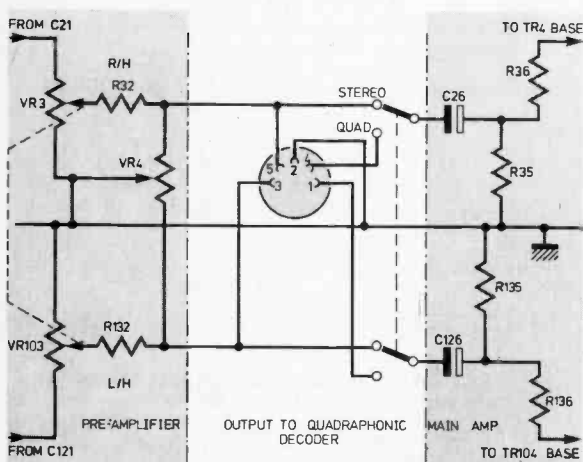


Fig. 1.12. Connections for quadrasonic decoder. DIN socket connections are as follows:—

1. Left channel front input from decoder
2. Earth
3. Left channel output to decoder
4. Right channel front input from decoder
5. Right channel output to decoder

a separate rumble filter is not necessary. The h.f. response of the tape input extends to 50kHz but the radio input has been restricted to 30kHz to attenuate multiplex and carrier components. With the scratch filter switched in all the inputs are 3dB down at 5kHz.

TRANSIENT RESPONSE

For good reproduction it is essential that the amplifier should have a good transient response with as little ringing as possible, even when fed into a highly reactive load such as an electrostatic loudspeaker.

In this amplifier a particular effort has been made to achieve a good transient response and Fig. 1.10 shows the performance of the amplifier under various load conditions. Note that with a 2µF capacitive load the ringing is of very low amplitude and soon dies away. If a 0.5 ohm resistor is connected in series with a 2µF load (as we recommended for the Quad speaker), then even this small amount of ringing is completely eradicated.

QUADRAPHONICS

No special provision has been made for quadrasonics in the prototype, mainly because of lack of space, but it is a simple matter for the enthusiast to adapt the circuit for use with a quadrasonic decoder.

All that is necessary is to break the connection between the preamplifier and the main amplifier and replace it with a switch and a DIN input socket, as shown in Fig. 1.12. The two front channels can then be fed back into the Orion main amplifiers whilst the back channels are fed to another amplifier. An additional pair of Orion main amplifiers would be ideal for this purpose.

Next month: Constructional details and setting up.

RE-READING one of the earliest publications on electronic music recently I came across the following statement made by Herbert Eimert, founder of the Cologne Radio Electronic Music Studio:

"That—electronic music cannot be performed on instruments is due to the fact that the number of individual sound elements is so great that any attempt to find means of instrumental realisation is doomed to failure."

One's immediate reaction is to wonder whether he would have ventured to say this now, in the age of the synthesiser, when many pop groups have some kind of synthesiser.

Perhaps even twenty-odd years ago, when Eimert's article was written, there was little excuse for such a statement; the electronic and electrophonic instrumental field was by then quite sophisticated. A little relatively recent history may be pulled in here to support, or maybe excuse, his apparently negative remark.

The Years Between

In the years between the two world wars Arnold Schoenberg, Austrian composer, systematised the 12 notes of the traditional chromatic scale to produce music which did not rely on key (i.e. the predominance of one note over any other) but used all the available pitches equally. Amongst his pupils was Anton Webern who went a stage further than his master; rather than treating the 12 notes in a fairly conventional linear manner he perfected a style of writing which laid weight on each individual note as and when it occurred in the musical flow.

The dynamic levels, pitch and timbre were carefully controlled in his sparsely written aphoristic instrumental and vocal compositions.

Lionised Webern

After the war a group of young German musicians picked up the almost submerged threads of these revolutionary concepts and made Webern their idol. Reinforced by similar pre-organised, or serial, ideas put forward in works by the French composer Olivier Messiaen, these young intellectuals went on to produce a new music in which all the parameters available to music were fully exploited, almost mathematically. The musical results were often impossible to perform by human beings, yet the European scene rapidly became thick with "avant-garde" concerts, many of dubious integrity.

That any worthwhile music has survived this period is a minor miracle, given the arrogance of the exponents and the loud raspberries



of the musical press.

It was during this babel of activity that the tape recorder came into general use, and with it the very latest in sensational sound, electronic music. Anything essentially of an acoustic nature was taboo. Needless to say electronic compositions were meticulously edited and fixed for all time on magnetic tape.

Colouristic Effect

Meanwhile in France there was another little sonic revolution taking place. Whilst those who whored after strange gods studied the latest serial techniques in Germany, others stayed behind to practice the art of colouristic effect for which the French have always been renowned.

Pierre Schaeffer founded a studio in Paris dedicated to the study of the physics and psycho-physics of acoustic phenomena and to the production, on discs initially, of musical compositions which took raw, natural sounds as their starting point. Plain aural effect was the ambition; Schaeffer and his colleague Pierre Henry had little time for the intricate number games which the Germans were playing. The search for "musique concrete" [natural or non-abstract music] ended with the arrival of the tape recorder and the simplicity of editing magnetic tape.

Partisan Factions

So electronic music began life in two partisan factions: the German-influenced found the French "musique concrete" positively naive and artless, whilst the French considered the Germans inhumanly mathematical

and equally artless. Both came together, however, in considering their respective tape compositions to be one-off, once-and-for-all performances.

Live electronics

So Eimert was right. Given the complexity of a totally serial composition with its rapidly changing rhythmic, pitch, spatial, dynamic and timbre elements, only a taped sequence could do justice to a particular concept. No amount of juggling around with electronic organs and peripheral sound effect units would reproduce on the concert platform what could be realised on tape.

The same applies to Schaeffer's collages, where natural sounds, recorded wherever they existed, were processed electronically, the result defying any musical instruments—save perhaps the Melotron, which is nothing more than a filing cabinet of tape recordings with a piano keyboard attached. Eimert lacks credence in his underlying assumption that Electronic Music is a *style* rather than a medium of expression.

Today's Electronic Music


In today's Electronic Music the factions have largely disappeared; Stockholm has cast off the strait-jacket of total serialisation and in his taped works uses the human voice, gramophone records, short-wave radios and acoustic instruments. Schaeffer and his colleagues rely quite heavily on purely electronic sound producers.

Along with this fusion of two differing approaches to taped material came the feeling that performers ought to take some share in the interpretation of this kind of music; hence "Live electronics".

Pop Sounds

By far the largest purveyors of live electronics are the pop groups. (Only a pedant would argue that their music is not strictly electronic.) Electronic instruments work admirably here since most of the music performed is geared to the traditional pattern of twelve notes to the octave and is old fashioned enough to use fairly common juxtapositions of these notes. Above all, pop-music is primarily melodic music and this means that a given instrumental line is unlikely to require rapid changes of timbre.

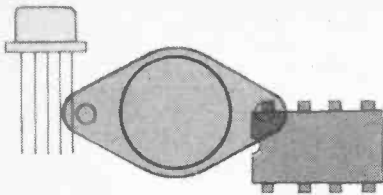To some extent "serious" live electronic groups have taken a lead from the pop world; the music they perform is no more complex to realise than an equivalent piece of acoustic instrumental music. Should they require complex arrangements of sound these still have to be pre-recorded on tape.



THE NEXT DECADE ?

Final selection of readers' predictions

ARMCHAIR VIEWING

I BELIEVE that in the next decade we could well see many changes in our everyday life due to electronics. Instead of travelling to conferences, businessmen might stay at home and "attend" the conference via video and audio links to a central conference control, through which they would be able to see and hear their colleagues. They would also be able to "look up" relevant information through the conference control and have it displayed on their screens for as long as they wish.

We could watch any television (if it could rightly be called this) programme whenever we pleased.

The printing world can throw away its presses, for we will be able to dial for, say, the front page of today's newspaper and have it displayed on our "newscreens." Yes! even our beloved *Practical Electronics* will come to us like this. (Don't worry Ed., you will still be needed.)

No-one will have to think as much, for we will all have our own computer calculators, and musical instruments will be replaced by synthesisers, so that the Pablo Casals' of tomorrow will play upon streamlined keyboards instead of peculiarly shaped pieces of wood.

All this sounds rather unlikely? Well, you wait and see.

S. J. Baxendale.

COMMON PLACE

IN the next ten years no progression is foreseeable in the direction of component miniaturisation, owing to the impossibility of decreasing pin and encapsulation size. It is likely that more will be fitted into a single module—Mr. Shaw's synthesiser on a chip, for example.

Specialisation of these circuits is almost inevitable, specifications going further and further towards the extreme, with fantastic power handling and even more fantastic frequency ranges, now only the dream of hi-fi enthusiasts. Technology cannot be underrated in sorting out the problems which may make these two characteristics (now) incompatible.

For the home constructor, today's high-powered technology may be tomorrow's workbench experiment. A home made integrated circuit kit for example; which is not such a far fetched idea if one looks at the basic simplicity

of overlaying the semiconducting layers, assuming there will be enough semiconducting material left by tomorrow!

Soon one may be able to leaf through a catalogue of "surplus" equipment, which at present is described as a technological breakthrough. Basic techniques could soon be outmoded, soldering and the printed circuit board might soon be replaced by the plug-in module.

In conclusion, it could be said that in the next decade, though there may not be the advances of the like of the integrated circuit in the last ten years, technology will push its usage to the limits. Also, present technology will be commonplace to the constructor in not so many years.

N. J. Eastaugh

MAN AND HIS ELECTRONICS

THE philosophy of electronics in the next decade is summed up by "digital is best, and smaller is better".

Compromised by cost, and using the results of researches into the nature of human perception, manufacturers will set lower standards of sound and image reproduction.

Enthusiasts will reconstruct the electronic achievements of the 1920's with antique components or replicas made by new cottage industries.

A wide range of games-machines designs will be published for the constructor. At best, they will be war games, or a form of Monopoly in which the players are relieved of the arithmetic of accounting and cannot break the rules.

The power of present-day mini-computers will be available in a single i.c. costing £20, or less.

The military applications of micro-electronics will shock and horrify us, but the constructor will find light relief from the problems of the day by assembling the parts of a micro-computerised mouse for his cat to play with.

There will be great interest in the generation of special effects. Today's Wind and Rain generator will be supplemented by tomorrow's Thunder and Lightning, the degree of authenticity rising according to ingenuity and the size of purse.

Electronic musical instruments will have substantial computer power, and the constructor will spend more time in programming than constructing his

creations, having purchased programmes from the lists in the advertisement pages of his favourite journal, P.E.

Seated at the console of his electronic organ, engaged in extempore musical invention, such will be the interaction between man and his electronics that the player may well exclaim from the profundity of philosophical doubt, "Just who is playing this machine?" The folly of the decade will be an attachment for colour TV receivers to permit the display of electronically simulated goldfish.

D. Letts

HIGHER QUALITY

THE next decade will not unveil any major electronic breakthroughs but instead, in a time of financial instability, manufacturers will concentrate on improving the quality of goods already available, the risks being too great for a large scale venture into something radically new. Maximum profit being essential, the fear of failure in a component would be too daunting.

Transistors and integrated circuits will continue to be the main "workbench" of electronics, both on an amateur and professional scale. The valve will still command itself a place but will always run a poor second to the modern semiconductor, as I feel it does now.

With everybody striving to attract the prospective customer to their particular line of components there will inevitably be many new i.c.s on the market, having better power handling capacities and such-like in an effort to better their predecessors, but none of them will be fundamentally different.

A shortage of raw materials, evident at the present time, will mean price rises and delivery delays (nothing new!) This could also result in the amalgamation of many small component retailers who would otherwise be forced into liquidation by the bigger concerns cornering all the custom.

The overall trend will be to encapsulate the components in plastic containers which constantly seem to diminish in size.

Finally, the high degree of competitiveness between manufacturers will result in a higher quality of components—which can only be to the good of the constructor in the end.

M. S. Johnson

ELECTRONIC LABEL

THE present trend of improvement in electronic technology is likely to provide some new and perhaps exciting uses of the circuits as we know them. It may be taken for granted that they will reduce in size, become more reliable and presentable, and who can say how long they would last.

The reading of domestic meters by remote computer, preparation of account, and even automatic payment of the bill by pre-arrangement, is but one aspect.

It is likely that television receivers will be used in the dual role of entertainment or access to information, such as availability of goods or prices. The telephone line perhaps, would be switchable to a number of facilities, with a "back up" visual display.

One possible change is in the use of pocket, or desk calculators. It is quite feasible to envisage these being used as mini computers without major circuit change. For instance, with a microfilm attachment, and "access code" operation using the same styled keypad, the film could be rotated by the command word, and illuminated on a slightly enlarged screen.

Finally, how about the "Electronic Label", a microcircuit, so small that it could be incorporated into almost any article at the manufacturing stage, and with its own identity calling signal, quiet, unless called by a master beacon. Nasty though, if you want to go into a pub for a quick one and the wife is looking for you!

A. J. Williams

DIGITAL TRACKS

THE next decade will be dominated by political change, which will include higher taxation for the individual, and wage rates so high that the cost of maintenance and repair will often exceed the value of the article to be repaired.

The first item will make it unlikely that the colour television boom will be repeated with video cassette recording or the Ceefax/Oracle system. However, this may well give rise to a new system of video recording towards the end of the period using digital methods with about 150 narrow tracks instead of the helical scan system with its mechanical complexity.

Such a change would be less likely if a large number of helical scan recorders were already in use.

The lack of money in the hands of individuals will be compensated by more in the hands of government, who will spend more on electronics.

One possibility taken at random could be a distress calling system for old and disabled people. The caller presses a button that activates a device to send a high frequency signal into the local mains electricity network. This signal is modulated by a series of pulses representing a number allocated to the caller.

A warden who has a receiver on the same local mains ring is alerted that the caller is in trouble.

A second is the introduction of automated speed traps, made necessary by increasingly restrictive speed limits due to overcrowding and fuel shortages. These would photograph offenders' cars showing the speed on a print-out. An official would collect the photographs every so often. To avoid the possibility of malfunction causing injustices, offenders would be prosecuted if caught more than once in a set period of time.

The second item, wages, will lead to novel methods of improving reliability of electronic goods. Touch-operated integrated circuit sub-systems will replace potentiometers and switches, and possibly i.c. optical modulators and demodulators coupled with optical fibres will replace plugs and sockets for connecting audio discrete units.

J. de Rivaz

INTEGRATED I.C.'S

TEN YEARS is not a long time, but I believe that man will advance more in the next ten years than in the last ten. After long consideration I came to the conclusion man's advancement was of a logarithmic nature and not a linear one. Our greatest advancement will be in the field of i.c.s and their interconnection.

Soon we will see the inductor being incorporated in i.c.s and midway through the decade we will see the key to a new kind of electronics. No more will i.c.s be coupled by wires, coupling will be similar to the lecher lines used in u.h.f. tuners. Simply placing the i.c.s one on top of another, rather like the child's building bricks only in a miniature form. From this giant leap electronics will virtually know no bounds. The solid state power pack recharging itself from air, light, heat, or vibration, for example.

Air and light may be used, as in plants, to create chemical changes. These we can change into electrical energy. Heat given off due to power loss will be channelled back to the power pack to help recharge power cells. Vibration as used in self winding watches, used to generate power.

These advancements will lead to vast developments, such as the pocket computer, rather similar to the pocket calculator we have today, only thousands of times better and incorporating an audio output.

Programme cartridges will also be solid state, as in microfilm one small block containing many hundreds of hours of information.

Such an instrument would place the home constructor almost on a par with the professional.

Roll on 1984.

A. Tannock.

DIODES AND ALL

EXPERIENCE shows that the development of technology follows something akin to a log. law curve. In semiconductor technology there has been a veritable explosion of new ideas and techniques. If interpolation of this curve is attempted then the results can be somewhat surprising.

Today's computers using holographic or ferrite memory stores are far too cumbersome, slow and expensive. Development of heavy metal organo compounds already well under way should bring about the production of high temperature (in excess of 100°K) superconducting memory stores:—possibly a very primitive forbear of Asimov's positronic brain!

For constructors, i.s.i. circuits are already available, the question remains how large (or small) can they get and for what purpose. Pocket calculators already have chips containing thousands of active elements, and I rather think that today's constructor in ten years will be in much the same boat as those are now who lament the passing of the valve, we shall be lamenting the passing of the discrete transistor.

Looking back, most developments seem to stem from the humble diode, the latest being the ubiquitous l.e.d. so the logical development of this would be the "light emitting transistor"—alter the base bias and "hey presto"; modulated light output.

E. J. Marchant.

SIMPLIFICATION

THE following decade, for myself and fellow constructors, should bring simplification in the form of reduced wiring and soldering for more complicated circuits with increasing use of i.c.s.

With spiralling cost of most products, the hope of continued amateur construction may lie in continued progress in i.c. technology to reduce manufacturing costs.

For the home constructor whose use of i.c.s was exclusively bipolar (TTL), he may find himself making adjustments in the not too distant future towards a different form (CMOS). In this increasing energy-conscious world, the life of the bipolar form of logic could be drawing to an end, with less power consuming logic forms such as CMOS becoming more and more popular.

Amateurs and professionals over the coming years will be made more power conscious and a tendency towards battery supplies in contrast to more expensive a.c./d.c. Transformation will be encouraged as a practical step for the home constructor.

Manufacturers will be responsible for this trend, as they become more aware of producing the form of logic which will be more financially secure for the future.

S. Naismith

Now - two fascinating ways to enjoy saving money!

NEW! Sinclair Scientific kit **£19.95** (INC.VAT)

Britain's most original calculator now in kit form

The Sinclair Scientific is an altogether remarkable calculator.

It offers logs, trig, and true scientific notation over a 200-decade range — features normally found only on calculators costing around £100 or more.

Yet even ready-built, the Sinclair Scientific costs a mere £32.35 (including VAT).

And as a kit it costs under £20!

Forget slide rules and four-figure tables!

With the functions available on the Scientific keyboard, you can handle directly

- sin and arcsin,
- cos and arccos,
- tan and arctan,
- automatic squaring and doubling,
- log₁₀, antilog₁₀, giving quick access to x^Y (including square and other roots),
- plus, of course, addition, subtraction, multiplication, division, and any calculations based on them.

In fact, virtually all complex scientific or mathematical calculations can be handled with ease.

So is the Scientific difficult to assemble?

No. Powerful though it is, the Sinclair Scientific is a model of tidy engineering.


All parts are supplied — all you need provide is a soldering iron and a pair of cutters. Complete step-by-step instructions are provided, and our Service Department will back you throughout if you've any queries or problems.

Of course, we'll happily supply the Scientific or the Cambridge already built, if you prefer — they're still exceptional value. Use the order form.

Components for Scientific Kit (illustrated)

1. Coil
2. LSI chip
3. Interface chips
4. Case mouldings, with buttons, windows and light-up display in position
5. Printed circuit board
6. Keyboard panel
7. Electronic components pack (diodes, resistors, capacitors, etc)
8. Battery assembly and on/off switch
9. Soft carrying wallet
10. Comprehensive instructions for use

Assembly time is about 3 hours.

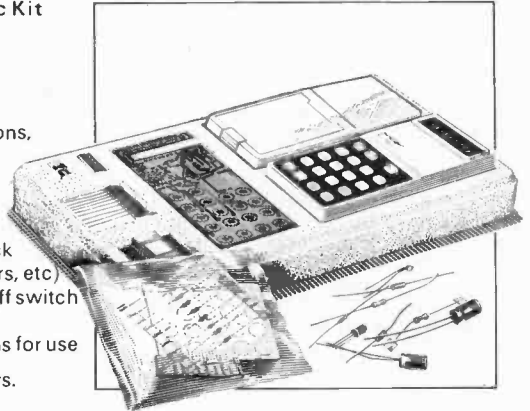

Features of the Sinclair Scientific



- **12 functions on simple keyboard**
Basic logs and trig functions (and their inverses), all from a keyboard as simple as a normal arithmetic calculator's. 'Upper and lower case' operation means basic arithmetic keys each have two extra functions.
- **Scientific notation**
Display shows 5-digit mantissa, 2-digit exponent, both signable.
- **200-decade range**
10⁻⁹⁹ to 10⁺⁹⁹.
- **Reverse Polish logic**
Post-fixed operators allow chain calculations of unlimited length — eliminate need for an = button.
- **25-hour battery life**
4 AAA manganese alkaline batteries (e.g. MN2400) give 25 hours continuous use. Complete independence from external power.
- **Genuinely pocketable**
4 1/3" x 2" x 11/16". Weight 4 oz. Attractively styled in grey, blue and white.

Sinclair Cambridge kit

Now only
£14.95
 (INC. VAT)

At its new low price, the original Sinclair Cambridge kit remains unbeatable value.

In less than a year, the Cambridge has become Britain's most popular pocket calculator.

It's not surprising. Check the features below – then ask yourself what other pocket calculator offers such a powerful package at such a reasonable price.

Components for Cambridge Kit

1. Coil
2. LSI chip
3. Interface chip
4. Thick film resistor pack
5. Case mouldings, with buttons, window and light-up display in position
6. Printed circuit board
7. Keyboard panel
8. Electronic components pack (diodes, resistors, capacitors, transistor)
9. Battery clips and on/off switch
10. Soft wallet

Assembly time is about 3 hours.

Take advantage of this

money-back, no-risk offer today

The Sinclair Cambridge and Scientific kits are fully guaranteed. Return either kit within 10 days, and we'll refund your money without question.

All parts are tested and checked before despatch – and we guarantee any correctly-assembled calculator for one year. (This guarantee also applies to calculators supplied in built form.)

Simply fill in the preferential order form below and slip it in the post today.

Scientific

Price in kit form £19.95 inc. VAT.

Price built £32.35 inc. VAT.

Cambridge

Price in kit form £14.95 inc. VAT.

Price built £21.55 inc. VAT.

Features of the Sinclair Cambridge



- Uniquely handy package. 4 1/3" x 2" x 11/16", weight 3 1/2 oz.
- Standard keyboard. All you need for complex calculations.
- Clear-last-entry feature.
- Fully-floating decimal point.
- Algebraic logic.
- Four operators (+, -, ×, ÷), with constant on all four.
- Powerful constant with separate 'K' button.
- Constant and algebraic logic combine to act as a limited memory, allowing complex calculations on a calculator costing less than £15.
- Calculates to 8 significant digits.
- Clear, bright 8-digit display.
- Operates for weeks on four AAA batteries.

To: Sinclair Radionics Ltd,
 FREEPOST St Ives,
 Huntingdon, Cambs. PE17 4BR

Please send me

- Sinclair Scientific kit at £19.95
- Sinclair Scientific built at £32.35
- Sinclair Cambridge kit at £14.95
- Sinclair Cambridge built at £21.55

All prices include 8% VAT.

*I enclose a cheque for £....., made out to Sinclair Radionics Ltd, and crossed.

*Please debit my *Barclaycard/ Access account. Account number

--	--	--	--	--	--	--	--	--	--	--	--

*Delete as required.

Signed _____

Name _____

Address _____

Please print. FREEPOST – no stamp needed. PE/1/75

sinclair
 Sinclair Radionics Ltd,
 FREEPOST St. Ives,
 Huntingdon, Cambs. PE17 4BR.


Reg. No: 699483 England. VAT Reg. No: 213 8170 88.

PE MINISONIC

By D. SHAW

PART THREE

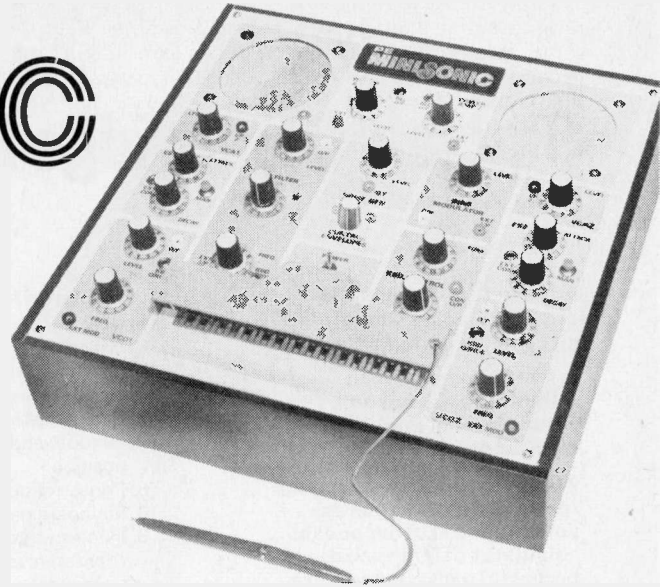- Keyboard Controller
- Noise Generator
- Ring Modulator
- Power Amplifiers



THIS month the remainder of the electronic circuitry in the synthesiser is described which includes KEYBOARD CONTROLLER, RING MODULATOR, NOISE GENERATOR and POWER AMPLIFIERS.

THE KEYBOARD CONTROLLER

The KEYBOARD CONTROLLER as illustrated in Fig. 3.1 is a relatively simple means of providing a range of voltages which, when applied to the input of a VCO, cause it to oscillate over a range of pitches normally associated with a chromatic scale or, alternatively, over a range of pitches quite outside what might be termed normal musical acceptance.

IC1 and IC2 are inverting operational amplifiers whose outputs are linked by a chain of resistors the junctions between which are connected to the keyboard contacts. R5 and VR1 form a divider between the positive rail and ground such that the swing of the potentiometer covers a range of about 4.7 volts.

The wiper of VR1 is linked to both i.c.'s so that the output of these devices will track, in unison, the setting of VR1. R1 and VR2 form a second divider between the negative rail and ground with the wiper linked to IC1 only. Thus VR2 is able to provide an offset to IC1 which is variable over 4.5 volts.

The purpose of the voltage difference between the swings of the two potentiometers, is so that, under normal conditions, the key contact voltages can never go positive and thus drive the vco's into saturation.

SPAN AND TUNE CONTROLS

The KEYBOARD CONTROLLER can be matched to a wide range of keyboard sizes and vco control voltages.

If, for example, a two octave keyboard is to be used and the required control voltage for the vco's is 600mV per octave, then VR2 (the "Span" control) will require to be offset by 1.2V with respect to the inverted value of VR1's setting. Once this has been used and the required control voltage for the vco's are able to reproduce a chromatic octave by making

a series of consecutive key contacts, then VR1 may be adjusted over a wide range without affecting the "tune" of the vco's.

In simple terms the "position" of the two-octave keyboard may be varied over the audio frequency range and the "white" notes may be made to play in any required key signature. This latter feature will commend itself to those "play-it-by-ear" musicians who may sometimes find difficulty in translating a well known melody in the key of C into its correct signature.

For more serious applications, however, the ability to swing the keyboard "position" enables the Minisonic to play in tune with a number of conventional acoustic instruments which may, themselves, not be precisely "spot-on" as far as tuning is concerned.

KEYBOARD RESISTOR CHAIN

No setting-up is required for the KEYBOARD CONTROLLER other than to check that the outputs of both IC1 and IC2 respond correctly to the settings of VR1 and VR2. Fig. 3.1 gives a table of resistor values which may be used for the divider system on keyboards of various sizes.

It will be noted that the overall value of resistance in each case is approximately the same in order that the loading on the i.c.'s will vary by a minimum amount regardless of the size of keyboard employed.

THE "HOLD" OR ANALOGUE MEMORY

Although covered by the general heading of KEYBOARD CONTROLLER the HOLD circuit is a quite separate entity which fulfils an important function in the scheme of the synthesiser.

Last month it was indicated that the ENVELOPE SHAPER could give a decay characteristic lasting up to 16 seconds. In other words, from the instant the key contact is broken, the audio signal will continue—at a diminishing level—for the prescribed period. It is obvious therefore that, for the best effect to be achieved, the vco frequency must remain constant for the period over which the decay is taking place.

With the key contact broken so too is the vco programming voltage disconnected unless there is some means by which the vco can continue to be programmed regardless of key contact condition. The HOLD circuit provides the means whereby the vco can continue to oscillate at the frequency prescribed by the last programmed voltage either until the ENVELOPE SHAPER completes its cycle or until another voltage is programmed in.

HOLD CIRCUIT

The circuit of the HOLD facility is shown in Fig. 3.2a. IC3 is an operational amplifier in which the output signal is divided by means of VR4, R8 and R9 to provide balanced levels of positive and negative feedback.

When the balancing is carefully done the circuit is theoretically capable of presenting an infinite impedance to incoming signals. In practice, however, it is more usual to calculate the input impedance on the basis of the parallel value of the feedback resistors times the open loop gain of the amplifier. Thus the input impedance is of the order of 2,500 megohms.

The hold capacitor (C2) is, ideally, a low leakage type. A charge applied to C2 is reflected at the output of IC3 with any drift at the output due to a combination of capacitor leakage and minor thermal effects within the i.c.

COMPONENTS . . .

KEYBOARD CONTROLLER AND HOLD

Resistors

- R1 10k Ω
- R2-R4 47k Ω (3 off)
- R5 9.1k Ω
- R6, R7 47k Ω (2 off)
- R8, R9 20k Ω (2 off)
- R10 47k Ω
- R11 et seq See text

Potentiometers

- VR1, VR2 10k Ω linear carbon (2 off)
- VR3 10k Ω sub-miniature horizontal skeleton preset
- VR4 10k Ω 15-turn preset

Capacitors

- C1 1,000pF
- C2 1 μ F 63V polycarbonate

Integrated Circuits

- IC1-IC3 Type 741 8-pin d.i.l. (3 off)

Miscellaneous

- SK1 2mm socket

KEYBOARD CONTROLLER

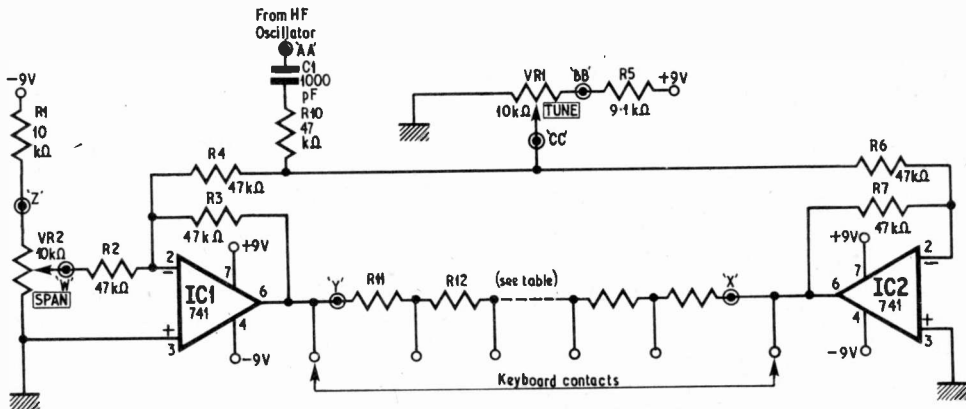


Fig. 3.1. Circuit of the KEYBOARD CONTROLLER (excluding the HOLD circuit). The table (below) shows values of resistors (R11 et seq) and numbers required for various length keyboards. This applies to both printed circuit and conventional keyboards

KBD DIVIDER RESISTORS

Size	Resistor	Number off
1 octave	150 Ω	13
2 octave	82 Ω	25
3 octave	51 or 56 Ω	37
4 octave	39 or 43 Ω	49
5 octave	33 or 36 Ω	61

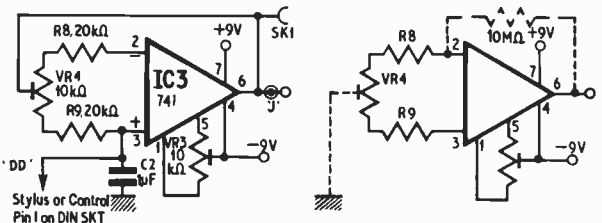


Fig. 3.2(a). The circuit of the HOLD section of the KEYBOARD CONTROLLER. (b) It is important that this circuit should be adopted when nulling the HOLD offset. Temporary links are shown dashed. The feedback resistor should be 10M Ω or more

It is possible to balance the circuit such that the output drift is better than 1mV/sec but to do so requires considerable patience and care, particularly when nulling the offset. The circuit for this latter procedure is shown in Fig. 3.2b. The component assembly should be as shown on the circuit board layout but the wiper of VR4, instead of being linked direct to the output of IC3, is temporarily connected to the 0V rail.

A second temporary feature is the inclusion of a high value feedback resistor (ideally 10M Ω or more) as shown hatched in Fig. 3.2b.

Adjust VR4 so that its wiper is close to the centre of travel and, with power on, adjust VR3 until the output of IC3 is *precisely* zero volts. The temporary links and feedback resistor may now be removed and the circuit completed as shown in Fig. 3.2a.

Minimising the drift in the HOLD circuit is best done by ear, i.e. using the Minisonic VCO's rather than an oscilloscope as part of the test equipment. Details of this procedure will be included as part of the final setting up.

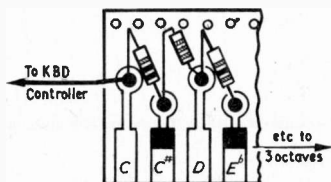


Fig. 3.3(a). Wiring of the edge connector strip as used on the prototype. Resistors are wired in from the conductor side of the board. Excess wire on the other side of the p.c.b. should be trimmed off and filed flush so that the board may be glued to the front panel

THE KEYBOARD

The Minisonic offers the possibility of being operated with a number of keyboard options, the cheapest being the edge-connector type. Other options will be discussed next month.

A printed circuit keyboard was adopted in order that the instrument could be both compact and fully self-contained. In the prototype a three-octave keyboard was made up using a standard edge-connector strip as shown in Fig. 3.3a but satisfactory operation could only be achieved after much practice due to the narrow conductors involved. Mounting of the divider resistors should be generally as shown in the diagram.

COMPONENTS . . .

HARDWARE

Control Knobs, 14mm—19 with skirt, 1 without skirt (ReAn Products—see *Market Place*)
On/off d.p.d.t. toggle
Battery connectors, PP9 2-off positive and negative
0.1in matrix Veroboard 45 x 34 holes
Keyboard 37-way edge connector strip (or see text)
Materials for stylus (see text)
5-pin 180° DIN socket

STYLUS

In the first prototype the stylus employed two contacts and was illustrated on the front cover of the November issue. The double contact, however, greatly added to the difficulties of playing the instrument and thus modifications were carried out so that a single contact stylus could be employed.

Perhaps the simplest stylus involves the adaptation of a ball-point pen (see Fig. 3.3b). If this method is chosen it is important that all traces of ink are removed from the ball end using an organic solvent before any attempt is made to solder in the wire lead.

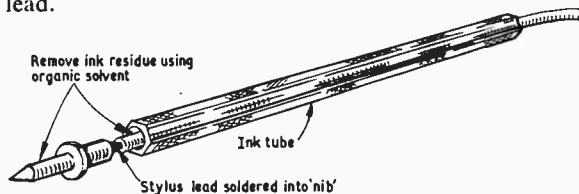


Fig. 3.3(b). A suggested construction method for the stylus using an old ball-point pen

Note that organic solvents should be treated with caution since most of them give off a vapour which can be harmful if inhaled continuously. The assembly when completed should be potted within the lower half of the pen by means of Araldite or Silicon Rubber Compound.

Those constructors having access to a lathe could make up a stylus from a piece of ¼in brass rod. If this method is used it is important that the extreme tip of the stylus should be rounded off and well polished to ensure a good contact.

ULTRASONIC TRIGGER SYSTEM

(The circuitry in this section is the subject of a Patent Application)

The changeover from a double-contact to a single-contact stylus presented a difficult problem simply because the signals required to set the HOLD circuit and to trigger the ENVELOPE SHAPERS are essentially incompatible. Direct coupling between the inputs of these two circuits was therefore not possible since, once the HOLD capacitor was charged, the d.c. level would remain on the stylus lead and the ENVELOPE SHAPER in the "on" condition, until the charge on the HOLD capacitor had leaked away.

This would occur quite rapidly in the circumstances thereby giving rise to an undesired portamento effect. Similarly it was not possible to decouple the ENVELOPE SHAPER from the stylus lead since so doing would restrict the "attack" phase to one rate only—and that very fast. The solution proved to be the application of a principle which is believed to be unique in electronic musical instruments.

HF OSCILLATOR

A HIGH FREQUENCY OSCILLATOR is coupled directly into the KBD CONTROLLER in such a way as to distribute the signal evenly across the divider. The stylus lead which now goes direct to the HOLD capacitor is also connected through a decoupling capacitor to an a.c. detector circuit which, through an integral switch, is used to trigger the ENVELOPE SHAPER.

Four components only go to make up the HF OSCILLATOR which is shown in Fig. 3.4.

VR1 controls the frequency of operation by prescribing the proportion of positive feedback and thereby varying the peak to peak value of the output signal. With the component values given the frequency range is from 2kHz at 18V peak-to-peak, to 250kHz at 80mV peak-to-peak. Output waveforms are also shown in Fig. 3.4.

OSCILLATOR FREQUENCY

The optimum setting of the HF OSCILLATOR is 40kHz at 6V p-p as measured at point "AA." The attenuating effect of C1, R10 and VR1 in the KBD CONTROLLER will combine to reduce the signal to 500mV p-p measured on the keyboard contacts.

It should be noted however that the setting of VR1 in the controller will affect the level of the h.f. signal—the lower the setting of VR1 the lower will be the level of the signal on the contacts. This is not really a problem since the detector sensitivity is around 50mV and also, for most applications, it will be found that VR1 will require to be at a relatively high setting.

HF DETECTOR

The circuit of the DETECTOR is shown in Fig. 3.5. IC2 is a high gain follower decoupled from the stylus lead by means of C2. C1 provides additional decoupling for the stylus lead thereby ensuring that hum signals which may be included in the lead do not cause triggering of the envelope shapers. C4 and C5 provide frequency compensation for IC2 which is a 709 operational amplifier for give the advantage of the higher gain bandwidth offered by this device.

The output of IC2 provides drive to TR1 the collector of which is coupled through R6 to the bases of TR1 and TR2 on both ENVELOPE SHAPERS. (Note that this latter coupling is via the DIN socket and JK1 on both ENVELOPE SHAPERS.) C6 blocks any d.c. appearing at the output of IC2 while R5 sets a current limit.

Under quiescent conditions the output of IC2 is nominally zero volts and TR1 is off. An a.c. signal of sufficient level on the stylus lead will cause IC2 to follow and each positive excursion of IC2 output will switch TR1 on causing the collector to go to about -8.5 volts. The ENVELOPE SHAPERS thus start to attack and C7 receives a negative charge.

H.F. OSCILLATOR AND DETECTOR

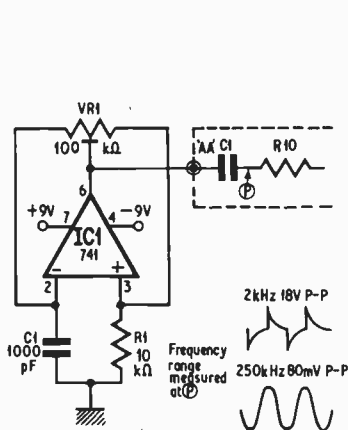


Fig. 3.4. Circuit of the HF OSCILLATOR. Components in the dotted box are on KBD CONTROLLER circuit and are mounted on main board. Typical waveforms at different settings of the VR1 are also shown

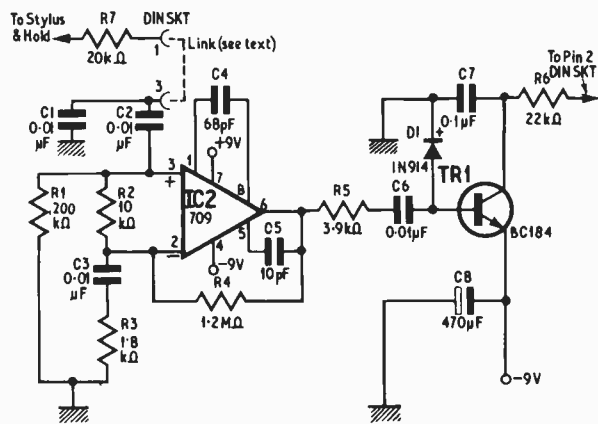


Fig. 3.5. Circuit of the HF DETECTOR. Resistor R7 is for isolation and was 20kΩ in the prototype. The DIN socket is for external keyboard attachment and wiring options will be described next month. C1 is mounted on the DIN socket

COMPONENTS . . .

HF OSCILLATOR

Resistors

R1	10kΩ	
VR1	100kΩ	subminiature horizontal skeleton preset

Capacitor

C1	1000pF
----	--------

Integrated Circuit

IC1	Type 741 8-pin d.i.l.
-----	-----------------------

HF DETECTOR

Resistors

R1	200kΩ	R5	3.9kΩ
R2	10kΩ	R6	22kΩ
R3	1.8kΩ	R7	20kΩ (see text)
R4	1.2MΩ		

Capacitors

C1-C3	0.01μF (3 off)	C6	0.01μF
C4	68pF	C7	0.1μF
C5	10pF	C8	470μF 16V elect.

Semiconductors

D1	1N914
IC2	Type 709 8-pin d.i.l.

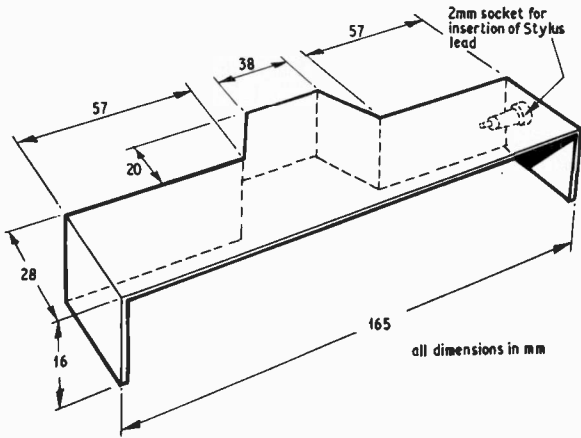


Fig. 3.6. Dimensions of the keyboard cover which was made from 3mm card

The time constant of C7 is such that it will lose only a small proportion of its charge during the negative half cycle of the h.f. signal. The result is that an effectively constant negative signal is presented to the ENVELOPE SHAPERS during the period that the stylus and/or key contacts are made.

ISOLATION RESISTOR

In addition to the components making up the DETECTOR Fig. 3.5 also shows a resistor, R7, in series with the stylus lead and HOLD circuit. The purpose of this resistor is to provide a degree of isolation for C2 in the HOLD circuit so that its relatively large capacity will not over-attenuate the signal on the stylus.

R7 (20k Ω in the prototype) also provides a delay in the d.c. charging rate of C2 with the result that there is a 20ms portamento effect. This effect is not really too noticeable unless consecutive KBD voltages are programmed from opposite ends of the KBD but it could perhaps be a source of irritation for the constructor wishing to use the Minisonic for serious musical purposes.

In these circumstances R7 could be replaced by an inductance which would provide the degree of a.c. isolation required whilst presenting only a nominal resistance to d.c. A suitable choke could be made up from a small ferrite ring toroidally wound with about 20 to 30 turns of 34 s.w.g. enamelled copper wire.

Some experimenting will possibly be required to get just the right value and it would be best to start with the greater number of turns and reduce these as necessary to get the best balance between a.c. isolation and d.c. resistance.

PORTAMENTO

As a modification to the prototype circuits some constructors may wish to incorporate a variable portamento control. In view of the lack of space on the front panel the best way to do this is to mount a miniature edgewise volume control—such as is used on some transistor radios—inside the upper edge of the printed circuit keyboard cover.

The cover is shown in Fig. 3.6. The wire from the stylus socket on the side of the KBD cover would then be routed to one end of the potentiometer while the slider would go via R7, or inductor as mentioned above, to pin 1 on the DIN socket.

RING MODULATOR

The Minisonic RING MODULATOR is an improved version of the circuit which originally appeared in the *P.E. Sound Synthesiser* (August 1973). The essential features of the circuit have been retained however and the circuit is shown in Fig. 3.7.

The RING MODULATOR produces a unique output waveform which comprises, at the same instant, the sum and difference between any two applied input frequencies. This function is carried out in a purpose-built integrated circuit, the SG3402N. With one of the input frequencies fixed, variation in the other will ring the changes in the output frequencies as shown in Table 3.1.

Referring to Fig. 3.7, R1 and R2 form an input attenuator on the so-called carrier input (pin 7) such that, when driven from a vco, the input signal level at C1 will be about 40mV.

Similarly R3 and R4 attenuate the modulator or control input so that, when driven by a vco, the input at C2 is about 200mV. This procedure results in an output signal of about 1.5 volts at pin 4 and the same signal in antiphase at pin 11. The anti-phase signals are amplified differentially by IC2 to give a peak output signal of three volts which is then attenuated by R9 and R10 to a level compatible with the remainder of the Minisonic circuits.

SETTING UP THE RING MODULATOR

Setting up the RING MODULATOR is very simple. With the circuit completed link the modulator input to the 0V rail and connect the output to a suitable power amplifier. Apply a signal of about 1kHz to the carrier input (normally connected direct to vco1) and adjust VR1 until the output signal reduces to the lowest possible level. This should, with a correctly wired circuit, be 50dB or more below the peak signal level. At this point the RING MODULATOR is correctly balanced with minimum carrier breakthrough.

NOISE GENERATOR

The NOISE GENERATOR is built round the highly successful Z1J noise diode manufactured by Semitron Ltd., and is shown in Fig. 3.8. Output from the Z1J

Table 3.1: OUTPUTS FROM THE RING MODULATOR

	Frequency						
Carrier	700	600	500	400	300	200	100
Modulator	400	400	400	400	400	400	400
Sum	1100	1000	900	800	700	600	500
Difference	300	200	100	0	100	200	300

RING MODULATOR

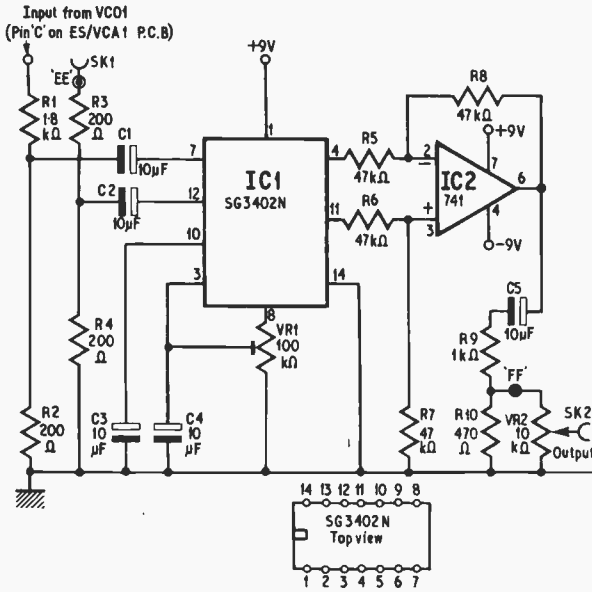


Fig. 3.7. Complete circuit of the RING MODULATOR

COMPONENTS . . .

RING MODULATOR

Resistors

- R1 1.8k Ω
- R2-R4 200 Ω (3 off)
- R5-R8 47k Ω (4 off)
- R9 1k Ω
- R10 470 Ω

Potentiometers

- VR1 100k Ω subminiature horizontal skeleton preset
- VR2 10k Ω log carbon

Capacitors

- C1-C4 10 μ F 6.3V tantalum (4 off)
- C5 10 μ F 16V tantalum

Integrated Circuits

- IC1 SG3402N
- IC2 Type 741 8-pin d.i.l.

Miscellaneous

- SK1, SK2 2mm sockets (2 off)

is amplified by the high gain follower IC1 and led, through decoupling capacitor C5, to the volume control VR1.

The NOISE GENERATOR is the only circuit in the Minisonic which does not operate completely successfully down to a battery voltage of ± 7.5 volts.

In the prototype the noise generator ceased to work when the battery voltage had reduced to ± 7.8 V. This situation may be corrected to a certain extent by shorting out R2 and R3 and/or by reducing the value of R1 to, say, 82k Ω . No setting up is required for this circuit.

NOISE GENERATOR

COMPONENTS . . .

NOISE GENERATOR

Resistors

- | | |
|----------------------------|------------------|
| R1 91k Ω | R5 200k Ω |
| R2, R3 22 Ω (2 off) | R6 56k Ω |
| R4 470k Ω | R7 1.2k Ω |

Potentiometer

- VR1 10k Ω linear carbon

Capacitors

- C1 0.01 μ F
- C2 100 μ F 25V elect.
- C3 0.01 μ F
- C4 100 μ F 25V elect.
- C5 0.01 μ F

Integrated Circuit and Diode

- IC1 Type 741 8-pin d.i.l.
- D1 Z1J noise diode (Semitron)

Miscellaneous

- SK1 2mm Socket

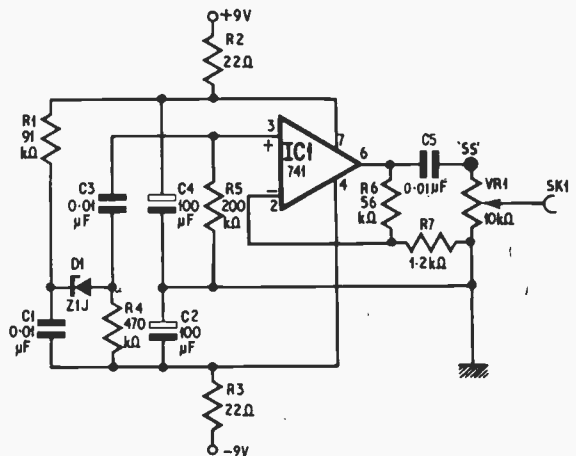


Fig. 3.8. Circuit of the NOISE GENERATOR

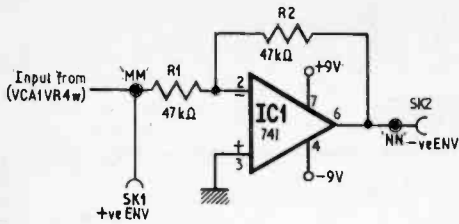


Fig. 3.9. Circuit of the **CONTROL ENVELOPE INVERTER**. This is fed with the output of ES/VCA1 via VR4 (see last month)

- COMPONENTS . . .**
 R1, R2 47kΩ (2 off)
 IC1 Type 741 8-pin d.i.l.
 SK1, SK2 2mm sockets (2 off)

POWER AMPLIFIER

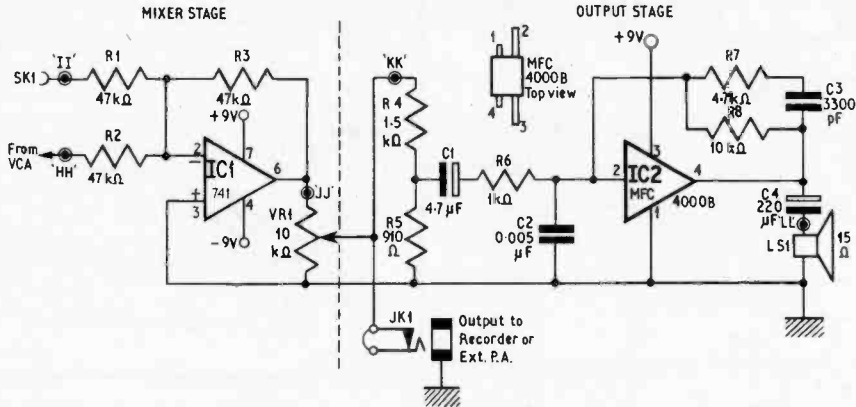


Fig. 3.10. Complete circuit diagram of one of the **POWER AMPLIFIERS** with integral two-input mixers. Note that the mixer stages are mounted on the main circuit board

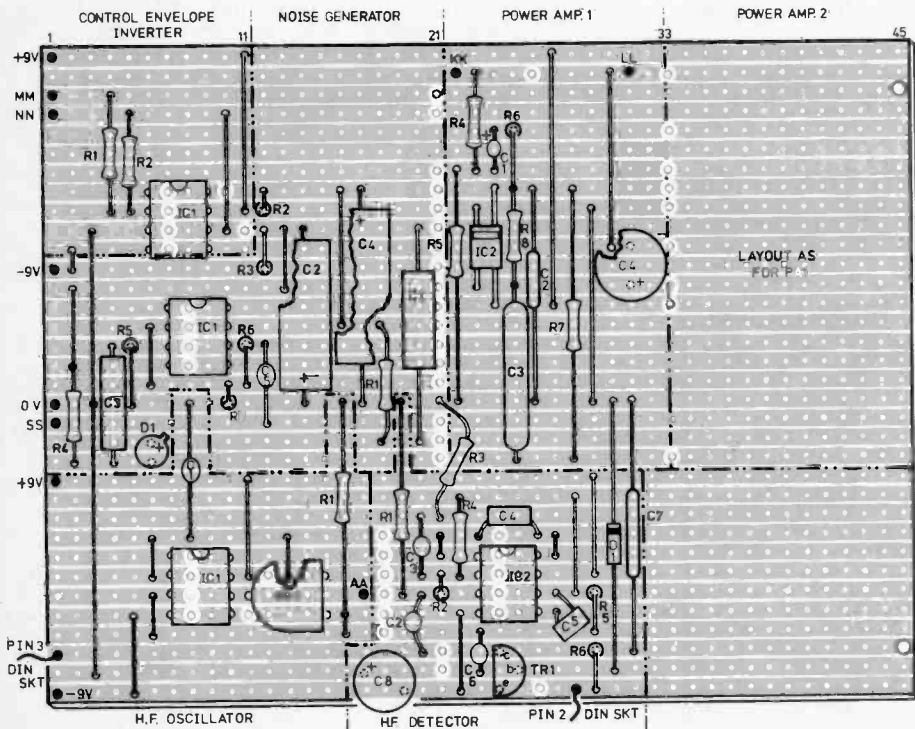


Fig. 3.11. The Veroboard panel which carries the **NOISE GENERATOR, HF OSCILLATOR AND DETECTOR, CONTROL ENVELOPE INVERTER, AND POWER AMPLIFIERS**

COMPONENTS . . .

POWER AMPLIFIERS AND MIXERS (2 off)

Resistors

- R1-R3 47kΩ (3 off)
 R4 1.5kΩ
 R5 910Ω
 R6 1kΩ
 R7 4.7kΩ
 R8 10kΩ

Potentiometer

- VR1 10kΩ log carbon

Capacitors

- C1 4.7μF 35V tantalum
 C2 0.005μF ceramic
 C3 3300pF
 C4 220μF 40V elect.
 (or 470μF 16V)

Integrated Circuits

- IC1 Type 741 8-pin d.i.l.
 IC2 MFC4000B

Miscellaneous

- LS1 3in 15 speaker
 SK1 2mm socket
 JK1 3.5mm jack socket

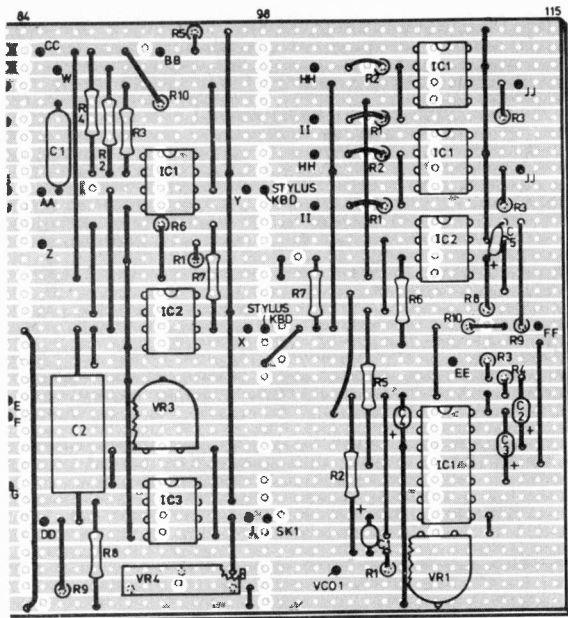


Fig. 3.12. The layout on the main Veroboard panel, the majority of which was shown last month

CONTROL ENVELOPE INVERTER

Shown in Fig. 3.9, the CONTROL ENVELOPE INVERTER represents a modification to the prototype instrument and has been included, principally, so that the VCF may be programmed automatically from ENVELOPE SHAPER 1. The inverter itself is a simple unity-gain inverting amplifier which requires no setting up procedure.

POWER AMPLIFIERS

The complete circuit of the power amplifiers, which includes a two-input inverting mixer, is shown in Fig. 3.10. As with all the virtual earth circuits in the Minisonic the mixer has the minimum number of inputs and almost any number of additional inputs may be applied by following the basic details given in Part 1 of the series.

The slider of the volume control (VR1) at the mixer output is wired directly to a jack socket from which may be taken a signal suitable for driving an external power amplifier, tape recorder, external mixer, etc.

CIRCUIT BOARD LAYOUT

The CONTROL ENVELOPE INVERTER, HF OSCILLATOR and DETECTOR, NOISE GENERATOR, and POWER AMPLIFIER stages are carried on a separate circuit board which is illustrated in Fig. 3.11.


The KEYBOARD CONTROLLER, RING MODULATOR and POWER AMPLIFIER/MIXER stages are all included on the main circuit board part of which was illustrated last month. The remainder of the board is shown in Fig. 3.12.

Next month: Final wiring-up and adjustments. Keyboard options, as well as circuit additions for more ambitious constructors will be discussed.

Stop Press: The author has developed a printed circuit board to carry all the Minisonic electronics. More details next month.

NEXT MONTH... MARINE SPEEDOMETER

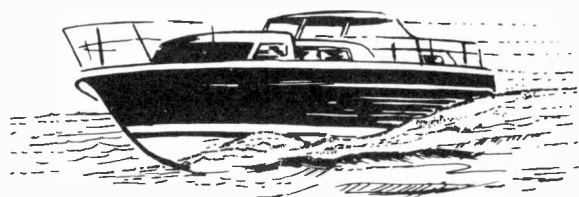Solid-state electronics provide an easy-to-make solution to the measurement of boat speed — suited to both motor and sail environments and giving reasonable accuracy at sensible cost.



AC/DC MILLIVOLTMETER

A fully protected voltmeter which will read a.c. voltages down to 5mV r.m.s. but will withstand overloads of up to 250V. Operates at all audio frequencies.

PROBABILITY ANOMALY DETECTOR

Investigate your powers of extra-sensory perception with this specially designed unit. A meter registers your influence on the random noise in a Zener diode — the greater your power the higher the reading.

PRACTICAL
ELECTRONICS

FEBRUARY ISSUE ON SALE JANUARY 10, 1975

INGENUITY UNLIMITED



A selection of readers' suggested circuits. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought. Any idea published will be awarded payment according to its merits. Why not submit YOUR IDEA?

A SERIAL CONNECTION MULTIVIBRATOR

A SIMPLE square wave generator with equally fast rise and fall times is always useful. The conventional astable multivibrator has the disadvantage that although one edge of the output waveform is fast, the other edge is comparatively slow. This is due to the fact that the collector of the off transistor has to recover to the potential of the supply in a time determined by the capacitor associated with the collector and the value of the collector load. Improving the output waveform by the use of extra diodes or perhaps an extra transistor are solutions but a novel approach is a serial connection.

Consider the circuit shown and let TR1 be fully conducting and TR2 cut off with C3 fully discharged. It will be evident that C3 has a charging path via R4 and

negative going transition at the collector of TR2 is communicated via the bootstrap connection of C2 to the base of TR1. This results in TR1 being cut off and C3 now acts as an effective collector potential for TR2. Therefore C3 discharges through R3 until the emitter potential of TR1 is again negative with respect to the base. Thus TR1 conducts and thereby completes the cycle and the whole sequence will start again.

If the time constants R1-C1 and R2-C2 are sufficiently large, the frequency of oscillation is predominantly determined by C3/R3 and C3/R4. Current consumption from a 9V battery is only 0.7mA since the circuit only consumes current during one half period of the cycle.

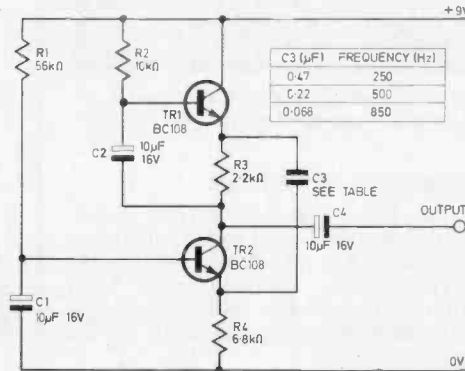


Fig. 1

so this capacitor charges exponentially allowing the emitter of TR2 to approach ground.

When the charging current has decreased sufficiently so that the base potential of TR2 is again more positive than its emitter, then this transistor promptly conducts. This

Unlike its more conventional counterpart the serial connection is always self starting. The output amplitude with the circuit shown is 5.5V peak-to-peak.

M. Harding,
Cheadle, Cheshire.

SOUND/LIGHT MODULATOR

A VERY simple sound/light modulator is shown in Fig. 1 which may be of use to experimenters. Input signals can be taken from the output (loudspeaker) of an audio amplifier since in most pop or disco environments the small amount of distortion introduced using this method will hardly be noticed.

Sensitivity is controlled by VR1 whilst the transformer provides isolation and the drive for triac

MAC 11-6. This is possible as the triac drive pulses need not be shaped.

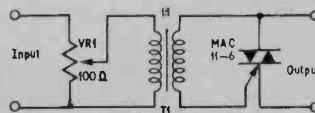


Fig. 1

To provide frequency sensitivity and/or other channels, capacity can be inserted in the triac gate circuit. Using 100V 1µF capacitors, bass response can be selected by inserting the capacitor in parallel with the secondary of the transformer. For the treble the capacitor is in series with the gate and for the mid ranges two capacitors are used, one in each of the foregoing positions.




In this way three circuits can be built up to control three separate lamps if desired.

P. Vleck
Cheltenham.

look! electronics really mastered

... practical
... visual
... exciting!

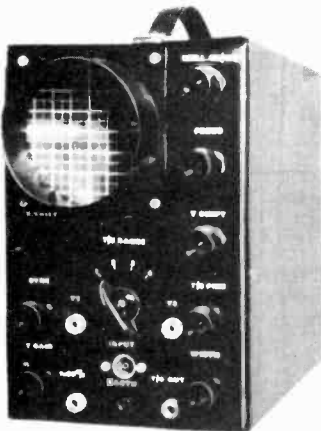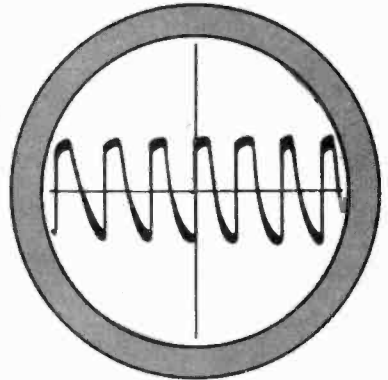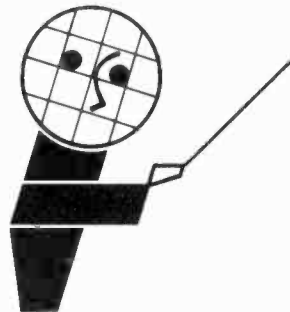no previous knowledge
no unnecessary theory
no "maths"



RAPY


BUILD, SEE AND LEARN

step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.

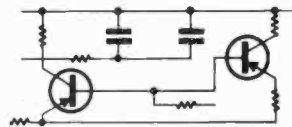2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including:

valve experiments, transistor experiments amplifiers, oscillators, signal tracer, photo electric circuit, computer circuit, basic radio receiver, electronic switch, simple transmitter, a.c. experiments, d.c. experiments, simple counter, time delay circuit, servicing procedures.

This new style course will enable anyone to really understand electronics by a modern, practical and visual method—no maths, and a minimum of theory—no previous knowledge required. It will also enable anyone to understand how to test, service and maintain all types of electronic equipment, radio and TV receivers, etc.

FREE POST NOW for BROCHURE

or write if you prefer not to cut page

To BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL, DEPT. EL124, P.O. BOX 156, JERSEY. Please send your free brochure, without obligation, to:
we do not employ representatives

NAME

BLOCK CAPS

ADDRESS

PLEASE EL15

special free gift also to all our students



WILMSLOW AUDIO

THE Firm for speakers!

SPEAKERS

Baker Group 25 3, 8 or 15 ohm	£7-75
Baker Group 35 3, 8 or 15 ohm	£8-50
Baker Group 50/12 8 or 15 ohm	£12-50
Baker Deluxe 12in d/cone	£10-75
Baker Major 12in d/cone	£8-50
Baker Regent	£7-75
Baker Superb	£14-50
Baker Auditorium 12	£12-50
Celestion MH1000, 8 or 15 ohm	£10-95
Celestion PST8 for Unilux	£2-55
Celestion G12M 8 or 15 ohm	£12-00
Celestion G12H 8 or 15 ohm	£15-00
Celestion G15C 8 or 15 ohm	£24-00
Celestion G18C 8 or 15 ohm	£33-00
Coral 6 1/2 in d/cone roll surr. 8 ohm	£2-50
Coral 8 in d/cone roll surr. 8 ohm	£3-25
EMI 13in x 8in 3, 8 or 15 ohm	£2-25
EMI 13in x 8in 150 d/c 3, 8 or 15 ohm	£2-50
EMI 13in x 8in 450 U/w. 3, 8 or 15 ohm	£3-75
EMI 13in x 8in type 350 8 or 15 ohm	£8-25
EMI 13in x 8in 20W base	£6-60
EMI 6 1/2 in 93850 4 or 8 ohm	£3-00
EMI 5in 98132CP 8 ohm	£2-50
EMI 8 x 5 d/cone, roll surr. 10W	£2-50
EMI 2 1/2 in tweeter 97492AT	£0-85
Eagle DT33 30W tweeter	£5-45
Eagle HT15 horn tweeter	£3-80
Eagle CT5 cone tweeter	£1-75
Eagle CT10 tweeter 8 or 16 ohm	£2-55
Eagle MHT10 horn tweeter	£3-80
Eagle crossover CN23, CN28, CN216	£1-50
Eagle FR4	£5-30
Eagle FR65	£8-35
Eagle FR8	£10-65
Elac 9 x 5 59RM109 15 ohm, 59RM114 8 ohm	£2-80
Elac 6 1/2 in 6RM171 d/c roll surr.	£3-50
Elac 6 1/2 in 6RM220 d/cone	£2-85
Elac 4in tweeter TW4	£1-21
Elac 10in d/cone 10RM239 8 ohm	£2-85
Elac 8in RCS175 3 ohm	£2-50
Fane Pop 15W 12in	£4-80
Fane Pop 25/2 25W 12in	£6-95
Fane Pop 40W 10in	£8-50
Fane Pop 50W 12in	£11-00
Fane Pop 55 60W 12in	£12-50
Fane Pop 60W 15in	£13-00
Fane Pop 100W 16in	£22-50
Fane Crescendo 12A 100W 12in	£29-00
Fane Crescendo 12B bass	£29-00
Fane Crescendo 15in 100W	£36-80
Fane Crescendo 18in 150W	£49-95
Fane 8011 8in d/c roll surr.	£7-00
Fane 8077 8in d/c roll surr.	£3-85
Fane 8087 8in d/c	£2-75
Fane 701 twin ribbon horn	£35-80
Fane 910 horn	£12-75
Fane 920 horn	£33-00
Goodmans 9P 8 or 15 ohm	£5-00

Goodmans 10P 8 or 15 ohm	£5-30
Goodmans 12P 8 or 15 ohm	£12-95
Goodmans 12P-D 8 or 15 ohm	£18-75
Goodmans 12P-G 8 or 15 ohm	£15-75
Goodmans Audiomax 12AX 100W	£39-65
Goodmans Audiomax 15AX	£42-00
Goodmans 15P 8 or 15 ohm	£21-00
Goodmans 18P 8 or 15 ohm	£36-00
Goodmans Midax 750	£18-00
Goodmans Axiom 100 tweeter	£7-25
Goodmans Audiom 100 12in	£12-00
Goodmans Axiom 401 12in	£17-25
Goodmans Twinaxiom 8	£8-25
Goodmans Twinaxiom 10	£9-00
Kef T27	£5-25
Kef T15	£6-00
Kef B110	£7-25
Kef B200	£8-25
Kef B139	£14-25
Kef DN8	£2-00
Kef DN12	£4-95
Kef DN13	£3-30
STC4001G super tweeter	£6-15
Richard Allan CG87 8in d/c r/surr	£6-35
2 1/2 in 64 ohm, 70mm 80 ohm, 70mm 8 ohm	£0-65
2 1/2 in 75 ohm	£0-50
7in x 4in 3 or 8 ohm	£1-40
8in x 5in 3 or 8 ohm	£1-50
10in x 6in 3, 8 or 15 ohm	£2-30

SPEAKER KITS

Baker Major Module	each £10-75
Fane Mode One	each £9-90
Goodmans DIN 20	each £9-75
Helme XLK25	pair £22-00
Helme XLK30	pair £14-95
Helme XLK50	pair £39-95
Kefkit 2	each £24-75
Kefkit 3	each £38-75
Richard Allan Twinkit	each £8-95
Richard Allan Triple 8	each £13-75
Richard Allan Triple	each £19-95
Richard Allan Super Triple	each £23-75
Wharfedale Linton 2 kit	pair £19-25
Wharfedale Glendale 3 kit	pair £34-50
Wharfedale Dovedale 3 kit	pair £52-50

PA/DISCO AMPLIFIERS

Baker Major 100 watt	£49-75
Linear 30/40	£30-00
Linear 40/60	£35-00
Linear 80/100	£59-75
Linear 100 watt slave	£44-00

(carr. and ins. £1)

Eagle PA range in stock—ask for catalogue

FREE with speaker orders over £7

"Hi-Fi Loudspeaker Enclosures" book.

All units guaranteed new and perfect Prompt despatch Carriage and packing: speakers 38p each, speaker kits 75p each (£1-50 pair), tweeters and crossovers 20p.

Send stamp for free booklet "Choosing a Speaker" ALL PRICES QUOTED INCLUDE VAT

WILMSLOW AUDIO (Dept. PE)

Loudspeakers: Swan Works, Bank Square, Wilmslow, Cheshire, SK9 1HF. Discount Radio, PA, Hi-Fi: 10 Swan Street, Wilmslow.



Cassettes

The best buy!

Agfa Low Noise Cassettes AT LESS THAN HALF PRICE!	C80	1	5	10
	C90	37p	£1-80	£2-50
	C120	56p	£2-48	£4-95
		63p	£3-10	£6-20
AGFA HIGH DYNAMIC SUPER	C80 + 6	50p	£2-40	£4-70
	C90 + 6	68p	£3-35	£6-60
	C120	99p	£4-90	£9-80
AGFA STEREO-CHROM CHROMIUM DIOXIDE	C80	1	5	10
	C90	85p	£4-20	£9-30
		£1-08	£5-35	£10-60

SAME DAY DESPATCH. P. & P. 15p per order

WILMSLOW AUDIO (DEPT. PE)

10 SWAN STREET, WILMSLOW, CHESHIRE, SK9 1HF

Cut-price prerecorded cassettes—send stamp for list

COLOUR TELEVISION WITH PARTICULAR REFERENCE TO THE PAL SYSTEM

by G. N. Patchett Price £5.10

ELEMENTS OF TRANSISTOR PULSE CIRCUITS by T. D. Towers. Price £3.70.

UNDERSTANDING IC OPERATIONAL AMPLIFIERS by R. Melen. Price £2.20.

BEGINNER'S GUIDE TO ELECTRONICS by T. L. Squires. Price £2.05.

ELECTRONIC EQUIPMENT RELIABILITY by J. C. Cluley. Price £2.65.

ELECTRONIC HOBBYIST'S IC PROJECTS HANDBOOK by B. Brown. Price £1.55.

DIGITAL ELECTRONIC CIRCUITS AND SYSTEMS by N. M. Morris. Price £2.40.

RADIO CONTROL HANDBOOK by H. G. McEntee. Price £2.10.

DIGITAL LOGIC BASIC THEORY AND PRACTICE by J. H. Smith. Price £1.65.

UNDERSTANDING AND USING THE VOM AND EVM by J. Cunningham. Price £1.65.

GE TRANSISTOR MANUAL Price £1.30.

★ TOTAL PRICE INCLUDES POSTAGE ★

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST of British and American Technical Books

19-21 PRAED STREET LONDON W2 1NP

Phone 01-723 4185 Closed Saturday 1 p.m.

CALCULATORS

SAVE MONEY! BUY DIRECT FROM THE SPECIALISTS

VATMAN

£14.91 + VAT

45p P & P. and please add 8% VAT on all total prices.



Model 1	Our Price	Functions
Decimo Vatman	14-91	P, [A], R, G, 8D, E, F, K2, H, I, J, C, L5, B, N.
Decimo Vatman	16-91	P, [A], R, G, 8D, E, F, K2, H, I, J, C, L5, BM, N.
Decimo Memory	23-88	P, M, [A], R, G, 8D, E, F, K2, H, I, J, C, L5, BM, N, [W].
Decimo Slide rule	25-88	P, M, [A], R, G, 8D, E, F, K2, [H], [X], [J], I, C, L5, BM, N.
Decimo 9202	39-83	S, M, [A], R, G, 8D, E, F, K2, H, I, J, C, L5, BM, N.
Anita 811	39-95	P, M, [A], R, 8D, E, F, K4, H, I, C, B, N.
Bohn Omnitrax*	44-95	T, M, [A], R, G, 8D, E, F2, K4, H, I, C, B, M, M.
Bohn Omnitrax SQ1*	50-95	T, M, [A], R, G, 8D, E, F7, G, [H], [X], [J], I, C, M, V, U.

JUST OUT: Bohn Metrix* 69-22 T, W, [A], R, G, 8D, E, F, K2, H, I, M, C, V also 12 conversions in/cm, ft, metres, yds/metres, miles/km, ozs/ccs, qts/litres, gal/litres.

F/CP, ozs/grams, lbs/kg, area measurement, cubic measurement

Bowmar MX75* 39-97 T, M, [A], R, 8D, E, F, K4, H, I, J, C, V

Bowmar MX100* 85-99 T, M, 8D, E, F, K4, C, V, J. true scientific 20 functions for algebra, geometry, log, calculus, integrals, etc.

Ricomac 121MD 44-16 H, I, J, (item count), Print-Out


Ricomac 1000P 81-97 2 colour print-out, A, 10D, F/S, K4, M, sub total, acc + X buffer

Ricomac 1220 121-19 Dtte, plus 12D, [A], 2M, rounding, [W] silent.

Code A - percentage, B - battery (mains adaptor extra), BM - battery (mains adaptor incl), C - carrying case, D - digits, E - +, x, =, F - floating decimal point, F/S - floating point and select, F2 - floating point and 2 places, F7 - floating point and 7 places, G - green display, H - x², I = x, J = x², K² - constant X +, K⁴ - constant x +, -

L5 = 50 hr. battery life, L10 = 100 hr. battery life, M - memory, N = negative entry, P = pocket, R - prorating, S = desk model, T = hand and desk, U = display blanking, V = rechargeable, W = exchange, X - Vx, [J] = extra separate keys, * = positive feed.

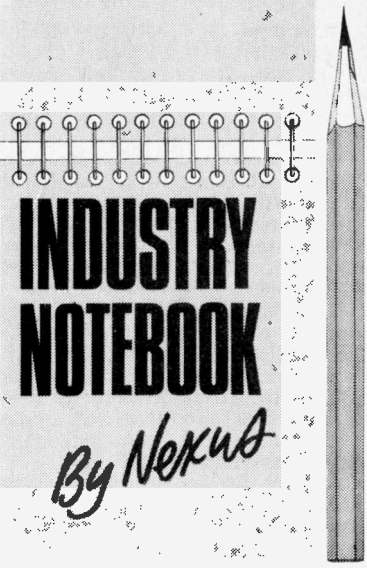BARCLAY ELECTRONICS STANLEY HOUSE, 1115 FINCHLEY ROAD LONDON, NW11



INDUSTRY NOTEBOOK

By Nexua

EASIER SERVICING

Colour television is easily the most complicated box of tricks in the home. Healthy competition has kept prices low, despite inflation. And that same competition, in effect the struggle for market share, is still spurring manufacturers to give the buying public more and more value for money.

It follows that the more complex a machine is the more it costs to service. And TV sets, by their very nature, have a fine in-built monitor, the screen itself, which instantly shows up defects or deterioration in performance. The broadcast authorities are even kind enough to transmit test patterns designed to highlight imperfections.

Every manufacturer has nightmares over servicing. Apart from losing goodwill, every time a set goes wrong during guarantee another chunk of profit goes down the drain. So in their own interests, manufacturers do genuinely try to make sets that are reliable and there has been a strong move over the past few years to build sets in modules to allow servicing by module replacement.

Now Grundig in Germany has gone one step further by building in a rapid diagnosis system in every set. Grundig had switched to a nearly fully modular system some three years ago in which 75 per cent of the circuitry is split among a dozen plug-in modules, each with a defined function. If any one module failed it was fairly obvious to the service engineer and he just plugged in a replacement. Now the diagnostic adaptor enables an instant check of the non-modular circuits.

Key check-points of the circuits are all brought to a single 13-way

socket into which the service engineer plugs his monitor. The monitor has 13 led's and if any one of these fails to light up there is an indication of a specific fault. It costs very little extra on each set to provide the facility and the saving in engineer's time can be enormous. And, of course, with soaring labour costs, time saved is very important, not to mention customer satisfaction. The plug-in diagnostic aid costs the dealer under £10. Quite a bargain. And the customer benefits, too. Other set makers are expected to follow the trend.

EXPORTS

If you've ever thought that export promotion is not given enough priority in Britain, reflect for a moment on the current trading quarter which ends on December 31, 1974. The British Overseas Trade Board is giving support to 1,360 British companies at 76 overseas trade fairs in 27 countries. In addition there are 54 outward trade missions representing 730 companies and involving 45 countries. These group activities are in addition to hundreds of "private" promotions by individual companies.

One of next year's big trade drives is to be centred on Western Canada and seminars are already being held in Britain which will brief exporters on trade opportunities in advance of parties of exporters visiting the two big growth areas of Alberta and British Columbia. In the direct field of electronics, one of our biggest 1974 efforts was at Munich's Electronica Exhibition at which 57 British companies took part in a joint venture.

PACEMAKER BOOM

It was only a few years ago that we were all marvelling at the way microelectronics had made possible the heart pacemaker which has done so much to extend human life. With improved techniques in implant surgery and technical advances in pacemakers this single branch of medical electronics has now blossomed into an industry in its own right with world sales this year expected to top £25 million and reach over £200 million by 1980.

The technical problem which has been engaging pacemaker researchers is how long they can be kept working without recourse to further surgery to replace the battery. One approach was to use nuclear power to give infinite life.

Another was a rechargeable unit that could be recharged by induction through an external unit. But both these solutions are losing favour, mainly expense in the nuclear field and susceptibility to outside interference with rechargeable units, apart from the occasional inconvenience to the user.

It seems now that long-life batteries will do the job quite well. Reasons are that in the early days pacemakers were more powerful than they needed to be, the new active devices using technologies such as CMOS take far less current, and battery technology itself has improved.

With current drain reduced to less than 20 micro-amps a three-year life can be obtained from mercury-oxide-zinc units and possible developments in sodium-bromine and lithium cells could give a battery life of seven years or more. This figure ties in well with the life-expectancy of pacemaker users who statistically have an average age at implant of 67 years and can expect another 5-7 years of life.

HUMBLE HARDWARE

Racks, panels, instrument cases hardly ever hit the headlines. Yet they are still big business in electronics clocking-up European sales of over £30 million a year and double that if you add in PCB edge connectors and other interconnection devices. So don't despise the metalwork in electronics. It might not make so much profit as glamour products but the commercial risk is much lower. Provided, of course, that you can get your materials. One prominent manufacturer, lamenting recently on production hold-ups, commented that "screws have seemingly ceased to exist, and costs have gone up alarmingly". And steel, plastics and paint have also been hard to get.

TAKE OFF

Great sighs of relief that the European Multi Role Combat Aircraft has received the go-ahead for its final development phase. This is the project that is exercising the best brains in electronics. It's costing the earth, of course, but how else do you keep ahead in technology?

At a more mundane level it's good to see Plessey has started delivering ILS systems for Chinese airfields in a contract worth £850,000. And British aerospace companies as a whole are doing well with exports worth more than £2 million every working day with our best customer still being the United States followed by France and Germany.

MARKET PLACE

Items mentioned in this feature are usually available from electronic equipment and component retailers advertising in this magazine. However, where a full address is given, enquiries and orders should then be made direct to the firm concerned. All quoted prices are those at the time of going to press.

MOUNTING PILLARS

A useful new product for the constructor has just been released by **West Hyde Developments Ltd.** Called Ilex pillars, they are designed to insulate circuit boards from cases or chassis and at the same time support them either vertically or horizontally one on top of another.

Made from moulded nylon, they have a rigid girder-shaped supporting section with a spring loop fastener at the top and tension feet together with a push-in clip at the base.

Suitable holes are drilled in the chassis and boards and the pillars are simply pressed into place and any subsequent boards mounted on the top of the pillars, see photograph. The sizes of the pillars vary from $\frac{1}{4}$ in to $1\frac{1}{4}$ in and cost approximately 3p each for a minimum order of 10 (for $\frac{1}{4}$ in size).

Full particulars and sizes together with price list can be obtained from **West Hyde Developments Ltd.**, Ryefield Crescent, Northwood Hills, Middlesex, HA6 1NN.

ON TAPE

Two new cassette tapes have been announced recently by **EMI Ltd** and **3M United Kingdom Ltd.**

The new X1000 ferric oxide cassette from EMI is claimed to give as good reproduction as chrome dioxide cassettes. A C60 cassette is expected to retail at 99p (excluding VAT).

The main technical improvements claimed for the X1000 are: an increase of 3-4dB in the 8-15kHz frequency range, compared to low noise tapes. A wider dynamic range due to the tape's increased magnetic remanence, resulting in less tape hiss. Improved high frequency response ensures a low level of intermodulation distortion.

When used with good quality audio equipment the tape is claimed to give excellent performance down to 25Hz and up to 15kHz.

Undoubtedly the new Scotch Classic tapes from 3M's, with a C90 cassette at £2.16, is aimed at the "serious" end of the market.

This new double coated or dual layer tape indicates the trend

towards the use of a product compatible with existing tape and equipment rather than the current trend of using metallic dioxide tape. It is claimed that the new tape combines the high frequency abilities of chromium dioxide with the bias characteristics and low frequency response of the low-noise ferric oxide tape.

Both the above tapes are available from all good audio shops and large stores.

LITERATURE

A comprehensive 724-page data book covering Motorola's range of linear i.c.s is available from **Semiconps Ltd.** The book contains not only full data but, in many cases, valuable application information on over 300 devices.

The range includes op. amps, drivers and line receivers, d/a and a/d converters, comparators, voltage regulators, timing and power control units, consumer TV, audio and radio circuits, r.f. amplifiers and automotive circuits.

For easy reference the data sheets are arranged in alpha numeric sequence without regard to product category.

The book costs £1.26 and is obtainable from **Semiconps Ltd.**, Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex, HA0 1SD.

NEWS BRIEFS

Readers who are building the "P.E. CCTV Camera" may be interested to know that **Crofton Electronics** are now able to offer a complete kit of parts for this project. They can also supply lenses,

coils, tubes and printed circuit boards separately.

For full details readers should write to **Crofton Electronics** at 124 Colne Road, Twickenham, TW2 6QS.

We understand that **Re An Products Ltd** are able to supply all the control knobs (19 with skirts and one without) for the P.E. Mini-sonic synthesiser. These knobs have a translucent numbered skirt and are available with coloured caps.

It has been suggested that by using a colour code system for the knobs the front panel layout of the Mini-sonic can be identified in colour groups (i.e. envelope shapers, voltage controlled oscillators and amplifiers, etc.), which can make the instrument easier to use.

A price list for the knobs, type R62, is obtainable from **Re An Products Ltd**, Burnham Road, Dartford, Kent, DA1 5BN.

What is believed to be a unique service for the private constructor, has been announced by **SCS Components**.

Now, branded guaranteed components are being offered at very competitive "one-off" prices, in fact the same as applying to industrial users. Included in this offer is a very large range of integrated circuits and transistors.

A complete price list (free) is obtainable from **SCS Components**, Northfield Industrial Estate, Beresford Avenue, Wembley, Middlesex.

To help beat rising costs **Amtron U.K. Ltd.** are now able to supply direct to the customer many of their more expensive electronic kits.

A full list of the construction kits available is obtainable from **Amtron U.K. Ltd.**, 4 Castle Street, Hastings, Sussex TN34 3DY.



New p.c.b. mounting pillars from West Hyde Developments


3M's Classic cassette tape

The X1000 cassette tape from EMI

HEADPHONES, CALCULATORS, DIGITAL CLOCKS, QUADRA-PHONIC RECORDS, TECHNICAL BOOKS, TESTGEAR, SQ. LOGIC DECODER, FREQUENCY COUNTERS, RECORD/TAPE ACCESSORIES, TURNTABLES, INSTRUMENT CASES—NOW 6 SIZES, METAL BOXES—LARGE STOCKS

SOUND SPHERES

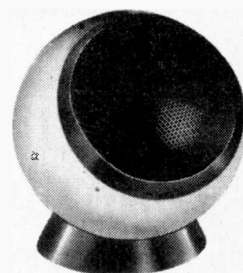Unique listening experience, these sound as though they were many times larger—try them and hear them—only 4½in diameter! £24.75 per pair. Available in black, white and orange



NEW PROJECTS

We will be supplying kits for the PE Joanna Electric Piano, the PW Electronic Organ, and PW Ascot Cassette Recorder.

All the above, and many other items are in our new 1975 catalogue available FREE NOW! A large S.A.E. (7p in stamps) would be appreciated.

Trade and export customers are invited to apply in writing for distribution terms of business.

SUPERB QUADRAPHONIC SYSTEM

P.E. Rondo

Complete kit with 4 speakers, u/c decoder, FM tuner and turntable. Value approx. £209 + £16.72 VAT.

£195 + £15.60 VAT

Fully built Rondo, complete as above. Value £266 + £21 VAT. Delivery on complete systems may be 6/8 weeks from date of order.

£245 + £19.60 VAT

Set of 4 speakers fully to specification with pre-built cabinets—very professional finish. Very comprehensive kits.

£62 + £4.96 VAT

We supply all Rondo parts and modules.

Quadraphonic headphones—a new experience!

£18.50 + £1.48 VAT


Stereo Headphones—padded with volume controls.

£4.80 + 38p VAT

ALL ITEMS ARE POST FREE.

We are appointed distributors for Uher quality tape recorders and Videosonic Dolby processors.

Have you had our book list?

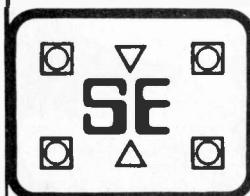

Studio Electronics
P.O. BOX 18 HARLOW
CM 18 6SH ESSEX

Telephone: Harlow (std 0279) 25457

NAME _____

ADDRESS _____

PE 1/75



BOOK REVIEWS

ROBOTICS

By John F. Young
Published by Butterworths
300 pages, 8½ in × 5½ in. Price £6.00

THERE is nothing mythical about this book. It is concerned with hard facts of engineering. Robots have a very real existence, and in various forms perform many useful tasks in industry and elsewhere. Tasks which range from the mundane and repetitive to those of a highly specialised and skilled nature.

All this is clearly brought out in *Robotics*. The author, who has had a long experience in this field, describes notable developments in robot design which have been or are currently being undertaken in various advanced countries. Some of the devices mentioned will be familiar, like the Lunakhod, the Robotug, and the mobile robot used by the army to explode bombs left in cars. But there are many other significant developments in robotics which this book now brings to the attention of a wider audience.

Underlying all this activity are unmistakable signs of the eventual appearance of the General Purpose Robot for domestic use. The idea of an automated housewife is not just wishful thinking; it is the target of many designers in a number of countries. Indeed, according to the author, the Japanese are already well advanced with plans for a G/P Robot suitable for mass production with the inevitable economic advantages this will bring.

This book does not cover the "brain" of the robot, but concentrates upon the engineering of the "body". Hydraulic, pneumatic, and electrical techniques for actuation of the "limbs" are discussed. Electronics comes into its own with the imitation of the human senses, and all the commonplace sensing devices are considered. Character and voice recognition pose greater problems; some indication of recent work by the author and his associates at Aston University in devising circuitry to solve some of the difficult problems in this frontier area of electronics is given.

Extensive lists of references accompany each chapter. Valuable as sources for the specialist researcher, these items provide additional evidence of the determined efforts that have already been made in this field of Robotics, and indicate how the robot has already become usefully employed in so many and varied everyday activities.

F.E.B.

ELECTRONICS — AN ELEMENTARY INTRODUCTION FOR BEGINNERS (SI UNITS)

By L. W. Owens
Published by Publication Mailing Services
120 pages. Price £1.45

IN LINE with the current tendency, this book is perfectly bound between linen covers to keep costs to a reasonable level. It is nonetheless a valuable introduction to electronics for any beginner, particularly those meeting this type of subject for the first time.

Diagrams are used extensively with the addition of formulae where necessary and these latter are spelt out in SI units to conform to international practice.

The reader is led by the hand through complexities of fundamental particles, atoms, energy in its various forms, static and current electricity and the basic raw materials of electronics from theory to simple example.

Finally, the theory is exemplified by discussions of the valve and semiconductor and their use in radio and television and other areas.

D.R.D.

NEWS BRIEFS

G. D. SHAW LECTURES AT AUDIO FAIR

THE tremendous interest in synthesisers was reflected by the massive attendance at the two lectures at this year's Audio Fair by G. D. Shaw, the author of P.E. Minisonic articles currently appearing in *Practical Electronics*.

Entitled "Sound Synthesis for the Amateur", the lectures described synthesisers ranging from the simplest, in the form of the Minisonic, to the synthesiser of the future in the form of a digitally organised instrument having full polyphony (the ability to play more than one note simultaneously), and a memory facility.

The part of the lecture dealing with the Minisonic was illustrated with some impressive tape recordings made, using the Minisonic, by Malcolm Pointon. Most people were amazed at the range of effects that could be produced by such a simple instrument.

In the realm of digital synthesisers, Mr Shaw hopes to be the first to produce a design suitable for the amateur, a formidable task when one appreciates the complexity of such a system. The instrument is to be designed in such a way as to allow expansion from a basic unit simply by plugging in printed circuit boards as and when they are needed (or can be afforded).

This was not the only area where P.E. scored a "sound" success. On our stand the "P.E. Joanna" piano, exhibited for the first time, created enormous interest amongst the public. This unique instrument, ideal for the modern home, features piano, harpsichord and honky-tonk facilities with true touch sensitive operation.

The P.E. Joanna is a future project and full details will be published in the next few months.

LINK(S) UP

AN almost unbelievable 5 watts of transmitted power was used, in conjunction with a satellite, to beam a transmission over a distance of more than 50,000 miles recently in America.

In an experiment involving a simple antenna made from a golfer's umbrella, an engineer from the General Electric Company of USA used a low power "walkie-talkie" radio to prove that even with such rudimentary equipment the only important requirement for long-range communication is the presence of a satellite overhead.

To be fair, the antenna was specially made up from the golfer's umbrella but nonetheless a morse message was beamed from the NASA headquarters to a geostationary satellite *ATS-3* and then to *GE (USA)'s* Radio-Optical Observatory near Schenectady, New York.

The demonstration shows all too clearly just how easy it would be for almost world-wide coverage to be provided for some form of search-and-rescue system based on a simple man-carried emergency transmitter. It is also envisaged that the system could carry phone signals, not just morse.

PRICE CUT

IN this period of constantly rising prices it is heartening to know that at least some items are becoming cheaper. Motorola have recently announced their second price reduction in the CMOS device area.

This second reduction, worth an average of 25 per cent, applies to standard MC14000 and the in-house MC14500 devices. When applied to MSI the new pricing will give an individual gate function cost at around just a few pence and when this is coupled to the saving in power supply requirements and package count the total effect is a distinct improvement when using CMOS.

Readout —

A SELECTION FROM OUR POSTBAG

Gas Detectors

Sir—As the comment appearing on page 794, September 1974 issue, may raise doubts as to the life of the TGS sensors, we trust the following brief outline of the operating principles of the sensor will indicate why we claim that their life is comparable to that of other semiconductor devices, rather than the catalytic type of gas detector.

Molecules of flammable or de-oxidizing gases are absorbed on the surface of the Taguchi sensors, resulting in electron transfer between absorbate and the solid sensor surface. In the case of hydrocarbon gases the reaction is related to the ionization potential of the gas absorbed on the surface of the pellet. The lower the ionization potential, the more readily is the gas detected. Hence isobutane (ionization potential 10.79eV) is detected more easily than methane (ionization potential 13.04eV).

The change in conductivity of the sensor is not caused by heat resulting from the combustion of a gas at its surface. The lack of combustion and relatively low operating temperature, 250°C, eliminates deterioration of the inert 82 per cent Palladium + 18 per cent Iridium filaments encapsulated in the bead.

The Taguchi gas detectors have been in continuous use in Japan for six years, and the only noticeable change in performance has been an increase in sensitivity with time, up to a maximum of 30 per cent when a levelling-off occurs.

Damage can occur to the sensor if it is exposed for long periods to high concentrations of gases containing sulphur or lead, and such gases will in any case inhibit the performance of most gas detectors.

There are of course, many applications where the catalytic type sensor is superior to the Taguchi especially in the areas of selectivity and long term repeatability, but where a pre-set low level long-life sensor is required, the Taguchi have found good acceptance. More than two million have been put in service to date.

From the design point of view, it is essential that a current limiting resistor be included in series with the sensor, or else the sensor may

be destroyed by excessive current at switch-on. For example, if a low voltage 6V to 24V circuit is used then the minimum value of load resistor is 2 kΩ. A variable resistor alone should not be used in this position as it is possible for the unit to be switched on with the variable resistor set to the low end of its range.

D. Lahiff,
Manager, Figaro Engineering,
Shannon, Ireland.


Gas Sense (or)

Sir—In the circuit of the "Boat/Caravan Gas Detector" (October 1974) the fact that the l.e.d. is alight proves that the heater side of the gas detector is connected and conducting. A dangerous situation could arise if the alarm circuitry, or more likely the wire connecting it to the detector, were to become open-circuited. This problem could arise from corrosion of the B7G socket or the gas detector pins (and boat bilges are known to be very damp places).

The simple modification shown in the enclosed diagrams will enable the detector to be fully tested each time it is turned on. The resistor R16 corresponds to a concentration of approximately 0.2 per cent of Butane or Propane in air, well below the inflammability range of 1.8 to 9 per cent.

R. A. Wood,
Wolverhampton.

C. R. Francis,
Sheffield.

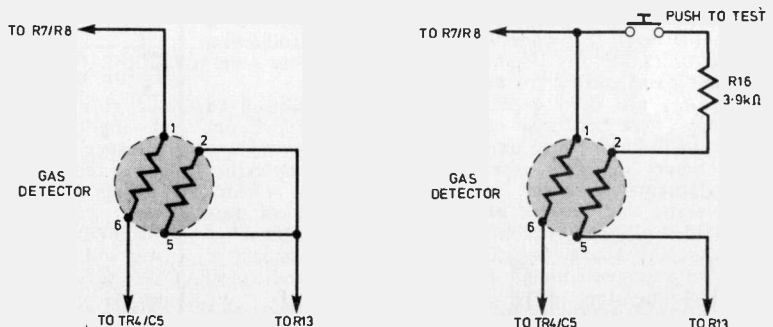

Growing Upwards!

Sir—With reference to Mr. Crilly's letter (*Readout*, September), I feel that I in turn must draw attention to two points.

Firstly, the magnetic properties of a material are determined by the spin configurations of the constituent atoms or ions. The vast majority of elements and compounds are said to be paramagnetic—this means that unbalanced spins among the electrons leave a nett magnetic moment on the atom. In the presence of a magnetic field, at low temperatures so that thermal vibrations do not upset things, a degree of alignment can occur.

In the case of iron and certain other materials, ferromagnetism is observed. This means that over small regions of the crystal the magnetic moments (which are due to the same mechanism as above) are aligned by an internal crystal field. These regions are called "domains", and may themselves be aligned by an external field. Thus, ferromagnetism is a bulk property of iron, and it is inaccurate to speak of iron-containing molecules as being more "magnetic" than magnesium containing ones without considering the nett spins for the molecules concerned.

Secondly, Mr. Crilly states that strong magnetic forces radiate from the centre of the earth. This is not strictly true; the earth's field is not a monopole but approximates to a dipole. As a result of this there are regions of the earth's surface at the geomagnetic equator, where the field is parallel to the surface—in fact it is vertical only at the geomagnetic poles.

The suggested mechanism of tropisms would, therefore, not work in general, producing horizontal roots at the geomagnetic equator, and roots inclined to the vertical in most regions. I should also point out that plants transplanted from the Northern hemisphere to the Southern would develop into roots growing upwards at an angle to maintain their accustomed orientation with respect to the field.

BI-PRE-PAK

SUPPLIERS OF SEMI-CONDUCTORS TO THE WORLD



Telephone Corner

COMPLETE TELEPHONES

NORMAL HOUSEHOLD TYPE

EX G.P.O. Only **99p** P. & P. 45p each

TELEPHONE DIALS

Standard Post Office type. Guaranteed in working order.

Only **25p** POST & PACKING 16p

Tested and Guaranteed Paks



B79	4	IN4007 Sil. Rec. diodes, 1,000 PIV 1 amp. plastic	50p
B81	10	Reed Switches, 1" long 3/8" dia. Highspeed P.O. type	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	50p
H38	30	Short lead Transistors, NPN Silicon Planar types	50p
H39	6	Integrated circuits 4 gates BMC 962, 2 flip flops BMC 945	50p
H41	2	BD131/BD132 Complementary Plastic Transistors	50p
H65	4	40361 Type NPN Sil. transistors TO-5 can comp. to H66	50p
H66	4	40362. Type PNP Sil. transistors TO-5 can comp. to H65	50p



Unmarked Untested Paks

B1	50	Germanium Transistors PNP, AF and RF	50p
B66	150	Germanium Diodes Min. glass type	50p
B83	200	Transistors, manufacturers' rejects, AF, RF, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. IN914 and IN916 types	50p
H20	20	BY126/7 Type Silicon Rectifiers 1 amp. plastic. Mixed volts	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	50p
H67	10	3B19N Channel FET's plastic case type.	50p

Make a rev counter for your car

The "TACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

£1 each

Electronic Transistor Ignition

Complete Kit **£6.00** P. & P. 11p

Now in kit form, we offer this "up-to-the-minute" electronic ignition system. Simple to make, full instructions supplied with these outstanding features. Transistor and conventional switchability, burglar proof lock-up and automatic alarm, negative and positive compatibility.

Extension Telephones


Ideal for children's toys, 70p each. P. & P. 25p.

New X Hatch

Our new vastly improved Mark Two Cross Hatch Generator is now available.

Will align the colour guns on a colour TV receiver. Featuring plug-in ICs and a more sensitive sync, pick-up circuit. The case is virtually unbreakable—ideal for the engineer's toolbox—and only measures 3in x 5 1/2in x 3in.

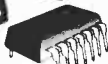Ready built unit only **£9.95** Complete Kit **£7.95** (includes P. & P. but no batteries)



LM380 AUDIO IC

We have just received a large consignment of LM380 ICs. These are specially selected to a higher grade and are marked with the number SL60745.

This fantastic little 3w audio IC only requires two capacitors and two potentiometers to make an amplifier with volume and tone control. The quality is good and has to be heard to be believed.

Our special **£1** each complete with data and projects book price

Over 1,000,000

Transistors in stock

We hold a very large range of fully marked, tested and guaranteed transistors, power transistors, diodes and rectifiers at very keen prices. Please send for free catalogue.

Our very popular 4p Transistors

TYPE "A" PNP Silicon Alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.
TYPE "G" NPN Silicon, similar ZTX300 range.

8 RELAYS FOR £1 P. & P. 27p.
Various types

UHF TV Tuner Units

Brand new by a famous manufacturer
Data supplied **£2.50**

Plastic Power Transistors



NOW IN TWO RANGES

These are 40W and 90W Silicon Plastic Power Transistors of the very latest design, available in NPN or PNP at the most shatteringly low prices of all time. We have been selling these successfully in quantity to all parts of the world and we are proud to offer them under our Tested and Guaranteed terms.

Range 1	VCE Min.	15	HFE Min.	15
		1-12		13-25
40 watt		20p		18p
90 watt		24p		22p
				20p
Range 2	VCE Min.	40	HFE Min.	40
		1-12		13-25
40 watt		30p		26-50
90 watt		35p		26p
				30p

Please state NPN or PNP on order.

HIGH-SPEED MAGNETIC COUNTERS

EX G.P.O. 4 digit (non-reset) 4 x 1 x 1" 30p.

INTEGRATED CIRCUITS. We stock a large range of ICs at very competitive prices. These are all listed in our FREE Catalogue, see coupon below.

METRICATION CHARTS now available. This fantastically detailed conversion calculator carries thousands of classified references between metric and British (and U.S.A.) measurements of length, area, volume, liquid measure, weights, etc. Pocket Size, 12p, Wall Chart, 18p.

LOW COST DUAL IN LINE I.C. SOCKETS

14 pin type at 15p each } Now new low
16 pin type at 17p each } profile type.

BOOKS

We have a large selection of Reference and Technical Books in stock, details are in our latest catalogue, send for it TODAY using the coupon below.

N.B.—Books are void of V.A.T.

Our famous P1 Pak is still leading in value

Full of Short Lead Semiconductors and Electronic Components, approx. 170. We guarantee at least 30 really high quality factory marked Transistors PNP and NPN, and a host of Diodes and Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P.1. only **50p**

Please send me the FREE Bi-Pre-Pak Catalogue.

I enclose large S.A.E. with 5p stamp
Please add V.A.T. at Current Rate

NAME.....

ADDRESS.....

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 15p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE.

BUY THESE GOODS WITH ACCESS

BI-PRE-PAK LTD

Co. Re. No 820919

Dept. A. 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX.


TELEPHONE: SOUTHEND (0702) 46344.

SAXON

Money saving high performance audio equipment
DIRECT FROM OUR OWN FACTORIES

GUARANTEED TESTED HIGH PERFORMANCE MODULES—now better value than ever

- | | | |
|---|--------------------------------|---|
| SA35
35W RMS 25-50V
7 transistors, 7 diodes | £5.45
Carriage free | ★ 25Hz-25kHz
★ 0.2% distortion
★ Noise—80dB
★ 500mV into 20K |
| SA50
50W RMS 25-65V
7 transistors, 7 diodes | £6.90
Carriage free | ★ 4-16 ohms
★ Simple wiring
★ Short and open circuit proof |
| SA100
100W RMS 45-70V
10 transistors, 7 diodes | £12.50
Carriage free | ★ Continuously rated
★ Top-grade components |
- 120 watt module complete with built-in supply—extra heavy duty £22.50 Carr. 60p**

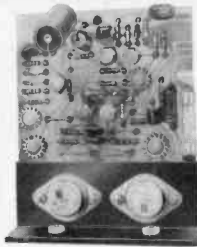

THE SA100 MODULE

POWER SUPPLIES

UNSTABILISED		—READY WIRED	
PU45	Suits 2 SA35 or 1 SA50 (4 ohm)	£5.45	Carriage 30p
PU70	Suits 2 SA50 or 2 SA100 (8 ohm)	£8.45	Carriage 40p
STABILISED			
PS45	Suits 2 SA35 or 2 SA50 (4 ohm)	£4.45	Carriage free
MT45	Transformer for above	£3.50	Carriage 30p
PS70	Suits 2 SA100	£5.45	Carriage free
MT70	Transformer for above	£4.90	Carriage 40p

N.B. PS70 is not suitable for the SA50

Mk II STEREO DISCO MIXER £22.50 Carr. 30p

This well tried unit mixes two decks, handles any ceramic cartridge, and features mic over-ride plus separate full range bass and treble controls on both mic and deck inputs. Ample headphone power is available for P.F.I. May be used for mono and is mains operated. Fitted with sturdy screening case. Controls: Mic vol, bass, treble. Left/Right fade, deck volume, bass, treble, h/phone select, vol, Mains. Size 17 1/2in x 3in x 4in deep.



DISCO MODULE £9.50 Carr. 20p

Thousands sold of this extremely popular mono version. A mic input may be fitted using the VA30 (see below). Low consumption from a 9V battery. Features the same high standards of reproduction as the Stereo version. Controls: H/phone select, vol, Left deck vol, Right deck vol, bass, treble, master vol. Size 12 1/2in x 3in x 2in deep.



3-CHANNEL SOUND-LITE £22.50 Carr. 30p

Only SAXON can supply such incredible value for money. This unit features 3kW power handling, full-wave control, bass, middle, treble AND master controls. Twin loudspeaker jacks for "through" connections. It may be used free standing or will panel mount next to either of the above. Also features unique CUT-BACK circuitry for extra wide range response. Size 12in x 3in x 2 1/2in deep. Professional standards at a price you can afford!




SINGLE CHANNEL VERSION £7.50 Carr. free
Recently reduced in price due to increasing sales, handles 1kW. Full wave operation

Add 8% VAT to all orders

MULTI-PURPOSE MIXERS

M4HL £19.50 Carr. 50p
M6HL £29.50 Carr. 50p
Featuring multiples of our VA30 module, the M4HL and M6HL fulfill the requirements of all clubs, groups, etc. where a high quality mixer is required. Each channel has one high and one low impedance input, plus volume, treble and bass controls. Input impedances may, if required, be easily changed. The M4HL has four channels, and one output, and the M6HL six channels (12 inputs) and a master control and two outputs. Either unit may be used free-standing or panel mounted. These mixers will feed all types of amplifier. Recommended for their versatility and high performance, and excellent value for money.

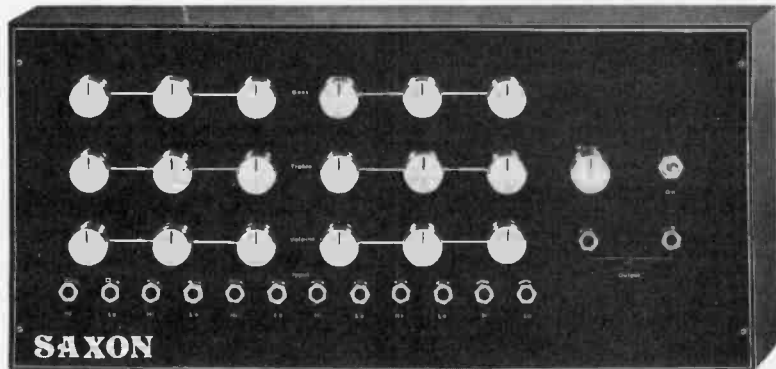


VA30 CHANNEL MODULE £3.50 Carr. free

This is the basic channel module in the above mixers and may also be used for extra inputs on either the mono or stereo mixers. Fitted with volume, bass and treble controls, requires just a jack and supply (9-100V)

SAXON CSE 100 COMPLETE AMPLIFIER

£34.90 Carr. free

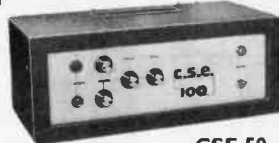100W of speech and music—Two separately controlled inputs. Wide range bass and treble controls. Sturdy and attractive vynide case. Twin outputs. Ideal for groups, discos, etc. Fully tested and guaranteed. 50W version identical in appearance.



CSE 50 £29.50 Carr. free



sockets. Sturdy case, and an attractive fascia make this excellent value for money. Hundreds in use by groups, discos, clubs, etc. 50W version identical in appearance.

Four individually controlled FET input stages plus wide range bass and treble controls. 120W of speech and music output from twin loudspeaker

SAXON 100 COMPLETE AMPLIFIER £53.00 Carr. free

SAXON 50 £37.50 Carr. free

CALLERS AND MAIL ORDER:

SAXON ENTERTAINMENTS LIMITED
327-333 WHITEHORSE ROAD · CROYDON CR0 2HS

(Please quote magazine when ordering)

SHOP HOURS: 9 a.m.-5 p.m. — LUNCH 12.30-1.30 p.m. MAIL ORDER DESK: 10 a.m.-3 p.m.
24-HOUR ANSWER SERVICE TEL. 01-684 6385. TECHNICAL ENQUIRIES 01-684 0098

SEND 10p FOR OUR NEW 26-PAGE MANUAL—full circuits and details.

TERMS OF BUSINESS: C.W.O., C.O.D. or ACCESS (just send in card number). Send 50p. for C.O.D.

Please include S.A.E. with all enquiries. VAT at 8% must be added to all orders including carriage charges.

Parapsychic phenomena

Sir—Sometimes I read your articles about "ESP" in PRACTICAL ELECTRONICS with great interest. I'm working in parapsychic phenomena as a "hobby" and I have some results, which may interest you and your readers.

During the spring and summer I discovered that a magnetic field stimulates germination and even growth of seeds and plants. I made experiments with lobelia, bindweed, pea, lentil and various other plants. In all cases germination increases about 20-30 per cent, germination time was shortened by approximately 30 per cent and plants were 50 per cent higher than in control tests. In addition, it is interesting that the same effect was caused by hand movement, so called "magnetisation", known 200 years ago and used by Mesmer for healing with "animal magnetism".

It is my opinion that these effects are caused by water polarisation in both cases. The same effect is obtainable by using "magnetised" water, activated by passing through a strong magnetic field.

These two phenomena will be discussed and published in two parapsychological magazines.

V. Patrovsky,
Czechoslovakia.

A Boolean Breakfast

Sir—I was recently having breakfast in an hotel and reading a book on Boolean Algebra. I had reached a point where the author stated that $A + (A \cdot B) = A$, when I realised that the waitress was looking over my shoulder. She asked whether I would like egg, or egg and bacon. My natural gluttony lead me to order egg and bacon. I continued reading and learnt that the expression above was read as "A or A and B equals A", and that if either A or B is present it is given a value of 1 and if absent its value, reasonably enough, is 0. The author proved the statement by a truth table.

At this moment the waitress placed in front of me a plate on which there was an egg but no bacon. Of course, I pointed out with maximum natural charm that I had ordered egg and bacon. I was surprised, even dismayed, when she said that what she had served was the same as egg and bacon, the book had just proved it by a truth table—egg, or egg and bacon equals egg.

Later, when the management presented me with the bill for bed and breakfast, I pointed out that the bill for bed, or bed and breakfast, should be the same. In the tariff, breakfast was a separate item, and although I had just eaten it, like the

bacon I could prove by Boolean Algebra that it did not exist. One could not be charged, even in these times of rampant inflation, for something that did not exist whether one ate it or not. The cost of breakfast should therefore be deleted.

The Manager appeared to have an entirely mistaken grasp of Boolean Algebra, and the adviser he called in had not even heard of it. Possibly Boolean Algebra does not form part of a constable's training.


Perhaps some of your more erudite readers can point out where the fallacy lies.

R. Parfitt,
Croydon.

Make an offer

Sir—Before my husband's death in May 1974 he had started to buy various parts for the "Electronic Piano", described in your Magazine some time ago. He already bought two manual contact assemblies, two C-C keyboards, digital master oscillator and other parts. Is it possible for you to help me to dispose of these items?

Mrs. E. Zwimer.



TRAMPUS


ELECTRONICS LTD

58-60 GROVE ROAD,
WINDSOR, BERKS.

MONEY BACK IF NOT SATISFIED.
LARGE STOCKS. LOW PRICES.
ALL BRAND NEW TOP GRADE FULL
SPEC DEVICES. CALLERS WELCOME.

FAST SERVICE.
SEND C.W.O. ADD VAT TO ALL PRICES IN U.K. P&P 15P. EUROPE 25P. OVERSEAS 65P.
CATALOGUE/LIST FREE SEND S.A.B.

Digital Displays



LEDS 14P.

MINI PIN SOURCE OR RED DIFFUSE
LEDS. 209 STYLE. NO CLIP. 14P ea
TIL209 RED LED & CLIP 17P ea
BIG 1" RED LED & CLIP 18P ea
ORANGE & GREEN LEDES:
MINI 25P ea. BIG & CLIP 33P ea
INFRA RED LED 1.2NS777 33P.
PS12 PHOTO IC/amp/switch 11P.

DIGITAL CLOCK

NOS INTEGRATED CIRCUITS.
AYS1224 4 DIGIT CLOCK supplied
with 14pin socket & data 14.25
MMS311/14 6 DIGIT CLOCK with
28 pin socket & data 17.50
3DIGIT DVM AYS3500 17.50
4DIGIT COUNTER/DRIVER 17.50

CASSETTE mechanics £12.50

STEREO CASSETTE MECHANISM.
As used in imported types
costing 1100. Only requires
a case & electronics. Heads
supplied. Send for data 15P.

IC's & Semiconductors

702 OPA	69p	MFC4000 1W AF	35p
703 RF/IF	28p	MFC4060	54p
709 TO99	21p	MFC6050	52p
709 DIL 14	29p	MFC6040	90p
710 DIL 14	36p	MFC8010	11.10
720 Radio	1.39	MFC8040	11
723 Regulator	67p	NE531 35V/us	12
741 TO99	29p	NE536 FET OPA	12
741 DIL8	31p	NE540 Driver	11
741 DIL14	31p	NE546 AM Rxl1.50	
747 Dual 741	89p	NE550 2v ref	79p
748 DIL 8	36p	NE555 TIMER	67p
1505 IC A/D		NE556 Dual	11.30
Converter f7		NE560 PLL	13.15
7805 IASV	11.59	NE561 PLL	13.15
7808 IABV	11.69	NE562 PLL	13.19
7812 IA12V	11.69	NE565 PLL	12.69
7815 IA15V	11.69	NE566 Gen	12.49
76009 1W AF	75p	NE567 code	12.69
76013 6W AF11.39		SN72709 709	29p
8038 Sig Gen	13	SN72741 741	31p
		SN72748 748	36p
		SN76131	11.20
		SN76660 FMIF	11
		SN76611 IF	11.25
		TAD 100 & IF	12
		2N100E	13
		2N4002	11.75
		2N403 Servo	12.50
		2N414 AM Rxl1.09	

7400 etc gates 16p
7413 schmitt 31p
7447 driver 11.09
7470/72 32p
7473/74/76 39p
7475 48p
7490 Counter 63p
7492 Counter 69p
74121 mono 45p
74141 driver 83p
Full range in Cat.

SPECIAL OFFERS

741 29p MFC4000 35p
555 67p 2N414 11.09

BC107, BC108, BC109 9p ea
2N305 39p Three for 11
115W/TO3 18p 90W plastic
2N3819E 16p 2N3053 17p
BFY50/51/52/53 all 18p
IASOVrect 4p ea IN914 4p

Price each:-
AC127/128 16p
AC187/188 19p
AD161/162 35p
BC107/8/9 9p
BC132/4/7 18p
BC147/8/9 10p
BC157/8/9 12p
BC167/8/9 12p
BC177/8/9 18p
BC182/3/4*11p
BC212/3/4*12p
*A or L
BCY70/1/2 15p
BD131/2 39p
BFY50/1/2 18p
BFY53 17p
BSX20 12p
MJE2955 95p
MJE3055 62p
MPU131put 49p
OA91 8p
TIP29A 48p
TIP30A 57p
TIP31A 61p
TIP32A 73p
TIP41A 78p
TIP42A 89p

BZY88 400mW TAG 1/400 55p
2ENERS 9p
BRIDGE RECT 4A/400V 55p
1A 50V 20p
GAS SENSOR 12
GAS "KIT 15

TIP2955 90p
TIP3055 55p
TIS43 UJT 25p
IN4001 4p
IN4004 6p
IN4148/914 4p
2N706/8 10p
2N2636 49p
2N2904/5 20p
2N2926royg 9p
2N3053 17p
2N3055 39p
2N3614 49p
2N3702/3 9p
2N3704/5 10p
2N3706/7 9p
2N3708/9 8p
2N3710/11 9p
2N3563/64 16p
2N3566/67 16p
2N3636 16p
2N3641/2 16p
2N3819E 16p
2N3832E 17p
2N3904/6 14p
2N4249 16p

vero

VERO PINSx36 25p. **NEW LOW PRICES!**
COPPER CLAD VEROBROAD 0.1"
2 1/2x5" 27p. 2 1/2x3 1/2" 24p. 3 1/2x3 1/2" 27p.
3 1/2x5" 29p. 3 1/2x1 7/8" 11.50
DIL IC's BOARDS 6x4 1/2" 11.50
24 way edge connector 60p
36way 90p. PLAIN 3 1/2"x1 7/8" 11
FACE CUTTER 45p. FEC ETCHANT

DAL@open69p

PRINTED CIRCUIT BOARD KIT 11.69
COPPER BOARD 6x4" 40p.
DESOLDER BRAID reel 59p
HEATSINKS
5F/TO5 & 18F/TO18 5p ea.
TV4 12p. TV3/TO3 16p. 4Y1/TO3 29p.

CAPACITORS

22pf to 0.1uf 4p ea. ELECTROLYTIC
25V 2/10/50/100uf 6p. 1000uf 20p
PRESETS VERT: sp. RESISTORS 51 11p


POTS ABoR EGIN

ROTARY: 12p. SWITCH 13p. DUAL 38p.
SLIDERS: SINGLE 26p. DOUBLE 48p.
SWITCHES: SPST 18p. DPDT 25p.
MINI 1/2": SPST 39p. PUSH 39p.
BENCH POWER SUPPLY 3-12V 15.
DIN PLUGS all 13p ea. Sockets 9p
TRANSFORMERS IA 6/12V 11.34
BHA 002 MODULE 15WATT AMP 15
EA1000 4W AF MODULE 12.49
8W/12V FLUORESCENT LIGHT 15

Oil sockets

PROFESSIONAL
GOLD PLATED
& GREY NYLON.
8, 14 or 16 PIN
ONLY 15p each.

Forward with Project 80 into

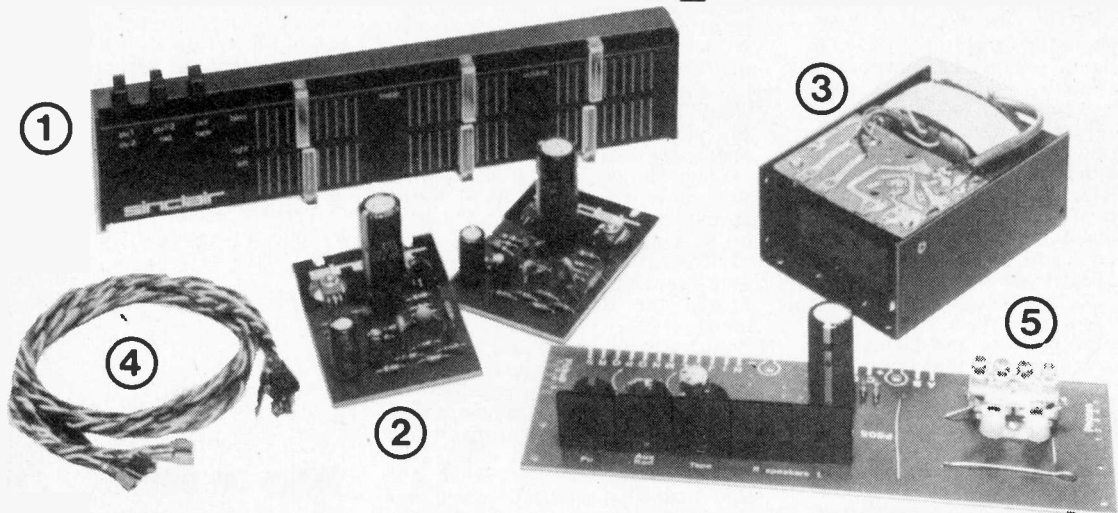

Everything you want in one pack to build the world's most advanced modular hi-fi WITHOUT SOLDERING

- 1 Stereo 80 Control Unit
For mag. and ceramic cartridges, radio and tape.
- 2 Project 80 power amplifiers
Two Z.40s to give 8/8 watts R.M.S. output per channel.
- 3 Power supply unit
One PZ.5.
- 4 Connecting wires
All wires plus nuts, bolts, screws etc.
- 5 Project 805 Masterlink
For input and output connections.
- 6 Mains switch block and instructions manual (not illustrated).

This is Project 80 made even easier to build

You have seen how the marvellously compact Project 80 modules (only 2" high x 3/4" deep) are so adaptable and easy to install. Now, with Project 805, this wonderful system is made easier still to put together. In this, you have not only all the Project 80 modules in one pack for building an 8/8 watt R.M.S. hi-fi amplifier – there is also a loom of colour coded wires cut to length and tagged for clipping on so that you don't even have to solder! Input and output connections go via the 805 Masterlink panel. With the explicit stage-by-stage large 32 page instructions manual included, it becomes easy for anyone, no matter how inexperienced to install an ultra-modern assembly so advanced in appearance and design that it sets brand new concepts in domestic hi-fi – and of course, you can convert to quadraphony just whenever you wish by adding 805SQ. Only Sinclair know-how and manufacturing facilities could hope to bring you such quality and versatility.

TAGGED WIRES CUT TO LENGTH · NO SOLDERING

Project 805

the complete ready-to-build hi-fi
STEREO AMPLIFIER

Project 805 comprises a Stereo 80 Pre-amp/Control Unit with input for both magnetic and ceramic cartridges, radio, tape; separate bass and treble cut/lift, and volume controls 2 x Z.40 power amplifiers, PZ.5 power unit, 805 Masterlink, wire loom, instructions manual, etc. down to nuts, bolts and washers.

For technical specifications, see third page of this advertisement.

£39.95


+£3.20 VAT (R.R.P.)



SINCLAIR RADIONICS LTD
London Rd, St. Ives, Huntingdon PE17 4HJ
Telephone St. Ives (0480) 64646


sinclair

true quadraphonics... *NOW!*

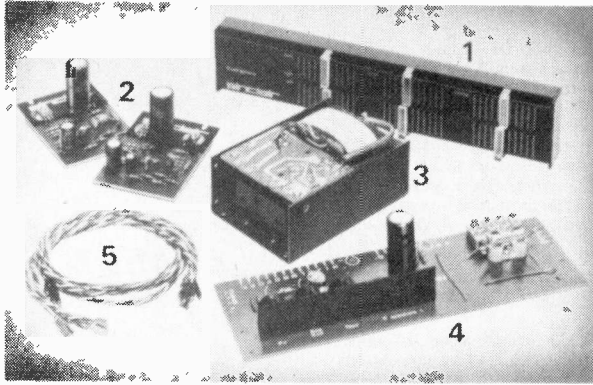

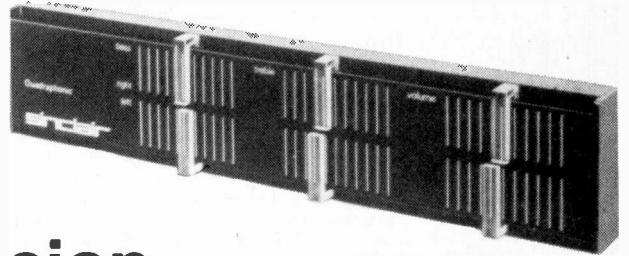1. Project 80SQ decoder with controls.
2. Two Z.40 power amplifiers.
3. PZ.5 power pack.
4. Project 80Q Masterlink unit.
5. Wire loom, with clip-on tags - NO SOLDERING!
6. (Not illustrated) Instructions manual, nuts bolts, washers, etc.


The most effective and economical way to enjoy this spectacular breakthrough in hi-fi listening




Add a fourth dimension to your stereo sound

It's so simple to convert to quadraphonics when you already have Project 80, or are about to start with Project 805. Project 805SQ is a complete add-on system at the heart of which is the Project 80SQ decoder. It uses the CBS.SQ matrix principle, by now the widest used method of containing four sound channels within the groove of the record. Project 805SQ includes two power amplifiers, power supply unit, connecting wire loom, 805Q Masterlink, switch block and instructions manual. The 805Q decoder (also obtainable separately) has independent tone and volume slider controls on the two rear channels for matching true four channel sound to domestic environment. Project 805SQ is money saving too since you do not have to scrap existing Project 80 equipment to enjoy the newest and most exciting form of home listening in the entire history of sound, and your Project 80 quadraphonic assembly is compatible with stereo and mono records.

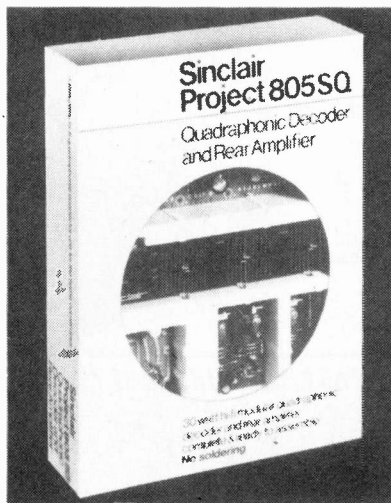- Frequency response $\pm 3\text{db}$ 15 Hz-25kHz
- Rated output 100mV
- S/N ratio 58dB
- Distortion 0.1%
- Power requirements 22-35 volts
- Phase shift network $90^\circ \pm 10^\circ$ 100 Hz-10kHz
- Adaptable to discrete (CD4) use



Project 805SQ

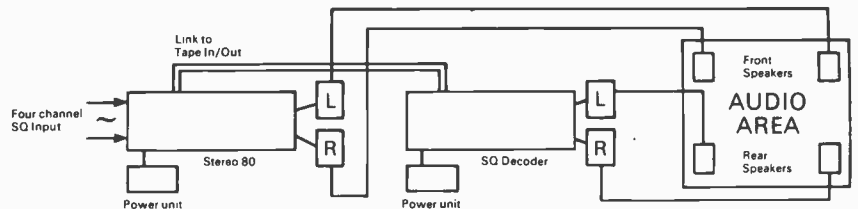

The output from any good stereo cartridge feeds into Stereo 80 and passes via the tape outlet to the 805Q decoder. Here the signal is separated into its constituent 4 channels, those for the front being accepted by the Stereo 80, those for the rear going from the decoder to the two additional power amplifiers and speakers.

£44.95

+£3.60 VAT (R.R.P.)


Guarantee If, within 3 months of purchasing any product direct from us, you are dissatisfied with it, your money will be refunded on production of receipt of payment. Many Sinclair Appointed Stockists also offer this guarantee. Should any defect arise in normal use within 2 years, we will service it without charge. For damage arising from mis-use a nominal charge will be made.

Project 80 quadraphonic modules may be purchased separately if required. The Project 805Q decoder may be used with any other amplifier having tape and monitoring facilities. Z40 or Z60 power amps can be used as required.

The Project 80 programme to date

KEEP THIS PAGE FOR HANDY REFERENCE USE THE PRIORITY ORDER FORM IN CASES OF DIFFICULTY

Stereo 80 pre-amp/control unit

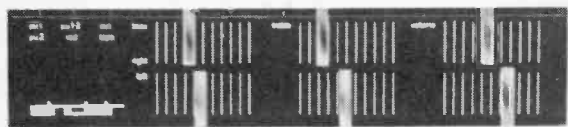

260x50x20mm (10½x2x¾ ins.) separate slider controls on each channel for treble, bass and volume. INPUTS – Mag. P.U 3mV (RIAA corrected) ceramic – 300mV, Radio 100mV, Tape 30mV. S/N ratio 60dB. Frequency range – 20Hz to 15KHz ± 1dB. OUTPUTS – 2.5V rms max (30V. supply) and tape plus AB monitoring. PRESS BUTTONS for P.U., Radio and Tape. Operating power – 20 to 35V. Black case with white indications

£13.95 +£1.12 VAT (R.R.P.)

Z.60

Size – 55x98x20mm
12 transistors
Input sensitivity – 100-250mV
Output – 25 watts RMS continuous into 8 Ω (50V).
Distortion – 0.02% at 10W/8 Ω/1KHz
Frequency response – 10Hz to more than 200KHz ± 3dB
S/N ratio – better than 70dB
Built-in protection against transient overload and short circuiting
Load impedance – 4 Ω min; max. safe on open circuit



£7.45 +60p VAT (R.R.P.)

Power-supply units

PZ.5 Unstabilized. 30 volts. Suitable for Z.40 assemblies, etc.


£5.95 +48p VAT (R.R.P.)

PZ.6 Stabilized. Output voltage adjustable between 20 and 50 volts approx. Protecting fuse.


£8.95 +72p VAT (R.R.P.)

PZ.8 Stabilized. Output adjustable from 20 to 60V. approx. Re-entrant current limiting makes damage from overload or even shorting, impossible. Without mains transformer.

£8.45 +68p VAT (R.R.P.)

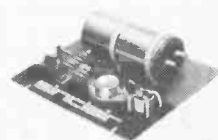

Project 80 F.M. tuner

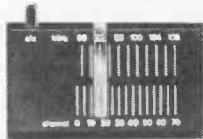

Size 85x50x20mm (3½x2x¾ ins.). Tunes 87.5 to 108MHz. DETECTOR – I.C. balanced coincidence (I.C. equivalent to 26 transistors) Distortion – 0.2% at 1KHz for 30% modulation. SENSITIVITY – 5 microvolts for 30dB quieting. Output – 300mV for 30% modulation. Aerial imp. – 75 Ω or 240-300 Ω. Dual Varicap tuning. 4 pole ceramic filter. Switchable A.F.C. Operating power 23-30 volts.

£13.95 +£1.12 VAT (R.R.P.)

Project 80 stereo decoder

Size 47x50x20mm. For adding to Project 80 FM tuner. With one I.C. equal to 19 transistors, and LED indicator which glows on tuning in stereo signal.


£8.95 +72p VAT (R.R.P.)



Project 805 (previous pages) £39.95 +£3.20 VAT (R.R.P.)

Project 805SQ quadraphonic add-on kit £44.95 +£3.60 VAT (R.R.P.)


Project 80SQ quadraphonic decoder

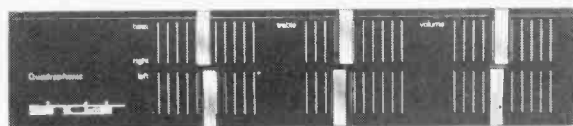

Size 260x50x20mm, matching Stereo 80 in style. Connects with tape socket on stereo 80 or similar facility on any stereo amplifier. Frequency response 15Hz to 25KHz ± 3dB. Distortion 0.1%. S/N ratio 58dB. Rated Output – 100mV. Separate bass and treble slider controls on each channel, also volume. Phase shift network 90° ± 10°, 100Hz to 10KHz. Operating power – 22-35V.

£18.95 +£1.52 VAT (R.R.P.)

Project 80 active filter unit (A.F.U.)

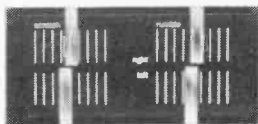

Size 108x50x20mm. Useful where there is need to eliminate unwanted high frequencies (scratch, whistle, etc) or low (rumble). Voltage gain – minus 0.2dB. Frequency response (filter at zero) 36Hz to 22KHz. H.F. cut (scratch) variable from 22KHz to 5.5KHz 12dB/octave slope. L.F. cut (rumble) – 28dB at 28Hz. slope 9dB/octave.


£7.45 +60p VAT (R.R.P.)

Project 80 power amplifiers

Intended for use in Project 80 installations, these modules readily adapt to an even wider range of applications. Both incorporate built-in protection against short circuiting and risk of damage from mis-use is greatly reduced

Z.40

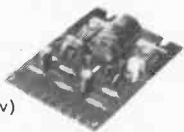
Size 55x80x20mm
9 transistors
Input sensitivity – 100mV
Output – 12 watts RMS continuous into 8 Ω (35V)
Frequency response – 10Hz – 100KHz ± 1dB
S/N ratio – 64dB
Distortion – 0.1% at 10 watts into 8 Ω at 1KHz
Power requirements – 12 to 35 volts



£5.95 +48p VAT (R.R.P.)

Sinclair Q.16 loudspeaker

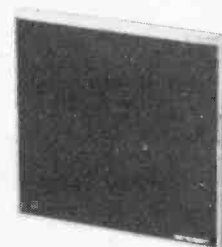An original and uniquely designed speaker of outstanding efficiency. Balanced sealed sound chamber and special driver assembly. Loads up to 14 W./R.M.S. 8 ohms imp. Size 248mm square x 120mm deep. Pedestal base. All-over black front, teak surround.



£8.95 +72p VAT (R.R.P.)

sinclair

Sinclair Radionics Ltd.,
London Road St. Ives
Huntingdonshire PE17 4HJ
Telephone St. Ives (0480) 64311
R.O. St. Ives; Reg No. 6994583 Eng.

USE THIS PRIORITY ORDER FORM IN CASES OF DIFFICULTY

To Sinclair Radionics Ltd.
Please send, (carriage paid in U.K.)

NAME

ADDRESS

For which I enclose £ cash/
cheque/money order INCLUDING V.A.T.

PE175

PHONOSONICS

SUPPLIERS OF QUALITY PRINTED
CIRCUIT BOARDS, KITS AND
COMPONENTS TO A WORLD-WIDE MARKET

SOUND-TO-LIGHT

The ever-popular AURORA—4 or 8 channels each responding to a different sound frequency and controlling its own light. Can be used with most audio systems and lamp intensities. A must for any Disco, and a fascinating visual display for the home.

4 channel component set (excl. thyristors)	£11-49
8 channel component set (excl. thyristors)	£20-32
Power supply component set	£4-78
PCB for 4 frequency channels	£2-50
PCB for power supply and 8 lamp drivers	£1-25

P.E. CCTV CAMERA Details in List

VOICE OPERATED FADER

For automatically reducing music volume during "talk-over"—particularly useful for Disco work, or for home-movie shows.

Component set, incl. PCB	£2-95
--------------------------	-------

P.E. GEMINI 30W STEREO AMPLIFIER

An exceptionally high quality Stereo Amplifier system, specifications for which are shown in detail in our list, together with semiconductor requirements.

Main Amplifier:	
Set of resistors, capacitors and presets	£5-96
Stereo printed circuit board	£1-20
Pre-Amplifier:	
Sets of resistors, capacitors, potentiometers and switches—	
Standard Tolerance Set	£10-57
Superior Tolerance Set	£16-04
Stereo PCB (as Published)	£2-20
Regulated Power Supply:	
Set of resistors, capacitors and preset	£4-58
Printed circuit board	72p

HI-FI TAPE LINK

Designed for use with reasonable quality tape decks, this high performance pre-amp includes record, playback and metering circuits.

Stereo component set (excl. panel meter)	£22-05
Mono component set (excl. panel meter)	£13-31
Power supply component set	£3-72
Stereo main PCB	£2-50
Stereo sub-assembly PCB	86p

TAPE-NOISE LIMITER

Very effective circuit for reducing the hiss found in most tape recordings.

Component set (incl. PCB)	£2-30
Regulated power supply (including printed circuit board)	£3-71

PROJECT Q4

Multi-system Quadraphonic Decoder.

Decoder component set	£13-74
Power supply components	£3-22
Set of PCBs	£2-60

SEMICONDUCTOR TESTER

Essential test equipment for the enterprising home constructor.

Set of resistors, capacitors, semiconductors, potentiometers, makaswitches and sub-assembly PCB (fuller details in list)	£6-06
--	-------

PHASING UNIT

A simple but effective manually controlled unit for introducing the "phasing" sound into live or recorded music.

Component set (incl. PCB)	£2-20
---------------------------	-------

P.E. SOUND SYNTHESISER


The well-acclaimed and highly versatile Synthesiser published in P.E. Feb. 1973 to Feb. 1974.

Component sets and printed circuit boards: Full details in list.

RHYTHM GENERATOR

Programmable for 64,000 rhythm patterns from 8 effects circuits (high and low bongos, bass and snare drums, long and short brushes, blocks and cymbal), and with variable time signatures.

Tempo, Timing and Logic Circuit	
Component set (excl. switches)	£17-25
Double-sided PCB for above	£2-30
Mixer, Pre-amp and Effects Circuits	
Component set	£12-70
PCB (illustrated)	£2-67
Monitor Amplifier	
Component set and PCB	£3-10
Power Supply	
Component set and PCB	£5-65

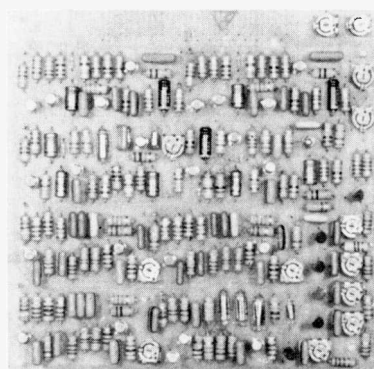

AUDIO MILLIVOLTMETER

Wide-ranges and good accuracy. Component set (excl. meter) while stocks last

Component set (excl. meter) while stocks last	£5-23
---	-------

ULTRASONIC TRANSMITTER-RECEIVER

A highly sensitive and long range "invisible beam" detection circuit with numerous applications.

Component set with PCBs, but excluding transducers	£4-40
--	-------

P.E. RONDO

PCB details in List.

P.E. ELECTRONIC PIANO

Details in List.

POWER SLAVES

PCB details in List.

HOME INTERCOM

Details in List.

SOUND BENDER

A multi-purpose sound controller, the functions of which include envelope shaper, tremolo, voice operated fader, automatic fader and frequency doubler.

Component set	£5-83
Printed circuit board	£1-44

REVERBERATION UNIT

A high-quality unit having microphone and line input pre-amps, and providing full control over reverberation level.

Component set (excl. spring unit)	£6-44
Printed circuit board	£1-40

P.E. MINISONIC Details in List

8W AMPLIFIER

A moderately powered amplifier of more than average performance.

Main Amplifier	
Mono component set	£4-18
Stereo component set	£8-38
Mono printed circuit board	72p
Pre-Amplifier	
Mono component set	£2-50
Stereo component set	£6-46
Stereo PCB	£1-66
Power Supply	
Component set	£3-90

BIOLOGICAL AMPLIFIER

Multi-function circuits that, with the use of other external equipment, can serve as lie detector, alphaphone, cardiophone, etc.

Pre-Amplifier Module	
Component set and PCB	£3-48
Basic Output Circuits	
Combined component set with PCBs, for alphaphone, cardiophone, frequency meter and visual feedback lamp driver circuits	£4-96
Audio Amplifier Module	
Type PC7	£5-20

PHOTOPRINT PROCESS CONTROL

For colour and B & W, an indispensable dark-room unit for finding exposure, controlling enlarger timing, and stabilising mains voltage.

Component set (excl. meter)	£8-65
Printed circuit board	£1-60

ENLARGER EXPOSURE METER AND THERMOMETER

Dual-purpose dark-room unit with good accuracy.

Component set with PCB, but excluding meter	£4-00
---	-------

WIND AND RAIN UNIT

A manually controlled unit for producing the above-named sounds.

Component set incl. PCB	£2-40
-------------------------	-------

PCB LAYOUT AND
CIRCUIT DIAGRAMS
SUPPLIED WITH ALL
PCBs DESIGNED BY
PHONOSONICS

P. & P.
Add 18p to all orders

VAT
Add 8% (or current
rate if different) to
total order cost in-
cluding P. & P.

LIST
Send S.A.E. for free list
giving fuller details of
kits, PCBs, and other
components.

OVERSEAS
P. & P. will be charged at cost.
VAT does not currently apply. List
gives fuller details including kit
weights. Charge for list: Europe
10p, other countries 20p.

COLOUR CODE
IDENTIFICATION
SUPPLIED WITH MOST
KITS AND AS PART OF
LIST


Semiconductors				Integrated Circuits				Zeners				Electrolytic Capacitors (µF/V)				Polyester (µF/V)		Tantalum (µF/V)	
AC128	20p	MJE3055	75p	2N3823E	39p	709 TO5	40p	0-47/63V	6p	47/63	7p	470/40	20p	0-01	3p	0-1/35	12p		
AC175	20p	NKT0033	112p	2N4870	36p	723 TO5	95p	3-3V 400mW	12p	10/63	6p	50/6-4	46p	0-015	5p	0-22/35	12p		
BC107	13p	OC29	85p	2N4871	36p	747 8-pin DIL	115p	4-7V 1W	25p	1-5/63V	6p	100/10	10p	0-022	3p	0-47/35	12p		
BC108	13p	OC71	14p	2N5777	45p	747 14-pin DIL	115p	5-6V 1-3W	20p	2-2/63V	6p	680/25	20p	0-033	3p	1-0/35	12p		
BC109	13p	OC84	25p			748 TO5	63p	6-2V 400mW	15p	4-7/63	6p	100/40	10p	0-047	3p	1-5/35	16p		
BC147	12p	ORP12	53p			748 8-pin DIL	63p	9-1V 400mW	15p	6-8/40	6p	100/63	12p	0-068	3p	2-2/35	12p		
BC148	12p	ZTX107	12p	1N814	4p	740 14-pin DIL	20p	11V 1W	20p	10/25	6p	1000/10	14p	0-1	1p	4-7/35	12p		
BC149	12p	ZTX503	15p	1N4001	6p	7402	20p	12V 400mW	15p	10/63	6p	1000/16	25p	0-15	5p	10/16	12p		
BC157	13p	ZTX531	23p	1N4002	7p	7402	20p	12V 1-3W	20p	15/40	6p	1000/25	25p	0-22	5p	10/25	16p		
BC158	13p	ZTX706	13p	1N4004	8p	7407	175p	18V 400mW	15p	22/25	6p	1000/40	40p	0-33	7p	15-6-3	16p		
BC159	13p	ZTX814	22p	1N4005	8p	7407	175p	18V 1W	20p	22/10	6p	2200/16	45p	0-47	8p	22/16	16p		
BC182L	12p	2N1304	22p	10D6	8p	7473	7489	20V 400mW	15p	33/6-3	6p	2200/25	50p	0-68	11p	47/6-3	16p		
BC204	14p	2N2219	27p	BA145	23p	7489	575p	20V 1-3W	23p	47/25	6p	2800/100	350p	1-0	14p	47/16V	25p		
BC209c	14p	2N2905	37p	OA81	7p	IA7815 TO3	250p	27V 400mW	15p	47/25	6p	3300/100	350p	2-2	24p	100/3	16p		
BC212L	15p	2N2907	22p	OA200	8p	IA7815 TO220	250p	20V 1-3W	23p	47/25	6p	4700/16	80p						
BC478	28p	2N3054	36p	CA3046	89p	CA3046	89p	Thyristors	33-50	47/25	6p	4700/25	75p						
BCY71	22p	2N3055	50p	LSJ50	11p	MC6040	85p	1A 400V	75p	47/40	6p	4700/40	93p						
BFY50	22p	2N3702	12p	Z1J	88p	PA263	169p												
BFY52	23p	2N3703	12p			SG3402N	169p												
BSY95A	12p	2N3704	12p			Miltron 3015F	225p												
MJE2955	110p	2N3819	35p																

PHONOSONICS, DEPT. PE2D, 25 KENTISH ROAD, BELVEDERE, KENT DA17 5BW
MAIL ORDER ONLY





I.L.P. (Electronics) Ltd

SHEER SIMPLICITY!

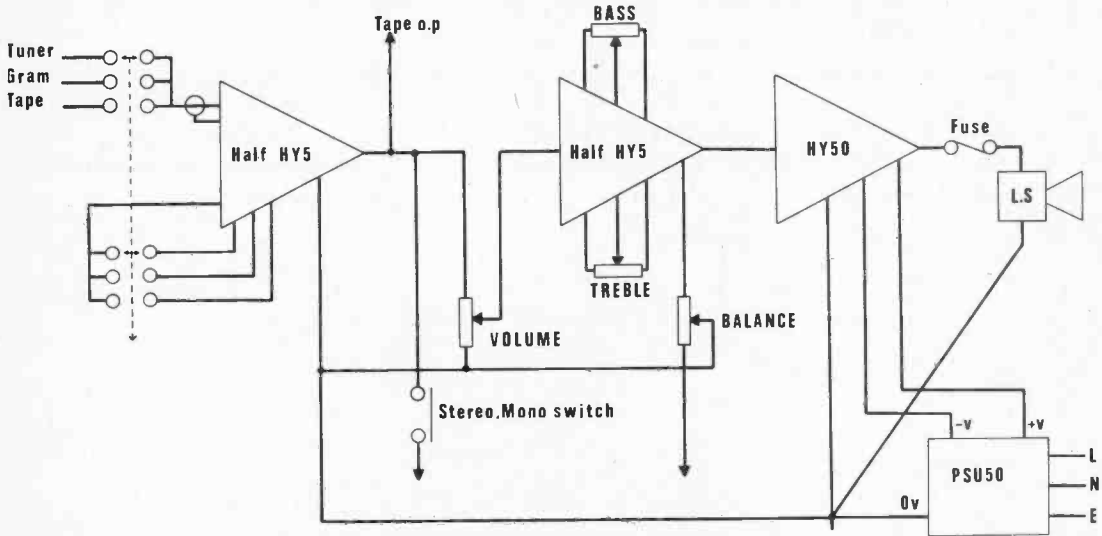

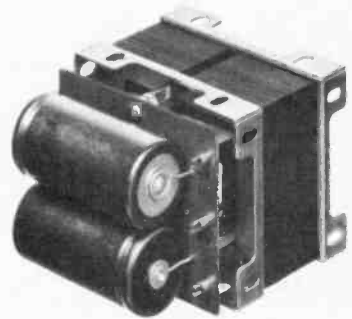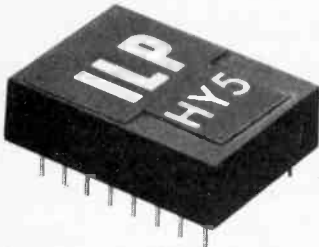MONO ELECTRICAL CIRCUIT DIAGRAM WITH INTERCONNECTIONS FOR STEREO SHOWN



The HY5 is a complete mono hybrid preamplifier. Ideally suited for both mono and stereo applications. Internally the device consists of two high quality amplifiers—the first contains frequency equalisation and gain correction, while the second caters for tone control and balance.

TECHNICAL SPECIFICATION

Inputs: Magnetic Pick-up 3mV RIAA, Ceramic Pick-up 30mV, Microphone 10mV, Tuner 100mV, Auxiliary 3-100mV; Input/impedance 47kΩ at 1kHz. Outputs: Tape 100mV; Main output 0db (0.775V RMS). Active Tone Controls: Treble ±12db at 10kHz, Bass ±12db at 100Hz. Distortion: 0.5% at 1kHz. Signal/Noise Ratio: 68db. Overload Capability: 40db on most sensitive input. Supply Voltage: ±16-25V.

The HY50 is a complete solid state hybrid Hi-Fi amplifier incorporating its own high conductivity heatsink hermetically sealed in black epoxy resin. Only five connections are provided: input, output, power lines and earth.

TECHNICAL SPECIFICATION

Output Power: 25W RMS into 8kΩ Load Impedance: 4-16kΩ. Input Sensitivity 0db (0.775V RMS). Input Impedance: 47kΩ. Distortion: Less than 0.1% at 25W typically 0.05%. Signal/Noise Ratio: Better than 75db. Frequency Response: 10Hz-50kHz ±3db. Supply Voltage: ±25V. Size: 105 x 50 x 25mm.

The PSU50 can be used for either mono or stereo systems.

TECHNICAL SPECIFICATIONS

Output voltage: ±25V. Input voltage: 210-240V. Size: L.70, D.90, H.60mm.

PRICE £5.98

+ 48p VAT
P. & P. free

PRICE £4.50

+ 36p VAT
P. & P. free

PRICE £5

TWO YEARS' GUARANTEE ON ALL OUR PRODUCTS

I.L.P. Electronics Ltd.
Crossland House,
Nacklington, Canterbury,
Kent CT4 7AD.
Tel. (0227) 63218

Please Supply
Total Purchase Price
I Enclose Cheque Postal Orders Money Order
Please debit my Access account Barclaycard account
Account number
Name and Address
Signature



GIRO NO. 331 7056
 C.W.O. only. P. & P. 10p on orders below £5
 Discount: £10-100%, £20-15% (except net items)
 Export Order enquiries welcome (VAT free)
 Official Orders accepted from
 Educational & Government Departments
ALL PRICES INCLUDE VAT

SPECIAL RESISTOR KITS (Prices include Post and Packing).

10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%). £3.65 net
 10E12 1/2W KIT: 10 of each E12 value, 22 ohms—1M, a total of 570 (CARBON FILM 5%). £3.85 net
 25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%). £8.35 net
 25E12 1/2W KIT: 25 of each E12 value, 22 ohms—1M, a total of 1425 (CARBON FILM 5%). £8.45 net
 5E12 1/2W KIT: 5 of each E12 value, 10 ohms—1M, a total of 305 (METAL FILM 5%). £2.85 net
PLEASE NOTE: DUE TO CURRENT WORLD SHORTAGES THESE KITS MAY TEMPORARILY CONTAIN BOTH WATTAGE AND VALUE SUBSTITUTIONS.

MULLARD POLYESTER CAPACITORS C280 SERIES
 250V P.C. Mounting: 0.01µF, 0.015µF, 0.022µF, 0.033µF, 0.047µF, 33p, 0.068µF, 0.1µF, 41p, 0.15µF, 41p, 0.22µF, 51p, 0.33µF, 81p, 0.47µF, 9p, 0.68µF, 12p, 1µF, 15p, 1.5µF, 23p, 2.2µF, 26p.

MULLARD POLYESTER CAPACITORS C296 SERIES
 400V: 0.001µF, 0.0015µF, 0.0022µF, 0.0033µF, 23p, 0.0047µF, 3p, 0.0068µF, 0.01µF, 0.015µF, 0.022µF, 0.033µF, 31p, 0.047µF, 0.068µF, 0.1µF, 41p, 0.15µF, 61p, 0.22µF, 81p, 0.33µF, 12p, 0.47µF, 14p.

MINIATURE CERAMIC PLATE CAPACITORS
 50V: (pF) 22, 27, 33, 39, 47, 56, 68, 82, 100, 120, 150, 180, 220, 270, 330, 390, 470, 560, 680, 820, 1K, 1K5, 2K2, 3K3, 4K7, 6K8, (µF) 0.01, 0.015, 0.02, 0.033, 0.047, 21p each, 0.1, 30p, 41p.

POLYSTYRENE CAPACITORS 160V 5%
 (pF) 10, 15, 22, 33, 47, 68, 100, 150, 220, 330, 470, 680, 1000, 1500, 2200, 3300, 4700, 10,000, 41p.

RESISTORS

W	Type	Range	1-99	100-499	500-999	1000+	Size mm
1/4	CF	22-1M	0.75	0.60	0.55	0.55	2.4 x 7.5
1/2	CF	22-2M2	0.75	0.60	0.55	0.55	3.9 x 10.5
1	CF	22-1M	1	0.75	0.60	0.55	5.5 x 16
1 1/2	MF	10-2M7	2	1.54	1.32	1.1	3 x 7
2	MF	10-2M2	2	1.43	1.21	1.09	4.2 x 10.8
2 1/2	MF	10-10M	3	1.98	1.81	1.65	6.6 x 18
3	MF	10-10M	4.5	3.52	3.08	2.75	8 x 17.5

For value mixing prices, please refer to our catalogue (price in pence each).
VALUES AVAILABLE—E12 Series only. Net prices above 100.

PRESET SKELETON POTENTIOMETERS

MINIATURE 0.25W Vertical or horizontal 6p each
 1/8, 2K2, 4K7, 10K, etc. up to 1MΩ
 SUB-MIN. 0.05W Vertical, 100Ω to 220KΩ 5p each

Wavchange Switches

1P, 4W; 1P, 12W; 2P, 2W; 2P, 4W; 2P, 6W; 3P, 3W; 4P, 2W; 3P, 4W; 4P, 3W, 30p

B. H. COMPONENT FACTORS LTD.

(P.E.) 61 CHEDDINGTON ROAD, PITSTONE, NR. LEIGHTON BUZZARD, BEDS, LU7 9AG
 Tel.: Cheddington 668446 (Std. Code 0296)
 CATALOGUE No. 3 20p.

Miniature Mullard Electronics

1.0µF 63V	61p	68µF 16V	61p
1.5µF 63V	61p	68µF 63V	12p
2.2µF 63V	61p	100µF 10V	61p
3.3µF 63V	61p	100µF 25V	61p
4.0µF 40V	61p	100µF 63V	14p
4.7µF 63V	61p	150µF 16V	61p
6.8µF 63V	61p	150µF 63V	15p
8.0µF 40V	61p	220µF 6.4V	61p
10µF 25V	61p	220µF 10V	61p
10µF 63V	61p	220µF 16V	8p
15µF 16V	61p	220µF 63V	21p
15µF 63V	61p	330µF 16V	12p
16µF 40V	61p	330µF 63V	25p
22µF 25V	61p	470µF 6.4V	9p
22µF 63V	61p	470µF 40V	20p
32µF 10V	61p	680µF 16V	15p
33µF 16V	61p	680µF 40V	25p
33µF 40V	61p	1000µF 16V	20p
32µF 63V	61p	1000µF 25V	25p
47µF 10V	61p	1500µF 6.4V	15p
47µF 15V	61p	1500µF 16V	25p
47µF 20V	61p	2200µF 10V	25p
47µF 63V	61p	3300µF 6.4V	26p

VEROBOARD 0.1 0.15

2 1/2 x 5"	36p	36p
2 1/2 x 3 1/2"	33p	25p
3 1/2 x 5"	42p	46p
3 1/2 x 3 1/2"	36p	36p
2 1/2 x 1"	9p	9p
2 1/2 x 5" (Plain)	—	19p
2 1/2 x 3 1/2" (Plain)	—	16p
5 x 3 1/2" (Plain)	—	29p
Insertion tool	73p	73p
Track Cutter	56p	56p
Pins, Pkt. 50	22p	22p

TRANSISTORS

AC126	16p	BC212L	12p
AC128	22p	BC213L	12p
BC107	11p	BC214L	17p
BC108	12p	OC44	18p
BC109	13p	OC71	13p
BC148	12p	OC81	16p
BC149	12p	OC170	23p
BC182L	12p	T1543	33p
BC183L	12p	2N2926	11p
BC184L	13p	2N3702	11p

POTENTIOMETERS

Carbon Track 5KΩ to 2MΩ, log or lin. Single, 16p. Dual Gang 46p. Log Single with Switch 26p.

DIODES

IN4001	61p
IN4002	73p
IN4003	9p
IN4004	91p
IN4005	12p
IN4006	14p
IN514	7p
IN516	7p
BA100	10p
OA5	42p
OA47	9p
OA81	11p
OA200	8p

PLUGS

DIN 2 Pin	12p
5 Pin 180°	16p
5 Pin Jack	20p
2.5mm Jack	13p
Phone	6p
DIN 2 Pin	10p
5 Pin	12p
5 Pin 180°	12p
Std. Jack	15p
2.5mm Jack	13p
Phone	6p

SOCKETS

DIN 2 Pin	10p
5 Pin	12p
5 Pin 180°	12p
Std. Jack	15p
2.5mm Jack	13p
Phone	6p

ELECTROLYTIC CAPACITORS. Tubular & Large Cans


(µF/V): 1/25, 2/25, 4/25, 4.7/10, 5/25, 8/25, 10/10, 10/50, 16/25, 22/63, 25/25, 25/50, 32/25, 50/25, 100/10, 100/25, 61p, 50/50, 8p, 100/50, 200/25, 11p, 250/50, 18p, 500/10, 11p, 500/25, 18p, 500/50, 18p, 1000/10, 9p, 1000/25, 22p, 1000/50, 40p, 2000/10, 20p, 1000/100, 90p, 2000/25, 30p, 2000/100, 95p, 2500/25, 38p, 2500/50, 62p, 3000/50, 80p, 5000/25, 66p, 5000/50, £1.10.
HI-VOLT: 8/350, 19p, 16/350, 22p, 32/350, 33p, 50/250, 20p, 100/100, 20p, 100/250, 30p, 4/450 14p, 16/450 23p.

METALLISED PAPER CAPACITORS

250V: 0.05µF, 0.1µF, 6p, 0.25, 6p, 0.5µF, 71p, 1µF, 9p, 500V: 0.025, 0.05, 6p, 0.1, 6p, 0.25, 71p, 0.5, 9p, 1000V: 0.01, 11p, 0.022, 13p, 0.047, 0.1, 15p, 0.22, 23p, 0.47, 28p.

NEW CAPACITOR KITS

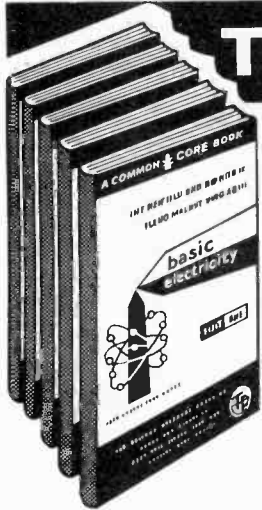— Please send for List
NOTE: ALL STOCK ADVERTISED IS SUBJECT TO AVAILABILITY



The Pictorial Method

**BASIC ELECTRICITY (5 vols)
 BASIC ELECTRONICS (6 vols)
 TELEVISION (3 vols)**

You'll find it easy to learn with this outstandingly successful PICTORIAL METHOD. The essential facts are explained in the simplest language, one at a time, and each is illustrated by an accurate cartoon-type drawing. These clear and concise illustrations make study a real pleasure. The books are based on the latest research into simplified learning techniques. This easy-approach-to-learning method has proved beyond doubt that acquiring knowledge can be an enjoyable experience.

YOUR 100% GUARANTEE
 Should you be, in any way dissatisfied with the MANUALS your money will be refunded by return of post.

The series will be of exceptional value in training mechanics and technicians in Electricity, Radio and Electronics.

WHAT READERS SAY

- At such a low cost they are a magnificent set of books.
W.L. Ladywell
- My sincere congratulations on describing everything so simply.
J.B. Retford
- I have received both enlightenment and pleasure from reading your manuals.
V.S. Huddersfield
- I am very satisfied with these carefully written and well expressed manuals.
A.W. Sandown
- They are concise and easily understood and I agree with everything that other readers have said in their favour.
W.W. Stockton
- Expressing my great delight with your excellent manuals.
S.S. Paddington

To The SELRAY BOOK CO., 60 HAYES HILL, HAYES, BROMLEY, KENT. BR2 7HP

Please find enclosed P.O./Cheque value £.....

BASIC ELECTRICITY 5 parts £6.50

BASIC ELECTRONICS 6 parts £7.50

BASIC TELEVISION 3 parts £4.25

Tick Set(s) required. Prices include Postage

YOUR 100% GUARANTEE. If after 10 days examination you decide to return the Manuals your money will be refunded in full.

NAME

BLOCK LETTERS

FULL POSTAL

ADDRESS

POST NOW FOR THIS OFFER!

FERRANTI

- ★ ALL DEVICES BRAND NEW, TOP GRADE AND TO FULL MANUFACTURERS SPECIFICATION. We do not sell seconds or rejects.
- ★ WE HAVE STOCKS OF ALL DEVICES FOR IMMEDIATE DELIVERY.
- ★ WE CAN SUPPLY ANY FERRANTI DEVICE TO ORDER. Send S.A.E. for quotation.
- ★ WE ARE SPECIALISTS IN FERRANTI SEMICONDUCTORS, WITH A STAFF OF EXPERIENCED ENGINEERS.

SCORPIO Mk. II Siemens BStBO246 SCR £1.25
Complete kit of semiconductors £5-65
(State 6V or 12V when ordering)

BFS59 18p	ZTX304 29p	ZTX504 55p	ZS170 14p
BFS60 21p	ZTX310 12p	ZTX510 25p	ZS171 16p
BFS61 21p	ZTX311 14p	ZTX530 29p	ZS172 22p
BFS96 19p	ZTX312 14p	ZTX531 34p	ZS174 26p
BFS97 23p	ZTX313 16p	ZTX550 25p	ZS176 33p
BFS98 23p	ZTX314 17p	ZTX551 27p	ZS178 58p
ZTX107 12p	ZTX330 21p	ZS270 15p	ZS271 22p
ZTX108 9p	ZTX331 22p	* DIODES *	ZS272 25p
ZTX109 14p	ZTX382 15p	ZS120 15p	ZS274 29p
ZTX212 14p	ZTX383 19p	ZS121 16p	ZS276 38p
ZTX213 15p	ZTX384 23p	ZS122 19p	ZS278 61p
ZTX214 19p	ZTX450 23p	ZS123 25p	* ZENERS *
ZTX239 16p	ZTX451 25p	ZS124 29p	KS030A to
ZTX300 16p	ZTX500 16p	ZS140 26p	KS180A 28p
ZTX301 17p	ZTX501 17p	ZS141 40p	BZV19 series 15p
ZTX302 23p	ZTX502 23p	ZS142 39p	
ZTX303 18p	ZTX503 18p		

MOTOROLA BD699 £1-10, BD700 £1-22, MJE2955 £1-30, MJE3055 75p.
RCA PRICES SLASHED! CA3090Q stereo decoder £3-25 each.
ZN414. THE FAMOUS FERRANTI RADIO I.C. ONLY £1-32 with data.
ORDIN. High quality printed circuit £2-95. Set of semiconductors £9-95.
SIGNETICS. UA748CV operational amplifier 55p.
SEMICONDUCTOR KITS FOR GEMINI AMPLIFIER AND PW DERBY HEADPHONE AMPLIFIER AVAILABLE. Send S.A.E. for details.

FREE! Our comprehensive price list giving data and connection diagrams for a wide range of Ferranti semiconductors. Just send a S.A.E. Copy sent with every order.

POSTAGE & PACKING 10p. FREE ON ORDERS OVER £3
ALL OUR PRICES INCLUDE V.A.T.

DAVIAN ELECTRONICS

P.O. BOX 38, OLDHAM, LANCS. OL2 6XJ

12in LONG PERSISTENCE CRT. Full spec. Price £8-50 to include V.A.T. and Carriage

MAKE YOUR SINGLE BEAM SCOPE INTO A DOUBLE WITH OUR NEW LOW PRICED SOLID STATE SWITCH. 2Hz to 8MHz. Hook up to a 9 volt battery and connect to your scope and have two traces for ONLY £8-25, P. & P. 25p. (Not cased, not calibrated.)

WIDE RANGE WOBBULATOR. 5MHz to 150MHz up to 15MHz sweep width. Only 3 controls. preset RF level, sweep width and frequency. Ideal for 10-7 or TV IF alignment, filters, receivers. Can be used with any general purpose scope. Full instructions supplied. Connect 6-3V a.c. and use within minutes of receiving. All this for ONLY £6-75, P. & P. 25p. (Not cased, not calibrated.)

20Hz to 200kHz WB, SINE and SQUARE GENERATOR. Four ranges. Independent amplitude controls, thermostat stabilised. Ready to use. 9V supply required. £8-95 each, P. & P. 25p. (Not cased, not calibrated.)

GRATICULES 12cm x 14cm high quality plastic 15p each, P. & P. 5p.

Large quantity of good quality components—NO PASSING TRADE—so we offer 3lb of **ELECTRONIC GOODIES** for £1-50. Post paid.

ROTARY SWITCH PACK—6 brand new switches (1 ceramic, 1 off 4 pole, 2 way, etc.). 50p, P. & P. 20p.

P.C.B. PACKS. S & D. Quantity 2 sq. ft.—no tiny pieces: 50p, P. & P. 20p.

CAPACITOR PACK—50 brand new components, only 50p, P. & P. 20p.

TRIMMER PACK. 2 twin 50/200pF ceramic, 2 twin 10/60pF ceramic; 2 min strip with 4 preset 5/20pF on each; 3 air spaced preset 30/100pF on ceramic base. ALL BRAND NEW. 25p the lot, P. & P. 10p.

PHOTOCELL equ. OCP71, 13p each. **MULLARD OCP70**, 10p each.

DELIVERED TO YOUR DOOR, 1cwt of Electronic Scrap chassis, boards, etc. No rubbish. FOR ONLY £4.

MODERN TELEPHONES. Type 706. Two-tone grey, £3-75 each. Two-tone green £3-75 each. Black £3-75 each, P. & P. 35p.

Ideal **EXTENSION TELEPHONES** with standard GPO type dial, bell and lead coding. £1-75 each, P. & P. 35p.

HANDSETS. Complete with 2 inserts and lead. 75p each, P. & P. 37p.

DIALS. ONLY 75p each, P. & P. 25p.

HIGH VALUE—PRINTED BOARD PACK. Hundreds of components, transistors, etc.—No 2 boards the same. No short leaded transistor computer boards. £1-75, post paid.

BEEHIVE TRIMMER 3/30 pF. Brand new. Qty 1-9 13p each, P. & P. 15p; 10-99 10p each, P. & P. 25p; 100-999 7p each, P. & P. free.

HE CRYSTAL DRIVE UNIT. 19in rack mount. Standard 240V input with superb crystal oven by Labgear (no crystals) £5 each. Carr. £2.

1,000pF FEED THRU CAPACITORS. Only sold in packs of 10, 30p, P. & P. 10p.

ALWAYS SOME CHEAP SCOPES AVAILABLE—or build your own. Send for our table list with a S.A.E.

PLEASE ADD V.A.T. AT 8%
OPEN 9 a.m. to 6.30 p.m. ANY DAY



CHILTMEAD LTD

7/9 ARTHUR ROAD, READING, BERKS.
(rear Tech College) Tel: Reading 582605-65916



ETI electronics today international

JAN 75
25p

ETI TOP PROJECTS
100-PAGE SPECIAL ISSUE
OF THE MORE POPULAR
PROJECTS FROM ETI

JANUARY ISSUE

OFFERS:

FIFTEEN BC108 TRANSISTORS £1

36 ELECTROLYTIC CAPACITORS £2.50

PROJECTS:

GRAPHIC EQUALISER

RUMBLE FILTER

PLUS:

SPECIAL SURVEY OF CONSTRUCTIONAL KITS

MATRIX TV FEATURE

AND MORE IN
JANUARY'S ETI
OUT NOW — **25p**
AT YOUR NEWSAGENT

electronics today international

SPECIAL
ISSUE
75p

TOP PROJECTS

REPRINTS OF OVER 20 OF THE MOST POPULAR CONSTRUCTIONAL ARTICLES

- 100W GUITAR AMP
- MIXER PREAMPLIFIER
- PHOTOGRAPHIC TIMER
- METAL LOCATOR
- BURGLAR ALARMS
- SOUND OPERATED FLASH
- AUDIO ATTENUATOR
- 8-CHANNEL MASTER MIXER
- LOWER POWER LASER
- ELECTRIC IGNITION
- UHF TV PREAMPLIFIER
- WIDE RANGE VOLTMETER
- SIMPLE LOUDSPEAKER
- TRANSISTOR TESTER
- PLUS MANY MORE


- 100W GUITAR AMP
- TRANSISTOR IGNITION
- 8-CHANNEL MIXER
- UHF TV PREAMP
- WIDE RANGE VOLTMETER
- METAL LOCATOR
- PHOTOGRAPHIC TIMER
- SOUND OPERATED FLASH
- BURGLAR ALARM SYSTEMS
- SIMPLE LOUDHAILER
- EASY PCB METHOD
- MIXER PREAMPLIFIER
- FET DC VOLTMETER
- BRAKE LIGHT INDICATOR
- AUDIO ATTENUATOR
- PLUS MANY MORE

OUT NOW— **75p**
AT YOUR NEWSAGENT


CUSTOM CABINETS

331 High Street, Rochester, Kent. Tel: Medway (0634) 404199

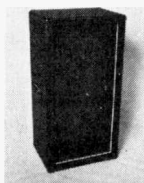
SPEAKER CABINETS IN KIT FORM REPRESENT **HUGE SAVINGS**



2' x 12" Cabinet

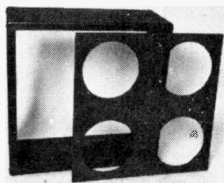

4' x 12" Cabinet

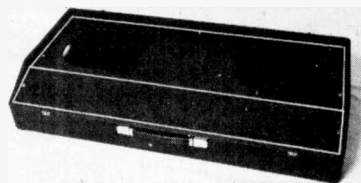

Disco Console (includes lid not shown)
Takes two slaves

For a long time now a large number of customers have asked us to produce cabinets in kit form, and above we show examples of cabinet styles and these are now available either fully built or in kit form ready for you to produce a professional finish in a very short time!


Kits are available in all specifications and all the kits contain everything you need as follows :-

- 1) 4 sides with handle cutouts, front edges rounded, 1 back with jack socket hole, and 1 baffleboard with speaker cutout
- 2) P.V.C. cut to size for frame and back, plus false front and back timbers, white front piping and speaker cloth
- 3) Recessed handles with fixing screws, jack socket, all fixing screws, corner plates, glue, and full instructions!


PRICE & TYPE LIST

Type	Size	Price manufactured	Kit price
2 x 12" (illustrated above)	36" x 18" x 13" x 3/4"	£21.45	£13.75
4 x 12" (illustrated above)	31" x 31" x 13" x 3/4"	£26.95	£19.25
4 x 12" P.A. Column	48" x 27" x 13" x 3/4"	£33.00	£23.65
1 x 18"	31" x 31" x 13" x 3/4"	£26.95	£19.25
1 x 15" with two top horn cutouts	36" x 20" x 13" x 3/4"	£23.10	£14.85
Mini Disco (state deck cutout BSR, GARRARD etc.)	33" x 20" x 8" x 1/2"	£22.00	£14.30
Maxi Disco (illustrated) (state deck cutout BSR, GARRARD etc.)	42" x 20" x 10" x 1/2"	£27.50	£19.25

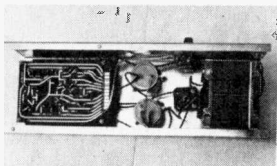Please ask for quotation on any other type or size of cabinet you may require.



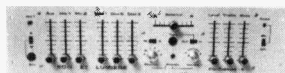- * 100w RMS slave amp for Disco
- * 100w RMS continuous sine wave output
- * Short and open circuit protection
- * Built to highest industrial spec.
- * Price £37.00 complete




- * Stereo studio disco mixer
- * Full PFL and Monitor facilities
- * As used by John Peel, Mark Wesley, Paul Burnett, DLT, Dave Christian, Tony Prince
- * Price £120.00



- ERC 100w power amplifier
- * Electrolytic capacitors and second generation ICs
- * Fully protected against short or open circuit
- * Less than 0.1% distortion at all powers
- * Rise time 4µs-stability- Unconditional Price £66.50

ALL OUR PRICES INCLUDE VAT AND UK DELIVERY

VALUE!!

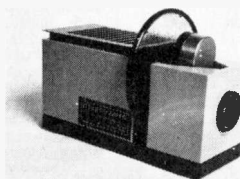

LOOK!!

Disco imp projector 150 watt tungsten
unbeatable price
Includes liquid wheel and postage
Normally sold between £24—£27.50

UNBEATABLE NOW ONLY £18


TRADE AND EXPORT ENQUIRIES WELCOME



ELECTRONICS

92 Warwick Road, Ealing, London W5 5PT
Telephone: 01-567 0424

HE 100 100 WATT POWER AMP MODULE

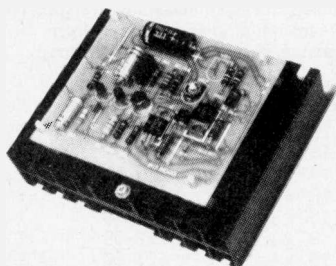

- ★ Includes large black anodised heatsink—no further heatsinks required.
- ★ Top grade glass-fibre P.C.B.
- ★ Uses high quality components.
- ★ Fully protected—short/open circuit proof.
- ★ Only 5 external connections.
- ★ Fully guaranteed.

TECHNICAL SPECIFICATIONS

- ★ Power output : 106W R.M.S. into 8 Ω
- ★ Distortion : 0.8% at full O/P. Typ. 0.4%
- ★ Frequency response : 15 Hz–23kHz
- ★ Signal to noise : Better than–96dB
- ★ Input sensitivity : 0dB (0.775V)
- ★ Input impedance : 10k Ω
- ★ Supply volts : 45–0–45V

Price £15.12 inc. VAT. (ready built)

OR

Complete kit (including P.C.B. and all components)

£11.88 inc. VAT. Enclose 50p postage & packing.

Power supply for HE 100 (including transformer, capacitors, rectifier) £8.95 inc. VAT. Postage & packing 85p.

Pre-amps etc., also available.
SAE for details.

CALLERS WELCOME

SYNTHESISER Modules by Dewtron[®]




The synthesiser illustrated was built using Dewtron modules, as sold to constructors for some years now. With over 10 years' experience in mail-order, we have supplied many famous people and groups. Over 30 types of synthesis modules, some of extremely precision design, e.g. VCO-2 log-law oscillator; 3-wave o/p/s; sample/hold/envelope module; pitch-to-voltage module allowing a whole equipment to "play itself" in unison/harmony with any solo input or voice. Modules for sequencer construction, too. Famous "Modumatrix" patching system makes other patching a thing of the past! Send just 15p for full catalogue to:

D.E.W. LTD.

254 Ringwood Road, Ferndown
Dorset BH22 9AR

Dimmit

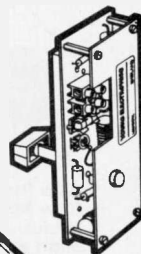range of light dimmers and lighting control systems



Illustrated is the popular PMSD1000 module. A 1000W professional quality dimmer, linear operation, interference suppressed, 60mm slider range, size 12 x 5 x 4cm. Ideal for low cost stage and disco lighting. Used by schools, theatres, studio, etc. Complete with scale plate, fixing screws and full instructions. £7.25 inc. VAT and P. & P.

Illustrated is the DD61 dimmer system. Contains: six 1000W slider dimmers type PD1000, six outlet sockets, a master control and a mains on/off switch. Size 59 x 22 x 12cm. A complete system in one unit for stage or disco lighting, etc. Other systems available with 1000W or 2000W dimmers with 2-preset and master controls.

The Dimmit range includes standard wall mounting models for home and office, etc. Professional modules for industrial heating applications, etc. Rotary and slider control versions. Ratings: 1000W; 2000W; 3000W; 110V and 240V.

Model SL800 sound to light converter. Modulates the light in time with sound. Built in microphone. Just place unit near any sound source—radio, hi-fi, TV, human voice, etc. No connections to speaker required, simple wiring—similar to dimmer. Rating 800W. Complete with full instructions.

For full information on all modules and lighting control systems send 15p for our illustrated catalogue and price list. Personal callers welcome, visit our showroom for a demonstration of any of the modules or systems.

YOUNG ELECTRONICS LTD.

184 Royal College Street, London NW1 9NN.

Tel. 01-267 0201

C. T. ELECTRONICS

NOW AT 267 & 270 ACTON LANE, LONDON W4 5DG

Now open—our new components shop. These premises are very much larger and will enable us to have greater stocks than we already have. Having all the components under one roof will now guarantee you speedier service on the counter, and on the mail order side. We have an enormous range of components to choose from. If you are having problems getting your components then come along. We are open from 9.30 a.m. through till 6 p.m. Monday to Saturday. The nearest underground is Chiswick Park, and there are no parking restrictions.

SEMICONDUCTORS

AC107	35p	BCY30	40p	MJ340	55p	OC6	65p	TIP41C	95p	2N2846	£1.50
AC125	25p	BCY31	55p	MJ481	85p	OC42	40p	TIP42C	£1.10	2N2904	25p
AC126	25p	BCY32	55p	MJ2801	£1.25	OC44	20p	T1850	40p	2N2905	25p
AC127	27p	BCY33	55p	MJ2801	£1.25	OC48	20p	ZTX107	15p	2N2906	25p
AC128	26p	BCY34	60p	MJ340	50p	OC70	15p	ZTX300	15p	2N2907	25p
AC176	27p	BCY38	85p	MJE370	75p	OC71	17p	ZTX500	18p	2N2926	12p
ACY17	25p	BCY39	£1.00	MJE371	90p	OC72	20p	ZTX501	20p	2N3053	25p
ACY18	30p	BCY55	£1.80	MJE520	65p	OC75	25p	ZTX504	50p	2N3054	65p
ACY19	30p	BCY70	22p	MJE2955E1	85p	OC78	25p	ZTX531	30p	2N3055	65p
ACY20	25p	BCY71	22p	MJE3055	85p	OC77	40p	ZTX550	25p	2N3232	85p
ACY21	30p	BCY72	25p	MM1613	43p	OC81	25p	IN659	8p	2N3255	78p
ACY39	55p	BD121	75p	MM1712	60p	OC83	25p	IN914	8p	2N3270	14p
AD140	60p	BD123	75p	MPF102	45p	OC84	25p	IN918	8p	2N3273	12p
AD142	65p	BD124	80p	MPF103	50p	OC89	25p	IN4001	8p	2N3274	12p
AD149	65p	BD131	75p	(2N5457)	35p	OC139	30p	IN4002	9p	2N3275	12p
AD161	40p	BD132	75p	MPF104	45p	OC171	30p	IN4003	9p	2N3276	12p
AD162	40p	BD153	75p	(2N5458)	35p	OC200	50p	IN4004	10p	2N3277	12p
AF114	25p	BD156	75p	MPF105	45p	OC201	80p	IN4005	12p	2N3278	12p
AF115	25p	BDY11	£1.40	(2N5459)	40p	OC202	75p	IN4006	15p	2N3279	12p
AF116	25p	BDY17	£1.80	MPSA06	35p	TIP29A	48p	IN4007	18p	2N3271	£2.70
AF117	25p	BDY19	£1.85	MPSA16	30p	TIP30A	50p	IN4008	18p	2N3272	£2.75
AF118	60p	BF152	20p	MPSA56	35p	TIP31A	52p	2N696	25p	2N3273	£2.25
AF172	30p	BF194	14p	MPSU06	75p	TIP32A	74p	2N697	20p	2N3819	35p
AS226	30p	BF195	15p	MPSU56	70p	TIP33A	£1.05	2N698	25p	2N3820	35p
AS221	60p	BFX29	30p	NKT222	25p	TIP33A	£1.55	2N708	12p	2N3866	85p
BA102	33p	BFY12	30p	NKT222	25p	TIP33A	£1.35	2N709	12p	2N3904	22p
BA112	50p	BFY85	30p	NKT401	85p	NTP36A	£2.65	2N718	15p	2N3905	25p
BA114	16p	BFY86	30p	NKT404	80p	TIP41A	75p	2N720	20p	2N4058	12p
BA156	15p	BFX88	30p	NKT774	30p	TIP42A	90p	2N1332	25p	2N4059	12p
BC107	14p	BFY12	30p	NKT774	30p	TIP29A	48p	2N1302	25p	2N4060	12p
BC108	14p	BFY44	50p	OA10	20p	TIP30B	66p	2N1303	16p	2N4061	12p
BC109	15p	BFY50	25p	OA47	10p	TIP31B	70p	2N1304	25p	2N4210	17p
BC147	12p	BFY51	25p	OA70	12p	TIP32B	82p	2N1305	25p	2N4286	15p
BC148	12p	BFX52	25p	OA70	12p	TIP32B	82p	2N1306	25p	2N4287	15p
BC149	12p	BFY52	25p	OA81	10p	TIP34B	£1.12	2N1307	25p	2N4288	15p
BC153	15p	BFY90	66p	OA90	10p	TIP35B	£2.81	2N1308	25p	2N4289	15p
BC157	14p	BSW63	85p	OA91	10p	TIP36B	£3.84	2N1309	25p	2N4290	15p
BC158	15p	BSW69	80p	OA200	10p	TIP41B	43p	2N1613	25p	2N4444	£1.80
BC159	15p	BSY58A	80p	OA202	10p	TIP42B	80p	2N1711	25p	2N4477	35p
BC169C	14p	C111	50p	OA210	35p	TIP29C	71p	2N1247	70p	2N4920	80p
BC182	14p	C426	40p	OA211	36p	TIP30C	78p	2N1260	65p	2N5191	96p
BC183	14p	BY100	15p	OC16	90p	TIP31C	55p	2N2217	25p	2N5194	£1.10
BC184	14p	BY101	15p	OC17	85p	TIP31C	55p	2N2218	25p	2N5195	96p
BC212	14p	BY127	20p	OC22	55p	TIP33C	£1.30	2N2219	25p	40360	50p
BC213	14p	BY164	85p	OC26	85p	TIP34C	£1.90	2N2222	20p	40362	50p
BC214	14p	IS100	15p	OC28	85p	TIP35C	£3.20	2N2222A	25p		
BC236	12p	IS103	20p	OC30	60p	TIP36C	£4.10	2N2929	25p		
BC239	12p							2N2646	90p		

S.C.R.s

CRS1/0	40p
CRS1/10	50p
CRS1/20	60p
CRS1/40	80p
CRS1/60	90p
CRS1/80	100p
CRS2/20	62p
CRS3/40	90p
CRS7/400	£1.00
CRS16/100	85p
CRS16/200	90p
CRS16/600	£1.60
C106B	45p
C106D	50p
40669	70p
T1044	35p
2N4444	£1.90
BTN1/500A	90p

TRIACS

TXL228B 8A 400V	95p
SC40D	£1.40
SC40E	£1.65
SC45D	£1.70
SC45E	£2.10
SC50D	£2.42
SC50E	£2.70
DIAC	25p

* * SPECIAL OFFERS * *

MINIATURE MAINS TRANSFORMER, P.R.I. 240V. SEC. 12V. 100MA Manuf. Hinchey Price 30 x 45 x 40mm F 53mm. Price 1.45p. 100-80p ea. 1000-40p ea.

3 CORE PVC INSULATED MAINS CABLE. GREY ML6650 3 x 7/20mm. Price 100-12.5p. 1000m-£35. 10,000m-£300.

0.47µF. 50V MYLAR FILM CAPACITOR Size 1in x 0.35in x 0.65in P.C Mount Price 100-4p ea. 1000-3p ea.

240V. A.C. SOLENOID. Reversible operation. Iwin coil. Size approx 2 1/2 x 1 1/2 x 1 1/2 in. Price 1.00p ea.

30 unmarked OC171 transformers £1-89

25 UNMARKED 250Wm Zenosoda. 4.7V. 5.1V. 8.2V. 7.5. 9.1V. 10V Measured and tested. State voltage required £1-08

50 GE Diode OA47 equivalent £1.00

TRANSFORMER: DOUGLAS P.R.I. 0. 115. 200. 220. 240 SEC 25-0.25-0.6V. 2A. £4-50

709C Op Amp D.I.L. TO99 45p

741C Op Amp 8.14 D.I.L TO99 55p

748C Op Amp D.I.L. TO99 75p

757C Dual Op Amp £1.20

ZN414 Radio I.C. £1.25

TAD100 Radio I.C. Inc. Filter £1.90

CA3014 £1.55

CA3018 £1.00

CA3028 £1.20

CA3036 30p

CA3046 95p

CA3048 £2.35

CA3075 £1.80

CA3090Q £4.65

MC1303L £2.20

BRIDGE RECTIFIERS

W02 1A 200V 3p	
BY164 1-4A 200V 5p	
MDA522	6A 100V 80p

ZENER DIODES

BZ98 Series 400mW	
3V-33V. 5% .1p	
1.5W range .25p	
10W range .45p	

LINEAR I.C.s

LM309 5V. 1A. Volt-age Reg. I.C. £2.10
LM723C 2.37V. 150mA Voltage Reg. £1.05
MFC 4000 250mW Audio 65p
TBA800 5 Watt Audio I.C. £1.50
709C Op Amp D.I.L. TO99 45p
741C Op Amp 8.14 D.I.L TO99 55p
748C Op Amp D.I.L. TO99 75p
601 0.2-2.2p } Price 100p ea.
601 0.2-2.2p } Price 100p ea.
601 0.5-1.5p } Price 100p ea.

TRANSFORMER

P.R.I. 0. 115. 160. 205. 225. 240 SEC 35-0.35. 1-2A £4-50 50p. p.p.

MULLARD TUBULAR CERAMIC UHF TRIMMERS (PROFESSIONAL)

Type 092 0 0.2-2p } Price 100p ea.

601 0.2-2.2p } Price 100p ea.

601 0.5-1.5p } Price 100p ea.

QUANTITY DISCOUNTS PLEASE TELEPHONE

1000p Feedthrough capacitor 7p ea.

Miniature tubular P.C trimmers 3-5.15p

3-5.15p 10p ea.

4p c/o Varley 700 relay 50p ea.

TO3 VOLTAGE REGULATORS

L005 5V 650mA £1.80

L036 12V 500mA £1.80

L037 15V 450mA £1.80 ea.

VERBOARDS

2 1/2 x 3	0-1	0.15
2 1/2 x 4	3p	2p
3 x 4	3p	3p
3 1/2 x 4	3p	3p
17 x 2 1/2	£1.05	£1.12
17 x 3	£1.43	£1.78
17 x 5	£1.64	£1.81
PIN INS TOOL	72p	72p
SP F. CUTTER	52p	52p
100 PINS DS	30p	30p
100 PINS SS	£1.20	£1.20
500 PINS DS	£1.20	£1.20
Prices Correct June 12		

DIGITAL INTEGRAL CIRCUITS

SN7400	20p	SN7428	50p	SN7473	40p	SN74107	90p	SN74166	£4.00
SN7401	20p	SN7430	20p	SN7474	40p	SN74110	80p	SN74167	£5.25
SN7402	20p	SN7432	42p	SN7475	45p	SN74118	£1.00	SN74170	£4.10
SN7403	20p	SN7433	70p	SN7476	45p	SN74119	£1.00	SN74171	£4.10
SN7404	20p	SN7434	85p	SN7477	55p	SN74121	85p	SN74175	£1.35
SN7405	20p	SN7438	85p	SN7481	£1.25	SN74122	£1.35	SN74176	£1.60
SN7406	30p	SN7440	20p	SN7482	87p	SN74123	£2.70	SN74177	£1.60
SN7407	30p	SN7441A	75p	SN7483	£1.00	SN74141	£1.00	SN74180	£1.55
SN7408	20p	SN7442	75p	SN7484	80p	SN74145	£1.50	SN74181	£7.00
SN7409	45p	SN7443	£1.00	SN7486	45p	SN74150	£3.35	SN74182	£2.70
SN7410	20p	SN7445	£2.00	SN7490	75p	SN74151	£1.10	SN74184	£2.45
SN7411	23p	SN7446	£2.00	SN7491A	£1.00	SN74153	£1.35	SN74185A	£2.40
SN7412	42p	SN7447	£1.75	SN7492	75p	SN74154	£2.00	SN74189	£1.95
SN7413	30p	SN7448	£1.75	SN7493	75p	SN74155	£1.55	SN74191	£1.95
SN7416	30p	SN7450	20p	SN7494	80p	SN74156	£1.55	SN74192	£2.00
SN7417	30p	SN7451	20p	SN7495	80p	SN74157	£1.60	SN74193	£2.00
SN7420	20p	SN7452	20p	SN7496	£1.00	SN74160	£2.60	SN74194	£2.50
SN7422	48p	SN7460	20p	SN7497	£2.25	SN74161	£2.60	SN74195	£1.85
SN7423	48p	SN7460	20p	SN74100	£2.50	SN74162	£3.40	SN74196	£1.80
SN7425	48p	SN7470	30p	SN74104	£1.45	SN74163	£3.40	SN74197	£1.50
SN7427	42p	SN7472	30p	SN74105	£1.45	SN74164	£2.75	SN74198	£4.00
						SN74165	£4.00	SN74199	£4.80

QUANTITY DISCOUNTS—12+ 10%, 25+ 15% 100+ 20%.


METAL BOXES

ALD P.K. SCREWS IDEAL FOR VERBOARD WITH BASE	
AB7 2x Long 1/2 x 5/16 1 High 50p	
AB6 4 x 1/2 1 1/2 1 1/2 50p	
AB5 4 x 1/2 1 1/2 1 1/2 50p	
AB10 4 x 5/16 1 1/2 1 1/2 50p	
AB11 4 x 2 1/2 2 1/2 60p	
AB12 3 x 3 1/2 2 1/2 44p	
AB13 6 x 4 2 1/2 2 70p	
AB14 7 x 5 2 1/2 2 84p	
AB15 8 x 6 2 1/2 2 98p	
AB16 10 x 7 3 1/2 3 £1.22	
AB17 12 x 8 4 1/2 3 £1.00	
AB18 12 x 8 3 1/2 3 £1.00	
AB19 12 x 8 3 1/2 3 £1.00	

ALUMINIUM BOXES WITH SLOPING TOP PANELS—IDEAL FOR PRE-AMPS. ETC. USING SLIDER CONTROLS

AB20 8 Long 8 Wide 3 1/2 High at back £2.

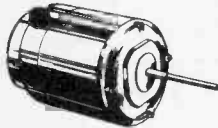"SLO-SYN" 3-LEAD SYNCHRONOUS STEPPING MOTOR



Type SS15 These fine motors are easily reversed, starting and stopping in less than 5¹/₂ without electrical or mechanical braking. Simple relay circuit can be applied to give DC to winding for a maximum holding torque of 300oz/in with 35v at 0.35 amps through winding. For AC (synchronous) operation at 120r, 50Hz. Speed 80 rpm at 60Hz, 72 rpm. STEPPING. Holding torque at 50 steps per second—100 oz/in. Can be wired to give 100 or 200 steps per revolution with accuracy of 0.1° per step non-cumulative. Torque characteristics can be modified by simple R.C. circuits. Dimensions dia. 4, body length 4 1/2, spindle length 2 1/2, dia. weight 6 1/2 lbs. BRAND NEW in maker's packing. Offered at less than 1/2 maker's price. OUR PRICE ONLY £15

NORPLEX

Fibre-glass copper-clad laminate. Finest quality epoxy resin base. Heat resistant. Ideal for P.C. Size 12" x 12" 24" x 12" 24" x 24". FULL SHEET 43" x 37" (11 sq ft.) Single-sided. Copper with thickness of 1/32". Also double sided. £1 per sq ft. Cut sizes (1-10 sq ft.) 25p P & P. Full Sheet £8 each. Carr £1 for 1st sheet plus 25p each additional sheet.


SMITHS RINGER-TIMER

Reliable 15 minute times, spring wound (concurrent with time setting) 15 x 1min divisions, approximately 1/2 divisions. Panel mounting with chrome bezel 3/4 dia. £1.40, 15p P & P.

KNOWLE (U.S.A.) MINIATURE MICROPHONE CAPSULES

Impedance approx. 200Ω, output 60 or 80 DB at 1 Kc. As used in deaf aids, bugging device, etc. Size (60 DB) 1/4" x 1/4" (80 DB) 1/4" x 1/4". Ex-equipment, all tested. £1-20 each. P & P. FREE.

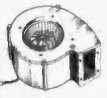Ultra PRECISION CENTRIFUGAL BLOWER by Air Control Ltd.



30 segments individually balanced in heavy cast alloy case. 2,300 r.p.m. 240 V a.c. Very powerful and silent running. 5 1/2" dia. 3" inlet dia. Outlet flange 3" x 2 1/2". Limited number only £8-95. P & P. 40p.


MAINS SOLENOID

This little unit gives vertical lift of approximately 1" through hinged 'elbow'. Bracket incorporates 2 fixing screws. Length of arm. 2 1/2". 240V AC Pull at coil is approximately 1lb. £1. FREE P & P. Special quotes for quantities.



SOLENOIDS by WESTOOL

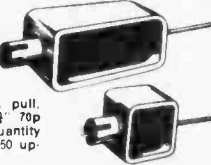240AC type MM6 3lb. pull, 2 1/2" x 1 1/2" Travel 1" 90p each. P & P 10p. 240AC type MM4 2lb. pull, 1 1/2" x 1 1/2" Travel 1" 70p each. P & P 10p. Quantity discounts: 10-50 10%, 50 upwards 25%.



OPEN FRAME shaded pole GEARED MOTORS

(Dural gear case) 240 AC, 28rpm NEW HIGH TORQUE, approx. overall size: 3 1/2" x 3 1/2" x 2 1/2" spindle 1/2" dia. as illustrated £2-70. P & P 30p. Similar to above, 19rpm. £2-70. P & P 30p. 110rpm with pressed steel gear case (similar to above but SLIGHTLY SMALLER). £2-70. P & P 30p.




SILVANIA MAGNETIC SWITCH

Now complete with reference magnet!



A magnetically activated switch, vacuum sealed in a glass envelope. Silver contacts, normally closed. Rated 3amp at 120v, 1amp at 240v. Size (approx.) 1 1/2" long x 1/2" dia. Ideal for burglar alarms, security systems etc. and wherever non-mechanical switching is required. 10 for £2-10; P & P. 15p. 50 for £8; 100 for £15-50. FREE P & P over 10.

AMPEX 7-5V. D.C. MOTOR

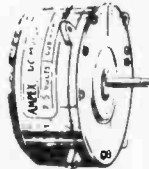

An ultra precision tape motor designed for use in the AG20 portable recorder. Torque 450GM/CM. Stall load at 500ma. Draws 60ma on run. 600rpm = speed adjustment. Internal AF/RF suppression. 1/2" dia. x 1" spindle, motor 3" dia. x 1 1/2". Original cost £15-50. OUR PRICE £3-30. P & P 25p. Quantities available. Mu-metal enclosure available 75p each. FREE P & P.

ALL PRICES INCLUDE V.A.T. Whilst we welcome official orders from established companies and Educational Departments, it is no longer practical to invoice goods under £5. Therefore, please remit cash with orders below this amount.

ELECTRO-TECH COMPONENTS LTD.

315/317, EDGWARE ROAD, LONDON, W2. Tel: 01-723 5667 01-402 5580

TRANSISTORS

AC126/7	11p	BC177	18p	BFR41	28p	ZTX500	15p	2N2905	18p	FETS	35p
AC128	11p	BC178	17p	BFX29	30p	ZTX300	14p	2N2928B	8p	BF244	31p
AC176	11p	BC179	18p	BFX30	30p	ZTX304	24p	2N2928V	9p	MPF102	31p
AC187	12p	BC182	10p	BFY30	15p	ZTX504	50p	2N3055	18p	MPF103	31p
AC188	11p	BC183	10p	BFY51	15p	ZTX505	50p	2N3442	140p	MPF104	31p
AD149	42p	BC184	11p	BFY52	15p	ZTX506	50p	2N3702/3	11p	MPF105	31p
AD161	37p	BC212	11p	BRY39	34p	2N705	12p	2N3704/5	11p	2N3819	20p
AD162	37p	BC213	10p	MJE2955	95p	2N708	18p	2N3708/9	9p	2N3820	57p
AF114/5	13p	BC214	13p	MJE3055	95p	2N710	18p	2N3772	181p	2N3823	60p
AF116/7	13p	BD115	55p	OC26	48p	2N1131/2	18p	2N3773	240p	2N3830	57p
AF139	41p	BD124	75p	OC28	48p	2N1302/3	17p	2N3803/4	15p	2N3832	60p
AF239	44p	BD131	42p	OC35	48p	2N1306/5	21p	2N4058	30p	2N4063	80p
BC107/8	9p	BD132	45p	OC36	52p	2N1308/9	28p	2N5191	95p	40841	75p
BC109	10p	BF115	22p	OC41/2	15p	2N1613	20p	2N5194	85p	3N128	50p
BC147/8	7p	BF167	23p	OC44/5	11p	2N1711	20p	UJTS	31p	3N140	85p
BC149	9p	BF173	25p	OC70/1/2	11p	2N2129	20p	TIS43	28p	3N141	75p
BC157	13p	BF184	22p	OC73	60p	2N2221	20p	2N2160	70p		
BC158	12p	BF194	11p	OC81/2	12p	2N2222	20p	2N2646	34p		
BC159	14p	BFR39	28p	OC83/4	28p	2N2369	14p	2N4871	31p		
BC169C	12p	BFR40	28p	TIP2955	70p	2N2484	30p				

SPECIAL OFFERS

555	55p	CA3046	55p
741	28p	ML723	55p
MC1310	245p	SN7447	95p
MC1312	220p	SN7490	52p

OPT-ELECTRONICS
Photo-Light Transistors Dependent
OC70 50p Resistors
OC71 65p ORP12 50p
2N5777 50p ORP60 55p
1-5 Amp
LEDS TIL209 16p ORP61 55p
Red 16p Green 35p Yellow 35p
MINITRON 3015F 120p

LATEST ICs—MANY APPLICATIONS
ICL8038 Voltage Controlled Oscillator 290p
NE567 Tone Decoder 250p
(Application Data 10p)

RECTIFIER DIODES

500mA	
BY100	15p
1 Amp	
BY126	12p
BY127	12p
1N4001	5p
1N4004	6p
1N4007	7p
1-5 Amp	
PL4004	10p
3 Amp	
PL7004	20p
6 Amp	
BY210	38p
BY211	35p
BY212	33p
BY213	38p

SIGNAL DIODES

BA100	10p
OA47	7p
OA70	8p
OA79	7p
OA81	7p
OA85	9p
OA90	6p
OA91	6p
OA95	7p
OA200	6p
OA202	7p
1N914	4p
1N916	6p
1N4148	4p

ZENER DIODES

3-3V to 33V	
400MW	9p
1-3W	18p
1-5W	25p
7W	40p
Other Diodes	
TUNNEL	
AEY11	50p
VARICAP	
BA145	17p
BA148	15p
BB103	15p
BB104	30p
BB105	30p

BRIDGE RECTIFIERS

50V	100V	400V	600V
250mA	18p	—	—
1 Amp	20p	21p	24p
2 Amp	30p	35p	45p
4 Amp	47p	48p	60p
6 Amp	55p	60p	78p

SCR-THYRISTORS

1 Amp	50V	100V	400V	600V	
3 Amp	42p	48p	60p	78p	
7 Amp	—	80p	84p	115p	
18 Amp	—	82p	88p	—	
Other					
CI06D	45p,	2N3525	81p,	2N4444	185p

TRIACS

100V	400V	500V			
3 Amp	85p	120p			
6 Amp	88p	150p			
10 Amp	109p	154p			
15 Amp	145p	180p			
Other					
40430	80p,	40486	85p,	40669	95p.
DIAC	S12	for use with above triacs	21p.		

VOLTAGE REGULATORS

ML723	55p	MFC080	70p
1 Amp		Plastic	
(TO220)	(TO5)	(TO3)	
7805	5V	140p	—
7812	12V	140p	—
7815	15V	140p	—
7818	18V	140p	—
7824	24V	140p	—

LINEAR ICs

CA3048	Transistor Array	55p
CA3048	4 Independent Amps	230p
CA3089	FM, IF Amp	250p
CA3090	FM Stereo Decoder	250p
LM301	OPA with int. comp.	40p
LM307	OPA with int. comp.	50p
MC1303	Stereo Pre-amp	150p
MC1307	FM Stereo Decoder	120p
MC1310	Collar FM Stereo Dec.	250p
MC1312	SO Quadraphonic Dec.	250p
MFC4000	1 Watt Audio Amp	40p
MFC8040	Electronic Attenuator	80p
MFC8070	Zero Voltage Switch	250p
TAA570	Limiting Amp	170p
TBA570	AM/FM Radio receiver	180p
TBA800	5 Watt Audio Amp	100p
TBA810	7 Watt Audio Amp	125p
TBA820	2 Watt Audio Amps	80p
TCA940	10 Watt Audio Amplifier	320p

Radio receiver

NE555	Timer	55p
NE558	Dual 555	120p
NE560	PLL	285p
NE561	PLL with AM Demod	285p
NE562	PLL with VCO	285p
NE565	Precision PLL	285p
NE568	Function Gen	200p
NE567	Tone Decoder	250p
Popular Op Amps		
ML708	OPA with ext. comp.	38p
ML710	DI1. com parat.	28p
ML741	OPA with int. comp.	28p
ML747	Dual 741	70p
ML748	OPA with ext. comp.	38p
TV ICs	Prices on application	
Data sheets on above ICs	10p each.	

TTL ICs

7400	14p	7441	75p	7476	37p
7401	16p	7442	70p	7480	85p
7402	16p	7443	95p	7486	41p
7404	18p	7448	120p	7489	30p
7408	20p	7450	22p	7490	52p
7410	16p	7454	22p	7492	68p
7412	16p	7460	22p	7493	55p
7413	28p	7470	30p	74107	45p
7414	72p	7472	30p	74121	34p
7416	33p	7473	30p	74122	78p
7420	16p	7474	34p	74123	110p
7430	16p	7475	52p	74141	85p

C-MOS ICs

CD4001AE	51p	CD4018AE	300p
CD4009AE	120p	CD4027AE	170p
CD4011AE	50p	CD4029AE	420p
CD4012AE	51p	CD4037AE	210p
CD4016AE	120p	CD4047AE	185p

We supply complete semiconductor parts including sockets for various projects. P.E., W. W. P. W. TELEVISION, etc.

TELENNIS
TRICOLOR LIGHT UNIT
RHYTHM GENERATOR
MINISONIC SYNTHESIZER
TGS GAS DETECTOR

Minimum order £2.
All prices exclusive of VAT.
P & P. 10p for orders under £5.

All goods brand new and guaranteed to manufacturers specification.
Money refunded if not satisfied.

TECHNOMATIC LTD.
54 Sandhurst Road, London NW9

DRY REED INSERTS



Overall length 1.85" (Body length 1.1").
Diameter 0.14". Max. ratings 250v D.C. and
500 mA. Gold clad normally open contacts. 69p
per dozen; £4.12 per 100; £30.25 per 1,000;
£275 per 10,000. VAT and post paid.

G.W.M. RADIO LTD.
40/42 Portland Road, Worthing, Sussex 0903 34897

SERVICE SHEETS

BELL'S TELEVISION SERVICES for service sheets, manuals, books on radios, T.V.s, etc. Service sheets 40p plus S.A.E. Free book lists on request. Back issues of P.W., P.E., E.E., TV available 25p plus 7p post. S.A.E. with enquiries: B.T.S. (Mail Order Dept.), 190 Kings Road, Harrogate, Yorks. Telephone (0423) 55885.

SERVICE SHEETS for over 6000 models of Televisions, Radios, Transistors, Stereo, Tape Recorders, Record Players, etc., at only 30p, plus S.A.E. with free Fault-Finding Guide. Over 50,000 sheets in stock for 10,000 models. S.A.E. enquiries. Catalogue 20p plus S.A.E. **HAMILTON RADIO**, 47 Bohemia Road, St. Leonards, Sussex. Telephone Hastings 429066.

SERVICE SHEETS, Radio, TV, etc. 8,000 models. Catalogue 20p. S.A.E. enquiries. **TELRAY**, 11 Maudland Bank, Preston.

SITUATIONS VACANT

Turn your practical experience into a career in Technical Sales

Our specialist sales support team provides a complete technical sales service to industrial and research laboratories. Some of our latest scientific weighing apparatus incorporates sophisticated electronic equipment and this is where your background comes in.

As long as you can understand the technical capabilities of our advanced equipment then we can train you to sell it.

The training is tough, so are our standards, that's why we are only looking for those who can be highly professional in this specialised and individual field of selling.

As well as a technical background in electronics we are looking for good organisation ability and plenty of self motivation.

In return we offer excellent opportunities to develop into management. Benefits include a Cortina 1600 Estate.

Write to your potential boss — W. Fergus Roy, Sales and Marketing Director, A. Gallenkamp & Co. Ltd., Christopher Street, London EC2P 2ER.

Europe's largest laboratory supply house

Gallenkamp

MEN! £70 p.w. can be yours

Jobs galore! Tens of thousands of new computer personnel needed over the next few years alone. With our revolutionary, direct-from-America, course, you train as a Computer Operator in only 4 weeks! Pay prospects? £3,500 + p.a. You know you can rely on us as we are the only computer school recognised by the Government backed National Computing Centre.

After training, our exclusive appointments bureau—one of the world's leaders of its kind—introduces you FREE to world-wide opportunities. Write or phone TODAY, without obligation.

London Computer Operators Training Centre Y31, Oxford Hse.
9-15 Oxford St., W.1. Tel. 01-734 2874

METER REPAIRS. Ammeters, voltmeters multi-range meters, etc. Send to METER, REPAIRS, 21 Mount Road, Thundersley, Benfleet, Essex, SS7 1HA.

FOR SALE

SEEN MY CAT? 5,000 items. Mechanical and Electrical Gear, and materials. S.A.E. K. R. WHISTON, Dept. PE, New Mills, Stockport.

VALVES, VALVES AND MORE VALVES. Large stocks 1930-1974, many obsolete. Also available many types of transistors and styli. Price lists available 15p. COX RADIO, The Parade, East Wittering, Sussex. West Wittering 2023.

BEAUTIFUL P.E. "GEMINI" AMPLIFIER all components as specified by designers in recommended cases built and working, £40. Buyer collects. Tel. 0702 77189 evenings. Box 57.

P.E. SYNTHESISER PROJECT. Brand new unbuilt keyboard and most components available. Send S.A.E. for details. FRANK MORTON, 65 Malmsey House, Vauxhall Street, London, SE11 5LU.

P.E. JAN. 1968 TO JULY 1974 (4 missing) Offers. Tel. Egham (Surrey) 2234.

SOLATRON DOUBLE BEAM OSCILLOSCOPE. Type CD1400 incorporating amplifiers. Type CX1441 bandwidth to 15 Mc/s. £85 O.N.O. Maidenhead 31339.

EAGLE K1400 AVOMETER for sale. New, under guarantee, £32. Write J. MVERE, 208 Sussex Gardens, London, W2.

3in. OSCILLOSCOPE home built but little used, £20. Bramley, Eastville, Eastfield, Pickering. Tel. 73270 W/Es only.

LADDERS

LADDERS, timber and aluminium. Tel. Telford 586644 for brochure.

BOOKS AND PUBLICATIONS

ELECTRONICS MEN. You are worth more than a measly £40 or £50 a week. Last year I earned £3,600 for six months work, the other six I had off. You could do similar, my booklet explains how. It's 65p from ALBEN, 3 Church Street, Diss, IP22 3DD.

YOU NEED COMPREHENSIVE TV REPAIR MANUALS

Colour TV 2—ITT/KB to 1973 plus foreign; inc. Sony, Nordmende, etc.

Colour TV 1—All other British manufacturers models to end 1973.

Mono TV 1—British sets to end 1973 covering from Alba to Ultra.

Mono TV 2—All Philips, Pye, Ekco and RBM models to end of 1973.

Mono TV 3—Due winter. Main British and Foreign portables used in UK.

Full money back assurance. Thousands of faults—hundreds of models. All written in a practical, easy to follow symptom, cause and cure style. Invaluable to amateurs and students as well as to practising engineers. Written for minimum use of instrumentation. £3 each (P. & P. 35p under 4).

SPECIAL OFFER TO READERS: First two mono and colour for £11.

COLOUR TV SIGNAL INJECTOR. A portable instrument capable of replacing both oscilloscope and colour bar generator. Traces quickly and simply faulty components, etc. Complete manufacturing instructions with full operating procedures. Manual price £1.20 (P. & P. 10p), printed circuit 75p post free. Easily made in under an hour.

TV TECHNIC PUBLICATIONS

Freeport, Larkhall, Lanarkshire, Scotland ML9 1BR
No postage needed

MISCELLANEOUS

FLUORESCENT LIGHT KIT

12 v
8 w

You can build this reverse polarity proof light for use in homes, garages, caravans, for camping, or emergency lighting. Everything is supplied: the tube, white enamelled metalwork, first quality components, P.C.B., instructions, etc.

Price only £3-19 Inc VAT post & packing
Ready built £3-78
Diffuser only 59p extra

ALUMINIUM BOXES

Prices include lid, screws, and V.A.T.
Post and packing 10p extra on all orders.

7	5 1/2"	by 2 1/2"	by 1 1/2"	high	39p
8	4"	by 4"	by 1 1/2"		39p
9	4"	by 2 1/2"	by 1 1/2"		39p
10	5 1/2"	by 4"	by 1 1/2"		39p
11	4"	by 2 1/2"	by 1 1/2"		39p
12	3"	by 2"	by 1"		29p
13	6"	by 4"	by 2"		59p
14	7"	by 5"	by 2 1/2"		69p
15	8"	by 6"	by 3"		82p
16	10"	by 7"	by 3"		89p

Order now to—

ELECTRONIC DESIGN ASSOCIATES
DEPT PE
82 Bath St., Walsall, WS1 3DE. Phone 33652

SINTEL

Add 10p P. & P. for orders under £2. Data, and circuits where appropriate, supplied with orders, or available separately (4p stamp each).

3 Digit DIP LED calculator display £1.20 - VAT = £1.29
High Quality 0.3in LED 7 seg. display 85p + VAT = £1.02
MK50250N Alarm Clock IC £3.90 - VAT = £7.45

Send for our new simple MK50250N circuit diagrams
Soldercon IC socket pins — 300 pins for £1.50 + VAT = £1.62
MK50250N + 4 x DL7800 3in LED's £1.20 - VAT = £1.01
Complete circuits and special prices for MK50250N with LED's, Minitrans or SP352's.
SINTEL, 53B ASTON STREET, OXFORD. Tel (0865) 43203

PRINTED CIRCUIT MANUFACTURERS offer any P.E. Project P.C. ready drilled. One Price 65p. C.W.O. Also P.C. production, Design, Art-Work and Photography undertaken. Send basic circuit, P.C. layout or P.C. Master stating quantity required for estimate by return or Phone: W.K.F. ELECTRONICS, Dept. P.C., Welbeck Street, Whitwell, Work-
son, Nott's., S80 4TW. Telephone Whitwell (Derbys) 695.

THE CHIPS ARE DOWN! AY-5-1224 digital clock chip now £3.95 inc. VAT, post free. Circuit and details S.A.E. GREENBANK ELECTRONICS, Dept. 320, 94 New Chester Road, Wirral, Merseyside, L62 5AG.

PSYCHEDELICATESSEN

is the only way to describe the *paradise* of FREAKY gear now available from Boffin.

LOOK!

Kits

NO LICENCE EXAM, Transmitter/Receiver £6-90
Variable-rate, BRIGHT-FLASH, Pocket Mini-Strobe £2-90

Ready-Made Experimental Modules

Maxi-Volt SPARK GENERATOR (1/2 inch spark), 15,000 Volts. £1-90
Mini DREAM-LABORATORY £3-20
SENSITIVE non-anatomical electronic STETHOSCOPE £3-20
Electronic 'VOICE-THROWER' £3-20
GHOST-HUNTING AID £3-20
PEOPLE DETECTOR £3-20
SPEAK-THRU-WATER-PHONE £6-40
PSYCHEDELIC MEDITATION AID £3-20
Bird-Watchers' REMOTE MONITOR £3-20
Psychological CROSS-EYED EARS Device £6-40
'Big Ear' SOUND-CATCHER £3-20

(All prices include VAT, packing & postage)

Send remittance to:

BOFFIN PROJECTS
4 Cunliffe Road, Stoneleigh
Ewell, Surrey

(Mail order U.K. only)

Or for more details, send 20p for lists, plus free design project sheet

AERIAL BOOSTERS £3. We make three types of aerial boosters: L45—UHF825, L12—VHF405, L11—VHF radio. TELEVISION VALVES. Most types. Any 5 45p. S.A.E. leaflets. LANCASHIRE MAIL-ORDER, 6 William Street, Stubbins, Ramsbottom, Bury, Lancs.

BUILD THE TREASURE TRACER MK III Metal Locator



- Varcap tuning
- Britain's best selling metal locator kit
- Weighs only 22oz
- Speaker and earphone operation
- Knocks down to only 17in
- Prebuilt search coil assembly
- Five transistor circuit
- Thoroughly professional finish
- You only need soldering iron, screwdriver, pliers and snips
- As seen on BBC-1 & BBC-2 TV

Send s.a.e. for leaflet

Complete kit P & P 25p + 70p VAT £9.80
Built tested and guaranteed P & P 25p + £1-10 VAT £13.75

MINIKITS ELECTRONICS, 35g LANGLEY DRIVE, WANSTEAD, LONDON E11 2LN (Mail Order Only)

MORE RANGES FOR LESS MONEY!

AC/DC Multimeter type U4324

A-DC 0-0.03-3A-6 Ranges.
A-AC 0-0.3-3A-5 Ranges.
V-DC 0-6-1200V-9 Ranges.
V-AC 3-900V-8 Ranges.
Frequency in the range of 45 to 20kHz. Resistance: 500 ohm to 5 Mohms. 5 ranges. Decibel: -10 to +12dB. Accuracy: $\pm 2.5\%$. DC $\pm 4\%$. AC Dimensions: 167 x 98 x 63mm.

Only **£8.85**




SUPERTESTER 680 R ICE

20,000 Ohm per Volt sensitivity
Fully screened against external magnetic fields
Scale width and small case dimensions (128 x 95 x 32mm)
Accuracy and stability (1% in D.C., 2% in A.C.) of indicated reading
Simplicity and ease of use and readability
Full ranges of accessories

£18.50

Accessories Extra

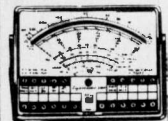


● 1,000 times overload
● Printed circuit board is removable without de-soldering
● More ranges than any other meter. Ask for free catalogue.

Accessories available to convert SuperTester 680R into following: SIGNAL INJECTOR, GAUSS METER, ELECTRONIC VOLTMETER, AMPERCLAMP, TRANSISTOR TESTER, TEMPERATURE PROBE, PHASE SEQUENCE INDICATOR—Send for details.

ALPHANUMERIC NIXIE TUBES B7971

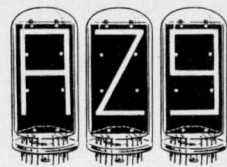The Alphameric NIXIE tube has the ability to display all the letters of the alphabet, numerals 0 thru 9 and special characters in a single tube.



From the stand-point of both readability and electrical characteristics, the Alphameric NIXIE tube provides many unique benefits including: * 17V-21mA * All d.c. operation * Uniform, continuous line characters of equal height * Memory with simple solid state drive circuits * Readability in high ambient light * 200 footcandle brightness * Long life with no loss of brightness * Character height 2 1/2in.

Bases for above 50p each

Price only **99p** each plus 16p P.P.

JUST ARRIVED!!

NUMERIC INDICATOR TUBES

Ultra-long life, high quality, 0-9 and 2 independent decimal points. Supply voltage 200V d.c. Current 14mA. Pulse duration 100us. Character height 0.51, overall size 1.4.

Brand new, guaranteed Surplus to manufacturers requirements Type B5853a1

1-25 **£1.00**; 25+ **90p**; 100+ **80p**;
1,000+ price on application.

Add 8% VAT to all items + 35p P&P

ELECTRONIC BROKERS LTD.

49-53 Pancras Road, London NW1 2QB
Tel. 01-837 7781

AUDIOSCAN, the "do-it-yourself" speaker mail-order specialists. High fidelity speaker kits, chassis units, sound absorbent, grille fabric and much more. Send 7p in stamps for bargain list to: **AUDIOSCAN**, Dept. P18, 4 Princes Square, Harrogate, Yorkshire.

SUPERB INSTRUMENT CASES by Bazelli, manufactured from heavy duty P.V.C. faced-steel. Hundreds of radio, electronic and hi-fi enthusiasts are choosing the case they require from our range of over 200 models. Generous trade discount. Prompt despatch. Free literature, **BAZELLI**, Department No. 23, St. Wilfrid's, Foundry Lane, Halton, Lancaster, LA2 6LT.

Lighting Modules and Kits Bought Direct From The Manufacturers

SOUND TO LIGHT: 3 x 1 1/2 kW channels with bypass, sensitivity and dimming controls. This unit was designed for use by hire firms and has proved to be very reliable.

MODULE (ready built), **£16.99**. **KIT**, **£14.99**.
DIMMERS: 2-way, wallmounting units, **89p**.
THEATRE AND DISCO/CLUB DIMMERS

CUSTOM BUILT

Written enquiries and Mail Order only to:

SELEKTRON

21 Priors Road, Windsor, Berks. SL4 4PD

fibre optic suppliers

MARE'S TAILS. Build a decorative display with this professionally finished unit. 22cm diameter with 7,000+ fibres. Looks immaculate. **£9.70.**

FIBROFLEX SIZE 1. Flexible 440 strand glass light conduit, bundle dia 1-14mm. 40p per metre (**£3 per 10m**)

FIBROFLEX SIZE 2. 2-28mm bundle dia. **£1.50 per metre** (**£12 per 10m**).

CROFON 1810. 64-strand plastic light conduit, bundle dia. 1-8mm, O.D. 3-3mm. **£1.20 per metre** (**£9.30 per 10m**)

PLASTIC OPTICAL MONOFIBRE. For multiple illumination from one source, displays, internal illumination, effects, optical coupling, etc.

FP20 (0.5mm dia.)—50p per 10m; **£4 per 100m**
FP40 (1mm dia.)—**£2.20 per 10m**; **£14 per 100m**
FP60 (1.5mm dia.)—**£4 per 10m**; **£30 per 100m**

OPTIKIT 183. Contains 2m Crofon 1810 plus 5m each **FP20**, **FP40**, **FP60** plus polishing compound A handy pack for the experimenter **£4.70.**

LENSES AND REFLECTORS. We stock a range of 6 lenses and 5 reflectors for use in proximity detectors, intruder detectors, batch counters, tachometers, short range optical communications.

OPTIKIT L8. 1 each of 6 lenses. **£2.50.**
OPTIKIT RRS. 1 each of 5 reflectors. **£1.50.**

CIRCULAR POLARISERS. Cut that glare. Reduce specular reflection by up to 20x—enhance contrast on CRTs, LED displays, nixies, instruments, etc. Available in red/amber/green/neutral 50mm square **89p**; 75mm **£1.20**; 150mm **£4.**

LINEAR POLARISERS. For light valves, stress analysis, type HN32. Type KN42 is for high temp. use in projectors. Use a pair to make a psychadelic light show. Price as for circular polarisers.

LIGHT SOURCES AND DETECTORS: MV54 Miniature (2mm) Red LED. 20p (10+ 18p); MLED500 T092 Red LED. 30p (10+ 18p); MLED92 Infra-Red Emitter. 30p (10+ 27p); XC209-R 3mm Red LED. 20p (10+ 18p); XC209-Y or-G Yellow/Green. 30p (10+ 27p); 2N577 High Sensitivity Photodarlington Silicon detector. gain x2,500. 50p (10+ 45p); MRD150 Silicon Phototransistor—high speed. 4us good sensitivity. 70p (10+ 87p).

****NEW ML8203.** Latest Motorola Light Activated SCR. High sensitivity 10mW/cm²; high current 400mA (5A peak); 60V. Switch small motors or relay direct from optical control, up to 24W power **£1.20** (10+ **£1.10**).

SEOS ULTRASONIC TRANSDUCER. For remote control 40kHz. Tx/Rx pair. **£3.50.**

Please add 8% VAT to prices above
Send 9in x 6in S.A.E. for short form list

FIBRE OPTIC SUPPLIERS

(Dept. PE), P.O. Box 702
London W10 6SL

CLEARING LABORATORY, scopes, recorders, testmeters, bridges, audio, R.F. generators, turntables, tapeheads, stabilised P.S.U.s, sweep generators, test equipment, etc. Lower Beeding 236.

P.C. BOARDS FOR THE P.E. CCTV CAMERA

Manufactured from highest grade glass fibre material, drilled, roller tinned and ready to assemble.

PCB1—**£1.10** plus 9p VAT.

PCB2—**90p** plus 7p VAT.

Or supplied cut to size but undrilled, **£1.25** the pair plus 12p VAT. All Post Eree.

WASCO ELECTRONICS
Queen Street, Lancaster LA1 1RX

P.C. ETCHING KIT

Contains 100 sq. in copper laminate board. Dalo etch resist pen. 1lb ferric chloride, etching dish, abrasive cleaner, and instructions, all for only **£3.30.**

RESISTORS AND CAPACITORS

500 ASSORTED RESISTORS. **£1.35**; 2,500. **£5.** 200 poly. mica, ceramic capacitors. **£1.** 250 hi-stab resistors. 1%, 2% and 5%. **£1.20.** 15 different airspaced and compression trimmers up to 1,250pF. **£1.**

VEROBOARD

100 sq. in, assorted sizes and pitches. About 8 pieces. **£1.10.**

3W TAPE AMPLIFIERS

Polished wooden cabinet 14 x 13 x 9in containing a sensitive (20uV) 4-valve amplifier with tone and volume controls; 3 watts output to the 7 x 4in. 30 loudspeaker. Also a non-standard tape deck. Supplied in good working condition with circuit. Standard mains operation. **£4.50.** Suitable cassette. **£1.10.** Spare head. **35p.** Tape (ex-computer). **75p.** Amplifier chassis only, complete and tested (2 x ECC83, EL84, E280) and speaker. **£3.**

VERSATILE POWER SUPPLY

Contains mains transformer, 2 amp thermal cut-out and bridge rectifier in neat plastic case. Will give 1-7-10-5V output with 2 extra capacitors (provided). Supplied complete with data sheet. Only **£1.20.**

SPECIAL OFFER OF 741s

Full spec. solidev devices 8-pin DIL
10 for **£2.60**; 25 for **£5.75**; 100 for **£21.**

All prices quoted include VAT and postage (mainland only) S.A.E. list, enquiries

GREENWELL ELECTRONICS (PE10)

Mail Order Dept., wholesale/retail shop: 51 Shirley Park Road, Southampton SO1 4FX (Tel. (0703) 772501). Other retail shops at: 21 Deptford Broadway SE8 (Tel. 01-892 2009), and 38 Lower Addiscombe Road, Croydon (Tel. 01-688 2950)

AMERICAN HI-POWER LOUDSPEAKERS

These powerful loudspeakers are ideal for disco, organ, P.A., guitar, etc., and are available in 8 or 16 ohm versions. The 'C' types incorporate an aluminium centre dome which extends the treble response.

M12A. 12" 50W R.M.S. ... **£19.50**

M12C. 12" 50W R.M.S. ... **£21.00**

M15E. 15" 100W R.M.S. ... **£32.40**

M15C. 15" 100W R.M.S. ... **£34.00**

Please state whether 8 or 16 ohm required when ordering.

All prices include V.A.T. and carriage.

Mail order to:

N. M. MUSIC

36 Ipswich Road + Debenham
Stowmarket + Suffolk IP14 6BH

SLOW SPEED MOTORS required (about 1 r.p.m.) any quantity considered. Phone Mr. SMITH, 061-833 3527.

HARDWARE. Comprehensive range of screws, nuts, washers, etc. in small quantities, and many useful constructors' items. Sheet aluminium to individual requirements, punched, drilled, etc. Fascia panels, dials, nameplates in etched aluminium. Printed circuit boards for this magazine, and other individual requirements, one-off's and small runs. Machine engraving in metals and plastics, contour milling. Send 2 4p stamps for catalogue. **RAMAR CONSTRUCTOR SERVICES**, Masons Road, Stratford on Avon, Warwick, CV37 9NF.

ENAMELLED COPPER WIRE

S.W.G.	1lb Reel	1/2lb Reel
10-14	£1.90	£1.05
15-19	£2.00	£1.10
20-24	£2.05	£1.15
25-29	£2.10	£1.20
30-34	£2.20	£1.28
35-40	£2.35	£1.35

All the above prices are inclusive in U.K.

COPPER SUPPLIES

102 Parrswood Rd., Withington, Manchester 20
Telephone 061-224 3553

P.O. AMPLIFIER UNIT

Contained in steel case 5 1/2 x 5 x 3 1/2in are 2 GET116 transistors on heat sinks. 3 pot cores. 2 30V zeners. 4 audio transformers. 1% resistors and capacitors. With circuit diagram. **£1.**

71b BARGAIN PARCELS

Swatches of new components—pols, resistors, capacitors, switches plus P.C. boards with transistors and diodes. Also loads of odds and ends. Contents always changing as new stocks arrive. Amazing value at **£2.30.**

COMPUTER PANELS

31b assorted **£1.40**; 71b **£2.65**; 561b **£15.** Pack: containing 500 components, including at least 50 transistors, 90p, 12 high quality panels with power transistors, trim pots, ICs, etc. **£2.50.** Pack with 20 trim pots plus other parts. **£1.** Pack with 24 FCH181 or (MC1818), **£1.**

MISCELLANEOUS


Transformers (all mains pri.): 16-0-16V with 9V tap at 1 1/2A. **£2.** 6-0-6V at 100mA. **85p**; 9-0-9V at 100mA **90p**; 12-0-12V at 100mA. **85p.** Balanced armature earpiece. Use as mic. or spkr. **20p**. 30p. 1in dia. crystal mic. insert. **35p.** Silicon grease. 2oz tube. **80p**; 1N4001 10/50p; 1N4004 10/80p; 1N4007 10/£1; SC40D Triac **£1**; 2200V/F 25V 28p. **AC127**. 128, 151, 178, 187, 188, all 20p; BC107, 108, 109, 109p; 2N3055 30p; 741C 35p.

FERRIC CHLORIDE

Anhydrous technical quality to Mil-spec in 1lb double sealed packs. 1lb **80p**; 3lb **£1.60**; 10lb **£4.45**; 100lb **£33.**

Good range of Multimeters in stock from **£3.50.**

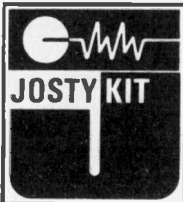SURPLUS COMPONENTS AND EQUIPMENT WANTED FOR CASH.



ONE OF
EUROPE'S
LEADING
ELECTRONIC KITS

Post free Mail Order
S.A.E. For Catalogue

TELEVIEW

414 CATCOTE ROAD
HARTLEPOOL
CLEVELAND

Build the Mullard C.C.T.V. Camera
Kits are now available with compre-
hensive construction manual (also
available separately at 80p).
SEND 5" x 7" S.A.E. FOR DETAILS TO:
CROFTON ELECTRONICS
124 Colne Road, Twickenham
Middlesex TW2 6QS

GADGETS GALORE!!

Alarms—Test Gear—Musical Instruments
Timers—Audio—Discs—Sound Effects
★ **READY BUILT AND TESTED** ★
Sample prices: Signal Injector £1.95
Signal Tracer £2.95
**PRICES INCLUDE U.K. POSTAGE
AND BATTERIES**
Mail Order Only S.A.E. list to:
G. K. SERVICES
83 Westdale Road, London SE18 3BQ

KEYBOARDS

4-OCTAVE WITH CONTACT ACTUATORS
£16 incl. VAT. Carriage £1.50
BARRY M. CHILDE
ELECTRONICS MART
370 Charminster Road, Bournemouth BH8 9RX

12 VOLT 21in 13 watt FLUORESCENT
LIGHTING (by THORN/AEI)
with diffuser and on/off switch.
Ideal, caravan, boat,
emergency lighting,
etc.
Guaranteed

£5.50
Inc. VAT and post.
List price £7.02 inc. VAT.

SALOP ELECTRONICS Tel. 53206
23 Wyle Cop, Shrewsbury, Shropshire

YATES ELECTRONICS

(FLITWICK) LTD.

DEPT. PE, ELSTOW STORAGE DEPOT
KEMPSTON HARDWICK, BEDFORD

C.W.O. PLEASE. POST AND PACKING
PLEASE ADD 10p TO ORDERS UNDER £2.

Catalogue sent free on request, 10p
stamp appreciated.

PLEASE ADD 8% VAT

RESISTORS

±W and ±W PIHER.
±W 2% ELECTROSIL

Power watts	Tolerance	Range	Values available	Price
1/4	5%	4.7 Ω - 2.2M Ω	E24	1-99 100+
1/2	10%	3.3M Ω - 10M Ω	E12	1-3p 1-1p
1	2%	10 Ω - 1M Ω	E24	3-5p 3-1p
2	10%	1 Ω - 3.9 Ω	E12	1-3p 1-1p
4	5%	4.7 Ω - 1M Ω	E12	1-3p 1-1p
4	10%	1 Ω - 10 Ω	E12	8p 7p

Quantity price applies for any selection. Ignore fractions on total order.

DEVELOPMENT PACK

0.5 watt 5% Piher resistors 5 off each value 4.7 Ω to 1M Ω.
E12 pack 325 resistors £2.40. E24 pack 650 resistors £4.70.

POTENTIOMETERS

Carbon track 5k Ω to 2M Ω, log or linear (log ±W, lin ±W).
Single, 14p. Dual gang (stereo), 49p. Single D.P. switch, 29p.

SKELETON PRESET POTENTIOMETERS

Linear: 100, 250, 500 Ω and decades to 5M Ω. Horizontal or vertical P.C. mounting
(0-1 matrix).
Sub-miniature 0.1W, 6p each. Miniature 0.25W, 7p each.

TRANSISTORS

AC107 16p	BC109 14p	BD115 75p	BF337 46p	ZTX300 18p
AC126 18p	BC115 16p	BD116 60p	BFY50 22p	ZTX302 20p
AC127 18p	BC116 15p	BD124 81p	BFY51 22p	ZTX341 18p
AC128 18p	BC117 23p	BD131 60p	BFY52 22p	ZTX500 18p
AC141K 22p	BC125 15p	BD132 64p	BRY39 41p	ZTX503 25p
AC142 25p	BC142 24p	BD140 66p	MJE340 47p	2N2646 60p
AC165 20p	BC143 21p	BDY32 57p	MJE370 68p	2N2904 28p
AC176 18p	BC147 12p	BF115 32p	OC26 90p	2N2905 32p
AC187 22p	BC148 12p	BF158 22p	OC28 90p	2N2926 12p
AC188 22p	BC149 12p	BF159 22p	OC35 90p	2N3053 31p
AC193K 28p	BC153 18p	BF160 23p	OC42 16p	2N3054 60p
AD140 53p	BC154 18p	BF161 26p	OC44 12p	2N3055 60p
AD143 73p	BC157 15p	BF164 22p	OC45 12p	2N3702 15p
AD149 70p	BC158 15p	BF173 28p	OC70 12p	2N3703 14p
AD161 42p	BC159 14p	BF177 29p	OC71 12p	2N3704 20p
AD162 42p	BC169 15p	BF178 43p	OC72 15p	2N3705 20p
AF114 25p	BC171 13p	BF179 43p	OC75 15p	2N3706 19p
AF115 25p	BC172 22p	BF180 42p	OC81 12p	2N3707 20p
AF116 25p	BC177 20p	BF181 32p	OC82 12p	2N3708 20p
AF117 25p	BC182 15p	BF182 41p	OC71 35p	2N3709 19p
AF118 50p	BC182L 16p	BF183 43p	ORP12 65p	2N3710 19p
AF121 50p	BC183 15p	BF184 32p	TIP29A 49p	2N3711 19p
AF126 50p	BC183L 16p	BF185 32p	TIP30A 58p	2N3819 25p
AF127 50p	BC184 16p	BF194 14p	TIP31A 62p	2N4062 25p
AF139 53p	BC186 25p	BF195 17p	TIP32A 74p	40360 46p
AF178 48p	BC187 25p	BF196 15p	TIP33A 98p	40361 43p
AF180 50p	BC212 13p	BF197 16p	TIP34A 148p	40362 45p
AF186 39p	BC212L 15p	BF200 40p	TIP41A 79p	40363 88p
AF239 48p	BC214L 19p	BF259 25p	TIP42A 90p	40406 44p
BC107 13p	BCY70 21p	BF262 26p	TIP43 35p	40466 90p
BC108 13p	BD112 52p	BF263 26p	ZTX108 18p	

ZENER DIODES

400mW 5% 3.3V to 30V, 12p.

WIRE WOUND POTS. 3W, 10, 25,

50 Ω and decades to 100k Ω, 50p.

DIODES

RECTIFIER

BY127	1250V	IA	12p
IN4001	50V	IA	7p
IN4002	100V	IA	8p
IN4004	400V	IA	8p
IN4006	800V	IA	10p
IN4007	1000V	IA	10p

SIGNAL

OA85	7p
OA90	5p
OA91	5p
OA202	7p
IN4148	5p
BA114	8p

MULLARD POLYESTER CAPACITORS C280 SERIES

250V P.C. mounting: 0.01μF, 0.015μF, 0.022μF, 0.033μF, 0.047μF, 3½p; 0.068μF, 4p; 0.1μF, 4½p; 0.15μF, 5p; 0.22μF, 5½p; 0.33μF, 7p; 0.47μF, 9p; 0.68μF, 12p; 1.0μF, 14½p; 1.5μF, 22p; 2.2μF, 26p.

MYLAR FILM CAPACITORS 100V
0.001μF, 0.002μF, 0.005μF, 0.01μF, 0.02μF, 3p.
0.04μF, 0.05μF, 0.068μF, 0.1μF, 6p.

CERAMIC DISC CAPACITORS
100pF to 10,000pF, 2p each.

ELECTROLYTIC CAPACITORS

(μF/v) 1/63, 1.5/63, 2.2/63, 3.3/63, 4.7/63, 6.8/40, 6.8/63, 10/25, 10/63, 15/16, 15/40, 15/63, 22/10, 22/25, 22/63, 33/63, 33/16, 33/40, 47/4, 47/10, 47/25, 47/40, 68/6.3, 68/16, 100/4, 100/10, 100/25, 150/6.3, 150/16, 220/4, 220/6.3, 220/16, 330/4, 6p, 47/63, 100/40, 150/25, 220/25, 330/10, 470/6.3, 7p, 68/63, 150/40, 220/40, 330/16, 1000/4, 10p, 470/10, 680/6.3, 11p, 100/63, 150/63, 220/63, 1000/10, 12p, 470/25, 680/16, 1500/6.3, 13p, 470/40, 680/25, 1000/16, 1500/10, 2200/6.3, 18p, 330/63, 680/40, 1000/25, 1500/16, 2200/10, 3300/6.3, 4700/4, 21p.

SOLID TANTALUM BEAD CAPACITORS

0.1μF	35V	2.2μF	35V	22μF	16V
0.22μF	35V	4.7μF	35V	33μF	10V
0.47μF	35V	6.8μF	25V	47μF	6.3V
1.0μF	35V	10μF	25V	100μF	3V

VEROBOARD

2½ x 3½	0.1	0.15	Standard screened	32p	2.5mm insulated	13p
2½ x 5	26p	28p	Standard insulated	18p	3.5mm insulated	13p
3½ x 5	28p	28p	Stereo screened	44p	3.5mm screened	22p
3½ x 3½	28p	28p	Stereo socket	15p	2.5mm socket	14p
3½ x 5	34p	34p	Stereo socket	22p	3.5mm socket	14p
17 x 24	95p	77p				
17 x 34	130p	108p				
17 x 38 (plain)	86p	72p				
17 x 24 (plain)	—	51p				
2½ x 5 (plain)	—	18p				
2½ x 3½ (plain)	—	15p				
Pin insertion tool	62p	62p				
Spot face cutter	32p	32p				
Pkt. 50 pins	20p	20p				

HIGH VOLTAGE TUBULAR CAPACITORS—1,000 VOLT

0.01μF	12p	0.047μF	16p	0.22μF	28p
0.022μF	14p	0.1μF	20p	0.47μF	36p

POLYSTYRENE CAPACITORS 160V 2½%

10pF to 1,000pF E12 Series Values, 4p each.

SMOKE AND COMBUSTIBLE GAS DETECTOR—GDI

The GDI is the world's first semiconductor that can convert a concentration of gas or smoke into an electrical signal. The sensor decreases its electrical resistance when it absorbs deoxidizing or combustible gases such as hydrogen, carbon monoxide, methane, propane, alcohol, North Sea gas, as well as carbon-dust containing air or smoke. This decrease is usually large enough to be utilized without amplification. Full details and circuits are supplied with each detector. Detector GDI £2. Smoke and Gas Detector Kits, mains operated with audible alarm £5-60. Mains operated Meter Indicator £7.90. Mains/Battery Gas Leak Detector £12-60. 12/24V Battery operated £8-40. 12V Battery operated Two Remote Sensors £12-80. NOTE: The battery operated kits incorporate our patented circuit to minimise battery drain. Typically 120mA for 12V. These kits contain all parts required with the exception of case. Suitable case mains operated kit £1-60. Battery operated kits £5.

PRINTED BOARD MARKER

97p
Draw the planned circuit onto a copper laminate board with the P.C. Pen, allow to dry, and immerse the board in the etchant. On removal the circuit remains in high relief.

EDUCATIONAL

TELEVISION TRAINING

16 MONTHS' full-time practical and theoretical training course in Radio and TV Servicing (Mono and Colour) for beginners.

13 WEEKS' full-time Colour TV Servicing course. Includes 100 hours practical training. Mono revision if necessary. Good electronics background essential.

NEXT SESSION commences on January 2nd.

Prospectus from London Electronics College, Dept. A1, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

WANTED

TOP PRICES PAID
NEW VALVES AND TRANSISTORS
Popular T.V. and Radio types
KENSINGTON SUPPLIES (B)
367 Kensington Street
Bradford 8, Yorks.

4-STATION INTERCOM



£15.15

Solve your communication problems with this 4-Station Transistor Intercom system (1 master and 3 Subs), in robust plastic cabinets for desk or wall mounting. Call/talk/listen from Master to Subs and Subs to Master. Ideally suitable for Business, Surgery, Schools, Hospital, Office and Home. Operates on one 9V battery. On/off switch. Volume control. Complete with 3 connecting wires each 66ft and other accessories. P. & P. 50p.

MAINS INTERCOM (new model)
No batteries—no wires. Just plug in the mains for instant two-way, loud and clear communication. On/off switch and volume control with lock system. Price £28.75 per pair. P. & P. 60p extra.

INTERCOM/BABY ALARM



£6.50

Same as 4-Station Intercom for two-way instant communication. Ideal as Baby Alarm and Door Phone. Complete with 66ft connecting wire. Complete with battery. P. & P. 40p.

Transistor TELEPHONE AMPLIFIER




£6.45

Why not boost business efficiency with this incredible Telephone Amplifier. Take down long telephone messages or converse without holding the handset. A useful office aid. On/off switch. Volume control. Complete with battery. P. & P. 30p. Full price refunded if not satisfied in 7 days.

WEST LONDON DIRECT SUPPLIES (PE.1)
169 KENSINGTON HIGH STREET, LONDON, W.8

SINCLAIR CALCULATORS

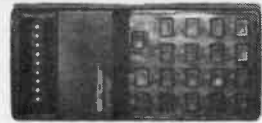


Cambridge Memory £20.95 (£1.95)
Cambridge Assembled £15.95 (£1.55)
Sinclair Scientific £22.45 (£2.05)
Executive with Memory £25.95 (£2.49)

FERRANTI ZN414

IC radio chip with data £1.20 (22p). Also available kit of extra parts to complete a radio £2.45 (42p). Send S.A.E. for free leaflet.

SINCLAIR PROJECT 80

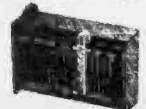AFU £6.38 (73p)
Z40 £5.12 (53p)
Z60 £6.38 (73p)
Q16 £7.21 (80p)
P25 £5.11 (53p)
P26 £7.78 (84p)
P28 £7.36 (82p)
Decoder, £7.75 (84p). Trans. for P78, £3.85 (50p).
Tuner, £11.62 (£1.37). Stereo 80, £11.62 (£1.37). Project 805, £29.95 (£2.80). Project 8055Q, £33.95 (£3.10).




ECONOMICAL QUADRAPHONICS

Introducing the Napoleo QA10 self-contained matrix quadraphonic synthesizer. Just feed the output of any stereo system (including Project 80 or 60) into It and hook on 4 speakers to obtain the latest experience in sound. Send S.A.E. for free leaflet. Only £10.15 (£1.10).



SINCLAIR SUPER IC12

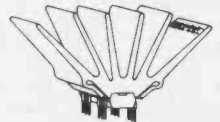6W rms power
With 44 page booklet and printed circuit
£1.80 (40p).



NEW SINCLAIR IC20

High power IC audio amplifier £8.45 (£1.05).

DELUXE KIT FOR THE IC12

Includes all parts for the printed circuit and volume, bass and treble controls needed to complete the mono version £1.70 (26p). Stereo model with balance control £3.70 (43p).

IC12 POWER KIT

Supplies 28V 0.5A £2.97 (52p).

LOUDSPEAKERS FOR THE IC12

5in 8 ohm £1.30 (29p). 5in x 8in 8 ohm £1.65 (37p).

PREAMP KITS FOR THE IC12

Type 1 for magnetic pickups, mics and tuners. Mono model, £1.40 (25p). Stereo model, £2.50 (33p). Type 2 for ceramic or crystal pickups. Mono, 79p. Stereo, £1.40 (24p).

SEND S.A.E. FOR FREE LEAFLET ON KITS


BATTERY ELIMINATOR BARGAINS

The most versatile battery eliminator ever offered. Switched output of 3, 4, 6, 7.5, 9 and 12V at 500mA. £3.90 (57p).
Other eliminators stocked: 250mA—3 way switched model giving 6, 7.5 and 9V. £2.25 (55p).
50mA—4V, £1.95 (40p). 6V, £1.95 (40p). 9V, £1.95 (40p).
7.5V cassette type, £2.50 (40p). Double 4V + 4V, £2.75 (43p). 6V + 6V £2.75 (43p). 9V + 9V, £2.75 (43p).
500mA—Heavy duty deluxe models 6V, £2.78 (55p). 7.5V, £2.78 (55p). 9V, £2.78 (55p).



S-DECS AND T-DECS

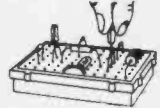S-DEC £1.98 (31p)
T-DEC £3.63 (47p)
µ-DEC A £3.99 (51p)
µ-DEC B £6.99 (81p)
IC carriers: 16 dil—plain 81p (15p). With socket, £1.77 (25p). 10 TO5—plain, 78p (15p). With socket, £1.68 (24p).



Experiment guides—A, £1.50 (26p). B, £1.77 (29p). C, 90p (18p). D, £2.40 (35p). E, £4.20 (53p).

SWANLEY ELECTRONICS

P.O. Box 68, Swanley, Kent BR8 8TQ.

Please add the sum shown in brackets after the price to cover the cost of post and new VAT. Official credit orders from schools, etc. welcome. No VAT charged on overseas orders.

PE MINI SONIC

TRANSISTORS	VOLTAGE REGULATORS	POWER SLAVE P.C.B.'s
BC204 11p	µA7815 220p	Designers Layout £1.65
BC209C 11p	723 180p	Master Board £1.10
BC182 10p	ARRAYS	Stabiliser
BC184 11p	ML3046P 75p	
BC212 14p	CA3056A 120p	
BC214 16p	OP. AMPS	
BC213 15p	709/8 Dip 39p	
BC213L 15p	710/TOS 39p	
ZTX300 15p	741 37p	
ZTX500 15p	748 48p	
2N2484 24p	FETMOPA 450p	
2N2904 30p		
2N2905 27p		
2N2219 22p		
2N3054 100p		
High Voltage	SPECIAL PURPOSE LINEARS	
MPS101 39p	SG3402N 174p	
MPS151 41p	SG3402T 174p	
MPSU07 69p	SG1495D 290p	
MPSU57 85p	MFC6040 100p	
SDT9203150p	MFC4000B 70p	
FETS	T.T.L.	
2N3819 46p	7473N 29p	
2N4559 60p	7475N 75p	
	7402N 38p	
	7404N 27p	
	7410PC 24p	
	7420N 24p	
	7430PC 23p	
	7473N 48p	
	7475N 75p	
	7476N 49p	
	7478N 660p	
	7493PC 89p	
	74121J 85p	
	74122N 80p	
	74123N 144p	
	74150N 210p	
NOISE DIODES	RESISTORS	
Z1J 53p	2% METAL	
Z1M 120p	OXIDE 16p for 5	
	5% CARBON	
	FILM 9p for 5	
RECTIFIERS		
REC41A 120p		
REC46 255p		
REC70 40p		
EA100/10		
MDA942A/1 100p		
210p		

COMPONENT KITS NOW AVAILABLE.
4½p STAMP BRING DETAILS. ASK ALSO FOR "POWER SLAVE" DETAILS.

SCOOP

Exclusive to Eaton Audio. PE minisonic demonstration cassettes. Hear the sounds produced at the Audio Fair 1974. £20 Mono Cassettes.

£1.15 each inc. VAT & postage

POTENTIOMETERS
MIN MOULDED CARBON
24mm dia.
LINEAR 5k Ω; 10k Ω; 25k Ω; 50k Ω; 100k Ω; 1M.
LOG. 10k Ω; 25k Ω; 50k Ω all at 21p each
GANGED. 100k Ω lin; 5k Ω log; 10k Ω log. all at 78p each

HEATSINKS
Marston type for POWER SLAVE 65W and 100W versions. £2.85 each
Type 154 for T05 9p each

CONSTANTAN WIRE
0.03 ohms/cm as specified for the POWER SLAVES. 20cm lengths 10p

CAPACITORS
Tubular Electro. 14p
25V, 25µF; 47µF
100µF 16p, 470µF 29p
1000µF 46p
50V, 1000µF 57p
63V, 10µF 22p
100µF 24p

PRINTED CIRCUIT ELECTROLYTIC
TYPE
4.7/40V; 10/63V
22/40V; 47/40V
100/63V; 470/16V
23p each

HIGH RIPPLE
TYPE
3300µF 63V £2.20
7100µF 40V £0.75p
10000µF 40V £1.44

TERMS: MAIL ORDER ONLY. C.W.O. Cheques or P.O.'s payable to Eaton Audio. Orders over £5 free of P.&P. Otherwise please add 10p in the £1.



MAPLIN ELECTRONIC SUPPLIES

ORGAN BUILDERS



Keyboards: High quality adjustable type Slipping front 61-note C to C. £18.50. Slipping front 49-note C to C. £14.35. Flat front 48-note F to F. £14.35. Contact blocks GB-2 (2 make contacts), 22p. Palladium earth bar per octave length, 15p. Stop tabs rocker type not engraved (white, red, grey or black) with DPDT switch, 49p. Gold clad phosphor-bronze contact wire per yard, 30p.

BASIC ORGAN CIRCUIT

Leaflet MES 51 shows a complete circuit for a basic fully polyphonic organ. Send only 15p for leaflet and start building now! **REMEMBER**—when you have built this organ you will later be able to use the same top quality component parts as the basis of a large sophisticated instrument with all the facilities you want. Watch our ads for details.

LEAFLET MES 52 shows how to extend your MES 51 basic organ to two keyboards with lots more stops. Just send 5p (stamp) with an S.A.E. and we will send you a copy.

REVERBERATION UNIT

Enhances the sound of any electronic musical instrument. Ready built spring line driver module suitable for use with almost any spring line. £5.34.

Two types of spring line available:

Short line. £1.05.

Long line. £7.59.

S.A.E. please for details. Leaflet MES 24.

MES announce the very latest development in organ circuitry.

THE DMO2

13 Master Frequencies on ONE tiny circuit board. LOOK AT THESE AMAZING ADVANTAGES

★ 13 frequencies from C8 to C9. ★ Each frequency digitally derived from a SINGLE h.f. master oscillator. ★ Initial tuning for the WHOLE ORGAN: ONE SIMPLE ADJUSTMENT. ★ Relative tuning NEVER DRIFTS! ★ External control allows instant tune-up to other musicians. ★ Outputs will directly drive most types of dividers including the SAJ110. ★ And each output can also be used as a direct tone source. ★ Variable DEPTH AND RATE tremulant optional extra. ★ Gold-plated plug-in edge connexion. ★ Complete fibre glass board (including tremulant if required) ONLY 3.7in. x 4.5in. ★ Very low power consumption.

★ EXTREMELY ECONOMICAL PRICE. ★ Ready built, tested and fully guaranteed.

DMO2 (with tremulant) ONLY £14.25.

DMO2 (without tremulant) £12.25.

SAJ110 7-stage frequency divider in one 14 pin DIL package. Sine or square wave input allows operation from almost any type of master oscillator including the DMO2 (when 97 notes are available). Square wave outputs may be modified to saw-tooth by the addition of a few components. SAJ110: £2.83 each. OR special price for pack of 12: £25.00. S.A.E. please for data sheet.

★ S.A.E. please for full technical details.

Trade enquiries welcome.

★ SAME DAY SERVICE



P.E. SOUND SYNTHESISER

If this project seems expensive YOU HAVEN'T SEEN OUR PRICES!

We are stocking all the parts for this exciting project, from the special I.C.'s right down to the nuts, bolts and spacers for mounting the Verboards.

Send S.A.E. now for our detailed price lists. Price list for Minisonic also available.

E.T.I. SYNTHESISER

We stock all the parts for the "Electronics Today International" synthesiser including all the P.C.B.'s required and all the metalwork including a drilled and printed front panel for a truly professional finish.

Some of the circuits in this brilliant design are entirely original. Independent authoritative opinions agree the E.T.I. International Synthesiser is technically superior to practically all synthesisers available today.

S.A.E. please for our detailed price lists.

CAPACITORS

Sub-miniature Axial lead electrolytic

Mfd V	Price	Mfd V	Price
1.5 6p	68	6 6p	6p
1.5 6p	68	10 14p	6p
2.2 6p	68	10 14p	6p
3.3 6p	100	4 6p	6p
4.7 6p	100	10 6p	6p
6.8 4p	100	25 6p	470
6.8 6p	100	40 6p	470
10 25 6p	100	63 16p	470
10 63 6p	150	5 6p	680
15 16 6p	120	16 6p	680
15 40 6p	150	25 6p	680
15 63 6p	150	40 14p	680
22 10 6p	150	63 16p	1000
22 25 6p	220	4 6p	1000
22 63 6p	220	10 6p	1000
33 6 3p	220	16 6p	1000
33 16 6p	220	25 14p	1500
33 40 6p	220	40 16p	1500
47 4 6p	220	63 25p	1500
47 10 6p	330	4 6p	2200
47 25 6p	330	10 6p	2200
47 40 6p	330	16 14p	3200
47 63 6p	330	63 28p	4700

PLUGS AND SOCKETS



DIN PLUGS

2 pin 11 flat 8p
3 pin 9p
4 pin, 5 pin A 4p
(180°), 5 pin B pair 30p
(240°), 6 pin 10p

DIN Sockets

2 pin 6p
3 pin, 4 pin, 5 pin 6p
A (180°), 5 pin B 28p
(240°), 7p, 6 pin 9p

MAINS

P360 3 pin 1.5A chassis plug with line socket. Per pair 30p
SA 2190 3 pin 5A chassis plug 22p
SA 1862 Line socket for above 25p

RSK way chassis socket

68p
PHONO Plug plastic 5p
Plug screened 12p
Chassis socket 4p

JACK

Sid. mono plug Plastic 13p
Screened 21p

WE KNOW YOU NEED IT!



The MES 1974 CATALOGUE IS STACKED with dozens of tempting new lines. BRIMMING OVER with clear illustrations and detailed data. WE'RE WAITING TO RUSH YOU A COPY. You'll be IMPRESSED with our POST FREE ordering system. EXCITED by our BIG VALUE discount vouchers. STAGGERED by our UNREPEATABLE speed of service. Take the first step towards real service NOW! Send ONLY 25p for our beautifully produced catalogue and leave the rest to us!

LINEARS

CA3046 Transistor array	69p
LH0042C TO99 (TOS) FET i/p Op Amp	£4.25
LM301A 8-pin DIL Op Amp	39p
MC1301L 14-pin Stereo Pre-amplifier	£1.39
MC1310P 14-pin DIL Four Stereo Decoder (no coils needed)	£2.50
MFC4000B 1W Audio Amp	75p
MFC6040 Electronic attenuator	86p
MFC8010 8-pin case. 1W Audio Power Amp	£1.20
MFC9020 10-lead case. 2W Audio Power Amp	£1.37
NE355V 8-pin DIL Precision Timer	69p
NE561B 16-pin DIL Phase Locked Loop	£4.48
SG1495D 14-pin DIL Four Stereo Analogue Multiplier	£2.70
SG3402N Amplifier/Multiplier	£1.69
µA723C TO99 (TOS), 2 to 37V Voltage Regulator	75p
µA723C 14-pin DIL 2 to 37V Voltage Regulator	75p
µA741C 8-pin DIL Op Amp	36p
µA741C 14-pin DIL Op Amp	45p
µA747C 14-pin DIL Dual Op Amp	£1.05
µA748C 8-pin DIL Op Amp	£1.20
ZN414 TOS TRF Radio	39p

Full data, pin connexions, etc., on nearly all types above in our catalogue. Price 25p.

OMNIUM GATHERUM

PP1.6 etc. battery clip dual min. 9p.
PP1.9 etc. battery clip separate per pair 6p.
Pair crocodile clips. 1 red. 1 black insulated sleeve 10p.
Solder. Multicore 22 s.w.g. 10 metres 25p.
Silicone grease in special dispenser 20ml 54p.
Terminal Block 12-way 5A 14p.
Probe clips spring loaded per pair 30p.
Panel fuse holders 20mm 20p; 14in 41p.

Transformers
LT700 min. output transformer Pri. 1 2kΩ Sec. 5Ω 200mV 50p.

Sub-main. Mains Transformer
6-0-6V 100mA 95p, 12-0-12V 50mA 95p.
Size: Both approx. 30 x 27 x 25mm

Min. Mains Transformer
Size: 46 x 31 x 38mm.
0-12V 250mA, 0-12V 250mA £1.36.


Mains Transformer MT3AT
Pri. 200-220-240V Sec. 12-15-20-24-30V 1A £3.60.

Mains Transformer MT206AT
Pri. 200-220-240V Sec. 0-15-20V 1A. 0-15-20V 1A £3.98.

POTENTIOMETERS

Rotary miniature carbon track 1/2 spindle

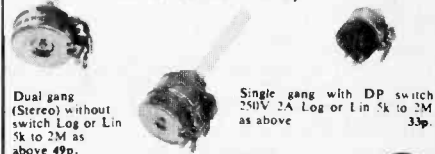Single gang Lin or Log
5k, 10k, 25k, 50k, 100k, 250k,
500k, 1M 2M (and 1k Lin) 10p



Dual gang (Stereo) Log or Lin 5k to 2M as above 49p.

Single gang with DP switch 250V 2A Log or Lin 5k to 2M as above 33p.

PRESETS

Sub-miniature 0.1W Vert or Horiz
100, 250, 600, 1k,
2.5k, 5k, 10k, 25k,
50k, 100k, 250k,
500k, 1M 7p

SWITCHES

Rotary with adjustable stop 1 pole 2 to 12 way; 2 pole 2 to 6 way; 3 pole 2 to 4 way; 4 pole 2 or 3 way, each 36p.
Mains rotary DPST 250V 2A 20p.

Slide

Sub-miniature DPDT 9p



Push to make non-locking 14p



Toggle 250V 1.5A with ON/OFF plate 25p.

High quality "sub-miniature" toggle switches.
SPDT 1.5A 240V a.c. 50p
DPDT 3A 240V a.c. 77p
Four Pole DT 3A 240V a.c. £1.37

RESISTORS

Carbon Film 1W 5% 1Ω to 1M; 10%, 1.2M to 10M E12 1p
Carbon Film 1/2W 5% 1Ω to 10Ω; 10% 1.2M to 10M E12 1p
Carbon Film 1/4W 5% 1Ω to 10kΩ E12 & E24 1p
Carbon Film 1W 5% 10Ω to 1M E12 3p
Metal Oxide 1/2W 2% 10Ω to 10M E12 & E24 4p
Wirewound 2 1/2W 10% 0.22ohms to 0.47ohms E12 14p
Wirewound 2 1/2W 5% 1ohm to 270ohms E12 12p

E12 values 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82 and decades
E24 values 11, 13, 16, 20, 24, 30, 36, 43, 51, 62, 75, 91 and decades

VAT Please add 8% to the final total.

Post and Packing FREE in U.K.
(15p handling charge on orders under £1)
First class post pre-paid envelope supplied free with every order.

Orders and enquiries for catalogues to **MAPLIN ELECTRONIC SUPPLIES, P.O. Box 3, Rayleigh, Essex. Tel. Southend-on-Sea 0702 44101**

BYWOOD CHANTICLEER

- * READ: TIME AND ALARM
- * ELECTRONIC 'BEEP' ALARM TONE
- * TEN MINUTE 'SNOOZE' FEATURE
- * BRIGHT, CLEAR DISPLAY
- * NO MOVING PARTS
- * EXECUTIVE STYLING
- * SOLID STATE RELIABILITY

COMPLETELY ELECTRONIC
NO MOVING PARTS



Digital clock

The heart of the CHANTICLEER is a tiny electronic package containing thousands of transistors which divide the 50 cycles/second mains frequency into precise time units. The clock "movement" in fact has no moving parts to wear out or tick or tock or hum or click.

Alarm

Has a.m. or p.m. setting with alarm on/off indicator. A gentle electronic 'beep' tone with special snooze feature that resets the alarm for ten-minute intervals. The snooze is activated by simply tilting the clock forward and then releasing. Upon cancelling, the alarm can be immediately reset for the same time next day.


RECOMMENDED PRICE **£19.95** + VAT

BYWOOD


BYWOOD ELECTRONICS
181 Ebbens Road
Hemel Hempstead
Herts. HP3 9RD
Tel. 0442 62757

G. F. MILWARD, 369 Alum Rock Road, Birmingham B8 3DR. Tel. 021-327 2339

12 VOLT FLUORESCENT LIGHTING

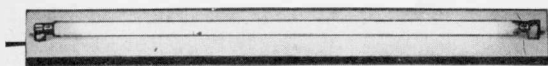

INVERTER TRANSFORMERS 13/15W **70p**
(CIRCUIT INCLUDED)
"CURRENT ECONOMY" TRANSISTOR (600 ma.) **50p**
"MAXIMUM LIGHT" TRANSISTOR (1.3A) **50p**
RESISTORS/CAPACITORS TO SUIT **15p**
LAMP HOLDERS (LONG LEAD) **30p PAIR**
(SHORT LEAD) **20p PAIR**
WHITE ENAMEL CASE, 18in or 21in (POSTAGE 30p) **70p**
TUBE, 18in-15W or 21in-13W **45p**
(NOTE: TUBE ONLY SUPPLIED IF CASE ORDERED, TO PREVENT POSTAL DAMAGE)
13W FITTING READY BUILT AND TESTED—INCLUDING TUBE (POSTAGE 30p) **£3.75**
POST/PACKING, 25p PER ORDER EXCEPT WHERE SHOWN

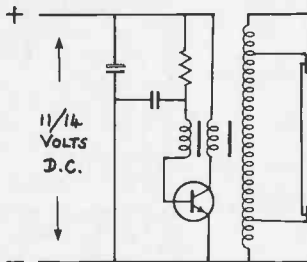

**NEW IMPROVED
CIRCUIT!**

Drives 21in 13W
18in 15W
or adaptable for
2 x 12in 8W

BRAN TUB!!!

- * Resistors—wire-wound and carbon
 - * Capacitors—silver-mica, paper, ceramic, polyester and electrolytic.
 - * Controls—volume, pre-set, carbon, wire
 - * Diodes—silicon, germanium, zener.
 - * Transistors—silicon, germanium.
- All the above are new and unused stock
We have made up packs of 2lb gross weight, all are different in content, and contain a mixture of components from the above list. This is a fantastic, unrepeatable offer that will enable you to get a good stock of spares at a tiny fraction of normal price!
To make things even more interesting—TWENTY OF THESE BAGS ALSO CONTAIN A POUND NOTE! TWENTY CUSTOMERS WILL BE VERY PLEASED INDEED!
And the price that we are asking? Only £1.50 including both postage and VAT!
Rush your order now! This offer is only made to reduce our surplus stock! It is unlikely that in these days of rising prices we shall ever be able to repeat!

£1 100 1/2 WATT RESISTORS
100 CERAMIC CAPACITORS
100 DIODES

POSTAGE 25p

PACK No. 1

£1 1 VEROBOARD CUTTER
5 2 1/2 in. x 1 in. x 0.15 BOARDS
50 sq. ins. ODD PIECES
VERO

POSTAGE 25p

PACK No. 3

£1 20 ASSORTED UNUSED MARKED, TESTED TRANSISTORS BC108 ETC.

POSTAGE 25p

PACK No. 5

£1 6 COMPUTER PANELS CONTAINING MASSES OF INDUCTORS, RESISTORS & CAPACITORS

POSTAGE 30p

PACK No. 7

£1 100 RESISTORS
100 CERAMIC CAPACITORS
100 POLYSTYRENE CAPACITORS

POSTAGE 25p

PACK No. 2

£1 100 RESISTORS
100 CERAMIC CAPACITORS
50 MULLARD POLYESTER CAPACITORS

POSTAGE 25p

PACK No. 4

£1 1 TRANSISTORISED SIGNAL TRACER KIT
1 TRANSISTORISED SIGNAL INJECTOR KIT

POSTAGE 25p

PACK No. 6

£1 100 RESISTORS
100 CAPACITORS (ASSORTED TYPES)

POSTAGE 25p

PACK No. 8

NOTE: ALL GOODS PLUS 8% VAT (EXCEPT OVERSEAS)

FREE!

Over 150 ways to engineer a better future

HIGHER PAY **A BETTER JOB**

SECURITY

find out how in just 2 minutes

That's how long it will take you to fill in the coupon. Mail it today and we'll send you full details and a free book. We have successfully trained thousands of men at home—equipped them for higher pay and better, more interesting jobs. We can do as much for YOU. A low-cost home study course gets results fast—makes learning easier and something to look forward to. There are no books to buy and you can pay-as-you-learn.

Why not do the thing that really interests you? Without losing a day's pay, you could quietly turn yourself into something of an expert. Complete the coupon (or write if you prefer not to cut the page). No obligation and nobody will call on you... but it could be the best thing you ever did.

Others have done it, so can you

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained, a view echoed by two colleagues who recently commenced the course."—Student D.I.B., Yorks.
 "Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects."—Student J.A.O., Dublin.
 "My training quickly changed my earning capacity and, in the next few years, my earnings increased fourfold."—Student C.C.P., Bucks.

FIND OUT FOR YOURSELF

These letters, and there are many more on file at Aldermaston College, speak of the rewards that come to the man who has given himself the specialised knowledge employers seek. There's no surer way of getting ahead or of opening up new opportunities for yourself. It will cost you a stamp to find out how we can help you. Write to:

ALDERMASTON COLLEGE

Dept. TPE01, Reading GR7 4PF

HOME OF BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Practical Radio & Electronics Certificate course includes a learn while you build **3 transistor radio kit.**

Everything you need to know about **Radio & Electronics** maintenance and repairs for a **spare time income** and a **career** for a better future.

This FREE 76 page book can put you on the road to success through a B.I.E.T. Home Study Course. Choose your subject now!



CUT OUT THIS COUPON
 Tick or state subject of interest. Post to address below.

MECHANICAL	DRAUGHTSMANSHIP	Construction
Society of Engineers—	Institute of Engineering	Surveyors Institute
A.M.S.E.(Mech.) <input type="checkbox"/>	Designers <input type="checkbox"/>	L.C.S.I.
Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/>	General (A.M.I.E.D.) <input type="checkbox"/>	CITY & GUILDS
CITY & GUILDS	General Draughtsmanship <input type="checkbox"/>	General Building (all branches) <input type="checkbox"/>
Gen. Mech. Eng. <input type="checkbox"/>	Flec. Draughtsmanship <input type="checkbox"/>	Heating & Vent. <input type="checkbox"/>
Maintenance Eng. <input type="checkbox"/>	Architectural <input type="checkbox"/>	Inst. Clerk of Works <input type="checkbox"/>
Welding <input type="checkbox"/>	Draughtsmanship <input type="checkbox"/>	Site Surveying <input type="checkbox"/>
Gen. Diesel Eng. <input type="checkbox"/>	Technical Drawing <input type="checkbox"/>	Health Engineering <input type="checkbox"/>
Sheet Metal Work <input type="checkbox"/>		Road Construction <input type="checkbox"/>
Eng. Inspection <input type="checkbox"/>	RADIO & TELE-COMMUNICATIONS	Quantities <input type="checkbox"/>
Eng. Metallurgy <input type="checkbox"/>	CITY & GUILDS	Estimates <input type="checkbox"/>
	Telecoms <input type="checkbox"/>	Hydraulics <input type="checkbox"/>
ELECTRICAL & ELECTRONIC	Gen. Radio & TV <input type="checkbox"/>	Structural Eng. <input type="checkbox"/>
CITY & GUILDS	Eng. Radio Amateurs <input type="checkbox"/>	GENERAL
Gen. Electrical Engineering <input type="checkbox"/>	Exam <input type="checkbox"/>	Agricultural Eng. <input type="checkbox"/>
Electrical Installations <input type="checkbox"/>	Radio Servicing <input type="checkbox"/>	Council of Eng. Institutions <input type="checkbox"/>
Electrical Maths <input type="checkbox"/>		Farm Science <input type="checkbox"/>
Computer Electronics <input type="checkbox"/>	AUTOMOBILE & AERONAUTICAL	Plastics <input type="checkbox"/>
Electronic Eng. <input type="checkbox"/>	Institute of the Motor Industry <input type="checkbox"/>	<i>Supplementary courses for Nat. Certificates.</i>
Practical Radio & Electronics (with kit) <input type="checkbox"/>	A.M.I.I. <input type="checkbox"/>	
MANAGEMENT & PRODUCTION	CITY & GUILDS	
Institute of Cost & Management <input type="checkbox"/>	Auto Eng. <input type="checkbox"/>	
Accountants <input type="checkbox"/>	Gen. Auto Eng. <input type="checkbox"/>	
Computer Programming <input type="checkbox"/>	Motor Mechanics <input type="checkbox"/>	
Works M'nt <input type="checkbox"/>	Auto Diesel Eng. <input type="checkbox"/>	
Work Study <input type="checkbox"/>	Garage M'nt <input type="checkbox"/>	
Gen. Production Eng. <input type="checkbox"/>	AFC. Aero <input type="checkbox"/>	
Estimating & Planning <input type="checkbox"/>	Engineering <input type="checkbox"/>	
Storekeeping <input type="checkbox"/>	Exams <input type="checkbox"/>	
Management <input type="checkbox"/>	Gen. Aero Eng. <input type="checkbox"/>	
Skills <input type="checkbox"/>		
Quality Control <input type="checkbox"/>	CONSTRUCTIONAL	
	Institute of Building <input type="checkbox"/>	
	I.I.O.B. <input type="checkbox"/>	
	A.B.T. Clerk of Works <input type="checkbox"/>	
	Works <input type="checkbox"/>	
		<i>Coaching for many exams, including C & G</i>

G.C.E.
 — choose from 58 'O' & 'A' level subjects.

POST TODAY FOR A BETTER TOMORROW

To Aldermaston College, Dept. TPE01, Reading RG7 4PF

NAME
 Block Capitals Please
 ADDRESS

POST CODE

OTHER SUBJECTS

AGE

Accredited by C.A.C.C.

Member of A.B.C.C.

Published approximately on the 15th of each month by IPC Magazines Ltd., Fleetway House, Farringdon Street, London, EC4A 4AD. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand—Gordon & Gotch (A/sia) Ltd.; South Africa—Central News Agency Ltd. Publisher's Subscription Rate including postage for one year, Inland £3.25, Overseas £4.10. International Giro facilities Account No. 5122007. Please state reason for payment. "message to payee".
 Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, excluding Eire where the selling price is subject to V.A.T., and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.


Henry's SO MUCH MORE - AND YOU PAY LESS VAT WITH HENRY'S LOW PRICES

NEW CATALOGUE
available
December.
75p with
vouchers



You can build the Texan and Stereo FM Tuner TEXAN 20 + 20 WATT IC STEREO AMPLIFIERS

Features glass fibre PC board, Gardners low field transformer, 6 ICs, 10 transistors plus diodes, etc. Designed by Texas Instruments engineers for Henry's (and P.W. 1972). Supplied with full chassis work, detailed construction handbook and all necessary parts. Full input and control facilities. Stabilised supply. Overall size 15 1/2in x 2 1/2in x 6 1/2in. Mains operated. Free teak sleeve with every kit. **£31-00 (G.B. post paid). BUILT AND TESTED £37-50.**

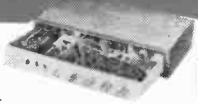

STEREO FM TUNER

Features capacity diode tuning, led and tuning meter indicators, stabilised power supply—mains operated. High performance and sensitivity with unique station indication IC stereo decoder. Overall size in teak sleeve 8in x 2 1/2in x 6 1/2in. Complete kit with teak sleeve. **£21-00 (G.B. post paid). BUILT AND TESTED £24-95.**

JOIN THE LARGE BAND OF HAPPY CONSTRUCTORS!

CALCULATORS




Sinclair Cambridge Kit	£13-50
Sinclair Cambridge (Built)	£17-50
Sinclair Memory	£22-50
Sinclair Scientific	£26-95
Sinclair Scientific Kit	£18-50

130 WAVE



TRANSISTORISED MODULES

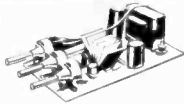

Tuners—Power Suppliers—Amplifiers

Amplifiers (All single channel unless stated)

4-300	9V	300mW O/P 3-8 ohm, 1-10mV I/P	£ 1.75
2004	9V	250mW O/P 3-8 ohm, 10-100mV I/P	2.70
104	9V	1W O/P 8-16 ohm, 10mV I/P	3.10
304	9V	3W O/P 4-8 ohm, 10mV I/P	3.95
555	12V	3W O/P 8-16 ohm, 150mV I/P	4.10
555ST	12V	1 1/2in + 1 1/2in O/P 8 ohm, 150mV I/P	5.95
E1208	12V	5W O/P 4-16 ohm, 25-50mV I/P	5.10
608	24V	10W O/P 4-8 ohm, 30-50mV I/P	4.95
410	28V	10W O/P 8 ohm, 160mV I/P	4.95
620	45V	30W O/P 4-8 ohm, 150mV I/P	9.95
Z40	30/35V	15W O/P 4-8 ohm, 100mV I/P	5.45
Z60	45/50V	25W O/P 4-8 ohm, 100-250mV I/P	6.95
SA6817	24V	6 - 6 O/P 8 ohm, 100mV I/P	10-20

EMI SPEAKERS SPECIAL PURCHASE



13in x 8in chassis speakers (carr./packing 30p each or 50p pair), + 150 TC 10W 8 ohm twin cone, £2-20. 450 TC 10W 4, 8, 15 ohm with twin tweeters and crossover £3-85 each.
EW 15W 8 ohm with tweeter £5-25
350 20W 8, 15 ohm with tweeter each £7-80
Polished wood cabinet £4-80 (carr. etc. 35p each or 50p pair)

PHILIPS 8 WATT FLUORESCENT UNIT EXCLUSIVE PURCHASE



Brand new Philips 12V operated 8W fluorescent tube units for standby lighting. Complete with tube and instructions. Price £3-50 (P. & P. 25p).

SINCLAIR SPECIAL PURCHASE

Project 60 Stereo Pre-Amplifier £6-75 P. & P. 20p
Project 60S Kit £19-95 P. & P. 25p
I.C. 12 6W Amplifier £2-10 P. & P. 15p

PORTABLE RADIO ACTIVITY COUNTER

Complete with Power Pack. £9-97 P. & P. £1.

DOSIEMETERS

0-5R	62p	} 45p each per dozen
0-50R	62p	
0-150R	62p	

Amplifiers with controls

E1210	12V	2 1/2 + 2 1/2W	8 ohms	8.25
RE500	Mains	5W	4-16 ohms	6.30
SAC14		7 - 7W	8 ohms	11.75
SAC30		15 + 15W	8 ohms	14.95
CAO38	9V	1 1/2 + 1 1/2W	8 ohms	6.95
CAO68	12V	3 - 3W	8 ohms	10.50

FM Modules

Mullard LP1186 FM tuner (front end) with data 10.7 MHz O/P	4.85
Mullard LP1185 10.7 MHz IF unit with data	4.50
Gorler Permeability FM tuner (front end) 10.7 MHz O/P	4.20

FM and AM tuners and decoders

FM5231 (Tu 2) 6V FM tuner	7.95
E1500 TU3 12V version (FM use with decoder)	7.95
SD4912 Decoder for Tu3 12V Stereo	14.95
SP62H 6V stereo FM tuner	6.80
A1007 9V MW-AM tuner	11.95
Sinclair 12.45V FM tuner stereo recorder for above	7.45
A1018 9V FM tuner in cabinet	13.95
A1005M (S) 9-12V stereo decoder FM for above	7.50
1062 12V stereo decoder, general purpose	6.50


Preamplifiers

Sinclair Stereo 60 Preamplifier	6.75
E1500 Cart. Tape/Mic inputs	2.85
E1310 Stereo 3-30mV mf cart	4.75
FF3 Stereo 3mV tape head	4.95
3042 Stereo 5-20mV Mag. cart mains	5.95
EQ25 Mono 3-250mV Tape/Cart./Play	1.95

HENRY'S HOME ENTERTAINMENT CENTRES

London:
354-6 Edgware Rd., W2 (01-402 5854), 376-8 Edgware Rd., W2 (01-723 0818), 372 Edgware Rd., W2 (01-402 8140), 120 Shaftesbury Ave., W1 (01-437 9692), 230 Tottenham Court Rd., W1 (01-580 1785), 144 Burnt Oak B way, Burnt Oak, Edgware (01-952 7402), 190/4 Station Rd., Harrow, Middx. (01-863 7788).
Out of Town:
256 Banbury Rd., Summertown, Oxford ((0865) 53072)
55 Gloucester Rd., Bristol 7 ((0272) 45791).

EXCLUSIVE 5 WATT IC AMPLIFIERS

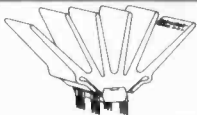

Special purchase 5W output, 8-16 ohm load, 30V max. d.c. operation complete with data. Price £1-50 each or 2 for £2-85. Printed Circuit Panels 50p.

UHF TV TUNERS

625 line receiver UHF transistorised tuners FM U.K. operation. Brand new IP & P. 25p each). TYPE C variable tuning £2-50. TYPE B 4-button push-button (adjustable) £3-50.

STC AND ITT MINIATURE RELAYS

150R 6V 2 p.c.o.	BRAND NEW 60p P. & P. 15p
180R 6/12V 2 p.c.o.	
185R 12V 2 p.c.o.	
1250R 12 55V 2 p.c.o.	
1700R 18/24V 2 p.c.o.	
1800R 24V 4 p.c.o.	
2500R 18/24V 2 p.c.o.	
4000R 24V 2 p.c.o.	

INVERTOR KITS

15W	£5-20 P. & P. 30p
40W	£6-80 P. & P. 40p

PP9 BATTERY ELIMINATOR

Complete Kits of Parts including P/C Boards £1-95 Complete Kit.

GRAVINER INFRA RED DETECTOR DESIGNED FOR HEAT OR LIGHT DETECTOR. CONTAINING 931A PHOTO MULTIPLIER AND GK45 AND NETWORK, £3-50.

AMTRON KITS AVAILABLE EX-STOCK. SEND FOR FREE LISTS.

JOSTY KITS AVAILABLE EX-STOCK. SEND FOR FREE LISTS.

40kHz ULTRA-SONICS TRANSDUCERS £5-90. P. & P. 25p.

TAA 960 40kHz AMP. £1-75. P. & P. 15p.

SUPPLIERS OF ELECTRONICS FOR OVER 30 YEARS. 8% VAT TO BE ADDED TO ALL ORDERS. VAT—UK ONLY.

Henry's RADIO

EDGWARE ROAD, W2

Electronic Centres
404-406 Electronic Components & Equipment 01-402 8381
309 PA-Disco-Lighting High Power Sound 01-723 6963
303 Special offers and bargains store
All mail to 303 Edgware Road, London W2 1BW
Prices correct at time of preparation. Subject to change without notice. E. & O. E.

Hi Fi and Electronics Centres Open 9 am - 6 pm