

PRACTICAL

ELECTRONICS

APRIL 1982

75p


Ultrasonic Vision System



Stereo Cassette Deck

FREE! 8 PAGE SUPPLEMENT...
6 SIMPLE PROJECTS

PRECISION - by POWERTRAN

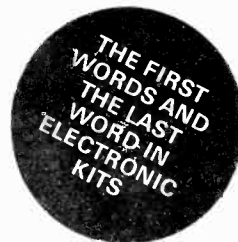

For more than eleven years Powertran have been designing and manufacturing the finest quality electronic kits. All of our now considerable range have featured in the electronics press and literally thousands have been bought and built by contractors in the UK and World-wide.

Our philosophy is always the same – we offer ingenuity and originality in the construction phase by using only top class designers. We offer machines with power, versatility and performance – capability fully equal to their factory built rivals. We offer only the highest quality materials and components throughout to ensure years of useful and reliable service, we offer clear comprehensive and easy to follow construction manuals to place our kits within the scope of the careful first time builder as well as the dedicated enthusiast.

Our hallmark of success lies in the number of our clients who have built our whole range – many assembling several units for others to use often on the professional music scene.

We believe in taking every care throughout – months spent checking and testing the design and development. Vigorous checking of every component, constant pre-despatch quality control, careful packaging . . . even door to door delivery by Securicor!

We are naturally very proud of our Transcendent range of synthesizers designed by Tim Orr and regularly featured in ETI. They represent the best in constructional interest and in musical performance.

TRANSCENDENT POLYSYNTH – A four octave polyphonic synthesiser with outstanding design characteristics and versatility and performance to match.
Complete kit £275.00 plus VAT (single voice).
Extra voice (up to three more) £42.00 plus VAT.


EXPANDER – A new matching 4 voice expander to team up with your polysynth for even a greater range and capability.
Complete kit £249.00 plus VAT.

TRANSCENDENT DPX – Offers a five octave keyboard with power to match. Two audio outputs (can be used simultaneously) to give harpsichord and piano/honkytonk or reed with strings/brass and both are fully polyphonic. Other features include switchable touch sensitivity and a chorus ensemble unit with strong/mild effect switching. An advanced design made simple with our clearly laid out instruction manual.
Complete kit £295.00 plus VAT.

TRANSCENDENT 2000 – Although only a 3 octave keyboard the '2000' features the same design ingenuity, careful engineering and quality components of its larger brethren. The kit is well within the scope of the first time builder – buy it, build it . . . play it! You will know you have made the right choice.
Complete kit £165.00 plus VAT.

1024 COMPOSER – Come right up to the minute with this new design. It will control your synthesiser with a sequence of up to 1024 notes – or an equal selection of shorter sequences. The Composer is mains powered with automatically charged battery to preserve your programme after switch-off.
Complete kit £85.00 plus VAT.

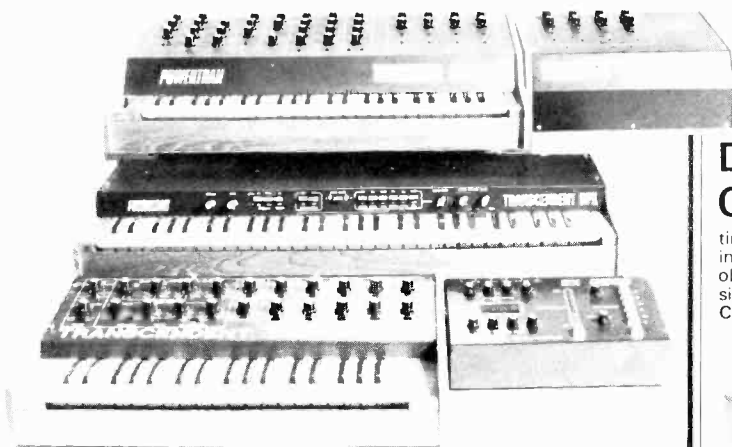DEMONSTRATION TAPE – 30 minute demonstration tape of all three synthesizers now available. £2.00



STUDIO QUALITY

DIGITAL DELAY LINE Our latest kit!

With its ability to give delay times from 0.3 to up to 1600msecs, many powerful effects including phasing, flanging, ADT, chorus, echo and vibrato are obtained. The basic kit is extended in 400ms steps up to 1.6 sec simply by adding more parts to the P.C.B.
Compare with units costing over £1,000!



Complete kit £13.00 plus VAT (400ms delay). Parts for extra 400ms delay £9.50 plus VAT.

... Quite simply the best way to
make music



WORLD LEADERS IN ELECTRONIC KITS

PRICE STABILITY: Order with confidence irrespective of any price changes we will honour all prices in this advertisement until the end of the month following the month of publication of this issue. (Errors and VAT rate changes excluded)
EXPORT ORDERS: No VAT. Postage charged at actual cost plus £1 handling and documentation.
U.K. ORDERS: Subject to 15% surcharge for VAT. No charge is made for carriage, or at current rate if changed. Cheques, Access, Barclaycard accepted.
SECURICOR DELIVERY: For this optional service (U.K. mainland only) add £2.50 (VAT inclusive) per kit. FREE ON ORDERS OVER £100.
SALES COUNTER: If you prefer to collect kit from the factory, call at Sales Counter. Open 9a.m. - 12 noon, 1-4.30p.m. Monday-Thursday.

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS SP10 3WN (0264) 64455.

Order by phone
(0264) 64455
Simply telephone us with your order and
quote Your Access or Barclaycard number
40 page catalogue free – contains full
details of all our kits.

PRACTICAL ELECTRONICS

VOLUME 18

No. 4

APRIL 1982

CONSTRUCTIONAL PROJECTS

STEREO CASSETTE DECK Part 1	18
The latest separate for the PE Quasar Stereo System	
ULTRASONIC VISION SYSTEM Part 1 <i>by Jeremy Bentham and Fred Bentham</i>	24
A radar style outlook for your computer	
ENLARGER TIMER <i>by Tom Gaskell BA</i>	32
Photographic aid for the darkroom	
MEDIUM RESOLUTION GRAPHICS <i>by N. A. Climpson</i>	41
User definable 4-times resolution for UK101	
PE ROBOTS Part 6 <i>by Richard Becker, Tim Orr and Richard Monkhouse</i>	46
Conclusion—software, construction and wiring	
TELETRIC ELECTRICITY COST MONITOR Part 2 <i>by Stephen Day BSc Eng MIEE</i>	58
Microprocessor circuitry and software; constructional details	

GENERAL FEATURES

SEMICONDUCTOR UPDATE <i>by R. W. Coles</i>	39
Featuring MC146818 TDS 934 6600	
STRICTLY INSTRUMENTAL <i>by K. Lenton-Smith</i>	52
History of an organ pioneer	
MICROPROMPT	54
Including a 48 x 32 video conversion for UK101	
INGENUITY UNLIMITED	61
Overload cutout for thyristor speed control—Button selector—Switch de-bounce—Quality mic amplifier—9V power supply—Octave bank for VCOs—Sound-to-light converter	

NEWS AND COMMENT

EDITORIAL	13
NEWS & MARKET PLACE	14
Including Countdown and Points Arising	
THE MACROCHIP	28
Hot news of a piece of innovative technology	
INDUSTRY NOTEBOOK <i>by Nexus</i>	30
Going off the rails?	
SPECIAL OFFER—LOUDSPEAKERS	31
Hi-fi speakers at a very low price	
BAZAAR	45
Buy, sell and swap service for readers	
SPECIAL OFFER—CASSETTES	51
Starting a regular bargain offer on high quality cassettes	
READOUT	53
Readers' criticism . . . and praise	
SPACEWATCH <i>by Frank W. Hyde</i>	66
PATENTS REVIEW	68

SPECIAL SUPPLEMENT

FREE TRANSISTOR PROJECTS	between pages 40 & 41
Logic probe, Light Delay Unit, Car Lights Reminder, Battery Monitor, Soil Moisture Meter, Snap Indicator	
OUR MAY ISSUE WILL BE ON SALE THURSDAY, 8th APRIL 1982	
(for details of contents see page 23)	

© IPC Magazines Limited 1982. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.


SPEAKERS 8Ω 0.3W, 2", 2.25", 2.5", 3" 80p 0.3W, 2.5" 40Q; 64Q 80p	DIODES AA119 15 BA100 15 BY100 24 BY126 12 BY127 12 CR303 250 OA9 40 OA7 12 OA79 15 OA85 15 OA90 8 OA91 8 OA95 8 OA200 8 OA202 8 1N414 4 1N916 5 1N4001/2 5 1N4003 6 1N4004/5 6 1N4006/7 7 1N4148 4 1N5401 15 1N5404 16 1N5406 17 1N5408 19 1S44 9 1S921 9 6A100V 40 6A400V 50 6A800V 65	BRIDGE RECTIFIERS (plastic case) 1A/50V 20 1A/100V 22 1A/200V 23 1A/500V 34 2A/50V 35 2A/100V 36 2A/200V 40 2A/400V 46 2A/600V 65 2A/100V 69 6A/600V 125 10A/200V 215 10A/600V 350 25A/200V 240 25A/600V 395	ZENERS Range 2V7 to 39V 400mW 5p each Range 3V3 to 33V 1.3W 15p each MVA1M2 185 MVA1M15 158 BA102 30 BB105B 40 BB106 40	VARIACAPS MVA1M2 185 MVA1M15 158 BA102 30 BB105B 40 BB106 40	Noise Diode Z5J 195
--	--	---	---	--	-------------------------------

OPTO ELECTRONICS LEDs including Clips TIL209 Red 125" 13 TIL211 Green 125" 18 TIL212 Yellow 18 TIL220 2" Red 15 0.2" Yel. Grn. Amber Red, Green and Yellow Rectangular LEDs. 29 Triangular LEDs R&G 18 0.2" Flashing LED Red 55 0.2" Bi colour LEDs Green/Yellow 65 2A/50V 35 Green/Yellow 80 Red/Green/Yellow 85 0.2" Red High Bright 59 LD271 6" C Cathod. 46 TIL32 Infra Red (emit) 52 SFH205 (detector) 91 TIL78 (detector) 54 TIL100 90	0.5" LIQUID CRYSTAL DISPLAYS 3 1/2 digit 550 4 digit 650 6 digit 750 NE555 1+ 50+ 2114L-3 87p 80p 2114L-2 87p 80p 2708 175p 160p 2532 450p 375p 2716 210p 195p 2732 400p 375p 4116 75p 68p 6116 580p 550p 6522 350p 320p 7805 1A/5V 45p 35p	OPTO SWITCH Reflective 170 TIL139 170 Slotted similar to RS 186	ALUM. BOXES 4x2 1/2" x 2" 85 4x2 1/2" x 1" 103 4x4x2 1" 120 5x4x2 1" 105 5x2 1/2" x 1" 90 5x4 1/2" x 2" 99 5x4x2 1/2" 120 6x4x2 1/2" 120 6x4x3 1/2" 150 7x5x3 1/2" 180 8x6x3 1/2" 210 10x4 1/2" x 3" 240 10x7x3 1/2" 275 12x5x3 1/2" 260 12x8x3 1/2" 295	FERRIC CHLORIDE 1 lb bag Anhydrous 195p + 50p p&p	DALO ETC RESIST Pen + Spare tip 90p
---	--	---	--	---	---

SPECIAL OFFER

CUSTOMER: How can Watford sell full spec devices so cheaply? WATFORD: It's simple. By bulk buying (direct from manufacturers where possible), low overheads and smaller margins which give us an edge over our competitors.

ANTEX Soldering Irons

Buy with 

Just phone your order through, we do the rest.

GAS & SMOKE DETECTORS TGS812 & 813 Sockets 575	ULTRASONIC TRANSDUCERS 40KHz Transmitter & Receiver 395p/pair
--	---

DIL SOCKETS (TEXAS) 8 pin 8p 14 pin 10p 16 pin 10p 18 pin 16p 20 pin 22p 22 pin 25p 24 pin 25p 28 pin 28p 36 pin 38p 40 pin 99p	DIL SOCKETS (Headers) 10 way 33 20 way 40 24 way 50 40 way 70	RIBBON CABLE 2x5 way 90p 2x8 way 130p 2x10 way 145p 2x13 way 175p 2x17 way 205p 2x20 way 220p 2x25 way 235p 2x60 way ---	Plugs DIN41618 31 way 180p DIN41612 2x32 way 270p DIN41612 3x32 way 370p	Socket 60p 70p 80p 95p 110p 125p 150p 200p	PCB Plugs 19p 70p 80p 95p 110p 125p 150p 200p	PCB Plug 65p 78p 92p 110p 135p 150p 175p 220p
--	--	---	--	---	--	--

WATFORD'S Ultimate Monitor IC.

A 4K Monitor Chip specially designed to produce the best from your: Superboard Series I & II, Enhanced Superboard & UK101. As reviewed by Dr. A. A. Berk In Practical Electronics, June 1981.
Price only £15.95 + 50p P&P.

EDGE CONNECTORS

JUMPER LEADS Ribbon Cable Assembly
Length 14pin 16pin 24pin 40pin
Single Ended DIP (Header) Lead 24" 145p 240p 380p
Double Ended DIP (Header) Lead 6" 185p 205p 300p 465p
12" 198p 215p 315p 490p
24" 210p 235p 345p 540p
36" 230p 250p 375p 595p
Single Ended Socket Lead 24" 15p 210p 265p 300p
Double Ended Socket Lead 24" 290p 385p 489p 540p

TRANSFORMERS (mains Prim. 220-240V)
6.0-6V 100mA, 9.0-9V 75mA, 12.0-12V 75mA 98p
6VA type: 6V-5A 6V-5A; 9V-4A 9V-4A; 12V-3A 12V-3A; 15V-2.5A 15V-2.5A 220p
12VA: 4.5-1.3A 4.5V-1.3A; 6V-1.2 6V-1.2A 12V-5A 12V-5A 295p (30p p&p)
24VA: 6V-1.5A 6V-1.5A; 9V-1.2A 9V-1.2A; 12V-1A 12V-1A; 15-8A 15-8A; 20V-6A 20V-6A 330p (44p p&p)
50VA: 2x6V-4A; 2x9V-2.5A; 2x12V-2A; 2x15V-1.5A; 2x20V-1.2A; 2x25V-2A; 2x30V-0.8A 440p (60p p&p)
100VA: 2x12V-4A; 2x15V-3A; 2x20V-2.5A; 2x30V-1.5A; 2x40V-1.25A; 2x50V-1A 920p (60p p&p)

COMPUTER CORNER

- VIC 20 MICROCOMPUTER.** Connects directly to a colour TV. 5K RAM expandable to 32K PET type graphics. **£165**
- CASSETTE DECK** for VIC20 including a free 6 programme Cassette. **£34**
- EPSON MX SERIES PRINTERS:** Full range available. Please phone for prices.
- SEIKOSHA GP80A** - Unihammer Printer, gives normal and double width characters as well as dot resolution graphics 8" Tractor feed. Parallel Interface standard. **£195**
- SOFTY-2.** As reviewed in PE September 1981. The complete microprocessor development system for Engineers & Beginners. New powerful instruction. Accepts any 24 pin 5V single rail EPROM. Supplied fully built, tested & enclosed in a black ABS case. Price incl. encapsulated plug in power supply. **£169**
- VIDEO MONITOR 9"** fully cased. B&W. Fully guaranteed. Excellent value for money at only **£69**
- TEX EPROM ERASER.** Erases up to 32 ICs in 15-30 min. **£33**
- TEX EPROM ERASER** with integral 30 min. Electronic timer **£45**
- Spare UV lamp bulbs** **£9**
- 5V/5A PSU** Ready built and tested **£25**
- Attractive Beige/Brown ABS CASE** for Superboard/UK101 or Home Brew **£26**
- Extra 4K of RAM** (8 off 2114L-300nS) **£7**
- Space Invaders** for Superboard **£6**
- Full ASC11** coded keyboard type '756' **£39**
- 4 x 4 matrix keypad** (reed switch assembly) **£4**
- C12 Cassettes** in Library Cases **40p**
- 8 1/2" Fan fold paper** (500 sheets) (no VAT) **£6**
- 9 1/2" Fan fold paper** (500 sheets) (no VAT) **£6**
- Teletprinter Roll** (no VAT) **£3.50**

TRIACS 3A/100V 48 3A/400V 56 3A/800V 85 8A/100V 60 8A/400V 69 8A/800V 115 12A/100V 78 12A/400V 82 12A/800V 135 16A/100V 103 16A/400V 118 16A/800V 220 25A/400V 185 25A/800V 295 25A/1000V 480 30A/400V 225 T2800D 120	COPPER CLAD BOARDS Fibre Single-sided 9.5"x8.5" 95p Glass Double-sided 9.5"x8.5" 95p 6"x6" 90p 6"x12" 150p	VEROBOARDS 0.1" Clad Plain 150 DIP Board 420 Vero Strip 330 S100 Board £14 VO Board 150 DIP Board 420 Vero Strip 330 S100 Board £14 PROTO-DECS Veroblock 375 S-Dec 350 Eurobreadboard 695 Spot Face Cutter 118p Pin Insertion Tool 162p	VERO WIRING PEN and Spool Spare Wire (Spool) 75p; Combs 8p ea.	VOLTAGE REGULATORS 1A T02 45p 5V 7805 145p 7905 220p 12V 7812 145p 7912 220p 15V 7815 145p 7915 220p 18V 7818 150p 1A T0220 Plastic Casing 55p 5V 7805 50p 7905 55p 12V 7812 50p 7912 55p 15V 7815 50p 7915 55p 18V 7818 50p 7918 55p 24V 7824 50p 100mA T092 Plastic Casing 80p 5V 78L05 30p 79L05 80p 8V 78L82 30p 12V 78L12 30p 79L12 80p 15V 78L15 30p 79L15 80p LM300H 170 LM309K 135 LM304M 140 LM317H 280 LM305H 140 LM317K 350 78H05 5V/5A 550p LM317P 99 78HG+5 to LM323K 500 +24V 5A 599p LM326N 240 79HG -2.25V to LM723 35 -24V 5A 785p TBA625B 75	SWITCHES SLIDE 250V TOGGLE 2A 250V 1A DPDT 14 SPST 33 1A DPDT C/OFF 15 DPDT 44 1A DP on/on/off 40 4 pole on off 54 PUSH BUTTON Spring loaded Latching or Momentary 6A SPST on/off 99 DPDT c/dover 145 SPDT c/off 84 DPDT c/dover 145 SPDT Biased 105 DPDT 6 tags 75 Non Locking DPDT C/OFF 88 Push to make 15p DPDT Biased 15p Push break 25p 3 pole c/dover 205 ROCKER: 5A, 250V, SPST 28p ROCKER: (white) 10A 250V SPDT 38p ROCKER: With neon lights red when on. 10A 250V DPST 85p ROCKER: (White) 10A/250V DPDT 72p ROTARY: Make your own Multiway Switch. Shafting Assembly accommodates up to 6 wafers 90p Break before make Wafers. Silver contacts. 1 pole/12 way; 2 pole/6 way; 3 pole/4 way; 4 pole/3 way; 6 pole/2 way 65p Mains DPST Switch to fit 45p Screen & Spacers 6p ROTARY: (Adjustable Stop Type) 1 pole/2 to 12 way, 2p/2 to 6 way, 3 pole/2 to 4 way, 4 pole/2 to 3 way 45p ROTARY: Mains 250V AC, 4 Amp 56p
---	---	---	---	---	--

WATFORD'S UNIVERSAL MICRO EXPANSION SYSTEM

Designed by Watford Electronics, this extremely versatile and economical Expansion System as published in E.T.I., starting from Dec., 81 issue, offers a low cost flexible expansion facility for ZX81, UK101, SUPERBOARD, ACORN ATOM, PET, TANGERINE, TRS80, VIDEO GENIE, VIC 20, ECT.


The Motherboard (Interfaces with the Computer) has capacity to accept up to five daughter cards and can be paralleled for even more daughter cards. All PCBs are of Computer grade finish and are supplied in Kit form.

Just look at the expansion possibilities:

- MOTHERBOARD** - Accepts up to five Daughter Cards **Full Kit: £36.50**
- SOUND CARD** - Utilising up to three AY-3-8910 Sound chips. (one supplied with every Kit) **Full Kit: £24.95**
- PIO CARD** - Using two 6520 PIA chips, this Board offers Centronics parallel printer driver, digital to analogue converter and a host of other out-put facilities. **Full Kit: £19.95**
- PROM PROGRAMMER** - This simple but extremely useful card can blow 2716 or 2732 single rail EPROMS. **Full Kit: £25.95**
- PROM CARD** - P.C.B. cards for housing four 2716 or two 2732 EPROMS. **Full Kit: £11.95**
(4x2716) **Full Kit: £11.75**
(2x2732)
- RAM CARD** - 8K RAM card. Accepts 16x2114 RAMs. The Board is supplied fully populated. **Full Kit: £28.50**
(N.B. PCBs may be bought separately)

WATFORD ELECTRONICS
Tel. (0923) 40588 Telex. 8956095

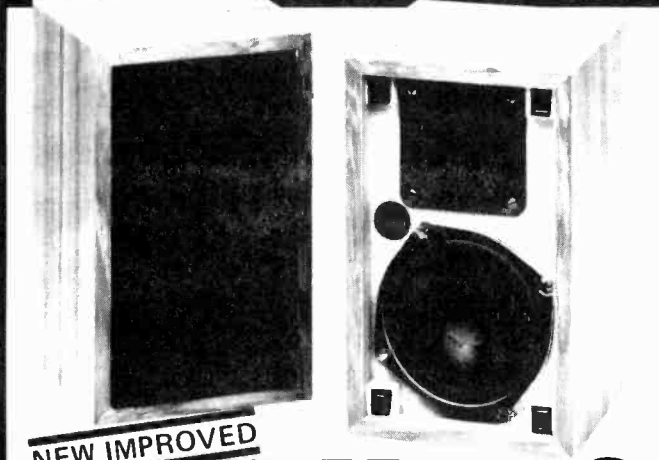Has seven years of success gone to our heads?



NEW IMPROVED

MINIMAX 2

With the Minimax II, Videotone revolutionised the market by establishing an opening for small, high quality speakers. Natural evolution has brought about the new Minimax 2, retaining all the qualities of clarity and sensitivity. This ideal combination of size and performance is a proven success, acclaimed by the press and public for seven years.

POPULAR HI-FI

"Switching to the Minimaxes' from any of the others produced an open and natural sound as though something had been taken away. It had, the colouration had gone." Comparative test **OCTOBER 1975**.

HI-FI ANSWERS

Their modest appearance and price disguise their startling abilities. Never have we heard such a small speaker sound so big!" **JANUARY 1975**.

PRACTICAL HI-FI & Audio

"The depth, clarity and openness of sound produced is quite astonishing". **JUNE '75**

WHAT HI-FI

"... the ability of the Mini-

max to take a lot of power and still sound good could be decisive" - Comparative test, **APRIL 1977**.

PRACTICAL HI-FI

The little Videotone scored highly for such a small inexpensive loudspeaker". **JANUARY 1981**.

Specification:

Recommended amplifier power: 10 to 40 watts rms into 8 ohms.
 Frequency Response: 80Hz - 20KHz \pm 5dB.
 Finish: natural teak, veneer with black frets.
 Size: 10 7/8" high, 6 3/4" wide, 7 1/2" deep.
 Weight: 4.1 Kgs (9 lbs) each.
ONLY £69.95 A PAIR

- We welcome callers to our South London Showroom for demonstrations.
- Enquiries and information phone: 01-690 8511, Ex. 32.
- All products are only available direct or from selected authorised dealers throughout the U.K.

VIDEOTONE

98 CROFTON PARK ROAD
LONDON SE4.

Send for our free brochure and details of outlets in the U.K.

Post to: Videotone, Crofton Park Road, London SE4. PE4

NAME _____

ADDRESS _____

TRAIN FOR SUCCESS

in Radio, Television & Electronics

ICS have helped thousands of ambitious people to move up into higher paid more secure jobs in the field of electronics - now it can be your turn. Whether you are a newcomer to the field or already working in the industry. ICS can provide you with the specialised training so essential to success.

Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful, is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed."

City and Guilds Certificates

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Telecommunications Technicians
 Radio, T.V. Electronics Technicians
 Radio Amateurs
 Electrical Installation Work

Diploma Courses

Colour T.V. Servicing
 CCTV Engineering
 Electronic Engineering & Maintenance
 Computer Engineering and Programming
 Radio, T.V. and Audio, Engineering & Servicing
 Electrical Engineering, Installations & Contracting

Other Career Courses

A wide range of other technical and professional courses are available including GCE.

FREE BOOK

Post this coupon or 'phone today for free Electronics careers guide.

Name _____

Address _____

Age _____

ICS

To ICS, Dept 273T, Intertext House,
 London SW8 4UJ
 or telephone 01-622 9911 (all hours)

KITS, COMPONENTS MICROS & PARTS

THE GARAGE DOOR AT YOUR COMMAND

At last, a kit to enable your motorised garage door to be opened without setting foot from your car, and also enable the lights in your garage and drive to be switched on or off at the touch of a button. A momentary relay output operating the door control circuits (relay closes only while a valid code is transmitted) is indicated by LED. It features two latched outputs with common reset for switching 240V a.c. mains loads via remote opto-isolated solid state switches (1kW maximum). A hand-held transmitter for 9V PP3 battery operation, auto-isolated 4 function keys: Open/Close, on 1, on 2, Off, giving a range of approximately 40 feet is included. As a general purpose remote control in the home for switching lights, television and other appliances. This unit is ideal for the aged or disabled.

ALL PRICES EXCLUDE VAT

£23.75

DISCO LIGHTING KITS

DL1000K
This value-for-money kit features a bi-directional sequence, speed of frequency and frequency of direction change, being variable by means of potentiometers and incorporates a master dimming control. Only £14.60

DL21000K
A lower cost version of the above, featuring unidirectional channel sequence with speed variable by means of a pre-set pot. Outputs switched only at mains zero crossing points to reduce radio interference to a minimum. Only £8.00

Optional opto input DLA1 60p
Allowing audio ("beat")—light response.



DO YOU LONG TO HEAR YOUR DOORBELL RING?

Our latest kit gives you a pleasing three-note harmonically related tone sequence (not a microprocessor controlled buzz or the same old ding dong) at a touch of a button. This kit, based on a new integrated circuit, is supplied complete with a printed circuit board, loudspeaker and drilled box and requires only 9V battery and push button common to most households. It may also be switched by logic in such applications as car alarms, clocks, toys, P.A. systems, etc. The unit produces a 150mW output and draws less than one 1uA from a PP3 battery when the tone ceases. Supplied complete with circuit and assembly instructions.

IDEAL PROJECT FOR BEGINNERS— ONLY £5.00



DVM/ULTRA SENSITIVE THERMOMETER KIT


This new design is based on the ICL7126 (a lower power version of the ICL7106 chip) and a 3 1/2 digit liquid crystal display. This kit will form the basis of a digital multimeter (only a few additional resistors and switches are required—details supplied), or a sensitive digital thermometer (-50°C to +150°C) reading to 0.1°C. The basic kit has a sensitivity of 200mV for a full scale reading, automatic polarity indication and an ultra low power requirement—giving a 2 year typical battery life from a standard 9V PP3 when used 8 hours a day, 7 days a week. Price £15.50



TRIACS

400V Plastic Case (Texas) 3A TIC206D 49p
8A TIC226D 58p
12A TIC236D 85p
16A TIC246D 96p
25A TIC263D 190p

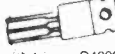6A with Trigger O4006LT 85p
8A isolated tab TXAL228B 65p
Diac 18p
Opto isolated triac MOC3020 0 6A/400V 110p



MEMORIES AND MICROS

2114	95	6810	4.80
2708	2.25	6821P	1.25
2716	2.45	6850P	1.50
		6852P	2.55

PRICES SLASHED

8035L	5.50
M6802P(CPU)	3.85
Z80ACPU	3.30
Z80A CTC	2.90
Z80APID	2.90

74 LS TTL

LS00	12	LS14	48	LS42	40	LS93	37
LS01	12	LS15	15	LS47	42	LS95	48
LS02	13	LS20	14	LS51	15	LS107	24
LS03	13	LS21	15	LS54	15	LS109	24
LS04	14	LS22	15	LS55	15	LS112	24
LS05	15	LS26	18	LS73	20	LS113	24
LS08	15	LS27	15	LS74	18	LS114	24
LS09	15	LS30	14	LS75	27	LS123	51
LS10	14	LS32	15	LS76	21	LS126	29
LS11	15	LS37	17	LS85	64	LS132	44
LS12	15	LS38	16	LS86	18	LS160	40
LS13	27	LS40	14	LS90	32	LS161	40

CMOS

4000	14	4026	1.05	4093	45
4001	14	4027	40	4501	24
4002	14	4028	50	4511	85
4007	14	4040	68	4514	180
4011	15	4049	30		
4012	17	4050	30		
4013	35	4050	90		
4015	70	4059	18		
4016	30	4070	24		
4017	65	4071	22		
4019	38	4077	24		
4023	22	4081	22		
4025	18				



THE KEY TO YOUR SECURITY IS IN OUR LOCK

If the thought of car thieves, house breakers or people tampering with your electrical and electronic equipment upsets you, have just the kit for you. Our ELECTRONIC LOCK KIT includes a 10-way keyboard and a special IC which provides a 750mA output to drive a solenoid or relay (not supplied) when four keys are depressed in the correct sequence. This gives over 5,000 possible combinations! The sequence is prewired and may be easily changed by means of a small plug and socket. A "SAVE" function is also available: enabling the open code to be stored (especially useful in a car when it is left in a garage for servicing as the open code need not be disclosed). Size: 7x6x3 cms. Power Consumption is 40uA at 5V to 15V d.c.

At only £10.50 + VAT, it will make a smaller hole in your pocket than a bunch of keys! Electric Lock Mechanism £12.50
Suitable for use with existing door locks and above electronic lock kit.

THE MULTI-PURPOSE TIMER HAS ARRIVED

Now you can run your central heating, lighting, hi-fi system and lots more with just one programmable timer. At your selection it is designed to control four mains outputs independently, switching on and off at pre-set times over a 7 day cycle, e.g. to control your central heating (including different switching times for weekends), just connect it to your system programme and set it and forget it—the clock will do the rest.

FEATURES INCLUDE—

- 0.5" LED 12 hour display
- Day of week, am/pm and output status indicators.
- 4 zero voltage switched mains outputs
- 50/60Hz mains operation
- Battery backup saves stored programmes and continues time keeping during power failures. (Battery not supplied)
- Display blanking during power failure to conserve battery power
- 18 programme time sets.
- Powerful "Everyday" function enabling output to switch every day but use only one time set
- Useful "sleep" function—turns on output for one hour
- Direct switch control enabling output to be turned on immediately or after a specified time interval
- 20 function keypad for programme entry
- Programme verification at the touch of a button


THERE HAS NEVER BEEN A CLOCK CAPABLE OF SO MUCH AT SUCH A LOW PRICE— ONLY £45.00
(including components, assembly and programme instructions in an attractive case)



THE PERFECT AID FOR "LAZYITIS"

Our Lamp Dimmer Kit with INFRARED REMOTE CONTROL will enable you to switch the lights on or off, and set the brightness, at a push of a button without leaving your armchair, water-bed, etc. Not only will you save time but it has also been estimated that the savings in shoe leather and carpet wear alone would pay for this unit in approximately 1 3697 years or more!

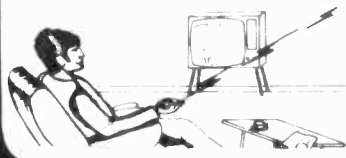This unit has considerable practical uses, especially for the old, infirm and disabled. It works like a conventional dimmer, enabling you to switch the lights on or off, or to dim them to whatever brightness you require, by touch or using the hand-held infra red transmitter. When assembled, it fits into a plaster depth box to replace your conventional switch or dimmer with no rewiring.



TDR300K Dimmer Kit £14.30
MK6 Transmitter Kit £4.20
We also still sell our highly popular TD300K Touch Dimmer Kit at £7.00 and the LD300K rotary controlled Dimmer Kit at only £3.50
All kits contain all necessary components and full instructions. You only need a soldering iron and cutters.

24 HOUR CLOCK/APPLIANCE TIMER KIT

Switches any appliance up to 1kW on and off at present times once per day. Kit contains AY-5-1230 IC, 0.5" LED display, mains supply, display drivers, switches, LEDs, triacs, PCBs and full instructions.

CT1000K Basic Kit £14.90
CT1000K with white box (56/131 x 71mm) £17.40
(Ready Built) £22.50

Add 50p postage & packing + 15% VAT to total.
Overseas Customers
Add £1.50 (Europe), £4.00 (elsewhere) for p&p
Send S.A.E. for further STOCK DETAILS
Goods by return subject to availability.

OPEN 9am to 5pm (Mon to Fri)
10am to 4pm (Sat)



FAST SERVICE - TOP QUALITY - LOW LOW PRICES

No circuit is complete without a call to

TELEVISION ELECTRONICS

11 Boston Road
London W7 3SJ



Telephone: 01-579 9794/2842



Sinclair ZX81 Personal Computer the heart of a system that grows with you.

1980 saw a genuine breakthrough – the Sinclair ZX80, world's first complete personal computer for under £100. Not surprisingly, over 50,000 were sold.

In March 1981, the Sinclair lead increased dramatically. For just £69.95 the Sinclair ZX81 offers even more advanced facilities at an even lower price. Initially, even we were surprised by the demand – over 50,000 in the first 3 months!

Today, the Sinclair ZX81 is the heart of a computer system. You can add 16-times more memory with the ZX RAM pack. The ZX Printer offers an unbeatable combination of performance and price. And the ZX Software library is growing every day.

Lower price: higher capability

With the ZX81, it's still very simple to teach yourself computing, but the ZX81 packs even greater working capability than the ZX80.

It uses the same micro-processor, but incorporates a new, more powerful 8K BASIC ROM – the 'trained intelligence' of the computer. This chip works in decimals, handles logs and trig, allows you to plot graphs, and builds up animated displays.

And the ZX81 incorporates other operation refinements – the facility to load and save named programs on cassette, for example, and to drive the new ZX Printer.



Every ZX81 comes with a comprehensive, specially-written manual – a complete course in BASIC programming, from first principles to complex programs

Kit: £49.⁹⁵

Higher specification, lower price – how's it done?

Quite simply, by design. The ZX80 reduced the chips in a working computer from 40 or so, to 21. The ZX81 reduces the 21 to 4!

The secret lies in a totally new master chip. Designed by Sinclair and custom-built in Britain, this unique chip replaces 18 chips from the ZX80!

New, improved specification

- Z80A micro-processor – new faster version of the famous Z80 chip, widely recognised as the best ever made.
- Unique 'one-touch' key word entry: the ZX81 eliminates a great deal of tiresome typing. Key words (RUN, LIST, PRINT, etc.) have their own single-key entry.
- Unique syntax-check and report codes identify programming errors immediately.
- Full range of mathematical and scientific functions accurate to eight decimal places.
- Graph-drawing and animated-display facilities.
- Multi-dimensional string and numerical arrays.
- Up to 26 FOR/NEXT loops.
- Randomise function – useful for games as well as serious applications.
- Cassette LOAD and SAVE with named programs.
- 1K-byte RAM expandable to 16K bytes with Sinclair RAM pack.
- Able to drive the new Sinclair printer.
- Advanced 4-chip design: micro-processor, ROM, RAM, plus master chip – unique, custom-built chip replacing 18 ZX80 chips.



Built: £69.⁹⁵

Kit or built – it's up to you!

You'll be surprised how easy the ZX81 kit is to build: just four chips to assemble (plus, of course the other discrete components) – a few hours' work with a fine-tipped soldering iron. And you may already have a suitable mains adaptor – 600 mA at 9 V DC nominal unregulated (supplied with built version).

Kit and built versions come complete with all leads to connect to your TV (colour or black and white) and cassette recorder.



uter-



Available now- the ZX Printer for only £49.⁹⁵

Designed exclusively for use with the ZX81 (and ZX80 with 8K BASIC ROM), the printer offers full alpha-numerics and highly sophisticated graphics.

A special feature is COPY, which prints out exactly what is on the whole TV screen without the need for further instructions.

At last you can have a hard copy of your program listings – particularly

useful when writing or editing programs.

And of course you can print out your results for permanent records or sending to a friend.

Printing speed is 50 characters per second, with 32 characters per line and 9 lines per vertical inch.

The ZX Printer connects to the rear of your computer – using a stackable connector so you can plug in a RAM pack as well. A roll of paper (65 ft long x 4 in wide) is supplied, along with full instructions.

16K-byte RAM pack for massive add-on memory.

Designed as a complete module to fit your Sinclair ZX80 or ZX81, the RAM pack simply plugs into the existing expansion port at the rear of the computer to multiply your data/program storage by 16!

Use it for long and complex programs or as a personal database. Yet it costs as little as half the price of competitive additional memory.

With the RAM pack, you can also run some of the more sophisticated ZX Software – the Business & Household management systems for example.

How to order your ZX81

BY PHONE – Access, Barclaycard or Trustcard holders can call 01-200 0200 for personal attention 24 hours a day, every day.

BY FREEPOST – use the no-stamp-needed coupon below. You can pay

by cheque, postal order, Access, Barclaycard or Trustcard.

EITHER WAY – please allow up to 28 days for delivery. And there's a 14-day money-back option. We want you to be satisfied beyond doubt – and we have no doubt that you will be.

To: Sinclair Research Ltd, FREEPOST, Camberley, Surrey, GU15 3BR.

Order

Qty	Item	Code	Item price £	Total £
	Sinclair ZX81 Personal Computer kit(s). Price includes ZX81 BASIC manual, excludes mains adaptor.	12	49.95	
	Ready-assembled Sinclair ZX81 Personal Computer(s). Price includes ZX81 BASIC manual and mains adaptor.	11	69.95	
	Mains Adaptor(s) (600 mA at 9 V DC nominal unregulated).	10	8.95	
	16K-BYTE RAM pack.	18	49.95	
	Sinclair ZX Printer.	27	49.95	
	8K BASIC ROM to fit ZX80.	17	19.95	
	Post and Packing.			2.95

Please tick if you require a VAT receipt

TOTAL £

*I enclose a cheque/postal order payable to Sinclair Research Ltd, for £

*Please charge to my Access/Barclaycard/Trustcard account no.

*Please delete/complete as applicable

Please print

Name: Mr/Mrs/Miss

Address:

sinclair ZX81

6 Kings Parade, Cambridge, Cambs., CB2 1SN.
Tel: (0276) 66104 & 21282.

FREEPOST – no stamp needed. Offer applies to UK only.

PRE 04

EXCITING OFFERS!

DIGITAL VOLTMETER MODULE

Fully built & tested



- Positive and negative voltages with an FSD of 999mV which is easily extended.
- Requires only single supply 7 - 12V.
- High overall accuracy $\pm 0.1\% + 1$ digit.
- Large bright 0.43" (11mm) LED displays.
- Supplied with full data and applications information.

ONLY
£11.95
+VAT

Using this fully built and calibrated module as a basis now means that you can easily build a wide range of accurate equipment such as multimeters, thermometers, battery indicators, etc. etc. at a fraction of the cost of ready-made equipment. Full details are supplied with each module showing how to easily extend the voltage range and measure current, resistance and temperature. Fully guaranteed, the unit has been supplied to electricity authorities, Government departments, universities, the P.O. and many companies.

Temperature Measurement

£2.15 +VAT

An easily constructed kit using an I.C. probe providing a linear output of 10mV/°C over the temperature range from -10°C to +100°C. The unit is ideal for use in conjunction with the above DVM module providing an accurate digital thermometer suitable for a wide range of applications.

Power Supply

£4.95 +VAT

This fully built mains power supply provides two stabilised isolated outputs of 9V providing current levels of up to 250mA each. The unit is ideally suited for powering the DVM and the Temperature Measurement module.

ULTRASONIC ALARM MODULE


Fully built & tested

ONLY
£10.95
+VAT

Power Supply & Relay Unit

£3.95 +VAT

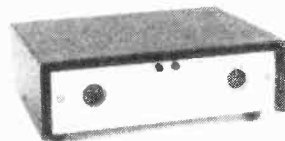Incorporating a stabilised 12V supply and a s.p.c.o. relay with 3A contacts, this unit is designed to operate in conjunction with the above ultrasonic unit. Fully built and tested, its compact size makes it ideal for constructing the smallest of units.



Range adjustable from 5' - 25'

A really effective fully built module which contains both ultrasonic transmitter and receiver, together with the necessary circuitry for providing the appropriate delays and false alarm suppression. Using this module with a suitable 12V power supply and relay unit such as that shown, a really effective though inexpensive intruder alarm may be constructed. The module, which is supplied with a comprehensive data sheet, is easily mounted in a wide range of enclosures. A ready drilled case, together with all the necessary hardware, is available below.

Siren Module

£2.57 +VAT

Producing a very loud and penetrating wailing sound, this module operates from 9-15 volts, capable of driving one or two 8 ohm speakers. Suitable horn speakers available at £4.30 each plus VAT.

Hardware Kit

£3.95 +VAT

A suitable ready drilled case together with the various mounting pillars, nuts and bolts, and including a mains switch and 2mm sockets designed to house the ultrasonic alarm module, together with its associated power supply. Size 153mm x 120mm x 45mm.

In addition to the above a wide range of competitively priced electronic components is stocked. Please telephone your specific requirements.



RISCOMP LIMITED

Dept. PE6,
21 Duke Street,
Princes Risborough, Bucks.
Tel: Princes Risborough (084 44) 6326

- V.A.T. must be added on all items.
- Shop hours 9 - 5.30 (Weds. 9 - 1)
- ex-stock delivery on all items.
- Units on demonstration, callers welcome.
- Post and packing charge 50p per order.
- S.A.E. with all enquiries please.



Just **50p** will bring you the latest Wilmslow Audio 80 page catalogue packed with pictures and specifications of HiFi and PA Speaker Drive Units, Speaker Kits, Cabinet Kits

1000 items for the constructor.

CROSSOVER NETWORKS AND COMPONENTS. GRILLES, GRILL FABRICS AND FOAM. PA, GROUP DISCO CABINETS - PLUS MICROPHONES - AMPLIFIERS - MIXERS - COMBOS - EFFECTS - SPEAKER STANDS AND BRACKETS - IN-CAR SPEAKERS AND BOOSTERS ETC. ETC.

- ★ Lowest prices — Largest stocks ★
- ★ Expert staff — Sound advice ★
- ★ Choose your DIY HiFi Speakers in the comfort ★ of our listening lounge. (Customer operated demonstration facilities)
- ★ Ample parking ★
- ★ Access . . . Visa . . . American Express accepted ★



0625 529599

35/39 Church Street, Wilmslow, Cheshire SK9 1AS



Lightning service on telephoned credit card orders! Please allow up to 7 days for delivery.



PARNDON ELECTRONICS LTD.

Dept. No 21 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel 0279 32700

RESISTORS: 1/4 Watt Carbon Film E24 range $\pm 5\%$ tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded/over and colour coded.
£1.00 per hundred mixed (Min 10 per value)
£8.50 per thousand mixed (Min 50 per value)
Special stock pack. 60 values. 10 of each £5.50

DIODES: IN4148 3p each Min order quantity - 15 items
£1.60 per hundred

DIL SWITCHES: Gold plated contact in fully sealed base - solve those programming problems
4 Way 86p each 6 Way £1.00 each 8 Way £1.20 each

DIL SOCKETS: High quality, low profile sockets.
8 pin - 10p 14 pin - 11p 16 pin - 12p 18 pin - 19p 20 pin - 21p
22 pin - 23p 24 pin - 25p 28 pin - 27p 40 pin - 42p

ALL PRICES INCLUDE V.A.T. & POST & PACKING — NO EXTRAS
MIN ORDER - U.K £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE
Same Day Despatch

IONISER KIT (MAINS OPERATED)

This negative ion generator gives you the power to saturate your home or office with millions of refreshing ions. Without fans or moving parts it puts out a pleasant breeze. A pure flow of ions pours out like water from a fountain, filling your room. The result? Your air feels fresh, pure, crisp and wonderfully refreshing.

All parts, PCB and full instructions £12.50
A suitable case including front panel, neon switch, etc. £6.50

HOURS:
Mon. to Fri. 9-5 pm.
Sat. 9-4.30 pm.

Price includes post & VAT.
Barclay/Access Welcome

Wide range of Japanese integrated circuits & transistors stocked.

T. POWELL,
Advance Works, P.E.,
44 Wallace Road,
London N1 1PQ.
Tel. 01-226 1489.

Please allow 14 days for delivery.

MASTER ELECTRONICS NOW!

The PRACTICAL way!


This new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn the practical way in easy steps mastering all the essentials of your hobby or to start or further a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi and microprocessor/computer equipment.

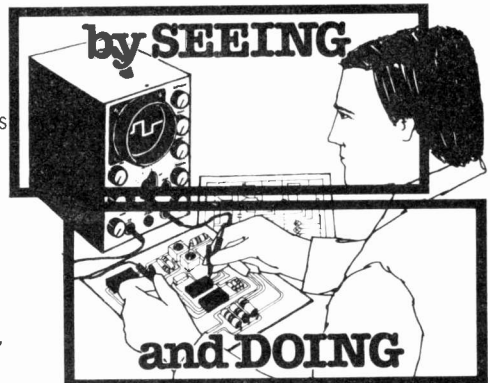

New Job? New Career? New Hobby? Get into **Electronics** Now!

FREE!
COLOUR BROCHURE



POST NOW TO:

Please send your brochure without any obligation to

NAME _____

ADDRESS _____

I am interested in:


- COURSE IN ELECTRONICS
as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- LOGIC COURSE

OTHER SUBJECTS _____

PE/4/821

BLOCK CAPS PLEASE

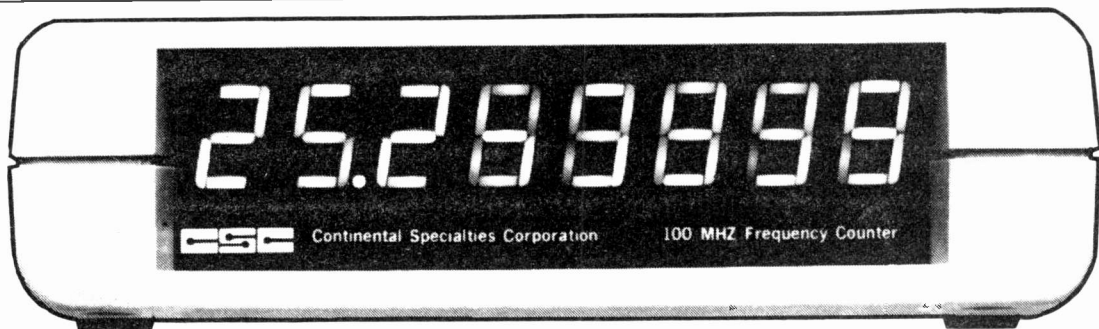British National Radio & Electronics School Reading, Berks. RG1 7BR



5HZ TO 100MHZ

TOMORROW'S TOOLS TODAY

GLOBAL SPECIALTIES CORPORATION



G.S.C. (UK) Limited Dept. 5D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex. CB11 3AQ
Telephone: Saffron Walden (0799) 21682
Telex: 817477

Instant frequency indication from 5Hz to 100MHz; no range selection problems; a brilliant 8-digit LED display; mains or battery operation; an accuracy of 4 parts per million ± 1 count; and totally automatic operation – all this for only £85.00* with GSC's new Max-100 frequency counter.

Just take a look at our spec. Where else could you find anything similar at the price?
*Frequency range 5Hz - 100 MHz *Input impedance 1M shunted by 10pF *Sensitivity 30mV from 1KHz up to 50MHz; 120mV r.m.s. over full frequency range *Timebase accuracy ± 4 parts in 10^6 (from 5 to 45°C) *Maximum aging rate 10 parts in 10^6 per year *Over-frequency indication *Low-battery-power alarm *Operates from dry or rechargeable cells, an external 7.5 to 10VDC supply, or a car battery (via an adaptor) *Dimensions: 45 x 187 x 143mm *Options: 12V adaptor; battery eliminator; r.f. antenna, low-loss r.f. tap, carrying case.

Despatched within 48 hrs.

Fill in the coupon for further details . . .

*price excludes post, packing and VAT

G.S.C. (UK) Limited, Dept. 5D, Unit 1, Shire Hill Industrial Estate, Saffron Walden, Essex CB11 3AQ.

MAX 100	FREQ. COUNTER	Unit price inc P&P 15% VAT £99.47	Qty Hrpt	
---------	---------------	-----------------------------------	-------------	--

Name _____
Address _____

I enclose cheque/P.O. for £ _____ or debit my Barclaycard/Access/
American Express card no. _____ exp. date _____

FOR IMMEDIATE ACTION – The G.S.C. 24 hour, 5 day a week service.
Telephone (0799) 21682 and give us your Barclaycard, Access, American
Express number and your order will be in the post immediately.

For Free
catalogue
tick box

POWER DIMMING MODULES

- ★ Fully isolated
- ★ Multi channel common wiring lines
- ★ Master dimming over banks
- ★ Remote override
- ★ Dead "kill" and "all on"
- ★ Low voltage feed lines
- ★ Common neutral or live outputs

A range of isolated digitally controlled dimming modules, complete with panels. Each type requires connection to the supply/reference board.

Slave power controllers (SPC)
Controls up to 1000W via the slider.
RFI suppressed/fused.

Slave power unit (SPU)
Controls up to 1000W via a logic signal from a remote slave.

Master controllers (MC)
Will master dim from 1 to a bank of 20 SPC units.

Remote slaves (RS) - (Preset)
Will override an SPC at a remote location to the main system or control an SPU.

Supply/reference board
Provides the necessary supply voltages and signals to all units. Facilities for "Kill" and "all on". Supplies up to any combination of 50 modules.

PRICES (1 of)

SPC	£13.90
SPU	£9.90
MC	£7.20
RS	£8.50
Supply	£18.20

SPECIAL DISCOUNTS
Are available on power dimmers.
Total your order up and deduct:
£100 to £199 20%
£200 to £299 25%
£300 to £399 30%
£400+ 40%

3 CHANNEL SOUND/LIGHT CHASER LB31000SLC £35.70



A high performance sound to light system which automatically switches to a chase when the music ceases. Super sensitive with an anti-interference circuit, the unit will operate from practically any amp and control up to 1,000W/channel, 5HZ to 70K. Controls: bass/mid/treble/master sensitivity/chase speed.

STEREO DISCO MIXER/PREAMP LBPA3 £33.70



Magnetic or ceramic deck versions - please state on one board, left and right deck mixers/controls/misc. mixer/tones/mic. auto fade over decks/and P.F.L. The unit can be used with either LB 100/150/250.


NEW! NEW! NEW! 4 CHANNEL SOUND LIGHT AUTO-CHASER (£49.90)

(panels, etc. £9.20)

- ★ Bass/mid/presence/treble
- ★ Automatic level filter control
- ★ Automatic input gain control
- ★ LED monitor drivers
- ★ 10Hz to 30KHz response
- ★ Super sensitive
- ★ Zero reference triggering
- ★ Fascia/LED, etc., available

Phone or write for immediate details of the LB41000SLC.

MULTI-4 £9.70 EXTRA



The Multi-4 is a comprehensive sound and chase module, offering a wide range of forward, reverse or random effects, with additional sound modulation facilities. Modes of operation are set on control pots which act as electronic switches. The unit has a wide speed range and will accept virtually any sound level input. The Multi-4 also provides monitor circuits for LED driving. The triac outputs may be used to drive up to 4000W of lighting or up to 30 metres of rope lights.

PRICE REDUCED! £48.90


Attractive blue panels with white letters, complete with LED monitors, knobs and mains illuminated switch.

NEW! NEW! NEW! 2/4/8 CHANNEL CHASER LB81000LC £28.00



An all logic chaser system for use with up to 8 channels at 1,000 watts each. Facilities include footswitch trigger and module cascading (16, 24, 32 channel, etc.), chase speed and re-cycle delay.

PROGRAMMABLE - 8 £114.90

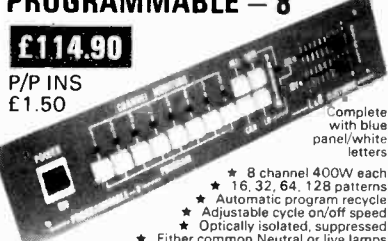

P/P IN \$ £1.50

Complete with blue panel/white letters

- ★ 8 channel 400W each
- ★ 16, 32, 64, 128 patterns
- ★ Automatic program recycle
- ★ Adjustable cycle on/off speed
- ★ Optically isolated, suppressed
- ★ Either common Neutral or live lamps

An advanced lighting module allowing any chase or sequence effects to be programmed, stored and recalled. Up to 128 patterns can then be replayed in the stored order, with control over the cycle on and off time. At the end of the program the system re-cycles to the start to maintain a continuous display. Full monitoring on the control panel over the outputs and control status is provided, and the program may be halted at any time. Although removing the mains supply to the module will delete the stored patterns the use of calculator type push buttons allows speedy programming ready for the following night's performance. The module obviously provides unlimited effects and is a must for all serious lighting shows.

3 CHANNEL SOUND/LIGHT LB31000SL £22.70



All the advantages of the SLC without chase Controls: bass/mid/treble/master sensitivity.

3-WAY ACTIVE CROSSOVER LBAC01 £17.90



Bass/mid/treble active crossover with stage booster! Available with crossover points of 200 or 300Hz, and 2K or 3KHz (please specify) LBPSU1 supply for LBAC01. (1 or 2).

4 CHANNEL SEQUENCER LB41000LS £19.20



A 4 channel sequence generator for banks of lamps up to 1,000W per channel. Two speed controls, cross effect to provide settings between seconds and rapid burst.

L & B ELECTRONIC MODULES

PROFESSIONAL ENGINEERING BY PROFESSIONALS

45 Wortley Road, West Croydon Surrey CR0 3EB. Tel. 01-689 4138

Goods by return of Post.

Each module is manufactured from the highest quality components, fully tested, supplied with a connection and circuit diagram and guaranteed for twelve months. All prices shown are VAT inclusive. Please include 75p post/packing except where individually stated. To mail order send cheque/P.O./Registered cash/Access number. C.O.D. service £1 extra. For further information send a s.a.e. stating which model.

PLEASE NOTE THIS COMPANY HAS NO CONNECTION WITH LB ELECTRONICS OF HILLINGDON

OVERSEAS DISTRIBUTORS

Enquiries are invited from overseas companies in distributing our high quality products.

PE CAR COMPUTER



This unit was described by Practical Motorist as: "One of the neatest, most comprehensive and most useful of these car computers that we have yet come across..."

The PE Car Computer was designed to exceed the specification of all others, both for number of functions and accuracy. As well as the usual functions, it can perform eleven "remaining" type calculations, has a unique "start-stop" mode (used for acceleration timing and the like) and has a combination lock for driving an alarm or ignition cut-out.

The unit is housed in a custom designed box with high quality printed panels having an overall size of 165 x 50 x 80mm deep, and can be fitted above or below the dashboard. The display is liquid crystal for clarity in all lighting conditions.

The kit includes all sensors, wiring, etc and is suitable for all cars except those fitted with diesel or fuel injection engines.

Kit price: £78.50 Assembled Price: £88.50
+ £1 p&p includes VAT.
Send S.A.E. for list of separately available parts.
Goods by return of post.



PIMAC SYSTEMS LTD
20 Bloomfield Road, Moseley, Birmingham B13 9BY.
Tel: 021-449 0384

HOW WOULD YOU LIKE YOUR ZX81 TO LOOK LIKE THIS?



IT COULD WITH THE CROFTON ZX81 ADAPTAKIT.

ONLY £35.00 plus VAT - total £40.25 plus £2.65 P&P. AND IT ALSO HAS A VIDEO OUTPUT TO DRIVE A STANDARD MONITOR.

SEND FOR DETAILS.

CROFTON ELECTRONICS LIMITED

35 Grosvenor Road, Twickenham, Middlesex TW1 4AD. Tel: 01 891 1923/1513
Telex: 295093. Up to 28 days for delivery.

BI-PAK BARGAINS



5T21 SCREWDRIVER SET
6 precision screwdrivers in hinged plastic case. Sizes: — 0.8, 1.4, 2, 2.4, 2.9 and 3.8mm **£1.75**

5T31 NUT DRIVER SET
5 precision nut drivers in hinged plastic case. With turning rod. Sizes: — 3, 3.5, 4, 4.5 and 5mm. **£1.75**

5T41 TOOL SET
5 precision instruments in hinged plastic case. Crosspoint (Phillips) screwdrivers — H 0 and H 1 Hex key wrenches: — 1.5, 2 and 2.5mm **£1.75**

5T51 WRENCH SET
5 precision wrenches in hinged plastic case. Sizes: — 4, 4.5, 5, 5.5 and 6mm. **£1.75**

BUY ALL FOUR SETS: 5T21-5T51 and get HEX KEY SET **FREE**
HEX KEY SET ON RING
Sizes: 1.5, 2, 2.5, 3, 4, 5, 5.5 and 6mm.
Made of hardened steel.
HX/1 **£1.25**




BI-PAK PCB ETCHANT AND DRILL KIT

Complete PCB Kit comprises
1 Expo Mini Drill 10,000RPM 12v DC incl 3 collets & 1 x 1mm Twist bit
1 Sheet PCB Transfers 210mm x 150mm.
1 Etch Resist Pen.
1 1/2 lb pack FERRIC CHLORIDE crystals
3 sheets copper clad board.
2 sheets Fibreglass copper clad board
Full instructions for making your own PCB boards.
Retail Value over **£15.00**
OUR BI-PAK SPECIAL KIT PRICE **£9.75**
ORDER NO. SX81



BI-PAK SOLDER - DESOLDER KIT

Kit comprises ORDER NO. SX80
1 High Quality 40 watt General Purpose Lightweight Soldering Iron 240v mains incl 3/16" (4.7mm) bit
1 Quality Desoldering pump. High Suction with automatic ejection. Knurled, anti-corrosive casing and teflon nozzle.
1.5 metres of De-soldering braid on plastic dispenser
2 yds (1.83m) Resin Cored Solder on Card.
1 Heat Shunt tool tweezers Type.
Total Retail Value over **£12.00**
OUR SPECIAL KIT PRICE **£8.95**

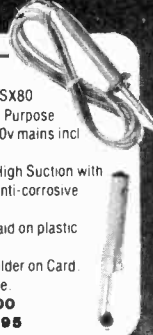

BRAND NEW LCD DISPLAY MULTITESTER.

RE 188m
LCD 10 MEGOHM INPUT IMPEDANCE
*3 1/2 digit * 16 rangos plus hFE test facility for PNP and NPN transistors *Auto zero, auto polarity *Single-handed, pushbutton operation *Over range indication *12 5mm (1/2-inch) large LCD readout *Diode check *Fused circuit protection *Test leads, battery and instructions included.
Max indication 1999 or — 1999
Polarity indication Negative only
Positive readings appear without + sign
Input impedance 10 Megohms
Zero adjust Automatic
Sampling time 250 milliseconds
Temperature range —5°C to 50°C
Power Supply 1 x PP3 or equivalent 9V battery
Consumption 20mW
Size 155 x 88 x 31mm
RANGES
DC Voltage 0-200mV
0-2-20-200-1000V Acc 0.8%
AC Voltage 0-200-1000V
Acc 1.2% DC Current 0-200uA
0-2-20-200mA 0-10 A Acc. 1.2%
Resistance 0-2-20-200K ohms.
0-2 Megohms Acc: 1%
BI-PAK VERY LOWEST POSS PRICE **£35.00** each



SEMICONDUCTORS FROM AROUND THE WORLD

100 A Collection of Transistors, Diodes, Rectifiers, Bridges, SCR's, Triacs, IC's both Logic and Linear plus Opto's all of which are current everyday usable devices. **100**

Guaranteed Value over £10 at Normal Retail Price

Yours for only **£4.00** Data etc. in every pack. Order No. SX56



EXPERIMENTER BOXES - ALUMINIUM - PLASTIC ALUMINIUM BOXES

Made with Bright Aluminium folded construction with deep lid and screws

SIZE	L	W	H	Order No.	Price
5 1/4	2 1/4	1 1/2	159	83p	
4	2 1/4	1 1/2	161	83p	
4	2 1/2	2	163	83p	
3	2	1	164	87p	
8	6	3	166	£1.88	
6	4	2	167	£1.12	

All measurements for boxes are shown in inches. L = Length W = Width. H = Height

Plastic Boxes

Coloured Black. Close fitting Flanged Lid, fixing screws into brass bushes

SIZE	L	W	H	Order No.	Price
4	2	1	141	£1.00	
4 1/4	2 1/2	1 1/2	143	£1.30	
6	3 1/2	2	144	£1.50	

Plastic as above but with aluminium top panel

SIZE	L	W	H	Order No.	Price
4	2 1/4	1	146	£1.40	

Plastic sloping front

SIZE	L	W	H	Order No.	Price
5 1/2	4 1/4	2 1/4	148	£2.14	

The Third and Fourth Hand...

... you always need but have never got until now
This helpful unit with Rod mounted horizontally on Heavy Base. Crocodile clips attached to rod ends. Six ball & socket joints give infinite variation and positions through 360° also available attached to Rod a 2 1/2" diam magnifier giving 2.5 x magnification. Helping hand unit available with or without magnifier. Our Price with magnifier as illustrated ORDER NO. T402 **£5.50**
Without magnifier ORDER NO. T400 **£4.75**



"IRRESISTABLE RESISTOR BARGAINS"

Pak No.	Qty*	Description	Price
SX10	400	Mixed "All Type" Resistors	£1
SX11	400	Pre-formed 1/4-watt Carbon Resistors	£1
SX12	200	1/4 watt Carbon Resistors	£1
SX13	200	1/4 watt Carbon Resistors	£1
SX14	150	1/2 watt Resistors 22 ohm 2m2 Mixed	£1
SX15	100	1 and 2 watt Resistors 22 ohm 2m2 Mixed	£1

Paks SX12-15 contain a range of Carbon Film Resistors of assorted values from 22 ohms to 2.2 meg. Save pounds on these resistor paks and have a full range to cover your projects.
Quantities approximate, count by weight.

"CAPABLE CAPACITOR PAKS"

Pak No.	Qty*	Description	Price
SX16	250	Capacitors Mixed Types	£1
SX17	200	Ceramic Capacitors Miniature	£1
SX18	100	Mixed	£1
SX19	100	Mixed Ceramics 1pt-5 pt	£1
SX20	100	Mixed Ceramics 68pf-0.5mf Assorted Polyester/Polystyrene Capacitors	£1
SX21	60	Mixed C280 type capacitors metal foil	£1
SX22	100	Electrolytics, all sorts	£1
SX23	50	Quality Electrolytics 50-1000mf	£1
SX24	20	Tantalum Beads, mixed	£1

*Quantities approximate, count by weight.

AUDIO PLUGS, SOCKETS AND ACCESSORIES

25 pieces of Audio Plugs, Sockets and Connectors to include DIN 180°, 240°, inline 3-6 Pin, at well over £3 normal. Order No. SX25. Our Price £1.50 per pak. Guaranteed to save you money.

SX26	3 Pcs.	of 6 pin 240° DIN Plugs and Chassis Sockets.	50p
SX38	100	Silicon NPN Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Real value.	£2.50
SX39	100	Silicon PNP Transistors—all perfect. Coded mixed types with data and eqvt sheet. No rejects. Fantastic value.	£2.50

Silicon NPN-L Type Transistors

10-92 Plastic centre collector
Like BC182L — 183L — 184L
VC80 45 VCE0 30 IC200mA Hfe 100-400
ALL perfect devices — uncoded ORDER AS SX183L
50c off 100c off 500c off 1000c off
£1.50 £2.50 £10.00 £17.00

PNP SILICON TRANSISTORS:

Similar ZTX500 — ZTX214 — E-Line
VCE0 40 VCB0 35 Ic 300mA Hfe 100-400
Brand New — uncoded — Perfect Devices
50c off 100c off 500c off 1000c off
£2.00 £3.50 £15.00 £25.00
Order as ZTXPNP

MOTOR LA PIEZO ELECTRIC TWEETER

Maximum Ratings:
25 volts rms which is equal to:
200 watts across 4 ohms
100 watts across 8 ohms
50 watts across 16 ohms
BI-PAK SPECIAL OFFER PRICE **£4.85**
ORDER NO. 1907




DOME TWEETER

Dome tweeter for systems up to 50w.
Impedance 8 ohms
Frequency Response 2000-20,000Hz
Dims 98mm diam x 31mm deep
Our Price **£2.85** DMT200

TECASBOTY

The Electronic Components and Semiconductor Bargain of the Year. A host of Electronic components including potentiometers — rotary and slider, presets — horizontal and vertical Resistors of mixed values 22ohms to 2M2 — 1/8 to 2 Watt. A comprehensive range of capacitors including electrolytic and polyester types plus disc ceramics etcetera. Audio plugs and sockets of various types plus switches, fuses, heatsinks, wire, nuts/bolts, gromets, cable clips and ties, knobs and P.C. Board. Then add to that 100 Semiconductors to include transistors, diodes, SCR's opto's, all of which are current everyday usable devices. In all a Fantastic Parcel. No rubbish! Identifiable and valued in current catalogues at well over £25.00. Our Fight Against Inflation — Beat the Budget — Down with Depression

Price — **JUST £6.50.**
ORDER NO. SX 85

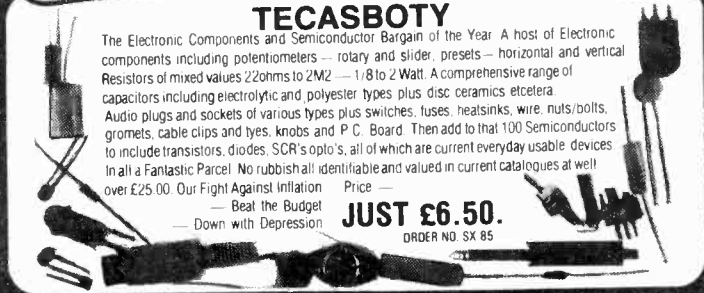

BI-PAK

Send your orders to Dept PE4 BI-PAK PO BOX 6 WARE HERTS
WHP AT 1 BALDOLK ST WARE HERTS
TERMS: CASH WITH ORDER. SAME DAY DESPATCH ACCESS.
BARCLAY BANK ALSO ACCEPTED TEL 0920 3182. GIRO 388 7006
ADD 15% VAT AND 50p PER ORDER POSTAGE AND PACKING



Use your credit card. Ring us on Ware 3182 NOW and get your order even faster. Goods normally sent 2nd Class Mail.
Remember you must add VAT at 15% to your order. Total. Postage add 50p per Total order.

LOOK

Kit includes tape transport mechanism, ready punched and back printed quality circuit board and all electronic parts i.e. semiconductors, resistors, capacitors, hardware, top cover, printed scale and mains transformer. You only supply solder & hook-up wire.

Self-assembly simulated wood cabinet. £4.50 + £1.50 p+p.

Featured in April issue Practical Electronics, reprint 50p - Free with Kit.

INTRODUCTORY OFFER - ONLY

£32⁹⁵


+ £2.75 p&p.



P.E. STEREO CASSETTE RECORDER KIT

- NOISE REDUCTION SYSTEM
- AUTO STOP
- TAPE COUNTER
- SWITCHABLE E.O.
- INDEPENDENT LEVEL CONTROLS
- TWIN V.U. METER
- WOW & FLUTTER 0.1%
- RECORD/PLAYBACK I.C. WITH ELECTRONIC SWITCHING
- FULLY VARIABLE RECORDING BIAS FOR ACCURATE MATCHING OF ALL TAPES

STEREO AMPLIFIER KIT

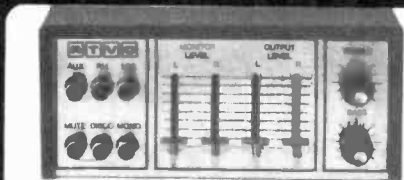

- Featuring latest SGS/ATES TDA 2006 10 watt output IC's with in-built thermal and short circuit protection.
- Mullard Stereo Preamplifier Module.
- Attractive black vinyl finish cabinet, 9" x 8" x 3 3/4" (approx).
- 10+10 Stereo converts to a 20 watt Disco amplifier.

To complete you just supply connecting wire and solder. Features include din input sockets for ceramic cartridge, microphone, tape or tuner. Outputs - tape, speakers and headphones. By the press of a button it transforms into a 20 watt mono disco amplifier with twin deck mixing. The kit incorporates a Mullard LP1183 pre-amp module, plus power amp assembly kit and mains power supply. Also features 4 slider level controls, rotary bass and treble controls and 6 push button switches. Silver finish fascia with matching knobs and contrasting cabinet. Instructions available, price 50p. Supplied FREE with kit.

£16-50

+ £2.90 p&p.

SPECIFICATIONS:
Frequency response
Input sensitivity

Tone controls

Distortion
Mains supply

8" SPEAKER KIT Two 8" twin cone domestic speakers. £4.75 per stereo pair plus £1.70 p&p, when purchased with amplifier. Available separately £6.75 & £1.70 p+p.

125W HIGH POWER AMP MODULE

KIT: **£10-50** BUILT: **£14-25**
+ £1.15 p&p + £1.15 p&p.

The power amp kit is a module for high power applications - disco units, guitar amplifiers, public address systems and even high power domestic systems. The unit is protected against short circuiting of the load and is safe in an open circuit condition. A large safety margin exists by use of generously rated components, result, a high powered rugged unit. The PC board is back printed, etched and ready to drill for ease of construction and the aluminium chassis is preformed and ready to use. Supplied with all parts, circuit diagrams and instructions.

ACCESSORIES: Suitable mains power supply kit with transformer: £7.50 plus £3.15 p&p.
Suitable LS coupling electrolytic: £1.00 plus 25p p&p.



SPECIFICATIONS:

Max. output power (RMS): 125W.
Operating voltage (DC): 50 - 80 mA.
Loads: 4 - 16 ohms.
Frequency response measured @ 100 watts: 25Hz - 20KHz.
Sensitivity for 100 watts: 400mV @ 47K.
Typical T.H.D. @ 50 watts, 4 ohms: 0.1%.
Dimensions: 205 x 90 and 190 x 36 mm.

HI-FI SPEAKERS AT BARGAIN PRICES



GOODMANS TWEETERS

8 ohm soft dome radiator tweeter (3 3/4" sq.) for use in up to 40W systems, with 2 element crossover.


£3.50 each (p&p £1) or £5.95 pair (p&p £2).

35 WATT MICRO 2-WAY SPEAKER SYSTEM

Unit comprises one 50w (4" app.) Audax soft dome tweeter HD100. And one 5" Audax bass/midrange 35w driver HIF11JSM. Complete with 2 element crossover. Total impedance of system 4 ohms.

£7.95

PER SET + £2.70 p&p.

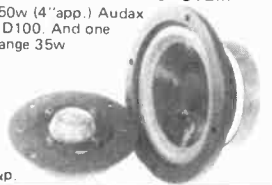


P.E. STEREO TUNER KIT

This easy to build 3 band stereo AM/FM tuner kit is designed in conjunction with Practical Electronics (July 81 issue). For ease of construction and alignment it incorporates three Mullard modules and an I.C. IF System. **FEATURES:** VHF, MW, LW Bands, interstation muting and AFC on VHF. Tuning meter. Two back printed PCB's. Ready made chassis and scale. Aerial: AM - ferrite rod, FM - 75 or 300 ohms. Stabilised power supply with 'C' core mains transformer. All components supplied are to P.E. strict specification. Front scale size: 10 1/2" x 2 1/2" approx. Complete with diagram and instructions.

£17-95

Plus £2.50 p&p.

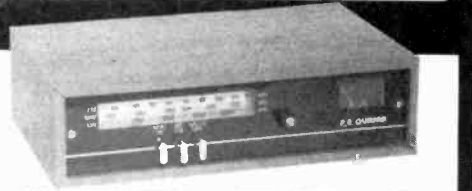Self assembly simulated wood cabinet sleeve to suit tuner only. Finish size: 11 1/4" x 8 1/2" x 3 3/4".
£3.50 Plus £1.50 p&p.



SPECIAL OFFER! TUNER KIT PLUS:

• Matching I.C. 10 watt per channel Power amp kit. • Mullard LP1183 built pre-amp, suitable for ceramic pick-up and aux. inputs. • Matching power supply kit with transformer. • Matching set of 4 slider **£21.95** controls for bass, treble and volumes. + £3.80 P&P.

PRACTICAL ELECTRONICS CAR RADIO KIT SERIES II



2 WAVE BAND, MW - LW

- Easy to build. • 5 push button tuning. • Modern design. • 6 watt output. • Ready etched and punched PCB. • Incorporates suppression circuits.

All the electronic components to build the radio, you supply only the wire and the solder, featured in Practical Electronics. Features: pre-set tuning with 5 push button options, black illuminated tuning scale. The P.E. Traveller has a 6 watt output neg. ground and incorporates an integrated circuit output stage, a Mullard IF Module LP1181 ceramic filter type re-aligned and assembled, and a Bird pre-aligned push button tuning unit.

Suitable stainless steel fully retractable aerial (locking) and speaker (6" x 4" app.) available as a complete kit. £2.50/pack + £1.50 p&p.

£12-95

+ £2.00 p&p.

BIRD AUDIO STEREO CAR RADIO BOOSTER



To boost your car radio or radio cassette to 15W r.m.s. per channel.

£9-95 + £1.50 p&p.

TV SOUND TUNER KIT



£11-45

+ £1.50 p&p.

As featured in E.T.I. December '81 issue. Kit of parts including PCB, UHF tuner and selector switch with all components excluding case.

• Transformer £1.50 + £1.50 p&p (p&p free on transformer if ordered with kit). • Ready built LP1183 Module for simulated stereo operation. **£1.95** + 75p p&p.

MONO MIXER AMP



£39-95

+ £3.70 p&p.

50 WATT Six individually mixed inputs for two pick ups (Cer. or mag.), two moving coil microphones and two auxiliary for tape, tuner, organs, etc. Eight slider controls - six for level and two for master bass and treble, four extra treble controls for mic. and aux inputs. Size: 13 1/4" x 6 1/2" x 3 3/4" app. Power output 50 watts R.M.S. (continuous) for use with 4 to 8 ohm speakers. Attractive black vinyl case with matching fascia and knobs. Ready to use.

ALL MAIL TO:

21B HIGH STREET, ACTON, W3 6NG.
Note: Goods despatched to UK postal addresses only. For further information send for instructions 20p plus stamped addressed envelope. All items subject to availability. Prices correct at 31/1/82 and subject to change without notice. Please allow 7 working days from receipt of order for despatch.

ALL PRICES INCLUDE VAT AT 15%.

ALL CALLERS TO: 323 Edgware Rd, London W2. Telephone: 01-723 8432.
Open 9.30 - 5.30pm. Closed all day Thursday.
RTVC Limited reserve the right to update their products without notice.



FAME AT LAST!

Sharp eyed readers will no doubt have noticed the *Telectric* being put through its paces on a certain national TV programme (minus its name of course) and listeners to local radio stations in various parts of the country may have heard the *PE Bandbox* (a recent project) and also an interview with Steven Day and Peter Hutt of Response—the company supplying kits and ready-made Telectrics. It's nice that our projects are attracting attention from the "National media".

Of course our projects can't all be new and innovative and many, like our *PE Quasar Stereo Cassette Deck* in this issue, have been around in similar commercial form for some time. However, this particular project is a first for PE and is one of the few cassette recorder designs available to the hobbyist in kit form—it is also another project that may become a commercial success story in ready-built form at a later date. Hobbyists have the advantage of time and price, thanks to our project.

While talking about price it is interesting to note that when *Telectric* was first designed about three years ago the cost of building it would have

been around £300. We have come to expect microprocessors for £5 or less, though we still happily pay relatively high prices for everyday items.

PRICES

We are all well aware of prices these days and we hope that PE can be of assistance in this area. This month we start two new services to readers, the first is a special arrangement with Videotone who are making their high quality cassette tapes available to PE readers on a regular basis at exclusive prices—see page 51—and the second is the appearance of the first readers' ads in *PE Bazaar* (page 45). You can't get an advertisement placed for less than our free readers' ad. service! Judging by the early replies we have received there should be some bargains in *PE Bazaar* and we hope it will lead to the development of a greater interchange of information, components and equipment between hobbyists—we anticipate many more ads. appearing next month when there has been more time for you to send them in.

CLUB

Interchange of information and assistance to all hobbyists are part of

the aims of the British Amateur Electronics Club (BAEC) which has been run by dedicated volunteers for many years and offers its members a quarterly newsletter containing articles, letters, news and views on all aspects of our hobby, special concessions from many component retailers and meetings at various venues.

BAEC can give the informal contact between fellow hobbyists that we are unable to arrange via the magazine. It is, therefore, a valuable asset to all who have electronics as their hobby and, among other things, provides valuable help to beginners. They can give advice, loan practical aids and have an extensive library covering most magazines and many technical books. In case our overseas readers are wondering, the club is also open to them. A letter from Cyril Bogod—chairman of BAEC—appears on page 53, contact him for further information.

By the way, we have no formal connection with BAEC but, as a magazine dedicated to the electronics hobbyist, like to give them our encouragement.

Mike Kenward

EDITOR Mike Kenward
Gordon Godbold ASSISTANT EDITOR
Mike Abbott TECHNICAL EDITOR
David Shortland PROJECTS EDITOR
Jasper Scott PRODUCTION EDITOR

Jack Pountney ART EDITOR
Keith Woodruff ASSISTANT ART EDITOR
John Pickering SEN. TECH. ILLUSTRATOR
Isabelle Greenaway TECH. ILLUSTRATOR
Colette McKenzie SECRETARY

Editorial Offices:
 Practical Electronics,
 Westover House,
 West Quay Road, Poole,
 Dorset BH15 1JG
Phone: Editorial Poole 71191

We regret that lengthy technical enquiries cannot be answered over the telephone (see below).

ADVERTISEMENT MANAGER **D. W. B. Tilleard** } **01-261 6676**
 SECRETARY **Christine Pocknell** }
 AD. SALES EXEC. **Alfred Tonge** **01-261 6819**
 CLASSIFIED SUPERVISOR **Barbara Blake** **01-261 5897**
 AD. MAKE-UP/COPY **Ian Sweeney** **01-261 6601**

Advertising Offices:
 Practical Electronics Advertisements,
 King's Reach Tower,
 King's Reach, Stamford Street, SE1 9LS
 Telex: 915748 MAGDIV-G

Technical Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or international reply coupons, and each letter should relate to **one published project only.**

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at 95p each including Inland/Overseas p&p.

Binders

Binders for PE are available from the same address as back numbers at £4.60 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. Orders should state the year and volume required.

Subscriptions

Copies of PE are available by post, inland or overseas, for £13.00 per 12 issues, from: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques and postal orders should be made payable to IPC Magazines Limited.

Edited by
Jasper Scott

Beckman Expansion means more jobs

Beckman Instruments is substantially expanding its resistor network manufacturing capacity at its plant in Glenrothes, Scotland. This expansion will provide a total of 100 new jobs.

The first phase of the expansion will immediately provide 40 new jobs for technicians, engineers, supervisors and assembly workers, and the second phase will involve further equipment and provide 60 more jobs.

The investment, backed by Locate in Scotland (LIS), is a result of the decision by Beckman Instruments Inc to concentrate the manufacture of selected models of resistor networks at the most efficient Beckman plants to meet the total worldwide demand for the products.

Managing director Eoin O'Cuilleain said:

"the expansion, which represents a 25% increase in the workforce, is a reflection of the company's confidence in the future and on the quality of work produced by all employees in Scotland. This increase in production capacity will enable us to offer an even more efficient service, with faster deliveries, to our customers worldwide. Without the co-operation of the LIS and the Glenrothes Development Corporation, it is unlikely that the expansion could have been successfully achieved in the current depressed economic environment," he added.

STEP FORWARD

Casio's latest addition to their range of keyboard instruments, the Casiotone 701, represents a major step forward in bringing music making within the reach of the uninitiated.

The biggest advance is in the use of a bar code reader to read and programme specially scored music, enabling playback in three ways:

- automatic playback of the entire piece;
- manual melody playing, guided by lamps above each key (with auto accompaniment);
- "One Key Play" which allows the melody to be played by touching one key. The 701 can also be programmed via the keyboard, and editing facilities are provided. Alternatively, the 701 can be played in the traditional manner, so its easy-play facilities do not limit it for use solely as a beginners instrument.

Features of the 701 include a five octave keyboard with eight-note polyphony, 20 pre-set voices, a chord system enabling one finger accompaniment, and 16 auto-rhythms. It is available at a price of £495 including VAT and p&p from Tempus, 38 Burleigh Street, Cambridge, CB1 1DG. (0223 312866)

Foiled again!

At a time of increasing concern that a limited nuclear war in Europe could be around the corner, a Wales based company appears to be cashing in on present fears with a claim that they have discovered the means of producing a lightweight radiation-proof material.

Sivoh Electronics Ltd., of Faol-Ydnah, Gwent, say that they discovered the materials special properties while experimenting on alternatives to Mica Foil for capacitors. Sivoh claim that the material, known as PROLAFOIL, (for which Patents are at present being applied for) could probably be used to make totally radiation-proof suits. The only obvious drawback at present is cost — production costs are estimated to be around £500 per square metre, though Sivoh say that they are looking into ways to cut that figure by about half.

Whether or not Sivoh succeed in producing a marketable product, the moral question remains — are we, by producing the means to survive a nuclear war (i.e. radiation-proof suits, fallout shelters, etc.) thereby increasing the likelihood of a nuclear disaster?

For further details, see page 51.

TANDY BREAKS INTO 16-BITS

The Tandy Corporation (Branch UK) has announced the introduction of TRS-80 Model 16 to its range of microcomputers.

The Model 16 features sixteen bit technology, dual processor architecture and a multi-user operating system. It is capable of 512K internal RAM memory storage, and 2½ megabytes of disk storage may also be added. This combination of large RAM and disk memory capacity will allow the Model 16 to use more sophisticated software with large file capacities.

The Model 16 desktop computer will be available late in 1982 in two versions, both with 128K memory. A single drive version with 1½ megabytes of disk storage, and a two-drive version with a total 2½ megabyte storage capacity.

The new TRS-80 Model 16 uses two microprocessors' the Z-80A and the 16-bit MC68000.

For TRS-80 Model II owners, there is the Enhancement Option, which is an upgrade board to 16-bits.

The upgrade board set for the TRS-80 Model II microcomputer provides it with the 16-bit, dual-processor, multi-user power of the TRS-80 Model 16 computer, and will also be available by the end of 1982.

QUASAR CASE



Pictured above is the PE Quasar Stereo Tuner (constructional details published in PE, July '81) now resplendent in a simulated wood cabinet. The cabinet will be available at the end of March for £3.50 (plus £1.50 p&p) from RT-VC, who also supply kits for the Quasar Tuner itself. RT-VC, 21b High Street, Acton, London W3.

MARKET PLACE

Items mentioned are available through normal retail outlets unless otherwise specified. Prices correct at time of going to press.

Briefly...

Two of the United Kingdom's microcomputing pioneers and founder member of the Computer Retailers Association (CRA). Tim Moore and Jon Day, have formed a new company called Kuma Computers to supply working microsystems, proven software, educational books and, it is claimed, *unreserved* personal service.

Blanket invitation goes out to anyone with marketable software to contact Kuma Computers, 11 York Road, Maidenhead, Berks SL6 1SQ.




Bruel & Kjaer (U.K.) Ltd., have just issued their 1982 Short Form Catalogue which is free upon application.

It is a 60-page colour illustrated booklet describing the full range of instruments, transducers, microphones and other accessories available for the measurement, analysis and recording of sound (or noise), vibration, strain, acoustic emission, hydro-acoustic signals, mechanical balance and illumination contrast.

B & K are located at: Cross Lances Road, Hounslow, Middlesex TW3 2AE.



 Grenson Electronics have informed us that they have had to increase the prices of kits for the Bench PSU, featured in our February issue. The complete kit is now priced at £35 plus VAT and £2.40 p&p. The price of the ready built unit has also been increased to £59 plus VAT and p&p.



Home Radio have recently moved premises. Personal callers should now go to 169 London Road, Mitcham, Surrey. Their mail order address is still the same: P.O. Box 92, 215 London Road, Mitcham, Surrey.

POINTS ARISING . . .

Microbus (Nov. '81)

There is an error in line 20 of the program for a ZX80 Crosshatch Generator (page 68). It should read as follows:
20 PRINT CHR \$(X);";";

VERSATILE MULTIMETER

Now available from Centemp, the Model 3T (pictured right) is a battery operated 3½ digit hand held digital multimeter with a bold 0.5" liquid crystal display.

The meter provides six functions in 16 ranges permitting measurement of DC voltage, AC voltage, DC current, resistance, Diode/continuity check and an h_{FE} measurement facility. Push button controls allow fast and easy operation whilst small size, robust construction and long battery life make the 3T truly portable. Supplied complete with battery, test leads and instruction manual.

Priced at £49.95 including VAT and p&p, the 3T is available from Centemp, 62 Curtis Road, Whitton, Hounslow, Middlesex TW4 5PT (01-894 2723).



ILLUMINATING

L & B Electronics have recently introduced another unit to their range of lighting control modules. The LB 41000SLC is an advanced 4 channel sound to light modulator with automatic chase, providing bass, middle, presence and treble separation. Using automatic level filters, coupled with a choice of automatic gain control in the input stage, the unit requires virtually no setting-up procedure whilst making excellent separation.

As with the 31000SLC, in the absence of a music signal the module automatically switches to a forward then reverse running chase.

All the usual advantages of L & B modules are incorporated with the addition of LED monitor drivers for each channel. The fused triac output stage will handle resistive loads of up to 750 watts/channel.

The price, £43.39 plus £6.57 VAT. A blue fascia panel complete with LED's, illuminated switch and controls is also stocked at £8.00 plus £1.20 VAT.

For further information contact: L & B Electronics, 45 Wortley Road, West Croydon, Surrey (01-689 4138).

Best of British...

Discom of Evesham have announced the launch of a new British microcomputer, a micro which they say "will take on the world and win".

The 'McCombo' computer has been designed and built by a U.K. development team after eight months' research into the micro market. Research identified a need for a powerful, CP/M based single board computer, small enough to fit inside a terminal or disk drive case. Using McCombo, terminal manufacturers can produce a fully integrated CP/M based system using their own product with little or no development cost.

The board incorporates state of the art technology, including 64k memory chips. It is multi-user in operation, handling up to 4 users.

Discom say that initial trade reaction has been so good that sales of 3000 units are anticipated in 1982. Introductory prices start at under £400.

For further details, contact Discom, Old Manor Farm, Ashton-under-Hill, Evesham, Worcs. (0386 881962).

IS YOUR MICRO BAUD STIFF?


There is a versatile memory machine on the market which features read/write speeds and data integrity comparable to disc, but at a fraction of the cost! With up to 64K bytes per side, it will replace disc where access time itself is not too critical.

What is this machine? The 220M Digital Tape Recorder! A low-cost, non-volatile data and program storage system, with rapid software controllable record/replay/fast-wind functions. The machine, which automatically rewinds to verify everything it records, is designed around the well proven Philips Mini-Digital Cassette Recorder, and is available from Currah. Anyone running a 6502 based microcomputer system who cannot afford disc, yet desires a fairly snappy bulk storage medium, should consider the 220M a viable proposition.

The memory unit jacks quickly into your PET or VIC etc., and will run immediately in command mode (no host software required), or can, of course, be manipulated under program control by your computer. Flags are generated by the unit to allow two-way communication. The interface is activated quite simply by SYSn, whereupon the screen will inform you that you are in conversation with the memory unit's operating firmware (CTOS). With no further ceremony there are twenty-one extra BASIC commands in addition to your existing interpreter's repertoire, such as: BS (Basic Save), BL (Basic Load), OF (Open File) or PD (Print Directory—to identify the tape).

With firmware to handle the technicalities, the 220M may be thought of as a fast intelligent cassette recorder, ex-

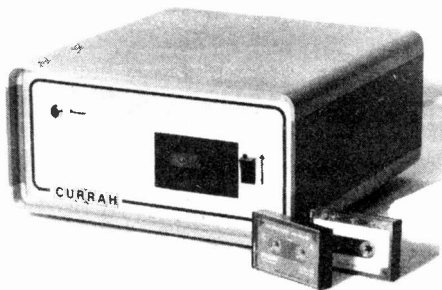cept that it automatically builds up a *directory* of your named files or programs. At the end of a session the directory itself may be *saved*. The operator, therefore, types in which file he wants and the 220M automatically finds and loads it into its Cassette Buffer RAM. This Tardis-like 2K of



RAM is memory mapped into the host computer. Individual variables may be read from a recovered file, and when storing program listings, chunks of software can be appended to each other, thus realising the possibility of a *dynamic* subroutine library.

Encountering the worst access time, when the sought after data is furthest from the directory, rewind might take 60 seconds, but normally would be only a few seconds. Reliability is boasted, and at the time of going to press a version for each of the following machines was anticipated, if not already available:


PET 3000 series, 4000 and 8000, UK101, Superboard, AIM65, Tangerine, VIC20, Atari 400 & 800 and Atom, etc.

The sluggish 300 Baud cassette loading of most rudimentary microcomputers makes them clumsy in response to multifarious needs. The 220M, however, would allow the computer to stand-by with no particular software in RAM, ready to load up and run a selected program promptly. The 220M costs £195, and is available from Currah Computer Components Ltd., Graythorpe Industrial Estate, Hartlepool, Cleveland TS25 2DF. Tel: 0429-72996.

BEAT THAT BURGLAR

To complement their Ultrasonic Burglar Alarm module (featured in News & Market Place, October '81) Riscomp Ltd have now introduced a siren module, known as the SL 157.

This siren module was developed to provide a high level warning signal for use with alarms in a wide range of applications. Its operating frequency has been chosen to provide the highest possible acoustible output when used with the horn type of speaker. It can, however, be used with a conventional type of loud speaker with slightly reduced output. A useful feature incorporated is the inhibit facility whereby the connecting of appropriate pins stops the alarm. This feature means that the module may be used as the basis of simple alarm systems or security loop.

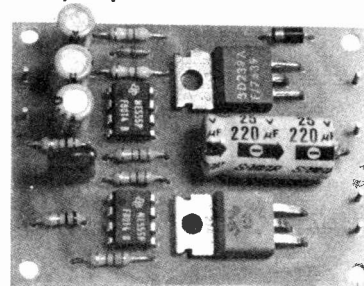

The module operates from supply voltages in the range 9–15V, although with reduced output at 9V. Such a supply may be provided from batteries or a suitable mains unit.

The SL 157 is priced at £12.59 including VAT, plus 50 p.p. It is available direct from Riscomp Ltd., 21 Duke Street, Princes Risborough, Bucks, HP17 0AT (08444 6326)

Countdown . . .

Please check dates before setting out, as we cannot *guarantee* the accuracy of the information presented below.

Seminex Mar. 29–Apr. 2. Imperial College, London. **HI**
 Laboratory Edinburgh Mar. 30–31. Ass. Rooms, Edinburgh. **E**
 CAD Mar. 30–Apr. 1. Metropole, Brighton. **Z1**
 Sensors & Systems Mar. 30–Apr. 1. The Forum, Wythenshawe, Manchester. **T**
 ETM Mar. 30–Apr. 1. The Forum, Wythenshawe. **T**
 Peripherals Mar. 31–Apr. 2. West Centre Hotel, London. **Z1**
 Laboratory Manchester Apr. 7–8. New Century Hall, Manchester. **E**
 All Electronics Show Apr. 20–22. Barbican Centre, London. **E**
 Communications Apr. 20–23. NEC Birmingham **I**
 BEX Brighton Apr. 28–29. **K**
 Compec Europe May 4–6. Centre Int. Rogier, Brussels. **Z1**


Scotex. Jun. 8–10. Roy. Highland Ex. Hall, Ingleston, Edinburgh. **A1**
 BEX Leeds Jun. 9–10. **K**
 Transducer/Tempeon Jun. 29–Jul. 1. Wemb. Conf. Centre. **T**
 BEX Croydon Jun. 30–Jul. **K**
 Leeds Electronics Show Jul. 6–8. University. **E**
 Laboratory London Sep. 14–16. Grosvenor House. **E**
 Two Counties Fair Sep. 15–18. Plymouth Ex. Centre, Millbray, Plymouth, Devon. **T**
 Testmex. Oct. 26–28. Wemb. Conf. Centre, London. **T**
 Compec Nov. 16–19. Olympia, London. **Z1**
A1 Institute of Electronics, Rochdale, Lancs.
E Evan Steadman, Saffron Walden ☎ 0799 22612
HI Seminex Ltd., Tunbridge Wells ☎ 0892 39664
I Industrial Trade Fairs, Solihull ☎ 021-705 6707
K Douglas Temple, Bournemouth ☎ 0202 20533
L1 World Trade Centre ☎ 01-488 2400
T Trident Tavistock ☎ 0822 4671
V SDL ☎ Dublin 763871
Z1 IPC Exhibitions, Sutton ☎ 01-643 8040

ELECTRONIC KITS


Velleman U.K. present their list of electronic kits together with prices which include V.A.T. and postage and packing. They are listed in "difficulty grades", for beginners and experienced kit-builders, with the lower skill level at 1, rising to 3. All include high-quality components, full instructions and technical data and come to you packaged in clear plastic boxes, ideal for component storage.

THE VELLEMAN KIT RANGE

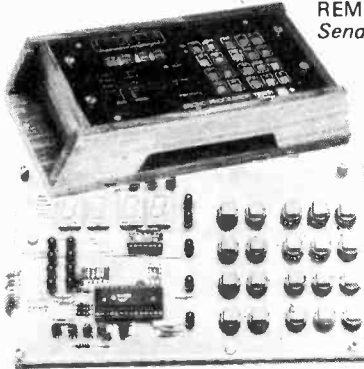
REMEMBER—We offer a free soldering iron with your first order over £10. Send today for the free Velleman Kit Journal.




K1682
Wooden housing extra

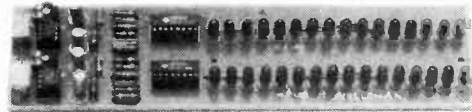


K1798

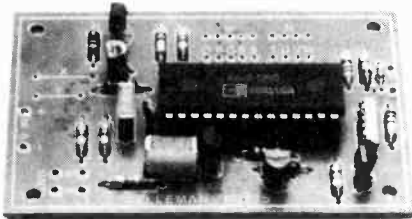


K2575

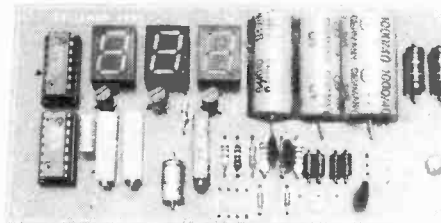

K2557

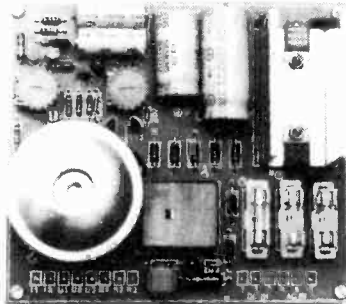


K2551

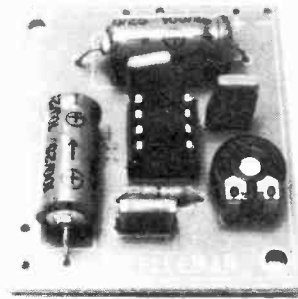

K2569



K2556

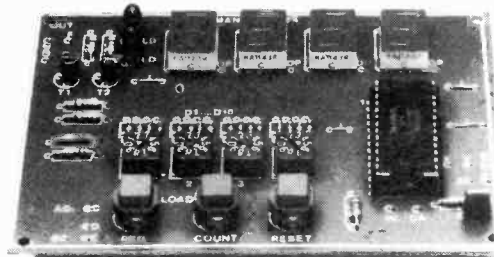

K2574

Difficulty Grade: 1		
K607	2.2W Mini Amplifier	5.00
K611	7W Amplifier	5.14
K612	Dimmer 1000W	5.59
K613	(Disparasite)	12.64
K1716	20W Amplifier	10.32
K1771	FM Oscillator	5.45
K1803	Universal Pre-Amplifier	3.62
K1823	1A Power Supply	6.99
K1861	Power Supply for 60W Stereo	12.94
K2542	Single digit counter	6.90
K2544	Complex Sound Generator	8.28
K2556	CB Power Supply	26.22
K2565	Tape/Slide Synchronizer	9.66
K2566	Coloured Light Unit	15.53
K2569	Three tone Bell	6.56
K2570	Power Supply 5-14V DC 1A	6.56
K2572	Universal Stereo Pre amplifier	6.56
K2573	Stereo RIAA Corrector Amplifier	6.56
K2575	Microprocessor Doorbell with 26 Tunes	15.53
K2579	Universal Start/Stop Timer	6.21
Difficulty Grade: 2		
K610	Mono VU using LED's	8.18
K1798	Stereo VU using LED's	16.91
K1804	60W Amplifier	15.15
K1874	Running Light Unit	12.56
K2543	Transistor Ignition	9.97
K2549	Infra-red Detection System (Transmitter)	10.63
K2550	Infra-red Detection System (Receiver)	12.42
K2553	FM Stereo Decoder	11.49
K2557	Digital Precision Thermometer	26.57
K2571	Light Computer	36.23
K2574	Four-digit up/down counter with comparator	34.16
K2576	40W Audio Amplifier	12.80
K2577	Universal AC Motor Speed Control	7.59
Difficulty Grade: 3		
K615	High Precision Stopwatch	43.13
K1682	Microprocessor Universal Timer	48.37
K2545	50Hz Crystal time Base	11.39
K2547	Four-channel Infra-red Remote Control (Transmitter)	17.32
K2548	Four-channel Infra-red Remote Control (Receiver)	23.12
K2551	Infra-red Central Alarm Unit	18.70
K2554	High quality FM Tuner	22.67
K2555	Digital Frequency Counter for Receiver	37.74
K2558	FM Stereo Receiver with housing	120.23
K2559	Two channel IR Remote Controlled Light Dimmer (Transmitter)	17.32
K2560	Two channel IR Remote Controlled Light Dimmer (Receiver)	38.64
K2562	Infra-red Receiver for K2558	30.02
K2563	Infra-red Transmitter for K2558	18.11
K2567	20CM Display (Common Anode)	21.05
K2568	20CM Display (Common Cathode)	21.05
K2578	Microprocessor Controlled EPROM Programmer	241.50



VELLEMAN UK Limited

P.O. Box 30, St. Leonards-on-Sea, East Sussex TN37 7NL Tel: Hastings (0424) 753246

TRADE ENQUIRIES WELCOMED

FREE Soldering iron
with your first order of £10 or over

Offer ends 31st March, 1982



Please send me your free catalogue of Velleman electronic kits:

Name

Address

PE

STEREO CASSETTE DECK part 1

ANOTHER SEPARATE FOR THE PE QUASAR STEREO SYSTEM

THE PE Stereo Cassette Deck is a versatile low cost system designed around a single p.c.b. The unit has the unusual facility of a variable bias control for optimum recording of all types of tape.

In addition to the basic circuitry a f.e.t. Gate Noise Reduction system has been designed which works on playback in two modes: Flat, all noise reduced in the absence of any signal, and High Frequency, only h.f. noise is reduced at low or no signal levels. This system has proved highly effective with all types of tape; its operation is more fully described later in the text.

The unit is also unusual because most of the switching is carried out electronically, thus reducing the need for complex, noisy and often unreliable switches on the deck mechanism. This design feature enables the p.c.b. to be used with almost any deck since it does not have to be closely coupled to the mechanism for switching purposes. The p.c.b. design is additionally simplified by the use of a LM1818 low noise i.c. in each channel. This i.c. carries the record/play logic switching, pre amps for record and play and VU meter drive. The i.c. also contains an auto record level circuit which is not employed on the p.c.b. shown but can be added as an addition if required—details are given later.

TAPE RECORDING SYSTEM

RECORD: The record/playback and erase heads are inductors with circular metal cores. The cores have narrow gaps at the point of contact with the tape, so that the tape coating

provides a low reluctance path to complete the magnetic circuit. The input signals are suitably amplified and are fed to the head, which converts them into a varying magnetic field. As the tape moves across the tape head gap the coating becomes magnetised.

Essentially there are two important factors required for recording:—

BIAS CURRENT: As well as the audio signal a constant frequency above the audio spectrum (50 to 200kHz) is passed through the head. Its amplitude determines the "operating point" of the magnetic recording process. Its function can be compared to the biasing of a transistor. Incorrect biasing in either case will result in distortion, signal deterioration etc. in respect of the tape head severe h.f. loss will also occur.

FREQUENCY EQUALISATION: During recording the record head current is to be boosted at a rate of 6dB/octave below a standard low frequency, and attenuated by 6dB/octave above a standard high frequency. During playback the low frequencies are attenuated and the high frequencies are boosted so that the overall record/playback frequencies are flat. There are several standard sets of turnover frequencies—CCIR, NAB, EIA and DIN. The cassette equalisation standards defined by DIN are the most commonly used; for ferric oxide cassettes it specifies 3dB frequencies of 50Hz (3180 μ s) and 1326Hz (120 μ s). The upper turnover frequency for CrO₂ type tapes is 2274Hz (70 μ s). On the Quasar a separate switch is provided for selecting the equalisation. With CrO₂ type tapes a higher bias current is required for correct "operating point".

PLAYBACK: The recorded flux on the tape induces a proportional current in the playback head. Since the head is inductive it will have a voltage amplitude response that increases by 6dB/octave of frequency. The playback amplifier provides the equalisation necessary to obtain a flat frequency response and sufficient gain to raise the head signal to a usable level.

OTHER CONSIDERATIONS: In an "ideal" magnetic recording system the use of the described complementary equalisation would result in a flat record/playback frequency response. There are several losses and errors associated with tape recording and these must be compensated for.

GAP LOSS (OCCURS ON PLAYBACK): The easiest way to compensate for gap loss is to make use of the head's inductance by tuning it with a capacitor to resonate at approximately 12kHz. During record mode this capacitor must be made ineffective.



TAPE THICKNESS LOSS (OCCURS ON RECORD): Tape thickness loss occurs when the tape coating thickness becomes significant compared to the recorded wavelength, resulting in a 6dB/octave high frequency roll-off. The DIN standard equalisation compensates for this.

BIAS ERASURE (OCCURS ON RECORD): If an excessive bias current setting is used for the record head it will cause high frequency erasure.

BIAS NOISE: This occurs due to the characteristics of the bias oscillator. Any d.c. current flowing through the record head will be modulated as would a signal. Although it is d.c. its noise spectrum will extend into the audio range. An a.c. bias signal can cause an effect similar to d.c. if the a.c. signal contains even harmonics of the fundamental frequency. Distortion, variations of frequency and amplitude of the recording bias will also result in undesirable modulations. To avoid these problems a well designed bias oscillator circuit is essential.

TAPE MODULATION NOISE: Ideally the coating on a piece of recording tape should be perfectly smooth. However in practice this is not the case. As the tape moves past the head variations in the coating thickness causes rapid changes in the tape speed. This modulation causes noise "sidebands" around the audio signal frequency. To minimise this problem always use good quality cassettes.

NOISE REDUCTION SYSTEM: In terms of signal-to-noise ratio the cassette deck is normally the poorest link in the home audio set-up. There are several types of noise reduction systems, each with their own particular drawbacks. Some are so expensive and complex they make the rest of the circuit appear like a "crystal set"—all just for a few extra dB's of noise reduction. For evaluation purposes only, these systems were tried out with the Quasar. Likewise the D.N.R. (dynamic noise reduction) employing dual i.c. and several transistors (per channel) gives the magical few extra dB's at the expense of h.f. loss. Indeed the effectiveness of the D.N.R. was not unlike the function of an h.f. filter.

After careful consideration and objective listening it was decided that the noise was acceptable during quiet passages but was disconcerting during no-signal conditions. From this it was obvious some sort of "gating" that is synchronised to the output signal on playback would offer the best compromise between cost, availability of components, and effectiveness. Indeed under no-signal condition this form of noise reduction beat even the most sophisticated systems hands down.

SPECIFICATION

Mechanism with automatic stop and tape counter with reset button.

Tape Speed: 4.76cm/sec. (1 7/8 in./sec.).

Wow & Flutter: Typically 0.1%.

Drive Motor: 12V d.c. with electrical governor.

Play Torque: 40-75g/cm (DYNAMIC).

Rewind & Fast Forward Torque: 60-140g/cm (STATIC).

Rewind & Forward Time: Less than 100 sec. for C60 tapes.

Bias/Erase Oscillator: Externally variable, frequency 90-100kHz.

Output: (Adjustable) Up to 1 volt r.m.s.

Mic. Sensitivity: 1mV @ 47k.

DIN Sensitivity: 30mV @ 47k.

Frequency Response: 30Hz-12.5kHz (-3dB).

Signal to Noise Ratio:

Noise reduction OFF -50dB

Noise reduction H.F. -56dB

Noise reduction FLAT -70dB

Cross Talk: Typically -50dB.

CIRCUIT DESCRIPTION

The complete circuit diagram of the Quasar is shown in Fig. 1. The LM1818 is a linear low noise i.c. (Fig. 2) containing all the active components for building a tape recorder (excluding bias oscillator).

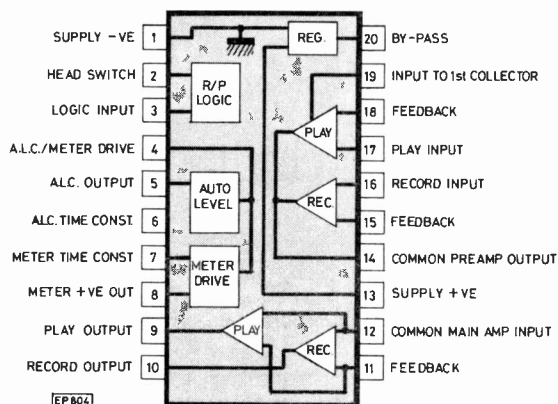


Fig. 2. The LM 1818

The electronic functions on the chip include mic. and playback pre amps, record and playback amplifiers, Automatic Level Control (ALC) and meter driving circuits. Internal electronic switching automatically selects record or play mode. A zero voltage at pin 3 switches on the record mode and a +ve (10V min) switches on the play mode.

RECORD


A recording signal is fed to the switched mic. input socket and when the mic. is used the input is connected directly to the level control VR2. The attenuating network R49 and R50 are connected into the circuit when the mic. plug is removed, thus allowing higher signal levels to be recorded via the 5 pin DIN socket. The input signal to IC1 is via pin 16 and the equalisation network for record and playback is shared. The value of C5 (6n2) and R6 (12k) give the required 70µs DIN equalisation for CrO₂ tape, the addition of R48 (6k8) extends it to 120µs for Fe type tape.

The output of the record pre amp is connected via C12 to pin 4 of the meter/ALC drive and via C11 to pin 12 of the main record amplifier. The amplified output to the head is via C17, L1 and C18; R19 and C22; L1 and C18 form the "bias trapping" circuitry. The resistors R19 and R23 reduce the non-linear effect of the head, while C22 increases the drive at high frequencies (resonance approximately 12kHz). C15 and R15 form a 3000µs equalisation—DIN l.f. end corner frequency. When S1 is in record mode pin 3 is at zero volts and the logic circuit connects pin 2 to earth and selects the record state inside the i.c. S1a also connects R47 to the -ve rail, thus enabling TR9 and TR10 to oscillate at a fixed frequency set by C43. The oscillator output is connected via bias preset PR3 (PR4) and C27 to the head. C27 is low value to prevent "cross-talk" recording between L and R channels.

The erase head voltage is taken from the tapped oscillator coil (L2) and earth with the time constant for meter-drive circuit set by C10 and R13 and the sensitivity via preset PR1. Note that meter is operational on both record and playback states.

PLAYBACK

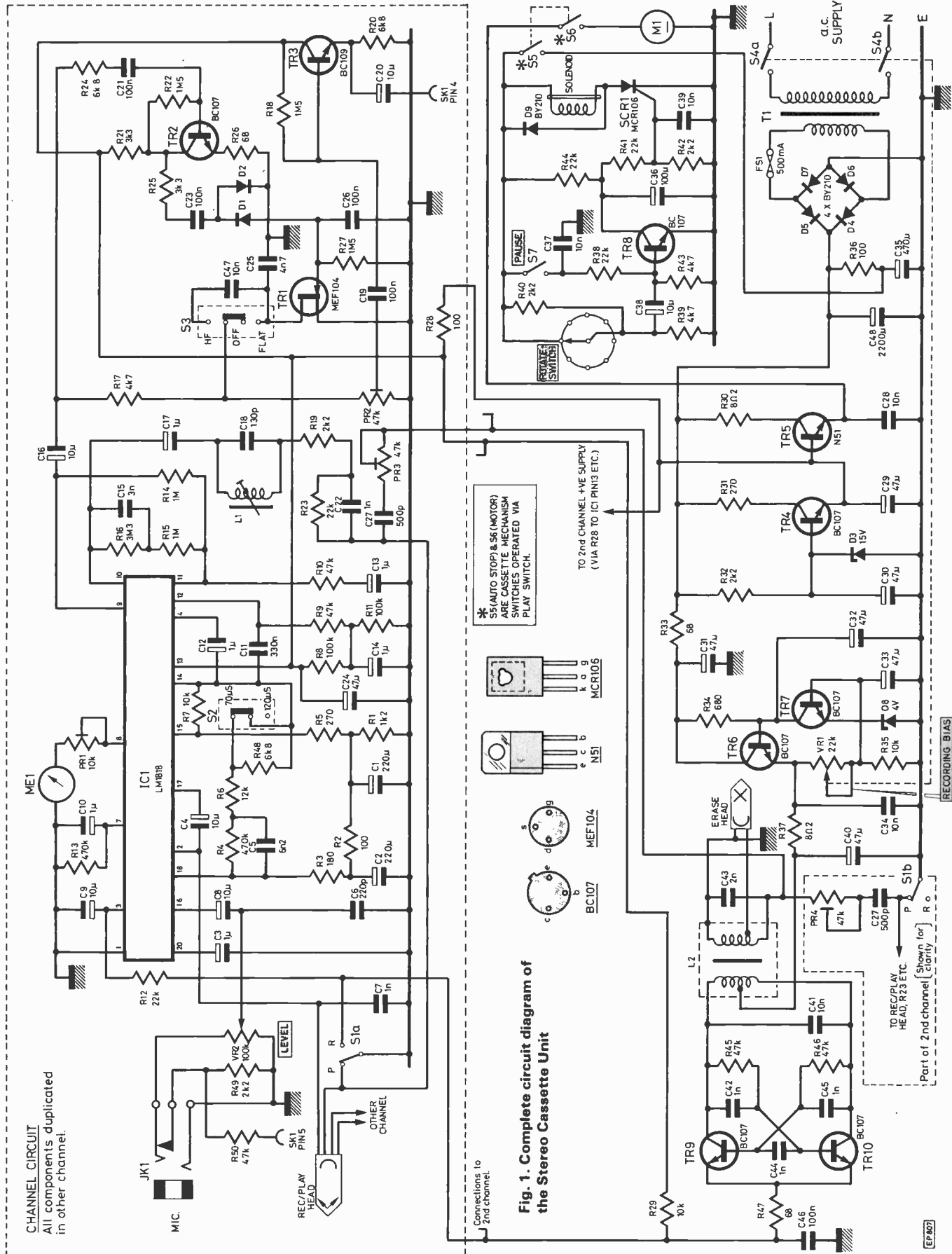In play mode S1a prevents oscillation by removing the earth from R47 and R12, and allowing the leakage voltage to switch the logic at pin 3 to "play" operation. Pin 2, which in record state was grounded, now "floats" and is connected to the play input at pin 17 via C4. The other side of the head



COMPONENTS

Resistors

* R1	1k2 (2 off)
* R2, R28	100 (4 off)
* R3	180 (2 off)
* R4, R13	470k (4 off)
* R5	270 (2 off)
* R6	12k (2 off)
* R7	10k (2 off)
* R8, R11	100k (4 off)
* R9, R10, R50	47k (6 off)
* R12, R23	22k (4 off)
* R14, R15	1M (4 off)
* R16	3M3 (2 off)
* R17	4k7 (2 off)
* R18, R22, R27	1M5 (6 off)
* R19, R49	2k2 (4 off)
* R20, R24, R48	6k8 (6 off)
* R21, R25	3k3 (4 off)
* R26	68 (2 off)
R29, R35	10k (2 off)
R30, R37	8Ω2 (2 off)
R31	270
R32, R40, R42	2k2 (3 off)
R33, R47	68 (2 off)
R34	680
R36	100½W
R38, R41, R44	22k (3 off)
R39, R43	4k7 (2 off)
R45, R46	47k (2 off)

Potentiometers

VR1	22k log combined with pull to make switch
* VR2	100k log slider (2 off)
* PR1	10k preset lin (2 off)
* PR2	47k preset (2 off)
PR3, PR4	47k preset (2 off)

Constructor's Note

A complete kit of parts for the Quasar is available from **R&TVC Ltd, 21B High Street, Acton W3 6NG**, price £32.95 plus £2.75 p&p. The cabinet is £4.50 plus £1.50 p&p.

Inductors

* L1	Bias trap coil (2 off) (22mH adjustable)
L2	Oscillator coil 114 TO 30035

Switches

S1	2 pole play/record
S2	2 way slide s/w
S3	3 way slide s/w
S4	See VR1
S5	} Fitted to cassette mech.
S6	

Miscellaneous

Cassette mech.
Dual VU meter (MEI)
Aluminium top cover
Printed fascia
Bracket for S1
Perspex lid
5 off normal cassette piano knobs
1 off record cassette piano knob
TR1 Mains transformer (18V sec)
Fuse holder and 500mA fuse
Case
5 pin DIN socket (SK 1)
2 off switched jack sockets (JK 1) p.c.b.

* INCLUDES SECOND CHANNEL COMPONENTS

Capacitors

* C1, C2	220μ 16V elect (4 off)
* C3, C10, C12, C13, C14, C17	1μ to 2μ 16V elect (12 off)
* C4, C8, C9, C16, C20	10μ 16V elect (10 off)
* C5	6n2 (2 off)
* C6	220p polystyrene (2 off)
* C7, C22	1n polystyrene (4 off)
* C11	330n (2 off)
* C15	3n (2 off)
* C18	130p polystyrene (2 off)
* C19, C21, C23, C26	100n (8 off)
* C24	47μ 16V elect (2 off)
* C25	4n7 (2 off)
* C27	500p polyester (2 off)
* C47	10n (2 off)
C28, C34, C37, C39	10n (4 off) axial
C29 to C33, C40	47μ 16V elect (6 off)
C35	470μ 25V elect
C36	100μ 16V elect
C38	10μ 16V elect
C41	10n vert.
C42, C44, C45	1n polystyrene (3 off)
C43	2n polystyrene
C46	100n
C48	2200μ 25V

Semiconductors

* D1, D2	Germanium diodes (4 off)
D3	15V Zener BZY88
D4, D5, D6, D7, D9	BY210 (5 off)
D8	4V Zener BZY88
SCR1	MCR 106
* TR1	MEF104 or MEF101 (2 off)
* TR2	BC107 or equiv. (2 off)
* TR3	BC109 or equiv. (2 off)
TR4, TR6 to TR10	BC107 or equiv. (6 off)
TR5	N51 (TIP 31A equiv)
* IC1	LM1818 (2 off)

is earthed by S1. C7 is chosen to resonate at approximately 12kHz—thus compensating for "gap loss" previously mentioned. All other functions are the same as in the record state except the corresponding circuitry is selected inside the i.c. The final output is taken from pin 9 via C16.

G.N.R. SYSTEM (GATE NOISE REDUCTION)

With S3 in the "flat" position R17 and TR1 form a simple potential divider. While there is no signal at the junction of C16 and R17 the f.e.t.s resistance is very low (approximately 100Ω)—thus virtually short-circuiting the output level preset PR2. As soon as the signal arrives, independent of the PR2, it is amplified by TR2. To ensure low voltage rectification D1 and D2 are germanium diodes. They rectify the signal and a doubled -ve voltage appears at TR1 gate, which goes high in resistance, thus allowing the signal from PR2 to TR3. The final output is taken via C20. C26 is the memory capacitor for the gating system.

Note: Without signal and S3 in FLAT position, the G.N.R. will reduce all unwanted hum or noise to almost an inaudible level, whilst in h.f. position the higher frequencies will be reduced at low or zero signal only.

AUTO STOP

The rotate switch is an integral part of the deck and is located under the "take up" mechanism. While rotating it is intermittently supplying a d.c. positive voltage to C38. This appears at TR8 base as a square-wave, saturating the transistor and only a very low voltage (Vbe) will occur at the

collector. As soon as the switch stops rotating (end of tape) TR8 ceases to conduct and the collector goes "high", and SCR1 is triggered by R41. Immediately the solenoid operates releasing the function keys (PLAY, F.F. or R.W.). The deck switches S5 and S6 also return to the OFF position. During the pause the pinch wheel on the mechanism is partly disengaged and S7 provides a +ve voltage via R38 to hold TR8 in saturated state.

POWER SUPPLY

The rectified output is decoupled by C48. C35 is a "storage" capacitor for the auto stop circuit. The value chosen enables enough energy to be stored (through R36) for one operation of the solenoid. TR4 regulates the voltage to the i.c.s and the G.N.R.

The same voltage is current amplified by TR5 to provide the motor supply. Under normal use TR5 can be operated without a heatsink but a small heatsink may be attached if excessive rewind or fast forward operation is required. (Note: the tab of TR5 is internally connected and must not be shorted to earth nor any other component.)

Transistors TR6 and TR7 form the variable-regulated supply for the bias oscillator; with D8 (4V Zener) it will vary the voltage from 4.5 to 15.5V. When VR5 and VR6 are set correctly the bias oscillator voltage at the head will correspond to the calibration around VR1. R29 ensures correct record/replay logic switching should the bias oscillator supply be below 10V.

NEXT MONTH: CONSTRUCTION

**next
month...**


**SPECIAL TEST GEAR
ISSUE!**

SIGNATURE ANALYSER

FUNCTION GENERATOR

FREQUENCY METER

Plus... FREE SUPPLEMENT

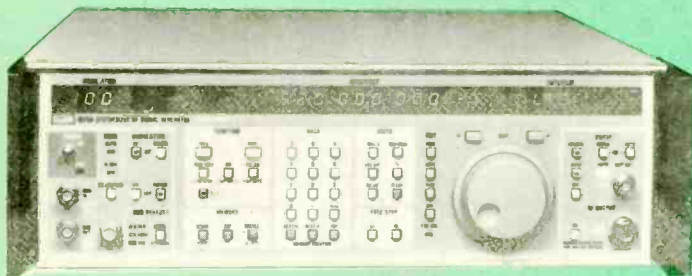

**IEEE-488/IEC-625
INTERFACE BUS
AND AUTOMATIC
TEST EQUIPMENT**

PRACTICAL

ELECTRONICS

MAY ISSUE ON SALE THURSDAY APRIL 8th

ULTRASONIC VISION SYSTEM

PART 1

Jeremy Bentham & Fred Bentham

THE ROBOT AGE is drawing closer, but the general use of robots is held up because of one major problem: how can a machine "see" the world around it? Research laboratories the world over are working on the problem, yet the systems produced are either elaborate and expensive, or simple and ineffective. This project is an advanced ultrasonic vision system which is within the means of the amateur constructor, yet is sophisticated enough to enable experimentation with computer measurement, image recognition, object tracking, and robot vision.

The use of ultrasonics for imaging is by no means new. It has long been known that bats emit ultrasonic squeaks, and use the resulting echoes to determine the range and position of nearby objects. Man has widely imitated this process, and many designs have been published for simple ultrasonic echo-rangers. Yet these designs ignore two important features of a bat's vision system that make it so accurate.

Firstly, a bat does not transmit a burst of one single frequency, since this frequency may be cancelled out due to the shape of the target. Instead, a burst of many different frequencies is transmitted, so that complete cancellation is unlikely. Secondly, a bat can intelligently move so as to determine the bearing of an object of interest. This permits a map of the surroundings to be formed.

This project incorporates these two improvements so as to form an ultrasonic vision system. The system consists of a rotating transducer unit, and an interface circuit. The system

is designed to be coupled to a home computer, which processes and displays the incoming data. Depending on the complexity of the software written, the display can be anything between simple range and bearing information, or a complex radar-type plot. There is tremendous scope for experimentation with the way the incoming data is used: in view of the impending arrival of domestic robots, the unit might well find application as a robot vision system.

HARDWARE AND SOFTWARE

The vision unit consists of a circuit board, an ultrasonic transducer, and a stepper motor. The unit is designed to plug into the printer port of an Acorn Atom, but it can be driven by any computer with five output lines and one input line (5 volt logic). The unit can be powered from an external 5 volt supply, or from an unregulated supply using the optional on-board regulator. Simple driving software for the Atom is described in Part Two. A typical scan of a room using more complex software and the Atom hi-res graphics is shown in Fig. 4. It is hoped to make this software available on cassette.

DESIGN

In order to make the system as flexible as possible and to minimise the amount of hardware, it was decided to implement most of the required functions in software. This means that the computer generates the transmit pulse sequence, times the returning echoes, and generates the stepper motor signals. The hardware amplifies the transmit pulse sequence, processes the received echoes, and amplifies the motor drive signals.

Fig. 3 is a complete circuit diagram of the unit. The transmit pulses emerge from bit 6 of the Atom printer port as a normally low signal, pulsed high at the transmit frequency. This signal is fed to the base of TR1 via C1, which blocks any continuous d.c. signal. The high pulses turn on TR1 and drive T1 which is a transformer broadly tuned to 50-60kHz. During transmission the inductive "kick-backs" from the primary are collected by D5 so as to charge up C5 to about 8 volts. This voltage is used as a supply for IC1,2, since they require more than 5 volts. Approximately 350V peak-to-peak is produced by the secondary of T1 to drive the transducer. As the transducer is of the capacitive type, it also



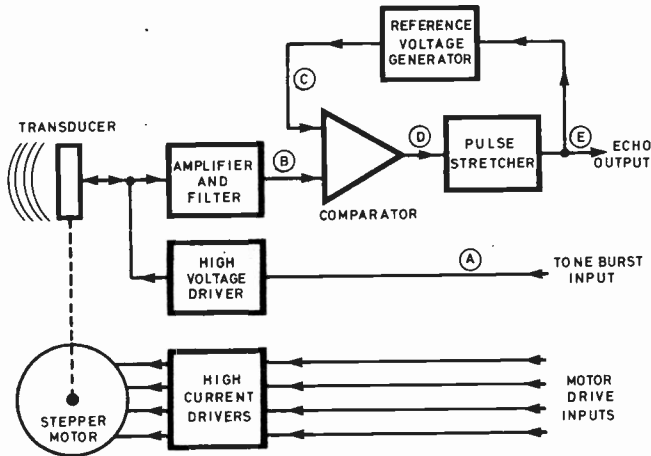


Fig. 1. Block diagram of system

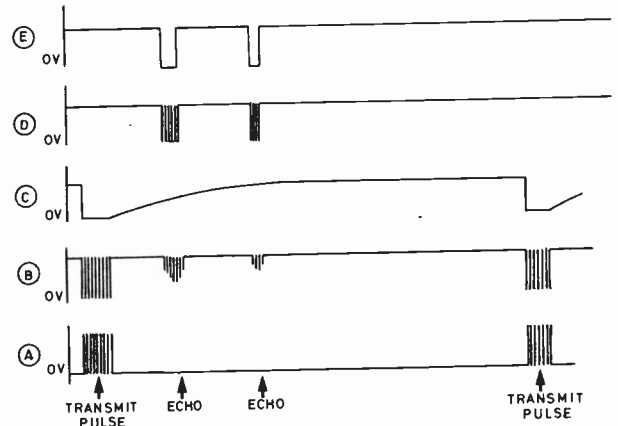


Fig. 2. Echo pulses

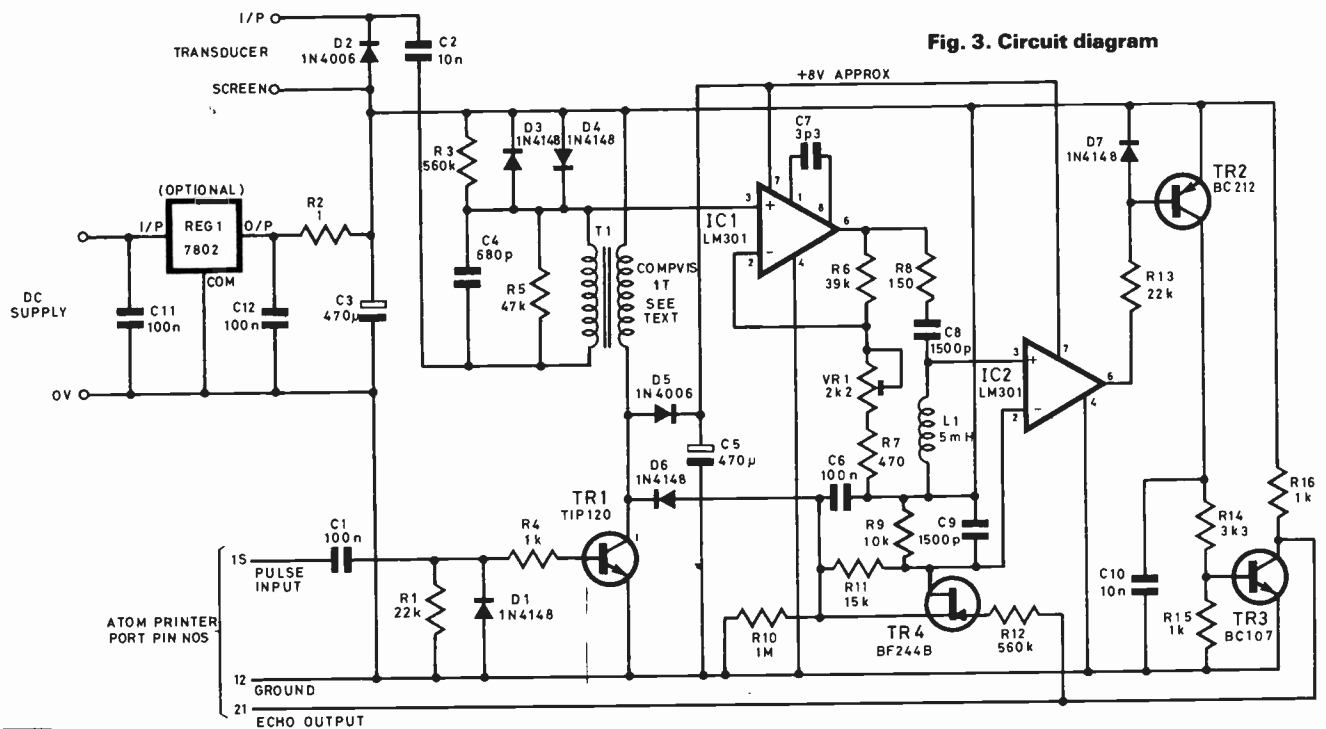



Fig. 3. Circuit diagram

requires a d.c. polarising voltage, which is supplied by D2 and C2. When the transmission has finished, the oscillations die away quickly due to the damping resistor R5, and the transducer can start receiving.

Echoes picked up by the transducer generate a small signal, which may be as low as 100 microvolts for a distant object. For amplification, the conventional 741 op-amp cannot be used, since it has inadequate gain at 60kHz. Instead, an LM301 is used, and it requires an external compensation capacitor C7. IC1 provides a voltage gain between 20:1 and 80:1 depending on the setting of gain control VR1. The output of IC1 feeds a 60kHz series tuned circuit. As those of you who have studied a.c. circuit theory will know, the tuned circuit not only filters out signals outside the passband, but also acts as a voltage multiplier at the resonant frequency. Since R8, C8, L1, give a Q-factor of approximately 10, we obtain a further voltage gain of 10 around 60kHz.

The amplified and filtered echo is fed to the non-inverting input of IC2, and a reference voltage is fed to the inverting

Fig. 4. A radar-type scan generated by the ultrasonic vision system. A "slice" view at about the height of the back of the chair is produced here

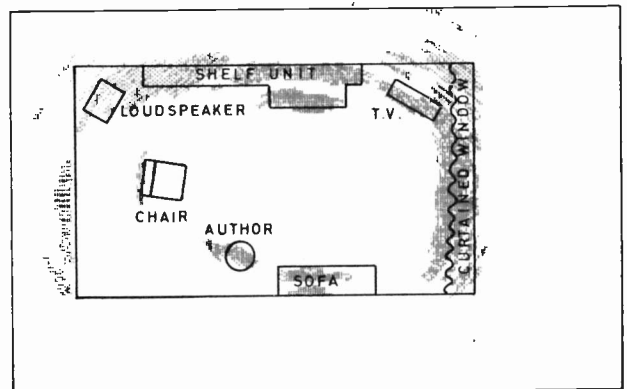

EG 808


input. The op-amp acts as a comparator: if the negative peaks of the received echo are more negative than the reference level, the output pulses low. Thus a stream of low pulses at the output indicates that a valid echo is being received. These pulses are fed to TR2, TR3 which stretch the individual pulses so that one echo is seen as one long pulse. (See Fig. 2). These echo pulses are fed into bit 7 (the most significant bit) of the atom printer port. The input is normally high, and is held low for the duration of each received echo.

From the above description it can be seen the reference voltage at the inverting input of IC2 determines the overall sensitivity of the system: if the reference voltage is at 0 volts, the system is least sensitive, and if it is nearly 5 volts, the system has maximum sensitivity. Components D6, C6, C9, R9, R10, R11, R12, TR4, all control the reference voltage so as to give the following features:

1) Hysteresis. When an echo is received, the field-effect transistor TR4 is turned off via R12. This raises the reference voltage, so that the circuit *locks on* to the incoming pulse.

2) Gain profile. During transmission, the switching of TR1 causes C6 and C9 to charge via D6, holding the reference voltage low. During reception, the reference voltage slowly rises as C6 and C9 discharge through R9 and R11. This means that the system gain is low after each transmission, and then slowly rises; this compensates for the fact that nearby objects give bigger echoes than far ones.

Bits 0, 1, 2, 3 of the printer port are outputs for the stepper motor drive. These signals are normally low; when one or more are switched high, the corresponding stepper motor coils are energised. Diodes D8, 9, 10, 11 are to protect the circuit against the inductive kick-back of the coils when de-energising. The stepper motor is a 4-phase unipolar type; although it is a 12 volt motor it is being under-run at 5V to save power. The angle per full step is 7.5 deg., but it can be half-stepped. The required drive signals are described next month.

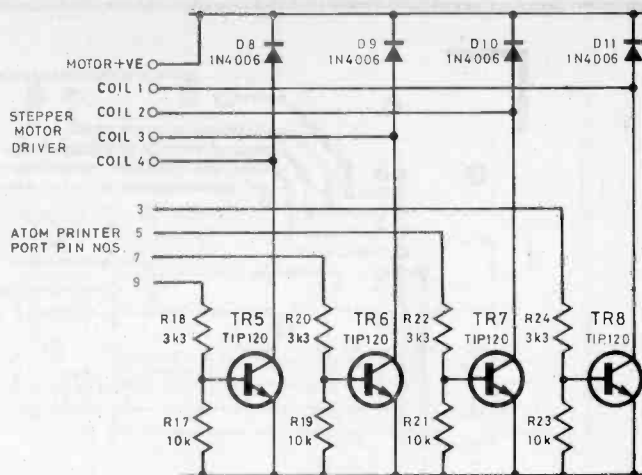

EG804

Fig. 5. Interfacing the stepper-motor to the Atom Printer Port

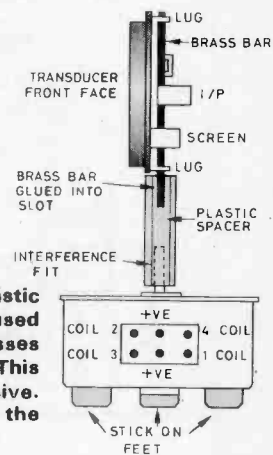


Fig. 6. Mounting the sensor. A plastic spacer with a slot cut in one end, is used to accept the flat brass bar which passes through the transducer's rear lugs. This end of the spacer is joined using adhesive. The other end is a push fit over the motor spindle

COMPONENTS . . .

Resistors

R1, R13	22k (2 off)
R2	½W 5%
R3, R12	560k (2 off)
R4, R15, R16	1k (3 off)
R5	47k
R6	39k
R7	470
R8	150
R9, R17, R19, R21, R23	10k (5 off)
R10	1M
R11	15k
R14, R18, R20, R22, R24	3k3 (5 off)

All resistors ½W 5% unless otherwise specified

Potentiometers

VR1 2k2 min. hor. preset

Capacitors

C1, C6, C11, C12	100n/250V 10% (4 off)
C2, C10	10n/250V 10% (2 off)
C3, C5	470/63V elect. (2 off)
C4	680p silver mica
C7	3p3 sub. min. plate ceramic

Transistors and Diodes

TR1, TR5-8	TIP120 (5 off)
TR2	BC212 (not L version)
TR3	BC107
TR4	BF244B
D1, D3, D4, D6, D7	1N4148 (5 off)
D2, D5, D8-11	1N4006 (6 off)

Inductors

L1	5mH choke (Repanco CH2)
T1	COMPVIS 1T

Integrated Circuits

IC1, IC2	LM301 (2 off)
REG 1	7805 regulator (not supplied in kit)

Miscellaneous

Polaroid ultrasonic transducer
8-pin d.i.l. socket (2 off)
Stepping motor. Impex 9904-112-31004 12 volt
Ribbon cable with 26-way header
30cm of coaxial cable for transducer
Adaptor to mount the transducer
P.c.b. Compvis 1

Constructor's Note

All parts (or complete kit) available from Technomatic Ltd.

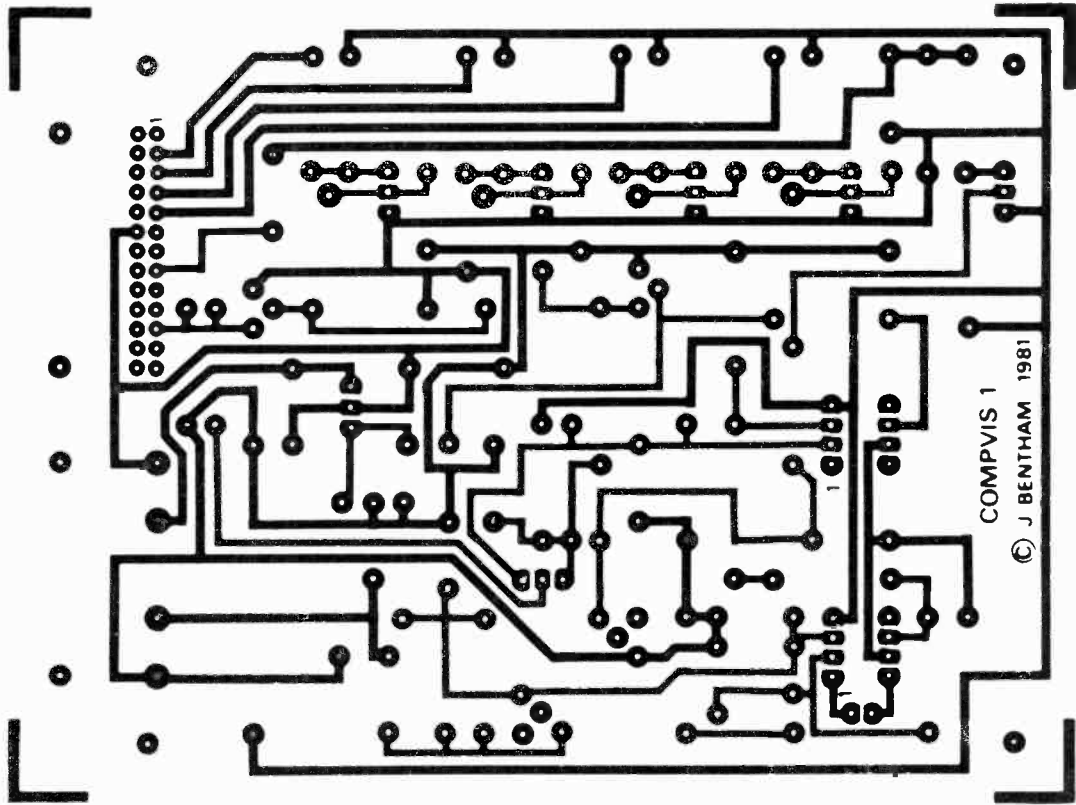


Fig. 7. Printed circuit layout (actual size)

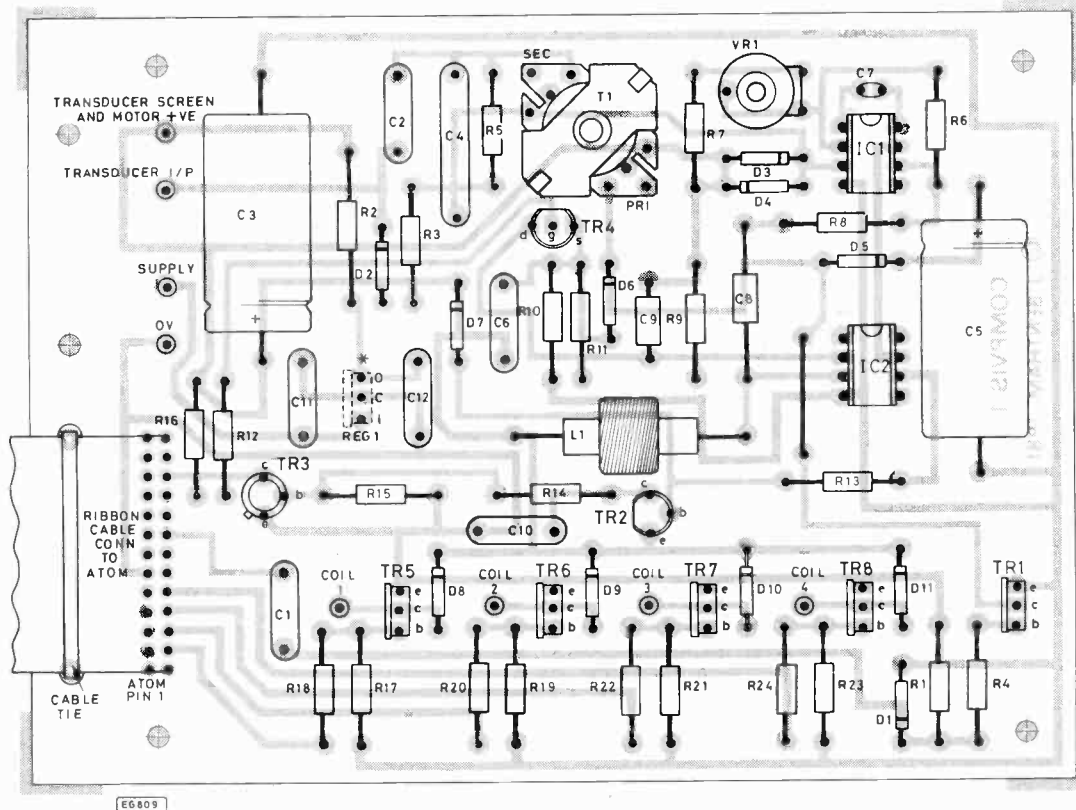


Fig. 8. Component layout

CONSTRUCTION

It is recommended that the p.c.b. be used, otherwise stability problems may occur. Assembly is straightforward, but pay special attention to the diode polarities, and the transistor orientation. The correct orientation for T1 is established by looking at the underside: the primary is wound with thicker wire than the secondary. The regulator IC3 is optional. If a 5 volt regulated supply is available, then IC3 should not be fitted, and its two outer holes on the p.c.b. should be linked together. During transmission, the unit requires 1 amp peak, so the external supply must be capable of this current without distress. For this reason, the supply from the Atom's internal regulators must not be used. The

screened cable must be soldered to lugs which push on to the transducer tabs. Do not solder direct to the transducer, as the heat will destroy it. The recommended length for the transducer cable is 30cm., greater lengths may cause problems. Before connecting the screened cable to the p.c.b. connect it to the transducer and fit the transducer to the motor. Measure the resistance between the centre core and the screen of the cable: it should be infinite, since the transducer does not present a resistive load. When connecting the ribbon cable, note the pin 1 identification on the p.c.b. This should correspond to the bottom left pin of the Atom printer port, viewed from the back.

NEXT MONTH Testing and software.

THE MACROCHIP

In recent years the phrase 'solid state' when applied to electronics has been almost universally equated with integrated circuitry and microminiaturisation. An advance in large scale solid state engineering is about to take industry by storm. This advance however has come from the most unlikely source.

The specialist firm of Puchemm & Long which produces conveyor belt systems for the confectionary trade is about to start production of its new solid state drive mechanism for conveyor belts. The principle is simple, but has required some sophisticated engineering to produce the hardware. The drive mechanism is a linear induction motor which instead of using magnetic induction uses an analogous system of electrostatic induction. A rubberized belt acts as an insulator with a high dielectric constant. A large scale solid state drive underneath the belt develops a rapidly changing pattern of electrostatic charge which induces the opposite charge on the belt above. As the driving charge changes the induced charge above it lags behind so that the two charges repel each other providing levitation and propulsion for the belt. A complex pattern of changing charges produced by the macrocircuit ensure a smooth controllable motion of the belt.

There are many advantages of this system over the conventional mechanical belt drive. Total solid state engineering means that there are no moving parts and hence greater reliability and less maintenance. The elimination of the noise and vibration of previous mechanisms improves the environment of the factory floor. The main advantage for the food industry however is the cleanliness of the system. The lack of moving parts means that 'dirty' lubricating oils can be eliminated from the track and little dust is stirred up by the mechanism.

It is not only on the factory floor that this system will find an application. Already P & L have started work on a personnel transport system. A high power version of the sweet makers continuous belts under development as a moving pavement although there is still a considerable number of problems to be overcome. This farsighted project is only the beginning of what could be a revolutionary move away from the wheel. Plans for the future include an electrostatically elevated and propelled automobile. In this development the drive 'chip' is turned upside down and induces its shadow charge on the dielectric which is the road.

The wheel-less car seems a very adventurous project but the P.L. planning department claim that this is only a beginning. However when pressed for details they would say no more than "The sky is the limit". An expression which may have referred to the fact that air itself has a moderately high dielectric constant, or... What is the dielectric constant of interstellar hydrogen?

See Page 51 for more details.

PE POPULAR PROJECTS...

Our book *PE Popular Projects* containing a selection of popular projects is now available. The book costs £1.25 from retail outlets and is also available for £1.50, UK post paid, or £1.80 overseas surface post paid, from Post Sales Department (PE Popular Projects), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF.

EASIBINDERS

Quick, neat and easy!

It's so easy and tidy with the Easibind binder to file your copies away. Each binder is designed to hold 12 issues and is attractively bound and blocked with the PRACTICAL ELECTRONICS logo. Price U.K. £4.60 including postage, packing and V.A.T. Overseas orders add 25p.

Please allow 3/4 weeks for fulfilment of order. Why not place your order now? Send the completed coupon below with remittance payable to:—I.P.C. Magazines Ltd., Post Sales Dept., Lavington House, 25 Lavington Street, London SE1 0PF.

Order Form PRACTICAL ELECTRONICS

I enclose P.O./cheque value for binders.

Years required

BLOCK LETTERS PLEASE

Name

Address

.....

Date

eb

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.

Sparkrite


BRANDEADING ELECTRONICS

NOW AVAILABLE IN KIT FORM





SX1000 Electronic Ignition

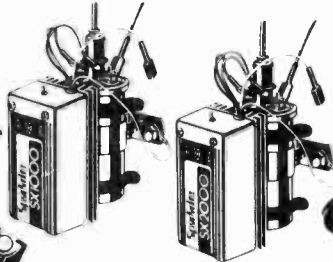- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles





SX2000 Electronic Ignition

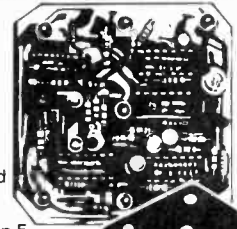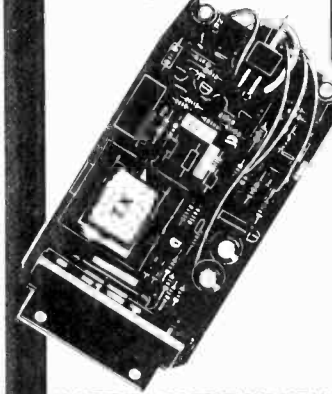- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg. earth vehicles




MAGIDICE Electronic Dice

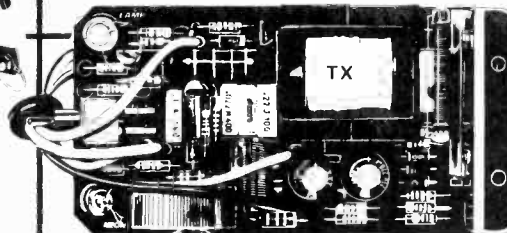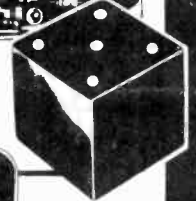
- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble



TX2002 Electronic Ignition

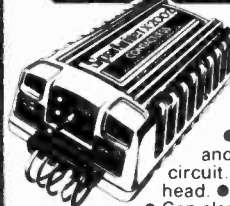

- The ultimate system ● Switchable contactless ● Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge. Combined capacitive and inductive. ● Extended coil energy storage circuit. ● Magnetic contactless distributor triggerhead. ● Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting ● Fits majority of 4 and 6 cylinder 12v neg. earth vehicles
- Over 150 components to assemble

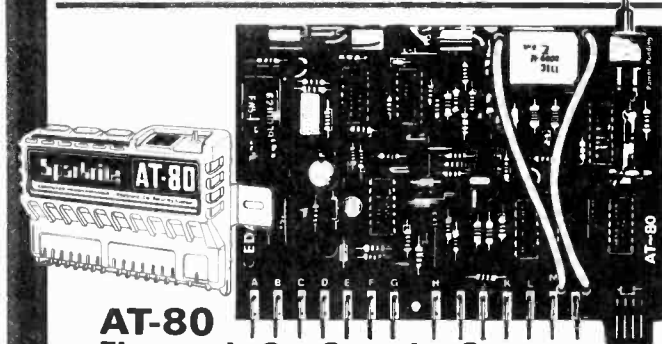


AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen ● Fits all 12V neg earth vehicles
- Over 250 components to assemble

VOYAGER Car Drive Computer

- A most sophisticated accessory ● Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd. ● Affords 12 functions centred on Fuel, Speed, Distance and Time. ● Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on. ● Facility to operate LOG and TRIP functions independently or synchronously
- Large 10mm high 400ft-L fluorescent display with auto intensity. ● Unique speed and fuel transducers giving a programmed accuracy of + or - 1% ● Large LOG & TRIP memories. 2,000 miles. 180 gallons. 100 hours. ● Full Imperial and Metric calibrations. ● Over 300 components to assemble
- A real challenge for the electronics enthusiast!

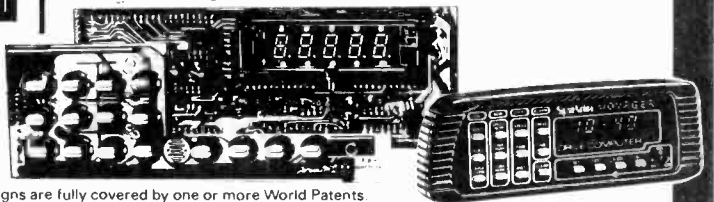

All EDA SPARKRITE products and designs are fully covered by one or more World Patents

EDA SPARKRITE LIMITED 82 Bath Street, Walsall, West Midlands, WS1 3DE England. Tel: (0922) 614791

Please allow 28 days for delivery

NAME _____ PE/4/82

ADDRESS _____

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ _____ KIT REF. _____


CHEQUE NO. _____
24 hr. Answerphone
PHONE YOUR ORDER WITH ACCESS/BARCLAYCARD
SEND ONLY SAE IF BROCHURE IS REQUIRED

	SELF ASSEMBLY KIT	READY BUILT UNITS
SX 1000	£12.95	£25.90
SX 2000	£19.95	£39.90
TX 2002	£29.95	£59.90
AT. 80	£29.95	£59.90
VOYAGER	£59.95	£119.90
MAGIDICE	£9.95	£19.90

PRICES INC. VAT. POSTAGE & PACKING

BRANDEADING BRITISH ELECTRONICS

CUT OUT THE COUPON NOW!

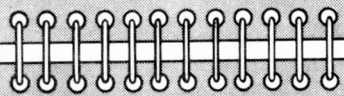

INDUSTRY NOTEBOOK

By Nexus



ASLEF Man

Perhaps unfairly, British Rail's modernisation programme has become a joke. The Advanced Passenger Train (APT) caused much merriment recently when its inaugural passenger runs were plagued with technical problems resulting in withdrawal from service. What should have been a technical triumph, though some years late, turned into a farce.

BR is typical of what remains wrong in British industry. On the one hand there is a dedicated team of scientists and engineers beavering away at Derby on developing and testing up-to-date systems with a view to improving efficiency and service. On the other hand, a trade union structure reluctant to admit any change in practices although paying lip-service to the need for progress.

ASLEF Man is the archetype of out-of-date attitudes. For the benefit of overseas readers, ASLEF is the acronym for the Associated Society of Locomotive Engineers and Firemen with a membership of little over 25,000, a sad decline since the great age of steam when, for example, in 1938 there were close on 20,000 steam locomotives running and only 43 diesel and 13 electric locomotives. By 1960 diesel traction was biting into steam and the switch from steam to diesel and electric traction was completed by 1968.

In some respects we can all sympathise with ASLEF Man. Not only has he declined in numbers but his elite qualities in the railway hierarchy of yesteryear are no longer needed. With steam, the driver and fireman, working as a team, were systems managers. Every locomotive was a self-contained energy converter from coal to heat to steam to tractive effort. There was constant balancing of water levels, firebox temperature, steam pressure, against the varying demands of speed, gradients, wind resistance and the clock. The team watched their gauges and, as part of the feedback loop, had to exercise technical judgement based on long experience throughout the

journey. Starting as a boy engine cleaner, you could hope to be entrusted with an express passenger train by middle age. Apart from the exercise of technical skill, the job was physically demanding, uncomfortable, and dirty.

Modern ASLEF Man, in association with the guard, is responsible for train and passenger safety as before. The rest of his job, in air-conditioned comfort, is less demanding than driving a car. He can't forget he is no longer a locomotive engineer and as long as he can get away with it will insist on having a 'fireman' in his cab, for thus it was always so.

While ASLEF Man dwells mentally in the past, the electronic boffins at BR laboratories are far into the future. Too far, I suspect, because they have an obsession that modern electronics is the solution to everything. This was apparent at a recent IEE conference on Railways in the Electronic Age. It came out that 'old-fashioned' signalling using electro-mechanical relays has reliability and fail-safe characteristics, developed over decades of in-field experience, very hard to improve by electronic switching and control. If this is true, why bother to change? Our experience with automation and modernisation on British Rail has often been unhappy.

The railway boffins are so far ahead with dreams of microprocessor control for everything that they seem to have overlooked one application of electronics, cheaply and easily installed, that could have saved many accidents and deaths. A radio communications link with every moving train. Well, not quite overlooked, for the conference revealed as something quite remarkably novel that one single-track line in the north of Scotland is now so equipped since overhead lines were brought down by snow. What a breakthrough!

With one vital section of the workforce of the railways with heads mostly buried in the sand, and another with heads often in the clouds, it is no wonder the outfit costs the taxpayer £2 million a day to keep going — when it is going.

New Era

'We are well and truly launched into the competitive era' says Sir George Jefferson, chairman of British Telecom, commenting on the new circumstances under which BT has had its former monopoly powers curbed, if not yet extinguished. BT has accepted the challenge and the equipment suppliers will also need to be more competitive to hold their business with their largest single customer.

Nonetheless, wholly British or British-based companies should retain most of the business which will remain substantial for many years to come. Electronic telephone exchanges alone will account for £600 million over the next three years, spread between GEC, Plessey and STC. By then, BT will have spent £750 million on TXE4 and the improved TXE4/4A exchanges with STC alone.

Then there is BT's new digital network, which has already topped 100,000 miles installed, and this is only the start of a

massive digital programme extending through the rest of the decade.

There still remains a big question mark over the highly publicised System X. At home, where BT is full committed to System X, its full implementation according to some forecasts will not be before the turn of the century. This is not a reflection on BT who must, of course, get a full service life from exchanges such as TXE4/4As now being installed. Nor does it mean that subscribers on TXE4/4As will be denied the sort of extra services promised by System X. In fact, further enhancement of TXE4/4As will provide most, if not all, of the facilities of System X.

Where the disappointment arises is in export orders for System X. A business consortium of BT, GEC, Plessey and STC was formed some three years ago to promote exports but no sales have resulted — so far. The Department of Industry has been asked for a grant to adapt System X to better meet overseas requirements but DOI has commissioned an independent study by consultants before committing itself.

Joy in Boredom

When Racal Electronics Group yet again produced a record financial result, half-year pre-tax profits up 45 per cent, the City yawned. What an utter bore, why don't they improve 100 per cent, or even go broke?

The trouble with Racal is that for over a quarter of a century the company has enjoyed a continuous upward growth. None of the dramatic upheavals, the ups and downs so beloved by financial journalists looking for newsy headlines. Racal growth is so regular it has now become routine, if not downright monotonous. And Racal shares have become so blue-chip that they tend to be overpriced. The result is that when, by ordinary standards, Racal produces a cracking result it can even provoke a 'Racal disappoints' comment — Racal shares dropped 33p the day after the results were declared.

The belief that Racal-style management would soon turn Decca round from loss to profit was confirmed in the figures. Most of the increased profit came from the turnaround, although some of the former Decca operations are not yet out of the red.

An interesting sidelight is the theory of horses for courses. Racal is a firm believer in sticking to what it knows it can do best, i.e. capital goods. Thus, having acquired Decca, one of the first tasks was to dispose of the domestic television manufacturing unit at Bridgnorth. This was bought by Taiwan's biggest electronics company, Tatung, who know the consumer side of the business and according to latest reports are making a real go of it, turning loss into profit within six months of taking over, production of TV sets having increased almost five-fold and still accelerating with substantial exports to the European mainland envisaged.


Another thoroughly boring outfit is GEC. Their current export order book stands at over £1,000 million, let alone the healthy home order book plus £800 million cash in the bank. Again, this is expected and causes little excitement.

SPECIAL PE LOUDSPEAKER OFFER.

£43.50

PER PAIR
INCLUDING V.A.T


PLUS £5 POSTAGE
& PACKING

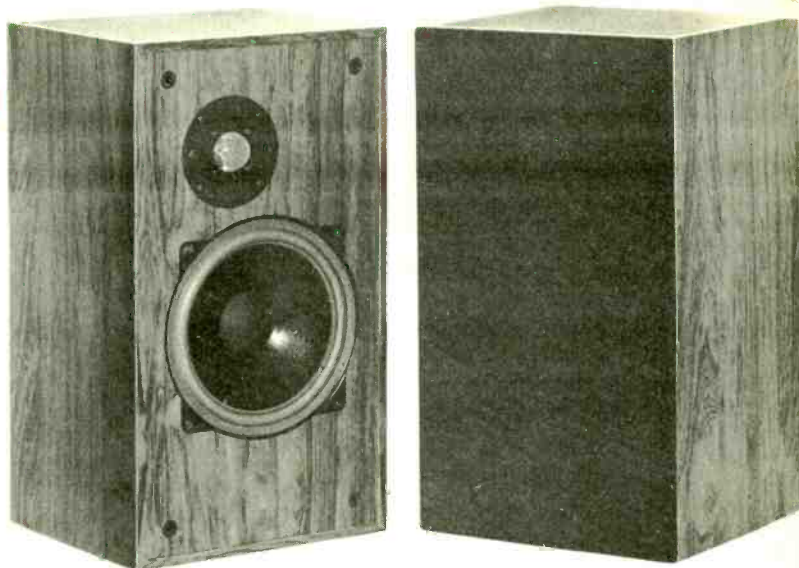

This excellent offer has been arranged by PE as a result of a frustrated export order. The speakers employ Audax drive units and were produced in the UK for a leading European hi-fi company. They are "mirror image" speakers with h.f. drive units mounted to the outside of the sound area.

Specifically designed to meet the need for a high quality moderately sized enclosure these speakers have a high sensitivity, extended bass response and will handle up to 45 watts peak, although they can be used with amplifiers rated as low as 15 watts.

SPECIFICATION: Two way infinite baffle; HIF20ESM bass unit 20cm diam. treated paper foam edged cone; HD100 high frequency unit 25mm soft dome radiator; 8 ohm nominal impedance; 45 watts peak power (35W r.m.s.); 86dB 1 watt 1 meter sensitivity; frequency range 45Hz-22kHz; resonance 80Hz; harmonic distortion ref. 96dB. SPL at 1 meter 3% max. second harmonic 140Hz-22kHz; 1% max. third harmonic 100Hz-22kHz; finished in rosewood p.v.c.; size 470 x 264 x 225mm; capacity 18 litres; weight 8 kilos; connections, DIN sockets and screw terminals.

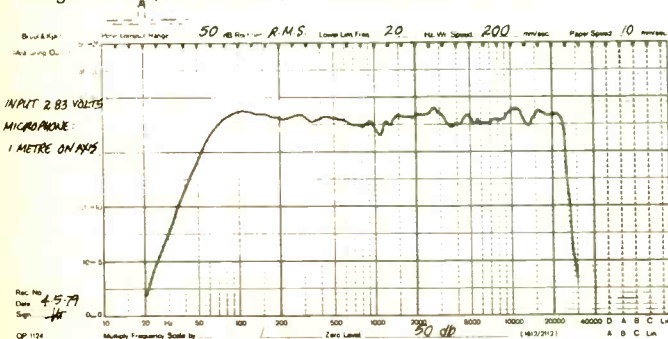

To: RTVC Ltd. (PE OFFER), 21b High St., Acton W3 6NG
(all mail), callers to 323 Edgware Road.

Please complete both parts of the coupon in BLOCK CAPITALS

Please send me pair(s) of speakers at £43.50 plus £5 post and packing (total £48.50) per pair.

I enclose P.O./Cheque No. Value

Make cheques payable to RTVC Ltd.

Name

Address

.

.

Please allow 28 days for delivery
PE OFFER CLOSSES FRIDAY 14th MAY 1982

Name

Address

.

.

From: RTVC Ltd., 21b High St., Acton W3 6NG.



PE ENLARGER TIMER

TOM GASKELL B.A. (Hons) ELEC. ENG.

THIS is a project designed primarily with the photographer in mind, but which could be readily adapted to many other uses. It can act as a straightforward stopwatch, counting with an accuracy of 0.1 seconds up to a total of 999.9 seconds duration; this is primarily for use when processing films or developing prints. It can also be made to count down from a preset number to zero, turning on an enlarger lamp during this counting period. To aid in the 'dodging' of prints (selective shading of part of the enlargement) a once-per-second 'bleeper' is provided; alternatively, the bleeper can be used as an alarm for when the count down period has ended. The count down facility can also be switched to repeat. In this mode, a short bleep is sounded when the counter reaches zero, then the unit re-sets itself to the starting value and counts down again. This arrangement simplifies the exposing of 'test strips'. A safelight socket is provided so that when the enlarger control is in the 'focus' position (continuously on), the safelight is turned off. An enlarger meter can then be used to determine the relative brightness of the negative; normally, such meters are adversely affected by the illumination from a safelight. Finally, a brightness control is provided for the l.e.d. display to allow it to be dimmed sufficiently to prevent fogging of the printing paper. Turning this control fully off also turns off the safelight; ideal for use when colour printing.

CIRCUIT DESCRIPTION

The whole enlarger timer is based on one LSI device, a CMOS 4 decade counter/driver i.c. type 7217. This is a 28 pin i.c. of considerable complexity; it isn't cheap, but it does replace dozens of simpler i.c.s.

The 7217 is, essentially, four up/down counters in one package. It has a built-in multiplexed l.e.d. driver circuit, which is fully buffered to remove the need for any external transistor or i.c. current driving stages. It has a tri-state input/output ('I/O') bus, pins 4, 5, 6 and 7, capable of feeding in an input into the device to preset it, or an output from the device (to supply count data to other external circuitry). We

shall only be using the 'input state' of the bus in this application. The preset information can be used to either preset the counter, or to preset a register which is then compared with the counter; when the two are equal, an output pin of the i.c. changes state. (We shall not be using this latter function, but you may be able to think of other applications for it!)

To provide an accurate source of clocking pulses for the 7217, a clock signal derived from the 50Hz waveform of the mains is used. D28, D29, D30 and D31 form a conventional bridge rectifier to supply the unregulated d.c. to the circuitry, but we also take one a.c. side of the bridge to IC9b, via R21. D25 and D26 limit the voltage excursions to within the supply rails, give or take a diode voltage drop, and C11 helps to filter out noise on the 50Hz waveform. IC9b is a Schmitt trigger NAND gate, which sharpens up the incoming waveform to the correct logic levels, with no noise spikes or other transient effects. IC2 is a pre-settable 'divide-by-n' counter, as discussed in the 'Digital Design Techniques' series. In this instance it is arranged to divide by 5; the \overline{Q}_2 and \overline{Q}_3 outputs are fed back to the data input via IC7a and IC7b. This 'data' signal is the 10Hz waveform used to feed both the clock input to IC1, and to IC3. The latter is a decade counter used merely to divide by 10; the 'carry out' signal from IC3 is a 1Hz square wave used to control the 'bleep' oscillator when in the 'bleep seconds' mode.

IC8c and IC8d are connected as a latch. Pressing the 'start' button causes IC8d pin 11 to go to logic 1, which then enables IC9b and allows IC's 1, 2 and 3 to start counting. When the 'start' button is pressed, IC8c is forced to go to logic 0, causing a negative going pulse, derived by C3, D21 and R13, to feed into IC4c. This is pulse stretched by C5, R19 and D23, and is fed into IC5b. If S6 is in the 'up' position, the output of IC5a is at logic 0, so IC5b is disabled. (Pins 9, 10 and 14 of IC1 all have internal 75k pull up resistors). If S6 is in the 'down/time' position, IC5b inverts the stretched pulse, which is inverted again by IC5d and used to strobe pin 12 of IC1. This loads (i.e. presets) the counter with the values of the BCD inputs to the i.c. The preset inputs are provided by S9, S10, S11 and S12; all BCD thumbwheel ('push-push') switches. These are strobed by the digit strobe outputs of IC1 to ensure that each switch feeds data into IC1 in a multiplexed arrangement, in sequence with the multiplexing of the display. D1 to D16 prevent interaction between switches.

By this means, as soon as the start button is pressed (in the 'down/time' mode) the counter assumes the value determined by the thumbwheel switches, then counts down from that value towards zero. Pin 2 of IC1 goes to logic 0 when the value of the counter output is zero. (This happens briefly when the counter is loaded, so the load pulse on Pin 12 is also used to disable the 'zero' output briefly, via pulse stretcher D27, R16, C4 and IC6c. This has a pulse derived from it by C2, D22 and R15. The pulse is enabled by IC4d in order that no output pulse is generated when the device is being reset to zero deliberately; if this were not done, unwanted effects would occur, for example, 'time-up' warning



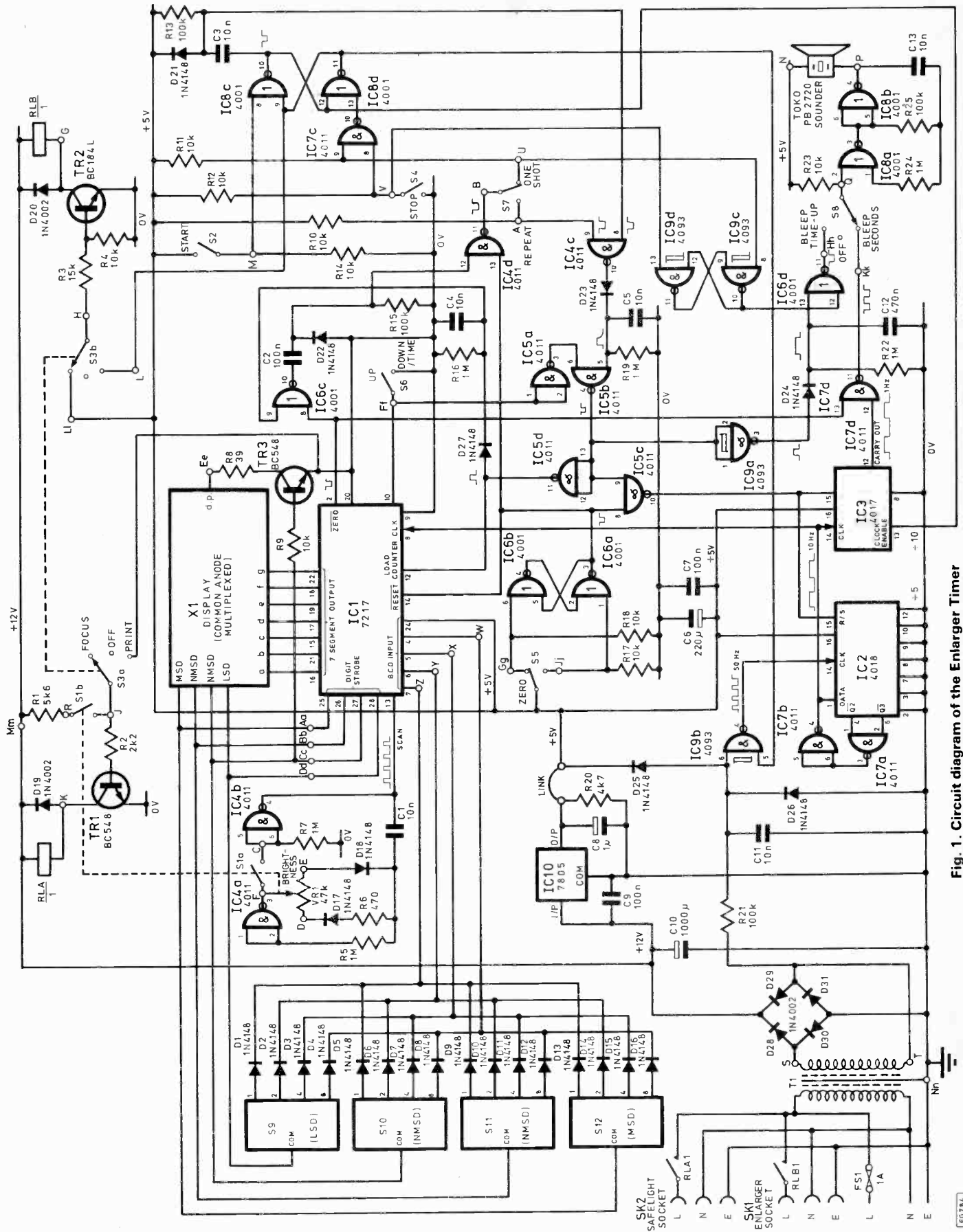


Fig. 1. Circuit diagram of the Enlarger Timer

COMPONENTS . . .

Resistors

R1	5k6
R2	2k2
R3	15k
R4, R9, R10, R11, R12, R14, R17, R18, R23	10k (9 off)
R5, R7, R16, R19, R22, R24	1MΩ (6 off)
R6	470
R8	39
R13, R15, R21, R25	100k (4 off)
R20	4k7

All resistors $\frac{1}{3}$ or $\frac{1}{4}$ watt, 5% Carbon

Potentiometers

VR1	47k lin., fitted with double pole single throw switch
-----	---

Capacitors

C1, C3, C4, C5, C11, C13	10n polyester (6 off)
C2	100n polyester
C6	220 μ 25V electrolytic
C7, C9	100n 30V disc ceramic (2 off)
C8	1 μ 35V tantalum bead
C10	1000 μ 25V electrolytic
C12	470n polycarbonate for miniature polyester)

Semiconductors

D1 to D18, D21 to D27	1N4148 (25 off)
D19, D20, D28, D29, D30, D31	1N4002 (6 off)
TR1, TR3	BC548 (2 off)
TR2	BC184L

IC1	ICM 7217 (4 decade counter/driver)
IC2	4018 CMOS divide-by-N
IC3	4017 CMOS decade counter
IC4, IC5, IC7	4011 CMOS quad NAND gate (3 off)
IC6, IC8	4001 CMOS quad NOR gate (2 off)
IC9	4093 CMOS quad Schmitt NAND gate
IC10	7805 +5V voltage regulator (plastic package)
DISPLAY XI	4 digit, multiplexed common anode i.e.d. display (or make up from individual common anode 7-segment displays)

Miscellaneous

T1	Mains transformer 9V r.m.s. secondary
1 off	TOKO PB2720 Piezo sounder (available from Ambient)
S2, S4, S5	SPDT pushbutton (momentary) (3 off)
S3, S8	DPDT, centre off, miniature toggle switch (2 off)
S6, S7	SPDT miniature toggle switch (2 off)
Relay RLA,	Miniature relay, 12 volt (nominal) coil, contacts capable of passing 240V a.c. at 1.6A or more
Relay RLB	
1 off	Knob for VR1
1 off	Global Specialties 'Design Mate' case, DMC1
1 off	Piece of red gelatine or perspex (see text)
1 off	Mains fuseholder, FS1, fitted with 1A fuse (slow blow)
2 off	'European' ('reversed') shuttered mains chassis mounting socket, with mating plug halves
S9, S10, S11, S12	BCD thumbwheels, push-push type preferably, with mounting cheeks and a spacer (for the decimal point)
	Threaded spacers, wire, screws, etc., to suit (see text).

bleeps, etc. When enabled, and with S7 in the 'one shot' position, the 'zero' pulse finally feeds into the IC8c, IC8d latch, resetting it and hence preventing any further counting of IC1, 2 or 3. This halting of the count, of course, can also be performed by pressing the 'stop' button, S4.

When S7 is in the 'repeat' position, the pulse-derived 'zero' output of IC1 is fed to IC4c. This has the same effect as pressing the 'start' button did; IC1 is preset to the value on the thumbwheel switches, from which it then counts down. The continual cycle of counting down to zero then jumping to the preset value and counting again, is only stopped by pressing the 'stop' button. The output pin 4 of IC5b (the inverted 'load counter' pulse) is also used to reset IC2 and IC3 via IC5c, and to cause a short bleep to be given out of the sounder. This is done by inverting it via IC9a, pulse stretching it to give a fairly long ($\frac{1}{3}$ rd of a second) pulse with D24, R22 and C12, then using it to gate on and off the 'bleep' oscillator via IC6d and S8.

The bleep oscillator is a conventional two-gate circuit formed by IC8a and IC8b directly driving a piezo sounder. IC9c and IC9d form a latch which is set by the 'zero' pulse (in the one-shot mode only) and reset by the 'stop' switch. The output of this latch, IC9c pin 10, feeds into IC6d, and is used to gate on the oscillator to give the 'time-up' signal. When S8 is in the 'bleep seconds' position, the 1Hz signal from IC3 is on via IC7d only when the counter output is NOT zero; this prevents the tone sounding continuously when the counter stops at zero. IC3 has its clock enabled by the 'stop-start'

latch of IC8c and IC8d, so that the seconds only bleep when the clock is running. The 'zero' switch S5 is contact debounced by the latch formed by IC6a and IC6b; it is a requirement of the 7217 i.c. that its reset input should be very clean, i.e. noise free. As well as resetting IC1 and gating off the pulse derived 'zero' output as already described, the debounced S5 signal also resets IC2 and IC3 via IC5c.

The safelight and enlarger light are both controlled by relays, rather than solid state triac or thyristor circuitry. This has been done because some enlargers (and a few safelights) have a complex and 'unusual' a.c. loading, and can respond badly to the slightly 'chopped' waveform of a solid state switched mains signal. Relay RLA is used to drive the safelight, primarily to obviate the necessity to pass mains voltages through S3a; a safety consideration. Note that S1b is used to switch the safelight off when the brightness control is turned off; S1b and S1a is the double pole switch fixed to the back of VR1.

Relay RLB is used to control the enlarger, and is driven from TR2; chosen to be a BC184L, to ensure that a high enough gain is obtained. Because of the BC184L's high gain, 65mA can be passed through Relay RLB with less than 0.3mA drawn from IC8d. IC1 has an internal oscillator to drive its multiplexing circuitry. In order to provide control over the brightness, though, we must provide an external oscillator with variable mark/space ratio (since this ratio determines the illumination duration of each display digit) and feed this into the IC1 'scan' input. IC4a and IC4b form the

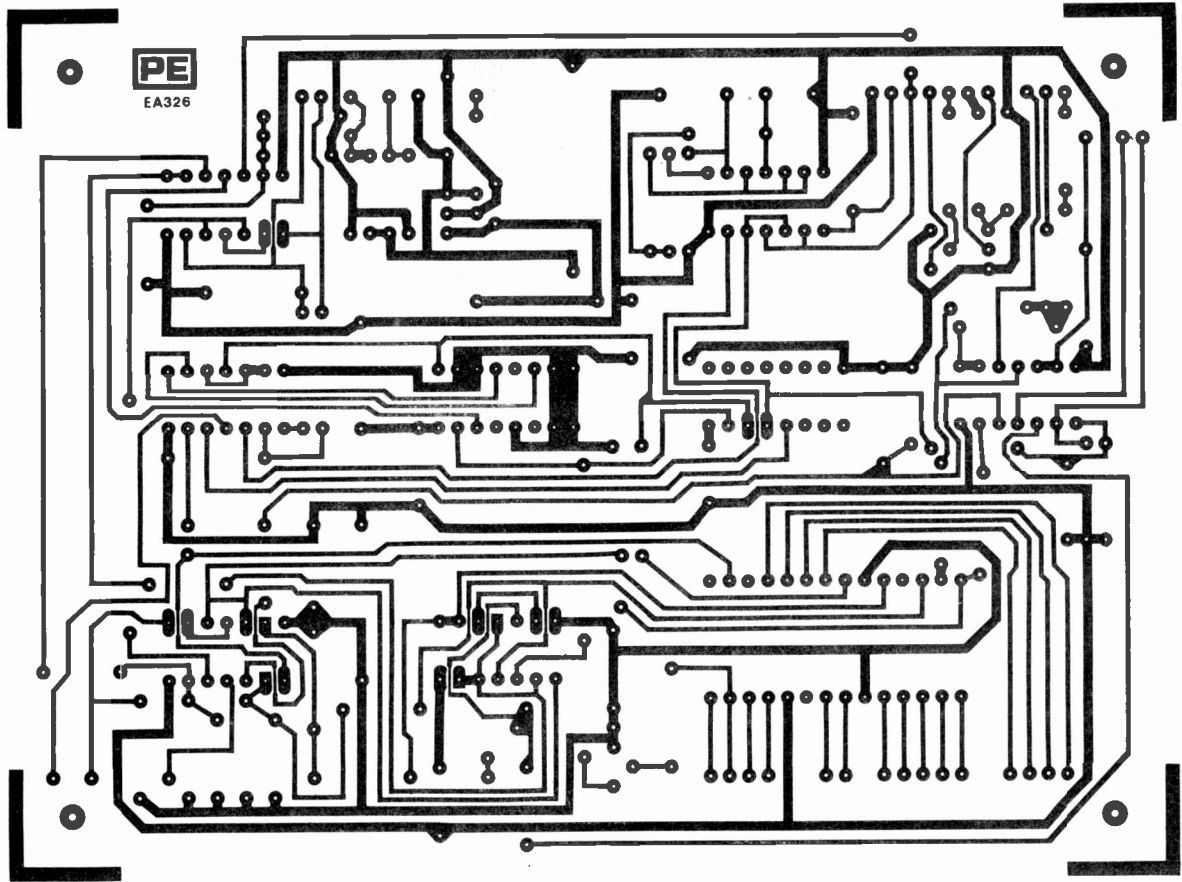


Fig. 2. P.c.b. design

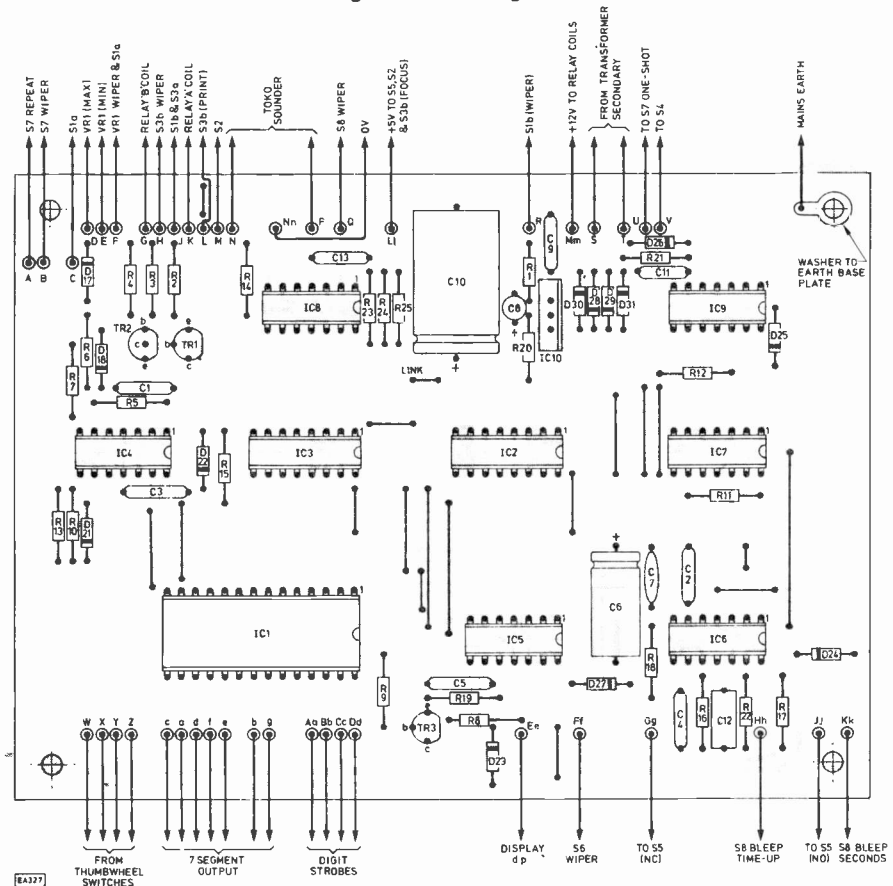


Fig. 3. Component layout

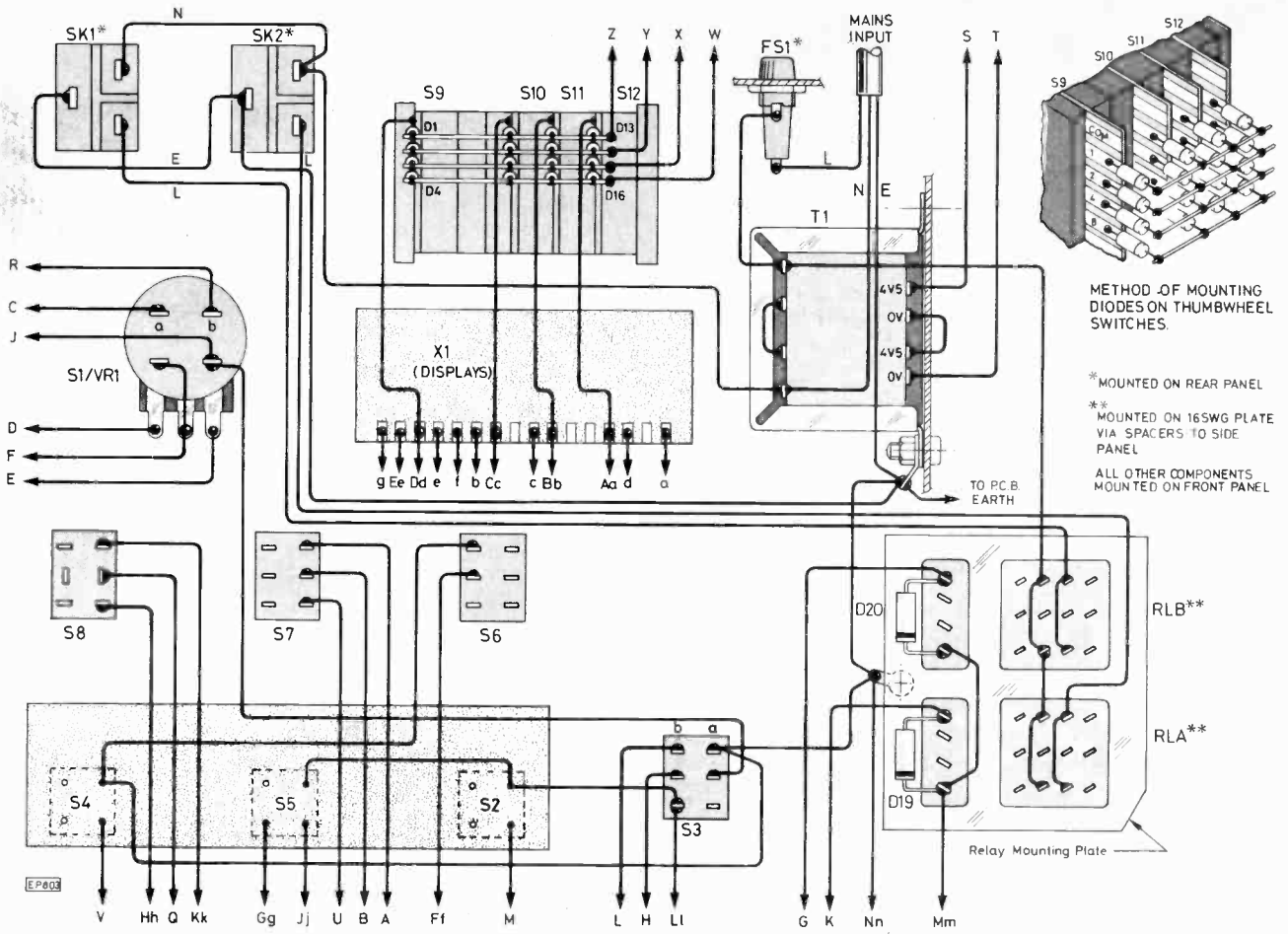


Fig. 4. Wiring diagram

oscillator with VR1 varying the mark/space ratio. S1a fully disables the oscillator for the 'brightness off' position of VR1.


TR3 is used to gate on the 'decimal point' i.e.d. in the display only when the '3rd digit' of the display (units of seconds) is being strobed; this is the only digit of the four which needs the decimal point. Finally, the +5V regulated supply is provided by IC10, a regulator i.c. with C8 and C9 preventing unwanted parasitic oscillations and R20 providing a local guaranteed loading. C10 provides the smoothing for the unregulated d.c. supply, with C6 and C7 providing de-coupling for the +5V supply.

CONSTRUCTION



The p.c.b. design for the Timer is shown in Fig. 2 with the component layout shown in Fig. 3.

The wire links should be added after all the other components with the exception of the +5V supply link, see later. After the p.c.b. has been soldered and checked the case should then be drilled, cut and filed to suit the switches, connectors, display, etc., to be used; see the photographs for a suggested layout. The prototype used p.c.b. mounting switches for stop, start and zero, so these needed a piece of 'Matchboard' held to the front panel of the case by threaded spacers. The two relays, likewise, were mounted on an aluminium bracket held to the side of the case by threaded spacers.

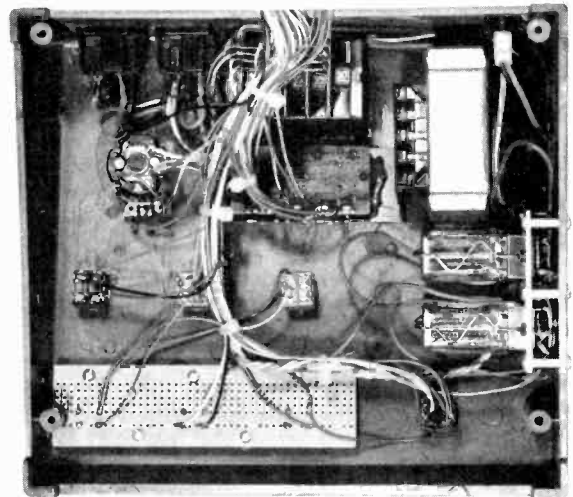The cut-out for the display should have a piece of red tinted 'perspex' or transparent plastic glued behind it. The display can then be supported behind this; the easiest way is



usually to very lightly glue the display to the 'perspex' or plastic sheet, around the edges ONLY, to make removal easy if necessary. (A complete multiplexed, display module is ideal for this. If individual 7-segment displays are to be used they will have to be mounted on a spare piece of Matchboard, and wired together). The aluminium base plate of the case should be drilled to enable the p.c.b. to be screwed to it via yet more of those threaded spacers! The

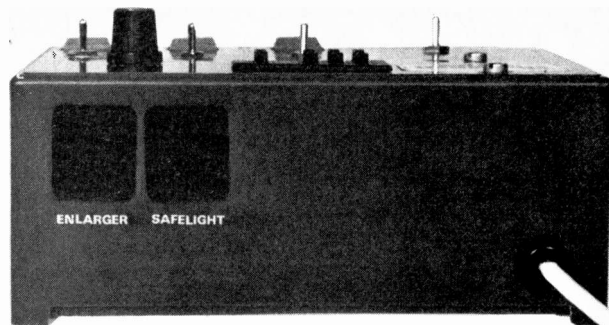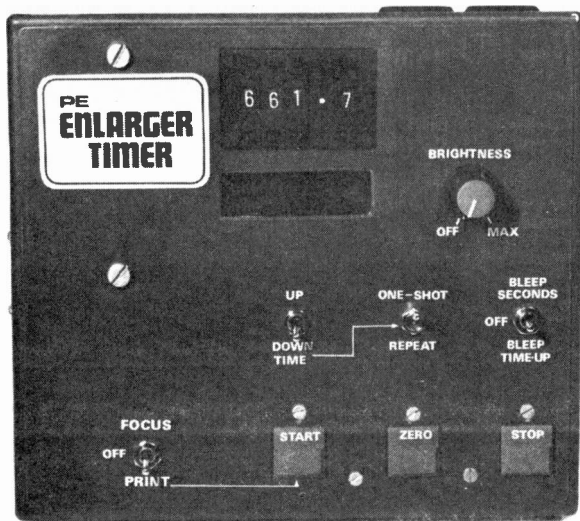

piezo sounder can also be mounted on the base plate, adjacent to the p.c.b., with a hole in the side of the case to let the sound out.

All the component parts should be screwed into the case and baseplate, then the remaining interwiring can be added (Fig. 4). Be careful; there is a lot of this and it is easy to make mistakes. Be especially careful with the mains wiring; keep it well away from the low voltage wiring, and preferably shroud all mains carrying terminals. I suggest that European(IEC) type 'reversed mains' shuttered facility chassis sockets are used for the enlarger and safelight sockets. These are safe outlet sockets for mains distribution,

and are readily available along with their mating halves. Remember to earth all metal parts, e.g. the baseplate (via a washer from 0 volts as shown), the transformer case, etc.

The short wire link between the output pin of the voltage regulator and the +5V supply track of the matchboard is left off initially, so that the operation of the +5V supply can be checked without risk to the expensive IC1! Only when this supply is proved to be of the correct voltage should the link be added. Note that diodes D1 to D16 should be soldered to the switches S9 to S12 directly, with the cathodes joined as shown in Fig. 4. This arrangement is quite robust enough if thick tinned copper wire is used to join the cathodes together. D19 and D20 should be soldered across their respective relay coils directly.

There is no setting up required for the enlarger/timer; it requires only switching on and testing out to make sure that all the functions operate correctly. Although the circuit description may sound complex, the use of an LSI 'chip' the 7217, has vastly simplified the circuitry required to perform all the functions required of such a unit. ★



Avoid a break in the middle

Make sure you get every issue when you're following projects in PRACTICAL ELECTRONICS. Use this order form for a year's supply to be posted to you.

ANNUAL SUBSCRIPTION RATES (including postage and packing) inland and overseas (surface mail) £13.00.

PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Please send me Practical Electronics each month for one year. I enclose a Sterling cheque/international money order for..... (amount).

PLEASE USE BLOCK LETTERS

NAME Mr/Mrs/Miss _____

ADDRESS _____

POSTCODE _____

Make your crossed cheque/MO payable to: IPC Magazines Ltd., and post to: Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH.

Practical Electronics is published in England by IPC Magazines Ltd. Regd. No. 53626. Regd. Office: King's Reach Tower, Stamford Street, London, SE1 9LS. A subsidiary of Reed International Ltd.

THE SENSATION OF THE JAPANESE MUSIC FAIR

Designed by a genius. Controlled by a computer. Programmed by a laser. Played by amateurs professionally and by professionals superbly.

THE NEW CASIOTONE 701

"... what is going to become THE instrument of 1982. ... probably the best instructive keyboard I have come across. But it is also a top line musical instrument capable of satisfying even the most proficient musician. ... I suggest you place your orders now." (*Keyboard & Music Player*)
 "... opens up home music making for all the family ... one of the most advanced music teaching aids so far developed ... this instrument is going to be one of the biggest sellers of 1982." (*Electronics & Music Maker*).



Complete Programmable Polyphonic Keyboard (RRP £555) ONLY £495


- ★ Input an entire piece of music, specially scored in bar code and read by a light pen attached to the instrument.
- ★ Alternatively, program your own melodies (max. 345 steps), chords (max. 201 steps) and tempo, via the keyboard, into the extensive memory, (up to 5 minutes playing or more) with full editing facilities.
- ★ **3-WAY PLAYBACK.**
- 1. Automatic playback of the entire piece; melody, chord, bass and rhythm with arpeggio. Follow the melody as it plays via lamps above each individual key.
- 2. Manual melody playing, guided by the keyboard lamps, with automatic bass and rhythm accompaniment.
- 3. **ONE KEY PLAY** facility, allows the melody line to be played, simply by stroking one key. Non-players can become Instant Musicians!
- ★ The 5 octave, 8-note polyphonic keyboard can be split into 2 & 3 octaves and a different voice can be selected for the accompaniment.
- ★ 20 "breath-takingly clear and bright" pre-set instruments and voices.
- ★ 3-way chord section:—Fingered, Memory and Casiochord auto accompaniment.
- ★ 16 rhythm accompaniments with "fill in" variation and two percussion effect buttons. Start/Stop, Synchro, Tempo and Balance controls. Variable Vibrato and Sustain. I/p & o/p jacks. Integral amplifier/speaker. Music book. AC only. Dims: 5' x 37 1/2' x 13-7/16". Optional extras: Foot pedals. Hard case.

FREE

CREDIT, 0% interest, 1/3 deposit, 12 monthly repayments. (Not MT-31, MT-40, or VL-1), or reduced rates for longer period. INTEREST (0%) on ACCESS, B'CARD or VISA for first 6 months, for any keyboard purchase over £90.

NEW PORTABLE KEYBOARDS

CASIOTONE MT-40

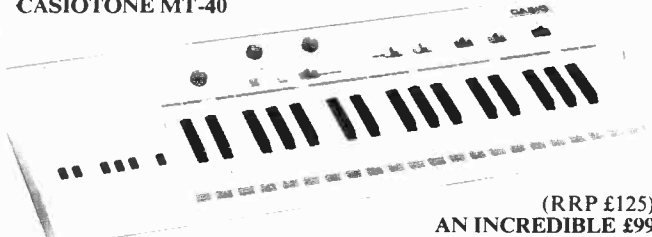

(RRP £125)
AN INCREDIBLE £99

- ★ 8-note polyphonic playing of this 37 key, 3 octave keyboard.
- ★ 15 key bass keyboard with automatic synchronised bass function.
- ★ 22 lively and realistic built-in instrument sounds and voices.
- ★ 6 built-in auto rhythms, with dual "Fill-in" rhythmic interludes.
- ★ Sustain, Vibrato and Pitch controls. Line out and Headphone jacks.
- ★ Integral amplifier and speaker. Battery powered, or optional AC adaptor. Dims: 61-6 x 584 x 178mm (2-7/16 x 23 x 7"). Weight: 2.2kg (4-9lb).

CASIOTONE MT-31



(RRP £79)
ONLY £69

"... basically a revision of the MT-30 (one of my all time favourite electronic keyboards)." *Electronics & Music Maker*.
 Similar to the MT-40 but without the rhythm box, bass and auto functions.
 Dimensions: As MT-40. Weight: 2.0kg (4-4lb) including batteries.

OTHER CASIOTONES

CT-101 £195. CT-202 £275. CT-403 £275. VL-TONE £35-95. Lists on request.

DELIVERY NORMALLY BY RETURN OF POST.

£100 COMPUTER

"Can do the job of a micro costing four times as much!"

Personal Computer World

CASIO FX-702P POCKET COMPUTER



ONLY £99.95

Plus FREE MiCROL Professional Programming Pack (RRP £9.95)
 Or we will beat any lower advertised price by 5%.

Eat your hearts out, H-P, Sharp and Texas!

The Casio FX-702P features: The biggest program storage capacity (up to 1680 steps), the biggest data storage capacity (up to 226 memories), the widest range of math, science and statistics functions (55 in all, including Regression and Correlation), the most powerful English-like BASIC program-writing language and the fastest operation, for results without waiting! Subroutines; 10 levels. FOR: NEXT looping; 8 levels. Comprehensive edit, debug and trace modes. 240 hours battery life. 17 x 165 x 82mm.

FA-2. Cassette adaptor for bulk storage of programs and data, with powerful file name and remote control options. **ONLY £19.95.**

FP-10. Permanent hard copy printer; full 20 character line width, fast 40 character per second print speed, 2,600 lines per roll. (Low cost replacement rolls, £2.50 for five), 6,000 to 9,600 lines battery life. Rechargeable battery pack, NP-4M, prints 13,000 lines (£6-90). Mains adaptor, AD-4150, £5.

FP-10 Printer **ONLY £44.95.**

Plus FREE Pack worth £5, or we will beat any lower price by 5%.

SYSTEM PRICES—Save up to £50 on RRP

PACK A: FX-702P + MiCROL Professional Programming Pack	£99.95
PACK B: FX-702P + FA-2 cassette interface + PPP + PROCOS	£139.95
PACK C: FX-702P + FP-10 Printer + FA-2 + PPP + PROCOS	£179.95

MiCROL PROCOS for the 702P. Exclusive to TEMPUS.

Now you can create powerful, reliable programs in just minutes with this advanced, integrated operating system, even if you have never programmed a computer before! "Visicalc-type" system answers "what if" questions and analyses trends. On ready-to-run cassette, with user manual. **£24.95**

CASIO FX-602P The World's Fastest Programmable?

Alpha/numeric scrolling display. From 32 program steps with 88 memories, to 512 steps with 22 memories, all non volatile. **ONLY £74.95**
 FA-2 £19.95. FP-10 £44.95. (Also compatible with FX-501/2P, and FX-601P).

CASIO FX-3600P low cost programmable.
 38 program steps, 7 memories, INTEGRALS AND REGRESSION. **£22.95**

50M WATER RESISTANT ANALOG/DIGITAL

Alarm chronograph with countdown alarm timer

CASIO AA-92W ONLY £25.95

Analog. Independent hours & minutes, with sync digital seconds. Dual time ability.
 Digital Hours, minutes, seconds, day & date.
 1/100 second stopwatch to 12 hours. Net, lap & 1st/2nd place. Start/stop & 10 min. signals.
 Alarm. For 30 seconds with carousel display.
 Countdown Alarm. Normal and net times to 1 hr. with amazing "Star Burst" flashing display. Half hourly & hourly chimes. Lithium battery. Stainless Steel W/R Case. Mineral glass face.



CATALOGUE ON REQUEST
 14p stamp appreciated

Price includes VAT and P&P. Send cheques, PO, or phone your ACCESS, VISA or B'CARD number to:

TEMPUS

LEADING CASIO SPECIALISTS
 Dept. PE,
 38 Burleigh Street, Cambridge CB1 1DG
 Telephone: 0223 312866

Semiconductor UPDATE...

FEATURING

MC146818 TDS 934 6600

R. W. Coles

MOTEL CLOCK

Anyone who has a disc based home computer such as the TRS80, the Apple or the PET, is probably familiar with the sort of interrupt driven "Real Time Clock" facility which many disc operating systems provide. Personally I have never found this facility at all useful because it is necessary to set the clock to the correct time of day each time the system is powered up and this can become quite a chore. Also, in some software clocks of this type, time is lost during disc access because the interrupts are temporarily disabled by this activity. What is needed is a clock which is independent of the processor power supply and processor interrupts and which will maintain an accurate time and date accessible from any program at any time.

This need has not gone unrecognised and hardware solutions have recently appeared from several CMOS chip manufacturers including National, Mostek, and Motorola. Each company has its own particular clock chip recipe, but for my money, the design which offers most is undoubtedly the Motorola MC146818. Inside the 24 pin plastic package of the Motorola clock chip there is a veritable cornucopia of desirable clock features not matched by any of the other devices available. Hook one of these on to your microprocessor bus and you will gain access to the time of day in seconds, minutes and hours, using either the twelve or the twenty-four hour format, in either straight binary or binary coded decimal (BCD). You get day of the week, date, month and year from a 100 year calendar which automatically compensates for the number of days in a month and leap years, and you also get a programmable alarm scheme which will interrupt the processor once per day or periodically at seconds, minutes, or hourly intervals. Actually, three sources of processor interrupt are provided and can be turned on or off under software control. In addition to the alarm interrupt there is a periodic heart-beat interrupt which can be programmed over the range of 30.5 microseconds to 500 milliseconds, and an "End of Update" interrupt which can indicate that a new time or date is now available. Heart-beat interrupts are particularly useful in microprocessor systems for the generation of the timing signals needed for all sorts of real time activities such as communication and sampling. An added bonus is the availability of a square wave output at the heart-beat interrupt rate.

The MC146818 will run from any one of three crystal frequencies to suit the application, but for lowest power consumption a 32.768KHZ crystal is best. At this fre-

quency the clock chip consumes only about 200 micro-watts of power and will survive for very long periods from a simple standby battery supply even when system power is turned off.

Interfacing the Motorola clock to a microprocessor bus is made easier by a built in "MOTEL" circuit designed to provide control signal compatibility with both Motorola and Intel micros, but since the MC146818 uses a multiplexed eight bit data and address, bus interfacing is easiest to processors such as the Intel 8085 and the Motorola 6805 which also have a multiplexed bus structure. Before long a non-multiplexed version of the MC146818 will be available in a bigger package, but if you are eager to use the MC146818 now, it will only require a few extra gates to interface it to a processor such as the 6800 or the Z80.

The device is very simple to access from a microprocessor program since the clock registers appear within 64 bytes of RAM memory, of which 14 bytes are read or write clock registers containing time and control information. The other 50 bytes are available for whatever other use you can dream up. Another useful feature.

At about £15 each these chips will certainly be very popular!

FREE SPEECH?

Probably the most fashionable electronic technique at the moment is speech synthesis, with major semiconductor manufacturers such as Texas, National and General Instruments all championing their own particular coding systems which allow human speed to be compressed into relatively few bytes of Read Only Memory (ROM).

Notice that all these manufacturers are from the USA which means that you get a trans-Atlantic "voice" and that specifying custom words or phrases can be expensive because most of the encoding work is done in the USA. For these reasons it is good to be able to welcome Triangle Digital Services as newcomers to the field, who are British and who have some unique advantages over the competition.

Triangle was set up by British engineer, Peter Rush, to develop a speech synthesis system which was as good as the competition's but more accessible to the smaller users who wished to specify their own vocabularies. The result is the unique TDS 934 chip set which consists of a synthesiser, a speech ROM, a memory decoder, two analogue filters and a regulator. When these chips are assembled as a system, a very versatile speech synthesiser results. The standard ROM supplied contains the words "Oh", one, two, three, four, five, six, seven, eight, nine,

point, grammes, kilo, ohms, volts, and amps, and further ROMs can be added to extend the vocabulary to almost any level. Between 5 and 32 words will fit into each ROM, depending on the required quality and complexity, and Triangle will encode the words of your choice at a rate of £30 each.

Users who prefer a complete system can buy the chip set assembled on a Eurocard p.c.b. with space for up to eight ROMs and with a variety of useful features such as a built-in RS232 UART so that words can be selected over a standard serial link for easy interfacing.

The TDS 934 set can also be hooked up to a parallel bus from a microprocessor, or for simple applications the words can be selected by an array of up to 16 switches.

For more information on this British innovation contact: Triangle Digital Services Limited, 23 Campus Road, London E17 8PG.

SUPER SONICS

Despite the tremendous advances in multi-channel proportional radio control systems which have been made since the days of valves, miniaturised remote control devices seemed unlikely until I saw data on a new chip from Commodore International called the 6600. This chip changed all that, because it is actually a remote control transmitter intended for use *inside* a digital wrist watch, alongside the watch chip itself.

The 6600 is not capable of controlling a complete army just yet, but no doubt the Mark III version is already on the drawing board at Commodore, and so it won't be long I am sure! Two versions of the 6600 are already available, one working in the audio region and the other using Ultrasound to generate remote control signals and provide simple on-off-on switching for any two appliances equipped with suitable sound receivers.

The chips use ordinary piezo-electric watch alarm-transducers as transmitters and operate from 1.5 volt battery supplies. The audio version generates two tones, which can be individually selected by watch buttons, at 8KHZ and 5.4KHZ and these tones can be used to control appliances at ranges of up to 40 feet. The ultrasonic version uses a 32.768KHZ watch-frequency carrier which can be modulated at either 128HZ or 256HZ to achieve the same effect.

At present the 6600 devices are available only as chips for the use of watch manufacturers, but no doubt they will eventually appear in 8 pin mini-DIPs for more general use.

BIMDICATORS



Just a few shining examples of
NEON, FILAMENT & LED

Oven Lamps,
Mains Indicators

& Instrument Lights

PCB, Push-on, Solder, Plug-in, Wire wrappable,
Flying lead & Screw Terminations

Now Sole UK Distributors for
Philips Miniature Neons
which are available individually or
bonded and formed to customers specification

BOSS

INDUSTRIAL MOULDINGS LTD

James Carter Road, Mildenhall, Suffolk IP28 7DE
Tel: Mildenhall (0638) 716101 Telex: 818758

ELECTRONIC IGNITION

Makes a good car
better



As a
KIT
or
READY
BUILT

TOTAL ENERGY DISCHARGE electronic ignition gives all the well known advantages of the best capacitive discharge systems.

PEAK PERFORMANCE — higher output voltage under all conditions.

IMPROVED ECONOMY — no loss of ignition performance between services.

FIRES FOULED SPARK PLUGS no other system can better the capacitive discharge system's ability to fire fouled plugs.

ACCURATE TIMING — prevents contact wear and arcing by reducing load to a few volts and a fraction of an amp.

SMOOTH PERFORMANCE — immune to contact bounce and similar effects which can cause loss of power and roughness.

PLUS

SUPER POWER SPARK — 3½ times the energy of ordinary capacitive systems — 3½ times the power of inductive systems.

OPTIMUM SPARK DURATION 3 times the duration of ordinary capacitive systems — essential for use on modern cars with weak fuel mixtures.

BETTER STARTING — full spark power even with low battery.

CORRECT SPARK POLARITY unlike most ordinary C.D. systems the correct output polarity is maintained to avoid increased stress on the H.T. system and operate all voltage triggered tachometers.

L.E.D. STATIC TIMING LIGHT for accurate setting of the engine's most important adjustment.

LOW RADIO INTERFERENCE fully suppressed supply and absence of inverter 'spikes' on the output reduces interference to a minimal level.

DESIGNED IN RELIABILITY an inherently more reliable circuit combined with top quality components — plus the 'ultimate insurance' of a changeover switch to revert instantly back to standard ignition.

IN KIT FORM

it provides a top performance electronic ignition system at less than half the price of competing ready-built systems. The kit includes everything needed, even a length of solder and a tiny tube of heatsink compound. Detailed easy-to-follow instructions, complete with circuit diagram, are provided — all you need is a small soldering iron and a few basic tools.

AS REVIEWED IN

ELECTRONICS TODAY INTERNATIONAL June '81 Issue
and EVERYDAY ELECTRONICS December '81 Issue

FITS ALL NEGATIVE EARTH VEHICLES,
6 or 12 volt, with or without ballast

OPERATES ALL VOLTAGE IMPULSE TACHOMETERS
Some older current impulse types (Smiths pre '74) require an adaptor —
PRICE £2.95

STANDARD CAR KIT £ 14.85
Assembled and Tested £ 24.95

TWIN OUTPUT KIT £ 22.95
For MOTOR CYCLES and CARS with twin ignition systems
Assembled and Tested £ 34.70

PLUS
£1.00
U.K.
P. & P.
Prices
Include
VAT.

ELECTRONIZE DESIGN


Dept. B, Magnus Road, Wilnecote
Tamworth, B77 5BY

Phone (0827) 281000



FREE TRANSISTOR PROJECTS...

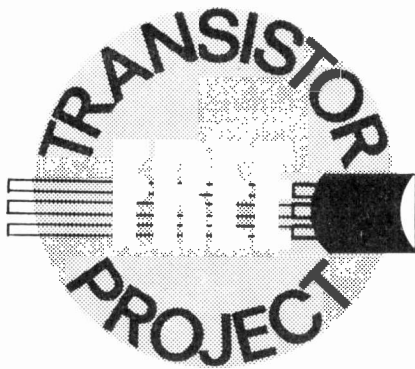★ SIX MORE PROJECTS FOR LAST MONTH'S FREE GIFT.



LOGIC PROBE

THIS logic probe is suitable for checking voltage levels in TTL circuits. The probe is powered from the circuit under test and will indicate either a high or low logic level.

CIRCUIT DESCRIPTION

The circuit diagram of the Logic Probe is shown in Fig. 1. When the input voltage to the probe tip is above 2.1V (the 'high' logic state) transistor TR1 is turned on, the l.e.d. D1 is

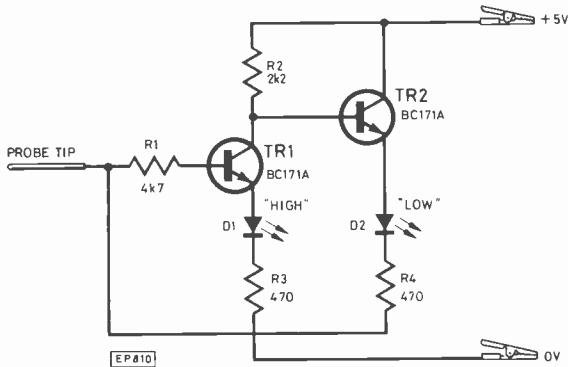


Fig. 1. Circuit diagram

forward biased and illuminated, indicating a 'high' logic level. As TR1 turns on its collector voltage falls and because the input to the probe tip is also connected to one end of resistor R4 the base/emitter junction of the transistor TR2 and the l.e.d. D2 are reverse biased keeping TR2 and D2 turned off.

If the input voltage to the probe tip switches to zero volts (the 'low' logic level) then TR1 receives no bias current and is switched off. With TR1 turned off the l.e.d. D1 is also turned off and the collector voltage of TR1 rises, forward biasing TR2, switching it on and illuminating the l.e.d. D2 indicating a 'low' logic level.

CONSTRUCTION

The Veroboard layout for the probe is shown in Fig. 2. Solder the resistors and wire links first and then the

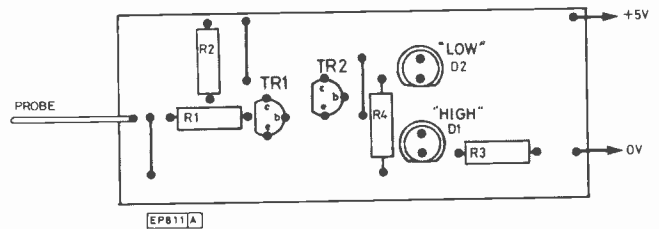


Fig. 2. Veroboard layout

COMPONENTS . . .

Resistors


R1	4k7
R2	2k2
R3, R4	470 (2 off)
All resistors 1/8W 10% carbon	

Semiconductors


D1	0.2in red l.e.d.
D2	0.2in green l.e.d.
TR1, TR2	BC171A (2 off)

Miscellaneous

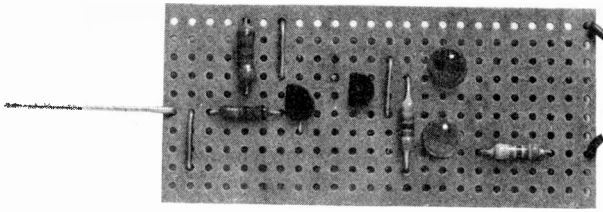Veroboard
Crocodile clips with red and black sleeves.



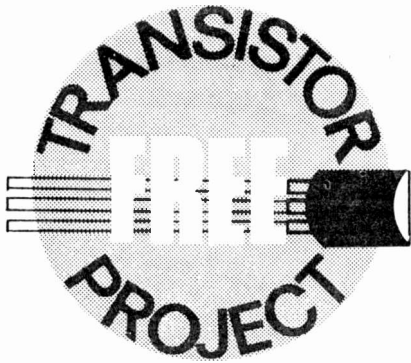transistors and I.e.d.s. Take care with the orientation of the semiconductors.



LIGHT DELAY UNIT

THIS simple delay unit enables a light or any other suitable load to be switched off automatically after a predetermined time period. Typical uses for the unit include the switching of staircase or pathway lighting, the delay of a car courtesy light and if correctly rated relay contacts are used, the control of car spotlights in a driveway.

CIRCUIT DESCRIPTION

The two transistors TR1 and TR2 (Fig. 1) are connected as a Darlington pair. This combination uses the current amplified by the first transistor (TR1) as the base current for the second transistor (TR2) where it is again amplified.

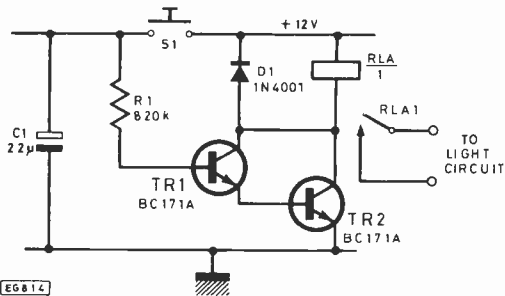


Fig. 1. Circuit diagram

In the prototype a green I.e.d. was used to indicate a 'low' logic level and a red I.e.d. for the 'high' level.

The probe can be made from a piece of tinned copper wire or a wiring pin and the supply leads should be fitted with miniature crocodile clips using red and black insulated sleeves. After soldering the components carefully check the Veroboard tracks for any solder splashes and then cut the tracks as shown in Fig. 2.

If the probe fails to operate when connected to a circuit check the orientation of the I.e.d.s and also check that the breaks in the copper tracks are completely cut.

Together the two devices act as a very high gain transistor with an overall gain determined by the product of their individual gains.

The switch S1 is a push button type and when it is pressed the capacitor C1 is charged to the potential of the supply voltage. The Darlington pair are turned on by the base current flowing through the resistor R1 and as the transistors saturate, their collector voltage falls, increasing the potential across the coil, energising the relay and closing its contacts RLA1.

When S1 is released the capacitor slowly discharges through the base bias resistor R1, maintaining the base current to TR1 and keeping the transistors and the relay turned on. The potential across the capacitor falls as it discharges and the base current to TR1 decreases until there is insufficient current flowing through R1 for TR1 to remain on. As the two transistors turn off, their collector voltage rises reducing the potential across the coil of RLA, de-energising

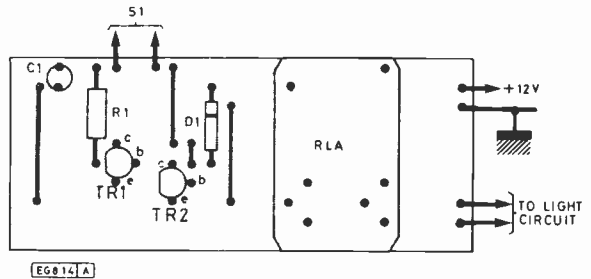


Fig. 2. Veroboard layout

COMPONENTS . . .

Resistor

R1 820k

Capacitor


C1 22µ 16V elect.

Semiconductors

TR1, TR2 BC171A (2 off)
D1 1N4001

Miscellaneous

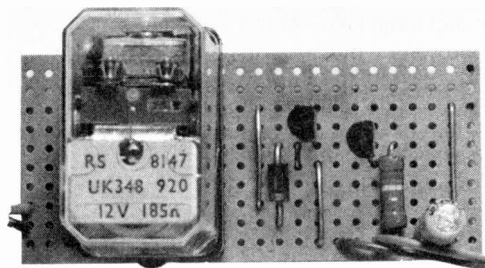RLA 12V 180Ω heavy duty relay (RS348-920)
S1 push button switch
Veroboard



the relay and opening its contacts, turning off the power to the load.

The switch S1 must be placed so that the capacitor C1 and the resistor R1 are isolated from the relay coil, otherwise it will discharge through the coil and TR2 as well as into the base of TR1 resulting in a very small time delay.

Although the voltage across the coil falls very slowly and there should be no transient voltages generated as the relay turns off, the diode D1 was included in case the capacitor was accidentally shorted during testing.

The relay specified has heavy duty contacts and is capable of handling currents up to 3 amps. If necessary the contacts can be connected in parallel to increase their current carrying capacity.

CAR SPOTLIGHTS

If the unit is to be used to delay car headlights then the specified relay should not be used. A suitable relay is the RS type 348-835 which can handle loads up to 10 amps.

DELAY TIMES

The delay time for the circuit is determined by the values of R1 and C1 and with the values given a delay of approximately 40 seconds can be obtained before the load is switched off. To increase this time the value of C1 can be increased, but do not increase the value of R1 to a much higher value or there might not be enough current to turn on the relay.

CONSTRUCTION


The Veroboard layout for the delay unit is shown in Fig. 2. After soldering, carefully check all the track breaks have been included and then connect the unit to a 12 volt supply. When S1 is pressed the relay contacts should close and after approximately 40 seconds you should hear the relay drop out.

INSTALLATION

The unit can either be powered from a 12V d.c. mains p.s.u. or from a battery. To delay a house light the leads from the relay contacts should be connected directly across the light switch. This will enable the light to be switched on using the normal switch or delayed using the unit via S1.

When installing the unit in a car it should be powered directly from the battery and not through the ignition or the auxiliary switches otherwise the unit will not work unless the key is left in the ignition switch.

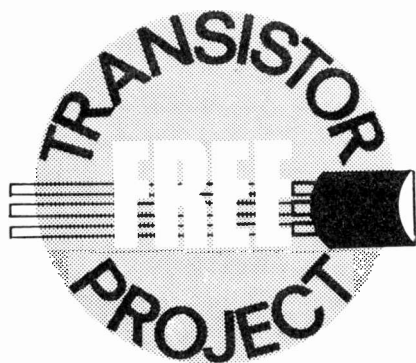Before fitting the unit to a courtesy light check with the car manual for the suitable place to make the connections.



CAR LIGHTS REMINDER

MOST car drivers have at some time returned to their car only to find it won't start because the lights have been left on. This system has been designed to overcome this problem by giving an audible warning as soon as the driver's door is opened, assuming the ignition has been switched off.

CIRCUIT DESCRIPTION

The circuit diagram of the Car Lights Reminder unit is shown in Fig. 1. The transistors TR1 and TR2 are connected as an astable multivibrator with the loudspeaker LS1 used as the collector load of TR2. Capacitors C1, C2 and resistors R3, R4 are the timing components of the circuit and determine the frequency of the output tone.

The positive supply to the circuit is obtained from the light switch via diode D1. The resistor R1 and the Zener diode D3 ensure the supply voltage remains at 9.1 volts.

The earth is connected via the interior light switch on the driver's door and the circuit is earthed only when the driver's door is opened.

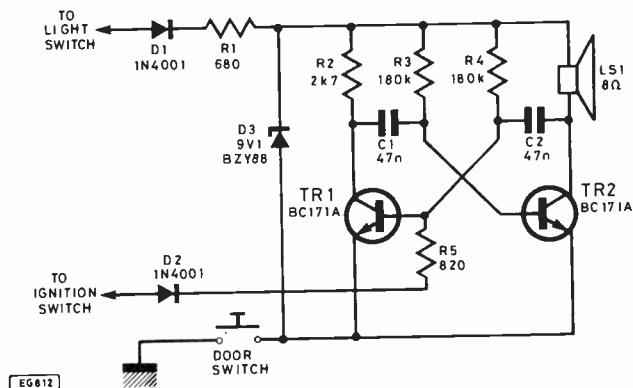


Fig. 1. Circuit diagram

COMPONENTS . . .

Resistors

R1	680
R2	2k7
R3, R4	180k (2 off)
R5	820
All resistors $\frac{1}{4}$ W 10% carbon	

Capacitors


C1, C2	47n (2 off)
--------	-------------

Semiconductors

D1, D2	1N4001 (2 off)
D3	BZY88 9V1 Zener
TR1, TR2	BC171A (2 off)

Miscellaneous

LS1	8 Ω speaker
Veroboard	

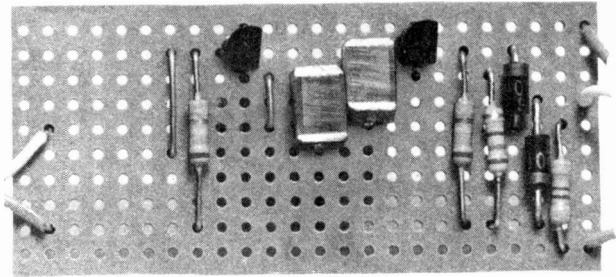

alarm is switched off. This enables the car lights to be left on for parking purposes without the alarm continuing to sound. The circuit is also disabled via D2 and R5 if the ignition switch is on.

CONSTRUCTION

The Veroboard layout of the unit is shown in Fig. 2. After the components have been soldered, cut the copper tracks as shown and then connect the speaker and the three switch supply leads.

TESTING

Before installing the unit, connect the door and light switch leads across the battery. This should produce an audible output from the loudspeaker, which should cease if the ignition switch lead is now touched to the positive terminal of the battery.

If the unit fails to operate, carefully recheck the resistor values are correct, the orientation of all the semiconductors and ensure the breaks in the copper tracks are in the right places.


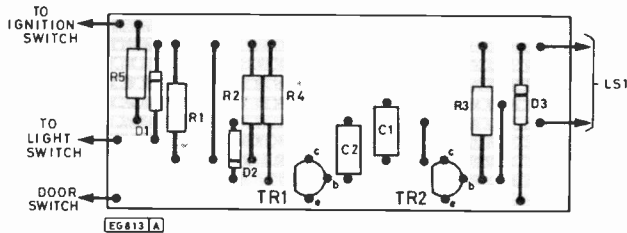


Fig. 2. Veroboard layout

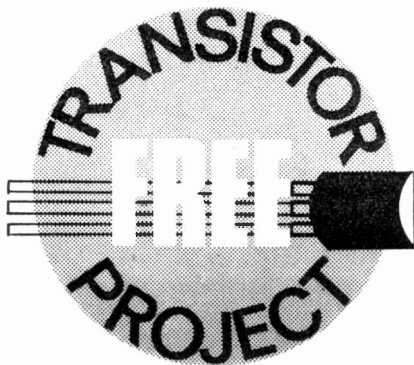If we assume that the ignition is off and the lights are on, then as the driver's door is opened the circuit will oscillate. As soon as the door is closed the earth is removed and the



A USEFUL addition to any piece of battery powered test equipment is an indicator to warn the user when the battery voltage is too low for reliable operation.

This circuit will monitor the supply voltage and illuminate an l.e.d. when the battery voltage falls below a preset level.

CIRCUIT DESCRIPTION

The circuit diagram of the voltage monitor is shown in Fig. 1. The unit is connected across the supply rails of the equip-

BATTERY MONITOR

ment to be monitored and VR1 sets the voltage at which the l.e.d. will be illuminated. When the supply voltage is above this preset value TR1 is turned hard on by R1 and part of VR1 with the result that the collector voltage of TR1 falls, keeping TR2 and the l.e.d. turned off.

As the supply voltage falls the bias current to TR1 decreases until it starts to turn off and its collector voltage rises. When the collector voltage of TR1 reaches 0.5 to 0.6V TR2 starts to turn on. As the base current to TR1 decreases its collector current decreases and TR2 takes more of the current flowing through R2. The collector voltage of TR1 rises until TR2 is turned fully on and TR1 is turned off. When TR2 turns on its collector voltage falls, the

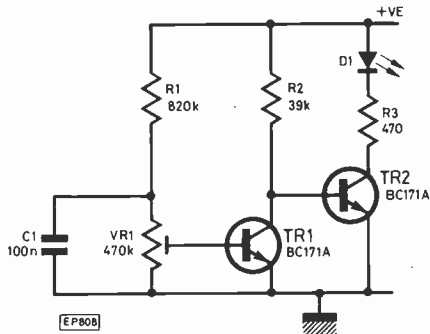


Fig. 1. Circuit diagram


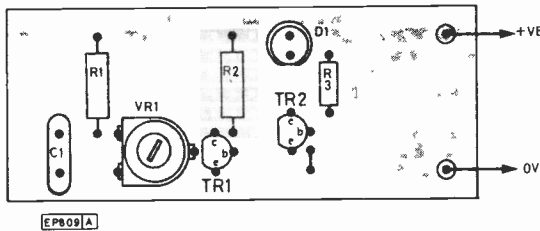


Fig. 2. Veroboard layout

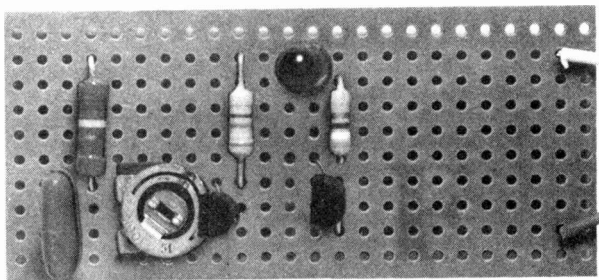

I.e.d. is forward biased and is illuminated. Resistor R3 is a current limiting resistor for the I.e.d.

The capacitor C1 prevents any instability when TR1 and TR2 are switching. The unit is suitable for monitoring supply voltages between 6 and 12V.

COMPONENTS . . .

Resistors

R1	820k
R2	39k
R3	470
VR1	470k min. preset lin.
All resistors $\frac{1}{3}$ W 10% carbon	

Capacitor

C1	100n polyester
----	----------------

Semiconductors

D1	0.2in red I.e.d.
TR1, TR2	BC171A (2 off)

Miscellaneous

Veroboard


CONSTRUCTION

A suitable Veroboard layout for the Monitor is shown in Fig. 2. The I.e.d. D1 is shown mounted on the board but can be mounted on a front panel and connected to the unit via connecting leads.

SETTING UP

The unit can be set up by connecting it across a supply voltage of the same value at which it is required to give warning. A suitable voltage level can be obtained using either a variable power supply unit or by connecting a preset across the terminals of a battery and then adjusting its wiper until the required voltage is obtained. The potentiometer VR1 should then be adjusted from the top end of its track until the I.e.d. just starts to glow. The monitor can then be installed into the equipment.

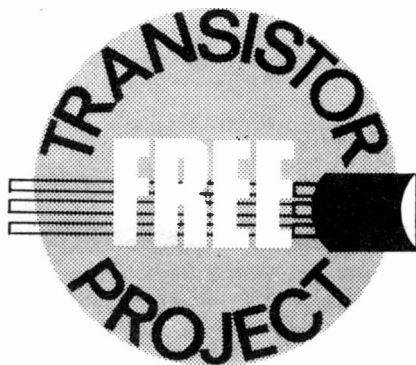If it is not necessary to constantly monitor the supply voltage a push-to-test switch may be incorporated into the supply line.



THIS Soil Moisture Meter can be used to test the water content of pot plants and help ensure the moisture level is kept constant. The advantage of the unit is that the probes enable the soil beneath the surface to be checked instead of just relying on its surface condition.

SOIL MOISTURE METER

CIRCUIT DESCRIPTION

The circuit of the Meter (Fig. 1) has been designed around a differential amplifier which is sometimes referred to as a long tailed pair.

The amplifier has two inputs (via the bases of the transistors TR1 and TR2) and an output (taken from between the two collectors). When both transistors are equally biased

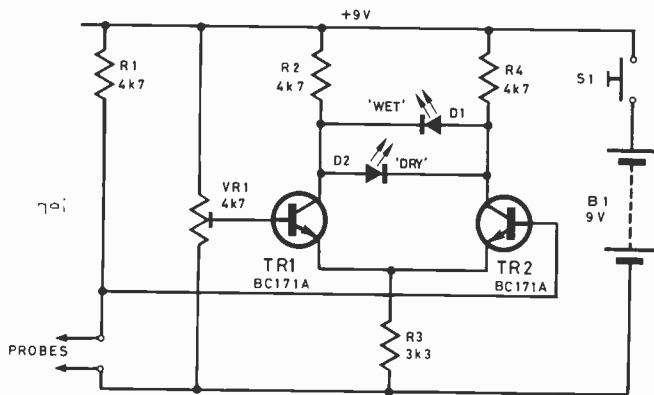


Fig. 1. Circuit diagram

and conducting they equally share the current flowing through the emitter resistor R3. Hence the voltages at their collectors are also equal and as no potential difference exists across the l.e.d.s they are both switched off.

If, however, the bias voltage applied to the base of either transistor is increased then the current through that particular transistor and the emitter resistor increases. This causes a rise in the voltage at the emitters of both transistors with the transistor to which the increased bias was applied still being turned on. At the same time the rise in emitter voltage reduces the base/emitter junction of the other transistor, turning it off. As one transistor turns on, its collector voltage falls, and as the other transistor turns off, its collector voltage rises, causing a potential difference across the collectors.

The transistor TR1 has a potential divider across its base formed by the preset VR1, whilst the resistor R1 and the resistance across the probes formed a second potential divider at the base of TR2.

PROBE RESISTANCE

The resistance across the probes when they are inserted into the soil is dependent upon the amount of moisture present, i.e. the more moisture the lower the 'resistance' of the soil and vice versa.

WET SOIL

When the probes are inserted into very moist soil the resistance across them is very low and so consequently is the voltage. If we assume that VR1 is set to a mid-range position when the switch S1 is pressed, TR1 will start to turn on. The current through R3 will increase causing the emitter voltages of TR1 and TR2 to rise, reducing the bias voltage across the base/emitter junction of TR2 (its base voltage being held by the potential divider R1 and the probe resistance) and TR2 will start to turn off.

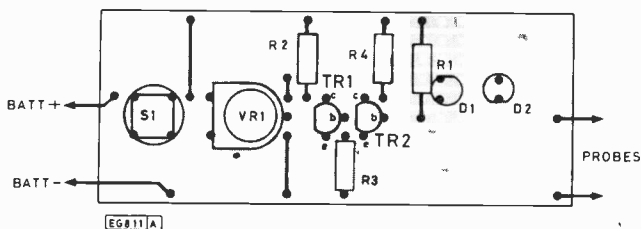



Fig. 2. Veroboard layout

As TR2 turns off, its collector voltage rises whilst the collector voltage of TR1 (as it turns on) falls.

When the difference between the two collector voltages reaches approximately 1.6V the l.e.d. D1 will start to turn on indicating the soil is 'wet' and l.e.d. D2 is reverse biased and remains off.

DRY SOIL

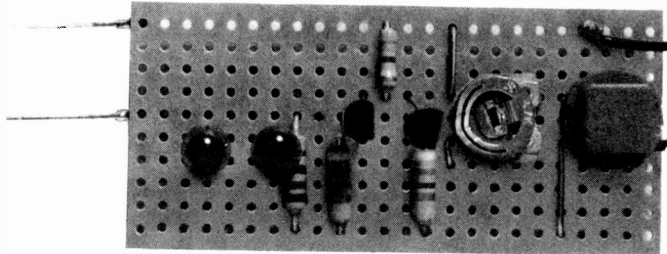If the probes are now placed in very dry soil, the resistance across them increases and TR2 will start to conduct whilst TR1 will turn off. This will cause the collector voltage of TR2 to drop and the collector voltage of TR1 to rise, switching off D1 and switching on D2, indicating the soil is 'dry'.



The soil 'resistance' value at which the l.e.d.s are illuminated is controlled by the preset VR1 and can be adjusted to suit different plants.

COMPONENTS ...

Resistors

R1, R2, R4 4k7 (3 off)
R3 3k3

All resistors 1/4W 10% carbon

Semiconductors

D1 0.2in red l.e.d.
D2 0.2in green l.e.d.
TR1, TR2 BC171A (2 off)

Miscellaneous

Veroboard
S1 keyboard switch
B1 9V PP3 battery
Battery connectors


CONSTRUCTION

The Veroboard design for the circuit is shown in Fig. 2. After the components have been soldered, cut the copper tracks as shown and carefully check the orientation of the l.e.d.s. The probes can be made of two suitable lengths of brass rod soldered to the tracks.

Connect the unit to a PP3 battery and set VR1 to its mid position. Check that when S1 is pressed D2 lights, then short out the probes and D2 should be extinguished and D1 should light.

SETTING UP

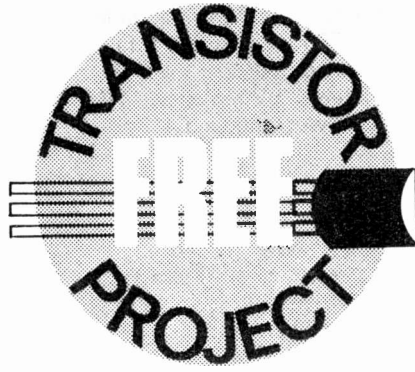To adjust the unit, fill a plant pot with soil and add water until it is sufficiently moist. Insert the probes into the soil, press S1 and adjust VR1 until D1 is just off and D2 is illuminated.



SNAP INDICATOR

DECIDING who was first when playing snap or quiz games often results in an argument. This circuit overcomes the problem by using an l.e.d. to indicate the winner. Each player has a push button and whoever presses first, lights their own l.e.d. whilst inhibiting the other players!

CIRCUIT DESCRIPTION

The circuit diagram of the Snap Indicator is shown in Fig. 1. With the battery connected the transistors (TR1 and TR2) are turned off because both switches (S1 and S2) are

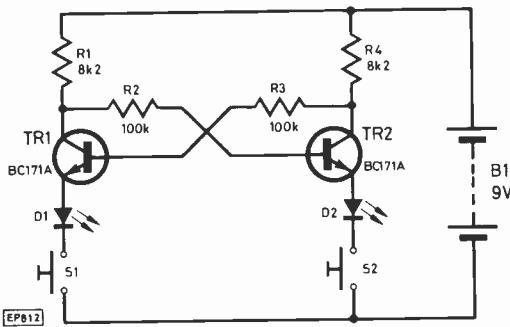


Fig. 1. Circuit diagram

open and so no collector current flows through either transistor.

With both transistors turned off there is no potential difference across either of the l.e.d.s and they remain off.

If S1 is closed first transistor TR1 is turned on by the bias current flowing through resistors R4 and R3. The current flowing through TR1 illuminates the l.e.d. D1 and the collector voltage of the transistor falls as the transistor saturates.

If S2 is now closed there is insufficient voltage at the base of TR2 to turn it on and the l.e.d. D2 remains off. For TR2 to turn on TR1 must be off. Once either of the transistors is turned on then the other is automatically held off.

The current flowing through each transistor and their l.e.d.s is limited by the resistors R1 and R4. As soon as the push buttons are released the circuit returns to its standby state ready for the next go.

CONSTRUCTION

The Veroboard layout for the circuit is shown in Fig. 2. The switches are shown mounted on the board but they can be connected off the board using wires if necessary. If hand held switches are to be used then a more suitable type is the RS miniature push-button type (337-914).

Solder the components onto the Veroboard and then add the links using tinned copper wire. Carefully check the orientation of the l.e.d.s before soldering them into place. Remember there is a flat on the side of the l.e.d.s body nearest to the cathode and also the lead of the cathode is longer. After soldering cut the tracks of the Veroboard as shown and then solder the battery connector in position.

There is no need to include an on/off switch in the supply line as the current drawn by the Snap Indicator when both switches are off is negligible.

COMPONENTS . . .

Resistors

R1, R4	8k2 (2 off)
R2, R3	100k (2 off)

Semiconductors

D1	0.2in red l.e.d.
D2	0.2in green l.e.d.
TR1, TR2	BC171A (2 off)

Miscellaneous

S1, S2	keyboard switch (2 off)
PP3 battery	
Battery connectors	
Veroboard	


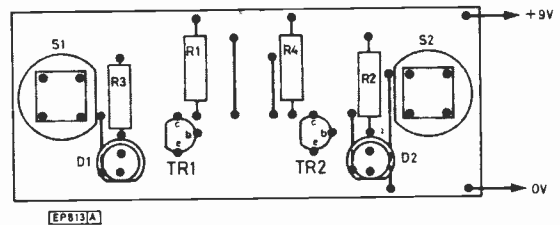


Fig. 2. Veroboard layout

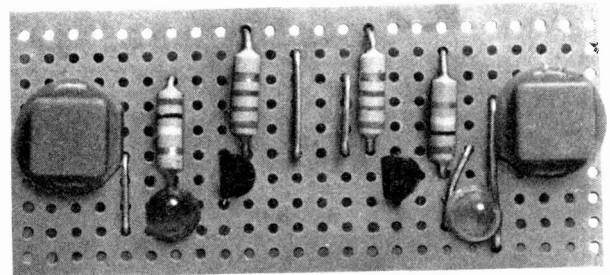

TESTING

After checking the components and track breaks connect the indicator to a PP3 battery. With both switches open the l.e.d.s should be off. Pressing either S1 or S2 should light its respective l.e.d. and once the l.e.d. is on pressing the other switch should have no effect on the second l.e.d. which should remain off.

Medium Resolution Graphics

N.A.Climpson

THE STANDARD UK 101 has an interesting character set consisting of the alphanumeric and 154 graphics characters with each character based on an 8x8 dot matrix. When displayed each row of the matrix is in fact repeated so that every column of the character is represented by 16 dots, although this will not concern us here. Whilst a certain amount of manipulation of the 154 graphics characters can give dramatic effects on the screen it is impossible to achieve very high pixel resolution and it is difficult to work out which character will fill a particular slot to the best effect. For plotting purposes some $\frac{1}{4}$ square graphics can be used but the $\frac{3}{4}$ filled characters are missing so that every possibility of plotting is not available. In addition the format of the characters is such that squares are not square but elongated vertically.

One method of achieving higher resolution is to use one of the recently available programmable graphics generators by which the precise character required to fill a slot to best effect can be defined in memory. One disadvantage is that these boards are expensive, and another is that the software to define and select a character to fit a specific situation is quite complicated.

FOUR TIMES RESOLUTION

This article describes an alternative approach, easily and cheaply implementing medium resolution pixel graphics on the UK 101 using a fixed set of 256 alternative characters, giving an improvement in resolution of *four times* over the standard character set.

If we imagine the standard character slot to be divided into two portions vertically and four horizontally we now have eight blocks to fill; the size of one of these blocks representing the ultimate resolution of this system. (See Fig. 2). To fill these eight spaces with all possible combinations of characters will require 2^8 or 256 characters, and since each row of a character is defined by one 8 bit byte in the character generator (see Fig. 1), we will require 2048 bytes of storage for the new characters. By this means we can achieve a horizontal resolution of 1×48 and a vertical resolution of 4×16 ; a total of 6144 individually addressable points on the screen, and furthermore each picture element is now nearly square. The storage requirements for the 256 new characters are simply fulfilled by a 2716 EPROM.

The order in which the characters are stored in the EPROM is important so that the appropriate character can easily be selected by software. The system used here is shown in Fig. 2 where the number of the character is represented by a binary count starting in the top left corner. Thus for example character 0 would be all blank, 255 would be all white, 64 would have only the bottom left space filled and 65 would have the bottom left and top left occupied.

Having programmed an EPROM with the correct pattern of bits, the complete listing of which is shown in Table 1, it would be possible to plug it into the existing character generator socket with some minor wiring changes. This would mean however that the standard graphics set including the alphanumeric would not be available. The solution proposed here is to mount the standard and alternative

character generators on a small sub-board which then plugs into the character generator socket on the main board. Selection of either one of the character sets is by software control, but it is unfortunately not possible to mix characters from the two sets on the screen at the same time.

HOW IT WORKS

The circuit design of the new board is shown in Fig. 3. You will notice that the address lines and data lines to the two chips are paralleled up and are fed from a d.i.l. plug. This d.i.l. plug is inserted in the character generator socket on the main board, the original character generator having moved to the sub-board. The chip selects for the two devices are wired differently from each other and are not connected to the main board. With pins 20 and 21 wired as shown it requires a high on pin 18 to select the standard character generator and a low on pin 18 to select the 2716. The signal for these pins is derived from the Q output of a 7474 D-type edge triggered flip-flop. This is acting as a latch in that it holds a high or low logic level on its output until it receives a clock pulse which transfers the data on the data input to the Q output and inverted to the \bar{Q} output. Since \bar{Q} is back connected to the data input the output at Q is alternately high and low. The clock input is derived from an unused partially address decoded line on the main board. There are several of these available and a convenient one is pin 14 on U20. This is decoded to a 1K block starting at D800 Hex or 55296 decimal. Any address issued in this range with a dummy POKE or PEEK will cause the 7474 to change state and hence select the other character set. The address 55555 decimal is in this range and is an easy one to remember.

The reset of the 7474 is connected to the reset line of the 6502 processor on the main board so that on RESET the standard character set is always selected.

CONSTRUCTIONAL DETAILS

The printed circuit design for the board is shown full size in Fig. 5. As you can see the board is tightly packed to keep the size to a minimum and will require some care in construction. An additional problem is that no suitable d.i.l. plug appears to be commercially available and it will be necessary to make your own directly onto the board. Proceed as follows.

Obtain a 24 pin d.i.l. header plug. These are rather like d.i.l. i.c. sockets except they have stronger pins and are designed to plug into i.c. sockets. Into each socket of the d.i.l. header (except 18, 20 and 21) is pushed a 1cm. length of 24 s.w.g. hard brass wire. When complete the wires are put through the holes for the d.i.l. plug in the circuit board so that the d.i.l. header is on the plain side of the board. Solder the pins to the pads keeping the solder close to the board. Trim the pins on the circuit side of the board to an even 3.5mm. length, remove the d.i.l. header and push onto the trimmed pins. Put a blob of solder on the pins on the plain side of the board as close as possible to the board to take any removal strains and then trim the excess length of pin off as short as possible. Remove the d.i.l. header.

	BIT PATTERN IN CHARACTER GENERATOR	HEXADECIMAL EQUIVALENT
	0000 0000	0D
	0000 0000	00
	0000 1111	0F
	0000 1111	0F
	0000 0000	00
	0000 0000	00
	1111 0000	F0
	1111 0000	F0

Fig. 1. Character 72 in the new character set

1	2
4	8
16	32
64	128

Fig. 2. Arrangement of characters in new character set

Solder on the two 24-pin and one 14-pin sockets in the usual way followed by the two flying wires. The wire from pin 11 on the 7474 should be soldered carefully to the top of the leg of pin 14 on U20. The wire from pin 10 should be soldered to the printed circuit track going to pin 40 on the 6502 processor U8. Fig. 4 shows the place to solder it, but remember that if you leave the 6502 in place while doing this you should be using a good quality soldering iron which has a well earthed tip.

Remove the character generator U41 from the main board and fit to the sub-board in its appropriate place and *correct orientation*. Fit the 7474 and 2716 EPROM and plug the sub-board into the character generator socket on the main board with the d.i.l. header in place. This completes the construction.

SOFTWARE


Although we now have higher resolution we are still using the old character slots to put one of 256 characters onto the screen at any one time. The heart of the software is to decide which character best represents the desired point to plot and to select the required character bearing in mind the character already occupying the slot.

Two programs are listed which use the character selection algorithm, one in BASIC to plot functions and a hybrid program in BASIC and machine code to draw pictures on the screen.

Table 2 is a program for plotting any mathematical function on the screen and will be described in some detail since it contains the routine needed for any plotting in medium resolution graphics.

The subroutine starting at line 1000 is the character selection and plotting portion.

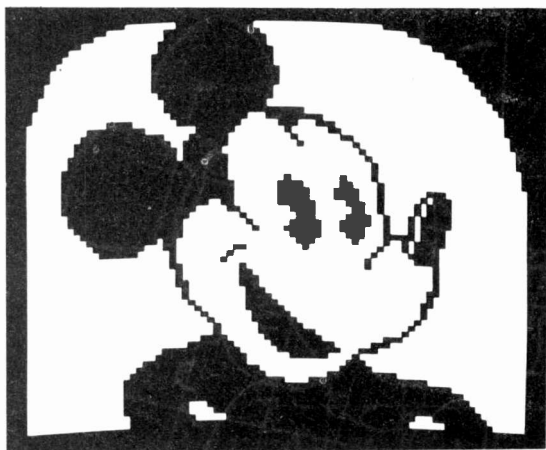X and Y are the new medium resolution co-ordinates relative to screen origin. X can range from -48 to +48 and Y from -32 to +32.



Line 1000 calculates the number of lines down the screen and the position across the screen of the standard character slot that X and Y fall in.

Line 1005 calculates the position of the individual $\frac{1}{8}$ character within the large character slot.

Line 1006 calculates the binary number of the character needed in this slot ignoring the character already there.

Line 1010 gets the present character in the slot.

Line 1012 decides the new character to put on the screen with reference to the one already there.

Line 1100 displays it.

Not strictly necessary in this program, but put in for completeness, are lines 1011, 1015 and 1017. These are used if the calculated $\frac{1}{8}$ graphics is to be deleted from the character that is already on the screen. The choice between subtracting and adding a character is controlled by flag D.

The function to be plotted is placed in a subroutine starting at line 2000, in this case an ellipse calculation, and the dimensions of the ellipse are controlled in lines 45-100.

POKE 5555,1 in lines 40 and 220 switches to the new character set at the start and back to the standard set at the end.

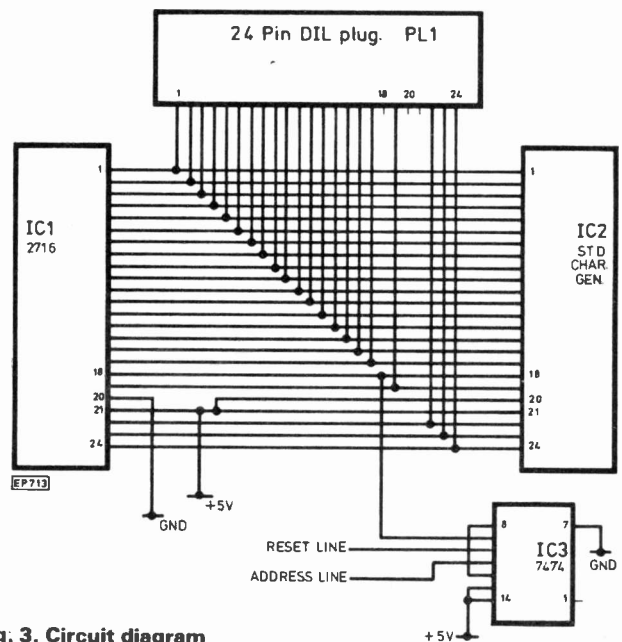


Fig. 3. Circuit diagram

000	00 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
010	0F 0F 00 00 00 00 00 00 FF FF FF FF FF FF 00 00
020	00 00 F0 F0 00 00 00 00 00 F0 F0 F0 F0 00 00
030	0F 0F F0 F0 00 00 00 00 FF FF FF FF FF FF 00 00
040	00 00 0F 0F 00 00 00 00 F0 F0 0F 0F 00 00
050	0F 0F 0F 0F 00 00 00 00 FF FF FF FF FF FF 00 00
060	00 00 FF FF FF 00 00 00 00 F0 F0 FF FF FF FF 00
070	0F 0F FF FF FF 00 00 00 00 FF FF FF FF FF FF 00 00
080	00 00 00 00 F0 F0 00 00 F0 F0 00 00 F0 F0 00 00
090	0F 0F 00 00 F0 F0 00 00 FF FF FF FF FF FF 00 00
0A0	00 00 F0 F0 F0 F0 00 00 F0 F0 F0 F0 F0 F0 00 00
0B0	0F 0F F0 F0 F0 F0 00 00 FF FF FF FF FF FF 00 00
0C0	00 00 0F 0F F0 F0 00 00 F0 F0 0F 0F F0 F0 00 00
0D0	0F 0F 0F 0F F0 F0 00 00 FF FF FF FF FF FF 00 00
0E0	00 00 FF FF FF F0 F0 00 00 F0 F0 FF FF FF F0 F0 00
0F0	0F 0F FF FF FF F0 F0 00 00 FF FF FF FF FF F0 F0 00
100	00 00 00 00 0F 0F 00 00 F0 F0 00 00 0F 0F 00 00
110	0F 0F 00 00 0F 0F 00 00 FF FF FF FF FF 00 00 00
120	00 00 F0 F0 0F 0F 00 00 F0 F0 F0 F0 0F 0F 00 00
130	0F 0F F0 F0 0F 0F 00 00 FF FF FF FF FF 00 00 00
140	00 00 0F 0F 0F 0F 00 00 F0 F0 0F 0F 0F 0F 00 00
150	0F 0F 0F 0F 0F 0F 00 00 FF FF FF FF FF 00 00 00
160	00 00 FF FF FF 0F 0F 00 00 F0 F0 FF FF FF 0F 0F 00
170	0F 0F FF FF FF 0F 0F 00 00 FF FF FF FF FF 0F 0F 00
180	00 00 00 00 FF FF FF F0 F0 00 00 FF FF FF FF 00 00
190	0F 0F 00 00 FF FF FF 00 00 FF FF FF FF 00 00 00
1A0	00 00 F0 F0 FF FF 00 00 F0 F0 F0 F0 FF FF FF 00 00
1B0	0F 0F F0 F0 FF FF 00 00 FF FF FF F0 F0 FF FF 00 00
1C0	00 00 0F 0F FF FF 00 00 F0 F0 0F 0F FF FF 00 00
1D0	0F 0F 0F 0F FF FF 00 00 FF FF FF 0F 0F FF FF 00 00
1E0	00 00 FF FF FF FF 00 00 F0 F0 FF FF FF FF 00 00
1F0	0F 0F FF FF FF FF 00 00 FF FF FF FF FF 00 00 00
200	00 00 00 00 00 00 F0 F0 00 00 00 00 00 00 F0 F0
210	0F 0F 00 00 00 00 F0 F0 FF FF F0 F0 00 00 F0 F0
220	00 00 F0 F0 00 00 F0 F0 F0 F0 F0 F0 00 00 F0 F0
230	0F 0F F0 F0 00 00 F0 F0 FF FF F0 F0 00 00 F0 F0
240	00 00 0F 0F 00 00 F0 F0 F0 F0 0F 0F 00 00 F0 F0
250	0F 0F 0F 0F 00 00 F0 F0 FF FF FF 0F 0F 00 00 F0 F0
260	00 00 FF FF FF 00 00 F0 F0 F0 F0 FF FF FF 00 00 F0 F0
270	0F 0F FF FF FF 00 00 F0 F0 FF FF FF FF 00 00 F0 F0
280	00 00 00 00 F0 F0 F0 F0 F0 F0 00 00 F0 F0 F0 F0
290	0F 0F 00 00 F0 F0 F0 F0 FF FF 00 00 F0 F0 F0 F0
2A0	00 00 F0 F0 F0 F0 F0 F0 F0 F0 F0 F0 F0 F0 F0 F0
2B0	0F 0F F0 F0 F0 F0 F0 F0 FF FF F0 F0 F0 F0 F0 F0
2C0	00 00 0F 0F F0 F0 F0 F0 F0 F0 0F 0F F0 F0 F0 F0
2D0	0F 0F 0F 0F F0 F0 F0 F0 FF FF 0F 0F F0 F0 F0 F0
2E0	00 00 FF FF FF F0 F0 F0 F0 F0 FF FF F0 F0 F0 F0
2F0	0F 0F FF FF FF F0 F0 F0 F0 FF FF FF F0 F0 F0 F0
300	00 00 00 00 0F 0F F0 F0 FF FF 00 00 0F 0F F0 F0
310	0F 0F 00 00 0F 0F F0 F0 FF FF 00 00 0F 0F F0 F0
320	00 00 F0 F0 0F 0F F0 F0 F0 F0 F0 F0 0F 0F F0 F0
330	0F 0F F0 F0 0F 0F F0 F0 FF FF F0 F0 0F 0F F0 F0
340	00 00 0F 0F 0F 0F F0 F0 F0 0F 0F 0F 0F F0 F0
350	0F 0F 0F 0F 0F 0F F0 F0 FF FF 0F 0F 0F 0F F0 F0
360	00 00 FF FF FF 0F 0F F0 F0 FF FF FF 0F 0F F0 F0
370	0F 0F FF FF FF 0F 0F F0 F0 FF FF FF 0F 0F F0 F0
380	00 00 00 00 FF FF F0 F0 F0 F0 00 00 FF FF F0 F0
390	0F 0F 00 00 FF FF F0 F0 FF FF 00 00 FF FF F0 F0
3A0	00 00 F0 F0 FF FF F0 F0 F0 F0 F0 F0 FF FF F0 F0
3B0	0F 0F F0 F0 FF FF F0 F0 FF FF F0 F0 FF FF F0 F0
3C0	00 00 0F 0F FF FF F0 F0 F0 0F 0F FF FF F0 F0
3D0	0F 0F 0F 0F FF FF F0 F0 FF FF 0F 0F FF FF F0 F0
3E0	00 00 FF FF FF FF F0 F0 F0 F0 FF FF FF FF F0 F0
3F0	0F 0F FF FF FF FF F0 F0 FF FF FF FF FF FF F0 F0

Table 1. EPROM program


400	00 00 00 00 00 00 0F 0F F0 F0 00 00 00 00 0F 0F
410	0F 0F 00 00 00 00 0F 0F FF FF 00 00 00 00 0F 0F
420	00 00 F0 F0 00 00 0F 0F F0 F0 F0 F0 00 00 0F 0F
430	0F 0F F0 F0 00 00 0F 0F FF FF F0 F0 00 00 0F 0F
440	00 00 0F 0F 00 00 0F 0F F0 F0 F0 F0 00 00 0F 0F
450	0F 0F 0F 0F 00 00 0F 0F FF FF FF 0F 00 00 0F 0F
460	00 00 FF FF 00 00 0F 0F F0 F0 FF FF 00 00 0F 0F
470	0F 0F FF FF 00 00 0F 0F FF FF FF FF 00 00 0F 0F
480	00 00 00 00 F0 F0 0F 0F F0 F0 00 00 F0 F0 0F 0F
490	0F 0F 00 00 F0 F0 0F 0F FF FF 00 00 F0 F0 0F 0F
4A0	00 00 F0 F0 F0 F0 0F 0F F0 F0 F0 F0 FF FF 0F 0F
4B0	0F 0F F0 F0 F0 F0 0F 0F FF FF F0 F0 F0 F0 0F 0F
4C0	00 00 0F 0F F0 F0 0F 0F F0 F0 0F 0F F0 F0 0F 0F
4D0	0F 0F 0F 0F F0 F0 0F 0F FF FF FF 0F 0F F0 F0 0F 0F
4E0	00 00 FF FF F0 F0 0F 0F F0 F0 FF FF F0 F0 F0 0F 0F
4F0	0F 0F FF FF F0 F0 0F 0F FF FF FF FF F0 F0 0F 0F
500	00 00 00 00 0F 0F 0F 0F F0 F0 00 00 0F 0F 0F 0F
510	0F 0F 00 00 0F 0F 0F 0F FF FF 00 00 0F 0F 0F 0F
520	00 00 F0 F0 0F 0F 0F 0F F0 F0 F0 F0 0F 0F 0F 0F
530	0F 0F F0 F0 0F 0F 0F 0F FF FF F0 F0 0F 0F 0F 0F
540	00 00 0F 0F 0F 0F 0F 0F F0 F0 0F 0F 0F 0F 0F 0F
550	0F 0F 0F 0F 0F 0F 0F 0F FF FF 0F 0F 0F 0F 0F 0F
560	00 00 FF FF 0F 0F 0F 0F F0 F0 FF FF 0F 0F 0F 0F
570	0F 0F FF FF 0F 0F 0F 0F FF FF FF FF 0F 0F 0F 0F
580	00 00 00 00 FF FF 0F 0F F0 F0 00 00 FF FF 0F 0F
590	0F 0F 00 00 FF FF 0F 0F FF FF 00 00 FF FF 0F 0F
5A0	00 00 F0 F0 FF FF 0F 0F F0 F0 F0 F0 FF FF 0F 0F
5B0	0F 0F F0 F0 FF FF 0F 0F FF FF F0 F0 FF FF 0F 0F
5C0	00 00 0F 0F FF FF 0F 0F F0 F0 0F 0F FF FF 0F 0F
5D0	0F 0F 0F 0F FF FF 0F 0F FF FF 0F 0F FF FF 0F 0F
5E0	00 00 FF FF FF FF 0F 0F F0 F0 FF FF FF FF 0F 0F
5F0	0F 0F FF FF FF FF 0F 0F FF FF FF FF FF FF 0F 0F
600	00 00 00 00 00 00 FF FF F0 F0 00 00 00 00 0F 0F
610	0F 0F 00 00 00 00 FF FF FF FF F0 F0 00 00 0F 0F
620	00 00 F0 F0 00 00 FF FF FF FF F0 F0 00 00 FF FF
630	0F 0F F0 F0 00 00 FF FF FF FF F0 F0 00 00 FF FF
640	00 00 0F 0F 00 00 FF FF F0 F0 0F 0F 00 00 FF FF
650	0F 0F 0F 0F 00 00 FF FF FF FF 0F 0F 00 00 FF FF
660	00 00 FF FF 00 00 FF FF F0 F0 FF FF 00 00 FF FF
670	0F 0F FF FF 00 00 FF FF FF FF FF FF 00 00 FF FF
680	00 00 00 00 F0 F0 FF FF F0 F0 00 00 F0 F0 FF FF
690	0F 0F 00 00 F0 F0 FF FF FF FF F0 F0 00 00 F0 F0
6A0	00 00 F0 F0 F0 F0 FF FF F0 F0 F0 F0 F0 F0 FF FF
6B0	0F 0F F0 F0 F0 F0 FF FF FF FF F0 F0 F0 F0 FF FF
6C0	00 00 0F 0F F0 F0 FF FF F0 F0 0F 0F F0 F0 FF FF
6D0	0F 0F 0F 0F F0 F0 FF FF FF FF 0F 0F F0 F0 FF FF
6E0	00 00 FF FF F0 F0 FF FF F0 F0 FF FF F0 F0 FF FF
6F0	0F 0F FF FF F0 F0 FF FF FF FF FF FF F0 F0 FF FF
700	00 00 00 00 0F 0F FF FF FF FF 00 00 0F 0F FF FF
710	0F 0F 00 00 0F 0F FF FF FF FF 00 00 0F 0F FF FF
720	00 00 F0 F0 0F 0F FF FF F0 F0 F0 F0 0F 0F FF FF
730	0F 0F F0 F0 0F 0F FF FF FF FF F0 F0 0F 0F FF FF
740	00 00 0F 0F 0F 0F FF FF F0 F0 0F 0F 0F 0F FF FF
750	0F 0F 0F 0F 0F 0F FF FF FF FF 0F 0F 0F 0F FF FF
760	00 00 FF FF 0F 0F FF FF FF F0 FF FF FF 0F FF FF
770	0F 0F FF FF 0F 0F FF FF FF FF FF FF 0F FF FF
780	00 00 00 00 FF FF FF FF F0 F0 00 00 FF FF FF
790	0F 0F 00 00 FF FF FF FF FF FF 00 00 FF FF FF
7A0	00 00 F0 F0 FF FF FF FF F0 F0 F0 FF FF FF
7B0	0F 0F F0 F0 FF FF FF FF FF F0 F0 FF FF FF
7C0	00 00 0F 0F FF FF FF FF F0 F0 0F 0F FF FF
7D0	0F 0F 0F 0F FF FF FF FF FF FF 0F 0F FF FF
7E0	00 00 FF FF FF FF FF FF F0 F0 FF FF FF
7F0	0F 0F FF FF FF FF FF FF FF FF FF FF FF FF

Table 2. Plotting program

```

1 REM ** BASIC MEDIUM RESOLUTION GRAPHICS ***
2 REII ***** PLOTTING ALGORITHM *****
5 O=53259+8*64+24
30 DATA 162,00,138,157,00,208,157,00,209
31 DATA 157,00,210,157,00,211,232,208,241,96
33 FORI=56570583:READA:POKEI,A:NEXT
40 POKE11,53:POKE12,2:POKE65555,I:X=USR(X)
45 A=20:B=30
50 FOR TH=0 TO 6.3 STEP .1
60 GOSUB 2000
80 GOSUB 1000
90 NEXT
100 A=A+1:B=B-1:IF B=0 THEN 200
110 GOTO 50
200 POKE 11,186:POKE 12,255:X=USR(X)
210 FOR I=1 TO 16:PRINT:NEXT
220 POKE 55555,1:END
999 REM * SELECT CHARACTER AND PLOT OR UNPLOT
1000 XP=INT(X/2):YP=INT(Y/4)
1005 XD=X-XP*2:YD=Y-YP*4+1
1006 CH=2*((YD-1)*2+XD)
1010 SC=PEEK(O+YP*64+XP)
1011 IF D=1 THEN 1015
1012 ST=SC OR CH
1013 GOTO 1100
1015 CH=255-CH
1017 ST=SC AND CH
1100 POKE O+YP*64+XP,ST
1500 RETURN
1999 REM * FUNCTION TO BE PLOTTED: ELLIPSE HERE
2000 R1=A*A*B*B
2010 R2=A*A*SIN(TH)*SIN(TH)+B*B*COS(TH)*COS(TH)
2020 R=SQR(R1/R2)
2030 Y=INT(R*SIN(TH)+.5)
2040 X=INT(R*COS(TH)+.5)
2050 RETURN
  
```

Fig. 4. Connection of reset line

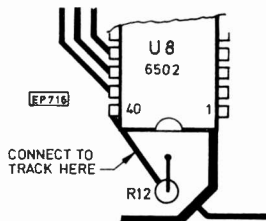

```

10 REM **** DRAWER IN BASIC/MACHINE CODE ****
20 REM **** HAVE YOU PROTECTED MEMORY AT 6500****
30 COSUB 5000
40 PRINT"
*****
50 PRINT" * MEDIUM RESOLUTION *
60 PRINT" * *
70 PRINT" * GRAPHICS DRAWER *
*****
90 PRINT:PRINT:PRINT:PRINT
100 PRINT"
By Nigel Climpson
110 PRINT:PRINT" A 25 sec delay whilst poking machine code"
199 REM POKE MACHINE CODE
200 M=6528
210 READ A$:IF A$="LAST" THEN 1095
220 FOR I=1 TO 16:S=ASC(MID$(A$,2*I-1,1))-48
230 IF S>9 THEN S=S-7
240 T=S*16:S=ASC(MID$(A$,2*I,1))-48:IF S>9 THEN S=S-7
250 T=T+S:POKE M,T:T=T+1:IF T=0:M=M+1:NEXT:GOTO 210
1095 POKE 21000,16
1100 GOSUB 5000
1110 PRINT:PRINT" OPTION MENU":PRINT
1120 PRINT" 1) Start a new picture.":PRINT
1130 PRINT" 2) Load a masterpiece from tape.":PRINT
1140 PRINT" 3) Save present picture to tape.":PRINT
1150 PRINT" 4) Change speed of cursor.":PRINT
1160 PRINT" 5) Display instructions.":PRINT
1170 PRINT" 6) Exit from programme.":PRINT
1180 GOSUB 5010
1190 ON CH GOTO 2000,2250,2500,2750,3000,3250
2000 POKE 11,128:POKE 12,25:X=USR(X)
2010 GOTO 1100
2249 REM LOAD FROM TAPE
2250 GOSUB 5000
2260 PRINT"TURN ON TAPE RECORDER IN LOAD MODE"
2270 POKE 11,50:POKE 12,27:X=USR(X)
2280 GOTO 1100
2499 REM SAVE TO TAPE
2500 GOSUB 5000
2510 PRINT"TURN ON TAPE RECORDER IN SAVE MODE"
2520 POKE 11,213:POKE 12,26:X=USR(X)
2530 GOTO 1100
2749 REM CHANGE SPEED
2750 GOSUB 5000
2760 PRINT"ENTER CURSOR SPEED (1-9)":
2770 GOSUB 5010
2780 PRINTCH
2790 POKE 7096,CH*5+1
2800 POKE 11,131:POKE 12,27:X=USR(X)
2810 GOTO 1100
2999 REM DISPLAY INSTRUCTIONS
3000 GOSUB 5000
3010 PRINT" The cursor is moved in the following manner":PRINT
3020 PRINT"
KEY 1"
3030 PRINT TAB(24);CHR$(16)
3040 PRINT TAB(8);"KEYS 1&3 ";CHR$(23);SPC(6);CHR$(16);
3050 PRINT SPC(6);CHR$(17);" KEYS 1&4"
3060 PRINT TAB(19);CHR$(23);SPC(4);CHR$(16);SPC(4);CHR$(17)
3070 PRINTTAB(21);CHR$(23);SPC(2);CHR$(16);SPC(2);CHR$(17)
3080 PRINT TAB(23);CHR$(23);CHR$(16);CHR$(17)
3090 PRINT TAB(5);"KEY 3 ";CHR$(22);" ";CHR$(22);" ";CHR$(22);
3100 PRINT" ";CHR$(22);" ";CHR$(22);" ";CHR$(22);" ";CHR$(22);
3110 PRINT CHR$(187);CHR$(18);" ";CHR$(18);
3120 PRINT " ";CHR$(18);" ";CHR$(18);" ";CHR$(18);" ";
3130 PRINT CHR$(18);" ";CHR$(18);" KEY 4"
3170 PRINT TAB(23);CHR$(21);CHR$(20);CHR$(19)
3180 PRINT TAB(21);CHR$(21);SPC(2);CHR$(20);SPC(2);CHR$(19)
3185 PRINTTAB(19);CHR$(21);SPC(4);CHR$(20);SPC(4);CHR$(19)
3190 PRINT TAB(8);"KEYS 2&3 ";CHR$(21);SPC(6);CHR$(20);
3195 PRINT SPC(6);CHR$(19);" KEYS 2&4"
3200 PRINTTAB(24);CHR$(20)
3210 PRINTTAB(22);"KEY 2"
3212 PRINT" Press any key";
3215 GOSUB 5010:GOSUB 5000:PRINT
3220 PRINT" KEY 5 TO PLOT":PRINT:PRINT
3225 PRINT" KEY 6 TO UNPLOT ":PRINT:PRINT
3230 PRINT" KEY 7 TO RETURN TO MENU":PRINT:PRINT
3235 PRINT" Press any key"
3247 GOSUB 5010:GOTO 1100
3249 REM GOOD-BYE
3250 GOSUB 5000
3260 PRINT" Thanks for playing-Bye for now Picasso."
4998 END
4999 REM CLEAR SCREEN
5000 FOR I=1 TO 16:PRINT:NEXT:RETURN
5009 REM GET CHARACTER FROM KEYBOARD
5010 POKE 11,186:POKE 12,255:X=USR(X):CH=PEEK(531)-48:RETURN
6000 DATA A000D8A900A89900D09900D19900D299
6010 DATA 00D3C8D0F180B418A98080B0180DB118
6020 DATA A978D00DFAD00DFC9FF9F3948ADB418
6030 DATA F0034C321A68C97FF047C9BF055C9EF
6040 DATA F048C9DF056C95FF034C96F039C9AF
6050 DATA F03EC9FF043C9F7F048C9FBF04CC9FD
6060 DATA D0034C81AA9008DB518203D1A20C91A
6070 DATA A9FF8DB518203D1A20C91A4CA019CEB0
6080 DATA 18CEB1184CE519CEB118EB0184CE519
6090 DATA EB018EB1184CE519EB118CEB0184C
6100 DATA E519A0FF8CB4184CE519A008CB4184C
6110 DATA E519A008DB518203D1A4CB519ADB018
6120 DATA 29018DB218ADB11829038DB3180A186D
6130 DATA B218AA901CAE0FF003AD0F88DB618
6140 DATA A91085F9A9C85FAADB018A41865F985
6150 DATA F99002E6FAADB11844AAA9401865F9
6160 DATA 85F99002E6FACAD0F2A000B1P9AE518
6170 DATA D0060DB6184CA51A48ADB61849FF8DB6
6180 DATA 18682DB61891F96A000B900D099001C
6190 DATA 8900D1990018900D299001E8900D399
6200 DATA 001FC8D0E5AD00D860AE8B18CEB718D0
6210 DATA FB8AD0F860A9FF8D0502201F18201F18
6220 DATA A00084F9A91C85FAA93A20EFFF1F94A
6230 DATA 4A4A4A200018B1F9290F2000184C0E18
6240 DATA 186930C93A300318690720EFFF60C8D0
6250 DATA DC6EFAA5FAC920D0DA9008D050260A9
6260 DATA 108DB918A0FFCAD0F88D0FAC9E918D0
6270 DATA F560A9FF8D0302A90085F9A91C85FAA0
6280 DATA 0020BAFFC93AD0F920EFFF20BAFF2067
6290 DATA 180A0A0A0A8D8A1820BAFF206718186D
6300 DATA BA1891F94C731820EFFF9C9419002E907
6310 DATA 290F60C8D0D5E6FAA5FAC920D0CDA900
6320 DATA 8D0302A000AD00D89001C9900D0B900
6330 DATA 1D9900D189001E9900D2B9001F9900D3
6340 DATA C8D0E5A9004C95190DF00520F9535441
6350 DATA LAST

```

Table 3. Drawer in M/C and BASIC

Note to CEGMON users:

In the *Plotting Algorithm* program line 200 will need to read:

```
200 POKE 11,70:POKE 12,251:X=USR(X)
```

In the *Graphics Drawer* program line 5010 will be:

```
5010 POKE 11,70:POKE 12,251:X=USR(X):
CH=PEEK(533)-48:RETURN
```

In line 6280 change two occurrences of BAFF to 46FB

In line 6290 change BAFF to 46FB

If your character generator has been supplied as an EPROM, then cut the track joining pin 18 on IC1 and IC2, leaving IC2 connected to pin 9 of the 7474. Connect pin 18 of IC1 to pin 8 of the 7474.

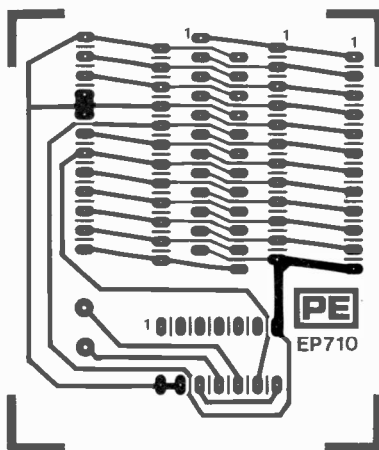


Fig. 5. Printed circuit layout

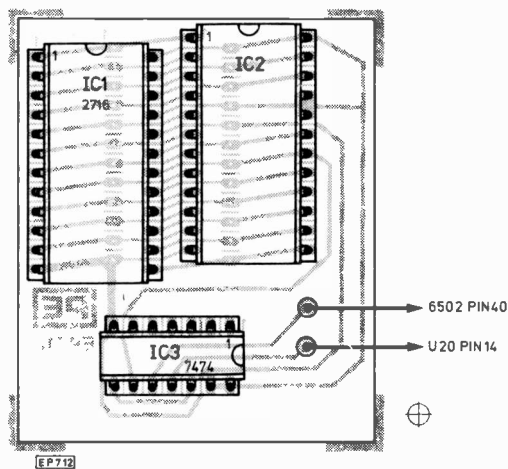


Fig. 6. Component overlay

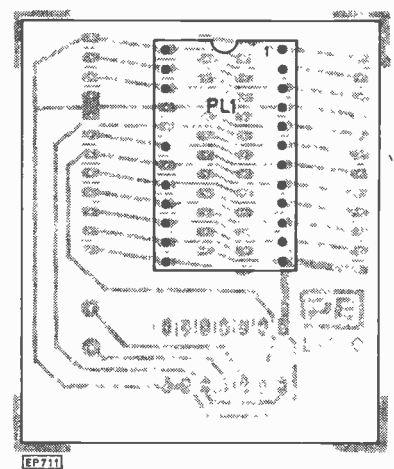


Fig. 7. Position of PL1


COMPONENTS...

Integrated circuits

IC1 2716
IC2 Standard Char. Gen. ROM
IC3 7474

Miscellaneous

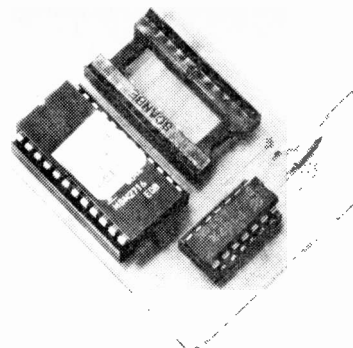24-way d.i.l. socket (2 off)
24-way d.i.l. plug
14-way d.i.l. socket
Printed circuit board



The program was originally intended for joy-stick control which explains the rather clumsy cursor movement keys, but on the standard keyboard I do not think that there are any better options.

The subroutine at line 5000 is to clear the screen and can be substituted by a more rapid routine if available.

To sum up then, this is a method of implementing $\frac{1}{8}$ th square graphics in a simple and non-destructive way. This system works equally well with the Superboard II but re-

quires a differently encoded EPROM since for reasons best known to the manufacturers, the wiring between the character generator and the data serialiser is slightly different on two machines. The Superboard requires each character row to be encoded in reverse. The software illustrated here will also have to be adjusted.

Thanks are due to the author's colleagues Dr. J. Ogle and D. Hazelden for ideas on the hardware and software of this project.

FREE! READERS' ADVERTISEMENT SERVICE

PE BAZAAR

RULES

Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns) Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad must be accompanied by a valid "date corner".

PRACTICAL Electronics one to December 81 offers. R&T servicing Vol 1-6 £10. Callers only. L. Marks, 14 Avenue Road, Kingston, Surrey.

ACORN Atom 12K RAM 8K BASIC £155. Portable music synthesiser-piano. Harpsichord, Brass, Strings, etc., £200. Don Pearson, 41 Ormonde Avenue, Chichester, Sussex. Tel: 0243 789748 or 943632 after 7 pm.

PRINTER and keyboard data dynamics ASRS390, complete with stand and paper, £99. S. L. Ross, 44 Premier Avenue, Grays, Essex RM16 2SD.

OSCILLOSCOPE single beam 5 inch screen Heathkit labscope model 10-12U suit young enthusiast. £18 only. A. R. Wiczorek, 11 Farsands, Oakley, Bedford, Tel: Oakley 3850.

I WISH to fit floppy disc drive to Superboard II. If anyone has done this contact: S. N. Hobson, 3 Church Close, Lindal, Ulverston, Cumbria LA12 0LS.

Advertise your spare parts, test gear, tools, computers, printers, instruments, synthesisers organs, books, etc., FREE. Yes, we will accept adverts from readers, *NOT TRADE*, on a one off basis to be published in the first available issue. Not only can you advertise parts for sale but your wanted or swap ad. will also be acceptable. The rules are straightforward but please read them and make sure you send in a **valid "date corner"** cut from the issue.

If you have a few components, a CompuKit or a computer organ we can help sell them for you. We reserve the right not to publish anything unacceptable to us or any ad. we believe is from a trader or anyone running a business involved in electronics; **it's a private readers only service. We cannot accept ads. for computer software.**

PLEASE NOTE: Due to the postal problems associated with the rail strikes, we have only received a few ads. at time of going to press. We expect to publish a larger number next month.

SHARP MZ80K, 48K extended BASIC, many games, one year old, as new condition £330. Mr P.J. Keen, "Cranfield", 37 Ivy Lane, Macclesfield. 0625-22649.

WANTED WW2 radios—38, 18, 19 sets, R1155 etc. Cash or swap Hitachi 19 inch colour TV. T.E.D. Levison, Bristol 681956.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment.

Signature

Date

Please read the **RULES** then write your advertisement here—one word to each box. Then add your name, address and/or phone no. Maximum of 16 words plus address.


COUPON VALID FOR POSTING BEFORE 8 APRIL, 1982. (One month later for overseas readers.)

SEND TO: PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

For readers who don't want to damage the issue send a photostat or copy of the coupon (filled in of course) with a **cut-out valid "date corner"**

BLOCK CAPITALS PLEASE

Name & Address:			

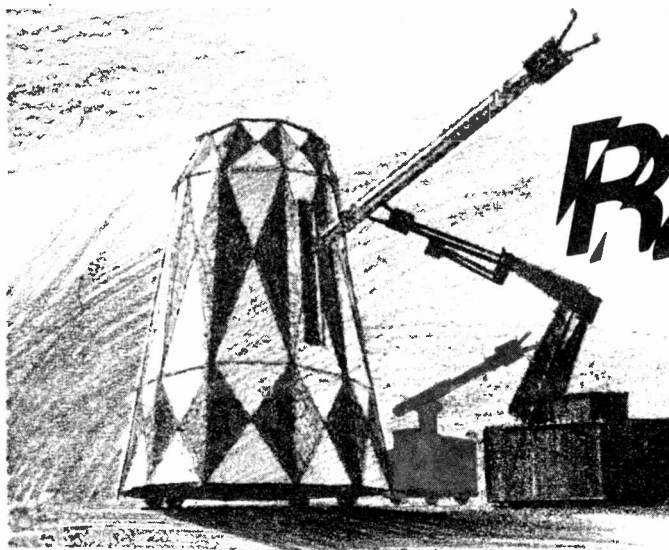

PE ROBOTS

PART 6

RICHARD BECKER · TIM ORR
RICHARD MONKHOUSE

THIS month, which represents the final part of the Robots series of articles, we look at the software and final assembly procedures.

SOFTWARE DESCRIPTION

Here are brief notes on some aspects of the control software for the robot.

Decoding the keyboard data via an interrupt routine

The clock pulses from the keyboard decoder are fed to one of the PIA's interrupt inputs. Each time an interrupt occurs, the new data bit from the keyboard decoder is read and shifted into a temporary data store by the software. When 56 bits have been received, the micro's internal button status bytes are updated. Synchronisation with the transmitted sequence is assured by resetting the bit count when a 'start' bit is decoded by the keyboard decoder. See Fig. 6.1a.

Jump node subroutine

To make button command controlled jumps from one part of the program to another easy to modify and expand, a special subroutine was written. This is entered with the X register pointing to the start of a particular jump table (Fig. 6.1c). If any of the listed button states are found, then the matched jump is made, otherwise the subroutine returns control to the part of the software it was called from. See Figs. 6.1b and 6.1c.

Servoing and deadband

On replay, the control of the robot to follow the stored data consists of a simple servo loop with a deadband, i.e. if the measured position is greater than the desired position plus the deadband, then the minus solenoid is activated.

i.e. $MP > DP + DB$:— -SOL ON
also $MP < DP$:— +SOL ON
and $DP < MP < DP + DB$:— BOTH OFF

As soon as an axis reaches the correct position, its appropriate solenoids are switched off. When all solenoids have reached their correct position, the software fetches the next position down from the sequence memory, and the process continues.

A full source listing (with comments!) of the control software is available from Powertran.

KITS

Constructor's Note

Complete kit of parts for this project can be obtained from **Powertran Cybernetics**, Portway Industrial Estate, Andover, Hants SP10 3WN. ☎ Andover (0264) 64455.

Prices are as follows . . .

Genesis M101 4 axis model (excluding wheel base)	£295.00
Genesis M101 5 axis model (excluding wheel base)	£345.00
Genesis M101 wheel base	£79.00
Genesis P101 4 axis model	£450.00
Genesis P101 6 axis model	£545.00
Genesis S101 4 axis model	£355.00
Genesis S101 5 axis model	£405.00
Position detector coil set for M101, S101 4 axis models	£15.00
Position detector coil set for M101, S101 5 axis models	£19.00
Position detector coil set for P101 4 axis model	£15.00
Position detector coil set for P101 6 axis model	£24.00
Position detector board for M101, S101 4, 5 axis models	£6.50
Position detector board for P101 4, 6 axis models	£7.50
Motor drive board for M101 wheel base (2 required per machine)	£11.50
Control electronics for M101 (microprocessor board, interface board, display board and mounting bracket)	£135.00
Processor box for S101, P101 (microprocessor board, interface board, display board, power supply, interface cables, conduit, cabinet)	£175.00
Parts for RS232C interface (fits on microprocessor board)	£14.50
Hand held controller box for M101 (includes infra red transmitter and rechargeable battery)	£47.00
Hand held controller box for S101	£33.00
Hand held controller box for P101	£33.50

All prices subject to 15% V.A.T.

Fig. 6.1a. Interrupt Service Routines

***GET KEY AND EXTERNAL DATA**

```

KBEX JSR BUSIN
      LDA B PIABD (THIS ALSO CLEARS
                  INTERRUPT)
      AND B #%01111111
      STA B PIABD
      LDA A PIAAD GET DATA
      PSH A
      ORA B #%10000000
      STA B PIABD
      JSR BUSOUT
      PUL A
      RTS
    
```

***TRANSFER/CHECK BUTTON DATA**

```

TRNFER LDA B #7
        LDX #BTS0
        STX FROMX
        LDX #BUTNS
        STX TOX
        JSR MOVE
        RTS
    
```

***INTERRUPT SERVICE ROUTINE**

```

INTSER JSR KBEX GET DATA AND CLEAR
        INTERRUPT
    
```

```

INT1 STA A KBEXD
      AND A #%00000010 GET START BIT
      BNE INT1 LOW MEANS START
      LDA A #56 INITIALISE BIT COUNT
      STA A BITCNT
      CLR BTRFLG CLEAR ALL READY FLAG
      LDA A KBEXD
      ROR A
      ROL BTS6
      ROL BTS5
      ROL BTS4
      ROL BTS3
      ROL BTS2
      ROL BTS1
      ROL BTS0 SHIFT DATA IN
      DEC BITCNT
      BEQ ALLDON
      RTI
    
```

```

ALLDON LDA A BTRFLG
        BNE INT2
        INC A
        STA A BTRFLG SET READY FLAG
        JSR TRNFER
        RTI
    
```

```

INT2 INTSER
    
```

***INTERRUPT VECTOR**

```

ORG #FFF8
FDB INTSER
    
```

***RESTART VECTOR**

```

ORG $FFFE
FDB START
END START
    
```

Fig. 6.1b. Jump Node Subroutine

***SEARCH JUMP TABLE POINTED TO BY**

```

*X AND JUMP IF NECESSARY
NODE LDA A 0, X
      CMP A #SFF END OF CURRENT TABLE?
      BEQ NODE2
      JSR TSTBUT
      BEQ NODE3 HAVE WE GOT A MATCH?
      INX
      INX
      INX
    
```

```

INX
BRA
LDX
LDS
JSR
JMP
RTS
NODE3
NODE2
*TEST PARTICULAR BUTTON BYTE FOR
*MATCH AGAINST TABLE ENTRY
TSTBUT STX TEMPX2
        LDX #BUTNS
        JSR ADDAX
        LDA A 0, X
        LDX TEMPX2
        CMP A 1, X
        RTS
*ADD A TO X
ADDAX STX TEMPX1
        CLR B
        ADD A TEMPX1+1
        STA A TEMPX1+1
        ADC B TEMPX1
        STA B TEMPX1
        LDX TEMPX1
        RTS
    
```

Fig. 6.1c. Jump Node Tables

***JUMP TABLES**

***INITIAL COMMAND NODE**

F81C 00 80	JT1	FDB	\$0080, SQM
F820 01 80		FDB	\$0180, SQP
F824 00 10		FDB	\$0010, EDIT
F828 02 08		FDB	\$0208, CLRMEM
F82C 00 20		FDB	\$0020, RPTP
F830 00 40		FDB	\$0040, PLAY
F834 01 20		FDB	\$0120, MCOM
F838 02 80		FDB	\$0280, MOCTRL
F83C FF		FCB	SFF

***PLAYBACK CONTROL NODE**

F83D 00 10	JT2	FDB	\$0010, EDIT
F841 01 20		FDB	\$0120, MCOM
F845 01 40		FDB	\$0140, PAUSE
F849 00 40		FDB	\$0040, PLAY
F84D 00 20		FDB	\$0020, RPTP
F851 FF		FCB	SFF

***EDIT CONTROL NODE**


F852 01 04	JT3	FDB	\$0104, STEPP
F856 00 04		FDB	\$0004, STEPM
F85A 01 20		FDB	\$0120, MCOM
F85E 00 08		FDB	\$0008, WAIT
F862 01 08		FDB	\$0108, INSERT
F866 01 10		FDB	\$0110, DELETE
F86A 00 20		FDB	\$0020, RPTP
F86E 00 40		FDB	\$0040, PLAY
F872 00 10		FDB	\$0010, EDIT
F876 02 40		FDB	\$0240, SLOW
F87A FF		FCB	SFF

***PAUSE WAIT NODE**


F87B 01 40	JT4	FDB	\$0140, PAUSE2
F87F 00 10		FDB	\$0010, EDIT
F883 01 20		FDB	\$0120, MCOM
F887 00 40		FDB	\$0040, PLAY
F88B 00 20		FDB	\$0020, RPTP
F88F FF		FCB	SFF

***MOTOR CONTROL NODE**


F890 01 20	JT5	FDB	\$0120, MCOM
F894 FF		FCB	SFF

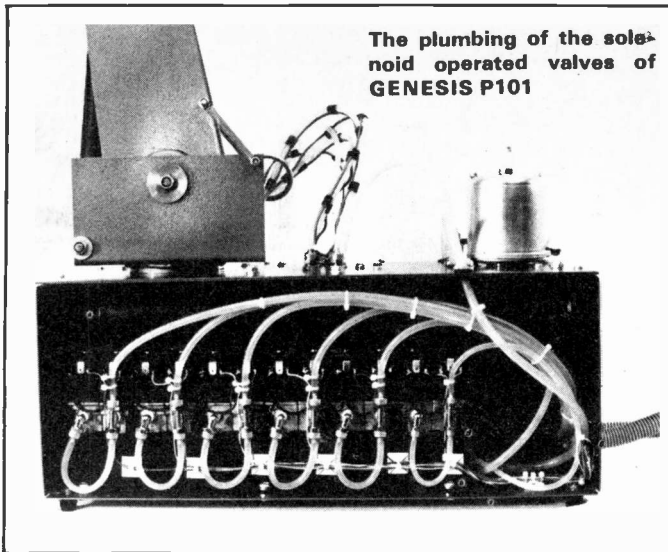

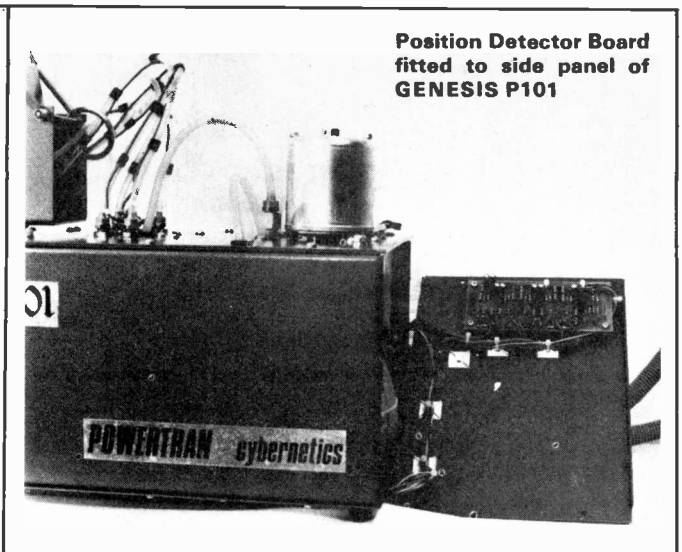
The plumbing of the solenoid operated valves of GENESIS P101



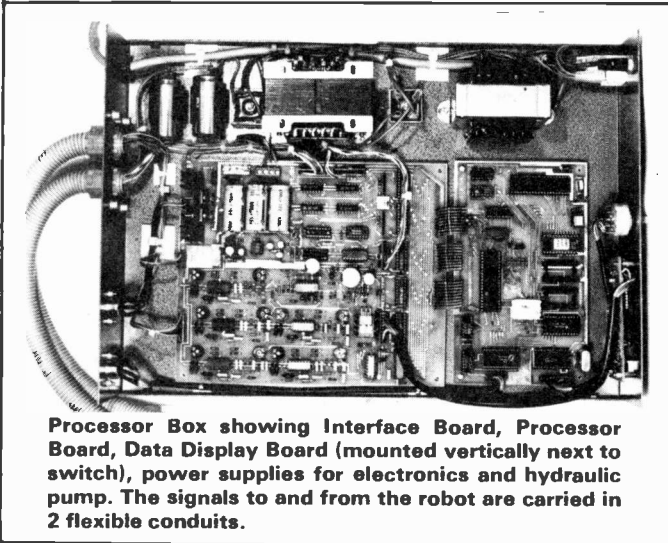Position Detector Board fitted to side panel of GENESIS P101



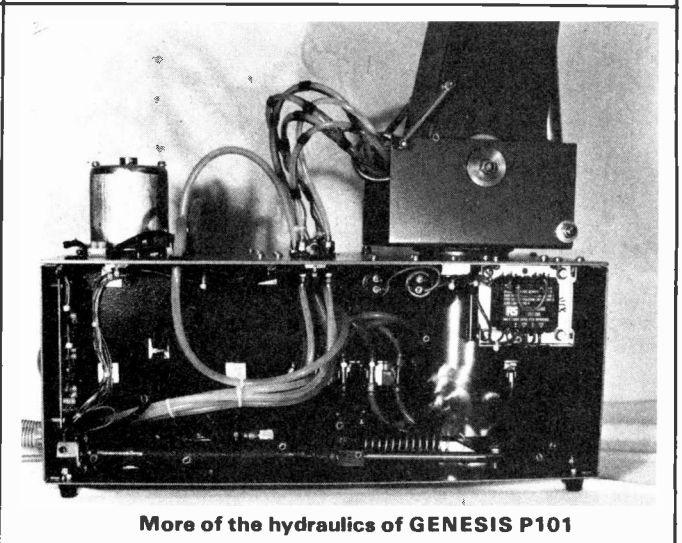Processor Box showing Interface Board, Processor Board, Data Display Board (mounted vertically next to switch), power supplies for electronics and hydraulic pump. The signals to and from the robot are carried in 2 flexible conduits.



More of the hydraulics of GENESIS P101

CONSTRUCTION OF THE ROBOTS

Despite the very large number of components making up each of the Genesis range of robots, construction is very straightforward, requiring no tools other than the screwdrivers and spanners found in most constructors' tool boxes. For convenience, in both packing and assembly, each kit is divided into a number of packs, each containing the parts for one section only of the machine together with its fixing components, so there's no chance of fitting the parts incorrectly. All details of assembly are covered in the handbook supplied with the kit. The prospect of assembling an hydraulic system may seem daunting, but with the components designed for these machines, no blowlamps, wrenches or similar tools of the plumbing trade are required. The fixed pipework is 8mm diameter flexible, clear polythene tube and the pipework on the arms is 5mm and 6mm flexible, clear nylon tube. The tube, which can be cut with scissors, is terminated with screw-on fittings (Figs. 6.2 and 6.3). The fittings which screw into the hydraulic cylinders are sealed with nylon washers whilst the larger fittings as used on the solenoid operated valves and non-return valve have tapered threads which are sealed by wrapping about 5 turns thin PTFE tape round them before screwing in.

After filling with oil, operation of the robots can be checked by applying 12V to the solenoids, either directly or via the Direct Solenoid Controller Board.

POWER-UP, TESTING AND CALIBRATION

There are several electronic units that comprise the robot system, and they are in some respects interdependent. That is, it will be difficult to test the boards in isolation, they have to be tested as a system. Wire up the interface board and the processor board (Tables 6.1-6.6). Do not insert any of the integrated circuits, other than the voltage regulators, which are soldered in anyway. Unplug index plugs PL2, 3, 5, 8, 9. Power-up the unit and test the supply rails. Check that you have two lots of +5V, a +12V rail (approximate) and a -9V rail. Refer to the circuit diagram of the interface board for these voltages. There should be very little current drain and so none of the components should be getting hot! Turn off the power and insert all i.c.s up to number IC7 on the interface board. Recheck the power supply rails. Turn off, and insert the rest of the i.c.s except IC21. Turn on and recheck the power supply rails. If everything is okay then the interface board has been safely powered up. There are a few things that can now be tested. IC5 pin 8, should be a low distortion sinewave of about 4Vpp amplitude, 100Hz frequency. The same sinewave will appear at IC6 pin 4 which is the power driver i.c. Pin 7 of IC5 is a stable voltage reference of +2.4V.

Now insert the i.c.s on the processor board. Power-up and test the supply rails. The heat sink on the interface board (+5V rails) will now begin to warm up but it should never

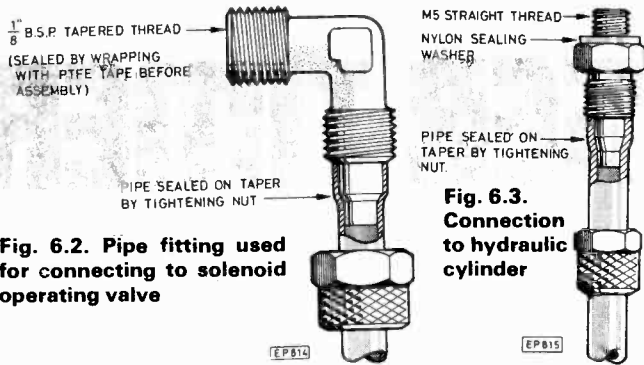


Fig. 6.2. Pipe fitting used for connecting to solenoid operating valve

Fig. 6.3. Connection to hydraulic cylinder

Fig. 6.4. Processor Box PSU wiring

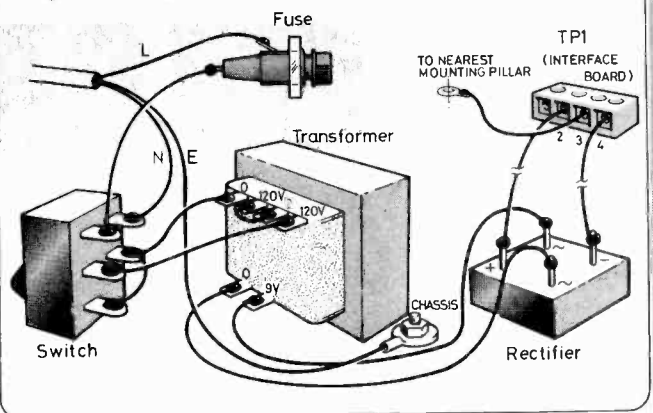


Table 6.1. Input wiring of Processor Box

Molex plug No.	DIN Skt pin	Signal
PL7-1	1	+12V
PL7-2	5	+5V
PL7-3	2	GND
PL7-4	4	—
PL7-5	3	DATA INPUT

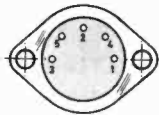


Table 6.2. Infra-red data link (Mobile only)

Molex plug No.	Receiver PCB No.	Signal
PL7-1	1	+12V
PL7-2	2	+5V
PL7-3	3	GND
PL7-4	4	-9V
PL7-5	5	DATA

Table 6.3. Display Board wiring

Molex plug No.	Display Board Pin No.	Signal
PL5-9	1	DA3
PL5-3	2	DA0
PL5-10	3	GND
PL5-7	4	DA2
PL5-5	5	DA1
PL5-6	6	DA5
PL5-1	7	+5V
PL5-8	8	DA4
PL5-2	9	DA7
PL5-4	10	DA6

Table 6.4. Baud rate wiring

Molex plug No.	Switch Contact	Signal
PL11-1	12	9600
PL11-2	11	4800
PL11-3	10	2400
PL11-4	9	1200
PL11-5	—	—
PL11-6	—	—
PL11-7	8	600
PL11-8	7	300
PL11-9	—	—
PL11-10	c	select

Molex plug

Molex plug No.	Destination	Signal
PL1-1	Solenoid common	+Vcc
PL1-2	+ Vcc (bridge rectifier or battery)	+ Vcc
PL1-3	—	—
PL1-4	0V (bridge rectifier or battery)	GND
PL2-1	S3+	SOLENOID VALVE
PL2-2	S3-	SOLENOID VALVE
PL2-3	S4+	SOLENOID VALVE
PL2-4	S4-	SOLENOID VALVE
PL2-5	S5+	SOLENOID VALVE
PL2-6	S5-	SOLENOID VALVE
PL2-7	S1-	SOLENOID VALVE
PL2-8	S2+	SOLENOID VALVE
PL2-9	S2-	SOLENOID VALVE
PL2-10	—	—
PL3-1	M13-4L, M13-4R Motor board	GND (MOBILE ONLY)
PL3-2	M13-2L Motor board	BL (MOBILE ONLY B Left)
PL3-3	M13-1L, M13-1R Motor board	STOP left and right
PL3-4	M13-5L Motor board	AL (MOBILE ONLY A Left)
PL3-5	M13-2R Motor board	BR (MOBILE ONLY B Right)
PL3-6	M13-5R Motor board	AR (MOBILE ONLY A Right)
PL3-7	—	—
PL3-8	S0+	SOLENOID VALVE
PL3-9	S0-	SOLENOID VALVE
PL3-10	S1+	SOLENOID VALVE
PL8-1	RPD pin No. 20	Detector coil 4
PL8-2	—	—
PL8-3	—	—
PL8-4	RPD pin No. 22	Detector coil 2
PL8-5	RPD pin No. 23	Detector coil 1
PL8-6	—	—
PL8-7	—	—
PL8-8	RPD pin No. 24	Detector coil 0
PL8-9	—	—
PL8-10	RPD pin No. 21	Detector coil 3
PL9-1	RPD pin No. 17	+12V
PL9-2	RPD pin No. 16	-9V
PL9-3	—	—
PL9-4	RPD pin No. 18	OSC
PL9-5	RPD pin No. 19	GND
PL10-1	—	GND
PL10-2	—	—
PL10-3	—	—
PL10-4	—	—
PL10-5	—	—
PL12-1	3	GND
PL12-2	2	CTS
PL12-3	5	RXD
PL12-4	4	RTS
PL12-5	1	TXD
PL6-4	centre	RS232 Enable

Table 6.5. Interface Board wiring



Table 6.6. RS232 wiring

Molex plug No.	DIN skt pin	Signal
PL12-1	3	GND
PL12-2	2	CTS
PL12-3	5	RXD
PL12-4	4	RTS
PL12-5	1	TXD
PL6-4	centre	RS232 Enable

become too hot to touch. The CMOS battery back-up will eventually charge up from 3.6V to 4.0V, but this may take an hour or so. A few things can be tested. The micro-processor should be generating a clock. Test IC1 pin 37; a 1MHz TTL level square wave should be generated. If the RS232 interface parts are fitted then the Baud rate generator can be tested. Test the wiper of the Baud rate selector switch. A TTL level squarewave at 16 times the Baud frequency will be seen. Next connect the position detector board into the system via molex connectors M8 and M9 on the interface board. There are 3 tags on the position detector coils. The braid of the screened cable goes to the common tag. As the coils are bifilar wound it does not matter which coil is the primary and which the secondary. Test the supply rails for a safe power-up and check for outputs which will be 100Hz sinewaves. The sinewave level will alter as the extension of the respective hydraulic actuator is changed. Next plug in the display board (molex connector M5). Upon power-up the bleeper will bleep several times. This will indicate that the program is to some extent operative. Pressing the Reset button on the processor board will repeat this event. Again recheck the supply rails. The next section to be tested is the Remote Control Unit. This will enable you to manipulate the robot and also to calibrate the presets in the system. There are two types of control unit: one is an infra-red device and the other is connected via a wire link. The infra-red unit has two analogue channels and an infra-red driver circuit, and is only intended for use with the M101 robot. All the test waveforms are shown in the timing diagram. Adjust VR1 for a clock frequency of 2KHz (IC10 pin 3). Presets VR2 to VR5 are only included on the M101 unit. Adjust VR2 so that the ramp waveform seen at IC8 pin 14 reaches a maximum of 2.4V. In fact, check that the Vref voltage is +2.4V. Put the steering pot (VR7) in its central position and adjust VR5 so that the potential on the wiper of VR7 is +1.2V. Repeat the procedure for VR3, IC8 pin 1, VR4 and VR6. These two circuits are both analogue to digital converters. VR6 and VR7 should produce full range changes in their output codes. This can be seen by monitoring the \bar{Q} outputs of IC9 pins 2 and 12.

INFRA-RED RECEIVER

Next the infra-red receiver, which is only used on the M101 unit is to be tested. Plug in the unit (molex PL7) and test the power supply rails. Check that the voltage regulator on the infra-red board is working. Check that the potential between the +12V rail and the emitter of T1 is 15V. Turn on the infra-red transmitter and point it at the receiver, using a separation of about three feet. You will be able to see the received data at IC1 pin 8 and IC2 pin 7. This data is then squared up by the comparator IC2 pins 1, 2, 3. Look at IC2 pin 1 and adjust VR1 so that nice clean waveforms are seen. Now move the transmitter away to a distance of 12 feet and readjust VR1 for the best output. The l.e.d. D5 will indicate that data is being received. You can use this as an indication of data being received. If you adjust VR1 so that it is too sensitive then the receiver will pick up noise and so generate erroneous commands. If you make it too insensitive, then the operating range will be limited. Optimum operation is at about twelve feet. Now that the manual control system is working the system can be tested. Connect the solenoids to the interface board via molex connectors PL2, PL3, plug in IC21 and power-up. For the M101 unit *do not connect the motor control* molex's PL13 as this may result in the robot dashing off and destroying itself! Upon power-up the robot arm may move which will indicate that there is life in the beast. Try out the manual control unit. Press SEQ+ a few times. The display should count up. SEQ- should make it count down. If nothing happens then test that the data is being received correctly, Fig. 6.5. Once this is working press EDIT on the control unit. The record l.e.d. on the display board will turn on and a bleep will be heard. Now you can directly manipulate the robot arm. Try moving the arm in all its axes. If nothing happens ask the following questions:

Is there any hydraulic pressure?

Can you hear the solenoid valves clicking on and off?

Is the common rail connected to the solenoids?

Do any control voltages appear at the solenoid drivers inputs (IC15 to 18, of the interface board)?

Do these voltages appear at the drivers output?

Are the drivers red hot?

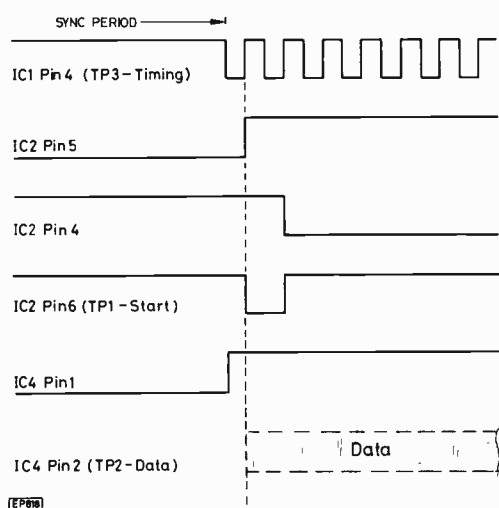


Fig. 6.5. Interface Board. Data decoding

DETECTOR CALIBRATION

When the arm actions are working it is then time to calibrate the detector circuits. Measure the voltage on pin 9 of the ADC chip (IC20). It should be +1.25V. The input range of the ADC should be twice this; that is 0V to +2.5V. Look at IC7A pin 14 and fully extend and then retract axis 0. The voltage at this point should move. Move the axis so that the voltage is at its most negative. Adjust VR2A so that the voltage is 0V. Now move the axis to its other extreme and adjust VR1A so that the voltage is +2.5V. Now return to the 0V end and readjust VR2A for an output voltage of -10mV, and then return to the +2.5V end and readjust VR1A for an output voltage of +2.51V. Now as the axis is moved, the position feedback voltage will change from -0.01V to +2.51V. Repeat this calibration process for all the other axes which have position feedback. The record mode can now be tested. Clear all memory locations. Enter EDIT mode. Move the robot arm to a position, Press INSERT. A bleep will be heard. Move the arm to another position, and press INSERT. This may be repeated until all 32 memory locations have been used up. When 24 have been used the memory full lamp will come on. When the sequence is complete, press the PLAY button. The robot will then step through the recording. The PLAY lamp will also come on. Press LOOP and the robot will repeat the sequence continuously. To use

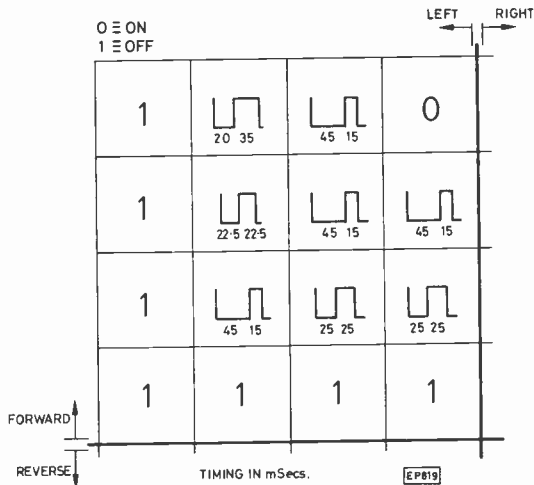


Fig. 6.6. Mark-space modulation chart. One of four quadrants (repeated symmetrically) Signal A

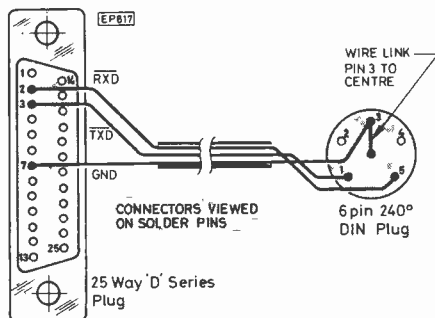


Fig. 6.7. RS232 lead. Note: The robot receives data on the RXD line, and transmits on the TXD line. It may be necessary to swap these two wires if your unit works the other way round

an external computer to control the robot, make up a lead as shown in Fig. 6.7. Plugging this in automatically puts the processor into RS232 mode.

When testing the motor control (M101 version only), jack the robot up in the air on blocks—you *don't want the thing zooming off leaving a trail of destruction!* Plug in the molex connectors (PL13) and turn on the power. Press MOTOR on the control unit. All three indicator l.e.d.s should turn on and the motors may start to rotate, this being determined by the speed and direction controls on the control unit. Centre the steering control and move the direction control. This should make the robot move forwards and backwards. There are three velocities which are obtained by using mark-space modulation. Steering is also obtained by using differential mark-space modulation, Fig. 6.6. Turn off the infra-red transmitter and the motors should stop. This is caused by the motor stop circuit IC2 pin 3 on the interface board which stops the robot when it travels out of control range. ★


THE MACROCHIP (page 28)

Did you fall for it? Puchem & Long! Just remember, it is our April issue so please don't ring us for more details like BBC Wales did the last time we published on April Fool.

Thanks to our reader Iain James for sending this in.

FOOLED AGAIN! (page 14)

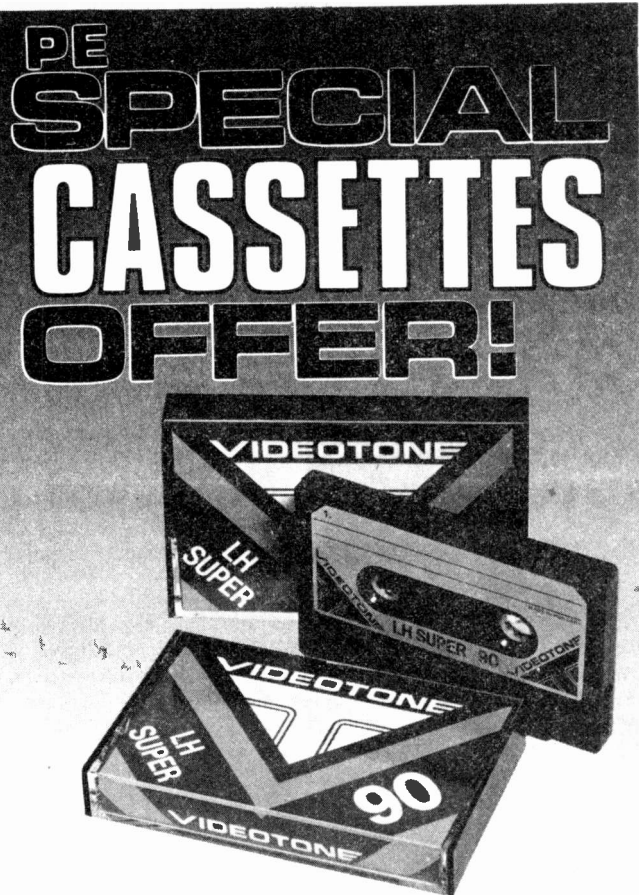You may have noticed that PROLAFOIL is an anagram of a particularly seasonal phrase—try reading the name and address of the company backwards.



C90LH CASSETTES

56p each (minimum of 5); 53p each (minimum of 25). Prices include VAT and postage

Made by a leading European manufacturer for Videotone, these tapes are of excellent quality and we are pleased to announce this new PE service.

Over the last couple of years PE offers arranged with Videotone have proved highly successful and we have now been able to arrange special prices (only available to PE readers) on these high quality tapes. The offer is a result of Videotone's direct selling policy; send in a current special PE coupon for prompt delivery of tapes.

We believe these tapes are the best value around and we are pleased to offer them to readers. They are covered by a money back guarantee (return within 21 days for refund). Not only are the tapes of high quality but the cassettes are of screw together construction and the case label has space for notes on the recordings.

Send valid coupon to: **Videotone Ltd., 98 Crofton Park Road, Crofton Park, London SE4.**

BLOCK CAPITALS PLEASE

Please send me tapes (minimum of 5) at p each. (56p for 5 to 24, 53p for 25 or more; including VAT & postage.)

I enclose cheque/PO for £

Name

Address

.....

.....

Coupon valid for posting before 8th April '82 (or one month later for overseas readers).

Strictly

Instrumental
by K. Lenton-Smith

THE American Federal Trade Commission once asserted that a certain inventor's claim that his instrument was an "organ" and that it could produce an "infinite number" of tone combinations was questionable.

The inventor, a quiet person who normally kept out of the limelight, decided to contest the government. The Trade Commission decided on an impartial panel which would listen to both an expensive pipe organ and the electric organ in question to see whether they could detect any difference. Both players were hidden from view and the speaker cabinets were concealed among the organ pipes in the Rockefeller Chapel, University of Chicago.

The jurors heard a number of test pieces played on these instruments and their answers were wrong in 10 cases out of 30. The organ's inventor was vindicated: it had been accepted as a true musical instrument. The Commission decided that the electro-mechanical device could be termed an organ but the company concerned should desist from claiming an infinite number of tones — as it could only produce 253,000,000!

THE ORGAN MAN

The year was 1937 and the inventor was Laurens Hammond. It was probably a turning point for electronic music (though Hammond called them electric organs) and was an enormous achievement in many ways, especially considering amplifier and speaker systems of the day.

Very few people have been responsible for *creating* an industry: George Eastman and Henry Ford are examples in other fields but undoubtedly Laurens Hammond laid the keel for the electronic music industry we have today. Born in 1895, he took an interest in engineering from an early age. He proposed a method of automatic transmission to the Renault Motor Co. when 14 years old and graduated from Cornell University with a degree in mechanical engineering in 1916. He served with the American Expeditionary Force in the First World War, acting as interpreter to the Commander, General Pershing.

Back in civilian life, Hammond became chief engineer to a marine engine concern but worked on his own ideas privately. Appropriately enough, his mother's maiden name was Idea Strong. His first success, a 'tickless clock', provided money enough to set himself up in business.

MOTOR

His mind turned to making a motor that would revolve in phase with the 60Hz supply: having succeeded, he found that a patent had been filed elsewhere. Even so, he discovered an application for his small, efficient motor and applied for his first patent — a three-dimensional movie system. Public interest was intense but only for a short period, despite his simplifying the method by using red and green spectacles (anaglyph principle).

Another early idea was a 'power pack' for operating dry battery receivers from the a.c. supply. This project went well — until complaints started to flood in that the converters were exploding and throwing acid over furniture and carpets! He was next to concentrate on perfecting a mains-driven electric clock and in 1928 formed the Hammond Clock Company. Profits soared over three years but the Depression saw not only his competitors going out of business but his own clocks being given away as a promotion for Wrigley's chewing gum.

Determined to survive, he produced a device for shuffling playing cards into four heaps: built into a bridge table, it was priced at \$25 but even at this level was difficult to sell when money was scarce.

Because of his connections with the cinema, he noted the revival of interest in the pipe organ. Used for accompanying the films of the day, cinema organs grew in complexity as more and more effects were required for silent movies. The quest for larger instruments culminated in the mammoth organ in the Convention Hall, Atlantic City: installed in 1932, it had seven manuals, over 1200 stops and 32882 pipes.

FLUTE

Surely, the organ was a product that could benefit from his synchronous motor, he reasoned. As a child, Hammond had seen the Teleharmonium (the first complex-tone generator), knew its principles and was determined to build a smaller and highly reliable instrument. After lengthy experimentation, he managed to produce a flute tone by using his motor to drive a contoured steel wheel in front of a permanent magnet.

Like those before him, he had produced an electrical waveform but he had also found out how it could be converted to a musical sound: the tiny current from a

winding on the magnet was fed into a radio amplifier (the valve by now being well established). The very next day, he and his team began to explore the possibilities of conventional, musical tones by electric synthesis.

Trial and error convinced him that 91 tone wheels were sufficient to produce all the musical sounds familiar to the ear. Accurate gearing had to be evolved for the twelfth-root of two ratios between tonewheel shafts but this was not a particularly difficult task for a clock company. An old piano keyboard was wired so that partials could be keyed with fundamentals — a veritable cat's cradle! Hammond's concept of an invention was coloured by his experience as a manufacturer: the product had to be rugged. The eventual solution was to key nine pitches and allow the player to mix these as he wished.

TRAILBLAZER

The patent for Model A was filed in 1934 and the instrument first available early in 1935. Many famous musicians bought the Model A, priced at \$1250: though small compared with a pipe organ, the cost was three times that of a Plymouth car in 1935. The Model B was produced in 1936 (merely a change in cabinet styling) and it was the claims for this organ that led to the story heading this article. Because very few organs from other origins existed at the time, the Hammond Organ was by now a household word for a new and exciting experience in music.

Harmonic synthesis methods were used from the earliest Hammonds but the first purely electronic synthesiser was produced in 1939 — the Novachord. Another idea from the fertile mind of Laurens Hammond, this six-octave keyboard instrument was capable of producing woodwind, brass, plucked and bowed strings, piano and organ tones. Based on master oscillator and divider strings with a wide range of envelope control and harmonic content, the Novachord was extremely popular in the field of broadcasting at the time.

His next instrument appeared in 1940. This was the Hammond Solovox, with a three-octave keyboard (capable of six octaves) designed to supplement the piano. Small dance bands used these instruments, attached below the piano keyboard, to add extra solo voices (of which it had 12) to the ensemble.

During the war years, the company produced large numbers of organs for the allied services and was also designing and manufacturing flight control systems, gyroscopes, light and infra-red sensing equipment and aerial cameras.

The few commercial organs available at the time had not been designed for use in the home as a first priority. Wartime servicemen had developed a taste for the Hammond, so the company decided to introduce the very first home spinet model in 1949 — the first of the M Series. Ethel Smith was among the many famous instrumentalists who helped to popularise these small, self-contained models. Their

great success prompted other manufacturers to follow suit.

By 1953 organs had outstripped clock manufacture, so the name was changed to the Hammond Organ Company. Laurens Hammond was determined to maintain his lead in the field and expanded his engineering staff. New instruments continued to make their appearance, percussion being introduced on Models B-3, C-3 and the M Series spinets. A self-contained console model, A-100, dispensed with the PR-40 tone cabinet required by earlier console organs. Model RT, a full concert instrument, was introduced and had an unique pedal solo system combining the synthesis methods used in the Novachord and Solovox.

The energetic founder retired in 1960, leaving others to continue the concern to which he had given so much impetus.

THE CHIP

Theatre organ sounds with an ultra-modern pedestal console were introduced with the X-66 in 1965. The X-77 was produced in recognition of the influence of jazz organists: essentially this was a new version of the popular B-3 but with extra tonal facilities and power output.

The beginning of the company's watershed was in 1967, when the J-Series all transistor organs first appeared: these were the first all-electronic tab-controlled Hammonds. The Piper Autochord made its debut in 1970 as the first automatic chording instrument: the circuitry provided the bass line so no pedals were fitted.

LSI circuitry was first incorporated in the Phoenix organ in 1972. This was a tab-controlled organ but later that year the Concorde became the first LSI/drawbar in-

strument. Many Hammond enthusiasts averred that nothing would ever equal the sound from tonewheel generators although I was impressed when I heard this organ at its presentation concert.

The company had to march with the times — the call for greater portability and consideration of the steeply rising costs of precision engineering. In turning from tonewheels to LSI, the company had created its own challenge: it handled that situation with flair, as subsequent models have proved.

No doubt Laurens Hammond was also pleased that this radical changeover had been so successful as this happened a year before his death in 1973. He left behind him a massive international industry, part of which bears his name and has continued in his inventive vein with the success and prestige it has always merited.

Readout...

Calling Members

Sir—Congratulations on your excellent stand at 'Breadboard 81', and I am only sorry that your fascinating Robot was not handing out B.A.E.C. forms, so obviously it was not programmed correctly!

I would appreciate it if you could mention in your very popular magazine the following B.A.E.C. members, as unfortunately their addresses have been mislaid, and I am holding for them a complete set of the B.A.E.C. 982 Newsletter.

O. Josephs (BE 81544)
R. P. Horne (BE 81546)
J. R. Woods (BE 81548)
A. Brookman (BE 81550)

If any of these members see this announcement, I would appreciate it if they would contact me at the address given below and send me their membership card, and address, of course, and I will then forward them their complete sets of 1981 Newsletters.

I appreciate your help, and would like to congratulate you on your excellent magazine for electronics enthusiasts.

Cyril Bogod,
B.A.E.C.
"Dickens",
26 Forrest Road,
Penarth,
S. Glam.

Too Much Detail?

Sir—Since you have stated from time to time that you welcome feedback from readers, may I make a few comments which may be helpful.

General layout is good and regular features such as Market Place, Microbus, Spacewatch, etc. are obviously of greater or less interest to readers depending upon their outlook.

The weakest point so far comes in the constructional projects. It looks as if these are being presented in their full length merely in order to pad out the magazine. Are you really so

short of material? To take one current example, how many readers are actually going to build an industrial robot? Very few I imagine. An article on the current state of the art, such as the first in the series, could have usefully been followed by an outline description with a block diagram of the available kits. It was hardly necessary to give such very detailed instructions unless it was to save the kit maker the cost of printing.

A similar criticism must also apply to other projects i.e. Ranger, etc. and Bandbox appears to be going the same way.

If you print p.c.b. layouts then how about a good article about making them from magazine articles. You seem to have ignored this, at least in the last three or four years. This could be linked with an offer from one of your advertisers.

The index to each volume is welcome but would be of much more use if it was a pull-out. Surely this is not too difficult to arrange?

CB? Yes, well it is in the news at the moment but don't go overboard, there are plenty of specialist mags dealing with it. In any case it will soon be the domain of a small band of enthusiasts. Remember the skateboard?

I hope these remarks have been of some use. I do not despair of the magazine entirely. If I did I would not have bothered to write to you. Best of luck for the future.

I. R. L. Morom,
Redditch.

Thanks for your comments—we are always pleased to see constructive criticism of this kind.

When I first took over as Editor of PE some four years ago, I felt (as you do) that much of the constructional information could be dispensed with. I was quickly put right by many readers who pointed out that this was the strength of PE. You would perhaps be surprised how many readers want even more constructional information on all our projects! Don't forget that in many cases there would be no kits without the magazine articles to

launch them. We are not short of material, but we will not lower our standards just to cram more in. However, we have now managed to add to the number of editorial pages to give us a little more space for everything.

Point taken on p.c.b.s.; what are other readers feelings on a pull-out index? Remember it would then take four pages rather than the two-and-a-half it took last year. Rest assured we won't go over the top on CB—Ed.

Unsatisfactory Update

Sir—When I first started reading Practical Electronics, it seemed to me that Semiconductor Update was one of the most useful features in the magazine. Until, that is, I tried to get some of the components described therein.

Take the November 1981 column for example. It describes an 8-channel, automatic-sampling ADC chip, the AD7581, that "does not cost an arm and a leg". This device sounds so good that it probably makes all other ADCs of equal accuracy obsolete, but so far as the hobbyist is concerned, it doesn't cost anything because it isn't obtainable. I picked this one example because it happens to be a device I would use, but the same is true of nearly all devices featured in Semiconductor Update.

A possible solution would be for you to give retailers who advertise in PE some advance notice of which devices are to be featured in Semiconductor Update, and then to mention in the column the names of any retailers who expressed an interest in stocking those devices. This isn't a perfect answer, but it would probably be better than the present unsatisfactory situation.

Dr. N. J. D. Jacobs,
Brentwood,
Essex.

The problem is that companies are not willing to stock items that may not sell—and who can blame them. If 'Update generates an interest then suppliers will take stock.

Of course many items mentioned are only just on the market—we like to be "up to date"—and it is often some time before they are available even from industrial distributors.—Ed.

MICRO PROMPT.

The hardware and software exchange point for PE computer projects

SIMPLE SAVE BY NAME

Sir—This program enables you to name all your programs and load them back from tape by name. It will work on both the UK101 and Superboard 11 computers.

To use it just add two lines to your programs both Rem's the first contains the program name the second is just padding.

```
eg: 5 REM* NAME# (Enclose the
      6 REM          program name
                    with * and #)
```

After putting these two lines at the beginning of your program save in the usual way.

ie: Type SAVE (return) then LIST (return).

The program will then be stored on tape. When the computer comes back with OK stop the tape, type PRINT "POKE 515, 0" restart the tape and press return. (This is used when loading back the program to switch off the load flag to stop any other information being loaded.)


If you use the same line numbers in your programs as in SEARCH program, not only will it load but while loading the SEARCH program will be automatically deleted leaving the entire memory for use.

```
10 REM:*SEARCH#
20 REM
30 FORX = ITO24: PRINT: NEXT:
  INPUT "Programme name"; NS
40 PRINT "Press play on tape"
50 FORT = ITO3000: NEXT:
  PRINT "Searching for"; NS
60 XS = " "; F = 0: CA = 61440:
  POKE515, 1
70 WAIT CA, 1: P = PEEK (CA + 1)
80 IFF = OANDP <> 42THEN70
90 IFP = 42THENF = 1: GOTO70
100 IFP = 35THEN160
110 IFP = 32THEN70
120 IFLEN(XS) > 7THEN60
130 XS = XS + CHR$(P): IFXS <>
  NSTHEN70
140 POKE515, 0: PRINT "Loading";
  XS
150 GOTO180
160 POKE515, 0: PRINT "Found ";
  XS; " "
170 GOTO60
180 LOAD
OK
RUN
```

```
Programme name? 3D
Press play on tape
Searching for 3D
Found 'SEARCH'
Found 'HEX'
Loading 3D
```

D. I. Swift,
Doncaster.

Fig. 1. Selective inverse video. S1 gives full field inverse, which could be made into another software option by using a second latch

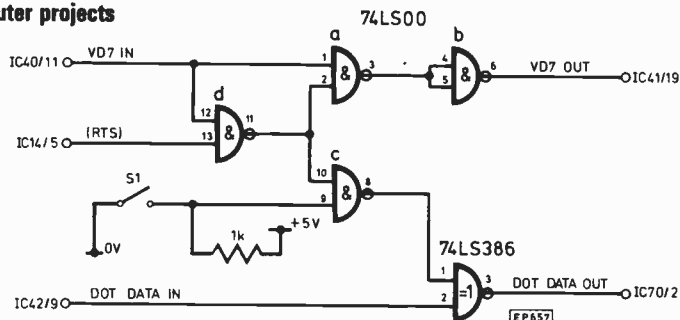

SECRET SCREENWRITING

Sir—I wonder if your readers would be interested in a simple extension of the "secret" key polling sub-routine by J. M. Leach of Deal, Kent, for the UK101 published last March.

This program based on the New Monitor allows you to write direct to the screen with full control of the cursor, viz:

RUB OUT: Moves Cursor LEFT: Retyping corrects any mistakes

CTRL RUB OUT: Moves Cursor UP

SPACE: Moves Cursor RIGHT

CTRL=/-: Moves Cursor DOWN

RETURN: Moves Cursor to LEFT margin and DOWN one line ie. carriage return.

```
10 GOSUB 100
15 REM HAS RETURN BEEN
  ENTERED?
20 IF A = 13 THEN 60
25 REM HAS RUB OUT BEEN
  ENTERED?
30 IF A = 28 THEN 62
35 REM HAS CTRL RUB OUT
  BEEN ENTERED?
40 IF A = 220 THEN 64
45 REM HAS CTRL =/- BEEN
  ENTERED?
50 IF A = 237 THEN 66
55 ? CHR$(A); : GOTO 10
60 ? CHR$(10); : ? CHR$(13); :
  GOTO 10
62 ? CHR$(8); : GOTO 10
64 ? CHR$(11); : GOTO 10
66 ? CHR$(10); : POKE 10
  POKE 11,0 : POKE 12,
  253 : X =USR(X) : A = PEEK
  (531) : RETURN
```

CTRL L Clears the screen as normal and returns the cursor to the home position (top left hand corner). This program allows messages to be displayed on the VDU and changed as required.

The alteration of line 55 to 55? A; : ? CHR\$(A); : GOTO 10 allows the values of A to be printed out so that new IF A = "" statements can be devised.

Revd. P. R. Miller,
Milton Keynes.

AUTO-RUN

Sir—When loading a BASIC program it is tedious to have to wait until the program is loaded from cassette to avoid loading un-

SOFT INVERSE VIDEO

Sir—By connecting the circuit shown in Fig. 1, to the video circuit of the Compukit, software control of inverse video is possible, which extends the flexibility of the

already extensive graphics. Programs can then include routines for displaying selected areas of the screen inversely (black letters on white background).

This is achieved by inserting an exclusive OR gate in the video line between IC42 and IC70. Its inverting input is controlled by software, operating a latch (this may be the inherent latch in IC14 RTS as shown in Fig. 1, or from a latch provided by any of the published Compukit Extension Projects).

The display data line 7 (VD7) is used for selectivity. When the latch (RTS) is low, VD7 in = VD7 out and the display is normal. When (RTS) is high AND VD7 in is high, then VD7 out is low. Characters having a value above 127 are reduced in value by 128 and displayed inversely.

This is shown by the following program which displays "UK101" in black, onto a white rectangle, below which is displayed "UK101" in white.

```
5 FOR I = ITO16 :? :NEXT
10 A = 53400 : POKE 61440,81
20 FOR I = A + 64 TO A + 79: READ
  B
30 POKE I,B: POKE I+ 320,B:
  NEXT:GOSUB 100
40 A=A+64 : GOSUB 100: A=A+64:
  GOSUB 100
50 GOTO 50
60 DATA32,32,85,32,75,32,32,32,49,32,
  48
70 DATA32,49,32,32,32
100 FOR I = A TO A + 15 : P =
  PEEK(I)
110 P = P+ 128: POKE I, P: NEXT:
  RETURN
```

Line 10 operates (RTS) latch and line 110 puts VD7 high over selected rectangle. Normal video can be restored by Warm Reset or in program by Poking 61440,17

wanted noise at the end.

Typing POKE515,0:RUN followed by Return in immediate mode after the program has been SAVED, records the latter on the tape. The recorder is then switched off, and on loading the program, the LOAD flag is turned off, and the program RUNS AUTOMATICALLY.

Roger Darbishire,
King's Lynn, Norfolk.

CEGMON COMPATIBLE TRACE

Here is a trace program for UK101 which runs under CEGMON without destroying the printing format. It should also run on the Superboard and under other monitors, providing the CTRL C routine is at HEX FB94. It takes advantage of the fact that BASIC stores any number to be output at locations HEX 0100 to 0105 in decimal digits.

After you've cold started, try this:

FOR I=256 TO 261: CHR\$(PEEK(I)); NEXT

The result will be the last number output, i.e. the number of free bytes. The program is adapted from the one in the CEGMON manual.

0294	A9	FF	LDA	£FF
0296	85	5F	STA	5F
0298	A9	80	LDA	£80
029A	85	64	STA	64
029C	20	53 B9	JSR	B953
029F	A2	05	LDX	£05
02A1	BD	00 01	LDA	0100,X
02A4	9D	36 D0	STA	D036,X
02A7	CA		DEX	
02A8	D0	F7	BNE	02A1
02AA	C6	64	DEC	64
02AC	4C	94 FB	JMP	FB94

If your screen is not 48 characters wide, then byte 02A5 can be changed from HEX 36. HEX 20 should suit even a 25 column screen.

As the program is in page 2 of memory, it is unaffected by a COLD START. It can be moved elsewhere but for ease of use it should start at XX94, i.e. any memory location ending in 94. As listed, it is turned on by POKE 541,2 and turned off by POKE 541,251. When a BASIC program is running, the current line number will be displayed at the top right corner of the screen, and the extra routine does not slow program execution too much, even in a long FOR-NEXT delay loop.

A simple modification will permit single-stepping line by line through a program, waiting until a key is pressed before going to the next line. Make the following changes:

02AC	20	00 FD	JSR	FD00	wait for key to be pressed
02AF	4C	94 FB	JMP	FB94	do CTRL C check (exit)

As the program occupies only 27 bytes, it's hardly worth putting it on cassette. Enter the program by RESET M 0294 then enter each byte (HEX pair) followed by RETURN. You can then COLD or WARM start as required.

Here is a subroutine which can be called from BASIC, which will scroll the screen contents down instead of up. This has applications in games where it is desired to

390 SUGGESTIONS

UK 101-to-Data Dynamics 390 problems? Try the following:

1) Make either 110 Baud rate mod of March/June 1980. Break connection between IC62/12 and R72/R63, then reconnect

02CC	A0	FF	LDY	£FF
02CE	A9	00	LDA	£00
02D0	85	13	STA	13
02D2	A9	D7	LDA	£D7 (D3 for 16 line screen)
02D4	85	14	STA	14
02D6	A9	40	LDA	£40
02D8	85	15	STA	15
02DA	A9	D7	LDA	£D7 (D3 for 16 line screen)
02DC	85	16	STA	16
02DE	B1	13	LDA	(13),Y
02E0	C9	CF	CMP	£CF
02E2	F0	0B	BEQ	02EF
02E4	91	15	STA	(15),Y
02E6	88		DEY	
02E7	D0	F5	BNE	02DE
02E9	C6	14	DEC	14
02EB	C6	16	DEC	16
02ED	D0	EF	BNE	02DE
02EF	60		RTS	

set CTRL O flag (don't print)
force current line no. into
0100-0105

get digits of line no. and
'poke' to top right corner of
screen

reset CTRL O flag
do CTRL C check (exit)

create an impression of moving forward through obstacles, or of falling missiles etc.

To use the scroll-down routine from BASIC, try

**10 POKE 11,204 : POKE 12,2
20 FOR I = 1 TO 32 : X = USR(X) :
NEXT**

or for new BAS 1/3 chips:

**10 FOR I = 1 TO 32 : CALL 716 :
NEXT**

To scroll diagonally, POKE 727 with 63 or 65 before calling the routine. It works by loading every screen byte in sequence starting at the bottom, and storing it at a location which is greater by HEX 40 (64 decimal). It ends when the byte loaded is CF, which is what it sees when it leaves the top of the screen, despite the fact that there are no memory locations from C00 to CFFF.

As it stands, the contents of the top line will be left over the other lines. An extra routine to clear the top line is:

02F0	A2	40	LDX	£40
02F2	A9	20	LDA	£20
02F4	9D	00 D0	STA	D000,X
02F7	CA		DEX	
02F8	D0	FA	BNE	02F4
02FA	60		RTS	


POKE 11 with 240 to let X=USR(X) know where to jump.

The following gives an effect of travelling through stars:

10 S=53248 : N=5
20 FOR I=0 TO N*RND(1) : POKE
S+63*RND(2),46 : NEXT
30 CALL 716 : CALL 752 : POKE S,32 :
GOTO 20

This works nicely even if the direction of scrolling is altered during the execution of the program, by POKEing 727 with 63 or 65, depending on which SHIFT key is pressed.

David Henniker,
Edinburgh.

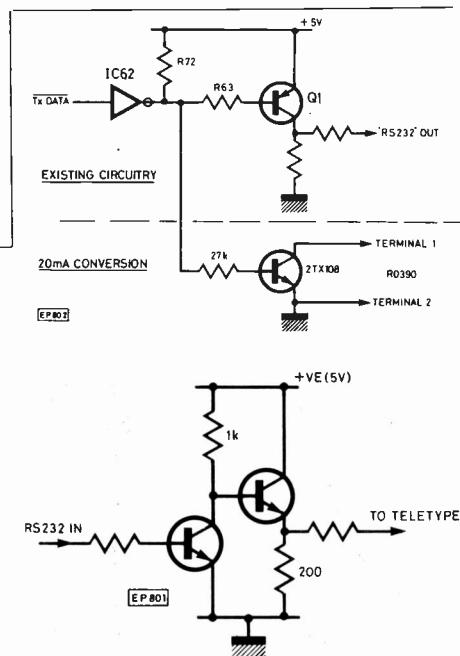

R72/R63 to Tx DATA (IC62/13), to remove data inversion. At the inside rear of the 390 is a 4-terminal block. Connect twin cable to the two left-hand terminals (facing block). Other end of the cable to pins 3 and 7 of J3 (RS232 out). A reduction in value of R65 cures any drop-outs. M. C. Saltmarsh, Chelmsford.

2) To obtain the required voltage swing from Compukit's serial output, the following circuit is recommended by S. Burton, York.

3) Clock IC57 from C5. Connect IC58/4 to IC58/5. Break between IC57/12 and IC58/4. ACIA will now transmit at 110 Baud. The 390 may require buffering and inverting. A circuit is supplied by B. J. Hill, Birmingham.

THE UK101 displays 48 characters per line on 16 lines. This conversion allows the user to select an optional 48 x 32 format. The characters become much more legible, and the doubling of the vertical resolution on display is a useful improvement when plotting graphs or drawing diagrams. Program listings provide double the information per page.

The VDU RAM is increased from 1K to 2K bytes, and is controlled by a modified version of the new monitor PROM, so that the line edit facility is available.

In order to check that the display being used has enough resolution for 32 lines, take IC60 pin 12 to +5V momentarily: two identical 16 line pages are displayed.

This conversion includes a means of selecting the three different monitor PROMS, (old 16 line, new 16 line, and new 32 line). Whilst Reset is held, this switch may be operated without losing programs.

One p.c.b. would be required; 8 new i.c.'s and the new PROM are required. Power can be obtained from the existing PSU.

HARDWARE

The current machine has 1K VDU RAM from D000 to D3FF. The hardware counting chain scans this onto the screen. C7 is not used, so each horizontal line is repeated (see p7, Fig. 2 in the manual).

The converted machine has 2K VDU RAM, D000 to D7FF. C7 is now used, and C14 is used to select between the two half pages, D000-D3FF and D400-D7FF. All the other counters are used as before.

A three way switch is provided to select between the three monitors. Six t.t.l. i.c.'s, two 2114's (for the extra RAM) and a new 2716 EPROM are required. If Reset is held while switching monitors, followed by warm start, programs are not lost. Thus program development can be carried out with 32 lines while setting up display graphics for 16 lines eg. for games.

IC102 and IC103 switch the counter outputs from IC60, 61 and 30 so that C7 is brought into use for 32 lines. They are activated by the three way switch. A change is needed to the VA signal generated by IC56 (currently active low when D000-D3FF selected, to enable the CPU to access the VDU RAM). IC56/2 is taken to +5V, instead of A10. VA becomes VA' active for D000-D7FF, VA' is used to activate IC105, which takes the place of the switch formed by pins 9, 10, 11 of IC55. IC104 is used to decode A10 and 02 into the memory select signals M1S, M2S, for the two page "halves".

The RVE and WVE signals also have to be changed to RVE', WVE' to allow 2K VDU RAM. IC106 provides this decoding replacing part of IC20's function.

IC101 provides six inverters required in various places in the circuit. IC107-110 are the 4 VDU RAM chips (two of which are already on the main p.c.b.: IC39, 40).

Besides the connections for data and address lines to the VDU RAM and the ROM'S, some 25 connections have to be made to the main p.c.b. along with a number of track cuts. (The prototype board is "piggy-backed" on two pillars on the main p.c.b. and the connections made with ribbon cable). The track cuts are needed to disconnect the lines from IC60, 61, 30 to

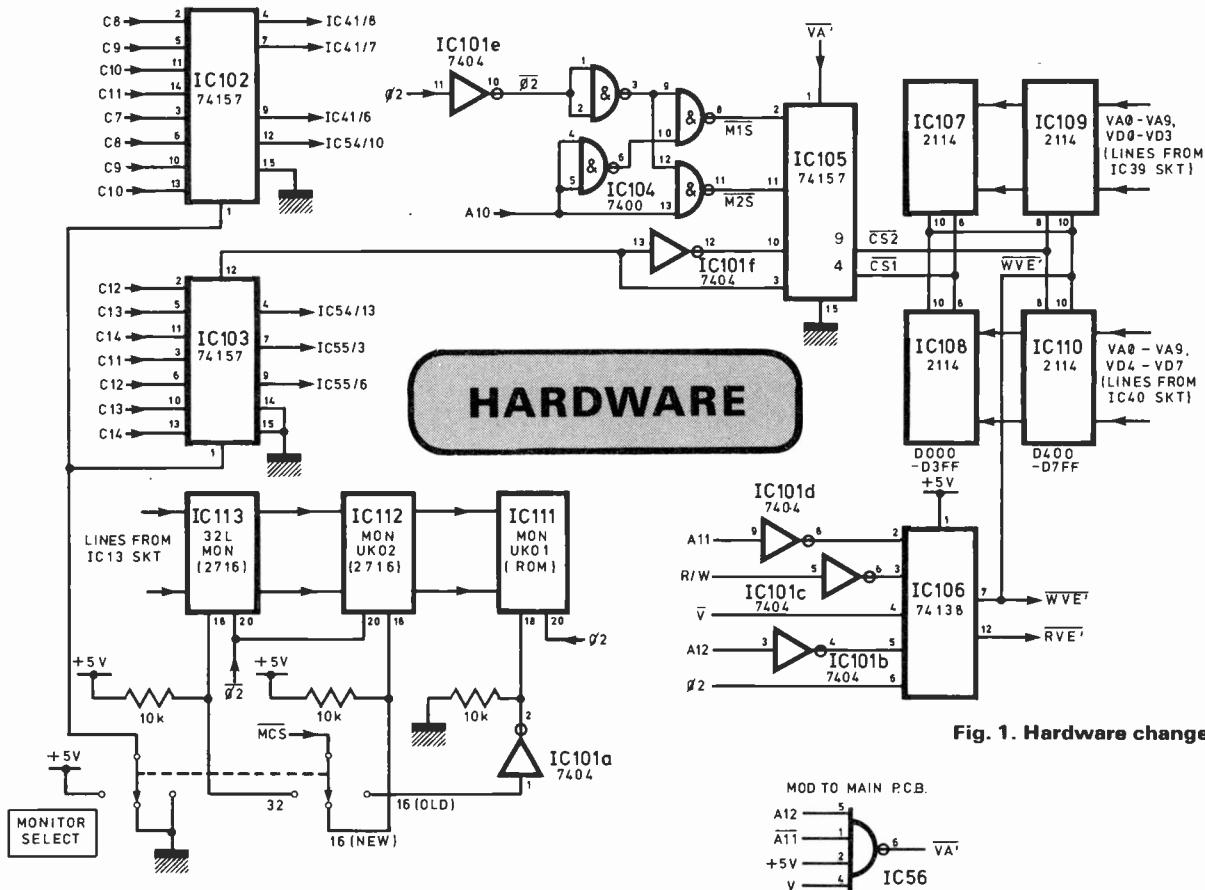


Fig. 1. Hardware changes required.

IC41, 54, 55, and to disconnect A10 from IC56, and WVE, WVE, RVE.

SOFTWARE

The program in the new monitor requires alteration to:

Screen print routine — to allow 32 lines

Clear screen routine — to allow 32 lines (and optionally remove the scroll when the top of the screen is blank)

More Display

Up one line routine — to allow 32 lines

Form Cursor Address

routine — to allow 2K VDU RAM

A total of 36 bytes require to be altered.

The firmware changes required are detailed below. The new program should be put into a 2716 (2K) EPROM, using the same address as the existing monitors (F800–FFFF).

The monitor program is completely unchanged except for the 36 bytes detailed.

Additionally, the byte at FB5B (currently FF) can be changed to 00 if desired. This removes the rather irritating scroll up on the screen every time the top line becomes blank for any reason.

POWER SUPPLY

No problems have been found driving the new board from the existing PSU, although the regulator is already mounted on a large heat sink outside the case. A simple 5V, 1A PSU using a 7805 3-terminal regulator could however be constructed if required. All the i.c.'s should be LS types.

POWER

+5V IC101/14, IC102/16, IC103/16, IC104/14
IC105/16, IC106/16, IC107–IC110/18, IC111–IC113/24
0V IC101/7, IC102/8, IC103/8, IC104/7, IC105/8
IC106/8, IC107–IC110/9, IC111–IC113/12

CONNECTIONS TO NEW BOARD

IC60/12 (C7)
IC60/11 (C8)
IC61/14 (C9)
IC61/13 (C10)
IC61/12 (C11)
IC61/11 (C12)
IC30/14 (C13)
IC30/13 (C14)
IC56/6 (VA)
IC18/5 (V)
IC8/22 (A12)
IC8/20 (A11)
IC8/19 (A10)
IC8/39 (02)
IC8/34 (R/W)

IC41/8
IC41/7
IC41/6
IC54/10
IC54/13
IC55/3
IC55/6

RVE'—CONNECT IN PLACE
WVE'—OF EXISTING RVE, WVE

(PLUS 5V, ZERO VOLTS)

VA0–VA9, VD0–VD7 (FROM IC39, 40 SOCKETS)

—BUS CONNECTIONS

ALL CONNECTIONS FROM MONITOR (IC13) SOCKET, EXCEPT PINS 18, 20

IC19/6 (MCS) FOR MONITOR SELECT SWITCH

CIRCUIT

The sockets for IC39, 40 were used to obtain the VDU data and address lines. Similarly, the socket for IC13, to obtain connections for the monitor ROM and PROMS.

The pin connections for +5V and 0V to all the i.c.'s are also listed below.

Ribbon cable forms a suitable flexible means of interconnection between the boards.

GENERAL

The prototype is made up on a piece of veroboard, about 205 × 102mm, with the i.c.'s all on d.i.l. sockets. Quite a bit of wiring is involved, so careful checking of all connections is essential.

A few 100n ceramic capacitors should be connected between +5V and 0V to aid decoupling.

SOFTWARE CHANGES (TO NEW MONITOR)

ADDRESS (ABSOLUTE)	ADDRESS (PROM)	FROM	TO (HEX)	CHANGE BYTE	ROUTINE
FACA	2CA	10	20		SCREEN PRINT
FAF1	2F1	10	20		
FB2D	32D	D4	D8		CLEAR SCREEN
FB61	361	D4	D8		MOVE DISPLAY
FB85	385	D3	D7		UP ONE LINE

NEW ROUTINE

Delete routine from FB8D (38D) to FBAB (3AB)

(This routine forms the cursor address and stores it in 00E3, 00E4)

REPLACE WITH:

FB8D	38D	A9	1A	LDA	#S1A
	38F	85	E4	STA	\$E4
	391	AD	08 02	LDA	\$0208
	394	0A		ASL	A
	395	0A		ASL	A
	396	0A		ASL	A
	397	0A		ASL	A
	398	26	E4	ROL	\$E4
	39A	0A		ASL	A
	39B	26	E4	ROL	\$E4
	39D	0A		ASL	A
	39E	26	E4	ROL	\$E4
	3A0	6D	07 02	ADC	\$0207
	3A3	69	0D	ADC	#\$0D
	3A5	85	E3	STA	\$E3
	3A7	60		RTS	
	3A8	EA		NOP	
	3A9	EA		NOP	
	3AA	EA		NOP	
FBAB	3AB	EA		NOP	

TRACK CUTS (ORIGINAL p.c.b.)

DISCONNECT CONNECTIONS BETWEEN:

IC60/11 (C8)	AND	IC41/8
IC61/14 (C9)	..	IC41/7
IC61/13 (C10)	..	IC41/6
IC61/12 (C11)	..	IC54/10
IC61/11 (C12)	..	IC54/13
IC30/14 (C13)	..	IC55/3
IC30/13 (C14)	..	IC55/6
IC56/2	..	AT0
IC20/12	..	RVE
IC20/7	..	WVE

MODIFICATION ON ORIGINAL p.c.b.

CONNECT IC56/2 TO +5V

SOFTWARE

telectric Electricity COST MONITOR

STEPHEN

B.Sc. C.Eng. M.I.E.E.

PART TWO

DETAILS of the display p.c.b. are shown in Figs. 9, 10, and 11. All links through the board should be soldered first and those underneath the l.e.d. displays should be cropped short on the component side. The top end of each seven segment display is marked with a coloured spot. The pins for attaching the connecting wires to the main p.c.b. are inserted from the component side so that they protrude inwards from the front panel. The legs of the push buttons are left full length and are also used to solder the connecting wires onto.

FRONT PANEL CUT-OUTS

Dimensions for the cut-outs in the front panel are shown in Fig. 12. The shape of the cut-out for the 13A socket can be adjusted to suit any particular make. The best way to mark out the front panel is first to cover it with strips of masking tape. This can then be drawn on and it also protects the surface from scratching during cutting. The rocker switch S1 is fitted through from the front of the panel before soldering the connecting wires to it. The display p.c.b. is held in place by making two plastic brackets from the spare plastic cut from the front panel holes as in Fig. 13. These are glued together with instant (cyanoacrylate) glue and then to the back of the front panel during final assembly after testing.

Fig. 14 shows how $1\frac{1}{2}$ turns of the neutral lead to the 13A socket are wound onto the current transformer after removal of the low voltage winding with a knife or wire cutters. Correct loading of the current transformer was discussed in Part 1 of this article. The voltage developed across the load resistor should be measured with a high impedance meter $>10k$ or else using an oscilloscope when the peak to peak voltage will be $2.83 \times \text{r.m.s.}$

THE MICROPROCESSOR

The 8035 microprocessor is one of a range of single chip microcomputers first manufactured by Intel. The internal architecture of the chip is shown in Fig. 15. The program counter contains the address of the next location to be read from the program memory. The contents of this memory location are decoded in the instruction decode register and then the instruction is executed, which might be to increment one of the data registers or to use the ALU to logical AND the accumulator with data contained in the next bytes of the program, etc. There are in fact nearly one hundred different instructions which the 8035 will execute making programming straightforward and efficient in program memory usage.

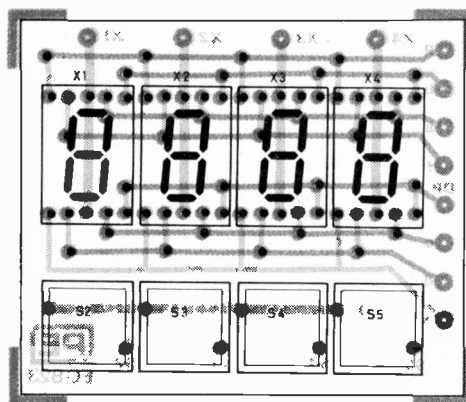


Fig. 9. The display p.c.b.

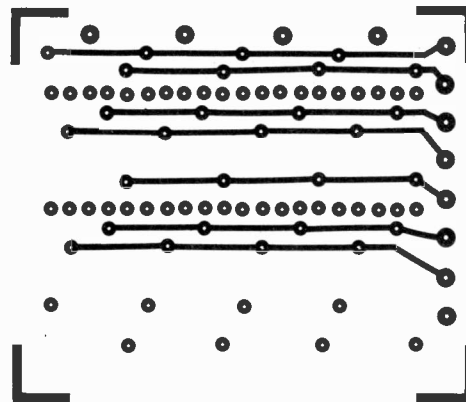


Fig. 10. P.c.b. topside

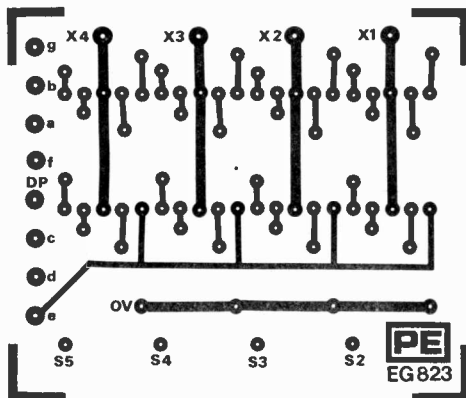


Fig. 11. P.c.b. underside

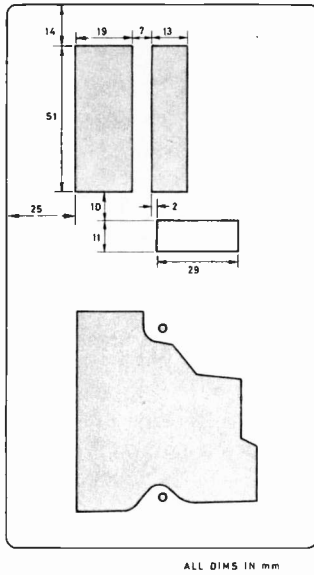


Fig. 12. Front panel cut-outs

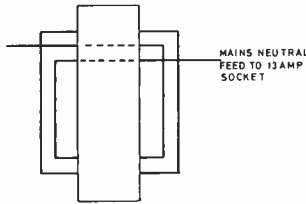


Fig. 14. Winding current transformer primary

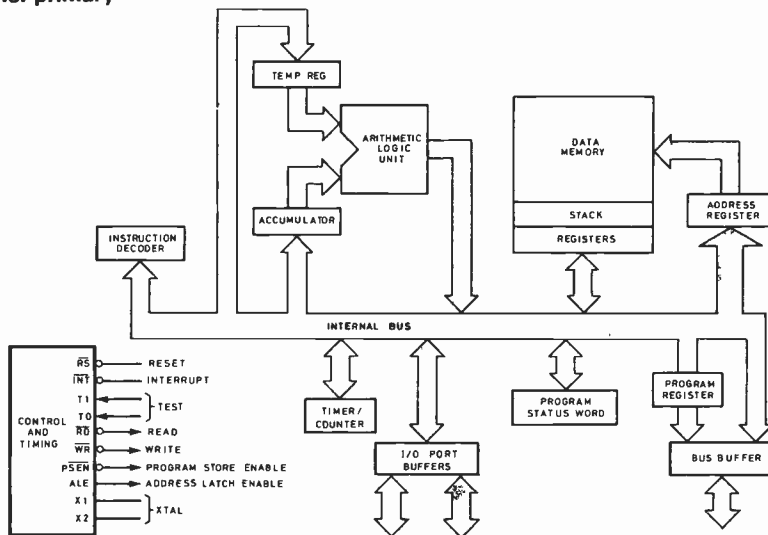


Fig. 15. Internal architecture

The on-chip data memory is 64 bytes and the division of this into two working register banks, stack and user RAM is shown in Fig. 16. The addressing modes for access to this memory area are also shown. The program is stored in EPROM and certain locations are reserved for special functions as shown in Fig. 17. When power is switched on the reset pin is held low by a capacitor until it has charged up and then the processor gets its first byte of program information from location zero. This will be a jump instruction to the start of the main program. As this is a two byte instruction, location 1 is also accessed.

The test inputs are provided which can be used to

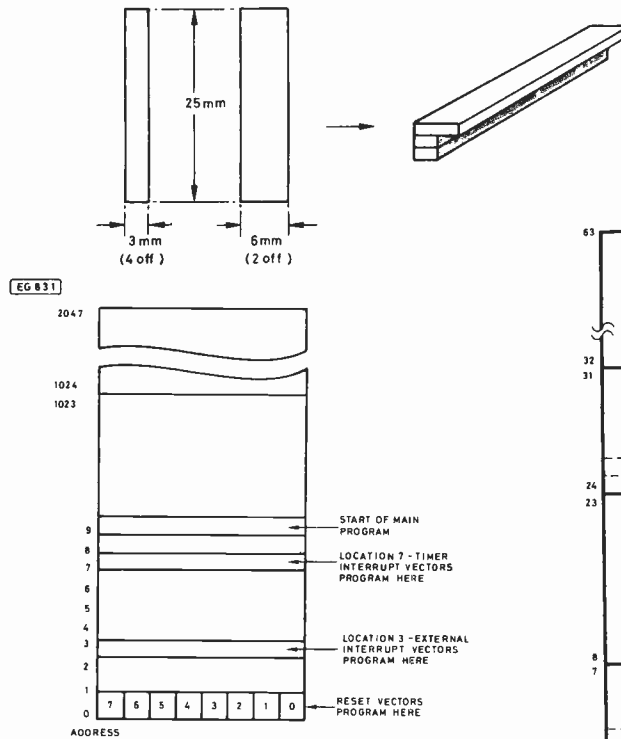


Fig. 17. External program memory map

Fig. 13. Making brackets to hold display p.c.b

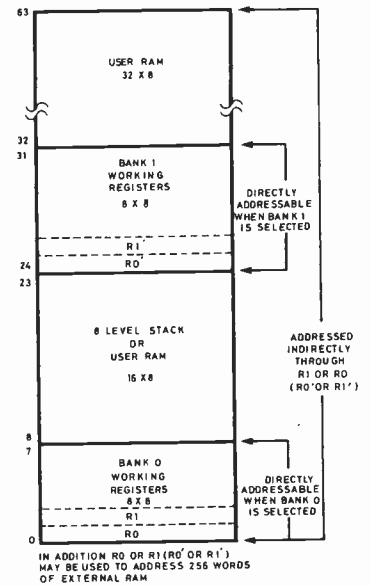
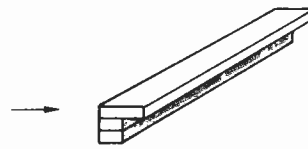


Fig. 16. Chip data memory

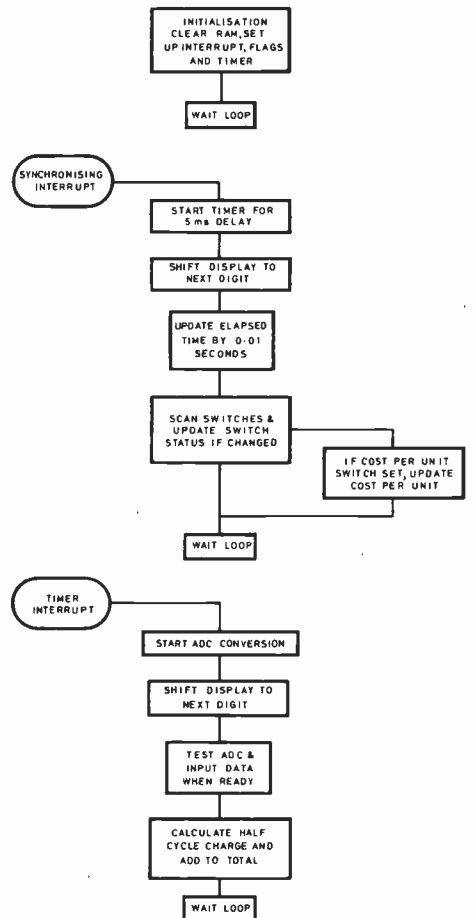


Fig. 20 (right). Software flowchart

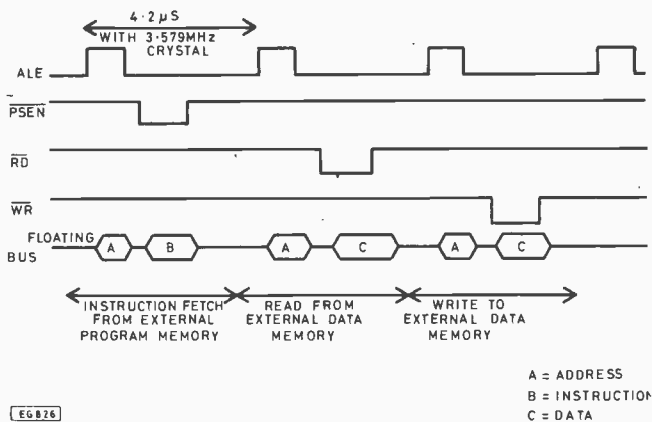


Fig. 18. Timing of external memory control signals

monitor external functions, the T1 input being used to test when the ADC conversion is complete. A low input to the interrupt pin causes the processor to terminate its current program sequence, store the next program address on the stack and then jump to location 3 where it gets the address of the interrupt service routine.

The relative timing of the external memory control signals is shown in Fig. 18. The falling edge of the address latch enable is used to strobe the address into the latch for both external data and program memory cycles. Program store enable occurs only during a program memory fetch and is used to enable the tri-state output buffers of the EPROM. The read and write signals are used to strobe data to or from external data memory.

In this particular implementation the two I/O ports are used to drive the display so that data from the ADC and the switches is read by considering them to be external data memory (memory mapped I/O). Also, as there are only two devices to select, a single address line can be used for each (a technique known as linear selection). This makes decoding easy as it is necessary to have only address line zero low for the ADC (address = 1111110) and address line one low for the switches (address = 1111101).

THE A/D CONVERTER

The ADC 0804 is a CMOS, 8-bit, successive approximation A/D converter with an accuracy of ± 1 bit and it will convert with an input voltage in the range of 0 to 5V in about 100 microseconds. It has control signals and a bus drive capability which makes it directly compatible with the 8035 microprocessor. The timing diagram of Fig. 19 shows how it is controlled. When addressed with \overline{CS} low, a \overline{WR} pulse starts the conversion and \overline{INTR} goes low when the

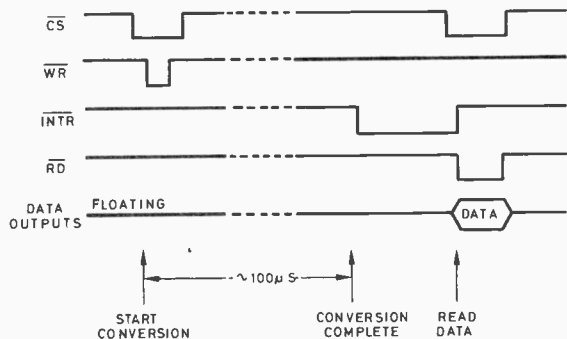


Fig. 19. A to D conversion timing

conversion is complete. This is tested by the micro and the data is read from the outputs by addressing with \overline{CS} and \overline{RD} low.


THE SOFTWARE


The flowchart of Fig. 20 shows diagrammatically all the functions which must be implemented in the software. When power is turned on, the initialisation routine is first executed, which ensures that data memory is cleared and that the display buffer contains the letters E, n, t, for the initial display. The internal flags are set and interrupts enabled. The processor then waits for the first interrupt by a sync pulse. When this interrupt occurs, the on-chip timer is loaded with a count value which will give a delay of 5 milliseconds in order to locate the peak of the sinusoidal mains voltage waveform and the counter is started. The next function is to change the data at output port 1 for the next digit in the display and then to shift the active bit of port 2 along one place to turn on this digit. The elapsed time is updated by one hundredth of a second.

Finally, before entering another loop to wait for the timer, the switches are scanned. If it is found that the switch conditions have changed, no immediate action is taken. Instead, the new switch condition is confirmed on the next mains cycle, 10ms later, to allow switch bounce to settle. The time to execute the above sequence is about 2ms so that there is a wait of 3ms for the timer to count out.

When the timer interrupt occurs, the ADC is started. The display is then updated as before and, as this is done every 5ms, it gives a flicker free multiplex frequency of 200Hz. The ADC is tested and when it is ready the digitised value of the current is read in via the bus. The sequence is completed by calculating the incremental charge for this half cycle and adding it to the running total for display. This calculation requires a four digit by four digit BCD multiplication and the time to execute this part of the program is about 3.5ms so there is a further wait of 1.5ms before the next sync pulse interrupt and the whole process is repeated.

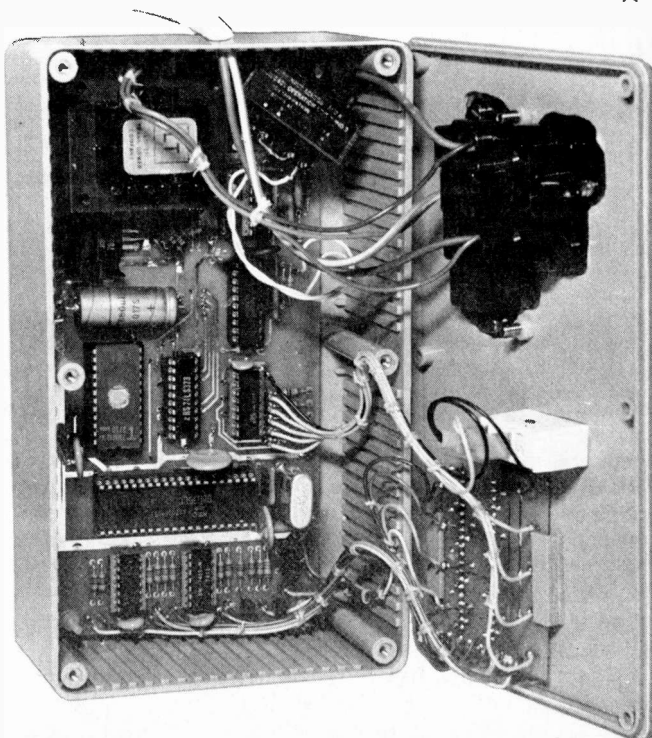Kits of parts and complete Teleetrics are available for purchase. See advert in this issue for details. Although construction is straight forward, a full service facility will be provided for anyone who has problems. ★



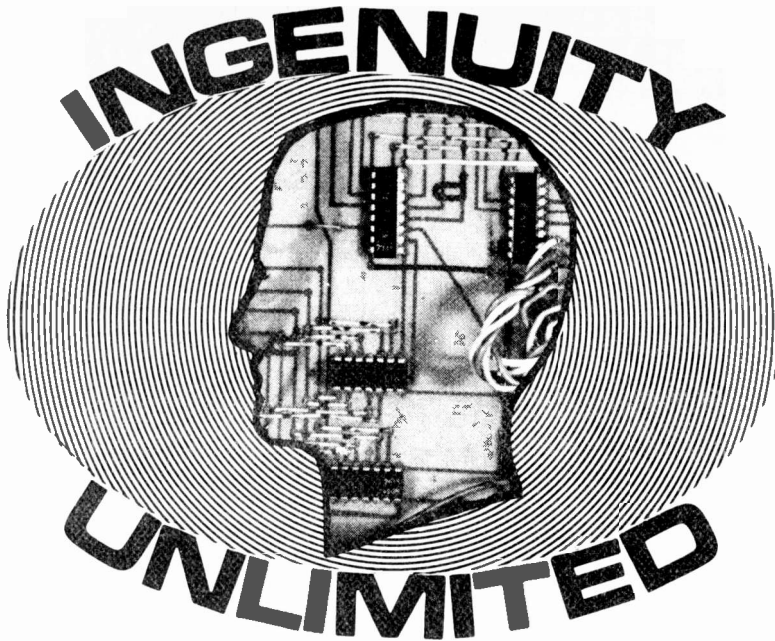


A selection of readers' original circuit ideas.

Why not submit *your* idea? Any idea published will be awarded payment according to its merits.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not inserted in the text.

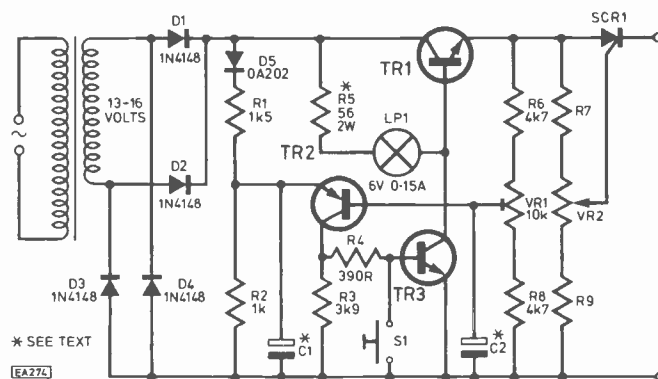OVERLOAD CUTOUT FOR THYRISTOR SPEED CONTROL



THIS circuit was designed to protect a thyristor-based model railway speed control. When the current drawn exceeds the value set by VR1, the supply is cut off completely, and remains off until reset by S1. The circuit is fast acting—it will close down for a short-circuit at very low speed settings—thus providing some protection against running an engine up to a set of 'closed' points.

TR1 is a conventional series regulator, but with deliberately poor regulation, so that the emitter voltage falls as the set maximum current is approached. TR2 compares the collector and emitter voltages of TR1. As the voltage on VR1

slider falls, TR2 switches on, switching on TR3, and shunting TR1 base current. The voltage on TR1 emitter falls further, and the process continues until TR1 is completely cut off.

C1 and C2 require some care in selection, since they provide partial smoothing of the voltages across TR2. C2 = 10 μ gives a rapid response; C1 should be selected from nominal 100 μ items to give minimal a.c. voltage across TR2 base-emitter at the chosen current limit.

Although VR1 gives a fair range of adjustment, the value of R5 may need to be altered for wide variations. The value shown provides a range of about 0.5 A to

2 A, at the expense of high power dissipation in TR1 near the current limit. For current limits above about 1 amp, the value of R5 should be decreased, in order to limit dissipation.

The transistors selected are as follows:


TR1—depends on current limit. A 6 W device will supply up to 1½ A; a 15 W type up to 2 A.

TR2—any of ACY 17 to 21 or BCY 30 to 34 will do.

TR3—any of BFY 50, S1 or S2.

W.S. Lymath
South Wirral
Cheshire.

BUTTON SELECTOR

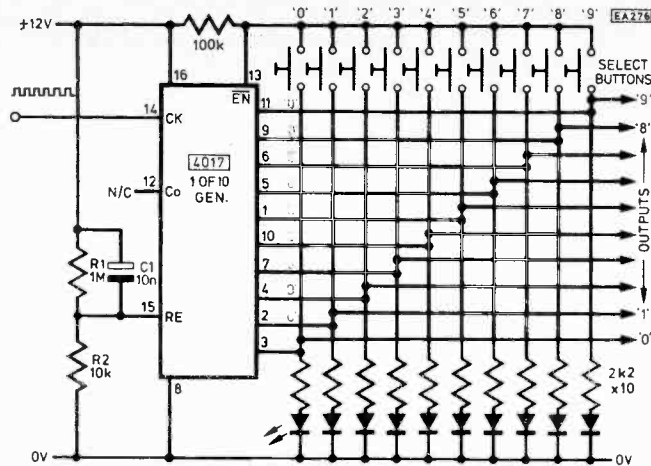

OFTEN it is desirable to replace the function of a rotary multi-position switch with the equivalent in push buttons. The advantages are evident in the push button car radio, where it's better to jab than to twiddle.

The circuit presented here performs the same 1 of n selecting function as the multi-position switch, whilst similarly cancelling previous selections.

The circuit uses the 4017, 1 of 10 selector, but one can easily make it into a 1 of less-than-ten, by just ignoring superfluous components.

Assume the last button to be pressed was the '0' button (or that the unit has been reset). A logic '1' will be standing on the No. 3 pin, the '0' l.e.d. will be alight, and all other outputs will be low.



If now the No. 4 button is pressed. Because the '10' pin and its associates are low, a low will be put on the otherwise high ENABLE-bar input. This will allow the unit to start clocking. When the logic '1' output steps up to the ten pin, it disenables the '13' pin, by placing a logic '1' on it. It remains so, whether or not the finger remains on the button.

Thus we have a 1 of n, self cancelling, remembering, data selector.

The unit has a self resetting function at switch-on, via the components R1, R2 and C1. By delivering a pulse to pin 15, it causes the stepper to stand with the '0' output line high, and all others low.

For eight or less outputs, the slightly cheaper 4022, 1 of 8 counter may be substituted.

Ron Mellor
Peakhurst,
New South Wales.

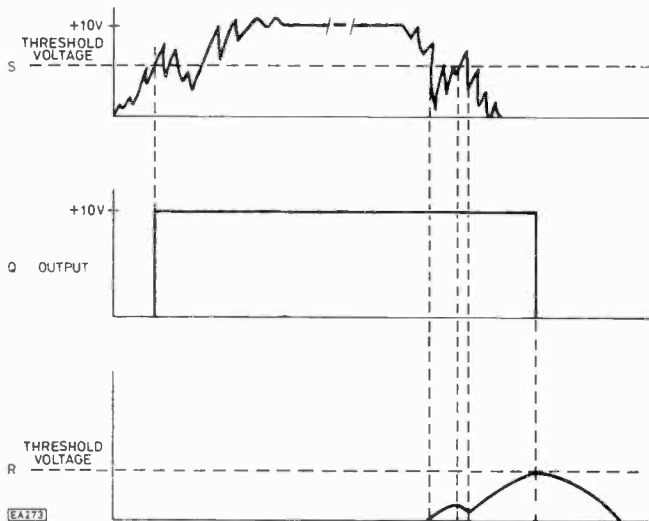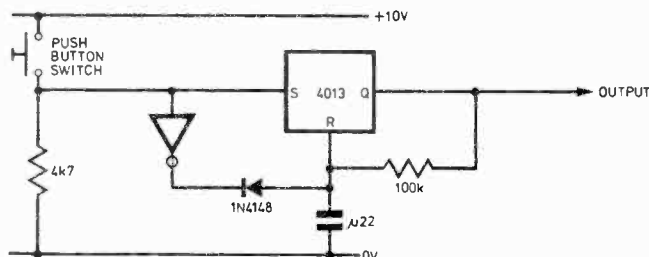

SWITCH DE-BOUNCE

DURING the design and construction of a TV pattern generator, I decided to use electronic switching of the video output patterns. The device used was a CMOS 4013 decade counter. The clock input is a simple push button switch. In anticipation of nasty switch bounce problems, I devised this circuit shown. The aim is to set a latch when the switch is closed and not permit it to reset until after the switch has been released.

When the switch is closed the Q output of the 4013 will become latched up. An inverter and diode will prevent the reset input from going high. When the switch is released, the set input will bounce back to a low state and the inverter output will go high, permitting the Q output to charge up the capacitor on the reset input through the 100k resistor. When this charge reaches the threshold level of the reset input, the Q output will be reset and the circuit will be ready to do some more de-bouncing. The graphs, show the input and output voltages. The choice of time constant $220n \times 100k$ is arbitrary and subject to variation, depending on how bad the switch is.

B.T. Black
Upper Stratton
Swindon

OCTAVE BANK FOR VCOs

THE use of multi-turn potentiometers for tuning the VCOs in synthesisers such as the Minisonic 2 is often not suitable for live performance situations. The octave bank described here gives quick, accurate and temperature stable octave switching.

The circuit consists of a Zener diode reference voltage, a resistor ladder and a buffer amplifier. The Zener value chosen is 5.6V since at this voltage the diode has an almost zero value of temperature coefficient, making the reference very stable. This voltage is then applied to the resistor divider which provides eight voltages at equal intervals from zero to -7V, the slider of VR1, the multi-turn cermet preset, being used as the -7V reference. The amplifier then provides buffered outputs at one volt intervals, which can be fed into the control nodes of the VCOs to be controlled.

The circuit is designed for use with synthesisers having a 1 volt/octave control law and thus for the Minisonic 2 the standard summing resistor of 47k should be


used for R_x . For synthesisers having a different control law relationship, R_x can be replaced by a preset of a suitable value, this can also be used to make the 'octave' span variable.

The circuit requires a stabilised supply of -9V and will draw just under 15mA from the rail.

All resistors should be 1% metal oxide or cermet film, if possible those in the ladder should be selected to be as close as possible. VR1 should be a cermet multi-turn preset potentiometer. The value of the summing resistor R_x is especially critical as this determines the actual span of the octaves provided by this circuit to the controlled VCOs. Trimming can be effected by replacing R_x with a cermet multi-turn preset potentiometer, in the case of the Minisonic 2 the value would be 100k.

In order to control more than one VCO, additional contacts should be added in parallel with S1, and a buffer amplifier/voltage follower as for IC1 added per extra oscillator.

Martin Russ,
Manchester.

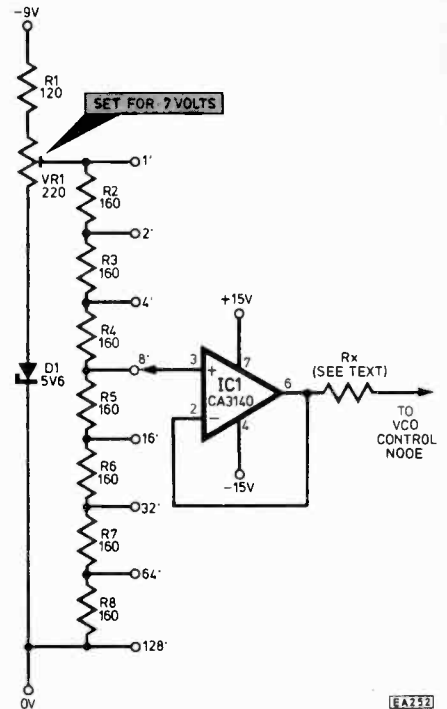

SOUND-TO-LIGHT CONVERTER


THIS circuit evolved from an idea in (PE) July 1976, for a simple sound to light converter in which the light was turned off in time to the music. This circuit is incorporated as one of the lamp drivers.

The potentiometer VR1 acts as a master level control for the unit which is connected directly to a loud-speaker. The transformer is used to protect the 'speaker' in the event of any short circuits. Transistors TR1 and TR2 form a buffer amplifier, the output of which is fed to VR2. This preset adjusts the balance between the two lamp drivers.

The bias on the driver transistors TR3 and TR4 is set by VR3 and VR4 respectively, and C3 ensures that the thyristor is normally turned on.

With the bias presets correctly set, careful adjustment of VR2 will yield a very pleasing light display when different coloured bulbs are used for each channel.

A. W. Cunningham,
Leven,
Fife

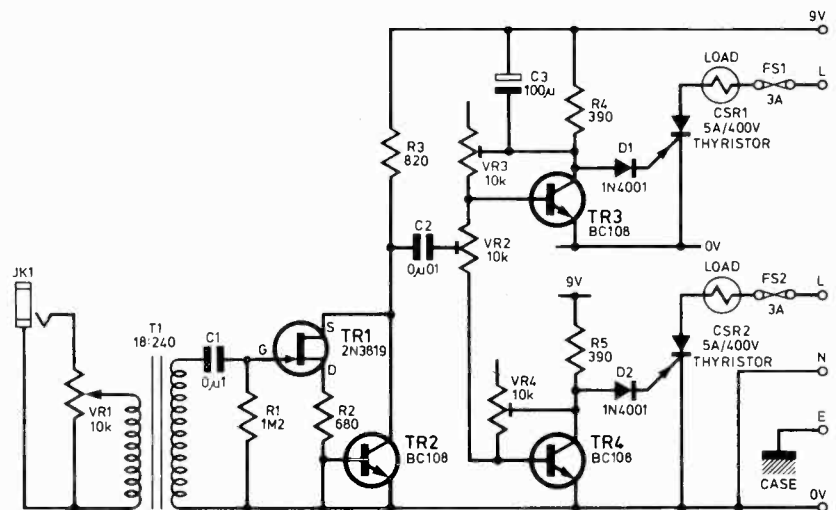


THIS amplifier has a frequency response of 20Hz to 25kHz, with a noise figure of -62db, making it suitable for high fidelity applications. As will be seen, the output impedance is low, by virtue of the emitter follower, and may be connected via a (screened) lead to other equipment. If required the input transformer may be omitted, and microphones of 47/50k used in an unbalanced input arrangement, connected directly to the point marked 'X' on the circuit diagram. Using high impedance microphones will mean that the input lead must not be much longer than about 1 metre, otherwise the high frequencies will tend to become attenuated, and the input will be more susceptible to hum problems. The amplifier should be powered from a well smoothed, low impedance supply.

The input transformer used in the prototype has a turns ratio of 6.45:1. This represents a bonus because it gives a voltage gain in the order of 16db, and since the transformer does not contribute noise the input to the amplifier is increased by 16db before the possibility of any noise arises. The first transistor base feed resistor R1, as will be seen, is 1M. In most cases this resistor on its own will be found to be too high a value, in order to obtain symmetrical clipping of the output. This should be experimentally paralleled with values of 2M2 or upwards. Using an oscilloscope, and before fitting the input transformer, check with a 1kHz tone fed into the point 'X' that a resistor is chosen that gives a symmetrically clipped output. Once this has been established, it may be permanently soldered in. If a tone generator and oscilloscope are not to hand the 1M resistor may be used alone; however, the overload point will be reached more quickly.

The a.c. part of the feedback loop has a

QUALITY MIC AMPLIFIER

EG 582

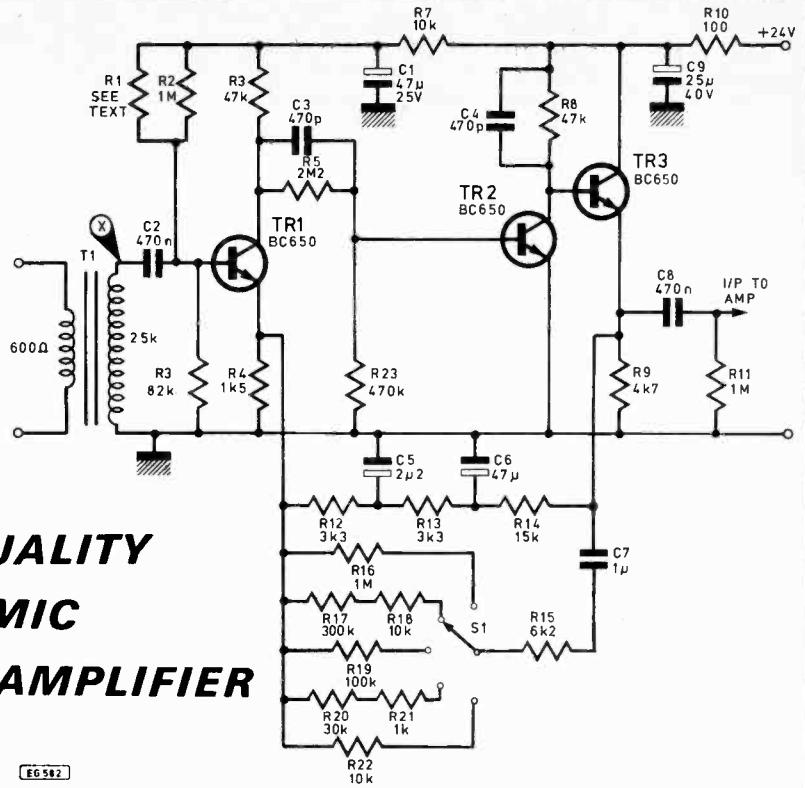


five way switch in series to select different series resistors. The overall gain is thus selectable from 20db to 60db in 10db steps. The resistors for the 30db and 50db positions will have to consist of two preferred values in series, as the actual values are unobtainable through normal retail outlets, and if more than one amplifier is to be built, it is suggested that they be 2% tolerance to match the gains. R.f.

interference is inhibited by means of the 470p in parallel with the collector load of the second transistor. The fairly high values of base and collector resistance around the first two stages help to keep the noise down by reducing the d.c. current flow. The 1M at the output ensures there is no d.c. voltage on the output of TR3.

Tony Sercombe,
Surbiton, Surrey.

9V POWER SUPPLY

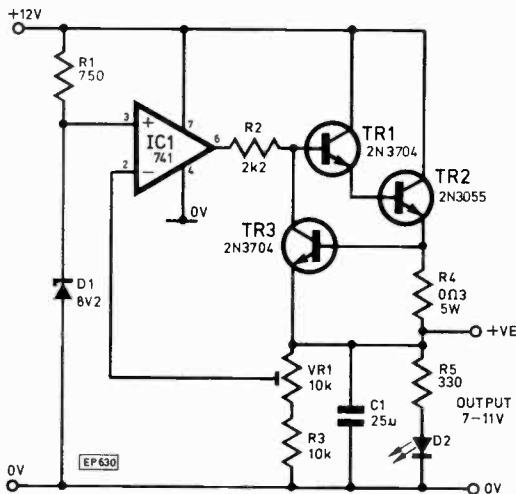

THIS unit was originally designed to run battery driven items requiring 9V or less from a 12V car supply. The voltage output is adjustable and stable over wide load fluctuations—up to the current limit of the 2N3055 provided the sinking on this is adequate.

The Zener provides a stable reference at pin 3 of IC1 and VR1 is adjusted to provide the output voltage.

Output from the i.c. is applied to TR1-TR2 turning on the latter sufficiently to maintain a constant voltage at the output irrespective of load. The output current flows through R4, which is made up of resistance wire. The design limit is fixed by the value of this resistor and when the load current reaches this the voltage developed switches on TR3 which in turn closes down TR1 and TR2.


S. A. R. Guest,
Grampound,
Truro.

CAMBRIDGE LEARNING

SELF-INSTRUCTION COURSES

A PRACTICAL DIGITAL ELECTRONIC KIT FOR

★ LESS THAN £20 ★

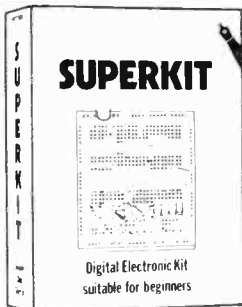

SUITABLE FOR BEGINNERS

Learn the wonders of digital electronics and see how quickly you are designing your own circuits. The kit contains:

seven LS TTL integrated circuits, breadboard, LEDs, and all the DIL switches, resistors, capacitors, and other components to build interesting digital circuits; plus a very clear and thoroughly tested instruction manual (also available separately). All this comes in a pocket size plastic wallet for only £19-90p inc VAT and p&p. This course is for true beginners:

- needs no soldering iron.
- asks plenty of questions, but never leaves you stuck and helpless.
- teaches you about fault-finding, improvisation, and subsystem checking.
- the only extra you need is a 4½V battery (Ever Ready 1289, or similar), or a stabilised 5V power supply.

Using the same breadboard you may construct literally millions of different circuits. This course teaches boolean logic, gating, R-S and J-K flipflops, shift registers, ripple counters, and half-adders. Look out for our supplementary kits which will demonstrate advanced arithmetic circuits, opto-electronics, 7-segment displays etc.

Other self-instruction courses from Cambridge Learning Ltd include:

COMPUTER PROGRAMMING IN BASIC	£10.50
DIGITAL COMPUTER LOGIC AND ELECTRONICS	£8.50
DESIGN OF DIGITAL SYSTEMS	£14.00

Please send for full details (see coupon below).

GUARANTEE No risk to you. If you are not completely satisfied, your money will be refunded upon return of the item in good condition within 28 days of receipt.

CAMBRIDGE LEARNING LIMITED, UNIT 24, RIVERMILL SITE, FREEPOST, ST IVES, CAMBS, PE17 4BR, ENGLAND. TELEPHONE: ST IVES (0480) 67446. VAT No. 313026022

All prices include worldwide postage (airmail is extra - please ask for prepayment invoice). Giro A/c No 2789159.

Please allow 28 days for delivery in UK

Please send me:
.....SUPERKIT(S) @ £19.90

.....Free details of your other self-instruction courses.

I enclose a *cheque/PO payable to Cambridge Learning Ltd for £..... (*delete where applicable)

Please charge my:

*Access / American Express / Barclaycard / Diners Club Eurocard / Visa / Mastercard / Trustcard

Expiry Date..... Credit Card No

Signature.....

Telephone orders from card holders accepted on 0480 67446 Overseas customers (including Eire) should send a bank draft in sterling drawn on a London bank, or quote credit card number.

Name.....

Address.....

Cambridge Learning Limited, UNIT 24, Rivermill Site, FREEPOST, St Ives, Huntingdon, Cambs, PE17 4BR, England. (Registered in England No. 1328762).

ILP TOROIDALS UNBEATABLE VALUE FOR MONEY!

New production capacity at Canterbury has increased our range, decreased our prices, improved our special customer design service. Choose from toroidal transformers in a range of 98 types.



Order using the FREEPOST coupon below

Trade enquiries are welcome.

Supplied with rigid mounting kit with centre bolt steel and neoprene washers GUARANTEED 5 YEARS

TYPE	SERIES No	SECONDARY VOLS	RMS CURRENT	PRICE inc. VAT	PRICE ex. VAT
30 VA 70 x 35mm 0.45 Kg Regulation 18%	1X010	6 + 6	1.50	£5.28	£4.48
	1X011	9 + 9	1.75	+ 0.87p	+ 0.87p
	1X012	12 + 12	1.75		
	1X013	15 + 15	1.00		
	1X014	18 + 18	0.81		
	1X015	22 + 22	1.68		
	1X016	25 + 25	0.60		
50 VA 80 x 35mm 0.9 Kg Regulation 13%	2X010	6 + 6	4.16	£5.83	£4.93
	2X011	9 + 9	2.77	+ £1.10	+ £1.10
	2X012	12 + 12	1.68		
	2X013	15 + 15	1.68		
	2X014	18 + 18	1.38		
	2X015	22 + 22	1.13		
	2X016	25 + 25	1.00		
80 VA 90 x 30mm 1 Kg Regulation 7%	3X010	6 + 6	6.64	£6.51	£5.47
	3X011	9 + 9	4.44	+ £1.43	+ £1.43
	3X012	12 + 12	3.33		
	3X013	15 + 15	2.66		
	3X014	18 + 18	2.22		
	3X015	22 + 22	1.81		
	3X016	25 + 25	1.60		
120 VA 90 x 30mm 2 Kg Regulation 11%	4X010	6 + 6	10.00	£7.55	£6.38
	4X011	9 + 9	6.66	+ £1.43	+ £1.43
	4X012	12 + 12	5.00		
	4X013	15 + 15	4.00		
	4X014	18 + 18	3.33		
	4X015	22 + 22	2.72		
	4X016	25 + 25	2.40		
160 VA 110 x 40mm 1.8 Kg Regulation 8%	5X010	9 + 9	8.89	£9.92	£8.44
	5X012	12 + 12	6.66	+ £1.43	+ £1.43
	5X013	15 + 15	5.33		
	5X014	18 + 18	4.44		
	5X015	22 + 22	3.63		
	5X016	25 + 25	3.20		
	5X017	30 + 30	2.66		
225 VA 110 x 40mm 7 Kg Regulation 5%	6X010	15 + 15	10.00	£13.67	£11.66
	6X011	18 + 18	8.33	+ £1.73	+ £1.73
	6X012	22 + 22	6.82		
	6X013	25 + 25	6.00		
	6X014	30 + 30	5.00		
	6X015	35 + 35	4.28		
	6X016	40 + 40	3.75		
300 VA 140 x 60mm 7 Kg Regulation 4%	7X010	25 + 25	10.00	£18.17	£15.53
	7X011	30 + 30	8.33	+ £2.05	+ £2.05
	7X012	35 + 35	7.14		
	7X013	40 + 40	6.25		
	7X014	45 + 45	5.56		
	7X015	50 + 50	5.00		
	7X016	55 + 55	4.54		
675 VA 140 x 75mm 5 Kg Regulation 4%	8X010	30 + 30	10.41	£25.10	£21.54
	8X011	35 + 35	8.92	+ £2.70	+ £2.70
	8X012	40 + 40	7.81		
	8X013	45 + 45	6.94		
	8X014	50 + 50	6.25		
	8X015	55 + 55	5.68		
	8X016	60 + 60	5.13		

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain full load voltage.

The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows:

For 110V primary insert "0" in place of "X" in type number

For 220V primary (Europe) insert "1" in place of "X" in type number

For 240V primary (UK) insert "2" in place of "X" in type number

How to order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent within 7 days of receipt of order for single and small quantity orders

Also available at Electrovalve, Maplin Marshalls, Technomatic and Watford Electronics
ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules PE 1/4

Total purchase price

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access / Barclaycard No

Name

Address

Signature

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780



STAY AHEAD. STAY WITH US



MOBILE SERVICE IN SPACE

From time to time mention has been made in *SPACEWATCH* of the plan to service satellites in orbit or retrieve them from their orbits and carry out service on board a space station or even aboard the Shuttle as well as return them to Earth. This is now a well advanced pilot programme. A vehicle module has already been operated in simulated conditions for this work at heights of 300m.

The task is directed in the first instance to the servicing of the Solar Maximum Mission spacecraft which is already degraded. It is expected that the space shuttle astronauts will be the first to use the system. The date set is 1983. As with much of the space programme the whole scheme is dependent on the funding available.

The procedure adopted for the servicing activity will be as follows. The Shuttle will approach the spacecraft to be serviced and stand off at a distance of about 300 feet. The astronaut will be deployed from the orbiter and dock with the satellite. Manoeuvring jets will be used to stabilise the satellite and the astronaut will attach him/herself to the satellite, then call for the orbiter manipulator arm to dock with the special attachment placed by the astronaut. When the orbiter takes over, the astronaut will detach and fly by the side of the satellite to photograph the operation. When the satellite is safely secured to the support cradle on board the orbiter the astronaut, still in the manoeuvring unit, will carry out the necessary repairs. Having done this he will fly back into the payload bay and be released from the manoeuvring unit. The replacement of the various fuses, which caused the degradation of performance, will then be carried out and the necessary checks with ground station completed, after which the satellite will be replaced in its correct orbital configuration and the observatory in full operation.

The manoeuvring unit itself is rather like a special chair. The control and life support systems are carried in the cradle unit with the

astronaut in a suit designed for extra-vehicular activities. In the case of the Solar Maximum Satellite the docking mechanism is carried in front of the astronaut and attached to the chest. The necessary controls are all within suitable controlling distance.

The docking and stabilising of a spacecraft for repair involves a number of special actions. For example in the case of the Solar Maximum Satellite which has a controlled rotation speed of the order of 0.8 to 0.9 deg/sec. it would not present a great problem. Attachment by the astronaut of special clamps to the outer edge of one of the solar panels would be sufficient and up to much higher rates of rotation also. Having nulled the rotation the astronaut is then able to reset his position and attach the grapple unit to the spacecraft. A number of alternative techniques are being developed because it is possible that conditions will change for individual spacecraft. Also there is the condition prevailing for the Solar Maximum Satellite for there is no special provision for dealing with the screws holding the units in place. In zero gravity with a moving vehicle a special technique will be required.

There is some speculation too about the difference in dealing with a spacecraft retrieved for return to earth and one to be returned to the Shuttle for repair. The clearance for example in the case of the Solar Maximum vehicle can be as little as 5 inches for the solar panels so that great care will be needed to avoid damage. It is being considered now whether it would be more prudent to bring the spacecraft back to earth in any case. This would call for a greater load facility of some 4,000lb. It is clear that a number of options are available and it is necessary to be able to fly alongside and move round an orbiting vehicle without disturbing its flight parameters. There are hazards such as the orbiter's exhaust which could be heating up the vehicle and disturb control. So far many aspects have been studied and these will be dealt with in order of priority against time and financial options. What is important is that the thinking from the early days and dreams of fully manned units operating in space for maintenance is now in sight. This alone is a great fiscal advantage.

FRANCE AND SPACE

France is developing her Spot satellite system. It is an Earth observation programme and will be operated by SPOT IMAGE, a commercial marketing group privately financed. The technical details will remain with the French Government. They will retain, under the CNES (Centre Nationale d'Etudes Spaciales), 34% of the shareholding. CNES will be responsible for the areas of manufacture and development. A United States subsidiary will be established for the benefit of users in America. It is stated that this is not a move to compete with the United States Land-Sat system. The data available from Spot-Sat will be compatible with Land-Sat.

France has said that they have found a market for Spot-Sat data among users looking for a truly commercialised system which does not function with or is not associated with, government bureaux control. There have been approaches by some who are now in the Land-Sat market who are not happy with the possible influence that American Government

policies might have on existing contracts particularly with regard to delays under the present administration.

The first of the operational satellites will be in 1984 launched by an Ariane-2 launcher. A second Spot vehicle has been approved by the French government to guarantee services throughout the 1980's. The design of the Spot vehicle will be a multitemission platform. It will be fitted with two HRV (High Resolution Visible) range instruments. The optical instruments consist of a 20 metre resolution instrument in a multispectral mode and a 10m. mode resolution instrument in black and white. The multispectral mode covers green, red and near infra-red bands. These have been selected to satisfy several mission objectives.

—Consistent relationship between spectral reflectance and vegetational properties.

—Compatible interpretation of the spectral signatures obtained by the Spot satellite and the Land-Sat D8 mapper.

—Improved radiometric sensitivity and resolution for surface-water work.

—Good discrimination within areas of vegetation of different types.

—At least one band to enable deep water penetration.

The markets expected to want these services are those of oil and mining exploration, topographic and land use, coastal studies and not least those who need crop and environment monitoring.

It is possible to provide stereoscopic images by processing two different orbital passes. Using the two resolutions, multispectral images can produce the appearance of enhancement better than the multispectral image.

CONTROL STATIONS

The central control will be at the CNES space centre at Toulouse. This will receive the direct transmissions from the spacecraft's earth coverage when in sight of the station. Images recorded earlier on tape recorders will also be collected during other passes. A second ground station will be at Kiruna, Sweden, with identical facilities. Other ground stations operated by countries with their own stations will be able to receive data when the spacecraft is within the beam of their aerials.

A MEETING OF THE AMERICAN AERONAUTICAL SOCIETY

Speaking at a meeting Robert S. Cooper, director of Defence Advanced Research Projects Agency, said:

'We have built a fatal flaw into our satellite systems and it is time we recognised this fact!' He was emphasising his contention that not enough attention was being given to the development of robotics. He claimed that it was necessary now to set up programmes to ensure that spacecraft could operate entirely independent of human ground control. He characterised current spacecraft operation as retarded technology. It was necessary to have surviveable space systems. He claimed also that it was a tragedy that with all the current facilities available for launching in America, countries were turning to other centres for launching facilities. He cited a recent Presidential directive in support of the Space Shuttle and space transport system.

MUSIC KITS

ALL WITH PRINTED CIRCUIT BOARDS!

128-NOTE SEQUENCER
A digital, Kbd controlled unit for most synths.
Kit incl Kbd = SET-76 **£120.45**

16-NOTE SEQUENCER
Analogue, panel controlled unit for most synthesisers = SET-86 **£64.63**

3-CHANNEL STEREO MIXER
With left, right & master level controls & headphone monitor = SET-107 **£21.50**

3-MICROPHONE STEREO MIXER
Improves stereo reality = SET-108 **£12.99**

6-CHANNEL MIXER
High spec mixer with variable impedances = SET-90 From **£96.67**

AUDIO EFFECTS UNIT
Variable siren gen = SET-105 **£16.12**

AUTOWAH UNIT
Automatic Wah & Swell sounds from each guitar note played = SET-58 **£14.01**

CHOROSYNTH
30-Note chorus synth with wide variety of voices. Kit incl Kbd = SET-100 **£126.04**

COMPRESSOR
With level & decay-rate controls, line & mic inputs with mixer = SET-120 **£25.05**

DISCOSTROBE
4-Chan 200W unit for sequential, random or full strobe use = SET-57 **£39.78**

DRUM SYNTHESIZER
Extremely versatile synthesiser for conventional & extraordinary drum sounds = SET-119 From **£50.11**

DYNAMIC NOISE LIMITER
Helps clean up noisy recordings. = SET-97 **£15.96**

ENVELOPE SHAPER
ADSR unit with own VCA = SET-50 **£14.96**

KIMBER-ALLEN KEYBOARDS
Details in lists = From **£32.43**

P. E. MINISONIC SYNTH*
Excellent 3-Oct multi-module portable synth. Kit incl Kbd = SET From **£181.56**

PHASER
6-Stage automatic unit with variable control = SET-88 **£21.08**

PHASING & VIBRATO
Manual & auto control producing superb full sounds = SET-70 **£36.25**

PULSE GENERATOR
Pulse width 100NS-2secs, freq 0.1 HZ-100KHZ = SET-115 **£24.84**

RHYTHM GENERATORS
Several in list = From **£81.71**

RING MODULATOR
Usable with most synths = SET-87 **£13.82**

SIGNAL TRACER & GENERATOR
Aids circuit testing. With frequency & level controls = SET-109 **£17.50**

SMOOTH FUZZ
As the name implies! = SET-91 **£11.68**

SPEECH PROCESSOR
Improves intelligibility of C.B. or P.A. speech signals = SET-110 **£12.18**

SPLIT-PHASE TREMOLO
Modulation, depth, rate & level under full control = SET-102 **£29.98**

SWITCHED TREBLE BOOSTER
4 Sectable preset tone changes = SET-89 **£12.51**

SYNTHESIZER INTERFACE
Enables guitars, mics etc to be synthesiser processed = SET-81 **£9.49**

10% OFF 10% OFF U.K. C.W.O. ORDERS OVER £20 FROM THIS AD UNTIL END OF MONTH ON COVER. (5% OFF FOR CREDIT CARDS). THIS COUPON MUST ACCOMPANY ORDER. CODE PE23.

EXPOSURE TIMER
Range up to 10 mins in 0.5sec steps, with audio alarm = SET-93 **£39.22**

FORMAT SYNTHESIZER*
Advanced 3-oct synth with multiple modules. Kit incl Kbd = SET-66 From **£342.71**

FUNNY TALKER
Fascinating sounds when used with speech & music = SET-99 **£16.55**

GUITAR EFFECTS
8-mode filter & envelope shaper for most instruments = SET-42 **£15.92**

GUITAR FREQUENCY DOUBLER
Orig & doubled signals can be mixed for greater depth = SET-98 **£11.75**

GUITAR MULTIPROCESSOR
Extremely versatile sound processor. Details in list.

GUITAR OVERDRIVE
Sophisticated fuzz with filter & shape controls = SET-56 **£21.17**

GUITAR PRACTISE AMPLIFIER
3-Watt practise or test-monitor amp. = SET-106 **£22.15**

GUITAR SUSTAIN
Retains natural attack whilst extending note duration = SET-75 **£11.77**

HEADPHONE AMPLIFIER
For most pick-ups, decks, tuners & headphones. RIAA specs = SET-104 **£21.15**

METRONOME
Variable for 40-240 beats per minute = SET-118 **£10.58**

EXPORTS WELCOME!
Sterling payment with order please. Postage rates in our lists. Europe send 50p for lists, other countries send £1.

TRANSIENT GENERATOR
Facilitates mandolin, banjo sounds etc. From a synthesiser = SET-63 **£16.86**

TREMOLO UNIT
For most instruments. Incl speed, depth & by-pass controls = SET-116 **£13.47**

TUNING FORK
Eases tuning of acoustic & electronic instruments = SET-46 **£13.04**

VOICE OPERATED FADER
Automatically reduces music volume during disco talk-over = SET-30 **£9.85**

VOICE SCRAMBLER
For coding or decoding speech signals for greater security. See list for details = SET-117 **£21.81**

WAVEFORM CONVERTER
Allows 5 different waveforms from synthesiser VCO = SET-67 **£21.98**

WAVEFORM GENERATOR
3 Waveforms, range 1HZ to 100KHZ, up to 10V P-P = SET-112 **£23.13**

WIND & RAIN EFFECTS
As the name says! = SET-28 **£11.39**

KIT CONTENTS
Sets include PCBs, U.K. P&P, 15% VAT, Res, Caps, S.c.s, Pts, Knobs, SW's, Skts, Wire, Solder, Photocopy of orig text, & a case unless marked *. Most are battery operated, but PSU units are also available. Most parts can be bought separately. Fuller details & more great kits in our catalogue. Send S.A.E. for free copy. Prices correct at press, E. & O.E., subject to stock. Despatch usually 24hrs on all ex-stock items.
Access, Barclay & Am-Express Credits Welcome.

PHONOSONICS
Dept. PE24, 22 High Street, Sidcup, Kent, DA14 6EH.
Telephone: 01-302 6184.

YOU CAN'T BEAT ILP BIPOLAR POWER AMPS FOR POWER AND PRICE

Get maximum power at minimum price, yet still with hi-fi specifications and a wide choice of outputs. ILP Bipolar power amps, now with or without heatsinks are unbeatable value for domestic hi-fi — but for disco, guitar amplifiers and PA choose the new range of heavy duty power amps, again with or without heatsinks, with protection against permanent short circuit, added safety for the disco or group user. Connection in all cases is simple — via 5 pins.



Every item has a 5 year no quibble guarantee and includes full connection data. So send your order FREEPOST today!
Load impedance, all models 4 ohm — infinity. Input impedance, all models 100K ohm. Input sensitivity, all models 500 mV. Frequency response, all models 15Hz-50kHz-3db.

BIPOLAR Standard, with heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		I.M.D 50Hz/7kHz 4 1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
HY 30	15w/4-8Ω	0.015%	< 0.006%		+18±20	76×68×40	240	£8.28	£7.29
HY 60	30w/4-8Ω	0.015%	< 0.006%		+25±30	76×68×40	240	£9.58	£8.33
HY 120	50w/4-8Ω	0.01%	< 0.006%		+35±40	120×78×40	410	£20.10	£17.48
HY 200	120w/4-8Ω	0.01%	< 0.006%		+45±50	120×78×50	515	£24.39	£21.21
HY 400	240w/4Ω	0.01%	< 0.006%		+45±50	120×78×100	1025	£36.60	£31.83

BIPOLAR Standard, without heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		I.M.D 50Hz/7kHz 4 1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
HY 120P	60w/4-8Ω	0.01%	< 0.006%		+35±40	120×26×40	215	£17.83	£15.50
HY 200P	120w/4-8Ω	0.01%	< 0.006%		+45±50	120×26×40	215	£21.23	£18.46
HY 400P	240w/4Ω	0.01%	< 0.006%		+45±50	120×26×70	375	£32.58	£28.33

Protection: Load line, momentary short circuit (typically 10 sec). Slew rate 15V/μs. Rise time 5μs. S/N ratio 100db. Frequency response (+3db) 15Hz-50kHz. Input sensitivity 500mV rms. Input impedance 100kΩ. Damping factor (8Ω/100Hz) > 400.
ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.
HEAVY DUTY with heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		I.M.D 50Hz/7kHz 4 1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
HD 120	60w/4-8Ω	0.01%	< 0.006%		+35±40	120×78×50	515	£25.85	£22.48
HD 200	120w/4-8Ω	0.01%	< 0.006%		+45±50	120×78×60	620	£31.49	£27.38
HD 400	240w/4Ω	0.01%	< 0.006%		+45±50	120×78×100	1025	£44.42	£38.63

HEAVY DUTY without heatsinks

Model No	Output power Watts rms	DISTORTION T.H.D. Typ		I.M.D 50Hz/7kHz 4 1	Supply voltage Typ/Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
HD 120P	60w/4-8Ω	0.01%	< 0.006%		+35±40	120×26×50	265	£22.82	£19.84
HD 200P	120w/4-8Ω	0.01%	< 0.006%		+45±50	120×26×50	265	£27.17	£23.63
HD 400P	240w/4Ω	0.01%	< 0.006%		+45±50	120×26×70	375	£39.42	£34.28

Protection: Load line, PERMANENT SHORT CIRCUIT (ideal for disco/group use should evidence of short circuit not be immediately apparent). The Heavy Duty range can claim additional output power devices and complementary protection circuitry with performance specs as for standard types.

How to order Freepost: Use this coupon, or a separate sheet of paper, to order these products or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

PE 2/4

Please send me the following
ILP modules _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access/Barclaycard No. _____

Name _____

Address _____

Signature _____

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780

ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US

PATENTS REVIEW

Copies of Patents can be obtained from:
the Patent Office Sales, St. Mary Cray, Orpington, Kent. Price £1.60 each.

PUSS-PROOF ALARM

British patent application 2 074 314, from American District Telegraph Company of New York, offers some interesting information on burglar alarms. The patent is aimed at improving passive infra-red detection systems, and lists a string of US patents on known systems of this type. Essentially an infra-red sensor trips an alarm if the infra-red reflection pattern in a room is disturbed by an intruder. But it has proved difficult to make the alarm sufficiently sensitive to detect an intruder on the other side of the room from the detector, but not so sensitive

that it goes off accidentally, for instance if the office cat prowls past.

The patented solution (Fig. 1) is a complex arrangement of spherical mirror segments. A large segment 12, a smaller segment 14 and two still smaller segments 16 are all mounted round a common optical axis 18. The mirrors all focus on an infra-red detector 20 which is supported on a U-shaped arm 44 (Fig. 2) mounted on tabs 46. The mirror segments are made of acrylic, with a coating of aluminium.

Fig. 3 explains the basic circuit. Detector 20 is a dual thermopile with its two elements connected in phase opposition. The detector output is amplified at 120, fed to threshold circuit 122, integrated at 126 and fed to second threshold 128. Logic 130 trips alarm 132 when the thresholds are exceeded. Background disturbance indicator 124 senses slow variations in radiation and

lights i.e.d. 134 if it exceeds a threshold level. Variations of sensitivity due to ambient temperature changes are compensated by the circuit of Fig. 4.

The mirror complex produces a sensitivity field pattern in azimuth shown in Fig. 5. Long central pattern 100 is created by large mirror 12 and has a range of 150ft. and beam width of 2.5°. Intermediate pattern 102 is provided by medium-sized mirror 14 and has a range of 80ft. and beam width of 5°.

The two short patterns 104 are provided by small mirrors 16 and have a range of 20ft. and 9° beam width.

The inventors claim that this arrangement provides the same sensitivity to an intruder at 100ft. range as to an intruder at 25ft. range, with the shorter, more divergent beams insensitive to small movements, for instance by animals.

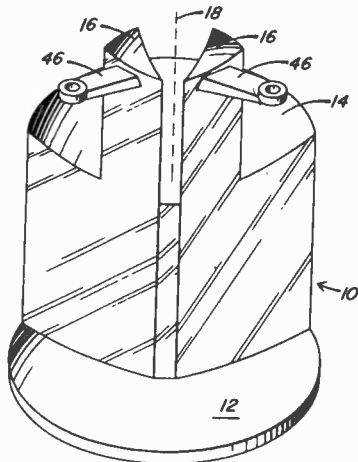


Fig. 1

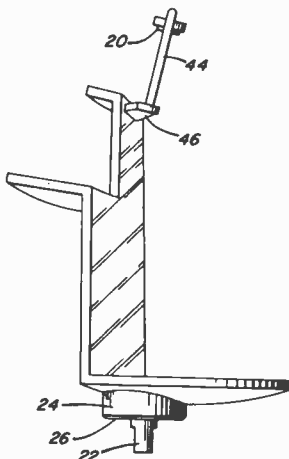


Fig. 2

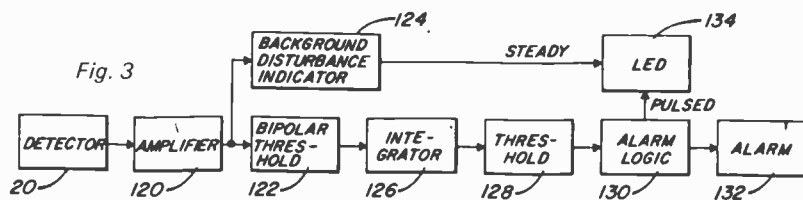


Fig. 3

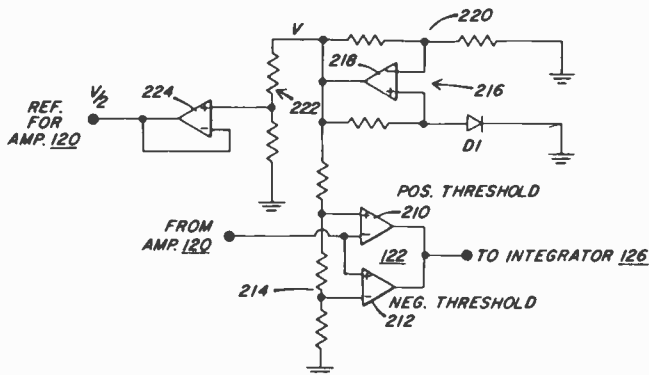


Fig. 4


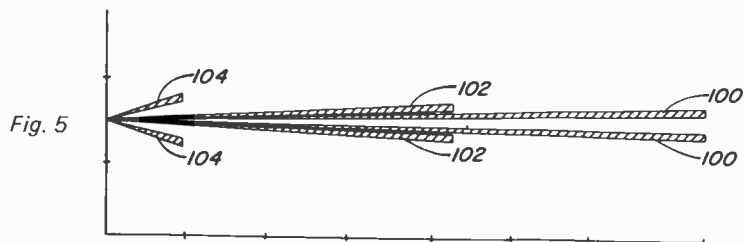


Fig. 5


From HAMEG...

HM307

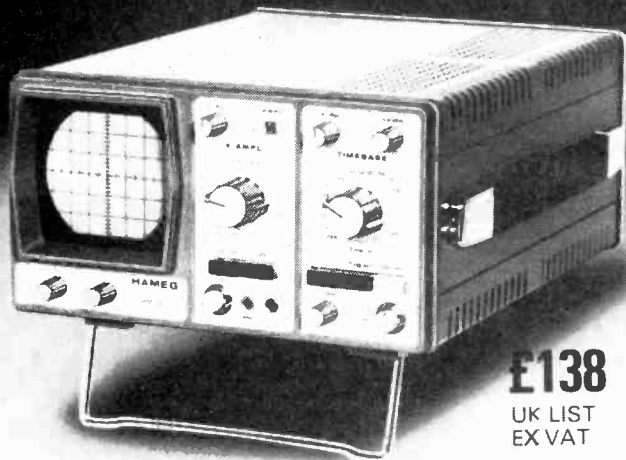

£138
UK LIST
EX VAT

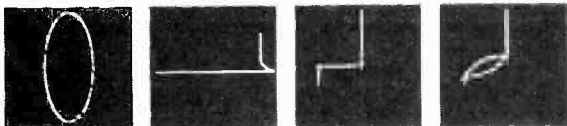The first portable scope with a component tester.



Capacitor 33uF Transistor E-C Transistor B-E B-E 1uF + 58 ohms

Oscilloscope Specifications:

Y Deflection

Bandwidth: DC - 10 MHz (-3dB)
Overshoot: Less than 1%
Sensitivity: 5 mV - 20 V/cm
Input Imp: 1 M ohm // 25pF

X Deflection

Timebase: 0.2s - 0.2 μs/cm
Triggering: 2 Hz - 30 MHz (3mm)
Auto + level control
Bandwidth: 2Hz - 1 MHz

General Information

Component Tester: For single components and **in circuit**
Calibrator: 0.2V ± 1% for probe alignment
Power Supplies: Regulated including high voltage
A.C. Input: 110, 127, 220, 237, V.A.C., 50 - 60 Hz
Weight: 8-1/4 Lbs.
Size: 4-1/2"H x 8-3/8"W x 10-7/16"D

For further information on HAMEG's full range of top performance oscilloscopes, contact:

HAMEG LTD.
74-78 Collingdon Street, Luton, Beds. LU1 1RX
Tel: (0582) 413174



WHY AN ILP MOSFET POWER AMP?

Because ILP MOSFET power amps give you ultra-fi performance without costing big money. Performance you thought you couldn't afford at a price you know you can.

All ILP modules are compatible with each other — you'll find many more in other ILP ads in this magazine. Choose ILP MOSFET power amps when you need the fastest possible slew rate, low distortion at high frequencies, better thermal stability. MOSFET power amps work with complex loads without difficulty and without crossover distortion. Connection is simple — via 5 pins. With other ILP modules you can create almost any audio system, whatever your age or experience.

ILP MOSFET power amps are now available with integral heatsink (no extra heatsink required) or ready for mounting on to your own heatsink or chassis. Full dissipation detail on data sheet, available on request. Each carries a 5 year no quibble guarantee and comes with full connection data.

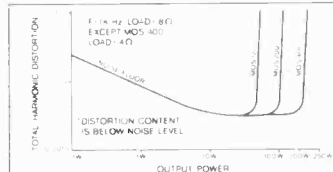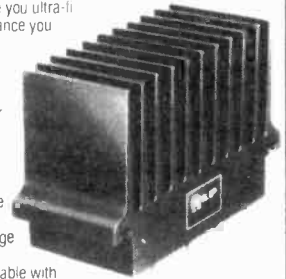Send your order FREEPOST today on the coupon at the foot of this ad.



Load impedance, all models 4 ohm — infinity
Input impedance, all models 100K ohm
Input sensitivity, all models 500 mV
Frequency response, all models 15Hz - 50KHz - 3db

MOSFET Ultra-Fi, with heatsinks

Model No	Output power Watts rms	DISTORTION THD typ at 1kHz	IM D 50Hz / 7kHz 4:1	Supply voltage typ / Max	Size mm	Wt gms	Price inc VAT	Price ex VAT
MOS 120	60w / 4.8Ω	< 0.005%	< 0.006%	+45 - 50	120 x 78 x 40	420	£24.76	£25.88
MOS 200	120w / 4.8Ω	< 0.005%	< 0.006%	+55 - 60	120 x 78 x 80	840	£38.48	£33.46
MOS 400	240w / 4Ω	< 0.005%	< 0.006%	+55 - 60	120 x 78 x 100	1070	£52.20	£45.39

MOSFET Ultra-Fi without heatsinks

MOS 120P	60w / 4.8Ω	< 0.005%	< 0.006%	+45 - 50	120 x 26 x 40	215	£26.82	£23.32
MOS 200P	120w / 4.8Ω	< 0.005%	< 0.006%	+55 - 60	120 x 26 x 80	420	£32.81	£28.53
MOS 400P	240w / 4Ω	< 0.005%	< 0.006%	+55 - 60	120 x 26 x 100	525	£44.75	£38.91

Protection

Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice).

Ultra-fi specifications:

Slew rate 20V/μs Rise time 3μs S/N ratio 100db Frequency response (-3db) 15Hz - 100kHz Input sensitivity 500mVrms Input impedance 100k Damping factor (8Ω/100Hz) > 400

How to order Freepost:

Use this coupon or a separate sheet of paper to order these products or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules PE 3/4

Total purchase price

I enclose Cheque

Postal Orders

Int. Money Order

Please debit my Access / Barclaycard No

Name

Address

Signature

Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone: (0227) 54778 Technical: (0227) 64723 Telex: 965780

ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US



**CELEBRATE
35 YEARS OF
CITIZENS'
BAND RADIO**
at
CB RADIO
MAGAZINE'S
NATIONAL
10-4 DAY

THE 1982 CB SHOW

See & Buy the very latest in

- RIGS ● ANTENNAS ●
- SWR METERS ●
- MICROPHONES ●

and a whole lot more
Plus

Amateur Radio Equipment
In-Car Entertainment
& Communications

ENJOY COMPETITIONS, FOOD,
BARS, ELECTRONIC GAMES
& MORE


"A DAY OUT FOR ALL THE FAMILY"
AT
WEMBLEY CONFERENCE CENTRE
APRIL 9th, 10th, 11th, 12th

Open from 10.00am every day

SEE CB RADIO MAGAZINE
FOR FURTHER DETAILS

ACORN ATOM
8K ram + 2K ram kit £120, built £150. 12K
ram + 12K ram kit £168, built £198. 4K ex-
pansion rom £25. Power supply £10.20.
UK101 AND SUPERBOARD
UK101 with 1K and free power supply and
modulator kit £120, built £149. The below
accessories suit both the UK101 and
superboard: Extra ram £2.70 per K. 16K
memory expansion complete kit £50, built
£58. 32K memory expansion kit £74, built
£82. Case £27. Cassette recorder £19.
Cesmon £22.50. Wemon £19.95. Word
processor program £10. Centronics interface
kit £10. 610 expansion board £179. New
stand-alone floppy disc controller board £75.
Cased minifloppy disc drive with DOS £275.
The below suit only superboard: Colour
adaptor board built £45. Assembler/Editor
tape £25. Guard band kit £10. Series 1 only
30 lines x 50 characters display expansion
kit £14. UK101 display expansion kit £14.
NEW GENIE 1 £299
EG3014 Expansion box with 16K/32K ram
£199/£213. Disk drive £220. Colourboard
£36. Parallel printer interface £36.
Monitors:- EG100 white £69. OVM9PGR
green £99. Colour Genie poa. Genie 3 poa.

SINCLAIR PRODUCTS*
ZX81 built + mains adaptor £69.95 (post
£2.95 extra). SC110 Oscilloscope £139.
PFM200 £49. PDM35 £32.95. DM450
£118. Microvision TV £69.
BATTERY ELIMINATORS*
3-way type 6/7.5/8V 300ma £3.50. 100ma
radio types with press studs 9V £4.95. 9+9V
£6.25. Car converter 12V input, output
3/4.5/6/7.5/9V 800ma £3.04.
BATTERY ELIMINATOR KITS*
100ma radio types with press-studs 9V
£179. 9+9V £2.50. Stabilized 8-way types
3/4.5/6/7.5/9/12/15/18V 100ma £3.12. 1
Amp £8.50. Stabilized power kits 2-18V
100ma £3.12. 1.30V 1A £8.50. 1-30V 2A
£15.30. TTL and computer supplies 5V
stabilized 1.5A £9. 3A £14. 6A £23. 12V
car converters 6/7.5/9V 1A £1.62.
TV GAMES*
AY-3-8600 kit £12.98. AY-3-8550+kit
£9.26.
81-PAK AUDIO MODULES*
AL30A £4.35. PA12 £9.31. PS12 £1.75.
T538 £2.90. S450 £27.90. AL60 £5.62.
PA100 £19.24. SPM80 £5.26. BMT80
£6.36. Stereo 30 £21.00. AL80 £8.56.
VIC 20 COMPUTER
VIC 20 £165. Cassette recorder £39.09. Kit
to allow the use of a normal cassette
recorder £6. 3K ram £26.04. 8K ram
£39.09. 16K ram £65.17. Vic printer £199.

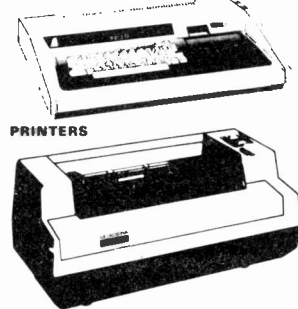

PRINTERS
Buy any of the below and get a free interface
kit and word processor program for UK101
or Superboard:- Epson MX70 £259. Epson
MX80T £359. Epson MX80F/T1 £359.
Epson MX80F/T2 £449. OKI Microline 90
£295. OKI Microline B2A £399. Centronics
737 £355. Seikosha GP80A £199.

COMPONENTS*
1N4148 1.5p. 1N4002 3.7p. NE555 8 dil
22p. 741 8 dil 16p. 2114 low current
300ns £1.35. BC182, BC184, BC212,
BC214, BC547, BC549 6p. Resistors 5%
1/4 watt £12 10R to 10M 1p, 0.8p for 50+
of one value. Polystyrene capacitors E12
63V 10 to 100pF 4p; 1n2 to 10n 5p.
Ceramic capacitors 50V E6 22pF to 47n
2.5p. Electrolytic capacitors 50V .5, 1, 2mf
6p; 25V 5, 10mf 6p; 16V 22, 33mf 6p;
47mf 4p; 100mf 7p; 330, 470mf 9p.
Zeners 400mw E24 2v7 to 33v 7p. Preset
pots subminiature 0.1W horiz or vert 100 to
2M2 8p. IC sockets 8 dil 8.7p, 14 dil 10.1p,
16 dil 12p.

SWANLEY ELECTRONICS,
Dept. PE, 32 Goldsrd Rd.,
Swanley, Kent BR8 2EZ.
Tel: Swanley (0322) 64851.
Please allow 14 Days For Delivery

Postage £3.50 on computers, £4.50 on
printers and 45p on other orders. Lists 27p
post free. Please add VAT to all prices except
those sections marked with a * which
already include it. Overseas and official
credit orders welcome.

TRANSFORMERS

MARCO TRADING
British made transformers at very attractive prices.

Primary	Secondary	Current	1+	10+	100+
240v:	4.5-0-4.5v	400m/a	50p	45p	35p
240v:	6-0-6v	100m/a	58p	52p	43p
240v:	6-0-6v	500m/a	65p	60p	48p
240v:	9-0-9v	200m/a	75p	70p	58p

Manufacturers note: We can supply FROM STOCK, 1000+ quantities of the above transformers and adaptors below.

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit the UK shaver socket.

REF.	D.C. Voltage	Current	1+	10+	100+
EOB	4.5V	200m/a	50p	45p	32p
EM3	6V	200m/a	£1.00	80p	55p
EO9	6V	400m/a	£1.50	£1.25	85p
ET4	9V	150m/a	£1.50	£1.25	85p

Please note that there is no extra P/P charge on the above transformers and adaptors.
Export please add Sea/Air mail at cost.
Callers welcome Mon-Fri 9-5.

This advert is only a fraction of our range, send 25p for our latest catalogue. Please add 35p P/P to all orders. (Free over £5.00). Add 15% VAT to total. Send orders to:
Dept. PE2, MARCO TRADING,
The Old School, Edstaston, WEM, Shropshire SY4 5RJ.
Special Offer Test Equipment Catalogue available upon request. Send S.A.E. or Telephone.
All order despatched by return of mail. **Tel: (094872) 464**

CELESTION **RICHARD ALLAN**

WE SELL FANE GOODMAN
High quality power speakers
12 in 50W
8 ohms
12 in 50W
16 ohms
12 in 80W
8 ohms
12 in 80W
16 ohms
15 in 150W
8 ohms
15 in 150W
16 ohms

PIEZO HORN TWEETERS
Up to 100 watts each No v-
over required Flared Horns
Mid range Flared Horns in
stock now Large range of
speakers, microphones
equipment, ham
Heavy chromed Floor Stand
£9.95
£8.50
£99.99
Boom Arm
Echo Chamber
Analogue Echo Chamber
£59.95

CROSSOVERS

100W	8 ohm	2 way
100W	8 ohm	3 way
80W	8 ohm	4 way
60W	8 ohm	2 way

Stockists of leading makes of Disco Units
& Lighting Equipment.
CITRONIC, FAL, TK, ICE,
OPTIKINETICS, PLUTO.
Give your cabinets the professional
finish.
Send 2 x 14p stamps for illustrated
catalogue.
Please allow 14 days for delivery.

MUSICRAFT
303 EDGWARE ROAD,
LONDON W.2, ENGLAND
TELEPHONE: 01 402 9729 / 01 402 2898



Metal cased 9" PM 101


CROFTON MONITOR

10 MHZ Bandwidth
P4 Standard. Also available with P31

PRICE ON APPLICATION

NEW-PRICE MONITOR

Plastic cased 12"

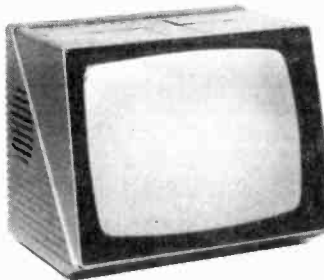

High resolution
24 MHZ Bandwidth
P31 (green) Standard and P4 high resolution Standard.

PRICE ON APPLICATION

Dealer and O.E.M. Enquiries Welcome

CROFTON ELECTRONICS LTD

35 Grosvenor Road, Twickenham, Middx TW1 4AD

01-891 1923/1513

Telex: 295093

Buy British—Buy Douglas Transformers
Mail Order from TITAN Transformers & Components
Central Hall Chambers, Duncombe Street, Grimsby, South Humberside DN32 7EG
Prices include 15% V.A.T. Send for our Catalogue.



12 24V RANGE PRI 220 240V				30.60V RANGE PRI 120 220 240V				AUTOTRANSFORMERS 240 220 115V			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
213	1	0.50	2.65	124	1	0.5	3.30	25	65	3.90	1.20
71	2	1	2.77	126	2	1	6.36	64	80	4.82	1.20
18	4	2	3.98	127	4	2	7.86	4	150	6.21	1.57
68	3	1.5	3.46	125	6	3	11.78	69	250	7.54	1.57
85	5	2.5	6.06	123	8	4	14.72	53	350	9.73	2.10
70	6	3	6.67	40	10	5	17.10	87	500	11.70	2.40
108	8	4	8.03	120	12	6	19.44	83	750	13.51	2.25
116	12	6	9.31	121	16	8	27.70	84	1000	18.31	2.55
17	16	8	11.46	122	20	10	32.05	95	2KVA	34.36	5.50
187	30	15	19.23	189	24	12	37.02	73	3	64.74	5.50
232	40	20	27.61					57	5	97.85	7.00
								101	10	179.05	10.50

15 30V RANGE PRI 220 240V				48 96V RANGE PRI 170 220 240V				CASED AUTOTRANSFORMERS			
TYPE	AMPS	PRICE	P/P	TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
112	1	0.50	2.84	430	1	0.5	4.69	56W	20	6.60	0.94
79	2	1	3.29	431	2	1	7.84	64W	80	8.43	1.57
3	4	2	6.18	432	4	2	12.94	4W	150	10.86	1.90
20	6	3	7.19	433	6	3	14.62	69W	250	13.17	2.10
21	8	4	8.52	434	8	4	20.04	67W	500	20.46	2.40
51	10	5	10.57	435	10	5	28.75	84W	1000	30.24	2.80
117	12	6	11.94	436	12	6	36.16	95W	2000	54.83	5.50
88	16	8	16.14	437	16	8	39.47	73W	3000	78.67	7.00
89	20	10	18.54								
90	24	12	20.57								
91	30	15	23.63								
92	40	20	33.21								

25 50V RANGE PRI 120 220 240V				LINE ADJUSTMENT AUTOTRANSFORMERS			
TYPE	AMPS	PRICE	P/P	TYPE	VA	PRICE	P/P
102	1	0.50	3.29	149F	60	8.40	1.90
103	2	1	4.09	150F	100	9.71	1.90
104	4	2	7.65	151F	200	13.84	2.25
105	6	3	9.09	152F	250	16.69	2.40
106	8	4	12.24	153F	350	20.77	2.80
107	12	6	16.15	154F	500	26.03	2.90
118	16	8	22.46	155F	750	36.75	5.50
119	20	10	27.05	156F	1000	47.42	6.50
109	24	12	32.44				

Send Today 50p (Refundable with First Order) for Catalogue
DEPT. PE TITAN TRANSFORMERS AND COMPONENTS
CENTRAL HALL CHAMBERS GRIMSBY DN32 7EG
MAIL ORDER ONLY - PRICES INCLUDE 15% VAT

LOTS OF NEW ILP ENCAPSULATED PRE-AMPS - COMPATIBLE WITH ALL ILP MODULES

Suddenly, instead of two ILP encapsulated pre-amps, there are eight — everything from the simple mono pre-amp (HY6), through mixing mono pre-amps (HY12 and HY69), to a dual stereo pre-amp (HY71). Plus a new guitar pre-amp (HY73).


Each gives the very best reproduction from your equipment that your money can buy, and all are protected against short circuit and wrong polarity.

All ILP modules are compatible with each other — combine them to create almost any audio system. Every item carries a 5 year no quibble guarantee and includes full connection data.

So send your order today — the Freepost coupon needs no stamp

ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, PRE-AMPS

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 6	Mono pre-amp	Provides inputs for mic/mag cartridge/tuner/tape/auxiliary with volume/bass/treble controls	10 mA	£7.41	£6.44
HY 9	Stereo pre-amp	Two channels mag cartridge mic + volume control	10 mA	£7.71	£6.70
HY 12	Mono pre-amp	Mixes two signals into one with bass/mid range/treble controls	10 mA	£7.71	£6.70
HY 66	Stereo pre-amp	Two channels with inputs for mic/mag cartridge/tape/tuner/auxiliary with volume/bass/treble/balance	20 mA	£14.02	£12.19
HY 69	Mono pre-amp	Two input channels mag cartridge mic with mixing and volume/treble/bass controls	20 mA	£12.02	£10.45
HY 71	Dual stereo pre-amp	Provides four channels for mag cartridge/mic with volume control	20 mA	£12.36	£10.75
HY 73	Guitar pre-amp	Provides for two guitars (bass + lead) and mic with separate volume/bass/treble and mixing	20 mA	£14.09	£12.25
HY 75	Stereo pre-amp	Two channels each mixing two signals into one with bass/mid-range/treble controls	20 mA	£12.36	£10.75

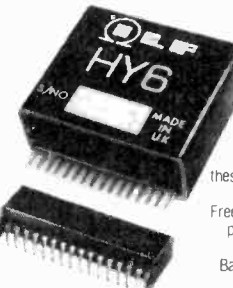

For easy mounting we recommend B 6 mounting board for modules HY6-HY13 £0.90 inc VAT (0.78 ex VAT) B 66 mounting board for modules HY66-HY77 £1.12 inc VAT (0.99 ex VAT). All modules are encapsulated and include clip-on edge connectors. All operate from +15V minimum to +30V maximum, needing dropper resistors for higher voltages. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

How to order Freepost:
Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

Please send me the following ILP modules

PE 4/4

Total purchase price

I enclose Cheque Postal Orders Int Money Order

Please debit my Access / Barclaycard No

Name

Address

Signature

Post to ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England
Telephone (0227) 54778 Technical (0227) 64723 Telex 965/80

ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US

ELECTROVALUE

CATALOGUE '82

A MUST FOR ANYONE USING A SCREWDRIVER OR SOLDERING IRON!



PACKED WITH INFORMATION ON MORE THAN 6000 ITEMS INCLUDING SIEMENS CAPACITORS, FERRITES AND SEMI-CONDUCTORS, ALSO SOLDER TOOLS, METERS ETC.

FOR YOUR COPY OF CATALOGUE 82 please send 70p (includes 70p voucher reclaimable against orders valued £10.00 or over).

DISCOUNTS

5% on orders over £23.00 (inc. VAT). 10% on orders over £57.50 (inc. VAT) on most catalogue items but not for payments by credit cards.

ALL ITEMS BRAND NEW AND GUARANTEED SPEEDY MAIL ORDER SERVICE

No P/P charges on U.K. C.W.O. orders over £5.75 inc. V.A.T. (add 40p handling charge if under).

PLEASE ADD 15% V.A.T. TO TOTAL VALUE OF ALL ORDERS

4000BE SERIES	74LS00 SERIES	74LS193	90p
4000BE 15p	74LS00 14p	74LS193 90p	
4001BE 18p	74LS02 14p	74LS195 87p	
4002BE 18p	74LS04 16p	74LS196 90p	
4006BE 89p	74LS05 23p	74LS197 85p	
4007BE 18p	74LS08 20p	74LS253 90p	
4008BE 65p	74LS10 19p	74LS257 75p	
4009BE 54p	74LS11 20p	74LS258 160p	
4010BE 45p	74LS14 18p	74LS266 31p	
4011BE 18p	74LS20 18p	74LS273 130p	
4012BE 19p	74LS30 21p	74LS279 78p	
4013BE 38p	74LS32 22p	74LS289 285p	
4014BE 96p	74LS37 24p	74LS367 56p	
4015BE 114p	74LS38 35p	74LS368 55p	
4016BE 38p	74LS42 58p	74LS373 150p	
4017BE 66p	74LS47 88p	74LS374 150p	
4018BE 64p	74LS51 25p	74LS378 84p	
4019BE 80p	74LS73 30p	74LS393 85p	
4020BE 90p	74LS74 30p		
4021BE 88p	74LS75 44p		
4022BE 70p	74LS76 30p		
4023BE 19p	74LS85 80p		
4024BE 88p	74LS86 38p		
4025BE 19p	74LS90 44p		
4026BE 175p	74LS92 50p		
4027BE 58p	74LS93 57p		
4028BE 104p	74LS107 40p		
4029BE 97p	74LS112 38p		
4030BE 51p	74LS123 85p		
4041BE 34p	74LS125 45p		
4042BE 75p	74LS126 42p		
4043BE 88p	74LS132 42p		
4044BE 93p	74LS136 42p		
4046BE 128p	74LS137 110p		
4049BE 48p	74LS138 45p		
4050BE 19p	74LS139 70p		
4060BE 133p	74LS145 120p		
4069BE 23p	74LS148 165p		
4070BE 27p	74LS151 77p		
4071BE 19p	74LS153 77p		
4072BE 19p	74LS155 94p		
4081BE 19p	74LS156 94p		
4082BE 19p	74LS157 60p		
4093BE 45p	74LS161 78p		
4510BE 65p	74LS163 90p		
4511BE 60p	74LS164 90p		
4514BE 39p	74LS165 75p		
4516BE 137p	74LS166 185p		
4518BE 50p	74LS173 100p		
4520BE 70p	74LS174 85p		
4543BE 100p	74LS175 90p		
4543BE 195p	74LS191 90p		

Computing IC's	REGULATORS	TRANSISTOR SELECTION	ANALOGUE IC SELECTION
2114 £1.50	7805/12/15/24 65p	2N3053 23p	741C8 18p
4116 27.90	7905/12/15/24 85p	2N3054 73p	748C8 35p
4116 200nS £1.50	78L05/12/15/24 32p	2N3055 70p	7555 86p
4116 250nS £1.30	79L05/12/15/24 67p	BC327 11p	CA3080E 86p
4116 300nS £0.90	723 (14 pin) 36p	BC337 11p	CA330E 99p
Z80A CPU £6.00	78H05 £5.55	BD130 45p	CA3140E 40p
Z80A P10 £6.00	78HGKC £7.20	BD131 77p	LM380N 99p
Z80A CTC £6.00	79HGKC £12.15	BD139 30p	LM381 £1.51
6402 UART £4.50	LM317K £3.21	BD140 32p	LM3914N £2.68
Special Offer		BD679 53p	NE555V 23p
25 x 4116 (300nS) £16.00 only		BC680 55p	NE566A 76p

Low Profile IC Holders - BICC	Low Profile IC Holders - BICC
pins 1 off, 25 off 8 3p £1.60	
14 12p £2.40	
16 14p £2.80	
18 16p £3.20	
20 18p £3.60	
22 21p £4.20	
24 21p £4.20	

SHOP HOURS 9-5.30 p.m. (1 p.m. Sat.) Please mention this journal when writing or ordering by post.

ELECTROVALUE LTD

YOU PUT MORE POWER IN YOUR £ WHEN YOU BUY FROM US!

NICADS AND CHARGERS

by Sanyo Cadnica

N450AA (AA size)	99p
N1800C (C size)	£2.27
N3500D (D size)	£4.10
6N75P (PP3 size)	£4.70
CHARGERS:	
NC75G (PP3)	£4.95
NC450S (4 x AA)	£4.95
NC1230 (AA, C, D)	£7.60

CAPACITOR PACK

Buy in quantity for best value.
CP1: 100 ceramic capacitors from 1p8 to 1µF. Selection determined by popular demand. Pack Price £3.50

RESISTORS IN HANDY PACKS

1W, 5% tolerance, each pack 100 items from one decade. Selection determined by popularly demanded values.
RD1: 1R0-8R2; RD2: 10R-82R; RD3: 100R-820R; RD4: 1K-8K2; RD5: 10K-82K; RD6: 100K-820K; RD7: 1M-10M, each decade pack £1.30

ALUMINIUM BOXES WITH LIDS

AB7	Size	Price
AB7	70x133x38	85p
AB8	101x101x38	85p
AB9	101x70x38	85p
AB10	101x133x38	85p
AB11	101x64x51	85p
AB12	76x51x25	67p
AB13	127x89x64	99p

TRANSISTOR SELECTION

2N3053	23p
2N3054	73p
2N3055	70p
BC327	11p
BC337	11p
BD130	45p
BD131	77p
BD139	30p
BD140	32p
BD679	53p
BC680	55p
BFY50	28p
MJE2955	£1.20
MJE3055	87p
TIP31A	44p
TIP32A	44p
TIP41A	45p
TIP42A	45p
TIP2955	55p
TIP3055	55p

ANALOGUE IC SELECTION

741C8	18p
748C8	35p
7555	86p
CA3080E	86p
CA330E	99p
CA3140E	40p
LM380N	99p
LM381	£1.51
LM3914N	£2.68
NE555V	23p
NE566A	76p
TDA2030	£1.45
TL071CP	45p
TL072CP	75p
TL074CN	£1.20
UA170	£1.52
XR2206	£4.60
ZN414	£1.22
ZN425E	£3.90

Dept. PE, 4, 28 St Jude Rd., Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 35603 (STD 0474; London 07) Telex 264475, Northern Branch (personal shoppers only) 880 Burnage Lane, Burnage, Manchester M19A 1MA. Phone (061) 4324945.

COMPUTERS

Our computer business is now transferred to:
EV COMPUTING LTD.
700 BURNAGE LANE, BURNAGE, MANCHESTER M19A 1MA.
Phone 061-432 4945
— A MICROVALUE FOUNDER MEMBER & DISTRIBUTOR.

Enquiries and orders may be sent to ELECTROVALUE for passing on to EV COMPUTING who will deal with you promptly and efficiently.

PANEL METERS

£2.20 each

instead of £2.69

until March 31st

TYPE MU

FSD 50µA, 100µA, 1mA, 5mA, 10mA, 50mA, 500mA, 1A.

SWITCHES AND CONNECTORS IN VERY GREAT VARIETY. VEROBOXES, I.L.P. TOROIDAL TRANSFORMERS.

SABTRONICS

FREQUENCY METER

Model 8000B: 9-digit 1GHz Frequency Meter. Professional specification: £160.00

OTHER SABTRONICS EQUIPMENT

2015A Bench DMM (LCD)	£83.00
2035A Hand-Held DMM (LCD)	£82.00
8110A 8 digit 100MHz DFM	£87.00
8610A 8 digit 600MHz DFM	£82.00
5020A 1-200KHz Function Generator, Sine, Square, Triangle and separate TTL Square wave outputs	£79.00

If you haven't bought me yet — it's high 'time You did! . . . I'm only £24.50

SPEECHTIME

It's true! Continuing our special offer (while stocks last) means there's still nearly £5.00 off the price of 'Speechtime' — the first ever easy-to-build speaking clock kit. 'Speechtime's' combination of electronics and quartz technology plus clear instruction manual make it fun to build and fun to own — equally suitable for beginner or expert. Speechtime also makes a great gift to build for someone else. Look at these 'plus' features:

- Accurate to a minute a year
- Adjustable voice pitch
- Pocket size — approx. 5in. x 2½in. x 1in.
- Grained stainless-steel case
- Useful in the home or office

Silicon Speech Systems (A Powertran Subsidiary)

PORTWAY INDUSTRIAL ESTATE, ANDOVER, HANTS., SP10 WN

EASY ORDERING BY TELEPHONE — RING ANDOVER (0264) 64455 AND GIVE YOUR ACCESS OR BARCLAYCARD NUMBER

Goods normally despatched 7 days.

JOIN UP WITH LITESOLD

Litesold's new 'L' Series soldering iron — now at a bargain price. Outstanding performance. Lightweight. Easy to maintain. Elements are enclosed in Stainless Steel shafts, insulated with mica and ceramic. Non-seize interchangeable bits. choose from 'copper' or 'long life'. A very special tool at a very special 'direct' price. Just £5.58 for iron fitted with 3.2mm copper bit. Just £2.40 for 3 spare copper bits (1.6, 2.4, 4, 7).

A mere £4.38 for professional spring stand! Or buy the lot for £11.12! and save 10%.

All prices inc. VAT P.&P. Please allow 14 days delivery. Write today. Send cheque/P.O. to Litesold, 97-99 Gloucester Road, Croydon CR0 2DN or phone 01-689 0574 for Barclaycard/Access sales.

£5.58 LITESOLD LIGHT SOLDERING DEVELOPMENTS LTD

The ONE catalogue you MUST have!

- About 2,000 items clearly listed.
- Profusely illustrated throughout.
- Large A-4 size pages.
- Bargain list, order form and 2 coupons each worth 25p if used as directed, all supplied free.

Price £1, plus 50p for post, packing and insurance.

Send cheque or P.O. for £1.50

HOME RADIO COMPONENTS LTD
Dept. PE, P.O. Box 92, 215 London Road, Mitcham, Surrey. 01-543 5659

Get a great deal from

Marshall's . . .

"PRACTICAL ELECTRONICS"
TV CAMERA PROJECT

We shall be pleased to receive enquiries for this fantastic Camera Kit, including Metal case, P.C. Board, Vidicon Tube Mounting and Screens, but excluding Lens and Power Supply, at **£166.50 inc.** Postage and Packing, plus VAT.

SPECIAL OFFERS THIS MONTH:-

Integrated Circuits:-

Numbers: 7404, 7410, 7412, 7420, 7440, 7446, 7447, 7448, 7453 and 7472

at £1.50 for 10 of any number, plus 60 pence Postage and Packing, and VAT.

Transistors:-

Numbers: BC347, BC350 and BC171

at £1 for 10 of any one Number, plus 60 pence Postage and Packing, and VAT.

SEND FOR OUR PRICE LIST, 50p Post Free.

A. MARSHALL (LONDON) LTD.,
Kingsgate House, Kingsgate Place, London, N.W.6.
Tel: 01-624 8582 and 01-624 0805.

INTERESTED IN ELECTRONICS?

TRY A ZEDPACK! COMPONENTS AT A PRICE EVERYONE CAN AFFORD

Z1 300 mixed 1 and 1/2 watt resistors £1-95
Z2 150 mixed 1 and 2 watt resistors £1-50
Z3 300 mixed capacitors, most types £3-95
Z4 100 mixed electrolytics £2-20
Z5 100 mixed polystyrene caps £2-20
Z6 300 mixed printed circuit components £1-95
Z7 300 mixed printed circuit resistors £1-45
Z9 100 mixed miniature ceramic and plate caps £1-20
Z10 25 assorted pots. £1-50
Z11 25 assorted prassets, skeleton etc. £1
Z12 20 assorted vdr's and thermistors £1-20
Z13 11b mixed hardware. Nuts, bolts self-tappers, s'aving, etc. £1-20
Z14 100 mixed, new and marked, full spec. transistors. Pack includes:- BC148, BF154, BF274, BC212L, BC238, BC184L, PBC108 and, or lots of similar types £4-95
Z15 100 mixed diodes including:-zener, power, bridge, signal, germanium, silicon etc. All full spec. £4-95
Z16 20 1N4148 £1
Z17 20 1N4003/10D2 £1
Z18 20 assorted zeners, 1 watt and 400mw £1-50
Z19 12-125" TIL 209 RED. LED'S £1
Z20 18 Assorted switches, including push button, slide, multipole, miniature etc. Fantastic value. £1-20.

UHF MODULATORS
Video in UHF out. Calibrated to channel 36 (625 line UHF) housed in metal box 2 1/2" x 2" x 1 1/2" with 9' coaxial lead, TV plug and connection data. £2-50 ea. 3 for £5.
200µA Miniature level/batt. meters, as fitted to many cassette recorders. 90p
Deluxe FIBREGLASS printed circuit etching kits.
Includes 150 sq ins. of copperclad F/G board, 1lb ferric chloride, (made for U.S. army to MIL. SPEC.), 1 dalo etch resist pen, abrasive cleaner, tweezers, etch resist dish and instructions. **OUR PRICE £5-95**
1lb of FeCl. £2-25.

**TO: "GEMINI ELECTRONIC COMPONENTS" DEPT PE
"THE WAREHOUSE" SPEEDWELL ST. LONDON S.E.8.**

Where shown. Send Cheque* or Postal Order. Plus 60p P&P, and 15% VAT.
Please Quote ZED Code. *Schools etc. SEND OFFICIAL ORDER
ZED PACKS now available for Callers at 50 Deptford Broadway, London, S.E.8.
Please allow 7 days for delivery. Send large S.A.E. for fuller list.

100 Miniature reed switches. £2-30
100 Subminiature Reed Switches. £4-20

SMALL MAGNETS 6 for £1

P/B SWITCH BANKS
These cost a fortune! Were made for various music centres. Includes independent and interdependent latching types multi pole c/o etc. Can be modified. Can't be repeated. 3 Banks for £1. **KNBS** for Switch Banks 10 for £1. Chrome or spun aluminium finish.

MINIATURE MAINS TRANSFORMERS
Top quality. Split bobbin construction will give 4-5V-0-4-5V at 250MA. 1 1/2" x 1 1/2" x 1 1/2", all sorts of uses. **ONLY £3** for £2-50.

PP3 Battery Connectors 10 for 50p.
Miniature Press to Make Switches, Red knob, 3 for 50p.
Subminiature S.P.C.O. Slide Switches, 6 for 50p.
Miniature D.P.C.O. Slide Switches, 6 for 50p.
Standard 2P, 3 Position Slide Switch, 4 for 50p.

TBA810P 7 Watt Amp. I.C. with circuits and data. only £1
MFC8010 1 Watt I.C. with data and circuits. 60p, 2 for £1
555 Timers. 30p ea., 4 for £1
6A 100V Bridge Rectifier. Small, 80p ea., 3 for £2
2N3055H. RCA. 60p, 3 for £1.50
9 Section, Chrome on Brass Telescopic Aerial. Plugs into any 3-5mm socket. Approx 25" extended £1 each, 3 for £2-50.
Hi Power Infra Red Transmitter 5mm LED. TIL 38 60p ea. 3 for £1-50.
Crystal Clear 3mm LEDs very pretty Red, Green, Yellow. 10 of one colour £1. 10 of each £2-50.

ALTERNATOR RECTIFIERS
Make lovely 60 amp bridges. Ideal for High Power Battery Chargers.
Type 4A.FI. Set of 4 (2 neg. case + 2 pos. case) £2.

Special Purchase enables us to offer Mullard C200 Polyester Capacitors (Liquorets Allsorts) at the unbeatable price of £2 for 100 mixed. £15 for 1000. These consist of factory clearance lots i.e. spillages, floor sweepings, cosmetic rejects etc. Also, Mullard Miniature Electrolytics. 200 mixed £2.

MIXERS, FADERS, VU METER DRIVERS AND MORE- ALL NEW FROM ILP!

Just some of the 28 new amazingly compact modules from ILP Electronics, Britain's leader in electronics modules — you'll find more new products in the amps and pre-amps advertisements.

All ILP modules are compatible with each other — you can combine them to create almost any audio system. Together they form the most exciting and versatile modular assembly system for constructors of all ages and experience.

Every item from ILP carries a 5 year no quibble guarantee and includes full connection data. So send your order on the Freepost coupon below today!

MIXERS

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 7	Mono mixer	Mixes eight signals into one	10 mA	£5 92	£5 15
HY 8	Stereo mixer	Two channels each mixing five signals into one	10 mA	£7 19	£6 25
HY 11	Mono mixer	Mixes five signals into one — with base/treble controls	10 mA	£8 11	£7 50
HY 68	Stereo mixer	Two channels each mixing ten signals into one	20 mA	£9 14	£7 95
HY 74	Stereo mixer	Two channels each mixing five signals into one — with treble and bass controls	20 mA	£13 17	£11 45

AND OTHER EXCITING NEW MODULES

Model No	Module	What it does	Current required	Price inc VAT	Price ex VAT
HY 13	Mono VU meter	Programmable gain/LED overload driver	10 mA	£6 84	£5 95
HY 67*	Stereo headphone driver	Will drive stereo headphones in the 4 ohm 2K ohm range	80 mA	£14 20	£12 35
HY 72	Voice operated stereo fader	Provides depth/delay effects	20 mA	£15 07	£13 10
HY 73	Guitar pre-amp	Handles two guitars (bass and lead) and mic with separate volume/bass/treble and mix	20 mA	£14 09	£12 25
HY 76	Stereo switch matrix	Provides two channels each switching one of four signals into one	20 mA	To be announced	
HY 77	Stereo VU meter driver	Programmable gain/LED overload driver	20 mA	£10 64	£9 25

For easy mounting we recommend

B 56 mounting board for modules HY6-HY13 £0 90 inc VAT (0 78 ex VAT)
B 66 mounting board for modules HY66-HY77 £1 12 inc VAT (0 99 ex VAT)
*All modules are encapsulated and include clip on edge connectors. All operate from +15V minimum to -30V maximum. Needing dropper resistors for higher voltages. HY67 can be used only with the PSU 30 power supply unit. Modules HY6 to HY13 measure 45 x 20 x 40mm. HY66 to HY77 measure 90 x 20 x 40mm.

FP 480 BRIDGING UNIT FOR DOUBLING POWER

Designed specially by ILP for use with any two power amplifiers of the same type to double the power output obtained and will function with any ILP power supply. In totally sealed case, size 45 x 50 x 20mm with edge connector. It thus becomes possible to obtain 480 watts rms (single channel) into 8Ω. Contributory distortion less than 0.005%. Price: £5 51 inc VAT (ex VAT £4 79.)

How to Order Freepost:

Use this coupon, or a separate sheet of paper, to order these products, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following ILP modules PE 5/4

Total purchase price _____
I enclose Cheque Postal Orders Int. Money Order


Please debit my Access/Barclaycard No _____

Name _____


Address _____

Signature _____

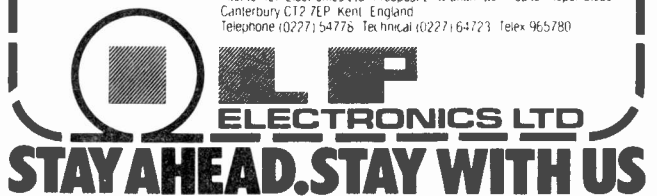Post to ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England.
Telephone (0227) 54776. Technical (0227) 64723. Telex 965780



1
9
8
2

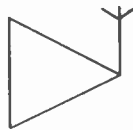

FINAL RADIO AND ELECTRONICS EXHIBITION AT BELLE VUE

by the NORTHERN AMATEUR RADIO SOCIETIES ASSOCIATION
in the

LANCASTER HALL BELLE VUE MANCHESTER

on Sunday 4th April 1982
doors open at 11 a.m.

The North's Premier Amateur Radio and Electronics Event.

Features Inter-Club Quiz, Grand Raffle, Construction Contest, Amateur Computer Stands, R.S.G.B. Bookstall, Radio Society's Stands and Trophy, Home Office and Raynet Stands.

The following traders have booked space:

Eurova Ltd	Amateur Radio Exchange	Stephens-James Ltd
J. Birkett	The Amateur Radio Shop	Isherwood Electronics
Radiotronics	Microwave Modules	Bredbury Electronics
Low Electronics	John's Radio	Display Electronics
P.M. Electronic Services	New Cross Radio	SGS Electronics
P.K.G. Electronics	W.H. Westlake	The Computer Junk Shop
DS Electronics	Telecom	Arrow Electronics Ltd
Thanet Electronics	Leeds Amateur Radio	Royd Electronics
Electrovalue Ltd	Newton Engraving	Ace Mailtronix Ltd
Elphan Electronics	Packer Communications	Gemini Electronic Components
J. Peterson	Micro Print Ltd	Tony's Radios
Elkan Electronics	Chris Moulding	J.M.G. Electronics
Sutton Electronics	Gemini Communications	Sota Comm. Syst Ltd
S.M.C. (Jack Tweedy) Ltd	R.S.G.B Books	M K Electronics
Wilson Valves	Scorpio Amateur Aerials	

Belle Vue has ample car parks.

F.M.Talk in on GB3NRS & G8NRS/A on 145MHz Chs 22 R2 R6
and on 433MHz Chs SU8-RB4-RB14

**ADMISSION 60p BY RAFFLE TICKET AND EXHIBITION PLAN
ENTER AT REAR OF BELLE VUE OPPOSITE MAIN CAR PARK
OFF HYDE ROAD A57**

"SEE SCAN" (PRINTOID LTD)

**FREEPOST,
20/21 ALFRIC SQUARE,
PETERBOROUGH PE2 0BR**

**The designers and manufacturers of the
PE Camera Project offer technical club
membership/certification to project enthusiasts.**

Camera technical support and
circuit testing/alignment service available.
Various kits and projects always on hand
(*simple/intermediate/advanced*).

Write for full parts list/club application forms
(camera/electronics/security products) or ring:

**Project "C" Engineer
on 0733 253447 (4 lines)**

Access/Barclaycard accepted.

ILP POWER SUPPLIES- MOST WITH ILP TOROIDAL TRANSFORMERS



Space-saving, efficient ILP power supplies are designed to give you flexibility in planning audio assemblies. Nine of the eleven models have toroidal transformers manufactured on new cost-efficient high technology machines in our own factory. So we keep the quality up and the price down.

ILP power supplies are compatible with all other ILP modules — combine them to produce almost any audio system. All carry the ILP 5 year no quibble guarantee and include full connection data.

So send your order on the Freepost coupon below today!

POWER SUPPLY UNITS

Model No	For use with	Price inc VAT	Price ex VAT
PSU 30	±15V combinations of HY6/66 series to a maximum of 100 mA or one HY67	£5 18	£4 50
	The following will also drive the HY6/66 series except HY67 which requires the PSU 30		
PSU 36	1 or 2 HY 30	£9 32	£8 10
PSU 50	1 or 2 HY 60	£12 58	£10 94
PSU 60	1 x HY 120/HY 120P/HD 120/HD 120P	£15 00	£13 04
PSU 65	1 x MOS 120/1 x MOS 120P	£15 32	£13 32
PSU 70	1 or 2 HY 120/HY 120P/HD 120/HD 120P	£18 31	£15 92
PSU 75	1 or 2 MOS 120/MOS 120P	£18 63	£16 20
PSU 90	1 x HY 200/HY 200P/HD 200/HD 200P	£18 63	£16 20
PSU 95	1 x MOS 200/MOS 200P	£18 77	£16 32
PSU 180	2 x HY 200/HY 200P/HD 200/HD 200P or 1 x HY 400/1 x HY 400P/HD 400/HD 400P	£24 54	£21 34
PSU 185	1 or 2 MOS 200/MOS 200P/1 x MOS 400/1 x MOS 400P	£24 68	£21 46

All models incorporate ILP toroidal transformers except PSU 30 and PSU 36 which include our own laminated transformers.

How to order Freepost:

Use this coupon or a separate sheet of paper, to order these modules, or any products from other ILP Electronics advertisements. No stamp is needed if you address to Freepost. Cheques and postal orders must be crossed and payable to ILP Electronics Ltd. Cash must be registered. C.O.D. — add £1 to total order value. Access and Barclaycard welcome. All UK orders sent post free within 7 days of receipt of order.

ILP Electronics Ltd., Freepost 2, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent.

Please send me the following PE 6/4
ILP modules _____

Total purchase price _____

I enclose Cheque Postal Orders Int. Money Order

Please debit my Access / Barclaycard No _____

Name _____

Address _____

Signature _____

Post to ILP Electronics Ltd Freepost 2 Graham Bell House Roper Close
Canterbury CT2 7EP Kent, England
Telephone (0227) 54778 Technical (0227) 64723 Telex 965780

ILP ELECTRONICS LTD
STAY AHEAD. STAY WITH US



SELLING OR BUYING

A classified advertisement could solve your problem at very little cost.

RING LINDA
01-261 5846

RECEIVERS AND COMPONENTS

300 SMALL COMPONENTS. Transistors, diodes £1.70. 7lbs assorted components £4.25. 10lbs £5.75. 20 wire ended neons £1. Forty 74 series ICs on panel £1.70. 500 capacitors £3.20. List 20p refundable. Post 60p, optional insurance 20p. JWB Radio, 2, Barnfield Crescent, Sale, Cheshire M33 1NL.

TURN YOUR SURPLUS Capacitors, transistors, etc., into cash. Contact COLES-HARDING CO., 103 South Brink, Wisbech, Cambs. 0945 4188. Immediate settlement.

BOURNEMOUTH/BOSCOMBE Electronic components specialists for 33 years. Foresters (National Radio Supplies), Late Holdenhurst Road. Now at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

50 COMPONENTS, assorted, transistors, resistors etc. £0.60 post paid. J & G Repairs, 100 Norman Rise, Livingstone, EH54 6LZ.

BRAND NEW COMPONENTS BY RETURN

Electrolytic Capacitors 15V, 25V, 50V.
0.47 — 1.0 — 2.2, 4.7 & 10 Mfds. — 5p.
22 & 47 — 6p. 100 — 7p. (50V — 8p). 220 — 8p.
(50V — 10p). 470 — 11p. (40V — 16p). 1000/15V — 15p.
1000/25V — 25p. 1000/40V — 35p.

Subminiature bead Tantalum electrolytics.
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.
2.2/35V, 4.7/25V — 15p. 10/25V, 15/16V — 20p.
22/16V, 33/10V, 47/6V, 68/3V & 100/3V — 30p.
15/25V, 22/25V, 47/10V — 35p. 47/16V — 80p.

Subminiature Ceramic Caps. E12 Series 100V.
2% 10 pf. to 47 pf. — 3p. 56 pf. to 330 pf. — 4p.
10% 390 pf. to 4700 pf. — 4p.

Vertical Mounting Ceramic Plate Caps. 50V.
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf. — 2p.

Polystyrene E12 Series 63V. Horizontal Mtng.
10 pf. to 820 pf. — 3p. 1000 pf. to 10,000 pf. — 4p.

Miniature Polyester 250V Vert. Mtg. E6 Series.
0.1 to 068 — 4p. 1 — 5p. 15, 22 — 6p. 33, 47 — 10p.
68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

Mylar (Polyester) Film 100V. Vertical Mounting.
0.01, 0.022, 0.047 — 3p. 0.1, 0.22 — 4p. 0.4, 0.05, 0.1 — 5p.

High Stability Miniature Film Resistors 5%
1W E24 Series 0.51R — 10M0. (Except 7M5, 9M1) — 1p.
1W E12 Series 1R0 to 10M0. — 1p.
1W E12 Series 10R to 10M0. — 3p.
1W metal film E12 Series 10R-1M0, 5% — 2p. 1% — 3p.
1N4148 — 2p. 1N4002 — 4p. 1N4006 — 6p. 1N4007 — 7p.
BC107/8/9 — 12p. BC147/8/9, BC157/8/9, 8F195 & 7 — 10p.
B Pin i.c.'s. 741 Op. amp. — 18p. 555 Timer — 24p.
DIL Holders B pin — 9p. 14 pin — 12p. 16 pin — 14p.
LED's, 3 & 5mm, Red — 10p. Green & Yellow — 14p.
Grommets for 3mm — 1p. Grommets for 5mm — 2p.
20mm. Q.B. Fuses 15, 25, 5, 1, 2, 3 & 5A — 5p.
20mm. Anti Surge 100mA to 5.0A — 8p.
20mm. Fuseholders P.C. or Chassis Mtg. — 8p.
Battery Snaps (pairs) PP3 — 6p. PP9 — 12p.
400mW Zener diodes E24 series 2V7 to 33V — 8p.
Prices VAT inclusive Post 15p. (Free over £5.00).

THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

SMALL ADS

The prepaid rate for classified advertisements is 32 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £10.70 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Bank Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Manager, Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

T & J ELECTRONIC COMPONENTS. quality components, competitive prices. Illustrated catalogue 45p. 98 Burrow Road, Chigwell, Essex.

1000 ASSTD 5% RESISTORS, pre-formed for PCB mounting £2.50. 50 asstd full-spec LED's, 3 & 5mm, all colours £3.20. 50 asstd full-spec transistors. BC182/212/237/308 etc. £3.00. 100 asstd PC mtng electrolytics £3.00. One of each pack £11. All post free. SAE Wholesale list. PC Electronics, 2 Thornhill, Romsey Road, Whiteparish, Salisbury, Wilts.

TELECTRIC

As featured in PE March & April 82
Self Assembly Kit £47.50 + VAT
Built and Tested £64.00 + VAT
Components available separately.
SAE for details.
P&P £1, CWO

Response Company,
Froxfield, Petersfield, Hants. GU32 1DX.

**WHEN REPLYING TO
ADVERTISEMENTS PLEASE MENTION
PRACTICAL ELECTRONICS**

**THE OUTSTANDING
PRACTICAL ELECTRONICS
MINIATURE**

SCORPIO
CAR IGNITION

- ★ NEAT & COMPACT
 - ★ EASY TO INSTALL
 - ★ AMAZING LOW PRICE
 - ★ ROBUST DIE-CAST CASE
 - ★ FULL CIRCUIT PROTECTION
 - ★ COMPLETELY WEATHERPROOF
- All parts as specified in PE for only*

£14.85 inc. VAT, p&p.

PCB only: £1.75 inc. VAT, p&p.

Re-prints of 1975 & 1982 articles available; send S.A.E. for full price list of parts.

**DEPT. PE,
MICROSTATE LIMITED,
5 NORTHFIELD CLOSE,
FERNHILL HEATH,
WORCESTER, WR3 7XB.**

BOOKS AND PUBLICATIONS

ANY SINGLE SERVICE SHEET £1/L.S.A.E. Thousands different repair/service manuals/sheets in stock. Repair data your named T.V. £6.50, (with circuits £8.50). S.A.E. Newsletter, pricelists, quotations. AUS (PE), 76 Churches, Larkhall, Lanarkshire, (0698 883334).

SOFTWARE

ZX 81 (16K) SOFTWARE. Champions Quiz — it's fun for all ages. Four quiz programs on one cassette. All questions use RND functions £4.50. ROSE CASSETTES, 148 Widney Lane, Solihull, West Midlands.

ZX81 3K RAMKIT expandable to 7K, see Microbus Nov. 81. Send £13.25. EDWARDS ELECTRONICS, 23 Princes Street, Perth.

Z x 81 TEMPERATURE SENSORS (plug-in compatible), including UK P & P £17.95. Leaflet, Cheshire Micro Design, 66 Close Lane, Alsager, Stoke-on-Trent.

FREE CATALOGUE. Everything for microcomputer users. Phone Croydon Computer Centre, 29A Brigstock Road, Thornton Heath, Surrey. 01-689 1280.

FOR SALE

UK101 CASED, 1-2 Meg, 1-2K, VDU, Cegmon, Sound, 300-1200 Cassette Interface. Joustick. £200. Brighton 551306.

121 P.E.'s FROM 1964, 81 P.W.'s from 1969. Offers. No singles. Wolverhampton (0704) 332017.

P.E. RANGER: Save £8 on ex-factory prices. 6CH kits £52, built £58 — £2.00 p.p. (0359) 30867.

CHEAP HARD COPY. Teletype 32 ASR 75 baud, as new. £55. Basildon 22254. around 6pm best.

NEW PAPST REWIND MOTORS 125v/220v, A.C. 1200 rpm, 14 watts. £5.90 (£16.80 elsewhere), P&P £1.60. GREYMOOR ROBOTICS, 247 Fieldgate Mansions, Romford Street, London E1.

NEW BACK ISSUES OF 'PRACTICAL ELECTRONICS' available 90p each Post Free. Cheque or uncrossed P/O returned if not in stock — BELL'S TELEVISION SERVICES, 190 Kings Road, Harrogate, N. Yorks. Tel: (0423) 55885.

OPEN UNIVERSITY GENERATORSCOPE, full TS 282 course material, numerous components £60 the lot. Chester 678770.

PERSONAL

CHRISTIAN SINGLES. Friendship, contacts. 1982 holidays. Weekend houseparties. — C.F.F., Dept N46, Edenthorpe, Doncaster.

SERVICE SHEETS

SERVICE SHEETS £1 each plus SAE. Individual T.V. repair data £6.50 (with circuits £8.50). Free electronics newsletter, pricelists unique publications. Auspe, 76 Churches, Larkhall, Lanarkshire ML9 1HE.

BELL'S TELEVISION SERVICES for Service Sheets on Radio, Tv, etc £1.25 plus S.A.E. Colour TV Service manuals on request. S.A.E. with enquiries to B.T.S. 190 Kings Road, Harrogate, N. Yorkshire, Tel: (0423) 55885.

EDUCATIONAL

CAREERS IN MARINE ELECTRONICS. Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel. 03917 79123.

MISCELLANEOUS

SECURITY ALARMS KITS FROM £37. Full range of accessories. MFP Ltd., Harrison Road, Erdington, Birmingham B24 9AB. 021-373 0450.

CLEARING LABORATORY: scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

ULTRASONIC TRANSDUCERS. miniature, 40KHz, £2.85p/pair + 25p p&p. Dataplus Developments, 81, Cholmeley Road, Reading, Berks.

MAKE YOUR OWN PRINTED CIRCUITS

Etch Resist Transfers - Starter pack (5 sheets, lines, pads, I.C. pads) £2.00. Large range of single sheets in stock at 43p per sheet.
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets negative paper, 2 sheets positive film (A4) £2.10. **Photo-resist spray** (200 ml) £3.25 (p.p. 65p). **Drafting Film** (A4) 25p. **Precision Grids** (A4) 65p.
 22p stamp for lists and information. P&P 50p per order except where indicated.

P.K.G. ELECTRONICS
 OAK LODGE, TANSLEY, DERBYSHIRE.

CORDLESS TELEPHONES. Build your own simple and inexpensive units, send £3.00 for plans to J F Ashley, Birley Grange Cottage Farm, Baslow Road, Cutthorpe, Derbyshire.

DOUBLE SIDED COPPER CLAD FIBREGLOSS 12" x8", 5 sheets £4; 10 sheets £6; 20 sheets £10 inc. P&P. - Davron Trading, 1 Bankside, New Street, Chelmsford, Essex.

PARAPHYSICAL JOURNAL (Russian Translations): Psychotronic Generators, Kirlianography, Gravity Lasers, Telekinesis. Details SAE 4"x9", Paralab, Downton, Wilts.

Cabinet and Flightcase Fittings

Fretcloths, Coverings, Handles, Castors etc. Jacks and Sockets, Cannons, Bulgins, Reverb Trays, Emilar Compression Drivers, P&N Stands, Celestion Speakers, ASS, Glass-fibre Horns.

Send 30p Postal Order for illustrated catalogues to:-

ADAM HALL (P. E. SUPPLIES)

Unit G, Carlton Court, Grainger Road, Southend-on-Sea, Essex SS2 5BZ.

SECURITY SYSTEMS KITS ... All components and full instructions. Send large SAE for latest catalogue of advanced projects for car, caravan and home. Computech Systems, Ind. Est., N. Walsham NR28 0AN. Tel: (0692) 5600.

THE SCIENTIFIC WIRE COMPANY
 PO Box 30, London, E.4. 01-531 1568.

ENAMELLED COPPER WIRE

SWG	1lb	8oz	4oz	2oz
8 to 34	3.30	1.90	1.00	0.80
35 to 39	3.52	2.10	1.15	0.85
40 to 43	4.87	2.65	2.05	1.46
44 to 47	8.37	5.32	3.19	2.50
48 to 49	15.96	9.58	6.38	3.69

SILVER PLATED COPPER WIRE

14 to 30	6.63	3.86	2.28	1.50
----------	------	------	------	------

TINNED COPPER WIRE

14 to 30	3.97	2.41	1.39	0.94
----------	------	------	------	------

10 x 10 Mtr reels 3 amp PVC cable mixed colours **£5.00.**

Prices include P&P, VAT. Orders under £2 add 20p.

SAE for list of copper and resistance Wire. Dealer enquiries welcome.

CENTURION BURGLAR ALARM EQUIPMENT. Send SAE for free list or a cheque/PO for £11.50 for our special offer of a full sized signwritten bell cover, to Centurion Dept PE, 265 Wakefield Road, Huddersfield, W. Yorkshire, Access & Barclaycard telephone orders on 0484-35527.

ANNOUNCING - THE SENSATIONAL

VIBROSCOPE



Once again, Stuart Systems have astounded the world with a totally new concept. The **Video Vibroscope** produces a fantastic multi-coloured display on any TV. The picture is controlled by music, using microphone or other direct input and forms an exciting, pulsating and rhythmic experience which cannot fail to turn them on! A must for parties, discos, etc.

NOW AVAILABLE FOR ONLY £49.95

9v POWER UNIT £4.95. PLEASE ADD VAT AT 15% (POST & PACKING INCLUDED)

Barclay/Access orders accepted on telephone

WILLIAM STUART SYSTEMS Ltd
 Dower House, Billerica Road, Herongate, Brentwood, Essex CM13 3SD
 Telephone Brentwood (0277) 810244

**WOULD ADVERTISERS
 PLEASE NOTE THAT
 OUR BOX NO SERVICE
 IS NOT AVAILABLE FOR
 MAIL ORDER ADVERTISERS**

ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for..... insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)

NAME

ADDRESS

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Advertisement Manager

PRACTICAL ELECTRONICS

GMG, Classified Advertisement Dept., Room 2612, King's Reach Tower, Stamford Street, London SE1 9LS. Telephone 01-261 5846

Rate: 32p per word, minimum 12 words. Box No. 60p extra.

MISCELLANEOUS — CONTD.

ENAMELLED COPPER WIRE. 10 swg to 45 swg. S.A.E. for quotation by return, cheapest prices. 102 Parrswood Road, Manchester 20.

BURGLAR ALARM EQUIPMENT. Ring Bradford (0274) 308920 for our catalogue or call at our large showrooms opposite Odsal Stadium.

BIG EARS STOP! GO! LEFT! RIGHT!

SPEECH INPUT FOR ANY COMPUTER



Hugely successful Speech Recognition System, complete with microphone, software and full instructions.

ONLY **£49**

PLEASE STATE COMPANY NAME, ADDRESS, SUPERBOARD, NASCOM, VIC 20, MICRO ZX80/B1, PET, TRS80, T2000, APPLE II, BBC MICRO

ZX80 ZX81
MUSIC SYNTHESISER
+ 16 LINE CONTROL PORT

Play 3-part music, sound effects, drums etc. Full control of attack, decay and frequency. Input/Output lines provide control and monitor facility for Home Security, Robot Control, Model Railway, etc. etc. Works with or without 16K RAM.

Add keyboard to make a live performance polyphonic synthesiser! Full instructions/software included.

AMAZING VALUE AT ONLY **£19.50** (KIT)

Extra connectors at £2.50 £25.00 (BUILT)

COLOUR MODULATOR KIT **£12**
BUILT **£18**

UK101/NASCOM COLOUR GRAPHICS KIT **£45**
BUILT **£60**

Inc. Modulator. Still the best selling system!

Please add VAT at 15% to all prices
Barclay/Access orders accepted by telephone.

WILLIAM STUART SYSTEMS Ltd
Dower House, Billericay Road,
Herongate, Brentwood,
Essex CM13 3SD
Telephone: Brentwood (0277) 810244

MICRO TRANSMITTER. VHF/FM, matchbox size, variable 70-150 MHZ, complete kit. £4.50. Microtronic, 9, Tennant, Simonside, South Shields.

PRACTICAL ELECTRONICS P.C.B.'s

Drilled, 1.5mm Glass fibre Fry's Roller Tinned
NOV 81 UK 10! Monitor change EP640 £1.87
DEC 81 Space Invaders EA303 EA305 £6.91 a pair
MAR 82 Emergency Light EP793 £1.56

For full list and current pcb's send SAE. Pcb's also produced to customers own masters. Trade enquiries welcomed. Write for quote. CWO Please. Postage — add 35p postage and packing to complete order. Europe 70p.

PROTO DESIGN
14 Downham Road, Ramden Heath,
Billericay, Essex CM11 1PU. Telephone 0268-710722

TIME WRONG?

MSF CLOCK is ALWAYS CORRECT — never gains or loses. SELF SETTING at switch-on. 8 digits show Date, Hours, Minutes and Seconds, auto GMT/BST and leap year, also parallel BCD output for computer etc. receives Rugby 60KHz atomic time signals, built-in antenna, 1000km range, GET THE TIME RIGHT, £62.80.

SIG. GEN. 10Hz-200KHz. Logic and 0-1V sine and square wave outputs. £16.80.

Each fun-to-build kit includes all parts, printed circuit, case, instructions, postage etc. money back assurance so GET yours NOW!

CAMBRIDGE KITS
45 (FD) Old School Lane,
Milton, Cambridge

When replying to Classified Advertisements please ensure:

- (A) That you have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

TRANSFORMERS +VAT 15%

UK Postages. Overseas extra.

30 VOLT RANGE (Split Sec)

Sec Voltages available 5, 6, 8, 9, 10, 12, 15, 18, 20, 24, 30V or 12V-0-12V or 15V-0-15V.

Ref.	Amps	Price	P&P
112	3V	2.90	1.00
79	5	3.93	1.00
3	2	4.35	1.20
20	3	7.39	1.44
21	4	8.79	1.60
51	5	10.86	1.60
117	6	12.29	1.72
88	8	16.45	1.96
89	10	18.98	1.84
90	12	21.09	O.A.
91	15	24.18	O.A.
92	20	32.40	O.A.

50 VOLT RANGE (Split Sec) Pri 120V/240V

Sec Voltages available 5, 7, 8, 10, 13, 15, 17, 20, 33, 40 or 20V-0-20V or 25V-0-25V.

Ref.	Amps	Price	P&P
102	5	3.75	1.20
103	7	4.57	1.20
104	8	7.88	1.44
105	3	9.42	1.60
106	4	12.82	1.72
107	6	16.37	1.84
118	8	22.29	2.20
119	10	27.48	O.A.
109	12	32.88	O.A.

MAINS ISOLATORS (SCREENED)

Pri 0-12V, 0-100-120V, (120, 220, 240V) Sec 0-CT-120V twice.

Ref.	VA	Price	P & P
*07	20	4.84	1.20
149	60	7.37	1.20
150	100	8.38	1.44
151	200	12.28	1.72
152	250	14.81	2.04
154	500	22.52	2.20
155	750	32.03	O.A.
156	1000	40.92	O.A.
157	1500	56.52	O.A.
158	2000	67.99	O.A.
159	3000	95.33	O.A.

*Pri 0-240V Sec. 115 or 240V only.
State sec. volts required.

CASED AUTO TRANSFORMERS

240V cable in 115V USA flat pin outlets

VA	Price	P & P
20	6.55	0.95
75	8.50	1.20
150	11.00	1.44
250	13.39	1.44
500	20.13	2.04
1000	30.67	2.20
2000	44.97	O.A.

AUTO TRANSFORMERS

Voltages available: 105, 115, 190, 200, 210, 220, 230, 240, for step up and step down.

Ref.	VA	£	P&P
13	15	2.73	1.00
64	80	4.41	1.20
4	150	5.89	1.20
53	350	10.00	1.44
67	500	12.09	1.84
84	1000	20.64	2.20
93	1500	25.61	O.A.
95	2000	38.31	O.A.
73	3000	65.13	O.A.
80	4000	84.55	O.A.
57	5000	98.45	O.A.

*0, 115, 220, 240.

Constant Voltage Transformers (1%)

Clean mains to computers/peripherals

Ref.	VA	Price	P&P
250	VA	£103.00	
500	VA	£136.40	
1000	VA	£162.20	

Also I.C. "sensing types" for low mains voltage fluctuations.

15V CT Range (7.5V-0-7.5V)

Ref.	VA	Price	P & P
171	500 mA	2.30	0.60
172	1A	3.26	1.00
173	2A	3.95	1.00
174	3A	4.13	1.20
175	4A	6.30	1.20

96/48/36V RANGE

Pri 0-120/240V
 Sec 2 windings 0-36-48V to give 36-0-36V or 48-0-48V or 72V or 96V.

Ref.	VA	Price	P&P
72v/96v	36v/48v	2.30	1.44
2	4	4.32	1.22
3	6	4.33	1.17
4	8	4.34	2.06
5	10	4.35	2.30
6	12	4.36	36.69
8	16	4.37	40.03

SCREENED MINIATURES

Ref	mA	Volts	£	P&P
238	200	3-0-3	2.83	0.50
212	1A	0-6-0-6	3.14	1.00
13	100	9-0-9	2.35	0.50
235	330	30-0-9-9	2.19	0.60
207	500	500-0-8-9-0-8-9	3.05	0.95
208	1A	0-8-9-0-8-9	3.88	1.20
236	200	200-0-15-0-15	2.19	0.60
214	300	300-0-20-0-20	3.08	1.00
221	700	700-12-0-12-20	3.75	1.00
206	1A	0-15-0-15 (x2)	4.99	1.20
203	500	500-0-15-27 (x2)	4.99	1.20
204	1A	0-15-27 (x2)	6.84	1.20
239	50	12-0-12	2.88	0.50
234	500	6-0-6	2.19	0.44

Send 20p stamps for Catalogue. Prices correct 21/4/81. Goods By Return

OTHER PRODUCTS

AVO TEST METERS

Model	Price
AVO 8 Mk5 Latest Model	£122.10
AVO 71 Electronics & TV Service	£45.40
AVO 73	£63.90
AVO MMS Minor	£40.50
AVO EM272 316KΩ/Volt input Z	£67.10
AVO DA116 L.C.D. Digital	£121.70
AVO DA211 L.C.D. Digital (Hand Held)	£58.50
AVO DA212 L.C.D. Digital	£81.90
Battery MEGGER BM7/500V	£65.30
Web MEGGER hand crank	£97.20

Plus P&P £1.32 + VAT 15%
All Avos Meggers & accessories available.

TUMBLER SWITCHES

30 amp 240V 4 pole on-off switch £6.50. P&P 90p+VAT. 16 amp 250V AC/DC 4 pole rotary switch £5.20+90p P&P.

TOROIDAL TRANSFORMERS Now Available

25W Soldering Iron to BS Spec. £1.75 P&P 30p + VAT 15%.

SPECIAL OFFER

25W Soldering Iron to BS Spec. £1.75 P&P 30p + VAT 15%.

PRECISION De-Solder Pumps

Quick action button release for one hand working. Large £5.86 (P&P 35p+VAT). Small £5.17 P&P 30p+VAT. Replacement tips: Small 65p+VAT. Large 86p+VAT.

METAL OXIDE RESISTORS £1 per 100 (Electrosil)

TR4 5% 47Ω/75Ω/180Ω/360Ω/390Ω/430Ω/470Ω/510Ω/560Ω/820Ω/1K/1K1/K2/1K3/1K6/1K8/2K/2K4/3K/16K/20K/22K/24K/47K/82K/100K/110K/120K/130K/180K/220K/270K/300K. P&P 50p+VAT.

100W Soldering Gun includes bulb for spot-on joints

£5.39 + VAT.

PANEL METERS

Model	Price
0-50mA	6.20
0-500mA	6.20
0-1mA	6.20
0-30V	6.20

BRIDGE RECTIFIERS

Model	Price
100V 25A	£1.80
100V 50A	£2.20
200V 2A	£0.52
200V 4A	£0.75
400V 1A	£0.25
400V 4A	£0.98
400V 6A	£1.44

Education metres

2 amp, 10 amp & 30V at £4.50. P&P 66p+VAT. Size 75 x 78mm Scaler.

Barrie Electronics Ltd.

3, THE MINORIES, LONDON EC3N 1BJ
 TELEPHONE: 01-488 3316/7/8
 NEAREST TUBE STATIONS: ALD GATE & LIFFORD ST

INDEX TO ADVERTISERS

Ace Mailtronix	80
Adam Hall Supplies	77
A.D. Electronics	80
Ambit	74
Barrie	78
Bi-Pak	11
Boss Industrial Mouldings	40
British National Radio & Electronics School	9
Cambridge Kits	78
Cambridge Learning	65
C.B. Radio Show	70
Clef Products	74
Crofton Electronics	10, 71
C.R. Supply Co.	76
Dataman Design	80
E.D.A.	29
Electronize Design	40
Electrovalue	72
Gemini	73
Global Specialties Corporation	9
Hameg Limited	69
Home Radio	72
ICS Intertext	4
ILP Electronics	65, 67, 69, 71, 73, 75
L & B Electronics	10
Litesold	72
Maplin Electronics	Cover 4
Marco Trading	70
Marshall A.	73
Microstate Ltd.	76

Midwich Computer	22
Millhill	80
Modern Book Co.	79
Musicraft	70
Northern Amateur Radio Exhibition	75
Parndon	8
Phonosonics	67
Pimac	10
P.K.G. Electronics	77
Powell T.	8
Powertran	Cover 2, 72
Printoid Ltd.	75
Proto Design	78
Radio Component Specialists	79
Radio and T.V. Components	12
Response Company	76
Riscomp Ltd.	8
Service Trading	VIII (Supp.)
Sinclair Research	6, 7
Swanley	70
Technomatic	80, Cover 3
Tempus	38
Titan	71
T.K. Electronics	5
Velleman U.K.	17
Videotone	4
Watford Electronics	2, 3
William Stuart Systems	78
William Stuart Systems (Vibroscope)	77
Wiimslow Audio	8

WORLD RADIO T.V. HANDBOOK

1982 ed. Price: £11.00

AMATEUR RADIO HANDBOOK 1982
by A.R.R.L. Price: £8.00

UNDERSTANDING MICROPROCESSORS
by D. L. Cannon Price: £4.50

PRACTICAL ELECTRONICS H/B
by I. Sinclair Price: £4.35

THE CATHODE-RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett Price: £4.00

INTRODUCING AMATEUR ELECTRONICS
2nd ed. by I. R. Sinclair Price: £4.00

INTRODUCING MICROPROCESSORS
by I. R. Sinclair Price: £5.00

H/B OF BASIC ELECTRONIC TROUBLESHOOTING
by J. D. Lenk Price: £4.65

67 READY TO RUN PROGRAMS IN BASIC: GRAPHICS, HOME & BUSINESS, EDUCATION, GAMES
by Wm. S. Watson Price: £4.60

COMPUTER PROGRAMMING IN BASIC
by P. Bishop Price: £3.50

* ALL PRICES INCLUDE POSTAGE *

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST
of British and American Technical Books

19-21 PRAED STREET
LONDON W2 1NP

Phone 01-402 9176 Closed Saturday 1 p.m.
Please allow 14 days for reply or delivery.

MAIL ORDER ADVERTISING

British Code of Advertising Practice

Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

Mail Order Protection Scheme

If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:

- (1) You have not received the goods or had your money returned; and
- (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.

We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.

This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example, payment made in response to catalogues etc, received as a result of answering such advertisements. Classified advertisements are excluded.

BAKER LOUDSPEAKERS "SPECIAL PRICES" POST £2

Model	Ohms	Inch	Watts	Type	Price
Major	4, 8, 16	12	30	Hi-Fi	£14
Deluxe Mk II	8	12	15	Hi-Fi	£14
Superb	8, 16	12	30	Hi-Fi	£24
Auditorium	8, 16	12	45	Hi-Fi	£22
Auditorium	8, 16	15	60	Hi-Fi	£34
Group 45	4, 8, 16	12	45	PA	£14
Group 75	4, 8, 16	12	75	PA	£22
Group 100	8, 16	12	100	PA	£24
Group 100	8, 16	15	100	PA	£32
Disco 100	8, 16	12	100	Disco	£24
Disco 100	8, 16	15	100	Disco	£32

DE-LUXE DISCO MIXER. 240V, 4 stereo channels, 2 magnetic, 2 ceramic/tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, suitable for panel or desk mounting, attractive grained aluminium fascia, silver knobs. £40. Post £2.

2 CHANNEL STEREO MIXER. 9 volt operated £9.50 p&p £1.

MINI MODULE LOUDSPEAKER KIT
15 x 8jin. 3-way Baffle, 5in. EMI, Bass, 5in. EMI, Middle, 3in. EMI, Tweeter; 3-way Crossover Full assembly instructions supplied. Response 60 to 20,000 c.p.s. 12 watt RMS 8 ohms £10 per kit. Two kits £18.50. Suitable Bookshelf Cabinet £10.50 each. Post £3.

GARRARD 6-200 SINGLE PLAYER DECK
Brushed Aluminium Arm with stereo ceramic cartridge and Diamond Stylus, 3-speeds. Manual and Auto Stop/Start. Large Metal Turntable. £22. Post £2.
Cueing Device and Pause Control.

METAL PLINTH CUT FOR GARRARD
Size: 16 x 14 x 3in. £3.00. Silver or Black finish. Post £2.

B.S.R. SINGLE PLAYER

Battery operated deck. 9 volt D.C. motor. Ceramic stereo cartridge. 'S' shaped arm, cueing device. £20. Post £2.

B.S.R. SINGLE PLAYER P170/2 £20.00

3-speeds 11in. aluminium turntable. "slim" arm, cueing device, stereo ceramic cartridge, silver trim, bias compensator, adjustable stylus pressure, plays all records, spring suspension, 240V AC. Post £2.

B.S.R. DE-LUXE AUTOCHANGER £20

with stereo cartridge, plays all size records. Post £2

DECCA B.S.R. TEAK PLINTH 18½ x 14½ x 4in
Space for small amplifier. Special price £5.95 post paid Ditto with Garrard Board £4.95 post paid.

TINTED PLASTIC COVERS POST £2

Sizes 14½ x 12½ x 3in £5. 17½ x 9½ x 3in £3. 14 x 13 x 3in £5. 18 x 12½ x 3in £6. 16½ x 13 x 4in £6. 17½ x 13½ x 4in £6. 21½ x 14½ x 2½in £6.

R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS £3.95. Post 65p.

All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7½ or 9 or 12V d.c. up to 100mA or less. Please state voltage required.

PP BATTERY ELIMINATOR BRITISH

Mains stabilized power-pack 9 volt 400mA max. with overload cut out. Size 5 x 3½ x 2½in. £4.50. Post 50p. Switched 3 x 6; 7½; 9 volt 400mA Stabilized £7.50. Post £1

MAINS TRANSFORMERS

	Post
250-0-250V 70mA 6-3V, 2A	£4.50 £2
250-0-250 80mA 6 3V, 3 5A, 6 3V 1A	£5.00 £2
350-0-350V 250mA 6-3V 6 amp.	£12.00 £2
300-0-300 120mA 2 x 6-3V 2A C.T., 6 3V 2A	£12.00 £2
220V 45mA, 6-3V 2A	£3.00 £1
250V 60mA, 6-3V 2A	£3.50 £1

GENERAL PURPOSE LOW VOLTAGE

	Post
2A, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 24 and 30V	£6.00 £2
1A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£6.00 £2
2A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£10.50 £2
3A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£12.50 £2
5A, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60	£18.00 £2
TOROIDAL 30-0-30V 4A, 20-0-20V 4A	£10.00 £2

	Post
6V, ½ amps	£2.00 £1
6-0-6V 1½ amps	£3.50 £1
9V 250mA	£1.50 80p
9V 3 amp.	£3.50 £1
9-0-9V 50mA	£1.50 80p
10-30-40V 2 amps	£3.50 £1
12V 3 amps	£3.50 £1
6-0-6V 1½A	£3.50 £1
15-0-15V 2 amps	£3.75 £1
20-0-20V 1 amp	£3.50 £1
20-40-60V 1 amp	£4.00 £2
28V 1 amp twice	£5.00 £2
30V 1½ amp	£3.50 £1
30V 5 amp and	£3.50 £1
17-0-17V 2a	£4.50 £2

AUTO TRANSFORMER 115V to 240V 500W £12.00 £2.00

CHARGER TRANSF.	Post	RECTIFIERS	Post
6-12V-3A	£4.00	6-12V-1A	90p
6-12V-4A	£5.50	6-12V-2A	£1.10
6-12V-6A	£8.50	6-12V-4A	£2.00

BLANK ALUMINIUM CHASSIS. 6 x 4in. £1.45; 8 x 6in. £1.80; 10 x 7in. £2.30; 12 x 8in. £2.60; 14 x 9in. £3.00; 16 x 6in. £2.90; 16 x 10in. £3.20. All 2½in. deep 18 swg.

ANGLE ALL. 6 x ½ x 3in. 18 swg. 25p.

ALUMINIUM PANELS: 18 swg. 6 x 4in. 45p; 8 x 6in. 75p; 14 x 3in. 75p; 10 x 7in. 95p; 12 x 8in. £1.10; 12 x 5in. 75p; 16 x 6in. £1.10; 14 x 9in. £1.45; 12 x 12in. £1.50; 16 x 10in. £1.75.

PLASTIC AND ALL BOXES IN STOCK. MANY SIZES
ALUMINIUM BOXES: 4 x 1½in. £1.4; 2½ x 2½in. £1.3; 2 x 1in. £1.6; 4 x 2in. £1.80; 7 x 5 x 3in. £2.40; 8 x 6 x 3in. £2.50; 10 x 7 x 3in. £3.12; 5 x 3in. £2.75; 12 x 8 x 3in. £3.60. All 18 swg with lids.

HIGH VOLTAGE ELECTROLYTICS

8/450V	45p	8+8/450V	75p	50+50/300V	50p
16/350V	45p	8+16/450V	75p	32+32/500V	£1.80
32/500V	75p	32+32/450V	£1.20	100+100/275V	£5p
50/500V	£1.20	32+32/350V	75p	150+200/275V	70p
8/800V	£1.20	32+32+32/325V	90p	220/450V	85p

HEATING ELEMENTS, WAFER THIN
Size 11 x 9 x ½in. Operating voltage 240V. 250V approx. Suitable for Heating Pads, Food Warmers, Convector Heaters, Propagation, etc. Must be clamped between two sheets of metal, etc. ONLY 60p EACH (FOUR FOR £2) ALL POST PAID.

Radio Component Specialists

337, WHITEHORSE ROAD
CROYDON, SURREY, U.K. TEL: 01-884 1865
Post 65p Minimum. Callers Welcome. Closed Wed.
Phone orders with Access-Barclay-Visa.
Lists 28p Stamps. Same day despatch.

EPROM PROGRAMMER


- 2716 ● HEX KEY PAD
- POWERFUL EDITOR
- 2732 ● TV (MONITOR) DISPLAY
- SERIAL/PARALLEL I/O
- 2532 ● CASSETTE BACK-UP
- ROMULATOR

SOFTY STANDS ALONE

£169+VAT, EX-STOCK, BY RETURN

DATAMAN DESIGNS, LOMBARD HOUSE,
DORCHESTER, DORSET DT1 1RX. (0305) 68066

STORAGE CABINETS

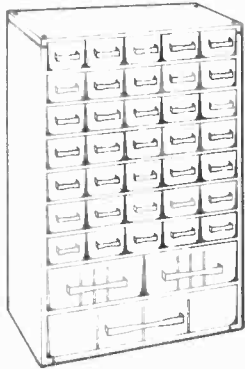

Type 1838

Metal Cabinets 12" wide x 5 3/4" deep, finished blue with transparent plastic drawers.

Type	H (ins)	No. of Drawers	Price	
	Sm	Med	Lge	
1118	11	15	2 1	£10.75
1633	16	30	2 1	£13.95
1838	18	35	2 1	£15.95
2236	22	30	4 2	£18.55
2260	22	60	-	£18.55

Access/Barclaycard welcome
Prices include VAT and Post. Cheque/P.O. to:
Millhill Supplies (Tools),
35 Preston Crowmarsh, Benson,
Oxon OX9 6SL.
Tel: Wallingford (0491) 38653

Goods by return of post.

ALARMS

DIY KITS 'N' BITS

PROFESSIONAL EQUIPMENT AT DISCOUNT PRICES!

- KITS £32, £50, £75, £85 INCLUDING FULL INSTRUCTIONS
- CONTROL PANELS £18, £23, £29, £37 ● BELL BOXES £6.25, £7.50
- PRESSURE PADS £1.06, £1.45, £1.95 ● 4 CORE CABLE (100m) £8.00
- SIRENS £7.50 ● CONTACTS 72p, 74p, 76p ● ULTRASONICS £34.50
- DOOR PHONES £49.42

BUY A KIT OR DESIGN YOUR OWN SYSTEM

SEND S.A.E. OR PHONE NOW FOR **FREE** FULLY ILLUSTRATED CATALOGUE.
IT TELLS YOU ALL YOU NEED TO KNOW!

CARRIAGE INCLUDED. VAT EXTRA 15%
Please allow 14 days for delivery

A.O. ELECTRONICS, 217 WARBECK MOOR, AINTREE, LIVERPOOL L9 0HU. 051 523 8440

TRADE ENQUIRIES WELCOME



ACE MAILTRONIX LTD
Dept. PE, 3A Commercial St.
Bately, W. Yorks. WF17 5HU

THIS MONTH'S SNIP!

NEW 1982 CATALOGUE
for your careful component purchasing

COMPONENTS — Over 1,000 types in stock.

SERVICE — Same day despatch.

QUALITY — All guaranteed products.

"Let us quote for your hard to get components for PE projects"

I enclose 30p please send catalogue

name _____

address _____

TECHNOMATIC TECHNOMATIC TECHNO

★ SPECIAL OFFER ★	1-24	25-99
2114 Low Power 200ns <i>1Kx4</i>	0.90	0.85
4116 200ns <i>16Kx1</i>	0.70	0.65
2716 (+5v)	2.10	2.00
2732 (+5v) <i>2Kx8</i>	4.25	4.00
6116 <i>CMOS</i>	5.50	5.00

CONNECTOR SYSTEM

I.O. CONNECTORS			25 WAY MINI D-CONNECTORS			DIL HEADER PLUGS			
HEADER	RECEP.	EDGE CABLES	Solder	Solder	Solder	Solder	IDC	IDC	
PLUG	TACLE	CONN	Bucket	Pin	Pin	(angled)	type	type	
10 Way	220p	160p	—	200p	215p	265p	14 pin	50p	130p
26 Way	350p	285p	390p	240p	255p	310p	16 pin	60p	140p
34 Way	450p	325p	450p	280p	—	—	24 pin	100p	200p
40 Way	525p	370p	—	330p	—	—	40 pin	275p	285p
50 Way	575p	450p	—	—	—	—	100p. Locking Lever	100p.	—

JUMPER LEADS				EDGE CONNECTOR		EURO CONNECTORS		
24" Ribbon Cable with headers				0.1"	0.156"	DIN STD	PLUG	SKT
14 pin	16 pin	24 pin	40 pin	2-18 Way	150p	41617 31 Way	200p	200p
145p	165p	240p	380p	2-22 Way	310p	41612 2x32 Way	300p	350p
210p	230p	345p	540p	2-23 Way	335p	2x32 Way (angled)	350p	400p
Cable with Sockets				2-25 Way	350p	41612 3x32 Way	370p	420p
20 pin	25 pin	34 pin	40 pin	1-43 Way	260p	3x32 Way (angled)	450p	—
160p	210p	270p	300p	2-43 Way	450p	(for 2x32 way please specify a-b or a+c)		
290p	385p	490p	540p	2-50 Way	—	400p	—	—
—	—	—	—	1-77 Way	700p	—	—	—

BOOKS (NO VAT) (P&P £1.00 per book)

The Pascal Handbook	£10.05	TTL Cookbook	£7.15
CRT Controller Handbook	£5.95	CMOS Cookbook	£7.95
Understanding Microprocessors	£3.50	T1 TTL Data Book	£7.50
Micros - Interfacing Techniques	£12.10	Video Cookbook	£5.95
Introduction to Micro Computers	£10.95	Z-80 Interfacing (1)	£7.95
6502 Assy. Lang. Prog.	£12.10	Z-80 Interfacing (2)	£9.75
8080A/8085 Assy. Lang. Prog.	£11.80	Prog. the Z80	£11.50
—	—	Prog. the 6502	£10.25
—	—	6502 Applications	£10.25

Please add £1.00 P&P per book

ADD SOUND - ★ ZX80/81 USER PORT ★

(As described in Oct/Nov PCW)

Port module plugs directly into ZX80/81 to provide 8 input and 8 output lines. These allow input of data from switches, photocells, sensors, joysticks etc and control of 8 relays. Also 7 segment displays and LED may be used - "VARIABLE TONE AUDIO OUTPUT CAN PRODUCE YOUR OWN SOUND EFFECTS." Port access is by simple PEEK & POKE COMMANDS. Kit £11.50.

READY BUILT AND TESTED UNIT £14.95 + 70p P&P

Reprint of PCW Oct/Nov. articles £1 + large SAE.

For ZX81 users: Extender cord provided i.o.c. to enable to be plugged directly.

EXPERIMENT WITH COMPUTER VISION

★ ATOM ULTRASONIC VISION ★

Module connects to the ATOM printer port to give an ultrasonic radar picture of the surroundings, eg. room, furnishings, people. Experiment with computer measurement, image recognition, movement tracking, robot vision. See this month's PRACTICAL ELECTRONICS.

★ UK101: INTERFACING SYSTEM ★

Two board interface system plugs directly into computer expansion socket to provide wide facilities accessible from BASIC or MACHINE CODE.

- 1) DECODING MODULE:** Providing a dual 5v supply, 16 bit programmable i/o port, plus extensive address decoding for a wide variety of interfaces, including full decoding for a programmable sound generator, and also a 40 pin skt for further expansion.
- 2) ANALOGUE BOARD:** Plugs into the decoding module to provide D/A converter, 8 channel multiplexed A/D converter with 20ns conversion time, AY3-8910 SOUND GENERATOR plus 6522 VIA provide complex timing & counting functions and additional 16 bit port.

DECODING MODULE KIT £27.50 ANALOGUE BOARD £39.95
P&P 0.75p/Kit

ACORN ATOM

A personal computer with full size QWERTY board and a built in UHF modulator to allow direct connection to domestic TV. A simple to build, simple to operate computer with all the features found in machines twice the price but with the advantage of expandability. Basic ATOM has 2K RAM and 8K ROM and on board expansion capability up to 12K + 12K. Basic built £135, Built & Fully Expanded £185, P&P £3. 4K Floating Point ROM £20, 1K RAM (2 x 2114!) £2. NEW 3A 5V Regulated Power Supply £22 + £1.50 P&P.

ATOM CONNECTORS	PLUG	SOCKET	ATOM SOFTWARE	£10 each
2x32 Way	£3.00	£4.00	Games Pack 1-10	£10 each
28 Way	£2.00	£2.00	Fr. Machine, Breakout, UFO Bomber,	£3.50 each
10 Way	£1.20	£1.20	Disassembler	£25.00
—	—	—	Prog. Tool Box ROM	—

Suitable high quality printers available soon, watch for details. Send SAE for ATOM memory expansion system
13K RAM or 64K ORAM.

BOOKS: Getting Acquainted with ATOM £7.95; ATOM Business £7.00; ATOM Magic Book £5.95.

UV EPROM ERASERS

UV18 (upto 6 EPROMS)	£42.00
UV140 (upto 14 EPROMS)	£61.50
UV141 (as UV140 but with timer)	£78.00

ALL ERASERS with built in safety devices.

SOFTY


ROM PROGRAMMER & ROMULATOR
Software development tool
MKII (for 2516/2716/2532/2732) Built complete
with psu £189.00 + £2 p&P

TECHNOMATIC TECHNOMATIC TECHNO

COMPUTER COMPONENTS



TTLS 7400 11p 74398 55p 7401 11p 74399 100p 7402 12p 74490 120p 7403 12p 74LS00 11p 7404 18p 74LS01 12p 7405 25p 74LS02 12p 7407 25p 74LS03 12p 7408 14p 74LS04 15p 7409 15p 74LS08 14p 7410 14p 74LS09 15p 7411 20p 74LS10 15p 7412 20p 74LS11 15p 7413 22p 74LS12 15p 7414 32p 74LS13 25p 7416 25p 74LS14 40p 7420 16p 74LS15 30p 7421 20p 74LS20 15p 7422 22p 74LS21 15p 7423 22p 74LS22 15p 7426 27p 74LS27 16p 7427 27p 74LS28 16p 7428 28p 74LS30 14p 7430 15p 74LS32 14p 7432 25p 74LS37 16p 7433 27p 74LS38 16p 7437 27p 74LS42 36p 7438 27p 74LS44 40p 7440 17p 74LS48 80p 7441 30p 74LS51 15p 7442A 76p 74LS55 30p 7446 60p 74LS73 25p 7447A 45p 74LS74 16p 7450 17p 74LS75 24p 7451 17p 74LS76 20p 7453 17p 74LS85 55p 7454 17p 74LS86 55p 7472 30p 74LS90 28p 7474 20p 74LS92 40p 7476 30p 74LS93 40p 7478A 45p 74LS96 100p 7485 60p 74LS107 45p 7486 210p 74LS109 30p 7490A 25p 74LS112 34p 7491 45p 74LS113 30p 7492A 30p 74LS114 30p 7493A 30p 74LS122 42p 7494 40p 74LS123 50p 7495A 45p 74LS124 20p 7496 50p 74LS125 30p 7497 120p 74LS126 30p 74100 85p 74LS133 30p 74107 22p 74LS136 30p 74109 30p 74LS138 34p 74116 60p 74LS139 36p 74118 75p 74LS145 75p 74119 90p 74LS147 90p 74120 70p 74LS148 90p 74121 27p 74LS151 30p 74122 45p 74LS152 40p 74123 45p 74LS153 40p 74125 40p 74LS154 90p 74126 40p 74LS155 40p 74128 40p 74LS157 35p 74132 30p 74LS158 36p 74136 32p 74LS160 40p 74141 60p 74LS161 40p 74142 200p 74LS162 40p 74148 75p 74LS165 100p 74150 60p 74LS166 90p 74151A 45p 74LS170 90p 74154 60p 74LS173 75p 74155 50p 74LS175 50p 74156 50p 74LS181 140p 74157 50p 74LS190 50p 74160 60p 74LS191 50p 74161 60p 74LS193 48p 74162 60p 74LS194 40p 74163 60p 74LS195 50p 74166 55p 74LS196 60p 74165 55p 74LS197 65p 74170 140p 74LS240 80p 74172 300p 74LS241 80p 74173 65p 74LS242 80p 74175 60p 74LS243 80p 74176 50p 74LS244 65p 74177 70p 74LS251 40p 74178 100p 74LS253 40p 74180 60p 74LS257 45p 74181 30p 74LS258 40p 74182A 90p 74LS260 24p 74184 90p 74LS266 25p 74186 500p 74LS273 70p 74188 325p 74LS279 45p 74191 50p 74LS280 250p 74192 50p 74LS293 50p 74193 50p 74LS298 160p 74195 60p 74LS299 400p 74196 60p 74LS323 250p 74197 60p 74LS324 180p 74198 100p 74LS352 100p 74221 60p 74LS353 100p 74259 150p 74LS363 160p 74278 150p 74LS364 160p 74279 80p 74LS365 32p 74283 75p 74LS368 50p 74284 200p 74LS373 70p 74285 200p 74LS374 70p 74293 100p 74LS375 50p 74298 100p 74LS378 50p 74365 40p 74LS390 55p 74366 40p 74LS393 60p 74367 40p 74LS399 200p		74LS545 110p 74LS540 135p 74LS541 135p 74LS564 200p 74LS564 200p 74LS564 250p 74LS568 200p 74LS569 200p 74LS570 170p 74S01 40p 74S02 60p 74S04 60p 74S05 75p 74S08 60p 74S10 60p 74S11 60p 74S12 60p 74S13 60p 74S14 40p 74S15 30p 74S16 30p 74S20 60p 74S21 60p 74S22 60p 74S26 90p 74S27 90p 74S28 90p 74S30 40p 74S32 40p 74S37 90p 74S38 90p 74S42 30p 74S44 30p 74S48 75p 74S51 75p 74S55 30p 74S73 225p 74S74 16p 74S75 24p 74S76 20p 74S85 55p 74S86 55p 74S90 28p 74S92 40p 74S93 40p 74S96 100p 74S107 45p 74S109 30p 74S112 34p 74S113 30p 74S114 30p 74S122 42p 74S123 50p 74S124 20p 74S125 30p 74S126 30p 74S133 30p 74S136 30p 74S138 34p 74S139 36p 74S145 75p 74S147 90p 74S148 90p 74S151 30p 74S152 40p 74S153 40p 74S154 90p 74S155 40p 74S157 35p 74S158 36p 74S160 40p 74S161 40p 74S162 40p 74S165 100p 74S166 90p 74S170 90p 74S173 75p 74S175 50p 74S181 140p 74S190 50p 74S191 50p 74S193 48p 74S194 40p 74S195 50p 74S196 60p 74S197 65p 74S240 80p 74S241 80p 74S242 80p 74S243 80p 74S244 65p 74S251 40p 74S253 40p 74S257 45p 74S258 40p 74S260 24p 74S266 25p 74S273 70p 74S279 45p 74S280 250p 74S293 50p 74S298 160p 74S299 400p 74S323 250p 74S324 180p 74S352 100p 74S353 100p 74S363 160p 74S364 160p 74S365 32p 74S368 50p 74S373 70p 74S374 70p 74S375 50p 74S378 50p 74S390 55p 74S393 60p 74S399 200p		4000 CMOS 4000 12p 4001 14p 4002 15p 4006 65p 4007 65p 4008 60p 4009 30p 4010 30p 4011 14p 4012 16p 4013 35p 4014 60p 4015 60p 4016 30p 4017 45p 4018 60p 4019 32p 4020 60p 4021 65p 4022 60p 4023 18p 4024 36p 4025 20p 4026 130p 4027 30p 4028 60p 4029 75p 4030 40p 4031 170p 4032 170p 4033 180p 4034 160p 4035 80p 4036 295p 4037 120p 4038 120p 4039 55p 4040 55p 4041 70p 4042 55p 4043 60p 4044 70p 4045 70p 4046 70p 4047 75p 4048 55p 4049 27p 4050 27p 4051 80p 4052 80p 4053 60p 4054 130p 4055 125p 4056 120p 4057 120p 4058 90p 4059 90p 4060 100p 4061 35p 4062 400p 4063 40p 4064 16p 4065 16p 4066 16p 4067 16p 4068 16p 4069 16p 4070 16p 4071 16p 4072 16p 4073 16p 4074 16p 4075 16p 4076 60p 4077 28p 4078 20p 4079 16p 4080 72p 4081 40p 4082 40p 4083 150p 4084 95p 4085 95p 4086 340p 4087 90p 4088 90p 4089 90p 4090 90p 4091 150p 4092 95p 4093 95p 4094 95p 4095 95p 4096 95p 4097 340p 4098 90p 4099 90p 4100 150p 4101 150p 4102 150p 4103 180p 4104 120p 4105 45p 4106 150p 4107 150p 4108 28p 4109 70p 4110 50p 4111 75p 4112 35p 4113 60p 4114 60p 4115 60p 4199 60p 4200 60p		LINEAR I.C.s AN103 200p AY1-0212 600p AY1-1313 668p AY1-1320 600p AY1-5050 140p AY3-8910 700p AY3-8912 650p AY5-1224A 240p AY5-1315 600p AY5-4007D 520p CA3086 75p CA3019 80p CA3046 70p CA3048 225p CA3059 300p CA3080E 75p CA3086 75p CA3089E 225p CA3090AQ 375p CA3130E 70p CA3102 50p CA3160E 100p CA3161E 190p CA3162E 450p CA3189E 300p CA3240E 120p CA3280G 200p DAC1408-8 200p HA1386 300p HA1388 270p ICL7106 850p ICL8038 800p ICL7120 350p ICL7130 350p ICL7347 100p LF551 48p LF553 100p LF566P 95p LF357 120p LM101C 40p LM301A 20p LM311 75p LM318 15p LM319 225p LM324 100p LM335Z 120p LM339 60p LM348 75p LM358P 75p LM377 175p LM380 100p LM381AN 180p LM382 120p LM386 95p LM387 120p LM389 95p LM393 100p LM394 100p LM709 36p LM710 50p LM711 100p LM725 35p LM733 100p LM747 70p LM748 35p LM1871 375p LM1872 375p LM1886 700p LM1889 50p LM2917 200p LM3302 140p LM3900 55p LM3909 55p LM3911 130p LM3914 210p LM3915 225p LM3916 125p LM5151L 300p M51516L 500p		MB3712 250p MC1310P 150p MC1458 40p MC1495L 350p MC1496 70p MC330P 120p MC3401 90p MC3403 120p OK50398 750p ML920 800p MM57160 600p NE567 140p NE555 80p NE566 50p NE567 425p NE570 425p NE571 425p NE574 425p PCL02A 500p RC4156 200p RC4157 200p RC4158 200p RC4159 200p RC4160 200p RC4161 200p RC4162 200p RC4163 200p RC4164 200p RC4165 200p RC4166 200p RC4167 200p RC4168 200p RC4169 200p RC4170 200p RC4171 200p RC4172 200p RC4173 200p RC4174 200p RC4175 200p RC4176 200p RC4177 200p RC4178 200p RC4179 200p RC4180 200p RC4181 200p RC4182 200p RC4183 200p RC4184 200p RC4185 200p RC4186 200p RC4187 200p RC4188 200p RC4189 200p RC4190 200p RC4191 200p RC4192 200p RC4193 200p RC4194 200p RC4195 200p RC4196 200p RC4197 200p RC4198 200p RC4199 200p RC4200 200p		CPU's 1802CE 750p 2650A £12 6502 450p 6502A 450p 6800 600p 6802 425p 6809 801 8009E £15 8035 750p 8039 850p 8080A 350p 8085A 550p 93210 4164.2 93211 5101 93212 6116P.3 93213 6514.45 93214 6810 93215 7489 93216 7489.189 93217 74S201 93218 74S289 93219 93415 93220 93425		MEMORIES 2101A 400p 2102-3L 120p 21078 500p 2111A 300p 2112 A 300p 2114 2L 160p 2114 4L 650p 2147 450p 4027 3 300p 4118 20 200p 4118 3 500p 4118 4 450p 4164 2 650p 5101 300p 6116P.3 900p 6514.45 300p 6810 200p 7489 210p 7489.189 300p 74S201 350p 74S289 325p 93415 600p 93425 600p		INTERFACE IC's AD558CJ 775p AD561J £14 AM25S10 350p AM26LS31 160p AM26LS32 190p COMB113 800p DAC08V 400p DM8131 375p DPR304 450p DS8833 225p DS8832 225p LF13201 450p MC1488 55p MC1489 55p MC3418 950p MC3446 300p MC3480 850p MC3486 500p MC3492 325p MC4044 325p MC14411 £7 MC14412 £12 MM58174 £9 ULN2003A 100p ULN2004A 100p 75107 160p 75110 160p 75112 160p 75114 160p 75115 160p 75150P 350p 75154 140p 75182 230p 75189 160p 75190P 160p 75457.4 72p 75453/4 72p 75491/2 70p 82T6 120p 82T8 120p 8T95 120p 8T97 120p 81LS95 90p 81LS96 90p 81LS97 90p 81LS98 90p 9602 220p 9637AP 160p ZN425E-8 350p ZN426E-8 350p ZN427E-8 650p ZN428E-8 500p		CRYSTALS 32 768kHz 100p 100kHz 300p 200kHz 370p 1.0MHz 320p 1.008MHz 350p 1.8432MHz 250p 2.0MHz 300p 2.45760MHz 250p 2.5MHz 250p 3.276MHz 150p 3.5795MHz 100p 3.686MHz 300p 4.00MHz 150p 4.194MHz 250p 4.43MHz 125p 5.0MHz 175p 6.0MHz 150p 6.144MHz 150p 7.0MHz 150p 7.168MHz 200p 8.00MHz 175p 8.86MHz 175p 10.00MHz 175p 10.7MHz 250p 12.0MHz 250p 13.0MHz 350p 14.3168MHz 150p 16.00MHz 250p 18.00MHz 250p 18.432MHz 350p 19.968MHz 300p 20.00MHz 175p 24.0MHz 350p 26.690MHz 250p 27.145MHz 300p 38.667MHz 350p 48.0MHz 400p 55.5MHz 400p 115MHz 350p		SUPPORT DEVICES 3242 800p 3245 450p 3522 500p 6532 775p 6551 650p 6821 160p 6845 110p 6847 110p 6850 170p 6852 300p 6875 600p 8154 950p 8155 800p 8205 320p 8212 800p 8216 180p 8224 220p 8226 250p 8228 250p 8243 450p 8244 450p 8251 350p 8253 350p 8255 300p 8256 300p 8257 800p 8259 800p 9279 95p TMS9927 £18 Z80PI0 300p Z80PAI0 350p Z80CCT 300p Z80ACT 350p Z80ADART 300p Z80ADM 800p Z80S10-1 £14		ROMS/PROM's 74S188 325p 74S287 300p 74S288 225p 74S387 325p 74S471 650p 74S473 850p 74S474 650p 74S470 650p 74S573 950p 75385 150p 75386 150p 75453/4 72p 75491/2 70p 82T6 120p 82T8 120p 8T95 120p 8T97 120p 81LS95 90p 81LS96 90p 81LS97 90p 81LS98 90p 9602 220p 9637AP 160p ZN425E-8 350p ZN426E-8 350p ZN427E-8 650p ZN428E-8 500p		CHARACTER GENERATORS	
---	--	--	--	---	--	---	--	--	--	--	--	---	--	--	--	--	--	---	--	---	--	-----------------------------	--

EXPRESS from MAPLIN

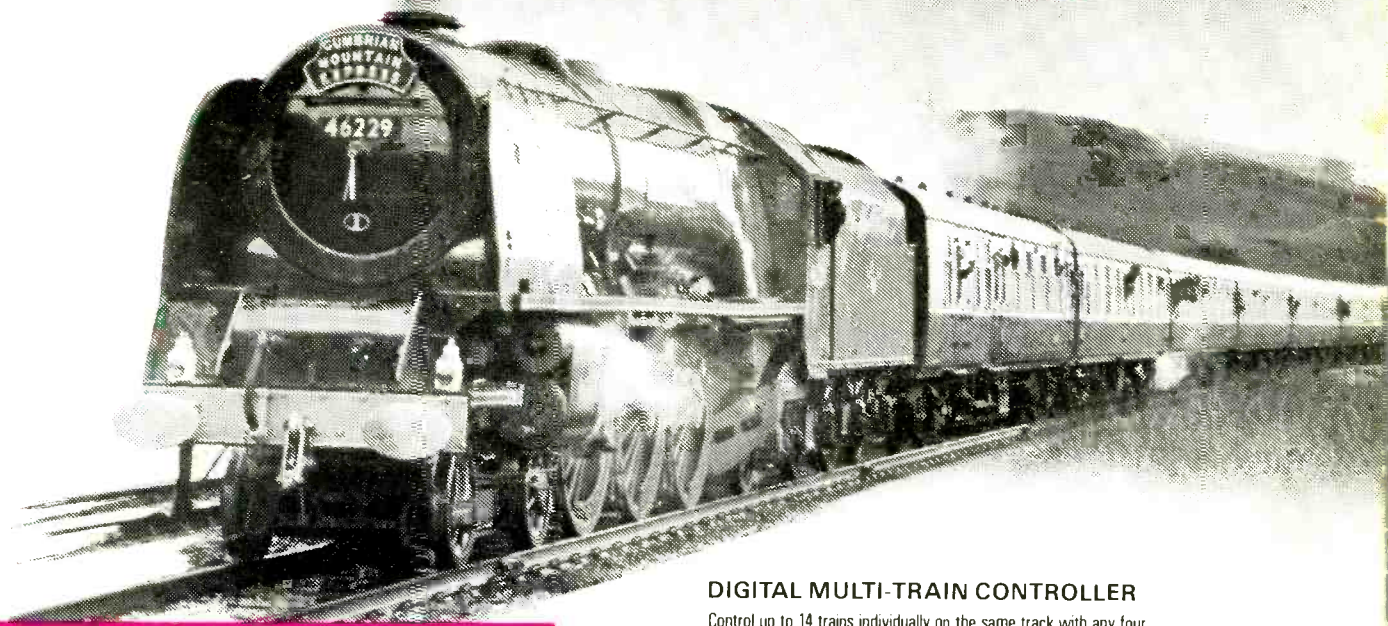

COMBO-AMPLIFIER

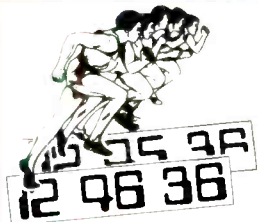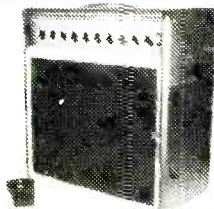Easy to build portable 120W MOSFET amp for all stage musicians. Built-in flanger, five step equaliser, two inputs for guitars, keyboards or microphones, low-noise pre-amp.
Full details in our book. Price 60p.
Order As XA01B.



STOP-WATCH

Multi-mode 8-digit stopwatch accurate to hundredths of a second. Easy to build - complete kits available.
Full details in our projects book.
Price 60p.
Order As XA02C.

MILES PER GALLON METER

Digital display shows you how economical your driving is as you go along.
Complete kits available.
Full details in our projects book.
Price 60p.
Order As XA02C.



DIGITAL MULTI-TRAIN CONTROLLER

Control up to 14 trains individually on the same track with any four simultaneously! Low cost kits available.
Full details in our projects book. Price 60p.
Order As XA02C.

Photo by W. A. Sharma n




HOME SECURITY SYSTEM

Six independent channels - 2 or 4 wire operation. External horn. High degree of protection and long term reliability.
Full details in our projects book.
Price 60p.
Order As XA02C.

MATINÉE ORGAN

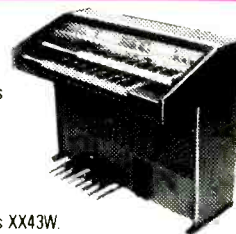Easy-to-build, superb specification. Comparable with organs selling for up to £1,000. Full construction details in our book. Price £2.50.
Order As XH55K.
Complete kits available:
Electronics - £299.95,
Cabinet - £99.50 (carriage extra).
Demo cassette price £1.99. Order As XX43W.



- * Don't miss out - get a copy of our catalogue now!
Over 140,000 copies sold already!
- * On sale now in all branches of WHSMITH price £1.
- * 320 big pages packed with data and pictures of over 5,500 items



Post this coupon now!

Please send me a copy of your 320 page catalogue. I enclose £1.25 (inc. 25p p&rp). If I am not completely satisfied I may return the catalogue to you and have my money refunded.
If you live outside the U.K. send £1.68 or 12 International Reply Coupons.

Name _____
Address _____

PE482

MAPLIN ELECTRONIC SUPPLIES LTD.

All mail to:

P.O. Box 3, Rayleigh, Essex SS6 8LR

Tel: Sales (0702) 552911 General (0702) 554155

Shops at:

159 King St., Hammersmith, London W6. Tel: 01-748 0926

284 London Rd., Westcliff-on-Sea, Essex. Tel: (0702) 554000

Note: Shops closed Mondays