

603

Australia \$1.50 New Zealand \$1.60 Malaysia \$4.95 IR £1.30 (inc. VAT)


PRACTICAL

# ELECTRONICS

SEPTEMBER 1983

90p

## A MORE RELIABLE MEMORY...

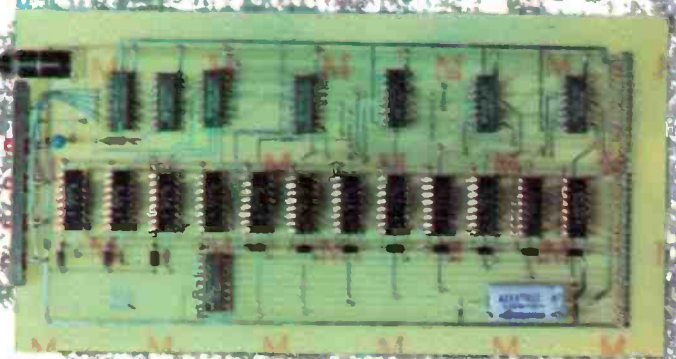

### Computer Soft Error Correction Board



## GUITAR ACTIVE TONE CONTROLS

## UK SATELLITE TV SYSTEM Explained

### Used Computer and Test Gear Bargains

# SAVE ON THE PRICE OF YOUR COLOUR PRINTS!

**NOW ONLY 12p EACH**

## with the Practical Electronics Colour Print Service

While prices go up elsewhere, Practical Electronics makes a bargain offer in its Colour Print Service. Now you can have as many films printed as you like, including Giant Superprints, at only 12p a print. There is no developing charge and just 25p towards postage and packing.

At this new price, the magazine Colour Print Service, already used by hundreds of thousands of readers, is as fast and efficient as ever. Here's all you have to do to enjoy its advantages.

Send any make of colour print film, including disc film, inside the envelope enclosed with this issue. Or fill in the coupon below and send with your colour print film in a strong envelope to: **Practical Electronics Colour Print Service, FREEPOST, READING RG1 1BR. No stamp is required.**

### SEND NO MONEY

We are so confident in the reliability of our service and the quality of our prints (each one date-stamped with the month and year of developing) that you don't pay until you've seen them.

### LUXURY COLOUR PRINTS

You will be amazed at the beautiful colours and sheen finish of these prints. They have elegant rounded corners and are borderless to give you maximum picture area. And with the Giant Superprints, you get 30 per cent more picture area than the standard enprints at no extra cost!

*Offer excludes Black & White, transparency, sub-miniature, C22 & Agfa CNS film. Superprints can only be produced from Kodacolor II, C41 cassette, cartridge and disc film not half frame. Prices correct at time of going to press.*

### UNBEATABLE VALUE

All you pay for the Colour Print Service is 12p for each good print received plus 25p towards postage and packing. The most you would pay us for processing and printing a 24-exposure film for example is £3.13. Compare that with the price you would pay in the shops.

### FREE ALBUM PAGES

With each film we process, you receive an album page voucher. Collect and return three vouchers, and you receive a set of FREE album pages to fit into our specially designed album for any size of print up to 4in. by 6in.

### HOW YOU BENEFIT


You benefit in three ways. Firstly, you pay nothing for the actual processing—only for prints and postage and packing. Secondly, you enjoy a personal service with every care taken over each individual order. And thirdly, you pay only for what you get—with no credit vouchers as with many other companies. An invoice comes with your prints, so it is a straight business transaction.

### 48 HOURS IN-LAB SERVICE

Your films will be processed within 48 hours\* of receipt, but please allow for postal delays.


The price of this offer is limited to the U.K.

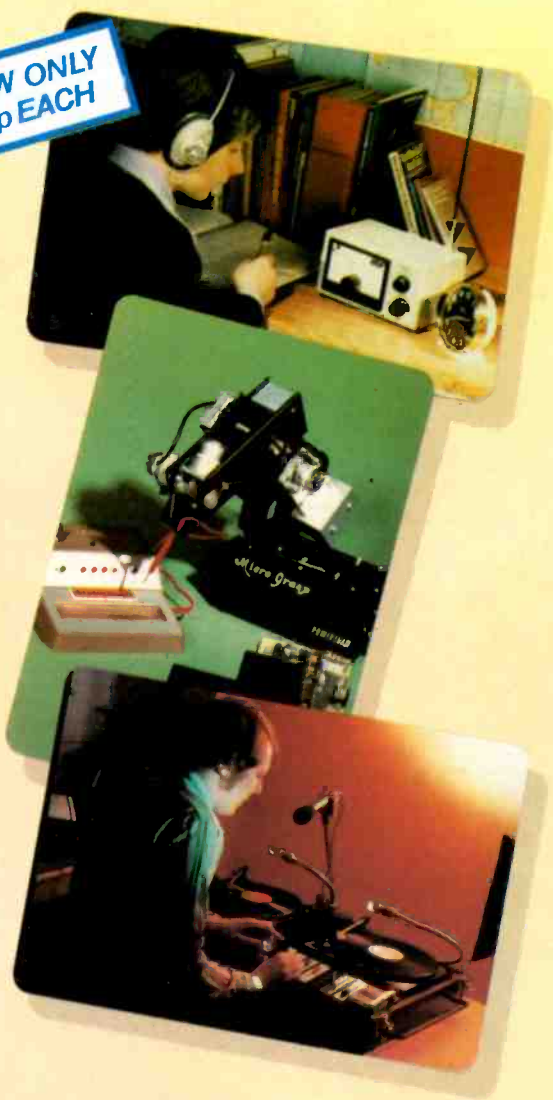\*C41 Process cassette and cartridge film only.


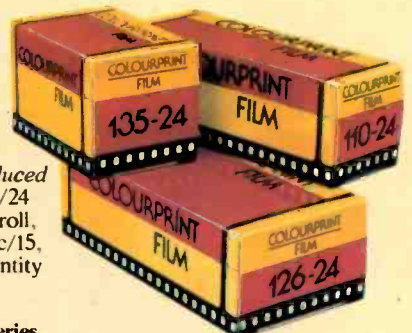
### FILMS AT REDUCED PRICES

Always keep your camera action-ready. Order replacement films at our specially reduced prices: 110/24, 126/24 or 35/24 at £1.20 a roll, or three for £3; disc/15, £1.30 each (no quantity discount).



**If you have any queries, contact our Customer Service on Reading (0734) 597332.**

Use this label if you have no envelope, or pass it to a friend. It is used to pack your prints.

To: Practical Electronics Colour Print Service  
FREEPOST, Reading RG1 1BR

- Please print my film Superprint size
- Standard Enprint size

If film is being ordered ● Please send me \_\_\_\_\_  
of 110/24  of 126/24  of 35/24  of disc/15

- Tick box(es) as required.

From: Practical Electronics Colour Print Service  
FREEPOST, READING RG1 1BR

Mr/Ms \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

Postcode \_\_\_\_\_

# PRACTICAL ELECTRONICS

VOLUME 19

No. 9

SEPTEMBER 1983

## CONSTRUCTIONAL PROJECTS

<b>555/741 TESTER</b> by <i>Stephen Ibbs</i> .. .. .	22
Function tester for two well known devices	
<b>SOFT ERROR DETECTION AND CORRECTION BOARD</b> by <i>A. Trebar</i> .. .. .	32
A more reliable memory system for your computer	
<b>GUITAR ACTIVE TONE CONTROL</b> by <i>A. Scragg</i> .. .. .	39
Provides crisper sound and larger tonal range	
<b>GROUND COMMUNICATION SYSTEM</b> by <i>R. A. Penfold</i> .. .. .	42
A battery operated transceiver for subterranean communications	
<b>LOGIC ANALYSER Part 2</b> by <i>D. Mandelzweig</i> .. .. .	52
Construction details	

## GENERAL FEATURES

<b>VERNON TRENT AT LARGE</b> .. .. .	24
<b>SEMICONDUCTOR CIRCUITS</b> by <i>Tom Gaskell BA (Hons)</i> .. .. .	26
Light spot driver (UAA170)	
<b>GETTING TO GRIPS WITH MAC</b> by <i>Pat Hawker</i> .. .. .	46
UK TV satellite system explained	
<b>INGENUITY UNLIMITED</b> .. .. .	62
Proportional a.c. control without RFI—General purpose timer—Over voltage protection— Pseudo telephone ringer—Automatic ni-cad charger—Sound chaser—Slide projector dimmer—Intruder alarm with camera unit—Shop bell delay	
<b>MICRO-BUS</b> by <i>DJD</i> .. .. .	70
A bi-monthly focus on micro's for the home constructor	

## NEWS AND COMMENT

<b>EDITORIAL</b> .. .. .	15
<b>NEWS AND MARKET PLACE</b> .. .. .	16
Including countdown	
<b>BAZAAR—USED COMPUTER AND EQUIPMENT BARGAINS</b> .. .. .	28, 60
Free readers' advertisements	
<b>INDUSTRY NOTEBOOK</b> by <i>Nexus</i> .. .. .	31
News and views on the electronics industry	
<b>SPACEWATCH</b> by <i>Frank W. Hyde</i> .. .. .	61
Extra-terrestrial activities chronicled	
<b>OVERSEAS SUBSCRIPTION AGENTS</b> .. .. .	66
<b>PATENTS REVIEW</b> .. .. .	69
Power-cut reserve—Sound switch—Wide screen TV	

## SPECIAL SUPPLEMENT

<b>MICRO-FILE</b> by <i>R. W. Coles</i> .. .. .	between pages 38 and 39
Filesheet 10 Z8000	

OUR OCTOBER ISSUE WILL BE ON SALE FRIDAY, SEPTEMBER 2nd, 1983  
(for details of contents see page 10/6 of Micro-file)

© IPC Magazines Limited 1983. Copyright in all drawings, photographs and articles published in PRACTICAL ELECTRONICS is fully protected, and reproduction or imitations in whole or part are expressly forbidden. All reasonable precautions are taken by PRACTICAL ELECTRONICS to ensure that the advice and data given to readers are reliable. We cannot, however, guarantee it, and we cannot accept legal responsibility for it. Prices quoted are those current as we go to press.





# Technical Training in Radio, Television and Electronics

ICS have helped thousands of ambitious people to move up into higher paid, more secure jobs in the field of electronics—now it can be your turn. Whether you are a newcomer to the field or already working in the industry, ICS can provide you with the specialised training so essential to success.

## Personal Tuition and Guaranteed Success

The expert and personal guidance by fully qualified tutors, backed by the ICS guarantee of tuition until successful is the key to our outstanding record in the technical training field. You study at the time and pace that suits you best and in your own home. In the words of one of our many successful students: "Since starting my course, my salary has trebled and I am expecting a further increase when my course is completed".

## CITY AND GUILDS CERTIFICATES

Excellent job prospects await those who hold one of these recognised certificates. ICS can coach you for:

Basic Electronic Engineering (C&G/ICS)  
Radio Amateurs

## CERTIFICATE COURSES

TV & Audio Servicing  
TV, Radio and Audio Engineering  
Radio & Amplifier Construction  
Electronic Engineering\*  
Computer Electronics\*  
Industrial Electronics\*  
Radio Frequency Electronics\*  
Electrical Engineering\*  
Electrical Contracting & Installation

\*Qualify for IET Associate Membership



Approved by CACC

**ICS**

Div. National Education Corporation



Member of ABCC

## POST OR PHONE TODAY FOR FREE BOOKLET

Please send me your FREE School of Electronics Prospectus.

Subject of Interest \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_


**ICS**  
Dept L273  
ICS School of Electronics  
160 Stewarts Road  
London SW8 4UJ



01-622 9911  
(All Hours)

Remember our low-cost mobile robot?

## ZEAKER MICRO-TURTLE

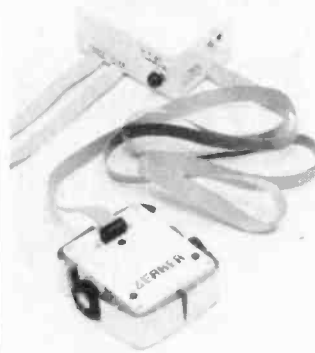

- Compact and rugged mobile robot, 5½ x 5 x 2" with two DC motor drive.
- Can be driven direct from the BBC micro and, using the special interfaces available, from ZX81 and Spectrum (can be adapted for use with other micros).
- Touch sensors register collisions so the robot can take avoiding action.
- Specially-written software includes learning program. Currently available for ZX81/Spectrum and BBC (others to follow).
- Computer-controlled, retractable pen lets ZEAKER trace its path. Logo software now available for Spectrum.
- LEDs and two-tone horn under computer control.
- 2 meter umbilical cable linking the robot to its control station/power supply. Requires 4 x 1.2 volt Nicad C-cells (not included in price).
- Available as a kit or assembled, at prices unmatched by any other turtle! Includes umbilical cable, control station and manual. (All software, and interfaces for ZX81/Spectrum extra).

**COLNE ROBOTICS Co. Ltd.**

BEAUFORT RD., OFF RICHMOND RD., EAST TWICKENHAM TW1 2PH

## ORIC AND SINCLAIR COMPUTERS




Oric 1 48K computer £147 (£158). Oric 1 16K n/a (n/a). Sinclair Spectrum 48K £113 (£133). Spectrum 16K £86.91 (£107). 32K memory upgrade kit for 16K Spectrum (Issue 2 only) £26.09 (£28). Fuller master unit for the Spectrum including speech synthesizer, sound synthesizer, amplifier and joystick ports £47.78 (£56). ZX microdrive n/a (n/a). ZX rs232 n/a (n/a). Keyboards with space bars for the ZX81 and the Spectrum £36 (£41). ZX printer £34.74 (£50). 5 printer rolls £10.43 (£16). ZX81 £43.43 (£52). ZX81 16K ram packs £26.04 (£28). New luxury spectrum computers 48K with full sized typewriter keyboards complete with normal space bar enclosed in a larger plastic case which also houses the power supply and the computer pcb £138.20 (£174).

## OTHER COMPUTERS

Colour Gentle £168 (£178). BBC Model B £424 (£440). Texas T199/4A £139 (£169). Atari 800 £347 (£380). Atari 400 16K with basic £173 (£215).

## PRINTERS

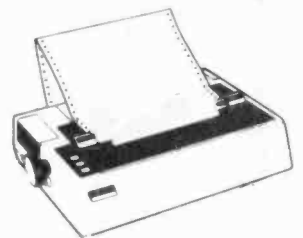

New Epson RX80 £279 (£309). The Epson MX80FT/3 has been replaced by the almost identical CTI CP80 £251 (£271) and the very similar Star DP510 £251 (£271). Epson FX80 £378 (£408). Epson MX100/3 £425 (£465). New Star DP515 15" carriage printer £346 (£386). Seikosha GP100A £199 (£219). Oki Microline 80 £207 (£227). Oki Microline 82A £360 (£400). Oki Microline 84 £730. Oki Microline 92 £470. The Silver Reed, the latest miracle, a combined daisy wheel printer and electric typewriter for only £385 (£425). Juki 6100 proportional daisy wheel printer £364 (£404). MCP 40 colour printer £139 (£159). Star STX 80 thermal printer £139 (£159). We can supply interfaces to run all the above from Sharp Computers.

## COMMODORE COMPUTERS

Commodore 64 £299 (£309). Special offer package: Vic 20 + cassette recorder + basic course + 4 games £121 (£149). Converter to allow the use of most ordinary mono cassette recorders with the Vic 20 and the Commodore 64 built £8 (£9), kit £6 (£7). Commodore cassette recorder £36.50 (£44). We stock most accessories.

## SWANLEY ELECTRONICS

Dept PE, 32 Goldsel Rd., Swanley, Kent BR8 8EZ, England.



Please allow 7 days for delivery.

UK prices are shown first. UK customers must add postage (£1 on Sinclair products, £3.50 on other computers and disc drives and £4.50 on other printers) and the 15% VAT. The bracketed prices are European export prices and include insured airmail postage to all the countries of Europe including Norway, Sweden, Finland, Denmark, Spain and Italy. No VAT should be added to export prices. We are the leading computer export specialist. Official UK credit orders welcome from government laboratories and educational establishments.

Step-by-step fully illustrated assembly and fitting instructions are included together with circuit descriptions. Highest quality components are used throughout.
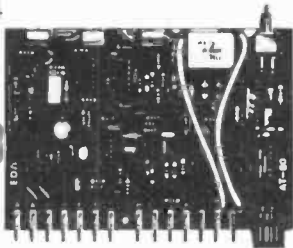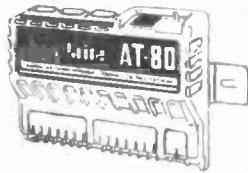
# Sparkrite

BRANDEADING ELECTRONICS  
NOW AVAILABLE IN KIT FORM





## AT-80 Electronic Car Security System

- Arms doors, boot, bonnet and has security loop to protect fog/spot lamps, radio/tape, CB equipment
- Programmable personal code entry system
- Armed and disarmed from outside vehicle using a special magnetic key fob against a windscreen sensor pad adhered to the inside of the screen
- Fits all 12V neg earth vehicles
- Over 250 components to assemble
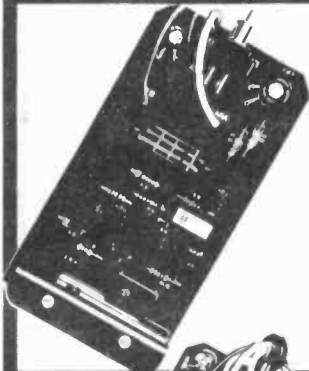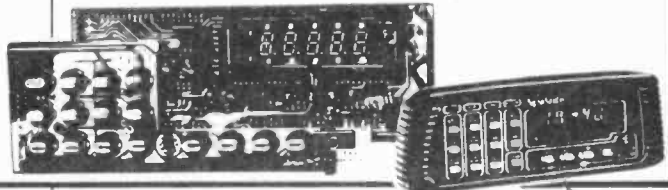
## VOYAGER Car Drive Computer

- A most sophisticated accessory
  - Utilises a single chip mask programmed microprocessor incorporating a unique programme designed by EDA Sparkrite Ltd
  - Affords 12 functions centred on Fuel, Speed, Distance and Time
  - Visual and Audible alarms warning of Excess Speed, Frost/Ice, Lights-left-on
  - Facility to operate LOG and TRIP functions independently or synchronously
  - Large 10mm high 400ft-L fluorescent display with auto intensity
  - Unique speed and fuel transducers giving a programmed accuracy of + or - 1%
  - Large LOG & TRIP memories 2,000 miles, 180 gallons, 100 hours
  - Full Imperial and Metric calibrations
  - Over 300 components to assemble
- A real challenge for the electronics enthusiasts!




## SX1000 Electronic Ignition

- Inductive Discharge
- Extended coil energy storage circuit
- Contact breaker driven
- Three position changeover switch
- Over 65 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg earth vehicles

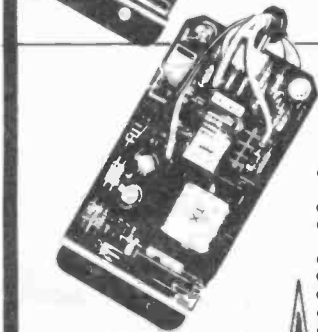
## TX1002 Electronic Ignition

- Contactless or contact triggered
- Extended coil energy storage circuit
- Inductive Discharge
- Three position changeover switch
- Distributor triggerhead adaptors included
- Die cast weatherproof case
- Clip-to-coil or remote mounting facility
- Fits majority of 4 & 6 cyl. 12V. neg. earth vehicles
- Over 145 components to assemble


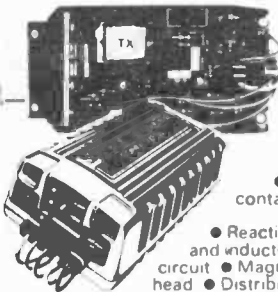
## SX2000 Electronic Ignition

- The brandleading system on the market today
- Unique Reactive Discharge
- Combined Inductive and Capacitive Discharge
- Contact breaker driven
- Three position changeover switch
- Over 130 components to assemble
- Patented clip-to-coil fitting
- Fits all 12v neg earth vehicles




## TX2002 Electronic Ignition

- The ultimate system
- Switchable contactless
- Three position switch with Auxiliary back-up inductive circuit
- Reactive Discharge
- Combined capacitive and inductive
- Extended coil energy storage circuit
- Magnetic contactless distributor triggerhead
- Distributor triggerhead adaptors included
- Can also be triggered by existing contact breakers
- Die cast waterproof case with clip-to-coil fitting
- Fits majority of 4 and 6 cylinder 12v neg earth vehicles
- Over 150 components to assemble

All SPARKRITE products and designs are fully covered by one or more World Patents
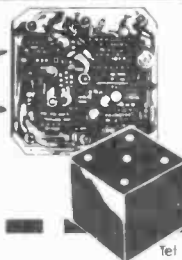
## SPECIAL OFFER

"FREE" MAGIDICE KIT WITH ALL ORDERS OVER £45.00



## MAGIDICE Electronic Dice

- Not an auto item but great fun for the family
- Total random selection
- Triggered by waving of hand over dice
- Bleeps and flashes during a 4 second tumble sequence
- Throw displayed for 10 seconds
- Auto display of last throw 1 second in 5
- Muting and Off switch on base
- Hours of continuous use from PP7 battery
- Over 100 components to assemble

SPARKRITE, 82 Bath Street, Walsall, West Midlands, WS1 3DE England.

SPARKRITE, 82 Bath St., Walsall, W. Midlands WS1 3DE

Tel (0922) 614791 Allow 28 days for delivery

	SELF ASSEMBLY KIT
SX 1000	£12.95
SX 2000	£19.95
TX 1002	£22.95
TX 2002	£32.95
AT 80	£32.95
VOYAGER	£84.95
MAGIDICE	£9.95

PRICES INC VAT POSTAGE & PACKING

NAME \_\_\_\_\_ PE.9.83

ADDRESS \_\_\_\_\_

I ENCLOSE CHEQUE(S)/POSTAL ORDERS FOR

£ \_\_\_\_\_ KIT REF \_\_\_\_\_

CHEQUE NO \_\_\_\_\_

PHONE YOUR ORDER WITH   
SEND ONLY SAE IF BROCHURE IS REQUIRED

BRANDEADING BRITISH ELECTRONICS  
CUT OUT THE COUPON NOW!

Where on Earth can I obtain  
top quality Transistors, Ic's,  
Capacitors, Resistors, Cases,  
Cable, Fuses, Bulbs, Plugs,  
Sockets, Nuts, Bolts, Coils,  
Chokes, Test Instruments &  
Books, all at a price I can  
afford ?



But of  
Course !!!

Express  
Mail  
Order  
Service

Callers  
Most  
Welcome

# Twyford

ELECTRONICS LIMITED

22 STATION ROAD, TWYFORD, near READING, BERKS.

Telephone 0734 340333

We  
accept

Send large S.A.E.  
for your  
CATALOGUE  
PRICE 25P

## CLEF ELECTRONIC MUSIC

### MICROSYNTH


2½ Octave Music Synthesizer with two Oscillators, two Sub-Oct's, Switched Routing and Thumbwheel. A comprehensive instrument offering the full range of Synth. Music & effects, FULL KIT £137 Also available in 3 parts.



(Published in P.E.)
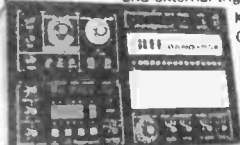
### PERCUSSION MICROSYNTH

Two Channel touch Sensitive unit plus variable angle L.F.O., phaser, internal and external triggering.



KIT £89  
CABINET  
£32  
(Published  
in P.E.)

### BAND-BOX PROGRAMMABLE BACKING TRIO

THREE PIECE BACKING BAND  
Generates the sounds of three Instrumentalists to back Soloists

### DRUMS + BASS + KEYBOARDS

Over 3,000 chord changes (60 scores) on 132 different chords - extendable to 200 scores. Master Rhythm also required.

FULL KIT £235 EXTENSION £82

(Published in P.E.)

### 88/72 NOTE PIANOS SPECIALISTS SINCE 1972

Using Patented electronic technique to give advanced simulation of Piano Key Inertia.



#### COMPONENT KITS

including Keyboard  
88 NOTE £266  
72 NOTE £234

The above may also be purchased in four parts.

#### DOMESTIC KITS

inc. Cabinet, P.A., & Spkr.  
88 NOTE £442  
72 NOTE £398

#### STAGE MODEL

inc. Cabinet & Stand  
72 NOTE £383

ALL PRICES INC. VAT. CARR. & TELEPHONE ADVICE S.A.E. for full Specs & MANF. PRICES. VISA-ACCESS Competitive quotations can be given for export. Please allow 3-14 days for normal despatch.

CLEF PRODUCTS (ELECTRONICS) LIMITED

(Dept PE)

44A BRAMHALL LANE SOUTH BRAMHALL  
STOCKPORT CHESHIRE SK7 1AH  
TEL 061 439 3297



### MASTER RHYTHM PROGRAMMABLE DRUMS

Twenty-Four Rhythm programmable Drum Machine with twelve instruments. Eight sections are extended to 24/32 measures for two bar programming. Sequence operation and instrument tone adjust.

COMPLETE KIT £79

STRING ENSEMBLE £198.50

ROTOR-CHORUS £98.00

SQUARE FRONT KEYBOARDS

88 NOTE £60 49 NOTE £29

73 NOTE £50 30 NOTE £19

KEYSWITCH ITEMS ALSO AVAILABLE

# ALARMS

FREE CATALOGUE!

OUR GREAT NEW ILLUSTRATED CATALOGUE IS PACKED WITH INFORMATION ON SUPERB QUALITY, PROFESSIONAL BURGLAR ALARM EQUIPMENT



AT UNBEATABLE PRICES!



SEND SAE OR PHONE NOW FOR YOUR COPY

A.D. ELECTRONICS  
DEPT. PE  
217 WARBECK MOOR  
AINTREE LIVERPOOL  
L19 0HU/051 523 8440



THIEFCHECK BURGLAR  
ALARM D-I-Y SYSTEM



MAIN  
DISTRIBUTOR

## Modem Kit Only £39.95

- \* CCITT standard
- \* 300 baud full duplex
- \* Direct connection:- greatly reduces data loss associated with acoustic couplers
- \* Powered from phone lines therefore no power supply required
- \* Opto coupled data in and data out for intrinsically safe operation

Build it yourself for £39.95 including VAT and postage (note - case not included).

Racom Ltd, Dept. C,  
81 Cholmeley Road, Reading, Berks RG1 3LY  
Tel: 0734 67027





# SUPERKITS!

## NOW WITH NEW CHOICE OF CASES

BOXES SUPPLIED WITH STANDARD UNITS ARE PLAIN ALUMINIUM WITH A LIPPED LID. THE 'BLK' UNITS HAVE ALUMINIUM BOXES WITH STEEL TOP COVERED IN STYLISH BLACK STELVITITE LAMINATE. UNITS MARKED WITH \* DO NOT INCLUDE BOXES (FURTHER DETAILS IN LIST).

SETS INCL PCBs, ELECTRONIC PARTS, INSTRUCTIONS. MOST ALSO INCL. KNOBS, SKTS, WIRE, SOLDER, BATTERIES NOT INCL. BUT MOST WILL RUN FROM 9V TO 15V DC SUPPLIES. FOR FULLER DETAILS SEE CATALOGUE (SEE BELOW).

	STD UNIT	BLK UNIT
<b>AUTOWAH:</b> Guitar-triggered wah-wah	SET 58	£14.01 £16.41
<b>BASS BOOST:</b> Increases volume of lower octaves	SET 138-B	£9.40 £11.80
<b>CALL SIGN:</b> Programmable 8-note musical call sign	SET 121	£14.23 £16.23
<b>CHORUS UNIT:</b> A solo voice or instr. sounds like more!	SET 162	£31.59 £34.49
<b>COMPARATOR:</b> LED level indicator for 2 channels	SET 129	£16.73 £18.73
<b>COMPRESSOR:</b> Limits & levels maximum signal strength	SET 133	£12.37 £14.77
<b>ECHO UNIT:</b> With double tracking	SET 168	£44.82 £47.72
<b>FREQUENCY DOUBLER:</b> Raises guitar frequency by 1 octave	SET 98	£11.75 £13.75
<b>FREQUENCY GENERATOR:</b> Multiple waveform test osc	SET 128	£19.15 £22.05
<b>FUNKY-WOBULO:</b> Novelty voice modulator for funny effects	SET 149	£12.78 £14.78
<b>FLANGER:</b> Fascinating delayed-feed-back effects plus phasing	SET 153	£22.54 £25.44
<b>FUZZ:</b> Smooth distortion whilst keeping natural attack & decay	SET 91	£11.68 £14.08
<b>GUITAR EFFECTS:</b> Multiple variation of level & filter modulation	SET 42	£16.58 £18.38
<b>GUITAR OVERDRIVE:</b> Fuzz plus variable filter quality	SET 56	£21.17 £24.07
<b>GUITAR SUSTAIN:</b> Extends effective note duration	SET 75	£11.77 £14.17
<b>HARMONOLA:</b> Versatile 3 octave organ*	SET 125-T	£166.97 —
<b>HUM CUT:</b> Tunable filter for reducing low frequency noise	SET 141	£12.02 £14.42
<b>JABBERVOX:</b> Voice disguiser with reverb & tremolo	SET 150	£23.64 £25.44
<b>MAD-ROJ:</b> Variable sirens, incl. police, galaxy machine-guns etc	SET 146	£10.47 £12.47
<b>METRONOME:</b> With audible & visual beat & down-beat marking	SET 143	£13.98 £15.98
<b>MICROPHONE PRE-AMP:</b> with switchable bass & treble response	SET 144	£9.12 £11.52
<b>MINISONIC (PE) MK2:</b> 3-octave very versatile music synthesiser*	SET 38	£181.92 —
<b>MIXERS:</b> Several - details in catalogue (see below)	SET 145	£10.59 £12.99
<b>NOISE LIMITER:</b> reduces tape & system hiss	SET 164	£21.20 £24.10
<b>PHASER:</b> with automatic & manual rate & depth controls	SET 122	£20.39 £22.19
<b>REVERB:</b> Analogue unit with variable delay & depth controls	SET 170	£38.27 £41.17
<b>RHYTHM GENERATOR:</b> 15 switchable rhythms (NEW UNIT)	SET 87	£13.62 £15.42
<b>RING MODULATOR:</b> for intermodulating 2 separate sine freqs.	SET 165	£21.89 £24.79
<b>ROBO BOX:</b> Versatile Robot type voice modifier	SET 126-LS	£12.55 £14.55
<b>ROGER 2-GONG:</b> 2 gongs sounded at end of transmission	SET 127-LS	£10.07 £12.47
<b>ROGER BLEEP:</b> Single bleep sounded at end of transmission	SET 117	£21.81 £23.61
<b>SCRAMBLER:</b> Codes & decodes transmissions authorised chans	SET 76	£110.99 £114.59
<b>SEQUENCERS:</b> 128-note keyboard controlled (keyboard incl.) 16 note (up to 64-bit pattern) panel controlled	SET 86	£53.15 £56.95
<b>SPEECH PROCESSOR:</b> for clearer transmission	SET 110	£12.10 £14.50
<b>STORM EFFECTS:</b> Automatic & manual wind, rain & surf	SET 154	£16.72 £19.62
<b>SWEEP GENERATOR:</b> Audio test unit	SET 169	£16.42 £18.22
<b>SYNTHESISER INTERFACE:</b> allows instrument to trigger synth	SET 81	£9.59 £11.99
<b>TREMULO:</b> Deep tremolo with depth & rate controls	SET 136	£10.71 £13.11
<b>TREBLE BOOST:</b> Increases volume of upper octaves	SET 138-T	£9.24 £11.64
<b>tone CONTROL:</b> bass & treble cut, gain & range (6 controls)	SET 139	£13.82 £16.72
<b>VIBRATO:</b> variable rate & depth plus additional phasing	SET 137	£23.99 £26.79
<b>VOCODAVOX:</b> Modular Vocoder	SET 152	£68.96 £72.76
<b>VODALEK:</b> Robot type voice modulator with depth & rate controls	SET 155	£12.75 £14.75
<b>VOICE FILTER:</b> tunable for selected freq bandwidth & gain	SET 142	£10.21 £12.61
<b>VOICE-OP-FAOER:</b> for reduction of music level during talk-over	SET 30	£10.02 £12.42
<b>VOICE-OP-SWITCH:</b> with variable sensitivity & delay	SET 123-LS	£13.80 £15.80
<b>WAH-WAH:</b> with auto-trigger, manual & oscillator control	SET 140	£17.31 £20.21
<b>WHEEBY—JEEBY:</b> 2 Intercoupled oscillators produce variable sirens	SET 151	£13.78 £15.58
<b>WIND &amp; RAIN:</b> manual control of these two effects	SET 28	£11.39 £13.79
<b>WOBBLE-WAH:</b> Oscillator controlled wah-wah	SET 161	£13.40 £15.40
<b>KIMBER ALLEN KEYBOARDS (surely the best?):</b>	3-Oct £32.43, 4-Oct £40.68, 5-Oct £48.52	
<b>KEYBOARD CONTACTS GJ (SPCD):</b>	3-Oct £20.29, 4-Oct £26.50, 5-Oct £32.71	
<b>KEYBOARD CONTACTS GB (DPST):</b>	3-Oct £23.27, 4-Oct £30.45, 5-Oct £37.62	

# PHONOSONICS

PHONOSONICS MAIL DROR, DEPT PE38, 22 HIGH STREET, SIDCUP, KENT DA14 6EH.  
01-302 6184

Please use full address. Payment CWO, CHQ, PO, Access, Barclay, or pre-arranged collection. Prices incl UK P&P & 15% VAT. E&OE. Despatch usually 10-14 days on most items. For comprehensive catalogue send S.A.E. (if you live overseas send £1.00 or equiv.). MORE KITS ARE IN CATALOGUE.



# MONITORS

IT'S A BETTER BUY THAN MOST AT LESS THAN £4 PER MHZ.

THE PRICE IS AS CRISP AS THE IMAGE. ORDER TODAY - WE'LL SHIP RIGHT AWAY. All major Credit Cards accepted.

Phone for details of cased and open frame monitors.

## CROFTON ELECTRONICS LTD.

35 GROSVENOR ROAD, TWICKENHAM, MIDDX O1-891 1923/1513 Telex 295093

### PARNDON ELECTRONICS LTD.

Dept. PE2 44 Paddock Mead, Harlow, Essex. CM18 7RR. Tel: 0279 32700

**RESISTORS:** 1/2 Watt Carbon Film E24 range ± 5% tolerance. High quality resistors made under strictly controlled conditions by automatic machines. Banded and colour coded.  
£1.00 per hundred mixed (Min 10 per value)  
£8.50 per thousand mixed (Min 50 per value)  
Special stock pack 60 values. 10 of each £5.50

**VOLUME DISCOUNTS AVAILABLE**

7106-CMOS 3 1/2 Digit A/D Converter  
£6.50 LCD Drive & Backplane Drive  
AND-0.5" 3 1/2 Digit LCD Display  
£3.50 includes colon ±

SPECIAL OFFER - BUY BOTH FOR £8.95

Full List Available - Send SAE

ALL PRICES INCLUDE V.A.T. & POST & PACKING - NO EXTRAS  
MIN ORDER - UK £1.00 OVERSEAS £5 CASH WITH ORDER PLEASE  
Same Day Despatch

## BECOME A RADIO AMATEUR

Train now for the Radio Amateur Licence examination. No previous knowledge needed, only a few hours per week of home study for 3 to 6 months. Post coupon now for details or tel. 0734 51515 (24 hr service)



British National Radio & Electronics School Reading, Berks. RG1 1BR

FREE brochure without obligation from:—  
**British National Radio & Electronics School**  
READING, BERKS. RG1 1BR

Name .....

Address .....

PE/9/846

BLOCK CAPS PLEASE



CALL IN AND SEE FOR YOURSELF

# AUDIO ELECTRONICS

ALL PRICES INCLUDE VAT

TEST EQUIPMENT CENTRES ALL MODELS ON DISPLAY OPEN SIX DAYS A WEEK

RETAIL • MAIL ORDER • EXPORT • INDUSTRIAL • EDUCATIONAL

## DIGITAL MULTIMETERS (UK C/P Free)



ALL MODELS 3½ DIGIT UNLESS STATED

- |   |                        |  |                  |
|---|------------------------|--|------------------|
| <b>HAND HELD</b>  | • With free carry case | <b>Beckman T110 As T100 plus Cont. test.</b> |                  |
| K025C=13 range 0.2A DC 2 meg ohm                            | £24.95                 | etc.   | £67.85           |
| K030S=16 range 10A DC 2 meg ohm                             | £29.95                 | <b>Sifam 2200B 21 range 2A AC/DC</b>         |                  |
| K030C=26 range 1A AC/DC 20 meg ohm                          | £34.95                 | 20 meg ohm                                   | £39.95           |
| K055C=28 range 10A AC/DC 20 meg ohm                         | £39.95                 | +Optional carry case £2.95                   |                  |
| 601D=28 range 10A AC/DC 20 meg ohm                          | £34.40                 | <b>BENCH MODELS</b>                          |                  |
| 703D=As 6010 but 0.1% basic                                 | £41.30                 | TM353=27 range LCD 2A AC/DC                  | £86.25           |
| K0615=16 range 10A DC 2 meg plus Hie tester                 | £39.95                 | TM355=29 range LCD 10A AC/DC                 | £86.25           |
| 189M 30 range 10A AC/DC 20 meg plus Hie tester              | £69.95                 | TM351=29 range LCD 10A AC/DC                 | £113.15          |
| <b>HD30 16 range 0.2A AC/DC 2 meg ohm</b>                   | £41.95                 | • Optional carry case £6.84                  |                  |
| <b>HD30/8 As Above plus cont. buzzer</b>                    | £44.50                 | *2001 28 range LCD 10A AC/DC plus 5 range    |                  |
| <b>HD31 22 range 10A AC/DC 2 meg ohms plus cont. buzzer</b> | £58.95                 | Cap. Meter with case                         | £108.00          |
| <b>DM2350 = 21 range 10A AC/DC 20 meg ohm</b>               | £49.95                 | TM 451 4½ digit LCD every facility 10 00% of | £171.00          |
| miniature hand held auto range                              |                        | 1503A 4½ digit LCD every facility 10 00% of  | £171.00          |
| <b>Beckman T100 34 range 10A AC/DC 20 meg ohm</b>           | £56.35                 | 1503Ma 0.03% basic version of above          | £189.00          |
|   |                        | 1504 true RMS version                        | £201.25          |
|   |                        | Sifam 2500 24 range LCD 2A AC/DC             | £99.95           |
|   |                        | Metrix (ITT) professional 3½ - 4½ digit      |                  |
|   |                        | OMM's standard & true RMS 4 models stocked   | £77.00 - £201.25 |

## FREQUENCY COUNTERS



- |   |         |
|---|---------|
| <b>PFM200A</b> MHz hand held pocket 8 digit LED     | £77.60  |
| <b>B110A</b> 8 digit LED bench 2 ranges 100 MHz     | £77.00  |
| <b>8510B</b> 9 digit LED bench 2 ranges 800 MHz     | £113.85 |
| <b>8000B</b> 9 digit LED 3 ranges 1 GHz             | £178.00 |
| <b>TF040</b> = 8 digit LCD 40 MHz                   | £126.50 |
| <b>TF200</b> = 8 digit LCD 200 MHz                  | £166.75 |
| • Optional carry case £6.84                         |         |
| <b>Prescalars</b> - Extended range of most counters |         |
| <b>TP600</b> 600 MHz                                | £43.00  |
| <b>TP1000</b> 1 GHz                                 | £74.00  |

## SIGNAL GENERATORS (220/240V AC)



- |  |  |         |
|--|--|---------|
| <b>FUNCTION</b> : All sine/square/triangle/TTL etc | <b>TG100</b> 1 Hz - 100 KHz                  | £90.00  |
|  | <b>TG102</b> 0.2 Hz - 2 MHz                  | £166.75 |
| <b>PULSE</b>                                       | <b>TG105</b> Various facilities 5 Hz - 5 MHz | £97.75  |
| <b>AUDIO</b> : Multiband Sine/Square               | <b>LAG27</b> 10 Hz to 1 MHz                  | £90.85  |
|  | <b>AG20A</b> 20 Hz to 200 KHz (List £94.50)  | £83.50  |
|  | <b>RF</b>                                    |         |
|  | <b>SG402</b> 100 KHz to 30 MHz (List £79.50) | £69.50  |
|  | <b>LSG17</b> 100 KHz to 150 MHz              | £79.35  |

## ELECTRONIC INSULATION TESTER

- |  |        |
|--|--------|
| <b>YF 501</b> 500 V/0-100m with carry case | £63.00 |
|--|--------|

## MULTIMETERS (UK C/P £65p)

- |   |        |
|---|--------|
| <b>HM102Z</b> 20K/V 10A DC 22 range & cont. buzzer              | £13.50 |
| <b>HM102Z</b> 20K/V   |        |
| 22 range & cont buzzer  | £14.95 |
| <b>ETS5000/5001</b> 21 ranges, 50K/V                            | £18.95 |
| Range doubler 10A DC  | £18.95 |
| <b>TKM500</b> 23 ranges 30K/V, 12A DC plus cont. buzzer         | £24.75 |
| <b>NH56R</b> 20K/V, 22 range pocket                             | £10.95 |
| <b>ETU102</b> 14 range 2K/V pocket                              | £6.50  |
| <b>830A</b> 26 range 30K/V, 10A AC/DC overload protection, etc. | £23.95 |
| <b>360TR</b> 23 range 100K/V, Large scale 10A AC/DC plus Hie    | £39.95 |
| <b>AT1020</b> 18 range 20K/V, Deluxe plus Hie tester            | £18.95 |
| <b>YN 360TR</b> 19 range 20K/V plus Hie tester                  | £15.95 |
| Metrix Professional multimeters<br>In stock 3 models from       | £74.75 |

## VARIABLE POWER SUPPLIES (UK C/P £1.00)

- |  |        |
|--|--------|
| <b>PP241</b> 0/12/24V, 0/1A            | £35.00 |
| <b>PP243</b> 3 amp version             | £59.95 |
| <b>PS 1307S</b> 8/15V 7 amp twin meter | £24.95 |

## DIGITAL THERMOMETER

- |  |        |
|--|--------|
| <b>TM301</b> LCD -50°C to +750°C with thermocouple | £68.43 |
|--|--------|

## AC CLAMP METER

- |   |        |
|---|--------|
| <b>ST300</b> 0/300A/0/600 VAC, 0/1 Kohm 9 ranges<br>With carry case (UK C/P £65p) | £28.50 |
|---|--------|

## LOGIC PROBES

- |   |        |
|---|--------|
| <b>LP10</b> 10 MHz                                  | £28.50 |
| <b>DLPS0</b> 50 MHz with carry case and accessories | £52.33 |

## AUDIO ELECTRONICS

301 EDGWARE ROAD, LONDON W2 1BN. TEL: 01-724 3564  
ALSO AT HENRYS RADIO,  
404/406 EDGWARE ROAD, LONDON, W2. TEL: 01-724 0323  
HENRY'S COMPONENT SHOP. TEL: 01-723 1008

Cubegate Limited

Order by Post with CHEQUES/ACCESSES  
We'll let you know responsive prior order  
All orders dispatched within 5 days unless otherwise stated

## KITS & PCB'S FOR P.E. PROJECTS

Full Kits including PCB's, Hardware and Cases (unless listed separately), I.C. Sockets, Veropins, Wire, Nuts & Bolts all included.

Reprints 45p extra.

Program Conditioner June 83	£16.98	Battery Tester April 83	£12.55
Automobile Test Set May 83	£32.56	Wiper Delay April 83 (Less Relay)	£7.44
Mains Watchdog May 83	£14.47	Car Audio Booster (Stereo) Jan 83 (Less Case)	£18.98
Personal Stereo Amplifier May 83 (Less case and transformer)	£26.98	Decast Case extra	£4.75
Switched Capacitance Phaser April 82	£20.48	Frost/Overheating Warning Jan 83	£6.20

## PCB'S Top quality printed Circuit Boards made from P.E. masters glass fibre board, roller trimmed & drilled.

M.W. Radio Aug. 83	£2.46	Digital Frequency Meter	£3.73
Soil Moisture Meter Aug. 83	£1.34	Car Accessory P.S.U. March 83	£1.53
Thermometer Aug. 83	£1.58	Car Radio Booster Feb. 83	£1.74
Inebnation detector Aug. 83	£1.83	Digital Tacho Jan. 83 (3)	£4.80
Continuity tester Aug. 83	£1.57	Car Audio Booster Jan. 83	£3.25
Transistor checker Aug. 83	£2.32	Stylochord Dec. 82 (3)	£7.49
2 Digit Down Counter July 83	£2.27	Mini Chorus Unit Oct. 82	£2.85
4 Digit LCD Up Counter July 83 (2)	£4.88	Audio Debug Probe Sept. 82	£1.58
4 Digit LED Down Counter July 83 (3)	£3.83	Combo Amp (Main) Aug. 82	£3.45
4 Digit LCD Down Counter July 83 (3)	£7.68	Combo Amp (Preamp) Aug. 82	£3.62
Program Conditioner June 83	£1.89	Audio Test Set July 82	£6.38
Automobile Test Set June 83	£3.47	Instrument Tuner July 82 (2)	£3.61
Mains Watchdog May 83	£2.07	Versatile Car Alarm July 82 (2)	£3.65
Personal Stereo Amp May 83	£4.54	Burglar Deterrent July 82	£2.74
Battery Tester April 83	£1.95	Prescaler + Freq. Meter May 82 (3)	£2.80
Wiper Delay April 83	£2.08	Function Generator May 82	£3.58
Switched Capacitor Phaser April 83	£2.26		

## MORE KITS AND COMPONENTS IN OUR LISTS

FREE PRICE LIST  
Price list included with orders or send sae (9 x 4)  
CONTAINS LOTS MORE KITS, PCBs & COMPONENTS

## ELECTRONICS CATALOGUE

Illustrations, product descriptions, circuits all included. Up-to-date price list enclosed. All products are stock lines for fast delivery. Send 80p in stamps or add 80p to order. Free to Schools/Colleges requested on official letterhead. Normal despatch by return of post.

## MAGENTA ELECTRONICS LTD

Magenta Electronics Ltd.  
PC13, 135 Hunter St.,  
Burton on Trent,  
Staffs. DE14 2ST  
MAIL ORDER ONLY  
0283 65435, Mon-Fri 9-5.  
Access/Barclaycard (VISA) by phone or post.

Add 45p P&P to all orders  
Prices include VAT.  
SAE all enquiries  
Official orders welcome  
OVERSEAS: Payment must be in sterling.  
IRISH REPUBLIC AND BFPO, UK PRICES.  
EUROPE: UK Prices plus 10%.  
ELSEWHERE: Write for Quote.

## PE CAR COMPUTER



"One of the neatest, most comprehensive and most useful of these car computers that we have yet come across...  
★ Economy - save petrol by improving your driving technique and improving the tuning of your car.  
★ Performance - dynamic checks on timing to improve performance and economy.  
★ Security - protect your car by disabling the ignition. Enter a personalized combination to restart.  
★ Attractive, easy to fit, easy to operate - comes complete with all parts needed. Full instructions provided.  
★ Imperial or metric read outs.  
PE car computer £88.50  
Easy-to-assemble kit of parts £78.50  
Ignition cut-out £7.75  
All prices include VAT. Allow £1 post & package. Goods by return. Send S.A.E. for list of separately available parts.

## PIMAC SYSTEMS LTD

20 Bloomfield Road, Moseley, Birmingham B13 9BY.  
Tel: 021-449 0384

## BUY NOW WHILE STOCKS LAST!

TRANSFORMERS		British made transformers at very attractive prices.			
		Primary	Secondary	Current	1+ 10+ 100+
		240v:	4.5-0-4.5v	400m/a	50p 45p 35p
		240v:	6-0-6v	100m/a	58p 52p 43p
		240v:	6-0-6v	500m/a	65p 60p 48p

(Postage & Packing: 45p per transformer or £1.60 per 10, £4.50 per 100)

These very high quality British made two pin European adaptors are ideal for driving Radios, cassette recorders, TV games, calculators etc. The adaptors fit in the UK shaver socket.

REF	D.C. Voltage	Current	1+	10+	100+
EOB	4.5V	200m/a	50p	45p	32p
EM3	6V	200m/a	£1.00	80p	55p
EO9	6V	400m/a	£1.50	£1.25	85p

(Postage & Packing: 45p per adaptor or £1.60 per 10, £4.50 per 100)

Send now for our latest catalogue, 35p plus 30p P+P. Over 72 pages packed with complete range of components. Includes Special Offer list, order form and prepaid envelope. Please add 15% VAT to the above prices.

**MARCO TRADING, DEPT. PE9,**  
THE MALTINGS, HIGH STREET, WEM, SHROPSHIRE, SY4 5EN.  
All orders despatched by return of mail. Tel: (0939) 32763



# AMBIT INTERNATIONAL

THE MOST COMPREHENSIVE RANGE OF COMPONENTS, KITS AND MODULES IN THE WORLD & THERE'S ONLY ROOM FOR A FRACTION HERE, GET THE CATALOGUE AND FIND THE REST. ALWAYS USE STOCK CODE WHEN ORDERING PLEASE.

4000 CMOS			74HCXX			M POWER			SMALL SIGNAL KIT			DIODES			ZENER DIODES			SPECIAL MIXERS			BALANCED MIXERS			ROBO POWER			PACKS			SMALL SIGNAL KIT		
Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price	Type	Stock No.	Price			
74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13	74V00	21 00000	0.13

RETAIL SHOP OPENING HOURS  
**VISA** Monday to Thursday 9.00-6.00  
 Friday 9.00-7.00 Saturday 9.00-5.30

ALL PRICES SHOWN EXCLUDE VAT. P&P 60p per order.  
**AMBIT INTERNATIONAL** DEPT. P.E.9  
**200 North Service Road, Brentwood, Essex**  
 TELEPHONE (STD 0277) 230909 TELEX 959194 AMBIT G POSTCODE CM14 5SG

# ELECTROVALUE

Understandably Britain's most popular and relied-upon suppliers of SEMI-CONDUCTORS I.C.s COMPONENTS COMPUTING EQUIPMENT TOOLS, BOXES, CONNECTORS and much, much more  
**OUR SUMMER PRICE LIST TELLS ALL**  
 Send for your FREE copy by return  
**BETTER PRICES, BETTER CHOICE, BETTER SERVICE**  
 Don't forget to mention PRACTICAL ELECTRONICS with your request.

**ELECTROVALUE LTD.**  
 Head Office, Mail Order Dept and Shop  
 28 St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB  
 Telephone Egham (STD 0784; London 87) 33603; Telex 264475  
 Also in Manchester for personal shoppers at  
 680 Burnage Lane, Burnage, Manchester M19 1NA. Telephone 061-432 4945  
 EV Computing Shop - 700 Burnage Lane, Manchester. Telephone 061-431 4866

## MAIL ORDER ADVERTISING

**British Code of Advertising Practice**  
 Advertisements in this publication are required to conform to the British Code of Advertising Practice. In respect of mail order advertisements where money is paid in advance, the code requires advertisers to fulfil orders within 28 days, unless a longer delivery period is stated. Where goods are returned undamaged within seven days, the purchaser's money must be refunded. Please retain proof of postage/despatch, as this may be needed.

**Mail Order Protection Scheme**  
 If you order goods from Mail Order advertisements in this magazine and pay by post in advance of delivery, PRACTICAL ELECTRONICS will consider you for compensation if the Advertiser should become insolvent or bankrupt, provided:  
 (1) You have not received the goods or had your money returned; and  
 (2) You write to the Publisher of PRACTICAL ELECTRONICS summarising the situation not earlier than 28 days from the day you sent your order and not later than two months from that day.

Please do not wait until the last moment to inform us. When you write, we will tell you how to make your claim and what evidence of payment is required.  
 We guarantee to meet claims from readers made in accordance with the above procedure as soon as possible after the Advertiser has been declared bankrupt or insolvent.  
 This guarantee covers only advance payment sent in direct response to an advertisement in this magazine not, for example payment made in response to catalogues etc. received as a result of answering such advertisements. Classified advertisements are excluded.

# MASTER ELECTRONICS NOW! The PRACTICAL way!

YOUR CAREER..YOUR FUTURE..YOUR OWN BUSINESS..YOUR HOBBY  
THIS IS THE AGE — OF ELECTRONICS!  
the world's fastest growth industry...

There is a world wide demand for designers/engineers and for men to service and maintain all the electronic equipment on the market today — industrial — commercial and domestic. No unemployment in this walk of life!

Also — the most exciting of all hobbies — especially if you know the basic essentials of the subject. . . .

A few hours a week for less than a year — and the knowledge will be yours. . . .

We have had over 40 years of experience in training men and women successfully in this subject.


Our new style course will enable anyone to have a real understanding of electronics by a modern, practical and visual method. No previous knowledge is required, no maths, and an absolute minimum of theory.

You learn by the practical way in easy steps, mastering all the essentials of your hobby or to start, or further, a career in electronics or as a self-employed servicing engineer.

All the training can be carried out in the comfort of your own home and at your own pace. A tutor is available to whom you can write personally at any time, for advice or help during your work. A Certificate is given at the end of every course.

You will do the following:

- Build a modern oscilloscope
- Recognise and handle current electronic components
- Read, draw and understand circuit diagrams
- Carry out 40 experiments on basic electronic circuits used in modern equipment using the oscilloscope
- Build and use digital electronic circuits and current solid state 'chips'
- Learn how to test and service every type of electronic device used in industry and commerce today. Servicing of radio, T.V., Hi-Fi, VCR and microprocessor/computer equipment.

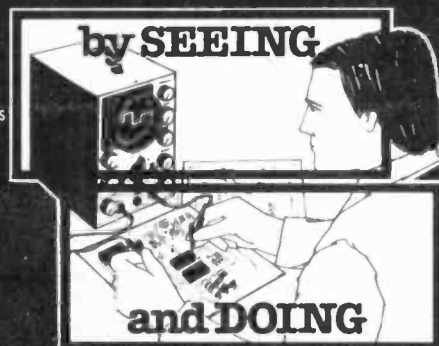

**British National Radio & Electronics School Reading, Berks. RG1 1BR**

**FREE!**

COLOUR BROCHURE



POST NOW TO

Please send your brochure without any obligation to

NAME \_\_\_\_\_ PE/9/841

ADDRESS \_\_\_\_\_

BLOCK CAPS PLEASE

I am interested in:

- COURSE IN ELECTRONICS as described above
- RADIO AMATEUR LICENCE
- MICROPROCESSORS
- OTHER SUBJECTS please state below

OR TELEPHONE US  
0734 51515 OR  
TELEX 22758  
(24 HR SERVICE)



**British National Radio & Electronics School Reading, Berks. RG1 1BR**

# Tandy®

The Largest Electronics Retailer In The World

## Compact 3 1/2-Digit 16-Range Multimeter



£34<sup>95</sup>

*Ideal For The  
Electronics Hobbyist*



- Fused and Overload Protected
- 10 Megohm Input

Digital accuracy at a practical price! DC volts: 2-20-200-2000V (max. 1000V), AC volts: 2-20-200-2000 (max. 500V), accurate from 45 Hz to 10 kHz. DC Current: 2-20-200mA-2A. Resistance: 2-20-200-2000k Ohms. 5<sup>9</sup>/<sub>16</sub> x 3<sup>1</sup>/<sub>4</sub> x 1<sup>7</sup>/<sub>16</sub>". Includes spare fuse, test leads. Requires 2 "AA" batteries. 22-189

## 27 Ranges - 30,000 Ohms/Volt Multimeter

£22<sup>95</sup>

*Ideal For  
Workshop And  
Field Testing*



- Colour-Coded 4" Mirrored Scale
- Single-Knob Function Switch
- Polarity Reverse Switch

Features output jack and DC polarity reverse switch. DC Volts: 0 to 1000, 8 ranges. AC Volts: 0 to 1000, 5 ranges. DC Current: 0-10 amps, 5 ranges. Resistance Rx1, Rx10, Rx1000, Rx10,000 (10 ohms centre scale). dB: -10 to +62, 5 ranges. Requires one "AA", one 9v battery. 6<sup>1</sup>/<sub>4</sub> x 4<sup>1</sup>/<sub>2</sub> x 1<sup>3</sup>/<sub>4</sub>" 22-203

### Micronta™ 50K Ohms/V Multitester



£27<sup>95</sup>

- Volts/Amps "Range-Doubler"
- 4 1/4" Mirrored Scale

Convenient single-knob function switch. DC Current: 0 to 10 amps. Resistance: Rx1, Rx10, Rx100, Rx1k, Rx10k. AC/DC V: 0 to 1000. Requires batteries. 22-204

### Dynamic Transistor Checker



£9<sup>95</sup>

- Makes Go/No-Go Tests On Small Signal and Power Types

Indicates relative current gain, "opens", "shorts". Socket plus hook clip leads for in-circuit tests. Output jacks for external meter or scope. 2<sup>3</sup>/<sub>4</sub> x 4<sup>3</sup>/<sub>8</sub> x 3<sup>1</sup>/<sub>16</sub>". Requires "AA" battery. 22-025

### Micronta™ Clamp Meter



£27<sup>95</sup>

- Overload Protected
- Pointer Lock Switch

Measure AC current without disconnecting or breaking the line being checked. Large range selector is positioned for one-hand operation. Incorporates a pointer lock switch (for reading later). AC current: 0-6-15-60-150-300 amperes. Accuracy: ±3%. 22-160

### Microwave Leakage Detector



£9<sup>95</sup>

- Checks Microwave Oven Door Seals

Compact and light microwave leakage detector is easy to use - move along the door seals of your microwave cooker and the meter indicates the relative amount of microwave energy. Not a certification instrument. Measures just 1<sup>1</sup>/<sub>16</sub> x 1<sup>7</sup>/<sub>8</sub> x 4<sup>1</sup>/<sub>2</sub>". 22-2001

**OVER 340 STORES AND DEALERSHIPS NATIONWIDE**

Check your phone book for the Tandy store or Dealer nearest you



**Known as Radio Shack in the USA**  
Prices may vary at dealers  
Offers subject to availability



## TOO GOOD

**Y**OU have never had it so good, a comment that is almost guaranteed to put backs up even before any clarification. However, this was felt recently when we needed to order some items. Perhaps it would be more accurate to say things are not good in other areas and this makes us thankful for the distributors and retailers in the electronics industry.

What was it we were ordering? Not a special gear wheel for a sewing machine made in Outer Mongolia but simply some control knobs for a current Thorn/EMI domestic appliance. Similar to the sort we fit every week to our projects, but of course the spindle size just had to be different and we wanted the knobs to match existing ones. Therefore it was no good ordering from one of our advertisers. Had we been able to the knobs would have cost about £1 each, we could have ordered with a credit card over the phone, or even by computer via a modem, and the order would probably have arrived after a few days. Not a bad service considering that many retailers stock more than 5000 items, most of which are worth less than about £2. Postage would have been about 50p maximum.

## LUCK

Just contrast this with the Thorn/EMI story: First we asked about replacement parts in the local appliance showroom — a large independent retail chain — a very helpful assistant informed us that it would be best and quickest to contact the manufacturer direct. The assistant supplied an address but did not have a phone number. He wished us luck; we later found out why! Back at the office a call to directory enquiries resulted in two phone numbers, for different factories, and a local Thorn/EMI department number. Now the story begins:

Dial the first number, a lady quickly answers, we inform her we want to order some replacement knobs. "You have to go to your local 'electric' to order them".

"But we were told to phone you direct, it would be quicker."

"Everyone knows we don't deal direct anymore" she says, ending the conversation.

We decide to try the other number — no reply. We try the local department instead. They are helpful and tell us to phone the second number, for a price and how to order, but since it is after 4.00 on Friday they will be closed.

Monday morning, we dial the num-

ber, engaged, try again — engaged, try later — engaged, try again... Anyway, Tuesday we get through, we even get to the right department (after being cut off once). "Yes Sir we can supply. The price is £3.28, how many do you want?"

"Only one set of four."

"No Sir, that is £3.28 each — plus VAT of course."

"Why are they so expensive? They are only simple knobs!"

"Don't know Sir, but the price is correct. Just send us a cheque."

Still amazed at the price we ring off and send the cheque, with a letter asking why they are so expensive. Ten days, £15.08 (we could buy five Z80 microprocessors for that!), four phone calls and a letter later the knobs arrive—they are not gold plated! The following printed note is attached: "... it should be remembered that recent inflation has upset the relationship between parts prices and the original cost of appliances".



**EDITOR** Mike Kenward  
**Gordon Godbold** ASSISTANT EDITOR  
**David Shortland** ASSISTANT EDITOR/PRODUCTION  
**Mike Abbott** TECHNICAL EDITOR  
**Brian Butler** TECHNICAL SUB EDITOR

**Jack Pountney** ART EDITOR  
**Keith Woodruff** ASSISTANT ART EDITOR  
**John Pickering** SEN. TECH. ILLUSTRATOR  
**Isabelle Greenaway** TECH. ILLUSTRATOR  
**Jenny Tremaine** SECRETARY

**ADVERTISEMENT MANAGER** **D. W. B. Tilleard** } 01-261 6676  
 SECRETARY **Christine Pocknell**  
 AD. SALES EXEC. **Alfred Tonge** 01-261 6819  
 CLASSIFIED SUPERVISOR **Barbara Blake** 01-261 5897  
 AD. MAKE-UP/COPY **Brian Lamb** 01-261 6601

*Technical and Editorial queries and letters (see note below) to:*  
 Practical Electronics Editorial,  
 Westover House,  
 West Quay Road, Poole,  
 Dorset BH15 1JG  
**Phone: Editorial Poole 671191**

**We regret that lengthy technical enquiries cannot be answered over the telephone**

*Queries and letters concerning advertisements to:*  
 Practical Electronics Advertisements,  
 King's Reach Tower,  
 King's Reach, Stamford Street, SE1 9LS  
 Telex: 915748 MAGDIV-G

## Letters and Queries

We are unable to offer any advice on the use or purchase of commercial equipment or the incorporation or modification of designs published in PE. All letters requiring a reply should be accompanied by a stamped, self addressed envelope, or addressed envelope and international reply coupons, and each letter should relate to one published project only.

Components and p.c.b.s are usually available from advertisers; where we anticipate difficulties a source will be suggested.

## Back Numbers

Copies of most of our recent issues are available from: Post Sales Department (Practical Electronics), IPC Magazines Ltd., Lavington House, 25 Lavington Street, London SE1 0PF, at £1 each including Inland/Overseas p&p. Please state month and year of issue required.

## Binders

Binders for PE are available from the same address as back numbers at £5.50 each to UK or overseas addresses, including

postage and packing, and VAT where appropriate. State year and volume required.

## Subscriptions

Copies of PE are available by post, inland or overseas, for £13.00 per 12 issues, from Practical Electronics, Subscription Department, Oakfield House, Perrymount Road, Haywards Heath, West Sussex RH16 3DH. Cheques, postal orders and international money orders should be made payable to IPC Magazines Limited. Payment can also be made using any credit card and orders placed via Teledata Tel. 01-200 0200.

Items mentioned are available through normal retail outlets, unless otherwise specified. Prices correct at time of going to press.

## JET START-UP


The JET (Joint European Torus) experiment which was the subject of a feature in the June issue of PE was operated for the first time at Culham in Oxfordshire during the weekend of 25/26 June 1983, having been completed on time and within a few per cent of the cost estimates made in 1975 (taking inflation into account). This marks the culmination of a five-year construction programme, costing £175 million at current prices, which has been carried through by an international team drawn from the 11 European countries participating in the Project.

JET is the largest and most ambitious tokamak in the world and has been constructed mainly with funds from the European Communities, as part of the EURATOM Fusion Programme. Completion of the construction enables the start of a 7 year programme of experiments to determine the feasibility of using nuclear fusion to provide a long term energy source. Several further steps beyond JET will be required to reach a commercial nuclear fusion power station in the next century.

The conditions obtained during the start-up operation of JET were very modest compared to the ultimate performance expected. A current of 60 thousand amperes was passed through a low density hydrogen gas for a period of one tenth of a second, converting the gas to a plasma. In the envisaged JET experimental programme this current will be progressively increased to around 5 million amperes. In later years massive additional heating equipment (25MW) will be added to the machine with the aim of raising the hydrogen plasma to a temperature around 50 million degrees for periods of about 10 seconds. If this is successful then towards the end of the project deuterium and tritium gas instead of hydrogen will be introduced into the machine to produce fusion reactions, when it is hoped that the self-heating effect will further raise the temperature to the required 100 million degrees centigrade, hotter than the centre of the sun, releasing

bursts of high energy neutrons. In a future fusion reactor these neutrons will be the source of heat for producing electricity. Of the various fusion experiments in the world only JET and the American TFTR tokamaks have been designed to operate with deuterium and tritium plasmas. Neither JET nor TFTR have, however, been designed to utilize the energy from these neutrons.

The successful completion of the JET device is a major step forward in the development of nuclear fusion as a new source of energy for Europe. If the outcome of the experiments on JET is positive then it will still be necessary to build another machine to study and solve the engineering and technological aspects of fusion before a demonstration reactor can be built. It will therefore be well into the next century, ie 2020 - 2030, before a commercial nuclear fusion power station could be built.

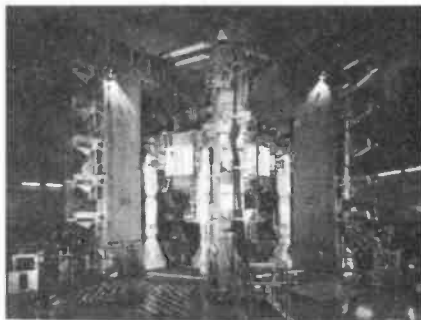

## CASE HARDENED

Crofton Electronics have just launched a replica of the case for the BBC Micro in sheet steel. Although the case is heavier than the original it is strong enough to support disk drives and a monitor.

Fitting the case is quite straightforward and only requires a few simple hand tools. The keyboard surround, back label and input/output labels are merely taken off the original case and refitted to the new one by means of double sided Sellotape.



Crofton also intend to produce an alternative top cover with an integral floppy disk housing with a platform large enough to support a 14" colour monitor.

The retail price of the standard case is £39.50 inclusive. Crofton Electronics Ltd., 35 Grosvenor Road, Twickenham, Middlesex TW1 4AD (01-891 1923).


The unit is priced at £19.95 including VAT and p&p. S&W Battery Charging Systems Ltd., Nailsea Trading Estate, Southfield Road, Nailsea, Bristol (0272 855161).

## BATTERY MONITOR

A new device has been developed by S&W Battery Charging Systems Limited to prevent premature battery failure and to reduce the costs of battery maintenance. This unit may be simply inserted between the charger and the battery.

No larger than a matchbox, the unit is designed to constantly monitor battery voltage without interrupting the system. Once the cells are fully charged, the controller will pass only sufficient current to maintain the battery in a fully charged condition without overcharge.

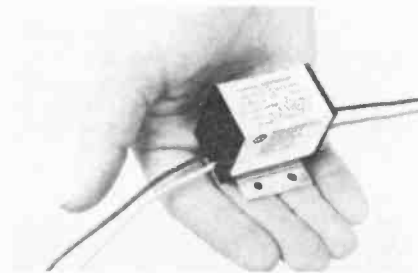The controller which can easily be fitted into existing charging systems can be adjusted externally to give a variety of voltages, thereby making one unit suitable for a wide range of lead acid or nickel cadmium batteries.



## Software Library

A program library is being formed to keep up the supply of software for OSI/UK101 computers.

Programs will be available, several to a tape, for a small charge to cover professional duplication, post and packing.

The library is looking for anyone who can

# MARKET PLACE

donate programs (a major ex-dealer has generously offered to donate his entire program range already) or help in any other way.

Tape 1, to get things moving, is available now for £2.50. Contents include games, novelties and BASIC Remember and tape file programs, all of which run under CE GMON, preferably with an enhanced screen. All cheques to the 'OSI/UK Program Library' please, to the address below.

For further details see the OSI/UK User Group Newsletter or contact Mr F. J. Leonhardt, 2, Birchmead Avenue, Pinner, Middlesex HA5 2BG (01-866 7010) weekends.

## PAN 2001

The Pantec Pan 2001 is a high quality multimeter which is available by mail order from Electronic & Computer Workshop Ltd., priced at £99.00 plus £1.00 p&p and VAT.

The unit will measure d.c.-a.c. voltages from 100µV to 1000V in 5 ranges; d.c.-a.c. current from 1µA to 10A in 6 ranges; resistances from 0.1 ohms to 20Mohms in 6 ranges and capacitance from 1pF to 20µF in 5 ranges. An optional temperature measuring facility gives a -50°C to +150°C measuring range.

Specifications include a 3½ digit 19mm l.c.d., automatic polarity, overload indication and battery test, a 10Hz to 30Hz frequency range, with protection on all ranges up to 250V a.c./d.c. Power consumption is low with battery life in excess of 200 hours' continuous operation.

Electronic & Computer Workshop Ltd., 171 Broomfield Road, Chelmsford, Essex (0245 62149).

## P.c.b. Services

Unless it is otherwise stated in the components list p.c.b.s for projects in PE can be obtained from the following suppliers:

**Proto Design**, 14 Downham Road, Ramsden Heath, Billericay, Essex CN11 1PU (0268 710722)

**Bradley Printed Circuits**, 9 Harcourt Terrace, Headington, Oxford (0865 60741)  
**Magenta Electronics Ltd.**, 135 Hunter St., Burton-on-Trent, Staffs DE14 2ST (0283 65435)


**Payne Electroprint Ltd.**, Marcus Road, Dunkswell, Honiton, Devon EX14 0RA (040 489 646)

**Stanfield**, 96 Woodend, Handsworth Wood, Birmingham (021 357 7621)
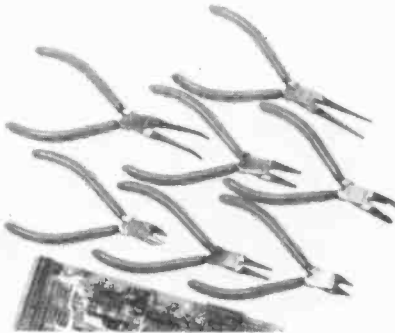
## TOOL RANGE

A range of seven precision instrument pliers have been added to the Draper selection of high quality hand tools for the electronics market.

The tools are intended to give lifelong trouble free service under everyday working conditions and are all manufactured in induction hardened chrome vanadium steel with blue PVC coated handles.



The range includes both short, straight and bent needle nose pliers. Flat nose pliers and plain, thin jaw and angle head cutting pliers. All are ideal for miniature electronic assembly, model making and precision

engineering applications.

They are priced between £5.26 and £6.85 each (plus VAT). Draper Tools Ltd., Hursley Road, Chandler's Ford, Eastleigh, Hants. SO5 5YF (04215 66355).

## 4½ DIGIT DMM

Keithley Instruments have announced a 4½ digit DMM with a current measuring capability to 20A. The unit, model 179A, has a large l.e.d. display with a full scale of 20,000 counts (4½ digits). It can measure a.c./d.c. voltages from 10µV to 1000V full scale, resistance from 0.1 ohms per digit to 20MΩ and a.c. and d.c. current from 10µA up to 20A. The a.c. conversion technique is TRMS which provides accurate readings of complex waveforms over the frequency range of 45Hz to 20kHz.

Hi-Lo ohms is fitted as standard for easy in circuit resistance measurements.

The 179A which is priced at £229.00 excluding VAT and p&p can be connected as a talker to a controller using the model 1793 IEEE interface. A BCD interface and rechargeable battery pack is also available. Keithley Instruments Limited, 1 Boulton Road, Reading, Berkshire RG2 0NL (0734) 861287.

## Silicon News Corner

Bulletins announcing new semiconductor devices arrive at PE daily, so it is possible only to describe them briefly. Details of how to obtain further information are included, however.

**Motorola** ♦ The H11AA1 and H11AA2 are two new dual l.e.d. opto-couplers with back-to-back (a.c. mode) IR l.e.d.s. Isolation is to 7500V and they are directly interchangeable with GE H11AA1/2.

♦ The LM137 series regulators are 3-terminal, adjustable negative voltage units with internal current limiting, thermal shut-down and safe area compensation. They are virtually blow-out proof, remaining so even if the adjustment terminal goes o/c.

♦ A 7-bit high speed parallel ADC employing ECL process. Comprises 128 parallel latched comparators across a high quality input reference network. Overrange output allows paralleling of the ADCs. These 15MHz devices are called MC10315L and MC10317L. Input from -2V to +2V.

♦ MOS power transistor range with breakdown voltages up to 900V. Eight types, each 3A Id: MTM3N55 to MTM2N90 (TO3), and MTP3N55 to MTP2N90 (TO-220). Motorola Ltd., York House, Empire Way, Wembley, Middlesex.

**Marconi** ♦ Unique rugged glass-wall diode with 2500GHz cut-off frequency, called the DC1346. Has low capacitance and resistance. Marconi Electronic Devices Ltd., Dodington Road, Lincoln LN6 0LF.

**Mitsubishi** ♦ A mass produced 64K Mask ROM capable of high speed reading (250ns access). Consumes 40mA (10mA standby), is TTL compatible, organised as 8192 x 8 bits, and is called the M5M2364P. Mitsubishi Electric Corp.


**RCA** ♦ 10A Versawatt SCR added to sensitive-gate family. The S4060 has µA gate sensitivity with working voltages up to 800V, and current surges up to 120A. Thermal resistance is only 2°C/W. Comes in plastic TO-220AB package. RCA, Lincoln Way, Windmill Road, Sunbury-on-Thames, Middlesex.

**Hitachi** ♦ DMA controller called HD68450 is first of a new family of intelligent 68000 support chips. Transfer rates of 2 megawords/Sec possible. Four channels/chip, each with 16MByte memory addressing. Can mix 8 and 16 bit operation, and can monitor system and then automatically adjust data rates to maximum efficiency. Hitachi Electronic Components (UK) Ltd., Hitec House, 221 Station Road, Harrow, Middlesex.
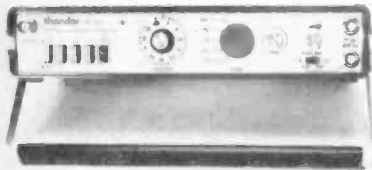
## FUNCTION GENERATOR

The TG101 is mains operated 0.02Hz to 200kHz function generator with selectable waveforms of sine, square, triangle and d.c. from a variable amplitude 600Ω output. A TTL output is also provided.

Frequency is selected by a five position range switch and a calibrated vernier or can be controlled by the sweep input which enables the generator frequency to be adjusted or modulated by an external control voltage. Both vernier and sweep input can give >1000:1 frequency change within the selected range. Typical external sweep range is 10,000:1.



A single vernier plus two position switched attenuator control the level of the 600Ω variable output over a >80dB range up to a maximum of 10V peak to peak. D.C. offset is switch selectable and the vernier provides adjustment of up to ±5V.

The TG101, which is priced at £99 plus VAT, is housed in a ABS case measuring 255x150x50mm and weighs 1200gms. It will operate from a 50/60Hz supply of 100–120V a.c. or 200–240V a.c.

Thandor Electronics Limited, London Road, St Ives, Huntingdon, Cambs PE17 4HJ (0480 64646).

## Table Tennis Challenge

The technical successes and popularity of the "Micromouse" competition has enthused Dr. John Billingsley, of the department of Electrical & Electronic Engineering, Portsmouth Polytechnic, to throw down the gauntlet to the robotics fraternity. This time, build robots that can play table tennis (modified ping-pong, really), and do it in readiness for 1986. Perhaps computerised mice can extricate themselves from a fiendish maze too easily, but the contending robots of ping-pong will need sophisticated vision systems if they are to avoid the humiliation of a comical defeat.

A number of rules have been decided upon: No mainframe link-ups. No laser vision systems, in deference to the ocular health of the spectators. The bat size is not to exceed a diameter of 12.5cm, but it needn't look like a conventional bat. The projecting force could come from a spring-

## Robot Race

Teenagers in 21 schools are tuning up their computers for Britain's first "race of the robots."

At stake is more than £2,000 prize money offered by BP Oil in their Buildarobot Competition in which schools have been challenged to design and build their own classroom robots.

Although the full details of the microchip marvels are remaining strictly under wraps until the competition finals in October, one school has already revealed that its robot could be used for finding lost golf-balls, while another could be adapted to serve afternoon tea.

The competition itself, run as part of the oil company's "Challenge to Youth" series, has actually set less daunting tasks. Teams have been given two options — to design a robot which will retrieve and return a cube, or to make a robot to carry out a specific task of their choosing.

The winners will be decided at the Royal Electrical and Mechanical Engineers' Arborfield Garrison on 23 and 24 October.

Boys at Shrewsbury School are using an immensely powerful microchip, and parts salvaged from a 20-year-old mainframe computer to build their self-contained robot in the "free choice" section. In the competition, its job will be to search out a route and then locate an object.

"We've tried it out in the school courtyard, and found that it could be programmed to bring me a gin and tonic without knocking over any ornaments, or else serve me with afternoon tea in my garden," said the school's head of computing, Mr Roscoe.

loaded mechanism within the bat, as opposed to a swing of the robot arm.

Doctor Billingsley points out that the fastest net-skimming return from a low ball takes just under 0.5 seconds from bat to bounce, and has a vertical velocity on bouncing of just over two metres per second—*"Within the performance of the servo's of any self-respecting high-speed plotter!"* A lob may allow more time for the opposing robot to respond, but will impart double the vertical ball velocity. The table is especially designed to accommodate a ball-serving mechanism, along with physical barriers to the robot competitors themselves, who must perform within specified boundaries. The scoring system will probably be based on the lengths of rallies, or number of returned shots. For more information, interested parties should contact Dr. Billingsley at Portsmouth Poly, Anglesea Road, PO1 3DJ.

Meanwhile, both the Royal Latin School, in Brookfields, Bucks, and the Rednock Comprehensive School in Dursley, Gloucestershire, are building robots for the cube-retrieval section of the competition.

Five boys at the Royal Latin School are using two miniature radar transmitters to home their robot in on the cube, guided by a special program they have written for the school's BBC computer.

Two Rednock schoolboys are using stereo ultrasonics for the miniature "guidance system" which will steer their robot close to the cube before arms fitted with sensors shoot out and grab it.


To prevent the competition from taking on too much of a "hi-tech" atmosphere, the organisers are planning an "It's a Knockout" interlude in which the schools will take on teams from REME, the judging panel, and BP in sports ranging from snooker to swimming.

More than 200 schools originally entered the competition, and the 21 who have reached the finals have each been given £100 to complete their robots. BP's "Challenge to Youth" series also includes competitions for young people to design and build their own cars, motorcycles and hovercraft, as well as providing grass-roots coaching in sports such as rugby and squash.
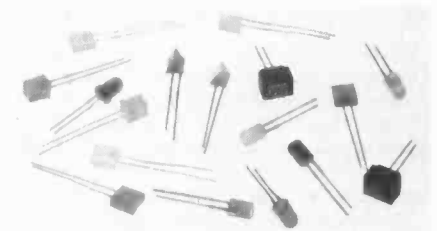
## COMPATIBLE I.e.ds

Stotron are now able to supply a range of standard and flat plane viewing I.e.d. lamps at competitive prices. Miniature and standard sized I.e.d. indicators are available, with red, green or yellow diffused lenses. These are all compatible with TTL, CMOS and MOS circuits.

Round I.e.d. lamps with a flat plane viewing surface are also available with the above three colour options, and triangular, rectangular and square lamps are available with orange lenses.



One rectangular series with a lighted area of 0.220" x 0.125" is stackable in X or Y direction and is supplied complete with mounting grommet.

Stotron Ltd, 72 Blackheath Road, Greenwich, London SE10 8DA (01-691 2031).

# MARKET PLACE

## Briefly...

BICC, the British cable manufacturer and Corning Canada, an optical fibre company, have formed a partnership to produce fibre optic cables. The two companies have set up a new firm called Optical Fibres and have built the World's first purpose-built factory for the production of optical fibres in Deeside, North Wales.

The latest technology has come to the aid of the visually handicapped writer, in the shape of a device called the Microbrailer MB2400. This 1Mbyte braille word processor is manufactured by Erleybridge Communications, and is interfaced to that company's speech terminal.

To assist the partially sighted, Wormald International Sensory Aids has produced an information handling system called the Viewscan Text System (VTS) that can receive information from public data bases. Viewscan comprises a display screen capable of presenting extra bright characters of up to three inches in height, and is linked to a miniature hand-held camera for reading the printed text.

Blind, and partially sighted DP

professionals, of which there are about 200 in Britain, are able to keep abreast of developments by way of courses documented in braille. The British Computer Association of the Blind organises two courses each year (courses which maintain very high standards) through the RNIB—this latter organisation being responsible for placement.

*The chemical giant ICI is investing £10 million over the next three years in the creation of an electronics group dedicated to technological advances, rather than the exploitation of existing markets. ICI's new venture will orbit around its 400,000 unmarketed chemicals; chemicals which might have applications in resists, display dyes and data storage, to an estimated value of £100 million by the end of the decade.*

**Scientists at the Texas Agricultural and Mechanical University have brought nearer the day when vehicles can be economically run on hydrogen extracted from water. Using electrolysis to separate water into its constituent components, hydrogen and oxygen, was previously only possible at an efficiency between one and five percent, but the new technique has**

**passed the 12 per cent mark. This breakthrough is considered very exciting because hydrogen, being a light element, is potentially suitable as an aircraft fuel. The exhaust created upon combustion is water, so hydrogen also has ecological advantages.**

Clive Sinclair is sinking £2 million into a Cambridge based research establishment, to be called MetaLab. This will be a think-tank and spawning ground for high risk ideas. MetaLab is intended to regurgitate actual commercial launches in fields ranging from battery technology to robotics.

**Graduates of French polytechnics can now circumvent conscription into national service for 12 months, by providing a term of computer training to the country's unemployed youngsters. 12,000 graduates have already given computer education to youths in this novel scheme which President Francois Mitterrand hopes will help to close socialist France's technology shortfall. It remains to be seen whether, or not, mere two-month crash courses will burgeon a Gallic workforce of competent computer technologists.**

## Countdown . . .


Please check dates before setting out, as we cannot *guarantee* the accuracy of the information presented below. Note: some exhibitions may be trade only. If you are organising any electrical/electronics, radio or scientific event, big or small, we shall be glad to include it here. Address details to Mike Abbott.

**Acorn Exhibition** Aug. 25–28. Cunard Int. Hotel, Hammersmith, London. J3  
**BARTAG Rally** (radio teleprinter) Aug. 29. Sandown Park, Esher, Surrey. E2  
**Light Aviation Show** Sept. 1–3. Cranfield Institute, Bedfordshire. Z1  
**Electro West** Sept. 6–8. Bristol Exhibition Centre. Q  
**CAST** (Cable And Satellite Television) Sept. 11–14. NEC. F5  
**Weldex** Sept. 12–16. NEC B/ham. I  
**Testmex** Sept. 13–15. Grosvenor House, Park Lane, London. E  
**Home Entertainment Spectacular** Sept. 17–25. Olympia. I2  
**Peterborough R & ES Mobile Rally** Sept. 18. Wirrina Stadium, Bishops Rd., Peterborough. L2  
**Personal Computer World Show** Sept. 28–Oct. 2. London. M  
**Laboratory London** Oct. 12–15. Barbican Centre. E  
**Drives/Motors/Controls** Oct. 12–14. Leeds University. E  
**Analyticon** (ex. & conf.) Oct. 12–14. Barbican Cntr., London. L4  
**Computer Graphics** Oct. 18–20. Wembley. O  
**PARC** (computers in architecture, conf.) Oct. 18–20. Wembley. O  
**International Business Show** Oct. 18–26. NEC. T  
**Business Efficiency Exhibition** Oct. 22–26. Earls Court, London. Z

**Electronics Hobbies Fair** Oct. 27–30. Alex Pavilion, London. Z1  
**Electronic Displays** Nov. 1–3. Kensington Ex. Centre, London. D4  
**Brainwave** (computing/video) Nov. 4–6. NEC Birmingham. G2  
**Home Tech** Nov. 11–13. Ex. Cntr., Bristol. F3  
**Test (and Environmental Test)**. Nov. 15–17. Wembley Conf. Cntr. T  
**Compec** Nov. 15–18. Olympia, London. Z1  
**Intron** Nov. 22–24. RDS Hall, Dublin. V  
**Northern Computer Fair** Nov. 24–26. Belle Vue, Manchester. Z1  
**Automatic Testing/Test/Instruments**. Dec. 13–15. Metropole, Brighton. D4  
**BEX Bournemouth 84** (Business Equipment). Feb. 8–9. Pavilion. K


D4 Network ☎ 02802 5226  
E Evan Steadman ☎ 0799 22612  
E2 BARTG 89 Linden Gdns., Enfield, Middx.  
F3 Tomorrow's World ☎ 0272 292156  
F5 Cable & Satellite ☎ 01-487 4937  
G2 Clapp & Poliak ☎ 01-747 3131  
I Industrial Trade Fairs ☎ 021 705 6707  
I2 Alan Taylor ☎ 01-486 1951  
J3 Computer Marketplace ☎ 01-930 1612  
K Douglas Temple ☎ 0202 20533  
L2 D. T. Wilson, 4 Conway Ave., Peterborough  
L4 Scientific Inst. Manufacturers' Assn. ☎ 01-437 0678  
M Montbuild ☎ 01-486 1951  
O Online ☎ 09274 28211  
Q Exhibitions for Industry ☎ 08833 4371  
T Trident ☎ 0822 4671  
V SDL Exhibitions ☎ Dublin 763 871  
Z BETA Exhibitions ☎ 01-405 6233  
Z1 IPC Exhibitions ☎ 01-643 8040

# GET BIG POWER

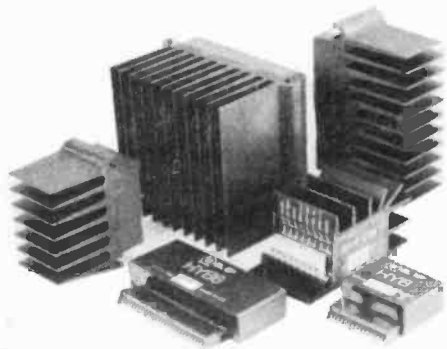
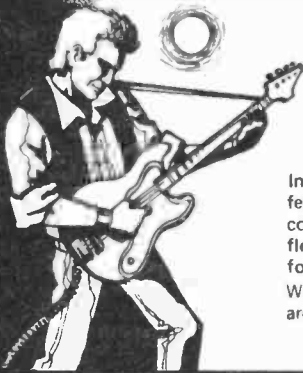
## Modular Amplifiers the third generation

Due to continuous improvements in components and design ILP now launch the largest and most advanced generation of modules ever.



### WE'RE INSTRUMENTAL IN MAKING A LOT OF POWER

In keeping with ILP's tradition of entirely self-contained modules featuring, integral heatsinks, no external components and only 5 connections required, the range has been optimized for efficiency, flexibility, reliability, easy usage, outstanding performance, value for money.

With over 10 years experience in audio amplifier technology ILP are recognised as world leaders.



#### BIPOLAR MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7kHz $\pm 1$	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
HY 81	15	4-8	0.015%	<0.006%	$\pm 18$	76 x 68 x 40	240	£8.40
HY 661	30	4-8	0.015%	<0.006%	$\pm 25$	76 x 68 x 40	240	£9.55
HY 661B	30 + 30	4-8	0.015%	<0.006%	$\pm 25$	120 x 78 x 40	420	£18.69
HY 124	60	4	0.01%	<0.006%	$\pm 26$	120 x 78 x 40	410	£20.75
HY 128	60	8	0.01%	<0.006%	$\pm 35$	120 x 78 x 40	410	£20.75
HY 234	120	4	0.01%	<0.006%	$\pm 35$	120 x 78 x 50	520	£25.47
HY 238	120	8	0.01%	<0.006%	$\pm 50$	120 x 78 x 50	520	£25.47
HY 364	180	4	0.01%	<0.006%	$\pm 45$	120 x 78 x 100	1030	£38.41
HY 368	180	8	0.01%	<0.006%	$\pm 60$	120 x 78 x 100	1030	£38.41

Protection: Full load line, Slew Rate: 15V/ $\mu$ s, Rise time: 5 $\mu$ s, S/N ratio: 100dB, Frequency response (-3dB) 15Hz - 50KHz, Input sensitivity: 500mV rms, Input Impedance: 100K  $\Omega$ , Damping factor: 100Hz > 400.

#### MOSFET MODULES

Module Number	Output Power Watts rms	Load Impedance $\Omega$	DISTORTION T.H.D. Typ at 1KHz	I.M.D. 60Hz/7kHz $\pm 1$	Supply Voltage Typ	Size mm	WT gms	Price inc. VAT
MOS 128	60	4-8	<0.005%	<0.006%	$\pm 45$	120 x 78 x 40	320	£18.69
MOS 248	120	4-8	<0.005%	<0.006%	$\pm 55$	120 x 78 x 80	850	£38.41
MOS 364	180	4	<0.005%	<0.006%	$\pm 55$	120 x 78 x 100	1025	£25.54

Protection: Able to cope with complex loads without the need for very special protection circuitry (fuses will suffice). Slew rate: 20V/ $\mu$ s, Rise time: 3 $\mu$ s, S/N ratio: 100dB, Frequency response (-3dB) 15Hz - 100KHz, Input sensitivity: 500mV rms, Input impedance: 100K  $\Omega$ , Damping factor: 100Hz > 400.

#### 'NEW to ILP' In Car Entertainments

**C15**  
Mono Power Booster Amplifier to increase the output of your existing car radio or cassette player to a nominal 15 watts rms.

Very easy to use. **£9.14 (inc. VAT)**

Robust construction.  
Mounts anywhere in car.  
Automatic switch on.

Output power maximum 22w peak into 4 $\Omega$ .  
Frequency response (-3dB) 15Hz to 30KHz, T.H.D. 0.1% at 10w 1KHz  
S/N ratio (DIN AUDIO) 80dB, Load Impedance 3 $\Omega$ .  
Input Sensitivity and Impedance (selectable) 700mV rms into 15K  $\Omega$  3V rms into 8 $\Omega$ .  
Size 95 x 48 x 50mm, Weight 256 gms.

**C1515**  
Stereo version of C15. **£17.19 (inc. VAT)**

Size 95 x 40 x 80, Weight 410 gms.

#### PRE-AMP SYSTEMS

Module Number	Module	Functions	Current Required	Price inc. VAT
HY 6	Mono pre-amp	Mic/Mag, Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble	10mA	£7.60
HY 66	Stereo pre-amp	Mic/Mag, Cartridge/Tuner/Tape/Aux + Vol/Bass/Treble/Balance	20mA	£14.32
HY 73	Guitar pre-amp	Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix	20mA	£15.36
HY 78	Stereo pre-amp	As HY66 less tone controls	20mA	£14.20

Most pre-amp modules can be driven by the PSU driving the main power amp. A separate PSU 30 is available purely for pre amp modules if required for £5.47 (inc. VAT). Pre-amp and mixing modules in 18 different variations. Please send for details.

#### Mounting Boards

For ease of construction we recommend the B6 for modules HY6-HY13 £1.05 (inc. VAT) and the B66 for modules HY66-HY78 £1.29 (inc. VAT).

#### POWER SUPPLY UNITS (Incorporating our own toroidal transformers)

Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT	Model Number	For Use With	Price inc. VAT
PSU 21X	1 or 2 HY30	£11.93	PSU 52X	2 x HY124	£17.07	PSU 72X	2 x HY248	£22.51
PSU 41X	1 or 2 HY60, 1 x HY606, 1 x HY124	£13.83	PSU 53X	2 x MOS128	£17.86	PSU 73X	1 x HY364	£22.54
PSU 42X	1 x HY128	£15.90	PSU 54X	1 x HY248	£17.86	PSU 74X	1 x HY368	£24.23
PSU 43X	1 x MOS128	£16.70	PSU 55X	1 x MOS248	£19.52	PSU 75X	2 x MOS248, 1 x MOS368	£24.20
PSU 51X	2 x HY128, 1 x HY244	£17.07	PSU 71X	2 x HY244	£21.75			

Please note: X in part no. indicates primary voltage. Please insert "0" in place of X for 110V, "1" in place of X for 220V, and "2" in place of X for 240V.

# WITH A LOT OF HELP FROM



# ILP ELECTRONICS LTD

## PROFESSIONAL HI-FI THAT EVERY ENTHUSIAST CAN HANDLE...

### Unicase

Over the years ILP has been aware of the need for a complete packaging system for its products, it has now developed a unique system which meets all the requirements for ease of assembly, adaptability, ruggedness, modern styling and above all price.

Each Unicase kit contains all the hardware required down to the last nut and bolt to build a complete unit without the need for any special tools.

Because of ILP's modular approach, "open plan" construction is used and final assembly of the unit parts forms a compact aesthetic unit. By this method construction can be achieved in under two hours with little experience of electronic wiring and mechanical assembly.


### Hi Fi Separates

**UC1 PRE AMP UNIT:** Incorporates the HY78 to provide a "no frills", low distortion, (<0.01%), stereo control unit, providing inputs for magnetic cartridge, tuner, and tape/monitor facilities. This unit provides the heart of the hi fi system and can be used in conjunction with any of the UP Unicase series of power amps. For ultimate hum rejection the UC1 draws its power from the power amp unit.

**POWER AMPS:** The UP series feature a clean line front panel incorporating on/off switch and concealed indicator. They are designed to compliment the style of the UC1 pre-amp. Performance for each unit which includes the appropriate power supply, is as specified on the facing page.
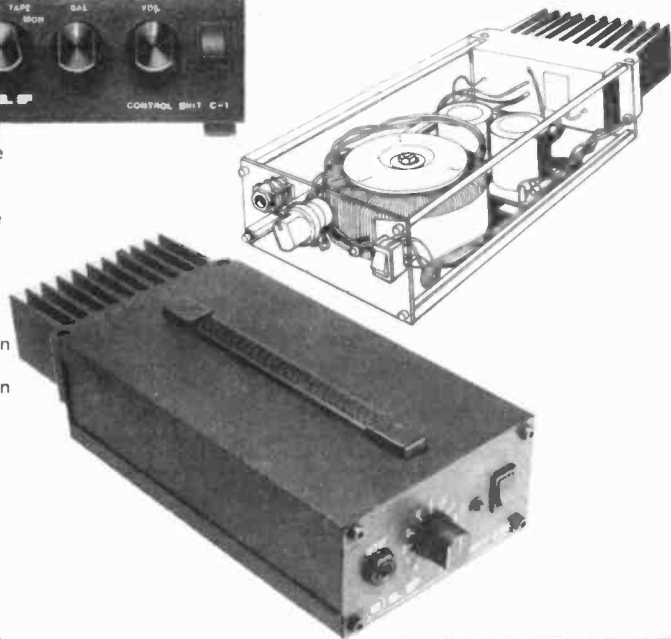
### Power Slaves

Our power slaves, which have numerous uses i.e. instrument, discotheque, sound reinforcement, feature in addition to the hi fi series, front panel input jack, level control, and a carrying handle. Providing the smallest, lowest cost, slave on the market in this format.



#### TO ORDER USING OUR FREEPOST FACILITY

Fill in the coupon as shown, or write details on a separate sheet of paper, quoting the name and date of this journal. By sending your order to our address as shown at the bottom of the page opposite, with FREEPOST clearly shown on the envelope, you need not stamp it. We pay postage for you. Cheques and money orders must be crossed and made payable to I.L.P. Electronics Ltd. if sending cash, it must be by registered post. To pay C.O.D. please add £1 to TOTAL value of order.

**PAYMENT MAY BE MADE BY ACCESS OR BARCLAYCARD IF REQUIRED. Allow 28 days for delivery.**



Post to: ILP Electronics Ltd, Freepost 2, Graham Bell House, Roper Close, Canterbury, CT2 7EP, Kent, England. Telephone (0227) 54778. Technical (0227) 64723. Telex: 965780.

#### UNICASES

HiFi Separates					Price inc. VAT
UC1	Preamp				£29.95
UP1X	30 + 30W/4-8Ω	Bipolar	Stereo	HiFi	£54.95
UP2X	60W/4Ω	Bipolar	Mono	HiFi	£54.95
UP3X	60W/8Ω	Bipolar	Mono	HiFi	£54.95
UP4X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP5X	120W/8Ω	Bipolar	Mono	HiFi	£74.95
UP6X	60W/4-8Ω	MOS	Mono	HiFi	£64.95
UP7X	120W/4-8Ω	MOS	Mono	HiFi	£84.95
Power Slaves					
US1X	60W/4Ω	Bipolar	Power	Slave	£59.95
US2X	120W/4Ω	Bipolar	Power	Slave	£79.95
US3X	60W/4-8Ω	MOS	Power	Slave	£69.95
US4X	120W/4-8Ω	MOS	Power	Slave	£89.95

Please note X in part number denotes mains voltage. Please insert '0' in place of X for 110V, '1' in place of X for 220V (Europe), and '2' in place of X for 240V (U.K.). All units except UC1 incorporate our own toroidal transformers.

Please send me the following

Total purchase price \_\_\_\_\_

I enclose Cheque  Postal Orders  Int. Money Order

Please debit my Access/Barclaycard No. \_\_\_\_\_

Name \_\_\_\_\_

Address \_\_\_\_\_

Signature \_\_\_\_\_

# 555

# 741 TESTER

STEPHEN IBBS

**A**MONGST the most common i.c.s used by hobbyists must be the humble 555 and 741. Many books have been written on how to use these versatile devices, but what if they go wrong? There is no easy way of telling if an i.c. has ceased to function by looking at it unless it quite literally does go up in smoke, so the author decided to build a very simple little tester. This unit gives a functional check to each device and whilst it doesn't claim to check many of the parameters, it should help to sort out the good from the bad. It uses the case given free by PE some time ago and which is available from the editorial offices at Poole (50p inclusive). It is very cheap to build, and even easier to use. Two wire-wrap sockets stand proud of the p.c.b. and project through the top panel of the case to enable suspect devices to be inserted quickly.


## HOW IT WORKS

The circuit diagram for the Tester is shown in Fig. 1. The test 555 is connected as an astable multivibrator whose frequency is determined by R1, C1 and R2, and with the component values stated it should oscillate at approximately 1Hz. The output (pin 3) drives D1, current limited by R5, and is also connected via S2a to one of the inputs of the test 741. The other input is connected via S2b to the potential divider formed by R3 and R4, biasing the pin at approximately half supply voltage. The effect of S2 is to alter the 741 from being an inverter to a buffer and vice-versa. The

output of the 741 drives D2, current limited by R6 which will flash either in phase, with the 741 as a buffer, or out of phase, with the 741 as an inverter.


## CONSTRUCTION

This can be either on Veroboard or a p.c.b., a suggested design for a p.c.b. is given in Fig. 2 with the component layout shown in Fig. 3. Mount the components, including the wire-wrap sockets which are soldered with a space of 10mm above the p.c.b. Cut a piece of black plastic to fit behind the case aperture, and mount the two switches and l.e.d.s in the panel before gluing it into position. Care must be taken to choose miniature toggle switches, otherwise they might foul the p.c.b. Two holes need to be cut in the top panel to allow the sockets to project through. Mount the p.c.b. using self-tapping screws, connect the battery and after the usual search for solder joins across tracks, track breaks etc, insert two working devices and check that the

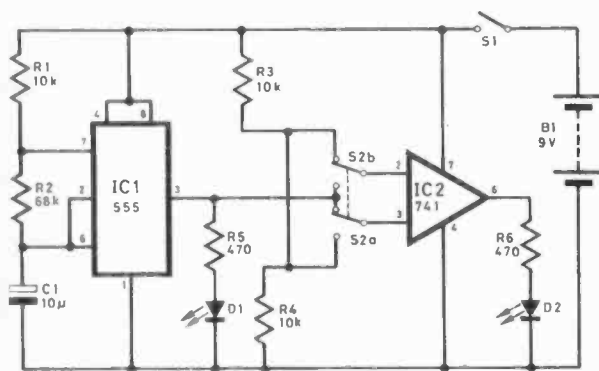

EG1216

Fig. 1. Circuit diagram

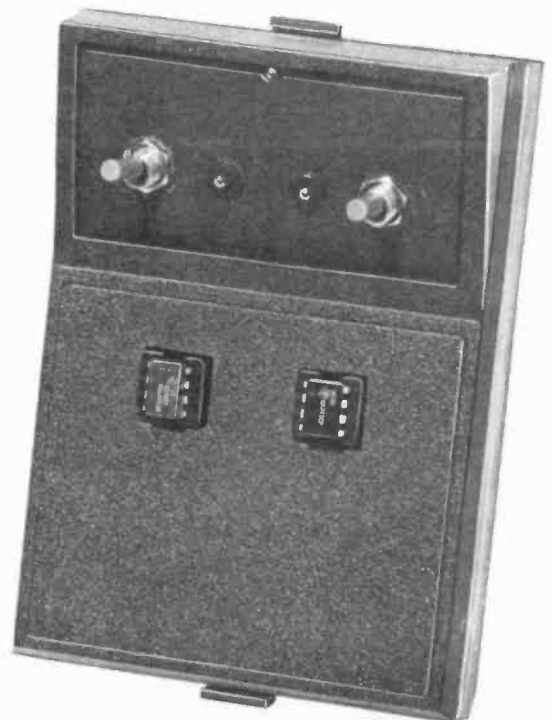



## COMPONENTS . . .

### Resistors

R1, R3, R4	10k (3 off)
R2	68k
R5, R6	470 (2 off)
All resistors $\frac{1}{4}$ W 5% carbon	

### Capacitors

C1	10 $\mu$ 16V tant.
----	--------------------

### Diodes

D1, D2	min red l.e.d. (2 off)
--------	------------------------

### Switches

S1	S.p.s.t. toggle switch
S2	D.p.d.t. toggle switch

### Miscellaneous

P.c.b.  
2 wire-wrap 8-pin d.i.l. sockets  
Case  
Battery connector


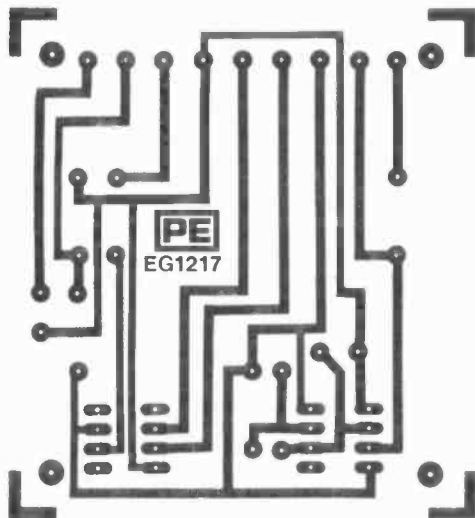


Fig. 2. P.c.b. design

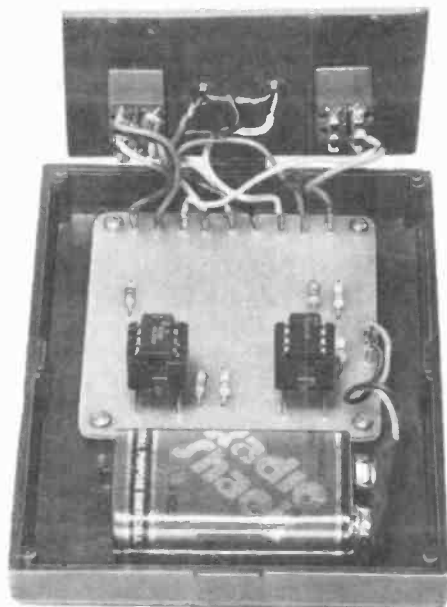

Internal view

unit functions properly. It is likely that l.e.d. D2 will glow slightly. This is normal and can be ignored, it also serves to show that the unit has been left on.

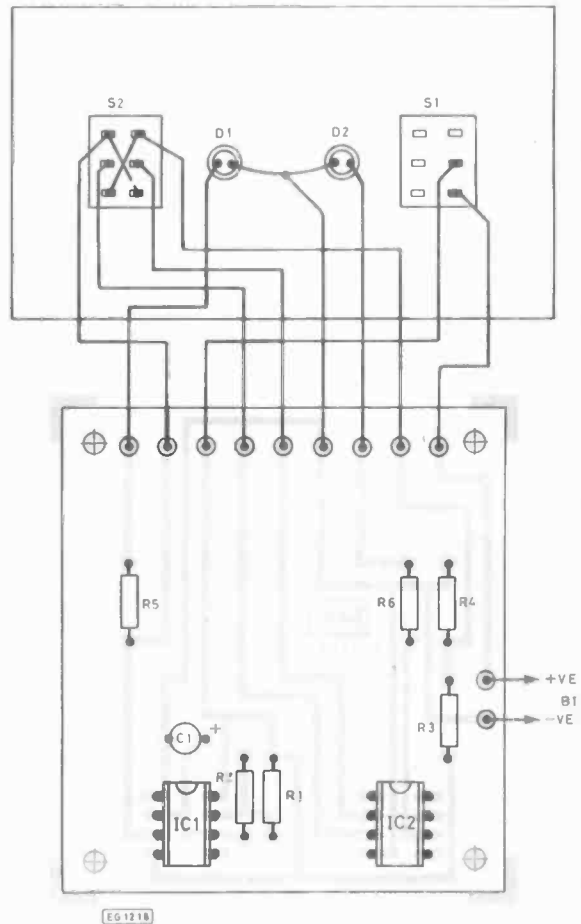


Fig. 3. Component layout

In use, two working devices are kept in the sockets, and then replaced with a suspect device for testing as and when necessary. There is no reason why other op-amps . . . e.g. CA3140, cannot be tested in the same way, providing the pin-out is the same. ★

## EVERYDAY ELECTRONICS and computer PROJECTS

### ★ STYLUS ORGAN ★

A full two octave stylus keyboard and switchable vibrato oscillator give this miniature organ a rich and interesting sound.

### ★ DISTRESS BEACON ★

Man Overboard! Provides a central point of reference for helmsman and swimmer to effect a speedy rescue.

A hand-held version specially for fell walkers and climbers is also described.

### ★ A-to-D CONVERTER for RM380Z COMPUTER ★

A multiplexed 8-channel 8-bit analogue-to-digital system tailored especially for use with the 380Z Computer User Port. Can be easily adapted for use with other Personal Computers.

Essential equipment for New Short Series—Computer-Aided Experiments for the Physics Lab.

### Plus

★ VOLTAGE DUALISER ★ CIRCUIT EXCHANGE—Readers' circuit ideas  
1983 Schools Electronic Design Award Competition Results and Report.

SEPTEMBER ISSUE ON SALE FRIDAY, AUGUST 19

Place a regular order with your NEWSAGENT—Now!

# VERNON TRENT *at Large!*

V.T.'s views and opinions are entirely his own and not necessarily those of PE

I RECKON it was Cleopatra who started this women's lib lark. The trouble was that she botched it up and, consumed with remorse, stuffed an asp down her cleavage. And that was the end of her.

Another front runner was Queen Boadicea who felt a natural feminine indignation about the tyranny of Roman rule. So she fixed blades to the wheels of her chariot and simply mowed down any cohorts she came across. Nothing very feminine about that.

Coming to modern times there's Germaine Greer who is said to have burnt her bra as a demonstration of her beliefs. In so doing she not only lost a lot of support, but did little to further what could have been a well-founded cause.

Tina Knight, whom I met recently over avocado, steak and kidney and a selection of cheeses, is, to my mind, though she scorns the suggestion, a women's libber of a sort. But as far as I know she has never provided personal accommodation for a snake, there are no blades on the wheels of her BMW and I am prepared to believe that not so much as a shoulder strap has ever been ignited.

Tina is the managing director of Global Specialties Corporation (UK) Ltd., a British-based autonomous offshoot of a company in the United States. As PE readers will know, Global enjoys a firm reputation with hobbyists and a growing popularity with industrial companies in the field of solderless breadboards and low-cost instrumentation.

"I am not a liberationist," says Tina, "but a fervent believer in equal opportunities. Yet—and this may sound like a paradox—I maintain that a woman still has the right to all those little courtesies and spoilings, like having the door opened for her, having a man stand up when she comes into the room and so on.

"Really, it boils down to a matter of good manners. And a woman's manners should be just as good as a man's. I've tried to bring the quality of good manners into my business, along with the old fashioned contention that the customer is always right. Apart from politeness, it's good common sense. A man buys a £3 breadboard and feels he's been treated as a customer should, may well turn out to be a major client. Even if he doesn't he still merits consideration and good service."

How did a young and attractive person like Tina get mixed up with the masculine-dominated, tough world of electronics?

"I started work in a bank," she told me. "Mum thought that was nice and respectable. I was supposed to be a junior shorthand-typist, but all I seemed to do was pick up paper clips. So I told the bank they'd have to try and get along without me. And I joined the ill-fated John Bloom empire. It was a pity about him, for he had a fine product, but not enough business flair. And when the crash came I took a job as secretary to the boss of a

cash-and-carry greetings cards operation. At his invitation, and expense, I did a management course and picked up many a wrinkle."

At the age of 19 Tina shoved another iron in the fire by becoming the manageress of an employment and accommodation bureau. It was there she met her husband, Mick, who was pad-hunting.

"It was what romantic novelists call a whirlwind romance and like a lot of euphoric newly-weds I saw the future as one of roses round the door, coffee mornings, marching round Sainsbury's and, who knows, the patter of little feet in the fullness of time. But fate had other plans up her sleeve. Mick works on a newspaper and one day a strike blew up. It promised to be a protracted one. So I found a job with a shipping company first and then moved on to a firm of investment brokers.

"This brought me into close contact with a management consultancy. They asked me whether I'd like to take on the task of setting up an office in London for a Greek ship-owner. This meant finding accommodation, arranging the decoration and furnishing and recruiting staff. I revelled in it. In fact I achieved something of a coup in getting offices in the Stock Exchange building, hitherto reserved exclusively for stockbrokers. The thing positively snowballed, for in no time at all I was doing the same for Arabs."

The real turning point in her career came when she was asked to take over the UK operation for Global. They were so impressed with her capabilities that they gave her a free hand to locate their UK activity wherever she wanted. She chose Saffron Walden in rural Essex. Tina calls it England's mini silicon valley, with firms like ITT and Pye-Unicam at Harlow and Cambridge respectively. Global then did something that was clearly written in the cards. They asked Tina to boss the outfit for them.

Now, from her Saffron Walden HQ, she covers the whole world except the Americas. Some 60 per cent of her business is in exports. She travels extensively in Europe and this year is off to Australia and South Africa.

At Saffron Walden she has a modest staff of only 18 people—13 of them women. Right now she's looking for her 19th. He has to be a versatile Man Friday, able to handle the exhibition side, take on some of the travelling and turn his hand to servicing. Any takers?

We sat and talked in the chintzy living room of her 13th (or most of it) century cottage a mile or two from her office. "Actually, I'm a reluctant career woman at heart," she said. "What I like most is to sit here in the evening in front of a log fire (you could stage a CND rally in the space it takes up) listening to music or watching the box. Or perhaps reading—the English classics like Trollope, Austen, Delderfield. Russian classics, too. Or maybe doing a bit of needle point."

Friends: "We've lots of close friends, though we don't get the time to do as much entertaining as we'd like. Some of my dearest pals live with me. There are the two Persians (they were lolling on the settee as though they owned the place) and then there's Jemima. She's a wild duck who dropped in one day in the garden and has been coming back at intervals ever since. She must like the cuisine. A while back she got herself pregnant and now all her little ones come back with her. Talk about getting the bird."

Marketing: "Some Americans are the finest marketing men in the world. They really get out there and sell with energy, enthusiasm and dedication. Far too many business men spend far too much of their time at meetings, gassing, investigating and drawing up four-year plans and suchlike. Where do they find the time to put what they've decided upon into effect? Of course you've got to have statistical information if you want to operate effectively and profitably. But don't get into a state where you can't see the end-product wood for the organisational trees."

Complaints: "An absolute essential is to deal with a customer's complaint fairly, swiftly and cheerfully. As I said over the avocado, the man who's spending his money with you is entitled to consideration and service. In any case, by complaining he could be doing you a favour in bringing to light some weakness in your working methods. I know that, as a customer, I've never been reluctant to complain. If a steak's tough or a soup cold, it's my duty to let the chap at the selling end know, if only in the interests of other customers."

These extracts from a long and highly-entertaining conversation, which tend, I fear, to sound like clips from the thoughts of Chairman Knight, are not only intended to illustrate the philosophy which guides a successful company, but also to show the kind of attitude that has enabled a woman to make it in a man's world.

You might pose the question: Where does this clever, quick-witted lady go next? I'd stick my neck out and say that the world is her Whitstable native. After all, how did Margaret Thatcher start? Weighing up sugar in her dad's grocery shop. You can't have a humbler beginning than that!

But even if she moves not a whit away from Global and the tranquil atmosphere of Rab Butler country, she has already made her point. That is, the hand that applies the eye-shadow is also pretty nifty at making a fairly high-technology business pay and prosper. And getting one in the eye of any man who thinks that Tina Knight and her gender are properly restricted to wielding a Hoover and making the odd, exciting excursion into sessions of pickled walnut bottling at the local Women's Institute.

One thing we haven't talked about is energy. When it was given out Tina was there at the front of the queue with a large sack. The evening before we met she'd been lashed to her desk, working out some complicated business deal, until 10.30. But as I left her and her husband at the cottage, she apologised for not coming personally to the station to see me off because she'd booked a game of squash.

How do you beat a woman like that?

# Worth more than just a look in / 83

1982 saw the first Electronic Hobbies Fair and immediately established itself as the foremost consumer electronics exhibition – the biggest attendance and the largest number of exhibitors.

The 1983 Fair will be bigger and even more exciting – offering visitors everything from resistors, IC's to home computers, transmitting and receiving units, and peripheral equipment, video games, musical instruments, radio control models. . . . In fact, whatever your particular electronic hobby you'll find this show will have something to excite you.

There will be plenty of other attractions too including radio and TV transmission; Robotics,

radio controlled models and demonstrations by local and national organisations. Again British Rail will be offering cheap-rate rail fares from all major stations in the country direct to the Alexandra Palace – a special bus will be waiting to ferry you direct to the show.

Your ticket also includes admission to the Exhibition.

Alternatively, for those wishing to travel independently ticket prices at the door are £2.00 for Adults, £1.00 for children. Party rates are available on request (minimum 20 people).

For more information contact the Exhibition Manager, Electronic Hobbies Fair, Reed Exhibitions, Surrey House, 1 Throwley Way, Sutton, Surrey SM1 4QQ. Tel: 01-643 8040.



## ELECTRONIC HOBBIES FAIR

Alexandra Palace, London – October 27-30, 1983

### Opening Times

Thursday 27 Oct – 10.00-18.00  
Friday 28 Oct – 10.00-18.00  
Saturday 29 Oct – 10.00-18.00  
Sunday 30 Oct – 10.00-17.00

Sponsored by Practical Electronics, Everyday Electronics and Practical Wireless

# SEMICONDUCTOR CIRCUITS

TOM GASKELL B.A. (Hons)

## LIGHT SPOT DRIVER (UAA 170)

THERE are a number of ways of displaying quantitative information electronically, from the simple analogue meter up to sophisticated alphanumeric readouts. Each of these techniques has its own specific advantages and disadvantages which affect suitability for any given application. As a rule, moving bars, pointers, or lights are most suitable for displaying information that varies for much of the time; they are good at indicating trends. 'Digital' displays such as alphanumeric readouts tend to be better for displaying fixed or static values, since they become difficult to comprehend when the measured parameter changes too rapidly.

For simple or non-critical measurements, a moving spot of light is often the ideal display system. Although it has a resolution which is limited by the finite number of lights used, trends can be shown very easily, and the circuitry can be made simple and inexpensive. The LM 3914 and LM 3915 i.c.s are very popular devices which can illuminate up to ten l.e.d.s, either as a spot (one lit) or as a bar (ten up to lit) in response to an analogue input signal. In many applications, however, ten l.e.d.s is not enough, yet cascading two devices to produce twenty l.e.d.s is far more than required, and is a considerable 'overkill'.

A recently introduced, but less frequently seen i.c. is the Siemens UAA 170. This is a Light Spot Driver with some unusual features which make it a better choice in some applications; namely, the capability of driving up to sixteen l.e.d.s from a sixteen pin package, and the ability to adjust the type of transition of illumination from one l.e.d. to the next between 'smooth' and 'abrupt'.

### L.E.D. DRIVING

Fig. 1 shows the pinout and specifications of the UAA 170, and Fig. 5 an applications circuit; for the moment, let us concentrate on the l.e.d. driving side of Fig. 5 only.

It can be seen that the l.e.d.s are driven as a matrix; they are arranged in four groups of four to reduce the total number of i.c. pins needed to connect to them from sixteen to

eight. The lowest analogue input voltage illuminates l.e.d. D1, and the highest illuminates D16. Because of the matrixing used to drive the l.e.d.s, a little care has to be taken when connecting up the display. Those used in each group of four should have the same characteristics, i.e. D1 to D4 should all be the same type, D5 to D8 should all be the same (not necessarily the same as D1 to D4, though), etc. Hence, if the display was to be part green and part red, the colour change should be done between one group of four and the next, not within a group. Within each group the forward voltage drop of the l.e.d.s ( $V_f$ ) should match within 0.5V. (Most l.e.d.s will easily achieve this.)

The type of circuit arrangement used to drive these l.e.d.s is the determining factor in

the requirement for a relatively high supply voltage needed for the i.c.; see Fig. 1. This is typically either 12 or 15 volts. When connecting up the l.e.d. driving pins of the UAA 170, beware of the rather odd way that the pins connect, especially the 'reversal' of pins 4 and 5; it's very easy to get it wrong! If only four, eight or twelve l.e.d.s are required, simply omit the highest relevant groups of four. If only one, two or three l.e.d.s from a given group of four are to be used, each missing l.e.d. must be replaced by its electrical equivalent, so use three ordinary diodes (1N 4148) in series to replace each omitted l.e.d. If two or more i.c.s are cascaded, beware that the top or bottom l.e.d.s of each i.c. glow continuously when the input voltage goes out of the relevant range (see Figs. 2 and 3) so these will need to be replaced by groups of three diodes as appropriate.

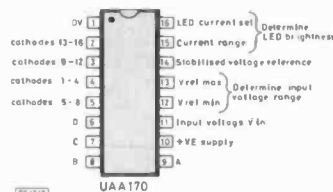


Fig. 1. UAA 170 pin-out with specification

Characteristic	Notes	Minimum	Typically	Maximum	Units
Supply voltage	All specs measured at +12V supply	11*		18	V
Quiescent current	No l.e.d.s driven, no load on pin 14	2	4	10	mA
Temp. range		-25		85	°C
Input voltage ( $V_{in}$ )		0		6.0	V
$V_{ref}$ min		0		4.6	V
$V_{ref}$ max		1.4		6.0	V
Stabilised $V_{ref}$	300µA load 5mA load	4.5	5.0	6.0	V
Current from stab. $V_{ref}$				5.0	mA
Voltage difference	( $V_{ref}$ max - $V_{ref}$ min)	1.4		6.0	V
L.e.d. current		0		50	mA
Permissible variation of $V_f$ of l.e.d.s				0.5	V
Input currents	Pins 11, 12 and 13	2			µA

\* For l.e.d.  $V_f > 1.5V$ , this lower limit will rise

### SMOOTH OR ABRUPT TRANSITIONS

Most conventional 'bargraphs' or 'light spot' meters illuminate their l.e.d.s in an abrupt way; one l.e.d. turns off at the moment that the next one turns on. This is often a valid

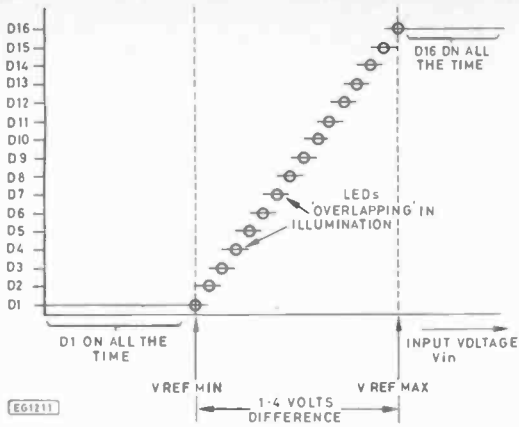


Fig. 2. 'Smooth' or overlapping I.e.d. illumination

requirement, as it makes the display very positive and unambiguous. However, if the adjacent I.e.d.s are made to 'crossfade' (one fading down as the other fades up in brightness), the light spot seems to move more smoothly, resembling a purely analogue meter, or one with a much higher resolution. This makes it ideal for displaying rapidly changing information. In the UAA 170 we have the facility for choosing just how smooth or abrupt we want the display to be; see Figs. 2 and 3.

The analogue input voltage to the i.c. ( $V_{in}$ ) should vary between two voltage reference inputs,  $V_{ref}$  minimum and  $V_{ref}$  maximum. Often,  $V_{ref}$  min will be set to 0V, but both are variable over the range indicated in the specifications (Fig. 1) to allow flexibility in operation. Input voltages below  $V_{ref}$  min cause D1 to be illuminated all the time, and voltages above  $V_{ref}$  max cause D16 to be lit all the time. (Note that  $V_{ref}$  min,  $V_{ref}$  max, and  $V_{in}$  should not exceed 6V.)

The difference between  $V_{ref}$  min and  $V_{ref}$  max determines the type of action of the display; 1.4V represents 'smooth' changes, with

the I.e.d.s fading into each other, i.e. overlapping, and 4V represents 'abrupt' changes, with the I.e.d.s turning on and off rapidly, and with no overlap. This effect changes proportionally for voltages between 1.4 and 4V. Since the difference between  $V_{ref}$  min and  $V_{ref}$  max represents the range of input voltages which are accepted, the design of any input circuitry will have to take into account the type of I.e.d. display changes required. For convenience, a stabilised voltage reference of nominally 5V is provided on pin 14, and this can be used directly, or via a potential divider, to provide the  $V_{ref}$  max voltage.

### DISPLAY BRIGHTNESS

The brightness of the display can be adjusted in rather a complex way by using pins 15 and 16; see Figs. 4 and 5. R11, between the stabilised voltage reference and pin 16, determines the I.e.d. drive current. The variation of current with R11 value is determined by another resistor, R10, from pin 15 to 0V. As can be seen from Fig. 4, for a low value of

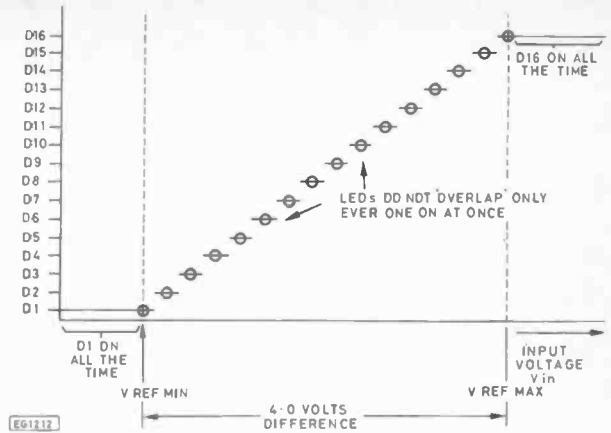


Fig. 3. 'Abrupt' or non-overlapping I.e.d. illumination

R10, the current can range from 0 to 20mA. For high values of R10 the range is 20mA to 40mA or thereabouts.

With the values shown in Fig. 5, the I.e.d. current is approximately 9mA. The reason

Fig. 4. Effects of resistance variation on I.e.d. current

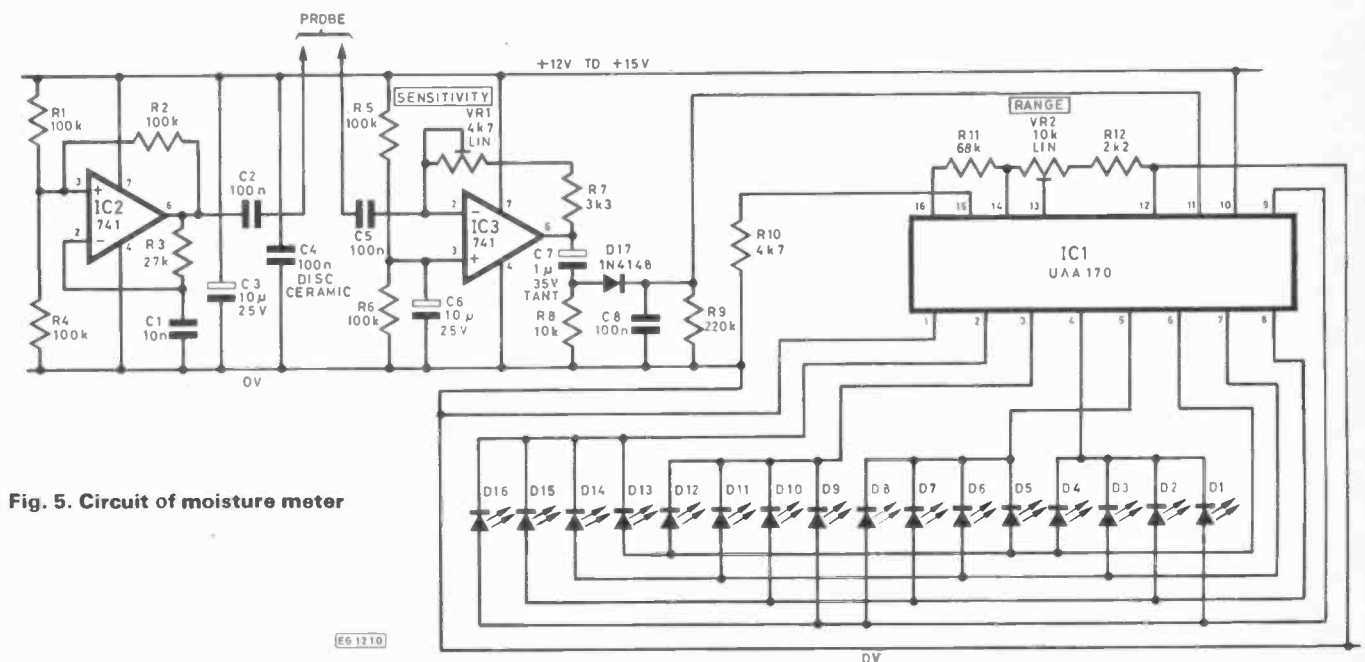
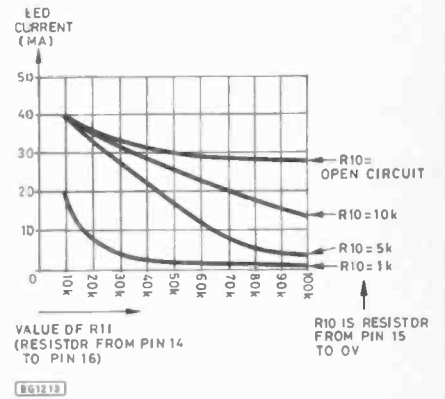


Fig. 5. Circuit of moisture meter

for this rather unusual design of brightness adjusting circuitry is to allow a phototransistor to be used to automatically adjust i.e.d. brightness to suit ambient conditions. R11 is replaced by an *npn* phototransistor in series with a 10k resistor. (Collector to pin 14, base open circuit, emitter to 10k resistor, 10k resistor to pin 16.) Another resistor, typically 18k, is connected between the emitter and collector of the phototransistor, and R10 is made a suitable value, chosen from the graph in Fig. 4.

## APPLICATIONS CIRCUIT

Fig. 5 shows a simple moisture meter for determining the water content of soil or similar substances. IC2 is a 741 (or similar) op-amp connected as a square wave oscillator with a frequency of approximately 2.8kHz. This is a.c. coupled via C2 to one half of the probe. The other half is again a.c. coupled via C5 to the virtual earth input of IC3, a 741 (or similar) op-amp connected as an inverting amplifier. The a.c. coupling is used to prevent electrolysis of the probe metal. The resistance of the material between the two halves of the probe, which is dependent on the moisture content, tends to act as the input resistor for IC3. The output of IC3 is therefore a square wave of amplitude determined by the resistance across the probe. R5, R6, and C6 ensure that IC3 is biased up to half the voltage of the supply rail. IC3 is then a.c. coupled via C7 to the network of D17, C8 and R9. This network acts as a simple means of rectifying and smoothing the signal, so that the voltage at pin 11 of IC1 is a d.c. signal of an amplitude dependent on the magnitude of signal

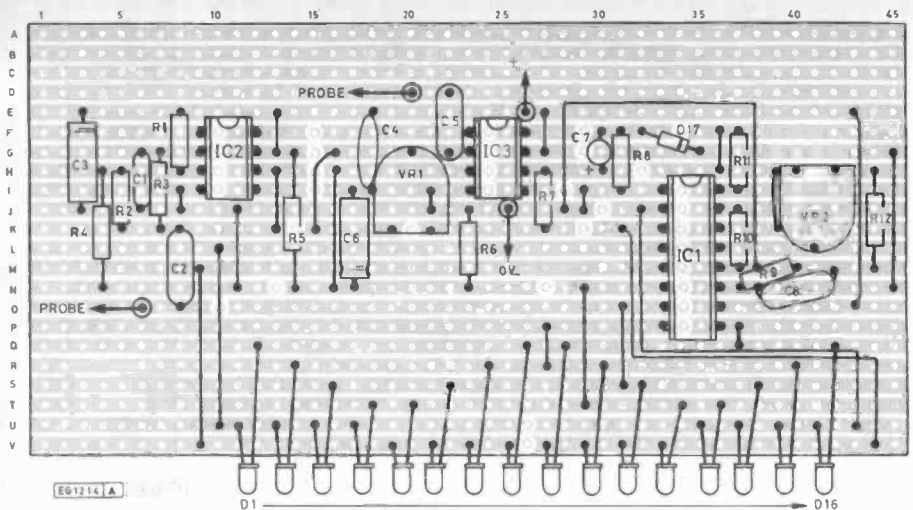


Fig. 6. The assembled moisture meter

at the output of IC3. The a.c. coupling of C7, and ground referencing of R8, ensure that this d.c. signal varies between 0V, and +6V maximum. IC1, of course, is connected as a Light Spot Driver, as already described.

VR1 adjusts the gain of IC3, and therefore determines the sensitivity of the system.  $V_{ref}$  min of IC1 is set at 0V, and  $V_{ref}$  max is set by VR2. Thus, the type of i.e.d. change, and the 'range' of the display can be adjusted by VR2. C3 and C4 provide supply decoupling for the +12 to +15V supply. This need not be regulated.

The probe can easily be made from a pair of stiff copper or brass wires set approximately 25mm apart. (Old ballpoint pen cases

can be used to mount the wires in.) When used in soil, these should be pushed in by 25mm or so. VR1 and VR2 can then be set accordingly, to suit the particular requirements in question.

The UAA 170 is also available with a logarithmic, rather than a linear, characteristic, and is known as a UAA 170L. However, Siemens do not suggest that it is used for new designs, so it has a somewhat limited market lifetime. For your next project using a light spot type of display, the UAA 170 offers an interesting and novel alternative to the more popular proprietary i.c.s, yet is very cheap and readily available.

The UAA 170 is available from Watford Electronics, and many other suppliers.

# BAZAAR

**PREMIER** "BASIC 5" excellent addition for Superboard UK101 with Cegmon. \$9000, new, perfect. Only £10. Cost £20. S. C. Robins, 6 Cleghorn Street, Dundee.

**SINCLAIR ZX 16K RAM pack** unused £18. K. A. Jones, 7 Harlech Rise, Chiltonwell, Nottingham NG9 5PD. Tel: 0602 23056.

**COSSOR** double beam oscillograph, model 1035 MKIII operating manual. Offers. Mr. J. Halsall, 47 Smalley St., Castleton, Rochdale, Lancs OL11 3EB. Tel: Rochdale 33511.

**WANTED** spark generator for gas cooker suit p.c. 1650 or circuit diagram for the generator 1½V input. Mr. Lea, 21 Ernard Gardens, Stone, Staffs ST15 0AE. Tel: Stone 816336.

**DITTON** 161 and Denton speakers, Sony TC377 recorder 4-channel adaptor, No. 7 AVO (broken) swap—sell w.h.y. Mel Saunders, 7 Drumcliff Road, Thurnby Lodge, Leicester LE5 2LH.

**PE** issues Sept. 77 to April 83 one of each, offers separately or bulk. S.a.e. for your reply. Mr. B. Cordes, 12 Avondale Gardens, North Seaton Estate, Ashington, Northumberland.

**TWO** b/w monitors. £40 either. One mono valve amp, suitable mad scientist £5. You collect. J. Dykes, 2 Aire Place, Winsford, Cheshire. Tel: 06065 51303.

**SPECTRUM** 16K, 2 books, 3 cassettes £100. ZX81 with 16K RAM pack 'Maplin' keyboard (uncased), will sell keyboard separate £65 c/p. G. Williams, 85 Salhouse Rd, Barrow-in-Furness, Cumbria LA13 9TN. Phone: 0229 29152 before 7p.m.

**MULLARD** 'Technical Communications' Jour-

nal, No. 13 to 140, most in easibinder. Offers. Collect or pay postage. Tel: Oxford (0865) 779855.

**INTERFACE** Commodore PET—Centronics disk. Also Datastream International printer. Serial interface. Phone Ray, Bursledon, Hants 4350.

**WANTED** manual and/or service information. Circuit diagram for Bird 'Futurist' organ. M. M. Browne, Cremer Hse, London Rd, St. Leonards on Sea, East Sussex TN37 6PE. Tel: Hastings 439344.

**ZX81** kit untouched £29. DMM kit (DP 2010) partly completed £15. With full instructions. Unwanted gifts. Q. Khuro, House SS, Freemans Common Houses, 167 Welford Road, Leicester LE2 6BF.

**VIDEO** Genie E63003 + ICL 7500 green monitor + parallel printer interface EG 3016 + progs, books. £299 o.n.o. Mikko Butt, 27 Park Road, Bushey, Herts. Tel: 01-950 3158.

**WANTED** data and service sheets for Russian scope type C.15. D. Beecher, 73 Gurnards Ave., Fishermead, Milton Keynes, Bucks. Tel: 0908 662903.

**WANTED** instruction book for Rigonda "Symphony" stereo radiogram. Mr. T. J. Stewart, 27 Westrock Drive, Belfast BT12 7LD. Northern Ireland.

**SEIKOSHA** GP80 printer with 500 sheets of paper £140 o.n.o. Pair of 85 watt speakers £55 o.n.o. T. P. Smith, Sunny Bank, Castle Street, Bletchingley, Tel: Godstone (0883) 843981.

**WANTED** old bar code reader, any type for teaching application. Tel: 0790 52506. P. Woodgate, Mavis Enderby, Nr. Spilsby, Lincs.

**PE** July 1980 to June 1983. PW March 1980 to June 1983 v.g.c. Best offer secures. Mr. S. Jenkins, 305 Havant Road, Farlington, Portsmouth PO8 1DD.

**ACORN** Atom, 12+12K, power supply, software, manual, books:—"Atomic Magic", etc. £100. Buyer collects. K. Martin, 1 Rutland Terrace, Sutton-on-Hull, North Humberside. Tel: (0482) 701013.

**SHARP** PC1500 with CE150 printer and CE155 8K memory complete with charger and manuals £300. J. C. Rawlings, 10A Drayton Gardens, West Drayton, Middlesex. Tel: West Drayton 40241.

**PET** Commodore 2001/16 mother board in order £130, add Key+Mon and you have the heart of a business system. Mr. G. Nicklin, 16 Auckland Drive, Halfway, Sheffield S19 5TP. Tel: 0742 483587.

**CASIO** VL-1 synth 10 rhythms 5 preset voices plus programmable sound mode £25 o.n.o. Tel: 061-881 3651 (Michael).

**WANTED** Data sheets for the 6845 CRT controller and AY-3-8190 sound generator. Dean Flower, 5 The Green, Littleham, Exmouth, Devon. Tel: Exmouth 70615 (after 6.00pm).

**WANTED** Sinclair Cambridge programmable, Oxford calculators, wrist calculator, micro f.m. radio, micromatic radio, working or broken. Mr. D. A. Portlock, 21 Anson Road, Locking, Weston-super-Mare, Avon.

**FREE** resistor colour code charts and some transistors. Just send s.a.e. Martin, 29 St. Johns Close, Leatherhead, Surrey.

**PE/CLEF** Joanna, 5½ octave electronic piano, complete with power amp and speaker in attractive wooden cabinet £150 o.n.o. A. Vinnell, 10 Linton Meadow, Linton-on-Ouse, York YO6 2AL. Tel: Linton-on-Ouse 412.

**MICROPROFESSOR** —1A, CTC, mainslead with plug, BASIC, v.g.c. manual, well used £50 post paid. Jeff Davies, The Waverley, 79 Rhosmaen Street, Llandilo, Dyfed SA19 6HD. Tel: (0558) 822509 after 5pm, weekdays.



# BUILD YOUR OWN

# Cortex

## 16 bit, 64 RAM colour computer

With this powerful machine (featured in Electronics Today International as a constructional project) you have access to highly advanced systems and software developed specially by MPE Ltd for the CORTEX. For business, education, R & D – or simply increasing your knowledge and understanding of computers – it beats comparably priced off-the-shelf machines hands down!

### Standard features –

- High speed 24K byte extended basic interpreter
- Powerful TMS9995 16 bit microprocessor
- 48 bit floating point gives 11 digit accuracy
- High resolution (256 x 192) colour graphics
- Screen memory does not use up user memory space
- 16 colours available on the screen together in graphic mode
- Fast line drawing and point plotting basic commands
- High speed colour shape manipulation from basic
- Full textual error messages
- String and Array size limited only by memory size
- Real time clock included in basic
- Interval timing with 10mS resolution via TIC function
- Named load and save of basic or machine code programs
- Auto-run available for any program
- Powerful machine code monitor
- Assembler and Disassembler included as standard
- Auto line numbering facility
- Full renumber command
- Simple but powerful line editor
- Buffered i/o allows you to continue executing the program while still printing
- Flexible CALL statement allows linkage to machine code routines with up to 12 parameters
- Basic programs may contain spaces between key words to make programs readable without using more memory
- Over 34K bytes available for basic programs
- Extended basic includes IF-THEN-ELSE
- Supports up to 16 output devices: Screen and cassette interfaces included as standard
- Supports bit manipulation of variables from basic
- Error trapping to a basic routine included
- Basic supports Hexadecimal numbers
- Separate 16K video RAM for graphics

STATEMENTS	PRINT	TIME	RENUM	MAG	MWD	( )	INT	POS	
IF	?	WAIT	BOOT	TOF	BASE	U	LOG	COL	
ELSE		SAVE	GRAPH	TON	COMMANDS	#	SQR	MOD	
ON		LCAD	TEXT	DIM	RUN		SYS	RND	
GOTO	1 UNIT	MOTOR	PLOT	LET	SIZE	:	TIC	KEY	
GOSUB	BAUD	ESCAPE	UNPLOT	DEF	CONT	:	SGN	OPERATORS	
POP	CALL	NOESC	COLOUR	NEW	MON	:	BIT	OR	
REM	DATA	RANDOM	CHAR	END		:	CRB	LOR	
FOR	READ	ENTER	SPRITE	BIT		:	ATN	CRF	
NEXT	RESTOR	LIST	SHAPE	TO		:	SIN	MEM	
ERROR	RETURN	PURGE	SPUT	TAB		:	COS	MWD	
INPUT	STOP	NUMBER	SGET	STEP		:	EXP	LEN	
				THEN		:	FRA	MCH	

### Self assembly kit

**£295**

Ready built **£395**

All prices + VAT  
Carriage paid



### Optional extras

RS232C interface kit	<b>£9.20</b>	Ready built	
Floppy disc interface	<b>£65.50</b>	CORTEX B – Basic machine + RS232C	<b>£410.00</b>
Pair of 5 1/2" disc drives and hardware kit	<b>£365.00</b>	CORTEX C – as above + disc drives	<b>£895.00</b>

Full assembly instructions and 216 page user's manual.

## POWERTRAN cybernetics

Portway Industrial Estate, Andover SP10 3NM. Tel: 0264 64455

To POWERTRAN CYBERNETICS, Portway Industrial Estate, Andover, Hants SP10 3NM.

Please send me \_\_\_\_\_

I enclose cheque for \_\_\_\_\_ or charge to:

Access/  
Barclaycard  
A/C No.

Name \_\_\_\_\_

Address \_\_\_\_\_

Tel. \_\_\_\_\_

# TOROIDALS


The toroidal transformer is now accepted as the standard in industry, overtaking the obsolete laminated type. Industry has been quick to recognise the advantages toroidals offer in size, weight, lower radiated field and, thanks to I.L.P., PRICE.

Our large standard range is complemented by our SPECIAL DESIGN section which can offer a prototype service within 7 DAYS together with a short lead time on quantity orders which can be programmed to your requirements with no price penalty.

\*Gold service available.  
21 days manufacture for urgent deliveries.

\*Orders despatched within 7 days of receipt for single or small quantity orders.

\*5 year no quibble guarantee.

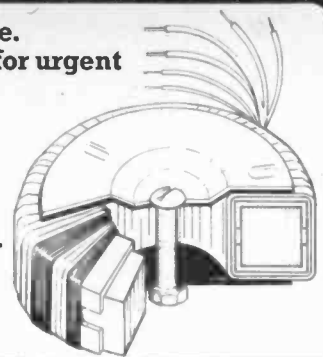

TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE	TYPE	SERIES No	SECONDARY Volts	RMS Current	PRICE																																								
<p><b>NEW!</b> <b>NEW!</b> <b>NEW!</b></p> <p><b>15 VA</b> 0x010 6+6 1.25 62 x 34mm 0x011 9+9 0.83 0.35Kg 0x012 12+12 0.63 Regulation 0x013 15+15 0.50 19% 0x014 18+18 0.42 0x015 22+22 0.34 0x016 25+25 0.30 0x017 30+30 0.25</p> <p><b>£5.12</b> + p &amp; p £0.78 + VAT £0.89 TOTAL £6.79</p> <p>(encased in ABS plastic)</p>					<p><b>120 VA</b> 4x010 6+6 10.00 90 x 40mm 4x011 9+9 6.66 1.2Kg 4x012 12+12 5.00 Regulation 4x013 15+15 4.00 11% 4x014 18+18 3.33 4x015 22+22 2.72 4x016 25+25 2.40 4x017 30+30 2.00 4x018 35+35 1.71 4x028 110 1.09 4x029 220 0.54 4x030 240 0.50</p> <p><b>£7.42</b> + p &amp; p £1.72 + VAT £1.37 TOTAL £10.51</p>					<p><b>300 VA</b> 7x013 15+15 10.00 110 x 50mm 7x014 18+18 8.33 2.6Kg 7x015 22+22 6.82 Regulation 7x016 25+25 6.00 6% 7x017 30+30 5.00 7x018 35+35 4.28 7x026 40+40 3.75 7x025 45+45 3.33 7x033 50+50 3.00 7x028 110 2.72 7x029 220 1.36 7x030 240 1.25</p> <p><b>£10.88</b> + p &amp; p £2.05 + VAT £1.94 TOTAL £14.87</p>					<p><b>30 VA</b> 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 0.45Kg 1x012 12+12 1.25 Regulation 1x013 15+15 1.00 18% 1x014 18+18 0.83 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p> <p><b>£5.49</b> + p &amp; p £1.10 + VAT £0.99 TOTAL £7.58</p>					<p><b>160 VA</b> 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 8% 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p> <p><b>£8.43</b> + p &amp; p £1.72 + VAT £1.52 TOTAL £11.67</p>					<p><b>500 VA</b> 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 4% 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p> <p><b>£14.38</b> + p &amp; p £2.40 + VAT £2.52 TOTAL £19.30</p>					<p><b>50 VA</b> 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p><b>£6.13</b> + p &amp; p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p><b>£9.81</b> + p &amp; p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p><b>£17.12</b> + p &amp; p £2.55 + VAT £2.95 TOTAL £22.62</p>					<p><b>80 VA</b> 3x010 6+6 6.64 90 x 30mm 3x011 9+9 4.44 1Kg 3x012 12+12 3.33 Regulation 3x013 15+15 2.66 12% 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x028 110 0.72 3x029 220 0.36 3x030 240 0.33</p> <p><b>£6.66</b> + p &amp; p £1.72 + VAT £1.26 TOTAL £9.64</p>					<p>ALSO AVAILABLE Sizes up to and including 5KVA are manufactured to order.</p>				
<p><b>30 VA</b> 1x010 6+6 2.50 70 x 30mm 1x011 9+9 1.66 0.45Kg 1x012 12+12 1.25 Regulation 1x013 15+15 1.00 18% 1x014 18+18 0.83 1x015 22+22 0.68 1x016 25+25 0.60 1x017 30+30 0.50</p> <p><b>£5.49</b> + p &amp; p £1.10 + VAT £0.99 TOTAL £7.58</p>					<p><b>160 VA</b> 5x011 9+9 8.89 110 x 40mm 5x012 12+12 6.66 1.8Kg 5x013 15+15 5.33 Regulation 5x014 18+18 4.44 8% 5x015 22+22 3.63 5x016 25+25 3.20 5x017 30+30 2.66 5x018 35+35 2.28 5x026 40+40 2.00 5x028 110 1.45 5x029 220 0.72 5x030 240 0.66</p> <p><b>£8.43</b> + p &amp; p £1.72 + VAT £1.52 TOTAL £11.67</p>					<p><b>500 VA</b> 8x016 25+25 10.00 140 x 60mm 8x017 30+30 8.33 4Kg 8x018 35+35 7.14 Regulation 8x026 40+40 6.25 4% 8x025 45+45 5.55 8x033 50+50 5.00 8x042 55+55 4.54 8x028 110 4.54 8x029 220 2.27 8x030 240 2.08</p> <p><b>£14.38</b> + p &amp; p £2.40 + VAT £2.52 TOTAL £19.30</p>					<p><b>50 VA</b> 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p><b>£6.13</b> + p &amp; p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p><b>£9.81</b> + p &amp; p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p><b>£17.12</b> + p &amp; p £2.55 + VAT £2.95 TOTAL £22.62</p>					<p><b>80 VA</b> 3x010 6+6 6.64 90 x 30mm 3x011 9+9 4.44 1Kg 3x012 12+12 3.33 Regulation 3x013 15+15 2.66 12% 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x028 110 0.72 3x029 220 0.36 3x030 240 0.33</p> <p><b>£6.66</b> + p &amp; p £1.72 + VAT £1.26 TOTAL £9.64</p>					<p>ALSO AVAILABLE Sizes up to and including 5KVA are manufactured to order.</p>																			
<p><b>50 VA</b> 2x010 6+6 4.16 80 x 35mm 2x011 9+9 2.77 0.9Kg 2x012 12+12 2.08 Regulation 2x013 15+15 1.66 13% 2x014 18+18 1.38 2x015 22+22 1.13 2x016 25+25 1.00 2x017 30+30 0.83 2x028 110 0.45 2x029 220 0.22 2x030 240 0.20</p> <p><b>£6.13</b> + p &amp; p £1.35 + VAT £1.12 TOTAL £8.60</p>					<p><b>225 VA</b> 6x012 12+12 9.38 110 x 45mm 6x013 15+15 7.50 2.2Kg 6x014 18+18 6.25 Regulation 6x015 22+22 5.11 7% 6x016 25+25 4.50 6x017 30+30 3.75 6x018 35+35 3.21 6x026 40+40 2.81 6x025 45+45 2.50 6x033 50+50 2.25 6x028 110 2.04 6x029 220 1.02 6x030 240 0.93</p> <p><b>£9.81</b> + p &amp; p £2.05 + VAT £1.78 TOTAL £13.64</p>					<p><b>625 VA</b> 9x017 30+30 10.41 140 x 75mm 9x018 35+35 8.92 5Kg 9x026 40+40 7.81 Regulation 9x025 45+45 6.94 4% 9x033 50+50 6.25 9x042 55+55 5.68 9x028 110 5.68 9x029 220 2.84 9x030 240 2.60</p> <p><b>£17.12</b> + p &amp; p £2.55 + VAT £2.95 TOTAL £22.62</p>																																												
<p><b>80 VA</b> 3x010 6+6 6.64 90 x 30mm 3x011 9+9 4.44 1Kg 3x012 12+12 3.33 Regulation 3x013 15+15 2.66 12% 3x014 18+18 2.22 3x015 22+22 1.81 3x016 25+25 1.60 3x017 30+30 1.33 3x028 110 0.72 3x029 220 0.36 3x030 240 0.33</p> <p><b>£6.66</b> + p &amp; p £1.72 + VAT £1.26 TOTAL £9.64</p>					<p>ALSO AVAILABLE Sizes up to and including 5KVA are manufactured to order.</p>																																																	

### The benefits of ILP toroidal transformers

ILP toroidal transformers are only half the weight and height of their laminated equivalents, and are available with 110V, 220V or 240V primaries coded as follows.

IMPORTANT: Regulation — All voltages quoted are FULL LOAD. Please add regulation figure to secondary voltage to obtain off load voltage.

For 110V primary insert "0" in place of "X" in type number.

For 220V primary (Europe) insert "1" in place of "X" in type number.

For 240V primary (UK) insert "2" in place of "X" in type number.

Also available at Electrovalue, Maplin, Technomatic and Barrie Electronics.


For mail order please make your crossed cheques or postal orders payable to ILP Electronics Ltd. Barclaycard/Access welcome. Trade orders standard terms.

Post to: ILP Electronics Ltd, Graham Bell House, Roper Close, Canterbury CT2 7EP, Kent, England  
Telephone (0227) 54778 Telex 965780.



**ILP TRANSFORMERS**  
(a division of ILP Electronics Ltd)
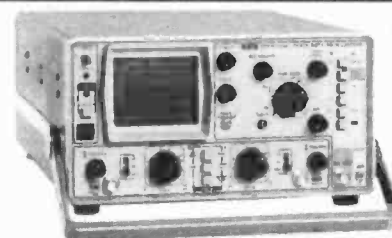
## LOW COST PROFESSIONAL TEST INSTRUMENTS




- ★ FREQUENCY COUNTERS
- ★ ANALOGUE METERS
- ★ DIGITAL METERS
- ★ FUNCTION GEN
- ★ OSCILLOSCOPES
- ★ POWER SUPPLIES
- ★ LOGIC PROBE
- ★ SCOPE PROBES

Write or phone for illustrated Test Instrument catalogue and price list.

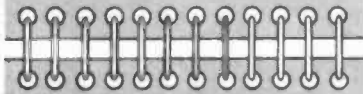**BLACK STAR LTD.**  
9A, Crown Street, St. Ives,  
Huntingdon, Cambs. PE17 4EB.  
Tel: (0480) 62440 Telex: 32339







# INDUSTRY NOTEBOOK

By Nexus



## Status Quo

So far as trade and industry are concerned the General Election killed uncertainty and it is quite clear that the socialist solution to economic problems if not completely discredited, then was certainly not trusted.

As I have often pointed out, all administrations when coming to power find themselves captive of influences outside their control. It is doubtful, had Labour won, that it would have been possible to implement their manifesto. In the event the prospect of implementation scared off the voters.

The popular vote did not in fact completely endorse the Conservative manifesto although, because of the electoral system, the Conservatives won the greatest number of seats. What the popular vote did demonstrate was that few people want more nationalisation in industry, withdrawal from the EEC, more power to the trade unions, spending our way out of recession, or unilateral nuclear disarmament. In fact the Labour manifesto was decisively rejected. A good result for industry.

## Swap-Shop

Before the invention of money as a medium of exchange, trade existed through barter. It still exists. A private swap of, say, a hi-fi for a good SLR camera is common enough. No cash changes hands, no tax is payable, both parties are satisfied.

Today, with so many nations virtually bankrupt, barter is growing in international trade with perhaps as much as 20 per cent of trade conducted in this primitive form. Recent swops have included motor vehicles and steel for coffee, tractors for fish, cars for bauxite. All these swops are in the multi-million pound bracket.

So far I have not heard of electronics goods being involved. It is conceivable that it will come. How about a computer network in exchange for a shipload of bananas? Or whatever? Watch this column.

## Telecom

Privatisation is once again on the agenda now the Conservatives are back in power. The biggest sell-off, if it ever happens, will be British Telecom. The new rival trunk network, Mercury, is already in place but with restricted service. The appearance of Mercury and the threat of privatisation has already worked miracles in BT under the leadership of Sir George Jefferson. The organisation is much more efficient than before both through new technology and vigorous marketing of services. There is possibility, indeed, probability, of further improvement but the Telecommunications Bill, lost in the General Election, has been revived in the new Parliament. This time it will be introduced by the new minister, Cecil Parkinson, and despite the huge government majority it is likely to have a turbulent passage.

Naturally, the Post Office Engineering Union will fight tooth and nail and threaten confrontation. But some user groups, formerly bitter critics of BT, are none too happy. Their change of heart may have come about from seeing that BT is pulling itself together or it may be cold feet at the prospect of the unknown. Either way the Bill will not have universal support. Getting it through the House may be easy. Implementing the Bill may prove much more difficult and may take a long, long while in a step-by-step procedure. That's why it may never happen in total though it is bound to happen in part. Selling 51 per cent of shares in BT worth up to £4 billion is still quite a problem.

## Finding the Slot

Small companies can best succeed by finding a slot in the general market as yet undiscovered by big firms or considered too small in volume to warrant serious attention. I notice, for example, that at the International Audio and Video Fair to be held in Berlin in September, a German company has spotted the rising popularity of collecting early 78 r.p.m. gramophone records. Modern stylis for use with microgroove recordings are unsuitable so the firm of Dreher and Kauf, who normally have supplied only diamond needles in the past, have added to their range "old-fashioned" needles to fill the need.

On show, too, though you need a microscope to see it adequately, is a Philips chip containing all the stages of a UHF radio receiver. The export slot is to Japan who have taken the chip in large quantities, proving once again that the Japanese market is not impenetrable.

## Buying In

The fast way to get into electronics is by acquisition, popular with outsiders wishing to broaden their business into fast-growth areas. An example is Lex Service in motors who import Volvo cars to the UK. Some 18 months ago the company acquired Hawke Electronics and now they have increased their stake in electronics by buying Jermyn Holdings, thus gaining control of the Jermyn Group. Both Hawke and Jermyn are component distributors. The purchase price

for Jermyn was a little over £15 million. For that they get all the Jermyn activities in the UK, France and Germany. Senior directors remain in place with three-year service contracts.

Before bringing the deal to a conclusion Lex studied all the market statistics and concluded that semiconductor sales in the UK would grow at an average of 19.5 per cent per year over the next five years but those sold through distributors would grow at 24.5 per cent per year. At present distributors are estimated to sell 30 per cent of all semiconductors in the UK. In the USA the figure is 40 per cent, so there appears to be room for further growth in market share for Jermyn and others within the total increased volume.

## Pirates

A big problem with innovative products is the "pirating" of designs. There is, of course, protection by patent but litigation can be lengthy and expensive. Such difficulties are often overcome by offering licences involving royalties to be paid to the patent holder.

In the ordinary way the public is unaffected by inter-company squabbles on possible infringement but I note with more than ordinary interest the public warning issued by Racal-Decca Navigator Ltd on unauthorised receivers now being offered for sale.

Decca Navigator "chains" which give navigational position to mariners are privately owned and thus not a public service. Recently, technical changes to the transmissions have been made to improve the service and Racal-Decca say that although their receivers and others manufactured with approval by Racal-Decca are unaffected, "pirate" receivers can give false readings. Naturally, official "Notices to Mariners" have been issued by the UK Hydrographer of the Navy to warn navigators of the possibility of error because safety-at-sea is of fundamental importance.

The unlicensed receivers, apparently of foreign manufacture, continue to be offered for sale. It seems to me that cheating is bad enough in itself but when safety-at-sea could be involved it is despicable conduct.

## Hoppers


Frequency-hopping tactical radios which are resistant to message interception and jamming had a high profile a couple of years ago. There was then an ominous silence during, presumably, a lengthy evaluation period by signals staffs. Now the orders are starting to filter through. Of course some armies keep quiet about new equipment but Marconi have announced orders for their Scimitar range from Portugal, Sweden and Finland with other countries still evaluating.

But rival Racal, who were the first to introduce frequency-hopping, have one order on which they have been allowed to publicly put a price-tag—a hefty £20 million contract with the Sultanate of Oman. Racal also claim 13 countries are already using their Jaguar-V frequency hoppers.



**... a more reliable memory**
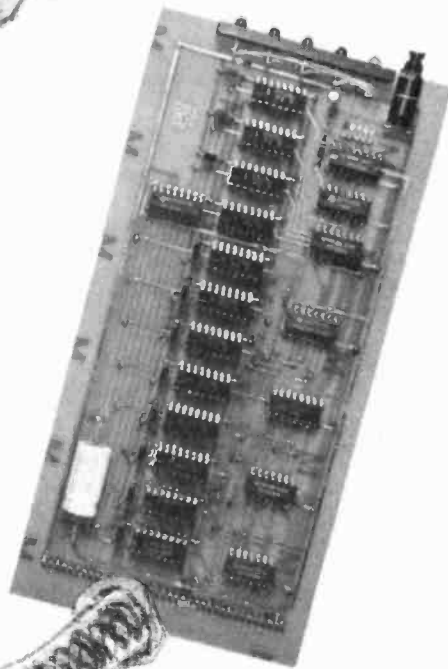
# Soft Error Detection and Correction Board



**A. Trebar**

**S**MALL business and personal computers often have the same configuration, they use the same microprocessors with the same performances, and yet the small business computers are often far more expensive when compared with personal computers; why such a difference? The answer is reliability, the small business computers are built for professional use and are designed to be as reliable as possible. The hardware is much more sophisticated and incorporates additional circuits for diagnostics which enables fault location, which in turn makes repair easier and faster. Every minute the system is not operable means a loss of money to the system user and should be kept at a minimum. On the other hand personal computers are intended for educational purposes and entertainment. With some additional hardware we can enhance the reliability of a personal computer to a degree that it can be used to do more

sophisticated tasks where a long term error free operation is a must.

One of the most error prone parts of a computer is the computer memory. Usually it is built with high density integrated circuits such as 16K and 64K RAMs, which can be affected by two types of errors: 'Hard' errors and 'Soft' errors.

Hard errors are caused by permanent damage of a memory chip or a part of it. They are mostly a stuck-to-zero or a stuck-to-one type of error. The erroneous location in memory cannot be overwritten with new data. They can easily be detected by a software memory checking program by writing some pattern to the memory and then reading it back. The same operation should be performed again with a complement pattern. Such a routine can be used as part of a power-up self test program.

Soft errors cannot be located so easily. There are several causes for soft errors: alpha radiation from packaging material, the noise can push the chip beyond limits of its normal operation, which can result in a loss of charge on storage capacitors. It is possible to observe from Table 1 that the soft errors appear more often than hard ones. The error rates of memory devices are given by manufacturers and are evaluated in an ideal testing environment. In real applications memory devices are exposed to interference and temperature variations, and this is why the error rate of a memory system is generally higher than evaluation from reliability data.

The most efficient method of coping with soft errors is the error detection and correction technique (Error Checking and Correction-ECC). The method of ECC was first described by R. W. Hamming more than 30 years ago in the article *Error detecting and error correcting codes* published in the Bell System Technical Journal, and after all these years this method is still used by most computer manufacturers for storage protection.


Error rate	16K	64K
Soft %/1000h	0.1	0.45
Hard %/1000h	0.02	0.02

Table 1. Error rates of memory devices
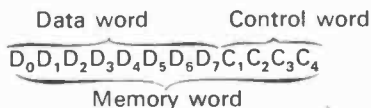
### CODE USAGE

Let's now take a look at how the Hamming code works. When the data is written into the memory, the control bits are generated and stored in a special part of the memory. The number of control bits needed depends on the number of bits in data word and on the number of errors we want to correct. The number of control bits required for single error detection and correction can be derived from the equation  $2^n \geq k + n + 1$  where  $k$  designates the number of data bits and  $n$  the number of control bits.

Data words with 8 bits require 4 control bits which will together represent a memory word.



The control word is generated as an exclusive OR (EXOR) combination of data bits as shown in Table 2.

	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
$C_1$	1	1	1	0	1	1	1	0
$C_2$	1	1	0	1	1	0	0	1
$C_3$	1	0	1	1	0	1	0	1
$C_4$	0	1	1	1	0	0	1	0

Table 2. Control word generation

Table 3 shows the system of equations which gives us control bits.

$C_1 =$	$D_0$	$\vee D_1$	$\vee D_2$	$\vee D_4$	$\vee D_5$	$\vee D_6$	
$C_2 =$	$D_0$	$\vee D_1$		$\vee D_3$	$\vee D_4$		$\vee D_7$
$C_3 =$	$D_0$		$\vee D_2$	$\vee D_3$		$\vee D_5$	$\vee D_7$
$C_4 =$		$D_1$	$\vee D_2$	$\vee D_3$			$\vee D_6$

Table 3. Control bit equations ( $\vee$  = for all values of)

When reading memory words from memory we must calculate the syndrome bits. This can be done in the following fashion: First we calculate control bits  $C'_i$  of data part of the memory word. A syndrome is an EXOR combination of control word and control bits calculated from the data part of

a memory word. The relationship between syndrome bits ( $S_1, S_2, S_3$  and  $S_4$ ) and memory bits is shown in Table 4.

	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$	$C_1$	$C_2$	$C_3$	$C_4$
$S_1$	1	1	1	0	1	1	1	0	1	0	0	0
$S_2$	1	1	0	1	1	0	0	1	0	1	0	0
$S_3$	1	0	1	1	0	1	0	1	0	0	1	0
$S_4$	0	1	1	1	0	0	1	0	0	0	0	1

Table 4. Syndrome/memory bit relationship

Since the D part of Table 4 corresponds to Table 2 the  $S_n$  bits can be calculated from the equations in Table 5.

$S_1 =$	$C_1 \vee C'_1$
$S_2 =$	$C_2 \vee C'_2$
$S_3 =$	$C_3 \vee C'_3$
$S_4 =$	$C_4 \vee C'_4$

Table 5. Syndrome bit equations

In the case that all syndrome bits are zero, we assume that there was no error in memory word. If the syndrome word is a non-zero combination there was an error. From the combination of ones and zeros in a syndrome word we can find out which bit is affected. From now on the correction of error is simple. All we have to do is to invert the bit in error and the data is correct again. If the combination of ones and zeros does not correspond to any column in Table 4 we have detected a multiple error. Such errors cannot be corrected, but we can suppress the execution of this instruction by the computer.

For example if we have the following data to be written into the memory:

$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7$   
1 1 0 0 1 1 1 0

The control bits calculated from the equation in Table 3 will be:

$C_1 = 1, C_2 = 1, C_3 = 0, C_4 = 0$

The memory word will be:

$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7 C_1 C_2 C_3 C_4$   
1 1 0 0 1 1 1 0 1 1 0 0

Let's assume that the error has affected one of the bits in the memory word. When reading from memory the memory word was:

$D_0 D_1 D_2 D_3 D_4 D_5 D_6 D_7 C_1 C_2 C_3 C_4$   
1 1 0 0 0 1 1 0 1 1 0 0

The syndrome bits calculated from the equations in Table 5 are:  $S_1 = 1, S_2 = 1, S_3 = 0, \& S_4 = 0$ . From Table 4 we see that this syndrome corresponds to  $D_4$ . By inverting it we have correct data bits.


### MULTIPLE ERRORS

Now it should be noted that some multiple errors can give us the same syndromes as single bit errors. This means that such errors will pass undetected, but fortunately it is not likely that two or more errors will occur simultaneously in the same memory word.

The method described above can give us the position of a single error in any bit of a memory word. Since only data bits are received by the processor, we do not correct the control part of the memory word in the case of an error.

A processor delivers 8-bit data to the memory unit and receives 8-bit data from the memory. All other functions are carried out automatically without the knowledge of the processor, so the ECC circuit can be regarded as transparent to the processor and thus applicable to different kinds of processors that are using an 8-bit data word system.

**Fig. 1. Block diagram of a memory system with ECC capability**

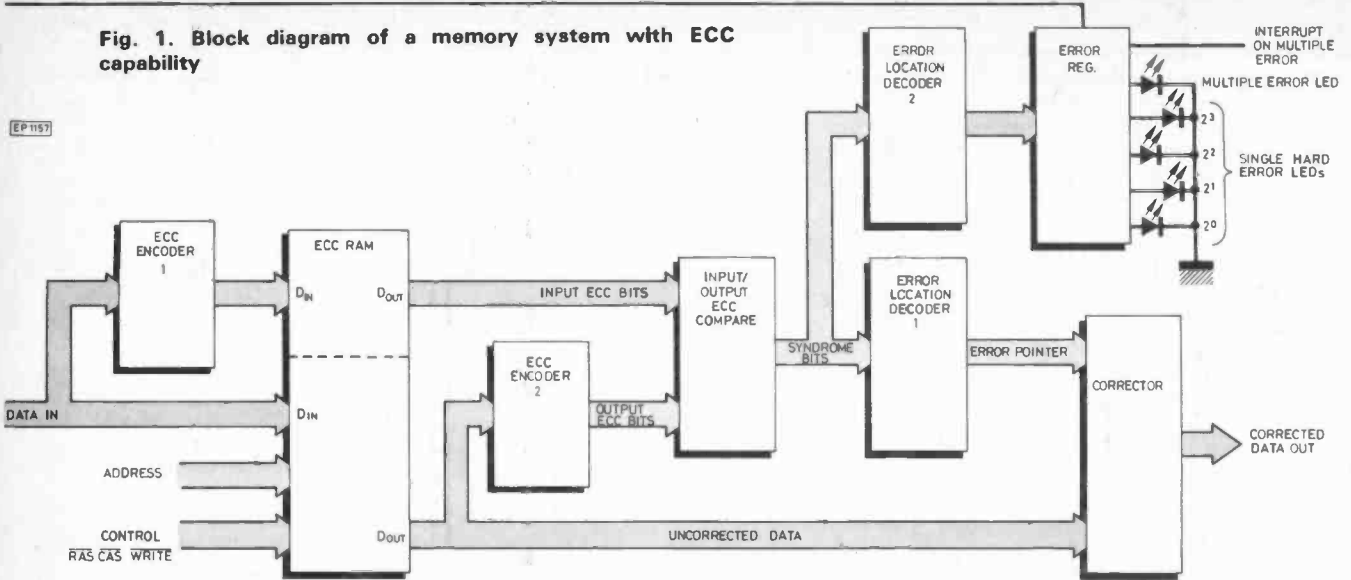

**ECC IMPLEMENTATION**

There are many single chip i.c.s presently available designed for detection and correction of a single bit in memory systems. These are very fast circuits that can detect and correct errors with propagation delay from 25 to 45ns. The major drawback for using these circuits in microprocessor based systems is their price which is prohibitively high for small quantities. Basically they are intended to be used in mini and medium size computers. The ECC circuit to be used with 8-bit data can be built with as few as 6 MSI chips.

Fig. 1 represents a block diagram of a memory system with ECC capability, five blocks are used for error detection and correction:

- ECC ENCODER 1** generates control bits from data to be stored in memory.
- ECC ENCODER 2** generates control bits from data read from the memory.
- INPUT/OUTPUT ECC COMPARE** generates syndrome bits according to the equations in Table 5.
- ERROR LOCATION DECODER** generates an error pointer from syndrome bits. The error pointer contains a single 1 at the place where the error occurred.
- CORRECTOR** is a controlled inverter that inverts the erroneous data bit from the error pointer and thus corrects it.

The upper part of Fig. 1 represents a diagnostic circuit that points to the faulty memory chip in case of a hard error. The error position is decoded in ERROR LOCATION DECODER 2 and latched in ERROR REGISTER. L.e.d.s D1, D2, D3 and D4 show the chip in error.

Fig. 2 represents a detailed schematic diagram of the ECC circuit together with memory (IC1 to IC12). Data bits  $D_{0in}$  to  $D_{7in}$  enter memory chips (IC1 to IC8) and IC13 simultaneously. IC13 is a bipolar 256 x 4 PROM which serves as ECC ENCODER 1. For every combination of input data there is a distinct combination of control bits programmed in IC9. Its contents are shown in Table 6. Control bits are stored in IC9 and IC12. When data bits are read from the memory, a new set of control bits is generated in IC17 (ECC ENCODER 2) and is equal to IC13. Syndrome bits are

**COMPONENTS ...**

**Resistors**

R1 6k8, 1/4W, 5% carbon

**Capacitors**

C1, C2, C3, C4, C5, C6, 2n2 ceramic (12 off)  
 C7, C8, C9, C10, C11, C12, C13 10µ/35V tant. bead (2 off)  
 C14 220µ/63V elect

**Semiconductors**

D1, D2, D3, D4 0.2 in red l.e.d.s (4 off)  
 D5 0.2 in green l.e.d.  
 IC1, IC2, IC3, IC4, IC5, IC6, IC7, IC8, IC9, IC10, IC11, IC12 4116 16K RAM or (4516 16K RAM)\*  
 IC13, IC17 or (4164 64K RAM)\* (12 off)  
 IC14, IC15, IC18 MMI 6301 256 x 4 PROM (2 off)  
 IC16, IC19 74LS86 QUAD EXOR (3 off)  
 IC20 74S188 32 x 8 PROM (2 off)  
 74174 HEX D FLIP FLOP

**Miscellaneous**

S1 Push to make switch  
 Terminal pins (39 off)  
 I.c. sockets (Soldercon type) (300 off)  
 Printed circuit board

\*See Fig. 4.

**Constructor's Note**

All components including Soldercon pins are available from **Watford Electronics, 35 Cardiff Road, Watford, Herts. (0923 40588.)**

calculated in IC18 and are EXOR combinations of stored control bits plus control bits generated from memory word that was read from the memory.

In case of error there will be a non-zero combination of syndrome bits. Syndrome will be 0, 0, 0, 0 if there is no error. Error location decoders are IC16 and IC19. These are 32 x 8 PROMS, both with the same contents. In the case of IC16 pin 14 is grounded. This means that only the lower part of the truth-table is selected (A<sub>4</sub> = 0). This part of PROM is programmed so that it gives us an error vector for syndromes tabulated in Table 7. The error vector is applied to

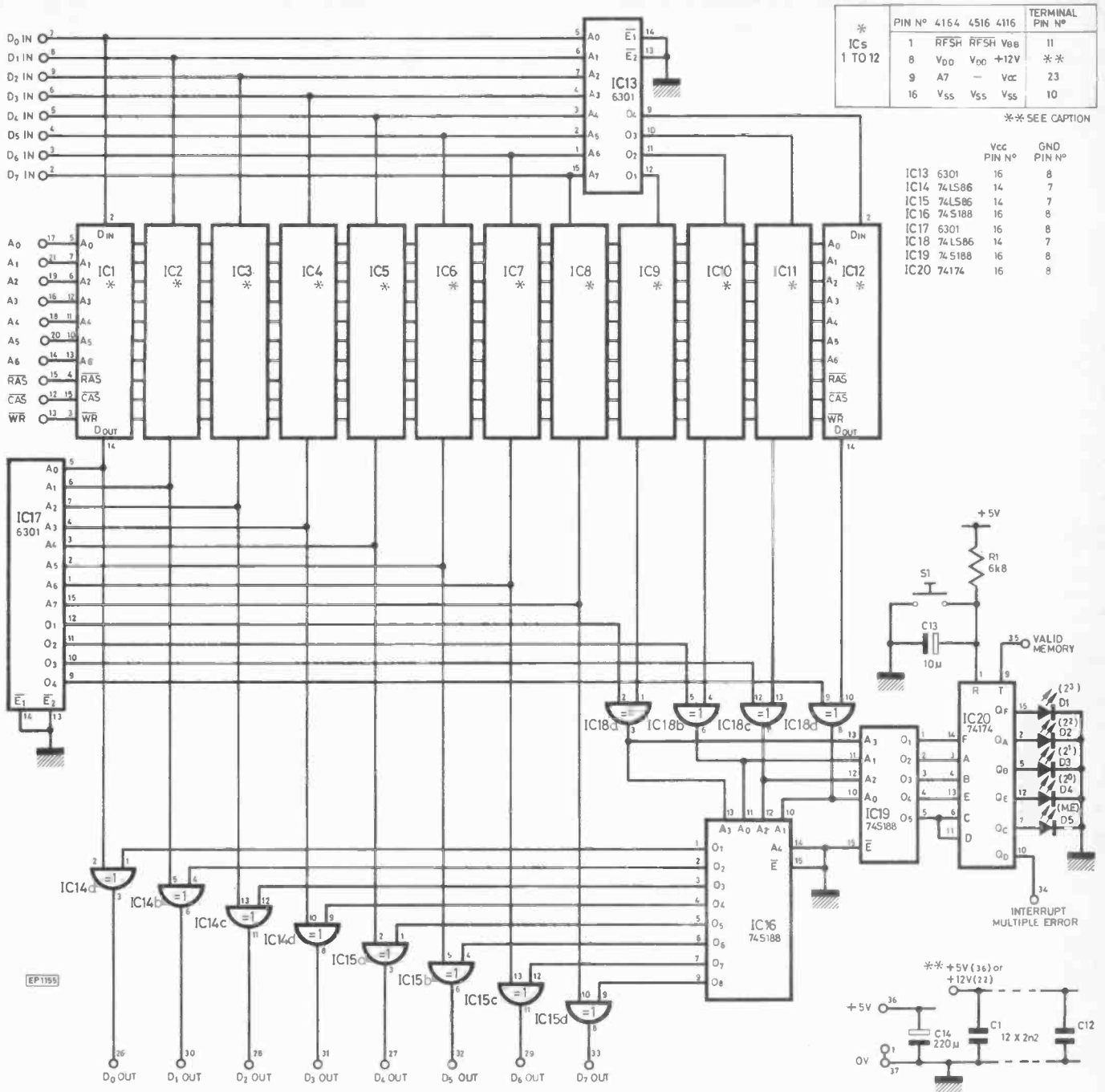


Fig. 2. Circuit diagram of the ECC circuit with memory array

IC14 and IC15 which are EXOR gates that serve as a controlled inverter. The data bit on position where error vector is 1 is inverted and thus corrected. The upper part of IC19 PROM ( $A_4 = 1$ ) contains memory chip location that corresponds to syndrome bits tabulated in Table 4.

The decoded position is stored in IC20. This is the ERROR REGISTER. L.e.d.s  $D_1$ ,  $D_2$ ,  $D_3$  and  $D_4$  show the memory chip in error.  $D_5$  is the indicator of multiple error. Error register IC20 is cleared at switch-on via R1 and C1 but can also be cleared by pressing pushbutton S1. Diagnostic data is written into the error register when memory word is valid. Otherwise we can get ambiguous information. When a multiple error is detected the signal at IC20 pin 10 (ME = high)

can be used to stop the processor.

The p.c.b. was developed so that different kinds of memory i.c.s can be used: 4116, 4516, 4164 and their equivalents. The pinouts are shown in Fig. 3. The signal information needed to interface the ECC memory to the microcomputer is given in Table 8.

The ECC circuit will enhance the reliability of the microcomputer; however there are disadvantages to the scheme: The access time of memory will be longer for the propagation delay through the ECC circuit; that is why the higher speed memories are recommended. Another disadvantage is the high price of memory array, since four additional memory chips are needed.


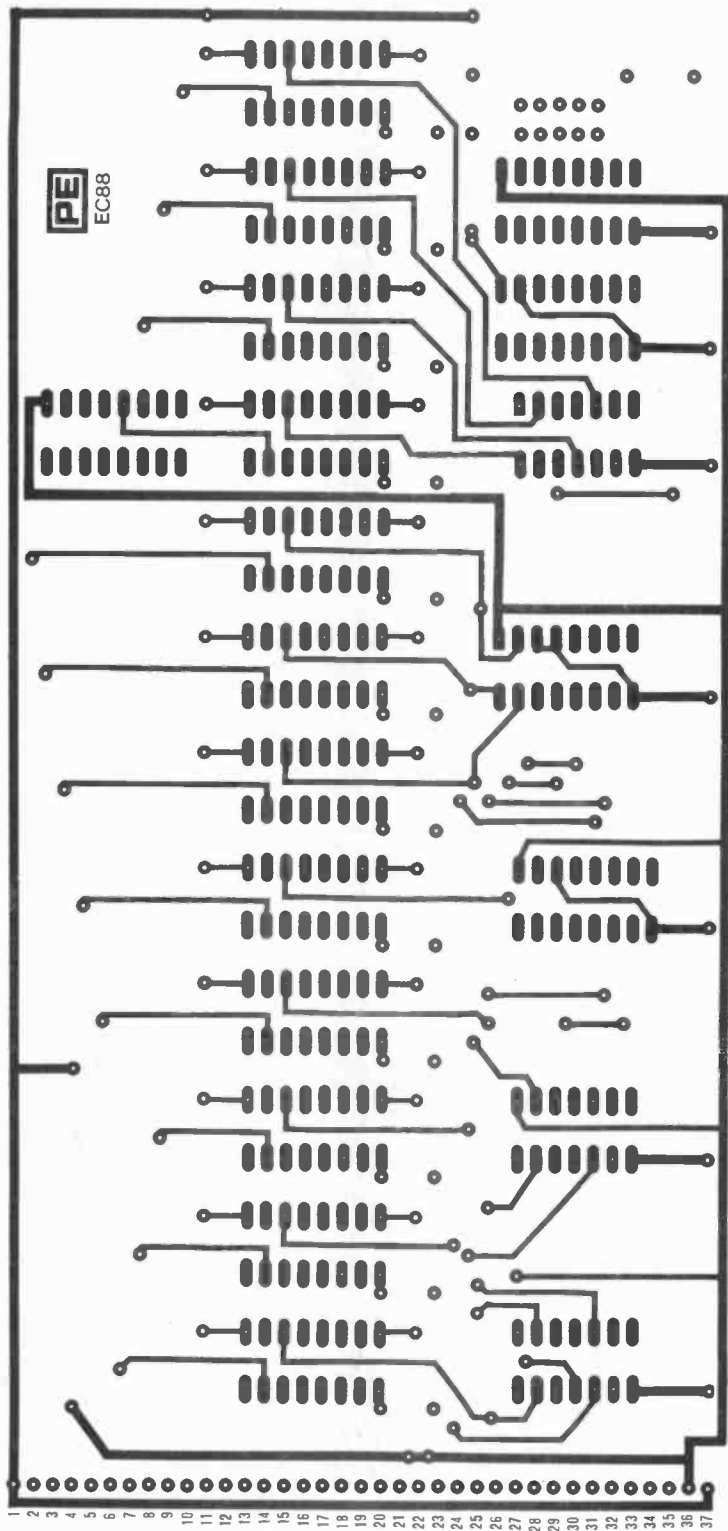


Fig. 3. P.c.b. design for ECC circuit (Topside)

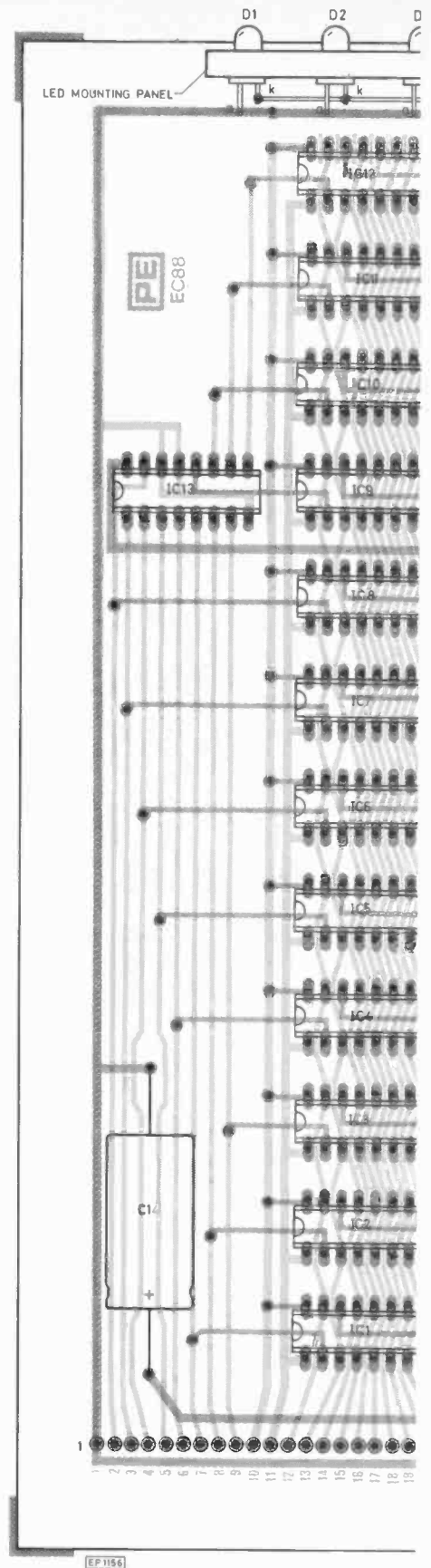

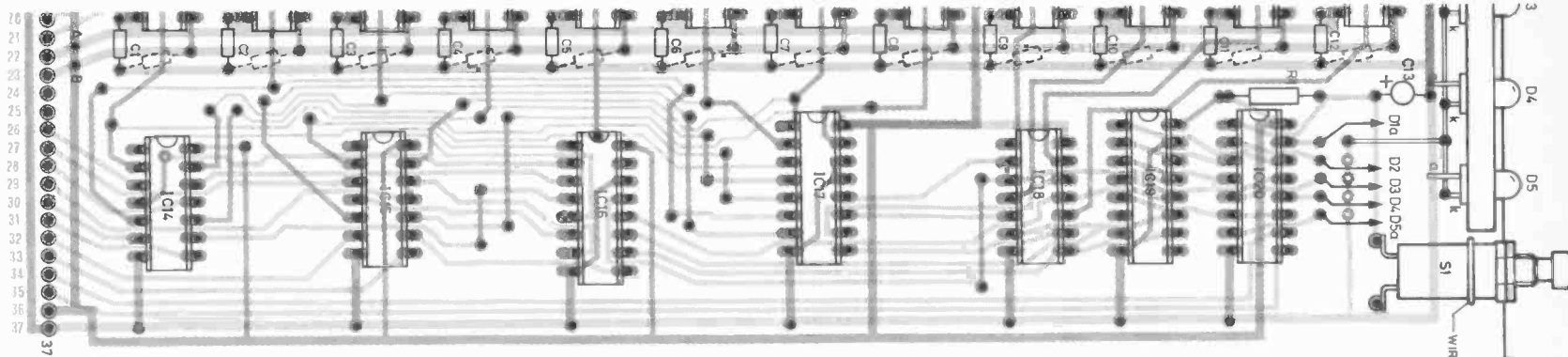


Fig. 4. Component layout for the ECC circuit. Note when a 4164 or 4516 memory device is used, pin A should be inserted and pin B omitted. This will connect pin 8 to  $V_{DD}$  (+5V) and pin 9 to terminal 23. When a 4116 device is used then pin B should be inserted and pin A omitted. This will connect pin 9 to +5V ( $V_{CC}$ ) and pin 8 to +12V via terminal 22. The capacitors C1 to C12 are shown connected for 4164 and 4516 devices. If .4116's are used then C1 to C12 should be connected in the dotted position

EC88

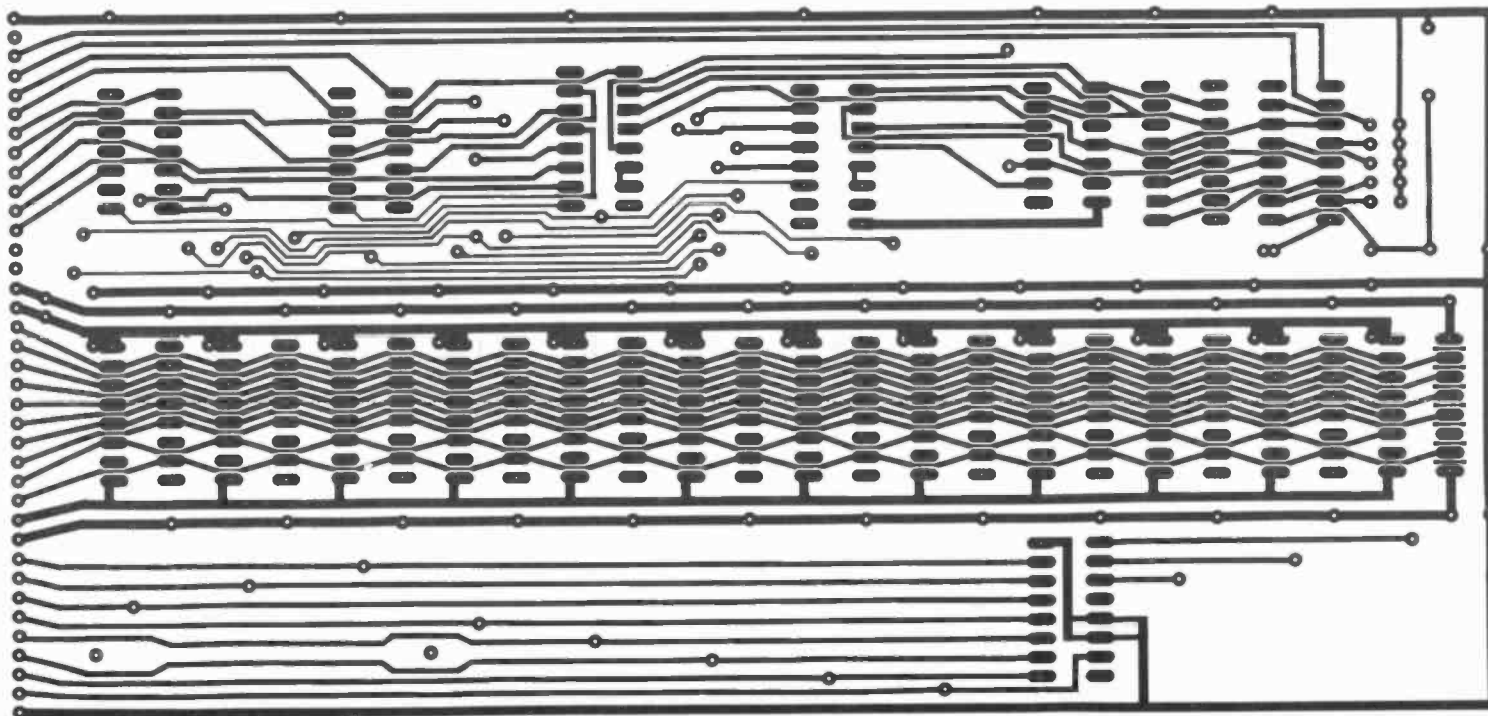


Fig. 5. P.c.b. design for ECC circuit (Underside)

00	0 6 9 F A C 3 5 C A 5 3 6 0 F 9
10	7 1 E 8 D B 4 2 B D 2 4 1 7 8 E
20	B D 2 4 1 7 8 E 7 1 E 8 D B 4 2
30	C A 5 3 6 0 F 9 0 6 9 F A C 3 5
40	D B 4 2 7 1 E 8 1 7 8 E B D 2 4
50	A C 3 5 0 6 9 F 6 0 F 9 C A 5 3
60	6 0 F 9 C A 5 3 A C 3 5 0 6 9 F
70	1 7 8 E B D 2 4 D B 4 2 7 1 E 8
80	E 8 7 1 4 2 D B 2 4 B D 8 E 1 7
90	9 F 0 6 3 5 A C 5 3 C A F 9 6 0
A0	5 3 C A F 9 6 0 9 F 0 6 3 5 A C
B0	2 4 B D 8 E 1 7 E 8 7 1 4 2 D B
C0	3 5 A C 9 F 0 6 F 9 6 0 5 3 C A
D0	4 2 D B E 8 7 1 8 E 1 7 2 4 B D
E0	8 E 1 7 2 4 B D 4 2 D B E 8 7 1
F0	F 9 6 0 5 3 C A 3 5 A C 9 F 0 6

Table 6. The contents of ECC ENCODER 1 and 2 PROM

ADDR	DATA	ADDR	DATA
00	00	10	10
01	00	11	0C
02	00	12	0A
03	04	13	03
04	00	14	0B
05	08	15	04
06	01	16	01
07	80	17	08
08	00	18	09
09	02	19	02
0A	00	1A	10
0B	20	1B	06
0C	00	1C	10
0D	40	1D	07
0E	10	1E	05
0F	00	1F	10

Table 7. Correcting and diagnostic PROM contents

### CONSTRUCTION

The assembly of the p.c.b. is quite straightforward and the following points should be considered. The ECC circuit is on a double-sided p.c.b. the design of which is shown in Figs. 3

PIN	SIGNAL	PIN	SIGNAL
1	GND	21	A <sub>1</sub>
2	D <sub>7</sub> in	22	{ V <sub>DD</sub> (4116)/ V <sub>CC</sub> (4164,4516)
3	D <sub>6</sub> in	23	{ V <sub>CC</sub> (4116)/ A <sub>2</sub> (4164)
4	D <sub>5</sub> in	24	N.C.
5	D <sub>4</sub> in	25	N.C.
6	D <sub>3</sub> in	26	D <sub>0</sub> out
7	D <sub>0</sub> in	27	D <sub>4</sub> out
8	D <sub>1</sub> in	28	D <sub>2</sub> out
9	D <sub>2</sub> in	29	D <sub>6</sub> out
10	V <sub>SS</sub> (+5V)	30	D <sub>1</sub> out
11	{ V <sub>BB</sub> (4116)/ RFSH(4164,4516)	31	D <sub>3</sub> out
12	CAS	32	D <sub>5</sub> out
13	WRITE	33	D <sub>7</sub> out
14	A <sub>6</sub>	34	INT
15	RAS	35	VALID MEM ADR
16	A <sub>3</sub>	36	+5V
17	A <sub>0</sub>	37	GND
18	A <sub>4</sub>		
19	A <sub>2</sub>		
20	A <sub>5</sub>		

Table 8. Memory/micro interface information

and 5 with the component layout shown in Fig. 4. In order to make the connections from the track-side to the component-side the i.c. sockets were soldered on both sides of the p.c.b.; Soldercon i.c. pins were used. In all other positions tinned copper links or the component leads themselves were used to make the through connections.

On the prototype the i.e.d.s were mounted on a piece of plastic and fixed to the p.c.b. along with the pushbutton switch; the constructor may wish to mount these components in a position more suited to their own equipment. Whether or not pins A and B are inserted will depend upon the type of memory i.c.s used. The use of the pins is explained in Fig. 4. When the p.c.b. has been soldered and checked the i.c.s can be inserted. ★

## PE SPECIAL CASSETTES OFFER

Over the last couple of years PE offers arranged with Videotone have proved highly successful and we have now been able to arrange special prices (only available to PE readers) on these high quality tapes. The offer is a result of Videotone's direct selling policy; send in a current special PE coupon for prompt delivery.

We believe these tapes are excellent value and we are pleased to offer them to readers. They are covered by a money back guarantee (return within 21 days for refund). Not only are the tapes of high quality but the cassettes are of screw together construction and the case labels have space for notes on the recordings.

BLOCK CAPITALS PLEASE

Please send me ..... CRO2 C60 Audio cassettes at ..... p each (90p for 5 to 24, 80p for 25 or more; including VAT and postage).

Please send me ..... CRO2 C90 Audio cassettes at .....p each (115p for 5 to 24, 105p for 25 or more; including VAT and postage).

Please send me ..... C90LH Audio tapes at ..... p each. (56p for 5 to 24, 53p for 25 or more; including VAT & postage.)

I enclose cheque/PO for £ ..... No.....

Name .....

Address .....

.....

.....

Coupon valid for posting before 2 Sept '83  
(or one month later for overseas readers)

### CHROME C60 & C90

**CRO2 C60 CASSETTES**  
90p each (minimum of 5); 80p each (minimum of 25)

**CRO2 C90 CASSETTES**  
115p each (minimum of 5); 105p each (minimum of 25)

### FERRIC C90 AUDIO

**C90LH CASSETTES**  
56p each (minimum of 5); 53p each (minimum of 25).

Send valid coupon to:  
**Videotone Ltd., 98 Crofton Park Road,  
Crofton Park, London SE4.**



run any CP/M80 software under it directly, because of course CP/M 8000 needs to run programs written in Z8000 code *not* 8080 code! As far as I have been able to discover, software to run under CP/M 8000 is pretty thin on the ground.

Things may improve in the future, since Commodore are planning to introduce a 16 bit personal computer based on the Z8000, but for the moment at least, you are on your own!

## INTERFACING

To continue time honoured Z80 traditions, the Zilog designers have put their stamp on the Z8000 by scrambling up all the pin locations on the package so that they do not appear in boring, logical, groups. Let's face it, who needs the regular D0, D1, D2, D3, D4, D5, D6, D7, D8 etc. of the 68000 when you can have the exciting AD12, AD11, AD10, AD9, AD0, AD8, SN6, SN5, AD7 of the Z8000!

Also traditional is the need for a fast, high-drive, clock generator. Most clock designs I have seen published require a couple of Shottky T.T.L. packages and a handful of discrete transistors and resistors even to operate at 4MHz. This seems to be an area neglected by Zilog and long overdue for a special clock-chip like the 8284 in the 8086 family.

Unlike the other 16 bit manufacturers Zilog have defined a specific bus interface standard for the Z8000, called the Z-BUS. The Z-BUS conforms generally with the pin-outs of the Z8001 processor, but can also be used as a board-to-board bus to support more than one CPU. The bus is asynchronous and supports five types of bus transaction as follows:

Memory access. I/O transfer. Interrupt. Bus request. Resource request.

Address and data information are multiplexed together on pins AD0 to AD15, and so an external address latch is needed in most systems. An address strobe  $\overline{AS}$ , and a data strobe  $\overline{DS}$ , are provided to control demultiplexing.

An additional seven non-multiplexed address bits are output by the Z8001 as the "segment number" to expand the address range to 8M bytes, and a Byte/Word control line is provided to indicate whether the current memory reference applies to a word or to a byte operand. Despite the use of a 16 bit data bus, memory data is byte addressable because  $A_0$  is available to select the upper or lower byte in a word and can be combined with the  $B/\overline{W}$  line to perform a similar function to the UDS and LDS strobes on the 68000. I/O transactions are indicated by the appropriate status code on ST0 to ST3 and use only the 16 bit address information on AD0 to AD15.

Three types of interrupt are provided, Non-Maskable (NMI), Non Vectored (NVI) and Vectored (VI). The only "funny" here is the NVI which is just an additional, simple, interrupt input for low priority applications which do not require the high status of the NMI or the complex vectoring of the VI.

The vectoring scheme used with the VI input should bring tears of nostalgia to the eyes of Z80 fans since it uses the same daisy chain prioritisation scheme. The interrupt outputs of all peripheral chips are wire-ORed together and to the  $\overline{INT}$  input of the Z8000. All peripheral devices are daisy chained together with the IEO (Interrupt Enable Output) of the highest priority device connected to the IEI (Interrupt Enable In) of the next highest and so on down the chain. If any peripheral has a pending interrupt it will be serviced only if no higher priority devices require service and the IEO of the next highest priority device is therefore a 1. When this condition is satisfied the peripheral in question pulls its  $\overline{INT}$  output low and the processor responds by performing an interrupt acknowledge cycle which causes the selected device to place its unique interrupt vector number on data lines AD0 to AD7.

During the acknowledge cycle the Z8001 stores its current status on the stack and reloads the four CPU status registers with the VI status block fetched from the Program Status Area of memory. You may remember from the register section that each exception class has its own four word status block, but since there can be more than one source of Vectored Interrupts, the four word block is extended to include a 256 entry vector table of new program counter values. The Interrupt Vector number from the interrupting device is used to select the appropriate entry from this table and the CPU recommences instruction execution at the start of the appropriate interrupt service routine.

This powerful interrupt scheme, while very similar to the Z80 arrangement, is not exactly the same (naughty old Zilog!) but fortunately it is still possible to connect Z80 peripherals to a Z8000 processor with the aid of some TTL translation logic.

One possible disadvantage of the Z80 and Z8000 interrupt scheme is that the priority status of all peripherals is fixed by the chip interconnections and cannot be changed. The Intel 8259 Programmable Interrupt Controller chip on the other hand, provides not only a fixed priority mode but also a rotating priority mode which can be used to ensure that a number of users of equal status get a fair crack of the whip.

Zilog have been generous in providing peripheral chips for the Z8000 family, although some of this apparent generosity is not quite what it appears! Since the Z80 family already had the most powerful 8 bit peripherals going, in some cases Zilog were able to simply modify their earlier designs slightly and give them a new number. By this means the Z80 CIO became the Z8036 CIO, with just a few pins changed to aid Z8000 interfacing! Needless to say, Zilog do not exactly shout about this feature.

To be fair to Zilog, this approach is perfectly sensible and gives them a big advantage over Motorola who have only a primitive 8 bit family to draw on and who are still struggling to get their 16 bit peripheral family together. It also allowed Zilog to concentrate effort on the relatively few *new* 16 bit peripherals like the Z8010 Memory Manager and to get these to market sooner.

The Zilog Z8010 Memory Management Unit (MMU) adds a new dimension to the memory addressing capability of the Z8001 by translating the physical address space of that processor into a logically segmented space which can be dynamically reconfigured under program control. In the basic Z8001 the 8M byte address space is divided up into 128 segments each 64K bytes long. The MMU divides the physical memory up into continuous 256 byte blocks to form 64 variable sized segments from 256 to 64K bytes positioned anywhere in the 16M byte address space, so that the logical addresses manipulated by the programmer can be flexibly transformed into the physical addresses required by the memory. The MMU therefore decouples the programmer from the memory and permits the relocation of available memory from one segment to another under system software control to suit the immediate needs of the system.

The technique of memory management has limited relevance to the small single user system, but is a very powerful technique, developed originally for large computers, to permit the optimum allocation of memory resources among competing tasks or users.

Since the segments recognised by the Z8010 have assignable attributes, memory protection schemes can be easily arranged in system software. Any request to access a segment illegally then causes a TRAP exception to the Z8001, and possible causes could be: writing to a read-only segment, a user trying to access a system (privileged) segment, or a detected segment overflow condition.

Another useful and original member of the Z8000 peripheral family is the Z8038 FIO First-In-First-Out (FIFO) buffer unit. This 40 pin device contains a 128 byte FIFO RAM which can be used to synchronise I/O or interprocessor transfers by accepting data from one device and holding it until it can be accepted by a destination device. Empty, Full, and Wait/Request control lines are available to manage Z8038 transfers.

## APPLICATIONS

The Z8001 processor is powerful, well supported by hardware, but unfortunately not yet as popular as the 8086 or the 68000. Perhaps this last fact will change when Commodore bring out their expected Z8000 based 16 bit personal computer, but meanwhile the application software base is very limited.

My personal feeling is that the Z8000 family is not the best choice if you have a data processing application in mind, but it might be a suitable candidate for a 16 bit control application thanks to its high speed, low cost, and powerful interrupt and peripheral structure.

For most small applications the simpler Z8002 with its 64K byte address range will probably be sufficient, but Z80 users should beware the non-compatibility of the Z8000 family with existing Z80 software. My advice would be to wait a little longer for the forthcoming Z800 family which offers *compatible* 16 bit power!

all in your  
**OCTOBER**  
issue!



# EXPANDING the VIC 20

The excellent VIC 20 from Commodore is unfortunately supplied with a very limited memory. We show how to build a motherboard and various plug-in RAM and ROM cards, thus expanding the memory and allowing the simultaneous use of such facilities as VICMON and SUPER EXPANDER.

## Introduction to Digital Electronics O & A LEVEL Part One

This series has been written and designed by two very experienced authors to complement the digital section of both the O and A level electronic courses.

It will also be an ideal introductory point for any electronic hobbyists or newcomers who have an interest in electronics and wish to obtain a firm foundation on which to build their knowledge. All that is required for the course is an elementary understanding of basic electricity (a familiarity with voltage, current and resistance), together with an understanding of basic wiring.



## Electronics in Photography

This feature article takes a look at photographic techniques from their birth some 150 years ago to the present day and beyond. Particular emphasis is paid to the role played by electronic technology in this infinitely interesting field.

## RELAXOMETER

It is a fact that most people do not know how to relax. This instrument simplifies the task as it provides continuous feedback of one's physical and mental state so that controlled relaxation can be achieved.

PRACTICAL

# ELECTRONICS

OCTOBER ISSUE WILL BE ON SALE FRIDAY, SEPTEMBER 2nd

# Guitar Active Tone Controls

A. Scragg

UNTIL quite recently most tone controls on an electric guitar consisted of a pot and capacitor configured as a low pass filter, with a 6dB per octave slope. This arrangement, although simple and reliable, does not give a large tonal range, tending to be dull and uninteresting with the treble thus removed. Increasingly, however, guitars and basses, particularly those of oriental origin, are being equipped with active tone controls giving separate treble and bass adjustment. This gives much better and variable sounds and has the additional advantage of buffering the guitar output, enabling a long cable to be used to the amplifier/mixing desk without noise pickup and the reactive loading reducing the treble response. This results in a crisper, punchier sound.

For those not wishing (or able) to invest in a new guitar simply for the benefit of active circuitry, this design is small enough to be built into the guitar body, or as a separate unit, into a small instrument case.


## CIRCUIT DESCRIPTION

The active tone controls circuit provides volume treble and bass controls with a switch giving extra treble boost, which is very useful for solos. For best performance the guitar pickup needs to see a high impedance, this is provided by a bootstrapped input amplifier, which also has a volume control incorporating a loudness circuit, which boosts the treble at low volume settings to give the impression of constant tone balance throughout the volume range—without this the sound becomes flat and uninteresting at low levels. This is due to the characteristics of the human ear which is less sensitive to the high frequencies of quieter sounds.

The input amplifier is followed by the tone control circuitry—which is of the active treble and bass type. This circuitry has a nominal voltage gain of one with 20dB of boost and cut at 40Hz and 10kHz. The output of the tone control circuit provides the low impedance drive to the amplifier cable. The circuit is automatically turned on when the output jack is plugged in and there is also a facility for charging a NiCad battery, if fitted, by using a stereo plug in the same socket. Fig. 1 shows the plug connections required for normal and charging use.
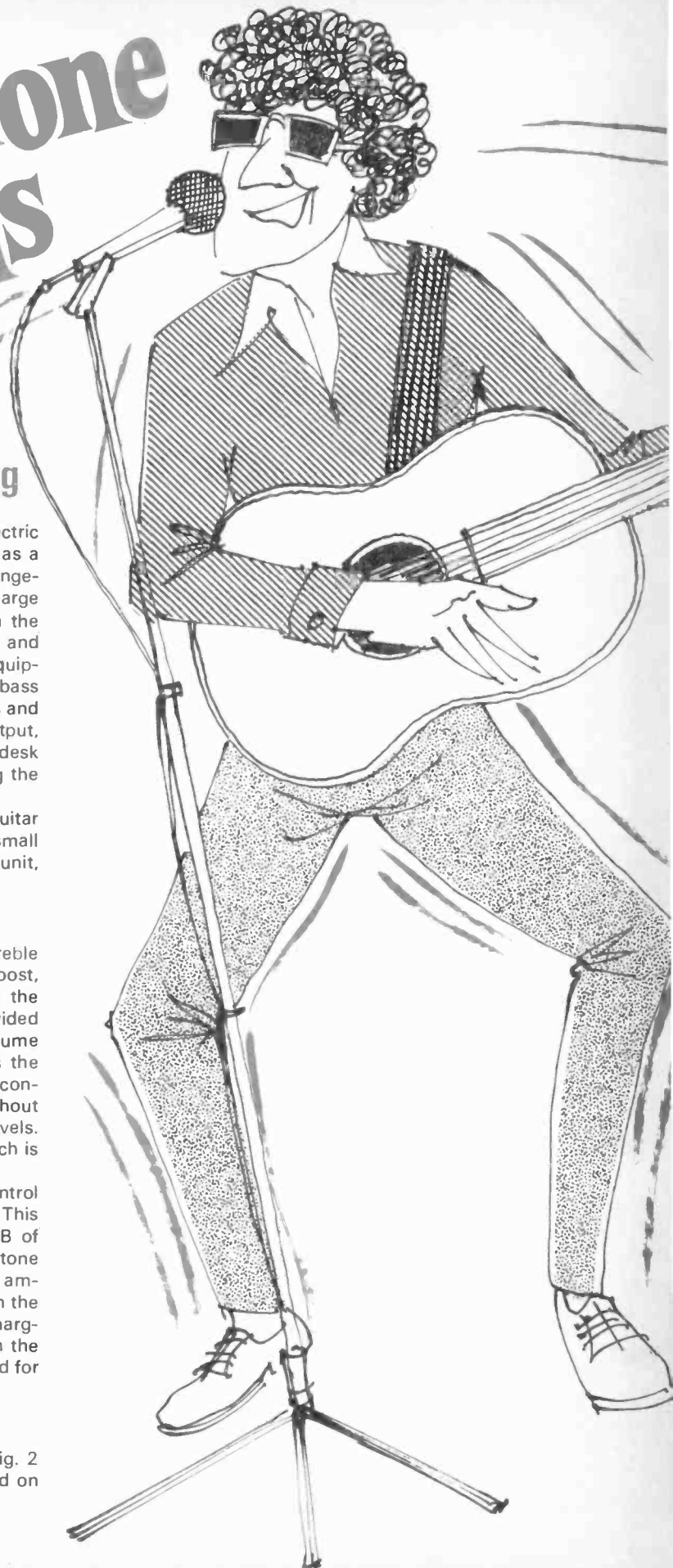
## HOW IT WORKS

The circuit of the active tone controls is shown in Fig. 2 and can be considered as three functional blocks based on the three i.c.s. They are:



1. A high input impedance amplifier incorporating the loudness, volume control and the treble boost circuitry.
2. A conventional Baxendall type active tone control circuit also providing the output.
3. A negative supply voltage generator.

The most unusual feature of the circuitry is the third functional block—the negative supply generator. The obvious question is why is it necessary at all as single supply op amp circuits could easily be used. There are two main reasons why. Firstly, the op amp used for the input amplifier is the Signetics NE 5534A (chosen for its excellent low noise audio performance) which requires a minimum supply voltage of  $\pm 3V$ . Using a PP3 battery of nominally 9V output, the battery life would be relatively short if used to power the circuit directly as its voltage soon decays from its nominal value, also the output from the guitar pickup has a very large dynamic range with large transients as the strings are played, so to avoid distortion due to op amp clipping as large a supply voltage as possible should be used. Another advantage of using positive and negative power supplies is that the signal path is referred to 0V avoiding the large switch on thump as coupling capacitors charge up. The supply currents are effectively separated from the signal path, reducing earth loop noise.



The negative supply generator uses an NE555 timer i.c. in its astable mode producing a square wave output at about 30kHz. This is outside the audio bandwidth to avoid any breakthrough to the output being heard.

The astable period is set by R7, R8, and C7 being the time for C7 to charge up to  $\frac{2}{3}V_{cc}$  through R7 and R8 and discharge to  $\frac{1}{3}V_{cc}$  through R8. The frequency of oscillation is given by:

$$f = \frac{1}{0.693(R7 \times 2R8)C7}$$

The output of the astable is a.c. coupled and clamped by C9 and D1 respectively. This is rectified and smoothed by D2, C10 and C13 resulting in a negative supply of 6V. The voltage loss is due to the two diode 0.6V drops and the fact that the 555 output swing is not to its supply voltage; however, with this supply an output signal of 3V peak is

Fig. 2. Circuit of active tone controls

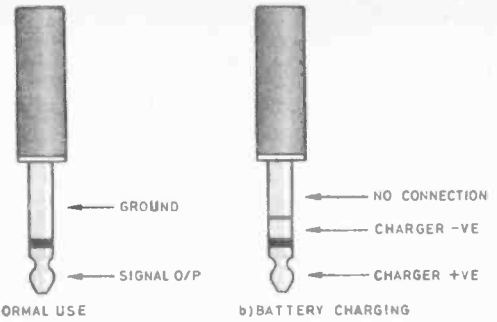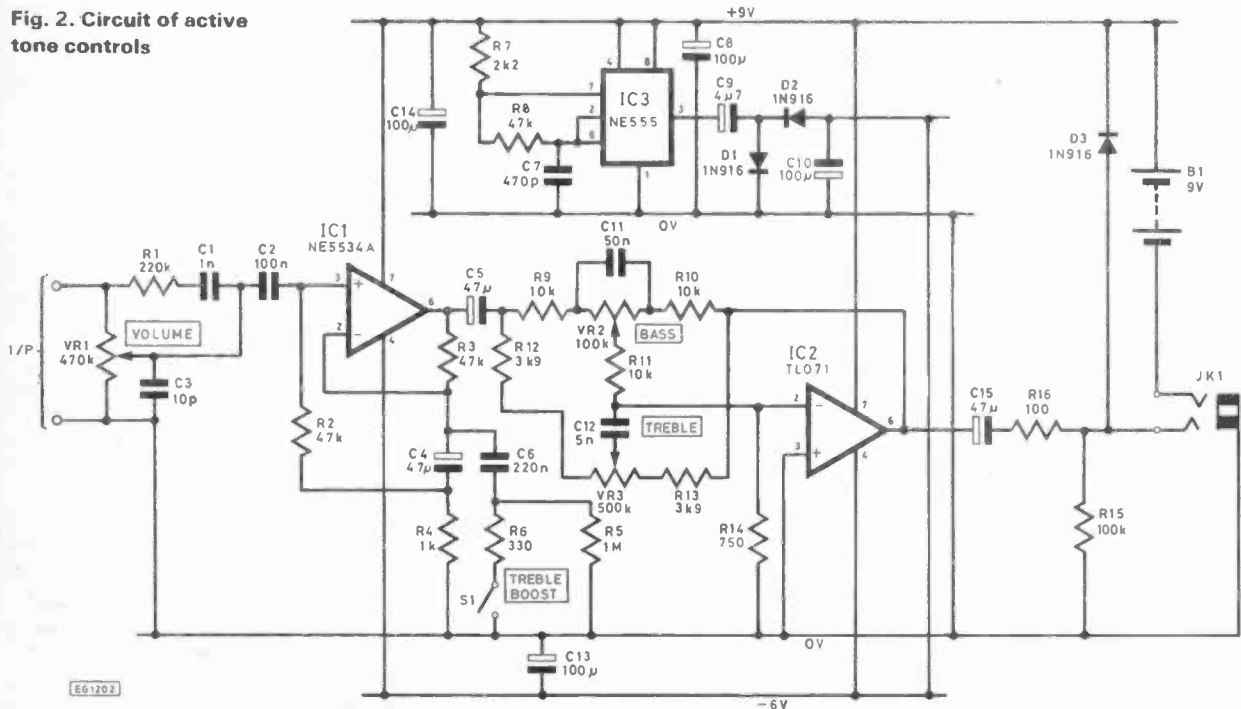

EG1244

Fig. 1. Jack plug connections

available, which is quite sufficient!

While on the subject of power supplies, the battery is connected to the circuit by inserting the mono jack plug of the guitar lead into the stereo (three pole) output jack socket; this connects the outer two poles together, completing the circuit. Additionally, diode D3 links the output to the supply line; in normal operation this is reversed biased and therefore high impedance; however, if a rechargeable battery is used a stereo jack plug can be used to charge the battery *in situ*. The charger positive is connected to the inner pole, negative to the centre pole. In this mode the active tone control circuit is not connected. The charger used should be of the constant current type—10mA in the case of a PP3-type battery. This is very convenient if the circuit is installed in the guitar. As the supply current is about 10mA it makes good sense to use a rechargeable battery, especially if the guitar is used often, as a dry cell will only last about ten hours continuous running.

## SPECIFICATIONS

Signal-to-noise ratio	64dB (referred to 5mV i/p)
Voltage gain	X48 (33dB)
Maximum signal output	3V peak
Supply current	10mA
Bass control	$\pm 20$ dB at 40Hz
Treble control	$\pm 20$ dB at 10kHz

The next functional block is the amplifier. VR1 is a simple volume control, R1, C1 and C3 give the loudness effect—being shorted out when the control is at full volume. C2 a.c. couples the input to stop the op amp bias current causing noisy pot operation. The amplifier itself is a bootstrapped non-inverting type. The purpose of the bootstrapping is to give a very high input impedance to the signal while providing a low impedance at d.c. so that the op amp bias current does not result in a large offset voltage. The circuit works as follows—initially with the treble boost switch open.

At d.c. capacitor C4 is an open circuit, giving the equivalent circuit shown in Fig. 3(a). It can be seen that the amplifier has unity gain and the input impedance at both op amp inputs is approximately the same (R3 and R2 + R4). They are arranged like this to balance out the bias current generated offset as far as possible so that in the worst case only a few millivolts of offset appears at the output.

At audio frequencies C4 is large enough to appear to be a short circuit. The equivalent circuit becomes that of Fig. 3(b). The gain and input impedance of this circuit are given by the following equations:

$$\text{Gain} = 1 + \frac{R3}{R4} \quad \text{Input impedance} = \frac{R2A}{\left(1 + \frac{R3}{R4}\right)}$$

## COMPONENTS . . .

### Resistors

R1	220k
R2, R3	47k
R4	1k
R5	1M
R6	330
R7	2k2
R8	47k
R9, R10, R11	10k
R12, R13	3k9
R14	750
R15	100k
R16	100
All 10% 1/4W carbon	

### Capacitors

C1	1n	ceramic
C2	100n	ceramic
C3	10p	ceramic
C4	47μ	10V bea
C5	47μ	10V bea
C6	220n	C280
C7	470p	ceramic
C8	100μ	10V bea
C9	4μ7	10V bea
C10	100μ	10V bea
C11	50n	C280
C12	5n	ceramic
C13	100μ	10V bea
C14	100μ	10V bea
C15	47μ	10V bea

### Semiconductors

D1, D2, D3	1N916
IC1	NE5534A
IC2	TL071
IC3	NE555

### Potentiometers

VR1	470k lin
VR2	100k lin
VR3	500k lin

### Miscellaneous

- S1—SPST miniature toggle switch
- JK1—1/2in stereo jack socket

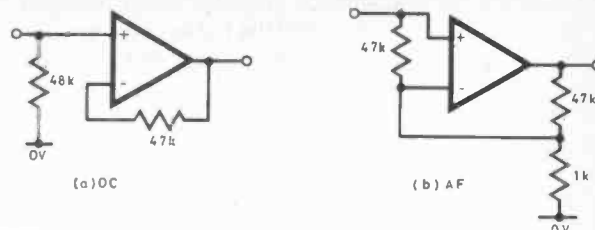


Fig. 3. Input amplifier equivalent circuits

Where A is the open-loop voltage gain of the op amp.

From the above equations it can be seen that the input impedance is very large and VR1 therefore defines the input impedance of the circuit as a whole. With the specified values the input impedance is 470k and the gain is x 48, but can be adjusted as required by altering R2 and R3.

When the treble boost switch is closed the feedback is reduced at high frequencies, giving a brighter, louder sound. R5 is used to stop thump when the switch is closed due to C6 charging up, through its own leakage resistance.

C5 a.c. couples the output of this stage to a Baxendall type active tone control circuit giving 20dB cut and boost at 40Hz and 10kHz.

## CONSTRUCTIONAL DETAILS

Tantalum electrolytic capacitors are specified for their good electrical performance and small size. If the pots used are p.c. mounting types, they can mount directly on to the board; if not, Harwin pins can be used on the board and the pots connected to these. The treble boost switch, input and output are connected to these. The treble boost switch, input and output are connected via flying leads, as is the battery.

The prototype was built into the body of the guitar but could equally well be built into a small instrument case using a mono jack socket for the input. ★

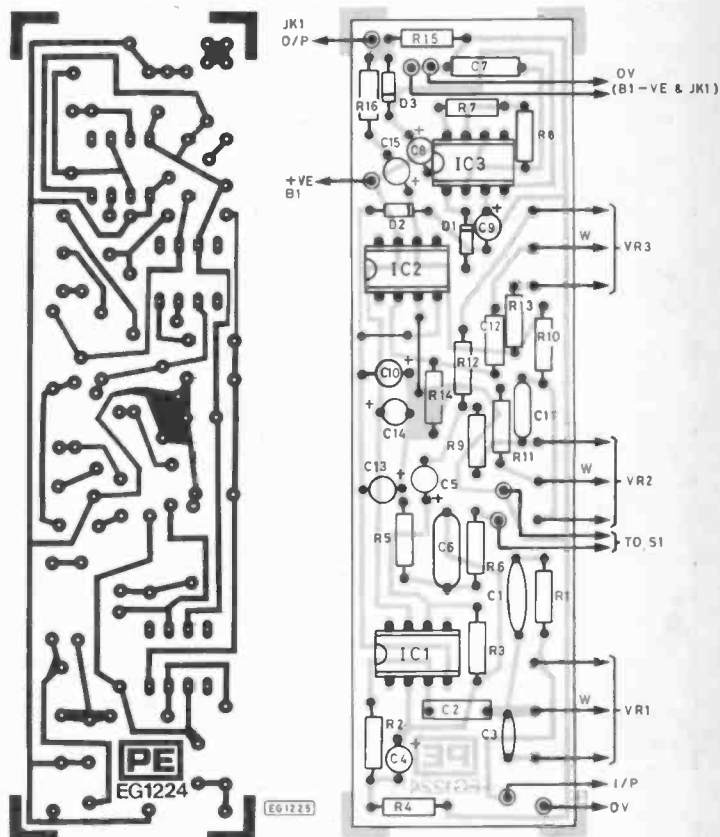


Fig. 4. Board and component layout



# Ground Communication System

R.A. PENFOLD

THE idea of using the ground as a medium for communication is by no means a new one, and dates back as far as World War 1 at least. The basic arrangement for a communications system of this type is shown in Fig. 1.

An ordinary audio power amplifier driven by a microphone is all that is needed at the transmitting end of the system, plus two earthing rods which are placed in the ground some distance apart. The earth usually provides a fairly low resistance path between the two rods, but this resistance is actually made up from an infinite number of paths through the earth from one rod to the other. Most of the current flow between the rods takes a more or less direct route from one rod to the other, but some of the signal takes a much longer route and can therefore be detected some way away from the transmitting earthing rods. However, the longer the route taken by the signal, the greater the resistance it has to overcome, and the weaker the signal that is available due to the lower current flow. All that is needed to pick up the signal is another set of earthing rods feeding a pair of headphones or an amplifier and loudspeaker, but the inefficiency of this system gives only a fairly limited operating range.

Systems of this type generally only operate up to an absolute maximum range of about two miles, and often the maximum attainable range will be very much less than this. This still gives an adequate range for some purposes, and ground communications is certainly an interesting subject for the experimenter. A novel feature of ground communications is that it can be used for subterranean communications, unlike normal radio communications.

## BLOCK DIAGRAM

Fig. 2 shows in block diagram form the simple ground communications system featured in this article. The transmitter consists of a microphone feeding a preamplifier stage, which in turn drives a power amplifier. A gain control is used in conjunction with an l.e.d. level indicator to ensure that the power amplifier is fully driven but not seriously overloaded.

The power amplifier is a bridge type, and this is necessary as a reasonably large output voltage swing is needed in order to give usable results. The amplifier uses a bridge amplifier integrated circuit which is normally used as a power booster for a car radio, giving an output power of about 18 to 20 watts r.m.s. into a 4 ohm impedance loudspeaker. In this case the output power is very much lower than this, and is likely to be in the region of 1 watt r.m.s. since the impedance across the earthing rods is

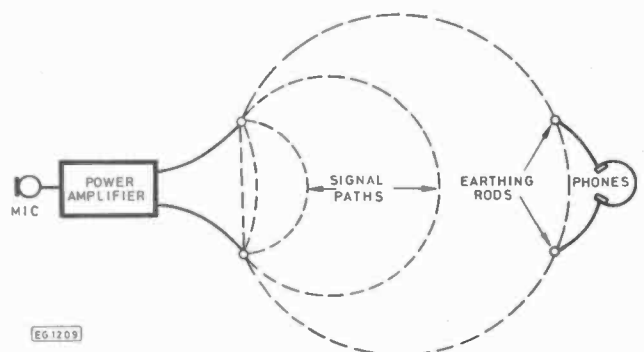


Fig. 1. Ground communication basic system

typically between 50 and 100 ohms. This relatively low output power gives the unit a reasonably low current consumption so that battery operation is possible.

The receiver uses a high gain preamplifier followed by a 200Hz highpass filter and a small audio power amplifier. The latter drives a miniature loudspeaker, or medium/high impedance headphones can be used if preferred. The purpose of the highpass filter is to combat mains hum which always seems to be present, and can be very strong if the system is used very near to houses or other places where mains powered equipment is used (and earthed). The filtering is only partially successful as there are quite strong harmonics on the 50Hz mains signal. With these harmonics spaced at 50Hz throughout the audio band, it is not really feasible to filter them out completely. A high slope 200Hz highpass filter gives a worthwhile reduction without affecting the intelligibility of the received signal. It does not seem to be possible to use a balanced input and a phasing technique to reduce mains hum.



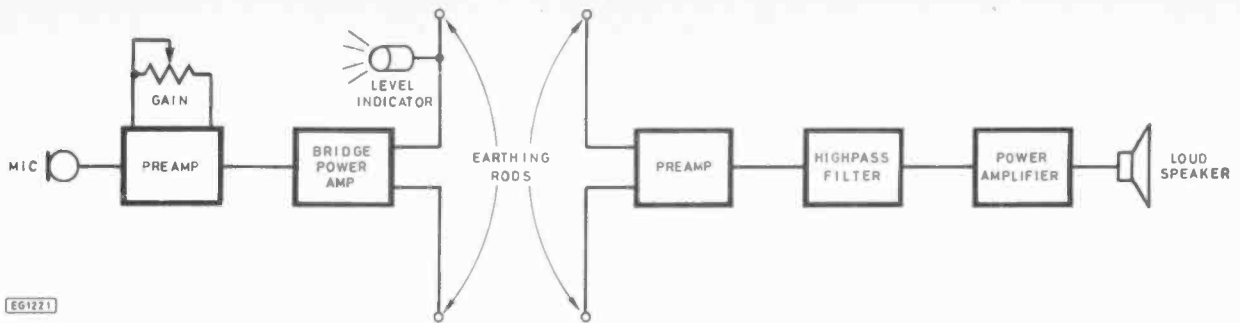


Fig. 2. The system in block diagram

It may seem wasteful to use separate circuits for the transmitter and the receiver when both are basically just high gain audio power amplifiers. However, circuits using a single amplifier with the loudspeaker used as a microphone in the transmit mode all provided mediocre results both in terms of audio quality and range, and a two amplifier circuit was therefore adopted for the final unit.

### TRANSMITTER CIRCUIT

Fig. 3 shows the circuit diagram of the transmitter. The power amplifier uses an HA1388 bridge amplifier which will give over 20 volts peak to peak at the output using a nominal 12 volt supply. C9 and C10 are bootstrapping capacitors which help to maximise the output voltage swing from the two power amplifier. C11 and C12 are needed to aid stability while D2 and its associated components are used to give an indication of the output signal level. D2 will be forward biased on one set of half cycles, but only if the

peak output voltage exceeds about 7 volts, since about 5.1 volts is needed to force D1 into conduction, while approximately 1.9 volts further is needed to overcome the threshold potential of D2. Thus about 14 volts or so peak to peak is needed at the output before D2 will light up, and the amplifier will be fully driven or nearly so provided D2 lights up when someone speaks into the microphone.

The voltage gain provided by IC1 is quite high and only about 10 millivolts r.m.s. is needed at the input (pin 3) in order to provide maximum output. This is still not sufficient to enable the circuit to be driven from a normal microphone, and TR1 is therefore used as a common emitter preamplifier stage which boosts the gain of the circuit by a factor of about one hundred. This enables the unit to be used with inexpensive low impedance (200 or 600 ohm) dynamic microphones. C13 rolls-off the high frequency response of the preamplifier which helps to prevent instability and also gives an improvement in the signal to noise ratio of the circuit.

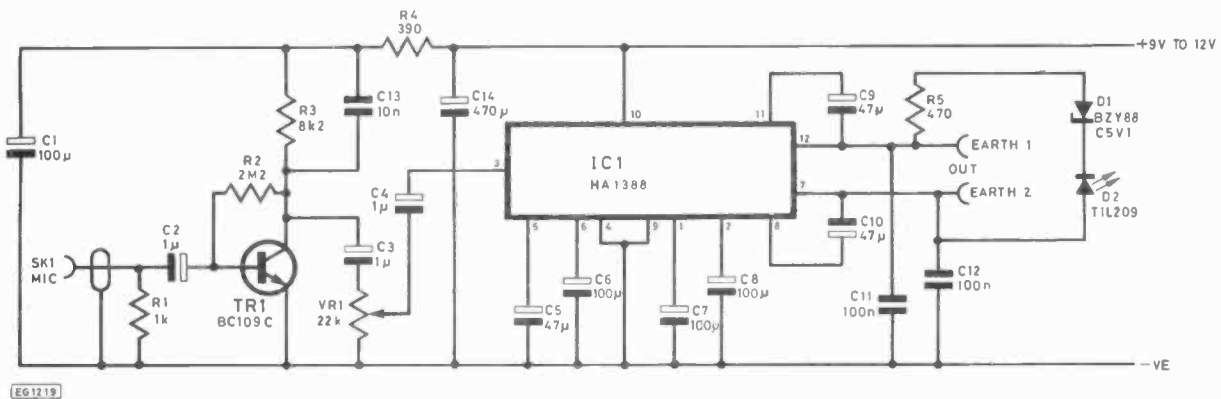


Fig. 3. The transmitter circuit. In use the current consumption can be in excess of 100mA so the battery should be a PP9 or six to eight HP7s. Ideally Ni-Cad cells are to be preferred


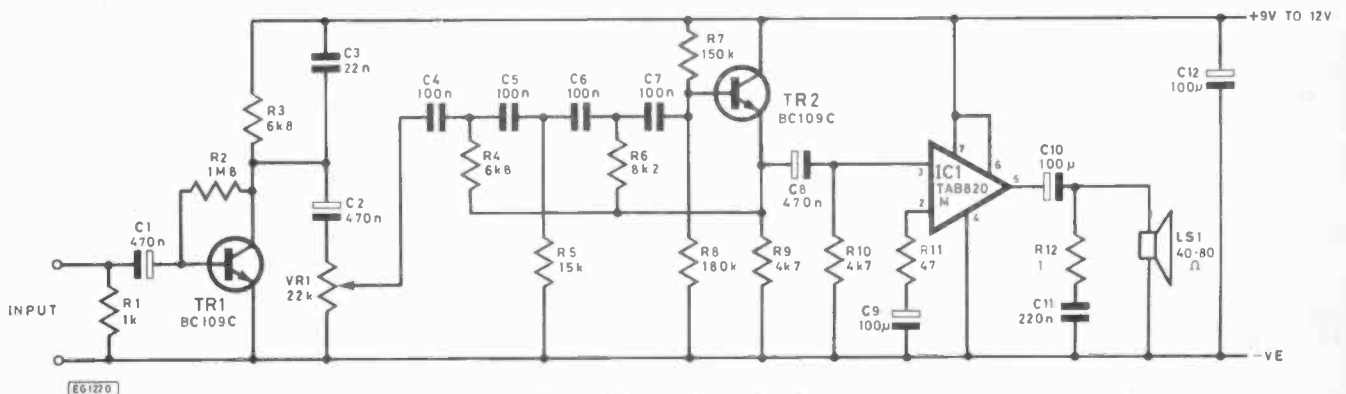
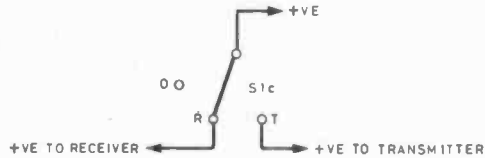


Fig. 4. The receiver circuit

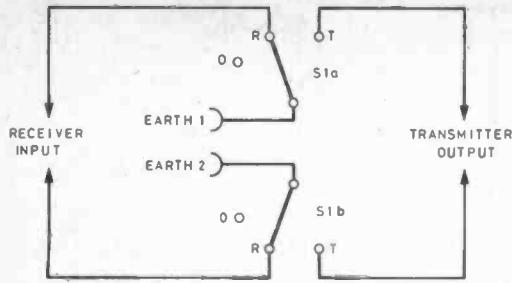

EG1222

Fig. 5. Transmit/Receive switching


### RECEIVER CIRCUIT

The receiver circuit uses a preamplifier which is similar to that employed in the transmitter, as will be apparent from the circuit diagram of Fig. 4.

From the output of the preamplifier the signal is passed via volume control VR1 to the highpass filter. This is a conventional active 24dB per octave type which uses TR2 as the unity voltage gain buffer stage and has a cutoff frequency of approximately 200Hz. Low frequencies do not significantly contribute to the intelligibility of a voice signal, and the filtering does not have any detrimental effect on the signal. There is little output from the transmitter below 200Hz anyway.

The power amplifier is a TBA820M (IC1) which gives an output power of about 150 milliwatts into a high impedance loudspeaker, and this gives a perfectly adequate volume level for this application. R11 is a feedback resistor which sets the closed loop voltage gain of IC1 at approximately 130 times. This gives the circuit an input sensitivity of about 2 millivolts r.m.s. for maximum output, and this is about the highest practical sensitivity.

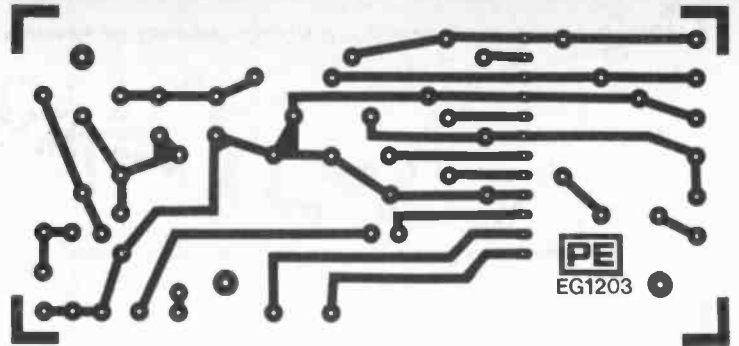For two way communications it is obviously necessary to have both a transmitter and a receiver plus transmit/receive switching at each end of the system. Suitable switching is shown in Fig. 5.




### CONSTRUCTION

The system can be built as separate transmitter and receiver units for one way communications, or as transceiver units for two way communications, but it will be assumed here that the system is constructed as two transceivers. The transmitter and receiver circuits are assembled on separate printed circuit boards which are shown in Fig. 6 and Fig. 7 respectively. Both boards are quite straight forward to construct, and the only unusual component used is the HA1388 (IC1 in the transmitter). This has a single line of twelve pins, but pin 1 is indicated in the standard fashion by a small dot or indentation on the body of the component. The HA1388 has a heat-tab which can be bolted to a heatsink, but in this application the output power is not likely to be sufficient to merit the fitting of even a small heatsink. This integrated circuit has comprehensive protection circuits incidentally, including a thermal shutdown circuit.

A metal instrument case measuring about 200 x 125 x 75mm will comfortably accommodate all the components including the batteries. The general layout of the unit can be seen from the photograph but is not especially critical. Miniature loudspeakers do not usually have provision for screw fixing and it will almost certainly be necessary to glue LS1 in position behind a grille made by drilling a matrix of small holes. The connections to the earthing rods can be made by way of a couple of 4mm sockets fitted on the rear panel of the case, plus a couple of leads fitted with 4mm plugs.

Once all the components have been installed in the case the point to point wiring can be added. The wiring to S1 is illustrated in Fig. 8.

Fig. 6. Constructional details of the transmitter board with the printed circuit shown top right

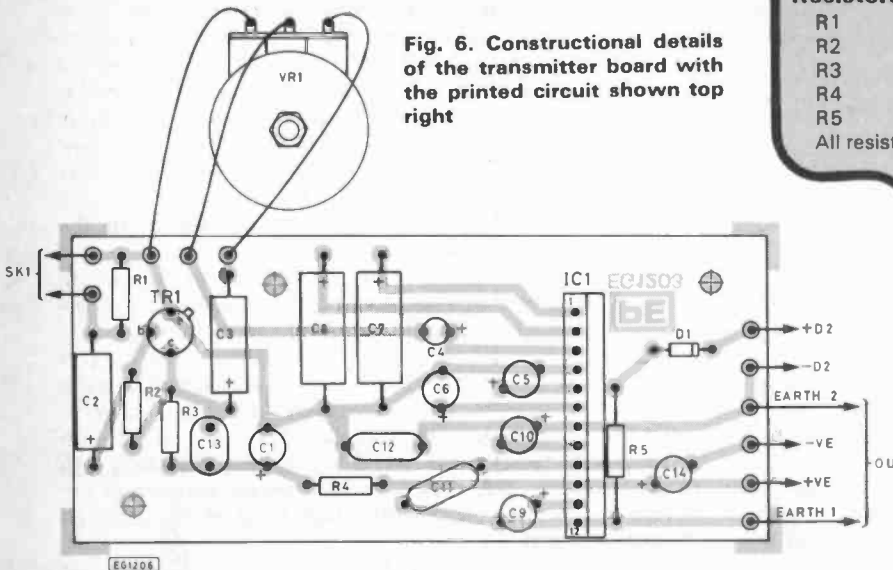

EG1206

### TRANSMITTER BOARD

#### Resistors

R1	1k
R2	2M2
R3	8k2
R4	390
R5	470

All resistors 1/4W 5% carbon film

#### Semiconductors

IC1	HA1388
TR1	BC109C
D1	BZY88C5V1
D2	TIL209 etc.

#### Capacitors

C1	100µ 16V radial electrolytic
C2, 3	1µ 63V axial electrolytic (2 off)
C4	1µ 63V radial electrolytic
C5, 9, 10	47µ 10V radial electrolytic (3 off)
C6	100µ 10V radial electrolytic
C7, 8	100µ 10V axial electrolytic (2 off)
C11, 12	100n polyester
C13	10n mylar
C14	470p 16V radial electrolytic

#### Miscellaneous

SK1	3.5mm jack socket
VR1	22k log. carbon
Printed circuit board, low impedance dynamic microphone, control knob, Veropins, wire, etc.	



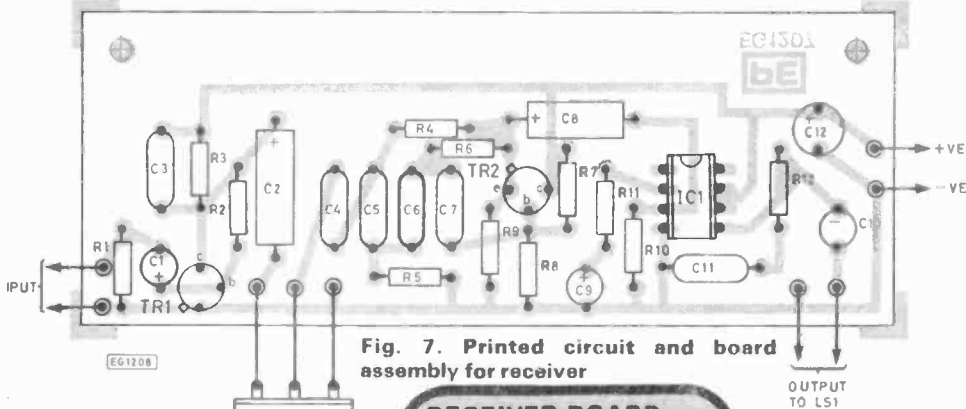
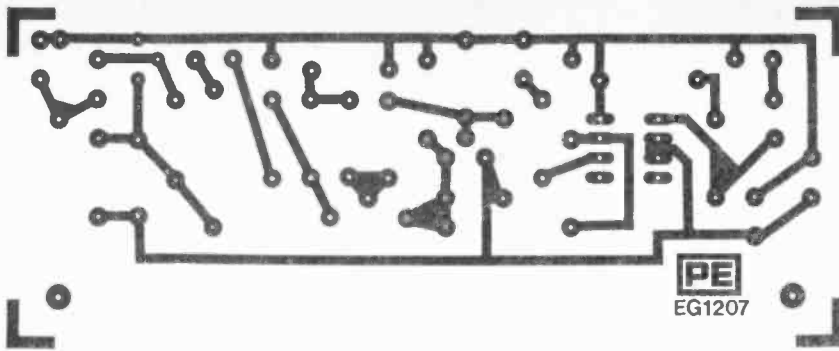


Fig. 7. Printed circuit and board assembly for receiver

### RECEIVER BOARD

#### Resistors

R1	1k
R2	1M $\Omega$
R3, 4	6k8 (2 off)
R5	15k
R6	8k2
R7	150k
R8	180k
R9, 10	4k7 (2 off)
R11	47
R12	1

All resistors  $\frac{1}{4}$ W 5% carbon film

#### Semiconductors

TR1, 2	BC109C (2 off)
IC1	TBA820M

#### Capacitors

C1	0.47 $\mu$ 63V radial electrolytic
C2, 8	0.47 $\mu$ 63V axial electrolytic (2 off)
C3	22n polyester
C4, 5, 6, 7	100n polyester (4 off)
C9, 10	100 $\mu$ 10V radial electrolytic (2 off)
C11	220n polyester
C12	100 $\mu$ 16V radial electrolytic

#### Miscellaneous

VR1	22k log. carbon
LS1	40 to 80R impedance miniature loud-speaker

Printed circuit board, control knob, Veropins, wire, etc.

### ADDITIONAL FOR TRANSCIVER

S1—3 way 4 pole rotary switch, control knob, two wander sockets, case, battery connector, wire, etc.

### IN USE

Results obtained with the finished system are largely dependent on factors such as the efficiency of the earths used, the conductivity of the soil, and the level of mains hum present, rather than on the level of performance provided by the transceivers. It is therefore impossible to predict how great or restricted the range obtained using the system will be. However, in order to obtain good results it is essential to observe a few simple rules.

The most important of these is to place the two earths as far apart as is reasonably possible. Placing them only a metre or so apart is unlikely to give usable results, and a

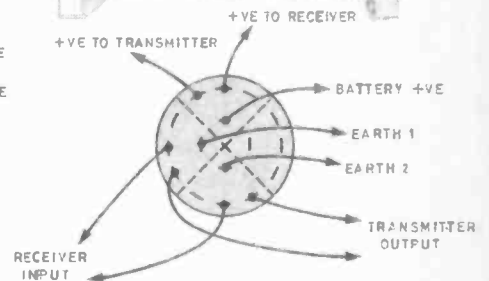
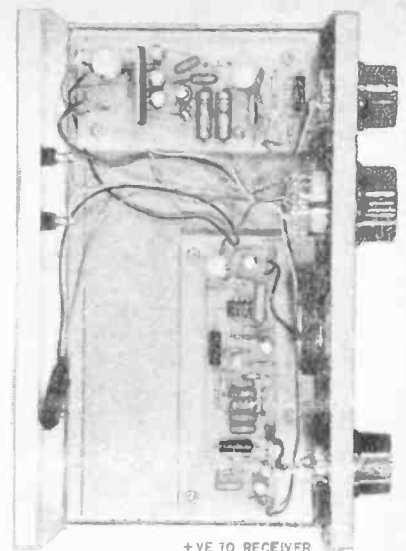


Fig. 8. Wiring to Transmit/Receive switch S1

spacing of around ten metres will give vastly superior results. Wide spacing of the earths seems to be beneficial for both transmission and reception.

It is essential for the earths to make good contact with the soil. Early experiments were made using earths that consisted of small sheets of metal pushed into the soil, but this gave a very limited range indeed. Much better results seem to be produced using metal rods about 12 to 30mm in diameter and about one metre long hammered as deep as possible. Ideally these should be made of a metal that is resistant to corrosion.

For best results the earths should be positioned so that the four of them roughly form a rectangle (as in Fig. 1 which was discussed earlier). At the other extreme, having all four earths roughly in line will give very poor results and would probably result in the system failing to work at all.

Mains hum can be quite strong in built-up areas, and it might be worthwhile experimenting with the earthing rods in various positions in an attempt to minimise hum. It will often be the level of this mains interference that determines the maximum usable range of the system, but even where mains hum is very strong, it should be possible to obtain a range of 50 to 100 metres if efficient and well placed earths are used so that a strong signal is produced by the transmitter. In the interest of minimising any interference received it is advisable to have the leads from the transceiver to the earths as short as possible.

Radio interference might be a problem at times, but adding a capacitor of a few nanofarads in value across the input/output sockets should eliminate this interference.

It is important to set the microphone gain control correctly, and with the aid of l.e.d. indicator D2 this is quite easy. The gain control should be advanced just far enough to make D2 flash on signal peaks, but it should not light up brightly and continuously while someone is speaking into the microphone. This would result in severe clipping at the output of the transmitter with a high level of distortion on the output signal.

# Getting to GRIPS with MAC



## UK SATELLITE SYSTEM EXPLAINED

A NUMBER of European countries, including the UK, plan to have Direct Broadcast Satellite (DBS) systems operational or pre-operational by 1985/86. The UK plans include the two-channel UNISAT being developed by British Aerospace for leasing to the BBC. UNISAT will weigh about 1400kg with solar generator panels that should still be generating 1.7kW at the end of its 10 year design life.

This electrical power is sufficient to provide only two DBS channels to the full international standards agreed in 1977 to permit programmes to be received virtually anywhere in the British Isles by means of a small dish aerial of about 70cm (2 feet) diameter, mounted on roof-tops or at ground level, or anywhere which has direct line-of-sight to the satellite to be positioned 36,000km above the Equator at 31° West.

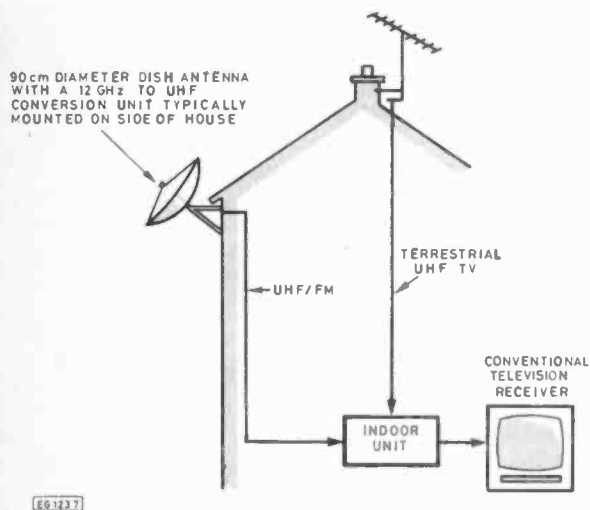


Fig. 1. Indoor unit selects satellite channel and converts satellite television standard to terrestrial television standard

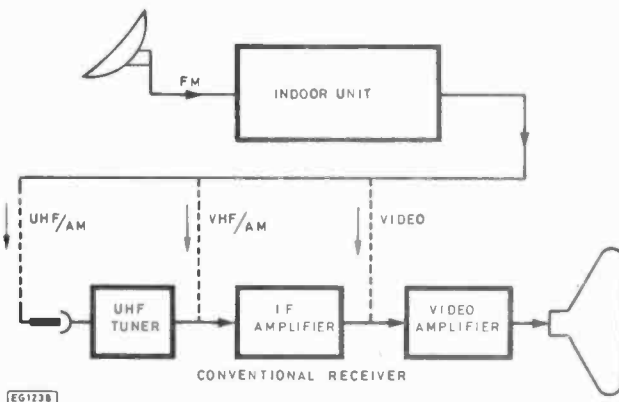


Fig. 2. Basic receiver options

### DISH DEBATE

There is some debate about how many viewers will have a suitable place for their own dish aerial. Some will find trees or other buildings blocking their direct reception, and those living in flats may not have access to the roof or live on the wrong side of the building for a wall-mounted aerial. For such viewers, satellite channels could reach them through a communal or "syndicate" aerial mounted on the roof or from a master-aerial system in conjunction with a cable network. Economically there are advantages in communal and cable systems since the signals could be distributed in a form suitable for use with a standard television receiver. Those with their own DBS aerial will need a 12GHz to UHF conversion unit mounted with the aerial unit and also an "indoor unit" to provide a signal suitable for use with the receiver, preferably linking into the receiver at video frequency (RGB signals) as shown in Fig. 1 or by using a UHF modulator and the aerial input socket. It can be seen from Fig. 2 that there are a number of basic receiver configurations which could be adapted to interconnect a 12GHz FM receiver/adaptor with a conventional UHF/AM receiver. An adaptor providing a UHF/AM output could be connected directly to the aerial

# PAT HAWKER

socket of an existing receiver. Alternatively an output at the IF of the main receiver could feed into the IF amplifier section. Output at video frequency is particularly attractive in that it eliminates distortion and spurious signals which are inherent in low-cost modulators and multiple-conversion receivers.

In practice a single DBS transmitter should be receivable in about 98-99% of homes. The limited electric power available at the satellite has an important effect on the form of transmission. For terrestrial TV the vision signal is transmitted as an amplitude-modulated vestigial sideband signal (VSB). In Europe the complete 625-line television signal, including the frequency-modulated mono audio channel, fits into an 8MHz channel (Fig. 3). All these systems use frequency interleaving in order to encode the luminance (black and white) picture information with the chrominance (colour) information, the method differs in the PAL and SECAM systems. The third main colour-encoding system NISC, is not used in Europe but is used in a number of countries having 525-line systems. In all these three colour-encoding systems a subcarrier is used to carry the chroma information. For 625-line PAL the colour subcarrier is at the precise frequency 4.4336MHz.


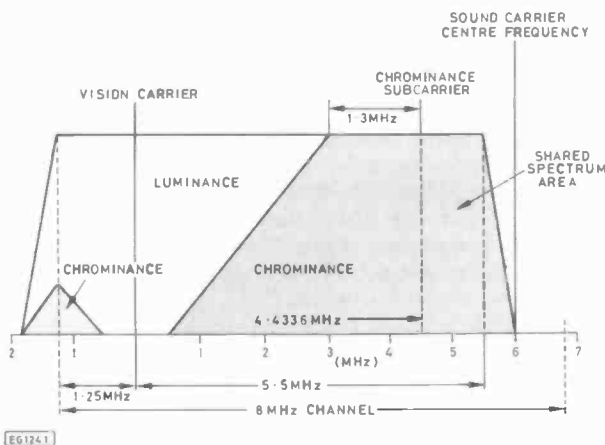


Fig. 3. The frequency bands occupied by the colour picture components and sound signals from an ideal transmitter

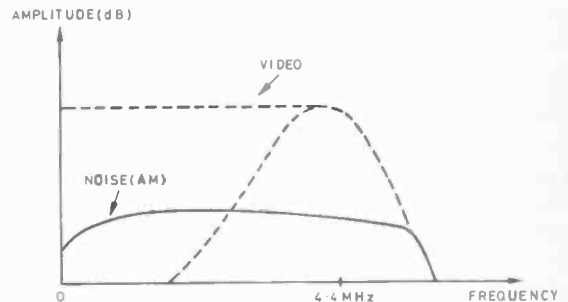


EG1239

Fig. 4a. The noise spectra associated with AM signals

The use of a colour subcarrier means that the chroma information is converted upwards in frequency, in other words chroma is transmitted between roughly 3 to 5.7MHz—frequencies shared with luminance information of fine detail patterns. The result of this sharing can clearly be seen on domestic receivers in the form of cross-colour effects, the spurious colours seen on striped clothing, patterned suits, shirts and ties, etc. This is because to the receiver the luminance “pattern” looks like chroma information and is amplified in the chroma circuits. Conversely problems can arise from chroma information being mistaken for luminance. This problem is inherent in all conventional colour-encoding systems although it tended often to pass unnoticed in the first decade of colour when the sensitivity and resolution of studio cameras etc tended to be insufficient to exploit the full potential of the system.

### TRIANGULAR NOISE SPECTRUM

However when a subcarrier colour-encoding system is used with a frequency-modulated vision signal there is a further problem that does not arise with amplitude-modulation. This is the so-called triangular noise spectrum. With an FM signal the noise rises with frequency, there is thus a higher noise content with chroma information transmitted at around 4.4MHz than when it is transmitted at its “baseband” frequency. For this reason a 625-line PAL picture transmitted over satellite circuits tends to suffer noise or “graininess” noticeable in the more highly saturated large colour areas shown in Figs. 4a and 4b.

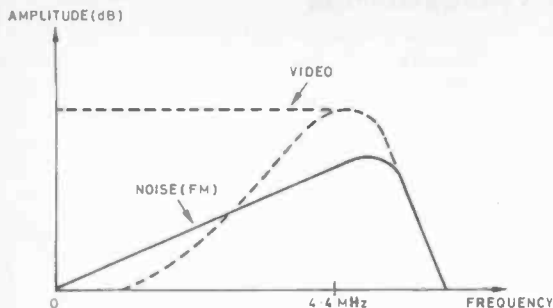

EG 1240

Fig. 4b. The noise spectra associated with FM signals

### MULTIPLE SOUND CHANNELS

There is a further important difference envisaged between conventional terrestrial TV transmissions and DBS—the carrying of multiple sound channels. In the first place there is the wish to transmit high-quality stereo with sufficiently low cross-talk to permit these channels to be used for such purposes as simultaneous multilingual broadcasts or the carrying of totally independent “radio” programmes and also, if required, data transmissions such as an extended-capacity Teletext service, optional subtitling for the hard-of-hearing etc. With modern technology it is logical to use a digital system capable of extremely high quality. In terrestrial networks a problem with digital transmission is vulnerability to multipath “echoes” but digital, via satellite appears to be virtually free of such problems. For the first time broadcast audio can be planned to standards significantly better than existing VHF/FM stereo.

The UK, acting on the recommendations of the Advisory Panel on Technical Transmission Standards for Direct Broadcasting by Satellite (chaired by Sir Antony Part), has adopted a transmission system that takes into account not only the technical factors outlined above but also the advantages to industry and to viewers in making extensive use of LSI technology. The system C-MAC was developed and proposed

CHANNEL NO.	ASSIGNED FREQUENCY (MHz)	CHANNEL NO.	ASSIGNED FREQUENCY (MHz)
1	11727.48	21	12111.08
2	11746.66	22	12130.26
3	11765.84	23	12149.44
4	11785.02	24	12168.62
5	11804.20	25	12187.80
6	11823.38	26	12206.98
7	11842.56	27	12226.16
8	11861.74	28	12245.34
9	11880.92	29	12264.52
10	11900.10	30	12283.70
11	11919.28	31	12302.88
12	11938.46	32	12322.06
13	11957.64	33	12341.24
14	11976.82	34	12360.42
15	11996.00	35	12379.60
16	12015.18	36	12398.78
17	12034.36	37	12417.96
18	12053.54	38	12437.14
19	12072.72	39	12456.32
20	12091.90	40	12475.50

Table 1. Assigned frequencies for the 12GHz Satellite broadcasting band (Europe). Note: UK channels are 4, 8, 12, 16 and 20. Orbit position—31°W. Polarisation—right-hand circular in now current convention viewed with signals approaching receiving aerial

by the IBA but is now the official UK standard, to be used for example on the first BBC channels on UNISAT. C-MAC has also been proposed as a European standard for DBS. 625-line PAL with VSB vision transmission will, of course, continue to be used over the terrestrial networks.

### TIME-COMPRESSION MULTIPLEXING

The C-MAC system is based on a single FM transmission channel with no sound carriers, colour carriers or subcarriers. It is designed to meet the European satellite transmission parameters which specify the use of 27MHz wide channels with the carriers only 19MHz apart but with adjacent channel interference limited to agreed figures; 40 channels have been assigned, the frequencies of which are listed in Table 1. The basic parameters of C-MAC are listed in Table 2.

Satellite channel bandwidth:	27MHz. Triangular energy dispersal waveform added to video signal.
Luminance (Y):	Uncompressed, up to 5.6MHz Compression ratio 3:2 Compressed, up to 8.4MHz
Chrominance (U, V):	Uncompressed, up to 1.6MHz Compression ratio 3:1 Compressed, up to 4.8MHz Each chroma signal, U or V, is transmitted on alternate lines.
Sound/data:	Digital synchronization: 8-bit burst at start of each line period Digital rate: 20.25Mbit/s Basic audio sampling frequency 32kHz, 14-bit words (linear), 10-bit words (companded) During normal picture transmission 186 bits per line, representing TV frame capacity of 2906.25kbit/s. In each 8 millisecond period (125 TV lines) exactly 256 samples of each sound channel are transmitted. Data frames similarly based on 8 millisecond periods.
Line period (64µs):	Each line is made up of: sync burst and digital sound (194 bits); then transition to main clamp (zero level) 15 samples; chrominance (U or V), 335 samples; grey-to-black transition and black-level clamp (14 samples); luminance, 710 samples; transition into data (4 samples). Sampling clock frequency 20.25MHz.
Line frequency	$\frac{2}{3} \times \frac{1}{864} \times 20250\text{kHz}$ .

Table 2. C-MAC basic parameters, 625-line, 50Hz interlaced

Instead of frequency-interleaving the system uses time-multiplexing to permit the luminance and chrominance information to be transmitted sequentially rather than simultaneously. To enable this to be done within the framework of a standard 625-line format, both luminance and chroma signals are time-compressed on transmission and subsequently time-stretched at the receiver. Time-compression and time-expansion of signals is the fundamental principle of digital standards converters, digital time-base correctors and some other applications of digital technology in television. Basically one can clock a signal into an electronic memory at one rate and take it out again at a different rate. Since in a MAC system this is done within each 64µs line period the amount of electronic memory required is relatively small (Fig. 5).

Decoders can use a charge coupled device (c.c.d.) which is a memory device capable of storing a signal in analogue form, or alternatively the process can be carried out, as in a modern standards converter, in digital form using conventional digital memory devices. In the early development of the MAC system it

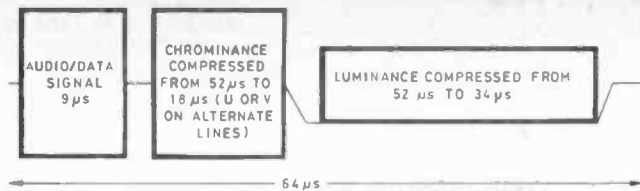


Fig. 5. Basic C-MAC Signal line format

was usually suggested that a c.c.d. analogue memory system should be used; however it has become evident that at least in the initial stages, the alternative and equally satisfactory digital system, using conventional digital memory, will prove the more economical process despite the requirement for simple A to D and D to A converters.

In practice, for mass production, the basic MAC video decoder is likely to take the form of two special-purpose large-scale-integrated (l.s.i.) devices, less than will be required for decoding the multiplexed digital audio channels; this factor is why it can be fairly claimed that C-MAC indoor units can be produced at virtually the same cost as a PAL plus multiplexed sound unit. Multiplexed sound of course does add fairly significantly to the cost of indoor units compared with the conventional single mono-channel sound system used for terrestrial television broadcasting. In practice the digital sound decoder needs roughly the same order of complexity as a Teletext decoder.

To sum up the MAC video system: The colour and luminance signals remain separate throughout the transmission system and are sent sequentially as Component signals by means of time compression in a time-Multiplexed form, with the FM transmission conveying the signals in Analogue form. Hence the name Multiplexed Analogue Component (MAC). In the decoder the time-stretching can be done using either analogue or digital techniques, with the digital approach being favoured currently on economic grounds.




IBA's mobile experimental satellite up-link terminal, first demonstrated at Wembley in 1978 and since used on a North Sea oil rig and in Austria, the Azores and Spain. This unit provided a vital test-rig for MAC sending up signals to the OTS satellite

## AUDIO TRANSMISSION

The audio signals are transmitted in digital form, as bursts of data at 20-25Mbit/s in the line-blanking interval at the start of each line-period. The C in C-MAC refers to the general form of the multiplexed sound system. It stems from the investigation by members of the European Broadcasting Union of a number of possible ways of transmitting digital sound with or without sub-carriers etc, designated as A, B or C-type sound. There are also further variations within these categories. The C system proposed and accepted by the UK is a complex but flexible system in which the multiplexing is defined by a regularly transmitted "structure map". This permits the exact mix of sound/data channels to be changed at will. Further when no video signal is present (for example outside TV broadcasting hours) the 20-25Mbit/s data signal can be run continuously, providing either a large number of very high quality sound-only services or an enormous data capacity for Teletext.

The digital burst normally consists of a run-in, a sync word and 174 bits of data. It should be appreciated that the circuitry required to demultiplex this data stream is complex but fortunately can be largely implemented in integrated form. To explain the flexible data structure in detail however would require an article in itself.

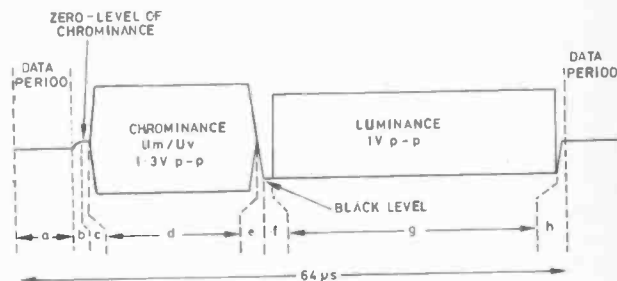

(EG1247)

- |                 |  |
|-----------------|--|
| a = 194 bits    | — synchronization, sound/data  |
| b = 4 samples   | — transition from end of data: includes leading edge of pedestal signal added to video to provide energy dispersal |
| c = 15 samples  | — main clamp period  |
| d = 355 samples | — chrominance (U or V)   |
| e = 4 samples   | — grey-to-black transition   |
| f = 10 samples  | — black-level clamp period   |
| g = 710 samples | — luminance  |
| h = 4 samples   | — transition into data: includes trailing edge of pedestal signal added to video to provide energy dispersal       |

Fig. 6. Detailed C-MAC Video waveform (lines 23 to 310 and 335 to 622) for normal picture transmission (not to scale)

## DATA STRUCTURE

Each TV line consists of a 9µs digital burst, then 17.5µs of colour information and finally 35µs of luminance information. A detailed illustration of the C-MAC video waveform is given in Fig. 6. Although the vision signal is analogue in form, it is convenient to think of it as being "sampled" at the same digital rate of 20-25MHz. This rate represents 1296 samples for each 64-microsecond line period of which 1114 sampling periods are used for the luminance and chrominance signals. The remaining 182 sampling periods correspond to the line blanking interval and represent the 182 bits of the 20-25Mbit/s digital signal (174 carrying the audio/data information). Both sound and video signals can be encrypted for subscription channels more readily than conventional composite-coded transmissions. It is easy to rearrange the luminance and chrominance information to "scramble" the pictures, and the digital sound can readily be made unintelligible to a standard decoder.

It should be appreciated that time-compression or "shrinking" of a signal represents an overall increase in video

bandwidth since each video component is actually transmitted in less time at a higher frequency. However the additional bandwidth remains within that available in a satellite channel, and the slight degradation in signal/noise ratio in no way compares with the additional chroma noise that would result from the use of a 4.43MHz subcarrier on an FM transmission. Because MAC reduces significantly the problem of noise in the highly coloured areas the overall effect is to provide the user with a picture that remains acceptable at lower signal inputs to the 12GHz front-end. This means in effect that the viewer can use a smaller dish aerial, or alternatively has more in hand to counter gradual deterioration of the dish reflector or aerial pointing errors. Since a smaller dish is less directional as well as offering less wind resistance, the installation of a DBS aerial for MAC is usefully less critical than for conventional colour-encoded signals.

### DIGITAL FILTERING

While C-MAC remains a 625-line system, the separation of colour and brightness information greatly facilitates the addition of digital signal-processing within the receiver. For this reason techniques that would provide additional luminance information within a MAC transmission by means of what is called "three-dimensional" digital filtering have been investigated by the IBA. This processing takes advantage of the series of gaps in the spectrum which carry only high-frequency diagonal information. If these HF diagonals are excluded the gaps become available to carry additional information. This extended-definition option would be useful for providing high-fidelity pictures, with a subjective resolution of roughly 1000 lines they would be suitable for use with future large-screen, high-resolution picture-display systems. Such a system requires several fields of digital memory within the receiver and is not at present economic for domestic sets. This can usefully be combined with the prospect of the

flicker-free pictures that can be provided by displaying 625-line 50Hz pictures at 100Hz and sequentially, rather than in interlaced form.

Digital processing in receivers has already been demonstrated by receiver manufacturers but a major advantage with the MAC system is that the requirement for motion-detection in order to suppress digital processing in areas of fast motion are greatly eased by component (YUV) rather than composite signals.

### VIDEO INTERFACE

To obtain the full advantages of MAC the interface between the "indoor unit" and the television receiver proper needs to be at video frequency, i.e. YUV signals (Fig. 7). The fitting of a

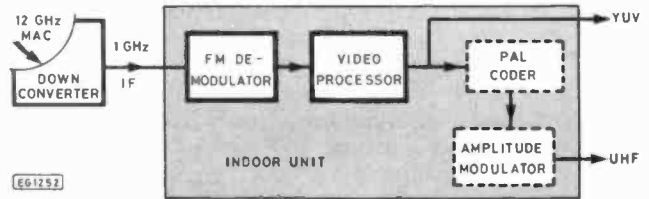


Fig. 7. Basic MAC satellite converter

suitable socket to receivers also offers very significant advantages—indeed such sockets have been mandatory in France since 1980. With a video socket, the need for the UHF modulators currently used in VCR machines, video games, Teletext adaptors, home computer etc. is eliminated, resulting in greatly improved displays when these units are in operation. The trend towards YUV interfacing can also be seen in the growth of "unit video". This does not mean that the current sets cannot be used with MAC but it does mean that the signal fed to an aerial socket has to be in composite-coded form and this reintroduces the problems of cross effects that MAC can eliminate. ★

# IT PAYS TO HAVE THE BEST CONNECTIONS

especially to PRACTICAL ELECTRONICS—the magazine for connecting hobbyists. The latest technology in a monthly selection of useful constructional projects for your home...for your car—in fact, there are hundreds of ways PRACTICAL ELECTRONICS can help you.

The biggest problem is avoiding breakdowns, like missing important issues—but now it's made easy with the PRACTICAL ELECTRONICS subscription service.

Just fill in the coupon below and have PRACTICAL ELECTRONICS delivered direct to your door every month. Avoid disconnection send off the coupon today.

Alternatively ring our special Teledata Hotline. And why not order a subscription for a friend too!

## PRACTICAL ELECTRONICS SUBSCRIPTION ORDER FORM

Annual Subscription Rates	
U.K.	£13.00
U.S.A. CANADA	\$28.60
Other Overseas Surface Mail	£13.00
(Students: Deduct £1.00 (\$2.20) and quote Student number.)	

Complete this form and post it, with payment or Credit Card authorisation to: IPC Magazines Ltd., Room 2816, King's Reach Tower, Stamford Street, London SE1 9LS. You can use this form to order a gift subscription too. Hotline. Phone TELEDATA 01-200 0200 with your Credit Card No. Allow 4 weeks for order processing.

Post copies to:

NAME: \_\_\_\_\_  
ADDRESS: \_\_\_\_\_  
Post Code: \_\_\_\_\_

If a Gift Subscription enter your own name and address here.

NAME: \_\_\_\_\_  
ADDRESS: \_\_\_\_\_  
Post Code: \_\_\_\_\_

I enclose my cheque/P.O. payable to IPC Magazines Ltd. for £ \_\_\_\_\_  
Charge my Credit Card A/C at quoted rate.


Card Valid from: \_\_\_\_\_ to \_\_\_\_\_

Signature: \_\_\_\_\_



**HOTLINE**  
PHONE  
TELEDATA

01 200 0 200

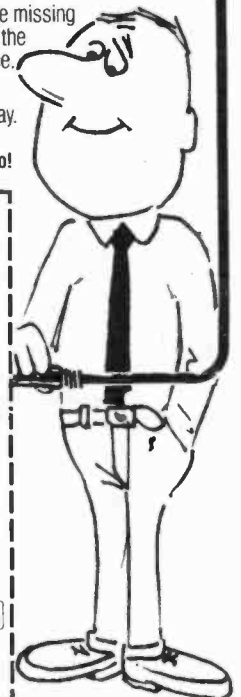

# Midwich

COMPUTER COMPANY LIMITED

## 1st choice for microcomputer components

### BBC COMPUTERS

Model B 346.95  
 (Carriage 5.50 by Securocr)  
**441.95**  
 NB: Credit cards not accepted in payment for BBC Micro

### BBC MICRO DISC DRIVES

BBC 31 Single 100K Drive Expandable to 2x100K 195.00  
 BBC 32 Dual 100K Drives 335.00  
 BBC 33 100K Upgrade for BBC 31 140.00  
 BBC 34 Dual 400K Drives 545.00  
 BBC 35 Utilities Disc 25.00  
 (supplied only with BBC 31, 32, 34)  
 All Disc Drives (except BBC 33) are complete with Manual, Utilities Disc, and Connecting Cables

### BBC MICRO UPGRADE KITS

BBCA2B Complete A to B Upgrade 44.75  
 BBC 1 16K Memory 18.00  
 BBC 2 Printer/User I/O Kit 7.50  
 BBC 3 Disc Interface Kit 95.00  
 only supplied with Disc Drives.  
 BBC 4 Analogue Input Kit 6.70  
 BBC 5 Serial I/O & RGB Kit 7.30  
 BBC 6 BUS Expansion Kit 6.45  
 All Kits are supplied with full fitting instructions

### PRINTERS

NEC 8023 Printer (Carriage 10.00) 320.00

### BBC CONNECTORS

BBC 21 Printer Cable and Amphenol Plug (not assembled) 13.00  
 BBC 22 User Port Connector and Cable 36" 2.46  
 BBC 23 Cassette Lead 3.50  
 BBC 24 7 Pin DIN Plug 0.60  
 BBC 25 6 Pin DIN Plug 0.60  
 BBC 26 5 Pin DIN Plug 0.60  
 BBC 25 Disc I/O Cable 34W IDC to 2x34 way card edge 12.00  
 BBC 36 Disc Power Cable 6.00  
 BBC 44 Analogue Input Plug and Cover 2.25  
 BBC 66 IM Bus Connector + 36" Cable 3.50

### BBC ACCESSORIES

BBC 45 Joysticks (per pair) 11.30  
 BBC 71 Teletext Receiver 225.00  
 BBC 72 Second Processor (6502) 170.00  
 BBC 73 Second Processor (Z80) 170.00

### ACORN/SOFT FOR THE BBC

SBEO3 Business Games 8.65  
 SBEO4 Tree of Knowledge 8.65  
 SBEO2 Peeko Computer inc Manual 8.65  
 SBEO1 Algebraic Manipulation Pk 8.65  
 SBX01 Creative Graphics Cassette 8.65  
 SBX02 Graphics and Charts Cassette 8.65  
 SB001 Desk Diary inc Manual 8.65  
 SBLO1 LISP Cassette 14.65  
 SBLO2 FORTH Cassette 14.65  
 SBG01 Philosophers Quest 8.65  
 SBG07 Sphinx Adventure 8.65  
 SBG03 Monsters 8.65  
 SBG04 Snapper 8.65  
 SBG15 Placid 8.65  
 SBG06 Arcade Action 10.35  
 SBG05 Rocket Raid 8.65  
 SBG13 Meteors 8.65  
 SBG14 Arcadians 8.65  
 SBG10 Chess 8.65

### ACORN/SOFT BOOKS FOR THE BBC MICRO

SBDO1 Creative Graphics 7.50  
 SBDO2 Graphs and Charts 7.50  
 SBDO4 LISP 7.50  
 SBDO3 FORTH 7.50

Please ring for current delivery on Acornsoft Products before ordering.

### BBC MICRO COMPONENTS

4516 100ns 2.25 8271 36.00  
 6522 3.19 20 Way Header 1.46  
 74LS244 0.59 26 Way Header 1.76  
 74LS245 0.69 34 Way Header 2.06  
 74LS163 0.34 40 Way Header 2.32  
 DS3691N 4.50 15 Way D Skt 2.15  
 DS89LS120N 4.50 6 Way DIN Skt 0.90  
 UPD7002 4.50 5 way DIN Skt 0.90

### BBC SOFTWARE IN EPROM

Wordprocessor "View" 52.00  
 1.2 MOS 10.00

### SPECIAL OFFER

Spectrum 32K Upgrade Kit 24.95

MEMORIES

2114L 200ns	D1 0.80	FD1795	D6 28.00
2706 450ns	D2 2.95	FD1797	D6 28.00
2716 450ns	D1 2.45	WD1691	D2 12.00
2716 350ns	D1 4.95	WD2143-01	D2 6.99
2716 3 rail	D1 7.25	6402	
2532 450ns	D2 3.45	75107	
2732 450ns	D1 3.45	75110	
2732 350ns	D1 5.45	75150	
2764 300ns	D1 5.99	75154	
4116 150ns	D2 0.95	75160	
4116 200ns	D2 0.80	75161	
4118 150ns	D1 3.25	75162	
5516 200ns	D2 9.45	75172	
6116 150ns	D1 3.30	75173	
6116 Low Power 150ns	D2 4.95	75175	
4164 150ns T1	D3 4.45	75182	
4164 200ns T1	D3 3.95	75183	
4164 150ns		75188	
Mostek	D3 4.45	75189	
4516/4816 100ns	D2 2.25	75451	
4532 200ns	D2 2.95	75452	
		75453	

### INTERFACE DEVICES

TL487 0.62  
 TL489 0.62  
 TL494 1.63  
 TL496 0.60  
 TL507 1.33  
 725 0.77  
 741 2.56  
 747 2.80  
 748 3.95  
 75174 1.44  
 78L05 1.95  
 78L12 1.44  
 78L15 0.50  
 7805 0.37  
 7815 0.37  
 7915 0.22  
 7912 0.22  
 7915 0.45  
 4051 0.45  
 4052 0.44  
 4053 1.20  
 4054 2.40  
 4055 4.50  
 4060 0.39  
 4061 0.85  
 4066 0.24  
 4068 0.14  
 4069 0.14  
 4070 0.13  
 4071 0.13  
 4072 0.13  
 4073 0.14  
 4075 0.13  
 4076 0.43  
 4077 0.13  
 4078 0.15  
 4081 0.13  
 4082 1.92  
 4085 2.00  
 4086 1.86  
 4093 0.64  
 4507 0.86  
 4508 0.86  
 4510 2.48  
 4511 0.41  
 4512 3.40  
 4514 0.96  
 4515 0.96  
 4516 0.40  
 4518 0.40  
 4519 0.27  
 4520 0.40  
 4521 0.90  
 4522 0.52  
 4526 0.52  
 4527 0.52  
 4528 0.52  
 4532 0.72  
 4541 0.50  
 4543 0.50  
 4553 1.57  
 4555 0.35  
 4556 0.35  
 4558 0.75  
 4565 0.20  
 4566 0.55  
 4567 0.55  
 4568 0.55  
 4569 0.55  
 4570 0.55  
 4571 0.55  
 4572 0.55  
 4573 0.55  
 4574 0.55  
 4575 0.55

TL014 0.36  
 TL021 0.34  
 TL061 0.29  
 TL062 0.49  
 TL064 0.98  
 TL066 0.29  
 TL068 0.32  
 TL071 0.29  
 TL072 0.47  
 TL074 1.00  
 TL081 0.26  
 TL082 0.46  
 TL084 1.58  
 TL091 0.40  
 TL092 0.58  
 TL094 1.34  
 TL487 0.62  
 TL489 0.62  
 TL494 1.63  
 TL496 0.60  
 TL507 1.33  
 725 0.77  
 741 2.56  
 747 2.80  
 748 3.95  
 75172 1.95  
 75173 1.44  
 78L05 1.95  
 78L12 1.44  
 78L15 0.50  
 7805 0.37  
 7815 0.37  
 7915 0.22  
 7912 0.22  
 7915 0.45  
 4051 0.45  
 4052 0.44  
 4053 1.20  
 4054 2.40  
 4055 4.50  
 4060 0.39  
 4061 0.85  
 4066 0.24  
 4068 0.14  
 4069 0.14  
 4070 0.13  
 4071 0.13  
 4072 0.13  
 4073 0.14  
 4075 0.13  
 4076 0.43  
 4077 0.13  
 4078 0.15  
 4081 0.13  
 4082 1.92  
 4085 2.00  
 4086 1.86  
 4093 0.64  
 4507 0.86  
 4508 0.86  
 4510 2.48  
 4511 0.41  
 4512 3.40  
 4514 0.96  
 4515 0.96  
 4516 0.40  
 4518 0.40  
 4519 0.27  
 4520 0.40  
 4521 0.90  
 4522 0.52  
 4526 0.52  
 4527 0.52  
 4528 0.52  
 4532 0.72  
 4541 0.50  
 4543 0.50  
 4553 1.57  
 4555 0.35  
 4556 0.35  
 4558 0.75  
 4565 0.20  
 4566 0.55  
 4567 0.55  
 4568 0.55  
 4569 0.55  
 4570 0.55  
 4571 0.55  
 4572 0.55  
 4573 0.55  
 4574 0.55  
 4575 0.55

### REGULATORS

78L05 1.95  
 78L12 1.44  
 78L15 0.50  
 7805 0.37  
 7815 0.37  
 7915 0.22  
 7912 0.22  
 7915 0.45  
 4051 0.45  
 4052 0.44  
 4053 1.20  
 4054 2.40  
 4055 4.50  
 4060 0.39  
 4061 0.85  
 4066 0.24  
 4068 0.14  
 4069 0.14  
 4070 0.13  
 4071 0.13  
 4072 0.13  
 4073 0.14  
 4075 0.13  
 4076 0.43  
 4077 0.13  
 4078 0.15  
 4081 0.13  
 4082 1.92  
 4085 2.00  
 4086 1.86  
 4093 0.64  
 4507 0.86  
 4508 0.86  
 4510 2.48  
 4511 0.41  
 4512 3.40  
 4514 0.96  
 4515 0.96  
 4516 0.40  
 4518 0.40  
 4519 0.27  
 4520 0.40  
 4521 0.90  
 4522 0.52  
 4526 0.52  
 4527 0.52  
 4528 0.52  
 4532 0.72  
 4541 0.50  
 4543 0.50  
 4553 1.57  
 4555 0.35  
 4556 0.35  
 4558 0.75  
 4565 0.20  
 4566 0.55  
 4567 0.55  
 4568 0.55  
 4569 0.55  
 4570 0.55  
 4571 0.55  
 4572 0.55  
 4573 0.55  
 4574 0.55  
 4575 0.55

### DATA SHEETS are available on items marked D.

D1 0.75 D5 2.50  
 D2 1.00 D6 3.00  
 D3 1.25 D7 4.00  
 D4 2.00

### DATA SHEETS are available on items marked D.

LM309K 1.20  
 LM317K 2.40  
 LM323K 4.50  
 LM338K 6.25

### DATA CONVERTERS

UPD7007 4.26  
 ZN425 1.45  
 ZN426 2.00  
 ZN427 0.59  
 ZN428 0.75  
 ZN429 0.21  
 ZN432 0.13  
 ZN439 0.25

### UNF MODULATORS

4M 0.64  
 6M 0.86  
 9.3004M 1.68  
 19.6608M 2.48  
 100M 2.75  
 1M 2.75  
 1.8432M 1.92  
 2.4576M 2.00  
 3.5864M 1.86  
 4M 0.64  
 6M 0.86  
 9.3004M 1.68  
 19.6608M 2.48  
 100M 2.75  
 1M 2.75  
 1.8432M 1.92  
 2.4576M 2.00  
 3.5864M 1.86

### BUFFERS

81LS95 0.80  
 81LS96 1.10  
 81LS97 0.80  
 81LS98 0.80  
 8T26A 0.90  
 8T28A 0.90  
 8T95 0.90  
 8T97A 0.90  
 8T98 0.90  
 81LS95 0.80  
 81LS96 1.10  
 81LS97 0.80  
 81LS98 0.80  
 8T26A 0.90  
 8T28A 0.90  
 8T95 0.90  
 8T97A 0.90  
 8T98 0.90

### FLOPPY DISC CONTROLLERS

8271 48.00  
 FD1771 0.39  
 FD1791 0.32  
 FD1793 0.34  
 LM348N 0.60  
 NE555P 0.16  
 NE556CP 0.45  
 TL010 0.39  
 TL011 0.32  
 TL012 0.34

### CMOS 4000

LM324N 0.30  
 LM348N 0.60  
 NE555P 0.16  
 NE556CP 0.45  
 TL010 0.39  
 TL011 0.32  
 TL012 0.34

### ZIF SOCKETS (TEXTTOOL)

24 pin 4.75  
 28 pin 0.48  
 40 pin 0.50  
 40 pin 0.50  
 50 pin 0.50  
 50 pin 0.50  
 50 pin 0.50

### IC SOCKETS (TEXAS)

16 pin 4.51  
 24 pin 4.51  
 28 pin 4.51  
 36 pin 4.51  
 40 pin 4.51  
 40 pin 4.51  
 48 pin 4.51  
 56 pin 4.51  
 68 pin 4.51  
 74 pin 4.51  
 84 pin 4.51  
 96 pin 4.51

### 74LS SERIES

04 0.24  
 05 0.10  
 08 0.16  
 09 0.20  
 10 0.40  
 11 0.36  
 12 0.20  
 13 0.32  
 14 0.36  
 15 0.40  
 16 0.26  
 17 0.40  
 18 0.46  
 19 0.50  
 20 0.26  
 21 0.40  
 22 0.40  
 23 0.26  
 24 0.32  
 25 0.40  
 26 0.32  
 27 0.36  
 28 0.13  
 29 0.12  
 30 0.12  
 31 0.12  
 99 0.12  
 00 0.12

01 0.12  
 02 0.12  
 03 0.12  
 04 0.12  
 05 0.12  
 06 0.12  
 07 0.12  
 08 0.12  
 09 0.12  
 10 0.12  
 11 0.12  
 12 0.12  
 99 0.12  
 00 0.12

### DIL JUMPERS

Single Ended 24" 1.45  
 14 pin 1.65  
 17 pin 2.40  
 40 pin 3.80

### Double Ended

14 PIN 5" 12" 18" 1.85  
 16 PIN 2.05 2.15 2.58  
 24 PIN 3.00 3.15 3.96  
 40 PIN 4.65 4.90 6.18

### 25 WAY D-TYPE CONNECTORS

Male: Male 12.00  
 Male: Female 12.00  
 Male single ended 18" Cable 4.95  
 Female single ended 18" Cable 3.95

### IDC CONNECTORS

(with ejectors) (Right Angle PCB Mtg)  
 10 PIN 0.86  
 14 PIN 1.22  
 30 PIN 1.46  
 20 PIN 1.46  
 26 PIN 1.75  
 34 PIN 2.06  
 50 PIN 2.32  
 60 PIN 2.35  
 30 PIN 3.20

### IOC SOCKETS

Fitted with 36" cable  
 10 PIN 1.40  
 14 PIN 1.82  
 30 PIN 1.34  
 20 PIN 2.10  
 26 PIN 2.48  
 34 PIN 3.24  
 50 PIN 3.50  
 60 PIN 4.90  
 30 PIN 5.48  
 60 PIN 6.38

### DATA BOOKS by Texas Instruments

Linear Control Circuits 4.00  
 Voltage Regulators 4.50  
 MOS Memory 3.95  
 Interface Circuits 7.00  
 TTL 5th Edition 8.50  
 Bipolar Micro 4.50  
 TTL Pkt Guide 3.50  
 Linear Pkt Guide 2.50

Carriage Orders up to £199 are sent by 1st class post, and £200 + by Securor.  
 £100 0.50 £100 £199 1.25 £200 + £50 by Securor  
 Prices quoted (+ carriage charges) are exclusive of VAT and are subject to change without notice.  
 Quantity Discounts are available on many products, please ring for details.  
 Official Orders are welcome from Educational Establishments, Government Bodies and Public Companies.  
 Credit Accounts are available to others subject to status.  
 Payment is due strictly nett by the 15th of the month.  
 Credit Cards are accepted (Access and Visa) for telephone and postal orders and NO SURCHARGE is made.  
 Out of stock items will follow automatically, at our discretion, or

# LOGIC ANALYSER

Part Two  
D. MANDELZWEIG


LAST month, the operation of the basic analyser was described in detail. This month we will describe the construction of the basic unit, and some initial tests that can be done. Interwiring has been kept to a minimum (in fact, besides the power supply, there is no interwiring for the basic unit) by the use of the front panel p.c.b., but due to the complexity of the project, it is suggested that only reasonably experienced constructors attempt to build the unit. It is also strongly recommended that the construction method described is followed closely. Failure to do so could result in an analyser that is difficult to complete!

## MAIN PCB


Refer to Fig. 2.3: Start construction of this p.c.b. with the soldercon i.c. socket strips (or wire-wrap sockets, although the former method is preferred). Cut the strips into 7, 8, 10 or 12 pin lengths as necessary. Place a strip at a time in the board, starting from the middle of the board (IC27 for example) working outwards. Solder, on the front side, only those pins of a strip which have a track coming to its pad on the front side of the board. When soldering the pin, be very careful that no solder flows between the contacts. If this should happen, the single pin can be replaced at a later stage, once the rest of the strip has been soldered under the board. (The top of the pins can be broken off and the soldered pin removed and replaced.) Before soldering in the pins for IC19 and IC18, solder in SK6. SK6 is cut to length from a piece of double-sided, wire-wrap, p.c.b. edge connector. Allow the connector to stand proud of the p.c.b. and solder the pins to the pads on the top of the board. As no tracks to SK4 and SK5 are on the front side of the p.c.b., proper 16-pin i.c. sockets can be used for these sockets. Once all the strips are in place, turn the board over and solder *all* the pins on the back of the board. *Do not* break off the tops of the pins until later, when the i.c.'s are to be inserted, to avoid the pins becoming misaligned.

Next solder in SK8 in a similar fashion to SK6, followed by the resistors and then the capacitors. Be sure to get the polarity of the capacitors correct. Solder in Vero pins for the screened wire that will go to SK7, as well as for the wire that will go to S20 wiper. Put in the links A, B, C and  $\pm 12V$  using thin insulated wire. IC40 and IC41 can be soldered in. Now, lying the board on a flat surface, component side up, use the discarded leads of the resistors and capacitors cut in half, to fill the remaining holes in the p.c.b.



Solder the leads on the top side, turn the board over and solder the leads on the underside. Finally, trim the leads on the front side, leaving neat through-hole connections. Solder lengths of hook-up wire to the p.c.b. for later connection to the PSU +5V, 0V, +15V and -15V. Now very carefully check that all socket pins, component leads, Vero pins, through-hole connections and wires have been soldered on the front side of the p.c.b. where necessary—i.e. where tracks lead to pads on the front side. Carefully break off the tops of the socket strips, and using an ohmmeter, check that

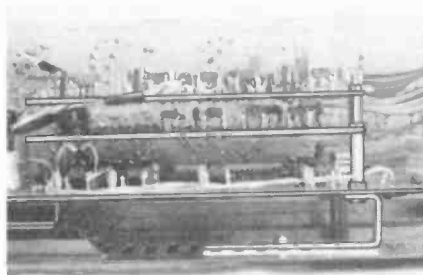


Sandwich construction of the Analyser

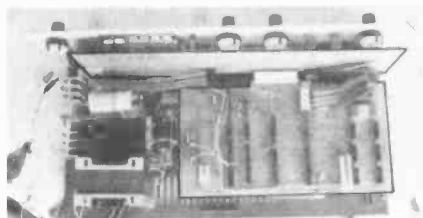

Plan view, showing PSU location

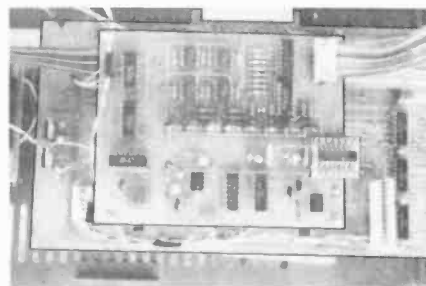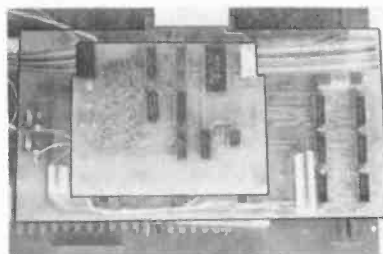

Coloured "Easy-Hooks" are used for the data probes

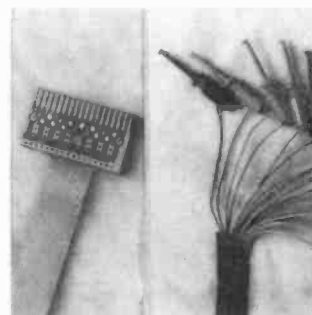



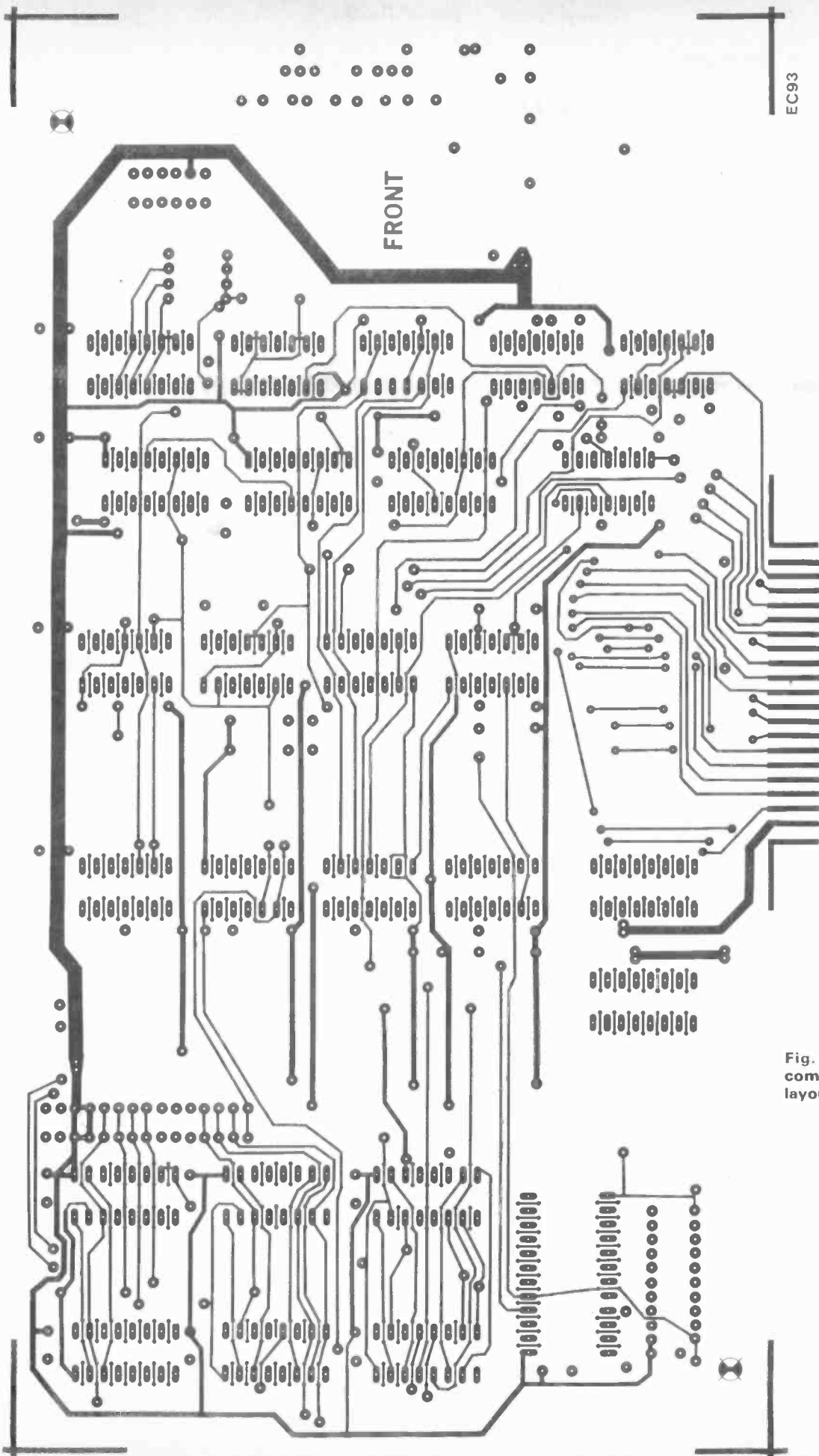


Fig. 2.1. Main p.c.b. component-side track layout (actual size)

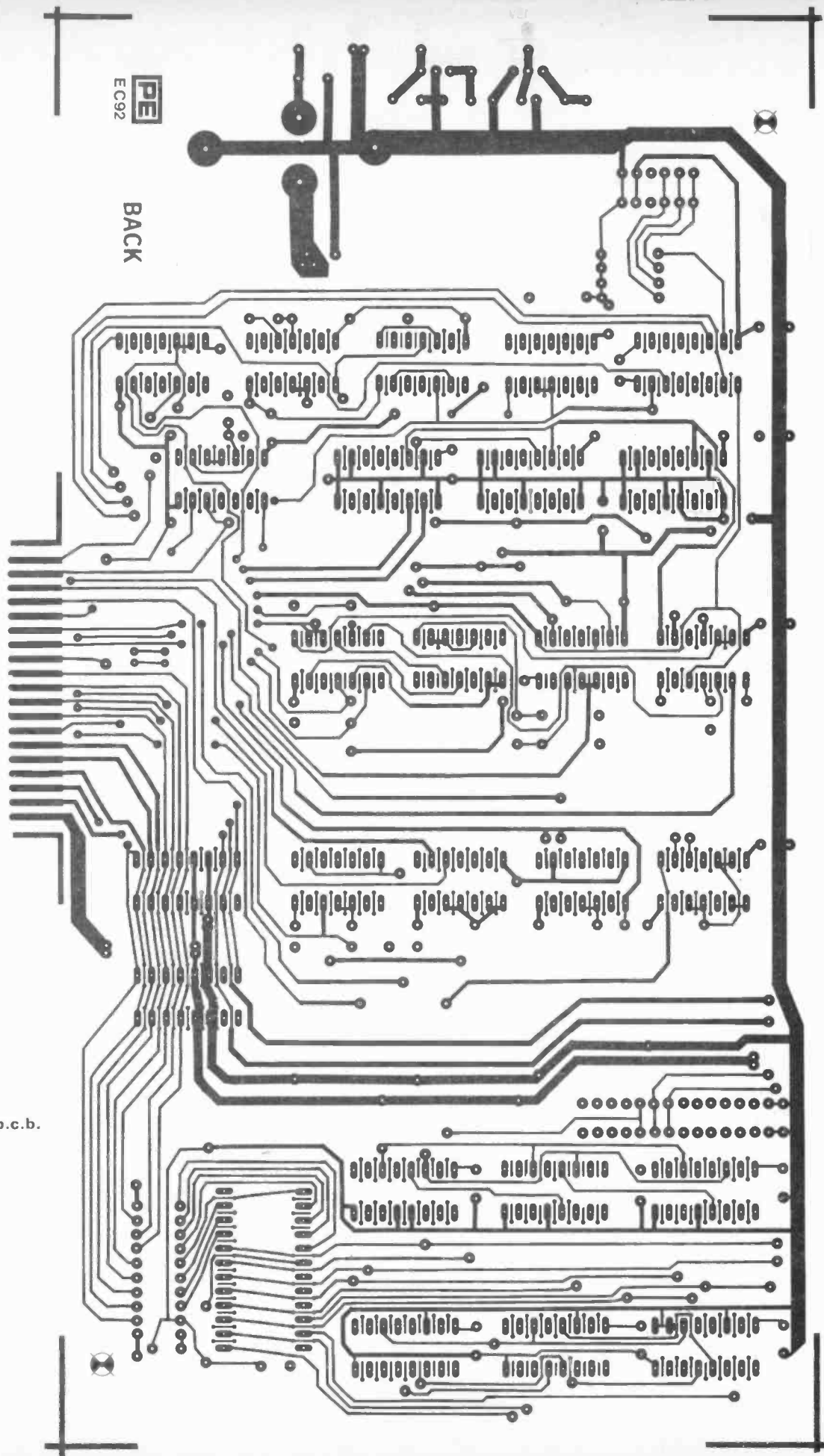


Fig. 2.2. Main p.c.b. track layout

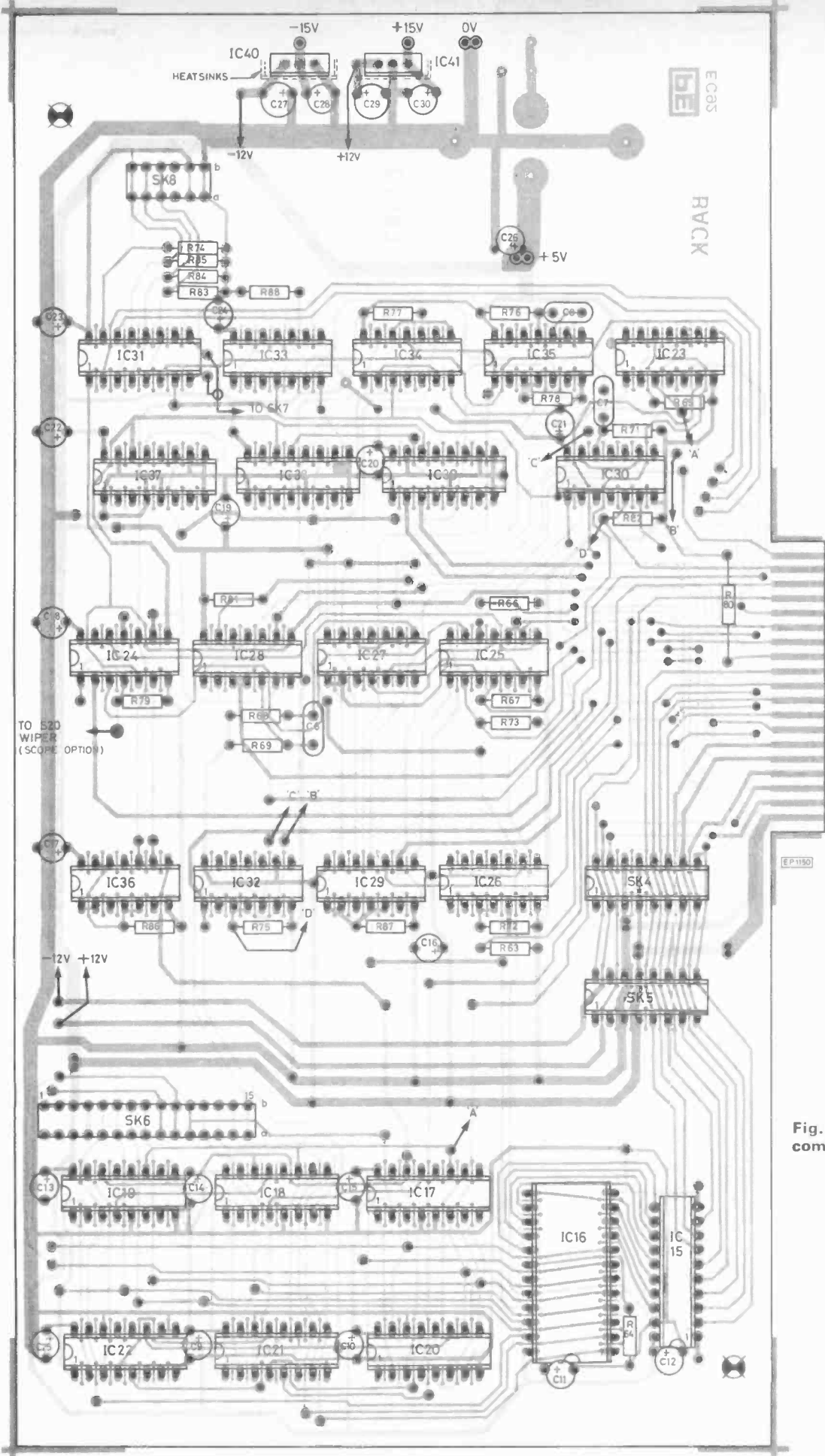



Fig. 2.3. Main p.c.b. component layout

there is no short across the +5V and 0V leads. Do a final inspection of both sides of the p.c.b., looking for track shorts and solder splashes. When satisfied, plug in all the i.c.'s, ensuring that the pins make positive connections with the sockets. Plug in the RAM (IC16) last of all. Finally screw a small heatsink to IC40 and IC41. If a single heatsink is used, IC40 must be insulated from the heatsink.

### FRONT PANEL PCB

This is the most difficult of the p.c.b.'s to construct, but if the following steps are followed carefully, there should be no trouble. First, drill the front panel to the dimensions given in Fig. 2.4, and fit the red perspex display filter. Do not letter the panel yet. Now cut 25mm lengths of stiff bare copper wire and solder the pieces to each contact of the switches which have a pad on the p.c.b. See Fig. 2.5 for an example of S4. When this has been completed, put all the switches in their positions (see Fig. 2.11) on the p.c.b., but do not solder the wires—just bend them slightly at the back of the p.c.b., so that they cannot fall out. Plug X 1 and X 6 into a wire-wrap socket each and position them on the p.c.b., also without soldering. Now align the loose switches with the holes in the front panel, fit the panel, and then tighten the switches in position, making sure they are straight and all fixed to the same depth. Gently ease the p.c.b. as close as possible to the switches—on the prototype, this was virtually as far as the original solder tags of S5, S14 and S19. Make sure the p.c.b. is parallel (in both directions) to the panel, and then solder all the switch leads on the rear of the p.c.b. Adjust displays X1 and X6 so that they lie flush with the perspex filter and solder the sockets on the rear of the p.c.b. Loosen the switches and remove the front panel. Solder the switch leads to the front of the p.c.b. where necessary. Fit the soldercon strips and, as with the main p.c.b., solder those pins where necessary on the front side of the p.c.b., one strip at a time. When finished solder the pins on the rear of the p.c.b. and fit and solder the resistors and capacitors. The other display sockets can be soldered to the board, ensuring that they are level with the two previously soldered in place. SK3 can be a proper 14 pin i.c. socket, as no tracks have to be soldered on the front of the p.c.b. to this socket.

Fig. 2.4. Front panel drilling details

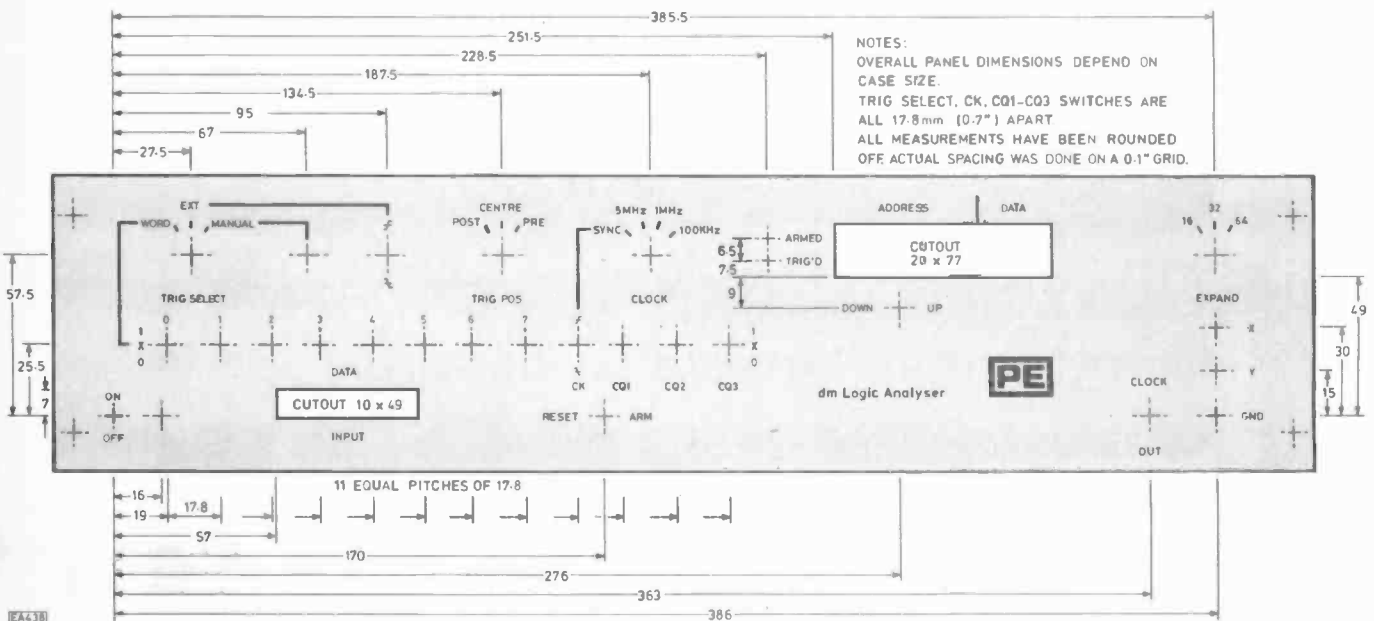

Fit and solder TR1 and then in the same manner as for the main p.c.b., make the through-hole connections, leaving the holes for D1-3 and SK1 and SK2 open. Cut a length of p.c.b. edge connector, 2 slots bigger than required, for SK2. Remove the two extra contacts from one side of the connector. Solder the connector to the rear side of the p.c.b., with the open slots on the right of the p.c.b., looking from the rear. Fill the second slot from the end with some stiff plastic to act as a key for the main p.c.b.

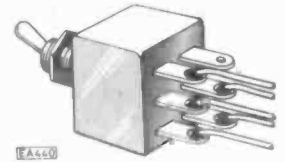


Fig. 2.5. Example of wiring to switch S4

In the prototype, SK1 was not mounted on the p.c.b. For this socket, a piece of single-sided edge connector (18 fingers long) was used, and was wired using 25mm lengths of wire-wrap wire to the p.c.b. Note that only 17 fingers are actually used. The connector was mounted using mounting ears bought with the connector and stand-off pillars, as shown in Fig. 2.6. At this stage however, only wire the connector to the p.c.b.—the connector need only be screwed to the front panel when finally completing the unit. Mount D1-3 on the panel and refit the p.c.b. It need only be held by two or three switch nuts. The l.e.d. leads will most likely be too short, so push some discarded resistor leads through the p.c.b., solder them to the l.e.d. leads (this can be done with the p.c.b. mounted behind the panel) and then solder the extended leads to the p.c.b. This completes the front panel p.c.b. Leave the assembly as is for the preliminary tests.

### POWER SUPPLY

Cut the key hole in the main p.c.b. and mate the p.c.b. with the front panel p.c.b. Place the assembly in the case and mark holes for mounting the main p.c.b. on stand-off pillars. In the prototype, small pieces of aluminium were bent and used. However, final mounting is left to the constructor, as it will be largely dependent on the case used. This applies to the layout of the power supply as well. The

photos show clearly how the prototype was arranged. Two separate transformers were used and were screwed to the case. The heatsink for IC42 was mounted on one side of the transformer and on the other to a small aluminium bracket. The capacitor C33 is mounted to the case and C31 and C32 are soldered directly to the regulator. BR1 was mounted on the side of the transformer, as can be seen. BR2, C34 and C35 were soldered to a piece of Vero board and mounted with a bracket to T2's mounting pillar. For test purposes, connect the mains via FS1 on the rear panel, direct to the transformer(s). Connect the +15V, -15V and 0V leads from the main p.c.b. to the power supply (use long leads for the meantime to aid testing) but do not connect the +5V lead just yet.

### PROBE

A photograph of the prototype probe shows the basic construction. A piece of Eurocard size Vero board with gold-plated edge connector fingers was cut to size. As no keying is used, cut the board slightly larger than the width of SK1's opening. Then file the board to just fit the socket. This will ensure repeatable alignment when inserting the probe. 14-way ribbon cable was soldered to the Vero board and on the other side, coloured Easy-hooks were used. The wiring for the probe is shown in Fig. 2.7.


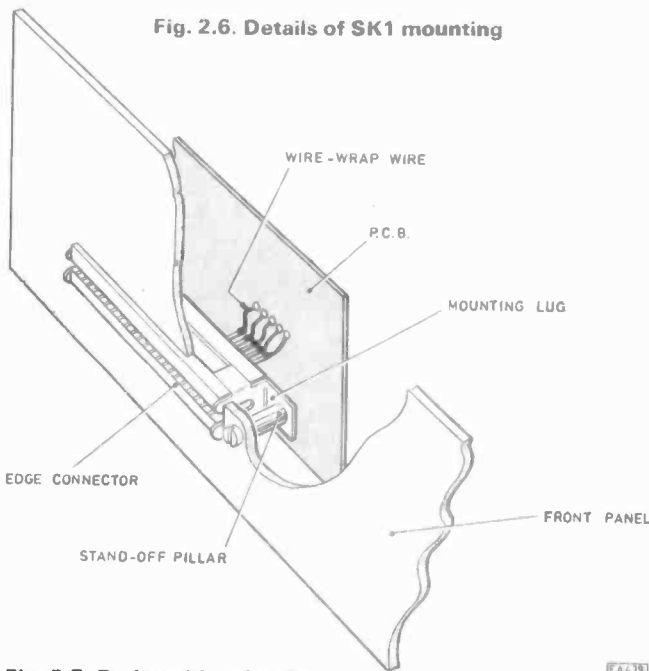


Fig. 2.6. Details of SK1 mounting


Fig. 2.7. Probe wiring details

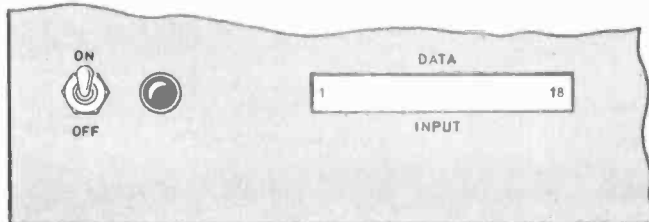

1	-	7	D5	13	C01
2	D0	8	D6	14	C02
3	D1	9	D7	15	C03
4	D2	10	0V	16	EXT TRIG
5	D3	11	+5V	17	+12V
6	D4	12	CLOCK	18	-12V

NOTE: +5V, +12V & -12V ARE NOT TAKEN TO THE PROBES


Fig. 2.8. Ribbon cable connections for options

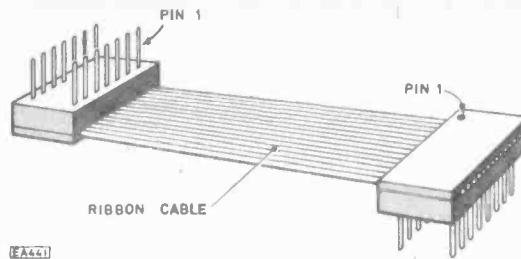

### PRELIMINARY TESTS

Switch on the power supply and check that IC42 has +5V on its output and that the outputs of IC40 and IC41 are at -12V and +12V respectively. If an oscilloscope is available, check that there is no oscillation on any of the power rails. If all is correct, switch off the power supply and solder the +5V lead to IC42. Connect the main p.c.b. to the front panel assembly, plug in the probe and switch on. The Address displays should have a random number between 0 and 1023 displayed. If the ARM and/or the TRIG l.e.d. is on, use S16 to reset the unit. The l.e.d.s should extinguish. Using S17 it should be possible to get the Address to increment or decrement. The Data display will remain blank. Select MANUAL trigger on S19 and PRE trigger on S5. Using S16 ARM the analyser and the ARM l.e.d. should light. Now press S15, the Address should show 1023 and TRIG l.e.d. should light. Pressing RESET (S16) should cause the l.e.d.s to extinguish. Repeat the procedure with CENTRE and POST selected. For CENTRE, 511 should be displayed and for POST 0 will be displayed and in this case, the TRIG and ARM l.e.d.s should extinguish. Monitor pin 2 of IC15 with an oscilloscope, while scanning up and down the memory with S17. Random highs and lows should be seen. Now connect a t.t.l. compatible clock to the clock input. If possible use a frequency of 100Hz. Select SYNCH CLOCK, PRE trigger, WORD trigger, WORD select switch S6 (D0) to '0' and the other data switches as well as the clock qualifier switches to "don't care". ARM the analyser, then switch D0 to "don't care". When this is done, the TRIG l.e.d. should light, the display should change to 1023 and then approximately 10 secs later (if a 100Hz clock has been used) the l.e.d.s should extinguish. If pin 2 of IC15 is now monitored, the output should always be high, regardless of the Address position. Repeat the above, but connect the D0 probe to 0V and start with the D0 switch switched to "1".

When the analyser has completed the store process, check pin 2 of IC15 once again and this time the output should be low for any Address position. If all has gone well, then it can be assumed that the basic unit is virtually operational. If not, use the circuit description to follow through the circuit, checking levels at each gate output in turn, until the fault is found.

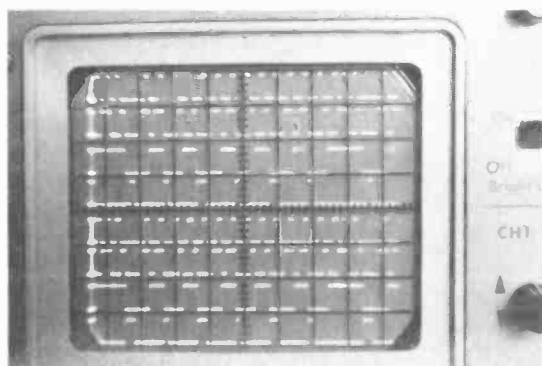



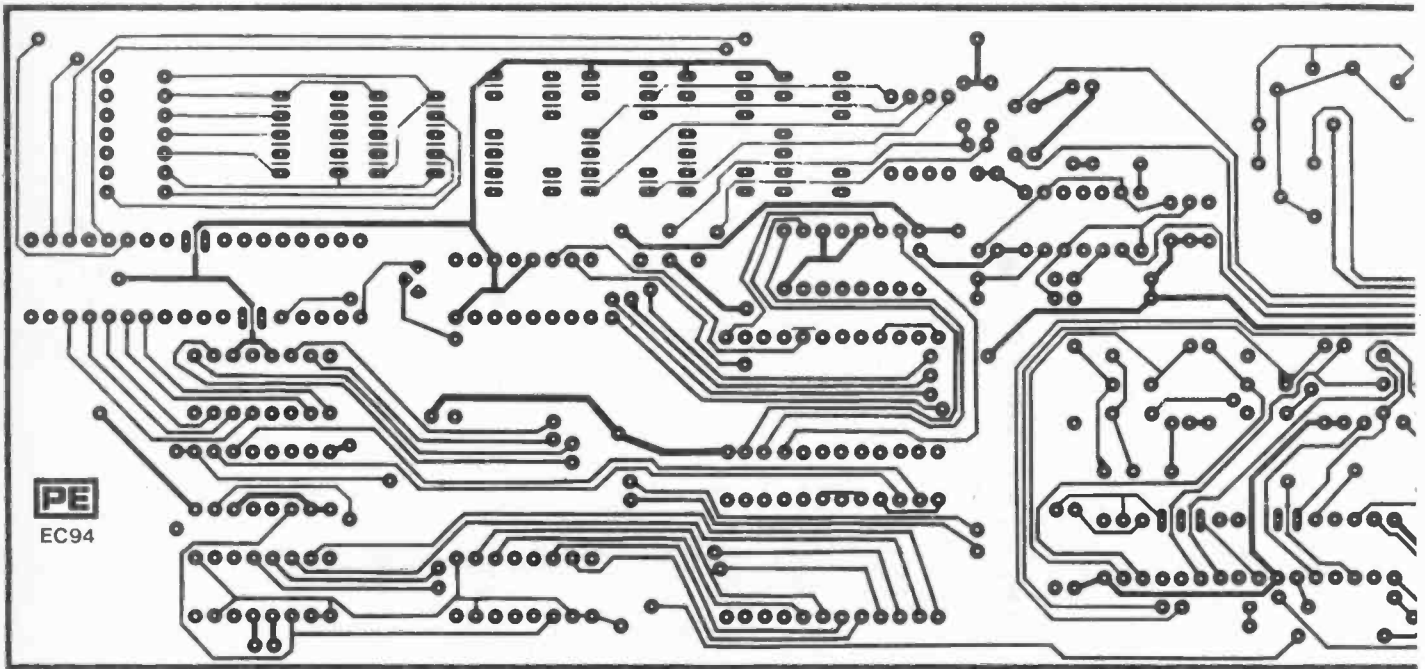
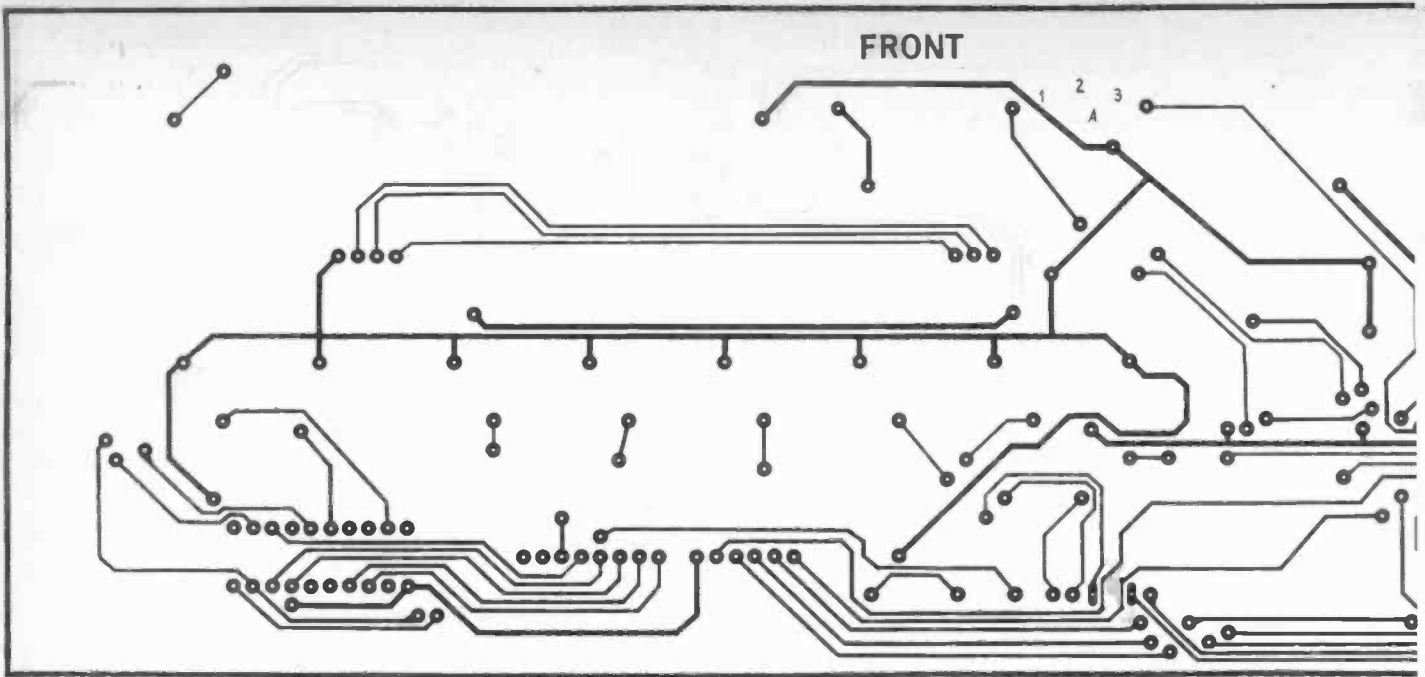


Fig. 2.9 (top). Front panel p.c.b. layout (component side, actual size)

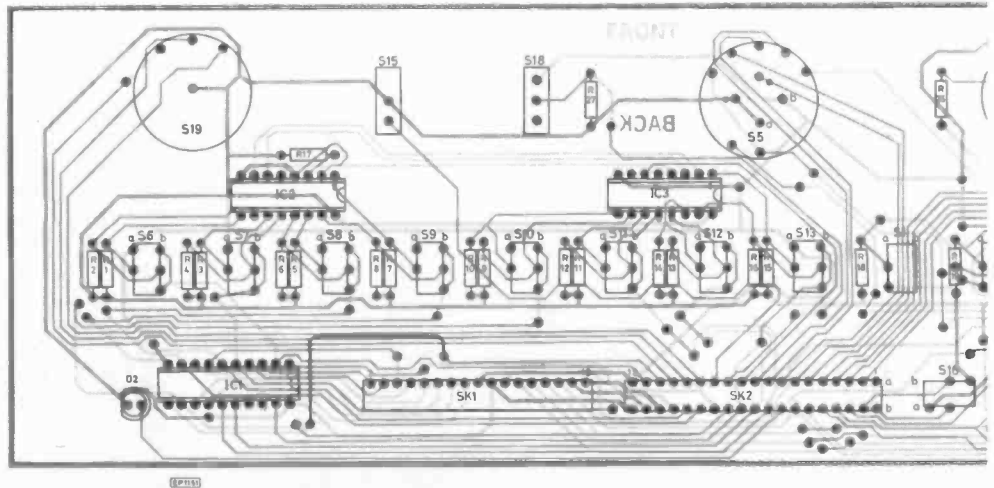

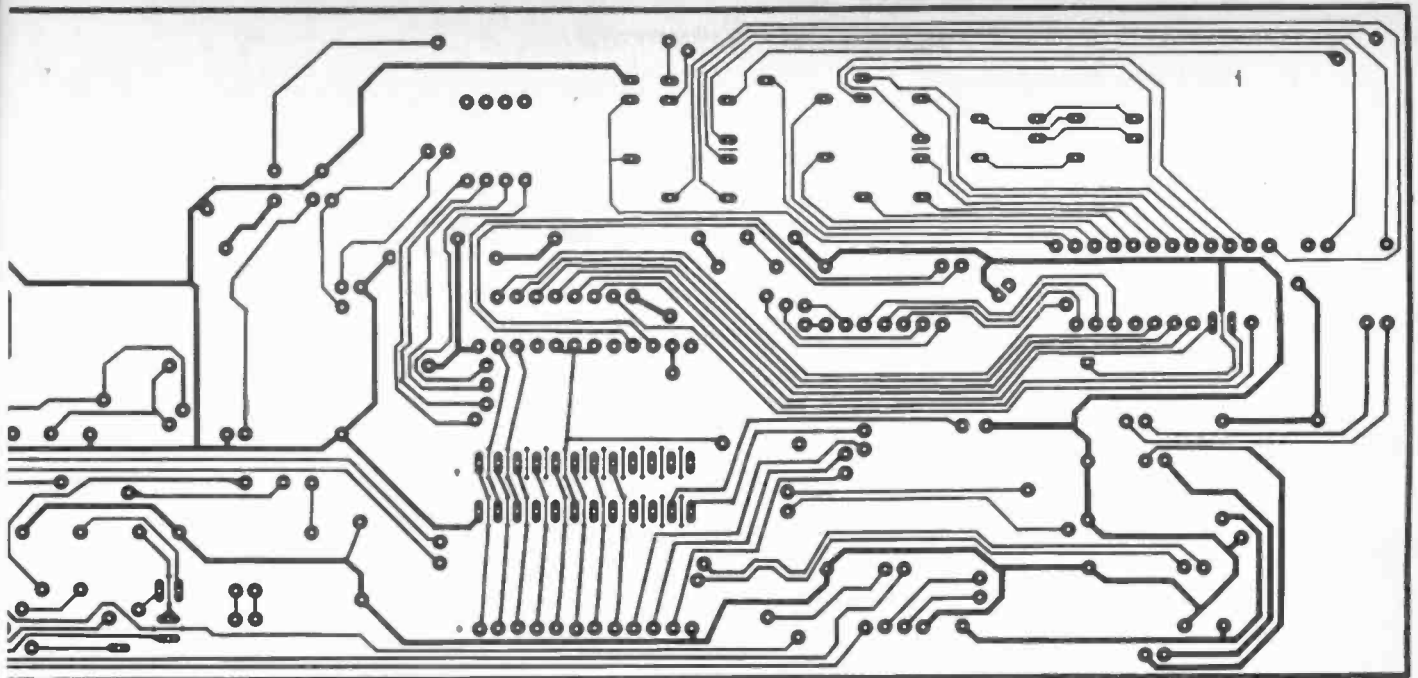

EC95

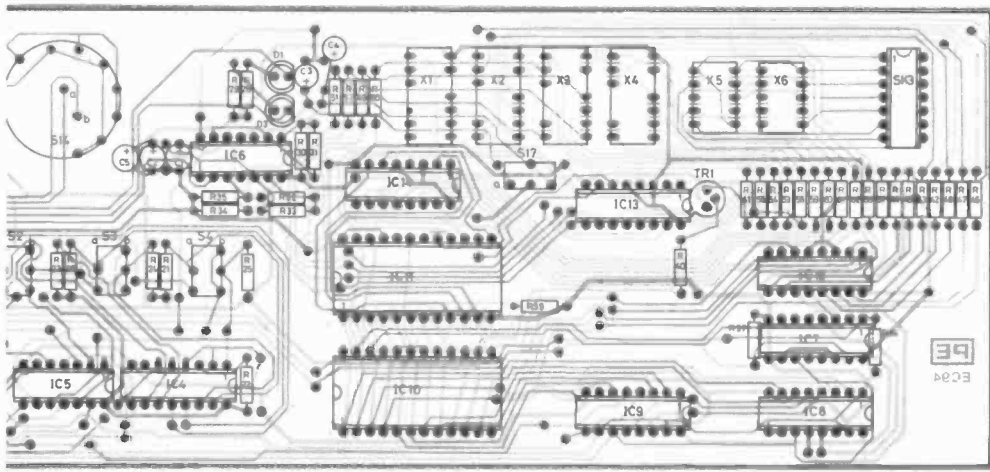
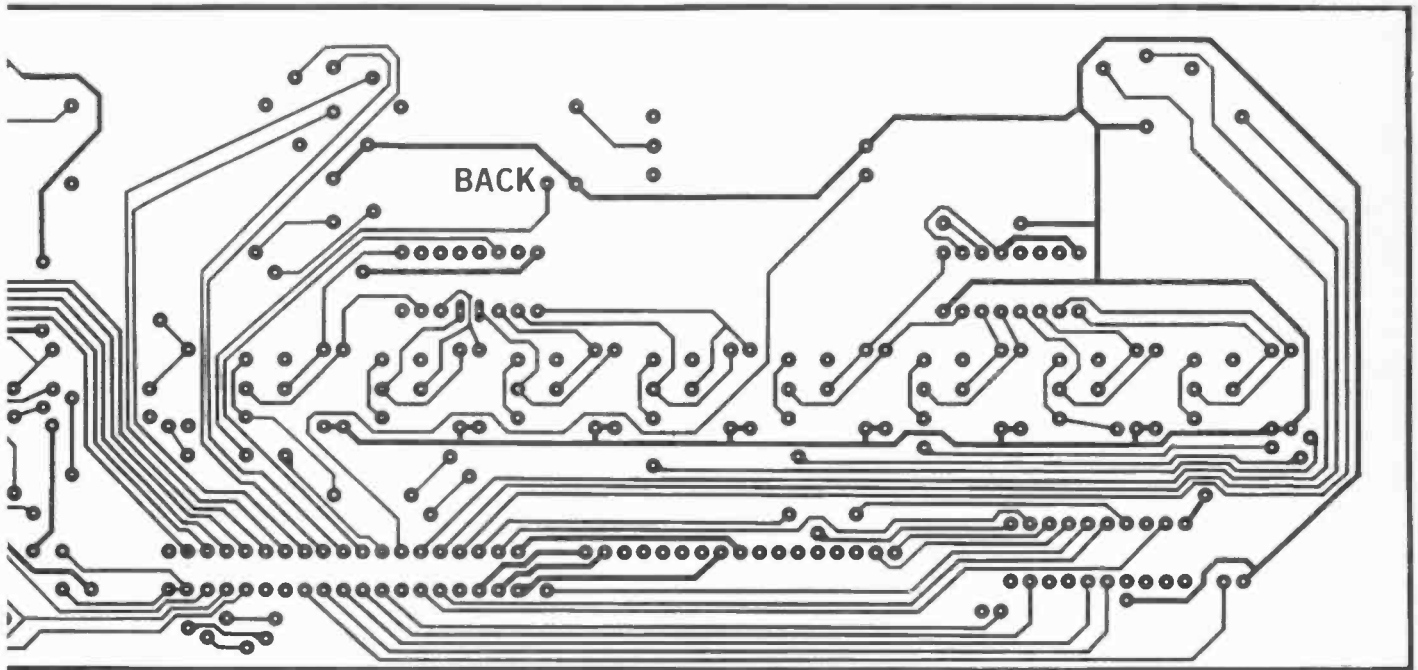


Fig. 2.10 (above). Front panel p.c.b. layout (track side, actual size)

Fig. 2.11. Front panel p.c.b. component layout

Initial calculations proved that a p.c.b. edge connector would conduct adequate current to supply the front panel p.c.b. However, the subsequent requirement of two 2716 EPROMS increased current consumption. To avoid a voltage drop due to track resistance a wire is connected between the +5V regulator and the front panel p.c.b. (close to the EPROMs). The 0V line could be similarly duplicated.

### COMPLETING THE BASIC UNIT

If the basic unit works as described, one can confidently complete the construction. Should problems arise, it is a simple matter to disassemble the unit because of the modularity of the design. Construction is completed as follows:

Remove the main p.c.b. from the front panel p.c.b., then

remove the p.c.b. from the panel. Mark the panel with Letraset, or if possible use the new photographic method using special sensitised sheets of aluminium. This method, although a little expensive, makes for a very neat finish. Mount the ON/OFF switch and S20 as well as SK101, SK102, SK103 and SK7. Refit the front panel p.c.b., using all the switch nuts. Fit the main p.c.b. to the case, as well as the front panel assembly. For the time being, leave the power supply leads longer than necessary and do not connect the ON/OFF switch up yet. Finally a 60mm length of ribbon cable can be prepared for one of the display options. Use 16-core ribbon cable and 16-pin headers. The headers should be fitted as shown in Fig. 2.8. (If both options are to be installed, make up two.)

**NEXT MONTH:** The Display Options.

## FREE! READERS' ADVERTISEMENT SERVICE

# PE BAZAAR

**RULES** Maximum of 16 words plus address and/or phone no. Private advertisers only (trade or business ads. can be placed in our classified columns). Items related to electronics only. No computer software. PE cannot accept responsibility for the accuracy of ads. or for any transaction arising between readers as a result of a free ad. We reserve the right to refuse advertisements. Each ad. must be accompanied by a cut-out valid "date corner". Ads. will not appear (or be returned) if these rules are broken.

**AKAI** 4000DS Tape Deck £60 o.n.o. Mattel Intellivision video games console with six cartridges £125 o.n.o. R. M. Potts, 1 St. Annes Crescent, Clenchwarton, King's Lynn, Norfolk. Tel: Kings Lynn 3171.

**KORG** MS10 Synthesiser as new, with guarantee £200, 16K ZX81 keyboard, I/O port, inverse video £100. J. Wilson, 36 Sunningdale Avenue, Lowestoft, Suffolk. Tel: (0502) 64729.

**WANTED** any polyphonic synthesiser, 3-6 octaves. Any offers? Mr. A. Goffart, Spindles, Lewannick, Launceston, Cornwall PL15 7QD. Tel: Coads Green 317.

**TECHNICAL** info. required for Olivetti TC800 floppy disk unit. Will pay for info. Mr. M. P. Morrow, 19 Rockhampton St., Gorton, Manchester 18. Tel: 061 231 3523.

**CROMEMCO** Bytesaver II S.100 board 8-Kbyte EPROM memory and programmer fully populated including 8 x 2708s £30. Tel: 0734 475180. Valentine Kassessloff, 372 Peppard Road, Caversham, Reading, Berks RG4 8UZ.

**EXIDY** Sorcerer Computer. P.W.O. 56K, 2 x 315K disk drives, MX80ft printer, monitor, lots programs. £7750 new—sell £2500 o.n.o. Mr. Hausser, 27 Fore Street, Bugle, nr St. Austell, Cornwall PL26 8PA. Tel: 0726 850129.

**VINTAGE** Wireless sets and spares urgently wanted. Must be pre-war equipment. Mr. S. Busbridge, 29 Clarence Drive, East Preston, Littlehampton, Sussex. Tel: Rustington (090-62) 5615.

**WANTED**, Sinclair t.v. 2 inch or 1 inch screen, must be in good condition. Phone Southampton 787960. John Marks, 92 Shirley Towers, Church Street, Shirley, Southampton.

**BBC** numeric keypad send s.a.e. for details. P.T. Squire, 16 Priory Park, Bradford on Avon, Wilts BA15 1QU.

**ZX81** + 16K with sounder + ZONIX prog. Sound generator + manual/books/tapes all nearly new £89. Peter Cunningham, 11 Berwyn Ave, Penyffordd, nr Chester, Clwyd. Tel: Caergwrlle 760172.

**AVO** valve (to collect) tester plus sundry electronic p.c.b.'s £10. P. Reynolds, 32 Common Approach, Benfleet, Essex SS7 3LA.

**UK101** 32 x 48 16K RAM 12K BASIC motherboard EPROMS + programmer, Sound 1/2MHz 3/600B + much software £170 o.n.o. N. Brooks, 103 Drake Rd., Harrow, Middx. HA2 9DZ. Tel: 01-868 9524.

**PRINTER** golfball type, 10 inch paper, serial I/O RS232 £75. Also PET interface to Centronic and disk. Both in good working order. R. Pearce, 8 Hollyoak Road, Cuxford, Southampton. Tel: (0703) 788278.

**ACORN** Atom full RAM. 3 introduction tapes, leads p.s.u. manual and circuit Acorn built £120 o.n.o. J. Brooks, 26 Duncan Way, Loughborough, Leics. LE11 0QN.

**SONY** open-reel VTR—offers. Maplin 2800 Synth, incomplete £100. Transcendent 2000 with carrying case £200. N. Dodsworth, 7 Neville House, George St., Corby, Northants. Tel: 0536 200105.

**WANTED** for UK101, new BASIC ROMS 1, 3 & 4. Frost, 133 Dorset Ave, South Wigston, Leicester. Tel: 0533 782852.

**PE** Micro Controller + data £35 carriage paid. D. Slater, 25 New Market St., Colne, Lancashire BB8 9BU.

**WANTED** video/audio u.h.f. modulator. UM1286 any reasonable price paid. Send details to: Mr. P. Rattray, 2 Dupplin Terrace, Kinnoull, Perth PH2 7DG.

**MICROTAN** 65 + manual, factory built. Never used. £30 o.n.o. Write to: Mr. D. Pritchard, 17 Effingham Rd, Billesley, Birmingham B13 0BN.

**NASCOM** 1 32K RAM 4800 Baud Cassette, with case, sep. ICL power supply 7 amp, what offers? Mr. P. Norman, 1 Blacksmiths Ct, Abbotsey, Cambridgeshire. Tel: Gt Gransden 479.

**OHIO** superboard £50 (faulty), various S100 boards cheap, scrap record decks £2 (direct drive) wanted minifloppy. Hugh Bridge, 363 Kennington Lane, Vauxhall, London SE11 5QY.

**RELAYS** 6-pole changeover 12V. coil (R.S. Stock No. 349-153) 40 off for sale new unused £1.25 each. Mr. D. Harries, 17 Eccleshall Ave, Oxley, Wolverhampton, Staffs. Tel: 0902 780958.

**ATARI** games console. Five cartridges including space invaders. Basic programming with keyboards, Joysticks and paddles £100. Mr. L. Allen, 14 Frampton Ct, Bournville, Birmingham B30 1QT.

**THANDAR** PFM200 Freq. meter, as new £55, PDM35 Microamps defective £15. Charles Bowden, 7 Parc Eglon, Helston, Cornwall TR13 8UP.

**WANTED** 20W amp. 2, 20W speakers. Hasan Abdulla, 58 Donnington Gdns, Reading, Berks RG1 5LZ.

**TEAC** 5½ inch twin disc drives 40 trk. single-sided cased + power supply, hardly used, £350. Also ROMDOS. C. Hellen, Vine Cott., Main Rd, Alresford, Colchester, Essex. Tel: 020622 5671.

Please publish the following small ad. FREE in the next available issue. I am not a dealer in electronics or associated equipment. I have read the rules. I enclose a cut-out valid date corner.

Signature ..... Date .....

Please read the RULES then write your advertisement here—one word to each box. Add your name, address and/or phone no.

**COUPON VALID FOR POSTING BEFORE 2 SEPTEMBER 1983.** (One month later for overseas readers.)

**SEND TO:** PE BAZAAR, PRACTICAL ELECTRONICS, WESTOVER HOUSE, WEST QUAY ROAD, POOLE, DORSET BH15 1JG.

BLOCK CAPITALS PLEASE

Name & Address:			

For readers who don't want to damage the issue send a photostat or a copy of the coupon (filled in of course) with a cut-out valid "date corner"





## Space Watch...

### THE SUN

It is rather difficult these days to select a theme for discussion from the multifarious new ideas around our own local star. At the present time there are arising a number of contradictory theories. To be fair, perhaps it might be kinder to say 'suggested ideas'. There is a point here about dispensing information. There abound suggestions of trouble internally, trouble externally and trouble at a distance.

A closer look at some of these is quite revealing. Over the last three or four years some doubts have arisen about current theories; some of these are the result of speculation. To bring the ideas together does present some difficulty but it is well worthwhile and an important consideration for the future of space activities. For obvious reasons in a review of this kind no persons are directly named or associated with any particular idea.

A steady watch has been kept on the rotation of the Sun for some time and these details are well documented. Conjectures as to whether it is a stable body, so far as position is concerned, are another matter. From Germany came information that the position of the centre of mass of the Sun undergoes continual change. It was shown that the centre of mass of the solar system changed its position relative to the Sun's centre for instance; observations made confirmed this shift.

The variations between 1945 and 1981 amounted to a spiral path which began half the Sun's diameter from outside the Sun to the centre of the Sun. This spiral continued until in 1982 it had passed still in spiral movement to a whole Sun's diameter outside the Sun. Extrapolation to 1990 shows it will again be at the centre of the Sun and thence—again on its way outside the Sun. Now the rate of this change is varying all the time, increasing as it moves nearer to the centre of the Sun and decreasing as it moves away from the centre. The speed is not constant but variable. This has been shown in some detail because it links with Sunspot cycles of various periods.

There is also current interest in matters dealing with unequal homogeneity of the Sun. This also adds to the confusion because here also there are different suggestions, such as sequential cycles of change of cyclic movements. Also there are doubts about some of the conclusions that have been drawn. Quite a

measure of new thinking is coming together at present—perhaps this is a sign. Perhaps the days when the populace took for granted what 'great men' said are over. Age offers the benefit of experience but that which is new or innovative belongs to all ages.

### SPACE FACTORIES

From the very beginning of the space era it has always been the plan to manufacture goods in space if possible. It has a simple answer to get away from Gravity. It is a little difficult to understand why it should be the cause of complaints. Now it is to be expected that better processes will be forthcoming from Earth based plants. It sounds very much like sour grapes on somebody's part. But then of course a band wagon is a band wagon. Perhaps it will be possible that people will get medication that is so badly needed. If the pilot attempts at electrophoresis were successful then the answer is 'go on'. If a better process is discovered let the people have the benefit.

### PIONEER 10

As this issue of *Spacewatch* is being written there are still a few hours to the time when Pioneer 10 will be the first man-made object to pass out of the Solar System. The spacecraft has far exceeded its design parameters. NASA hope to go on with tracking procedures until the 1990s. It survived the Jupiter hazards with striking success and taught us much. It takes some 4-5 hours for signals from the spacecraft to reach the Earth and now difficulties are arising. Navigation is a problem that is being dealt with at the present time.

At the great distance that exists between the spacecraft and the Sun preparations are now being made for an alternative system. NASA has been instructing the vehicle to make certain Moon Maps for itself. The Sun would by now only be a pin point. This then is the nature of this distant piece of equipment of man's devising which can now be taught from afar how to care for itself and its mater. It is rather a slow process though, for it takes a working day of some 9 hours for each session.

### A PIECE OF JUPITER

A small part of Oxfordshire has almost become a part of the planet Jupiter. At a cost of some £200,000 there will be an attempt to simulate the conditions that would be encountered by a visitor to that planet. This is the sample cell. It consists of a metal tube, double walled, some ten metres long. The imitation planet is like a gigantic thermos flask. It is expected to commence operations in October. At that time it will be fed with samples of gases to simulate atmospheric conditions virtually anywhere in the Solar System. When liquid nitrogen is passed through it, the double walled tube cools down the gases to as low as 170°C. The pressure in the tube can be varied between one millionth of an atmosphere to five times the Earth's atmospheric pressure at sea level. There is a spectrometer which records the spectral signatures of the gases within the tube.

A library of spectra would be available for researchers and they would save much time by

simply comparing spectrometer readings from a spacecraft with known readings gained on Earth. This will enable the NASA team to ensure that they gain full benefit from the results of the Galileo probe due to be launched in 1988. The Rutherford and Appleton Research Establishment will once again make contributions to the space age.

### UNREST ABOUT SATELLITE SPACE

Considerable concern is being expressed by many nations because of the amount of now useless hardware circulating in space. Complaints about this from those ready to take part in the Space Age have become very noticeable. A meeting is now being arranged for some thirty nations. The Third World is particularly annoyed with the present state of affairs. They are putting their case very strongly and saying that the developed countries already have more than their fair share.

Space above 30,000km contains the valuable geostationary orbits that are vital for communications such as television and telephone. Everybody naturally wants a part of it. The real trouble now is congestion—the frequency band allocated for this purpose is the 4GHz band; this means restraints. Not least of these is the fact that vast areas need to be covered in many cases and this would mean overlapping, and since some would call for areas as large as Western Europe the problem is very forbidding. It would mean that those countries wishing to cover large areas would dominate distribution.

Since this space has in many cases already been allocated the bands are full. The outcome is a very difficult problem under the circumstances since in the hands of some elements World chaos could be caused. Since the frequency bands allocated to television are in the 12.2–12.7GHz band and since also some 32 bands are allocated it means a separation of 20° for each band. The threat of 'overspill' is the real danger since each channel may need 200 watts. The Tower of Babel?

### VENERA

The Soviet Space Agency has launched two Venera space-craft for the exploration of Venus and other tasks. Accurate information is a little confusing with regard to these missions. It is certain that they are much more limited than the projects by NASA. According to American sources these two space-craft were launched on the 5th of June 1983 and the second on June 16th 1983. They are expected to begin their mission of imaging the surface of the planet or taking detailed radar altimeter data around October, probably in the early part of the month. The United States vehicle cannot be launched until 1986.

## Frank W. Hyde

# Ingenuity Unlimited

A selection of readers' original circuit ideas. Why not submit *your* idea? Any idea published will be paid for at £40 per magazine page.

Each idea submitted must be accompanied by a declaration to the effect that it has been tried and tested, is the original work of the undersigned, and that it has not been offered or accepted for publication elsewhere. It should be emphasised that these designs have not been proven by us. They will at any rate stimulate further thought.

Articles submitted for publication should conform to the usual practices of this journal, e.g. with regard to abbreviations and circuit symbols. Diagrams should be on separate sheets, not in the text.

## PROPORTIONAL A.C. CONTROL WITHOUT RFI

THE Versatile IC 555 timer is used here as a simple zero-crossing-detector of an a.c. mains supply, for proportional control of a.c. power. IC1 is connected as a monostable multivibrator as shown in Fig. 4, and is triggered at the crossing of every half cycle of the a.c. waveform. Two types of triggering control circuits are given in Figs. 1 & 2.

In Fig. 1, R1 and D1 form a potential divider across the a.c. mains supply and produce an approximate square wave output, which is in perfect phase relation with the input a.c. This is 180° phase shifted by the transistor stage TR1 and is added up by diodes D2 and D3 to generate negative

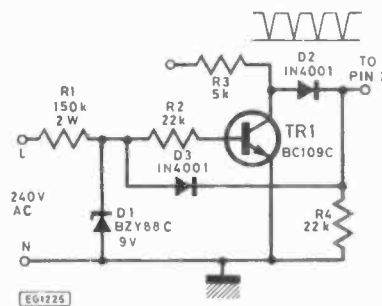


Fig. 1

pulses at each zero-crossing. This is fed to the trigger point IC1, pin 2 (Fig. 4). Alternatively the non-ideal square wave output from the potential divider itself can be used to trigger IC1, as shown in Fig. 2. This is possible because it is found that when the input at the trigger point (pin 2) either exceeds 1/3 Vcc or falls below -0.6V, the output at pin 3 goes high. Using this property IC1 is set and re-set every time these parameters occur and pulses are generated at the output pin 3, in proportion. However, the output pulses can be

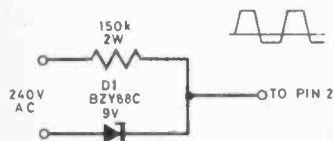


Fig. 2

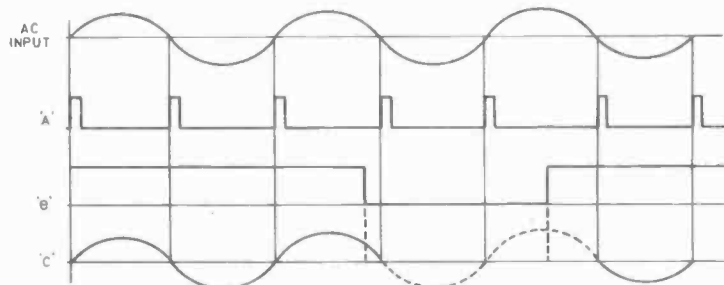


Fig. 3

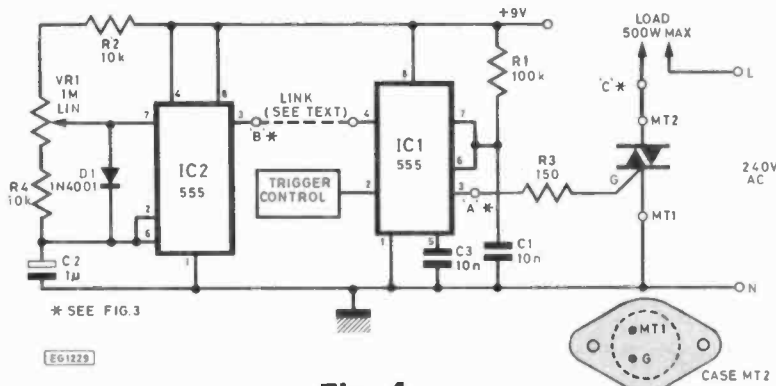


Fig. 4

widened by properly choosing the monostable time period. In both cases, the monostable time period is set by R1 and C1 to about 1ms to ensure firing of the triac.

Switching IC1, pin 4 (reset point) either to Vcc or ground, the triac makes simple On-Off control of power without RFI generation. For continuous control of power IC2, which is connected as a variable duty-ratio astable multivibrator, can drive pin 4 of IC1. The On-Off ratio is variable from about 1% to 99%. When the output of IC2 goes high, the triac is fired at every zero-crossing of a.c. supply as shown in Fig. 3. The output a.c. power is variable in discrete steps of half cycles, over the full range.

D. Venkatasubbiah,  
New Delhi.

# GENERAL PURPOSE TIMER

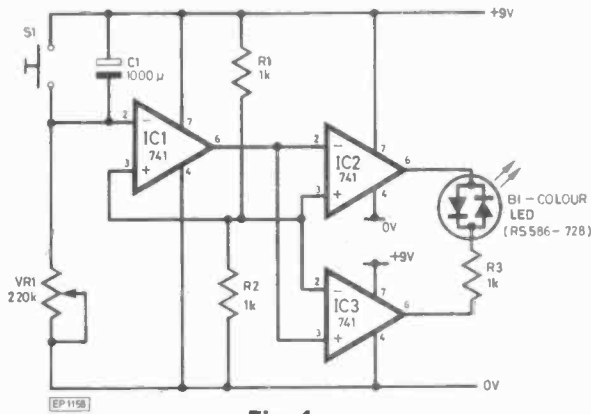


Fig. 1

THE circuit shown in Fig. 1 is a general purpose timer, which has a variety of uses. It is adjustable up to about three minutes and at the end of the timed sequence gives a visible output in the form of a colour change of the two-colour l.e.d.

The circuit operation is as follows:

When the push button is depressed C1 is momentarily short-circuited, which leaves IC1 (pin 2) at 9 volts. This voltage slowly reduces towards zero, as the capacitor is charged up. The charging rate is dependent upon the value set by the variable resistor (VR1). When the voltage is reduced to less than the voltage at IC1 (pin 3) (half supply voltage), the output of IC1 switches from zero to 9 volts, which in turn causes a change in the output states of IC2 and IC3. This reverses the direction of the current between these two outputs and so changes the colour displayed by the l.e.d.

This prototype was based on a 9 volt supply though the time constant should remain the same irrespective of the supply voltage.

A. Marshall,  
Old Basford,  
Nottingham.

## OVER VOLTAGE PROTECTION

THE above circuit was developed for an existing variable 3-20V 0-20A stabilised power supply, based on a 741 design. It should work with any similar power supply with little or no modification.

Obviously with a power supply of such a large current rating, an over voltage circuit was considered essential.

The protection circuit is designed to operate at about 1V above the output

voltage of the p.s.u. i.e. if the p.s.u. was set to 10V then it would trip at about 11V and so on.


IC1 is used as a comparator and compares, via R3 and R4, the reference voltage for IC2 with its feedback voltage from the output. Normally, when the regulator stage is working correctly these two voltages are the same, regardless of what the p.s.u. is set at. If however a fault occurs causing the output to go above the set voltage, IC1 senses the change between the reference and feedback voltages and turns TR1 on. This energises the relay which self latches via the normally open

contacts and disconnects the mains supply from the regulator circuit.



Pre-set R5 determines the point at which the circuit operates above the output voltage of the p.s.u., and should be adjusted to between  $\frac{1}{2}$ V and 1V across R4.

If the output voltage of the p.s.u. is turned down quickly with a fairly large capacitive load, the circuit will trip. This however can be reset by S1 'push to break' which unlatches the relay, the contacts of which must be capable of carrying 20A.

N. Wilson,  
King's Lynn,  
Norfolk.

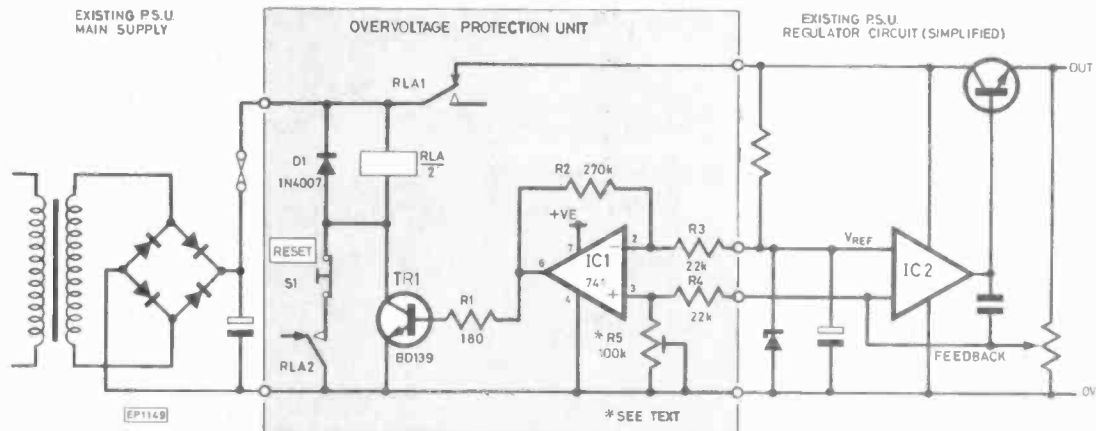

# PSEUDO TELEPHONE RINGER

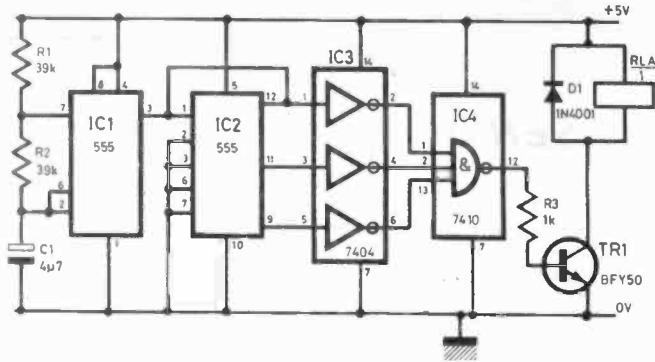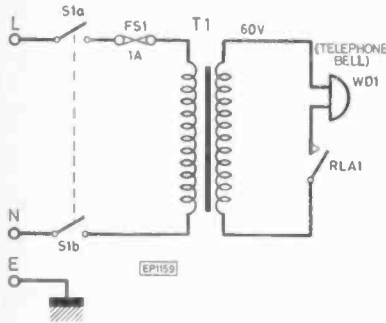

THIS circuit was used in our school play in order to simulate a telephone ringing sound using a standard telephone (WD1).

IC1 provides a square wave with a frequency pulse of around 0.6 sec which is

fed to the decade counter (IC2). Two pulses are selected by the gates of IC3, which through IC4 switch the relay and sound the bell.

J.K. Yeoman,  
Haywards Heath.

# AUTOMATIC NI-CAD CHARGER

THE circuit shown permits mass-plate ni-cad cells to be left unattended while charging at their maximum rate (one tenth capacity), automatically giving an indication and switching off the current when charging is complete, thus preventing damage to the cells. Battery voltages from 1.2V to 12V with charging rates of 6mA to 1A can be accommodated simply by selecting the appropriate component values.

The charging current is generated by IC2 which is a 5V regulator connected as a constant current source, the output of which is set by R8. IC1 is an 8211 voltage detector chip. At switch-on C2 holds pin 3

of IC1 low, producing a 0V condition on pin 4 which operates TR1 and hence D6 and RLA. RLA1 connects the constant current-output to the battery to be charged.

As the battery charges the voltage at 'A' increases until eventually pin 3 of IC1 reaches 1.15V, at this point pin 4 goes from 0V to open circuit, TR1 switches off and TR2 operates causing RLA to release, D6 to extinguish and D8 to light. This disconnects the charging current to the battery and holds pin 3 of IC1 high, hence to reset it is necessary to switch the power off and then on again.

To initially set the circuit up calculate the required value of R8 and assemble the components, omitting VR1 and R1 with a strap between points A and B. Connect up the battery to be used in conjunction with the charger and switch on. When satisfied that it is fully charged measure the voltage at A, from this determine the values of

VR1 and R1 to be used and connect them in circuit. VR1 is selected to provide a degree of fine adjustment because as the cells approach their fully charged state the increase in voltage is small.

With the battery connected and charged adjust VR1 until D6 just extinguishes. When satisfied that it is properly set up the strap between A and B can be removed and the circuit function rechecked.


$$I_c = \frac{\text{Capacity of battery to be charged}}{10}$$

$$R8 = \frac{5}{(I_c - (5 \times 10^{-3}))} \Omega$$

$$R1 + R2 = (\text{voltage at A} \times (10.43 \times 10^4)) - (12 \times 10^4)$$

See text for (voltage at A).

G. Francis,  
Filton,  
Bristol.

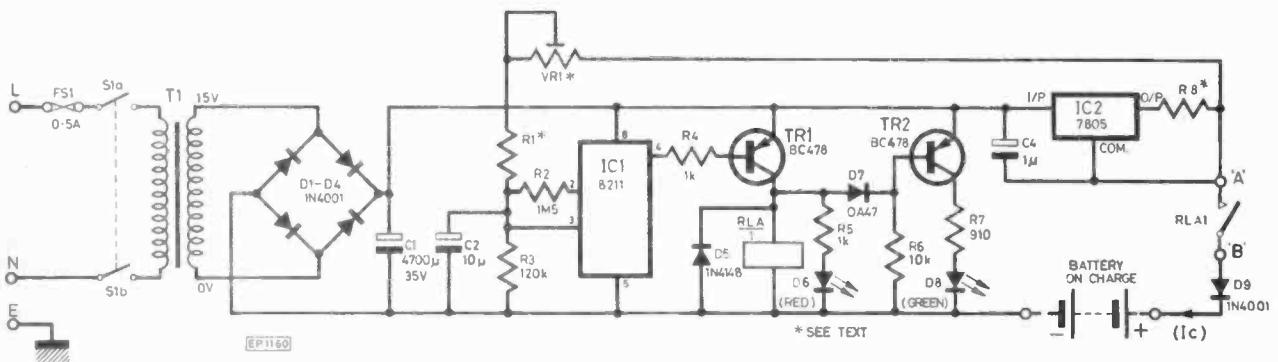

## SOUND CHASER

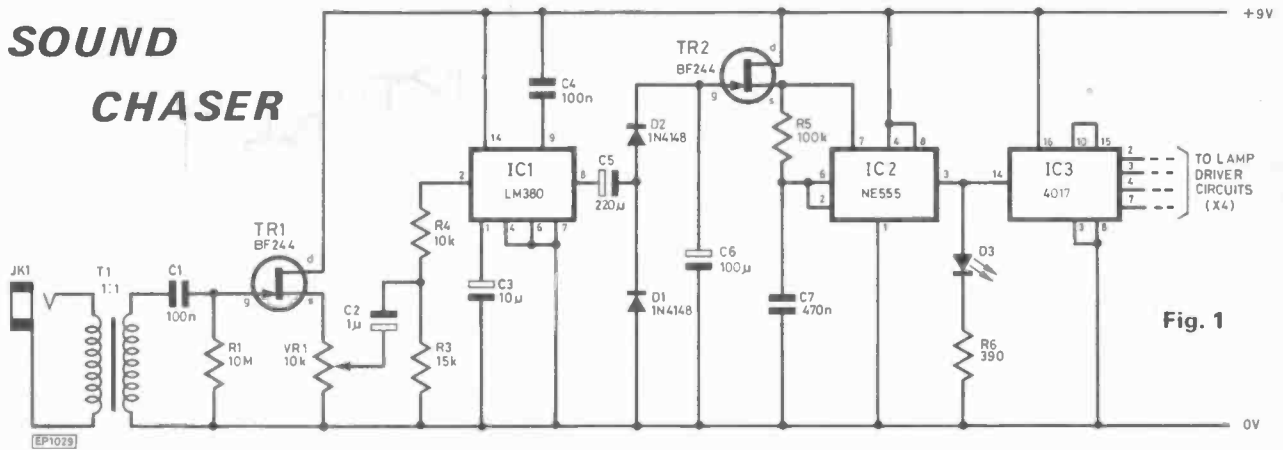


Fig. 1

NUMEROUS circuits for disco light displays have been published but there still remains a gap in the market. On one hand there are sound to light displays, but these generally give an ambiguous flickering light display. Alternatively there are chasers which, while not flickering, are not related to the music and so do not stimulate dancing.

This circuit is for a sequencer where the light change frequency is determined by the tempo and volume of the music which is more interesting than the more usual types of display.

TR1 and IC1 are used to amplify the input signal to the correct level which is then rectified by D2 to give an envelope of what appears across C6. The voltage of the gate determines the source-drain impedance of the f.e.t., TR2, which is one of the frequency determining components of IC2. The oscillator output is fed to IC3. The four outputs of this are each fed to a driver circuit (Fig. 2) which drives the bulbs.

A. Garraway,  
Ashford,  
Kent.

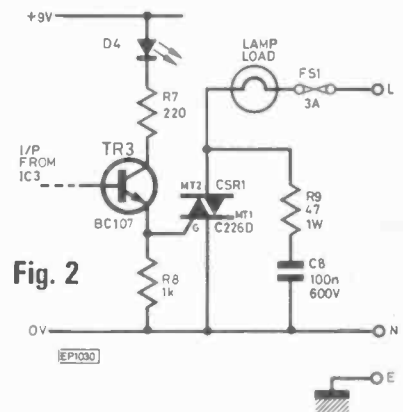


Fig. 2

THIS circuit combines reasonable simplicity with good control of the lamp from zero to maximum brightness.


CSR1 is a low current triac (RS 262-028) which acts as a zero crossing detector, R2 being too great to allow it to turn on permanently. The pulses so obtained are used to discharge C2 via TR1 every half cycle. C2 is charged by R3 and VR2. When the voltage across C2 exceeds about 8V, the Zener conducts switching on the main triac CSR2 via TR2.

Lamp intensity is controlled by VR2. When this is set to zero the lamp will be at maximum brightness. With VR2 set to maximum resistance, VR1 can be adjusted so that the lamp goes out.

When installing the unit into your projector remember that CSR2 must have an adequate heat sink. R1 and R4 should be 0.5W resistors.

J. O. Linton,  
Harrogate.

## SLIDE PROJECTOR DIMMER

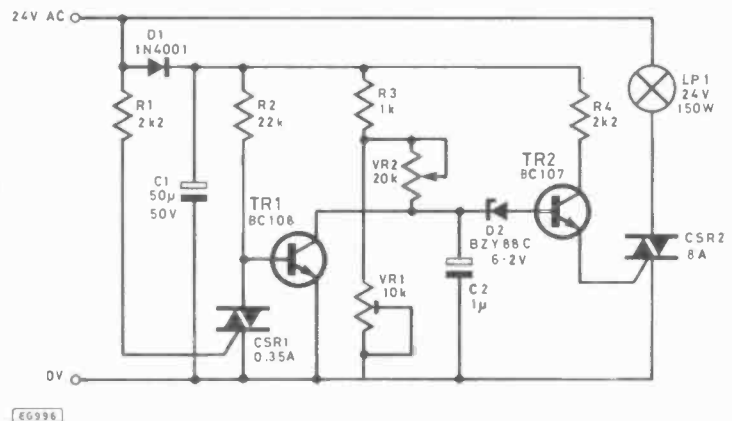


EG996

## INTRUDER ALARM WITH CAMERA UNIT

A desirable feature for intruder alarms is to identify the intruder when the location is unoccupied.

This is easily achieved by incorporating a camera unit with an auto-wind facility, the shutter release being triggered at the moment of intrusion.

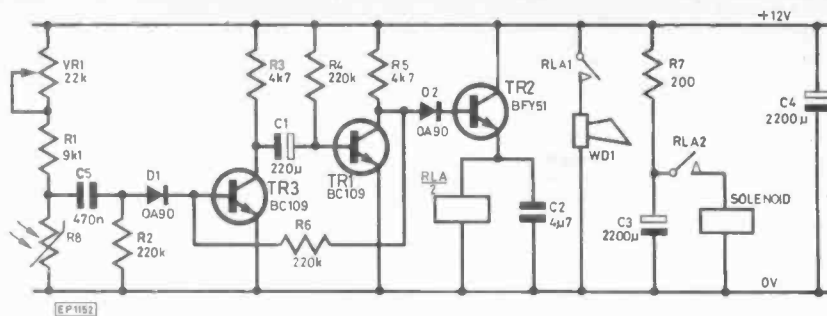The circuit is light to dark activated. By enclosing the photo cell in a 20mm dia by 50mm long tube, high directional sen-



sitivity can be achieved, coupled with high immunity to false alarms.

TR1 and TR3 form a monostable network, while TR2 acts as a relay driver, drawing virtually no current in the quiescent state.

The relay (RLA) is used to switch on a

siren (WD1) as well as energise a solenoid activated striker attached to the shutter release.

S. N. Rumala,  
Minna,  
Nigeria.


## SHOP BELL DELAY

MANY small shops have a switch and bell system connected to their door. The owner has provided this so that he is informed of the arrival of a customer in the shop when he is elsewhere. However, during busy periods, the noise of the bell repeatedly sounding can be unpleasant.

This simple circuit reduces the number of times the bell will ring by preventing a second sounding shortly after the first. It will operate directly from a 12V or 8V bell transformer supply, since diode D1 performs rectification. Alternatively, it may

be run from a battery—in which case it will give very long battery life as it draws only  $\frac{1}{2}$  mA, even when the bell is ringing.

Operation is as follows—when the bell

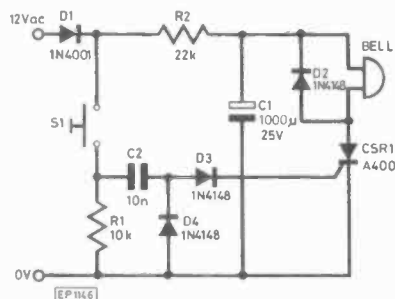

has not been rung for a time, C1 is fully charged through R2, and once charged no more current is taken from the supply. When the door operated switch S1 is closed, C2 is charged through the gate of the SCR, which in turn connects the bell across C1 which discharges through the bell giving a ring of about one second. D2 protects the SCR by damping spikes produced by the bell. Since the time constant C1/R2 is many seconds, the bell cannot immediately be rung again.

The type of SCR used is not critical and the CSR1A400 or a similar TO5 device will work well.

D. J. Greaves,  
Cambridge.

## OVERSEAS AGENTS

Subscriptions to PE are available direct from us — see notice on page 50 — however, there are also a number of overseas agents around the world who can accept your subscription order. These agents are listed below for your information and assistance.

### BELGIUM

Agence et Messageries  
De La Press SA  
1 Rue de la Petite-Ile  
B-1070 Brussels

Industrial & Business Pubs.  
200 Avenue de Messidor  
BTE 4  
1180 Brussels

Office International De Librairie  
S.P.R.L.  
30 Avenue Marnix  
1050 Brussels 5

Scientific & Technical Book  
Centre  
Rue de Neuchatel 12  
1060 Brussels

W. H. Smith & Son (Belgium)  
S.A.N.V.  
Boulevard A Max Lean 71-79  
B-1000 Brussels

### DENMARK

Arnold Busck Boghandel  
Kjobmagergade 49  
Copenhagen K DK 1150

Dansk Centralagentur D C A  
/inc Tidskrift Service/  
Slusholmen 6-8  
DK-2450 Copenhagen SV

Dansk Bladdistribution  
v/Mogens Schroder  
Rosenberggade 54  
P.O. Box 2125  
DK-1015 Copenhagen K

DBK Subscription Service  
Sijjangan 6  
DK-2300 Copenhagen 5

Jul Gjallerups Boghandel  
Solvgade 87  
DK-1307 Copenhagen K

N J Haaseg BogImport A/S  
Loevstraede 8  
1132 Copenhagen K

Munksgaard Int.  
Book & Pubs Ltd.  
35 Norre Sogade  
DK-1370 Copenhagen K

Rhodos International  
Subscription Agency  
Strandgade 36  
Copenhagen DK-1401

### SCIENTIA

International Sub Agency Aps  
Loevstraede 4A  
DK-1152 Copenhagen K

### FINLAND

Akateeminen Kirjakauppa Oy  
P.O. Box 128  
SF 00101 Helsinki 10

Lehtimarket Oy  
P.O. Box 16  
SF-00311  
Helsinki 51

Lehtitoimisto Kankainen  
P 119  
SF-28101 Pori 10

Suomalainen Kirjakauppa Oy  
C/o Rautakirja Oy  
Subscription Department  
P.O. Box 2  
01641 Vantaa 64

### FRANCE

B E D I  
8 Place de la Republique  
75011 Paris

### S. Brentano

Subscription Department  
37 Avenue de L'Opera  
75002 Paris

Dawson-France SA  
B P 40  
F-91121 Palaiseau

Europériodiques SA  
31 Avenue de Versailles  
78170 La Celle St. Cloud

France Publications  
108 Rue Reaumur  
Paris 75002

Lavoisier Abonnements  
Technique et Documentation  
11 Rue Lavoisier  
F-75384 Cedex 08

Mons. R. Martin  
Boite Postale 22  
92420 Vaucresson

Office International de  
Documentation et Librairie  
48 Rue Gay-Lussac  
75240 Paris Cedex 05

W. H. Smith & Son SA  
248 Rue de Rivoli  
75001 Paris  
Attn: Miss M. Nolot  
Subscription Department

**W. GERMANY**

Ex Libris Buchhandelsges  
Ferdinand-Dirichs-Weg 28  
6 Frankfurt-AM-Main

Philip Korter & Co.  
Mode-Press-Vertrieb  
P.O. Box 1536  
D-6800 Mannheim 1

Kunst & Wissen-Erich Bieber  
Postfach 46  
Wilhelmstrasse 4  
7000 Stuttgart 1

W. E. Saarbach GmbH  
Postfach 10 16 10  
Follerstrasse 2  
5 Cologne 1

H. G. Schaderbrodt  
St. Andre Strasse 26A  
6105 Ober-Ramstadt

Buchhdig Konrad Wittwer  
Koenigstr 30  
Postfach 147  
7 Stuttgart

**D.D.R.**

Buchexport Volkseigener  
Ausserhandelsbetrieb Der  
D.D.R.  
701 Leipzig Postfach 160  
Leninstrasse 16

**ITALY**

Anglo American Book Co. SRL  
Via Della Vite 57  
00187 Roma

Bozzi F. Illi S.A.S.  
Piazza Della Meridiana 2  
16124 Genova

Centre Edizioni Technische  
Internazionali SRL  
Via Pordonone 17  
20132 Milan  
Attn: Mr. A. Vais

Goerlich & Co.  
Via San Senatore 6/2  
Casella Postale 1712  
Milan 20100

Ulrich Hoepfli  
Casa Editrice Libreria  
Via U Hoepfli 5  
20121 Milan

Interscientia  
Via Mazze 28  
10149

Nuova Stampamerica Subs  
Agency SAS  
Via P. Mcca 3  
10121 Torino

Sperling & Kupfer  
Piazza San Babila 1  
20122 Milan

Lib. Internazionale Di Stefano  
Via C Roccatagliata Ceccardi  
16121 Genova

**NETHERLANDS**

Bookimpex B.V.  
Veenkade 26/27  
The Hague 2513 EG

D & N-Faxon B.V.  
Subscription Service  
P.O. Box 197 1000 AD  
Amsterdam

International Journals Group  
P.O. Box 2192  
1000 CD Amsterdam  
For the attention of: Ms. W.  
Boenker

Kniphorst's Boekhandel  
Postbus 67  
6700 VB Wageningen

De Muiderkring N.V.  
Nijverheidswarf 17-21  
1400 AA Bussum

Martinius Nijhoffs Boekhandel  
P.O. Box 269  
250 AX The Hague

Swets Subscription Service  
P.O. Box 830  
2160 SZ Lisse

**NORWAY**

A/S Narvesnes  
Litteraturtjenste  
Box 6125 Etterstad  
Oslo 6

Tidsskriften Sentralen Tanum-  
A/S  
P.O. Box 1177 Sentrum  
Oslo 1

**SPAIN**

Commercial Atheneum S.A.  
Apartado De Correos 1148 de  
Barcelona  
E-Barcelona

Diaz De Santos  
Wholesale Subscription Agency  
Lagasca 95  
Madrid 6

Distribuidora Internacional-  
Dinter  
Apartado 9156  
Duque de Sesto 38  
Madrid 9

Libreria Mundi-Prensa  
Apartado 1223  
Castello 37  
Madrid 1

**SWEDEN**

Esselte Tidsskrifts Centralen  
Subscription Agency  
P.O. Box 62  
Gamla Brogatan 26  
S-101 20 Stockholm  
Attn: Mr. D. Schuttz-Subs  
Manager

Lundgrens Bokhandel  
Sodergatan 3  
S-211 34 Malmö

SCI-TECH Publications AB  
Box 73  
122 21 Enskede 1

Utlandsk Facklitteratur  
Tage Nilsson  
Tranaskvarnsgatan 6 C  
S-573 00 Tranås

Wennergren Williams AB  
Fack  
S-104 25 Stockholm 30

**SWITZERLAND**

J. de Croze International  
Establishment  
81 Avenue Louis Casai  
P.O. Box 44-1216  
Geneva

Hans Huber Booksellers  
Langgasstrasse 76  
CH 3000 Bern 9

Neville and CIE  
5-7 Rue Levlir  
Case Postale 887  
CH 1211 Geneva 1

Kurt Staheli & Co.  
Bahnhofstrasse 70  
CH-8021 Zurich

**U.S.S.R.**

Mezhdundarodnaja Kniga  
G-200  
Moscow

**AUSTRALIA**

Collins Booksellers Pty Ltd  
115 Elizabeth Street  
Melbourne  
Victoria 3000

Attn: Subscription Dept. 2nd  
Floor

Engineering Publications (Aust)  
P.O. Box 319  
Spit Junction  
N.S.W. 2088

Globe Subscription Agency Pty  
Ltd  
P.O. Box 471  
Double Bay  
N.S.W. 2028

Gordon & Gotch Limited  
P.O. Box 29  
Burwood 3125  
Victoria

John Hinton Pty Ltd  
P.O. Box 311  
Chatswood  
N.S.W. 2067

International Subscription  
Agencies Pty Ltd  
P.O. Box 709  
Toowong Qld 4066

McGills Authorised  
Newsagency Pty Ltd  
187-193 Elizabeth Street  
Melbourne  
Victoria 3000

Robinson Mantony Pty Ltd  
190 Bourke Street  
Melbourne  
Victoria 3000

Standard Book Suppliers Pty  
Ltd  
Subs Department  
136 Rundle Street  
Adelaide 5000

Tait Book Shop  
415 Bourke Street  
Melbourne C1

Mrs. Camille Sandham  
The Technical Book & Magazine  
Co.  
289-299 Swanston Street  
GPO Box 2192 T  
Melbourne  
Victoria 3000

Thoroughbred & Classic  
Agencies  
321 Warrigall Road  
Cheltenham  
Victoria 3192

University Co-operative  
Bookshop  
76-84 Bay St  
Broadway  
N.S.W. 2007

**ARGENTINA**

Carlos A. Traboulsi (Bookstore)  
Casilla de Correo 4574  
1000 Buenos Aires

**BRAZIL**

P.T.I. Ltda  
Subscription Agents  
Caixa Postale 1703  
01000 Sao Paulo SP

**CHINA**

China National Pubs Import  
CDR  
P.O. Box 88  
Peking

**INDIA**

Allied Publishers Ltd  
Post Box 155  
13/14 Asaf Ali Road  
New Delhi 110002

Allied Publishers Subscription  
Agency  
15 J.N. Heredia Marg.  
Ballard Estate  
Bombay 400038

Allied Publishers Subscription  
Agency  
750 Mount Road  
Madras 600002

Central News Agency  
23/90 Connaught Circus  
New Delhi 110001

Creative Books & Periodicals  
Pvt Ltd  
7 Nanabhal Lane  
Bombay 400-023

Higginbothams Private Ltd  
165 Anna Salai  
(Post Box 311)  
Madras 600002

Global Publishers Service Pte  
Ltd  
Block A31 3rd Floor  
Shai Ram Industrial Estate  
GD Ambekar Road, POB No  
7121  
Bombay 400 031

International Book House Pte  
Ltd  
Indian Mercantile Mansion Extn  
Madame Cama Road  
Bombay 400 039

L. B. Publishers & Distributors  
(Private) Ltd  
90-91 Mahatma Gandhi Road  
Bangalore 560 001

Macmillan India Limited  
Subscription Department  
21 Patullo Road  
Madras 600 002  
Tamil Nadu

Mahajan Brothers  
Super Market-Basement  
Ashram Road  
Ahmedabad-9 (GS)

Strand Book Stall  
Dhanur  
Sir P M Road  
Bombay 1

Subscribers Subscription  
Services India  
21 Raghunath Dadaji Street  
2nd Floor  
Bombay 400 001

Universal Subscription Agency  
Pvt Ltd  
117/H-1/294-B Model Town  
Pandu Nagar  
Kanpur 208005

**ISRAEL**

Hakhen Agencies Ltd  
44 Derekh Petah Tikva  
Tel Aviv  
P.O. Box 36125

ABC Bookstore  
71 Allenby Road  
Tel Aviv  
P.O. Box 1283

Sifriat Poalim Limited  
Supply Department  
73 Allenby Street  
Post Box 526  
Tel Aviv

**JAPAN**

Asahiya Shoten Ltd  
Foreign Books Dept  
Central POB 398  
Osaka 530-91

Hokuto Trading Co. Ltd  
4-5 Aizumi-Cho  
Shinjyuku-Ku  
Tokyo 160

Kjokuniya Company Ltd  
Attn: Teruzo Kubota  
General Manager, Journal Dept  
Odakyu West-Shinjyuku Bldg  
47-1, 1 Chome, Hatsudai  
Shibuya-Ku  
Tokyo 151

Japan Pub Trading Co. Ltd  
P.O. Box 5030  
Tokyo International  
Tokyo 100-31

Kaigai Publications Ltd  
P.O. Box 5020  
Tokyo International  
100-31 Tokyo

Kitao Publications Trading Co.  
Ltd  
New Asaki Bldg  
3-18 Nakanoshima 2-chome  
Kita-ku C P O Box 936  
Osaka 530-91

Kokusai Shobo Ltd  
5 Ogawamachi 3-chome  
Kanda  
Chiyoda-ku  
Tokyo 101

Koyo Shoji Co. Ltd  
Nitto Bldg  
4-10 Nihonbashi Hongoku-Cho  
Chuo-Ku  
Tokyo 103

Maruzen Co. Ltd  
P.O. Box 5050  
Tokyo International  
100-31

Oriental Book Service Co. Ltd  
C/o Roppongi Building  
11-4 Roppongi 4-chome  
Minato-Ku  
Tokyo 106

O.T.O. Research Corporation  
Takeuchi Bldg.  
1-34-12 Takatanobaba  
Shinjyuku-Ku  
Tokyo 160

Pacific Book Inc  
Morikawa Building  
7-41 Idabashi 1-Chome  
Chiyoda-Ku  
Tokyo 102

Sanyo Shuppan Boeki Co. Inc  
Chief Foreign Dept  
P.O. Box 5037  
Tokyo International 100-31

Shimada & Co. Inc  
9-29 Minami-Aoyama 5-Chome  
Minato-Ku  
Tokyo 107

Tokyo Publications Service Ltd  
P.O. Box 5085  
Tokyo International  
Tokyo 100-31

U.S. Asiatic Co. Ltd  
Tsutsumi Building  
13-12 1-Chome Shimbashi  
Minato-Ku  
Tokyo

**MALAYSIA**

S S T Trading Sdn Bhd  
385 Jln 5/59 P.O. Box 227  
Petaling Jaya  
Selangor

**NEW ZEALAND**

Gordon & Gotch (NZ) Ltd  
P.O. Box 3207  
Auckland

R. Hill & Son Ltd  
Ideal House  
Eden Street  
Newmarket, Auckland 1

Peryer Educational Books (S.I.)  
Ltd  
8 Yaldhurst Road, Upper  
Riccarrton  
Christchurch 4  
P.O. Box 6034

Technical Books Ltd  
P.O. Box 5174  
1st Floor, McKenzies Bldg.  
(Opp. Kirkcaldies)  
222 Lambton Quay  
Wellington

**SOUTH AFRICA**

American & Overseas  
Publications (Pty) Ltd  
Box 42476 Fordsburg  
Johannesburg Tvl 2033

Argo Publications  
Post Box 1475  
Johannesburg 2000

Messrs. M & L Ettin  
International Journals  
P.O. Box 68321, Broadway  
Johannesburg 2020

Mr. Harold C. Leon  
P.O. Box 6114  
Marshalltown 2107  
Transvaal

Technical Books (Pty) Ltd  
P.O. Box 2866  
Capetown 8000

Trelaw Subscription Agency  
P.O. Box 8255  
Johannesburg

Universitas Books (Pty) Ltd  
P.O. Box 775  
Pretoria 0001

# Computer Hobbyists... £50 for your program!

PE is interested in buying software written by hobbyists for popular microcomputers. If you have a game, biorhythm, mortgage, bank, filing, calendar or other general purpose program you have written yourself we would like to see it—even if you are new to software writing.

We will offer £50 for each accepted program, so send it in, you have nothing to lose.

Program tapes carrying your name and address and, if possible, a listing should be sent to Practical Electronics Software, IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset. Each program should be accompanied by the following signed declaration:

The enclosed program entitled ..... is my own work and has not been offered to any other company. The program is for a ..... machine (state type of computer it will run on). It requires . . . .K of memory.


If you are under 16 years please get your parent or guardian to countersign the declaration.

All tapes will be returned.
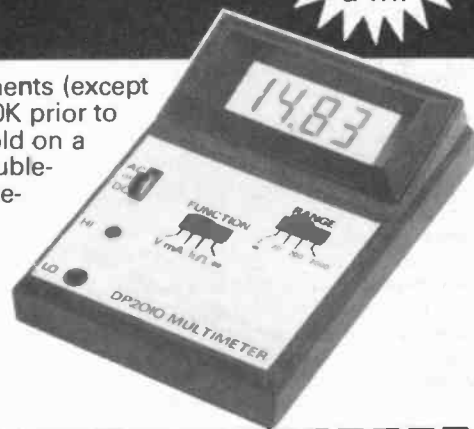
## SUMMER SALE! DIGITAL MULTIMETER KITS

ONLY  
£9.95 ea  
PLUS P&P  
& VAT

These 3½ digit handheld DMM's are fully complete with all components (except PP3 battery) and test leads. We are using up all stocks of the DP2010K prior to launch of a new range of meters in the Autumn. The Kits will be sold on a 'first come first served' basis, and are fully guaranteed. A trouble-shooting and calibration service will be maintained. This is a once-only opportunity to make a DMM at an incredibly low price. Supplied with a comprehensive description of operation and full constructional data.



### TYPICAL SPECIFICATION

Function	PSD	Accuracy	Function	FSD	Accuracy
Volts (d.c.)	2V	1.5% ±1 digit	Current (a.c.)	2mA	2%±5 digit
	20V			20mA	2%±5 digit
	200V			200mA	4%±5 digit
	500V			2000mA	12%±5 digit
Current (d.c.)	2mA	1%±1 digit	Resistance	2k	1%±1 digit
	20mA	1%±1 digit		20k	1%±1 digit
	200mA	3%±1 digit		200k	1%±1 digit
	2000mA	10%±1 digit		2000k	1%±1 digit
Volts (a.c.)	2V	2% ±5 digit	Diode Test	2V	1%±1 digit
	20V				
	200V				
	500V				

Please allow 28 days for delivery.

**LASCAR ELECTRONICS LIMITED**  
Module House, Whiteparish, Salisbury, Wilts. Tel. 07948-567

**LASCAR ELECTRONICS LIMITED**  
Module House, Whiteparish, Salisbury, Wilts.  
Tel. 07948-567

PLEASE SEND ME .....kits at £12.59 each  
I enclose cheque/P.O./Access no. ....  
Amount .....  
NAME .....  
ADDRESS .....

Export Orders please add £5 for airmail despatch.



# Patents Review

Copies of Patents can be obtained from:  
the Patents Office Sales, St. Mary Cray, Orpington, Kent. Price £1.60 each.

## POWER-CUT RESERVE

Precise Power Corporation of Florida has filed a European patent application 0069568 on a clever system for saving computer data during a power-cut. According to the inventor it can also insulate computer users from related problems, like unstable mains frequency and voltage.


Fig. 1 shows a patented solution. Three-phase mains comes in at 20 to drive synchronous motor 12 which is in direct mechanical connection with generator 14. This produces a replica of the mains voltage which is fed out on line 22 to the computer load 24. The motor 12 also drives a second

## SOUND SENSITIVE SWITCH

James Taylor of Oregon has filed a European patent application 0067502 on a sound sensitive light switch. The idea is to replace an existing wall switch with a sensor that turns the lights on when it hears a noise. It then leaves them on while the noise continues, and switches them off after a period of silence. This way you can turn the lights on in a dark room simply by tapping the wall or making a noise. People who leave the lights on when they leave a room will no longer waste electricity because the lights will switch off automatically. There is an over-ride for people who like to make a noise in the dark


or sit silently with the lights on.

In the circuit (Fig. 1) a microphone feeds a signal on line 22 to fixed gain amplifier 24 which is connected to variable gain amplifier 26. Sensitivity is controlled by variable resistor 27. Transistor 30 is normally biased on, but when the signal from amplifier 26 exceeds a threshold it is shut off. A re-set signal on line 8 triggers oscillator and counter chip 33 to produce a timed control signal on line 12 for triacs 44, 64. Photo resistor 32 biases transistor 30 when the switch is in a well-lit area, so that sensitivity to noise is less in daylight. On/off over-ride is provided by circuit 14. Variable resistor 54 controls triac 44 so that the unit can also be used as a conventional dimmer.

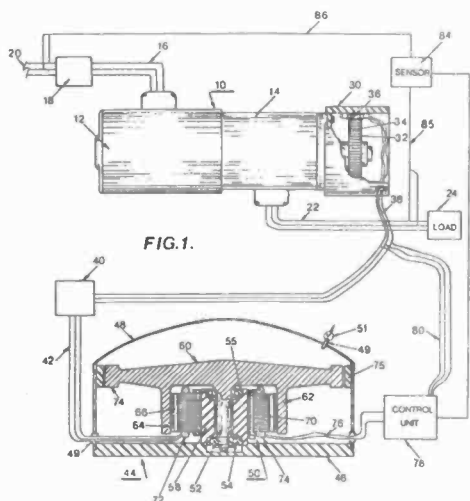

generator 30, which outputs a high frequency supply, e.g. ten times the mains frequency, on line 38. This high frequency current drives a motor 50 which carries a heavy flywheel 60 running in a vacuum or other low windage-loss atmosphere. The wheel takes around half an hour to run up to full speed, but when it is running it stores around 5kW hours of energy.

Under normal mains supply conditions, the computer takes its power from the mains via the ganged motor 12 and generator 14. If the mains supply fails or falls the flywheel keeps running, with its speed falling only slightly over a period of minutes. The second generator 30 now functions as a drive motor for the mains generator 14. So the computer receives a constant power supply. When power is restored, the flywheel works up to full speed again, which takes between 15 and 30 minutes.

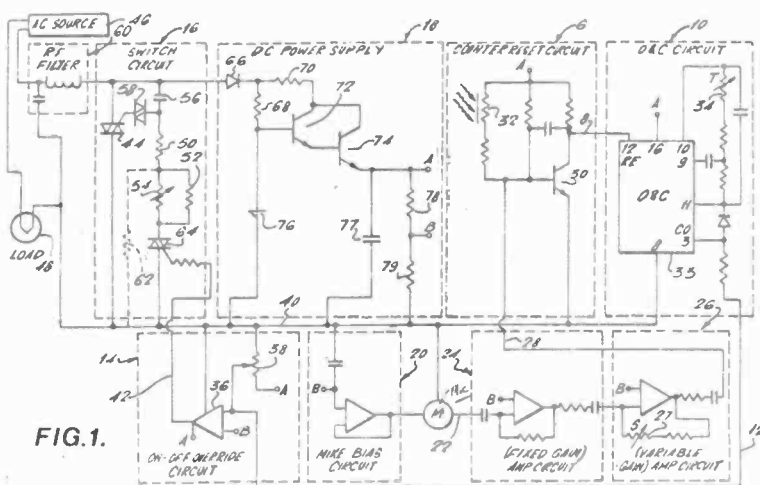

## QUART INTO PINT POT

The BBC, in British patent 2 105 548, suggests a simple approach to modifying the aspect ratio of a TV picture, to give wide screen images, without using up more transmission bandwidth. The traditional 4:3 ratio is of course now out of date, because most films are shot in a wider screen format. For projection television there is much to be said for widening the ratio. But this normally requires a complete re-think on the technology, as for instance pursued by Sony with its 1125 line, high definition, 5:3 wide screen TV system.

The BBC believes that the existing 625 line, PAL system can be easily modified to give a wider aspect ratio. Conventionally each picture line is transmitted in 64 microseconds, but only 52 microseconds are used for picture display. The remaining 12 microseconds, known as the horizontal

blanking interval, are used to carry a synchronizing pulse for the horizontal sync circuits, a black level clamp pulse and a colour burst to synchronize the PAL decoder.

The blanking interval is also used to let the scanning spot glide back to the start of the next line. But in future solid state displays, such as i.c.d. or l.e.d. screens, won't need fly back time. Also, according to the BBC, the colour synchronizing information can be drastically shortened in time, or eliminated altogether, and the receiver locked by the sound carrier. This leaves up to 60 microseconds of each 64 microsecond line available for picture display, which in turn can give a wide screen aspect ratio with no increase in video bandwidth. Although the system would be impractical for broadcast transmission, because it would require receiver modifications, it could be used over existing channels for closed circuit TV of wide screen format.

# MICRO-BUS

Compiled by DJD.

Appearing every two months, Micro-Bus presents ideas, applications, and programs for the most popular microprocessors; ones that you are unlikely to find in the manufacturers' data. The most original ideas often come from readers working on their own systems; payment will be made for any contribution featured.

THIS month's Micro-Bus features an EPROM extension board for the ZX81 or ZX80, a BASIC program to solve simultaneous equations, and the solutions to the BASIC problems featured in the last Micro-Bus.

## EPROM EXTENSION BOARD

The circuit shown in Fig. 1 was submitted by I. P. Bryant, and will add up to 8K of EPROM or RAM to a ZX80 or ZX81. The extra memory appears in the memory space directly above the 8K monitor ROM, and the circuit uses 2716 or 2516 EPROMs as these are available at a reasonable price.

The circuit is interfaced to the ZX81 bus by means of the edge connector. For ZX80 users there is no ROM chip select signal on the connector, but this can be created by connecting IC6 pin 6 to the spare edge connector, and then cutting the track between IC12 pin 11 and IC6 pin 6 and connecting a 680 ohm resistor across the break. The edge connector will now be identical to the ZX81's.

The circuit does not need to include any write protection because the 1k resistors in the ZX80/81's data bus provide this.

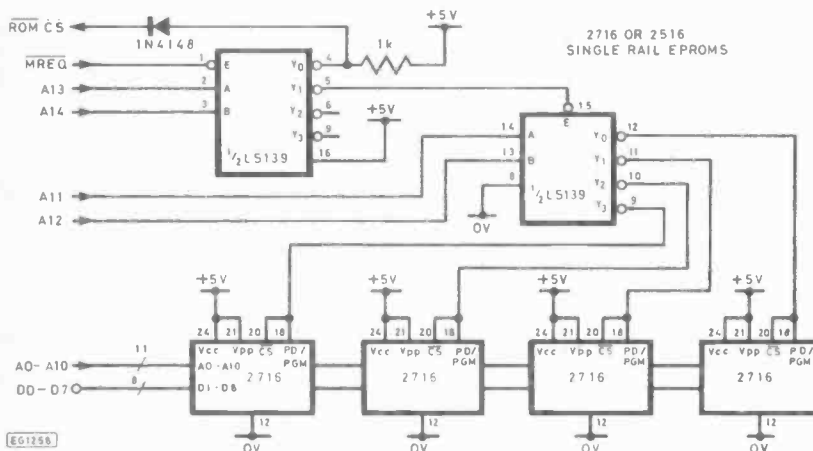


Fig. 1. Circuit adds 8K of EPROMs to a ZX80 or ZX81

## SIMULTANEOUS EQUATIONS

Simultaneous equations crop up in many different branches of electronics. For example, one can determine the resistive, capacitive, and inductive components of a passive component by measuring its impedance at three

different frequencies, and then solving three simultaneous equations to find R, C, and L. The BASIC program of Fig. 2 was submitted by A. Schoutz of South Africa, and can be used to solve such equations. The program was developed on a ZX81, but can fairly easily be modified to run on any BASIC-speaking microcomputer.

The number of equations which can be solved is dependent only on the amount of available memory. On a ZX81 with a 16K RAM pack the program has no trouble solving ten equations with ten unknowns, and takes about 22 seconds. As an example, to solve the three equations:

$$a + 2b + 3c = 42$$

$$7a + b - 8c = 36$$

$$3a - 2b + 2c = 54$$

one enters the coefficients in order:

1, 2, 3, 42, 7, 1, -8, 36, 3, -2, 54.

The program should then produce the correct answer:

$$a = 14, b = 2, c = 8.$$

## PROGRAM OPERATION

The program, lines 10 to 150, first inputs the number of equations and sets up three

```

5 REM *** SIMULTANEOUS EQUATIONS ***
10 PRINT "NO. OF EQUATIONS = ";
15 Q=37
20 INPUT N
30 PRINT N
40 DIM A(N,N)
50 DIM B(N)
60 DIM X(N)
70 LET C=INT(30/(N+1))
80 FOR I=1 TO N
90 FOR J=1 TO N
100 INPUT A(I,J)
110 PRINT AT I*2,J*2;"A(I,J)";" ";CHR$(J+Q)
120 NEXT J
130 INPUT B(I)
140 PRINT AT I*2,J*2;"B(I)";" ";B(I)
150 NEXT I

1000 FAST
1001 FOR I=1 TO N-1
1002 LET R=I
1003 LET M=A(I,I)
1004 FOR J=I+1 TO N
1005 IF A(J,I)<M THEN GOTO 1008
1006 LET R=J
1007 LET M=A(I,J)
1008 NEXT J
1009 IF M=0 THEN PRINT "SOLUTION ABORTED."
1010 IF R=I THEN GOTO 1019
1011 FOR K=1 TO N
1012 LET S=A(I,K)
1013 LET A(I,K)=A(R,K)
1014 LET A(R,K)=S
1015 NEXT K
1016 LET S=B(I)
1017 LET B(I)=B(R)
1018 LET B(R)=S
1019 FOR J=I+1 TO N
1020 LET M=A(J,I)/A(I,I)
1021 FOR K=1 TO N
1022 LET A(J,K)=A(J,K)-M*A(I,K)
1023 NEXT K
1024 LET B(J)=B(J)-M*B(I)
1025 NEXT J
1026 NEXT I
1027 REM BACK SUBSTITUTION
1028 LET X(N)=B(N)/A(N,N)
1029 FOR I=N-1 TO 1 STEP -1
1030 LET S=0
1031 FOR J=I+1 TO N
1032 LET S=S+X(J)*A(I,J)
1033 NEXT J
1034 LET X(I)=(B(I)-S)/A(I,I)
1035 NEXT I
1036 PRINT "-----"
1037 SLOW
1038 FOR I=1 TO N
1039 LET J=(N+1)*I*2
1040 IF J<=20 THEN GOTO 1046
1041 SCROLL
1042 SCROLL
1043 PRINT AT 20,0;CHR$(I+Q);"=";" ";X(I)
1044 NEXT I
1045 STOP
1046 PRINT AT J,0;CHR$(I+Q);"=";" ";X(I)
1047 NEXT I
1048 STOP
    
```

Fig. 2. Program for the ZX81 will solve simultaneous equations

those features peculiar to the ZX81 will have to be altered. The value of Q on line 15 is chosen so that CHR\$(Q+1) will give the letter A, for the printing of the equation variables; other machines that use ASCII will need Q=64. The PRINT AT Y,X statement in lines 110, 140, 1043, and 1046 can be replaced by

a TAB(X,Y) function, but note that the order of row and column is the other way round. Finally, the commands FAST, SLOW, and SCROLL can be removed.

## PUZZLE SOLUTIONS

Here we present the solutions to the six problems featured in the last Micro-Bus. Each problem centred around a program written in BBC BASIC, and readers were invited to send in solutions.

### NUMBER TRICK

In the first problem you were asked to explain how a "number trick" worked. The appearance of the trick was as follows: a spectator was shown 60 random numbers, and asked to remember one; they were then shown a selection of numbers, and asked to say whether their number was present. After 6 such selections the program was (usually) able to name the number they were thinking of.

The trick works on the principle that six yes/no (binary) pieces of information will serve to distinguish between up to 64 different things (since  $2^6=64$ ). For the sake of screen layout the trick used only 60 different numbers, and random numbers are substituted for the numbers 1 to 60 simply to disguise the trick. These random numbers are stored in an array numbered 1 to 60 and the following explanation refers to them as A(1) to A(60).

Each selection shows only those numbers that have a '1' in a particular position in their binary representation. This is achieved in the program by the expression:

```
IF (N DIV 2^(6-M)) MOD 2 THEN PRINT A(N);
```

which only prints the Nth number if N has a '1' in position M. For example, if M is 6 the expression is effectively:

```
IF N MOD 2 THEN PRINT A(N);
```

and the numbers A(1), A(3), A(5) . . . etc will be printed. The selection procedure is repeated for values of M from 1 to 6. The spectator's six yes/no replies are then assembled into a binary number which directly gives the position N of the chosen random number.

As a postscript to the trick you were asked whether the trick might ever fail. The answer is yes! If, by chance, a random number appears more than once in the initial set of 60 numbers the spectator's replies will cause an incorrect identification; in fact, the computer will reply with the number whose position N is the logical OR of the positions of the spectator's numbers. This unlikely event could easily be avoided by ensuring that the 60 random numbers were all different.

### MYSTERIOUS SEQUENCE

The next problem was to explain why the sequence of numbers:

2, 5, 10, 17, 26, 37, 50, 65, 82

was printed out by a program which performed some manipulations on an array of 100 numbers. The operation of the program can be made slightly more obvious if it is modified, as shown in Fig. 3, so that the arrays start from 0 rather than 1; the sequence printed out is then: 1, 4, 9, 16, 25, 36, 49, 64, 81, 100

which may be familiar as the squares of the numbers 1 to 10. These result for the following reason: we start off with an array A(0) to A(100) whose elements are all zero, or 'false'.

```
10 DIM A(100)
20 FOR N=1 TO 100
30 FOR J=0 TO 100 STEP N
40 A(J)=NOT A(J)
50 NEXT J: NEXT N
60 REM
70 FOR N=0 TO 100
80 IF A(N) THEN PRINT N;
90 NEXT N
```

**Fig. 3. The Mysterious Sequence problem is revealed by this BASIC program which prints out a series of squares**

Then, for each value of N from 1 to 100 every Nth element is inverted. For example, A(6) will be inverted for N=1, 2, 3, and 6, and since it has been inverted four times it will end up with the value 'false'. It is clear that each element of the array is inverted once for each of its divisors, so only numbers with an odd number of divisors will end up 'true'. Now, only perfect squares have an odd number of different divisors, since all other numbers can be expressed only as the product of two different numbers, so the numbers printed out by the program in Fig. 3 will be all the squares. The program given in the original problem adds one to these numbers by starting the array from 1 rather than 0.

### NUMBER TRAILS

The next puzzle program took a starting number, and found the sum of the squares of the digits of that number. This process was repeated until a stable result, such as '1', was obtained, which was printed out. The examples 7 and 19 were given, each of which gives 1 as an eventual result. In the latter case we obtain the trail:

19 → 82 → 68 → 100 → 1

If you tried the program with other starting numbers you were probably frustrated to find that the program 'hung up'; we can see why if we take the starting value '4':

4 → 16 → 37 → 58 → 89 → 145 → 42 → 20 → 4 . . . .

and so the sequence repeats for ever, never reaching a stable value. However, if we add a test for this loop to the terminating condition by altering line 60 to:

```
60 UNTIL S=T OR T=4
```

we find that every number up to 99 either ends on 1, or reaches 4 indicating that it is in this loop. It is fairly easy to see that all starting values above 99 will soon lead to a value below 99, so every starting number, however large, will eventually lead to one of these two possibilities.

If the rule is to cube each digit before adding, the picture is somewhat more complicated, and we leave this for exploration by the reader; suffice it to say that the system contains five stable end numbers (one of which is 371), and two loops.

### DECIMAL TO HEX

The decimal-to-hex program used the unusual recursive definition of a function FNHEX shown in Fig. 4 to convert a number

```
10 DIGITSS="0123456789ABCDEF"
20 DEF FNHEX(DEC)
30 IF DEC<16 THEN =MID$(DIGITSS,DEC+1,1)
40 =FNHEX(DEC DIV 16)+FNHEX(DEC MOD 16)
```

**Fig. 4. Recursive function converts decimal number DEC to a hexadecimal string**

DEC into a string representation of its hex equivalent. The definition, in plain English, is as follows: "To convert a number into hexadecimal: if it is less than 16 then the result is the corresponding hex digit extracted from the string DIGIT\$; otherwise the answer is a string formed by the hex equivalent of the number divided by 16, followed by the hex equivalent of the number mod 16.

The problem was to explain why the hex equivalents of the decimal numbers in the series 1111, 11111, 111111, 1111111 . . . all end in the digit '7'. Looking at this series, it is obvious that each term differs from the previous one by a multiple of 10000; for example, 1111111 - 111111 is 1000000, obviously a multiple of 10000. Now, this number 10000 is itself a multiple of 16, so in hex it is a number which ends in zero. Thus adding multiples of 10000 to 1111 does not effect the last digit of the hexadecimal form of the result. The same is obviously true for series consisting of any repeated digit.

Incidentally, the problem of generating a series of N '1's is made especially simple by using the EVAL and STRING functions with the expression:

```
40 J=EVAL$(STRING$(N,"1"))
```

The same method can be used for investigating the behaviour of other series.

### RECURSIVE FUNCTION

The last of the puzzle programs printed out the first ten values of a mystery function. For

```
2 MODE 0: DIM A(250)
5 FOR N=0 TO 250
7 DRAW N*4, FNH(N)*7: NEXT: END
10 DEF FNH(N)
20 IF N<2 THEN A(N)=1: =1
30 A(B)=A(N-A(N-1))+A(N-A(N-2)): =A(N)
```

**Fig. 5. Program plots the behaviour of a non-recursive version of the FNH function**

fairly large values of the function it takes a long time to calculate values, but we can rewrite it non-recursively to calculate the first 250 values and plot them; see Fig. 5.

### TWICE FUNCTION

As a postscript, readers were asked to construct a function FNTWICE which would

```
FNTWICE(AS,N) = EVAL
(AS + "(" + AS + "(" + STR$(N) + ")")"
```

**Fig. 6. TWICE function in BBC BASIC evaluates any given function twice**

take any function, and perform its operation twice in succession. The solution is shown in Fig. 6, and makes use of the versatile EVAL function provided in BBC BASIC which evaluates an expression passed to it.

The function works as follows. Suppose we call it to evaluate:

```
FNTWICE("SQR",256)
```

The function will construct the string:

```
"SQR(SQR(256))"
```

and pass it to EVAL to be evaluated, giving the result 4.

### BEST SOLUTIONS

The next Micro-Bus will give the names of the readers who sent in the best solutions to these problems.



# SMALL ADS

The prepaid rate for classified advertisements is 34 pence per word (minimum 12 words), box number 60p extra. Semi-display setting £11.20 per single column centimetre (minimum 2.5 cms). All cheques, postal orders etc., to be made payable to Practical Electronics and crossed "Lloyds Banks Ltd". Treasury notes should always be sent registered post. Advertisements, together with remittance, should be sent to the Classified Advertisement Dept., Practical Electronics, Room 2612, IPC Magazines Limited, King's Reach Tower, Stamford St., London, SE1 9LS. (Telephone 01-261 5846).

## NOTICE TO READERS

Whilst prices of goods shown in classified advertisements are correct at the time of closing for press, readers are advised to check with the advertiser to check both prices and availability of goods before ordering from non-current issues of the magazine.

When replying to Classified Advertisements please ensure:

- (A) That your have clearly stated your requirements.
- (B) That you have enclosed the right remittance.
- (C) That your name and address is written in block capitals, and
- (D) That your letter is correctly addressed to the advertiser.

This will assist advertisers in processing and despatching orders with the minimum of delay.

## RECEIVERS AND COMPONENTS

300 SMALL COMPONENTS, including transistors, diodes £2.20. 7lbs assorted components £6.00. Fifty 74 series I.C.s on panel £2.20 post paid. List 25p refundable. J.W.B. RADIO, 2 Barnfield Crescent, Sale, Cheshire, M33 1NL.

JULY PCB'S. Solder resist coated. Down counter - £2.44, up counter - £4.70. Down counter/controller - £4.05. Complete set - £10.00. All prices include P&P. Tel: (0865) 60741 for August prices/trade enquiries. - Bradley Printed Circuits (G.D. Cowan), 9 Harcourt Terrace, Headington, Oxford OX3 7QF.

ELECTRONIC COMPONENTS MERSEYSIDE, MYCA Electronics, 2 Victoria Place, Seacombe Ferry Square, Wallasey, Merseyside L44 6NR. Tel: 051-638 8647. Open Mon - Sat, 10 am - 5.30 pm.

## RESISTOR PACKS FOR ALL PROJECTS

1/2 watt carbon film resistors 5% 1 ohm to 10M E24 series. Packs of 10 each value (1690 resistors) £12.50. Your choice of quantities/values 100 for £1.00. VAT and Post Free.

GORDON HALLET

20 Bull Lane, Maiden Newton, Dorchester, Dorset DT2 0BG

**BOURNEMOUTH/BOSCOMBE.** Electronic components specialists for 33 years. Forresters (National Radio Supplies). Late Holdenhurst Road, Npw at 36, Ashley Road, Boscombe. Tel. 302204. Closed Weds.

**TURN YOUR SURPLUS** capacitors, transistors, etc. into cash. Contact **COLES HARDING & CO** 103 SOUTH BRINK, WISBECH, CAMBS. TEL: 0945 584188. Immediate settlement.

### NDW OPEN IN NEWCASTLE

For the best in Electronic Components. Test Equipment and Accessories.

#### MARLBOROUGH ELECTRONIC COMPONENTS

15 Waterloo Street, Newcastle NE1 4DE Tel. 618377

Open 9am-6pm Mon-Sat - Easy Parking  
Stockists of:  
Transistors, Resistors, Capacitors, I.C. Diodes, Electronic Books, Etc.

### BRAND NEW COMPONENTS BY RETURN

**Electrolytic Capacitors 16V, 25V, 50V.**  
0.47, 1.0, 2.2, 4.7 & 10 Mfds. — 5p.  
22 & 47—6p. 100—7p. (50V—8p). 220—8p.  
(50V—10p). 470—11p. (40V—16p). 1000/15V—15p.  
1000/25V—25p. 1000/40V—35p.

**Subminiature bead Tantalum electrolytics.**  
0.1, 0.22, 0.47, 1.0 & 35V, 4.7 & 6.3V — 14p.  
2-2/35V, 4.7/25V—15p. 10/25V, 15/16V—20p.  
22/16V, 33/10V, 47/8V, 68/3V & 100/3V—20p.  
15/25V, 22/25V, 47/10V—35p. 47/16V—80p.

**Subminiature Ceramic Caps. E12 Series 100V.**  
2% 10 pf. to 47 pf.—3p. 56 pf. to 330 pf.—4p.  
10% 390 pf. to 4700 pf.—4p.

**Vertical Mounting Ceramic Plate Caps. 50V.**  
E12 22 pf. to 1000 pf. E6 1500 pf. to 47000 pf.—2p.  
**Polystyrene E12 Series 63V. Horizontal Mntg.**  
10 pf. to 820 pf.—3p. 1000 pf. to 10,000 pf.—4p.

**Miniature Polyester 250V Vert. Mtg. E6 Series.**  
01 to 068—4p. 1—5p. 15, 22—6p. 33, 47—10p.  
68 — 12p. 1.0 — 15p. 1.5 — 22p. 2.2 — 24p.

**Mylar (Polyester) Film 100V. Vertical Mounting.**  
001, 0022, 0047—3p. 01, 022—4p. 04, 05, 0.1—5p.

**High Stability Miniature Film Resistors 5%.**

1/4W E24 Series 0.51R—10MΩ (Except 7MΩ)—1p.

1/4W E12 Series 1R0 to 10MΩ.—1p.

1/4W E12 Series 10R to 10MΩ.—5p.

1/4W metal film E12 Series 10R-1MΩ. 5% — 2p. 1% — 3p.

1N4148—2p. 1N4002—4p. 1N4006—8p. 1N4007—7p.

BC107/B/9—12p. BC147/B/9, BC157/B/9, BF195 & 7—10p.

8 Pin I.C.s. 741 Op. amp.—18p. 555 Timer—24p.

Dil. Holders 8 pin—3p. 14 pin—12p. 16 pin—14p.

LED's 3 & 5mm. Red—10p. Green & Yellow—14p.

Grommets for 3mm—1p. Grommets for 5mm—2p.

20mm. Q.B. Fuses. 15, 25, 5, 1, 2, 3 & 5A—5p.

20mm. Anti Surge 100mA to 5.0A—8p.

20mm. Fuseholders P.C. or Chassis Mtg.—8p.

Battery Snaps (pairs) PP3—6p. PP9—12p.

400mW Zener diodes E24 series 2V7 to 33V—8p.

Prices VAT Inclusive Post 15p. (Free over £5.00).

### THE C. R. SUPPLY CO.

127, Chesterfield Rd., Sheffield S8 0RN.

**PROBLEMS GETTING COMPONENTS?** Try Commercial Products. We have access to all the latest devices and hardware. Ring: 0293 30174.

Ex-Govt transmitter type 440 complete station in used condition £17. Telephonists headset & mic (sound powered) new in box £4.00. Basic oscilloscope unit 240V AC contains X & Y amps, all solid state. size 14 1/2" x 9", tube dia 5", most units have tube burn marks £15.00. Aircraft mounted 35m/m camera contains precision mirror, lens, small 24V motor etc. £10.00. 24V ni-cad battery contains 20 x 0.4 A/H cells (new) £7.00. CCTV cameras sold for spares £20. 24V ni-cad battery contains 20 D type cells, used condition £10.00. Stereo type BU802 battery contains 9 x 225 MA/H £3.00. Pye PF70 batteries £3.00. 10 type date rate meter £2.50. A14 ex-govt manpacks 2 to 8 MHz £80 each. Ex-Govt field telephone type J £8 each. Large packs miscellaneous electronic equipment available to callers £25. All goods are surplus ex-ministry.

A. C. ELECTRONICS Tel. 0532 496048 after 6.30 pm.

## AERIALS

### AERIAL BOOSTERS

Next to the set fitting

B45H/G-UHF TV, gain about 20db, Tunable over the complete UHF TV band. PRICE £8.70.

B11-VHF/FM RADIO, gain about 14db, when on the off position connects the aerial direct to the radio. £7.70.

All Boosters we make work off a PP3/006p/6F22 type battery or 8v to 18v DC. P&P 30p PER ORDER.

ELECTRONIC MAILORDER LTD, 62 Bridge St, Ramsbottom, Lancs BL0 9AG. Tel (070682) 3036

Access/Visa Cards Welcome SAE Leaflets

## SOFTWARE

CONVERT ZX81 to EPROM programmer with ZP4000 unit. S.A.E. details, ENTERPRISE TECHNOLOGY LTD, P.O. Box 140, Wigan, WN3 6LF, Lancs.

## BOOKS AND PUBLICATIONS

COMPLETE FULL-SIZE SETS any published service sheets, £2 + LSAE except CTVs/Music Centres from £3 + LSAE. Manuals from 1930 to latest. Quotations, free 50p magazine, price lists unique technical publications for LSAE. Repair data/circs almost any named TV/VCR £8.50 by return. TIS PE, 76 Church Street, Larkhall, Lanarks, ML9 1HE. Phone (0698-883334).

## ORDER FORM PLEASE WRITE IN BLOCK CAPITALS

Please insert the advertisement below in the next available issue of Practical Electronics for.....

insertions. I enclose Cheque/P.O. for £.....

(Cheques and Postal Orders should be crossed Lloyds Bank Ltd. and made payable to Practical Electronics)


NAME.....

ADDRESS.....

Company registered in England. Registered No. 53626. Registered Office: King's Reach Tower, Stamford Street, London SE1 9LS.

Send to: Classified Department,

### PRACTICAL ELECTRONICS

Classified Advertisement Dept. Room 2612,

King's Reach Tower, Stamford Street,

London SE1 9LS. Telephone 01-261 5846

Rate:

34p per word, minimum 12 words. Box No. 60p extra.

9/83

## SERVICE SHEETS

**BELL'S TELEVISION SERVICES** for service sheets on radio, TV, etc. £1.25 plus SAE. Service Manuals on Colour TV and Video Recorders, prices on request. SAE with enquiries to B.T.S., 190 Kings Road, Harrogate, N. Yorkshire. Tel. (0423) 55885.

## FOR SALE

**MICROTRAINER**, New Power Supply, Extra 2532, PPI. drivers etc. desk-top vero case, £70.00. I. Standish, 123 Draperfield, Eaves Green, Chorley, Lancs. Tel. 63741.

**STOCK OF VARIOUS COMPANIES** in liquidation for sale/tender. Large quantity various electronic components, resistors, capacitors, etc. Quantity various electronic equipment, oscilloscope, DBX unit, VHF/receivers, etc. Phone Ongar 362987.

## COURSES

**CONQUER THE CHIP...** Master modern electronics the PRACTICAL way by SEEING and DOING in your own home. Write for your free colour brochure now to British National Radio & Electronics School, Dept. C2, Reading, Berks. RG1 1BR.

## EDUCATIONAL

**CAREERS IN MARINE ELECTRONICS.** Courses commencing September and January. Further details, The Nautical College, Fleetwood FY7 8JZ. Tel: 03917 79123.

# FULL-TIME TRAINING COURSES

## 15 MONTHS TEC CERTIFICATE in TELEVISION & VIDEO SERVICING

## 15 MONTHS TEC CERTIFICATE in COMPUTING TECHNOLOGY

## 6 MONTHS TEC HIGHER CERT in COMPUTING TECHNOLOGY & ROBOTICS

- PRINCIPLES OF ELECTRONICS
- TELEVISION (MONO/COLOUR)
- VIDEO CASSETTE RECORDERS & CCTV
- COMPUTERS & MICROPROCESSORS
- INDUSTRIAL ROBOTICS

Short courses (from 6 weeks) with previous electronics knowledge.

Next course starts Sept. 19th.

Prospectus from:

## LONDON ELECTRONICS COLLEGE

Dept: AA, 20 Penywern Road, London SW5 9SU. Tel: 01-373 8721.

## BUSINESS OPPORTUNITIES

**REDUNDANT? ELECTRONICS HOBBIST? —** An opportunity for you to participate in a new venture selling components, test equipment, kits, etc., to the hobbyist and industry. The operation is already well established and needs somebody to manage it — with particular emphasis on the retail side. If you have spare capital, there is also a chance to purchase some equity in the company.

Telephone: Stuart Taylor — 03272 5521

## MISCELLANEOUS

**ELECTRONIC ORGAN KEYBOARDS** and other parts being cleared out as special offer. — Elvins Electronic Musical Instruments, 40A Dalston Lane, London E8. Tel: 01-986 8455.

**BURGLAR ALARM EQUIPMENT.** Ring Bradford (0274) 308920 for our Catalogue or call at our large showrooms opposite Odsal Stadium.

**SUPERB INSTRUMENT CASES** by Bazelli, manufactured from PVC faced steel. Vast range. Competitive prices start at a low £1.50. Punching facilities at very competitive prices. — Bazelli (Dept 23), St Wilfreds, Foundry Lane, Halton, Lancaster LA2 6LT.

**IONIZER.** Feel alert, invigorated and healthier with the amazing ZEPHION negative ion generator. Kit: £21.50p. Built: £29.80p or S.a.c. brings leaflets. Dataplus Developments, 81 Cholmeley Road, Reading, Berks, RG1 3LY. Tel: 073 67027.

**CLEARING LABORATORY:** scopes, generators, P.S.U.'s, bridges, analysers, meters, recorders, etc. 0403-76236.

## CABINET FITTINGS

Fretcloths, Coverings, Handles, Castors, Flight Case Locks & Parts, Jacks, XLRs, Bulgins, Reverb Trays, P & N mic Stands, ASS Glassfibre Horns, CELESTION POWER Speakers.

**ADAM HALL SUPPLIES LTD.** Send 30p cheque/ P.O. for illustrated catalogue: Adam Hall (PE Supplies), Unit G, Carlton Court, Gralnger Road, Southend-on-Sea.

THE SCIENTIFIC WIRE COMPANY				
811 Forest Road, London E17, Telephone 01-531 1568				
ENAMELLED COPPER WIRE				
SWG	1 lb	8 oz	4 oz	2 oz
8 to 34	3.63	2.09	1.10	0.88
35 to 39	3.82	2.31	1.27	0.93
40 to 43	6.00	3.20	2.25	1.61
44 to 47	8.67	5.80	3.49	2.75
48	15.96	9.58	6.38	3.69
SILVER PLATED COPPER WIRE				
14 to 30	9.09	5.20	2.93	1.97
TINNED COPPER WIRE				
14 to 30	3.97	2.41	1.39	0.94
Fluxcore Solder	5.90	3.25	1.82	0.94

Prices include P&P VAT. Orders under £2 add 20p. SAE for list of copper and resistance wire. Dealer enquiries welcome.

MAKE YOUR OWN PRINTED CIRCUITS			
Etch Resist Transfers — Starter pack (5 sheets, lines, pads, I.C. pads) £2.50. Large range of single sheets in stock at 50p per sheet.			
Master Positive Transparencies from P.C. layouts in magazines by simple photographic process. 2 sheets negative paper, 2 sheets positive film (A4) £2.25.			
Photo-resist spray (200 ml) £3.90 (p+p 65p).			
Drafting Film (A4) 25p. Precision Grids (A4) 65p.			
20p stamp for lists and information. P&P 50p per order plus extra where indicated.			
P.K.G. ELECTRONICS			
OAK LODGE, TANSLEY, DERBYSHIRE.			

## BAKER LOUDSPEAKERS

Model	Inches	Ohms	Watts	Type	Price	Post
Major	12	4-8-16	30	Hi-Fi	£16	£2
Superb	12	8-16	30	Hi-Fi	£26	£2
Auditorium	12	8-16	45	Hi-Fi	£24	£2
Auditorium	15	8-16	60	Hi-Fi	£37	£2
Group 45	12	4-8-16	45	PA	£16	£2
Group 75	12	4-8-16	75	PA	£20	£2
Group 100	12	8-16	100	Guitar	£26	£2
Disco 100	12	8-16	100	Disco	£26	£2
Group 100	15	8-16	100	Guitar	£35	£2
Disco 100	15	8-16	100	Disco	£35	£2

**LOUDSPEAKER BARGAINS**  
4 ohm, 5in. 7 x 4in. £2.50; 6in. 8 x 5in. £3.50; 8in. £4.50; 10in. £5. 8 ohm, 2 1/2in. 3in. £2; 5in. 6 x 4, 7 x 4in. £2.50; 6in. 8 x 5in. £3; 8in. £4.50; 10in. £5; 12in. £6; 8in. 50W £10; 8in. 60W £12.50. 15 ohm, 3in. 5 x 3in. 6 x 4in. £2.50. 35 ohm 5 in. £2.50. 25 ohm, 3in. £2; 5 x 3in, 7 x 4in. £2.50. 120 ohm, 3 1/2in dia. £1.

**BAKER AMPLIFIERS**  
Bargain prices, post £2.00  
80w, 4 inputs, mains and 12V DC £89.00  
150w, 4 inputs, mains, all purpose £99.00  
150w, 4 inputs, mains PA amplifier £129.00  
150+150w stereo slave amplifier £125.00

**DISCO MIXER.** 240V, 4 stereo channels, 2 magnetic, 2 ceramic/tape, 1 mono mic channel, twin v.u. meters, headphone monitor outlet, slider controls, panel or desk mounting, graded aluminium fascia £46. Post £1. Tape output facility.  
**DELUXE STEREO DISCO MIXER/EQUALISER** as above plus L.E.D. V.U. displays 5 band graphic equaliser, left/right fader, switchable inputs for phone/line, mike/line. Headphone Monitor, Mike Talkover Switch £108 PP £2

Make	Model	Drive	Cartridge	Price
BSR	P170	Rim	Ceramic	£20
GARRARD	6200	Rim	Ceramic	£22
GARRARD	Delux	Belt	Magnetic	£40

BSR	P232	12 volt	Magnetic	£24
-----	------	---------	----------	-----

BSR	Budget	Rim	Ceramic	£16
BSR	Delux	Rim	Ceramic	£18
BSR	Delux	Rim	Magnetic	£26

**HEAVY METAL PLINTHS** Post £1.00  
Suits almost Garrard decks  
Silver grey or black finish. Size 16 x 13 1/2in. £4

**DECCA TEAK VENEERED PLINTH.** Post £1 50  
Superior finish with space and panel for small amplifier. Board is cut for BSR or Garrard £5

18in. x 14 1/2in. x 4in. Black/Chrome fascia trim.  
Tinted plastic cover £5

TINTED PLASTIC COVERS	for Decks, Music Centres, etc.	Post £1
17 1/2 x 13 1/2 x 3 1/2in.	£5	18 1/2 x 12 1/2 x 3 1/2in. £5
17 1/2 x 9 1/2 x 3 1/2in.	£3	14 1/2 x 12 1/2 x 2 1/2in. £5
16 1/2 x 15 x 4 1/2in.	£5	16 1/2 x 13 x 4 1/2in. £5
17 x 12 1/2 x 3 1/2in.	£5	14 1/2 x 13 1/2 x 2 1/2in. £5
22 1/2 x 13 1/2 x 4 1/2in.	£5	17 1/2 x 13 1/2 x 4 1/2in. £5
21 1/2 x 14 1/2 x 2 1/2in.	£5	21 x 13 1/2 x 4 1/2in. £5
23 1/2 x 14 x 3 1/2in.	£5	30 1/2 x 13 1/2 x 3 1/2in. £5

MAINS TRANSFORMERS		Post
250-0-250V 80mA, 6.3V 3.5A, 6.3V 1A		£6.00 £2
350-0-350V 250mA, 6.3V 6A CT		£12.00 £2
220V 25ma 6V 1amp £2.50	220V 45ma 6V 2 Amp	£4.00 £1
250V 60mA, 6V 2A		£4.75 £1
AUTO 115V to 240V 150W/9. 250W £10. 500W £12.00		£2

GENERAL PURPOSE LOW VOLTAGE MAINS TRANSFORMERS	Tapped outputs available	Price Post	
2 amp, 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V		£6.00 £2	
1 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£6.00 £2	
2 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£10.50 £2	
3 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£12.50 £2	
5 amp, 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60		£16.00 £2	
5-8-10-16V. 1/2 amp	£2.50 £1	15-0-15V, 1 amp	£4.00 £1
6V. 1/2 amp	£2.00 £1	15-0-15V, 2 amps	£4.50 £1
6-0-6V, 1 1/2 amp	£3.50 £1	20V 1 amp	£4.00 £1
9V, 250ma	£1.50 £1	20-0-20V, 1 amp	£4.50 £1
9V, 3 amps	£4.50 £1	20-40-60V, 1 amp	£4.50 £2
9-0-9V, 50 ma.	£1.50 £1	25-0-25V, 2 amps	£5.50 £1
9-0-9V, 1 amp	£3.50 £1	28V 1 amp Twice	£6.00 £2
10-0-10V, 2 amps	£4.00 £1	30V, 1 1/2 amp	£4.50 £1
10-30-40V, 2 amps	£4.50 £1	30V 5 amp and	
12V, 300 ma	£2.00 £1	17-0-17 2a	£5.50 £2
12V, 750 ma	£2.50 £1	35V, 2 amps	£4.50 £1
12V, 3 amps	£4.50 £1	TOROIDAL 30-0-30V, 4a	
12-0-12V, 2 amps	£4.50 £1	and 20-0-20V, 1a	£10.00 £2
<b>CHARGER TRANS</b>	Post	<b>RECTIFIERS</b>	Post
6-12 volt 3a	£4.50+£2	6-12 volt 2a	£1.10+80p
6-12 volt 4a	£6.50+£2	6-12 volt 4a	£2.00+80p

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS** £3.95. Post 65p  
All parts and instructions with Zener diode printed circuit, mains transformer 240V a.c. Output 6 or 7i or 9 or 12V d.c. up to 100mA or less. Please state voltage required.  
**PP BATTERY ELIMINATOR BRITISH** £4.50  
Mains stabilized power pack 9 volt 400mA D.C. with overload cut out. Size 5 x 3 1/2 x 2 1/2in. Post £1.

**ALUMINIUM CHASSIS.** 6x4—£1.75; 8x6—£2.20; 10x7—£2.75; 12x8—£3.20; 14x9—£3.60; 16x11—£2.50; 16x10—£3.80; 12x3—£2.20; 14x3—£2.50.

**ALUMINIUM PANELS.** 6x4—55p; 8x6—90p; 14x3—90p; 10x7—£1.15; 12x8—£1.30; 12x5—90p; 16x11—£1.30; 14x9—£1.75; 12x12—£1.80; 8x10—£2.10. ANGLE ALU 6x1/2x1/2in. 50p.

**ALUMINIUM BOXES.** 4x4x1 1/2 £1.20; 4x2 1/2 £1.20; 3x2 1/2 £1.20; 6x4x2 £1.90; 7x5x3 £2.90; 8x6x3 £3; 10x7x2 £3.60; 12x5x3 £3.60; 12x8x3 £4.30.

**BLACK PLASTIC BOX with Ali Fascia 6 1/2" x 3 1/2" £1.50**

HIGH VOLTAGE ELECTROLYTICS				
2/350V 35p	8 + 8/450V 75p	16 + 16-16/275V 50p		
4/350V 35p	8 + 16/450V 75p	50 + 50/300V 50p		
8/450V 45p	16 + 16/450V 85p	100 + 100/275V 50p		
32/350V 50p	32 + 32/450V £1.20	150 + 200/275V 50p		
32/500V 95p	32 - 32/350V 75p	32 + 32 + 16/350V 75p		
50/450V 95p	32 + 32/500V £2.00	32 + 32 + 32/325V 50p		

## RADIO COMPONENT SPECIALISTS

Dept 3, 337, WHITEHORSE ROAD, CROYDON SURREY, U.K. Tel: 01-684 1665

Post 50p Minimum. Orders Welcome. Closed Wed. Same day despatch. Access-Barley-Via, 1.3ts 25p.

## OPERATIONAL AMPLIFIER EXPERIMENTAL MANUAL

by G. B. Clayton

Price: £3.50

### DIGITAL ELECTRONIC CIRCUITS & SYSTEMS

by N. M. Morris

Price: £5.50

### ELECTRONIC MUSIC CIRCUITS

by B. Klein

Price: £15.00

### THE CATHODE-RAY OSCILLOSCOPE & ITS USE

by G. N. Patchett

Price: £5.50

### VIDEOTAPE RECORDING

by J. F. Robinson

Price: £14.50

### DOMESTIC VIDEOCASSETTE RECORDERS

#### A SERVICING GUIDE

by S. Beeching

Price: £15.00

### MICRO COOKBOOK VOL I: FUNDAMENTALS

by D. Lancaster

Price: £13.50

### AN INTRODUCTION TO MICROCOMPUTERS

#### VOL I: BASIC CONCEPTS

by A. Osborne

Price: £10.50

### WORLD RADIO T.V. HANDBOOK

by J. Frost

Price: £12.00

### 1983 THE RADIO AMATEUR'S H/B

by A.R.R.L.

Price: £10.00

★ ALL PRICES INCLUDE POSTAGE ★

## THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books

19-21 PRAED STREET  
LONDON W2 1NP

Phone 01-402 9176 Closed Saturday 1 p.m.  
Please allow 14 days for reply or delivery.

## INDEX TO ADVERTISERS

A.C. Electronics	72
A.D. Electronics	6
Ambit	12
Audio Electronics	10
Bi-Pak	7
Blackstar	30
British National Radio & Electronics School	8, 13
Clef Products	6
Colne Robotics	4
Cricklewood	11
Crofton	8
C.R. Supply Co.	72
Electronic Mail Order Co.	72
Electrovalue	12
Adam Hall	73
Gordon Hallett	72
ICS Intertext	4
ILP Electronics	20 & 21, 30
Lascar	68
London Electronic College	73
Magenta	10
Maplin	Cover IV
Marco Trading	10
Marlborough Electronics	72
Midwich	51
Modern Book Co.	74
Parndon	8
Phonsonics	8
Pimac Systems	10
PKG Electronics	73
Powertan	29
Racom	6
Radio Component Specialists	73
Scientific Wire Co.	73
Sparkrite	5
Swanley	4
Tandy	14
Stuart Taylor	73
Technomatic	74 & Cover III
T.K. Electronics	9
Twyford	6
Watford	2 & 3

Published approximately on the 7th of each month by IPC Magazines Ltd., Westover House, West Quay Road, Poole, Dorset BH15 1JG. Printed in England by Chapel River Press, Andover, Hants. Sole Agents for Australia and New Zealand - Gordon & Goreh (A/sia) Ltd.; South Africa - Central News Agency Ltd. Subscriptions INLAND and OVERSEAS £13.00 payable to IPC Services, Oakfield House, Perrymount Road, Haywards Heath, Sussex. Practical Electronics is sold subject to the following conditions, namely, that it shall not, without the written consent of the Publishers first given, be lent, resold, hired out or otherwise disposed of by way of Trade at more than the recommended selling price shown on the cover, and that it shall not be lent, resold or hired out or otherwise disposed of in a mutilated condition or in any unauthorised cover by way of Trade, or affixed to or as part of any publication or advertising, literary or pictorial matter whatsoever.

# TECHNOMATIC LTD

01-452 1500 01-450 6597

## CONNECTOR SYSTEMS

I.D. CONNECTORS (Speedblock Type)		D-CONNECTORS 9 way 15 way 25 way 37 way				DIL HEADER PLUGS		RIBBON CABLE (Grey)		
No. of ways	Header Recept. Plug	Edge Conn.	Solder	80p	105p	160p	250p	RS 232 Connectors Available from Stock	19 way 40p	
10	90p	85p	Angled	150p	210p	250p	365p	14 way 60p	16 way 60p	
20	145p	125p	FEMALE		Solder	105p	160p	200p	26 way 85p	
26	175p	150p	240p	335p	Angled	165p	215p	230p	26 way 120p	
34	200p	160p	320p	440p	Hood	90p	85p	90p	34 way 160p	
40	220p	190p	340p	100p	36 way Centronix Type Conn. £5.50		24 pin 100p	200p	40 way 180p	
50	235p	200p	390p	25 way 1EEE Type Conn. £5.50	40 pin 200p		225p	64 way 280p	50 way 200p	
RS 232 JUMPERS (25 way D)			EURO CONNECTORS (Indirect Edge Conn.)			EDGE CONNECTORS			0.1" 0.156"	
24" Single end Male	£5.00	24" Single end Female	£5.25	DIN STD	Plug	Skt	2x18 way	—	140p	
24" Female-Female	£10.00	41617 21 way	160p	41617 21 way	160p	165p	2x22 way	190p	240p	
24" Male-Male	£9.50	41617 31 way	170p	41617 31 way	170p	170p	2x23 way	175p	—	
24" Female-Male	£9.50	41612 2x32 way	220p	41612 2x32 way	275p	275p	2x25 way	225p	220p	
DIL SWITCHES			4 way 70p			8 way 90p			10 way 140p	
			6 way 85p			Angled 2x32 way			275p 320p	
						41612 3x32 way			260p 300p	
						Angled 3x32 way			375p 350p	
						2x32 way IDC a+c			525p	
						(for 2x32 way Specify a+b or a+c)			S100 Conn — 600p	

### ★ SPECIAL OFFER ★

2114L-450	80p	25-99	75p	1-24	25-99
4164-2	450p	430p	6116-150	375p	350p
2716(+5V)	250p	225p	6522	310p	300p
2532	350p	335p			

## OFFICIAL BBC DEALER

BBC Model B £399 including VAT. (Carr. £8)

Model A to B upgrade kit £49.50. Installation charge £15  
Individual upgrades and all mating connectors available.

### BBC FLOPPY DISC DRIVES

Disc Interface Kit £95 Installation £20  
Single Drive 5 1/4" 100K £230 Dual Drive 5 1/4" 800K £699

### BBC COMPATIBLE 5 1/4" DISC DRIVES

These drives are available in BBC matching colour case.  
Single: 100K £150 200K £215 \* 400K £265 \*  
Single with PSU: 100K £185 200K £260 \* 400K £330  
Dual with PSU: 200K £355 400K £475 \* 800K £595

\* These drives are provided with a switch between 40 and 80 tracks.

Cable for Single Drive £8. Dual Drive £12.

(Carr. Single Drive £6, Dual Drive £8)

Disc Manual & Formatting Diskette £17.50  
Diskettes: 40 track SS £15, 80 track SS £24, 80 track DS £32.

(Price for 10 carr. £2)

VIEW 16K WORD PROCESSOR ROM £52

TELETEXT RECEIVER £195.65 + £2 p&p

TORCH Z80 DISC PACK £780.00 + £2 p&p

WORDWISE 8K ROM £39 + £2 p&p

BUSINESS, EDUCATION AND FUN SOFTWARE IN STOCK

Please phone to confirm delivery details.

BOOKS (No VAT £1 p&p)

BASIC PROGRAMMING ON BBC £5.95

LET YOUR BBC TEACH YOU TO PROGRAM £6.95

BBC MICRO REVEALED £7.95

BBC MICRO AN EXPERT GUIDE £6.95

BBC COMPUTERS PLAY £6.95

ASSY LONG PROGRAM ON BBC £8.95



## PRINTERS

### NEC PC 8023 BE

80 col 100 cps dot matrix printer. Bi-directional. Logic seeking, 2K buffer.  
Forward and Reverse line feed. Hi Res & Block Graphics, Proportional Spacing,  
International and Greek character sets, Auto underline, Friction/tractor selectable.  
£345 + £8 carr.

### EPSON RX80 and EPSON FX80

RX80 100CPS 80 col Tractor Feed. FX80 160CPS 80 col F & T Feed. Logic seeking,  
Bi-directional, Bit Image Printing, 9 x 9 Matrix, Auto Underline. RX80 £298, FX80 £389  
MX100 F/T3 £425

Carr. £8/Unit

### SEIKOSHA GP100A & 250A

80 col. 30 cps dot matrix printer. High Res Graphics - Std & double with  
characters. £180 + £6 carr.  
GP250A £235 + £8 carr.



# MAKE ALL THE RIGHT CONNECTIONS

with a MAPLIN MODEM KIT

Exchange programs with friends, leave or read messages from the various Billboard services, talk to computer bureaux, or place orders and check stock levels on Maplin's Cashtel service. A Maplin Modem will bring a whole new world to your computer and vastly increase its potential.

Now you can exchange data with any other computer using a 300 baud European standard (CCITT) modem and because the Maplin Modem uses this standard, you could talk to any one of tens of thousands of existing users.

Some computers need an interface and we have kits for the ZX81, VIC20/Commodore 64, Dragon and shortly Spectrum and Atari, whilst the BBC needs only a short program which is listed in Projects Book 8.

A Maplin Modem will add a new dimension to your hobby.

Order As LW99H (Modem Kit) excluding case. Price £39.95.  
YK62S (Modem Case). Price £9.95.

Full construction details in Projects Book 5.



## NEW MAPLIN STORE OPENS IN MANCHESTER

Our new Manchester store offering the full range of Maplin's electronic components, computers and software will be opening 16th August, 1983. Part of the new store will be a self-service area where you can browse around and choose the parts you want. Counter service will be available as well. Upstairs you will find our computer demonstration area with displays of hundreds and hundreds of different software packages for Atari, BBC, Commodore 64, Dragon, Sord M5, Spectrum and VIC20.

You will find us at 8, Oxford Road opposite the BBC, between Piccadilly and the University complex. We're just a few steps from



Manchester's Oxford Road station and about five minutes walk from the city centre. There is excellent parking on meters in the adjacent sideroads and we're about five minutes drive straight in from junction 10 on the M63 at the start of the M56.

Call in and see us soon!

## Maplin's Fantastic Projects



Full details in our project books. Price 70p each.

In Book 1 (XA01B) 120W rms MOSFET Combo-Amplifier ● Universal Timer with 18 program times and 4 outputs ● Temperature Gauge ● Six Vero Projects.

In Book 2 (XA02C) Home Security System ● Train Controller for 14 trains on one circuit ● Stopwatch with multiple modes ● Miles-per-Gallon Meter.

In Book 3 (XA03D) ZX81 Keyboard with electronics ● Stereo 25W MOSFET Amplifier ● Doppler Radar Intruder Detector ● Remote Control for Train Controller.

In Book 4 (XA04E) Telephone Exchange for 16 extensions ● Frequency Counter 10Hz to 600 MHz ● Ultrasonic Intruder Detector ● I/O Port for ZX81 ● Car Burglar Alarm ●

Remote Control for 25W Stereo Amp.

In Book 5 (XA05F) Modem to European standard ● 100W 240V AC Inverter ● Sounds Generator for ZX81 ● Central Heating Controller ● Panic Button for Home Security System ● Model Train Projects ● Timer for External Sounder.

In Book 6 (XA06G) Speech Synthesiser for ZX81 & VIC20 ● Module to Bridge two of our MOSFET amps to make a 350W Amp ● ZX81 Sound on your TV ● Scratch Filter ● Damp Meter ● Four Simple Projects.

In Book 7 (XA07H) Modem (RS232) Interface for ZX81/VIC20 ● Digital Enlarger Timer/Controller ● DXers Audio Processor ● Sweep Oscillator ● CMOS Crystal Calibrator.

In Book 8\* (XA08J) Modem (RS232) Interface for Dragon ● VIC Extendiboard ● Synchime ● Electronic Lock ● Minilab Power Supply ● Logic Probe ● Doorbell for the Deaf.

\* Projects for Book 8 were in an advanced state at the time of writing, but contents may change prior to publication (due 13th August 1983).

## LEARN ROBOTICS

— with Hero 1: the new robot who sees, hears, speaks and detects movement!

This remarkable microprocessor-controlled robot is the perfect robotics training system for industry, home and schools. Hero 1 can see, hear, speak, detect moving and stationary objects and determine their distance, pick up small objects, move in any direction and can learn from your instructions.

Hero 1 is a superbly documented Heathkit kit.

Order As HK20W (Robot Kit) Price £1,599.95.



## Great Projects From E&MM

Our new book "Best of E&MM Projects Vol. 1" brings together 21 fascinating and novel projects from E&MM's first year.

Projects include Harmony Generator, Guitar Tuner, Hexadrum, Syntom, Auto Swell, Partylite, Car Aerial Booster, MOS-FET Amp and other musical, hi-fi and car projects.

Order As XH61R. Price £1.

## ★ 1983 CATALOGUE ★

Over 390 pages packed with data and pictures and all completely revised and including over 1000 new items. On sale in all branches

of W.H. Smith. Price £1.25. Or send £1.50 (including p&p) to our mail-order address.



**MAPLIN**  
ELECTRONIC SUPPLIES LTD

Mail Order: P.O. Box 3, Rayleigh, Essex SS6 8LR. Tel: Southend-on-Sea (0702) 552911.  
Shops at: 159-161 King Street, Hammersmith, London W6. Tel: 01-748 0926.

284 London Road, Westcliff-on-Sea, Essex. Tel: (0702) 554000.

Lynton Square, Perry Barr, Birmingham. Tel: 021-356 7292.

8 Oxford Road, Manchester. Tel: 061-236 0281. (Opens 16th Aug. 1983)

All shops closed Mondays.

All prices include VAT & carriage. Please add 50p handling charge if total order value is under £5.