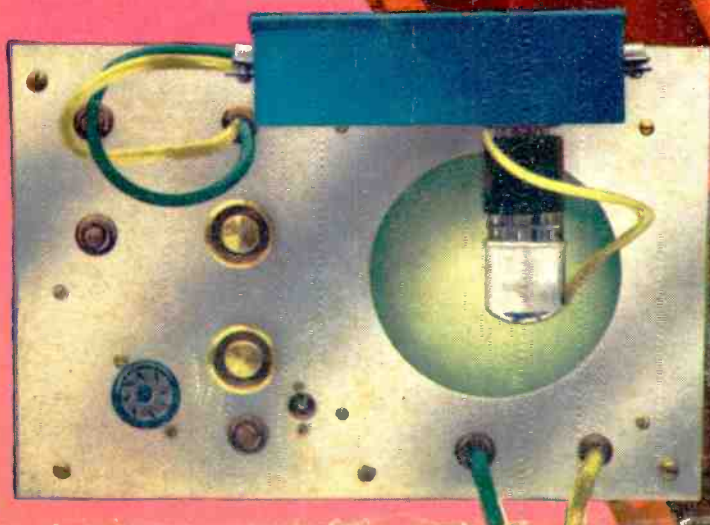


# Practical TELEVISION

JANUARY 1964

2/-

Building a Flying-Spot  
Transparency Scanner



# for everything in..

## COMPLETELY REBUILT, RE-SCREENED, RE-ALUMINISED TELEVISION TUBES ' SUFFOLK & MIDLAND LEAD THE WAY!

Regular buyers of Suffolk and Midland Tubes have learnt to rely on their outstanding quality.  
Every tube guaranteed 12 months with proved PERFORMANCE & RELIABILITY

**SUFFOLK TUBES LTD**  
1/3 UPPER RICHMOND ROAD  
PUTNEY, LONDON, S.W.15  
Tel: Vandyke 4304 5267

**MIDLAND TUBES LTD**  
477/483 OLDHAM ROAD  
MANCHESTER 10  
Tel: Collyhurst 4412

THE LARGEST INDEPENDENT REBUILDERS IN THE U.K.

### VALVES SAME DAY SERVICE NEW! TESTED! GUARANTEED!

**SETS** 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94 ... Set of 4 for 15/-  
DAF96, DF96, DK96, DL96 ... 4 for 23/6

1A7GT 9/-	6V6GT 8/6	DAF91 3/9	ECL80 6/3	PCC89 8/-	U52 4/3
1D5 6/6	6X1 3/9	DAF96 6/-	ECL82 7/6	PCF60 5/9	U78 3/9
1H5GT 8/3	6X5GT 6/9	DCC90 6/9	ECL85 9/-	PCF82 6/9	U191 11/-
1N5GT 8/-	7B7 8/-	DF33 8/-	EP37A 5/6	PCF84 11/9	U281 9/6
1R5 4/9	7C5 7/9	DF91 2/8	EP39 3/9	PCF86 8/-	U282 14/6
1S5 3/9	7C6 7/6	DF96 8/-	EP41 6/6	PCF806 14/-	U291 8/-
1T4 2/6	7H7 5/9	DH76 3/8	EP42 5/-	PCL82 7/3	U301 12/8
3A5 6/9	7S7 12/6	DH77 4/9	EP80 4/3	PCL83 9/-	U801 17/9
3Q4 5/8	7Y4 5/-	DK32 9/-	EP85 5/-	PCL84 6/6	UABC80 5/8
3S4 4/9	10C1 9/6	DK40 15/6	EP86 6/3	PCL85 8/6	UAF42 8/-
3V4 5/6	10C2 13/-	DK91 4/9	EP89 4/-	PEN4DD	UBC41 6/11
5C4G 4/8	10F9 10/-	DK92 6/6	EP91 3/3	PENAA 19/8	UBC81 7/3
5Y3GT 5/-	12AT6 4/9	DK96 6/6	EP92 2/6	PENAA4 7/3	UBF80 7/3
6Z4G 8/9	12AT7 3/9	DL33 7/3	EP184 8/9	PEN36C 8/-	UBF89 7/9
6A8G 6/9	12AX7 4/9	DL35 6/9	EL33 7/6	PEN383 10/6	UBL21 10/-
6AL5 2/-	12AX7 4/9	DL92 4/9	EL41 8/6	PL36 8/9	UC92 6/6
6AQ5 6/-	12K8GT 4/3	DL94 5/8	EL42 5/8	PL38 10/6	UCC84 9/-
6AT6 4/9	12K8GT 8/9	DL96 6/6	EL84 5/6	PL81 7/6	UC85 6/9
6BA6 6/-	12C7GT 4/3	EABCR80 5/8	EM34 7/3	PL82 5/6	UCF80 10/3
6BE6 5/3	12Z3 7/6	EAF42 8/-	EM80 6/9	PL83 5/6	UCH42 7/6
6BG6G 12/6	19BG6G 13/6	EB91 2/-	EM81 7/9	PL84 5/9	UCH81 7/6
6BH6 5/-	20P2 11/9	EBE33 5/-	EM84 8/3	PX4 9/-	UCL82 8/3
6BJ6 5/6	20P4 14/9	EBE41 7/3	EM87 8/9	PX25 7/9	UCL83 9/-
6CD6G 26/6	20P5 14/9	EBE81 6/9	EY51 6/-	PY32 9/-	UF41 7/3
6F1 5/6	25L8GT 5/9	EBF90 7/3	EY86 8/-	PY33 10/-	UF42 5/-
6F13 4/9	25U4GT 10/6	EBF83 7/9	EZ40 5/6	PY80 5/3	UF89 6/3
6F14 9/-	30FL1 9/6	EBF89 6/9	EZ41 7/6	PY81 5/9	UL41 7/-
6F23 9/6	30L15 9/9	EBL21 8/9	EZ80 4/8	PY82 5/9	UL44 10/6
6K7G 1/6	30PL1 9/-	EBL31 19/6	EZ81 4/8	PY83 6/9	UL46 8/9
6K7GT 4/-	35A5 14/6	ECC40 7/6	KT32 5/-	PY88 8/-	UL84 8/3
6K8G 4/6	35A5 14/6	ECC81 3/9	KT36 14/-	TH21C 10/6	UU7 7/6
6K8G1' 7/9	35L6GT 7/9	ECC82 4/9	KT61 7/6	TH233 15/-	UY21 8/9
6L6G 5/9	35Z4GT 4/11	ECC83 7/-	KT63 3/9	TY86F 11/3	UY41 4/9
6LD20 5/3	AZ31 6/11	ECC84 6/3	MU14 5/-	U22 6/-	UY85 4/3
6P25 7/9	B36 4/9	ECC85 7/3	MX40 9/-	U24 15/-	VP48 9/6
6P28 9/6	CCH35 12/9	ECC86 6/3	N418 5/8	U25 8/6	VP41 5/-
6Q7G 4/9	CL1 9/6	ECC87 6/6	PC95 9/-	U26 10/6	VP1321 15/-
6Q7GT 7/9	CY3 8/6	ECC88 6/6	PC97 8/-	U37 3/9	W76 3/9
6SN7GT 4/-	CY31 5/9	ECH42 8/3	PCC84 8/-	U47 8/6	W77 2/6
6V6G 3/9	DAC32 8/3	ECH81 8/6	PCC85 7/6	U50 4/8	X63 6/6

### FIRST-CLASS RADIO AND T/V COURSES... GET A CERTIFICATE!

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure a recognised qualification or extend your knowledge of Radio and T.V. Let us show you how.

**FREE GUIDE**  
The New Free Guide contains 120 pages of information of the greatest importance to both the amateur and the man employed in the radio industry. Chambers College provides first rate postal courses for Radio Amateurs' Exam., R.T.E.B. Servicing Cert., C. & C. Telecoms., Grad. Brit. I.R.E. Guide also gives details of range of diploma courses in Radio T.V. Servicing, Electronics and other branches of engineering, together with particulars of our remarkable Guarantee of

**SUCCESS OR NO FEE**  
Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.  
**FOUNDED 1885—OVER 150,000 SUCCESSES**

**CHAMBERS COLLEGE**  
(Incorp. National Inst. of Engineering)  
(Dept. 462), 148 HOLBORN  
LONDON, E.C.1

**READERS RADIO**  
24 COLBERG PLACE, STAMFORD HILL  
LONDON N.16 STA. 4587

Post 6d. per valve extra.  
Part 1 Insured Against Damage in Transit 6d. extra.  
Any C.O.D. Parcel 4/3 extra

Get **10%** off your next order at [worldofrarebooks.com](http://worldofrarebooks.com)



# World *of rare* Books


Just use the code: **WORB10** in your cart


Offer redeemable at <http://www.worldofrarebooks.com> only.

**World** *of rare* **Books & ebay**

**Any issues? Talk to us first**

 01903 708 111

 [support@worldofrarebooks.com](mailto:support@worldofrarebooks.com)

 [worldofrarebooks.com](http://worldofrarebooks.com)

You can get an instant response over the phone and we aim to answer emails within 24 hours.

January, 1964

PRACTICA

TITLE: Practical Television 1964  
- January, March, April,  
May, July, September, Oc  
tober, December (set o...  
ASIN:  
SIZE: Normal

145

**Just  
Out!**

# COMP LAW

**LY**

*Your Rights fully explained*

## ● IN BUSINESS


PATENTS · COPYRIGHT · TRADE UNIONS  
EMPLOYMENT · SALE OF GOODS  
PARTNERSHIP · STARTING A BUSINESS  
INSURANCE · INVESTMENT · TAX  
CONTRACTS · BANKRUPTCY

## ● IN PERSONAL AFFAIRS

BUYING AND SELLING · LEASES  
ACCIDENTS · MARRIAGE · SEPARATION,  
DIVORCE · SLANDER · HP  
AND CREDIT SALE · NEIGHBOURS  
WILLS · FREE LEGAL AID

EDITED  
BY  
**Dudley  
Perkins**

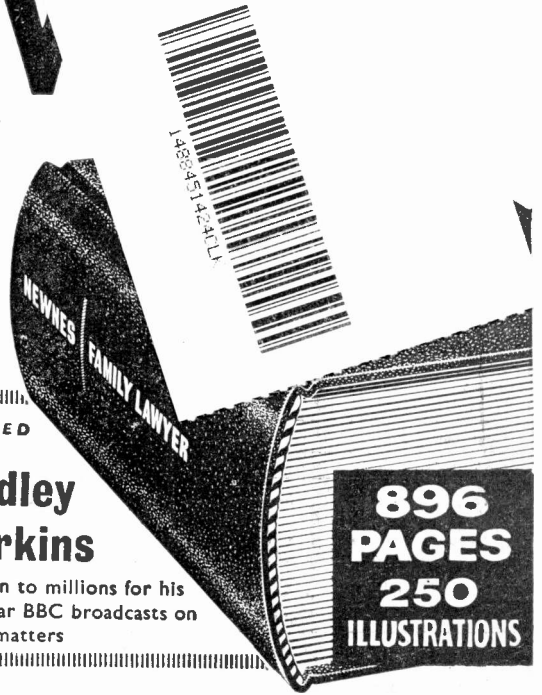Known to millions for his  
popular BBC broadcasts on  
legal matters



## STUDY IT FREE FOR 7 DAYS

Written in Everyday Language by  
leading Barristers and Solicitors

Everything in Law—Land ownership, Leases, Tenancy Agreements, Repairs, Sub-letting, Rent-control, Parents and Children, Changing your name, Negligence, Blackmail, Misrepresentation, Pensions, IOUs, Libel, Slander, Damages, Town and Country Planning, Provocation, Trespass, Nuisance from noise, Factories Act, Cheques, Road Traffic Laws, Rights of a finder, Neighbours, Investments, Annuities, Insurances, Wills, Law on Clubs, Gaming, Lotteries, Fishing Laws, FREE LEGAL AID explained . . . And much more besides.

HANDSOME DURABLE BINDING  
WITH CONTEMPORARY DESIGN

THIS IS THE FIRST  
ILLUSTRATED FAMILY LAWYER

DUDLEY PERKINS clarifies points of law with 250 special illustrations—the modern way to explain simply! Send now and see this practical new Home Lawyer for a week without cost.

In this complex age of do's and don'ts, rules and regulations, laws and liabilities, the need for an understanding home legal guide is urgent. You know that ignorance of the law is no excuse—yet you are burdened by complicated language which only a legal mind can fathom! Here at last is the answer—NEWNES FAMILY LAWYER which explains your rights and privileges and liabilities in all your personal, family and business affairs. It will save you annoyance and anxiety . . . and prevent you from taking risks. Study it free for a week without obligation to buy!

**Post To-day**

To: GEORGE NEWNES LTD., 15-17 LONG ACRE, LONDON, W.C.2.

Please send NEWNES FAMILY LAWYER without obligation to purchase. I will return it in 8 days or send 5/- deposit 8 days after delivery, then ten monthly payments of 10/-, paying 105/- in all. Alternatively, in 8 days I will remit the full cash price of 105/-.

If you are under 21 your father must fill up coupon.  
If married woman your husband must fill up.

Full name \_\_\_\_\_  
(BLOCK LETTERS)

Address \_\_\_\_\_

Occupation \_\_\_\_\_

Signature \_\_\_\_\_  
(Mr., Mrs., Miss)

Mr.  
Mrs.  
Miss

Tick V where applicable  
The address on left is—


My Property	<input type="checkbox"/>
Rented unfurnished	<input type="checkbox"/>
Parents' Home	<input type="checkbox"/>
Furnished Accom.	<input type="checkbox"/>
Temporary Address	<input type="checkbox"/>

(FL)39/369




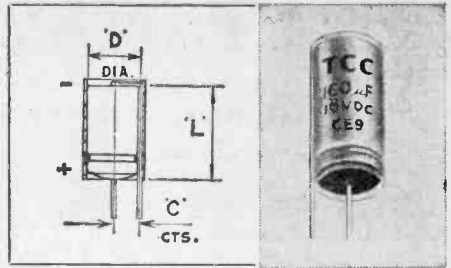
## Sub-miniature Electrolytics for Transistor Circuits



T.C.C. TYPE No.	Case Size in inches			Maximum D.C. Wkg. Voltages and Cap. (µF)					
	D	L	C	3V.	6V.	9V.	12V.	15V.	25V.
CE.2 'V' or 'H'	1/8	1/8	0.07	8	6	4	3	2	—
CE.3 "	7/16	7/16	0.1	25	20	15	10	6	4
CE.4 "	7/16	1/2	0.1	40	30	20	15	8	6
CE.5 "	1/2	7/16	0.14	50	40	25	20	10	8
CE.6 "	1/2	1/2	0.14	80	60	40	30	15	12
CE.7 "	7/16	1/2	0.18	100	75	50	40	20	15
	D	L	C	3V.	6V.	10V.	15V.	25V.	50V.
CE.8 "	1/2	3/4	0.14	100	80	60	40	25	8
CE.9 "	3/8	3/8	0.2	250	200	160	100	60	20

V = Vertical Mounting      H = Horizontal Mounting

**Operating Temperature Range.** -20 C. to +60°C.

**Connection wires** are welded for low resistance contact, and solder-coated for ease of assembly, the standard length being 1 1/2" for the horizontal range, cropped to 3/8" long for the vertical range.

**The capacitors** are in insulated seamless aluminium cases, sealed with a synthetic rubber bung.

**Cap. Tolerance.** The standard tolerance of all capacitors is -20% + 100% of the rated capacitance.

**Leakage Current.** This may be determined from the following:  $1(\mu A) = .01 \text{ C.V.} + 10$  at applied working voltage and at 20°C.

## THE TELEGRAPH CONDENSER CO. LTD.

Radio Division · NORTH ACTON · LONDON · W.3 · Tel. ACOrn 0061 · Telex: 261383  
(also at) CHESSINGTON, SURREY :: BATHGATE, SCOTLAND

VACUUM  
ELECTRONIC  
LIMITED

## KEEPS YOU IN THE PICTURE

WITH THE  
FINEST REBUILT CATHODE RAY TUBES  
12 MONTHS  
GUARANTEE

12" - 14" £4-15-0  
15" - 17" £5-5-0  
21" £7-15-0

CASH WITH ORDER OR  
PRO FORMA, ADD 12/6 FOR  
CARRIAGE AND INSURANCE.

DELIVERY FREE IN LONDON AREA

15/-

ALLOWED  
ON RECEIPT  
OF OLD  
TUBE

WRITE PHONE OR CALL

VACUUM ELECTRONIC LTD.

35, SACKVILLE STREET  
LONDON, W.1  
REGENT 6404 (5 lines)

## YOUR CAREER in TELEVISION?

Big opportunities and big money await the qualified man in every field of Electronics today—both in the U.K. and throughout the world. We offer the finest home study training for all subjects in radio, television, etc., especially for the CITY & GUILDS EXAMS. (Technicians' Certificates); the Grad. Brit. I.R.E. Exam.; the RADIO AMATEURS' LICENCE, P.M.G. Certificates; the R.T.E.B. Servicing Certificates; etc. Also courses in Television; Transistors; Radar; Computers; Servomechanisms; Mathematics and Practical Transistor Radio course with equipment. We have OVER 20 YEARS' experience in teaching radio subjects and an unbroken record of exam. successes. We are the only privately run British home study college specialising in electronic subjects only. Fulliest details will be gladly sent without any obligation.

To: BRITISH NATIONAL RADIO SCHOOL, Dept. 2  
RADIO HOUSE, READING, Berks.

Please send FREE BROCHURE to:

NAME ..... Block

ADDRESS ..... Caps.

..... Please  
1.64

BRITISH NATIONAL RADIO SCHOOL

# Practical Television

AND TELEVISION TIMES

VOL. 14, No. 160, JANUARY, 1964

Editorial and Advertisement  
Offices:

## PRACTICAL TELEVISION

George Newnes Ltd., Tower House  
Southampton Street, W.C.2.

© George Newnes Ltd., 1964

Phone: Temple Bar 4363.

Telegrams: Newnes, Rand, London.

## SUBSCRIPTION RATE

including postage for one year

To any part of the World £1.9.0

## Contents

	Page
Editorial ... ..	147
Teletopics ... ..	148
A Flying-Spot Transparency Scanner ... ..	150
How to Receive BBC 2 ... ..	154
On the Air ... ..	157
Evasive Picture Faults ... ..	158
Principles and Practice of Colour Television ... ..	161
DX-TV ... ..	167
New Thoughts on TV Aerials ... ..	168
Using the BY100 Silicon Diode	171
Servicing Television Receivers	172
A Closed Circuit TV Camera ... ..	175
Underneath the Dipole... ..	182
Your Problems Solved ... ..	184
Test Case ... ..	188

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television". Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, "Practical Television", George Newnes Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

## One More Year

AT this time of year, it is traditional to reflect on the twelve months that have ticked by and to wax enthusiastic (and usually optimistic) on days to come.

Cynics might argue that the datum line of the year-end is purely arbitrary and that a more effective close season for reflection and resolution might be devised at any time. The fact remains, however, though the opportunity is always there, it never seems to materialise. Yet the calendar is irrevocable. One day it is December 31st. The next it is January 1st.

How do we, at PRACTICAL TELEVISION, react to this season of meditation? Looking over the last twelve issues, we feel some modest satisfaction, and this is justified by the reaction of readers.

Most tastes have been catered for, with constructional articles on Closed Circuit TV apparatus, equipment to receive amateur TV transmissions on 70cm, pieces of test gear such as the Henlow oscilloscope, a transistor pattern generator, a grid dip meter, and articles on building set top aerials, a TV deaf aid, attenuators, etc.

A quick flip through these pages shows a high level of authoritative supporting articles on aspects of fault finding and alignment, in addition to regular features and series of practical value—most of these being written by widely experienced professional contributors.

The subject of 625-line conversion and associated topics have been given the wide coverage they merited. So has colour TV, for though this is unlikely to be launched for at least another year, most TV enthusiasts will have to obtain at least a working knowledge of the principles involved.

And what of the New Year? We shall, of course, give you more articles on CCTV, on aspects of amateur transmitting and on the recently introduced activity of DX searching. We shall also continue to cater for those whose main interest is in the maintenance and servicing of domestic TV sets.

In short, we shall do our best to provide the kind of magazine readers want and our policy will be moulded partly by our own judgement and partly by comments and constructive suggestions received in our mail from readers. We look forward to another mutually satisfactory year in 1964.

## Christmas 1963

Seasonal Good Wishes

to all readers

from the Editor, staff and contributors  
of Practical Television

Our next issue dated February, will be published on January 22nd.

# TELETOPICS

## INDUSTRIAL APPLICATIONS OF TV INCREASE

LAST month's Industrial Photographic and Television Exhibition had the effect of making it clear to anyone who remained uncertain of the importance of television in industrial concerns, just how seriously British Industry takes the introduction of TV into every aspect of production. To any visitors who took the role of CCTV, for example,

to be merely a means of keeping an eye on things this Exhibition must have been something of a revelation.

The manufacturers of CCTV systems at the show—and there were many of them—illustrated such a variety of applications for their products, that visitors must have wondered how the country had survived before the wide-

spread use of CCTV had become accepted. The simple, single-lens camera is apparently no longer sufficiently versatile to meet the needs of industry, and the manufacturers have done an admirable job in designing much more sophisticated equipment without making the units too large or clumsy. Remotely-controlled zoom lenses and motorised turrets have left the camera still compact and relatively easy to operate, and the adaptability of complete systems, which makes their operation possible under the most varied conditions, remove many of the restrictions which faced earlier equipment.

Much in evidence at this exhibition were special housings for TV cameras to protect them during heavy-duty operation, some of which included remote-control pan and tilt heads.

The value of a closed circuit TV system to relay documented information to one or more television screens, depends on the definition it is possible to achieve and some very impressive demonstrations of document transmissions were to be seen at the show.

CCTV has recently been introduced as an aid to television film making, where a TV camera mounted behind the film camera, views the same scene and relays a picture on to a monitor screen, so that the operator can see the scene as it will appear finally on television receivers.

One other aspect of television which is finding acceptance in industry is TV tape recording. Several equipments were displayed at the show, including one American-made portable unit which weighs only 75 lbs., and which uses tape only 1in. wide as opposed to the usual 2in. tape.

## Transmitting Mast Re-erected

THE ITA's Channel Islands transmitting mast at Fremont, St. John's Bay, Jersey, was originally built at the Lichfield ITA station in Staffordshire. This 445ft. tower, which was erected eight years ago by British Insulated Callender's Construction Co., was replaced at Lichfield recently by a taller structure. However, when BIC Construction Co. dismantled the original mast, it was found that the metal was still sound and so its re-erection began at Fremont after the steelwork had received nothing more than a clean and a coat of paint.



The ITA's mast at Fremont, Jersey.

## London Festival of Television

THE first London Festival of World Television ended on December 14th, after a period of nine days when televised tapes and films from countries throughout the world had been shown mainly at the National Film Theatre in London. The Festival was presented by the television quarterly *Contrast* (published by the British Film Institute) and arranged by the National Film Theatre Division of the Institute, in association with the BBC, the ITA and the ITV Companies. Towards the cost of the running of the Festival, equal cash contributions totalling £6,000 were made by the BBC, the ITA and the Companies.

Approximately 15 per cent of the total screen time was given over to British work.



## CCTV in St. Paul's Cathedral

WHEN H.R.H. The Duke of Edinburgh attended the Dedication Service for the Most Excellent Order of the British Empire in St. Paul's Cathedral recently, four television cameras relayed pictures of the Service to 30 23in. receivers placed in many parts of the Cathedral. The complete system had been installed for the occasion by Kolster Brandés Ltd., using KB receivers and cameras supplied by Television Advisers Ltd.

## £8,000 TV SYSTEM FOR LONDON COLLEGE

THE University College, London, is to have an £8,000 closed circuit television system installed to aid biological science studies. The Rank Audio Visual Division of the Rank Organisation has received the order to install this equipment in the new year.

The two vidicon cameras to be employed in the system are of studio type incorporating zoom and four-turret lenses. A mobile control unit will monitor the outputs to six 23in. 625-line receivers.

## 300 See Queen Mother on CCTV

ON November 14th, Queen Elizabeth, the Queen Mother, opened the new Shire Hall in Gloucester. Four hundred and fifty guests had been invited to the ceremony, but because of the limited seating in the Council Chamber, 300 viewed the entire event on television receivers. Television pictures from three points in the building were relayed from three cameras to the 12 receivers, over a closed circuit link which had been installed for the occasion by EMI Electronics Limited.

## Television Navigation Aid for Tanker


IN November this year, the largest tanker ever built in Norway was launched at Stavanger. An important part of the navigational equipment fitted to this new ship is a British-made CCTV system which will provide the ship's captain with an extra "eye" when entering harbours and docks. The equipment, which was supplied by the Rank Organisation, consists basically of a specially designed television camera and a viewing monitor.

## OPERATIONS TELEVISED IN COLOUR

ONE of the most ambitious programmes of televised medical operations in colour was successfully carried out recently, when a Marconi vidicon colour camera channel relayed pictures from the operating theatre of Hammersmith Hospital in London to the Isaac Wolfson Institute adjoining the hospital, and to the Royal College of Surgeons at Lincoln's Inn Fields. During the five days of the demonstrations, many operations were shown to the audiences which assembled in the two terminal points of the link, making it possible for a total of 1,300 people to watch any of the operations.

At each operation the surgeon gave a running commentary of his work, and members of the audience were able to put questions to him at any time throughout the operation. The audience viewed the televised scenes on 9ft. by 12ft. screens on to which the pictures were projected by Marconi colour projectors.

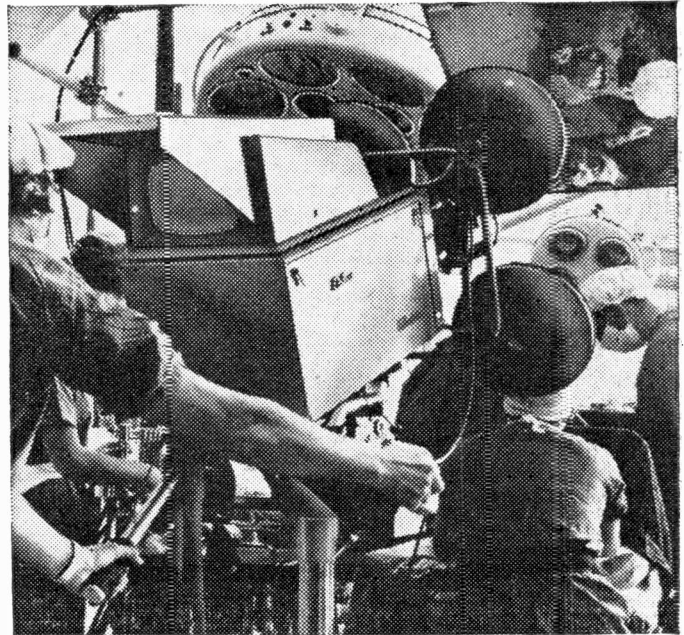The camera took the pictures from the reflected image in a mirror suspended above the operating table.



A colour television camera televising an operation at London's Hammersmith Hospital.

## "Dawn University" TAM Rating

THE first audience research figures reaching the ITA from TAM indicate that about 200,000 homes tuned in to one or more of the "Dawn University" lectures broadcast at 7.15 each morning during a week in October. These lectures were by way of being an experiment and were at first year undergraduate level.

Although no conclusions can be drawn from these figures until a more detailed assessment of the lectures has been presented to the Authority, it is interesting to note that 200,000 is nearly double the total university population of Great Britain.

# A Flying-Spot Transparency Scanner

BY J. G. RANSOME

WHEN the writer first contemplated this television system he was advised by the wise-heads amongst his friends (those whose job was the designing and construction of television systems) that he might as well stop before he began as the problems involved were formidable and virtually insurmountable for the average amateur. Undaunted by this pessimistic counsel the system has been designed and built and the writer has had the satisfaction of seeing behind-the-hand comments turn into enthusiastic advice.

It must be emphasised from the outset that the picture quality is not that of the highest professional standards; however, this is not to belittle the performance of the system which is quite capable of resolving typescript legibly and is excellent for the display of black and white negatives.

Whilst the writer believes that the construction of the unit is beyond the absolute beginner, he is

convinced that it is not purely the province of the advanced constructor, for in this design it is the "middle-man" who is being catered for and anyone competent with a soldering iron and willing to tackle simple radio-type circuits should be able to undertake the construction of this apparatus.

A block diagram of the complete flying-spot scanner is shown in Fig. 1.

As can be seen from this diagram, the unit is designed to feed an ordinary domestic television receiver; however, should this be inconvenient a simple monitor may be constructed. Subsequent articles will be devoted to the construction of two different types of monitors—one of simple design, and the other a more advanced design.

## THE SYSTEM DESCRIBED

The basic operation of a flying-spot scanner is very simple. The timebases of the scanner and monitor are run in step. The photo-multiplier "sees" the trace on the scanner tube through the transparency and transmits a signal which is proportional to the light incident on its cathode and this signal is amplified and used to modulate the monitor tube.

To illustrate the point let us take a fairly simple example. Consider a scanner and monitor running in step each producing an eight-line picture the scanned transparency being a cross as shown in Fig. 2.

Starting at the top left-hand corner of the picture and looking at line 1, the sequence of operations is as follows.

The line and frame timebases fire and as the spot draws out the first section of the line (up to A) the photo-cell receives full illumination and holds the monitor tube (to which it is connected) at full brilliance. Then as the line is drawn from A to B the photo-multiplier receives no light and thus cuts off the monitor tube so that that part of the trace is not visible, then from B to the end of the line full brilliance is restored.

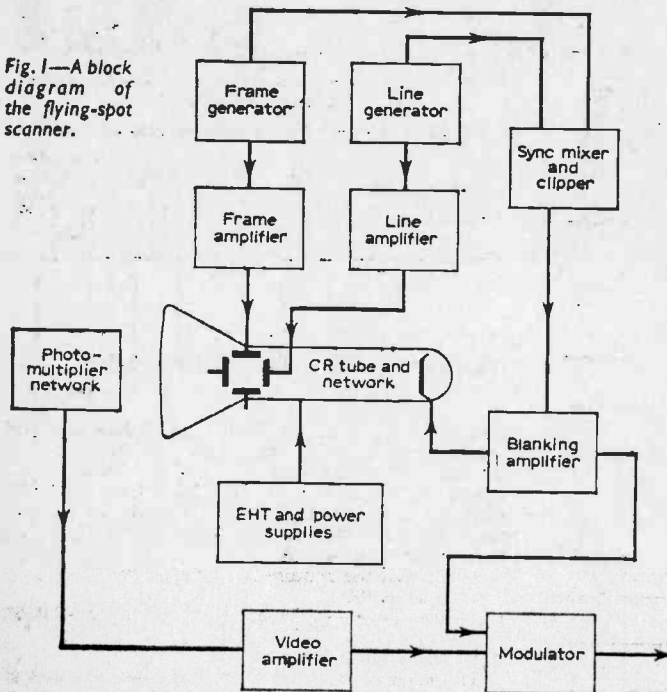


Fig. 1—A block diagram of the flying-spot scanner.

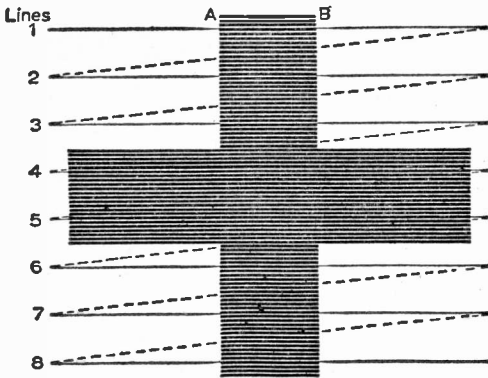


Fig. 2—This diagram helps to illustrate the principle of the scanner (see text).

A graphical representation of the photo-tube output is shown in Fig 3(a). The same series of events occurs for lines 2 and 3 but when we come to lines 4 and 5 we find that they are cut off altogether and so the monitor tube does not display these two lines. For lines 6, 7 and 8 a similar effect to that for line 1 is evident. The resultant trace on the monitor tube is shown in Fig. 3(b). If we imagine the lines as shown to be white then the places where the trace has been cut off will appear dark and so the eye will make out the outline shown by the dotted lines. The signal that appears at the photo-tube anode to modulate the monitor during one such complete frame is shown in Fig. 3(c).


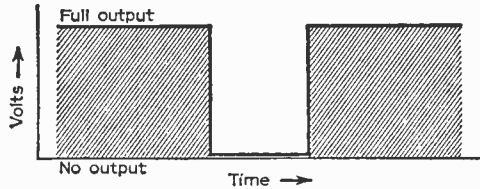


Fig. 3a (above)—The photo-tube output.

Fig. 3b (below)—The resultant trace on the monitor screen.

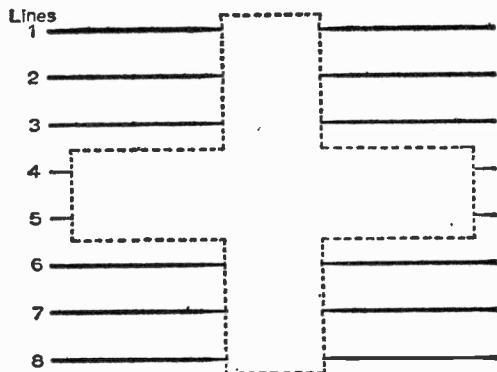

Unfortunately the situation is not quite as simple as this as we have to make sure that the timebases run in step; that is to say that each line has to begin and end at the same time on both the scanner and monitor tubes. Thus we need to synchronise the two traces. Fortunately television timebases can be designed so that we can cause a new line stroke to commence if we arrange a suitable pulse to be fed to the timebase at approximately the right time.

These pulses are available from the scanner timebases and are mixed with the video signal and fed into the monitor set. Such pulses are known as synchronising (sync) pulses. Thus a full composite signal containing all the information needed to reproduce the shape of Fig. 2 is shown in Fig. 3(d).

This then is the theory and a brief idea of what the design is trying to achieve. We now move on to the actual construction.

### THE POWER UNIT

The circuit of the power unit is shown in Fig. 4 and there is little here that is out of the ordinary.

The main h.t. is derived from a 350-0-350V transformer T2, and is rectified by the 5Z4 in a full-wave circuit. As can be seen from the circuit, choke smoothing is employed and this is to be preferred to resistive smoothing because of the need for a fairly ripple-free h.t. line together with the best possible regulation. The stabilised h.t. line is


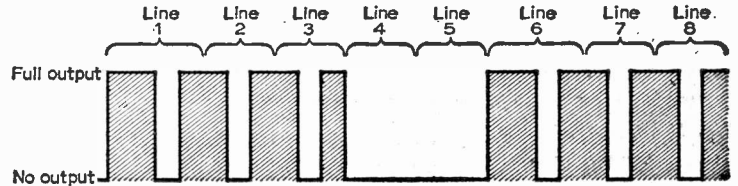


Fig. 3c (above)—The signal as it appears at the photo-tube anode.

Fig. 3d (below)—The composite video output signal.

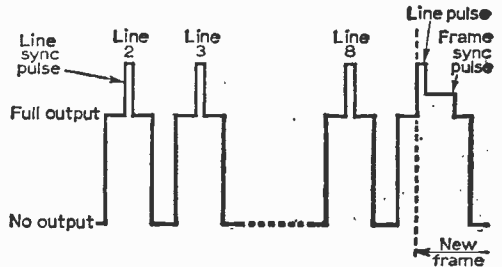

obtained by use of the VR150/30 regulators. The series resistor, R2, regulates the current flow through the regulator system and the value of this resistor assumes a raw h.t. potential of 350V. Should the h.t. voltage exceed this value, R2 will have to be adjusted to limit the current drawn by the stabilisers to 40mA.

The resistance required is given by:


$$R2 = \frac{V \text{ h.t.} - 300}{40}$$

Where V h.t. = raw h.t. voltage  
this gives a value for R2 in kΩ.

The negative h.t. line is derived from one side of the transformer, and although the circuit is



Fig. 5—The wiring diagram.

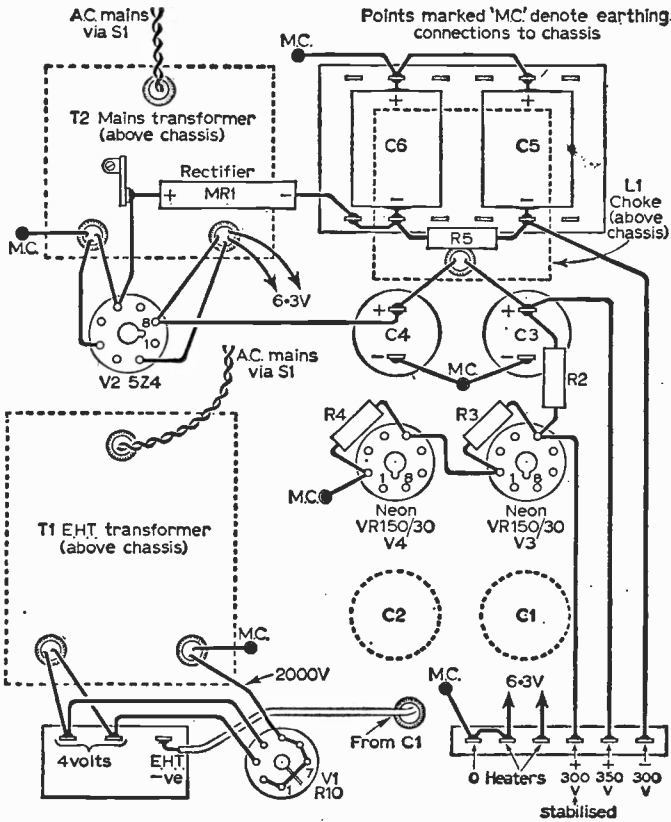

With reference to Fig. 7 the circuit description is as follows.

Point A is at  $-2,300\text{V}$  compared to the chassis and is the most negative part of the circuit. As we go up the chain from A the voltage becomes more positive with respect to A until we get to the h.t. connection which is  $2,650\text{V}$  positive with respect to A.

Across this potential is connected the bleeder chain of R7, VR1, VR2 and R8. Grid bias (which controls the electron flow in the tube and hence the brightness) is

—continued on page 180

COMPONENTS LIST	
<b>C.R. TUBE UNIT (Fig. 7)</b>	
<b>Resistors:</b>	
R6 $47\text{k}\Omega$	R8 $3.3\text{k}\Omega$
R7 $2\text{M}\Omega$ (4 x $500\text{k}\Omega$ —see text)	
VR1 $500\text{k}\Omega$ potentiometer	
VR2 $100\text{k}\Omega$ potentiometer	
<b>Valve:</b>	
V5	VCR517C

**THE C.R. TUBE UNIT**

The tube unit and network is shown as Fig. 7. The tube used is the VCR517C which has a short persistence blue trace with a long yellow afterglow. The photo-cell is insensitive to yellow light and extremely sensitive to blue, and thus the effect of the afterglow is eliminated so that only the very short persistence blue trace is used for the scanning and this is precisely what is required.

The characteristics of the VCR517C are shown below:

Heater 4V	1.0A
Va1 and Va3	2,500V
Va2 ("focusing")	260 to 470V
Vg ("brightness")	-1 to -100V


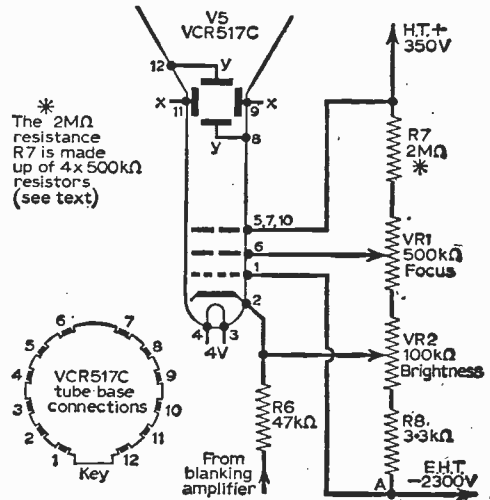


Fig. 7 (above)—The tube unit and network.

Fig. 6 (left)—The wiring of the rectifier and smoothing components.

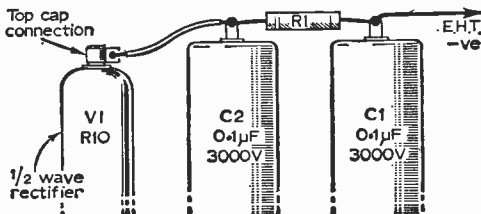

# How to Receive

BY K. ROYAL

# BBC 2

**M**OST of our readers are now well aware that the new 625-line television programmes will occupy channels in the u.h.f. bands, Bands IV and V. Eventually, there will be two extra programmes at 625-line u.h.f. The first is the second programme of the BBC, called BBC-2, and later there will be a second ITV programme.

The first London u.h.f. 625-line station is due to start a complete service on April 1st, 1964. This will be on Channel 33, and at the time of writing test transmissions are already being carried out on that channel from Crystal Palace.

## U.H.F. Development

In addition to the London station, there has been Government approval for the building of seventeen u.h.f. stations in two stages. That is, eight stations by the end of 1965 and nine more by the end of 1966 or a little after.

Areas to be covered in the first stage are the Midlands, Lancashire, South Yorkshire, Central Scotland, North-East England, Northern Ireland and the Isle of Wight. In the second stage the Bristol area, Norfolk, Anglesey, North-East Scotland, South-East Kent, Nottinghamshire, North Yorkshire and Northamptonshire will be embraced.

These two stages of development will bring 625-line u.h.f. television programmes to about 75 per cent of the population, and small booster and relay stations will fill in the signal shadow zones around the areas mentioned. About 95 per cent coverage will be given by stage three of exercise 625-line u.h.f. This will take place after 1966, and by about 1969 will include almost 50 main u.h.f. stations and many boosters and relays.

Each u.h.f. station and aerial system will be engineered for four eventual u.h.f. channels, so that ITV-2 and extra programmes, up to a total of four, can be transmitted in any given area. This will include the possible changeover of existing 405-line programmes to 625 lines so that these could be broadcast together with BBC-2 and ITV-2.

Each u.h.f. channel is 8Mc/s wide and each station group is allotted a piece of u.h.f. spectrum eleven channels wide (e.g. 88Mc/s) into which its four channels are placed. Each of the four channels is identified relative to the lowest frequency channel of the group, where "n" signifies the lowest frequency channel. The London area group is n, n+3, n+7 and n+10, where n is Channel 23. Thus, the four London u.h.f. channels are 23, 26, 30 and 33 respectively. The highest frequency channel (n+10) is the first to be used on a permanent basis, as previously intimated.

## Channel Identification

This method of channel identification makes it also possible to determine the frequency of a

channel of the group provided the frequency of the lowest number channel is known. For example, the vision carrier frequency of London n (Channel 23) is 487.25Mc/s. This means, then, that n+3, for instance, has a frequency of  $487.25 + (3 \times 8)$ Mc/s, which works out to 511.25Mc/s. This, of course, is the frequency of Channel 26. The "times 8" factor of the formula simply relates to the fact that each channel is 8Mc/s wide. The "3" puts the channel being identified three channels up from n, or Channel 23, making it Channel 26, of course.

In many cases the u.h.f. transmitters and aerials will be co-sited with existing v.h.f. 405-line stations. This is desirable since it means that a composite receiving aerial need be adjusted only for maximum reception on the u.h.f. programmes, with the knowledge that it is also pointing in the right direction for the v.h.f. programmes.

It must be emphasised that the new programmes of BBC-2 will in no way affect the existing 405-line programmes of BBC-1. BBC-1 will continue for many years to come, and when the time eventually comes for the old 405-line system to be replaced completely by the better 625-line system, the 405-line programmes will probably be duplicated on the 625-line system during the period of the changeover. However, there is no absolute decision on this at the time of writing.

While the existing 405-line sets will continue to receive the 405-line programmes on the v.h.f. channels, a new type of dual standard set is needed to receive both the 405-line programmes and the new 625-line u.h.f. programmes of BBC-2.

## Four Types

During the last year or so four types of sets have been sold. These are (i) 405-line-only, (ii) convertible to dual standard, (iii) dual standard without u.h.f. tuner and (iv) dual standard with u.h.f. tuner. Sets in category (i) are the original 405-line models which have been used over the years. These are not suitable for receiving the 625-line programmes on u.h.f., and there is definitely no simple kind of 625-line converter or adaptor for this type of set.

Experimenters with a spare, early type set to experiment with will no doubt try their hands at rebuilding for 625-line u.h.f. operation.

Full details of an experiment of this kind are given in the July, August, September and October, 1963 issues of PRACTICAL TELEVISION, under the title "Towards 625 Lines", by D. Elliott.

Sets under category (ii) are not immediately suitable for reception of BBC-2 as they stand. Early purchasers of these models may not be clear that, in some cases, substantial modifications are required to get them to work on both standards. These sets were sometimes called "convertible to switchable", since conversion is required to make them switchable from one standard to the other.

They need a u.h.f. tuner in addition to the internal modifications, and the overall cost of conversion, including a u.h.f. aerial (required by all dual standard sets) could well exceed £20. The method of this type of conversion varies between makes and models, and in many cases it was originally envisaged that a 625-line i.f. strip and video stage (plus flywheel line sync unit) would be installed by the side of the existing 405-line i.f. strip.

Slightly later convertible to switchable models were designed so that the whole of the original 405-line i.f. strip could be replaced by a single i.f. strip of the dual standard variety, as used in true dual standard models. It should be noted, however, that the original conception of conversion may not apply in practice with all models. There have been second thoughts on the problem by some makers, but viewers can rest assured that where a manufacturer has committed himself to convertibility when selling the set, the original or a new method of conversion is, or will be made, available.

### **Transistorised 625-line Strip**

A new thought by Ekco, for instance, abandons the original idea of replacing the existing i.f. strip with a dual standard strip. Conversion of these models now adopts a transistorised 625-line-only strip, incorporating an f.m. sound detector. The strip is fed with signal from the u.h.f. tuner and itself supplies suitable signal direct to the video amplifier stage.

Sets under the Thorn banner (such as Ferguson, HMV, Marconiphone, Philco and Ultra) are converted by the addition of a 625-line-only strip with its own u.h.f. tuner. This works side-by-side with the original 405-line strip.

A similar technique is adopted by Phillips, Pye and Baird. Murphy uses a plinth unit beneath the cabinet where there is a mechanism which couples to a toggle-type standard change switch. Connection is essentially by plug-and-socket, as with Decca and others.

It is not possible within the compass of this article to provide details of individual conversions, but viewers in doubt about the convertibility of their sets would be well advised to consult their dealers as soon as possible, for once the new programmes are underway there is almost certain to be a rush for conversions, as when the ITV programmes started.

### **Plugs and Sockets**

Sets under category (iii) are properly engineered for operation on both standards, but before the new programmes can be received a u.h.f. tuner and aerial will need to be fitted. The retail price of u.h.f. tuners seems to have settled around the seven-guinea mark, and for fitting them into the type of set now under discussion plugs and sockets are invariably provided. The actual fitting, compared with converting to switchable, is relatively inexpensive and should not present too many problems. Many of our readers should be able to tackle this job for themselves.

Sets under category (iv) are completely ready to receive the new programmes, and many of these sets are, at the time of writing, successfully receiving the 625-line u.h.f. test transmissions.

Readers with this type of set need only instal a suitable u.h.f. aerial to get BBC-2, as well as the existing BBC-1 and ITV-1 programmes.

It is impossible to say just how much a u.h.f. aerial system is likely to cost, for very much depends upon the strength of the u.h.f. signals in the area and upon whether the receiving site is screened from the transmitter by rising ground or large buildings. The u.h.f. characteristic makes the signals behave rather more like light than the v.h.f. signals that we are used to. This means that u.h.f. signals find it more difficult to penetrate massive hills and structures than v.h.f. signals. There is also less bending of the signals at u.h.f. compared with at v.h.f., making shadow areas much more defined so far as the new signals are concerned.

There is no simple remedy for these problems, and if the signal is just not present due to an intervening hill, for example, there is no point in adding preamplification or extra aerial elements. The solution lies in increasing the height of the aerial so that it "looks" over the top of the hill.

In weak signal areas generally, however, improved signal pickup can often be secured by the use of extra elaborate aerial systems. At this juncture it should be noted that to avoid confusion when referring to the number of elements on a u.h.f. aerial British manufacturers have agreed that the reflector will always be counted as one, regardless of the form or number of rods used.

### **Reflector Counts as One Element**

While ordinary v.h.f. aerials usually have just but a single reflector rod, u.h.f. aerials often have a reflector made either of four or more rods of wire or metal mesh. The overall gain of the former is probably not any greater than the latter, so it would be misleading to add the number of rods making up the reflector to the number of aerial elements.

As a rough guide in areas where the screening is average, a nine-element array will give reasonable reception within a radius of about 15 miles from the transmitter, a thirteen-element up to about 20 miles, an 18-element beyond 20 miles and in "difficult" locations nearer to the transmitter.

For extreme fringe area working and in extra difficult areas, stacked, broadside and "quad" arrays of the above aerials may well be needed. Fortunately, the length of u.h.f. aerial elements is around about a foot or a little under, so many of them can be used without the array becoming too unwieldy. In general, however, a u.h.f. array ends up with about the same amount of metal as a v.h.f. array operating in a "reasonable" reception area from a co-sited transmitter. This means that although the u.h.f. elements are smaller than v.h.f. ones, there are about four or five times as many of the former than the latter.

### **8Mc/s Wide**

Whilst as a general rule v.h.f. aerials are tuned to a specific channel, u.h.f. aerials nearly always embrace a group of eleven 8Mc/s channels. The reason for this is two-fold. Firstly, the u.h.f. characteristic automatically endows the array with a relatively wide band and, secondly, the aerial must be suitable to receive the eventual four u.h.f. channels of a local group (see the first part of this article).

The relatively large number of u.h.f. elements in an aerial array, makes the array far more directional than an ordinary v.h.f. array. High directivity is desirable at u.h.f. since these signals are more easily reflected than v.h.f. signals. The directivity factor means that the array can be carefully orientated to provide the best possible signal/"ghost" ratio. It also means, however, that incorrect orientation over just a few degrees, which would have no effect at v.h.f. is likely to attenuate the aerial signal by two or more times.

It is essential, therefore, that the u.h.f. aerial is carefully set up in the first place, either on a transmission or, preferably, on a signal strength meter, for the maximum signal pickup. Sets (of all types) are less sensitive on the u.h.f. channels than on the v.h.f. channels. In general, this means that the set needs more u.h.f. signal to give a picture which is no more grainy than the v.h.f. picture. Sometimes the u.h.f. signal has to be about twice as strong as the v.h.f. signal to satisfy this condition.

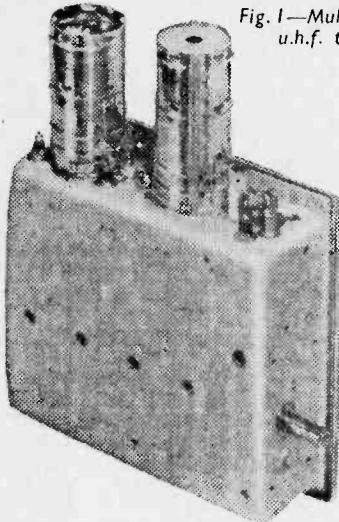


Fig. 1—Mullard's new u.h.f. tuner.

The extra strong u.h.f. signal can only be obtained by using an aerial system which is suitable for the area, ensuring that it is adjusted for maximum signal pickup and that it is connected to the set through super low-loss coaxial cable. The latter is necessary since ordinary medium-loss v.h.f. coaxial cable could reduce the u.h.f. signal relatively by about four times—the losses at u.h.f. being that much greater.

The u.h.f. array should be mounted as far as possible away from the v.h.f. array and other metal objects, for otherwise "proximity effects" could detract seriously from the u.h.f. signal pickup.

#### Separate Inputs

All dual standard sets (and converted models) have separate inputs for v.h.f. and u.h.f. This is good since it means that the ordinary v.h.f. installation and feeder can remain as it is and that an extra low-loss feeder can be employed on the u.h.f. aerial.

Later, sets will probably be made with a common aerial input socket, but this would not be very

suitable for low signal working owing to the extra losses in the combining filter. A commercial combining filter is available, but it is recommended only in those areas where the u.h.f. signal is extra strong, so that it can be routed via the ordinary v.h.f. feeder.

In some locations very close to a transmitter a set-top u.h.f. aerial may be suitable. Normally, however, a good outside array will be the order of the day. If there is insufficient chimney room to cater for the extra u.h.f. aerial, it may be worth considering bringing the v.h.f. aerial indoors so that the chimney can accommodate the u.h.f. aerial without proximity troubles. These days, a set-top or roof-space v.h.f. aerial system generally serves quite well.

#### Signal Probing

Aerial positioning at u.h.f. is far more critical than for v.h.f. In fringe areas the presence of "standing waves" may make it necessary to "probe" for the signal. Merely changing the aerial from one corner to an opposite corner of the same chimney stack could make a great difference in signal pickup.

Most u.h.f. tuners have some kind of scale calibrated in channel numbers. The tuners employ ganged capacitive tuning (like ordinary radio sets) and channel coverage is continuous over the scale. The tuner spindle is coupled to the knob through a slow-motion drive. On no account should a u.h.f. tuner be dismantled, for even a small change of stray capacitance or inductance could swing the alignment out and reduce the overall sensitivity. A tuner of the new Mullard design is shown in Fig. 1.

This is continuously variable over the range from 470 to 860Mc/s. It incorporates two frame grid triodes: a PC88 operating as a grounded-grid r.f. amplifier and a PC86 as a self oscillating mixer with an i.f. output over the range 33.4 to 38.9Mc/s.

Remember that dual standard receivers have two line hold controls, one for 625 lines and the other for 405 lines. The appropriate control comes into operation when the front controls are set for 405 lines or 625 lines. On the u.h.f. channels the v.h.f. tuner is muted and the u.h.f. tuner is switched into circuit, and the opposite happens on the v.h.f. channels. ■

★ ★ ★ ★ ★ ★ ★ ★

## LAST MINUTE CHRISTMAS GIFTS

★ No need to rush out to the shops. Here's one you can arrange now... in a few moments... in the comfort of your own armchair. A year's subscription for PRACTICAL TELEVISION is the ideal gift for friends who are television enthusiasts. ★  
★ But hurry! You must send now to make sure that the first copies arrive in time for Christmas. Simply send your friends' names and addresses, together with your own and remittance \* to cover each subscription to The Subscription Manager (G.3), PRACTICAL TELEVISION, Tower House, Southampton Street, London, W.C.2. An attractive Christmas Greetings Card will be sent in your name to announce each gift. ★  
★ \* RATES (INCLUDING POSTAGE) FOR ONE YEAR (12 ISSUES): U.K. AND OVERSEAS £1. 9s. 0d. U.S.A. \$4.25. ★

★ To make sure of your own copy why not place a regular order with your newsagent. ★

★ ★ ★ ★ ★ ★ ★ ★

# ON THE AIR

## Amateur Band Topics

### RECEPTION OF AMATEUR TV SIGNALS

THE following notes are intended to assist the enthusiast who has built the 70cm receiving equipment described in last month's issue of PRACTICAL TELEVISION.

When searching for 70cm signals always remember to rotate the aerial into the required direction because signals can be missed due to the directivity of the aerial (the 16-element stack array has a beamwidth of about 30 deg.). At some time during the operation of the receiver signals will be received which are not strong enough to please the operator and he may then wonder what improvement, if any, can be made. Obviously improvements can be made at the transmitter end as well as the receiving side to increase signal strengths, however only the receiving end will be considered.

#### The Basic Receiver

Before trying to increase signal strengths it is important to ensure that the television receiver is making the best out of the existing signal. The performance of television receivers with weak signals varies enormously, the locking qualities of the timebases being paramount.

The line frequency locking circuit should be reasonably immune from noise influence though still being capable of a good solid lock on noisy signals. The flywheel synchronising circuit used on some receivers can be excellent in this respect but may have undesirable features for other uses.

The frame lock circuit should be as solid as possible with weak signals. Good interlace, which is sometimes lacking in these sort of circuits, is not necessary for weak signals; anyway, many amateurs do not transmit 405-line interlace.

Assuming that the TV receiver has a good performance, as above, its signal-to-noise performance and that of the whole system can be improved by limiting the i.f. video bandwidth to about 1Mc/s. This should only be done using a wobulator and after all other methods of improving the signals have been exhausted. The definition, of course, will be limited but the improvement on very weak signals is quite surprising.

A higher-gain aerial will give better signal-to-noise ratio although, depending on the particular type of aerial used, a narrower beamwidth usually results. As mentioned previously, the higher the beam is mounted the better; this is especially true until it clears immediate surrounding obstructions. Once clear there is still further improvement by going even higher—but at a smaller rate.

#### A Pre-amplifier Stage

The converter only uses a diode mixer and by using a preamplifier with a suitable valve or valves the signal-to-noise ratio of the converter can be

raised by several dB. A suitable valve is the G.E.C. A2521 grounded grid triode, which at 70cm will improve the signal-to-noise ratio of the converter by some 5dB. There are other more expensive valves available but the improvement will only be marginally better than with the A2521.

However, before investing in a preamplifier it is worth trying a selection of diodes in V2 position, especially if they have been obtained from a Government surplus store. A rough check on the diode is to measure its forward and reverse resistance (do not pass more than a few milliamps through the diode). In general the greater the ratio the better the diode.

Readers may be wondering over what sort of distance signals can be expected. Apart from unusual conditions, the distance covered depends a great deal on the location of the transmitter and receiver and the terrain between. With very favourable sites 100 miles is a realistic distance. On the other hand, from very poor locations less than ten miles can be expected. However, when propagation conditions are very good, hundreds of miles may be expected even from poor locations.

—G3LGJ/T

### AMATEUR TELEVISION BANDS

425—445Mc/s	70.0cm
1,225—1,290Mc/s	23.0cm
2,300—2,450Mc/s	13.0cm
5,650—5,850Mc/s	5.2cm
10,000—10,500Mc/s	3.0cm
21,000—22,000Mc/s	1.4cm

The maximum d.c. input power to the final stage is limited to 150W. Classes of emission permitted: A1, A2, A3, A5, F1, F2, F3 and F5.

### BRITISH AMATEUR TELEVISION CLUB

THIS club was founded in 1949 to inform, instruct and co-ordinate the activities of amateur radio enthusiasts experimenting with television transmission. The BATC is affiliated to the Radio Society of Great Britain. About one-third of the membership reside abroad. Other countries where there is considerable amateur activity are Australia, Canada, France, the Netherlands and the USA.

In the U.K. there are local groups and activities range from constructional work to lectures. Public demonstrations of equipment at local exhibitions are frequently given by members of such groups.

Further information about the BATC can be obtained from the Hon. Secretary, c/o 4 Inwood Close, Shirley, Croydon, Surrey.

# ELUSIVE PICTURE FAULTS

BY T. S. SMITH

**M**ANY of our readers are now well able to relate particular picture symptoms to definite fault conditions within the set. As an example, the symptom of a bright, horizontal line on the screen instead of a picture or raster signifies to many that something fairly drastic has gone wrong with the frame timebase section of the set. Similarly, a lack of picture width is often correctly interpreted as low h.t. voltage due to a bad rectifier or as a low emission line output valve or booster diode.

There are numerous equally as well known "stock" symptoms which are mentioned time and time again in the literature. The difficulty is, however, when the symptom is one of infrequent display or is rarely written about. With this in mind, the author has taken a series of photographs showing the more elusive kind of symptoms as actually displayed on the screens of faulty receivers so that they and their remedies may be brought to the attention of our readers.

## BEAM MODULATION

In Fig. 1 is shown the symptom of modulation of the electron beam in the picture tube with ripple. The alternate light and dark vertical bars at the left of the screen are best displayed on a blank raster. That is, with the aerial disconnected from the set, the contrast control turned right down and the brightness turned up sufficiently to give screen illumination (raster). The diagonal lines are not uncommon when there is no signal. These are the flyback lines, of course.

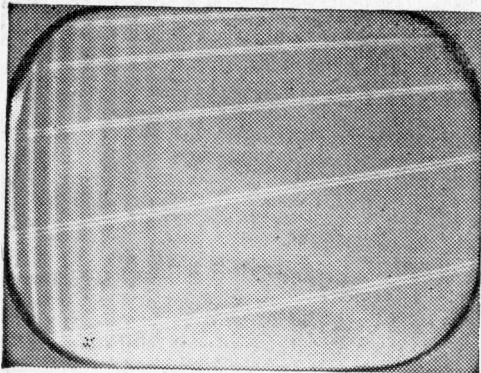


Fig. 1—The symptom of "electron beam" modulation from the ripples in the line output current.

On the line flyback, ripples may occur in the line amplifier causing rising and falling currents. These are sometimes radiated and picked up on the grid circuit of the picture tube, where they cause the *brightness* of the scanning spot to change as it scans the screen, and thus give rise to the symptom as shown.

Proof is readily available, all that being necessary is to connect the grid of the tube to chassis through a large value capacitor. If this causes the screen to clear or, at least, the severity of the symptom to decrease, the trouble is undoubtedly modulation of the electron beam.

The remedy lies first in establishing the whereabouts of the unwanted coupling. A misplaced grid lead hanging near the line output stage is one possibility. Another is incorrect earthing of the metal case of the brightness control potentiometer. If the receiver features frame flyback suppression (in which case the flyback lines as in Fig. 1 would not be displayed when the circuit is working correctly), attention should be given to the capacitors and resistors connected directly to the grid circuit of the tube to the brightness control.

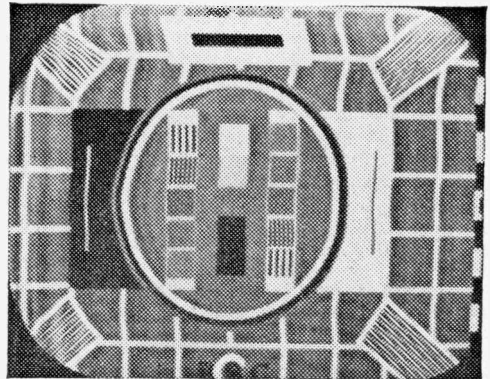


Fig. 2—Kinking at the top of the picture is caused by crosstalk due to coupling (or unbalance) between the line and frame scanning coils (see text).

## VELOCITY MODULATION

Now should it happen that the symptom remains when the tube grid is connected to chassis through a capacitor (use a value of, at least,  $0.1\mu\text{F}$ ), modulation of the electron beam is *not* the cause of the symptom. Here, then, the effect would be caused by the *speed* of the scanning spot changing in sympathy with the line timebase disturbances as the spot scans from the left to the right across the screen.



This effect is often called "ringing" in the line timebase, and used to be very troublesome in early receivers. Indeed, in some of these models the effect is always present to some degree, even when the set is without fault. However, it can be aggravated by a faulty resistor and/or capacitor in a circuit shunting the width or linearity inductor of the line output stage.

Other possibilities are low emission line output valve or booster diode, low h.t. voltage necessitating full setting of the width control to give anywhere near a full line scan and trouble in the line scanning coils or in the line output transformer proper (check for a fractured core).

## CROSSTALK

A similar kind of symptom is seen in Fig. 2; but here the line ripples are induced into the frame scanning coils, causing the kinking effect at the top of the picture. This is called "crosstalk interference".

Fig. 3—Intermittent vibration of the picture.

A defective set of scanning coils can cause the trouble, but more likely is failure or value increase of one (or both) of the low value resistors connected across the frame coils. There are two resistors here, one connected across one half section of the coils and a like value component connected across the other half, with the two connected together at the centre. The value is usually in the region of hundreds of ohms.

On some models a so-called "anti-crosstalk trimmer" is situated on or near the scanning coils on the tube neck. The procedure is to adjust this very carefully until the effect on the picture is minimised. Where it is present, it is rarely possible to

Fig. 4—"Ringing" in the vision channel, a symptom which can be caused by mismatch or trouble in the aerial system, as described in the text.

delete it completely! Note that a high pulse voltage may be present on the trimmer, so use a well insulated trimming tool, such as a suitably tailored plastic knitting needle.


In Fig. 3 we come to something with a different flavour. Here the picture is vibrating up and down at an intermittent and inconsistent rate. This is not really frame judder, which was explained in a previous article, and it may not appear until the set has been running for fifteen minutes or so.

The curious thing is that frame-wise the picture effectively locks, so adjustment to the frame hold control will not cure the fault but will cause it to be superimposed upon a rolling (unlocked) picture. In some instances, the height control may effect a temporarily cure, but then it may well be necessary either to suppress or expand the picture, thereby making it unviewable. Adjustment to the frame linearity control may affect the picture likewise.

Sets with triode-pentode frame timebase valves of the ECL80 and similar category may appear to be cured when the valve is replaced, but this is not always the case, for there is every possibility that the symptom may appear again after a frustrating pause. Resistor and capacitor checks in and around

the frame timebase seem to indicate perfect order, and it is only when the frame blocking oscillator transformer is checked is the culprit brought to light. Tests of winding resistance and insulation of the defective part does not always give a clue as to the fault, and all that can be said is that the insulation possibly breaks down on the frame fly-back when high voltage pulses occur across the windings.

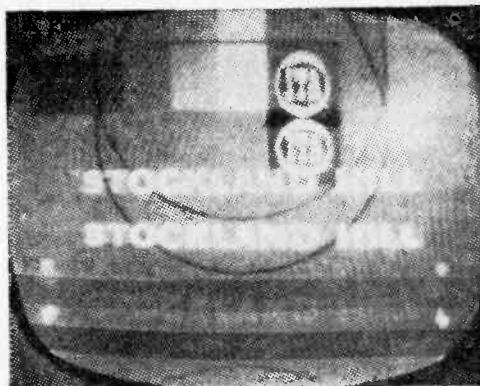It is worth mentioning that similar transformer trouble can affect the frame lock without disturbing the timebase action on certain sets. The photograph in Fig. 3 is taken from an English Electric model with a defunct frame blocking oscillator transformer.



The symptom seen in Fig. 4 is revealed best on pictures with sharp changes from black and white and vice versa in the horizontal direction. It can be caused to happen on some models and under certain conditions by carefully setting the fine tuning control close to the "sound-on-vision" point.

The symptom of Fig. 4 was taken from a receiver which suffered the effect only on the ITV programmes, but at all settings of the fine tuning control. It was noticed, however, that the set appeared to be almost on the verge of instability and, indeed, instability could be promoted at high contrast settings with the downlead at the back of the set placed in a certain way.


The trouble was eventually traced to the ingress of moisture into the diplexer coupling the BBC

and ITV aerials to the common downlead. Replacement of the diplexer effected a complete cure.

Similar trouble has been observed due to old coaxial downlead which was probably installed on the set before one! Damp or water in the downlead not only incites instability but it seriously reduces the signal applied to the set and is a big cause of picture grain, especially on the ITV channels.
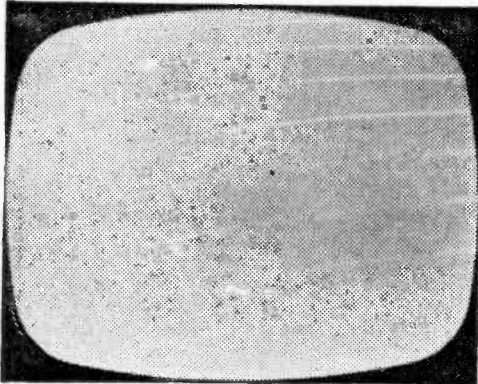
## AERIAL TROUBLE

One can be fairly certain that something is badly amiss with the aerial system if the symptom or picture is influenced by moving the downlead at



the back of the set. Change of impedance at the aerial, reflecting back into the downlead and causing instability or "ringing", as the symptom of Fig. 4 is sometimes called, can also be the result of a next door neighbour putting up a new aerial on

Fig. 6—A lingering spot of sufficient intensity can cause local discoloration of the screen phosphors. The text tells the main causes of this symptom.

a shared chimney stack. This impedance change arises from "proximity effects" and is the cause of more trouble than is realised these days when it is necessary to have so many aerials close together. It will not be tolerable so much on the new u.h.f. bands which are used for BBC-2.

On all receivers without flyback line blanking, flyback lines will be displayed when the raster is produced without a signal present. As the signal falls from video into the sync region the grid of the tube (relative to cathode) is pushed hard negative, thereby cutting off the beam current and the flyback lines. This is the normal action. If the brightness control is set too high, then, in spite of the picture signal going negative, screen illumination will still be present during the flyback period and the flyback lines will be seen, as shown in Fig. 5.

If a set which features flyback blanking shows the symptom, then there is something very wrong with the blanking circuit. This was, in fact, the trouble with the set from which Fig. 5 was photographed.

The circuit consists essentially of a "hold-off" resistor between the tube grid and the slider of the brightness control, a resistor-capacitor potential-divider across a part of the frame circuit and a

resistive and/or capacitive feed from the junction of the potential-divider to the tube grid.


The part of the frame circuit selected may be in the oscillator or amplifier. Some models have a tapping on the output transformer to take off a suitable blanking pulse. All that is necessary is to select a part of the frame circuit where the voltage pulses *negative* on the frame flyback, which then pushes the grid of the tube extra heavily negative (along with the signal as mentioned above) and makes totally sure that the flyback is suppressed.

If the symptom is present on models with a suppression circuit, the components in the tube grid circuit should be checked preferably by substitution, and the faulty one will soon be discovered. The symptom in excess on sets without a suppression circuit usually signifies that the tube is low emission and that an extra high setting of brightness is necessary to obtain a picture of viewable brightness.

However, another cause is the frame locking on hum instead of on the frame sync pulses. This can

Fig. 5—Flyback lines on a plain but modulated raster.

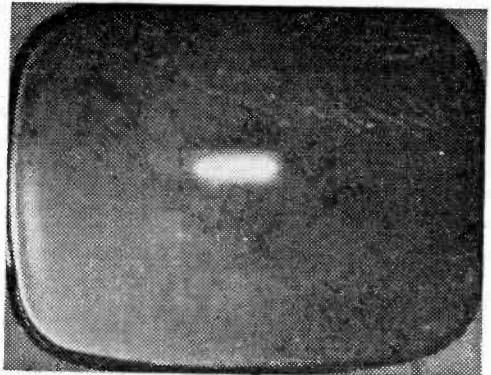happen due to heater/cathode leakage in one of the vision valves or sync or frame valves. In some receivers only a slight hum is sufficient to shift the frame lock from the sync pulses to the 50c/s ripple voltage. The picture may then divide into two, with a wide, black, horizontal line at the top or bottom of the screen.



## LINGERING SPOT

Readers are sometimes concerned about the bright spot of diminishing brightness which may develop in the centre of the screen when the set is switched off (Fig. 6). There is the possibility that the spot may be of sufficient intensity and duration to cause localised phosphor discoloration.

The symptom results because of the high charge retained by the e.h.t. filter capacitance, and because of the reducing emission of electrons from the cathode, even after switch-off. The electrons are thus accelerated in the normal way, and since by this time the timebases have ceased working a spot is produced.

Two main circuit arrangements are adopted to minimise the effect. An early idea was to arrange for the tube to be cut off for a while immediately following switch-off.

—continued on page 166

# PRINCIPLES AND PRACTICE OF COLOUR TELEVISION

## PART 7

CONTINUED FROM PAGE 109 OF THE DECEMBER ISSUE

BY G. J. KING

**L**AST month we saw how the chroma information of the televised scene is added to the mono information at the transmitter and how the combined information is then applied to the v.h.f. or u.h.f. carrier wave.

At the time of writing colour test transmissions are actually taking place on 625 lines. While it is impossible at this time to say exactly when a colour service will be established, the situation now is much clearer than it was a few months ago. Tests have been made to find out the type of system which is most suitable for use in these islands, having in mind programme interchange between European and American stations.

Whatever system is finally decided upon, the basic principles will be as expounded in this series of articles. There are, at present, three systems under review: the American NTSC, the French SECAM and a German version known originally as the Bruch 3 system, but now colloquially termed the PAL system, short for "phase alteration line system". We shall be looking more closely at the differences between these three systems next month.

### Compatibility

At this juncture it is necessary for us to see what happens to the combined chroma and mono signals when they arrive at the set end of the chain. The best way of looking at this first of all is to consider a colour television receiver working from an ordinary black-and-white television signal, of the kind that ordinary monochrome sets work from.

A domestic colour television system must be compatible. That means a colour receiver must be

capable of producing a picture in black-and-white from a mono transmission and, conversely, a mono set must be able to give a picture in black-and-white from a colour transmission.

All the systems proposed for domestic colour are compatible and they incorporate receiver circuits which are similar to those used in mono sets. Actually, about 75 per cent of a colour receiver consists of circuits which are virtually the same as those in a mono set. There is the tuner, the i.f. stages and the detector. The extra 25 per cent relates to circuits which are designed specifically for the colour signal.

Compatibility starts at the transmitter. Fig. 23 in Part 6 shows how a televised scene is analysed in terms of the three primary colours to create the Y' or luminance signal which is almost equal to the signal produced by a mono camera for a mono television system, as we have seen in past articles.

### Colour Signal to Mono Set

The Y' signal, it will be seen, is applied to the transmitter modulator along with the chroma information, and the sidebands of the latter are exploited at this time, the sub-carrier being suppressed (more about the sub-carrier and the carrying of the chroma information later).

Sidebands on their own "look" to a mono set as spurious signals which, as purposely arranged, do not interfere with the basic mono information. Thus, in a mono set the colour sidebands are bypassed to chassis in the detector circuit and only the Y' signal is permitted to pass. This is processed in exactly the same way as a true mono signal,

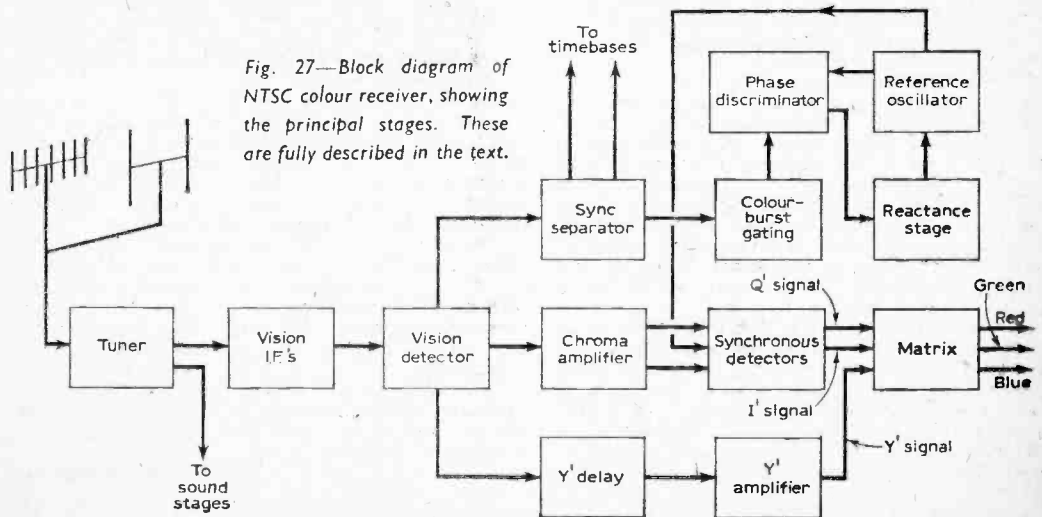


Fig. 27—Block diagram of NTSC colour receiver, showing the principal stages. These are fully described in the text.

thereby resulting in a black-and-white picture, even though the original signal carries information which is also capable of working a colour set.

Now let us investigate the happenings when a mono signal is fed into a colour set. Fig. 27 shows a block diagram of the principle elements of a colour receiver. The tuner, vision i.f. stages and the detector are common to both mono and chroma sets, and the sound signal is extracted either from the output of the tuner or from a common i.f. amplifier stage, depending upon the type of set. The receiver may be designed for 405-line, 625-line, or dual standard working, using a.m. or f.m. intercarrier sound in accordance with normal practice. The exact type of design at this juncture does not particularly interest us.

The demodulated vision signal from the detector is applied to a sync separator stage in the usual manner and to a Y' amplifier (equivalent to the mono video amplifier). The latter is fed through a delay network to ensure the correct "timing" of the mono and chroma signals at the picture tube, bearing in mind that the chroma signals have to pass through a greater number of circuits than the mono signal and are thus delayed more than the mono signal. The Y' delay compensates for this.

### Mono Signal to Colour Set

Now, a mono transmission is carried by such a receiver quite normally. Sync pulses are produced for the line and field timebases and the video from the detector is fed to the Y' amplifier just as it would be fed to the video amplifier in a mono set. The Y' or mono video output, instead of being applied direct to the cathode of the picture, as in the case of a mono set, is applied to a "matrix" stage.

This, in effect, adds the I' and Q' signals when colour is being received to produce the correct range of red, green and blue signals, in conjunction with the Y' signal, and when mono is being received it lets through the correct values of signals corresponding to the red, green and blue inputs of the colour tube so as to produce a display in monochrome without colour distortion.

Past articles have shown how a picture in monochrome can be derived from the three primary colours and displayed on the screen of a tricolour picture tube. Those readers who are still not sure of the principles of colour mixing, refer to Parts 1 and 2 of this series.

### Colour Signal to Colour Set

Now to see what happens when a colour signal is applied to a colour set. The Y' signal is fed through the receiver in the manner already described; but the sidebands of the chroma signals (I' and Q' signals) are not this time bypassed to chassis at the vision detector, but instead extracted and applied to a chroma amplifier (still referring to Fig. 27). This is really like a video amplifier, but is designed to handle the colour signals.

The I' and Q' sidebands are absolutely no use at all as they stand, since they have no carrier (this was suppressed at the transmitter). They cannot thus be detected in the usual manner. Before they can be processed the carrier has to be reinserted, and this is accomplished by a reference oscillator.

This has a nominal frequency the same as that of the suppressed subcarrier at the transmitter. The

signal is applied to a rather special synchronous detector in the receiver along with the signals from the chroma amplifier. In the detector, the I' and Q' sidebands are added to the synthetically-produced sub-carrier and, provided the phase of the reference oscillator signal is within a few degrees of the phase of the original sub-carrier signal, detected I' and Q' signals appear at the output of the stage.

In practice, there are two synchronous detectors, one for the I' signals and the other for the Q' signals (only a single block is shown in Fig. 27). In order to ensure that the phase of the reference signal matches that of the original sub-carrier and, equally as important, that the phase of the colour sidebands relative to the reference frequency is maintained, the reference oscillator signal is "locked" to the colour burst signals which are carried on the back porch to the line sync signals (see Fig. 24, Part 6).

In effect, the colour burst signals control the reference oscillator in rather the same way as the sync pulses control the line and field timebases. However, the colour control is extremely critical from the colour rendering aspect. Deviation of phase will impair the colours and modify their hues.

### Hue Control

While the line and field timebases feature hold controls, the reference oscillator has a hue control. This is a preset which is adjusted on installation of the set for the best colouring. Sometimes a user's hue control is fitted, and then the viewer himself is faced with the problem of its adjustment. This is best made by adjusting for the most natural "flesh" tones, but the difficulty is in knowing whether a particular face should be pink, brown or white!

The correct relative phase is maintained once the hue control has established the setting initially by the colour burst signals, as intimated. These signals are picked out from the sync pulses at the output of the sync separator and are then fed through a colour gating circuit. This deletes all traces of sync signal and leaves only the colour bursts.

The colour burst signals are fed to a phase discriminator circuit, which is akin to the same circuit used in flywheel sync circuits and in some f.m. receivers (also for automatic frequency correction), to which is also fed a sample of the reference oscillator signal.

Now, when the reference oscillator signal and the colour burst signals are in phase (or within the correct phase relationship) the output from the phase discriminator is zero (or a nominal pre-arranged value). Should the phase of the reference signal tend to alter from that of the colour burst signals, a positive or negative voltage, depending upon which way the relative phase alters (i.e., plus or minus), is produced at the output of the phase discriminator.


### Reactance Control

The frequency of the reference oscillator is set initially by the normal LC constants of the tuned circuit in the conventional manner. However, across the tuned circuits is connected a "reactance valve". This is a triode or pentode valve arranged basically as shown in Fig. 28. From the aspect of the oscillator signal voltage applied as shown, the circuit "looks" like a reactance in the capacitive

# **FACTS! FACTS! FACTS!**

*... the up-to-the minute*

*data book for all enthusiasts -*

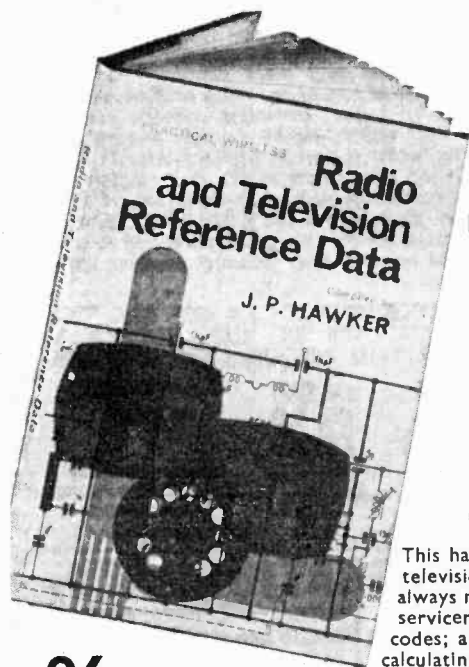

**"PRACTICAL WIRELESS"**

# **RADIO and TELEVISION REFERENCE DATA**

**Compiled by J. P. Hawker**

This handy book provides the practical reference data that radio and television servicemen, radio constructors, enthusiasts and amateurs always need. It has been compiled with the day-to-day requirements of servicemen particularly in mind. Contents include: full details of colour codes; a comprehensive collection of practical, everyday formulae for calculating the values of biasing components, potential dividers, etc. aerial dimensions; a quick frequency-wavelength conversion table; full lists of radio and television broadcasting stations and frequencies; common symbols and abbreviations; notes on Amateur radio and a list of call-sign prefixes; communication receiver I.F.s; mathematical data including logarithm tables; wire and cable data; battery equivalents; and a full and up-to-date listing of valve, transistor and cathode-ray tube pin connections, bases, ratings and equivalents, including selected CV types.

A worthwhile reference source for all who are in any way concerned with installing, maintaining, constructing, operating or servicing radio equipment.

**96 pages**  
of factual tabulated data ... should be on the workbench of every serious constructor and service man

**Make sure of your copy NOW - only 10s 6d**

**FULLY COVERS**

- Colour Codes : Formulae : Aerials
- Frequency and Wavelength
- Broadcasting Allocations and Station Frequencies
- Television Standards
- Symbols : Abbreviations
- Amateur Radio : Useful Constants
- Amateur Radio Prefixes
- I.F. List for Communications Receivers
- Mathematical Data
- Wire and Cable Data
- Valve, Picture-Tube, Battery and Transistor Data

**ORDER HERE**

Please send me by return .....copy copies of the new

**"P.W. RADIO AND TELEVISION REFERENCE DATA" 10s. 6d. (11s. 6d. by post)**

Name \_\_\_\_\_

Address \_\_\_\_\_

\_\_\_\_\_

**10s. 6d. FROM ALL BOOK SELLERS**

... or in case of difficulty, use this handy order form.

Simply complete this order and post with cheque/postal order for 11s. 6d. per copy to GEORGE NEWNES LTD., Tower House, Southampton Street, London, W.C.2.

PT/Jan/64.

**ONLY 10s 6d**

**NEWNES**



# LAWSON

## DIRECT REPLACEMENT TELEVISION TUBES



LAWSON TUBE WITH NEW SILVER ACTIVATED SCREEN AND "MICRO FINE" ALUMINISED

12 MONTHS' FULL REPLACEMENT GUARANTEE

### DESIGNED FOR PERFORMANCE

The Modern Lawson television tubes are specially designed to give all types of television set very much improved performance. Their new silver activated screens are much brighter with better contrast, exclusive "microfine" controlled thickness aluminising gives 50% more light output (superb daylight viewing). New small anode aperture electron guns by Mullard, Mazda, G.E.C., Brimar, E.E., Cossor, etc., ensure needle sharp definition and focus, and silicon vacuum pumping plus depth formed cathodes give very long life. Each tube is 100% BRAND NEW (glass excepted), and Lawson are the only tubes guaranteed to be exact replacement for the original tube, ensuring complete accuracy and efficiency.


FROM THE LARGEST STOCKS OF ALL TYPES OF C.R.T.s IN BRITAIN WE CAN SUPPLY THE EXACT TUBE YOU REQUIRE BY RETURN.

- 12" — £4.10.0
- 14" — £5. 5.0
- 15" - 17" — £5.15.0
- 19" - 21" — £7.10.0

C.O.D. 6r C.W.O.

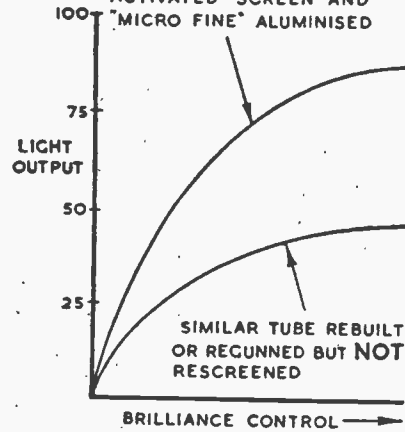**10/-**

Gladly refunded if you wish to return your old tube (excepting 12")



EXPRESS PASSENGER TRAIN SERVICE  
Our service is countrywide and whether you live in the Outer Hebrides, or at No. 10, we can guarantee the fastest and finest CRT service in Great Britain.

Full fitting instructions with every tube.

**LAWSON TUBES LTD.** Tel. 2100  
2 PEACHFIELD CLOSE, MALVERN WELLS,  
WORCESTERSHIRE

Delivered Free in London Postal Districts  
CARR. and INS. 7/6

# BENTLEY ACOUSTIC CORPORATION LTD.

EXPRESS SERVICE!!!  
C.O.D. ORDERS RECEIVED BY 3.30 P.M. EITHER BY LETTER, PHONE OR WIRE, DESPATCHED SAME AFTERNOON

THE NEW VALVE SPECIALISTS  
38 CHALCOT RD., LONDON, N.W.1  
Nearest tube Chalk Farm All goods advertised are in stock Primrose 9090

MULLARD BY100 MIDGET SILICON RECTIFIERS  
Output 250v. at 1 amp.  
No larger than a shirt button! 7/6 each.

0A2	4/8	6BR5	9/3	7V7	5/-	30FL12	11/-	DF66	15/-	ECC85	6/3	EL36	1/9	HVR2	3/9	PEN45DD	U10	9/-	UCL83	8/6	0A73	3/-	
0B2	6/-	6BW6	6/9	7Y4	5/6	30L16	8/9	DF96	5/9	ECC88	10/-	EL38	12/-	HVR2A	4/9	PEN46	4/3	U12-12	1/16	UFL4	6/6	0A79	3/6
0Z4GT	4/8	6BW7	5/-	9BW6	9/6	30P4	12/3	DF37	10/-	ECC91	3/-	EL41	7/3	KT33C	4/9	PEN33	9/6	U14	8/9	UFL42	5/6	0A51	3/6
1C5	6/3	6C9	10/9	10C1	9/3	30P12	7/6	DH101	25/-	ECC189	10/6	EL42	7/6	N736	29/1	PEN38	U19	48/6	UF90	6/6	0C19	25/-	
1D6	9/9	6CD6G	15/-	10C2	10/3	30P19	12/3	DH107	16/11	ECCF80	6/3	EL43	8/3	KT41	7/8	PEN33	11/6	U22	6/9	UF85	7/6	0C22	25/-
1L4	2/3	6CH6	5/-	10F1	10/-	30PL1	9/-	DK92	6/9	ECCF82	6/9	EL44	4/9	KT61	10/9	PEN38	8/6	U35	5/9	UF89	6/6	0C25	12/6
1B5	4/-	6CW4	24/-	10LD11	9/-	30PL13	9/6	DK96	8/3	ECCF86	11/6	EL44	4/9	KT68	4/9	PEN38	6/9	U37	7/6	UL44	23/3	0C35	18/6
1B6	5/6	6D3	9/8	10P13	8/3	30PL14	12/6	DL68	15/-	ECH21	10/6	EL45	7/-	KT68	4/9	PEN38	10/6	U38	7/6	UL46	8/9	0C36	21/6
1L4	2/3	6F1	9/8	10P14	11/6	3515GT	6/9	DL86	5/9	ECH42	7/9	EL41	2/6	KT78	28/-	PEN38	5/3	U33	13/6	UL46	8/9	0C36	21/6
2D21	5/6	6F13	4/9	12AC6	8/6	35W4	4/9	DM70	5/6	ECH81	8/9	EL86	5/6	KT78	28/-	PEN38	5/3	U35	15/6	UL84	6/6	0C41	8/6
3A4	3/9	6F23	9/9	12AD6	8/6	35Z4	4/9	DM71	9/9	ECH84	9/6	EL820	10/4	KTW63	5/6	PEN38	6/6	U37	25/3	UM4	15/2	0C44	8/6
3A5	6/9	6F25	4/9	12AE6	8/6	35Z4GT	4/9	DM78	7/9	ECL80	6/6	EL820	13/6	MHLD12	6/6	PEN38	6/6	U35	25/3	UM34	16/10	0C48	9/6
3AU6GT	7/6	6J7G	4/8	12AH7	4/8	35Z5GT	5/9	EY87	24/-	ECL80	6/6	EL820	13/6	MHLD12	6/6	PEN38	6/6	U35	25/3	UM34	16/10	0C48	9/6
3S4	4/8	6K7G	7/6	12A18	9/9	35C5	6/8	E90F	24/-	ECL82	7/-	EL820	20/6	MKT14	17/6	PY31	6/8	U19	10/9	UM80	8/6	0C68	25/6
3V4	5/6	6K9G	3/9	12AT6	4/8	35L6GT	6/8	E98CC	10/-	ECL82	7/-	EL820	20/6	MKT14	17/6	PY31	6/8	U19	10/9	UM80	8/6	0C68	25/6
5H4GY	9/9	6K25	12/-	12AV6	6/8	53KU	14/6	E180F	19/6	ECL86	8/9	EM34	5/9	N37	28/6	PY80	5/3	U29	18/6	UY1N	11/8	0C71	3/6
5U4G	4/8	6L1	10/-	12AV6	6/8	72	6/8	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
5V4G	7/6	6L6G	6/6	12BA6	8/9	85A2	3/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
5Y3GT	4/8	6L7GT	4/8	12BE6	4/8	90AV	6/8	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
5Z3	7/6	6L18	10/-	12BH7	6/9	90AV	6/8	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
5Z4G	7/6	6LD20	5/6	12K5	10/-	90C1	16/-	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6A7	8/9	6P28	11/8	19A05	7/8	90CC	42/-	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6A8	5/6	6Q7G	4/8	19H1	6/6	90CV	42/-	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6AC7	3/6	6RTG	5/9	20D1	10/-	136BT	34/11	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6AG7	6/6	6V4GT	8/8	20P2	11/6	150B2	19/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6AQ5	5/9	6V6GT	8/8	20P1	12/6	186A	12/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6AT6	3/9	6X4	3/9	20P1	12/6	186A	12/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6AV6	5/9	6X0L2	3/6	20T4	13/6	AC8PEN	4/8	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6RA6	4/8	7B6	12/6	20P5	13/6	AZ1	6/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6RE6	4/8	7B7	7/6	20T4	13/6	AZ1	6/6	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G	13/8	7C5	10/-	25Y6G	7/9	B36	4/4	E180F	19/6	ECL86	8/9	EM34	5/9	N78	28/6	PY80	5/3	U30	12/6	UY21	8/6	0C72	3/6
6R6G																							

sense. That is, the oscillator voltage lags  $90^\circ$  on the current.

If Fig. 28 is considered first without C and R, the oscillatory current  $i$  flowing in the valve will be in phase with the oscillatory voltage  $e$ . In other words the circuit is purely resistive.

The presence of C and R alters this condition, however, since by tapping of a portion of  $e$  and applying this to the grid, C gives a phase advance of almost  $90^\circ$ .

Owing to the amplification effect of the valve, the anode current produced by this out-of-phase voltage is greater than  $i$  and the valve passes an a.c. component  $90^\circ$  ahead of the applied voltage  $e$ . This is equivalent to a capacitive shunt across the oscillator tuned circuit.

The value of this virtual capacitance depends upon the grid bias applied to the valve, and as the bias is altered so the capacitance value changes. This means, therefore, that the frequency of the reference oscillator can be varied simply by altering the grid bias on the reactance valve. This is where the hue control may be connected. As this control is adjusted so the grid bias is varied and hence the phase of the reference signal over a few degrees.

The oscillator is phase-locked and maintained in correct phase over long periods by the use of the voltage at the output of the phase discriminator as a control bias. Should the phase of the oscillator tend to drift away from that originally established by the hue control, correction is accomplished by

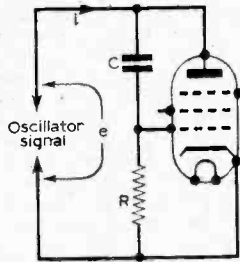


Fig. 28—Basic circuit of reactance valve, arranged to reflect capacitive reactance.

the capacitance of the reactance valve altering in a manner to compensate due to the output of the discriminator rising in a positive or negative direction.

### Obtaining the Colour Signals

When the synchronous detectors receive a reference signal of correct phase, relative to the  $I'$  and  $Q'$  sidebands, demodulated  $I'$  and  $Q'$  signals (corresponding to the red- and blue-difference colour signals respectively) are produced at the output of the detectors. Thus, we have the  $Y'$  signal and the colour-difference signals applied to the matrix.

In this sense the matrix subtracts the  $Y'$  signal from the red- and blue-difference signals, leaving just the red and blue signals. The green signal is derived, in effect, by the red and blue signals being subtracted from the  $Y'$  signal.

The end result is that red, green and blue signals are produced which operate the tricolour display device in exactly the same way as if the three colour signals were carried over separate and isolated circuits, as in closed circuit television.

In this article we have seen how a mono set responds to a colour transmission, how a colour set responds to a mono transmission and how a colour set gives a correct colour display due to the modulation of  $I'$  and  $Q'$  signals, in addition to the mono luminance signal, upon the common vision carrier signal.

We must now see how it is possible to transmit the colour information without causing interference to the mono signal. The energy of a mono television signal is concentrated in small "packets" of energy instead of being spread evenly over the video bandwidth. Each packet of signal energy is separated from its neighbour by the line scanning frequency (10,125c/s 405 lines and 15,625c/s 625 lines), and at each packet there are energy components at multiples of the field frequency.

The energy is greatest at line frequency and the energy output falls fairly quickly at field frequency

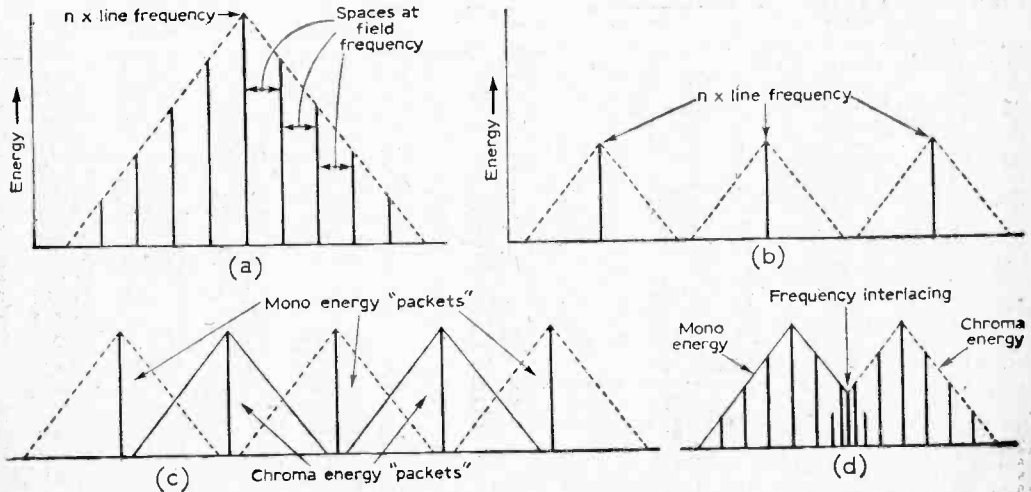


Fig. 29—Mono signals produce "packets" of signal energy over the video spectrum at line frequency intervals with components at field frequency as shown at (a) and (b). Similar "packets" of energy are produced by the chroma signals and by correct selection of the sub-carrier frequency these can be made to fall between the packets of mono energy as shown at (c). Frequency interlacing of the energy components then occurs as shown at (d).

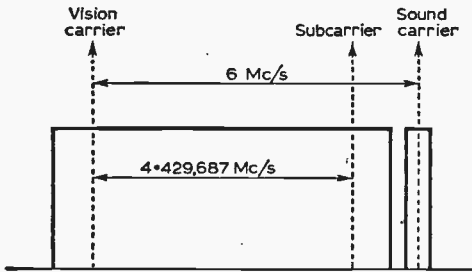


Fig. 30—Showing the position of the sub-carrier in the video passband.

spacings away from 1, 2, 3, 4, 5 . . . n times the line frequency. The idea is shown in Fig. 29 (a), while at (b) it is shown that very little energy due to the mono signal exists between the line frequency intervals.

The chroma signals also produce packets of energy of a similar kind, also spaced at line-frequency intervals. The position of the chroma energy packets relative to those of the mono signals is governed by the frequency of the sub-carrier upon which the 'I' and 'Q' signals are first modulated at the transmitter.

### Sub-Carrier Frequency

The sub-carrier frequency is towards the top end of the video spectrum (about 4.5Mc/s in the case of 625 lines). However, if the exact frequency is made an odd multiple of half the line frequency, the

packets of chroma energy will fall exactly between the packets of mono energy, as shown in Fig. 29(c). Moreover, the energy components will interlace, as shown in Fig. 29(d). On the 625-line system this effect is achieved when the sub-carrier frequency is exactly 4.429,687Mc/s, as obtained by multiplying one-half of the line frequency by 567.

Other factors which include the sub-carrier frequency are dot pattern, which occurs if the frequency is too low and interference between the sound carrier and the sub-carrier. The latter is minimised by arranging for the sub-carrier to interlace with the sound carrier. We thus have a somewhat complex set of conditions to satisfy.

Fig. 30 shows how the sound, vision and sub-carrier signals are spaced relative to each other. The sub-carrier is usually made the "master frequency" from which the line and frame frequencies are derived, the master being held to an accuracy in the order of 0.0003 per cent.

On mono systems the master frequency is that of the power supply. That is, the field is locked to the power supply and from there the line frequency is obtained. On colour systems this is not possible, and as a consequence it is not possible to lock the field frequency to the power frequency. This results in so-called asynchronous working which, on some of the older type of receiver, produces slowly rolling hum bars due to residual hum in the vision stages. When the hum is locked to frame, of course, the hum bar is still present, but since it is stationary is not usually discernible.


PART 8 APPEARS NEXT MONTH

## Elusive Picture Faults

—continued from page 160

The latest, and best, idea is for the tube itself to discharge the e.h.t. capacitance on switch-off due to it passing a very high beam current. This is arranged either by coupling the tube grid back to the mains supply circuit (to the

Fig. 7—In this circuit a VDR is used to hold the tube grid positive with respect to cathode on switch-off and thus discharge the e.h.t. filter capacitance due to excessive beam current.

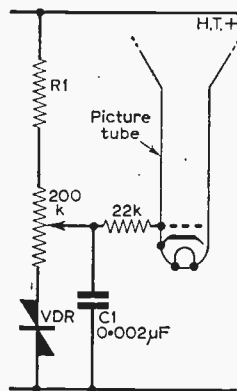

on/off switch), via a current limiting resistor, or by some other method causing the grid to go highly negative with respect to the cathode immediately on switch-off. With this technique the line and frame scans are in the process of collapsing when the beam is discharging the e.h.t. filter capacitor, so the illumination is spread over a greater area of screen and localised burning is avoided.

Most modern receivers use this idea, and a prerequisite is that the first anode potential on the tube

remains at a high value during the whole of the discharge period. This is necessary, of course, to maintain a high value beam current for the discharging action. A collapse of first anode voltage would reduce the beam density, the opposite to the requirements.

Thus, on sets which have suddenly exhibited the "lingering spot" symptom, attention should be given to the filter capacitor on the tube first anode, for it is this which charges and holds the anode at the required potential during the critical period. If this goes open-circuit or low in value, the discharge will not be complete at the final anode and the spot may well linger.


On earlier models, where the tube is pushed for a while into beam cut-off, trouble in the video amplifier stage or brightness control circuits can prevent the spot from being suppressed.

### NEW CIRCUIT

A circuit by Mullard Limited to cause a rapid discharge through the beam current is shown in Fig. 7. Here a voltage-dependent resistor (VDR) is connected between the bottom of the brightness control and chassis. The action is as follows: capacitor C1 charges through R1, and the brightness control from the h.t. line. On switch-off the voltage across the VDR decreases and its resistive value increases, thereby preventing C1 charge from being quickly exhausted and holding the tube grid positive with respect to the cathode for the time required for the beam-discharge action. ■

A MONTHLY FEATURE  
FOR DX ENTHUSIASTS

by Charles Rafarel

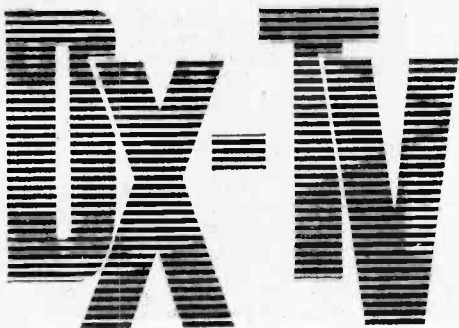

**T**HE choice of a receiver for DX TV is, of course, of the greatest importance. It might seem that the obvious plan would be to buy one of the new 625-line receivers now on sale, but don't do it!

Firstly, only certain models can be switched to 625 lines with the Band I/III tuner in operation, the rest are only operational on 625 lines in the u.h.f. position.

The second snag is the one already discussed; that the new u.h.f. system here is designed for a sound-to-vision separation of 6Mc/s, whereas our Continental friends mainly use 5.5Mc/s separation, so we will not be able to get sound and picture together even if we can use the 625 model for DX work.

In the relatively small area of the British Isles we are cluttered up with over 20 TV stations in Bands I and III, with powers of 100kW or over, apart from the numerous low power relays.

Our worst enemy for DX reception, in fact, is not going to be atmospheric conditions but local station interference.

The Continental channels fortunately lie between the British ones, and therefore provided our receivers are selective enough we should at least be able to separate them from our own.

The new 625-line sets have a vision bandwidth of approximately 5Mc/s, whereas the old 405-line set is only 3Mc/s, so an old 405 set is obviously preferable despite a slight loss of picture quality. I have tried a 625-line export model and have discarded it as useless for channels adjacent to the local channels.

There are five requirements for success.

(1) Continuous (incremental) tuning over Bands I and III to tune Continental channels lying between British ones. The spread of a fine tuner in a turret is about 1Mc/s only and continuous resetting of turret slugs is inconvenient and accurate calibration is out of the question.

(2) We want a set which can be run reasonably efficiently on 625 and 819 lines without too much loss of scan and e.h.t. Our 405-line set is likely to have a harmonic tuned line output transformer and this can be troublesome with some makes.

(3) It should have flywheel sync for weak signals.

(4) It should be reasonably easy to arrange switching for negative going pictures.

(5) It should have good overall vision gain with at least three vision i.f. stages.

In connection with (5) I suggest the "best buy" is a second hand Bush 14in. of the TV53, 62 or 63 range or the TV66 17in. model. In fact these types

comply very well with our requirements and can often be purchased very reasonably.

Apart from arranging an inverting switch for the video diode and arranging for some adjustment of video amplifier valve bias for negative pictures, they will work quite well without further alteration, and I will be pleased to give details for switching for those who require them.

What are we going to do about sound? A separate sound receiver is the answer here, as this will overcome problems about the different sound-to-vision separations.

For a.m. sound from France, Belgium and Luxembourg any old set will do, provided the sound section is operative and it has incremental tuning. For f.m. sound we must employ other methods.

My solution is to use a continuous Band I/III tuner feeding into the i.f. stages of a broadcast f.m. set. Watch the i.f. frequencies however.

## DX NEWS

Now for a few notes for established DX viewers. I hope you all profited by the wonderful tropospheric opening of October 10-12th. Here in Poole, 13 new ones were caught, including Tele Luxembourg, also received by at least two other viewers. Yes, it can be done on u.h.f. too, with London (Ch33) Paris (Ch22) and three West Germans picked up here in Poole.

Further East, scores of over ten West Germans have been recorded and the experts say that RAI/UHF Italy may well be possible, so if you are not yet active on u.h.f. get busy. It is worth it!


H. A. Ballard of Hastings writes to say that so far as he is concerned, our concluding remark (3) in the October issue, concerning DX u.h.f., has proved to be true. He writes:

*"On August 15th I was able to lock three faint Continental stations—all different programmes—but was unable to identify them, although one was obviously Dutch. These were between channels 23 and 33. On October 12th I was more fortunate and secured the enclosed photos which may help in station location."*

These photos showed that Mr. Ballard's station was Lopik, N.T.S., Holland on channel 27. Details are: 625 lines, negative modulation with f.m. sound, 250kW e.r.p. vision, 50kW e.r.p. sound, horizontal polarisation, omni-directional propagation, site at sea level but mast 1,170 feet high.

Mr. Ballard says that his receiver started life as a 14in. Bush Model TV53 but now bears little resemblance to the original as it has been progressively rebuilt over the past two years as circuit improvements have been introduced.

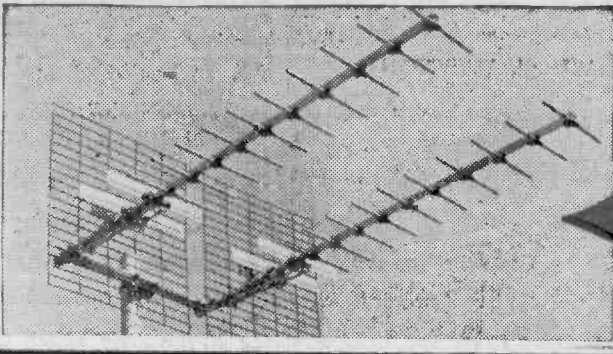Unfortunately he did not give sufficient information to identify his stations between channels 23 and 33, but strong possibilities are Aachen, West Germany, on channel 24; Koblenz, West Germany, on channel 31; Wuppertal on channel 22.



NI  
THOUG

AER

**H**IGH definition television was put out on a regular transmission basis way back in 1936. Then came the war and a pause in its development. We are now in the second decade of the post-war television era. Television started in the very high frequency (v.h.f.) bands first in Band 1 on channel 1, then on channels 2, 3, 4 and 5, and in 1954 in Band III on channels 8, 9, 10, 11, 12 and 13. So it is today.

Tomorrow television will have graduated into the ultra high frequency (u.h.f.) bands (Bands IV and V) to give us BBC2, to be followed later by ITA2. Soon the test transmissions from the BBC's London u.h.f. station will be replaced by "programme test transmissions", to be followed later (April) by regular transmissions. The test programmes will be in addition to the BBC2 test card and will be advertised in the *Radio Times*.

Channel grouping is to be adopted for u.h.f. television in Great Britain. Each transmitter area is to be allotted a group of 11 consecutive channels and the London area has already been allotted the group comprising Channels 23 to 33. The immediate need, then, is for a revision of thoughts on aerial problems.

#### Unsafe

Some Band III aerials have been on chimney stacks and fully exposed to all weathers for nearly 10 years and some Band I arrays have been up longer than this. A country tour will reveal many old aerials in various conditions of disrepair and quite a few will be seen to be distinctly unsafe with elements missing and the masts leaning at curious angles, especially in exposed places near the coast.

The time will shortly come when more chimney adornments will be needed to get BBC2 and this aerial will be somewhat more critical both in choice and erection than the earlier v.h.f. aerials if good, consistent pictures are to be expected.

#### Local Booster

Some of the old, worn-out v.h.f. aerials are far more complicated than they need be for present-day reception, for it is probable that when they were erected, reliance had to be placed on a distant station, while of recent years (or months) a local, or a "booster" station may have changed the district from "fringe" to "service" area.

This could mean that the old, complicated aerial is working inefficiently not only off direction but also on the wrong channel for the local station. When a booster comes to town many aerials are left to work in that way, the signal field being so strong

that the picture even on the wrong aerial is far better than what it was from the distant station before the booster arrived.

#### Set Factor

There is also the factor of the set itself. The aerial may have been erected high and in complicated configuration to do full justice to a relatively insensitive receiver of past ages and is left in use still for the new set which needs considerably less signal than the old one to give a good picture.

Modern sets are much more sensitive on the v.h.f. channels than their older counterparts, meaning that less elaborate aerials than of earlier days often do a far better job than is generally realised.

#### Signal/Noise Ratio


The lowest limit of signal pick-up is reached when grain (due to valve and circuit "noise") makes the picture difficult to view. The only way to reduce the grain is to improve the signal/noise ratio of the installation either by making the set less "noisy" or the aerial deliver more signal. Modern sets are less "noisy" than old ones, meaning that a picture of given grain can be maintained on a new set when the signal is some two times below that necessary for the same amount of grain on the old set.

Although an aerial may supply sufficient signal to give a reasonable signal/noise ratio, a more elaborate aerial may, nevertheless, be required to get rid of interference or ghosts due to the pick-up of reflected signals. The picture in Fig. 1 suffers



Fig. 1—A picture of poor signal/noise ratio (approximately 18dB) with a negative ghost towards the left-hand side of the main image.

# NEW TECHNIQUES ON AERIALS

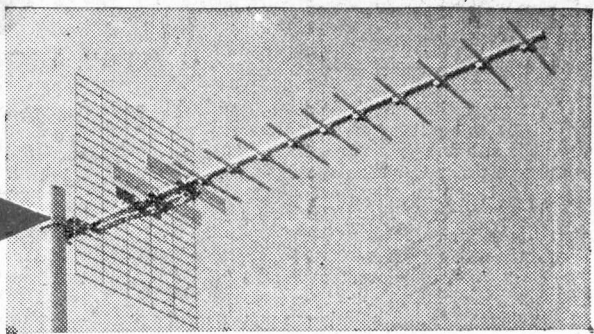

By J. Longrise

both from excessive grain due to a poor signal/noise ratio and from slight ghosting (seen vaguely to the right-hand side of the main image).

If the interfering signal (or reflected signal) arrives some 50 deg. or more off the bearing of the main signal an aerial with reasonable "directivity" can be orientated so that the maximum ratio of response of the wanted to unwanted signal can be achieved. A directional aerial requires a reflector and a number of directors in addition to the dipole; the greater the directivity the greater the number of elements required.

If a directional aerial is needed in a fairly high signal field area to reduce interference or ghosts, an attenuator may be necessary in the coaxial downlead to cut down the strength of the main signal, for directivity leads to extra aerial gain and too great a signal applied to the set may cause overloading, giving the symptoms of sound-on-vision and vision-on-sound.

Owing to the higher frequencies, signals in Bands IV and V are not quite so obliging as their v.h.f. counterparts, since they have trouble in penetrating massive objects and in bending. This means that the u.h.f. signals will require relatively complicated aerials, while the v.h.f. signals from a co-sited station may make do quite well with a simple array on the roof or even indoors.

To reduce interaction between a rash of aerials on a common chimney stack, the u.h.f. aerial should, if possible, be mounted in isolation, for this will be the most critical array of the group.

## Simplified v.h.f. Aerials

At the time when the u.h.f. aerial is erected, however, attention should definitely be directed to the possibility of simplifying the v.h.f. aerials and the best way of doing that is by bringing them indoors! Having in mind the thoughts of the earlier part of this article it will probably be discovered that in many areas (especially with new sets) attic aerials will work quite well, leaving clear chimney space for the u.h.f. aerial.

Another angle on this—when a shared chimney stack is involved—is to share the v.h.f. aerials with the next-door neighbour. This, at least, will mean that only one set of v.h.f. aerials will adorn the roof. A small dual-band amplifier and a star network (Fig. 2) represent an inexpensive solution to the problem.

Unfortunately it will not be quite such a simple matter to share the u.h.f. aerial, since the losses

are much higher and so far an inexpensive u.h.f. amplifier is not available. The amplifier used should be of the low-noise variety, for the sharing process should enhance, rather than detract from, the signal/noise performance of the system.

One of the new low-noise transistor amplifiers could, in fact, be used close to the set if necessary so as to raise the level of the signals from an indoor v.h.f. aerial system. It may also be a good idea to try one of the recently developed set-top aerials, for it may well be found that up to about 20 miles from a primary station nothing more elaborate is required for good pictures.

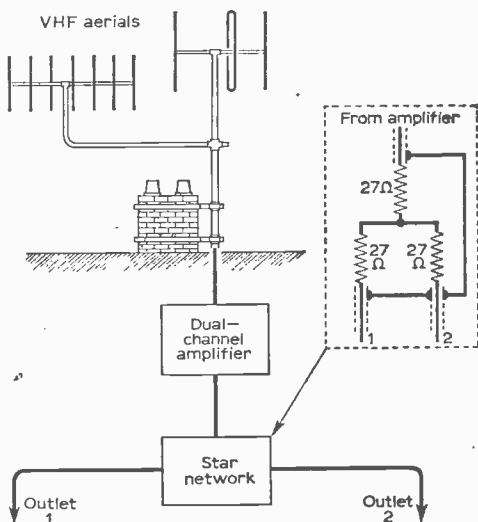


Fig. 2—To eliminate one set of v.h.f. aerials, the receivers of the adjacent neighbours are fed from a common aerial system via a dual-band amplifier and star network. The resistors of the "star" should be non-inductive, carbon type.

## Set-top Aerials

Some set-top aerials are also designed for reception of the u.h.f. signals, but results on this band cannot be predicted with any certainty as much will depend upon the local signal field, height of house above sea level, screening over the signal path and local proximity effects such as metal pipes, electrical wiring and any other large (particularly metal) objects.



Moreover, the signal field on Bands IV and V will usually be less than that on the v.h.f. bands and the u.h.f. sensitivity of dual-standard sets is some two times less than the v.h.f. sensitivity. The signal/noise ratio may thus suffer slightly towards the u.h.f. fringe. At this stage it should also be noted that the u.h.f. signals are horizontally polarised but that over the transmission path, the wavefront may twist and end up almost as vertical polarisation at the receiving site.

Fortunately, u.h.f. aerials are considerably scaled-down versions of their lower frequency partners, making it possible to employ more elements per array than with v.h.f. aerials. The u.h.f. dipole is only about 10in. long, with the reflector elements (or mesh) about 5% longer (or square) and the directors about 5% progressively shorter, depending upon exact design and channel. It is not intended here to delve into design considerations as these have been given in the past and will be published in various forms in future issues of this journal.

There is a limit economically to the increase in gain which can be obtained simply by adding directors to a u.h.f. aerial, but owing to the small physical sizes involved there is no great difficulty in stacking arrays and making them co-linear.

One of the heading pictures shows two u.h.f. aerials mounted side by side to form a co-linear configuration. While this arrangement does not double the gain of a single array, also shown in the heading, it does improve the directivity considerably and provide two or three extra decibels of u.h.f. signal, which can most certainly be very important where one is fighting to get the last dB on the edge of the fringe or in a difficult reception area.

Folded dipoles are used for matching and in the Belling and Lec arrays in the photographs, the dipoles are formed by the cutting of slots in a piece of suitable metal (not to be confused with a slot

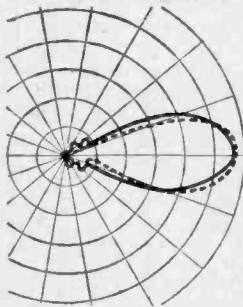


Fig. 3—Response polar diagram of Yagi u.h.f. aerial with the coaxial feeder connected direct to the dipole. The broken line curve reveals how the polar diagram is changed by the use of a "balun". The use of a "balun" also simplifies the positioning of the feeder by the aerial erector.

aerial). Various artifices are adopted to balance the aerial against unbalanced coaxial feeder. This is rather important to avoid undesirable "feeder effects" which occur, as shown in Fig. 3, when coaxial cable is connected direct to a dipole which is arranged for horizontal polarisation. The "unbalance to balance" device is called "balun" for short.

The losses in the coaxial feeder downlead are also about four times greater at, say, 800Mc/s (Band V) than what they are at 50Mc/s (Band I). It is of vital importance, therefore, that good-quality, low-loss coaxial cable be used to connect the u.h.f. aerial to the set and this, as with v.h.f., applies particularly towards the fringe of the station.

### Choice of u.h.f. Aerial

While it is impossible to be specific regarding the type of u.h.f. aerial required at various distances from the station, a general guide is possible based on normal reception conditions. Abnormal conditions arising, for instance, from local screening, rising ground along the signal path, proximity effects and so on may well severely distort the guide.

It is assumed that all aerials considered below possess an efficient reflector system, a folded dipole and a balun arrangement. Thus seven directors should give good results within a radius of about 15 miles from the station, 11 directors about 20 miles, 16 directors (on a single "in-line" Yagi array) about 25 miles. Stacked and co-linear arrays will be necessary in certain cases around the 20-25 mile mark and such arrays with high directivity will be essential to eliminate ghosting due to multipath interference. Fortunately, attenuation of the ghost signal is greater than experienced at v.h.f.

Other points to remember are that car ignition and electrical interference is less troublesome at u.h.f. than at v.h.f. and that u.h.f. aerials have a natural embracement of about 11 channels (this being necessary, anyway, to cover the 11 channels of a station group).

Also the signal field falls rapidly at u.h.f. away from the "radio horizon", thereby considerably curtailing the "fringe" area. On Band I, for instance, the fringe may spread out some 20 miles from the radio horizon, while on Band V the signal field may collapse almost to zero at about two miles away from the radio horizon. It is for this reason, of course, that several times more u.h.f. stations are required to cover the whole of the country than v.h.f. stations.

Now is the time, then, to start investigating ways of reducing the complexity of v.h.f. aerials—preferably by taking them off the chimney—so as to make room for the more demanding u.h.f. aerial. It is obviously impossible to keep on adding to the roof-top ironmongery!

## HELP FOR HOME BUYERS

When you are buying or selling property it is vitally important to know where you stand as far as the law is concerned. Ignorance or carelessness might cost you hundreds of pounds. There's sure to be a big welcome, then, for the new FREE LEGAL ADVICE SERVICE just announced by *Newnes Property Advertiser and Holiday Guide*. Every week, from now on, this paper will carry questions and answers on such topics as mortgages, insurance, surveying and general legal points. In addition any reader may have his own particular questions answered by a panel of experts simply by filling in a Query Coupon on the Legal Advice Page. *Newnes Property Advertiser and Holiday Guide*, which contains details of thousands of houses, flats, shops, business and holiday addresses, is on sale every Friday, price 4d.

# Using the BY100 silicon diode in Television Receivers

By K. Berry

THE BY100 silicon diode is primarily intended for use as a mains rectifier in television receivers and may be used to replace both metal rectifiers and valve rectifiers with a considerable saving in cost and greatly increased life.

When the BY100 is used in an a.c.-d.c. receiver to replace a thermionic rectifier (which has poor emission but whose heater is intact) it is convenient to leave the original valve in the receiver, using it as a "dropping resistor" for the heater chain. If, however, the rectifier heater has burnt out, then a suitable resistor must be added to complete the heater "chain" and preserve the correct current in the chain. This resistor should be mounted in a position where it will not overheat other components and will receive a reasonable air circulation. A list of resistors required to replace specific rectifiers is given in Table I.

In addition to looking after the heater chain it is necessary to make some provision for reducing the voltage applied to the rectifier, since the voltage drop across the BY100 is only about 1V and direct replacement of a metal or valve rectifier results in the h.t. voltage increasing by up to 30 or 40V which, if not reduced, will rapidly lead to trouble elsewhere in the receiver. Unfortunately it is not possible to give any precise information regarding the value of the resistor required for this purpose, since its value will vary from receiver to receiver, depending, as it does, upon:

- the size of the reservoir capacitor;
- the current consumption of the receiver;
- the type of rectifier being replaced.

However, in practice, values of between 33 and 82Ω have been used at power ratings of 10 to 15W and this will give some guide as to what is likely to be required.

This resistor is connected in series with the diode (either side will do) and limits the rate at which the reservoir capacitor can be charged and hence the mean output voltage. The experimental approach is usually required to determine the exact value needed. Connect initially a 47Ω resistor in series with the diode, switch the receiver on and measure

the smoothed h.t. voltage. This should usually be about 210/220V for most receivers. If the voltage obtained with the 47Ω resistor is lower than this then try a lower value, if it is higher then try a higher value of resistor.

The instructions earlier in this note concerning the positioning of the resistor possibly required to replace the rectifier heater apply, also to this surge limiting resistor.

It should be noted that this additional resistor is not always required; for instance, in some receivers the voltage applied to the rectifier is taken from an auto-transformer. In such a case it may be possible to take the rectifier feed from a lower voltage tap. In other cases, if the supply voltage from which it is desired to run the receiver is less than the highest input voltage tapings provided by the receiver manufacturer, it may be possible to use the additional (unused) resistor(s) provided for use when the receiver is worked off the highest voltage mains in order to drop the voltage applied to the rectifier.

For example, if the set is to be run from a 210V supply then the resistors provided for using the set from a 250V supply may be available for use in dropping the voltage applied to the silicon diode.

TABLE I  
Rectifier, Type BY100

Maximum Peak Inverse Voltage	800V
Maximum Forward Current at 50°C	550mA
Typical Reverse Current at 25°C	less than 10μA

Valve Type	Replacement Heater Resistor	
	Ohms	Watts
PZ30	180	15
PY32	100	10
2x PY82	120	10
PY82	68	5
U801	390	15

These notes so far have been mainly applicable to television receivers but, of course, the BY100 can equally well be used in some radios, amplifiers, etc. A single BY100 will replace half-wave rectifiers such as the 25Z4, 35Z4, 117Z4, etc., whilst a pair will replace full-wave rectifiers such as the 5Z4, 6X4, etc.—provided that the r.m.s. voltage applied to each diode does not exceed 250V. This means that when the rectifier is fed by a transformer, if the voltage applied is greater than 250-0-250 one cannot use a pair of BY100s. (Note: Two pairs of BY100s will handle 500-0-500V.)

When the silicon diode is used in radio receivers, amplifiers, etc., considerations similar to those outlined earlier in this article regarding the heater chain in a.c.-d.c. receivers and surge limiting resistors apply, excepting that the increase in h.t. voltage is often not so marked owing to the smaller value of reservoir capacitors used in radio receivers, etc.

One final word of warning: silicon rectifiers are unlike old soldiers in that they do not slowly fade away; make a mistake and they will "die" at once! So please check the circuit carefully and in particular ensure that the rectifier is connected into circuit with the correct polarity. ■

# SERVICING TELEVISION RECEIVERS

By L. Lawry-Johns

## No. 97 THE RAYMOND F93 AND BEETHOVEN B94

**T**HE potentiometer VR3, is the frame hold control. If this control is at the end of its travel check V13 (ECC82) and R69 (470k $\Omega$ ), which is in series with VR3 to pin 7 of the V13 base. A defective ECC82 in this position can also cause frame jitter, i.e. rapid vertical bounce not corrected by the controls.

### Lack of Height

Loss of height which is even top and bottom should direct attention to the ECC82 and to R70 (1.8M $\Omega$ ), which sometimes goes high.

### Bottom Compression

If the bottom of the picture is compressed and the top appears extended (in relation to the bottom) check the ELC80 (V14) and if a new valve does not improve matters check the 250 $\mu$ F 25V

bi $\bar{a}$ s electrolytic capacitor C80. This capacitor will probably be found to be open circuited. If the valve and capacitor are in order check the linearity capacitor C76, C77 and C78.

### Hum Bars

Quite often a considerable amount of a.c. ripple is injected into the video circuit causing wide bands of light and dark areas across the screen making overall illumination of the screen impossible. This should direct attention to V9 (EB91) and V10 (PCF80), either of which may have heater-to-cathode leakage.

### No picture, Charred Resistors

V10, the video amplifier, is biased by R51 (560 $\Omega$ ). This resistor is held at a fairly constant current level by R49 (33k $\Omega$ ). Quite often R49

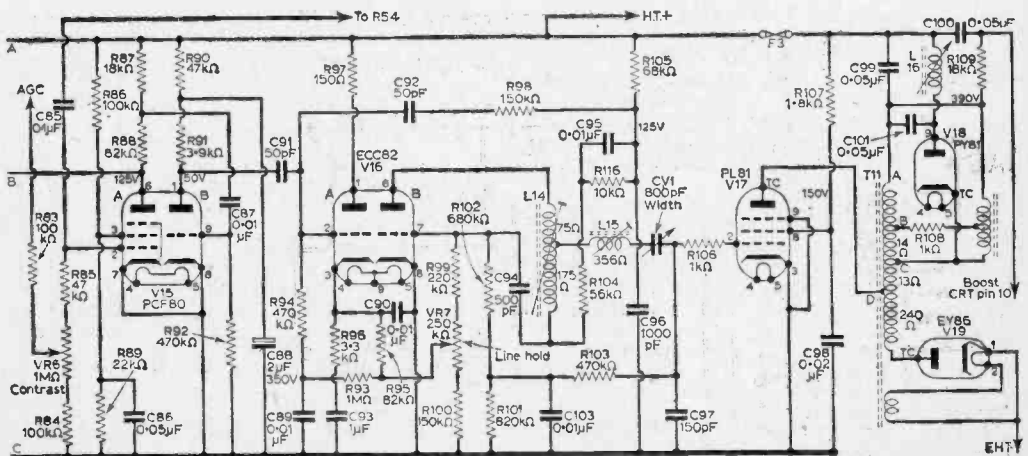


Fig. 2(a)—The power pack, frame timebase and part of the sync separator stages of the circuit.

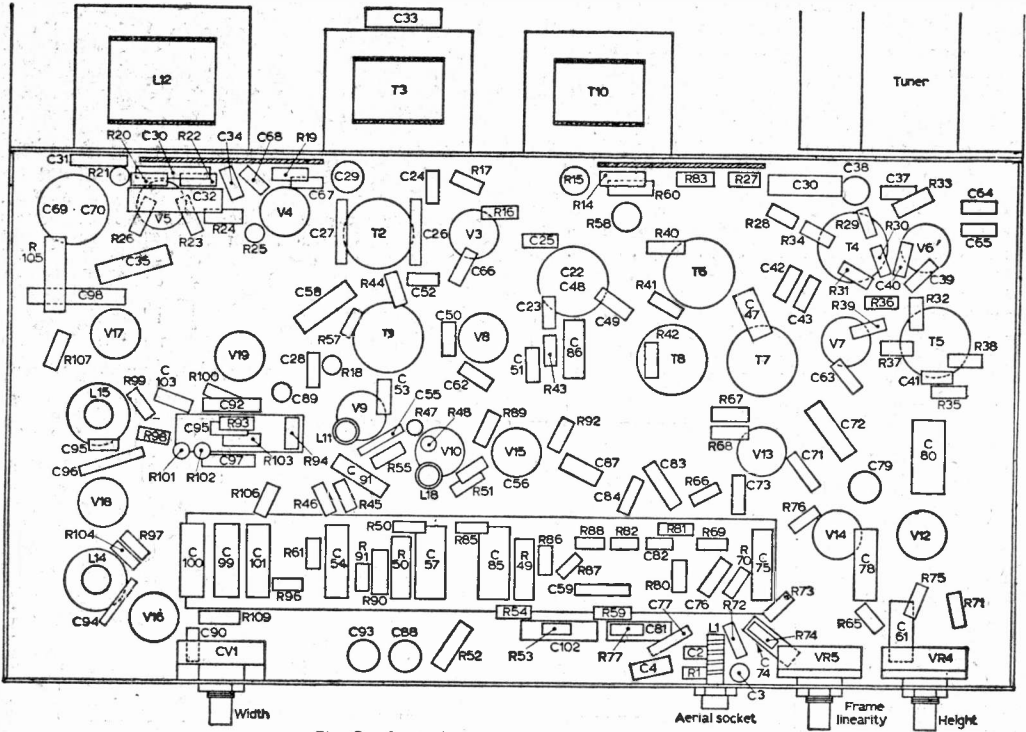


Fig. 3—An underchassis view of the receiver.

changes value thus causing excess current both through itself and R51 resulting in damage to both.

This can cause R51 to become open circuit or, more seriously, to become a virtual short circuit with the result that the h.t. line is shorted to chassis, blowing one of the main fuses and/or damaging the PY82 rectifier which is normally run at its limit and is intolerant of overload.

**Poor Contrast**

If the contrast control functions but the picture is weak and lacking in "attack" although the overall brightness is good, check V10 which may be failing in emission, then check V6, 7 and 8, the resistors associated with V10 and the decoupling components of V7 and V8.

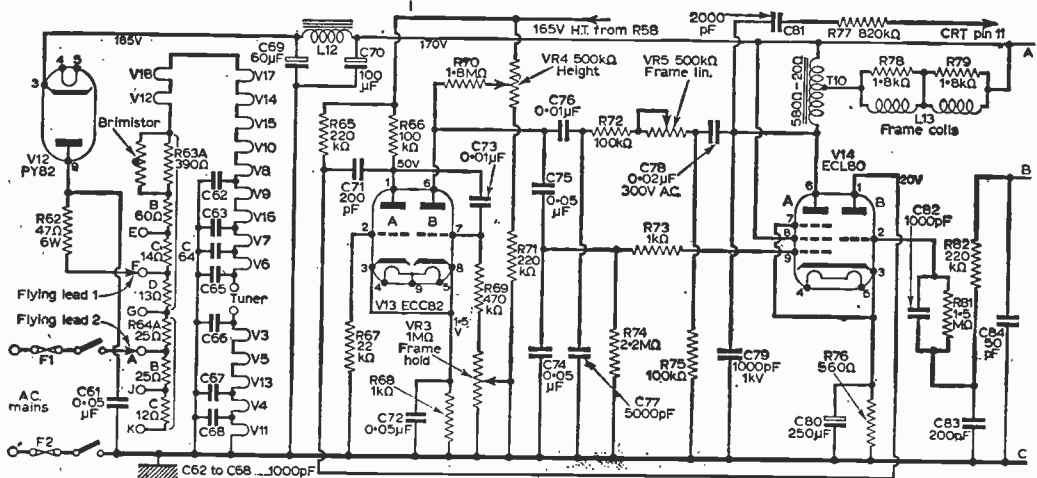


Fig. 2(b)—The remainder of the sync separator stage and the line-timebase circuits.



# A CLOSED CIRCUIT

# TV

# Camera

By E. McLoughlin

## PART FOUR: THE CAMERA CONTROL UNIT

CONTINUED FROM PAGE 119 OF THE DECEMBER ISSUE

**T**O give adequate ventilation for the control unit, the top of the chassis is covered by a perforated steel grid hood attached to the narrow sides of the chassis by means of two flanges and four self-tapping screws. This arrangement is exceedingly simple, provides all-sided ventilation as freely as if the chassis were entirely open, permits very rapid opening of the unit for work above or below the chassis and has a very pleasing and professional appearance.

It must be pointed out that this unit definitely requires an efficient forced-ventilation fan if housed in any form of semi-closed metal cabinet, as self cooling will then certainly be insufficient. A fan is not required in the arrangement as published, in which all major heat-producing components have been grouped above the chassis and can cool freely by convection through the steel grid hood.

Do not operate the unit standing in a narrow alcove, in a cupboard of small dimensions, or other confined space. Do not place papers, books,

other apparatus or other combustible articles on top of the covering hood. This could lead to damage, overheating or fire.

### Power Supplies

Fig. 15 shows the complete theoretical circuit of all power supplies for feeding the control unit and the camera head.

Two conventional fullwave valve rectifier and smoothing circuits, having only the mains transformer in common, are employed. Ample smoothing capacities and chokes are used. As a result, two separate main h.t. feeds, each capable of delivering about 75mA maximum, are available.

The whole video amplifier and preamplifiers in the camera head are fed from the one h.t. line and the entire scan and focus circuits and the r.f. section from the other. This gives minimum unwanted interference at the sensitive input stages to the video amplifier, the screening and layout adopted giving further assistance in this respect.

An important feature is, furthermore, the accommodation of all branch-decoupling components, for both h.t. systems, on an aluminium bracket above chassis. Respective "trunk" cables connect to the consumer circuits below chassis (Fig. 14).

This arrangement has several advantages. Firstly, it removes nearly all major-heat-producing components out of the sub-chassis wiring, permitting very compact layout of the latter. Secondly, it removes nearly all large components out of the sub-chassis circuits, particularly out of the video and r.f. sections, so that these can be wired in the compact form necessary for optimum stability and correct performance. Thirdly, it groups all h.t. check-points very conveniently together on the aluminium bracket, in an easily-accessible position above chassis.

Accordingly, the voltage and current measurements obtained for the prototype, once this was working as desired, are shown in Fig. 15. Constructors may find slight variations from unit to unit, but any gross departures indicate the need

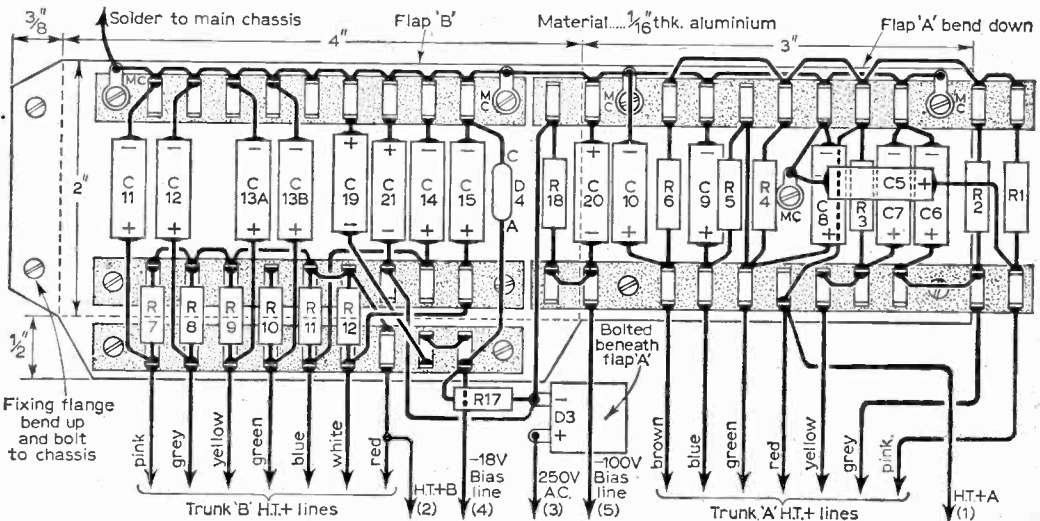


Fig. 14—The h.t. and bias distribution bracket.



for further investigation of the branch circuit concerned, to remove any fault conditions.

The trunk cables used in the prototype between the h.t. distribution bracket and the sub-chassis wiring were lengths of plastic-insulated multiway office telephone cable, with conductors covered with plastic insulation of various colours.

**Bias Supplies**

D3 is a metal rectifier in a halfwave circuit, for bias supply voltages. The vidicon grid bias line (-100 volts) receives extremely heavy smoothing through 8μF and 2.2MΩ, and the -18V bias line for other circuits is stabilised and well smoothed by the Zener diode D4 shunted with a high capacity. Such smoothing is essential, as any hum or fluctuations on the bias lines would be amplified directly in the amplifier chain.

The EZ80 type rectifier valve is designed for full h.t. voltage insulation (up to 500 volts working) between heater and cathode, and correct operation is with one side of the heaters earthed to chassis. This heater circuit must not be earthed both at the camera head chassis and at the control unit chassis, as such measures would create a hum-loop injecting hum into the video amplifier. On the other hand, earthing at the camera head chassis alone has the disadvantage that, should the camera power-feed plug be removed, the rectifier heaters "float" free, which is not permissible.

Thus earthing of this heater line at the control unit *only* has been adopted, both wires being taken insulated to the camera head and there grounded only for high frequencies via a pair of capacitors.

It is important to load the heater windings approximately fully, i.e. not to use heater windings

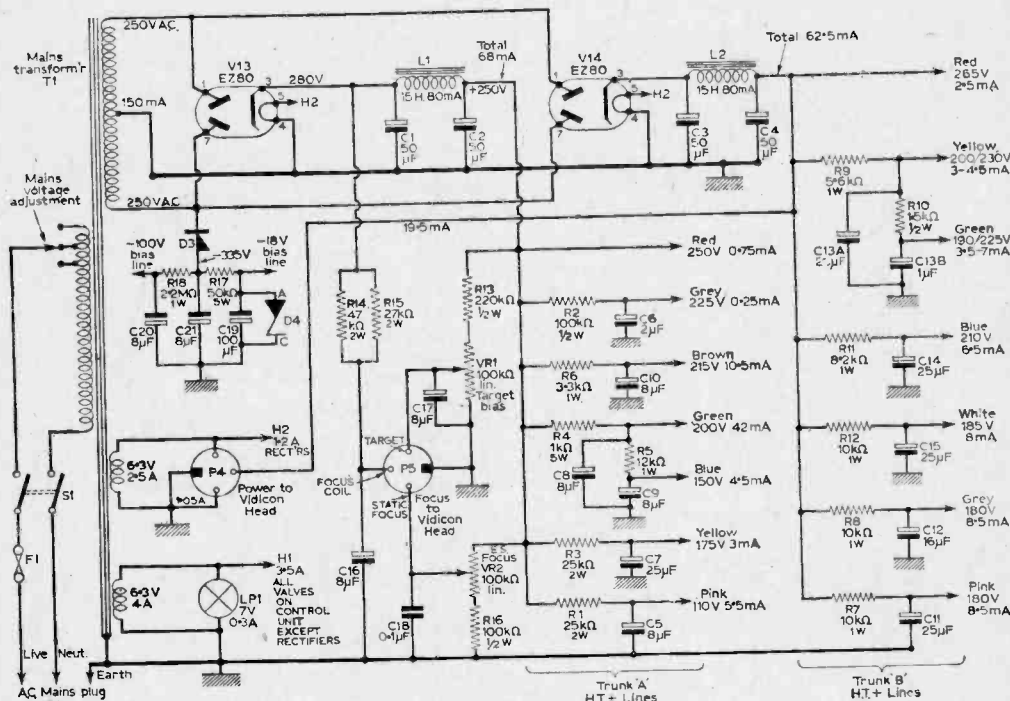


Fig. 15—The circuit of the power supplies.

**Heater Supplies**

Note the distribution of heaters between the two heater windings present on the transformer. The ratings shown in Fig. 15 were those actually present in the prototype and also represent those most likely to be found on the average mains transformer. A total of some 6A heater current at 6.3V is required for the entire equipment, including the camera head. All valves in the control unit (except the rectifiers) and the pilot lamp together correctly load a standard 4A winding. The rectifiers and the camera head heaters are run off a second 2.5A winding.

capable of delivering much more current than actually drawn, otherwise the voltage will be too high in many cases, which can seriously shorten the life of the vidicon tube. In the case of this tube the heater voltage lies between 6.0 and 6.6V.

**Focus Supplies**

The value of R14 may need to be varied once the unit is completed, to obtain correct focus action. The value shown for R14 and the focus coil current in Fig. 15 are the values obtained with the finally adjusted prototype. The ultimate criterion is to get the point of exact focus on the electro-static fine focus control VR2 into the

approximate middle of the track of VR2, and the value of R14 should be adjusted with this aim.

The value of R14 requires reduction if the focus point is too near the bottom end of VR2, or if no focus point is present at all, merely "least confusion" resulting with VR2 slider at the bottom end—and vice-versa.

**The Video Amplifier**

The output signal from the camera head unit (see Fig. 9, November issue) is further amplified in the four-valve video amplifier chain shown in the top section of Fig. 16.

The output after the first three of these stages is a composite positive video signal of about 1½V amplitude, suitable for feeding a video monitor unit. Details of a suitable monitor unit will be published later. The sync pulses generated in the scan circuits (Fig. 17) are inserted into the video signal at V6.

The fourth stage, V7, is operative only for modulating the r.f. section. It gives the slight additional gain required to match the circuit used, and, as shown in Fig. 16, inverts the composite

video signal for achieving the necessary negative modulation of the 625-line CCIR standard.

If 405-line BBC standard is to be adopted, V7 must be driven at the cathode. The actual changes to be effected are then: remove C53 from pin 2 and connect to top of R90. Discard C55. Reduce R88 to a suitable value between 270Ω and 1kΩ giving satisfactory modulation depth. Make L7 similar to L5 instead of to L4. Connect two 0.05μF 500V paper capacitors between pins 2 and 8 and chassis respectively on V7. In addition, C52 may need to be increased to 0.05μF and R85 to 270kΩ; these two measures also being worth trying for 625-line operation if difficulty is experienced in obtaining satisfactory frame lock on the particular receiver employed. No other changes are necessary to the circuitry of V4—V7 when converting between 405/625 lines.

**Amplitude Compensation**

We pointed out in the introductory article on amateur CCTV, that a target load not exceeding about 4.7kΩ is required on the vidicon, if sufficiently linear response is to be maintained over

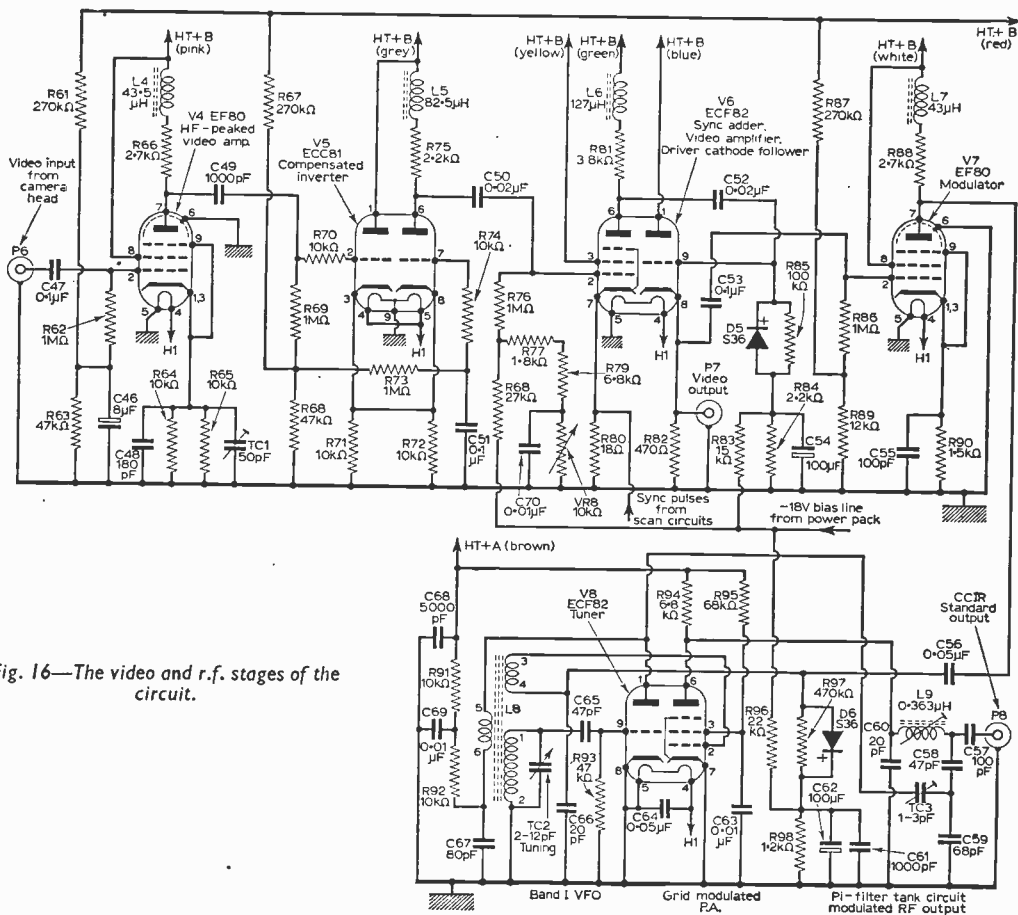


Fig. 16—The video and r.f. stages of the circuit.

the entire range of video frequencies in the face or target stray capacities. At normal signal currents of about  $0.25\mu\text{A}$ , such a load would give a signal of some  $1\text{mV}$  amplitude, requiring an amplifier of reasonable gain. The amplifier itself would need to have as linear a frequency response as possible.

Now, whilst such an arrangement would certainly give optimum performance as far as phase response (see below) is concerned, it brings a number of practical disadvantages and complications. It is a better compromise to use a much larger target load on the vidicon (in our present actual circuit, twelve times as large). This gives severe loss of high frequencies in relation to low frequencies from the camera head, and the video amplifier chain must be arranged to have a compensatory frequency characteristic.

The design shown in Fig. 16 meets these requirements. The major disadvantage of the low target load condition is that the mean signal level is low compared with residual mains hum and other spurious injections at the camera. Now losses at the camera and compensations in the video amplifier do not affect the low and mains frequency response, so that use of a twelvefold larger target load means that only a twelfth of the low frequency gain is required in the complete system, improving the signal-to-noise ratio with regard to low frequency interference by a factor of twelve. Furthermore, it is possible to achieve some measure of improved general signal-to-noise ratio too by using the larger target load.

### Phase Response

It is not sufficient in video amplifiers to cater for uniform amplification of the amplitude of signals at all frequencies (linear frequency response); the phase-shift must also be as constant as possible.

The first condition, that of level frequency response as far as amplitudes are concerned, is relatively easy to satisfy. Where compensations are required, suitable frequency dependent R/C networks are easy to arrange, yet by their very nature these produce severe phase shifts. Satisfactory phase response of a frequency compensated video amplifier is thus not possible with the use of capacitors and resistors alone; inductances must be used as well for a final net cancellation of undesired effects.

The design of an ultimately suitable amplifier is, as a result, a mathematically very involved operation and we cannot go into details here. It may merely be stated, that the actual version here used is based on a development by Messrs. EMI Ltd., and some general principles are easily understood.

Two forms of "peaking" (rising gain for high frequencies) are employed in a staggered fashion. V4 and V7 use the first kind at their respective cathodes. Here, very large cathode resistors are used (with corresponding return of gridleaks to a positive point on respective h.t. bleeders to re-establish Class-A operating points, a method of bias also very favourable for stabilising the operating points of high-slope valves), with very small bypass capacitors. Negative feedback is thus very great at low frequencies. At some cross-over frequency, determined by the value of the small bypass capacitor, the latter "begins to be effective", so that negative feedback falls and gain rises above this frequency.

For V4 alone, TC1 permits adjustment of the cathode crossover frequency between approximate limits  $120 - 150\text{kc/s}$ ; if the required value during subsequent adjustments lies outside this range, the value of C48 can be altered.

The crossover frequency in the cathode circuit of V7 is just above the top limit of the video passband, so that only very slight rise of gain to compensate losses in C66 in the modulation feed of the tuner results.

### Peaking Coils

The second form of compensation uses peaking coils, and is here employed in the anode circuit of every stage contributing to the total amplification, i.e. it is absent only in the two triode sections functioning merely as cathode followers (V5, pins 1, 2, 3 and V6, pins 1, 8, 9).

The anode to chassis stray capacity in each case is effectively in parallel with the peaking coil and anode load resistor themselves in series and behaving as a coil of high resistance, i.e. low Q. The combination represents an extremely heavily damped tuned circuit, giving increased gain over a broad band of frequencies in the neighbourhood of the resultant resonant frequency.

TABLE 2  
PEAKING COIL DETAILS

Ref.	Nominal Inductance $\pm 10\%$	No. of Turns	Self Resonance	Resonance with 100pF in parallel
L4, 7	$40\mu\text{H}$	35	13.5 Mc/s	2.38 Mc/s
L5	$80\mu\text{H}$	55	8.5 Mc/s	1.71 Mc/s
L6	$125\mu\text{H}$	62	6.3 Mc/s	1.38 Mc/s

All cores are ferrite threaded slugs, 1in. long,  $\frac{1}{16}$ in. dia. Windings are single layer, closewound, except L6, where the winding consists of three sections of 21T, 10+10T (double layer) and 21T. 30s.w.g. enamelled copper wire is used for all these coils.

In the video amplifier for the present unit, we do not desire level response, but rising response. Accordingly, the resonant frequency of the peaking circuits is lower than for level response, i.e. the inductance values are greater. The resulting Q-values are greater.

Each peaking circuit has a second resonance of High Q at a much higher frequency, given by the self-resonance of each coil alone with its stray capacity. All self-resonances must lie above the video-passband of the complete amplifier, and, to prevent instability, they must be well staggered in frequency. It is of advantage to place the lowest self-resonance just outside the passband and the highest at about double that frequency.

Table 2 shows winding details for the four peaking coils found satisfactory in the prototype and in the layout of wiring shown later in this article. It is seen that not only are the inductance values important but also the self-capacities.

It is probably simpler to use the last two columns of check-values in Table 2, in conjunction with a grid-dip meter, as amateur grid-dip meters are generally more reliable than amateur r.f. bridges required when using the check-values in the other two columns. Grid-dip meter measurements should be made on the bench, before wiring the coils into their positions in the units.

#### Other Features of the Video Amplifier Chain

A total of four stages contributing amplification are required between vidicon and the video output socket, P7. As the signal polarity must undergo net inversion by the entire system, one amplifier stage (V5) is arranged to produce no signal inversion. The first triode of V5 is a cathode follower and the second a grounded grid amplifier; the complete stage has here been termed a compensated inverter.

V4 is a normal amplifier stage. The pentode section of V6 also serves as a normal amplifier stage, with a measure of variable-mu gain control by means of VR8. This gain control is placed at such a late stage in the chain in the interests of signal-to-noise ratio. V6 pentode also performs the further function of sync-addition to the video waveform.

The sync mixer stage, V12 in Fig. 17, cuts off about 10mA of current through R80 (cathode current, pin 3, of V12) during all sync pulses, thereby injecting a sync signal of 0.2V at V6 pentode cathode. The triode section of V6 is a cathode follower, and provides a low impedance output to permit transmission of the signal through considerable length of coaxial cable connected to P7. NOTE: Fig. 17 will appear in next month's article.

D5 restores the bottoms of the sync pulses to about -2V at grid pin 9 of V6, so that these become the reference level, as required, in the composite output signal. Speaking in the more usual terminology, this simply means that D5 clamps the black-level of the output signal, since R80 guarantees sync pulses of definite amplitude.

#### The Tuner

The great advantage of a CCTV circuit with r.f. output compared to one with only a video output is that much greater lengths of coaxial cable are permissible between "transmitter" and receivers.

A one-valve tuner is relatively simple to construct, and thus a definite asset unfortunately not found on all CCTV equipments.

Considerable numbers of unmodified domestic television receivers can be fed simultaneously (via suitable matching networks of resistors) since the output at P8 is 100mV in 60-80Ω.

The tuner signal output is quite ample and lengths of coaxial cable up to a mile would probably be usable. On the prototype, P8 is in the form of two coaxial sockets in parallel. When both sockets are in use, for feeding two receivers, an 80Ω resistor must be wired in series with the inner conductor in each plug inserted, as the matching is otherwise disturbed. A couple of short adapters containing an 80Ω resistor each have been made for the prototype. These can be inserted externally when required between the receiver lines and P8.

**TABLE 3**  
**TUNER COIL DETAILS**

#### V.F.O. Coil L8

Former  $\frac{1}{4}$ in. approx. diameter, with v.h.f. slug.  
Grid Winding 1,2: 12 turns of 20 s.w.g. tinned copper wire spaced over  $\frac{3}{4}$ in.

Anode Winding 5, 6: 4 turns of 24 s.w.g. enamelled copper wire, between first 4 turns of winding 1, 2—at end 2.

P.A. Drive Winding 3, 4: 4 turns of 24 s.w.g. enamelled copper wire between first 4 turns of winding 1, 2—at end 1.

All three windings to run in same sense, starting from 2, 4, 5 and ending at 1, 3, 6 respectively.

Wire 100pF ceramic capacitor temporarily in parallel with grid winding 1, 2 and adjust slug for resonance at 18 Mc/s with aid of grid dip meter.

#### P.A. Anode Coil L9

Former  $\frac{1}{4}$ in. approx. diameter, with v.h.f. slug.  
6 turns of 20 s.w.g. bare silvered copper wire, spaced over  $\frac{1}{2}$ in.

Wire 250pF ceramic capacitor temporarily in parallel and adjust slug for resonance at 16.7 Mc/s with aid of grid dip meter.

#### The VFO Carrier Oscillator

The triode section of V8 is operated as an ordinary grid-tuned oscillator circuit with anode reaction of sufficient intensity to maintain oscillation without squegging. If squegging is observed (saw-tooth waveform observable on oscilloscope connected to junction of R91/R92 with C69 disconnected, and intense black bars in displayed picture; frequency probably around 100kc/s; black bars not locked to line scan), the values of C67 (increase) and R93 (reduce) may be adjusted.

It is important to use a good ceramic air-spaced shortwave tuning capacitor for TC2. With the specified capacity values and tuning range adjustment as explained in Table 3, slow motion drive is not necessary, a small knob directly on the spindle of TC2 giving the right action for smooth tuning through all Band 1 channels.

An aperiodic third winding on the oscillator coil picks up the carrier drive signal for the pentode section of V8 functioning as grid modulated p.a. The modulation voltage is applied in series with the grid winding.

#### Modulation

Adjustments for optimum modulation must be carried out with care. Details given for L8 in Table 3 proved satisfactory for the prototype.

The arrangement shown is for 625-line operation. D6 restores the negative video signal from the modulator V7 so that it is entirely negative going from a voltage set by R98 (approximately -1V) and defining full carrier amplitude. Peak white video should drive the p.a. grid sufficiently negative for reduction of the carrier amplitude to 10% of peak value.

Static checks should be made with a wavemeter connected to P8 (r.f. valve voltmeter). Disconnect C56 from D6 and observe the wavemeter reading. Temporarily connect an additional resistor of value 2.2k $\Omega$  between the bottom end of R98 and chassis, and note the new wavemeter reading. If this does not lie between 10% and 20% of the former value, adjust the value of R98 if only small corrections are required, or the number of turns between connections 3 and 4 on L8 if larger corrections are required.

TC3, which neutralises direct-through coupling of unmodulated carrier between the two anodes, must be adjusted for minimum reading on the wavemeter before taking any readings. As an alternative to changing the number of turns on L8 (winding 3, 4) the modulation depth can be influenced by intermediate amounts by changing the value of R88 in the modulator anode circuit.

#### Modification if 405-line Standard Operation Desired

The modulation signal from V7 will in this case be positive, the necessary modifications to V7 circuitry to achieve this having already been discussed. The signal must now be d.c. restored at V8 pentode grid such that it is entirely positive-going from a reference voltage 1.8V more negative than in the case for 625-line operation.

This is simply achieved by reversal of D6 and increase of R98 to 3.8k $\Omega$  of 4.7k $\Omega$ , whichever value is found to be more satisfactory. For subsequent adjustments, temporarily disconnect C56 and note the wavemeter reading at P8 after adjusting TC3 for minimum reading. Then temporarily connect a

1.8k $\Omega$  resistor in parallel with R98. The wavemeter reading should rise to 5-10 times the former value if all is well. Otherwise make appropriate adjustments to R98, R88 (modified anyway) or, at a last resort, L8, winding 3, 4.

Note that TC3 must be able to pass through a definite minimum output setting under all conditions. If this is impossible, the capacity range covered must be changed—probably reduced, indicated by lowest output with TC3 at minimum capacity.

#### The Output Tank Circuit

The output circuit is in the form of a low-pass pi filter prototype section. Although having the appearance of a tuned circuit, it is not one, but rather a low-pass filter having the characteristics of a pure resistance up to a certain cut-off frequency, above which it gives high attenuation. The characteristic resistance over the passband is designed to be the output impedance matching ordinary coaxial cable. Table 3 summarises the design formulae and criteria, and gives full details of the calculation of the filter used in the author's prototype.

The simple prototype section designed according to Table 3, with a cut-off frequency just above the top of Band II, proved sufficiently effective for reduction of harmonics to enable the receiver to be switched over to interference-free reception of Band III and IV broadcast signals (Continental site) with the CCTV equipment still feeding a full-power Band I signal in at the aerial terminals.

CONTINUED NEXT MONTH

## A Flying-Spot Scanner

—continued from page 153

provided by varying the voltage to the cathode; this has the effect of making the grid more or less negative with respect to the cathode and hence suitable bias is achieved.

We now need to design the bleeder chain to produce the correct potentials at the electrodes. The tube itself takes very little current—in the order of a few microamps, and the e.h.t. rectifier is capable of supplying up to 5mA of current. The current flow along the bleeder chain is designed to be 1mA—this being well within the capabilities of the rectifier and satisfactory from the point of view of the tube. Also, this current is convenient from the point of view of calculation since we have a voltage drop of 1V across each thousand ohms of resistance (e.g. a 100k $\Omega$  resistor passing 1mA will have 100V across it).

The total resistance of the bleeder chain is given by:

$$R = \frac{E}{I}$$

$R$  = resistance  
 $E$  = voltage  
 $I$  = current

in our case  $E = 2,650V$ ,  $I = 1mA$  and so  $R = 2.65M\Omega$ .

Having arrived at this value we must now decide how it is to be made up.

From the table of characteristics of the tube we see that the minimum bias on the grid of the tube

is  $-1V$  and the grid must not become more positive than this. The resistance R8 takes care of this and since it has a value of 3.3k $\Omega$  it means that there is a minimum bias of  $-3V$  at the grid of the tube which gives a safety margin for all possible conditions.

CONTINUED NEXT MONTH

### JUST OUT! THE PRACTICAL TELEVISION DIARY FOR 1964

A must for all TV enthusiasts.

Not only a diary—but also a concise pocket reference book. Indispensable to both the amateur and professional engineer. Contains 140 pages of technical matter.

MANY TABLES OF USEFUL DATA: base connections for current valve and tube types; tube equivalents; decibel calculations; wire gauges; screw threads; metric conversions; BBC and ITA stations, etc.

PLUS ARTICLES ON


Fault findings. Aerials. Television transmission. Basic meter circuits. Glossary of Technical Terms.

Bound with Levant Duroskin cover.  
Price 6/3 or with pencil 7/1.

Obtainable from Stationers, Booksellers, Newsagents everywhere. In case of difficulty write to: Practical Television, Post Sales, Tower House, Southampton Street, London, W.C.2. State which type you require and enclose crossed P.O., including additional 6d. for postage.
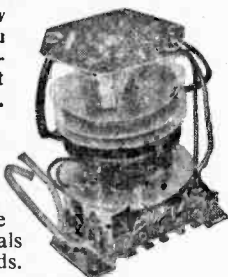
# THAT 'DIFFICULT' COMPONENT ... SAME DAY!

No matter how old or how new the set you are servicing, if you require a line output transformer it is 999-1 that we will have it in stock or can rewind it quickly.



We operate same day despatch service from the largest stocks of television components in the U.K., including a comprehensive range of accessories, materials and test gear of all kinds.

TERMS: C.W.O. or C.O.D.

Retail quotations gladly given on receipt of s.a.e.  
Trade—Please send your letter headings for data charts.

## DIRECT TV REPLACEMENTS

\*Please Note our New Address: LTD.  
**DEPT. PTV, 126 HAMILTON RD., WEST NORWOOD, LONDON, S.E.27**  
Telephone: GIP 6166 (P.B.X.)  
Day and Night Ansafone Service

**J. V. ELECTRONICS LTD.**  
BRUNSWICK WORKS  
NOTTE STREET, PLYMOUTH

FIRST GRADE

## REGUNNED TELEVISION TUBES

**£1** 12 MONTHS' GUARANTEE  
ALLOWED ON YOUR OLD TUBE

Size	Price	If old tube is returned
9", 12" & 14"	£4 5 0	... <b>£3. 5.0</b>
15" & 17"	£5 10 0	... <b>£4.10.0</b>
21"	£7 0 0	... <b>£6. 0.0</b>
Slim Line 110°		
17" & 19"	£6 10 0	... <b>£5.10.0</b>

ALL TUBES CARRIAGE PAID. DESPATCHED BY RETURN ON RECEIPT OF YOUR REMITTANCE

Service Engineers' & Maintenance Contractors' Special Discounts

★ We still manufacture the famous  
**J.V. PRE-AMPLIFIER Channel 1-12**

Telephone PLYMOUTH 64797

# EXCEL



## RADIO & TELEVISION

Through this ICS  
**3-way Training Method**

- 1** MASTER THE THEORETICAL SIDE  
From easy-to-understand courses! Designed to teach you the theory of radio and television engineering quickly and easily.
- 2** MASTER THE PRACTICAL SIDE  
With the help of easy-to-follow illustrations! Designed to show you how to develop your practical abilities in radio and television engineering alongside your theoretical studies.
- 3** MASTER THE MATHEMATICAL SIDE  
Through a new easy way to learn maths! Designed to teach the subject that's so often a headache, but so essential to anyone in radio and television engineering.

### THERE IS AN ICS COURSE FOR YOU!

For your career or your own business, courses are available in: Radio and Television Engineering, Industrial Television, Radio and Television Servicing, VHF Engineering, Electronics, Computer Technology and Programming, Electronic Technicians, Servomechanisms; Telemetry, Instrumentation, Principles of Automation and Calculus for Electronics.

And for your hobby, there are practical "learn as you build" radio courses as well.

POST THIS COUPON TODAY FOR FREE BROCHURE TO:

ICS (Dept. 164) Intertext House Parkgate Rd. London SW11.

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
AGE \_\_\_\_\_  
OCCUPATION \_\_\_\_\_ 1.64

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Member of the Association of British Correspondence Colleges.



## A MONTHLY COMMENTARY



# Underneath the Dipole

BY ICONOS

**"BAD Taste Charges Split BBC's Top Men"** was the shrill banner headline above a national newspaper's story of differences of opinion between Sir Arthur fford, chairman of the BBC, and Mr. Hugh Carlton Greene, the Director-General. It seems that, spurred on by Sir Edward Fellows, chairman of the BBC's Advisory Council, Sir Arthur has circulated to top executives a confidential 3,000-word document setting out the principles of broadcasting. This unprecedented step has been precipitated by the rapid decline of BBC standards during the last few months, the errors of taste and the smut, sneers, bad language, offensive interviewers and near-pornographic TV plays which have been broadcast. Ironically this decline has affected another branch of show business—the cinema. Certain film producers complain that the BBC has knocked the financial bottom out of the "near-the-knuckle" film market! Cinemagoers say why pay to see kitchen sinks and the vice dens of Soho when you can see them free on the BBC? The film censor has himself told me that the BBC regularly broadcasts scenes and dialogue that he would not pass, a fact which should be noted by Sir Arthur.

### Misguided Hughie

One of the most respected Sunday newspaper TV critics addressed an "Open Letter to

*Hughie*", his friend, Mr. Hugh Carlton Greene. In it he put forward in a most diplomatic manner views about the declining tone of BBC programmes which were along the same lines as those much more bluntly set out in the "Open Letter to the Postmaster-General" printed in these columns three months ago. It is not surprising that the BBC Advisory Council, which includes the Bishop of Manchester, Sir Stanley Rous, Sir Harold Grime and other eminent people, are not very delighted with the present trends. It would be a good idea if this confidential code-of-practice memorandum was accompanied by a copy of the Duke of Edinburgh's famous speech about the "rat race" of declining taste in broadcasting, newspapers, plays and films—a race in which BBC-TV is an easy winner. Statesmanship is required, not the feverish pursuit of TAM ratings, shock treatment for viewers and a lack of policy which would be more appropriate for an irresponsible scandal magazine.

There are already signs that the BBC is modifying its policy—or lack of it—by the abrupt termination of TW3. Attention should now be focussed upon the TV play department, and those current affair programmes which bend backwards to give undue publicity to anti-British points of view. After all, it is supposed to be the *British Broadcasting Corporation*, or is it?

### The Telegoons

After this further instalment of nagging about the tarnished image of Auntie BBC it is pleasant to be able to pay at least one compliment to our blowsy old aunt. She has provided the children with a real treat in *The Telegoons*, a series of marionette films in which the puppets mime to the voices of Peter Sellers,

Harry Secombe and Spike Milligan.

There are certain technical advances in these puppet films which are worth noting. The eyes and eyelids seem more life-like than on any other puppets I have seen and the synchronisation of dialogue and mouth movement is perfect. The story-line is excellent, too, based on real goonish scripts by Eric Sykes and Spike Milligan and produced by Tony Young for Grosvenor Films under a contract with the BBC for Saturday afternoon Children's Hour. *The Last Tram* episode must have amused and delighted children of all ages up to 90 and I understand that there are even more hilarious adventures on the way. I would like to see more about the fantastic lost London tram, which was marooned on Clapham Common for ten years, complete with passengers!

### Royal Variety Performance

What a magnificent evening's broadcasting ATV gave us on the occasion of the Royal Variety Performance. Viewers who switched on early on the same evening for *About Religion* saw a special Remembrance Sunday programme, entitled *The Two Faces of War*, in which John Slater narrated to a series of films, stills and drawings. Beautifully edited and directed by Shaun O'Riordan, this production was a sincere and moving commentary on the follies and the heroisms of war. I have always thought John Slater was a fine actor, but in this instance he was not acting at all; he was speaking a magnificently written script in a manner which conveyed his intense belief in the words.

After a suitable "buffer" item of news headlines, the Royal Variety Performance recording was played off and what a splendid entertainment it was!

Everybody seems to have seen it and each has his own special favourite items. My own were: Dickie Henderson, the brilliantly professional compère, and the ubiquitous Steptoe and Son, Wilfred Brambell and Harry H. Corbett—with whom one must couple the unseen scriptwriters, Galton and Simpson. But it hardly seems fair to pick out two turns when all the performers were so good, the orchestra excellent, the production numbers slick and the television presentation smooth. Bill Ward, ATV's ace director (and head of light programmes) has a magic touch that never misses. I run short of superlatives when describing his shows.

### *Nice Break for the Boys*

The direction of a television play is not always easy, particularly if there is a large cast. Add to this a script which calls for a lot of movement by the actors, small-part players and crowd in and around a number of settings and the director is faced with more problems, not to mention headaches. Add to these the complications of camera and microphone movements, the silent revamping of sets, lens changes, zooms, vision mixing, playback—all to be deployed in fairly long sequences of 15 or 20 minutes each—and you have a potential chaos.

Yet in the A.R. production of *Nice Break for the Boys*, director Ian Fordyce must have kept full control, because this fast-moving television play about the troubles which stirred and finally broke out at an approved school, moved with the smoothness of a motion picture that has had individual attention for every camera set-up

and has taken weeks of shooting in a traditional film studio to complete. The play itself, by John Wiles, centred around the headmaster of the school, played with power and understanding by Leslie Sands. There may have been a message in the problems he was faced with and the way he tried to maintain discipline, but this rather got lost in the rapid build-up of events which culminated in rebellion. This did not matter. It presented quite clearly the difficult task of the masters at such schools, which could only be undertaken by dedicated men—and if this was the message it was a valid one. Since writing the above I have discovered that this complicated production was accomplished with ten days of rehearsal (in rehearsal rooms) and two days of "hot" rehearsals and recording on video tape on the Wembley stage of Associated Rediffusion. There were five main settings, three of which were "revamped" into other settings during the actual shooting. If this same production was made with traditional film studio methods, it would have occupied a fully equipped stage for three or four weeks at least. Yet film producers and technicians put up intense resistance to the adoption of any of the time-saving devices which are commonplace in British television studios. No wonder the film studios are closing down one by one—and in this National Productivity Year, too!

### *Video Tape Developments*

One of the most interesting exhibits at the recent Industrial Photographic and Television Exhibition at Earls Court, was the first small portable television tape

recorder to achieve its "production model" stage. This is an equipment made by the Precision Instrument Company, of the USA, which uses magnetic tape only 1in. wide, travelling at 6½in. per sec. The equipment is fully transistorised and operates on a helical system with scanning across the tape, skewed so that the effective track width is about 12in. long. The 1in. tape carries a sound track ⅛in. wide on one edge and a similar control track on the other edge. Aimed mainly at the rapidly expanding closed-circuit TV market in educational, industrial, medical and military applications, it does not achieve the quality of the large (and expensive) R.C.A. and Ampex installations. But its cost—in the region of £4,500—is about one-sixth of the cost of the larger professional equipments used in television studios. Nevertheless, I would think that it is a most useful tool for TV newsreel interviews and topical events. The quality on the demonstration reel I viewed was about the same as the average 16mm newsreel film, with negative film transmitted on vidicon telecine by phase reversal to turn it into positive.


There are other makers who are proposing to make economical 1in. television tape recorders—about six of them—but they are still in their last stages of development. It is one thing to look at a prototype, but much more important to see a production model in operation with the knowledge that it has been time-tested and is backed with a full service of spare parts. I would say that it will not be long before this type of equipment is in regular use for news and magazine operation at regional TV stations, if not in London.

## THE "PRACTICAL WIRELESS" AND "PRACTICAL TELEVISION" FILM SHOW

The "Practical Wireless" Film Show which is held annually and to which readers of P.T.V. are invited, is to be held, as before, at Caxton Hall, Westminster. The date and time of the Show, which is arranged in collaboration with Mullard Limited, is the 31st January, 1964, at 7.30 p.m.

The programme will appeal to all readers of "Practical Television" and of especial interest will be the illustrated talk on colour, 625-line and u.h.f. television, which will form the first part of the programme. After a break for refreshments, the programme will continue with a film entitled "Ultrasonics".

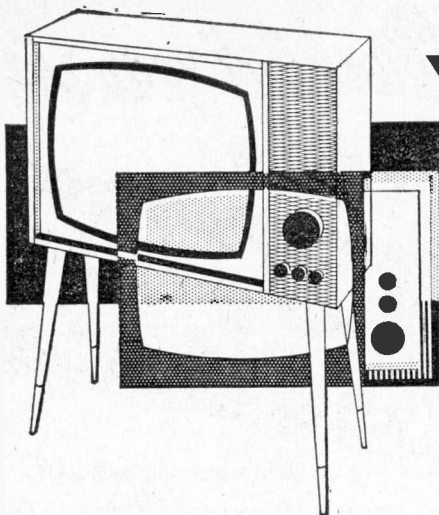Tickets may be obtained free on request from these offices. A stamped addressed envelope must be enclosed with all applications for tickets.



# Your Problems Solved

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 188 must be attached to all Queries, and a stamped and addressed envelope must be enclosed.

## PYE VI4

When I advance the volume control, the sound increases as normal until the mid-way position is reached when volume drops suddenly. Further advancing the control again increases sound but with a considerable amount of distortion.

I have checked the volume control, the i.f. valves and output valve. The fault occurs on both channels but is more noticeable on BBC.—J. Morris (Swinderby, Lincolnshire).

We suggest you check for leakage the 0.04 $\mu$ F capacitor between pin 1 of the PCL83 and the upper end of the volume control.

## COSSOR 938

The contrast control on this set will suddenly become inoperative, accompanied by an increase in gain so that the picture blurs and reduces in size. The sound improves in quality and strength at the same time. A picture may then only be obtained by reducing the contrast control setting or cutting brightness to a minimum. The resultant picture is then very poor with little contrast at all.

I have checked all the obvious components without tracing the fault.—T. Eckersley (Bolton, Lancashire).

We advise a check of the 9A8 a.g.c. valve on the left of the lower chassis, and also its associated M3 diode on the adjacent tagstrip.

## PILOT TV110F

The picture fails to fill the screen leaving a 2in. gap at the bottom, with the height control fully advanced.—C. Meheffey (Belfast).

We would advise you to replace V9 (PCL83) and check associated components if necessary. V9 is virtually in the centre of the timebase chassis.

## ALBA T644

On switching on, the picture does not appear for some time after the sound has come up. The picture then remains for about half-an-hour before it disappears leaving a dark screen. If the brilliance or contrast control is now advanced the picture will return once again but after a further hour or two will become too bright, when either of the two controls must be retarded to correct brightness.

The c.r.t. was replaced recently and nearly all the valves are new. The GEX34 diodes are also new.—D. Earle (Birmingham 21).


We are inclined to suspect the c.r.t. despite the fact that it is a recent replacement. If it is a regunned tube, we would advise you to send this back to the suppliers for their inspection. If the tube is brand new, however, you will have to check the video amplifier components with particular reference to R18 (3.9k $\Omega$ ) also checking the voltage at pin 7 which, under normal conditions, should be 145V. Also check the bias voltage (3V) and the V6 and V7 pin 8 voltages.

## EKCO TMB 272

This is a mains/battery set. The h.t. on mains reads 200V, while on battery it registers as low as 165V with a corresponding drop in performance. The battery consumption at 12.3V is also less than specified.

I have substituted the smoothing capacitor and checked the vibrator pins. I have substituted a Mallory 629 vibrator for the Plessey type 1214 which was the original, but have not improved the h.t.—J. C. Boylan (West Monkseaton, Northumberland).

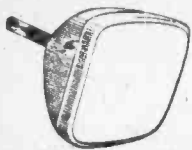This trouble is caused by a faulty pair of metal h.t. rectifiers which are sandwiched between the back of the chassis and the back of the set.



**"SABRINA"  
STILL WELL IN  
FRONT**

**STOP FIDDLING WITH KNOBS . . . ABSOLUTELY UNNECESSARY . . .** Our Automatic Regulator ensures constant voltage on TV, even with Mains of 180,265 v. YES, we know it's wonderful. "Have a heart for your Valves and Tube."  
S.A.E. details. *Conditional Free Trial.*

**COMPLETELY REBUILT C.R. TUBES ALL TYPES**

12" now ... .. **£5. 0.0** } For  
14" to 17" now ... .. **£5.10.0** } Single  
21" now ... .. **£8. 0.0** } Tubes

ALL C.W.O.—TRADE SUPPLIED

**Special Bonus Scheme for Service Engineers—Reducing to:**

12"—87/6; 14"/17"—97/6; 21"—147/6  
**FREE** Pass. transit & Ins. anywhere in British Isles or N. Ireland (12 months' guarantee).

**ALSO FULL RANGE OF VALVES**  
(Guaranteed 12 months)

**SABRINA C.R. TUBE CO.**

Electron Works, North Bar  
BANBURY, OXON  
Telephone 2390

**NEW VALVES!**

**GUARANTEED SET TESTED  
24-HOUR SERVICE**

1RS, 1SS, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DL92, DL94, SET of 4, 1S7-  
DAF96, DF96, DK96, DL96, SET of 4, 237-

OA2	4/6	DAF91	3/6	ECH42	7/9	PL84	5/6
ID5	4/9	DAF96	5/9	ECL80	5/9	PY31	6/-
1RS	4/6	DF33	7/6	EF41	6/6	PY32	8/6
1SS	3/6	DF91	2/3	EF80	4/-	PY80	5/-
1T4	2/3	DF96	5/9	EF85	4/9	PY81	5/6
3S4	4/9	DH77	4/3	EF86	6/-	PY82	5/3
3V4	5/6	DK32	8/6	EF89	3/9	PY83	6/3
5U4G	4/3	DK91	4/6	EF91	2/9	U25	8/6
5Y3GT	4/3	DK92	6/9	EL41	8/6	U26	10/6
5Z4G	7/-	DK96	6/3	EL84	5/3	UABC80	5/6
6K7G	1/3	DL33	7/-	EY51	5/9	UAF42	7/6
6K8G	3/6	DL35	6/3	EY86	5/9	UBC41	6/6
6Q7G	4/3	DL92	4/9	EZ40	5/3	UBF80	6/-
6U7G	7/6	DL94	5/6	EZ80	4/6	UCC85	6/6
6V6G	3/9	DL96	5/9	EZ81	3/9	UCH42	7/3
6X5GT	5/6	EB91	2/-	MU14	4/6	UCH81	7/3
12K7GT	3/6	EB41	7/-	PCC84	5/9	UCL81	7/3
12K8GT	8/6	EBF80	7/-	PCC89	7/9	UCL82	7/9
12Q7GT	3/6	EBL21	8/-	PCF80	5/6	UCL83	8/6
12S7GT	5/6	ECC40	7/-	PCF82	6/6	UF41	6/9
35L6GT	7/3	ECC81	3/6	PCL82	6/9	UF89	6/3
35Z4GT	4/9	ECC82	4/6	PCL83	8/6	UL41	6/11
85A2	6/6	ECC83	4/6	PCL84	6/6	UL84	6/3
AC/TP	18/6	ECC84	5/9	PL36	7/9	UJ8	11/6
AZ31	6/9	ECC85	7/-	PL81	6/9	UY21	8/3
CL33	8/6	ECF80	6/-	PL82	5/3	UY41	4/6
DAC32	8/-	ECF82	6/6	PL83	5/3	UY85	4/-

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra. Any C.O.D. Parcel 4/3 extra.

Office address, no callers:

**CERALD BERNARD**

83 OSBALDESTON ROAD  
STOKE NEWINGTON, LONDON, N.16

*Build your  
OWN*



**Learn-as-you-build  
the ICS way—it's easier!**

**1**

**YOU BUILD YOUR OWN SETS**

You build your own 5-valve radio receiver portable transistor (or A.F. Amplifier) signal generator and your own high-quality multi-meter. All under expert tuition! In this way you master the practical side of radio quickly and easily—in your own home in your own time. The course booklets are packed with helpful easy-to-follow illustrations.

**2**

**YOU MASTER THE THEORY OF RADIO**

With your own home laboratory you carry out experiments and learn the theory of radio and electronics. This practical ICS course is the surest way to become a radio expert. To ensure this all lessons are set out in simple easy-to-understand terms.

**3**

**YOU GET THESE FREE KITS**



With the ICS Complete Radio Construction Diploma Course you get six kits—including instruments tools testing units and all the parts for your own equipment. And your ICS instruction manuals become a personal "library" yours for constant reference.

**FREE! ICS brochure on radio courses. For your copy post this coupon today, to**

ICS (Dept. 161) Intertext House, Parkgate Rd., London SW11

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

AGE \_\_\_\_\_ 1.64

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

Member of the Association of British Correspondence Colleges.

**GUARANTEED REPLACEMENT  
LINE OUTPUT TRANSFORMERS**

**EMERSON** all models 50/-, **EKCO T 231**,  
**TC 267**, **T 284**, **T 293**, **T 326**, **T 221**,  
**T 283**, **T 311**, **T 327**, **T 330**, **TMB 272**, 50/-,  
**FERRANTI T 1002**, **T 1004**, **T 1005**, 50/-,  
**COSSOR 931**, **934**, **935**, **938**, **939**, 50/-,  
**FERGUSON 306**, **308**, 60/-, **PYE VT4**,  
**52/6**, used 30/-, **P. & P. 3/6**, over £5 Post  
Free, Trade supplied. Three-day rewind  
service. S.A.E. if your type not listed.  
All L.O.P.T.s in stock.

If valve not listed send S.A.E. TERMS: C.W.O., C.O.D., S.A.E. for all enquiries.  
Satisfaction guaranteed. Return Post Service.

**WITWORTH T.V. SERVICE, 32a, All Saints Road, London, W.11**  
Tel. **PARK 9972.** Open all day Mon.-Sat. inc

**PADGETTS RADIO STORES  
OLD TOWN HALL  
KNOWLER HILL  
LIVERSEDGE, YORKS.**

Telephone: **Cleckheaton 2866**

**COMPLETE TV SETS UNTESTED**

Bush 12in. 13 channels, TV24C .. .. 30/-  
Bush 14in. 13 channels, TV43 .. .. 70/-  
Bush 14in. 13 channels, TV53 .. .. 75/-  
Pye 14in. 13 channels, V14C console .. 50/-  
Pye 14in. 13 channels, V14 .. .. 50/-  
Philips 14in. 2 and 10 channels, 1446 .. 35/-  
We have 17in. TV Sets with rough cabinets,  
coils fitted 2 and 10, at 50/-. Carriage on any  
TV Set 10/- per B.R.S. Well packed but  
sent at owner's risk.

Valves Removed from TV Sets. Tested  
on Mullard Valve Tester, and are 100% as  
new. Three months unconditional guar-  
antee. POST FREE.

ECL80	2/-	10P1	1/-	PY81	4/-
ECC82	5/-	10P13	5/-	PY82	5/-
EY81	2/6	10P14	5/-	PZ30	5/-
EBF90	4/6	20D1	3/-	PCF80	4/6
EB91	9d.	20P1	5/-	PCO84	4/6
EF91	9d.	20L1	5/-	EAC91	1/6
6SN7	2/6	U281	5/-	PL33	5/-
6F1	1/-	U282	5/-	PL33	4/-
6F14	5/-	U329	5/-	B36	4/-
6F15	5/-	KT36	5/-	N37	5/-
6LD20	5/-	PL81	5/-	G35	3/-
10C2	5/-	PL82	5/-	U12	4/-
		PY80	5/-	9S4	1/3

EF80 1/6 or 10/- per doz. Grade 2 EF80 for  
test purposes, 4/- doz.

New Valves Ex. Units. POST FREE.  
ARF12 1/6, 6 for 5/6, box of 50 20/-, IT4 2/-,  
AR8 2/-, ART2 2/-, APT4 2/-, APP3 2/-,  
6K7 2/-, 6K8 4/-, 5U4 3/-, 6SN7 3/-, 6V6 3/-,  
6V6CT 4/6, 6C4 2/-, EL91 1/6, EF91 1/6,  
EF80 1/-, 6/- doz., 6F6 2/6, 6X5 4/6.

**P.M. Speakers.** Removed from TV Sets.  
All perfect condition. Rola and Plysesey,  
6 x 4in., 5/-; Goodman and R. and A., 7 x 4in.,  
6/-; Rola and R. and A. 6in. round, 3/6;  
6in. Dish. round, 5/-; 8in. round, 6/-. Post  
on any speaker, 2/-.

**TV Tubes Picture Tested.** Reclaimed  
from TV Sets, 12in., 17-, 14in., 30/-. Carr.  
7/6. 6 months unconditional guarantee.

**TV Tubes.** Completely rebuilt and refaced.  
12 months guarantee. Old glass not re-  
quired. 12, 14, 15 and 17 ins. Any make.  
Special trade price of £3.15.0. Carr. In-  
surance, 7/6.

**Few Top Grade Diodes, 1/3 each, 4/6 per  
doz. Post free.**

**Special offer.** Few 12in. speakers with built-  
in tweeter. 28/-. Post free.

**RES/CAP. BRIDGE 39/6**  
p. & p. 2/6  
Checks all types of resistors, condensers  
Built in 1 hour. Direct reading.  
**READY CALIBRATED**  
Stamp for details of this and other kits.  
**RADIO MAIL (Dept. VT)**  
Raleigh Mews Raleigh Street, Nottingham

**BRAND NEW VALVES**

90-Day Guarantee		Revised Prices		Always in Stock	
DAF 91	5/3	EL 41	8/-	U 191	11/9
DAF 96	7/9	EL 84	6/3	U 301	15/-
DF 91	3/9	EY 51	7/3	U 801	19/-
DF 96	7/3	EY 86	8/3	UABC 80	7/3
DK 91	5/9	EZ 40	6/-	UCH 81	7/6
DK 96	7/9	PCC 84	8/-	UCL 93	12/-
DL 92	6/9	PCF 80	8/-	UF 89	6/3
DL 94	6/9	PCL 82	8/6	UL 84	6/6
DL 96	7/3	PCL 83	9/8	UU 8	14/6
ECC 81	4/9	PCL 85	9/-	5Y3 GT	6/6
ECC 82	4/6	PL 81	9/-	6V6 G	4/6
ECC 83	6/6	PL 83	8/9	20L 1	16/6
ECC 84	7/-	PY 33	10/-	20P 4	18/-
ECC 85	7/-	PY 81	7/-	30FL 1	9/-
ECH 81	7/-	PY 82	6/8	30PL 1	10/6
ECL 80	7/6	PY 800	9/6	30PL 13	10/-
EF 80	5/-	U 25	10/9	185BT	19/-
EF 86	7/9	U 26	9/6		

If valve not listed send S.A.E. TERMS: C.W.O., C.O.D., S.A.E. for all enquiries.  
Satisfaction guaranteed. Return Post Service.

**WITWORTH T.V. SERVICE, 32a, All Saints Road, London, W.11**  
Tel. **PARK 9972.** Open all day Mon.-Sat. inc

**"PRACTICAL WIRELESS"  
RADIO AND TELEVISION  
REFERENCE DATA**

Contents include Colour Codes:  
Formulae: Aerials; Frequency &  
Wavelength; Television Standards;  
Symbols; Abbreviations; Amateur  
Radio; Useful Constants; Amateur  
Radio Prefixes; I.F. List for Com-  
munications Receivers; Mathemati-  
cal Data; Wire & Cable Data.  
Compiled by J. P. Hawker.  
10/6 Postage 1/-

**FREQUENCY DIVIDER ORGANS**  
by A. Douglas. 25/-. Postage 9d.

**AUDIO & ACOUSTICS** by G. A.  
Briggs. 10/6. Postage 1/-.

**PRINCIPLES OF COLOUR TELE-  
VISION** by G. N. Patchett, 16/-.  
Postage 9d.

**RADIO SERVICING PROBLEMS**  
by W. A. L. Smith. 5/-. Postage 6d.


**RADIO & TELEVISION TEST  
INSTRUMENTS** by G. J. King.  
25/-. Postage 1/6.

**RADIO VALVE DATA.** 7th Edition.  
Compiled by "VW" 6/-. Postage  
10d.

**COMPLETE CATALOGUE 1/-.**

**THE MODERN BOOK CO.**  
BRITAIN'S LARGEST STOCKIST  
of British and American Technical Books  
**19-21 PRAED STREET  
LONDON, W.2**  
Phone: **PADDington 4185**  
Open 6 days 9-6 p.m.

**BBC • ITV • F.M. AERIALS**



**B.B.C. (BAND 1).** Tele-  
scope loft, 21/-. External  
S/D 30/-.

**I.T.V. (BAND 3).** 3 Ele-  
ment loft array, 25/-, 5  
Element, 35/-. Wall  
mounting, 3 Element, 35/-,  
5 Element, 45/-.

**COMBINED B.B.C./I.T.V.**  
Loft 1+3, 41/3; 1+5, 48/9;  
Wall mounting 1+3, 56/3;  
1+5, 83/9. Chimney 1+3,  
63/9; 1+5, 71/3.

**F.M. (BAND 2).** Loft S/D, 12/6; "H"  
30/-. 3 Element, 52/6. External units  
available. Coax. cable 8d. yd. Coax.  
plugs 1/3. C.W.O. or C.O.D. P.P. 3/-  
Send 6d. stamps for illustrated lists.  
Band IV 625 line Aerials also available.

**K.V.A. ELECTRONICS (Dept. P.T.)**  
3B, Godstone Road, Kenley, Surrey.  
CRO. 2527

**HERE'S A LOW COST WAY  
TO GET INTO  
REALLY PROFITABLE  
T.V. SERVICING FAST!**

Maybe you enjoy fixing electrical gadgets or  
the odd radio or two. Maybe you wish you  
could. In either case you are probably just  
the man who could benefit from a new  
revolutionary type of television training  
programme now being introduced for the  
first time.  
Knowing that early success will usually  
spur you on to greater achievement, we  
have made a point of teaching first how to  
make the easiest T.V. repairs. Since the  
easiest T.V. repairs are the ones most often  
found on service calls, you are ready to  
make money right after the first lesson.  
Then as you progress you will learn how to  
handle every kind of trouble found in all  
makes of T.V. sets.

Here for example are some of the items  
covered in the course:

1. Simple adjustments to correct poor pictures.
2. Circuit faults indicated by a poor pattern.
3. Finding bad valves by observing picture faults.
4. Antenna principles and practices.
5. Facts about the T.V. signal to help you in repair work.
6. All about Cathode Ray tubes.
7. How to tell what is at fault.
8. Explanation of television circuits.
9. U.I.F. converters and tuners.
10. Television test equipment and alignment.
11. Advanced trouble shooting by picture analysis.

This is a real home study course that has been  
bound into one giant 8 x 11in., 192 page manual  
to reduce cost.

Compare favourably with some courses  
costing very much more! By creating a  
mass market through large volume sales  
and eliminating individual letter writing  
we are able to pass on these savings directly  
to you!

The course features over 325 different line  
drawings, circuits, servicing charts and  
illustrations to simplify the text and make  
your study more enjoyable. Soon you  
will be well on your way to becoming a first-class  
television repair technician!

**YOU TAKE NO CHANCES WHEN YOU  
DEAL WITH SIM-TECH**

You must be convinced that this is the best  
value you have ever seen in television  
training, otherwise you can return the  
course (or have your money refunded if sent  
with order) after you have examined it in  
your own home for a period of seven full  
days.

The price? Only 38/- per course, plus postage  
and packing, 1/6.

**FREE TRIAL OFFER**  
Terms only 5/- per week if you wish.

To **SIM-TECH BOOK COMPANY Dept. AT2**  
West End, Southampton, Hants.

Please send your Television Course for a full  
seven days' free trial. If not delighted I may  
return the course post-paid without further obliga-  
tion on my part. Otherwise I will pay cash or 5/-  
weekly until 37/6 plus 2/6 service charge, total 40/-,  
is paid.  
 Tick here if enclosing full price of 37/6. (Same  
7-day money back guarantee.) NOTE: Customers  
will send cash with order get in addition a 71-page  
book on TELEVISION FAULTS. (This offer  
closes March 31st, 1964).  
Overseas customers please send full amount (In-  
cluding Ireland).

Name .....

Address .....

City..... County.....

**FERRANTI 17SK6**

The picture on this set occasionally develops a vertical "shudder." Also the picture is subject to slipping downwards rapidly. This latter fault may be corrected for varying lengths of time by adjusting the hold control.

The valves in the sync separator and frame circuits have been changed but these same intermittent faults recur.

Both faults may appear as soon as the picture comes up after the set is switched on, or after a long warming-up period.—C. E. Carter (London, W.3).

Whilst a component associated with the sync separator or frame oscillator may or could be responsible, we have found that the frame oscillator transformer is more often at fault in these Ferranti models. We would, therefore, advise you to first check the small capacitors and resistors associated with the interlace diode and sync separator, and then change the oscillator transformer.

**MURPHY V204**

The fault on this set is poor focus at the sides of the picture. The areas out of focus extend inwards about 3in. The remainder of the picture is excellent.

The fault is worsened by increasing the brightness. The U281 has been checked and found to be in order.—L. Evans (London, S.E.6).

This fault could be due to low e.h.t., caused by low main h.t., or to a faulty picture tube.

**BUSH TV66**

Two faults have developed on this set. The first is that on switching on, a crackling noise is present on the sound. This disappears after about a minute leaving a slight hiss permanently on the sound. I have changed the PCL83 without curing the fault.

The other fault is on vision. When first switched on a picture very diminished in size appears. After a while, this picture gradually fills the screen. The two PY82s have been changed without success.—J. Culligan (Liverpool).

If you are sure that the front right side PCL83 is in order, check the associated bias components and the volume control. If the audio trouble persists, check the sound strip valves on the left-hand side of the receiver unit.

With regard to the vision fault, we would advise you to replace the ECC82 and the PL81 and also check the PY81 and the screen dropping resistor to pin 8 of the PL81 base.

**PYE VT7**

The screen is only very faintly illuminated when the set is switched on and only a very dim picture and no raster is visible. Also the picture is badly out of focus.

On advancing the brightness control, the heater of the e.h.t. rectifier dims and the timebase whistle alters slightly. Adjusting the ion trap magnet does not affect the screen.

The tube has been tested and found to be in good order.—C. H. Bateman (Norwich, Norfolk).

You should check the ion trap magnet by substitution as the appearance of the EY51 suggests that the e.h.t. unit is providing adequate e.h.t. and the tube is taking current.

**ALBA T909**

The fault on this set is excessive sound-on-vision on the BBC channel. This fault gradually clears after the set has been operating on the one channel for about half-an-hour.—B. Williams (Yeovil, Somerset).

If the fine tuner is at one end of its travel for optimum results, remove the channel selector and fine tuner knobs and insert a suitable trimming tool to adjust the channel 5 oscillator coil core.

If the fine tuner is not at the end of its travel and best results are obtained with the control set mid-way, and there is evidence that the signal input is excessive, you will have to fit an attenuator. If the signal input is not excessive, you will have to realign the sound rejector coil cores.

**EKCO 330T**

The picture suddenly faded away leaving a raster; the sound also faded gradually to a muffled, distorted sound. When next switched on no raster appeared but the sound came up at first, only to fade once again.

I have replaced the U26 and U191 and the line output transformer was renewed recently.—R. James (Dagenham, Essex).

You should check the line linearity choke, which frequently slides down the former to short to chassis. Also suspect a faulty new line output transformer.

**ULTRA VT915**

I am considering replacing the failing 14in. tube in this set with the 17in. MW34-69 c.r.t. I realise the obvious mechanical changes of course, but apart from these could you indicate any other difficulties involved in the operation.—K. Fordham (Fulbourn, Cambridge).

The CRM141 and CRM142 have smaller neck diameters than the MW43-69 and the scanning coils would therefore be a tight fit. The correct 17in. tube to be used is the Mazda CRM171.

**INVICTA 126**

After giving good service, it suddenly became impossible to obtain a good picture with this receiver. On both channels the picture tends to roll and tear and the BBC picture is also very weak. The tearing is worse on the ITA channel. Adjustment of either hold control only worsens the situation.

If the brightness control is advanced, the images become grey and "watery" with the raster becoming exceedingly prominent until finally the picture "blows-up" and disappears.

I have checked by substitution three EF80s and



the ECC82, but without improvement.—G. Aspin (Bessacarr, Doncaster, Yorkshire).

We would advise you to check both PCF80 valves on the top left side. If there is no improvement, check the crystal diode detector which is a CG12E inside the final i.f. coil can, beneath the lower PCF80, which appears to be faulty.

#### PYE V4

The receiver has given good service for a number of years but now the width of the picture has decreased leaving a gap of  $\frac{1}{2}$  in. on either side of the screen. Adjusting the width control does not alter this situation.—A. Green (Barnehurst, Kent).

Check the PL81 line output valve, and its 3.3k $\Omega$  screen grid feed resistor.

#### BUSH TV43

There is a good raster but neither sound nor vision. I have changed the tuner unit valves without improvement. I have also tried alternative aerials but without any results.—W. Wilkinson (Belfast 13).

It would appear that there is a fault in one of the two i.f. stages common to both sound and vision, V3 and V4. Check the h.t. supplies to these stages, checking at pins 7 and 8 in each case, and replacing any burnt-out resistors and shorted 0.001 $\mu$ F capacitors.

#### RGD 1756

On switching on the picture is normal. After a few seconds, however, the screen loses contrast, leaving a picture which is almost negative. This fault will sometimes correct itself, very often remaining normal for hours. This trouble first presented itself after the picture positioning adjustment had been altered.—P. B. Fincher (Brighton, Sussex).

If the brilliance (as opposed to the contrast or signal strength) remains normal, check the crystal diode detector and the video amplifier circuit components. If the brilliance is also lacking and the whole effect is "washed out," check the tube heater voltage across pins 1 and 12. Tap the neck of the tube sharply to clear any particles or embers which may be partially shorting the heater element.

The tube may have to be changed.

## TEST CASE -14

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions, but are based on actual practical faults.

? *The receiver would work normally on sound and vision for almost an hour after switching on and then the picture would fairly quickly lose brilliance and the symptoms of a low-emission tube would develop. For example, the picture would tend to go negative on increasing the setting of the brightness control to counteract the previous loss.*

*The geometry of the picture was not impaired, however, and the timebases as well as the sound remained unaffected. What was the most likely cause of this trouble and what simple method could be used to prove the trouble?*

See next month's PRACTICAL TELEVISION for the solution to this Test Case and for another problem.

### SOLUTION TO TEST CASE 13 (Page 138 last month)

Modern receivers use the energy recovery type of line timebase where a booster diode is employed, to reclaim some of the energy stored in the inductive and capacitive elements of the line output stage, at the finish of each scanning cycle. And it is the current which is circulating through the booster diode at the end of the line flyback which is used to deflect the scanning spot over the first half of each line scan.

Now, should a fault occur which prevents the line output valve from conducting when the booster

energy has been exhausted—e.g. resulting in late conduction—the booster diode current will cease before the line output valve current starts, and the line scan will be cramped at that point as no source of current is available.

The symptom will also result should the booster diode fail to conduct and supply energy for sufficient length of time to cater for the first part of the line scan.

Thus, typical causes of the symptom are: low-emission booster diode or low value of the booster reservoir capacitor; incorrect operating conditions of the line output valve due to low emission or incorrect electrode potentials (e.g. low screen grid voltage); incorrect connection to the booster diode from the line output transformer after a servicing operation.

If the set features a line drive control, maladjustment here could well be responsible in upsetting the desirable mark/space ratio of the line drive waveform to the line output valve. Similarly, alteration in value of a component between the line oscillator and line output valve could produce the same effect.

### QUERIES COUPON

This coupon is available until JANUARY 22nd, 1964, and must accompany all Queries sent in accordance with the notice on page 184.

PRACTICAL TELEVISION, JANUARY, 1964

TELEVISION TUBES		REG UNNED.	E.-MAINTENANCE TESTED TUBES
21 in. 99/6	Guaranteed 1 Year Ins. and Carr. 10/6.	15/-	Satisfaction Guaranteed. 36/24, 14K 74, Carr. 5/- 141, 121, 31/74, and others.
17 in. 79/6	Add 10/- refundable on OLD TUBE.		
15, 14, 12 in. 59/6	110° Tubes in stock.		

17" - £11.10.0		<b>TV EXTRAS</b> <b>TV AERIALS</b> 25/- Indoor combined. Complete with 12ft. co-ax. and plug. P. & P. 2/6. <b>AERIALS</b> Loft Combined 35/6. BBC with 3 element ITA universal fitting. P. & P. 3/6. Co-ax Cable 6d. per yd. Plugs 1/3 ea. <b>LEGS</b> —Complete with fittings for any set, 35/6.
14" - £7.10.0		

12 months' Full Written Guarantee.  
Channels for all areas.  
Demonstrations daily in our Shop.  
Personal collection advised.  
Carr. 14in., 20/-, 17in., 30/-.

SPEAKERS	TELEPHONE HANDSETS	SPARES
7/9 each. 6in. Bin. 7in x 4in. Money back guaranteed. Enquire for other sizes. Ex. mfd. salvage. P.P. 1/3.	15/6 pair. G.P.O. standard pattern. House to Workshop, garage, inter-office, etc. Works off any small battery. P. & P. 4/6.	Condensers. 100, 10/-. New Assorted electrolytics & PFs. Resistances. 100—5/-. Assorted sizes, watts, grades. VALVES 9d. each. 40—£1. Thousands of Valves available. P.P. on 1 - 4 6d., 12 1/6.

**RECTIFIERS** 2/9. Metal, 250v. 100mA. J wave. Salvage Guaranteed. P. & P. 1/3.  
**PENCIL RECTIFIERS** 2/9. New. K300 Sentercel. 10mA. E.H.T. P. & P. 6d.

**DUKE & CO. (LONDON) LTD.**  
621/3 Romford Road, Manor Park, E.12  
Liverpool St.—Manor Pk.—10 mins. Phone ILFord 6001/2/3

## Better, Brighter, Picture Tubes

BRAND NEW THROUGHOUT excepting glass

12in. ...	£4.10.0	14in. ...	£5. 5.0
15-17in. ...	£5.15.0	21in. ...	£7.15.0

New Silver Screen and Alumining. All makes Mullard, Mazda, Emiscope, Cossor, Brimar, Emitron, etc.

**REBUILT MULLARD AND MAZDA TUBES**

12in. ...	£3. 0.0	14in. ...	£4. 0.0
15-17in. ...	£4.10.0	21in. ...	£6.10.0


All Tubes Fully GUARANTEED 12 MONTHS. Dispatch same day. Cash with Order. Carriage and Insurance 10/-.

**S.T.S. Ltd.**  
35 POUND STREET, CARSHALTON, SURREY  
Telephone: WALLINGTON 9665
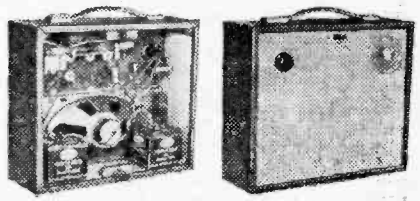
# Build your OWN TRANSISTOR PORTABLE

Learn-as-you-build the ICS way—it's easier!

- 1 YOU BUILD YOUR OWN SETS**  
You build your own portable transistor receiver (or A.F. Amplifier), 6-valve radio receiver, signal generator and your own high-quality multimeter. All under expert tuition! In this way you master the practical side of radio, quickly and easily—in your own home, in your own time. The course booklets are packed with helpful, easy-to-follow illustrations.
- 2 YOU MASTER THE THEORY OF RADIO**  
With your own home laboratory you carry out experiments and learn the theory of radio and electronics. This practical ICS course is the surest way to become a radio expert. To ensure this all lessons are set out in simple easy-to-understand terms.
- 3 YOU GET THESE FREE KITS**



With the ICS Complete Radio Construction Diploma Course you get six kits—including instruments, tools, testing units and all the parts for your own equipment. And your ICS instruction manuals become a personal "library", yours for constant reference.

**FREE! ICS brochure on radio courses. For your copy post this coupon today, to**  
 ICS (Dept. 162), Intertex House, Parkgate Rd., London, SW11

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 \_\_\_\_\_ AGE \_\_\_\_\_ 1.64

**INTERNATIONAL CORRESPONDENCE SCHOOLS**

# TELEVISION TECHNICIANS LINE OUTPUT TRANSFORMERS SCAN COILS, ETC.

## LABORATORY TESTED

ALBA: T301, T304, T394, T484, T494, etc. . . . .	40/6
BUSH: TV11A, 11B, 12A, 12B, TVG12A, 12B, TRQ12A, 12B	44/-
TV926, TV32, TV33, TV934, TVG34A, TV9, TV36, TVG36, TV36C, TVG36C	88/6
TV43	94/-
TV53, TV56, TV57, TV58, TV63, TV63, TV66, TV67, etc. . . . .	109/-
TV80 with EY51 . . . . .	61/8
COSSOR: 930 and T931, 933-4-5, 937, 938A and F, 939 and A and F . . . . .	58/8
943T, 940-946, 949, 945B, 954F, 947, 949 . . . . .	88/8
954F, 947, 949 . . . . .	88/8
DECCA: D17 and C . . . . .	74/-
DM1, DM2C, DM3, DM4/C, DM5, DM14, DM17, 444, 565 . . . . .	58/8
DEFIANT: TR1453, TR1753 . . . . .	58/8
DYNATRON: EKCO: T893, TC8102, TS105, TS114, TRC124, TC138, TS183, TS193 . . . . .	54/-
TRC138, TC140, T141, TV142 . . . . .	78/6
T161, TC162, T164, T165, etc. . . . .	78/6
TC208, TV209, T231, T231, T231F, T248, T283, T284, T293, etc. . . . .	58/8
FERGUSON: 103T, 105T, 113T, 135T, 145T, 941T-953T inclusive . . . . .	65/8
991T-997T inclusive . . . . .	88/8
308T, 308T . . . . .	64/-
FERRANTI: 14T3, 14T3F, 13TA, 17K3 and F, 17T3 and F . . . . .	47/6
17K4 and F, 178K4 and F . . . . .	17/8
17T4 and F . . . . .	47/6
14T5, 178K5, 17K5 . . . . .	47/6
G.E.C.: BT1251, BT1262, BT1746, BT1748, BT4643, BT5147, BT5246-48 . . . . .	88/6
BT4743 . . . . .	48/6
BT5348-BT5643B inclusive . . . . .	88/6
H.M.V.: 1824 and 1 to 1831 inclusive 1840, 1841, 1842-1848 . . . . .	88/6
All models available. . . . .	88/6
INVICTA: T118, T119, T120 . . . . .	54/-
All other models available. . . . .	100/6
K.B.: LFT50, LVT50, LFT60, MY60 . . . . .	100/6
All models available. . . . .	100/6
MARCONI: All models available. . . . .	100/6
MASTERADIO: Most models in stock. . . . .	58/8
McMICHAEL: Most models in stock. . . . .	94/8
MURPHY: V200, V2020 . . . . .	94/8
V240, V250 . . . . .	94/8
PETO SCOTT, PHILCO: Most models in stock. . . . .	54/-
PAM: 908, 909, 952, 953, 958 . . . . .	104/-
PHILIPS: 1785U, 2168U . . . . .	74/-
1130V, 1204V . . . . .	74/-
1220U, 1236V, 1238V . . . . .	74/-
114UF, 114UM, 115U . . . . .	74/-
1437U, 1440U . . . . .	74/-
Most models in stock. . . . .	74/-
PILOT: Most models in stock. . . . .	54/-
PYE: CTM4, FV4C, FV4COL . . . . .	54/-
V4, VV4, V7, VV7 . . . . .	54/-
LV30, FV1, FV1C . . . . .	88/8
CS17F, CSM17F, CW17 . . . . .	88/8
CW17C, CW17CF, CW17F, etc. . . . .	88/8
Most models in stock. . . . .	88/8
RAYMOND: Most models in stock. . . . .	58/8
REGENTONE: All models available. . . . .	58/8
R.G.D.: 6017T, 7017, C54, etc. . . . .	58/8
Most models in stock. . . . .	58/8
SOBELL: TS17, T246 . . . . .	64/-
Most models in stock. . . . .	64/-
STELLA: ST5721U . . . . .	104/-
ST8817U, ST8621U . . . . .	104/-
ST8917U . . . . .	104/-
ST8414U, ST8417U . . . . .	74/-
ST8314U . . . . .	74/-
ULTRA: 86 series, 186 series, with U25, etc., complete . . . . .	78/8
Most models in stock. . . . .	78/8
VIDOR: CN4217-CN4231 inclusive . . . . .	64/-
Post and Packing 3/6. C.W.O. Only . . . . .	64/-
Also: Used O.P. Tex., Scan Coils, etc. . . . .	64/-
<b>ALL GUARANTEED 90 DAYS</b>	
(All enquiries S.A.E.)	

**WYNDSOR TELEVISION  
TECHNICAL DIVISION**  
ST. ALBANS RD., BARNET, HERTS.  
BAR 1769

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisement must be prepaid and addressed to Advertisement Manager, "Practical Television", Tower House, Southampton St., London, W.C.2.

## SETS & COMPONENTS

**DIRECT TV REPLACEMENTS LTD.**, largest stockists of TV Components in the U.K. Line Output transformers. Frame Output Transformers, Deflector Coils for most makes. Official sole suppliers for many set makers. Same Day Despatch Service Terms. C.O.D. of C.W.O. Send S.A.E. for quotes. Day and night telephone: GIPsy Hill 6166, 126 Hamilton Road, West Norwood, SE27.

## EKCO-FERRANTI L.O.T.s U25 Type

**PERSPEX HOUSINGS** to suit 16/- Quantity Discounts. Post Free.  
6 at £4.7.0; 12 at £8.2.0; 50 at £30.  
**BOYLAN**  
Duke St., Warrenpoint, N. Ireland.

**A CLOSED CIRCUIT T/V CAMERA.** S.A.E. for itemised price list. **AJAX ELECTRONICS**, 573 Fulham Road, London, SW6.

"HEATHKITS" can now be seen in London and purchased on H.P. Free Brochure. **DIRECT TV REPLACEMENTS, LTD.**, 126 Hamilton Road, West Norwood, SE27. GIPsy Hill 6166.

## TV SPARES

**Fully Guaranteed Makers Parts.** Telephone orders sent same day. Line Output Transformers.

**Ekco** T221, 231, 311, 284, TC208, T310, T331, T327, TU209, T248, TC267, all 62/6; Ferranti T1001-5, 62/6; 14T3-6, 47/6; Murphy V240/250, 62/6; V270/280, 79/6; Pye V4-7, UT4-7 and Pam 906-53, 55/-; H.M.V. 1840-9, 2805-5902, only 62/6; Bush TV53, 79/6; TV24C, TV80 etc., 89/6; Philips 1768U, 92/6; 1114-5, 1437-46 89/6; Masteradio T917, TETT, T409-12 etc., 75/-; Alba T301, 304, 394, 484, 494, 55/-; Cossor 930-8, 58/6; Ferg. 992-8, 62/6; Baird P2014/7, 21147, 59/6.  
**L.O.P.T.s FOR ANY MAKE** and Model supplied. USED trans., often available, ask for quote. **SCAN COILS.** Ekco T221, T231, etc. Pye VT4-7, both 50/-; Used 14in. ex-Rental 13 Ch. sets: Pye/Ferg./Sobell, 10/- each. Lots of 20 Lots of 6 for £5. (Callers only). 110 Con. Kit, 125/-; 625 LOP, 90/-; Double-Six Transistor, comp. with leather case, bat. earphone, etc., limited supply 82/6.

Free Insurance and Quantity discounts Callers Welcome. Open all day Saturdays Terms: C.W.O. or C.O.D. Post & Pack 4/-

## TELEVISION CONSUMER SERVICES LIMITED

112 CAMBERWELL ROAD  
LONDON, S.E.5. Tel.: RODney 7917  
Also at:  
8 CRAY PARADE, MAIN ROAD,  
ST. PAUL'S CRAY, KENT.  
Tel.: Orpington 30566.

# TELEVISION TUBE SHOP

We have the following

## Unused, Guaranteed Tubes in Stock now

AW36-20, 21 . . . . .	£5. 2.6
AW36-80 . . . . .	£5. 7.6
AW43-80, 88 . . . . .	£6. 7.6
AW43-89 . . . . .	£6.12.6
AW47-90, 91 . . . . .	£7.10.0
AW53-80 . . . . .	£7.12.6
AW53-88 . . . . .	£7.17.6
C14BM, FM . . . . .	£5. 5.0
C17BM, FM, HM . . . . .	£6. 7.6
C17LM, PM, SM . . . . .	£6.12.6
C21 HM, SM, TM . . . . .	£7.17.6
CME1402 . . . . .	£5. 7.6
CME1702, 1703 . . . . .	£6.12.6
CME1705 . . . . .	£7. 7.0
CME2101 . . . . .	£8. 7.6
CRM93 . . . . .	£4. 2.6
CRM124 . . . . .	£4.12.6
CRM141, 2, 3, 4 . . . . .	£5. 7.6
CRM152, 153 . . . . .	£5.17.6
CRM171, 2, 3 . . . . .	£6. 7.6
CRM211, 212 . . . . .	£7.17.6
MW6-2 . . . . .	£6.17.6
MW22-16 . . . . .	£4. 2.6
MW31-16, 74 . . . . .	£4. 2.6
MW36-24, 44 . . . . .	£5. 2.6
MW41-1 . . . . .	£6.12.6
MW43-64, 69 . . . . .	£6. 7.6
MW43-80 . . . . .	£6. 7.6
MW53-20 . . . . .	£7.12.6
MW53-80 . . . . .	£7.12.6
T901A . . . . .	£6.12.6
14KP4A, 141K . . . . .	£5. 2.6
171K, 172K, 173K . . . . .	£6. 7.6
6901A . . . . .	£6.12.6
7201A, 7203A . . . . .	£5. 2.6
7204A . . . . .	£5. 5.0
7401A . . . . .	£6. 7.6
7405A . . . . .	£6.12.6

All tubes tested before despatch and guaranteed for 12 months.

**CARRIAGE 7/6**, via B.R.S. or 12/6 via passenger train.  
**TERMS £2 down** (plus carriage) balance £1 per month.

Midland Stockists:—  
**Amateur Electronics Co.**  
240 Lichfield Road, Aston,  
Birmingham.

## Shop Soiled Tubes (unused)

(Subject to Availability)  
14in. CRM141, 2 67/6. Others 57/6  
17in. CRM171, MW43-69, 43-64,  
75/- Plus Carriage. Guaranteed  
for 12 months.

# TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD  
LONDON, S.W.11. BAT 6859  
South of the Bridge. Open Sats.  
until 4 p.m.

Dept. PTA—NEW X7152

# Arion Television

4 MAXTED ROAD  
PECKHAM, S.E.15

## SALVAGED VALVES

TESTED ON A MULLARD  
HIGH SPEED VALVE TESTER

B36	2/6	EBC33	2/6	EF91	1/3
B329	4/-	ECC34	2/6	KT33C	1/3
D1	2/6	ECC81	4/-	KTZ41	2/6
D77	2/6	ECC32	4/-	L63	2/6
DD4	2/6	ECL80	4/-	N308	4/-
DD41	2/6	EF80	1/3	N339	4/-
DDL4	2/6	EF80	2/6	N389	4/-

MANY OTHERS. WRITE FOR FREE LIST  
POST 3d.  
SERVICE DATA 4/- ea.  
MOST SETS AVAILABLE

## NEW VALVES

FULLY GUARANTEED BY  
MANUFACTURERS

B309	10/-	HL41	7/6	LL4	7/6
CBL1	10/-	HL133DD	7/6	LP220	5/6
DD13	7/6	HL1320	7/6	MS/PEN	7/6
C30B	7/6	HP106	7/6	PEN44	10/-
ECL80	7/6	HP4106	7/6	PL13A	10/-
EF80	6/-	HP4115	7/6	PL81	10/-
HL23	7/6	K80A	7/6	PCC84	10/-
				PCF80	10/-

MANY OTHERS. WRITE FOR FREE LIST  
POST 3d.

## NEW TRANSISTORS

BOXED BY MANUFACTURERS  
AND FULLY GUARANTEED

OC18W	35/-	OC70	6/6	OC78	8/-
OC19	25/-	OC71	6/6	OC81	8/-
OC26	25/-	OC75	8/6	OC82	10/-
OC44	9/3	OC76	7/6	OC139	12/-
OC45	9/-	OC77	8/6	OC170	9/6
GET104	9/6	OC7874	9/6	GET111	12/-
GET114	6/6	GET113	6/6	XAI02	6/6

MANY OTHERS. WRITE FOR FREE LIST  
POST 3d.

## CRYSTAL DIODES

OA5	6/-	OA81	3/-	GEX34	3/-
OA70	3/-	OA85	3/-	GEX35	3/-
OA79	3/-	OA91	3/-	CGGE	3/-

Full Range Available  
WRITE FOR FULL LIST. POST 3d.

## RESISTORS

## CONDENSERS

## POTENTIOMETERS

## PLUGS & SOCKETS

## TRANSFORMERS

## TUNERS

FULL RANGE AVAILABLE  
WRITE FOR CATALOGUE. PRICE 9d.

TERMS: C.W.O. or C.O.D.

Orders under £1, P. & P. 1/3

Open till 11 p.m. most days.

Dept. PTA

# Arion Television

4 Maxted Road, Peckham, S.E.15  
NEW X 7152

## SETS & COMPONENTS

(continued)

**EXCEPTIONAL VALUE:** Picture tubes, brand new, Mazda 19in., CME1901, Mullard 19in., AW47-90/91, £4/10/-; Mullard 19in., AW59/90, £6/10/-; carriage (insured) paid, 12 months' guarantee. Note: All brand new. We also supply most other sizes, completely regunned at £4/17/6, guaranteed 12 months. TOMLINS, 156 Lewisham Way, New Cross, SE14. TID 3657.

## TUBES-AERIALS-VALVES

Regunned tubes, guaranteed one year, full range of aerials and fittings, I.T.V. boosters, valves, brayhead tuners, TV sets, transistor radios and all electrical appliances. Co-axial cables and house wiring cables, fluorescent fittings. All quotations without obligations. Special terms to the trade and Home Engineers S.A.E. for Catalogue.

## G. A. STRANGE

BROADFIELD, NORTH WRAXHALL,  
nr. Chippenham, Wilts. Tel. Marshfield 236

## AERIALS

## 625 Band T.V. AERIALS B.B.C. I.T.A. F.M.

Field tested. Complete to install. Money back guarantee.  
Band 4 (625). Grid Reflector. 8 Elmnt. 33/-. 14 Elmnt. 44/-.  
B.B.C. 'H' 37/-. Fringe 60/-.  
I.T.A. 5 Elmnt. 27/-. Double 5 10/-.  
Special 'X' B.B.C. array 30/-.  
Coaxial cable 4d. per yard.  
P.P. 4/- per aerial. C.W.O./C.O.D.

Free installation instructions, and price list of all equipment S.A.E.

## ELECTRONIC INSTALLATIONS

81 Garstang Road, Preston, Lancs.  
Tel.: 5159

## FOR SALE

**VALVE CARTONS** at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a Godwin Street, Bradford 1.

**EXCEPTIONAL TRANSISTOR** Portable Tape Recorders, value £5/19/6, complete with crystal microphone, earphone, spools, tape, batteries, instructions, presentation box (extra tapes, 100 ft. 4/6), ideal gift, £5/19/6. Satisfaction guaranteed. Postage packing 2/6. TOMLINS, 156 Lewisham Way, New Cross, SE14.

## METAL RECTIFIERS

**RECTIFIERS—CONTACT COOLED**  
14RA1292 (FC101) type 250 v., 200 mA 13/6;  
12RA1283 (FC31) type 250 v., 300 mA 17/6;  
350 mA, 19/6; FAX 13/-; FC116, 7/6.  
**RECTIFIERS—IN TYPES**  
Equivalent for RM4 250 v., 250 mA 13/6; RM5 250 v., 300 mA, 17/6; 14A989 400 mA, 18/6;  
14A86 14/6; 14A97 19/-; 14A100 22/6; 14A99, 20/-; LW7 17/6; LW15 20/-; EK6 20/-.  
**MULTIMETERS** from 39/6.  
Stamped envelope for full latest selection and bargain offers.  
Under 21 p. & P. 6d., over 21 Post Free.  
NO C.O.D.

## DURHAM SUPPLIES

176 Durham Road, Bradford 8, Yorkshire

## FOR SALE

(continued)

**1,000 TELEVISIONS**, all makes, from £33 working, 10/- not. Callers only. 9 till 6, including Sats. 39 Whitehorse Lane, Stepney, London.

## GET PLASTERED!! FREE

**POINTING TROWEL** with each ORDER OVER 45/- ALL NEW COMPONENTS  
T.V. PACK No. 2:—Turret Tuner, Chassis, 2 T.V. Droppers, 3 Pots, Mains Panel, 8/9, T.V. PACK No. 4:—AC/DC Power Unit, 3 Pots on Panel, 2 Electrolytics, 5 Knobs, 14/8. T.V. PACK No. 5:—Twin Ion Trap, 9t Co-ax and 2 PYE Plugs, 1 Cathode ray 0.1umfd 7K VDC Convl. 6/9. RADIO PACK No. 7:—Variable Cond., 3 Trimmers, 3 Coils, 2 Water Switches, 9/8. **CONSTRUCTORS' PACK** No. 10:—Variable Cond., 2 Coils, 3 Pots, Dropper, 25 Resistors, 15 Condars, 17/6. PARCEL No. 15:—100 ast Resistors, 8 Trimmers, 2 Misc Dropper, 4 Term Hooks, 2 Water Switches, 15 Tag Brds with 52 Components, 2 Valves, 2 AVO Rectifiers, 250 Sleeves and Grommets, 19/8. **BUMPER PACK** No. 17:—360 sq. in. Insulating Board, 10 Tag Strips, 2 HD Carbon Brushes, 5 Topcaps, 3 Vac ctnr parts, 36ft. PVC Sleeving, 15 Term Springs, 100 Sleeves and Grommets, 50 Self Tap Screws, 5 Knobs, 18/9. **HARDWARE PACK** No. 32:—25 asstd Clamps and Brackets, 25 Cond Clips, 25 Springs, 25 Self Tap Screws, 8/8. **SOFTWARE PACK** No. 41:—1,000 sleeves and Grommets, 248 sq. in. Felt Tape, 24 L/B Gauzes, 30 Felt Washers, 15 Tag Brds with 52 Resistors, 5 W, 5 Pots, 5 Droppers, meter Shunt, 8/9. **CONDENSER PACK** No. 71:—50 Ceramics, 10 Micaf, 15 Pfr and in Metal Tube, 5 Electrolytics, 9/8. **SWITCH PACK** No. 104:—5 Single Gang, 5—3, 3, 4 Gang Water Switches, 10 Wtr Biscuits, 4 Sliders, 5 Add-ons 10/8. **TAG-STRIP PACK** 127:—60 Binjie, 10-2w, 5-7w, 4-9w, 5-10 and 11 way, 4 way. **SOCKET PACK** No. 129:—20 asstd Pax mntd, 5 2a 2 pin Porcelain, 4-2 amp 2 pin Switched Sats, 5/8. **VALVE HOLDER PACK** No. 133:—20 270, 20 Printed out types, 5 B9G, 5 MO, 5 asstd, 5 B4 Ceramics 13/8, 5 6-pin Vibrators 7/9. **KNOB HANDLE KIT**, 30 Knobs, 10 Handles, 8 feet, 3/8. **POCKET VOLTMETERS** 0-15v and 0-150v DC with Probe, 9/8. **VALVE VOLTMETERS**, Grey metal case, 3 Valves, Inc. Diode Test Probe 7/6, less mtr mvmt. Please add small amount for P. & P. S.A.E. List. 1/- for Catalogue.

## ALBATROSS ENGINEERING COMPANY

Dept. PWT, 78-80 High Street, GOSEBERTON, SPALDING, Lincs. (Gos 458)

## WANTED

**NEW VALVES WANTED**—EY51, EY86, PL81, PCC84, PCF80, PCL82, PCL83, PY81, R19, 30P19, U25 etc. Best cash prices by return. DURHAM SUPPLIERS, 175 Durham Road, Bradford 9, Yorks.

**A PROMPT CASH OFFER** for your surplus brand new Valves and Transistors R.H.S., Beverley House, Manville Terrace, Bradford 7

## SERVICE SHEETS

**TRADE SERVICE SHEETS** offered by retired engineer. If I haven't got it you won't get it! All 4/- each by return. Please include large S.A.E. Mail orders only. ETZION1, 80 Merrion Avenue, Stanmore, Middx.

**S.P. DISTRIBUTORS** is now under New Management. Try our streamlined service. We supply Service Sheets for Radios, Televisions, Tape Recorders, Amplifiers, etc., etc. by Return of Post at 4/- each, plus postage. Send s.a.e. with inquiries. New 1963 list now available at 1/6 plus postage. Mail Orders Only please to S.P. DISTRIBUTORS, 44 Old Bond Street, London W1.

(Continued on next page)

**SERVICE SHEETS**  
(continued)

**SERVICE SHEETS**, Radio TV, 5,000 models. List 1/-. S.A.E. inquiries: TELRAY, 11 Mauldini Bk., Preston.

**SERVICE SHEETS**, also Current and Obsolete Valves for sale. JOHN GILBERT TELEVISION, 1b Shepherd's Bush Road, London W6. Tel: SHE 8441. Nr Goldhawk Rd. Station.

**SERVICE SHEETS** (30,000) 8/- each with S.A.E. DARWIN, 19 George Street, St. Helens, Lancs.

**S.E.S. SERVICE SHEETS** for all TV Radio, including Transistors. Tape Recorders, Echo Units, Amplifiers, Record Players and Autochangers etc., also various domestic appliances. List 1/-. S.A.E. Mail orders only. SUN ELECTRICAL SERVICES, 38 St. Georges Road, Hastings.

**SERVICE SHEETS** at 2/- each. With fault finding advice 6/-. Post Free. HANDLEY, 112, Baysham St., Hereford.

**SERVICE SHEETS**, Radio and TV, 4/- each. 1963 list now available at 2/-. All orders dispatched on day received. Also Manuals for sale and hire. S.A.E. please. SULTAN RADIO, 29 Church Road, Tunbridge Wells, Kent.

**TELEVISION CHARTS** 1/9; with layout details 2/9; Makers Service Manuals from 3/8; TV type valves E7C, B9A, B9A 2/9; All by rapid return post service. Send s.a.e. for lists; Back issues PTV 1/6. All post paid; Send now to Shaw, 64 Standish Street, Burnley, Lancs.

**SERVICE SHEETS**  
For all makes of Radio and Television—1925-1963. Prices from 1/-. Free fault-finding guide with all Service Sheets. Please send S.A.E. with enquiries Catalogue of 6,000 models, 1/6. Special offer of 125 Radio/TV Sheets covering many popular models, 21/-. All types of modern and obsolete valves. Radio and TV books. S.A.E. lists/enquiries.

**HAMILTON RADIO**  
Western Road, St. Leonards, Sussex.

**EDUCATIONAL**

**THE INCORPORATED PRACTITIONERS** in Radio & Electronics (I.P.R.E.) Ltd., Membership Conditions booklet 1/-. Sample copy of I.P.R.E. official Journal 2/- post free. Dept. C Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

**Radio  
Television  
& Electronics**

Learn at home with the world's largest home study organisation, Brit.I.R.E.; City & Guilds; R.T.E.B., Radio Amateurs' P.M.G.'s certs., etc. Also Practical Courses with equipment. All books supplied.

Write for FREE prospectus stating subjects to

**I.C.S.**

(Dept. 168), Intertext House, Parkgate Road, London, S.W.11

**SITUATIONS VACANT**

**RADIO & TV Exams and Courses** by Britain's finest home study School. Coaching for Brit. I.R.E.; City and Guilds Amateur's Licence; R.T.E.B.; P.M.G. Cert., etc. FREE Brochure from British National Radio School, Russell St., Reading.

**BOOKS & PUBLICATIONS**

**FIND TV SET TROUBLES IN MINUTES** from that great book The Principles of TV Receiver Servicing, 10/6 all book houses and radio wholesalers. If not in stock from Dept. C Secretary, 32 Kidmore Road, Caversham, Reading, Berks.

**NYLON-P.T.F.E.**

ROD, BAR, SHEET, TUBE, STRIP, WIRE  
No quantity too small  
List on application

**ALUMINIUM, LIGHT ALLOYS  
BRASS, COPPER, BRONZE**

**H. ROLLET & CO., LTD.**

HOWE STREET, S.W.11  
BATtersea 7872  
Works:  
36 ROSEBERY AVE., LONDON E.C.1  
Branches at Liverpool, Manchester, Birmingham, Leeds, Glasgow

What they are saying about the **KING TELEBOOSTER**

"astounded with performance" . . . "working very well, buying another" . . . "good gain in extremely difficult fringe area" . . . "can thoroughly recommend" . . . "very good" . . . "recently bought two, every satisfaction".

The Telebooster is a low-noise, two-channel pre-amp., self-contained with battery in 3½ x 3½ x 2in. plastic case. Uses the very latest VHF transistor and printed circuit. Gives at least 5 times boost on BBC and ITA simultaneously (two amps. in one!). Pulls good pictures out of grain, permits indoor aerials, DX TV and works up to 6 sets from one aerial. Just plug between aerial and set and switch on! No mains connections.

NOW also **KING FM BOOSTER** Same price and style but 6 times boost on any group of 3 or 4 FM stations. Each booster only 75/6 with PP3 battery (Post & Packing 2/6 extra). State BBC and ITA channels required. From:

**GORDON J. KING LIMITED**  
6 New Road, Brixham, Devon.  
Telephone: Brixham 2304

**TELEVISION, TAPE RECORDER & RADIO COMPONENTS SUPPLIED**

**LINE OUTPUT TRANSFORMERS.** All popular types available brand new, exact replacements, fully guaranteed. A selection which can be supplied:

PHILIPS 1756 to 177G100 U, etc., STELLA 8617 to 1007 etc.	90/-	ALSO L.O.T.s Available for
EKCO T164 to 383 etc. (U25 types) ... ..	55/-	Alba Marooni
FERRANTI T1001 " (U26 types) ... ..	59/6	Bush Pam
FERRANTI T1001 to 1023 etc. (U25 types) ... ..	55/-	Cosmor Pilot
FERGUSON 306 to 606 etc. " (U26 types) ... ..	59/6	Decos R.G.D.
PYE V4, V7, V14, VT17, CTM17, etc. ... ..	67/6	Defiant Regentia
HMV 1840 to 1854 ... 60/-, 1865 to 1921 ... ..	56/-	G.E.C. Sobell
	67/6	K.B. Ultra
		Invicta Murphy

Postage & Packing for above L.O.T.s 3/6. C.O.D. 2/6 extra.  
★ Also available for all sets ★

**SCAN COILS.** Frame output transformers, line and frame oscillator trans., width/linearity coils, sound output trans., mains trans., control knobs, electrolytics. Rectifiers, dual vol. controls, tuners, etc.

**C.R.T.s**—Rebuilt with new guns by long established Nat. Co. Guaranteed 12 months.  
MULLARD, MAZDA, BRIMAR, EMISCOPE 14in. ... £4 7 6 London  
MULLARD, MAZDA, BRIMAR, EMISCOPE 17in. ... £4 10 0 Callers  
MULLARD, MAZDA, BRIMAR, 21in. ... £6 10 0 Only

**TAPE RECORDER CHANGER SPARES.** Drive belts, heads, pulleys, motors, styli, etc., for most British and some foreign makes.

**TUNER UNITS.** Fireball, incremental and turret types—replacement service available. U.H.F. Tuners, I.F. Panels, etc.

**STANDARD COMPONENTS.** Resistors, Capacitors, Electrolytics, Drive Cord, Pilot Lamps, Vol. Controls, Presets, Ion Traps.

**SALVAGED COMPONENTS.** Large selection available including tuner units, loudspeakers, transformers, valves, etc.

Your enquiries invited, prices by return; or prompt despatch C.O.D.

**MANOR SUPPLIES** 64 GOLDERS MANOR DRIVE LONDON, N.W.11 SPE4032

# REBUILT TUBES!

*You're safe when you buy from RE-VIEW!*

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for a year against all but breakage.
- ★ Each tube is delivered **free** anywhere in the U.K. and insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

## RE-VIEW ELECTRONIC TUBES

385 LONDON ROAD, WEST CROYDON, SURREY. Tel. THOrnton Heath 7735



HERE IS WHAT YOU PAY:

12in. ... ..	£4.10.0
14in. ... ..	£4.15.0
15in. ... ..	£5. 0.0
17in. ... ..	£5. 0.0
21in. ... ..	£7. 0.0

Cash or cheque with order, or cash on delivery

—Discount for Trade—

# FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

### Have you sent for your copy?

ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the B.I.E.T. School of Electronics, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

**We definitely Guarantee**  
**“NO PASS — NO FEE”**

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £25 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

### WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,  
Electrical Eng.,  
Civil Engineering,  
Radio Engineering,  
Automobile Eng.,  
Aeronautical Eng.,  
Production Eng.,  
Building, Plastics,  
Draughtsmanship,  
Television, etc.

### GET SOME LETTERS AFTER YOUR NAME!

A.M.I.Mech.E.  
A.M.I.C.E.  
A.M.I.Prod.E.  
A.M.I.M.I.  
A.I.O.B.

B.Sc.  
A.M.Brit.I.R.E.  
City & Guilds  
Gen. Cent. of Education  
Etc., etc.

### PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V., Electronics, Etc., A.M.Brit.I.R.E. City & Guilds Radio Amateurs' Exam. R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

### INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with practical equipment. Ask for details.

### B.I.E.T. SCHOOL OF ELECTRONICS



### POST COUPON NOW!

Please send me your FREE 156-page "ENGINEERING OPPORTUNITIES"  
 (Write if you prefer not to cut page)  
 NAME.....  
 ADDRESS.....  
 .....  
 SUBJECT OR EXAM THAT INTERESTS ME..... (SE/20)

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
(Dept. SE/20), 29 Wright's Lane, London, W.8

**THE B.I.E.T. IS THE LEADING ORGANISATION OF ITS KIND IN THE WORLD**



# D. & B. TELEVISION (WIMBLEDON) LTD.

131 KINGSTON ROAD, SOUTH WIMBLEDON,  
LONDON, S.W.19. 'Phone: CHerrywood 3955

"COMPARE OUR SERVICE WITH ANY OTHER"

For the finest service in the Country. We are open from 9 a.m. to 6 p.m.—1 p.m. on Wednesdays. For any information or problems you have, call or phone, we are always pleased to help. Line output and Scan Coil specialists.

## EXAMPLE OF LINE OUTPUT TRANSFORMERS FROM OUR STOCKS.

<b>ALBA</b> —T301, T304, T394, T481, T494, T504, TR1974, TR9874 at 49/7	<b>MASTERADIO</b> —All types can be rewound, some can be supplied on our Exchange Unit Plan.
T313 Rewind at 75/-	<b>McMICHAEL</b> —M14T, M17T, M17LC at 81/-
T321, T324, T424, T524, T524FM at 44/9	M21T, M21TLC, M22C, M23HFC, M27T, M77HFC at 87/9
T331, MT341, T352, MT362, T431, T432, MT441, MT442 at 51/9	All types available, earlier Models, Rewind or Exchange Units.
T641, T644, T724FM, T744FM at 70/10	<b>MURPHY</b> —240-250 at 78/6
T555, T909, T717 at 57/9	V270, V290 at 82/-
<b>BEEHOVEN</b> —B105, B109, B208 at 57/9	V310, V350, V470 to V540 inclusive at 82/-
<b>BUSH</b> —TV32, TV33, TUG34A, T36, TV36, TUG36, TV36C, TUG36c, TV43, TV53, TV36, TV37, TUG58, M39, TUG59, TV62, TV63, TV66, TV67, Rewind or Exchange Unit at 70/-	V410, V420 at 97/6
TUG68, M69, TUG69, Rewind or Exchange Unit at 70/-	All spares available. Prices on request, S.A.E.
TV80 at 128/9	<b>PAM</b> —908, 909, 952, 953, 958 at 57/9
TV85 at 103/9	754, 764, 765C at 63/9
TV75 Rewind Only at 70/-	501, 501A, 501F, 517, 517A, 517C, 517F, 521, 531CA, 521CF, 521F, 560F at 67/6
<b>COSSOR</b> —R17A, 930, 931, 933, 934, 935, 937, 938, 938A, 939FA, 940, 942, 942A, 943, 944, 946 at 63/-	With INVICTA, PAM or PVE spares please state serial number and maker's part number.
945, 945B, 945 at 64/-	<b>PETO SCOTT</b> —148A, TR16, 178A, TV1415, T1418, T1419, TV1710, TV1719, TV1720. These are supplied as inserts only at 38/6
<b>DECCA</b> —DM1, DM2/C, DM3, DM4, DM4/C, DM5, DM14, DM17, 444, 555, DM35 at 72/6	<b>PHILCO</b> —1000, 1010 at 91/5
DM35, DM45, DM21/C, DM621, DM22/C at 74/6	1019 at 92/6
<b>DEFIANT</b> —all Rewinds only at 52/6	1021, 1023 at 91/5
<b>DYNATRON</b> —All early models Rewinds TV35, TV30 at 52/6	1800, 1840 at 72/3
<b>ERCO</b> —TC208, TV209, T209A, T221, T231, T231C, T240, TC267, TC267T, T290, T294, T298, T311, TGC310, T326, T327, T330, T330F, T331, TCG337 at 52/6	1900, 1910, 1968, 2160, 2161 at 86/-
TM8272, T344, T344F, T348, T348F, T356 at 73/9	1962M, 1967, 1967M at 73/9
TC312, T313, T331F, T335 at 52/6	All Philco spares are available, some being exchange units, some are rewinds (older models). Please send S.A.E. for quotation on any not listed.
<b>EMERSON</b> —E700, E701, E704, E708, Port O Rama, E707, E709, E710, E711. These are supplied as an exchange unit at 52/6	<b>PILOT</b> —CV76, TV76, CV77, CV84, TV84, CV84/2, TV82/2, DD87, CV87, TV87, DD87/2, CV87/2, TV87/2. These are supplied as inserts only at 41/-
<b>ENGLISH ELECTRIC</b> —All these components are rewound only, S/Coils and line output, although some we can do on exchange unit basis at 85/5	TV84, DD87, TV87. These are supplied as inserts only at 44/-
<b>FERGUSON</b> —45T 454T at 66/9	110F, 111, 117, TV107 at 63/11
103T, 105T, 113T, 135T, 142T, 143T, 145T, 990T, 991T, 992T, 993T at 66/9	All other types available, prices on request.
994T, 995T, 996T, 997T, 998T at 86/9	<b>PORTADYNE</b> —All types are rewound only at 70/-
988T, 989T at 52/6	<b>PYE</b> —V14, V14C, V4, VT4, V7, VT7 at 52/6
203T, 204T, 205T, 206T, 214T, 235T, 236T, 244T, 246T at 69/9	Luxury 17 series at 86/-
305T, 307T, 315T, 317T at 91/5	17TCDL, CB17, CB17C, CB17F, CB17FC, CTM17F, CTM17S, CMT17T, CW17, CW17A, CW17CF, CW17F at 66/-
306T, 308T at 57/9	CTM178, CW1708, CW175 at 87/6
406T, 408T, 410T, 436T, 438T, 405T, 407T at 91/5	CTM218, CWW218, CT158F at 87/6
500 Series 604T at 81/5	CTM21, CTM21C, CT212F, VT21, VT21C/D at 72/8
<b>FERRANTI</b> —14T2, 14T3, 14T3E, 14T4, 14T4F, 14T5, 14T5, 14T5, 17K3, 17K3A, 17T3, 17T3A, 17K4, 17K4F, 17K5, 17K5A, 17K6, 17K6, 17K6, 17K6, 17K6, 17T4, 17T4F, 17T5, 17T5, 17T5. These are supplied as inserts only at 38/6	V200, V200LB at 57/9
20T4D, 21K6, 21K6V, 22K3, 24K4. These are rewinds or exchange units. at 52/6	V110, PV110, V3008, V300F, V3108, V310F, V210, V210LB, V220, V230, V410, V430, V510, V720, V800A at 72/6
T1001, T1002, T1002/1, T1004, T1005, T1011 at 66/-	V700 P.No. 782740 at 42/8
T1012, T1023, T1024, T1027 at 80/-	V700 P.No. 716373 or V700 P.No. 782643 at 61/9
<b>G.E.C.</b> —BT1251, BT1252, BT1252A, BT1746, BT1748, BT2250, BT2745, BT2745R, BT2747, BT4743, BT5248, BT5347, BT5348, BT5643, BT5643R, BT8245, BT8246, BT8640. All these are supplied on Exchange Unit basis at 80/-	V700A P.No. 782740 at 42/8
BT8742, BT1156, BT1154, BT2154, BT2155, BT8149, BT8248A at 69/9	V700LBA P.No. 716373 at 58/8
<b>H.M.V.</b> —1821, 1824A, 1824B, 1825, 1826, 1826A, 1827, 1827A, 1829, 1829A at 67/6	V830A, V830LBA, V710A at 58/9
1840, 1841, 1842, 1843, 1844, 1845, 1846, 1847, 1848 at 67/6	TT1 at 42/9
1865, 1869 at 57/9	VB20A, V700D, 710D, 830D, Model 1, Model 2, Model 11, Model 15 at 59/9
1870, 1871, 1872, 1873, 1874, 1875, 1876 at 91/5	Other Pye spares quotation on request, S.A.E. please. When ordering Pye spares please state model No. and serial No. also state if printed or wired circuit.
<b>INVICTA</b> —T118, T119, T120 at 57/8	<b>RAYMOND</b> —All S/Coils and line outputs are rewound only at 67/6
T122, T126 at 61/9	<b>REGENTONE</b> —All early models rewound or exchange unit. at 114/-
T123, T124, T125, T133, T134 at 64/6	TR10-8 (or rewound at 72/-) at 38/6
237, 237SP, 437 at 66/-	10-4 and 1017 supplied as insert at 114/-
537, 538, 539 at 61/5	<b>R.G.D.</b> —DEEPT7TME, ITM2E1T1 rewound only at 114/-
With INVICTA, PAM or PVE spares please state serial number and maker's part number.	710, 611, 610 at 81/-
<b>KOLSTER BRANDES</b> —All types available, some of these are rewinds. at 87/9	<b>SOBELL</b> —TS17, T347 at 87/9
PVP20, PVP30, Royal Star at 108/9	T21, T21C, T21LC, T22 at 87/9
QV10R, QP20, QV30 at 97/3	TP8147, T178 at 87/9
PV40 at 102/-	T171, T171C, T172 at 66/-
QVP20, QVP30 at 104/3	T181, SC34, SC54, SC270, SC370 at 87/9
PV100, PV100/1 at 121/6	<b>ULTRA</b> —V814, V815, V817, V915, V917. These are exchange units at 97/6
<b>MARCONI</b> —All types available, some are rewinds. at 87/8	1453, VPI453, V15-60, V1750, VR1783, V1753, V1760, VR1762 at 63/6
68 series, VTC84DA, VCL63 at 52/6	WR1782, V1763, V1764, V21-50, V21-52, V21-60 at 80/9
VT158, VT155, VT156 at 52/6	V17-70, V17-71, V17-72, V17-73, V17-74, V17-75 at 80/-
VT157, VT158, VT159, VT160 at 91/5	V17-80, V17-81, V17-82, V17-83 at 72/8
	V19-80, V19-84, V19-85 at 81/3
	V23-80, V23-84 at 70/-
	All S/Coils can be supplied on the above Ultra range.

This list of line outputs is the most comprehensive and up-to-date yet published by anyone, if you do not see what you require, we may still hold this in our stocks, or if not we can rewind it for you. Send S.A.E. all enquiries, and remember... All goods if in stock will be despatched the same day.

## OUR STREAMLINED RE-WIND SERVICE IS NOW ONLY 7 DAYS

Send S.A.E. for free list of valves, and quality re-built CRT's at bargain prices

TERMS: C.W.O. or C.O.D., Postage on all L.O.P.T.S and S/Coils, 3/-. C.O.D., 5/-.